

PRACTICAL WIRELESS

M. Binell

MAY
1974

25p

SPECIAL PULL-OUT FEATURE

**ALSO:
HOW TO MAKE**

GUIDE TO
LONG-RANGE
RECEPTION
of
RADIO & TV



**OSCILLOSCOPE
TRACE DOUBLER**




**CAR CASSETTE
AUDIO BOOSTER**



'MINI-POP'



PW

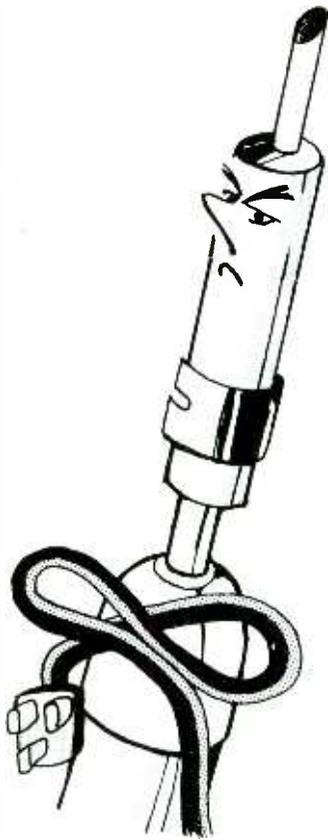

The Iron Will...

You know the type . . . whenever you need him to do one thing he'll want to do the other. And nothing will make him change his mind.

It's the same with some people's soldering irons.

Hopelessly inefficient heat control can give an iron a will of its own and make soldering operations a nightmare. If this is what soldering means to you it's time you woke up to Antex.

Just choose a new model from the comprehensive Antex range of advanced soldering instruments, with unique constructional advantages . . . low leakage characteristics, interchangeable bits to match solder-joint requirements, and really precise heat control.

Choose ANTEX—the warm hearted iron

(and keep your cool)

MODEL X25 ▶

220-240 Volts or 100-120 Volts. The leakage current of the NEW X25 is only a few microamps and cannot harm the most delicate equipment even when soldered "live". Tested at 1500v. A.C. This 25 watt iron with its truly remarkable heat-capacity will easily "out-solder" any conventionally made 40 and 60 watt soldering irons, due to its unique construction advantages. Fitted long-life iron-coated bit 1/8", 2 other bits available 3/32" and 3/16". Totally enclosed element ceramic and steel shaft. Bits do not "freeze" and can easily be removed.

PRICE £2.05
(rec. retail) P & P 10p.
Suitable for production work and as a general purpose iron.

MODEL SK.1 KIT

Contains 15 watt miniature iron fitted with 3/16" bit, 2 spare bits 5/32" and 3/32", heat sink, solder, stand and "How to Solder" booklet.

PRICE £3.48 (rec. retail)
P & P 12p.



MODEL G. ▶

18 watt miniature iron, fitted with long-life iron-coated bit 3/32". Voltage 240, 220 or 110. 2 other spare bits available 1/8" and 3/16".

PRICE £2.26 (rec. retail)
P & P 10p.

MODEL CCN

220 volts or 240 volts. The 15 watt miniature model CCN also has negligible leakage. Test voltage 4000v. A.C. Totally enclosed element in ceramic shaft. Fitted long-life iron-coated bit 3/32". 4 other bits available 1/8", 3/16", 1/4" and 3/64" including Heat Shield.


PRICE £2.48 (rec. retail) P & P 10p.



MODEL MLX KIT

Battery operated 12v. 25 watt iron fitted with 15' lead and 2 heavy clips for connection to car battery. Packed in strong plastic wallet with booklet "How to Solder".

PRICE £2.54
(rec. retail) P & P 12p.

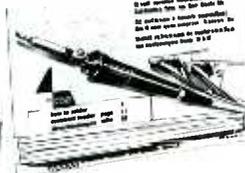

MODEL SK.2 KIT

Contains 15 watt miniature iron fitted with 3/16" bit, 2 spare bits 5/32" and 3/32" heat sink, solder, and "How to Solder" booklet.

PRICE £3.25 (rec. retail)
P & P 10p.



ST3 Stand — This stand is made from high grade insulation material with a chromium plated strong steel spring. It is suitable for all models and replaces all previous stands. The two sponges at the side which are easily replaceable serve to keep the soldering bits clean. Spare bits can be accommodated as shown on the illustration.



PRICE: £1.00
(rec. retail) P & P 10p.

ALL PRICES include VAT at 10%



Please send the following:

Please send the ANTEX colour catalogue.

From radio or electrical dealers, car accessory shops or in case of difficulty direct from:

**ANTEX LTD. FREEPOST
PLYMOUTH PL1 1BR**
(no stamp required) Tel 0752 67377

I enclose cheque/P.O./Cash
(Giro No. 258 1000)

PW4

NAME _____

ADDRESS _____



PRACTICAL WIRELESS

VOL. 50 NO. 1

ISSUE 807

MAY 1974

BRITAIN'S PREMIER MAGAZINE FOR THE DO-IT-YOURSELF RADIO AND ELECTRONICS CONSTRUCTOR

EDITOR Morris A. Colwell

ASSISTANT EDITOR
Lionel E. Howes, G3AYA

ART EDITOR Peter Metalli

TECHNICAL EDITOR
Eric Dowdeswell, G4AR

**PRODUCTION & NEWS
EDITOR** Colin R. Riches

PROJECTS SUB-EDITOR
Geoffrey C. Arnold

TECHNICAL ARTIST
Alan Martin

SECRETARIAL Jenny Maunder
01-634 4292 Susan Corne

ADVERTS. MANAGER
01-634 4293 Roy Smith

CLASSIFIED ADVERTS.
01-634 4301 Colin R. Brown

Published by IPC Magazines Ltd.,
Fleetway House, Farringdon Street,
London EC4A 4AD. Tel. 01-634 4444

SUBSCRIPTIONS

Publisher's Subscription Rate for one year to the UK is £3.25 and to the rest of the world £3.50 including postage. Enquiries to Subscription Department, IPC Magazines Ltd., Carlton House, 68 Gt. Queen Street, London, WC2 5DD. Phone 01-242 4477. International Giro facilities Account No. 5122007. Please state reason for payment "message to payee". Binders (£1.34) and indexes (11p) can be supplied by the Binders Dept at the same address.

BACK NUMBERS

We regret that we are unable to supply back numbers of Practical Wireless. Readers are recommended to enquire at a public library to see copies. Requests for specific back numbers of *Practical Wireless* and *Television* only can be published in our CQ Column.

COPYRIGHT AND QUERIES

© IPC Magazines Limited 1974. Copyright in all drawings, photographs and articles published in "Practical Wireless" is fully protected and reproduction or imitation in whole or in part is expressly forbidden. All reasonable precautions are taken by "Practical Wireless" to ensure that the advice and data given to readers are reliable. We cannot, however, guarantee it and we cannot accept legal responsibility for it. Prices are those current as we go to press. We regret that we cannot answer technical queries by telephone nor can we provide information or advice on manufacturers' products other than that given in the magazine. We will endeavour to assist readers who have queries relating to articles published but we cannot offer advice on modifications to our published designs. All correspondents expecting a reply should enclose a stamped addressed envelope.

● NEWS & COMMENT

- 24 100 YEARS ON—Leader article and June preview
 - 25 NEWS . . . NEWS . . . NEWS . . .
 - 34 HOTLINES on recent developments by *Ginsberg*
 - 47 TELEVISION Coming in the May issue
 - 48 PRODUCTION LINES—Products reviewed by *Colin Riches*
 - 48 COMING SOON IN P.W.
 - 49 NEXT MONTH IN PRACTICAL WIRELESS
 - 73 ON THE AIR
 - 73 Broadcast Bands, Short Wave—*Malcolm Connah*
 - 74 Medium Wave—*Charles Molloy*
 - 74 VHF/FM—*Simon David*
 - 77 Amateur Bands, Short Wave/VHF—*David Gibson G3JDG*
-

● CONSTRUCTIONAL

- 26 OSCILLOSCOPE TRACE DOUBLER—*A. Foord*
 - 41 TAKE 20 No. 59, Electronic Timer—*David Andrews*
 - 42 CAR CASSETTE AUDIO BOOSTER—*D. Welch*
 - 50 EXPERIMENTAL WORKSHOP—*M. J. Hughes, M.A.*
 - 56 THE MINI-POP Pocket m.w. receiver—*F. G. Rayer, G3OGR*
 - 59 "P.W. CRATA" Cassette Recorder and Tuner Amplifier Part 3—*Richard Collin*
-

● OTHER FEATURES

- 37 GOING BACK—Marconi Centenary—*Colin Riches & Arthur Dow*
 - 63 TECHNICROSS No. 4
 - 64 OSCILLOSCOPE TECHNIQUES Part 3—*Alan C. Ainslie*
-

● EXTRA WITH THIS ISSUE

SUPPLEMENT—"GUIDE TO LONG RANGE RECEPTION OF RADIO AND TELEVISION"

RSC DISCO SYSTEM


50 WATT SPEAKER

100 WATT AMPLIFIER

50 WATT SPEAKER



HEADPHONES MICROPHONE

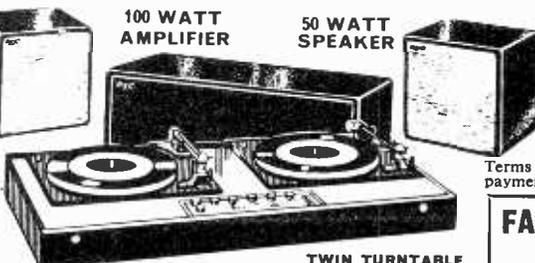

TWIN TURNTABLE WITH PRE-AMP

- Units listed below
 (a) 100w POWER AMPLIFIER
 (b) PAIR OF HI-FI HEAD- PHONES
 (c) MATCHING DYNAMIC 'MIKE' (attached to hi'phone)
 (d) PAIR 50 WATT SPEAKERS Black Rexine covered Cabinets Size approx. 18" x 18" x 8"
 (e) RSC TDI DISCO CONSOLE

RSC TDI DISCO CONSOLE

Incorporating twin Garrard SP25 or BSR MP60 type turntables and Sonotone or Acco Cartridges with diamond stylus. Separate Vol. controls for each turntable. Also MONITORING FACILITIES, plus Treble and Bass Controls. Separate input for 'mike' with vol. control switch. Black Vynair covered Cabinet with lid, see illustration on left. Or Dep. £23-50 and 12 mthly pymts £4-54 (Total £77-98) Carr. £1-50

£149-95

Terms Deposit £50 and 18 monthly payments of £7-06 (Total £177-08).

£69-95

FANE ULTRA HIGH POWER LOUDSPEAKERS

All power ratings are R.M.S. continuous. 2 YEARS' GUARANTEE High flux ceramic magnets. ALL CARRIAGE FREE.



'POP' 100

18" 100 Watt
14,000 gauss
8/15Ω
£27-50

Dep. £3-50 and 8 mthly payments £3-50 (Total £31-50)

'POP' 60

15" 60 Watt
14,000 gauss
8/15Ω
£15-95

Dep. £2-45 and 8 mthly payments. £2 (Total £18-45)

'POP' 50

12" 50 Watt
13,000 gauss
15Ω
£12-75

Dep. £1-71 and 8 mthly payments £1-71 (Total £15-39)

FOR BASS GUITAR, ELECT. ORGAN, ETC.

'POP' 55 12" 60W

Gauss 15,000 Imp 8/15Ω Or Dep £2-45 & 8 monthly payments £2 (Total £18-45)

£15-95

Carr. Free

FANE SPEAKERS 'POP' 25/2 12 in. 25 WATT

Dual Cone 15 Ω (for uses other than Bass Guitar or Electronic Organ). Carr. free

£8-75

CREDIT TERMS (PAIRS ONLY) Dep. £2-30 & 8 mthly pymts. £2-30 (Total £20-70).

GROUP EQUIPMENT PACKAGE OFFERS

F.A.L. PHASE 50 MK.III AMPLIFIER £39-98
 PR. FANE POP 25/2 5W L/SPEAKERS £17-50
 Terms: Deposit £17-38 and 12 monthly payments of £3-88 (Total £27-88)

PACKAGE PRICE £51-95

F.A.L. PHASE 50 MK.III AMPLIFIER £39-98
 PR. FANE POP 50 L/SPEAKERS £25-50
 Terms: Deposit £20 and 12 monthly payments of £3-90 (Total £66-80)

PACKAGE PRICE £59-99

F.A.L. PHASE 50 AMPLIFIER £39-98
 PAIR L12/20 5FKES (in Cabinets) £26-30
 Terms: Deposit £20-00 and 12 monthly payments £3-90 (Total £66-80)

PACKAGE PRICE £59-99

HIGH QUALITY LOUDSPEAKER UNITS

ALL TWO TONE REXINE AND VYNAIR FINISH L125 50 WATT Fitted pair of 12" 50 watt high flux speakers for conservative rating. Impedance 8-15 ohms. Carr. £1-50

£39-95

Or deposit £7-95 and 8 monthly pymts. of £4-78. Total £45-71
 L12/20 12" 25 WATT 13,000 lines 15 ohms
 Dep. £4-15 & 8 mthly pymts £1-42 (Total £15-61) Carr. 55p.

£7-95
 L12/10 10-15 Watt vaneer finish cabinet 12" unit 8-15 ohm. Size approx. 14" x 14" x 9". Carr. 55p. Dep. £2-25 & 8 mthly pymts £1-04 (Total £10-57)

R.S.C. COLUMN SPEAKERS IDEAL FOR VOCALISTS AND PUBLIC ADDRESS

All types 15 Ohms covered in Rexine and Vynair TYPE C4100 IS ALSO SUITABLE FOR BASS GUITAR OR ELECTRONIC ORGAN
 TYPE C132 30-40 WATTS Fitted two exceptionally efficient, low feedback hawl characteristic high flux 13" x 8" 20 watt speakers. Terms: Dep. £23-95 and 8 mthly payments £2-67 (Total £28-31) Carr. 65p.
 TYPE C818 50 WATTS Low feedback characteristic. Fitted three 13" x 8" deep cone high flux speakers with high power voice coils. Size approx. 54" x 14" x 11". Dep. £4-72 & 8 mthly pymts £4-15 (Total £37-92) Carr. 85p.
 TYPE C4100 100 WATTS Inc. four 12" 60 watt speakers for conservative rating. Extra heavy construction. Size approx. 58 x 16 x 10". Acoustically filled and pressurized. Terms: Dep. £20-00 & 12 mthly. pyts. £3-90 (Total £66-80). Carr. £1-50

ALL RSC PRICES INCLUDE VAT INTEREST CHARGES REFUNDED on Credit Purchases settled in 3 months



MINSTREL 8W GUITAR AMP.

Incorporating Tremolo and 13" x 8" or 10" Speaker. Output 8 watts R.M.S. Continuous. 3 Jack Inputs for Microphone and Instrument. Mains Neon Controls: Volume, Tone, Tremolo Speed Tremolo Intensity. Terms: Deposit £23-95 and 8 monthly payments £2-39 (Total £28-07). Carr. free

£19-95

FANE CRESCENDO SPEAKERS

Full range available at ALL BRANCHES

FAL PHASE 50 MK.III AMPLIFIER 50 WATT.

Solid state. 4 Separately controlled inputs Plus master vol. control. Ind. Bass and Treble Controls. Protective Circuitry against serious output overloading. Output for Speaker's 3 to 30 ohms. Size 17" x 7" x 7". 200-250v. A.C. mains. Output 50 watts music rating. Or deposit £9-93 & 8 monthly payments £4-31. Total £44-41.



£39-93

RSC PHANTOM '50' Combined 50W Amplifier and 12in. Loudspeaker.

For Lead Guitar, Mic., Gram, Radio, Tape (Not for use with Bass Instruments). Inc. 3 inputs and 2 vol. controls plus Treble, Bass and Presence. Output Jack for additional 15 ohm Speaker. Attractively finished in black with silver-finished fascia and trimmings. Compact size. Fitted carrying handle. Terms: Deposit £20-00 and 12 monthly payments £3-90 (Total £66-80). Carr. £1-50 SAE for leaflet UK Mainland

ONLY £59-95

REGENT 50 AMPLIFIER

A powerful high quality all-purpose unit for lead, rhythm, bass guitar, vocalists, gram, radio, tape. Peak Output rating. Loudspeaker unit either horizontal or vertical mounting.
 ★ Two extra heavy duty 12in. 50w Loudspeakers.
 ★ Four Jack inputs and two Volume Controls for instant use of up to four pickups or 'mikes'. Bass and Treble controls. Send S.A.E. for leaflet. Credit Terms: Deposit £25 & 12 monthly payments of £4-88. (Total £68-56.) Carr. £2-50

£74-95



GP30 AMPLIFIER

For Guitar, Vocal or Instrumental Group
 A 4 input, 2 vol. control Hi-Fi 30 watt unit with Separate Bass and Treble controls. Current valve. Peak output rating. Strong Rexine covered cabinet with handles. Attractive black/silver P.V.C. fascia. Neon indicator. For 200-250v. A.C. mains. For 3 or 15 ohm speakers. Send S.A.E. for leaflet. Terms: Deposit £4-40 and 8 monthly payments of £3-09 (Total £29-12). Carr. 75p

£25-85

R.S.C. BATTERY/MAINS CONVERSION UNITS

TYPE BMI. An all-dry battery eliminator. Size 5 1/2 x 4 1/2 x 2 1/2 in. approx. Completely replaces batteries supplying 1-5v and 90v, to battery radio where A.C. mains 200/250v. 50c/s is available. Carr. 30p. £4-15

NOW SEVEN NEW BRANCHES BOLTON, COVENTRY DONCASTER, STOCKPORT SUNDERLAND, PRESTON and NOTTINGHAM



R.S.C. BRANCHES OPERATE A 5-DAY WEEK OPEN ALL DAY SATURDAY

- BRADFORD 10 North Parade (Closed Wed.). Tel. 25349
- BOLTON 23 Deansgate. (Closed Wed.). Tel. 33512
- BIRMINGHAM 30/31 Great Western Arcade. Tel. 021-236 1279 (Closed Wed.)
- COVENTRY 17 Shelton Square, The Precinct.
- DERBY 97 St. Peter's Street. (Closed Wed.). Tel. 41381
- DARLINGTON 19 Northgate (Closed Wed.). Tel. 68043

NEW LARGER PREMISES AT HULL, DARLINGTON, NEWCASTLE & DERBY

- DONCASTER 3 Queensgate, Waterdale Centre. (Closed Thurs) Tel. 229 9501
- EDINBURGH (Closed Thurs) Tel. 229 9501
- GLASGOW 325 Argyle St. (Closed Tues.). Tel. 248 4158
- HULL 7 Whitefriargate (Closed Thurs.). Tel. 20505
- LEICESTER 32 High Street (Closed Thurs.). Tel. 56420
- LEEDS 5-7 County (Mecca) Arcade, Briggate (Closed Wed.). Tel. 28252
- LIVERPOOL 73 Dale St. (Closed Wed.). Tel. 238 3573
- LONDON 238 Edgware Road, W.2. (Closed Thurs.). Tel. 723 1629

All items subject to availability. Prices correct at 18.3.74 E. & O.E.

HI-FI CENTRES LTD.

MAIL ORDERS & EXPORT ENQUIRIES TO:- AUDIO HOUSE, HENCONNER LANE, LEEDS, 18. Tel: Pudsey (09735) 77681.

TERMS C.W.O. or O.O.D. No C.O.D. under £1. POSTAGE 28p EXTRA UNDER £2. 33p EXTRA OVER £2 OR AS QUOTED. TRADE SUPPLIED. S.A.E. PLEASE WITH ENQUIRIES.

SUPPLIERS TO GOVT. DEPTS. H.M. FORCES. EDUCATION AUTHORITIES & HOSPITALS. Etc. MAIL ORDERS MUST NOT BE SENT TO SHOPS

- MANCHESTER 60A Oldham Street (Closed Wed.). Tel. 236 2778
- MIDDLESBROUGH 106 Newport Rd. (Closed Wed.).
- NEWCASTLE UPON TYNE 24 Newgate Shopping Centre (Closed Wed.). Tel. 21489
- NOTTINGHAM 19/19A Market Street (Closed Thurs.). Tel. 48068
- PRESTON 41 Friargate Walk, St. Georges Shoppa Prec SHEFFIELD 13 Exchange Street (Castle Mkt. Blds. STOCKPORT (Closed Thurs.). Tel. 20716
- 8 Little Underbank (Closed Thurs.). Tel. 480-0777
- SUNDERLAND 5 Market Sq. (Closed Wed.). Tel. 70573

HUGE DISCOUNTS

ON LEADING BRAND HI-FI
ALL R.S.C. PRICES INC VAT

*Full labour and material guarantees for 12 months
LOW DEPOSIT TERMS OVER 8 MONTHS

	List Price	RSC Price
Wharfedale 150 DYNAMIC HI-PHONES	£24.05	£17.95
WHARFEDALE DENTON	£43.09 Pr.	£27.50
WHARFEDALE LINTON	£33.35 Pr.	£35.95
LEAK 150 SPEAKERS	£51.30 Pr.	£29.95
LEAK 250 SPEAKERS	£60.86 Pr.	£42.50
LINEAR 202 AMPLIFIER	£39.93	£24.75
Wharfedale Denton Tuner/Amp	£95	£59.95

Prices shown correct at time of going to press 18.3.74

AKAI TAPE UNITS	Rec. Price	GXR 82D	£89.95	£124.90
GXC 36D	£64.95	4000 DS	£78.95	£132.50
GXC 38D	£96.95	1721 L	£79.95	£120.75
GXC 36	£85.95	CR 81D	£58.95	£84.10
GXC 40T	£135.95	£1 Carriage All Models.		
GXC 46D	£105.95	GOLDRING GL72 T/Table & P.U. £29.95 (Rec. Price £37.29) Carr. 75p with Free Goldring G800 Cartridge worth over £10 fitted to above unit.		
GOLDRING GL75 T/Table & P.U. £34.95 (Rec. Price £57.19) Carr. 85p with Free Goldring G800 Cartridge worth over £10 fitted to above unit.				
T/TABLES with MAGNETIC CARTRIDGE/PLINTH & COVER				
GARRARD SP25 with G850	SPECIAL PRICE £19.50 (Carr. £1)			
MacDonald MP60 with G800	SPECIAL PRICE £17.95 (Carr. £1)			
GARRARD AP76 with G800	SPECIAL PRICE £28.95 (Carr. £1)			



A HIGH FIDELITY 30 + 30W STEREO SYSTEM

AUDIO FIDELITY MODEL 60 AMPLIFIER.
PAIR AUDIO FIDELITY MARQUESS 30 SPKRS.
GARRARD SP25 Mk IV or McDONALD MP60 with G800 Cartridge. Ready wired on Plinth with Cover. Cabinets finished in Teak Veneer. Send S.A.E. for leaflet. Carr. £3

Total Value approx. £165
£99.95

HI-FI 10 + 10W STEREO SYSTEM

AUDIOTRINE STEREO 20 AMPLIFIER SPECIAL PURCHASE £55
GARRARD TURNTABLE with Sonotone Cartridge wired-on Plinth with cover. Worth Double
PAIR DIPLOMAT 10W SPEAKERS, Teak Veneer finish. Carr. £2

RSC G66 MkII 6.6 WATT hi fidelity STEREO AMPLIFIER

Controls: Bass, Treble, Vol. and Bal. 10 Transistors plus Diodes. Output rating 1 H.F.M. Frequency range 20-20,000 c.p.s. Bass Control ± 12db. Treble Control ± 13db. Selector switch for P.U. or Tape/Radio. For loudspeaker output impedances of 3 to 15 ohms. For standard 200-250v. A.C. mains operation. Attractive Black and Silver finished metal fascia plate and matching control knobs. COMPLETE KIT OF PARTS INCLUDING FULLY WIRED PRINTED CIRCUIT and COMPREHENSIVE WIRING DIAGRAMS & INSTRUCTIONS £12.75 Carr. 40p
OR FACTORY BUILT IN TEAK VENEERED CABINET as illustrated £16.50 or dep. £2.12 and 8 monthly payments £2.12 (Total £19.08).



HI-FI SPEAKER ENCLOSURES

Teak veneer finish. Acoustically lined. Sizes approx. Carr. 45p. per enc.
JE8 Size 16" x 11" x 9". Pressurised. Gives pleasing results with any 8in. Hi-Fi speaker. £5.50
SE10 For outstanding results with 10in. Hi-Fi spkr. Size 25 1/2 x 16 x 9in. Ported £6.75
SE8 For optimum performance with any 8in. Hi-Fi speaker. £6.50
SE12 For excellent performance with 12in. Hi-Fi speaker and tweeter. £7.95
SE12 25 1/2 x 16 x 9in.

AUDIOTRINE HI-FI SPEAKER SYSTEMS

Consisting of matched 12in. 11,000 line 15 Watt 15 ohm high quality speaker, cross-over unit and tweeter. Smooth response and extended frequency range ensure surprisingly realistic reproduction. £6.50 Carr. 33p
OR SENIOR 15 WATT INCLUDING HF126 15,000 LINE SPEAKER £7.65 Carr. 39p




AUDIOTRINE HIGH FIDELITY SPEAKERS

Heavy construction. Latest high efficiency ceramic magnets. Plasticized Cone surround. "D" or "T" indicates Tweeter Cone providing extended frequency range up to 15,000 c.p.s. Impedance 3 or 8-15 ohms. PLEASE STATE CHOICE.
Exceptional performance at low cost:
HF808T 8" 10W £2.55 HF120D 12" 15W £5.50
HF102D 10" 10W £3.30 HF128 12" 15W £6.35
HF120 12" 15W £4.95 HF128D 12" 15W £6.85

FANE 807T HIGH FIDELITY SPEAKER

A full range 8in. 10 watt unit for excellent sound quality, in suitable enclosure. Cast chassis Ioli P.V.C. cone surround and long throw voice coil to achieve very low fundamental resonance of 30 c.p.s. Tweeter cone is fitted to extend high note response. Frequency range 25 Hz to 15 KHz. Gauss 10,000. Impedance 3 or 8-15 Ω. £3.99
PLEASE STATE IMPEDANCE REQUIRED List 84-99
MODEL 808T 8" 15w with parasitic Tweeter. £5.50
Response 25 Hz to 16 KHz. Gauss 13,000 Imp 3 or 8-15 Ω. List £8.99

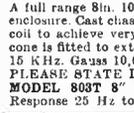

R.S.C. TA6 6 Watt HI-FI AMPLIFIER

200-250v. AC mains operated. Response 30-20,000 c.p.s. -2db. Separate Bass and Treble 'lift and cut' controls. 3 input sockets for Mike, Gram, Radio or Tape. Input selector switch. Output for 3-15 ohm spkrs. Max. sensitivity 6mV. O/P rating 1 H.F.M. Enclosed enamelled case 8 1/2 x 2 1/2 x 5 1/2 in. Wiring finish fascia 10 1/2 x 3 1/2 in. COMPLETE KIT OF PARTS WITH FULL £12.99 Carr. 40p. WIRING DIAGRAMS & INSTRUCTIONS
Factory built with Teak Veneer housing £19.95 Dep. £2.50 & 8 mthly pymts 12 mths guarantee £16.95 Veneer housing £19.95 Dep. £2.50 (Total £22.50).

R.S.C. TA12 MKIII 6.5 + 6.5 WATT STEREO AMPLIFIER

Fully Transistorised. Hi-Fi o/p of 6.5 watts per channel. Optimum performance with any crystal or ceramic F.U. Cartridge, Radio Tuner, Tape Rec. etc. Input Sel. Switch, Bass, Treble, Vol. & Bal. Controls. COMPLETE KIT OF PARTS WITH FULL £12.99 Carr. 40p. Send S.A.E. for leaflet. WIRING DIAGRAMS & INSTRUCTIONS
Factory built with Teak Veneer housing £19.95 Dep. £2.50 & 8 mthly pymts 12 mths guarantee £16.95 Veneer housing £19.95 Dep. £2.50 (Total £22.50).

AUDIO FIDELITY FRI SPEAKER KIT

Response 30Hz-15KHz. Rating 15 Watts. Imp. 8-15 ohms.
8" Bass Unit, 2" Tweeter, Cross-over etc. £11 each. Carr. Free.

SPECIAL OFFER £14.99 Pair

R.S.C. MkIII SUPER 30 HIGH FIDELITY STEREO AMPLIFIER

BUILD AN AMPLIFIER WORTH APPROXIMATELY DOUBLE THE KIT PRICE INCLUDING CABINET
Only high grade components by leading manufacturers
* Push Button Selector Switching
* Jack Socket for Headphones
* Neon Indicator
* Satin Silver Finish Metal Fascia
* Solid State Circuitry
* Twenty Silicon Transistors
* Four Diodes, Four Rectifiers
Send S.A.E. for full descriptive leaflet.
R.S.C. STEREO FM III TUNER. in cabinet
Visually matches Super 30 Mk. III £37.50



COMPLETE KIT (less cabinet). Carr. 70p. Cabinet if req. £5 extra.
£22.50
FACTORY BUILT UNIT INC. CABINET with 12 months' guarantee. Or Dep. £7 and 8 monthly payments £5.17 (Total £48.36). £42.50

'YORK' HIGH-FIDELITY 3 SPEAKER SYSTEM

★ Moderate size only 25 x 14 x 10in. approx.
★ Response 30-20,000 c.p.s.
★ Impedance 15 ohms
★ Performance comparable with units costing considerably more
£25 Carr. 75p
Consists of (1) 12in. 15 watt Bass unit with cast chassis. Roll rubber cone surround for ultra low resonance. (2) 3-way quarter section series cross-over system. (3) 8 x 5in. high flux middle range speaker. (4) Dome Pressure Tweeter. (5) Quantity acoustic damping material. (6) Handsome Teak veneered cabinet. (7) Circuit and full instructions. Terms: Deposit £3.71 and 8 monthly payments £3.12 (Total £28.67).


R.S.C. TRANSFORMERS, L.F. CHOKES & RECTIFIERS FULLY GUARANTEED. Impregnated and interleaved where necessary.

MIDGET CLAMPED TYPE 21 x 21 x 2 1/2 in.	TOP SHROUDED DROP-THRO' TYPE	CHARGER TRANSFORMERS 0.9-15v. 1 1/2a. £1.10, 2 1/2a. £1.25, 3a. £1.40, 5a. £1.60, 6a. £1.85, 8a. £2.20	SELENIUM RECTIFIERS F. W. (Bridged) All 6/12v. D.C. output. Max. A.C. input 15v. Ia. 25p. 2a. 38p. 3a. 55p. 4a. 72p. 6a. 88p.
250V.-60mA. 8.3v. 2a. £1.10	250-0-250V. 70mA. 6.3v. 2a. 0.5-6.3v. 2a. £1.40	AUTO (Step Up/step DOWN) TRANSFORMERS 0-110/120v. 200-230-250v. 50-80 watts £1.25, 150 watts, £2.10 220 watts £3.00; 500 watts £5.40	L.F. CHOKES 150mA. 7-10H. 250 Ω 77p; 100mA. 10H. 200 Ω 98p; 80mA. 10H. 350 Ω 55p; 60mA. 10H. 400 Ω 28p.
250-0-250V. 60mA. 6.3v. 2a. £1.18	250-0-250V. 100mA. 6.3v. 2a. 0.5-6.3v. 2a. £1.49		
	250-0-250V. 100mA. 6.3v. 3.5a. £1.71		
	250-0-250V. 100mA. 6.3v. 2a. 6.3v. 1a. £1.75		
	350-0-350V. 80mA. 6.3v. 2a. 0.5-6.3v. 2a. £1.81		
	250-0-250V. 100mA. 6.3v. 4a. 0.5-6.3v. 3a. £2.45		
	300-0-300V. 100mA. 6.3v. 4a. 0.5-6.3v. 3a. £2.45		
	300-0-300V. 130mA. 6.3v. 4a. c.t. 6.3v. 1a. £2.85		
	Suitable for Mullard 610 Amplifier. £2.85		
	350-0-350V. 100mA. 6.3v. 4a. 0.5-6.3v. 3a. £2.45		
	350-0-350V. 150mA. 6.3v. 4a. 0.5-6.3v. 3a. £2.85		
	FILAMENT or TRANSISTOR POWER PACKS		
	Types 6-3v. 1.5a. 55p; 6-3v. 2a. 80p; 6-3v. 3a. 85p; 6-3v. 6a. £1.45; 12v. 1a. 61p; 12v. 3a. or 24v. 1.5a. £1.50; 0.9-18v. 1 1/2a. £1.25; 0.12-22-24v. 2a. £1.95.		

BI-PRE-PAK

AUDIO BARGAINS

STEREO

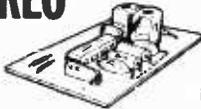

DECODER
£4.95

incl. P. & P. and V.A.T.

Ready built unit, ready for connection to the I.F. stages of existing FM Radio or Tuner. A tell take light can be connected. The Unit is a small printed circuit, no further alignment necessary.

L.E.D. is recommended as the indicating light. Suitable device available from us at 36½p. Instructions included.


3 W.R.M.S. I.C. AMP

only £1.65 Incl. P. & P. and VAT
Order Code I.C.A. 1


on P.C. Board with all components
or 2 on one board for £2.86

Order Code I.C.A. 1/S

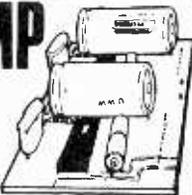These amps. are supplied with a free booklet on connecting up, specifications and easy to build projects using the I.C.A.1



5W & 10W AMPS

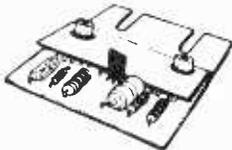

5W ONLY £1.98

10W ONLY £2.49

incl. P. & P. and VAT

These matchbox size amplifiers have an exceptionally good tone and quality for the price. They are only 2½" x 1½". The 5W amp will run from a 12V car battery making it very suitable for portable voice reinforcement such as public functions. Two amplifiers are ideal for stereo. Complete connection details and treble, bass, volume and balance control circuit diagrams are supplied with each unit. Discounts are available for quantity orders. More details on request. **Cheapest in the UK. Built and tested.**

Now available for 5 & 10W AMPS

Pre-assembled printed circuit boards 2" x 3" available in stereo only, will fit .15 edge connector.

Stereo Pre-Amp 1 (Pre 1). This unit is for use with low gain crystal or ceramic pick-up cartridges. **£1.21**

Stereo Pre-Amp 2 (Pre 2). This unit is for use with magnetic pick-up cartridges. **£1.69**

Stereo Tone Control (STC). This unit is an active tone control board and when used with the right potentiometers will give bass and treble boost and cut. **£1.21**

Instruction leaflet supplied with all units. Post and packing and VAT included in prices.

I enclose £..... for..... Decoders.....

3W Amps/..... 5W Amps..... 10W Amps.....

Stereo Pre-Amps 1..... Stereo Pre-Amps 2.....

Stereo Tone Controls.....

(Please insert quantities and delete those not applicable)

Name.....

Address.....

BI-PRE-PAK
Co. Regn. No. 820919

Dept. D, 222/224 West Road,
Westcliff-on-Sea, Essex SS0 9DF
Telephone: Southend (0702) 46344

NEW
ALL
SILICON!



**PRACTICAL
WIRELESS**

ELECTRONIC IGNITION SYSTEM

This Capacitor-Discharge Electronic Ignition System was recently described in Practical Wireless and has proved extremely popular. We are able to offer the kit in two forms; the standard kit containing the electronic components only, enabling the customer to tailor these to his own layout, or the de-luxe version containing a ready-drilled roller-tinned printed-circuit board and fully machined die-cast case with A.M.P Electrical Spade Connector Block. Each kit is supplied with a custom wound transformer, first grade components and full constructional details.

The original circuit employed Germanium Power Transistors for the negative earth version. **WE NOW SUPPLY SILICON P.N.P. POWER DEVICES AT NO EXTRA COST!** All components available separately. Case size 4½" x 3½" x 2". Complete assembly and wiring manual 25p, supplied with deluxe kit only, refundable on purchase of kit.

Suitable for 12v systems with Pos. or Neg. earth.

Price: Standard Kit£7.97 U.K. Post Free
De-Luxe Kit£9.62 U.K. Post Free

Quantity Discounts:

Trade and Overseas	1-5	Nett	6-9	Less 10%
Enquiries Invited	10-49	Less 15%	50-99	Less 20%
Mail Order Only	100-999	Less 25%	1000 up	Less 30%

ALL PRICES INCLUDE VAT

PLEASE STATE POS. OR NEG. EARTH WHEN ORDERING.

DABAR ELECTRONIC PRODUCTS

98A LICHFIELD STREET,
WALSALL, STAFFS. WS1 1UZ
Tel. Walsall 34365

TOP QUALITY SPEAKERS FROM CORAL AUDIO CORPORATION



12" 30W 8 ohms roll surround 3 cones flat 30 Hz to 18 kHz. The very best. Worth at least £25. Yours for **£15 + vat.**

8" 10W 8 ohms roll Surround and tweeter cone. Acclaimed by many as the clearest Speaker yet. Give away price **£2.50 + vat.**

Coral Audio Agency,
13 Banff Rd., Manchester M14 5TA.

Callers—242 Claremont Rd., by Wimslow Rd., Manchester.

Free brochures and specifications on request.

TWO NEW ADDITIONS TO FANE 'POP' RANGE LOUDSPEAKERS

POP 40 10" 40 Watt

Impedance
8-15 ohms
Gauss 14,000
Voice Coil
Diam. 1 1/2 in
Fitted
Tweeter Cone
Range
50-15,000 Hz
Rec. Retail Price



£10.95

Also for those who can
afford the very best
For Bass Instrument
Reproduction

BASS CRESCENDO '12'

12" 100 Watt 3" Pole Diam.

BASS CRESCENDO '15'

15" 100 Watt 3" Pole Diam.



Rec. Retail Price
CRESCENDO '12'

£39.95


Rec. Retail Price
CRESCENDO '15'

£48.83

Please send S.A.E. for leaflet on
'POP' or 'CRESCENDO'
Range Speakers

POP 55 12" 60 Watt

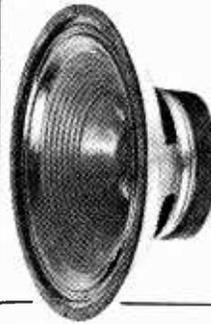Impedance
8-15 ohms
Gauss 15,000
Voice Coil
Diam. 2 in
Range
50-9,000 Hz
AN ALL PURPOSE
UNIT OF HIGH
sensitivity
Rec. Retail Price



£15.95

There is also a 12" Crescendo
Speaker for General Purpose
Public Address, and another
one for Lead or Rhythm Guitar

**PRICES QUOTED
INCLUDE VAT**

Prices correct at 18.3.74

Brief details of other 'POP' Speakers

POP '15'	12"	15 Watt	£5.75
	1" Voice Coil		
POP '25/2'	12"	30 Watt	£8.75
	2" Voice Coil		
POP '50'	12"	50 Watt	£12.75
	2" Voice Coil		
POP '60'	15"	60 Watt	£15.95
	2" Voice Coil		
POP '100'	18"	100 Watt	£27.50
	3" Voice Coil		

Distributors to Wholesale and Retail Traders—**LINEAR PRODUCTS LTD., ELECTRON WORKS, ARMLEY, LEEDS.**
Manufacturers enquiries to—**FANE ACOUSTICS LTD., 286 BRADFORD ROAD, BATLEY, YORKS**

FERRIC CHLORIDE

Anhydrous to Mil-spec in 1lb sealed packs, 1lb 50p (20p), 3lbs £1.20 (30p), 10lbs £3.50 (60p).

VERSATILE POWER UNIT

Contains mains transformer, 2A thermal cut-out and bridge rect. Will give 1.7V-10.5V output with 2 extra capacitors. Ideal for Nickel-Cad battery chargers, 5V TTL supply, cassette or radio etc. Brand new, British made, complete with Information. ONLY 75p (20p).

AMPLIFIER UNIT

In fully screened case 5 1/2 x 5 x 3 1/2". 2 GET116 on heat sink, 2 zeners, 3 pot cores, 4 transformers, 1% R's & C's, 40 way tag-board and fuse. With circuit £55p (30p), 4 for £2 (65p). Qty. discount.

3W CASED AMPLIFIER

Polished wooden cabinet 14 x 13 x 9" containing a sensitive (20uV) 4 valve amplifier with tone and volume controls, 3 watts output to the 7 x 4" 3Q speaker. Also included is a non-standard tape deck. Supplied in good working condition with circuit. Mains operated £3 (£1 up to 200 miles, £1.25 over). Suitable cassette £1 (30p); spare head 30p; tape (ex-code) 85p (20p); Amplifier chassis, complete and tested (2xECC83 EL84, EZ80) + speaker £2 (45p); motors 35p (30p).

71b BARGAIN PARCELS

Hundreds of new components: resistors, capacitors, pots, switches, + PC boards with transistors and diodes, also crystals and loads of odds and ends. Amazing value at £1.65 (40p).

COMPONENT PACKS

500 asstd. resistors £1 (20p); 2500 £4 (40p); 10000 £12 (£1); 100000 £80 + carr. 150 poly, mica, ceramic caps 60p (10p); 25 10X crystals £1 (30p).

COMPUTER PANELS

3lbs asstd. £1 (30p); 7lbs £2 (40p); 12 High quality boards with IC's, power transistors, trim pots etc £2 (30p); 100 ditto £12 (£1); Pack of boards containing at least 500 components with at least 50 transistors 60p (20p); Panel with 20 resistors 50p (10p); 2N2926 type transistors + other parts 20p (10p); Pack with 25 flat pack IC's (no info.) 30p (10p).

NEW COMPONENTS

400V 5A scr 60p; 200V 40p; OC16 20p; OC45 8p; OC71 8p; OC171 15p; BFY18 12p; BCY72 8p; 741C 32p.
Trendata Keyboard, Computer data input terminal with display. Converts to IFO code. Brand new and boxed less than 2 years old and cost £650. No data available, so only £80 (£2). Send 10p for photo.
80 + 80 + 20uF 350V 10p; 10 75p (30p); 8uF 2500V £2 (50p); 4uF 2000V £1 (40p); 10uF 235V 40p (15p); 1G resistor 2W 4p; 10p 2W 10/25p 100k 1W 50p/100 (10p); 4 pole 8 way waxy switch 30p (8p); Crystal + cats whisker 15p; 20k 10 turn Colvern wirewound pot 75p (10p); Miniature 50V ceramic plate caps 22pF-1000pF 2p; Heavy duty heat sink 6 x 5 x 3" with 2 power transistors 80p (30p); 230V fan 2800 rpm 6 1/2" dia blades complete with grill and mounting plate £2.50 (40p); Scopes in stock for callers, ring for details.

PADGETTS RADIO STORE OLD TOWN HALL, LIVERSEDGE, YORKS WF15, 6PQ

TEL. HECKMONDWIKE 405285

SPECIAL OFFER

Used 19" TV Tubes. Type AW 47-91. Perfect condition. 6 months guarantee. £3 carr. paid.

Complete untested TV Sets 19" 405-line Types £3.50 carr. and ins. paid.

19" 625-line types untested. Complete with UHF Tuner £5.50 carr. and ins. paid.

One Student and One Instructors Wireless Procedure Training Set, each unit housed in a small wood box and comprises Mike, Single L.R. Phone and connectors. Requiring Bell Battery (not supplied) to make intercom. £1.30 post paid.

Small Clock Type Sangamo Weston 200-250v 200 r.p.m. mains motor with Gear train (ex slot machine) Fair condition 60p post paid.

1/4 cwt. of ex Government Scrap Resistors, Panels, Gears, etc 30p carr. 80p.

Speakers removed from TV sets. All 3 ohm, 2 1/2 watts 7 x 4, 6 x 4, 8 x 2 1/2. All at 27p. Post and packing 12p.

Top Quality Tape, Reel to Reel 5" LP 55p. 5 1/2" LP 60p. 7" ST 66p. 7" LP 80p. Cassette Types C60 35p, C90 45p. Post on any tape 12p.

Jan Earpiece, 8 ohm, magnetic, 3.5 12p post paid.

Ex Equipment Valves all Tested before despatched. 3 months guarantee on all valves. Single valves post 3p, over post paid.

ARP12	6p	EF184	20p	PY801	17p
DY86	20p	PCF80	6p	PY82	10p
EB91	5p	PCC84	6p	PY33	20p
EF80	10p	PCL82	15p	UI91	20p
EBF89	15p	PCL84	15p	6BV7	12p
ECC81	12p	PCL85	20p	6F23	15p
ECC82	12p	PCL86	17p	30F5	12p
EY86	20p	PY81	10p	30FL1	20p
EF183	20p	PY800	17p	30P19	10p

ABOVE PRICES INCLUDE V.A.T.

VAT NOT INCLUDED, ADD 10% TO TOTAL
Carriage in brackets, small parts 5p. SAE list.

GREENWELD ELECTRONICS (PW2)


24 GOODHART WAY, WEST WICKHAM, KENT

Shops at 21 Deptford Broadway SE8, Tel. 01-692 2009, and
38 Lower Addiscombe Road, Croydon. E & OE

NEW EDU-KIT MAJOR

Completely Solderless Electronic Construction Kit
Build these projects without soldering iron or solder

- ★ 4 Transistor Earpiece Radio.
- ★ Signal Tracer.
- ★ Signal Injector.
- ★ Transistor Tester NPN-PNP.
- ★ 4 Transistor Push Pull Amplifier.
- ★ 5 Transistor Push Pull Amplifier.
- ★ 7 Transistor Loudspeaker Radio MW/LW.
- ★ 5 Transistor Short Wave Radio.
- ★ Electronic Metronome.
- ★ Electronic Noise Generator
- ★ Batteryless Crystal Radio.
- ★ One Transistor Radio.
- ★ 2 Transistor Regenerative Radio.
- ★ 3 Transistor Regenerative Radio.
- ★ Audible Continuity Tester.
- ★ Sensitive Pre-Amplifier.

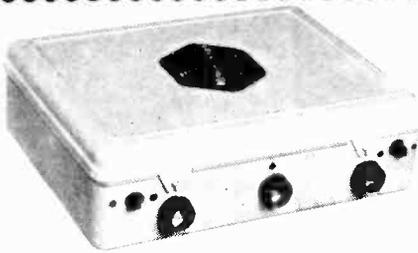


Total Building Costs
£7-23 P P & Ins. 44p
(Overseas P & P £1-85)
(+ 10% VAT 72p)

Components Include: 24 Resistors • 21 Capacitors • 10 Transistors • 3 1/2" Loudspeaker • Earpiece • Mica Baseboard • 3 12-way connectors • 2 Volume controls • 2 Slider Switches • 1 Tuning Condenser • 3 Knobs • Ready Wound MW/LW/SW Coils • Ferrite Rod • 6 1/2 yards of wire • 1 Yard of sleeving etc. • Parts Price List and Plans 50p. (Free with parts).

NEW ROAMER NINE

WITH V.H.F. INCLUDING AIRCRAFT

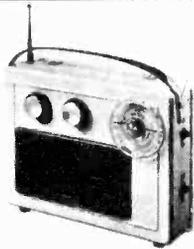

Nine Transistors, 9 Tuneable wavebands as Roamer Ten Built in ferrite rod aerial for MW/LW. Retractable chrome-plated telescopic aerial for VHF and SW. Push Pull output using 600 mW transistors. 9 Transistors and 3 diodes, tuning condenser with V.H.F. section, separate coil for aircraft, moving coil loudspeaker, volume ON/OFF and wavelange controls. Attractive all white case with red grille and carrying strap. Size 9 1/2" x 7" x 2 1/2" approx. Parts Price List and Plans 30p (Free with parts).

Total Building Costs **£6-95** P P & Ins. 44p
(Overseas P & P £1-85)
(+ 10% VAT 69p)

NEW Everyday Series

Build this exciting New series of designs



E.V.5. 5 Transistors and 2 diodes. MW/LW. Powered by 4 1/2 volt Battery. Ferrite rod aerial, tuning condenser, volume control, and loudspeaker. Attractive case with red speaker grille. Size 9" x 5 1/2" x 2 1/2" approx. Parts Price List and Plans 15p. Free with parts.

Total Building Costs **£2-73** P P & Ins. 30p
(+ 10% VAT 27p)
(Overseas P & P £1-25)

E.V.6. Case and looks as above. 6 Transistors and 3 diodes. Powered by 9 volt battery. Ferrite rod aerial, 3" loudspeaker, etc. MW/LW coverage. Push Pull output. Parts Price List and Plans 15p. Free with parts.

Total Building Costs **£3-60** P P & Ins. 30p
(+ 10% VAT 36p)
(Overseas P & P £1-25)

E.V.7. Case and looks as above. 7 Transistors and 3 diodes. Six wavebands. MW/LW, Trawler Band, SW1, SW2, SW3, powered by 9 volt battery. Push Pull output. Telescopic aerial for short waves. 3" Loudspeaker. Parts Price List and Easy Build Plans 20p. Free with parts. Overseas P & P £1-05.

Total Building Costs **£4-08** P P & Ins. 31p
(Overseas P & P £1-85)
(+ 10% VAT 40p)

ROAMER EIGHT Mk I


NOW WITH VARIABLE TONE CONTROL



7 Tuneable Wavebands: MW1, MW2, LW, SW1, SW2, SW3 and Trawler Band. Built in Ferrite Rod Aerial for MW and LW. Retractable chrome plated Telescopic aerial for Short Waves. Push pull output using 600mW transistors. Car aerial and Tape record sockets. Selectivity switch. 8 transistors plus 3 diodes. Latest 4 1/2 watt ferrite magnet loudspeaker. Air spaced ganged tuning condenser. Volume on/off, tuning, wave change and tone controls. Attractive case in rich chestnut shade with gold blocking. Size 9 x 7 x 4in. approx. Easy to follow instructions and diagrams. Parts price list and plans 25p (FREE with parts).

Total building costs **£6-98** P P & Ins. 47p
(Overseas P & P £1-85) (+ 10% VAT 89p)

POCKET FIVE

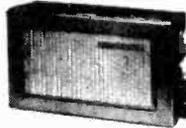

3 Tuneable wavebands. M.W. L.W. and Trawler Band, 7 stages, 5 transistors and 2 diodes, supersensitive ferrite rod aerial, moving coil loudspeaker, attractive black and gold case. Size 6 1/2" x 1 1/2" x 3 1/2" approx. Plans and Parts Price List 15p (Free with parts). (+10% VAT 22p) (Overseas P & P £1-25)

Total Building Costs **£2-28** P P & Ins. 26p
(+10% VAT 22p)
(Overseas P & P £1-25)



TRANSONA FIVE

Wavebands, transistors and speaker as Pocket Five Larger Case with Red Speaker Grille and Tuning Dial. Plans and Parts Price List 15p (Free with parts). (+10% VAT 25p) (Overseas P & P £1-25)

Total Building Costs **£2-50** P P & Ins. 26p
(+10% VAT 25p)

TRANS EIGHT

8 TRANSISTORS and 3 DIODES


6 Tuneable Wavebands: MW, LW, SW1, SW2, SW3 and Trawler Band. Sensitive ferrite rod aerial for M.W. and L.W. Telescopic aerial for Short Waves. 3in. Speaker. 8 improved type transistors plus 3 diodes. Attractive case in black with red grille, dial and black knobs with polished metal inserts. Size 9 x 5 1/2 x 2 1/2in. approx. Push pull output. Battery economiser switch for extended battery life. Ample power to drive a larger speaker. Parts price list and plans 25p (FREE with parts).

Total building costs **£4-48** P P & Ins. 33p
(+ 10% VAT 44p)
(Overseas P & P £1-25)

ROAMER SIX


CASE AND LOOKS AS TRANS-EIGHT

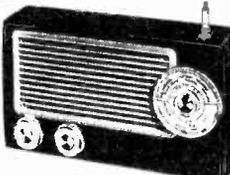6 Tuneable Wavebands: MW, LW, SW1, SW2, etc. Sensitive ferrite rod aerial and telescopic aerial for Short Waves. 3in. Speaker 8 stages - 6 transistors and 2 diodes. Attractive black case with red grille, dial and black knobs with polished metal inserts. Total building costs **£3-98** P P & Ins. 31p
(+ 10% VAT 39p) (Overseas P & P £1-85)



ROAMER TEN

WITH VHF INCLUDING AIRCRAFT

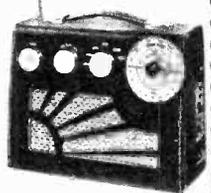

10 Transistors. Latest 4 1/2 watt Ferrite Magnet Loudspeakers. 9 Tuneable Wavebands, MW1, MW2, LW, SW1, SW2, SW3, Trawler Band. VHF and Local Stations also Aircraft Band. Latest 4 1/2 watt ferrite magnet loudspeaker.

Built in Ferrite Rod Aerial for MW/LW. Retractable chrome plated 7 section Telescopic Aerial, can be angled and rotated for peak short wave and VHF listening. Push Pull output using 600mW Transistors. Car Aerial and Tape Record Sockets. 10 Transistors plus 3 Diodes. Ganged Tuning Condenser with VHF section. Separate coil for Aircraft Band. Volume on/off. Wave Change and tone Controls. Attractive Case in black with silver blocking. Size 9" x 7" x 4". Easy to follow instructions and diagrams. Parts price list and plans 30p (FREE with parts).

Total building costs **£8-50** P P & Ins. 52p
(Overseas P & P £1-85) (+ 10% VAT 85p)



"EDU-KIT"

Build Radios, Amplifiers, etc. from easy stage diagrams.

Five units including master unit to construct.

Components include:
Tuning Condenser: 2 Volume Controls: 2 Slider Switches: Fine Tone 3" Moving Coil Speaker: Terminal Strip: Ferrite Rod Aerial: Battery Clips: 4 Tag Boards: 10 Transistors: 4 Diodes: Resistors: Capacitors: Three 1" Knobs. Units once constructed are detachable from Master Unit, enabling them to be stored for future use. Ideal for Schools, Educational Authorities and all those interested in radio construction. Parts price list and plans 25p (FREE with parts).

Total building costs **£5-50** P P & Ins. 33p
(Overseas P & P £1-85) (+ 10% VAT 55p)

RADIO EXCHANGE LTD


★ Callers side entrance "Lavelle" shop.
★ Open 10-1, 2.30-4.30, Mon.-Fri. 9-12 Sat.

To RADIO EXCHANGE CO., 61a HIGH STREET, BEDFORD, MK40 1SA
Tel.: 0234 52387. Reg. No. 788372.

I enclose £..... for.....
Name.....
Address.....
(Dept. PW24.)

R T V C

COMPLETE* STEREO SYSTEM

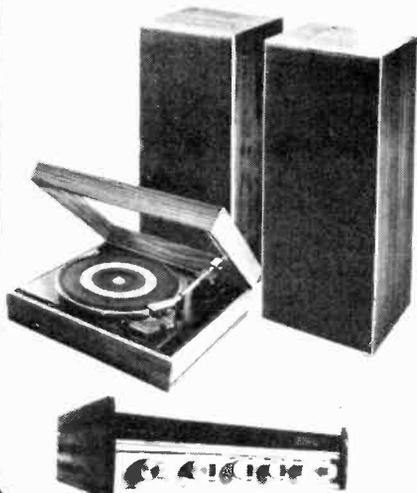

£51.00

40 Watt Amplifier.
Viscount III - R102 now 20 watts per channel.
System I includes.
Viscount III amplifier - volume, bass, treble and balance controls, plus switches for mono/stereo on/off function and bass and treble filters. Plus headphone socket.

Specification
20 watts per channel into 8 ohms.
Total distortion @ 10W @ 1kHz 0.1%. P.U.1 (for ceramic cartridges) 150mV into 3 Meg. P.U.2 (for magnetic cartridges) 4mV @ 1kHz into 47K. equalised within ± 1 dB R.I.A.A. Radio 150mV into 220K. (Sensitivities given at full power).
Tape out facilities: headphone socket, power out 250mW per channel. *None controls and filter characteristics.* Bass: +12dB to -17dB @ 60Hz. Bass filter: 6dB per octave cut. Treble control: treble +12dB to -12dB @ 15kHz. Treble filter: 12dB per octave. *Signal to noise ratio:* (all controls at max.) -58dB.

Crosstalk better than 35dB on all inputs.
Overload characteristics better than 26dB on all inputs. Size approx. 13 $\frac{1}{2}$ " x 9" x 3 $\frac{1}{2}$ ".

Garrard SP25 deck, with magnetic cartridge, de luxe plinth and hinged cover.

Two Duo Type II matched speakers - Enclosure size approx. 17 $\frac{1}{2}$ " x 10 $\frac{1}{2}$ " x 6" in simulated teak. Drive unit 13" x 8" with parasitic tweeter

Complete System £51.00

£69.00

System II
Viscount III amplifier (As System I)
Garrard SP. 25 (As System I)
Two Duo Type IIIA matched speakers—
Enclosure size approx. 31" x 13" x 11 $\frac{1}{2}$ ".
Finished in teak veneer. Drive units approx. 13 $\frac{1}{2}$ " x 8 $\frac{1}{2}$ " with 3 $\frac{1}{2}$ " HF speaker. Max. power 20 watts, 8 ohms. Freq. range 20Hz to 20kHz.

Complete System £69.00

PRICES: SYSTEM 1

Viscount III R102 amplifier	£24.20 + £1 p & p
2 Duo Type II speakers	£14.00 + £2.20 p & p
Garrard SP25 with MAG. cartridge de luxe plinth and hinged cover	£21.00 + £1.75 p & p.
	total £59.20

Available complete for only £51.00 + £3.50 p. & p.

PRICES: SYSTEM 2

Viscount R 102 amplifier	£24.20 + £1 p & p
2 Duo Type IIIA speakers	£39.00 + £4.00 p & p
Garrard SP25 with MAG. cartridge de luxe plinth and hinged cover	£21.00 + £1.75 p & p.
	total £84.20

Available complete for only £69.00 + £4 p & p

STEREO 21



QUALITY SOUND* FOR LESS THAN £19.00

Stereo 21 easy to assemble audio system kit, - no soldering required. Includes:-

BSR 3 speed deck, automatic, manual facilities together with ceramic cartridge.

Two 8" x 5" speakers with cabinets.

Amplifier module. Ready built with control panel, speaker leads and full, easy to follow assembly instructions.

For the technically minded:-

Specifications:

Input sensitivity 600mV; Aux. input sensitivity 120mV; Power output 2.7 watts per channel; Output impedance 8-15 ohms. Stereo headphone socket with automatic speaker cutout.

Provision for auxiliary inputs - radio, tape, etc., and outputs for taping discs. **Overall Dimensions.** Speakers approx.

15 $\frac{1}{2}$ " x 8" x 4". Complete deck and cover in closed position

approx. 15 $\frac{1}{2}$ " x 12" x 6". Complete only **£18.95**

Extras if required.

Optional Diamond Stylus **£1.37** + £1.60 p & p.

Specially selected pair of stereo headphones with individual level controls and padded earpieces to give optimum performance. **£3.85.**



DISCO AMPLIFIER

Reliant Mk IV Mono Amplifier, ideal for the small disco or house parties.

Outputs 20 watts R.M.S. into 8 ohms (suitable for 15 ohms).

Inputs *5 Electrically Mixed Inputs. *3 Individual Mixing controls. *Separate bass and treble controls common to all 5 inputs.

*Mixer employing F.E.T. (Field Effect Transistors). *Solid State Circuitry. *Attractive Styling.

INPUT SENSITIVITIES

1) Crystal Mic or Guitar 9mV. 2) Moving coil Mic or Guitar 8mV. 3), 4), 5) Medium output equipment (Gram. Tuner, Monitor, Organ, etc.) - all 250mV sensitivity.

AC Mains 240V. operation.
Size approx. 12 $\frac{1}{2}$ ins x 6 ins x 3 $\frac{1}{2}$ ins

£13.50 + 60p.

postage & packing.



8 TRACK CARTRIDGE PLAYER*

Elegant self selector push button player for use with your own stereo system. Compatible with Viscount III system, the Stereo 21 and the Unisound module.

Technical specification.

Mains input, 240V. Output sensitivity 125mV

Comparable unit sold elsewhere at £24.00 approx.


Yours for only £10.95 + 90p. p & p



BUILD YOUR OWN STEREO AMPLIFIER*


For the man who wants to design his own stereo - here's your chance to start, with Unisound - pre-amp, power amplifier and control panel. No soldering - just simply screw together. 4 watts per channel into 8 ohms. Inputs: 120mV (for ceramic cartridge). The heart of Unisound is high efficiency I.C. monolithic power chips which ensure very low distortion over the audio spectrum. 240V. AC only. **£7.64 + 55p. p & p**

PE TAPE LINK CONSTRUCTORS

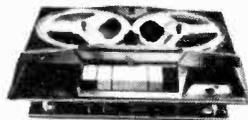

A suitable 3 speed tape deck, less heads. Caters up to 5 $\frac{3}{4}$ ins. spools. 240V AC mains.

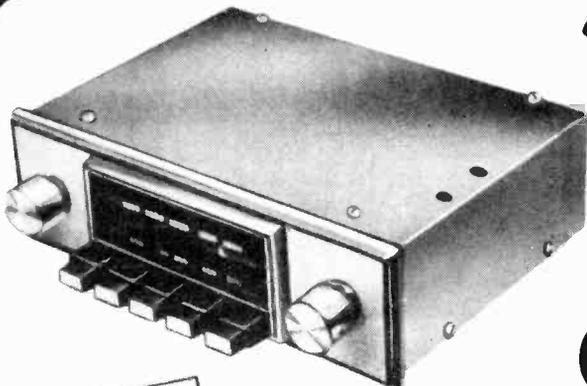Unused but store soiled hence no warranty. **£4.00 + £1.00 p & p**



BUILD YOUR OWN TOURIST PUSH BUTTON CAR RADIO

Technical specification:
 1.) Output 2.5 watts R.M.S. into 8 ohms. For 12 volt operation on negative or positive earth.
 2.) Integrated circuit output stage, pre built three stage IF Module.
 Controls Volume, manual tuning and five push buttons for station selection, illuminated tuning scale covering full medium and long wave bands.
 Size Chassis 7 ins. wide, 2 ins. high and 4 1/8 ins. deep approx.

Remember! one of the Top Ten Accessory Awards from Motor magazine **PUSH BUTTON* CAR RADIO KIT**


NOTE: The ability to solder on a printed circuitboard is necessary to complete this kit successfully. Circuit diagram and comprehensive instructions 55p. free with kit.

Car Radio Kit
£6.60 + 55p. postage & packing.

Speaker including baffle and fixing strips
£1.65 + 23p. postage & packing.

Recommended Car Aerial - fully retractable and locking.
£1.35 post paid.

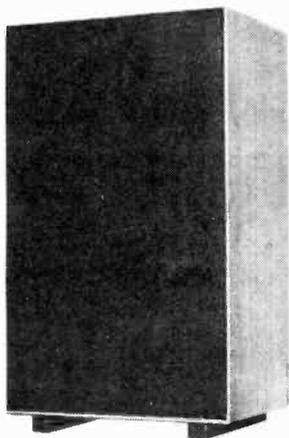
THE ULTIMATE COMPLETE SPEAKER SYSTEM EMI LE 315



Recommended retail selling price, £86-00.
Our price £45-00 + £3.50 postage & packing.

A professional standard five way speaker system with enclosure giving top quality performance.
Enclosure Dimensions approx. (3ft. x 2ft. x 1ft.).
Drive Units
 Hand built - 15" diameter bass with 3" voice coil.
 - two 5" diameter Mid Range units,
 - two 3 1/4" HF. units, plus matching crossover panel with two variable potentiometers for mid and high frequency adjustment.
Powder Handling
 Continuous rating 35 W rms., Peak power rating 70 W.
Frequency Response 20 Hz 20,000 Hz.
 Impedance 8 ohms.

EMI SPEAKERS FANTASTIC REDUCTION

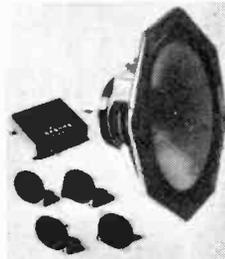

15" 14A/780. Bass unit on a rigid diecast chassis. Superior cone material handles up to 50 watts RMS, and is treated to give a smooth frequency response. Resonance 30 Hz. Flux density 360,000 Maxwells. Impedance at 1 kHz is 8 ohms. 3" voice coil.

Recommended retail price **£40-80.**
OUR PRICE £18-70 + £1-50 p & p

950 Kit - Five matched speakers and crossover unit for handling up to 45 watts, frequency response from 20 to 20,000 Hz.

Huge 19" x 14" (approx.) high efficiency Bass-Speaker with 16,500-gauss magnet built on a heavy diecast frame.

The four 10,000 gauss tweeters, each 3 1/2" dia. approx., are fed by the crossover which critically adjusts signal for maximum fidelity. Impedance at 1 kHz is 8 ohms. Bass coil 2", others 0.5". Recommended list price £44-00.

OUR PRICE £25-00 + £1-50 p & p Special Offer.



Just write your order giving your credit card number

DO NOT SEND YOUR CARD

● Mail orders to Acton. Terms C.W.O. All enquires Stamped Addressed Envelope. Goods not despatched outside U.K.

● Leaflets available for all items listed. * Send stamped addressed envelope.



Radio and TV Components (Acton) Ltd.
21 High Street, Acton, London W3 6NG (C)
323 Edgware Road, London W2

Edgware: 9 a.m.-5.30 p.m. Half day Thurs.
 Acton: 9.30 a.m.-5 p.m. Closed all day Wed.

"SLO-SYN" 3-LEAD SYNCHRONOUS STEPPING MOTOR



MOTOR

Type SS15. These fine motors are easily reversed, starting and stopping in less than 5° without electrical or mechanical braking. Simple relay circuit can be applied to give DC., to winding for a maximum holding torque of 300oz/in with 35v at 0.35 amps through winding. For AC. (synchronous) operation at 120v., 50Hz. Speed 60 rpm at 60Hz., 72 rpm. STEPPING. Holding torque at 50 steps per second—100 oz/in. Can be wired to give 100 or 200 steps per revolution with accuracy of 0.1° per step non-cumulative. Torque characteristics can be modified by simple R.C. circuits. Dimensions: dia. 4", body length 4 1/2", spindle length 2 1/2" x 3/8" dia. Weight 6 1/2 lbs. BRAND NEW in maker's packing. Offered at less than 1/2 maker's price.

OUR PRICE ONLY £15

NORPLEX

Fibre-glass copper-clad laminate. Finest quality epoxy resin base. Heat resistant, ideal for P.C.'s Sizes: 12" x 12"; 24" x 12"; 24" x 24". FULL SHEET 43" x 37" (11 sq ft). Single-sided Copper with thickness of 1/32", 3/64", 3/32". Also double-sided 1/32", 1/16", 3/32". £1 per sq ft. Cut sizes (1-10 sq. ft) 25p. P. & P. Full Sheet £8 each. Carr. £1 for 1st sheet plus 25p each additional sheet.




SMITHS RINGER-TIMER

Reliable 15 minute times. Spring wound (concurrent with time setting) 15 x 1min divisions, approximately 1/2" between divisions. Panel mounting with chrome bezel 3 1/2" dia. £1.40. 15p P. & P.

KNOWLE (U.S.A.) MINIATURE MICROPHONE CAPSULES

Impedance approx. 200Ω, output 60 or 80 DB at 1 Kc. As used in deaf aids, bugging devices, etc. Size (60 DB) 7/32" x 5/32" x 1/4"; (80 DB) 1/2" x 5/32" x 1/4". Equipment, all tested. £1.20 each. P. & P. FREE.

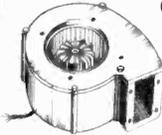Ultra PRECISION CENTRIFUGAL BLOWER by Air Control Ltd.



30 segments individually balanced in heavy cast alloy case. 2,300 r.p.m. 240 A.C. Very powerful and silent running. 5 1/2" dia. 3" Inlet dia. Outlet flange 3" x 2 1/2". LIMITED NUMBER ONLY £8.95. P & P 40p.


MAINS SOLENOID

This little unit gives vertical lift of approximately 1" through hinged "e i b o w". Bracket incorporates 2 fixing screws. Length of arm. 2 1/2". 240V A.C. Pull at coil is approximately 11b. £1. FREE P. & P. Special quotes for quantities.




SOLENOIDS by WESTOOL

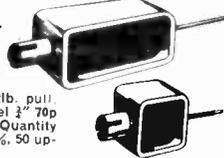240AC type MM6. 3lb. pull, 2 1/2" x 1" x 1 1/2". Travel 1", 90p. each. P. & P. 10p.
240AC type MM4. 2lb. pull 1 1/2" x 1 1/2" x 1". Travel 1/2" 70p each. P. & P. 10p. Quantity discounts: 10-50 10%, 50 upwards 25%.



OPEN FRAME shaded pole GEARED MOTORS

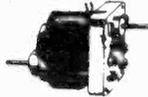(Dural gear case) 240 A.C., 28rpm. NEW HIGH TORQUE approx. overall size: 3 1/2" x 3 1/2" x 2 1/2" + spindle 1/2" dia. as illustrated. £2.70. P. & P. 30p. Similar to above, 19rpm. £2.70. P. & P. 30p. 110rpm with pressed steel gear case (similar to above but slightly smaller). £2.70. P. & P. 30p.




SILVANIA MAGNETIC SWITCH

Now complete with reference magnet!



A magnetically activated switch, vacuum sealed in a glass envelope. Silver contacts, normally closed. Rated 3amp at 120v. 13amp at 240v. Size: (approx.) 1 1/2" long x 1/2" dia. Ideal for burglar alarms, security systems etc., and wherever non-mechanical switching is required. 10 for £2.10; P. & P. 15p. 50 for £8; 100 for £15.50. FREE P. & P. over 10.

AMPEX 7.5v. D.C. MOTOR

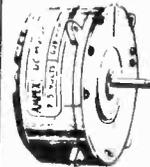


An ultra precision tape motor designed for use in the AG20 portable recorder. Torque 450GM/CM. Stall load at 500ma. Draws 60ma on run. 600rpm ± speed adjustment. Internal AF/RF suppression. 1/2" dia. x 1" spindle, motor 3" dia. x 1 1/2". Original cost £16.50. OUR PRICE £3.30. P. & P. 25p. Quantity available. Mu-metal enclosure available 75p each. FREE P. & P.

ALL PRICES INCLUDE V.A.T.

Whilst we welcome official orders from established companies and Educational Departments, it is no longer practical to invoice goods under £5. Therefore, please remit cash with orders below this amount.

ELECTRO-TECH COMPONENTS LTD.

315/317, EDGWARE ROAD, LONDON, W2.
Tel : 01-723 5667 01-402 5580

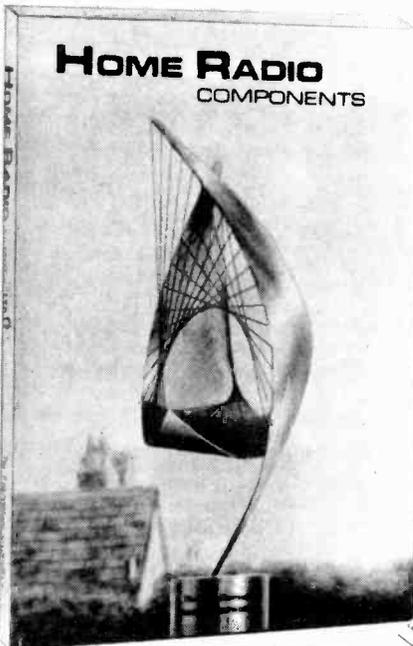

Only 55p.

plus 22p POST AND PACKING

POST THIS COUPON with cheque or P.O. for 77p.

The price of 77p applies only to catalogues purchased by customers in the U.K. and to BFPO addresses.

250 page 11 1/4" x 8 1/4"

6,785 electronic components clearly listed and indexed

1,750 pictures

10 free Vouchers each worth 5p.

Price list regularly updated

Bookmark with useful list of technical abbreviations

The Catalogue you MUST have!

Details of our popular Credit Account Service and our Easy Ordering System are included in the catalogue.

Name _____

Address _____

HOME RADIO (Components) LTD. Regd. No. 912966 London Dept. PW, 234-240 London Road, Mitcham CR4 3HD

BRITAIN'S FASTEST SERVICE!



A SELECTION FROM OUR COMPREHENSIVE CATALOGUE

ALL ITEMS ARE BRAND NEW AND FULLY GUARANTEED

AA119	6p	BCV72	14p	CA3043	£1.57	NKT403	71p	1N4001	4p	2N6027 (D13T1)	45p
AC107	50p	BD124	75p	CA3044	£1.28	NKT404	66p	1N4002	4p	3N84	£1.30
AC126	20p	BD131	40p	CA3046	70p	NKT405	87p	1N4003	5p	3N128	73p
AC127	25p	BD132	40p	CA3048	£2.11	NKT406	69p	1N4004	7p	3N140	92p
AC128	24p	BD131/132	80p	CA3052	£1.62	NMC 409	£1.00	1N4005	8p	3N152	92p
AC128/AC176	44p	BDY20	91p	CA3053	47p	NMC489	66p	1N4006	9p	3N152/TO5	45p
AC151	20p	BF115	23p	CA3065	£1.28	NMC505	£3.00	1N4148	4p	741/8D1L	34p
AC152	25p	BF163	35p	CA3088E	£1.24	NTG D10	40p	1N5400	14p	723/TO5	£1.02
AC153	26p	BF173	29p	CA3089E	£1.94	OA10(NTGD10)	40p	1N5404	18p	723/14D1L	£1.02
AC176	20p	BF167	25p	CA3090Q	£4.23	OA47	8p	1N5408	25p	747/14D1L	48p
AC153/176K	52p	BF178	31p	CA3123E	£1.80	OA79	8p	1S44	4p	748/14D1L	£1.40
AC187K	17p	BF180	35p	CD4000AE	55p	OA90	8p	1S520	7p	30155G	£2.00
AC188K	23p	BF194	15p	CD4001AE	55p	OA91	5p	1S540	6p	30155G	£2.00
AC187/188K	40p	BF195	15p	CD4002AE	£1.11	OA95	5p	2N404	23p	7400	24p
ACV17	27p	BF198	15p	CD4011AE	55p	OA200	6p	2N696	15p	7401	24p
ACV18	20p	BF200	15p	CD4012AE	55p	OA202	7p	2N697	17p	7402	24p
ACV19	20p	BF254	14p	CD4013AE	£1.00	OC25	45p	2N898	37p	7403	24p
ACV20	20p	BF255	15p	CD4015AE	£2.82	OC28	78p	2N708	10p	7404	24p
ACV21	19p	BFX13	25p	CD4017AE	£2.92	OC29	79p	2N708A	12p	7405	30p
ACV22	10p	BFX29	32p	CD4020AE	£3.25	OC36	69p	2N708	18p	7408	30p
AD140	60p	BFX84	25p	CD4022AE	£2.09	OC41	40p	2N911	50p	7409	30p
AD149	44p	BFX85	35p	CD4024AE	£1.73	OC42	40p	2N914	20p	7410	24p
AD161	44p	BFX86	35p	CD4027AE	£4.12	OC44	20p	2N918	42p	7413	30p
AD182	44p	BFX87	24p	CD4029AE	£4.12	OC44	20p	2N929	25p	7420	24p
AD161/162	88p	BFX88	24p	CD4049AE	99p	OC45	20p	2N930	28p	7425	30p
AF106	22p	BFY50	22p	CR1105IC	54p	OC71	20p	2N1131	24p	7430	24p
AF114	27p	BFY51	19p	CRS3/05AF	OC75	OC72	25p	2N1132	24p	7440	24p
AF115	25p	BFY52	20p	CRS3/40AF	OC76	OC75	25p	2N1302	17p	7442	£1.39
AF116	25p	BFY53	17p	CRS3/40AF	OC77	OC81	20p	2N1303	17p	7443	£1.74
AF117	25p	BFY53	17p	CZ6	17p	OC81D	20p	2N1304	24p	7444	£1.74
AF118	44p	BPX66	£1.50	D10 (NTGD)	OC83	OC83	23p	2N1306	30p	7446	£1.74
AF124	25p	BR100	45p	HPS082	29p	OC139	25p	2N1307	39p	7447	£1.50
AF125	24p	BRY39	45p	HS822-33	46p	OC170	25p	2N1308	34p	7450	24p
AF126	24p	BSX19	19p	HT841-33	£2.24	OC171	30p	2N1309	34p	7451	24p
AF139	24p	BSX20	19p	HT891-33	£2.90	OCPT71M	30p	401C	71p	7454	24p
AF186	40p	BSX21	20p	HT341-33	£1.02	ORP12	50p	2N1613	35p	7460	24p
AF239	52p	BSY27	25p	IR2150	35p	ORP69	50p	2N1893	54p	7472	30p
AF279	58p	BSY29	25p	IR2160	46p	ORP61	50p	2N2218	54p	7473	30p
ASV26	25p	BSY95A	12p	IR2160	46p	ORP69	50p	2N2218A	44p	7474	55p
ASV27	30p	BTY79/400R	£1.80	IR220	£2.24	ORP72	50p	2N2219	36p	7475	54p
ASV28	22p	BT106	£1.20	JA424	£2.08	PM742	£1.85	2N2219A	35p	7476	54p
BA138	15p	BY100	20p	MC1303L	£1.75	PM7A6	£2.50	2N2219B	35p	7478	54p
BB103	20p	BY127	22p	MC1305P	£2.80	PN70	10p	2N2368	17p	7480	80p
BB104	34p	BZY88C3V3	10p	MC1307P	£1.65	PN71	10p	2N2369	17p	7482	£1.04
BB105	28p	BZY88C3V6	10p	MC1310P	£2.80	PN107	8p	2N2464	17p	7483	£1.58
BC107	16p	BZY88C3V9	10p	MC1330P	80p	PN108	8p	2N2889A	42p	7486	39p
BC107/BC178	36p	BZY88C4V3	10p	MC1352P	£2.00	PN109	8p	2N2646	45p	7490	84p
BC108	16p	BZY88C4V7	10p	MC1466L	£4.28	PN3619 (2N3819)	20p	2N2904	44p	7491A	£1.54
BC108/BC178	32p	BZY88C5V1	10p	MC1488L	£2.88	SL103A	20p	2N2904A	48p	7492	£1.02
BC109	16p	BZY88C6V2	10p	MC1488L	£2.88	SL403A	50p	2N905	65p	7493	90p
BC109/BC178	32p	BZY88C6V8	10p	MFC4000B	65p	(Rectifier)	60p	2N924	18p	7495	96p
BC109C	18p	BZY88C7V5	10p	MFC6030	£1.18	SL803A	80p	2N925	20p	7496	£1.78
BC117	15p	BZY88C8V2	10p	MFC6040	£1.18	ST2	20p	2N926	10p	74100	£1.97
BC140	30p	BZY88C9V1	10p	MFC8010	£1.38	TA A263	£1.12	2N3053	24p	74107	82p
BC141	12p	BZY88C11V	10p	MFC9020	£2.12	TA A323	£1.25	2N3054	65p	74121	£1.20
BC148	11p	BZY88C12V	10p	MJE371	66p	TA A320	75p	2N3228	£1.10	74150	£4.02
BC149	12p	BZY88C13V	10p	MJE520	65p	TA A861	45p	2N3391A	29p	74151	£1.32
BC157	13p	BZY88C15V	10p	MJE521	62p	TAD100	£1.97	2N3525	£1.04	74153	£1.82
BC158	12p	BZY88C18V	10p	MJE2955	£1.06	TAD110	£1.98	2N3702	14p	74155	£2.40
BC159	13p	BZY88C19V	10p	MJE3065	166p	TBA810S	£1.88	2N3703	12p	74155	£1.86
BC147/157	12p	BZY88C20V	10p	MJ480	97p	TIL112	£2.00	2N3704	12p	74156	£1.86
BC148/158	23p	BZY88C22V	10p	MJ481	£1.25	TL209	30p	2N3705	12p	74190	£2.18
BC149/159	25p	BZY88C24V	10p	MJ491	£1.35	TIP31A	60p	2N3706	12p	74191	£2.09
BC167	11p	BZY88C27V	10p	MJ802	£4.12	TIP32A	70p	2N3707	12p	74192	£2.09
BC168	10p	BZY88C30V	10p	MJ802/MJ4502	£1.94	TIP41A	85p	2N3708	12p	74193	£2.09
BC169	11p	BZY88C32V	10p	MJ900	£1.80	TR3	30p	2N3709	12p	74196	£1.80
BC177	20p	BZX61C9V1	28p	MJ1000	£1.50	T543	30p	2N3710	12p	74197	£1.80
BC178	16p	BZX61C10V	28p	MJ4502	£4.44	VA1039	15p	2N3711	12p	74197	£1.80
BC179	20p	BZX61C11V	28p	MLM309K	£1.90	VA1040	15p	2N3712	12p	74197	£1.80
BC182	14p	BZX61C12V	28p	MPF102	37p	VA1066S	15p	2N3713	£2.50	40309	40p
BC182L	14p	BZX61C13V	28p	MPF103 (2N5457)	VA1077	15p	2N3820	60p	40311	40p	
BC183	13p	BZX61C15V	28p	W05	49p	W005	25p	2N3823E	20p	40312	62p
BC183L	14p	BZX61C16V	28p	MPF104 (2N5458)	W01	26p	2N3826	£1.10	40360	56p	
BC184	17p	BZX61C18V	28p	W02	49p	W02	26p	2N3904	20p	40361	45p
BC184L	16p	BZX61C20V	28p	MPF105 (2N5459)	W04	27p	2N3906	28p	40362	45p	
BC212	18p	BZX61C22V	28p	NE555	78p	W08	32p	2N3958	15p	40406	52p
BC212L	16p	BZX61C24V	28p	NK70033	96p	ZT X108	12p	2N4060	15p	40407	54p
BC238	20p	BZX61C27V	28p	NK7211	25p	ZT X107	11p	2N4062	15p	40409	82p
BC257	11p	BZY93C9V1	70p	NK7212	25p	ZT X302	13p	2N4444	70p	40410	82p
BC258	10p	BZY93C12V	70p	NK7213	25p	ZT X302	13p	2N4444	£2.20	40430	44p
BC259	12p	BZY93C15V	70p	NK7216	46p	ZT X303	15p	2N4571	44p	40468A	£1.92
BC307	12p	BZY93C18V	70p	NK7217	50p	ZT X304	23p	2N4990	66p	40511	£1.54
BC308	10p	CA3001	£2.03	NK7218	25p	ZT X314	11p	2N4991	46p	40575	£1.46
BCY30	25p	CA3005	£1.35	NK7223	27p	ZT X320	30p	2N5245	45p	40576	70p
BCY31	48p	CA3011	83p	NK7271	18p	ZT X330	18p	2N5457 (MPF103)	40600	40601	70p
BCY32	50p	CA3013	£1.17	NK 274	18p	ZT X500	14p	2N5458 (MPF104)	40602	40602	45p
BCY33	20p	CA3014	£1.37	NK7275	20p	ZT X501	15p	2N5458 (MPF105)	40603	40603	50p
BCY34	25p	CA3018	72p	NK7279A	12p	ZT X502	18p	2N5459 (MPF105)	40609	40609	£1.92
BCY38	30p	CA3018A	79p	NK7281	29p	ZT X503	45p	2N5756	£1.20	40739	£1.50
BCY58	18p	CA3020	£1.39	NKT351	75p	TN914	4p	2N5757	£1.20	40739	£1.50
BCY70	15p	CA3028A	79p	NKT401	83p	TN3754	20p	2N5777	45p		
BCY71	26p	CA3035	£1.37	NKT402	83p	TN3754	20p				

CAPACITORS—ELECTROLYTIC AXIAL LEADS

Mfd.	Working Voltage	Price	Mfd.	Working Voltage	Price
1-0	40v	11p	100	15v	10p
1-01	100v	9p	100	25v	10p
2-2	25v	11p	100	40v	11p
2-2	63v	9p	100	63v	14p
4-7	40v	9p	220	25v	12p
10	25v	9p	220	40v	13p
10	63v	10p	270	25v	15p
22	25v	10p	270	25v	23p
47	25v	10p	4700	25v	43p
47	40v	10p		16v	51p

CAPACITORS—METALLISED POLYESTER

Stock values: MFD Price each

0-01, 0-015, 0-022, 0-033	4p
0-047, 0-068, 0-10	5p
0-150, 0-220	6p
0-33	8p
0-47	9p
0-68	12p
1-0	15p
1-5	22p
2-2	26p

Order as "Polyesters" + Capacitance.

CAPACITORS—POLYSTYRENE

Axial leads, Clear encapsulation, 5% Tolerance. 160 volt working. Stock values Price each

10pF, 15pF, 22pF, 33pF, 47pF, 68pF, 100pF, 150pF, 220pF, 330pF, 470pF, 560pF, 680pF, 820pF, 1000pF, 1500pF, 2200pF, 3300pF, 4700pF, 5600pF, 6800pF	4p
--	----

Order as: "Polystyrenes" + Capacitance.

INTEGRATED CIRCUIT PINS

The lowest priced IC mounting available. Pin Sockets come in a reel, just drill your board at required centres, drop in pins and solder,

NEW MULLARD & MAZDA VALVES

All individually boxed and guaranteed. Full trade discounts to bona fide companies. Price and availability lists on application.

EXPRESS POSTAGE

5p for 1 Valve.
Each additional Valve add 2p

DM70	0.88	EF80	0.46	PC86	0.75
DY51	0.88	EF83	1.03	PC88	0.75
DY86/7	0.42	EF86	0.43	PC97	0.45
DY802	0.45	EF86	0.43	PC900	0.58
EABC80	1.00	EF89	0.81	PC884	0.52
EB91	0.78	EF91	1.30	PC889	0.60
EB8C1	0.36	EF92	1.40	PC889	0.61
EBF80	0.80	EF95	1.35	PCF82	1.30
EBF83	0.62	EF183	0.60	PCF86	0.65
EBF89	0.68	EF184	0.60	PCF200	0.95
EC86	0.75	EL90	0.68	PCF201	0.87
EC88	0.77	EL34	0.95	PCF801	0.85
EC8C1	0.45	EL36	1.05	PCF802	0.71
EC8C2	0.45	EL81	0.90	PCF806	0.70
EC8C3	0.45	EL84	0.47	PCF806	0.88
EC8C4	0.55	EL85	0.55	PCF82	0.98
EC8C5	0.58	EL86	0.55	PCF83	0.98
EC8C6	0.75	EL95	0.70	PCL44	0.59
EC8C9	0.71	EL91	1.81	PCL85	0.63
ECF80	0.66	ELL80	1.80	PCL86	0.63
ECF82	0.75	EM64	1.18	PCL805/85	0.63
ECF86	1.01	EM87	1.18	PD500	1.55
ECH81	1.00	EY71	0.88	PL200	0.80
ECH83	1.00	EY86/87	0.42	PL36	0.88
ECH84	0.78	EY88	0.94	PL36	0.88
ECL80	0.53	EZ80	0.51	PL81	0.75
ECL82	0.61	EZ81	0.40	PL81A	0.88
ECL83	0.68	EY601	0.80	PL82	0.60
ECL86	0.63	GZ34	0.78	PL83	0.98

PL84	0.86	30C15/	
PL504	0.88	PCF800	1.05
PL650	1.05	30C17	1.00
PL509	1.55	30C18/	
PL802	0.98	PCF805	0.90
PY33	0.88	30F5/PF818	
PY81/800	0.50		1.10
PY82	0.55	30FL1/	
PC800	0.75	PC800	0.75
PCF12	0.75	30FL12	1.05
30FL14	0.85	30FL14	0.85
30FL1/PC805		30FL1/PC805	
30L15	1.05	30L17	1.30
30P12/PC801		30P12/PC801	
30P19/PC805		30P19/PC805	
30P13/PC801		30P13/PC801	
30P14/PC801		30P14/PC801	
30P15/PC801		30P15/PC801	

TRANSISTORS-INTEGRATED CIRCUITS

All transistors, I.C.'s offered are new and branded. Manufactured by Mullard, Texas, RCA, Ferranti, Motorola, ITT, Fairchild, Lucas, etc. Quantity discounts on application. Send SAE for full lists.

EXPRESS POSTAGE

3p for first Transistor, for each additional add 1p

AA119	0.7	BD132	0.50
AAZ15	0.10	BF115	0.22
AC107	0.35	BF167	0.28
AC126	0.25	BF179	0.33
AC127	0.25	BF180	0.35
AC128	0.20	BF181	0.35
AC176	0.25	BF194	0.13
AC187	0.20	BF195	0.13
AC189	0.20	BF197	0.15
ACY21	0.22	BF200	0.32
ACY39	0.65	BF561	0.25
AD140	0.50	BF598	0.25
AD149	0.50	BFX29	0.28
AD161	0.39	BFX88	0.22
AD162	0.39	BFY50	0.20
AF115	0.25	BFY51	0.20
AF116	0.25	BFY52	0.20
AF117	0.20	BFW10	0.61
AF186	0.40	BY100	0.15
AF239	0.44	BY126	0.14
AFY27	0.80	BY127	0.15
AS528	0.25	BZX61 series	
BA102	0.25	BZX61 series	0.20
BA115	0.10	BZY88 series	
BC107	0.12	CR81-05	0.30
BC108	0.12	CR81-40	0.45
BC109	0.12	CR85-05	0.40
BC113	0.18	CR85-40	0.55
BC117	0.21	CR83-40	0.55
BC143	0.30	MJE340	0.50
BC147	0.12	MJE370	0.68
BC148	0.10	MJE520	0.65
BC169C	0.14	MJE2955	1.10
BC182	0.12	MPE102	0.40
BC184L	0.13	MPE103	0.38
BCY32	1.20	MPE104	0.35
BCY33	0.38	MPE105	0.46
BCY34	0.45	NK7404	0.80
BCY70	0.15	OA5	0.60
BCY71	0.20	OA10	0.40
BCY72	0.15	OA79	0.10
BCZ11	0.65	OA81	0.10
BD121	1.00	OA91	0.07
BD124	0.80	OA300	0.78
BD131	0.45	OA202	0.10
BD132	0.50	ZTX500	0.15
BD133	0.45	ZTX500	0.15
BD134	0.45	ZTX500	0.15
BD135	0.45	ZTX500	0.15
BD136	0.45	ZTX500	0.15
BD137	0.45	ZTX500	0.15
BD138	0.45	ZTX500	0.15
BD139	0.45	ZTX500	0.15
BD140	0.45	ZTX500	0.15
BD141	0.45	ZTX500	0.15
BD142	0.45	ZTX500	0.15
BD143	0.45	ZTX500	0.15
BD144	0.45	ZTX500	0.15
BD145	0.45	ZTX500	0.15
BD146	0.45	ZTX500	0.15
BD147	0.45	ZTX500	0.15
BD148	0.45	ZTX500	0.15
BD149	0.45	ZTX500	0.15
BD150	0.45	ZTX500	0.15
BD151	0.45	ZTX500	0.15
BD152	0.45	ZTX500	0.15
BD153	0.45	ZTX500	0.15
BD154	0.45	ZTX500	0.15
BD155	0.45	ZTX500	0.15
BD156	0.45	ZTX500	0.15
BD157	0.45	ZTX500	0.15
BD158	0.45	ZTX500	0.15
BD159	0.45	ZTX500	0.15
BD160	0.45	ZTX500	0.15
BD161	0.45	ZTX500	0.15
BD162	0.45	ZTX500	0.15
BD163	0.45	ZTX500	0.15
BD164	0.45	ZTX500	0.15
BD165	0.45	ZTX500	0.15
BD166	0.45	ZTX500	0.15
BD167	0.45	ZTX500	0.15
BD168	0.45	ZTX500	0.15
BD169	0.45	ZTX500	0.15
BD170	0.45	ZTX500	0.15
BD171	0.45	ZTX500	0.15
BD172	0.45	ZTX500	0.15
BD173	0.45	ZTX500	0.15
BD174	0.45	ZTX500	0.15
BD175	0.45	ZTX500	0.15
BD176	0.45	ZTX500	0.15
BD177	0.45	ZTX500	0.15
BD178	0.45	ZTX500	0.15
BD179	0.45	ZTX500	0.15
BD180	0.45	ZTX500	0.15
BD181	0.45	ZTX500	0.15
BD182	0.45	ZTX500	0.15
BD183	0.45	ZTX500	0.15
BD184	0.45	ZTX500	0.15
BD185	0.45	ZTX500	0.15
BD186	0.45	ZTX500	0.15
BD187	0.45	ZTX500	0.15
BD188	0.45	ZTX500	0.15
BD189	0.45	ZTX500	0.15
BD190	0.45	ZTX500	0.15
BD191	0.45	ZTX500	0.15
BD192	0.45	ZTX500	0.15
BD193	0.45	ZTX500	0.15
BD194	0.45	ZTX500	0.15
BD195	0.45	ZTX500	0.15
BD196	0.45	ZTX500	0.15
BD197	0.45	ZTX500	0.15
BD198	0.45	ZTX500	0.15
BD199	0.45	ZTX500	0.15
BD200	0.45	ZTX500	0.15

NEW VALVES

Individually boxed and guaranteed but of European or other origin at greatly reduced prices. Quotations for any valve not listed. Send SAE for lists.

A21	0.60	EF80	0.25	PC86	0.80
AZ21	0.55	EF86	0.85	PC88	0.60
CH131	1.20	EF86	0.30	PC97	0.50
CL35	1.50	EF89	0.28	PC900	0.48
CV31	0.50	EF91	0.37	PC884	0.40
DAF91	0.30	EF92	0.50	PC888	0.55
DAF96	0.50	EF95	0.40	PC889	0.50
DDC90	1.85	EF98	0.75	PC889	0.60
DF91	0.80	EF183	0.30	PCF80	0.30
DF96	0.50	EF184	0.35	PCF82	0.35
DK91	0.45	EL32	0.60	PCF86	0.60
DK92	0.70	EL33	1.75	PCF801	0.50
DK96	0.80	EL34	0.50	PCF802	0.50
DL92	0.40	EL36	0.50	PCF805	0.90
DL94	0.48	EL37	2.50	PCF806	0.75
DL96	0.55	EL41	0.90	PCF808	0.90
DY86/7	0.38	EL42	0.90	PCL82	0.35
DY802	0.27	EL84	0.28	PCL83	0.66
EABC80	0.38	EL95	0.40	PCL84	0.45
EAF42	0.75	ELL80	1.00	PCL85	0.50
EB91	0.22	EM80	0.45	PCL86	0.45
EB93	1.00	EM81	0.30	PCL805/85	0.50
EB94	0.75	EM84	0.35		
EB9C1	0.83	EM85	1.00	PD500	1.30
EBF80	0.40	EY51	0.40	PEN45	0.75
EBF83	0.40	EY86	0.40	PL36	0.55
EBF89	0.82	EZ40	0.50	PL508	0.90
ECH31	1.50	EZ41	0.75	PL82	0.45
ECH32	0.40	EZ80	0.28	PL83	0.45
ECH33	0.38	EZ81	0.29	PL84	0.40
ECH34	0.38	EZ82	0.29	PL85	0.75
ECH35	0.38	EZ83	0.29	PL86	0.75
ECH36	0.38	EZ84	0.29	PL87	0.75
ECH37	0.38	EZ85	0.29	PL88	0.75
ECH38	0.38	EZ86	0.29	PL89	0.75
ECH39	0.38	EZ87	0.29	PL90	0.75
ECH40	0.38	EZ88	0.29	PL91	0.75
ECH41	0.38	EZ89	0.29	PL92	0.75
ECH42	0.38	EZ90	0.29	PL93	0.75
ECH43	0.38	EZ91	0.29	PL94	0.75
ECH44	0.38	EZ92	0.29	PL95	0.75
ECH45	0.38	EZ93	0.29	PL96	0.75
ECH46	0.38	EZ94	0.29	PL97	0.75
ECH47	0.38	EZ95	0.29	PL98	0.75
ECH48	0.38	EZ96	0.29	PL99	0.75
ECH49	0.38	EZ97	0.29	PL00	0.75
ECH50	0.38	EZ98	0.29	PL01	0.75
ECH51	0.38	EZ99	0.29	PL02	0.75
ECH52	0.38	EZ00	0.29	PL03	0.75
ECH53	0.38	EZ01	0.29	PL04	0.75
ECH54	0.38	EZ02	0.29	PL05	0.75
ECH55	0.38	EZ03	0.29	PL06	0.75
ECH56	0.38	EZ04	0.29	PL07	0.75
ECH57	0.38	EZ05	0.29	PL08	0.75
ECH58	0.38	EZ06	0.29	PL09	0.75
ECH59	0.38	EZ07	0.29	PL10	0.75
ECH60	0.38	EZ08	0.29	PL11	0.75
ECH61	0.38	EZ09	0.29	PL12	0.75
ECH62	0.38	EZ10	0.29	PL13	0.75
ECH63	0.38	EZ11	0.29	PL14	0.75
ECH64	0.38	EZ12	0.29	PL15	0.75
ECH65	0.38	EZ13	0.29	PL16	0.75
ECH66	0.38	EZ14	0.29	PL17	0.75
ECH67	0.38	EZ15	0.29	PL18	0.75
ECH68	0.38	EZ16	0.29	PL19	0.75
ECH69	0.38	EZ17	0.29	PL20	0.75
ECH70	0.38	EZ18	0.29	PL21	0.75
ECH71	0.38	EZ19	0.29	PL22	0.75
ECH72	0.38	EZ20	0.29	PL23	0.75
ECH73	0.38	EZ21	0.29	PL24	0.75
ECH74	0.38	EZ22	0.29	PL25	0.75
ECH75	0.38	EZ23	0.29	PL26	0.75
ECH76	0.38	EZ24	0.29	PL27	0.75
ECH77	0.38	EZ25	0.29	PL28	0.75
ECH78	0.38	EZ26	0.29	PL29	0.75
ECH79	0.38	EZ27	0.29	PL30	0.75
ECH80	0.38	EZ28	0.29	PL31	0.75
ECH81	0.38	EZ29	0.29	PL32	0.75
ECH82	0.38	EZ30	0.29	PL33	0.75
ECH83	0.38	EZ31	0.29	PL34	0.75
ECH84	0.38	EZ32	0.29	PL35	0.75
ECH85	0.38	EZ33	0.29		

The Largest Selection

BRAND NEW FULLY GUARANTEED DEVICES

Type	Price p	Type	Price p	Type	Price p	Type	Price p	Type	Price p	Type	Price p	Type	Price p	Type	Price p	Type	Price p		
AC107	22	AD161	22	BC150	22	BD131	22	BF182	44	MAT121	22	2G308	39	2N2193	39	2N3391A	18	2N4062	18
AC115	20	AD162(MP)	75	BC151	22	BD132	22	BF183	44	ME2955	95	2G309	39	2N2193	39	2N3392	16	2N4284	19
AC123	22	AD1740	55	BC152	19	BD133	72	BF184	28	ME3055	62	2G339	22	2N2194	39	2N3393	16	2N4285	19
AC117K	32	AF114	27	BC153	31	BD135	44	BF185	33	ME3440	58	2G339A	18	2N2217	24	2N3394	16	2N4286	19
AC122	19	AF115	27	BC154	33	BD136	44	BF187	30	MPF102	46	2G344	29	2N2218	22	2N3402	23	2N4287	19
AC126	19	AF117	27	BC157	20	BD137	50	BF188	44	MPF104	41	2G345	18	2N2219	22	2N3403	16	2N4288	19
AC127	20	AF118	39	BC158	13	BD138	55	BF194	13	MPF105	41	2G371	18	2N2220	24	2N3404	31	2N4289	19
AC128	20	AF124	33	BC160	50	BD140	85	BF195	13	OC19	39	2G371B	13	2N2221	22	2N3404	31	2N4290	19
AC132	18	AF125	33	BC161	55	BD145	81	BF197	16	OC20	70	2G373	19	2N2222	22	2N3405	46	2N4291	19
AC134	18	AF126	31	BC167	13	BD175	66	BF200	50	OC22	52	2G374	19	2N2223	19	2N3414	17	2N4292	19
AC137	18	AF127	31	BC168	13	BD176	66	BF222	£1.05	OC24	62	2G378	18	2N2224	16	2N3415	17	2N4293	19
AC141	20	AF129	33	BC169	13	BD177	72	BF257	50	OC25	42	2G381	18	2N2411	16	2N3416	31	2N5172	13
AC141K	32	AF178	55	BC170	13	BD178	72	BF258	66	OC26	32	2G382	18	2N2412	27	2N3425	31	2N5173	60
AC142	20	AF179	55	BC171	16	BD179	77	BF259	84	OC28	55	2G401	33	2N2416	52	2N3614	74	2N5458	35
AC142K	28	AF180	55	BC172	16	BD180	77	BF262	61	OC29	46	2G417	33	2N2417	22	2N3615	82	2N5459	44
AC151	17	AF181	55	BC173	16	BD185	72	BF263	61	OC35	55	2N2712	23	2N2712	23	2N3616	82	2N6211	75
AC154	22	AF186	55	BC174	16	BD186	72	BF270	39	OC36	55	2N2712	23	2N2712	23	2N3616	10	2N6211	75
AC155	22	AF187	55	BC175	24	BD187	77	BF271	33	OC41	22	2N2712	23	2N2712	23	2N3616	10	2N6211	75
AC156	22	AL102	72	BC177	21	BD188	77	BF272	88	OC42	27	2N2712	23	2N2712	23	2N3616	10	2N6211	75
AC157	27	AL103	72	BC178	21	BD189	83	BF273	39	OC44	27	2N2712	23	2N2712	23	2N3616	10	2N6211	75
AC165	22	ASV26	28	BC179	21	BD190	83	BF274	39	OC45	14	2N2712	23	2N2712	23	2N3616	10	2N6211	75
AC166	22	ASV27	33	BC180	27	BD195	94	BF275	88	OC47	14	2N2712	23	2N2712	23	2N3616	10	2N6211	75
AC167	22	ASV28	28	BC181	27	BD196	94	BF276	88	OC48	14	2N2712	23	2N2712	23	2N3616	10	2N6211	75
AC168	22	ASV29	28	BC182	11	BD197	99	BF277	88	OC49	14	2N2712	23	2N2712	23	2N3616	10	2N6211	75
AC169	16	ASV30	28	BC183	11	BD198	99	BF278	88	OC50	14	2N2712	23	2N2712	23	2N3616	10	2N6211	75
AC176	22	ASV61	28	BC183	11	BD199	£1.05	BF279	88	OC51	14	2N2712	23	2N2712	23	2N3616	10	2N6211	75
AC177	27	ASV62	28	BC183L	11	BD200	£1.05	BF280	88	OC52	14	2N2712	23	2N2712	23	2N3616	10	2N6211	75
AC178	31	ASV63	28	BC184	13	BD205	88	BF281	88	OC53	14	2N2712	23	2N2712	23	2N3616	10	2N6211	75
AC179	31	ASV64	28	BC184L	13	BD206	88	BF282	88	OC54	14	2N2712	23	2N2712	23	2N3616	10	2N6211	75
AC180	31	ASV65	28	BC185	31	BD207	£1.05	BF283	88	OC55	14	2N2712	23	2N2712	23	2N3616	10	2N6211	75
AC180K	32	ASV67	28	BC185L	31	BD208	£1.05	BF284	88	OC56	14	2N2712	23	2N2712	23	2N3616	10	2N6211	75
AC181	22	ASV68	28	BC207	12	BD209	£1.10	BF285	88	OC57	14	2N2712	23	2N2712	23	2N3616	10	2N6211	75
AC181K	32	ASV73	28	BC208	12	BD210	£1.10	BF286	88	OC58	14	2N2712	23	2N2712	23	2N3616	10	2N6211	75
AC187	24	AS221	44	BC209	13	BD211	50	BF287	88	OC59	14	2N2712	23	2N2712	23	2N3616	10	2N6211	75
AC187K	25	BC107	12	BC212L	12	BF118	77	H8X19	17	OC60	14	2N2712	23	2N2712	23	2N3616	10	2N6211	75
AC188	24	BC108	13	BC213L	12	BF119	77	H8X20	17	OC61	14	2N2712	23	2N2712	23	2N3616	10	2N6211	75
AC188K	25	BC109	12	BC214L	12	BF120	77	H8X21	17	OC62	14	2N2712	23	2N2712	23	2N3616	10	2N6211	75
AC189	28	BC113	11	BC215	11	BF121	50	H8X22	17	OC63	14	2N2712	23	2N2712	23	2N3616	10	2N6211	75
AC191	28	BC113	11	BC216	11	BF122	50	H8X23	17	OC64	14	2N2712	23	2N2712	23	2N3616	10	2N6211	75
AC1918	22	BC114	17	BC217	11	BF123	55	H8X24	17	OC65	14	2N2712	23	2N2712	23	2N3616	10	2N6211	75
AC1919	22	BC115	17	BC218	11	BF124	55	H8X25	17	OC66	14	2N2712	23	2N2712	23	2N3616	10	2N6211	75
AC1920	22	BC116	17	BC219	11	BF125	55	H8X26	17	OC67	14	2N2712	23	2N2712	23	2N3616	10	2N6211	75
AC1921	22	BC117	17	BC220	11	BF126	55	H8X27	17	OC68	14	2N2712	23	2N2712	23	2N3616	10	2N6211	75
AC1922	22	BC118	17	BC221	11	BF127	55	H8X28	17	OC69	14	2N2712	23	2N2712	23	2N3616	10	2N6211	75
AC1923	22	BC119	17	BC222	11	BF128	55	H8X29	17	OC70	14	2N2712	23	2N2712	23	2N3616	10	2N6211	75
AC1924	22	BC120	17	BC223	11	BF129	55	H8X30	17	OC71	14	2N2712	23	2N2712	23	2N3616	10	2N6211	75
AC1925	22	BC121	17	BC224	11	BF130	55	H8X31	17	OC72	14	2N2712	23	2N2712	23	2N3616	10	2N6211	75
AC1926	22	BC122	17	BC225	11	BF131	55	H8X32	17	OC73	14	2N2712	23	2N2712	23	2N3616	10	2N6211	75
AC1927	22	BC123	17	BC226	11	BF132	55	H8X33	17	OC74	14	2N2712	23	2N2712	23	2N3616	10	2N6211	75
AC1928	22	BC124	17	BC227	11	BF133	55	H8X34	17	OC75	14	2N2712	23	2N2712	23	2N3616	10	2N6211	75
AC1929	22	BC125	17	BC228	11	BF134	55	H8X35	17	OC76	14	2N2712	23	2N2712	23	2N3616	10	2N6211	75
AC1930	22	BC126	17	BC229	11	BF135	55	H8X36	17	OC77	14	2N2712	23	2N2712	23	2N3616	10	2N6211	75
AC1931	22	BC127	17	BC230	11	BF136	55	H8X37	17	OC78	14	2N2712	23	2N2712	23	2N3616	10	2N6211	75
AC1932	22	BC128	17	BC231	11	BF137	55	H8X38	17	OC79	14	2N2712	23	2N2712	23	2N3616	10	2N6211	75
AC1933	22	BC129	17	BC232	11	BF138	55	H8X39	17	OC80	14	2N2712	23	2N2712	23	2N3616	10	2N6211	75
AC1934	22	BC130	17	BC233	11	BF139	55	H8X40	17	OC81	14	2N2712	23	2N2712	23	2N3616	10	2N6211	75
AC1935	22	BC131	17	BC234	11	BF140	55	H8X41	17	OC82	14	2N2712	23	2N2712	23	2N3616	10	2N6211	75
AC1936	22	BC132	17	BC235	11	BF141	55	H8X42	17	OC83	14	2N2712	23	2N2712	23	2N3616	10	2N6211	75
AC1937	22	BC133	17	BC236	11	BF142	55	H8X43	17	OC84	14	2N2712	23	2N2712	23	2N3616	10	2N6211	75
AC1938	22	BC134	17	BC237	11	BF143	55	H8X44	17	OC85	14	2N2712	23	2N2712	23	2N3616	10	2N6211	75
AC1939	22	BC135	17	BC238	11	BF144	55	H8X45	17	OC86	14	2N2712	23	2N2712	23	2N3616	10	2N6211	75
AC1940	22	BC136	17	BC239	11	BF145	55	H8X46	17	OC87	14	2N2712	23	2N2712	23	2N3616	10	2N6211	75
AC1941	22	BC137	17	BC240	11	BF146	55	H8X47	17	OC88	14	2N2712	23	2N2712	23	2N3616	10	2N6211	75
AC1942	22	BC138	17	BC241	11	BF147	55	H8X48	17	OC89	14	2N2712	23	2N2712	23	2N3616	10	2N6211	75
AC1943	22	BC139	17	BC242	11	BF148	55	H8X49	17	OC90	14	2N2712	23	2N2712	23	2N3616	10	2N6211	75
AC1944	22	BC140	17	BC243	11	BF149	55	H8X50	17	OC91	14	2N2712	23	2N2712	23	2N3616	10	2N6211	75
AD130	42	BC141	33	BC244	11	BF150	55	H8X51	17	OC92	14	2N2712	23	2N2712	23	2N3616	10	2N6211	75
AD140	53	BC142	33	BC245	11	BF151	55	H8X52	17	OC93	14	2N2712	23	2N2712	23	2N3616	10	2N6211	75
AD142	53	BC143	33	BC246	11	BF152	55	H8X53	17	OC94	14	2N2712	23	2N2712	23	2N3616	10	2N6211	75
AD143	53	BC144	33	BC247	11	BF153	55	H8X54	17	OC95	14	2N2712	23	2N2712	23	2N3616	10	2N6211	75
AD1																			

-the lowest prices!

BRAND NEW TEXAS GERM. TRANSISTORS

Coded and Guaranteed

Pak No.	QVVT
T1	8 203713 OC71
T2	8 11374 OC75
T3	8 11216 OC81D
T4	8 20381 OC82
T5	8 20382T OC82
T6	8 20344B OC44
T7	8 20345B OC45
T8	8 20378 OC78
T9	8 20399A 2N1307
T10	8 20417 AF117

All 55p each pak

ND 120 NIXIE DRIVER TRANSISTOR.

Suitable replacement for 8BX21, C407, 2N 1893 120vcb.

	25	100
0.19	0.17	0.18

80L trans. suitable for P.E. Organ. Metal TO-18 Evt. ZFN300 8p each. Any Qty.

GP 100 TO3 METAL CASE GERMANIUM

V_{be} = 80V. V_{ceo} = 50V. I.C. = 10 amps. Ptot = 30W. hfe = 30-170. Replaces the majority of germanium power transistors in the OC, AD and NKT range.

	25	100
0.48	0.44	0.40

GP 800 TO3 METAL CASE SILICON

V_{be} = 100V. V_{ceo} = 60V. I.C. = 15 amps. Ptot = 115W. hfe = 20-100T. M.H.Z. Suitable replacement for 2N 3055, BDY 11 or BDY 20.

	25	100
0.55	0.53	0.51

NEW 8th EDITION TRANSISTOR EQUIVALENTS BOOK.

A complete cross reference and equivalents book for European, American and Japanese Transistors. Exclusive to BI-PAK. £1.85 each.

A LARGE RANGE OF TECHNICAL AND DATA BOOKS ARE NOW AVAILABLE EX STOCK. SEND FOR FREE LIST.

UT 48 UNIJUNCTION TRANSISTORS

Direct replacement for TIS 43rand REN 3000 also electrically equivalent to 2N2642

	25	100
0.30	0.28	0.22

GENERAL PURPOSE NPN SILICON SWITCHING TRANS. TO-18 SIM TO 2N706/8. BSY-27/28/95A.

All usable devices no open or short circuits. ALSO AVAILABLE in PNP Sim. to 2N2906, BSY70. When ordering please state preference NPN or PNP.

	20	For	5p
20	For	0.55	
50	For	1.10	
100	For	1.92	
1000	For	8.25	
1000	For	14.30	

SIL. G.P. DIODES 5p

	300mW	300..0.55
40PIV(Min.)	100..1.85	
Sub-Min.	500..5.50	
Fully Tested 1,000..8.90		
Ideal for Organ Builders.		

R 2400 TO3 NPN SILICON HIGH VOLTAGE

V_{be} 250V. V_{ceo} 100V. I.C. = 6 amps. Ptot = 30W. hfe typ. 20 FT. 5MHz.

	25	100
0.55	0.50	0.44

AD161/162

M/P COMP GERM TRANS. OUR LOWEST PRICE OF 75p PER PAIR.

LOOK FOR OUR AUDIO & ELECTRONIC COMPONENTS ADVERTISEMENTS in PRACTICAL ELECTRONICS RADIO CONSTRUCTOR

SILICON PHOTO TRANSISTOR.

TO-18 Lens end NPN Sim. to BPX25 and P21. BRAND NEW. Full data available. Fully guaranteed.

Qty. 1-24 25-99 100 up
Price ea. 80p 44p 38p

INTEGRATED CIRCUIT PAKS

Manufacturers "Fall Outs" which include Functional and Part-Functional Units. These are classed as out-of-spec from the maker's very rigid specifications, but are ideal for learning about I.C.'s and experimental work.

Pak No.	Contents	Price
UI000	-12 x 7400	0.55
UI001	-12 x 7401	0.55
UI002	-12 x 7402	0.55
UI003	-12 x 7403	0.55
UI004	-12 x 7404	0.55
UI005	-12 x 7405	0.55
UI006	-8 x 7406	0.55
UI007	-8 x 7407	0.55
UI010	-12 x 7410	0.55
UI020	-12 x 7420	0.55
UI030	-12 x 7430	0.55
UI040	-12 x 7440	0.55
UI041	-5 x 7441	0.55
UI042	-5 x 7442	0.55
UI043	-5 x 7443	0.55
UI044	-5 x 7444	0.55
UI045	-5 x 7445	0.55

QUALITY TESTED SEMICONDUCTORS

Pak No.	Description	Price 5p
Q1	20 Red spot transistors PNP	0.55
Q2	16 White spot R.F. transistors PNP	0.55
Q3	4 OC 77 type transistors	0.55
Q4	6 Matched transistors OC44/45/81/81D	0.55
Q5	4 OC 75 transistors	0.55
Q6	5 OC 72 transistors	0.55
Q7	4 AC 128 transistors PNP high gain	0.55
Q8	4 AC 128 transistors PNP	0.55
Q9	7 OC 81 type transistors	0.55
Q10	7 OC 71 type transistors	0.55
Q11	2 AC 127/128 Complementary pairs PNP/NPN	0.55
Q12	3 AF 116 type transistors	0.55
Q13	3 AF 117 type transistors	0.55
Q14	3 OC 171 H.F. type transistors	0.55
Q15	7 2N2926 80. Epoxy transistors mixed colours	0.55
Q16	2 GET880 low noise Germanium transistors	0.55
Q17	5 NPN 2 x HT.141 & 3 x HT.140.	0.55
Q18	4 MATT8 2 x MAT 100 & 2 x MAT 120	0.55
Q19	3 MATT8 2 x MAT 101 & 1 x MAT 120	0.55
Q20	4 OC 44 Germanium transistors A.F.	0.55
Q21	4 AC 127 NPN Germanium transistors	0.55
Q22	20 NKT transistors A.F. R.F. coded	0.55
Q23	10 OA 202 Silicon diodes sub-min.	0.55
Q24	8 OA 81 diodes	0.55
Q25	15 IN914 Silicon diodes 75 PIV 75mA	0.55
Q26	4 OA95 Germanium diodes sub-min	0.55
Q27	2 10A PIV Silicon rectifiers 18428 R.	0.55
Q28	2 Silicon power rectifiers BYZ 13	0.55
Q29	4 Silicon transistors 2 x 2N690, 1 x 2N697, 1 x 2N698	0.55
Q30	7 Silicon switch transistors 2N706 NPN	0.55
Q31	6 Silicon switch transistors 2N708 NPN	0.55
Q32	3 PNP Silicon transistors 2 x 2N1131, 1 x 2N1132	0.55
Q33	3 Silicon NPN transistors 2N1711	0.55
Q34	7 Silicon NPN transistors 2N2369, 600MHz (code P397)	0.55
Q35	3 Silicon PNP TO-5, 2 x 2N2904 & 1 x 2N2905	0.55
Q36	7 2N3646 TO-18 plastic 300 MHz NPN	0.55
Q37	3 2N3053 NPN Silicon transistors	0.55
Q38	7 NPN transistors 4 x 2N3703, 3 x 2N3707	0.55

ELECTRONIC SLIDE-RULE

The MK Slide Rule, designed to simplify Electronic calculations features the following scales: Conversion of Frequency and Wavelength. Calculation of L, C and f of Tuned Circuits. Reactance and Self Inductance. Area of Circles. Volume of Cylinders. Resistance of Conductors. Weight of Conductors. Decibel Calculations. Angle Functions. Natural Logs and 'e' Functions. Multiplication and Division. Squaring, Cubing and Square Roots. Conversion of kW and Hp.

A must for every electronic engineer and enthusiast. Size: 25 cm x 4cm. Complete with case and instructions. Price each: £3.69

FULL RANGE OF ZENER DIODES

2-33V. 400mW (D0-7 Class) 12p ea. 11W (Top Hat) 18p ea. 10W (80-10 Stud) 32p ea.

NEW LOW PRICED TESTED D.C.'S

PIV 1A	3A	5A	5A	7A	10A	16A	30A
T05	T06	T06	T06	T04	T04	T04	T04
50	0.26	0.28	0.39	0.52	0.55	0.59	1.27
100	0.28	0.37	0.52	0.52	0.55	0.64	1.54
200	0.39	0.41	0.54	0.54	0.63	0.67	1.76
400	0.48	0.52	0.62	0.62	0.74	0.83	1.93
800	0.59	0.63	0.75	0.75	0.85	1.07	1.38
800	0.70	0.77	0.88	0.88	0.99	1.32	1.65

F.E.T.'S

2N3819	31p	2N5458	35p
2N3820	55p	2N5459	44p
2N3821	80p	BFW10	80p
2N3823	31p	MPE105	41p

CADMIUM CELLS

ORP12 48p

FREE

One 55p Pak of your own choice free with orders valued £4 or over

2N3055

115 WATT SIL POWER NPN 55p EACH

KING OF THE PAKS Unequaled Value and Quality

SUPER PAKS NEW BI-PAK UNTESTED SEMICONDUCTORS

Money back refund if not satisfied

Pak No.	Description	Price 5p
U 1	120 Glass Sub-Min. General Purpose Germanium Diodes	0.55
U 2	60 Mixed Germanium Transistors AF/RFF	0.55
U 3	75 Germanium Gold Bonded Sub-Min. like OA5, OA47	0.55
U 4	40 Germanium Transistors like OC81, AC128	0.55
U 5	60 200mA Sub-Min. Silicon Diodes	0.55
U 6	30 80L Planar Trans. NPN like B8Y96A, 2N706	0.55
U 7	16 80L Rectifiers TOP-HAT 750mA VLTG. RANGE up to 1000 0.55	
U 8	50 80L Planar Diodes DO-7 Glass 260mA like OA200/202	0.55
U 9	20 Mixed Voltages, 1 Watt Zener Diodes	0.55
U10	20 BA750 charge storage Diodes DO-7 Glass	0.55
U11	25 PNP Sil. Planar Trans. TO-5 like 2N1132, 2N2904	0.55
U12	12 Silicon Rectifiers Epoxy 500mA up to 800 PIV	0.55
U13	30 PNP-NPN Sil. Transistors OC200 & 2N 104	0.55
U14	150 Mixed Silicon and Germanium Diodes	0.55
U15	25 NPN Sil. Planar Trans. TO-5 like BFY51, 2N697	0.55
U16	10 3 Amp Silicon Rectifiers Stud Type up to 1000PIV	0.55
U17	30 Germanium PNP AF Transistors TO-5 like ACY 17-22	0.55
U18	8 4 Amp Silicon Rectifiers BYZ13 Type up to 600 PIV	0.55
U19	25 Silicon NPN Transistors like BC108	0.55
U20	12 1.5 Amp Silicon Rectifiers Top Hat up to 1000 PIV	0.55
U21	30 AF Germanium Alloy Transistors 20300 Series & OC71	0.55
U22	30 MATT8 like MHz Series PNP Transistors	0.55
U23	20 Germanium 1 Amp Rectifiers GJM Series up to 300 PIV	0.55
U24	25 300 MHz NPN Silicon Transistors 2N708, BRY27	0.55
U25	30 Fast Switching Silicon Diodes like IN914 Micro-Min.	0.55
U26	12 NPN Germanium AF Transistors TO-1 like AC127	0.55
U27	10 1 Amp SCR's TO-5 can. up to 600 PIV CRN1/25-600	1.10
U30	15 Plastic Silicon Planar Trans. NPN 2N2926	0.55
U31	20 Silicon Planar Plastic PNP Trans. Low Noise Amp 2N3707	0.55
U32	25 Zener Diodes 400mW DO-7 case 3-18 volts mixed	0.55
U33	15 Plastic Case 1 Amp Silicon Rectifiers IN4000 Series	0.55
U34	30 Silicon PNP Alloy Trans. TO-5 BCU26 28302/4	0.55
U35	25 Silicon Planar Transistors PNP TO-5 2N2906	0.55
U36	25 Silicon Planar NPN Transistors TO-5 BFY50/51/52	0.55
U37	30 Silicon Alloy Transistors 80-2 PNP OC200, 28322	0.55
U38	20 Fast Switching Silicon Trans. NPN 400 MHz 2N3011	0.55
U39	30 RF, Germ. PNP Transistors 2N1303/5 TO-5	0.55
U40	10 Dual Transistors 6 lead TO-6 2N2060	0.55
U41	25 RF Germanium Transistors TO-1, OC45, NKT72	0.55
U42	10 VHF Germanium PNP Transistors TO-1 NKT667, AF117	0.55
U43	25 Sil. Trans. Plastic TO-18 A.F. BC113/114	0.55
U44	20 Sil. Trans. Plastic TO-5 BCU115/116	0.55
U45	7 3A SCR. TO68 up to 600PIV	1.10

Code No's. mentioned above are given as a guide to the type of device in the pak. The devices themselves are normally unmarked.

SIL. RECTS. TESTED

PIV 300mA	750mA	1A	1.5A	3A	10A	30A
50	0.04	0.06	0.06	0.08	0.16	0.23
100	0.04	0.07	0.06	0.15	0.18	0.26
200	0.06	0.10	0.07	0.16	0.22	0.27
400	0.07	0.15	0.08	0.22	0.30	0.41
600	0.08	0.18	0.11	0.26	0.38	0.50
800	0.11	0.19	0.12	0.28	0.41	0.51
1000	0.12	0.24	0.18	0.33	0.51	0.70
1200	0.12	0.28	0.18	0.33	0.51	0.72

DIACS

FOR USE WITH TRIACS. BR100 (D32) 41p each

10 AMP POTTED BRIDGE RECTIFIER

on heat sink. 100PIV. 99p each

Giro No. 388-7006

Please send all orders direct to warehouse and despatch department

BI-PAK

P.O. BOX 6, WARE - HERTS

Postage and packing add 11p. Overseas add extra for airmail. Minimum order 55p. Cash with order please. Guaranteed Satisfaction or Money Back

2 Amp. BRIDGE RECTS.

	50 v RMS	85p each
100 v RMS	40p ..	
400 v RMS	50p ..	
812 v 16 mm x 16 mm.		

D1699 NPN SILICON DUAL TRANSISTOR

(Similar to 2N2906)

	1	25	100
0.28	0.28	0.23	0.38

BIP 18/20 TO3 NPN PLASTIC SILICON

V_{be} = 100V. V_{ceo} = 50V. I.C. = 10 amps. Ptot = 50W. hfe = typ. 100 FT = 3MHz.

	25	100
0.35	0.25	0.10
0.38	0.25	0.32
0.58	0.61	0.55

Out now!

HEAT Free



Get the Heathkit Catalogue..and save

Handcrafted electronics with built-in quality and kit form savings. Heath offer you outstanding specifications and plus values that will impress you, your family and friends. Want to know more? Send for your personal introduction to the international world of Heathkit electronics... the Free Heathkit Catalogue.


Free Please send me the FREE Heathkit Catalogue & details of Monthly budget plans.

NAME _____

ADDRESS _____

HEATH Schlumberger
HEATH (GLOS.) LTD. DEPT. PW 5/74
 Bristol Road,
 Gloucester GL2-6EE


EnCase ENVIRONMENTAL HOUSING

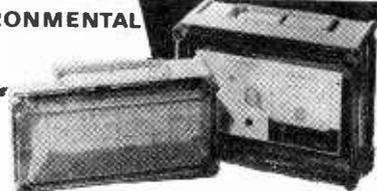

A cleverly designed protected polycarbonate enclosure; weatherproof, dustproof and damp and heat protecting. It's high impact strength will withstand rough handling. The seven sizes can interconnect and any case will extend vertically or horizontally or both, while maintaining full protection. Send for new catalogue. Many extras available incl. hinges etc.

Encase includes chassis, retaining screws, cover, gasket, cover retaining screws; price includes P. & P. and 10% VAT.

ENA	7 1/2" x 7 1/2" x 5"	£4-15
ENB	11" x 7 1/2" x 5"	£5-32
ENC	15" x 7 1/2" x 5"	£7-07
END	11" x 11" x 5"	£7-22
ENE	15" x 11" x 5"	£9-24
ENF	22" x 11" x 5"	£12-77
ENG	22" x 15" x 7"	£17-66

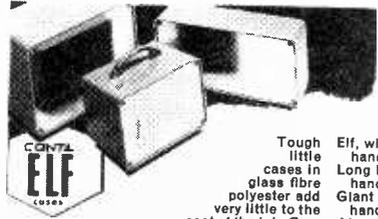

Tough little cases in glass fibre polyester add very little to the cost of the job. Grey or blue with protected aluminium front panel (16 s.w.g.)

1 off	4 off
Elf, with handle 6" x 4" x 4"	£1-76 £1-35
Long Elf, no handle 9" x 4" x 3"	£1-81 £1-81
Giant Elf, no handle 8" x 5 1/2" x 5"	£2-97 £2-97


Also available without panels. Less for quantities. Prices include feet, P. & P. and 10% VAT.



A smart miniature case in tough, rigid, high-gloss black A.B.S. Front panels in either aluminium or white PVC/Steel. Built-in slots for PC cards, dividers, or screens. Chassis or PC boards can be supported on 'I' clips from internal pillars. Excellent as encapsulation boxes. Also available without panel and screws. Minimum order £1.

1 off	1 off
M2 65mm x 100mm x 50mm	47p 40p
2 1/2" x 3 1/2" x 2"	63p 55p
M3 100mm x 130mm x 50mm	
3 1/2" x 5" x 2"	

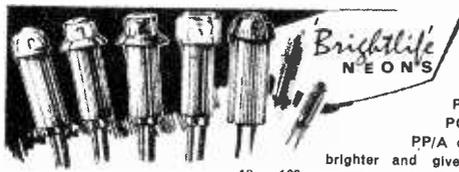Prices include P. & P. and 10% VAT. Less for quantities.



dia.	leads	volts	10 off	100 off
1/4" PC/A to I	6"	110 or 160-260	16p	15p
1/4" PC/A to I	30"	110 or 160-260	18p	17p
1/4" PP/A	6"	110 or 160-260	16p	15p
1/4" PP/A	30"	110 or 160-260	18p	17p
Q type	none	110 or 160-260	28p	26p
S type	none	160-260	28p	26p

Add 15p P. & P. any quantity, then add 10% VAT. Min. quantity each type 10 off.

Brightlife neons, illustrated are PC/A or C, PC/F, PC/D, PC/G or I, PP/A or B, Q & S, are brighter and give an average of 25,000 hrs. life. The 0.375" dia. are red or white, the 0.375" are red, amber or all may be supplied for 115, 240V, or the PP neons in 110, 240 and 440V. with 6" or 30" leads. Send for details in new catalogue.



W.	H.	D.	1 off	W.	H.	D.	1 off
A	4-5"	3"	£3-17	M	4-5"	3"	£3-91
B	4-5"	7"	£2-91	N	4-5"	7"	£4-79
C	4-5"	10"	£4-32	O	4-5"	10"	£6-07
D	9"	3"	£4-32	P	9"	3"	£4-79
E	9"	7"	£4-79	Q	9"	7"	£4-79
F	9"	10"	£5-32	R	9"	10"	£7-39
G	13"	3"	£4-79	S	13"	3"	£6-07
H	13"	7"	£5-52	T	13"	7"	£7-39
I	13"	10"	£6-07	U	13"	10"	£8-95
J	18"	3"	£5-52	V	18"	3"	£8-95
K	18"	7"	£7-39	W	18"	7"	£7-39
L	18"	10"	£8-95	X	18"	10"	£10-70

Woodgrain: D @ £4-79, E & G @ £5-52, H @ £9-07. Includes screws, feet, chassis, P. & P. and 10% VAT. Prices correct to 30th April.


The design of these cases permits the instrument to be built or serviced within their external panels. 48 shapes. Low cost. Blue PVC/Steel with white P.V.C./aluminium.

WEST HYDE
WEST HYDE DEVELOPMENTS LTD., RYEFIELD CRES., NORTHWOOD HILLS, MIDDX. HA9 1NN.
 Tel: Northwood 24941 or 26732 Telex: 922321

Cool lighting **for hot parties.**

Velvet dim to full brightness at a touch of the finger. Off/on and infinitely variable.

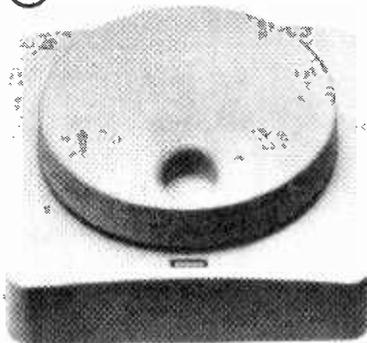Beta light glow makes switch easy to find in the dark and consumes no current.



Economical too!

As the light is progressively dimmed, so the current consumption drops – think of it as an electric tap. 300 watt capacity, straight replacement for standard light switch.

Complete kit of parts £2.80 or made up £2.90.



Hot Ignition **for cold mornings.**

The Jermyn capacitor discharge ignition system.


Instant starting in all weathers. Even with a near flat battery, the unit will produce a full sized spark.

Just one of the many advantages of an electronic ignition system, the others are:

High energy spark even at maximum revs.

Smoother running.
Less strain on battery and starter.
Lower petrol consumption.
Long plug life with infrequent adjustment (typically 20,000 miles, gapped at .050").
No contact breaker arcing giving long life and less adjustment (typically 20,000 – 25,000 miles)

STATE + or – earth when ordering.

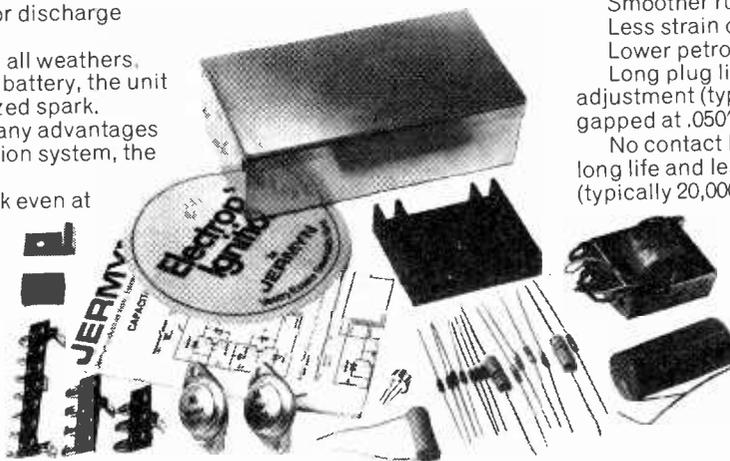

Complete set of parts to build it yourself for only £7.75, as described in Practical Wireless and fully approved by the author.

Save 55p
Buy both for £10.00

Reprints of the two part feature are available at 25p.

To Jermyn Industries, 149 Vestry Estate, Sevenoaks, Kent.

All Prices Exclusive of V.A.T.

Please despatch return of post light dimmer kit light dimmer
Ignition Kits + or – earth £10 pair. Enclose cheque or postal order.

BLOCK CAPITALS

NAME


ADDRESS.....

JERMYN

MANUFACTURERS OF ELECTRONIC AND AMPLIFICATION EQUIPMENT
SPECIALISTS IN QUALITY TRANSISTOR EQUIPMENT
OPEN 6 DAYS A WEEK. 9.00 a.m.-6.00 p.m.



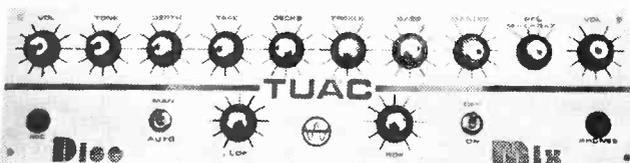TRANSISTOR UNIVERSAL
AMPLIFICATION COMPANY LTD.
DEPT. W
163 MITCHAM ROAD, LONDON SW17 9PG
01-672 3137/9080



TUAC DISCOTHEQUE MIXER WITH AUTO FADE

Designed for the discerning D.J. of professional standard. Offering a vast variety of functions.

£25.50

Controls: Mic Vol, Tone, Over-ride depth, Auto Manual Sw. Tape Vol, L&R Deck Faders. Deck Volume. Treb. & Bass. H. Phon Vol, Selector. Master Vol, on/off sw. Max. output 1V RMS.

PANEL SIZE 18" x 4 1/2" DEPTH 3"

POWER SUPPLY £4.00p


NEW!

3 CHANNEL LIGHT MODULATOR

- ★ 1,000 watts per channel
- ★ Operates from 1/8th watt to 100 watts
- ★ Full wave control
- ★ Fully fused and suppressed
- ★ 10 easy connections

£17.25

Single channel version £6.50p

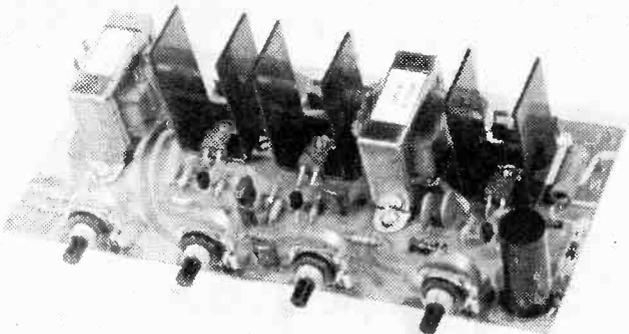

ALL PRICES INCLUDE V.A.T. AND POSTAGE AND PACKING

ACCESS & BARCLAY CARDS ACCEPTED, JUST SEND US YOUR NUMBER. H.P. ARRANGED THROUGH PAYBONDS

TRANSISTORISED F.M. tuner head with A.M. gang, slow motion drive. 88-108Mcs, with circuit diagram. £2.30p.

P-C BOARDS (not computer panels)

1 off 6 transistors single wave band

1 off 4 transistor audio

1 off 3 transistor £1.60 the three.

LIGHT DEPENDENT RESISTORS (RCA sq3536) 30p each, 4 for £1.00.

ELECTROLYTIC CAPACITORS.

32/32 32µf. 325v. 2" x 1 1/4", 35p.

3000µf. 500v. 4" x 1 1/4", 40p.

2000µf. 300v. 2" x 1 1/4", 25p.

2000µf. 30v. 2 1/4" x 1", 25p.

2000µf. 35v. 3" x 1", 30p.

470µf. 100v. 3" x 1 1/4", 25p.

2000/2000µf. 25v. 2" x 1 1/4", 35p.

30,000µf. 25v. 4 1/2" x 2 1/4", 50p.

200µf 350v/300/100/32µf. 300v 3" x 2", 50p.

700µf 200v. 3 1/4" x 1 1/4", 30p.

16/16µf. 275v. 1 1/4" x 1 1/4", 20p.

40/40/20µf. 275v. 3" x 1", 20p.

4000/500/900/900µf. 30v. 2 1/4" x 1 1/4", 50p.

2500µf. 40v. 3" x 1 1/4", 40p.

4000µf. 35v. 3" x 1 1/4", 40p.

200/100/50/100µf. 325v. 3" x 1 1/4", 50p.

CRYSTAL CALIBRATOR (Second Hand) No. 10 crystal controlled heterodyne wave-meter covering 500KHz-10MHz (harmonics up to 30MHz) power required 300V DC 15mA. 12V 0.3A DC. Test equipment for 62T M/RC. £2.50 each.

WIRE-WOUND RESISTORS. Our selection of mixed Ohms and Watts. 25 for £1.50, 50 for £2.50, parcel of 1,000 £30.00.

AUDIO AMPLIFIER MODULE. Due to bulk purchase we can now offer the Audio Amplifier Module (Mullard LP1173) output power, nominal 10 watt. Supply voltage + 24 volt, with reference data for £2.50.

ALL ITEMS INCLUDE VAT

All items post paid in GREAT BRITAIN

SURPLECTRONICS

216 LEAGRAVE ROAD, LUTON, LU3 1JD, BEDS.

PLUGS & LEADS

Plugs
Pack 107 5 pin Din 25p
Pack 108 3 pin Din 20p
Pack 135 1/4" jack 30p
Pack 130 1/4" Jack Stereo 50p
Pack 103 Loudspeaker Plug 20p
Pack 100 Phono Plug 10p
Pack 230 3 pin Socket 25p
Pack 236 5 pin Socket 35p
Pack 234 Loudspeaker Socket 35p

Ready-made Leads
3 pin to 3 pin Din 70p
3 pin to open end 55p
5 pin to 5 pin Din £1.00
5 pin to open end 70p
5 pin to 4 phono plugs £1.00
All leads approx. 6ft. in length
Speaker lead Din to spade 12ft 50p
Extension lead Din plug to socket 12ft. 80p

DIAMOND STYLI
8TA; 9TA; 9TAHC; GP91; ST4; ST9; EV26; GC8.All at 80p each.
Double Diamond £1.25
Diamond suitable for Orbit NM22; G800; M3D £2.25 each

CARTRIDGES
Goldring G800 £6.00
Orbit NM22 £4.00
Shure 75/6 £6.00
Sonotone 9TAHC (Dia) £2.00
Sonotone 8T4A (Dia) £1.50
Ronnette 105 (Dia) £1.25

Prices include VAT and post
Prices correct at time of going to press but subject to change without notice

RECORD CARE

Cecil Watts Dust Bug £1.20
Parastatic Disc Preener 45p
Antistatic Fluid 20p
Dust Bug Spares (Brush & Roller) 15p
CASSETTE TAPES
Audio-Magnetic C60
Qty 3 6 10 20
Price|£1.00|£1.90|£3.20|£6.30
Cassette Caddy £1.20
Cassette Head Cleaner 35p

ZONAL ILFORD TAPE
5" Standard 600ft 25p
5 1/2" Standard 900ft 50p
7" (Plain boxed) 1200ft 60p
7" (Westminster Boxed) 1800ft £1.25
7" Reel of Leader Tape (Blue or green) 75p

HEADPHONES
Sennheisser HD414 £12.50
AKG K50 £6.50
Beyer DT485 £35.00

MICROPHONES
AKG D109 £12.65
AKG D202E1 £43.45
AKG D190C £18.70
AKG D190E £20.02
AKG D224 £55.00
Sennheisser MD211N £49.50
Sennheisser MD413N £29.70
Sony ECM50 £93.50
Audio RMS7F Radio Mike £231.00

SPEAKERS
E.M.I. 350 Kit 8ohms £8.20
E.M.I. 450 Kit 8ohms £4.50

J. J. Francis (Wood Green) Ltd


MANWOOD HOUSE, MATCHING GREEN, HARLOW, ESSEX CM17 0RS Telephone: Matching 476

MANUFACTURERS OF ELECTRONIC AND AMPLIFICATION EQUIPMENT
SPECIALISTS IN QUALITY TRANSISTOR EQUIPMENT
OPEN 6 DAYS A WEEK. 9.00 a.m.-6.00 p.m.



TRANSISTOR UNIVERSAL AMPLIFICATION COMPANY LTD.
DEPT. W
163 MITCHAM ROAD, LONDON SW17 9PG
01-672 3137/9080

NEW TUAC POWER MODULES

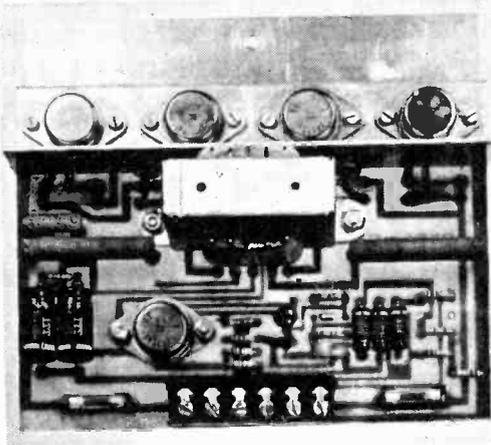

TP125
illustrated

£15-25

- ★ 125 Watts RMS continuous sine wave output
- ★ 4 RCA 150 Watt 15 Amp output transistors
- ★ Special layer wound driver transformer
- ★ Short, open, and thermal overload protection
- ★ Compact size: 7 x 6½ x 3 in.

TL100

£11-50

- ★ 100 Watts RMS sine wave
- ★ 2 RCA 15 Amp output transistors
- ★ Rugged transformer driver
- ★ Full thermal overload protection
- ★ Compact size: 5 x 5 x 3in.

TL60

£9-75

- ★ 60 Watts RMS sine wave
- ★ RCA 115 Watt output transistors
- ★ Only six connections to make
- ★ Same size as TL100

TL30

£7-50

- ★ 30 watts RMS sine wave
- ★ Rugged transformer driver
- ★ 2 RCA output transistors
- ★ Full thermal overload protection

Power supplies vacuum impregnated Transformers with supply board incorporating stabilised pre-amp supply:

PS 125 + 50 volts for one TP125	£8 75
PS 100 + 45 volts for one TL100	£8 00
PS 60 + 40 volts for one TL60	£6 75
PS 30 + 30 volts for one TL30	£4 50
PSU 2 for supplying disco mixer	£4 00


Specification on all three power modules:

All output power ratings + 1dB. Output impedance 8-15 Ohms. THD at full power 1% typically 0.5%. Input sensitivity 60mV into 10k. Frequency response 10Hz-25kHz +2dB. Hum and noise better than -75dB.

ALL PRICES INCLUDE V.A.T. AND POSTAGE AND PACKING
ACCESS & BARCLAY CARDS ACCEPTED, JUST SEND US YOUR NUMBER
H.P. ARRANGED THROUGH PAYBONDS

Why pay more - look at our Fantastic Bargain Offer!


THE AVON AUDIO SYSTEM

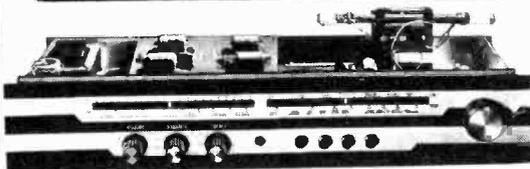

The uncabineted system is ideal as an economical replacement for an outdated chassis. Stereo Amplifier for Stereo/Mono record reproduction. Tuner with medium, long and short wavebands provides Worldwide coverage, even the weakest continental stations can be received with superb clarity. Push button band selection, 10 watts total output. Frequency response 25-18000 Hz.

LATEST BSR STEREO/MONO RECORD CHANGER plays all types of 7in., 10in., and 12in. Mono or Stereo records. Manual or automatic play.

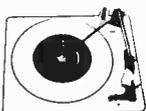TWIN ELLIPTICAL SPEAKERS These low impedance, permanent magnet units have been specially selected to provide the fullest range of audio reproduction.



EASY TO INSTALL—NO TECHNICAL KNOWLEDGE REQUIRED. List Price £45-74. OUR PRICE £35-00. Credit Terms £3-50 deposit plus £2 Post & Packing followed by 9 payments of £4-10 (Total Credit Terms £44-40) Don't miss this bargain.

SEND £5-50 TODAY

ALL EQUIPMENT COVERED BY OUR 12 MONTHS FULL GUARANTEE

CALLERS WELCOME

LEWIS radio PW 5/74

100 Chase Side, Southgate,
London N14 5PL
Tel: 01-886 3733/9666

Are you an inventor?

Newnes-Butterworths, the technical publishers, invite you to enter for —

THE NEWNES-BUTTERWORTHS PRIZE

- Worth £250
- Awarded for the "most novel application of an electronic device"
- Judged by a distinguished panel of experts.

Entry forms should be available at your local bookseller, but in case of difficulty please contact the publisher direct.




Newnes-Butterworths

The big name in technical publishing
Borough Green, Sevenoaks, Kent TN15 8PH

"Stella 99"

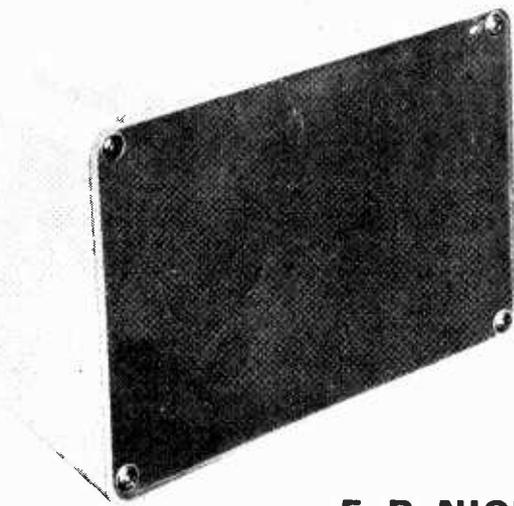**WE BELIEVE THE FINEST INSTRUMENT CASE IN THE COUNTRY
BEATS ALL COMPETITORS FOR PRICE AND STRENGTH**



SIZES	PRICE
5" x 3" x 1½"	50p
6" x 4" x 4"	£1.40
9" x 4" x 3"	£1.60
8" x 5½" x 5"	£2.30

TRADE PRICES ON APPLICATION


FIBREGLASS PRESS MOULDED IN GREY. SUPPLIED WITH 4 RUBBER FEET. 18 SWG ALLOY CHASSIS. 16 SWG ALLOY FRONT PANEL. FRONT PANEL HAS PROTECTIVE FILM FOR MARKING OUT AND PROTECTION. THE CASE HAS TWO SETS OF RUNNERS MOULDED IN WHICH WILL TAKE ALLOY OR P.C. BOARD CHASSIS. SAME DAY OFF-THE-SHELF DELIVERY. PANEL PUNCHING AVAILABLE ON 100 UP. TRADE AND QUANTITY DISCOUNTS ON REQUEST.

**V.A.T. ADD 10% ON TOTAL ORDER + POST AND PACKING 25p. CASH WITH ORDER.
N.B. 5" x 3" x 1½" NO FEET OR CHASSIS.**

E. R. NICHOLLS,

46 Lowfield Road, Stockport, Cheshire. Tel: 061-480 2179

PRINTED CIRCUIT BOARD TRANSFER SYSTEMS

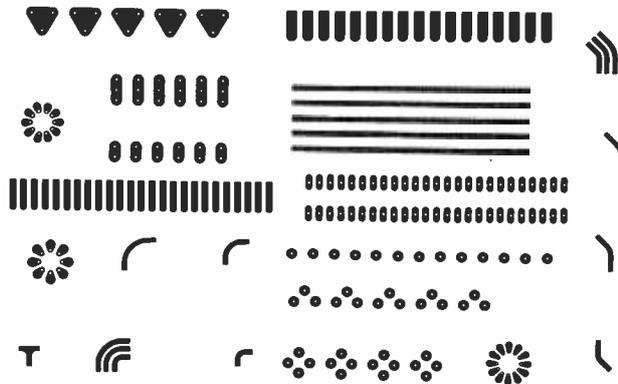

Acid resistant transfers for direct application to P.C. Board. This is a new approach to printed circuit board manufacture, giving a professional finish with all details that an electronics engineer would require, including all drilling positions automatically marked.

Ideal for single unit boards or small quantities. All at a very low cost—for example an average 6" x 4" layout would cost less than 30p, and the time taken under one hour, including etching to complete.

The system is simple, briefly it consists of 10 sheets of self adhesive acid resistant transfers made in required shapes—i.e. edge connectors, lines, pads, dual in line I.C.'s, 8-10-12. T.O.S Cans, 3-4 lead transistors, etc., etc., which only require pressing into the required positions on the printed circuit board before etching.

The printed circuit transfer system is a genuine offer to the public and industry. A full money back guarantee is sent with each order, trade prices on application.

List of Prices

Complete system including post and VAT	£2.00
Individual sheets	22p
Sample sheet	22p
Copper laminate (boards) size 6" x 4½" 6 sheets	50p
(with six months guarantee)	

Printed circuit board PCB transfer systems patent applied for.

E. R. NICHOLLS, 46 LOWFIELD ROAD, STOCKPORT, CHESHIRE

TELEPHONE NUMBER: 061-480-2179

Trannies

All orders to be sent to our new retail shop at:—

4 Bush House, Bush Fair, HARLOW, ESSEX.

Telephone: 37739 — P. & P. 10p. — Catalogue 10p.

74 Series TTL

(National Semiconductors and I.T.T.)
LOW PRICES, HIGH QUALITY

* 100 plus less on 10% the 25+ column	No's 1+	1+	25+	No's 1+	1+	25+	
7400	1+	25+	7446	£2-31	£2-18	74122	£1-70
7401	20p	18p	7447	£1-48	£1-34	74123	£3-35
7402	20p	18p	7448	£1-98	£1-81	74141	£1-10
7403	20p	18p	7450	20p	16p	74145	£1-65
7404	21p	18p	7451	20p	19p	74150	£3-30
7405	21p	18p	7452	20p	19p	74151	£1-21
7406	54p	48p	7453	20p	18p	74153	£1-32
7407	54p	48p	7454	20p	18p	74154	£2-20
7408	20p	18p	7455	20p	18p	74155	£2-20
7409	20p	18p	7456	20p	18p	74156	£2-20
7410	20p	18p	7457	20p	18p	74157	£2-20
7411	23p	21p	7458	£1-10	99p	74158	£2-20
7412	40p	35p	7459	£1-37	£1-23	74159	£1-65
7413	31p	29p	7460	£1-10	99p	74160	£1-65
7414	49p	47p	7461	£1-32	£1-21	74161	£2-18
7415	57p	55p	7462	£1-32	£1-21	74162	£2-18
7420	20p	18p	7463	£2-75	£2-64	74163	£1-94
7422	60p	58p	7464	£4-86	£4-71	74164	£1-99
7423	60p	58p	7465	£4-85	£4-70	74165	£1-85
7425	60p	58p	7466	£1-10	99p	74166	£2-73
7426	35p	31p	7467	£2-84	£2-69	74167	£2-73
7427	55p	51p	7468	£1-18	£1-14	74168	£2-28
7428	85p	79p	7469	£1-04	£0-93	74169	£2-28
7430	20p	18p	7470	£1-14	£1-03	74170	£3-08
7432	42p	38p	7471	£1-25	£1-13	74171	£3-30
7433	97p	91p	7472	£2-75	£2-58	74172	£2-53
7437	77p	74p	7473	£1-18	£1-14	74173	£2-53
7438	77p	74p	7474	£1-18	£1-14	74174	£2-27
7440	20p	18p	7475	£1-07	£0-96	74175	£2-42
7441	81p	78p	7476	£1-10	£1-00	74176	£2-18
7442	81p	78p	7477	£1-12	£1-04	74177	£2-18
7443	£1-40	£1-32	7478	£1-18	£1-10	74178	£2-85
7444	£1-57	£1-52	7479	£1-19	£1-14	74179	£2-85
7445	£2-31	£2-18	7480	£1-21	£1-17	74200	£28-40

All Prices FULLY INCLUSIVE of VAT



Linear Intergrated Circuits

No's	1+	25+	No's	1+	25+
301	DIL	50p	709	DIL	55p
301A	DIL	46p	709B	DIL	35p
301A	DIL	69p	709C	DIL	35p
301A	DIL	69p	709D	DIL	35p
301A	DIL	69p	709E	DIL	35p
301A	DIL	69p	709F	DIL	35p
301A	DIL	69p	709G	DIL	35p
301A	DIL	69p	709H	DIL	35p
301A	DIL	69p	709I	DIL	35p
301A	DIL	69p	709J	DIL	35p
301A	DIL	69p	709K	DIL	35p
301A	DIL	69p	709L	DIL	35p
301A	DIL	69p	709M	DIL	35p
301A	DIL	69p	709N	DIL	35p
301A	DIL	69p	709O	DIL	35p
301A	DIL	69p	709P	DIL	35p
301A	DIL	69p	709Q	DIL	35p
301A	DIL	69p	709R	DIL	35p
301A	DIL	69p	709S	DIL	35p
301A	DIL	69p	709T	DIL	35p
301A	DIL	69p	709U	DIL	35p
301A	DIL	69p	709V	DIL	35p
301A	DIL	69p	709W	DIL	35p
301A	DIL	69p	709X	DIL	35p
301A	DIL	69p	709Y	DIL	35p
301A	DIL	69p	709Z	DIL	35p

£1 BARGAIN PACKS

- £1 10 Silicon NPN Power transistors (2N3055) tested/unmarked.
- £1 30 Plastic FET's unmarked/untested, similar to 2N3819.
- £1 20 TO6 Transistors NPN 2 to 5 amp untested/unmarked.
- £1 20 TO18 transistors NPN like BC178, BC179 etc. untested/unmarked.
- £1 30 Plastic 2N3055 unmarked/untested TO220 case.
- £1 10 General Purpose, fully tested FET's.
- £1 500 carbon resistors 1/4, 1/2, 1 watt.
- £1 90 Electrolytic condensers.
- £1 250 Ceramic Polystyrene, Silver Mica etc. Condensers.
- £1 250 Polyester, Polycarbonate, Paper, etc. condensers.
- £1 25 Potentiometers assorted.
- £1 15 Assorted nuts, bolts, washers, spacers, etc.
- £1 25 Assorted Switches, rotary, lever, micro, toggle, etc.
- £1 50 Preset Potentiometers

★ any 5 packs £4 ★
P/P 10p for each Pack.

Transformers

Primary	200-220-240 volt.	P/P
HT111	12 volt -5 amps	£111 16p
MT111/B	24 volt -25 amp	£135 20p
MT71	12 volt 2 amp	£176 22p
MT71/B	24 volt 1 amp	£176 22p
MT18	12 volt 4 amp	£247 39p
MT18/B	24 volt 2 amp	£247 39p

30 volt transformers	Prim 200-220-240v. Secondary voltage.
12 15, 20, 24, 30v or 12-0-12v or 15-0-15v.	
MT112	5 amps £132 32p
MT79	1 amp £180 26p
MT 3	2 £236 36p
MT20	3 £230 42p
MT61	2 £484 49p

50 volt transformers	Prim 200-220-240v. Secondary volt. 19, 25, 30, 40, 50v or 25-0-25 volt.
MT102	5 amps £176 30p
MT103	1 £258 38p
MT104	3 £484 49p
MT106	4 £602 52p

60 volt transformer	Prim 200-220-240 Secondary 24, 30, 40, 48, 60v or 24-0-24v or 30-0-30v.
MT124AT	5 amp £176 38p
MT125AT	1 amp £247 34p
MT127	2 £230 44p

Miniature transformers	Prim 220 volt
BT606	100mA 6-0-6v 98p 15p
BT607	100mA 9-0-9v 98p 15p
BT12012	100mA 12-0-12v £1-08 15p
BT24024	100mA 24-0-24v £1-95 15p

SSEMICONDUCTOR	BRIDGE RECTIFIERS
AC126 14p	OC44 16p
AC127 16p	OC45 10p
AC128 15p	OC71 11p
AC141K 28p	OC81 12p
AC142K 28p	2N706 14p
AC178 18p	2N1181 34p
AC187 24p	2N1132 28p
AC188 24p	2N2904 20p
AC187K 28p	2N2926 11p
AC188K 28p	2N3053 26p
AD149 49p	2N3054 55p
AD107 13p	2N3055 49p
AD102 40p	2N3702 14p
AF114 20p	2N3703 13p
AF115 20p	2N3704 14p
AF116 20p	2N3705 13p
AF117 20p	2N3706 12p
BC108 13p	2N3707 13p
BC108 13p	2N3708 11p
BC109 13p	2N3709 12p
BC147 13p	2N3710 12p
BC148 13p	2N3711 12p
BC149 13p	2N3712 12p
BC151 13p	40361 55p
BC183 11p	40362 55p
BC184 14p	40536 20p
BC212 13p	1N914 8p
BC213 13p	1N916 8p
BC214 13p	1N4001 7p
BD121 18p	1N4002 8p
BD132 90p	1N4003 10p
BF194 16p	1N4004 10p
BF195 17p	1N4005 15p
BF244 27p	1N4148 8p
BFY50 18p	1N5400 16p
BFY51 18p	1N5401 17p
BFY52 17p	1N5402 19p
MF8111 36p	1N5403 24p
OC28	50p 1N5404 28p
OC36	50p 1N5405 28p

BIG DISCOUNTS

PLUS full 12 months guarantee and after sales service.



★ All prices INCLUDE VAT
★ Callers welcome - listen and look at our new retail premises

Amstrad 4000 Stereo System. Includes IC4000 Amp, 12 watts RMS, Hilton speakers, Garrard SP25 Mk IV turntable, G800 cartridge, P. & C. R.R.P. £112.00. OUR PRICE £69.80 (carr. £1.50) or £1.08 weekly.

Amstrad 2000 System. Includes IC2000 Mk II Amp, 20 watt RMS, Hilton 20+20 speakers, Garrard SP25 Mk IV turntable, G800 cartridge, P. & C. R.R.P. £112.00. OUR PRICE £84.20 (carr. £1.50) or £1.15 weekly.

Hilstone 10+10 System. Includes Hilton 10 watt RMS Amp, Hilton speakers, Garrard SP25 turntable, complete cartridge and P/C. R.R.P. £83.00. OUR PRICE £54.80 (carr. £1.50) or £1.00 weekly.

Hilstone 20+20 System. Includes Hilton 20 watt RMS Amp, Hilton speakers, SP25 Mk IV turntable, G800 cartridge, P. & C. R.R.P. £104.00. OUR PRICE £78.60 (carr. £1.80) or £1.08 weekly.

Hilstone TA100 Systems. Hilton 10 watt Tuner Amp, Hilton speakers, Garrard SP25C turntable with cartridge and P. & C. R.R.P. £114.00. OUR PRICE £84.50 (carr. £1.80) or £1.20 weekly.

Trannies Disco Unit



Includes: ★ DJ 100 watt discotheque amp with full mixing & PFL facilities £90.75

★ Stereo Headphones with boom microphone £29.90

★ Trannies Disco Console with 2 Garrard SP25 Mk IV turntables with G800 cartridges £27.50

★ Pair 50 watt Speakers £43.00 or Complete System £182.50 (carr. £3.00)

★ Terms £9.38 weekly over two years (total £225) ★

We stock a full range of Disco Equipment send for list or pay us a visit

Resistors

1 watt 5% carbon	1p
1/2 watt 5% carbon	1p
1 watt 10% carbon	21p
range 10 ohms to 4.7 megohms.	
1/2 watt m/o 2%	4p
range 10 ohms to 1 megohms.	

MINITRON DIGITAL INDICATOR TYPE 3015F

Read 0-9 and decimals. ONLY £1.65

VEROBOARD

0-1	0-15
21 x 3 1/2	24p 18p
21 x 5	27p 23p
31 x 5	27p 23p
31 x 8	31p 27p
17 x 2 1/2	82p 63p
17 x 3 1/2	£1-10 87p
17 x 5 (Plain)	90p 87p
Print insertion too	57p 57p
Spot face cutter	46p 46p
Fit 36 Pins	20p 20p

VOLUME CONTROLS

Potentiometers
Carbon track 500Ω to 2.2MΩ.
Log or Linear.

Single 13p. Dual gang (stereo) 44p.
Single type with D.P. switch 13p extra.

CARBON SKELETON PRESETS

Small high quality type (linear only). All valves 100-5 meg ohms.
- 1 watt 8p each
- 2.5 watt 61p each

THRISTORS

PE RONDO
KIT AVAILABLE
SAE for List

SLIDE SWITCH

SPST 11p each. D.P.D.T. 13p each.

MINIATURE NEON LAMPS

240V or 110V 1.4 5p. 5 plus 41p each.

Electrolytic Capacitors



4 VOLT	16 VOLT	40 VOLT
47µF 61p	15µF 61p	47µF 61p
100µF 61p	33µF 61p	100µF 61p
220µF 61p	150µF 61p	68µF 10p
330µF 61p	150µF 61p	220µF 11p
1000µF 13p	220µF 61p	100µF 19p
4700µF 29p	680µF 17p	680µF 25p
	1000µF 17p	1000µF 25p
	1500µF 25p	2200µF 44p
	33µF 61p	
	68µF 61p	
	150µF 61p	
	470µF 11p	
	680µF 13p	
	1500µF 18p	
	2200µF 18p	
	3300µF 20p	
	220µF 10p	
	470µF 13p	
	150µF 18p	
	47µF 61p	
	61p	
	100µF 61p	
	100µF 61p	

The Sinclair Cambridge... no other calculator is so powerful and so compact.

Complete kit-£24.95! (PLUS VAT)

The Cambridge – new from Sinclair

The Cambridge is a new electronic calculator from Sinclair, Europe's largest calculator manufacturer. It offers the power to handle the most complex calculations, in a compact, reliable package. No other calculator can approach the specification below at anything like the price – and by building it yourself you can save a further £5.50!

Truly pocket-sized

With all its calculating capability, the Cambridge still measures just $4\frac{1}{2}'' \times 2'' \times \frac{11}{16}''$. That means you can carry the Cambridge wherever you go without inconvenience – it fits in your pocket with barely a bulge. It runs on ordinary U16-type batteries which give weeks of life before replacement.

Easy to assemble

All parts are supplied – all you need provide is a soldering iron and a pair of cutters. Complete step-by-step instructions are provided, and our service department will back you throughout if you've any queries or problems.

Total cost? Just £27.45!

The Sinclair Cambridge kit is supplied to you direct from the manufacturer. Ready assembled, it costs £32.95 – so you're saving £5.50! Of course we'll be happy to supply you with one ready-assembled if you prefer – it's still far and away the best calculator value on the market.



Features of the Sinclair Cambridge


- * Uniquely handy package. $4\frac{1}{2}'' \times 2'' \times \frac{11}{16}''$, weight $3\frac{1}{2}$ oz.
- * Standard keyboard. All you need for complex calculations.
- * Clear-last-entry feature.
- * Fully-floating decimal point.
- * Algebraic logic.
- * Four operators (+, -, x, ÷), with constant on all four.
- * Constant acts as last entry in a calculation.
- * Constant and algebraic logic combine to act as a limited memory, allowing complex calculations on a calculator costing less than £30.
- * Calculates to 8 significant digits, with exponent range from 10^{-20} to 10^{79} .
- * Clear, bright 8-digit display.
- * Operates for weeks on four U16-type batteries. (MN 2400 recommended.)

A complete kit!

The kit comes to you packaged in a heavy-duty polystyrene container. It contains all you need to assemble your Sinclair Cambridge. Assembly time is about 3 hours.

Contents:

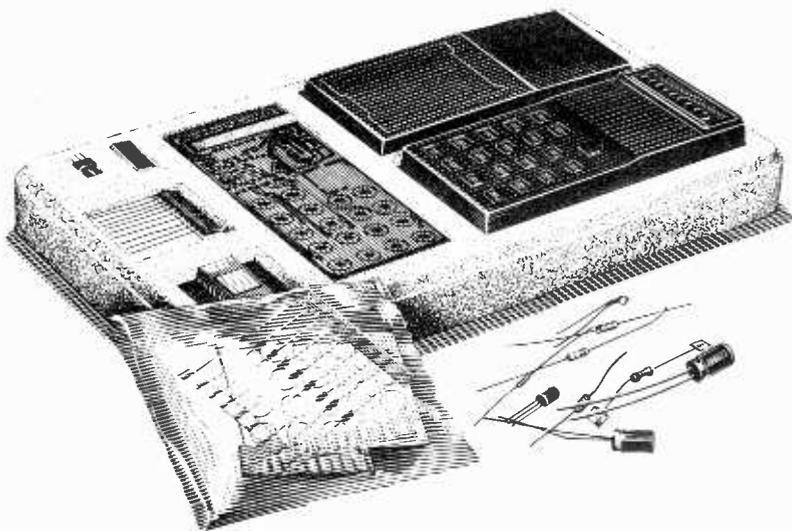
1. Coil,
2. Large-scale integrated circuit.
3. Interface chip.
4. Thick-film resistor pack.
5. Case mouldings, with buttons, window and light-up display in position.
6. Printed circuit board.
7. Keyboard panel,
8. Electronic components pack (diodes, resistors, capacitors, transistor).
9. Battery clips and on/off switch,
10. Soft wallet.



This valuable book – free!

If you just use your Sinclair Cambridge for routine arithmetic – for shopping, conversions, percentages, accounting, tallying, and so on – then you'll get more than your money's worth.

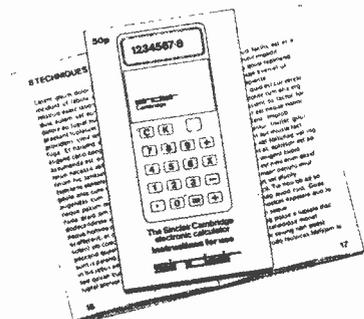But if you want to get even more out of it, you can go one step further and learn how to unlock the full potential of this piece of electronic technology.



How? It's all explained in this unique booklet, written by a leading calculator design consultant. In its fact-packed 32 pages it explains, step by step, how you can use the Sinclair Cambridge to carry out complex calculations.

sinclair

Sinclair Radionics Ltd, London Road,
St Ives, Huntingdonshire
Reg. no: 699483 England
VAT Reg. no: 213 8170 88

Why only Sinclair can make you this offer

The reason's simple: only Sinclair – Europe's largest electronic calculator manufacturer – have the necessary combination of skills and scale.

Sinclair Radionics are the makers of the Executive – the smallest electronic calculator in the world. In spite of being one of the more expensive of the small calculators, it was a runaway best-seller. The experience gained on the Executive has enabled us to design and produce the Cambridge at this remarkably low price. But that in itself wouldn't be enough. Sinclair also have a very long experience of producing and marketing electronic kits. You may have used one, and you've almost certainly heard of them – the Sinclair Project 60 stereo modules.

It seemed only logical to combine the knowledge of do-it-yourself kits with the knowledge of small calculator technology. **And you benefit!**

Take advantage of this money-back, no-risks offer today

The Sinclair Cambridge is fully guaranteed. Return your kit within 10 days, and we'll refund your money without question. All parts are tested and checked before despatch – and we guarantee a correctly-assembled calculator for one year. Simply fill in the preferential order form below and slip it in the post today.

Price in kit form: £24.95 + £2.50 VAT. (Total: £27.45)
Price fully built: £29.95 + £3.00 VAT. (Total: £32.95)

PW 5 74

To: Sinclair Radionics Ltd, London Road,
St Ives, Huntingdonshire, PE17 4HJ

Please send me Name _____
 a Sinclair Cambridge calculator kit at £24.95 + £2.50 VAT (Total: £27.45)
 a Sinclair Cambridge calculator ready built at £29.95 + £3.00 VAT (Total: £32.95) _____
 Address _____

*I enclose cheque for £ _____, made out to Sinclair Radionics Ltd, and crossed.
 *Please debit my *Barclaycard/Access account. Account number _____

*Delete as required.

PLEASE PRINT

100 YEARS ON...

ON April 25th, 100 years ago, Guglielmo Marconi was born. It would be fair to say that the present day conglomerate of wireless, electronics and television owes its existence to Marconi for his teenage experimental studies of the behaviour of electromagnetic waves as a possible means of communication.

It could be that, had Marconi not been instrumental in putting the theory into practice, someone else may have done so. Whilst not detracting from his real talent, one has to admit that it takes courage and determination to convince others of the long-term practical prospects of such an idea in its infancy. Marconi's fortune turned in 1897 when William Preece, at that time Engineer-in-Chief of the G.P.O., had tried without much success to transmit radio waves. Marconi demonstrated a 8.7 mile hop, having succeeded in short distance experiments two years before. It was sufficiently convincing for Marconi to set up his own radio company.

From that day, his work developed into a multiplicity of activity for himself and other scientists, including Sir Watson-Watt (radar) Dr. Fleming (thermionic radio valve), and Brattain, Bardeen, and Shockley (transistor). In the earlier days, it is interesting to note that wireless was used in such "way-out" ventures (then) as aircraft communication in 1910 and the capture of Dr. Crippen the notorious murderer. Then followed wartime activities involving the detection of Zeppelin airships, naval telegraphy and aircraft telephony.

Soon afterwards the small transmitting station 2MT was born, followed by 2LO later to become the nucleus of the P.M.G.'s British Broadcasting Company.

Looking back over the past 80 years or so we have seen exciting developments, far too numerous to list here. There still remains for many who are not closely associated with wireless and electronics an air of mystery about the whole subject.

Practical Wireless is commemorating Marconi's centenary this month by helping newcomers in the art of DXing. We have produced a special pull-out feature that provides a wealth of advice and information for everybody who listens to the radio or watches television, and that is almost everyone.

Marconi was the "father" of practical wireless, the launching vehicle of all other electronics fields. His example of putting ideas into practice was never more true than it is today. For this, his centenary year, we acknowledge a true master of the art.

M. A. COLWELL—Editor.

The June issue will be the first of the series of summer issues. We hope to provide you with some unusual ideas, some of which will be new to this magazine. We start with a feature on in-car entertainment for your leisure driving, including an article on the techniques used in present day car radio design. We also have a Sound to Light Display Control Box for discos and parties. Also watch out for details of our exciting new project "Games on Television". Further details on pages 54 and 57. All advanced details are subject to change without notice according to the current national industrial situation.

NEWS...

Ambisonic system

THE Ambisonic system of quadrasonic sound reproduction, described in the February issue of *Practical Wireless*, was greeted with considerable enthusiasm at Sonex and the Festival du Son in Paris.

Of the systems currently in use, the Ambisonic system, otherwise referred to in the category of "Kernel" systems, looks like solving much of the problems of compatibility. The mathematics used is different from that used in matrix systems, although it does not employ full discrete channel methods either. The significant difference is in the carefully controlled mixing of signals using pan-pots (although suitable commercial types are not yet available) during recording or transmission on f.m. radio, so that the various decoding systems now employed, except SQ, can be used for reproduction at home. The SQ system needs a vari-matrix interface unit to convert Kernel recordings to SQ.

The results are quite remarkable and it is likely to be the answer to rationalised and compatible quad better than any of the current matrix or discrete systems. The added bonus is that this system could be used for compatible f.m. radio and television broadcasts. Other examples of the Kernel system are the UMX family from Nippon Columbia and the Japanese RM (regular matrix) system, which does not include Sansui's QS approximation to RM. This Japanese RM facility was provided for in the *Practical Wireless* Q4 Decoder published recently. The other matrix and discrete systems are also available in the Q4 design, making it eminently suitable for immediate use with Ambisonics without fear of obsolescence.

CQ column

[THE CQ column is a valuable way of obtaining back numbers from other readers, but please reimburse expenses and the price of the magazines to those who have kindly offered to help!]

BBC on Radio reception

ON Radio reception, the sub-committee of the General Advisory Council of the BBC has recognised that the continued expansion of Radio broadcasting throws an increasing load on channels at present allocated for broadcasting purposes. They accept that the additional coverage required must be provided in the v.h.f. band, and they advise the BBC to pursue representations to the Ministry of Posts and Telecommunications as the urgency of transferring service users to other bands in order to clear, at the very least, the 96.7-100MHz band for broadcasting, as is the case in other countries.

They also suggest that the BBC should carry out a determined programme to inform listeners about the desirability of buying multi-wave receivers, having long, medium wave and v.h.f. capability, many of which are available at reasonable prices, in view of the likelihood that increasing reliance will have to be placed on v.h.f. in the future because of international frequency allocations.

The Council accepts that changes in the present frequency patterns for radio might be forced on the BBC by international developments. It urges, therefore, that specific and continuing research on current listening habits in terms of set and waveband usage should be undertaken so that any future changes which might become necessary could be designed to secure as much public acceptability as possible.

WIRELESS TELEGRAPHY ACT

Readers and advertisers are reminded of the requirements laid down by the Wireless Telegraphy Act. It is an offence in the U.K. to install or operate wireless telegraphy apparatus except under the provisions of the Act and, except in the case of broadcast sound-only receivers, a licence must be obtained from the Minister of Posts and Telecommunications.

Included within the provisions of the Act are any apparatus transmitting deliberate signals for any purpose such as "walkie-talkies", radio-controlled models or servos and some types of metal detectors. Apparatus radiating interference signals are subject to controls which also come under the administration of the same Ministry. If you require full information, please write to the *Ministry of Posts and Telecommunications, Waterloo, Bridge House, Waterloo Road, London SE1 8UA.*

New catalogue

ELECTROVALUE have now issued the seventh edition of their catalogue. This firm has built up a reputation over the past nine years of giving excellent service, good quality components at competitive prices, and a range ideally suited to the needs of amateur and professional constructor.

EMI equip Canadian tower

A £1.25 million contract to equip the new third-of-a-mile high CN observation and communications tower in Toronto, Canada, with a complete antenna complex for all f.m. and TV broadcasting services has been won by the Telecommunications Division of EMI Sound & Vision Equipment Ltd, Hayes, Middlesex.

The contract was awarded to EMI in the face of intensive international competition, reflecting the company's extensive experience of such special-purpose multiple antenna systems. EMI is established as a major supplier to many broadcasting authorities. In the UK the large number of systems supplied includes the multiple antenna system on the IBA's 1100 foot tower at Emley Moor.

When completed, the 1805 foot high CN tower in Toronto will be the tallest self-supporting structure in the world. The antenna system surmounting the main concrete tower will be carried on a 220 ton needle-shaped steel structure over 300 feet tall.

Transmissions from this height give major benefits in range and the elimination of "ghosting" but, at over 1500 feet, the arduous climatic conditions found normally even at ground level during the Canadian winter are aggravated by extremely severe icing, snow and high winds.

For this reason, an important part of the contract comprised the provision of a glass reinforced plastic radome. This will be designed and constructed in Britain by Hunting Industrial Plastics Ltd, and erected to protect the mast structure during the winter.

The complete installation to be provided by EMI comprises a formation of four arrays arranged as follows:—

Channel 5, Canadian Broadcasting Corporation. Intended for colour

TV transmissions, this is a single channel, directional v.h.f. antenna having a gain of 8. The array is 55 feet tall and is at a mean height of 1,572 feet.

Channel 9, CFTO—TV Ltd. Also intended for colour TV transmissions this second directional v.h.f. is similar to that for channel 5, but has a gain of 11 radiated from a 49 foot high array located at a mean height of 1,635 feet.

Channel 19 and 25, CBC and Educational. An omnidirectional u.h.f. array for colour TV. It is arranged as a dual antenna, with one channel allocated to CBC and the second to the educational transmissions. Positioned on the mast at a mean height of 1,695 feet, this array is 60 feet tall and has a gain of 31.


FM Transmissions. The master f.m. antenna occupies the lowest section of the mast, and has a mean height of 1,513 feet. Measuring 60 feet high by 26 feet diameter, this antenna is being manufactured under licence from Alford Manufacturing Co of the USA, and is based upon those supplied for the Empire State Building and Hancock Tower, Chicago.

Scottish Audio Fair

THE Scottish Audio Fair, due to take place at the Kelvin Hall, Glasgow, in April has been cancelled due to the current economic circumstances. The London Audio Fair is still expected to go ahead at Olympia.

OSCILLOSCOPE

TRACE DOUBLER

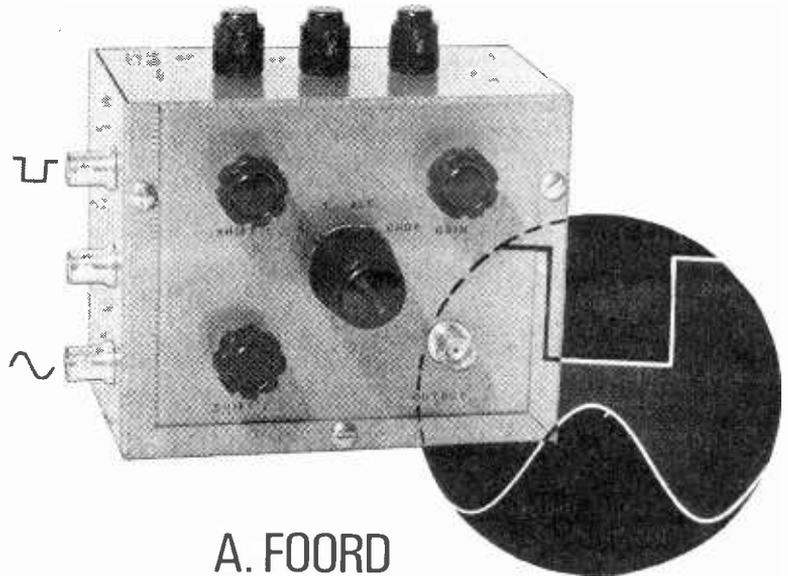

FOR some oscilloscope measuring applications it is essential to display a number of recurrent signals simultaneously. When a true double beam CRT is not available, an electronic switching system can be used to display two (or more) channels on a single beam CRT. The basic block diagram for this arrangement is shown in Fig. 1. In the ALTERNATE mode the channel is changed at the end of each timebase sweep. This mode is suitable when the sweep rate is high enough to avoid a flickering display. In the CHOPPED mode the beam is time-shared between the traces at a fixed rate, and this arrangement is suitable for low frequency signals. Under the chopped mode of operation care has to be taken with the oscilloscope triggering, and it is usual to externally trigger the oscilloscope from the channel signal as required.

Basic switching circuits

Chopping (or switching) circuits are used in many electronic instrumentation applications and are

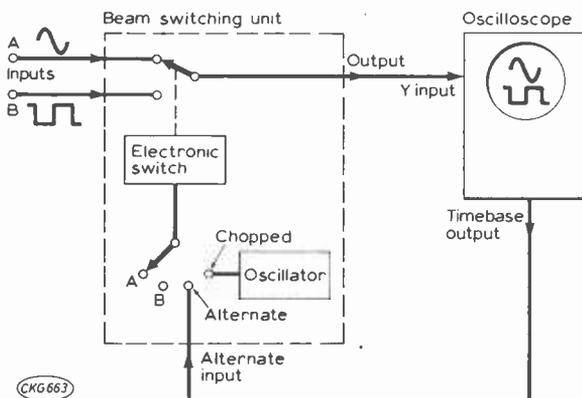


Fig. 1: Block diagram for an oscilloscope trace doubling unit.

A. FOORD

basically of either the shunt or series type, as shown in Fig. 2, or a combination. The relative merits of the shunt or series arrangement depends on the source and load resistance. For a low source resistance a series chopper is suitable and, in general, the load resistance should be higher than the source resistance. Where the highest performance is required the series-shunt circuit is equal to or better than either the series or shunt chopper alone for any combination of load and source resistance.

Field effect transistors are preferred as switches to bipolar transistors because they do not have an offset voltage when turned on. Even for a zero input voltage, a bipolar transistor has an offset voltage equivalent to the collector-to-emitter saturation voltage between its collector and emitter terminals.

MOS-FET characteristics

For MOS transistors, where the gate is insulated from the source to drain channel by an oxide layer, four basic types are possible. These are:

- P channel depletion
- P channel enhancement
- N channel depletion
- N channel enhancement

An N channel depletion type such as the RCA 3N138 offers the best switching characteristics, with the lowest 'on' resistance for a given geometry, due to the higher mobility of electrons. When the gate-to-source voltage V_{GS} is zero the effective resistance between drain and source is about 200 ohms. If V_{GS} is made positive this decreases to about 100 ohms.

No significant increase in gate current occurs when V_{GS} is made positive for the MOS type. (Unlike a junction-gate field-effect transistor, where the gate and channel form a pn junction and a low gate current can only be obtained when this junction is reverse biased). When a negative voltage of about 6 volts or more is applied between the gate and

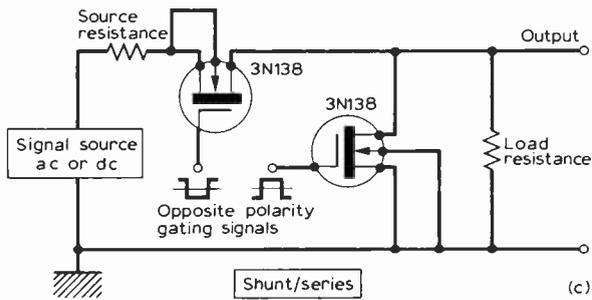
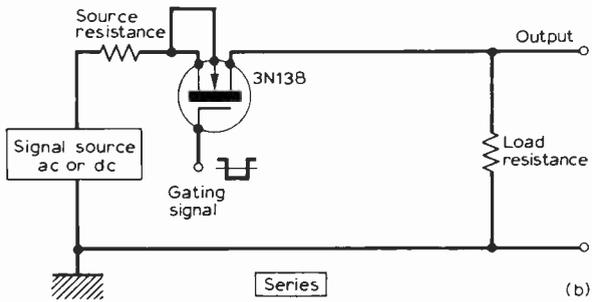
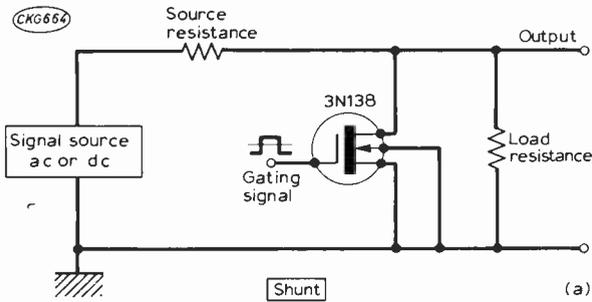


Fig. 2: Chopping circuits (a) shunt (b) series and (c) shunt-series.

source, the channel resistance between drain and source becomes extremely high (thousands of megohms). These characteristics are shown in Fig. 3 for the 3N138.

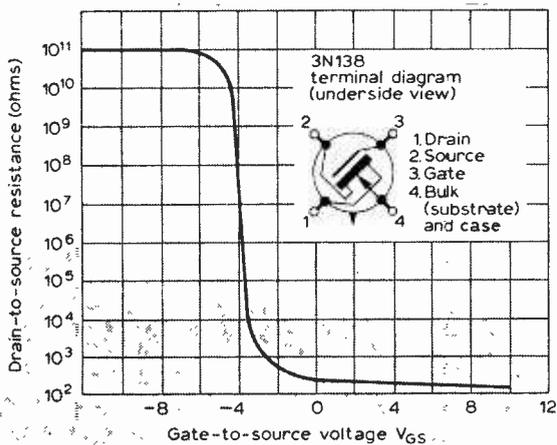


Fig. 3: Characteristics of the 3N138 MOS-FET.

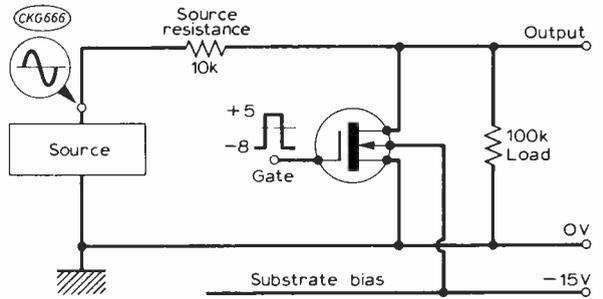


Fig. 4: Typical shunt chopper circuit using the 3N138.

Basic MOS-FET circuit

Figure 4 shows a basic shunt chopper circuit. The gating signal should swing from zero to at least -6 volts and may cover a range of ± 10 volts. The substrate (and thus the case) is usually connected to the source. However if the incoming signal to be chopped exceeds -0.3 volts the substrate must be 'floated', connected to the drain, or biased negatively so that the source-to-substrate and drain-to-substrate voltages never exceed -0.3 volts. If the value is exceeded, the substrate, which forms two p-n junctions with the drain and the source, becomes forward biased, and the resulting flow of diode current shunts the incoming signal to earth.

Virtual earth switching circuit

One difficulty with MOS-FET's is that if large signals have to be switched then the high drain-to-source (or gate-to-source) voltages needed cannot always be provided without exceeding the maximum ratings of the device. Under these circumstances a current mode switch may be used instead of the voltage mode switches previously discussed, as shown in Fig. 5. Here Tr1 and Tr2 form a shunt-series switch where an input current is diverted to earth or allowed to reach the virtual earth point Y. Since either Tr1 or Tr2 is always on, the VOLTAGE at point X is always low (a few millivolts) and large input signals can be handled readily. Where the highest performance is not required, Tr1 can be replaced by silicon diodes which keep point X close to earth potential while Tr2 is off.


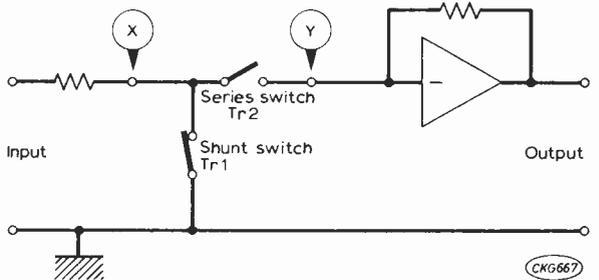
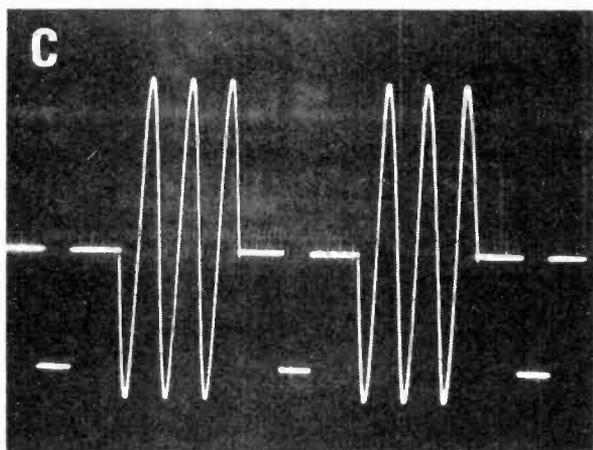
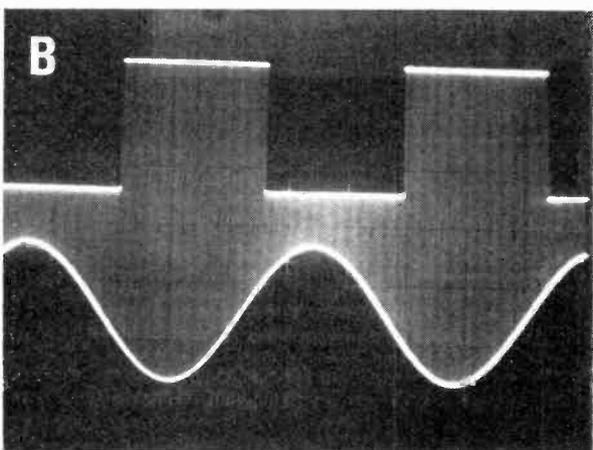


Fig. 5: A current mode shunt-series chopper circuit.

This virtual earth current switching arrangement is particularly convenient for our application because a DC shift voltage can be added into the virtual earth point. The disadvantage of this circuit is that switching spikes tend to be higher than with the voltage switching arrangement, but this is not significant here because the bandwidth is limited by the integrated circuit and not by the switching speed of the FET.

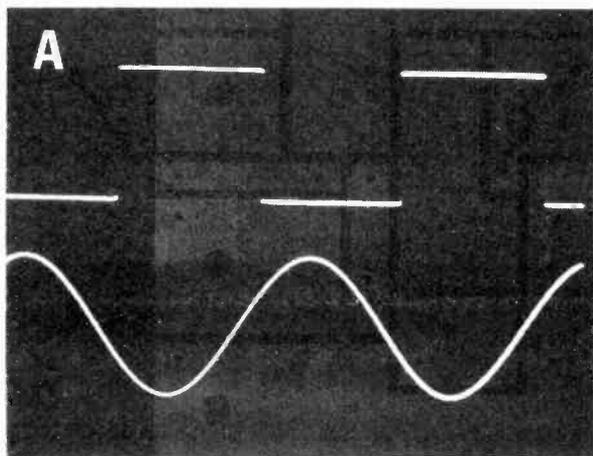

A The unit used in the ALTERNATE mode to display a 10kHz sine and square wave on a single-beam oscilloscope.

B The CHOPPED mode is being used here to display a 100Hz sine and square wave. The switching waveform may be visible, depending upon the signal frequency and the oscilloscope's intensity setting.

C A complex tone burst. The sine wave is 1kHz.

★ components list

Resistors

R1 330Ω	R5 2.2kΩ	R9 560Ω	R13 10kΩ
R2 1kΩ	R6 1kΩ	R10 470Ω	R14 10kΩ
R3 1kΩ	R7 1kΩ	R11 470Ω	R15 47kΩ
R4 2.2kΩ	R8 560Ω	R12 47Ω _{ww}	R16 47kΩ
		R17 22kΩ	

All $\frac{1}{2}$ or $\frac{1}{4}$ W 10%

VR1/2/3 10kΩ linear pots

Capacitors

C1 10μF 25V	C5 10μF 25V
C2 0.1μF 30V disc	C6 10μF 25V
C3 0.1μF 30V disc	C7 0.1μF 30V disc
C4 125μF 16V	C8 0.1μF 30V disc

Semiconductors

Tr1 BCY71	Tr3 3N138	D1-4 1N914
Tr2 BCY71	Tr4 3N138	RV1 LM309H


Miscellaneous

Veroboard $4\frac{1}{2} \times 3\frac{1}{8}$ in. 0.1 in. matrix, plain. 3 terminals.
S1, 2 pole 4 way wafer. 4 sockets. Aluminium box
5 x 4 x 3 in. Knobs. Veropins 0.1 in. Heatsink for
RV1. IC holders, 14 pin DIL (3), 8 pin TO5 (1).

Practical two channel switching circuit

The practical two channel switching circuit is shown in Fig. 6 and 7. In Fig. 7 two FETs are used to switch channels 1 and 2 into the summing point of a virtual earth amplifier. Independent shift controls are provided for each channel for trace positioning purposes, while a common gain control allows the total waveform amplitude to be controlled. In Fig. 6 the switching waveforms are generated and S1 allows the operational mode to be selected. This gives the choice of 1 only, 2 only, alternate or chopped.

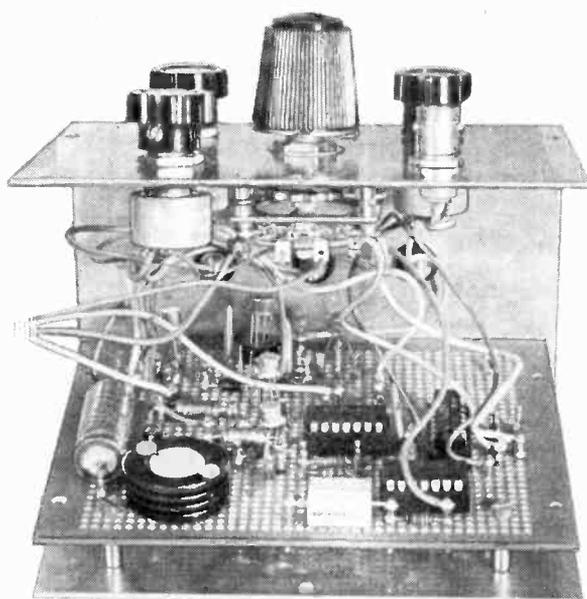In the 1 only mode, the bistable IC2 is preset so that Q is a logical 1 with \bar{Q} a logical 0. Then pin 1 of



A general view inside the finished switching unit.

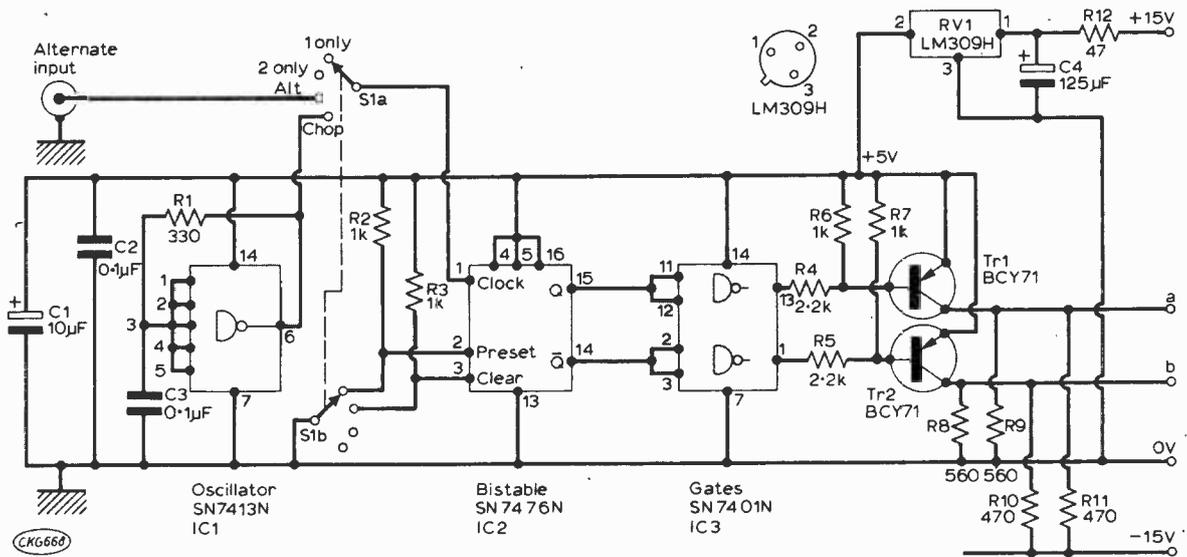


Fig. 6: The digital section of a practical two channel switching circuit.

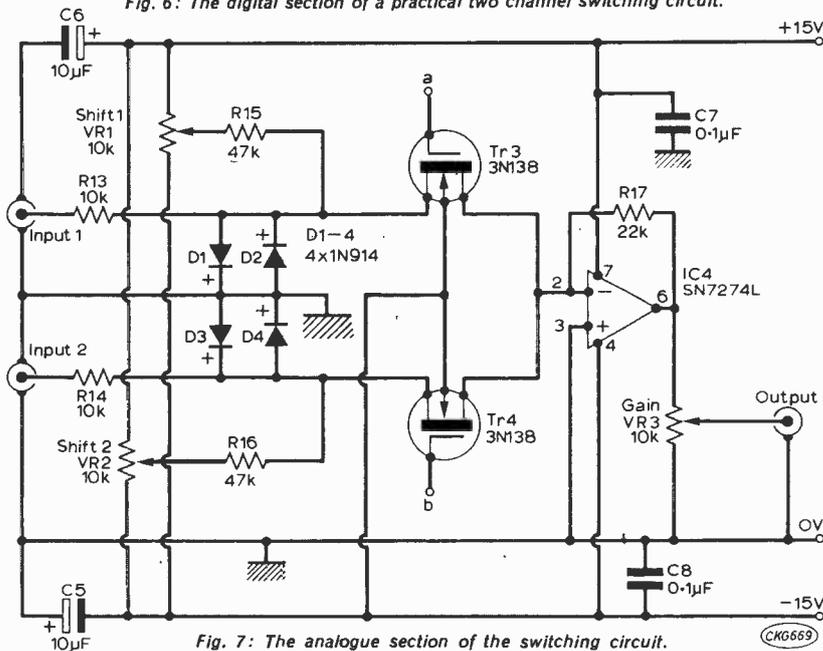


Fig. 7: The analogue section of the switching circuit.

IC3 will be at a logical 0 and Tr1 will be on. This makes waveform 1 become +5 volts, turning on Tr3. Pin 13 of IC3 will be at a logical 1 and Tr2 will be off. This makes waveform 2 become -8 volts, turning off Tr4. Open collector gates have to be used for IC3 so that Tr1 and Tr2 can be held completely off when required.

In the alternate mode bistable IC2 has to be triggered by the oscilloscope timebase. Most oscilloscopes have an output trigger, but this may need converting by a comparator or limiter to produce a suitable logic compatible signal. In the chopped mode the bistable is switched by the Schmitt trigger oscillator IC1. This oscillator runs at approximately 20kHz, so that the chopping rate is half this, or 10kHz.

Use as a Tone burst generator



Since the two channels are direct coupled, and can be DC shifted individually, the unit is very versatile. Although primarily designed for oscilloscope trace doubling applications, it can also be used as a tone burst generator if some external circuits are available. Tone bursts are extensively used in audio amplifier testing, where their complex waveforms can give a better measure of a system's performance under music conditions than using only sinusoidal or square waveforms.

For example, if required, a sinusoidal tone burst with a rectangular pulse may be generated. A divider chain is synchronised to the sinusoidal clock,

look! electronics really mastered

...practical
...visual
...exciting!

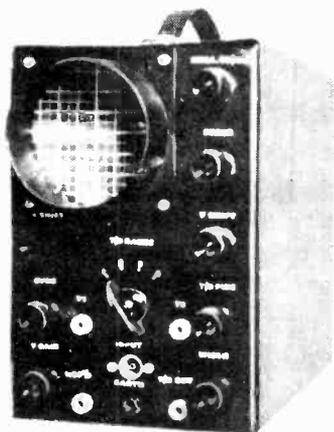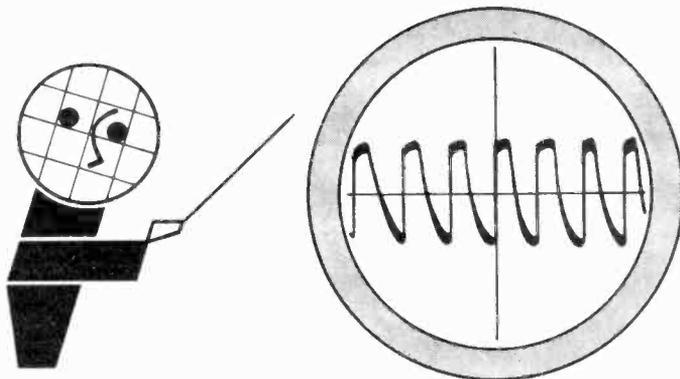no previous knowledge
no unnecessary theory
no "maths"



RAPY


BUILD, SEE AND LEARN

step by step, we take you through all the fundamentals of electronics and show how easily the subject can be mastered. Write for the free brochure now which explains our system.

1/ BUILD AN OSCILLOSCOPE

You learn how to build an oscilloscope which remains your property. With it, you will become familiar with all the components used in electronics.

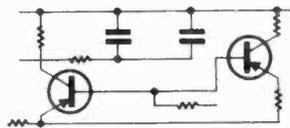2/ READ, DRAW AND UNDERSTAND CIRCUIT DIAGRAMS



as used currently in the various fields of electronics.

3/ CARRY OUT OVER 40 EXPERIMENTS ON BASIC ELECTRONIC CIRCUITS & SEE HOW THEY WORK, including :

valve experiments, transistor experiments amplifiers, oscillators, signal tracer, photo electric circuit, computer circuit, basic radio receiver, electronic switch, simple transmitter, a.c. experiments, d.c. experiments, simple counter, time delay circuit, servicing procedures.

This new style course will enable anyone to really understand electronics by a modern, practical and visual method—no maths, and a minimum of theory—no previous knowledge required. It will also enable anyone to understand how to test, service and maintain all types of electronic equipment, radio and TV receivers, etc.

FREE POST NOW
for
BROCHURE

or write if you prefer not to cut page

To: **BRITISH NATIONAL RADIO & ELECTRONICS SCHOOL,**

P.O. Box 156, JERSEY. Please send your free brochure, without obligation, to:
we do not employ representatives

NAME

BLOCK CAPS

ADDRESS

PLEASE WL54

special free gift also to all our students



WILMSLOW AUDIO

THE Firm for speakers!


SPEAKERS

Baker Group 25, 3, 8 or 15 ohm	£7.75
Baker Group 35, 3, 8 or 15 ohm	£8.50
Baker Group 50/12, 8 or 15 ohm	£12.50
Baker Deluxe	£10.75
Baker Major	£8.50
Baker Superb	£14.50
Baker Regent	£7.75
Celestion PST8 (for Unilex)	£2.55
Celestion MF1000, 8 or 15 ohm	£10.45
Celestion HF1300, Mk II	£6.16
Celestion G12M, 8 or 15 ohm	£12.00
Celestion G12H, 8 or 15 ohm	£15.00
Celestion G15C, 8 or 15 ohm	£24.00
Celestion G18C, 8 or 15 ohm	£33.00
EMI 13 x 8, 3, 8 or 15 ohm	£2.15
EMI 13 x 8 d/c, 3, 8 or 15 ohm	£2.35
EMI 13 x 8 t/rw, 3, 8 or 15 ohm	£3.60
EMI 13 x 8 type 350, 8 or 15 ohm	£8.25
EMI 8 x 5, cer. mag., 8 ohm	£1.65
EMI 8 x 5, 10 watt d/c roll surr., 8 ohm	£2.50
EMI 6 1/2" 93850, 4 or 8 ohm	£2.80
EMI 5" 98132CP, 8 ohm	£2.30
Elac 9 x 5, 59RM109 15 ohm, 59RM114 8 ohm	£2.65
Elac 6 1/2" d/c roll surr., 8 ohm	£3.35
Elac 6 1/2" d/cone, 8 ohm	£2.65
Elac Tweeter TW4 4"	£1.21
Elac 10" 8 ohm	£2.65
Fane Pop 100 watt 18"	£22.50
Fane Pop 60 watt 15"	£13.00
Fane Pop 50 watt 12"	£11.00
Fane Pop 25/2 12"	£6.40
Fane Pop 15 watt 12"	£4.40
Fane Crescendo 12A or 12B	£29.00
Fane Crescendo 15	£36.00
Fane Crescendo 18	£47.50
Fane 807T 8" d/c roll surr. 8 or 15 ohm	£3.85
Fane 808T 8" d/c 8 or 15 ohm	£2.75
Goodmans 8P 8 or 15 ohm	£4.49
Goodmans 10P 8 or 15 ohm	£4.70
Goodmans 12P 8 or 15 ohm	£11.65
Goodmans 15P 8 or 15 ohm	£18.00
Goodmans 18P 8 or 15 ohm	£31.00
Goodmans 12P-D 8 or 15 ohm	£15.25
Goodmans 12P-G 8 or 15 ohm	£14.50
Goodmans 12AX Audiomax 8 or 15 ohm	£39.65
Goodmans Audiom 100	£9.50
Goodmans Axent 100	£6.60
Goodmans Axiom 401	£15.10
Goodmans Twinaxiom 8, 8 or 15 ohm	£6.79
Goodmans Twinaxiom 10, 8 or 15 ohm	£7.61
Kef T27	£4.75
Kef T15	£5.50
Kef B110	£6.50
Kef B200	£7.50
Kef B139	£11.75
Kef DN8	£1.92
Kef DN12	£4.12
Kef DN13	£2.75
Richard Allan 12" d/c 3 or 15 ohm	£2.50
Richard Allan CG8T 8" d/c 8 ohm	£6.35
WMT1 speaker match. trans. 3-15 ohm	£1.10
Wharfedale Super 10 RS/DD	£9.80
2 1/2" 64 ohm, 70mm 8 ohm, 70mm 80 ohm	65
7" x 4" 3, 8 or 15 ohm	£1.38
8" x 5" 3, 8 or 15 ohm	£1.38
10" x 6" 3, 8 or 15 ohm	£1.92
S.T.C.4001 G Super Tweeter	£6.19

SPEAKER KITS

Wharfedale Linton 2 (pair)	£19.25
Wharfedale Glendale 3 (pair)	£34.50
Wharfedale Dovedale 3 (pair)	£52.00
Richard Allan Twinkit (each)	£8.25
Richard Allan Triple 8 (each)	£13.00
Richard Allan Triple (each)	£18.00
Richard Allan Super Triple (each)	£21.50
Goodmans DIN 20 (each)	£8.75
Fane Mode 1 (each)	£9.90
Peerless 20-2 (each)	£10.41
Kefkit 2 (each)	£23.50
Kefkit 3 (each)	£34.00
Helme XLK25 (pair)	£18.17
Helme XLK50 (pair)	£37.18
Baker Major Module	£10.75

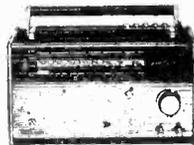P.A. and Hi-Fi Speaker Cabinets.
Send for Free booklet "Choosing a Speaker".
Carr. and Insurance 75p per kit (£1.50 pair).



PA/DISCO AMPLIFIERS

Carriage and Insurance £1.00	
Baker Major 100 watt	£46.00
Linear 30/40	£25.00
Linear 40/60	£30.00
Linear 80/100	£55.00

RADIOS/CASSETTES

Grundig Solo Boy	£16.00
Grundig Top Boy	£17.75
Grundig Party Boy 500	£22.75
Grundig Melody Boy 500	£26.75
Grundig Elite Boy 500	£26.75
Grundig Signal 500	£26.50
Grundig Yacht Boy 210	£34.00
Grundig Melody Boy 1000	£38.75
Grundig Satellite 2000	£121.00
Grundig C410 Cassette	£28.50
Grundig RF430 mains radio	£26.75
Grundig RF310 mains radio	£22.00
Tandberg TP41	£43.00
ITT Weekend Auto	£18.00
ITT Golf Preset	£24.50
ITT Colt	£11.50
ITT Europa	£20.50
ITT SL53 Cassette	£25.75
ITT Studio 60M Cassette	£32.75
ITT Studio 73 Cassette	£48.00
Bush VTR178 5 band (inc. air)	£29.00
Koyo KTR1770 11 band	£58.95
Koyo KTR1663 or 1664 8 band	£42.00
Koyo KTR1883 5 band	£22.00
Murphy BA209 Radio/Cassette	£32.75
Carriage and Insurance 75p.	
FREE with each radio—World radio stations book.	

Ambit International

We are not just another component retailer—but a complete semiconductor service. We can either supply or tell you where to get any 'hard to find' I.C.'s, and can now provide data on most devices you can think of. See our latest datalogue issue for full information.

15p—no S.A.E. required

For those of you who already have an AMBIT datalogue, send us an A5 S.A.E. plus 10p, stating the date of your datalogue—and we will send you all the latest update releases (to page 25).

AMBIT—the linear microcircuit specialists—for Phase Locked Loops	
NE561B AM/FM coil-less radio receiver or IF (16 DIL) strip	£3.19
AM/FM demodulator kits with mechanical filter—see October's PW	£5.00
NE562B Similar to the 561, but without AM (18 DIL) facility. The VCO output is separately available for synthesizer applications.	£3.15
NE565 High stability-low frequency telemetry (14 DIL) demodulator and NBFM demodulator.	£2.55
567 A P.L.L. for tone, NBFM and AM decoding (5-9V working)	£2.75
555 Versatile timing IC, use as 'one-shot' or multi-vibrator	£0.78
LS8038 A unique triangle/square/sine wave function generator up to 1MHz—complete signal generator in a chip. A data sheet is included with each device on request	£3.10

for Audio

LM380N Simple, safe and versatile 2W RMS (14 DIL) at 12V: 4W RMS at 18V	£1.30
Stereo Stereo AMP P.C.B. for 2 x LM380N	£0.80
TBA810S 7W RMS 14v	£1.65

for Radio

(see last month's advertisement for our radio IC features)	
TBA651 1µV sensitivity AM/FM/SSB with RF mixer and IF low external parts count (16 DIL)	£1.82
TBA120 FM IF strip and detector	£1.00
CA3089E FM IF system AFC-AGC-SQUELCH-TUNING-METER OUTPUT—the very best FM IC	£4.95
MC1310P P.L.L. Stereo decoder IC with layout spec.	£2.85
Stereo Decoder Kit with socket, LED, etc.	£5.10

for TOKO filters at 455KHz and 10-7MHz	
Ceramic CFT455B 8KHz bandwidth	£0.45
CFT455C 6KHz bandwidth	£0.45
CFU455C 4-8KHz bandwidth	£0.50
CF510-7 Wide band FM (2 required per set)	£0.37
455KHz MFH-T 4, 5 or 7KHz versions	£1.35
Mech-LPF2016 A stereo pilot tone notch filter (19 and 38KHz) for HiFi, recording, etc. Both channels	£1.80
Plus LED displays, 250MHz decade counters, voltage regulators kits for tone coders, Hi Cads—in fact everything to lead you through the microcircuit maze.	

ULTRASONIC REMOTE CONTROL PROJECT. S.A.E. for details of kits and availability.
PW FERRET KIT. Electronics only £9.50

LARSHOLT VHF FM TUNERSETS

1µV Input for 26dB S/N. INCLUDES SQUELCH, TUNING METER DRIVE BAND SCAN FACILITY, 4 VARICAP CONTROL £16.00
S.A.E. for specification details

FOR ELECTRONIC SUB ASSEMBLIES
Audio SINE/SQUARE/TRIANGLE generator with sweep facility .001Hz-1MHz.
Full kit of components and instructions £11.50
7 Segment LED display with decode counter/decoder driver and latch on min PCB (kit) £4.50
Active Filters with 741 OP Amp bandpass filter for sound to light converter systems. Full kit £17.75

S.A.E. FOR DETAILS

PLEASE NOTE ALL PRICES NOW EXCLUDE VAT

37A HIGH STREET, BRENTWOOD, ESSEX CM14 4RH Tel: (0277) 216929

Terms: C.W.O. All prices EXCLUDE VAT
Handling charge of 10p per order.
FIRST CLASS POSTAGE on all items under 80z.

FREE with speaker orders over £7

"Hi-Fi Loudspeaker Enclosures" book. All units guaranteed new and perfect. Prompt despatch.


Carriage and insurance 35p per speaker (tweeters and crossovers 20p)

ALL PRICES QUOTED INCLUDE V.A.T.


WILMSLOW AUDIO Dept. P.W.

Loudspeakers: Swan Works, Bank Square, Wilmslow, Cheshire SK9 1HF. Radios etc: 10 Swan St., Wilmslow, Cheshire SK9 1HF.

Telephone Wilmslow 29599

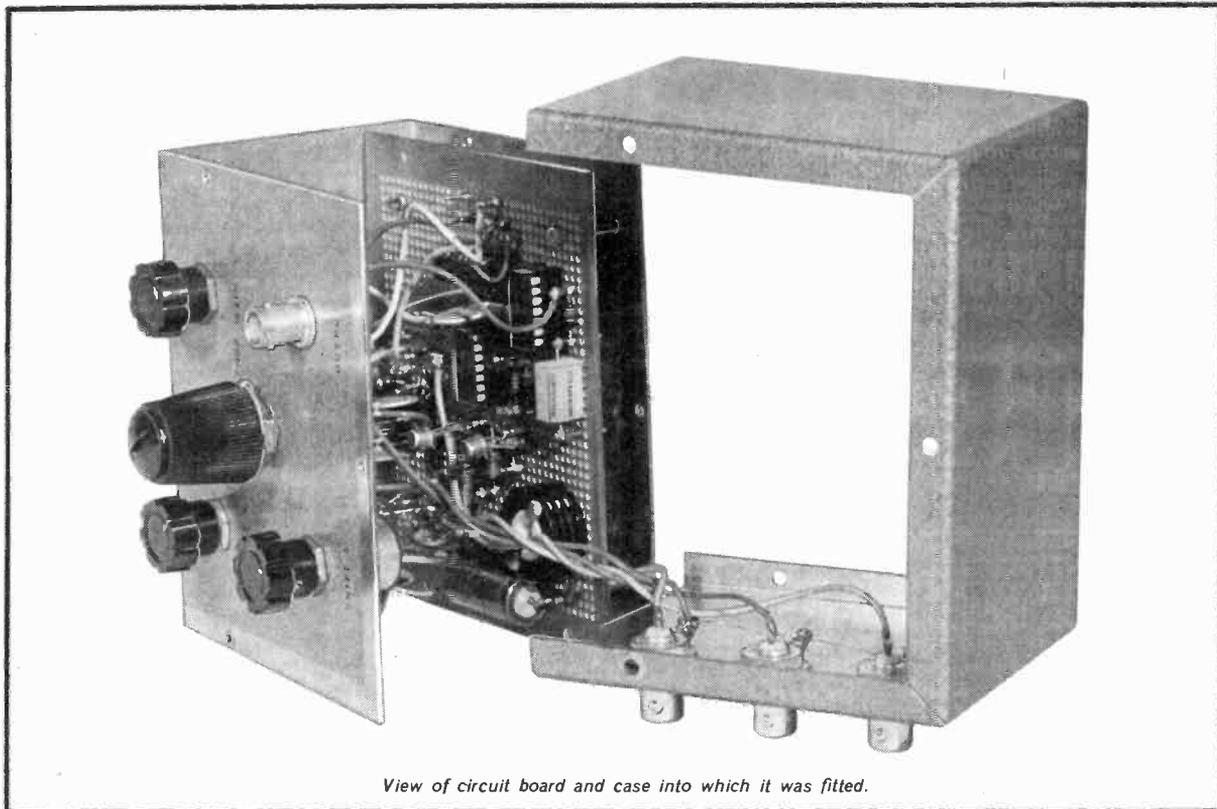

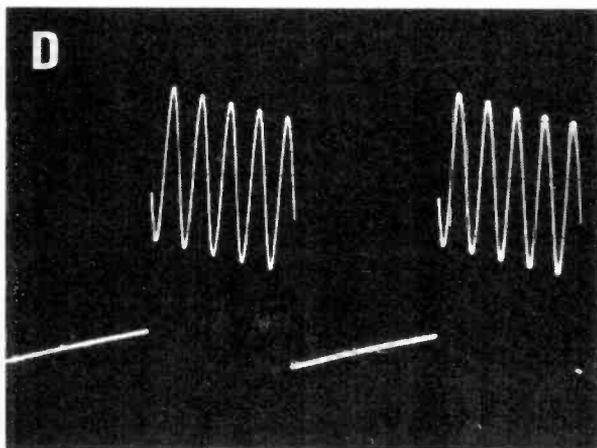
View of circuit board and case into which it was fitted.



and switches the unit between channels 1 and 2 at a rate lower in frequency than the clock. A pulse generator allows the rectangular pulse to be added into the 2 channel.

Construction

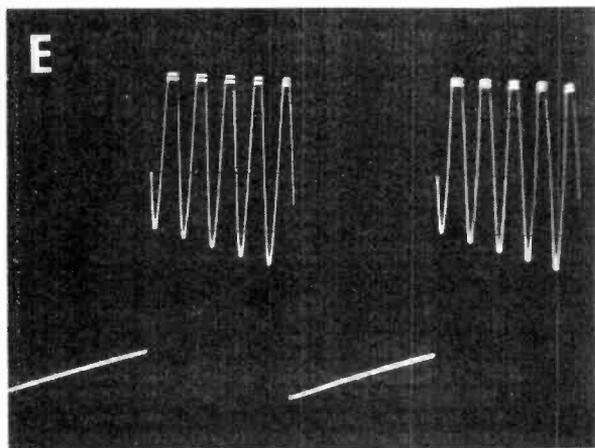The two channel switching circuit of Figs. 6 and 7 is built on a piece of veroboard using veroboard pins as anchoring points. A heatsink is fitted to the 5V voltage regulator which is fed from the +15V line. Layout and wiring is shown in Fig. 8. The board is fitted to one side of the aluminium box using 1/2in spacers. The type of socket used may be changed to suit the particular equipment in use.



Photograph D, left, shows output of an amplifier driven by a 100Hz square wave and a 1kHz sinusoidal tone burst. Photograph E, above, shows same signals at a slightly higher power level so that clipping occurs. The difference in clipping levels occurs because of the 100Hz ripple on the power supply which is not synchronised with the tone burst.

Note:—The 3N138 transistors are supplied with a shorting clip on the leadouts and this clip must be kept in position until the transistor has been completely wired into the circuit otherwise the transistor may be permanently damaged. If it is necessary to remove one of these transistors the clip must be placed on the leadout wires before unsoldering.

The LM309H voltage regulator may be replaced by the later LM309K available from Athena Ltd., 140 High Street, Egham, Surrey for £2.48 inc. ■

HOTLINES

ON RECENT DEVELOPMENTS

IT'LL CELL WELL!

THE classification of cells in the human body is not an easy task. Things called bulk separators are commonly used but these units suffer from the disadvantage that although they can handle a very large number of cells, they cannot separate them into many individual classes. A School of Medicine has come up with a novel use of a laser. The technique is to employ two laser beams which are passed through a fine column or jet of liquid which contains the human cells. The technique has proved successful in classifying rare cells (in addition to the more common ones). These rare cells are barely one thousandth of one per cent (0.001%) of the total mass of cells which make up the entire human body. This is one instrument which should, if marketed, cell very well.

THE LM195

On to the market has come a strange beast which can only be accurately described as a three-terminal monolithic circuit. It's a power transistor and yet it isn't—if you see what I mean? Well, look at it this way, this device simulates a power transistor but it has a number of features which, claims the manufacturers, makes it more attractive. For example, not only will it protect itself, but it will also protect anything which it is connected to.

Magic number for the device is the LM195. The chip contains some 50 components and the gain is around one million. Power capability is 40W and the chip is "blow-up proof" at currents up to 2A. Included in the safety circuitry on the chip are sections which handle or effect current-limiting and thermal shut-down which disconnect the power stage if the current rises above 2A. They will also do this if the chip temperature rises above 165°C.

If a conventional power transistor blows it can become a virtual short circuit and can thus pass excessive current and ruin other, often costly components. The LM195 however, becomes an open circuit even if the chip itself is destroyed. With a

switching threshold of 2V, a switching speed of around 500ns the device looks very useful for a number of applications. Base input current is 3 μ A over the whole of the voltage input range of 0-42V. This device is quite remarkable when compared to early power transistors which were happy to melt quietly into diodes at the first sign of trouble.

Power is not only for the lower frequencies. Impatt diodes are currently available which can handle 12W of peak power at 10GHz. Others of the silicon mesa type have a similar rating at 16GHz.

RADAR CARS

One of the dreams of the boffins is a radar system for motor cars. Late last year, a British company showed a Triumph PI fitted with a form of radar system. A foreign company has now released details about its approach to the problem. Use is made of pulsed radar principles (this is common to most systems under investigation) because it gives a better performance under bad weather conditions than some other methods.

A small horn antenna under the car bonnet is employed to transmit and receive the beam of radar pulses at around 9GHz. When the distance between the moving vehicle and an object ahead becomes less than that permissible in terms of safety, an alarm is sounded. As the moving vehicle gets closer to the object, the alarm increases in its intensity.

For those who are thinking about "knocking up" such a system, let's look at the internal circuitry/system within the vehicle. In the arrangement described, a computer is employed (albeit a small one). This makes all the necessary calculations and takes into account the speed of the host vehicle (picked up from a transducer), the speed difference between the object ahead and the host vehicle, the rate of braking or deceleration of the two.

Before starting his journey, the driver tells the computer what the road conditions are like—icy, wet or dry, etc. The computer can thus make due allowance for these. It also allows about 1.5 seconds for driver

reaction time too. If the driver forgets to tell the computer what the conditions are like then the computer will assume the very worst conditions and proceed accordingly with its calculations. The system is still under development and other workers are also experimenting with various ideas, meanwhile it is the computer between the drivers ears which will have to do the work of obstacle avoidance on the roads.

SOLAR CELLS

In earlier Hotlines, comment has been made about solar cells. The Plessey Company has managed to achieve efficiencies of some 20% although these items are still in the laboratory. In a more practical vein, Ferranti Limited are gearing up to produce panels of solar cells which are intended to be offered to the small boat market. The panel of cells will be used to keep the craft's batteries charged. The cells will have a rating of around 14V at 500mA in sunlight. Rumoured price is between £100 and £200, clearly not a thing to be bought lightly.

CALCULATORS

Electronic calculators are still making amazing progress. The latest is the HP-65 which does just about everything and could very, very nearly qualify for the title of hand-held computer. It will even accept programmed magnetic cards. Diagnostic cards are supplied and thus the user is able to test the calculator quite simply. Individual programs can be made and sent to the manufacturer who will test them if required. Most of the circuitry is located on 12 specially designed l.s.i. chips. Price at the moment is around the £300 mark. However, calculators which sold last year for £60 are now selling at £25 so perhaps the average housewife will find herself in the supermarket juggling with cost or even finding exponential creeping into the price of a can of baked beans.

Ginsberg

C. T. ELECTRONICS

267 ACTON LANE, LONDON
W4 5DG 01-994 6275

MAIL ORDER DEPT./REGISTERED OFFICE/COMPONENT COUNTER

SEMICONDUCTORS

AC107	35p	BCY33	45p	MJE370	75p	OC77	40p	ZTX501	20p	2N2905	45p
AC125	25p	BCY34	45p	MJE371	80p	OC81	25p	ZTX504	50p	2N2906	25p
AC128	25p	BCY38	65p	MJE520	60p	OC83	25p	ZTX531	30p	2N2907	30p
AC127	25p	BCY39	85p	MJE521	75p	OC84	25p	ZTX550	30p	2N2926G	13p
AC128	25p	BCY55	£1-20	MJE2955	£1-95	OC139	40p	1N914	8p	2N3053	25p
AC176	25p	BCY70	22p	MJE3955	85p	OC140	25p	1N916	8p	2N3054	60p
AC187	25p	BCY71	20p	MM1613	43p	OC170	25p	1N4001	7p	2N3055	65p
AC188	30p	BCY72	20p	MM1712	60p	OC171	25p	1N4002	8p	2N3232	70p
AD140	55p	BD121	75p	MPF102	45p	OC200	50p	1N4003	9p	2N3440	60p
AD149	65p	BD123	75p	MPF103	60p	OC201	60p	1N4004	10p	2N3702	14p
AD181	44p	BD124	75p	(2N5457)	35p	OC202	75p	1N4005	12p	2N3703	12p
AD182	44p	BD131	75p	MPF104	80p	OC205	80p	1N4006	13p	2N3704	12p
A F114	25p	BD132	75p	(2N5458)	40p	TIP29A	50p	1N4007	14p	2N3705	12p
A F115	25p	BD137	75p	MP1450	60p	TIP30A	60p	1N4149	7p	2N3706	12p
A F116	25p	BD156	75p	(2N5459)	40p	TIP31A	65p	2N696	30p	2N3707	12p
A F117	25p	BDY11	£1-40	NKT135	35p	TIP32A	75p	2N697	25p	2N3708	12p
A F118	50p	BF152	20p	NKT222	25p	TIP33A	£1-05	2N698	25p	2N3709	14p
A F172	30p	BF194	14p	NKT401	75p	TIP34A	£1-55	2N706	12p	2N3771	£2-80
BA102	30p	BF195	15p	NKT404	80p	TIP35A	£3-35	2N708A	15p	2N3772	£3-00
BA112	50p	BF196	15p	NKT773	25p	TIP36A	£3-65	2N708	15p	2N3773	£3-40
BA114	18p	BFX29	30p	NKT774	25p	TIP41A	75p	2N930	20p	2N3819	35p
BC107	14p	BFX84	30p	OA5	25p	TIP42A	95p	2N1132	25p	2N3820	55p
BC108	14p	BFX85	30p	OA10	50p	TIP29B	60p	2N1302	20p	2N3866	85p
BC109	14p	BFX86	30p	OA47	10p	TIP30B	70p	2N1303	20p	2N3904	22p
BC109c	10p	BFX87	30p	OA70	12p	TIP31B	75p	2N1304	25p	2N3905	22p
BC147	12p	BFY41	30p	OA81	10p	TIP32B	85p	2N1305	25p	2N4058	12p
BC148	12p	BFY44	50p	OA90	10p	TIP33B	£1-20	2N1306	25p	2N4059	12p
BC149	12p	BFY50	25p	OA91	10p	TIP34B	£1-75	2N1307	35p	2N4060	12p
BC157	14p	BFY51	25p	OA200	10p	TIP35B	£2-90	2N1308	35p	2N4061	14p
BC158	14p	BFY52	25p	OA202	10p	TIP36B	£3-80	2N1309	35p	2N4126	17p
BC159	14p	BFY53	25p	OA210	35p	TIP29C	75p	2N1613	25p	2N4286	15p
BC159c	15p	BFY90	60p	OA211	35p	TIP30C	85p	2N1711	25p	2N4287	15p
BC182	13p	BSW63	60p	OC16	90p	TIP31C	90p	2N1660	65p	2N4288	15p
BC183	13p	BSW68	75p	OC19	85p	TIP32C	£1-10	2N2217	35p	2N4289	15p
BC184	13p	BSY95A	12p	OC22	55p	TIP33C	£1-35	2N2218	30p	2N4290	15p
BC212	15p	BY127	20p	OC26	65p	TIP34C	£2-00	2N2219	35p	2N4444	£1-90
BC213	15p	BY164	60p	OC28	65p	TIP35C	£3-25	2N2222	25p	2N4871	35p
BC214	15p	IS103	15p	OC35	90p	TIP36C	£4-25	2N222A	25p	2N5191	90p
BC238	14p	MJ340	50p	OC44	20p	TIS50	20p	2N2398	70p	2N5194	£1-10
BC239	14p	MJ481	95p	OC45	20p	ZTX107	15p	2N2646	50p	40360	50p
BCY30	40p	MJ2801	£1-20	OC71	17p	ZTX300	15p	2N2846	£1-50	40361	50p
BCY31	55p	MJ2901	£2-20	OC75	25p	ZTX500	16p	2N2904	30p	40362	55p
BCY32	95p	MJE340	50p	OC76	25p						

DIGITAL INTEGRATED CIRCUITS

SN7400	28p	SN7423	52p	SN7451	25p	SN7493	75p	SN74151	£1-10	SN74176	£1-60
SN7401	38p	SN7425	48p	SN7454	28p	SN7494	80p	SN74153	£1-35	SN74177	£1-60
SN7402	28p	SN7427	48p	SN7456	25p	SN7495	80p	SN74154	£2-00	SN74180	£1-55
SN7403	28p	SN7428	50p	SN7470	30p	SN7496	£1-00	SN74155	£1-55	SN74181	£7-00
SN7404	40p	SN7430	30p	SN7472	30p	SN7497	£6-25	SN74156	£1-55	SN74182	£2-00
SN7405	40p	SN7432	48p	SN7473	57p	SN74100	£2-50	SN74157	£1-80	SN74184	£2-45
SN7406	40p	SN7433	70p	SN7474	50p	SN74104	£1-45	SN74160	£2-60	SN74185	£2-40
SN7407	50p	SN7437	70p	SN7475	96p	SN74105	£1-45	SN74161	£2-40	SN74190	£1-85
SN7408	50p	SN7438	85p	SN7476	85p	SN74107	80p	SN74162	£2-40	SN74191	£1-85
SN7409	45p	SN7440	35p	SN7478	80p	SN74110	80p	SN74163	£2-60	SN74192	£2-00
SN7410	28p	SN7441	75p	SN7481	£1-25	SN74118	£1-00	SN74164	£2-75	SN74193	£2-00
SN7411	24p	SN7442	75p	SN7482	40p	SN74119	£1-90	SN74165	£4-00	SN74194	£2-00
SN7412	42p	SN7443	£1-05	SN7483	£1-00	SN74121	65p	SN74166	£4-00	SN74195	£1-85
SN7413	60p	SN7445	£2-00	SN7484	95p	SN74122	£1-35	SN74167	£6-25	SN74196	£1-50
SN7414	40p	SN7448	£2-00	SN7485	95p	SN74123	£2-70	SN74170	£2-10	SN74197	£1-50
SN7417	40p	SN7447	£1-75	SN7490	75p	SN74141	£1-00	SN74174	£2-00	SN74198	£4-60
SN7420	20p	SN7448	£2-00	SN7491	£1-20	SN74145	£1-50	SN74175	£1-35	SN74199	£4-60
SN7422	48p	SN7450	25p	SN7492	75p	SN74150	£3-35				

S.C.R.s

CRS1/05	40p
CRS1/10	55p
CRS1/20	60p
CRS1/40	65p
CRS1/60	90p
CRS3/10	62p
CRS3/20	62p
CRS4/00	90p
CRS7/400	90p
CRS16/100	85p
CRS16/200	90p
CRS16/600	£1-60
C106B	45p
C106D	70p
40669	35p
TIC44	35p
2N4444	£1-90

TRIACS

TXL228B	8A 400V	95p
SC40D		£1-40
SC40E		£1-65
SC45D		£1-70
SC45E		£2-10
SC50D		£2-42
SC50E		£2-70
DIAC		25p

LINEAR I.C.s

LM309K	5V. 1A. Volt- age Reg.	£2-10
LM723C	2-37V. 150mA	
MFC4000	250mW Audio 60p	£1-05
TBA800	5Watt Audio	£1-50
709C	Op Amp D.I.L./ TO99	45p
741C	Op Amp 8/14	55p
741C	Op Amp D.I.L.	75p
747C	Dual Op Amp.	£1-20
ZN414	Radio I.C.	£1-25
TAD100	Radio I.C. Inc. Filter	£1-90
CA3014		£1-55
CA3018		£1-00
CA3028		£1-20
CA3036		£1-00
CA3044		95p
CA3048		£2-35
CA3075		£1-60
CA3090Q		£4-85
MC1303L		£2-20

LOW COST OSCILLOSCOPES

Cossor	Solartron
1035 D.B.	CD643.1
1049 Mk. 3A	CD7115.2
D.B.	
1049 Mk.4.	EMI
D.B.	WM2
Solartron	WM3B
AD557	WM7
CD513.2	WM8
CD523 S.2	WM16
CD643	WM18
	WM26

All prices and details on applications, phone 01-994 6275. Inspection welcome—call at warehouse.

V.A.T.

Unless otherwise stated all prices are EXCLUSIVE of V.A.T. Please add 10% to all orders. Carriage: orders under £5 + 20p. Over £5 post free.

WAREHOUSE

20-24 BEAUMONT ROAD, W.4.
SURPLUS COMPONENTS, TEST EQUIPMENT, etc. etc.

THOUSANDS OF BARGAINS

Test Equipment ★ Oscilloscopes ★ Signal Generators ★ Counters
Cabinets ★ Bridges ★ Meters ★ Transmitters ★ Receivers ★ Power
Supplies ★ Laboratory Equipment ★ Galvanometers ★ Audio Equipment
★ Video Equipment ★ Meters ★ Battery Chargers ★ Motors ★ Etc. ★ Etc.

20 TONS OF ELECTRONIC EQUIPMENT

Resistors ★ Relays ★ Capacitors ★ Switches ★ Transformers ★ Meters
★ Potentiometers ★ Component Panels ★ Semiconductors ★ Cable ★
Values ★ Etc. ★ Etc. ★ Etc.

Regret no lists available. Personal callers only. Cash and Carry only.

AUDIO ACCESSORY SHOP

17, TURNHAM GREEN, TERRACE,
CHISWICK W4.

VALVE AMPLIFIERS

5 Watt	£12-50	50 Watt	£36-25
15 Watt	£24-50	150 Watt	£75-90
30 Watt	£29-50	500 Watt	£124-50

TRANSISTOR AMPLIFIERS

FAL Phase 50W	£39-93	FAL Phase 100W	£69-95
---------------	--------	----------------	--------

DISCO CONSOLES

FAL Disco Mk 2	£82-99	FAL Power Disco	£123-75
----------------	--------	-----------------	---------

(with 70W RMS Amp)

HEAVY DUTY LOUDSPEAKERS

★ SPECIAL OFFER PRICE ★	DISCO LIGHTING
Decca 8in 10 watt Hi-Fi speaker, plus matching tweeter £7-50 complete	Sound-lighting module £7-90
Suitable 2 way Xover	3 channel sound-light £22-50
15in. 70W E.M.I. 8 ohm	Oilwheel 6in dia. £5-25
	Suitable irpm motor £1-00
	Strobe 4 Joule £25-00
	Single flash box £7-50
	(1003R Red, Blue, Gn. Yel.)
	Triple flash box £16-25
	150W Projector and Wheel £25-00

TEAK VENEERED SPEAKER CABINETS

For 8 x 8in Speaker	Size 7½ x 11½ x 5½	£3-50
8in + Tweeter	9½ x 13½ x 5½	£5-00
13 x 8in	10½ x 17 x 6	£5-75
13 x 8in + Tweeter	12 x 18½ x 8½	£7-50
12in + Tweeter	15½ x 18 x 8½	£9-00

REXING COVERED SPEAKER CABINETS

Suitable for P.A. or DISCO use; takes 12in. speaker unit. Size approx. 18 x 18 x 8in. £9-00

SPEAKER CLOTH

Available In Black or Green; approx. width 54in. £1-75/yd.

HEADPHONES

Type H-20. Features: Mono/stereo switch, Volume controls on each channel. Freq. response: 20-20,000Hz. Impedance: 4-16ohms. £4-50

ELECTRONIC COMPONENTS BARGAIN COMPONENT PACKS

SGS EA1000	Pack No.
3W AMPLIFIER	1 500 Carbon resistors, ½, 1, 1, 2 watt
MODULE £2-45.	2 100 Electrolytic Condensers
Handbook 10p	3 250 Ceramic, Polystyrene, Silver Mica, etc., Condensers
	4 250 Polyester, Polycarbonate, Paper, etc., Condensers.
Solidev 15W Class B	5 25 Potentiometers, assorted
Audio Amp thick film	6 250 High-stab. 1%, 2%, 5% resistors.
Circuit £3-65.	7 50 Assorted Tagstrips
Handbook 15p.	8 1lb Assorted nuts, bolts, washers, spacers, etc.
	9 25 Assorted switches, rotary, lever, micro, toggle, etc.
TBA 800 5W Audio	10 50 Preset Potentiometers.
I.C. £1	

TRANSFORMERS

SAFETY MAINS ISOLATING TRANSFORMERS
Pri. 120/240 V Sec. 120/240 V Centre Tapped and Screened

Ref. No.	VA (Watts)	Weight lb oz	Size cm.	P & P £ p
07	20	1 8	7.0 x 6.0 x 6.0	2.32 30
149	60	3 12	9.9 x 7.7 x 8.6	3.45 36
150	100	5 8	9.9 x 8.9 x 8.6	3.79 52
151	200	8 0	12.1 x 9.3 x 10.2	6.45 52
152	250	13 12	12.1 x 11.8 x 10.2	8.41 67
153	350	15 0	14.0 x 10.8 x 11.8	11.22 82
154	500	19 8	14.0 x 13.4 x 11.8	16.25 --
155	750	29 0	17.2 x 14.0 x 14.0	22.10 --
156	1000	38 0	17.2 x 16.6 x 14.0	29.87 --
158	2000	60 0	21.6 x 15.3 x 18.1	49.25 --

PLEASE NOTE NEW ADDRESS AS BELOW

AUTO TRANSFORMERS

Ref. No.	VA (Watts)	Weight lb oz	Size cm.	Auto Taps	P & P £ p
113	20	1 0	5.8 x 5.1 x 4.5	0-115-210-240	1.22 22
64	75	2 4	7.4 x 6.7 x 6.1	0-115-210-240	2.40 30
4	150	3 4	8.9 x 7.7 x 7.7	0-115-200-220-240	2.89 36
66	300	6 4	9.9 x 9.6 x 8.6	..	5.63 52
67	500	12 8	12.1 x 11.2 x 10.2	..	8.36 67
84	1000	19 8	14.0 x 13.4 x 14.3	..	15.19 82
93	1500	30 0	17.2 x 16.6 x 14.0	..	21.99 --
95	2000	32 0	17.2 x 16.6 x 14.0	..	28.70 --
73	3000	40 0	21.6 x 13.4 x 18.1	..	39.17 *

CASED AUTO TRANSFORMERS

115V 500W enclosed transformer, with mains lead and two 115V outlet sockets. £9.49, P & P 67p. 20 Watt version £2.02 P & P27p

TRANSFORMERS

PRIMARY 240-250 VOLTS 12 AND OR 24 VOLT RANGE

Ref. No.	Amps.	Weight lb oz	Size cm.	Secondary Windings	P & P £ p
111	0.5-0.25	1 8	4.8 x 2.9 x 3.5	0-12V at 0.25A x 2	1.22 22
112	1.0	1 4	6.1 x 5.8 x 4.8	0-12V at 0.5A x 2	1.44 22
18	4	2 2	6.1 x 6.4 x 6.1	0-12V at 1A x 2	1.90 22
70	6	3 8	8.9 x 8.0 x 7.7	0-12V at 2A x 2	2.66 30
108	8	4 5	9.9 x 8.9 x 8.6	0-12V at 4A x 2	3.60 52
72	10	5 6	9.9 x 9.6 x 8.6	0-12V at 5A x 2	4.25 52
116	12	6 12	9.9 x 10.2 x 10.2	0-12V at 5A x 2	5.10 52
17	16	0 8	12.1 x 9.9 x 8.6	0-12V at 8A x 2	6.56 52
115	20	11 8	14.0 x 9.6 x 11.8	0-12V at 10A x 2	8.36 67
187	30	15 15	14.0 x 12.1 x 11.8	0-12V at 15A x 2	15.40 82
226	60	32 0	17.2 x 15.3 x 14.0	0-12V at 30A x 2	28.44 *

30 VOLT RANGE

Ref. No.	Amps.	Weight lb oz	Size cm.	Secondary Taps	P & P £ p
112	0.5	1 4	6.1 x 5.8 x 4.8	0-12-15-20-24-30V	1.42 22
79	1.0	2 4	7.0 x 6.7 x 6.1	..	1.92 36
3	2.0	3 4	8.9 x 8.3 x 8.6	..	2.90 36
20	3.0	4 8	9.9 x 8.3 x 8.6	..	3.58 42
21	4.0	6 4	9.9 x 9.6 x 8.6	..	4.25 52
51	5.0	6 12	12.1 x 8.6 x 10.2	..	5.30 52
117	6.0	8 0	12.1 x 9.3 x 10.2	..	6.31 52
88	8.0	12 0	12.1 x 11.8 x 10.2	..	8.18 67
89	19.0	13 12	14.0 x 10.2 x 11.8	..	10.33 67

50 VOLT RANGE

Ref. No.	Amps.	Weight lb oz	Size cm.	Secondary Taps	P & P £ p
102	0.5	1 12	7.0 x 6.4 x 6.1	0-19-25-33-40-50V	1.90 30
103	1.0	2 12	8.3 x 7.4 x 7.0	..	2.80 36
104	2.0	5 8	9.9 x 8.9 x 8.6	..	3.87 42
105	3.0	6 12	9.9 x 10.2 x 8.6	..	5.26 52
106	4.0	10 4	12.1 x 10.5 x 10.2	..	6.99 52
107	6.0	12 14	12.1 x 10.2 x 11.8	..	10.09 67
118	8.0	18 0	14.0 x 12.7 x 11.8	..	13.51 82
119	10.0	25 0	17.2 x 12.7 x 14.0	..	16.93 *

60 VOLT RANGE

Ref. No.	Amps.	Weight lb oz	Size cm.	Secondary Taps	P & P £ p
124	0.5	2 4	7.0 x 6.7 x 6.1	0-24-30-40-42B-69C	1.93 36
126	1.0	3 4	8.9 x 7.7 x 7.7	..	2.70 36
127	2.0	6 4	9.9 x 9.6 x 8.6	..	3.58 42
125	3.0	8 12	12.1 x 9.9 x 10.2	..	4.66 52
123	4.0	13 12	12.1 x 11.8 x 10.2	..	8.36 67
40	5.0	12 00	14.0 x 10.2 x 11.8	..	9.85 87
120	6.0	15 8	14.0 x 12.1 x 11.8	..	12.14 82
121	8.0	25 00	14.0 x 14.7 x 11.8	..	13.65 **
122	10.0	25 0	17.2 x 12.7 x 14.0	..	20.09 **
189	12.0	29 00	17.2 x 14.0 x 14.0	..	22.49 **

MINIATURE TRANSFORMERS WITH SCREENS P & P

Ref. No.	MA	Weight lb oz	Size cm.	VOLTS	P & P £ p
238	200	2	2.8x2.6x2.0	3-0-3	1.31 10
212	1A 1A	1 4	6.1x5.8x4.8	0-6-0-6	1.52 22
13	100	4	3.9x2.6x2.9	9-0-9	1.12 10
235	330,330	4	4.8x2.9x3.5	0.9-0.9	1.52 10
207	500, 500	4	6.1x5.4x4.8	0.8-9.0-8.9	2.03 22
208	1A, 1A	1 12	7.0x6.4x6.1	0.8-9.0-8.9	2.73 30
236	200, 200	4	4.8x2.9x3.5	0-15, 0-15	1.52 10
214	300, 300	1 4	6.1x5.8x4.8	0-20, 0-20	1.60 22
221	700 (D.C.)	1 8	7.0x6.1x6.1	20-12-0-12-20	1.41 30
206	1A, 1A	2 12	8.3x7.7x7.7	0-15-20, 0-15-20	3.08 36
203	500, 500	2 4	8.3x7.0x7.0	0-15-27, 0-15-27	2.82 38
204	1A, 1A	3 4	8.9x7.7x7.7	0-15-27, 0-15-27	2.86 38

PLEASE ADD 10% FOR V.A.T. INCLUDING P. & P.

BARRIE electronics

3, THE MINORIES, LONDON EC3N 1BJ

TELEPHONE: 01-488 3316/8

NEAREST WIRE STATIONS: ALDGATE & LIVERPOOL ST.

STILL at £42.50
Solartron CD 711S.2 Double Beam Oscilloscope DC-9 mc/s; 3 mv/cm; trigger delay; crystal calibrator; 4; flat faced tube, in good working condition. Carr. £1.50.

12" LONG PERSISTENCE CRT.
Full spec. Price £7.50 to include V.A.T. and Carriage.

MAKE YOUR SINGLE BEAM SCOPE INTO A DOUBLE WITH OUR NEW LOW PRICED SOLID STATE SWITCH. 2 Hz to 8 MHz. Hook up a 9 volt battery and connect to your scope and have two traces for ONLY £5.50, P. & P. 25p. (Not cased, not calibrated.)

NEW WIDE RANGE WOBBULATOR. 5 MHz to 150 MHz up to 15 MHz sweep width. Only 3 controls, preset RF level, sweep width and frequency. Ideal for 10-7 or TV IF alignment, filters, receivers. Can be used with any general purpose scope. Full instructions supplied. Connect 6.3V A.C. and use within minutes of receiving. All this for ONLY £5.75, P. & P. 25p. (Not cased, not calibrated.)

20 Hz to 200 kHz WB.

SINE and SQUARE GENERATOR. Four ranges. Independent amplitude controls, thermistor stabilised. Ready to use, 9V supply required. £7.85 each, P. & P. 25p. (Not cased, not calibrated.)

GRATICULES. 12cm x 14cm high quality plastic 15p each, P. & P. 5p. £1 worth of 'UFS'. Six Brand New capacitors all between 15V and 100V. Total capacitance not less than 7,000mfd. P & P 45p.

ROTARY SWITCH PACK—6 brand new switches (1 ceramic; 2 off 4pole 2 way etc.). 50p P & P 20p.

PLEASE ADD 10% V.A.T.

CHILTMead LTD
7/9 ARTHUR ROAD, READING, BERKS.
(rear Tech. College) Tel.: Reading 582605/65916

COMPONENT PACK consisting of 5 pots, various, brand new; 250 resistors 1/4 and 1/2 watt, many high stabs, etc. Fine value at 50p, P. & P. 17p.

P.C.B. PACKS S & D. Quantity 2 sq ft—no tiny pieces. 50p plus P. & P. 20p.

FIBRE GLASS as above £1 plus P. & P. 20p.

5 CRYSTALS 70 to 90kHz. Our choice. 25p, P. & P. 15p.

SANGO 50 micro amp meter 2 1/2" diameter. Ex-new radiation equip. £1.25 each P. & P. 17p.

CAPACITOR PACK—50 Brand new components, only 50p, P. & P. 17p.

POTS—10 different values. Brand new. 50p, P. & P. 17p.

TRIMMER PACK. 2 Twin 50/200pF ceramic 2 Twin 10/60pF ceramic; 2 min. strip with 4 preset 5/20pF on each; 3 air spaced preset 30/100pF on ceramic base. ALL BRAND NEW. 25p the lot, P. & P. 10p.

FLAT FACED 4" TWIN BEAM TUBE type Cossor 89D. Green trace. Brand new £4 each, P. & P. 37p.

LIGHT EMITTING DIODES (Red) from Hewlett-Packard. Brand New. 38p each. Holder 1p each. Information 5p.

PHOTOCELL equ. OCP71, 13p each. **MULLARD** OCP70—10p each.

MODERN TELEPHONES type 706. Two-tone grey. £3.75 each. Two-tone green £3.75 each. Black £2.75 each. P & P 25p ea.

Ideal EXTENSION TELEPHONES with standard GPO type dial, bell and lead coding. £1.75 each P. & P. 25p.

DELIVERED TO YOUR DOOR
1 cwt of Electronic Scrap chassis, boards, etc. No Rubbish. FOR ONLY £3.50.

Open 9 a.m. to 6.30 p.m. any day.



for fast, easy reliable soldering

Ersin Multicore Solder contains 5 cores of non-corrosive flux, instantly cleaning heavily oxidised surfaces. No extra flux is required.

EASY-TO-USE DISPENSERS



Size 5
Savbit alloy
18 swg, 24p (illustrated).
Size 19A
60/40 alloy
18 swg, 25p
Size 15
60/40 alloy
22 swg, 28p

IDEAL FOR HOME CONSTRUCTORS


Size 1 cartons in 40/60, 60/40 and Savbit alloys in 7 gauges 36p



Size 12 Reel
for Service Engineers and Electricians.
18 swg
Savbit alloy. £1.16




BIB WIRE STRIPPER AND CUTTER

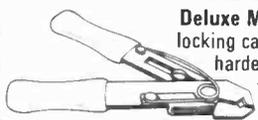


Deluxe Model 9 Automatic opening spring, locking catch, plastic-covered handles. Case hardened and precision ground. Adjusts to most wire sizes. Cuts and strips flex, splits plastic twin flex. 75p

Prices shown are recommended retail, excluding V.A.T. From Electrical and Hardware Shops. If unobtainable, send 10p p&p direct to **Bib Hi-Fi Accessories Limited, Hemel Hempstead, Herts HP2 7EP**

GOING BACK...

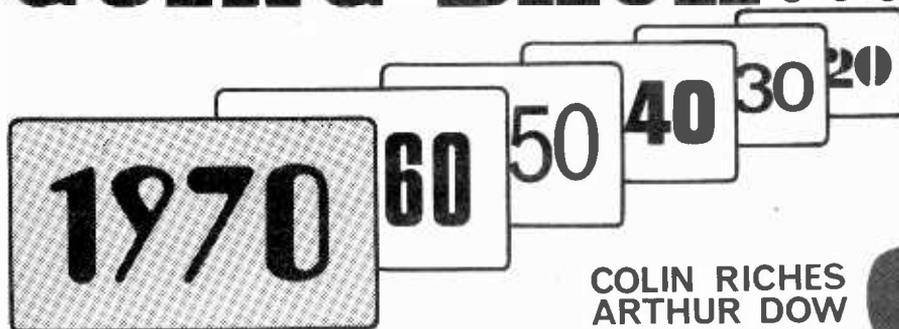

COLIN RICHES
ARTHUR DOW

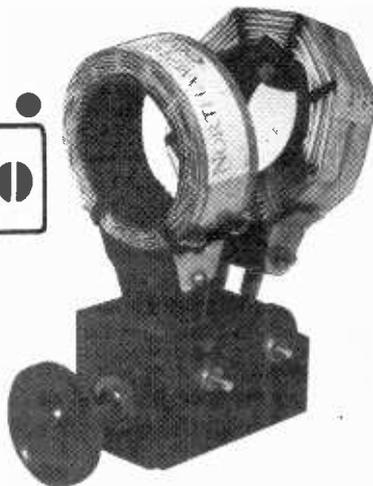

Guglielmo Marconi 1874-1937

ONE HUNDRED years ago (April 25th, 1874) Guglielmo Marconi was born in Bologna, the younger son of a wealthy Italian landowner, Giuseppe Marconi, and his Irish wife Annie, the daughter of Andrew Jameson, the whiskey distiller from County Wexford in Ireland.

To Guglielmo Marconi must go the credit for seeing the wider possibilities of wireless, of taking it out of the laboratory where pure science had shackled it, and developing practical systems for the benefit of mankind. His work, and that of the brilliant men with whom he surrounded himself in the company he formed, laid the foundations of the electronics industry as we know it today.

From an early age he was interested in science and by his late teens, at his home, the Villa Grifone, he was experimenting with electro-magnetic waves as a communication medium. By the summer of 1895 he had succeeded in transmitting signals over a few yards of space and in August, using an earth and an elevated aerial at both transmitter and receiver, he was able to pass Morse code over $1\frac{3}{4}$ miles.

The Italian Government was not greatly interested in Marconi's invention, so in 1896 he came to England where he filed the world's first patent for a system of telegraphy using Hertzian waves. A letter of introduction to William Preece, Engineer in Chief of the



Marconi pictured shortly after his arrival in England (1896).

GPO, led to a series of demonstrations culminating in 1897 in a record transmission across 8.7 miles of the Bristol Channel, where Preece himself was experimenting with inductive methods, with far less success.

The potential of wireless telegraphy was becoming clear and in 1897 the world's first radio company was formed to develop Marconi's apparatus commercially. First called the Wireless Telegraph and Signal Company, it was later renamed Marconi's Wireless Telegraph Company and in 1963, The Marconi Company.

By the end of the century, wireless had been adopted by the British and the Italian Navies, it had spanned the English Channel, it had proved its worth to the mercantile navy as a life saver and Marconi had introduced his system to the USA, where he registered The Marconi Wireless Telegraph Company of America—later to become the Radio Corporation of America (RCA).

One of Marconi's ambitions had been to use wireless as a means of ending the isolation of those at sea, and in 1900 the Marconi International Marine Communication Company was created to work an exclusive licence for all maritime purposes. At this time also he took out his famous Four Sevens patent for tuned coupled circuits.

In 1901, the world's first wireless school opened at Frinton, later transferring to Chelmsford where it still flourishes as Marconi College. This was a vintage year for Marconi. Having achieved communication over 198 miles between the Isle of Wight and the Lizard, he embarked, with the assistance of Dr. J. A. Fleming (Scientific Adviser to the Company), R. N. Vyvyan, G. Kemp and P. W. Paget, on his famous transatlantic experiment. After many vicissitudes he succeeded in receiving, through an earpiece, signals at St Johns, Newfoundland, transmitted from Poldhu, Cornwall. Even at the moment of this, his greatest triumph, some said that he mistook atmospherics for the Morse code "S". To those doubters it has been pointed out that for long distance communication to have evolved from the system that pushed three faint dots across 2,000 miles is a marvel; had there been no dots, its evolution would have been a miracle. Two months later, signals from Poldhu were recorded on a morse inker on s.s. *Philadelphia*—2099 miles away—thus dispelling any doubt about his original claim. In December 1902, Poldhu's permanent opposite number was built at Glace Bay.

During the next few years, many important patents were filed, notably those for the magnetic detector, the radio valve developed by Dr. Fleming, and the directional aerial, which was used at Clifden, in Ireland—a station that took over the transatlantic service from Poldhu. In 1909, Marconi shared a Nobel Prize for Physics in recognition of his contribution to wireless telegraphy.

The decade that preceded the First World War also saw the first use of wireless in the air, transmission initially being achieved from a captive balloon and then, in 1910, from an aeroplane flown by J. D. A. McCurdy. It also saw wireless used to assist the capture of the notorious murderer, Dr. Crippen, and to save lives when the ill-fated *Titanic* foundered.

When war broke out in 1914, the Admiralty at once took over the Marconi radio factory. This, the first in the world, had transferred in 1912 from Hall Street, Chelmsford, to a new, purpose-designed building a mile or so away. The Clifden station and Marconi's operational equipment in Chelmsford and London were also taken over, along with the first long-wave transatlantic wireless station for direct communication with the USA, completed by Marconi during 1914.

The Company, having developed direction-finding techniques before the war, established a chain of stations that were used to devastating effect against enemy Zeppelins, submarines and surface ships, and led, indeed, to the Battle of Jutland. For the Royal Navy's world-wide communications network, the Company built a dozen widely dispersed stations.

Air-to-ground telegraphy was perfected and the difficulties of ground-to-air telephony were overcome by three Marconi engineers, Major C. E. Prince, Capt. H. J. Round and Lt. J. M. Furnival—the last named also supervising the achievement of inter-plane telephony in 1917.

Marconi himself was commissioned in the Italian Army. He later became heavily engaged on diplomatic work for Italy and after the war was appointed Plenipotentiary Delegate to the Paris Peace Conference.


In 1919, Marconi bought his yacht, *Elettra*, which he equipped as a laboratory; a Marconi engineer made the first east to west transatlantic telephony transmission; and the embryo of broadcasting took shape in Chelmsford.

In 1920, at Marconi's Works, Nellie Melba gave a song recital for Britain's first advertised public broadcast. Twenty months later the Company was licensed for regular broadcasting and erected the famous 2MT station in an ex-army hut at its Writtle Laboratories. A licence was also granted for the 2LO station in Marconi House, London. Later in 1922, at the instigation of the PMG, Marconi's and five other manufacturers formed the British Broadcasting Company, superseded in 1926 by the British Broadcasting Corporation.

The Marconiphone Company, formed in 1922 to satisfy the demand for domestic receivers, was sold to RCA in 1929 and later merged with two other companies to become EMI, of which Marconi was President.

Meanwhile, the Company supplied the equipment for the BBC's new longwave station at Daventry, which took over the 5XX call sign of an earlier station built at Chelmsford.

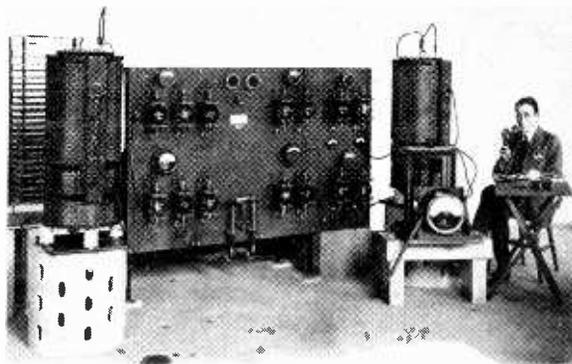Running parallel with the Company's broadcasting activity was Marconi's involvement with the Govern-



Experimental transmitter at Marconi's Chelmsford works. It inaugurated the world's first broadcast news service in February 1920.

ment's plan to link the Empire through a wireless communication network. First mooted in 1906, the Imperial Wireless chain contract was awarded to Marconi in 1924, exactly fifty years ago. The first station was opened in 1926 and, in common with all those that followed, used the Marconi-Franklin Beam System—a newly developed, revolutionary form of shortwave directional transmission. The Company too built its own beam stations for communicating with countries outside the Empire.

The success of the Imperial Wireless Chain so threatened the Empire cable companies that, in 1929, at the instigation of the respective governments, their interests were merged with those of the Marconi Company in a new organisation, Cable and Wireless Limited.

This step shattered Marconi's life-long ambition to control an Empire-wide wireless network. Disappointed and in ill-health, he was increasingly drawn to his home in Italy, from which he conducted microwave experiments, installing the first microwave telephone link in 1932, and in 1935 demonstrating principles of radar.

Meanwhile his company in England was advancing the new medium of television, its interests in which it merged with those of EMI to form The Marconi-EMI Television Company Limited (later dissolved) whose system was adopted in 1936 by the BBC for the world's first public high definition television service.

In Italy, Marconi's health was deteriorating rapidly. He was taken ill on 19th July, 1937 and died the following day. Of all the tributes that followed, the most impressive, the gesture that was unique, was the closing down for two minutes of wireless stations throughout the world. The "ether" was as quiet as it had been before Marconi.


The years following Marconi's death saw far-reaching changes in the Company that bore his name. After the merger in 1968 of the General Electric Company and the English Electric Company, which had bought The Marconi Company from Cable and Wireless after the war, it became responsible, through its newly created subsidiary, GEC-Marconi Electronics Limited, for the management of all GEC's major capital electronics interests, which at the present time are represented in eight autonomous UK companies and nine overseas subsidiaries.

We would like to extend our thanks to GEC-Marconi Electronics Ltd. for supplying the information used in this article.



WORK WITH ADCOLA AND YOU KNOW YOU ARE USING THE BEST ELECTRICAL SOLDERING EQUIPMENT!

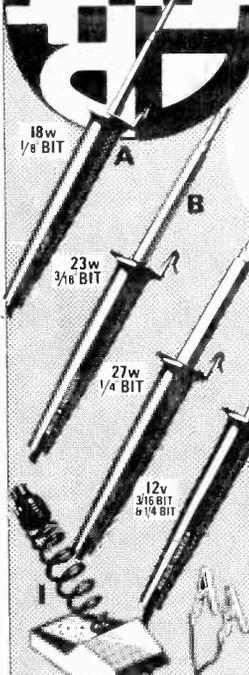When you buy ADCOLA equipment you are purchasing the best soldering merchandise. These instruments identical to those used in industry world wide. The electronics industry use ADCOLA for our reliability, efficiency, precision and high safety standards. ADCOLA must be right for you! Treat yourself to the BEST! Order on your coupon NOW




Please send me the following items

- A L706 INVADER Soldering instrument £2.42
- B L646 INVADER Soldering instrument £2.66
- C L1676 INVADER Soldering instrument £2.73
- D BL646 INVADER 12v Battery model £3.35
- E BL1076 INVADER 12v Battery model £3.50
- F INVADER Soldering Kit £4.73
- G R500 ELECTRIC Desoldering tool £9.79
- H REEL Desoldering Braid £0.75
- I L686 SOLDERING stand £1.97
- J L68 PROTECTIVE stand £1.31
- K 1/2 KILO SOLDER REEL £1.74
- L 3oz SOLDER REEL £0.52
- M SOLDER PACK £0.10

New Catalogue All prices include 10% VAT Please tick items required

PRINT NAME _____
 PRINT ADDRESS _____

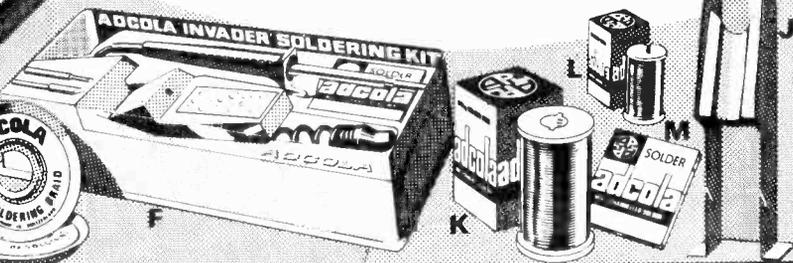

Post to ADCOLA PRODUCTS LTD. ADCOLA HOUSE GAUDEN ROAD LONDON SW4 6LH VAT REGD No. 235 6153 72 REGD No. 442762

GIRO NO. 331 7056
 C.W.O. only, P. & P. 10p on orders below £5
 Discount: £10-10%, £20-15% (except net items)
 Export Order enquiries welcome (VAT free)
 Official Orders accepted from Educational & Government Departments
ALL PRICES INCLUDE VAT

SPECIAL RESISTOR KITS (Prices include post & packing)
 10E12 1W KIT: 10 of each E12 value, 22 ohms—1M, a total of 570 (CARBON FILM 5%), £3.65 net
 10E12 1W KIT: 10 of each E12 value, 22 ohms—1M, a total of 570 (CARBON FILM 5%), £3.85 net
 25E12 1W KIT: 25 of each E12 value, 22 ohms—1M, a total of 1425 (CARBON FILM 5%), £8.35 net
 25E12 1W KIT: 25 of each E12 value, 22 ohms—1M, a total of 1425 (CARBON FILM 5%), £8.45 net
 20E12 1W KIT: 20 of each E12 value, 22 ohms—2M2, a total of 1220 (METAL FILM 5%), £11.05 net
 15E12 1W KIT: 15 of each E12 value, 10 ohms—1M, a total of 915 (METAL FILM 5%), £11.35 net
 10E12 2W KIT: 10 of each E12 value, 10 ohms—1M, a total of 610 (METAL FILM 5%), £17.15 net

MULLARD POLYESTER CAPACITORS C280 SERIES
 250V P.C. Mounting: 0.01µF, 0.015µF, 0.022µF, 0.033µF, 0.047µF, 3p, 0.068µF, 0.1µF, 4p, 0.15µF, 4p, 0.22µF, 5p, 0.33µF, 8p, 0.47µF, 9p, 0.68µF, 12p, 1µF, 15p, 1.5µF, 23p, 2.2µF, 26p.

MULLARD POLYESTER CAPACITORS C296 SERIES
 400V, 0.001µF, 0.0015µF, 0.0022µF, 0.0033µF, 0.0047µF, 2p, 0.0068µF, 0.01µF, 0.015µF, 0.022µF, 0.033µF, 0.047µF, 0.068µF, 0.1µF, 4p, 0.15µF, 6p, 0.22µF, 8p, 0.33µF, 12p, 0.47µF, 14p.

MINIATURE CERAMIC PLATE CAPACITORS
 50V: (pF) 22, 27, 33, 39, 47, 56, 68, 82, 100, 120, 150, 180, 220, 270, 330, 390, 470, 560, 680, 820, 1K, 1K5, 2K2, 3K3, 4K7, 6K8, (µF) 0.01, 0.015, 0.022, 0.033, 0.047, 21p, each, 0.1, 30V, 43p.

POLYSTYRENE CAPACITORS 160V 5%
 (pF) 10, 15, 22, 33, 47, 68, 100, 150, 220, 330, 470, 680, 1000, 1500, 2200, 3300, 4700, 4p, 6800, 10,000, 43p

RESISTORS
 CF—High Stab Carbon Film, 5%, MF—High Stab Metal Film, 5%
 W, Type Range 1-99 100-499 500-999 1000+ Size mm

CF 22-1M	1	0.75	0.60	0.55	2.4 x 7.5
CF 22-2M2	1	0.75	0.60	0.55	3.9 x 10.5
CF 22-1M	1	0.75	0.60	0.55	5 x 16
MF 10-2M7	2	1.54	1.32	1	3x7
MF 10-2M2	2	1.43	1.21	1	4.2 x 10.8
MF 10-10M	3	1.98	1.81	1	6.6 x 13
2 MF 10-MIX	4, 5	3.52	3.08	2.75	8.17 x 5

For value mixing prices, please refer to our catalogue. (price in pence each)
 VALUES AVAILABLE—E12 Series only. NET PRICES ABOVE 100.

PRESET SKELETON POTENTIOMETERS
 MINIATURE 0.25W Vertical or horizontal 6p each 1K, 2K2, 4K7, 10K, etc. up to 1M Ω
 SUB-MIN 0.05W Vertical, 100 Ω to 220K Ω 5p each

B. H. COMPONENT FACTORS LTD.

(P.W.) 61 CHEDDINGTON ROAD, PITSTONE, NR. LEIGHTON BUZZARD, BEDS, LU7 9AQ
 Tel.: Cheddington 668446 (Std. Code 0296)
 PLEASE WRITE FOR FREE CATALOGUE

Miniature Mullard Electrolytics

1.0µF 63V 6p	68µF 16V 6p
1.5µF 63V 6p	68µF 16V 12p
2.2µF 63V 6p	100µF 10V 6p
3.3µF 63V 6p	100µF 25V 6p
4.0µF 40V 6p	100µF 63V 14p
4.7µF 63V 6p	150µF 16V 6p
6.8µF 63V 6p	150µF 63V 15p
8.0µF 40V 6p	220µF 6.4V 6p
10µF 16V 6p	220µF 10V 6p
10µF 25V 6p	220µF 16V 8p
10µF 63V 6p	220µF 63V 21p
15µF 16V 6p	330µF 16V 12p
15µF 63V 6p	330µF 63V 25p
16µF 40V 6p	470µF 6.4V 9p
22µF 25V 6p	470µF 40V 20p
22µF 63V 6p	680µF 16V 15p
32µF 10V 6p	680µF 40V 25p
33µF 16V 6p	1000µF 16V 20p
33µF 40V 6p	1000µF 25V 25p
32µF 63V 6p	1500µF 6.4 15p
47µF 10V 6p	1500µF 16V 25p
47µF 25V 6p	2200µF 10V 25p
47µF 63V 8p	3300µF 6.4 26p

VEROBOARD 0.1 0.15

21 x 5"	28p 28p
21 x 3"	26p 19p
31 x 5"	32p 33p
31 x 3"	28p 28p
21 x 1"	7p 7p
21 x 5" (Plain)	— 14p
21 x 3" (Plain)	— 12p
5 x 31" (Plain)	— 22p
Insertion tool	59p 59p
Track Cutter	44p 44p
Pins, Pkt. 25	10p 10p

TRANSISTORS

AC127 16p	BC212L 12p
AC128 22p	BC213L 12p
BC107 11p	BC214L 17p
BC108 12p	OC44 18p
BC109 13p	OC71 13p
BC148 12p	OC81 16p
BC149 12p	OC170 23p
BC182L 12p	TIS43 33p
BC183L 12p	2N2925 11p
BC184L 13p	2N3702 11p

POTENTIOMETERS
 Carbon Track 5K Ω to 2M Ω, log or lin, Single, 16p Dual Gang 46p, Log Single with switch 26p
 Slider Posts, 10K, 100K, 500K, 30mm, 34p, 45mm, 47p, 60mm, 55p.

DIODES

IN4001 6p
IN4002 7p
IN4003 9p
IN4004 9p
IN4005 12p
IN4006 14p
IN914 7p
IN916 7p
BA100 10p
OAS 42p
OAA7 9p
OAB1 11p
OAZ20 8p

PLUGS

DIN 2 Pin 12p
3 Pin 13p
5 Pin 18p 15p
5 Pin 18p 14p
2.5mm Jack 11p
Phono 5p

SOCKETS

DIN 2 Pin 10p
3 Pin 10p
3 Pin 12p
5 Pin 18p 15p
5 Pin 18p 14p
2.5mm Jack 11p
Phono 5p

Integrated Circuits

HA709C 50p
HA741C 55p
HA723C 11p
HL914 35p

Screened Wire, Metre 6p
Twin Screened Wire, Metre 12p
Stereo Screened Wire, Metre 12p
Connecting Wire, All colours, Metre 21p
Neon Bulb, 90V Wire Ended 5 for 24p
Panel Neon, 240V Red, Amber, Clear 16p

ELECTROLYTIC CAPACITORS. Tubular & Large Cans (µF/V): 1/25, 2/25, 4/25, 4 7/10, 5/25, 8/25, 10/10, 10/50, 16/25, 22/63, 25/25, 25/50, 32/25, 50/25, 100/10, 100/25, 61p, 50/50, 8p, 100/50, 200/25, 11p, 250/50, 18p, 500/10, 11p, 500/25, 15p, 500/50, 18p, 1000/10, 15p, 1000/25, 22p, 1000/50, 40p, 2000/10, 20p, 1000/100, 90p, 2000/25, 30p, 2000/100, 95p, 2500/25, 38p, 2500/50, 62p, 3000/50, 80p, 5000/25, 66p, 5000/50, £1.10.

HI-VOLT: 4/450, 14p, 8/350, 19p, 8/450, 20p, 16/350, 22p, 16/450, 23p, 32/350, 33p, 50/250, 20p, 100/500, 88p.

METALLISED PAPER CAPACITORS
 250V: 0.05µF, 0.1µF, 6p, 0.25, 6p, 0.5µF, 7p, 1µF, 9p, 500V: 0.025, 0.05, 6p, 0.1, 6p, 0.25, 7p, 0.5, 9p, 1000V: 0.01, 11p, 0.022, 13p, 0.047, 0.1, 15p, 0.22, 23p, 0.47, 28p.

(NEW KIT)
 SE12 VV Metal Film 5% Ultra Low Noise New Resistors with full colour coding, 5 each E12 value 10ohm/1 amp total 305 £2.75.

BENTLEY ACOUSTIC CORPORATION LTD.

7a GLOUCESTER ROAD, LITTLEHAMPTON, SUSSEX
All prices inclusive of V.A.T. Telephone 6743

0A2	.40	6BC8	.60	6LD20	.55	128J7	.44	50L6GT	.65	EAB0C80	.30	EF183	.29	KT2	.50	PL84	.38	UL82	.88	AAZ13	.80	BA153	.17	OA73	.17
0B2	.40	6BE6	.28	6N7GT	.60	128Q7	.65	85A24	.60	EAC91	.75	EF184	.32	KT41	.98	PL504/600	UM80	.44	AC187	.37	BC107	.14	OA79	.10	
0Z4	.47	6BH6	.70	6Q7G	.50	14H7	.55	85A3	1.00	EAF42	.60	EF80A	1.20	KT44	.75	.45	UF86	.80	AC126	.14	BC113	.28	OA85	.09	
1A3	.52	6CB6	.50	6Q7GT	.60	19AQ5	.45	90C1	.75	EAF901	.55	EH90	.45	KT66	2.40	PL505	1.15	UF86	1.00	AC132	.22	BC118	.25	OA95	.10
1AS2	.50	6CQ7A	.50	6Q7M	.55	19Q6	1.40	90C2	2.40	EB34	.85	EL32	.60	KT81	2.00	PL608	.90	U10	1.00	AC154	.28	BCY10	.50	OA290	.10
1A7GT	.65	6BR7	.85	6R7M	.85	20D4	2.00	15B22	.75	EB91	.15	EL34	.54	KT82	.21	PL509	1.15	U191/14	1.00	AC158	.28	BCY15	.55	OA302	.11
1BSGT	.52	6BR8	.85	6R7M	.75	20F2	.75	2155G	.50	EB041	.55	EL35	1.00	KTW62	.81	PL802	.95	U1	1.70	AC157	.28	BCY33	.22	OC29	.48
1HGT	.65	6B87	1.40	68A7	.44	20L1	.88	807	.59	EB031	.35	EL37	1.00	KTW63	1.00	PY33/2	.50	U25	.65	ACV18	.28	BF163	.22	OC46	.17
1L4	.14	6BW6	.85	68C7GT	.38	20P3	.80	5702	.80	EBF80	.89	EL41	.60	MHLD6	.21	PY81	.31	U26	.60	ACV19	.21	BF173	.22	OC70	.14
1NGT	.65	6BW7	.68	68G7	.44	20P4	.88	6057	1.00	EBF83	.43	EL41	.60	P61	1.00	PY82	.35	U81	.80	ACV20	.20	BF180	.33	OC71	.18
1R5	.38	6BZ6	.49	68H7	.44	20P6	1.30	6080	1.00	EBF89	.30	EL83	.55	PABC80	.38	PY83	.33	U91	.70	ACV21	.21	BF181	.44	OC72	.18
1S4	.38	6CB6A	.40	68K7GT	.44	25A6G	.88	6077	1.00	EBL21	1.50	EL84	.28	PC88	.60	PY88	.33	U281	.80	ACV22	.17	BF185	.44	OC74	.25
1U4	.85	6C4	.28	68Q7GT	.38	25L6G	.50	7474	1.00	EC86	.59	EL85	.40	PC88	.60	PY800	.80	U301	.58	ACV28	.20	BF194	.17	OC75	.18
1U5	.90	6C9	1.25	6V6G	.17	25Y6G	.70	AC/PEN	.98	EC88	.59	EL86	.88	PC95	.75	PY800A	.80	U403	.75	AD140	.40	BFY50	.25	OC76	.17
2D21	.49	6C9DG	.80	6V6GT	.38	25ZAG	.38	AC2/PEN	.98	EC92	.45	EL91	.38	PC97	.45	PY801	.81	U404	.49	AD145	.55	BFY51	.21	OC77	.18
2GK5	.45	6C9GA	.75	6X4	.30	25Z5	.80	DD	.98	ECC33	1.50	EL95	.39	PC90	.45	PY801	.81	U801	.76	AD161	.50	BFY52	.21	OC78	.17
2A4	.42	6C8B	.60	6X6GT	.28	25Z6G	.70	AC/PEN	.38	ECC35	.95	EL96	1.20	PC94	.40	PZ30	.48	U4020	.55	AD162	.50	BY100	.20	OC8D	.17
2E6	.19	6CL6	.55	7B6	.75	28D7	1.00	AC/TH1	.21	ECC40	1.00	ELL80	1.00	PC98	.44	QQV03/10	VP23	.75	AF106	.55	BY105	.20	OC81	.12	
3Q4	.49	6CM7	.75	7B7	.50	30A5	.65	A56	1.00	ECC81	.39	EM80	.40	PC98	.60	40	40	U301	.58	ACV28	.20	BF194	.17	OC75	.18
3Q8GT	.55	6C9U5	.75	7H7	.75	30C15	.75	ATP4	.40	ECC82	.28	EM81	.65	PC99	.60	40	40	Q875/20	.21	AF115	.17	BY128	.11	OC89D	.18
3S4	.33	6CW4	.70	7R7	1.50	30C17	.90	A21	.60	ECC83	.28	EM83	.55	PC99	.60	40	40	Q875/20	.21	AF115	.17	BY128	.11	OC89D	.18
4CB8	.55	6DE7	.75	7Y4	.65	30C18	.75	A231	.60	ECC84	.30	EM84	.40	PCF80	.28	QV04/7	.81	X65	.65	AF123	.33	BY210	.28	OC83	.28
5C08	.65	6DT8A	.75	7Z4	.80	30F5	.85	A241	.65	ECC85	.36	EM85	1.00	PCF82	.38	R19	.81	X66	.65	AF124	.28	BY211	.28	OC84	.28
5R4G	.70	6EW6	.75	7D7	.65	30FL1	.75	BL63	2.00	ECC86	.85	EM87	.68	PCF84	.59	TH233	.98	Transistors	AF125	.19	BY212	.28	OC123	.25	
5U4G	.80	6E5	1.00	10C2	.65	30FL2	.75	CL33	1.50	ECC89	.44	EM88/03	.28	PCF86	.55	TF2020	.98	& Diodes	AF126	.20	BY213	.28	OC139	.25	
5V4G	.54	6F1	.70	10D7	.55	30FL3	1.00	30P4MR	.70	ECC91	.58	EY1	.40	PCF200	.40	40	40	UABC80	.38	2N404	.20	AF139	.72	OC169	.25
5Y3GT	.38	6F6G	.60	10P1	.50	30FL13	.55	CY31	.45	ECC80A	.60	EY81	.40	PCF801	.48	UAF42	.55	2N966	.58	AF178	.75	GDS	.22	OC173	.89
5Z3	.58	6F13	.55	10P9	.65	30FL14	.65	DAF91	.30	ECC807	1.00	EY83	.54	PCF802	.50	UBC41	.55	2N1766	.55	AF180	.53	GF113	.22	OC200	.24
6Z4G	.85	6F14	.75	10P18	.55	30L15	.75	DAF96	.44	ECC80	.34	EY84	.70	PCF806	.70	UBC81	.45	2N1247	.94	AF186	.61	OA5	.81	OC201	.42
5Z4GT	.85	6F18	.55	10L1D11	.70	30L17	.70	DF91	.80	ECC82	.34	EY87/8	.38	PCH200	.70	UBF80	.38	2N297	.25	BA115	.15	OA9	.14	OC202	.47
6F0L2	.60	6F2U3	.85	12A75	.35	30FL13	.75	DM70	.75	ECC81	.30	EY85	.40	PCF82	.82	UBF69	.35	2N369	.24	BA116	.55	OA10	.47	OC203	.88
6ASG	1.25	6F24	.85	10P14	2.00	30FL14	.80	DM71	2.00	ECC83	.44	GZ23	.54	UB121	.77	2N2613	.45	BA129	.14	OA	.11	OC204	.38		
6AC7	.49	6F28	1.00	12A6	1.00	30P12	.80	DK92	.70	EZ40	.20	EZ40	.20	EY41	.58	PC184	.38	UC92	.45	2N3053	.38	BA130	.11	OA70	.17
6A65	.27	6F28	.70	12AC6	.65	30P19/	.75	DK96	.55	ECH21	1.50	EZ41	.50	PC186	.47	UC88A	.75	2N3121	2.75	UC88B	.75	2N3703	.21		
6A8H	.50	6F32	.65	12AD6	.65	30P4	.75	DL92	.38	ECH35	.65	EZ80	.24	PD500	1.44	UC88	.88	2N3709	.22	UCF80	.65	2N3709	.22		
6A75	.75	6G08A	.75	12AE6	.65	30P11	.68	DL96	.44	ECH42	.70	EZ81	.25	PCN45	.80	UCF80	.65	2N3709	.22	UCF81	.65	2N3709	.22		
6A65	.34	6G15	.65	12AT6	.35	30FL13	.75	DM70	.75	ECC81	.30	EY85	.40	PCF82	.82	UBF69	.35	2N369	.24	BA116	.55	OA10	.47	OC203	.88
6A8E	.60	6G07	.75	12AU6	.45	30FL14	.80	DM71	2.00	ECC83	.44	GZ23	.54	UB121	.77	2N2613	.45	BA129	.14	OA	.11	OC204	.38		
6A8SA	.55	6H6GT	.18	12AV6	.40	30P15	.85	DY76/7	.30	ECC84	.44	GZ33	.54	UB121	.77	2N2613	.45	BA129	.14	OA	.11	OC204	.38		
6A8N	.49	6J6GT	.12	12BA6	.30	35A3	.68	DY802	.38	ECC80	.40	GZ33	.54	UB121	.77	2N2613	.45	BA129	.14	OA	.11	OC204	.38		
6A65	.40	6J6	.35	12BE8	.38	35D5	.75	280CC	1.65	ECL82	.32	EY86	.60	PC186	.47	UC88A	.75	2N3121	2.75	UC88B	.75	2N3703	.21		
6A85	.55	6J7G	.30	12BH7	.27	35L6GT	.55	280F	1.80	ECL83	.57	EY87	.60	PC186	.47	UC88A	.75	2N3121	2.75	UC88B	.75	2N3703	.21		
6A87	1.00	6J78A	.75	12E1	3.00	35W4	.38	280F	1.80	ECL84	.60	EY87	.60	PC186	.47	UC88A	.75	2N3121	2.75	UC88B	.75	2N3703	.21		
6A76	.35	6K70	.18	12I7GT	.65	32Z3	.75	280CC	1.65	ECL85	.60	EY86	.60	PC186	.47	UC88A	.75	2N3121	2.75	UC88B	.75	2N3703	.21		
6A76	.30	6K8G	.85	12K15	1.00	35Z4GT	.42	280CC	1.65	ECL86	.40	EY86	.60	PC186	.47	UC88A	.75	2N3121	2.75	UC88B	.75	2N3703	.21		
6A76	.35	6L1	.50	12K7GT	.38	35Z5GT	.40	280CC	1.65	ECL87	1.50	EY86	.60	PC186	.47	UC88A	.75	2N3121	2.75	UC88B	.75	2N3703	.21		
6AW8A	.65	6L6GT	2.00	12Q7GT	.45	50B5	.85	E192CC1	1.00	EF40	.75	EY86	.60	PC186	.47	UC88A	.75	2N3121	2.75	UC88B	.75	2N3703	.21		
6AX4	.55	6L7	2.00	128C7	.60	50C5	.45	E148	.58	EF41	.70	EY86	.60	PC186	.47	UC88A	.75	2N3121	2.75	UC88B	.75	2N3703	.21		
6B8G	.30	6L18	.49	128G7	.38	50D6G	1.25	EAS0	.27	EF42	.55	EY86	.60	PC186	.47	UC88A	.75	2N3121	2.75	UC88B	.75	2N3703	.21		
6BA6	.25	6L19	2.00	128H7	.35	50EH6	.55	EAT6	1.00	EF73	1.50	EY86	.60	PC186	.47	UC88A	.75	2N3121	2.75	UC88B	.75	2N3703	.21		

MATCHED TRANSISTOR SETS:-
LP15 (AC113, AC164, AC174, AA120) 58p
per pack. 1-OC81 & 2-OC81, 47p.
1-OC44 & 2-OC45, 47p. 1-OC82D &
2-OC82, 52p. Set of 3-OC83, 72p.

VALVES ALSO REQUIRED FOR CASH. LOOSE OR BOXED, BUT MUST BE NEW. OFFERS MADE BY RETURN.
All parts are unused and subject to the standard 90 day guarantee. Cash or cheque with order only.
Despatch charges:- Orders below £25 add 10p per order up to three items, each additional item 3p
extra. Orders between £25 and £10 add 25p total. Orders over £10 are post free. Same day despatch
by first class mail. Any parcel insured against damage in transit for only 3p order extra. Terms
of business free on request.
Business hours: Mon.-Fri. 9-5.30 p.m. Closed 1-2 p.m. and Sat.
Please enclose S.A.E. for reply to any correspondence. All prices valid until 3.5.74, budget
alterations excepted.

ENGINEERS

FREE

YOURSELF FOR A
BETTER JOB WITH MORE PAY!

This 76 page
FREE book
shows how!

Do you want promotion, a better job, higher pay? "New Opportunities" shows you how to get them through a low-cost B.I.E.T. home study course. There are no books to buy and you can pay-as-you-learn.

The B.I.E.T. guide to success should be read by every ambitious engineer. Send for this helpful 76 page FREE book now. No obligation and nobody will call on you. It could be the best thing you ever did.

CUT OUT THIS COUPON

CHOOSE A BRAND NEW FUTURE HERE!

Tick or state subject of interest. Post to the address below.

<input type="checkbox"/> Practical Radio & Electronics (Technician) <input type="checkbox"/> Electronic Engineering <input type="checkbox"/> TV Maintenance & Servicing <input type="checkbox"/> General Radio & TV Engineering <input type="checkbox"/> Radio Servicing, Maintenance & Repairs <input type="checkbox"/> City & Guilds Radio, TV Electronics Mechanics	<input type="checkbox"/> Radio Amateurs <input type="checkbox"/> Practical TV <input type="checkbox"/> Colour Television <input type="checkbox"/> Computer Electronics <input type="checkbox"/> C & G LI Radio <input type="checkbox"/> TV Servicing Cert. <input type="checkbox"/> Post Master General <input type="checkbox"/> 1st & 2nd Class Certs. <input type="checkbox"/> C & G Electrical Engineering <input type="checkbox"/> Practise <input type="checkbox"/> C & G LI Installations and Wiring	<input type="checkbox"/> General Electrical Engineering <input type="checkbox"/> Society of Engineers (Electrical Eng.) <input type="checkbox"/> Electrical Installations and Wiring <input type="checkbox"/> C & G Electrical Technicians (Primary) <input type="checkbox"/> C & G Telecommunications
---	--	--

To B.I.E.T. BPW 02 Aldermaston Court, Reading RG7 4PF QK **BPW 02**

NAME (Block Capitals Please)
ADDRESS

Other subjects Age

Accredited by C.A.C.C. Member of A.B.C.C.

BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY

16 CHERRY LANE BRISTOL BS1 3NG THE RADIO SHOP TELEPHONE 0272-421196

TRIACS

1-6AMP PLASTIC T05	5-5AMP ISOLATED TAB	10AMP ISOLATED TAB
NAS0181W 100V -27	NAS0651W 100V -46	NAS1001W 100V -63
NAS0181X 100V -26	NAS0651X 100V -45	NAS1001X 100V -60
NAS0182W 200V -38	NAS0652W 200V -58	NAS1002W 200V -78

TAKE 20

DAVID ANDREWS

No. 59 ELECTRONIC TIMER


A series of simple transistor projects, using not more than twenty components.

THIS is probably one of the simplest possible indicating timers that can be made using electronic principles. It relies on measuring the voltage developed across a capacitor, C1, that is being charged up towards 6V through a resistor, R1. The slope of the charge curve follows an exponential function but over the first half of its charging range the slope is reasonably linear and the circuit operates only on this part of the range.

The application the writer had in mind for the device was as a simple darkroom clock for use with an enlarger, but no doubt many other uses could be found for such an instrument.

Operation

Because silicon transistors are used as a super-alpha pair it is necessary to introduce an offset voltage at the input so that even the smallest charge on C1 will display on the meter. This ensures that there is no "dead band" at the bottom end of the meter's scale. The offset is obtained by using two silicon diodes operating under forward bias conditions, D1 and D2. Any voltage at the positive plate of C1 is displayed at the emitter of Tr2.

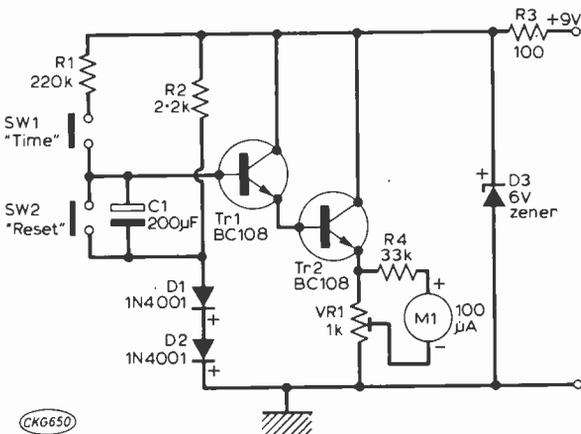


Circuit of the electronic timer using a meter to display the time interval.

Due to the extremely high gain of the two transistors very little current is drawn from the capacitor consequently the state of charge can be displayed for a considerable period, even though timing might have stopped with SW1 being opened. There is thus the possibility of using the device as a simple elapsed time meter. At the end of a timing operation the meter has to be reset to zero and this is done by pressing the reset button, SW2, which shorts out the capacitor momentarily.

★ components list

R1	220kΩ 1/4W	R3	100Ω 1/4W
R2	2.2kΩ 1/4W	R4	33kΩ 1/4W
C1	200μF 12V	D1/2	1N4001
D3	6V 400mW zener	Tr1/2	BC108
M1	Meter 100μA	SW1/2	Push button switches

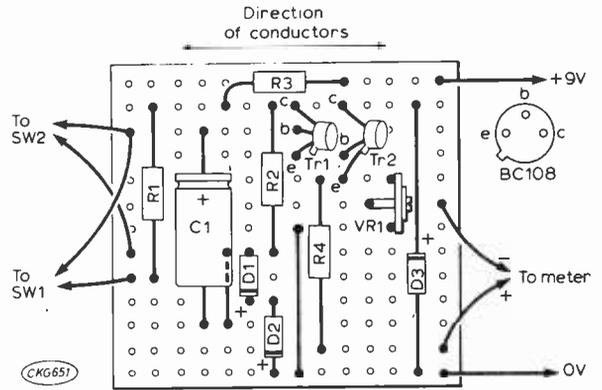

Layout of circuit on Veroboard. No breaks are necessary in the copper rails.

Circuit

With the values of R1 and C1 shown, the timing range for the meter circuit, which actually measures up to 3 volts, is approximately 45 seconds but this can be varied with different values of R1. It is better to calibrate the meter by experiment and VR1 is incorporated to set the maximum reading of the meter to a convenient whole number of seconds, say some multiple of ten, which will make calibration simpler. For best linearity the wiper of VR1 should be kept as near the "earthy" end of the track as possible.


When the capacitor is discharged by SW2 there might still be a small reading on the meter, due to lack of balance in the various offset voltages, but this can be removed by the mechanical "zero set" screw on the meter movement. It is obviously desirable to have a stable power source for the unit so a 6V zener diode is fitted, running from a 9V battery. To save expense the zener and R3 can be omitted and the unit run directly from a 6V lantern battery.

ERRATUM

Zener Diode Tester. Feb 1974

The 150 turn secondary winding of the oscillator transformer should be wound with 36 SWG enamelled wire and not 30SWG as specified on page 977.

CAR CASSETTE AUDIO BOOSTER

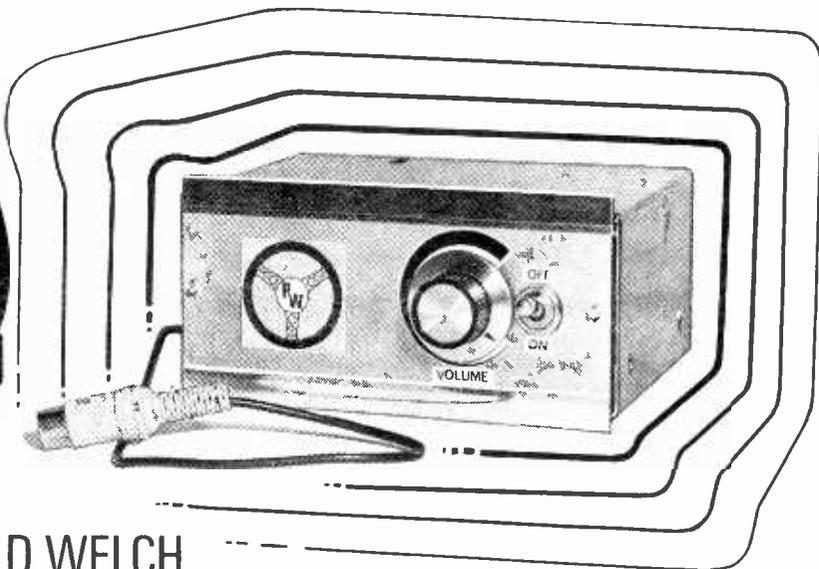

D. WELCH

NORMAL cassette players cannot be used in the car with much success for three main reasons. These are:—

- (1) The output of most portable cassette players is fairly low, in the order of 250-750mW, which is inadequate for car use.
- (2) The internal dry cells, with the player being run at high levels, will rapidly run down.
- (3) The audio quality of most popular players, at high volume, leaves a lot to be desired.

This unit overcomes these disadvantages by enabling the player to be powered from the vehicle's 12V battery as well as boosting the output to a more than adequate level by inclusion of a good quality amplifier.

THE CIRCUIT

Many of the amplifiers designed for car use are of the class 'A' variety as a car battery is quite capable of supplying the 500mA or so quiescent current of a typical 2-3W class 'A' amplifier. However, for low distortion and ample power reserve, it was decided that at least 5W of audio was needed. For a class 'A' type this meant up to 1A quiescent current, which was considered excessive even for a high capacity accumulator. Therefore, a class 'B' type, with much lower quiescent requirements was employed.

The circuit shown in Fig. 1 comprises a conventional four transistor class 'B' amplifier which will deliver 6W RMS into a 3Ω speaker, plus a stabilised supply offering a continuously variable voltage from 0-9V at a maximum current of 350mA. The input to the amplifier, taken from the low-level output of the player, is applied to the base of Tr1, the first audio amplifier. The emitter of Tr1 obtains its bias from the output pair emitters, thus introducing negative feedback, improving quality and frequency response. This stage is directly coupled to Tr2, the driver stage, which is, in turn, directly coupled to the output pair. The emitter of Tr2 is connected straight to the supply line, no emitter resistor being necessary due to the low supply voltage.

The small bias required between the bases of Tr3 and Tr4 to eliminate cross-over distortion is

provided by R7 in parallel with VR3, which sets the output stage quiescent current. The output is coupled to the loudspeaker by C5, large enough to ensure good bass performance. The stabilised power supply, comprising Tr5 and Tr6, provides a 0-9V output, which can be set by adjusting VR2. The zener voltage of D1 appears across VR2 and it can be seen that any voltage between zero and the zener voltage can be tapped off from the slider to the base of Tr5. The small current taken from VR2 is amplified by Tr5 and Tr6, enabling a larger current to be drawn from the emitter of Tr6.

CONSTRUCTION

The circuit excluding the power transistors, is constructed on a printed circuit board measuring 4³/₄ × 3¹/₂in. This is shown in Fig. 2 full size. Lay-out of the components on the board is shown in

★ components list

Resistors

R1	15kΩ	R5	10Ω	R8	150Ω
R2	120kΩ	R6	1.2kΩ	R9	1kΩ
R3	47kΩ	R7	27Ω	R10	33kΩ
R4	2.2kΩ				

All ¼W 10%

VR1 50kΩ log VR2 10kΩ pre-set VR3 50Ω pre-set

Capacitors

C1	4μF 16V	C4	4.7nF polyester
C2	16μF 16V	C5	1000μF 16V
C3	200μF 16V		

Semiconductors

Tr1	BC108	Tr3	AD161	Tr5	BC107
Tr2	BFX88	Tr4	AD162	Tr6	AD161

Miscellaneous

S1, Single pole on-off. Insulating kits (3) for power transistors. Aluminium box 6 x 4 x 5in. Circuit board 4³/₄ x 3¹/₂in. D1, 10V 400mW Zener.


SUPERSOUND 13 HI-FI MONO AMPLIFIER



A superb solid state audio amplifier. Brand new components throughout. 5 silicon transistors plus 2 power output transistors in push-pull. Full wave rectification. Output approx. 13 watts.

r.m.s. into 8 ohms. Frequency response 12Hz - 30KHz \pm 3db. Fully integrated pre-amplifier stage with separate Volume, Bass boost and Treble cut controls. Suitable for 8-15 ohm speakers. Input for ceramic or crystal cartridge. Sensitivity approx. 40mV for full output. Supplied ready built and tested, with knobs, excitation panel, input and output plugs. Overall size 3" high x 6" wide x 7 1/2" deep. AC 200/250V. PRICE £18.00. P. & P. 50p.

DE LUXE STEREO AMPLIFIER

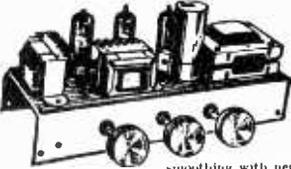

A.C. mains 200-240 v. U. a. i. n. g. heavy duty fully isolated mains transformer with full wave rectifier. Sine wave x 312 deep x 6in. high. Ready built and tested. PRICE £50.00. P. & P. 50p.

something with negligible hum. Valve line up: 2 x ECL86 Triode Pentodes, 1 x E280 as rectifier. Two dual potentiometers are provided for bass and treble control, giving bass and treble boost and cut. A dual volume control is used. Balance of the left and right hand channels can be adjusted by means of a separate 'Balance' control fitted at the rear of the chassis. Input sensitivity is approximately 300mV for full peak output of 4 watts per channel (8 watts mono), into 8 ohm speakers. Full negative feedback in a carefully calculated circuit, allows high volume levels to be used with negligible distortion. Supplied complete with knobs, chassis size 11" w x 4" d. Overall height including valves 6". Ready built & tested to a high standard.

PRICE £10.40. P. & P. 50p.

POWER SUPPLY UNIT 200/240v. A.C. input. Four switched fully smoothed D.C. outputs giving 6v. and 7.5v. and 9v. and 12v. at 1 amp on load. Fitted insulated output terminals and pilot lamp indicator. Hammer finish metal case overall size 6" x 3 1/2" x 2 1/2". Suitable for Transistor Radios, Tape Recorders, Amplifiers etc. etc. Ready built and tested. PRICE £5.00 P. & P. 35p.

FEW ONLY!

High grade mains transformer with grain orientated lamination. Primary 200/240 secondary 18.5 volts at 0.6 amps and 4.6 volts at 0.3 amps. Size 2 1/2" h x 2 1/2" w x 2 1/2" d overall. £1.25 plus 25p P. & P.

BRAND NEW MULTI-RATIO MAINS TRANSFORMERS. Giving 13 alternatives. Primary: 0-10-240v. Secondary combinations 0-5-10-15-20-25-30-35-40-50v. half wave at 1 amp, or 10-0-10, 20-0-20, 30-0-30, at 2 amps full wave. Size 3in. long x 3 1/2in. wide x 3in. deep. Price £2.81 P. & P. 40p.

MAINS TRANSFORMER. For transistor power supplies. Pri. 200/240v. Sec. 9-0-9 at 500 mA. £1.10. P. & P. 25p. Pri. 200/240v. Sec. 12-0-12 at 1 amp. £1.21. P. & P. 25p. Pri. 200/240v. Sec. 10-0-10 at 2 amp. £1.82. P. & P. 35p.

HI-GRADE COPPER LAMINATE BOARDS 8" x 6", Five for 60p plus 30p P. & P.

For personal callers only!

Limited number of stereo radiogram chassis, covering LW/MW/FM bands. Mono radio and stereo gram. Overall size—approx. 16 1/2" W, 6 1/2" H, 8" Depth. 4 watts per channel output. only £18.50.

GENERAL PURPOSE HIGH STABILITY TRANSISTOR PRE-AMPLIFIER

For P.U. Tape, Mike, Guitar, etc. and suitable for use with valve or transistor equipment. 9-18v. battery or from H.T. line 200/300v. Frequency response 15Hz—20KHz. Gain 26dB. Solid encapsulation size 1 1/4" x 1 1/4" x 3". Brand new complete with instructions. Price £1.00. P. & P. 15p.

HANDBOOK OF TRANSISTOR EQUIVALENTS AND SUBSTITUTES

A must for servicemen and home constructors. Including many 1000's of British, U.S.A. European and Japanese transistors. ONLY 40p. Post 5p.

3 Reference Encyclopedias for Electronic Engineers and Designers, covering between them transistor characteristics, diode and transistor equivalents. Many thousands of up to date European types listed.

Diode Equivalents 80p
Transistor Equivalents 90p
Transistor Characteristics £1.15
POST FREE
All three together £2.80

NEW ISSUE

Thyristor, Triac, Diac etc. encyclopedias 95p, Post Free 8 pence 3 way 2 bank low loss Yaxley type switches 1 1/2" sections. Standard spindle. 2 switches 60p + 10p P. & P.

Open 9-5.30 Monday to Friday, 9-5 Saturday

Closed Wednesday.

A few minutes from South Wimbledon Tube Station.

SPECIAL BARGAIN OFFER!
Limited number of BSR C129 Auto Changer De Luxe with lightweight tubular arm and stereo cartridge. Brand new. ONLY £3.00 + p. & 60p.

PRECISION ENGINEERED PLINTHS
Beautifully constructed in heavy gauge "Colorcoat" plastic coated steel. Resonance free. Designed to take Garrard 1025, 2000, 2025, 2500, 2500, 2500, 5100, SP25 II and III, SL65B, AT60 etc. or B.S.L. C109, C129, A21 etc. Black leatherette finish. Size 12 1/2" x 14 1/2" x 3 1/4" high (approx. 7 1/2" high, including right smoked acrylic cover). NOW ONLY £4.95, P. & P. 70p.

LATEST ACOS GP01/138 mono compatible cartridge with T/O stylus for LP/EP/78. Universal mounting bracket. £1.50, P. & P. 15p.

SONOTONE 9TAC COMPATIBLE STEREO CARTRIDGE T/O stylus Diamond Stereo LP and Sapphire 78. ONLY £2.30 P. & P. 10p. Also available fitted with twin Diamond T/O stylus for Stereo LP. £2.80, P. & P. 15p.

LATEST RONETTE T/O STEREO COMPATIBLE CARTRIDGE for EP/LP/78. £1.65 P. & P. 15p.

LATEST RONETTE T/O MONO COMPATIBLE CARTRIDGE for playing EP/LP/78 mono or stereo records on mono equipment. Only £1.50, P. & P. 15p.

QUALITY RECORD PLAYER AMPLIFIER MK. II
A top quality record player amplifier employing heavy duty double wound mains transformer. ECC83, EL84, and rectifier. Separate Bass, Treble and Volume controls. Complete with output transformer matched for 8 ohm speaker. Sine wave 7in wide x 3in deep x 6in. high. Ready built and tested. PRICE £50.00, P. & P. 50p.
ALSO AVAILABLE mounted on board with output transformer and speaker. PRICE £2.30, P. & P. 60p.

SPECIAL OFFER! HI-FI LOUSPEAKER SYSTEMS

Beautifully made teak finish enclosure with most attractive Tygan-Vynair front. Size 16" high x 10 1/2" wide x 6" deep. Fitted with E.M.I. Ceramic Magnet 13" x 8" bass unit, two H.F. tweeter units and crossover. Maximum power handling, 10 watts. Available 3 or 8 or 15 ohms impedance.

OUR PRICE £9.25 Carr. 75p
Cabinet Available Separately £4.95, Carr. 65p.
Also available in 8 ohms with EMI 13" x 8" bass speaker with parastic tweeter £7.15, Carr. 75p.

HARVERSON'S SUPER MONO AMPLIFIER
A super quality grain amplified mono amplifier fully isolated mains transformer, rectifier and ECL82 triode pentode valve as audio amplifier and power output stage. Impedance 3 ohms. Output approx. 3.5 watts. Volume and tone controls. Chassis size only 7in. wide x 3in. deep x 6in. high overall. AC mains 200/240v. Supplied absolutely Brand New completely wired and tested with good quality output transformer. PRICE £3.85 P. & P. 40p BARGAIN PRICE

LOUDSPEAKER BARGAINS
5in. 3 ohm £1.25, P. & P. 15p. 7 x 4in. 3 ohm £1.40, P. & P. 20p. 10 x 6in. 3 or 15 ohm £2.10, P. & P. 30p. E.M.I. 8 x 5in. 3 ohm with high flux magnet £1.70, P. & P. 20p. parastic tweeter 3, 8 or 15 ohm £3.50, P. & P. 30p. E.M.I. 13 x 8in. 3 or 8 or 15 ohm with two inbuilt tweeters and crossover network £4.65, P. & P. 30p. E.M.I. Ceramic magnet heavy duty tweeter. Approx. 3 1/4". Available 3 or 8 or 15 ohms, £1.25 + 20p, P. & P.
BRAND NEW 12in. 15w. H/D Speakers, 3, 8 or 15 ohms. State which. Current production by well-known British maker. Now with Hi-Fi car stereo ceramic magnet assembly £29.90. Guitar models: 25w. £9.90, 35w. £11.00, P. & P. 45p.



SPECIAL OFFER!

LIMITED NUMBER OF BRAND NEW ELAC 16" TWIN CONE LOUSPEAKERS
With large ceramic magnet and plasticised cone surround. 8 ohm impedance. £3.70. P. & P. 35p.

Also available specification as above but size 10" x 6" £2.70 and size 8" round £2.60. P. & P. 35p.


LIMITED NUMBER EMI 2 1/2" 8 ohm Tweeters. Mounted on flat bracket size 2 1/2" wide x 7 1/2" long. Ex equipment but new and tested 70p per pair plus 15p P. & P.

12in. "RA" TWIN CONE LOUSPEAKER. 10 watts peak handling. 3, 8 or 15 ohm £2.75, P. & P. 36p.

"POLY PLANAR" WAFER-TYPE, WIDE RANGE ELECTRO-DYNAMIC SPEAKER
Size 11 1/2" x 14 1/2" x 1 1/2" deep. Weight 19oz. Power handling 20W r.m.s. (40W peak). Impedance 8 ohm only. Response 40Hz-20KHz. Can be mounted on ceilings, walls, doors, under tables, etc., and used with or without baffle. Send S.A.E. for full details. Only 26.55 each. P. & P. 34p.

VYNAIR & REKINE SPEAKERS & CABINET FABRICS app. 54 in. wide. Our price £1.10 yd. length. P. & P. 15p per yd. (min. 1 yd.). S.A.E. for samples.

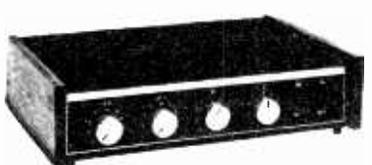HARVERSONIC SUPER SOUND 10 - 10 STEREO AMPLIFIER KIT



NEW FURTHER IMPROVED MODEL WITH HIGHER OUTPUT AND INCORPORATING HIGH QUALITY READY DRILLED PRINTED CIRCUIT BOARD WITH COMPONENT IDENTIFICATION CLEARLY MARKED FOR EVEN EASIER CONSTRUCTION

A really first-class Hi-Fi Stereo Amplifier Kit. Uses 14 transistors including Silicon Transistors in the first five stages on each channel resulting in even lower noise level with improved sensitivity. Integrated pre-amp with Bass, Treble and two Volume Controls. Suitable for use with Ceramic or Crystal cartridges. Very simple to modify to suit magnetic cartridge—instructions included. Output stage for any speakers from 6 to 15 ohms. Compact design, all parts supplied including drilled metal work, high quality ready drilled printed circuit board, smart brushed anodised aluminium front panel with matching knobs, wire, solder, nuts, bolts—no extras to buy. Simple step by step instructions enable any constructor to build an amplifier to be proud of. Brief specification; Power output: 14 watts r.m.s. per channel into 8 ohms. Frequency response \pm 3dB 12-30,000 Hz. Sensitivity: better than 80mV into 1M Ω . Full power bandwidth: \pm 3dB 12-15,000 Hz. Bass boost approx. to \pm 12dB. Treble cut approx. to -16dB. Negative feedback 18dB over main amp. Power requirements 35v. at 1.0 amp. Overall Size 12" w. x 6" d. x 2 1/2" h. Fully detailed 7 page construction manual and parts list free with kit and send 18p plus large S.A.E. **AMPLIFIER KIT £11.55 P. & P. 25p** (Magnetic input components 33p extra) **POWER PACK KIT £3.50 P. & P. 35p** **CABINET £3.50 P. & P. 35p** (Post Free if all units purchased at same time) Full after sales service


Also available ready built and tested £25.10. Post Free. Note: The above amplifier is suitable for feeding two mono sources into inputs (e.g. mike, radio, twin record decks, etc.) and will then provide mixing and fading facilities for medium powered Hi-Fi Discographic use, etc.



3-VALVE AUDIO AMPLIFIER HA34 MK II.

Designed for Hi-Fi reproduction of records. A.C. Mains operation. Ready built on plated heavy gauge metal chassis, size 7 1/2" x 4 1/2" x 4 1/2". Incorporates ECC83, EL84, E280 valves. Heavy duty, double wound mains transformer and output transformer matched for 8 ohm speaker. Separate volume control and now with improved wide range tone controls giving bass and treble lift and cut. Negative feedback line. Output 4 1/2 watts. Front panel can be detached and leads extended for remote mounting of controls. Complete with knobs, valves, etc., wired and tested for only £6.00 P. & P. 45p. **EGE "POUR" AMPLIFIER KIT.** Similar in appearance to HA34 above but employs entirely different and advanced circuitry. Complete set of parts, etc. £5.00. P. & P. 45p.

1014 WATT HI-FI AMPLIFIER KIT

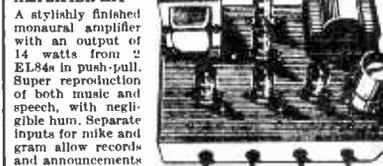

A stylishly finished monaural amplifier with an output of 14 watts from 2 EL84s in push-pull. Super reproduction of both music and speech, with negligible hum. Separate inputs for mike and gram allow records and announcements to follow each other. Fully shrouded section wound output transformer to match 3-15 Ω speaker and 2 independent volume controls, and separate base and treble controls are provided giving good lift and cut. Valve line-up 2 EL84s, ECC83, EP86 and E280 rectifier. Simple instruction booklet 15p + S.A.E. (Free with party). All parts sold separately. ONLY £9.80 P. & P. 60p. Also available ready built and tested £13.00 P. & P. 70p.

HI-FI STEREO HEADPHONES

Adjustable headband with comfortable flexifoam ear-muffs. Wired and fitted with standard stereo jn jack plug. Frequency response 30-15,000Hz. Matching impedance 8-16 ohms. Easily converted for Mono. PRICE £3.30, P. & P. 25p.

PRICES INCLUDE VAT

(Please write clearly)
PLEASE NOTE: P. & P. CHARGES QUOTED APPLY TO U.K. ONLY. P. & P. ON OVERSEAS ORDERS CHARGED EXTRA.

HARVERSON SURPLUS CO. LTD.

(Dept. P.W.) 170 HIGH ST., MERTON, LONDON, S.W.19 Tel.: 01-540 3985

SEND STAMPED ADDRESSED ENVELOPE WITH ALL ENQUIRIES

TO SPARK YOUR IMAGINATION!

Kit comprises **EVERYTHING:**
 Case, cables,
 coil connectors,
 Silicon grease,
 8-page
 instruction
 leaflet.



NEW

the SPARKRITE Mk II

Electronic Ignition Kit only £11.62

Fascinating to build. Fantastic improvement to your car's performance. Complete Capacitive Discharge ignition system, fully proven, components fully guaranteed. Printed circuit design. All metalwork drilled ready. Fitted to car in 15 minutes when built.

- Sustained peak performance. • Up to 20% fuel saving.
- Instant all-weather starting. Faster acceleration, higher top speed.
- Suitable for all engines up to 8 cyls. • Longer spark plug life. • Longer battery life. • Contact breaker burn eliminated. • Purer exhaust gas emission.

A new development from the manufacturers of Gunton ignition. Price: £11.62 inc. V.A.T. and postage. (12 volt only. State Pos. or Neg. earth). Ready built unit also available £14.85 inc. V.A.T. and postage. GUARANTEED 5 YEARS.

ORDER NOW To: ELECTRONICS DESIGN ASSOCIATES,
 82 Bath Street, Walsall WS1 3DE. Phone: 33652

Please send me one SPARKRITE Kit complete. I enclose P.O./Cheque for £11.62. Or for ready built unit £14.85

NAME

ADDRESS

(Live near Walsall? Call in for an actual workshop demo. It really is convincing.)

PW.5

TRAMPUS

MONEY BACK IF NOT SATISFIED

All brand new, full spec. Top grade.
 FREE fabulous NEW catalogue. Send S.A.E.



Red + data, 1/8" pin source LED's 17p. TI 209 and clip 22p
 BIG 1/4" panel clip and RED LED 28p. GREEN and clip 59p.
 INFRA RED LED £1. IC photo amp 44p and amp/switch 85p.

DIGITAL DISPLAY. LEO 1/3" 0-9 DP. DIL. £1.69. Minitor type 0-9 DP DIL £1.19. SOCKETS 13p. Calculator batt/mains from £19.

IC DIGITAL CLOCK CHIPS. Texas etc. with 4 displays £12.6 displays and chip £14. Mostek data and alarm chips with 6 displays £19. pcb £1.49. KIT: All parts and case, National chip. 4 digit £20. 6 x £23. GAS sensor TGS 308 £7. KIT £4.89. Fully built £8.

With data INTEGRATED CIRCUITS 741: 8 pin 29p, to 99 and 14 pin 27p, 748 33p, 709 21p, 710 35p, 723 59p, 555 timer 79p, ZN414 rx. £1-10. 703 rf if 28p, mc 1310 and led £2.76, mc 1339 £1.20, TAD 100 and if £2

1 AMP + REGULATOR 7805, 5 (& 7-20) V. also 12 & 15V £1.49.
 AUDIO AMPS: mfc 4000 50p; 1 and 2W £1.19; 3W £1.29.

74N TTL low prices

Gates 7400, etc. 16p, 7413 32p, 7447 £1.25, 7470/72 32p, 7474/76 39p, 7490 63p, 7492 89p, 74121 49p and all others in cat.
 NEW 16 pin counter/driver 90/47 £2.25. DALO p.c.b. PEN 69p, DIL SOCKETS: Professional/gold P. Pins hi or lo Profile 8, 14, 16 Pin 13p. 2N3055 33p four £1. BC107, BC108, BC109 all 7p each. IN914 3p, ZENERS BZY88 8p, 1A RECTS 50V 34p, 400V 5p, BRIDGE 20p, FETS: 2N3819 19p, 2N3823E 20p, 4416E 25p, BC182/3/4 10p, BC212/3/4 11p, BCY70 13p, BD131/2 35p ea., BFY51/2/3 15p, TIS43 25p, 2N2928 Oy 7p, 2N3055 15p, 2N3702/3/4/5/6/7/8/9/10/11 all 9p ea., 2N3904/6 14p. HEATSINKS 51/TOS, 181/TO18 5p, TO3: 4YL 29p, TV3 14p
 CAPACITORS: 25V 10, 50, 100 of 5p, DISCS 4p, PRESETS 5p, CARBON-PTS 11p. Switch + 11p, Dual 55p. ULTRASONIC TRANSDUCERS £2 ea.
 FLUORESCENT LIGHTS, 8W 13" 12 VOLT £2.59.

Trampus electronics


ADD 10% VAT TO PRICES.
 P. & P. 10p CWO.
 P.O. BOX 29, BRACKNELL, BERKS.

Newest, neatest system ever devised for storing small parts and components: resistors, capacitors, diodes, transistors, etc.

INTER-LOCKING PLASTIC STORAGE DRAWERS

NEAT!
 HANDY!
 TIDY!

DISCOUNT PRICES

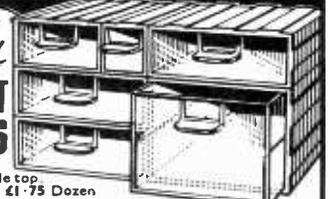

Rigid plastic units, interlock together in vertical and horizontal combinations. Transparent plastic drawers have label slots. Build up any size cabinet for wall, bench or table top
 SINGLE UNITS (5" x 2 1/2" x 2 1/2") £1.75 Dozen
 DOUBLE UNITS £3.00 Dozen
 TREBLE (3D) £2.90 for 8

DOUBLE TREBLE 2 drawers in one outer case (6D2) £4.25
 for 8 EXTRA LARGE SIZE (6D1) £3.90 for 8, Carriage 35p Orders over £10 post free. QUANTITY DISCOUNTS! 5% in £1 for orders over £10, 7 1/2% over £20, 10% over £50. Quotations for large quantities.
 PLEASE ADD 10% VAT TO TOTAL REMITTANCE.

FLAIRLINE (Dept. PW3), 124 CRICKLEWOOD BROADWAY, LONDON N.W.2 01-450 4844

PW Q4 PROJECT

- UNIT "A" (Rs, Cs, S/c's) £1.20
- UNIT "B" (Rs, Cs, S/c's) £3.88
- MULTI-SYSTEM DECODER ADDITIONAL
- ALL THESE PARTS ARE FOR THE SAME Q4 PROJECT
- PARTS (Rs, Cs, Pots, Switch) £4.91
- POWER SUPPLY (R, Cs, S/c's T/former) £2.52
- PRINTED CIRCUIT BOARDS (set of 5) £2.25 (Fibreglass, drilled, tinned)

ADD 10p P & P ADD 10% V.A.T.

S.A.E. for free list of Q4 and other kits and PCB's for P.W. and P.E. Projects, and with all other enquiries.

PHONOSONICS

Dept PW4, 25 KENTISH ROAD, BELVEDERE, KENT, DA17 5BW
 MAIL ORDER ONLY


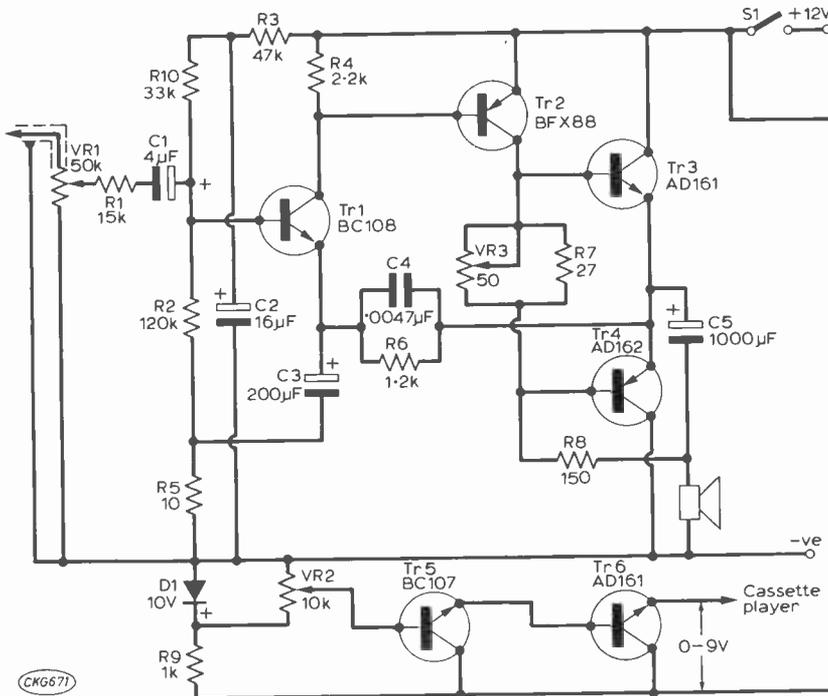


Fig. 1: (left) Circuit of the amplifier and power supply for the cassette recorder.

Fig. 2: (below) Full size layout of the printed circuit board used in the amplifier.

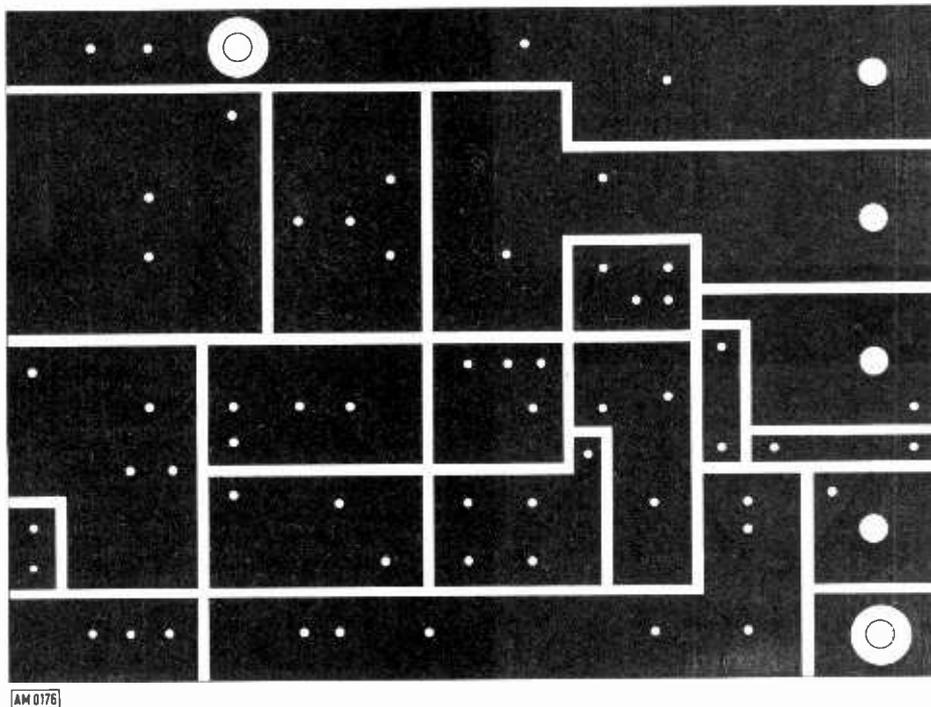

AM 0176

Fig. 3. Rectangular-shaped lands are employed on the board to simplify etching. The board itself is mounted in a $6 \times 4 \times 2\frac{1}{2}$ in. chassis with the power transistors mounted on the rear panel. The leads from the terminals are brought out through holes on the rear of the chassis and taken to their respective plugs.

Tr3, Tr4 and Tr6 must be insulated from the chassis with mica washers. The body of Tr4,

although at negative potential, has to be insulated due to reasons stated later. No heatsink is needed for Tr2 as it is being run well within its power rating.

It should be noted that the common negative line of the circuit is not connected to the unit chassis. This is to enable the unit to be operated in a positive earth vehicle by merely connecting the positive supply line to the vehicle chassis and connecting


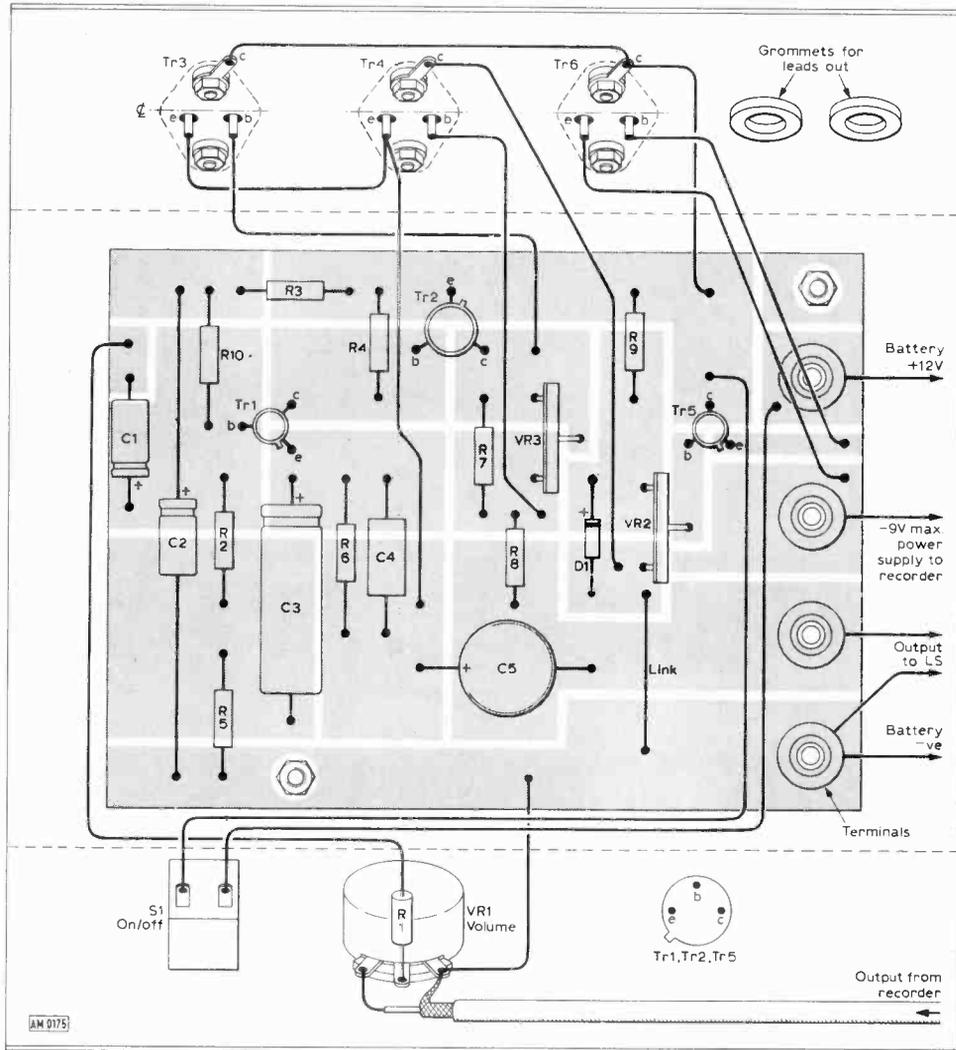


Fig. 3: (above) wiring of PCB to power transistors and volume control.

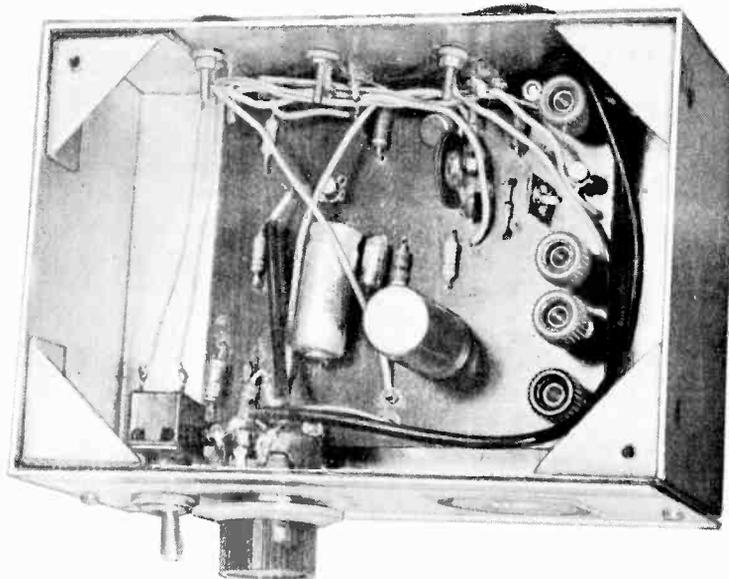

the common negative to the negative terminal of the battery. The chassis of the unit can then be earthed in the normal manner to the vehicle chassis to provide screening. For a negative chassis vehicle the unit's negative terminal is connected to the car chassis and the supply line to battery positive. If this procedure were not adopted, and the negative line directly earthed, then the circuit described here would be satisfactory for a negative earth car, but if employed in a positively earthed vehicle, Tr3 and Tr4 would have to be reversed and Tr1, Tr2, Tr5 and Tr6 replaced by opposite polarity equivalents. Also D1 and the electrolytics would need to be reversed.

TESTING THE AMPLIFIER

Before applying power, VR3 should be adjusted to insert MINIMUM resistance between the bases of Tr3 and Tr4. A loudspeaker is connected between the negative terminal of C5 and the common negative line. The power can now be applied whereupon a small thump should be heard from the speaker. An audio signal is fed into the input and VR3 backed off until any distortion just disappears. Do not rotate VR3 any further than is necessary as this will cause the output pair to take a greater current than is required, causing overheating.

Alternatively, a milliammeter may be inserted in the collector of Tr3, and VR3 adjusted for a reading of 30mA with no signal. The amplifier should give clean, good quality output at high levels.

TESTING THE POWER SUPPLY

A voltmeter is connected between the emitter of Tr6 and the negative line and power applied. On rotation of VR2, voltages of between 0-9V should be obtained, the voltage varying linearly with the rotation of the preset. The output voltage should not vary with the battery voltage fluctuations experienced with a vehicle, or by varying load currents. VR2 can now be set so that the output voltage is the same as that required by the particular player which is going to be used with the unit.

INTERCONNECTIONS

The actual plugs employed to connect the unit to the player depend of course on the make of cassette player employed, a Philips EL3302 being used in the author's installation. Power supply connection to this model is made by a 240° 5-pin DIN plug. On insertion of this plug the internal power source is disconnected. Signal from the recorder/player is also obtained via a 5-pin 180° DIN plug.

Although the input section of the amplifier was designed to handle the output of the Philips unit, it will cope with a wide range of input voltages. If overloading should occur at moderately high settings of the volume control, then R1 can be increased, or, if greater sensitivity is required, reduced.

The unit has been in use for some time in a Land-rover (not the quietest of vehicles!) and the quality is very impressive up to high output levels. An advantage of the unit is the ease with which it can be connected and disconnected, no more than two plugs having to be disconnected to enable the player to be used in its normal way. ■

TELEVISION

IN THE MAY ISSUE

OSCILLOSCOPE CALIBRATOR

The usefulness of an oscilloscope is greatly increased if its calibration can be checked periodically: the equipment described enables you to undertake this operation for yourself. The unit uses a crystal oscillator and i.c. dividers to provide the required outputs.

INTERCARRIER SOUND

The intercarrier sound system gives rise to more reception problems than any other aspect of the 625-line system. The basic principles and the circuits used will be outlined and guidance given on fault conditions.

CRT REJUVENATOR

A design which can be used to give a new lease of life to either monochrome or colour CRTs.

PHILIPS FIELD TIMEBASES

In his next Fault Finding Guide John Law looks at the valve field timebase circuits used from the 152 series up to the 310 chassis, and the faults commonly found.

ASSEMBLING A COLOUR RECEIVER

In the final part of his series David Robinson describes the most tricky part of the exercise, setting up the signal circuits.

PLUS ALL THE REGULAR FEATURES

Details of the May issue are subject to the current national situation at the time of going to press.

TO
(Name of Newsagent)

Please reserve/deliver the MAY issue of TELEVISION (25p) and continue every month until further notice.

NAME

ADDRESS

.....

PRODUCTION LINES

colin riches



Two of the "Josty" Kits.

JOSTY KITS

I recently had the chance of trying out a couple of "Josty" kits. They come complete with all components, printed circuit, construction plans and even solder. The instructions are clear and simple and only an elementary knowledge of soldering is required to build the more simple of the units. All the component positions are marked on the p.c. boards so it is difficult to make a mistake.

Josty is a Danish firm but the sole distributors for Great Britain are Radio Supplies Ltd.

Josty kits available range from a simple diode receiver and a wind-screen wiper control to an automatic light control and an f.m. tuner.

A book called *Amateur Electronics* has been produced by the company to complement the kits. The author, Jan Soelbjerg begins with the basic

theory of electronics and progresses through to more complicated designs and advanced theory.

The book comes with a free printed circuit board for 10 of the Josty designs which are described in the



"Amateur Electronics" and the P.C. board.

text. Complete kits of parts for these and other constructional projects described in the book are available from Josty.

Amateur Electronics is written in a form of 'programmed instruction' and, although some of the translation leaves something to be desired (I've never heard of the word 'og' in English) it's a good instructional volume for both beginner and more experienced constructor alike.

Further details and prices are available from *Radio Supplies (components) Ltd., P.O. Box 27, Hartlepool, TS24 7BR.*

COMING SOON IN P.W.

JUST when you are probably thinking about holidays, we are too! But we are also thinking about the summer issues of *Practical Wireless*—and so should you.

We constantly hear that readers require our summer issues when they are sold out, so let us suggest some very good reasons why you should not only buy a copy every month, but make sure by ordering in advance from your newsagent or by writing to our subscriptions department (see contents page).

TV GAMES

You may have seen those fascinating games in pubs and restaurants where you can play "tennis" electronically with the action displayed on a television screen. Want to know more?

STEREO TUNER

Are you thinking of building an f.m. stereo tuner?

COMMUNICATIONS RECEIVER



Do you want a communications receiver?

For more details on these and other projects, stay tuned to P.W.

YOUR PULL-OUT SUPPLEMENT



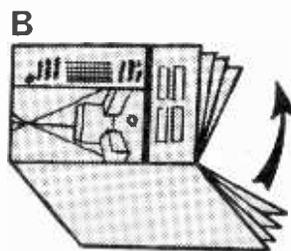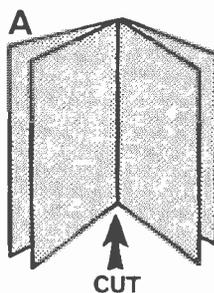- Lift staples at centre page
- Pull out the Supplement
- Cut along centre of pages A
- Put pages together again
- Fold up along dotted line B



FINALE

Having been bitten by the DX bug the pay-off comes when the first confirmation card, or QSL, is received from some DX station. Most stations send such a card on receipt of an accurate report, and this can be the start of a big collection, the initial aim often being 100 countries confirmed. But it will be obvious that some sort of log of stations heard must be kept containing such information as the date, time heard (always in GMT regardless of location of the station concerned or such vagaries as BST), frequency on which station was heard, signal strength, degree of fading, content of programme heard. The SINPO code is fairly widely used when sending reports to broadcast stations, a five figure group conveying a great deal of information, 34454 meaning 'Fair signal strength with slight interference, slight atmospherics but no fading and good overall readability'. The log will be in the form of ruled columns in a notebook but don't forget to add two for QSL's 'in' and 'out'!

What to do with the report? The World Radio and TV Handbook* contains all the information that is required on almost every radio station in the world, together with a mass of relevant information. The

report should be sent air mail together with enough International Reply Coupons to cover return air mail. IRC's can be obtained at Post Offices. There is nothing more calculated to diminish enthusiasm in DX than the months it can take to get a QSL card back if sent surface mail. The station will not be interested in a report that can easily be a month or so old. Air mail is not cheap so choose the stations carefully before sending a report. Don't get too excited at receiving some of the very high powered propaganda stations, even if they are DX. They use fantastic aerial systems to make sure that you do hear them! Look for the ordinary and comparatively low powered stations, they are much more interesting. Initially the Guide to Broadcasting Stations** may be sufficient, containing a listing of stations on the long, medium and short waves, by frequency and wavelength as well as geographical-ly. TV and FM station allocations are also included. Further general information on DX-ing can be found in several monthly magazines.


* Fountain Press (Model & Allied Publications) Station Road, Kings Langley, Herts. £3 post paid.

** Butterworth Ltd., 88 Kingsway, London, WC2B 6AB. 90p post paid.

SINPO REPORTING CODE

Rating Scale	Signal Strength	Interference	Noise	Propagation Disturbance	Overall Readability
5	Excellent	Nil	Nil	Nil	Excellent
4	Good	Slight	Slight	Slight	Good
3	Fair	Moderate	Moderate	Moderate	Fair
2	Poor	Severe	Severe	Severe	Poor
1	Barely audible	Extreme	Extreme	Extreme	Unusable

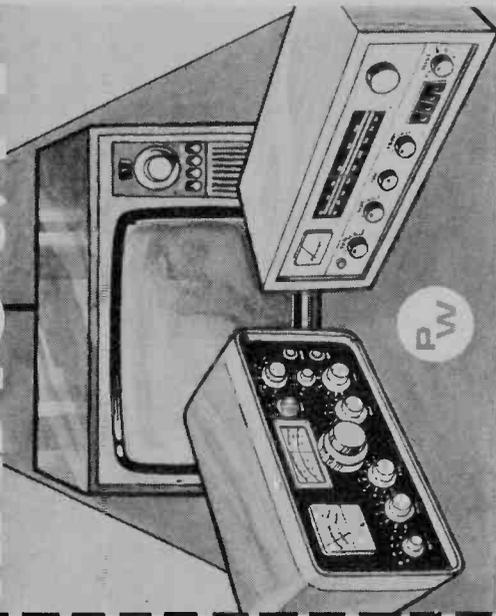GUIDE TO LONG-RANGE RECEPTION OF RADIO & TV



* **SPECIAL PULL-OUT FEATURE**

PRACTICAL WIRELESS
MAY - 1974

CONTENTS:

INTRODUCTION	p 2	SHORT WAVE BANDS	p 7
Long distance reception or DX-ing for the newcomer		Herein lies the main interest of the DX-er	
RADIO WAVES	p 2	TV FROM AFAR	p 12
How those radio signals travel thousands of miles		Don't be restricted to the locals for TV viewing	
MEDIUM WAVE DX-ING	p 5	FM DX	p 15
There are more stations here than just the locals		Europe on the domestic FM receiver, with stereo	
FINALE	p 16		
Logging, reporting and getting that confirmation			

INTRODUCTION

Tuning around the medium wave band on even a simple transistor radio will reveal at least a couple of foreign stations which can usually be identified fairly quickly. If the listening is done at night many more foreign stations will be heard but not all will be identified, by any means. This is the critical point! The options are a return to the noise of Radio 1 or a letter to Practical Wireless asking for help in identification! If the latter we have a new devotee to the art of 'DX' listening and a whole new world of interest will be revealed to the lucky one.

The term 'DX' will be met with frequently and in the early days of wireless it meant the reception of signals over unusually long distances, compared to normal expectations, and generally was unexplainable. The two-way contacts with the moon are the result of a highly sophisticated communication system and can hardly be called DX although it is over a quarter of a million miles away. It would have been surprising if it had not worked! But the DX enthusiast with a home-made receiver and 50 feet of aerial wire can rightly call it DX when he hears a low power station from somewhere in Central America which is only meant to serve some small community over a radius of a few miles.

Something has affected those radio waves and caused them to travel over thousands of miles. Checking again the next evening, just to prove the point, lo! and behold! the station is not there! Something has changed, again. It is this random changing of radio

'conditions' that provides the fascination of DX-ing whether it be enjoyed on the medium, short or very high frequency (VHF) bands. The last we normally associate with high quality FM local stations. Even TV pictures on VHF and the ultra high frequencies (UHF) bands are not beyond the capabilities of the DX-er. Not every day by any means but often enough to make the pursuit of DX TV a very intriguing pastime.

Here we shall describe the means by which the radio signals are propagated over great distances on the different frequency bands and the basic requirements in the way of equipment. Most people already have a receiver suitable for DX-ing on one or more bands, although they may not realise it. The main aerial for the frequencies involved. The aerial is the vital link between the signal and the receiver but nevertheless it seldom gets the attention it deserves, either when being installed or afterwards.

Finding one's way around the various bands is not so very difficult and can be made very much easier with the help of various books and guides that list vital information on frequencies and times of operation of almost every station in the world.

RADIO WAVES

Enveloping the earth are several layers or shells which become electrically conductive when subject to the ionising effect of the sun on the gases in the layers. The two principal layers are called the Heaviside or E layer and the F or Appleton layer, Fig. 1. Each of these layers may split into the E1/E2 and

SOME EUROPEAN TV BANDS

Band Channels	Freq. Range (MHz)
System A	
1	B1 to B5 41.50 to 66.75
3	B6 to B14 176.25 219.75
System B (C in Belgium)	
1	2-3-4 48.25 67.75
3	5 to 12 175.25 229.75
1	A-B-C 53.75 87.75
3	D to H1 175.25 222.75
System D	
1	R1 to R5 49.75 99.75
3	R6 to R12 175.25 229.75
System I	
1	1B 53.75 59.75
3	1D to 1J 175.25 221.25
System G, I, L	
4	21 to 34 470 to 582
5	39 to 68 614 to 854

FM DX

The FM Band 2 runs from 88 to 108MHz but allocations in UK are restricted to 88 to 97MHz, the balance allocated to public services. On the Continent, Channels 2 to 56 occupy 87.6 to 103.8MHz. Although we regard FM as a local service these frequencies can travel a thousand miles or so. Located between the TV bands 1 and 3, these frequencies are subject to the same effects as TV signals, as previously described. The low end of the band will be the first to be affected by unusual propagation so that is where to listen for DX. E-Layer signals around midday in summer will give the longest ranges.

Commercial multi-element aeri- als are eminently suitable for FM DX, the more elements the merrier, within reason. More elements mean

a sharper forward beam so searching for DX around the compass can be tedious. A simple dipole or two element affair is ideal for general searching switching to the main beam as required. Orientation must be the same, simplified by placing both aeri- als on the same mast.

With a domestic FM receiver there are two points to watch when using it for DX-ing. Most sets are fitted with automatic frequency correction (AFC) circuits which alter the local oscillator frequency to compensate for mis-tuning. When DX-ing switch off the AFC, otherwise signals can be chased up and down as the AFC operates. Secondly, some sets are fitted with a control which governs the level at which a signal passes through the receiver. It can be set for local station operation only, and generally is! This adjustment must be set for maximum sensitivity otherwise the DX will never appear. Inter- station noise will be greatly in- creased but the control can be returned to normal for domestic use.

Check the dial calibration against local station frequencies, with the AFC off, of course. If there are large errors fix a strip of white along the dial and recalibrate using a hard pencil. Looking for a partic- ular station on a known frequency will now be much easier.

When the band is 'open' TV sound and vision signals may be heard at the low end of the band, originating from East European stations. Many Continental stations can be heard especially after the BBC has closed down but remember that many openings occur around midday. Some of these stations also transmit stereo so there is no need to switch to mono for DX-ing.

TV SYSTEMS BASIC DATA

	A	B	C	D	G	I	L
Lines	405	625	625	625	625	625	625
Ch. Bandwidth MHz	5	7	8	8	8	8	8
Video B'width MHz	3	5	5	6	5	5	6
Modulation (Video)	+	-	+	-	-	-	+
Modulation (Audio)	AM	FM	AM	FM	FM	FM	AM

An 819 line system (E) is in use in France (VHF)

System	A	B	C	D	G	I	L
A	UK, Eire (VHF)						
B	Austria, W. Germany, Italy, Holland, Norway, Portugal, Spain, Sweden, Switzerland and Yugoslavia (VHF)						
C	Belgium (VHF)						
D	Czechoslovakia, E. Germany, Poland, USSR (VHF)						
G	Austria, W. Germany, Italy, Holland (UHF)						
I	UK, Eire (UHF)						
L	France (UHF), Luxembourg (VHF)						


(see Table of Systems), regardless of whether the signal is on VHF or UHF. This can usually be done by alterations to the switch wafers. Since some of the DX signals may only be present for a short time it is important that the line timebase be capable of very fast synchronisation with the signal. If a choice is available a set with 'flywheel' sync should be chosen, with this end in mind. For maximum flexibility the timebases and IF amplifier will also be separated electrically as well as the detector circuits. This will be found to be easier with some sets than others.

It is likely that a turret tuner will be fitted for VHF so this can be fully utilised by fitting additional coil units for the empty channels. These can be for Band 1, Band 2(TV) and Band 3 depending upon requirements. On UHF the dozens of channels available make the usual four station push-button selector something of a joke to the DX-er! Continuous tuning is a must and

with modern varicap tuners this is a simple business.

In the process of setting up the equipment it is likely that a picture of some sort, that is obviously not BBC or ITV, will be picked up and the identification chase will be on. All TV stations have test and identification cards, usually with station or network names, but because of the common practice of relaying other stations or networks too much credence should not be given to first conclusions.

If a reception report is sent to a distant TV station it should contain plenty of information on the programme content, plus other information seen or heard which will assist the station in confirming the report. The DX-TV-er's 'bible' is *Long Distance Television* by Roger Bunney obtainable from Weston Publishing, 33 Cherville Street, Romsey, Hants SO5 8FB for 55p postpaid. It can be thoroughly recommended to the newcomer to DX TV.

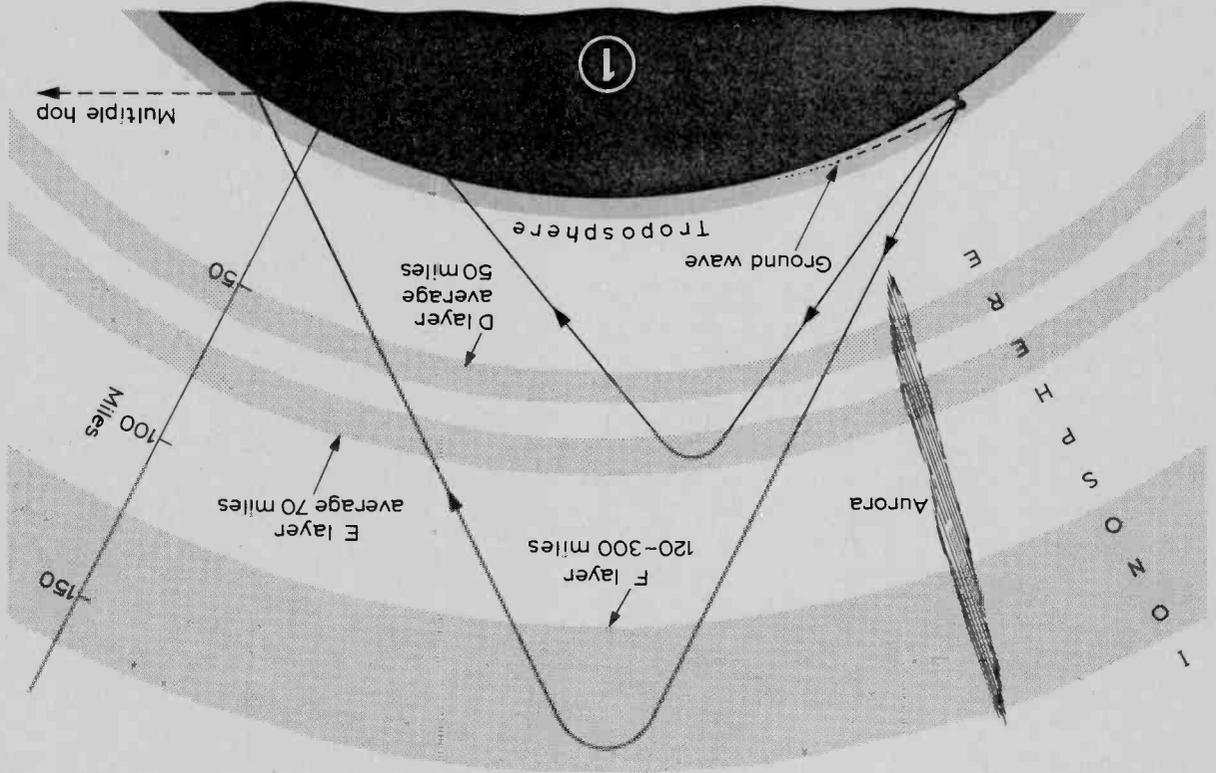

F1/F2 layers with increasing ionisation. Being conductive these layers are capable of reflecting radio waves. The height of the layers will vary with the degree of ionisation and other factors. During the dark hours, in the absence of the sun, the layers become less reflective so that in winter they lose much of their reflecting powers and DX becomes impossible. In the summer, being subject to almost continuous ionisation, they can remain reflective throughout the 24 hours. Severe, relatively short term eruptions on the sun, called sunspots, can cause the complete disruption of all short wave long distance communications.

GROUND WAVE

All transmitters have a ground wave which follows the surface of the earth, dying out very rapidly, Fig. 1, after 20 or 30 miles depending upon the frequency, in the case of short wave stations. The main signal goes upwards before being reflected by, usually, the E layer in the daytime and the F layer at night, but much would depend upon the frequencies involved, time of year and position of the sunspot cycle. The distance between the end of the ground wave and the first point of return of the reflected signal is known as the 'skip distance', no signals being heard in this area from the station concerned.

On the medium waves the ground wave is extended much further and constitutes the normal service area of the transmitter. At night however the skip distance can become nil the sky wave causing severe distortion of the signal due to its interaction with the ground wave. Hence the constant reminder by our local broadcasting stations to change

over to FM for better reception at night!

The degree to which a short wave radio signal penetrates a layer and is then reflected depends upon its frequency. As the frequency increases penetration increases and reflection decreases until a frequency is reached when reflection ceases and the signal is lost. This frequency, in relation to a vertically transmitted signal, is used by radio research laboratories to predict propagation conditions. It will be seen that since the transmitted signal is in reality a diverging signal the way in which it penetrates and is reflected from a layer means that the received signal will consist of several components which may add together or subtract from each other thus producing a signal that will be varying in strength all the time, causing the well-known phenomenon of 'fading'.

Below the E layer is the D layer which exists only during daylight hours when it is mainly responsible for absorbing any upward radiation from medium wave stations. The D layer disappears as soon as the sun's effect on it goes at sunset.

TROPOSPHERE

A very important factor in the propagation of VHF and UHF transmissions over long distances is the troposphere which is that part of our atmosphere up to a height of about five miles. On clear, warm days, usually associated with high pressure areas, the troposphere can carry these frequencies over many hundreds of miles.

The DX modes of transmission appropriate to the various frequency bands will be discussed in subsequent chapters.


is the enormous frequency bandwidth involved, 45 to 850MHz approximately, with the odd gap here and there.

On Band 1 and Band 2(TV) an aerial that has proved very effective uses crossed horizontal dipoles set at 90° to each other, giving all-round coverage, Fig. 9. (*Practical Television July 69*). Remember that as Band 1 TV is rapidly becoming redundant in the UK it is possible to buy quite cheaply new aerial kits which can be used to make up any special arrays Bits and pieces of old used aerials should not be used as these will invariably be corroded. Other wide-band arrays for Band 1 were discussed in *Television May 72*. A useful aerial for sole use in Band 2(TV) is shown in Fig. 10. It can be made of ½" diameter aluminium tube and mounted on a larger size boom.

Aerials for Band 3 do not present any problem as there are a number of suitable wideband arrays on the market which will be hard to beat. At present prices it certainly does not pay to try to make them at home. The UHF bands can be covered by a choice of aerials from the three groups currently available commercially:—

- Channels 21 to 34
- Group A Colour Code Red
- Channels 39 to 53
- Group B Colour Code Yellow
- Channels 48 to 68
- Group C/D Colour Code Green

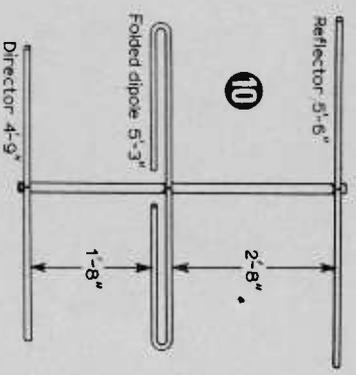These aerials, in various configurations, are available from a number of manufacturers and again it pays to take advantage of the development work that has been done by the makers rather than to use home made aerials of unknown characteristics. Whatever combination of aerials it is decided to use they should all be fitted with the best



quality UHF coaxial feeder, choosing the shortest path back to the TV set. Mount them as high as possible, on an aluminium pole preferably, with a separation of around three feet between aerials. Clamps or simple bearings on the pole will enable it to be rotated quite easily by hand. Mains operated aerial rotators are available complete with remote indicating control boxes thus obviating the need to move at all when changing the beam heading!

Masthead preamplifiers are sometimes considered a bit of a refinement but for the real DX TV-er they are essential if he is to take advantage of very weak signals, especially in tropospheric reception. It is best if the coaxial cable is used to convey the few volts needed to power the amplifier.

In order to be able to receive the various systems being transmitted it will be necessary to make certain alterations to the standard circuitry of the ordinary TV set. For this reason it is advisable to start by buying an old dual standard set for a few pounds and modifying that. The first change is to the video (vision) detector to enable either positive or negative vision modulation signals to be accommodated

TV FROM AFAR

Once again the mechanics of DX signal paths must be investigated, this time for TV signal frequencies. The European TV bands and channel designations are given in the Tables. Band 1 signals can be propagated long distances by means of the reflective E layer but the real TV enthusiast is more interested in 'Sporadic E' (SpE) signals. For reasons that are not too well understood, patches of intense ionisation occur in the E layer, mostly during the summer months. These patches can produce DX signals of great strength but, sometimes, of short duration depending upon the movement of the SpE 'cloud'. As the cloud moves different DX TV stations will be received and then fade out again. Like all DX reception it is the uncertainty of the situation that provides the excitement!


The passage of meteors through the E layer also causes local ionisation which is capable of reflecting Band 1 and 3 TV signals but only for comparatively short periods, often measured in seconds.

As we approach the minimum of the sun's 11 year sunspot cycle the interest in DX reception of TV signals via the upper F layer is minimal but at sunspot peaks Band 1 TV signals, such as BBC1 on 45MHz, have been received as far away as Australia! These periods also produce increased auroral activity at the north (and south) pole which is capable of reflecting VHF TV signals.

The last DX TV mode of propagation to be discussed is perhaps the most predictable. The daily weather charts on domestic TV are closely watched by the DX stalwart who looks for approaching high

pressure areas when clear skies at night allow the earth to give up its heat quickly to the upper atmosphere thus creating an 'inversion' when the surface temperature is lower than that of the air mass above, contrary to normal stable conditions. The TV signal is gradually bent more and more as it passes through the troposphere and it can eventually be returned to earth, perhaps a thousand miles away. VHF and UHF signals are affected by tropics as evidenced by the occasional interference experienced by viewers of the domestic TV services for which BBC and ITV often apologise! 'Ducting' is a form of tropo producing signals only over a well defined path between a particular receiver and transmitter usually to the exclusion of other signals originating along the path.

Now to the equipment required to be able to receive DX TV. Not so complicated or expensive as might at first be imagined. While high gain beam aerials have their advantages quite simple arrays will allow the reception of TV signals from around Europe. The main problem

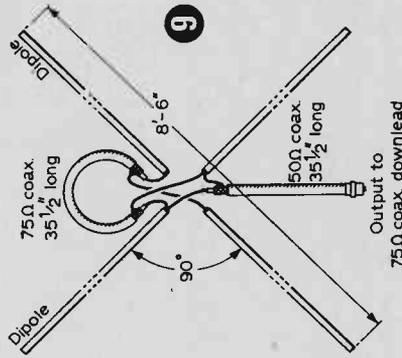

Dipole X-array mounted in horizontal plane

MEDIUM WAVE DX-ING

The medium wave band extends from 525 to 1605kHz or 571 to 187 metres. During daylight hours the service area of a MW transmitter is provided entirely by the ground wave, see Fig. 1, which is gradually attenuated as it travels over the earth's surface. Any signal traveling upwards will be absorbed by the D layer (see Propagation) but around sunset the D layer dissipates and the signal passes through that level and on to the E layer from whence it is reflected back to earth. The E layer at this time is also becoming weaker so the reflections tend to be very variable as the density and height of the layer changes continuously. Interaction between the ground wave and the reflected wave can occur especially with stations at the high frequency end of the MW band and particularly around sunrise and sunset. The result is very bad distortion of the speech or music in parts of the service area.

AT NIGHT


After dark, stations in Europe and North Africa up to a radius of roughly 1300 miles can be heard in the UK via the sky wave propagation. Sometimes the signal may make more than one hop between earth and the E layer producing the real DX which the enthusiast is seeking. The long winter nights produce many signals from the USA and Canada and down into the Caribbean area. Station CJON at St. John's, Newfoundland, can often be heard well before midnight on 930kHz and is a good station for the

newcomer to look for, for encouragement if nothing else! Others include CHER Sydney, Nova Scotia on 950kHz, CFRB Toronto 1010kHz, WABC New York City 770kHz, WOR New York 710kHz and many others. Good catches among the rarer stations include Radio St. Pierre in the St. Pierre and Miquelon Islands on 1375kHz, Bermuda ZBM1 1235kHz and ZFB1 960kHz plus WIV 1970kHz and WBNB on 1000kHz in the US Virgin Islands. Even around Europe there are stations such as Torshaven in the Faroe Islands on 584kHz which represents quite a good catch, together with Hofn in Iceland on 665kHz.

MIDWINTER




The afternoons in midwinter are the time to look for Asiatic stations just before the invasion by the European stations via the E layer. All-India Radio represented by Calcutta on 1130kHz uses no less than 1000kW in power so it should not be too difficult to find. There is Baghdad on 760kHz, Kabul in Afghanistan on 1280kHz and Radio Iraq on 841kHz, not bad DX for the medium waves!

Having whetted the appetite, what sort of equipment is needed to hear this sort of DX? A good domestic receiver with a reasonably large tuning dial and provision for the attachment of an external aerial is about the minimum. The portable transistor radio with its microscopical dial is out but the older vaired receivers had quite good dials in many cases and often an RF stage, which can be a distinct advantage, so these old sets should not be overlooked and after overhaul and re-alignment can give a good account of themselves. Of course, a communication class receiver is

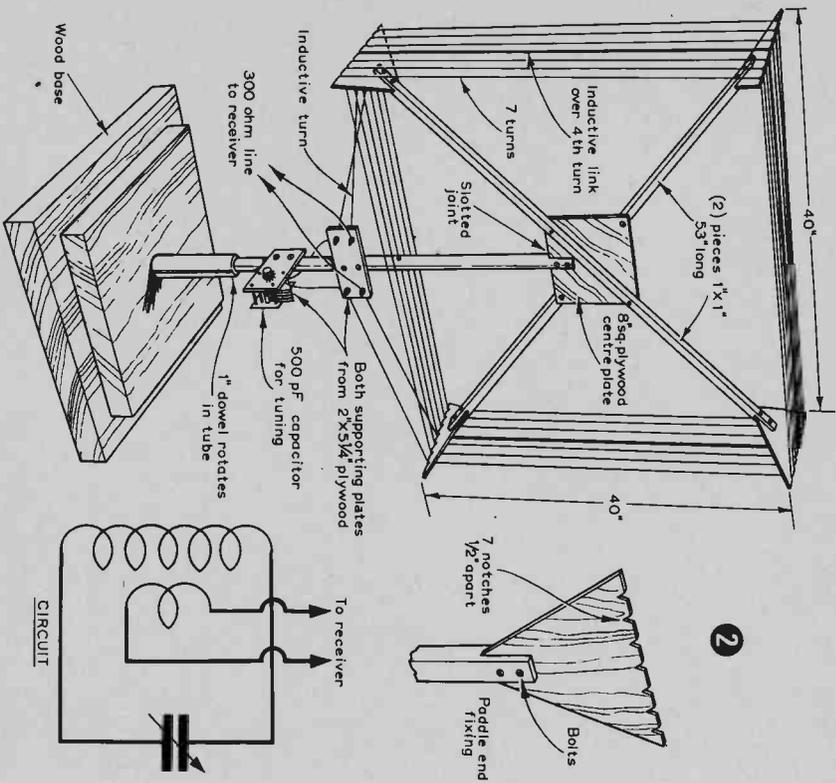

much better mainly because of the increased selectivity and sensitivity it can bring to bear in the chase for the DX. Refer to the section on short wave listening for information on choosing a communication receiver. Ek-Government surplus receivers of the AR88 type are excellent for both medium and short wave DX-ing and generally represent a very good bargain.

The aerial for MW ought to be about 100 to 150 feet long including any down lead. As the length is less than half a wavelength this aerial will not show any particular directive properties. The seasoned DX-er will also possess a loop or frame aerial, Fig. 2, which he can rotate in order to null out an unwanted station and leave the wanted station. Naturally the signal strengths will be down on those obtainable with the outside aerial but it is the ratio of wanted to unwanted signal that really matters. The loop aerial's pick-up pattern is similar to a figure 8 and the loop is rotated so that the line of minimum pick-up is towards the unwanted signal. Maximum dis-

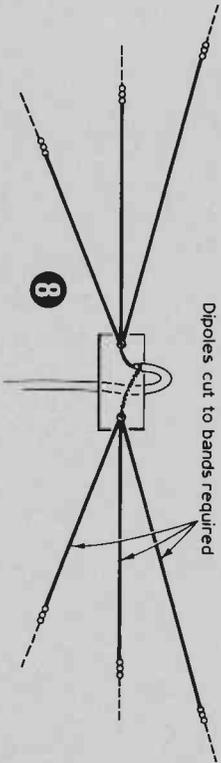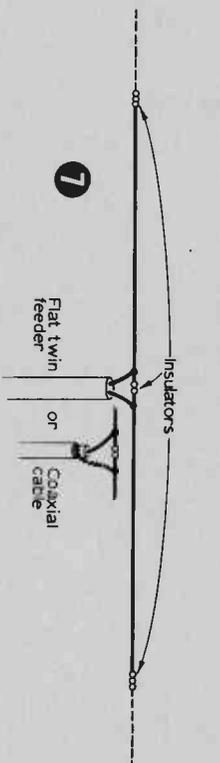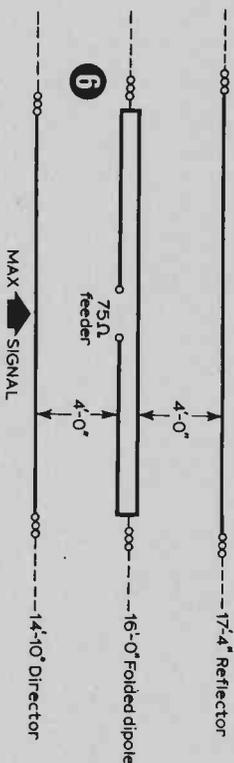

SHORT WAVE DIPOLES		Broadcast		Amateur	
Band	Length	Band	Length	Band	Length
49m	76ft	160m	256ft		
41	65	80	128		
31	48	40	66		
25	39	20	33		
19	30	15	22		
16	26	10	16		
13	21-7in				
11	18-2in				

in from the horizontal wire to the receiver being counted as part of the 132 feet or other half wave chosen. Use good insulators where the wire is supported and avoid sharp bends at all times. There is

nothing magic about 132 feet so it is quite in order to make the aerial as long and as high as is possible in the circumstances, but the ATU is a must whatever length is chosen. In the interests of safety never run an aerial wire over or near any power supply line or telephone wires.

A half wave dipole suitable for a single band only may be constructed as in Fig. 7 from the dimensions given in the Table, but the multi-band dipole of Fig. 8 may be preferable for listening on several bands. The length of the feeder should be kept to a minimum after it has been allowed to drop vertically downwards from the centre for a short way.

station so that it can be easily found again. With a communication type receiver the existing calibration ought to be quite accurate but if a new station's frequency is to be measured the crystal calibrator will provide two marker points 10kHz apart from which the frequency can be estimated to a kHz or so.

SHORT WAVE BANDS

At the outset of his DX-ing career the newcomer to the short wave bands will, understandably, be a little hesitant to spend a lot of money on a receiver, especially if he is not quite sure what he is really looking for. He ought to go for a communication receiver but unfortunately there are a number of so-called 'communication' sets on the market which do not, in fact, meet the accepted specification for this type of equipment. They are only glorified all-band domestic receivers lacking several of the essential features of a proper communication receiver.

Short wave receivers fall into two general categories, those with continuous coverage across all the short wave bands, (see the Tables) including the amateur bands, from about 1.5MHz to 30MHz in a number of switched ranges and those intended for use on the amateur bands only, with the range switch selecting part or whole of a particular band, typically 1.8, 3.5, 7, 14, 21 and 28MHz. The newcomer will be more interested in the broadcast bands so the general coverage receiver is likely to be his first choice.

The following points should be considered when weighing up the


crimination will occur when the lines in the direction of the two transmitters are roughly at 90°. A frame aerial will also be less sensitive to general noise and static.

The receiver should be connected to a good earth point such as a copper rod or tube driven a few feet into the soil, the connection being made with heavy copper wire which should be as short as possible. In the past the lead piping of the domestic cold water system was recommended as an earth but with the widespread use today of plastic piping this can no longer be relied upon unless a check on the electrical continuity can be made.

CALIBRATION


Before DX-ing begins in earnest it is important that the receiver, if of the domestic type, should be calibrated fairly accurately and this may be done by first sticking a strip of white paper or thin card along the length of the dial and marking it at intervals with a hard pencil. Initially the reference points can be taken from broadcast stations, picking those that have a frequency in round numbers such as Budapest 539kHz (540), Lyons 602kHz (600), Brussels 620kHz, Rennes 710kHz, Munich 800kHz, Milan 899kHz (900) and so on. Mark the reference points in kHz from one end of the band to the other. The original dial markings are unlikely to be at all accurate except at a couple of places. Later, if a crystal calibrator is acquired, it will be possible to mark the dial down to 10kHz intervals.

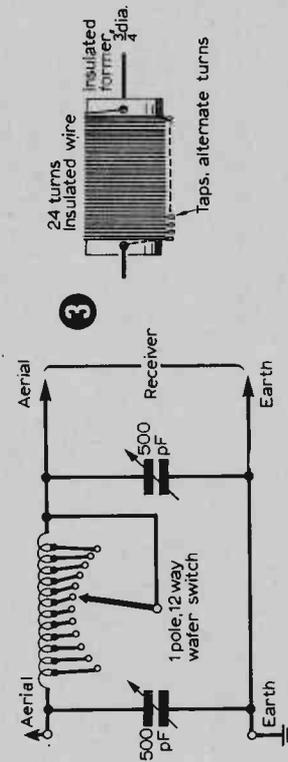The calibration will enable the search for a particular station to be narrowed down to a small part of the dial as well as permitting the recording of the frequency of a new



three, element wire beam, Fig. 6, which is not so impossible as it may seem considering the 'wing-span' is only about 17 feet. However it will tend to be quite directional unless a bi-directional beam is made, which will not be any more difficult.

An outside aerial will be a big improvement on all the short wave bands especially if it can be made about 132 feet long which will be around half wave long on the 80 metre band. Again, an ATU will be highly desirable to take maximum advantage of the aerial. Install the wire as high as possible taking advantage of any trees or buildings to act as supports. The wire may be horizontal or sloping, the final lead-

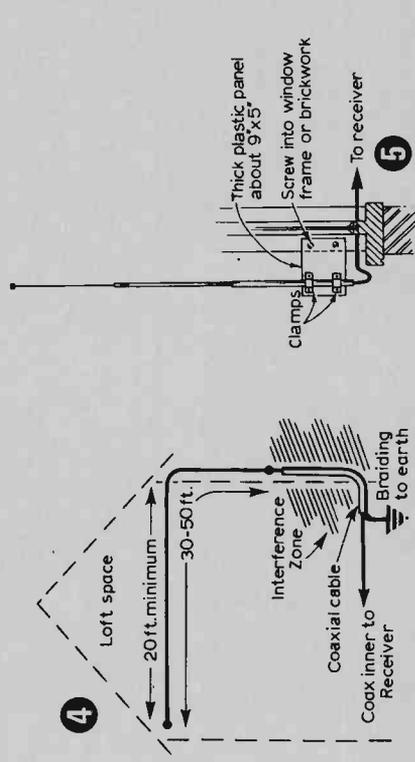

than the desired half wave then the ATU will make up the length electrically and this it can do over all the short wave spectrum, Fig. 3. A loft aerial suitable for use in an electrically noisy location is shown in Fig. 4.

A vertical rod aerial mounted on an insulator can be fitted to an outside window ledge and joined to the receiver via the ATU, Fig. 5, the signal pick-up being approximately the same from all directions. A half wave horizontal wire will have maximum response from stations at right angles to the line of the wire. When conditions favour the 10/11 metre bands during periods of high sunspot activity, thought should be given to erecting a two, or even

pros and cons of a particular short wave set:—

1. **Adequate Bandspread** or the ability to 'stretch' out any part of the frequency range to permit easier tuning. Bandspread is often achieved with a 'band-set' dial which is adjusted to the end of a band, a separate 'bandspread' dial spreading the band over most of its travel. The main dial will be calibrated for each of its switched ranges while the bandspread dial may be calibrated for each band or simply in degrees, for logging purposes. This permits the rapid return to a particular station or frequency. This type of bandspread is invariably a small capacitor in parallel with the main tuning capacitor. Another bandspread system uses a direct mechanical reduction drive on the main tuning capacitor and is to be preferred if it provides sufficient bandspread.

2. **Adequate Frequency Coverage**, including the 11 and 13 metre bands which really come alive during periods of high sunspot activity. The lowest frequency bands, 90 and 120 metres, can be sacrificed if necessary. Broadly speaking, 3-5 to 26MHz is the minimum coverage to aim at.

3. **Provision of a BFO** or beat frequency oscillator, which permits the reception of continuous wave (CW) or Morse code signals, especially useful on the amateur bands. Single sideband (SSB) telephony is widely used on all amateur bands and this can only be resolved if a stable BFO is fitted. SSB transmissions use either upper (USB) or lower (LSB) sideband and the BFO control may be so marked as a guide, and no more, to the correct position for these modes. The BFO may be crystal controlled and switched for USB or LSB. An altern-

SHORT WAVE BROADCAST BANDS
Band (metres) Frequency (MHz)

120	2.300 to 2.495
90	3.200 to 3.400*
75	3.900 to 4.000
60	4.750 to 5.060
49	5.950 to 6.200
41	7.100 to 7.300
31	9.500 to 9.775
25	11.700 to 11.975
19	15.100 to 15.450
16	17.700 to 17.900
13	21.450 to 21.750*
11	25.600 to 26.100*

SHORT WAVE AMATEUR BANDS
Band (metres) Frequency (MHz)

160	1.800 to 2.000
80	3.500 to 4.000*
40	7.000 to 7.300**
20	14.000 to 14.350
15	21.000 to 21.450
10	28.000 to 29.700

* UK 3.500-3.800
** UK 7.000-7.100

ative name for the BFO, the Carrier Insertion Oscillator, is sometimes encountered.

4. **Sensitivity** or ability to resolve weak signals is not likely to be lacking in a decent communication receiver but it is important to check that the sensitivity remains reasonably constant over any one switched range. Disconnect the aerial and turn up the RF gain control for a reasonable background level and tune from one end of a band to the other. The noise level should remain fairly constant but may fall a little at each end.

5. **Selectivity** is, perhaps, the most important characteristic of a

good short wave receiver since it determines its ability to select a wanted signal and exclude those on adjacent channels. For reasonable audio quality a bandwidth at the IF of about 6kHz is required. At the other extreme 500Hz is not too narrow for the reception of CW signals, with 2.5 to 3kHz for SSB transmissions. The ideal is a number of switched bandwidths which is very expensive if separate crystal or mechanical filters are employed although the 6kHz bandwidth can be obtained with tuned circuits alone. If necessary, the very narrow CW filter can be left out, and the required selectivity obtained by a 'Q-Multiplier' which increases the gain of one of the IF stages to the point of oscillation when the stage bandwidth becomes very narrow. The Q-Multiplier, if allowed to oscillate, functions as a BFO in some receivers. Filters are expensive but this is the one point in a receiver where expense is well justified and will never be regretted.

6. **Gain Controls** must include a minimum of an RF gain control and a separate audio volume control. The RF gain control will vary the gain of an RF stage, if fitted, as well as the IF gain. On cheaper receivers it is essential to be able to vary the RF gain independently of the audio level when receiving SSB stations. Every set will have automatic gain control (AGC) circuits but nevertheless the manual control is necessary to cope with the very wide range of signal strengths that will be encountered.

7. **AGC Circuits** are designed to hold the output of the receiver reasonably constant over a wide range of input signal levels, generally due to fading. With broadcast stations the carrier is used and attenuate the AGC but with SSB and

CW there is no continuous carrier and so the resultant audio signal is often used to operate the AGC circuits. This means that there must be a facility for switching off the AGC when receiving SSB or CW or switching to alternative circuitry for these modes. On a good communications receiver this will be done automatically when the function switch is changed from AM to SSB/CW.

8. **Product Detectors** seem to cause more controversy than anything else! When receiving AM signals it is likely that a diode detector will be used and in a cheap receiver it could be used also for SSB/CW. On SSB the ratio of signal to BFO voltage is likely to be wrong and SSB will be difficult to resolve. Hence the comment that the RF gain control must be separate, so that this ratio can be achieved. Look for a product detector on SSB, where the applied signal levels will be correct and the reception of SSB thus made easier.

The aerial is a very important link between the signal and the receiver. The best communication receiver in the world will be reduced to mediocrity with a bad aerial. If restricted to a flat or similar accommodation then 40 or 50 feet of insulated wire round the picture rail may be the best aerial obtainable but its effectiveness can be considerably increased by using an aerial tuning unit (ATU) between the aerial and the receiver. This ensures that the aerial is working at maximum efficiency at all frequencies. The length of a wire for best results ought to be about half a wavelength long, say 65 feet for the 40 metre band. The exact length need not be calculated since reception is being carried out over quite wide bands of frequency. If the wire is shorter


*SPECIAL
FEATURES
for your
SUMMER LEISURE

IN NEXT MONTH'S PRACTICAL WIRELESS

SOUND TO LIGHT CONVERTER

One of the most popular features in any discotheque is the psychedelic multi-colour light display. This unit will handle up to 250 watts of lighting on each of three channels, pulsing in time with the bass, middle and treble notes.

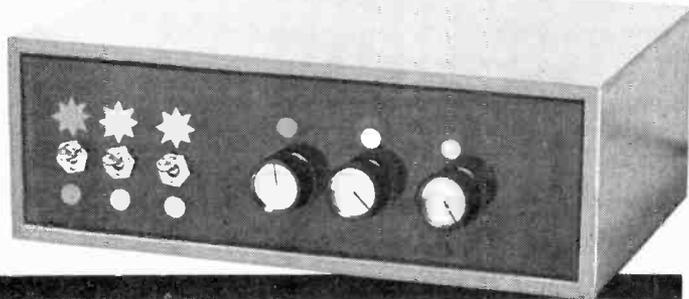By taking advantage of the higher amplifier power which is available in most discos, this constructional project employs simplified circuitry and avoids the use of difficult-to-get specialised components, so often a problem in these days of shortages.



Car Radio Design

Following a brief description of the history of the car radio, general information is given on a practical up-to-the-minute design. Just two IC's are used, simplifying the construction.



In-Car Entertainment

A special feature to guide you through some of the car radios, cassette and cartridge tape players currently on the market.

Supplies of Practical Wireless are limited. Don't be disappointed—order early from your newsagent.

JUNE ISSUE ON SALE IN MAY

The above details are subject to the national industrial situation at the time of going to press.

COMING IN THE JULY ISSUE

TELE-TENNIS

The new popular game you can play on your television screen.
MORE DETAILS NEXT MONTH

EXPERIMENTAL WORKSHOP

M. J. HUGHES M.A.

LEARNING BY PRACTICAL PROJECT STEPS

PART 7—GROUNDED EMITTER AMPLIFIERS

Continued from the April issue

Instead of deriving our bias from the collector of the transistor in question we can, as is shown in Fig. 49, directly couple the collector of the first transistor to the base of an emitter follower. Because the voltage at B follows that at A (apart from the forward voltage drop of Tr2's base emitter junction) there is clearly no difference if we decide to take our bias source as point B. It may not be clear, at this stage, why one should wish to introduce an apparently redundant stage but there is a very good reason. We have deliberately reduced the value of the feedback resistors so that the potential at B is quite a lot below midrail—it should be at about 1 to 1.5V. This is necessary for what is to follow.

We can connect up a microphone exactly as before and introduce a feedback decoupling capacitor as shown in Fig. 51. By measuring the amplified a.c. signal at the emitter of Tr2 you should see a signal comparable to that obtained from the single stage of Fig. 52. This would appear quite natural because we have only introduced an emitter follower. However we can go a step further as shown in Fig. 53. Any current flowing through R2 of the emitter

follower must (in the main) have come from the collector circuit so if we introduce a resistor in the collector circuit of Tr2 we should see voltage swings across it. The value of R3 has to be carefully chosen so that there is sufficient scope for a symmetrical voltage swing about the quiescent voltage of the collector. We can now remove the feedback decoupling capacitor we previously used and substitute a much higher value capacitor between the emitter of Tr2 and ground (C1). At the same time we can drop one of the feedback resistors. This serves two purposes; C1 prevents feedback of signal to the base of Tr1 and allows any a.c. component of current flowing through R1 to pass readily into the base circuit of Tr2. In the absence of a.c. the biasing of the circuit is unaffected. By enhancing the a.c. component of base current into Tr2 we can get quite high voltage swings at its collector; in fact almost

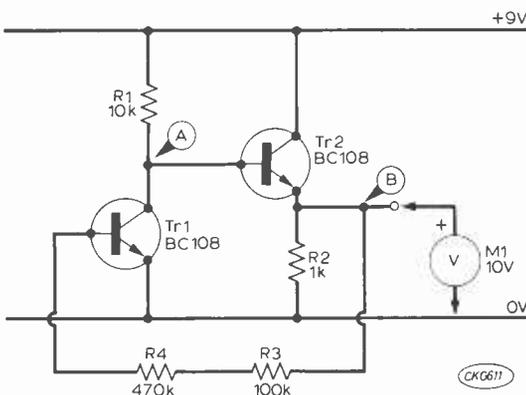


Fig. 49: Bias is derived from the output of the emitter follower.

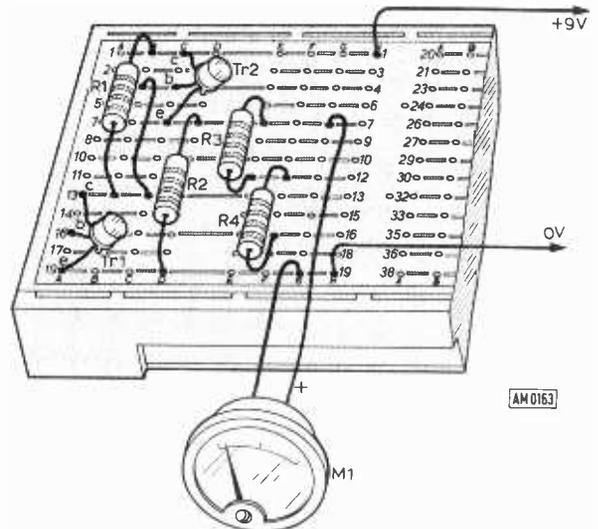


Fig. 50: Component layout for Fig. 49.

identical to those obtained from the previous two stage amplifier (Fig. 47). Notice, however, that there is a considerable saving in components. One advantage of deriving the bias in this way should now be clear.

Just as before, we can add on a current amplifying stage and produce an intercom amplifier having very similar characteristics to those we have already obtained (Fig. 55). It is still necessary to incorporate a degree of frequency correction with C4 across R4. You can experiment with different values to determine what effect C4 will have on the overall performance of the amplifier. Values should be in the range of 2,200pF to 33,000pF (0.033μF). The capacitor in this case is *not* introducing feedback (because all a.c. signals on the bias line have already been removed by C1); it is simply "slugging" the microphone and hence attenuating high frequency signals at source. Because of the high output impedance of the microphone it will have a much more dramatic effect on all frequencies in the spectrum but will reduce the amplitude of higher ones more than lower ones. Negative feedback, of a frequency selective nature, could be provided by a small value capacitor (say 2,200pF) between the collector of Tr2 and its base; try this as an alternative.

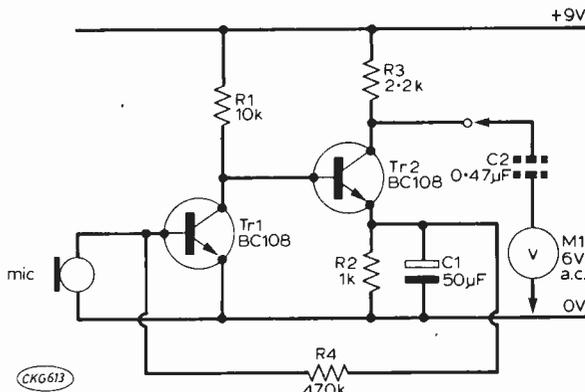


Fig. 53: The voltage gain of this circuit is similar to the first two stages of Fig. 47 but uses fewer components.

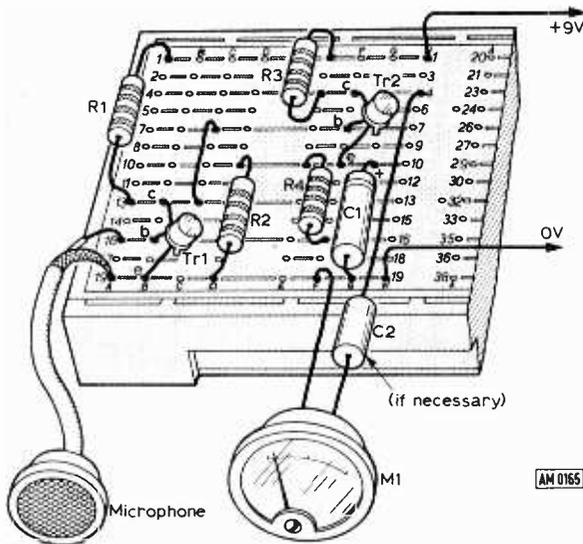


Fig. 54: Component layout for Fig. 53.

Although we have economised on components we still have not improved our degree of control over the voltage gain of the amplifier—it is still controlled by the transistors' parameters.

To produce a circuit that has a voltage gain virtually independent of the transistors' parameters we have to introduce a form of negative feedback. Apart from the frequency selective feedback we have just mentioned there is no other feedback in the circuit of Fig. 55 that controls the signal. There is, of course, feedback associated with the bias stabilisation but we have by-passed this as far as signal is concerned with C1. The simplest way to provide negative feedback that is not frequency selective is to use two extra resistors as in Fig. 57. These are R2 and R8. We have introduced a tendency to making Tr1 an emitter follower so the voltage at point A will follow any signal at the transistors' base.

Say the a.c. signal at the base was to rise in a positive direction the potential at A will also rise to match it—thus trying to keep the base current in its original quiescent state. However, with the value of R2 it cannot track exactly and there is bound to be some variation in base current due to the a.c. signal. The mere addition of R2 reduces the

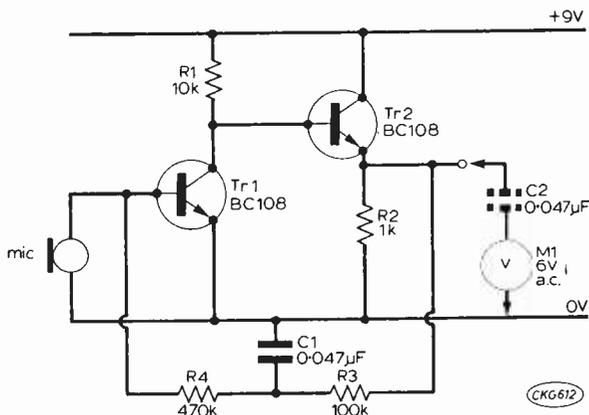


Fig. 51: The signal level at Tr2's emitter is comparable to that produced by the circuit of Fig. 45.

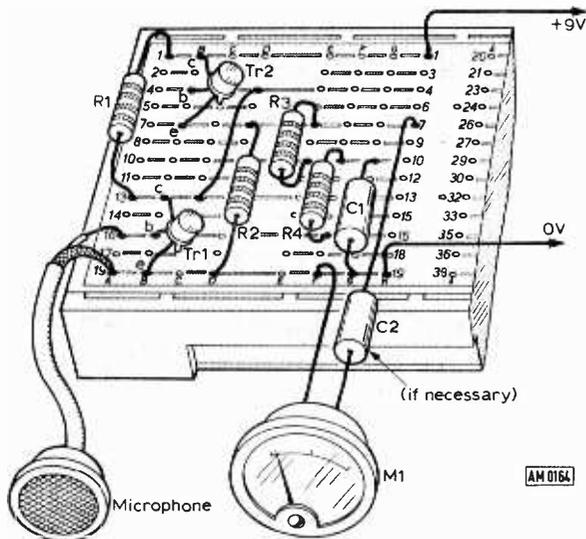


Fig. 52: Component layout for Fig. 51.

gain of the first stage because of this interaction (a form of negative feedback) but the attenuation should not be too great. We can, however, take the considerably amplified—and phase reversed—signal at point B (collector of Tr2) and use this to provide current into the emitter circuit of Tr1 via R8. Because of the phase reversal this current will negate the base current. By adjusting the value for R8 we can inject more or less of this opposing current; the higher the current the more negative feedback we get for our signal and hence the lower the overall gain of the amplifier.

We call the raw gain of the two stage amplifier of Fig. 55 the *open loop* gain because no feedback is applied. Provided the open loop gain is very high there is a simple relationship that controls the voltage gain of the amplifier shown in Fig. 57; the gain is approximately equal to R8 divided by R2. Thus to make a high gain amplifier with no feedback use the circuit of Fig. 55 but to have the refinement of an amplifier having slightly less, but controllable, gain use the feedback circuit of Fig. 57. For example make R8 = 22kΩ and the voltage gain of the circuit is approximately 44; change R8 to 10kΩ and you slightly more than halve its former

gain. As before you can introduce a frequency selective element to compensate for the rising gain with frequency for the crystal microphone by introducing C4 across R8. Start with 2,200pF; the more capacitance you introduce the more you will attenuate the higher frequencies.

If you do not use C4 you can introduce a variable feedback control that will act as a volume control. Substitute a 2·2kΩ fixed resistor and a 100kΩ potentiometer in series for R8.

When making up the circuit of Fig. 57 note that we are now using a super alpha pair to drive the loudspeaker. This is to prevent the quiescent potential at B being influenced by the load of the output stage; this is obviously necessary because we are relying very much on the potentials at point B being what we expect! If wired up on Veroboard this circuit forms a very useful general purpose low power microphone amplifier for intercom or other domestic purposes.

Further thoughts

It is worth pausing a little to compare the simple feedback biased single transistor stage (last month) and the feedback pair. Obviously this month's circuit is somewhat more complex and hence more expensive to build so what are the pros and cons of the two alternatives we have come across so far?

The simple answer is "predictability of the performance". This includes both the overall gain and frequency response. The single stage can have a very high gain and this is set by the h_{FE} of the transistor together with the values of input and output impedance. Whether one is more interested in voltage gain or power gain one can juggle with the component values to give predominantly one or the other within reasonable limits. To some extent the frequency response can be controlled by the introduction of high frequency "roll off" capacitors between the bias feedback resistor chain and ground. So why bother to introduce the complexities of this month?

The problem is that one cannot ever be too certain what the h_{FE} of the transistor is going to be (in this series we are using mainly BC108 devices and in this single type number one can buy devices having gains ranging from 100 to 400). Hence the absolute gain of the single stage amplifier—which is proportional to the transistor's h_{FE} —is going to be pretty undefinable unless one is able to select a device with a precise gain. This is, obviously, not a practical

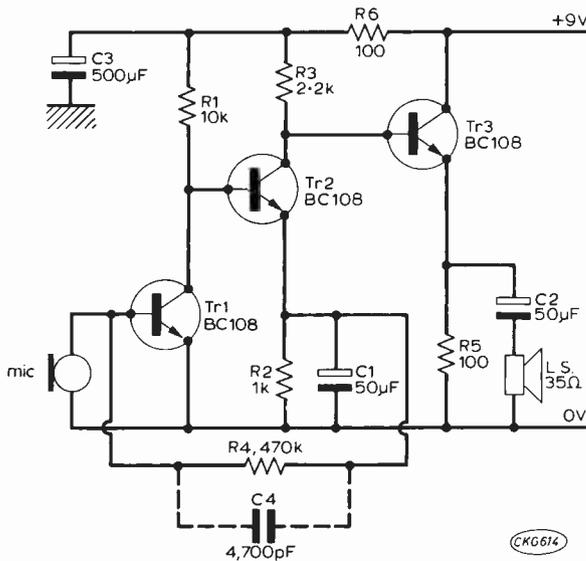


Fig. 55: This circuit has almost identical performance to that of Fig. 47 but is much more economic on components. Its gain, however, is uncontrolled and unpredictable.

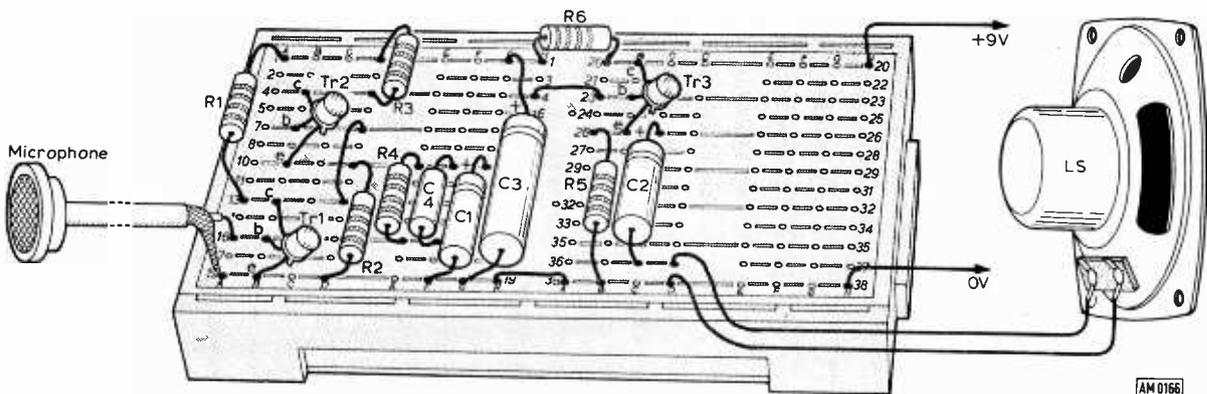


Fig. 56: Component layout for Fig. 55.

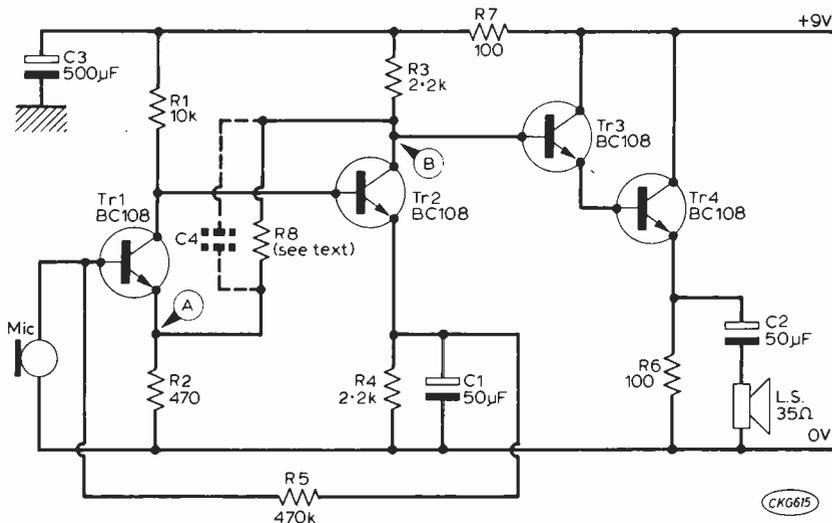


Fig. 57: A refined version of Fig. 55. The gain is set by the ratio of R8 with R2. R4 has a different value to increase the quiescent potential at Tr2's collector and a super alpha pair is used to drive the speaker—reducing the load on Tr2.

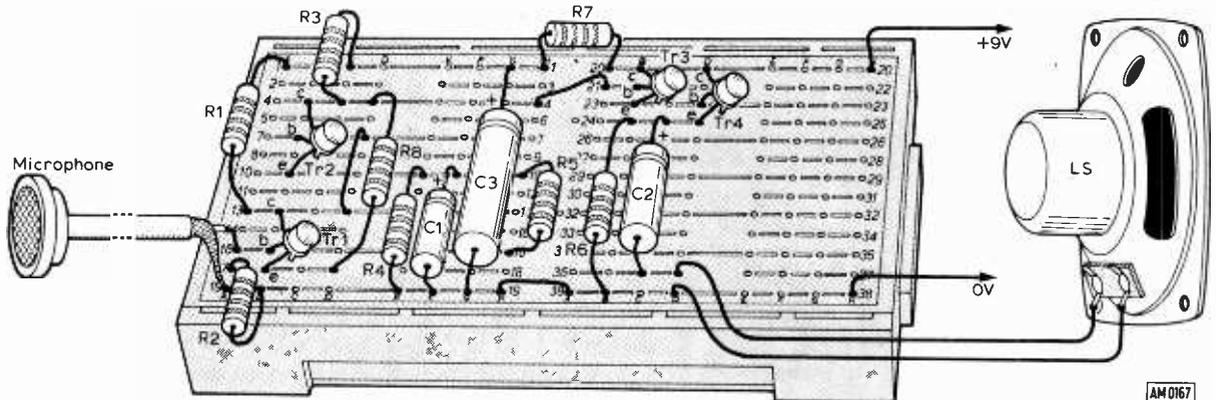


Fig. 58: Component layout for Fig. 57.

proposition. Just try going into a shop asking for a BC108 having a gain of exactly 165 and see the response from over the counter! On second thoughts perhaps you had better not! Having unpredictable gain means that you can never be sure that the circuit is going to be biased exactly mid rail and the result of this might mean that signals of one polarity are clipped by the transistor "bottoming" (going into full conduction) or "topping" (going completely out of conduction). Another effect from the same cause is that some transistors will give a very high output signal for a given input while others will give less. If you are making a preamplifier to go between a pick-up and a power amplifier that needs as input of 100mV for maximum output you can see that there could be problems. Admittedly this can be compensated for, to some extent, by the use of a volume control but one would hardly describe the amplifier as being of good design. Worse than this, though, there is the chance of never getting maximum power out on the one hand or overdriving the output stage of the power amplifier with horrible consequences to the output transistors!

This month's "feedback pair" circuit enables one to set the gain of the amplifier to a precise value—controlled solely by the ratio of feedback resistor to the emitter resistor of Tr1. The controlled gain must,

of course, always be considerably less than the "open loop" gain of the two stage circuit but this is usually no hardship. Thus, if one was using a magnetic cartridge (capacitively coupled to the base of Tr1 through a capacitor having a very low reactance compared with the output impedance of the cartridge) that gives an output voltage of, say 20mV at 1kHz, one could calculate the precise ratios of the feedback resistors to give a predictable output voltage of 100mV. In this case the gain required is 50 so the resistor ratio should be 50 to 1. Notice that we have stipulated the frequency because, of course, the output from a magnetic cartridge increases as frequency

increases (by approximately a factor of 2—or 6dB per octave). This, however, is no problem because we can compensate for this and provide a "flat" output response by introducing a frequency selective component (or components) between the collector of Tr2 and the emitter of Tr1. This would take the form of a simple RC network that increases the amount of negative feedback by 6dB per octave to neutralise the rising response of the cartridge. Obviously care has to be taken in calculating component values—particularly when meeting certain rigid specifications such as the RIAA law—but this is not a major problem. A simple magnetic cartridge preamplifier and equaliser can be made from our basic circuit by replacing R8 with a 150kΩ resistor in series with a 10kΩ resistor and a 0.022µF capacitor across the 150kΩ device with 0.0068µF across the 10kΩ. The 150kΩ resistor goes to Tr2 collector.

A similar technique can be used to compensate for the low frequency losses associated with connecting a crystal cartridge to Tr1. In this case the losses at low frequency are caused by mismatching the high output impedance of the crystal with the medium input impedance of Tr1. The output signal from a

—continued on page 58

4-STATION INTERCOM



£13.95

Solve your communication problems with this 4-Station Transistor Intercom system (1 master and 3 Subs), in robust plastic cabinets for desk or wall mounting. Call/talk/listen from Master to Subs and Subs to Master. Ideally suitable for Business, Surgery, Schools, Hospital, Office and Home. Operates on one 9V battery. On/off switch. Volume control. Complete with 3 connecting wires each 66ft. and other accessories. P. & P. 47p

MAINS INTERCOM NEW MODEL

No batteries—no wires. Just plug in the mains for instant two-way, loud and clear communication. On off switch and volume control. Price £22.95 per pair P. & P. 60p

INTERCOM/BABY ALARM



OUR PRICE ONLY **£6.50**

Same as 4-Station Intercom for two-way instant communication. Ideal as Baby Alarm and Door Phone. Complete with 66ft. connecting wire and Battery. P. & P. 35p



£4.95

Why not boost business efficiency with this incredible De-luxe Telephone Amplifier. Take down long telephone messages or converse without holding the handset. A useful office aid. On/off switch. Volume Control. Complete with Battery. P. & P. 27p. Full price refunded if not satisfied in 7 days.

WEST LONDON DIRECT SUPPLIES (PW.12)
169 KENSINGTON HIGH STREET, LONDON, W.8.

RECHARGEABLE

Mallory Cells in U2, U11 and Penlite U7 sizes, **KESTREL BATTERY CHARGING UNIT . . .**



Use for

Tape recorders, Portable radio and TV, Radio controlled model aircraft and boats, Cine cameras, Flashguns, Cordless shavers and other battery appliances.

Whenever you *must* have utterly dependable battery power—then these new **Alkaline-Manganese** rechargeable cells will provide it. The cells can be recharged many times, a simple job with the **Kestrel Charging Unit** which has been specially designed for these new type batteries.

PRICES
Batteries U2 equiv. £1.92 tax paid

Penlite U equiv. 6tp tax paid

U11 equiv. £1.24 tax paid

Charging unit £8.72 tax paid with one battery holder

ALL PRICES INCLUDE V.A.T.



Send to:
**275 WEST END LANE
LONDON, N.W.6 1QS
01-794 9611**

MAINS UNITS for all types of TRANSISTOR EQUIPMENT

RUN YOUR TAPE RECORDER OFF AC MAINS

Mains unit supplied complete and ready to plug into your cassette-recorder. (State voltage, make and type of plug required. If in doubt send diagram of recorder socket).



ONLY **£2.75** P & P 20p

PLUS-3 MAINS UNIT

Provides three separate switched output voltages 6v., 7½v. and 9v. DC. Attractive case mains lead output socket, plug and lead. Size 4½ x 3½ x 2½in.



ONLY **£3.30**
P & P 20p

Extra lead with plug to fit your cassette recorder 50p. (State model and plug required.)



MAINS UNIT FOR TRANSISTOR RADIO ONLY

For single outputs, 6v, 9v £2.20
For two separate outputs, 6v + 6v., 9v + 9v, £2.75 P. & P. 20p per unit. (Please state outputs required.)

All units are completely isolated from mains by double wound transformer ensuring 100% safety.

ALL PRICES INC VAT

R.C.S. PRODUCTS (RADIO) LTD.
(Dept. P.W.)
36 Raymond Ave., South Woodford
London, E18 2HG

The Pictorial Method



BASIC ELECTRICITY (5 vols) ELECTRONICS (6 vols) TELEVISION (3 vols)

You'll find it easy to learn with this outstandingly successful PICTORIAL METHOD. The essential facts are explained in the simplest language, one at a time, and each is illustrated by an accurate cartoon-type drawing. These clear and concise illustrations make study a real pleasure. The books are based on the latest research into simplified learning techniques. This easy-approach-to-learning method has proved beyond doubt that acquiring knowledge can be an enjoyable experience.

The series will be of exceptional value in training mechanics and technicians in Electricity, Radio and Electronics.

WHAT READERS SAY

I am amazed at the ease a layman can understand these books.

G. P. Bexhill

At such a low cost they are a magnificent set of books.

W. I. Ladywell

My sincere congratulations on describing everything so simply.

J. B. Reiford

I have received both enlightenment and pleasure from reading your manuals.

V. S. Huddersfield

YOUR 100% GUARANTEE

Should you be, in any way dissatisfied with the MANUALS your money will be refunded by return of post.

To The SELRAY BOOK CO., 60 HAYES HILL, HAYES, BROMLEY, KENT. BR2 7HP

Please find enclosed P.O./Cheque value £.....

BASIC ELECTRICITY 5 parts £5.30

BASIC ELECTRONICS 6 parts £6.40

BASIC TELEVISION 3 parts £3.60

Tick Set(s) required.

Prices include Postage and Packing.

YOUR 100% GUARANTEE. If after 10 days examination you decide to return the Manuals your money will be refunded in full.

NAME
BLOCK LETTERS
FULL POSTAL.....
ADDRESS

POST NOW FOR THIS OFFER!

Henry's

**DON'T RELY ON YOUR MEMORY
BUY NOW AT BARGAIN PRICES**
*Hi Fi and Transistors - Up to date
Brochures on request*

**HENRY'S
CATALOGUE**
Due to rapid price changes,
shortages of paper and raw
materials, all prices in the
existing catalogues no longer
apply. Call or phone for latest
prices. A new catalogue will
be available for Aug/Sept. 1974.



**UK's
LARGEST RANGE
OF KITS &
GADGETS**

TEST EQUIPMENT

MULTIMETERS

(carr. etc. 30p)

ITI-2	20K/Volt Slimline	5.95
TLH33D	2K/Volt Robust	7.50
U437	10K/Volt Steel case. AC up to 40 KHz	4.95
U4324	20K/Volt with AC current ranges	8.00
U4105	(Case £1.90) 50K/Volt	11.95
U4313	20K/Volt AC current. Steel case	10.50
U4341	Plus Built In transistor tester	10.50
Model 500	(Case £1.95), 30K/Volt	9.95



OTHER EQUIPMENT

SE250B	Pocket Signal Injector	2.10 carr. 15p
SE500	Pocket Signal Tracer	1.70 carr. 15p
TE15	Grid Dip meter 440kHz-280mHz	15.00 carr. 30p
TE40	AC Millivoltmeter 1-2mHz	19.75 carr. 30p
TE65	28 Range valve voltmeter	22.50 carr. 40p
TE220	120kHz-500mHz RF Generator	18.95 carr. 40p
TE22D	20Hz-200kHz Audio Generator	19.95 carr. 40p
SE350A	Deluxe Signal Tracer	12.50 carr. 20p
SE400	Volts/ohms/R-C sub./RF field/R.F. gen.	14.75 carr. 20p

New Revolutionary Supertester 680R

680R Multi-tester	Accessories	
£18.50	Transistor tester	11.00
	Electronic voltmeter	18.00
	Amplclamp	11.95
	Temperature probe	11.95
	Guass meter	11.95
	Signal Injector	5.95
	Phase Sequence	5.95
	EHT Probe	5.95
	Shunts 25/50/100A	4.50

A SELECTION OF INTERESTING ITEMS

C3025	Compact transistor tester	6.95 p & p 15p
Q4002	Photoelectric System	£13.70
E1310	Stereo mag. cart. preamp.	4.80 p & p 25p
Easiphone	D1201 telephone amplifier	7.50 p & p 25p
D1203	Tealemp. with PU coil	4.95 p & p 20p
LL1	Door Intercom. and chime	8.40 p & p 25p
1 Kw Dimmer/contoller		3.00 p & p 10p
9" Twin spring unit	For	3.30 p & p 15p
16" Twin spring unit	Reverbs	6.85 p & p 25p
US50	Ultrasonic Switch Transmitter/Receiver	£12.75
C3041	1-250 MHz	£4.25
C3043	5CH 1-300 MHz	£5.75
VHF 105	Aircraft Band Converter	4.50 p & p 15p
B2005	4 Ch. mic. mixer	4.20 p & p 15p
B2004	2 ch. Stereo mixer	6.75 p & p 15p
PK3	Kit. Etch your own printed circuits	£1.95 p & p 20p

BUILD THIS RADIO

Portable MW / LW radio kit using Mullard RF/IF module. Features MW - bandspread for extra selectivity. Slow motion tuning. Fibre glass PVC cabinet. 600mW output. All parts £7.98 (Special 22p), carr. etc. 32p.



EXCLUSIVE: SPECIAL OFFERS

MW/LW CAR RADIO	Rotel RA310 15+15 watt + or - Earth with speaker Stereo Amplifier (List and fixings. £6.50 carr./£52.00) £34.52.
Pods & fixings.	£12.50 Stereo cassette recorder. carr./pack. 40p. £59.95 carr./pack. 50p.
Portable Battery Cassette Pair Akai ADM microphones.	£6.95 carr./pack. Car Lighter Plug and adaptor 20p.
for all cassette and radio PORTABLE CASSETTE 671/9 volt output (state TAPE PLAYER—width) £1.95 each	for car or carry around. £7.25
Model Stereophones	
RH630	£4.50 HANIMAX BC808 POCKET
RH700	£6.75 CALCULATOR WITH
RH430	£3.30 % KEY. £28.95 (continued)

SPECIAL PURCHASES

HANIMAX BC811M MEMORY VERSION £37.50
MAINS UNIT for BC808, BC811M £2.85 (state model)

HANIMAX H101 STEREO COMPACT RECORD PLAYER 2 x 7 watts. Complete with Speakers (List £54.50) Price £39.95. Plus free pair of stereo phones.

UHF TV TUNERS

CHANNELS 21 TO 64
8 watt transistorised geared tuners for 825 Line Receiver IF output. £2.50, Post 20p.



EASY TO BUILD KITS BY AMTRON—EVERYTHING SUPPLIED

Model No.		
31D	Radio control receiver	2.98
300	4-channel R/C transmitter	5.95
345	Superhet R/C receiver	5.95
455	AM signal generator	12.33
65	Simple transistor tester	1.40
115	8 watt Amplifier	3.90
120	12 watt amplifier	4.70
125	Stereo control unit	5.70
130	Mono control unit	3.60
605	Power supply for 115	4.55
610	Power supply for 120	4.55
615	Power supply for 2 x 120	5.73
230	AM/FM aerial amplifier	2.93
240	Auto parking light	5.90
275	Mic. preamplifier	6.08
570	LF generator 10Hz-1mHz	15.80
575	Sq. wave generator 20Hz-20KHz	14.60
590	SWR meter	12.85
629	Ni-CAD Charger 1-2-12v	8.00
639	STAB Power supply 6-12v 0-25-0-1A	8.15
699	DC motor speed	2.87
700	Electronic Chaffinch	7.00
705	Windscreen wiper timer	6.80
760	Acoustic switch	10.75
780	Metal Detector (electronics only)	9.65
790	Capacitive Burglar alarm	6.85
835	Guitar preamp.	4.25
840	Delay or alarm	6.15
875	CAP. Discharge ignition for car engine (-Ve Earth)	13.15
80	Scope Calibrator	2.25
255	Level indicator	6.15
525	120-160mHz VHF timer	11.30
715	Photo cell switch	4.30
795	Electronic continuity tester	7.70
860	Photo timer	13.25
871	Slide projector auto feed control	7.15
235	Acoustic Alarm for driver	7.60
465	Quartz XTAL checker	8.75
220	Signal Injector	2.30
390	VOX	15.50
432	Testakit	19.30
670	Buffer Battery Charger	6.55
885	Capacitive Contact Alarm	6.25
850	Electronic Keyer	18.75
820	Electronic Digital Clock	58.50



ALL KITS OFFERED
SUBJECT TO
STOCK
AVAILABILITY
Prices correct at
time of preparation.
Subject to change
without notice.

BUILD THIS TUNER

MW/LW Radio Tuner to use with any amplifier. Features Mullard RF/IF module Ferrite aerial, built in battery. Excellent results. Size 7" x 2 1/2" x 3 1/2". All parts £4.85, carr. 15p.

MULTI-USE & RADIONIC KITS

10-1	10 Projects	3.60
50-1	10 Projects	8.00
150-1	150 Projects	13.20
Telephone Communicator		7.20
X20	20 (Elec.)	4.95
X40	40 (radio)	9.45

All transistor circuits with hand books

TBA800 5 WATT I.C.

Suitable alternative to SL403D.
5/30 volt operated. 8/16 ohm 5 watt output.
With circuits and data £1.50.



STROBE TUBE

ZFT4A. Suitable for December '73 Pract. Electronics £3.00.



ST2 (D32) DIAC 25p

CRS1/40 SCR 45p.

ZFT4 £3.00
ZFT8 £3.50
ZFT12 £4.50



UK'S LARGEST RANGE OF TRANSISTORS AND DEVICES

JUST A SELECTION

*TBA800 5 Watt IC	£1.50
*Sinclair ICR 6 Watt IC	£1.80
*ZN414C Radio	£1.20
*Ultrasonic Transducers	£5.90 pr.
*3015F T5EG Indicator	£1.70
TIL 209 LED	24p each. 22p each per 10

OVER 1500 DIFFERENT SEMI-CONDUCTOR DEVICES IN STOCK

Free stock list—latest edition (Ref. 36) on request. Includes radio valves, I.C.'s Rectifiers, Triacs, SCR's, LED's, etc. More types—better prices—discounts for quantity small or large.

GARRARD BATTERY TAPE DECK



GARRARD 2 speed 9 volt tape decks. Fitted record 1 play and oscillator/Eraser heads. Wind and rewind controls. Takes up to 4" spools. Brand new complete with head circuits. £9.50 carr. 30p.

TOP QUALITY SLIDER CONTROLS

60mm stroke high quality controls complete with knobs (post, etc. 15p any quantity).

Singles Log and Lin 5K, 10K, 22K, 50K, 100K, 250K, 500K, 1 Meg. 45p each.

Ganged Log and Lin 10K, 22K, 50K, 100K, 250K, 65p each. (Quantity discounts available)

SINCLAIR, MINIATURE AMPLIFIERS & TUNER/DECODER

4-300, 0-3 watt 9 volt	1-75	SAC14, 7+7 watt Stereo with controls	11-75
104, 3 watt 9 volt	3-10	SAC13, 15+15 watt Stereo with controls	14-95
304, 3 watt 12 volt	3-95		
555, 3 watt 12 volt	4-10		
E1208, 5 watt 12 volt	5-10		
608, 10 watt 24 volt	4-95		
410, 10 watt 28 volt	4-95		
E1206, 30 watt 45 volt	9-95		
E1210, 2 1/2+2 1/2 watts	12-volt		7-75
RE500, 5 watt IC mains operated Amplifier with controls	6-30		

POWER SUPPLIES FOR EVERY PURPOSE

(All cased unless stated chassis)
470C 671/9 volt 300 mA (includes Multi-Adaptor for Tape Recorders, etc.)
Car Lighter Voltage Adaptors 300mA 2-15 post 20p
6v, 7.5v, 9v 1-95 ea. post 25p
SC202 3/6/7/9 volt 400mA
HC244R Stabilised version 3-65 carr. 30p
P500 9 volt 500mA 4-90 carr. 30p
P11 20 watt 1.500mA (chassis) 3-20 post 20p
P15 26/28 volt 1 amp (chassis) 2-90 post 20p
P1080 12v 1 amp (chassis) 4-50 post 20p
P1081 45v 0.9 amp (chassis) 7-50 post 20p
P12 43-12 volt 0.4-1 amp 7-15 post 30p
SE101A 3/6/9/12 volt 1 amp (Stab.) 12-90 post 25p
RP164 671/9/12 1 amp (Stab.) 12-95 post 30p

FIBRE OPTICS

0.01 Diam. Mono Filament £3.00 per 50 metre reel 0.13 Diam. 64 Fibres Sheathed, £1.00 per metre. SPRAYS 15mm Diam. (Mares Tail Spray £10.50 7mm. Diam. £5.00)



All types offered subject to availability. Prices correct at time of press E & OE. 10% VAT TO BE ADDED TO ALL ORDERS. UK post etc. 15p per order unless stated.

Henry's RADIO LIMITED
EDGWARE ROAD, LONDON W2


404-408 Electronic Components and Equipment 01-402 8391
309 Pa - Disco - Lighting High Power Sound 01-723 6963
303 Bargains Store (Callers only)
Home and Car Entertainment Centres, London and branches now open.
120 Shaftesbury Avenue, London W1 01-437 9692
104 Burnt Oak Broadway, Burnt Oak, Edgware 01-852 7402
190-194 Station Road, Harrow, Middlesex 01-663 7788/9
354-358 Edgware Road, London W2 01-402 5854/4736

All mail to 303 Edgware Road, London W2 1BW
All stores open 9 am to 6 pm six days a week
Hi-Fi - Tape Equipment
Discount Stock List
Free at all stores

the "MINI-POP"

POCKET Medium Wave RECEIVER

F.G. RAYER G30GR

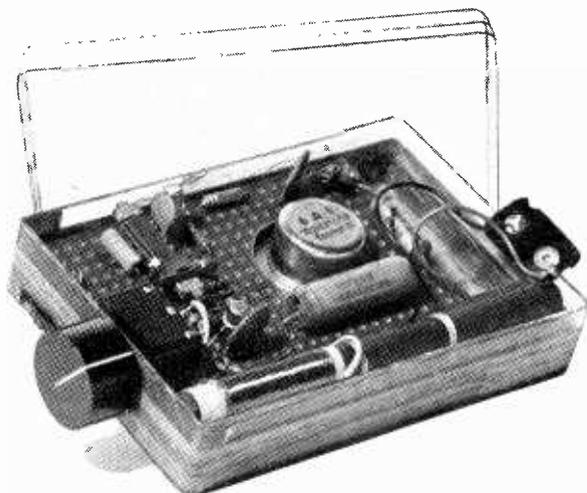

THIS receiver is designed to fit the pocket, having the tuning control and edge-operated potentiometer and switch at one end of the case, so that there are no projections elsewhere. It provides good volume. The actual external dimensions are $4\frac{3}{4} \times 3\frac{1}{4} \times 1\frac{3}{8}$ in., and this allows easy construction without cramping of the components.

The Circuit

This uses two IC's and a transistor, see Fig. 1. IC1 is the popular ZN414 "front end" network. The input is tuned by VC1, and the ferrite rod aerial L1 gives a frequency coverage of approximately 550-1600kHz. After r.f. amplification and demodulation in this IC, its audio output is taken to the audio gain control VR1. This has R2 in parallel, as small edge-operated potentiometers of the correct value to use alone here are not readily available.

The voltage for IC1 is derived from the potential divider R5, R3 and VR2. The 250 Ω pre-set resistor VR2 and R3 in series give a combination which can be adjusted from 470 Ω (R3 alone) to 720 Ω (with VR2 at maximum value). This allows easy setting of working conditions for the IC. Though a nominal voltage of about 1.3V is usually satisfactory, changing the potential of the supply by even 0.1V can have quite an effect on results. VR2 thus allows compensation for the tolerances in the actual values of R3 and R5.

Tr1 is a high gain audio amplifier, which supplies IC2 through C5. This IC has six transistors in a driver/push-pull circuit, with compensatory diodes, and a low standing current of only about 3.5mA. Its maximum output is up to about 250mA with a 9V supply and 16 Ω speaker, which is easily sufficient for this type of receiver. By using a speaker of higher impedance, peak current is reduced, without much significant loss of maximum volume.

There are no alignment or similar adjustments, which helps to make the receiver a very straightforward project. It is completely portable, using a PP3 or similar small 9V battery.

Circuit board

This is shown in Fig. 2. It should be cut so that it is a proper fit inside the case used. Approximately $2 \times \frac{5}{8}$ in. is cut away to take the battery, and $1 \times \frac{1}{8}$ in. for VC1. A hole about $1\frac{1}{8}$ in. in diameter is cut to clear the magnet of the speaker.

As the board and case must fit correctly, it is as well to prepare both at the same time. VR1 is secured to the board with a small bolt, as in Fig. 2. A slot is cut in the end of the box or case, to clear this control. A clearance hole should also be drilled for the spindle of VC1, and two holes for the short 6BA bolts which secure this item.

An opening for the speaker can be cut, and subsequently covered with silk or similar material. Or a number of holes can be drilled to form a grille. The opening, or area covered by the holes, should be approximately the same size as the loudspeaker cone. When the case is finished, the speaker is fixed with adhesive.

The transparent box actually used was approximately $4\frac{1}{2} \times 3 \times 1\frac{1}{8}$ in. inside dimensions, but provided the parts can be accommodated there is no reason why this size should be used. Though boxes of this kind are reasonably strong, the material can be easily cracked when drilling or filing. To avoid this, use a sharp drill, and work with quite light pressure.

With the receiver shown, the front and sides of the box were covered with a single piece of silken material, fixed with adhesive round the edges only, and drawn tight. The lid of this box was completely removable, and formed the back. This section was left uncovered. When a clear, transparent box of this kind is used, it can if preferred be painted *inside*. This requires a household or similar oil paint. If

applied with a soft brush, the appearance from the outside will be completely uniform.

When it is assured that the board will fit as in Fig. 2, with VR1 coming into position and projecting through the slot, the components can be added and wired. The board fits the case so that it does not have to be secured with screws or other means.

Components

Place these as in Fig. 2, noting the correct polarity of the electrolytic capacitors. It may be preferred to wire one or two as they are fitted, or to put them all in place, then turn the board over, and complete most of the wiring. The projecting wire ends can be spread out, to hold the components in place until they are soldered.

Fig. 2 also shows the underside of the board. Add insulated sleeving wherever necessary, and cut off excess leads.

The slider of VR2 is connected at one end by a short piece of thin flex, to allow adjustment. A small rotary pre-set is equally suitable. If a fixed resistor were to be used, with no provision for adjustment, it would be 680Ω, 5%. It would replace R3, and be connected from C3 positive to C3 negative.

★ components list

Resistors

R1	100kΩ	} All \pm w 5%
R2	1kΩ	
R3	470Ω	
R4	2.2MΩ	
R5	3.9kΩ	
R6	8.2kΩ	
R7	10kΩ	
VR1	Miniature edge-control 5kΩ pot with switch	
VR2	Pre-set slide resistor, 250Ω	

Capacitors

C1	0.01μF
C2	0.1μF
C3	6μF 2.5V
C4	0.047μF
C5	2.5μF 6.4V
C6	0.02μF
C7	200μF 6.4V
C8	100μF 10V
VC1	Jackson Dilemin 300pF single variable
Tr1	BC109
IC1	ZN414
IC2	MFC4000B (C.T. Electronics, see advert)

2½in. miniature speaker, 16 to 75Ω impedance.
Ferrite rod approx. 4½in. x ¾in. diameter, 26 s.w.g. enamelled wire, Veroboard, Plastic box, Knob.

The IC's

Fig. 2 shows the connections to the IC's. Spread the IN and OUT leads of IC1, and bring the E lead in line between them, so that the three wires pass through the holes. Check that all leads are clear of each other, and solder.

IC2 has two long and two short tags, with a marked end for tags 1 and 2. The tags will fit the board as in Fig. 2. Leads are soldered to them.

Tr1 is fitted in a similar way, its wires being arranged to come through the holes as shown.

Prolonged heating must be avoided when soldering these items, and it should only be necessary to

keep the iron in contact with the joint for a second or two.

Ferrite Rod Aerial

This is approximately 4½in. long, and has 65 turns of 26 s.w.g. enamelled wire, side by side. One layer of fairly stout paper is put on the rod, and the winding is on this. It is possible to slide L1 on the rod, to modify band coverage, but this should not be necessary if the winding begins about ¼in. from the end of the rod.

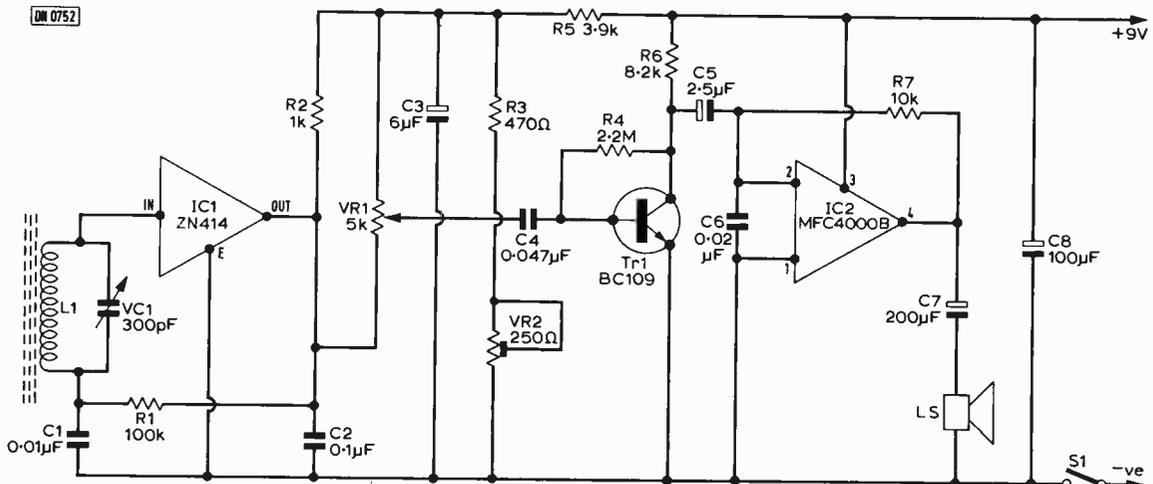


Fig. 1: Circuit of the Mini-Pop.

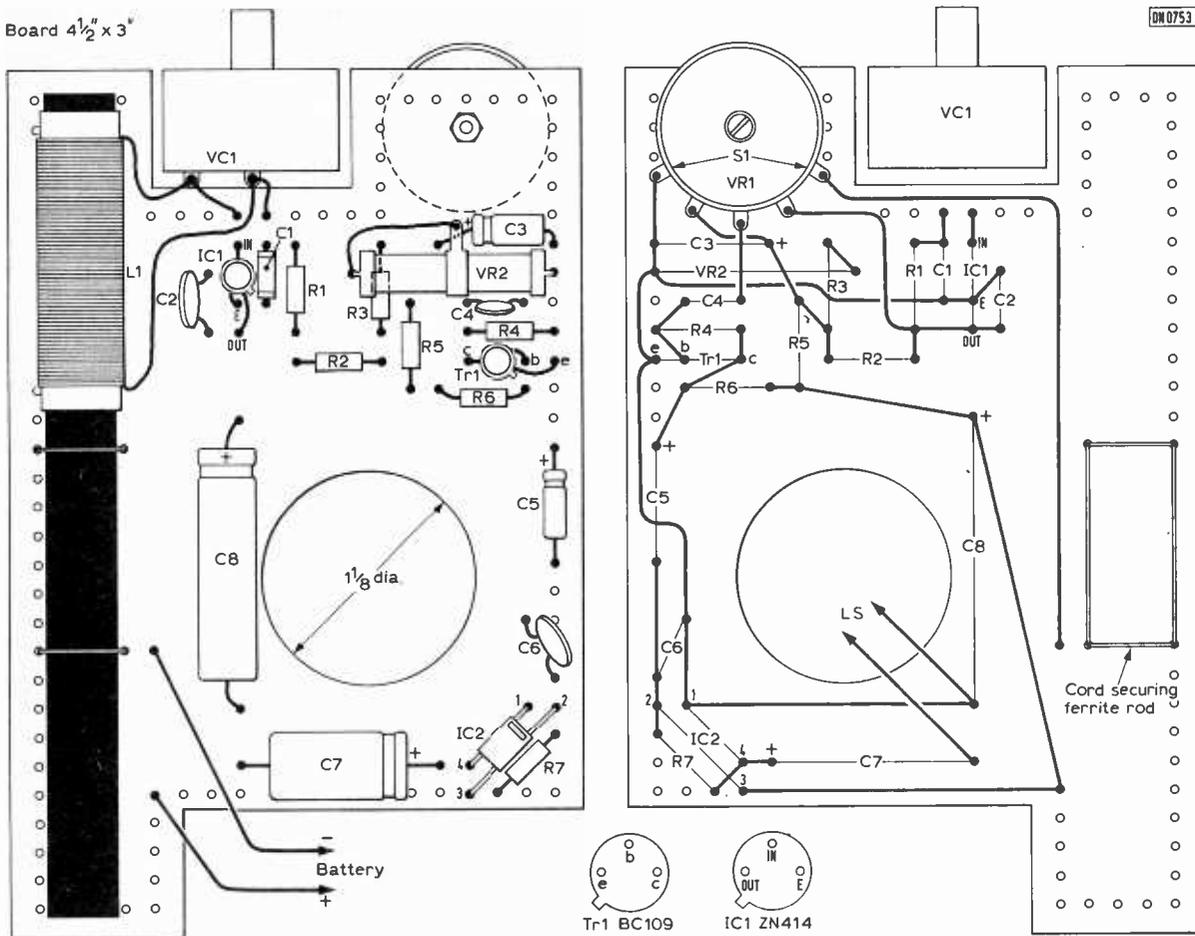


Fig. 2: Component layout and wiring. The circuit board is 0.15in. matrix plain Veroboard.

Adjustment

Results should be satisfactory with VR2 set at about its middle position. The potential across C3, as measured with a *high resistance* voltmeter, should be about 1.2V to 1.6V.

If the voltage is a little low, the receiver is likely to be lacking in sensitivity and volume. On the other hand, if the voltage is too high, whistles may arise at some frequencies, when tuning. The adjustment,

and exact voltage, is by no means critical. Should VR2 be re-adjusted to compensate for a discharging battery, remember to move it back to its original position when fitting a new battery.

The ferrite aerial is directive, and this may prove of advantage, either to bring up the volume of a weak signal, or to help reduce interference from an unwanted transmission. Though a 16Ω speaker is recommended for IC2, it is quite practicable to use a speaker of up to 75Ω impedance. ■

EXPERIMENTAL WORKSHOP

—continued from page 53

cartridge (off load) is in the order of 100mV so, in theory, no extra gain is needed. Because of the mismatch one would only expect to get that sort of signal at high frequencies and considerably less at low frequencies. Hence we need to tailor the response of the pre-amplifier to have approximately unity gain at high frequencies and high gain at the bottom end of the spectrum. This is very easily accomplished by replacing R5 with a high value capacitor (in the order of 10μF) in series with a 4.7kΩ resistor. It might be necessary—at the same time—to attenuate the signal from the crystal cartridge with a potential divide circuit prior to capacitively coupling it to the base of Tr1.

These examples are just a couple of suggestions

to show the versatility of the feedback pair. Although the single stage can give very good results, if you are lucky, the extra cost of the two stage circuit almost guarantees perfect results every time.

Next month we shall deal with the potential divide technique for biasing a transistor together with the grounded base amplifier.

(To be continued)

DRY BATTERY CHARGER

(MARCH '74 ISSUE)

The author has drawn our attention to the **charging current** levels which were given in the table on page 1058.

These should have read as follows:

U2 50mA (min) 150mA (max)

U7 25mA (min) 100mA (max)

U11 25mA (min) 100mA (max)

CASSETTE RECORDER AND TUNER AMPLIFIER

PART 3 RICHARD COLLIN


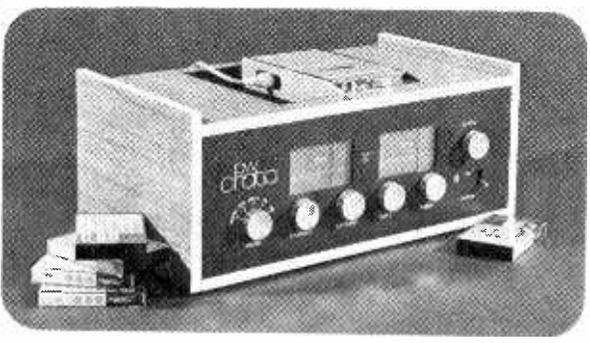


Fig. 14: Circuit of the Stereo Decoder using a phase-locked loop Integrated circuit.


DECODER BOARD (UNIT 4)

The stereo decoder section is designed around the RCA phase locked loop decoder, CA3090Q. This integrated circuit features low distortion, automatic stereo switching, a stereo beacon driver stage and requires only one tuning coil making alignment simple. An improved version, the CA3090AQ, is expected to be available in the near future. This offers improved stereo separation and lower noise, and may be used in this circuit without any other alteration to components.

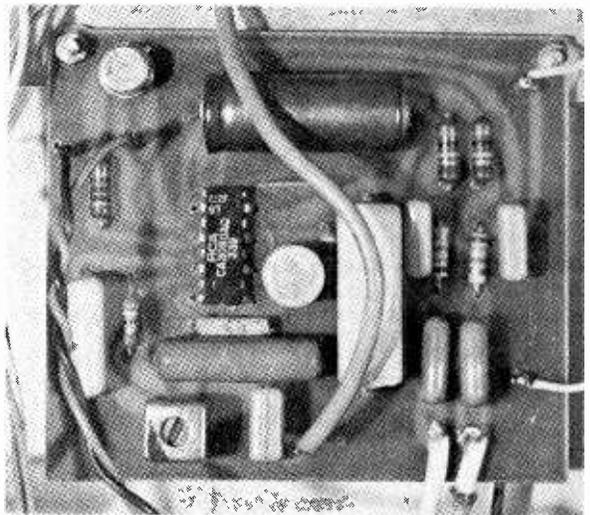De-emphasis of the audio signals is provided by R4/C9 and R5/C10, whilst resistors R6 and R7 are fitted to ensure that the volume level when switched to FM is comparable with that from other programme sources. Transistor Tr1 is used to switch the stereo indicator beacon, an LES lamp mounted in a small push-on holder which locates onto a tab provided on the dial backplate.



A view of the completed Stereo Decoder board.

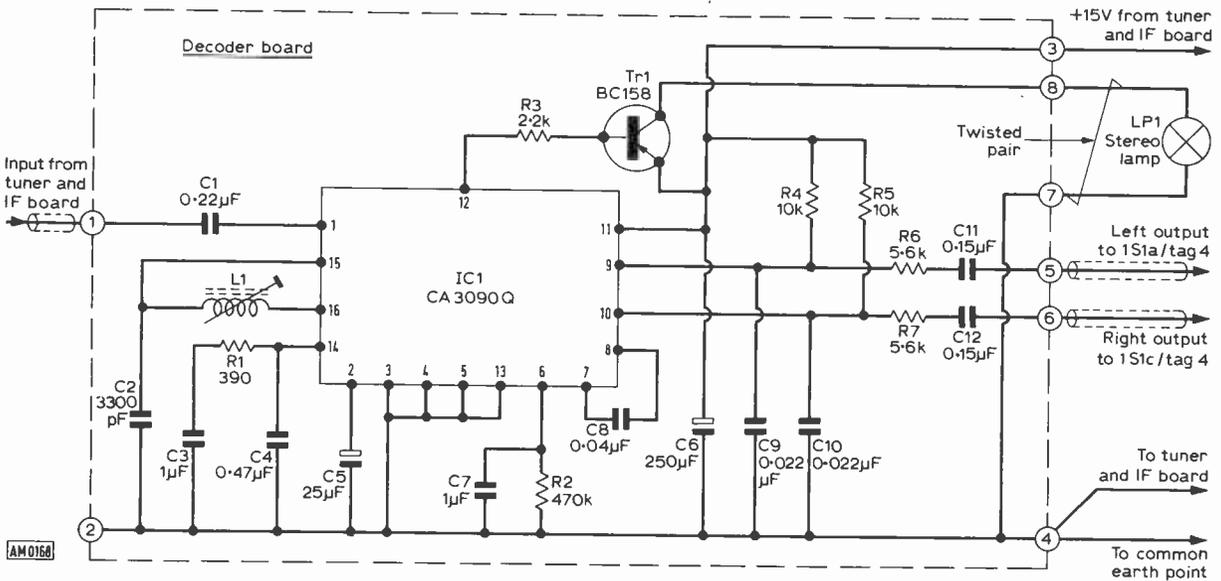

AM0168

FRONT PANEL

The front panel is made from 3mm perspex sheeting. The prototype design incorporated two dial plates as shown in the layout drawing, Fig. 16. Some constructors may prefer to dispense with dials and associated drives. An alternative circuit giving pre-selected FM tuning appeared in Fig. 11. A 4-way push-button switch could then be mounted on the front panel in place of the dials. This is a matter of individual taste, as indeed may be the complete panel layout. It is important, however, that the general control positioning is followed since vastly differing layouts could lead to hum or instability problems.

When supplied, the perspex has a protective paper covering on each side and this is used to mark out the panel and also to mask areas for indicator lights and dials (shown shaded in Fig. 16) when the panel

★ components list

DECODER BOARD

Resistors

R1 390Ω	R5 10kΩ
R2 470kΩ	R6 5.6kΩ
R3 2.2kΩ	R7 5.6kΩ
R4 10kΩ	All ¼W 5% carbon film

Capacitors

C1 0.22μF polyester	C7 1μF polyester
C2 3300pF polyester	C8 0.047μF ceramic
C3 1μF polyester	C9 0.022μF polyester
C4 0.47μF polyester	C10 0.022μF polyester
C5 25μF 25V PC mtg.	C11 0.15μF polyester
C6 250μF 25V	C12 0.15μF polyester

Semiconductors

Tr1 BC158
IC1 CA3090Q (RCA) (see text)

Miscellaneous

L1 Toko YXNS-30450-NK.	LP1 14V LES
Printed circuit board	Lampholder LES push-on

POWER SUPPLY

R1 1.5Ω 5W wirewound
C1 0.1μF 250VAC
C2, C3 2500μF 40V
D1—D4 44001 (RCA) or 1N4001
T1 240V: 25V 1.2A Drake Transformers Ltd., Cat. 294—140 (see note)
S1 SPST 250V 5A toggle switch with long dolly
F1 1A fuse with holder
N1 Neon indicator 240V

NOTE: Equivalent mains transformers are manufactured by:

Colne Electric Ltd., Cat. 20043
Gardners Transformers Ltd., Cat. GR97183

REAR PANEL

SK1 Insulated coaxial socket (FM Aerial)
SK2 Wander-plug socket (AM Aerial)
SK3 Min. 3 pin mains socket (Mains out)
SK4 Min. 3 pin mains socket (Mains out)
SK5 2 pin DIN socket (Right L.S.)
SK6 2 pin DIN socket (Left L.S.)
SK7 5 pin DIN socket (Mag. P.U.)
SK8 5 pin DIN socket (Cer. P.U.)
SK9 5 pin DIN socket (Tape Head)
SK10 5 pin DIN socket (Tape Recorder)

Notes:—

- SK3/SK4 may be Bulgin P438 or similar.
- 5 pin DIN sockets are 180° type.

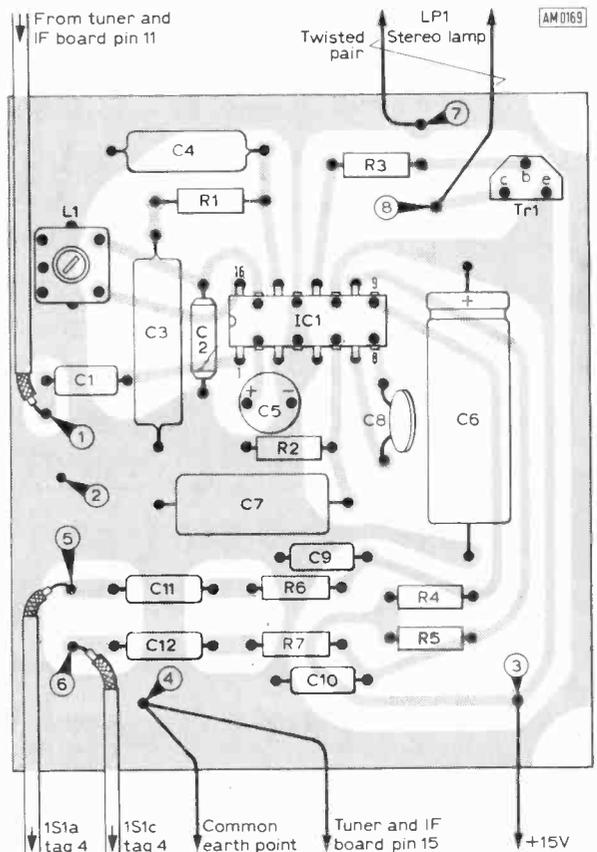


Fig. 15: Component location and printed circuit layout for the Stereo Decoder board. Both drawings are actual size.



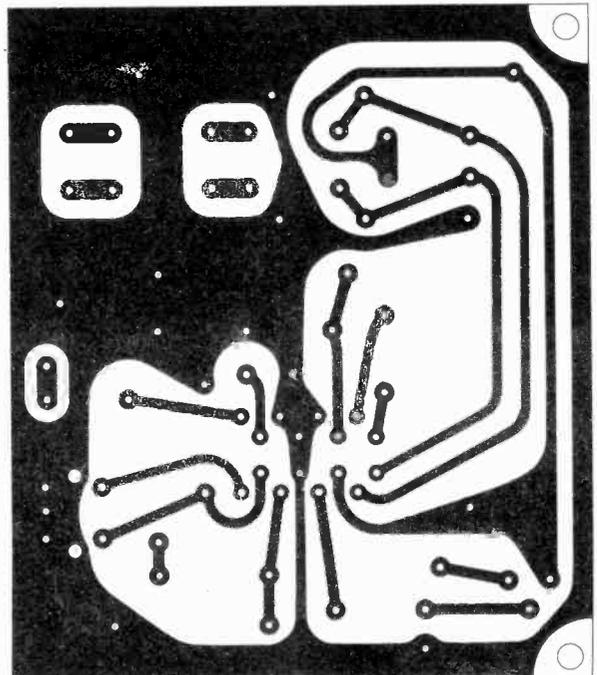
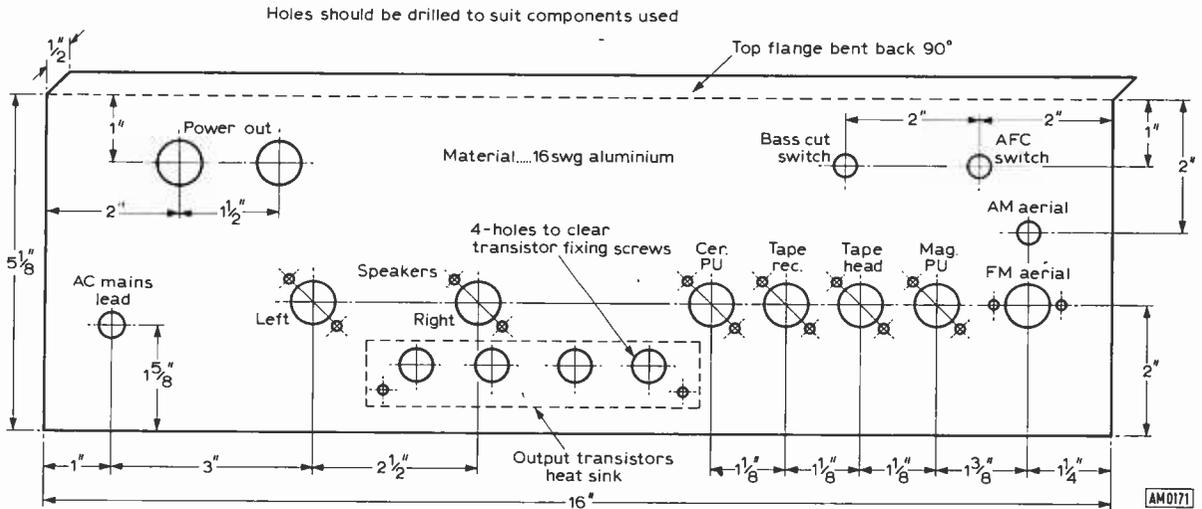


Fig. 16: Layout for the Front Panel showing positions of the controls and dial and pilot lamp windows.

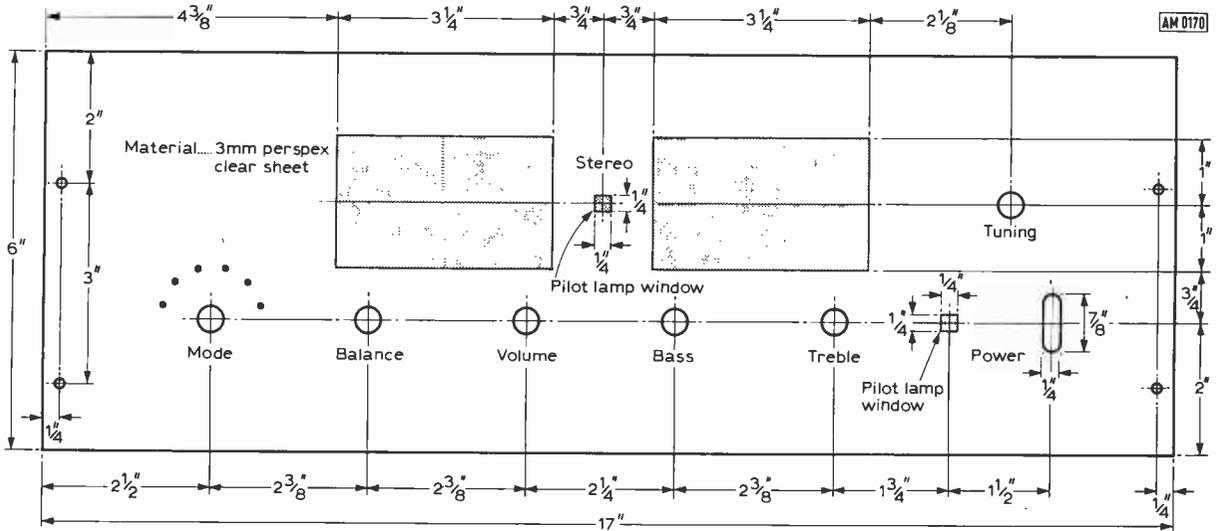

This rear view of the prototype shows the type of chassis construction used.

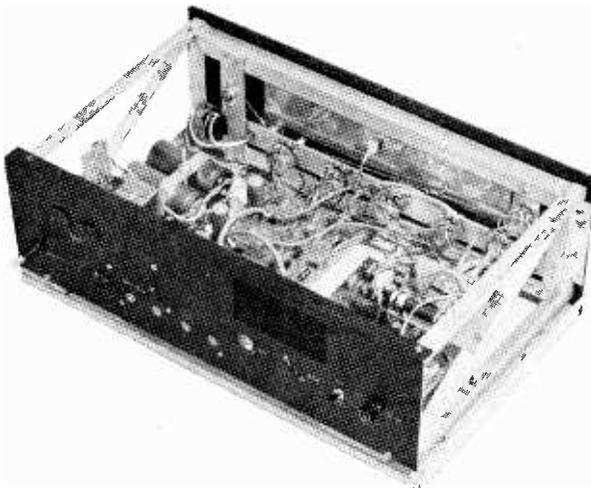▲ Fig. 17: Layout of the Rear Panel which carries the input and output sockets and also forms the heatsink for the amplifier output transistors.



is spray painted. After marking and drilling all holes the paper coating on the rear side is removed except for masked areas and several coats of cellulose paint sprayed on. The original was sprayed black.

After spraying, the front side paper coating should be removed (again except for the masked areas) and Letraset, Blick or other dry-print lettering applied. The finished panel should then be sprayed with Letracote-matt varnish to protect the lettering. The masking paper can then be removed. Pilot lamp apertures may be painted on the rear side with red or orange cellulose paint.

CHASSIS

The chassis is a skeleton framework made from aluminium strip and angle. A sheet aluminium rear panel, Fig. 17, carries the input and output sockets and also forms the heat sink for the power amplifier output transistors. The rear panel should be sprayed matt black and the various sockets labelled using Letraset.

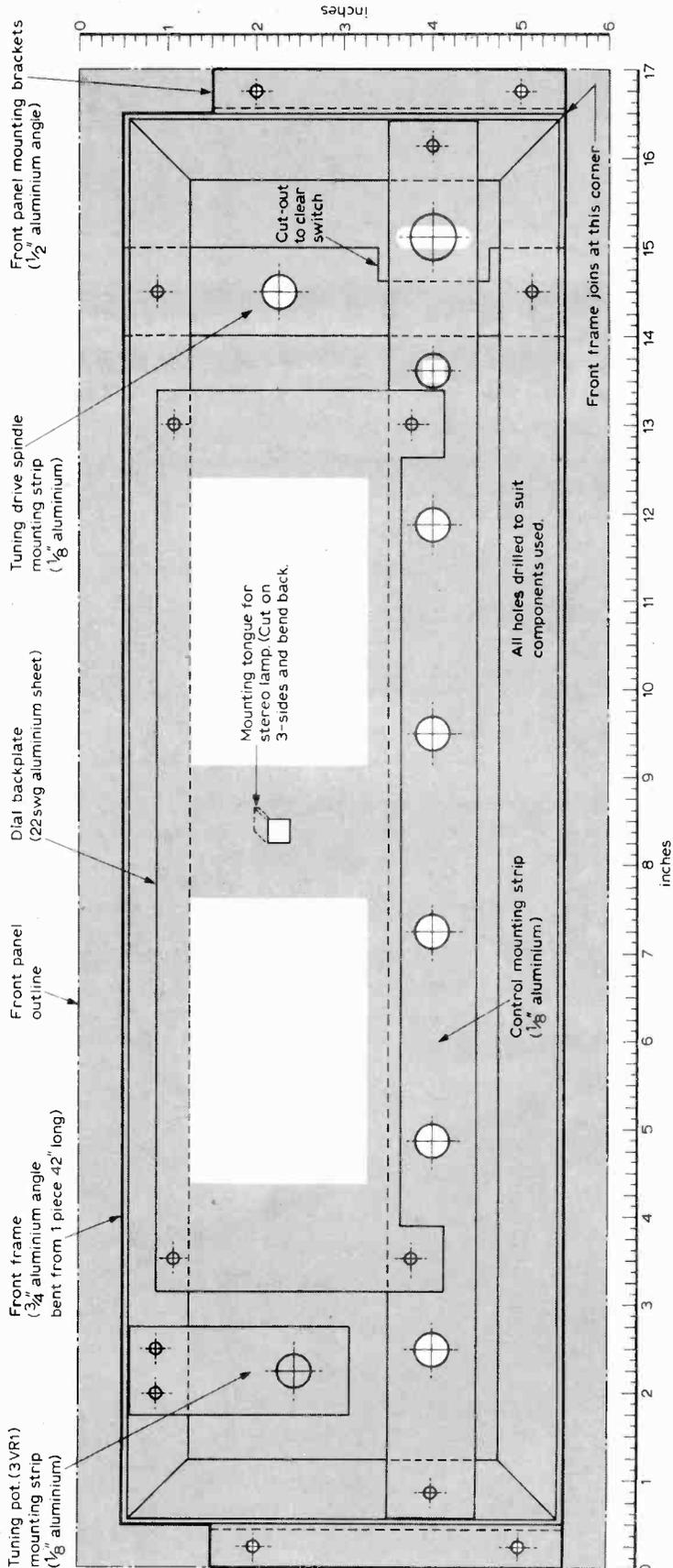
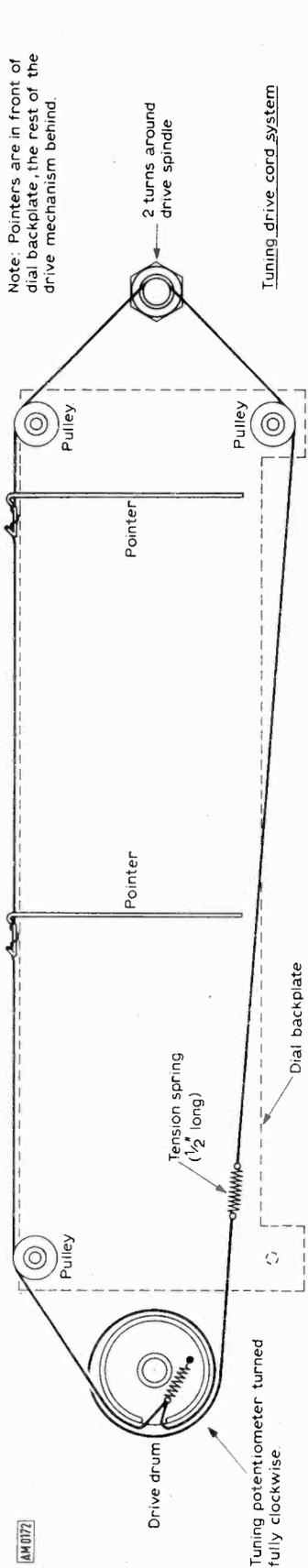


Fig. 18. Constructional details of the framework carrying the front panel and controls (shown half-scale) and the drive cord arrangement.

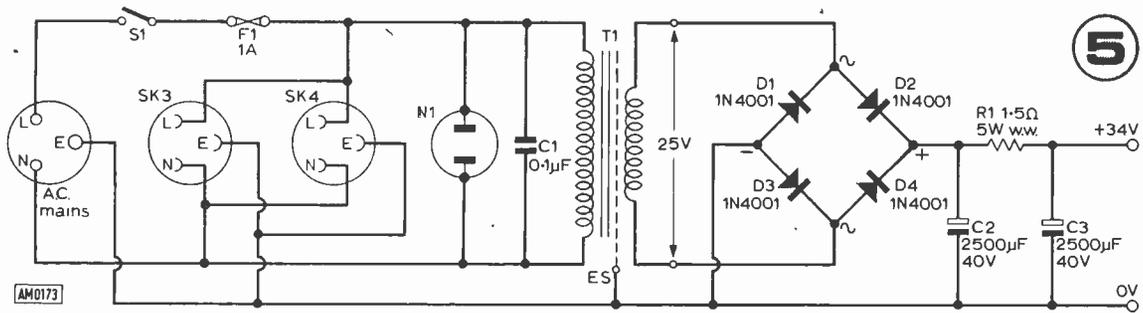


Fig. 19: Circuit of the Power Supply. C1 reduces interference from mains-borne transients.

POWER SUPPLY (UNIT 5)

The power supply, Fig. 19, is mounted directly on the chassis using a $1\text{in} \times \frac{1}{8}\text{in}$ aluminium bar running from front to back to carry the transformer and smoothing capacitors. The diodes may be mounted on a small printed board or tagstrip on or beside the transformer tagboard.


Sockets SK3 and SK4 carry switched AC mains out to the associated record deck or tape deck. The total load should not exceed 1A.

On the prototype the depth of the chassis (front to back panels) was 10in. This dimension and the size of the cabinet should be adjusted to suit whichever cassette recorder is to be used.

The framework carrying the front panel, the tuning drive and the various controls is shown in Fig. 18. The dial back plate, which is made from thin sheet aluminium, is mounted on the bolts carrying the drive cord pulleys. It should be sprayed in the chosen colour and the scales marked with Letraset. Calibration is best done when the tuner is complete and functioning—that way the station markings cannot fail to be accurately placed. Note that the drive cord passes behind the dial back plate.

**Our next issue will cover
connecting up, testing and
alignment**

Pw TECHNIGROSS PUZZLE No.4

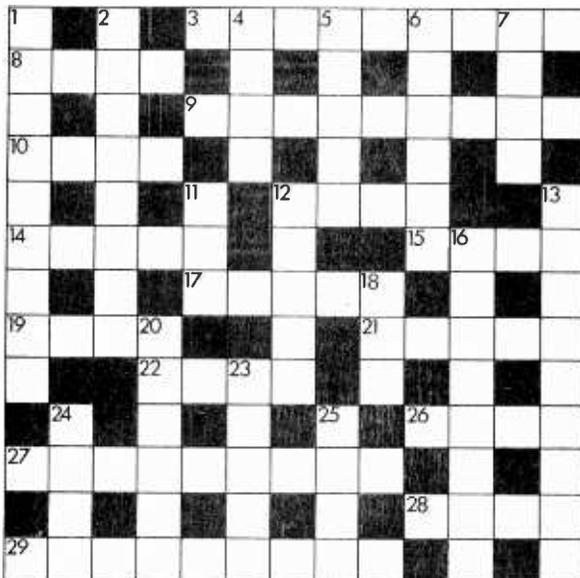

ACROSS

- 3 Serious parallels for such vibration? (9)
- 8 Simple to select four negative-feedback components? (4)
- 9 Orchestral extension measured in kc/s? (9)
- 10 Did a terminal fuse around that time? (4)
- 12 Such electrons currently at liberty? (4)
- 14 Rows about television screening (5)
- 15 Its wave's plotted without Latin! (4)
- 17 He's a king about such diodes (5)
- 19 Assumed superiority of some tuning? (4)
- 21 His F-layers lose weight but bear fruit? (5)
- 22 Echo metallic with a domestic connection (4)
- 26 Dwelling on such useless batteries? (4)
- 27 It turned the tables on the wireless! (9)
- 28 Champion fellow linked with the ends of radio (4)
- 29 Sort of circuit for the pick-up man? (9)

DOWN

- 1 Polar bear with it may be resistive (5, 4)
- 2 Magazine that should be on tape? (8)
- 4 Bit of cheese in the choked amplifier! (4)
- 5 Do err in our switching instruction? (5)
- 6 Whispers that are audio-frequencies? (6)
- 7 Enthusiasts putting out feelers for old sets (4)
- 11 Employ Sue on distortion correction (3)
- 12 Bordering on a picture with such an aerial? (5)
- 13 Welcome that means a signal success (9)
- 16 They urge us into radio-activity? (8)
- 18 Scotsman in multi-antennae manufacture (3)
- 20 High in the charts with such a sound! (6)
- 23 Radio to primitive peoples? (5)
- 24 Palm-product in Goa's transformers (4)
- 25 Overhead waveband, for goodness sake! (4)

**FOR AMUSEMENT ONLY
ANSWERS NEXT MONTH**



oscilloscope

PART 3

techniques ALAN AINSLIE

Y DEFLECTION

It is normal practice to amplify the Y signal before applying it to the deflection plates. Fig. 1 shows a simple AC amplifier that provides an asymmetrical output. This means that special measures have to be taken in the design of the CRT to avoid trapezium distortion. However, the circuit is not quite so simple as it looks and a stray capacity (plus CRT plate capacity) of well over 30pF may exist between the anode and earth. At 1MHz this stray capacity would take 25mA if the tube were being driven with 150V. This situation can only be improved by reducing the anode load, and increasing the current to maintain output, so that it is negligible in comparison to the reactance of this stray at the highest frequency of interest. This is only possible, within reason, as the anode current gets very large. Therefore this amplifier is capable of results only up to a maximum of a few MHz.

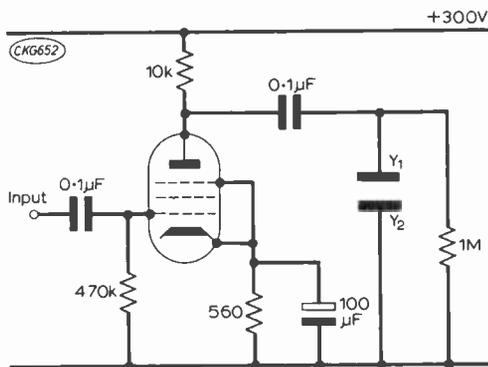


Fig. 1. Simple AC amplifier with asymmetrical output, not recommended for scope use.

There are several methods of producing true wide band performance and we shall look at these shortly after considering how we might modify the circuit to produce symmetrical deflection and be DC coupled.

DC AMPLIFIERS

DC coupled amplifiers along the lines of the cascade AC amplifiers are not really successful due to drift causing the trace to shift as if varying DC were being applied to the input. Balanced amplifiers are therefore used which balance out any drifts and also provide symmetrical deflection. Simple oscilloscopes have need for only moderate gain and the circuit of Fig. 2 is fairly typical. V2 and V3 form a phase

splitter and each valve drives one deflector plate. V2 grid is undriven except by the shift control and this can be calibrated directly in volts of shift. The grid of V3 is driven from V1 in a normal manner and the input applied to V1 grid. The 2kΩ preset varies the sensitivity of the amplifier enabling a certain height of deflection to be achieved for a given input. It does not change the calibration of the shift control. Several laboratory scopes use calibrated shift controls as well as graticule measurement and we shall shortly discuss the calibration of such a system.

It is common practice to use a cathode follower input stage driving the first valve, and to arrange the circuit between positive and negative supply rails to ensure that shorting the input does not shift the trace and also to reduce influence from supply variations. Usually more amplification follows after the phase splitter. Fig. 3 shows the input stages of an EMI WM16 scope. The phase splitter is V3 and V4, V3 being the driven valve. The two outputs are fed to further amplifiers including a distributed amplifier before being applied to the tube.

Fig. 4 shows the general arrangement of a high quality Y amplifier system. In a large complex oscilloscope the components to the left of the dotted line would be constructed on a small plug-in chassis, allowing great flexibility. The signal level at the dotted line is about 0.5V each side of zero.

The circuitry of a plug-in of high quality (rise time 5ns) is basically very simple, the signal levels being fairly low. In fact the simpler the circuit the better the chance of good HF performance as complicated wiring only introduces stray capacities.

ATTENUATORS

The input is fed through a high frequency connector to the AC/DC switch which allows for DC blocking of the signal if required. The basic sensitivity of the Y channel is generally about 50mV/cm and the input capacitance looking into the cathode follower plus strays may be 20pF. In order to reduce the sensitivity an attenuator is interposed between the cathode follower and the signal. It is important to keep the DC input resistance constant, usually 1MΩ, and the capacity constant so that external probes can be used.

Fig. 5a shows a typical attenuator in the direct, most sensitive range, and at a divide-by-10 position, Fig. 5b. The attenuator is switched at the point A by a low loss, carefully screened, low capacity switch. Often, after a few years of dust has accumulated, the attenuators need setting and the following method is recommended.

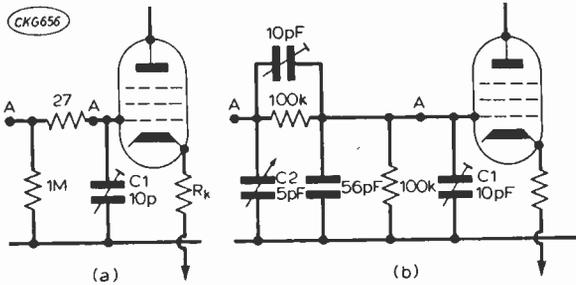


Fig. 5. (a) A simple direct attenuator and (b) a -10 dB attenuator with compensating capacitors.

10:1 or, even better, a 50:1 probe to give correct results on the direct range. C2 can then be set on each range for the fidelity of the square wave. The only snag is the high voltage needed for the high voltage ranges to give a reasonable deflection but in the absence of the proper gear this is the best that can be done.

Not all attenuators are built in this manner, where individual sections are switched in, but in a manner where the sections are interdependent. These attenuators usually tap the signal off a $1M\Omega$ chain of resistors and the capacitor settings are interdependent. It is best to obtain a manual if readjustment is necessary.

The attenuator feeds the cathode follower which is arranged between symmetrical supply lines to help eliminate drift. The cathode follower and phase splitter are arranged as in Fig. 3. The small anode loads and L1, L2, L3 maintain a good HF response. The balanced amplifier and buffer (usually a cathode follower) are fairly conventional with the addition of a few coils to help the HF response. The coil is arranged to resonate with the stray it is introduced to overcome, at a frequency higher than the required -12 dB point. Care has to be taken to ensure that transients do not cause ringing and the criterion for good transient response is that the response curve should have a "Gaussian" fall-off. The -12 dB point then occurs at twice the frequency of the -3 dB point. In this way the amplifier will show no ringing on transients and consequently most high grade amplifiers are tailored to this requirement.

GAUSSIAN FALL-OFF

For a perfectly gaussian response the result obtained earlier that $\text{Rise Time} \times \text{Response} = 365$ is found to be untrue and the true figure for the product is 350. However this gives erroneous results in several cases where the rise time and bandwidth are measured separately. The product of the two values is usually found to be about 365 and so this value is taken for most calculations. Most practical amplifiers produce the required gaussian fall-off, but, if not, can easily be tailored for the required performance. Small inductors and capacitors are used, these being adjusted so that a known "good" pulse (say a 500kHz square wave, rise time less than 10ns) produces no ringing. This condition gives the fastest rise time as well and so ringing of transients in a wide band amplifier may be an indication that the response is not as it should be.

One other factor is the delay of the amplifier and this must be considered for all frequencies significantly within the pass band. Fortunately we do not need to worry too much about the delay changing

with frequency as the adjustment to a gaussian fall-off produces the required group delay characteristics.

While discussing frequency relationships within the amplifier it is perhaps as well to consider non-linear HF distortion. This is usually noticed as an inability of the amplifier to produce more than a small deflection at a high frequency regardless of how large an input is present. The effect usually occurs outside the normal pass band of the amplifier, but is worth having in mind when using a wobulator (FM oscillator, deviated by the time-base) to check responses of external circuits as the amplitude of the trace may have a bearing on what is presented on the screen.


Y DRIVE CIRCUITS

We now come to consider the business end of the Y amplifier, the CRT driver circuits. These are always housed in the main frame of a plug-in type of oscilloscope as they are rather bulky and the shortest possible leads to the Y plates are required. Narrow band oscilloscopes, say up to 5 or 6MHz, use conventional output stages with low anode loads and peaking coils. The anode current to produce the 30 or 40V output needed is rather high. Typical valves used are ECC88, but they are rather overrun. A large DC signal may cause heating of the valve electrodes and a shift of the trace as the valve characteristics change. This effect is also present in the early balanced stages, but is not nearly so bad as in this type of output stage. However suitable feedback between the halves of the output stage can reduce the effect to an acceptable level.

To obtain 30 or 40MHz bandwidths by the above method of balanced single output stages would be pretty hopeless and so use is made of the distributed amplifier, a transmission line with gain, if one likes to think of it that way.

DISTRIBUTED AMPLIFIERS

Fig. 6 shows the general arrangement of a balanced Y amplifier. The valves are effectively in parallel from a DC point of view. If pentodes are used the screen grid is taken to the positive supply in the normal way. The anode and grid lines form delay lines and the mode of operation is to make the wave velocity the same in each line. The velocity is dependent upon the inductance of the lines and the capacitance at each stage, the valve anode or grid capacity.

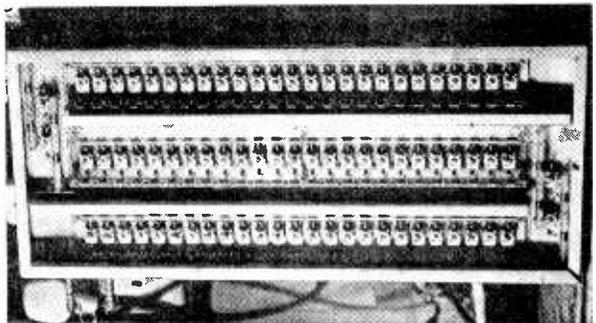

A 79-section 170ns delay line showing capacitors for adjusting line impedance and velocity.

NO EXTRAS
ALL PRICES INC. VAT
FREE! P. & P.

AMPLIFIERS	
Keltron KSA 700 7+7 watt	23-00
MK II KSA 1500 15+15 watt	32-50
Tripletone MkII Hi-Fi 1777+7 watt	27-50
MK II Hi-Fi 1818 18+18 watt	35-00
Teleton MkII SAQ3078+8 watt	27-00
EMI 1515 15+15 watt	37-00
Rotel RA210	32-00
RA310	44-00
Rotel Tuner/Amp. RX150A	51-00
SANSUI models in stock.	
RECORD DECKS	
Garrard 2025TC/STAHG/G	11-00
SP25 Mk. III	11-00
BSR MP60/SX5H	11-00
Connoisseur BD1 Kit	11-00
BD2 Chassis	29-50
SAU2 Pick-up Arm	12-25
SCU1 Cartridge	4-95
RECORD DECK PACKAGES	
SP25 Mk. II. in Plinth & Cover	
Garrard wired	219-95
SP25 Mk. III/G800 C. & P.	19-50
AP76/G800 C. & P.	30-00
Plinth & Cover for Garrard	
SP25/2025TC	3-95
SPEAKER BARGAINS	
EMI 13" x 8" 3, 8 or 15 ohm	
Plain	2-35
with Co-Axial Tweeter	2-50
Twin Tweeter	3-95
Type 350 8 ohm, 20 watt	3-50
6 1/2" 8 ohm, 10 watt	2-55
8" 8 ohm, 10 watt	3-90
12" 8 ohm, 20 watt	5-75
8" x 5" C/Mag, 5 watt	1-40

8" x 5" Dualcone 8 ohm	
10 watt	2-70
FANE 7" x 4" 3 or 8 ohm	1-15
5" Dualcone 8 ohm	2-60
CELESTION 8" 15 ohm	3-25
ADASTRA 10" 8 or 15 ohm,	
10 watt	3-25
BAKER GROUP 25	
12" 8 or 15 ohm, 25 watt	6-50
5" 8 ohm, 5 watt C/Mag.	95
2 1/2" 8 ohm or 64 ohm	60
SELECTION OF GOODMAN AND	
WHARFEDALE SPEAKERS ALSO	
AVAILABLE.	
KIT FORM CABINETS—TEAK	
VENEER	
12 x 12 x 6 with 8", 8" x 5"	
or 6 1/2" and 3 1/2" cutout	2-75
17 x 10 x 9 with 8" or 13" x 8"	
cutout	3-95
18 x 11 x 9 with 13" x 8" cut	
out for EMI 350	4-60
TWEETER & CROSSOVER	
EMI 3 1/2" 3 or 8 ohm C/Mag.	1-10
Cone Tweeter 8 or 15 ohm, 10 watt	2-50
Cone Tweeter 8 ohm, 3 watt	1-50
Horn Tweeter 8 ohm, 20 watt	5-95
Dome Tweeter 8 ohm, 30 watt	1-75
Crossovers CN23 (3 ohm), CN28	
(8 ohm), CN216 (16 ohm)	4-15
CARDRIDGES	
ACOS GP91/28C or GP91/38C	
Stereo comp.	1-05
GP93/1 Stereo crys.	1-35
GP94/1 Stereo crys.	1-75
GP95/1	1-25
GP96/1	1-75
GP101	75
SONOTONE	
STAHG Stereo ceramic, diam.	1-80
STAHG/G Slim fit, stereo cer.	1-80
diam	1-75
19-T1 Stereo crystal	85
BSR SC5M Stereo ceramic	2-25

SX5H Stereo crystal	1-65
SX5M Stereo crystal	1-65
X5H Mono/stereo	1-30
X5M Mono/stereo	1-30
GOLDRING G800	2-55
G850	2-55
STYLI For Above Cartridges	
Sapphire	30
D. Diamond	1-25
GOLDRING G800 G850	1-95
MICROPHONES	
CM20 Crystal Hand	60
CM70 Planet stick metal switch	
crystal	1-70
DM160 Dynamic uni-dir, ball	
metal	4-00
UD130 50K/600 ohm, uni-dir,	
ball metal	5-65
TW206	5-90
CONDENSER MIKE 600 ohm,	
uni-dir	7-90
Cassette STICK MIKE with R	
Control on/off switch (2-5 &	
3-5 mm J/Play)	1-45
MIKE MIXERS Mono	4-10
Mono/stereo de luxe	5-50
CASSETTES	
Type Low Pin-Phil-Mem-Am-	
noise nacln lips orx	per
C45	50p 45p
C60	35p 40p 50p 55p 55p
C90	45p 55p 60p 75p 75p
C120	65p 75p 105p 110p 110p
Cassette Head Cleaner	45
BIB Stereo Test Cassette	1-65
AMPEX Head Cleaner De-	
magnetiser	1-65
PLASTIC LIBRARY CASES for 5"	
Reels 20p, 5 1/2" Reels 25p, 7" Reels 30p.	
CASSETTE CASES	
12p	
TAPES	
8 1/2" L.P.	D.P.
55p	65p
85p	75p
80p	£1-05



Credit Terms for Callers

BUDGET SPEAKER SYSTEMS	
1. Pr. of 10watt 8ohm 2 speaker system in deluxe teak veneer cabinet 18" x 11" x 9" wired, inc. plugs.	£25 00 per pair.
2. Pr. of 20watt 8ohm 2 speaker system freq. response 80c.p.s. to 17,000c.p.s. Teak veneer cab. 21 1/2" x 12" x 9" with 12ft. cable and plugs.	£29-95 per pair.

AKAI TAPE DECK	
400DS Tape	73-50
GXC40D Cassette	64-95
HEADPHONES	
AMSTRAD HP55A	5
ROTEL 430	4-90
630	6-20
700	8-45
AKAI ASE 115	5-75
ASE 20	7-95
ASE 22	9-25
KOSS K711 (Black or Red)	9-95
R6	11-95
R6M (with Vol. control)	13-25
K0727B	15-75
K0747	19-50
AL11	19-50
PRO4AA	26-95
PRO5LC	28-75
ESP6	42-75
LEESON ELECTROSTATIC	19-50
Mono/stereo super de luxe 8-16Ω	1-75
Headphone Adaptor	2-50
Curly Ex. Lead 20ft.	1-10
IN-CAR ENTERTAINMENT SECTION	
Car Cassette Stereo Player and Two Speakers	20-95
Car 8-track Stereo Player and Two Speakers	18-50
Pair of Car Stereo Speakers	3-85
Pair of Car Stereo Speakers (Door Mounting)	8-95

NEWMART ELECTRONICS

MAIL ORDER DEPT. (PW/5)
BELMONT STREET
MONTON, ECCLES
MANCHESTER
Tel. 061-789 5268

CALLERS WELCOME AT OUR BRANCHES
Manchester Liverpool
30-32 Shudehill 15 Whitechapel
061-832 7710 051-236 0738
Leeds
4 New Market St.
0532 42708

ALL MERCHANDISE FULLY GUARANTEED

Train for television

Course commences 4th September, 1974

This is your opportunity to train as a television and radio engineer on our full-time Two-Year College Diploma Course specially designed to cover the examinations of the City and Guilds Radio, Television and Electronics Technicians' Certificate. Full theoretical and practical instruction on all types of modern receivers—including the latest colour sets.

Minimum entrance requirements are Senior Cambridge or 'O' Level, or equivalent in Mathematics and English.

Please send free prospectus to:

Name _____
Address _____

THE PEMBRIDGE COLLEGE OF ELECTRONICS
(Dept. pw2) 34a Hereford Rd., London W2 5AJ

DIODES 800 PIV 750 Ma new 15 for £1.10, also 200 PIV 8 amp 4 for 70p. **FILTER UNITS** contains toroids, precision conds etc. new 3 for £1. **WAVEMETER ASS** tunes 420 to 460 Mc/s with knob and dial (not cal in freq) £2. **VALVES** QQV03-20 with base £2 ea 5763 60p ea. **TRANSISTOR MOD TRANS** matches 2xOC35 to QQV03-20 £1.45. **X POINTER IND** as dual 115 Ua movements for use with R1155 £1.58. **METER UNIT** nav display special purpose cent reading type new with circ £1.15. **CARBON MIKES** 100 ohm with swt type T17 new £1.15. **AMERICAN 73** Radio Mags back issues 6 different for £1. **SCREW TERM** none insul type 3/8th head 4 Ba stud 5 for 60p. **SPEAKER UNITS P.A.** type 8 ohm in case size 9 x 9 x 8" by Truvox £3.30. **RADIO TELE-METER** units L.F. radio Rx with 6 valves, 3 1/2" spk, 2 motors, coin box unit in neat case with int main P.U. will mod to radio 2 with circ £4.95. **CODER UNIT** contains 10 min valves, 13 min. 12v relays 12 min micro swts plus misc parts in case £3.23. **B.N.C.** type coax sks single nut fix type 75 ohm with short length of cable 5 for 70p. **R.F. SWT** relays 12v coil as 2 N.O. and 1 N.C. RF contacts plus 2 N.O. aux contacts uses reeds 75 ohm Z 55p ea. **REED RELAYS** coil 110 ohm 10/14v plug in type, two types available, 6 N.C. or 6 N.O. contacts with base 44p ea. **COAX CABLE** good quality 75 ohm type UR56 20 yds for £1.42. **PRESS GAUGE** thought to be Oil scale 0/120 elec operated vehicle type new 50p. **DUAL GANG** 10K ohm w.w. pot 2 1/2" dia with knob and dial with circ of AF Osc £1.35. **TEST SET 502** with 2.5 Ma FSD meter 3 yax swts, terminal, neons etc in case with mod for 5 range DC voltmeter £2-10.

The above goods are ex. equipment unless stated otherwise, prices include Vat & postage.

A. H. SUPPLIES
57 MAIN ROAD, SHEFFIELD, S9 5HL
444278 (0742)

ESSENTIAL BOOKS FOR RADIO AMATEURS

RADIO AMATEURS' EXAMINATION MANUAL

by G. L. Benbow, G3HB

The standard work for all would-be licensed radio amateurs studying for the Radio Amateurs' Examination. Success in the RAE should be assured if all that it contains is understood and remembered.
84 pages 90p post paid

TELEPRINTER HANDBOOK

by D. J. Goacher, G3LLZ, and J. G. Denny, G3NTT

A brand new book covering all aspects of modern teleprinter techniques. Full descriptions and maintenance data for all widely-used machines, together with design and use of ancillary equipment. Definitely a book for the teleprinter enthusiast's work bench.
376 pages £5.35 post paid

A GUIDE TO AMATEUR RADIO

by Pat Hawker, G3VA

This extensively revised 15th edition is an indispensable aid to all who want to know more about amateur radio. Specially designed to assist the newcomer to the hobby, it covers technical, operating and licensing matters.
96 pages 90p post paid

AMATEUR RADIO TECHNIQUES

by Pat Hawker, G3VA

(4th Edition)

A source book for many useful circuits and aeriels. An *ideas* book aimed at extending the reader's awareness of new devices and techniques.
256 pages £1.80 post paid

These are just four of a complete range of technical publications, log books and maps for the radio amateur. Send a large s.a.e. for the complete list.

The **RSGB** is the national society representing all **UK** radio amateurs. Membership is open to all interested in the hobby: write to the General Manager and ask for full details.



RADIO SOCIETY OF GREAT BRITAIN

35 DOUGHTY STREET, LONDON, WC1N 2AE TEL: 01-837 8688

CHROMASONIC electronics

Dept. I.

56, Fortis Green Road, London, N10 3HN.

THE P.I.E. LIQUID CRYSTAL CLOCK

- 12 or 24 hour operation
- Hours and Minutes to Minutes and seconds at a touch
- Audible Electronic Alarm
- Liquid Crystal Display



- Visual Alarm Set
- Extra "Snooze" Time Alarm
- Radio On/Off facility
- Mos I.C. Clock Chip

A complete set of parts to build this up-to-the-minute (sorry) project at a special price. All parts available separately. Ask for Price List

MM5316 Alarm, Clock Chip	£16.50	RS Reed Relay	80p
40 pin I.C. Socket	44p	Dil Switch	85p
AN4132 4 digit display (inc. socket)	£14.37	Xtal. Mike insert	44p
LM3900 quad amplifier	77p	14 pin I.C. Socket	15½p

NEW

Mullard LP1400 Stereo Decoder Module. £4.96 p & p 15p. Ex stock. Leaflet 10p. If purchased with LP1185 & 6 normally £13.96—now £13.49 Dual 555 Timer 2556 only £1.65

VAT INCLUSIVE PRICES

OVERSEAS CUSTOMERS DEDUCT ONE ELEVENTH.

P & P 10p

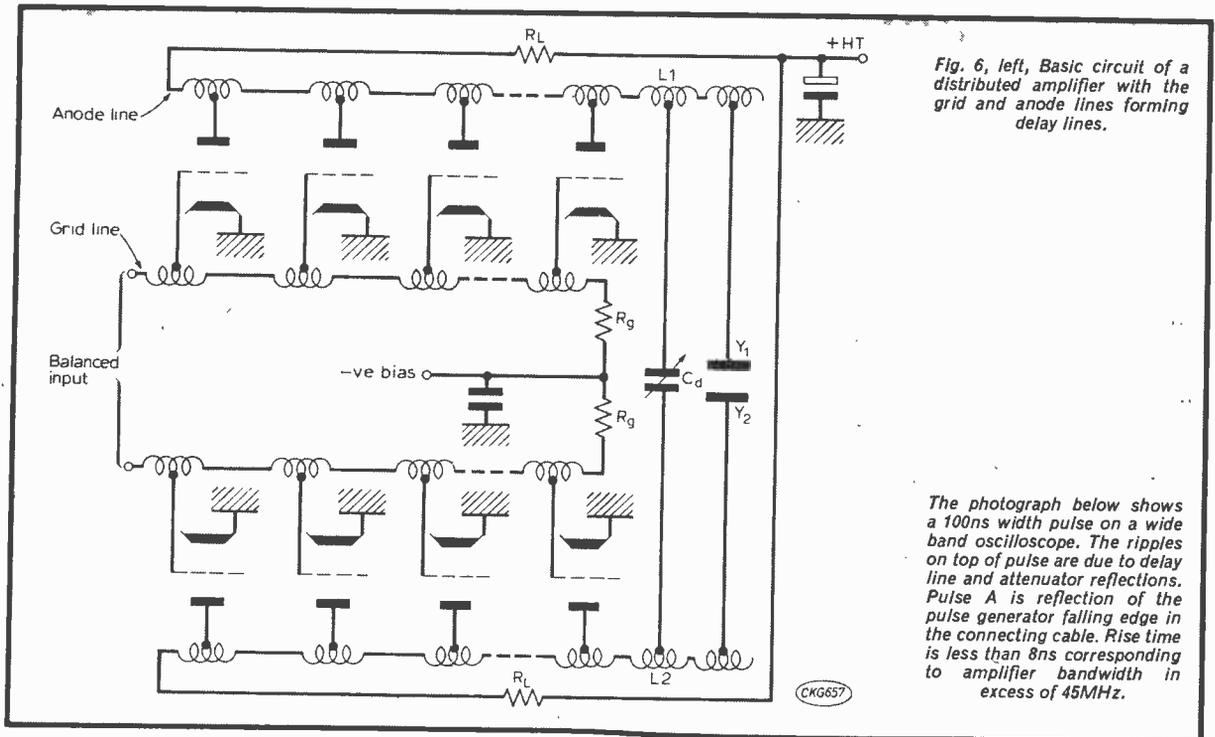


Fig. 6, left, Basic circuit of a distributed amplifier with the grid and anode lines forming delay lines.

The photograph below shows a 100ns width pulse on a wide band oscilloscope. The ripples on top of pulse are due to delay line and attenuator reflections. Pulse A is reflection of the pulse generator falling edge in the connecting cable. Rise time is less than 8ns corresponding to amplifier bandwidth in excess of 45MHz.


By providing trimmers to earth the lines can be tuned to give the same velocities, shown by the best response to a pulse. With a large number of stages, say more than five, then a gaussian fall-off occurs and very good pulse response is possible not limited so much by the valve capacitances as by the adjustment of trimmers.

The value of R_L is such that the wave, reflected at the open circuit CRT end of the line is absorbed on reflection, is therefore equal to the impedance of the line, usually about 250 ohms. R_g similarly loads the grid line to prevent reflections.

L_1 , L_2 and C_d do not form part of the distributed amplifier but show how the anode lines may be extended to form a delay line. The delay line is made up of sections such as this, carefully sealed from dust and terminating in the CRT plate capacitance. The delay obtained may be several hundred nano-seconds, but a usual figure is a total delay of 200ns, 30ns in the distributed amplifier and 170ns in the delay line. Generally about 2 or 3ns delay is given per section (i.e. one L_1 , one L_2 , one C_d).

The delay is used to enable the timebase to start up before the appearance of a fast transient and so triggering is taken from the amplifier driving the grid lines, usually by a cathode follower to minimise loading. The effect of a mistuned delay line is that internal reflections may occur due to changes in impedance and the rise time may suffer. The latter effect is obvious if the rise time is not meeting specification, but the first fault causes a small ripple on the top of a displayed fast square wave (500kHz). The delay line trimmers nearest the CRT plates affect the leading edge and the trimmers further back affect later portions of the pulse.

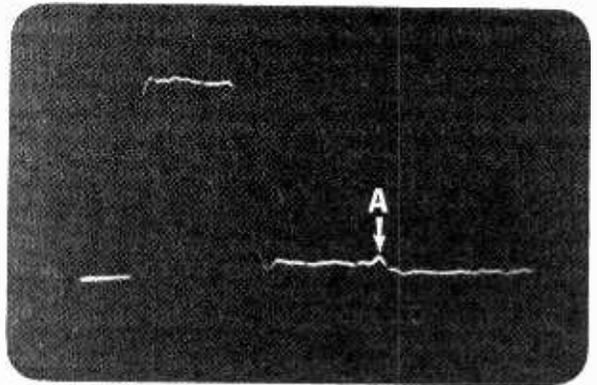If a pulse generated from a reliable generator and correctly terminated shows this type of distortion the first step is to measure the time from the pulse edge to the ripple using the scope timebase calibration.



This time is then halved, because of the reflection, and the number of stages of delay back from the CRT plates is determined from the time per section (found by dividing total delay as quoted in the manual by the number of stages assuming 2.5ns per section). The trimmers in this region can then be touched with a metal screwdriver, taking care not to turn them and the presence of the screwdriver will cause a hump or dip to appear in the top of the displayed 500kHz square wave. The trimmer needing adjustment can be located when the screwdriver increases or decreases the fault. The trimmer is then trimmed with a plastic trimming tool, and all should be well. It is not advisable to play with delay lines as once upset they can take hours or days of hard work to sort out.

FAULTS

Sometimes failure of a valve in the distributed amplifier can give rise to reflections indicating a faulty delay line or distributed amplifier line. Before

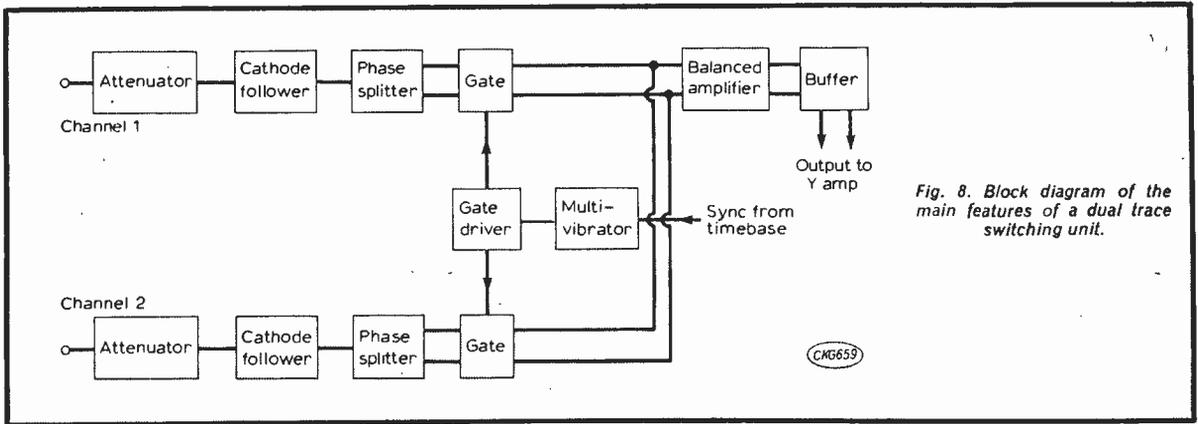


Fig. 8. Block diagram of the main features of a dual trace switching unit.

making any adjustments to the lines it is best to remove each of the amplifier valves in turn. The faulty valve when removed will clear the fault. An ideal pulse to display when making these adjustments is the timebase "bright up" or gating pulse, with the timebase on a suitably fast range. When a valve is replaced in the distributed amplifier it may be necessary to make a small adjustment to that valve's anode trimmer capacitor, and possibly to the trimmers on either side, but not to any more.

It cannot be emphasised too much that the delay line and distributed amplifier should need only small adjustment very rarely indeed. Playing about will only result in hours of work, possibly requiring the scope to be returned to the manufacturers for a major overhaul (probably costing £50 or more).

DELAY LINES

The advantages of a delay line for pulse work are many, the main one being that a signal can trigger the timebase, and then, when it is running, the signal arrives at the Y plates. There are several good scopes around of quite wide bandwidth, but lacking a delay line, and so are limited in their applications to pulse work. However coaxial cable can be used for delay purposes. Standard 70 ohm cable is suitable and has a wave velocity factor of about 0.66. This gives 195m of cable for a 1 μ sec delay or, for the more usual 250ns delay, a cable length of 48m, which can be conveniently bought as a 50m drum of cable and left coiled on the drum.

It is necessary to load the cable at either the scope or source end with a 70 ohm resistor to prevent reflections. In use, one end of the cable is plugged into the scope input socket and the signal is applied at the other end. The timebase is set to external trigger and the trigger lead is connected to the source end of the cable. Fig. 7 shows the general idea which although it seems crude is a useful method of obtaining a constant delay without upsetting the input wave.

BEAM SWITCHING

We have so far considered only a single beam Y deflection system. Often two traces are required simultaneously and the obvious method would be a double beam tube and two Y deflection systems. In the light of the above discussion two distributed amplifiers and delay lines would cost a lot of money and the time taken in adjustment would be enormous,

not to mention 36 Y output valves (9 valves per half section)!

Usually wide band scopes employ beam switching techniques where two signals are displayed

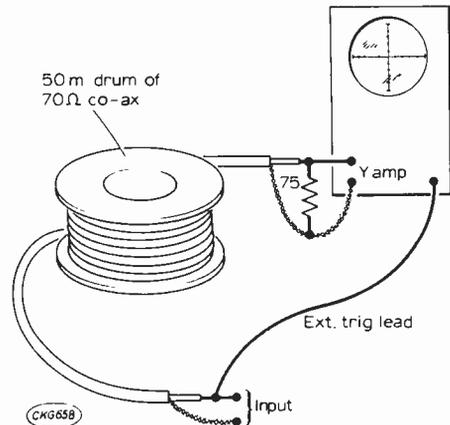


Fig. 7. Set-up using a 50m drum of co-axial cable as a simple delay line.

alternately. The Y amplifier requirements are the same as for single trace operation and so one good amplifier can be built into the main frame and a dual trace plug-in used.

Fig. 8 shows the bare essentials of a dual trace unit the heart of which is the multivibrator. In the simplest mode of operation the multivibrator changes state during each flyback period, triggered by the sync feed. For each scan the multivibrator is in alternate states and the gates alternately open and close. When CH1 gate is open CH2 gate is closed and the CH1 signal is displayed. On the next scan CH2 is displayed and so on. By manipulating the separate shift controls two separate traces are seen.

At fairly low timebase sweep rates the traces are seen to alternate and this is known as the "alternate" mode or just ALT. To overcome the flicker the multivibrator can be free run at 100kHz or so. Thus CH1 and CH2 signals are displayed in quick succession. This method, called CHOP is useful at all sweep speeds but especially at low sweep speeds where the ALT mode produces flicker. The display is simultaneous in real time up to the switching speed, but sometimes beat effects occur with the switching waveform and in these cases ALT is used.

To be continued

Mc Murdo PP10 and PS10 10way edge plugs and sockets with cover ex brand new equipment 25p.

Mc Murdo B11A Nylon Valveholder or Relay Base. Ex brand new equipment 10p.

Flexible Connecting Wire, assorted colours. 100 yards for £1.00.

Eddystone Die-Cast Boxes with Lid 4 1/2" x 2 1/2" x 1 1/2" 50p.

Brand New Wire-Wound Resistors 1-7 watts. Good selection. 100 for £1 0p. & p. 15p.

Assorted Capacitors, Silver Mica, Tubular and Disc Ceramics, Polystyrene. Tremendously good selection. 300 for £1.00. p. & p. 20p.

Mullard Pot Cores LA3 50p, LA4 75p, LA2100 50p.

Rotary Switch 1 pole, 14 way, 3 bank, good quality, excellent value 35p.

Colvern W/Wound Potentiometer Splndle Type 10 ohms 35p.

Add 10% VAT to total order.

MAIL ORDER ONLY

XEROZA RADIO


1 EAST STREET, BISHOPS TAWTON, DEVON

PROJECT CASES

ALL ALUMINIUM EASIER TO WORK SIDE AND TOP RICH BLUE HAMMER FINISH FACIA MATT BLACK, SILVER or BRUSHED FEET and four Vero P.C.B. 'snap in' fixing posts with each case.

Sizes in inches

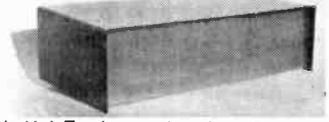2 x 8 x 4 £1.20
2 x 10 x 6 £1.50
3 x 10 x 6 £1.75
4 x 10 x 6 £2.00



All prices include V.A.T. plus post and packing.

SOUND SYSTEMS

30 FOXHOLES ROAD, BOURNEMOUTH

YATES ELECTRONICS

(FLITWICK) LTD.

DEPT PW, ELSTOW STORAGE DEPOT
KEMPSTON HARDWICK
BEDFORD

C.W.O. PLEASE. POST AND PACKING PLEASE ADD 10p TO ORDERS UNDER £2.

Catalogue which contains data sheets for most of the components listed will be sent free on request. 10p stamp appreciated.

Callers Welcome Mon. to Sat. 9 a.m. 5 p.m.

PLEASE ADD 10% VAT

RESISTORS

1/2W Iskra high stability carbon film—very low noise—capless construction.
1/2W Mullard CR25 carbon film—very small body size 7.5 x 2.5 mm.
1/2W 2% ELECTROSIL TR5.

Power watts	Tolerance	Range	Values available	Price
1/2	5%	4.7Ω-2.2MΩ	E24	100+
1/2	10%	3.3MΩ-10MΩ	E12	1p
1/2	2%	10Ω-1MΩ	E24	0.9p
1/2	10%	1Ω-3.9Ω	E12	0.9p
1/2	5%	4.7Ω-1MΩ	E12	1p
1/2	10%	1Ω-10Ω	E12	0.9p
4	10%	1Ω-10Ω	E12	5.5p

Quantity price applies for any selection. Ignore fractions on total order.

DEVELOPMENT PACK

0.5 watt 5% Iskra resistors 5 off each value 4.7Ω to 1MΩ.
E12 pack 325 resistors £2.40. E24 pack 650 resistors £4.70.

POTENTIOMETERS

Carbon track 5kΩ to 2MΩ, log or linear (log 1/2W, lin 1/2W).
Single. 12p. Dual gang (stereo), 40p. Single D.P. switch, 24p.

SKELETON PRESET POTENTIOMETERS

Linear: 100, 250, 500Ω and decades to 5MΩ. Horizontal or vertical P.C. mounting (0.1 matrix).
Sub-miniature 0.1W, 5p each. Miniature 0.25W, 7p each.

TRANSISTORS

AC107	15p	AF126	20p	BF115	25p	OC42	12p	2N3707	12p
AC126	12p	AF139	32p	BF173	20p	OC44	12p	2N3708	10p
AC127	15p	AF178	32p	BF177	28p	OC45	12p	2N3709	11p
AC128	15p	AF180	40p	BF178	32p	OC70	12p	2N3710	11p
AC131	12p	AF181	40p	BF179	32p	OC71	12p	2N3711	11p
AC132	12p	BC107	12p	BF180	32p	OC72	12p	2N3819	32p
AC176	15p	BC108	12p	BF81	32p	OC81	12p	2N4062	12p
AC187	22p	BC109	12p	BF194	14p	OC82	12p	2N4286	20p
AC188	22p	BC147	12p	BF195	14p	2N2646	60p	2N4289	20p
AD140	50p	BC148	12p	BF197	15p	2N2904	20p	40360	35p
AD149	45p	BC149	12p	BF200	32p	2N2926	10p	40361	35p
AD161	33p	BC157	14p	BFY50	20p	2N3054	58p	40362	40p
AD162	36p	BC158	14p	BFY51	20p	2N3055	60p	40408	40p
AF114	20p	BC159	14p	BFY52	20p	2N3702	13p	ZTX108	15p
AF115	20p	BC187	22p	BU105	225p	2N3703	12p	ZTX300	15p
AF116	20p	BD131	75p	OC26	45p	2N3704	13p	ZTX302	20p
AF117	20p	BD132	75p	OC28	50p	2N3705	12p	ZTX500	15p
AF118	38p	BD133	75p	OC35	50p	2N3706	11p	ZXT503	20p

ZENER DIODES

400mW 5% 3.3V to 30V, 12p.

WIRE WOUND POTS. 3W, 10, 25, 50Ω and decades to 100kΩ, 45p.

DIODES

RECTIFIER	VOLTS	CURRENT	SIGNAL	PRICE
BY127	1250V	1A	OA85	7p
IN4001	50V	1A	OA90	5p
IN4002	100V	1A	OA91	7p
IN4004	400V	1A	OA202	7p
IN4006	800V	1A	IN4148	8p
IN4007	1000V	1A	BA114	8p

SLIDER POTENTIOMETERS

86mm x 9mm x 16mm, length of track 59mm.

DUAL GANG, 10K + 10K etc. log. or lin. 60p.

KNOB FOR ABOVE, 12p.

FRONT PANEL, 65p.

18 Gauge panel 1 1/2in x 4in with slots cut for use with slider pots. Grey or matt black finish complete with fixings for 4 pots.

THYRISTORS

2N5060 50V 0.8A 65p
2N5064 200V 0.8A 80p
106F 50V 5A 85p
106D 400V 5A 80p

MULLARD POLYESTER CAPACITORS C280 SERIES

400V: 0.001μF, 0.0015μF, 0.0022μF, 0.0033μF, 0.0047μF, 21p, 0.0068μF, 0.01μF, 0.015μF, 0.022μF, 0.033μF, 0.047μF, 3p, 0.047μF, 0.068μF, 0.1μF, 4p, 0.15μF, 6p, 0.22μF, 7p, 0.33μF, 11p, 0.47μF, 13p.
160V: 0.01μF, 0.015μF, 0.022μF, 0.033μF, 0.047μF, 0.068μF, 3p, 0.1μF, 3p, 0.15μF, 4p, 0.22μF, 5p, 0.33μF, 6p, 0.47μF, 7p, 0.68μF, 11p, 1.0μF, 13p.

MULLARD POLYESTER CAPACITORS C280 SERIES

250V P.C. mounting: 0.01μF, 0.015μF, 0.022μF, 0.033μF, 0.047μF, 0.068μF, 3p, 0.1μF, 4p, 0.15μF, 5p, 0.22μF, 6p, 0.33μF, 7p, 0.47μF, 8p, 0.68μF, 11p, 1.0μF, 13p, 1.5μF, 20p, 2.2μF, 24p.

MYLAR FILM CAPACITORS 100V

0.001μF, 0.002μF, 0.005μF, 0.01μF, 0.02μF, 21p, 0.04μF, 0.05μF, 0.068μF, 0.1μF, 31p.

CERAMIC DISC CAPACITORS

100pF to 10,000pF, 2p each.

ELECTROLYTIC CAPACITORS

(μF/v) 1/63, 1.5/63, 2.2/63, 3.3/63, 4.7/63, 6.8/40, 6.8/63, 10/25, 10/63, 15/16, 15/40, 15/63, 22/10, 22/25, 22/63, 33/6.3, 33/16, 33/40, 47/4, 47/10, 47/25, 47/40, 68/6.3, 68/16, 100/4, 100/10, 100/25, 150/16, 150/6.3, 150/16, 220/4, 220/6.3, 220/16, 330/4, 6p, 47/63, 100/40, 150/25, 220/25, 330/10, 470/6.3, 7p, 68/63, 150/40, 220/40, 330/16, 1000/4, 10p, 470/10, 680/6.3, 11p, 100/63, 150/63, 220/63, 1000/10, 12p, 470/25, 680/16, 1500/6.3, 13p, 470/40, 680/25, 1000/16, 1500/10, 2200/6.3, 18p, 330/63, 680/40, 1000/25, 1500/16, 2200/10, 3300/6.3, 4700/4, 21p.

SOLID TANTALUM BEAD CAPACITORS

Value	Price	Value	Price	Value	Price
0.1μF 35V	2.2μF 35V	22μF 16V	10p		
0.22μF 35V	4.7μF 35V	33μF 10V	10p		
0.47μF 35V	6.8μF 25V	47μF 6.3V	10p		
1.0μF 35V	10μF 25V	100μF 3V	10p		

VEROBOARD

Size	Price
2 1/2 x 3 1/2	0.1
2 1/2 x 5	22p
3 1/2 x 3 1/2	16p
3 1/2 x 5	24p
4 1/2 x 5	24p
17 x 2 1/2	27p
17 x 3 1/2	75p
17 x 5	57p
17 x 5 (plain)	100p
17 x 3 1/2 (plain)	82p
17 x 2 1/2 (plain)	60p
2 1/2 x 5 (plain)	42p
2 1/2 x 3 1/2 (plain)	12p
Pin insertion tool	52p
Spot face cutter	52p
Pkt. 50 pins	42p
	20p

JACK PLUGS AND SOCKETS

Standard screened	28p	2.5mm insulated	12p
Standard insulated	18p	3.5mm insulated	12p
Stereo screened	40p	3.5mm screened	18p
Standard socket	20p	2.5mm socket	11p
Stereo socket	30p	3.5mm socket	11p

D.I.N. PLUGS AND SOCKETS

2 pin, 3 pin, 5 pin 180°, 5 pin 240°, 6 pin, 7 pin
Plug 12p. Socket 8p.
4 way screened cable, 25p/metre.
6 way screened cable, 30p/metre.

BATTERY ELIMINATOR

£1.50
9V mains power supply. Same size as PP9 battery.

LARGE (CAN) ELECTROLYTICS

1600μF 64V 74p
2500μF 40V 74p
2500μF 50V 58p
2500μF 64V 80p
2800μF 100V £3.20
3200μF 16V 50p
4500μF 16V 50p
4500μF 25V £1.68
5000μF 50V £1.10

HIGH VOLTAGE TUBULAR CAPACITORS—1,000 VOLT

0.01μF 10p
0.022μF 12p
0.047μF 13p
0.1μF 13p
0.22μF 20p
0.47μF 22p

POLYSTYRENE CAPACITORS 160V 2 1/2p

10pF to 1,000pF E12 Series Values, 4p each.

SMOKE AND COMBUSTIBLE GAS DETECTOR—GDI

The GDI is the world's first semiconductor that can convert a concentration of gas or smoke into an electrical signal. The sensor decreases its electrical resistance when it absorbs deoxidizing or combustible gases such as hydrogen, carbon monoxide, methane, propane, alcohol, North Sea gas, as well as carbon-dust containing air or smoke. This decrease is usually large enough to be utilized without amplification. Full details and circuits are supplied with each detector.

Detector GDI, £2. Kit of parts for detectors including GDI and P.C. board but excluding case. Mains operated detector £3.20, 12 or 24V battery operated audible alarm £7.30. As above for PP9 battery, £6.40.

PRINTED BOARD MARKER

97p
Draw the planned circuit onto a copper laminate board with the P.C. Pen, allow to dry, and immerse the board in the etchant. On removal the circuit remains in high relief.

ALL OUR PRICES INCLUDE V.A.T.

BSR LATEST SUPERSLIM

STEREO AND MONO

Plays 12", 10" or 7" records. Auto or Manual. A high quality unit backed by BSR reliability with 18 months' guarantee. AC 200/250V. Size 13 1/2 x 11 1/2 in. Above motor board 3 1/2 in. Below motor board 2 1/2 in. With STEREO and MONO XTAL



£6.75 Post 35p.

PORTABLE PLAYER CABINET

Modern design. Black zinc covered silver front grille. Chrome fittings. Motor board cut for BSR deck.

£4.50 Post 25p.

COMPACT PORTABLE STEREO HI-FI

Two full size loudspeakers 1 1/2 x 10 x 3 1/2 in. Player unit clips to loudspeakers making it extremely compact. Overall size only 11 1/2 x 10 x 3 1/2 in. 3 watts per channel, plays all records 33 rpm, 45 rpm. Separate volume & tone controls. 240V AC mains.



Attractive Teak finish Weight 13lbs. Bargain Price **£25** 85p carriage

SPECIAL OFFER

SMITH'S CLOCKWORK 15 AMP

TIME SWITCH 0-40 MINUTES Single pole two-way. Surface mounting with fixing screws. Will replace existing wall switch to give light for return home, garage, automatic anti-burglar lights, etc. Variable knob. Turn on or off at full or intermediate settings. Makers last list price £4.50. Brand new and fully guaranteed. Fully insulated. **OUR PRICE £1.95** Post 25p



WEYRAD P50—TRANSISTOR COILS

RA2W Ferrite Aerial. 85p Driver Trans. LFDTA. 65p Osc. P50/LAC. 40p I.F. P50/2CC 470 kc/s. 40p 3rd I.F. P50/3CC. 40p Spare Cores. 8p OPT1. 20p OPT2. 65p Ferrite Rod 8 x 1/2 in. 20p x 1/2 in. 10p

VOLUME CONTROLS

5 K. ohms to 2 Meg. LOG or LIN. L/S 15p. D.P. 25p. STEREO L/S 55p. D.P. 75p. Edge 5K.S.P. Transistor 25p

80 Ohm Coax 5p. yd. BRITISH AERIALITE AERIAL-AIR SPACED 40 yd. £1.40; 60 yd. 23p. FRINGE LOSS LOSS Ideal 625 & colour 10p yd.

8in & 10 x 6in ELAC

HI-FI SPEAKER

Dual cone plasticised roll surround. Large ceramic magnet. 50-16,000 c/s. Bass resonance 55 c/s. 8 ohm impedance. Sin. 10 watt.



£3.75 Each Post 25p

E. M. I. 13 1/2 x 8in.

SPEAKER SALE!

With twin tweeters and crossover, 10 watt. State 3 or 8 or 15 ohm. (As illustrated) Post 25p



£4.50

With flared tweeter cone and ceramic magnet, 10 watt.

Bass res. 45-50 c/s. Flux 10,000 gauss. State 3 or 8 or 15 ohm. Post 25p



£2.75

BOOKSHELF CABINET

Size 16 x 10 x 8 in. teak finish **£6.60** Post 25p

SET OF 3 MOTORS FOR COLLARO STUDIO, 115 VOLT

TAPE DECK £2.50 Post 50p.

BLANK ALUMINIUM CHASSIS. 18 s.w.g. 2 1/2 in. sides 6 x 4 in. 45p; 8 x 6 in. 55p; 10 x 7 in. 65p; 12 x 8 in. 85p; 14 x 9 in. 90p; 16 x 8 in. 90p; 12 x 8 in. 50p; 16 x 10 in. £1. ALUMINIUM BOXES 3 x 9 x 3 in. 60p; 4 x 4 x 4 in. 70p; 6 x 4 x 4 in. 80p; 9 x 4 x 4 in. £1; 12 x 4 x 4 in. £1.30. ALUMINIUM PANELS 18 s.w.g. 6 x 4 in. 12p; 8 x 6 in. 19p; 10 x 8 in. 20p; 10 x 7 in. 24p; 12 x 6 in. 25p; 12 x 8 in. 34p; 16 x 8 in. 34p; 14 x 8 in. 40p; 12 x 12 in. 47p; 16 x 10 in. 60p. PAXOLIN PANEL 10 x 8 in. 20p.

SPECIAL OFFER

3 INCH PANEL METRE 50 MICRO AMPS, UNUSUAL SCALE REQUIRES RECALIBRATING **£1.75** Post 20p

ANOTHER RCS BARGAIN!

ELAC 9 x 5 in. HI-FI SPEAKER. TYPE 59RM. THIS FAMOUS AND WIDELY USED UNIT NOW AVAILABLE AT BARGAIN PRICE £3.30. 10 WATT, 8 OHM. CERAMIC MAGNET.

R.C.S. STABILISED POWER PACK KITS

All parts and instructions with Zener Diode, Printed Circuit, Bridge Rectifiers and Double Wound Mains Transformer. Input 200/240V a.c. output voltages available 6 or 9 or 12 or 15 or 18 or 20V d.c. at 100mA or less. PLEASE STATE VOLTAGE REQUIRED. **£2.20** Post 20p Details S.A.E. Size 3 1/2 x 1 1/2 in.

R.C.S. GENERAL PURPOSE TRANSISTOR PRE-AMPLIFIER BRITISH MADE

Ideal for Mike, Tape, P.T., Guitar, etc. Can be used with Battery 9-12v. or H.T. line 200-300V. d.c. operation. Size 1 1/2 x 1 1/2 x 1 1/2". Response 25 c/s. to 25 Kc/s. 25 dB gain. For use with valve or transistor. **99p** Post Full instructions supplied. Details S.A.E. 20p

E.M.I. WOOFER AND TWEETER KIT

Wooler 10 1/2 x 6 1/2 in. Ceramic Magnet, 440z. 13,000 lines. Tweeter 3 1/2 in. square, 10,000 lines. Crossover condenser full instructions supplied. Impedance 8 ohms. Power 12 watts. **£6.75** Post 45p.

BRITISH FM/VHF TUNING HEART

88 to 108 Mc/CS British made. 2 Transistors ready aligned requires 10-7 M/CS I.F. Complete with tuning gang. Connections supplied but some technical experience essential. **Our price £3.95** Post 20p

MAINS TRANSFORMERS

All post 25p each
Eagle MT12 12-0-12V 50mA 80p
250-0-250 80 mA. 6-3V 2-5A 6-3V 1A or 5V 2A £2.50
350-0-350 80 mA. 6-3V 2-5A. 6-3V 1A or 5V 2A £2.00
300-0-300V 120mA. 6-3V 4A C.T. 6-3V 2A £2.25
MINTA TUBE 200V 20mA. 6-3V 1A 2 1/2 x 2 1/2 x 2 1/2 in. 75p
MIDGET 220V 45mA. 6-3V 2A 2 1/2 x 2 1/2 x 2 1/2 in. 90p
HEATER TRANS. 6-3V 3A 75p
GENERAL PURPOSE LOW VOLTAGE. Trapped outputs at 2 amp. 3, 4, 5, 6, 8, 9, 10, 12, 15, 18, 24 and 30V 23-00
1 amp. 6, 8, 10, 12, 15, 18, 20, 24, 30, 36, 40, 48, 60 23-00
3 amp. 6, 8, 10, 12, 15, 18, 20, 24, 30, 36, 40, 48, 60 24-00
5 amp. 6, 8, 10, 12, 15, 18, 20, 24, 30, 36, 40, 48, 60 29-75
5, 8 and 13V 5 amp £1.20. 3 amp. 3, 5, 8, 10, 13 and 5-0-5V 21.30. Dittos 5 amp. £1.80; 8-0-8V 500mA 90p
9V 1 amp 99p 12V 300mA 75p 12V 500mA 85p 12V 750mA 95p. 40V 1 amp £1.75
AUTO TRANSFORMERS, 115V to 230V or 230V to 115V 150W £2.25; 500W £2.25; 750W £1.10; 1000W £1.5
CHARGER TRANSFORMERS. Input 200/250V for 6 or 12V, 1 amp £1.50; 2 amp £1.80; 4 amp £2.80
BATTERY CHARGERS. Ready built with leads and clips 11 amp 22; 4 amp 24; 5 amp 24.50
FULL WAVE BRIDGE CHARGER RECTIFIERS: 6 or 12V outputs. 11 amp 40p; 2 amp 55p; 4 amp 85p.

MAINS ISOLATING TRANSFORMER

Primary 0-110-240V. Secondary 0-240V. 2A. 720W. Insulated terminals. Varnish impregnated. Fully enclosed in steel case with fixing feet. **OUR PRICE £10** Carr. 50p Famous make. (Value £19)
Can be used as 800W auto transformers 240-110V. IDEAL FOR COLOUR T.V. OR GARDEN TOOLS.

NEW ELECTROLYTIC CONDENSERS

2/350V .. 14p	100/25V .. 10p	32+32/350V .. 40p
4/350V .. 14p	250/25V .. 15p	50+50/350V .. 40p
6/450V .. 15p	500/25V .. 20p	60+100/350V .. 85p
15/450V 25p	1000/25V .. 35p	32+32/250V .. 20p
32/450V 35p	1000/50V .. 47p	32+32/450V .. 60p
32/500V 50p	8+8/450V .. 25p	350+50/325V .. 55p
25/25V .. 10p	8+16/450V 25p	32+32+32/350V 65p
60/50V .. 10p	16+16/450V 40p	32+32+32/450V 85p

LOW VOLTAGE ELECTROLYTICS

1, 2, 4, 5, 8, 16, 25, 30, 50, 100, 200mF. 15V. 10p.
500mF. 12V. 15p; 25V. 20p; 50V. 30p.
1000mF. 12V. 20p; 25V. 35p; 50V. 47p; 100V. 70p.
2000mF. 8V. 25p; 25V. 12p; 50V. 87p.
2500mF. 50V. 62p; 5000mF. 25V. 47p; 50V. 65p.
5000mF. 6V. 25p; 12V. 42p; 25V. 75p; 35V. 85p; 50V. 95p.

CERAMIC 1pF to 0.01mF, 4p. Silver Mica 2 to 5000pF. 4p. PAPER 350V-0.1 4p. 0.5 12p; 1mF 15p; 2mF 150V 15p. 500V-0-01 to 0-05 4p; 0-1 5p; 0-25 5p; 0-47 25p. SILVER MICA. Close tolerance 1% 2-2-500pF 5p; 500-2-200 pF 10p; 2-700-5-600pF 20p; 6-800pF-0-01, mid 30p; each TWIN GANG. "0-0" 208pF = 176pF. 85p; 600pF standard 75p; 365+365 with 25+25pF Slow motion drive 50p. SERRA WAVE SINGLE. 10pF 20p; 25pF 55p; 50pF 55p. NEON PANEL INDICATORS. 250V AC/DC Amber 20p. RESISTORS. 1W, 1W, 1W, 20%; 1/2W, 5p, 10 to 10M. HIGH STABILITY. 1 w. 2% 10 ohms to 6 meg., 10p. Dittos 5% Preferred values 10 ohms to 10 meg., 4p. WIRE-WOUND RESISTORS. 5 watt, 10 watt, 15 watt 10 ohms to 100K 10p each; 0.5 ohm to 3-2 ohm 10p. TAPE OSCILLATOR COIL. Valve type 35p.

NEW MODEL "BAKER LOUDSPEAKER" 12in. 50 watt GROUP 50/12 8 or 15 ohm high power full range. Professional quality. £17.60

BAKER MAJOR 12" £9.90

30-14,500 c/s. Post free cone, woofer and tweeter cones together with a BAKER ceramic magnet assembly having a flux density of 14,000 gauss and a total flux of 145,000 Maxwells. Bass resonance 40 c/s Bated 20 watts. NOTE: 3 or 8 or 15 ohms must be stated. Module kit, 30-17,000 c/s with tweeter, crossover, baffle and instructions. **£12.50** Post free Please state 3 or 8 or 15 ohms.

BAKER "BIG-SOUND" SPEAKERS

'Group 25'	'Group 35'	'Group 50'
12 inch £8.80	12 inch £9.90	15 inch £22
35 watt	35 watt	50 watt
3 or 8 or 15 ohm	3 or 8 or 15 ohm	8 or 15 ohm

TEAK VENEERED HI-FI SPEAKER CABINETS For 12in. or 10in. dia. speaker 20 x 13 x 6in. £9.90 Post 25p For 13 x 6in. or 8in. speaker 16 x 10 x 6in. £5.50 Post 25p For 8 x 5in. speaker 16 x 8 x 6in. £4.40 Post 25p For 6in. and tweeter 12 x 8 x 6in. £4.00 Post 25p LOUDSPEAKER CABINET WADDING 18in. wide, 15p ft

EMI 6 1/2 in. HI-FI WOOFER

8 ohm, 10 watt. Large ceramic magnet. Special Rubber cone surround. Frequency response 30-12,000 c/s. Ideal P.A. Columns, etc. Hi-Fi Enclosure Systems, etc. Suitable cabinet 12 x 8 x 6 1/2 in. Suitable Tweeter £2.00.

ELAC CONE TWEETER

The moving coil diaphragm gives a good radiation pattern to the higher frequencies and a smooth extension of total response from 1,000 c/s to 18,000 c/s. Size 3 1/2 x 3 1/2 in. deep. Rating 10 watt, 3 ohm Suitable **£1.90** Post 20p Crossover £1.30

SPEAKER COVERING MATERIALS. Samples Large S.A.E.

Horn Tweeters 2-16kc/s, 10W 5 ohm or 15 ohm £1.95. CROSSOVERS TWO-WAY 3000cps 8 or 8 or 15 ohm £1.30 LOUDSPEAKERS 3 OHMS. 7 x 4in. £1.25; 6in. £1.60. 8 x 5in. £1.60 8in. £1.75; 10 x 4in. £1.90; 10in. £2.00. SPECIAL OFFER: 80 ohm, 2 1/2in.; 2 1/2in. 35 ohm, 2 1/2in.; 2 1/2in. 25 ohm, 2 1/2in. dia.; 5in. dia., 6" x 4" £1 RACH TYPES 16 ohm, 3 1/2in. dia.; 8 x 4in.; 7 x 4in.; 8 x 5in. 8 ohm, 3 1/2in.; 2 1/2in.; 3 1/2in. dia.; 6 x 4in. 8 ohm £1.50 RICHARD ALLAN TWIN CONE LOUDSPEAKERS. 8 in. diameter 4 watt £2.50. 10in. diameter 5 watt £2.50; 12 in. diameter 6 watt £2.95. VALVE OUTPUT TRANS. 40p; MIKE TRANS. 50:1 40p. 5 WATT MULTI-RATIO, 3, 8 and 15 ohms. 80:1. Mike trans. mu metal 100:1 £1.25.

MAJOR 100 WATT ALL PURPOSE GROUP AMPLIFIER

All purpose transistorised. Ideal for Groups, Disco and P.A. 4 inputs speech and music. 4 way mixing. Output 8/15 ohm. a.c. Mains. Separate treble and bass control. **£49** Carr. £1.00 SUPER VALVE MODEL 100 WATT CALLERS ONLY £69.

BARGAIN AM TUNER. Medium Wave. £4.95

Bargain Superhet. Ferrite aerial. 9 volt.

BARGAIN 4 CHANNEL TRANSISTOR MONO MIXER. £4.50

Add musical highlights and sound effects to recordings. Will mix Microphone, records, tape and tinner with separate controls into single output. 9 volt.

TWO CHANNEL STEREO VERSION £5.95

BARGAIN 3 WATT AMPLIFIER. 4 Transistor. £4.50

Push-Pull Ready built, with volume, treble and bass controls 18v. DC operation.

COAXIAL PLUG 10p. PANEL SOCKETS 10p. LINE 17p

COAXIAL OUTLET BOXES, surface, 35p. BALANCED TWIN FEEDER 300 ohms 5p yard. JACK Chrome Lead Socket 45p. Phone Plug 5p. Phone Socket 5p. JACK PLUGS 8d. Chrome 20p; 3-5mm Chrome 12p. DIN SOCKETS Chassis 3-pin 10p; 5-pin 10p. DIN SOCKETS Lead 3-pin 18p; 5-pin 25p. DIN PLUGS 3-pin 15p; 5-pin 25p. VALVE HOLDERS. 5p; CERAMIC 10p; GANS 5p.

REVERSIBLE 4 POLE MOTOR £1.95

1,400 r.p.m. Reversible 42 Watt. Post 25p spindle 1 1/2 x 7/32 in. size 3 1/2 x 8". As illustrated. With Cooling Fan 240V A.C.

E.M.I. GRAM MOTOR £1.00

120v. or 240V. A.C. 2,400 rpm. 2-pole 70mA. Size 2 1/2 x 2 1/2 in. Post 25p.

RADIO COMPONENT SPECIALISTS 337 WHITEHORSE ROAD, CROYDON

Minimum post 10p. Illustrated Brochure, Radio Books & Components Lists 10p. Open 9-6 Wed. 9-1 Sat. 9-5 (Closed for lunch 1.15-2.30) Buses 50, 68, 159. Rail Selhurst. Tel. 01-684 1665



BROADCAST BANDS

SHORT WAVE DX by MALCOLM CONNAH

TO those of you have not been up in the loft for some time I would suggest that you nip up there a bit sharpish and have a look round. This all stems from the mention in the March column that **Richard Staples** had found an Eddystone 680X in his loft.

Shortly after publication of that issue I received a letter from **H. B. Sheward** of Tavistock in Devon who wrote: "Knowing I would not be so lucky (as **Richard Staples**) I ventured into my loft with the aid of a ladder on Sunday last and came up with the following odd items:—BC1147A, Heathkit VF1, Heathkit HG 10, R109, No. 62 set, No. 38 set, No. 18 set, No. 19 set, No. 22 set, PCR 1, Class D Wavemeter, R103, No. 52 set, B23, several vintage sets and, wait for it, a Hallicrafters S120 and a Hammarlund HQ 140 X."

With that little lot Mr. Sheward could almost open a shop. I do not suggest that you will all be as lucky but if you live in a fairly elderly house there could well be an old piece of radio equipment in the loft which could be put to better use.

Readers' Logs

The first log this month comes from **John Spinks** of Norwich who has been concentrating on the 60 metre band. This concentration plus a Trio 9R-59DS, 75 foot long-wire and an A.T.U. produced the following excellent results:

- 4790 *Springbok Radio, South Africa* at 2135.
- 4800 *R. Lara, Venezuela*, heard at 2348.
- 4825 *Moscow, news in Russian* at 2030.
- 4860 *AIR, Delhi*, chanting at 2110.
- 4880 *R. Peking* in Chinese at 2155.
- 4900 *R. Juventud, Ven.*, in Spanish at 0040.
- 4904 *Fort Lamy, Chad Rep.*, in French at 2035.
- 4905 *R. Relogio, Brazil*, pop music at 0020.
- 4930 *Majek, USSR*, in Russian & English at 2130.
- 4940 *Frunz, USSR*, Russian opera at 2115.
- 4972-5 *R. Yaounde, Cameroon* in French at 2150.
- 4980 *R. Ghana*, African news at 2105.
- 4980 *Ecos del Torbes, Ven.*, heard at 0001.
- 4990 *Lagos, Nigeria*, sports news at 2230.
- 5010 *R. Garoua, Cameroon*, French talk at 2205.

5030 *R. Continente, Ven.*, music at 0034.

5035 *R. Alma Ata, USSR*, Russian talk at 0040.

Paul Broadhurst, who lives near Bristol, used his Trio 9R-59DS with a 150 foot long-wire and 19 metre dipole to hear the following stations:

6025 *R. Lisbon, Portugal* noted at 2045.

6050 *Rome, Italy* sign on at 2030.

6070 *R. Sofia, Bulgaria*, sign on at 1600.

6150 *R. Belgrade, Yugoslavia* at 2020.

6160 *Brussels, Belgium* noted at 2315.

6165 *R. Kiev*, noted at 1940.

6190 *Vatican Radio* noted at 2050.

7195 *AIR, Delhi* at 2200.

9550 *Radio Finland*, sign on at 2030.

9610 *R. Canada Int.*, sign on at 2058.

9735 *VOA, Monrovia, Liberia* at 2120.

9760 *Accra, Ghana* noted at 2115.

11880 *Voice of Turkey* noted at 2200.

15120 *Voice of Nigeria* noted at 1620.

15155 *RSA, South Africa*, sign on at 1800.

15300 *HCJB, Quito, Ecuador* at 2010.

15425 *Vienna, Austria* noted at 1840.

Steve Davis of Hanworth in Middlesex has a Satellit 6001 receiver and 10 metre dipole enabling him to hear:

3985 *SBC, Berne* in English at 1530.

5000 *WWV, Colorado, USA* at 0900.

5000 *IBF, Turin, Italy* at 1000.

6155 *Vienna, Austria* in English at 1830.

9480 *R. Tirana, Albania* in English at 1630.

9505 *R. Prague* in English at 1500.

11720 *R. Nacional, Brazil* in English at 2300.

15130 *Kol Israel* in English at 1130.

15415 *R. Kuwait* in English at 1730.

21525 *WYFR, USA* noted at 1600.

Don Kelly of Co. Cork in Eire used his B40 receiver to hear the following stations:

9535 *SBC, Berne* in English at 1100.

9550 *R. Norway* in English at 1400.

11755 *R. Finland* in English at 1405.

11765 *Deutsche Welle* in English at 1700.

11835 *R. Sudan* noted at 1600.

11855 *R. Prague* in English at 1545.

11940 *R. Bucharest* in English at 1300.

15165 *R. Denmark* noted at 1400.

15250 *RSA, South Africa* noted at 1700.

15440 *WYFR, USA* at 1800.

Mr. M. C. Smith of Blackpool has a 'PW' 9/12 receiver, an A.T.U. and an 80 foot long-wire, this set up enabling him to hear:

6055 *R. Australia* in English at 2100.

7065 *R. Tehran, Iran* in English at 1637.

7145 *R. Australia* in English at 1500.

9005 *R. Tehran, Iran* in English at 2000.

11765 *R. Australia*, sign off at 1230.

11790 *R. Australia* in Thai at 1330.

17935 *R. Pakistan* noted at 0830.



MEDIUM WAVE BROADCASTS by CHARLES MOLLOY

BRENDON McNAMEE (Portrush, N. Ireland) has a Sharp BZ-23 portable receiver with internal ferrite rod aerial and he reports daytime reception of BBC Radio Blackburn on 854kHz at 1355hrs; Radio Merseyside 1484kHz at 1200hrs; Radio Clyde 1151kHz at 1100hrs. After dark Brendon has logged Radio Bristol 1546kHz at 1905hrs and Trans World Radio, Montecarlo at 2300hrs. **Christopher Beaver** (Stoke-on-Trent) is another local radio enthusiast. With his GEC domestic radio and selection of four 50ft outdoor antennas he has heard Radio Solent on 998kHz; Radio Birmingham on 1457kHz; Radio Manchester on 1457kHz; London Broadcasting on 719kHz; Manx Radio (Isle of Man) on 1594kHz. Christopher has received verifications (QSLs) from BBC local radio stations at Blackburn, Stoke, Nottingham, Bristol, Teesside and Leicester.

P. Grace (Belfast) refers to the enquiry in the February issue of Practical Wireless about White's Radio Log and mentions that it now appears in Communications World which is published in the United States by Science and Mechanics. White's Radio Log contains listings of AM-FM-TV-SW stations in Canada and the United States.

VHF/FM DXING

by SIMON DAVID

HOW many of you had a bumper bundle on Sunday 20th January? An example of what I mentioned last month, propagating conditions in the upper atmosphere, caused some fascinating things to happen. A tropospheric opening occurred for a few days starting on the 18th. On the 19th we thought that France had moved into England and on the 20th and 21st we were truly "in Europe".

Straight after writing last month's column, **E. W. Earnshaw, G3ZXN**, of Newcastle-on-Tyne wrote to me. "FM DXing is not impossible from the North of England", he writes. He picked up a number of German and French stations plus—wait for it—Spain, Yugoslavia and, would you believe, Ankara in Turkey.

Of course, there were unusual conditions, but it is great if you have the patience to wait for them. For the record a Metrosound FMS20 was used with an aerial designed for 145MHz (outside U.K. FM broadcasting). I hasten to add that readers should not expect such results with the wrong type of aerial normally. He has now installed an 8-element beam, 40 feet up, with a rotator.

I have also received a log from our friend **Roy Patrick** in Derby for 20th January. This includes SWF Germany Haardtkopf on 97.7MHz, HR Frankfurt Meissner on 99.0MHz and Boulogne on 99.9MHz. His receiver is a Grundig portable. BBC Radio Humberside has sent Roy a QSL letter for 96.8 and he also picked up Capital Radio (95.8MHz).

I heard that a reader in Ipswich who has a 6-

William F. Kitching (Telford, Shropshire) uses a Grundig Yacht Boy receiver and a 25 metre outdoor aerial when DXing on the medium waves. His log includes Radio Nacional Espana stations at Madrid on 584kHz; Coruna on 638kHz; Seville 683kHz; Barcelona 737kHz; San Sebastian 773kHz together with the Voice of America relay at Kavalla in Greece on 791kHz; Sud Radio, Andorra on 818kHz; American Forces Network at Munich on 1106kHz and Stuttgart on 1142kHz; Vatican Radio on 1529kHz. William has been a medium wave DXer for two years and he has received a total of 40 MW QSLs.

Roy Patrick (Derby) has received the following details from the Independent Broadcasting Authority's Engineering Department. Radio Clyde 1151kHz transmits from Dechmont Hill with a power of 4kW; Radio Birmingham 1151kHz uses 3kW into a vertical antenna located at Langley Mill; Radio Manchester is due to start in April on 1151kHz with a power of 4kW from a site at Ashton Moss. Later in 1974 Radio Swansea will be on 1169kHz; Radio Tyneside will be on 1151kHz with 2.5kW while Radio Edinburgh, Radio Liverpool (Rainford) and Radio Sheffield (Skew Hill) will all be on 1546kHz.

A number of readers have asked if it is possible to use a MW loop aerial with a transistor portable which has its own internal ferrite rod aerial. One method tried by the writer is to attach the portable receiver to the centre of the loop in such a way that the nulls of the loop and the ferrite rod aerial coincide. Generally, this will mean that the portable will be mounted at right angles to the plane of the loop windings. Coupling between the loop and ferrite aerial is by induction and the loop and receiver are rotated together to null-out interference.

element aerial directed towards Wrotham (North Kent), has picked up BBC Radio Bristol on 95.5MHz and Rouen (station frequency not stated). His tuner is a home made design.

The General Advisory Council of the BBC have advised the BBC to make representations with a view to clearing the 97.6 to 100MHz band of all service users. That would mean that the police frequencies would have to be revised so that the U.K. can make maximum use of the internationally agreed 88-100MHz band for broadcasting. I, for one, am delighted to hear of this and sincerely hope that they successfully seek the necessary legislation.

Good DXing! Don't forget to keep in touch. Please state the approximate frequencies of stations heard and the signal strength. Also of interest is your receiver type and aerial used, and the date when you heard the reported stations.

How about this for a jumbo bag? **Peter Taylor** writes from Whitton in Middlesex: "I have an Armstrong 624 tuner and 3-element Yagi aerial in the loft". So far Peter says that he has received most of the French stations in N.E. France, apart from those masked by British stations. He also receives the three Lille transmissions virtually all the time. On the 20th-21st January he received (and sent me a cassette recording) the following: Radio Austria Pfander I 98.2; AFN Frankfurt 98.7; Sddeutscher Rundfunk I 98.8; Bayerischer Rundfunk, Munich III 97.3 (including signature tune); Sudwestfunk, Haardtkopf I 97.7 and II 93.0; Westdeutscher Rundfunk, Teutob. Wald II 93.2 and III 97.0; Hessischer Rundfunk, Biedenkopf I 91.0; ORTF, Besancon, France Musique 92.9, France Culture 97.7MHz.

BI-PRE-PAK

SUPPLIERS OF SEMI-CONDUCTORS TO THE WORLD



Telephone Corner

COMPLETE TELEPHONES

Normal Household Type

EX. G.P.O. Only **£1-05p** P & P 45p each

TELEPHONE DIALS

Standard Post Office type. Guaranteed in working order.
Only **27 1/2p** POST & PACKING 16p

Tested and Guaranteed Paks



B79	4	IN4007 Sil. Rec. diodes. 1,000 PIV lamp plastic	55p
B81	10	Reed Switches, 1" long, 1/4" dia. High Speed P.O. type	55p
B99	200	Mixed Capacitors. Approx. quantity, counted by weight	55p P & P 15p
H4	250	Mixed Resistors. Approx. quantity, counted by weight	55p P & P 15p
H35	100	Mixed Diodes, Germ. Gold bonded, etc. Marked and Unmarked.	55p
H38	30	Short lead Transistors, NPN Silicon Planar types	55p
H39	6	Integrated Circuits. 4 Gates BMC 962, 2 Flip Flops BMC 945	55p
H41	2	Sil Power transistors comp pair BD131/132	55p



Unmarked Untested Paks

B1	50	Germanium Transistors PNP, AF and RF	55p
B66	150	Germanium Diodes Min. glass type	55p
B84	100	Silicon Diodes DO-7 glass equiv. to OA200, OA202	55p
B86	100	Sil. Diodes sub. min. IN914 and IN916 types	55p
H16	15	Experimenters' Pak of Integrated Circuits, Data supplied	55p
H20	20	BY126/7 Type Silicon Rectifiers 1 amp plastic. Mixed volts.	55p
H34	15	Power Transistors, PNP, Germ. NPN Silicon TO-3 Can.	55p

Make a rev counter for your car

The 'TACHO BLOCK'. This encapsulated block will turn any 0-1mA meter into a linear and accurate rev. counter for any car with normal coil ignition system.

£1-10p each

Ex GPO Push Button Intercom Telephones

Exactly as internal telephone systems still in everyday use where automatic internal exchanges have not yet taken over. Available in 5, 10 or 15 ways. Complete with circuits and instructions. Necessary 24 pair cable 22p per yard. Price of each instrument is independent of the number of ways.

£2.75 p.p. 38 1/2p Per instrument

Cable can be sent by Parcel Post. Post and Packing per 50 yds. 73p.
Extension Telephones. 71p each. p.p. 27p.
£1.97p for 2. P.&P. 55p.
These phones are extensions and do not contain bells.

A Cross Hatch Generator £3-85 post paid

A complete kit of parts including Printed Circuit Board, A four position switch gives X-hatch, Dot, Vertical or Horizontal lines. Integrated Circuit design for easy construction and reliability. A project in the Sept. '72 edition of Television.

New Paks

TESTED & GUARANTEED			
H63	4	2N3055 type NPN Sil. power transistors. Below spec. devices	55p
H64	4	3B19 N Channel FETs 3B19N in plastic case	55p
H65	4	40361 Type NPN Sil. transistors TO-5 can comp to H66	55p
H66	4	40362 Type PNP Sil. transistors TO-5 can comp to H65	55p
UNTESTED, UNMARKED			
H67	10	3B19N Channel FETs plastic case type	55p

Over 1,000,000 Transistors in stock

We hold a very large range of fully marked, tested and guaranteed transistors, power transistors, diodes and rectifiers at very competitive prices. Please send for free catalogue.

Our very popular 4p transistors

TYPE "A" PNP Silicon alloy, TO-5 can
TYPE "B" PNP Silicon, plastic encapsulation
TYPE "C" PNP Germanium (AF R)
TYPE "D" NPN Silicon plastic encapsulation
TYPE "E" NPN Silicon similar ZTX 300 range
TYPE "F" NPN silicon similar ZTX 500 range

8 RELAYS FOR VARIOUS TYPES P & P 27 1/2p £1-10p

High Speed Magnetic Counter



4 digit (non-reset) 24V or 48V (state which)
4 x 1 x 1 in. 33p. P.&P. 5p.

Plastic Power Transistors



NOW IN TWO RANGES

These are 40W and 90W Silicon Plastic Power Transistors of the very latest design, available in NPN or PNP at the most shatteringly low prices of all time. We have been selling these successfully in quantity to all parts of the world and we are proud to offer them under our Tested and Guaranteed terms.

Range 1. VCE. Min 15. HFE Min 15.	
40 Watt	1-12 13-25 26-50
90 Watt	22p 23p 18p
	26p 24p 22p
Range 2. VCE. Min. 40. HFE Min 40	
40 Watt	1-12 13-25 26-50
90 Watt	33p 31p 29p
	38p 36p 33p

Complementary pairs matched for gain at 3 amps. 11p extra per pair. Please state NPN or PNP on order.

LM380 Audio I.C. as featured in *Practical Wireless* Dec. issue, complete with application data £1-10p.

INTEGRATED CIRCUITS

We stock a large range of I.C.s at very competitive prices (from 11p each). These are all listed in our FREE Catalogue, see coupon below.

METRICATION CHARTS now available
This fantastically detailed conversion calculator carries thousands of classified references between metric and British (and U.S.A.) measurements of length, area, volume, liquid measure, weights etc.
Pocket Size 15p Wall Chart 18p

LOW COST DUEL IN LINE I.C. SOCKETS
14 pin type at 16p each } Now new low profile
16 pin type at 16p each } type

BOOKS

We have a large selection of Reference and Technical Books in stock. Details are in our latest Catalogue. Send for it TODAY, using the coupon below. N.B. Books are void of V.A.T.

Send for lists of publications

Our famous P1 Pak is still leading in value

Full of Short Lead Semiconductors & Electronic Components, approx. 170. We guarantee at least 30 really high quality factory marked Transistors PNP & NPN, and a host of Diodes & Rectifiers mounted on Printed Circuit Panels. Identification Chart supplied to give some information on the Transistors.

11p P & P on this Pak.

Please ask for Pak P.1. only 55p

Please send me the FREE Bi-Pre-Pak Catalogue.

NAME

ADDRESS

ALL PRICES INCLUDE 10% VAT

MINIMUM ORDER 50p. CASH WITH ORDER
PLEASE. Add 11p post and packing per order
OVERSEAS ADD EXTRA FOR POSTAGE

BUY THESE GOODS WITH ACCESS

BI-PRE-PAK LTD

Dept. D: 222-224 WEST ROAD, WESTCLIFF-ON-SEA, ESSEX.

TELEPHONE: SOUTHEND (0702) 46344.

Co. Reg. No B20919

NELSON-JONES FM TUNER KIT



VARICAP TUNING

as in 'W.W.' June '73

Now available to readers of 'Practical Wireless'. The Nelson-Jones tuner uses dual gate MOSFET's in the RF stages, integrated circuits and ceramic filters in the IF stages, for very high performance and quick assembly. Do not confuse with tuners using only bipolar transistors and IF coils!

Tuning is accomplished by variable capacitance diodes and a Push Button Unit with 6 positions. AFC disable is incorporated as well as a pointer for each button showing tuning position in the range 87.5-108MHz, i.e. each 'button' is fully tuneable simply by turning.

Our complete metalwork system is supplied with nuts, bolts, board standoffs, push button mains on/off and stereo mute assembly, sockets, fuse and holder. Printed and Anodised Front Panel and Veneered Teak case. Power supply kits are supplied with complete kits of parts, or separately. LED tuning ind. is also supplied.

Prices for complete kits start at £23.95 + 50p pp. + VAT for mono tuners, (phase locked decoders are also available to fit in the cabinet). Please send large SAE for complete details of special offers and our complete lists.

GREEN LED's—the latest for 'stereo' lamps. 1-9 69p, 10+ 59p.

TEXAN AMPLIFIER

The Cabinet of the Nelson-Jones Tuner is specially designed to match the Texan amplifier cabinet, see photographs, so that owners of Texan's are assured of compatibility, both in superb performance and appearance.

Texan amplifier kits are available at £28.50 + 50p pp. + VAT.


Worried about tuner alignment? then let our alignment service take over.

Telephone queries. We have REAL ENGINEERS, not salesmen, to answer queries.



INTEGREX LIMITED, Dept. P.W., P.O. Box 45, Derby, DE1 1TW. Tel. Repton (028389) 3580

Verobox

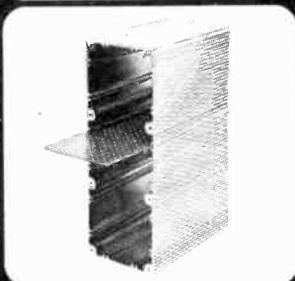

ALUMINIUM ENCLOSURES

- 6 standard sizes available from your local retailer.
- Made from precision extrusions with integral board guide slots.
- Finned sides improve appearance and radiate heat.
- Parallel sides for ease of component mounting.



VERO ELECTRONICS LTD.


Eastleigh, Hants. SO5 3ZR

Tel: Chandler's Ford 2952 Telex: 47551

Subsidiaries and Agents
throughout the World

AUTOMATIC WIRE STRIPPER

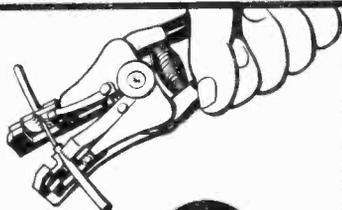AS SUPPLIED TO
LEADING ELECTRONIC COMPANIES



PRICE
£2.95

INCL. PP & VAT


GRIPS AND STRIPS
WIRE

IN ONE OPERATION

IDEAL GIFT ELECTROLINK

ULLSWATER CRESCENT
COULSDON CR3 2UG SURREY

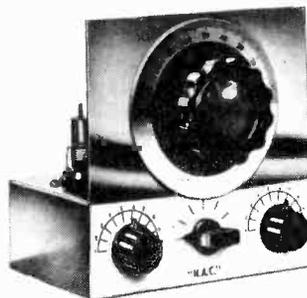H.A.C. SHORT-WAVE KITS WORLD-WIDE RECEPTION




Famous for over 35 years for Short-Wave Equipment of quality, "H.A.C." were the Original suppliers of Short-Wave Receiver Kits for the amateur constructor. Over 10,000 satisfied customers—including Technical Colleges, Hospitals, Public Schools, R.A.F., Army, Hams, etc.

1974 "DX" RECEIVER

Complete kit—Price £4.30 (incl. p. & p. & V.A.T.). Customer writes: "Australia, India and America at loud volume."—"I have now heard over 900 stations including many Amateurs. I have received 32 Q.S.L. verified reports—from all continents. An amazing one-valve kit." This kit contains all genuine short-wave components, drilled chassis, valve, accessories and full instructions. Ready to assemble, and of course, as all our products—fully guaranteed. Full range of other S.W. kits, including the famous model "K plus" (illustrated above). All orders despatched by return. Send now for free descriptive catalogue, of kits & components. Test Report available. EXCITING COMPETITION for Short-Wave listeners. Send stamped envelope for details.

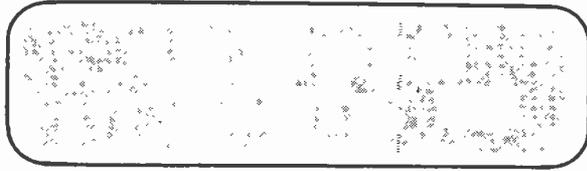"H.A.C." SHORT-WAVE PRODUCTS
29 Old Bond Street, London W.1



SHORT WAVES by DAVID GIBSON, G3JDG

IT seems that all the staunch supporters of 20 metres and the other two h.f. bands have fled. In the absence of easy DX it appears that we are separating the real s.w.l.s from the "Sunday Listeners". Most logs which arrived this month were for 80 metres, although very few dared brave 7MHz.

Some ideas for **Glyn Fisher** who requested a good modern receiver covering 4-6MHz continuously. Two suggestions: **P. Maynard** (Lancs) proposes the EC10 pointing out that it works off six U2 batteries and can be used anywhere. **Barry Keal**, G8H DU (Lancs) reckons the SW717 from Heathkit would suit, having used one himself for the past two years as a tuneable i. f. for listening on two metres.

Readers' Logs

Jon Hirst (Cams) claims to have discovered a very large l.f. net which involves the Royal Signals Amateur Radio Society. Net controller is said to be GW3ASW and the frequency for interested s.w.l.s is 3.720MHz—listen Tuesdays and Thursdays at 2000hrs and on 7.050MHz at 1030hrs on Sundays.

Stanley Sharred (Birmingham) is sticking to his permanent resolution of never making New Year resolutions. He spent the time instead listening on topband and offers some juicy call signs heard on Trawler territory; G13YFY, GW3ZQN, EI8H, EP2BQ, KV4FZ, OE8DM, OL5AQC, OK1FCW, PY1RO, VE1AX, VE1CO, VE1CD, VE1MX, VE1ASJ, VE3DN, VO1KE, W1GJE, W1HGT, W2DED, W3BJZ. All these were c.w. signals which just goes to show what you're missing if you can't read Morse—yet? Amongst the s.s.b. stations heard by Stanley on 80 metres were; CT1HE, JY3ZH, K2RM, K4GSU, KH4NCA, KZ5JM, TI2WD, TI2YF, VE2BZA, VP2VPU, VX1BT, VX1FG, VX2AS, W1MX, WB2KQC/P/2, W3TTW, W3ZBY, W4YN, WB4KDR, W8FIE, YV3TN, 3A0FY, A peep on 7MHz c.w. revealed; OA2NYD, PY7BTX, PY7CAR, VK3MR. No mention of any receiver or aerial with these logs so one must presume that earholes in the Birmingham area are considerably more sensitive

than those in Harpenden (maybe it's something to do with the drinking water).

First of the 3.5MHz logs comes from **John Porter** (Derbyshire) who used a 9R59DS and a 30 metre wire to bag these on s.s.b.; CR3WB, CT1ATV, EP2BQ, HB9AFM, I3BYT, JY3ZH, KV4AB, K2BT, LA9LSV, OH1TY, ON4UN, PJ9KH, PY2FOT, VE1BB, VE1JA, W1AA, WB8HDR/P1, 9E5CQ. John also managed OL7AQX and ZS6ZE on topband c.w.

Letter which appears to be from **Steve Tiltell** (bad writing, I expect it's Ena Boggins or something) in the Isle of Wight tells tales of eighty metre s.s.b. signals from; EA3JE, HA0KDA, K5EKD, OH7RM, OK3RJ, PY1FI, PZ1DR, VE3ARR/P, VE3FMJ, VE3GO, VK2LW, W9ADN, W5WZ, YD9AB/P, YO3AC. Steve (or Ena) says this was the result of giving the receiver a quick work out coz it was new. Gear is a RA1 plus PR40 and a "70ft. or so" wire.

Brian Smith has sent in his first log from Somerset. He reckons to have many more hours of s.w.ing to go coz he's only 15. Squeaks of 80 metre s.s.b. were logged on a 9R59DS and a 130ft. loft aerial from the following; CT1VY, CT3AB, EA4LK, EA6BG, HB9ADN, ON5JY, OZ3SS, VU1SX, W1CR, 5B4KP.

Craig Ashby (Bucks) has made unspecified changes in his aerial and earth system which feeds his UR-1A receiver. Best on eighty metres were; CT3AB, OK1KPU and SM6CWK. On 7MHz; DK7KS, ON6OS.

Hilton Helm (no relation to Matt, I hope?) writes from Salisbury in Rhodesia. The receiver is a homebrew five-transistor regen fed with 50ft. of wire. Hilton built the receiver during the school holidays and managed to bag some s.s.b. signals from; A4XFD, CR6RJ, CR6UE, CX4CR, DJ4KB, DK8FZ, EA3UU, EL2CJ, G2JZ, G4ADU, HS1BG, HS4AKF, I8ZPQ, I0DLP, K4YYL, PY1ZAE, PY2CRN, VE7FI, VE7MT, VK2SG, VK5QX, VS9MJ, VU2AIK, VU2MX, WB2ZHY, W2HIN, W2ONV, W4QAW, W7APA, W8GKQ, XW8ES, YB9ABH, 3B8CJ, 3B8DX, 4Z4EV, 4Z4MQ, 5U7AZ, 5Y4XYP, 5Z4FB, 9H1CW, 9M2AT, 9M2FX, 9M2GO, 9V1RR, 9X5NA, 9X5VA. All these were on 14MHz which just goes to show what's about.

A. McNeill (Berks) queries some funny call signs—CK8T, HE7MW, KU7KJW, LY1DYM/9 and PT1RA. Anyone making any sense out of these should consult a psychiatrist immediately. Meanwhile, with an ex-RAF R108Z receiver and 33ft end fed, the following presented themselves on 14MHz; CR6AL, EL2OSB/MM, FG5P, FP8PR, FC8TT, HK1FL, KP4DLC, LU9CV, OA7WA, PY1LA, TI2WD, TF3SE, VK6FT, VP9HL, VE3AHB, W5MJQ, W6OV, W7AYO, YK1OK, YV5BLT, ZS6JK, ZE8JJ, 9H1DQ, 9H4C, 4S7CF, 5Z4JDP, 5U7AZ.

Glyn Fisher (Rutland) uses a dipole, MOS FET converter and an HRO tuning 4-6MHz to log these on 14MHz; DJ9PCA, DK2RY, DL3SPA, F1BHL, F1BJD, F1RM, F6ANW, F9FT, G2BAR, GI3GXP, HB9QQ, PA0VV, all on s.s.b.

Contests for April include: April 7, 3.5MHz low power; 20-21, Bermuda (phone); 21, 4 metre open; 27-28, National Amateur Television; May 4-5, 2 metre open and s.w.l.; May 4-5, second Bermuda (phone).

BROADCAST BANDS

Short Wave Reports by 15th of the month to Malcolm Connah, 27 Lismore Road, Highworth, Wiltshire, SN6 7HU.

Medium Wave Logs to Charles Molloy, 132 Segars Lane, Southport, PR8 3JG.

VHF/FM Reports to Simon David, c/o Practical Wireless, Fleetway House, Farringdon Street, London, EC4A 4AD.

AMATEUR BANDS

Short Wave/VHF

Logs in alphabetical order please by 15th of the month to David Gibson, G3JDG, 12 Cross Way, Harpenden, Hertfordshire.

SPECIAL OFFER ! ! !

SMALL ELECTROLYTICS

Ref. No.	Capacity	Voltage	Price	Ref. No.	Capacity	Voltage	Price
H8/1	1µF	150V	4p	H7/4A	64µF	35V	5p
H8/2	2-2µF	25V	4p	H7/5	80µF	16V	4p
H8/2A	3-3µF	25V	4p	H7/8	125µF	16V	5p
H8/3	3µF	50V	4p	H7/8A	100µF	35V	6p
H8/3A	4µF	50V	4p	H7/9	100µF	63V	6p
H8/4	4-7µF	25V	4p	H7/9A	125µF	4V	4p
H8/4A	5µF	64V	4p	H7/10	125µF	25V	6p
H8/5	5µF	10V	4p	H7/10A	160µF	2-5V	3p
H8/5A	5µF	150V	4p	H7/11	160µF	25V	6p
H8/6	10µF	10V	4p	H7/11A	150µF	16V	5p
H8/6A	10µF	70V	4p	H7/13A	200µF	25V	8p
H8/8A	16µF	16V	4p	H7/14	220µF	50V	10p
H8/9	20µF	6V	2p	H7/14A	220µF	16V	6p
H8/9A	20µF	70V	4p	H7/15	220µF	25V	5p
H8/10	22µF	50V	4p	H7/15A	220µF	35V	10p
H8/10A	22µF	100V	4p	H6/1A	250µF	4V	3p
H8/11	25µF	12V	4p	H6/2	250µF	25V	3p
H8/11A	24µF	275V	4p	H6/3A	320µF	2-5V	3p
H8/12	32µF	15V	4p	H6/4	320µF	10V	4p
H8/12A	30µF	10V	4p	H6/4A	330µF	16V	5p
H8/13A	32µF	50V	4p	H6/5	330µF	25V	10p
H8/14	40µF	25V	5p	H6/5A	330µF	35V	15p
H8/14A	40µF	16V	4p	H6/8	470µF	25V	10p
H8/15	47µF	50V	4p	H6/8A	470µF	35V	20p
H8/15A	40µF	35V	4p	H6/9A	400µF	40V	20p
H7/1	50µF	6V	3p				
H7/1A	50µF	10V	4p				
H7/2A	64µF	2-5V	2p				
H7/3A	64µF	25V	4p				
H7/4	64µF	15V	4p				

POSTAGE: 15P PER ORDER

ALL GOODS PLUS 10% V.A.T.

MULLARD ELECTROLYTIC CAPACITORS

071 and 072 Series		Capacitance µF	Max. Ripple Current at 50°C	Weight	Price
Type No.	Working Voltage Vdc.				
071 15332	16	3300	2-4 amps	1oz	15p
071 15472	16	4700	3-9 amps	1oz	17p
071 15682	16	6800	5-8 amps	1½oz	22p
072 15752	16	7500 + 7500	10-5 amps	3oz	37p
072 15113	16	11000 + 11000	13-8 amps	4½oz	49p
071 16472	25	4700	5-4 amps	1½oz	22p
072 16502	25	5000 + 5000	9-6 amps	3½oz	37p
072 16752	25	7500 + 7500	12-6 amps	4½oz	49p
071 18681	63	680	2-1 amps	1oz	15p

106 and 107 series		Capacitance µF	Weight	Price	
Type No.	Voltage				
106 16223	25	22000	17 amps	10oz	£1-12
106 17103	40	10000	12 amps	7½oz	94p
107 10222	100	2200	10 amps	5½oz	74p

Type No.	Voltage	Capacitance µF	Weight	Price
102 15163	16	16000	8oz	20p
104 90003	20	39000	16oz	30p
102 16802	25	8000	7oz	25p
104 90001	45	20000	16oz	50p

A further 10% discount on lots of 100 of any one type.
Please calculate the weight of your order and include appropriate postage.

Not over	Ordinary Parcels	Not over	Ordinary Parcels
1½lb	16p	10lb	37p
2½lb	21p	14lb	47p
4lb	25p	18lb	57p
6lb	29p	22lb	67p

UNIUNCTION TRANSISTORS SIMILAR TO 2N 2646 25p

£1 100 ½-WATT RESISTORS
100 CERAMIC CAPACITORS
100 DIODES

POSTAGE 20p PACK No. 1

£1 1 VERO-BOARD CUTTER
5 2½ in. x 1 in. x .15 BOARDS
50 SQ. INS. "ODD PIECES"
VERO

POSTAGE 20p PACK No. 3

£1 20 ASSORTED UNUSED
MARKED, TESTED
TRANSISTORS
BC108 ETC.

POSTAGE 20p PACK No. 5

£1 6 COMPUTER PANELS
CONTAINING MASSES OF
DIODES, TRANSISTORS,
INDUCTORS, RESISTORS
& CAPACITORS

POSTAGE 27p PACK No. 7

£1 100 RESISTORS
100 CERAMIC
CAPACITORS
100 POLYSTYRENE
CAPACITORS

POSTAGE 20p PACK No. 2

£1 100 RESISTORS
100 CERAMIC
CAPACITORS
50 MULLARD POLYESTER
CAPACITORS

POSTAGE 20p PACK No. 4

£1 1 TRANSISTORISED
SIGNAL TRACER KIT
1 TRANSISTORISED
SIGNAL INJECTOR KIT

POSTAGE 20p PACK No. 6

£1 100 RESISTORS
100 CAPACITORS
(ASSORTED TYPES)

POSTAGE 20p PACK No. 8



become a RADIO-AMATEUR!

learn how to become a radio-amateur in contact with the whole world. We give skilled preparation for the G.P.O. licence

free! Brochure, without obligation to:

BRITISH NATIONAL RADIO & ELECTRONICS SCHOOL P.O. Box 156, JERSEY

NAME: _____

ADDRESS: _____

WB54
BLOCK CAPS please

Run your own hi-fi store

A unique opportunity to become the outright owner of a franchise that's the first of its kind in Britain.

Tandy Corporation (Branch UK) is completely new to Britain. A division of the Tandy Corporation of America, where its 'Radio Shack' operation has now grown to approaching some 2,000 outlets.

Nowhere else will you find a similar operation, because a Tandy franchise is your very own business.

You'll be selling exclusive Tandy brands of radio, audio and communications equipment, plus parts and kits. All of the highest possible quality, yet so competitively priced that you can be assured of high volume and substantial profits within a surprisingly short time.

Previous radio trade experience is not essential. You get the full benefit of Tandy's 50 years' experience covering everything from your grand opening to everyday routines plus regular newspaper advertising and full merchandising and promotional support.

A minimum of £14,000 initial investment is required. Company-owned and managed shops are now actively trading and are available for franchise in Birmingham, Coventry, the Potteries, West Midlands and Manchester areas. Additional shops will also shortly be available for franchise in Bristol, Cheltenham, Doncaster, Gloucester, Liverpool, Nottingham and Worcester.

If you would like more information, please write in confidence to the Senior Vice-President, Mr. Richard N. O'Brien.

TANDY TANDY Corporation
(Branch UK) Bilston Rd
Wednesbury, WS10 7JN, Staffs.



MODEL AF.105 VOM

50,000 opv. Mirror scale. Meter protection. 0/3/12/60/120/300/600/1200V DC. 0/6/30/120/300/600/1200V AC. 0/30A/1/60/300 mA. 12 Amp. 0/10K/1m/10m/100 Meg Ohms. -20 to +17 dB.



OUR PRICE £12.50 P&P 20p.

LB4 TRANSISTOR TESTER

Tests PNP or NPN transistors. Audio indication. Operates on two 1.5V batteries. Complete with instructions etc.



OUR PRICE £4.50 P&P 20p

U4341 Multimeter & Transistor Tester

27 ranges, 16,700 opv. Overload protected. Ranges: 0.3/1.5/6/60/600/1500/3000V DC. 1.5/7.5/30/300/750V AC. 0.05/0.5/5/50/500mA DC. Resistance: 5/50/500 ohms/5/10/100k ohms/1 Meg. Battery operated. Size: 160 x 97 x 40mm. Supplied in carrying case complete with test leads.



OUR PRICE £10.50 P&P 20p

KAMODEN HMG500 insulation resistance tester

Range 0-1,000 Megohms/500/1000V DC. Battery operated. Wide range clear meter 4" x 4 1/2". Complete deluxe carrying case, batteries and instructions.



OUR PRICE £19.95 P&P 30p

ST00TR MULTIMETER TRANSISTOR TESTER

100,000 opv. Mirror scale. Overload protection. 0/0.12/0.6/3/12/30/120/600V DC. 0.6/3/12/60V AC. 0.05/0.5/5/50/500mA DC. Resistance: 10/100/100k/1M/10M. Battery operated. Size: 190 x 172 x 99mm.



OUR PRICE £15.95 P&P 25p

C15 PULSE OSCILLOSCOPE

For display of pulsed and periodic waveforms in electronic circuits. VERT. 500V. Bandwidth: 10MHz. Sensitivity at 100kHz VRMS/mm: 0.1-25. 7.5A DC AMP. Bandwidth: 500kHz. Sensitivity at 100kHz VRMS/mm: 0.3-25. Free running sweep 1-3000usec. Free running 20-200 kHz in nine ranges. Calibrator pips. 225 x 360 x 430mm. 115-230V AC.



OUR PRICE £39.00 Carr. paid

RUSSIAN C116 Double Beam OSCILLOSCOPE

5 MHz pass band. Separate Y1 and Y2 amplifiers. Rectangular 4" CRT. Traced triggering sweep from 0.2usec. to 100 milli-sec/cm. Free running time base. 50Hz/500Hz. Built-in time base. Calibrator and amplitude Calibrator. Supplied complete with all accessories and instruction manual.



OUR PRICE £87.00 Carr. paid

MODEL TE15 GRID DIP METER

Transistorised. Operates as Grid Dip Oscillator, Absorption Wave Meter and Oscillating Detector. Frequency range: 440kHz-280MHz in six coils. 500mA 800mA battery operation. Size: 180 x 80 x 40mm.



OUR PRICE £19.95 P&P 20p

Also see following pages

ALL PRICES EXCLUDE VAT

AUDIOTRONIC Model ATM1

Top value 1,000 opv pocket multi-meter. Ranges: 0/10/50/250/1,000 volt AC and DC. DC current 0.1mA/100mA. Resistance: 0/150k ohms. Decibels: -10 to +22dB. Size 90 x 60 x 28mm. Complete with test leads.



OUR PRICE £2.95 P&P 15p

AUDIOTRONIC Model ATM5

Jewel movement, attractively moulded case with edgewise ohms adjustment. Ranges: 0.3/15/150/300/1200V AC. (2500 opv). 0.6/3/30/600V DC. (5000 opv). 0.300A/0.300mA DC. Resistance: x10 & x100. -10 to +16dB. Supplied with battery test leads and data booklet. Size: 121 x 73 x 29mm.



OUR PRICE £3.50 P&P 15p

MODEL C1092 MULTIMETER

Features 5,000 opv jewel movement and a good selection of range functions. Edgewise ohms adjustment. Ranges: 0-3/15/150/300/1,200V AC (2,500 opv). 0-6/30/300/600V DC (5,000 opv). DC current: 0-300mA/300mA. Resistance: R x 10, R x 1,000. -10 to +16dB. Complete with battery, test leads and data booklet. Size: 120 x 73 x 28mm.



OUR PRICE £3.75 P&P 35p

MODEL U437 MULTIMETER

10,000 opv. A first class, instrument manufactured in USSR to the highest standards. Ranges: 2.5/10/50/250/500/1000V DC. 2.5/10/50/250/500/1000V AC. DC current: 0-300mA/300mA. Resistance: 1/10/100mA/1A. Resistance 300 ohms/3/30/300k/3 Meg. ohms. Complete with batteries, test leads, instructions and a sturdy steel carrying case.



OUR PRICE £4.95 P&P 25p

MODEL TH12

20,000 opv. Overload protection. Slide switch selector. 0/0.25/2.5/10/50/150/1000V DC. 0/10/50/250/1000V AC. 0/50A/25/250mA DC. 0/3k/30k/300k/3 Megohms. -20 to +50dB.



OUR PRICE £5.95 P&P 15p

HIOKI Model 720X VOM

A versatile, accurate measuring instrument. 20,000 opv. 0/5/25/100/500/1000V DC. 0/10/50/250/1000V AC. 0-50A/250mA DC. 2 Megohms.



OUR PRICE £3.97 P&P 20p

MODEL PL436


20,000 opv DC. 8000 opv AC. Mirror scale. 6/3/12/30/120/600V DC. 3/30/120/600V AC. 50/600A/60/600mA. 10/100k/1 Meg/10 Meg Ohm. -20 to +46 dB.



OUR PRICE £6.97 P&P 15p.

U4323 MULTIMETER

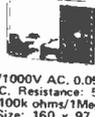20,000 opv. Simple unit with audio/IF oscillator. Suitable for general receiver tuning. Ranges: 0.5/5.2/10/50/250/500/1000V DC. 2.5/10/15/250/500/1000V AC. 0.05/0.5/5/50/500mA DC. Resistance: 5/50/500 ohms/5/10/100k ohms/1 Meg. Battery operated. Size: 160 x 97 x 40mm. Supplied in carrying case complete with test leads.



OUR PRICE £7.00 P&P 20p

MODEL HIOKI 730X

30,000 opv. Overload protection. 6/30/60/300/600/1200V DC. 12/60/120/600/1200V AC. 60/100A. 30mA/300mA. 2K/200K. 2 Meg Ohm. 10 to 63 dB.



OUR PRICE £7.50 P&P 15p.

MODEL TE300

30,000 opv. Mirror scale. Overload protection. 0/0.6/3/15/30/120V DC. 0.6/3/12/60/120V AC. 0/30A/300mA. 2K/200K. 2 Meg Ohm. 10 to 63 dB.



OUR PRICE £7.50 P&P 15p

U4324 MULTIMETER

High sensitivity, overload protected. Ranges: 0.6/1.2/3/12/30/60/120V DC. 0.6/3/12/60/120V AC. 0.05/0.5/5/50/500mA DC. Resistance: 25/250 ohms/5/50/500k ohms/5 Megohms. Decibels: -10 to +12dB. Size: 167 x 98 x 63mm. Supplied complete with test leads, spare diodes and instructions.



OUR PRICE £8.00 P&P 20p

TMK MODEL TW50K

46 ranges, mirror scale. 50kV/DC. DC Volts: 0.125/0.25/1.25/2.5/5/10/25/50/125/250/500/1000V. Polarity change switch. Ranges: 0.5/2/5/10/25/50/100. DC current: 25/50A/1.5/5/25/50A. 50/250/500mA/5/10A. Resistance: 10k/100k/1 Meg/10 Meg ohm. -20 to +81.5dB.



OUR PRICE £8.50 P&P 17p

U435 MULTIMETER

20,000 opv. Overload protected. Ranges: 75mV/2.5/10/25/100/250/500/1000V DC. 0.5/10/25/100/250/500/1000V AC. Current: 50A/1.5/25/100mA/0.5/2.5A DC. 5/25/100A. Resistance: 0.5/2.5/5A. Resistance: 0.3/30/300k ohms. Size: 205 x 110 x 84mm. Supplied complete with leads, crocodile clips and steel carrying case.



OUR PRICE £8.75 P&P 20p

U91 Clamp VOLT AMMETER

For measuring AC voltage and current without breaking circuit. Ranges: 300/600V AC. Current: 10/25/100/250/500A. Accuracy 4%. Size 283 x 94 x 36mm. Complete with carrying case, leads and test leads.



OUR PRICE £10.50 P&P 20p

U4312 MULTIMETER

extremely sturdy instrument for general electrical use. 667 opv. 0/0.3/1.5/7.5/30/60/150/300/600/900V DC. 75mV/0/0.3/1.5/7.5/30/60/150/300/600/900V AC. 0.300A/1.5/6/15/60/600mA/1.5/6A DC. 0/1.5/6/15/60/150/300k ohms. DC accuracy 1%. AC 1.5%. Knife edge pointer, mirror scale. Complete with sturdy metal carrying case, leads and instructions.



OUR PRICE £9.75 P&P 25p

MODEL 500

30,000 opv with overload protection. Mirror scale. 0/0.5/2.5/10/25/100/250/500/1000V DC. 0/0.5/10/25/100/250/500/1000V AC. Decibels: 10 to +17dB. Output: -0.3/6/15/30/60/120/300/600/1,200V AC. 0/50A/5/50/500mA. 12A DC. 0.6k/6 meg/60 megohms.



OUR PRICE £13.95 Carr. paid

HIOKI 750X VOLT-OHM-MILLIAMETER

43 ranges 0-0.3/0.6/1.5/3/6/12/30/60/150/300/600/1,200V DC. 0-0.6/1.5/3/6/12/30/60/120/300/600/1,200V AC. Current: 0-30/60A/300mA/150/300mA. Resistance: 0.6/6/60/600/3/30 Megohms. Decibels: 10 to +17dB. Output: -0.3/6/15/30/60/120/300V AC. Accuracy: 3% DC, 4% AC. Sensitivity: 50,000 opv DC, 5,000 opv AC. 4 inch meter. Built in protection. Size: 57 x 120 x 153mm.



OUR PRICE £11.95 P&P 40p

HIOKI MODEL 700X


100,000 opv. Overload protection. Mirror scale. 0/3/0.6/1.2/1.5/3/6/12/30/60/120/300/600/1200V DC. 1.5/3/6/12/30/60/150/300/600/1200V AC. 15/30A/3/6/30/60/150/300mA/7.5/15/30/60/120/240V. 2k/20k/200k/2M Ohms. -20 to +63dB.



OUR PRICE £14.95 P&P 20p

Model HT100B4 MULTIMETER

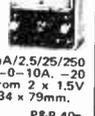Overload protected, shock proof circuits. 9.5uA Meter with mirror scale. Sensitivity 200uV. Polarity change switch. Ranges: 0.5/2/5/10/25/50/100/250/500/1,000 Volts DC. 2.5/10/50/250/1,000 Volts AC. DC resistance: 0-20/200k/2/20 Meg. ohms. DC current: 10-125/500A/2.5/25/250mA/1.5A. AC current: 0-10A. -20 to +62dB. Operates from 2 x 1.5V batteries. Size: 180 x 134 x 79mm.



OUR PRICE £15.00 P&P 40p

MODEL AS 1000 VOM

100,000 opv. Mirror scale. Built-in meter protection. 0/3/1.5/60/120/300/600/1200V DC. 0/6/30/120/300/600V AC. 0/100A/60/300mA. 12 Amp. 0/2K/200K/2M/200 Meg Ohm. -20 to +17 dB.



OUR PRICE £17.50 P&P 20p

KAMODEN HM720B FET VOM

Input impedance 10 Megohms. Ranges: 0/0.2/1.5/10/50/100V DC. 0/2.5/10/50/100V AC. 0/25uA/2.5/25/250mA DC. 0/5k/50k/500k/5M 500 Megohms



OUR PRICE £21.00 P&P 30p

KAMODEN 72.200 Multitester


High sensitivity tester. 200,000 opv. Overload protected. Mirror scale. Ranges: -0/06/3/30/120/600/1200V DC. 0/3/12/60/300/1200V AC. 0.6/6A/1.2mA/120mA/600mA/12A DC. 0/12A AC. -20 to +63dB. 0/2k/200k/2 Meg/200 Megohms.



OUR PRICE £22.50 P&P 30p

U4317 MULTIMETER

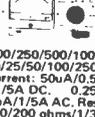High sensitivity instrument for field and laboratory work. Knife edge pointer. 96mm. mirror scale. Ranges: 100mV/0.5/2.5/10/25/50/100/250/500/1000V DC. 0.5/2.5/10/25/50/100/250/500/1000V AC. Current: 0.06/0.6/6/60/600mA DC. Resistance: 0.5/10/100/200 ohms/1/3/30/300k ohms. Decibels: -5 to +10dB. Battery operated. Size: 210 x 115 x 90mm. Supplied in carrying case complete with leads.



OUR PRICE £15.00 P&P 20p

TMK 100K LAB TESTER

100,000 opv. 6 1/2" scale. Built-in short circuit check. Sensitivity 100,000 opv DC. 5kV AC. DC Volts: 0.5/2.5/10/50/250/1000V AC. 3/10/50/250/500/1000V DC. current: 10/100A/10/100/500mA/2.5/10A. Resistance: 1k/10k/100k/10 Meg/100 Meg ohms. Decibels: 10 to +49dB. Plastic case with carrying handle. Size: 190 x 172 x 99mm.



OUR PRICE £19.95 P&P 25p

MODEL U4311 Sub-standard Multi-range Volt-Ammeter


Sensitivity 330 Ohms/Volt AC and DC. Accuracy 0.5% DC. 1% AC. Scale length: 165mm. 0/300/750A/1.5/3/7.5/15/30/75/150/300/750mA/1.5/3/7.5/15/30/75/150/300/750V AC. Automatic cut out device. Supplied complete with test leads, manual and test certificates.



OUR PRICE £49.00 P&P 50p

TE40 HIGH SENSITIVITY AC VOLTMETER

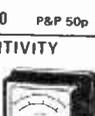10 Meg input. 15-1500V AC. Ranges: 0.001/0.05/0.1/0.5/1/3/11/30/100/300V RMS. Secs. 2/4/0.3/1. -40 to +50dB supplied complete with leads and instructions.



OUR PRICE £17.50 P&P 25p

TE65 VALVE VOLTMETER

28 ranges. DC volts 1.5-1500V. AC volts 1.5-1500V. Resistance up to 1000 Megohms. 200/240V AC. Battery operation. Complete with probe and instructions.



OUR PRICE £17.50 P&P 30p

LB3 TRANSISTOR TESTER

Tests ICO and B. PNP/NPN. Operates from 9V battery. Instructions supplied.



OUR PRICE £3.95 P&P 20p



Also see previous page

SWR METER Model SWR3
Handy SWR meter for transmitter antenna alignment, with built-in field strength meter. Accuracy 5%. Impedance 52 Ohm. Full scale 5 section collapsible antenna. Size 145 x 50 x 60mm.
OUR PRICE £4.25 P&P 25p

AT201 Decade ATTENUATOR
Frequency range 0-200kHz. Attenuator 0-111dB, 0.1dB steps. Impedance 600 ohms. Input power maximum 30dBm. Size 180 x 90 x 55mm.
OUR PRICE £12.50 P&P 37p

TRANSORISED I.C.R. A.C. BR/8 MEASURING BRIDGE
A new portable bridge offering 193 excellent range and accuracy at low cost. Ranges R 1 11.1 meg 6 Ranges 1% L1 H-111 HENRY 6 Ranges 2% C 10pF 1110mFd 6 Ranges 2% TURNS RATIO 1 1/1000 1 1/100 6 Ranges 1 1%. Bridge voltage at 1,000 cps. Operated from 9 volts 100 A. Meter indication. Attractive 2 tone metal case. Size 7 1/2 x 5 x 2 in.
OUR PRICE £25.00 P&P 25p

TE16A TRANSISTORISED SIGNAL GENERATOR
5 ranges, 400kHz to 30 MHz. An inexpensive instrument for the handy-man. Operates on 9V battery. Wide easy to read scale, 800kHz modulation. Size: 149 x 149 x 92mm. Complete with instructions and leads.
OUR PRICE £8.97 P&P 25p

MODEL TE20 RF SIGNAL GENERATOR
Six bands, 120kHz-260MHz. Dual output RF terminals. Separate variable audio output. Accuracy ± 2%. Audio output to 8V. Power requirements: 105-125V, 220-240V AC. Size: 193 x 265 x 150mm. Complete with test leads etc.
OUR PRICE £17.50 P&P 40p

TE-20D RF SIGNAL GENERATOR
Accurate wide range signal generator covering 120 kHz 500 MHz on 6 bands. Directly calibrated. Variable R.F. attenuator audio output. Xtal socket for calibration. 220/240V a.c. Brand new with instructions. Size 140mm x 215mm x 170mm.
OUR PRICE £17.50 P&P 30p

ARF 300 AF/RF SIGNAL GENERATOR
All transistorised compact fully portable. AF sine wave 18Hz to 220 kHz. AF square wave 18Hz to 100k Hz. Output Square/Sine wave 10V. P.P. RF 100kHz to 200MHz. Output TV maximum. 220/240V AC operation. Complete with instructions and leads.
OUR PRICE £29.95 P&P 50p

MODEL MG100 SINE SQUARE WAVE AUDIO GENERATOR
Range 19-220,000Hz Sine Output Sine or Square wave 10V. P to P Size 180 x 90 x 90mm Operation 220/240V AC.
OUR PRICE £19.95 P&P 37p

MCA220 Automatic Voltage Stabiliser
Input 88-125V AC or 176-250V AC. Output 120V AC or 240V AC. 200V/A rating. P&P 50p.
OUR PRICE £11.97

PS100B Regulated POWER SUPPLY UNIT
Solid state. Output 6, 9 or 12V DC up to 3 Amp. Meter to monitor current. Input 220/240V AC. Size: 100 x 82 x 159mm.
OUR PRICE £11.97 P&P 25p

PS200 Regulated POWER SUPPLY UNIT
Solid state. Variable output 5-20V DC up to 2 Amp. Independent meters to monitor voltage and current. Output 220/240V AC. Size: 190 x 136 x 98mm.
OUR PRICE £19.95 P&P 25p

POWER RHEOSTATS
High quality ceramic construction. Windings embedded in vitreous enamel. Heavy duty brush wiper. Continuous rating. Wide range available ex-stock. Single hole fixing. 3/4" diameter shafts. Buy in quantities available.
25 WATT 10/25/50/100/250/500/1000/2500 Ohms £1.15 P&P 10p
50 WATT 10/25/50/100/250/500/1000/2500/5000 Ohms £1.62 P&P 10p
100 WATT 1/5/10/25/50/100/250/500/1000/2500 Ohms £2.34 P&P 15p

AUTO TRANSFORMERS
0/115/250V. Step up or step down. Fully shrouded.
80 WATTS £2.75 P&P 18p
150 WATTS £3.50 P&P 18p
300 WATTS £4.50 P&P 23p
500 WATTS £6.95 P&P 33p
1000 WATTS £9.50 P&P 38p
1500 WATTS £12.50 P&P 43p
2250 WATTS £20.95 P&P 50p
5000 WATTS £44.95 P&P £1

CP110 CHASSIS PUNCH SET
Carefully machined top grade steel. Contains 1/2", 5/8", 3/4", 1" and 1 1/8" punches complete with gripper and accessories.
OUR PRICE £3.00 P&P 40p

YAMABISHI VARIABLE VOLTAGE TRANSFORMERS
Excellent quality at low cost. Input: 230V 50/60Hz. Output 0-260V.
MODEL S260 BENCH MOUNTING P&P
1A £10.50 30p
2.5A £12.00 35p
5A £17.50 37p
8A £30.35 50p
10A £33.75 75p
12A £29.50 75p
20A £85.00 125p
25A £95.00 130p
40A £120.00 150p
MODEL S260B PANEL MOUNTING
1A £10.00 30p
2.5A £12.00 35p

240° Wide Angle 1mA METERS
MW 1-6x60x60mm £6.50 P&P 15p
MW 1-8x80x80mm £6.90 P&P 15p

BVD5 Vernier TUNING DIAL
App. 7:1 ratio planetary drive vernier dial. Log scale 0-180 degrees. Blank scales 1-5. Dial size 128 x 76mm. Overall size 190 x 117 x 41mm. Cover including knob and coupling. 1/2" diam. shaft.
OUR PRICE £1.62 P&P 15p

WALKIE TALKIES
SKYFON 100mW **OUR PRICE £24.95** per pair
P302 Two Channel 300mW **OUR PRICE £52.50** per pair
P1003 Three Channel 1 Watt **OUR PRICE £71.25** per pair
P&P 50p per pair
NB. Licence required for use in UK

RUH6 Reflex Horn Speaker
Built-in driver unit. Impedance 16 ohms. Power rating 10W. Response 380-7000Hz. Size 85mm dia. Weather and shock protected.
OUR PRICE £4.97 P&P 30p

TRIO 9R59DS RECEIVER
Four bands covering 550kHz to 30 MHz continuous and electrical band spread on 10, 15, 20, 40, and 80 mtrs. 8 valve plus 7 diode circuit. 4 to 8 ohm output and phone jack. SSB-CW, ANL, variable BFO. S Meter and separate band spread dial. Ifreq. unused 45kHz. audio output 1/2 watt. Variable RF and AF gain controls. 115/250V AC, with instructions.
Our Price £42.50 CARR. PAID

TRIO TR2200 TRANSCIVER
Fully transistorised portable VHF transceiver. Will transmit and receive on six channels between 144-146MHz. 1 watt transmitter. 12V DC internal or external supply. Built-in charger for Ni-Cad cells. Power/volume switch, squelch control, channel selector, mic. socket, earphone/external speaker socket. Complete with microphone and 144.48, 144.72 & 145.32 crystals. Size: 134 x 58 x 180mm.
OUR PRICE £79.50 Carr. paid

BELTEK WS400 CAR TRANSCIVER
Solid state mobile transceiver for 12 volt DC neg. Transmits and receives on any 12 of 28 channels between 144 and 146MHz. Power output 10W and 1W switchable. Controls: On/off, volume, squelch and channel selector. Internal 3" speaker. Complete with dynamic mic. PTT switch, three sets of crystals for 144.48, 144.6 and 145MHz, mounting bracket and instructions. Size: 150 x 70 x 220mm.
OUR PRICE £75.00 P&P 50p

OT55G DIGITAL CLOCK MECHANISM
Features 24 hour alarm setting. on/off and auto alarm 'sleep' switch. Illuminated rotary dial with hours, minutes and seconds. Automatically turns off radio, TV, light etc. and with auto-switching will turn on again when required. 240V AC operation. Switch rating 250V-3 Amp.
OUR PRICE £5.95 P&P 30p

KE630 3 Station INTERCOM
Master and two sub-stations. Can be used on desk or wall mounted. Complete with cable and batteries.
OUR PRICE £5.25 P&P 50p

LH02S STEREO HEADPHONES
Light weight head-phones with padded ear pieces. 4/16 ohms 20-20,000Hz. Complete with 6' lead and plug.
OUR PRICE £1.97 P&P 30p

TE1018 Deluxe Mono High Impedance Headset.
Sensitive magnetic headset with soft ear pads. Impedance 2,600 ohms (600 ohms DC). Frequency response: 200-4,000Hz.
OUR PRICE £2.25 P&P 30p

DH02S STEREO HEADPHONES
Wonderful value and excellent performance combined. Adjustable headband. Impedance 8 ohms. 20-12,000Hz. Complete with lead and plug.
OUR PRICE £2.50 P&P 30p

TE1035 Stereo HEADPHONES
Low cost with excellent response. Foam rubber ear pads. Adjustable headband. 8 ohms impedance. Frequency response 20-18kHz. Complete with cable and stereo jack plug.
OUR PRICE £2.60 P&P 30p

SH8DV MONO/STEREO HEADPHONES
Volume control for each channel. 8/16 ohms impedance. Frequency response 20Hz-18kHz. Complete with 10ft. coiled lead and jack plug.
OUR PRICE £4.97 P&P 30p

BH001 HEADSET and Boom Microphone
Moving coil. Ideal for language teaching, communications etc. Headphone impedance 16 ohms. Microphone impedance 200 ohms.
OUR PRICE £5.95 P&P 30p

EMI LDOUSPEAKERS
Model 350 13 x 8" with single tweeter/crossover. 20-20,000Hz. 15 watts RMS. Available 8 or 15 ohms.
OUR PRICE £7.25 each P&P 37p
Model 450 13 x 8" with twin tweeter/crossover. 55-13,000Hz, 8 watts RMS. Available 8 or 15 ohms.
OUR PRICE £3.62 each P&P 25p

HIGH QUALITY CONSTRUCTION KITS
WE ARE APPOINTED STOCKISTS AT ALL BRANCHES

All kits are complete with comprehensive easy to follow instructions and covered by full guarantee.
Post and Packing 15p per kit.

AF20 Mono amplifier.....	£4.80
AF25 Mixer.....	£3.60
AF30 Mono pre-amplifier.....	£2.61
AF35 Emitter amplifier.....	£2.27
AF80 0.5W mic. amplifier.....	£4.22
AF305 Intercom.....	£9.52
AF310 Mono amplifier.....	£5.91
AT5 Automatic light control.....	£2.55
AT25 Window wiper robot.....	£5.82
AT30 Photo cell switch unit.....	£5.70
AT50 400W triac light dimmer/speed control.....	£4.80
AT52 2,200W true light dimmer/speed control.....	£6.90
AT60 1 channel light control.....	£7.80
AT65 3 channel light control.....	£14.55
GP304 Circuit board.....	£4.94
GP310 Stereo pre-amplifier for use with 2 x AF310.....	£21.27
GP312 Circuit board.....	£11.45
GU330 Tromlo unit.....	£7.50
HF61 Diode detector.....	£3.32
HF65 FM transmitter.....	£2.70
HF75 FM receiver.....	£2.87
HF310 FM tuner.....	£15.81
HF325 Deluxe FM tuner.....	£24.12
HF330 Decoder (HF310/325).....	£9.96
HF380 UHF aerial amplifier.....	£4.94
HF395 broadband aerial amp. L.F380 Quadraphonic device.....	£11.36
M160 Multi-vibrator.....	£4.55
M19 VU Meter.....	£4.71
M192 Stereo balance meter.....	£4.97
M1302 Transistor tester.....	£8.45
NT10 Stabilised power supply 100mA, 9V.....	£6.15
NT300 Stabilised p. supply.....	£12.51
NT305 Voltage converter.....	£4.50
NT315 Power supply 250mA, 5V, 500mA, 5V.....	£9.57

Amateur Electronics by Josty-Kit, the professional book for the amateur - covers the subject from basic principles to advanced electronic techniques. Complete with circuit board for AE1 to AE10.
OUR PRICE £3.30 (No VAT) P&P 25p plus VAT.
AE1 100mV output stage..... £1.65
AE2 Pre-amplifier..... £1.26
AE3 Diode receiver..... £2.00
AE4 Flasher..... £1.09
AE5 Astable multi-vibrator..... £1.05
AE6 Monostable multi-vibrator..... £1.02
AE7 RC generator..... £1.06
AE8 555 timer..... 99p
AE9 Treble filter..... 99p
AE10 CCIR filter..... 99p

2 TRANSISTOR RADIO KIT
No Soldering required. All connect-made with spring clips. Kit includes all parts and wire including ear-piece. Complete with all normal broadcasts on Medium Wave 535-1605kHz. Operates from standard 9V battery or Solar Cell included.
OUR PRICE £1.30 P&P 30p

SPECIAL BARGAIN!! STEREO SOUND SPEAKERS
Matched pair of stereo bookshelf speakers. Deluxe teak veneered finish. Size 368 x 229 x 190mm. 8 ohms. 8 watts RMS. 16 watts peak. Complete with Din lead.
OUR PRICE £12.95 P&P 50p

SPECIAL BARGAIN! FERGUSON 3406 HI-FI SPEAKERS
High quality 2 way speaker systems. 25 Watts 4-8 ohms 40Hz-18kHz. Size: 560 x 340 x 255mm approx. Wood grain finish with black fronts.
OUR PRICE £26.95 PR. P&P £1

Model A1018 FM TUNER
5 transistor high quality unit - 3 IF stages and double tuned discriminator. For use with most amplifiers. Covers 88-108MHz. Powered by 9V battery.
OUR PRICE £13.50 P&P 30p
Stereo multiplex adapter £5.95 extra.

ALL PRICES EXCLUDE VAT

SINCLAIR CALCULATORS

Cambridge Kit £23.95 (£2.80)
Cambridge Assembled £25.95 (£3.00)
Executive Memory £39.95 (£4.40)
New Sinclair Scientific £43.95 (£4.80)

FERRANTI ZN414

IC radio chip with data £1.20 (23p). Also available kit of other parts to complete a radio £2.39 (40p). Send sae for free leaflet.

SINCLAIR PROJECT 80

AFU £5.95 (80p)
Z40 £4.85 (67p)
Z60 £5.95 (80p)
Q16 £6.70 (87p)
PZ5 £4.28 (55p)
PZ6 £8.95 (92p)
PZ8 £6.95 (92p)
Decoder £8.45 (85p) Trans for PZ8 £2.95 (50p)
Tuner £9.95 (£1.20) Stereo 80 £9.95 (£1.20)
Send sae for free leaflet on new quadrasonic adapter for use with Project 80 £9.95 (£1.20)



SINCLAIR SUPER IC 12

6W rms power with 44 page booklet and printed circuit £2.10 (43p)



SWANLEY IC TOMORROW

The world's most powerful IC amplifier. Similar to the IC12 but rated at 10W rms power. Supplied with data but no printed circuit £2.60 (47p). 20% discount on 10 + quantities.

DELUXE KIT FOR THE IC12

Includes all parts for the printed circuit and volume, bass and treble controls needed to complete the mono version £1.55 (26p). Stereo model with balance control £3.50 (46p).

IC12 POWER KIT

Supplies 28V 0.5 Amps £2.47 (50p)

LOUDSPEAKERS FOR THE IC12

5" 8 ohm £1.10 (27p). 5" x 8" 8 ohm £1.55 (37p).

PREAMP KITS FOR THE IC12

Type 1 for magnetic pickups, mics and tuners. Mono model £1.30 (24p). Stereo model £2.30 (34p)
Type 2 for ceramic or crystal pickups. Mono 80p (17p). Stereo £1.20 (23p).

SEND SAE FOR FREE LEAFLET ON KITS

BATTERY ELIMINATOR BARGAIN

The most versatile battery eliminator ever offered. Switched output of 3, 4, 6, 7, 9 and 12V at 500 mA £3.95 (70p)



Other eliminators stocked:
500mA—6V £1.50 (30p). 9V £1.50 (30p). 7.5V cassette type £2.25 (30p). Double 6 + 6V £2.50 (35p). 9 + 9V £2.50 (35p).
500mA:—Higher current deluxe models. 6, 7 or 9V (state which) £2.85 (50p).

S-DECS AND T-DECS

S-DEC £1.98 (31p)
T-DEC £3.43 (47p)
M-DEC A £3.99 (51p)
M-DEC B £3.99 (51p)



IC carriers:—
16 dll:—plain 81p (15p). With socket £1.77 (25p).
10 TOS:—plain 78p (15p). With socket £1.66 (24p).
Experiment guides:—A £1.50 (26p). B £1.77 (29p). C 90p (15p). D £2.40 (35p). E £4.20 (53p).

ZIPPY CABINETS

Attractive plastic instrument cases in 4 sizes.
80 x 50 x 30mm 80p (25p). 115 x 65 x 40mm 87p (30p).
155 x 90 x 50mm £1.20 (35p). 210 x 125 x 70mm £1.80 (45p)

ECONOMICAL QUADRAPHONICS

£9.95 (£1.30)
Complete self contained matrix quadrasonic synthesizer in attractive cabinet. Just feed output of ordinary stereo hi-fi into it and hook up to 4 speakers to obtain the latest experience in sound. Send sae for free leaflet.

SWANLEY ELECTRONICS

PO BOX 68, SWANLEY,
KENT BR8 8TQ.

Please add the sum shown in brackets after the price to cover the cost of post and VAT. Official credit orders from schools etc. welcome. No VAT charged on overseas orders.

Surplus Handbooks

R1155 A to N	£2.42
R1392 A & B	£1.43
B40 Rx A to D	£3.85
CR100	£3.85
CT38	£2.42
13A Scope	£2.42
CD518 (CT316)	£2.20
CT52/84	£1.32
730/4 Ex.	£2.20
HRO Ux & Oct.	£2.64
BC221 AF	£2.20
AR88D or L.F.	£2.42
S640 Rx	£1.10
R107 Rx	£1.43
R209	£1.21
19 Set	£2.42
31 Set	£1.65
88 Set	£1.21
Ind 103 & P.U. 917	£1.10
52 Rx	£1.10
62 set inc. xtal Cal.	£2.42
R1475 Rx	£2.42
TF144G	£1.21

Circuits only TF801a, R3673, R220, CRT26, 1035 Mk 1, 2 or 3, 1049 Mk 3a, PCR 2 & 3, ARR-2, APN-9, BC624/5 all 66p ea. Prices inc. Post & VAT.

Above are photostat copies.

A. H. SUPPLIES

57 Main Road, Sheffield S9 5HL
(0742 444278)

RADIO OFFICERS

DO YOU HAVE PMG 1, PMG 11, MPT 2 YEARS OPERATING EXPERIENCE?

Possession of one of these qualifies you for consideration for a Radio Officer post with composite signals organisation.

On satisfactory completion of a 7 month specialist training course, successful applicants are paid on a scale rising to £2893 pa; commencing salary according to age—25 years and over £2126 pa. During training salary also by age, 25 years and over £1604 pa with free accommodation. The future holds good opportunities for established status, service overseas and promotion. Training courses commence at intervals throughout the year. Earliest possible application advised. Applications only from British-born UK residents up to 35 years of age (40 years if exceptionally well qualified) will be considered. Full details from:

RECRUITMENT OFFICER
GOVERNMENT COMMUNICATIONS
HEADQUARTERS

Room A/1105, Priors Road, Oakley,
CHELTENHAM, Glos. GL52 5AJ
Telephone: Cheltenham 21491, Ext. 2270

HONEYWELL PROGRAMMER

This is a drum type timing device, the drum being calibrated in equal divisions for switch setting purposes with trip which are infinitely adjustable for position. They are also arranged to allow 2 operations per switch per rotation. There are 10 changeover micro switches each of 10 amp type operated by the trips thus 10 circuits may be changed per revolution. Drive motor is mains operated 5 revs per min. Some of the many sets of this timer are Machinery control, Boiler firing, Dispensing and Vending machines, Display lighting animated and signs, Signalling, etc. Price from makers probably over £10 each. Special snip price £8.33 plus 25p post and insurance. Don't miss this terrific bargain



12 VOLT 15 AMP. POWER PACK



This comprises double-wound 230/240V mains transformer with full wave rectifier and 3000 µF smoothing. Price £2.20 plus 20p post & packing.

Heavy Duty Mains Power Pack. Output voltage adjustable from 15-40V in steps—maximum load 250W—that is from 6 amp at 40V to 15 amp at 15V. This really is a high power heavy duty unit with dozens of workshop uses. Output voltage adjustment is very quick—simply interchange push on leads. Silicon rectifiers and smoothing by 3,000µF. Price £8.33 plus 63p post.

ISA ELECTRICAL PROGRAMMER



Learn in your sleep! Have radio playing and kettle boiling as you awake — switch on lights to ward off intruders — have a warm house to come home to.

All these and many other things you can do if you invest in an electrical programmer. Clock by famous maker with 15 amp. on/off switch. Switch-on time can be set anywhere to stay on up to 6 hours. Independent 60 minute timer jogger. A beautiful unit. Price £2.15 + 20p p. & p. or with glass front, chrome bezel, 85p extra.

MINI POP RADIO AND CAR CASSETTE BOOSTER

As featured this issue! Our 1974 catalogue lists hundreds of bargains and probably many of the parts needed for this project. 66p brings the catalogue and the next 6 monthly supplements.



DRILL CONTROLLER

NEW IKW MODEL

Electronically reduces speed to approximately 10 revs. Ample power at all speeds. Full power at all speeds by finger-tip control. Kit includes all parts, case, everything and ample instructions. £1.95. Made up model also available £2.95.

MAINS TRANSISTOR P.P.

Designed to operate transistor sets and amplifiers. Adjustable output, 6v, 9v, 12 volts for up to 500mA (class B working). Takes the place of any of the following batteries: PP1, PP3, PP4, PP6, PP7, PP9, and others. Kit comprises: mains transformer, rectifier, smoothing and load resistor, condensers and instructions. Real snip at only £1.10.

MINIATURE SEALED RELAY

American made. Our Ref. No. REL A1. Measures only 1 1/2" wide x 1 1/2" thick and 1 1/2" high and it's a double change over, we don't know the contact rating but estimate this at 3/5 amps. The coil resistance is 600 ohms and 9-12 volt will close it. Ideal for models and miniaturised equipment. It's a plug in relay but we supply complete with base. Price 38p including base.



MINIATURE WAFER SWITCHES

2 pole, 2 way—4 pole, 2 way—3 pole, 3 way—4 pole, 3 way—2 pole, 4 way—3 pole, 4 way—2 pole 6 way—1 pole, 12 way. All at 25p each.

TERMS: 10% discount if ten or an item ordered, send postage where quoted—other items, post free if order for these items is £8.00 otherwise add 20p. ADD 10% VAT.

J. BULL (ELECTRICAL) LTD.

(Dept. pw) 7 Park Street,
Croydon CRO 1YD. Callers to:
102/103 Tamworth Rd, Croydon

Have you done your sums?

**Add THE WORLD RECORD ANTENNA
to THE WORLD FAMOUS TRIO
and YOU HAVE A COMPLETE RADIO STATION
equal TO THE BEST FOR ANY LOCATION—**

**READY TO PLUG TOGETHER IN MINUTES AT A COST LITTLE MORE
THAN THE COST OF THE TRIO ALONE!!!**

FREE

Speaker; Suitably Terminated Connectors; Handbook; Carriage; Insurance. In addition a JOYSTICK V.F.A.; JOYMATCH A.T.U.; feeder external mounting insulators are greatly reduced when you buy a PARTRIDGE PACKAGE.

A PARTRIDGE PACKAGE constitutes a COMPLETE RADIO STATION—ready to use however confined your domestic space. The World renowned TRIO range of Communications Receivers and Transceivers, the WORLD RECORD, internationally patented JOYSTICK V.F.A. (all band aerial) only 7' 6" long (assembled) and a JOYMATCH aerial tuning unit, internal speaker, plus accessories, go to complete your READY TO USE RADIO STATION at a price that truly represents VALUE FOR MONEY!—24 HOUR DELIVERY (MON.-FRI.) ADD £4.00—OUR RISK!

PARTRIDGE PACKAGE (Write for details of more Partridge Packages)
No. 1 with Gen. Coverage AM/CW/SSB (MW/SW) 9R59DS Receiver (£46.75)
PACKAGE PRICE £64.52 (Save £14.28)

NOTHING TO PAY! **OUR RISK** Access/Barclaycard orders accepted by 'phone
JOYSTICK V.F.A. £13.75; JOYMATCH TX/RX A.T.U. 111A 1.6-32 MHz £13.75; JOYMATCH A.T.U. 111 RX only 500 kHz-32 MHz £13.75; JOYMATCH A.T.U. LO-Z500 TX/RX 500w SSB (PA input), Built-in RF meter £19.91; Communications 8Ω headphones (suitable TRIO, EC10 etc.) £3.14; Matching Speaker (with instructions for internal fitting in 9R59DS £2.00; TRIO: Linear Amplifier TL911 £172.15 PLUS £32.50 worth of Partridge equipment FREE; TRIO TR2200 2m personal transceiver £87.45 PLUS £17.50 worth of Partridge equipment FREE; TRIO TR7200 2m car transceiver £142.45 PLUS £28.50 worth of Partridge equipment FREE; 6 spare valves for 9R59DS £2.35; OA2 Mains Stabiliser 74p; 9R59DS £46.75 (VAT incl.) plus FREE Speaker del. OUR RISK.

Amazing "DX-CRYSTAL SET" £2.42 incl. unique aerial. Free with your Partridge Package.

**NEW: AMTRON QUALITY KITS—send for brochure and prices.
PARTRIDGE BUDGET LINE**

Artificial Earth—solves receive and transmit earth problems (as used on North Sea Rigs!) £5.80; Aerial Bandswitch—tuned aerial for domestic receivers £5.80; A.T.U. KIT—for use with transmitters and Communications Receivers £5.80; (assembled £7.01); Mini SWR Bridge—1.8 to 180 MHz, 2kw P.E.P., 75 or 50Ω SO239 sockets; 1:1 to 1:3 ratio, 80 x 30 x 30mm £5.60. (All prices quoted INCLUDE V.A.T., CARRIAGE, PACKING, INSURANCE.)
Send 3½p stamp for full illustrated details. Special TRIO brochures (state which) 3½p stamp extra.

NO V.A.T. ON OVERSEAS ORDERS! Carriage and insurance extra overseas orders.


BOX 5 **PARTRIDGE**
BROADCASTERS WEST ENGLAND
ELECTRONIC LTD

G3CED — G3VFA
FOR EXPERT ADVICE AND INFORMATION
Telephone: 0843 62535 or 62839
evenings and weekends



ELECTROVALUE

CATALOGUE 7

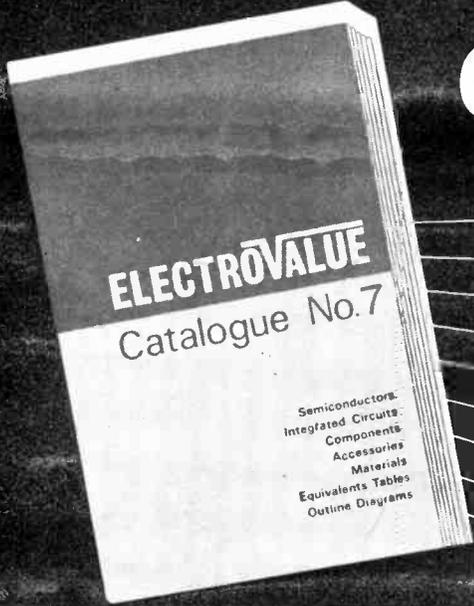

An A to Z guide to component buying

On the index page of Catalogue 7, between "Aluminium Boxes" and "Zener Diodes" are over 200 references to contents amounting in all to thousands of items, classified, described, often illustrated, and priced. There is a wealth of technical diagrams and data. At 25p, Catalogue 7 is excellent value by any standard. With the 25p Refund Voucher it costs you virtually nothing when you order £5-worth or more.

25p INCLUDING 25p REFUND VOUCHER ALLOWABLE ON ORDERS £5 OR MORE LIST VALUE

★ A SELECTION FROM EV CATALOGUE 7

TRANSISTORS

and semi-conductors of many types from simple diodes to ICs photo-sensitive devices, threshold switches, etc. etc.

MINITRON DIGITAL INDICATORS

3015F Seven segment filament, compatible with standard logic modules, 0-9 and decimal point; 9mm characters in 16 lead DIL (some alphabetical symbols available) £1.20
Suitable BCD decoder driver £1.15
3015G showing + or - & 1 & dec. pt. £1.20

DALY ELECTROLYTIC CAPACITORS

in cans, plastic sleeved

1000mF/25V 28p 1000/50 41p
5000/100 £2.91 2000/50 57p
5000mF/25V 62p 5000/50 £1.18

POLYESTER CAPACITORS TYPE C.280

Radial leads for P.C.B. mounting. Working voltage 250V d.c.

0-01, 0-015, 0-022, 0-033, 0-047 ea. 3p
0-068, 0-1, 0-15 ea. 4p
0-22, 5p; 0-33 7p; 0-47 8p; 0-68 11p; 1-0 14p;
1-5 21p; 2-2 24p

SILVERED MICA CAPACITORS

Working voltage 500V d.c.

Values in pFs—2 to 820 in 32 stages ea. 6p
1000, 1500 7p; 1800 8p; 2200 10p; 2700, 3600 12p;
4700, 5000 15p; 6800 20p; 8200, 10,000 25p

POTENTIOMETERS

ROTARY, CARBON TRACK. Double wipers for good contact and long working life

P.20 SINGLE linear 100ohms to 2-2megohms, ea. 14p
P.20 SINGLE log. 4-7Kohms to 2-2megohms, ea. 14p
JP.20 DUAL GANG lin. 4-7Kohms to 2-2megohms, ea. 48p

JP.20 DUAL GANG log. 4-7Kohms to 2-2megohms, ea. 48p

JP.20 DUAL GANG Log/antilog 10K, 22K, 47K, 1 megohm only ea. 48p

JP.20 DUAL GANG antilog 10K only 48p
2A DP mains switch for any of above 14p extra.
Decades of 10, 22 and 47 only available in ranges above.

Skeleton Carbon Presets Type PR, horizontal or vertical 6p each.

SLIDER POTENTIOMETERS

Linear or log, 10K to 1 meg. in all popular values ea. 30p
Escutchion plates, black, white or light grey, ea. 10p
Control knobs, blk/wht/red/yel/grn/blue/dk. grey/lt. grey ea. 7p

ZENER DIODES

Full range E24 values: 400mW: 2-7V to 36V, 14p each;
1W: 6-8V to 82V, 21p each; 1-5W: 4-7V to 75V, 48p each. Clip to increase 1-5W rating to 3 watts (type 266F), 5p.

RESISTORS

Code	Watts	Ohms	1 to 9	10 to 99	100 up
C	1/20	82-220K	9	8	7-5
C	1/3	4-7-470K	1-3	1-1	0-9 nett
C	1/2	4-7-10M	1-3	1-1	0-9 nett
C	3/4	4-7-10M	1-5	1-2	0-9 nett
C	1	4-7-10M	3-2	2-5	1-9 nett
MO	1/2	10-1M	4	3-3	2-3 nett
WW	1	0-22-3-9	9	9	8
WW	3	1-10K	7	7	6
WW	7	1-10K	9	9	8 nett

Codes:

C = carbon film, high stability, low noise.
MO = metal oxide, ElectroSil TR5, ultra low noise.
WW = wire wound, Plessey.

Values: All E12 except C 1/3W, C 1/2W, and MO 1/2W.
E12: 10, 12, 15, 18, 22, 27, 33, 39, 47, 56, 68, 82 and their decades.

E24: as E12 plus 11, 13, 16, 20, 24, 30, 36, 43, 51, 62, 75, 91 and their decades.

Tolerances:

5% except WW 10% ±0.05Ω and MO 1/2W 2%.

Prices are in pence each for quantities of the same ohmic value and power rating. NOT mixed values. (Ignore fractions of one penny on total value of resistor order.) Prices for 100 up in units of 100 only.

VEROBOARD

Copper clad 0-1 matrix—2-5 x 3-75 ins. 24p; 3-75 x 3-75 ins.—27p; 2-5 x 5 ins.—27p; 3-75 x 5 ins.—30p.
Copper clad 0-15 lin. matrix 2-5 x 3-75 ins.—18p;
3-75 x 3-75 ins.—27p; 2-5 x 5 ins.—27p; 3-75 x 5 ins.—33p.

Vero spot face cutter (any matrix) 43p.
0-040 pins (for 0-1 matrix) per 100—30p.
0-052 pins (for 0-15 matrix) per 100—30p.

ELECTROVALUE LTD

28, ST. JUDES ROAD, ENGLEFIELD GREEN, EGHAM, SURREY TW20 0HB
Telephone Egham 3603 Telex 264475 Shop hours 9-5.30 daily Sat. 9-1 p.m.

NORTHERN BRANCH: 680, Burnage Lane, Burnage, Manchester M19 1NA
Telephone (061) 432 4945 Shop hours 9-1 p.m. 2-5.30 daily Sat 9-1 p.m.

Hours of business (both addresses) 9-5.30 p.m., 9-1.30 Saturdays.

U.S.A. CUSTOMERS are invited to contact ELECTROVALUE AMERICA, P.O. Box 27, Swarthmore PA 19081.

BAXANDALL SPEAKER KIT

As designed by P. J. Baxandall and described originally in "Wireless World." Simple to assemble, fantastically good results and a greater money saver. Carries 10 watts RMS, 15 ohms impedance. Size 18ln x 12ln x 10ln. Complete kit, including pack-flat cabinet, £14.90. The size and weight of this product obliges us to charge 70p part cost of carr. in U.K. Equaliser Assembly, £2.30. Loudspeaker Unit 59RM109, £2.45. Cabinet Kit (to Baxandall design), £10.45. Cross-over choke included in full kit above, £1.30.

This is EV Service

DISCOUNTS

Available on all items except those shown with NETT PRICES. 10% on orders from £5 to £14.99. 15% on orders £15 and over.

PACKING AND POSTAGE FREE

in U.K. For mail orders for £2 list value and under there is an additional handling charge of 10p.

GUARANTEE OF QUALITY

All goods are sold on the understanding that they conform to manufacturers' specifications and satisfaction is guaranteed as such—no rejects, 'seconds' or sub-standard merchandise is offered for sale.

Prices quoted do not include V.A.T., for which 10% must be added to total net value of order. Prices subject to alteration without notice.

GIRO ACCOUNT No. 38/671/4002


All postal communications, mail orders etc. to Head Office at Egham address. S.A.E. with enquiries requiring answers.

SAXON

Money saving high performance audio equipment
DIRECT FROM OUR OWN FACTORY

GUARANTEED TESTED HIGH PERFORMANCE MODULES—now better value than ever

- | | | | |
|---|---------------|---------------|---|
| SA35
35W RMS 25-50V
7 transistors, 7 diodes | £4-45 | Carriage free | <ul style="list-style-type: none"> ★ 25Hz-25kHz ★ 0.2% distortion ★ Noise—80dB ★ 500mV into 20K ★ 4-16 ohms ★ Simple wiring ★ Short and open circuit proof ★ Continuously rated ★ Top-grade components |
| SA50
50W RMS 25-65V
7 transistors, 7 diodes | £5-65 | Carriage free | |
| SA100
100W RMS 45-70V
11 transistors, 6 diodes | £10-90 | | |
| 120 watt module complete with built-in supply—extra heavy duty | | | |
| | £19-75 | Carr. 60p | |

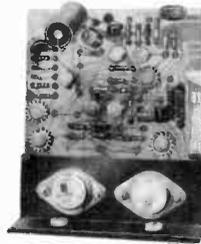

THE SA100 MODULE


POWER SUPPLIES

- | | | | |
|---------------------|-------------------------|--------------|---------------|
| UNSTABILISED | | | |
| PU45 | Suits 2 SA35 or 1 SA50 | £4-90 | Carriage 30p |
| PU70 | Suits 2 SA50 or 2 SA100 | £7-75 | Carriage 40p |
| STABILISED | | | |
| PS45 | Suits 2 SA35 or 2 SA50 | £3-50 | Carriage free |
| MT45 | Transformer for above | £3-50 | Carriage 30p |
| PS70 | Suits 2 SA100 | £4-90 | Carriage free |
| MT70 | Transformer for above | | |

N.B. PS70 is not suitable for the SA50

Mk II STEREO DISCO MIXER £19-75 Carr. 30p

This well tried unit mixes two decks, handles any ceramic cartridge, and features mic override plus separate full range bass and treble controls on both mic and deck inputs. Ample headphone power is available for P.F.L. May be used for mono and is mains operated. Fitted with sturdy screening case. Controls: Mic vol, bass, treble. Left/Right fade, deck volume, bass, treble, headphone select, vol, Mains. Size 17 1/2in x 3in x 4in deep.

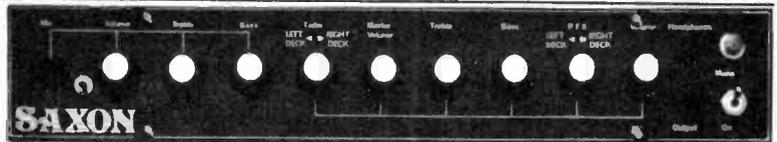

DISCO MODULE £8-00 Carr. 20p

Thousands sold of this extremely popular mono version. A mic input may be fitted using the VA30 (see below). Low consumption from a 9V battery. Features the same high standards of reproduction as the Stereo version. Controls: H/phone select, vol, Left deck vol, Right deck vol, bass, treble, master vol. Size 12 1/2in x 3in x 2in deep.



3-CHANNEL SOUND-LITE £22-50 Carr. 30p


Only SAXON can supply such incredible value for money. This unit features 3kW power handling, full-wave control, bass, middle, treble AND master controls. Twin loudspeaker jacks for "through" connections. It may be used free standing or will panel mount next to either of the above. Also features unique CUT-BACK circuitry for extra wide range response. Size 12in x 3in x 2 1/2in deep. Professional standards at a price you can afford!



SINGLE CHANNEL VERSION £7-50 Carr. free
Recently reduced in price due to increasing sales, handles 1kW. Full wave operation

MULTI-PURPOSE MIXERS

M4HL £18-50 Carr. 50p
Featuring multiples of our VA30 module, the M4HL and M6HL fulfil the requirements of all clubs, groups, etc. where a high quality mixer is required. Each channel has one high and one low impedance input, plus volume, treble and bass controls. Input impedances may, if required, be easily changed. The M4HL has four channels, and one output, and the M6HL six channels (12 inputs) and a master control and two outputs. Either unit may be used free-standing or panel mounted. These mixers will feed all types of amplifier. Recommended for their versatility and high performance, and excellent value for money.

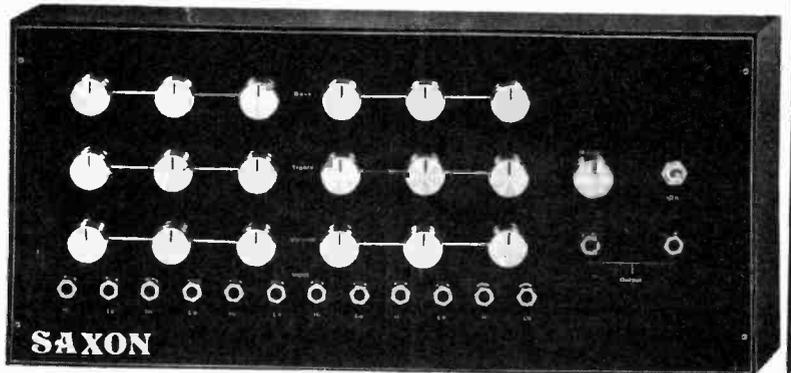


VA30 CHANNEL MODULE £3-50 Carr. free

This is the basic channel module in the above mixers and may also be used for extra inputs on either the mono or stereo mixers. Fitted with volume, bass and treble controls, requires just a jack and supply (9-100V)

SAXON CSE 100 COMPLETE AMPLIFIER £34-90 Carr. free

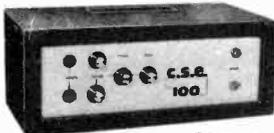100W of speech and music—Two separately controlled inputs. Wide range bass and treble controls. Sturdy and attractive vinyl case. Twin outputs. Ideal for groups, discos, etc. Fully tested and guaranteed. 50W version identical in appearance.



CSE 50 £29-50 Carr. free



Four individually controlled FET input stages, plus wide range bass and treble controls. 120W of speech and music output from twin loudspeaker sockets. Sturdy case, and an attractive fascia make this excellent value for money. Hundreds in use by groups, discos, clubs, etc. 50W version identical in appearance.

SAXON 100 COMPLETE AMPLIFIER £53-00 Carr. free
SAXON 50 £37-50 Carr. free

CALLERS AND MAIL ORDER:

SAXON ENTERTAINMENTS LIMITED
327-333 WHITEHORSE ROAD • CROYDON CR0 2HS

(Please quote magazine when ordering)
SHOP HOURS: 9 a.m. - 5 p.m. — LUNCH 12.30 - 1.30 p.m. MAIL ORDER DESK: 10 a.m. - 3 p.m.
24-HOUR ANSWER SERVICE TEL. 01-684 6385


SEND 10p FOR OUR NEW 26-PAGE MANUAL which gives full details of the above products.

TERMS OF BUSINESS: C.W.O. or C.O.D. on receipt of 50p C.O.D. charge.

Please include S.A.E. with all enquiries. VAT at 80% must be added to all orders including postage and carriage charges.

YOU AIN'T HEARD NOTHIN' YET !!

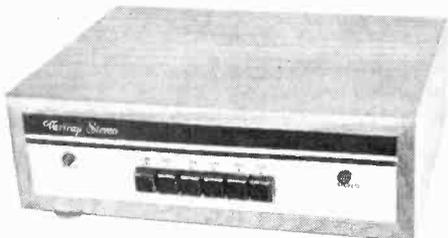... until you tune in to stereo
perfection with 'Varicap'



'p.e.' f.m.
varicap stereo tuner

Size approx.
8½" x 2½" x 6½"

This elegant and practical stereo tuner features push button 'spot-on' tuning with up to five simple pre-set stations (no difficult tuning dial and drive cord). It's easy 'no problem' construction requires only a few simple setting adjustments with a D.C. Voltmeter. It incorporates NEW pre-set modules for R.F. and I.F. circuits, this eliminates the need for the usually difficult circuit alignment.

All this, coupled with the latest Motorola high efficiency, Integrated Circuit 'phase lock loop' stereo decoder and automatic stereo lamp indicator, ensures perfect stereo reception.

The 'Varicap' is, in our opinion, THE most easily constructed stereo tuner available which will achieve professional results.

The kit comprises Fibre glass P.C. board, elegant slimline leak veneer cabinet, brushed aluminium front panel, push buttons, instructions, in fact everything you need.

We also supply any of these kit components as separate items.

Total kit price ONLY £28.50 (inclusive of VAT and postage).

IDEAL FOR USE WITH THE 'TEXAN', 'GEMINI' OR ANY OTHER GOOD QUALITY STEREO AMPLIFIER.

PARTS FOR PRACTICAL WIRELESS PROJECTS:

After many requests, Electro Spares are supplying lists of components for ALL projects featured in 'Practical Wireless' from July 1973 issue onwards. We regret that we cannot supply lists for projects published before this date.

All you have to do is send us a stamped addressed envelope, not less than 9" x 4", stating which project is of interest to you. We will then forward you an individually priced list of the components required, there is, of course, no necessity to purchase a full kit, you may purchase only the parts you require at any one given time. We believe this method of 'one source' buying can save you time and postage—AND THAT MEANS MONEY !!

ALL COMPONENTS SUPPLIED BY ELECTRO SPARES ARE NEW, BRANDED PRODUCTS OF REPUTABLE MANUFACTURERS AND THEREFORE CARRY THE MAKERS FULL GUARANTEE.

'P.E.' 'GEMINI' STEREO AMPLIFIER

The 'Gemini' is a quality hi-fi stereo amplifier for the home constructor, featuring a genuine 30 watt R.M.S. per channel output into 8 ohms. Total harmonic distortion of 0.02% and a frequency response (-3dB) 20Hz - 100kHz, at all power levels.

We are continuing to supply components for this fabulous amplifier, which is now recognised as practically THE ultimate in High-Fidelity.

We know no better unit for the home constructor—hundreds have been supplied throughout the world.

Electro Spares have available a booklet containing full specification, complete constructional information, wiring diagrams and fault finding guide etc.

The price is 55p + 4p postage, along with which we will send you our new LOW PRICE LIST. Price list available separately on receipt of a large S.A.E.

Our new Mail Order department address is set below. We aim for quick, efficient service—or why not pay us a call, we make all enthusiasts welcome and there are no parking problems.

ELECTRO SPARES

288 ECCLESALL ROAD
SHEFFIELD S11 8PE
Tel. (0742) 668888

'The Component Centre of the North'

es

Radio Control Kits from AMTRON

New from AMTRON—these Radio Control units in kit form. Enjoy building your own Radio Control Receivers and Transmitters and Field Strength Meters. An accurate setting up of Radio Control Transmitters can be made with the help of the UK 555 Field Strength Meter. 3 transistors, 1 diode plus meter make this unit a very sensitive device.



PRICES

UK 300 Four Channel Radio Con. Transmitter £6.55
UK 310 Radio Control Receiver £3.28
UK 345 Radio Control Receiver £6.55
UK 555 Field Strength Meter £10.61

All prices inclusive of VAT

**AMTRON
UK**


THE BIG NAME IN ELECTRONIC KITS

4 & 7 Castle Street Hastings Sussex TN34 3DY.
Telephone: Hastings 2875



I.L.P. (Electronics) Ltd

SECOND GENERATION 25 WATT HYBRID

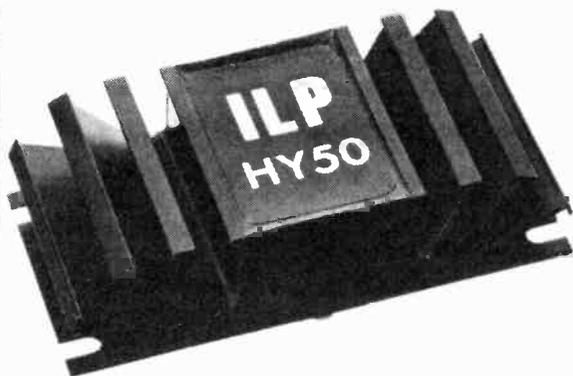


A brand new hybrid fabrication technique, recently perfected in our laboratories, has enabled us to achieve our latest range of completely integrated devices. We have now finally reduced the modular amplifier to a simple input/output device requiring only the addition of a basic unregulated (split line) power supply. The HY50 takes medium power modules to their logical conclusion by incorporating with it a heatsink, which is designed in special high conductivity alloy, sufficient for normal audio use without additional chassis sinking. All this without significantly increasing the size of the module comparable in size to a packet of 'King-size' cigarettes.

Consistent with modern thinking a triple rated output circuit with a load fuse allows for peak transient response without distortion but ensures the necessary protection.

OUTPUT POWER: 25 watts RMS. 50 watts peak music power
LOAD IMPEDANCE: 4-16Ω into 8Ω
INPUT SENSITIVITY: 0db (0.775 volts RMS)
INPUT IMPEDANCE: 47KΩ
TOTAL HARMONIC DISTORTION: Less than 0.1% at 25 watts typically 0.05 better than 75db
SIGNAL/NOISE RATIO: 10Hz-50KHz ± 1db
FREQUENCY RESPONSE: ± 25 volts
SUPPLY VOLTAGE: 105 x 50 x 25 mm
SIZE:

Price £5.80 mono, £11.60 stereo
Price inclusive of VAT & P & P

NEW HY5 PRE-AMPLIFIER

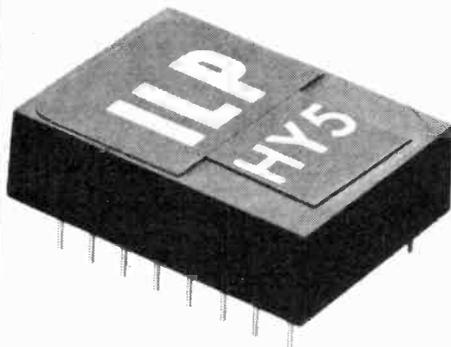

Unchallenged for two years, the HY5, our unique multifunction preamplifier/tone hybrid, has been brought into line with the advancements in our power hybrids. Like the HY50, the new HY5 has no external components & has been redesigned to run off a split power-line with improvements in signal/noise, overload, capability & reduced distortion. The output has been increased to match the power module (Odb), and to share the same power supply. Overall size is reduced by the use of a new thin film circuitry while the device still retains all the functions of the earlier device.

When combined with the HY50 & power supply only potentiometers are required to complete a simple mono amplifier with input & output facilities expected to be found on Hi-Fi amplifiers. The combination of two HY5's two HY50's sharing a common power supply (PSU50) are linked by a balance control to form a complete stereo system.

INPUTS
Magnetic Pick-up 3mV (within 1db RIAA curve)
Ceramic Pick-up up to 3mV
Microphone 10mV
Tuner 250mV
Auxiliary 3-100mV
Input impedance 47kΩ 1kHz

OUTPUTS
Tape 100mV
Main output, 0db (0.775volts)

ACTIVE TONE CONTROLS
Treble ± 12db at 10kHz
Bass ± 12db at 100Hz

OVERLOAD CAPABILITY (equalization stage) 40db on most sensitive input

OUTPUT NOISE LEVEL (below 10mV magnetic input) 68db

DISTORTION 0.05% at 1kHz

SUPPLY VOLTAGE ± 16-25 volts

SUPPLY CURRENT 15mA

Price £4.85 mono, £9.70 stereo

Price inclusive of VAT & P & P



POWER SUPPLY PSU50

The new PSU50 has a low profile look being only 2 1/2 inches high and can be used for either mono or stereo systems.

SPEC.
OUTPUT VOLTAGE ± 25 volts
INPUT VOLTAGE 210-240 volts
SIZE L. 70, D. 90, H. 60 mm

Price £5.23
Price inclusive of VAT & P & P

CROSSLAND HOUSE · NACKINGTON · CANTERBURY · KENT

CANTERBURY 63218

Please note we reserve the right to substitute at our discretion updated versions of advertised designs where applicable.

Practical Wireless Classified Advertisements

The pre-paid rate for classified advertisements is 10p per word (minimum 12 words), box number 20p extra. Semi-displayed setting £8.00 per single column inch. All cheques, postal orders, etc., to be made payable to PRACTICAL WIRELESS and crossed "Lloyds Bank Ltd." Treasury notes should always be sent *registered post*. Advertisements, together with remittance, should be sent to the Classified Advertisement Manager, PRACTICAL WIRELESS, IPC Magazines Ltd. Fleetway House, Farringdon Street, London, EC4A 4AD for insertion in the next available issue.

Aerials

GENUINE FULL SIZE
18 element TV aerial
 as used by leading
 TV companies



FOR ONLY **£2.20**
 + 35p carr

ITV, BBC1 & 2B/W & Colour Guaranteed Perfect Pictures. Save £15. We supply this genuine UHF aerial for only £2.20 can be fitted outside or inside. Quality made technically advanced design. Precision grid/reflector elements ghosting. Complete with clamp instructions advice. Money Back Refund. Wall/Caravan Bracket 25p. Low Loss Cable 10p per yard. Plug 8p & FREE with order maps & channel reference for all Radio & TV Transmitters AND DIRECT TO DEPT. PW10
 219 Mansfield Rd. Nottingham.

IMPERIAL TRADING (AERIALS) LTD.
 the quality Aerial Specialists.

J. AND A. TWEEDY LTD. incorporating **BAINES HIGH FREQUENCY AERIALS**
 VAT Incl. Postage paid inland.
Parabeams UHF Aerials. PBM 12 £3-60. PBM 18 £4-60
Multibeams UHF Aerials. MBM 30 £4-70.
 MBM 46 £7-40. MBM 70 £12-95
 Multibeam Stacking Kit £4-99. Log Periodic £8-40
Stereobeams FM/VHF. SBM2 £3-15. SBM3 4-70
 SBM4 £5-15. SBM 6 £7-75. Stacking Kit £2-35
 Aerial Rotator £31-50. Balun £1-60
Amplifiers. Masthead VHF or UHF Grouped £8-95
 Setback £4-50.
Accessories. SAE for list. Coax 5p/m and 10p/m
 79 Chatsworth Road, Chesterfield S40 2AP
 Telephone 34982 863755 (Evenings)

Service Sheets

LARGE SUPPLIER OF SERVICE SHEETS

(T.V., RADIO, TAPE RECORDERS, RECORD PLAYERS, TRANSISTORS, STEREOGRAMS, RADIOGRAMS, CAR RADIOS)
 ALL AT 40p EACH

"PLEASE ENCLOSE LARGE S.A.E. WITH ALL ENQUIRIES & ORDERS"

Otherwise cannot be attended to
 (Uncrossed P.O.'s please, original returned if service sheets not available.)

PLEASE NOTE

We operate a "by return of post" service. Any claims for non-delivery should be made within 7-days of posting your order.

C. CARANNA
 71 BEAUFORT PARK
 LONDON, N.W.11 6BX

We have the largest supplies of Service Sheets (strictly by return of post). Please state make and model number alternative. Free TV fault tracing chart or TV list on request with order.

Mail order or phone 01-458 4882

SERVICE SHEETS • MANUALS • BOOKS

SERVICE SHEETS 40p plus S.A.E. ★ SERVICE SHEET CATALOGUE 25p
 OVER 12,000 SERVICE SHEETS & MANUALS IN STOCK ON COLOUR/MONO TELEVISIONS
 RADIOS, RADIOGRAMS, T/RECORDERS, R/PLAYERS, ETC. S.A.E. WITH ENQUIRIES

- NEW BOOKS & PUBLICATIONS**
- | | |
|--|-------|
| HANDBOOK OF TRANSISTOR EQUIVALENTS & SUBSTITUTES. 1st. Book by Babani | £0.40 |
| HANDBOOK OF TRANSISTOR EQUIVALENTS & SUBSTITUTES. 2nd. Book by Babani | £0.95 |
| HANDBOOK OF RADIO TV TUBE & VALVE EQUIVALENTS by Babani | £0.40 |
| HANDBOOK OF INTEGRATED CIRCUITS (ICs) EQUIVALENTS & SUBSTITUTES | £0.75 |
| COMPREHENSIVE COLOUR TV MANUAL. Pinpoints faults with cures on Colour TVs | £2.80 |
| COMPREHENSIVE BLACK & WHITE TV MANUAL. Vol. 1. by McCourt. Also lists faults | £2.80 |
| RAPID SERVICING OF TRANSISTOR EQUIPMENT 2nd. Edition by G.J. King. 184pp. | £1.90 |
| HOW TO CHOOSE AND USE TAPE RECORDERS by H.W. Hellyer. 239pp | £2.25 |
| HOW TO GET THE BEST OUT OF YOUR TAPE RECORDER by P.J. Guy. 142pp. | £1.50 |
| WORLD RADIO TV HANDBOOK 1972. 26th Edition. 384pp. Special reduced offer | £0.90 |
| QUESTIONS & ANSWERS ON INTEGRATED CIRCUITS by R.G. Hibberd. 96pp | £0.75 |
| BEGINNERS GUIDE TO ELECTRONICS 3rd. Edition. by T.L. Squires. 240pp | £1.90 |
| 110 THYRISTOR PROJECTS USING SCRs AND TRIACS by R.M. Marston. 146pp | £1.40 |
| 110 INTEGRATED CIRCUIT PROJECTS FOR THE HOME CONSTRUCTOR. Marston | £1.20 |
| 50 SEMICONDUCTOR PROJECTS FOR THE HOME CONSTRUCTOR. Marston. 134pp | £1.20 |
| 50 PHOTOELECTRIC CIRCUITS AND SYSTEMS by P.S. Smith. 88pp | £1.30 |
| TV TECHNICIANS BENCH MANUAL by G.R. Wilding. 187pp | £2.50 |
| TELEVISION ENGINEERS POCKET BOOK by P.J. McGoldrick. 6th Edition. 400pp | £2.50 |
| TRANSISTOR AUDIO & RADIO CIRCUITS by Mullard Ltd. 2nd Edition. 230pp | £1.80 |
| MAZDA BOOK OF PAL RECEIVER SERVICING by D.J. Seal. 288pp. | £3.80 |
- ★ A LARGE SELECTION OF OTHER TITLES AVAILABLE AT OUR NEW SHOP PREMISES ★
 OPEN UNTIL 6pm DAILY & 8pm SATURDAY. CALLERS WELCOME TO COME AND BROWSE
 NEWNES RADIO & TELEVISION SERVICING books bought & sold (all years) good prices paid
 BACK ISSUES OF PW, PE, PT, ETC. WANTED ANY QUANTITY. Please write for quotation.
 Please add 10% for Postage and Packing on all books. Send large S.A.E. for FREE booklists

BELL'S TELEVISION SERVICES

190, KINGS ROAD, HARROGATE, YORKSHIRE. Telephone 0423-55885

SERVICE SHEETS, Radio, TV etc., 8,000 models. Catalogue 15p. S.A.E. enquiries. Telray, 11 Maudland Bank, Preston.

SERVICE SHEETS for Televisions, Radios, Transistors, Record Players, Tape Recorders, etc., from 5p with free Fault-Finding Guide. Over 10,000 models available. S.A.E. enquiries. Catalogue 20p and S.A.E. Hamilton Radio, 47 Bohemia Road, St. Leonards, Sussex. Telephone Hastings 29066.

For Sale

TV LINE OUTPUT TRANSFORMERS
 Tidman Mail Order Ltd., 236 Sandycombe Rd., Richmond, Surrey, TW9 2EQ. 01-948 3702.

SEEN MY CAT? 5,000 items. Mechanical & Electrical Gear, and materials. S.A.E. K. R. WHISTON, Dept. PW, NEW MILLS, Stockport.

LIGHTSHOW PROJECTORS from only £17, effect wheels from only £4. Many lightshow bargains at ROGER SQUIRE'S (Disco Centre), 176 Junction Road, London N19. Tel. 01-272 7474.

BURNDEPT, 3 valve receiver with horn loudspeaker. Working. £40 O.N.O. Tel. Aylesbury 630257.

PHILIPS Cassette recorder spares. S.A.E. with enquiries. Sweeney Limited, 94 Derby Lane, Liverpool L13 3DW.

P.W. 100—1961 to 1971. P.T. 198 No. 2 to 240, speakers. Valves new and used. S.A.E. L. Fenton, 25 Queen Street, East Ardsley, Wakefield, Yorks.

VARIOUS numbers of PRACTICAL WIRELESS from 1957 to 1972. 92 different numbers. Offers for the lot to Webb, Neasden Hill, Green Lane, Dockenfield, Farnham, Surrey.

Offers invited for redundant **STORNO VHF RADIO COMMUNICATION EQUIPMENT** 68/88 megacycles 50 watt module stations, 10 watt static and mobile transceivers.

Write to County Surveyor, The Castle, Winchester, by 30 April 1974 for further details.

Wanted

TOP PRICES PAID FOR NEW VALVES and TRANSISTORS

popular T.V. and Radio types.
KENSINGTON SUPPLIES (C),
 367 Kensington Street, Bradford 8, Yorkshire.

WE BUY New Valves, Transistors and clean new components, large or small quantities, all details, quotation by return. **WALTON'S,** 55 Worcester Street, Wolverhampton.

EARLY WIRELESS LITERATURE before 1934. Johnson Raffles, Haverbreaks, Lancaster. Telephone 67770 evenings.

Situations Vacant

Bench Service Engineers

GILDERSOME, LEEDS

Bench Service Engineers with previous experience of TV (Monochrome and Colour), Radio, Hi-Fi and Tape Recorders will find our wide product range interesting and absorbing.

We have vacancies for 3 Bench Servicing Engineers, one of whom should also have VTR experience. Preference will be given to holders of C. & G. qualifications, though proven practical experience may outweigh formal qualifications. We have a progressive grading system approved by the Pay Board with basic salary on starting up to £2054, depending upon the grade achieved on examination. With Company bonus and overtime Grade I engineers can obtain earnings around £2400 in their first year. In addition there are L.V.'s, discounted staff purchases and a contributory pension scheme.

Interested candidates are invited to apply with details of past experience, age and current salary, (or ring Morley 69421 for an application form) to:—

Regional Manager, Sony (U.K.) Ltd., Universal Estate, Wakefield Road, Gildersome, Morley, Leeds, LS27 7JJ.

SONY®

**MEN!
£70p.w.
can be yours**

Jobs galore! 144,000 new computer personnel needed by 1977. With our revolutionary, direct-from-America, course, you train as a Computer Operator in only 4 weeks! Pay prospects? £3500 — p.a. After training, our exclusive appointments bureau—one of the world's leaders of its kind—introduces you FREE to world-wide opportunities. Write or 'phone TODAY, without obligation.

London
Computer Operators
Training Centre
T66, Oxford House
9-15, Oxford Street, W.1.
Telephone: 01-734 2874

Educational

ENGINEERS—get a technical certificate. Postal courses in Engineering, Electronics, Radio, T.V. Computers, Draughtsmanship, Building, etc. FREE book form: BIET (Dept. BPW.4 Aldermaston Court, Reading, RG7 4PF. Accredited by CACC. Member A.B.C.C.

CITY & GUILDS EXAMINATIONS

Make sure you succeed with an ICS home study course for C & G Electrical Installations, Telecommunications Technicians and Radio Amateurs. Free details from: International Correspondence Schools, Dept. 732H, Intertext House, London, SW8 4UJ.

COLOUR TV SERVICING

Make the most of the current boom. Learn the techniques of servicing Colour & Mono TV sets through new home study courses, approved by leading manufacturers. Also radio and audio courses. Free details from: International Correspondence Schools, Dept. 732H2, Intertext House, London, SW8 4UJ.

TECHNICAL TRAINING

Get the qualifications you need to succeed. Home study courses in Electronics and Electrical Engineering, Maintenance, Radio, T.V. Audio, Computer Engineering & Programming. Also self build radio kits. Free details from: International Correspondence Schools, Dept. 732H3, Intertext House, London, SW8 4UJ.

AMIMI, MAA/LMI DIPLOMA, City & Guilds, etc. Thousands of passes. For details of postal courses in all branches of Engineering and illustrated book—FREE—BIET (Dept. BPW.3) Aldermaston Court, Reading RG7 4PF. Accredited to CACC. Member A.B.C.C.

Books and Publications

Technical Books — Radio & Electronics

Handbook of Tested Transistor Circuits.....	£0-40
Radio Servicing for Amateurs.....	£0-20
Coil Design and Construction Manual.....	£0-30
Boys Bk of Crystal Sets and Simple Circuits.....	£0-18
Transistor Circuits Manual No. 1.....	£0-15
Transistor Circuits Manual No. 2.....	£0-15
Transistor Circuits Manual No. 4.....	£0-40
Transis Circuits for Radio Controlled Models.....	£0-15
Rad & Electr Colour Codes and Data Charts.....	£0-40
Handbk of Transistor Equiv. and Substitutes.....	£0-40
Hi Fi, PA & Disco Amplifier Design Hndbk.....	£0-75
Radio Servicing Problems.....	£0-45
Electronic Circuits for the Amat Photographer.....	£0-60
Handbook of Simple Transistor Circuits.....	£0-35
Modern Transistor Circuits for Beginners.....	£0-40
Sound and Loudspeaker Manual.....	£0-50
Practical Car Radio Handbook.....	£0-30
Radio TV and Industrial Tube & Valve Equiv.....	£0-40
Know Your Oscilloscope.....	£1-70
Television Servicing Vol. No. 1.....	£0-85
Television Servicing Vol. No. 3.....	£0-60
Television Servicing Vol. No. 4.....	£0-85
Using an Oscilloscope.....	£0-70
Servicing Transistor Radio Receivers.....	£0-75
Television Timebase Circuits.....	£1-00

NEW TITLES NOW AVAILABLE

2nd Book of Hi Fi Loudspeaker Enclosures.....	£0-60
Manual of Electronic Circuits for the Home.....	£0-50
Modern Crystal Set Circuits for Beginners.....	£0-35
Electronic Novelties for the Motorist.....	£0-50
2nd Book of Transistor Equiv. & Substitutes.....	£0-95
Handbook of Electronic Musical Novelties.....	£0-50
Transistorised Novelties for Hi Fi Enthusiast.....	£0-35
Fault Location Exercises in Rad. & TV Vol.1.....	£0-80
Fault Location Exercises in Rad. & TV Vol.2.....	£1-35
Colour TV Picture Faults.....	£2-50
99 Ways to Improve your Sh.Wave Listening.....	£1-90
Semi-conductors from A—Z.....	£1-50
Modern Electronic Troubleshooting.....	£1-30
104 Ham Rad. Proj. for Novice & Technician.....	£1-25
How to Solve Solid State Circuit Troubles.....	£1-75
Integrated Circuits Equiv. & Substitutes Hbk.....	£0-75

PLEASE ADD 10% FOR POSTAGE & PACKING

FREE lists of other titles avail on request. Send to:

RADIO BOOK SERVICE
40 Elwill Way, Beckenham BR3 2RZ

FOR SHORT WAVE LISTENERS:

We publish World Radio Bulletin
We stock World Radio TV Handbook
Sole agency for Giffler Associates, Inc.
We publish Broadcasts to Europe
We import I.T.U. handbooks and lists
No other British trader is connected.

DAVID MCGARVA

PO Box 114 - Edinburgh - EH1 1HP

Please send an S.A.E. for lists

"FROM SEMAPHORE TO SATELITE", a 300-page hardcovered history of communications with 1000 illustrations, is sent from Geneva to readers who send £1.99 to David McGarva, PO Box 114, Edinburgh EH1 1HP. We sell books, publish World Radio Bulletin and print monitors' reporting forms.

UFO Charts: Wave Prediction, 49p; Daily Flight Pattern, 44p; Map, 44p; TV UFO Detection, 2 Optical Circuits, 55p; Propulsion Theory, 55p; Circuits: Transistor Optical, 66p; Radiation/Optical, 40p; Microdetector with memory, LSI 75p. R. & E., Highlands, Needham, Suffolk.

WE HAVE your World Radio TV Handbook, the guide to broadcasts, at David McGarva. Just send £3.15, or pay the postman £3.56 on delivery. Box 114, Edinburgh EH1 1HP.

Receivers and Components

**GUARANTEED SEMICONDUCTORS
FAST SERVICE — LOW PRICES**

AC125	14p	2N706	12p	ZENER DIODES
AC126	14p	2N930	22p	400 mW 5%
AC127	14p	2N1131	24p	3.3 to 33 volts.
AC128	14p	2N1132	24p	10p each
BC107	10p	2N2139	14p	
BC108	10p	2N2904	18p	1 Watt 5%
BC109	10p	2N2905	25p	3.3 to 200 volts
BC157	18p	2N3053	20p	20p each
AF114	16p	2N3054	44p	
AF115	16p	2N3055	44p	
AF116	16p	2N3702	11p	RECTIFIERS
AF117	16p	2N3703	11p	P.I.V. 1 amp.
BCY71	21p	2N3704	11p	60 1N4001 5p
BCY72	16p	2N3705	11p	100 1N4002 5p
BFX84	28p	2N3706	11p	200 1N4003 8p
BFX86	28p	2N3707	11p	400 1N4004 8p
BFX87	28p	2N3708	11p	600 1N4005 7.1p
BFX87	28p	2N3709	11p	800 1N4006 8.1p
BFX88	22p	2N1711	22p	1000 1N4007 9.1p

CASH W.O. PLUS P.P. 10p TO
ROGESS SERVICES, PARNDON HALL,
HAMSTEL ROAD, HARLOW, ESSEX

PRECISION POLYCARBONATE CAPACITORS

Close tolerance. High stability. Extremely low leakage. All 63V D.C. Plus or minus 1% tolerance: 0.47 μ F—56p; 1.0 μ F—66p; 2.2 μ F—80p; 4.7 μ F—110p; 10 μ F—140p; 15 μ F—160p; 22 μ F—180p; 33 μ F—200p; 47 μ F—220p; 100 μ F—240p. Also available \pm 2% and \pm 5%, ex-Stock.

TANTALUM BEAD CAPACITORS—Values available: 0.1, 0.22, 0.47, 1.0, 2.2, 4.7, 6.8 μ F at 15V/25V or 35V; 10.0 μ F at 16/20V or 25V; 22.0 μ F at 6/10V or 16V; 33.0 μ F at 6V or 10V; 47.0 μ F at 3V or 6V; 100 μ F at 3V. All at 10p each; 10 for 95p; 50 for £4.00.

TRANSISTORS: BC107, BC108, BC109; All at 9p each; 6 for 51p; 12 for 96p. May be mixed for quantity price. BC182 and BC212 at 10p each; AF178 at 30p each. All brand new and marked. Full spec. devices.

POPULAR DIODES: IN914, 6p each; 8 for 45p; 18 for 90p IN916, 8p each; 6 for 45p; 14 for 90p; IS44, 5p each; 11 for 50p; 24 for £1. All brand new and marked.

NEW LOW PRICE—400 mW Zeners. Values available 4.7, 5.6, 6.8, 7.5, 8.2, 9.1, 10, 11, 12, 13.5, 15V. Tol. \pm 5% at 5 mA. All new and marked. Price \times each; 10 for 39p; 14 for 84p. Special offer 6 off each voltage (66 zeners): £3.65.

RESISTORS. Carbon film 5%. 1W at 40°C \pm 1W at 70°C. Range from 2.2 Ω to 2.2M Ω in E12 series, i.e. 10, 12, 15, 18, 22, 27, 33, 39, 47, 56, 68, 82 and their decades. High stability, low noise. All at 1p each; 100 of any one value; 70p for 100 of any one value. Special pack—10 of each value 2.2 Ω to 2.2M Ω (730 resistors) £5.

440V A.C. CAPACITORS: 0.1 μ F, size 1/4in x 1/4in—40p; 0.25 μ F (1 1/4" x 1 1/4")—55p; 0.47 and 0.5 μ F (1 1/2" x 1 1/2")—66p; 1.0 μ F (2" x 2")—85p; 2.0 μ F (2 1/2" x 1 1/2")—£1.15.

SILICON PLASTIC RECTIFIERS 1.5 amp. Brand new wire-ended DO27. 100 P.I.V. at 7p each; 4 for 26p. 400 PIV at 8p each; 4 for 30p; 800 PIV at 11p each; 4 for 42p.

7p Post and Packing on all orders below £5.00. Export orders—please add cost of air/sea mail.

PLEASE ADD 10% V.A.T.

TO ALL ORDERS

Send S.A.E. for lists of other ex-stock items, E.D.'s, disc capacitors, electrolytics etc. Wholesale price lists available to bona fide companies.

MARCO TRADING

Dept. W5, The Maltings, Station Road,

WEM, Salop.

Tel: NANTWICH (Cheshire) 63291.

BETA DEVICES FOR BETTER PRICES

TRANSISTORS	I.C.'s	DIODES & RECT.
AC187/188	709C TO.99 0.80	IN914 0.04
PR.	709C D.I.L. 0.80	1N4148 0.04
BC107	741C TO.99 0.88	OA202 0.06
BC108	741C D.I.L. 0.88	1N4001/2 0.05
BC109C	0.11 723C D.I.L. 0.80	1N4003/4/5 0.06
BC147/8/9	0.10 747C D.I.L. 0.85	1N4006/7 0.08
BCY70/71/72/13	748C D.I.L. 0.88	
BFX86/87/88		
	BRIDGES	
	5Watt Audio I.C.	W01 1A 0.20
BFY80	0.18 TBA 800 £1.50	100V 1A 0.20
BFY81/52	0.18 Data. fr. with	W06 1A 0.20
OC28	0.45 every order	600V 0.80
OC35	0.85	
2N2646	0.80 D.I.L. SOCKETS	ZENERS
2N3053	0.14 8-Pin 0.12	BZY88 3.3-33V 5% 0.06
2N3055	0.28 14-Pin 0.12	33V 5% 0.06
2N3442	£1.40 8-Pin 0.14	1 Watt 6.8-200V 5% 0.16
2N3773	£2.20	
40411	£2.20	L.E.D.
40636	£1.00	209-Red 0.17
		129-Ed. Clip 0.02

C.W.O. PLUS P.P. 10p TO

BETA DEVICES,

263 THE RIDGEWAY, ENFIELD, MIDD.

TEXAN AMPLIFIER



Pack

1. Resistors, 80p post 15p
2. Small Caps, 1.50 post 15p
3. Large Caps, 1.40 post 15p
4. Sundries, 2.50 post 15p
5. Potentiometers, 1.45 post 15p
6. Semi Conductors, 8.25 p. 15p
7. Transformer, 5.95 post 25p
8. Printed Circuit, 2.50 post 15p
9. Chassis, 3.00 post 25p
- 10a. Front Panel, 1.50 post 15p
11. Preformed Cables, 40p p. 15p
12. Handbook, 30p post 6p
13. Teak Veneer Case, 2.75 p. 30p

Complete Kit £29.50 Post, Ins 75p
Add 10% V.A.T.

TELERADIO ELECTRONICS
325 Fore St., LONDON, N.9

Tel. 01.807.3719. 4p will bring
full lists of available kits.

TAPE HEADS

Send stamp for lists

R.D.I. Ltd.

Chilton Works,

Garden Rd.,

Richmond,

Surrey,

TW9 4NS

For valve and
transistorized re-
corders from £2 ea.

INCOMPARABLE V.H.F. KIT

CV2—unique triple-purpose (converter, Receiver, Tuner—Feeder) kit for the amateur enthusiast. Fantastic transistorised performance. World Wide Sales. Complete kit of top grade parts covers 80-180 mHz with easy build diagrams only £5 direct from makers or S.A.E. for free literature. (S.W. Kits also available).

JOHNSONS (RADIO) Est. 1943

SHAW ST., WORCESTER WR1 399.

TRANSISTOR AMPLIFIERS 50p. Vol/tone pre-amps 30p, LW-MW osc. panels 50p. All with circuits. Radio cabinets, suitable ext. speakers; colours: yellow or teak finish requires sides trimmed. Mains droppers, 76 Ω + 66 Ω + 66 Ω + 25 Ω + 24 Ω + 26 Ω 30p. Skeleton pre-set 25 assorted 50p. Archer, 9 Pine Grove, Maidstone, Kent.

BRAND NEW COMPONENTS by return. Electrolytics 16V, 25V, 50V—0.47, 1, 2.2, 4.7, 10mfd.—4p. 22, 47—4 1/2p. (50V—5p.) 100—5 1/2p. (50V—7p.) 220—6p. (50V—9p.). Subminiature bead-type tantalums 0.1/35V, 0.22/35V, 0.47/35V, 1/35V, 2.2/35V, 4.7/35V, 10/16V—8p. Mylar Film 100V—0.001, 0.002, 0.005, 0.01, 0.02—2 1/2p. 0.04, 0.05—3p. 0.068, 0.1—3 1/2p. Polystyrene 63V, E12 series 10 pf.—1.00p pf.—2p. 1,200 pf.—10,000 pf.—5p. Miniature Highstab resistors, 5%, E.12 series—Carbon Film 1/2 W 1 Ω —10M Ω (10% over 1 Meg.) Metal Film 1/2 W 10 Ω —2.2M Ω and 1W. 27 Ω —10M Ω all 3/4p each. Postage 8p. The C.R. Supply Co., 127 Chesterfield Rd., Sheffield S8.

610 MINIATURE Highstab Resistors. 5% 1/4 W. 22 ohms to 2.2M E12 series. 10 each value £3.10. Miniature ceramic Capacitors 50V, 25 each E6 value 22pf to 1,000pf. Total 275 £3.75. NEK ELECTRONICS (W4), 28 Carnegie Road, St. Albans, Herts.

5-N CHANNEL FETS TYPE 3819E—£1 (incl VAT). Full spec devices complete with circuit details for building volt-meter, timer, etc. For full list of fets and other transistors available, send 10p. Redhawk Sales Ltd, 45 Station Road, Gerrards Cross, Bucks. Mail Order Only.

COMPONENTS GALORE. Pack of 500 mixed components manufacturers surplus plus once used. Pack includes resistors, carbon and W.W., capacitors various, transistors, diodes, trimmers, potentiometers etc. Send £1+10p p&p. C.W.O. To: Caledonian Components, Strathore Road, Thornton, Fife.

TUNBRIDGE WELLS. Components from Teleservice, 108 Camden Road, Tunbridge Wells, Kent. Telephone 31803.

EX-COMPUTER EQUIPMENT: Wide selection digital linear and power components. Large S.A.E. Lists, T. J. Oxborough, "Wimborne", Walton Road, Kirby-le-Soken, Frinton-on-Sea, Essex.

Miscellaneous

MORE RANGES FOR LESS MONEY!



MULTIMETER AC-DC Type U-437

10kOhms/V 2.5% Precision
A-DC 0-1A - 5 Ranges
V-DC/AC 2.5 to 1000 V - 6 Ranges.
Ohms-100 to 1 MegOhm - 4 Ranges
Frequency: 45-40kHz - 2 Ranges

TAUT SUSPENSIONS

Complete with steel case.

Dimensions without case:

212x118x

75mm **£4.95**

AC/DC Multimeter type U4324

A-DC 0-06-3A - 6 Ranges

A-DC 0-3-3A - 5 Ranges

V-DC 0-6-1200 V - 9 Ranges

V-AC 3-900 V - 8 Ranges

Frequency: 45 to 20kHz - 2 Ranges

Resistance: 500 Ohm to 5 MOhm -

5 Ranges. Decibel: -10 to +12dB

2 Ranges. Accuracy: \pm 2.5%

Dimensions: 167 x 98 x 63 mm

Only **£8.00**

SUPRETESTER 680 RICE

10 Fields - 80 Ranges: Plus

a lot of accessories for

measurements of 500A-AC

100 A/DC - Temperature-

-50C to +200C - Magnetic

fields up to 15 KGauss-

Phase indicator- EHT 25kV

Electronic Volt Ohm - meter

Transistor Diode Tester etc

Dimensions: 128 x 95 x 32 mm

300 grams 20kOhm/V Accuracy

1% DC Ask for free catalogue

Accessories Extra

AC-CLAMP Type U-91

7 ranges 10-500 A

Dimensions: 283 x 94

x 38mm. 680 grams

with case **£10.50**

Add 10% VAT to all items + 35p P&P

ELECTRONIC BROKERS LTD.

49-53 Pancras Road, London NW1 2QB Tel: 837 7781

FIBREGLASS

PRINTED CIRCUIT BOARD

"1" - "1/2" - Your size cut - no extra - no V.A.T.
Single 6p 12 sq. ins. 60p sq. ft. Double 8p 12
sq. ins., 70p sq. ft. Post 10p per sq. ft.

EASY PRINTED CIRCUIT MAKING! DALO 8S
MARKER (spare tip included) 80p post free.

From: **BBE, 17 SUTHERBEE RISE,**

WORKSOP, NOTTS. S80 2UP.

DON'T LOOK

unless you can resist the temptation to get these super 'attention-getters'!

- ★ Pocket-sized **MAXI-VOLT** Big 4 inch Spark Generator (instant 15,000 volts!). Ready-made, needs no batteries. Carry it around anywhere. Only weighs about 3 oz. (89g.) send £1.35 for your Maxi-Volt now!
- ★ Unique **TRANSMITTER/RECEIVER** Kit. No licence examinations or tests required to operate this transistorised equipment. Easy to build. Get transmitting. Send £5.90 for yours now!
- ★ Psychedelic **MINI-STROBE** Kit. Take a pocket-sized lightning storm to Disco's & parties. 'Brain-freeze' 'em with vari-speed stop-motion flashes. Includes super case too. Send £2.20 now! (all prices include V.A.T., packing & postage.)

Send remittance to:

**BOFFIN PROJECTS,
4 CUNLIFFE ROAD,
STONELEIGH, EWELL, SURREY**
(Mail order U.K. only)

Or for more details, send 15p for lists plus free design project sheet.

Darned Electronic Wizardry

by Dewtron (VAT extra.)

Famous kits, e.g. waa-waa complete kit £2.95; Fuzz kit £5.50 auto rhythm modules P & P 20p min Ring Modulator modules £8 and whole range of synthesiser modules, musical novelties, etc. Catalogue 15p from D.E.W. Ltd., 254 Ringwood Road, Ferndown, Dorset.

FIBRE OPTICS OPTIKIT 103 contains 2 m. Crofon 1010, 64 Strand Light Conduit plus 5 metres each FP20, FP40, FP60 Plastic Monofibre (diameter 0.5, 1.0, 1.5mm), Price £4.84 inc. booklet, pp., VAT.

2N577 SILICON PHOTODARLINGTON AMPLIFIER sensitive light detector, supercedes CdS cell. Price 1 off 55p, 5 off £2.53 inc. pp and data.

RED LIGHT EMITTING DIODES MLED 500 in TO92 case, MV54 miniature (2mm). Price (both types) £1.10 for 5 inc. pp and data.

40 kHz ULTRASONIC TRANSDUCER T/R PAIR Type SE05B. £3.85 per pair.

C.W.O. please to **FIBRE OPTIC SUPPLIERS (PW)**, P.O. BOX 702, LONDON, W10 6SL

Build your next project in a BEC (Book end chassis)



New improved with alloy trim on bottom of all cabinets. Now in easy to assemble kits.

GB3 (Illustrated) ... 14" x 9" x 4". £4.90 P & P 45p. Plus 10% VAT

Other sizes. SAE with enquiries. Callers welcome after 10 a.m.

P.C. BOARDS & PANELS

We specialise in small runs of P.C. Boards and screen printed or anodised aluminium panels. From 1 to 500, send sketch or negative and we will send you our quotation.

H. M. ELECTRONICS 275a, Fulwood Rd, Sheffield S16 3BD (Behind Broomhill P.O.)

BUILD THE **TREASURE TRACER MK III Metal Locator**

- Varicap tuning
- Britain's best selling metal locator kit
- Weighs only 22oz.
- Speaker and earphone operation
- Knocks down to only 17in.
- Prebuilt search coil assembly
- Ministry approved design
- As seen on BBC1 and BBC2 TV
- You only need soldering Iron, screwdriver, pliers and snips
- Five transistor circuit

Send s.a.e. for leaflet

Concrete Post: **£9.80** Mail tested and guaranteed Post 50p: **£13.75**

MINIKITS ELECTRONICS
35a LANGLEY DRIVE, WANSTEAD
LONDON, E11 2LN (Mail order only)

Versatile
10 in ONE



MIN-LAB

Comprising:

- AC and DC Voltmeter
- Ohm Meter
- Capacitance Substitution
- Battery Supply
- RF Field Strength Indicator
- Audio Generator
- Resistance Substitution
- DC Ammeter
- RF Signal Generator

This new, unique instrument combines all you need for testing. Money back if not satisfied. Includes VAT & p. & p.

Cash with order or send s.a.e. for illustrated data sheet to:

J. H. ASSOCIATES LTD. (DEPT. PW)
Cricketfield Lane, Bishop's Stortford, Herts.

BUILD OR BUY a

MINIATURE TRANSMITTER



A precision piece of equipment that has been designed and produced after 2 years research and development. The smallest transmitter available in the U.K. 2" x 1" approx. Fits in the palm of your hand. Can pick up and transmit voices and minute sounds, excellent range up to ½ mile. Can be worn round the neck, held in the hand or placed on a shelf. Receive on a VHF radio. Universal battery connections enable use of PP3 battery operates 9-15 volts, no other connections, completely self contained; to operate, simply switch on. Used the world over, many applications. Fully transistorised printed circuit. Guaranteed for 12 months.

Assembled unit ready to use £15.50
Kit with step-by-step assembly Instructions £11.50
If required, suitable radio for receiving transmitter £13.50

Ins., P. & P. 45p.

MULHALL ELECTRONICS (PW)

Ardglass, Co. Down, U.K. BT30 78P
(Exporters to 14 countries)
(R.A.E. licence required.)

HARDWARE SUPPLIES. Sheet aluminium individual sizes or standard packs, drilled to spec. Screws, nuts, washers etc. Fascia panels in aluminium individual requirements. Printed circuit boards, one-off or small runs. Printed circuit drafting tapes etc. 7p for list. Ramar Constructor Services, 29 Shelbourne Road, Stratford on Avon. Warwks. CV37 9JP.

WIRE. H.C. Copper, P.V.C. Insulated 24 A.W.G. (0.2 m.m.) in P.V.C. Colours Black, Yellow, Blue or White. Reels 8ozs £0.95; 1lb £1.80; 2lbs £3.50; 4lbs £6.75 including VAT and postage larger Reels available C.W.O.
H. A. WAINWRIGHT & CO. LTD.
9A Farncombe Street, Farncombe, Godalming, Surrey.
Tel. Godalming 23545



**BRIGHT - VERY ATTRACTIVE
LOW COST**

SPERRY Planar Gas Discharge displays, continuous 7-segment, v. attractive orange, viewing up to 40 feet. SP151 as above (actual size), 3½ digit am/pm, .5" character ht, £7.20 + 72p vat, incl. p and d, data and instructions for use with MM5316 and other popular clock ICs.

For prices, data etc. only, on SP151 and other Sperry displays for clocks and instruments (e.g. for 8 digits or .3") send 15p to:

SINTEL
53 ASTON STREET, OXFORD

12 VOLT FLUORESCENT LIGHTS

(as illustrated by Thorn/AEI)



Beat power cuts. Be independent. Ideal for caravans, tents, emergency lighting, etc. Works anywhere where 12v is available. Guaranteed for six months. Ready to use at:

12 ins. 8 watt £4.00 post paid

Including V.A.T.

Callers Welcome

For lists or enquiries, large s.a.e.
**SALOP ELECTRONICS, 23 WYLE COP
SHREWSBURY, SHROPSHIRE.**
Tel.: Shrewsbury 53206

AMAZING OFFER! **ELECTRIC SOLDERING GUN**
WITH BUILT IN TRANSFORMER

A MUST FOR EVERY DIY MAN

UNIQUE SEE IN THE DARK LIGHT

INSTANT HEAT

ONLY £2.25
P&P25p

This Soldering Gun is a MUST for D.I.Y. Men, Motorists, Mechanics, etc. A rugged, strong construction that will last a lifetime. Now you can do all those repairs that would normally cost you £2's at any electrical shop. Voltage 240 AC. 50c/s. LIMITED QUANTITY AVAILABLE. Similar product, sells at £4.50. C.W.O. Immediate despatch. Refund if not delighted.

V.G.S. INTERNATIONAL (SGW10)
Pickworth, Sleaford, Lincolnshire.

PRINTED CIRCUIT BOARDS. Any P.C.B. Published in **PRACTICAL WIRELESS/ELECTRONICS**, E.T.I. etc. etc. Any month any year. 5p/sq in. Postage Free. (Min. 50p). Also Artwork and/or photography undertaken. Return of post service. S.A.E. Footscap for full details. P. Lancaster, 11 Chesterton Road, Cambridge CB4 3AD.

AERIAL WIRE. PVC covered multi-strand copper. 25ft—23p (6p), 50ft—45p (9p), 75ft—67p (12p), 100ft—89p (15p), 150ft—£1.32 (23p), 200ft—£1.76 (25p), 250ft—£2.21 (27p), 300ft—£2.66 (30p). P&P in brackets. S.A.E. all enquiries. A.I. Radio Components 14 The Borough, Canterbury, Kent CT1 2DR.

BUILD IT in a **DEWBOX** quality cabinet. 2in x 2½in x any length. D.E.W. Ltd., Ringwood Road, FERN-DOWN, Dorset. S.A.E. for leaflet. Write now—Right now.

AUDIOSCAN, the "do-it-yourself" speaker mail-order specialists. High fidelity speaker kits, chassis units, sound absorbent, grille fabric and much more. Send S.A.E. for bargain list to: Audioscan, Dept. PW1, 4 Princes Square, Harrogate, Yorks.

LOUDSPEAKER KITS for hi-fi stereo by **HELME**, the speaker kit people, all complete with full instructions. Prices from as little as £14.95 per pair including VAT! Send NOW for free illustrated brochure and stockist list to: Helme Audio Products Ltd, Dept. PWA-74, Summerbridge, Harrogate, Yorks (Tel: Darley 279).

HOME DISCO! Comprehensive sound to light kits. Three channel 3kW £18.50. Single channel units £8 and £11. P&P 50p. W. T. Electronics, Gazeley Road, Kentford, Suffolk.

VALVES Large Stock 1930 to 1973. S.A.E. for quotation. Cox Radio, The Parade, East Wittering, Sussex.

ANTIQUE Wireless Collectors! For everything in wireless 1920-1950 contact Tudor Rees. S.A.E. with your wants or 25p for catalogue to: 18 Brook Road, Mangotsfield, Bristol, BS17 3DY. Tel. Bristol 565238 evenings before 9 p.m.

Ladders

LADDERS. 'Special Offer' Unvarnished triples. 9ft 7in closed—23ft lin extended. £18.90 delivered. Home Sales Ladder Centre (WLS2) Haldane (North) Halesfield (1) Telford, Shropshire. Tel: 0952 586644.

Personal

S.I.M. COMPUTER DATING. The most exciting way to make friends. Write, S.I.M. (E/17) 109 Queens Road, Reading.

AERIAL BOOSTERS—£3.25

We make three types of Aerial Boosters: B45-UHF 625, B12-VHF 405, B11-VHF RADIO

VALVE BARGAINS

ANY 5—50p, 10—75p, 50—£3.30:—ECC82, ECL80, EB81, EBF80, EF80, EF85, EF183, EF184, EY85, PC804, PC808, PC8189, PC97, PCF80, PCF86, PCF805, PCF808, PCL82, PCL83, PCL84, PCL85, PFL200, PL36, PL81, PL504, PY33, PY82, PY800, PY801, 30L15, PC86, PC88.

19" UHF/VHF (BBC2) £6.00

Thorn-850 or Pye, with set of spare valves. Carriage £2.00 (Untested).

100 MIXED RESISTORS—85p

½ to 2 watt—10 ohms to above 1m-ohms (our choice) 100 mixed Ceramic Capacitors from 1PF to 8200PF (our choice) 65p.

BARGAINS PARTS

Transistor UHF Tuners—£2.40, 500K-ohms V/C with Switch—20p, 50 mixed Tuner Valves—£2.25. Brand New Transistors 8F173, BA171, BC153, BC135, BC113, BC117, BC115, BA102, BA129. All 10p each.

All prices include V.A.T. p. & p. 10p per order. Money back guarantee. S.A.E. for leaflets.

ELECTRONIC MAILORDER (BURY) LTD.

62 Bridge St., Ramsbottom, Bury, Lancs. Tel. Rams 3036

EX COMPUTER PC PANELS

4 x 2in packed with semiconductors and top quality resistors, capacitors, diodes etc. Guaranteed min. 35 transistors, plus data. 10 boards 50p (12p) 25 boards for £1 (30p)

Panels with 4 Power transistors sim OC28 50p (10p) Dural extruded heatsinks outline 10D black anodised. Drilled for 4 x TO3 transistors. 5 x 4 x 1½" 40p (14p) Similar to above but 5 x 8 x 1½" drilled for 8 x TO3 70p (26p)

COMPUTER GRADE

ELECTROLYTICS
12,000µ 100v, 5 x 2½ dia £1 (25p)
30,000µ 25v 65p (20p)

ELECTROLYTICS

4,000µ 70v, 3,600µ 40v, 10,000µ 50v, 4½ x 2 in dia 55p (14p)
10,000µ 35v, 5,000µ 35v, 4½ x 2 in 40p (12p)

2,000µ 30v, wire ends 15p (6p)

100 piv 20A, Si diodes 4 for £1 (10p)

100 piv 3A, Si diodes 4 for 50p (7p)

250 mixed resistors 60p (9½p)

250 mixed capacitors 60p (9½p)

200 Si planar diodes 50p (7p)

Min. glass neons 8 for 50p (7p)

Reed relays mixed 10 for 50p (7p)

Micro switches 8 for 50p (9p)

Papst extractor/blower fans

100 c.f.m. 4½ x 4½ x 2in £3.50 (28p)

QH bulbs 12v 55w 50p (6p)

Postage and package shown in brackets.

"ADD 10% VAT TO TOTAL"

KEYTRONICS

(Mail Order only)

44 EARLS COURT ROAD
LONDON W8. 01-478 8499

M & B COMPONENTS (Leeds) LTD.

86 BISHOPGATE STREET,
LEEDS 1. Phone 35649

SPECIAL OFFER

MOTOROLA CAR RADIO CHASSIS. (Net complete) Chassis—I.F. Transformers—Trimmers—Res/Caps Transistors 25B RF/Ampl. M25A Mix. M540/M241 AF *Transistor may vary slightly. Complete with Circuit 60p each, 15p P. & P. LIMITED STOCK.

Few only as above, complete with P.A. Transistors 60p each, 15p P. & P.

STOCK CLEARANCE LINE

Small 12 Volt Model Makers Motor. New. 60p each, 10p P. & P. Also available 6 Volt (few only). Size approx. 1¼" x 1¼".

MARCONI SIGNAL GENERATOR TYPE TF867 (Modulation and CARRIER Meter) 15 Kcs to 30 MEG.

Nice Condition £85.00. BRS Delivery £5.00.

BULK PURCHASE


GREEN TRACE/MAGNETIC SQUARE FACED TUBES. Ideal Monitor/T.V. Size approx. 5" x 3" face, 12" neck. New boxed. £1.00 each, P. & P. 40p each.

ELECTROLYTIC TV CAPACITORS (New) 200µf 100µf, 100µf 350V DC. 4 for £1.00. P. & P. 20p.

When in Leeds visit our Walk Round Showroom—near City Square, Queens Hotel. Many BARGAINS FOR SHOP CALLERS. We shall be visiting all the MAJOR BALLIES in the NORTHERN ZONE!

(ALL PRICES INCLUDE V.A.T.)

NEW! TODAY'S MOST EXCITING SPEAKERS

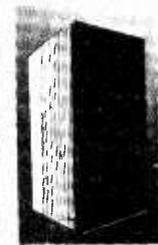

Never before have speakers of such superb performance and low cost been available. Produced by us to quality standards the new **GS Range** offer you true high fidelity at a fraction of the cost. Both models employ fully sealed bass reflex enclosures made from quality compressed woods and our modern compact designs ensure optimum performance at all times. Finished in Rich American Walnut effect, Black Satin front these speakers offer today's best value in high quality equipment.

TECHNICAL SPECIFICATIONS GS500 Power 30 Watts Peak (15 Watts RMS) Frequency Range 33Hz to 19000Hz Impedance 8 Ohms Bass Unit 16 cm round long throw Treble Unit 7.5cm round Crossover 5000Hz Dimensions 45cm x 22.5cm x 22.5cm (18" x 8" x 8") Volume 17 Litres **TECHNICAL SPECIFICATIONS GS300 Power 20 Watts Peak (10 Watts RMS) Frequency Range 42Hz to 16500Hz Impedance 8 Ohms Drive Unit 20 cm x 13cm long throw with integral coaxial tweeter Crossover 5000Hz Dimensions 40 cm x 30cm x 20cm (16" x 8" x 8") Vol 12 Litres**

GS 500 £11.98 post free GS 300 £9.98 post free
ECONOMY Speaker System Ideal for budget hi-fi Stereo Etc. This unique 8 Ohm system comes complete with leads and super trade grain finish £8.99 pair post free

PLEASE ADD 10% VAT TO ALL ORDERS TRADE ENQUIRIES WELCOME

GREGG ELECTRONICS PW4 24 Cranbourn Street
Lbicester Square London WC2

GREGG



AMAZING MINI-DRILL

**FOR
PRECISION
MODEL
WORK**



+ 6 TOOLS

Indispensable for precision drilling, grinding, polishing, etching, gouging, shaping. Precision power for the enthusiast. Shockproof. Completely portable power from 4½ volt external battery. So much more scope with MINI-DRILL. Super Kit (extra power, interchangeable chuck) £6.35 p.p. 13p. De Luxe Professional Kit with 17 tools £9.40 p.p. 23p. Prices include V.A.T.

Money ref. g'tee.

MERLIN SUPPLY CO.

Dept. PW 574 Nailsea, Bristol BS19 2LP

**ONLY
£2.55**



BAKER 12" MAJOR £11.55
30-14,500 cps. Double cone woofer and tweeter loudspeaker. Baker ceramic magnet assembly, flux density 145,000 gauss. BASS RESONANCE 40 cps 20 watt RMS.

MAJOR MODULE KIT £14.85
30-17,000 cps. woofer, tweeter, crossover and baffle as illustrated. Size 19in x 13in.
NOTE—When ordering state 3 or 8 or 15 ohms.

BAKER LOUDSPEAKERS 100% BRITISH MADE

Regent 12 in. 15W £10.45	Superb 12 in. 20W £18.70	New Group 50/12
Major 12 in. 20W £11.55	Group 25 12 in. 25W £10.45	12 in. 50W £17.60
Deluxe 12 in. 15W £18.20	Group 35 12 in. 35W £11.55	

**BAKER LOUDSPEAKER CO., BENSAM MANOR PASSAGE
THORNTON HEATH, SURREY Tel. 01-684 1665**
ALL PRICES INCLUDE V.A.T. HI-FI ENCLOSURE PLANS 42p



DOUBLE-SIDED WALL CHART

'How to build and use the P.E. Sound Bender'

Centred around a simple constructed "audio modulator" unit, the P.E. Sound Bender is not just a single sound effects unit, but your key to a host of exciting with-it sounds.

Just feed a music or speech signal to one input and a control signal to the other and you can have a tremolo, a frequency doubler, a ring modulator, or a voice-operated fader.

**PRACTICAL
ELECTRONICS**

MAY ISSUE ON SALE MID APRIL* 25p

* subject to the current national industrial situation at the time of going to press

Head Office and Warehouse
44A WESTBOURNE GROVE
LONDON W2 5SF
Tel: 727 5641/2/3


Z & I AERO SERVICES LTD.

Please send all correspondence and Mail-Orders to Head Office
When sending cash with order, please include 0.15 in £ for postage and handling
MINIMUM CHARGE 15p. No C.O.D. orders accepted

Retail Shop
85 TOTTENHAM COURT ROAD
LONDON W1
Tel: 580 8403
Open all day Saturday

THE MANAGEMENT ADVISES WITH REGRET THAT DUE TO RISING COSTS AND STAFF SHORTAGE THE MAIL ORDER SERVICE HAS TO BE CURTAILED. FROM 1ST JANUARY 1974 ALL MAIL ORDERS ACCOMPANIED BY REMITTANCE WILL BE SUBJECT TO A MINIMUM CHARGE OF £5.00 EXCLUDING V.A.T., I.E. £5.50 INCLUDING V.A.T. GOODS OF VALUE UNDER £5.00 WILL BE AVAILABLE ONLY TO PERSONAL CALLERS, EITHER AT OUR RETAIL BRANCH, 85, TOTTENHAM COURT ROAD, W.1, OR TRADE COUNTER AT 44A WESTBOURNE GROVE, LONDON W2. MINIMUM ORDER CHARGE FOR APPROVED ACCOUNT CUSTOMERS IS £10.00 EXCLUSIVE OF V.A.T.

TAUT SUSPENSION MULTIMETERS MADE IN USSR

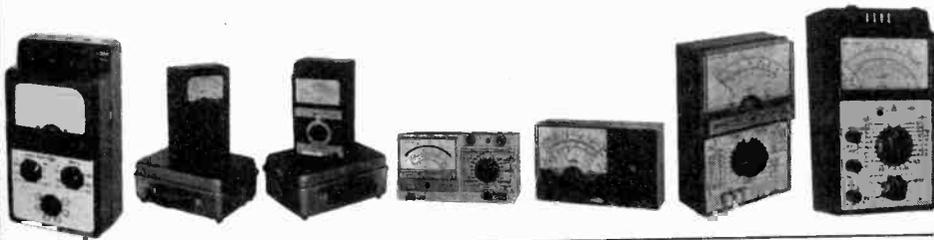

8 models of multimeters from simple 22-range instrument priced at £4.95 to sophisticated 43-range instrument with transistorised safety trip circuit, priced at £17.00. Models available with transistor testing facilities (U4341) and built-in audio/I.F. oscillator (U4323).

All the above instruments and full range of other test equipment are included in our new 1973/74 combined catalogue/price list which covers valves, semi-conductors and passive components, basic specifications of semiconductors, cathode ray tubes, Klystrons and magnetrons, as well as transistor substitution list.

WATFORD ELECTRONICS

35 CARDIFF ROAD, WATFORD, HERTS, ENGLAND
MAIL ORDER. CALLERS SATURDAYS ONLY

C.W.O. Please. P. & P. add 10p to orders under £2. Prices exclusive of VAT
Send 10p Postage for our comprehensive catalogue.

TRANSISTORS			
AC125 12p	BC109 10p	BFY53 17p	TIP30 48p
AC126 12p	BC147 11p	MJE370 63p	TIS43 25p
AC127 12p	BC148 11p	MJE371 63p	ZTX107 12p
AC128 12p	BC149 11p	MJE520 52p	ZTX108 12p
AC176 14p	BC182 11p	OC26 35p	ZTX109 12p
AC187 12p	BC183 11p	OC35 40p	ZTX300 14p
AC188 12p	BC184 11p	OC41 35p	ZTX301 14p
ACY17 21p	BC212 11p	OC42 38p	ZTX302 18p
ACY19 22p	BC213 11p	OC44 12p	2N1131 20p
ACY20 20p	BC214 11p	OC45 12p	2N1132 20p
ACY21 16p	BCY70 15p	OC70 12p	2N1301/2 20p
ACY22 16p	BCY71 20p	OC71 12p	2N1303/4 24p
AD140 40p	BCY72 15p	OC72 12p	2N1307 26p
AD145 40p	BD131 45p	OC74 22p	2N1671 B 99p
AD161 30p	BD132 45p	OC81 12p	2N1990 45p
AD162 30p	BF194 15p	OC82 15p	2N2217 23p
AF114/5 14p	BF195 15p	OC83N 20p	2N2218A 20p
AF116/7 14p	BF196 16p	OC201 60p	2N2906 15p
AF118 40p	BFY50 20p	OC202 80p	2N2907 18p
BC107 10p	BFY51 20p	OCF71 95p	2N2926 8p
BC108 10p	BFY52 20p	TIP29 43p	2N2053 20p

DIGITAL IC'S 74 SERIES			
7400 17p	7426 28p	7472 28p	74111 85p
7401 17p	7427 37p	7473 37p	74118 99p
7402 17p	7428 43p	7474 37p	74121 63p
7403 18p	7430 18p	7475 55p	74141 95p
7404 18p	7432 37p	7476 37p	74182 £1.42
7405 18p	7433 43p	7480 60p	74193 £2.28
7406 39p	7437 43p	7481 £1.10	74194 £1.65
7407 39p	7438 43p	7482 86p	74196 £1.45
7408 21p	7440 18p	7483 £1.10	
7409 24p	7441 75p	7484 95p	
7410 18p	7442 15p	7485 £1.87	
7411 22p	7443 £1.20	7486 38p	
7412 28p	7444 £1.20	7490 69p	
7413 28p	7447 £1.30	7491 99p	
7414 60p	7448 £1.18	7492 69p	
7416 35p	7450 18p	7493 69p	
7417 35p	7451 18p	7494 80p	
7420 18p	7453 17p	7495 80p	
7422 24p	7454 17p	7496 99p	
7423 38p	7460 18p	74104 60p	
7425 38p	7470 28p	74105 59p	

POLYESTER CAPACITORS. Axial lead type.
400V: 0.001µF, 0.0015µF, 0.0022µF, 0.0033µF, 0.0047µF, 0.0068µF, 2µF; 0.01µF, 0.015µF, 0.022µF, 3p; 0.047µF, 0.068µF, 0.1µF, 0.15µF, 4p; 0.22µF, 7p; 0.33µF, 10p; 0.47µF, 13p; 0.68µF, 16p; 1µF, 19p; 1.5µF, 22p; 2.2µF, 25p; 3.3µF, 29p; 4.7µF, 33p; 6.8µF, 37p; 10µF, 43p; 15µF, 47p; 22µF, 53p; 33µF, 60p; 47µF, 67p; 68µF, 75p; 100µF, 83p; 150µF, 90p; 220µF, 100p; 330µF, 110p; 470µF, 120p; 680µF, 135p; 1000µF, 150p; 1500µF, 165p; 2200µF, 180p.

Radial lead P.C. type:
250V: 0.01µF, 0.015µF, 0.022µF, 3p; 0.033µF, 0.047µF, 0.068µF, 3p; 0.1µF, 4p; 0.15µF, 4p; 0.22µF, 5p; 0.33µF, 5p; 0.47µF, 5p; 0.68µF, 5p; 1.0µF, 5p; 1.5µF, 5p; 2.2µF, 5p; 3.3µF, 5p; 4.7µF, 5p; 6.8µF, 5p; 10µF, 5p; 15µF, 5p; 22µF, 5p; 33µF, 5p; 47µF, 5p; 68µF, 5p; 100µF, 5p; 150µF, 5p; 220µF, 5p; 330µF, 5p; 470µF, 5p; 680µF, 5p; 1000µF, 5p; 1500µF, 5p; 2200µF, 5p.

ELECTROLYTIC CAPACITORS. Miniature axial lead type.
63V: 1µF, 1.5µF, 2.2µF, 3.3µF, 4.7µF, 6.8µF, 10µF, 15µF, 22µF, 47µF, 68µF, 6p each
40V: 100µF, 6p; 150µF, 6p; 25V: 220µF, 11p; 470µF, 13p; 1000µF, 24p.
100V: 0.1µF, 0.22µF, 0.33µF, 0.47µF, 0.68µF, 1µF, 1.5µF, 2.2µF, 3.3µF, 4.7µF, 6.8µF, 10µF, 15µF, 22µF, 33µF, 47µF, 68µF, 100µF, 150µF, 220µF, 330µF, 470µF, 680µF, 1000µF, 1500µF, 2200µF, 3300µF, 4700µF, 6800µF, 10000µF, 15000µF, 22000µF, 33000µF, 47000µF, 68000µF, 100000µF, 150000µF, 220000µF, 330000µF, 470000µF, 680000µF, 1000000µF, 1500000µF, 2200000µF, 3300000µF, 4700000µF, 6800000µF, 10000000µF, 15000000µF, 22000000µF, 33000000µF, 47000000µF, 68000000µF, 100000000µF, 150000000µF, 220000000µF, 330000000µF, 470000000µF, 680000000µF, 1000000000µF, 1500000000µF, 2200000000µF, 3300000000µF, 4700000000µF, 6800000000µF, 10000000000µF, 15000000000µF, 22000000000µF, 33000000000µF, 47000000000µF, 68000000000µF, 100000000000µF, 150000000000µF, 220000000000µF, 330000000000µF, 470000000000µF, 680000000000µF, 1000000000000µF, 1500000000000µF, 2200000000000µF, 3300000000000µF, 4700000000000µF, 6800000000000µF, 10000000000000µF, 15000000000000µF, 22000000000000µF, 33000000000000µF, 47000000000000µF, 68000000000000µF, 100000000000000µF, 150000000000000µF, 220000000000000µF, 330000000000000µF, 470000000000000µF, 680000000000000µF, 1000000000000000µF, 1500000000000000µF, 2200000000000000µF, 3300000000000000µF, 4700000000000000µF, 6800000000000000µF, 10000000000000000µF, 15000000000000000µF, 22000000000000000µF, 33000000000000000µF, 47000000000000000µF, 68000000000000000µF, 100000000000000000µF, 150000000000000000µF, 220000000000000000µF, 330000000000000000µF, 470000000000000000µF, 680000000000000000µF, 1000000000000000000µF, 1500000000000000000µF, 2200000000000000000µF, 3300000000000000000µF, 4700000000000000000µF, 6800000000000000000µF, 10000000000000000000µF, 15000000000000000000µF, 22000000000000000000µF, 33000000000000000000µF, 47000000000000000000µF, 68000000000000000000µF, 100000000000000000000µF, 150000000000000000000µF, 220000000000000000000µF, 330000000000000000000µF, 470000000000000000000µF, 680000000000000000000µF, 1000000000000000000000µF, 1500000000000000000000µF, 2200000000000000000000µF, 3300000000000000000000µF, 4700000000000000000000µF, 6800000000000000000000µF, 10000000000000000000000µF, 15000000000000000000000µF, 22000000000000000000000µF, 33000000000000000000000µF, 47000000000000000000000µF, 68000000000000000000000µF, 100000000000000000000000µF, 150000000000000000000000µF, 220000000000000000000000µF, 330000000000000000000000µF, 470000000000000000000000µF, 680000000000000000000000µF, 1000000000000000000000000µF, 1500000000000000000000000µF, 2200000000000000000000000µF, 3300000000000000000000000µF, 4700000000000000000000000µF, 6800000000000000000000000µF, 10000000000000000000000000µF, 15000000000000000000000000µF, 22000000000000000000000000µF, 33000000000000000000000000µF, 47000000000000000000000000µF, 68000000000000000000000000µF, 100000000000000000000000000µF, 150000000000000000000000000µF, 220000000000000000000000000µF, 330000000000000000000000000µF, 470000000000000000000000000µF, 680000000000000000000000000µF, 1000000000000000000000000000µF, 1500000000000000000000000000µF, 2200000000000000000000000000µF, 3300000000000000000000000000µF, 4700000000000000000000000000µF, 6800000000000000000000000000µF, 10000000000000000000000000000µF, 15000000000000000000000000000µF, 22000000000000000000000000000µF, 33000000000000000000000000000µF, 47000000000000000000000000000µF, 68000000000000000000000000000µF, 100000000000000000000000000000µF, 150000000000000000000000000000µF, 220000000000000000000000000000µF, 330000000000000000000000000000µF, 470000000000000000000000000000µF, 680000000000000000000000000000µF, 1000000000000000000000000000000µF, 1500000000000000000000000000000µF, 2200000000000000000000000000000µF, 3300000000000000000000000000000µF, 4700000000000000000000000000000µF, 6800000000000000000000000000000µF, 10000000000000000000000000000000µF, 15000000000000000000000000000000µF, 22000000000000000000000000000000µF, 33000000000000000000000000000000µF, 47000000000000000000000000000000µF, 68000000000000000000000000000000µF, 100000000000000000000000000000000µF, 150000000000000000000000000000000µF, 220000000000000000000000000000000µF, 330000000000000000000000000000000µF, 470000000000000000000000000000000µF, 680000000000000000000000000000000µF, 1000000000000000000000000000000000µF, 1500000000000000000000000000000000µF, 2200000000000000000000000000000000µF, 3300000000000000000000000000000000µF, 4700000000000000000000000000000000µF, 6800000000000000000000000000000000µF, 10000000000000000000000000000000000µF, 15000000000000000000000000000000000µF, 22000000000000000000000000000000000µF, 33000000000000000000000000000000000µF, 47000000000000000000000000000000000µF, 68000000000000000000000000000000000µF, 100000000000000000000000000000000000µF, 150000000000000000000000000000000000µF, 220000000000000000000000000000000000µF, 330000000000000000000000000000000000µF, 470000000000000000000000000000000000µF, 680000000000000000000000000000000000µF, 1000000000000000000000000000000000000µF, 1500000000000000000000000000000000000µF, 2200000000000000000000000000000000000µF, 3300000000000000000000000000000000000µF, 4700000000000000000000000000000000000µF, 6800000000000000000000000000000000000µF, 10000000000000000000000000000000000000µF, 15000000000000000000000000000000000000µF, 22000000000000000000000000000000000000µF, 33000000000000000000000000000000000000µF, 47000000000000000000000000000000000000µF, 68000000000000000000000000000000000000µF, 100000000000000000000000000000000000000µF, 150000000000000000000000000000000000000µF, 220000000000000000000000000000000000000µF, 330000000000000000000000000000000000000µF, 470000000000000000000000000000000000000µF, 680000000000000000000000000000000000000µF, 1000000000000000000000000000000000000000µF, 1500000000000000000000000000000000000000µF, 2200000000000000000000000000000000000000µF, 3300000000000000000000000000000000000000µF, 4700000000000000000000000000000000000000µF, 6800000000000000000000000000000000000000µF, 100µF, 15000000000000000000000000000000000000000µF, 22000000000000000000000000000000000000000µF, 33000000000000000000000000000000000000000µF, 47000000000000000000000000000000000000000µF, 68000000000000000000000000000000000000000µF, 1000µF, 1500µF, 2200µF, 3300µF, 4700µF, 6800µF, 100µF, 15000µF, 22000µF, 33000µF, 47000µF, 68000µF, 1000µF, 1500µF, 2200µF, 3300µF, 4700µF, 6800µF, 100µF, 15000µF, 22000µF, 33000µF, 47000µF, 68000µF, 1000µF, 1500µF, 2200µF, 3300µF, 4700

FREE!

Over 150 ways to engineer a better future

HIGHER PAY **A BETTER JOB**

SECURITY

find out how in just 2 minutes

That's how long it will take you to fill in the coupon. Mail it to B.I.E.T. and we'll send you full details and a free book. B.I.E.T. has successfully trained *thousands* of men at home - equipped them for higher pay and better, more interesting jobs. We can do as much for YOU. A low-cost B.I.E.T. home study course gets results fast - makes learning easier and something to look forward to. There are no books to buy and you can pay-as-you-learn.

Why not do the thing that really interests you? Without losing a day's pay, you could quietly turn yourself into something of an expert. Complete the coupon (or write if you prefer not to cut the page). No obligation and nobody will call on you . . . but it could be the best thing you ever did.

Others have done it, so can you

"Yesterday I received a letter from the Institution informing that my application for Associate Membership had been approved. I can honestly say that this has been the best value for money I have ever obtained - a view echoed by two colleagues who recently commenced the course". - Student D.L.B., Yorks.

"Completing your course, meant going from a job I detested to a job that I love, with unlimited prospects". - Student J.A.O. Dublin.

"My training with B.I.E.T. quickly changed my earning capacity and, in the next few years, my earnings increased fourfold" - Student C.C.P., Bucks.

FIND OUT FOR YOURSELF

These letters - and there are many more on file at Aldermaston Court - speak of the rewards that come to the man who has given himself the specialised know-how employers seek. There's no surer way of getting ahead or of opening up new opportunities for yourself. It will cost you a stamp to find out how we can help you. Write to **B.I.E.T. Dept. BPW51 Aldermaston Court, Reading RG7 4PF.**

Published on approximately the 7th of each month by IPC Magazines Limited, Fleetway House, Farringdon Street, London EC4A 4AD. Printed in England by Index Printers, Dunstable, Beds. Sole Agents for Australia and New Zealand - Gordon and Gotch (Asia) Ltd.; South Africa - Central News Agency Ltd. Publisher's subscription rate (including postage): for one year conditions, namely that it shall not, without the written consent of the Publishers first having been given, be lent, resold, hired out or otherwise disposed of by way of Trade at more than the recommended selling price shown on the cover, and that it shall not be lent, resold, hired out or otherwise disposed of in a mutilated condition or in any unauthorised cover by way of Trade or affixed to or as part of any publication or advertising, literary or pictorial matter whatsoever.

Practical Radio & Electronics Certificate course includes a learn while you build **3 transistor radio kit.**

Everything you need to know about **Radio & Electronics** maintenance and repairs for a **spare time income** and a **career** for a better future.



CUT OUT THIS COUPON

Tick or state subject of interest. Post to address below.

<input type="checkbox"/> MECHANICAL Society of Engineers— A.M.S.E. (Mech.) <input type="checkbox"/> Institute of Engineers & Technicians (A.M.I.E.) <input type="checkbox"/> CITY & GUILDS Gen. Mech. Eng. <input type="checkbox"/> Maintenance Eng. <input type="checkbox"/> Welding <input type="checkbox"/> Gen. Diesel Eng. <input type="checkbox"/> Sheet Metal Work <input type="checkbox"/> Eng. Inspection <input type="checkbox"/> Eng. Metallurgy <input type="checkbox"/>	<input type="checkbox"/> DRAUGHTSMANSHIP Institute of Engineering Designers (A.M.I.E.D.) <input type="checkbox"/> General Draughtsmanship <input type="checkbox"/> Elec. Draughtsmanship <input type="checkbox"/> Architectural Draughtsmanship <input type="checkbox"/> Technical Drawing <input type="checkbox"/>	<input type="checkbox"/> A.B.T. Clerk of Works <input type="checkbox"/> Construction Surveyors Institute—L.C.S.I. <input type="checkbox"/> CITY & GUILDS General Building (all branches) <input type="checkbox"/> Heating & Vent. Inst. Clerk of Works <input type="checkbox"/> Site Surveying <input type="checkbox"/> Health Engineering <input type="checkbox"/> Road Construction <input type="checkbox"/> Quantities <input type="checkbox"/> Estimates <input type="checkbox"/> Hydraulics <input type="checkbox"/> Structural Eng. <input type="checkbox"/>
<input type="checkbox"/> ELECTRICAL & ELECTRONIC Society of Engineers— A.M.S.E. (Elec.) <input type="checkbox"/> CITY & GUILDS Gen. Electrical Engineering <input type="checkbox"/> Electrical Installations <input type="checkbox"/> Electrical Maths <input type="checkbox"/> Computer Electronics <input type="checkbox"/> Electronic Eng. <input type="checkbox"/> Practical Radio & Electronics (with kit) <input type="checkbox"/>	<input type="checkbox"/> RADIO & TELE-COMMUNICATIONS CITY & GUILDS. Radio, TV, Electronics <input type="checkbox"/> CITY & GUILDS Telecoms. <input type="checkbox"/> Gen. Radio & TV Eng. <input type="checkbox"/> Radio Amateurs Exam <input type="checkbox"/> Radio Servicing <input type="checkbox"/> Colour TV <input type="checkbox"/>	<input type="checkbox"/> GENERAL Agricultural Eng. <input type="checkbox"/> Council of Eng. Institutions <input type="checkbox"/> Farm Science <input type="checkbox"/> Plastics <input type="checkbox"/>
<input type="checkbox"/> MANAGEMENT & PRODUCTION Institute of Cost & Management Acctnts. <input type="checkbox"/> Computer Programming <input type="checkbox"/> Works M'ment. <input type="checkbox"/> Work Study <input type="checkbox"/> Gen. Production Eng. <input type="checkbox"/> Estimating & Planning <input type="checkbox"/> Storekeeping <input type="checkbox"/> Management Skills <input type="checkbox"/> Quality Control <input type="checkbox"/>	<input type="checkbox"/> AUTOMOBILE & AERONAUTICAL Institute of the Motor Industry A.M.I.I. <input type="checkbox"/> MAA IMI <input type="checkbox"/> CITY & GUILDS Auto Eng. <input type="checkbox"/> Gen. Auto Eng. <input type="checkbox"/> Motor Mechanics <input type="checkbox"/> Auto Diesel Eng. <input type="checkbox"/> Garage M'ment. <input type="checkbox"/> ARB Aero Engineering Certs. <input type="checkbox"/> Gen. Aero Eng. <input type="checkbox"/>	<input type="checkbox"/> Supplementary courses for Nat. Certificates.
G.C.E. — choose from 58 'O' & 'A' level subjects.		
<i>Coaching for many exams, including C & G</i>		

POST TODAY FOR A BETTER TOMORROW

To B.I.E.T., Dept. BPW1 QN
Aldermaston Court, Reading RG7 4PF **BPW1**

NAME
Block Capitals Please
ADDRESS

OTHER SUBJECTS AGE

Accredited by C.A.C.C.

BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY

Henry's

**DON'T RELY ON YOUR MEMORY
BUY NOW AT BARGAIN PRICES**
Hi Fi and Transistors - Up to date
Brochures on request

**HENRY'S
CATALOGUE**
Due to rapid price changes,
shortages of paper and raw
materials, all prices in the
existing catalogues no longer
apply. Call or phone for latest
prices. A new catalogue will
be available for Aug/Sept. 1974.



You pay less
VAT with Henry's
Low Prices

BUILD THE TEXAN

Now built and used by thousands
of satisfied customers. Features
slim design overall size in cab-
inet 15 1/2" x 2 1/2" x 6 1/2". 6-IC's, 10
transistors, stabilisers Gardners
low field transformer. Fibre
Glass PC Panel, complete chassis
work. Now available built and tested as well as in
kit form. **HIGH QUALITY & STABILITY ARE
PREDOMINATE FEATURES - DEVELOPED BY
TEXAS ENGINEERS FOR PERFORMANCE,
RELIABILITY AND EASE OF CONSTRUCTION.
FACILITIES.** On/off switch indicator, headphones
socket, separate treble, bass, volume and balance
controls, scratch and rumble filters, mono/stereo
switch, input selector; Plug. P.U., Radio Tuner,
Aux. Can be altered for Mic., Tape, Tape-head, etc.
Constructional details Ref. No. 21
30p. Distributed by Henry's throughout UK. FREE—Teak cabinet with complete kit.

Kit price **£28.50** (+VAT +50p carr/packing) or built and tested **£35.00** (+VAT +50p carr/packing) as illustrated.



BUILD THE NEW HENELEC STEREO FM TUNER

A completely new high stability stereo
FM tuner. Features variable capacity
diode tuning, stabiliser power
supply, IC Decoder, high gain
low noise. IF stages. LED indicators.
Tuning meter, AFC, easy
to construct and use. Mains
operated. Slim modern de-
sign with fibre glass PC, teak
cabinet, etc. Available as a
kit to build or ready built.
Overall size 8" x 2 1/2" x 6 1/2". Pro-
duced to give high performance
with a realistic price. (Parts list and
constructional details Ref. No. 530p).
Henry's are sole distributors UK and Europe.

Kit Price **£21.00** (+VAT) or built and tested **£24.95** (+VAT)



EARN YOURSELF EASY MONEY, WITH PORTABLE DISCO EQUIPMENT

DISCO MINI A complete portable
disco, fitted mixer/preamp, 2 decks all
facilities. **£98.50**
As above but with Slider Controls **£118.50**
100 watt amplifier for above **£49.50**
SDLS 100 watt mixer/amplifier with
slider controls **£69.00**
RS50 50 watt mixer/amplifier **£49.50**
R100 100 watt mixer/amplifier **£57.50**
DISCO AMP 100 watt mixer/amplifier **£73.00**

Northcourt:
400 40 watt mixer/amp **£37.50**
800 80 watt mixer/amp **£45.00**

DISCO MIXER/PREAMPLIFIERS
(OP for up to 6-1000 watt amplifiers)
SDLI (rotary controls) **£49.50**
SDLI (slider controls) **£58.50**

DISCO VOK (slider controls) the
complete disco preamp **£72.00**

DJ100 100 watt power amplifier for
above **£49.50**

DJ30L Mk II 3 channel 3kw sound to
light **£41.25**
DJ30L Mk III slider controls **£45.50**
DJ DISC LITE as 30L+2 plus variable
speed flasher **£54.00**

DIMAMATIC 1 kW adjustable speed
auto dimmer **£25.00**
Carlsbro Reverberation Unit **£44.00**
Disco anti-feedback microphone **£11.95**
Cote 150 watt liquid wheel projector **£23.50**
150 watt QI liquid wheel projector **£50.00**
150 watt QI cassette wheel projector **£50.00**

Spare Effects and liquid cassettes large
range of patterns **£6.00**
6 inch Liquid wheels **£5.00**
Various cassettes **£6.00**
Mini spot bank fitted 3 lamps **£12.95**
Auto Trilite (mini with flashers) **£17.00**
Bubblemaker with liquid **£22.50**
Mixers/Mics/Speakers/Lighting

EXCLUSIVE DECCA KELLY SPEAKERS

12 watt speaker Tweeter
systems. 8" Bass/Midrange
and Melinex Domed HF
radiator plus crossover **£12.50**
per pair of systems (carr./pack. 40p)
or built into veneered cabinets, size 18 x
12 x 6 1/2" **£19.50** pair (carr. £1)



HI-FI TAPE EQUIPMENT

U.K.'s largest range with
discounts and demonstra-
tions for callers. Latest
stock lists on request (Ref. No. 17).
Phone 01-402-4736 for Barclay/Access
Card. Direct orders and latest prices.



TRANSISTORS/SEMI- CONDUCTORS

U.K.'s largest range for every application.
Small quantity discounts. Also Trade,
Export and Industrial enquiries invited.
Latest stock list (Ref. No. 36) including
valves on request.

ELECTRONICS SUPPLIES

Specialists in electronics for more than
30 years. Trade and industry supplies—
every type of component and equipment.



NEW SINCLAIR PROJECT 80

Stereo PreAmplifier **£11.95**
Audio Filter Unit **£6.95**
Z40 15 Watt Amplifier **£5.45**
Z60 25 Watt Amplifier **£6.95**
PZ5 Mod. (5 Tab) 1 or 2 Z40 **£4.98**
PZ6 Mod. (5 Tab) 1 or 2 Z40 **£7.98**
PZ8 Mod. (5 Tab) 1 or 2 Z60 **£7.98**
TRANSFORMER FOR PZ8 **£3.95**

NEW FM TUNER **£11.95**
STEREO DECODER **£7.45**

All items post paid.

LIVING SOUND LOW NOISE TOP QUALITY CASSETTES MADE BY EMI TAPES LTD. TO INTERNATIONAL STANDARDS ESPECIALLY FOR HENRY'S.

ALL POST PAID LESS THAN 1/2 REC. PRICES COMPLETE
WITH LIBRARY CASES

	3 for	6 for	10 for	25 for
C 60	£1.10	£1.98	£3.00	£7.40
C 90	£1.46	£2.80	£4.60	£11.25
C 120	£1.80	£3.45	£5.45	£13.45

Quantity and trade enquiries, invited

LEARN A LANGUAGE—complete with phrase
book. German — French — Spanish —
Italian **£1.36** per course. **£5** for any 4.



LOW COST HI-FI SPEAKERS

SPECIAL OFFERS
EMI 13" x 8"—full range speakers
(post 20p each or 30p pair)
*150TC—8 ohms Twin Cone 10 watt
£2.20 each or **£4.00** pair.
*450 10 watt C/o Twin Tweeters 3, 8 or
15 ohms **£3.85** each
EW 15 watt 8 ohms C/o Tweeter **£5.25**
350 20 watt C/o Tweeters 8 or 15 ohms
£7.80 each
* Polished wood cabinet **£4.80** post 35p.

8 ohms full range (post 20p)

FR4	4"	5 watt	£4.75
FR65	6 1/2"	10 watt	£6.30
FR8	8"	15 watt	£8.50
FR23	9 x 6"	15 watt	£8.90

BASS & MID RANGE—8 ohms (post 20p)


AA12	5"	15 watt	£3.75
B110	5 1/2"	15 watt	£7.20
B200	8"	15 watt	£8.50
B139/2	13" x 8"	30 watt LF	£13.75

TWEETERS AND CROSSOVERS (post 20p)

K2006	10 watt	8 or 15 ohms	£2.10
FHT6	15 watt	8 ohms	£3.35
K2011	3 watt	8 ohms	£4.80
T27	KEF		£5.30
Axcnt 100	30 watt	8 ohms	£5.52
K4009	1kHz/5kHz C/o		£2.70
SN75	3kHz var. C/o		£3.10

SPEAKER KITS (carr. etc. 35p)

20-2	8"	30 watt	£24.50 pair
20-3	8"	40 watt	£35.95 pair
LINTON 2		20 watt	£18.30 pair
GLENDALE 3		30 watt	£32.95 pair
DOVEDALE 3		30 watt	£51.50 pair
KEF KK2			£55.00 pair
KEF KK3			£78.00 pair

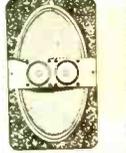

U.K.'s largest range of Disco Lighting,
FREE STOCK LIST REF. NO. 18 ON
REQUEST

AKG / RESLO / DJ / CARLSBRO / EAGLE
MICS, STANDS, MIXERS, CABINETS,
CHASSIS AND COMPLETE SPEAKER
SYSTEMS, MEGAPHONES, TURN-
TABLES, PUBLIC ADDRESS COM-
PONENTS.



All prices carr. paid (UK) (VAT EXTRA)
Barclaycard/Access call, write or phone your
order 01-723-6963—easy terms for callers.

BUILD YOURSELF A POCKET CALCULATOR

A complete kit, packaged in a polystyrene con-
tainer and taking about 3 hours to assemble—
that's the Sinclair Cambridge pocket calculator
from Henry's. Some of the many features include
interface chip, thick-film resistor pack, printed
circuit board, electronic components pack.
Size 4 1/2" long x 2 1/2" wide x 1 1/2" deep.
Free of charge with the kit for the more advanced
technologist is a 32-page booklet explaining how
to calculate Logs, Tangents, Sines etc.

£24.95 Also available **£27.20**
+ VAT. assembled ready to use. + VAT.



10% VAT to be added to all orders. Export supplied. Prices and descriptions correct at time of proof. Subject to change without notice. E & O E. Like a permanent job at Henry's? Experienced and trainee salesmen required. Tel. 01-402 8791. See page 55 of this magazine

Henry's

LIMITED

EDGWARE ROAD, LONDON W2

404-406 Electronic Components and Equipment 01-402 8381
309 PA - Disco - Lighting High Power Sound 01-723 6963
303 Bargains Store (Callers only)

Home and Car Entertainment Centres. London and branches now open.
120 Shaftesbury Avenue, London W1 01-437 9692
104 Burnt Oak Broadway, Burnt Oak, Edgware 01-952 7402
190-194 Station Road, Harrow, Middlesex 01-663 7788/9
354-356 Edgware Road, London W2 01-402 5854/4736

All mail to:
303 Edgware Road
London W2 1BW

All stores open 9 am to
6 pm six days a week.
Hi-Fi - Tape Equipment
Discount Stock List
Free at all stores