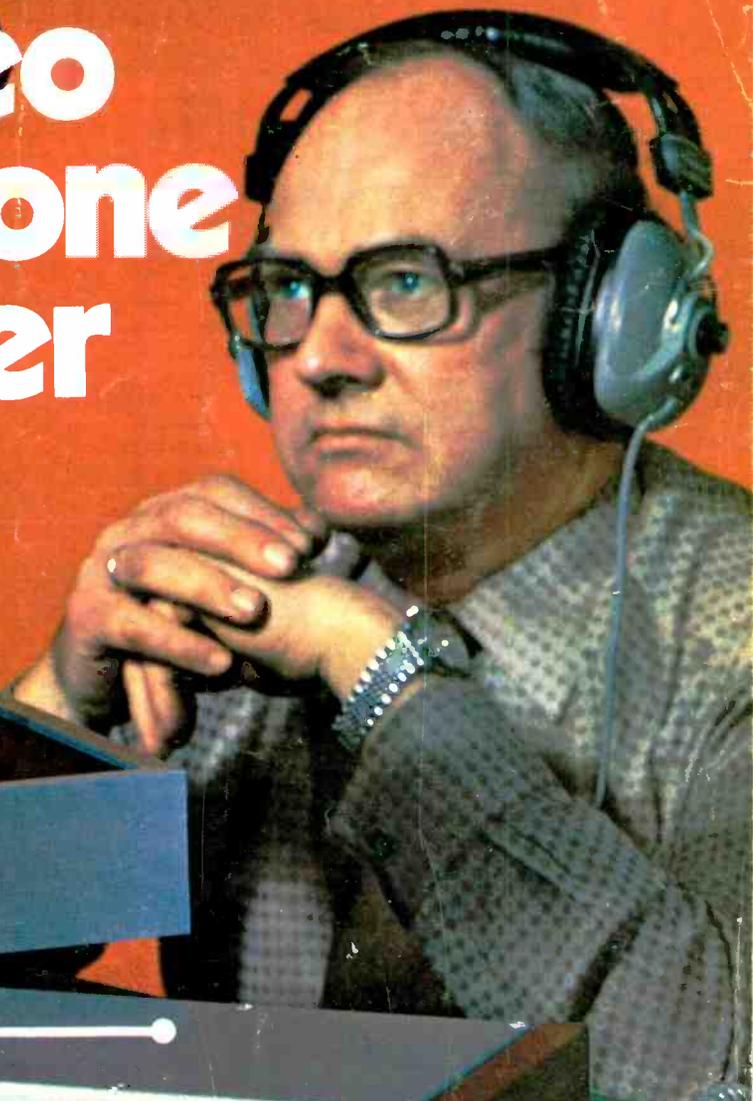


# PRACTICAL WIRELESS

AUGUST  
1974

25p

## PW DERBY Stereo Headphone Amplifier



TWO METRE CONVERTER

HIGH QUALITY SOUND LINKS

# ELECTROVALUE

Present

## THIS MONTH'S SELECTION OF GUARANTEED-TO-SPECIFICATION COMPONENTS

Everything Brand New ★ Attractive Discounts ★ Free Postage (U.K.)

### TRANSISTORS

and semi-conductors of many types from simple diodes to ICS photo-sensitive devices, threshold switches, etc. etc.

#### MINITRON DIGITAL INDICATORS

3015F Seven segment filament, compatible with standard logic modules, 0-9 and decimal point; 9mm characters in 16 lead DIL (some alphabetical symbols available) £1 20  
Suitable BCD decoder driver 7447 £1 15  
3015G showing + or - & 1 & dec. pt. £1 20

### CAPACITORS

#### DALY ELECTROLYTIC

in cans, plastic sleeved  
1000mF/25V 28p 1000/50 41p  
5000/100 £2 91 2000/50 57p  
5000/25V 62p 5000/50 £1 18  
2200/100 £1 56

#### POLYESTER TYPE C.280

Radial leads for P.C.B. mounting. Working voltage 250V d.c.

0-01, 0-015, 0-022, 0-033, 0-047 ea. 3p  
0-068, 0-1, 0-15 ea. 4p  
0-22, 5p, 0-33 7p, 0-47 8p; 0-68 11p; 1-0 14p;  
1-5 21p; 2-2 24p

#### SILVERED MICA

Working voltage 500V d.c.

Values in pF's—2-2 to 820 in 32 stages ea. 6p  
1000, 1500 7p; 1800 8p; 2200 9p; 2700, 3600 12p;  
4700, 5000 15p; 6800 20p; 8200, 10,000 25p

#### TANTALUM BEAD

0-1, 0-22, 0-47, 1-0 mF/35V, ea. 14p  
2-2/16V, 2-2/35V, 4-7/16V, 10/6 3V ea. 14p  
4-7/35V, 10/16V, 22/6 3V ea. 18p  
10/25V, 22/16V, 47/6 3V 100/3V ea. 20p

#### POLYCARBONATE

Type B42540 Working Voltage—250V

Values in mF: ea. 3p  
0-0047, 0-0068, 0-0082, 0-01, 0-012, 0-015  
0-018, 0-022, 0-027, 0-033, 0-039, 0-047, 0-056  
0-068, 0-082, 0-1 ea. 4p

#### CERAMIC PLATE

Working voltage 50V d.c.

In 26 values from 22pF to 6800pF, each, 2p

### POTENTIOMETERS

#### ROTARY, CARBON TRACK. Double wipers

for good contact and long working life

P.20 SINGLE linear 100ohms to 4-7megohms, ea. 14p

P.20 SINGLE log. 4-7Kohms to 2-2megohms, ea. 14p

JP.20 DUAL GANG lin. 4-7Kohms to 2-2megohms, ea. 48p

JP.20 DUAL GANG log. 4-7Kohms to 2-2megohms, ea. 48p

JP.20 DUAL GANG Log/antilog 10K, 22K, 47K, 1 megohm only ea. 48p

JP.20 DUAL GANG antilog 10K only ea. 48p

2A DP mains switch for any of above 14p extra.

Decades of 10, 22 and 47 only available in ranges above.

Skeleton Carbon Presets Type PR, horizontal or vertical 6p each.

#### SLIDER

Linear or log. 4-7K to 1 meg. in all popular values ea. 30p

Escutcheon plates, black, white or light grey, ea. 10p

Control knobs, blk/whl/red/yel/grn/blu/dk. grey/lt. grey ea. 7p

### JACKS AND PLUGS

#### Sockets

2-circuit unswitched S1/SS 12p

2-circuit /2 break contacts S1/BB 15p

3-circuit unswitched (Not GPO) S3/SSS 17p

3-circuit with 3 break contacts S3/BBB 20p

2 circuit with chrome nut and black/white/red/green or grey unswitched S5/SS 16p

with 2 break contacts S5/BB 20p

Miniature 3.5mm 2-circuit, (black) 2 br. cont S6/BB 9p

#### Plugs

2 circuit screened top entry P1 24p

side entry SEP 36p

Line socket mono 231 40p

Line socket stereo 244 45p

3 circuit unswitched, bl/grey/wh. P4 46p

2 circuit, unswitched, bl/whl/red/bl/grn/gry P2 18p

3 circuit screen top entry P3 53p

side entry SEP3 55p

Miniature 3.5mm 2-circuit screened P5 13p

Min. 3.5mm 2-circ. unscrnd. various colours P6 10p

## EV CATALOGUE

2nd printing  
(Green and yellow cover)

112 pages, thousands of items; illustrations; diagrams; much useful technical information. The 2nd printing of this catalogue has been updated as much as possible on prices. It costs only 25p post free and includes a refund voucher for 25p for sending when ordering goods list value £5 or more.

### INSULATED SCREW TERMINALS

In moulded polypropylene, with nickel plate on brass. With insulating set, washers, tag & nuts. 15A/250V in blk/bwn/red/yel/grn/bl/gry/wh. Type TP.1, ea. 14p

Suitable plugs Type TP4, 4mm each 7p  
Type TP2, 2mm each 4p

### ZENER DIODES

Full range E24 values: 400mW: 2-7V to 33V, 14p each; 1W: 6.8V to 82V, 21p each; 1.5W: 4-7V to 75V, 67p each. 20W: 7.5V to 75V, 94p each. Clip to increase 1.5W rating to 3 watts (type 266F), 5p.

### RESISTORS

Code Watts Ohms 1 to 9 10 to 99 100 up  
(see note below)

C	1/3	4-7-470K	1-3	1-1	0-9 nett
C	1/2	4-7-10M	1-3	1-1	0-9 nett
C	3/4	4-7-10M	1-5	1-2	0-97 nett
C	1	4-7-10M	3-2	2-5	1-92 nett
MO	1/2	10-1M	4	3-3	2-3 nett
WW	1	0-22-3-9	9	9	8
WW	3	1-10K	7	7	6
WW	7	1-10K	9	9	8

#### Codes:

C = carbon film, high stability, low noise.  
MO = metal oxide, Eloxal TR5, ultra low noise.  
WW = wire wound, Plessey.

Values: All E12 except C 1/3, C 3/4, and MO 1/2 W. E12: 10, 12, 15, 18, 22, 27, 33, 39, 47, 56, 68, 82 and their decades

E24: as E12 plus 11, 13, 16, 20, 24, 30, 36, 43, 51, 62, 75, 91 and their decades.

#### Tolerances:

5% except WW 10% ±0.05Ω under 10Ω and MO 1/2 2%.

Prices are in pence each for quantities of the same ohmic value and power rating. NOT mixed values. (Ignore fractions of one penny on total value of resistor order.) Prices for 100 up in units of 100 only.

### VEROBOARD

Copper clad 0-1 matrix—2-5 x 3-75 ins. 30p; 3-75 x 3-75 ins.—30p; 2-5 x 5 ins.—30p; 3-75 x 5 ins.—33p.

Copper clad 0-15 in. matrix 2-5 x 3-75 ins.—20p;

3-75 x 3-75 ins.—30p; 2-5 x 5 ins.—30p; 3-75 x 5 ins.—36p.

Vero spot face cutter (any matrix) 48p.

0-040 pins (for 0-1 matrix) per 100—36p.

0-052 pins (for 0-15 matrix) per 100—36p.

APPOINTED STOCKISTS FOR SIEMENS QUALITY PRODUCTS

## ELECTROVALUE LTD

28, ST. JUDES ROAD, ENGLEFIELD GREEN, EGHAM, SURREY TW20 0HB  
Telephone Egham 3603 Telex 264475 Shop hours 9-5.30 daily: Sat. 9-1 p.m.

NORTHERN BRANCH: 680, Burnage Lane, Burnage, Manchester M19 1NA  
Telephone (061) 432 4945 Shop hours 9-1 p.m. 2-5.30 daily: Sat 9-1 p.m.

U.S.A. CUSTOMERS are invited to contact ELECTROVALUE AMERICA, P.O. Box 27, Swarthmore PA 19081.

### ELECTROLYTICS

Axial Lead	3V	6.3V	10V	16V	25V	40V	63V	100V
0-47	—	—	—	—	—	—	11p	8p
1-0	—	—	—	—	—	—	—	8p
2-2	—	—	—	—	11p	—	—	9p
4-7	—	—	—	—	—	8p	9p	8p
10	—	—	—	—	—	8p	8p	8p
22	—	—	—	—	8p	9p	8p	10p
47	8p	—	—	—	—	—	—	—
100	9p	8p	8p	8p	8p	8p	10p	13p
220	8p	8p	9p	10p	10p	11p	17p	28p
470	9p	10p	10p	11p	13p	17p	24p	45p
1,000	11p	13p	13p	17p	20p	25p	41p	—
2,200	15p	18p	23p	26p	37p	—	—	—
4,700	26p	39p	44p	58p	—	—	—	—
10,000	42p	46p	—	—	—	—	—	—

### KNOPS

In a great variety of modern types, for 1/4" shaft, from plastic to solid aluminium as well as pointer and numbered types.

### CONNECTORS

DIN from two way to 7 way plugs and sockets, phono types mains connections, etc. etc. Page 88 in Catalogue 7

### BAXANDALL SPEAKER KIT

As designed by P. J. Baxandall and described originally in "Wireless World." Simple to assemble, fantastically good results and a greater money saver. Carries 10 watts RMS, 15 ohms impedance. Size 18in x 12in x 10in. Complete kit, including pack-flat cabinet, £14 90.

The size and weight of this product obliges us to charge 70p port cost of carr. in U.K.  
Equaliser Assembly, £2 30.  
Loudspeaker Unit 59RM109, £2 45.  
Cabinet Kit (to Baxandall design), £10 45.  
Cross-over choke for additional woofer to above £1 50.

**This is EV Service**

### DISCOUNTS

Available on all items except those shown with NETT PRICES. 10% on orders from £5 to £14-99. 15% on orders £15 and over.

### PACKING AND POSTAGE FREE

in U.K. for pre-paid mail orders, except Baxandall. For order list value £2 and under there is an additional handling charge of 10p.

### GUARANTEE OF QUALITY

All goods are sold on the understanding that they conform to manufacturers' specifications and satisfaction is guaranteed as such—no rejects, "seconds" or sub-standard merchandise is offered for sale.

### GIRO ACCOUNT—No. 38/671/4002

Prices quoted do not include V.A.T., for which 10% must be added to total nett value of order. Every effort is made to ensure correctness of information and prices at time of going to press. Prices subject to alteration without notice.

All postal communications, mail orders etc. to Head Office at Egham address, Dept. EE7. S.A.E. with enquiries requiring answers.

# PRACTICAL WIRELESS

VOL. 50 NO. 4

ISSUE 810

AUGUST 1974

BRITAIN'S PREMIER MAGAZINE FOR THE DO-IT-YOURSELF RADIO AND ELECTRONICS CONSTRUCTOR

**EDITOR** Morris A. Colwell

**ASSISTANT EDITOR**  
Lionel E. Howes, G3AYA

**ART EDITOR** Peter Metalli

**TECHNICAL EDITOR**  
Eric Dowdeswell, G4AR

**PRODUCTION & NEWS  
EDITOR** Colin R. Riches

**PROJECTS SUB-EDITOR**  
Geoffrey C. Arnold

**TECHNICAL ARTIST**  
Alan Martin

**SECRETARIAL** Jenny Maunder  
01-634 4292 Susan Corne

**ADVERTS. MANAGER**  
01-634 4293 Roy Smith

**CLASSIFIED ADVERTS.**  
01-634 4301 Colin R. Brown

---

Published by IPC Magazines Ltd.,  
Fleetway House, Farringdon Street,  
London EC4A 4AD. Tel. 01-634 4444

---

## SUBSCRIPTIONS

Publisher's Subscription Rate for one year to the UK is £3.25 and to the rest of the world £3.50 including postage. Enquiries to Subscription Department, IPC Magazines Ltd., Carlton House, 68 Gt. Queen Street, London, WC2 5DD. Phone 01-242 4477. International Giro facilities Account No. 5122007. Please state reason for payment "message to payee".

Binders (£1.34) and indexes (11p) can be supplied by the Binders Dept at the same address.

## BACK NUMBERS

We regret that we are unable to supply back numbers of Practical Wireless. Readers are recommended to enquire at a public library to see copies. Requests for specific back numbers of Practical Wireless and Television only can be published in our CQ Column.

## COPYRIGHT AND QUERIES

© IPC Magazines Limited 1974. Copyright in all drawings, photographs and articles published in "Practical Wireless" is fully protected and reproduction or imitation in whole or in part is expressly forbidden. All reasonable precautions are taken by "Practical Wireless" to ensure that the advice and data given to readers are reliable. We cannot, however, guarantee it and we cannot accept legal responsibility for it. Prices are those current as we go to press.

We regret that we cannot answer technical queries by telephone nor can we provide information or advice on manufacturers' products other than that given in the magazine. We will endeavour to assist readers who have queries relating to articles published but we cannot offer advice on modifications to our published designs. All correspondents expecting a reply should enclose a stamped addressed envelope.

## ● NEWS & COMMENT

- 304 SURPRISE!—Leader article and September preview
  - 305 NEWS . . . NEWS . . . NEWS . . .
  - 310 TELEVISION—Coming in the August issue
  - 318 CQ! CQ! CQ!
  - 326 HOTLINES on recent developments by Novus
  - 327 NEXT MONTH IN PRACTICAL WIRELESS
  - 348 SPECIAL PRODUCT REPORT—Cortina Major Multimeter
  - 353 ON THE AIR
  - 353 Broadcast Bands, Short Waves—*Malcolm Connah*
  - 354 Medium Waves—*Charles Molloy*
  - 354 VHF/FM—*Simon David*
  - 357 Amateur Bands, Short Wave/VHF—*Eric Dowdeswell, G4AR*
  - 358 BOOK REVIEW
- 

## ● CONSTRUCTIONAL

- 306 TWO-METRE CONVERTER—*L. Case, G8BJQ*
  - 322 TAKE 20 No. 62, Variable Ratio Counter—*David Andrews*
  - 323 EXPERIMENTAL WORKSHOP Loudspeaker Drivers—*M. J. Hughes, M.A.*
  - 328 P.W. "DERBY" STEREO HEADPHONE AMPLIFIER—*D. S. Gibbs*
  - 334 TELE-TENNIS, Part 2 Power Supply and Modulator—*M. J. Hughes, M.A.*
- 

## ● OTHER FEATURES

- 311 I.C. OF THE MONTH No. 46 LM381N Dual low noise amplifier—*M. J. Darby*
- 314 HIGH QUALITY SOUND LINKS—*Vivian Capel*
- 341 OSCILLOSCOPE TECHNIQUES Part 6—*Alan C. Ainslie*
- 349 GOING BACK—Equipment of yesteryear—*Colin Riches*

# HUGE DISCOUNTS

**ON LEADING BRAND HI-FI**

**All R.S.C. Prices include VAT**

\*Full labour and material guarantees for 12 months  
LOW DEPOSIT TERMS OVER 8 MONTHS

**WHARFEDALE DENTON**

List Price RSC Price

**WHARFEDALE LINTON**

£43.09 Pr. £29.95

**LEAK 150 SPEAKERS**

£53.35 Pr. £35.95

**LEAK 250 SPEAKERS**

£51.30 Pr. £31.95

**LINEAR 202 AMPLIFIER**

£60.86 Pr. £42.50

**Rotel RT222 AM/FM Tuner**

£39.93 £24.75

**Wharfedale Denton Tuner/Amp**

£51.50 £36.95

Also Shure Cartridges, Basf Tape, Koss H/Phones, etc.  
Prices shown correct at 30th May 1974

## AKAI TAPE UNITS

All £1 carr.

**GXC 36D** Rec. £112.75 **£64.95**

**GXC 38D** Rec. £139.90 **£99.95**

**GXC 36** £125.50 **£89.95**

**GXC 40T** £189.50 **£135.95**

**GXC 46D** Rec. £160.50 **£114.95**

**GXR 82D** £124.90 **£89.95**

**4000 DS** £132.50 **£94.95**

**1721 L** £120.75 **£86.95**

**CR 81D** £84.10 **£69.95**

**GOLDRING GL72 T/Table & G800 £29.95** (Approx. value £47.30) Carr. 75p

**GOLDRING GL75 T/Table & G800 £34.95** (Approx. value £67.20) Carr. 85p

**PIONEER PL12D T/Table on plinth & cover £39.95** List £55.97

**McDonald MP60 T/Table and P.U. £9.95** List £14.94

**BSR TD85 8 track player. Special price £12.95**

**T/TABLES with MAGNETIC CARTRIDGE/PLINTH & COVER**

**GARRARD SP25 MK IV with G850 Special Price £19.95** (Carr. £1)

**McDonald MP60 with G800 or G850** " " **£19.95** (Carr. £1)

**GOLDRING GL75 with G800** " " **£39.95** (Carr. £1)



**MARQUESS 30 MARQUESS 30**  
MacDONALD MP60  
**MODEL 60**  
AMPLIFIER

## A HI-FI 30 + 30W STEREO SYSTEM

**AUDIO FIDELITY MODEL 60 AMPLIFIER. £99.95**  
**PAIR AUDIO FIDELITY MARQUESS 30 SPKRS.**  
**GARRARD SP25 Mk IV or McDONALD MP60**  
with G800 Cartridge. Ready wired on Plinth with Cover.  
Cabinets finished in Teak Veneer. Send S.A.E. for leaflet.  
Or Deposit £11.48 and 18 fortnightly payments £5.74 (Total £114.80)

## HI-FI 10 + 10W STEREO SYSTEM

**AUDIOTRINE STEREO 20 AMPLIFIER**  
**GARRARD TURNTABLE** with Sonotone  
Cartridge wired on Plinth with cover.  
**PAIR DIPLOMAT 10W SPEAKERS**, Teak Veneer finish. Carr. £2

**£55**

## RSC G66 MkII 6+6 WATT high quality STEREO AMPLIFIER

Controls: Bass, Treble, Vol. and Bal. 10 Transistors plus Diodes. Output rating I.H.F.M. Frequency range 20-20,000 c.p.s. Bass Control ± 12db. Treble Control ± 13db. Selector switch for Crystal P.U. or Tape/Radio. For speaker output impedances of 3 — 15 ohms. For standard 200-250v. A.C. mains operation. Attractive Black and Silver finished metal fascia plate and matching control knobs. **COMPLETE KIT OF PARTS INCLUDING FULLY WIRED PRINTED CIRCUIT** and **COMPREHENSIVE WIRING DIAGRAMS & INSTRUCTIONS** **£12.75** Carr. 40p  
OR **FACTORY BUILT IN TEAK VENEERED CABINET** **£18.50** dep. £2.12 and 8 monthly payments £2.12 (Total £18.08)



## HI-FI SPEAKER ENCLOSURES

Teak veneer finish. Acoustically lined. Sizes approx. Carr. 45p per enc.  
**JE8 Size 16" x 11" x 9".** For optimum performance with any 8in. Hi-Fi speaker. **£5.95**  
**SE10 For outstanding results** with 10in. Hi-Fi speaker. **£6.95**  
**SE12 For excellent performance** with 12in. Hi-Fi speaker and tweeter. **£7.95**  
2 1/2 x 16 x 9in. Ported



## AUDIOTRINE HI-FI SPEAKER SYSTEMS

Consisting of matched 12in. 11,000 line 15 Watt 15 ohm high quality speaker, cross-over unit and tweeter. Smooth response and extended frequency range ensure surprisingly realistic reproduction. **£7.45** Carr. 45p  
OR **SENOR 15 WATT INCLUDING** **£7.95** Carr. 50p  
**HF126 15,000 LINE SPEAKER**



## AUDIOTRINE HIGH FIDELITY SPEAKERS

Heavy construction. Latest high efficiency ceramic magnets. Plasticised Cone surround. "D" or "T" indicates Tweeter Cone providing extended frequency range up to 15,000 c.p.s. Impedance 3 or 8-15 ohms. **PLEASE STATE CHOICE.**  
Exceptional performance at low cost.

HF908T	8"	10W	£2.55	HF180D	12"	15W	£6.50
HF108D	10"	10W	£3.80	HF126	12"	15W	£7.95
HF120	12"	15W	£5.95	HF180D	12"	15W	£6.50

## FANE 807T HIGH FIDELITY SPEAKER

A full range 8in. 10 watt unit for excellent sound quality, in suitable enclosure. Cast chassis Roll P.V.C. cone surround and long throw voice coil to achieve very low fundamental resonance of 30 c.p.s. Tweeter cone is fitted to extend high note response. Frequency range 25 Hz to 15 KHz. Gauss 10,000. Impedance 3 or 8-15 Ω. **PLEASE STATE IMPEDANCE REQUIRED** List £4.50 **£3.99**  
**MODEL 808T 8" 15w.** with parasitic Tweeter. **£5.50** List £6.50  
Response 25 Hz to 15 KHz. Gauss 13,000 Imp 3 or 8-15Ω.



## R.S.C. TA6 6 Watt HI-FI AMPLIFIER

200-250v. AC mains operated. Response 30-20,000 c.p.s. — 2dB. Separate Bass and Treble 'lift and cut' controls. 3 input sockets for Mike, Gram, Radio or Tape. Input selector switch. Output for 3-15 ohm spkrs; Max. sensitivity 5mV. O/P rating I.H.F.M. Enclosed enamelled case 9 1/2 x 2 1/2 x 5 1/2in. Silver finish fascia 10 1/2 x 3 1/2in. **FACTORY BUILT** Complete kit, wiring diagrams and instructions. **£7.95** Carr. 40p. **£10.95**



## R.S.C. TA12 MKIII 6.5+6.5 WATT STEREO AMPLIFIER

Fully Transistorised. Hi-Fi/Op of 6.5 watts per channel. Optimum performance with any crystal or ceramic P.U. Cartridge, Radio Tuner, Tape Rec. etc. Input Sel. Switch, Bass, Treble, Vol. & Bal. Controls. **COMPLETE KIT OF PARTS WITH FULL £12.99** Carr. 40p.  
**WIRING DIAGRAMS & INSTRUCTIONS** **£16.95** Or In Teak Veneer housing **£19.95** Dep. £2.50 & 8 monthly payments 12 mths guarantee **£22.50** (Total £22.50)

## AUDIO FIDELITY FRI SPEAKER KIT

Response 30Hz-15KHz. Rating 15 watts in sealed cabinet. Imp. 8-15 ohms. 8" Bass Unit with P.V.C. Cone surround for ultra low resonance. Pressure Tweeter. Printed Circuit. Inductive/Capacitive Cross-over. Damping Material, Screws, Terminal Panels. **£11** each. **SPECIAL £14.99** Pair Carr. Free. **OFFER** Carr. 50p



## R.S.C. MkIII SUPER 30 HIGH FIDELITY STEREO AMPLIFIER

**BUILD AN AMPLIFIER WORTH APPROXIMATELY DOUBLE THE KIT PRICE INCLUDING CABINET**  
Only high grade components by leading manufacturers  
\* Push Button Selector Switching  
\* Jack Socket for Headphones  
\* Neon Indicator  
\* Satin Silver Finish Metal Fascia  
\* Solid State Circuitry  
\* Twenty Silicon Transistors  
\* Four Diodes, Four Rectifiers  
Send S.A.E. for full descriptive leaflet.

For Magnetic or Ceramic Pick-Ups regardless of Price. Output (per channel) 15 watts RMS into 8Ω. Frequency Response 7 Hz to 70 KHz ± 1 dB.



**COMPLETE KIT** (less cabinet). **£22.95**  
Carr. 70p.  
Cabinet if req. £3 extra.

## R.S.C. STEREO FM III TUNER

in cabinet  
Visually matches Super 30 Mk. III **£37.95**

## 'YORK' HIGH-FIDELITY 3 SPEAKER SYSTEM

★ Moderate size only 25 x 14 x 10in. approx.  
★ Response 30-20,000 c.p.s. Impedance 15 ohms  
Performance comparable with **COMPLETE KIT** units costing considerably more **£25.95** Carr. 75p  
Consists of (1) 12in. 15W Bass Unit with cast chassis. Roll rubber cone surround for ultra low resonance. (2) 3-way quarter section series cross-over system. (3) 8 x 5in. high flux middle range speaker. (4) Dome Pressure Tweeter. (5) Quantity acoustic damping material. (6) Handsome Teak veneered cabinet. (7) Circuit and full instructions. Terms. Deposit £4.71 and 8 monthly payments £3.12 (Total £29.67)



## R.S.C. TRANSFORMERS, L.F. CHOKES & RECTIFIERS FULLY GUARANTEED. Impregnated and interleaved where necessary. Primaries 200-350v. 50c/s. Screened

<b>MIDGET CLAMPED TYPE 2 1/2 x 2 1/2 in.</b> 250v., 60mA, 6.3v. 2a ..... £1.10 250-0-250v., 60mA 6.3v. 2a ..... £1.16	<b>TOP SHROUDED DROP-THRO' TYPE</b> 250-0-250v. 70mA, 6.3v. 2a., 0-5-6.3v. 2a. £1.49 250-0-250v. 100mA, 6.3v. 3.5a. £1.71 250-0-250v. 100mA, 6.3v. 2a., 0-5-6.3v. 1a. £1.75 350-0-350v. 80mA, 6.3v. 2a., 0-5-6.3v. 2a. £1.81 250-0-250v. 100mA, 6.3v. 4a., 0-5-6.3v. 3a. £2.45 300-0-300v. 100mA, 6.3v. 4a., 0-5-6.3v. 3a. £2.45 300-0-300v. 130mA, 6.3v. 4a., c.t., 6.3v. 1a. £2.85 Suitable for Mullard 510 Amplifier. £2.85 350-0-350v. 100mA, 6.3v. 4a., 0-5-6.3v. 3a. £2.85 350-0-350v. 150mA, 6.3v. 4a., 0-5-6.3v. 3a. £2.85	<b>SELENIUM RECTIFIERS</b> F. W. (Bridged) All 6 1/2v. D.C. output. Max. A.C. input 15v. 1a. 25p. 2a. 39p. 3a. 55p. 4a. 78p. 6a. 88p.
<b>FULLY SHROUDED UPRIGHT MOUNTING</b> 250-0-250v. 60mA, 6.3v. 2a., 0-5-6.3v. 2a. £1.55 250-0-250v. 100mA, 6.3v. 4a., 0-5-6.3v. 3a. £2.45 300-0-300v. 100mA, 6.3v. 4a., 0-5-6.3v. 3a. £2.45 300-0-300v. 130mA, 6.3v. 4a., c.t., 6.3v. 1a. £2.85 For Mullard 510 Amplifier. £2.85 350-0-350v. 100mA, 6.3v. 4a., 0-5-6.3v. 3a. £2.85 350-0-350v. 150mA, 6.3v. 4a., 0-5-6.3v. 3a. £2.85	<b>CHARGER TRANSFORMERS 0-9-15v. 1 1/2a. £1.10.</b> 2 1/2a. £1.25; 3a. £1.40; 5a. £1.60; 6a. £1.85; 8a. £2.20 <b>OUTPUT TRANSFORMERS</b> 0-110/120v. 200-250-0. 60-80 watts £1.25. 150 watts. £2.10 250 watts £2.80; 500 watts £6.40	<b>L.F. CHOKES</b> 150mA, 7-10H, 250 Ω 77p; 100mA, 10H, 200 Ω 86p; 80mA, 10H, 350 Ω 85p; 60mA, 10H, 400 Ω 85p.
<b>FILAMENT or TRANSISTOR POWER PACK</b> Types 6.3v. 1.5a. 55p; 6.3v. 2a. 80p; 6.3v. 3a. 85p; 6.3v. 6a. £1.45; 12v. 1a. 61p; 12v. 3a. or 24v. 1.5a. £1.50; 0-9-18v. 1 1/2a. £1.25; 0-12-26-42v. 2a. £1.95.	<b>OUTPUT TRANSFORMERS</b> Push-Pull 8 watts EL84 to 3 Ω or 15 Ω ... 95p Push-Pull 10 watts 6V6 3-8-15 Ω ... £1.25 Push-Pull EL84 to 3 or 15 Ω 10-12 watts ... £1.50 Push-Pull Ultra Linear for Mullard 510, etc. £2.45 Push-Pull 15-18 watts, sectionally wound 6L6, KT66, etc., for 3 or 15 Ω ... £2.20 Push-Pull 20 watt high quality sectionally wound EL34, 6L6, KT66 etc. to 3 or 15 Ω £3.85	

# RSC 100 watt DISCO SYSTEM



Units listed below  
 (a) DISCOMASTER TWIN TABLE CONSOLE with integral 100W amp.  
 (b) PAIR OF HI-FI HEAD-PHONES  
 (c) MATCHING DYNAMIC 'MIKE' (attached to telephone)  
 (d) PAIR 50 WATT SPEAKERS  
 Black Rexine covered Cabinets Size approx. 18" x 18" x 8"  
**£149-95**  
 (a) (b) (c) & (d) Carr. £3-00

## RSC TDI DISCO CONSOLE

Incorporating twin Garrard SP25 or BSR MP60 type turntables and Sonotone or Acos Cartridges with diamond styli. Separate Vol. controls for each turntable. Also MONITORING FACILITIES, plus Treble and Bass Controls. Separate input for 'mike' with vol. control switch. Black Vynide covered Cabinet with lid, see illustration on left.  
 Or Dep. £7-98 and 18 fortnightly pmts. **£69-95**  
 £3-98 (Total £79-80) Carr. £1-50

Deposit £19-95 & 19 fortnightly payments of £7-87 (Total £169-48).

## DISCOMASTER TWIN TURNTABLE POWER CONSOLE

Garrard SP25 or McDonald MP60 turntables, Sonotone or Acos cartridges with diamond styli. Facilities as TDI Console but with built-in 100 watt Power Amplifier, complete with lid. Or Deposit £11-48 and 18 fortnightly payments £5-74 Carr. £2-50 (Total £114-80)

### R.S.C. COLUMN SPEAKERS IDEAL FOR VOCALISTS AND PUBLIC ADDRESS

All types 16 Ohms covered in Rexine and Vynair

<b>TYPE C132 30-40 WATTS</b> Fitted two exceptionally efficient, low feedback howl characteristic high flux 13" x 8" 20 watt speakers. Terms: Dep. £2-95 and 8 mthly payments £2-51 (Total £29-03) Carr. 65p.	<b>TYPE C3/70 70 WATTS</b> Fitted three 12" 25 watt Highly sensitive high flux speakers with high power voice coils. Size approx. 54" x 14" x 11". Dep. £9-95 & 8 mthly pmts. £4-31 (Total £44-43) Carr. 86p
---	--

## FANE ULTRA HIGH POWER LOUDSPEAKERS

All power ratings are R.M.S. continuous. 2 YEARS' GUARANTEE High flux ceramic magnets. ALL CARRIAGE FREE.

<b>'POP' 100</b> 18" 100 Watt 14,000 gauss 8/15Ω <b>£29-70</b> Dep: £3-80 and 5 mthly payments £3 80 (Total £34-20)	<b>'POP' 60</b> 15" 60 Watt 14,000 gauss 8/15Ω <b>£16-95</b> Dep. £2-17 and 8 monthly payments. £2-17 (Total £19-53)	<b>'POP' 50</b> 12" 50 Watt 13,000 gauss 15Ω <b>£12-99</b> Dep £1-95 and 8 monthly payments £1-71 (Total £15-63)
--	---	---

FOR BASS GUITAR, ELECT. ORGAN, ETO. PAIR SUITABLE ALL PURPOSES

## NEW 'POP' 55 12" 60W £15-95

Gauss 15,000 Imp 8/15Ω Or Dep £2-45 & 8 monthly payments £2 (Total £18-45) Carr. Free

## ALL RSC PRICES INCLUDE VAT

INTEREST CHARGES REFUNDED on Credit Purchases settled in 3 months

### MINSTREL 8W GUITAR AMP.

Incorporating Tremolo and 13" x 8" or 10" Speaker. Output 8 watts R.M.S. Continuous. 3 Jack Inputs for Microphone and Instrument. Mains Neon Controls: Volume, Tone, Tremolo Speed Tremolo Intensity.  
 Terms: Deposit £2-95 and 8 monthly payments £2-39 (Total £29-07). Carr. free

### FANE CRESCENDO SPEAKERS

Full range available at ALL BRANCHES

## FAL PHASE 50 Mk. III AMPLIFIER 50 WATT

Solid state. 4 Separately controlled inputs Plus master vol. control. Ind. Bass and Treble Controls. Protective Circuitry against serious output overloading. Output for Speakers/3 to 30 ohms. Size 17" x 7" x 7 1/4". 200-250v. A.C. mains. Output 50 watts music rating. Or deposit £9-93 & 8 monthly payments £4-81. Total £44-41.



## FANE SPEAKERS 'POP' 25/2 12 in. 30 WATT

Dual Cone 15 Ω (for uses other than Bass Guitar or Electronic Organ). Carr. free **£8-99** CREDIT TERMS (PAIRS ONLY) Dep. £2-80 & 8 mthly pmts. £2-80 (Total £21-20).

## GROUP EQUIPMENT PACKAGE OFFERS

F.A.L. PHASE 50 MK. III AMPLIFIER PR. FANE POP 66/8 30W L/SPEAKERS Terms: Deposit £6-77 and 8 monthly payments of £6-77 (Total £60-93)	£39-93 £17-98 <b>£57-91</b>	PACKAGE PRICE <b>£52-95</b> carr. £1-10
F.A.L. PHASE 50 MK. III AMPLIFIER PR. FANE POP 60 L/SPEAKERS Terms: Deposit £10-05 and 18 fortnightly payments of £3-33 (Total £69-99)	£39-93 £25-98 <b>£65-91</b>	PACKAGE PRICE <b>£59-99</b> carr. £1-10
F.A.L. PHASE 50 AMPLIFIER PAIR L12/20 SPEAKERS (in Cabinet) Terms: Deposit £10-05 and 18 fortnightly payments £3-33 (Total £69-99)	£39-93 £25-90 <b>£65-83</b>	PACKAGE PRICE <b>£59-99</b> carr. £2-00

## HIGH QUALITY LOUDSPEAKER UNITS

ALL TWO TONE REXINE AND VYNAIR FINISH  
 L125 50 WATT Fitted pair of 12" 50 watt high flux speakers for conservative rating. Impedance 8-15 ohms. Carr. £1-50  
 Or deposit £7-95 and 8 monthly pmts. of £4-72. Total £45-71

L12/20 12" 25 WATT 13,000 lines 16 ohms Terms for Pairs. Dep. £2-32 & 8 mthly pmts £3-82 (Total £29-88) Carr. 65p.	L12/10 10-15 Watt Veneered cabinet 12" unit 8-15 ohm. Approx. 13" x 14" x 9". Carr. 65p. Terms for Pairs. Dep. £2-05 & 8 mthly pmts £2-05 (Total £18-45).
--	---

## RSC PHANTOM '50' Combined 50W Amplifier and 12in. Loudspeaker.

For Lead Guitar, Mic., Gram, Radio, Tape (Not for use with Bass Instruments). Inc. 3 inputs and 2 vol. controls plus Treble, Bass and Presence. Output Jack for additional 16 ohm Speaker. Attractively finished in black with silver-finished fascia and trimmings. Compact size. Fitted carrying handle.  
 Terms: Deposit £6-99 and 8 monthly payments £6-39 (Total £57-81). Carr. £1-50  
 SAE for leaflet UK Mainland

**ONLY £49-95**  
 SPECIAL PRICE for limited period

## REGENT 50X AMPLIFIER

A powerful high quality unit for lead, rhythm, guitar, vocalists, gram, radio, tape. Peak Output rating. Not for Bass Guitar.  
 ★ Two extra heavy duty 12in. speakers.  
 ★ Four Jack inputs and two Volume Controls for instant use of up to four pick-ups or 'mikes'. Bass and Treble controls. Send S.A.E. for leaflet. Credit Terms: Deposit £7-98. & 18 fortnightly payments of £3-99 (Total £79-80). Carr. £2-50.  
 REGENT 50B for Bass Guitar and general purposes. Or Dep. £9-18 & 18 fortnightly payments £4-69. (Total £91-80). Carr. £2-50

### GP30 AMPLIFIER For Guitar, Vocal or Instrumental Group

A 4 Input, 2 vol. control Hi-Fi 30 watt unit with Separate Bass and Treble controls. Current valves. Peak output rating. Strong Rexine covered cabinet with handles. Attractive black/silver P.V.C. fascia. Neon indicator. For 200-250v. A.C. mains. For 3 or 16 ohm speakers. Send S.A.E. for leaflet.  
 Terms: Deposit £3-58 and 8 monthly payments of £3-58 (Total £32-22).

## C4/100 HEAVY DUTY COLUMN SPEAKERS

Suitable for Public Address or Vocal and Instrumental Groups. Fitted four 12" 50 watt speakers. Robust attractive Vynide covered cabinet 58" x 16" x 10" approx.  
**SPECIAL PRICE £59-95**  
 Or Dep. £9-50 and 12 mthly pmts £3-90 (Total £66-80).

## NOW SEVEN NEW BRANCHES NEW LARGER PREMISES AT HULL, BOLTON, COVENTRY DONCASTER, STOCKPORT SUNDERLAND, PRESTON and NOTTINGHAM

**RSC**

HI-FI CENTRES LTD.

R.S.C. BRANCHES OPERATE A 5-DAY WEEK OPEN ALL DAY SATURDAY

BRADFORD 10 North Parade (Closed Wed.). Tel. 25349  
 BOLTON 23 Deansgate (Closed Wed.). Tel. 33512  
 BIRMINGHAM 30/31 Great Western Arcade. Tel. 021-236 129 (Closed Wed.).  
 COVENTRY 17 Shelton Square, The Precinct. Tel. 25983  
 DERBY 97 St. Peter's Street. (Closed Wed.). Tel. 41364  
 DARLINGTON 19 Northgate (Closed Wed.). Tel. 68043

Barclaycard and Access accepted

All items subject to availability. Prices correct at 30.5.74 E. & O.E.

DONCASTER 3 Queensgate, Waterdale Centre. EDINBURGH (Closed Thurs.). Tel. 63069  
 101 Lothian Rd. (Closed Wed.). Tel. 229 9501  
 GLASGOW 326 Argyle St. (Closed Tues.). Tel. 248 4158  
 HULL 7 Whitefriargate (Closed Thurs.). Tel. 20505  
 LEICESTER 32 High Street (Closed Thurs.). Tel. 56420  
 LEEDS 5-7 County (Mecca) Arcade, Briggate (Closed Wed.). Tel. 28252  
 LIVERPOOL 73 Dale St. (Closed Wed.). Tel. 236 3573  
 LONDON 238 Edgware Road, W.2. (Closed Thurs.). Tel. 723 1629

MAIL ORDERS & EXPORT ENQUIRIES TO:—  
 AUDIO HOUSE, HENCONNER LANE, LEEDS, 18. Tel: Pudsey (09735) 77631.  
 TERMS C.W.O. or O.O.D. No O.O.D. under £1. POSTAGE 28p EXTRA UNDER £2. 83p EXTRA OVER £2 OR AS QUOTED. TRADE SUPPLIED. S.A.E. PLEASE WITH ENQUIRIES.  
 SUPPLIES TO GOVT. DEPTS. H.M. FORCES. EDUCATION AUTHORITIES & HOSPITALS, ETC.  
 MAIL ORDERS MUST NOT BE SENT TO SHOPS

MANCHESTER 60A Oldham Street (Closed Wed.). MIDDLESBROUGH Tel. 236 2778  
 106 Newport Road (Closed Wed.). Tel. 47096  
 NEWCASTLE UPON TYNE 24 Newgate Shopping Centre (Closed Wed.). Tel. 21469  
 NOTTINGHAM 19/19A Market Street. PRESTON (Closed Thurs.). Tel. 48068  
 41 Friarfield Walk, St. Georges Shopp. Pct. Tel. 51979  
 SHEFFIELD 13 Exchange Street (Castle Mkt. Bldg. (Closed Thurs.). Tel. 20716  
 STOCKPORT (Closed Thurs.). Tel. 480-0777  
 SUNDERLAND 5 Market Sq. (Closed Wed.). Tel. 70573

# ESSENTIAL BOOKS FOR RADIO AMATEURS

## TEST EQUIPMENT for the radio amateur

by H. L. Gibson, CEng, MIEE, G8CGA

Explains in detail the theory behind modern measurement techniques, and describes many items of equipment of special interest to the home constructor. Topics include signal sources, attenuators, oscilloscopes, swept measurements, aerials and transmission lines. Detailed instructions are given for the construction of many items of test gear.

120 pages £2 post paid

## TELEPRINTER HANDBOOK

by D. J. Goacher, G3LLZ, and  
J. G. Denny, G3NTT

A brand new book covering all aspects of modern teleprinter techniques. Full descriptions and maintenance data for all widely-used machines, together with design and use of ancillary equipment. Definitely a book for the teleprinter enthusiast's work bench.

376 pages £5.35 post paid

## A GUIDE TO AMATEUR RADIO by Pat Hawker, G3VA

This extensively revised 15th edition is an indispensable aid to all who want to know more about amateur radio.

Specially designed to assist the newcomer to the hobby, it covers technical, operating and licensing matters.

96 pages Price 90p post paid

## AMATEUR RADIO AWARDS by C. R. Emary, G5GH

Lists all the world's major awards from national societies and how to obtain them.

Includes reproductions of certificates and maps, and operating information.

Loose-leaf binding allows insertion of amendment pages at a later date.

194 pages Price £1.40 post paid

These are just four of a complete range of technical publications, log books and maps for the radio amateur. Send a large s.a.e. for the complete list.

The RSGB is the national society representing all UK radio amateurs. Membership is open to all interested in the hobby: write to the General Manager and ask for full details.



# RADIO SOCIETY OF GREAT BRITAIN

35 DOUGHTY STREET, LONDON, WC1N 2AE TEL: 01-837 8688

## ENGINEERS

# FREE

## YOURSELF FOR A BETTER JOB WITH MORE PAY!

Do you want promotion, a better job, higher pay? "New Opportunities" shows you how to get them through a low-cost B.I.E.T. home study course. There are no books to buy and you can pay-as-you-learn.

The B.I.E.T. guide to success should be read by every ambitious engineer. Send for this helpful 76 page FREE book now. No obligation and nobody will call on you. It could be the best thing you ever did.



**CUT OUT THIS COUPON**  
**CHOOSE A BRAND NEW FUTURE HERE!**

Tick or state subject of interest. Post to the address below.

- |  |   |   |
|--|---|---|
| <input type="checkbox"/> Practical Radio & Electronics (Technatron)    | <input type="checkbox"/> Radio Amateurs Practical TV                | <input type="checkbox"/> General Electrical Engineering         |
| <input type="checkbox"/> Electronic Engineering                        | <input type="checkbox"/> Colour Television                          | <input type="checkbox"/> Society of Engineers (Electrical Eng.) |
| <input type="checkbox"/> TV Maintenance & Servicing                    | <input type="checkbox"/> C & G LI Radio                             | <input type="checkbox"/> Electrical Installations and Wiring    |
| <input type="checkbox"/> General Radio & TV Engineering                | <input type="checkbox"/> TV Servicing Cert.                         | <input type="checkbox"/> C & G Electrical Technicians (Primary) |
| <input type="checkbox"/> Radio Servicing, Maintenance & Repairs        | <input type="checkbox"/> Post Master General 1st & 2nd Class Certs. | <input type="checkbox"/> C & G Telecommunication                |
| <input type="checkbox"/> City & Guilds Radio, TV Electronics Mechanics | <input type="checkbox"/> C & G Electrical Engineering Practise      |   |
|  | <input type="checkbox"/> C & G LI Installations and Wiring          |   |

To B.I.E.T. BPW 05 Aldermaston Court, Reading RG7 4PF QK **BPW 05**

NAME (Block Capitals Please)

ADDRESS

Other subjects


Accredited by C.A.C.C.

Member of A.B.C.C.

**BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY**

## Why pay more - look at our Fantastic Bargain Offer!

### THE AVON AUDIO SYSTEM

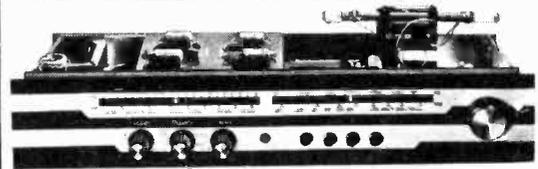

The uncabineted system is ideal as an economical replacement for an outdated chassis. Stereo Amplifier for Stereo/Mono record reproduction. Tuner with medium, long and short wavebands provides Worldwide coverage, even the weakest continental stations can be received with superb clarity. Push button band selection, 10 watts total output, Frequency response 25-18000 Hz.

LATEST BSR STEREO/MONO RECORD CHANGER plays all Mono or Stereo records. Manual or automatic play.

TWIN ELLIPTICAL SPEAKERS These low impedance, permanent magnet units have been specially selected to provide the fullest range of audio reproduction.



EASY TO INSTALL—NO TECHNICAL KNOWLEDGE REQUIRED. List Price £45.74. OUR PRICE £35.00. Credit Terms £3.50 deposit plus £2 Post & Packing followed by 9 payments of £4.10 (Total Credit Terms £44.40) Don't miss this bargain.

SEND £5.50 TODAY

ALL EQUIPMENT COVERED BY OUR 12 MONTHS FULL GUARANTEE

**CALLERS WELCOME**

**LEWIS radio**

PW 8/74

100 Chase Side, Southgate,  
London N14 5PL  
Tel: 01-886 3733/9666

# G. T. ELECTRONICS

NOW AT 267 AND 270 ACTON LANE,  
LONDON W4 5DG

Now open our new components shop. These premises are very much larger and will enable us to have greater stocks than we already have. Having all the components under one roof will now guarantee you speedier service on the counter, and on the mail order side. We have an enormous range of components to choose from. If you are having problems getting your components then come along. We are open from 9.30 am. through till 6.00 pm. Monday to Saturday. The nearest underground is Chiswick Park, and there are no parking restrictions.

## SEMICONDUCTORS

AC107	35p	BCY70	22p	MPSA06	40p	TIP34A	£1.55	2N1308	25p
AC125	25p	BCY71	22p	MPSA16	35p	TIP35A	£2.25	2N1309	25p
AC126	25p	BCY72	22p	MPSA56	35p	TIP36A	£2.85	2N1613	25p
AC127	27p	BD121	75p	MPSU06	75p	TIP41A	75p	2N1711	25p
AC128	25p	BD124	75p	MPSU56	70p	TIP42A	80p	2N2147	70p
AC176	27p	BD124	75p	NK1135	35p	TIP29B	50p	2N2160	65p
ACY17	25p	BD131	75p	NK1222	25p	TIP30B	60p	2N2217	25p
ACY18	30p	BD132	75p	NK1401	85p	TIP31B	70p	2N2218	25p
ACY19	30p	BD153	75p	NK1404	80p	TIP32B	82p	2N2219	25p
ACY20	25p	BD156	75p	NK1773	30p	TIP33B	£1.12	2N2222	20p
ACY39	35p	BDY11	£1.40	NK1774	25p	TIP35B	£2.81	2N2306	70p
ACZ1	30p	BDY17	£1.60	OA51	20p	TIP36B	£3.44	2N2640	50p
AD140	60p	BDY19	£1.95	OA10	20p	TIP41B	83p	2N2846	£1.50
AD149	65p	BF152	20p	OA47	10p	TIP42B	80p	2N2904	25p
AD161	40p	BF194	14p	OA70	12p	TIP29C	70p	2N2905	25p
AD182	40p	BF195	15p	OA79	12p	TIP30C	78p	2N2906	25p
ADZ11	£1.80	BFK29	30p	OA81	10p	TIP31C	85p	2N2927	12p
AF114	25p	BFK84	30p	OA80	10p	TIP32C	£1.45	2N2926	12p
AF115	25p	BFK85	30p	OA81	10p	TIP33C	£1.30	2N3055	25p
AF116	25p	BFK86	30p	OA200	10p	TIP34C	£1.40	2N3054	65p
AF117	25p	BFK88	30p	OA202	10p	TIP35C	£2.10	2N3055	25p
AF118	60p	BFY10	35p	OA210	35p	TIP36C	£4.10	2N3232	70p
AF172	30p	BFY44	50p	OA211	36p	TIP37C	95p	2N3252	95p
AFY28	30p	BFY50	25p	OC16	90p	TIP42C	£1.10	2N3702	14p
ASZ21	60p	BFY51	25p	OC19	90p	TIS50	40p	2N3703	12p
BA102	33p	BFY52	25p	OC22	55p	TI307	15p	2N3707	12p
BA112	50p	BFY53	25p	OC26	65p	ZT X300	15p	2N3705	12p
BA114	16p	BFY90	66p	OC28	65p	ZT X500	16p	2N3706	12p
BA156	15p	BSW63	65p	OC36	60p	ZT X501	20p	2N3707	12p
BC107	12p	BSW68	80p	OC38	65p	ZT X504	50p	2N3708	12p
BC108	12p	BSY95A	12p	OC39	65p	ZT X550	12p	2N3709	12p
BC109	11p	BSY95B	10p	OC44	20p	IN659	50p	2N3712	£2.70
BC147	12p	CA26	40p	OC45	20p	IN914	1p	2N3773	£2.95
BC148	12p	BY100	15p	OC70	15p	IN916	1p	2N3819	35p
BC149	12p	BY126	20p	OC71	17p	IN4001	1p	2N3820	55p
BC153	15p	BY127	20p	OC72	20p	IN4002	1p	2N3826	85p
BC157	14p	BY164	85p	OC75	25p	IN4003	3p	2N3904	22p
BC158	15p	IS100	15p	OC76	25p	IN4004	10p	2N3905	25p
BC158	15p	IS103	12p	OC77	40p	IN4005	12p	2N4058	12p
BC169C	14p	MJ340	55p	OC81	25p	IN4006	15p	2N4059	12p
BC182	14p	MJ481	95p	OC83	25p	IN4007	15p	2N4060	12p
CI183	14p	MJ2801	£1.25	OC84	25p	IN4148	7p	2N4061	12p
CI184	14p	MJ2901	£2.20	OC139	30p	IN696	2p	2N4126	17p
CI212	14p	MJ340	50p	OC140	30p	IN697	2p	2N4286	15p
CI213	14p	MJE370	75p	OC170	25p	2N688	25p	2N4287	15p
CI214	14p	MJE370	75p	OC171	30p	2N706	12p	2N4288	15p
BC000	12p	MJE520	65p	OC200	50p	2N706A	15p	2N4289	15p
BC000	12p	MJE2955	65p	OC201	60p	2N708	15p	2N4290	15p
BCY30	40p	MJE3055	85p	OC202	75p	2N930	25p	2N4444	20p
BCY31	50p	MME1712	43p	TIP29A	45p	2N932	25p	2N4920	35p
BCY32	95p	MME1713	43p	TIP30A	58p	2N1302	15p	2N4920	60p
BCY33	45p	MME1714	43p	TIP31A	62p	2N1303	15p	2N5191	96p
BCY34	60p	MME1712	43p	MPE104	25p	2N1304	25p	2N5194	£1.10
BCY38	65p	MPE102	45p	(2N5458)	35p	2N1305	25p	40360	50p
BCY39	£1.00	MPE103	45p	TIP32A	74p	2N1306	25p	40361	50p
BCY55	£1.00	MPE104	35p	TIP33A	£1.00	2N1307	25p	40362	50p

QTY. DISCOUNTS: 12+ less 10%; 25+ less 15%; 100+ 20%.

## DIGITAL INTEGRAL CIRCUITS

SN7400	20p	SN7430	20p	SN7474	40p	SN74110	80p	SN74167	£6.25
SN7401	20p	SN7432	42p	SN7475	55p	SN74118	£1.00	SN74170	£4.10
SN7402	20p	SN7433	70p	SN7476	45p	SN74119	£1.90	SN74174	£2.00
SN7403	20p	SN7437	65p	SN7480	80p	SN74121	65p	SN74175	£1.35
SN7404	20p	SN7438	85p	SN7481	£1.25	SN74122	£1.35	SN74176	£1.60
SN7405	20p	SN7440	20p	SN7482	70p	SN74123	£2.70	SN74177	£1.60
SN7406	30p	SN7441	75p	SN7483	70p	SN74124	£1.00	SN74180	£1.55
SN7407	30p	SN7442	75p	SN7484	90p	SN74145	£1.50	SN74181	£7.00
SN7408	20p	SN7443	75p	SN7485	45p	SN74150	£3.35	SN74182	£2.00
SN7409	45p	SN7443	£1.00	SN7490	75p	SN74151	£1.10	SN74184	£2.45
SN7410	20p	SN7445	£2.00	SN7491A	75p	SN74153	£1.35	SN74185A	£2.40
SN7411	23p	SN7446	£2.00			SN74154	£2.00	SN74186	£2.40
SN7412	42p	SN7447	£1.75	SN7492	75p	SN74155	£1.55	SN74191	£1.95
SN7413	30p	SN7448	£1.75	SN7493	80p	SN74157	£1.80	SN74192	£2.00
SN7416	30p	SN7450	20p	SN7494	80p	SN74160	£2.00	SN74193	£2.00
SN7417	30p	SN7451	20p	SN7495	80p	SN74161	£2.00	SN74194	£2.50
SN7420	20p	SN7453	20p	SN7496	£1.00	SN74162	£2.00	SN74195	£1.85
SN7422	40p	SN7454	20p	SN7497	£2.25	SN74163	£2.00	SN74196	£1.50
SN7423	40p	SN7460	20p	SN74100	£2.50	SN74163	£2.00	SN74196	£1.50
SN7425	40p	SN7470	30p	SN74104	£1.45	SN74164	£2.75	SN74197	£1.50
SN7427	42p	SN7472	30p	SN74105	£1.40	SN74165	£2.00	SN74198	£4.60
SN7428	50p	SN7473	40p	SN74107	54p	SN74166	£4.00	SN74199	£4.60

## S.C.R.s

CRS1/05	40p
CRS1/10	50p
CRS1/20	60p
CRS1/40	80p
CRS1/60	90p
CRS1/10	£2.40
CRS1/20	£2.40
CRS1/40	£2.40
CRS1/60	£2.40
CRS1/100	£1.00
CRS16/200	90p
CRS16/600	£1.60
C106S	45p
C106D	70p
40669	90p
TIC44	35p
2N4444	90p
BT10/500A	90p

## BRIDGE RECTIFIERS

W021A 200V	38p
BY1641-4A 200V	57p
MDA952/2	57p
6A 100V	80p

## ZENER DIODES

BZY88. Series	
400mW 3-3V	
33V. 5% tolerance	15p
1.5W range	25p
10W range	45p

## L.E.D.

TL1209	28p
HP5082	28p
MA2082R	25p
L.D.R.	
ORP12	25p
NE555 timer	90p

## ALUMINIUM BOXES

L	W	H	Price
AB7	2 1/2	5 1/2	1 1/2in 50p
AB8	4	4	4 1/2in 30p
AB9	4	4	2 1/2in 50p
AB10	4	4	2 1/2in 50p
AB11	4	4	2 1/2in 60p
AB12	3	2	1 1/2in 44p
AB14	7	5	2 1/2in 80p
AB15	8	6	3in £1.00
AB16	10	7	3in £1.00
AB17	10	4 1/2	3in £1.20
AB18	12	5	3in £1.20
AB19	12	8	3in £1.60

## ALUMINIUM BOXES WITH SLOPING TOP PANEL

AB20	8" Length x 7" Width x 3" Height at back with P.K. Screws	£2.00
AB21	As above but 10" long	£2.20
AB22	As above but 12" long	£2.40

## V 41 Vu meter

The V41 is calibrated -20 to +3 and 0-100%, making it suitable for use as a recording level meter or as a power output indicator. Sensitivity: 130 µA. Internal resistance: 600 ohms. Dimensions: 40 x 40 x 29mm.

## V.A.T.

Unless otherwise stated all prices are EXCLUSIVE of V.A.T. Please add 10% to all orders. Carriage: orders under £5 + 20p. Over £5 post free.

## TRIACS

TXL228B 8A 400V 95p	
SC40D	£1.40
SC40E	£1.85
SC45D	£1.70
SC45E	£2.10
SC50D	£2.42
SC50E	£2.40
DIAC	25p

## LINEAR I.C.s

LM309K 5V. I.A.	
Voltage Reg	£2.10
LM723C 2-3Vt.	
150mA Op Amp	£1.95
MFC4000 250mW	
Audio	60p
TBA800 5Watt	
Audio	£1.50
709C Op Amp	
D.I.L./T099	45p
741C Op Amp	
814 D.I.L./T099	55p
748C Op Amp	
D.I.L.	75p
747C Dual Op Amp	£1.20
ZN414 Radio I.C.	£1.25

## TAD100 Radio I.C. Inc. Filter

CA3014	£1.55
CA3018	£1.90
CA3028	£1.20
CA3036	£1.50
CA3046	95p
CA3048	£2.35
CA3075	£1.60
CA3090Q	£4.85
MC1303L	£1.20
SN7023 6V Audio with circuit	£1.75

## ★ SPECIAL OFFERS ★

**MINIATURE MAINS TRANSFORMER**  
BRI. 240V. SEC. 12V. 100MA Manuf.: Hinchley  
Size: 36 x 45 x 40mm. F.C. 53mm.  
Price 1-65p. 100-60p ea. 1,000-50p ea. 10,000-40p ea.

**3 CORE PVC INSULATED MAINS CABLE, GREY ML650. 3 x 7/0-2mm**  
Price 100m-£4.50, 1000m-£35, 10,000m-£330, 0-47mfd. 50V MYLAR FILM CAPACITOR. Size 1" x 0.35" x 0.65" P.C. Mount. Price 100-60p ea. 1000-5p ea. 10,000-4.5p ea.

**240V. A.C. SOLENOID.** Reversible operation; twin coil. Size approx. 2 1/2 x 1 1/2 in. 90p ea.  
30 unmarked OC71 transistors £1.00  
25 unmarked 250mW Zenerdiode. 4-7V. 5-1V 6-2V. 7-5. 9-1V. 10V. Measured and tested. £1.00

Please state voltage required.  
50 GE Diode OA47 equivalent. £1.00  
**TRANSFORMER:** DOUGLAS PRI. 0, 115, 200, 220, 240 SEC. 25-0-25-0-8V. 2 1/2A

# PE SCORPIO Mk 2 ignition system kit new from ELECTRO SPARES

- \* 6 OR 12 VOLT
- \* + VE AND - VE GROUND

Here's the new, improved version of the original PE Scorpio Electronic Ignition System—with a big plus over all the other kits—the PE Scorpio Kit is designed for both positive and negative ground automotive electrical systems. Not just +ve ground. Nor just -ve ground. But both! So if you change cars, you can be almost certain that you can change over your PE Scorpio Mk. 2 as well. Containing all the components you need, this Electro Spares PE Scorpio Mk. 2 Kit is simply built, using our easy-to-follow instructions. Each component is a branded unit by a reputable manufacturer and carries the manufacturer's guarantee. Ready drilled for fast assembly. Quickly fitted to any car. When your PE Scorpio Mk. 2 is installed, you instantly benefit from all these PE Scorpio Mk. 2 advantages.

- ★ Easier starting from cold
- ★ Firing even with wet or oiled-up plugs
- ★ Smoother running at high speed
- ★ Fuel saving
- ★ More power from your engine
- ★ Longer spark plug life
- ★ No more contact-breaker burn

Electro Spares prices:

De luxe Kit only £11.50 inc. VAT and p & p.  
Ready Made Unit £14.75 inc. VAT and p & p.  
State 6V or 12V system.

Send SAE now for details and free list.

## FM VARICAP STEREO TUNER

As featured in the May 1973 issue of 'Practical Electronics'. Superb Hi-Fi tuner Kit now available from Electro Spares. Including cabinet and all components — pre-set Mullard modules for R.F. and I.F. circuits. Motorola I.C. Phase Lock Loop Decoder for perfect stereo reception. No alignment needed. Guaranteed first time results — or send it back, and we'll return it in perfect order (for a nominal handling charge). Electro Spares price only £28.50 inc. VAT and p & p.

## 'GEMINI' STEREO AMPLIFIER

A superb unit with a guaranteed output of 30 watts RMS per channel into 8 ohms. Full power THD is a mere 0.02%, and frequency response is —3 dB from 20 Hz to 100 kHz into 8 or 15 ohms. Electro Spares have already sold 100s and 100s of these Kits. Get yours now! Depending on your choice of certain components, the price can vary from £50 to £60 inc. VAT and p & p.

- ★ All components as specified by original authors, and sold separately if you wish.
- ★ Full constructional data book with specification graphs, fault finding guides, etc. 55p plus 4p postage.
- ★ Price List only. Please send S.A.E. (preferably 9 x 4 minimum) for full details.

# ELECTRO SPARES



The Component Centre of the North  
288 ECCLESALL RD., SHEFFIELD S11 8PE (C)  
Tel: Sheffield (0742) 668888

**THE FOLLOWING ITEMS ARE NEW. TUNING COILS** S.W. type size 4½ x 2½ 3 for 85p. **HEAD & MIKE SETS** for use with 19 Set low res. M.C. type, Hand mike, adjustable headband with ear pads £2. **DIODES 100 PIV** at 3 amps wire ended 4 for 60p. **C.R.T.** type 7BP7A 7" flat face. 6-3 heater, Blue/Yell phosfor, okay for slow scan T.V. with base connections £2. **BLOWER MOTORS** for use on 6 to 28V DC double ended type size overhaul 6 x 3½", outlets 1½ x 1½" boxed £2-55. **TRIMMERS** Air spaced ceramic base 20pf 10 for 65p. 100 for £4-40. **METER UNIT X** pioneer ind for use with 115Rx as dual 115 Ua movements £1-79. **CONTROL UNIT** with valves 6BA6, 6AS6, 12AU7, pot core 1½ x 1" .1uf 1% conds, relay etc £1-15. **SILICON DIODES** Ferranti type ZS78 800 PIV 750 Ma 15 for £1-10. **INSULATED TERMINALS** slim style will take 4mm plug in Red, Blk, Blue, Gr, Yell, Wht, Grey, Brown 4 for 60p. **COAX CABLE** grey sheath 75 ohm ½" dia 15 meters for £1-20. **COAXIAL LEADS BNC UHF, N** type etc list on request.

**THE FOLLOWING ARE EX EQUIPMENT. EXTRACTOR FANS** 8" dia with grill 115v 50c/s 3000 RPM 2 phase motor heavy duty unit £3-90. **SCOPE EHT CONDS** .5uf 1 Kv, .25uf 1-5 Kv, .1uf 2-5 Kv all 25p ea. **DIODES** type ZR22 200 PIV 8 amps 4 for 75p. **CRT** type VCR138 3-5" dia, green screen, supplied with base, mu met shield & front mount req 1 to 2Kv EHT ideal for scope use with base conn. £4-40. **WAVEMETER ASS.** absorption type range 420 to 460 Mc/s approx with Det, with dial & knob not cal in freq 11 x 2½" £2. **METERS** 270' scale 1 Ma FSD scale 0 to 20 with 100-0-100 Ua in same case size 3½ x 3½ £3-38. **HIGH VOLTAGE DIVIDER** for use with scope ratio 10 & 100.1 up to 20Kv Wk £3-20. **VIDICON C.C.T.V.** camera tubes E.E. type P862 with data sheet 6-3 95 Ma heater grade A & B £9-50 A. £6-50 B. **CRYSTAL OVEN** with 12 type Hc6/u holders can be removed. 76p. **PLUGS & SKS** Belling Lee type with cable cover & clamp 25 way 55p, 18 way 35p, 8 way 25p, 4 way 20p.

Above prices include Postage & V.A.T. S.A.E. for list or inquiry.

## A. H. SUPPLIES

57 MAIN ROAD, SHEFFIELD S9 5HL. Tel: 444278 (0742)



## for fast, easy reliable soldering

Ersin Multicore Solder contains 5 cores of non-corrosive flux. Instantly cleaning heavily oxidised surfaces. No extra flux is required.

## EASY-TO-USE DISPENSERS



- Size 5  
Savbit alloy  
18 swg. 30p  
(illustrated).
- Size 19A  
60/40 alloy  
18 swg. 30p
- Size 15  
60/40 alloy  
22 swg. 34p


## IDEAL FOR HOME CONSTRUCTORS

Size 1 cartons in 40/60, 60/40  
and Savbit alloys  
in 7 gauges 46p



Size 12 Reel  
for Service  
Engineers and  
Electricians.  
18 swg  
Savbit alloy. £1-46

## BIB WIRE STRIPPER AND CUTTER

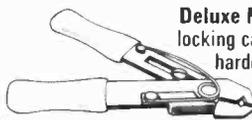

Deluxe Model 9 Automatic opening spring, locking catch, plastic-covered handles. Case hardened and precision ground. Adjusts to most wire sizes. Cuts and strips flex, splits plastic twin flex. 75p

Prices shown are recommended retail, excluding V.A.T.  
From Electrical and Hardware Shops. If unobtainable, send 10p p&p direct to  
Bib Hi-Fi Accessories Limited, Hemel Hempstead, Herts HP2 7EP

## RECORD PLAYBACK HEADS (TRUVOX)

Individual prices of these are:  
2 track record playback heads 50p each.  
4 track record playback heads 75p each.  
Erase heads are also available separately—  
2 track 38p—4 track 55p.

## NEED A SPECIAL SWITCH

Double Leaf Contact. Very slight pressure closes both contacts. 8p each, 10 for 60p. Plastic pushrod suitable for operating. 6p each, 10 for 54p.



## I R.P.M. MOTOR+GEAR BOX

Made by the famous Chamberlain & Hookham Ltd. These could be made to drive clock or similar. Really robust reliable unit. Price £1.10 each.

## AUTO-ELECTRICAL CAR AERIAL

With dashboard control switch—fully extendable to 40in or fully retractable. Suitable for 12V positive or negative earth. Supplied complete with fitting instructions and ready wired dashboard switch. £6.85 plus 25p post and insurance.



## MAINS TRANSISTOR POWER PACK

Designed to operate transistor sets and amplifiers. Adjustable output 6v., 9v., 12 volts for up to 500mA (class B working). Takes the place of any of the following batteries: PP1, PP3, PP4, PP6, PP7, PP9 and others. Kit comprises: mains transformer rectifier, smoothing and load resistor, condensers and instructions. Real snip at only £1.10, plus 20p postage.

## MINIATURE WAFER SWITCHES

2 pole, 2 way—4 pole, 2 way—3 pole, 3 way—4 pole, 3 way—2 pole, 4 way—3 pole, 4 way—2 pole, 6 way—1 pole, 12 way. All at 25p each.



## MULTI-SPEED MOTOR.

Six speeds are available 500, 850 and 1,100 r.p.m. and 8,000, 12,000 and 15,500 r.p.m. Shaft is 1/8 in. diameter and approximately 1 in. long. 230/240v. Its speed may be further controlled with the use of our Thyristor controller. Very cheap on powerful and useful motor size approx. 2 in. dia. x 5 in. long. Price 97p plus 25p postage and insurance.



## SLIDE SWITCHES


Slide Switch, 2-pole changeover panel mounting by two 6B.A. screws. Size approx. 1in x 1in rated 250V lamp. 8p each, 10 for 73p. Ditto as above but for printed circuit 6p each 10 for 63p. Sub Miniature Slide Switch. DPDT 19mm (1in approx.) between fixing centres. 20p each or 10 for £1.90. SP Change over spring return 250V 1 amp. 11p.


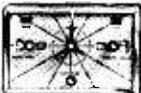
## 15A ELECTRICAL PROGRAMMER


Learn in your sleep! Have radio playing and kettle boiling as you awake—switch on lights to ward off intruders—have a warm house to come home to.

All these and many other things you can do if you invest in an electrical programmer. Clock by famous maker with 15 amp. on/off switch. Switch-on time can be set anywhere to stay on up to 6 hours. Independent 60 minute memory jogger. A beautiful unit. Price £2.15 + 20p p. & p. or with glass front, chrome bezel, 83p extra.


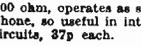
## BALANCED ARMATURE UNIT

500 ohm, operates as speaker or microphone, so useful in intercom or similar circuits, 37p each.



## 12 VOLT 15 AMP. POWER PACK

This comprises double-wound 230/240V mains transformer with full wave rectifier and 2000 mF smoothing. Price £2.20 plus 20p post & packing.

Heavy Duty Mains Power Pack. Output voltage adjustable from 15-40V in steps—maximum load 250W—that is from 6 amp at 40V to 15 amp at 15V. This really is a high power heavy duty unit with dozens of workshop uses. Output voltage adjustment is very quick—simply interchange push on leads. Silicon rectifiers and smoothing by 3,000mF. Price £8.33 plus 65p post.




## RESETTABLE FUSE

How long does it take you to renew a fuse? Time yourself when next one blows. Then reckoning your time at £1 per hour see how quickly our resettable fuse (auto circuit breaker) will pay for itself. Price only £1.10 each or £12 per dozen, specify 5, 10 or 15 amp—simply fit in place of switch.


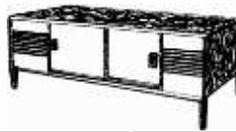
## STEREO RADIO CABINET

Long, Low and Modern. Teak veneered with sliding front and tapered legs. Speaker spaces each end. Size approx. 4ft. 2in x 13in x 15in. Probably cost over £20 to make. Our Price £8.10 post.



## THIS MONTH'S SNIP ULTRA MODERN RECORD CHANGER.

Famous BSR deck with stereo cart-ridge. £6.95 + £1.00 post.



## HORSTMANN 24-HOUR TIME SWITCH

With 6 position programmer. When fitted to hot water systems this could programme as follows:—

Programme	Hot Water	Central Heating
0	Off	Off
1	Twice Daily	Off
2	All Day	Off
3	Twice Daily	Twice Daily
4	All Day	All Day
5	Continuously	Continuously



Suitable, of course, to programme other than central heating and hot water, for instance, programme upstairs and downstairs electric heating or heating and cooling or taped music and radio. In fact there is no limit to the versatility of this Programmer. Mains operated. Size 3in. x 3in. x 2in. deep. Price £3.85 as illustrated but less case.

## PORTABLE RADIO CASE DE-LUXE

A similar size to the above but a more expensive design. Used with the Good Companion de-luxe model. £2.20 plus 50p post and insurance.




## KETTLE ELEMENTS

Made by the famous A.E.I. Co. Complete with washers and combined fixing nuts and plug shroud. Normal 2 round pin and flat pin earth connection and overload reset push button. 2 Models—1 1/2in (approx.) suitable for Swan and other similar models—1 1/4in (approx.) suitable for G.E.C., Hotpoint, etc. All quick boil 2 1/2kW elements at 240V. Price £1.88.

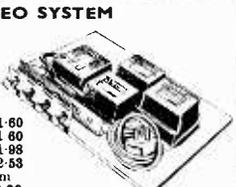
## MULLARD UNILEX STEREO SYSTEM

There is no doubt that it is a good system, we believe that for the money it is without comparison. We demonstrate gladly at our Tanworth Road depot. Prices of the individual items for this—  
1 Unilex Amplifier Ref. EP.9000 £1.60  
1 Unilex Amplifier Ref. EP.9000 £1.60  
1 Unilex Pre-Amp Ref. EP.9001 £1.88  
1 Unilex Power Unit Ref. EP.9002 £2.53  
1 Control panel kit with spun aluminium face knobs £3.80  
Or the complete outfit—£11.30 post paid.  
Pair of 15 ohm speakers made by F.M.I. are also available if required price £3.30 the pair. No extra postage if ordered with the above, otherwise add 25p.


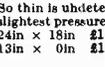
## SWITCH TRIGGER MATS

So thin is undetectable under carpet but will switch on with slightest pressure. For burglar alarms, shop doors, etc.  
24in x 18in £1.69  
13in x 0in £1.21




## HORSTMANN "TIME AND SET" SWITCH

(A 30 amp Switch). Just the thing if you want to come home to a warm house without it costing you a fortune. You can delay the switch on time of your electric fires, etc., up to 14 hours from setting time or you can use the switch to give a boost on period of up to 3 hours. Equally suitable to control processing.

Two models 15 amp £1.98, 30 amp £2.58. P. & P. 25p each

**SMOKE WILL KILL—GAS WILL KILL—FIRE WILL KILL**  
But, if you install SAGA (our smoke and gas alarm) your family will have the latest electronic protection against these killers.  
Saga uses a fantastic electronic sensor which "smells" smoke and gas and sounds the alarm immediately. In a neat case measuring approx. 3" x 3 1/2" x 2 1/2" it has its own internal alarm, also a connector for additional bells. You just plug it in to the mains and hang it near the ceiling. Saga uses so little electricity that it will hardly move the meter, leave it on always to give night and day protection. £8.99 plus 30p post.

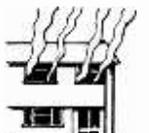

**OUR 1974 CATALOGUE LISTING HUNDREDS OF BARGAINS, NOW AVAILABLE. PRICE 30p POST PAID.**


## CENTRIFUGAL BLOWER

Miniature mains driven blower centrifugal type blower unit by Woods. Powerful but specially built for quiet running—driven by cushioned induction motor with specially built low noise bearings. Overall size 4 1/2" x 4 1/2" x 4". When mounted by flange, air is blown into the equipment but to suck air out, mount it from centre using clamp. Ideal for cooling electrical equipment or fitting into a cooker hood, film drying cabinet or for removing flux smoke when soldering etc., etc. A real bargain at £2.05.


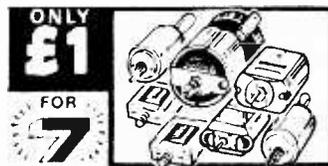
## UNILEX MULLARD 4 WATT HI-FI AMPLIFIER FOR ONLY £1.60

Sensational "once in a lifetime offer" because Mullard over-produced—definitely not repeatable once our stocks (now over half sold) are cleared. Hi-Fi 4 transistor amplifier complete in case ready to use. Batt., car or mains operated—free, range 50Hz-15kHz—distortion better than 2%. Comes complete with guarantee and data FREE to purchasers. Great handbook published by Mullard "tells all you need to know" to build your own stereo. Complete Unilex Stereo System £11.30, pair of speakers for same £3.80.



## ONLY £1 FOR 7 ELECTRIC MOTORS

7 powerful battery motors as used in racing cars and power models. Output and types vary to make them suitable for hundreds of different projects—tools, toys, models, etc. All brand new reversible and for 10 to 12v. Bats., wiring diagrams included. Post and VAT 80p.

**FREE** Details of how to make miniature power station.

## FERRITE RODS

For aeriols, etc. The following types are in stock  
Dia. 3", 4" long 15p, 5" long 15p. Dia. 5/16", 5" long 20p, 6" long 25p, 8" long 30p. Dia. 3/8", 4" long 20p, 5" long 25p, 6" long 30p, 8" long 40p. Dia. 1/2", 6" long 35p; Ferrite Slab 3" long x 1" x 1/8th—20p

## MINIATURE SEALED RELAY

American made. Our Ref. No. REL. A1. Measures only 1/2" wide x 1" thick and 1" high and it's a double change over, we don't know the contact rating but estimate this at 3/5 amps. The coil resistance is 600 ohms, and 9-12 volt will close it. Ideal for models and miniaturised equipment. It's a plug in relay but we supply complete with base. Price 33p including base.



## TELESCOPIC AERIAL

For portable, car radio or transmitter. Chrome plated—six sections, extends from 7in to 47in. Hole in bottom for 6BA screw  
42p. KNUCKLED MODEL FOR F.M. 55p



## TREASURE TRACER

Complete Kit (except wooden battens) to make the metal detector as the circuit in Practical Wireless, August issue. £3.30 plus 20p post and insurance.



## MIDGET TWO GANGS

Tuning condenser as fitted to many Japanese and Hong Kong radios—probably 200pf each section with 1/2" spindle with terminal-less trimmers. Price 38p. With trimmers 50p.



## NUMICATOR TUBES

For digital instruments, counters, timers, clocks, etc. Hi-vac XN.3 Price 99p each, 10 for £9.



## MAINS OPERATED SOLENOIDS

Model 2—small but powerful line pull—approx size 1 1/2 x 1 1/2 x 1 1/2in. 66p.  
Model 4001—1/2in. pull. Size 2 1/2 x 2 x 1 1/2in. 88p.  
Model TT1—1 1/2in. pull. Size 3 x 2 1/2 x 2in £1.98 plus 20p post and insurance



## RADIO STETHOSCOPE

Easiest way to fault find—traces signal from aerial to speaker—when signal stops you've found the fault. Use it on Radio, TV amplifier, anything—complete kit comprises two special transistors and all parts including probe tube and crystal earpiece. £2.20, twin stethoscope instead of earpiece 88p extra—post and ins. 20p.



**TERMS:—**  
ADD 10% V.A.T.  
Send postage where quoted—other items, post free if order for these items is £6.00, otherwise add 20p.

**J. BULL (ELECTRICAL) LTD.**  
(Dept. PW), 102/3 Tamworth Road,  
CROYDON CRO IXX

# The largest selection

## EX COMPUTER BOARDS

Packed with transistors, diodes, capacitors and resistors—COMPONENT VALUE £1.50. 3 for ONLY 55p + p & p 30p

**SPECIAL ONE.** As above PLUS Power Transistors ONLY 55p each + p & p 15p

## STABILISED POWER MODULES

Complete with circuit diagrams, etc. 99p each + p & p 15p

**PAXOLINE BOARDS** 7½" x 9" approx. 4 for 30p + p & p 20p.

## FIBRE-GLASS PRINTED CIRCUIT BOARDS

16½" x 4" approx. 2 for 55p

## DECON-DALO 33PC Marker

Etch resistant printed circuit marker pen 80p each

## VEROBOARDS

Packs containing approx. 50sq. ins. various sizes, all 1 matric 55p

## REPANCO CHOKES & COILS

RF Chokes

CH1. 2.5mH 25p CH2. 5.0mH 25p  
CH3. 7.5mH 25p CH4. 10mH 25p  
CH5. 1.5mH 25p

COILS

DRX1 Crystal set 81p DRR2 Dual range 45p

## COIL FORMERS & CORES

NORMAN ½" Cores & Formers 7p  
½" Cores & Formers 8p

## SWITCHES

DP/DT Toggle 25p 8P/BT Toggle 18p

## FUSES

1½" and 20mm. 100mA, 200mA, 250mA, 500mA, 1A, 1.5A, 2A

QUICK-BLOW 4p ea. ANTI-BURGE 5p ea.

## EARPHONES

Crystal 2.5mm plug 33p

Crystal 3.5mm plug 33p

8 ohms 2.5mm plug 22p

8 ohms 3.5mm plug 22p

## DYNAMIC MICROPHONES

B1223. 200 ohms plus on/off switch and 2.5mm and 3.5mm plugs £1.80

## 3-WAY STEREO HEADPHONE JUNCTION BOX

H1012 £1.87

## 2-WAY CROSSOVER NETWORK

K4007. 80 ohms Imp. Insertion loss 3dB £1.21

## CAR STEREO SPEAKERS

(Angled) £3.85 per pair.

## BI-PAK

CATALOGUE AND LISTS

Send S.A.E. and 10p.

## INSTRUMENT CASES



(Black Vinyl covered)

No.	Length	Width	Height	Price
BV1	8"	4½"	2"	90p
BV2	11"	6"	3"	£1.20

## ALUMINIUM BOXES

BA1	5½"	4"	1½"	42p
BA2	4"	4"	1½"	41p
BA3	4"	3½"	1½"	41p
BA4	5½"	4"	1½"	47p
BA5	4"	2½"	2"	41p
BA6	3"	2"	1"	34p
BA7	7"	5"	3"	86p
BA8	8"	6"	3"	84p
BA9	6"	4"	2"	64p

## VISIT OUR COMPONENT SHOP

18 BALDOCK ST., WARE, Herts. (A10)

Open Mon.-Sat. 9-5.30 p.m. Tel. 61593

## BIB HI-FI ACCESSORIES

### De Luxe Groov-Kleen

Model 42 £1.84

Chrome Finish Model 60 £1.50



Ref. 36A. Record/Stylus Cleaning Kit 28p

Ref. 43. Record Care Kit £2.35

Ref. 31. Cassette Head Cleaner 54p

Ref. 32. Tape editing Kit £1.54

Model 9. Wire Stripper/Cutter 83p

Ref. P. Hi-Fi Cleaner 31p

Ref. 32A. Stylus Balance £1.38

Ref. J. Tape Head Cleaning Kit 61p

Ref. 34. Cassette Case £1.27

Ref. 66. Hi-Fi Stereo Hints & Tips 32p

## ANTEX SOLDERING IRONS

X25. 25 watt £1.93

CCN 240. 15 watt £2.15

Model G. 18 watt £2.15

8K2. Soldering Kit £2.88

STANDS: 8T1 £1.21. 8T2 77p

8OLDER: 188WG Multigrade 7oz 82p

228WG 7oz 82p. 188WG 22ft 28p

228WG Tube 22p

## ANTEX BITS and ELEMENTS

Bits No.

102 For model CN240 3/32" 38p

104 For model CN240 3/16" 38p

1100 For model CCN240 3/32" 38p

1101 For model CCN240 3/8" 38p

1102 For model CCN240 1" 38p

1020 For model G240 3/32" 38p

1021 For model G240 1/8" 38p

1022 For model G240 3/16" 38p

50 For model X25 3/32" 38p

51 For model X25 1/8" 38p

52 For model X25 3/16" 38p

## ELEMENTS

ECN 240 £1.16 ECCN 240 £1.32

EG 240 £1.16 EX 25 £1.16

## ANTEX HEAT SINKS 10p

V.A.T. included in all prices. Please add 10p P. & P. (U.K. only). Overseas orders—please add extra for postage.

## NEW COMPONENT PAK BARGAINS

Pack No. Qty. Description Price

C1 250 Resistors mixed values approx. count by weight 0.55

C2 200 Capacitors mixed values approx. count by weight 0.55

C3 50 Precision Resistors 1%, 2%, mixed values 0.55

C4 75 ¼th W Resistors mixed preferred values 0.55

C5 5 Pieces assorted Ferrite Rods 0.05

C6 2 Tuning Gangs, MW/LW VHF 0.55

C7 1 Pack Wire 50 metres assorted colours 0.55

C 8 10 Reed Switches 0.55

C 9 3 Micro Switches 0.55

C10 15 Assorted Pots & Pre-Sets 0.55

C11 5 Jack Sockets 3 x 3-5m 2 x Standard Switch Type 0.55

C12 40 Paper Condensers preferred types mixed values 0.55

C13 20 Electrolytics Trans. types 0.55

C14 1 Pack assorted Hardware—Nuts/Bolts, Grommets etc.—0.55

C15 4 Mains Slide Switches 0.55

C16 20 Assorted Tag strips & Panels 0.55

C17 10 Assorted Control Knobs 0.55

C18 4 Rotary Wave Change Switches 0.55

C19 3 Relays 6—24V Operating 0.55

C20 4 Sheets Copper Laminates approx. 10" x 7" 0.55

## PLUGS AND SOCKETS

### SOCKETS

PS 35 DIN 2 Pin (Speaker) 0.06

PS 36 DIN 3 Pin 0.10

PS 37 DIN 5 Pin 180° 0.10

PS 38 DIN 5 Pin 240° 0.10

PS 39 Jack 2.5mm Switched 0.09

PS 40 Jack 3.5mm Switched 0.10

PS 41 Jack 1" Switched 0.17

PS 42 Jack Stereo Switched 0.28

PS 43 Phono Single 0.06

PS 44 Phono Double 0.10

PS 45 Car Aerial 0.09

PS 46 Co-Axial Surface 0.09

PS 47 Co-Axial Flush 0.14

### INLINE SOCKETS

PS 21 D.I.N. 2 Pin (Speaker) 0.13

PS 22 D.I.N. 3 Pin 0.17

PS 23 D.I.N. 5 Pin 180° 0.17

PS 24 D.I.N. 5 Pin 240° 0.17

PS 25 Jack 2.5mm Plastic 0.10

PS 26 Jack 3.5mm Plastic 0.12

PS 27 Jack 1" Plastic 0.24

PS 28 Jack 1" Screened 0.28

PS 29 Jack Stereo Plastic 0.23

PS 30 Jack Stereo Screened 0.32

PS 31 Phono Screened 0.14

PS 32 Car Aerial 0.15

PS 33 Co-Axial 0.17

### PLUGS

PS 1 D.I.N. 2 Pin (Speaker) 0.11

PS 2 D.I.N. 3 Pin 0.12

PS 3 D.I.N. 4 Pin 0.15

PS 4 D.I.N. 5 Pin 180° 0.14

PS 5 D.I.N. 5 Pin 240° 0.15

PS 6 D.I.N. 6 Pin 0.16

PS 7 S.I.N. 7 Pin 0.15

PS 8 Jack 2.5mm Screened 0.10

PS 9 Jack 3.5mm Plastic 0.09

PS 10 Jack 3.5mm Screened 0.12

PS 11 Jack 1" Plastic 0.13

PS 12 Jack 1" Screened 0.18

PS 13 Jack Stereo Screened 0.29

PS 14 Phono 0.06

PS 15 Car Aerial 0.15

PS 16 Co-Axial 0.10

### CABLES

CP 1 Single Lapped Screen 0.06

CP 2 Twin Common Screen 0.08

CP 3 Stereo Screened 0.08

CP 4 Four Core Common Screen 0.23

CP 5 Four Core Individually Screened 0.30

CP 6 Microphone Fully Braided Cable 0.10

CP 7 Three Core Mains Cable 0.07

CP 8 Twin Oval Mains Cable 0.06

CP 9 Speaker Cable 0.04

CP 10 Low Loss Co-Axial 0.10

## CARBON POTENTIOMETERS

Log and Lin

4.7K, 10K, 22K, 47K, 100K, 220K, 470K, 1M, 2M

VC 1 Single less Switch 0.14

VC 2 Single D.P. Switch 0.26

VC 3 Tandem Less Switch 0.44

VC 4 1K Lin Less Switch 0.14

VC 5 100K Log anti-Log 0.44

## HORIZONTAL CARBON PRESETS

0.1 watt 0.06 each

100, 220, 470, 1K, 2.2K, 4.7K, 10K, 22K, 47K, 100K, 220K, 470K, 1M, 2M, 4.7M

## WORLD SCOOP

### JUMBO SEMICONDUCTOR PACK

Transistors - Germ. and Silicon Rectifiers - Diodes - Triacs - Thyristors - I.C.s and Zeners ALL NEW AND CODED.

### APPROX 100 PIECES

Offering the amateur a fantastic bargain Pak and an enormous saving—identification and data sheet in every Pak.

Only £2 p. & p. 20p

## EX-COMPUTER BOARDS BY THE BOXFULL!

20 Boards packed with Semiconductors and other Electronic Components. Each board approx. size 8" x 7". All known type nos. and easily recognisable.

**FANTASTIC VALUE AT £2.20 per BOX p. & p. 52p**

## SPECIAL PURCHASE

2K3055. Silicon Power Transistors NPN. Famous manufacturers out-of-spec devices free from open and short defects—every one able 115W. T03. Metal Case.

OUR SPECIAL PRICE 8 for £1

## LOW COST CAPACITORS

01UF 400v. 3p. each  
500UF 50v. Elect. 10p each

## RECORD STORAGE/CARRY CASES

7" EP. 18½" x 7" x 8". (50 records) £2.10  
12" LP. 13½" x 7½" x 12½". (50 records) £2.95

## CASSETTE CASES

Holds 12. 10" x 3½" x 5". Lock & Handle. £1.30

## 8-TRACK CARTRIDGE CASES

Holds 14. 13" x 5" x 6". Lock & Handle. £1.95

Holds 24. 13½" x 8" x 5½". Lock & Handle. £2.70

COLOURS: Red, Black and Tan—Please state preference.

## REPANCO TRANSFORMERS

240v. Primary. Secondary voltages available from selected tappings 4v, 7v, 8v, 10v, 14v, 15v, 17v, 19v, 21v, 25v, 31v, 33v, 40, 50 and 25v-0-25v.

Type	Amps.	Price	P & P
MT50/1	1	£1.93	80p
MT50/1	1	£2.42	35p
MT50/2	2	£3.30	40p

## CARTRIDGES

ACOS GP91-18C. 200mV at 1.2cms/sec £1.16

ACOS GP93-1. 280mV at 1cm/sec £1.65

ACOS GP96-1. 100mV at 1cm/sec £2.65

TTC J-2005. Crystal/Hi Output 95p

TTC J-20 10C Crystal/Hi Output Compatible £1.10

TTC J-200 CS Stereo/Hi Output £1.60

TTC J-2105 Ceramils/Med. Output £1.64

## CARBON FILM RESISTORS


The E12 Range of Carbon Film Resistors, 1/8th watt available in PAKS of 50 pieces, assorted into the following groups:—

R1 50 Mixed 100 ohms-820 ohms 40p

# -the lowest prices!

## BI-PAK QUALITY COMES TO AUDIO!
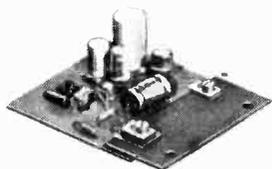
### AL10/AL20/AL30 AUDIO AMPLIFIER MODULES



The AL10, AL20 and AL30 units are similar in their appearance and in their general specification. However, careful selection of the plastic power devices has resulted in a range of output powers from 3 to 10 watts R.M.S. The versatility of their design makes them ideal for use in record players, tape recorders, stereo amplifiers and cassette and cartridge tape players in the car and at home.

Parameter	Conditions	Performance
HARMONIC DISTORTION	$P_o = 3$ WATTS $f = 1$ KHz	0.25%
LOAD IMPEDANCE	—	8 - 16 $\Omega$
INPUT IMPEDANCE	$f = 1$ KHz	100 k $\Omega$
FREQUENCY RESPONSE $\pm 3$ dB	$P_o = 2$ WATTS	50 Hz - 25KHz
SENSITIVITY for RATED O/P	$V_s = 25$ V, $R_l = 8 \Omega$ $f = 1$ KHz	75mV, RMS
DIMENSIONS	—	3" x 2 1/2" x 1"

The above table relates to the AL10, AL20 and AL30 modules. The following table outlines the differences in their working conditions.

Parameter	AL10	AL20	AL30
Maximum Supply Voltage	25	30	30
Power output for 2% T.H.D. (RL = 8 $\Omega$ $f = 1$ KHz)	3 watts RMS Min.	5 watts RMS Min.	10 watts RMS Min.

#### AUDIO AMPLIFIER MODULES

AL 10, 3 watts RMS	£2.19
AL 20, 5 watts RMS	£2.59
AL 30, 10 watts RMS	£3.01

#### POWER SUPPLIES

PS 12, (Use with AL10 & AL20)	88p
SPM 80, (Use with AL30 & AL50)	£3.25
FRONT PANELS SP 12 with Knobs	£1.10

#### PRE-AMPLIFIERS

PA 12, (Use with AL10 & AL20)	£4.35
PA 100, (Use with AL30 & AL50)	£13.15

#### TRANSFORMERS

T461 (Use with AL10)	£1.38 P & P 15p
T538 (Use with AL20)	£1.93 P & P 15p
BMT80 (Use with AL30 & AL50)	£2.15 P & P 25p

#### PA 12, PRE-AMPLIFIER SPECIFICATION

The PA 12 pre-amplifier has been designed to match into most budget stereo systems. It is compatible with the AL 10, AL 20 and AL 30 audio power amplifiers and it can be supplied from their associated power supplies. There are two stereo inputs, one has been designed for use with Ceramic cartridges while the auxiliary input will suit most Magnetic cartridges. Full details are given in the specification table. The four controls are, from left to right: Volume and on/off switch, balance, bass and treble. Size 152mm x 84mm x 35mm.


Frequency response—  
20Hz - 50KHz ( $\pm 3$ dB)  
Bass control—  
 $\pm 12$ dB at 60Hz  
Treble control—  
 $\pm 14$ dB at 14KHz  
\*Input 1, Impedance  
1 Meg. ohm  
Sensitivity 300mV  
†Input 2, Impedance  
30 K ohms  
Sensitivity 4mV

Look for our  
SEMICONDUCTOR ADVERTISEMENTS in  
Practical Wireless Everyday Electronics  
Wireless World Audio  
Radio Constructor Electronics Today International

ALL PRICES INCLUDE V.A.T.
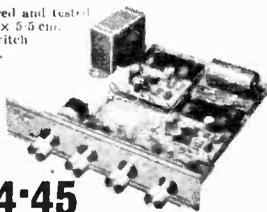
### The STEREO 20

The 'Stereo 20' amplifier is mounted, ready wired and tested on a one-piece chassis measuring 20 cm x 14 cm x 5.5 cm. This compact unit comes complete with on/off switch volume control, balance, bass and treble controls, Transformer, Power supply and Power amps. Attractively printed front panel and matching control knobs. The 'Stereo 20' has been designed to fit into most turntable plinths without interfering with the mechanism or alternatively, into a separate cabinet. Output power 20w peak. Input 1 (Cer.) 300mV into 1M. Freq. res. 25Hz-25kHz. Input 2 (Aux.) 4mV into 30K. Harmonic distortion: Bass control  $\pm 12$ dB at 60Hz typically 0.25% at 1 watt. Treble con.  $\pm 14$ dB at 14kHz.



£14.45


### NOW WE GIVE YOU 50w PEAK (25w R.M.S.) PLUS THERMAL PROTECTION! The NEW AL60 Hi-Fi Audio Amplifier FOR ONLY £3.95



- Max Heat Sink temp. 90°C.
- Frequency Response 20Hz to 100KHz
- 0.1% Distortion
- Distortion better than 1% at 1KHz
- Supply voltage 10-35 volts
- Thermal Feedback
- Latest Design Improvements
- Load—3, 4, 8 or 16 ohms
- Signal to noise ratio 80dB
- Overall size 63mm x 105mm x 13mm

Especially designed to a strict specification. Only the finest components have been used and the latest solid state circuitry incorporated in this powerful little amplifier which should satisfy the most critical A.F. enthusiast.

### STABILISED POWER MODULE SPM80

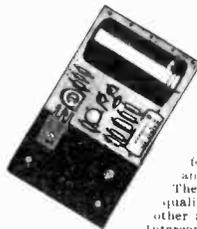

SPM80 is especially designed to power 2 of the AL50 Amplifiers, up to 15 watt (r.m.s.) per channel simultaneously. This module embodies the latest components and circuit techniques incorporating complete short circuit protection. With the addition of the Mains Transformer MT80, the unit will provide outputs of up to 1.5 amps at 35 volts. Size: 63mm x 105mm x 30mm. These units enable you to build Audio Systems of the highest quality at a hitherto unobtainable price. Also ideal for many other applications including: Disc Systems, Public Address Intercom Units, etc. Handbook available 10p **PRICE £3.25**

TRANSFORMER BMT80 £2.15 p. & p. 28p

### STEREO PRE-AMPLIFIER TYPE PA100

Built to a specification and NOT a price, and yet still the greatest value on the market the PA100 stereo pre-amplifier has been conceived from the latest circuit techniques. Designed for use with the AL50 power amplifier system, this quality made unit incorporates no less than eight silicon planar transistors, two of these are specially selected low noise NPN devices for use in the input stages. Three switched stereo inputs, and rumble and scratch filters are features of the PA100, which also has a STEREO/MONO switch, volume, balance and continuously variable bass and treble controls.



#### SPECIFICATION

Frequency Response 20Hz - 20KHz  $\pm 1$ dB  
Harmonic Distortion better than 0.1%  
Inputs: 1. Tape Head 1-25 mV into 50K  $\Omega$   
2. Radio, Tuner 35 mV into 50K  $\Omega$   
3. Magnetic P.U. 1-5 mV into 50K  $\Omega$   
All input voltages are for an output of 250mV. Tap and P.U. inputs equalised to RIAA curve within  $\pm 1$ dB, from 20Hz to 20KHz.  
Bass Control  $\pm 15$ dB at 20Hz  
Treble Control  $\pm 15$ dB at 20 KHz  
Filters: Rumble (High Pass) 100Hz  
Scratch (Low Pass) 8KHz  
Signal/Noise Ratio better than -65dB  
Input overload - 26dB  
Supply + 35 volts at 20mA  
Dimensions 292mm x 82mm x 35mm

**ONLY £13.15**  
SPECIAL COMPLETE KIT COMPRISING 2 AL50's, 1 SPM80, 1 BMT80 & 1 PA100 ONLY £25.30 FREE p. & p.

Giro No. 388-7006

Please send all orders direct to warehouse and despatch department

# BI-PAK

P.O. BOX 6, WARE, HERTS

Postage and packing add 11p. Overseas add extra for airmail.

Minimum order 55p. Cash with order please.

Guaranteed Satisfaction or Money Back

**BUNKER  
RAMO**

# AMPHENOL POPULAR COAXIAL CONNECTORS



31-221 (UG 1094/U)	BNC Socket 50 $\Omega$	Price each per 100 PCS. <b>40.5p</b>
31-002 (UG 88/U)	BNC Plug $\Omega$	<b>43.5p</b>
31-010 Isolated	BNC Socket 50 $\Omega$	<b>55p</b>
83-1SP (PL 259)	UHF Plug 50 $\Omega$	<b>38p</b>
83-1R (SO 239)	UHF Socket 50 $\Omega$	<b>33p</b>
83-185 (UG 175/U)	UHF Reducer	<b>12p</b>
83-168 (UG 176/U)	UHF Reducer	<b>12p</b>

U.K. DISTRIBUTORS

Available from Amphenol Distributors

**Caldis Ltd.**,  
37/39 Loverock Road,  
Reading, RG3 1ED,  
Berks.  
Tel: Reading (0734) 582211  
Telex: 848370.

**Intel Group of Companies,**  
Henlow Trading Estate,  
Henlow, Beds.  
Tel: Hitchin (0462) 812505  
Telex: 825637

**Invader Components Ltd.**,  
30 Tribune Drive,  
Trinity Trading Estate,  
Milton, Sittingbourne, Kent.  
Tel: Sitt. (0795) 705333  
Telex: 965313.

**S.A.S.C.O. Ltd.**,  
P.O. Box No. 2000,  
Gatwick Road,  
Crawley, Sussex.  
Tel: Crawley (0293) 28700  
Telex: 87131.

**Townsend-Coates Ltd.**,  
Coleman Road,  
Leicester.  
Tel: Leicester (0533) 768561  
Telex: 34321

## NEW PRACTICAL PAPERBACKS FROM FOULSHAM-TAB


Colour TV Repair by Martin Clifford	£1.40	Modern Radio Repair Technique by Art Margolis	£1.70
Basic Audio Systems by Norman H. Crowhurst	£1.60	Practical Colour TV Service Techniques by Robert L. Goodman	£1.95
Everymans Guide to Car Maintenance by George Zwick	£1.50	TV Troubleshooters Handbook by Editors of Electronic Technician/Dealer	£1.75
Matv Systems Handbook by Allen Pawlowski	£1.40	Acoustic Techniques for Home & Studio by F. Alton Everest	£1.50
Mobile Radio Handbook by Leo G. Sands	£1.50	199 Colour TV Troubles & Solutions by R. L. Goodman	£1.50
Rapid Radio Repair by G. Warren Heath	£1.60	IC Projects for Amateur & Experimenter by Wayne Green	£1.45
Understanding & Using the VOM & EVM by John Cunningham	£1.50	Japanese Colour TV Service Manual by Hitachi etc.	£1.90
Handbook of Electronic Tables by Martin Clifford	£1.40	Radio Electronics Hobby Projects by Editors of Radio- Electronics	£1.45
How to use your VOM & VTVM and Oscilloscope by Martin Clifford	£1.50		
Introduction to Medical Electronics by Burton R. Klein	£1.70		

## SOLDERING GUN



New surplus stock as illustrated. AC240 volts. Input power 100 VA. Instant heat at touch of trigger switch in handle. Constructed in robust plastic casing with work light in front and 4' x 3' core cable.

## PROGRAMME TIME SWITCHES

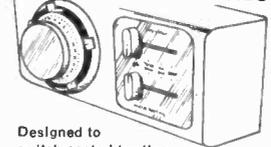

New surplus stock as illustrated. Size 7"x 4" x 3"

Smiths Time Switch with 24 hour dial which is simple to set to switch on/off twice per day at any times required. Also fitted with two lever switches which can be set to operate two circuits which can each be set to operate on Time Switch twice per day, all day, continuous, or off. Mounted in robust white plastic casing Drilled for fixing on back supplied with wiring instructions. Ideal for shop lighting and many other applications.

Designed to switch central heating and hot water on/off twice a day. Suitable for any electrical appliance up to 3 amps 240 volts A.C.

**£5.50 P&P 28p**

VAT paid.

**SAE FOR CATALOGUE WITH MANY  
OTHER BARGAINS TO**

**C. W. WHEELHOUSE & SON,**  
9/13 BELL ROAD,  
HOUNSLOW.

PHONE 01-570-3501.



**FOULSHAM-TAB LTD.**  
YEOVIL ROAD. SLOUGH. BUCKS.

# SAXON

Money saving high performance audio equipment  
DIRECT FROM OUR OWN FACTORY

## GUARANTEED TESTED HIGH PERFORMANCE MODULES—now better value than ever

<b>SA35</b> £4-45	Carriage free	★ 25Hz—25kHz ★ 0.2% distortion ★ Noise—80dB ★ 500mV into 20K 30p
35W RMS 25-50V 7 transistors, 7 diodes		
<b>SA50</b> £5-65	Carriage free	★ 4-16 ohms ★ Simple wiring ★ Short and open circuit proof ★ Continuously rated ★ Top-grade components
50W RMS 25-65V 7 transistors, 7 diodes		
<b>SA100</b> £10-90		
100W RMS 45-70V 11 transistors, 6 diodes		

120 watt module complete with built-in supply—extra heavy duty £19-75 Carr. 60p



THE SA100 MODULE

## POWER SUPPLIES

<b>UNSTABILISED</b>			
<b>PU45</b>	Suits 2 SA35 or 1 SA50	£4-90	Carriage 30p
<b>PU70</b>	Suits 2 SA50 or 2 SA100	£7-75	Carriage 40p
<b>STABILISED</b>			
<b>PS45</b>	Suits 2 SA35 or 2 SA50	£3-50	Carriage free
<b>MT45</b>	Transformer for above	£3-50	Carriage 30p
<b>PS70</b>	Suits 2 SA100	£4-90	Carriage free
<b>MT70</b>	Transformer for above	£4-90	Carriage 40p

N.B. PS70 is not suitable for the SA50

## Mk II STEREO DISCO MIXER £19-75 Carr. 30p

This well tried unit mixes two decks, handles any ceramic cartridge, and features mic over-ride plus separate full range bass and treble controls on both mic and deck inputs. Ample headphone power is available for P.F.L. May be used for mono and is mains operated. Fitted with sturdy screening case. Controls: Mic vol, bass, treble. Left/Right fade, deck volume, bass, treble, h/phone select, vol. Mains. Size 17½in x 3in x 4in deep.



## DISCO MODULE £8-00 Carr. 20p

Thousands sold of this extremely popular mono version. A mic input may be fitted using the VA30 (see below). Low consumption from a 9V battery. Features the same high standards of reproduction as the Stereo version. Controls: h/phone select, vol, Left deck vol, Right deck vol, bass, treble, master vol. Size 12½in x 3in x 2in deep.



## 3-CHANNEL SOUND-LITE £22-50 Carr. 20p

Only SAXON can supply such incredible value for money. This unit features 3kW power handling, full-wave control, bass, middle, treble AND master controls. Twin loudspeaker jacks for "through" connections. It may be used free standing or will panel mount next to either of the above. Also features unique CUT-BACK circuitry for extra wide range response. Size 12in x 3in x 2½in deep. Professional standards at a price you can afford!




**SINGLE CHANNEL VERSION** £7-50 Carr. free  
Recently reduced in price due to increasing sales, handles 1kW. Full wave operation

ADD 10% VAT TO ALL ORDERS
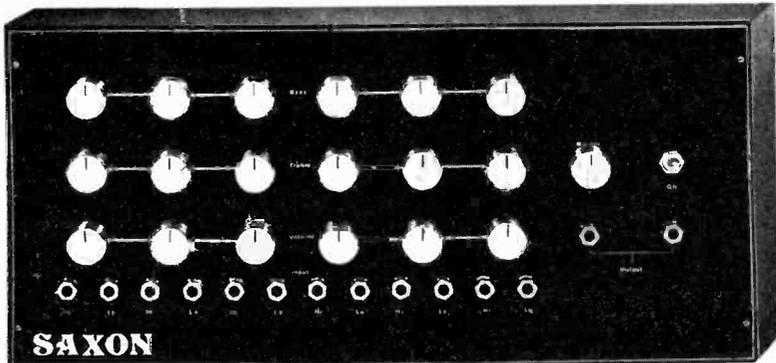
## MULTI-PURPOSE MIXERS

**M4HL** £18-50 Carr. 50p  
**M6HL** £27-50 Carr. 50p  
Featuring multiples of our VA30 module, the M4HL and M6HL fulfil the requirements of all clubs, groups, etc. where a high quality mixer is required. Each channel has one high and one low impedance input, plus volume, treble and bass controls. Input impedances may, if required, be easily changed. The M4HL has four channels, and one output, and the M6HL six channels (12 inputs) and a master control and two outputs. Either unit may be used free-standing or panel mounted. These mixers will feed all types of amplifier. Recommended for their versatility and high performance, and excellent value for money.



**VA30 CHANNEL MODULE** £3-50 Carr. free  
This is the basic channel module in the above mixers and may also be used for extra inputs on either the mono or stereo mixers. Fitted with volume, bass and treble controls, requires just a jack and supply (9-100V)

## SAXON CSE 100 COMPLETE AMPLIFIER

£34-90 Carr. free

100W of speech and music—Two separately controlled inputs. Wide range bass and treble controls. Sturdy and attractive vinyl case. Twin outputs. Ideal for groups, discos, etc. Fully tested and guaranteed. 50W version identical in appearance.



CSE 50 £29-50 Carr. free



sockets. Sturdy case, and an attractive fascia make this excellent value for money. Hundreds in use by groups, discos, clubs, etc. 50W version identical in appearance.

Four individually controlled FET input stages plus wide range bass and treble controls. 120W of speech and music output from twin loudspeaker


**SAXON 100 COMPLETE AMPLIFIER** £53-00 Carr. free  
**SAXON 50** £37-50 Carr. free

CALLERS AND MAIL ORDER:  
**SAXON ENTERTAINMENTS LIMITED**  
327-333 WHITEHORSE ROAD • CROYDON CR0 2HS

(Please quote magazine when ordering)  
SHOP HOURS: 9 a.m. 5 p.m. — LUNCH 12.30 1.30 p.m. MAIL ORDER DESK: 10 a.m. 3 p.m.  
24-HOUR ANSWER SERVICE TEL. 01-684 6385

SEND 10p FOR OUR NEW 26-PAGE MANUAL which gives full details of the above products.  
TERMS OF BUSINESS: C.W.O. or C.O.D. on receipt of 50p C.O.D. charge.  
Please include S.A.E. with all enquiries.  
VAT at 10% must be added to all orders including postage and carriage charges.

# BIG Discounts

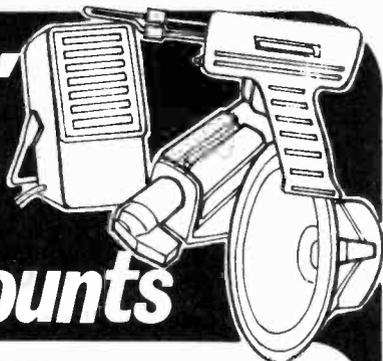

## ALL PRICES INCLUDE V.A.T.

SPEAKER BARGAINS		£
EMI 13" x 8" 3, 8 or 15 ohm		
Plain	2.05	
With Co-Axial Tweeter	2.20	
Twin Tweeter	3.70	
Type 350 8 or 15 ohm,		
20 watt	7.50	
6 1/2" 8 ohm, 10 watt	2.40	
8" 8 ohm, 10 watt	3.75	
12" 8 ohm, 20 watt	5.70	
8" x 5" C/Mag. 5 watt	1.25	
8" x 5" Dualcone	2.45	
GOODMANS 6 1/2" 8 ohm	2.15	
Dualcone		

TWEETER & CROSSOVER		£
EMI 3 1/2" or 8 ohm C/Mag.	1.00	
Cone Tweeter 8 or 15 ohm,		
10 watt	2.40	
Cone Tweeter 8 ohm, 3 watt	1.45	
Horn Tweeter 8 ohm, 20 watt	6.40	
Dome Tweeter 8 ohm, 30 watt	5.40	
Crossovers CN23 (3 ohm),		
CN28 (8 ohm), CN216 (16 ohm)	1.10	
	P. & P.	10

KIT FORM CABINETS TEAK VENEER		£
12 x 12 x 8 with 8" 8" x 5" or		
6 1/2" and 3 1/2" cut out.	2.45	
17 x 10 x 9 with 8" or 13" x 8" cutout	3.50	
18 x 11 x 9 with 13" x 8" cutout for EMI 350	4.25	
	P. & P. ea.	45

MICROPHONES		£
CM70 Planet stick metal, switch crystal	1.55	
DM160 Dynamic omni-dir. ball metal	3.85	
UD130 50K/600 ohm, uni-dir ball me at	5.75	
TW209	5.75	
CONDENSER MIKE 600 ohm, uni-dir	9.35	
Cassette Stick Mike with R. Control on/off switch (2.5 & 3.5mm J/Ply)	1.45	
	P. & P.	20

SOLDERING IRONS		£
ANTEX CN240 15 watt	1.90	
SK 1 Kit (15 watt Iron 2 spare Blb etc.)	3.30	
X25 25 watt (low leakage)	1.90	
	P. & P.	10

CARTRIDGES		£
ACOS GP91/25C or GP91/35C Stereo comp.	1.00	
GP93/1 Stereo crys.	1.25	
GP94/1 Stereo crys.	1.85	
GP95/1	1.35	
GP96/1	1.65	
GP101	80	
GP104	1.85	
BSR SC5M Stereo ceramic	2.70	
SX6H Stereo crystal	1.70	
SX6M Stereo crystal	1.70	
X5M Mono/stereo	1.40	
X5M Mono/stereo	1.40	
GOLDRING G800, G850 £3.85 £2.95		
G800E	7.15	
	P. & P.	10p

SONOTONE		£
9THAC Stereo cor. diam.	1.70	
19-TI Stereo crystal	80	
Saphire .35 D. Diamond	1.25	
Styll for GOLDRING G800 G8501	95	
G800E	3.95	
	P. & P.	05

BATTERY ELIMINATORS		£
240v Input 6, 7.5 or 9 300mA	2.75	
12v d.c. Input (specify output)		
6, 7.5 or 9 d.c. output at 300mA	2.15	
	P. & P.	15

TAPES		£
5" 50p	85p	
5 1/2" 85p	1.15p	
7" 85p	1.15p	
	P. & P. 1-3, 9p ea. 4 or more, lot 30p	

LOW NOISE CASSETTES		£
C80	35p	
C90	45p	
CT20	55p	
6-10	11-20	
33p	30p	
43p	40p	
52p	50p	
Cassette Head Cleaner	35p	
	P. & P. 1-5, 3p ea. 6-10, 15p lot. 11-20, Post Free.	

PLASTIC LIBRARY CASES		£
For 5" Reels	18p	
5 1/2" Reels	22p	
7" Reels	25p	
CASSETTE CASES	10p	
	P. & P. 1-3, 5p ea. 4 or more, 20p	

BIB ACCESSORIES		£
Tape Editing Kit Ref. 23	1.25	
Recording Tape		
Splicer Ref. 20	1.15	
Cassette Tape, editing Ref. 24	1.40	
Cassette Salvage Kit Ref. 29	40p	
12" Cassette Case Ref. 34	£1.50	
Stylus Balance Ref. 32A	1.15	
Spirit Lever Ref. 46	50	
Hi-Fi Stereo Test Cassette	1.90	
Groove-Kleen Record Cleaner	1.90	
	P. & P.	10

**SPECIAL OFFER**  
**SINCLAIR CAMBRIDGE CALCULATOR (BATT.)**  
 • 4 1/2" x 2" x 1 1/8", wt. 3 1/2 oz.  
 • Floating Dec. Point  
 • Algebraic Logic  
 • 4 Operators with Constant  
 • 8 Digit Display  
 Build £19.95  
 Kit £14.95

Send 25p for COMPLETE CATALOGUE, refundable upon first order. ALL OUR MERCHANDISE IS FULLY GUARANTEED. Subject to manufacturer increase and availability.

# Riversdale Electronics

Mail Order Department **PW8**

P.O. Box 470, Manchester M60 4BU.

## EEMI ELECTRONIC ORGAN KITS



There are four excellent quality Models for the do it yourself enthusiast

★ Portable—4 octave keyboard with 10 voices, 3 pitches—vibrato, £145.29. ★ Console—5 octave keyboard with 10 voices, 3 pitches. Keyboard can be split into solo and accompaniment. Vibrato, built in amplifier and speaker £250.93. ★ Console—2 x 4 octave keyboards and 13 note pedal board, 29 voices. Vibrato, Delay Vibrato, Sustain, Reverberation, Percussion, Wah Wah, £406.00. ★ Console—2x5 octave keyboards and 32 note pedal board, 32 voices. Vibrato, Delay Vibrato, Sustain, Reverberation, Percussion, 3 Couplers, etc., at £572.55.

V.A.T. please add 10%—show separately on order.

All components can be bought separately. Send 50p for 24-page catalogue which includes details of specialised components plus free vouchers worth 50p.

Also available—WIRELESS WORLD SOUND SYNTHESIZER KITS complete with reprinted instructions.

## Elvins Electronic Musical Instruments

SUPPLIERS OF COMPONENTS TO THE MUSICAL INDUSTRY

12 Brett Road, Hackney, London, E.8. Tel: 01 986 8455  
 8 Putney Bridge Rd., London, SW16 1HU. Tel: 01 870 4949

# Train for television

Course commences 4th September, 1974

This is your opportunity to train as a television and radio engineer on our full-time Two-Year College Diploma Course specially designed to cover the examinations of the City and Guilds Radio, Television and Electronics Technicians' Certificate. Full theoretical and practical instruction on all types of modern receivers—including the latest colour sets. Minimum entrance requirements are Senior Cambridge or 'O' Level, or equivalent in Mathematics and English.

Please send free prospectus to:

Name \_\_\_\_\_

Address \_\_\_\_\_


**THE PEMBRIDGE COLLEGE OF ELECTRONICS**

(Dept. PW5) 34a Hereford Rd., London W2 5AJ



**I.L.P. (Electronics) Ltd**

## SECOND GENERATION 25 WATT HYBRID

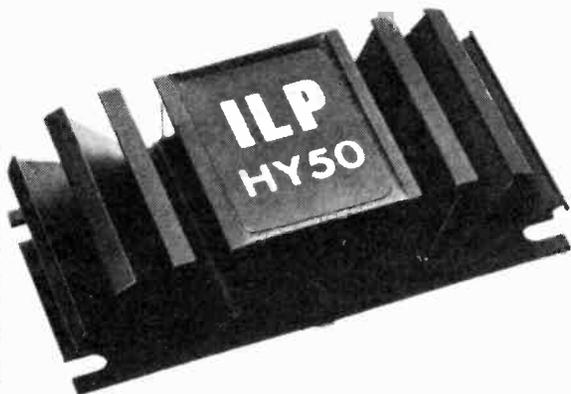

A brand new hybrid fabrication technique, recently perfected in our laboratories, has enabled us to achieve our latest range of completely integrated devices. We have now finally reduced the modular amplifier to a simple Input/output device requiring only the addition of a basic unstabilized (split line) power supply. The HY50 takes medium power modules to their logical conclusion by incorporating with it a heatsink, which is designed in special high conductivity alloy, sufficient for normal audio use without additional chassis sinking. All this without significantly increasing the size of the module comparable in size to a packet of 'King-size' cigarettes.

Consistent with modern thinking a triple rated output circuit with a load fuse allows for peak transient response without distortion but ensures the necessary protection.

**OUTPUT POWER:** 25 watts RMS, 50 watts peak music power  
**LOAD IMPEDANCE:** 4-16Ω into 8Ω  
**INPUT SENSITIVITY:** 0db (0-775 volts RMS)  
**INPUT IMPEDANCE:** 47KΩ  
**TOTAL HARMONIC DISTORTION:** Less than 0-1% at 25 watts typically 0-05 better than 75db  
**SIGNAL/NOISE RATIO:** 10Hz-50KHz ± 1db  
**FREQUENCY RESPONSE:** ± 25 volts  
105 x 50 x 25 mm

**Price £5-80 mono, £11-60 stereo**

**Price inclusive of VAT & P & P**

## NEW HY5 PRE-AMPLIFIER

Unchallenged for two years, the HY5, our unique multifunction preamplifier/tone hybrid, has been brought into line with the advancements in our power hybrids.

Like the HY50, the new HY5 has no external components & has been redesigned to run off a split power-line with improvements in signal/noise, overload, capability & reduced distortion. The output has been increased to match the power module (Odb), and to share the same power supply.

Overall size is reduced by the use of a new thin film circuitry while the device still retains all the functions of the earlier device.

When combined with the HY50 & power supply only potentiometers are required to complete a simple mono amplifier with input & output facilities expected to be found on Hi-Fi amplifiers.

The combination of two HY5's & two HY50's sharing a common power supply (PSU50) are linked by a balance control to form a complete stereo system.

**INPUTS** **SPEC.**

Magnetic Pick-up 3mV (within 1db RIAA curve)  
Ceramic Pick-up up to 3mV  
Microphone 10mV  
Tuner 250mV  
Auxiliary 3-100mV  
Input impedance 47kΩ 1kHz


**OUTPUTS**  
Tape 100mV  
Main output, 0db (0-775volts)

**ACTIVE TONE CONTROLS**  
Treble ± 12db at 10kHz  
Bass ± 12db at 100Hz

**OVERLOAD CAPABILITY** (equalization stage) 40db on most sensitive input  
**OUTPUT NOISE LEVEL** (below 10mV magnetic input) 68db

**DISTORTION** 0-05% at 1kHz  
**SUPPLY VOLTAGE** ± 16-25 volts  
**SUPPLY CURRENT** 15mA

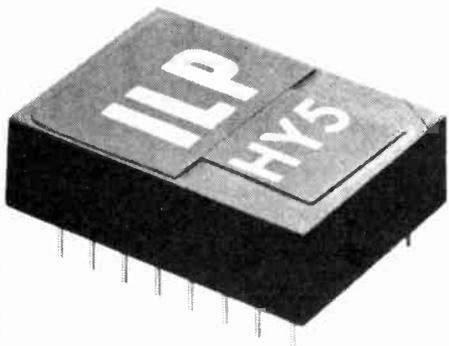**Price £4-85 mono, £9-70 stereo**  
**Price inclusive of VAT & P & P**




## POWER SUPPLY PSU50

The new PSU50 has a low profile look being only 2½ inches high and can be used for either mono or stereo systems.

**SPEC.**  
**OUTPUT VOLTAGE** ± 25 volts  
**INPUT VOLTAGE** 210-240 volts  
**SIZE** L. 70, D. 90, H. 60 mm

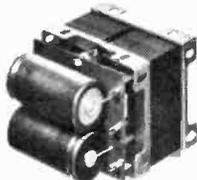**Price £5-23**  
**Price inclusive of VAT & P & P**



CROSSLAND HOUSE · NACKINGTON · CANTERBURY · KENT

CANTERBURY 63218

Please note we reserve the right to substitute at our discretion updated versions of advertised designs where applicable.

# CHROMASONIC electronics

Dept. 1  
56, Fortis Green Road, London, N10 3HN.  
telephone: 01 883 3705

## LINEAR I.C.'s

## DIODES

## TRANSISTORS

709 (8 pin dip)	34c	MC1303L	E1 89	TAA330	E1 79	AA119	10p	82X70	27p	AC107	16p	AFZ39	41p	BC309	14p	BF179	33c	85X21	22p	ZTK109	15p	2N3706	14c
709 (TO-99)	40p	MC1306P	55p	TAA310	E1 37	AA120	10p	Series		AC126	13p	ASV26	33p	BC212L	125p	BF180	33p	85Y55A	14c	ZTK300	11p	2N3707	12c
709 (14 pin dip)	35p	MC1310P	E3 05	TAA320	99p	AA129	10p	82Y68B	11p	AC127	13p	BC107	11p	BC213L	13p	BF181	33p	BU10502E1	9c	ZTK301	13p	2N3708	10c
710 (8 pin dip)	35p	MC1320P	(see below)	TAA350	81p	BA100	10p	Series		AC176	15p	BC109	12p	BC266	15p	BF185	38p	D13V	53p	ZTK302	17p	2N3709	11p
710 (TO-99)	40p	MC1330P	80p	TAA370	E1 65	BA110	45p	9A279	10p	AC187K	20p	BC148	10p	BC268	15p	BF190	38p	D40N3	61p	ZTK303	14c	2N3710	11p
710 (14 pin dip)	39p	MC1339P	E1 29			BA102	27p	9A27	11p	AC187	20p	BC117	22p	BC407	16p	BF195	15p	MAJ480	95p	ZTK304	21p	2N3711	11p
711 (TO-99)	45p	MC1350	83p	TAA320	E2 71	BA115	19p	0A81	9p	AC188	20p	BC147	10p	BCY70	17p	BF195	17p	MAJ481	E1 20	ZTK311	10p	2N3712	E2 75
711 (14 pin dip)	39p	MC1351	E1 10	TAA330	E1 98	BA144	20p	0A85	10p	AC188K	25p	BC149	10p	BCY72	17p	BF197	16p	MAJ491	E1 45	ZTK312	10p	2N3713	E3 20
723 (TO-99)	96p	MC1352	E1 10	TAA340	E2 05	BA145	20p	0A90	8p	AC189	25p	BC150	12p	BD124	80p	BF202	25p	MAJ501	E1 82	ZTK501	13p	2N3714	55p
723 (14 pin dip)	95p	MC1357	E1 59	TAA360C	E2 98	BA148	20p	0A90	8p	AC189K	25p	BC151	12p	BD115	74p	BF200	33p	MAJ900	E1 24	ZTK384	18p	2N3821	81p
741 (8 pin dip)	42p	MC1338	E1 08	TAA625A	E1 04	BA154	20p	0A91	9p	AC190	20p	BC159	14p	BD124	80p	BF202	25p	MAJ900	E1 24	ZTK500	12p	2N3823	99p
741 (TO-99)	45p	MC1375	E1 41	TAA625B	E1 04	BA156	18.5p	ZS120	8p	AD140	49p	BC167	17p	BD131	55p	BF203	25p	MAJ955	E1 82	ZTK501	13p	2N3903	163p
741 (14 pin dip)	43p	MC1456CC	E1 75	TAA625C	E1 04	BA155	15.5p	9A202	25p	AD149	49p	BC168	11p	BD132	55p	BF222	42p	MAJ900	E1 24	ZTK502	17p	2N3904	19p
747 (8 pin dip)	92p	MC1456PI	E2 42	TAA651	E2 00	BAX16	10p	ZS140	25p	AD161	36p	BC169	12p	BD133	44p	BF248	27p	MAJ955	E1 23	ZTK503	14p	2N3905	23p
748 (8 pin dip)	47p	MC1469G	E1 59	TAA800	E1 59	8B104	40p	ZS141	40p	AD162	39p	BC171	20p	BD135	42p	BF250	23p	MAJ955	E1 92	ZTK504	43p	2N3906	25p
748 (TO-99)	45p	MC1495	E3 65	TAA810S	E1 70	8B108	14.5p	ZS170	10p	AD162	39p	BC172	17.5p	BD136	44p	BF250	23p	MAJ955	E1 92	ZTK505	22p	2N4058	133p
748 (14 pin dip)	43p	MC1496G	E1 49	TAA810AS	E1 49	8B108	40p	ZS142	43p	AD162	39p	BC172	17.5p	BD136	44p	BF250	23p	MAJ955	E1 92	ZTK506	17p	2N4059	25p
		MC1302	77p			8B108	14.5p	ZS270	11p	AD162	39p	BC172	17.5p	BD136	44p	BF250	23p	MAJ955	E1 92	ZTK507	17p	2N4060	10p
AY-5-5310	E7 79	MC3401	63p	1CA790	E2 64	8B109	10p	ZS271	11p	AD162	39p	BC172	17.5p	BD136	44p	BF250	23p	MAJ955	E1 92	ZTK508	17p	2N4061	10p
BHA0002	E3 95			TDA1200	E2 15	8B110	10p	ZS272	11p	AD162	39p	BC172	17.5p	BD136	44p	BF250	23p	MAJ955	E1 92	ZTK509	17p	2N4062	10p

CA3046	95p	MFC4000A	49p		
CA3045	95p	MFC4000B	78p	ULN2111A	E1 59
CA3075	E1 58	MFC4003A	53p		
CA3081	E1 64	MFC4004	E1 10	ZNA402E	E1 98
CA3082	E1 65	MFC4005	E1 10	ZNA403E	E1 60
		MMS314	E7 92	ZNA14	E1 32
		MMS316	E1 30		

### THYRISTORS SCR's

V	300mA	6A	8A
30V	MCR102	32p	106Y 39p
50V			106F 46p
60V	MCR103	44p	106G 48p
100V	MCR104	49p	106H 50p
200V	MCR120	51p	106J 52p
400V			106K 53p
600V			106L 54p

### REGULATORS

100mA	500mA	500mA	1A
(TO-39)	(TO-3)	(SOT-22)	(TO-220)
5V	TBA625A	(005T1)	L129
		(MVR5V)	1DA1405
		E1 30	E1 65
12V	TBA625B	(005T1)	L320
		(MVR12V)	1DA1412
		E1 30	E1 65
15V	TBA625C	(005T1)	L321
		(MVR15V)	1DA1415
		E1 30	E1 65

### RECTIFIERS

V	1A	3A	6A
50	IN4001	63p	IN5400
100	IN4002	73p	IN5401
200	IN4003	9p	IN5402
400	IN4004	9p	IN5403
600	IN4005	11p	IN5404
1000	IN4006	13p	IN5405
	IN4007	16p	IN5406

## VAT INCLUSIVE PRICES

OVERSEAS CUSTOMERS DEDUCT ONE ELEVENTH VAT INVOICES ON REQUEST  
P&P Dn U.K. Orders min. 10p. Overseas Orders at Cost

WE WILL QUOTE FOR QUANTITIES ON REQUEST



... there are over 8,000 electronic components WITHIN A FEW FEET OF YOU!

That is, assuming you are on the telephone.

If you're not, the distance is between you and your nearest post box.

The first thing you need, to enable you to get your components quickly, easily, economically, is a copy of the 240 page Home Radio Components Catalogue. Apart from listing the vast range of lines we stock, it contains details of our popular Credit Account Service and many other items of useful information. For example, as there are several ways of ordering, several ways of paying and several ways of delivery, the pros and cons of all methods are clearly set out in the catalogue.

We have the reputation of providing the best-organised service ever offered to buyers of electronic components. Of course, to make good use of this service you need the catalogue. It costs 55 pence, plus 22p post and packing, and when you receive your copy you'll agree it's the best investment you've made for a long time. Moreover with the catalogue we give you 10 Vouchers each worth 5 pence against orders, an up-to-date price list and a Bookmark with a useful list of technical abbreviations.

Please write your Name and Address in block capitals

Name \_\_\_\_\_

Address \_\_\_\_\_

Home Radio (Components) Ltd. Road No. 912066, London Dept. P.W. 234-240 London Road, Mitcham, CR4 3HD.

Send off the coupon today with cheque or Postal Order for 77p. It's your first step to solving your component buying problems.

The price of 77p applies only to catalogues purchased by customers in the U.K. and in BFPO addresses.

# Henry's

**DON'T RELY ON YOUR MEMORY  
BUY NOW AT BARGAIN PRICES**  
Hi Fi and Transistors - Up to date  
Brochures on request

**HENRY'S  
CATALOGUE**  
Due to rapid price changes,  
shortages of paper and raw  
materials, all prices in the  
existing catalogues no longer  
apply. Call or phone for latest  
prices. A new catalogue will  
be available for Aug/Sept. 1974.



**UK's  
LARGEST RANGE  
OF KITS &  
GADGETS**

## TEST EQUIPMENT

### MULTIMETERS

- (carr. etc. 30p)
- ITI-2 20K/Volt Slimline £5-95
- M210 (Case £1-25) 20K/Volt Slimline de-luxe £6-75
- TLH33D 2K/Volt Robust £7-50
- U4323 (+IF8AF Oac) £12-50
- AF105 (Case £2-25) 50K/Volt £10-50
- U4313 20K/Volt AC current. Steel case £10-50
- U4341 Plus Built in transistor tester £10-50
- Model 500 (Case £2-25), 30K/Volt £11-75



### OTHER EQUIPMENT

- SE250B Pocket Signal Injector £2-25 carr. 15p
- TE15 Grid Dip meter 440kHz-280MHz £18-50 carr. 30p
- TE40 AC Millivoltmeter 1-2mHz £19-75 carr. 35p
- TE8528 Range valve voltmeter £22-50 carr. 40p
- TE20D 120kHz-500mHz RF Generator £18-95 carr. 40p
- TE22D 20Hz-200kHz Audio Generator £19-95 carr. 40p
- SE350A Deluxe Signal Tracer £12-95 carr. 20p
- SE400 Volts/ohms/R-C sub./RF field/RF gen. £15-50 carr. 20p

### New Revolutionary Supertester 680R

- 680R Multi-tester £18-50
- Accessories
- Transistor tester £11-00
- Electronic voltmeter £16-00
- Ampclamp £11-95
- Temperature probe £11-95
- Gauss meter £11-95
- Signal Injector £3-95
- Phase Sequence £3-95
- EHT Probe £3-95
- Shunt 25/50/100A £4-50



### A SELECTION OF INTERESTING ITEMS

- C3025 Compact transistor tester £6-95 p & p 15p
- Q4002 Photoelectric System £13-70
- E1310 Stereo mag. cart. preamp. £4-80 p & p 25p
- Easiphone D1201 telephone amplifier £7-50 p & p 25p
- D1203 Teleamp. with PU coil £4-95 p & p 20p
- L11 Door Intercomm. and chime £8-40 p & p 25p
- 9" Twin spring unit For £3-30 p & p 15p
- 18" Twin spring unit Reverba £6-85 p & p 25p
- UJ50 Ultrasonic Switch Transmitter/Receiver £12-75
- SC3041 1-250 MHz £4-25
- SC3043 5CH 1-300 MHz £4-50 p & p 15p
- VHF 105 Aircraft Band Converter £4-20 p & p 15p
- B2004 4 ch. Stereo mixer £6-75 p & p 15p
- BK3 Kit. Etch your own ptd. circuits £1-95 p & p 20p

### BUILD THIS RADIO

Portable MW/LW radio kit using Mullard RF/IF module. Features MW-bandspread for extra selectivity. Slow motion tuning. Fibre glass PVC cabinet. 600mW output. All parts £7-98 (battery 22p), carr. etc. 32p.




### EXCLUSIVE: SPECIAL OFFERS

- MW/LW CAR RADIO + or - Earth with speaker and fixings. £6-50 c./p. 30p.
- 8 TRACK CAR STEREO ( - Earth) with speakers in Pds & fixgs. £12-50 c./p. 40p.
- Portable Battery Cassette Tape Player £7-25.
- Car Lighter Plug hood adaptor for all cassette and radio. 6/7 1/2 volt output (state width) £1-95 each.
- Rotel Stereophones RH630 £6-80
- RH700 £10-25
- RH430 £4-14
- Welin W500 Battery/Mains Cassette Recorder £12-75
- PORTABLE CASSETTE TAPE PLAYER—for car or carry around. £7-25 c./p. 20p.
- HANIMAX BC808 POCKET CALCULATOR (PDS) % KEY. £28-95
- HANIMAX BC811M MEMORY RECALLER £33-75
- BC807 % Key £22-95
- BCM850 % Key + Memory £33-95
- MAINS UNIT £3-25 Extra
- COMPACT RECORD PLAYER 2 x 7 watts. Complete with Speakers (List £54-50) Price £39-95. Plus free pair of stereo phones.
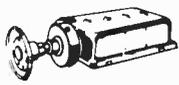
## SPECIAL PURCHASES


**UHF TV TUNERS CHANNELS 21 TO 6**  
Brand new transistorised geared tuners for 625 Line Receiver IF output. £2-50, Post 20p.


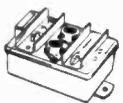
## EASY TO BUILD KITS BY AMTRON—EVERYTHING SUPPLIED

- Model No.
- 310 Radio control receiver £3-20
- 300 4-channel R/C transmitter £6-81
- 345 Superhet R/C receiver £8-81
- 65 Simple transistor tester £4-50
- 115 8 watt Amplifier £4-73
- 120 12 watt amplifier £8-01
- 125 Stereo control unit £24-16
- 130 Mono control unit £25-31
- 605 Power supply for 118 £21-45
- 615 Power supply for 120 £19-77
- 230 AM/FM aerial amplifier £8-90
- 240 Auto packing light £8-98
- 275 Mic. preamplifier £21-45
- 570S LF generator 10Hz-1mHz £28-47
- 575S Sq. wave generator 20Hz-20KHz £28-24
- 590 STAB Power supply 6-12v 0-25-0-1A £23-31
- 690 DC motor speed Gov. £7-92
- 700 Electronic Chaffinch Acoustic switch £12-57
- 730 Metal Detector (electronics only) £10-91
- 790 Capacitive Burglar alarm £4-99
- 835 Guitar preamp. £8-99
- 840 Delay car alarm £13-99
- 875 CAP. Discharge Ignition for car engine (-V-E Earth) £2-85
- 80 Scope Calibrator £6-98
- 255 Level Indicator £11-31
- 525 120-160mHz VHF timer £8-97
- 715 Photo cell switch £4-97
- 795 Electronic continuity tester £15-51
- 860 Photo timer £8-61
- 235 Acoustic Alarm for driver £29-90
- 465 Quartz XTAL checker £2-30
- 220 Signal Injector £15-50
- 390 VOX £19-30
- 432 Testakit £8-55
- 670 Buffer Battery Charger £18-75
- 850 Electronic Keyer £58-50
- 820 Electronic Digital Clock

ALL KITS OFFERED SUBJECT TO STOCK AVAILABILITY Prices correct at time of preparation. Subject to change without notice.



### BUILD THIS TUNER ML3

MW/LW Radio Tuner to use with any amplifier. Features Mullard RF/IF module Ferrite aerial, built in battery. Excellent results. Size 7" x 2 1/2" x 3 1/2". All parts £5-25, carr. 15p.

- Mullard FM Modules LP1188 Tuning Heart Module. LP1185 IF Module complete with data. Price £9-00 pair.

- FM Tuner Module FM5231 12v FM Tuner £7-95. SD4912 Stereo Decoder £1-95. SF82H 8v Stereo FM Tuner £14-95.

- PP3 Eliminator Kit Complete module kit 9v 100mA output £1-95, p & p 25p.

### TBA800 5 WATT I.C.

Suitable alternative to SL403D. 5/30 volt operated. 8/16 ohm 5 watt output. With circuits and data £1-50. Kit with printed circuit panel £2-70. All kits available from stock.

### STROBE TUBE

ZFT4A. Suitable for December '73 Pract. Electronics £3-50. ST2 (D32) DIAC 25p CR51/40 SCR 45p. ZFT4 £3-50. ZFT8 £4-00



### UK'S LARGEST RANGE OF TRANSISTORS AND DEVICES

- JUST A SELECTION
- \*TBA800 5 Watt IC £1-50
- \*Sinclair IC12 6 Watt IC £2-00
- \*ZN141C Radio £1-20
- \*Ultrasonic Transducers £3-90 pr.
- \*3015F 75EG Indicator £1-70
- \*TIL 209 LED 24p each. 22p each per 10
- \*With circuits/data sheet
- OVER 1500 DIFFERENT SEMI-CONDUCTOR DEVICES IN STOCK
- Free stock list—latest edition (Ref. 36) on request. Includes radio valves, I.C.'s Rectifiers, Trlacs, SCR's, LED's, etc. More types—better prices—discounts for quantity small or large.

### GARRARD BATTERY TAPE DECK



GARRARD 2 speed 9 volt tape decks. Fitted record / play and oscillator/erase heads. Wind and rewind controls. Takes up to 4" spools. Brand new complete with head circuits. £9-50 carr. 30p.

### TOP QUALITY SLIDER CONTROLS

60mm stroke high quality controls complete with knobs (post, etc. 15p any quantity).


### MARRIOT TAPE HEADS

4 TRACK MONO or 2 TRACK STEREO '17' High Impedance £2-50 '18' Med. Impedance £3-50 '38' Med. Impedance £3-00 R730/E73 2 track mono Record/Erase low Imp. 75p pair. Erase Heads for '17' '18' and '38' £1-00 '63' 2 track mono, Hi Imp. £1-75 '43' Erase Head for '63' 75p (Post, etc. 15p any qty).

Singles Log and Lin SK, 10K, 22K, 50K, 100K, 250K, 500K, 1 Meg. 45p each. Ganged Log and Lin SK, 22K, 50K, 100K, 250K, 500K, 1 Meg. 65p each. Quantity discounts available. Complete with knobs.
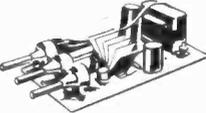
### SINCLAIR. MINIATURE AMPLIFIERS & TUNER/DECODER

- AMPLIFIERS (carr. etc. 20p)
- 4-300, 0-3 watt 9 volt £1-75
- 104, 1 watt 9 volt £3-10
- 304, 3 watt 9 volt £3-95
- 555, 3 watt 12 volt £4-10
- IE208, 5 watt 12 volt £5-10
- 508, 10 watt 24 volt £4-95
- 410, 10 watt 28 volt £4-95
- IE208, 30 watt 45 volt £9-95
- IE120, 2 1/2 + 2 1/2 watt 12 volt £8-25
- RE500, 5 watt IC mains operated Amplifier with controls £6-30
- SAC14, 7 + 7 watt Stereo with controls £11-75
- SAC13, 15 + 15 watt Stereo with controls £14-95
- SP40-5 2240/stereo 08/PZ5 £25-00
- SP40-6 2240/stereo 80/PZ8 £27-75
- SP60 2260/stereo 80/PZ8 £30-45
- Transformer PZ8 £3-95



### POWER SUPPLIES FOR EVERY PURPOSE

- (All cases unless stated chassis)
- 470C 6/7 1/2 volt 300 mA (Includes Multi-Adaptor for Tape Recorders, etc.) £2-25 post 20p
- Car Lighter Voltage Adaptors 300mA (State voltage 8v, 7 1/2v, 9v) £1-95 ea. post 25p
- SC202 3/6/7 1/2 volt 400mA £4-25 carr. 30p
- HC244a Stabilised version £5-50 carr. 30p
- P500 9 volt 500mA £3-20 post 20p
- P11 24 volt 500mA (chassis) £2-80 post 20p
- P15 26/28 volt 1 amp (chassis) £2-90 post 20p
- P1080 12 volt 1 amp (chassis) £2-70 post 20p
- P1091 45v 0-9 amp (chassis) £7-80 post 20p
- P12 44-12 volt 0-4-1 amp £7-15 post 30p
- SE101A 3/6/9/12 volt 1 amp (Stab.) £12-75 post 25p
- RP164 6/7 1/2/9/12 1 amp (Stab.) £13-45 post 30p

### FIBRE OPTICS

0-01 Diam. Mono Filament £5-50 per 100 metre reel 0-13 Diam. 54 Fibres Sheathed. £1-00 per metre. SPRAYS 15mm Diam. (Mares Tail Spray) £10-50



All types offered subject to availability. Prices correct at time of press. 10% VAT TO BE ADDED TO ALL ORDERS. UK post etc. 15p per order unless stated.

# Henry's

## RADIO LIMITED

EDGWARE ROAD, LONDON W2

404-406 Electronic Components and Equipment 01-402 8381  
309 PA - Disco - Lighting High Power Sound 01-723 6963  
303 Bargains Store (Callers only)  
Home and Car Entertainment Centres London and branches now open  
120 Shaftesbury Avenue, London W1 01-437 9692  
144 Burnt Oak Broadway, Burnt Oak, Edgware 01-952 7402  
190-194 Station Road, Harrow, Middlesex 01-663 7788/9  
354-356 Edgware Road, London W2 01-402 8584/4736

All mail to 303 Edgware Road, London W2 1BW  
All stores open 9 am to 6 pm six days a week  
Hi-Fi - Tape Equipment Discount Stock List Free at all stores

# ALL OUR PRICES INCLUDE V.A.T.

## BSR HI-FI AUTOCHANGER

**STEREO AND MONO**  
Plays 12", 10" or 7" records  
Auto or Manual. A high  
quality unit backed by BSR  
reliability with 12 months'  
guarantee. AC 300/250v.  
Size 13 1/2 x 11 1/2 in.  
Above motor board 2 1/2 in.  
Below motor board 3 1/2 in.  
With STEREO/MONO CARTRIDGE



£6-75 Post 35p.

## PORTABLE PLAYER CABINET

Modern design. Size 18" x 15" x 7" Black resin  
covered. Silver front grille. Padded Lid. Chrome  
fittings. Motor board cut for above BSR deck. Post 45p.

£4-50

## METAL PLINTH AND PLASTIC COVER

Cut out for most Garrard or B.S.R.  
Most will play with cover in position.  
12 1/2 x 14 1/2 x 7 1/2 in.  
Covered in black leatherette. Post 45p

£4-95

ALSO AVAILABLE IN SOLID NATURAL MAHOAGANY  
WAX POLISHED FINISH—£5-95

## BSR JUNIOR SINGLE PLAYER

Heavy duty 4-speed motor with  
separate pick-up arm fitted  
LF78 turnover motor. £4-95 Post 25p  
compatible cartridge.



## R.C.S. DISCO DECK SINGLE RECORD PLAYER

Fitted with auto stop. Acos stereo/mono cartridge. Base-  
plate. Size 11 1/2 x 8 1/2 in. Turntable. Size 7 in diameter. A/C  
mains. 220/250V motor has a separate winding 14 volt to  
power a small amplifier.  
3 speeds plays all size  
records.

£5-50 Post 25p

## COMPACT PORTABLE STEREO HI-FI

Two full size loudspeakers 1 1/2 x 10 x 3 1/2 in. Player  
unit clips to loudspeakers making it extremely compact.  
Overall size only 13 1/2 x 10 x 8 1/2 in. 3 watts per  
channel, plays all records 33  
rpm 45 rpm.  
Separate vol-  
ume & tone  
controls 240v  
AC mains



Attractive  
Teak finish  
Weight 13lbs.

Bargain Price  
£25  
85p carriage

## SPECIAL OFFER! SMITH'S CLOCKWORK 15 AMP TIME SWITCH 0-60 MINUTES



Single pole two-way surface mounting  
with fixing screws. Will replace existing  
wall switch to give light for return home,  
garage, automatic anti-burglar lights etc. Variable knob  
Turn on or off at full or intermediate settings.  
Fully insulated. Makers last list price £4-50. Brand new and  
fully guaranteed. OUR PRICE £1-95 Post 25p.

BLANK ALUMINIUM CHASSIS. 18 s.w.g. 2 1/2 in sides  
6 x 4 in 45p; 8 x 6 in 53p; 10 x 7 in 65p; 12 x 8 in 85p;  
14 x 9 in 90p; 16 x 6 in 90p; 12 x 3 in 50p; 16 x 10 in 61.  
ALUMINIUM BOXES 3 x 3 x 3 in. 60p; 4 x 4 x 4 in. 70p.  
6 x 4 in. 80p. 9 x 4 x 4 in. 21. 12 x 4 in. 21-30.  
ALUMINIUM PANELS 18 s.w.g. 6 x 4 in 12p; 8 x 6 in 19p;  
14 x 3 in 20p; 10 x 7 in 24p; 12 x 5 in 25p; 12 x 8 in 34p;  
16 x 6 in 34p; 14 x 9 in 40p; 12 x 12 in 47p; 16 x 10 in 60p.  
S.R.B.P. PAXOLIN PANEL 10 x 8 in 20p.

1 1/2 inch DIAMETER WAVECHANGE SWITCHES, 25p. EA.  
2 p. 2-way, or 2 p. 6-way, or 3 p. 4-way.  
1 p. 1 2-way, or 4 p. 2-way, or 4 p. 3-way, 25p.

TOGGLE SWITCHES, sp. 18p; dp. 22p; dp. dt. 22p.  
Sub-miniature, sp. 38p; dp. 40p; dp. dt. 50p.

## R.C.S. STABILISED POWER PACK KITS

All parts and instructions with Zener Diode. Printed Circuit  
Bridge Rectifiers and Double Wound Mains Transformer.  
Input 200/240V a.c. Output voltages available 6 or 8 or 12  
or 15 or 18 or 20V d.c. at 100mA or less.  
PLEASE STATE VOLTAGE REQUIRED. £2-20 Post  
Details S.A.E. Size 3 1/2 x 1 1/2 in. 20p

## R.C.S. GENERAL PURPOSE TRANSISTOR PRE-AMPLIFIER BRITISH MADE

Ideal for Mike, Tape P.U., Guitar, etc. Can be used with  
Battery 9-12v. or E.P. line 200-300V. D.C. operation. Size  
1 1/2 x 1 1/2 x 1 1/2 in. Response 25 c.p.s. to 25 Kc/s. 26 db gain.  
For use with valve or transistor equipment. 99p Post  
Full instructions supplied. Details S.A.E. 10p

NEW TUBULAR ELECTROLYTICS		CAN TYPES	
2/350V 14p	250/25V 14p	16+16+16/275V45p	
4/350V 14p	500/25V 20p	50+50/300V 60p	
8/450V 18p	1000/25V 35p	60+100/350V 85p	
16/450V 22p	1000/50V 47p	32+32/250V 20p	
32/500V 50p	8+16/450V 25p	32+32/450V 60p	
25/25V 10p	8+16/450V 25p	350+50/325V 85p	
50/50V 10p	16+16/450V 40p	100+50+50/350V85p	
100/25V 10p	32+32/350V 40p	32+32+32/350V85p	

LOW VOLTAGE ELECTROLYTICS.  
1, 2, 4, 5, 8, 16, 25, 30, 50, 100, 200mF 15V 10p.  
100mF 12V 15p; 25V 20p; 50V 30p.  
1000mF 12V 20p; 25V 35p; 50V 47p; 100V 70p.  
200mF 6V 25p; 25V 42p; 50V 57p.  
2500mF 50V 82p; 3000mF 25V 47p; 50V 45p.  
5000mF 6V 25p; 12V 42p; 25V 70p; 35V 85p; 50V 95p.  
CERAMIC 1pF to 0.01mF, 4p, Silver Mica 2 to 5000pF, 4p.  
PAPER 350V-0.1 4p; 0.5 13p; 1mF or 2mF 150V 15p.  
500V-0.001 to 0.05 4p; 0.1 5p; 0.25 9p; 0.47 25p.  
SILVER MICA. Clearance 100p. E-2-500pF 8p; 500-  
2200pF 10p; 2700-5600pF 20p; 6800pF-0.01, mid 30p each.  
TWIN GANG. "0-0" 208pF+176pF, 75p.  
Slow motion drive 385pF+385pF with 25pF+25pF, 50p;  
500pF standard twin gang 75p.  
SHORT WAVE SINGLE. 10pF, 30p; 25pF, 55p; 50pF, 55p.

## SHORT WAVE SINGLE GANG. Precision Silver Plated Gangable Tuning Condensers.

Values up to 100pF. 50p each  
Section Couplers supplied FREE with two or more gangs.

NEON PANEL INDICATORS. 250V AC/DC Amber, 20p.  
RESISTORS; 1 w., 1/2 w., 1 w. 20p; 1/2 w. 5p, 10p to 10M.  
HIGH STABILITY. 1/2 w. 2% 10 ohms to 6 meg. 10p.  
Ditto 5%, Preferred values 10 ohms to 10 meg. 4p.  
WIRE-WOUND RESISTORS. 5 watt, 10 watt, 15 watt,  
10 ohms to 100K, 10p each; 2w 0.5 ohm to 8.2 ohms 10p.  
TAPE OSCILLATOR COIL. Valve type, 35p.  
FERRITE ROD 8" x 1/2" 20p; 6" x 1/2" 20p; 3" x 1/2" 10p.

## MAINS TRANSFORMERS ALL POST 25p each

Eagle MT12 12-0-12v 50MA 90p  
250-0-250 80 mA. 6.3 v. 3.5 a. 6.3 v. 1 a. or 5 v. 2 a. £2-50  
350-0-350 80 mA. 6.3 v. 3.5 a. 6.3 v. 1 a. or 5 v. 2 a. £3-00  
300-0-300 v. 120 mA. 6.3 v. 4 a. C.T.; 6.3 v. 2 a. £2-25  
MILITARY 200 v. 20 mA. 6.3 v. 1 a. 2 1/2 x 2 1/2 in. 75p  
MIDGET 220 v. 45 mA. 6.3 v. 2 a. 2 1/2 x 2 1/2 in. 80p  
HEATER TRANS. 6.3 v. 11 amp. 85p  
GENERAL PURPOSE LOW VOLTAGE. Tapped output  
at 2 amp., 3, 4, 5, 6, 8, 9, 10, 12, 15, 18, 24 and 30 v. £3-00  
1 amp., 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60 24-00  
2 amp., 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60 24-00  
5 amp., 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60 24-00  
5, 8 and 13 v. 5 amp. £1-20, 3 amp., 8, 5, 8, 10, 15 and  
5-0-5 v. £1-30, Ditto 5 amp. £1-50; 6-0-6 v. 500 mA 90p,  
9 v. 1 amp 95p, 12 v. 300 mA 75p, 12 v. 500 mA 85p,  
12 v. 750 mA 95p, 40v. 1 amp £1-75.  
AUTO TRANSFORMERS. 115v to 230v or 230v to 115v.  
150w. £3-00; 500w £6-25; 750w. £10; 1000w. £15.  
CHARGER TRANSFORMERS. Input 200/250v.  
for 6 or 12v. 1 amp. £1-50; 2 amp. £1-80; 4 amp. £3  
BATTERY CHARGERS. Ready built with leads and clips  
1 1/2 amp. £2; 4 amp. £4.5; 8 amp. £4-50.  
FULL WAVE BRIDGE CHARGER RECTIFIERS:  
6 or 12v. outputs. 1 1/2 amp. 40p; 2 amp. 55p; 4 amp. 85p.

## MAINS ISOLATING TRANSFORMER

Primary 0-110-240v. Secondary 0-240v. 3 amps. 720  
watts. Insulated terminals. Varnish impregnated. Fully  
enclosed in steel case with fixing feet. £10 Carr.  
Famous make. (Value 219) OUR PRICE 50p  
Can be used as 800 watt auto transformers 240-110V.

## SET OF 3 MOTORS FOR COLLARO STUDIO 115 volt TAPE DECK £2-50 Post 50p.

VOLUME CONTROLS 80 Ohm Coax 5p yd.  
5 K. ohms to 2 Meg. LOG or  
LIN. L/S 15p. D.P. 25p.  
STEREO L/S 55p. D.P. 75p.  
EDGE 5K. S.P. Transistor 25p.  
BRITISH AERIALITE  
AERIAL-AIR SPACED  
40 yd. £2; 60 yd. £3.  
FRINGE LOW LOSS 10p per  
Ideal 625 and colour. yd

Wirewound controls 1 1/2 in. diam. 3 watts, 10 ohms to 100K  
British made with long spindles lin. dia 45p ea.  
DUAL CONCENTRIC POT 500K LOG + 500K LIN D.P.  
switch. Inner spindle 3 1/2 in; outer spindle 2 1/2 in. 75p.

## E.M.I. 13 1/2 x 8 in. SPEAKER SALE!

With twin tweeters.  
And crossover. 10  
watt. State 3 or 8  
or 15 ohm. As illustrated. Post 25p

£4-50

With fixed tweeter cone and ceramic  
magnet. 10 watt.  
Bass res. 45-60 ohm. £2-75  
Flux 10,000 gauss.  
State 3 or 8 or 15 ohm. Post 25p



## Bookshelf Cabinet

16 x 10 x 8 in. £6-60  
Teak Veneer Post 35p

## E.M.I. 6 1/2 in. HI-FI WOOFER

8 ohm, 10 watt. Large ceramic magnet  
Special Rubber cone surround.  
Frequency response 30-12,000 cps  
Ideal P.A. Columns.  
Hi-Fi Enclosure Systems, etc.  
Suitable cabinet 12 x 5 x 6 1/2 in.  
Suitable Tweeter £2-00.



## ELAC CONE TWEETER

The moving coil diaphragm gives a good  
radiation pattern to the higher frequencies  
and a smooth extension of total response  
from 1,000 cps to 15,000 cps. Size 3 1/2 x  
3 1/2 x 2 in. deep. Rating 10 watt, 3 ohm.  
Crossover £1.25  
Post 20p



## GOODMANS 8 in. WOOFER

8 ohm 12 watt. Deep cone.  
Heavy ceramic magnet. Bass  
resonance 35 cps. Frequency  
response 30-8,000 cps.  
Hi-Fi bass unit for  
Hi-Fi systems £3-75



LOUDSPEAKERS P.M. 3 OHMS. 7 x 4 in. £1-25; 6 1/2 in. £1-50;  
8 x 5 in. £1-60; 8 in. £1-75; 10 x 6 in. £2-00; 10 in. £2-00.  
SPECIAL OFFER LOUDSPEAKERS! All Brand New.  
3 ohm, 2 1/2 in; 3 1/2 in; 5 in. 8 ohm, 2 1/2 in; 5 in x 3 in;  
5 in. 15 ohm, 3 1/2 in; 5 in; 6 x 4 in; 5 in x 3 in; 7 x 4 in; 8 x 5 in  
25 ohm, 2 1/2 in; 3 in; 5 x 3 in; 5 in. 35 ohm, 2 in; 3 in; 5 in.  
£1 EACH

LOUDSPEAKER VOLUME CONTROL 15 ohm 10 watt  
with 1 1/2 in long threaded bush for wood panel mounting 65p.  
RICIARD ALLAN TWIN CONE LOUDSPEAKERS. 8 in.  
diameter 4W £2-50, 10 in. diameter 5W £2-75; Post 25p.  
12 in. diameter, 6W, £3-30; 3 or 8 or 15 ohm models.  
SPEAKER COVERING MATERIALS. Samples Large S.A.E.  
Horn Tweeters 2-16Kc/s. 8W 8 ohm or 8 ohm £2-20.  
De Luxe Horn Tweeters 2-18 Kc/s. 15W. 8 ohm £3-50.  
TWO-WAY 3,000 c.p.s. CROSS OVERS 3, 8 or 15 ohm £1-25.  
3-WAY CROSSOVER 850 cps and 3000 cps £1-85.

TWO-WAY CROSSOVER NETWORK 3,000 c/s  
With variable tweeter attenuator giving accurate high/low  
frequency balance. Mounted on panel 5 1/2 x 4 1/2 in. with  
control knob, tweeter and woofer leads and input. £3-75 Post  
terminals. Suitable for 3 to 8 ohm impedance. 80p

## ELECTRO MAGNETIC PENDULUM MECHANISM

1-5v d.c. operation over 250 hrs. continuous on 8PE battery.  
Fully adjustable swing and speed. Ideal displays teaching  
electro magnetism or for metronome; strobe etc. 95p, Post 20p

## R.C.S. VALVE AMPLIFIER

2 Stage Triode Pentode valve. 3 watts 3 ohm output. Volume  
on/off and tone controls AC mains. Complete and tested.  
With Loudspeaker. £4-50 Post 25p.

## WEYRAD COILS

P50/CC-40p. RA2W 85p.  
P50/CC-40p. OPTI 85p.  
LFDT4. 85p.  
Printed Circuit 60p. Twin Gang 75p.

COAXIAL PLUG 10p. PANEL SOCKETS 10p. LINE 18p  
OUTLET BOXES, SURFACE MOUNTING 25p.  
BALANCED TWIN RIBBON FEEDER 300 ohms, 5p yd.  
JACK SOCKET Std. open-circuit 14p, closed circuit 23p;  
Chrome Lead Socket 45p. Phone Plugs 5p. Phone Socket 5p  
SOCKETS CHASSIS 3-pin 10p; 5-pin 10p. DIN SOCKETS  
Lead 3-pin 18p; 5-pin 15p. DIN PLUGS 3-pin 18p; 5-pin 25p.  
VALVE HOLDERS 5p; CERAMIC 10p; CANS 5p.

BRITISH FM/VHF TRACING HEART  
88 to 108 Mc/s British made. 2 Tuning  
Stations ready aligned—requires 10.7  
Mc/s IF. Complete with tuning gang.  
Connections supplied but some  
technical experience essential.  
Our Price  
£3-95  
Post 20p.

ALL PRICES INCLUDE VAT MINIMUM POST AND PACKING 20p. CALLERS WELCOME

# RADIO COMPONENT

Illustrated Colour Brochure, Radio Books & Component Lists 10p. Written guarantee.

# ALL OUR PRICES INCLUDE V.A.T.

## E.M.I. WOOFER AND TWEETER KIT

THE PAIR. Post 25p.  
(Available separately.)  
**£6-75** Woofer £2-25; Tweeter £1-90).

Comprising a fine example of a Woofer 10 1/2 x 8 1/2 in. with a massive Ceramic Magnet. 440c. Gauss 18,000 lines. Aluminium Cone centre to improve middle and top response. Also the E.M.I. Tweeter 8 1/2 in. square has a special lightweight paper cone and magnet flux 10,000 lines. Crossover condenser and full instructions supplied.

Impedance Standard 8 ohms  
Maximum power 12 watts  
Useful Response 25 to 18,000 cps  
Bass Resonance 45 cps

**SUITABLE ENCLOSURE 20 x 18 x 9 in.**  
MODERN DESIGN. TEAK WOOD FINISH. **£10-50** Post 45p



## ELAC 8 in. or 10 x 6 in. HI-FI SPEAKER



Dual cone plasticised roll surround. Large ceramic magnet. 50-18,000 cps. Bass resonance 55 cps. 8 ohm impedance. 8 in. 10 watts **£3-75**

## TEAK VENEER HI-FI SPEAKER CABINETS

### Fluted Wood Fronts

MODEL "A". 20 x 18 x 9 in.  
For 12 in. dia. **£10-50** Post 10 in. speaker. 45p

MODEL "B". 16 x 10 x 9 in.  
For 13 x 8 in. or **£6-60** 35p  
MODEL "B2" ditto. Triangular corner version.


MODEL "C". 16 x 8 x 6 in.  
For 8 x 5 in. **£5** 25p  
LOUDSPEAKER CABINET  
WADDING 18 in. wide. 20p ft.



Callers only—HI-FI CABINET  
Baker Recommended 12 inch Enclosure 4 cubic ft. Size 30 x 20 x 12 in. Teak Finish Fluted Front. **£18-50**
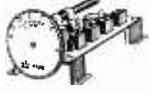
## BARGAIN AM TUNER.

Medium Wave.  
Transistor Superhet **£4-95**  
Ferrite aerial. 9 volt.



## BARGAIN 4 CHANNEL TRAnsISTOR D I O N O MIKER

Add musical highlights and sound effects to recordings. Will mix Microphone, records, tape and tuner with separate controls into single output. 9 volt battery operated. **£4-50**



## STEREO VERSION OF ABOVE £5-95.


## BARGAIN FM TUNER.

SS-108 Mc/s Six Transistor. 9 volt. Printed circuit. Calibrated slide dial tuning. Walnut Cabinet. **£12-85**


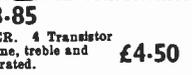
## BARGAIN FM TUNER. £8-85

As above less cabinet.  
**BARGAIN 3 WATT AMPLIFIER.** 4 Transistor Push-Pull Ready built with volume, treble and bass controls. 18 volt battery operated. **£4-50**



## WAFER HEATING ELEMENTS THIN

OFFERING 1001 USES for every type of heating and drying applications in the home, garage, greenhouse, factory (available in manufacturing quantities). Approx. size 10 1/2 x 8 1/2 x 1/4 in. Operating voltage 200/250V. a.c. 250 watts approx. Printed circuit element enclosed in asbestos fitted with connecting wires. Completely flexible providing safe Black heat. British-made for use in photocopyers and print drying equipment. Ideal for home handmen and experimenters. Suitable for Heating Pads, Food Warmers, Convector Heaters, etc. Must be clamped between two sheets of metal or asbestos, etc., to make efficient clothes dryers, towel rails—ideal for airing cupboards. Ideal for anti-frost device for the garage—preventing frozen radiators or acting as oil sump heater. Use in the greenhouse for seed raising and plant protection. Invaluable aid for bird houses, incubators, etc., can be used in series for lower heat. Or in parallel for higher heat applications.

**ONLY 40p EACH (FOUR FOR £1-50)**  
ALL POST PAID—Discounts for quantity.

## BAKER MAJOR 12" £9-90



Post Free  
30-14,500 c/s. 12 in. double cone, woofer and tweeter cone together with a BAKER ceramic magnet assembly having a flux density of 14,000 gauss and a total flux of 145,000 Maxwells. Bass resonance 40 c/s Rated 20 watts. NOTE: 3 or 8 or 15 ohms must be stated.

Module kit, 30-17,000 c/s with tweeter, crossover, baffle and instructions. **£12-50**

Please state 3 or 8 or 15 ohms. Post Free

## "BIG SOUND" BAKER SPEAKERS

Robustly constructed to stand up to long periods of electronic power. As used by leading groups. Useful response 30-13,000 cps. Bass Resonance 55 cps.

GROUP "25" **£8-80**  
12 in. 25 watt  
3, 8 or 15 ohms. Post Free

GROUP "35" **£9-90**  
12 in. 35 watt  
3, 8 or 15 ohms. Post Free

GROUP "50" **£20-00**  
15 in. 50 watt  
3 or 15 ohms.

GROUP 50/12 in. **£16-00**  
50 watt 8 or 15 ohms

Group + PA Cabinets in stock. Callers only. Send for Leaflet.



## MAJOR 100 WATT ALL PURPOSE TRANSISTOR AMPLIFIER

All purpose transistorised. Ideal for Groups, Disco and P.A. 4 inputs speech and music. 4 way mixing. Output 8/15 ohm. a.c. Mains. Separate treble and bass controls. Guaranteed. Details SAE. **£49** Carr. £1-00



## CALLERS ONLY! DE LUXE 100 WATT VALVE AMPLIFIER CHASSIS

4 input 10 wide range controls. For Mixes, Discos, Organs, Guitars, etc. 4, 8 & 16 ohm loudspeakers matching £89-00.

## THE "INSTANT" BULK TAPE ERASER & HEAD DEMAGNETISER.

Suitable for cassettes, and all sizes of tape reels. A.C. mains 200/250V. Leaflet S.A.E. **£3-50** Post 20p



## QUALITY LOUDSPEAKER ENCLOSURE

Teak veneered finch thick wood cabinet. Size 18 1/2 in x 18 1/2 in x 8 1/2 in. Weight 23 lbs. This cabinet features a wide mesh Silver Grill covering a separate compartment for mounting Tweeters or Mid-Range Horns. The fully sealed bass compartment is cut out for a 8 inch Woofer. £7-50 Carr. 85p. Rosewood Version £8-50. Carr. 85p.



## SPECIAL OFFER 95p. Post 25p.

100 Ohm 20 watt Rheostat 2 1/2 in diam. Ceramic Former. Screw Terminals 1/4 in. diam. spindle.

## REVERSIBLE 4 POLE MOTOR

1,400 r.p.m. Reversible 42 Watt, spindle 1 1/2" x 7/32", size 3 1/2" x 3". As illustrated, 240v. AC mains. Post 25p **£2-25**

## E.M.I. GRAM MOTOR

120v. or 240v. A.C. 2,400 rpm. 2-pole 70mA. Size 2 1/2 x 2 1/2 x 2 1/2 in. **£1-00** Post 25p.

## BAKER HI-FI SPEAKERS HIGH QUALITY — BRITISH MADE

### REGENT 12 in. 15 watts

An inexpensive unit for the beginner in high fidelity and for general purposes. May be used to improve any Radio, Amplifier, Hi-Fi or Television receiver.

Bass Resonance 45cps  
Flux Density 12,000gauss  
Useful response 45-13,300cps  
3 or 8 or 15 ohm models.

**£8-80** Post Free



### DE-LUXE Mk II 12 in 15 watts

Especially designed to provide full range reproduction at an economical cost. Suitable for use with any high fidelity system. Built-in concentric tweeter cone. Bass Resonance 30cps  
Flux Density 14,000gauss  
Useful response 25-16,000cps  
8 or 15 ohms models.

**£11** Post Free



### SUPERB 12 in. 20 watts

A high quality loudspeaker. Its remarkable low cone resonance ensures clear reproduction of the deepest bass. Fitted with a special copper drive and concentric tweeter cone resulting in full range reproduction with remarkable efficiency in the upper register. Bass Resonance 25cps  
Flux Density 16,500gauss  
Useful response 20-17,000cps  
8 or 15 ohms models.

**£16-50** Post Free



### AUDITORIUM 12 in. 25 watts

A full range reproducer for high power Electric Guitars, public address, multi-speaker systems, electric organs. Ideal for Hi-Fi and Disco-theques. Bass Resonance 35cps  
Flux Density 15,000gauss  
Useful response 25-18,000cps  
8 or 15 ohms models.

**£15-40** Post Free



### AUDITORIUM 15 in. 35 watts

A high wattage loudspeaker of exceptional quality with a level response to above 8,000 cps. Ideal for Public Address, Discotheques, Electronic instruments and the home HI-FI. Bass Resonance 35cps  
Flux Density 15,000gauss  
Useful response 20-14,000cps  
8 or 15 ohms models.

**£22** Post Free



Hi-Fi Enclosure Manual containing 20 plans, designs, crossover data and cubic tables. 42p. Post Free.

CUSTOMERS FREE CAR PARK OPEN 9-6. WEDNESDAY 9-1. SATURDAY 9-5. Closed for lunch 1-15-2-30

# SPECIALISTS

(Exports Remit cash and extra postage.) **337 WHITEHORSE ROAD . CROYDON** Telephone 01-684-1665

Buses 50, 68, 159. Rail Selhurst





# PADGETTS RADIO STORE

## OLD TOWN HALL, LIVERSEDGE, YORKS WF15, 6PQ

TEL. HECKMONDWIKE 405285

Small 24 Volt Motor with Gear Train 60p Post Paid.

Small 24 Volt Blower Motor. 50p Post Paid.

Two Students Wireless Procedure Training Sets, each unit in a small wood box and comprises Mike, Single LR Phone and connectors £1.30 Post Paid.

Small Clock Type Sangamo Weston 200-250 v. 200 r.p.m. Mains Motor with Gear Train (ex-Slot Machine). Fair condition. 60p Post Paid.

Used 19in. TV Tubes Type AW47-91. Perfect condition. Six months guarantee. £3.00 Carr. Paid.

Complete untested TV Sets 19in 405 Line Types £3.50 Carr. Paid.

19in 625 Line Types untested. Complete with UHF Tuner. £5.50 Carr. Paid.

Speakers Removed from TV Sets, all 3 ohm 2½ watts. 7 x 4in. 6 x 4in, 8 x 2½in. All at 27p each. Post and packing 12p.

Top Quality Tapes. Reel to Reel. 5in L.P. 55p. 7in ST 66p, 7in L.P. 80p. Post on any tape 12p.

**BERNARDS BOOKS.** Send S.A.E. for FREE LIST.

Ex Equipment Valves all Tested before despatched. 3 months guarantee on all valves. Single valves post 3p, over post paid.

ARP12	6p	EF184	20p	PY801	17p
DY86	20p	PCF80	6p	PY82	10p
EB91	5p	PCC84	6p	PY33	20p
EF80	10p	PCL82	15p	UI91	20p
EBF89	15p	PCL84	15p	6BW7	12p
ECC81	12p	PCL85	20p	6F23	15p
ECC82	12p	PL36	17p	30F5	12p
EY86	20p	PY81	10p	30FL1	20p
EF183	20p	PY800	17p	30P19	10p

ABOVE PRICES INCLUDE V.A.T.

**NEW**  
ALL  
SILICON!



PRACTICAL  
WIRELESS

## ELECTRONIC IGNITION SYSTEM

This Capacitor-Discharge Electronic Ignition System was described in *Practical Wireless*, and has proved extremely popular.

The kit is supplied with a ready-drilled roller-tinned printed-circuit board and fully machined die-cast case with AMP Electrical Spade Connector Block together with a custom wound transformer, first grade components and full constructional details.

The original circuit employed Germanium Power Transistors for the negative earth version. WE OFFER SILICON P.N.P. POWER DEVICES AT NO EXTRA COST! All components are available separately. Case size 4½" x 3½" x 2". Complete assembly and construction manual free with kit, available separately 25p.

SUITABLE FOR 12V SYSTEMS WITH NEG. OR POS. EARTH.

PRICE: £9.50 U.K. ORDERS PLEASE ADD VAT

Quantity Discounts:

Trade and Overseas	1-5 Nett	6-9 less 10%
Enquiries Invited	10-49 less 15%	50-99 less 20%
Mail Order Only.	100-999 less 25%	1000 up less 30%

PLEASE STATE POS. OR NEG. EARTH WHEN ORDERING



**DABAR ELECTRONIC PRODUCTS**

98, LICHFIELD STREET,  
WALSALL, STAFFS. WS1 1UZ

# TRANSFORMERS

## SAFETY MAINS ISOLATING TRANSFORMERS

Ref. No.	VA (Watts)	Weight lb oz	Size cm.	£	P & P
07	20	1 8	7.0 x 6.0 x 6.0	2.55	30
149	60	3 12	9.9 x 7.7 x 8.6	3.79	36
150	100	5 8	9.9 x 8.9 x 8.6	4.17	52
151	200	8 0	12.1 x 9.3 x 10.2	7.09	52
152	250	13 12	12.1 x 11.8 x 10.2	9.25	67
153	350	15 0	14.0 x 10.8 x 11.8	12.32	82
154	500	19 8	14.0 x 13.4 x 11.8	17.87	-
155	750	29 0	17.2 x 14.0 x 14.0	24.31	-
156	1000	38 0	17.2 x 16.6 x 14.0	29.87	-
158	2000	60 0	21.6 x 15.3 x 18.1	49.25	-

PLEASE NOTE  
NEW ADDRESS  
AS BELOW

## AUTO TRANSFORMERS

Ref. No.	VA (Watts)	Weight lb oz	Size cm.	Auto Taps	£	P & P
113	20	1 0	5.8 x 5.1 x 4.5	0-115-210-240	1.34	22
64	75	2 4	7.4 x 6.7 x 6.1	0-115-210-240	2.64	30
4	150	3 4	8.9 x 7.7 x 7.7	0-115-200-220-240	3.18	36
66	300	6 4	9.9 x 9.6 x 8.6	..	6.19	52
67	500	12 8	12.1 x 11.2 x 10.2	..	9.20	67
84	1000	19 8	14.0 x 13.4 x 14.3	..	16.71	82
93	1500	30 4	14.0 x 15.9 x 14.3	..	24.19	-
95	2000	32 0	17.2 x 16.6 x 14.0	..	31.57	-
73	3000	40 0	21.6 x 13.4 x 18.1	..	39.17	-

## CASED AUTO TRANSFORMERS

115V 500W enclosed transformer, with mains lead and two 115V outlet sockets. £9.49. P & P 67p. 20 Watt version £2.02 P & P7p

## TRANSFORMERS

### PRIMARY 240-250 VOLTS 12 AND OR 24 VOLT RANGE

Ref. No.	Amps.	Weight lb oz	Size cm.	Secondary Windings	£	P & P
111	0.5	0.25	8 4	8 x 2.9 x 3.5 0-12V at 0.25A x2	1.34	22
213	1.0	0.5	1 4	6.1 x 5.8 x 4.8 0-12V at 0.5A x2	1.58	22
71	2	1	1 2	7.0 x 6.4 x 6.1 0-12V at 1A x2	2.09	22
18	6	2	1 2	8.3 x 7.7 x 7.0 0-12V at 2A x2	2.95	30
70	6	3	4	8.9 x 8.0 x 7.7 0-12V at 3A x2	3.52	42
108	8	4	5	8.9 x 8.9 x 8.6 0-12V at 4A x2	3.96	52
72	10	5	6	4 9.9 x 9.6 x 8.6 0-12V at 5A x2	4.67	52
116	12	6	6	12 9.9 x 10.2 x 8.6 0-12V at 5A x2	5.61	52
17	16	8	11	12 12.1 x 9.9 x 10.2 0-12V at 8A x2	7.22	52
115	20	10	11	14.0 x 9.6 x 11.8 0-12V at 10A x2	9.20	67
187	30	15	18	14.0 x 12.1 x 11.8 0-12V at 15A x2	16.94	82
226	60	30	32	0 17.2 x 15.3 x 14.0 0-12V at 30A x2	31.28	-

### 30 VOLT RANGE

Ref. No.	Amps.	Weight lb oz	Size cm.	Secondary Taps	£	P & P
112	0.5	1 4	6.1 x 5.8 x 4.8	0-12-15-20-24-30V	1.56	22
79	1.0	2 4	7.0 x 6.7 x 6.1	..	2.11	36
3	2.0	3 4	8.9 x 7.7 x 7.7	..	3.18	36
20	3.0	4 8	9.9 x 8.3 x 8.6	..	3.96	42
21	4.0	6 4	9.9 x 9.6 x 8.6	..	4.67	52
51	5.0	6 12	12.1 x 8.6 x 10.2	..	5.83	52
117	6.0	8 0	12.1 x 9.3 x 10.2	..	6.94	52
88	8.0	12 0	12.1 x 11.8 x 10.2	..	9.00	67
89	10.0	13 12	14.0 x 10.2 x 11.8	..	11.36	67

### 50 VOLT RANGE

Ref. No.	Amps.	Weight lb oz	Size cm.	Secondary Taps	£	P & P
102	0.5	1 12	7.0 x 6.4 x 6.1	0-19-25-33-40-50V	2.09	30
103	1.0	2 12	8.3 x 7.4 x 7.0	..	3.08	36
104	2.0	5 8	9.9 x 8.9 x 8.6	..	4.26	42
105	3.0	6 12	9.9 x 10.2 x 8.6	..	5.79	52
106	4.0	10 0	12.1 x 10.5 x 10.2	..	7.69	52
107	6.0	12 0	14.0 x 12.1 x 11.8	..	11.38	67
118	8.0	18 0	14.0 x 12.7 x 11.8	..	12.40	97
119	10.0	25 0	17.2 x 12.7 x 14.0	..	18.62	-

### 60 VOLT RANGE

Ref. No.	Amps.	Weight lb oz	Size cm.	Secondary Taps	£	P & P
124	0.5	2 4	7.0 x 6.7 x 6.1	0-24-30-40-48-60	2.12	36
126	1.0	3 4	8.9 x 7.7 x 7.7	..	2.97	36
127	2.0	6 4	9.9 x 8.3 x 8.6	..	4.67	42
125	3.0	8 12	12.1 x 9.9 x 10.2	..	7.11	52
123	4.0	13 12	12.1 x 11.8 x 10.2	..	9.20	67
40	5.0	12.00	14.0 x 10.2 x 11.8	..	10.83	87
120	6.0	15 8	14.0 x 12.1 x 11.8	..	13.35	82
121	8.0	25.00	14.0 x 14.7 x 11.8	..	15.01	*
122	10.0	35 0	17.2 x 12.7 x 14.0	..	22.10	*
189	12.0	29.00	17.2 x 14.0 x 14.0	..	24.74	*

### MINIATURE TRANSFORMERS WITH SCREENS P & P

Ref. No.	MA.	Weight lb oz	Size cm.	VOLTS	£	P & P
238	200	2	2.8x2.6x2.0	3-0-3	1.44	10
212	1A 1A	1	4 6.1x5.8x4.8	0-6-0-6	1.67	22
13	100	4	3.9x2.6x2.9	9-0-9	1.23	10
235	330,330	4	4.8x2.9x3.5	0.9-0.9	1.67	10
207	500, 500	1	00 6.1x5.4x4.8	0.8-9.0-8-9	2.23	22
208	1A 1A	1	12 7.0x5.4x6.1	0.8-9.0-8-9	3.00	30
236	200, 200	1	4 4.8x2.9x3.5	0-15, 0-15	1.67	10
214	300, 300	1	4 6.1x5.8x4.8	0-20, 0-20	1.76	22
221	700 (D.C.)	1	8 7.0x6.1x6.1	20-12.0-12-20	1.55	30
206	1A 1A	2	12 8.3x7.7x7.0	0-15-20, 0-15-20	4.05	36
203	500, 500	2	4 8.3x7.0x7.0	0-15-27, 0-15-27	3.10	38
204	1A 1A	3	4 8.9x7.7x7.7	0-15-27, 0-15-27	3.15	38

PLEASE ADD 10% FOR V.A.T.  
INCLUDING P. & P.

# BARRIE electronics

3, THE MINORIES, LONDON EC3N 1BJ

TELEPHONE: 01-488 3316/8

NEAREST TUBE STATIONS: ALDGATE & LIVERPOOL ST.

# If you're looking for trouble you needn't look any further.



It's not only technicians who can see the finer points of Eagle multi-meters.

Every handyman notices them too.

They're easy to read.

They're tough.

Their construction comes up to laboratory standards.

Even our inexpensive pocket sized models have features you'd usually only find on professional equipment.

Take a look through our catalogue.

You'll see over twenty models.

Specifications that would impress the most experienced technician.

And a price range that takes in amateurs as well as professionals.

We guarantee every one for two years.

With parts to service them in no time.

So you can confidently find fault in anything.

**Eagle**  
international

The name on Britain's widest range of electronic equipment.

Please send me the Eagle electronics catalogue containing the complete range of test equipment.

Name \_\_\_\_\_


Address \_\_\_\_\_

PW1

Eagle International Precision Centre Heather Park Drive  
Wembley HA0 1SU Telephone 01 903 0144

# Project 80


a brilliant new concept in modular hi-fi

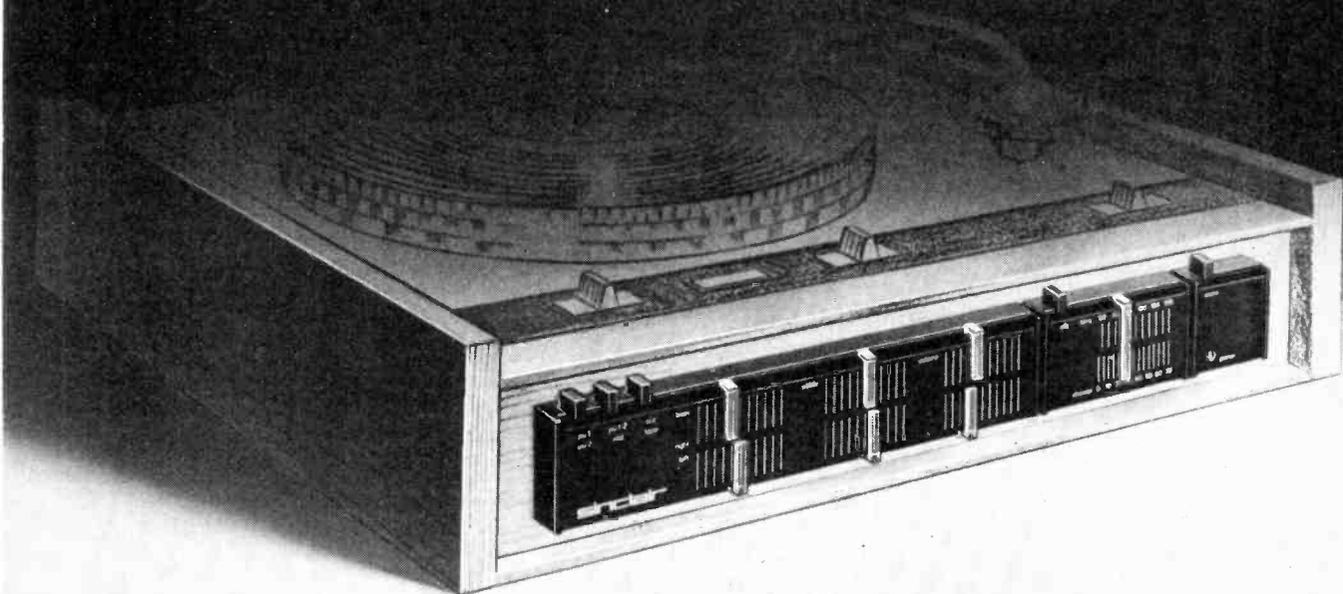

Project 80 is going to be the ultimate in modular hi-fi construction for a very long time to come. It combines the qualities most demanded of any modern domestic system – good circuitry, reliability and fine performance – with other features to be found nowhere else in the world. For example, *compactness* – Project 80 control units are  $\frac{3}{4}$ " deep  $\times$  2" high, and each one is completely self-contained.

*Elegance* – all of Sinclair's design leadership has been concentrated on producing designs of outstanding functional elegance unsurpassed for styling and simplicity. *Flexibility* – the size and styling of Project 80 modules makes them the most versatile units ever. Combine them how you will, where you will, the Project 80 System of your choice gives you the best.

**sinclair**

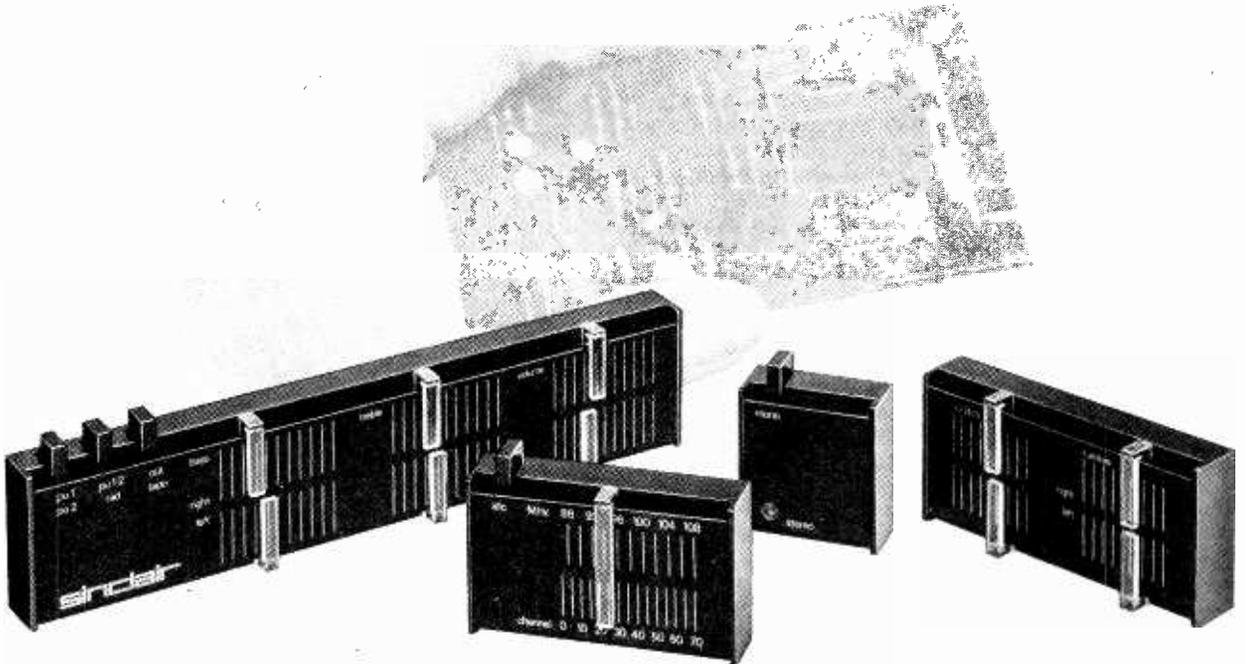

## technically the world's most advanced

Project 80 gives you choice from a range of 9 different modules for combining in a variety of ways to suit your requirements. The Stereo 80 is a versatile pre-amp control unit designed to meet all domestic hi-fi requirements including tape monitoring, high sensitivity magnetic cartridge input, and of course, individual slide controls on each channel for precise output matching. By separating the F.M. tuner and stereo decoder, useful economies can be effected where stereo radio reception is not needed. Two power amplifiers - Z.40 (18 watts RMS continuous into 4 ohms using 35V) and Z.60 (25 watts RMS continuous into 8 ohms using 50V) are available with choice of 3 different power supply units. The PZ.8 with its virtually indestructible circuitry is particularly recommended. For the final word in system building, the Active Filter Unit puts the finishing touch of quality to what are easily the world's most technically advanced hi-fi modules. Any further units likely to be added to Project 80 range will be compatible with those already available.

### Guarantee

If, within 3 months of purchasing any product direct from us, you are dissatisfied with it, your money will be refunded on production of receipt of payment. Many Sinclair appointed stockists also offer this guarantee. Should any defect arise in normal use, we will service it without charge.

# sinclair

Sinclair Radionics Ltd  
London Rd. St Ives  
Huntingdon PE17 4HJ  
Telephone  
St Ives (0480) 64646

**Stereo 80 Control Unit** Size - 260 · 50 · 20mm (10 $\frac{1}{2}$  · 2 ·  $\frac{3}{8}$ ins)  
Finish - Black with white indicators and transparent sliders Inputs - Magnetic pick up 3mV RIAA corrected. Ceramic pick up 350mV Radio 100mV; Tape 30mV Signal/noise ratio - 60dB Frequency range - 20Hz to 15KHz 1dB, 10Hz to 25KHz · 3dB Power requirements - 20 to 35 volts Outputs - 100mV AB monitoring for tape Controls - Press button tape radio and P U Sliders on each channel for volume bass treble R R P (add £1 19 V A T) **£11.95**

**Project 80 FM Tuner** Size - 85 · 50 · 20mm (3 $\frac{1}{4}$  · 2 ·  $\frac{3}{8}$ ins)  
Tuning range Dual varicap - 87.5 to 108MHz Detector - 1 C balanced coincidence One I.C. equal to 26 transistors Distortion - 0.2% at 1KHz for 30% modulation 4 pole ceramic filter in I.F. section Aerial impedance - 75  $\Omega$  or 240 300  $\Omega$  Sensitivity - 5 microvolts for 30dB S/N ratio Output - 300mV for 30% modulation Power requirements - 25 to 35 volts R R P (add £1 19 V A T) **£11.95**

**Project 80 Stereo Decoder** Size - 47 · 50 · 20mm (1 $\frac{7}{8}$  · 2 ·  $\frac{3}{8}$ ins) One 19 transistor I.C. Channel separation greater than 30dB Power requirements - 25V Output 150mV per channel R R P (add 74p V A T) **£7.45**

**Active Filter Unit** Separate controls on each channel Size - 108 · 50 · 20mm (4 $\frac{1}{4}$  · 2 ·  $\frac{3}{8}$ ins) Voltage gain - minus 0.2dB Frequency response - 40Hz to 22KHz controls minimum Distortion - at 1KHz - 0.03% using 30V supply H F cut off (scratch) - 22 KHz to 5.5KHz, 12dB/oct slope L.F. cut off (rumble) - 28dB at 20Hz 9dB/oct slope R R P (add 69p V A T) **£6.95**

**Z.40 Power Amplifier** Size - 55 · 80 · 20mm (2 $\frac{1}{4}$  · 3 $\frac{1}{4}$  ·  $\frac{3}{8}$ ins) 9 transistors Input sensitivity - 100mV Output 18 watts RMS continuous into 4  $\Omega$  (35V) Frequency response - 30Hz-100KHz; 3dB S/N ratio - 64dB Distortion - at 10 watts into 8  $\Omega$  less than 0.1% Power requirements - 12 to 35 volts, built in protection against overload R R P (add 54p V A T) **£5.40**

**Z.60 Power Amplifier** Size - 55 · 98 · 15mm (2 $\frac{1}{4}$  · 3 $\frac{3}{8}$  ·  $\frac{3}{8}$ ins) 12 transistors Input sensitivity - 100-250mV Output - 25 watts RMS continuous into 8  $\Omega$  (50V) Distortion - typically 0.03% Frequency response - 15Hz to more than 200KHz; 3dB S/N ratio - better than 70dB Built-in protection against transient overload and short circuiting Load impedance - 4  $\Omega$  min safe on open circuit R R P (add 69p V A T) **£6.95**

**Power Supply Units** PZ.8 Stabilised Re-entrant current limiting makes damage from overload or even direct shorting impossible Normal working voltage (adjustable) 50V R R P £7.98 - 79p V A T Without mains transformer PZ.6 35V stabilised R R P £7.98 - 79p V A T PZ.5 30V un-stabilised R R P £4.98 - 49p V A T

To Sinclair Radionics Ltd. St. Ives Huntingdon PE17 4HJ

Please send post paid \_\_\_\_\_

for which I enclose Cash/Cheque for £ \_\_\_\_\_ including V A T \_\_\_\_\_

Name \_\_\_\_\_

Address \_\_\_\_\_

# SURPRISE!

**P**ROBABLY one of the most interesting features about our activities is that there is always a chance of the unexpected happening. It may be an unusual DX contact, or a circuit design that behaves in a different manner than expected. It could be that someone comes up with a new integrated circuit that can replace a mass of discrete circuitry. The element of surprise always helps to make a magazine interesting; readers are incredibly thirsty for such information because it is born out of curiosity (see last month's leader). Whilst curiosity is the expectation, you may describe surprise as "unexpectation"—if there was such a word.

At the same time, to preserve the value of surprise, one must exercise some degree of secrecy until it is reasonably sensible to release the full details. However, we often find ourselves caught between these two positions when we have to judge how much we can tell you in advance and how much to leave until the last minute.

For this reason, little information was released about Tele-Tennis, much to the disappointment of our competitors and those who have a commercial interest, and little was released about the "PW Super Separates" that are being started in this issue. So far, we can tell you that the "PW Derby" is a high quality amplifier designed specially for us and described by the co-designer of the "Gemini" amplifier. What follows in future articles in this series must remain secret until the time is right to let readers know.

However, we can tell you that these designs are of a very high standard. For those readers who have a good domestic set-up already, we can probably help you to fill the gaps. If you are looking for a second set-up for the bedroom or spare room, then stay tuned to P.W. every month.

The great advantage of the "P.W. Super Separates" is their flexibility; you don't have to spend a lot of money to build a complete integrated unit, that seems to go on endlessly for about a year. Take your choice and we shall try to publish all the required details of each project.

What better to start with than a stereo headphone amplifier, rapidly becoming the accepted way of personal listening, where the 20 or 30 watt amplifier is more expensive and often too much for personal listening. For information on future projects watch our advance notices each month.

Before packing my bags for a fortnight's holiday, there is just one more point. We understand that some readers are having difficulty in obtaining P.W. and that the Tele-Tennis game has created a rapid demand as soon as it appears. If there are none left on display in your news-agents shop, ask the assistant if they have any more. The chances are that there may be some in the stockroom. Better still, why not place a regular order or take out a subscription and be sure of it.

M. A. COLWELL—*Editor*.

The September issue brings you to the second in the "P.W. Super Separates"—the P.W. Epsom Short Wave Receiver, designed to provide wide coverage of both amateur and broadcast transmissions; a very useful practical article on the use of field transistors; an add-on "squelch" for suppressing noise in audio systems; and of course part 3 of "Tele-Tennis".

Further details on page 327

(All advanced details are subject to the current industrial situation)

# NEWS...

## BBC and quadraphony

**T**HE BBC has been working for some time on the possible applications of quadraphony to broadcasting. A number of four channel recordings have been made using different production techniques and several transmission systems have been examined. Unfortunately, no system has yet been devised which would enable quadraphonic material to be broadcast from a single v.h.f. transmitter while at the same time providing fully satisfactory reception to listeners using monophonic or stereophonic receivers.

The results obtained with some quadraphonic recordings are impressive, and there is considerable public interest in this development. To enable those who were interested to hear a number of recent BBC quadraphonic recordings, there was an experimental broadcast from 12.05 am to 1 am on the early morning of Saturday, 6 July. Two groups of stereo transmitters were used, Radio 2 carrying the left and right front signals, with Radio 3 carrying the left and right rear signals. To take full advantage of the quadraphonic transmission, listeners required two complete stereophonic receivers, one tuned to Radio 2, feeding the 'front' loudspeakers; a second stereo receiver tuned to Radio 3 connected to the 'rear' speakers.

The special programme included a variety of different musical items as well as some drama and outside broadcast material. The BBC would be grateful for reports from listeners who were able to hear this experimental broadcast.

It must be emphasised that there is no possibility of a regular quadraphonic service on the basis of two separate transmitter networks, but the BBC will continue its investigations into the possibility of a system to provide quadraphonic programmes from a single transmitter, without degrading the results obtained by those with mono or stereo receivers.

## Interface 74

TEXAS Instruments recently held a very interesting seminar called 'Interface 74'.

Several excellent lecturers spoke on new bipolar IC's and their applications and a very interesting talk on new optoelectronic products by Martin Abbott followed.

An ultrasonic remote-controlled-colour TV was demonstrated by Clive Hoggar, Product Marketing Manager (Consumer IC's) and this was followed by a talk on power transistors presented by John Thorogood and Bryan Norris, Texas Instruments' Applications Manager.

The "star of the day" was Pauline Hamill, Product Marketing Manager for Small Discrete Products. She gave a most interesting lecture (despite a dodgy radio mike!) on Timtor transistors to over 300 male delegates who sat in awed silence. At the end of her talk, Pauline received a great round of applause. (think what courage you would need fellas, to lecture to over 300 women!) Well done Pauline!

Millis Miller, in a lilting Texan accent told the delegates all about the various applications of optoelectronics and this was followed by a talk describing new MOS products.

The day's lectures finished with a question and answer session chaired by Richard Mann, the "mann" who very ably organised and produced the seminar. Richard is the Market Communications Manager of Texas Ltd.

All the delegates were presented with a very comprehensive Data Pack.


Texas hold these seminars every year and they're jolly good value for money, so if you want details of future presentations, contact T. I. Limited at Manton Lane Bedford (0234-67466).

## Preston rally

ON 18th August Preston Amateur Radio Society are holding their mobile rally at Deepdale Primary School, St. Stephen's Rd., Preston.
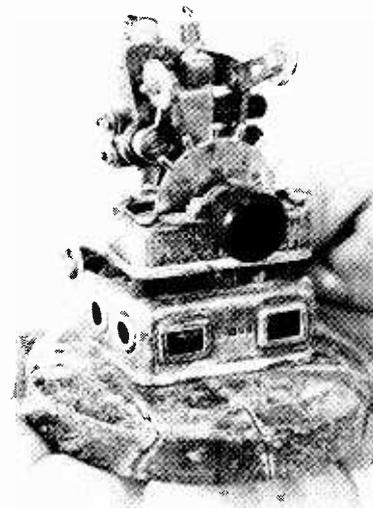
## Marconi Exhibition at Science Museum

INCLUDED in the Science Museum, London, exhibition commemorating the centenary of Guglielmo Marconi is a case of personalia like this silver table lighter made in the form of a disc discharger used in the Marconi Company's early long range transmitters. A number of these lighters were made for presentation to delegates attending a conference arranged by the Company in 1912.



(Science Museum photo).

## Lee Products

LEE PRODUCTS (GB) are marketing a range of Aiko home entertainment and ICE products under an agreement with the Japanese manufacturer.

Aiko products are added to the existing Elizabethan, Elpico and Dulci brand names.

The 14 Aiko products range from portable cassette tape recorders to a stereo cassette deck operating with the Dolby system and priced at £135 including VAT.

The announcement of the Aiko range coincides with Lee Products move to their new premises at Dallas House, Aintree Road, Perivale, Middlesex.

## Sinclair price drop

EUROPE's largest manufacturer of pocket calculators, Sinclair, has cut the retail price of its "Cambridge" model to £24.95 plus VAT.

Mr. R. Helmer, Sinclair's marketing manager stated recently that the firm's motive for making the price reduction is to open up a vast new market potential which recent research shows exists around the £20 mark.

The firm state that they are able to bear the price cut because of the scale already achieved on the production of the Cambridge. More than 200,000 units have been sold since its introduction last August.

Mr. Helmer said that 17,000 of the 25,000 units manufactured every month were required for export.

The Cambridge is still available in kit form at £14.95 plus VAT.

## Our Front Cover

THE Zero 100 SB automatic single player featured on our cover this month was kindly loaned by Garrard Engineering. The Zero 100 was first introduced in 1971 and has established an excellent reputation, especially for its tangential tracking arm. This unique arm, with its pivoted head is claimed to economically reduce tracking error and harmonic distortion to virtually zero.

The Zero 100 SB retains the refinements included in the earlier decks but has the added advantage of belt drive and an automatic record counter to help monitor stylus wear.

Recommended retail price of the unit, fitted with a Shure M93E cartridge is £69.72. Further information may be obtained from Garrard Engineering Ltd., Newcastle Street, Swindon, Wiltshire.

### SORRY WE ARE LATE!

We apologise for the late appearance of Practical Wireless. The delay has been caused by an industrial dispute within the printing industry.

# two metre CONVERTER

L. CASE  
G8BJQ

A COMMON procedure used to obtain reception of signals in the 2m Amateur band is to employ a crystal-controlled converter the output of which is coupled to the aerial input of a standard short wave communications receiver, which is utilised as a tunable IF strip.

Commercial converters are, in the main, quite expensive and in some cases can cost nearly as much as the listener's main receiver. The converter to be described can be built at less than half the cost of its commercial counterpart but, unfortunately, many constructors have a great deal of difficulty, if not in the actual constructional work involved, then in the alignment of the various stages of the converter.

Perhaps the biggest problem in attempting to construct a published design is the duplication of the low inductance coils and persuading them to resonate at the desired frequencies. The problem is made doubly difficult, if not impossible, by the lack of the appropriate test equipment.


On first inspection of the various component catalogues and coil data available no coils are specifically manufactured for frequencies higher than approximately 80 MHz. The types available nearest to our requirements are the Denco Range 7 coils, intended initially for valve usage to cover a frequency range extending up to 78 MHz. Comparatively large parallel capacitance is used to achieve this coverage and simple calculations reveal that, using much smaller values of parallel capacitance, coverage to at least 150 MHz was possible. With this fact in mind the present design was evolved.

## THE CIRCUIT

The circuit of the complete converter is shown in Fig. 1. The RF stage Tr1 employs an AF139 in the common-base mode with untuned input from the aerial and a double-tuned bandpass arrangement at the output to feed the mixer, top capacitance coupling being provided by means of C4. Extra gain could have been achieved by employing the same transistor in the common-emitter configuration, but this would have required some form of neutralisation so in the

interests of simplicity this was not thought to be desirable. The circuit used has been found, in practice, to provide ample gain and has at no time showed any signs of instability when using such diverse aerials as random lengths of wire and multi-element Yagi arrays.

The crystal oscillator stage Tr3 employs an AF115 as does the common-base frequency multiplier Tr4. The frequency of oscillation is controlled by the quartz crystal X1, C10 providing the necessary feedback capacitance to maintain oscillation. The circuit will not oscillate unless the tuned circuit L4/C9 is resonant near to the frequency of the crystal, which in this case is 38.666 MHz, adjustment of the tuned circuit being achieved by means of the core in L4. The 38.666 MHz output is then link coupled to the tripler stage Tr4, the output of which is tuned to 116 MHz and link coupled via L5 to the gate circuit of the 2N3819 FET mixer Tr2.

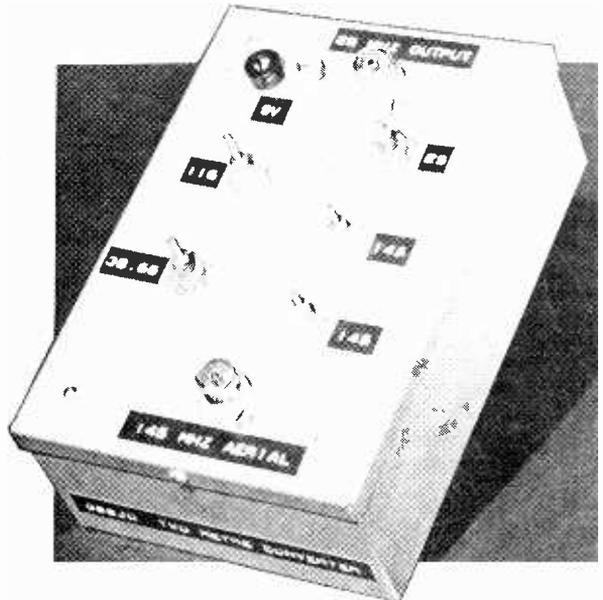

The amplified RF signal at  $145 \pm 1$  MHz is then mixed with the oscillator output frequency at 116 MHz. The difference frequency  $29 \pm 1$  MHz is then extracted from the FET drain circuit and fed via L3, which is tuned to 29 MHz by C7, to the main receiver aerial socket. With the converter oscillator frequency operating below signal frequencies, the direction of tuning on the main receiver will be maintained. This means that when tuning from 28 MHz up to 30 MHz on the main receiver, the converter is tuning from 144 MHz to 146 MHz.

## CONSTRUCTION

The converter is housed in a readily available aluminium box with lid measuring  $6 \times 4 \times 2$  in allowing ample room for the coils and other components. Most of the wiring and small components are accommodated on a  $5\frac{1}{2} \times 3\frac{1}{2}$  in piece of single sided copper clad board Fig. 2 which has the advantage that components and screens can be soldered directly to it, enabling short earth returns to be made.

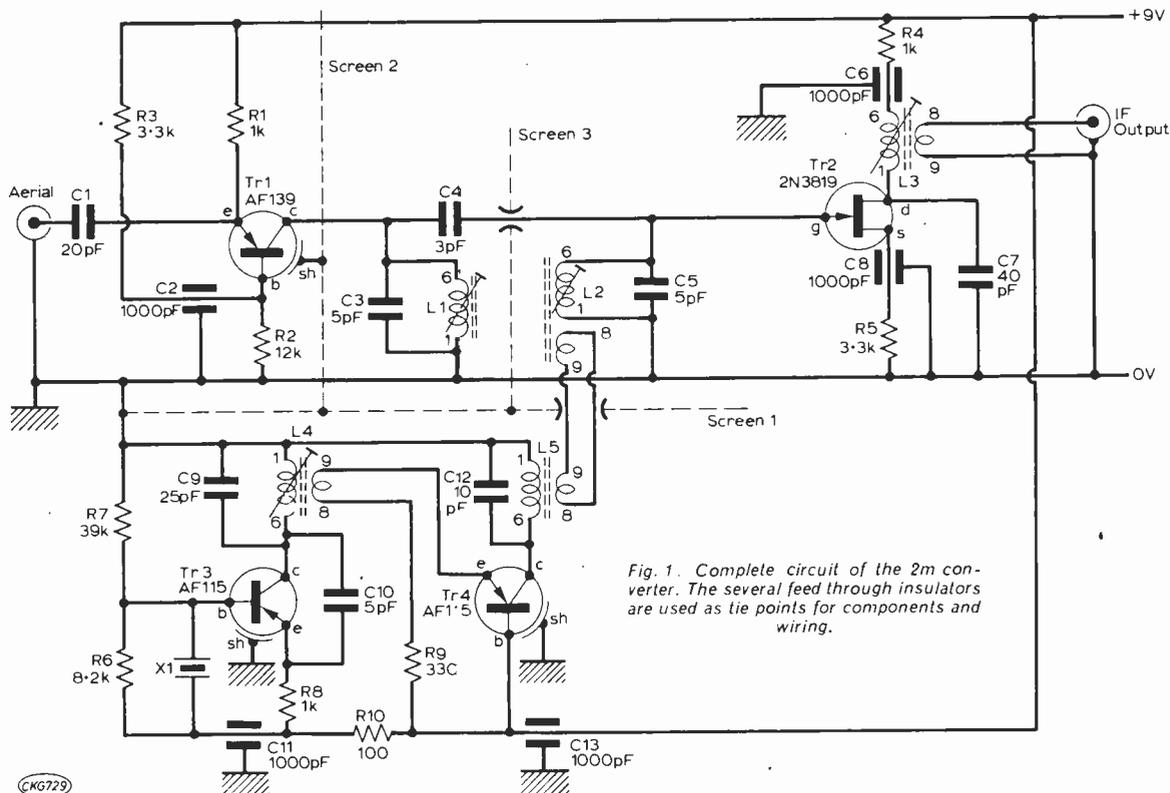


Fig. 1. Complete circuit of the 2m converter. The several feed through insulators are used as tie points for components and wiring.

## ★ components list

### Resistors

R1 1k $\Omega$	R6 8.2k $\Omega$
R2 12k $\Omega$	R7 39k $\Omega$
R3 3.3k $\Omega$	R8 1k $\Omega$
R4 1k $\Omega$	R9 330 $\Omega$
R5 3.3k $\Omega$	R10 100 $\Omega$

All resistors  $\frac{1}{4}$  or  $\frac{1}{2}$ W 10%

### Capacitors

C1 20pF TC	C8 1000pF FT
C2 1000pF FT	C9 25pF TC
C3 5pF TC	C10 5pF TC
C4 3pF TC	C11 1000pF FT
C5 5pF TC	C12 10pF TC
C6 1000pF FT	C13 1000pF FT
C7 40pF TC	

TC Tubular Ceramic FT Feedthrough

### Semiconductors

Tr1 AF139	Tr3/4 AF115
Tr2 2N3819	

### Inductors

L1/2/5/ Range 7 Red	
L3/4 Range 5 Blue	

All Denco miniature dual-purpose (valve type) coils. Cores must be specifically requested for the Range 7 coils.

### Miscellaneous


Aluminium box 6 x 4 x 2in (Type AB13). Copper-clad board  $5\frac{1}{2}$  x 3 $\frac{1}{2}$ in. Coaxial sockets (2). Battery plugs/sockets (2). Crystal 38.666MHz HC6U or HC18U (Serator Crystals, 36 Valleyfield Rd., London, SW16 2HR).

The copper clad board is mounted on  $\frac{3}{8}$ in spacers, one at each corner, and the five Denco coils are mounted on the aluminium box lid. This means that although  $\frac{1}{4}$ in fixing holes are needed in the lid,  $\frac{1}{2}$ in holes are required in the board so as to clear the main form of the coils. This method of construction, in effect, lowers the coil pins enabling shorter coil connections to be made, which is a distinct advantage at the frequencies involved. The two coaxial sockets and the battery sockets are also mounted on the box lid, holes being suitably provided in the copper board to take their connections.

The copper board should be cut and drilled Fig. 3, making sure that holes have been provided for all the coils, the feedthrough capacitors and the aerial, IF output and battery leads plus of course the holes for the 6BA fixing nuts and bolts. This board can then be used as a template for drilling the box lid. The feedthrough capacitors can now be soldered or bolted into position cutting off just enough of the pins on the non-copper side of the board so that they do not make contact with the underside of the box lid when it is in position.

At this point R10 must be soldered into position between the projecting pins of C11 and C13 on the non-copper side of the board. The aerial, IF output and battery sockets can now be fixed in position on the box lid and the copper board mounted on its spacers ready for wiring the remainder of the components.

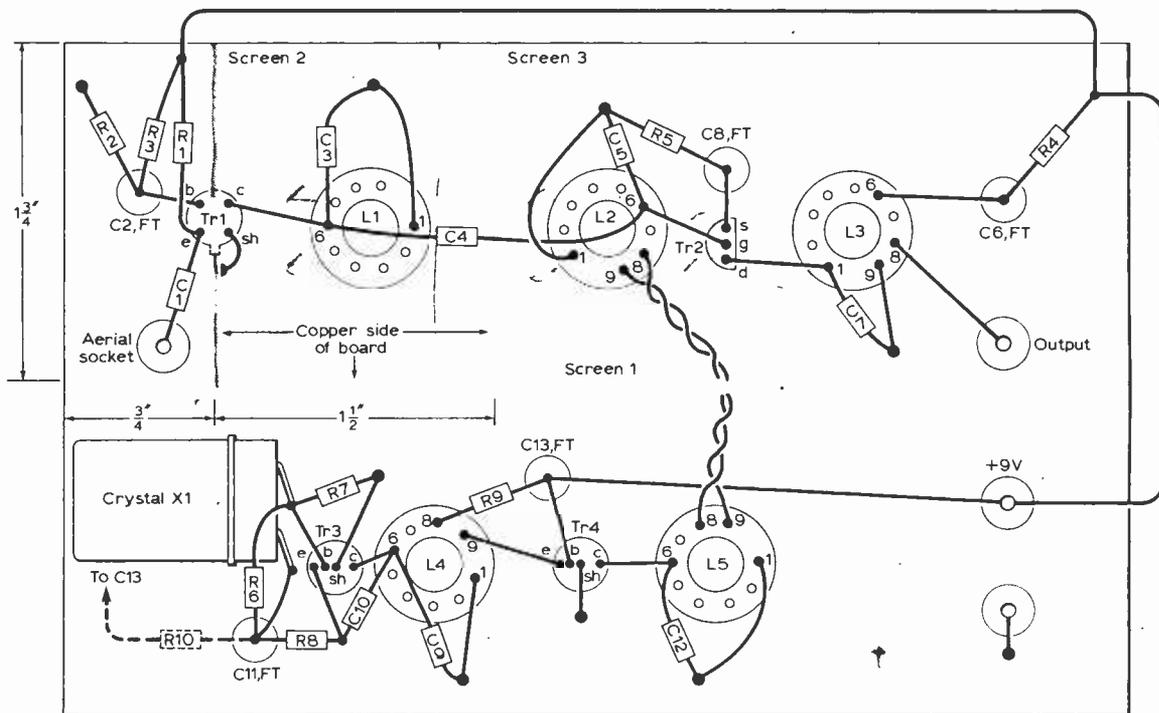
Short direct wiring must be used and special care taken when soldering to the coil pins. The polystyrene formers used for the coils will melt if subjected to excessive heat and it is perhaps a good idea to use a heat sink on the coil pins, as well as on all the transistor leads, when soldering.



● Chassis  
 FT—Feedthrough capacitor  
 Board 5 1/2 x 3 1/2

CKG730

Fig. 2: Layout of components and screens on the copper-clad board. The board is shown actual size. The photograph below shows the crystal oscillator and trioler stages of the converter.

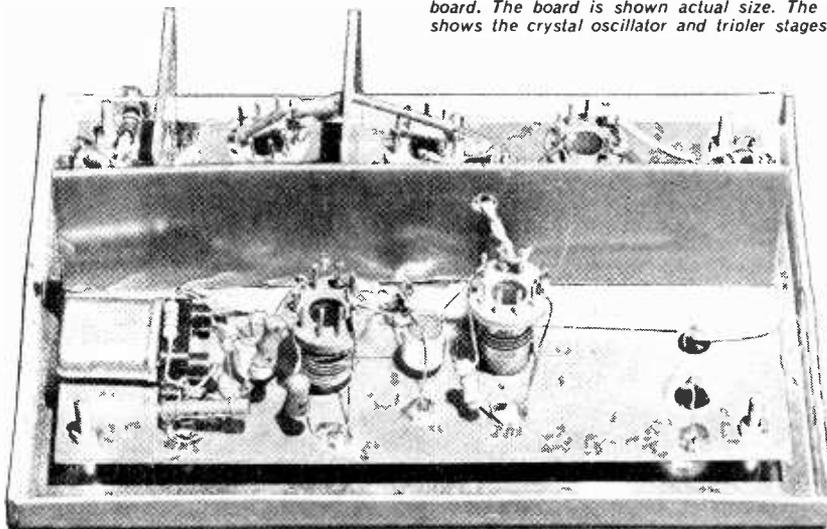

The crystal used in the original converter was of the HC6U type and the necessary crystal holder was glued in position on the copper board.

A wire ended crystal of the HC18U type could also be used, no holder then being required.

### ALIGNMENT


Before any 2m signals can be heard with the converter the crystal oscillator stage Tr3 must be operating. Adjustment of L4 core will make the oscillator work. This can be checked by connecting a meter in series with one of the battery leads and adjusting L4 for a peak in current, indicating that the

oscillator is functioning correctly. The battery supply should be switched on and off several times to ensure that the oscillator works every time. If the oscillator fails to restart at any time, tune L4 very slightly to the high frequency side of the current peak, i.e. anti-clockwise about half a turn. Adjustment of L5 core should now produce another similar but smaller increase in current when tuned to 116 MHz.

Operation of the oscillator on any frequency other than 38.666 MHz and thus the multiplier on 116 MHz, was found to be impossible with the values of parallel capacitance used. In order to align the remaining tuned circuits the converter should now be coupled to the main receiver by means of a short length of



use. It is realised that not all general coverage receivers provide adequate performance at such high frequencies, often lacking in sensitivity, image frequency rejection and bandspreading facilities. In such cases a lower tunable IF is desirable, the most popular seeming to be 4 to 6 MHz. For this lower IF the crystal must be changed to 46.666 MHz, C9 to 18pF, C12 to 6.8pF, C7 to 35pF and L3 to a Range 3 Blue coil.

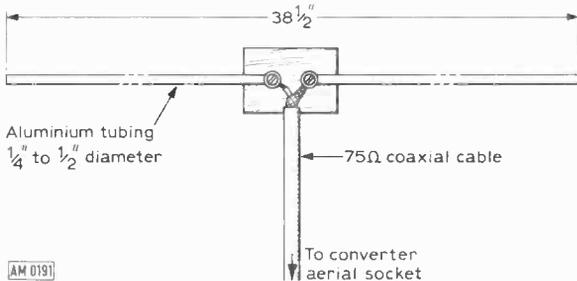

AM 0191

Fig. 4: This simple dipole will do for initial tests of the converter but a beam aerial will greatly improve results.

Although the converter is fully screened, if the lower IF is used trouble may be experienced with signals breaking through at the tunable IF frequencies, especially if the main receiver is not fully screened. The shortest practicable length of coupling coax should be used in these cases and if this is unsuccessful the metal case of the converter should be bonded to the main receiver case by a short metal strap.

# PW TECHNICAL CROSS PUZZLE No. 5 Solution

1	C	2	S	3	R	4	A	5	D	6	I	7	O	8	W	9	A	10	V	E
8	O	P	A	L	I	N	A	I												
	N	T			9	R	E	S	I	S	T	O	R							
10	D	R	E	A	M	S	E	P	L											
	U	L	E			12	S	T	D		13	E		14	M					
15	C	A	L	M	S	T					16	M	A	M	A					
	T	I			17	H	E	E	D	18	S	R	S							
19	O	A	T	H		A				20	T	A	P	E	S					
	R	E			21	A		22	R	M	U	H	M							
		23	L		24	A		E		25	U	N	D	O	N	E				
26	B	O	X	S	E	A	T	S				N	D							
	B	I	C	E						27	S	E	M	I						
28	S	E	M	A	P	H	O	R	E	S	A									

# TELEVISION

## IN THE AUGUST ISSUE

### COMPONENT DISTRIBUTION SURVEY

Along with the rapid growth of the electronics industry in recent years there has arisen a very complex component distribution system. In fact there are so many manufacturers and suppliers operating with many different trading policies that it can be difficult and time consuming to find out what is the best course to adopt in seeking supplies, whether for one-off construction, servicing requirements or equipment manufacture. "Television's" survey next month examines this field with the aim of giving readers a clear picture of the current situation, and lists the trading policies and stock lines of a number of suppliers who are likely to be useful to readers.

### SERVICING TELEVISION RECEIVERS

The next chassis to be covered by Les Lawry-Johns is the BRC/TCE 1590/1591 solid-state mains-battery portable chassis.

### LINE OUTPUT STAGE PROTECTION CIRCUIT

When the line generator fails to oscillate the line output pentode is left without bias and draws a very heavy current. This can damage not only the line output valve but the boost diode and line output transformer as well. It is tempting to speculate on how many line output valves and other components have been unnecessarily destroyed in this way over the years. Keith Cummins decided to see whether there was a simple solution to the problem and found that for a matter of pence an effective protection circuit could be built.


### PLUS ALL THE REGULAR FEATURES

TO .....  
(Name of Newsagent)

Please reserve/deliver the AUGUST issue of TELEVISION (25p)—on sale July 15th—and continue every month until further notice.

NAME .....

ADDRESS .....

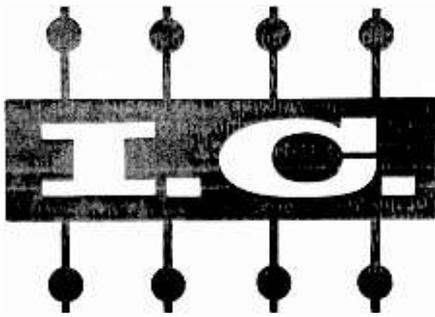

# OF THE MONTH

Number 46

LM381N DUAL LOW NOISE AMPLIFIER

**T**HE National Semiconductor LM381N device contains two similar low noise preamplifiers in a single integrated circuit. It has a wide range of uses in entertainment equipment, such as amplifying the signals from stereo tape recorder heads or cartridges. It is an ideal device for amplifying low level signals in low noise applications. The amplifiers are completely independent and each provides a gain, without feedback, of about 112dB; a voltage gain of 160,000.

The device provides a channel separation of 60dB whilst the internal power supply decoupling and regulator circuits provide 120dB rejection of signals on the power supply line, such as mains hum. Although many attempts have been made to use suitable operational amplifiers for low noise audio applications, the availability of the new LM381N designed specifically for these applications makes it possible to obtain lower noise levels, better rejection of signals on the power supply lines, wider bandwidth, with fewer external components.

A specially selected ultra-low noise version of the LM381N is available under the coding LM381AN. It is used in critical applications requiring the lowest possible noise levels, such as hydrophone amplifiers, studio sound equipment, scientific instrumentation etc. The LM381AN is naturally somewhat more expensive than the more commonly used LM381N.

The LM381N operates from a single power supply in the range 9V to 40V. The typical supply current is 10mA. The device contains internal circuits which protect it from damage if the output is accidentally shorted limiting the output current to about 12mA. The maximum output voltage swing which can be

obtained from the LM381N is only 2V less than the power supply voltage used. The total harmonic distortion is typically 0.1%.

## Input

The basic circuit of the input stage of one of the amplifiers in the device is shown in Fig. 1. In the circuits and text the pin numbers of the **second** amplifier will be shown in brackets. The optimum noise performance is obtained with 'single ended operation'. In this case Tr2 is biased OFF and feedback is taken to the common emitter of pin 3 (pin 12). Noise figures with single ended operation are typically 1dB with 50kΩ input impedance, 1.3dB with 10kΩ and 1.6dB with 5kΩ input over the frequency bandwidth 10Hz to 10kHz.

When the extra noise contributed by Tr2 can be tolerated, the feedback may be taken to the inverting input of pin 2 (pin 13). The impedance at the base of Tr2 is about one hundred times higher than that at the emitter; smaller capacitors and larger resistors can therefore be employed when the feedback in tone and equalization circuits is returned to the base. However, in this 'differential' configuration the noise is increased by a factor of  $\sqrt{2}$ . The input impedance is of the order of 100kΩ whilst the output impedance is 150Ω.

## Bandwidth

The amplifiers each contain an internal frequency compensating capacitor which results in a gain-bandwidth product of about 15MHz. This is the frequency at which the gain falls to unity. This compensation is adequate to preserve stability at a

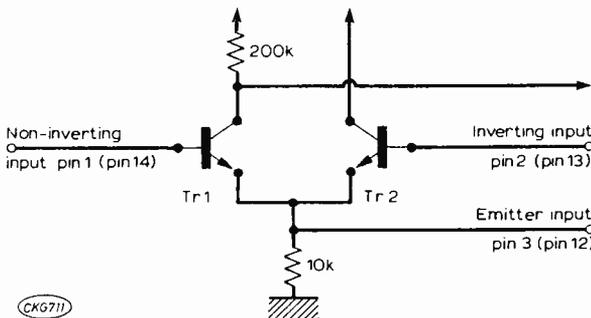


Fig. 1: The internal input circuit of the LM381N.

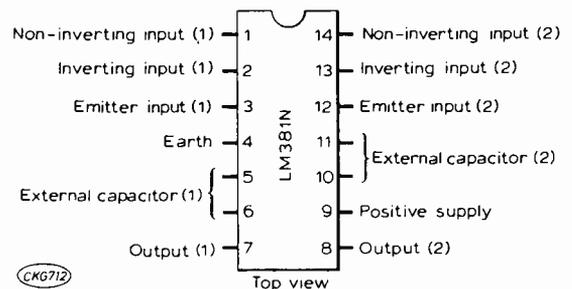


Fig. 2: The connections of the LM381N. The connections to the two internal amplifiers are distinguished by the numbers in brackets.

closed loop gain of 10. A suitable external capacitor may be placed in parallel with the internal capacitor connecting between pins 5 and 6 (pins 10 and 11), Fig. 2. This reduces the amplifier bandwidth and thus removes most of the high frequency noise.

## Applications

**Tape Playback Preamplifier** using the LM381N is shown in Fig. 3. Tape playback amplifiers must contain frequency compensation circuits so that the overall record-replay operation shall produce a level frequency response. The capacitor C1 provides an amount of negative feedback which increases with rising frequency. The gain therefore decreases with rising frequency, the circuit being designed to have a response complying with the NAB standard for a tape speed of 3 $\frac{3}{4}$  i.p.s.

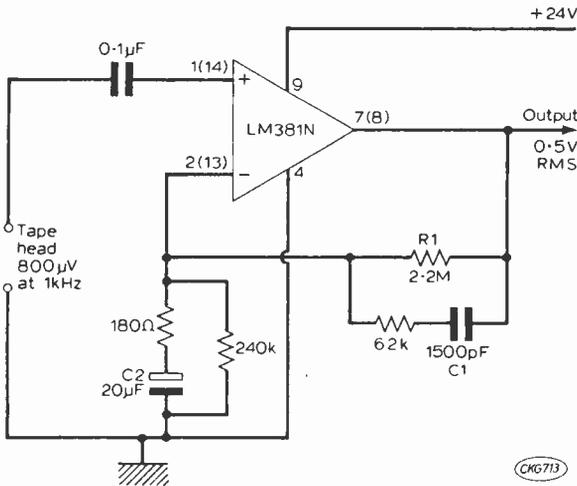


Fig. 3: A typical tape playback preamplifier.

The circuit will convert an output of 800 $\mu$ V from a playback head into a 0.5V RMS signal at the preamplifier output at a frequency of 1kHz, a voltage gain of 56dB. This circuit requires about five seconds before it can be used after the power has been supplied since C2 takes time to charge through R1.

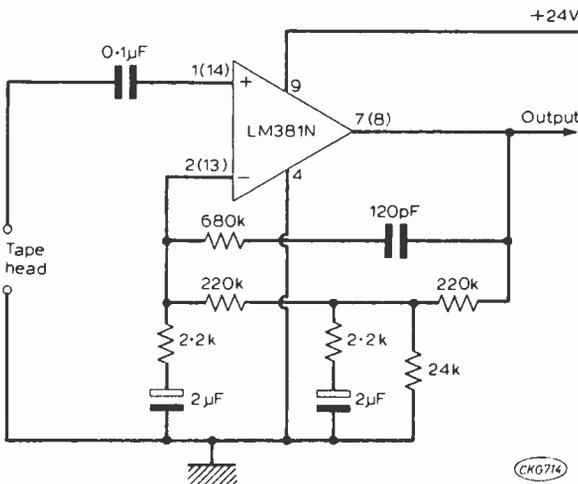


Fig. 4: A fast turn-on tape playback amplifier.

The circuit of Fig. 4, is slightly more complex than Fig. 3 but it has the advantage that it can be used immediately the power is applied. It has been designed to have a similar performance to that of the Fig. 3 circuit. The 120dB rejection of signals on the power supply line has been preserved in this circuit.

**Tape Record Preamplifier** used to feed tape recording heads must also be tailored to produce the correct response. Consider the case where a microphone producing a peak output signal of 10mV is required to drive a tape recording head which requires 30 $\mu$ A of audio drive current. This requirement can be met by the circuit of Fig. 5. A single ended input circuit is used for optimum noise performance.

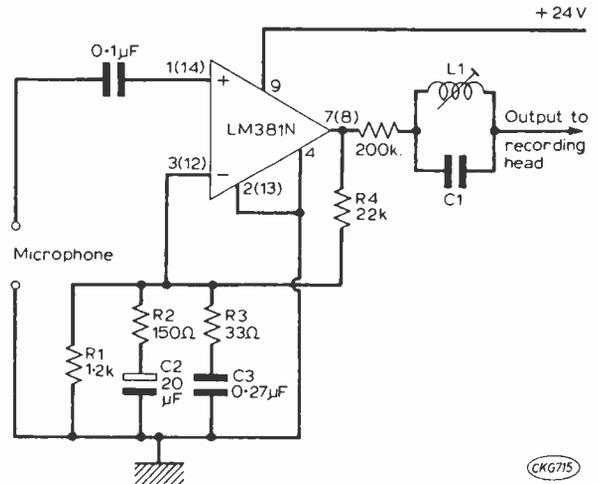


Fig. 5: A preamplifier for driving a tape recording head.

The values of the inductance L1 and of the capacitor C1 should be chosen to suit the particular recording head used. The feedback network R1 to R4, C2 and C3 provides the required frequency response.

**Magnetic Pick-ups** provide outputs which are typically in the range 3.5mV to 8mV at a velocity of 5cm/second; high quality recordings use velocities of this order. The output is proportional to the velocity.

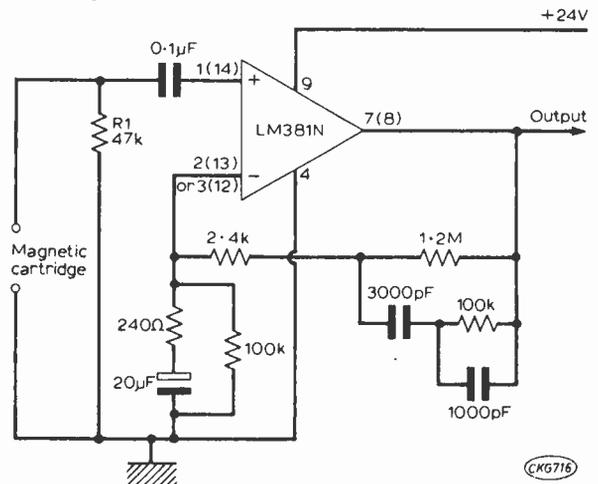


Fig. 6: A preamplifier for use with a magnetic cartridge in a record player.

A typical preamplifier for use with a magnetic pick-up is shown in Fig. 6. It provides the required response which falls with increasing frequency and has been designed for use with a cartridge of 0.5mV/cm/sec sensitivity. The circuit will drive a power amplifier which reaches the overload level when a signal of 5V RMS is applied to its input. The resistor R1 provides the load to a standard cartridge with the normal RIAA characteristics.

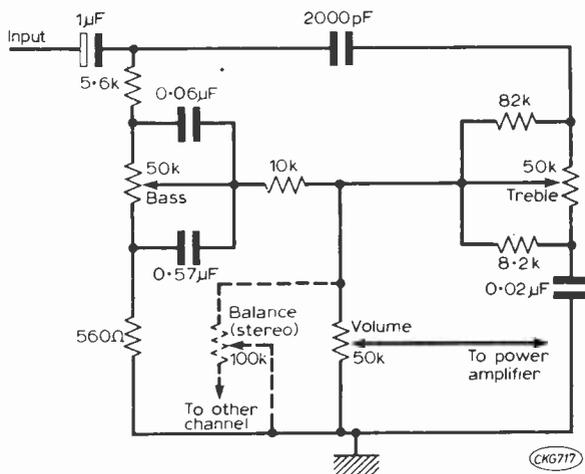


Fig. 7: A tone control circuit suitable for use between the output of the Fig. 6 circuit and the input of a power amplifier.

**Tone controls.** In many circuits two preamplifiers are employed, one before and one after the tone control circuits, in order to compensate for the insertion loss in the tone control network. However, when the LM381N is used as a preamplifier, only a single preamplifier stage is required owing to the high gain and high maximum output voltage provided by this device. A simple tone control circuit with bass and treble boost and cut facilities is shown in Fig. 7 which can, for example, be placed directly between the output of the record player amplifier of Fig. 6 and a power amplifier.

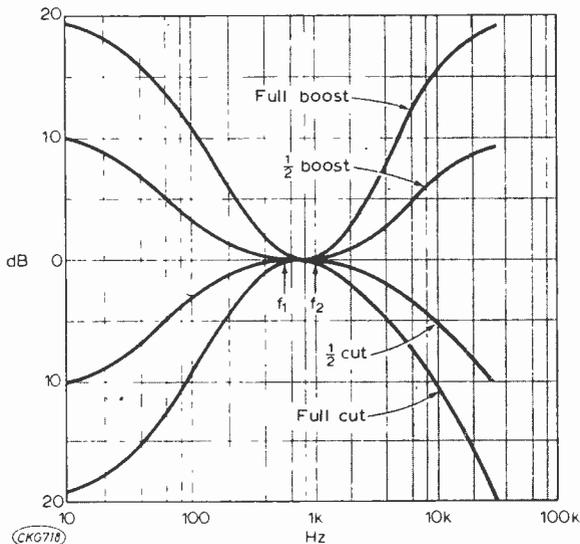


Fig. 8: The characteristics of the tone control circuit of Fig. 7.

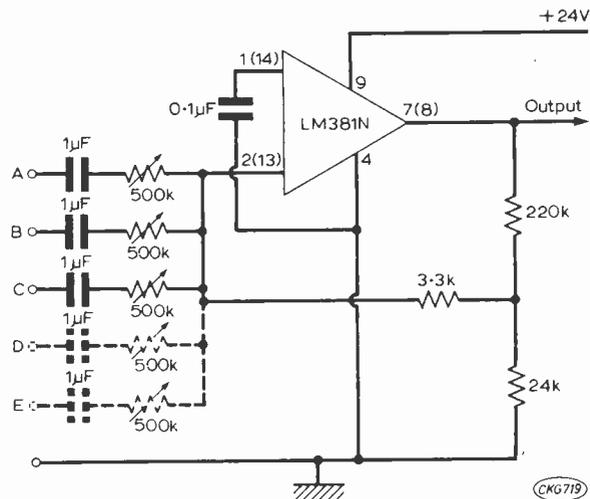


Fig. 9: An audio mixer circuit. Further inputs can be added, if required as indicated by the components shown in dotted lines.

The characteristics of the tone control circuits of Fig. 7 are shown in Fig. 8. It can be seen that a maximum boost or cut of about 20dB is available on both treble and bass.

**Audio Mixer** is the final example of the versatility of the LM381N, Fig. 9 designed for use with 600Ω dynamic microphone providing output level of 10mV. The circuit provides an output signal of 5V and can be used over a dynamic range of 80dB. A number of input signals (A to E) can be selected or combined with any other input signal.

The LM381N and AN are available from Athena Semiconductor Ltd., 140 High St., Egham, Surrey.

# TELEVISION & PRACTICAL WIRELESS DOUBLE SCOOP

YOU CAN RUN YOUR OWN "WORLD-CUP" SOCCER OR "OPEN TENNIS" CHAMPIONSHIPS.  
BUILD THE

## TV FOOTBALL GAME


Suitable for colour or monochrome television sets.

Simulate the green football pitch, red and blue players, pink touch-line. See the ball kicked hard or soft across the pitch. Move your players to any position on the screen. Simple to operate joystick control.

This project appears in **TELEVISION** only, starting in the July issue. Not to be confused with **TELE-TENNIS**, another TV game project appearing in **PRACTICAL WIRELESS**.

Ideal for fund raising events.


# HIGH QUALITY SOUND LINKS

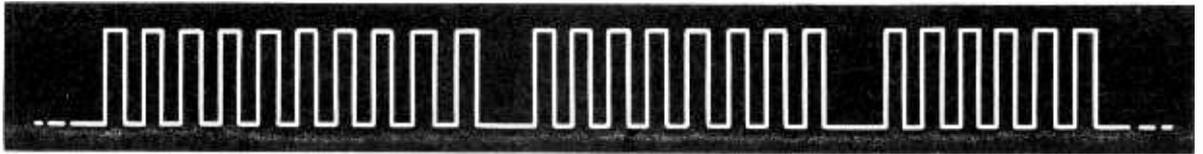

VIVIAN CAPEL

THE quality of the signals dispatched from the BBC studios for broadcast over the VHF frequency-modulation network is of a very high standard indeed. Development of domestic tuners and amplifiers over recent years has been such as to enable justice to be done to the high standard of received signals. Hi-fi radio enthusiasts will readily confirm the excellent results that can be obtained, yet sometimes with a note of reservation. It is often found that broadcasts originating in an area remote from the regional transmitter are of a lower standard than those coming from the local studio. So listeners in the South cannot expect as good results from a live broadcast at the Edinburgh Festival as from London's Festival Hall.


The reason for this is the links that are used to convey the signals from the studio or concert hall to the various transmitters. Owing to the limited range of VHF transmitters these must be sited within the locality they serve, hence the inescapable need for long studio links, often of several hundred miles. Many things can happen to a signal on a journey of that length, the higher frequencies can be lost, there can be phase differences due to varying transit times of different frequencies, any non-linearity will produce harmonic and intermodulation distortion, and of course noise can be picked up from numerous sources, thus imposing a restriction on the dynamic range which can be allowed. Furthermore reactive elements can give rise to 'ringing', the spurious oscillation produced by transients in the signal.

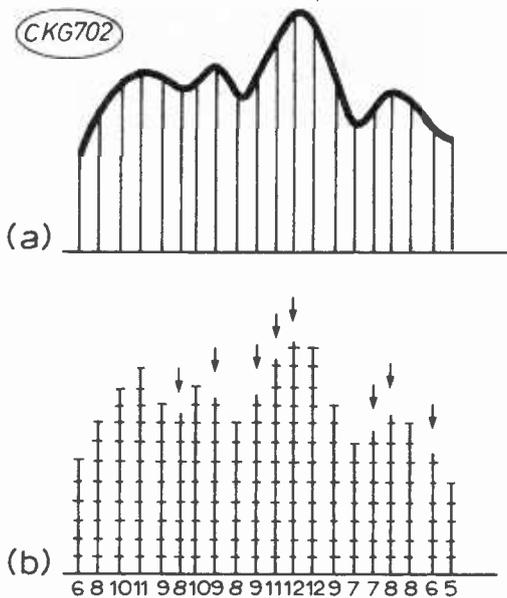
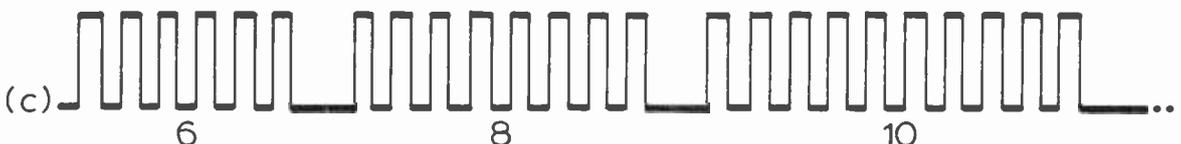
## NEW LINKS

All this will be a thing of the past as the new pulse-code-modulation (PCM) links are installed between studios and transmitters all over the country. The South East is already so equipped and the links are being extended Westward and Northward, so that within two or three years the same standard of quality will be transmitted irrespective of the area of origin. By means of PCM, signals can be sent over great distances without any loss of information and with zero noise and distortion. This like the perpetual-motion machine may seem to be a science-fiction dream, but it really does work. Like a lot of 'new' ideas, it is not new at all, having been invented in 1938, but the complex circuitry required, had to wait until IC's were developed before it could become a practical proposition.



In order to understand how it works we must first consider the nature of the normal audio signal such as the output of a microphone. It takes the form of a constantly varying voltage which in fact is comparable or analogous to the varying pressures of the sound-wave producing it. For this reason it is termed an **analogue** signal, and, because it consists of a wide range of frequencies and amplitude levels, it needs equipment capable of handling such ranges without modification of the signal in order to process it. Therein lie the difficulties.


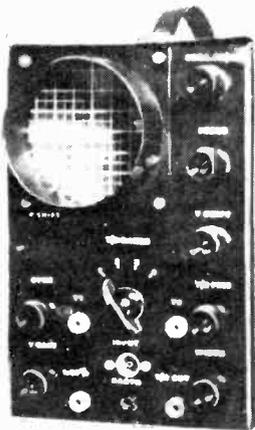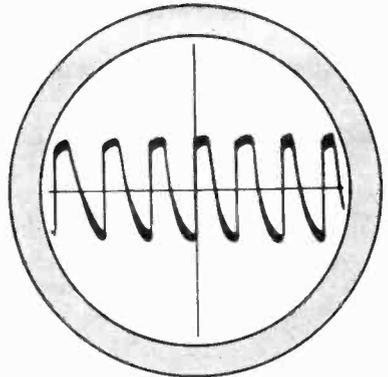
# look! electronics really mastered

... practical  
... visual  
... exciting!

no previous knowledge  
no unnecessary theory  
no "maths"



RAPY


## BUILD, SEE AND LEARN

step by step, we take you through all the fundamentals of electronics and show how easily the subject can be mastered. Write for the free brochure now which explains our system.

### 1/ BUILD AN OSCILLOSCOPE

You learn how to build an oscilloscope which remains your property. With it, you will become familiar with all the components used in electronics.
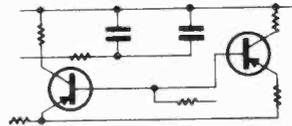
### 2/ READ, DRAW AND UNDERSTAND CIRCUIT DIAGRAMS



as used currently in the various fields of electronics.

### 3/ CARRY OUT OVER 40 EXPERIMENTS ON BASIC ELECTRONIC CIRCUITS & SEE HOW THEY WORK, including :

valve experiments, transistor experiments amplifiers, oscillators, signal tracer, photo electric circuit, computer circuit, basic radio receiver, electronic switch, simple transmitter, a.c. experiments, d.c. experiments, simple counter, time delay circuit, servicing procedures.

This new style course will enable anyone to really understand electronics by a modern, practical and visual method—no maths, and a minimum of theory—no previous knowledge required. It will also enable anyone to understand how to test, service and maintain all types of electronic equipment, radio and TV receivers, etc.

**FREE** POST NOW  
for  
BROCHURE

or write if you prefer not to cut page

To: **BRITISH NATIONAL RADIO & ELECTRONICS SCHOOL,**

P.O. Box 156, JERSEY. Please send your free brochure, without obligation, to:

*we do not employ representatives*


NAME

**BLOCK CAPS**

ADDRESS

PLEASE WL84

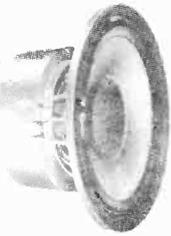**special free gift also to all our students**



# WILMSLOW AUDIO

**THE Firm for speakers!**

## SPEAKERS

Baker Group 25 3, 8 or 15 ohm	£7.75
Baker Group 35 3, 8 or 15 ohm	£8.50
Baker Group 50 12 8 or 15 ohm	£12.50
Baker Deluxe 12" d/cone	£10.75
Baker Major ..	£8.50
Baker Regent ..	£7.75
Baker Superb	£14.50
Baker Auditorium 12	£12.50
Celestion MF1000 horn	£10.95
Celestion PST9 for Unilux	£2.55
Celestion G12M 8 or 15 ohm	£12.00
Celestion G12H 8 or 15 ohm	£15.00
Celestion G15C 8 or 15 ohm	£24.00
Celestion G18C 8 or 15 ohm	£33.00
Coral 6 1/2" d/cone roll surr. 8 ohm	£2.42
Coral 8" d/cone roll surr. 8 ohm	£3.11
EMI 13 x 8 3, 8 or 15 ohm	£2.15
EMI 13 x 8 150 d/c 3, 8 or 15 ohm	£2.35
EMI 13 x 8 450 1/tw 3, 8 or 15 ohm	£3.60
EMI 13 x 8 type 350 8 or 15 ohm	£8.25
EMI 13 x 8 20 watt base	£6.60
EMI 6 1/2" 93850 4 or 8 ohm	£3.00
EMI 5" 98132CP 8 ohm	£2.50
EMI 8 x 5 d/cone, roll surr 10 watt	£2.50
EMI 2 1/2" tweeter 97492AT	.65
Eagle DT33 30 watt tweeter	£5.45
Eagle HT15 horn tweeter	£3.80
Eagle CT5 cone tweeter	£1.50
Eagle CT10 tweeter 8 or 16 ohm	£2.54
Eagle MHT10 horn tweeter	£3.80
Eagle crossover CN23, CN28, CN216	£1.20
Eagle FR4	£5.30
Eagle FR65	£7.15
Eagle FR8	£9.50
Elac 9 x 5, 59RM109 15 ohm,	
59RM114 8 ohm	£2.65
Elac 6 1/2" 6RM171 d/c roll surr.	£3.50
Elac 6 1/2" 6RM220 d/cone	£2.65
Elac 4" tweeter TW4	£1.21
Elac 10" d/cone 10RM239 8 ohm	£2.65
Elac 8" 8CS175 3 ohm	£2.50
Fane Pop 15 watt 12"	£4.50
Fane Pop 25/25 watt 12"	£7.00
Fane Pop 40 watt 10"	£8.50
Fane Pop 50 watt 12"	£11.00
Fane Pop 55 12" 60 watt	£12.50
Fane Pop 60 watt 15"	£13.00
Fane Pop 100 watt 18"	£22.50
Fane Crescendo 12A 100 watt 12"	£29.00
Fane Crescendo 12B bass	£29.00
Fane Crescendo 15" 100 watt	£36.00
Fane Crescendo 18" 150 watt	£49.50
Fane 807T 8" d/c roll surr.	£7.00
Fane 807T 8" d/c roll surr.	£3.85
Fane 808T 8" d/c	£2.75
Fane 701 twin ribbon horn	£23.00
Fane 910 horn	£10.75
Fane 920 horn	£38.50

Goodmans 8P 8 or 15 ohm	£4.65
Goodmans 10P 8 or 15 ohm	£4.95
Goodmans 12P 8 or 15 ohm	£11.95
Goodmans 12P-D 8 or 15 ohm	£15.25
Goodmans 12P-G 8 or 15 ohm	£14.50
Goodmans Audiomax 12AX 100 watt	£39.65
Goodmans Audiomax 15AX	£42.00
Goodmans 15P 8 or 15 ohm	£19.50
Goodmans 18P 8 or 15 ohm	£33.00
Goodmans Midax 750	£15.00
Goodmans Axent 100 tweeter	£6.60
Goodmans Audiom 100 12"	£9.50
Goodmans Axiom 401 12"	£15.95
Goodmans Twinaxiom 8	£7.50
Goodmans Twinaxiom 10	£8.25
Kef T27	£4.75
Kef T15	£5.75
Kef B110	£6.75
Kef B200	£7.50
Kef B139	£11.75
Kef DNE	£4.12
Kef DN12	£2.75
Kef DN13	£2.75
STC4001G super tweeter	£6.19
Richard Allan CG8T 8" d/c r/surr.	£6.35
Wharfedale Super 10RS/DD	£9.80
2 1/2" 64 ohm, 70mm 80 ohm, 70mm 8 ohm	.65
2 1/2" 75 ohm	.50
7" x 4" 3 or 8 ohm	£1.38
8" x 5" 3 or 8 ohm	£1.38
10" x 6" 3, 8 or 15 ohm	£1.92

## SPEAKER KITS

Baker Major Module	each £10.75
Fane Mode One	each £9.90
Goodmans D11 20	each £8.75
Helme XLK 25	pair £18.17
Helme XLK 30	pair £14.95
Helme XLK 50	pair £37.18
Keffit 2	each £23.50
Keffit 3	each £34.00
Richard Allan Twinkit	each £8.25
Richard Allan Triple 8	each £13.00
Richard Allan Triple	each £18.50
Richard Allan Super Triple	each £21.50
Wharfedale Linton 2 kit	pair £19.25
Wharfedale Glendale 3 kit	pair £34.50
Wharfedale Dovedale 3 kit	pair £52.50

## PA/DISCO AMPLIFIERS

(carr. and ins. £1)	
Baker Major 100 watt	£49.75
Linear 30/40	£30.00
Linear 40/50	£35.00
Linear 80/100	£59.75
Linear 100 watt slave	£44.00

Eagle PA range in stock—ask for catalogue.

**Free with speaker orders over £7—**

"Hi-Fi Loudspeaker Enclosures" book. All units guaranteed new and perfect. Prompt despatch. Carriage and packing: speakers 38p each, speaker kits 75p each (£1.50 pair) tweeters and crossovers 20p.

**ALL PRICES QUOTED INCLUDE VAT.**

**WILMSLOW AUDIO (Dept. PW)**

Loudspeakers: Swan Works, Bank Square, Wilmslow, Cheshire. SK9 1HF  
Discount Radio, PA, Hi-Fi: 10 Swan St. Wilmslow  
Send stamp for free booklet "Choosing a Speaker"



## Cassettes

The best buy!

**Agfa Low Noise Cassettes AT LESS THAN HALF PRICE!**

**AGFA HIGH DYNAMIC SUPER**

**AGFA STEREO-CHROM CHROMIUM DIOXIDE**

	1	5	10
C60	37p	£1.80	£3.50
C90	50p	£2.48	£4.95
C120	63p	£3.10	£6.20
	1	5	10
C60+6	50p	£2.40	£4.70
C90+6	68p	£3.35	£6.60
C120	99p	£4.90	£9.80
	1	5	10
C60	85p	£4.20	£8.30
C90	£1.08	£5.35	£10.60

**SAME DAY DESPATCH. P. & P. 15p per order**

## WILMSLOW AUDIO

(DEPT. PW)  
10 SWAN STREET, WILMSLOW,  
CHESHIRE, SK9 1HF

Cut-price prerecorded cassettes—send stamp for list

# AMBIT INTERNATIONAL

'74 Datologue issue:

The latest datologue has more data, more new devices than ever. Linear, Digital, Discrete, LEDS. now 20p

New trade and professional price structure for quantity buyers.

NE561B AM/FM PLL	£3-19
NE 562B FM (synth)	£3-19
NE565A FM/FSK	£2-55
NE567V AM/FM tone	£2-75
NE555V Timer	77p
CA3089E FM IF	£1-95
CA3090Q Stereo dec.	£3-55
SN76660N FM IF	£1-00
µA753 FM gain	£0-99
MC1310P Stereo dec	£2-85
TBA651 AM/FM/SSB	£1-81
TAD 100 AM	£1-47
LM309K 5v 1amp	£1-90
NE550/µA723 reg. IC	£0-85
710 comparator	£0-47
741 op amp	£0-38
3900 quad amp in 14 DIL really versatile	£0-68
1496 bal mix. (SSB)	£1-02
LM380 audio power amp	£1-00
TBA810S 7w rms AF	£1-50
8038 sine : square : triangle generator. 1000 : 1 sweep complete audio generator—including 12 pages of data	£3-10 each

See the datologue for more details of more devices.

## TOKO INDUCTORS AND FILTERS. Only from AMBIT

CFS 10-7 FM ceramic	£0-40
CFT 455 ceramic	£0-45
CFU 455 ceramic	£0-50
MFH *T mechanical	£1-35
KACS 586 HM (CA3089)	30p
150J now 220K	15p
CA3090Q 2mH coil	30p
MW & IF coils (10mm)	30p
BLR2011N 19 & 38kHz filter for stereo	£1-80
TOKO inductors and filters—only from Ambit.	

DFM & TIMER constructors:  
FND70 7 seg. LED display with 7490 & 9368 on a DS FG PCB  
£5-00 ea. £4-50 ea 4 off  
1 MHz TTL Clock—Divided down to 1 Hz £9-50 inc. xtal.

## AMBIT INTERNATIONAL (PW7)

37a High Street, Brentwood, Essex CM14 4RH. (216029)

New devices + data .....  
PLEASE ADD 10% VAT. P.P. 10p.

## QUANTISATION

If we take a typical audio signal, and sample the level at regular intervals we will get the result as shown in Fig. 1. Each sample represents the instantaneous level of the audio signal at the moment of sampling, and this level can be expressed by a certain number of electrical pulses. The individual samples are known as **words**, and the pulses making up each sample as **bits**. The conversion of the analogue signal into pulses is termed **quantisation** because it is quantitatively expressed as a certain number of bits. As the signal is now a series of digits or numbers it is described as **digital**. This information can be later decoded and used to construct a wave identical to the original.

The quality of the result depends on two main factors. First, the number of samples or words that are taken in a given time. Any alteration of the wave-shape that occurred between two successive samples would be lost. Such an event would occur if the sampling rate was lower than the highest frequency contained in the signal. In practice it has been found that the sampling rate must be at least twice as high as the highest frequency to be sent. BBC FM broadcasts transmit frequencies up to 15kHz, and so the sampling rate is a little higher than twice this at 32kHz.

The other factor is the number of bits contained in each sample. If the amplitude of the original wave is to be accurately represented, the maximum number of levels definable must be large. Should the analogue wave amplitude fall between two specified levels, it will be assigned the value of the lower one and be reproduced at that level in the decoding process. Thus the wave shape will not be identical to that of the original and harmonic distortion will be added. This type of distortion arising during quantisation is the only type of distortion than can arise. Once the signal is encoded no further distortion can appear in the transmission. Thus it is always a known quantity and does not depend on outside variables.

## BBC PCM

The BBC system uses a large number of sampling levels, actually 8191 different amplitudes, and so quantisation distortion is kept to a very low level. It is in fact 1 part in 8191, maximum, which is 0.0122%, far better than the domestic equipment used to reproduce it.

As described here though, the system has one major snag. With a sampling frequency of 32kHz, and each sample can contain up to 8000 bits, the resulting frequency will be 262MHz! This is completely unrealistic, and no link would have the bandwidth to accommodate anything like such a frequency, especially for a single audio channel.

Many readers who have followed thus far, will, by now, have cast their eyes down the following paragraphs with some apprehension and perhaps disgust. Practical men are often allergic to maths, and so the tendency may be to finish about here and turn over to the constructional features. However, don't be put off by what may appear to be a formidable array of figures. It's much easier than it looks, and actually it is very interesting to see the rather ingenious way by which the bandwidth problem has been solved. On the other hand, mathematical types, will probably have solved it already.

## BINARY CODE

The solution lies in the use of the binary code by which large numbers can be represented by a small number of digits of only two factors, 0 and 1. To start with, most readers will know that when a number is multiplied by itself (squared), it is said to be raised to the second power and written  $n^2$ ; when so multiplied twice ( $n^3$ ) it is raised to the third power, and so on. The table lists 13 values, the twelve powers of 2, and also 1. When all these are added the result is 8191 and it is a fact that any number between 1 and 8191 can be obtained by taking one or more of these numbers and adding them. None need be used more than once.

To illustrate the point consider a couple of examples. The number 3417 can be obtained by adding:  $2^{11}=2048$ ;  $2^{10}=1024$ ;  $2^8=256$ ;  $2^6=64$ ;  $2^5=16$ ;  $2^3=8$  and 1. Agreed? Well, that wasn't too bad, so we will try another one, this time let's choose a nice round number, 5000. This is made up of:  $2^{12}=4096$ ;  $2^9=512$ ;  $2^8=256$ ;  $2^7=128$  and  $2^3=8$ .

In these examples we only listed the values actually used and ignored the others. However, to enable us to get the sequence right we must list all 13 even if it means assigning a zero value to the unused ones by multiplying by 0.

Going back to our first example then, the sequence is:  $2^{12} \times 0$ ;  $2^{11} \times 1$ ;  $2^{10} \times 1$ ;  $2^9 \times 0$ ;  $2^8 \times 1$ ;  $2^7 \times 0$ ;  $2^6 \times 1$ ;  $2^5 \times 0$ ;  $2^4 \times 1$ ;  $2^3 \times 1$ ;  $2^2 \times 0$ ;  $2^1 \times 0$ ;  $1 \times 1$ .

The second example gives us:  $2^{12} \times 1$ ;  $2^{11} \times 0$ ;  $2^{10} \times 0$ ;  $2^9 \times 1$ ;  $2^8 \times 1$ ;  $2^7 \times 1$ ;  $2^6 \times 0$ ;  $2^5 \times 0$ ;  $2^4 \times 0$ ;  $2^3 \times 1$ ;  $2^2 \times 0$ ;  $2^1 \times 0$ ;  $1 \times 0$ .

Then, if both sending and receiving equipment 'understand' that they refer to a consecutive series of powers of 2, each sample of up to 8191 amplitude levels can be accurately represented by thirteen digits of either 0 or 1. In our examples the series would be 3417=0110101011001 and 5000=1001110001000. In the transmission, 1 is represented by a pulse and the 0 by a space.

**BINARY TABLE**

1	1	1
2	$2^1$	2
3	$2^2$	4
4	$2^3$	8
5	$2^4$	16
6	$2^5$	32
7	$2^6$	64
8	$2^7$	128
9	$2^8$	256
10	$2^9$	512
11	$2^{10}$	1024
12	$2^{11}$	2048
13	$2^{12}$	4096

*This table shows the 13 binary bits, 1 and the 12 powers of 2. Any number between 1 and 8191 can be obtained by adding specified bits. Use or omission of a bit is indicated by 1 or 0 expressed electrically by pulse or space.*

Thus there is a dramatic saving in bandwidth; now the frequency will be 13 binary bits  $\times$  32000 (the sampling frequency) or just over 400kHz. It may be thought that this is still rather high for an audio link that handles just the same programme as a 15kHz analogue link. This, of course, is true, but if we consider the advantages the extra bandwidth is well worth it.

Take noise, for example. Radio amateurs know from experience that when conditions are poor and noise levels high, that the morse code is far more

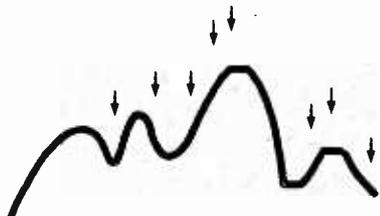


Fig. 2: Quantisation distortion. Wave-form of Fig. 1 distorted because number of bits (12) is insufficient to accurately represent amplitude levels as indicated by arrows in Fig. 1.

intelligible than speech. Morse is, of course, a digital signal being composed of a series of pulses and spaces similar to our PCM. A feature of both is that the pulses are all of the same amplitude, irrespective of whether the modulated audio signal in the case of PCM, is of high or low level. Low audio signals cannot then get lost in a high noise-level, so this in turn enables a higher dynamic range (ratio of high to low-level signals) to be sent. As the receiving equipment responds only to the pulses, noise originating in the link has no effect at all, so it is, in fact, noiseless. Only if the noise approached the level of the pulses would it have an effect but this would be extremely unlikely.

## PULSE SHAPE

Pulse-shape is of minor importance as long as the receiver recognises it as a pulse and counts it; harmonic distortion therefore will likewise not affect the signal and there can be no loss of information contained within the modulation, so the audio frequency response cannot be modified. Hence there is zero distortion over the link. It can be seen then that high bandwidth requirement is more than compensated for by the virtually ideal transmission characteristics.

The BBC links combine 13 PCM channels into one having an overall bandwidth of 5.5MHz, the same as for a single television channel, which enables the links and associated equipment to be standardised with that of the television service. The 13 channels can be used for separate mono programmes or six stereo with one spare.

## NOISE

Although the signal becomes unaffected by noise once it is encoded, noise in the analogue or encoder circuits will be encoded along with the audio signal. The noise is stated to be -69dB weighted, which is of

a very low order, much less than could be picked up on a long analogue studio link. The possibility of error in the signal has been provided for. Each sample, as we have seen, consists of thirteen pulses or spaces. If, due to an error in the encoder or elsewhere, there is a discrepancy, the decoder will recognise the error and hold the value at the last error-free sample until the next such one arrives.

## RESULTS

For high-quality results the sampling rate and bit quantity used by the BBC is necessary, but good results are possible with more modest parameters. Some private telephone systems which carry speech only use an 8kHz sampling rate to give a 4kHz upper frequency response and 7 binary bits. An interesting feature of some of these systems is the polarity reversal of alternate pulses. Thus two pulses form a complete cycle and thus halve the bandwidth requirement.

A demonstration at the Sonex 1973 exhibition gave a direct comparison, with recorded piano music, of results obtained with different bit quantities. When using 12 bits, results were indistinguishable from the 13. At 11, results were still very good but there was a barely perceptible trace of distortion, while at 10 it was more easily detected. From 9 down it became progressively worse. The quantisation distortion has a rather unusual sound which can best be described as a 'crumbling' effect. It should be noted that each binary digit reduction corresponds to a halving of the actual sampling levels, and a doubling of the distortion.

It should be emphasised too, that PCM applies only between studios and transmitters, the broadcast signal being in the normal analogue form irrespective of the type of link used. Digital broadcasting is possible but existing receivers would be rendered obsolete unless both forms existed together, since compatibility is always a major consideration when contemplating any change in a broadcasting system. Furthermore, with the present congestion of the radio bands, the extra bandwidth, although technically easy to achieve, would be impractical. ■




### INFORMATION WANTED

- ...Late registered Student of "Radiostruc" Electronics Training Course. Picking up threads, requires complete set of examination papers including Final Revision Course No. 1A.—W. R. Sharples, 371 Whalley New Road, Blackburn, Lancs.
- ...Any info. on tube in Cossor 3339 serial no. 3'scope. Tube has 'serial no. V10684 Type 09J' on it.—M. Westwood, 103 Mandeville Road, Hertford, Herts.
- ...Circuit diagram or any information on Cossor Oscilloscope (double beam oscilloscope) Model 339. Loan or purchase.—J. L. Bennett, 29 Cleveland Road, Chichester, Sussex.
- ...any info. on "TWIZEHILL" scope Type 0.13L.—J. M. Knight, 32 Malda Road, Bevedere, Kent DA17 6JP.
- ...gen on the Radio Rentals receiver No. 218. Circuit and component types/valves, most helpful.—Stephen Harrold, White Horse, Saham Toney, Thetford, Norfolk P25 7ET.
- ...Wanted to buy or loan, manual or circuit diagram for TCS-6 ex USN Rx.—S. Withnell, 18 Russell Square, Chorley, Lancs.
- ...I wish to purchase the manuals for 62 set Mk II and No. 10 crystal calibrator (including mods.).—M. J. Pearce, 21 Hall Meadow, Wedges Mills, Cannock, Staffs. WS11 1TB.
- ...Information on converting the 1155 Communication receiver to the Aircraft Band.—W. Stanley, 95 Bangor Road, Newtonards, Co. Down, Northern Ireland BT23 3BZ.
- ...any gen on the R and TV Components 3-speed tape deck. What amp should I use, which heads and where should the pressure pads be fitted?—John Watkins, 91 Coniston Road, Patchway, Bristol BS12 5JS.
- ...service sheet for Grundig "Elite-Boy".—W. McQuilston, 16 Eastermeade Gardens, Ballymoney, Co. Antrim, Northern Ireland BT53.
- ...Service sheet/circuit for J & A Margolin Stereophonic A45 Record Player. With photocopy and return.—A. Jones, 11 New Road, Hatfield Peveril, Chelmsford, Essex.
- ...Any info. on receiver valves B.V.A. 276D, B.V.A. 246A, and B.V.A. 266D.—C. R. Jolly, 9 Woodside Road, Bickley, BR1 2ES
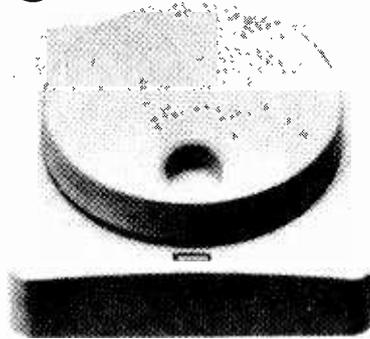
# Cool lighting **for hot parties.**

Velvet dim to full brightness at a touch of the finger. Off/on and infinitely variable.

Beta light glow makes switch easy to find in the dark and consumes no current.



Economical too!

As the light is progressively dimmed, so the current consumption drops – think of it as an electric tap. 300 watt capacity, straight replacement for standard light switch.

Complete kit of parts £2.80 or made up £2.90.



# Hot Ignition for cold mornings.

The Jermyn capacitor discharge ignition system.

Instant starting in all weathers. Even with a near flat battery, the unit will produce a full sized spark.

Just one of the many advantages of an electronic ignition system, the others are:

High energy spark even at maximum revs.



Smoother running.  
Less strain on battery and starter.  
Lower petrol consumption.  
Long plug life with infrequent adjustment (typically 20,000 miles, gapped at .050").  
No contact breaker arcing giving long life and less adjustment (typically 20,000 – 25,000 miles)

STATE + or – earth when ordering.



Complete set of parts to build it yourself for only £7.75, as described in Practical Wireless and fully approved by the author.

**Save 55p**  
Buy both for £10.00

Reprints of the two part feature are available at 25p.

To Jermyn Industries, 161 Vestry Estate, Sevenoaks, Kent.

**All Prices Exclusive of V.A.T.**

Please despatch return of post ..... light dimmer kit ..... light dimmer .....  
Ignition Kits ..... + or – earth ..... £10 pair. Enclose cheque or postal order.

BLOCK CAPITALS

## JERMYN

NAME .....

ADDRESS .....

### SINCLAIR CALCULATORS

Cambridge Kit £14.95 (£1.80)  
Cambridge Assisted £16.95 (£2.00)  
Executive £27.95 (£3.05)  
Executive With Memory £34.95 (£3.75)  
New Sinclair Scientific £39.95 (£4.25)

### FERRANTI ZN414

IC radio chip with data £1.20 (23p). Also available kit of extra parts to complete a radio £2.39 (40p).  
Send sae for free leaflet.

### SINCLAIR PROJECT 80

AFU £6.95 (95p)  
Z40 £5.45 (54p)  
Z60 £6.95 (69p)  
Q16 £7.70 (77p)  
PZ5 £4.98 (49p)  
PZ6 £7.98 (79p)  
PZ8 £7.98 (79p)  
Decoder £7.45 (74p) Trans for PZ8 £3.35 (50p)  
Tuner £11.95 (£1.19) Stereo 80 £11.95 (£1.19)  
Project 80s £28.95 (£2.69)  
2 x Z40/Stereo 80/PZ5 £25.00 (£2.50)  
2 x Z40/Stereo 80/PZ6 £27.75 (£2.77)  
2 x Z60/Stereo 80/PZ8/Transformer £33.11 (£3.31)  
Write for our most competitive quotation




### SINCLAIR GOES QUADRAPHONIC!!

Introducing the Napoles QA10 self-contained matrix quadraphonic synthesizer. Just feed the output of a Project 80 stereo system into it and hook on 4 speakers to obtain the latest experience in sound.  
Send for free leaflet.  
Only £9.95 (£1.30)


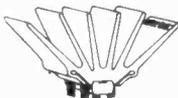
### SINCLAIR SUPER IC12

6W rms power.  
With 44 page booklet and printed circuit  
£2.10 (43p)



### SWANLEY IC TOMORROW £1.80 (40p)

The world's most powerful IC amplifier. Similar to IC12 but rated at 10W r.m.s. power. Supplied with data but no printed circuit. Write for leaflet.

### DELUXE KIT FOR THE IC12

Includes all parts for the printed circuit and volume, bass and treble controls needed to complete the mono version £1.60 (27p). Stereo model with balance control £3.60 (48p)

### IC12 POWER KIT

Supplies 28V 0.5 Amps £2.67 (50p)

### LOUDSPEAKERS FOR THE IC12

5" 8 ohm £1.10 (27p). 5" x 8" 8 ohm £1.55 (37p)

### PREAMP KITS FOR THE IC12

Type 1 for magnetic pickups, mics and tuners. Mono model £1.35 (25p). Stereo model £2.40 (36p)  
Type 2 for ceramic or crystal pickups. Mono 65p (18p). Stereo £1.30 (25p)

### SEND SAE FOR FREE LEAFLET ON KITS

### BATTERY ELIMINATOR BARGAIN

The most versatile battery eliminator ever offered. Switched output of 3, 4.5, 6, 7.5, 9 and 12V at 500mA.  
£4.15 (70p)



### Other eliminators stocked:

250mA.—3 way switched model giving 6, 7.5 and 9V £2.95 (60p).

50mA: 6V £1.80 (40p), 9V £1.80 (40p), 7.5V cassette type £2.25 (40p). Double 6V+6V £2.50 (45p). 9V+9V £2.50 (45p)

### S-DECS AND T-DECS

S-DEC £1.98 (31p)  
T-DEC £3.63 (47p)  
µ-DEC A £3.99 (51p)  
µ-DEC B £6.99 (81p)



### IC carriers:

16 dil: plain 81p (15p) with socket £1.77 (25p)  
10 TO5: plain 78p (15p) with socket £1.68 (24p)  
Experiment guides: A £1.50 (26p), B £1.77 (29p), C 90p (15p), D £2.40 (35p), E £4.20 (53p)

## SWANLEY ELECTRONICS

PO BOX 68, SWANLEY,  
KENT BR8 8TQ.

Please add the sum shown in brackets after the price to cover the cost of post and VAT. Official credit orders from schools etc. welcome. No VAT charged on overseas orders.

### EX COMPUTER PC PANELS

4 x 2in packed with semiconductors and top quality resistors, capacitors, diodes etc. Guaranteed min. 35 transistors, plus data.

10 boards 50p (12p)  
25 boards for £1 (30p)  
Dural extruded heatsinks outline 10D black anodised. Drilled for 4 x TO3 transistors. 5 x 4 x 1 1/4" 40p (14p)  
Similar to above but 5 x 8 x 1 1/4" drilled for 8 x TO3 70p (26p)

### COMPUTER GRADE ELECTROLYTICS

12,000µ 100v, 5 x 2 1/2 dia £1 (25p)  
30,000µ 25v 65p (20p)

### ELECTROLYTICS

4,000µ 70v, 3,600µ 40v, 4 1/2 x 2 in dia 55p (14p)  
10,000µ 35v, 5,000µ 35v, 4 1/2 x 2 in 40p (12p)

100 piv 20A, Si diodes 4 for £1 (10p)  
100 piv 3A, Si diodes 4 for 50p (7p)  
250 mixed resistors 60p (9p)  
250 mixed capacitors 60p (9p)  
200 Si planar diodes 50p (7p)  
Min. glass neons 8 for 50p (7p)  
Reed relays mixed 10 for 50p (7p)  
Micro switches 8 for 50p (9p)  
Papst extractor/blower fans

100 c.f.m. 4 1/2 x 4 1/2 x 2in £3.50 (28p)  
QH bulbs 12v 5w 50p (6p)

Postage and package shown in brackets.  
ADD 10% VAT TO TOTAL


## KEYTRONICS

(Mail Order only)

44 EARLS COURT ROAD  
LONDON W8. 01-478 8499

## H.A.C. SHORT-WAVE KITS

### WORLD-WIDE RECEPTION

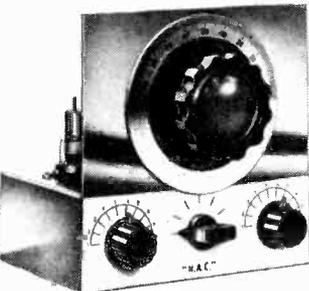

Famous for over 35 years for Short-Wave Equipment of quality. "H.A.C." were the Original suppliers of Short-Wave Receiver Kits for the amateur constructor. Over 10,000 satisfied customers—including Technical Colleges, Hospitals, Public Schools, R.A.F., Army, Hams, etc.

### 1974 "DX" RECEIVER

Complete kit—Price £4.80 (incl. p. & p. & V.A.T.). Customer writes: "Australia, India and America at loud volume." "I have now heard over 300 stations including many Amateurs. I have received 32 Q.S.L. verified reports—from all continents. An amazing one-valver." This kit contains all genuine short-wave components, drilled chassis, valve, accessories and full instructions. Ready to assemble, and of course, as all our products—fully guaranteed. Full range of other S.W. kits, including the famous model "K plus" (illustrated above). All orders despatched by return. Send now for free descriptive catalogue of kits & components. Test Report available. EXCITING COMPETITION for Short-Wave listeners. Send stamped envelope for details.

"H.A.C." SHORT-WAVE PRODUCTS  
P.O. BOX No. 16, EAST GRINSTEAD,  
SUSSEX RH19 3SN

Wire Wound Resistors. Our selection of mixed values. 30 for £1.50. 100 for £4.00.

Audio Amplifier Module. Mullard LP1173, output power, nominal 10 watt, supply voltage +24 volt, with data and circuit, £2.50.

Ferguson Stereogram chassis, Model 3357, all transistor, medium, long, VHF/FM. 3 watts per channel S/M, with connection data, less tuning scale, £20.

Crystals HCSU: 52-03333 MHz: 52-02500: 52-01667: 51-56667: 51-58330: 37-76250: 37-75000: 12-895-8: 12-891-6: 12-700-0: 9-458-33: 9-456-25: 9-455-35: 9-533-35: 9-531-94: 9-530-55: 9-090-62: 9-087-5: 9-096-87: 50p each.

Electrolytics: 32/32/32µF, 325v. 2" x 1 1/2" 35p: 3000µF 50v, 4" x 1 1/2" 40p: 2000µF 30v, 2" x 1 1/2" 25p: 2000µF 50v, 4" x 1 1/2" 25p: 2000µF 35v 3" x 1 1/2" 30p: 470µF 100v 3" x 1 1/2" 25p: 2000/2000µF 25v 2" x 1 1/2" 35p: 30,000µF 25v 4 1/2" x 2 1/2" 50p: 200µF 350v/300/100/32µF 300v 3" x 2" 50p: 700µF 200v 3 1/2" x 1 1/2" 30p: 16/16µF 275v 1 1/2" x 1" 20p: 40/40/20µF 275v 3" x 1" 20p: 4500/900/900µF 30v 2 1/2" x 1 1/2" 50p: 4000µF 35v 3" x 1 1/2" 40p: 200/100/50/100µF 325v 3" x 1 1/2" 50p: 4000µF 18v 2" x 1" 20p: 470µF 25v 1 1/2" x 1 1/2" 15p.

Matched pair of bookshelf speakers. Teak finish, size 12" x 8" x 5". 8 x 5 Ω ohms ceramic, 5 watts RMS. Complete with dia leads. £11.00 pair.

Thorn TV IF chassis, 950 series (less valves), £1.75.

UHF 625-transistor push button tuner (NSF Telefunken) as used on Decca MS2400. Brand new and boxed, £3.25. Light Dependent Resistors (RCA sc3536) 30p each, 4 for £1.00.

Crystal Calibrator (second hand) No 10 crystal controlled heterodyne wave meter covering 500KHz-10MHz. (harmonics up to 30MHz) power required 300V DC 15mA, 12V 0-3A DC test equipment for 62T M/R/C £2.50 each.

P-C Boards (not computer panels) 1 off 6 transistor single wave band. 1 off 4 transistor audio. 1 off 3 transistor £1.60, three boards.

Rank EVR Teleplayer colour translator panels, type and components on new panels listed as follows, £2.50, each panel. Z605-14 off BC148: 2 RCA ca3054 (ic): crystal 4-4336:8 MHz-Z607-12 off BC148: 1 BC108: 1 BC158: 1 RCA ca3046 (ic), 1 RCA ca3045 (ic): Z608-23 off BC14E: 2 BC158-Z612-12 off ME4103: 2 BC-251B: 1 BFY50.

Mains Droppers, 10 mixed values, £1.00.

Edgewise Level meters, 20µA, size 1" overall, 50p.

Chrome Plastic knobs, 3 types, 4 off each with spring clip, £1.25.

Die Cast Boxes, 4 1/2" x 3 1/2" x 3" 95p: 8 1/2" x 5 1/2" x 2" £1.20. 3 1/2" x 5 1/2" x 4" £1.70.

Aluminium Chassis, 7 1/2" x 5 1/2" x 2 1/2" 70p: 10" x 7 1/2" x 2 1/2" 85p. 11" x 7 1/2" x 2 1/2" 95p.

BSR P123, similar to HT70 single play, with heavy die cast turntable, less cartridge, £11.00.


Transistorised FM tuner head, with A.M. gang, slow motion drive 88-108 Mcs, with circuit diagram, £2.30.

ALL ITEMS INCLUDE VAT  
All items post paid in GREAT BRITAIN

## SURPLECTRONICS

216 LEAGRAVE ROAD,  
LUTON, LU3 1JD, BEDS.

TOP QUALITY—LOW COST

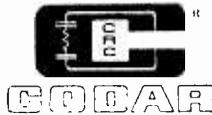


AMATEUR RADIO EQUIPMENT




**P.R.40**  
SOLID STATE  
R.F. PRESELECTOR

The PR40 R.F. Preselector is the solid state version of the world famous PR30 which is now superseded.  
It employs Silicon "N" Channel FET (Field Effect Transistor) front end followed by silicon NPN Broad Band R.F. Amp., and will substantially improve receiver performance over the range 1.5 to 35 MHz, providing a considerable increase in gain up to an overall average of 30dB, with improved image rejection and noise ratio.  
Supplied complete with co-ax plug (less standard 9 volt PP6 Battery). 12 months Guarantee.  
£11-13 Carr./VAT Paid

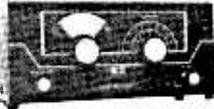

**MULTIBAND—6**  
SOLID STATE  
SHORT WAVE RECEIVER KIT

All transistor 1.R.F. Receiver tunes 550 KHz to 30 MHz (540 to 10 metres) complete coverage—no gaps. Medium waves—Trawlers—Ship / Shore Telephone—All Six Amateur Bands 160-10 metres—International Broadcast from Australia, Far East, Russia, USA etc. using 4 miniature plug in Coils. Hi-Gain FET Regen. Det./AF Module giving full loudspeaker output to any external 2/3 ohm speaker. Receives AM/CW/SSB. Separate Electrical Bandspread, Calibrated Main Tuning. A Quality CODAR-KIT with 12 months Guarantee. No technical knowledge required, simple to build, printed circuit and Pictorial instruction Manual, fully detailed step by step.  
Complete Kit with 4 Coils (less standard PP6 battery).  
Stamp brings illustrated leaflets.  
£16-40 Carr./VAT Paid

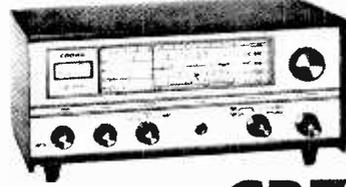

**CR70A**  
COMMUNICATION RECEIVER

The CODAR CR70A is an outstanding general coverage communication receiver, ideal for the keen S.W.L.  
It tunes from 540 metres medium through to 10 metres with no gaps. Covers shipping, coastguard and distress frequencies, all six amateur bands 160-10 metres, International broadcast, Met. stations etc. etc. giving world-wide reception. Exclusive features include Air-spaced CODAR-COIL Hi-"Q" Aerial input, illuminated Meter and Slide Rule Scale, Two Speed vernier tuning, Switched B.F.O. for CW/SSB signals. Separate output for Tape recorder.  
Ready to plug in to 200/240 volts A.C. it only needs your aerial and a 2/3 ohm loudspeaker to bring the world to your finger tips. 12 months full guarantee.  
Complete factory tested £32-56 VAT Paid/Carr. 80p.

NOTE: The CR70A has achieved a world wide reputation for quality and performance, and is exported to many countries throughout the world.

Illustrated leaflets are sent on request, together with lists of unsolicited testimonials, the original letters being available for inspection at any time.

ON THE DESIGN STAFF—  
G3SZM G3JRE

**CODAR**

TELECOMMUNICATIONS AND ELECTRONIC  
EQUIPMENT SUPPLIERS TO H.M. AND OVERSEAS  
GOVERNMENTS

VALCON WORKS · BURRELL BUILDINGS · CHURCHILL INDUSTRIAL ESTATE · LANCING · SUSSEX

Tel. 090-63-61901

BN15 - 8TZ



**BENTLEY ACOUSTIC CORPORATION LTD.**

7a GLOUCESTER ROAD, LITTLEHAMPTON, SUSSEX  
All prices inclusive of V.A.T. Telephone 6743

0A2	.40	8BA6	.58	1L80T	.58	12K70T	.45	35Z40T	.55	8P200	1.00
0B2	.40	8CB8	.60	6L7	.50	12Q70T	.45	35Z60T	.75	8180F	1.00
0Z4	.47	6BE6	.32	6L16	.55	12B7C	.50	50B85	.65	8182CC1.00	
1A3	.45	6BH6	.70	5L19	3.00	12B7G	.40	50C25	.45	81148	.58
1A6GT	.60	6BJ6	.55	6L1D20	.75	12B7H	.55	60D60	1.25	EA90	.87
1A7GT	.65	6B7A	.65	6N7GT	.80	12B7J	.45	50E16	.55	EA78	1.00
1B8T	.50	6B8T	1.00	6Q70	.60	12B7K	.55	60L60T	.55	EA3C80	.85
1H4T	.55	6BR8	.35	6Q70T	.60	14H7	.55	85A24	.60	EAC91	.75
1L4	.20	6B8T	1.40	6Q7(M)	.55	1487	.55	85A43	1.00	EAF42	.60
1N64T	.65	6BW6	.60	6R70	.60	19A46	.60	90C1	2.40	EAF801	.75
110	.45	6BW7	.65	6R7M	.75	19G6	1.40	90C9	2.75	EA34	.85
1B4	.38	6BZ6	.49	6BA7	.44	30D4	.80	100B24	.75	EB91	.10
1U4	.40	6CB8A	.40	6BC7GT	.38	30P2	.75	21680	.60	EB41	.65
1U5	.75	6C4	.30	6B3T	.44	20L1	.85	807	.65	EB081	.35
2D21	.40	6C8	.40	6BH7	.44	20P3	.60	5702	.80	EBF80	.80
2QK6	.55	6C8	1.25	6B3T	.55	20P4	1.00	8057	.80	EBF81	.40
2X2	.50	6CD6G	1.00	6BK7GT	.44	20P5	1.00	6080	1.00	EBF89	.30
3A4	.50	6C8A	.75	6B3GT	.45	25A6G	.38	8087	1.00	EBL21	2.00
8D6	.40	6C116	.60	6V6G	1.17	25L40	.80	7475	1.00	EC86	.70
8Q4	.60	6C116	.55	6V6GT	.45	25Y5G	.70	AC/PEN	.98	EC88	.70
8Q4GT	.85	6C15A	.80	6X4	.40	25Z4G	.38	AC/PEN	.98	EC92	.45
8M4	.85	6CM7	.75	6X6GT	.40	25Z6	.80	DD	.98	EC035	1.50
4CB4	.55	6C8U5	.75	7B6	.75	25Z6G	.70	AC/6P	.98	EC036	.95
6C8	.55	6CW4	1.00	7B7	.70	28B7	1.00	AC/AT1	.81	EC040	1.00
6Y40Y	.75	6D6T	.75	7B7	.70	80A5	.55	AL80	1.00	EC081	.34
6U40	.35	6L70A	.75	7B7	.80	80C15	.75	AT14	.40	EC082	.38
6V40	.64	6E6	.75	7Y4	.65	80C17	.90	AZ1	.60	EC083	.88
5Y8GT	.45	8E6	1.00	7Z4	.80	80C18	.78	AZ31	.60	EC084	.80
5Z3	.70	8F1	.70	9D7	.65	80F6	.60	AZ41	.65	EC085	.35
0Z40	.65	8F6G	.40	10C2	.65	80ML1	.75	BL83	2.00	EC086	.85
0Z44T	.45	8F13	.65	10D7K	.65	80FL2	.75	CL88	1.65	EC088	.44
6S012	.30	8F14	.75	10E1	.60	80FL11	1.00	CY1C	1.00	EC089	.65
6AB1	1.25	8F18	.65	10F9	.65	80FL13	.55	CY13	.45	EC089.65	
6AC7	.49	8F23	.80	10F18	.55	80FL14	.70	DAF91	.30	EC08701.00	
6AG5	.87	8F24	.85	10L11	.70	30L15	.78	DAF96	.44	EC0F80	.34
6AH6	.60	8F25	1.00	10P13	.70	30L17	.70	DF91	.30	EC0F82	.75
6AJ3	.75	8F28	.60	10P14	2.00	30P4MR	.80	DF92	.44	EC0F85	.85
6AK6	.35	8F32	.65	12A6	1.00			DK40	.70	EC0F84	.75
6AK6	.80	8G0G	.75	12AC5	.65	80P12	1.80	DK92	.70	EC0E1	2.00
6AN8A	.65	8G18A	.75	12AD6	.65	80P19	.80	DK96	.60	EC0E2	2.00
6AN8	.60	8G16	.65	12AE8	.65	80P4	.75	DL92	.85	EC0E3	2.25
6AQ5	.42	8G07	.75	12AT6	.38	80P11	.65	DL96	.55	EC0E4	.70
6AR5	.65	8H0GT	.25	12AU6	.45	80P19	.75	DM70	.44	EC0E1	.20
6AR5	1.00	8J5GT	.40	12AV6	.60	80P14	.80	DM71	2.00	EC0E3	.44
6AT6	.35	8J6	.25	12BA6	.40	80P15	.90	DY787	.80	EC0E4	.44
6AV6	.60	8J70	.30	12BE6	.50	35A3	.65	DY802	.33	EC0L80	.40
6AU6	.38	8J8A	.75	12BH7	.50	85D5	.75	28B00C	1.65	EC0L82	.34
6AW8A	.65	8K72	.25	12E1	3.00	35L6GT	.55	28B0F	1.30	EC0L83	.87
6AX4	.75	8K8G	.45	12J7GT	.55	35W4	.40	28B3F	1.80	EC0L84	.60
618G	.80	8L1	2.00	12K6	1.00	35Z3	.75	28BCC	1.00	EC0L85	.60

8CL86	.40	EZ41	.27	8EN45	.60	UHF80	.65	AA119	.17	BA129	.14	OA70	.17
8F29	1.60	GY601	.75	8EN45DD	.70	UCH912	.00	AA120	.17	BA130	.11	OA75	.10
8F40	.75	GZ22	.64	8EN45	.60	UCH42	.70	AA129	.17	BA153	.17	OA79	.10
8F41	.75	GZ23	1.00	8EN46	.50	UCH81	.88	AA213	.20	BC107	.14	OA81	.10
8F42	.65	GZ24	.65	8EN45DD	.70	UCL82	.88	AC107	.17	BC138	.14	OA85	.09
8F73	1.60	GZ37	.67	PENDD	2.00	UCL83	.85	AC113	.28	BC113	.28	OA90	.14
8F80	.80	HABCO	.50	HL2ADD	.75	4020	2.00	UF42	.70	BC115	.17	OA91	.10
8F93	.35	HL41DD	.42	HL33	.50	UF80	.85	AC128	.22	BC118	.25	OA95	.10
8F96	.30	HL42DD	.70	PL36	.55	UF86	.44	AC132	.22	BCY10	.50	OA200	.10
8F99	.37	HN309	1.50	PL81	.44	UF86	1.00	AC154	.28	BCY12	.55	OC22	.48
8F91	.37	HV82	1.00	PL81A	.65	UF89	.88	AC156	.22	BCY3	.22	OC23	.48
8F92	.40	HV82A1	.00	PL82	.40	UL41	.65	AC157	.28	BCY38	.25	OC24	.48
8F98	.80	KT4	.98	PL83	.50	UL64	.42	AC165	.28	BCY38	.25	OC25	.48
8F183	.89	KT44	1.00	PL84	.38	UM80	.44	AC166	.28	BCY39	.28	OC38	.47
8F184	.38	KT65	2.40	PL504/500	U741	.49	AC168	.42	BC211	.48	OC44	.11	
8F86	.80	KT81	2.00	PL505	1.15	U10	1.00	AC176	.61	BF188	.58	OC45	.18
8F89	.45	KW61	1.00	PL508	.90	U12/14	1.00	AC177	.81	BF189	.58	OC46	.18
8F82	.50	KW82	1.00	PL609	1.15	U19	1.75	ACY18	.22	BF183	.82	OC70	.14
8F83	2.50	MHLD2	81	PL802	.95	U25	.80	ACY19	.21	BF180	.38	OC72	.18
8F84	2.50	MHL62	1.00	PL802	.95	U26	.60	ACY20	.20	BF181	.44	OC74	.95
8F85	2.50	MHL62	1.00	PL802	.95	U26	.60	ACY21	.21	BF185	.44	OC75	.18
8F86	2.50	MHL62	1.00	PL802	.95	U26	.60	ACY22	.17	BF194	.17	OC76	.17
8F87	2.50	MHL62	1.00	PL802	.95	U26	.60	ACY23	.20	BFY60	.25	OC77	.18
8F88	2.50	MHL62	1.00	PL802	.95	U26	.60	ACY24	.20	BFY61	.25	OC78	.17
8F89	2.50	MHL62	1.00	PL802	.95	U26	.60	ACY25	.20	BFY62	.25	OC78D	.17
8F90	2.50	MHL62	1.00	PL802	.95	U26	.60	ACY26	.20	BFY63	.25	OC78D	.17
8F91	2.50	MHL62	1.00	PL802	.95	U26	.60	ACY27	.20	BFY64	.25	OC78D	.17
8F92	2.50	MHL62	1.00	PL802	.95	U26	.60	ACY28	.20	BFY65	.25	OC78D	.17
8F93	2.50	MHL62	1.00	PL802	.95	U26	.60	ACY29	.20	BFY66	.25	OC78D	.17
8F94	2.50	MHL62	1.00	PL802	.95	U26	.60	ACY30	.20	BFY67	.25	OC78D	.17
8F95	2.50	MHL62	1.00	PL802	.95	U26	.60	ACY31	.20	BFY68	.25	OC78D	.17
8F96	2.50	MHL62	1.00	PL802	.95	U26	.60	ACY32	.20	BFY69	.25	OC78D	.17
8F97	2.50	MHL62	1.00	PL802	.95	U26	.60	ACY33	.20	BFY70	.25	OC78D	.17
8F98	2.50	MHL62	1.00	PL802	.95	U26	.60	ACY34	.20	BFY71	.25	OC78D	.17
8F99	2.50	MHL62	1.00	PL802	.95	U26	.60	ACY35	.20	BFY72	.25	OC78D	.17
8F00	2.50	MHL62	1.00	PL802	.95	U26	.60	ACY36	.20	BFY73	.25	OC78D	.17
8F01	2.50	MHL62	1.00	PL802	.95	U26	.60	ACY37	.20	BFY74	.25	OC78D	.17
8F02	2.50	MHL62	1.00	PL802	.95	U26	.60	ACY38	.20	BFY75	.25	OC78D	.17
8F03	2.50	MHL62	1.00	PL802	.95	U26	.60	ACY39	.20	BFY76	.25	OC78D	.17
8F04	2.50	MHL62	1.00	PL802	.95	U26	.60	ACY40	.20	BFY77	.25	OC78D	.17
8F05	2.50	MHL62	1.00	PL802	.95	U26	.60	ACY41	.20	BFY78	.25	OC78D	.17
8F06	2.50	MHL62	1.00	PL802	.95	U26	.60	ACY42	.20	BFY79	.25	OC78D	.17
8F07	2.50	MHL62	1.00	PL802	.95	U26	.60	ACY43	.20	BFY80	.25	OC78D	.17
8F08	2.50	MHL62	1.00	PL802	.95	U26	.60	ACY44	.20	BFY81	.25	OC78D	.17
8F09	2.50	MHL62	1.00	PL802	.95	U26	.60	ACY45	.20	BFY82	.25	OC78D	.17
8F10	2.50	MHL62	1.00	PL802	.95	U26	.60	ACY46	.20	BFY83	.25	OC78D	.17
8F11	2.50	MHL62	1.00	PL802	.95	U26	.60	ACY47					

# TAKE 20

DAVID ANDREWS


No. 62

VARIABLE RATIO COUNTER

A series of simple transistor projects, using not more than twenty components.

THIS circuit gives a fast 9V positive-going pulse for a preset number of operations of the push button PB1. The principal of operation is the diode pump circuit. When the button is pressed C1 discharges into C2 through D1; as soon as the discharge is complete D1 prevents any back flow of the charge out of C2 and provided D1 and Tr1 and Tr2 all have low leakage characteristics this charge will remain on C2 as a voltage.

Repeated pressing of PB1 will build up the potential on C2 until it exceeds the level set at the base of Tr1 which is preset by VR1. When this happens Tr1 and Tr2 go rapidly into conduction, aided by regenerative feedback, and C2 is discharged giving rise to a negative going signal at the collector of Tr2. This is fed to the PNP transistor (Tr3) and generates a 9V spike with a reasonably low source impedance.

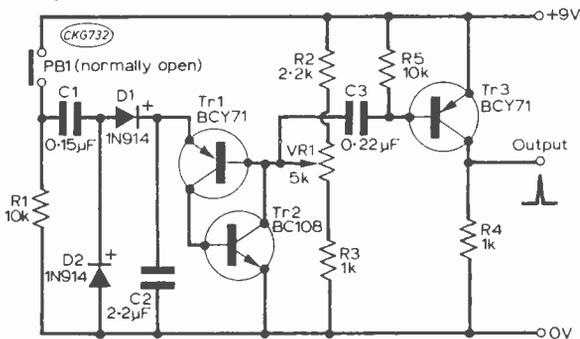


Circuit of the variable ratio electronic counter.

With the values shown the circuit should divide satisfactory up to frequencies of about 1kHz. To interface the input with an electronic drive source PB1 and R1 should be discharged and C1 should be taken straight to a point that can give DC voltage swings from 0V to +9V at low impedance, e.g. the emitter of an emitter follower that is normally held at 0V. The output of the circuit can easily be used to drive a pulse stretching circuit which could trip a low speed counter or a relay.

## ★ components list

R1 10kΩ ½W	R4 1kΩ ½W
R2 2.2kΩ ½W	R5 10kΩ ½W
R3 1kΩ ½W	
VR1 5kΩ linear pot.	
C1 0.15μF	C3 0.22μF
C2 2.2μF low leakage polycarbonate	
D1/D2 1N914	
Tr1 BCY71 (general purpose pnp silicon)	
Tr2 BC108	Tr3 BCY71
PB1 Normally open push button	

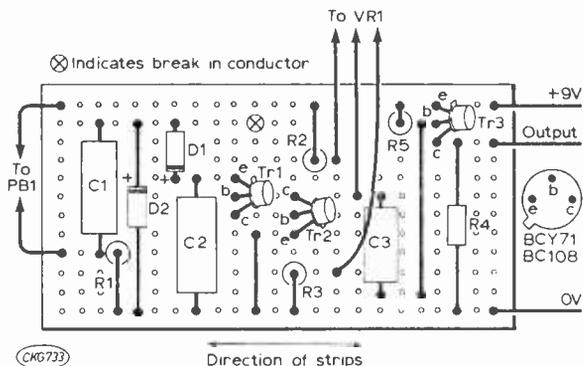

Circuit arranged on Veroboard, VR1 and pushbutton being mounted externally.

The divide ratio is given by the number of times PB1 has to be pressed before C2 is discharged by the transistors and with the values given in this circuit is adjustable, by means of VR1, between about 3 and 20. If the repetition rate of button pressing is low there is bound to be some charge lost from C2 due to its own and transistor leakage. However, the prototype worked quite reliably at a rate of approximately one press per second. It is, however, anticipated that this circuit would interface with an electronic source of signal operating at a low audio frequency and this problem is then not likely to arise.

## P.W. ELECTRONIC COMPONENTS BUYERS' GUIDE

Special supplement in the October issue giving details of components commonly available, followed by additional sections in succeeding issues. More details on page 116 of the June issue.

## WIRELESS TELEGRAPHY ACT

Readers and advertisers are reminded of the requirements laid down by the Wireless Telegraphy Act. It is an offence in the U.K. to install or operate wireless telegraphy apparatus except under the provisions of the Act and, except in the case of broadcast sound-only receivers, a licence must be obtained. Included within the provisions of the Act are any apparatus transmitting deliberate signals for any purpose such as "walkie-talkies", radio-controlled models or servos and some types of metal detectors. Apparatus radiating interference signals are subject to controls which also come under the administration of the same Ministry. If you require full information, please write to *Waterloo, Bridge House, Waterloo Rd., SE1 8UA.*

## P.W. TOOL KIT OFFER

Demand for the above tool kit far exceeded expectations and we have had to look for alternative supplies. We apologise to all those readers who have been kept waiting. By the time this issue appears we expect to have cleared the arrears of orders.

# EXPERIMENTAL WORKSHOP

M. J. HUGHES M.A.

## LEARNING BY PRACTICAL PROJECT STEPS

### PART 10—LOUDSPEAKER DRIVERS

IN ANY audio system there comes a time when it is necessary to use electronic signals to drive a loudspeaker. This part of the series will describe several alternative ways this can be done but we shall limit ourselves to considering only low powers in the experimental projects mentioned. The reason for this is solely to keep construction simple and to ensure that only low cost components need be used. Having said that let us hasten to add that the principles to be described are also applicable to the highest of power amplifiers, however, there are usually special protection circuits in these cases which tend to complicate the issue—and in many instances the protection circuitry can be more complex than the amplifier itself.

In one or two previous projects we have driven loudspeakers without saying too much about the method we have adopted; now is the time to fill the omission.

In an amplifier we have to provide several logical stages of amplification some of which we have already covered; basically these can be summarised as, (a) an input pre-amplifier which helps compensate for the impedance of the signal source, (b) a stage which will tailor the frequency response or provide a degree of tone control and (c) a stage that increases the level of signal voltage; this latter stage often brings the signal level up to the maximum needed for the application but usually the output impedance of such a stage is fairly high and certainly cannot be used to pass sufficient current through the low impedance of a loudspeaker speech coil—which can be anything in the range of from 3 to 70 ohms. The prime objective of a power stage is to take the output from the voltage amplifier and match this to the low impedance of the loudspeaker's coil; at the same time a degree of voltage amplification might also be applied.

The loudness of a loudspeaker is proportional to the amount of electrical power one can dissipate within the speech coil of the loudspeaker. If one knows the impedance of the loudspeaker the power can be quite simply calculated in terms of either the voltages developed across the speech coil or the current flowing through it. These, of course, are a.c. quantities because we are dealing with signals as opposed to bias currents—in some instances (as

we shall see) we have to take account of the latter. If we assume that all the current flowing through the coil is a.c. and comprises signal current the power dissipation can be stated as

$$I^2 \times Z \text{ or } \frac{V^2}{Z}$$

where  $I$  is the current through the coil and  $V$  is the voltage developed across it (these can be peak or r.m.s. values depending on whether we are dealing with r.m.s. or peak power).  $Z$  is the loudspeaker's impedance. It is simpler to take the second equation for most purposes and we can see from it that for a given signal voltage we get most power dissipation for the smallest loudspeaker impedance; however we must ensure that the voltage source is not "current limiting" i.e. it must come from a very low source impedance.

For maximum power coupling the source impedance should equal the loudspeaker's impedance. Assuming ideal impedance matching ;if we have a signal amplified to 1V r.m.s. and apply this to a 35Ω loudspeaker the output power will be

$$\frac{1 \times 1}{35}$$

which is just under 30mW; reducing the speaker impedance to 3Ω would, theoretically, give about 300mW of power but the current requirement would be up by a factor of about ten.

It would be better to double the voltage of the signal to get higher power, because there is a square law relationship between the two, and one does not have to provide a very low source impedance—this is always difficult and provides other problems with power supplies etc. For highest powers it is obviously desirable to have as high a signal voltage as possible together with a low impedance output. To obtain 50W into a 15Ω loudspeaker would require signal voltages in the order of 27.5V r.m.s. To obtain this high signal level it is necessary to have power rail voltages in excess of 50V. It is thus impossible to get really high powers unless one is prepared to operate with reasonably high voltages as well as low loudspeaker impedances.

Throughout this series we have operated, in the main, with a 9V supply rail and a 35Ω loudspeaker. Assuming we made preamplifiers with ideal mid rail

biasing the peak signal voltages we could obtain would be 4.5V which corresponds to about 3.2V r.m.s. Given these parameters the maximum powers we could produce would not exceed 300mW r.m.s.

Summing up, we need to get as high a current with as high a voltage as possible across the speech coil and the experiments that follow show various attempts at getting to this end by different methods—each method has its pros and cons which we shall discuss.

Fig. 71 shows an obvious way of driving a loudspeaker and is an extension of the grounded emitter amplifier—covered in previous parts. Strictly speaking we should consider the loudspeaker as having an impedance a.c. signal but in practice this is very close to its d.c. resistance; inductance is low and hence inductive reactance at low frequencies is fairly small. If one considers LS1 of Fig. 71 as being a 35Ω resistor we can select a value for R1 which will give us a mid rail bias at the collector of Tr1.

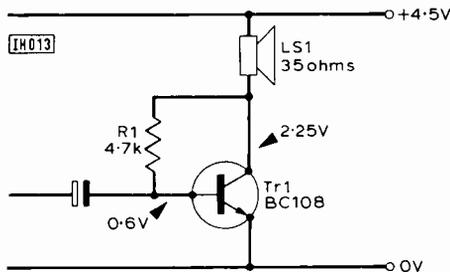


Fig. 71: For the collector potential to be mid rail  $I_c$  65mA and hence R1 must be about 5kΩ. Quiescent power dissipation in Tr1 is about 150mW. Input impedance is low.

Before doing this we have to consider the maximum current rating of the transistor with reference to the maximum current that might flow through LS1 when the transistor is fully conducting. Imagine that the supply voltage was our usual 9V and that Tr1 was fully conducting; the potential at the collector would be a fraction of a volt (the saturation voltage) and the current flowing would be nearly

$$\frac{9}{35} = \text{approx } 250\text{mA.}$$

This is more than twice the current rating for the transistor hence if a.c. input signals were of sufficient amplitude we might drive the transistor into saturation and burn it out at the same time. By reducing the supply rail to 4.5V we would only just be exceeding  $I_c(\text{max})$  for the BC108 even if we applied this maximum input signal. Due to saturation voltages and forward drops in the preceding circuits it would be unlikely that the collector current would exceed the maximum rating of 100mA. We have thus deduced that with this particular transistor the maximum supply voltage in this application is 4.5V for safety. R1 is calculated in the same way as in a previous part to give a mid rail collector voltage so that signals can give peak positive and negative going excursions of 2.25V.

Wire up the circuit of Fig. 71 and measure the quiescent voltages but also take special note of the quiescent current being drawn in the absence of input signal. It is comparatively high and causes power to be dissipated in the transistor and the

speech coil of the loudspeaker to no useful effect. This is a feature of this type of amplifier which comes into the general class of Type A circuits. The maximum r.m.s. power output for a 2.25V peak signal would be approximately 70mW and this compares with nearly 150mW of static dissipation caused by the quiescent current. Not very efficient!

In theory the maximum efficiency of a Class A amplifier is 50 per cent and this is its main drawback; it means that transistors get unduly hot, a lot of current is drawn from the supply under quiescent conditions and, in the case of portable equipment, one would suffer from rapid battery exhaustion. Some Hi-Fi purists will claim—probably correctly—that the class A circuit will provide the best fidelity of signal reproduction because the transistor is operating as a “more or less” linear amplifier, i.e. the current through the loudspeaker is directly proportional to the signal current and there is no way that distortion can creep in. This, of course, is not strictly true—particularly in a simple circuit such as this one because, for a start,  $h_{FE}$  for a transistor varies with collector current and thus the true linearity (assumed) is not realisable in practice without considerably more complexity. Nevertheless this is a very simple way of providing an audio low power output in simple applications—in particular those that will be subjected to intermittent use.

An example is shown in Fig. 72 where the output from a simple oscillator is used to drive a loudspeaker as a morse practice oscillator. When constructing this unit observe that LS1 must be 35Ω and the supply should not exceed 4.5V.

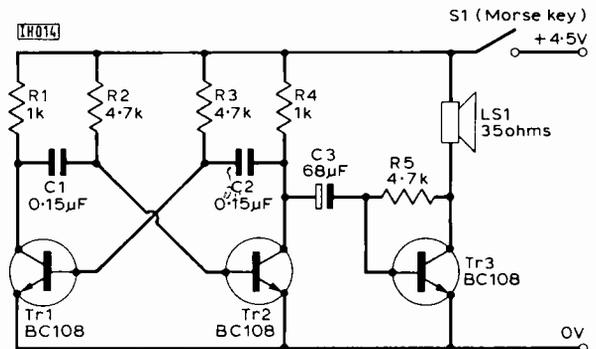


Fig. 72: Using the simple class A power stage in a morse practice oscillator circuit. As the signal voltage is high C3 could be omitted and R5 is then connected directly between Tr2's collector and Tr3's base.

Because we have signals as high as 4.5V at the collector of Tr2 it is not necessary to have C3 in circuit because the signal will be driving Tr3 from one extreme of conduction to the other and the sophistication of mid rail biasing is not necessary hence the circuit can be simplified by taking R5 from the collector of Tr2 direct to the base of Tr3.

To obtain a higher output power we need to increase the supply voltage and reduce the loudspeaker's impedance. If this is done we have to use a transistor with a higher current and power dissipation rating; at the same time we illustrate, in Fig. 74, how we can use the simple expedient of making the power stage from an emitter follower (the input signal is so high that we do not need any form of voltage amplification). To provide sufficient

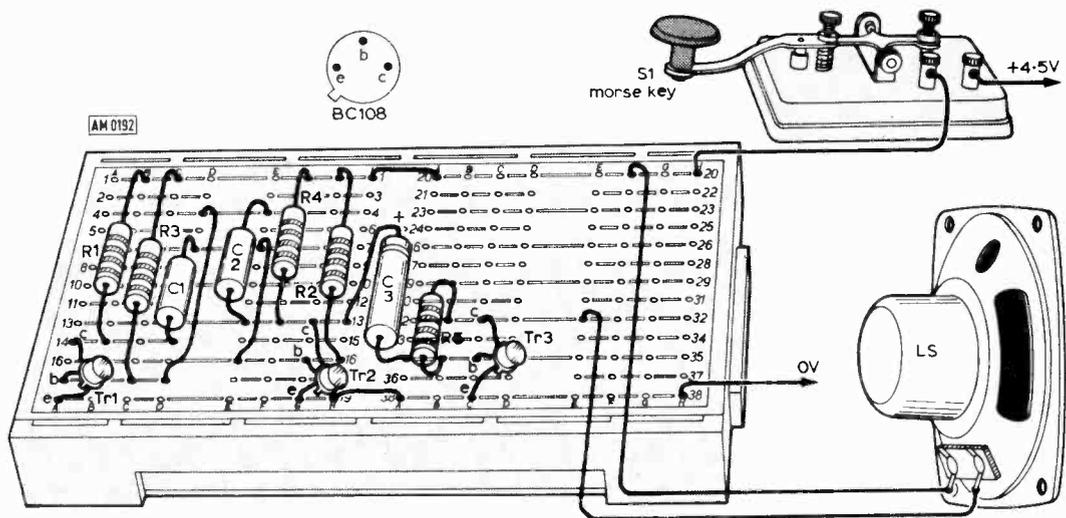


Fig. 73: Layout for Fig. 72

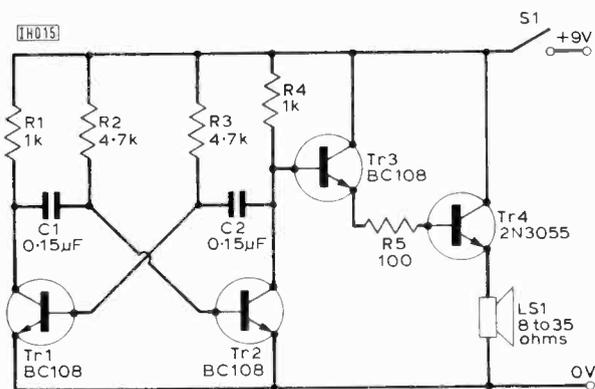


Fig. 74: Using a power transistor and an emitter follower driver enables us to use a lower resistance load (giving more power) and at the same time we can increase the supply voltage for more power.

signal base current into Tr4 without loading the output of the multivibrator we have inserted Tr3 making, in effect, a super alpha pair. This type of output is ideal if we are not worried about mid rail biasing in the output stage.

The base of Tr3 could have been connected directly to the collector of a conventional grounded emitter amplifier and the mid rail voltage would automatically have been reflected in the quiescent potential at Tr4's emitter—if one allows for base/emitter forward drops. The only problem with that would be that there is a high standing quiescent current flowing through the speech coil of the loudspeaker giving rise to heating and also the cone would be displaced preferentially in one direction.

**To be continued**

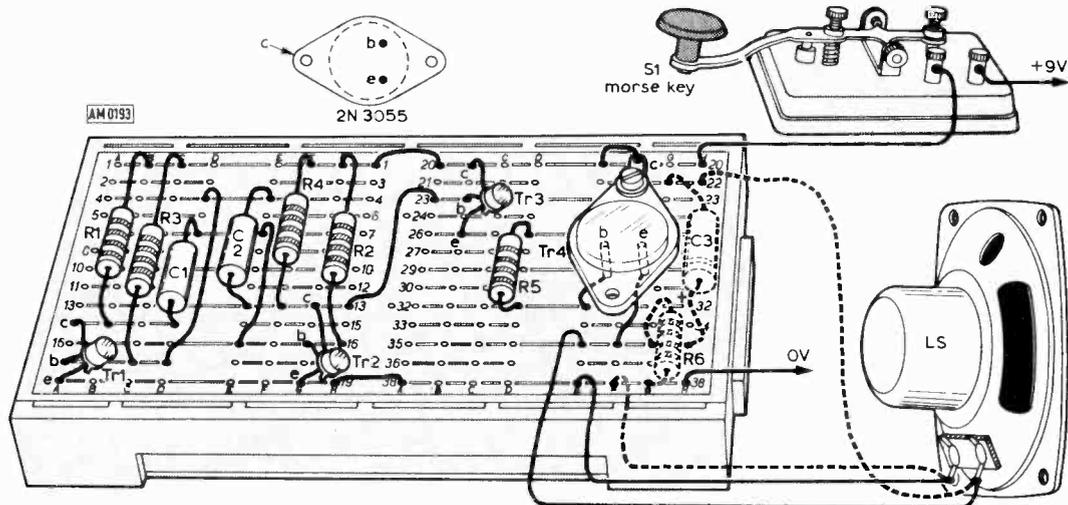


Fig. 75: Layout for Fig 74

# HOTLINES

ON RECENT DEVELOPMENTS

## NO TICK GIVEN HERE

CMOS circuits intended to form a two-chip digital watch system have recently gone into quantity production at Intel. A total average power consumption of only  $15\mu\text{W}$  means that the watch will operate for more than a year from one mercury cell.

The oscillator/divider chip is intended for use with a 32kHz crystal and is capable of an accuracy of better than 1 minute per year. The other chip contains the decoder/driver circuitry and is offered in two versions. One of these provides the facility of being able to switch the display to show minutes and seconds. The hours display is then blanked. To help you time intervals of a few seconds, both versions of the output chip cause the colon separating the hours and minutes to flash at 1Hz.

## GROWING

Developments in liquid crystal displays continue apace. A French company has recently exhibited a 5000-point matrix display giving a text of 96 characters and, even more intriguing, a simple animated picture display twelve inches square.

At the IEA exhibition in London, an Austrian firm was showing a seven-segment display some 6 inches high.

## MORE SCOPE OR LESS?

Whilst television CRTs have got a lot shorter over the years, those used in oscilloscopes have stayed much the same length, mainly as a result of the good deflection linearity required. Now Philips have developed a new type of CRT which has a diverging lens in the form of a domed mesh between the deflection plates and the screen. The tube length for a given size of display is considerably reduced as a result.

## ELECTRIFYING

News from the USSR that scientists at the Latvian Academy of Sciences have discovered a method of rotating non-metallic objects by passing them through an intense electric field. This effect, similar to that of a magnetic field upon ferromagnetic materials, has been demonstrated using wood, mica and plastics components. Suggested practical applications include alignment of parts on a conveyor belt or in other assembly systems.

## SOMETHING'S MOVING

Small enough to be held in the palm of the hand, Mullard's new X-band (3cm.) Doppler transmitter-receiver modules may well find application in future vehicle collision alarms.

Greatly enhanced signal-to-noise ratio has been achieved by using separate cavities for the transmitter oscillator and receiver detector, both coupled to a single integral antenna.

When used in an intruder detection system, the module can pick out a man moving at a range of 50 feet. Just the thing to protect your priceless art treasures!

## SUNPOWER

In the United States, a Senate investigation has been set up to consider Federal support for a programme of solar energy development. Giving evidence to the investigating committee, RCA Research director Paul H. Rappaport forecast that economical solar energy systems could be in widespread use in the U.S. within five years.

A planned extension to the RCA Building in New York will use solar energy to help run its heating and air-conditioning system.

## FACE TO FACE

A spin-off resulting from the recently introduced local government changes is a new video-telephone system developed by Rediffusion Industrial Services.

The idea was that members of the public wanting to make an enquiry or complaint should not have to travel long distances to one of the new regional government offices in order to see an officer specialising in a particular field. Instead they would go to their local office where an automatically operated console would give them "across-the-desk" contact with the regional office via video-phone. Also included is a document scanner large enough to show household goods or package foods which may be the subject of complaint.

Already, one large company has expressed interest in the system as a means of providing conference facilities for its senior managers.

It would appear that the system has great potential for saving time and fuel by reducing the need for travel.

## MULTIPLEX


More news from British Rail on improved communications, this time aboard Inter-City expresses.

Equipment being fitted will provide three channels—guard to passenger, guard to driver and an audio message playback system which is controlled by distance travelled along the track. All this information is distributed through the train on only two wires, which are also used to control the train lighting.


Rather special measures have been taken to protect the audio equipment from spikes on the train wiring. These spikes can reach 7kV!

*News*

# Listen clearly!

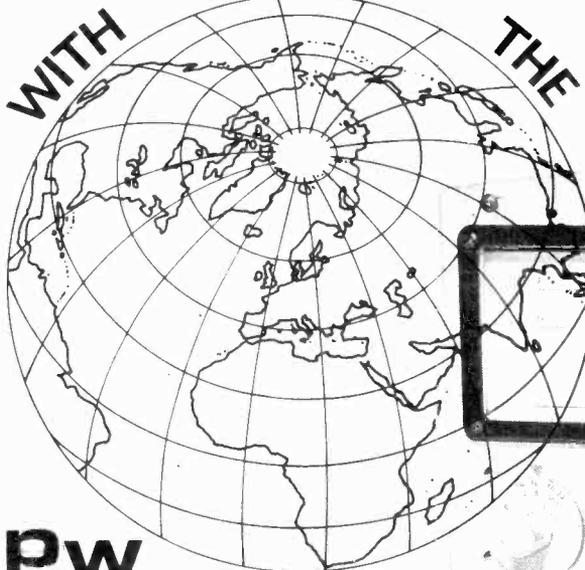


# IN NEXT MONTH'S PRACTICAL WIRELESS

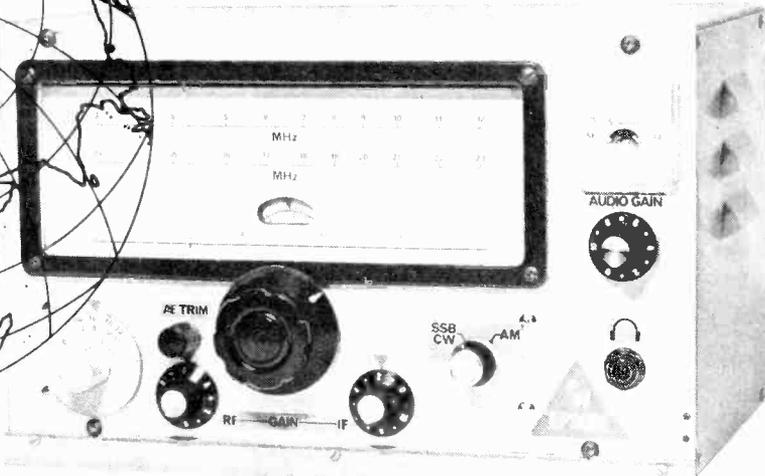

**PW  
EPSOM  
GENERAL COVERAGE  
SHORT WAVE  
RECEIVER**

Do you get annoyed at interference apparent on some short wave stations? Do you find the same station twice, once where it should be on the dial and again where it shouldn't? These problems are frequently generated in the receiver itself. Listen to the bands as they really are, on the 'Epsom' receiver. Alignment is simplicity itself—no expensive test gear needed. One range calibration method sets up whole spectrum 2.5 to 23MHz. Copies AM, CW and SSB signals with automatic sideband switching. Its special features can be built into your own receiver.

**add-on AUDIO  
SQUELCH**

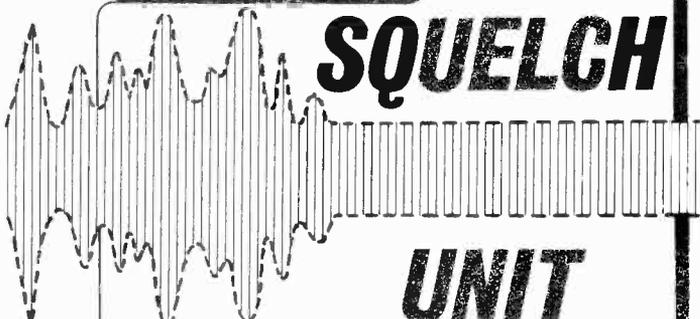

**UNIT**

Audio squelch circuits are frequently found in radiotelephones, cutting out objectionable noise in the absence of a signal. This simple one-IC unit can be fitted to a public address, intercom or other audio system where a high background noise level presents a problem.

**ALL ABOUT  
FET'S**

Field-effect transistors are quite common nowadays in D-I-Y electronic projects but what do you really know about them? We eliminate the mystery and show how they work and describe their advantages. Many practical circuit applications complete a useful guide to FET's.

**MANY OTHER CONSTRUCTIONAL  
ARTICLES, SPECIAL FEATURES  
AND REGULAR COLUMNS  
ON SALE IN AUGUST**

The above details are subject to the national industrial situation at the time of going to press.

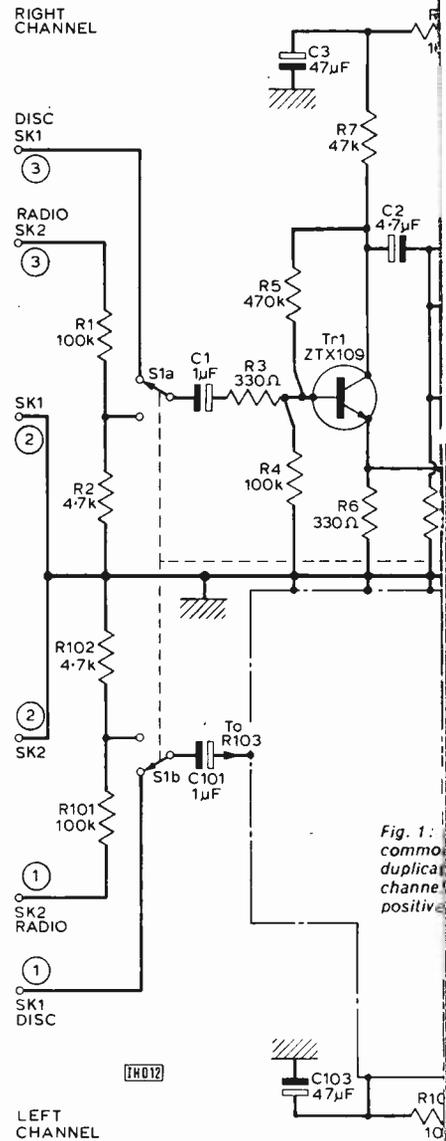
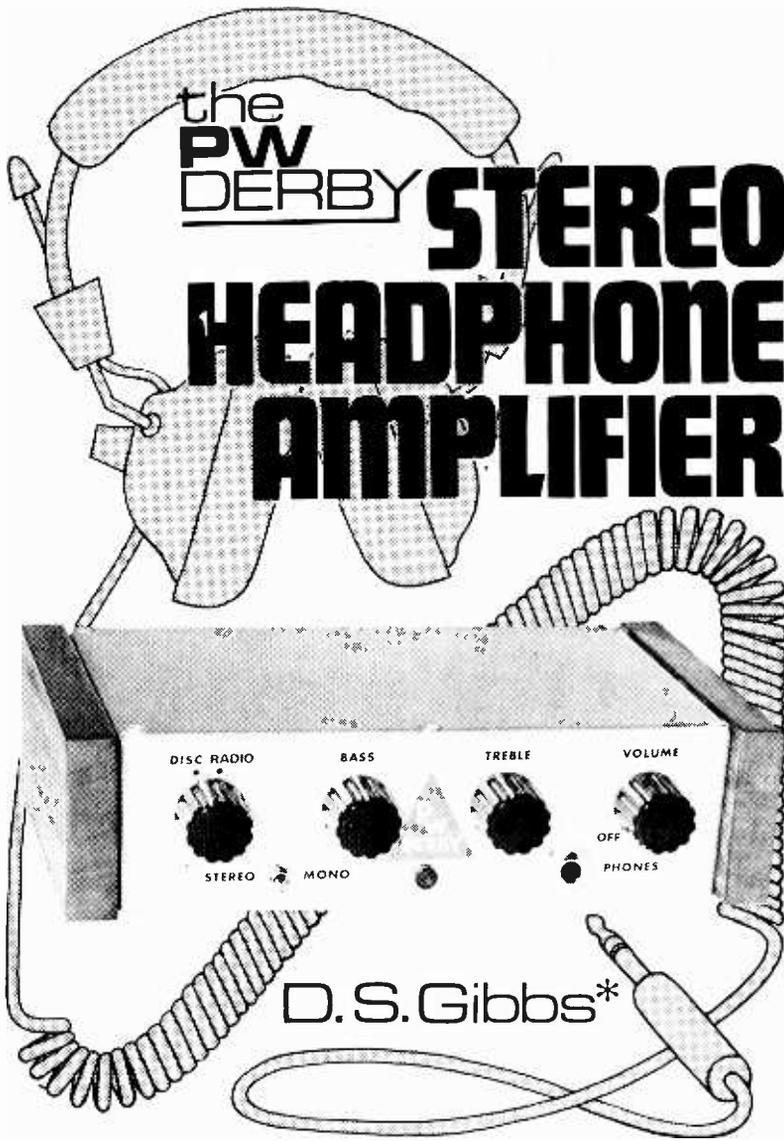


Fig. 1: common duplicate channel positive feedback amplifier

MANY hi-fi enthusiasts tend to dismiss headphones out of hand, probably through memories of the strangled reproduction of the Services surplus 'cans'. In contrast, modern stereo headphones are capable of giving a startlingly clear and well defined stereo image, with a quality of reproduction exceeding that of the best loudspeakers. By isolating the listener from his environment they give a sense of detachment, enabling one to devote one's entire attention to the music. For the same reason they are excellent for studying languages or for those whose musical tastes differ from those of their family.

Headphones are ideal for those just starting to acquire a hi-fi system as they minimize the expenditure required. Later, when it is desired to expand the system, it is only necessary to add a pair of amplifier modules, a power supply and a pair of


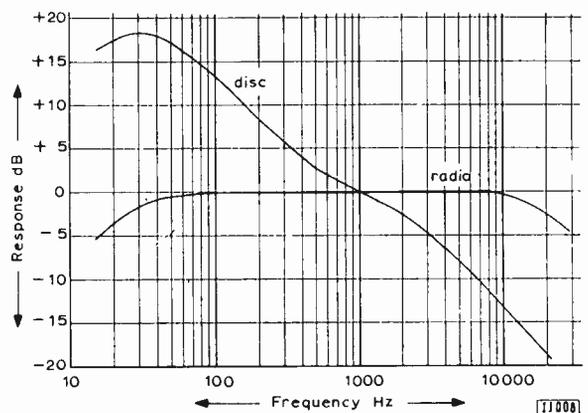


Fig. 3: Response curves of the amplifier for record or radio.

\* Ferranti Ltd.

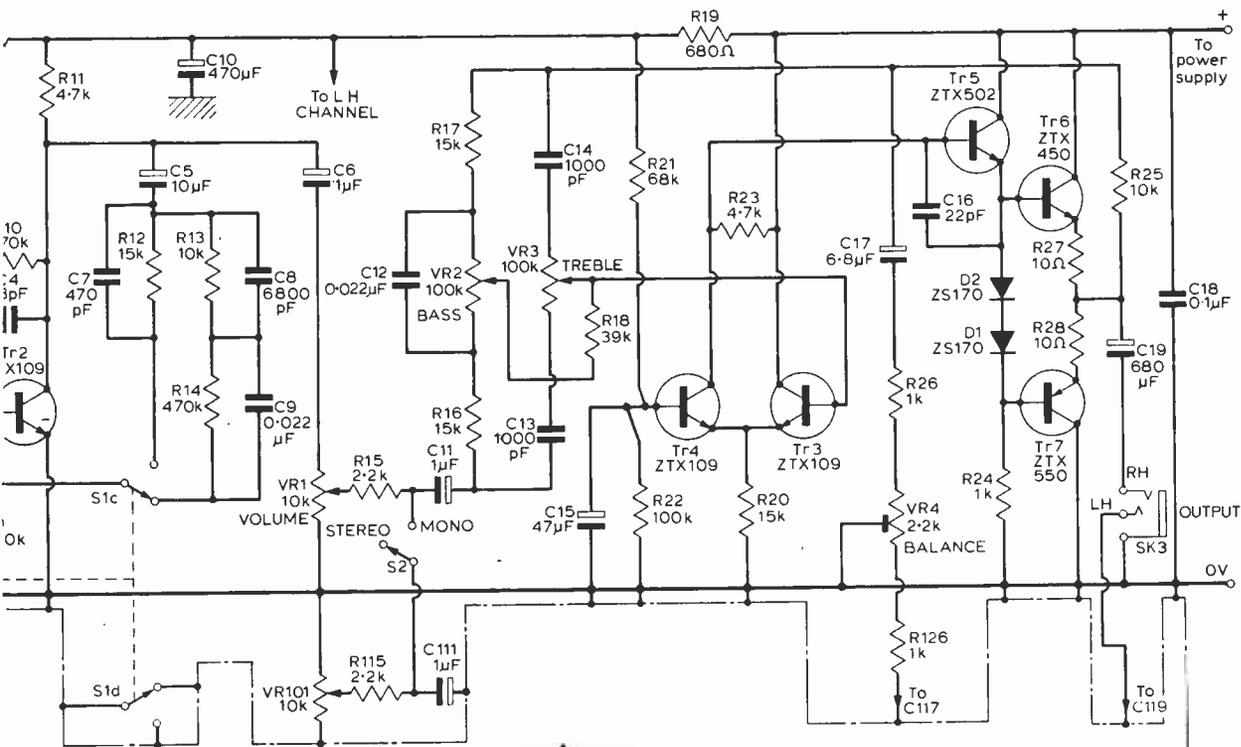

put and right channel circuits together with components. The right channel circuit is 1 within the dotted lines to the left  
**Note:**—Tr5 should be pnp with emitter to supply.

# PW SUPER SEPARATES

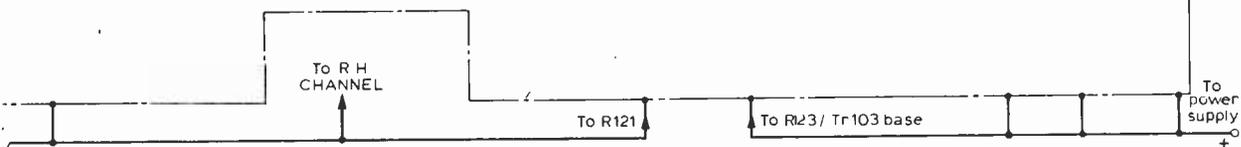


Fig. 2: Circuit of the power supply section of the 'Derby'.

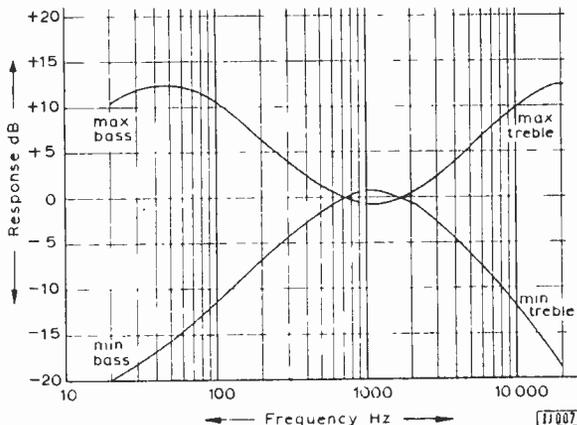


Fig. 4: The effects of the tone controls are shown in these curves.

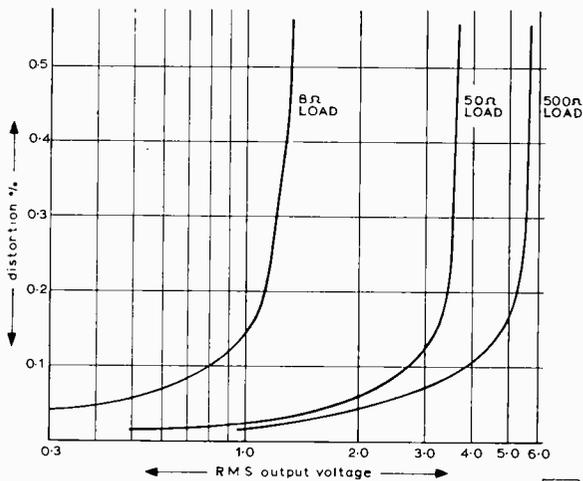


Fig. 5: Curves relating distortion with output voltage and load impedance.

loudspeakers as the headphones amplifier serve as a preamplifier. The circuit described here gives a standard of performance equal to a good hi-fi amplifier and it can be used with any make of headphones provided the impedance is greater than 8 ohms. The circuit is designed to give an output level of at least 1 volt into any impedance and this will be sufficient to generate a sound pressure level of 90dB or more with most types of stereo headphones.

## CIRCUIT

The circuit diagram of the amplifier is shown in Figs. 1 & 2. The input stage comprising Tr1 and Tr2 is conventional and provides a 5mV input with RIAA equalisation for magnetic cartridges and a 100mV input with a flat frequency response for radio etc. Other inputs can be added by the constructor if desired. The response curves of the radio and disc inputs are shown in Fig. 3.

The output stage, comprising Tr3-Tr7, follows the same general lines as a normal hi-fi power amplifier but has been designed for a very much lower power level. The tone control is of the Baxendall type and is incorporated into the feedback loop of the amplifier. The response curves of the tone control are shown in Fig. 4. The output stage thus serves as both a power amplifier and a tone control stage.

The balance control operates by varying the feedback and hence the gain of the output stage and for this reason it cannot reduce the signal level to zero. It does however provide a variation of  $\pm 9$ dB between channels. This is entirely adequate for use with headphones as the headphones themselves are usually well matched. The variation of distortion with output level is shown in Fig. 5.

## CONSTRUCTION

The prototype was constructed in a  $7\frac{1}{4} \times 4\frac{1}{2} \times 2$ in. diecast box which was decorated with a coat of silver paint and a pair of wooden ends, to give a domestically acceptable appearance. However, any suitable case can be used, provided that the same layout is adhered to. A duplicate of the prototype has been constructed in a record player plinth on a small aluminium chassis. Drilling details for the diecast

## ★ components list

### Resistors

R1	R101	100k $\Omega$	R11	R111	4.7k $\Omega$	R21	R121	68k $\Omega$
R2	R102	4.7k $\Omega$	R12	R112	15k $\Omega$	R22	R122	100k $\Omega$
R3	R103	330 $\Omega$	R13	R113	10k $\Omega$	R23	R123	4.7k $\Omega$
R4	R104	100k $\Omega$	R14	R114	470k $\Omega$	R24	R124	1k $\Omega$
R5	R105	470k $\Omega$	R15	R115	2.2k $\Omega$	R25	R125	10k $\Omega$
R6	R106	330 $\Omega$	R16	R116	15k $\Omega$	R26	R126	1k $\Omega$
R7	R107	47k $\Omega$	R17	R117	15k $\Omega$	R27	R127	10 $\Omega$
R8	R108	10k $\Omega$	R18	R118	39k $\Omega$	R28	R128	10 $\Omega$
R9	R109	220k $\Omega$	R19		680 $\Omega$	R29	R129	Fig.
R10	R110	470k $\Omega$	R20	R120	15k $\Omega$	R30	R130	10

All  $\frac{1}{2}$ W or  $\frac{1}{4}$ W 5% carbon film  
LH channel numbers have 100 prefix

VR1 VR101 10k $\Omega$  log dual gang with DPST switch.  
VR2 VR102 100k $\Omega$  linear dual gang  
VR3 VR103 100k $\Omega$  linear dual gang  
VR4 2.2k $\Omega$  skeleton preset pot

If a fully variable balance control is desired VR4 should be made a 2.2 or 2.5k $\Omega$  pot (linear law) and mounted on the front panel

### Capacitors

C1	C101	1 $\mu$ F 35V TB	C12	C112	0.022 $\mu$ F 160V P
C2	C102	4.7 $\mu$ F 35V TB	C13	C113	1000pF 125V Poly
C3	C103	47 $\mu$ F 25V Elec	C14	C114	1000pF 125V Poly
C4	C104	33pF 125V Poly	C15	C115	47 $\mu$ F 10V Elec
C5	C105	10 $\mu$ F 25V Elec	C16	C116	22pF 125V Poly
C6	C106	1 $\mu$ F 35V TB	C17	C117	6.8 $\mu$ F 40V Elec
C7	C107	470pF 125V Poly	C18	C118	0.1 $\mu$ F 250V P
C8	C108	6800pF 160V P	C19	C119	680 $\mu$ F 16V Elec
C9	C109	0.022 $\mu$ F 160V P	C20		2200 $\mu$ F 25V Elec
C10		470 $\mu$ F 25V Elec	C21		0.01 $\mu$ F 750V D
C11/111		11 $\mu$ F 35V TB			

TB—Tantalum bead Elec—Electrolytic  
Poly—Polystyrene P—Polyester D—Disc ceramic

### Semiconductors


		Recommended	Alternatives
Tr1	Tr101	ZTX109	ZTX108B/C, ZTX382, ZTX383, ZTX384
Tr2	Tr102	ZTX109	as above
Tr3	Tr103	ZTX109	as above
Tr4	Tr104	ZTX109	as above
Tr5	Tr105	ZTX502	ZTX550, BFS97, ZTX537/538, ZTX212
Tr6	Tr106	ZTX450	ZTX337/338, BFS60
Tr7	Tr107	ZTX550	ZTX537/538, BFS97
D1	D101	ZS170	ZS270 or any ZS170/270 series
D2	D102	ZS170	as above
D3		ZS170	as above
D4		ZS170	as above

### Miscellaneous

S1, 4 pole 3 way rotary switch. S2, Single pole toggle switch. LP1, Miniature neon indicator lamp. SK1/2, 5 pin DIN sockets (2). SK3, Stereo jack socket. T1, Mains transformer 12V+12V 6VA (RS Components Ref. Min. Tr. 12V). Knobs (4). Diecast box Eddystone 6827P.

Davian Electronics, PO Box 38, Oldham, Lancs, OL2 6XJ can supply PCB at £1.85, kit of semi-conductors at £3.10 or both for £4.75, all inclusive of VAT and P/P.

<b>OUTPUT</b>	1.3V into 8 ohms 4V into 50 ohms 6V into 500 ohms	} This is sufficient to generate a sound pressure level of over 90dB with most headphones
<b>DISTORTION</b>	0.14% with 8 ohm load 0.02% with 50, 500 ohm load	
<b>TO NE CONTROLS</b>	Bass $\pm 12$ dB at 50Hz Treble $\pm 12$ dB at 15kHz	
<b>DYNAMIC RANGE (Input)</b>	25dB referred to 1V output	
<b>SIGNAL/NOISE RATIO</b>	Disc 67dB unweighted 20Hz to 20kHz 80dB weighted, 30 phon curve Radio 69dB unweighted 72dB weighted	} referred to 1V output
<b>BALANCE CONTROL</b>	$\pm 9$ dB variation between channels	
<b>FREQUENCY RESPONSE</b>	Disc within 1dB of RIAA curve 20Hz to 20kHz Radio -3dB at 20Hz and 22kHz	

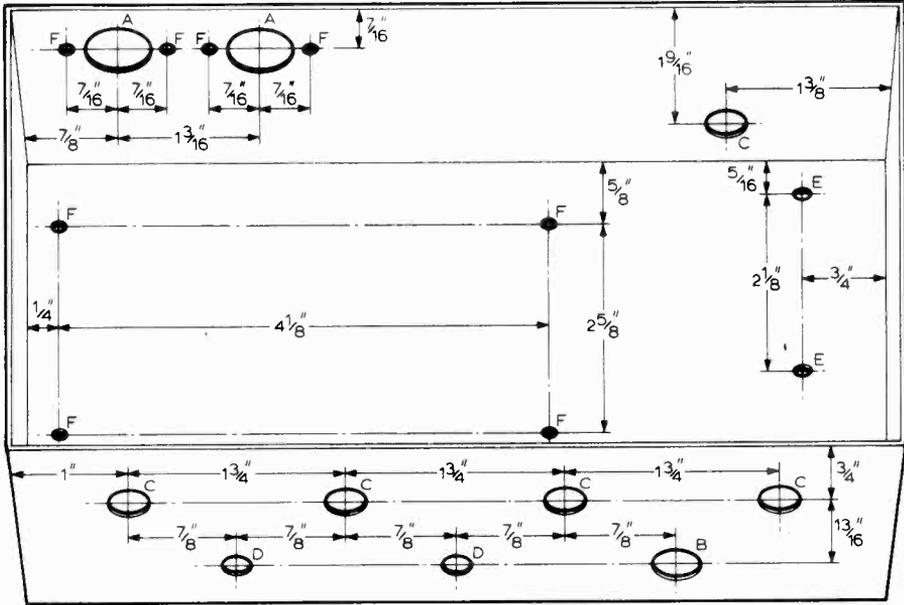


Overall dimensions of case:  
7 1/4 x 4 3/4 x 2' deep

- Hole drilling key:
- A... 5/8 dia.
  - B... 7/16 dia.
  - C... 3/8 dia.
  - D... 1/4 dia.
  - E... 4BA clearance
  - F... 6BA clearance

AM 0202

Fig 6 above, gives drilling information for the diecast box while in Fig. 7 below, the printed circuit board is shown actual size.

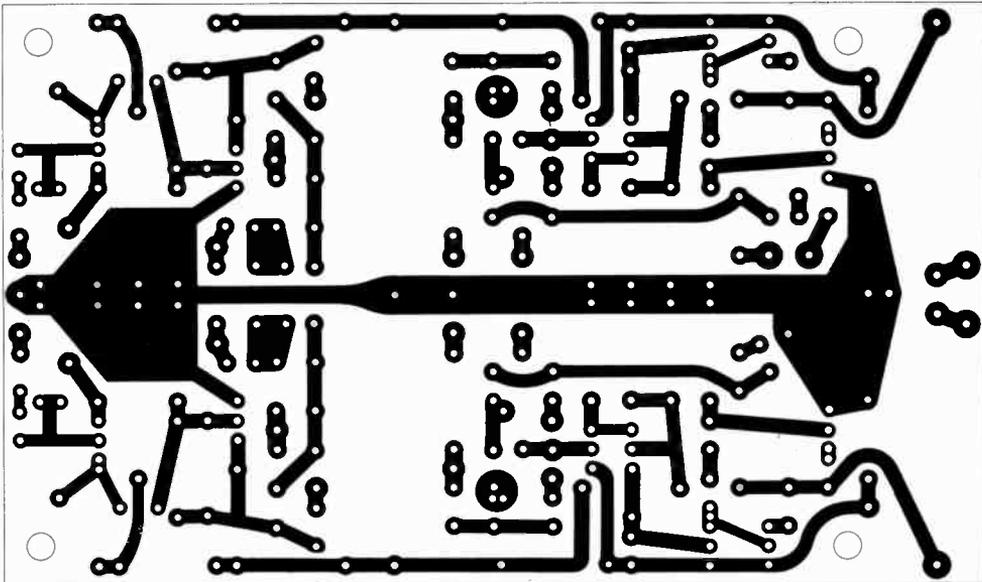

AM 0203


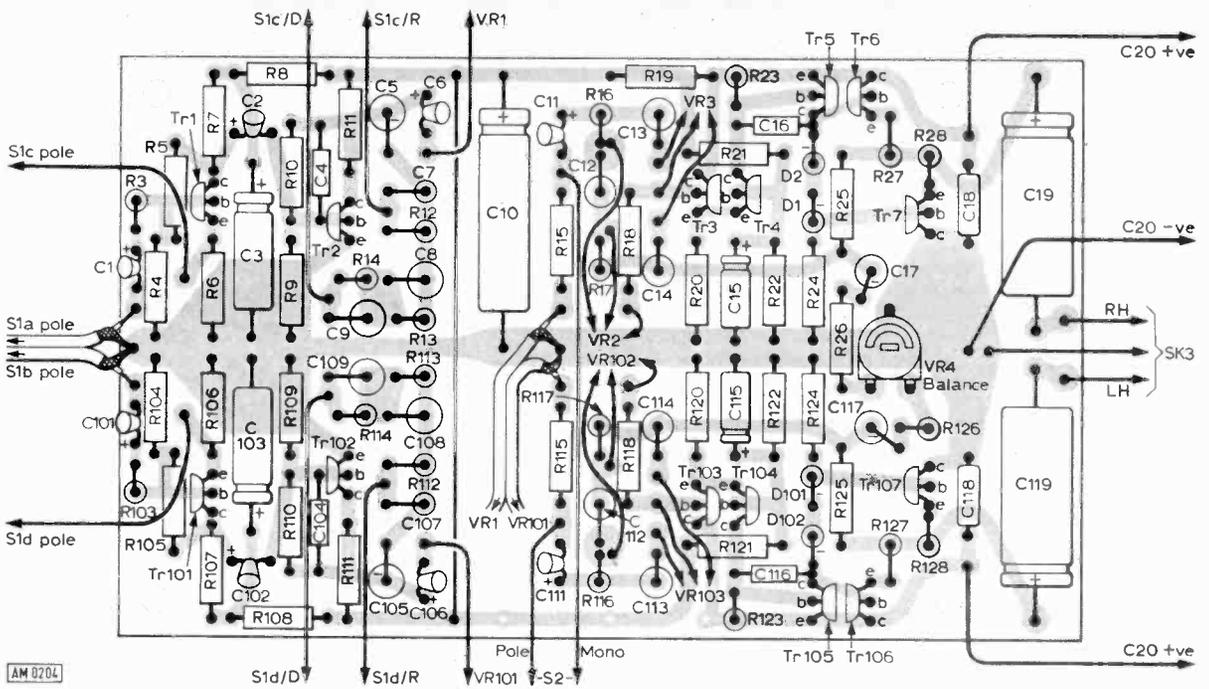


Fig. 8: Layout of components on the PCB and details of the associated wiring. The photograph shows the location of the components mounted on the box.

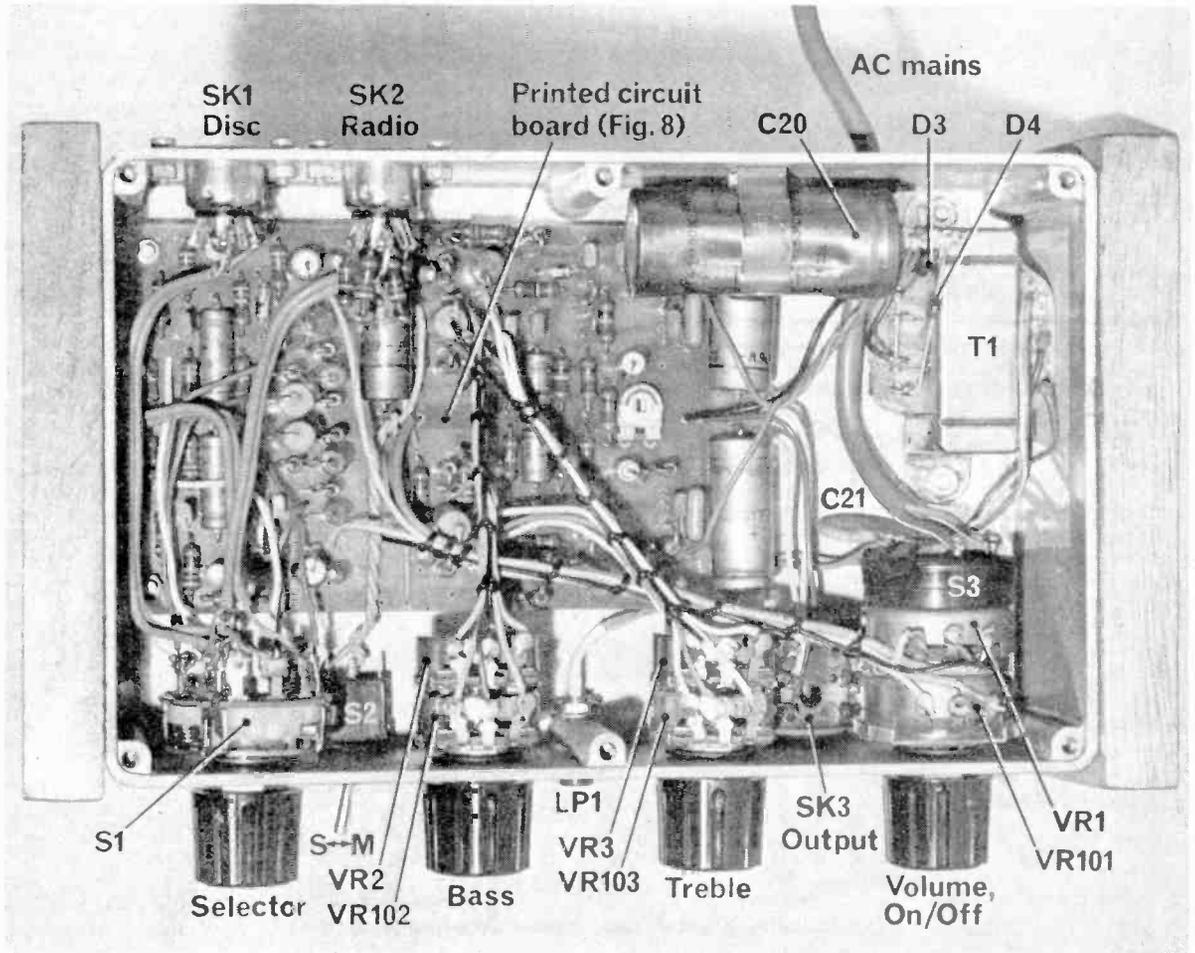

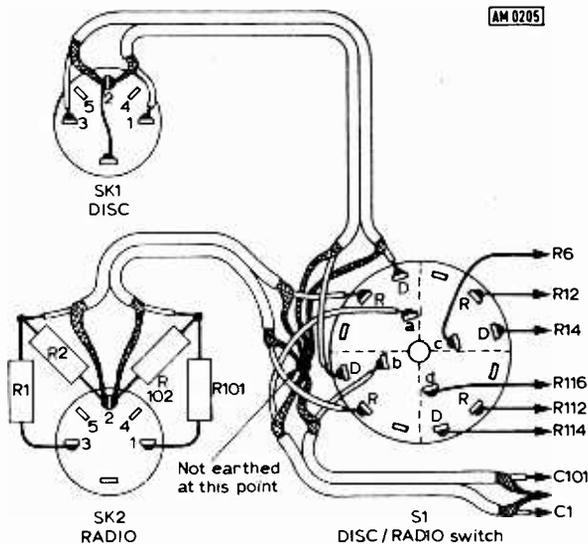


Fig. 9: Detailed information on the connections to the input sockets and various controls.

box are given in Fig. 6, and after drilling the box should be painted as desired. If wooden ends are required the ends of the box should be left unpainted.

Most of the small components are mounted on a single fibreglass printed circuit board, Fig. 7, measuring 5×3in. There is not a great deal of room to spare and miniature components should be used throughout. The first step is to assemble all the components on the board as shown in Fig. 8, and then to solder all wires for the external connections. Twin screened wire should be used at the input and between the volume control and R15/R115, but ordinary thin connecting wire is satisfactory elsewhere. All leads should be as short and direct as possible.

Mount the stereo/mono switch S2, the pilot lamp and the output jack socket SK3 on the front panel of the case and then mount the mains transformer inside. The assembled printed circuit board can now be fixed in place on ¼in. spacers and wired up to S2 and SK3. Then mount the three potentiometers and the selector switch and wire up as shown in Fig. 9. Finally mount the two DIN input sockets and C20 and complete the wiring. The two rectifier diodes D3 and D4 are wired directly between the transformer and the positive tag of C20. It may be necessary to cut short the negative tag of C20, or bend it down, to avoid shorting against the transformer. After assembly the wooden ends can be fixed in place with contact adhesive.

The specified selector switch has three 'ways', so an extra input can be added if desired. All that is necessary is to provide an extra DIN input socket and wire it as for the Radio input. If a sensitivity differing from 100mV is required R1 and R2 can be altered appropriately.

## HEADPHONES

Headphones specifications tend to be rather confusing, as they are often specified as "suitable for 4/16 ohm amplifiers" when the impedance of the phones themselves is usually much higher than 4 ohms. Most commercial hi-fi amplifiers feed the phones output through a high value series resistor,

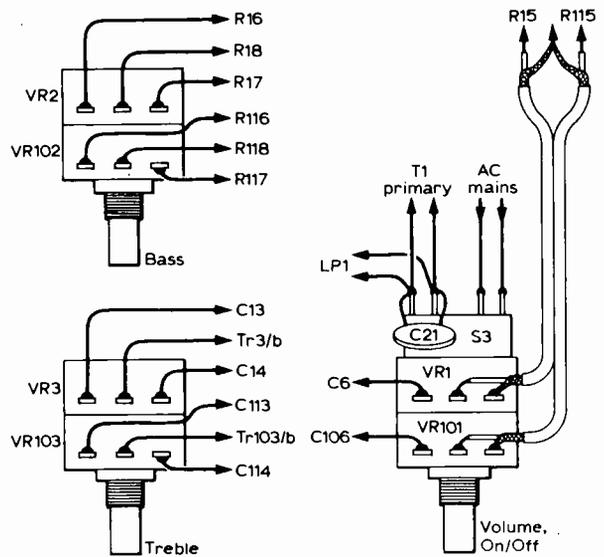



Fig. 10: Attenuator circuit for use when 'Derby' is employed to drive power amplifiers. Take values of resistors from table below.

AMPLIFIER SENSITIVITY	R29 R129	R30 R130
50mV	1kΩ	47Ω
100mV	1kΩ	100Ω
200mV	1kΩ	220Ω
500mV	1kΩ	1kΩ
1V	0	1kΩ

to reduce the signal level to an acceptable level. This unit feeds the headphones direct and has a very low output impedance, giving good electrical damping. If the reader is in any doubt about the correct impedance of his headphones the best course is to measure the DC resistance with an ohmmeter. The impedance is not likely to be less than this figure.
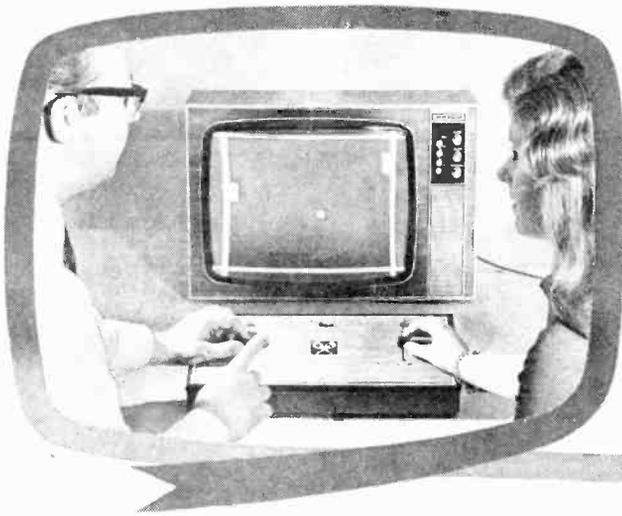
## USE AS A PREAMPLIFIER

As stated earlier, this circuit will make a very satisfactory preamplifier. The output of 1V is rather too high for most power amplifier modules, so it will be necessary to interpose an attenuator between the unit and the power amplifier. Suitable values for various amplifier sensitivities are given in Fig. 10. If the attenuator resistors are connected via a switched jack socket then the amplifiers will be automatically muted when the headphones are plugged in.



THE POPULAR NEW ELECTRONIC GAME

# TELE- TENNIS

PLAYED ON THE TELEVISION SCREEN

PART 2

M. J. HUGHES MA

## Physical Features

Apart from the modulator itself, layout of the game is not critical; nevertheless constructors are strongly advised to use printed circuit boards due to the large number of integrated circuits. Mechanical construction of the prototype was kept as simple as possible. In many respects the single plane layout adopted proved to be ideal, allowing easy access to all the preset controls. Another advantage of the planar construction is that you can build the unit in stages without having to keep it inside its case—this is useful for carrying out tests and checking each board as you go along.

Six circuit boards are used, each secured to a sub-frame made of lengths of aluminium bar or extrusion; when completed this subframe is lowered inside a case. The only extra connections then required are to the front panel controls and the output points. The case was made from bent aluminium sheet carefully glued at the corners with an epoxy resin. The sloping front panel is hinged.

The six boards are designated A to F and these are laid out on the sub frame as shown in Fig. 7. The mains transformer is bolted on to an aluminium plate shaped to screw under the longer struts of the subframe. When making the subframe ensure that you allow sufficient clearance between the aluminium struts so that there can be no chance of short circuits between them and the pcb tracks. (About  $\frac{3}{8}$ in. clearance is allowed between the longer edges of each board and the copper to prevent such short circuits.)

Apart from Board F each printed circuit has overall dimensions of  $3\frac{3}{4}$ in. x  $5\frac{1}{2}$ in. Board F has a length of 3in. but it has the mains transformer alongside it. The overall length of your subframe should take into account the dimensions of the transformer used if different to that in the prototype. By making this subframe first you can get the system partly functioning at each stage. Make sure that there is at least one inch clearance between the underside of the circuit boards and the lowest points on the subframe. This is to prevent the modulator screening box,

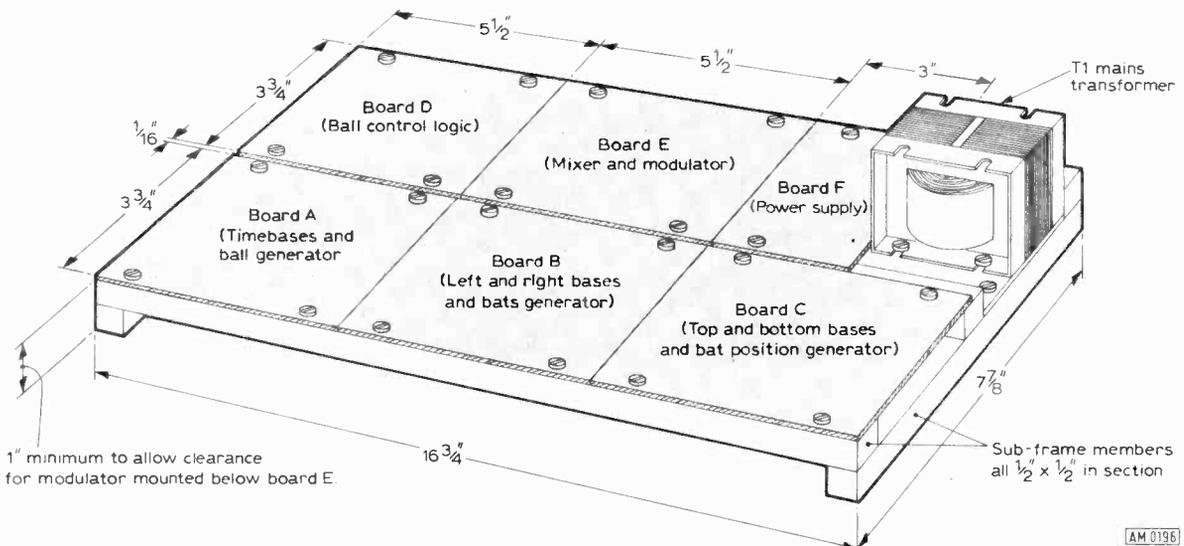


Fig. 7: Layout of printed circuit boards and mains transformer on the subframe. In the prototype this was made from aluminium bar but any material of similar size may be used.

which is live, touching the bottom of the Tele Tennis final enclosure.

This month we shall describe the operation and construction of boards E and F. If these are built first it is then possible to monitor the signals from other boards on your own television set—this obviates the need for an oscilloscope (although if you have one it would be most useful for setting up purposes!).

## Power Supplies

Three power rails are needed; a stabilised +5V for the logic circuits, +12V (nominal) for the Ball control ramp generators and +12V (nominal) for the modulator. We have separated the latter two 12V supplies with heavy decoupling to prevent hum on the RF carrier and to prevent the ball control ramps altering the supply level to the modulator. Apart from this heavy smoothing and decoupling it is not necessary to stabilise the 12V rails.

The circuit for the power supply board is shown in Fig. 8. The stable 5V rail is provided by a TO-3 encapsulated voltage regulator 7805. Other similar devices could be used but some are prone to high frequency oscillation which could present problems. A 1000 $\mu$ F capacitor on board A provides LF decoupling, while 0.1's at various points on other boards reduce the chances of noise spiking from the TTL. The smoothing capacitors for the two 12V rails are located on boards D and E respectively.

Layout is pretty straightforward but it is essential to heat-sink the voltage regulator with a piece of shaped aluminium sandwiched between the IC and the board. This heatsink can be live and there is thus no

## ★ PCB functions

Board	Function
A	Time bases, Sync mixer, Ball generator, Ball vertical change control
B	Left and Right Base generators, Bat width generators, Bat output
C	Top and Bottom Base generators, Bat height and position generators
D	Ball control ramp generators, Ball control logic, Service and Ball Boy control, Ball blanking
E	Video mixer, Video blanking, Sync/Video mixer, UHF Modulator
F	Power supply

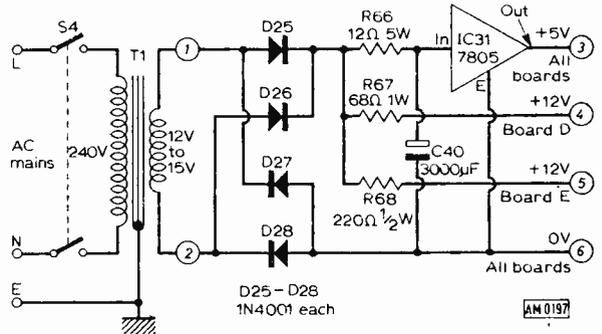


Fig. 8: Power supply circuit diagram. Smoothing capacitors for the +15V rails are mounted on Boards D and E.


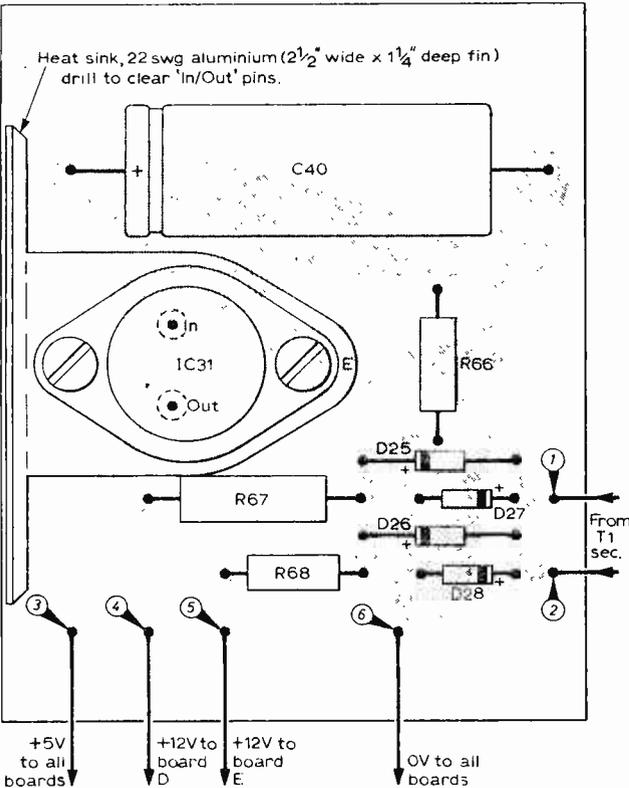


Fig. 9: Actual size layout of Board F and location of components.

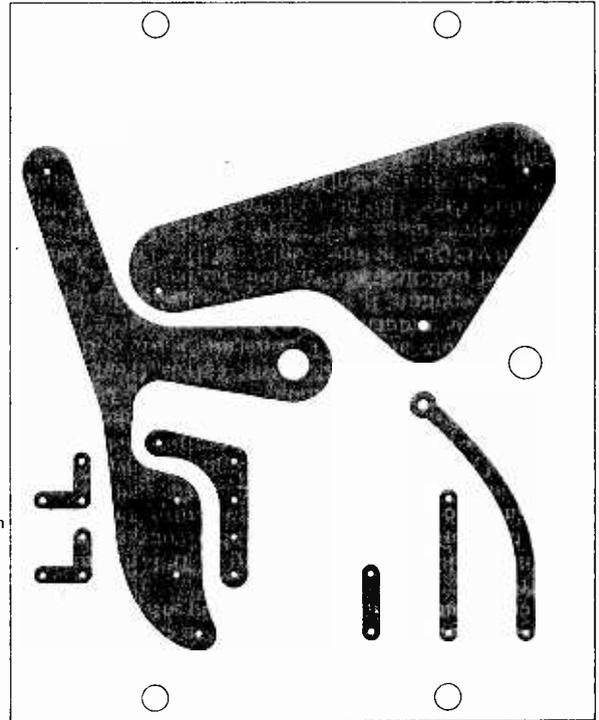

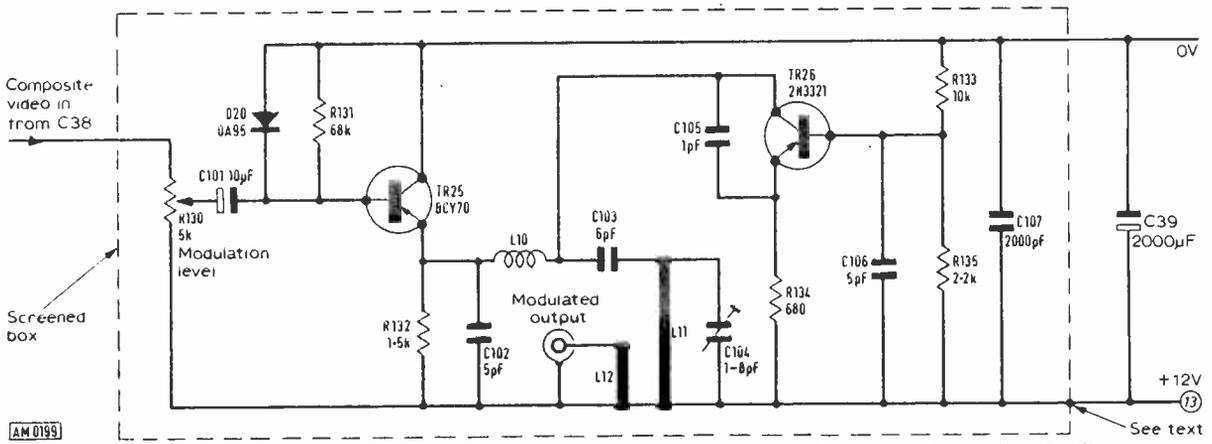


Fig. 10: Circuit diagram of the UHF modulator. Component references within the shaded area are those used by the kit suppliers and should not be confused with references in the rest of the project.

need for insulating mountings. Mount board F and the transformer on to the subframe and check that the correct voltages are present. Do not worry if the 12V rails are reading high (probably around 15V) because they are off load.

### Modulator

The next step is to assemble the modulator. The circuit is shown in Fig. 10 and we are indebted to Crofton Electronics for permission to publish it here. Provided the kit's instructions are carefully followed in every detail there are no major problems to be expected. Remember, though, to take care with the ceramic feedthrough capacitors and ensure that the strip inductors L11 and L12 are precisely cut and positioned. Mark and drill or cut holes in the uniform copper area of the Mixer/Modulator board so that the modulator will rest flush against the square copper land. Bolt the modulator case firmly into position under the board by means of the potentiometer bush, so that the control spindle and input and output connections all protrude through the plain side of the board.

Using a large soldering iron you should, eventually, run a fillet of solder between the tinned modulator case and the copper land to give extra mounting support. Before doing this, however, it is as well to test the modulator. Connect temporary leads between the +12V and 0V pins of the modulator

board and the corresponding points on board F and fit the 2000µF smoothing capacitor (C39) on board E. Set the tuning trimmer of the modulator and the modulation potentiometer to mid positions and connect the output socket of the modulator to the aerial socket of a 625 line standard television set via a short length of coaxial cable. Switch on the power and there should immediately be some indication on the television screen that something has happened—maybe the screen will brighten up or blacken off.

Check that the supply voltage is now about +12V and try adjusting the tuning of the television set. In the absence of any modulating signal there will be no picture as such, but it should be quite obvious that there is a carrier present as you tune through the range. By turning up the modulation control (turning anticlockwise) and touching the input pin with a finger you might be able to display a faint hum bar. At this stage it is sufficient to know that there is a carrier. You can now progress with the rest of board E.

### Video mixer

The circuit for the mixer stages is shown in Fig. 11. Diodes D17 and D23 in conjunction with R61 form a diode OR gate which assembles all the waveforms that define portions of the final picture. We call this stage the Video Mixer. The combined output of this stage is fed to the blanking circuit where the mixed


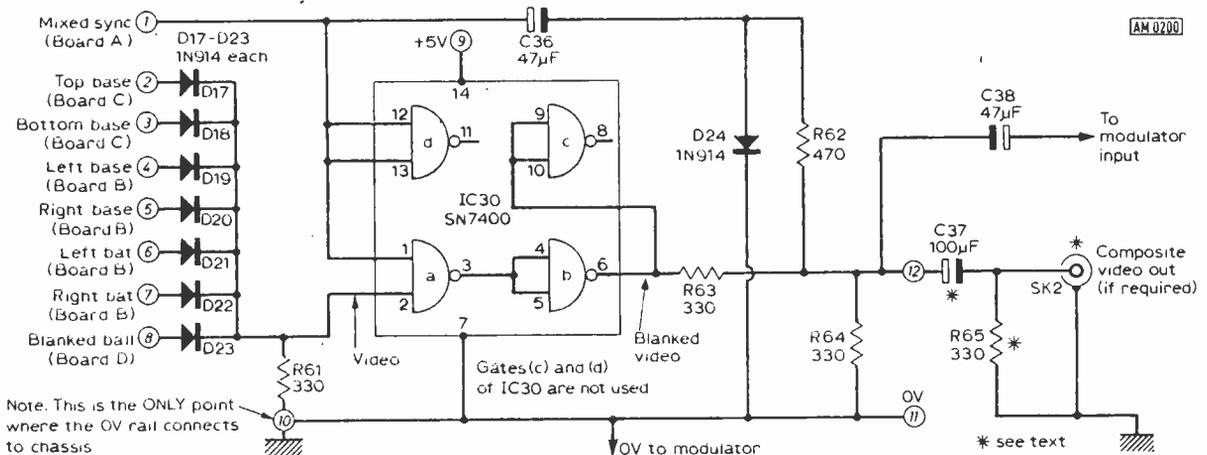


Fig. 11: Circuit diagram of Board E, including Video Mixer, Blanking and Sync/Video Mixer.

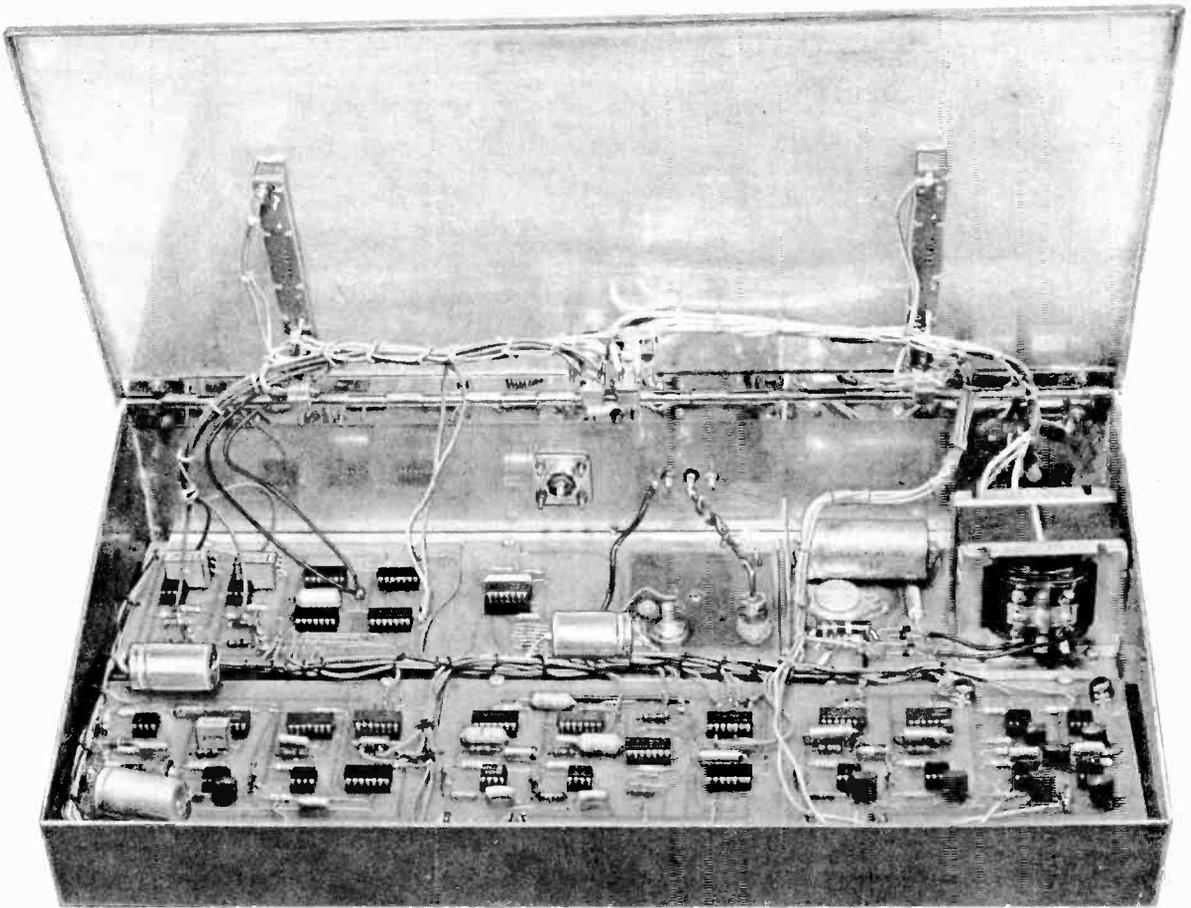

Interior view of the prototype Tele-Tennis unit. The composite video output socket is not connected up.

sync (from board A) is ANDED with it by IC30a. This has the function of ensuring that no video signal is present during periods when we shall be adding the field and line sync pulses.

The next stage is to combine synchronisation pulses with blanked video. R62, R63 and R64 form an additive mixer for the two signal sources, whilst D24 clamps the tops of the sync pulses to ground. Therefore, whenever a sync pulse occurs this is added to the video in a negative going direction. The ratios of the resistors in this stage are important to ensure the correct proportions of video and sync.

Two outputs are provided from this point. The composite video signal can be taken straight to a monitor if required, however we expect that most constructors would not possess such an instrument, and in that case C37 and R65 can be omitted. The alternative is to feed the composite signal to the modulator input via C38. Make sure that you connect this capacitor with the correct polarity because the case of the modulator is connected to the positive rail.

Throughout this project we recommend that you use dual-in-line sockets for all the integrated circuits. Apart from allowing you to replace suspect devices you will protect the guarantee given by most reputable suppliers. Do **NOT** connect any of the power lines to the subframe as chassis grounds. There is only one connection to chassis and this is made on final assembly into the case.

## ★ components list

### BOARD 'E'

#### Resistors—all $\frac{1}{4}$ or $\frac{1}{2}$ W

R61 330 $\Omega$	R62 470 $\Omega$	R63 330 $\Omega$
R64 330 $\Omega$	R65 330 $\Omega$	

#### Capacitors—all 25V electrolytics

C36 47 $\mu$ F	C37 100 $\mu$ F	C38 47 $\mu$ F
C39 2000 $\mu$ F		

#### Semiconductors

D17-D24 1N914 IC30 S87400

#### Miscellaneous

PCB; DIL14 IC socket; 14 wiring pins; Modulator kit from Crofton Electronics, 15/17 Cambridge Road, Kingston-upon-Thames, Surrey KT1 3NG, price £7.30 including p.p. and VAT.

### BOARD 'F'

#### Resistors

R66 12 $\Omega$ 5W	F67 68 $\Omega$ 1W
R68 220 $\Omega$ $\frac{1}{2}$ W	

#### Capacitor

C40 3000 $\mu$ F 25V electrolytic

#### Semiconductors

D25-D28 1N4001 IC31 7305 regulator

#### Miscellaneous

T1 Pri: 240V, Sec: 12-15V  $\frac{1}{2}$ A; PCB; 6 wiring pins; material for heat-sink, transformer mount and sub-frame.

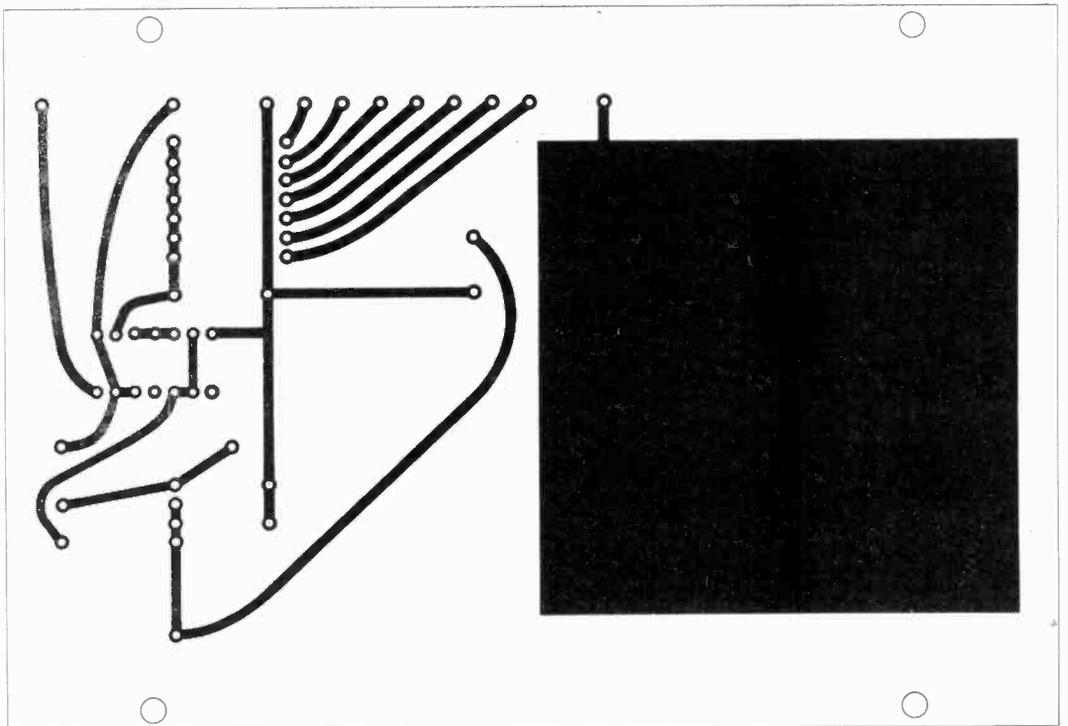
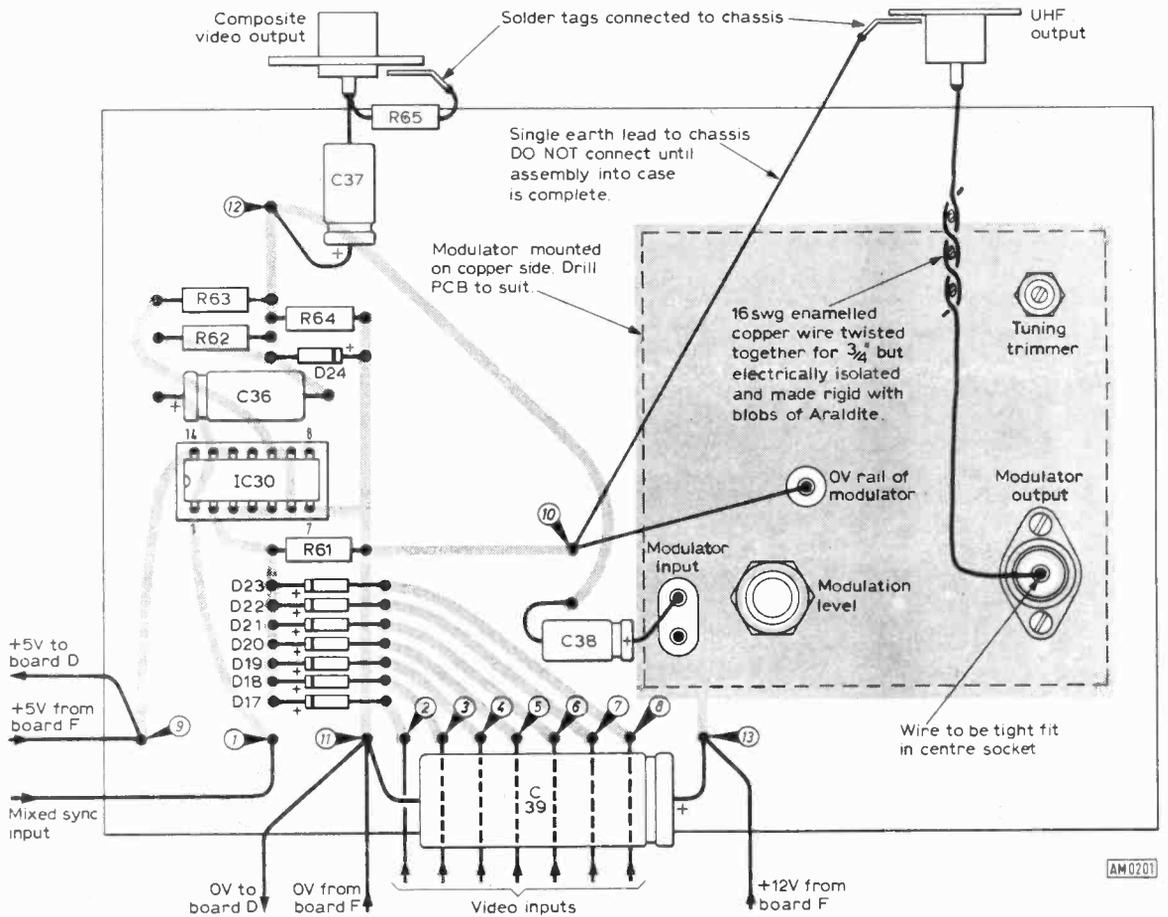



Fig. 12: Actual size layout of Board E and location of components.

—continued on page 346
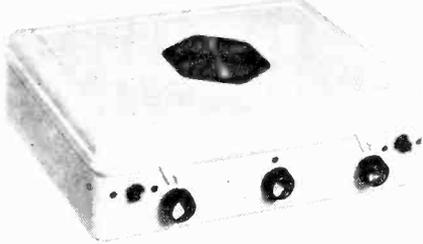
# NEW EDU-KIT MAJOR

Completely Solderless Electronic Construction Kit  
Build these projects without soldering iron or solder

- ★ 4 Transistor Earpiece Radio.
- ★ Signal Tracer.
- ★ Signal Injector.
- ★ Transistor Tester NPN-PNP.
- ★ 4 Transistor Push Pull Amplifier.
- ★ 5 Transistor Push Pull Amplifier.
- ★ 7 Transistor Loudspeaker Radio MW/LW.
- ★ 5 Transistor Short Wave Radio.
- ★ Electronic Metronome.
- ★ Electronic Noise Generator.
- ★ Batteryless Crystal Radio.
- ★ One Transistor Radio.
- ★ 2 Transistor Regenerative Radio.
- ★ 3 Transistor Regenerative Radio.
- ★ Audible Continuity Tester.
- ★ Sensitive Pre-Amplifier.




**Total Building Costs**  
**£7-23** P P & Ins. 44p  
(Overseas P & P £1-85)  
(+ 10% VAT 27p)

Components Include: 24 Resistors • 21 Capacitors • 10 Transistors • 3 1/4" Loudspeaker • Earpiece • Mica Baseboard • 3 12-way connectors • 2 Volume controls • 2 Slider Switches • 1 Tuning Condenser • 3 Knobs • Ready Wound MW/LW/SW Coils • Ferrite Rod • 6 1/2 yards of wire • 1 Yard of sleeving etc. • Parts Price List and Plans 50p. (Free with parts).

## NEW ROAMER NINE

WITH V.H.F. INCLUDING AIRCRAFT

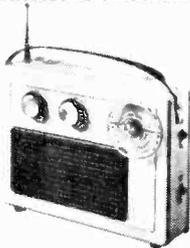

Nine Transistors, 9 Tunable wavebands as Roamer Ten. Built in ferrite rod aerial for MW/LW. Retractable chrome-plated telescopic aerial for VHF and SW. Push Pull output using 600mW transistors, 9 Transistors and 3 diodes, tuning condenser with V.H.F. section, separate coil for aircraft, moving coil loudspeaker, volume ON/OFF and wavechange controls. Attractive all white case with red grille and carrying strap. Size 9 1/2" x 7" x 2 1/2" approx. Parts Price List and Plans 30p (Free with parts).

**Total Building Costs** **£6-95** P P & Ins. 44p  
(Overseas P & P £1-85)  
(+ 10% VAT 69p)

## NEW Everyday Series

Build this exciting New series of designs



E.V.5. 5 Transistors and 2 diodes. MW/LW. Powered by 41 volt Battery. Ferrite rod aerial, tuning condenser, volume control and loudspeaker. Attractive case with red speaker grille. Size 9" x 5 1/2" x 2 1/2" approx. Parts Price List and Plans 15p. Free with parts.

**Total Building Costs** **£2-73** P P & Ins. 30p  
(+ 10% VAT 97p)  
(Overseas P & P £1-25)

E.V.6. Case and looks as above. 6 Transistors and 3 diodes. Powered by 9 volt battery. Ferrite rod aerial, 3" loudspeaker, etc., MW/LW coverage. Push Pull output. Parts Price List and Plans 15p. Free with parts.

**Total Building Costs** **£3-60** P P & Ins. 30p  
(+ 10% VAT 36p)  
(Overseas P & P £1-25)

E.V.7. Case and looks as above. 7 Transistors and 3 diodes. Six wavebands. MW/LW, Trawler Band, SW1, SW2, SW3, powered by 9 volt battery. Push Pull output. Telescopic aerial for short waves. 3" Loudspeaker. Parts Price List and Easy Build Plans 20p. Free with parts. Overseas P & P £1-03.

**Total Building Costs** **£4-08** P P & Ins. 31p  
(Overseas P & P £1-85)  
(+ 10% VAT 40p)

## ROAMER EIGHT Mk I

NOW WITH VARIABLE TONE CONTROL




7 Tunable Wavebands: MW1, MW2, LW, SW1, SW2, SW3 and Trawler Band. Built in Ferrite Rod Aerial for MW and LW. Retractable chrome plated Telescopic aerial for Short Waves. Push pull output using 600mW transistors. Car aerial and Tape record sockets. Selectivity switch. 8 transistors plus 3 diodes. Latest 4" 2 watt ferrite magnet loudspeaker. Air spaced ganged tuning condenser. Volume/on/off, tuning, wave change and tone controls. Attractive case in rich chestnut shade with gold blocking. Size 9" x 7" x 4 1/2" approx. Easy to follow instructions and diagrams. Parts price list and plans 25p (FREE with parts).

**Total building costs** **£6-98** P P & Ins. 47p  
(Overseas P & P £1-85)  
(+ 10% VAT 69p)

## ROAMER TEN

WITH VHF INCLUDING AIRCRAFT

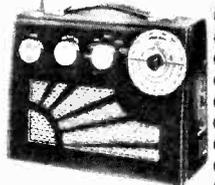

10 Transistors. Latest 4" 2 watt Ferrite Magnet Loudspeakers. 9 Tunable Wavebands, MW1, MW2, LW, SW1, SW2, SW3, Trawler Band, VHF and Local Stations also Aircraft Band. Latest 4" 2 watt ferrite magnet loudspeaker.

Built in Ferrite Rod Aerial for MW/LW. Retractable, chrome plated 7 section Telescopic Aerial, can be angled and rotated for peak short wave and VHF listening. Push Pull output using 600mW Transistors. Car Aerial and Tape Record Sockets. 10 Transistors plus 3 Diodes. Ganged Tuning Condenser with VHF section. Separate coil for Aircraft Band. Volume on/off, Wave Change and tone Controls. Attractive Case in black with silver blocking. Size 9" x 7" x 4". Easy to follow instructions and diagrams. Parts price list and plans 30p (FREE with parts).

**Total building costs** **£8-50** P P & Ins. 52p  
(Overseas P & P £1-85)  
(+ 10% VAT 85p)

## POCKET FIVE



3 Tunable wavebands. M.W., L.W. and Trawler Band. 2 stages, 5 transistors and 2 diodes, supersensitive ferrite rod aerial, moving coil loudspeaker, attractive black and gold case. Size 3 1/2" x 1 1/2" x 3 1/2" approx. Plans and Parts Price List 15p (Free with parts). (+10% VAT 22p) (Overseas P & P £1-25)

**Total Building Costs** **£2-28** P P & Ins. 26p  
(+ 10% VAT 22p)  
(Overseas P & P £1-25)



## TRANSONA FIVE


Wavebands, transistors and speaker as Pocket Five. Larger Case with Red Speaker Grille and Tuning Dial. Plans and Parts Price List 15p (Free with parts). (+10% VAT 25p) (Overseas P & P £1-25)

**Total Building Costs** **£2-50** P P & Ins. 26p  
(+ 10% VAT 25p)  
(Overseas P & P £1-25)
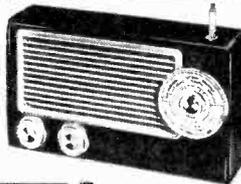
## TRANS EIGHT 8 TRANSISTORS and 3 DIODES

6 Tunable Wavebands: MW, LW, SW1, SW2, SW3 and Trawler Band. Sensitive ferrite rod aerial for M.W. and L.W. Telescopic aerial for Short Waves. 3in. Speaker. 8 improved type transistors plus 3 diodes. Attractive case in black with red grille, dial and black knobs with polished metal inserts. Size 9" x 5 1/2" x 2 1/2" approx. Push pull output. Battery economiser switch for extended battery life. Ample power to drive a larger speaker. Parts price list and plans 25p (FREE with parts).

**Total building costs** **£4-48** P P & Ins. 33p  
(+ 10% VAT 44p)  
(Overseas P & P £1-25)



## ROAMER SIX

CASE AND LOOKS AS TRANS-EIGHT

6 Tunable Wavebands: MW, LW, SW1, SW2, Trawler band plus an extra Medium waveband for easier tuning of Luxembourg, etc. Sensitive ferrite rod aerial and telescopic aerial for Short Waves. 3in. Speaker. 8 stages—6 transistors and 2 diodes. Attractive black case with red grille, dial and black knobs with polished metal inserts. Size 9" x 5 1/2" x 2 1/2" approx. Plans and parts price list 25p (FREE with parts).

**Total building costs** **£3-98** P P & Ins. 31p  
(+ 10% VAT 39p)  
(Overseas P & P £1-85)

## "EDU-KIT"



Build Radios, Amplifiers, etc. from easy stage diagrams.

Five units including master unit to construct.

Components include:  
Tuning Condenser: 2 Volume Controls: 2 Slider Switches: Fine Tone 3" Moving Coil Speaker: Ferrite Rod Aerial: Battery Clips: 4 Tag Boards: 10 Transistors: 4 Diodes: Resistors: Capacitors: Three 1" Knobs. Units once constructed are detachable from Master Unit, enabling them to be stored for future use. Ideal for Schools, Educational Authorities and all those interested in radio construction. Parts price list and plans 25p (FREE with parts).

**Total building costs** **£5-50** P P & Ins. 33p  
(Overseas P & P £1-85)  
(+ 10% VAT 55p)

## RADIO EXCHANGE LTD

★ Callers side entrance "Lavells" shop.  
★ Open 10-1, 2.30-4.30, Mon.-Fri. 9-12 Sat.

To RADIO EXCHANGE CO., 61a HIGH STREET, BEDFORD, MK40 1SA  
Tel.: 0234 52367. Reg. No. 788372.

I enclose £..... for .....

Name .....

Address .....

(Dept. PW25.)



## become a RADIO-AMATEUR!

learn how to become a radio-amateur  
in contact with the whole world. We give  
skilled preparation for the G.P.O. licence

**free!**

Brochure, without obligation to:


**BRITISH NATIONAL RADIO &  
ELECTRONICS SCHOOL** P.O. Box 156, JERSEY

NAME: \_\_\_\_\_

ADDRESS: \_\_\_\_\_

WBC1  
BLOCK CAPS please

# Out now! Free

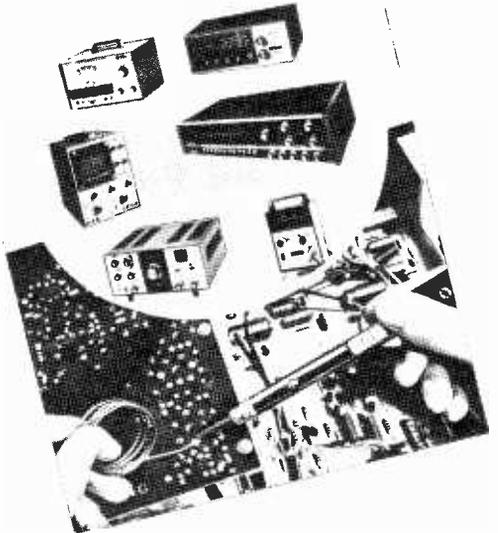

HEATHKIT offer you this colourful guide to  
electronic kits—FREE!

All our kits are designed to be built by you, whether  
beginner or professional. Even soldering experience  
is unnecessary as every kit contains a construction  
manual to lead you step by step through the assem-  
bly, testing and operation of your Heathkit.

Our extensive range includes Metal Detectors,  
Black and White TV, Intercoms, Burglar Alarm,  
Automotive, Amateur and Shortwave equipment,  
Portable Radios, Instruments and a complete range  
of Stereo Hi-Fi. All available on extended credit  
terms with our Monthly Budget Plan.

Post the coupon now for your free copy of the  
Heathkit Catalogue.

### SHOWROOMS:

London: 233 Tottenham Court Road.

Gloucester: Cole Ave. Roundabout, Bristol Road.

(Open office hours and Saturday mornings).

## Free

Please send me a FREE Heathkit Catalogue and  
details of your Monthly Budget Plans.

NAME \_\_\_\_\_

ADDRESS \_\_\_\_\_

\_\_\_\_\_

HEATH  
**Schlumberger**

HEATH (GLOS) LTD DEPT: PW/8/74  
Bristol Road,  
Gloucester GL2-6EE

**SOLARTRON** Precision Laboratory Oscilloscope type CD643. DC-15 MHz. 5" flat face-tube. £45 each. Carr. £1-50.

**12" LONG PERSISTENCE CRT.** Full spec. Price £7-50 to include V.A.T. and Carriage.

**MAKE YOUR SINGLE BEAM SCOPE INTO A DOUBLE WITH OUR NEW LOW PRICED SOLID STATE SWITCH.** 2 Hz to 8 MHz. Hook up a 9 volt battery and connect to your scope and have two traces for ONLY £5-50, P. & P. 25p. (Not cased, not calibrated.)

**NEW WIDE RANGE WOBBULATOR.** 5 MHz to 150 MHz up to 15 MHz sweep width. Only 3 controls, preset RF level, sweep width and frequency. Ideal for 10-7 or TV IF alignment, filters, receivers. Can be used with any general purpose scope. Full Instructions supplied. Connect 6 3V A.C. and use within minutes of receiving. All this for ONLY £5-75, P. & P. 25p. (Not cased, not calibrated.)

**20 Hz to 200 kHz WB. SINE and SQUARE GENERATOR.** Four ranges. Independent amplitude controls, thermistor stabilised. Ready to use, 9V supply required. £7-85 each, P. & P. 25p. (Not cased, not calibrated.)

**GRATICULES.** 12cm x 14cm high quality plastic 15p each, P. & P. 5p. £1 worth of 'UFS'. Six Brand New capacitors all between 15V and 100V. Total capacitance not less than 7,000mfd. P & P 45p.

Large quantity of good quality components — **NO PASSING TRADE** — so we offer 3lbs of **ELECTRONIC GOODIES** for £1-50. Post paid.

Open 9 a.m. to 6.30 p.m. anyday.  
PLEASE ADD 10% V.A.T.

7/9 ARTHUR ROAD, READING, BERKS.  
(rear Tech. College) Tel.: Reading 582605/65916

**ROTARY SWITCH PACK**—6 brand new switches (1 ceramic; 2 off 4pole 2 way etc.). 50p P. & P. 20p.

**COMPONENT PACK** consisting of 5 pots, various, brand new; 250 resistors  $\frac{1}{2}$  and  $\frac{1}{4}$  watt, many high stabs, etc. Fine value at 50p, P. & P. 27p.

**P.C.B. PACKS S & D.** Quantity 2 sq in—no tiny pieces. 50p plus P. & P. 20p.

**FIBRE GLASS** as above £1 plus P. & P. 20p.

**5 CRYSTALS** 70 to 90kHz. Our choice. 25p, P. & P. 15p.

**SANCO** micro ammeter 24" diameter. Ex-new radiation equip. £1-25 each P. & P. 17p.

**CAPACITOR PACK**—50 Brand new components, only 50p, P. & P. 20p. **POTS**—10 different values. Brand new. 50p, P. & P. 20p.

**TRIMMER PACK.** 2 Twin 50/200pF ceramic 2 Twin 10/60pF ceramic; 2 min. strip with 4 preset 5/20pF on each; 3 air spaced preset 30/100pF on ceramic base, ALL BRAND NEW. 25p the lot, P. & P. 10p.

**Replacement TUBES** for Cossor 1035 Mk 1, 2 & 2A & Cossor 1049 Mk 1, 2 & 3. Used—guaranteed. £3 ea. P. & P. 37p.

**LIGHT EMITTING DIODES (Red)** from Hewlett-Packard. Brand New. 30p each. Holder 1p each. Information 5p.

**PHOTOCELL** equ. OCP71, 13p each.

**MULLARD OCP70**—10p each.

**CRYSTALS.** Brand New. 4-43 MHz £1-25 ea. P. & P. 10p.

**MODERN TELEPHONES** type 708. Two-tone grey, £3-75 each. Two-tone green £3-75 each. Black £3-75 each. P & P 25p ea.

**Ideal EXTENSION TELEPHONES** with standard GPO type dial, bell and lead coding. £1-75 each P. & P. 25p.

**DELIVERED TO YOUR DOOR**  
1cwt of Electronic Scrap chassis, boards, etc. No Rubbish. FOR ONLY £3-50.

# Oscilloscope

PART 6

## techniques ALAN AINSLIE

### POWER SUPPLIES

It is not intended in this section to go into all aspects of power supply theory as it is very involved and all manner of supplies are used in oscilloscopes. However we can take a general look at power supplies and some of the problems encountered.

#### VALVE HEATERS

Valve heaters are usually wired in parallel, in groups of perhaps 5 or 6A maximum. Because of considerations of heater-cathode voltages some of the heater lines may be at certain potentials, e.g. 0V, +100V or -150V etc. Perhaps the most obvious case of this is in the case of the CRT heater which must be at -1 or -2kV. The bright up bistable is usually at EHT potential as would be the EHT series regulator if fitted. All these heaters would be run from one transformer winding and strapped to the negative EHT supply.

We shall shortly look at RF EHT generators which provide an output that is usually doubled or tripled to provide the 10 or 12kV needed on a high voltage tube. If the tripler uses valves then the heaters are usually run from a winding on the EHT transformer. A failure of the EHT generator will therefore cause these valves not to light.

In order to prevent hum and drift the input valves to the Y amplifier are sometimes fed from a stabilised HT line in series. One open circuit heater will therefore cause the whole lot to go out. One further difficulty is that heater cathode shorts can put a few valves out without affecting the others, giving rise to very misleading faults. However this practice of series valves is limited to only a few valves in very complex oscilloscopes and is not usually found in fairly simple ones.

Also supplied from a heater line is the graticule illumination, if fitted. This usually consists of a pair of small 6.3V, 0.1A bulbs in parallel, fed from a 6.3V line by a 100ohm pot. This enables the illumination to be changed to suit the display intensity.

#### HT SUPPLIES

The HT requirements of a small AC coupled scope may be quite modest and if no accurate calibration is intended the power supply can follow normal radio practice, i.e. a full wave rectifier and simple smoothing. Both metal and valve rectifiers are used but care should be taken when replacing a valve with a couple of BY127's, as is often done for economy in the event

of a failure having occurred. In general it is very bad practice as the HT comes on straight away and decoupling capacitors can short circuit through over-voltage and electrolytics can blow up making a mess when they do so and that can be dangerous so always replace a valve with a valve, or provide a thermal switch to put the HT on after 30 seconds or so.

This is the method incorporated in several large oscilloscopes where valve rectifiers would waste too much power. A small thermal switch puts 6.3V on to a relay after 30 seconds or so. The relay flips over and connects the HT windings to their rectifiers as well as providing a "holding" current for the relay and taking the supply off the terminal switch which cools down. If there is a small power break the relay loses its holding current and the HT cannot be re-connected until the thermal switch has heated up again. This protection can be extended to switch off the HT in the event of a plug-in unit being removed and another inserted, HT taking another 30 seconds to come on.

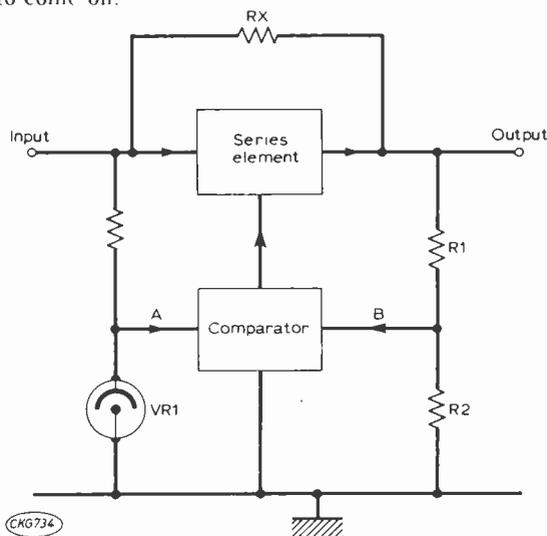


Fig. 1. Circuit requirements for a series stabilised HT line.

If some valve heaters are run from the HT line then there is also a delay while these warm up. In general this type of scope takes about 5 minutes to switch on and sort itself out, but the advantage of circuit protection is well worth the operating delay.

In most oscilloscopes some or all of the HT lines are stabilised. Because the HT load is predictable (except under fault conditions) the series stabiliser can be arranged to stabilise with little loss of power.

Fig. 1 shows the general arrangement of this type of stabiliser.  $R_x$  can be made such that the power dissipation in the stabiliser valve is kept to a reasonable level, whilst maintaining adequate stabilisation. The comparator, usually a long-tailed pair, senses the difference in potential between the points A and B and drives the series element so as to correct the difference. The ratio  $R1/R2$  sets the output voltage and  $R1$  is usually made preset so that the HT rail can be accurately set to its prescribed value.

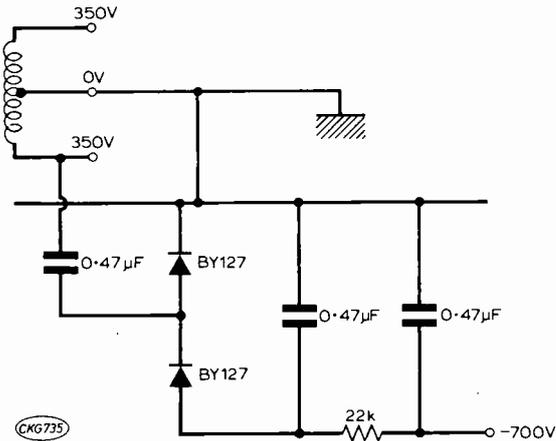


Fig. 2. Method of obtaining EHT for a small CRT using a standard mains transformer.

The circuit also has a hum reducing action in that no hum exists at point A (set by VR1) and so the comparator "makes sure" that no hum exists at point B. Hum can be injected into the comparator as well to give virtually perfect DC (ripple less than 25mV) with a ripple input of several volts. The series element is usually a power pentode or triode. If the current demand is large several valves may be placed in parallel to meet the current requirements.

If more than one HT line is required to be stabilised it is usual to make a very good job of stabilising one of the lightly loaded lines and to use this to stabilise all higher voltage lines. A typical oscilloscope would usually have HT rails at -150, +150, +400V to cover the requirements of the Y amplifier and timebase.

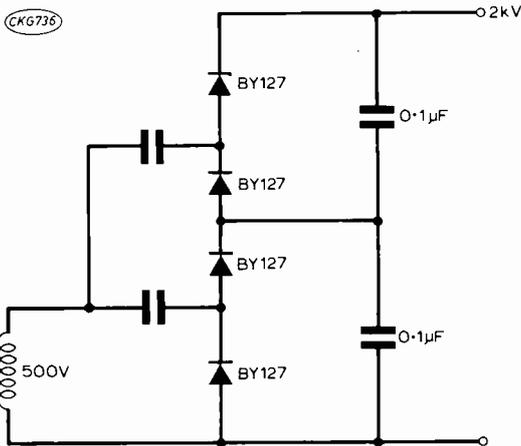


Fig. 3. Development of the voltage multiplier to produce 2kV.

EHT can be derived from one winding of the mains transformer at full voltage (say 1.5kV) and rectified and smoothed. If the oscilloscope is calibrated then the EHT must be regulated and a small series pentode is generally used for this purpose. The provision of a 1.5kV winding on a mains transformer is difficult and expensive (also lethal if you happen to get hold of it!) and so many scopes use voltage multiplication from a low voltage winding, followed by a series regulator if necessary.

Fig. 2 shows how 700V can be obtained from the 350-0-350 mains transformer of a small oscilloscope and Fig. 3 shows how the idea is extended to give 2kV from 500V. The Solartron D1400 used this principle to produce nearly 1.5kV from a 140V transformer winding.

These methods of deriving HT from a mains transformer are satisfactory up to a few kV but when 8 or 10kV is needed RF supplies are usually employed. These have the advantage that the supply can be self stabilising, can supply all the EHT supplies, operates at a high frequency and so does not need bulky smoothing capacitors and is fairly harmless in the event of accidents. Fig. 4 shows a block diagram of a typical form of this type of generator. The oscillator is self-oscillating by virtue of positive feedback from the transformer (a small winding feeding the output valve grid). The comparator provides an error signal to maintain the potential at point A as it should be, obviating any changes in the cathode supply. The PDA supply tends also to be stabilised but not so well, but in any case not so important.

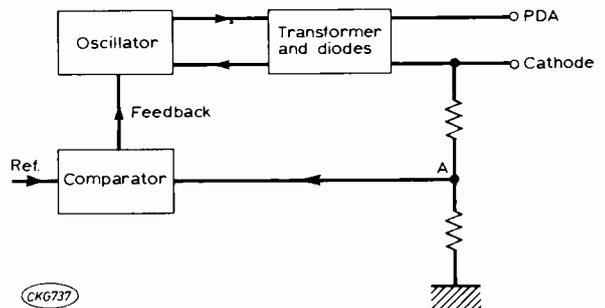


Fig. 4. Block diagram of RF generator producing 8 to 10kV.

The oscillator is tuned by a capacitor across the anode transformer winding and normally runs at 25 to 30kHz. The transformer is usually a ferrite toroid for high efficiency with the windings on polythene bobbins. As we have already mentioned, there are also windings for the voltage multiplier valve heaters if fitted. The whole EHT unit is usually isolated in a small compartment and the supply leads decoupled to prevent RF appearing everywhere. It is advisable to keep dust and damp out of this compartment and vulnerable points are usually given a coat of shellac during manufacture. Any damp might cause tracking which can cause a surprising amount of damage. In damp environments it is perhaps useful to place a small bag of silica gel in the compartment to keep the area as dry as possible.

When setting the EHT voltage with the "SET EHT PRESET" it is as well not to go over the voltage prescribed as this overruns the output valves, overruns the multiplier heaters and puts a strain on the insulation and the CRT. Any repairs in the EHT unit must

# MAPLIN ELECTRONIC SUPPLIES

## ORGAN BUILDERS

MES announce the very latest development in organ circuitry.

### THE DMO2

13 Master Frequencies on ONE tiny circuit board. LOOK AT THESE AMAZING ADVANTAGES

★ 13 frequencies from C8 to C9. ★ Each frequency digitally derived from a SINGLE h.f. master oscillator. ★ Initial tuning for the WHOLE ORGAN: ONE SIMPLE ADJUSTMENT. ★ Relative tuning NEVER DRIFTS! ★ External control allows instant tune-up to other musicians. ★ Outputs will directly drive most types of dividers including the SAJ110. ★ And each output can also be used as a direct tone source. ★ Variable DEPTH AND RATE tremulant optional extra. ★ Gold-plated plug-in edge connexion. ★ Complete fibre glass board (including tremulant if required) ONLY 3.7in. x 4.5in. ★ Very low power consumption.

★ EXTREMELY ECONOMICAL PRICE. ★ Ready built, tested and fully guaranteed.

DMO2T (with tremulant) ONLY £14.25

DMO2 (without tremulant) £12.25.

SAJ110 7-stage frequency divider in one 14 pin DIL package. Sine or square wave input allows operation from almost any type of master oscillator including the DMO2 (when 97 notes are available). Square wave outputs may be modified to saw-tooth by the addition of a few components. SAJ110: £2.63 each OR special price for pack of 12: £25.00. S.a.e. for data sheet.

Keyboards: High quality adjustable type.

Sloping front 49-note C to C	£14.35
Flat front 48-note F to E	£14.35
Contact Blocks G12 (2 make contacts)	16p
Palladium earth bar over octave length	20p
Stop Tabs rocker type not engraved (white, red, grey or black) with DPDT switch	49p

### REVERBERATION UNIT

Enhances the sound of any electronic musical instrument.

Ready built spring line driver module suitable for use with almost any spring line £5.34

Two types of spring line available:  
Short line £3.05

Long line £7.59

S.a.e. please for details, leaflet MES 24

### BASIC ORGAN CIRCUIT

Leaflet MES 51 shows complete circuit for a basic fully polyphonic organ. Send only 10p for leaflet and start building now! REMEMBER—when you have built this organ you will later be able to use the same top quality component parts as the basis of a large sophisticated instrument with all the facilities you want. Watch our ads for details.

★ SAME DAY SERVICE

## Centurion

PROFESSIONAL QUALITY INSTRUMENT CASE—4 MODELS

Model 129 all aluminium two part construction. Top and sides, blue hammer finish, front, rear and base; white. Others: mid steel three part construction.

Top, base, sides and detachable rear panel, blue hammer. Detachable aluminium front panel finished in white.

Dimensions in inches.		Model 320		
Model	W	H	D	Price
129	8	2½	6	£2.37
220	8	6	3½	£3.75
221	8	6	6	£4.07
320	12	8	12	£8.42

Chassis for model 320 £2.34 extra.

Please send s.a.e. for free illustrated leaflet.



## CAPACITORS

Sub-miniature Axial lead electrolytic

Mfd V Price	Mfd V Price	Mfd V Price
1.5 63 6p	68 6.3 6p	
1.5 63 6p	68 16 6p	
2.2 63 6p	68 63 10p	
3.3 63 6p	100 4 6p	
4.7 63 6p	100 10 6p	470 6.3 6p
6.8 40 6p	100 25 6p	470 10 10p
6.8 63 6p	100 40 6p	470 25 12p
10 25 6p	100 63 12p	470 40 15p
10 63 6p	150 6.3 6p	680 6.3 10p
15 16 6p	150 16 6p	680 16 12p
15 40 6p	150 25 6p	680 25 18p
15 63 6p	160 40 10p	680 40 22p
22 10 6p	150 63 12p	1000 4 10p
22 25 6p	220 4 12p	1000 10 12p
22 63 6p	220 10 6p	1000 16 18p
33 6.3 6p	220 16 6p	1000 25 22p
33 16 6p	220 25 10p	1500 6.3 12p
33 40 6p	220 40 12p	1500 10 18p
47 4 6p	220 63 18p	1500 16 22p
47 10 6p	330 4 6p	1000 6.3 12p
47 25 6p	330 10 6p	2200 10 22p
47 40 6p	330 16 10p	3300 6.3 22p
47 63 6p	330 63 22p	4700 4 22p



## PLUGS AND SOCKETS



### DIN PLUGS

2 pin (1 dat) 8p  
3 pin 8p  
4 pin, 5 pin A (180°), 5 pin B (240°), 6 pin 10p

### MAINS

P360 3 pin 1.5A chassis plug with line socket. Per pair 28p

### R88 8 way chassis socket

62p

### PHONO

Plug plastic 5p  
Plug screened 12p  
Chassis socket 4p

### JACK

Std. 1/4" mono plug Plastic 18p  
Screened 21p

### DIN Sockets

2 pin 6p  
3 pin, 4 pin, 5 pin A (180°), 5 pin B (240°), 7p, 6 pin 9p

### McMURDO

RP8 8 way chassis plug 47p

## POTENTIOMETERS

Rotary miniature carbon track 1/2" spindle.



Single gang Lin or Log 5k, 10k, 25k, 50k, 100k, 250k, 500k, 1M, 2M (and 1k Lin) 14p



Single gang with DP switch 250V 2A Log or Lin 5k to 2M as above 28p



Dual gang (Stereo) without switch Log or Lin 5k to 2M as above 44p.

### PRESETS

Sub-miniature 0-1W Vert or Horiz. 100, 250, 500, 1k, 2.5k, 5k, 10k, 25k, 50k, 100k, 250k, 500k, 1M

## OMNium GATHERUM

PF3, 6 etc. battery clip dual min. 9p  
PFI, 9 etc. battery clip separate per pair 6p  
Pair crocodile clips 1 red, 1 black insulated sleeve. 10p

Solder Multicore 22swg 10 metres 20p  
Silicone grease in special dispenser 20ml. 43p

Red neon 240V panel mounting 25p  
Lacing Cord Strong rayon cored PVC 25m. 51p

Panel fuse holders 20mm 20p; 1 1/2" 35p

Transformers  
LT700 min. output transformer Pri. 1.2k Ω Sec. 5 Ω 200mW 60p

Sub-min. Mains Transformer  
6.0-6V 100mA 85p  
12.0-12V 50mA 95p

Size: Both approx. 30 x 27 x 25mm.  
Min. Mains Transformer (Size: 46 x 31 x 38mm) 0-12V 250mA, 0-12V 250mA £1.38

Mains transformer MT3AT  
Pri. 200-220-240V, Sec. 12-15-20-24-30V 2A £3.31

Mains Transformer MT206AT  
Pri. 200-220-240V, Sec. 0.15-20V 1A, 0.15-20V 1A £3.96

### MES CATALOGUE 25p

Our 80 page catalogue has over 20 pages showing connexion details and data for our complete range of transistors, diodes, I.C.'s etc. + Over 100 Photographs + Over 100 line drawings. Seeing exactly what you're buying makes ordering so easy!

## VAT

Please add 10% to the final total.

## NE555V 8-pin DIL 69p

## RESISTORS

Carbon Film 1/4W 5% 1 Ω to 1M; 10%, 1/2M to 10M E12	1p
Carbon Film 1/4W 5% 1 Ω to 10 Ω; 10%, 1/2M to 10M E12	1p
Carbon Film 1/4W 5% 1 Ω to 910 Ω E12 & E24	1p
Carbon Film 1W 5% 10 Ω to 10M E12	34p
Metal Oxide 1/4W 2%, 10 Ω to 1M E12 & E24	4p
Wirewound 24W 10%, 0.22ohms to 0.47ohms E12	15p
Wirewound 24W 5% 1ohm to 270ohms E12	12p

E12 values 10, 12, 15, 18, 22, 27, 33, 39, 47, 56, 68, 82 and decades E24 values 11, 13, 16, 20, 24, 30, 36, 43, 51, 62, 75, 91 and decades

## WE KNOW YOU NEED IT!

The MES 1874 Catalogue is STACKED with dozens of tempting new lines. BRIMMING OVER with clear illustrations and detailed data. WE'RE WAITING TO RUSH YOU A COPY.

You'll be IMPRESSED with our POST FREE ordering system, EXTENDED by our BIG VALUE discount vouchers. STAGGERED by our UNBEATABLE speed of service. Take the first step towards real service NOW! Send ONLY 25p for our beautifully produced catalogue and leave the rest to us!



## LINEARS

CA3046	89p
LH0042C, T099 (T05), FET 1/4p Op Amp	£4.25p
LM301A, 8-pin DIL, Op Amp	38p
MC1303L, 14-pin DIL, Stereo Preamplifier	£1.39p
MC1310P, 14-pin DIL, FM Stereo Decoder (no coils needed)	23-15p
MFC0640, electronic attenuator	86p
MFC8010, 8-pin base, 1W Audio Power Amp	£1.37p
MFC4000B 1/2 watt Audio Amp	38p
NE555V, 8-pin DIL, Precision Timer	89p
NE561B, 16-pin DIL, Phase Locked Loop	£4.48p
SG3402N Amplifier/Multiplier	£1.89p
SG1496D, 14-pin DIL Four Quadrant Analogue Multiplier	£2.70p
UA723C, T099 (T05), 2 to 37V Voltage Regulator	75p
UA723C, 14-pin DIL, 2 to 37V Voltage Regulator	75p
UA741C, 8-pin DIL, Op Amp	38p
UA741C, 14-pin DIL, Op Amp	45p
UA747C, 14-pin DIL, Dual Op Amp	£1.05p
UA748C, 8-pin DIL, Op Amp	39p
ZN414, T05, TRF Radio	£1.20p

Full data, pin connexions, etc., on nearly all types listed in our catalogue. Price 25p

## SWITCHES

Rotary with adjustable stop 1 pole 2 to 12 way; 2 pole 2 to 6 way; 3 pole 2 to 4 way; 4 pole 2 or 3 way, each 32p.  
Mains rotary DPST 250V 2A 20p



Push to make non-locking 14p



Toggle 250V 1.5A with ON/OFF plate 25p.



Slide Sub-miniature DPDT 8p

High quality "sub-miniature" toggle switches

SPDT 1.5A 240V AC	58p
DPDT 1.5A 240V AC	75p
DPDT 3A 240V AC	77p
Four Pole DT 3A 240V AC	£1.37

## Post & packing FREE in U.K.

(15p handling charge on orders under £1).  
First class post pre-paid envelope supplied free with every order.

Orders and enquiries for catalogues to MAPLIN ELECTRONIC SUPPLIES, P.O. Box 3, Rayleigh, Essex.  
PHONE SOUTHEND (0702) 44101

# NO QUIBBLING!

IF THE PARTRIDGE WORLD RECORD V.F.A. SYSTEM DOES **NOT** SIGNIFICANTLY IMPROVE THE EFFICIENCY OF YOUR **SHORT WAVE** TRANSMITTING OR RECEIVING STATION—**WHATEVER THE LOCATION**—PARTRIDGE WILL **REFUND** THE PURCHASE PRICE (on return of resaleable goods).

COST DELIVERED (OUR RISK) OF A COMPLETE PARTRIDGE V.F.A. SYSTEM FOR: **RECEIVING** (and if required for low power transmitting—300w P.E.P. input) IS £27.16. **RECEIVING** (and transmitting—500w P.E.P. input) IS £33.22.

**HIGH SIGNAL/NOISE RATIO ON RECEPTION—HARMONIC FREE TRANSMISSION!**

TRADE INS?—Write or telephone 0843 (Thanet) 62535.

Send 5p stamp for complete details of PARTRIDGE PRODUCTS.

BOX 5

**PARTRIDGE**  
BROADCASTERS NENT ENGLAND  
**ELECTRONIC LTD**

—G3CED—G3VFA



## ALL PRICES INCLUDE VAT

**AERIAL MAST POLES.** Approx. 5ft. 2in. high, 2in. dia. Interlocking ends. Minimum order 3. As new, £1.25 (each) P. & P. 40p each.

**AERIALS.** As new. Whip Type 11ft. £1 each. Collapsible type. P. & P. 20p. New Bases for the above 75p. P. & P. 30p.

**PAIR OF 4 x 150A VALVES** complete with bases ex-equip not tested. Good condition £3. P. & P. 30p.

**BARGAIN PARCELS** 14lb at £1.60 plus 35p p.p.: 28lb at £3.00 plus 57½p p.p.: 56lb at £4.95 plus £1.37½ p.p. Contains pots, Res. Valves, Diodes, Tagboards, Chassis, Valveholders, etc. Good value save £££. Lucky Dip Service.

**FANTASTIC BARGAIN.** New 6 inch tubes. E450 4/B/16 4VH. medium Persistence, green. Ideal scope tube.

Also 7BP7. All unused as new. Price £2 post paid.

**TRANSISTOR BOARDS**—consisting of transistors, diodes and resistors etc. Long leads. Good value 12 for £1.00 (min. order) P. & P. 30p. Quotations for quantity.

**OUR SELECTION OF 6-Ex. Equ. METERS** consisting of 3in., 2½in., 2in. mill amps, volts, amps. Mixed at the bargain price of £2.20 P. & P. 30p. minimum order of six.

**NEW AERIAL WIRE ON BOARDS 7/22 UNCOVERED 90ft** £1. p. & p. 25p.

**AERIAL POLES** 4ft high 2" in diameter push-in type as new £1 each p. & p. 25p each minimum four.

C.W.O. CARRIAGE CHARGES MAINLAND ONLY

WOULD CUSTOMERS PLEASE ENSURE THAT ALL ORDERS ARE PRINTED IN BLOCK CAPITALS AND INCLUDE YOUR ADDRESS.

## A. H. THACKER & SONS LTD.

Radio Dept., High Street, Cheslyn Hay, Nr Walsall, Staffs.

### Base Mobile 1 Watt, Stabilised Multi Channel 2 Meter band Transmitter.

A complete 2 meter band transmitter with 144-146 mhz frequency transmission. Suitable for home installation or as a quality portable transmitter, completely self contained. Supplied ready to use and constructed on double sided printed board using high quality components. Unit and power supply housed in strong case with metal facia. Straight forward frontal controls. Hand held dynamic microphone with stand. Internal 12v power supply. Connection for external battery eliminator. Overall size 6 x 4 x 2in. app. Output 1 watt min. Aerial 19in, whip. G.P.O. approved. Base Mobile supplied ready to use **£39.50**

1 Watt Chassis with all connections and ready to use (complete with microphone)

Specifications as

Base Mobile

Chassis size 4in x 1in.



**£29.50**

KIT 1 Watt, with all components and full assembly instructions

**£22.00**

Specifications as Base Mobile.

For use in UK an Amateur Transmitting Licence is required.

Radio Receiver covering FM, AIR, PB, MW, and 144-146 mhz.

**£20.50**

Suitable for above transmitters.

Reg P. & P. 45p all items. Full Guarantee all items.

Mail Order all items. Mulhall Electronics Ardglass Co., Down U.K. BT30 7SF. **Tel: 039 684 461.**

be done with neat, round soldered joints to prevent corona discharge which produces ozone which destroys the insulators. It is also important to replace all screening and earth braidings. Spark gaps are often provided, especially in equipment with transistors, to break down when excess voltages occur, preventing damage to other parts of the circuit and they should be kept free of dirt otherwise they will flash over for no apparent reason.

The EHT generator is usually supplied from the highest available voltage rail in the oscilloscope and the supply line is very well decoupled. The current taken is usually only about 50 or 60mA and so represents a light load on the line.


Taking into account the overall power requirements of a complete oscilloscope the mains transformer is physically rather large (weight perhaps 10 or 15lb) and tends to produce a large magnetic field. In order to guard against this field and external magnetic fields the CRT is enclosed in a Mumetal shield which acts as a magnetic screen. The excellent screening properties of Mumetal make it possible to mount the transformer fairly near to the tube without ill effects. When removing a CRT it is important not to bend the Mumetal as it loses its properties if bent and replacement shields are expensive. The Mumetal is also earthed to prevent external electric fields penetrating the tube and causing deflection.

The internal layout of the oscilloscope is to a great extent governed by thermal considerations. For example the X and Y output stages and the power supply regulator valves are situated so that they can lose their heat easily. Small signal stages can be tucked away in any odd corners without coming to much harm. Power valves are always operated vertically for maximum reliability as the grids may sag when used horizontally. This should be borne in mind if the scope is run on its side for long periods during calibration etc.

Signal leads also play a part in dictating the layout in that signal-carrying leads are kept as short as possible to reduce capacitance and stray pick-up. When undertaking any modifications on oscilloscopes it is important to bear the above facts in mind as regards positioning of any extra stages or wiring.
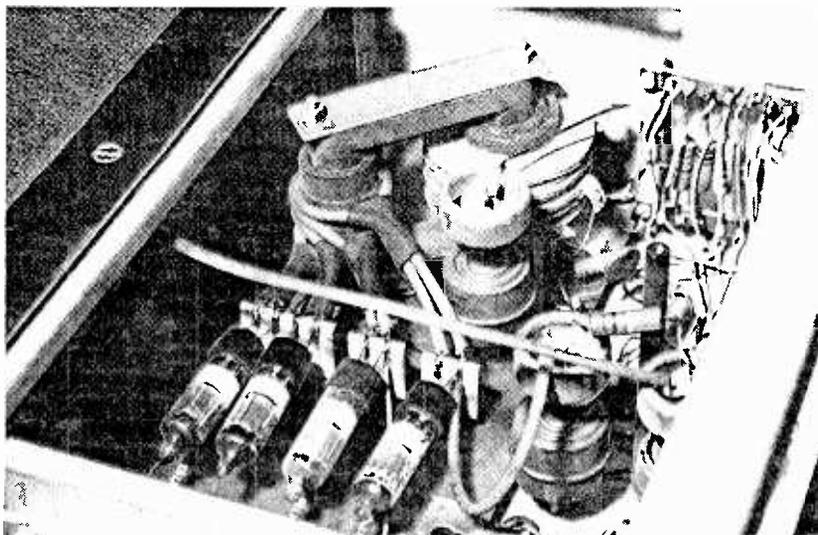
## GENERAL MAINTENANCE

Apart from recalibration, say every 6 months, or if obviously needed, an oscilloscope needs additional care and attention. The heat generated causes dirt and dust to stick and if a fan is fitted this makes matters worse. When used in a dusty environment it is as well to keep the oscilloscope covered with a plastic sheet to keep out unnecessary dust. However when the scope is in use there is little that can be done because to obstruct the dust is to obstruct the



*The EHT section of an oscilloscope, the rectifier valves heaters being fed from individual windings on the transformer.*

## COOLING

Large oscilloscopes usually have a fan at the back to keep the scope cool and the field from the fan motor is such that a piece of Mumetal is often needed around the motor. This should always be replaced when servicing of the motor is completed. The danger of an excessive rise in internal temperature is so great in some scopes that a thermal cut-out is incorporated to switch off the HT, but leave the fan running if the temperature should become too high. Clogged air filters can cause this to happen and it should not be ignored because all manner of awkward faults can be brought on by excessive temperatures.

airflow necessary to maintain a safe working temperature.

The author used to think that a scope could not be cleaned and pampered too much but is now a bit wiser! When cleaning out dust with a small brush connections become dislodged and dust gets into switches and controls. So it is best to keep the number of "spring cleans" to as few as are really necessary and to allow a bit of time for fault finding afterwards. But do not be put off—the result of a clean scope is a more reliable scope that is much easier to work on when it does break down.

For general chassis cleaning a brush round with a 1" paint brush is usually adequate unless the dirt is greasy when the chassis may be rubbed down with a

rag soaked in acetone or carbon tetrachloride. It is important not to disturb any preset pots or trimmers, especially in the distributed amplifier and attenuator and in the timebase. The EHT generator whether RF or from the mains should be kept clean as the dust builds up quickly in this area and also can do the most damage. Oil from leaking EHT capacitors also aggravates the situation but a cloth soaked in acetone will probably clear up the mess.

## CONTROLS

Controls quite naturally come in for a lot of hard wear and pots and switches tend to become erratic. A gentle squirt of "SERVISOL" aerosol will sort out most problems. It is important not to spray too much as it can make rather a mess. Beware of the cheaper brands, they dissolve plastic switch parts in a flash, leaving a gooey mess in place of the switch! When potentiometers become noisy or erratic in operation a gentle squirt of "SERVISOL" on the track will probably effect a lasting cure. Some spurious effects can be traced to the spindle bearing and a gentle squirt here may well help, but it is important not to get the fluid on to the front panel as it can make rather a mess and dissolve some types of lettering.

Input sockets (especially the UHF83) sometimes need tightening to ensure reliable contact but it is necessary to be careful not to cause too great a deformation especially with the BNC sockets which are quite fragile. Oscilloscopes equipped with plug-in units often need a little lubrication on their runners and it is advisable to keep the rear connector clean otherwise erratic operation will result. One point often overlooked is that power valves (regulator, X and Y outputs and EHT generator) when they are greasy suffer a much higher running temperature due to lack of cooling. It is a good idea to keep all valves clean and polished and to give the base a tiny squirt of "SERVISOL" before replacing the valve. Several oscilloscopes place the EHT generator valves in screening cans (to prevent radiation) and if these fill up with dust, as often happens, the valve tends to run scorching hot with the possibility of early failure.

## SERVICING

With regard to the electronics there is little that can be done in the way of maintenance on a regular basis, it being necessary to wait for faults to occur before they can be rectified. Fortunately the majority of oscilloscopes are constructed to be as reliable as possible for the price and consequently the fault rate is low. Most faults can be found with a multimeter and a signal source applied to the scope. When found the faults usually turn out to be due to faulty valves, faulty rectifiers, open circuit or "high" resistors or short circuited capacitors. When making replacements it is important to keep to a high standard of workmanship and to use good quality components of adequate rating.

## COMPONENT REPLACEMENT

A word is perhaps of use here concerning the AC qualities of resistors. The reactances of resistors becomes important at high frequencies in critical cir-

cuits, such as the Y amplifier and timebase. The standard carbon rod type of resistor, usually 10% tolerance at best, is perhaps one of the best types with regard to its AC performance. Its inductance is zero and the capacitance is usually less than 1pF. Metal film resistors are also as good in this respect and are available in a wide range of ratings and with tolerances as close as 0.5% if necessary. Other types of carbon resistor although of high reliability may have quite significant inductance and also fairly high self-capacitance. Wirewound resistors are absolutely useless in such applications and should only be used where they are well decoupled and their reactance of no consequence.

In general it is best to replace any components by identical types, which can be ordered from the scope manufacturer if necessary. Replacement component tolerances should be better or the same as the item they replace. Servicing of oscilloscopes, particularly by their owner, rarely creates any problems as the circuits are well defined in their operation and the layout in the majority of cases is intended to aid servicing.

To be continued

---

## TELE-TENNIS

—continued from page 338

The reason for making an issue over grounding is that the Crofton modulator has inverted supply rails, i.e. its case is at +12V, whereas we shall ultimately be making our system ground OV. **Do not under any circumstances** let the case of the modulator come into contact with other metal work or you will put a dead short across the power supply. It is best to cover all exposed metal work of the modulator's case with a couple of layers of PVC tape.

When Board E is complete it can be screwed to the subframe alongside the power supply board and the supply leads wired in. Apply power and check that a carrier is present by watching the television screen. If you have a signal generator (you can make a simple one from a standard multivibrator circuit) giving outputs of up to 5V you can inject a 15.625kHz signal into the mixed sync input. Turn up the brightness of the television set and you should—if the set is in tune—see a dark band running down the left hand side of the screen. Adjust the tuning for maximum signal—it is easier to adjust the set rather than the modulator—and then see the effect of varying the modulation level. Alternatively injecting a 50Hz square wave into the same point should produce a dark horizontal band running across the screen. The signal generator will need fine adjustment to obtain precise field or line lock. A square wave having a frequency between 50Hz and a few hundred kilohertz connected to the inputs of diodes D17 to D23 should cause a random array of white dots to appear on the face of the television set. Further tests must wait until we have produced a correctly generated set of field and line sync pulses. This we shall do next month when we describe the circuitry and construction of boards A and B.

**no extras**  
all prices inc VAT  
FREE delivery

BARCLAYCARD

Buy it with Access



High Quality  
Construction  
Kits, stocked at  
all branches  
Send for  
catalogue!

**AMPLIFIERS**

**Keletron**  
KSA1000 10+10 watt £25 95  
KSA1500 15+15 watt  
Mk. II £29 95  
**Tripleton**  
Hi-Fi Mk. II 7+7 watt £36 50  
Hi-Fi 1818 Mk. II  
18+18 watt £40 00  
Rotel RA211 £39 45  
Teleton 5AQ307 8+8 watt £27 00  
**Sansui**  
AU101 15+15 watt £43 95  
AU505 25+25 watt £71 00  
AU555A £99 95  
Sinclair 3000 £34 95  
Sinclair 4000 £45 95

**TUNERS & TUNER  
AMPLIFIERS**

Sinclair 3000/4000 Tuner £34 95  
Rotel RX150A Tuner/  
Amp. £59 95  
**Sansui**  
210 AM/FM/MPX £80 50  
310 AM/FM/MPX £95 75  
350A AM/FM/MPX £106 95

**RECORD DECKS**

Garrard SP25 MkIV £12 95  
Garrard 2025TC/9TAHC £9 00  
BSR MP60 £11 00  
BSR Invicta P & C/5C7M £9 95  
Garrard  
SP25 MkIV P & C/G/800 £19 95  
AP76 Module £30 00  
Goldring GL78 P & C/  
G800E £59 95  
**Connoisseur**  
BD1 Kit £12 25  
BD2 Chassis/SAU2 £29 95  
SAU2 £13 00  
SCU1 £4 95  
Plinth & Cover for Garrard  
SP25 MkIV Mk. III  
2025TC £3 50

**TAPE DECKS**

**Akai**  
4000DS £93 95  
1721L £87 95  
GXC36D £82 00  
GXC38D £103 95  
CS33D £79 95  
Akai CR81D 8-track Rec.  
player £73 95

**SPEAKERS**

**Wharfedale**  
Denton 2 (pair) £33 00  
Linton 2 (pair) £42 95  
Linton 2 Kits (pair) £19 95  
Glendale 3 Kit (pair) £36 95  
Dovedale 3 Kit (pair) £59 95

**Chassis Speakers**

EMI (Plain) 13in x 8in,  
3, 8 or 15 ohm Bass unit £2 30  
with Single Tweeter £2 45  
with Twin Tweeter £3 95  
Type 350 Kit 15 watt 8 ohm £8 25  
13in x 8in Bass unit  
15 watt 8 ohm £4 95  
8in x 5in 5 watt 3, R or  
15 ohm £1 50  
8in x 5in 10 watt  
Dualcone 8 ohm £2 50  
6 1/2" 10 watt 8 ohm £2 65  
8in 10 watt 8 ohm £3 90

12in 20 watt 8 ohm £5 95  
Fane 8in 4 ohm £2 25  
Fane 7in x 4in 3 or 8 ohm £1 20  
Celestion 8in 15 ohm £1 75  
Elac 8in 8 ohm Dualcone £2 50  
Elac 10in 8 ohm Dualcone £3 75  
Goodman 6 1/2in 8 ohm  
Dualcone £2 40  
Baker Group 25 12in 8 or  
15 ohm £7 75  
Adastra 'Top 20' 12in  
25 watt 8 or 15 ohm £8 25  
Adastra 'Hi-Ten' 10in  
10 watt 8 or 15 ohm £3 60  
Also 5in 8 ohm speaker  
2 1/2in 8 or 64 ohm  
speaker £0 50

**SPEAKER CABINETS IN  
KIT FORM (Teak Veneer)**

12in x 8in x 6in  
(8 x 5 or 7 x 4 cutout) £2 50  
14in x 12in x 9in  
(8 x 5, 8", 6 1/2" & 3 1/2") £3 75  
18in x 11in x 9in  
(8" x 1 1/2" or 13 x 8) £4 50  
22in x 14in x 9in  
(12" x 1 1/2" or 13 x 8) £6 25

**TWEETERS & CROSSOVERS**

EMI 3 1/2" c/magnet in 3 or  
8 ohm £1 10  
Cone Tweeter 10 watt  
8 or 15 ohm (K2006) £2 50  
Cone Tweeter 3 watt  
8 ohm (K2003) £1 55  
Horn Tweeter 8 ohm  
(K2007) £6 50  
Dome Tweeter 8 ohm  
(K2011) £5 50  
2-way Crossovers (CN23,  
CN28, CN216) £1 20  
3-way Crossover (CN38) £2 75

**CARTRIDGES**

**Acos**  
GP1/25C or 35C £1 10  
GP93/I £1 35  
GP94/I £1 75  
GP96/I £1 75  
GP101 £0 90  
GP104 £1 75  
**BSR**  
5C6M £2 75  
5X6M £1 80  
5X6H £1 80  
X5M £1 50  
X5H £1 50  
**Sonotone**  
9TAHC (Diamond) £1 80  
9TAHC/G (Diamond) £1 80  
Double Diamond Styli  
for above £1 25  
Goldring  
G850 Cartridge £2 95  
G800 £3 95  
G800E £7 25  
Audio Technica AT55 £1 95  
Empire 999 REX £3 95

**STYLII for:**

G850/G800/G800H £1 95  
CC90/7 £1 00  
G800E £3 60  
CS91/E £2 25  
AT66 £3 60  
N44-5 £2 25  
N44-7 £2 50

N55-E £3 95  
N75-E2 £3 95  
N75-EJ2 £3 95  
M3D £2 25  
N75/6 £1 95

**MICROPHONES**

UDI130 50K/600 ohm  
uni-dir. ball metal £5 65  
UDI47 £9 25  
Condenser Mic. 600 ohm  
uni-dir. £9 50  
Cassette Stick Mic. with  
R/Control £1 60  
Mic-Mixers Mono/stereo £5 50  
AKAI ADM14 £5 95

**HEADPHONES**

RH430 £4 75  
RH 630 £7 75  
RH 700 £11 50  
Akai ASE 11 £7 00  
Akai ASE20 £8 95  
Koss  
K711 £10 95  
KR0711 £10 95  
K6 £11 50  
K6LC £14 00  
KO727B £16 00  
KO747 £20 75  
HVI £21 95  
PRO4AA £26 95  
PRO54 £29 95  
K6LCQ £26 00  
Sansui SS10 £14 20  
Headphone adaptor  
(Junction box) £2 50  
extension lead 2ft curly £1 35

**CASSETTES**

C40 C60 C90 C120  
Low Noise — 35p 45p 55p  
Philips — 50p 69p 105p  
Memorex 55p 65p 85p 120p  
Amplex (360) 45p 55p 70p 99p  
Amplex  
(20-204) 59p 65p 99p 135p  
Amplex  
Chromium — 99p 140p —  
Dioxide — 99p 140p —  
Cassette Head Cleaner 45p  
Amplex Head Cleaner  
Demagnetiser £1 65  
Cassette Racks (hold 6) £0 45  
Cassette Rotating Racks  
(hold 20) £3 50  
Cassette Carrying Case  
(BIB) (hold 12) £1 60  
**8-Track Cartridge Blanks**  
C40 C64 C80  
Amplex 80p 95p £1 10  
8-track H/Cleaner  
Demagnetiser £1 90  
8-track Carrying Cases  
(BIB) £1 65

**TAPES**

	Std.	L/P	D/P
5"	55p	69p	90p
5 1/2"	69p	88p	1 25p
7"	88p	1 20p	1 60p
High frequency			
5"	—	1 40p	1 55p
7"	—	1 90p	2 95p

**CALCULATORS**

Sinclair Cambridge Build £19 95  
Sinclair Cambridge Kit £17 95  
Scientific £45 95

**SINCLAIR PROJECT 80**

Stereo Pre-amp. £11 95  
Active Filter Unit £6 95  
Z40 15 watt Amp £5 45  
Z60 25 watt Amp £6 95  
P25 Power Supply for 240 £4 98  
P26 Power Supply for 240 £7 98  
P28 Power Supply for 240 £7 98  
FM Tuner £11 95  
Stereo Decoder £7 45

**PORTABLE RADIOS**

Vega Jade £5 75  
Vega Zircon £7 50  
Vega Sapphire £6 45  
Vega VEF206 £12 75  
Micado LM/MW/FM/5SW  
Murphy £18 95  
BB33 MW/VHF £9 95  
BA838 LW/MW/VHF  
M/Batt £18 50  
MA5003 Head Set  
Radio LW £7 95  
**Bush**  
VTR165 LW/MW/VHF £22 00  
VTR127 LW/MW/VHF £15 50  
VTR178 VHF/MW/25W/  
AIR M/Batt £13 95  
VTR 175 LW/MW/VHF £25 00  
VTR188 LW/MW/VHF/  
25W M/Batt £31 95  
BY5661 LW/MW/VHF £14 95

**CLOCK RADIOS**

Bush CR128 LW/MW £13 60  
Bush CR232 MW/VHF £24 95  
Murphy MV5600  
MW/VHF £22 95

**CASSETTE RECORDERS**

Murphy BA206 £16 95  
Bush TP66 M/Batt £25 75  
Murphy BA200 M/Batt £22 75  
Bush BT8504 (miniature) £25 50  
Wien 500 M/Batt £14 95

**RADIO CASSETTES**

(Mains/Batt.)  
Micado 8155 AM/FM £25 95  
Sharp RD4225 MW/35W £46 50  
Hanimex HRC3070  
AM/FM £29 95  
Murphy BA209 MW/VHF £33 50

**STEREO RECORD PLAYER  
& SYSTEM**

Bush SPR58 £29 50  
Bush SPR59 £31 50  
Bush A1005 £56 50  
Hanimex H101 £39 95  
Hanimex HRC5060 8-track  
AM/FM/MPX + Speaker £116 95

**CAR AUDIO**

Bush Car Cassette BT8501 £36 75  
Hitachi Car Radio  
WM702R LW/MW £16 50  
KM1510 LW/MW/VHF £32 50  
Hitachi Car Cassette  
CS114 £45 00  
with Radio CSW17  
LW/MW £57 00

ALL ITEMS SUBJECT TO  
MANUFACTURERS INCREASE  
AND AVAILABILITY

**PERSONAL CALLERS  
WELCOME**

ALL MERCHANDISE FULLY GUARANTEED

**NEWMART  
ELECTRONICS**

Mail Order Dept PW/8  
Belmont St, Monton,  
Eccles, Manchester.  
Tel: 061-789 5268

Manchester  
30-32 Shudehill. tel 061-832 7710  
Leeds  
4 New Market St tel 0532 42708  
Liverpool  
15 Whitechapel tel 051-236 0738

# SPECIAL PRODUCT REPORT

# CORTINA- MAJOR MULTIMETER

If you are a conscientious constructor, you would not be able to get very far without getting frustrated by the need for a multi-range meter. It is almost as essential as a speedometer to a motorist. Without one, how can you locate fault conditions, or check component values.

Practical Wireless recently published an article on this subject, illustrating examples of well known types. When looking around to buy a multimeter what should you look for? Well this will depend to some extent on the usage expected of it. There are meters renowned for robustness and the ability to withstand fairly rough handling. There are those that have a high sensitivity, or an extended voltage range, or built-in capacitance meter. Good ones are not cheap to buy, but this does not mean that cheap ones are not worth having.

There has been a recent introduction of some Italian instruments into the U.K. which are certainly worth looking

## MANUFACTURER'S SPECIFICATION

Sensitivity	A.C. & D.C., 40k $\Omega$ /V
Accuracy	D.C. $\pm 2.5\%$ Ohms $\pm 2\%$
Bandwidth	20Hz to 10kHz
Dimensions	156 x 100 x 40mm
Weight	650 grammes
Power requirements	Internal, 2 x 1.5V HP7 or similar) 1 x 22.5 (B 122 or similar) for resistance. External, 220-240V 50Hz for capacitance and frequency only.

## RANGES

Volts		Current	
D.C.	A.C.	D.C.	A.C.
0-420mV	0-3V	0-30 $\mu$ A	0-3-0mA
0-1.2V	0-12V	0-300 $\mu$ A	0-30mA
0-3.0V	0-30V	0-3mA	0-0.3A
0-12V	0-120V	0-30mA	0-3-0A
0-30V	0-300V	0-0.3A	
0-120V	0-1,200V	0-3-0A	
0-300V			
0-1,200V			

## Resistance $\Omega$

0-2k $\Omega$	-10 to +11
0-20k $\Omega$	+ 2 to +23
0-200k $\Omega$	+10 to +31
0-2M $\Omega$	+22 to +43
0-20M $\Omega$	+30 to +51
0-200M $\Omega$	+42 to +63

## Power dB

-10 to +11
+ 2 to +23
+10 to +31
+22 to +43
+30 to +51
+42 to +63

## Frequency Hz

0-50Hz
0-500Hz
0-5kHz

## Capacitance $\mu$ F


0-0.05 $\mu$ F
0-0.5 $\mu$ F

## Ballistic Capacitance

Extends ranges up to one Farad.

## Universal Signal Injector

Frequencies	500kHz modulated at 1kHz
Harmonic content	Usable up to 500MHz
Output	20V peak-to-peak
Isolation	Probe will withstand 500V d.c. at circuit under test
Power requirements	25mA from internal battery

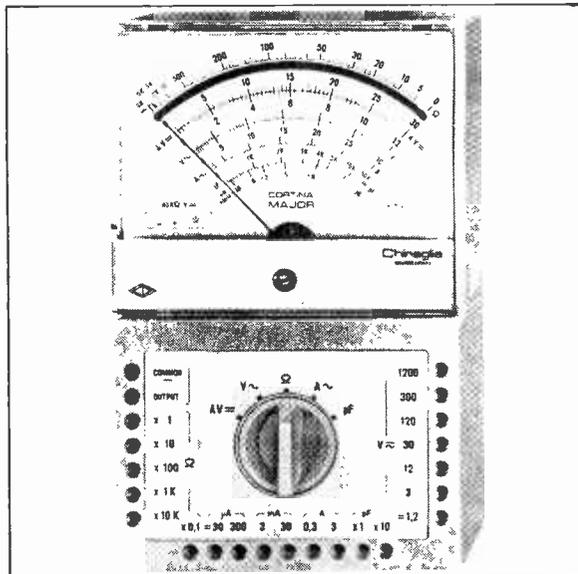

into for several reasons. These are made by Chinaglia Dino and are being distributed in this country by Chinaglia (UK) Ltd\*. There are several types, each having its own performance/cost parameters; we have selected as being a very useful all-rounder, the "Cortina Major" which costs £22.27 or, if you want the Universal Signal injector with it, will cost £27, plus VAT in each case. There are lower priced meters in the range that are also worth looking into, but with more modest performance.

## PERFORMANCE

The quoted performance figures are tabulated here and straight away, readers will notice the sensitivity of 40k $\Omega$ /volt. This is adequate for transistor and i.c. circuitry and brings the meter into possible applications even with high impedance work without serious shunting errors in the readings indicated. When used as a voltmeter across any a.c. or d.c. load, the internal resistance of the instrument will often have some effect on the reading accuracy. The higher the sensitivity in terms of kilohms per volt, the less will be that error.


The Major will handle a.c. and d.c. voltage and current measurements. The a.c. current facility is particularly interesting; although not required very often, it can be a nuisance if you are using a meter that does not have this facility, as is the case with some earlier models from other makers. The main problem with this range is that its accuracy really depends upon the frequency of the current being measured because of the reactance effects of the meter coil. For inductive loads, it can be a little misleading unless the frequency is taken into account. In the absence of any other figures of measurement than the claimed accuracy of  $\pm 2.5$  per cent for a.c. ranges, we assume this to apply within the quoted bandwidth.

## RANGES


The d.c. current ranges are very useful for transistor circuits, being based on a common scale of 0 to 30 with

—continued on page 350

# GOING BACK...

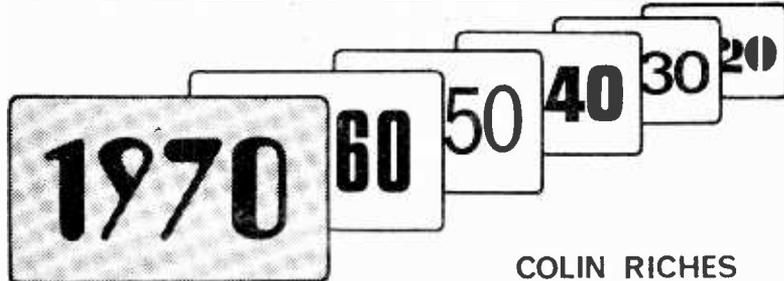

COLIN RICHES

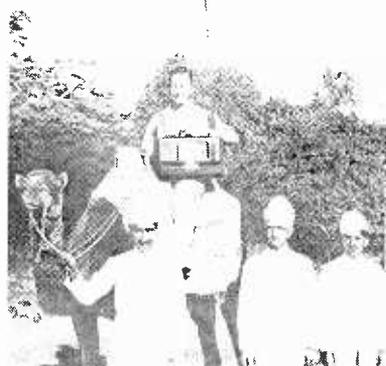

An early "mobile" Trans-Oceanic

**T**HIRTY-FIVE years ago this year the Zenith Trans-Oceanic was born.

Over the years new knowledge and improved technology have gone into successive improved versions. The latest—the Trans-Oceanic Royal D-7000Y — is equipped to tune to 11 wave bands. (1) a.m., 540-166MHz, (2) f.m., 88-108MHz, (3) l.w., 150-400kHz, (4) s.w., 1.6-3.5MHz, (5) 3.5-90MHz, (6) 9.4-10.1MHz, (7) 11.4-12.33MHz, (8) 14.6-15.8MHz, (9) 17.1-18.5MHz, (10) 20.6-22.4MHz and (11) 161-164MHz.

It is designed and treated to operate in extreme climatic conditions, and incorporates r.f. gain control, b.f.o., vernier tuning and battery level meter, illuminated dial and chart panel, telescopic aerial and personal earphone. Navigational benefits include a time zone indicator, logging scale and azimuth compass. A swivel base platform can be supplied to aid directional tuning. It operates on 9 standard U2 type batteries but also has a built-in a.c. power

supply for either 115V or 230V a.c.

The Trans Oceanic theory was developed into practice in 1939, when Commander E. F. McDonald (Zenith's late founder-president), having asked the company's engineering department to produce a shortwave battery operated radio, found that he could sit in his Canadian fishing lodge and pick up both the weather forecast from Ohio and broadcasts from London.

After a combination broadcast and shortwave receiver with broad bandspread for easier tuning had been produced, McDonald took one to Northern Canada and sent another to Commander Donald B. McMillan in the Arctic. McMillan tested it on Baffin Island, and then further north on Ellesmere and Greenland. Finding it fully satisfactory, he radioed McDonald to express his approval.

When some further 20 experimental models had been tested and subsequent modifications

adapted, the set went into production several months before the Zenith factory was converted for the war effort in 1941. At that stage 100,000 Trans-Oceanic radios were on the order books, and though many of these were never completed, several thousand had been by the time the US entered the war. Members of the allied forces were frequently comforted throughout the duration of the war by broadcasts from their native countries, the radio set often being their only link with home.

About his Trans-Oceanic radio, a British army officer wrote,



First multiband receiver made in 1941

"During the whole war, it was either with me or close behind with my luggage. Besides being under enemy fire, it has stood in the open in blistering heat and sandstorms, likewise in monsoon rain and snow. I have watched it dropped into cargo holds by coolies and have sympathised with it after suffering a kick by a donkey. In spite of such treatment, there has been no occasion during its ten years life that the set has failed to work."

Since introduction in 1941, a number of major improvements have taken place. Announced to yachtsmen in 1951, as a "king-size

—continued on page 350



Experimental S.W. transmission with singing Eskimos (1925). Zenith's founder-president Commander McDonald is standing on the right.

## SPECIAL PRODUCT REPORT—continued from page 348

appropriate range multiplication factors. The  $30\mu\text{A}$  range enables low leakage currents to be detected, whilst the 3 amp range is useful for average thyristor d.c. load measurement.

The voltage ranges are divided into two scales—0 to 12 and 0 to 30 with appropriate multipliers. The advantage of using two scales is to maintain average meter indications between a half and full scale deflection, usually recommended for most measurements on load, without having to interpolate at the low end of the scale. The 1,200V ranges will cope with most applications except e.h.t. for cathode ray tubes; the optional extra probe will extend this range to 30kV d.c., sufficient for most oscilloscope or television c.r.t.s., for an additional £7.27 plus VAT.

The resistance ranges are from 0 to  $2\text{k}\Omega$  (useful readings) on a  $20\text{k}\Omega$  scale, up to 0 to  $20\text{M}\Omega$  (useful readings) on a  $200\text{M}\Omega$  scale. This will cater for a very wide range of measurements from 1 ohm to  $20\text{M}\Omega$  d.c. but does not, as is usual, mean that "cold insulation" tests on capacitors or wiring will necessarily give reliable results.

Two 1.5V batteries have to be fitted to give the low resistance ranges and one 22.5V battery for the high resistance ranges.

Decibel measurements are based on the standard  $0\text{dB} = 1\text{mW}$  in 600 ohms, or 0.775V a.c., using the a.c. voltage circuit for measurements ranging from  $-10$  to  $+63\text{dB}$ .

Using an interpolation scale in the instructions an indication of frequency is possible based on the use of the capacitance circuit and, in the case of the X100 range, it depends on an external accurate 4,700pF capacitor being applied. Both the frequency and capacitance ranges require this instrument to be connected to an accurate 50Hz mains supply of 220 to 240V for which a lead is provided. The meter uses a resistance measurement circuit to determine reactance, and hence interprets the result as a direct capacitance reading up to a maximum  $0.5\mu\text{F}$ . For most purposes the  $10,000\mu\text{F}$  "ballistic capacitance" range is likely to be the maximum required, and this is achieved by interpolation of the d.c. AV scale using the chart given in the instructions.

The optional extra U.S.I. (Universal Signal Injector) is virtually a square wave signal generator using two transistors and mounted inside a "pen" type tube with a 1.5V battery. It provides a 1kHz "pulse" waveform from a blocking oscillator suitable for signal tracing and fault finding procedures in a wide range of radio, audio and TV equipment. The probe is claimed to withstand, on test, 500V d.c. and provide 20V peak-to-peak output.

In the event of repairs being needed, the manufacturers have appointed Coates-Clarke (Services) Ltd., of 110a St. Margarets Road, Hanwell, London W.7. to carry out this service.

\*Chinaglia (UK) Ltd., 19 Mulberry Walk, London SW3 6DZ


## GOING BACK

—continued from page 349

aspirin for the headaches of amateur sailors" and "the world's newest aid to navigation," the new Trans-Oceanic had had added to it two new continuous tuning bands that covered the entire 38 to 150 metre band, (2 to 8MHz).

In 1954 another new version of the Trans-Oceanic was introduced and included a ferrite rod aerial which, in conjunction with new circuits, was said to "treble the range" for standard broadcast reception. Other additions included a horizontal slide-rule type tuning dial. Push-button band selection and a reel-away take-up on the power control. Inside the set's cover were located a series of flip charts, a world-wide time map and listings for all major short-wave stations.

McDonald's next challenge to his company engineers was to develop a transistorised Trans-Oceanic portable radio that would "equal or better the performance" of the valved version. Compactness was his stipulation to the engineers. Whether for yachts or expeditions, it was paramount that weight and bulk size was kept to a minimum but without the sacrifice of performance. There was not to be room for a teaspoon of sugar, or the engineers "would get it back." After three years of research and development Zenith announced "the world's first all-transistor band-spread short wave portable radio" in 1957.

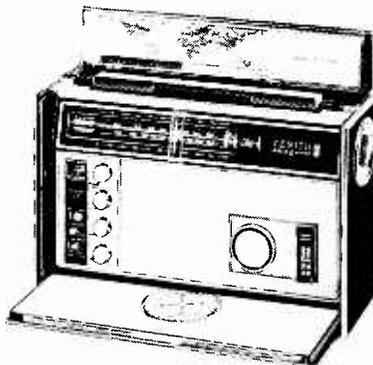

The 1974 version of the Trans-Oceanic. Recommended retail price is £247.50 inc. VAT.

Components and circuitry were built into a case measuring  $10\frac{1}{4} \times 12\frac{1}{2} \times 4\frac{7}{8}$ in representing a major achievement in miniaturisation and space efficiency. It included a new rotary band switch and associated circuits for electrical band-spread tuning which occupied a fraction of the space required in valved short wave sets. The band selector switch rotated a "rolling pin" dial scale so that only one tuning band was visible at a time.

"The ultimate in personal radios" was announced in 1962—this was a 9-band Trans-Oceanic, the Royal 3000. This transistorised receiver combined superlative performance and virtually

"drift-free" tuning of the f.m. broadcast band with new sensitivity on short wave, long wave and standard broadcast bands. It was similar to the previous model but less the 13 metre band and plus the f.m. broadcast band (88 to 108MHz).

August 1964 saw the one millionth Trans-Oceanic portable radio roll off the Zenith production line.

In 1968 the Trans-Oceanic was again altered quite significantly with the addition of the wave bands. The Royal 7000, as the new model was called, featured 11 bands and incorporated a v.h.f. fixed crystal U.S. "weather" band at 162.55MHz. The set was tuned to the weather position to hear up-to-the-minute weather reports. The second band addition was short wave (a division of the earlier 2.9MHz spread), making a total of seven short wave bands, long wave, f.m. a.m. and weather band. Other improvements in the Royal 7000 included a b.f.o. and manual r.f. gain controls.

In 1971, the Royal 7000 was further refined with replaceable crystals for the weather band, enabling the listener to receive weather stations assigned to frequencies other than the common 162.55MHz (U.S.), in 1972 the Royal D-7000Y was improved again with the addition of the adjustable weather band and minor cabinet changes. The 1974 version is shown in our picture.

# BI-PRE-PAK

SUPPLIERS OF SEMI-CONDUCTORS TO THE WORLD



## Telephone Corner

COMPLETE TELEPHONES

Normal Household Type

EX. G.P.O. Only **£1-05p** P & P 45p each

### TELEPHONE DIALS

Standard Post Office type. Guaranteed in working order.

Only **27 1/2p** POST & PACKING 16 1/2p

## Ex GPO Push Button Intercom Telephones

Exactly as internal telephone systems still in everyday use where automatic internal exchanges have not yet taken over. Available in 5, 10 or 15 ways. Complete with circuits and instructions. Necessary 24 pair cable 22p per yard. Price of each instrument is independent of the number of ways.

**£2.75 p.p. 38 1/2p** Per Instrument

Cable can be sent by Parcel Post. Post and Packing per 50 yds. 73 1/2p.

Extension Telephones. 71p each. p.p 27 1/2p.

£1 37 1/2 for 2. P.&P. 55p.

These phones are extensions and do not contain bells.

## Electronic Transistor Ignition £6.60

Complete kit incl. V.A.T. p. & p. 11p. Ready built & tested unit £9.90 inc. V.A.T. Now in kit form, we offer this "up-to-the-minute" electronic ignition system. Simple to make. Full instructions supplied with these outstanding features. Transistor and conventional switchability, burglar proof lock-up and automatic alarm, negative and positive compatibility.

## New X Hatch

Our new vastly improved Mark Two Cross Hatch Generator is now available

Essential for alignment of colour guns on all colour T.V. receivers. Featuring plug in IC's and a more sensitive sync. pick-up circuit. The case is virtually unbreakable—ideal for the engineer's tool box—and only measures 3" x 5 1/4" x 3". We have already received a large order from a major T.V. Rental company.

Ready built unit only **£10-92** Complete kit **£8-72**

(Includes V.A.T. and p. & p. but no batteries)

## Over 1,000,000 Transistors in stock

We hold a very large range of fully marked, tested and guaranteed transistors, power transistors, diodes and rectifiers at very competitive prices. Please send for free catalogue.

### Our very popular 4p transistors

TYPE "A" PNP Silicon alloy, TO-5 can  
TYPE "B" PNP Silicon, plastic encapsulation  
TYPE "E" PNP Germanium AF or RF  
TYPE "F" NPN Silicon plastic encapsulation  
TYPE "G" NPN Silicon similar ZTX 300 range  
TYPE "H" PNP silicon similar ZTX 500 range

**8 RELAYS FOR VARIOUS TYPES P & P 27 1/2p £1-10p**

## High Speed Magnetic Counter



4 digit (non-reset) 24V or 48V  
4 x 1 x 1 in. 33p. P.&P. 5p.

## Plastic Power Transistors



NOW IN TWO RANGES

These are 40W and 90W Silicon Plastic Power Transistors of the very latest design, available in NPN or PNP at the most shatteringly low prices of all time. We have been selling these successfully in quantity to all parts of the world and we are proud to offer them under our Tested and Guaranteed terms.

Range 1. VCE. Min 15. HFE Min 15.

40 Watt	1-12	13-25	26-50
90 Watt	22p	20p	18p
	26 1/2p	24 1/2p	22p

Range 2. VCE. Min. 40. HFE Min 40

40 Watt	1-12	13-25	26-50
90 Watt	33p	31p	29p
	38 1/2p	36 1/2p	33p

Complementary pairs matched for gain at 3 amps. 11p extra per pair. Please state NPN or PNP on order.

LM380 Audio I.C. as featured in *Practical Wireless* Dec. issue, complete with application data £1-10p.

### INTEGRATED CIRCUITS

We stock a large range of I.C.s at very competitive prices (from 11p each). These are all listed in our FREE Catalogue, see coupon below.

### METRICATION CHARTS now available

This fantastically detailed conversion calculator carries thousands of classified references between metric and British (and U.S.A.) measurements of length, area, volume, liquid measure, weights etc.

Pocket Size 15p Wall Chart 18p

**LOW COST DUEL IN LINE I.C. SOCKETS**  
14 pin type at 16 1/2p each } Now new low profile  
16 pin type at 18p each } type

### BOOKS

We have a large selection of Reference and Technical Books in stock. Details are in our latest Catalogue. Send for it TODAY, using the coupon below. N.B. Books are void of V.A.T.

Send for lists of publications

## Our famous P1 Pak is still leading in value

Full of Short Lead Semiconductors & Electronic Components, approx. 170. We guarantee at least 30 really high quality factory marked Transistors PNP & NPN, and a host of Diodes & Rectifiers mounted on Printed Circuit Panels. Identification Chart supplied to give some information on the Transistors.

11p P & P on this Pak.

Please ask for Pak P.1. only **55p**

Please send me the FREE Bi-Pre-Pak Catalogue

NAME .....

ADDRESS .....

ALL PRICES INCLUDE 10% VAT

MINIMUM ORDER 50p. CASH WITH ORDER PLEASE. Add 11p post and packing per order OVERSEAS ADD EXTRA FOR POSTAGE

BUY THESE GOODS WITH ACCESS

## Tested and Guaranteed Paks



- B79 4 IN4007 Sil. Rec. diodes. 55p
- 1,000 PIV lamp plastic
- B81 10 Reed Switches, 1" long, 55p
- 1/4" dia. High Speed P.O. type
- H35 100 Mixed Diodes, Germ. 55p
- Gold bonded, etc. Marked and Unmarked.
- H38 30 Short lead Transistors, 55p
- NPN Silicon Planar types
- H39 6 Integrated Circuits. 55p
- 4 Gates BMC 962, 2 Flip Flops BMC 945
- H41 2 Sil Power transistors 55p
- comp pair BD131/132
- H43 4 2N3055 type NPN Sil. 55p
- power transistors. Below spec. devices
- H44 4 3819 N Channel FETs 55p
- 2N3819 in plastic case



## Unmarked Untested Paks

- B1 50 Germanium Transistors 55p
- PNP, AF and RF
- B66 150 Germanium Diodes 55p
- Min. glass type
- B83 200 Transistors, manufacturers 55p
- rejects, AF, RF, Sil. and Germ.
- B84 100 Silicon Diodes DO-7 55p
- glass equiv. to OA200, OA202
- B86 100 Sil. Diodes sub. min. 55p
- IN914 and IN916 types
- H34 15 Power Transistors, PNP, 55p
- Germ. NPN Silicon TO-3 Can.
- H67 10 3819N Channel FETs 55p
- plastic case type

## Make a rev counter for your car

The 'TACHO BLOCK'. This encapsulated block will turn any 0-1mA meter into a linear and accurate rev. counter for any car with normal coil ignition system.

**£1-10p each**

**BI-PRE-PAK LTD**

Co Reg No 820919

Dept. D. 222-224 WEST ROAD, WESTCLIFF-ON-SEA, ESSEX.

TELEPHONE: SOUTHEND. (0702) 46344.

NEW from A.S.P.

**2" and 4" PANEL METERS**  
2" 4"

SIZE: 60mm Wide x 45mm High x 30mm Deep.	SIZE: 110mm Wide x 82mm High x 45mm Deep.	Ohms	Ohms
0-50 micro A.	1350	0-50 micro A.	1400
0-100 micro A.	580	0-100 micro A.	730
0-500 micro A.	170	0-500 micro A.	200
0-1 mA	170	0-1 mA	200
0-5 mA	170	0-5 mA	200
0-10 mA	5	0-10 mA	5
0-50 mA	0.5	0-50 mA	0.5
0-100 mA	0.5	0-100 mA	0.5
0-500 mA	0.5	0-500 mA	0.5
0-1 AMP	0.5	0-1 AMP	0.5
0-2 AMP	0.5	0-2 AMP	0.5
0-25 Volt	15K	0-25 Volt	15K
0-50 Volt	50K	0-50 Volt	50K
0-300 Volt	300K	0-300 Volt	300K
"g" Meter	170	"g" Meter	200
VU Meter	5250	VU Meter	5250

VU Meters are complete with detectors. Modern wide view can be illustrated. Price 2" £2.95 Post 10p. Price 4" £3.95 Post 10p. Lamps 55p per set.

**CARBON FILM RESISTORS**

also available 1 watt at 70°C E 12 range 10Ω-1MΩ 5% tol above 470 KΩ 10% tol at 97p per 100.

**POWER UNIT Type A125**

Supplying 6 or 9 Volt DC at 200 mA.

In moulded case forming a 2 pin 5 A mains plug. 2 metre output lead with 4-way multiplying giving 2:1 and 2.5 mm sockets and 3.5 mm plugs.

Price £2.25. Post 10p.



**ELECTRONIC MAINS TIMER**

A reliable unit ideal for timing Bathroom/Toilet Ventilators Stairways Clockwork Lighting etc.

Gives up to 20 mins delay before switching off. Delay 1-30 mins. adjustable. Max Load 400A or 1000 watts resistive. White Case 3 1/2" x 3 1/2". Fitting instructions included.

Trade Price £5.80. Post 20p.



**MAINS KEYNECTOR**

The safe, quick, connector for electrical appliances.

13 Amp rating, fused, will connect a number of appliances quickly and safely to the mains.

Ideal for testing, demonstrating, window displays, etc. Warning Light, interlocked to prevent connecting when live.

Trade Price: £2.95. Post 25p.



# TRANSFORMERS

**SAFETY ISOLATING**

Prim. 120/240V. Sec. 120/240V. Centre Tap with Screen.

VA (watts)	Ref. No.	Price Case	Open	Post
60	149	—	£3.74	0.38
100	150	—	4.16	0.52
200	151	£9.48	7.48	0.52
250	152	12.05	9.57	0.65
350	153	14.00	11.44	0.80
500	154	15.80	13.20	1.00
1000	156	30.70	27.46	1.20
2000	158	60.95	55.44	—
3000	159	79.53	72.49	—

**12 & 24 Volts Prim. 200-240V.**

Atms 12V	24V	Ref. No.	Price £	Post
0.3	0-15	242	1.34	0.22
0.5	0-25	111	1.34	0.22
1	0-5	213	1.89	0.22
2	1	71	2.09	0.22
4	2	18	2.75	0.38
6	3	70	3.58	0.42
8	4	108	3.96	0.52
10	6	72	4.67	0.52
12	6	116	5.97	0.52
16	8	17	6.64	0.52
20	10	115	10.23	0.69
30	15	187	13.75	0.97
40	20	232	18.26	1.00
50	30	226	22.52	1.10

**30 Volts**

Prim. 200 240V. Sec. 12, 15, 20, 24, 30V.

Amps	Ref. No.	Price £	Post
0.5	112	1.58	0.22
1	79	2.20	0.38
2	3	3.18	0.58
3	20	3.98	0.42
4	41	4.68	0.52
5	51	5.80	0.52
6	117	6.93	0.52
8	88	9.00	0.67
10	89	10.00	0.67

**AUTO TRANSFORMERS**

Cased versions are 240 Volt Mains to 115 Volts, smart cast enameled units coated in tough resin with power lead, fuse and 115 Volt American type socket up to 500VA, above 500VA cable entry.

VA (Watts)	Ref. No.	Price Case	Open	Post
Tapped at 115, 200, 220, 240 Volts				
20	113	—	1.32	0.22
75	64	—	2.63	0.30
Tapped at 115, 220, 240 Volts				
150	4	—	3.29	0.39
200	65	5.56	3.96	0.40
300	66	—	4.84	0.52
500	67	9.50	8.03	0.67
1000	84	15.92	13.50	0.82
2000	95	29.70	25.30	1.50
3000	73	—	33.00	1.20
20VA version uncased, no fuse			£2.52	0.30

**PLEASE ADD 10% FOR V.A.T.**

**50 Volts**

Prim. 200-240V. Sec. 19, 25, 33, 40, 50V.

Amps	Ref. No.	Price £	Post
0.5	102	2.11	0.30
1	103	3.08	0.38
2	104	4.29	0.42
3	105	5.77	0.52
4	106	7.48	0.52
6	107	11.00	0.67
8	118	14.19	0.97
10	119	17.60	0.97

**60 Volts**

Prim. 200-240V. Sec. 24, 30, 40, 48, 60V.

Amps	Ref. No.	Price £	Post
0.5	124	2.10	0.38
1	126	2.97	0.38
2	127	5.77	0.42
3	125	7.15	0.52
4	123	9.35	0.67
5	40	11.55	0.67
6	129	13.57	0.82
8	121	16.00	1.00
10	122	19.40	1.00
12	180	21.62	1.10

**MINIATURE AND EQUIPMENT**

Prim. 240V with screen.

Sec. 1 Volts	Sec. 2	Milliamps	Ref. No.	Price £	Post
3-0-3	—	200	338	1.23	0.10
0-4	0-6	500	334	1.30	0.10
0-6	0-5	1000	112	1.88	0.22
0-0-9	—	100	13	1.23	0.10
0-9	0-9	330	330	2.35	1.43
0-8-9	0-8-9	500	297	2.28	0.22
0-8-9	0-8-9	1000	208	3.08	0.30
15-0-15	—	40	240	1.23	0.10
0-15	0-15	200	236	1.30	0.10
20-0-20	—	30	241	1.23	0.10
0-20	0-20	150	337	1.30	0.10
0-15-20	0-15-20	500	205	2.97	0.38
0-15-20	0-20	300	300	2.14	1.76
0-20	—	3500	NO SCREEN	1116	3.00
20-12-0-12-20	—	700 (D/C)	—	221	1.55
0-15-20	0-15-20	1000	1000	2.06	8.80
0-15-27	0-15-27	500	500	2.93	3.08
0-15-27	0-15-27	1000	1000	2.94	0.38

**PLASTIC CASED SILICON BRIDGE RECTIFIERS**

One Amp	Two Amp	Four Amp	Six Amp
60 P.I.V. 25p	60 P.I.V. 35p	100 P.I.V. 55p	50 P.I.V. 85p
100 P.I.V. 25p	100 P.I.V. 40p	200 P.I.V. 58p	100 P.I.V. 70p
200 P.I.V. 28p	200 P.I.V. 45p	400 P.I.V. 65p	200 P.I.V. 80p
600 P.I.V. 80p	400 P.I.V. 75p	600 P.I.V. 75p	400 P.I.V. 80p

ADD 10p P & P PER ORDER



**QUALITY INSTRUMENT CASE**

Strongly moulded in High Gloss Grey Plastic (Flame Retardant ABS).

Two interlocking halves secured by four corner bolts (supplied).

Interior Size: 6 1/2" x 5 1/2" x 2 1/2"

Wall Thickness: 1/4"

Weight: 1 1/2 lbs.

Price: £1.50. Post 15p.

## A.S.P. LTD.

BYRE HOUSE, SIMMONDS ROAD, WINCHEAP, CANTERBURY, KENT. Tel: (0227) 52436

### NEW! TODAY'S MOST EXCITING SPEAKERS



Never before have speakers of such superb performance and low cost been available. Produced by us to quality standards the new *GS Range* offer you true high fidelity at a fraction of the cost. Both models employ fully sealed bass reflex enclosures made from quality compressed woods and our modern compact designs ensure optimum performance at all times. Finished in Rich American Walnut effect, Black Satin front these speakers offer today's best value in high quality equipment.

**TECHNICAL SPECIFICATIONS GS500** Power 30 Watts Peak (15 Watts RMS) Frequency Range 33Hz to 19000Hz Impedance 8 Ohms Bass Unit 16 cm round long throw Treble Unit 7.5cm round Crossover 5kHz Dimensions 45cm x 22.5cm x 22.5cm (18" x 9" x 9") Volume 17 litres.

**TECHNICAL SPECIFICATIONS GS300** Power 20 Watts Peak (10 Watts RMS) Frequency Range 42Hz to 16500Hz Impedance 8 Ohms Drive Unit 20cm x 13cm long throw with integral coaxial tweeter Crossover 5kHz Dimensions 40cm x 20cm x 20cm (16" x 8" x 8") Volume 12 litres.

GS 500 £11.98 post free GS 300 £9.98 post free

**ECONOMY Speaker System** Ideal for budget hi-fi Stereo Etc. This unique 8 Ohm system comes complete with leads and super woodgrain finish £9.80 pair post free

PLEASE ADD 10% VAT TO ALL ORDERS TRADE ENQUIRIES WELCOME

GREGG ELECTRONICS PW4 24 Cranbourn Street Leicester Square London WC2

**GREGG**

Please mention

# PRACTICAL WIRELESS

when replying to advertisements



## BROADCAST BANDS

### SHORT WAVE DX by MALCOLM CONNAH

**A** 'Radio Australia Listeners' Club Group' has been formed by **George Hewlett** of 22 Park Hill Road, Torquay, Devon and **Miriam Bryant** of 2 Broad Street, St. Columb, Cornwall. The club is not only for members of the official Listeners' Club but for anyone interested in listening to Radio Australia.

Although the club will mainly serve the South West of England the founders are prepared to answer any queries about the reception of Radio Australia. They would appreciate a stamped addressed envelope with any query requiring an answer.

### Readers' Logs

The first two logs this month come from the husband and wife team of **Douglas** and **Rita Malpus** from Cumberland. Douglas uses a 5 valve domestic receiver and a 25 foot end-fed antenna, which is often used at an alternative address in Scotland. Rita uses a Ferguson-Caravelle Transportable with a 120 feet long-wire and ATU. The results achieved were as follows.

#### Douglas Malpus

6205 R. North Sea International at 1900.  
9670 IBRA Radio noted at 2100.  
11775 R. Nacional D'Espana at 1715.  
15185 R. Finland noted at 1820.  
15295 ORTF, Paris, France at 1110.  
15305 SBC, Berne, Switzerland at 1100.  
15415 R. Kuwait noted at 1850.  
15440 WYFR, USA noted at 2230.  
17770 Radio Sweden at 1400.  
17885 HCJB, Quito, Ecuador at 2130.

#### Rita M. Malpus

9525 AIR, General Overseas Service at 2020.  
9535 SBC, Berne, Switzerland at 2200.  
9650 Deutsche Welle, Cologne at 2145.  
9690 R. Bucharest, Rumania at 1315.  
9833 R. Budapest, Hungary noted at 2230.  
9750 R. Vilnius, Lithuania at 2230.  
11810 V. of Turkey, Ankara noted at 2230.  
15185 R. Finland noted at 2030.

**Christopher L. Hodgson** of Sunderland used his

Codar MultiBand 6 with a 50 foot end-fed, 9 metre inverted vee and an ATU to hear:

9455 Radio Pyongyang noted at 2015.  
9540 Radio Australia, S/on at 1800.  
9695 Trans World Radio, Monte Carlo at 0820.  
11720 R. Nacional, Brazilia at 2315.  
11905 UN Radio, Greenville at 2205.  
15084 R. Tehran, Iran in Farsi at 1030.  
15310 BBC, Far East Relay (Malaysia) at 1530.  
15410 UN Radio, Greenville at 1625.  
15570 Radio Pakistan, S/on at 1530.  
17820 Radio Canada Int. in Czech. at 1715.  
17885 BBC, Cyprus relay at 1155.  
21685 Radio Kuwait, S/off in Arabic at 1505.

**William F. Kitching** of Telford in Shropshire has a Grundig Satellit 2000 receiver and using only the telescopic aerial he heard the following:

3980 VOA, Munich noted at 2100.  
3985 SBC, Berne, Switzerland at 0700.  
6015 ORTF, Paris, France noted at 0515.  
11730 Radio Nederland, Bonaire relay at 0630.  
15012 Voice of Vietnam at 1800.  
15195 R. Afghanistan noted at 1130.  
17855 NHK, Radio Japan at 0900.  
21535 RSA, South Africa noted at 1500.  
21655 R. Norway (Sundays) at 1400.  
21740 VOA, Greenville at 1700.  
25790 RSA, South Africa noted at 1330.

**Albert E. Ord** of South Shields again used his Trio 9R59DS with a Joystick antenna and Hamgear pre-selector the log for this month including:

3905 AIR, India in English at 2330.  
4955 R. Nacional, Colombia in Spanish at 0530.  
5990 HCJB, Quito, Ecuador in English at 0645.  
9410 R. Pyongyang in English at 2140.  
9570 R. Australia noted at 0800.  
9620 S.O.D.R.E., Uruguay in Spanish at 2200.  
11775 R. Bucharest in English at 0430.  
11780 R. New Zealand heard at 0730.  
11825 V. of Free China, Taiwan, English at 1930.  
15415 R. Kuwait, Pop Music at 1945.  
17755 HCJB, Quito, Ecuador in English at 1900.  
21540 R. Ghana heard in English at 1500.

**Trevor Bland** of Lea, near Gainsborough in Lincolnshire, used his Telton TF-182 to log the following:

5960 R. Canada Int. in English at 1030.  
6030 AFRTS, Washington in English at 0130.  
6040 VOA, Washington in English at 1935.  
7280 R. Moscow in English at 2025.  
9022 R. Tehran, Iran in English at 2005.  
9585 R. Finland in English at 2030.  
9625 R. Canada Int. in English at 2400.  
11815 TWR, Bonaire relay in English at 0100.  
15385 R. Nacional, Brazil in English at 2015.  
15430 AFRTS, Washington in English at 1730.  
17880 HCJB, Quito, Ecuador in English at 2015.



## MEDIUM WAVE BROADCASTS by CHARLES MOLLOY

**N**ICHOLAS Taylor who lives at Sunbury-on-Thames does his medium wave DXing with an Ultra 4175 receiver and a medium wave loop antenna. Local radio stations logged include IBA London on 719kHz; BBC Radio Blackburn on 854kHz; Solent on 998kHz; Medway on 1034kHz; Leeds on 1106kHz; Derby on 1115kHz; London on 1457kHz; Brighton on 1484kHz; Nottingham on 1520kHz; Bristol on 1546kHz. Nicholas has been hunting-out the stations on the American Forces Network in West Germany and he reports hearing AFN Frankfurt on 872kHz; Berlin on 935kHz; Munich on 1106kHz; Stuttgart on 1142kHz; Heidelberg on 1304kHz; Augsburg on 1394kHz and low power relays on 611kHz and 1502kHz. Karlsruhe on 1034kHz is another outlet to look for. The Armed Forces Radio and Television Service (AFRTS) operates in many countries other than Germany. Stations heard occasionally in the UK are Keflavik, Iceland on 1484kHz; Lajes, Azores on 1500kHz; Kenitra, Morocco also on 1484kHz and Athens, Greece on 1594kHz.

**Kevin Peel** (Hornchurch, Essex) has been busy with his Astrad receiver and 100ft outdoor aerial. He reports hearing BBC Radio Derby on 1115kHz; AFN Munich on 1106kHz; AFN Stuttgart 1142kHz and the 1000kW station at Cluj in Romania on 1151kHz. During the summer months Cluj along with Lugof on 755kHz carry a multi-lingual programme for

tourists at 2230hrs GMT with programmes of Romanian music and announcements in English, French and German. Both stations will verify a correct reception report with a QSL card.

**Brendon McNamee** reports again from Portrush in N. Ireland. With his Sharp BZ-23 receiver and whip antenna he has logged BBC Radio Derby 1115kHz at 2338hrs; Manx Radio, Isle of Man on 1295kHz at 1655hrs; Radio Sweden 1178kHz with its international service at 0020hrs.

Our regular reporter **Brian Murray** (Edinburgh) has been concentrating on the local radio networks. With his Astrad VEF 204 receiver connected to an externally mounted TV aerial he has heard IBA Birmingham on 1151kHz with close down at 0105hrs; IBA Manchester also on 1151kHz testing at 0130hrs; BBC local radio stations at Carlisle on 755kHz at 1415hrs; Blackburn on 854kHz at 1410hrs; Sheffield on 1034kHz at 0100hrs; Medway 1034kHz at 2245hrs; Leeds 1106kHz at 2350hrs; Derby 1115kHz at 2240hrs; Bristol 1546kHz at 2258hrs and Leicester 1594kHz at 2255hrs. Brian also reports hearing two stations from the Iberian peninsula. From Spain, Radio Centro, Madrid on 1385kHz at 0155hrs and from Portugal CSB2, Radio Club Portugues in Lisbon on 1034kHz at 0020hrs. Externally mounted TV aerials often give good results as a medium wave antenna. Try connecting both the inner and the outer of the co-axial down lead to the aerial socket of the MW receiver. The outer (shield) will make a good vertical aerial in localities free from electrical interference.

Radio Algeria can be heard on 251kHz (1195m) on the long waves in English between 1900hrs and 1930hrs GMT every evening. The signal, which comes from a 750kW transmitter at Tipaza, is heard well in the UK. The station asks for reception reports which should be sent to Radio Algeria, 21 Boulevard des Martyrs, Algiers, Algeria.

## VHF/FM DXING

by SIMON DAVID

**I**F we could forecast, with a useful degree of accuracy, likely openings for f.m. DXing then one could assume that we would be able to tune in together and all obtain near perfect results. It is easy to assume this, but the facts are different. What one DXer may pick up at one instant may be very different from the fortunes of another 100 miles or more away. It is sometimes forgotten that some British local radio stations may be as far away as some of the continentals, for example, North France and North England are approximately the same distance from Bristol or Oxford.

Here is a useful idea that could be helpful to f.m. DXers. For 50p you can buy the new large British Rail timetable. Now why should this be of any value to DXing? Well, included with it are two large double-sided maps—one of Gt. Britain and the other of Europe as far east as the Black Sea. These are clearly marked with the main towns and railways and make a very clear f.m. DXers map. (These maps are worth the 50p alone in my opinion.) If you cannot get one then any other flat map of Europe will do. ("Global" maps tend to distort distance lines.)

Now use a large pair of compasses, or the cotton-and-pencil technique, to draw concentric circles about the centre point representing your home town. These circles can be drawn to the scale of the map to represent distances of 25, 50, 75, 100 etc. miles from

your home. Next go over the map thoroughly and pick out all the known f.m. transmitting stations and draw a box around the place name to help it to stand out. When you have received any of these stations on your f.m. radio receiver, you can fill in the box with a light coloured pencil.

If your aerial is installed in a fixed position, determine as accurately as possible the compass point or transmitter towards which it is directed. Draw a straight line on the map through your home town representing this aerial direction and continue that line as far as possible across the map. You now have a quick reference chart to locate any station that comes in within a reasonable distance of that aerial line. If you want a reference for marking f.m. transmitters on the map you can either do it the hard way by going through all the radio station details in the World Radio and TV Handbook or use the f.m. station list that I mentioned last month.

My thanks to all readers who have written to me including **Bob Bonsall** of Buxton, **F. Walshe** of Southport who has picked up the Isle of Man, R.T.E., Lille and several northern local stations using a Stolle rotator. **Geoffrey Tyrell** writes from Aylesbury who (I am delighted to learn) has come back to P.W. after four years in the wilderness. He makes some observations about stations that he can pick up with only a single dipole arrangement and a Hacker Hunter portable radio. These include BRMB, LBC, Capital, BBC Radio London, Medway, Birmingham, Oxford and Stoke.

The new Oryx 50 is temperature controlled, light, small, easy to handle, rapid heating and high performance. It has a temperature control within  $\pm 2^{\circ}\text{C}$  and adjusted in seconds whilst running to any value between  $200^{\circ}\text{C}$  and  $400^{\circ}\text{C}$ . Long life iron coated tip as standard (11 sizes available).

Oryx De-Soldering Irons—small model SR3A instantly removes solder from printed circuits etc. accurate, reliable, simple. PTFE nozzle. Larger instrument SR2 gives more suck, less recoil as only piston moves.



De-Soldering Tools  
SR3A £5.06  
SR2 £6.65  
Oryx 50 Iron  
1 at £6.60



**ORYX 50**  
TEMPERATURE  
CONTROLLED IRON  
**ORYX SR3A**  
DESOLDERING  
TOOL

Lower prices for quantities

Safety Stand £2.44


Prices Correct May 1974  
Prices include P & P and 10% VAT

## WH-MK spacemiser storage system

Cabinets have stove enamelled steel frames in three heights all of equal width and depth. The frames are strong and rigid, fitted with top and bottom locating pegs and rear slots making stacking, wall or frame mounting positive and simple.

	1 off	4 off
121, 122, 123, 124	£4.07	£3.70
251, 252, 253	£6.15	£5.50
501, 502, 503	£10.67	£9.68
254, 257, 258	£5.83	£5.30
504, 507, 508	£10.01	£9.06

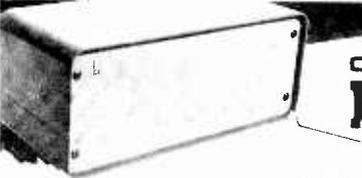Less for quantities  
All prices include P & P and 10% VAT. Prices correct May 1974.



**CONTIL  
MOD-3**

Width Height Depth

Contil Mod-3 cases are in six sizes and offer the manufacturer of small instruments an attractive low cost case available ex stock. Made in blue PVC coated steel and complete with front and rear panels and chassis they are light, strong and rigid. PCE and PSU mounting systems available.	Mod-301	£4.02	7	3	5
	Mod-302	£4.72	7	4	5
	Mod-303	£4.78	7	6	5
	Mod-304	£4.78	11	3	5
	Mod-305	£5.69	11	4	5
	Mod-306	£6.58	11	6	5

Less for quantities. Prices correct May 31  
Prices include P & P 10% VAT feet and screws



**BRADRAD**  
DRILLING AND  
DEBURRING  
TOOL

**BRADRAD DRILLING AND DEBURRING TOOL** equals eleven drills. One cut drills and deburrs the normal run of steels, aluminium, brass, copper and all types of plastics, perspex, fibre glass, etc. and hardboard should the need arise it is designed to overcome all the problems associated with drilling the materials—it drills interlocking holes for instance.

**Q-MAX  
METAL PUNCH**

Q-MAX PUNCHES

1/2" - 2 1/2" in 1/8" steps or 6-36mm in 3mm steps. Both with 1/8" shanks	£11.38
1/8" - 7/8" Also 1/2" - 2 1/2" and 36-60 mm. £27.88.	£11.47
All prices include P & P and 10% VAT. Prices correct May 31	£11.88
	£2.22



**ADEL  
NIBBLING TOOL**

**ADEL** The Adels cuts holes of virtually any shape and size starting from a 1/8" hole, cutting cleanly like a punch and die. Ideal for notching clearances on flanges of cabinets or chassis £8.78.



**CONTIL  
MOD-2**

W.	H.	D.	1 off	W.	H.	D.	1 off
A 4 1/2"	3"	5 1/2"	£3.60	M 4 1/2"	3"	13"	£4.44
B 4 1/2"	7"	6 1/2"	£4.44	N 4 1/2"	7"	13"	£5.44
C 4 1/2"	10"	6 1/2"	£4.91	O 4 1/2"	10"	13"	£8.91
D 9"	3"	6 1/2"	£4.91	P 9"	3"	13"	£5.44
E 9"	7"	6 1/2"	£5.44	Q 9"	7"	13"	£6.91
F 9"	10"	6 1/2"	£6.28	R 9"	10"	13"	£8.41
G 13"	3"	6 1/2"	£5.44	S 13"	3"	13"	£6.91
H 13"	7"	6 1/2"	£6.28	T 13"	7"	13"	£8.41
I 13"	10"	6 1/2"	£8.91	U 13"	10"	13"	£10.20
J 18"	3"	6 1/2"	£6.28	V 18"	3"	13"	£8.41
K 18"	7"	6 1/2"	£8.41	W 18"	7"	13"	£10.20
L 18"	10"	6 1/2"	£10.20	X 18"	10"	13"	£12.21

The design of these cases permits the instrument to be built or serviced within their external panels. 48 shapes. Low cost. Blue PVC/Steel with white P.V.C./aluminium panels. Prices correct May 1974.

Woodgrain: D £5.44, E & G £6.28, H £8.91. Prices include screws, rubber feet, one or two chassis according to size and P & P, and VAT.  
**WEST HYDE DEVELOPMENTS LTD., RYEFIELD CRE., NORTHWOOD HILLS, MIDD. X46 1NN.** Tel: Northwood 24941 or 26732 Telex: 923231

# Trannies

4 BUSH HOUSE,  
HARLOW, ESSEX

Retail shop open 9 to 5.30  
Mon. to Sat.

Telephone: 37739

P. & P. 15p.

Catalogue 20p.

## 74 Series TTL

(National Semiconductors and I.T.T.)  
LOW PRICES, HIGH QUALITY

* 100 plus less on 10% the 25+ column	No's 1+ 7416	1+ 22-81 7447	25+ 22-81 7448	1+ 22-81 7449	25+ 22-81 7450	1+ 22-81 7451	25+ 22-81 7452	1+ 22-81 7453	25+ 22-81 7454	1+ 22-81 7455	25+ 22-81 7456	1+ 22-81 7457	25+ 22-81 7458	1+ 22-81 7459	25+ 22-81 7460	1+ 22-81 7461	25+ 22-81 7462	1+ 22-81 7463	25+ 22-81 7464	1+ 22-81 7465	25+ 22-81 7466	1+ 22-81 7467	25+ 22-81 7468	1+ 22-81 7469	25+ 22-81 7470	1+ 22-81 7471	25+ 22-81 7472	1+ 22-81 7473	25+ 22-81 7474	1+ 22-81 7475	25+ 22-81 7476	1+ 22-81 7477	25+ 22-81 7478	1+ 22-81 7479	25+ 22-81 7480	1+ 22-81 7481	25+ 22-81 7482	1+ 22-81 7483	25+ 22-81 7484	1+ 22-81 7485	25+ 22-81 7486	1+ 22-81 7487	25+ 22-81 7488	1+ 22-81 7489	25+ 22-81 7490	1+ 22-81 7491	25+ 22-81 7492	1+ 22-81 7493	25+ 22-81 7494	1+ 22-81 7495	25+ 22-81 7496	1+ 22-81 7497	25+ 22-81 7498	1+ 22-81 7499	25+ 22-81 7500																																																							
	7416	22-81	7447	22-81	7448	22-81	7449	22-81	7450	22-81	7451	22-81	7452	22-81	7453	22-81	7454	22-81	7455	22-81	7456	22-81	7457	22-81	7458	22-81	7459	22-81	7460	22-81	7461	22-81	7462	22-81	7463	22-81	7464	22-81	7465	22-81	7466	22-81	7467	22-81	7468	22-81	7469	22-81	7470	22-81	7471	22-81	7472	22-81	7473	22-81	7474	22-81	7475	22-81	7476	22-81	7477	22-81	7478	22-81	7479	22-81	7480	22-81	7481	22-81	7482	22-81	7483	22-81	7484	22-81	7485	22-81	7486	22-81	7487	22-81	7488	22-81	7489	22-81	7490	22-81	7491	22-81	7492	22-81	7493	22-81	7494	22-81	7495	22-81	7496	22-81	7497	22-81	7498	22-81	7499	22-81	7500	22-81

## Linear Integrated Circuits

301 DIL	50p
301 TO99	55p
301 8 PIN DIL	48p
301A DIL	69p
301A TO99	69p
301A 8 PIN DIL	66p
307 DIL	69p
307 TO99	69p
307 8 PIN DIL	66p
308 TO99	64p
308A TO99	64p
709C DIL	35p
709C TO99	31p
723C DIL	99p
723C TO99	95p
741C 8 PIN DIL	38p
741C 14 PIN DIL	39p
741C TO99	41p
747C DIL	86p
748C DIL	39p
748C TO99	41p
MC1310P	1.88
	3.38

## Resistors

1/2 watt 5% carbon	1p
1/2 watt 5% carbon	1p
1 watt 10% carbon	21p
range 10 ohms to 47 megohms.	
1/2 watt m/o 2%	4p
range 10 ohms to 1 megohms.	

This is only a small selection from our range of components. Send 20p for our SUMMER 74 CATALOGUE.

## VOLUME BOARD

0.1	0.15
2 1/2 x 3 1/2	18p
2 1/2 x 5	27p
3 1/2 x 3 1/2	27p
3 1/2 x 5	31p
17 x 2 1/2	82p
17 x 3 1/2	£1.10
17 x 5 (Plain)	90p
Pin insertion too	57p
Spot face cutter	46p
Pk 36 Pins	20p

## Electrolytic Capacitors

4 VOLT		16 VOLT		40 VOLT	
47µF	61p	15µF	61p	47µF	61p
100µF	61p	33µF	61p	100µF	61p
220µF	61p	150µF	61p	220µF	11p
330µF	61p	150µF	61p	220µF	11p
1000µF	18p	220µF	61p	470µF	18p
4700µF	28p	680µF	17p	680µF	25p
6.3 V 20p		1000µF	17p	1000µF	25p
33µF	61p	1500µF	25p	2200µF	44p
68µF	61p	2000µF	48p		
150µF	61p				
470µF	11p	25 VOLT			
680µF	13p	10µF	61p		
1500µF	18p	22µF	61p		
2200µF	18p	100µF	61p	63 VOLT	
3300µF	26p	150µF	61p	2.2µF	61p
		220µF	61p	6.8µF	61p
		220µF	61p	10µF	61p
		470µF	10p	22µF	61p
		1000µF	10p	68µF	10p
		220µF	61p	100µF	11p
		470µF	61p	1000µF	11p
		8p	5000µF	68p	100µF
		330µF	10p	220µF	10p
		1000µF	10p	220µF	10p
		1500µF	11p	330µF	25p
		1500µF	20p	470µF	25p
		2200µF	24p	1000µF	44p

## VOLUME CONTROLS

**Potentiometers**  
Carbon track 500Ω to 2.2MΩ.  
Log or Linear.  
Single 18p. Dual gang (stereo) 44p.  
Single type with D.P. switch 18p extra.

## CARBON SKELETON PRESETS

Small high quality type (linear only). All values 100-5 meg ohms.  
-1 watt 6p each  
-2.5 watt 61p each

## THYRISTORS

See our advertisements in Practical Electronics and Everyday Electronics for range of transistors and diodes.

## SLIDE SWITCH

8PST 11p each. D.P.D.T. 18p each.

## MINIATURE NEON LAMPS

240V or 110V 1.4 5p. 5 plus 41p each.

## Mullard Polyester Capacitors

### C280 SERIES

250V P.C. mounting: 0.01µF, 0.015, 0.022 81p. 0.033, 0.047, 0.068 4p. 0.1 41p. 0.15, 0.22 51p. 0.33 7p. 0.47 91p. 0.68 12p. 1µF 14p. 1.5µF 22p. 2.2µF 27p.

### C295 SERIES

400V: 0.001µF, 0.0015, 0.0022, 0.0033, 0.0047 3p. 0.0068, 0.01, 0.015, 0.022, 0.033 81p. 0.047, 0.068, 0.1 41p. 0.15 81p. 0.22 81p. 0.33 12p. 0.47 14p. 150V: 0.01µF, 0.015, 0.022, 0.033, 0.047, 0.068 81p. 0.1 41p. 0.15 4p. 0.1 41p. 0.15, 0.22 51p. 0.33 7p. 0.47 91p. 0.68 12p. 1µF 14p. 1.5µF 22p. 2.2µF 24p.

**CUSTOM CABINETS 328/30 The Banks, Rochester, Kent. Tel : Medway (0634) 404199**

**Speaker Cabinets in kit form represent HUGE SAVINGS**



2' x 12" Cabinet



4' x 12" Cabinet



Disco Console (includes lid not shown)  
Takes two slaves

For a long time now a large number of customers have asked us to produce cabinets in kit form, and above we show examples of cabinet styles and these are now available either fully built or in kit form ready for you to produce a professional finish in a very short time!

Kits are available in all specifications and all the kits contain everything you need as follows:-

- 1) 4 sides with handle cutouts, front edges rounded, 1 back with jack socket hole, and 1 baffleboard with speaker cutout
- 2) P.V.C. cut to size for frame and back, plus false front and back timbers, white front piping and speaker cloth
- 3) Recessed handles with fixing screws, jack socket, all fixing screws, corner plates, glue, and full instructions!

**PRICE & TYPE LIST**

Type	Size	Price manufactured	Kit price
2 x 12" (illustrated above)	36" x 18" x 13" x 3/4"	£19.50	£12.50
4 x 12" (illustrated above)	31" x 31" x 13" x 3/4"	£24.50	£17.50
4 x 12" P.A. Column	48" x 27" x 13" x 3/4"	£30.00	£21.50
1 x 18"	31" x 31" x 13" x 3/4"	£24.50	£17.50
1 x 15" with two top horn cutouts	36" x 20" x 13" x 3/4"	£21.00	£13.50
Mini Disco (state deck cutout BSR, GARRARD etc.)	33" x 20" x 48" x 1/2"	£20.00	£13.00
Maxi Disco (illustrated) (state deck cutout BSR, GARRARD etc.)	42" x 20" x 10" x 1/2"	£25.00	£18.50

Please ask for quotation on any other type or size of cabinet you may require.

**ALL OUR PRICES INCLUDE VAT AND UK DELIVERY**

# YOUR CAREER in RADIO & ELECTRONICS ?

Big opportunities and big money await the qualified man in every field of Electronics today—both in the U.K. and throughout the world. We offer the finest home study training for all subjects in radio, television, etc., especially for the CITY & GUILDS EXAMS (Technicians' Certificates); the Grad. Brit. I.E.R. Exam.; the RADIO AMATEUR'S LICENCE; P.M.G. Certificates; the R.T.E.B. Servicing Certificates; etc. Also courses in Television; Transistors; Radar; Computers; Servo-mechanisms; Mathematics and Practical Transistor Radio course with equipment. We have OVER 20 YEARS' experience in teaching radio subjects and an unbroken record of exam. successes. We are the only privately run British home study College specialising in electronics subjects only. Full details will be gladly sent without any obligation.

To: British National Radio & Electronics School, P.O. Box 156, Jersey, C.I.

Please send FREE BROCHURE to

NAME ..... Block  
 ADDRESS ..... Caps.  
 ..... Please  
 ..... W.C. 84

**BRITISH NATIONAL RADIO  
AND ELECTRONICS SCHOOL**

# FERRANTI



**Buy from the experts!**

- \* ALL DEVICES BRAND NEW, TOP GRADE, AND TO FULL MANUFACTURERS SPECIFICATION. WE DO NOT SELL SECONDS OR REJECTS.
- \* WE HAVE STOCKS OF ALL DEVICES FOR IMMEDIATE DELIVERY
- \* WE CAN SUPPLY ANY FERRANTI DEVICE TO ORDER. Send SAE for quotation.
- \* WE ARE SPECIALISTS IN FERRANTI SEMICONDUCTORS, WITH A STAFF OF EXPERIENCED ENGINEERS.

## ZN414 £1-32 WITH CIRCUITS AND DATA

BFS59	15p	ZTX310	9p	ZTX504	43p	ZS170	10p
BFS60	20p	ZTX311	10p	ZTX510	17p	ZS171	13p
BFS61	20p	ZTX312	10p	ZTX530	21p	ZS172	16p
BFS96	15p	ZTX313	11p	ZTX531	22p	ZS174	17p
BFS97	23p	ZTX314	13p	ZTX550	17p	ZS178	23p
BFS98	20p	ZTX320	31p	ZTX551	17p	ZS178	38p
ZTX107	9p	ZTX330	15p	2N3055	76p	ZS270	11p
ZTX108	8p	ZTX331	16p			ZS271	16p
ZTX109	11p	ZTX382	13p	* DIODES *		ZS272	18p
ZTX212	14p	ZTX383	15p	ZS120	8p	ZS274	19p
ZTX213	14p	ZTX384	18p	ZS121	10p	ZS276	26p
ZTX214	15p	ZTX450	17p	ZS122	13p	ZS278	37p
ZTX300	12p	ZTX451	17p	ZS123	18p		
ZTX301	13p	ZTX500	15p	ZS124	19p	* ZENERS *	
ZTX302	17p	ZTX501	13p	ZS140	25p	KS030A	to
ZTX303	14p	ZTX502	17p	ZS141	43p	KS180A	all
ZTX304	21p	ZTX503	14p	ZS142	33p	types 19	

MOTOROLA MJE2955 £1-30, MJE3055 75p.  
 RCA PRICES SLASHED! CA3075 99p; CA3090Q £3-25 limited quantity only.  
 P.E. TRIFFID ZT1711 24p; 2N1132 25p.  
 GEMINIS AMPLIFIER P.C.B.'s and Semiconductor kits still available.  
 SCORPIO Mk II IGNITION SYSTEM. P.C.B. and all semi-conductors available.

**FREE!** Our comprehensive catalogue giving data and connection diagrams for a wide range of Ferranti semiconductors. Just send an SAE.

POSTAGE & PACKING 10p. FREE ON ORDERS OVER £2.00.  
 ALL OUR PRICES INCLUDE V.A.T.

**DAVIAN ELECTRONICS**

PO BOX 38 OLDHAM, LANCS, OL2 6XJ



by Eric Dowdeswell G4AR

HURRAH! First past the post to drop a report into my lap was Stanley Sharred (Birmingham) who is no newcomer to this page. To refresh your memories he has a CR100 with a horizontal centre-fed aerial, feeding an aerial tuning unit I am glad to note! An ATU will produce more extra 'S' points on the meter than anything else! The 60ft legs of Stan's aerial are in a Vee configuration so the aerial becomes quite a useful beam at the higher frequencies. His Morse is obviously pretty good so it's high time he went off to get his RAE, providing he doesn't neglect his reports of course!

Dave Patrick (Carlisle) at 15 is a regular reader of PW and honoured this page with his first-ever report. His set-up of an R1475 plus two 150ft wires 25ft up should pull in most signals. Try combining the aerials Dave, with an ATU, as does Stanley, above. Switch in one or the other or both. If they can be arranged more or less at right angles good all-round coverage can be obtained. I suppose many readers of this page wouldn't mind being able to get just one 150 footer hanging on the aerial socket!

John Porter (Baslow, Derbys.) wrote an extremely short note with his list of goodies, but very welcome, nevertheless. All I can say about John is that he uses the 9R59DS and 33ft of aerial which is obviously a good combination in the right hands. Incidentally, I am sending out some log sheets which I have run off to those who kindly report in to this feature, hoping that they will jot down for me any worthwhile DX that they hear, at the time they hear it. I know only too well what a bore it is to copy out logs especially some time after the event when interest has waned. A sheet of carbon paper slipped in the log is also a good way of saving time if a copy is wanted. As I point out on the log sheets, it is the rare country or prefix or QRP stations that I would like to know about.

It seems that BV2A on Taiwan (Formosa of old) now has the OK from the authorities to operate and is active on 14218 SSB and 14025 CW. QSL's

have been forthcoming from BV land in the past but this ought to make it very much easier now. You might like to get excited over OJOMA who is expected on from Market Reef with SSB on 14 and 21MHz. The number of these DX-peditions that do eventually get on the air seems to be quite small compared to the number of rumours that one hears and I long ago learnt to wait until the pileup hits the headphones before letting the blood pressure rise at the thought of a 'new one' for the log!

I expect to hear from some of you on the Royal Signals Amateur Radio Society expedition to the British Honduras spot of English Cay, active mid-June as VP1B probably. QSL's to the Society's headquarters station G4RS.

Don't despair of conditions on the HF bands—the information-crammed 160m DX Bulletin of Stew Perry WIBB reckons that things have not been so good last season on our 'DC' band possibly due to too many sunspots around! They would indeed come in useful on the higher frequencies. In spite of all this, however, Stew still lists many prefixes worked on 160m that would grace any 20m log. How about 4S7, VP2, VP8, ZP9, PJ8, ZP1 etc? 'Worked All Continents' is always an exciting achievement, even on the HF bands, but W5RTQ almost did it in one evening on 160m! Only missed out on Africa.

### Log Extracts

S. Sharred:—160m GC5BGV GD4BEG G13YFY GM6CH OE5ANL OH1SJ VE2DN VP2EEL WIHGT (599) WB8APH 80m 7X2AH 9K2DC HC8GI HI8EJH OA4OS ZL2BCG ZL4KF 40m 3D6AW G4AKQ/7Q7 JY3ZH MIC OH2BGM/OH0 T12SW VK2WC VP9AO ZP5AR ZS6ME 20m CR4BS WA2ZDF/CPI KL7BJW KM6DZ OA3XI PJ2CW PJ9JR VE6RP VK7PR OK8OM VP2AB VP2MW VP2VBH VP8LP VRIAC ZL4AD 4S7PB 5X5NK 6Y5ED 8P6EX 15m CR7EK FM7WG HK3CTJ JH3GET KG4FX SV0MEE (Crete) TJ1EZ TU2DV.

D. Patrick:—80m CR4BS EP2VJ OY1M 9H4L 40m CR6CD JW8IL 20m CP1DN CR4BS PJ9DI 9Y4MA.

J. Porter:—15m 9G1AR 9W1BX 20m CP1QCC CP3BY EL5C HK3BET JA0CRL PJ9EE T12CF ZB2CJ CR4LA

S. Sharred again:—160m KZ5AA VE1MX VP2LPJ (St. Lucia) 80m CP1EU EP2VJ (0200) HZ1AB (0200) KV4FZ (2300) VP8NP (0030) ZS6DW (0330) 40m JY3ZH (Amman 0400) KV4FZ (0130) LU8AHW (2330) TR8DG (2130) 20m HM1AQ (1330) KH6BB (1000) KS6UA (1600) FL8BH (1900) PJ9EE (2130) TA2SC (1530) VE8RCS (0900) YB1AY (1730) ZL1AXT (1030) 5U7HA (1730) 15m A51PN (1230) CX8BZ (2030) EL2KS (1230) FG0BAR (1800-QSL to F6CXL) KZ5CZN (2130) VP2SQ (1800-St. Vincent) VP2VBU (1300-Tortola)

CW stations in bold, remainder SSB.

#### BROADCAST BANDS

Short Wave Reports by 15th of the month to Malcolm Connah, 27 Lismore Road, Highworth, Swindon, Wiltshire, SN6 7HU.

Medium Wave Logs to Charles Molloy, 132 Segars Lane, Southport, PR8 3JG.

VHF/FM Reports to Simon David, c/o Practical Wireless, Fleetway House, Farringdon Street, London, EC4A 4AD.

#### AMATEUR BANDS

Logs covering any amateur band/s in band/alphabetical order by the middle of the month to Eric Dowdeswell G4AR, Silver Firs, Leatherhead Road, Ashstead, Surrey, KT21 2TW.



Chapter 2, written by John Borwick delves into the whys and wherefores of pickups, and illustrates how sound is reproduced from tape or record.

Clement Brown, in Chapter 3 writes on pickups and motors and John Gilbert in Chapter 4 expounds on tuners and amplifiers. Chapter 5 is written by Michael Mayer of the BBC's Engineering Information Department. It's entitled The Broadcast Signal and the title really speaks for itself. Chapter 6, by Pat Hawker is called Commercial Radio and includes a useful question and answer section.

Chapter 8 is on tape recorders for the home and car. Chapter 9 on purchase and care of records and tapes and Chapter 10 describes the ins and outs of 4-channel sound. Chapter 11 helps the reader decide which system to use and how to get value-for-money and Chapter 12 explains how your audio unit is manufactured.

The final chapter helps you decide where to place your audio set-up in your home, and the end of the book contains a useful little glossary of audio terms.

There's only one strange thing in this work that I spotted and that is where a beautiful colour picture of a vintage Thorens phonograph is shown. There is a disc on the turntable but the caption tells us that the machine had a cabinet with facilities for storing the playing cylinders—strange!

Well, Messrs Pye, you are to be congratulated on producing a very well written, well illustrated book which I know will be of great interest and help to many people who are thinking about or are just entering the world of audio.

With the price of 95p, this book just cannot go wrong and I thoroughly recommend it. Excellent value.—Colin Riches

**The Pye Book of Audio**  
Published by Pye Limited, Cambridge. Produced by Daily Mirror Books, 79 Camden Road, NW1 9NT  
124 pages, 12 x 8 1/2 in. Price 95p.

WHEN I first heard about the Pye Book of Audio, I thought "Oh no, another advertising gimmick," but how wrong I was.

This book is a profusely illustrated guide to audio in general and is aimed at the beginner and possibly first-time buyer rather than the man with all the gear already installed in his Hi-Fi den.

The contents are divided into thirteen chapters and there is a foreword written by Benny Green the musician. Chapter 1, The Original Sound, by Tom Stephenson describes what goes on at the recording studio and explains how a record is made.

Fully guaranteed Individually packed VALVES				TRANSISTORS, DIODES etc.												ColomOR ALL valves guaranteed			
A1065 1.25	ECH81 30p	GY501 70p	PL509 1.20	AC 113	AF 139	BSY 27	OA 202	OC 200	2N 3053	6L7G 40p	14N7 80p	2051 80p							
AR8 50p	ECH83 45p	GZ34 65p	PL502 95p	AC 126	AF 178	BSY 38	OAZ 200	OC 206	2N 3054	6Q7G 45p	19A05 50p	5933 23.00							
ATP4 50p	ECH84 45p	GZ37 1.00	PL503 85p	AC 127	AF 186	BSY 95A	OC 22	OC 22	2N 3055	68A7 45p	19G3 28.00	6057 80p							
B12H 28.00	ECL80 50p	KT66 22.50	PL504 1.00	AC 128	AF 212	BYZ 16	OC 25	OC 26	2N 3390	68ATGT 30p	19G6 28.00	6060 60p							
CY31 50p	ECL82 35p	KT88 22.90	PL505 1.00	AC 176	ASY 26	CRS 1/10	OC 26	OC 26	2N 3391	68CTGT 30p	19H4 27.00	6064 50p							
DAF96 50p	ECL83 70p	MM4 75p	PL506 1.00	AC 178	ASY 27	CRS 1/20	OC 28	OC 28	2N 3730	68G7 45p	20P3 75p	6065 70p							
DF96 50p	ECL86 40p	ML5 80p	PL507 1.00	AC 191	ASY 28	CRS 1/30	OC 28	OC 28	2N 3731	68J7 50p	20P4 1.00	6080 22.20							
DK96 60p	EF36 85p	OA2 40p	PL508 1.00	AC 20	BC 108	CRS 1/40	OC 35	OC 35	2N 3819	68J7GT 30p	25L6GT 30p	6146 22.00							
DL92 40p	EF37A 70p	OA2 40p	PL509 1.20	AC 20	BC 118	CRS 3/10	OC 36	OC 36	2N 4038	68K7 45p	30C15 1.00	9001 30p							
DM70 60p	EF40 62p	PABCS0	PL510 1.00	AC 20	BC 137	CRS 3/40	OC 44	OC 44	2N 4061	68L7GT 45p	30C17 1.00	9002 50p							
DY86/87 35p	EF41 65p	PC800	PL511 1.00	AC 20	BC 148A	CRS 25/25	OC 70	OC 70	2N 4285	68N7GT 30p	30C18 90p	9003 65p							
DY802 35p	EF80 25p	PC97 45p	PL512 1.00	AC 162	BC 172	GET 115	OC 73	OC 73	2N 5295	68Q7 45p	30F5 1.00	9004 30p							
E88CC 70p	EF85 35p	PC88 45p	PL513 1.00	AC 162	BC 172A	GET 116	OC 78	OC 78	2N 5295	68Q7GT 30p	30FL1 80p	9006 30p							
E92CC 65p	EF86 30p	PC88 55p	PL514 1.00	AC 172	BC 172A	GET 116	OC 85	OC 85	2N 5295	68R7 45p	30FL2 80p								
E88CC/01 1.15	EF91 37p	PC189 60p	PL515 1.00	ADZ 12	BC 212A	GEX 46	OC 139	OC 139	2N 5295	68V8GT 50p	30FL12 1.00								
E180CC 65p	EF92 50p	PCF80 40p	PL516 1.00	ADZ 12	BC 212A	GEX 46	OC 139	OC 139	2N 5295	68V8GT 50p	30FL12 1.00								
E182CC 1.25	EF183 30p	PCF82 35p	PL517 1.00	AF 114	BCY 31	NKT 222	OC 140	OC 140	2N 2147	68V8GT 50p	30FL12 1.00								
E182CC 1.25	EF183 30p	PCF84 50p	PL518 1.00	AF 115	BCY 33	OA 5	OC 140	OC 140	2N 2147	68V8GT 50p	30FL12 1.00								
E182CC 1.25	EF183 30p	PCF84 50p	PL519 1.00	AF 116	BCY 33	OA 5	OC 140	OC 140	2N 2147	68V8GT 50p	30FL12 1.00								
E182CC 1.25	EF183 30p	PCF84 50p	PL520 1.00	AF 117	BCY 33	OA 5	OC 140	OC 140	2N 2147	68V8GT 50p	30FL12 1.00								
E182CC 1.25	EF183 30p	PCF84 50p	PL521 1.00	AF 118	BCY 33	OA 5	OC 140	OC 140	2N 2147	68V8GT 50p	30FL12 1.00								
E182CC 1.25	EF183 30p	PCF84 50p	PL522 1.00	AF 119	BCY 33	OA 5	OC 140	OC 140	2N 2147	68V8GT 50p	30FL12 1.00								
E182CC 1.25	EF183 30p	PCF84 50p	PL523 1.00	AF 120	BCY 33	OA 5	OC 140	OC 140	2N 2147	68V8GT 50p	30FL12 1.00								
E182CC 1.25	EF183 30p	PCF84 50p	PL524 1.00	AF 121	BCY 33	OA 5	OC 140	OC 140	2N 2147	68V8GT 50p	30FL12 1.00								
E182CC 1.25	EF183 30p	PCF84 50p	PL525 1.00	AF 122	BCY 33	OA 5	OC 140	OC 140	2N 2147	68V8GT 50p	30FL12 1.00								
E182CC 1.25	EF183 30p	PCF84 50p	PL526 1.00	AF 123	BCY 33	OA 5	OC 140	OC 140	2N 2147	68V8GT 50p	30FL12 1.00								
E182CC 1.25	EF183 30p	PCF84 50p	PL527 1.00	AF 124	BCY 33	OA 5	OC 140	OC 140	2N 2147	68V8GT 50p	30FL12 1.00								
E182CC 1.25	EF183 30p	PCF84 50p	PL528 1.00	AF 125	BCY 33	OA 5	OC 140	OC 140	2N 2147	68V8GT 50p	30FL12 1.00								
E182CC 1.25	EF183 30p	PCF84 50p	PL529 1.00	AF 126	BCY 33	OA 5	OC 140	OC 140	2N 2147	68V8GT 50p	30FL12 1.00								
E182CC 1.25	EF183 30p	PCF84 50p	PL530 1.00	AF 127	BCY 33	OA 5	OC 140	OC 140	2N 2147	68V8GT 50p	30FL12 1.00								
E182CC 1.25	EF183 30p	PCF84 50p	PL531 1.00	AF 127	BCY 33	OA 5	OC 140	OC 140	2N 2147	68V8GT 50p	30FL12 1.00								
E182CC 1.25	EF183 30p	PCF84 50p	PL532 1.00	AF 127	BCY 33	OA 5	OC 140	OC 140	2N 2147	68V8GT 50p	30FL12 1.00								
E182CC 1.25	EF183 30p	PCF84 50p	PL533 1.00	AF 127	BCY 33	OA 5	OC 140	OC 140	2N 2147	68V8GT 50p	30FL12 1.00								
E182CC 1.25	EF183 30p	PCF84 50p	PL534 1.00	AF 127	BCY 33	OA 5	OC 140	OC 140	2N 2147	68V8GT 50p	30FL12 1.00								
E182CC 1.25	EF183 30p	PCF84 50p	PL535 1.00	AF 127	BCY 33	OA 5	OC 140	OC 140	2N 2147	68V8GT 50p	30FL12 1.00								
E182CC 1.25	EF183 30p	PCF84 50p	PL536 1.00	AF 127	BCY 33	OA 5	OC 140	OC 140	2N 2147	68V8GT 50p	30FL12 1.00								
E182CC 1.25	EF183 30p	PCF84 50p	PL537 1.00	AF 127	BCY 33	OA 5	OC 140	OC 140	2N 2147	68V8GT 50p	30FL12 1.00								
E182CC 1.25	EF183 30p	PCF84 50p	PL538 1.00	AF 127	BCY 33	OA 5	OC 140	OC 140	2N 2147	68V8GT 50p	30FL12 1.00								
E182CC 1.25	EF183 30p	PCF84 50p	PL539 1.00	AF 127	BCY 33	OA 5	OC 140	OC 140	2N 2147	68V8GT 50p	30FL12 1.00								
E182CC 1.25	EF183 30p	PCF84 50p	PL540 1.00	AF 127	BCY 33	OA 5	OC 140	OC 140	2N 2147	68V8GT 50p	30FL12 1.00								
E182CC 1.25	EF183 30p	PCF84 50p	PL541 1.00	AF 127	BCY 33	OA 5	OC 140	OC 140	2N 2147	68V8GT 50p	30FL12 1.00								
E182CC 1.25	EF183 30p	PCF84 50p	PL542 1.00	AF 127	BCY 33	OA 5	OC 140	OC 140	2N 2147	68V8GT 50p	30FL12 1.00								
E182CC 1.25	EF183 30p	PCF84 50p	PL543 1.00	AF 127	BCY 33	OA 5	OC 140	OC 140	2N 2147	68V8GT 50p	30FL12 1.00								
E182CC 1.25	EF183 30p	PCF84 50p	PL544 1.00	AF 127	BCY 33	OA 5	OC 140	OC 140	2N 2147	68V8GT 50p	30FL12 1.00								
E182CC 1.25	EF183 30p	PCF84 50p	PL545 1.00	AF 127	BCY 33	OA 5	OC 140	OC 140	2N 2147	68V8GT 50p	30FL12 1.00								
E182CC 1.25	EF183 30p	PCF84 50p	PL546 1.00	AF 127	BCY 33	OA 5	OC 140	OC 140	2N 2147	68V8GT 50p	30FL12 1.00								
E182CC 1.25	EF183 30p	PCF84 50p	PL547 1.00	AF 127	BCY 33	OA 5	OC 140	OC 140	2N 2147	68V8GT 50p	30FL12 1.00								
E182CC 1.25	EF183 30p	PCF84 50p	PL548 1.00	AF 127	BCY 33	OA 5	OC 140	OC 140	2N 2147	68V8GT 50p	30FL12 1.00								
E182CC 1.25	EF183 30p	PCF84 50p	PL549 1.00	AF 127	BCY 33	OA 5	OC 140	OC 140	2N 2147	68V8GT 50p	30FL12 1.00								
E182CC 1.25	EF183 30p	PCF84 50p	PL550 1.00	AF 127	BCY 33	OA 5	OC 140	OC 140	2N 2147	68V8GT 50p	30FL12 1.00								
E182CC 1.25	EF183 30p	PCF84 50p	PL551 1.00	AF 127	BCY 33	OA 5	OC 140	OC 140	2N 2147	68V8GT 50p	30FL12 1.00								
E182CC 1.25	EF183 30p	PCF84 50p	PL552 1.00	AF 127	BCY 33	OA 5	OC 140	OC 140	2N 2147	68V8GT 50p	30FL12 1.00								
E182CC 1.25	EF183 30p	PCF84 50p	PL553 1.00	AF 127	BCY 33	OA 5	OC 140	OC 140	2N 2147	68V8GT 50p	30FL12 1.00								
E182CC 1.25	EF183 30p	PCF84 50p	PL554 1.00	AF 127	BCY 33	OA 5	OC 140	OC 140	2N 2147	68V8GT 50p	30FL12 1.00								
E182CC 1.25	EF183 30p	PCF84 50p	PL555 1.00	AF 127	BCY 33	OA 5	OC 140	OC 140	2N 2147	68V8GT 50p	30FL12 1.00								
E182CC 1.25	EF183 30p	PCF84 50p	PL556 1.00	AF 127	BCY 33	OA 5	OC 140	OC 140	2N 2147	68V8GT 50p	30FL12 1.00								
E182CC 1.25	EF183 30p	PCF84 50p	PL557 1.00	AF 127	BCY 33	OA 5	OC 140	OC 140	2N 2147	68V8GT 50p	30FL12 1.00								
E182CC 1.25	EF183 30p	PCF84 50p	PL558 1.00	AF 127	BCY 33	OA 5	OC 140	OC 140	2N 2147	68V8GT 50p	30FL12 1.00								
E182CC 1.25	EF183 30p	PCF84 50p	PL559 1.00	AF 127	BCY 33	OA 5	OC 140	OC 140	2N 2147	68V8GT 50p	30FL12 1.00								
E182CC 1.25	EF183 30p	PCF84 50p	PL560 1.00	AF 127	BCY 33	OA 5	OC 140	OC 140	2N 2147	68V8GT 50p	30FL12 1.00								
E182CC																			

# TWO NEW ADDITIONS TO FANE 'POP' RANGE LOUDSPEAKERS

## POP 40 10" 40 Watt

Impedance  
8-15 ohms  
Gauss 14,000  
Voice Coil  
Diam. 1 1/4 in  
Fitted  
Tweeter Cone  
Range  
50-15,000 Hz

Rec. Retail Price  
inc. VAT

**£10.95**



Also for those who can  
afford the very best  
For Instrument Reproduction

## CRESCENDO '12' B

Two Super Sensitive Models  
Ideal for Lead Guitar etc.  
12" 75 Watt 2" Pole Diam. Gauss 20,000

## CRESCENDO '15'

15" 100 Watt 2" Pole Diam. Gauss 20,000



Rec.  
Retail  
Price

CRESCENDO '12'  
**£39.95**

Rec.  
Retail  
Price

CRESCENDO '15'  
**£48.83**

There is also a 12" Crescendo  
Speaker for General Purpose  
Public Address, and a 12" and 15"  
for Bass Guitar etc.

Please send S.A.E. for leaflet on  
'POP' or 'CRESCENDO' Range Speakers

## POP 55 12" 60 Watt

Impedance  
8-15 ohms  
Gauss 15,000  
Voice Coil  
Diam. 2in

Range  
50-9,000 Hz  
AN ALL PURPOSE  
UNIT OF HIGH  
SENSITIVITY  
Rec. Retail Price  
inc. VAT

**£15.95**



Brief details of other 'POP' Speakers  
Rec. Retail

POP '15' 12" 15 Watt **£5.95**

1" Voice Coil inc. VAT

POP '25/2' 12" 30 Watt **£8.99**

2" Voice Coil inc. VAT

POP '50' 12" 50 Watt **£12.99**

2" Voice Coil inc. VAT

POP '60' 15" 60 Watt **£16.95**

2" Voice Coil inc. VAT

POP '100' 18" 100 Watt **£29.70**

3" Voice Coil inc. VAT

## HIGH FREQUENCY HORN UNITS

MODEL 910


Rating 25 to  
50 Watts  
according to  
filter capacity

**£15.95**

inc. VAT

MODEL 920 Rating with recommended  
filter 100 watts

**£39.95** inc. VAT

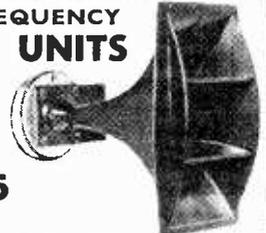

Distributors to Wholesale and Retail Traders—LINEAR PRODUCTS LTD., ELECTRON WORKS, ARMLEY, LEEDS.  
Manufacturers enquiries to—FANE ACOUSTICS LTD., 286 BRADFORD ROAD BATLEY, YORKS  
Prices shown correct at May 14, 1974

# TRAMPUS

## MONEY BACK IF NOT SATISFIED

All brand new, full spec. Top grade.

FREE fabulous NEW catalogue. Send S.A.E.



Red + data. 1/8" pin source LED's 17p; T11 209 and clip 22p  
BIG 1/2" panel clip and RED LED 28p. GREEN and clip 59p.  
INFRA RED LED £1. IC photo amp 44p and amp/switch 85p.

DIGITAL DISPLAY. LEO 1/3" 0-9 DP. DIL. £1.69. Minitor type 0-9 DP DIL  
£1.19. SOCKETS 13p. Calculator batt/mains from £19.

CHIPS. Texas etc. with 4 displays £12.6 displays  
and chip £14. Mostek data and alarm chips with 6 displays £19. pcb £1.49.  
KIT: All parts and case. National chip. 4 digit £20. 6 x £23.  
GAS sensor TGS 308 £2. KIT £4.69. Fully built £8.

With data INTEGRATED CIRCUITS 741: 8 pin 29p, to 99 and 14 pin 27p,  
748 33p, 709 21p, 710 35p, 723 59p, 555 timer 79p. ZN414 rx. £1.10. 703 rf if 28p,  
mc 1310 and led £2.78. mc 1339 £1.20. TAD 100 and if £2

1 AMP + REGULATOR 7805, 5 (4 & 7-20) V. also 12 & 15V £1.49.  
AUDIO AMPS: mc 4000 50p; 1 and 2W £1.19; 3W £1.29

74N TTL low prices



Gates 7400, etc. 16p, 7413 32p, 7447 £1.25, 7470/72 32p, 7474/76 39p, 7490 63p,  
7492 69p, 74121 49p and all others in cat.  
NEW 16 pin counter/driver 9047 £2.25. DALO p.c.b. PEN 69p.  
DIL SOCKETS: Professional/gold P. Pins hi or lo Profile 8, 14, 16 Pin 13p.  
2N3955 33p four £1. BC107, BC108, BC109 all 9p each.  
IN814 3p, ZENERS BZY88 9p, 1A RECTS 50V 33p, 400V 5p, BRIDGE 28p,  
FETS: 2N3819 19p, 2N3823E 20p, 4416E 25p, BC182/3/4 10p, BC212/3/4 11p,  
BCY70 13p, BD131/2 35p ea. BF51/2/3 15p, T1S43 35p, 2N2328 Oy 7p, 2N3053 15p,  
2N3072/3/4/5/6/7/8/9/10/11 all 9p ea. 2N3904/6 14p. HEATSINKS 51/TO5, 181/TO18  
5p. TO3: 4YL 29p. TV3 14p

CAPACITORS: 25V 10, 50, 100 uf 5p. DISCS 4p. PRESETS 5p. CARBON-  
PTS 11p. Switch + 11p. Dual 35p. ULTRASONIC TRANSDUCERS £2 ea.  
FLUORESCENT LIGHTS. 8W 13" 12 VOLT £2.59.

**Trampus**  
**electronics**

ADD 10% VAT TO PRICES.

P. & P. 10p CWO.

58/60 GROVE RD., WINDSOR, BERKS.

## FERRIC CHLORIDE

Anhydrous to Mil-spec In 1lb sealed  
packs. 1lb 55p (20p); 3lb £1.32 (30p);  
10lb £3.85 (60p).

## VERSATILE POWER UNIT

Contains mains transformer, 2A  
thermal cut-out and bridge rect. Will  
give 1.7-10.5V output with 2 extra  
capacitors. Brand new, only 83p (20p).  
Also available in a toy garage with  
press switch, lamp, etc. (Used for  
'Hot Wheels'). Only £1.65 (30p).

## AMPLIFIER UNIT

In fully screened case 5 1/2 x 5 x 3 1/2"  
2 GET116 on heat sink, 2 zeners, 3 pot  
cores, 4 small transformers, 1 1/2 R's,  
C's, etc. 70p (30p).

## 3W CASED AMPLIFIER

Polished wooden cabinet 14 x 13 x 9",  
containing a sensitive (20µV) 4 valve  
amplifier with tone & volume controls.  
Gives 3 watts output to the 7 x 4" 3Ω  
speaker. Also a non-standard tape  
deck. Supplied in good working  
condition with circuit. Standard mains  
operation. £3.50 (£1). Suitable cas-  
sette £1.10 (30p). Spare head 33p.  
Tape (ex-computer) 75p (20p). Amplifier  
chassis only, complete and tested  
(2 x ECC83, EL84, EZ80) + speaker  
£2.50 (40p).

## 71B BARGAIN PARCELS

Hundreds of new components—resistors,  
capacitors, pots, switches, +  
PC boards with transistors & diodes,  
also crystals and loads of odds and  
ends. Amazing value £1.82 (40p).

Scopes in stock for callers, ring for  
details. SAE List. All prices include  
VAT. Carriage in brackets, small  
parts 5p.

## DEKATRON UNITS

Contain 2 CV2271 dekatrons, 2 4-digit  
resettable counters, 2 sealed relays,  
2 x ECC81, R's, C's, etc. Only £1.78  
(30p).

## COMPUTER PANELS

3lbs asstd £1.10 (30p); 7lb £2.20 (40p);  
56lb £12 (£2). 12 high quality panels  
with IC's, power transistors, trim pots  
etc. £2.20 (30p), 100 £13 (£1). Panel  
with 72k trim pots 33p (10p). Pack  
containing 50 14pin DIL IC's, inc. 7400,  
04, 10, 20, 30 7474 etc, also MC types  
£2.20 (20p).

## COMPONENT PACKS

500 asstd resistors £1.10 (20p), 2500  
£2.50p 10000 £13 (£1), 100000 £89 +  
carr. 150 poly, ceramic, mica caps  
60p (10p).

## NEW COMPONENTS

400V 5A SCR 66p, 200V 44p, OC71 8p,  
14 for £1.10, OC81D 8p, 100/£5.50,  
741C TO99 35p, 2N3055 38p, .05/500V  
discs 100/£1.65, 1000pF disc £1.65/100  
80+80+20µF 350V 10p, 10/83p 30p,  
8µF 2500V £2.20 (50p), 4 pole 8-way  
Yaxley switches 33p (8p), 2 pin DIN  
plug 18p, 5 pin 180° 11p, 3-5mm plug  
8p, phone 50p, 7 pin DIN plug 11p, 6 pin  
DIN plug 11p, speaker cable 5p/metre  
4 core individually screened 20p/  
metre.

Transformers, mains PRI, SEC 16-  
0.16V @ 1A+9V tap £1.65 (30p);  
360V @ 375 mA, 280V @ 75mA, 6-3V  
@ 1A, 6-3V @ 4A £2.20 (65p). P.O. 4  
Digit Counters 2500Ω 50V 53p (12p)  
2µF 600V block paper 33p (10p)  
G150/2 Thyratrons ex-equip 33p 6 x 4"  
4Ω New Speakers £1.10p (20p).  
Hewlett-Packard 100MHz counter/  
timer 524D £86+carr.

## GREENWELD ELECTRONICS (PW4)

51 SHIRLEY PARK ROAD, SOUTHAMPTON

New wholesale/retail shop and mail order dept. Other retail shops at  
21 Depiford Bdy, SE8 & 38 Lower Addiscombe Rd, Croydon.

**R T V C**

**FOR AUDIO  
ON A BUDGET**

# PUSH BUTTON CAR RADIO KIT



## The Tourist II

**NO SOLDERING  
REQUIRED!**

### NOW BUILD YOUR OWN PUSH BUTTON CAR RADIO

Easy to assemble construction kit comprising fully completed and tested printed circuit board on which no soldering is required. All connections are simple push fit type making for easy assembly. Fine tuning push button mechanism is fully built and tested to mate with printed circuit board.

Technical specification:

- (1) Output 4 watts R.M.S. output. For 12 volt operation on negative or positive earth.
- (2) Integrated circuit output stage, pre-built three stage IF Module.

Controls volume manual tuning and five push buttons for station selection, illuminated tuning scale covering full, medium and long wave bands. Size chassis 7" wide, 2" high and 4 $\frac{5}{8}$ " deep approx

**Car Radio Kit £7.70 + 55p post. & pack.**  
**Speaker** including baffle and fixing strip  
**£1.65 + 23p postage & packing**  
**Car Aerial** Recommended - fully retractable and locking  
**£1.35 post paid**

## STEREO 21



## QUALITY SOUND<sup>(\*)</sup> FOR LESS THAN £19.00

Stereo 21 easy to assemble audio system kit, - no soldering required. Includes:-  
**BSR 3 speed deck**, automatic, manual facilities together with ceramic cartridge.  
**Two speakers** with cabinets.  
**Amplifier module**. Ready built with control panel, speaker leads and full, easy to follow assembly instructions.


For the technically minded:-

### Specifications:

Input sensitivity 600mV; Aux. input sensitivity 120mV; Power output 2.7 watts per channel; Output impedance 8-15 ohms. Stereo headphone socket with automatic speaker cutout. Provision for auxiliary inputs - radio, tape, etc., and outputs for taping discs. **Overall Dimensions**. Speakers approx. 15 $\frac{1}{2}$ " x 8" x 4". Complete deck and cover in closed position approx. 15 $\frac{1}{2}$ " x 12" x 6". Complete only **£18.95**
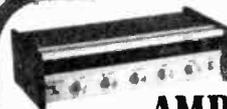
### Extras if required.

Optional Diamond Stylus **£1.37** + £1.60 p & p.  
 Specially selected pair of stereo headphones with individual level controls and padded earpieces to give optimum performance. **£3.85.**



## DISCO AMPLIFIER

Reliant Mk IV Mono Amplifier, ideal for the small disco or house parties.  
**Outputs** 20 watts R.M.S. into 8 ohms (suitable for 15 ohms).


**Inputs** \*4 Electrically Mixed Inputs \*3 Individual Mixing controls. \*Separate bass and treble controls common to all 4 inputs \*Mixer employing F.E.T. (Field Effect Transistors). \*Solid State Circuitry. \*Attractive Styling.

### INPUT SENSITIVITIES

-Input-1.) Crystal mic, guitar or moving coil mic, 2, and 10 mV. (selector switch for desired sensitivity.-Inputs-2), 3), 4, Medium output equipment-ceramic cartridge, tuner, tape recorder, organs etc.  
 - all 250mV sensitivity.  
 AC Mains 240V. operation.

Size approx. 12 $\frac{1}{2}$  ins x 6 ins x 3 $\frac{1}{2}$  ins  
**£15.00 + 60p. post & pack**

## DISCO 50

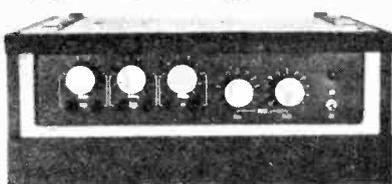

### 45 WATT R.M.S. MONO DISCOTHEQUE AMPLIFIER

Ideal for Disco Work. Output Power: 45 watts R.M.S. Frequency Response 3dB points 30Hz and 18KHz. Total Distortion: less than 2% at rated output. Signal to noise ratio: better than 60dB. Bass Control Range: 13dB at 60Hz. Treble Control Range: 12dB at 10KHz. Inputs: 4 inputs at 5mV into 470K. Each pair of inputs controlled by separate volume control. 2 inputs at 200mV into 470K. Size: 19 $\frac{1}{4}$  x 10 $\frac{1}{2}$  x 8 ins. approx. Amplifier **£27.50 + £1.50 p. & p.**

**Special Offer:** Disco 50 plus two 15" E.M.I. speakers type 14A/780 (as illustrated on opposite page). Complete **£57.00 + £4.00 p & p.**

# COMPLETE (\*) STEREO SYSTEM



**£51.00**

**40 Watt Amplifier.**  
Viscount III - R102 now 20 watts per channel. System I includes,  
**Viscount III amplifier** - volume, bass, treble and balance controls, plus switches for mono/ stereo on/off function and bass and treble filters. Plus headphone socket.  
**Specification**  
20 watts per channel into 8 ohms.  
Total distortion @ 10W @ 1kHz 0-1%. *P.U.1* (for ceramic cartridges) 150mV into 3 Meg. *P.U.2* (for magnetic cartridges) 4mV @ 1kHz into 47K. equalised within  $\pm 1$ dB R.I.A.A. *Radio* 150mV into 220K. (Sensitivities given at full power).  
Tape out facilities: headphone socket, power out 250mW per channel. *Tone controls and filter characteristics:* Bass: +12dB to -17dB @ 60Hz. Bass filter: 6dB per octave cut. Treble control: treble +12dB to -12dB @ 15kHz. Treble filter: 12dB per octave. *Signal to noise ratio:* (all controls at max.) -58dB.  
Crosstalk better than 35dB on all inputs. Overload characteristics better than 26dB on all inputs. Size approx. 13 $\frac{1}{2}$ " x 9" x 3 $\frac{1}{2}$ "  
**Garrard SP25 deck**, with magnetic cartridge, de luxe plinth and hinged cover.  
**Two Duo Type II matched speakers** - Enclosure size approx. 17 $\frac{1}{2}$ " x 10 $\frac{1}{2}$ " x 6" / in simulated teak. Drive unit 13" x 8" with parasitic tweeter 10 watts handling

**Complete System £51.00**

**£69.00**

**System II**  
Viscount III amplifier (As System I)  
Garrard SP. 25 (As System I)  
**Two Duo Type IIIA matched speakers** - Enclosure size approx. 31" x 13" x 11 $\frac{1}{2}$ ". Finished in teak veneer. Drive units approx. 13 $\frac{1}{2}$ " x 8 $\frac{1}{2}$ " with 3 $\frac{1}{4}$ " HF speaker. Max. power 20 watts. 8 ohms. Freq. range 20Hz to 20kHz.  
**Complete System £69.00**

**PRICES: SYSTEM 1**  
Viscount III R102 amplifier £24.20 + £1 p & p  
2 Duo Type II speakers £14.00 + £2.20 p & p  
Garrard SP25 with MAG. cartridge de luxe plinth and hinged cover \* £21.00 + £1.75 p & p.  
total £59.20

**Available complete for only £51.00 + £3.50 p. & p.**


**PRICES: SYSTEM 2**  
Viscount R102 amplifier £24.20 + £1.00 p. & p.  
2 Duo Type IIIA speakers £39.00 + £4.00 p. & p.  
Garrard SP25 with MAG cartridge de luxe plinth £21.00 + £1.75 p. & p. and hinged cover  
total £84.20

**Available complete for only £69.00 + £4 p. & p.**

# EMI SPEAKERS AT FANTASTIC REDUCTIONS


## THE ULTIMATE COMPLETE SPEAKER SYSTEM EMI LE 315

List Price £86.00

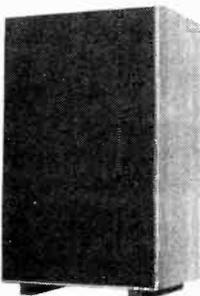

A professional standard five way speaker system with enclosure giving top quality performance  
**Enclosure Dimensions**  
approx. (3ft. x 2ft. x 1ft.).  
**Drive Units**  
Hand built - 15" diameter bass with 3" voice coil, - two 5" diameter Mid Range units, - two 3 $\frac{1}{2}$ " HF. units, plus matching crossover panel with two variable potentiometers for mid and high frequency adjustment.  
**Power Handling**  
Continuous rating 35 W rms., Peak power rating 70 W.  
**Frequency Response**  
20 Hz 20,000 Hz. Imp. 8 ohms.


**Our price £45.00 + £3.50 p. & p.**

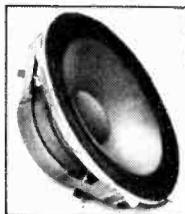
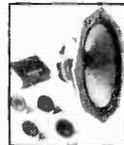
## 15" 14A/780 BASS UNIT

Bass unit on a rigid diecast chassis. Superior cone material handles up to 50 watts RMS, and is treated to give a smooth frequency response. Resonance 30 Hz. flux density 360,000 Maxwells. Impedance at 1 kHz is 8 ohms. 3" voice coil.


**Recommended retail price £40.80.**  
**OUR PRICE £18.70 + £1.50 p & p + £1.50 p & p Special Offer.**



## 950 KIT

Five matched speakers and crossover unit for handling up to 45 watts, frequency response from 20 to 20,000 Hz.  
Huge 19" x 14" (approx.) high efficiency Bass-Speaker with 16,500-gauss magnet built on a heavy diecast frame.  
The four 10,000 gauss tweeters, each 3 $\frac{1}{4}$ " dia. approx., are fed by the crossover which critically adjusts signal for maximum fidelity. Impedance at 1 kHz is 8 ohms.  
Bass coil 2", others 0.5". Recommended list price £44.00.

**OUR PRICE £19.50**

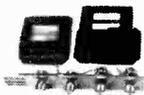

## BUILD YOUR OWN STEREO AMPLIFIER (\*)

For the man who wants to design his own stereo - here's your chance to start, with Unisound - pre-amp, power amplifier and control panel. No soldering - just simply screw together. 4 watts per channel into 8 ohms. Inputs: 120mV (for ceramic cartridge). The heart of Unisound is high efficiency I.C. monolithic power chips which ensure very low distortion over the audio spectrum.  
240V. AC only.

**£7.64 + 55p. p & p**



## 8 TRACK CARTRIDGE PLAYER (\*)

Elegant self selector push button player for use with your stereo system. Compatible with Viscount III system, Unisound module and the Stereo 21.  
Technical specification Mains input, 240V, Output sensitivity 125mV  
Comparable unit sold elsewhere at £24.00 approx.

**Yours for only £10.95 + 90p. p & p**



Just write your order giving your credit card number

**DO NOT SEND  
YOUR CARD**

● Mail orders to Acton. Terms C.W.O.  
All enquires Stamped Addressed Envelope.  
Goods not despatched outside U.K.

● Leaflets available for all items listed thus (\*)  
Send stamped addressed envelope.



Radio and TV Components (Acton) Ltd.

**21 High Street, Acton, London W3 6NG /c**  
**323 Edgware Road, London W2**

Personal — Edgware Road: 9a.m.—5.30p.m. Half day Thurs.  
Shoppers — Acton: 9.30 a.m.—5 p.m. Closed all day Wed.

**G. F. MILWARD, 369 Alum Rock Road, Birmingham B8 3DR. Tel. 021-327 2339**

**12 VOLT FLUORESCENT LIGHTING**



**INVERTER TRANSFORMERS 13/15 WATT 70p**  
**(CIRCUIT INCLUDED)**  
**"CURRENT ECONOMY" TRANSISTOR (600 ma.) 50p**  
**"MAXIMUM LIGHT" TRANSISTOR (1-3A) 50p**  
**RESISTORS/CAPACITORS TO SUIT 15p**  
**LAMP HOLDERS (LONG LEAD) 30p PAIR**  
**(SHORT LEAD) 20p PAIR**  
**WHITE ENAMEL CASE, 18" or 21" 70p**  
**TUBE, 18"-15 WATT or 21"-13 WATT 45p**  
**(NOTE:- TUBE ONLY SUPPLIED IF CASE ORDERED, TO PREVENT POSTAL DAMAGE)**  
**13 WATT FITTING READY BUILT AND TESTED—INCLUDING TUBE £3.75**  
**POST/PACKING 20p PER ORDER**

**ALL GOODS PLUS 10% V.A.T.**

SILICON P.N.P.			
Type	Voltage	Frequency	Price
BCY 71	45	200 MHz	12p
BFS 92	100	70 MHz	28p
BFS 95	40	70 MHz	17p
BFX 12	25	210 MHz	10p
2N 2906	60	200 MHz	18p
2N 3702	40	100 MHz	11p
2N 3703	50	100 MHz	12p

SILICON N.P.N.			
Type	Voltage	Frequency	Price
BC 108	30	150 MHz	15p
BC 109	30	150 MHz	15p
BF 179	225	125 MHz	48p
BF 180	30	925 MHz	25p
BFW 58	80	80 MHz	18p
BFX 43	30	500 MHz	28p
BFX 86	40	50 MHz	17p
BFY 53	30	50 MHz	16p
2N 709	15	900 MHz	38p
2N 718	60	80 MHz	12p
2N 753	25	250 MHz	12p
2N 744	20	300 MHz	12p
2N 1813	75	50 MHz	17p
2N 2220	60	250 MHz	18p

SILICON N.P.N.			
Type	Voltage	Frequency	Price
2N 3035	60	100 MHz	17p
2N 3707	30		12p
2N 5179	20	900 MHz	40p

GERMANIUM P.N.P.			
Type	Voltage	Frequency	Price
ACY 44	50	1 MHz	10p
ADY 28	80	75 watts	£1
AF 124	20	75 MHz	28p
AFY 19	32	350 MHz	20p
ASY 32	25	5 MHz	10p
ASZ 21	15	450 MHz	28p
GET 113	32		10p
GET 120	32	2 watts	10p
OC 123	50	1 MHz	28p
OC P 70		Light-sensitive	10p
2N 1307	30	10 MHz	15p
2N 1309	30	15 MHz	15p
2N 448	60	150 watts	£1

**MICROWAVE DEVICES**

Type	Price	Frequency	Price
CL 8300	£40	9-4 GHz	£40
CL 8370	£10	9-5 GHz	£10
CL 8380	£10	10-5 GHz	£10
CL 8390	£10	11-3 GHz	£10
CL 8430	£40	9-35 GHz	£40
CL 8450	£40	9-35 GHz	£40
CL 8490	£10	9-35 GHz	£40
BXY 27	£1	70 GHz	£1
BXY 28	£1	100 GHz	£1
BXY 32	£1	150 GHz	£1
BXY 35A/C	£1	25 GHz	£1
BXY 36C/D	£1	75 GHz	£1
BXY 37C/D	£1	100 GHz	£1
BXY 38C/E	£1	120 GHz	£1
BXY 39C/D	£1	150 GHz	£1
BXY 40D/E	£1	180 GHz	£1
BXY 41C/D/E	£1	200 GHz	£1

**£1 100 ±1 WATT RESISTORS**  
**100 CERAMIC CAPACITORS**  
**100 DIODES**

POSTAGE 23p

**£1 1 VERO-BOARD CUTTER**  
**5 1/2 in. x 1 in. x 15 BOARDS**  
**50 SQ. INS. "ODD PIECES" VERO**

POSTAGE 23p

**£1 20 ASSORTED UNUSED MARKED TESTED TRANSISTORS**  
**BC108 ETC.**

POSTAGE 23p

**£1 1 COMPUTER PANELS CONTAINING MASSES OF DIODES, TRANSISTORS, INDUCTORS, RESISTORS & CAPACITORS**

POSTAGE 23p

**£1 100 RESISTORS**  
**100 CERAMIC CAPACITORS**  
**100 POLYETHYLENE CAPACITORS**

POSTAGE 23p

**£1 100 RESISTORS**  
**100 CERAMIC CAPACITORS**  
**50 MULLARD POLYESTER CAPACITORS**

POSTAGE 23p

**£1 1 TRANSISTORISED SIGNAL TRACER KIT**  
**1 TRANSISTORISED SIGNAL INJECTOR KIT**

POSTAGE 23p

**£1 100 RESISTORS**  
**100 CAPACITORS (ASSORTED TYPES)**

POSTAGE 23p

**SUPERSOUND 13 HI-FI MONO AMPLIFIER**

A superb solid state audio amplifier. Brand new components throughout. 5 silicon transistors plus 2 power output transistors in push-pull. Full wave rectification. Output approx. 13 watts r.m.s. into 8 ohm. Frequency response 12Hz-30KHz ± 3dB. Fully integrated pre-amplifier stage with separate Volume, Bass boost and Treble cut controls. Suitable for 8-15 ohm speakers. Input for ceramic or crystal cartridge. Sensitivity approx. 40mV for full output. Supplied ready built and tested, with knobs, escutcheon panel, input and output plugs. Overall size 3" high x 6" wide x 7 1/4" deep. AC 200/250V. PRICE £12.00. P. & P. 50p.

**DE LUXE STEREO AMPLIFIER**

A.C. mains 200-240 V. Using heavy duty fully isolated mains transformer with full wave rectification giving adequate smoothing with negligible hum. Valve line up:- 2 x ECL86 Triode Pentodes. 1 x EZ80 as rectifier. Two dual potentiometers are provided for bass and treble control, giving bass and treble boost and cut. A dual volume control is used. Balance of the left and right hand channels can be adjusted by means of a separate 'Balance' control fitted at the rear of the chassis. Input sensitivity is approximately 300mV for full peak output of 4 watts per channel (8 watts mono), into 3 ohm speakers. Full negative feedback in a carefully calculated circuit, allows high volume levels to be used with negligible distortion. Supplied complete with knobs, chassis size 11" w x 4" d. Overall height including valves 8". Ready built & tested to a high standard. PRICE £10.40. P.&P. 50p.

**LOUDSPEAKER BARGAINS**

5in 3 ohm £1.25. P. & P. 15p 7 x 4in 3 ohm £1.40 P. & P. 20p. 10 x 6in 3 or 15 ohm £3.10. P. & P. 30p. E.M.I. 8 x 6in 3 ohm with high flux magnet £1.70. P. & P. 20p. E.M.I. 13 1/2 x 8in with high flux ceramic magnet with parasitic tweeter 3, 8 or 15 ohm £3.50 P. & P. 30p. E.M.I. 13 x 8in, 3 or 8 or 15 ohm with two inbuilt tweeters and crossover network £4.65. P. & P. 30p. EMI CERAMIC MAGNET HEAVY DUTY TWEETER. approx. 3 1/2 in. Av. 3 or 8 or 15 ohms. £1.25 plus 20p p. & P. BRAND NEW. 12in 15W H/D Speakers, 3, 8 or 15 ohm. (state which). Current production by well-known British maker. Now with HiFlux ceramic ferrobar magnet assembly £9.90. (uitar models: 25w £9.90. 35w £11.00. P. & P. 45p each.

**PRICES INCLUDE VAT**

**SPECIAL OFFER ! HI-FI LOUSPEAKER SYSTEMS**

Beautifully made task finish enclosure with most attractive Tygan-Vynair front. Size 16" high x 10 1/2" wide x 6" deep. Fitted with E.M.I. Ceramic Magnet 13" x 8" base unit, two H.F. tweeter units and crossover. Maximum power handling 10 watts. Available 3 or 8 or 15 ohms impedance. **OUR PRICE £9.25** Carr. 75p Cabinet Available Separately £4.95, Carr. 65p. Also available in 8 ohms with EMI 13" x 8" base speaker with parasitic tweeter £7.15, Carr. 75p.

**3-VALVE AUDIO AMPLIFIER HA34 MK II**

Designed for Hi-Fi reproduction of records. A.C. Mains operation. Ready built on plated heavy gauge metal chassis, size 7 1/2" w. x 4" d. x 4 1/2" h. Incorporates ECC83, EL84, EZ80 valves. Heavy duty, double wound mains transformer and output transformer matched for 3 ohm speaker. Separate volume control and now with improved wide range tone controls giving bass and treble lift and cut. Negative feedback line. Output 4 1/2 watts. Front panel can be detached and leads extended for remote mounting of controls. Complete with knobs, valves, etc., wired and tested for only £6.00. P. & P. 45p.

**HEL "FOUR" AMPLIFIER KIT.** Similar in appearance to HA34 above but employs entirely different and advanced circuitry. Complete set of parts, etc. £5.00. P. & P. 45p.

**LIMITED BARGAIN OFFER!** Special number of BSR C123 Auto Changer De Luxe with lightweight tubular arm and stereo cartridge. Brand new. ONLY £8.00 + p. & p. 80p.

**BATTERY OPERATED MEGA CIRCUIT TESTER**

made by Evershed and Vignoles Ltd., Measures from 0-1 ohm to 200,000 ohms in 2 switched ranges. Used but in perfect condition. Complete with test probes, Leather carrying case and 4 1/2 volt standard battery. Only £7.00 + 40p p & p.

**HARVERSONIC SUPER SOUND 10 + 10 STEREO AMPLIFIER KIT**

**NEW FURTHER IMPROVED MODEL WITH HIGHER OUTPUT AND INCORPORATING HIGH QUALITY BEAD DRILLED PRINTED CIRCUIT BOARD WITH COMPONENT IDENTIFICATION CLEARLY MARKED FOR EVEN EASIER CONSTRUCTION**

A really first-class Hi-Fi Stereo Amplifier Kit. Uses 14 transistors including Silicon Transistors in the first five stages on each channel resulting in even lower noise level with improved sensitivity. Integrated pre-amp with Bass, Treble and two Volume Controls. Suitable for use with Ceramic or Crystal cartridges. Very simple to modify to suit magnetic cartridge—instructions included. Output stage for any speakers from 5 to 15 ohms. Compact design, all parts supplied including drilled metal work, high quality ready drilled printed circuit board, smart brushed anodised aluminium front panel with matching knobs, wire, solder, nuts, bolts—no extras to buy. Simple step by step instructions enable any constructor to build an amplifier to be proud of. Brief specification: Power output: 14 watts r.m.s. per channel into 8 ohms. Frequency response ± 3dB 12-30,000 Hz Sensitivity: better than 80mV into 1M Ohm. Full power bandwidth: ± 3dB 12-15,000 Hz. Bass boost approx. to ± 12dB. Treble cut approx. to -16dB. Negative feedback 18dB over main amp. Power requirements 35v. at 1.0 amp. Overall Size 12" w. x 8" d. x 2 1/2" h. £8.60 P. & P. 50p. Fully detailed 7 page construction manual and parts list free with kit or send 18p plus large S.A.E.

**AMPLIFIER KIT** £11.55 P. & P. 25p (Magnetic input components 33p extra)  
**POWER PACK KIT** £8.60 P. & P. 35p  
**CABINET** £8.60 P. & P. 50p (Post Free if all units purchased at same time)

Also available ready built and tested £25.10. Post Free. Note: The above amplifier is suitable for feeding two mono sources into inputs (e.g. mtkr, radio, twin record decks, etc.) and will then provide mixing and fading facilities for medium powered Hi-Fi Discoteque use, etc.

**SPECIAL OFFER**

LIMITED NUMBER OF BRAND NEW ELAC 10" TWIN CONE LOUSPEAKERS. With large ceramic magnet and plasticised cone surround. 8 ohm impedance. £8.70. P. & P. 35p.

Open 9.30-5.30 Monday to Friday. 9.30-5 Saturday. Closed Wednesday. A few minutes from South Wimbledon Tube Station.

**HARVERSON SURPLUS CO. LTD.**

(Dept. P.W.) 170 HIGH ST., MERTON, LONDON, S.W.19 Tel.: 01-540 3985

SEND STAMPED ADDRESSED ENVELOPE WITH ALL ENQUIRIES

(Please write clearly) PLEASE NOTE: P. & P. CHARGES QUOTED APPLY TO U.K. ONLY. P. & P. ON OVERSEAS ORDERS CHARGED EXTRA.



**SWR METER Model SWR3**  
Handy SWR meter for transmitting or antenna alignment, with built-in field strength meter. Accuracy 5%, impedance 50Ω indicator 1000A DC. Full scale 5 section collapsible antenna. Size 145 x 50 x 60mm.  
**OUR PRICE £4.25** P&P 30p

**AT201 Decade ATTENUATOR**  
Frequency range 0-2000Hz. Attenuator 0-111dB. 0.1dB steps. Impedance 600 ohms. Input power maximum 30dBm. Size: 180 x 80 x 55mm.  
**OUR PRICE £12.50** P&P 50p

**TRANSISTORISED L.C.R. A.C. BR/8 MEASURING BRIDGE**  
A new portable bridge offering excellent range and accuracy at low cost. Resistance: 0.1 ohms-111 megohms ± 1% Inductance: 6 ranges: 1 microhenry-111 henries ± 2% Capacity: 6 ranges: 10pF-1110 mfd ± 2% Turns Ratio: 6 ranges: 1:1/1000-1:11100 ± 1% Bridge Voltage at 1,000cps. Operated from 8-volt battery. 100 micro-ohm meter indication. Size 7 1/2" x 6" x 2"  
**OUR PRICE £25.00** P&P 30p

**TE16A TRANSISTORISED SIGNAL GENERATOR**  
6 ranges, 400kHz to 40 MHz. An inexpensive instrument for the handy-man. Operates on 9V battery. Wide easy to read scale, 800kHz modulation. Size: 148 x 148 x 92mm. Complete with instructions and leads.  
**OUR PRICE £8.97** P&P 30p

**MODEL TE20 RF SIGNAL GENERATOR**  
Six bands, 120kHz-250MHz. Dual output RF terminals. Separate variable audio output. Accuracy ± 2%. Audio output to 6V. Power requirements: 105-125V, 220-240V A.C. Size: 193 x 286 x 150mm. Complete with test leads etc.  
**OUR PRICE £17.50** P&P 50p

**TE-200 RF SIGNAL GENERATOR**  
Accurate wide range signal generator covering 120 kHz-500 MHz on 8 bands. Directly calibrated. Variable RF, transmitter audio output, Xtal socket for calibration. 220/240V a.c. Brand new with instructions. Size 140mm x 215mm x 170mm.  
**OUR PRICE £17.50** P&P 50p

**TE22 SINE SQUARE WAVE AUDIO GENERATOR**  
Sine 20cps to 2000Hz on 4 bands. Squares 20 cps to 30 kHz. Output impedance 5000 Ohms. 220/240V A.C. operation. Supplied brand new guaranteed, with instruction manual and leads.  
**OUR PRICE £24.95** P&P 50p

**ARF 300 AF/RF SIGNAL GENERATOR**  
All transistorised compact fully portable. AF sine-wave 18Hz to 220 kHz. AF square wave 18Hz to 100kHz. Output Squares/Sine wave 10V. P.P RF 100kHz to 200MHz. Output 1V maximum. 220/240V AC operation. Complete with instructions and leads.  
**OUR PRICE £37.50** P&P 50p

**MODEL MG100 SINE SQUARE WAVE AUDIO GENERATOR**  
Range 19-220,000Hz Sine Wave 19-100,000 Hz Square Wave. Size 180 x 90 x 90mm. Operation 220/240V. A.C.  
**OUR PRICE £19.95** P&P 50p

**PS200 Regulated POWER SUPPLY UNIT**  
Solid state. Variable output 5-20V DC up to 2 Amp. Independent meters to monitor voltage and current. Output 220/240V A.C. Size: 190 x 136 x 96mm.  
**OUR PRICE £19.95** P&P 50p

**POWER RHEOSTATS**  
High quality ceramic construction. Windings embedded in vitreous enamel. Heavy duty brush vane. Continuous rating. Wide range available ex-stock. Single hole fixing. "X" diameter shafts. Both quantities available.  
**25 WATT** 10/25/50/100/500/1000/2500 ohms. **£1.15** P&P 10p  
**50 WATT** 10/50/100/250/500/1500/5000 ohms. **£1.62** P&P 10p  
**100 WATT** 1/5/10/25/50/250/500/2500 ohms. 100 Ohms. **£2.34** P&P 15p

**YAMABISHI VARIABLE VOLTAGE TRANSFORMERS**  
Excellent quality at low cost. Input: 230V 50/60Hz. Output 0-250V.  
**MODEL S260 BENCH MOUNTING**  
P&P  
1A £10.50 50p  
2.5A £12.00 50p  
5A £17.50 50p  
8A £30.35 £1.00  
10A £33.75 £1.00  
12A £35.40 £1.00  
20A £85.00 £1.50  
25A £95.00 £1.50  
40A £120.00 £1.50  
**MODEL S260B PANEL MOUNTING**  
1A £10.00 50p  
2.5A £12.00 50p

**240° Wide Angle 1mA METERS**  
MW 1-6 60x60mm  
**£6.50** P&P 15p

**CP110 CHASSIS PUNCH SET**  
Carefully machined top grade steel. Contains 1/2", 5/8", 3/4", 1" and 1 1/8" punches complete with gripper and accessories.  
**OUR PRICE £3.00** P&P 40p

**HITACHI FLUORESCENT LANTERN LI91D**  
A portable battery operated lantern ideal for home, motoring, camping etc. Approx. 10" tall. Provides brilliant light from 9 1.5v batteries (not supplied).  
**OUR PRICE £7.19** P&P 50p

**KE630 3 Station INTERCOM**  
Master and two sub-stations. Can be used on desk or wall mounted. Complete with cable and batteries.  
**OUR PRICE £5.25** P&P 50p

**SINCLAIR IC12 INTEGRATED CIRCUIT AMPLIFIER**  
Complete with printed circuit mounting board.  
**OUR PRICE £2.35** P & P 15p

**DT55G DIGITAL CLOCK MECHANISM**  
Features 24 hour alarm setting, on/off, alarm and auto alarm 'sleep' switch. Illuminated oral dial with hours, minutes and seconds. Automatically turns off radio, TV, light etc. and with auto-switching will turn on again when required. 240V AC operation. Switch rating 250V-3 Amp.  
**OUR PRICE £5.95** P&P 30p

**SUMMER SALE AN EXTRA 10% OFF ALL THESE PRICES**

**LH025 STEREO HEADPHONES**  
Light weight headphones with padded ear pieces, 4/16 ohms 20-20,000Hz. Complete with 6' lead and plug.  
**OUR PRICE £1.97** P&P 30p

**DH025 STEREO HEADPHONES**  
Wonderful value and excellent performance combined. Adjustable headband. Impedance 8 ohms. 20-12,000Hz. Complete with lead and plug.  
**OUR PRICE £2.25** P&P 30p

**TE1035 Stereo HEADPHONES**  
Low cost with excellent response. Foam rubber earcups. Adjustable headband. 8 ohms impedance. Frequency response 25Hz-18kHz. Complete with cable and stereo jack plug.  
**OUR PRICE £2.50** P&P 30p

**SH00V MONO/STEREO HEADPHONES**  
Volume control for each channel. 4/16 ohms impedance. Frequency response 20Hz-18kHz. Complete with 10ft. coiled lead and jack plug.  
**OUR PRICE £4.97** P&P 30p

**BH001 HEADSET and Boom Microphone**  
Moving coil. Ideal for language teaching, communications etc. Headphone impedance 16 ohms. Microphone impedance 200 ohms.  
**OUR PRICE £5.95** P&P 30p

**EMI LOUDSPEAKERS**  
Model 350 13 x 8" with twin tweeter/crossover. 20-20,000Hz. 15 watts RMS. Available 8 or 15 ohms.  
**OUR PRICE £7.50** each P&P 37p  
Model 450 13 x 8" with twin tweeter/crossover. 55-13,000Hz. 8 watts RMS. Available 8 or 15 ohms  
**OUR PRICE £3.62** each P&P 35p

**SPECIAL PURCHASE LIMITED QUANTITY! Tannoy 12" DR/8**  
Bass Speakers 8 ohms 30 watt. Heavy duty, ideal for Hi-Fi. P.A. Group.  
**OUR PRICE £12.50** P&P 50p.

**SPECIAL BARGAIN! FERGUSON 3406 HI-FI SPEAKERS**  
High quality 2 way speaker systems 25 Watts. 4-8 ohms. 40Hz-18kHz. Size: 560 x 340 x 255mm. approx. Wood grain finish with black fronts.  
**OUR PRICE £26.95** PR, P&P £1

**SPECIAL BARGAIN!! STEREOSOUND SPEAKERS**  
Matched pair of stereo bookshelf speakers. Deluxe task veneered finish. Size: 365 x 229 x 190mm. 8 ohms. 8 watts RMS, 16 watts peak. Complete with Din lead.  
**OUR PRICE £12.95** P&P 50p

**FM TUNER CHASSIS**  
6 transistor high quality tuner. Size only 153 x 101 x 63mm 3 1/2 stages. Double tuned discriminator. Ample output to feed most amplifiers. Operates on 9V battery. Covers 88-108MHz. Ready built, ready for use. Fantastic value for money.  
**OUR PRICE £8.95** P&P 20p  
Stereo Multiplex Adaptor £5.95 extra

**Model A1018 FM TUNER**  
6 transistor high quality unit-3 1/2 stages and double tuned discriminator. For use with most amplifiers. Covers 88-108MHz. Powered by 9V battery.  
**OUR PRICE £13.50** P&P 30p  
Stereo multiplex adaptor £6.95 extra.

**SINCLAIR "SCIENTIFIC" CALCULATOR**  
8 digit display. Four functions plus logarithms to base 10, antilog, sine, cosine, tangent, arcsine, arcCosine and arcTangent. Complete with instructions, case and batteries. Rec. Price £49.00  
**OUR PRICE £44.50** P & P 25p plus VAT.

**SINCLAIR SYSTEM 2000 STEREO AMPLIFIER AND TUNER**

**AMPLIFIER**  
Amplifier output 8 watts per channel RMS. Distortion less than 0.06%. Silicon transistors. Two pick-up plus radio and tape inputs. tape output and scratch filter. Excellent Value.  
**OUR PRICE £28.50** P & P 60p.

**FM TUNER**  
Excellent selectivity and sensitivity. Twin dual-varicap tuning. 4 pole ceramic filter. 19 transistor stereo demodulator giving 40 dB separation. Distortion 0.2% output. Fantastic Value.  
**OUR PRICE £28.50** P & P 60p.

**SINCLAIR Project 80 Modules**  
Z40 Power Amp. £5.45 P & P 15p  
Z60 Power Amp. £6.95 P & P 15p  
Stereo 80 Pre-Amp. £11.95 P & P 15p  
Active Filter Unit. £6.95 P & P 15p  
Project 80S. £26.95 P & P 50p  
P25 Power Supply. £4.98 P & P 30p  
P26 Power Supply. £7.98 P & P 30p  
P28 Power Supply. £7.98 P & P 30p  
Transformer for P28. £4.05 P & P 50p  
**SINCLAIR Project 80 Packages**  
2 x Z40/Stereo 80/P25. £25.00  
2 x Z40/Stereo 80/P26. £27.75  
2 x Z60/Stereo 80/P28. £30.45  
POST & PACKING 35p each.

**AUDIOTRONIC AHA101 Stereo Headphone Amplifier**  
All silicon, transistor amplifier operates from magnetic, ceramic or transformer inputs with twin stereo headphone outputs and separate volume controls for each channel. Operates from 9V battery. INPUTS: 5mV and 100mV. OUTPUT: 50mV per channel.  
**OUR PRICE £8.50** P&P 30p

**JUSTY KIT HIGH QUALITY CONSTRUCTION KITS**  
WE ARE APPOINTED STOCKISTS AT ALL BRANCHES

All kits are complete with comprehensive easy to follow instructions and covered by full guarantee.

Post and Packing 15p per kit.

AF20 Mono amplifier.....	£4.80
AF25 Mono amplifier.....	£3.80
AF30 Mono pre-amplifier.....	£2.61
AF35 Emitter amplifier.....	£2.27
AF80 0.5W mic. amplifier.....	£4.22
AF305 Intercom.....	£9.52
AF310/2 Mono Amplifier.....	£7.56
AT5 Automatic light control.....	£2.58
AT25 Window wiper robot.....	£5.82
AT30 Photo cell switch unit.....	£5.70
AT50 400W triac light dimmer/speed control.....	£4.80
AT68 2,200W triac light dimmer/speed control.....	£6.90
AT60 1 channel light control.....	£7.80
AT65 3 channel light control.....	£14.56
GP304 Circuit board.....	£2.87
GP310 Stereo pre-amplifier for use with 2 x AF310.....	£21.27
GP312 Circuit board.....	£11.45
GU330 Tremolo unit.....	£7.50
HF61 Diode detector.....	£3.32
HF65 FM transmitter.....	£2.70
HF75 FM receiver.....	£2.87
HF310 FM tuner.....	£15.81
HF325 Deluxe FM tuner.....	£24.12
HF330 Decoder (HF310/325).....	£9.98
HF335 Frasher headlamp amplifier.....	£4.94
HF395 broadband aerial amp.....	£1.77
LF380 Quadraphonic device.....	£11.36
M180 Multi-vibrator.....	£1.71
M191 VU meter.....	£4.55
M192 Stereo balance meter.....	£4.97
M1302 Transistor tester.....	£8.45
NT10 Stabilised power supply 100mA 9V.....	£6.15
NT300 Stabilised p. supply.....	£12.51
NT305 Voltage converter.....	£4.60
NT315 Power supply 240V AC to 5V/12V DC, 500mA.....	£9.57

**Amateur Electronics by Justy-Kit**, the professional book for the amateur - covers the subject from basic principals to advanced electronic techniques. Complete with circuit board for AE1 to AE10 listed below.

**OUR PRICE £3.30** (No VAT) P&P 25p plus VAT.

AE1 100mW output stage.....	£1.50
AE2 Pre-amplifier.....	£1.18
AE3 Diode receiver.....	£1.32
AE4 100mW output stage.....	95p
AE5 Astable multi-vibrator.....	95p
AE6 Monostable multi-vibrator.....	93p
AE7 RC generator.....	97p
AE8 VU meter.....	90p
AE9 Traps filter.....	90p
AE10 OCIR filter.....	90p

**1021 Stereo Listening Station**  
For balancing and gain selection of loudspeakers with additional facility for stereo headphone switching. Two gain controls, speakers on-off slide switch, stereo headphone socket.  
**OUR PRICE £2.25** P&P 15p

**AUDIOTRONIC LOW NOISE CASSETTES**

TYPE	10	25
C60	£1.57	£3.00 £7.08
C90	£2.24	£4.25 £10.00
C120	£2.73	£5.17 £12.24

**AUDIOTRONIC CR02 CASSETTES**

TYPE	10	25
CR90	£3.92	£7.72 £19.12
CR95	£5.32	£10.46 £25.22

**AUDIOTRONIC 8 TRACK CARTRIDGES**

TYPE	Each	5	10
40M	85p	£4.00	£7.50
80M	£1.15	£5.40	£10.25

P&P Cartridges 5p each OVER 10 or other POST FREE!

**MP7 MIXER-PREAMPLIFIER**  
5 Microphone inputs each with individual gain controls enabling complete mixing facilities. Battery operated. Size: 235 x 127 x 78mm. Input Mic. 3 x 3mV 50k; 2 x 3mV 600 ohms. Phono. Meg. 4mV 50k; Phono Ceramic 100mV/V. Output 250mV 100p.  
**OUR PRICE £9.97** P&P 20p

**EA41 REVERBERATION AMPLIFIER**  
Self contained, transistorised, battery operated. Simply plug in microphone, guitar etc. and output to your amplifier. Volume control and depth of reverberation control. Resonant cabinet. 184 x 77 x 106mm.  
**OUR PRICE £7.50** P&P 30p

**ALL PRICES EXCLUDE VAT**

Also see previous page



# CLEAR PLASTIC PANEL METERS

USED EXTENSIVELY BY INDUSTRY, GOVERNMENT DEPARTMENTS, EDUCATIONAL AUTHORITIES ETC.

Over 200 ranges in stock—other ranges to order. Quantity discounts available. Send for fully illustrated brochure.

### CLEAR PLASTIC MODEL SD640

Size: 85 x 64mm

50uA .....	£3.80
100uA .....	£3.75
200uA .....	£3.70
500uA .....	£3.65
50-0-50uA .....	£3.75
100-0-100uA .....	£3.70
1mA .....	£3.85
5mA .....	£3.85
10mA .....	£3.85
50mA .....	£3.85
100mA .....	£3.85
500mA .....	£3.85
1A DC .....	£3.85
5A DC .....	£3.85
10A DC .....	£3.85
5V DC .....	£3.85



\*Items with asterisk are Moving Iron type, all others are Moving Coil

### CLEAR PLASTIC MODEL SD830

Size: 110 x 83mm

50uA .....	£4.30
100uA .....	£4.25
200uA .....	£4.20
500uA .....	£4.15
50-0-50uA .....	£4.25
100-0-100uA .....	£4.20
1mA .....	£4.10
5mA .....	£4.10
10mA .....	£4.10
50mA .....	£4.10
100mA .....	£4.10
500mA .....	£4.10
1A DC .....	£4.10
5A DC .....	£4.10
10A DC .....	£4.10
5V DC .....	£4.10



### CLEAR PLASTIC MODEL MR 65P

Size: 86 x 78mm

50uA .....	£3.95
100uA .....	£3.85
200uA .....	£3.80
500uA .....	£3.75
50-0-50uA .....	£3.85
100-0-100uA .....	£3.80
500-0-500uA .....	£3.70
1mA .....	£3.70
1-0-1mA .....	£3.70
5mA .....	£3.70
10mA .....	£3.70
50mA .....	£3.70
100mA .....	£3.70
500mA .....	£3.70
1A DC .....	£3.70
5A DC .....	£3.70
10A DC .....	£3.70
5V DC .....	£3.70



### CLEAR PLASTIC MODEL SW100

Size: 100 x 80mm

50uA .....	£4.80
100uA .....	£4.80
500uA .....	£4.30
50-0-50uA .....	£4.80
100-0-100uA .....	£4.45
1mA .....	£4.30
1A DC .....	£4.30
5A DC .....	£4.30
20V DC .....	£4.30
50V DC .....	£4.30
300V DC .....	£4.30



### CLEAR PLASTIC MODEL MR 45P

Size: 50 x 50mm

50uA .....	£3.20
100uA .....	£3.15
200uA .....	£3.10
500uA .....	£3.00
50-0-50uA .....	£3.15
100-0-100uA .....	£3.10
500-0-500uA .....	£2.95
1mA .....	£2.95
5mA .....	£2.95
10mA .....	£2.95
50mA .....	£2.95
100mA .....	£2.95
500mA .....	£2.95
1A DC .....	£2.95
5A DC .....	£2.95
10V DC .....	£2.95
20V DC .....	£2.95
50V DC .....	£2.95
300V DC .....	£2.95
15V AC .....	£3.05



### BAKELITE MODEL S80 Enlarged Window

Size: 80 x 80mm

50uA .....	£4.50
100uA .....	£4.45
500uA .....	£4.20
50-0-50uA .....	£4.45
100-0-100uA .....	£4.40
1mA .....	£4.20
5mA .....	£4.20
10mA .....	£4.20
50mA .....	£4.20
100mA .....	£4.20
500mA .....	£4.20
1A DC .....	£4.20
5A DC .....	£4.20
10V DC .....	£4.20
20V DC .....	£4.20
50V DC .....	£4.20
300V DC .....	£4.20
15V AC .....	£4.30
VU Meter .....	£4.70



### EDGWISE MODEL PE70

Size: 90 x 34mm

50uA .....	£4.15
100uA .....	£4.10
200uA .....	£4.05
500uA .....	£3.90
50-0-50uA .....	£4.10
100-0-100uA .....	£3.95
1mA .....	£3.85
300V AC .....	£3.95
VU Meter .....	£4.30



### MODEL ED107 EDUCATIONAL METER

Size: 100 x 90 x 150mm including terminals

A range of high quality moving coil instruments ideal for school experiments and other bench applications. 3" mirror scale. The meter movement is easily accessible to demonstrate internal working.



50uA .....	£8.50
100uA .....	£7.90
50-0-50uA .....	£7.90
1mA .....	£7.80
1-0-1mA .....	£7.80
5A DC .....	£7.80
5V DC .....	£7.80
10V DC .....	£7.80
15V DC .....	£7.80

### CLEAR PLASTIC MODEL MR 38P

Size: 42 x 42mm

50uA .....	£3.10
100uA .....	£3.05
200uA .....	£3.00
500uA .....	£2.85
50-0-50uA .....	£3.05
100-0-100uA .....	£3.00
500-0-500uA .....	£2.80
1mA .....	£2.80
1-0-1mA .....	£2.80
2mA .....	£2.80
5mA .....	£2.80
10mA .....	£2.80
20mA .....	£2.80
50mA .....	£2.80
100mA .....	£2.80
500mA .....	£2.80
1A DC .....	£2.80
5A DC .....	£2.80
10V DC .....	£2.80
20V DC .....	£2.80
50V DC .....	£2.80
100V DC .....	£2.80
300V DC .....	£2.80
15V AC .....	£2.80



### CLEAR PLASTIC MODEL MR 52P

Size: 60 x 60mm

50uA .....	£3.70
100uA .....	£3.50
500uA .....	£3.35
50-0-50uA .....	£3.50
100-0-100uA .....	£3.35
1mA .....	£3.30
5mA .....	£3.30
10mA .....	£3.30
50mA .....	£3.30
100mA .....	£3.30
500mA .....	£3.30
1A DC .....	£3.30
5A DC .....	£3.30
10V DC .....	£3.30
20V DC .....	£3.30
50V DC .....	£3.30
300V DC .....	£3.30
15V AC .....	£3.40
30V AC .....	£3.40



### CLEAR PLASTIC MODEL MR 85P

Size: 120 x 110mm

50uA .....	£5.45
100uA .....	£5.40
200uA .....	£5.35
500uA .....	£5.25
50-0-50uA .....	£5.40
100-0-100uA .....	£5.35
500-0-500uA .....	£5.20
1mA .....	£5.20
1-0-1mA .....	£5.20
5mA .....	£5.20
10mA .....	£5.20
50mA .....	£5.20
100mA .....	£5.20
500mA .....	£5.20
1A DC .....	£5.20
5A DC .....	£5.20
10A DC .....	£5.20
20V DC .....	£5.20
50V DC .....	£5.20
150V DC .....	£5.20



### CLEAR PLASTIC MODEL SD460

Size: 59 x 46mm

50uA .....	£3.50
100uA .....	£3.45
200uA .....	£3.40
500uA .....	£3.35
50-0-50uA .....	£3.45
100-0-100uA .....	£3.40
1mA .....	£3.30
5mA .....	£3.30
10mA .....	£3.30
50mA .....	£3.30
100mA .....	£3.30
500mA .....	£3.30
1A DC .....	£3.30
5A DC .....	£3.30
10A DC .....	£3.30
5V DC .....	£3.30



### BAKELITE MODEL MR 65 Size 80 x 80mm

25uA .....	£5.25
50uA .....	£4.00
100uA .....	£3.95
500uA .....	£3.95
50-0-50uA .....	£3.95
100-0-100uA .....	£3.90
500-0-500uA .....	£3.80
1mA .....	£3.80
1-0-1mA .....	£3.80
5mA .....	£3.80
10mA .....	£3.80
50mA .....	£3.80
100mA .....	£3.80
500mA .....	£3.80
1A DC .....	£3.80
5A DC .....	£3.80
10V DC .....	£3.80
20V DC .....	£3.80
50V DC .....	£3.80
300V DC .....	£3.80
15V AC .....	£3.80
30V AC .....	£3.80



### CENTRAL LONDON

481 OXFORD ST. 01-493 8641  
 10 TOTENHAM CT. RD. 01-637 2232  
 27 TOTENHAM CT. RD. 01-636 3715  
 33 TOTENHAM CT. RD. 01-636 2605  
 42/45 TOTENHAM CT. RD. 01-580 0845  
 87 TOTENHAM CT. RD. 01-580 3739  
 257/8 TOTENHAM CT. RD. 01-580 0670  
 3 LITTLE ST. WC2 01-437 8204  
 34 LITTLE ST. WC2 01-437 9155  
 118 EDGWARE RD. W2 01-723 9789  
 193 EDGWARE RD. W2 01-723 6211  
 207 EDGWARE RD. W2 01-723 3271  
 311 EDGWARE RD. W2 01-262 0387  
 346 EDGWARE RD. W2 01-723 4453  
 382 EDGWARE RD. W2 01-723 4194  
 109 FLEET ST. EC4 01-353 5812  
 152/3 FLEET ST. EC4 01-353 2833

### ESSEX

86 SOUTH ST. ROMFORD 70-20218

### KENT

53/57 CANNEN RD., TUNBRIDGE WELLS 0892-23242

### LEICESTERSHIRE

45 MARKET PLACE, LEICESTER 0533-537678

### SURREY

1046 WHITGIFT CENTRE, CROYDON 01-881 3027  
 27 EDEN ST. KINGSTON 01-546 7845  
 32 HILL ST. RICHMOND 01-948 1441

### WARWICKSHIRE

116 CORPORATION ST., BIRMINGHAM 021-236 3503

ALL BRANCHES OPEN FROM 9am to 6pm MON. TO SAT.

### BARCLAYCARD & ACCESS

Holders welcome call into any branch or telephone your order to head office. CREDIT TERMS available for Personal Shoppers

### EXPORT

Personal reports arranged for overseas visitors. Goods, specially packed, insured and despatched to all parts of the world at minimum cost exclusive of VAT. Payment by bank transfer, certified cheque, postal order or money order in any currency.

CHEQUES TO THE VALUE OF £30 ACCEPTED FROM PERSONAL SHOPPERS WITH BANKERS CARD. IN OTHER CASES AND FOR AMOUNTS IN EXCESS OF £30, PLEASE ALLOW TIME FOR CLEARANCE. BANKERS DRAFTS ACCEPTED.

All prices correct at 13/6/74 but subject to change

## ALL PRICES EXCLUDE VAT



Yes, Laskys are reducing all prices including Hi Fi during the month of July by 10% subject to the items being currently in stock. Excluding Quad, Armstrong and Technics.

A member of the Audiotronic Group of Companies

FREE HI-FI PRICE LIST

ASK LASKYS

about Hi fi

TO LASKYS AUDIOTRONIC HOUSE, THE HYDE LONDON NW9 6JJ

Please send me a copy of the latest price list

NAME \_\_\_\_\_

ADDRESS \_\_\_\_\_

PW8

FOR MAIL ORDER

We offer a speedy and efficient service by mail order. Remember to add 10% VAT to total value of goods including post and packing.

TO LASKYS HEAD OFFICE AND MAIL ORDER DEPARTMENT  
 Audiotronic House, The Hyde, London NW9 6JJ Tel: 01-205 5651/3735

Please send me the following items

enclose cheque postal order money order

I wish to pay by Barclaycard/Access and my number is \_\_\_\_\_

Signature \_\_\_\_\_

Registered in England No. 347947 at 12 Lower Grosvenor Place London SW10 9EX PW8

# YATES ELECTRONICS

(FLITWICK) LTD.

DEPT PW, ELSTOW STORAGE DEPOT  
KEMPSTON HARDWICK  
BEDFORD

C.W.O. PLEASE. POST AND PACKING  
PLEASE ADD 10p TO ORDERS UNDER £2.

Catalogue which contains data sheets for most of the  
components listed will be sent free on request.  
10p stamp appreciated.

Callers Welcome Mon. to Sat. 9 a.m.-5 p.m.

**PLEASE ADD 10% VAT**

## RESISTORS

±W Iskra high stability carbon film—very low noise—capless construction.  
±W Mullard CR25 carbon film—very small body size 7.5 x 2.5 mm.  
±W 2% ELECTROSIL TRS.

Power watts	Tolerance	Range	Values available	1-99	Price	100+
1/4	5%	4.7Ω-2.2MΩ	E24	1-3p	1-1p	1-1p
1/2	10%	3.3MΩ-10MΩ	E12	1-3p	1-1p	1-1p
1	2%	10Ω-1MΩ	E24	3-5p	3p	3p
2	10%	1Ω-3.9Ω	E12	1-3p	1-1p	1-1p
4	5%	4.7Ω-1MΩ	E12	1-3p	1-1p	1-1p
4	10%	1Ω-10Ω	E12	8p	7p	7p

Quantity price applies for any selection. Ignore fractions on total order.

## DEVELOPMENT PACK

0.5 watt 5% Iskra resistors 5 off each value 4.7Ω to 1MΩ.  
E12 pack 325 resistors £2.40. E24 pack 650 resistors £4.70.

## POTENTIOMETERS

Carbon track 5kΩ to 2MΩ, log or linear (log ± W, lin ± W).  
Single, 14p. Dual gang (stereo), 49p. Single D.P. switch, 25p.

## SKELETON PRESET POTENTIOMETERS

Linear: 100, 250, 500Ω and decades to 5MΩ. Horizontal or vertical P.C.  
mounting (0.1 matrix).  
Sub-miniature 0.1W, 5p each. Miniature 0.25W, 7p each.

## SMOKE AND COMBUSTIBLE GAS DETECTOR-GDI

The GDI is the world's first semiconductor that can convert a concentration of  
gas or smoke into an electrical signal. The sensor decreases its electrical  
resistance when it absorbs deoxidizing or combustible gases such as hydrogen,  
carbon monoxide, methane, propane, alcohol, North Sea gas, as well as carbon-  
dust containing air or smoke. This decrease is usually large enough to be utilized  
without amplification. Full details and circuits are supplied with each detector.  
excluding case, £5.60. Suitable case £1.50. Kit of parts for 12 or 24V battery  
operation, including GDI and P.C. Board, £7.70. As above for PP9 battery, £6.90.  
NOTE: The battery operated kits incorporate our patented circuit to minimise  
battery drain. Typically 90mA for 24V.

## PRINTED BOARD MARKER

Draw the planned circuit onto a copper laminate board with the P.C. Pen, allow to  
dry, and immerse the board in the etchant. On removal the circuit remains  
in high relief. 97p

## MULLARD POLYESTER CAPACITORS C296 SERIES

400V: 0.001μF, 0.0015μF, 0.0022μF, 0.0033μF, 0.0047μF, 5p. 0.0068μF, 0.01μF, 0.015μF,  
0.022μF, 0.033μF, 3p. 0.047μF, 0.068μF, 0.1μF, 5p. 0.15μF, 6p. 0.22μF, 7p. 0.33μF, 11p.  
0.47μF, 13p.

160V: 0.01μF, 0.015μF, 0.022μF, 0.033μF, 0.047μF, 0.068μF, 3p. 0.1μF, 3p. 0.15μF, 4p.  
0.22μF, 5p. 0.33μF, 6p. 0.47μF, 7p. 0.68μF, 11p. 1.0μF, 13p.

## MULLARD POLYESTER CAPACITORS C280 SERIES

250V P.C. mounting: 0.01μF, 0.015μF, 0.022μF, 0.033μF, 0.047μF, 0.068μF, 3p.  
0.1μF, 4p. 0.15μF, 0.22μF, 5p. 0.33μF, 6p. 0.47μF, 8p. 0.68μF, 11p. 1.0μF, 13p. 1.5μF,  
20p. 2.2μF, 24p.

## MYLAR FILM CAPACITORS 100V

0.001μF, 0.002μF, 0.005μF, 0.01μF, 0.02μF,  
3p. 0.04μF, 0.05μF, 0.068μF, 0.1μF, 4p.

## CERAMIC DISC CAPACITORS

100pF to 10,000pF, 2p each.

## ELECTROLYTIC CAPACITORS

(μF/V) 1/63, 1.5/63, 2.2/63, 3.3/63, 4.7/63, 6.8/40, 6.8/63, 10/25, 10/63, 15/16, 15/40, 15/63,  
22/10, 22/25, 22/63, 33/6.3, 33/16, 33/40, 47/4, 47/10, 47/25, 47/40, 68/6.3, 68/16, 100/4, 100/10,  
100/25, 150/6.3, 150/16, 220/4, 220/6.3, 220/16, 330/4, 6p. 47/63, 100/25, 220/25, 330/10,  
470/6.3, 7p. 68/63, 150/40, 220/40, 330/16, 1000/4, 10p. 470/10, 680/6.3, 11p. 100/63, 150/63,  
220/63, 1000/10, 12p. 470.25, 680/16, 1500/6.3, 13p. 470/40, 680/25, 1000/16, 1500/10, 2200/6.3,  
18p. 330/63, 680/40, 1000/25, 1500/16, 2200/10, 3300/6.3, 4700/4, 21p.

## SOLID TANTALUM BEAD CAPACITORS

0.1μF 35V	2.2μF 35V	22μF 16V	12p
0.22μF 35V	4.7μF 35V	33μF 10V	
0.47μF 35V	6.8μF 25V	47μF 6.3V	
1.0μF 35V	10μF 25V	100μF 3V	

## VEROBOARD

2 1/2 x 3 1/2	0.1	0.15
2 1/2 x 5	24p	20p
3 1/2 x 5	28p	28p
3 1/2 x 5	28p	28p
17 x 2 1/2	32p	32p
17 x 2 1/2	85p	67p
17 x 3 1/2	120p	108p
17 x 3 1/2 (plain)	76p	52p
17 x 2 1/2 (plain)	—	41p
2 1/2 x 5 (plain)	—	11p
2 1/2 x 5 (plain)	—	12p
Pin insertion tool	62p	62p
Spot face cutter	52p	52p
Pkt. 50 pins	20p	20p

## JACK PLUGS AND SOCKETS

Standard screened	28p	2.5mm insulated	12p
Standard insulated	18p	3.5mm insulated	12p
Stereo screened	40p	3.5mm screened	18p
Standard socket	20p	2.5mm socket	11p
Stereo socket	30p	3.5mm socket	11p


## D.I.N. PLUGS AND SOCKETS

2 pin, 3 pin, 5 pin 180, 5 pin 240, 6 pin, 7 pin.  
Plug 12p. Socket 8p.  
4 way screened cable, 25p/metre.  
6 way screened cable, 30p/metre.

## BATTERY ELIMINATOR

£1.70  
9V mains power supply. Same size as PP9 battery.

# Verobox

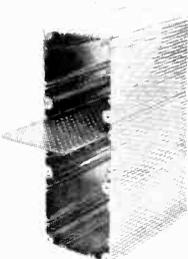

## ALUMINIUM ENCLOSURES

- 6 standard sizes available from your local retailer.
- Made from precision extrusions with integral board guide slots.
- Finned sides improve appearance and radiate heat.
- Parallel sides for ease of component mounting.



VERO ELECTRONICS LTD.

Eastleigh, Hants. SO5 3ZR  
Tel: Chandler's Ford 2952 Telex: 47551

Subsidiaries and Agents  
throughout the World

## BETTER GET 'SET'

### FAMOUS NO. 19 SET TRANS/RECEIVER



TR50/51 2-8 MHz in 2 bands. 11 valve. 807 PA  
Power reqs 12VLT 275-  
VHT REC 500VTM. Rebuilt  
£12.50, Carr. £1.

Complete station 12 VDC PSU. Mic. Cables  
£23.50, Carr. £2.50.

### TR55 VHF 60-90 MHZ XTAL 3C

3 channel 12 valve  
super Het. 12 VDC  
Sync Internal Sup-  
ply, size 14" x 12"  
x 7" as new £16.50  
Carr. £1.25.



TE76/CT52  
A superb Miniature Oscil-  
loscope £25, Carr. £1.50.  
Mains operation.

### RE102 42/MAST

12-3' 6" x 2" sections WIRE  
GUYS STRAINERS in carry  
holdall £23.50 Carr. £2.

### AERIAL RODS

3' x 1" screwed M & F  
ends 10 £2 Post 75p.  
25 £5 c.p.

AE101. Telescopic mast  
antenna £3.75. Carr. £1.25  
List 25p refundable with  
purchase.

### XTAL CALIBRATOR

No. 10  
1/2 10MHZ Harmonics 30 MHZ  
£3 Post 50p.

No. 62 RC/TM 1.5-10MHz £15 Carr. £2.

Add VAT 10% Prices and Carriage


**Surplus Electronic Trading**

P.O. BOX No. 19, HITCHIN, HERTS. SG4 8TN

## MAINS UNITS for all types of TRANSISTOR EQUIPMENT
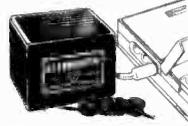
### RUN YOUR TAPE RECORDER OFF AC MAINS

Mains unit supplied  
complete and ready to  
plug into your cas-  
sette recorder. (State  
voltage, make and  
type of plug required.  
If in doubt send dia-  
gram of recorder  
socket).



**ONLY £2.95**

### PLUS-3 MAINS UNIT

Provides three separate  
switched output voltages  
6v., 7 1/2v. and 9v. DC.  
Attractive case mains lead  
output socket, plug and  
lead. Size 4 1/2 x 3 1/2 x 2 1/2 in.

**ONLY £3.50**

Extra lead with plug to fit your cassette recorder  
65p. (State model and plug required.)

### MAINS UNIT FOR TRANSISTOR RADIO ONLY

For single outputs, 6v or 9v £2.40.  
For two separate outputs, 6v + 9v. or  
9v. + 9v. £2.95 per unit. (Please state  
outputs required.)

All units are completely isolated from mains by  
double wound transformer ensuring 100% safety.

ALL PRICES INC VAT & P. & P

R.C.S. PRODUCTS (RADIO) LTD.  
(Dept. P.W.J.)

36 Raymond Ave., South Woodford  
London, E18 2HG

# NELSON-JONES FM TUNER KIT



## VARICAP TUNING

as in 'W.W.' June '73

Now available to readers of 'Practical Wireless'. The Nelson-Jones tuner uses dual gate MOSFET's in the RF stages, integrated circuits and ceramic filters in the IF stages, for very high performance and quick assembly. Do not confuse with tuners using only bipolar transistors and IF coils!

Tuning is accomplished by variable capacitance diodes and a Push Button Unit with 6 positions. AFC disable is incorporated as well as a pointer for each button showing tuning position in the range 87.5-104MHz, i.e. each 'button' is fully tuneable simply by turning.

Our complete metalwork system is supplied with nuts, bolts, board standoffs, push button mains on/off and stereo mute assembly, sockets, fuse and holder. Printed and Anodised Front Panel and Veneered Teak case. Power supply kits are supplied with complete kits of parts, or separately. LED tuning ind. is also supplied.

Prices for complete kits start at **£24.95** + 60p pp. + VAT for mono tuners, (phase locked decoders are also available to fit in the cabinet). Please send large SAE for complete details of special offers and our complete lists.

## NEW LOW COST STEREO TUNER

No alignment required. Mullard LP1186 front end module used with Ceramic IF and IC amplifier. Push button tuning (6 position) with **Interstation Mute**, restricted range **AFC**, single LED tuning indicator, phase locked IC decoder, and complete metalwork and veneered cabinet. Complete with IC regulated PSU and full assembly instructions. (Mechanically identical to N-J Tuner.)

**TYP. SPECIFICATION 2µV for 30dB S/N. Image rejection 40dB. IF rejection 65dB.**

**PRICE:** Complete Mono kit **£22.40** Complete Stereo kit **£26.82** p.p. 60p.

## THE RONDO QUADRAPHONIC SYSTEM (20 WATTS/CHANNEL)

Complete designer approved kits for this outstanding Quadraphonic Sound System ('P.E.' Sep. '73, etc.) with the following features:

- ★ Switching Facilities and Modules for SQ, QS and CD4.
- ★ Individual Kits may be incorporated in existing equipment.
- ★ Complete Loudspeaker systems available.
- ★ Complete Loudspeaker Enclosure design.
- ★ Low cost, fully engineered, integral design.
- ★ Modular built in AM/FM radio.
- ★ Kits available as published.

**INTEGREX LIMITED,** Dept. P.W., P.O. Box 45, Derby, DE1 1TW. Tel. Repton (028389) 3580

## TELEVISION SERVICE ENGINEERS, INSTALLATION ENGINEERS, C.C.T.V. ENGINEERS, AUDIO-VISUAL ENGINEERS AND CABLE INSTALLERS

are urgently required to cope with our rapidly increasing business in hotels, banks and industrial premises in London and the South East. If you are experienced in any of these fields, we will welcome you with open arms.

Salaries start at about £2,000. Fringe benefits include private use of Company estate car, bonus scheme, lunch allowance, pension and life assurance schemes, staff status.

If you are a television enthusiast with sound technical knowledge but without previous experience in the industry, we can probably find a place for you.

## TELEVISION SYSTEMS & RESEARCH LIMITED

Southern Regional Office, Market Road, Richmond, Surrey

Telephone 01-560 3246

# Sinclair Cambridge kit.

Was £27.45.

Now only £14.95!

(INC VAT)

You save £12.50!

## An advanced 4-function calculator in kit form

The Cambridge kit is the world's largest-selling calculator kit.

It's not surprising – no other calculator matches the Sinclair Cambridge in functional value for money; and buying in kit form, you make a substantial saving.

Now, simplified manufacture and continuing demand mean we can reduce even the kit price by a handsome £12.50. For under £15 you get the power to handle complex calculations in a compact, reliable package – plus the interest and entertainment of building it yourself!

## Truly pocket-sized

With all its calculating capability, the Cambridge still measures just  $4\frac{1}{3}'' \times 2'' \times \frac{11}{16}''$ . That means you can carry the Cambridge wherever you go without inconvenience – it fits in your pocket with barely a bulge. It runs on ordinary U16-type batteries which give weeks of normal use before replacement.

## Easy to assemble


All parts are supplied – all you need provide is a soldering iron and a pair of cutters. Complete step-by-step instructions are provided, and our service department will back you throughout if you've any queries or problems.

## Total cost? Just £14.95!

The Sinclair Cambridge kit is supplied to you direct from the manufacturer. Ready assembled, it costs £21.95 – so you're saving £7! Of course we'll be happy to supply you with one ready-assembled if you prefer – it's still far and away the best calculator value on the market.
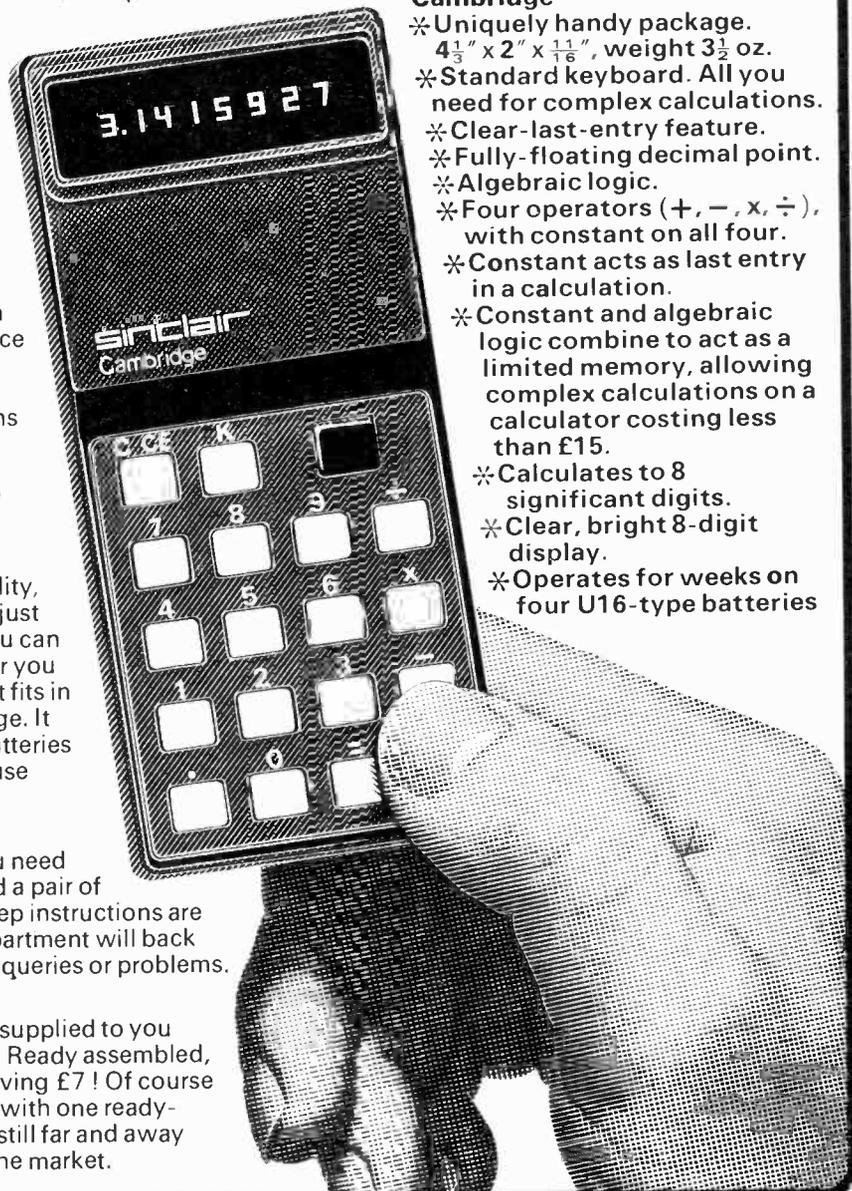
## Features of the Sinclair Cambridge

- \* Uniquely handy package.  $4\frac{1}{3}'' \times 2'' \times \frac{11}{16}''$ , weight  $3\frac{1}{2}$  oz.
- \* Standard keyboard. All you need for complex calculations.
- \* Clear-last-entry feature.
- \* Fully-floating decimal point.
- \* Algebraic logic.
- \* Four operators (+, -, x, ÷), with constant on all four.
- \* Constant acts as last entry in a calculation.
- \* Constant and algebraic logic combine to act as a limited memory, allowing complex calculations on a calculator costing less than £15.
- \* Calculates to 8 significant digits.
- \* Clear, bright 8-digit display.
- \* Operates for weeks on four U16-type batteries




# A complete kit!

The kit comes to you packaged in a heavy-duty polystyrene container. It contains all you need to assemble your Sinclair Cambridge. Assembly time is about 3 hours.

**Contents:**

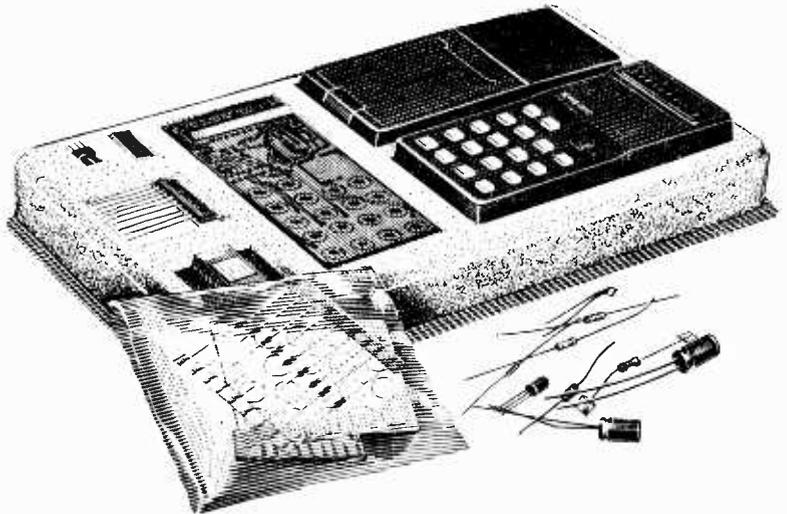1. Coil,
2. Large-scale integrated circuit.
3. Interface chip.
4. Thick-film resistor pack.
5. Case mouldings, with buttons, window and light-up display in position.
6. Printed circuit board.
7. Keyboard panel.
8. Electronic components pack (diodes, resistors, capacitors, transistor).
9. Battery clips and on/off switch.
10. Soft wallet.



**This valuable book – free!**

If you just use your Sinclair Cambridge for routine arithmetic – for shopping, conversions, percentages, accounting, tallying, and so on – then you'll get more than your money's worth.

But if you want to get even more out of it, you can go one step further and learn how to unlock the full potential of this piece of electronic technology.



How? It's all explained in this unique booklet, written by a leading calculator design consultant. In its fact-packed 32 pages it explains, step by step, how you can use the Sinclair Cambridge to carry out complex calculations.

**sinclair**

Sinclair Radionics Ltd, London Road,  
St Ives, Huntingdonshire  
Reg. no: 699483 England  
VAT Reg. no: 213 8170 88

**Why only Sinclair can make you this offer**

The reason's simple: only Sinclair – Europe's largest electronic calculator manufacturer – have the necessary combination of skills and scale.

Sinclair Radionics are the makers of the Executive – the smallest electronic calculator in the world. In spite of being one of the more expensive of the small calculators, it was a runaway best-seller. The experience gained on the Executive has enabled us to design and produce the Cambridge at this remarkably low price. But that in itself wouldn't be enough. Sinclair also have a very long experience of producing and marketing electronic kits. You may have used one, and you've almost certainly heard of them – the Sinclair Project 80 stereo modules.

It seemed only logical to combine the knowledge of do-it-yourself kits with the knowledge of small calculator technology. And *you* benefit!

**Take advantage of this money-back, no-risks offer today**

The Sinclair Cambridge is fully guaranteed. Return your kit within 10 days, and we'll refund your money without question. All parts are tested and checked before despatch – and we guarantee a correctly-assembled calculator for one year. Simply fill in the preferential order form below and slip it in the post today.

**Price in kit form: £13.59 + £1.36 VAT. (Total: £14.95)**  
**Price fully built: £19.95 + £2.00 VAT. (Total: £21.95)**

To: Sinclair Radionics Ltd, London Road,  
St Ives, Huntingdonshire, PE17 4HJ

Name \_\_\_\_\_

Please send me \_\_\_\_\_

a Sinclair Cambridge Calculator kit at  
£13.59 + £1.36 VAT (Total: £14.95)

a Sinclair Cambridge calculator ready  
built at £19.95 + £2.00 VAT  
(Total: £21.95)

Address \_\_\_\_\_

\*I enclose cheque for £ \_\_\_\_\_, made  
out to Sinclair Radionics Ltd, and  
crossed. \_\_\_\_\_

\*Please debit my \*Barclaycard/Access  
account. Account number \_\_\_\_\_

\*Delete as required.

PW 8/74

PLEASE PRINT

# Practical Wireless Classified Advertisements

Classified advertisements 10p per word (minimum 12 words). Box No. 20p. Semi-display setting £8 per single column inch. Advertisements must be prepaid and addressed to Classified Advertisement Manager, PRACTICAL WIRELESS, IPC Magazines Ltd., Fleetway House, Farringdon Street, London EC4A 4AD. All cheques, postal orders, etc., to be made payable to PRACTICAL WIRELESS and crossed "Lloyds Bank Ltd."

## Aerials

**GENUINE FULL SIZE**  
18 element TV aerial  
as used by leading  
TV companies

FOR ONLY  
**£2.20**  
+ 35p carr

ITV, BBC1 & 2B/W & Colour Guaranteed Perfect Pictures. Save £15. We supply this genuine U.H.F. aerial for only £2.20 can be fitted outside or inside. Quality made technically advanced design. Precision grid/reflector eliminates ghosting. Complete with clamp, instructions advice. Money Back Refund. Wall/Caravan Bracket 25p. Low Loss Cable 10p per yard. Plug & FREE with order maps & channel reference of all Radio & TV Transmitters. SEND DIRECT TO DEPT. PW10 219 Mansfield Rd. Nottingham.

**IMPERIAL TRADING (OVERSEAS) LTD.**  
The quality Aerial Specialists

J. and A. Tweedy Limited Incorporating Baines High Frequency Aerials  
All prices include postage and VAT  
Full range of TV, FM and Amateur aerials by J Beam  
Parabeams PBM 12 £3.60 PBM 18 £4.60  
Multibeams MBM 30 £4.70 MBM 46 £7.40 MBM 70 £12.95  
Log Periodic £8.40  
Stereobeams SBM 2 £3.15 SBM 3 £4.70 SBM 4 £5.15  
SBM 6 £7.95  
Aerial Rotators AR30 £27.50 AR 40 £33.00  
Amplifiers Masthead £9.07 Setback £4.50  
We are local stockists of AMTRON KITS and BIB  
Accessories CERTRON CASSETTES and COPAL  
DIGITAL CLOCKS  
79 Chatsworth Road, Chesterfield, S40 2AP  
Telephone 34982-863755 (evenings).

## Educational

### TELEVISION TRAINING

16 MONTHS' full-time practical and theoretical training course in Radio and TV Servicing (Mono and Colour) for beginners.

13 WEEKS' full-time Colour TV Servicing course. Includes 100 hours practical training. Mono revision if necessary. Good electronics background essential.

Next session commences on September 9th.

Prospectus from: London Electronics College, Department A8, 20 Penywern Road, London SW5 9SU. Tel. 01-373 8721.

## C AND E EXAM

Make sure you succeed with an ICS home study course for C and E Electrical Installation Work & Technicians, Radio/TV/Electronics Technicians, Telecomms Technicians and Radio Amateurs.

## COLOUR TV SERVICING

Make the most of the current boom! Learn the techniques of servicing Colour and Mono TV sets through new home study courses, approved by leading manufacturers.

## TECHNICAL TRAINING

Home study courses in Electronics and Electrical Engineering, Maintenance, Radio, TV, Audio, Computer Engineering and Programming. Also self-build radio kits.

Get the qualifications you need to success. Free details from: International Correspondence Schools, Dept 732P, Interlex House, London SW8 4UJ. Or phone 01-622 9911.

**ENGINEERS**—get a technical certificate. Postal courses in Engineering, Electronics, Radio, T.V. Computers, Draughtsmanship, Building, etc. FREE book form: BIET (Dept. BPW.04 Aldermaston Court, Reading, RG7 4PF. Accredited by CACC. Member A.B.C.C.

**GO TO SEA** as a Radio Officer. Write: Principal, Nautical College, Broadwater, Fleetwood FY7 8JZ.

**AMIMI, MAA/LMI DIPLOMA**, City & Guilds, etc. Thousands of passes. For details of postal courses in all branches of Engineering and illustrated book—FREE—BIET (Dept. BPW.03) Aldermaston Court, Reading RG7 4PF. Accredited to CACC. Member A.B.C.C.

## Situations Vacant

**MEN!**  
£70p.w.  
can be yours

Jobs galore! 144,000 new computer personnel needed by 1977. With our revolutionary, direct-from-America, course, you train as a Computer Operator in only 4 weeks! Pay prospects? £3500 + p.a. After training, our exclusive appointments bureau—one of the world's leaders of its kind—introduces you FREE to world-wide opportunities. Write or phone TODAY, without obligation.

London  
Computer Operators  
Training Centre

T69, Oxford House

9-15, Oxford Street, W.1.  
Telephone: 01-734 2874

## For Sale

TV LINE OUTPUT TRANSFORMERS  
Tidman Mail Order Ltd., 236 Sandycroft Rd., Richmond, Surrey, TW9 2EQ. 01-948 3702.

**LIGHTSHOW PROJECTORS** from only £17, effect wheels from only £4. Many lightshow bargains at ROGER SQUIRE'S (Disco Centre), 176 Junction Road, London N19. Tel. 01-272 7474.

**SEEN MY CAT?** 5,000 items. Mechanical & Electrical Gear, and materials. S.A.E. K. R. WHISTON, Dept. PW, NEW MILLS, Stockport.

**SOUND TO LIGHT CONVERTORS** 3-channel, 1.5 kW £18, 3 kW £25, single channel £9; Sequencer £95; Strobes from £19; Projectors from £24; etc. Call or mail Aarvak Electronics, 12A Bruce Grove, London N17 6RA. 01-808 9096.

**NEWNES RADIO, TELEVISION** Servicing 10 Volumes 1956-67. Perfect. £3-10 each. £30 Set. King, 975 Middleton Road, Chadderton, Oldham, Lancs.

**VALVES.** Large stocks 1930 to 1974. Many obsolete types. S.A.E. for quotation. List 10p. Cox Radio, The Parade, East Wittering, Sussex. West Wittering 2023.

**NORMENDE GLOBETRAILER III** Superb Allwave Band Battery/Mains Portable. 11 S.W. Bands, Micro Tuning, M.F., L.F., Marine, V.H.F. Own Aerials. Very good condition. £40. Harpenden 64463.

**MICROPHONES:** AKG D109, £12.65; AKG D202EI, £43.45; AKG D190C, £18.70; AKG D190E, £20; AKG D224 £55; Sennheiser MD211N, £49.50; Sennheiser MD413N, £29.70. All brand new and boxed. Send CWO to J. J. Francis, (Wood Green) Ltd., Manwood House, Matching Green, Harlow, Essex. Tel: Matching 476.

## Wanted

**TOP PRICES PAID** for NEW VALVES and TRANSISTORS

popular T.V. and Radio types.

KENSINGTON SUPPLIES (C).

367 Kensington Street, Bradford 8, Yorkshire.

**WE BUY** New Valves, Transistors and clean new components, large or small quantities, all details, quotation by return. WALTON'S, 55 Worcester Street, Wolverhampton.

**EARLY WIRELESS** receivers, components and magazines, details to Johnson Raffles, Haverbreaks, Lancaster.

**WANTED.** Radio and TV Servicing books from 1964 onwards. £2.00 per copy, paid by return of post. Bell's Television Services, 190 Kings Road, Harrogate, Yorkshire. Telephone 0423-55885.

**WODEN UM3 50W** Modulation transformer, or similar. Roberts, Bala-Bangor College, Bangor, Wales.

## Ladders

**LADDERS.** 'Special Offer' Unvarnished triples. 9ft 7in closed—23ft lin extended. £18.90 delivered. Home Sales Ladder Centre (WLS2) Haldane (North) Halesfield (1) Telford, Shropshire. Tel: 0952 586644.

## Service Sheets

**SERVICE SHEETS** for Televisions, Radios, Transistors, Record Players, Tape Recorders, etc., from 5p with free Fault-Finding Guide. Over 10,000 models available. S.A.E. enquiries. Catalogue 20p and S.A.E. Hamilton Radio, 47 Bohemia Road, St. Leonards, Sussex. Telephone Hastings 429066.

# LARGE SUPPLIER OF SERVICE SHEETS

(T.V., RADIO, TAPE RECORDERS, RECORD PLAYERS, TRANSISTORS, STEREOGRAMS, RADIOGRAMS, CAR RADIOS)  
ALL AT 40p EACH

"PLEASE ENCLOSE LARGE S.A.E. WITH ALL ENQUIRIES & ORDERS"

Otherwise cannot be attended to  
(Uncrossed P.O.'s please, original returned if service sheets not available.)

### PLEASE NOTE

We operate a "by return of post" service. Any claims for non-delivery should be made within 7-days of posting your order.

## C. CARANNA

71 BEAUFORT PARK  
LONDON, N.W.11 6BX

We have the largest supplies of Service Sheets (strictly by return of post). Please state make and model number alternative. Free TV fault tracing chart or TV list on request with order.

Mail order or phone 01-458 4882

SERVICE SHEETS, Radio, TV etc., 8,000 models. Catalogue 20p. S.A.E. enquiries. Telray, 11 Maudland Bank, Preston.

## Receivers and Components

### Teleradio and the Rondo

Stocks are now available of system units as follows:

Pre-Amp £3.30 ea. p.p. 15p  
Controls and panel £9.35 ea. p.p. 25p

Power Amp units, Stereo pair £8.25 p.p. 15p

Power Supply Parts £5.50 p.p. 25p

Mains Transformer £6.87 p.p. 40p

Smoothing Capacitors (2) £1.65 p.p. 15p

Chassis & Metalwork £3.57 p.p. 30p

Hardware pack £2.20 p.p. 30p

Also, Case, Control fascia, Stereo Decoder, Matrix decoder, Speaker Units, Playing Deck.

Further information available on request.

Teleradio, 325-7 Fore Street, Edmonton, London N.9 OPE.  
Tel.: 01-807 3719

250mA Cartridge Fuses 1 1/2". 75p for 100.  
Unused Carbon Resistors. 100 different 38p (state high, medium or low range pack). Your choice 65p per 100.  
Unused Wirewound Resistors—100 assorted £1.  
150 Unused Capacitor Mixture incl. Electrolytic—Silver Mica—paper—Metalized. 65p  
8BA to 2BA. Nut-bolt washer mixture—Brass 30p per 1lb—Steel 25p per 1lb.  
Ex G.P.O. Dial Telephones £1.40p.  
20 Assorted Potentiometers Unused £1.00.  
Ex Govt. Standard Jack Plugs 4 for 50p.  
New 6 volt 36 watt SBC Bulbs 85p per doz.  
Earphones Ex Govt. 45Ω a side 60p per pair.  
(All postage included in price.)

SOUND SYSTEMS OF SUFFOLK  
676 Foxhall Rd., Ipswich, Suffolk IP3 8NQ

## Precision Polycarbonate Capacitors

All High Stability—Extremely Low Leakage

440V AC (±10%)	63V Range	±1%	±2%	±5%
0.1µF (1" x 1") 50p	0.47µF	50p	45p	25p
0.22µF (1" x 1") 60p	1.0µF	60p	50p	45p
0.47µF (1" x 1") 71p	2.2µF	80p	65p	55p
0.5µF (1" x 1") 75p	4.7µF	£1.80	£1.05	85p
0.68µF (2" x 1") 80p	6.8µF	£1.64	£1.20	£1.90
1.0µF (2" x 1") 91p	10.0µF	£2.00	£1.80	£1.40
2.2µF (2" x 1") £1.22	15.0µF	£2.75	£2.15	£1.90

TANTALUM BEAD CAPACITORS—Values available: 0.1, 0.22, 0.47, 1.0, 2.2, 4.7, 22.0µF at 15V/25V or 35V; 10.0µF at 16V/20V or 2V, 2.2µF at 6V/10V or 16V; 33.0µF at 6V or 10V; 47.0µF at 3V or 6V; 100.0µF at 3V. ALL at 10p each, 10 for 95p, 50 for £4.

TRANSISTORS:	BC183/183L	11p	BFY50	20p	
BC197/8/9	9p	BC184/184L	12p	BFY51	20p
BC114	12p	BC212/212L	14p	BFY52	20p
BC147/8/9	10p	BC547/558A	15p	AP177A	30p
BC143/7/8	12p	BF194	12p	OC71	12p
BC182/182L	11p	BF197	13p	2N3053	50p

POPULAR DIODES—1N914 6p, 8 for 45p, 18 for 90p; 1N916 8p, 6 for 45p, 14 for 90p; 1N44 5p, 11 for 60p, 24 for £1.00, 1N414 5p, 6 for 27p, 12 for 48p; 1N4001 5p, 602 6p, 603 6p, 604 7p, 605 7p, 606 8p, 607 8p.

LOW PRICE ZENER DIODES 400V. Values available: 5A. Values available: 3V, 3.6V, 4.7V, 5.1V, 5.6V, 6.2V, 6.8V, 7.5V, 8.2V, 9.1V, 10V, 11V, 12V, 13V, 13.5V, 15V, 16V, 18V, 20V, 22V, 24V, 27V, 30V. All at 7p each, 6 for 39p, 14 for 84p. SPECIAL OFFER: 100 Zeners for £5.50.

RESISTORS—High stability, low noise carbon film 5%, 1W at 40°C, 1W at 70°C. E12 series only—from 2.2Ω to 2.2MΩ. ALL at 1p each, 8p for 10 of any one value, 70p for 100 of any one value. SPECIAL PACK: 10 of each value 2.2Ω to 2.2MΩ (730 resistors) 45p.

SILICON PLASTIC RECTIFIERS—1.5 amp. brand new wire ended D027, 10V P.I.V. 7p (4 for 25p); 400 P.I.V. 6p (4 for 30p); 800 P.I.V. 11p (4 for 42p).

BRIDGE RECTIFIERS—24 amp: 200V 40p; 360V 45p; 600V 65p.

SUBMINIATURE VERTICAL PRESETS—0.1W only: ALL at 8p each; 50Ω, 100Ω, 220Ω, 470Ω, 880Ω, 1kΩ, 2.2kΩ, 4.7kΩ, 6.8kΩ, 10kΩ, 15kΩ, 22kΩ, 47kΩ, 100kΩ, 1MΩ.

PLEASE ADD 10p POST AND PACKING ON ALL ORDERS BELOW £5. ALL EXPORT ORDERS ADD COST OF SEA/AIRMAIL.

PLEASE ADD 10%, V.A.T. TO ORDERS.  
Send S.A.E. for lists of additional ex-stock items.  
Wholesale price lists available to bona fide companies.  
MARCO TRADING (Dept. W/8),  
The Maltings Station Road, West Shropshire,  
Tel: Warrich (Cheshire) 43591 (ST.9270)  
(Proprs.: Minicost Trading Ltd.)

## BETA DEVICES

MANUFACTURERS BRANDED PRODUCTS

TRANSISTORS	I.P.'s	DIODES & RECT.
AC187/188	709C TO.99 0-30	1N914 0-04
PR.	709C D.I.L. 0-80	1N4148 0-04
BC107	741C TO.99 0-88	0A209 0-09
BC109	0-40 101C D.I.L. 0-36	1N4001/2 0-06
BC109C	0-11 723C D.I.L. 0-80	1N4003/4/5 0-06
BC147/8/9	0-10 747C D.I.L. 0-85	1N4006/7 0-08
BCV70/71/72/13	748C D.I.L. 0-88	BRIDGES
BFX86/87/88	0-90 5 Watt Audio I.C.	W01 1A 0-20
BFY50	0-18 TBA 800 £1.50.	W06 1A 0-80
BFY51/52	0-12 Data free with every order.	
OC28	0-45	ZENERS
OC25	0-85	BZY56 3-3
2N2646	0-20 D.I.L. SOCKETS	33V 5% 0-09
2N3053	0-14 6-Pin 0-12	1 Watt 6-8
2N3055	0-88 14-Pin 0-12	200V 5% 0-15
2N3442	£1.40 16-Pin 0-14	L.E.D.
2N3773	£2.20	209—Red 0-17
40411	£2.20	109—Red 0-17
40636	£1.00	Include V.A.T. L.E.D. Clip 0-02

C.W.O. PLUS P.P. 10p TO BETA DEVICES.

263 THE RIDGEWAY, ENFIELD, MIDDXX.

## TAPE HEADS

Send stamp for lists  
**R.D.I. Ltd.**  
Chilton Works,  
Garden Rd.,  
Richmond,  
Surrey,  
TW9 4NS

For valve and transistorized recorders from £2 ea.

### INCOMPARABLE V.H.F. KIT

CV2—unique triple-purpose (Converter, Receiver, Tuner—Fader) kit for the amateur enthusiast. Fantastic transistorised performance, World Wide Sales. Complete kit of top grade parts covers 80-180 MHz with easy build diagrams only £5 direct from maker or S.A.E. for free literature. (S.V. Kits also available).

**JOHNSONS (RADIO) Est. 1943**  
SHAW ST., WORCESTER WR1 3QQ.

**GAS SENSOR TGS105** with circuits £1.80 post free.

**15-0-15V Power Supply Card**, 100mA outputs, foldback limiting, 240 vac.  
Built and tested £9.71 + 22p P & P.  
Also, built into diecast box with on/off switch, neon, 3 terminals and mains lead £14.09 + 22p P & P.

Electronic thermometer for use with multimeter (1mA). Range 0-100°C. Requires 2 x PP3's. Built into box with on/off switch, leads, sensing probe, etc. £8.87 + 22p P & P.

### BARON ELECTRONICS,

176 Brookhurst Ave., Bromborough, Wirral, Merseyside L63 0PF.

**ELEVEN BAND RADIOS**, SW 1-4 Marine, LW, MW, FM, PSB (76-86), Aircraft (108-136), PSB (148-176), Batt/Mains, BFO, Squelch, Fine Tune, Output, 1.3W. Latest Model £60, also Grundig Bargains, Satellit £120, etc. SAE Lists, Multi-Band Radios, Langton Radios, High Street, Rochester, Staffs. 088-923 388.

**BRAND NEW COMPONENTS** by return, Electrolytics 16V, 25V, 50V—0.47, 1, 2.2, 4.7, 10mfds.—4p, 22, 47—4.2p (50V—5p), 100—5.2p (50V—7p), 220—6p (50V—9p). Subminiature bead-type tantalums 0.1/35V, 0.22/35V, 0.47/35V, 1.35V, 2.2/35V, 4.7/35V, 10/16V, 22/16V, 47/6V, 100/3V—8p. Mylar Film 100V 0.001, 0.002, 0.005, 0.01, 0.02—2.2p, 0.04, 0.05—3p. Polystyrene 63V F12 series, 10pf—1,000pf—2p, 1,200pf—10,000pf—3p. Miniature Highstab. resistors 5%, E12 series Carbon film 1/2 W, 1Ω-10MΩ, (10% over 1M). Metal film 1/2 W 10Ω-2.2MΩ and 1W 27Ω-10MΩ all 1p ea. Postage 8p. The C.R. Supply Co., 127 Chesterfield Road, Sheffield.

**COMPONENTS GALORE**. Pack of 500 mixed components manufacturers surplus plus once used. Pack includes resistors, carbon and W.W., capacitors various, transistors, diodes, trimmers, potentiometers etc. Send £1+10p p&p. C.W.O. To: Caledonian Components, Strathore Road, Thornton, Fife.

**PRINTED CIRCUIT BOARDS**. Any PCB published in Practical Wireless/Electronics ETI, WW, etc. Any month any year. In fibreglass at 5p/sq. in. Postage free (min. 50p). Also Artwork and/or photography undertaken. SAE for full details. PW CRATA complete set—£3.95. P. Lancaster, 11 Chesterton Road, Cambridge, Cambs CB4 3AD.

**MIXER KIT**. Professional standard 5 channel mono and stereo kits. Full assembly instructions, fibre glass printed circuits, front panel, case and all components. Slider controls—mains power—pre-fade listen—magnetic cartridge input—auto fade. Dimensions: 24 x 6 x 3in. Mono kit: £33. Stereo kit: £49 inc. VAT. Details, specification, picture. SAE to Harwell Instruments, Department BPC, Spice's Yard, South End, Croydon CR0 1BF.

**TRANSISTOR Amplifier 50p**; LW/MW Mixer Panels 50p, 25 Assorted skeleton presets 50p. Radio Cabinets, suitable ex-speakers 50p. Archer, 9 Pine Grove, Maidstone, Kent.

**LEDs**. Three colours, Red, Green, Yellow. Four sizes, 0.1in, 0.125in, 0.16in, 0.2in. Mixtures all sizes and colours. 50—£5, 100—£9, including VAT and postage. C.W.O. Larger quantities by negotiation. Industrial Electronic Supplies (Stockport) Ltd., 181a Bramhall Lane, Davenport, Stockport, Cheshire.

## Miscellaneous

### MORE RANGES FOR LESS MONEY

AC/DC Multimeter type U4324  
 A-DC 0-06-3A - 6 Ranges.  
 A-AC 0-3-3A - 5 Ranges.  
 V-DC 0-6-1200 V - 9 Ranges.  
 V-AC 3-300 V - 8 Ranges.  
 Freq.: in the range of 45 to 20kHz  
 Resistance: 500 Ohm to 5 MOhm  
 5 Ranges. Decibel: -10 to +12dB  
 Accuracy  $\pm 2.5\%$  DC  $\pm 4\%$  AC  
 Dimensions: 167 x 98 x 63 mm.



Only **£8.00**

### SUPRETESTER 600R ICE

10 Fields - 80 Ranges: Plus a lot of accessories for measurements of 500A-AC 100 A/DC - Temperature -50C to +200C - Magnetic fields up to 15 KGauss - Phase Indicator - EHT 25kV Electronic Volt Ohm-meter Transistor Diode Tester etc.



Dimensions: 128 x 95 x 32 mm - 300 grams-20kOhm/V Accuracy 1% DC. Ask for free catalogue

**£18.50**

Accessories Extra

### ALPHANUMERIC NIXIE TUBES B7971

The Alphanumeric NIXIE tube has the ability to display all the letters of the alphabet numerals 0 thru 9 and special characters in a single tube. From the standpoint of both readability and electrical characteristics, the Alphanumeric NIXIE tube provides many unique benefits including  $\star$  All DC operation  $\star$  Uniform, continuous line characters of equal height  $\star$  Memory with simple solid state drive circuits  $\star$  Readability in high ambient light—200 foot-lamberts brightness  $\star$  Long life with no loss of brightness  $\star$  Character height  $2\frac{1}{2}$ ".



Price only **99p** each plus 16p P/P.

Add 10% VAT to all items + 35p P & P

**ELECTRONIC BROKERS LTD.**

49-53 Pancras Road, London NW1 2QB  
 Tel: 837 7781

# Darned Electronic Wizardry

by Dewtron (VAT extra.)

Famous Kits, e.g. waa-waa complete kit £2.95; Puzzle kit £5.50 auto rhythm modules P & P 20p min. Ring Modulator modules £8 and whole range of synthesiser modules, musical novelties, etc. Catalogue 15p from D.E.W. Ltd., 254 Ringwood Road, Ferndown, Dorset.

### BE PROUD OF YOUR WORK AND BUILD IT IN A BEC (Book End Chassis)

#### PUNCHING SERVICE IF REQ'D

Prices include V.A.T. & Postage

A beautifully designed modern cabinet with simulated black leatherette top (PVC bonded to metal) solid wooden end cheeks, with room at the back for Output Sockets etc. Felt pads are fitted on bottom of cheeks for non-scratch.

Other Styles available, please send S.A.E. for details.

#### P.C. BOARDS & PANELS

We specialise in small runs of P.C. Boards and screen printed or anodised aluminium panels. From 1 to 500 send sketch or negative and we will send you our quotation.

**H.M. ELECTRONICS (PW)**, 275a Fulwood Road, Sheffield S10 3BD (Behind Broomhill P.O.)

### We've been in a mess . . .

and I apologise publicly to every customer who suffered delays when we found there were more of you wanting our services than we were ready to deal with. There's been a reorganisation to make things quicker and easier for all of us.

By now, all our customers should have been sent copies of the new, simpler order form with the redesigned Price List. If not, would you please send a stamped addressed envelope?

**DAVID MCGARVA - PO Box 114 - Edinburgh EH1 1HP**

New customers are asked to write for a list before ordering.

## PSYCHEDELICATESSEN

is the only way to describe the paradise of Freaky gear now available from Boffin. Look!

### KITS

No Licence Exam Transmitter/Receiver **£8.40**  
 Variable-rate, Bright-Flash, Pocket Mini-Strobe **£2.40**

### READY-MADE MODULES

Maxi-Volt Spark Generator ( $\frac{1}{2}$  Inch spark), 15,000 Volts! **£1.35**  
 Experimental Mini Dream-Laboratory **£2.20**  
 Sensitive non-anatomical electronic Stethoscope **£2.20**  
 Electronic 'Voice-Thrower' **£2.20**  
 Ghost-Hunting Aid **£2.20**  
 People Detector **£2.20**  
 Experimental Water-Fone **£4.40**  
 Psychedelic Meditation Aid **£2.20**  
 Bird-Watchers Remote Monitor **£2.20**  
 Psychological Cross-Eyed Ears Device **£4.40**  
 Super Sound-Catcher **£2.20**

(All prices include VAT, packing & postage)

Send remittance to:

### BOFFIN PROJECTS

4 Cunliffe Road, Stoneleigh Ewell, Surrey

(Mail order U.K. only)

Or for more details, send 20p for lists, plus free design project sheet

### P.W. F.M. TUNER AMP + CASSETTE

(P.W. MARCH—MAY 74)

Printed Circuits 75p ea (pp 15p)

Separate Components available


FREE LISTS (S.A.E.)

**LIMITED NUMBER DIGITAL CLOCK KITS**  
 12 OR 24HR USING NIXIE READ OUTS TEAK CASE.

LIST £32 (12HR) OFFERED AT £25  
 FURTHER INFORMATION ON REQUEST
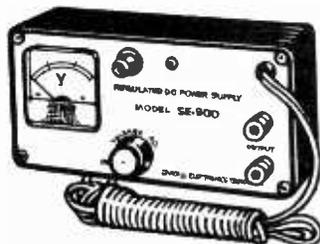
### TELETRADIO ELECTRONICS

325 FORE STREET, LONDON N.9. OPE. 01-807-3719



## DC POWER SUPPLIES

Regulated power supply variable up to 15V 0.5A. Model SE800. Ideal for development work. **£11**

Cash with order includes VAT & p. & p.  
**J. H. ASSOCIATES LTD.** Cricketfield Lane, Bishop's Stortford, Herts.

### TREASURE TRACER

#### MK III Metal Locator

- Varicap tuning
- Britain's best selling metal locator kit
- Weighs only 22oz.
- Speaker and earphone operation
- Knocks down to only 17in.
- Prebuilt search coil assembly
- Ministry approved design
- As seen on BBC1 and BBC2 TV
- You only need soldering Iron, screwdriver, pliers and snips
- Five transistor circuit

Send s.a.e. for leaflet

Contains 100 Parts

**£9.80**

Full, quick and guaranteed Post 35p

**£13.75**

MINIKITS ELECTRONICS  
 35a LANGLEY DRIVE, WANSTAD LONDON, E11 2LN (Mail order only)

**BUILD IT** in a DEWBOX quality cabinet. 2in x 2 $\frac{1}{2}$ in x any length. D.E.W. Ltd., Ringwood Road, FERN-DOWN, Dorset. S.A.E. for leaflet. Write now—Right now.

**LOW COST I.C. MOUNTING.** Lengths of 100 I.C. pin sockets, 60p (p & p 5p). Quantity rates, SAE details & sample. L.E.D. (MLED500), 20p each. (post paid). P.K.G. Electronics, "Oak Lodge", Tansley, Derbyshire.

**HARDWARE SUPPLIES.** Sheet aluminium individual sizes or standard packs, drilled to spec. Screws, nuts, washers etc. Fascia panels in aluminium individual requirements. Printed circuit boards, one-off or small runs. Printed circuit drafting tapes etc. 7p for list. Ramar Constructor Services, 29 Shelbourne Road, Stratford on Avon. Warwks. CV37 9JP.


**PRINTED CIRCUITS.** For any PW project, 65p each, ready drilled for assembly. Where more than one in project £1.20 the set. CWO plus 5p p&p. All PC work undertaken. W.K.F. Electronics, Welbeck Street, Whitwell, Worksop, Notts.

**SUPERB INSTRUMENT CASES** by Bazelli, manufactured from heavy duty PVC faced steel, choice of 70 types, send for free list, Bazelli Instrument Cases, Dept 25, St. Wilfrids, Foundry Lane, Halton LA2 6LT, Nr. Lancaster.

**AERIAL WIRE.** High quality p.v.c. covered multi-strand copper 25ft-25p (6p). 50ft-45p (9p). 75ft-67p (12p). 100ft-89p (15p). 150ft-£1.32p (25p). 200ft-£1.76p (25p). 250ft-£2.21p (26p). 300ft-£2.66p (30p). EGG insulators 11p pair (5p). P&P in brackets, SAE all enquiries. A.I. Radio Components, 14 The Borough, Canterbury, Kent CT1 2DR.

**LOGIC TEST PROBES:** indicates logic levels single pulses, pulse trains. Excellent value. £7 inclusive. Crudwell Electronics, 7 The Dawneys, Crudwell, Nr. Malmesbury, Wiltshire.

# put an end to this...

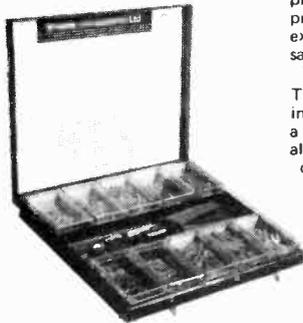

Now you can complete that wiring job the professional way. Whether you're working on prototypes, original equipment or servicing existing installations, Invader offer this indispensable aid - Termi-Kit.

The kit contains a choice of 14 different types of insulated lugs in 10 different compartments with a sturdy pair of crimping pliers for every size. The all metal box is designed to last, so by simply re-ordering individual terminal packs from us you can ensure you're never without the correct item for the job.

Each kit comprises a divided metal storage case containing 10 plastic boxes. Each box pre-packed with any one type of ring spade or lug type terminals, the quantity

per box depending on size and type plus one universal crimping and stripping tool, and the ordering information for replenishing your stock is clearly printed on the lid.

There is a choice of 36 termination styles to choose from yet ordering is uncomplicated as there is one standard price.

Invader Termi-Kit with 10 terminal packs and crimping tool ... .. £16.50  
Replacement packs ... .. .96 ea.

## Invader Components Ltd.

30 Tribune Drive, Trinity Trading Estate, Sittingbourne, Kent.  
Tel: Sittingbourne 70533. Telex: 965313.

# NEW~Termi kit from Invader

## Never be without the right Termination



### AERIAL BOOSTERS—£3.30

We make three types of Aerial Boosters :-  
B45-UHF 625, B12-VHF 405, B11-VHF RADIO.

### VALVE BARGAINS

ANY 5—50p, 10—75p, 50—£3.30 :-  
ECC82, ECL80, EB91, EBF89, EF80, EF85, EF183,  
EF184, EY86, PCC84, PCC89, PCC189, PC97,  
PCF80, PCF86, PCF805, PCF808, PCL82, PCL83,  
PCL84, PCL85, PFL200, PL36, PL81, PL504, PY33,  
PY82, PY800, PY801, 30L15, PC86, PC88.

### COLOUR TV VALVES

PL508, PL509, PY500/A—25p each.

### UHF TRANSISTOR TUNERS

Rotary Type—£2.00. 4 Button Type—£2.50.

### PLUGS — SOCKETS

Price per item, in brackets for ten.  
CO-AX Plugs—6p (50p), Socket Surface—7p (10p),  
Connectors—4p (35p).

### D.I.N. PLUGS

2 Pin, 3 Pin and 5 Pin—20p (£1.65).


JACK PLUGS, Standard—18p (£1.50), 3.5mm—  
10p (80p), 2.5mm—10p (80p)

All prices include V.A.T. p. & p. 10p per order  
Money back refund. S.A.E. for leaflets.

### ELECTRONIC MAILORDER (BURY) LTD.

62 Bridge St., Ramsbottom, Bury,  
Lancs. Tel. Rams 3036
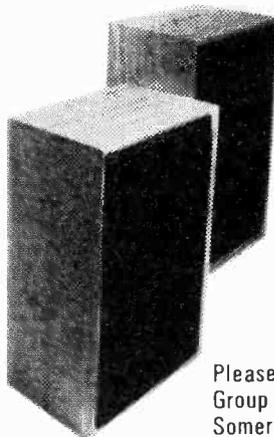
# Quality Loudspeaker Systems at half price



Direct from manufacturer as supplied by us to the trade.

Finished in natural Teak veneer 15 watt 8ohm speaker system containing Goodmans 8" bass + 3" tweeter speakers.


Two cabinet sizes:

- \*a) 17" high x 10" wide x 7" deep.
  - \*b) 20" high x 12" wide x 8½" deep.
- Price of a) £12.50 per pair incl. VAT.  
b) £14.50 per pair incl. VAT.

plus £1.25 packing and carriage U.K.  
(50p only if collected from Rugby).

Please send cash with order direct to  
Group 3 Cabinets Ltd.,  
Somers Road Industrial Estate,  
Rugby,  
Warwickshire. Tel: 0788-78211
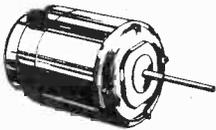
## "SLO-SYN" 3-LEAD SYNCHRONOUS STEPPING MOTOR



Type SS15. These fine motors are easily reversed, starting and stopping in less than 5 without electrical or mechanical braking. Simple relay circuit can be applied to give DC, or winding for a maximum holding torque of 300oz/in with 35v at 0.35 amps through winding. For A.C. (synchronous) operation at 120v, 50Hz. Speed 60 rpm at 60Hz., 72 rpm. STEPPING. Holding torque at 50 steps per second—100 oz/in. Can be wired to give 100 or 200 steps per revolution with accuracy of 0.1° per step non-cumulative. Torque characteristics can be modified by simple R.C. circuits. Dimensions: dia. 4", body length 4 1/2", spindle length 2 1/2" x 3/8" dia. Weight 6 1/2 lbs. BRAND NEW in original maker's boxes. Offered at less than 1/2 maker's price. **OUR PRICE ONLY £15**

### MAINS SOLENOID by MAGNETIC DEVICES LTD.

A beautifully constructed solenoid at half normal price. A 2-sided bracket is incorporated for vertical or horizontal mounting. Size: 2" x 1 1/2" x 1 1/2". Pull is approximately 2lbs., plunger travel 1 1/2". Fixing eye takes up to 1/2" bolt, plunger non-captive. NEW in original maker's boxes. £1.20. P. & P. 20p. Large number available, special price for quantity.



### SMITHS RINGER-TIMER

Reliable 15 minute times, spring wound (concurrent with time setting) 15 x 1min divisions, approximately 1/2" between divisions. Panel mounting with chrome bezel 3 1/2" dia. £1.40. 15p P. & P.

### KNOWLE (U.S.A.) MINIATURE MICROPHONE CAPSULES

Impedance approx. 200Ω, output 60 or 80 DB at 1 Kc. As used in deaf aids, bugging devices, etc. Size (6 DB) 7/32" x 5/32" x 1/8"; (80 DB) 3/8" x 5/32" x 1/8". Equipment, all tested. £1.20 each. P. & P. FREE.


### MAINS SOLENOID

This little unit gives vertical lift of approximately 1" through hinged "e.l.b.o.w.". Bracket incorporates 2 fixing screws. Length of arm, 2 1/2". 240V A.C. Pull at coil is approximately 11lb. £1 FREE P. & P. Special quotes for quantities.


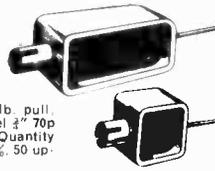
### SOLENOIDS by WESTOOL

240AC type MM6. 3lb. pull, 2 1/2" x 1" x 1 1/2". Travel 1". 90p each. P. & P. 10p. 240AC type MM4. 2lb. pull. 1 1/2" x 1 1/2" x 1". Travel 3/4" 70p each. P. & P. 10p. Quantity discounts: 10-50 10%, 50 upwards 25%.



### OPEN FRAME shaded pole GEARED MOTORS

(Dural gear case) 240 A.C., 28rpm. NEW HIGH TORQUE, approx. overall size: 3 1/2" x 3 1/2" x 2 1/2" & spindle 1/2" dia. as illustrated. £2.70. P. & P. 30p. Similar to above, 19rpm. £2.70. P. & P. 30p. 110rpm with pressed steel gear case (similar to above but slightly smaller). £2.70. P. & P. 30p.



### NORPLEX

The famous American fibre-glass copper-clad laminate. Finest quality with woven glass base of Epoxy-resin. Excellent Mech. and Elec. conductive properties. Heat resistant, ideal for P.C.'s etc. THIS IS A SPECIAL PURCHASE AND ONLY AVAILABLE WHILE STOCKS LAST! Sizes: 12" x 12"; 24" x 12"; 24" x 24"; FULL SHEET 43" x 37" (11 sq. ft.). Single-sided Copper with thickness of 1/32", 3/64", 3/32". Also double-sided 1/32", 1/16", 3/32", £1 per sq. ft. Cut sizes (1-10 sq. ft.) 25p. P. & P. Full Sheet £8 each. Carr. £1 for 1st sheet plus 25p each additional sheet.

### SILVANIA MAGNETIC SWITCH


Now complete with reference magnet!

A magnetically activated switch, vacuum sealed in a glass envelope. Silver contacts, normally closed. Rated 3amp at 120v, 1 1/2amp at 240v. Size: (approx.) 1 1/2" long x 1/2" dia. Ideal for burglar alarms, security systems etc., and wherever non-mechanical switching is required. 10 for £2.10; P. & P. 15p. 50 for £8; 100 for £16.50. FREE P. & P. over 10.


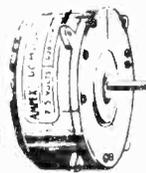
### AMPEX 7.5v. D.C. MOTOR

This is an ultra precision tape motor designed for use in the AMPEX model AG20 portable recorder. Torque 450GM/CM. Stall load at 500ma. Draws 60ma on run. 600rpm ± speed adjustment. Internal AF/RF suppression, 1/2" dia. x 1" spindle, motor 3" dia. x 1 1/2". Original cost £16.50. OUR PRICE £3.30. P. & P. 25p. Large quantities available (special quotations). Mu-metal enclosure available 75p each. FREE P. & P.



### ALL PRICES NOW INCLUDE V.A.T. UNLESS OTHERWISE STATED

All items are NEW and UNUSED. Postal or carriage charges are for Gt. Britain only. We welcome orders from established companies, educational depts., etc. All orders under £2.50 C.W.O., please. Company orders under £2.50, surcharge 60p unless C.W.O.

# ELECTRO-TECH COMPONENTS LTD.

315/317, EDGWARE ROAD, LONDON, W2.  
Tel: 01-723 5667 01-402 5580

## QUALITY STEREO SOUND.

ALMOST 1/2 PRICE OFFER! SOLENT AUDIO SYSTEM

MADE TO SELL AT DOUBLE THE PRICE IN CABINET FORM  
OUR PRICE £49.95



£5 down

\*Stereo Tuner Amplifier chassis with AM/FM radio covering long medium short and Stereo FM wavebands. Separate Base and Treble controls. Power output 7 watts R.M.S. per channel (frequency response 25-20,000 Hz) Tape record and playback facilities. Dimensions 18" x 8 1/2" x 3 1/4". The very latest BSR automatic record deck with cue and pause control. Two matching elliptical speaker units.

Order early limited stocks available cash price £49.95. Credit Sale £5.00 deposit 9 monthly payments of £5.75 (Total Credit price £56.75). P. & P. £2.50. Send £7.50 today.

Chassis only available for cash at £35.00.

Full 12 months Guarantee.


CALLERS WELCOME.

Stereo headphones supplied with every order.

LEWIS radio

WS 8/74, 100 CHASE SIDE SOUTHGATE LONDON N14 5PL Telephones: 01-886 9666/3733
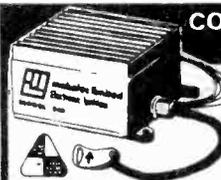
## CONTACTLESS ELECTRONIC IGNITION BY MOBELEC



FROM ONLY £13.95 p&p 25p

We break the price barrier with this trouble-free inductive discharge contactless ignition which replaces contact points by a solid-state trigger-head giving high energy spark for excellent cold-weather starting and super-smooth tick-over. Designed for 4 or 6 cylinder neg. earth cars at a price you can afford. Easy to fit, clear illustrated instructions, free fitting kit. State model, make and year. Other Mobelec capacitive discharge E series models available. Mobelec E series for high performance engines. 4 & 6 cylinder NEG. AND POS. EARTH. £22.82. 8 cyl. £24.75. Post free.

Dept. PW/6, 226 Mary Street, Birmingham B12 9RJ. Tel: 021-440 3600  
**SILHILL PRODUCTS**

### MASSIVE CLEARANCE BARGAINS

Bargain component parcels contain Resistors, Capacitors, Switches, Potentiometers, Knobs, IF's, Tag Strips, Drive Drums, Transistor Panels etc., etc. Save yourself £s on these well selected parcels 6lbs net weight £1.00, p.p. 50p.

Brand new Wire-wound Resistors. Good Selection. 100 for £1.00, p.p. 20p.

Flexible Connecting Wire, assorted colours. 100 yards for £1.00.

Eddystone Die-Cast Boxes with Lid 4 1/2" x 2 1/2" x 1 1/4" 50p.

Assorted Capacitors, Silver Mica, Tubular and Disc Ceramics, Polystyrene. Tremendously good selection. 300 for £1.00, p.p. 20p.

Mullard Ferrite Cores. LA3 100 to 500kHz 50p. LA4 10 to 30kHz 75p. LA2100 3 to 200kHz 50p.

Rotary Switch 1 pole. 14 way, 3 bank, good quality, excellent value 35p.

Colvern W/Wound Potentiometer Spindle Type 10 ohms 35p.

Please include 10% VAT to total cost of goods.

MAIL ORDER ONLY

**XEROZA RADIO**  
1, EAST STREET, BISHOPS TAWTON, DEVON

# WATFORD ELECTRONICS

35 CARDIFF ROAD, WATFORD, HERTS, ENGLAND  
MAIL ORDER. CALLERS SATURDAYS ONLY

C.W.O. Please P. & P. add 15p to orders under £3. Prices exclusive of VAT  
Send 10p Postage for our comprehensive catalogue.

## TRANSISTORS (All Components Brand New and Fully Guaranteed)

AC125 14p	BC148/9 11p	MEJ520 52p	PIP29 43p	2N2894 30p	DIODES
AC126/7 14p	BC182 11p	MPP102 38p	TIP30 48p	2N2906 15p	AA120 10p
AC128 14p	BC183/4 11p	MPP103 38p	TIS43 25p	2N2907 18p	BA116 15p
AC176 14p	BC212 11p	MPP104 35p	ZTX107 12p	2N2926 9p	BY164 35p
AC187/8 12p	BC213/4 11p	MPP105 42p	ZTX108 12p	2N3053 20p	BY211 25p
AC1917 21p	BCY70 15p	OC26 48p	ZTX109 12p	2N3054 42p	OA5 30p
AC1919 22p	BCY71 20p	OC28 48p	ZTX300 14p	2N3055 42p	OA9 9p
AC1920 20p	BCY72 15p	OC35 48p	ZTX301 14p	2N3702/3 11p	OA79 10p
AC1921 18p	BD121 £1-00	OC41 15p	ZTX302 18p	2N3703/4 12p	OA81 8p
AC1922 18p	BD131 45p	OC42 15p	2N1131 20p	2N3705/6 10p	OA85 10p
AD140 60p	BD132 45p	OC44/45 12p	2N1132 20p	2N3707 10p	OA90/1 6p
AD145 40p	BDY19 £1-95	OC70/71 12p	2N1301/2 20p	2N3708/9 7p	OA200/1 6p
AD161 30p	BF194/5 15p	OC72 12p	2N1303/4 24p	2N3819 25p	PL4001 6p
AD182 30p	BF196 18p	OC74 22p	2N1305/6 24p	2N3803/4 15p	PL4004 8p
AF114/5 14p	BFY50 20p	OC81 12p	2N1307 20p	2N3905/5 17p	PL4007 12p
AF116/7 14p	BFY51 20p	OC82 15p	2N1671B 90p	2N4444 £1-98	1N914 5p
AF118 40p	BFY52 20p	OC83N 20p	2N1990 45p	ZENER	1N4011/2 8p
BC107 10p	BFY53 17p	OC140 80p	2N2217 23p	BZY88	1N4003/4 7p
BC108 10p	BSX29 40p	OC201 60p	2N2218A 28p	400mW	1N4005 7p
BC109 10p	MJE370 83p	OC202 80p	2N2303 75p	3-3V-33V	1N4006/7 8p
BC147 11p	MJE371 63p	OC204 65p	2N2483 75p	10p each	1N4148 5p

## TTL 74 SERIES

(less 10%, 50 + mixed)

7400 18p	7427 37p	7472 28p
7401 18p	7428 43p	7473 37p
7402 18p	7430 18p	7474 37p
7403 18p	7432 37p	7475 55p
7404 20p	7433 43p	7476 37p
7405 18p	7437 43p	7480 80p
7406 18p	7438 43p	7481 £1-10
7407 30p	7440 18p	7482 80p
7408 21p	7441 75p	7483 £1-10
7409 24p	7442 15p	7484 95p
7410 20p	7443 £1-20	7485 £1-87
7411 22p	7444 £1-20	7486 38p
7412 20p	7445 £1-89	7490 60p
7413 20p	7446 £1-89	7491 80p
7414 60p	7447 £1-30	7492 60p
7416 35p	7448 £1-18	7493 60p
7417 35p	7450 18p	7494 80p
7420 18p	7451 18p	7495 80p
7422 75p	7453 17p	7496 90p
7423 35p	7454 17p	7497 £3-00
7425 38p	7460 18p	74104 60p
7426 28p	7470 28p	74105 50p

## LINEAR ICs

709C DIL/TO99	35p
723C DIL/TO99	80p
741C DIL/TO99	38p
748C	45p
CA3018	75p
CA3020	£1-40
CA3050	£1-35
CA3048	80p
CA3075	£1-65
CA3090Q	£4-25
LM300	£1-70
LM305	£1-70
MFC4000B	£1-70
MC305	£1-70
MC24P	£1-90
MC1303L	£1-90
MC1304P	£1-80
MC1310P	£2-75
MC1710CG	40p
PA246	£1-50
TAD100	£1-50
TBA809	£1-35
ZN414	£1-15

## OPTO ELECTRONICS

Minitrans 3015F only £1-29

OC70	50p
OC71	70p
ORP12	45p
ORP60	45p
ORP61	46p
Light Emitting Diode	
TIL209 Red	21p

Also available  
More ICs, Transistors,  
Fuses, Fuse Holders,  
Transistor Insulation  
Kits, Transformers 5V,  
8V, 9V; Miniature toggle  
switches, (centre off  
and changeover type)  
chokes, etc.

## DIL SOCKETS

8, 14, 18 pin 15p each

## POLYESTER CAPACITORS. Axial lead type.

400V: 0-001µF, 0-0015µF, 0-0022µF, 0-0033µF, 0-0047µF, 0-0068µF, 24p; 0-01µF, 0-015µF, 0-022µF, 3p; 0-047µF, 0-068µF, 0-1µF, 0-15µF, 4p; 0-22µF, 7p; 0-33µF, 10p; 0-47µF, 13p; 180V: 0-1µF, 0-15µF, 4p; 0-22µF, 5p; 0-33µF, 6p; 0-47µF, 7p; 0-68µF, 10p; 1µF, 13p; 250V: 0-22µF 6p 0-68µF 12p; 0-33µF 8p; 0-47µF 9p; 2-2µF 18p.  
Radial lead P.C. type:  
250V: 0-01µF, 0-015µF, 0-022µF, 3p; 0-033µF, 0-047µF, 0-068µF, 34p; 0-1µF, 4p; 0-15µF, 4p; 0-22µF, 0-33µF, 5p; 0-47µF, 7p; 0-68µF, 10p; 1-0µF, 11p.

## ELECTROLYTIC CAPACITORS. Miniature axial lead type.

63V: 1µF, 1-5µF, 2-2µF, 3-3µF, 4µF, 4-7µF, 6-8µF, 10µF, 15µF, 20µF, 22µF, 47µF, 68µF, 100µF, 25V: 33µF, 6p; 68µF, 6p; 150µF, 6p; 220µF, 11p; 470µF, 15p; 680µF, 18p; 1,000µF, 24p; 100µF 12p, 16V: 40µF, 100µF, 125µF, 250µF, 6p; 1,000µF, 1,500µF, 18p, 10V: 4µF 5p, 60µF 10p, 1,000µF 14p, 2,200µF 18p.

## CERAMIC CAPACITORS

50V d.c. Plaquette body 25mm leads.  
Range: 5pF-10,000pF. Price 2p each.  
0-015µF, 0-022µF, 0-033µF, 0-047µF 3p.

## POTENTIOMETERS AB Carbon Track

0-25W, log and linear values.  
1kΩ-2MΩ Single gang 12p  
5kΩ-2MΩ s/gang w/switch 24p  
2kΩ-2MΩ Dual gang 37p

## SLIDER POTENTIOMETERS

0-25W Log and linear  
10K-100KΩ Single Gang 40p  
10K-100KΩ Dual Gang 55p  
KNOBs for above Black or Silvered 10p

## BRIDGE RECTIFIERS

1A 50V	25p	100V 1A	45p
1A 100V	25p	600V 1A	55p
1A 200V	28p	100V 3A	40p
1A 500V	30p	400V 3A	55p
2A 50V	35p	600V 5A	75p
2A 200V	45p	600V 7A	95p
2A 600V	50p	ALUM. BOXES	
4A 200V	60p	2 1/2" x 5 1/2" x 1 1/2"	42p
4A 500V	80p	4" x 4" x 1 1/2"	42p
6A 200V	90p	4" x 2 1/2" x 1 1/2"	42p
6A 600V	120p	4" x 5 1/2" x 1 1/2"	45p

## THYRISTORS

100V 1Amp	30p
400V 1A	45p
600V 1A	55p
100V 3A	40p
400V 3A	55p
600V 5A	75p
600V 7A	95p

## VEROBOARD

	0-1	0-15	0-15
			plain
2 1/2" x 3 1/2"	30p	23p	14p
2 1/2" x 5"	32p	32p	15p
3 1/2" x 3 1/2"	32p	32p	35p
3 1/2" x 5"	38p	38p	35p
3 1/2" x 7"	80p	75p	55p
3 1/2" x 17"	130p	105p	70p
5 x 17"	173p		105p
Pkt of 36 pins			20p
Spot face cutter			48p
Pin insertion tool			69p

## MYLAR FILM CAPACITORS

100V: 0-001µF, 0-002µF, 0-005µF, 0-01µF, 0-02µF, 0-04µF, 0-05µF, 3p.  
100V: 0-1µF, 0-2µF, 5p.

## PRESET POTENTIOMETERS

0-25W 1kΩ-1MΩ Hor. and Vert. 8p  
0-1W 50Ω-470kΩ Vert. only 4p

## KNOBs (To fit 1/2" shaft)

Black Pointer Type 8p  
Slim Silvered Aluminum 18p  
Black 1 1/2" with Chrome Rim 15p

## RESISTORS

Tol.	Range	Values	1-24	25+
1W	5%	2-2R-10M	E12	1p 0-8p
1W	5%	2-2R-10M	E12	1p 0-8p
1W	5%	2-2R-10M	E12	2p 1-5p
4W	10%	1-10 ohm	E12	8p

Do not mix Ohmic values to obtain quantity prices.

## SWITCHES Toggle SPST

DPDT	18p
Slide 1/4 A D.P. sub-min. 120V	22p
Slide 1/8 A D.P. 250V	16p
Push Button min. P/M or P/B	15p
Rotary Wavechange 1 pole 12 way, 2p/6w, 3p/4w, 4p/3w	24p

## JACK PLUGS (chrome) SOCKETS

Standard Screened 17p Standard 15p  
Stereo Screened 30p Stereo 15p  
2-5mm Screened 10p 2-5mm 8p  
3-5mm Screened 14p 3-5mm 8p

## DIN PLUGS, SOCKETS & COUPLERS

Pins: 2, 3, 4, 5 (180°, 240°), 6, 7  
Plugs, 12p; Sockets, 8p; Couplers, 10p  
Coaxial Plugs, 10p; Sockets, 8p

## PHONO PLUGS, SOCKETS & COUPLERS

Assorted Coloured Plugs: 6p  
COUPLERS: 8p. SOCKETS Single: 5p, Double: 7p, Triple: 10p

## INDEX TO ADVERTISERS

A. H. Supplies	286
Ambic International	316
Amphenol	290
A.S.P. Ltd.	352
Audiotronics	363, 364, 365
Baker Loudspeaker Ltd.	376
Baron Electronics	371
Barrie Electronics	300
Bentley Acoustics	321
Beta Devices	371
B.H. Component Factors Ltd.	298
Bi-Pak Semiconductors	288, 289
Bi-Pre-Pak Ltd.	351
Boffin Projects	372
British Institute of Engineering Technology	284, IBC
British National Radio & Electronics School	315, 340, 356
Bull, J. (Electrical) Ltd.	287
Caranna, C.	371
Chiltmead Ltd.	340
Chromasonic Electronics	294
Codar	321
Colomor (Electronics) Ltd.	358
C.T. Electronics	285
Custom Cabinets	356
Dabar Electronic Products	300
Davian	356
D.E.W. Ltd.	372
Eagle International	301
Electronic Brokers	372
Electronic Design	376
Electronics Mailorder Ltd.	373
Electropares	286
Electro-Tech	374
Electrovalve Ltd.	IFC
Elvins	292

Felstead Electronics	376
Foulsham Tab	290
Gregg Electronics	352
Greenweld Electronics	359
Group Three	373
HAC (Shortwave) Products	320
Harverson Surplus Co. Ltd.	362
Heath (Gloucester) Ltd.	340
Henry's Radio Ltd.	295, OBC
H.M. Electronics	372
Home Radio (Components) Ltd.	294
I.C.S.	370
I.L.P. (Electronics) Ltd.	293
Imperial Trading	370
Integrex	367
Invader Components	373
Jermyn Industries Ltd.	319
J.H. Associates	372
Johnsons (Radio)	371
Kensington Supplies	370
Keytronics	320
Lewis Radio	284, 374
Linear Products Ltd.	359
London Computer Operators Training Centre	370
London Electronics College	370
Maplin Electronic Supplies	343
Marco Trading	371
McGarva, D.	372
Milward, G. F.	362
Minikits Electronics	372
Mullhall Electronics	344
Multicore Solders	286
Newmart Electronics	347

Padgetts Radio Store	300
Partridge Electronic Ltd.	344
Pembridge College of Electronics	292
RCS Products	366
Radio Components Specialists	296, 297
R.D.I.	371
Radio Exchange Ltd.	339
Radio Society of Great Britain	284
RSC (Hi-Fi) Centres Ltd.	282, 283
RST Valley Mail Order Co.	299
R & TV Components Ltd.	360, 361
Riversdale Electronics	292
Saxon Entertainments Ltd.	291
Silhill Products	374
Sinclair (Cambridge) Ltd.	368, 369
Sinclair Radionics Ltd.	302, 303
Sound Systems of Suffolk	372
Surplustronics	320
Surplus Electronic Trading	366
Swanley Electronics	320
Teleradio	371, 372
Television Systems	367
Thacker, A. H. & Sons Ltd.	344
Tidman Mail Order	370
Trampus Electronic	359
Trannies	355
TUAC Ltd.	298
Tweedy Ltd. (J.A.)	370
Vero	366
Watford Electronics	375
West Hyde Developments Ltd.	355
Wheelhouse, C. W. & Son	290
Wilmslow Audio	316
Xeroza Radio	374
Yates Electronics	366
Z & I Aero Services Ltd.	376


Head Office and Warehouse  
44A WESTBOURNE GROVE  
LONDON W2 5SF  
Tel: 727 5641/2/3

## Z & I AERO SERVICES LTD.

Please send all correspondence and Mail-Orders to Head Office  
When sending cash with order, please include 0.15 in £ for postage and handling  
MINIMUM CHARGE 15p. No C.O.D. orders accepted

Retail Shop  
85 TOTTENHAM COURT ROAD  
LONDON W1  
Tel: 580 8403  
Open all day Saturday

### AC/DC MULTIMETER TYPE U4324

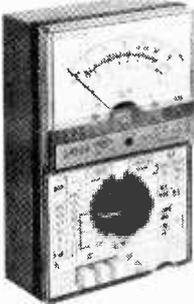

33 ranges up to  
3 Amps AC/DC;  
1200V DC, 900V  
AC, 500kΩ, +12  
db.

Sensitivity:  
20kΩ/V DC;  
4kΩ/V AC

Accuracy:  
±2.5% DC;  
±4% AC


Movement is protected by silicon  
diodes.

Dimensions 167 × 98 × 63 mm. Weight:  
1.5lb.

PRICE: complete with test leads,  
instruction manual and fibre-board  
storage case £9.25. Packing & carr.  
£0.50.

### MULTIMETER TYPE U4323

Sensitivity: 20,000Ω/V.

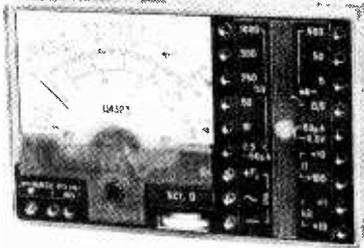

7 D.C. Voltage ranges 0.5-1000V  
6 A.C. Voltage ranges 2.5-1000V  
5 D.C. Current ranges 0.05-500mA  
4 Resistance ranges 1kΩ-1mΩ

Built-in oscillator providing AF output of  
1kHz and I.F. output of 465kHz with an ampli-  
tude of 1 volt minimum.

Dimensions: 140 × 87 × 40 mm. Weight 0.5kg

PRICE complete with leads and plastic  
storage case £7.70. Packing & postage £0.50

### AC/DC MULTIMETER TYPE U4313



39 ranges:  
600μA to 1.5A  
AC  
60μA to 1.5A DC  
75mV to 600V  
DC

1.5V to 600V AC  
1MΩ, 0.5μF, 12db

Accuracy: 1.5%  
DC; 2.5% AC  
Sensitivity: 20k  
Ω/V DC; 2kΩ/V  
AC

Mirror scale 86mm long.

Dimensions: 115 × 215 × 90 mm, Weight 3.3lb.

PRICE, complete with test leads, service  
manual and steel carrying case £12.50.  
Packing & carriage £0.50.

ALL THE ABOVE INSTRUMENTS FEATURE TAUT SUSPENSION MOVEMENTS  
PRICES ARE EXCLUSIVE OF V.A.T.

## SPARKRITE Mk II

Electronic Ignition...  
Better on all points  
Because you keep your points!

The SPARKRITE MK 2 is a full capacitive discharge electronic system  
Specifically designed to retain the points assembly with all the  
advantages and none of the disadvantages. No misfire because contact  
breaker bounce is eliminated electronically by a pulse  
suppression circuit which prevents the unit firing if the  
points bounce open at high rpm. Contact breaker burn is  
eliminated by reducing the current to about 1/50th of  
normal, thus avoiding arcing. But you can still revert  
to normal ignition if need be. In seconds. If points  
go (very unlikely) you can get replacements  
anywhere. All these advantages.

- Fitted in 15 minutes ● Up to 20% better fuel  
consumption ● Instant all weather starting ● Clean  
plugs they last 5 times longer without attention
- Faster acceleration ● Faster top speeds
- Cool and battery last longer ● Efficient fuel  
burning with less air pollution

The kit comprises  
everything needed

Ready drilled scratch and rust resistant case  
metalwork, cables, coil connectors, printed  
circuit board, top quality 5 year guaranteed  
transformer and components, full  
instructions to make positive or negative  
earth system, and 6 page installation  
instruction leaflet!

WE SAY IT IS THE BEST SYSTEM AT  
ANY PRICE!

#### PRICES

D11 Kit (incl. VAT and P & P)  
Ready Built Unit £14.85 incl. VAT and P & P  
(Both to fit all cars with coil distributor ignition up to  
8 cylinders)

We can supply units for any petrol engined vehicle (that  
motorcycle incl) with coil contact breaker ignition  
Details on request. Call in and see us for a demonstration

ELECTRONICS DESIGN ASSOCIATES  
(Dept P W 8) 82 Bath Street, Walsall WS1 3DE Phone 33652



### BAKER 12" MAJOR £11.55

30-14,500 cps. Double cone woofer and  
tweeter loudspeaker. Baker ceramic mag-  
net assembly, flux density 145,000 gauss.  
BASS RESONANCE 40 cps 20 watt RMS.

### MAJOR MODULE KIT £14.85

30-17,000 cps. woofer, tweeter, crossover  
and baffle as illustrated. Size 19in × 12½in.

NOTE—When ordering state 3 or 8 or 15 ohms.

#### BAKER LOUSPEAKERS 100% BRITISH MADE

Regent 12 in. 15W £10.45	Superb 12 in. 20W £18.70	New Group 50/12
Major 12 in. 20W £11.55	Group 25 12 in. 25W £10.45	12 in. 50W £17.60
Deluxe 12 in. 15W £18.20	Group 35 12 in. 35W £11.55	

#### BAKER LOUSPEAKER CO., BENSAM MANOR PASSAGE

THORNTON HEATH, SURREY Tel. 01-684 1665  
ALL PRICES INCLUDE V.A.T. HI-FI ENCLOSURE PLANS 42p

### FELSTEAD ELECTRONICS (PW82), LONGLEY LANE, GATLEY.

CHEADLE, CHESHIRE SK6 4EE

STYLII Replacements for virtually all ACOS, BSR, COLLARO, GARRARD, PHILIPS,  
RONETTE, SONOTONE. Single Tip: Sapphire 18p, Diamond 37p. Double Tip: Can be  
Stereo/LP+78 or ST/LP+ST/LP Sapphire 37p. Double Tip: Diamond ST/LP+Sapphire  
78 65p. Diamond ST/LP+Diamond ST/LP £1.25. For GOLDRING Diamond G800, G800H  
and G850 at £2.10 each. G800E at £4.10. FREE LIST (FOR SAE) FULL DETAILS  
STYLII AND CARTRIDGE EQUIVALENTS including SHURE, PICKERING, AUDIO-  
TECH, B & O., AND MANY MORE STYLII FOR MAGNETIC AND CRYSTAL  
PICK-UPS. Charges 10p any quantity.

CARTRIDGES. All with stylus and fittings. Replacements for ACOS GP/81 SC (Stereo-  
mono compatible series) at £1.05, GP93 Stereo at £1.45, GP94 Stereo Ceramic at £1.95;  
for RONETTE DC/4008CM (Speed change switch at front for GP67, TC8 & c.) at £1.25;  
for BSR X3H, X5H and X5M at £1.25 each, BX5H and BX5M at £1.70 each. TC8H at  
£1.50, TC8 Stereo, 3 pins, £2.15; charges 10p any quantity.

RECORDING TAPE. ALL FINEST BRITISH MYLAR: 5" 600 ft. 40p; 5" 900 ft. 55p;  
3½" 1200 ft. 75p; 7" 1800 ft. £1.05. Charges for 5" and 5½", 1-4, 13p each; 5 and over, 33p  
the lot. Charges for 7", 1-3 15p each, 4-5 25p the lot, 6 and over 40p the lot.  
SPEAKERS 2½", 3, 8 or 64 ohms (state which) 55p. Charges 10p each. 12" round, fitted  
cone tweeter, 6 watt, indistorted, 3, 8 or 15 ohms (state which) £2.40 (charges 35p);  
OR, PAIR FOR STEREO, £5.30 charges paid.

CONNECTING WIRE. Pkts. of 5 coils, asstd. coils, each 5 yds. Solid core 10p (10p charges)  
Flexible 21p (10p charges).

EARPIECES. Magnetic. 2.5 or 3.5mm plug (state which) 15p. CRYSTAL (3.5mm only)  
85p (all 10p up to 6).

VIBRATORS. 7 pin SYNCH. (12SR7 type) 75p, 4-pin NON-synch (121HD4) 45p (all  
10p each).

Send SAE for free stylus, cartridge and components list. All prices include VAT.

# FREE!

## Over 150 ways to engineer a better future

HIGHER PAY

A BETTER JOB

SECURITY

### find out how in just 2 minutes

That's how long it will take you to fill in the coupon. Mail it to B.I.E.T. and we'll send you full details and a free book. B.I.E.T. has successfully trained *thousands* of men at home - equipped them for higher pay and better, more interesting jobs. We can do as much for YOU. A low-cost B.I.E.T. home study course gets results fast - makes learning easier and something to look forward to. There are no books to buy and you can pay-as-you-learn.

Why not do the thing that really interests you? Without losing a day's pay, you could quietly turn yourself into something of an expert. Complete the coupon (or write if you prefer not to cut the page). No obligation and nobody will call on you . . . but it could be the best thing you ever did.

#### Others have done it, so can you

"Yesterday I received a letter from the Institution informing that my application for Associate Membership had been approved. I can honestly say that this has been the best value for money I have ever obtained" - a view echoed by two colleagues who recently commenced the course". - Student D.I.B., Yorks.

"Completing your course, meant going from a job I detested to a job that I love, with unlimited prospects". - Student J.A.O. Dublin.

"My training with B.I.E.T. quickly changed my earning capacity and, in the next few years, my earnings increased fourfold" - Student C.C.P., Bucks.

#### FIND OUT FOR YOURSELF

These letters - and there are many more on file at Aldermaston Court - speak of the rewards that come to the man who has given himself the specialised know-how employers seek. There's no surer way of getting ahead or of opening up new opportunities for yourself. It will cost you a stamp to find out how we can help you. Write to B.I.E.T. Dept. BPW01 Aldermaston Court, Reading RG7 4PF.

Practical Radio & Electronics Certificate course includes a learn while you build **3 transistor radio kit.**

Everything you need to know about **Radio & Electronics** maintenance and repairs for a **spare time income** and a **career** for a better future.



**CUT OUT THIS COUPON**  
Tick or state subject of interest.  
Post to address below.

<input type="checkbox"/> MECHANICAL	<input type="checkbox"/> DRAUGHTSMANSHIP	<input type="checkbox"/> A.B.T. Clerk of Works
<input type="checkbox"/> Society of Engineers—	<input type="checkbox"/> Institute of Engineering Designers (A.M.I.E.D.)	<input type="checkbox"/> Construction Surveyors Institute—L.C.S.I.
<input type="checkbox"/> A.M.S.E. (Mech.)	<input type="checkbox"/> General Draughtsmanship	<input type="checkbox"/> CITY & GUILDS General Building (all branches)
<input type="checkbox"/> Institute of Engineers & Technicians (A.M.I.E.)	<input type="checkbox"/> Elec. Draughtsmanship	<input type="checkbox"/> Heating & Vent. Inst. Clerk of Works
<input type="checkbox"/> CITY & GUILDS Gen. Mech. Eng. Maintenance Eng.	<input type="checkbox"/> Welding	<input type="checkbox"/> Technical Drawing
<input type="checkbox"/> Gen. Diesel Eng.	<input type="checkbox"/> Sheet Metal Work	<input type="checkbox"/> Eng. Inspection
<input type="checkbox"/> Eng. Metallurgy	<input type="checkbox"/> ELECTRICAL & ELECTRONIC	<input type="checkbox"/> Society of Engineers—
<input type="checkbox"/> A.M.S.E. (Elec.)	<input type="checkbox"/> CITY & GUILDS	<input type="checkbox"/> Gen. Electrical Engineering
<input type="checkbox"/> Electrical Installations	<input type="checkbox"/> Electrical Maths	<input type="checkbox"/> Computer Electronics
<input type="checkbox"/> Electronic Eng.	<input type="checkbox"/> Practical Radio & Electronics (with kit)	<input type="checkbox"/> MANAGEMENT & PRODUCTION
<input type="checkbox"/> Institute of Cost & Management	<input type="checkbox"/> Accnts.	<input type="checkbox"/> Computer Programming
<input type="checkbox"/> Works M'ment.	<input type="checkbox"/> Work Study	<input type="checkbox"/> Gen. Production Eng.
<input type="checkbox"/> Estimating & Planning	<input type="checkbox"/> Storekeeping	<input type="checkbox"/> Management Skills
<input type="checkbox"/> Quality Control	<input type="checkbox"/> AUTOMOBILE & AERONAUTICAL	<input type="checkbox"/> Institute of the Motor Industry
<input type="checkbox"/> A.M.I.	<input type="checkbox"/> MAA/IMI	<input type="checkbox"/> CITY & GUILDS Auto Eng.
<input type="checkbox"/> Gen. Auto Eng.	<input type="checkbox"/> Motor Mechanics	<input type="checkbox"/> Auto Diesel Eng.
<input type="checkbox"/> Garage M'ment.	<input type="checkbox"/> ARB Aero Engineering Certs.	<input type="checkbox"/> Gen. Aero Eng.
<input type="checkbox"/> CONSTRUCTIONAL	<input type="checkbox"/> Society of Engineers—	<input type="checkbox"/> A.M.S.E. (Civ.)
<input type="checkbox"/> Institute of Building—L.I.O.B.	<input type="checkbox"/> Supplementary courses for Nat. Certificates.	<input type="checkbox"/> G.C.E. - choose from 58 'O' & 'A' level subjects.
<input type="checkbox"/> Coaching for many exams, including C & G		

## POST TODAY FOR A BETTER TOMORROW

To B.I.E.T., Dept. BPW01 Aldermaston Court, Reading RG7 4PF

NAME \_\_\_\_\_  
Block Capitals Please  
ADDRESS \_\_\_\_\_

OTHER SUBJECTS \_\_\_\_\_

Accredited by C.A.C.C. Member of A.B.C.C.

**BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY**

# Henry's

**DON'T RELY ON YOUR MEMORY  
BUY NOW AT BARGAIN PRICES**  
Hi Fi and Transistors - Up to date  
Brochures on request

**HENRY'S  
CATALOGUE**  
Due to rapid price changes,  
shortages of paper and raw  
materials, all prices in the  
existing catalogues no longer  
apply. Call or phone for latest  
prices. A new catalogue will  
be available for Aug/Sept. 1974

130 WOVE




You pay less  
VAT with Henry's  
Low Prices

## BUILD THE TEXAN

Now built and used by thousands of satisfied customers. Features slim design overall size in cabinet 15 1/2" x 2 1/2" x 6 1/2", 6-IC's, 10 transistors, stabilisers Gardners low field transformer. Fibre Glass PC Panel, complete chassis work. Now available built and tested as well as in kit form. **HIGH QUALITY & STABILITY ARE PREDOMINATE FEATURES** - DEVELOPED BY TEXAS ENGINEERS FOR PERFORMANCE, RELIABILITY AND EASE OF CONSTRUCTION. FACILITIES: On/Off switch indicator, headphones socket, separate treble, bass, volume and balance controls, scratch and rumble filters, mono/stereo switch, input selector: Mag. P.U., Radio Tuner, Aux. Can be altered for Mic., Tape, Tape-head, etc. Construction details Ref. No. 21

### 20 + 20 WATT IC STEREO AMPLIFIER

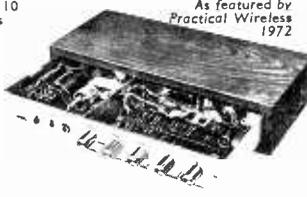

As featured by Practical Wireless 1972  
KIT PRICE **£28.50** (+VAT +50p carr/packing) or built and tested **£35.00** (+VAT +50p carr/packing) as illustrated.

## BUILD THE NEW HENELEC STEREO FM TUNER


A completely new high stability stereo FM tuner. Features variable capacity diode tuning, stabiliser power supply, IC Decoder, high gain low noise, IF stages, LED indicators. Tuning meter, AFC, easy to construct and use. Mains operated. Slim modern design with fibre glass PC, teak cabinet, etc. Available as a kit to build or ready built. Overall size 8" x 2 1/2" x 6 1/2". Produced to give high performance with a realistic price. (Parts list and constructional details Ref. No. 530p) Henry's are sole distributors UK and Europe.



KIT PRICE **£21.00** (+VAT) or built and tested **£24.95** (+VAT)
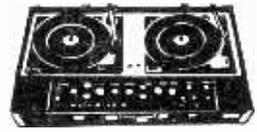
## EARN YOURSELF EASY MONEY, WITH PORTABLE DISCO EQUIPMENT

- DISCO MINI** A complete portable disco, fitted mixer preamp, 2 decks all facilities. **£98.50**  
As above but with Slider Controls **£118.50**  
100 watt amplifier for above **£49.50**  
**SDL5** 100 watt mixer/amplifier with slider controls **£69.00**  
**R50** 50 watt mixer/amplifier **£49.50**  
**R100** 100 watt mixer/amplifier **£57.50**  
**DISCO AMP** 100 watt mixer/amplifier **£73.00**  
**Northcourt:**  
400 40 watt mixer/amp **£37.50**  
800 80 watt mixer/amp **£45.00**  
**DISCO MIXER/PREAMPLIFIERS**  
(OP for up to 6-1000 watt amplifiers)  
**SDL1** (rotary controls) **£49.50**  
**SDLII** (slider controls) **£58.50**  
**DISCO VOX** (slider controls) the complete disco preamp **£72.00**  
**DJ100** 100 watt power amplifier for above **£49.50**  
**DJ30L** Mk II 3 channel 3kw sound to light **£41.25**  
**DJ30L** Mk III slider controls **£45.50**  
**DJ DISC LITE** as 30L-2 plus variable speed flashes **£54.00**  
**Carlsbro** Reverberation Unit **£44.00**  
Disco anti-feedback microphone **£11.95**  
Cote 150 watt liquid wheel projector **£23.50**  
150 watt QI liquid wheel projector **£50.00**  
150 watt QI cassette wheel projector **£50.00**  
Spare Effects and liquid cassettes large range of patterns **£6.00**  
6 inch Liquid wheels **£5.00**  
Various cassettes **£6.00**  
Mini spot bank fitted 3 lamps **£12.95**  
Auto Trilite (mini with flashers) **£17.00**  
Bubblemaker with liquid **£22.50**  
**MIXERS/MICS/SPEAKERS/LIGHTING**  
U.K.'s largest range of Disco Lighting. **FREE STOCK LIST REF. NO. 18 ON REQUEST.**  
**AKG / RESLO / DJ / CARLSBRO / EAGLE MICS., STANDS, MIXERS, CABINETS, CHASSIS AND COMPLETE SPEAKER SYSTEMS, MEGAPHONES, TABLES, PUBLIC ADDRESS COMPLEMENTS.**



All prices carr. paid (UK) (VAT EXTRA). Barclaycard/Access call, write or phone your order 01-723-6963—easy terms for callers.

## EXCLUSIVE DECCA KELLY SPEAKERS



12 watt speaker Tweeter systems. 8" Bass/Midrobe and Melinex Domed HF radiator plus crossover **£12.50** per pair of systems (carr./packg. 40p) or built into veneered cabinets, size 18 x 12 x 6 1/2" **£19.50** pair (carr. £1).

## HI-FI TAPE EQUIPMENT



U.K.'s largest range with discounts and demonstrations for callers. Latest stock lists on request (Ref. No. 17). Phone 01-402-4736 for Barclay/Access Card. Direct orders and latest prices.

## TRANSISTORS/SEMI-CONDUCTORS

U.K.'s largest range for every application. Small quantity discounts. Also Trade. Export and industrial enquiries invited. Latest stock list (Ref. No. 36) including valves on request.

## ELECTRONICS SUPPLIES

Specialists in electronics for more than 30 years. Trade and industry supplies—every type of component and equipment.

## NEW SINCLAIR PROJECT 80



- Stereo Pre-Amplifier **£11.95**
- Audio Filter Unit **£6.95**
- Z40 15 Watt Amplifier **£5.45**
- Z60 25 Watt Amplifier **£6.95**
- PZ5 Mod. for 1 or 2 Z40 **£4.98**
- PZ6 Mod. (S Tab) 1 or 2 Z40 **£7.98**
- PZ8 Mod. (S Tab) 1 or 2 Z60 **£7.98**
- TRANSFORMER FOR PZ8 **£3.95**

**NEW FM TUNER** **£11.95**  
**STEREO DECODER** **£7.45**  
All items post paid.

## LIVING SOUND LOW NOISE TOP QUALITY CASSETTES MADE BY EMI TAPES LTD. TO INTERNATIONAL STANDARDS ESPECIALLY FOR HENRY'S. ALL STOP PAID LESS THAN 1/2 REC. PRICES COMPLETE WITH LIBRARY CASES

C 60	3 for	6 for	10 for	25 for
C 90	£1.10	£1.98	£3.00	£7.40
C 120	£1.46	£2.80	£4.60	£11.25
	£1.80	£3.45	£5.45	£13.45

Quantity and trade enquiries, invited  
LEARN A LANGUAGE—complete with phrase book. German — French — Spanish — Italian **£1.36** per course. **£5** for any 4.



## LOW COST HI-FI SPEAKERS

**SPECIAL OFFERS**  
EMI 13" x 8" full range speakers (post 20p each or 30p pair)  
\*150TC—8 ohms Twin Cone 10 watt **£2.20** each or **£4.00** pair.  
\*450 10 watt C/o Twin Tweeters 3, 8 or 15 ohms **£3.85** each  
EW 15 watt 8 ohms C/o Tweeter **£5.25** each or **£7.40** pair  
350 20 watt C/o Tweeters 8 or 15 ohms **£7.80** each  
\* Polished wood cabinet **£4.80** post 35p.



8 ohms full range (post 20p)			
FR4	4"	5 watt	<b>£4.75</b>
FR5	6 1/2"	10 watt	<b>£6.30</b>
FR8	8"	15 watt	<b>£8.50</b>
FR23	9 x 6"	15 watt	<b>£8.40</b>
BASS & MID RANGE—8 ohms (post 20p)			
AA12	5"	15 watt	<b>£3.75</b>
B110	5 1/2"	15 watt	<b>£7.20</b>
B200	8"	15 watt	<b>£8.50</b>
B139/2	13" x 8"	30 watt LF	<b>£13.75</b>
TWEETERS AND CROSSOVERS (post 20p)			
K2000	10 watt	8 or 15 ohms	<b>£2.10</b>
FHT6	15 watt	8 ohms	<b>£3.35</b>
K2011	30 watt	8 ohms	<b>£4.80</b>
T27	KEF		<b>£5.50</b>
Axcent 100	30 watt	8 ohms	<b>£5.50</b>
K4009	1k Hz/5k Hz C/o		<b>£3.30</b>
SN75	3k Hz var. C/o		<b>£2.70</b>
SPEAKER KITS (carr. etc. 35p)			
20-2	8"	30 watt	<b>£24.50</b> pair
20-3	8"	40 watt	<b>£35.95</b> pair
LINTON 2		20 watt	<b>£18.30</b> pair
GLENDALE 3		30 watt	<b>£32.95</b> pair
DOVEDALE 3		50 watt	<b>£51.50</b> pair
KEF KK2			<b>£55.00</b> pair
KEF KK3			<b>£78.00</b> pair

## BUILD YOURSELF A POCKET CALCULATOR

A complete kit, packaged in a polystyrene container and taking about 3 hours to assemble—this is the Sinclair Cambridge pocket calculator from Henry's. Some of the many features include interface chip, thick-film resistor pack, printed circuit board, electronic components pack. Size 4 1/2" long x 2" wide x 1 1/2" deep. Free of charge with the kit for the more advanced technologist is a 32-page booklet explaining how to calculate Logs, Tangents, Sines etc.



**SPECIAL OFFER**  
**£13.60** Also available assembled ready to use. **£19.95** + VAT.

10% VAT to be added to all orders. Export supplied. Prices and descriptions correct at time of proof. Subject to change without notice. E & O. ALWAYS BARGAINS FOR CALLERS.

**Henry's RADIO LIMITED**  
EDGWARE ROAD, LONDON W2

404-406 Electronic Components and Equipment 01-402 8381  
308 PA - Disco - Lighting High Power Sound 01-723 8863  
303 Bargains Store (Callers only)  
Home and Car Entertainment Centres: London and branches now open  
120 Shaftesbury Avenue, London W1 01-437 9692  
144 Burnt Oak Broadway, Burnt Oak, Edgware 01-952 7462  
190-194 Station Road, Harrow, Middlesex 01-663 7788/9  
354-356 Edgware Road, London W2 01-402 8554/4736

All mail to  
303 Edgware Road,  
London W2 1BW  
All stores open 9 am to  
6 pm six days a week  
Hi-Fi - Tape Equipment  
Discount Stock List  
Free at all stores