

# PRACTICAL WIRELESS

DECEMBER  
1974

25p



## PW 'KEMPTON' CAR STEREO CASSETTE PLAYER

PART 1



Also:-  
INEXPENSIVE CAPACITY BRIDGE  
THIRD SECTION OF P.W. BUYERS' GUIDE 74/5

# NEW EDU-KIT MAJOR

Completely Solderless Electronic Construction Kit  
Build these projects without soldering iron or solder


- ★ 4 Transistor Earpiece Radio.
- ★ 5 Transistor Push Pull Amplifier.
- ★ Batteries Crystal Radio.
- ★ Signal Tracer.
- ★ 7 Transistor Loudspeaker Radio MW/LW.
- ★ One Trilaterator Radio
- ★ Signal Injector.
- ★ 5 Transistor Short Wave Radio.
- ★ 2 Transistor Regenerative Radio.
- ★ Transistor Tester NPN-PNP
- ★ Electronic Metronome.
- ★ 3 Transistor Regenerative Radio.
- ★ 4 Transistor Push Pull Amplifier.
- ★ Electronic Noise Generator.
- ★ Audible Continuity Tester.
- ★ Sensitive Pre-Amplifier.

**Total Building Costs**  
**£7.23**  
P & Ins. 14p  
(Overseas P & P £1.85)  
(+ 8% VAT 57p)

Components Include: 24 Resistors • 21 Capacitors • 10 Transistors • 3 1/2" Loudspeaker • Earpiece • Mica Baseboard • 3 12-way connectors • 2 Volume controls • 2 Slider Switches • 1 Tuning Condenser • 3 Knobs • Ready wound MW/LW/SW Coils • Ferrite Rod • 6 1/2 yards of wire • 1 Yard of sleeving etc. • Parts Price List and Plans 50p. (Free with parts).

## NEW ROAMER NINE

WITH V.H.F. INCLUDING AIRCRAFT

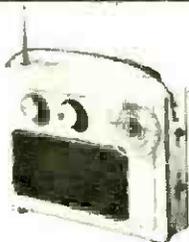

9 Tunable wavebands as Roamer Ten. Built in ferrite rod aerial for MW/LW. Retractable chrome plated telescopic aerial for V.H.F. and 9W. Push Pull output using 600mW transistors, 9 Transistors and 3 diodes, tuning condensers with V.H.F. section, retrograde coil for aircraft, moving coil loudspeaker, volume ON/OFF and wavechange controls. Attractive all white case with red grille and carrying strap. Size 9 1/2" x 7" x 2 1/2" approx. Parts Price List and Plans 40p (Free with parts).

**Total Building Costs** **£6.95**  
P & Ins. 44p  
(Overseas P & P £1.85)  
(+ 8% VAT 56p)

## NEW Everyday Series

Build this exciting New series of designs



E.V.5. 5 Transistors and 2 diodes. MW/LW. Powered by 41 volt battery. Ferrite rod aerial, tuning condenser, volume control, and now with 3" loudspeaker. Attractive case with red speaker grille. Size 9" x 5 1/2" x 2 1/2" approx. Parts Price List and Plans 20p. Free with parts.

**Total Building Costs** **£2.95**  
P & Ins. 30p  
(+ 8% VAT 23p)  
(Overseas P & P £1.25)

E.V.6. Case and looks as above. 6 Transistors and 3 diodes. Powered by 9 volt battery. Ferrite rod aerial, 3" loudspeaker, etc. MW/LW coverage. Push Pull output. Parts Price List and Plans 30p. Free with parts.

**Total Building Costs** **£3.60**  
P & Ins. 30p  
(+ 8% VAT 29p)  
(Overseas P & P £1.25)

E.V.7. Case and looks as above. 7 Transistors and 3 diodes. With a variable MW/LW. Trilaterator Hand, 8x3 SW2, SW3, powered by 9 volt battery. Push Pull output. Telescopic aerial for short waves. 3" Loudspeaker. Parts Price List and Plans 30p. Free with parts. Overseas P & P £1.60.

**Total Building Costs** **£4.08**  
P & Ins. 31p  
(Overseas P & P £1.85)  
(+ 8% VAT 32p)

## ROAMER EIGHT Mk I

NOW WITH VARIABLE TONE CONTROL




7 Tunable Wavebands MW1, MW2, LW, SW1, SW2, SW3 and Trilaterator Hand. Built in Ferrite Rod Aerial for MW and LW. Chrome plated Telescopic aerial can be angled and rotated for peak short wave listening. Push pull output using 600mW transistors. Car aerial and tape record sockets. Selectivity switch. 6 transistors plus 3 diodes. Latest 4 1/2 watt ferrite magnet loudspeaker, air spaced tuned tuning condenser. Volume on/off, tuning, wave change and tone controls. Attractive case in red chestnut shade with gold blocking. Size 9 x 7 x 2 1/2 in. approx. Easy to follow instructions and diagrams. Parts Price List and Plans 50p (FREE with parts).

**Total building costs** **£6.98**  
P & Ins. 47p  
(Overseas P & P £1.85)  
(+ 8% VAT 59p)

## ROAMER TEN

WITH V.H.F. INCLUDING AIRCRAFT

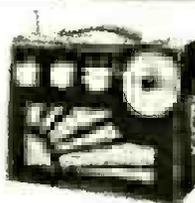

10 Transistors. Latest 4 1/2 watt Ferrite Magnet Loudspeakers. 9 Tunable Wavebands, MW1, MW2, LW, SW1, SW2, SW3. Trilaterator Hand, V.H.F. and Local Stations also Aircraft Band.

Built in Ferrite Rod Aerial for MW/LW. Chrome plated 7 section Telescopic aerial, can be angled and rotated for peak short wave and V.H.F. listening. Push Pull output using 600mW Transistors. Car Aerial and Tape Record Sockets. 10 Transistors plus 3 Diodes. Air spaced Tuning Condenser with V.H.F. section. Separate coil for Aircraft band. Volume on/off. Wave Change and tone Controls. Attractive Case in black with silver blocking. Size 9 1/2" x 7" x 2 1/2" approx. Easy to follow instructions and diagrams. Parts Price List and Plans 50p (FREE with parts).

**Total building costs** **£8.50**  
P & Ins. 50p  
(Overseas P & P £1.85)  
(+ 8% VAT 68p)

## POCKET FIVE

NOW WITH 3" LOUD-SPEAKER



5 Tunable wavebands, M.W. LW, and Trilaterator Hand. 7 transistors and 2 diodes, super-sensitive ferrite rod aerial, attractive black and gold case. Size 4 1/2" x 1 1/2" x 5 1/2" approx. Plans and Parts Price List 20p (Free with parts).

**Total Building Costs** **£2.50**  
P & Ins. 26p  
(Overseas P & P £1.20)  
(+ 8% VAT 20p)



## TRANSONA FIVE NOW WITH 3" LOUDSPEAKER


Wavebands, transmitter and speaker as Pocket Five. Larger Case with Red Speaker Grille and Tuning Dial. Plans and Parts Price List 20p (Free with parts).

**Total Building Costs** **£2.75**  
P & Ins. 50p  
(+ 8% VAT 21p)
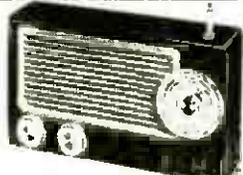
## TRANS EIGHT 8 TRANSISTORS and 3 DIODES

8 Tunable Wavebands: MW, LW, SW1, SW2, SW3 and Trilaterator Hand. Sensitive ferrite rod aerial for M.W. and L.W. Telescopic aerial for Short Waves. 3in. Speaker. 8 improved type transistors plus 3 diodes. Attractive case in black with red grille, dial and black knobs with polished metal inserts. Size 9 x 5 1/2 x 2 1/2 in. approx. Push pull output. Battery economiser switch for extended battery life. Ample power to drive a larger speaker. Parts price list and Plans 35p (FREE with parts).

**Total building costs** **£4.48**  
P & Ins. 33p  
(+ 8% VAT 36p)  
(Overseas P & P £1.55)



## ROAMER SIX

CASE AND LOOKS AS TRANS-EIGHT

6 Tunable Wavebands: MW, LW, SW1, SW2, etc. Sensitive ferrite rod aerial and telescopic aerial for Short Waves. 3in. Speaker. 8 stages - 6 transistors and 3 diodes. Attractive black case with red grille. Dial and black knobs with polished metal inserts. Size 9 x 5 1/2 x 2 1/2 in. approx. Plans and Parts price list 35p (FREE with parts).

**Total building costs** **£3.98**  
P & Ins. 31p  
(Overseas P & P £1.85)  
(+ 8% VAT 32p)

## "EDU-KIT"



Build Radio-Amplifier, etc. from easy stage diagrams.

Five units including master unit to construct

Components include:

Tuning Condenser; 2 Volume Controls; 2 Slider Switches; Two 1000 3" Matching Coil Makers; Terminal Strip; Ferrite Rod Aerial; Battery Clips; 4 Test Boards; 10 Transistors; 4 Diodes; Resistors; Capacitors; Three 3" Coils. Only once constructed are detachable from Master Unit, enabling them to be stored for future use. Ideal for Schools, Educational Authorities and all those interested in radio construction. Parts price list and plans 40p (FREE with parts).

**Total building costs** **£5.50**  
P & Ins. 33p  
(Overseas P & P £1.85)  
(+ 8% VAT 44p)

## RADIO EXCHANGE LTD

★ Callers visit attractive "Lavelle's" shop.  
★ Open 10-1, 2.30-4.30. Mon.-Fri. 9.15-8.15.

To RADIO EXCHANGE CO., 61a HIGH STREET, BEDFORD, MK40 1SA  
Tel.: 0834 62367. Ref. No. 78837R.

I enclose £..... for .....

Name .....

Address .....

(Dept. PW12.)

# PRACTICAL WIRELESS

VOL. 50 NO. 8  
ISSUE 814  
DECEMBER 1974

BRITAIN'S PREMIER MAGAZINE FOR THE DO-IT-YOURSELF RADIO AND ELECTRONICS CONSTRUCTOR

## EDITOR

Lionel E. Howes, G3AYA

## ASSISTANT EDITOR

Eric Dowdeswell, G4AR

## ART EDITOR

Peter Metall

## PRODUCTION & NEWS

EDITOR Colin R. Riches

## PROJECTS SUB-EDITOR

Geoffrey C. Arnold

## TECHNICAL ARTIST

Alan Martin

## SECRETARIAL

Susan King

01-634 4292

## ADVERTS. MANAGER

01-634 4293

Roy Smith

## CLASSIFIED ADVERTS.

01-634 4301

Colin R. Brown

Published by IPC Magazines Ltd.,  
Feelway House, Farringdon Street,  
London EC4A 4AD. Tel. 01-634 4444

## SUBSCRIPTIONS

Publisher's Subscription Rate for one year to the UK is £3.25 and to the rest of the world £4.35 including postage. Enquiries to Subscription Department, IPC Magazines Ltd., Carlton House, 68 St. Queen Street, London, WC2 8DD. Phone 01-242 4477. International Giro facilities Account No. 5122007. Please state reason for payment "message to payee". Binders (£1.34) and indexes 30p (inc. VAT) can be supplied by the Binders Dept at the same address.

## BACK NUMBERS

We regret that we are unable to supply back numbers of Practical Wireless. Readers are recommended to enquire at a public library to see copies. Requests for specific back numbers of Practical Wireless and Television only can be published in our CQ Column.

## COPYRIGHT AND QUERIES

© IPC Magazines Limited 1974. Copyright in all drawings, photographs and articles published in "Practical Wireless" is fully protected and reproduction or imitation in whole or in part is expressly forbidden. All reasonable precautions are taken by "Practical Wireless" to ensure that the advice and data given to readers are reliable. We cannot, however, guarantee it and we cannot accept legal responsibility for it. Prices are those current as we go to press. We regret that we cannot answer technical queries by telephone nor can we provide information or advice on manufacturers' products other than that given in the magazine. We will endeavour to assist readers who have queries relating to articles published but we cannot offer advice on modifications to our published designs. All correspondents expecting a reply should enclose a stamped addressed envelope.

## ● NEWS & COMMENT

702 CHIPS UNLIMITED!—Leader article

703 NEWS ... NEWS ... NEWS ...

709 TELEVISION—Coming in the December issue

710 HOTLINES on recent developments by Ginsberg

725 NEXT MONTH IN PRACTICAL WIRELESS

742 PRODUCTION LINES Products reviewed by Colin Riches

748 ON THE AIR

748 Amateur Bands—Eric Dowdeswell, G4AR

749 Broadcast Bands—Medium Wave—Charles Molloy

—Short Wave—Derek Bell

## ● CONSTRUCTIONAL

706 INEXPENSIVE CAPACITY BRIDGE—Eric Dowdeswell, G4AR

713 MAKE YOUR OWN PCBs—John Jackson

717 ADD-ON BEAT FREQUENCY OSCILLATOR—F. G. Rayer, G3OGR

721 ANOTHER BATTERY SAVER—Arthur Dow

726 P.W. 'KEMPTON'—CAR STEREO CASSETTE PLAYER—PART 1  
—Keith Cummins & Tony Francis

732 TAKE 20 No. 66 IC PHOTO TRIGGER—David Andrews

733 P.W. "SANDOWN" FM STEREO TUNER—PART 3—J. R. W. Ames  
B.Sc. and M. J. Carey, B.Sc.

738 EXPERIMENTAL WORKSHOP Phase Shift Circuits—M. J. Hughes,  
M.A., C.Eng. MIERE.

744 2W I.C. AUDIO AMPLIFIER—R. A. Penfold

## ● OTHER FEATURES

704 SPECIAL PRODUCT REPORT—R-T-V C 'TOURIST' II Car Radio Kit

709 TECHNICROSS SOLUTION No.7


736 IC OF THE MONTH—SGS TBA790 Audio Power Amplifier.

747 GOING BACK—Equipment of yesteryear—Colin Riches

FREE PRACTICAL WIRELESS SCREWDRIVER (page 702)  
PLUS BUYERS' GUIDE to Radio and Electronic Components—PART 3

# ADCOLA

ELECTRICAL SOLDERING INSTRUMENTS

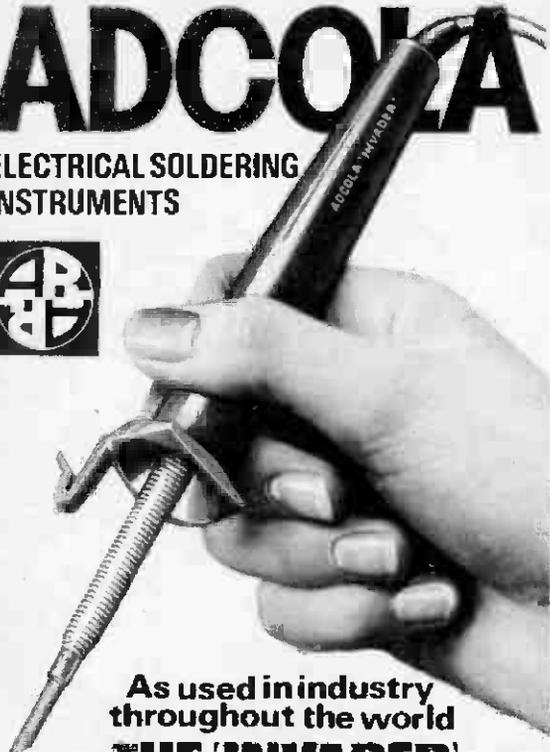

As used in industry throughout the world  
**THE 'INVADER'**

BRITISH MADE, HAND BUILT, PRECISION INSTRUMENT

'Invader' low leakage, high efficiency professional soldering instruments as used in industry worldwide, and why not you! Precision designed handle moulded of flame resistant material (SEI) and European safety standards. Stainless steel construction throughout with elements precision wound, earthed at two points, test run and finally flash tested at 2,000 v A/c. Low cost internally fitted bits with large range of bit faces for your future use. Can you afford not to have the 'Invader'.

MODEL 706 £2.88, 646 £3.13, 1076 £3.22  
1" Bit 19watt      3/4" Bit 23watt      1/2" Bit 27watt



## ADCOLA MULTI-CHANNELLED SOLDER IN HANDY SIZES!

Adcola have designed solder packs to fulfil all your needs—manufactured to B.S.I. 44.1 60/40/18 swg. Multi channelled resin cored. If your need is small the dispenser or the three oz reel will do you if you are keener try the 1/2 kilo reel.

Dispenser 08p. 3oz 57p. 1/2 Kilo £2.58

**It makes sense to use the best! post your coupon now**

ADCOLA PRODUCTS LTD. GAUDEN RD.  
LONDON SW4 6LH  
VAT Regd. No 235 6153 72      Regd No 442762

Please send me  
MODEL 706      MODEL 646      MODEL 1076

SOLDER Dispenser      3oz REEL      1/2 Kilo REEL

Price include VAT. Add 10p for postage and packing  
Inclosing P.O. cheque for £

NAME \_\_\_\_\_

ADDRESS \_\_\_\_\_

PWT

678

**NEW**

**PRACTICAL PAPERBACKS FROM FOULSHAM-TAB**

**BASIC TV COURSE**  
by George Kravitz      £1.50

**NEW SKILL-BUILDING TRANSISTOR PROJECTS AND EXPERIMENTS**  
by Louis E. Gardner Jr.      £1.45

**RADIO CONTROL HANDBOOK**  
by Howard G. McEntee      £1.90

**TRANSISTORS: THEORY AND PRACTICE**  
by Rufus P. Turner      £1.40

**WORKING WITH SEMICONDUCTORS**  
by Albert C. W. Saunders      £1.50

**CASSETTE TAPE RECORDERS—HOW THEY WORK—CARE & REPAIR**  
by Walter Salm      £1.60

**ELECTRONIC MEASUREMENTS SIMPLIFIED**  
by Clayton Hallmark      £1.70

**SOLID-STATE CIRCUITS GUIDEBOOK**  
by Brice Ward      £1.75

**10 MINUTE TEST TECHNIQUES FOR PC SERVICING**  
by Arc Margolis      £1.60

**TV BENCH SERVICING TECHNIQUES**  
by Arc Margolis      £1.65

**MINIATURE PROJECTS FOR ELECTRONIC HOBBYISTS**  
by Ken W. Sessions Jr.      £1.45

**FM STEREO/QUAD RECEIVER SERVICING MANUAL**  
by Joseph J. Carr      £1.55

**TROUBLESHOOTING SOLID-STATE WAVE GENERATING AND SHAPING CIRCUITS**  
by Ben Gaddis      £1.55

**THE 2-METRE FM REPEATER CIRCUITS HANDBOOK**  
by Ken W. Sessions      £1.90

**PINPOINT TRANSISTOR TROUBLES IN 12 MINUTES**  
by Louis E. Gardner Jr.      £1.50



**FOULSHAM-TAB LTD.**  
YEovil ROAD, SLOUGH, BUCKS.

**CJL PRICES INCLUDE P&P AND V.A.T.**

**COMBINATION TRY & MITRE SQUARE** (Ranone Chesterman), Cabinet/chassis work. Try & Mitre Square. Depth, Height & Marking Gauges. 300mm/12" Rule. Spirit Level & Steel Scriber.      £1.85

**HAND DRILL** (Leybold), Compact precision drill. 5/16" (8mm) chuck. Gears totally enclosed.      £2.90

### INTEGRATED CIRCUITS

VOLTAGE REGULATOR (Fairchild)      uA7805      £1.70  
 VOLTAGE REGULATOR (Signetics)      NE550A      £0.80  
 AUDIO POWER AMPLIFIER (National)      LM380      £1.00  
 A.M. RADIO RECEIVER (RCA)      CA3123E      £1.40  
 F.M. STEREO DECODER (Motorola)      MC1310P      £2.80  
 I/C TIMER (Signetics)      NE555V      £0.78

### DUAL IN LINE SOCKETS

8 pin (Pk of 3)      £0.50      14 pin (Pk of 3)      £0.55

KEYNECTOR, rapid connect/disconnect to mains. Built-in piano switches, neon & 13A fuse.      £3.20

LOCKFLEX RULE (RCF), 3m/10ft precision rule. Blade length lockable—power return.      £0.93

SOLDERING IRON, 25 WATT (Analex), x25, 220/240V. Low leakage. 1/8" bit (interchangeable).      £1.85  
3/32" bit      £0.45      3/16" bit      £0.45      Element      £0.95

SOLDERING IRON STAND (Analex), Model ST3.      £0.95

TRIMMING KNIFE (RCF), New style, Retractable, 5 heavy duty blades. Ident. co-axial cables.      £0.65

SILICON BRIDGE RECTIFIER, 100 P.I.V./2A      £0.40

ELECTROLYTIC CAPACITOR, 2,200µF/50V      £0.57

ELECTROLYTIC CAPACITOR, 5,000µF/25V      £0.63

SILICON POWER TRANSISTOR, 2N3055      £0.60

Please tick box. Crossed cheque/P.O. for £..... enclosed

NAME \_\_\_\_\_

ADDRESS \_\_\_\_\_

**CJL**

CJL LTD. P.O. BOX 34, CANTERBURY, KENT.



and make no mistake

**AUDIOTRONIC Model ATM1**  
Top value 1,000 ohm pocket multi-range meter. Range: 0.1/10/50/250/1,000 volt AC and DC. DC current 0.1mA/100mA. Resistance: 0.150k ohms. Decibels: -10 to +22dB. Size 90 x 68 x 29mm. Complete with test leads.  
**OUR PRICE £3.25** P&P 15p



**AUDIOTRONIC Model ATMS**  
Jewell mounted attractively moulded case with edgewise ohms adjustment. Range: 0.1/15/150/300/1200V AC. (2500 ohm). 0.5/10/30/300/600V DC. (15000 ohm). 0.300 uA/0.300mA DC. Resistance, a 10 x 100, -10 to +10dB. Supplied with battery test leads and data booklet. Size 121 x 73 x 29mm.  
**OUR PRICE £3.95** P & P 20p



**MODEL TH12**  
20,000 ohm. Overload protection. Slide switch selector. 0/0.25/2.5/10/50/160/1000V DC. 0/10/50/250/1000V AC. 0/50 uA/25/150mA DC. 0/3k/30k/300k/3 Megohms. -20 to +50dB.  
**OUR PRICE £5.95** P&P 30p



**HIDKI 720X VOM**  
A versatile, accurate measuring instrument. 20,000 ohm. 0/5/25/100/500V DC. 0/10/50/250/1000V AC. 0/50 uA/50mA. 0/20k/2 Megohms.  
**OUR PRICE £5.97** P&P 30p



**MODEL PL436**  
30,000 ohm. AC. 8000 ohm AC. Mirror scale. 6/1/2/30/120/600V DC. 3/30/120/600V AC. 50/500uA/50mA. -10/100k/1 Meg/10 Meg Ohm. -20 to +48 dB.  
**OUR PRICE £6.97** P&P 30p



**U4323 MULTIMETER**  
20,000 ohm. Simple unit with auto/IF oscillator. Suitable for general receiver tuning. Range: 0.5/2.5/10/50/250/1000V DC. 2.5/10/50/250/1000V AC. 0.05/0.5/5/50/500mA DC. Resistance, x10, x100, x1,000, x10,000 (50k, 500k, 5k). (50k) centre scale. Battery operated. Size 180 x 97 x 40mm. Supplied in carrying case complete with test leads.  
**OUR PRICE £7.70** P&P 30p



**HIDKI 730X**  
30,000 ohm. Overload protection. 6/30/60/300/600/1200V DC. 12/60/1200V AC. 80 uA/30mA/300mA. 2k/200k. 2 Meg Ohm. 10 to 63dB.  
**OUR PRICE £7.50** P&P 30p.



**U4324 MULTIMETER**  
High sensitivity, over load protected. 20,000 ohm. Range: 0.1/2.5/12/30/60/120/600/1200V DC. 3/6/15/30/150/300/600/1000V AC. Current: 0.06/0.6/5/80/500mA/3A DC. 0.3/3/30/300mA/3A AC. Resistance: 25/500 ohm/0.3/5/50/500k ohms/5 Megohms. Decibels: -10 to +12dB. Size 157 x 98 x 63mm. Supplied complete with test leads, spare diode and instructions.  
**OUR PRICE £9.25** P&P 30p



**U435 MULTIMETER**  
20,000 ohm. Range: 75mV/2.5/10/25/100/250/500/1000V DC. 1.5/10/25/50/100/250/500/1000V AC. Current: 50uA/1/5/25/100mA/0.5/2.5A DC. 0.5/2.5A AC. Resistance: 0.3/3/30/300 ohms. Size: 205 x 110 x 64mm. Supplied complete with test leads, crocodile clips and steel carrying case.  
**OUR PRICE £8.75** P&P 30p



**U4312 MULTIMETER**  
extremely sturdy instrument for general electrical use. 66Tops. 0/0.3/1.5/3/30/60/150/300/600V DC. 0/5mV/0/0.1/0.5/1/5/30/60/150/300/600/300V AC. 0/300uA/1.5/6/15/30/60/600mA/1/1.5/6A DC. 0/1/5/6/15/60/150/300mA/1.5/6A AC. 0/200/3k/30k ohms. DC accuracy 1%. AC 1.5%. Knife edge pointer, mirror scale. Complete with sturdy metal carrying case, leads and instructions.  
**OUR PRICE £10.25** P&P 60p



**U81 Clamp VOLT AMMETER**  
For measuring AC volt. Age and currents without breaking circuit. Range: 300/600V AC. Current: 10/25/100/250/500A. Accuracy 4%. Size 283 x 36 x 26mm. Complete with carrying case, leads and fuse.  
**OUR PRICE £13.50** P&P 30p



**MODEL 500**  
30,000 ohm with overload protection. Mirror scale. 0/0.5/5/50/500V DC. 0.5/5/50/500/1000V AC. 50/500uA/50mA. 2k/20k/200k/2M/20M Ohms. -20 to +63dB.  
**OUR PRICE £13.95** P&P 30p



**HIDKI 750X VOLT-OHM-MILLIAMMETER**  
43 ranges. 0-0.3/0.6/1.5/3/6/12/30/60/120/300/600/1200V DC. 0-3/6/15/30/60/120/300/600/1200V AC. Current: 0-30/300mA/300mA/6/12A. Resistance: 0-3/300k/3/30Megohms. Decibels: -10 to +17dB. Output: 50,000 ohm DC, 5,000 ohm AC. Accuracy  $\pm 3\%$  DC,  $\pm 4\%$  AC. Sensitivity 50,000 ohm DC, 5,000 ohm AC. 4 inch meter. Built in protection. Size 57 x 102 x 153mm.  
**OUR PRICE £11.95** P&P 40p



**TAK MODEL TW50K**  
46 ranges, mirror scale. 50kV DC. 50kV AC. DC Volt: 0.125/0.25/1.25/2.5/5/10/25/50/125/250/500/1000V AC. AC Volt: 0.125/0.25/1.25/2.5/5/10/25/50/100/250/500/1000V AC. Resistance: 10k/100k/1 Meg. -20 to +81.5dB.  
**OUR PRICE £12.50** P&P 70p



**HIDKI MODEL 700X**  
100,000 ohm. Overload protection. Mirror scale. 0.300/6/12/1/5/3k/6/12/30/60/120/300V DC. 1.5/3/6/12/30/60/150/300/600/1200V AC. 15/300/3k/30/300/60/150/300/600/1200V AC. 2k/20k/200k/2M/20M Ohms. -20 to +63dB.  
**OUR PRICE £14.95** P&P 30p



**Model RT190B4 MULTIMETER**  
Overload protected, built-in proof circuit. 9.5uA Meter with mirror scale. Sensitivity 100kV. Polarity change switch. Range: 0.5/2.5/10/50/250/500/1,000 Volts DC. 2.5/10/50/250/1,000 Volt AC. DC Resistance: 0-20/200k/120k Meg. ohms. DC current: 10/250uA/2.5/25/250 mA/10A. AC current: 0-10A. -20 to +152dB. Operates from 2 x 1.5V batteries. Size: 180 x 134 x 79mm.  
**OUR PRICE £17.50** P&P 40p



**MODEL AS.1000 VOM**  
100,000 ohm. Built-in meter protection. 0/3/12/60/120/300/600/1200V DC. 0/6/30/120/300/600V AC. 0/10/50/100/500mA. 6/60/300mA. 12 Amp. 0.2k/200k/2M/20M Ohm. -20 to 17 dB.  
**OUR PRICE £17.50** P&P 30p.



**MODEL C720ZEN**  
20,000 ohm. DC. 10,000 ohm. AC. Mirror scale. 0/2.5/10/50/100/1000/2800V DC. 10/50/100/500/1000V AC. DC Resistance x1, x10, x100 (30k). 2mA/20mA/200mA/2A. 2.5mA/25mA. -20 to +68 dB.  
**OUR PRICE £8.50** P & P 30p



**KAMODEN HM720B FET VOM**  
input impedance 10 Megohms. Range: 0/25/125/5/10/50/100V DC. 0/1.5/10/50/250/1000V AC. 0/25uA/2.5/25/250mA. 0/5k/50k/500k/5M. 500 Megohms.  
**OUR PRICE £21.00** P & P 30p



**KAMODEN 360 MULTIMETER**  
High sensitivity. DC 100 ohm/V. AC 10kohm/V. 5" mirror scale. overload protected. Range: 0.5/2.5/10/50/250/1000V DC. 5/10/50/250/1000V AC. Current: 0.01mA/0.5/5/50/500mA/10A. Resistance: 0.1/1/10/100 ohms/1/10/100k ohms/10/100M ohms. Decibels: -20 to +62dB. Battery operated. Size: 180 x 140 x 80mm. Supplied complete with test leads etc.  
**OUR PRICE £17.50** P & P 40p



**TAK MODEL 117 FET ELECTRONIC VOLTMETER**  
Battery operated. 11 Meg input. 28 range. 5" mirror scale. Size 149x117x68mm. 0.3-17000V DC. 2-3000V AC. 8-800V P.P. DC current 0.12-12mA. Resistance up to 200k ohms. Decibels: -20 to +51dB. Supplied complete with leads and instructions.  
**OUR PRICE £18.50** P&P 20p



**TAK 100K LAB TESTER**  
100,000 ohm. 5k scale. Battery operated. short circuit check. Sensitivity 100,000 ohm DC. 5kV AC. DC Volt: 0.2/2.5/10/50/100/500/1000V AC. 3/10/50/250/500/1000V DC. Resistance: 1k/10k/100k/10 Meg. 100 Meg ohms. Decibels: -10 to +49dB. Plastic case with carrying handle. Size: 150 x 172 x 99mm.  
**OUR PRICE £19.95** P&P 30p




**378WTR MULTIMETER**  
Features AC current meter. 20,000 ohm. 0/0.5/2.5/10/50/250/1000V DC. 0/2.5/10/50/250/1000V AC. 0.50uA/1/10/100 uA/1/10A DC. 0/100mA/100k/100k/100k/100k/5 Meg. 500V. Decibels: -20 to +62dB.  
**OUR PRICE £19.95** P&P 30p



**KAMODEN 72.200 Multitester**  
High sensitivity. Input: 200,000 ohm. Overload protected. Mirror scale. Range: 0-0.6/3/3/12/60/600/1200V DC. 0/2/20/300/1000V AC. 0.50uA/1/10/100 uA/1/10A DC. 0/100mA/100k/100k/100k/100k/5 Meg. 500 Megohms. Decibels: -20 to +62dB.  
**OUR PRICE £22.50** P&P 30p



**U4317 MULTIMETER**  
High sensitivity. Built-in lead and laboratory work. Knife edge pointer. 36mm mirror scale. Overload protection. Range: 100mV/0.5/2.5/10/25/50/100/250/500/1000V DC. 0.5/2.5/10/25/50/100/250/500/1000V AC. Current: 50uA/0.5/1/5/10/50/250mA/1/5A DC. 0.25/0.5/1/5/10/50/250mA/1/5A AC. Resistance: 0.5/10/100/200 ohm/1/3/30/300k ohms. Decibels: -5 to +105dB. Battery operated. Size: 210 x 115 x 90mm. Supplied in carrying case complete with leads.  
**OUR PRICE £16.50** P&P 40p

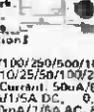

**MODEL C720BFM**  
30,000 ohm. DC. 15,000 ohm. AC. 6/3/1/6/50/300/800/1200V DC. 0/30/120/600/1200V V AC. DC Resistance x1, x10, x100, x1,000 (50k) centre scale. -20 to +63dB. DC Current 30uA/3/30/600mA. -20 to +63dB.  
**OUR PRICE £8.95** P & P 30p



**MODEL U4311 Sub-standard Multi-range Volt-Ammeter**  
Sensitivity 330 Ohm/Volt AC and DC. Accuracy 0.5% DC. 1% AC. Scale length: 165mm. 0/200/750uA/1.5/3/7.5/30/75/150/300/750mA/1.5/3/7.5A DC. 0/3/7.5/15/30/75/150/300/750V AC. Automatic cut out device. Supplied complete with test leads, manual and test case. P&P 50p



**MODEL AF.105 VOM**  
80,000 ohm. Mirror scale. Meter protection. 0/3/3/18/60/120/300/600/1200V DC. 0/6/30/120/300/600/1200V DC. 0/30uA/3/60/300mA/12 Amp. 0/10k/12 Amp. 0/10k/100 tm/10m/100 Meg Ohms. -20 to +17 dB.  
**OUR PRICE £12.50** P&P 30p.



**LB3 TRANSISTOR TESTER**  
Tests ICB and B. PNP/NPN. Operates from BV battery. Instructions included.  
**OUR PRICE £3.95** P&P 20p




**LB4 TRANSISTOR TESTER**  
Tests PNP or NPN transistors. Audio indication. Operates on two 1.5V batteries. Instructions complete with instructions etc.  
**OUR PRICE £4.50** P&P 20p



**KAMODEN TT35 TRANSISTOR TESTER**  
High quality instrument to test bipolar and unijunction transistors. SCR's etc. 4" square clear plastic meter. Operates from 2x1.5V internal batteries. Complete with instructions, leads carrying handle.  
**OUR PRICE £17.50** P & P 40p



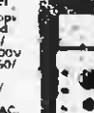**U4341 Multimeter & Transistor Tester**  
27 ranges, 18,700 ohm. Overload protected. Range: 0.3/1.5/3/10/50/100/300/600V DC. 1.5/7.5/30/150/300/750V AC. Current: 0.05/0.5/5/50/500mA DC. Resistance: 0.06/0.6/2/20/200k ohms/2 Megohm. Battery operated. Supplied complete with probes, leads and steel carrying case. Size: 115 x 215 x 90mm.  
**OUR PRICE £10.50** P&P 30p



**S100TR MULTIMETER TRANSISTOR TESTER**  
100,000 ohm. Mirror scale. Overload protection. 0/0.12/0.6/3/12/30/120/600V DC. 0/5/30/120/600V AC. 0/12/300uA/12/300mA/1/12A DC. 0/10k/1 Meg. 100 Meg. -20 to +50dB. 0.01-C 2MPD. Transistor tester, antenna alignment, and ICB. Complete with instructions, batteries and leads.  
**OUR PRICE £19.95** P&P 25p



**SWR METER Model SWR3**  
Handy SWR meter for transmitter antenna alignment, with built in fold strength meter. Accuracy 5%. Impedance 52. Indication 1000. DC. Full scale section collapsible antenna. Size 145 x 50 x 60mm.  
**OUR PRICE £4.25** P&P 30p



**ALL PRICES EXCLUDE VAT**  
Also see following pages

**CIS PULSE OSCILLOSCOPE**

For display of pulsed and periodic wave forms in electronic circuits. VERT. AMP Bandwidth 10MHz. Sensitivity at 100kHz 1V/5cm/mm. D 1-25. HOR. AMP. Bandwidth: 500kHz. Sensitivity at 100kHz 1V/5cm/mm. D 3-25. Preset triggered sweep 1-3000/sec. Free running time base 0.2 to 360 x 430mm. 115-230V AC.  
**OUR PRICE £43.00** Carr. paid



**RUSSIAN C116 Double Beam OSCILLOSCOPE**

Separate X1 and X2 amplifiers. Rectifying 5" x 4" CRT. Cable and triggered sweep from oscilloscope to 100 millivolt/cm. Free running time base 0.2 to 360 x 430mm. 115-230V AC. Calibration and amplitude calibration. Supplied complete with all accessories and instruction manual.  
**OUR PRICE £87.00** Carr. Paid




**MODEL TE15 GRID OUP METER**

Grid Current Operation at Grid Dip Oscillator, Absorption Wave Meter and Oscillation Detector. Frequency range 40kHz - 280MHz in coils. 500mA meter. 5V battery operation. Size: 180 x 80 x 40mm.  
**OUR PRICE £19.95** P&P 30p



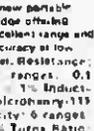**TRANSISTORISED L.C.R. A.C. BR/B MEASURING BRIDGE**

A new portable bridge offering excellent range and accuracy at low cost. Resistance: 6 ranges, 0.1 Ohm-11.1 megohms. Inductance: 6 ranges: 1 microhenry-119 microhenry. Capacitance: 6 ranges: 10pF-1110 pF in 2k Turns Ratio. 6 ranges: 1.1/300Hz-11100 x 1% Bridge Voltage at 1,000cps. Operated from 6-volt battery. 100 micro amp meter indication. Size 74" x 5" x 2".  
**OUR PRICE £25.00 P&P 30p**



**TE16A TRANSISTORISED SIGNAL GENERATOR**

5 ranges, 400kHz to 100MHz. An indispensable instrument for the ham/fun. Operates on 9V battery. Wide range to read scale. 800kHz modulation. Size: 149 x 149 x 92mm. Complete with instructions and leads.  
**OUR PRICE £8.97** P&P 30p



**TE-200 HF SIGNAL GENERATOR**

Accurate wide range signal generator covering 120 x 100-500 MHz on 4 bands. Directly calibrated. Variable R.F. attenuator audio output. Xial socket for calibration. 220/240V A.C. Broad range with instructions. Size 148mm x 215mm x 170mm.  
**OUR PRICE £17.50** P&P 50p



**TE22 SINE SQUARE WAVE AUDIO GENERATOR**

Sine 20cps to 200kHz on 4 bands. Square 20 cps to 200 kHz. Output impedance 5000 Ohms. 200/250V AC operation. Supplied brand new guaranteed, with instruction manual and leads.  
**OUR PRICE £24.95** P&P 50p




**ARF 300 AF/RF SIGNAL GENERATOR**

All transistorised compact fully portable AF sine wave 15Hz to 220 kHz. AF square wave 15Hz to 1000 Hz. Output Square wave wave 100 P.P.F. RF 100kHz to 200MHz. Output 1mA max. 220/240V AC operation. Complete with instructions and leads.  
**OUR PRICE £37.50** P&P 50p



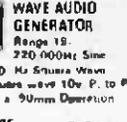**MODEL MC100 SINE SQUARE WAVE AUDIO GENERATOR**

Wave 15-100,000 Hz Sine Wave Output Sine or Square wave 10V P. to P. Input 180 x 90 x 90mm Operation 220/240V A.C.  
**OUR PRICE £19.95** P&P 50p



**SPECIAL BARGAIN!! FERGUSON 3406 M.F.I. SPEAKERS**

High Quality 2 way speaker systems. 20 Watts 4-8 ohm 40Hz-18kHz. Size: 160 x 140 x 25mm approx. Wood grain finish with black fronts.  
**OUR PRICE £22.50 P&P £1**



**POWER RMEOSTATS**

High quality ceramic construction. Wind 1% embedded in vitreous enamel. Heavy duty brass water. Continuous rating. Single hole for 1/8" diameter shafts. Bulk 90 entries available.  
**25 WATT 10/25/50/100/200/1000 2500 ohms £1.15 P&P 10p**  
**50 WATT 10/50/100/250/500/1500/5000 ohms £1.62 P&P 10p**  
**100 WATT 15/70/25/50/250/500/2500 ohms. 10ms. £2.34 P&P 15p**



**EMI LOUSPEAKERS**

Model 350 13 x 6" with single woofer/woofer. 20-20,000Hz 15 watts RMS. Available 8 or 16 ohms.  
**OUR PRICE £7.50 each P&P 37p**  
Model 450 13 x 6" with twin woofer/woofer. 55-13,000Hz. 8 watts RMS. Available 8 or 15 Ohms.  
**OUR PRICE £3.62 each P&P 35p**



**SPECIAL PURCHASE LIMITED QUANTITY! TANNY 12" DR/8 Bass Speakers**

8 ohms 30 watt heavy duty, ideal for H.F.I.P.A. Group.  
**OUR PRICE £12.50** P&P 50p



**PS208 Regulated POWER SUPPLY UNIT**

Solid state. Variable output 1.5-20V DC. Up to 2A amp. Includes pendulum meter to monitor voltage and current. Output 220/240V AC. Size: 190 x 136 x 95mm.  
**OUR PRICE £19.95** P&P 50p



**AUDIOTRONIC LE-102A INTERCOM**

Great new made and finished in two-tone luvly/auit. The LE-102A is suitable for the home, office or shop and is suitable for use as a baby alarm. Will record on 1/2" cassette. 57mm speaker/mic gives clear 2 way communication with on/off and volume control on master unit. Operates on 9V batt. Approx. 60H lead.  
**OUR PRICE £3.95** P & P 30p



**TRITON 4318 PORTABLE 8 TRACK CARTRIDGE PLAYER WITH MW/LW RADIO**

Will play 8 track stereo cartridge manually. Channel selector switch. Covers medium and long wave bands. Volume and tone controls. Earphone socket. Battery/ mains operation.  
**OUR PRICE £11.95** P & P 50p



**EASI REVERBERATION AMPLIFIER**

Self contained, transistorised, battery operated. Simply plug in microphone, guitar etc. and output to your amplifier. Volume control and depth of reverb control. Beautifully styled. 134 x 77 x 138mm.  
**OUR PRICE £7.50** P&P 30p



**SPECIAL PURCHASES! RECORD DECK PACKAGE**

By Famous Manufacturer GARRARD SP28 Mark 111 with C800 cartridge in luxurious plinth with door.  
**OUR PRICE £13.95 P & P 75p**  
GARRARD SP25 Mark 111 Record Deck fitted with C800 cartridge.  
**OUR PRICE £9.95 P & P 50p**



**LIGHTS STEREO HEADPHONES**

Light weight headphones with padded ear pieces 4/16 ohms. 20-12,000Hz. Adjustable headband. Impedance 8 ohms. 20-12,000Hz. Complete with lead and plug.  
**OUR PRICE £1.97** P&P 30p



**DH025 STEREO HEADPHONES**

Wonderful value and excellent performance. Adjustable headband. Impedance 8 ohms. 20-12,000Hz. Complete with lead and plug.  
**OUR PRICE £2.25** P&P 30p




**TE1035 Stereo HEADPHONES**

Low cost with excellent response. Form rubber earcups. Adjustable headband. 8 ohms impedance. Frequency response 20-12,000Hz. Complete with cable and stereo jack plug.  
**OUR PRICE £2.60** P&P 30p



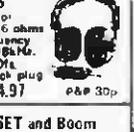**SDRBV MONO/STEREO HEADPHONES**

Volume control for stereo channel, 4/16 ohms impedance. Frequency response 20Hz-18kHz. Complete with 10ft. coiled lead and jack plug.  
**OUR PRICE £4.97** P&P 30p



**BROOK HEADSET and Boom Microphone**

Moving coil. Ideal for language teaching, communications etc. Headphone impedance 16 ohms. Microphone impedance 200 ohms.  
**OUR PRICE £5.95** P&P 30p



**HANIMEX HRC 3075 CASSETTE RADIO**

Covers Medium and FM wave bands. 500w volume and tone controls. Battery/ Mains operation. Will record direct transmission through built in condenser microphone. Complete with batteries, earphone, and cassette.  
**OUR PRICE £24.30** P & P 50p



**SPECIAL BARGAIN!! STEREO/SOUND SPEAKERS**

Matched pair of stereo bookshelf speakers. Durable tear-resistant finish. Size 368 x 220 x 190mm. 8 ohms. 8 watts RMS. 16 watts peak. Complete with 0m lead.  
**OUR PRICE £12.95 P&P 50p**



**FM TUNER CHASSIS**

8 transistors high quality tuner. Size only 153 x 101 x 63mm. 3 1/2" track. Double tuned discriminator. Ample output to feed most amplifiers. Operates on 9V battery. Covast 88-100MHz. Ready built, ready for use. Fantastic value for money.  
**OUR PRICE £8.95** P&P 20p  
Stereo Multiplex Adapter £5.95 extra



**SPECIAL OFFER! SAVE OVER 50%**

AMSTRAD 8000 2 Stereo amplifier 7 watts per channel. 4 inputs for tuner, tape, phono. Headphone socket. List price £29.95.  
**OUR PRICE £12.95 P & P 60p**



**SPECIAL OFFER! CONVERT YOUR STEREO SYSTEM TO 4D SOUND FOR UNDER £15**

Exclusive offer of GOODWIN 4-CHANNEL CONVERTER and a pair of AD15 10 watt 8 ohm bookshelf speakers enables you to add 4D sound to your existing system. Complete with simple connection details. Normal retail value £25.50.  
**OUR PRICE £15.80 P & P £1**  
GOODWIN CONVERTER available separately £3.35 P & P 50p.



**Model A1018 FM TUNER**

6 transistor high quality unit - 5 1/2 stage and double tuned discriminator. For use with most amplifiers. Covers 88-108MHz. Powered by 9V battery.  
**OUR PRICE £13.50** P&P 30p  
Stereo multiplex adapter £5.95 extra.



**ELECTRONIC CALCULATORS**

We carry a tremendous range of both pocket and desk calculators from as little as £8. Owing to the demand it is not possible to include them in this advertisement. So send for our latest price list or call into any branch.




**SINCLAIR SYSTEM 2000 STEREO AMPLIFIER AND TUNER**

2000 AMPLIFIER  
Amplifier output 8 watts per channel RMS. Distortion less than 0.06%. Silicon transistors. Two pick-up plus radio and tape inputs. Tape output and scratch filter. Excellent Value. List £39.95.  
**OUR PRICE £27.50** P & P 80p.



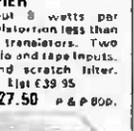
**2000 FM TUNER**

Excellent selectivity and sensitivity. Twin dual-voltage tuning. 4 pole ceramic filter. 19 transistor stereo demodulator giving 40 dB separation. Distortion 0.2% output. Fantastic Value. List £39.95.  
**OUR PRICE £27.50** P & P 80p.



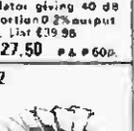**SINCLAIR IC12 INTEGRATED CIRCUIT AMPLIFIER**

Complete with printed circuit mounting board.  
**OUR PRICE £1.50** P & P 15p.



**SINCLAIR Project 80 Modules**

240 Power Amp. £6.95 P & P 15p  
240 Power Amp. £7.45 P & P 15p  
Stereo 80 Pre-Amp. £13.95 P & P 15p  
Tape Unit. £7.45 P & P 15p  
FM Tuner. £13.95 P & P 15p  
Stereo Decoder. £8.95 P & P 15p  
PZS Power Supply. £6.95 P & P 15p  
PZS Power Supply. £7.45 P & P 15p  
PZS Power Supply. £8.45 P & P 15p  
Transformer for PZS. £4.05 P & P 15p  
IC 20 Stereo Amp. £8.95 P & P 15p  
PZ20 Power Supply. £6.95 P & P 15p  
2x240 Stereo Amp. £21.30 P & P 30p  
2x240 Stereo Amp. £23.35 P & P 30p

**TE1021 Stereo Listening Station**

For balancing and gain selection of headphones with additional facility for stereo headphones. Switching two gain controls, switches on off slide switch, stereo headphone socket.  
**OUR PRICE £2.25** P & P 15p



**AUDIOTRONIC LOW NOISE CASSETTES**

TYPE 5 10 25  
C60 £1.57 £3.00 £7.08  
C90 £2.24 £4.25 £10.00  
C120 £2.73 £5.17 £12.24

**AUDIOTRONIC 8 TRACK CARTRIDGES**

TYPE 5 10 25  
40M £1.50 £3.00 £7.50  
80M £1.15 £2.40 £10.25  
P&P Cassette 3p. Cartridges for each OVER 10 at either. POST FREE!

**MP7 MIXER-AMPLIFIER**

5 Microphone inputs each with individual gain control. 2 stereo inputs. Complete main function. Battery operated. Size: 235 x 127 x 75mm. Inputs: Max 3 x 3mV 50K. 3 x 3mV. 3 x 3mV. 4mV 50K. Phono Ceramic 100mV. Max. Output 250mV 100K.  
**OUR PRICE £8.97** P&P 20p



**AUDIOTRONIC AH101 Stereo Headphone Amplifier**

All circuit amplifier operation from magnetic or tone inputs with twin stereo headphone outputs and separate volume controls for each channel. Operates from 9V battery. INPUTS: 5mV and 100mV. OUTPUT: 50mV per channel.  
**OUR PRICE £8.50** P&P 30p



**HIGH QUALITY CONSTRUCTION KITS**

WE ARE APPOINTED STOCKISTS AT ALL BRANCHES  
All kits are complete with comprehensive notes and full instructions and covered by full guarantee.  
Post and Packing 15p per kit.



AE 20 Mono amplifier	£5.61
AF 150 Mixer	£3.18
AF 300 Mono pre-amplifier	£3.20
AF 350 Stereo amplifier	£2.42
AF 80 0.5W max. amplifier	£4.86
AE 305 Intercom	£7.87
AF 310 2 Mono Amplifier	£7.55
M160 Multi-vibrator	£2.18
M1302 Transistor tester	£6.33
M191 VU Meter	£5.27
M192 Stereo balance meter	£1.83
LE 380 Audio-graphic device	£ 6.42
AT8 Automatic light control	£ 3.75
AT 30 Photo cell switch unit	£ 6.58
AT 150 400W trace light	£ 6.18
AT 50 200W trace light	£ 6.18
AT 50 200W trace light control	£ 6.75
AT 60 1 channel rms control	£10.82
AT 53 2 channel rms control	£18.82
GU 330 Terminal unit	£ 10.10
HF 61 Diode detector	£ 3.87
HF 65 FM transmitter	£ 3.21
HF 75 R.F. tuner	£ 16.32
HF 25 DeLuxe FM tuner	£ 6.73
HF 30 Decoder IMF 310/325	£10.35
GP 310 Stereo or mono amplifier for use with 2 x AE 310	£ 22.90
GP 312 Circuit board	£10.02
GP 304 Control board	£ 9.33
HF 380 In/Out signal amplifier	£ 8.02
HE 395 Broadband aerial amp	£ 7.70
AT 10 Stabilised power supply 100V/4, 9V	£ 6.17
NT 300 Stabilised u. supply	£ 13.18
NT 310 Power Supply 240 V AC on 2 x 18 V D.C. at 2amps	£ 6.90
AT 305 VHF range converter	£ 5.64
NT 315 Power supply 240V AC on 10 x 15V DC 500mA	£12.06

Amateur Electronics by Jasty Kit, the professional book for the amateur - covers the subject from basic principles advanced electronic techniques. Complete with circuit board for AE1 or AE10 listed below.

<b>OUR PRICE £3.30</b> (No VAT) P&P 25p plus VAT	
AE1 100Wm output stage	£1.55
AE2 Pre-Amplifier	£1.32
AE3 Diode rectifier	£ 2.05
AE4 Filter	£1.45
AE5 Adjustable multi-vibrator	£1.14
AE6 Monostable multi-vibrator	£1.11
AE7 RC generator	£ 0.90
AE8 Basic filter	£1.00
AE9 Y-coupler	£1.00
AE10 CCR filter	£ 0.95

Also see previous page  
**ALL PRICES EXCLUDE VAT**

# SEW PANEL METERS

SEW PANEL METERS ARE STOCKED AT OUR  
3 LISTS AT 301 EDGWARE RD. & 102 FLEET  
ST., BRANCHES or under By post.



USED EXTENSIVELY BY INDUSTRY, GOVERNMENT DEPARTMENTS, EDUCATIONAL AUTHORITIES ETC.

Over 200 ranges in stock—other ranges to order. Quantity discounts available. Send for fully illustrated brochure.

## CLEAR PLASTIC MODEL SB640

Size: 85 x 66mm

50uA	£3.80
100uA	£3.75
200uA	£3.70
500uA	£3.65
500-0-500uA	£3.75
100-0-100uA	£3.70
1mA	£3.66
5mA	£3.66
10mA	£3.66
50mA	£3.66
100mA	£3.66
500mA	£3.66
1A DC	£3.85
5A DC	£3.85
10A DC	£3.85
50V AC	£3.85
300V AC	£3.75
15V DC	£3.85
300V AC	£3.90
VU Meter	£3.90



\*Items with asterisk are Moving Iron type, all others are Moving Coil

## CLEAR PLASTIC MODEL SB030

Size: 710 x 93mm

50uA	£4.30
100uA	£4.25
200uA	£4.20
500uA	£4.16
500-0-500uA	£4.26
100-0-100uA	£4.20
1mA	£4.10
5mA	£4.10
10mA	£4.10
50mA	£4.10
100mA	£4.10
500mA	£4.10
1A DC	£4.10
5A DC	£4.10
10A DC	£4.10
50V AC	£4.10
300V AC	£4.20
VU Meter	£4.40



## CLEAR PLASTIC MODEL MR 65P

Size: 96 x 78mm

50uA	£3.95
100uA	£3.85
200uA	£3.80
500uA	£3.75
50-0-50uA	£3.85
100-0-100uA	£3.80
500-0-500uA	£3.70
1mA	£3.70
1-0-1mA	£3.70
5mA	£3.70
10mA	£3.70
50mA	£3.70
100mA	£3.70
500mA	£3.70
1A DC	£3.70
5A DC	£3.70
10A DC	£3.70
15A DC	£3.70
20A DC	£3.70
30A DC	£3.70
50A DC	£3.70
5V DC	£3.70
10V DC	£3.70
15V DC	£3.70
20V DC	£3.70
50V DC	£3.70
150V DC	£3.70



## CLEAR PLASTIC MODEL SW100

Size: 100 x 80mm

50uA	£4.60
100uA	£4.55
200uA	£4.50
50-0-50uA	£4.50
100-0-100uA	£4.48
1mA	£4.38
1A DC	£4.38
5A DC	£4.38
20V DC	£4.38
50V DC	£4.38
300V AC	£4.45
300V DC	£4.30
VU Meter	£4.30



## CLEAR PLASTIC MODEL MR 45P

Size: 80 x 50mm

50uA	£3.20
100uA	£3.15
200uA	£3.10
500uA	£3.00
500-0-500uA	£3.15
100-0-100uA	£3.10
500-0-500uA	£2.95
1mA	£2.95
5mA	£2.95
10mA	£2.95
50mA	£2.95
100mA	£2.95
500mA	£2.95
1A DC	£2.95
5A DC	£2.95
10V DC	£2.95
20V DC	£2.95
50V DC	£2.95
300V AC	£2.95
15V AC	£3.08



## BAKELITE MODEL S80 Enlarged Window

Size: 80 x 80mm

50uA	£4.50
100uA	£4.45
200uA	£4.40
500uA	£4.35
50-0-50uA	£4.45
100-0-100uA	£4.40
1mA	£4.20
5mA	£4.20
10mA	£4.20
50mA	£4.20
100mA	£4.20
500mA	£4.20
1A DC	£4.20
5A DC	£4.20
20V DC	£4.20
50V DC	£4.20
300V AC	£4.20
300V DC	£4.20
VU Meter	£4.20



## EDGWISE MODEL PE70

Size: 90 x 34mm

50uA	£4.15
100uA	£4.10
200uA	£4.05
500uA	£4.00
50-0-50uA	£4.10
100-0-100uA	£4.05
1mA	£3.85
5mA	£3.85
10mA	£3.85
50V AC	£4.45
300V AC	£4.45
300V DC	£4.30
VU Meter	£4.30



## CLEAR PLASTIC MODEL MR 38P

Size: 42 x 42mm

50uA	£3.10
100uA	£3.05
200uA	£3.00
500uA	£2.85
50-0-50uA	£3.05
100-0-100uA	£3.00
500-0-500uA	£2.80
1mA	£2.80
1-0-1mA	£2.80
5mA	£2.80
10mA	£2.80
20mA	£2.80
50mA	£2.80
100mA	£2.80
150mA	£2.80
200mA	£2.80
300mA	£2.80
500mA	£2.80
750mA	£2.80
2A DC	£2.80
5A DC	£2.80
10A DC	£2.80
20A DC	£2.80
30V DC	£2.80
10V DC	£2.80
15V DC	£2.80



## CLEAR PLASTIC MODEL MR 62P

Size: 60 x 60mm

50uA	£3.70
100uA	£3.60
200uA	£3.55
500uA	£3.50
50-0-50uA	£3.60
100-0-100uA	£3.55
1mA	£3.30
5mA	£3.30
10mA	£3.30
50mA	£3.30
100mA	£3.30
500mA	£3.30
1A DC	£3.30
5A DC	£3.30
10V DC	£3.30
20V DC	£3.30
50V DC	£3.30
300V DC	£3.30
15V AC	£3.40
30V AC	£3.40



## MODEL ED107 EDUCATIONAL METER

Size: 100 x 80 x 150mm including terminals

50uA	£8.50
100uA	£8.40
200uA	£8.30
500uA	£8.20
50-0-50uA	£8.30
1mA	£7.80
1-0-1mA	£7.60
1A DC	£7.49
5A DC	£7.50
10V DC	£7.49
50V DC	£7.49
15V DC	£7.60



## CLEAR PLASTIC MODEL SD460

Size: 59 x 46mm

50uA	£3.50
100uA	£3.46
200uA	£3.40
500uA	£3.35
50-0-50uA	£3.45
100-0-100uA	£3.40
1mA	£3.10
5mA	£3.10
10mA	£3.10
50mA	£3.10
100mA	£3.10
500mA	£3.10
1A DC	£3.10
5A DC	£3.10
10A DC	£3.10
20A DC	£3.10
30V DC	£3.10
10V DC	£3.10
15V DC	£3.10



## BAKELITE MODEL MR 65 Size: 80 x 80mm

25uA	£5.25
50uA	£4.00
100uA	£3.95
500uA	£3.85
50-0-50uA	£3.95
100-0-100uA	£3.90
500-0-500uA	£3.60
1mA	£3.60
1-0-1mA	£3.60
5mA	£3.60
10mA	£3.60
50mA	£3.60
100mA	£3.60
500mA	£3.60
1A DC	£3.60
5A DC	£3.60
10A DC	£3.60
15A DC	£3.60
20A DC	£3.60
30A DC	£3.60
50A DC	£3.60
5V DC	£3.60
10V DC	£3.60
15V DC	£3.60
20V DC	£3.60
50V DC	£3.60
150V DC	£3.60



## 240° Wide Angle

### 1mA METERS

MW1 - 6.80 x 60 mm

ES 60 P & P 15p

MW1 - 8.80 x 80mm

ES-90 P&P 15p



## YAMABISHI VARIABLE VOLTAGE TRANSFORMERS

Excellent quality at low cost. INPUT.

230V 50/60Hz. Output 0-260V.

MODEL S260 BENCH MOUNTING

ES-95

1A £10.50 50p

2.5A £12.00 50p

5A £17.50 50p

8A £30.35 £1.00

10A £33.75 £1.00

12A £36.40 £1.00

20A £85.00 £1.50

25A £95.00 £1.50

40A £120.00 £1.50

MODEL S260R PANEL MOUNTING

2.5A £12.00 50p



**ALL PRICES EXCLUDE VAT**



## FOR MAIL ORDER

We offer a speedy and efficient service by mail order. Remember to add 8% VAT to total value of goods including Post and Packing.

## TO LASKYS CUSTOMER SERVICES DIVISION

Audiotronic House, The Hyde, London NW9 6JJ Tel. 01 200 1321

Please send me the following items

TOTAL PURCHASE PRICE (inc P&P and VAT)

I enclose Cheque postal order money order

I wish to pay by Barclaycard/ACCESS and my number is

NAME

ADDRESS

Signature

Registered in England No. 347241 at 12 Lower Grosvenor Place London SW1H 0EX

16 Page Hi Fi PRICE LIST

CALL TO YOUR NEAREST LASKY'S BRANCH OR SEND COUPON BELOW FOR NEW 16 PAGE HI-FI PRICE LIST

### CENTRAL LONDON

481 OXFORD ST.	01-493 8641
1 LITTLE ST. WC2	01-437 8204
34 LITTLE ST. WC2	01-437 9155
118 EDGWARE RD. W2	01-723 9789
193 EDGWARE RD. W2	01-723 6211
207 EDGWARE RD. W2	01-723 3271
311 EDGWARE RD. W2	01-261 0387
348 EDGWARE RD. W2	01-723 4483
383 EDGWARE RD. W2	01-723 4174
109 FLEET ST. EC4	01-351 5812
152/3 FLEET ST. EC4	01-353 2833
10 TOTTENHAM CT. RD.	01-837 2332
27 TOTTENHAM CT. RD.	01-836 3715
33 TOTTENHAM CT. RD.	01-836 2645
42/45 TOTTENHAM CT. RD.	01-836 5445
237/8 TOTTENHAM CT. RD.	01-580 0670

### EBBEX

86 SOUTH ST. ROMFORD	20218
205-206 CHURCHILL WYEST.	0702 612241
VICTORIA CIRCUS SOUTHEND	

### KENT

13/57 CAMDEN RD. TUNBRIDGE WELLS	0892-23142
----------------------------------	------------

### LEICESTERSHIRE

45 MARKET PLACE, LEICESTER.	0533-537674
-----------------------------	-------------

### NORTHAMPTONSHIRE

73 BRINGTON STREET, NORTHAMPTON (Opening November)	
--	--

### STAFFORDSHIRE

30 WULFRUN WAT. WOLVERHAMPTON	Now Open
-------------------------------	----------

### SURREY

1088 WHITGIFT CENTRE, CROYDON	
27 EDEH ST. KINGSTON	01-481 3027
38/40 EDEH ST. KINGSTON	01-546 1271
32 HILL ST. RICHMOND	01-948 1441

### WARWICKSHIRE

116 CORPORATION ST., BIRMINGHAM	021-236 3503
---------------------------------	--------------

### WILTSHIRE

111 THE WINDMILL TOWER, TURTLETON, WILTSHIRE	
--	--

### WILTSHIRE

111 THE WINDMILL TOWER, TURTLETON, WILTSHIRE	
--	--

### WILTSHIRE

111 THE WINDMILL TOWER, TURTLETON, WILTSHIRE	
--	--

### WILTSHIRE

111 THE WINDMILL TOWER, TURTLETON, WILTSHIRE	
--	--

### EXPORT

Specialist in the export of Hi-Fi components and accessories. Please contact us for a list of our products and prices. Payment by bank transfer, credit card, cheque or cash. We accept all major credit cards.

**NO DEPOSIT TERMS** available on most goods for personal callers

CHEQUES TO THE VALUE OF £10 ACCEPTED FROM PERSONAL SENDERS WITH BANKERS CASH IN OTHER CASES ALSO FOR AMOUNTS IN EXCESS OF £30 PLEASE ALLOW FIVE JOB CLEARANCE BANKERS DRAWS ACCEPTED

All prices correct as at 15/14 but subject to change without notice. R.E.D.E.

A member of the Audiotronic Group of Companies.



GIRO NO. 331 7056  
 C.W.O. only. P. & P. 10p on orders below £5  
 Discounts: £10-100p, £20-15% (except net items)  
 Export Order enquiries welcome (VAT free)  
 Official Orders accepted from  
 Educational & Government Departments  
**ALL PRICES INCLUDE VAT AT 8%**

**SPECIAL RESISTOR KITS** (Prices include post & packing)  
 10E12 1W KIT: 10 of each E12 value, 22 ohms—1M, a total of 570 (CARBON FILM 5%), £3.58 net  
 10E12 1W KIT: 10 of each E12 value, 22 ohms—1M, a total of 570 (CARBON FILM 5%), £3.77 net  
 25E12 1W KIT: 25 of each E12 value, 22 ohms—1M, a total of 1425 (CARBON FILM 5%), £8.19 net  
 25E12 1W KIT: 25 of each E12 value, 22 ohms—1M, a total of 1425 (CARBON FILM 5%), £8.28 net  
 5E12 1W KIT: 5 of each E12 value, 10 ohms—1M, a total of 305 (METAL FILM 5%), £2.80 net  
 Due to current world shortages, resistor kits may contain some wattage and value substitutions

**MULLARD POLYESTER CAPACITORS C280 SERIES**  
 250V P.C. Mounting: 0.01µF, 0.015µF, 0.022µF, 0.033µF, 0.047µF, 33p, 0.068µF, 0.1µF, 44p, 0.15µF, 22p, 0.22µF, 51p, 0.33µF, 6p, 0.47µF, 9p, 0.68µF, 12p, 1µF, 15p, 1.5µF, 33p, 2.2µF, 26p.  
**MULLARD POLYESTER CAPACITORS C290 SERIES**  
 400V: 0.001µF, 0.0015µF, 0.0022µF, 0.0033µF, 0.0047µF, 24p, 0.0068µF, 0.01µF, 0.015µF, 0.022µF, 0.033µF, 33p, 0.047µF, 0.068µF, 0.1µF, 44p, 0.15µF, 68p, 0.22µF, 84p, 0.33µF, 13p, 0.47µF, 14p, 160V: 0.01µF, 0.015µF, 0.022µF, 3p, 0.047µF, 0.068µF, 3p, 0.1µF, 44p, 0.15µF, 5p, 0.22µF, 5p, 0.33µF, 6p, 0.47µF, 8p, 0.68µF, 12p, 1µF, 14p.  
**MINIATURE CERAMIC PLATE CAPACITORS**  
 50V: (DF) 22, 27, 33, 39, 47, 56, 68, 82, 100, 120, 150, 180, 220, 270, 330, 390, 470, 560, 680, 820, 1K, 1K5, 2K2, 3K3, 4K7, 6K8. (µF) 0.01, 0.015, 0.022, 0.033, 0.047, 21p; each, 0.1, 30V, 5p.  
**POLYESTER CAPACITORS 160V 5%**  
 (pF) 10, 15, 22, 33, 47, 68, 100, 150, 220, 330, 470, 680, 1000, 1500, 2200, 3300, 4700, 6800, 10000, 15000, 22000, 33000, 47000, 68000, 100000, 150000, 220000, 330000, 470000, 680000, 1000000, 1500000, 2200000, 3300000, 4700000, 6800000, 10000000, 15000000, 22000000, 33000000, 47000000, 68000000, 100000000, 150000000, 220000000, 330000000, 470000000, 680000000, 1000000000, 1500000000, 2200000000, 3300000000, 4700000000, 6800000000, 10000000000, 15000000000, 22000000000, 33000000000, 47000000000, 68000000000, 100000000000, 150000000000, 220000000000, 330000000000, 470000000000, 680000000000, 1000000000000, 1500000000000, 2200000000000, 3300000000000, 4700000000000, 6800000000000, 10000000000000, 15000000000000, 22000000000000, 33000000000000, 47000000000000, 68000000000000, 100000000000000, 150000000000000, 220000000000000, 330000000000000, 470000000000000, 680000000000000, 1000000000000000, 1500000000000000, 2200000000000000, 3300000000000000, 4700000000000000, 6800000000000000, 10000000000000000, 15000000000000000, 22000000000000000, 33000000000000000, 47000000000000000, 68000000000000000, 100000000000000000, 150000000000000000, 220000000000000000, 330000000000000000, 470000000000000000, 680000000000000000, 1000000000000000000, 1500000000000000000, 2200000000000000000, 3300000000000000000, 4700000000000000000, 6800000000000000000, 10000000000000000000, 15000000000000000000, 22000000000000000000, 33000000000000000000, 47000000000000000000, 68000000000000000000, 100000000000000000000, 150000000000000000000, 220000000000000000000, 330000000000000000000, 470000000000000000000, 680000000000000000000, 1000000000000000000000, 1500000000000000000000, 2200000000000000000000, 3300000000000000000000, 4700000000000000000000, 6800000000000000000000, 10000000000000000000000, 15000000000000000000000, 22000000000000000000000, 33000000000000000000000, 47000000000000000000000, 68000000000000000000000, 100000000000000000000000, 150000000000000000000000, 220000000000000000000000, 330000000000000000000000, 470000000000000000000000, 680000000000000000000000, 1000000000000000000000000, 1500000000000000000000000, 2200000000000000000000000, 3300000000000000000000000, 4700000000000000000000000, 6800000000000000000000000, 10000000000000000000000000, 15000000000000000000000000, 22000000000000000000000000, 33000000000000000000000000, 47000000000000000000000000, 68000000000000000000000000, 100000000000000000000000000, 150000000000000000000000000, 220000000000000000000000000, 330000000000000000000000000, 470000000000000000000000000, 680000000000000000000000000, 1000000000000000000000000000, 1500000000000000000000000000, 2200000000000000000000000000, 3300000000000000000000000000, 4700000000000000000000000000, 6800000000000000000000000000, 10000000000000000000000000000, 15000000000000000000000000000, 22000000000000000000000000000, 33000000000000000000000000000, 47000000000000000000000000000, 68000000000000000000000000000, 100000000000000000000000000000, 150000000000000000000000000000, 220000000000000000000000000000, 330000000000000000000000000000, 470000000000000000000000000000, 680000000000000000000000000000, 1000000000000000000000000000000, 1500000000000000000000000000000, 2200000000000000000000000000000, 3300000000000000000000000000000, 4700000000000000000000000000000, 6800000000000000000000000000000, 10000000000000000000000000000000, 15000000000000000000000000000000, 22000000000000000000000000000000, 33000000000000000000000000000000, 47000000000000000000000000000000, 68000000000000000000000000000000, 100000000000000000000000000000000, 150000000000000000000000000000000, 220000000000000000000000000000000, 330000000000000000000000000000000, 470000000000000000000000000000000, 680000000000000000000000000000000, 1000000000000000000000000000000000, 1500000000000000000000000000000000, 2200000000000000000000000000000000, 3300000000000000000000000000000000, 4700000000000000000000000000000000, 6800000000000000000000000000000000, 10000000000000000000000000000000000, 15000000000000000000000000000000000, 22000000000000000000000000000000000, 33000000000000000000000000000000000, 47000000000000000000000000000000000, 68000000000000000000000000000000000, 100000000000000000000000000000000000, 150000000000000000000000000000000000, 220000000000000000000000000000000000, 330000000000000000000000000000000000, 470000000000000000000000000000000000, 680000000000000000000000000000000000, 1000000000000000000000000000000000000, 1500000000000000000000000000000000000, 2200000000000000000000000000000000000, 3300000000000000000000000000000000000, 4700000000000000000000000000000000000, 6800000000000000000000000000000000000, 10000000000000000000000000000000000000, 15000000000000000000000000000000000000, 22000000000000000000000000000000000000, 33000000000000000000000000000000000000, 47000000000000000000000000000000000000, 68000000000000000000000000000000000000, 100000000000000000000000000000000000000, 150000000000000000000000000000000000000, 220000000000000000000000000000000000000, 330000000000000000000000000000000000000, 470000000000000000000000000000000000000, 680000000000000000000000000000000000000, 1000000000000000000000000000000000000000, 1500000000000000000000000000000000000000, 2200000000000000000000000000000000000000, 3300000000000000000000000000000000000000, 4700000000000000000000000000000000000000, 6800000000000000000000000000000000000000, 100, 15000000000000000000000000000000000000000, 22000000000000000000000000000000000000000, 33000000000000000000000000000000000000000, 47000000000000000000000000000000000000000, 68000000000000000000000000000000000000000, 1000, 1500, 2200, 3300, 4700, 6800, 100, 15000, 22000, 33000, 47000, 68000, 1000, 1500, 2200, 3300, 4700, 6800, 100, 15000, 22000, 33000, 47000, 68000, 1000, 1500, 2200, 3300, 4700, 6800, 100, 15000, 22000, 33000, 47000, 68000, 1000, 1500, 2200, 3300, 4700, 6800, 100, 15000, 22000, 33000, 47000, 68000, 1000, 1500, 2200, 3300, 4700, 6800, 100, 15000, 22000, 33000, 47000, 68000, 1000, 1500, 2200, 3300, 4700, 6800, 100, 15000, 22000, 33000, 47000, 68000, 1000, 1500, 2200, 3300, 4700, 6800, 100, 15000, 22000, 33000, 47000, 68000, 1000, 1500, 2200, 3300, 4700, 6800, 100, 15000, 22000, 33000, 47000, 68000, 1000, 1500, 2200, 3300, 4700, 6800, 100, 15000

**no extras**  
all prices inc VAT  
FREE delivery

BARCLAYCARD

Buy it with Access



High Quality  
Construction  
Kits, stocked  
at all branches  
Send for  
catalogue!

**AMPLIFIERS**  
Teletron SAQ3078 18 watt £27.00  
Rotel RA211 £42.95  
RA311 £54.95  
RA611 £86.95  
Leak Delta 30 £54.75  
Samsul AU101 £48.25  
AU505 £74.95  
Sinclair 2000 £34.95  
Sinclair 4000 £45.95

**TUNERS & RECEIVERS**  
Leak Delta FM £58.75  
Sinclair 2000/4000 Tuner £34.95  
Rotel RT222 £42.75  
Rotel RX150A Tuner/  
Amp. £59.95  
Rotel 152A £69.95  
Samsul  
210 AM/FM/MPX £84.25  
310 AM/FM/MPX £99.50  
350A AM/FM/MPX £106.95

**RECORD DECKS**  
SP25 Mk III £11.00  
Garrard SP25 MKIV £12.95  
BSR MP60 £11.00  
BSR Invicta P & C/SC7M £9.95  
Garrard  
SP25 MKIV P & C/G/800 £21.00  
AP76 Module £30.00  
Goldring GL78 P & C/  
GB00E £56.95  
Connoisseur  
BD1 Kit £13.50  
BD2 Chassis/SAU2 £32.50  
SAU2 £14.25  
SCU1 £5.95

**TAPE DECKS (Insurance 2.00)**  
Akai  
4000DS Reel to Reel £93.95  
4000DB Reel to Reel  
Dolby £149.50  
1721L Special Offer £77.95  
GX36D £82.00  
GX38D £103.95  
CS33D £79.95  
Akai CR61D 8-track Rec.  
player £73.95

**SPEAKERS**  
Chassis Speakers  
EMI (Plain) 1 1/2in x 8in.  
3, 8 or 15 ohm Bass unit £2.30  
with Single Tweeter  
(only Bohm) £2.45  
with Twin Tweeter £3.95  
Type 350 Kit 15 watt 8 ohm £8.25  
1 1/2in x 8in Bass unit  
15 watt 8 ohm £4.95  
8in x 5in 5 watt 3, 8 or  
15 ohm £1.50  
8in x 5in 10 watt  
Dualcone 8 ohm £2.50  
6 1/2" 10 watt 8 ohm £2.65  
8in 10 watt 8 ohm £3.90  
12in 20 watt 8 ohm £6.95  
Fane 8in 4 or 15 ohm £2.25  
Fane 7in x 4in 3 or 8 ohm £1.20  
Elae 8in 8 ohm Dualcone £2.50  
Elae 10in 8 ohm Dualcone £3.75  
Goodman 6 1/2in 8 ohm  
Dualcone £2.40  
Baker Group 25 12in 8 or  
15 ohm £7.95  
Adastra 'Top 20' 12in  
25 watt 8 or 15 ohm £8.25

Adastra 'Hi-Ten' 10in  
10 watt 8 or 15 ohm £3.60  
Also 5in 8 ohm speaker £0.99  
2 1/2in 8 or 64 ohm  
speaker £0.50

**WHARFEDALE SPEAKER  
BARGAINS**  
Denton 1 pr. £26.75  
Denton 2 pr. £38.00  
Linton 2 pr. £38.95  
Glendale 3 pr. £58.95  
Kingsdale 3 ea. £60.95  
Dovedale 3 ea. £42.95

**KITS**  
Linton 2 £19.50  
Glendale 3 £33.95  
Dovedale £53.95

**SPEAKER CABINETS IN  
KIT FORM (Teak Veneer)**  
12in x 8in x 6in  
(8 x 5 or 7 x 4 cutout) £2.50  
14in x 12in x 9in  
(10", 8 x 5, 8", 6 1/2" & 3 1/2") £3.75  
18in x 11in x 9in  
(8" x 7" or 13 x 8) £4.50  
22in x 14in x 9in  
(12" & 7" or 13 x 8) £6.25

**TWEETERS & CROSSOVERS**  
EMI 3 1/2" c/magnet in 3 or  
8 ohm £1.25  
Cone Tweeter 10 watt  
8 or 15 ohm (K2006) £2.50  
Cone Tweeter 3 watt  
8 ohm (K2003) £1.55  
Horn Tweeter 8 ohm  
(K2007) £6.50  
Dome Tweeter 8 ohm  
(K2011) £5.50

**2-way Crossovers (CN23,  
CN28, CN216) £1.20**

**3-way Crossover (CN38) £2.75**

**CARTRIDGES & STYLII**

Cartridge	D/D	Stylus
ACOS GP91/2SC or 3CS (Isocr. comol)	1-10	1-25
GP93/1 or 95/1 ster. cryst.	1-35	1-25
GP94/1 or 96/1 ster. ceram.	1-75	1-25
GP101 cryst. comp.	90	—
GP104 ster. ceram.	1-75	1-25
BSR X5M or X5H cryst. comp.	1-75	1-25
SX6M or SX6H cryst. ster.	2-00	1-25
SC5M ster./ceram	2-75	1-25

**SONOTONE**  
9TAHC or  
9TAHC/G  
(Diam.) 1-85 1-25  
1-90 1-25  
3509 Magnetic  
AUDIO TECNICA  
AT55 1-95 —  
EMPIRE 999 REX 3-95 —  
GOLDRING  
GB50 2-95 1-95

G800 3-95 1-95  
G800H 3-95 1-95  
G800E 6-99 3-95  
**SHURE**  
M44G 4-75 3-45  
M55E 5-50 4-25  
M75ED Type 2 10-75 6-99  
M5EJ Type 2 8-75 4-99  
V15 Type 3 29-95 —

**MICROPHONES**  
UD130 50K/600 ohm  
uni-dir. ball metal £5.95  
UD147 £9.25  
Condenser Mic. 600 ohm  
uni-dir. £9.50  
Cassette Stick Mic. with  
R/Control £1.60  
Mic-Mixers Mono/stereo £5.50  
AKAI ADM14 £5.95

**HEADPHONES**  
Rotel  
RH430 £4.75  
RH 630 £7.75  
RH 700 £11.50  
Koss  
K711 £10.95  
KRO711 £10.95  
K6 £11.50  
K6LC £14.00  
KO72B £16.00  
KO747 £20.75  
HVI £21.95  
PRO4AA £26.95  
PRO54 £29.95  
K6LCQ £26.00  
Samsul SS10 £14.20  
Headphone adaptor  
(junction box) £2.50  
extension lead 2ft curly £1.35

**CASSETTES**

	C40	C60	C90	C120
Low Noise	35p	45p	55p	—
Phillips	55p	75p	110p	—
Memorex	65p	75p	110p	155p
Amplex (360)	45p	55p	70p	99p
Amplex (20.20+)	59p	65p	99p	135p
Chromium	—	—	—	—
Dioxide	—	99p	140p	—

Cassette Head Cleaner 45p  
Amplex Head Cleaner/Damag £1.65  
BIB Stereo Test Cassette £2.15  
Cassette Racks (hold 6) £0.45  
Cassette Rotating Racks  
(hold 20) £3.50  
Cassette Carrying Case  
(BIB) (hold 12) £1.60  
8-Track Cartridge Blanks  
C40 C64 C80  
80p 95p £1.10  
Amplex  
8-track H/Cleaner  
Demagnetiser £1.90  
8-track Carrying Cases  
(BIB) £1.45

**TAPES & CASSETTES**

	Std	LP	DP	Cases
5"	55p	65p	1.00	20p
5 1/2"	65p	86p	1.35	25p
7"	80p	110p	1.85	30p
High frequency	—	—	—	—
Amplex	—	1.40p	1.55p	—
7"	—	1.90p	2.95p	—
AKAI Metal Reel 7"	—	—	—	£1.99

**CALCULATORS**  
Sinclair Cambridge Build £19.95  
Scientific £29.95

**SINCLAIR PROJECT 80**  
Stereo Pre-amp. £11.95  
Active Filter Unit £6.95  
240 15 watt Amp £5.45  
P60 35 watt Amp £6.95  
P25 Power Supply for 240 £4.98  
P26 Power Supply for 240 £7.98  
P28 Power Supply for 260 £7.98  
FM Tuner £11.95  
Stereo Decoder £7.45  
Q16 Speaker £7.10

**PORTABLE RADIOS**  
Vega Jade £5.75  
Vega Zircon £8.25  
Vega Sapphire £7.25  
Vega VEF206 £13.95  
Micado LM/MW/FM/SSW  
Murphy £18.95  
B833 MW/VHF £9.95  
BA838 LW/MW/VHF  
M/Batt £18.50  
MA5003 Head Set  
Radio LW £7.95

Bush  
VTR165 LW/MW/VHF £22.00  
VTR127 LW/MW/VHF £15.50  
VTR178 VHF/MW/2SW/  
AIR M/Batt £27.50  
VTR 175 LW/MW/VHF £13.95  
VTR188 LW/MW/VHF/  
2SW M/Batt £31.95  
BY5661 LW/MW/VHF £14.95

**CLOCK RADIOS**  
Bush CR128 LW/MW  
£13.60  
Bush CR232 MW/VHF £24.95  
Murphy MYS600  
MW/VHF £22.95

**CASSETTE RECORDERS**  
Murphy BA206 £16.95  
Bush TP66 M/Batt £25.75  
Murphy BA200 M/Batt £22.75  
Bush BT8504 (miniature) £25.50

**RADIO CASSETTES**  
(Mains/Batt.)  
Micado 8155 AM/FM £25.95  
Murphy BA209 MW/VHF £33.50

**STEREO RECORD PLAYER  
& SYSTEM**  
Bush SPR58 £29.50  
Bush SPR59 £31.50  
Bush AJ005 £56.50  
Hanimax H101 £39.95  
Hanimax HRC5060 8-track  
AM/FM/MPX + Speaker £116.95

**CAR AUDIO**  
Bush Car Cassette BT8501 £36.75  
Hitachi Car Radio  
WM702R LW/MW £16.50  
KM1510 LW/MW/VHF £32.50  
Hitachi Car Cassette  
CS114 £45.00

ALL ITEMS SUBJECT TO  
MANUFACTURERS INCREASE  
AND AVAILABILITY

**PERSONAL CALLERS  
WELCOME**

ALL MERCHANDISE FULLY GUARANTEED

**NEWMART  
ELECTRONICS**


Mail Order Dept PW.12  
Belmont St, Monton,  
Eccles, Manchester.  
Tel: 061-789 5268

Manchester  
30-32 Shudehill, tel 061-832 7710  
Leeds  
4 New Market St tel 0532 42708  
Liverpool  
15 Whitechapel tel 051-236 0738

# R T V C FOR AUDIO ON A BUDGET

## PUSH BUTTON CAR RADIO KIT

### The Tourist II

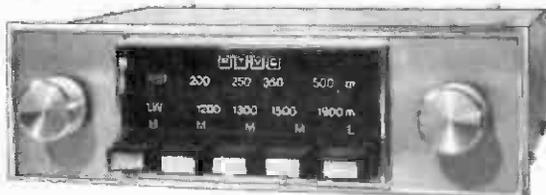

**NO SOLDERING  
REQUIRED!**

#### NOW BUILD YOUR OWN PUSH BUTTON CAR RADIO

Easy to assemble construction kit comprising fully completed and tested printed circuit board on which no soldering is required. All connections are simple push fit type making for easy assembly.

Fine tuning push button mechanism is fully built and tested to mate with printed circuit board.

**Car Radio Kit £7.70 + 55p p & p**

**The Tourist I Kit** For the experienced constructor  
If you can solder on a printed circuit board you can build this model.  
Some technical specification as Tourist II  
**Price £6.60 + 55p p & p.**

#### Technical specification :

- (1) Output 4 watts R.M.S. output. For 12 volt operation on negative or positive earth.
- (2) Integrated circuit output stage, pre-built three stage IF Module.

**Controls** volume manual tuning and live push buttons for station selection, illuminated tuning scale covering full, medium and long wave bands.

Size chassis 7" wide, 2" high and 4 1/4" deep approx

**Speaker** including baffle and fixing strip **£1.65+23p.p&p.**

**Car Aerial** Recommended — fully retractable and locking  
**£1.37+20p. postage & packing**



## \* STEREO 21 QUALITY SOUND FOR LESS THAN £20.00

Stereo 21, easy to assemble audio system kit. No soldering required. The unit is finished in white P.V.C. and the acrylic top presents an unusually interesting variation on the modern deck plinths.

**Includes:**— BSR 3 speed deck, automatic, manual facilities together with ceramic cartridge.

**Two speakers** with cabinets.

**Amplifier module.** Ready built with control panel, speaker leads and full, easy to follow assembly instructions.

**Specifications:** For the technically minded:—

Input sensitivity 80mV. Aux. input sensitivity 120mV. Power output 2.7 watts per channel.

Output impedance 8-15 ohms. Stereo headphone socket with automatic speaker cutout. Provision for auxiliary inputs—radio, tape, etc., and outputs for taping discs. **Overall Dimensions.** Speakers approx. 15 1/2" x 8" x 4". Complete deck and cover in closed position approx. 15 1/2" x 12" x 6".

**Complete only £19.95 — £1.60 p & p.** Extras if required. **Optional Diamond Stylus £1.37.**

Specially selected pair of stereo headphones with individual level controls and padded earpieces to give optimum performance. **£3.85.**



## BUILD YOUR OWN \* STEREO AMPLIFIER

For the man who wants to design his own stereo—here's your chance to start, with Unisound—pre-amp, power amplifier and control panel. No soldering—just simply screw together. 4 watts per channel into 8 ohms. Inputs: 120mV (for ceramic cartridge). The heart of Unisound is high efficiency I.C. monolithic power chips which ensure very low distortion over the audio spectrum. 240V. AC only.

**£7.64 + 55p. p & p**

## 8 TRACK HOME CARTRIDGE PLAYER\*



Elegant self selector push button player for use with your stereo system. Compatible with Viscount III system, Unisound module and the Stereo 21. Technical specification Mains input, 240V. Output sensitivity 125mV. Comparable unit sold elsewhere at £24.00 approx. Yours for only

**£11.95 + 90p p & p.**

# COMPLETE\* STEREO SYSTEM



## System 1. £51.00

40 Watt Amplifier. Viscount III - R102 now 20 watts per channel.

System 1 includes:

Viscount III amplifier - volume, bass, treble and balance controls, plus switches for mono/stereo on/off function and bass and treble filters. Plus headphone socket.

Specification

20 watts per channel into 8 ohms. Total distortion @ 10W @ 1kHz 0-1%. P.U.1 (for ceramic cartridges) 150mV into 3 Meg. P.U.2 (for magnetic cartridges) 4mV @ 1kHz into 47K, equalised within  $\pm 1$ dB R.I.A.A. Radio 150mV into 220K. (Sensitivities given at full power). Tape out facilities: headphone socket, power out 250mW per channel. *Tone controls and filter characteristics.* Bass:  $\pm 12$ dB to  $-17$ dB @ 60Hz. Bass filter: 6dB per octave cut. Treble control: treble  $\pm 12$ dB to  $-12$ dB @ 15kHz. Treble filter: 12dB per octave. *Signal to noise ratio:* (all controls at max.) -58dB. Crosstalk better than 35dB on all inputs. Overload characteristics better than 26dB on all inputs. Size approx. 13 $\frac{1}{2}$ " x 9" x 3 $\frac{1}{2}$ ".

Garrard SP 25 Mk III deck with magnetic cartridge, de luxe plinth and hinged cover.

Two Duo Type II matched speakers - Enclosure size approx. 17 $\frac{1}{2}$ " x 10 $\frac{1}{2}$ " x 6" in simulated teak. Drive unit 13" x 8" with parasitic tweeter. 10 watts handling.

Complete System £51.00

## System 2. £69.00

Viscount III amplifier (As System 1)

Garrard SP 25 Mk III deck (As System 1)

Two Duo Type III matched speakers - Enclosure size approx. 27" x 13" x 11 $\frac{1}{2}$ "

Finished in teak veneer. Drive units 13" x 8" bass driver, and two 3" (approx.) tweeters.

20 watts R.M.S., 8 ohms frequency range - 20 Hz to 18,000 Hz.

Complete System £69.00

### PRICES: SYSTEM 1

Viscount III R102 amplifier	£24.20 + £1 p & p
2 Duo Type II speakers	£14.00 + £2.20 p & p
Garrard SP 25 with Mag. cartridge de luxe plinth and hinged cover	£21.00 + £1.75 p & p
<b>total:</b>	<b>£59.20</b>

Available complete for only:

**£51.00**  
- £3.50 p & p

### PRICES: SYSTEM 2

Viscount III R102 amplifier	£24.20 + £1 p & p
2 Duo Type III speakers	£39.00 + £4.00 p & p
Garrard SP 25 with Mag. cartridge de luxe plinth and hinged cover	£21.00 + £1.75 p & p
<b>total:</b>	<b>£84.20</b>

Available complete for only:

**£69.00**  
+ £4.00 p & p

# EMI SPEAKERS AT FANTASTIC REDUCTIONS

## 20 WATT SPEAKER SYSTEM

System consists of a 13" x 8" (approx.) elliptical woofer unit with a 8" x 5" (approx.) mid range unit incorporating parasitic tweeter and crossover components.

**Technical Specification:**

**Bass Unit**  
Flux density-100 K, speech coil-1 $\frac{1}{2}$ ", Cone, Triple laminated paper with P.V.C. surround.  
**Mid Range Unit**  
Flux density-33K, speech coil-1" with parasitic tweeter.  
**Power Handling**  
20 watts R.M.S., impedance - 8 ohms, frequency response - 20 Hz to 18,000 Hz.

**OUR PRICE**  
**£6.60. Complete**  
+ 90p p & p.



## 15" 14A/780 BASS UNIT

Bass unit on a rigid diecast chassis. Superior cone material handles up to 50 watts RMS, and is treated to give a smooth frequency response. Resonance 30 Hz. Flux density 360,000 Maxwell. Impedance at 1 kHz is 8 ohms. 3" voice coil.

**Recommended retail price £40.80.**  
**OUR PRICE £18.70 + £1.50 p & p**



## 950 KIT

Five matched speakers and crossover unit for handling up to 45 watts, frequency response from 20 to 20,000 Hz.

Huge 19" x 14" (approx.) high efficiency Bass Speaker with 16,500-gauss magnet built on a heavy diecast frame. The four 10,000 gauss tweeters, each 3 $\frac{1}{2}$ " dia, approx., are fed by the crossover which critically adjusts signal for maximum fidelity. Impedance at 1 kHz is 8 ohms Bass coil 2", others 0-5".  
**Recommended list price £44.00**

**Special Offer**  
**OUR PRICE £19.50 + £1.50 p & p**

FOR DISCO PAGE AND DETAILS OF HOW TO ORDER - TURN OVER...




# PORTABLE DISCO CONSOLE

**INCORPORATES:** Pre-Amp with full mixing facilities, including switched input for mic with volume control, switched input for auxiliary with volume control, bass and treble controls, volume control and blend control for turntables.

Two B.S.R. single play professional series decks, fitted with crystal cartridges.

The turntables are designed and precision engineered. They combine clean modern styling with superb reproduction. Their many special features include square section aluminium tonearms. (high precision low mass design fully counterbalanced, with calibrated stylus pressure control for perfect tracking), and conveniently grouped easy to read linear controls. The turntables have viscous cueing devices which allows the tonearms to be placed or lifted at any point on the record.

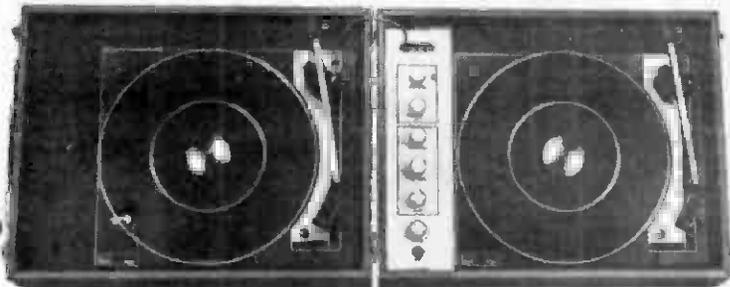The two lightweight cartridge shells have slide-in-holders to facilitate easy inspection of needles and cartridges.



## TECHNICAL SPECIFICATION:

Pre-amp - Output - 200mV. Auxiliary inputs - 200mV and 750mV into 1 meg. Mic Input - 6mV into 100K. 240 volt operation.

Turntables capacity - 7", 10" or 12" records.

Rumble, wow and flutter - Rumble - Better than -35dB. Wow - Better than 0.2%. Flutter - Better than 0.05% (Gaumont kalee meter).

Finish - Satin black mainplate with black turntable mat inlaid with brushed aluminium trim. Tonearm and controls in black and brushed aluminium.


Console size - Unit Closed - 17 1/2" x 13 1/2" x 8 1/2" (approx.)  
Unit Open - 35 1/2" x 13 1/2" x 4 1/2" (approx.)

This disco console is ideally matched for the Reliant IV and Disco 50 or any other quality amplifier.

The unit is finished in black PVC with contrasting simulated teak edging diamond spun control knobs with matching control panel.


Yours for only **£45.00 + £3.50 P. & P.**

# DISCO 50

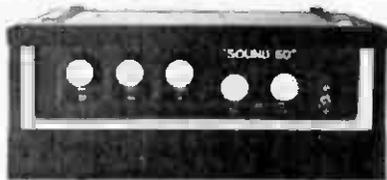
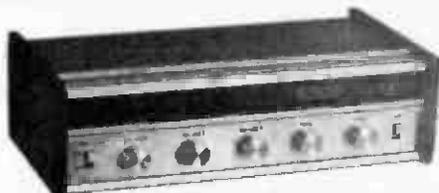
## 45 WATT R.M.S. MONO DISCOTHEQUE AMPLIFIER

Ideal for Disco Work. Output Power: 45 watts R.M.S. Frequency Response 3dB points 30Hz and 18KHz. Total Distortion: less than 2% at rated output. Signal to noise ratio: better than 60dB. Bass Control Range: 13dB at 60Hz. Treble Control Range: 12dB at 10KHz. Inputs: 4 inputs at 5mV into 470K. Each pair of inputs controlled by separate volume control. 2 inputs at 200mV into 470K. Size: 19 1/4" x 10 1/2" x 8" (approx.) Amplifier **£27.50 + £1.50 p. & p.**



# DISCO AMPLIFIER

Reliant Mk IV Mono Amplifier, ideal for the small disco or house parties.

Outputs 20 watts R.M.S. into 8 ohm (suitable for 15 ohms).

Inputs \*4 electrically mixed inputs. \*3 individual mixing controls.

\*Separate bass and treble controls common to all 4 inputs.

\*Mixer employing F.E.T. (Field Effect Transistors) \*Solid State circuitry.

\*Attractive styling.

## INPUT SENSITIVITIES

-Input - 1.) Crystal mic, guitar or moving coil mic. 2 and 10mV.

(Selector switch for desired sensitivity).

-Inputs - 2), 3), 4). Medium output equipment - ceramic cartridge, tuner, tape recorder, organs, etc. - all 250mV sensitivity. AC Mains, 240V operation.

Size approx: 12 1/2" x 6" x 3 1/2".

**£15.00 + 60p. post & pack.**



**DO NOT SEND YOUR CARD**

Just write your order giving your credit card number

Mail orders to Acton. Terms C.W.O. All enquires Stamped Addressed Envelope. Goods not despatched outside U.K.

Leaflets available for all items listed thus ✱ Send stamped addressed envelope.



Radio and TV Components (Acton) Ltd.

21 High Street, Acton, London W3 6NG  
323 Edgware Road, London W2

Personal Shoppers — Edgware Road: 9a.m.-5.30p.m. Half day Thurs.  
Acton: 9.30a.m.-5p.m. Closed all day Wed.

# TRANSFORMERS

**SAFETY MAINS ISOLATING TRANSFORMERS**  
Prr. 120/240 V Sec. 120/240 V Centre Tapped and Screened

Ref. No.	VA (Watts)	Weight lb oz	Size cm.	£	P & P
07	20	1 8	7.0 x 6.0 x 6.0	2.55	38
149	60	3 12	9.9 x 7.7 x 8.6	3.79	45
150	100	5 8	9.9 x 8.9 x 8.6	4.17	45
151	200	8 0	12.1 x 9.3 x 10.2	7.39	53
152	250	13 12	12.1 x 11.8 x 10.2	9.45	73
153	350	15 0	14.0 x 10.8 x 11.8	11.35	73
154	500	19 8	14.0 x 13.4 x 11.8	13.30	91
155	750	29 0	17.2 x 14.0 x 14.0	21.05	*
156	1000	38 0	17.2 x 16.6 x 14.0	27.20	*
158	2000	60 0	21.6 x 15.3 x 18.1	50.25	*

**AUTO TRANSFORMERS**

Ref. No.	VA (Watts)	Weight lb oz	Size cm.	Auto Taps	£	P & P
113	20	1 0	5.8 x 5.1 x 4.5	0-115-210-240	1.34	30
64	75	2 4	7.4 x 6.7 x 6.1	0-115-210-240	2.64	38
4	150	3 4	7.7 x 7.2	0-115-200-220-240	3.29	45
66	100	6 4	9.9 x 9.6 x 8.6	...	5.29	53
67	500	12 8	12.1 x 11.2 x 10.2	...	8.02	67
84	1000	19 8	14.0 x 13.4 x 14.3	...	13.50	91
93	1500	30 4	14.0 x 15.9 x 14.3	...	17.50	*
95	2000	32 0	17.2 x 16.6 x 14.0	...	25.35	*
73	3000	40 0	21.6 x 13.4 x 18.1	...	32.80	*

**CASED AUTO TRANSFORMERS**  
115V mains lead input and U.S.A. 2-pin outlets. 20VA £2.64 pp 38p  
500VA £9.50 pp 80p 1000VA £15.92 via B.R.S.

**TRANSFORMERS**

**PRIMARY 240-250 VOLTS 12 AND OR 24 VOLT RANGE**

Ref. No.	Amps.	Weight lb oz	Size cm.	Secondary Windings	£	P & P
111	0.5	0.25	4.8 x 1.9 x 3.5	0-12V at 0-25A x 2	1.34	23
213	1.0	0.5	6.1 x 5.8 x 4.8	0-12V at 0-5A x 2	1.58	30
71	2	1	12.7 x 7.0 x 6.4	0-12V at 1A x 2	2.09	38
18	4	2	12.8 x 8.3 x 7.7	0-12V at 2A x 2	2.60	38
70	6	3	8.9 x 8.0 x 7.7	0-12V at 3A x 2	3.52	45
108	8	4	9.9 x 8.9 x 8.6	0-12V at 4A x 2	3.96	45
72	10	5	9.9 x 9.6 x 8.6	0-12V at 5A x 2	4.67	53
116	12	6	12.9 x 10.2 x 8.6	0-12V at 5A x 2	5.61	53
17	16	8	12.1 x 9.9 x 10.2	0-12V at 8A x 2	6.62	60
115	20	11	8.1 x 14.0 x 11.8	0-12V at 10A x 2	10.20	73
187	30	15	8.1 x 14.0 x 11.8	0-12V at 15A x 2	13.70	85
226	60	30	12.0 x 17.2 x 15.3	0-12V at 30A x 2	22.50	*

**30 VOLT RANGE**

Ref. No.	Amps.	Weight lb oz	Size cm.	Secondary Taps	£	P & P
112	0.5	1 4	6.1 x 5.8 x 4.8	0-12-15-20-24-30V	1.58	30
79	1.0	2	7.0 x 6.7 x 6.1	...	2.18	38
3	2.0	3 4	8.9 x 7.7 x 7.7	...	3.18	38
20	3.0	4 8	9.9 x 8.3 x 8.6	...	4.12	45
21	4.0	6 4	9.9 x 9.6 x 8.6	...	4.67	53
51	5.0	6 12	12.1 x 8.6 x 10.2	...	5.83	53
117	6.0	8 0	12.1 x 9.3 x 10.2	...	6.99	60
88	8.0	12 0	12.1 x 11.8 x 10.2	...	9.00	67
89	10.0	13 12	14.0 x 10.2 x 11.8	...	9.80	73

**50 VOLT RANGE**

Ref. No.	Amps.	Weight lb oz	Size cm.	Secondary Taps	£	P & P
102	0.5	1 2	7.0 x 6.4 x 6.1	0-19-25-33-40-50V	2.09	30
103	1.0	2 12	8.3 x 7.4 x 7.0	...	3.08	38
104	2.0	5 8	9.9 x 8.9 x 8.6	...	4.26	45
105	3.0	6 12	9.9 x 10.2 x 8.6	...	5.79	53
106	4.0	10 0	12.9 x 10.5 x 10.2	...	7.41	67
107	6.0	12 0	14.0 x 10.2 x 11.8	...	11.00	67
118	8.0	18 0	14.0 x 12.7 x 11.8	...	13.40	85
119	10.0	25 0	17.2 x 12.7 x 14.0	...	17.60	*

**60 VOLT RANGE**

Ref. No.	Amps.	Weight lb oz	Size cm.	Secondary Taps	£	P & P
124	0.5	2 4	7.0 x 6.7 x 6.1	0-24-30-40-48-60	2.12	38
126	1.0	3 4	7.0 x 7.7 x 7.7	...	2.97	38
127	2.0	6 4	9.9 x 9.6 x 8.6	...	5.40	45
125	3.0	8 12	12.1 x 9.9 x 10.2	...	7.11	60
123	4.0	13 12	12.1 x 11.8 x 10.2	...	9.20	67
40	5.0	12 00	14.0 x 10.2 x 11.8	...	10.83	73
120	6.0	15 8	14.0 x 12.1 x 11.8	...	13.35	85
121	8.0	21 00	14.0 x 14.7 x 11.8	...	15.01	*
122	10.0	25 0	17.2 x 12.7 x 14.0	...	19.60	*
189	12.0	29 00	17.2 x 14.0 x 14.0	...	21.60	*


**MINIATURE TRANSFORMERS WITH SCREENS P & P**

Ref. No.	MA	Weight	Size cm.	VOLTS	£	P
238	200	2	2.8x2.6x2.0	3-0-3	1.40	10
212	1A 1A	1	4.6x5.8x4.8	0-6-0-6	1.67	30
13	100	1	4.9x2.6x2.9	9-0-9	1.28	13
235	230, 330	4	4.8x2.9x3.5	0-8-9-0-8-9	2.23	30
207	500, 500	1 00	6.1x5.4x4.8	0-8-9-0-8-9	3.00	35
208	1A 1A	1	7.0x6.4x6.1	0.15, 0.15	1.70	19
236	200, 200	4	4.8x2.9x3.5	0.20, 0.20	1.34	30
214	300, 300	1	4.6x5.8x4.8	20-12-0-12-20	1.98	38
226	700 (D.C.)	1	8.7x6.1x6.1	0-15-20, 0-15-20	3.78	38
201	1A 1A	2	12.8x3.2x7.0	0-15-27, 0-15-27	3.06	38
203	500, 500	2	4.8x3.7x5.7	0-15-27, 0-15-27	3.06	38
204	1A 1A	3	8.9x7.7x7.7	0-15-27, 0-15-27	3.27	38

PLEASE ADD 8% FOR V.A.T.  
INCLUDING P. & P.

**BARRIE electronics**  
3, THE MINORIES, LONDON EC3N 1BJ  
TELEPHONE: 01-488 3316/8  
NEAREST TUBE STATIONS: ALDGATE & LIVERPOOL ST.
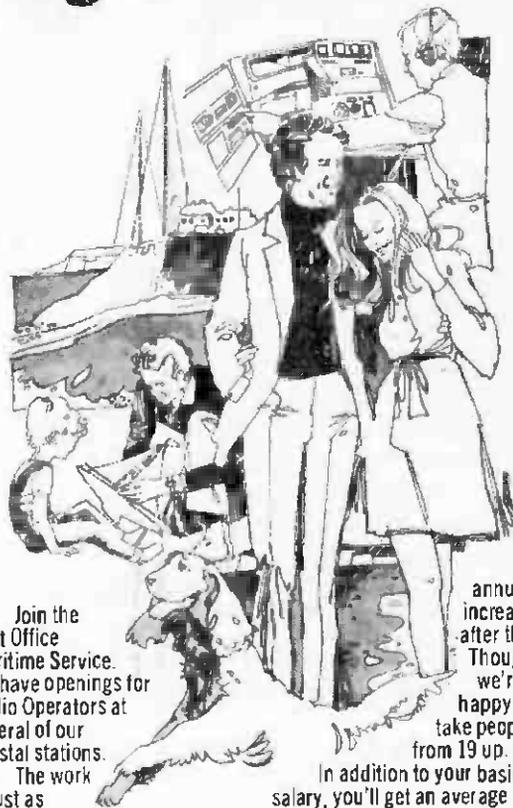
# Radio Operators. How to see more of your wife without losing sight of the sea.



Join the  
Post Office  
Maritime Service.  
We have openings for  
Radio Operators at  
several of our  
coastal stations.

annual  
increases  
after that.  
Though  
we're  
happy to  
take people  
from 19 up.

The work  
is just as  
interesting, just  
as rewarding as aboard ship,  
but you get home to see your  
wife and family more often. You  
need a United Kingdom General  
or First Class Certificate in  
Radiocommunications, or an  
equivalent certificate issued by a  
Commonwealth Administration  
or the Irish Republic.

In addition to your basic  
salary, you'll get an average  
allowance of £450 a year for  
shift duties and there are  
opportunities for overtime.

Other benefits include a  
good pension scheme, sick pay  
and prospects of promotion to  
Senior Management.

For more information, write  
to: ETE Maritime Radio Services  
Division (RC12), ET 17.1.1.2.,  
Room 643, Union House,  
St. Martins-le-Grand, London,  
EC1A 1AS.

Starting pay for a man of  
25 or over is £2,270, plus cost of  
living allowance with further

Post Office  
Telecommunications


**FIRST TIME EVER! SAVE £15.12!**

**BRAND NEW AC/DC BATTERY/MAINS**

**Cassette**

**TAPE RECORDER & PLAYER**

With remote control microphone

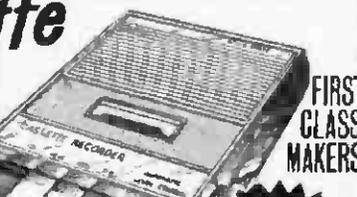

**FIRST CLASS MAKERS**

WE COULD CHARGE UP TO £26.97!

**OUR PRICE £11.85**  
POST ETC. 50p

Due to price we cannot name 'makers' but rest assured you're getting one of the BEST! Expensive "PIANO KEYBOARD" CONTROL PANEL (or latest MASTER SWITCH control) and AUTOMATIC LEVEL CONTROL. No fiddling with awkward tape and reels, just "slap-in" a cassette. Superb taping & reproduction! Takes 30, 60 or 90 minute standard cassette tapes. Beautiful, tone from a whisper to a roar! Remote control microphone! Rapid rewind! Fast forward! Complete record & replay. Indoors or out! Runs on standard batteries AND 220/240V A.C. mains. Separate jacks for remote-control microphone, etc. 9 1/2" x 5 1/2" x 2 1/2" approx. Design can vary slightly. With carry handle. **WRITTEN GUARANTEE** and instructions. (Importers recommended selling price £26.97) **OUR PRICE £11.85**, post, etc., 50p. ★ Save quickly, test on mail order 7 days approval from receipt of goods. Refund if not delighted. **BONUS OFFER:** Cassette tapes, batteries and microphone stand 35p if required. A.S.C.O. Super deluxe model with VHF, AM/FM radio (recommended retail price £49), only £22.15, carr. 50p (batteries and cassette tape 45p extra if required).

CALLERS: ACCESS & BARCLAYCARDS ACCEPTED AT STORES.

**SHOPERTUNITIES LTD.**

**SAVE £21.56!**

**FABULOUS BRAND NEW SOLID STATE AC/DC MAINS/BATTERY**

**COMBINED V.H.F. AM/FM RADIO AND CASSETTE TAPE RECORDER AND PLAYER**



IMPORTERS RECOMMENDED SELLING PRICE £44.51!

**OUR PRICE £22.95**

Latest sensation in the world of sound! First class makers! Fabulous VHF AM/FM RADIO and CASSETTE TAPE RECORDER & PLAYER combined! Runs off standard batteries or Mains (simply plug in mains 220/240V. A.C. line cord supplied)—NOW you can record & play back anything, anywhere! **IMPORTERS RECOMMENDED SELLING PRICE £44.51! WE OFFER AT ALMOST HALF PRICE!** Fantastic specification— "Automatic" recording level control! "Monitor" switch! "Expensive" calibrated "slider" volume and tone controls! "MASTER SWITCH" fast forward, stop, play & rapid rewind control! "Suparb" built-in Speaker! "Takes standard 30, 60, or 90 minute Cassette tapes, obtainable everywhere. "Earphone" & extension speaker sockets PLUS separate input/output DIN Jack socket! "Built-in" swivel 7 section telescopic aerial (12" approx.) "Magnificent" case (approx. 10ins. high in luxurious Black & Silver finish with "teak-grain" speaker grille. "Built-in" carry handle. "Wonderful" VHF AM/FM Radio with instant switch-over waveband selection & pin-point station tuner. Superb clarity and tone. Amazing station selection home & abroad including local reception of city & regional stations in every part of the country (even those scheduled for the future) plus BBC National VHF. Also fabulous in Car! You could pay £££'s more for a Radio or Car Cassette player ALONE! Yes, only £22.95 carr. etc. 50p, complete with remote control microphone, etc. Written Guarantee & simple instructions. **BONUS OFFER:** Batteries, Cassette Tape, personal listening cassette, and microphone stand, all for only 55p extra, if required. Send total £24 (to include Bonus Carr. etc.) and test on 7 days mail order approval from receipt of goods. **REFUND IF NOT DELIGHTED.** Or call at either Showpartunities store.

Dept. WPH/1, 164 UXBRIDGE RD. (facing Shepherds Bush Green), LONDON W12 8AQ. (Thurs. 1, Fri. 2). Also at 37/39 HIGH HOLBORN (opposite "Control") LONDON W.C.1. (Thurs. 7 P.M.). BOTH OPEN MON. TO SAT. 9 A.M. TILL 5 P.M.

**BENTLEY ACOUSTIC CORPORATION LTD.**

76 GLOUCESTER ROAD, LITTLEHAMPTON, SUSSEX  
All prices inclusive of V.A.T. Telephone 6742

089 .40	5BC8	80	6L13	58	128C7	50	252G7	78	83F3	1.50	EC186	50	2Z21	58	PCL84	46	UC92	46	Transistor	AF117	21	BY218	88	
024 .47	6B86	86	6L18	6.00	128G7	60	42	1.00	83B0C	76	EC186	46	B280	28	PCL86	47	UC94	76	3N4744	16	AF124	98	OA10	47
1A8 .45	6B86	86	6L18	6.00	128G7	75	128H7	36	60B85	86	EC20C	76	GT01	70	PCL306	86	UC94	8.00	3N4744	20	AF126	19	OA47	11
1AG70 .50	6B10	55	6N74T	60	18H7	44	10C8	60	8100T	1.00	EP91	87	Q233	80	PN248	80	UCM1	8.00	PN248	58	AF130	80	OA10	17
1AGT8 .55	6B10	55	6Q7Q	50	128Q7	55	60D05	1.25	81P2C1	25	EP92	87	Q233	80	PN248	80	UCM1	8.00	PN248	58	AF130	80	OA10	17
1B80T .80	6B17	1.00	6Q7Q	60	128H7	75	60R06	76	81J48	58	EP97	80	Q233	80	PN248	80	UCM1	8.00	PN248	58	AF130	80	OA10	17
1B80T .80	6B17	1.00	6Q7Q	60	128H7	75	60R06	76	81J48	58	EP97	80	Q233	80	PN248	80	UCM1	8.00	PN248	58	AF130	80	OA10	17
1B80T .80	6B17	1.00	6Q7Q	60	128H7	75	60R06	76	81J48	58	EP97	80	Q233	80	PN248	80	UCM1	8.00	PN248	58	AF130	80	OA10	17
1L4 .25	6B87	1.40	6R7Q	60	128T7	80	81A7	50	81A75	1.00	EP18	80	Q233	80	PN248	80	UCM1	8.00	PN248	58	AF130	80	OA10	17
1N80T .45	6B70	50	6R75	75	128A7	80	81A7	50	81A75	1.00	EP18	80	Q233	80	PN248	80	UCM1	8.00	PN248	58	AF130	80	OA10	17
1R9 .45	6B77	70	6A71	44	19G8	6.00	90AC	2.50	80A91	76	EP504	1.25	ET41	1.00	PL84	40	UW41	45	AC107	17	BC115	28	OC70	14
1R9 .45	6B77	70	6A71	44	19G8	6.00	90AC	2.50	80A91	76	EP504	1.25	ET41	1.00	PL84	40	UW41	45	AC107	17	BC115	28	OC70	14
1R9 .45	6B77	70	6A71	44	19G8	6.00	90AC	2.50	80A91	76	EP504	1.25	ET41	1.00	PL84	40	UW41	45	AC107	17	BC115	28	OC70	14
1R9 .45	6B77	70	6A71	44	19G8	6.00	90AC	2.50	80A91	76	EP504	1.25	ET41	1.00	PL84	40	UW41	45	AC107	17	BC115	28	OC70	14
1R9 .45	6B77	70	6A71	44	19G8	6.00	90AC	2.50	80A91	76	EP504	1.25	ET41	1.00	PL84	40	UW41	45	AC107	17	BC115	28	OC70	14
1R9 .45	6B77	70	6A71	44	19G8	6.00	90AC	2.50	80A91	76	EP504	1.25	ET41	1.00	PL84	40	UW41	45	AC107	17	BC115	28	OC70	14
1R9 .45	6B77	70	6A71	44	19G8	6.00	90AC	2.50	80A91	76	EP504	1.25	ET41	1.00	PL84	40	UW41	45	AC107	17	BC115	28	OC70	14
1R9 .45	6B77	70	6A71	44	19G8	6.00	90AC	2.50	80A91	76	EP504	1.25	ET41	1.00	PL84	40	UW41	45	AC107	17	BC115	28	OC70	14
1R9 .45	6B77	70	6A71	44	19G8	6.00	90AC	2.50	80A91	76	EP504	1.25	ET41	1.00	PL84	40	UW41	45	AC107	17	BC115	28	OC70	14
1R9 .45	6B77	70	6A71	44	19G8	6.00	90AC	2.50	80A91	76	EP504	1.25	ET41	1.00	PL84	40	UW41	45	AC107	17	BC115	28	OC70	14
1R9 .45	6B77	70	6A71	44	19G8	6.00	90AC	2.50	80A91	76	EP504	1.25	ET41	1.00	PL84	40	UW41	45	AC107	17	BC115	28	OC70	14
1R9 .45	6B77	70	6A71	44	19G8	6.00	90AC	2.50	80A91	76	EP504	1.25	ET41	1.00	PL84	40	UW41	45	AC107	17	BC115	28	OC70	14
1R9 .45	6B77	70	6A71	44	19G8	6.00	90AC	2.50	80A91	76	EP504	1.25	ET41	1.00	PL84	40	UW41	45	AC107	17	BC115	28	OC70	14
1R9 .45	6B77	70	6A71	44	19G8	6.00	90AC	2.50	80A91	76	EP504	1.25	ET41	1.00	PL84	40	UW41	45	AC107	17	BC115	28	OC70	14
1R9 .45	6B77	70	6A71	44	19G8	6.00	90AC	2.50	80A91	76	EP504	1.25	ET41	1.00	PL84	40	UW41	45	AC107	17	BC115	28	OC70	14
1R9 .45	6B77	70	6A71	44	19G8	6.00	90AC	2.50	80A91	76	EP504	1.25	ET41	1.00	PL84	40	UW41	45	AC107	17	BC115	28	OC70	14
1R9 .45	6B77	70	6A71	44	19G8	6.00	90AC	2.50	80A91	76	EP504	1.25	ET41	1.00	PL84	40	UW41	45	AC107	17	BC115	28	OC70	14
1R9 .45	6B77	70	6A71	44	19G8	6.00	90AC	2.50	80A91	76	EP504	1.25	ET41	1.00	PL84	40	UW41	45	AC107	17	BC115	28	OC70	14
1R9 .45	6B77	70	6A71	44	19G8	6.00	90AC	2.50	80A91	76	EP504	1.25	ET41	1.00	PL84	40	UW41	45	AC107	17	BC115	28	OC70	14
1R9 .45	6B77	70	6A71	44	19G8	6.00	90AC	2.50	80A91	76	EP504	1.25	ET41	1.00	PL84	40	UW41	45	AC107	17	BC115	28	OC70	14
1R9 .45	6B77	70	6A71	44	19G8	6.00	90AC	2.50	80A91	76	EP504	1.25	ET41	1.00	PL84	40	UW41	45	AC107	17	BC115	28	OC70	14
1R9 .45	6B77	70	6A71	44	19G8	6.00	90AC	2.50	80A91	76	EP504	1.25	ET41	1.00	PL84	40	UW41	45	AC107	17	BC115	28	OC70	14
1R9 .45	6B77	70	6A71	44	19G8	6.00	90AC	2.50	80A91	76	EP504	1.25	ET41	1.00	PL84	40	UW41	45	AC107	17	BC115	28	OC70	14
1R9 .45	6B77	70	6A71	44	19G8	6.00	90AC	2.50	80A91	76	EP504	1.25	ET41	1.00	PL84	40	UW41	45	AC107	17	BC115	28	OC70	14
1R9 .45	6B77	70	6A71	44	19G8	6.00	90AC	2.50	80A91	76	EP504	1.25	ET41	1.00	PL84	40	UW41	45	AC107	17	BC115	28	OC70	14
1R9 .45	6B77	70	6A71	44	19G8	6.00	90AC	2.50	80A91	76	EP504	1.25	ET41	1.00	PL84	40	UW41	45	AC107	17	BC115	28	OC70	14
1R9 .45	6B77	70	6A71	44	19G8	6.00	90AC	2.50	80A91	76	EP504	1.25	ET41	1.00	PL84	40	UW41	45	AC107	17	BC115	28	OC70	14
1R9 .45	6B77	70	6A71	44	19G8	6.00	90AC	2.50	80A91	76	EP504	1.25	ET41	1.00	PL84	40	UW41	45	AC107	17	BC115	28	OC70	14
1R9 .45	6B77	70	6A71	44	19G8	6.00	90AC	2.50	80A91	76	EP504	1.25	ET41	1.00	PL84	40	UW41	45	AC107	17	BC115	28	OC70	14
1R9 .45	6B77	70	6A71	44	19G8	6.00	90AC	2.50	80A91	76	EP504	1.25	ET41	1.00	PL84	40	UW41	45	AC107	17	BC115	28	OC70	14
1R9 .45	6B77	70	6A71	44	19G8	6.00	90AC	2.50	80A91	76	EP504	1.25	ET41	1.00	PL84	40	UW41	45	AC107	17	BC115	28	OC70	14
1R9 .45	6B77	70	6A71	44	19G8	6.00	90AC	2.50	80A91	76	EP504	1.25	ET41	1.00	PL84	40	UW41	45	AC107	17	BC115	28	OC70	14
1R9 .45	6B77	70	6A71	44	19G8	6.00	90AC	2.50	80A91	76	EP504	1.25	ET41	1.00	PL84	40	UW41	45	AC107	17	BC115	28	OC70	14
1R9 .45	6B77	70	6A71	44	19G8																			

At three ha'pence a pint  
you gotta pick a  
packet, or two!



Around 1780 Sarah Oliver kept the colourful Bay Horse Inn in North Shields - the haunt of sailors, labourers, thieves and gentlemen who settled to her much-loved brew, said by many to "preserve the wind".

Times change, but good things don't.

Now from the same building on Horse Ferry Landing, Geordie Home Brews bring you all the natural, wholesome ingredients you need to brew a strong, natural beer like the one Sarah Oliver served. And still at a ridiculous 13p per pint!



**Sarah Oliver's Home Brew**

BY GEORDIE HOME BREWS  
from your usual Geordie Stockist  
Enquiries to: VIKING BREWS LTD.  
CLIVE STREET NORTH SHIELDS



# WILMSLOW AUDIO

THE Firm for speakers!

## SPEAKERS

Baker Group 25 3, 8 or 15 ohm £7-75  
Baker Group 38 3, 8 or 15 ohm £8-50  
Baker Group 50/2 8 or 15 ohm £12-50  
Baker Deluxe 12" d/cone £10-75  
Baker Major " " £8-50  
Baker Regent " " £7-75  
Baker Superb " " £14-50  
Baker Auditorium 12" £12-50  
Celebration PS79 for Unilux £18-95  
Celebration G12M 8 or 15 ohm £2-55  
Celebration G12H 8 or 15 ohm £12-00  
Celebration G15C 8 or 15 ohm £15-00  
Celebration G18C 8 or 15 ohm £24-00  
Coral 6 1/2" d/cone roll surr. 8 ohm £33-00  
Coral 8" d/cone roll surr. 8 ohm £2-50  
EMI 13 x 8 3, 8 or 15 ohm £3-25  
EMI 13 x 8 150 d/c 3, 8 or 15 ohm £2-50  
EMI 13 x 8 450 t/w 3, 8 or 15 ohm £3-75  
EMI 13 x 8 type 350 8 or 15 ohm £8-25  
EMI 13 x 6 20 watt base £8-80  
EMI 6 1/2" 91350 4 or 8 ohm £2-50  
EMI 5" 90130C 2 ohm £2-50  
EMI 8 x 5 d/cone roll surr 10 watt £2-50  
EMI 25" tweeter 97492AT -85  
Eagle DT38 30 watt tweeter £5-45  
Eagle HT15 horn tweeter £3-00  
Eagle CTS cone tweeter £1-75  
Eagle CT1D tweeter 8 or 16 ohm £2-55  
Eagle MHT10 horn tweeter £3-80  
Eagle crossover CN23, CN28, CN216 £1-50  
Eagle FR4 £5-30  
Eagle FR65 £8-35  
Eagle FR8 £10-65  
Elec 9 x 5, 59RM109 15 ohm £2-80  
59RM114 8 ohm £2-80  
Elec 6 1/2" 6RM171 d/c roll surr. £3-90  
Elec 6 1/2" 6RM220 d/cone £2-85  
Elec 4" tweeter TW4 £1-21  
Elec 10" d/cone 10RM229 8 ohm £2-83  
Elec 8" 8CS175 3 ohm £2-50  
Fane Pop 15 watt 12" £4-80  
Fane Pop 25/2 25 watt 12" £6-45  
Fane Pop 40 watt 10" £8-50  
Fane Pop 50 watt 12" £11-00  
Fane Pop 55 12" 60 watt £12-50  
Fane Pop 60 watt 15" £13-00  
Fane Pop 100 watt 18" £32-50  
Fane Crescendo 12A 100 watt 12" £38-00  
Fane Crescendo 12B bass £20-00  
Fane Crescendo 15" 100 watt £38-00  
Fane Crescendo 18" 150 watt £48-50  
Fane 801T 8" d/c roll surr. £7-00  
Fane 807T 8" d/c roll surr. £2-85  
Fane 808T 8" d/c £2-75  
Fane 101 twin ribbon horn £35-00  
Fane 910 horn £12-75  
Fane 920 horn £33-00

Goodmans 8P 8 or 15 ohm £5-00  
Goodmans 10P 8 or 15 ohm £5-30  
Goodmans 12P 8 or 15 ohm £12-95  
Goodmans 12P-D 8 or 15 ohm £18-75  
Goodmans 12P-G 8 or 15 ohm £15-75  
Goodmans Audiomax 12A X 100 watt £37-50  
Goodmans Audiomax 15AX £40-00  
Goodmans 15P 8 or 15 ohm £21-08  
Goodmans 18P 8 or 15 ohm £38-00  
Goodmans Midax 75D £18-00  
Goodmans Axent 100 tweeter £7-23  
Goodmans Audiom 100 12" £12-00  
Goodmans Axium 401 12" £17-25  
Goodmans Twinastom 8 £8-25  
Goodmans Twinastom 10 £9-00  
Kel T27 £5-25  
Kel T15 £6-00  
Kel B110 £7-25  
Kel B200 £7-25  
Kel B131 £14-25  
Kel DN8 £2-00  
Kel DN12 £4-95  
Kel DN13 £3-30  
STC4001G super tweeter £8-15  
Richard Allen CG8T 8" d/c r/surr. £8-35  
Wharfedale Super 10RS1DD 2 1/2" 8 ohm, 70mm 30 ohm, 70mm 8 ohm -95  
2 1/2" 75 ohm 50  
7" x 4" 3 or 8 ohm £1-40  
8" x 5" 3 or 8 ohm £1-50  
10" x 6" 3, 8 or 15 ohm £2-30

## SPEAKER KITS

Baker Major Module each £10-75  
Fane Mode One each £9-99  
Goodmans DIR 20 each £9-75  
Helm XLK 30 pair £22-00  
Helm XLK 35 pair £14-95  
Helm XLK 50 pair £39-95  
Kofit 2 each £24-75  
Kofit 3 each £36-75  
Richard Allen Twinklil each £8-99  
Richard Allen Triple 8 each £13-75  
Richard Allen Super Triple each £19-95  
Wharfedale Linfon 2 kit each £23-75  
Wharfedale Glendale 5 kit pair £19-25  
Wharfedale Dovedale 3 kit pair £32-50

## PA/DISCO AMPLIFIERS

(carr. and ins. £1)  
Baker Major 100 watt £49-75  
Linear 30/40 £30-00  
Linear 40/60 £35-00  
Linear 80/100 £38-95  
Linear 100 watt slave £44-00  
Eagle PA range in stock—ask for catalogue.

Free with speaker orders over £7—

"Hi-Fi Loudspeaker Enclosures" book. All units guaranteed new and perfect. Prompt despatch. Carriage and packing: speakers 38p each, speaker kits 75p each (£1.50 pair) tweeters and crossovers 20p.

ALL PRICES QUOTED INCLUDE VAT.  
WILMSLOW AUDIO (Dept. PW)

Loudspeakers: Swan Works, Bank Square, Wilmslow, Cheshire. SK9 1HF  
Discount Radio, PA, Hi-Fi: 10 Swan St, Wilmslow  
Send stamp for free booklet "Choosing a Speaker"



## Cassettes

The best buy!

Agfa Low Noise Cassettes  
AT LESS THAN  
HALF PRICE!

AGFA HIGHDYNAMIC  
SUPER

AGFA STEREO-CHROM  
CHROMIUM DIOXIDE

	1	5	10
C60	37p	£1-80	£3-50
C90	50p	£2-48	£4-95
C120	43p	£3-10	£8-20
	1	5	10
C50+6	50p	£2-40	£4-70
C90+6	68p	£3-35	£8-60
C120	99p	£4-80	£9-85
	1	5	10
C60	35p	£2-20	£4-30
C90	£1-08	£3-35	£7-10-60

SAME DAY DESPATCH. P. & P. 15p per order

**WILMSLOW AUDIO**  
(DEPT. PW)  
10 SWAN STREET, WILMSLOW,  
CHESHIRE, SK9 1HF


Cut-price prerecorded cassettes—send stamp for list

# RADIO & TV SERVICING


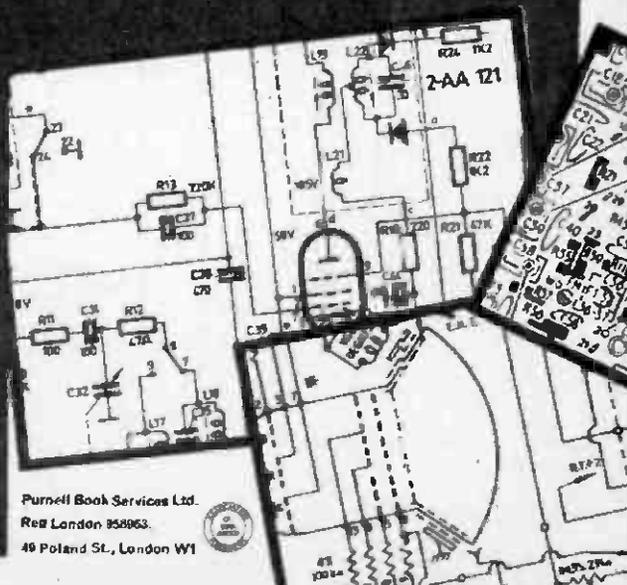
## Essential data for over 1500 popular models

With this vast 6-volume library at your fingertips you have all the necessary servicing data you need covering almost every popular model from 1968 to the very latest on the market today. And not only radio and TV but stereograms, record players and tape recorders too. Much of the earlier information on this equipment is quite unobtainable elsewhere and *Radio & TV Servicing* is now the only available source of technical data. The 1974 edition, now ready, brings the library right up-to-date with abstracts from manufacturers' service bulletins issued during the past year. *Radio & TV Servicing* is the only work of its kind—a money-spinner that no service engineer should be without.



Purnell Book Services Ltd.  
Reg London 350963.  
49 Poland St., London W1



## TWO NEW ADDITIONS TO FANE 'POP' RANGE LOUDSPEAKERS

### POP 20T 10" 20 Watt

Impedance  
8 ohms or  
15 ohms  
Gauss 14,000  
Voice Coil  
Diam. 1"  
Fitted  
Tweeter Cone  
Range  
50-15,000 Hz



**£8.50**

Rec. Retail Price inc. VAT


Also for those who can  
afford the very best  
For Instrument Reproduction

### Two Super Sensitive Models CRESCENDO '12' B

Ideal for Lead Guitar etc.  
12" 75 Watt 2" Pole Diam. Gauss 20,000
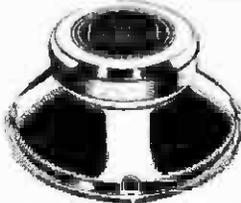
### CRESCENDO '15'

General Purpose  
15" 100 Watt 2" Pole Diam. Gauss 20,000



Rec.  
Retail  
Price

CRESCENDO '12' B  
**£39.95**

Rec.  
Retail  
Price


CRESCENDO '15'  
**£46.59**

There is also a 12" Crescendo  
Speaker for General Purpose  
Public Address, and a 12" and 15"  
for Bass Guitar etc.

Please send S.A.E. for leaflet on HORN  
UNITS & 'POP' or 'CRESCENDO' Range  
Speakers
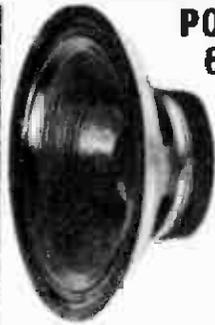
### POP 55 12" 60 Watt

Impedance  
8-15 ohms  
Gauss 15,000  
Voice Coil  
Diam. 2"  
Range 50-9,000 Hz  
AN ALL PURPOSE  
UNIT OF HIGH  
SENSITIVITY  
Rec. Retail Price  
inc. VAT



**£15.99**

### HIGH FREQUENCY HORN UNITS

#### MODEL 910

Rating 50  
watts with  
recommended  
filter

**£15.95**

Int. VAT

#### MODEL 920 Mk II (as illust)

SIGNIFICANTLY  
INCREASED SENSITIVITY.  
UNCHANGED PRICE. Rating with  
recommended filter

**£39.95** Inc. VAT

Filters for either model available if required



BRIEF DETAILS OF 'POP' RANGE  
NOW AVAILABLE IN 8 ohms or 15  
ohms

			Rec. Retail
POP '15'	12" 15 Watt	1" Voice Coil	£6.30 inc. VAT
POP '25T'	12" 25 Watt	1" Voice Coil	£8.95 inc. VAT
POP '50'	12" 50 Watt	2" Voice Coil	£12.95 inc. VAT
POP '60'	15" 60 Watt	2" Voice Coil	£16.95 inc. VAT
POP '100'	18" 100 Watt	3" Voice Coil	£31.00 inc. VAT

Distributors to Wholesale and Retail Traders—LINEAR PRODUCTS LTD., ELECTRON WORKS, ARMLEY, LEEDS.  
Manufacturers enquiries to—FANE ACOUSTICS LTD., 284 BRADFORD ROAD, BATLEY, YORKS  
Prices shown correct at Sept 2, 1974

## THE NEW NELSON-JONES FM TUNER



PUSH-BUTTON VARICAP DIODE  
TUNING (6 Position)

('WW' JUNE '73)

Exclusive Designer Approved Kits

What are the important features to look for in an FM tuner kit? Naturally it must have an attractive appearance when built, but it must also embody the latest and best in circuit design such as—

MOSFET front end for excellent cross modulation performance and low noise.  
3 GANG tuning for high selectivity.  
VARICAP tuning diodes in back to back configuration for low distortion.  
CERAMIC filters for defined IF response.  
INTEGRATED circuit IF amplifiers for reliability and excellent limiting/AM rejection.

The Nelson-Jones Tuner has all of these features and many more, and more importantly the design is fully proven not just with a few prototypes but with many thousands of working tuners spread across the world.

Typ. Specn: 20 dB quieting @ 75uV. Image rejection —70dB. I.F. Rejection —35 dB.

Basic tuner module prices start as low as £12.31, with complete kits starting at £26.95 (mono) + P.P. 65p, and of course all components are available separately.


Our low cost alignment service is available to customers without access to a signal generator. Please send large SAE for our latest price lists which details all of the many options and special low prices for complete kits. All our other products remain available.

PORTUS and HAYWOOD PHASE LOCKED DECODER (W.W. Sept. '70). Still the lowest distortion P.L. decoder available. THD typically 0.05% (at Nelson-Jones Tuner O/P level). Supplied complete with Red LED.

Price £7.92 when bought with a complete N-J tuner kit or £8.28 if bought separately (P.P. 21p). PLEASE NOTE: Existing tuners are readily convertible and kits/parts are available for this purpose.

TEXAN AMPLIFIER. We have designed the tuner case and metalwork to match the Texan amplifier (see photograph). Complete designer approved Texan kits are available at £30.78 plus P.P. 65p including Teak Sleeve.

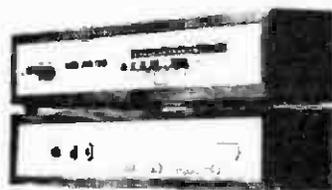PHASE LOCKED Stereo decoder with Stereo mute, see below  
LED fine tuning indicators.  
PUSH BUTTON tuning (with AFC disable) over the FM band (88-104)  
IC STABILISED and SIC protected power supply.  
CABINET double veneered against warp.



## NEW LOW COST STEREO TUNER Available as basic or complete kits

Basic stereo tuner £15 post free.  
Basic mono tuner £12 post free.  
8 position push button units with  
Integral pots £2.92.



No alignment required. Mullard LP1188 front end module used with Ceramic IF and IC amplifier.  
Push button tuning (8 position) with Interstation Mute, restricted range AFC, single LED  
tuning indicator, phase locked IC decoder, and complete metalwork and veneered cabinet.  
Complete with IC regulated PSU and full assembly instructions. (Mechanically identical to  
N-J Tuner.)

PRICE Complete stereo kit £28.42

Complete mono kit £24.19

P. & P. 65p

TYP. SPECIFICATION  
2kV for 30dB S/N  
Image rejection 40dB  
IF rejection 65dB

VAT at 8% is included in all prices

INTEGREX LIMITED, P.O. Box 45, Derby, DE1 1TW Phone Swadlincote (028387) 5432 Telex 377106



# The largest selection

## EX COMPUTER BOARDS

Packed with transistors, diodes, capacitors and trimmers—COMMON KWT VALUE £1.50. 3 for ONLY 55p + p & p 30p

**SPECIAL** One at above PLUS Power Transistor ONLY 55p each + p & p 15p

**PAKOLINE BOARDS** 7 1/2 x 9" APPROX. 4 for 80p + p & p 20p

## FIBRE-GLASS PRINTED CIRCUIT BOARDS

164 x 4" APPROX. 2 for 55p

## DECON-DALO 33PC Marker

Each radiant printed circuit marker pen 89p each

## VEROBOARDS

Packs containing approx. 50m. ins. various sizes. all 1 multi 65p

## REPANCO CHOKES & COILS

RF Chokes  
CR1. 2.5mH 89p CR2. 4.0mH 89p  
CR4. 7.5mH 81p CR4. 10mH 33p  
C16. 1.5mH 28p

## COILS

IRX1 Crystal set 81p DRB2 Dual table 45p

## COIL FORMERS & CORES

NORMAN 1" Cores & Formers 3p  
1" Core & Formers 10p

## SWITCHES

DF/DT Toggle 36p SP/ST Toggle 30p

## FUSES

1 1/2" and 20mm, 100mA, 200mA, 250mA, 500mA, 1A, 1.5A, 2A  
QUICK-BLOW 6p ea.

## EARPHONES

Crystal 2.5mm plug 42p  
Crystal 3.5mm Plug 42p  
8 ohms 2.5mm plug 22p  
8 ohms 3.5mm plug 22p

## DYNAMIC MICROPHONES

R123. 200 ohms plus on/off switch and 2.5mm and 3.5mm plugs £1.50

## 3-WAY STEREO HEADPHONE JUNCTION BOX

H1012 H187

## 2-WAY CROSSOVER NETWORK

K4067 50 ohms Imp. Insertion loss 3dB £1.91

## CAR STEREO SPEAKERS

(Angled) £3.85 per pair.

## BI-PAK

CATALOGUE AND LISTS

Send S.A.E. and 10p.

## INSTRUMENT CASES



(Black Vinyl covered)

No.	Length	Width	Height	Price
BV1	8"	5 1/2"	2"	£1.10
BV2	11"	6"	3"	£1.45

## ALUMINIUM BOXES

BA1	5 1/2"	2 1/2"	1 1/2"	42p
BA2	4"	4"	1 1/2"	42p
BA3	4"	3 1/2"	1 1/2"	42p
BA4	5 1/2"	4"	1 1/2"	50p
BA5	4 1/2"	4 1/2"	1 1/2"	34p
BA6	3"	3"	1"	70p
BA7	7"	5"	2 1/2"	90p
BA8	8"	6"	3"	90p
BA9	8"	4"	2"	52p

1" & 2" 10p on each box

## VISIT OUR COMPONENT SHOP

18 BALDOCK ST., WARE, Herts. (A10)

Open Mon.-Sat. 9.30-5.30 p.m. Tel. 61563

## BIB HI-FI ACCESSORIES

### De Luxe Groov-Kleen

Model 42 £1.95

Chrome Finish

Model 60 £1.50



Ref. B Stylus 3 Turntable Cleaning Kit 34p

Ref. 36A. Record/Stylus Cleaning Kit 33p

Ref. 48. Record Care Kit 28 42

Ref. 31. Comette Head Cleaner 68p

Ref. 32. Tape Editing Kit £1.95

Model 9. Wire Stripper/Cutter 82p

Ref. 48. Spirit Level 62p

Ref. P. Hi-Fi Cleaner 31p

Ref. 32A. Stylus Balance £1.37

Ref. J. Tape Head Cleaning Kit 62p

Ref. 38. Hi-Fi Stereo Binz & Tips 42p

Ref. 45. Auto changer groove cleaner £1.00

## ANTEX SOLDERING IRONS

X25. 25 watt £2.05

CON 210. 15 watt £2.48

Model G. 15 watt £2.38

SK2. Soldering Kit £3.25

STANDS: ST3. Suitable for all models £1

SOLDER: 196W/G Multigrain 7oz £1.81

228W/G 7oz £1.81. 189W/G 1/2oz 51p

228W/G Tube 33p

## PLUGS AND SOCKETS

### PLUGS

PS 1 D.I.N. 2 Pin (Speaker) 0-11

PS 2 D.I.N. 3 Pin 0-12

PS 3 D.I.N. 4 Pin 0-13

PS 4 D.I.N. 5 Pin 180° 0-14

PS 5 D.I.N. 5 Pin 240° 0-15

PS 6 D.I.N. 6 Pin 0-17

PS 7 S.I.N. 7 Pin 0-18

PS 8 Jack 2.5mm Screened 0-19

PS 9 Jack 3.5mm Plastic 0-20

PS 10 Jack 3.5mm Screened 0-21

PS 11 Jack 1" Plastic 0-22

PS 12 Jack 1" Screened 0-23

PS 13 Jack Stereo Screened 0-24

PS 14 Phono 0-25

PS 16 Car Aerial 0-26

PS 18 Co-Axial 0-27

## ANTEX BITS and ELEMENTS

### Bits No.

103 For model CS240 3/32" 42p

104 For model CON240 3/16" 42p

1100 For model CON240 3/32" 42p

1101 For model CON240 3/8" 42p

1102 For model CON240 1" 42p

1020 For model G240 3/32" 42p

1021 For model G240 1/8" 42p

1022 For model G240 3/16" 42p

50 For model X25 3/32" 48p

51 For model X25 1/8" 48p

52 For model X25 3/16" 48p

## ELEMENTS

EON 240 £1.32 EON 240 £1.32

EG 240 £1.87 EG 240 £1.16

## ANTEX HEAT SINKS 10p

V.A.T. included in all prices. Please add 10p P. & P. (U.K. only). Overseas orders—Please add extra for postage.

## NEW COMPONENT PAK BARGAINS

### Pack

No. Qty. Description Price

C1 200 Resistors mixed values approx. count by weight 0.55

C2 150 Capacitors mixed values approx. count by weight 0.55

C3 50 Precision Resistors 1%, 2% mixed values 0.55

C4 75 1/2 W Resistors mixed Preferred values 0.55

C5 5 Pieces assorted Ferrite Rods 0.55

C6 2 Tuning Gans. M.V./L.V. VHF 0.55

C7 1 Pack Wire 50 metres assorted colours 0.55

C 8 10 Reed Switches 0.55

C 8 3 Micro Switches 0.55

C10 15 Assorted Pots & Pre-sets 0.55

C11 5 Jack Sockets 3 x 3.5mm 2 X Standard Switch Type 0.55

C12 30 Paper Condensers Preferred values 0.55

C13 20 Electrolytic Trans. types 0.55

C14 1 Pack assorted Hardware—Nuts/Bolts, Washers etc. 0.55

C15 5 Mains Slide Switches 0.55

C16 20 Assorted Tag Strips & Panels 0.55

C17 10 Assorted Control Knobs 0.55

C18 4 Rotary Wave Change Switches 0.55

C19 2 Relays & 24V Operating 0.55

C20 1 Pack sheets of Copper Laminates 20 sq. ins 0.55

## SOCKETS

PS 35 D.I.N. 2 Pin (Speaker) 0-28

PS 36 D.I.N. 3 Pin 0-29

PS 37 D.I.N. 5 Pin 180° 0-30

PS 38 D.I.N. 5 Pin 240° 0-31

PS 39 Jack 2.5mm Switched 0-32

PS 40 Jack 3.5mm Switched 0-33

PS 41 Jack 1" Switched 0-34

PS 42 Jack Stereo Switched 0-35

PS 43 Phono Single 0-36

PS 44 Phono Double 0-37

PS 45 Co-Axial Surface 0-38

PS 47 Co-Axial Flush 0-39

## LEADS

LS1 Speaker lead 2 Pin D.I.N. plug in Open ends APPROX 3 metres long (coded) 0.20

## CABLES

CP 1 Single Layered Screen 0-17

CP 2 Twin Common Screen 0-18

CP 3 Stereo Screened 0-19

CP 4 Four Core Common Screen 0.23

CP 5 Four Core Individually Screened 0-20

CP 6 Microphone Fully Braided Cable 0-10

CP 7 Three Core Mains Cable 0-09

CP 8 Twin Oval Mains Cable 0-07

CP 9 Speaker Cable 0-06

CP 10 Low Loss Co-Axial 0-16

## CARBON POTENTIOMETERS

Log and Lin

47K, 10K, 22K, 47K, 100K, 200K, 470K, 1M, 2M

VC1 Single Res Switch 0-15

VC2 Single D.P. Switch 0-28

VC3 Tandem Res Switch 0-48

VC4 1K Lin Res Switch 0-15

VC5 100K Log anti-Log 0-48

## HORIZONTAL CARBON PRESETS

0-1 watt 0-08 each  
10K, 22K, 47K, 10K, 22K, 47K, 100K, 220K, 470K, 1M, 2M, 47M

## IT'S NEW IT'S POWERFUL AND— IT LOOKS GOOD!

(15 + 15w R.M.S.)

## THE LEGIONAIRE

STEREO AMPLIFIER

ORDER NOW— ONLY £39.95 p & p 50p  
Or write for full details

## WORLD SCOOP JUMBO SEMICONDUCTOR PACK

Transistors—Germ. and Silicon Rectifiers—Diodes—Triacs—Thyristors—IC's and Zeners ALL NEW AND CODED.

APPROX 100 PIECES  
Offering the amateur a fantastic bargain Pack and an enormous saving—identification data sheet in every Pack.  
Only £2 p. & p. 20p

## RECORD STORAGE/ CARRY CASES

7" EP. 18 1/2" x 7" x 8". (50 records) £2.1

12" LP. 12 1/2" x 7 1/2" x 1 1/2" (50 records) £2.9

## CASSETTE CASES

Holds 12. 10" x 3 1/2" x 8". Lock & Handle £1.80

## SPECIAL PURCHASE

2R3055. Silicon Power Transistor Pack  
Famous manufacturers out-of-spec device free from open and short defects—every one able 115v. T09. Metal Case.  
OUR SPECIAL PRICE 8 for £1

## LOW COST CAPACITORS

81UF 400v. 80. each  
500UF 50v. Elect. 10p each.

## REPANCO TRANSFORMERS

240v. Primary. Secondary voltage available from selected tapplings 4v, 5v, 8v, 10v, 15v, 17v, 19v, 21v, 25v, 51v, 33v, 40v, 60v and 250v-0-25v.

Type	Amps.	Price	P & P
MT500/1	1	£1.98	30p
MT500/2	1	£2.48	30p
MT600/2	2	£3.80	40p

## CARTRIDGES

### AC08

OP91-18C 200mV at 1-2cm/sec £1.80

OP93-1 280mV at 1cm/sec £1.80

OP95-1 100mV at 1cm/sec £2.80

ITC

J-2105 Crystal/Hi Output £1.00

J-2106J Compatible £1.20

J-2008 Stereo/Hi Output £1.70

J-2103 Ceramic/Hi Output £1.90

J-2203 Magnetic Hi-V/Bcm/sec. including stylus £4.80

J-2005 Replacement stylus for above £2.80

AT-65 Anti-static magnets carriage 4mV/cm/sec £3.80

## CARBON FILM RESISTORS

The E12 Range of Carbon Film Resistors 1/8th watt available in PAKS of 50 pieces assorted into the following groups—

R1 50 Mixed 100 ohms-820 ohms 50p

R2 50 Mixed 1K ohms-8.2K ohms 50p

R3 50 Mixed 10K ohms-82K ohms 50p

R4 30 Mixed 100K ohms-1 Meg ohms 50p

THESE ARE UNBEATABLE PRICES—JUST 1p EACH INCL. V.A.T.

## BI.PAK SUPERIOR QUALITY LOW - NOISE CASSETTES

C90, 36P, C90, 48P, C120, 60P

# -the lowest prices!

## BI-PAK QUALITY COMES TO AUDIO!

### AL10/AL20/AL30 AUDIO AMPLIFIER MODULES



The AL10, AL20 and AL30 units are similar in their appearance and in their general specification. However, careful selection of the plastic power devices has resulted in a range of output powers from 3 to 10 watts R.M.S. The versatility of their design makes them ideal for use in record players, tape recorders, stereo amplifiers and cassettes and cartridge tape players in the car and at home.

Parameter	Conditions	Performance
HARMONIC DISTORTION	Po - 3 WATTS f - 1KHz	0.25%
LOAD IMPEDANCE	—	8 - 16 Ω
INPUT IMPEDANCE	f - 1KHz	100 k Ω
FREQUENCY RESPONSE ± 3dB	Po - 2 WATTS	50 Hz - 20KHz
SENSITIVITY FOR RATED O/P	Vs = 26V, RL = 8 Ω f - 1KHz	75mV. R.M.S.
DIMENSIONS		3" x 2 1/2" x 1"

The above table relates to the AL10, AL20 and AL30 modules. The following table outlines the differences in their working conditions.

Parameter	AL10	AL20	AL30
Maximum Supply Voltage	25	30	30
Power output for 2% T.H.D. (RL = 8 Ω f = 1 KHz)	3 watts R.M.S. MIN.	5 watts R.M.S. MIN.	10 watts R.M.S. MIN.

### AUDIO AMPLIFIER MODULES

L 10 3 watts R.M.S. £2.10  
L 20 5 watts R.M.S. £2.60  
L 30 10 watts R.M.S. £3.01

### POWER SUPPLIES

PS 12. (Use with AL10, AL20, AL30) 68p  
PS 30. (Use with AL30) 23.25  
FRONT PANELS RP 12 with Knobs £1.10

### PRE-AMPLIFIERS

PA 12. (Use with AL10 & AL20) £4.35  
PA 100. (Use with AL30 & AL60) £13.15

### TRANSFORMERS

T481 (Use with AL10) £1.38 P & P 13p  
T635 (Use with AL20, AL30) £1.88 P & P 11p  
BMT80 (Use with AL30) £2.16 P & P 22p

### PA 12. PRE-AMPLIFIER SPECIFICATION

The PA 12 Pre-amplifier has been designed to match into most budget stereo systems. It is compatible with the AL 10, AL 20 and AL 30 audio power amplifiers and it can be supplied from their associated power supplies. There are two stereo inputs, one has been designed for use with Cerafonic cartridges while the auxiliary input will suit most magnetic cartridges. Full details are given in the specification table. The four controls are, from left to right: Volume and on/off switch, balance, bass and treble. Size 102mm x 84mm x 35mm.

Frequency response - 20Hz - 20KHz (-3dB)  
Bass control - ± 12dB at 60Hz  
Treble control - ± 14dB at 14KHz  
\*Input 1. Impedance 1 Meg. Ohm  
Sensitivity 300mV  
\*Input 2. Impedance 80 K Ohms  
Sensitivity 4mV

Look for our

SEMICONDUCTOR ADVERTISEMENTS in Practical Wireless Wireless World Radio Constructor

ALL PRICES INCLUDE V.A.T.

## The STEREO 20

The 'Stereo 20' amplifier is mounted, ready wired and tested in a one-piece chassis measuring 20 cm x 14 cm x 6.6 cm. This compact unit comes complete with on/off switch volume control, balance, bass and treble controls. Transformer, Power supply and Power amps. Attractively printed front panel and matching control knobs. The 'Stereo 20' has been designed to fit into most suitable plinths without interfering with the mechanism or dialing. It is a separate cabinet output power 30w peak. Input 1 (Car.) 100mV into 1M. Freq. res 20Hz-25KHz. Input 2 (Aux.) 4mV into 30K. Harmonic Distortion: Bass control ± 12dB at 60Hz; typically 0.25% at 1 watt. Treble out. ± 14dB at 14KHz.



£14.45

### TC20 TEAK VENEERED CABINET

For Stereo 20 (front board undrilled) size 10 1/2" x 8 1/2" x 3", £9.95, plus 30p postage

### SHR60 STEREO HEADPHONES


1-16 ohms impedance. Frequency response 20 to 20,000Hz; Stereo/mono switch and volume controls £4.95

## NOW WE GIVE YOU 50w PEAK (25w R.M.S.) PLUS THERMAL PROTECTION! The NEW AL60 Hi-Fi Audio Amplifier FOR ONLY £3.95

- Max Heat Sink temp. 90°C.
- Frequency Response 20Hz to 100KHz
- Distortion better than 0.1% at 0.1KHz
- Supply voltage 15-50 volts
- Thermal Feedback
- Latest Design Improvements
- Load - 3, 4, 8 or 16 ohms
- Signal to noise ratio 80dB
- Overall size 63mm x 105mm x 13mm

Especially designed to a strict specification. Only the finest components have been used and the latest solid state circuitry incorporated in this powerful little amplifier which should satisfy the most critical A.F. enthusiast.

### STABILISED POWER MODULE SPM80

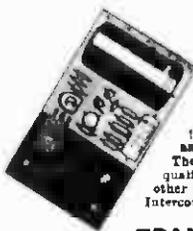

SPM80 is especially designed to power 7 of the AL60 Amplifiers, up to 15 watt (r.m.s.) per channel simultaneously. This module embodies the latest components and circuit techniques incorporating complete short circuit protection. With the addition of the Main Transformer BMT80, the unit will provide outputs of up to 1.6 amps at 25 volts. Size: 50mm x 100mm x 30mm. These units enable you to build Audio Systems of the highest quality at a hitherto unobtainable price. Also ideal for many other applications including: Disco Systems, Public Address Intercom Units, etc. Handbook available 10p PRICE £3.25

TRANSFORMER BMT80 £2.15 p. & p. 28p

### STEREO PRE-AMPLIFIER TYPE PA100

Built to a specification and NOT a price, and yet still the greatest value on the market, the PA100 stereo pre-amplifier has been conceived from the latest circuit techniques. Designed for use with the AL60 power amplifier system, this quality made unit incorporates no less than eight silicon planar transistors, two of these are specially selected low noise NPN devices for use in the input stages. Three switched stereo inputs, and rumble and scratch filters are features of the PA100, which also has a STEREO/MONO switch, volume, balance and continuously variable bass and treble controls.



### SPECIFICATION

Frequency Response 20Hz - 20KHz ± 1dB  
Harmonic Distortion better than 0.1%  
Inputs: 1. Tape Head 2.25 mV into 50K Ω  
3. Radio, Tuner 75 mV into 50K Ω  
4. Magnetic P.U. 3 mV into 60K Ω  
All input voltages are for an output of 200mV. Tone and P.U. inputs equalised to RIAA curve within ± 1dB from 20Hz to 20KHz.  
Bass Control ± 12dB at 60Hz  
Treble Control ± 14dB at 20 KHz  
Filters: Rumble (Low Pass) 100Hz  
Scratch (High Pass) 8KHz  
Signal/Noise Ratio better than -65dB  
Input overload ± 26dB  
Supply + 25 volts at 20mA  
Dimensions 292mm x 52mm x 35mm

ONLY £13.15

SPECIAL COMPLETE KIT COMPRISING 2 AL50's, 1 SPM80, 1 BMT80 & 1 PA100 ONLY £25.30 FREE p. & p.

### MK 60 AUDIO KIT

Comprising: 1 x AL60, 1 x SPM80, 1 x BMT80, 1 x PA 100, 1 front panel, 1 kit of parts to include on-off switch, neon indicator, stereo head/phone sockets plus instruction booklet. Complete Price: £28.75 plus 30p postage

### TEAK 60 AUDIO KIT

Comprising: Teak veneered cabinet size 10 1/2" x 11 1/2" x 3 1/2", other parts include aluminium chassis, heat sink and front panel bracket, plus back panel and appropriate sockets etc. Kit price: £9.95 plus 30p postage

Giro No. 388-7006

Please send all orders direct to warehouse and despatch department

# BI-PAK

P.O. BOX 6, WARE, HERTS

Postage and packing add 11p. Overseas add extra for airmail.

Minimum order 55p. Cash with order please.

Guaranteed Satisfaction or Money Back

# NEW MULLARD & MAZDA VALVES

All individually boxed and guaranteed. Full trade discounts to bona fide companies. Price and availability lists on application.

## EXPRESS POSTAGE

5p for 1 Valve  
Each additional Valve add 2p

DM70	0-61	ECL33	0-66	PL2501	1-05	PL12	0-48	30CL1/PCF60	
DY567	0-80	ECL36	0-68	QZ34	0-77	PL23	1-09	PL23	0-54
DE400	0-41	EP80	0-42	PC88	0-95	PL54	0-87	30CL15	
EABCA0	1-08	EP85	0-98	PC89	0-93	PL50A	0-89	PCF800	1-01
EB91	0-64	EP86	1-15	PC87	0-42	PL50B	1-18	30CL17	1-01
EB01	0-75	EP89	1-14	PC89	0-56	PL509	1-56	30CL18	
EP80	0-50	EP91	0-80	PC109	0-80	PL802	1-89	PCF805	1-00
EP82	0-50	EP92	1-37	PCF80	0-54	PL802	1-89	PCF815	1-00
EP89	0-73	EP93	1-16	PCF82	1-22	PL809	1-56	30CL19	
EC86	0-78	EP94	0-60	PCF86	0-64	PL809	1-56	30CL19	0-84
EC88	0-76	EP184	0-60	PCF700	1-00	PL809	1-56	30CL19	0-84
EC86	0-60	EP90	0-98	PCF701	1-01	U36	0-88	30CL1/PC88A	
EC87	0-40	EL84	0-92	PCF801	0-40	U191	0-85		0-54
EC81	0-47	EL30	1-01	PCF802	0-70	U193	0-54	30LL15	
EC82	0-44	EL91	0-85	PCF806	0-84	U193	0-54	PCCA05	1-08
EC83	0-47	EL84	0-47	PCF809	1-14	U3601	0-71	30LL17	0-88
EC84	0-54	EL84	0-47	PCF809	1-14	U1909	0-55	30P4MR	1-27
EC85	0-47	EL84	0-47	PCF83	0-64	U3605	0-55	30P19	
EC86	0-84	EL91	0-60	PCF84	0-60	U3605	0-55	30P19	1-01
EC8189	0-85	EL55	0-70	PCF85	0-64	U3605	0-55	30P19	1-01
EC86	0-57	EL80	2-06	PCF88	0-64	U3605	0-55	30P19	1-01
EC82	0-58	EL84	1-10	PCF805/85		U3605	0-55	30P19	1-01
EC86	0-84	EL87	1-10	PCF805/85		U3605	0-55	30P19	1-01
EC81	1-15	EY51	0-70	PD500	1-85	U3605	0-55	30P19	1-01
EC82	0-84	EY86/7	0-70	PL500	0-85	U3605	0-55	30P19	1-01
EC84	1-02	EY88	0-72	PL36	0-89	U3605	0-55	30P19	1-01
ECL80	0-87	EZ20	0-64	PL81	0-77	U3605	0-55	30P19	1-01
ECL82	0-80	EZ81	0-38	PL91A	0-89	U3605	0-55	30P19	1-01

# NEW VALVES

Individually boxed and guaranteed but of European or other origin at greatly reduced prices. Quotations for any valve not listed. Send SAE for lists.

A21	0-75	EP39	1-25	N78	3-80	6F20	0-75
A21	0-60	EP80	0-35	0A2	0-45	6J5M	0-65
CB131	1-40	EP80	0-45	0B2	0-45	6J6	0-45
CL38	1-60	EP85	0-30	PC86	0-85	6Y70	0-80
CY21	0-60	EP85	0-28	PC88	0-65	6Y70	0-80
DAF91	0-40	EP91	0-40	PC87	0-55	6Y70	0-80
DAF90	0-60	EP82	0-30	PC890	0-55	6Y70	0-80
DC950	1-35	EP56	0-45	PC824	0-45	6Y70	0-80
DF91	0-40	EP98	0-80	PC885	0-82	6Y70	0-80
DF96	0-60	EP182	0-40	PC889	0-45	6Y70	0-80
DE91	0-60	EP184	0-40	PC109	0-58	6Y70	0-80
DK92	1-00	EL32	2-00	PC885	0-40	6Y70	0-80
DK96	0-75	EL33	2-00	PCF82	0-42	6Y70	0-80
DL92	0-50	EL34	0-70	PCF86	0-65	1R5	0-50
DL94	0-48	EL36	0-80	PCF801	0-40	1R5	0-50
DL98	0-85	EL37	2-30	PCF82	0-65	1A17	0-45
DY86	0-42	EL41	0-50	PCF86	0-30	1A4	0-80
DY87	0-48	EL42	1-05	PCF86	0-80	1A4	0-80
DY902	0-47	EL84	0-55	PCF800	0-80	3V3	0-85
EABCA0	0-58	EL96	0-60	PC182	0-45	6A4G	0-45
EAF42	0-70	ELL80	2-00	PC183	0-70	5Y3GT	0-45
EB91	0-25	EM80	0-55	ICL84	0-60	5Y40	0-40
EB93	1-03	EM81	0-60	PC186	0-60	6Z4G	0-85
EB94	0-60	EM84	0-60	PC186	0-50	6A15	1-00
EB91	0-40	EM85	1-00	PC1805/85		6B0L2	0-85
EB90	0-40	EY61	0-45			6A15	1-00
EB93	0-40	EY86	0-45	PD500	1-50	6A06	0-50
EB98	0-32	EZ40	0-60	PEN45	0-88	6A270	1-00
EB131	2-00	EZ41	0-75	PL35	0-83	6A76	0-80
EC83	0-45	EZ30	0-50	PL81	0-55	6A08	0-40
EC82	0-38	EZ81	0-31	PL82	0-50	6BAC	0-38
EC83	0-38	QY301	0-50	PL82	0-50	6B25	0-45
EC84	0-35	GZ30	0-45	PL84	0-50	6B85	0-75
EC85	0-45	GZ39	0-55	PL800	0-85	6B15	0-75
EC88	0-60	GZ34	0-75	PL504	0-85	6BQ7A	0-85
EC83	1-50	GZ37	1-25	PL505	0-90	6B77	1-40
EC84	0-65	HN80	1-50	PL506	1-35	6B77	1-40
EC881	0-35	KT61	2-00	PL802	1-00	6B77	1-40
EC883	0-50	KT66	2-50	PK4	3-50	6B77	1-40
ECL80	0-60	ET81 (FC5)		EX26	3-50	6C4	0-40
ECL82	0-48			PY33	0-88	6C10A2	1-25
ECL83	0-75	KT91	1-75	PT81	2-45	6C16	1-50
ECL84	0-65	KT86	2-50	PY82	0-45	6C74	1-50
ECL860	3-50	KT861	1-50	PY82	0-45	6C74	1-50
EF97A	1-20	WU14	1-00	PY88	0-50	6P25	1-90

# TRANSISTORS-INTEGRATED CIRCUITS

All transistors, I.C.'s offered are new and branded. Manufactured by Mullard, Texas, RCA, Ferranti, Motorola, ITT, Fairchild, Lucas, etc. Quantity discounts on application. Send SAE for full lists.

## EXPRESS POSTAGE

5p for first Transistor  
For each additional add 1p

AA119	0-7	BD152	0-50	OC16	1-00	ZTX501	0-15	2N2904	0-20
AA121	0-10	BF116	0-22	OC20	2-00	ZTX503	0-15	2N2904A	0-25
AZ15	0-10	BF167	0-15	OC23	1-25	ZTX504	0-25	2N2905	0-25
AC107	0-25	BF171	0-28	OC23	1-25	ZTX505	0-15	2N2906	0-25
AC126	0-25	BF179	0-35	OC29	0-70	1N914	0-05	2N3006	0-20
AC127	0-25	BF180	0-35	OC35	0-65	1N4001	0-04	2N3026	0-10
AC128	0-20	BF181	0-35	OC36	0-65	1N4002	0-07	2N3003	0-20
AC176	0-25	BF194	0-12	OC38	0-65	1N4003	0-08	2N3065	0-20
AC187	0-25	BF196	0-12	OC42	0-60	1N4004	0-07	2N3023	0-20
AC188	0-20	BF197	0-15	OC44	0-60	1N4005	0-12	2N3014	0-25
AC192	0-25	BF200	0-32	OC45	0-60	1N4006	0-12	2N3015	0-25
AC193	0-25	BF201	0-32	OC46	0-60	1N4007	0-12	2N3016	0-25
AD140	0-40	BF298	0-25	OC48	0-60	1N4008	0-12	2N3017	0-25
AD149	0-40	BF299	0-25	OC49	0-60	1N4009	0-12	2N3018	0-25
AD181	0-35	BF285	0-25	OC50	0-60	1N4010	0-12	2N3019	0-25
AD182	0-35	BF286	0-25	OC51	0-60	1N4011	0-12	2N3020	0-25
AF115	0-25	BFY01	0-20	OC52	0-60	1N4012	0-12	2N3021	0-25
AF116	0-25	BFY02	0-20	OC53	0-60	1N4013	0-12	2N3022	0-25
AF117	0-20	BFY10	0-20	OC54	0-60	1N4014	0-12	2N3023	0-25
AF196	0-40	BY100	0-15	OC55	0-60	1N4015	0-12	2N3024	0-25
AF239	0-44	BY126	0-14	OC56	0-60	1N4016	0-12	2N3025	0-25
AF237	0-40	BY137	0-15	OC57	0-60	1N4017	0-12	2N3026	0-25
AF238	0-40	BY138	0-15	OC58	0-60	1N4018	0-12	2N3027	0-25
BA103	0-25	BZ361	0-20	OCB10	0-20	OCB10	0-20	2N3028	0-25
BA115	0-20	BZV62	0-20	OCB12	0-20	OCB12	0-20	2N3029	0-25
BC107	0-12			OCB15	0-20	OCB15	0-20	2N3030	0-25
BC108	0-12	CR81-05	0-30	OC149	0-85	2N3031	0-25	2N3031	0-25
BC109	0-12	CR81-06	0-30	OC170	0-25	2N3032	0-25	2N3032	0-25
BC110	0-12	CR81-07	0-30	OC171	0-25	2N3033	0-25	2N3033	0-25
BC117	0-21	CR83-04	0-35	OC200	0-55	2N3034	0-25	2N3034	0-25
BC143	0-20	ME140	0-65	OC301	0-80	2N3035	0-25	2N3035	0-25
BC147	0-12	ME370	0-65	OC202	0-90	2N1151	0-25	2N3036	0-25
BC148	0-10	ME370	0-65	OC203	0-90	2N1152	0-25	2N3037	0-25
BC198C	0-14	ME2505	1-10	OCUP1	1-00	2N1302	0-18	2N3038	0-25
BC199	0-12	ME3065	0-75	OP12	0-35	2N1303	0-18	2N3039	0-25
BC192L	0-12	ME3065	0-75	OP12	0-35	2N1304	0-18	2N3040	0-25
BC184L	0-13	MEF103	0-45	TI005	0-20	2N1305	0-18	2N3041	0-25
BCY32	1-20	MEF104	0-35	TIC44	0-82	2N1306	0-25	2N3042	0-25
BCY33	0-38	MEP105	0-45	TIC266D	1-50	2N1307	0-25	2N3043	0-25
BCY34	0-45	NKT404	0-40	TIL200	0-25	2N1308	0-25	2N3044	0-25
BCY70	0-15	DA5	0-10	ZTX107	0-12	2N1309	0-20	2N3045	0-25
BCY71	0-15	DA5	0-10	ZTX108	0-12	2N1310	0-20	2N3046	0-25
BCY72	0-15	DA5	0-10	ZTX109	0-12	2N1311	0-20	2N3047	0-25
BCZ11	0-65	CA81	0-10	ZTX301	0-14	2N2187	0-15	2N3048	0-25
BD121	1-00	CA81	0-10	ZTX302	0-30	2N1160	1-00	2N3049	0-25
BD124	0-80	CA300	0-10	ZTX304	0-24	2N2388A	1-15	2N3050	0-25
BD131	0-45	CA303	0-10	ZTX300	0-18	2N2646	0-80	2N3051	0-25

**VAT**  
8% to be added to all orders including postage!

## THIS MONTH'S

● OSCILLOSCOPE TUBE TYPE VCR 139A  
Price £8'00 p & p 25p

## SPECIAL OFFER

TERMS OF BUSINESS: C.W.O. A/c's available to approved companies on application. Telephone and telex orders accepted. Export and trade enquiries welcomed. Lists, etc. on application. Open daily to callers 9 a.m.-5 p.m. Mon.-Sat. Closed Sat. 1-3 p.m. Prices correct when going to press.


**VALVE MAIL ORDER CO.**  
16a Wellfield Rd., London, SW16 2BS  
Tel: 01-677 2424 Telex: 946 708.

CUSTOM CABINETS, 331 High Street, Rochester, Kent. Tel: Medway (0634) 404199.


Speaker Cabinets in kit form represent HUGE SAVINGS



2' x 12" Cabinet

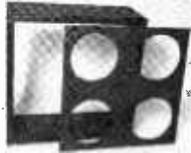

4' x 12" Cabinet

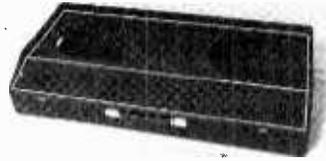

Disco Console (includes lid not shown)  
Takes two slaves

For a long time now a large number of customers have asked us to produce cabinets in kit form, and above we show examples of cabinet styles and these are now available either fully built or in kit form ready for you to produce a professional finish in a very short time!

Kits are available in all specifications and all the kits contain everything you need as follows :-

- 1) 4 sides with handle cutouts, front edges rounded, 1 back with jack socket hole, and 1 baffleboard with speaker cutout
- 2) P.V.C. cut to size for frame and back, plus false front and back timbers, white front piping and speaker cloth
- 3) Recessed handles with fixing screws, jack socket, all fixing screws, corner plates, glue, and full instructions!

PRICE & TYPE LIST

Type	Size	Price manufactured	Kit price
2 x 12" (illustrated above)	36" x 18" x 13" x 3/4	£19.50	£12.50
4 x 12" (illustrated above)	31" x 31" x 13" x 3/4	£24.50	£17.50
4 x 12" P.A. Column	48" x 27" x 13" x 3/4	£30.00	£21.50
1 x 18"	31" x 31" x 13" x 3/4	£24.50	£17.50
1 x 15" with two top horn cutouts	36" x 20" x 13" x 3/4	£21.00	£13.50
Mini Disco (state deck cutout BSR, GARRARD etc.)	33" x 20" x 10" x 1/2	£20.00	£13.00
Maxi Disco (illustrated) (state deck cutout BSR, GARRARD etc.)	42" x 20" x 10" x 1/2	£25.00	£18.50

Please ask for quotation on any other type or size of cabinet you may require.

ALL OUR PRICES INCLUDE VAT AND UK DELIVERY



# The Pictorial Method

## BASIC ELECTRICITY (5 vols) BASIC ELECTRONICS (6 vols) BASIC TELEVISION (3 vols)

You'll find it easy to learn with this outstandingly successful PICTORIAL METHOD. The essential facts are explained in the simplest language, one at a time, and each is illustrated by an accurate cartoon-type drawing. These clear and concise illustrations make study a real pleasure. The books are based on the latest research into simplified learning techniques. This easy-approach-to-learning method has proved beyond doubt that acquiring knowledge can be an enjoyable experience.

The series will be of exceptional value in training mechanics and technicians in Electricity, Radio and Electronics.

WHAT READERS SAY

I am amazed at the ease a layman can understand these books.

G.P. Bexhill

At such a low cost they are a magnificent set of books.

W. I. Ladywell

My sincere congratulations on describing everything so simply.

J. B. Retford

I have received both enlightenment and pleasure from reading your manuals.

V. S. Huddersfield

**YOUR 100% GUARANTEE**

Should you be, in any way dissatisfied with the MANUALS your money will be refunded by return of post.

To The SELRAY BOOK CO., 60 HAYES HILL, HAYES, BROMLEY, KENT. BR2 7HP

Please find enclosed P.O./Cheque value £.....

BASIC ELECTRICITY 5 parts £6.50

BASIC ELECTRONICS 6 parts £7.50

BASIC TELEVISION 3 parts £4.25

Tick Set(s) required. Prices include Postage and Packing.

**YOUR 100% GUARANTEE. If after 10 days examination you decide to return the Manuals your money will be refunded in full.**

NAME .....  
BLOCK LETTERS

FULL POSTAL.....

ADDRESS .....

**POST NOW FOR THIS OFFER!**

# PE SCORPIO Mk2 ignition system kit new from ELECTRO SPARES

\* 6 OR 12 VOLT  
\* + VE AND - VE GROUND

Here's the new, improved version of the original PE Scorpio Electronic Ignition System—with a big plus over all the other kits—the PE Scorpio Kit is designed for both positive and negative ground automotive electrical systems. Not just +ve ground. Nor just -ve ground. But both! So if you change cars, you can be almost certain that you can change over your PE Scorpio Mk. 2 as well. Containing all the components you need, this Electro Spares PE Scorpio Mk. 2 Kit is simply built, using our easy-to-follow instructions. Each component is a branded unit by a reputable manufacturer and carries the manufacturer's guarantee. Ready drilled for fast assembly. Quickly fitted to any car.

When your PE Scorpio Mk. 2 is installed, you instantly benefit from all these PE Scorpio Mk. 2 advantages.

- ★ Easier starting from cold
- ★ Firing even with wet or oiled-up plugs
- ★ Smoother running at high speed
- ★ Fuel saving
- ★ More power from your engine
- ★ Longer spark plug life
- ★ No more contact-breaker burn

Electro Spares prices:

De luxe Kit only £11.50 inc. VAT and p & p.  
Ready Made Unit £14.75 inc. VAT and p & p.  
State 6V or 12V system.

Send SAE now for details and free list.

## FM VARICAP STEREO TUNER

As featured in the May 1973 issue of 'Practical Electronics'. Superb Hi-Fi tuner kit now available from Electro Spares. Including cabinet and all components—pre-set Mullard modules for R.F. and I.F. circuits. Motorola I.C. Phase Lock Loop Decoder for perfect stereo reception. No alignment needed. Guaranteed first time results—or send it back, and we'll return it in perfect order (for a nominal handling charge). Electro Spares price only £28.50 inc. VAT and p & p.

## 'GEMINI' STEREO AMPLIFIER

A superb unit with a guaranteed output of 30 watts RMS per channel into 8 ohms. Full power THD is a mere 0.02%, and frequency response is -3 dB from 20 Hz to 100 kHz into 8 or 15 ohms. Electro Spares have already sold 100s and 100s of these kits. Get yours now! Depending on your choice of certain components, the price can vary from £50 to £60 inc. VAT and p & p.

- ★ All components as specified by original authors, and sold separately if you wish.
- ★ Full constructional data book with specification graphs, fault finding guides, etc. 55p plus 4p postage.
- ★ Price List only. Please send S.A.E. (preferably 9 x 4 minimum) for full details.

# ELECTRO SPARES



The Component Centre of the North  
288 ECCLESALL RD., SHEFFIELD S11 8PE (C)  
Tel: Sheffield (0742) 668888

### PC ETCHING KIT

Contains 1lb Ferric Chloride, 100 sq. ins. copper-clad board, BALO etch-resist pen, abrasive cleaner, etching dish & instructions, all for only £3.30

### RESISTORS & CAPACITORS

500 assorted resistors £1.35, 2500 £4.70, 150 poly. ceramic, mica etc capacitors 80p, 15 different trimmers airspaced and compression, up to 1250pF £1.

### VEROBOARD

100 sq. ins. assorted sizes and pitches (no tiny pieces) £1-10, approx 2 bits.

### 1W TAPE AMPLIFIERS

Polished wooden cabinet 14 x 13 x 9" containing a sensitive (20uV) 4 valve amplifier with tone & volume controls. Gives 3 watts output to the 7 x 4" 512 speaker. Also a non-standard tape deck. Supplied in good working condition with circuit. Standard mains operation. £4.50. Suitable cassette £1-10. Spare head 30p. Tape (ex-computer) 75p. Amplifier cassette only, complete and tested (2x ECC83, EL84, EZ80) and speaker £3.

### VERSATILE POWER UNIT

Contains mains transformer, 2A thermal cut-out and bridge rectifier. Will give 1.7-10.5V output with 2 extra capacitors (supplied) £1.20. Also available as model garage with switch, lamp, jack plug etc. (Used for 'Hot Wheels?') £1.70.

### LEO III COMPUTER

Arriving late-October. All parts available, including 2 3000 reels tape, 3" disks, power units, etc.

All prices shown include 8% VAT and postage (mainland only) SAE list, enquiries.

## GREENWELD ELECTRONICS (PW9)

Mail order dept., wholesale/retail shop 51 SHIRLEY PARK ROAD, SOUTH-AMPTON. Tel 0703 772501. Other retail shops at 21 Deptford Broadway SE8, Tel 01-892 2009 and 38 Lower Addiscombe Road, Croydon. Callers Welcome.

### FERRIC CHLORIDE

Anhydrous technical quality to Mill Spec in 1lb double sealed packs, 1lb 80p, 3lbs £1.55, 10lbs £4.45, 100lbs £35.

### PO AMPLIFIER UNIT

Contained in steel case 5 1/2 x 5 x 3 1/2" are 2xGET115 transistors on heat sinks, 3 pol cores, 2 30V zeners, 4 audio transformers, 1% resistors & caps. With circuit diagram £1.

### 7b BARGAIN PARCELS

Hundreds of new components—Pots, resistors, capacitors, switches, + PC boards with transistors and diodes, and loads of odds and ends. Amazing value at only £2.30.

### COMPUTER PANELS

3lbs ass'd £1.40, 7lbs £2.65, 56lbs £15. Pack containing 500 components with at least 50 transistors 95p, 12 high quality panels with power transistors, trim pots, IC's etc £2.50. Thousands of boards at shops for callers from 5p.

### SLOT METER

Ex-Pay TV, takes 100 pieces, has 3 digit mechanical counter, coin counter, Sengamo-Weslon impulse movement, nylon gearing, switch, etc. Only £1.20. Impulse movement only, 40p.

### MISCELLANEOUS

Transformer, Mains Pri 16.0-16V with 5V tap sec 15A £2. Post office 4 digit counters 60p, balanced armature earpieces, use 85 mic or 20k 200 Impedance 30p, 2N3055 38p, Multimeter: good range in stock from £3.50.

# Tele-Tennis

As described in Practical Wireless

Play the game that's sweeping the nation. You've seen it in pubs, clubs and arcades—now you can play it in the comfort of your own home.

Plugs into the aerial of your V.H.F. 625 Black & White or Colour television. No internal connections to your T.V. set. Does not interfere with other T.V. programmes. Built from 6 neat sub-sections, purchase a complete kit or sub-section at a time.

All parts available separately including P. C. boards, case and ready punched and slotted fascia panel.

S.A.E. for full details.

## DABAR ELECTRONIC PRODUCTS




98 LICHFIELD STREET  
WALSALL, Staffs WS1 1UZ


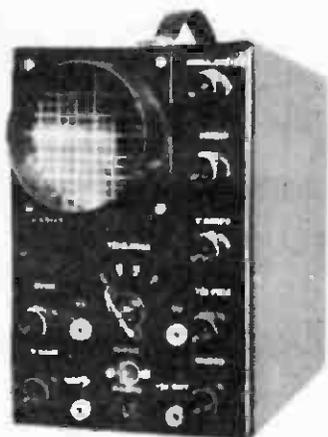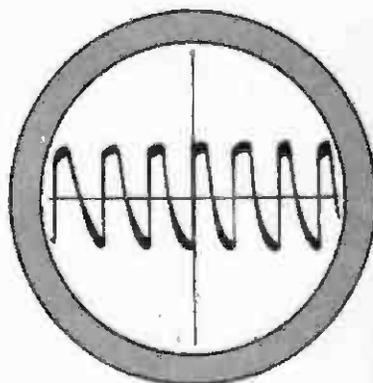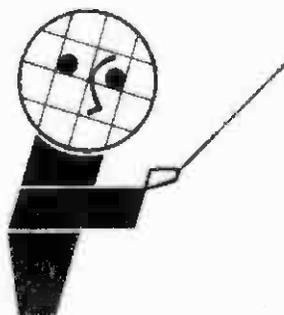
# look! electronics really mastered

...practical  
...visual  
...exciting!

no previous knowledge  
no unnecessary theory  
no "maths"



RAPY


## BUILD, SEE AND LEARN

step by step, we take you through all the fundamentals of electronics and show how easily the subject can be mastered. Write for the free brochure now which explains our system.

### 1/ BUILD AN OSCILLOSCOPE

You learn how to build an oscilloscope which remains your property. With it, you will become familiar with all the components used in electronics.
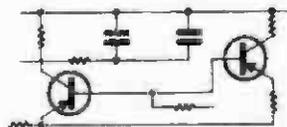
### 2/ READ, DRAW AND UNDERSTAND CIRCUIT DIAGRAMS



as used currently in the various fields of electronics.

### 3/ CARRY OUT OVER 40 EXPERIMENTS ON BASIC ELECTRONIC CIRCUITS & SEE HOW THEY WORK, including:

valve experiments, transistor experiments amplifiers, oscillators, signal tracer, photo electric circuit, computer circuit, basic radio receiver, electronic switch, simple transmitter, a.c. experiments, d.c. experiments, simple counter, time delay circuit, servicing procedures.

This new style course will enable anyone to really understand electronics by a modern, practical and visual method—no maths, and a minimum of theory—no previous knowledge required. It will also enable anyone to understand how to test, service and maintain all types of electronic equipment, radio and TV receivers, etc.

**FREE** POST NOW for BROCHURE

or write if you prefer not to cut page

To: **BRITISH NATIONAL RADIO & ELECTRONICS SCHOOL,**  
P.O. Box 156, JERSEY. Please send your free brochure, without obligation, to:  
*we do not employ representatives*

NAME

BLOCK CAPS

ADDRESS

PLEASE WLI24

**special free gift also to all our students**

## "SLO-SYN" 3-LEAD SYNCHRONOUS STEPPING MOTOR



Type SS15. These fine motors are easily reversed, starting and stopping in less than 5° without electrical or mechanical braking. Simple relay circuit can be applied to give DC., to winding for a maximum holding torque of 300oz/in with 35v at 0.35 amps through winding. For A.C. (asynchronous) operation at 120v., 50Hz. Speed 60 rpm at 60Hz., 72 rpm. STEPPING. Holding torque at 50 steps per second—100 oz/in. Can be wired to give 100 or 200 steps per revolution with accuracy of 0.1° per step non-cumulative. Torque characteristics can be modified by simple R.C. circuits. Dimensions: dia. 4", body length 4 1/2", spindle length 2 1/2" x 1/2" dia. Weight 6 1/2 lbs. BRAND NEW in maker's packing. Offered at less than 1/2 maker's price. **OUR PRICE ONLY £15**

### NORPLEX

Fibre-glass copper-clad laminate. Finest quality epoxy resin base. Heat resistant, ideal for P.C. Sizes: 12" x 12", 24" x 12", 24" x 24", FULL SHEET 43" x 37" (11 sq ft.) Single-sided Copper with thickness of 1/32", 3/64", 3/32". Also double-sided 1/32", 1/16", 3/32". £1 per sq ft. Cut sizes (1-10 sq. ft.) 25p. P & P Full Sheet £8 each. Carr. £1 for 1st sheet plus 25p each additional sheet.

### SMITHS RINGER-TIMER



Reliable 15 minute times, spring wound (concurrent with time setting) 15 x 1min divisions, approximately 1/2" between divisions. Panel mounting with chrome bezel 3 1/2" dia. £1.40. 15p. P. & P.

### KNOWLE (U.S.A.) MINIATURE MICROPHONE CAPSULES

Impedance approx. 200Ω, output 60 or 80 DB at 1 Kc. As used in desk adding devices, etc. Size (50 DB) 7/32" x 5/32" x 1/4" (80 DB) 3/4" x 5/32" x 1/4". Ex-empirical, all tested. £1.20 each. P. & P. FREE.

## Ultra PRECISION CENTRIFUGAL BLOWER



by Air Control Ltd.  
30 segments individually balanced in heavy cast alloy case. 2,300 r.p.m. 240 A.C. Very powerful and silent running. 5 1/2" dia 3" inlet dia. Outlet flange 3" x 2 1/2". LIMITED NUMBER ONLY £8.95. P & P 40p.


### MAINS SOLENOID

This little unit gives vertical lift of approximately 1" through hinged "t e b o w". Bracket incorporates 2 fixing screws. Length of arm. 2 1/2". 240V A.C. Pull at coil is approximately 1lb. £1. FREE P. & P. Special quotes for quantities.


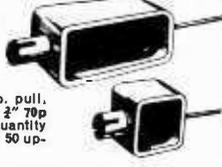
### SOLENOIDS by WESTOOL

240AC type MM6. 3lb. pull, 2 1/2" x 1 1/2". Travel 1". 90p. each. P. & P. 10p.  
240AC type MM4. 2lb. pull. 1 1/2" x 1 1/2" x 1". Travel 2" 70p each. P. & P. 10p. Quantity discounts: 10-50 10%, 50 upwards 25%.



### OPEN FRAME shaded pole GEARED MOTORS

(Dural gear case) 240 AC, 28rpm. NEW HIGH TORQUE, approx. overall size: 3 1/2" x 3 1/2" x 2 1/2" + spindle 3/4" dia. as illustrated. £2.70. P. & P. 30p. Similar to above, 19rpm. £2.70. P. & P. 30p. 110rpm with pressed steel gear case (similar to above but slightly smaller). £2.70. P. & P. 30p.



## SILVANIA MAGNETIC SWITCH

Now complete with reference magnet!

A magnetically activated switch, vacuum sealed in a glass envelope. Silver contacts, normally closed. Rated 3amp at 120v. 1amp at 240v. Size: (approx.) 1 1/2" long x 1/2" dia. Ideal for burglar alarms, security systems etc., and wherever non-mechanical switching is required. 10 for £2.10. P. & P. 15p. 50 for £8.80; 100 for £15.50. FREE P. & P. over 10.



## AMPEX 7.5v. D.C. MOTOR



An ultra precision tape motor designed for use in the AG20 portable recorder. Torque 450GM/CM. Stall load at 500ma. Draws 60ma on run. 800rpm ± speed adjustment. Internal AF/RF suppression 1" dia. x 1" spindle, motor 3" dia. x 1 1/2". Original cost £16.50. **OUR PRICE £3.30. P. & P. 25p.** Quantity available. Mu-metal enclosure available 75p each. FREE P. & P.

**ALL PRICES INCLUDE V.A.T.**

Whilst we welcome official orders from established companies and Educational Departments, it is no longer practical to invoice goods under £5. Therefore please remit cash with orders below this amount.

# ELECTRO-TECH COMPONENTS LTD.

315/317, EDGWARE ROAD, LONDON, W2.  
Tel: '01-723 5667 01-402 5580

### A V.C.O. by FHACHI 1Hz to 100kHz for £5.75 P. & P. 15p

Size 2" L; 1 1/2" W; 1 1/2" H.  
Input 12 to 24V DC (not centre tapped)  
18V input giving 10 volt constant amplitude output  
Requires only a 1 meg ohm pot to tune entire range—or can be swept with a saw tooth input.  
Enormous possibilities—music; synthesizers; filters; communications; frequency modulation etc.  
Detailed application sheet with all purchases

### FHACHI RAMP MODULE FX21

24 volt DC input for 18 volt sawtooth output. Requires only external capacitor and 100K ohm potentiometer to control frequency range up to 100kHz (eg 50 mfd electrolytic gives sweep of approx 1 cm per second). In or out sync capability.  
**Price £5.75 P. & P. 15p**

### FHACHI FILTER MODULE FX31

Designed for use with VCO FX11 and RAMP FX21. This completes the 3 building blocks required for a basic low-frequency Spectrum Analyser that covers 100Hz to 50kHz. The additional components required are discrete resistors and capacitors, etc. (No inductances or specialized components are needed). **Price £13.00 P. & P. 30p.** Fibre glass P.C. board to mount FX11, 21 and 31 ready drilled. Connection details and list of additional component required supplied with each order. **£2.50 P. & P. 30p.**

### LOW FREQUENCY WOBBLATOR

Primary Intended for the alignment of AM Radios Communication Receivers: Filters, etc. in the range of 250 kHz to 5 MHz, but can be effectively used to 30 MHz. Can be used with any general purpose oscilloscope. Requires 12V A.C. input. Three controls—RF level sweep width and frequency. Price £8.50 A second model is available as above but which allows the range to be extended down in frequency to 20 kHz by the addition of external capacitors. Price £11.50. Both models are supplied connected for automatic 50 Hz sweeping. An external sweep voltage can be used instead. These units are encapsulated for additional reliability, with the exception of the controls (not cased not calibrated).

PLEASE ADD V.A.T. AT 8%  
OPEN 9 a.m. to 6.30 p.m. ANY DAY

**CHILTEAD LTD**

7/9 ARTHUR ROAD, READING, BERKS.  
(near Tech. College) Tel.: Reading 582995/65916



### ALL PRICES INCLUDE VAT

**AERIAL MAST POLES.** Approx. 5ft. 2in. high, 2in. dia. Interlocking ends. Minimum order 3. As new, £1.25 (each) P. & P. 40p each.

**AERIALS.** As new. Whip Type 11ft. £1 each. Collapsible type. P. & P. 20p. New Bases for the above 75p. P. & P. 30p.

**PAIR OF 4 x 150A VALVES** complete with bases ex-equip not tested. Good condition £3. P. & P. 30p.

**BARGAIN PARCELS** 14lb at £1.60 plus 35p p.p.; 28lb at £3.00 plus 57p p.p.; 56lb at £4.95 plus £1.37 p.p. Contains pots, Res. Valves, Diodes, Transformers, Chassis, Valveholders, etc. Good value save £££. Lucky Dip Service.

**FANTASTIC BARGAIN.** New 6 inch tubes. E450 4B/16 4VH. medium Persistence, green. Ideal scope tube.

Also 7BP7. All unused as new. Price £2 post Paid.

**TRANSISTOR BOARDS**—consisting of transistors, diodes and resistors etc. Long leads. Good value 12 for £1.00 (min. order) P. & P. 30p. Quotations for quantity.

**OUR SELECTION OF 6-Ex. Equ. METERS** consisting of 3in., 2 1/2in., 2in. mill amps, volts, amps. Mixed at the bargain price of £2.20 P. & P. 30p. minimum order of six.

**NEW AERIAL WIRE ON BOARDS 7/22 UNCOVERED** 90ft £1. p. & P. 25p.

**AERIAL POLES** 4ft high 2" in diameter push-in type as new £1 each p. & P. 25p each minimum four.

**DLR No. 5 HEADPHONES**—High impedance. Good condition £1.30 postage paid.

### C.W.O. CARRIAGE CHARGES MAINLAND ONLY

WOULD CUSTOMERS PLEASE ENSURE THAT ALL ORDERS ARE PRINTED IN BLOCK CAPITALS AND INCLUDE YOUR ADDRESS.

**A. H. THACKER & SONS LTD.**  
Radio Dept., High Street, Cheslyn Hay, Nr Walsall, Staffs.

# MAPLIN ELECTRONIC SUPPLIES

**\* SAME DAY SERVICE**

## ORGAN BUILDERS

MES announce the very latest development in organ circuitry.

### THE DMO2

12 Masts: Frequencies on ONE tiny circuit board. LOOK AT THESE AMAZING ADVANTAGES

★ 12 frequencies from C8 to C5. ★ Each frequency digitally derived from a SINGLE hf master oscillator. ★ Initial tuning for the WHOLE ORGAN ONE SIMPLE ADJUSTMENT. ★ Relative tuning NEVER drifts! ★ External control allows instant tune-up to other musicians. ★ Outlets will directly drive most types of dividers including the SAJ110. ★ And each outlet can also be used as a direct tone source. ★ Variable DRPTH AND RATE tremulant optional extra. ★ Gold-plated plug-in edge connection. ★ Complete five glass board (including tremulant if required) ONLY 3.7in. x 4.8in. ★ Very low power consumption.

★ EXTREMELY ECONOMICAL PRICE. ★ Ready built, tested and fully guaranteed. DMO2 (with tremulant) ONLY £14.85. DMO2 (without tremulant) £12.25.

★ R.a.c. Please for full technical details.

Trade enquiries welcome.

SAJ110 7-stage frequency divider in one 14 pin DIL Package. sine or square wave input allows operation from almost any type of master oscillator including the DMO2 (when 97 notes are available). Square wave outputs may be modified to saw-tooth by the addition of a few components. SAJ110: £2.83 each OR special Price for pack of 12: £25.00. R.a.c. please for data sheet.

Keyboards: High quality adjustable type

Sloping front 61-note C to C	£18.50
Sloping front 49-note C to C	£14.85
Flat front 45-note F to F	£14.85
Contact Blocks GR2 (2 make contacts)	13p
Palladium earth bar over octave length	15p
Stop Tabs rocker type not engraved (white, red, grey or black) with DPDT switch	49p
8-well pedal 10k log pot fitted	25-98

### REVERBERATION UNIT

Enhances the sound of any electronic musical instrument. Ready built spring line driver module suitable for use with almost any spring line

Two types of spring line available	25-34
Short line	22.05
Long line	27.99

R.a.c. please for details. Leaflet MES 24

## DISCOUNTS! DISCOUNTS!

Every time you spend over 42 (excluding VAT) you will receive some MES Discount Vouchers. One for each full pound spent on goods, two for each full pound 1p you spend over 42 on goods. When you've collected over 25 vouchers send them to us with an order and we'll give you FREE GOODS TO THE VALUE OF 41.

## BASIC ORGAN CIRCUIT

Leaflet MES 61 shows complete circuit for a basic fully polyphonic organ. Send only 15p for leaflet and start building now! R.E.M. EMERSON - has you have built this organ you will later be able to use the same top quality component parts as the basis of a large sophisticated instrument with all the facilities you want. Watch our ads for details. Leaflet MES 62 shows how to extend your MES 61 basic organ to two keyboards with lots more stops. Just send 30 (stamp) with an a.e. and we will send you a copy.

## CAPACITORS

Sub-miniature

Axial lead electrolytic

Mfd V	Price	Mfd V	Price
1.63 5p	65	6.3 6p	
1.63 6p	68	15 6p	
2.2 6p	68	43 14p	
3.3 6p	100	4 8p	
4.7 5p	100	10 8p	
6.8 4p	100	20 8p	
8.2 3p	100	40 8p	
10 2p	100	63 10p	
10 6p	150	6.3 6p	
10 14p	150	10 8p	
10 40p	150	25 8p	
15 6p	150	40 14p	
22 10p	150	63 15p	
22 25p	150	40 15p	
22 45p	150	10 15p	
33 4 30p	220	15 6p	
33 16p	220	20 14p	
33 40p	220	40 16p	
47 4 4p	220	63 25p	
47 10p	220	4 20p	
47 25p	220	10 20p	
47 40p	220	15 18p	
47 63p	220	25 22p	
47 100p	220	40 22p	
47 150p	220	63 22p	
47 220p	220	100 22p	

## PLUGS AND SOCKETS



### DIN PLOGS

2 pin (1 flat) 8p  
3 pin 8p  
4 pin, 5 pin A 10p  
A (180°), 5 pin B 10p

### MAINS

230V 2 pin 1.5A socket 8p  
chassis plug with line socket. Per pair: 25p  
SA 2100 8 pin 5A chassis plug 20p  
SA 1882 line socket for above 2p

### MSS 8 way chassis

8 pin socket 68p  
PHONO Plug plastic 5p  
Plug screened 12p  
Chassis socket 4p

### 8 pin stereo plug

Plastic 12p  
Screened 12p  
Chassis socket 4p

### DIN Sockets

2 pin 8p  
3 pin, 4 pin, 5 pin A (180°), 5 pin B (240°), 7p, 6 pin 9p

### MONURDIO

RFB 5 way chassis plug 52p

### JACK

8 pin mono plug Plastic 12p  
Screened 21p

## WE KNOW YOU NEED IT!



The MES 1974 Catalogue is STACKED with dozens of tempting new lines. BRIMMING OVER with clear illustrations and detailed data. WE'RE WAITING TO RUSH YOU A COPY. You'll be IMPRESSED with our FAST FREE ordering system, EXCITED by our BIG VALUE Account vouchers, STAGGERED by our UNBEATABLE speed of service. Take the first step towards real service NOW! Send ONLY 25p for our beautifully produced catalogue and leave the rest to us!

## OMNIUM GATHERUM

- Pr. 3, 6 etc. battery clip dual min. 9p
- Pr. 1, 9 etc. battery clip separate per pair 6p
- Pair crocodile clips 1 red, 1 black insulated sleeve. 10p
- Solder Multicore 22swg 10 metres 25p
- Silicone grease in special dispenser 20ml. 54p
- Red neon 240V panel mount 23p
- Lacing Cord Strong rayon core PVC 2mm. 51p
- Panel fuse holders 20mm 20p; 1 1/2" 41p
- Transformers  
1/2700 min. output (resistorless) Pri 1.2k Ω Sec. 5 Ω 200mW 50p
- Sub-min. Mains Transformer 6-0-6V 100mA 95p
- 12-0-12V 50mA 95p
- Size: Both approx. 30 x 27 x 25mm
- Min. Mains Transformer (Size: 48 x 31 x 35mm) 0-12V 250mA. £1.98
- Mains transformer MT3AT Pri 200-220-240V, Sec. 12-15-20-24-30V 2A £3.21
- Mains Transformer MT26AT Pri. 200-220-240V, Sec. 0-16-20V 1A, 0.15-20V 1A £3.98

### MES CATALOGUE 25p

Our 50 page catalogue has over 20 pages showing connection details and data for over complete range of instruments. 4 dozen I.C.'s etc. + Over 100 Photographs + Over 100 line drawings. Being exactly what you're buying makes ordering so easy!

## POTENTIOMETERS

Rotary miniature carbon track 1" spindle.



Single gang Lin or Log 5k, 10k, 25k, 50k, 100k, 250k, 500k, 1M, 2M (and 1k 1M) 12p



Single gang with DP switch 250V 2A Log or Lin 5k to 2M as above 32p

Dual ganged (Stereo) without switch Log or Lin 5k to 2M as above 49p.

### PRESETS

Sub-miniature 0-1W Vert or Horiz. 100, 200, 300, 1k, 2.5k, 5k, 10k, 20k, 50k, 100k, 200k, 500k, 1M 5p

## NE555V 8-pin DIL 69p

## RESISTORS

Carbon Film 1/2W 5% 1Ω to 1M, 10% 1/2W to 10M E12 E2 1p
Carbon Film 1/4W 5% 1Ω to 10Ω; 10% 1/2W to 10M E12 E2 1p
Carbon Film 1/4W 5% 1Ω to 10Ω E12 A E24 1p
Carbon Film 1/4W 5% 10Ω to 10M E12 A E13 5p
Metal Oxide 1/4W 5% 10Ω to 1M E12 A E24 4p
Wirewound 2W 10% 0.22ohms to 0.47ohms E12 14p
Wirewound 2W 5% 1ohms to 270ohms E12 12p

E12 values 10, 12, 15, 18, 22, 27, 33, 39, 47, 56, 68, 82 and decades  
E24 values 11, 13, 16, 20, 24, 30, 36, 43, 51, 62, 75, 91 and decades

## LINEARS

CAR055	69p
LR0402C T099 (T05), NET 1/2p Op Amp	£4-25p
LM3501A, 8 pin DIL, Op Amp	25p
MC1301L, 14-pin DIL Stereo Pre-amplifier	21-89p
MC1310P, 14-pin DIL PN Stereo Decoder (no audio needed)	21-15p
MFC0490, electronic attenuator	26p
MP0410, 8-pin base, 1W Audio Power Amp	£1-27p
MPC4000B 1/2 watt Audio Amp	89p
NE555V, 8-pin DIL, Precision Timer	69p
NE561B, 16-pin DIL, Phase Locked Loop	£4-48p
OP3402N Amplifier/Multiplier	21-69p
801495D, 14-pin DIL, Four Q	22-70p
MA723L, T099 (T05), 2 to 37V Voltage Regulator	75p
MA723C, 14-pin DIL, 2 to 37V Voltage Regulator	75p
MA741C, 8-pin DIL, Op Amp	85p
MA741C, 14-pin DIL, Op Amp	85p
MA747C, 14-pin DIL, Dual Op Amp	21-05p
MA748C, 8-pin DIL, Op Amp	85p
ZN414, T08, TRF Radio	21-80p

Full data, pin connections, etc., on nearly all types listed in our catalogue. Price 25p

## SWITCHES

Rotary with adjustable stop 1 pole 2 to 12 way; 2 pole 2 to 6 way; 3 pole 2 to 4 way; 4 pole 2 or 3 way, each 30p  
Mains rotary DPDT 250V 2A 20p



Push to make non-locking 14p



Toggle 250V 1.5A with ON/OFF plate 25p.

High quality "sub-miniature" toggle switches

SPDT 1.5A 200V AC	58p
DPDT 1.5A 200V AC	75p
DPDT 3A 240V AC	77p
Four Pole DT SA 240V AC	£1-27

## VAT

Please add 8% to the final total.

## Post & packing FREE in U.K.

(15p handling charge on orders under £1). First class post free-hand envelope supplied free with every order.

Orders and enquiries for catalogues to MAPLIN ELECTRONIC SUPPLIES, P.O. Box 3, Rayleigh, Essex. PHONE SOUTHEND (0702) 4401

# CHIPS UNLIMITED!

WE have, from time to time, taken a peep at the pocket calculator market. It has been currently estimated that the world-wide production of chips for electronic calculators for 1974 will be of the order of 28 million units. This exploding market is one of the few fields in which prices are constantly dropping. If the present growth rate continues, it is estimated that there will be an electronic calculator shortage within two years!

There exists a veritable jungle in both price and selection. The prolific arrays of pocket calculators that are available to the consumer that dominate the windows and counters of our local high street shops are indeed bewildering. There appears to be a greater variety of pocket calculators than transistor radios!

A price war has emerged amongst major manufacturers—prices being slashed overnight and indeed putting many retail distributors and 'special offer' organisations on the spot! A recent overnight price reduction by a major manufacturer caused considerable embarrassment to many of his trade and retail outlets. This sort of fiasco is being repeated over and over again. Where will it all end?

One enterprising calculator manufacturer determined to display his 'chips' to members of the public has opened up a 'mobile shop' at a London main line railway station. By all reports, he is doing *fantastic* business.

What of the 'domestic' pocket calculator? Rumour has it that a basic calculator especially designed for the housewife may be launched. If so, this could be just the thing for calculating and analysing those shopping expeditions to the supermarket. The shopper would be able to check his totals at any time and at the till check-out point. I can foresee many red-faced supermarket managers attempting to explain away the differences that may occur between store and customer calculated totals.

The pocket 'memory' calculator with its inherent potential as a pocket computer, with the ability to recall stored information at the press of a button could be just around the corner!

What of the future? The pocket calculator could become as prolific as the ball-pen—a must for everyone.

However, the pessimists (optimists, if you prefer) are chanting 'Beware, Big Chip is watching you!' (shades of 1984). They could however be forecasting our future.

There is no doubt that the calculator chip has, in many ways, dramatically changed our whole way of life. The question is: are we all in the hands of the Big Chip?

LIONEL E. HOWES—Editor.

We're off to a good start in the New Year with our three part series on Model Control by Radio and we tell you how to get your licence for this most interesting of hobbies. Do you sometimes wish you had a small audio amplifier around for testing purposes? Our 2 watt IC audio amplifier will fill the bill. The Special Pre-publication Book Offer ought to appeal to many of our readers for all the useful information contained in Radio Servicing Pocket Book, a new 3rd edition. Finally, you won't want to miss the fourth and final part of the PW Buyers' Guide 1974/75. All in the January issue of Practical Wireless.

## NEWS...

### From Partridge . . .

AN ever increasing number of people are living in space restricted environments. Either through sheer lack of external facilities for the erection of aerials, the inability to receive radio signals inside ferro concrete walls, or the existence of local government legislation preventing the use of outdoor space for aerials, there are ever growing numbers of frustrated readers unable to pursue their hobby of Amateur Radio or Short Wave Listening.

For many years now Partridge Electronics Ltd., of Broadstairs, Kent have specialised in equipment designed to overcome this problem. Five years ago they published a reproduction of a World Record Certificate awarded to American Radio Amateur W6TYP. This was achieved by Mr. Art Child of San Francisco using the Partridge system operated from a hotel room at the foot of San Francisco's famous Nob Hill.

Partridge have now developed a device known as A.G.T.U., an Aerial Tuning Unit which also incorporates an Artificial Earth (or ground). This overcomes the only remaining problem of the high-rise apartment or flat dweller having no access at all to natural earth.

### ON THE COVER...

#### PW's MINIATURE SCREWDRIVER

Don't despise this very useful workshop aid because it seems to be so small! How many times have you found that your 'small' screwdriver is just too wide or too thick for the grub screw in a knob or the adjusting slot in a subminiature potentiometer?? The more you use it the more uses you will find for our little present!

## Harrogate Fair

**A**UDIO '74 or the Northern International High Fidelity Festival at Harrogate was the biggest and best-attended ever. In 1970 there were only 50 exhibitors. 1972 saw 70 firms exhibiting their wares and this year over 90 companies decided to show their faces.

Over the last couple of years, there has been a marked increase in the amount of quadrasonic equipment on show. It is a pity that there seems to be little or no agreement on the kind of system to be favoured for quadrasonic reproduction.

We hope to include a short report on "Audio '74" in a future issue.

## BBC tape deal

**A** CONTRACT to supply the BBC with more than 100,000 reels of TS Scotch 262 recording tape for stereo broadcasting has been awarded to 3M United Kingdom.

The contract, which is due to run until next June, is in addition to the 70,000 reels supplied to the BBC last year after close liaison between the Corporation's sound engineers and technicians from 3M's magnetic tape facilities at Gorseinon, near Swansea, and Caserta in Italy.

## BEAB approval list

**T**HIS list covers the first category of audio products in the BEAB Approval Scheme which have successfully met the requirements of the British Safety Standard BS.415: 1972.

Decca Radio & Television with the Decca DS623, ITT Consumer Products Ltd. (ITT KP 820, KP 821, KA 1026, and RGD PA 30, P 83). Pye Limited (Pye 5000 and Invicta 8040). Sony (UK) Limited (Sony HMW-20). Rank Radio International Ltd. (Bush A 1005, A 1016, BS 3013, Dansette A 4005, A 4016, and Murphy MS 3014). Thorn Consumer Electronics Ltd. (HMV 2046, Ferguson 3047, Marconiphone 4047, 4049, Ultra 6046, 6048.

## Computer club

**N**OW moving into its second year of existence the Amateur Computer Club of Basildon, Essex has now formulated its activities into a constitution and elected officers for the year.

The club now has a firm membership of over 200 with a regular newsletter forming the nucleus of the club.

After two Annual General Meetings in London and committee meetings the start of a club activity schedule has emerged. The first of which was an open afternoon on the 25th May, 1974, at the Galdor Centre, 52 Brighton Road, Surbiton, Surrey.

The people at the Galdor Centre own and run an ICL 1301A computer (1960 vintage) which they have installed and made working to provide them and similarly interested persons with computer time at "materials only" cost.

## Heathrow computer

**C**ABLE and Wireless Ltd. have installed a new computer-based departure control system for airline passengers at London Airport. Japan Air Lines will use the system named "Lopac" which has been jointly developed by C & W and Scientific Control Systems Ltd.

Apart from speeding passengers' baggage check-in procedure, the system also allows for productivity expansion.

Lopac, incidentally, stands for Load Optimisation and Passenger Acceptance Control.

### PW TOOL KIT OFFER

**We apologise to our readers for the delay in dealing with their orders. The overwhelming demand created problems with delivery. If any readers have not received their tool kits, or a suitable alternative, would they kindly contact the Editor.**

Further activities are being arranged and will be announced in the newsletter which has also provided a unique forum for the airing of ideas and introducing basic principles to the beginner.

Articles in the newsletter have covered transistor working, design and operation of a digital core store, digital computer elements, computer software, software routines, descriptions of various computer systems both working and under design/development, news information items and computer games!

Club members are contributing articles to the newsletter resulting in some cross fertilisation of ideas among the members, which is one of the most important objectives of the club.

New members and ideas are very welcome, membership is £1.00 per year (that includes the near monthly newsletter) and applications should be directed to *Mike Lord, 7, Dordells, Basildon, Essex.*

## Javelin move

**J**AVELIN Electronics have closed down their City offices and moved to Javelin House, Second Way, Exhibition Grounds, Wembley, Middlesex HA9 OUA. (01-903-6821).

The new building contains the service department, a dealers' advice centre and a customer relations department.

## Sansui 4-channel

**T**HE sponsors of the "QS" 4-channel system, Sansui, are making moves to persuade artists in the UK to record material using their system.


The "QS" regular matrix system has been accepted by the American and Japanese Recording Industries Associations and over 20 record manufacturers are producing software in the system.

It has been stated that at least one commercial radio station in the United Kingdom is thinking of using "QS" which has now been adopted by all f.m. stations in Japan.

**SPECIAL  
PRODUCT  
REPORT**



**TOURIST II  
CAR RADIO KIT**

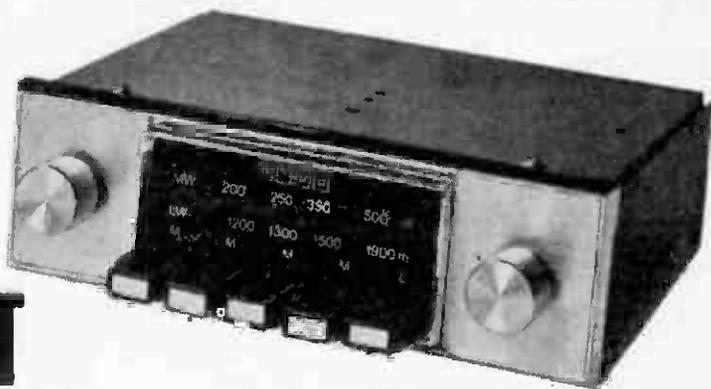

I MUST confess from the start that I am not entirely unfamiliar with the RT-VC car radio having bought an earlier version some time ago. I spent a couple of evenings leisurely soldering the bits and pieces to the printed circuit board and putting the thing together, following the instructions most meticulously. On connecting it up to a 12 volt battery in the workshop the radio worked first time and with a tweak of the oscillator capacitor the calibration was done.

The set soon disappeared into the innards of my daughter's Triumph Herald. I was about to say 'never to be seen or heard of again' but that would be patently untrue since the radio is simple but elegant in appearance and can certainly be heard! Subsequently, the set came out for a further fiddle on the oscillator trimmer to enable London's Capital Radio to be tuned in right at the low frequency end of the medium wave band. A big improvement on the side-band splash that had been tolerated up to then!

This latest Tourist Two car radio kit has taken all the fun out of the home construction of kits and one would be hard pushed to say, with a clear conscience, that 'I made it myself'. Admittedly the earlier version of the PCB had a few components plus the audio IC already soldered in position but I suspect that RT-VC did this so that they could say 'look at our soldering . . . now you do the same'. In fact, they insisted that the constructor's soldering was as good as theirs before accepting back any kits for servicing or checking . . . and quite rightly so.

Now, alas, the PCB comes completely assembled and the soldering iron remains cold and unwanted! A pair of long nosed pliers and a small screwdriver are all the tools required with this new kit and the remaining assembly work is child's play. In the words of RT-VC 'the kit can be assembled in less than two hours by anyone who has the ability to wire a normal household three pin plug'.

**Assembly**

The assembly instructions are extremely detailed and I cannot think of any point that would arise that isn't dealt with already. RT-VC's guarantee says 'If, after receiving your Tourist kit, you feel that its construction is not within your capabilities we will refund you the full price of the goods, less post and packing, upon the return of all parts supplied on the condition that no constructional work been attempted and all parts are received in the same condition as dispatched'. I hope that the formidable appearance of the assembly instructions, fault-finding guide, Installation instructions and six annotated photographs will not have the opposite effect and frighten off the prospective constructor!

Having completed the assembly you will want to know the polarity of your car's electrical system. If it is negative earth then the set is ready to go but if it is a positive earth then you have to change over two of the push-on tag connectors. Not very difficult! Should you decide ever to transfer the radio to a car of opposite polarity the change back can be made more quickly than it takes to tell.

**Installation**

RT-VC recommend a check-out of the set with the car battery before final installation in the car. Calibration takes a moment and the aerial trimmer is adjusted using the aerial that is to be fitted to the car. If all is well, and I'd be surprised if it wasn't, installation can now begin. RT-VC's instructions on this aspect are, again, as complete as they


**SPECIFICATION**

- Tuning Range :-** Medium Waves 185 to 555m (1620 to 540kHz)  
Long Waves 1153 to 2000m (260 to 150kHz)
- Sensitivity :-** Better than 15µV at 1MHz
- Output :-** 4 watts to 4 ohm speaker
- Controls :-** Push-buttons (4 MW 1 LW), manual tuning control, volume/on-off
- Dimensions :-** 7" wide 2" high 4½" deep approx.

The supply voltage is nominally 12 volts. The polarity, relative to the case, can be changed over internally simply by reversing two push-on tags. The circuit is protected by an internal fuse and a VDR (voltage dependent resistor) against static discharge.


**Prices :-** Car Radio Kit £17.70 +55p P/P. Speaker, including baffle and fixing strip £1.65 +23p P/P. Car Aerial, fully retractable and locking £1.37 +20p P/P.

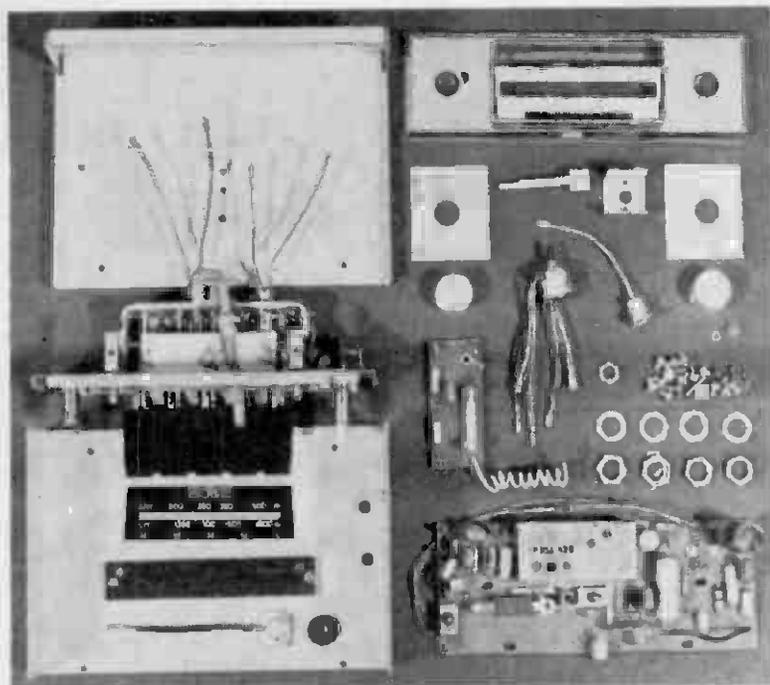**Radio and TV Components (Acton) Ltd., 21 High Street, Acton, London, W3 6NG**



The contents of your kit will look like this, left. Between the metal casing is the permeability tuning unit and pushbutton assembly. Bottom right shows the complete PCB which is fully tested before despatch.

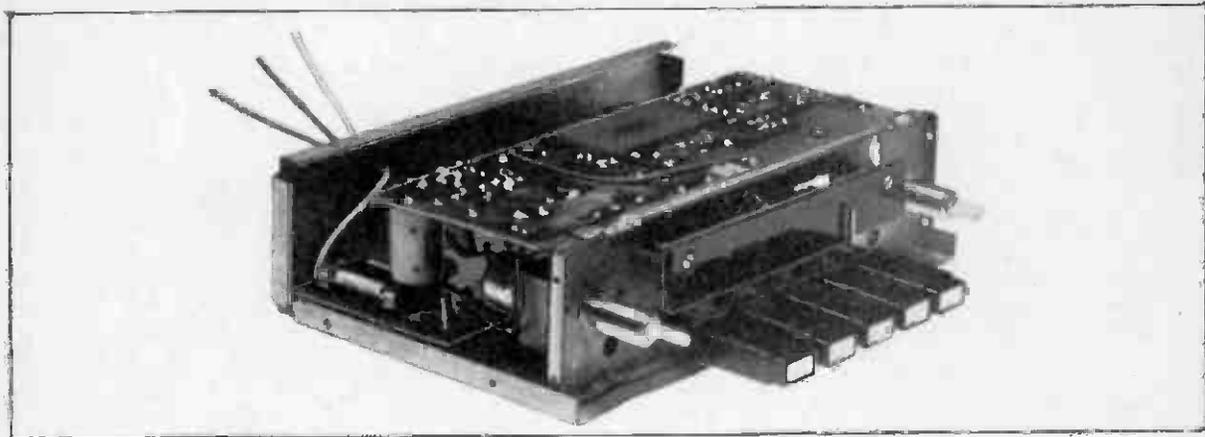If the simple instructions are followed the almost finished set should look like that in the photograph below. Only the dial, escutcheon and knobs remain to be fitted plus the cover.



can be and cover every contingency. There is one point here that might be stressed. If you use the aerial available from RT-VC the feeder is about 4' 5" long and the aerial trimmer works perfectly, peaking signals as it should do, when the overall performance is excellent. However, if you need to fit the aerial to the car in such a position that requires the feeder to be extended then this must be done using a special extension lead otherwise performance will definitely be impaired. Using ordinary coaxial cable just will not work. This point is fully covered in the instructions.

Apart from the manual tuning over both bands, four of the push-buttons can be set very easily to any desired stations on the MW band, the fifth push-button selecting a station on the LW band, usually BBC Radio 2, the band change being automatically effected by the action of the push-button. If, for some strange reason, the set does not work at all, or unsatisfactorily, then the Fault Finding Guide will come to your aid and the answer found very quickly.

## Interference

Having completed the installation and tested the radio to your satisfaction there is a chance that you will suffer a slight set-back when starting the car, because of inter-



ference to the radio from the various bits of electrical equipment. Generally, unless the car is a real old 'banger', normal suppression capacitors and other devices will be fitted to the car already and little trouble will arise. However, this matter is dealt with fully in the notes and if the logical sequence of checking is followed a rapid solution will be found.

## Conclusions

A very well designed kit with all the bugs ironed out long ago. Being a bit of a fiddler myself I would have liked the oscillator and aerial trimmer capacitors to be accessible from the outside of the case when the radio is installed in the car. I compromised by very carefully marking out and drilling two holes in the top cover of the case above the trimmers, sticking a bit of Sellotape over the holes when I had done fiddling. I wouldn't expect RT-VC to do anything about this point but I thought I'd mention it, got to complain about something!

Finally, I don't know how RT-VC do it at the price but I understand it is due to the purchasing in volume of proven components and direct retail sales. Certainly they are not contributing to the present inflationary movement!

# INEXPENSIVE CAPACITY BRIDGE

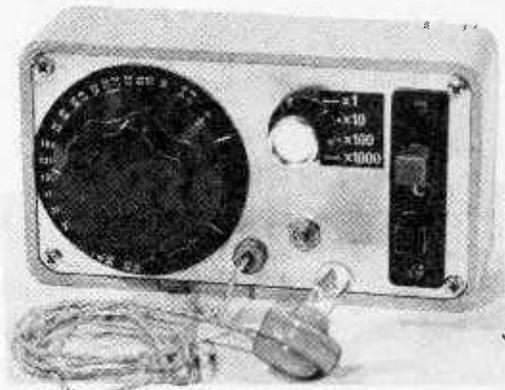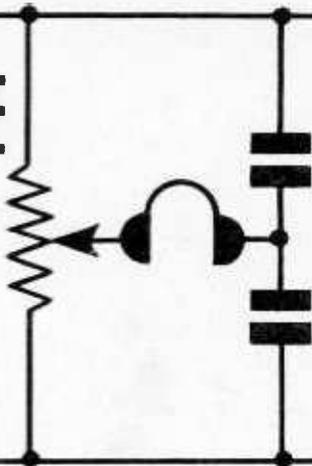

ERIC DOWDESWELL G4AR

TEST gear is often conspicuous by its absence from the amateur's workshop, possibly because such equipment can be expensive to buy but, more likely, because it is not a justifiable outlay considering the relatively few occasions on which it would be used.



The capacity bridge described here is very cheap to make, will measure capacities from as low as 2pF and up to about 10μF and will be found to be quite adequate for general workshop use. Over a period the constructor manages to collect unto himself a quantity of capacitors that have had their markings removed in one way or another. This bridge will enable them to be measured, checked and used again. Incidentally, it is a very wise man who checks the value of every component before using it, regardless of colour code or marking, saving a lot of time and temper.

It is not everyone who has good eyesight and even slight colour blindness can cause confusion with colour coded components, generally with blues, browns and greens, which can lead to wrong values of resistors and capacitors being fitted to PCBs etc. This bridge will eliminate any such problems especially if it is used as a matter of routine.

The dial is simple and easily calibrated and used in conjunction with a four step multiplier switch. The consumption of the bridge is very low and the internal 9 volt battery will last a very long time.

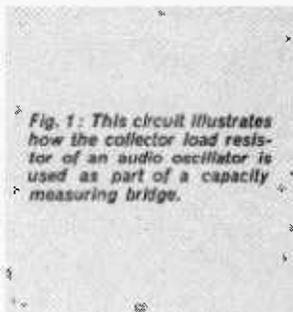
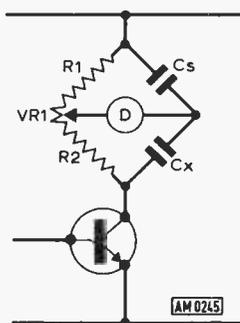
## DESIGN


As you may have guessed, a bridge circuit is used, what else! and was last seen in the Take 20 series




in this magazine. In essence, the collector load resistor of the second transistor of an audio oscillator forms two sides of the bridge, Fig. 1, and, in practice, is a potentiometer. The other two sides of the bridge comprise a capacitor Cs of known value and Cx, the capacitor under test. If these capacitors have the same value then, for the bridge to balance, R1 will equal R2. A detecting device 'D' placed across the bridge will indicate a null in the audio tone under these conditions. If Cx is any other value then the bridge is unbalanced and 'D' will indicate this. Balance can be restored if the ratio of R1/2 is adjusted to have the same ratio as Cs/Cx.

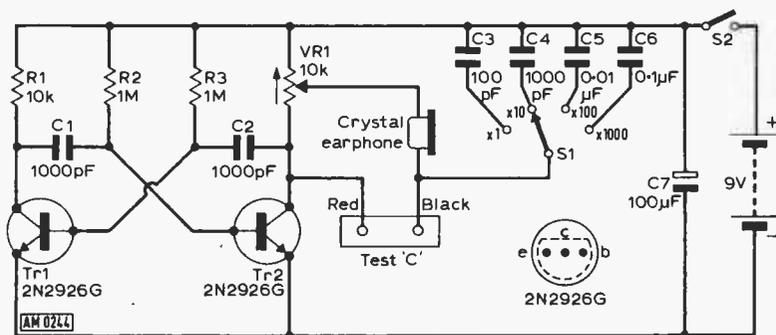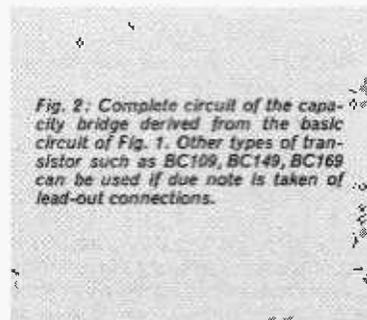In the practical circuit, Fig. 2, Cs is in the form of a four position multiplier switch with capacitors of 100pF, 1000pF, 0.01μF and 0.1μF all of close tolerance, the switch being marked x1, x10, x100



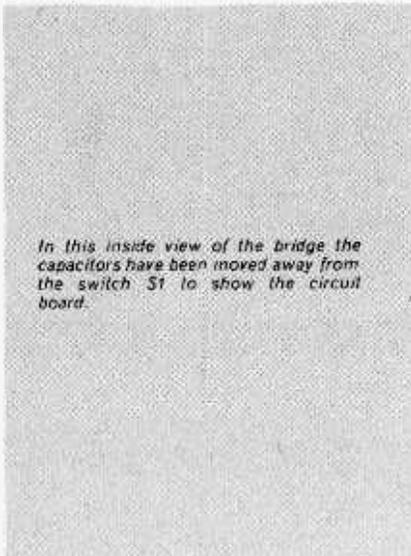

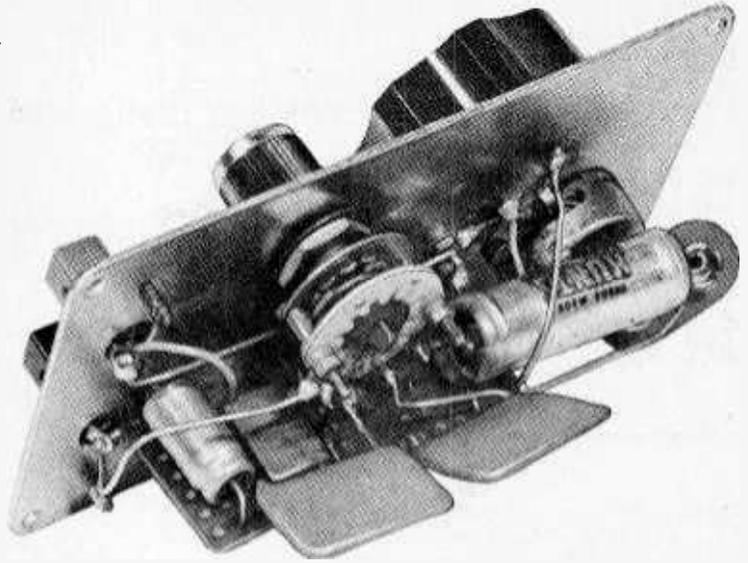In this inside view of the bridge the capacitors have been moved away from the switch S1 to show the circuit board.



and x1000. The capacitor under test is connected to the two terminals. Transistors Tr1 and Tr2 form a multivibrator circuit running at about 1kHz but the actual frequency is not of any great importance.

The detector is a simple crystal earphone of very high impedance, this factor contributing very significantly to the excellent performance of the bridge, the minimal damping imposed by the earphone providing a deep sharp null at balance.

## CONSTRUCTION

The bridge is housed in a heavy plastic box with all the components mounted on an aluminium panel. The oscillator components, with the exception of the potentiometer VR1, are assembled on a small piece of Veroboard as in Fig. 3. The bottom rail of the board is soldered to a tag bolted to the panel, providing adequate support for the board.

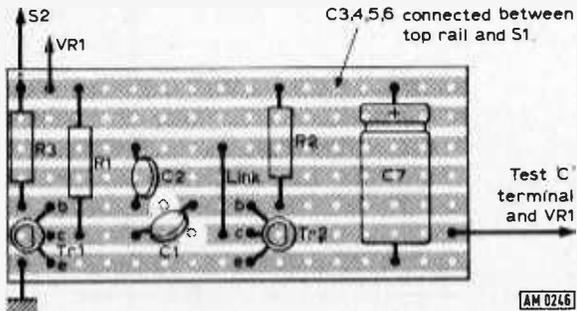


Fig. 3: Components comprising the audio oscillator are mounted on Veroboard as shown above.

The test terminals are spring loaded, their soldering tags passing through  $\frac{3}{8}$ in. holes drilled in the panel. The holes are purposely large to reduce self capacity. An alternative might be to use feedthrough insulators terminated on top of the panel with miniature crocodile clips on stiff leads. Whatever arrangement is used it is essential that a capacitor can be connected to the bridge and removed again very easily.

The potentiometer is a very ordinary linear carbon one with a plastic spindle, which, again, reduces self capacity but one with a metal spindle would probably work just as well. The dial was made from a disc of card held under the potentiometer fixing nut together with a pointer knob of such a size as to allow a single range of calibration figures to be marked on the dial. The dial is marked in the 'preferred' range of values corresponding to the standard markings on capacitors.


The crystal earphone is wired directly into the circuit, which again helps to reduce capacity. A combined phone jack and on/off switch was contemplated but a switch and isolated jack could not be found. If any doubt exists as to whether an earpiece is crystal or magnetic it can be checked with an ohmmeter. A magnetic one will show very low resistance whereas a crystal one will show, effectively, an open circuit. Just to make sure that you haven't got an open circuited magnetic earphone put it in the ear and check again with the meter when clicks should be heard even though the meter indicates an open circuit.

The multiplier switch used here is a miniature ceramic one but the more common plastic or paxolin wafer type will suffice. However, if the switch chosen has been used before it must be very thoroughly cleaned before using it in this bridge, for reasons which will be noted later. The standard capacitors C3 to C6 are wired directly between the switch tags and the top 9 volt rail on the circuit board. If a standard size switch is used it will be necessary to move the board down from the position shown in the prototype. It is a good idea anyway, with any project, to shuffle the components around for best positioning before drilling panels etc.
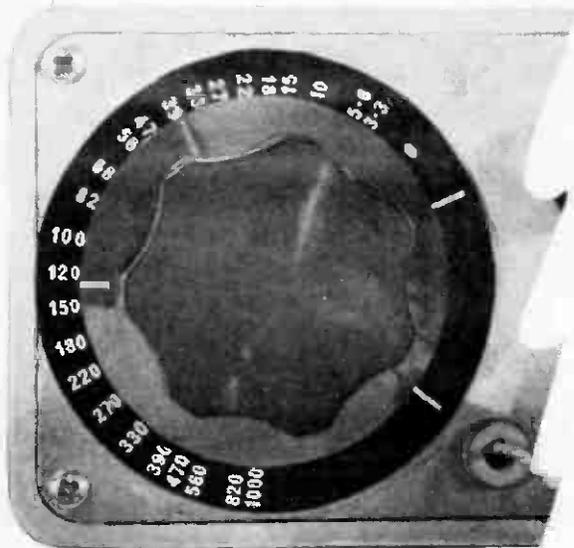
## CALIBRATION

After the small amount of wiring is completed and checked, fit the PP3 battery and switch on when the audio tone should be heard in the earphone. The volume should be adjustable from maximum to zero using the potentiometer. Adjust the position of the knob on the potentiometer spindle so that the ends of its travel are positioned as shown in

the photograph of the bridge. Mark these positions on the dial with a sharp pencil. With the multiplier switch on x1 a null should be found near the top of the dial, if the potentiometer has been wired as shown in Fig. 2. This represents the zero position of the bridge without any external test capacitor. Mark this point on the dial.



Close-up of the dial of the bridge. Note that the limits of travel of the potentiometer are also marked.

With a 100pF 1% capacitor connected to the terminals and multiplier on x1 find a new null at about mid position on the dial, then mark it. Turn multiplier to x10 and locate null not far inside the 0 mark. This is marked 10. Note that we have been able to find two points on the dial for one capacitor, using the multiplier. This feature can be used to cross check dial readings.

Change the test capacitor for one of 100pF 1% and mark the null at the bottom end of the dial. Switching to x10 should locate the null at the 100 point, already marked. The remainder of the calibration is done using 1% or 2% capacitors in the preferred range of 120, 150, 180, 220, 270, 330, 390, 470, 560, 680 and 820pF. The x1 multiplier is used to mark the remaining points between 100 and 1000pF and x10 for the points between 10 and 100pF.

## TOLERANCES

For a general purpose bridge the cheaper 5% tolerance capacitors are quite adequate for calibration purposes but instead of having to buy the thirteen preferred values it is possible to make do with eight only, the missing values being obtained by paralleling certain capacitors as shown in the Table. There are probably other combinations possible by connecting capacitors in series or even series parallel!

The calibration can be completed with a fine ball point pen or a more fancy dial constructed, as shown in the photograph. As the end points of the

potentiometer travel have been marked the dial can be removed for finishing or copying and then replaced without losing calibration.

### CALIBRATION CAPACITORS (pF)

100	220	470
120	270*	560*
150	330*	680*
180	390*	820
	1000	

The capacitors marked \* may be obtained by connecting other values in parallel, as follows:—

270	120 + 150	330	150 + 180
390	220 + 180	560	220 + 180 + 150
680	220 + 180 + 150 + 120		

## EXTENDING RANGE

As shown, the maximum capacity indicated on the dial is 1000 x 1000pF or 1 $\mu$ F but it was later found possible to extend this range to 10 $\mu$ F enabling small value electrolytic capacitors to be checked, although it should be remarked that there is no polarising voltage applied to the capacitor under test. Nevertheless the bridge has been found very useful for this purpose.

The accuracy of this extension to 10 $\mu$ F will depend upon the accuracy of a 1 $\mu$ F capacitor that is required for calibration. Again, a 5% tolerance will do as a 1% capacitor of this value is rather expensive. Connect across the test terminals and locate a null near to the bottom end of the travel, past the 1000 mark. The multiplier should be on x1000. The point can be marked 10nF for simplicity. Only two or three intermediate points are required such as 2200, 4700 and 6800.

## IN USE

Normally the null will be very deep and sharp. In my own case, the audio tone actually disappears at the null point and I generally consider my hearing

## ★ components list

### Resistors

R1 10k $\Omega$  10%  $\frac{1}{4}$  or  $\frac{1}{2}$ W R2/3 1M $\Omega$  10%  $\frac{1}{4}$  or  $\frac{1}{2}$ W  
VR1 10k $\Omega$  linear carbon potentiometer. See text

### Capacitors

C1 1000pF 10% C5 0.01 $\mu$ F 1% SM or  
C2 1000pF 10% Polystyrene  
C3 100pF 1% SM C6 0.1 $\mu$ F 1% Poly-  
C4 1000pF 1% SM styrene  
C7 100 $\mu$ F 16V electrolytic

Calibration Capacitors:—see text and table

### Miscellaneous

Tr1/2 2N2926G. Crystal earphone. Battery 9V PP3, battery clips. On/off switch. Veroboard 0.15in. matrix, approx. 2 $\frac{1}{2}$  x 1 $\frac{1}{2}$ in. Knob and dial. Terminals (2). Case and panel 5 x 2 $\frac{1}{2}$  x 1 $\frac{1}{2}$ in. deep (Stella 99 series, from E. R. Nicholls 46 Lowfield Rd., Stockport, Cheshire.) S1, Single pole 4-way wafer switch.

to be better than average. If the null is not deep and seems to be undefined then the capacitor is probably leaky although it may be of the order of a few megohms. The effect can be simulated by connecting a high value resistor across a known good capacitor and testing the combination on the bridge. The lower the resistance the poorer will be the null. In the long run it is better to destroy such leaky capacitors at the time of testing rather than to leave them around to be used in equipment where the leakage might prove highly detrimental to the operation of a circuit.

### AUDIO OSCILLATOR

The bridge can also be used as a source of audio tone for testing amplifiers and suchlike, the output being taken from the test terminals and adjustable from zero to maximum output with the potentiometer. The waveform is very rough, of course, coming from a multivibrator but quite adequate for general audio testing. If a Morse key is connected across the on/off switch the unit can be used as a Morse code practice set. A second crystal earpiece can be connected across the test terminals and, if two keys are connected in parallel, two-way simulated signalling will be possible.

# PW TECHNICAL CROSS PUZZLE No. 7

presented last month

1	I	2	A	3	S	4	H	5	O	6	R	7	T	8	W	9	A	10	V	11	E
12	M	13	A	14	P	15	S	16	I	17	H	18	I	19	E						
20	P	21	P	22	S	23	P	24	I	25	N	26	N	27	E	28	R	29	S		
30	E	31	R	32	A	33	S	34	E	35	S	36	N	37	D	38	A				
39	D	40	R	41	W	42	S	43	E	44	T	45	C	46	E						
47	A	48	M	49	A	50	Z	51	E	52	T	53	C	54	O	55	I	56	L		
57	N	58	T	59	S	60	C	61	A	62	N	63	S	64	N	65	E				
66	C	67	H	68	U	69	M	70	F	71	A	72	S	73	D	74	I	75	C		
76	E	77	S	78	V	79	H	80	F	81	S	82	E	83	T						
84	G	85	T	86	U	87	S	88	H	89	I	90	N	91	E	92	R				
93	F	94	E	95	R	96	R	97	A	98	N	99	T	100	I	101	S	102	O		
103	N	104	A	105	C	106	G	107	L	108	E	109	A	110	D						
111	H	112	E	113	A	114	D	115	P	116	H	117	O	118	N	119	E	120	R	121	E

# TELEVISION

## IN THE DECEMBER ISSUE

### SIGNAL STRENGTH METER

Correct aerial alignment is important if bright, sharp pictures free from blurring due to multipath reception, stably synchronised and with accurate grain-free colour are to be achieved. This is difficult without a signal strength meter since the receiver's a.g.c. system will hide signal strength variations—quite apart from the physical problems. The TV signal strength meter described is portable and can be used to ensure that any u.h.f. TV aerial is aligned for optimum reception: it is equally useful in local and fringe areas. Features include varicap tuning, three gain ranges and a unique indicator of vision carrier reception by means of a light-emitting diode. Construction is easy since a ready-made surplus i.f. strip is used.

### DECODER FAULT-FINDING

Colour receiver decoders are generally reliable but when they do give trouble fault-finding can be a headache. In "Practical Decoder Fault Finding" in this issue a number of useful hints and tips based on practical experience are given together with guidance on the logical approach to tracing faults.

### SELF-CONVERGING COLOUR C.R.T.s

The next generation of colour sets—already beginning to appear on the market—will be fitted with self-converging c.r.t./deflection yoke systems. How these operate, with particular reference to the Mitsubishi SSS tube, will be described.

### SERVICING TELEVISION RECEIVERS

The Baird/Radio Rentals 660, 670 and 680 series of TV receivers and their faults will be described by Les Lawry-Johns.

### PLUS ALL THE REGULAR FEATURES

TO .....  
(Name of Newsagent)

Please reserve/deliver the DECEMBER issue of TELEVISION (25p) and continue every month until further notice.

NAME .....

ADDRESS .....

# HOTLINES

ON RECENT DEVELOPMENTS

## MEASUREMENT

IT never ceases to amaze me that measurement in electronics gets more and more sophisticated as every day passes. On reflection this must be so because as the very latest devices are born, some means must be to hand with which to measure, accurately, their performance. At the recent International Microwave Exhibition at Montreux, for example, there were switches shown which could switch at 26GHz—that's twenty-six thousand million times every second! I might add that the man on the stand eagerly told me, "... and of course we're working on higher frequencies right now".

While frequency must be measured accurately, what about time? Latest to come to my attention is a time interval counter which is soon to be launched in America. The amazing thing about this one is that it has a resolution of 100 Femtoseconds. If you are not impressed then let me add that a Femtosecond is 0.001 of a picosecond and a picosecond is one millionth of a microsecond which, of course, is one millionth of the common or garden everyday household second. For the technical/boffin types it's  $10^{-15}$  seconds. Just think if every Amateur radio station had one of these, it could tell its transmission frequency to a fraction of a cycle even at v.h.f.

## TIMED CALCULATION

Electronic calculators and digital wrist watches always create interest but now I really have heard it all. The ultimate is about to be launched onto the market, something that will satisfy even the most pedantic of tios. It's a digital wrist watch and calculator combined! The calculator part has a nine digit readout and offers forty functions. When it's not used as a calculator it functions as a digital watch. There are only 20 buttons on the calculator and here the designers have introduced a very crafty dodge.

Although only twenty buttons are employed (because of space considerations) there's a "shift key" which, when activated, gives the twenty buttons other functions thus

giving a 40 button capability. This shift key acts something like the shift key on a typewriter which allows the same keys to be either capital letters or small, lower case letters. The watch/calculator measures about 1.5in x 1.5in x 0.5in. deep. The first models are rumoured to be priced at around £200-£250 but they're not available yet and probably won't be for some time. The buttons, incidentally, are depressed with a small probe, or tip of a ballpoint pen as far as I can ascertain. Information is rather scant because this is a state of the art unit and the information is red hot.

## SOLID-STATE C.R.T?

A colleague in Washington reports that the US Army may soon lay its hands on a liquid crystal display which gives an 84-character output. It also might be used as a liquid crystal cathode ray tube. At present the company doing the development is waiting to get a Government grant with which to continue work. It is also rumoured that the prototype device is coupled up to a miniature warfare computer. If this development is well funded, it could be another avenue of development for the solid state c.r.t. for television receivers.

## SOLID-STATE CAMERA

At the other end of the television signal—the camera, developments are pressing on with solid state sensors which will replace the vidicon camera tubes. This was highlighted at the recent conference on charge coupled devices (c.c.ds) which took place at Edinburgh University. Of great interest was mention (plus photograph) of a miniature entirely solid state television camera which was constructed by Bell Labs at Murray Hill, New Jersey. Another interesting fact about this television camera is that it is battery operated. The size was not mentioned but from objects in the photograph which include a ruler, it is judged to be of the order of 11cm x 6cm.

The camera uses a chip sensor which has 256 x 220 element array gives excellent results using NTSC scan rates and the author claims

that television image sensors with 525 and 625 line capability are now a viable product. It must be remembered that solid state cameras will not come in over night. At present, users of the "valve" type camera tubes have only to plug in a component and it works whereas these solid state items are still being developed. However, with the world shortage of silver and the search for some other means of photography, it isn't too difficult to see the amateur photographer of the future holding a tiny solid state twin lens reflex which records directly onto tape which can then be played back on the television receiver at home.

These CCD devices are well worth watching. New applications are coming up and are being enthusiastically worked on. To date they are being used in TV applications, infra red cameras, delay lines, telecommunications, memories for computers and are even employed to generate a s.s.b. signal.

## IT'S SIMPLE!

The servicing of television sets has taken a step nearer to being automated. Grundig colour television receivers are currently manufactured in modular form. A number of modules are used in a plug-in fashion, each unit looking after a specific function within the receiver.

The offending module (in the case of malfunction) is simply unplugged and either repaired immediately or just replaced and then repaired at leisure in the workshop.

Some 75% of the colour television circuitry is catered for in this way. Now, Grundig has taken care of the other 25% by adding a simple socket to the receivers. A small diagnostic unit is then simply plugged in. The circuitry is featured on the lid of the diagnostic box, and i.e.ds mounted in this circuit diagram illuminate to pinpoint any fault.

The logo for Ginsberg, written in a stylized, cursive script.



# Now there's Doram, you need never wait for electronic components.

## 7-day service.

Buy the new Doram catalogue and you could have your components within 7 days of our receipt of your order.

If you don't, you'll have your money back and no questions asked.

What you won't get is a tedious wait. Which goes on. And on. And on. And on. You know just where you are with Doram.

## Millions of components.

Doram is a brand-new deal for serious amateurs. It's a complete door-to-door components service operated by mail order.

You buy the Doram catalogue for 25p (that's a yearly reference book for the price of a pint) and then you order from it.

We're big enough to offer you stocks of millions of components on over 4,000 product lines.

And so confident of our service that if we can't supply the part you want within 7 days of receiving your order, we'll give you your money back. Immediately.

## No-quibble guarantee.

It's just about impossible to buy a defective part from us. Because our checking is so pains-taking.

But even if the unthinkable does happen—and you're unlucky—then we'll still make you happy quickly.

Because we offer a no-quibble replacement part service.

And our guarantee is guaranteed by the fact that we belong to the biggest electronics distribution Group in Britain.

## All branded goods.

All goods supplied are branded goods. Made by big-name manufacturers like RS, Mullard, SGS-ATES, Ferranti,

[www.americanradiohistory.com](http://www.americanradiohistory.com)

Doram brings the amateur the sort of service only professionals have enjoyed before.

So don't delay. Use the coupon. Send today for your first Doram catalogue. It can make your life a whole lot easier.

For 25p that can't be bad, can it?

**I ENCLOSE 25p: PLEASE SEND ME THE NEW DORAM CATALOGUE.**

Name

Address

**Doram Electronics Limited,**  
PO Box TR8,  
Wellington Road Industrial Estate,  
Wellington Bridge, Leeds LS12 2UF.


\*This will be refunded on orders of £5 (less VAT) or more received by us before March 31st, 1975.

**DORAM**  
pwl1217a

LISTEN TO

**CODAR** THE WORLD!

★ **CR70A**

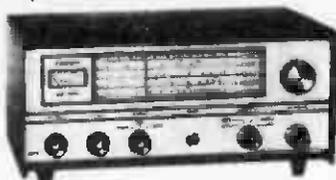

**COMMUNICATION RECEIVER**

The CODAR CR70A is an outstanding general coverage communication receiver, ideal for the keen S.W.L. It covers from 540 metres medium through to 10 metres with no gaps. Comes shipping, coastguard and distress frequencies, all six amateur bands 160-10 metres, International broadcast, Met. stations etc. etc. giving world-wide reception. Exclusive features include Air-spaced CODAR-COIL Hi-'Q' Aerial input, illuminated Meter and Slide Rule Scale, Two Speed vernier tuning, Switched B.F.O. for CW/SSB signals. Separate output for Tape recorder. Ready to plug in to 200/240 volts A.C. it only needs your aerial and a 2/3 ohm loudspeaker to bring the world to your finger tips. 12 months full guarantee.

★ **IMPORTANT NOTE**

This fine receiver is not a mass produced item, but each set is hand built to your order, individually checked and air tested. Please allow for this when ordering—your delivery date will be shown on your order receipt, sent by return.


★ **MADE TO ORDER!**

**£34.14!**

VAT PAID  
CARR. 87p



★ **P.R.40** ★

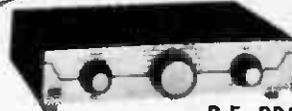

**£10.93!**  
VAT PAID  
CARR. 32p

**R.F. PRESELECTOR**

The PR40 R.F. Preselector is the solid state version of the world famous PR30 which is now superseded. It employs Silicon "NPN" Channel FET (Field Effect Transistor) front end followed by silicon NPN Broad Band R.F. Amp., and will substantially improve receiver performance over the range 1.5 to 35 MHz, providing a considerable increase in gain up to an overall average of 30dB, with improved image rejection and noise ratio. Supplied complete with co-ax plug (less standard 9 volt PP6 Battery). 12 months Guarantee.



**MULTIBAND-6** ★

**SHORT WAVE RECEIVER KIT**

**£16.90!** CARR. 43p

All transistor T.I.F. Receiver tunes 550 KHz to 30 MHz (540 to 10 metres) complete coverage—no gaps. Medium waves—Trawlers—Ship / Shore Telephone—All Six Amateur Bands 160-10 metres—International Broadcast from Australia, Far East, Russia, USA etc. using 4 miniature plug in Coils. Hi-Gain FET Regen. Det./AF/AF Module giving full loudspeaker output to any external 2/3 ohm speaker. Receives AM/CW/SSB. Separate Electrical Bandspread, Calibrated Main Tuning. A Quality CODAR-KIT with 12 months Guarantee. No technical knowledge required, simple to build, printed circuit and Pictorial Instruction Manual, fully detailed step by step. Complete Kit with 4 Coils (less standard PP6 battery).

ILLUSTRATED LEAFLETS FREE ON REQUEST

ON THE DESIGN STAFF—  
G3SZM G3IRE

**CODAR**

TELECOMMUNICATIONS AND ELECTRONIC  
EQUIPMENT SUPPLIERS TO H.M. AND OVERSEAS  
GOVERNMENTS

VALCON WORKS · BURRELL BUILDINGS · CHURCHILL INDUSTRIAL ESTATE · LANCING · SUSSEX

Tel. 090-63-61901

BN15 - 8TZ



**NEW**

ALL  
SILICON!



PRACTICAL  
WIRELESS

**ELECTRONIC IGNITION SYSTEM**

This Capacitor-Discharge Electronic Ignition System was described in *Practical Wireless*, and has proved extremely popular.

The kit is supplied with a ready-drilled roller-tinned printed-circuit board and fully machined die-cast case with AMP Electrical Spade Connector Block together with a custom wound transformer, first grade components and full constructional details.

The original circuit employed Germanium Power Transistors for the negative earth version. **WE OFFER SILICON P.N.P. POWER DEVICES AT NO EXTRA COST!** All components are available separately. Case size 4 1/2" x 3 1/2" x 2". Complete assembly and construction manual free with kit, available separately 25p.

SUITABLE FOR 12V SYSTEMS WITH NEG. OR POS. EARTH.

PRICE: **£9.50** U.K. ORDERS PLEASE ADD VAT.

Quantity Discounts:

Trade and Overseas	1-5 Nett	6-9 less 10%
Enquiries Invited	10-49 less 15%	50-99 less 20%
Mail Order Only.	100-999 less 25%	1000 up less 30%

PLEASE STATE POS. OR NEG. EARTH WHEN ORDERING


**DABAR ELECTRONIC PRODUCTS**

98 LICHFIELD STREET  
WALSALL, Staffs WS1 1UZ



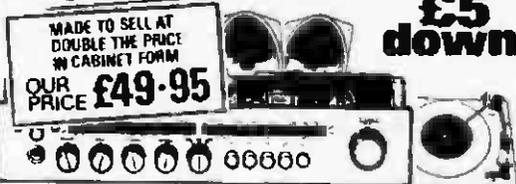**QUALITY STEREO SOUND.**

ALMOST 1/2 PRICE OFFER! SOLENT AUDIO SYSTEM



\*Stereo Tuner Amplifier chassis with AM/FM radio covering long medium short and Stereo FM wavebands. Separate Base and Treble controls. Power output 7 watts R.M.S. per channel (frequency response 25-20,000 Hz) Tape record and playback facilities. Dimensions 18" x 8 1/2" x 3 1/2". The very latest BSR automatic record deck with cue and pause control. Two matching elliptical speaker units.

Order early limited stocks available cash price **£49.95**. Credit Sale **£5.00** deposit 9 monthly payments of **£5.75** (Total Credit price **£56.75**). P. & P. **£2.50**. Send **£7.50** today.

Chassis only available for cash at **£35.00**.


Full 12 months Guarantee.

CALLERS WELCOME.

Stereo headphones supplied with every order.

**LEWIS radio** PW12/74 100 CHASE SIDE SOUTHGATE  
LONDON N14 5PL Telephone: 01-866 9666/3733

# MAKE YOUR OWN

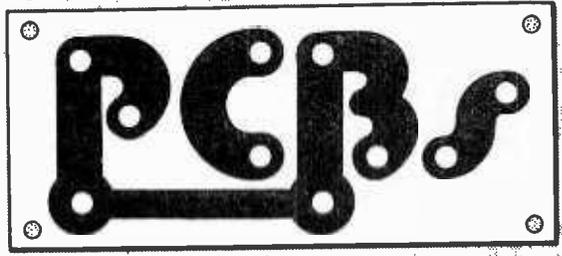

JOHN JACKSON

For the amateur, printed circuit boards have good and bad points. They are neat, reduce free wiring, make assembly mistakes less likely and can support large items such as transformers. On the other hand, they take time to make and subsequent modification to them can be difficult.

Ready-made "universal" printed circuit boards may have no copper where it is required, will have it where it is not needed and mistakes during soldering are easy as different areas look alike. The design and preparation of individual boards is easy and the materials readily available.

## DESIGN

The method used successfully for many projects is as follows. A fairly large copy of the circuit is drawn on thin paper, such as that used for typing (thin paper saves time later). All component junctions are ringed, as shown dotted in Fig. 1, to give the basic copper plan. Beneath this is drawn an outline, the size of the intended circuit board and, using components to check spacings, the basic plan is adapted to give a full size layout, Fig. 2.

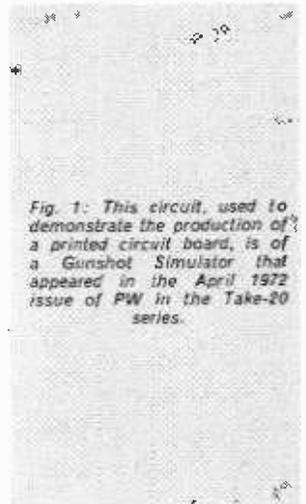
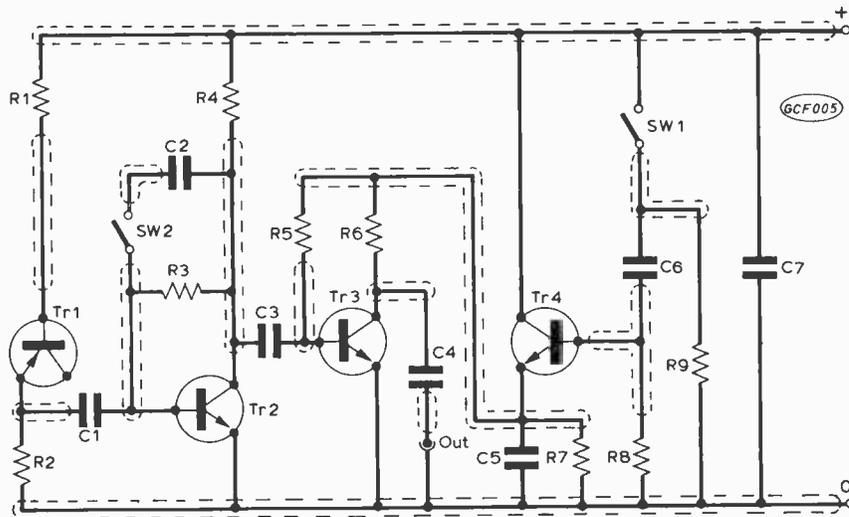


Fig. 1: This circuit, used to demonstrate the production of a printed circuit board, is of a Gunshot Simulator that appeared in the April 1972 issue of PW in the Take-20 series.

Tr1.1.1. A number can be crossed off each time a connection is allowed for.

A negative of the plan must now be made. This is easily done by turning the paper over and drawing over the lines that should be visible. This plan is the master diagram, see Fig. 3.

It is possible to forget to reverse the plan, which is not serious with transistor circuits, but it will be tricky reversing a nine-pin valve-holder to match!

## PREPARING THE BOARD

Copper laminate may be backed by fibreglass or SRBP, the latter being cheaper. Areas requiring copper, the "fields", are covered with resist and the unwanted metal is etched away. Resist can be from a purpose-made pen, such as a "Dalo" or use can be made of nail lacquer or paint (thinned enamel or cellulose).

First the board must be cut to size, with a hacksaw having a fine blade, cutting with the copper side up. After filing off any burred edges the copper must be thoroughly cleaned of grease or tarnish, using

In the final layout it is advisable to keep input and output points apart and wires leaving the board are better near the edges. Fixing holes must be taken into account and copper should not be too close to these, to prevent shorting to metalwork. To avoid missing a component, a list can be made with each component written once for each wire: R1.1, R2.2,

scouring powder on cotton wool. After rinsing and drying on a soft cloth the copper is ready for the resist and the board must be held only at the edges, as any grease may cause the resist to flake off and prevent areas from etching.

The board is then stuck beneath the master diagram, with a piece of Sellotape to reduce handling,

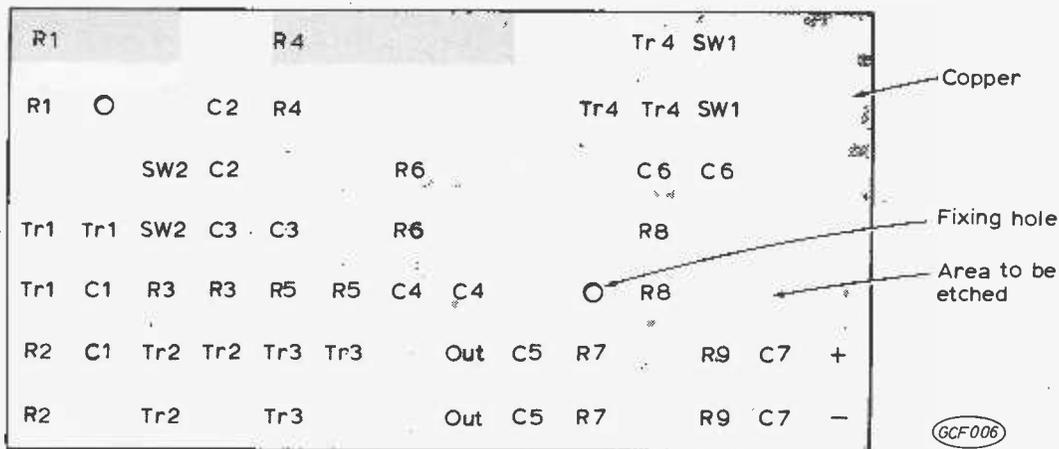


Fig. 2: The dotted areas of Fig. 1 are transferred to the paper master as shown here, the final layout depending upon the sizes of the components to be used. The copper will be on the other side of the board, which is shown here twice final size.

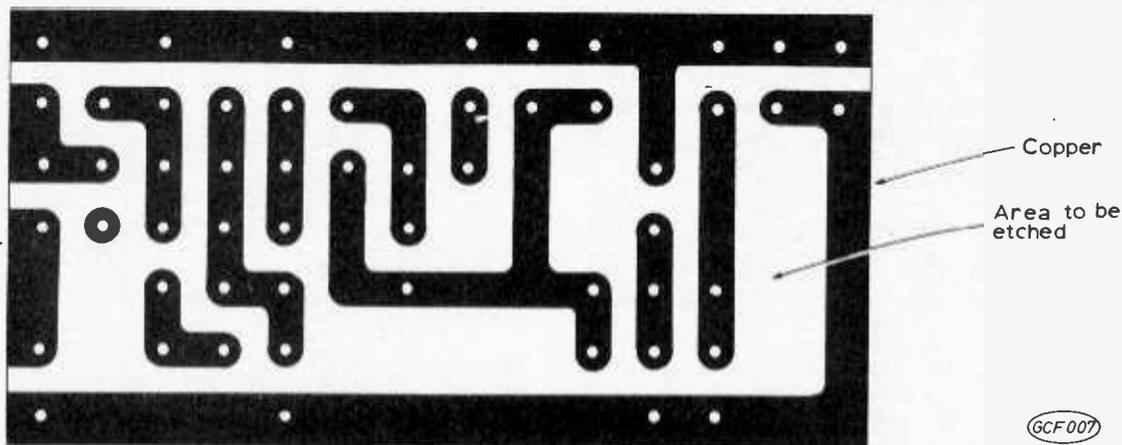


Fig. 3 When the layout is finalised it must be reversed on to the board as shown here, complete with the holes required, drilled after etching.

and a piece of carbon paper in between, carbon side down against the copper surface. Draw over the master with a pencil which will leave the outlines on the copper. Remove master and carbon paper after which the resist can be painted on the areas of copper which are to be retained. While the resist dries the etching solution can be prepared.

## ETCHING

Ferric chloride is used which can be bought from advertisers in this magazine. One pound will etch many boards. A suitable strength is about one tablespoon per fluid ounce of water. The crystals should be added to the water, not vice versa, and this should be done with care as a lot of heat is generated. The solution may attack skin if splashes are not rinsed off and it will stain cloth and wood, so work over newspaper. The solution must be used in a non-metal dish, a saucer is ideal, and after use it can be stored in an old bottle with a plastic top.

If the prepared board is carefully levered off the paper, the Sellotape can be used as a handle. The board is placed gently on the etching solution **copper side down**. Surface tension will support it and the insoluble etching product can sink to the bottom, no agitation being necessary. After five minutes or so

lift the board and see that all the copper shows pink. Greasy finger marks show brown and unetched. If all is well, allow the process to continue, taking roughly twenty minutes. When all the unwanted copper has gone the board should be thoroughly rinsed with water and then the resist can be removed. "Dalo" or nail varnish will come off with nail varnish remover (acetone) while paint will require white spirit or stripper. A final wash with soapy water will leave the board ready for drilling.

## DRILLING AND SOLDERING

Drilling should be done with as fine a drill as possible, for a hand drill this will be about  $\frac{1}{16}$  in. dia. The slow speed on an electric drill is suitable but only gentle pressure must be used or the board will crack. It will be helpful to mark all the holes with a sharp point (a centre punch will not do) first, then hold the board in front of a piece of wood, in a vice, and drill all the holes. Any burrs can be removed with a larger drill. The board is now ready for use.

The bond holding the copper to the board material is strong but too much applied heat may cause the copper to peel off. As usual, resistors and other passive components should be soldered before semiconductors, though connecting wires should be left until last. ■

# We promise you the world

## From 550 kHz to 30 MHz

Our SW-717 shortwave receiver is an excellent low cost introduction to short wave listening.


It gives you continuous tuning from 550 kHz to 30 MHz in four bands. To let you hear broadcasts from as far away as Asia and America. Together with many amateur transmissions.

But that's not all we promise.

Because being a Heathkit, the SW-717 comes to you in kit form. A complete kit with absolutely nothing left out. And the very clear instruction manual you get makes assembly superbly straightforward. And very enjoyable.

So besides the pleasure of listening to short wave radio, you'll also have the pleasure of building it yourself.

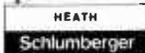Heath (Gloucester) Limited, Dept PW124,  
Bristol Road, Gloucester, GL2 6EE.  
Tel: (0452) 29451.



## From 190 kHz to 30 MHz



We make no bones about it. The GR-78 is one of the finest short wave receivers you can get.

Like the SW-717 it comes to you as a complete kit. The end result of which will be a superb receiver giving you short wave coverage of everything from 190 kHz to 30 MHz, in six bands.

It's also fully portable, with its own nickel-cadmium battery and built-in charger. For use anywhere in the world. And, at home, you can use it from the mains.

Post the coupon now for full details. Or, if you're in London or Gloucester, listen to the SW-717 and GR-78 for yourself. The London Heathkit Centre is at 233 Tottenham Court Road. The Gloucester showroom is next to our factory in Bristol Road. You'll soon realise that both models represent excellent value for money.

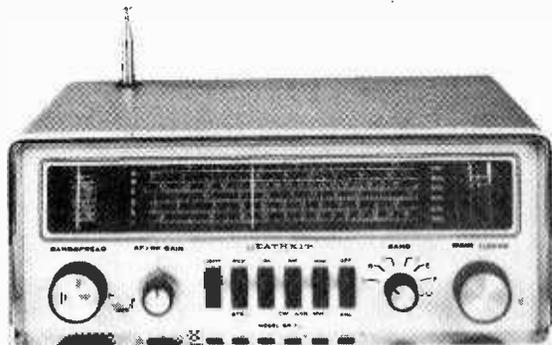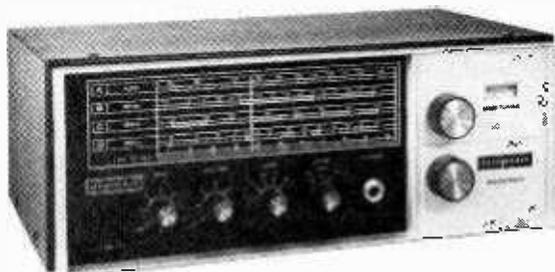So, to get the world, you won't have to pay the earth.



HEATHKIT



To: Heath (Gloucester) Limited, Dept PW124, Gloucester, GL2 6EE.

Please send me full technical data on:

the GR-78  the SW-717  together with a free Heathkit catalogue.

Name \_\_\_\_\_ Address \_\_\_\_\_

Postcode \_\_\_\_\_

Remember easy terms are available with the Heathkit Monthly Budget Plan.

# Trannies LTD.

4 BUSH HOUSE, HARLOW, ESSEX

Retail shop open  
9.30 to 5.30 Monday to Saturday  
Closed all day Wednesday

**ALL PRICES FULLY INCLUSIVE OF VAT**

## SEMICONDUCTORS

### TRANSISTORS—DIODES—RECTIFIERS—THYRISTORS—TRIACS—74 SERIES—IC'S—THERMISTORS

<b>Transistors</b>	BA145 24p	BCY30 58p	ME04075 24p	NKT713 34p	2N930 22p	<b>Ther-</b>	IN5407 28p	7437 77p	74154 22-0
AC107 7p	BA154 14p	BCY31 69p	ME0402 28p	NK7773 30p	2N1131 28p	<b>mistors</b>	IN5408 24p	7738 77p	74155 21-75
AC126 25p	BA156 18p	BCY70 17p	ME0492 28p	OA8(GH5001) 28p	2N1332 28p	VA10868 16p	400mW Zener	7440 20p	74156 21-75
AC127 18p	BAX16 8p	BCY71 27p	ME0493 21p	OA10 24p	2N1302 28p	VA10868 16p	Diodes	7441 81p	74157 21-75
AC128 18p	BC107 14p	BCY72 14p	ME1001 17p	OA47 9p	2N1303 30p	VA1085 15p	3-8v to 33v 12p	7442 81p	74160 22-75
AC141 28p	BC109 14p	BD124 1-30	ME1002 17p	OA90 9p	2N1304 38p	VA1087 15p		7443 81p	74161 22-75
AC141k 28p	BC113 18p	BD128 17p	ME1075 19p	OA91 9p	2N1305 38p	VA1089 14p	<b>Thyristors</b>	7444 81p	74162 22-75
AC142 28p	BC114 18p	BD131 M/P	ME1100 20p	OA92 9p	2N1306 47p	VA1090 14p	1 amp	7445 81p	74163 22-75
AC142k 28p	BC115 18p	BD132 41-18	ME1120 20p	OA95 6p	2N1307 47p	VA1091 14p	50v	7446 81p	74164 22-75
AC151 28p	BC117 28p	BDY20 25p	ME2001 15p	OG15 (HG1005 7p	2N1308 58p	VA1077 16p	100v	7447 81p	74165 22-75
AC152 28p	BC125 17p	BF167 25p	ME2002 16p	OA200 9p	2N1309 58p	VA1100 14p	200v	7448 81p	74166 22-75
AC153k M/P	BC126 17p	BF173 25p	ME3001 21p	OA202 9p	2N1310 58p		400v	7449 81p	74174 22-75
AC153k M/P	BC128 18p	BF177 27p	ME3002 28p	OA19 55p	2N1311 25p		3 amp	7450 81p	74175 22-75
AC176k 28p	BC137 19p	BF178 34p	ME4001 16p	OC25 45p	2N2218 48p		1 amp	7451 81p	74177 22-75
AC176k 28p	BC140 28p	BF179 34p	ME4002 17p	OC28 55p	2N2218a 48p		50v	7452 81p	74180 22-75
AC176 24p	BC147 18p	BF194 10p	ME4003 19p	OC29 58p	2N2219 48p		200v	7453 81p	74181 22-75
AC187 28p	BC148 11p	BF195 10p	ME4101 16p	OC35 58p	2N2219a 58p		400v	7454 81p	74182 22-75
AC187k 28p	BC149 18p	BF244 27p	ME4102 17p	OC41 20p	2N2484 48p		5 amp	7472 28p	74184 22-00
AC188 28p	BC157 17p	BF254 14p	ME4103 16p	OC44 20p	2N2646 51p		2 amp	7473 28p	74190 22-00
AC188k 28p	BC158 18p	BFX29 24p	ME4104 16p	OC45 20p	2N2904 24p		1 amp	7474 28p	74191 22-00
AC197 28p	BC159 18p	BFX34 24p	ME6001 18p	OC70 28p	2N2905a 28p		5 amp	7475 28p	74192 22-00
AC197k 28p	BC159 18p	BFX35 24p	ME6002 18p	OC71 15p	2N2904 24p		50v	7476 28p	74193 22-00
AC197k 28p	BC159 18p	BFX36 24p	ME6003 17p	OC72 18p	2N3053 28p		80v	7477 28p	74194 22-00
AC197k 28p	BC159 18p	BFX37 27p	ME6004 17p	OC73 24p	2N3055 48p		400v	7478 28p	74195 22-00
AC197k 28p	BC159 18p	BFX38 27p	ME6101 19p	OC75 24p	2N3702 18p		10 amp	7479 28p	74196 22-00
AC197k 28p	BC159 18p	BFX39 27p	ME6102 20p	OC81 28p	2N3702 18p		400v	7480 28p	74197 22-00
AC197k 28p	BC159 18p	BFX40 27p	ME6201 19p	OC82 28p	2N3703 11p		50v	7481 28p	74198 22-00
AD140 67p	BC178 24p	BFY61 19p	ME6602 21p	OC83 24p	2N3704 12p		100v	7482 28p	74199 22-00
AD142 67p	BC182 12p	BFY62 23p	ME6903 28p	OC84 28p	2N3705 12p		400v	7483 28p	74200 22-00
AD143 65p	BC183 11p	BFY64 30p	ME6904 18p	TIP29a 44p	2N3706 11p		100v	7484 28p	74201 22-00
AD149 65p	BC184 12p	BFY90 11-15	ME9002 18p	TIP30a 44p	2N3707 11p		400v	7485 28p	74202 22-00
AD161 46p	BC212 13p	BY100 17p	ME9003 16p	TIP31a 77p	2N3708 10p		50v	7486 28p	74203 22-00
AD162 44p	BC213 16p	BY127 17p	ME9021 19p	TIP32a 28p	2N3709 11p		100v	7487 28p	74204 22-00
AD161 M/P	BC214 16p	BFZ10 30p	ME9022 18p	TIP33a 11-12p	2N3710 11p		400v	7488 28p	74205 22-00
AD162 M/P	BC217 16p	BFZ11 30p	ME9023 18p	TIP34a 11-12p	2N3711 11p		50v	7489 28p	74206 22-00
AF114 80p	BC258 18p	BFZ12 30p	ME9112 28p	TIP35a 21-19p	2N3819 27p		100v	7490 28p	74207 22-00
AF115 80p	BC259 16p	BY213 28p	ME9813 49p	TIP36a 24-07p	2N3874 20p		400v	7491 28p	74208 22-00
AF116 80p	BC267 14p	C407 18p	NKT211 20p	TIP41a 88p	2N3928 28p		100v	7492 28p	74209 22-00
AF117 80p	BC268 18p	MA8001 30p	NKT212 20p	TIP42a 11-10p	2N3904 17p		400v	7493 28p	74210 22-00
AF124 28p	BC269 14p	MA8002 40p	NKT213 20p	TIP255a1-05p	2N3906 17p		100v	7494 28p	74211 22-00
AF128 28p	BC270 15p	MA8003 40p	NKT214 20p	TIP305a 85p	2N4038 57p		400v	7495 28p	74212 22-00
AF128 28p	BC271 24p	ME0401 28p	NKT215 20p	TIP305b 85p	2N4038 57p		100v	7496 28p	74213 22-00
AF127 28p	BC272 25p	ME0402 24p	NKT216 20p	TIP305c 85p	2N4038 57p		400v	7497 28p	74214 22-00
AF139 82p	BC297 24p	ME0403 24p	NKT217 20p	TIP305d 85p	2N4038 57p		100v	7498 28p	74215 22-00
AF239 82p	BC298 24p	ME0404 18p	NKT218 20p	TIP305e 85p	2N4038 57p		400v	7499 28p	74216 22-00
AF239 82p	BC299 24p	ME0404/1 18p	NKT219 20p	TIP305f 85p	2N4038 57p		100v	7500 28p	74217 22-00
AF279 75p	BC300 41p	ME0404/2 18p	NKT220 20p	TIP305g 85p	2N4038 57p		400v	7501 28p	74218 22-00
AS729 28p	BC301 40p	ME0411 28p	NKT404 72p	TIP305h 85p	2N4038 57p		100v	7502 28p	74219 22-00
AS729 28p	BC302 38p	ME0412 18p	NKT405 96p	TIP305i 85p	2N4038 57p		400v	7503 28p	74220 22-00
AS729 28p	BC303 38p	ME0413 18p	NKT406 96p	TIP305j 85p	2N4038 57p		100v	7504 28p	74221 22-00
AS729 28p	BC304 38p	ME0414 18p	NKT407 96p	TIP305k 85p	2N4038 57p		400v	7505 28p	74222 22-00
BA111 35p	BC441 35p	ME0462 28p	NKT615F 38p	TIP305l 85p	2N4038 57p		100v	7506 28p	74223 22-00
BA115 10p	BC461 35p	ME0463 28p	NKT674F 38p	TIP305m 85p	2N4038 57p		400v	7507 28p	74224 22-00
			NKT677 30p	2N706 15p	40635 68p				

**Resistors**

1 watt 5% carbon 3-9 ohms to 10 meg	1p
1 watt 5% carbon " " " "	1p
1 watt 2% m/o 10 ohms to 1 meg	41p
1 watt 5% carbon 5-8 ohms to 10 meg	8p
3 watt wirewound 1 ohm to 6K8 ohms	10p
5 watt wirewound " " " "	18p
10 watt wirewound " " " "	18p

**Volume Controls**

Potentiometers

Carbon track 1k to 2meg

Log or Linear

Single 141p

Dual Gang Stereo 42p

Single type with D.P. Switch 22p

**Mixature Presets**

Carbon Skeleton type

All values 100 ohms to 5 meg ohms

1 watt 8p each

25 watt 7p each

**Neons**

6mm neon indicators

Red or Amber 28p each

at 6v, 12v, 28v, 110v or 230 volt.

miniature neon lamps

240v or 110v 8p each

**Tantalum Bead**

Solid tantalum capacitors Tol ± 20%.

All values 20p each.

MF/voltage: 1/35, 22/35, 33/35, 47/35, 1/35, 2/35, 2-2/35, 4-7/35, 10/35, 10/16, 10/25, 22/16, 47/6, 100/3.

**Mullards Polyester Capacitors**

**CS90 SERIES**

250V P.C. mounting: 0-1µF, 0-015, 0-022 81p, 0-033, 0-047, 0-068 4p, 0-1 41p, 0-15, 0-22 51p, 0-33 7p, 0-47 91p, 0-68 11p, 1-µF 14p, 1-5µF 22p, 2-2µF 27p.

**CS96 SERIES**

400V: 0-001µF, 0-0015, 0-0022, 0-0033, 0-0047 3p, 0-0068, 0-01, 0-015, 0-022, 0-033 31p, 0-047, 0-068, 0-1 41p, 0-15 61p, 0-22 81p, 0-33 12p, 0-47 14p, 0-68 16p, 1-µF 14p, 1-5µF 22p, 2-2µF 27p.

**Veroboard**

24 x 31 28p	25p	Pin Insertion tool 68p	68p
24 x 5 21p	31p	Spot face cutter 57p	57p
31 x 31 21p	31p	Pkt 50	22p
31 x 5 35p	35p	Pin 50	22p
17 x 24 89p	74p		
17 x 31 41-33	41-18		
17 x 5 Plain	41-10		

**Electrolytic Capacitors**

<b>4 VOLT</b>	<b>10 VOLT</b>	<b>25 VOLT</b>	<b>40 VOLT</b>
47µF 61p	220µF 8p	47µF 61p	470µF 10p
100µF 61p	330µF 10p	100µF 8p	680µF 25p
200µF 61p	470µF 10p	150µF 8p	1000µF 25p
320µF 61p	1000µF 11p	220µF 10p	2200µF 44p
1000µF 13p	1500µF 20p	470µF 13p	
4700µF 29p	2200µF 24p	680µF 20p	
		1000µF 25p	
		2200µF 29p	
<b>6-3 VOLT</b>	<b>16 VOLT</b>	<b>50 VOLT</b>	<b>63 VOLT</b>
33µF 61p	15µF 61p	1000µF 25p	1µF 61p
150µF 61p	33µF 61p	2200µF 29p	2-2µF 61p
150µF 61p	150µF 61p	5000µF 85p	4-7µF 61p
470µF 11p	150µF 8p		6-8µF 61p
680µF 18p	220µF 9p		10µF 61p
1500µF 18p	680µF 17p		22µF 61p
2200µF 18p	1000µF 17p		68µF 10p
3300µF 28p	1500µF 25p		100µF 11p
	2000µF 45p		33µF 61p
			100µF 18p
			220µF 22p
			470µF 25p
			1000µF 44p

**Ceramics**

Miniature Ceramics 50V DC.

All values 1-8pF to 10,000pF 5p each.

- £1 BARGAIN PACKS**
- £1 10 Silicon npn power transistors (2N3055), tested/unmarked.
  - £1 30 Plastic FET's unmarked/untested. Similar to 2N3810.
  - £1 20 TO18 transistors npn 2 to 5A, untested/unmarked.
  - £1 20 TO18 transistors pnp like BC178, BC179, etc., untested/unmarked.
  - £1 20 Silicon 2N3055, unmarked/untested. TO220 case.
  - £1 10 General purpose, fully tested FET's.

**COMPLETE 100watt DISCO SYSTEM £194.95 inc. V.A.T.**



- Complete System includes:
- ★ DJ DISCO Amp a real 100 watt RMS full mixing and PFL facilities.
  - ★ Trannies DISCO console with two Garrard SP25 Mk IV or McDonald M60 turntables fitted with diamond high compliances cartridges.
  - ★ Pair robust 50watt speakers.
  - ★ Stereo headphones and microphone.
  - Complete System £189.95 Carriage £4.00.
  - ★ NO DEPOSIT terms available £10-63 monthly over two years.
- We stock a full range of Disco Equipment. Send for list or pay us a visit at Bush fair.

# ADD-ON Beat Frequency Oscillator


F.G.RAYER G3OGR

THIS receiver accessory allows the reception of CW (Morse) and SSB (single sideband) signals particularly with receivers whose coverage includes any of the amateur bands. These bands are given below for the guidance of listeners who have not so far paid much attention to them.

160 metres	or	1.8 to 2.0MHz
80 metres	or	3.5 to 3.8MHz
40 metres	or	7.0 to 7.1MHz
20 metres	or	14.0 to 14.35MHz
15 metres	or	21.0 to 21.45MHz
10 metres	or	28.0 to 29.7MHz

Short wave broadcasts use AM (amplitude modulation) and an envelope detector in the receiver demodulates this but this detector cannot provide the wanted audio output with CW or SSB signals. CW will be heard as an intermittent clicking and SSB as an unintelligible sound varying at syllabic rate. To receive CW a signal from the beat frequency oscillator is combined with the carrier, provided by the CW transmission, the difference in frequency between BFO and CW signals providing an audio output after detection. As a superhet receiver converts all incoming signals to a frequency of, usually, about 470kHz (the intermediate frequency) the BFO is adjustable around this frequency. So if the BFO is set to 469kHz or 471kHz the CW is heard as a kHz audio tone.

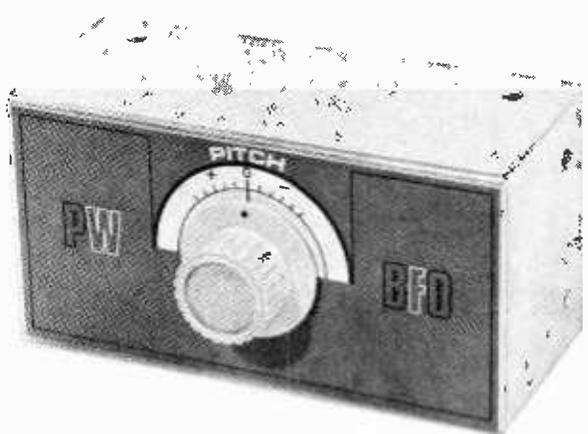With SSB the carrier and one sideband are suppressed before transmission. When the BFO is adjusted to occupy the position of the missing carrier the transmission can be resolved and the detector provides intelligible speech.



## BFO CIRCUIT

This is shown in Fig. 1. The frequency is determined by the coil L1, with fine manual adjustment by the variable capacitor VC1. The coil is suitable for receivers with an intermediate frequency of about 455kHz to 470kHz but the actual frequency need not be known. Windings must be in the phase shown, to secure oscillation.

It is quite a good plan to operate the BFO from its own 9V battery, the zener voltage regulator is not then necessary as satisfactory results can be obtained without it. But if current is taken from the battery running the receiver the current drawn by the receiver will vary considerably, especially at high volume level, so that stable operation of the BFO is impossible. In these circumstances, the zener is required for satisfactory reception.

## ASSEMBLY

The components are assembled on a small piece of perforated board, Fig. 2, with wiring underneath. The two points MC are 1/2in. 6BA bolts, with tags, providing the chassis or negative return.

A piece of aluminium about 3x1 3/4in is bent at right-angles about 1 3/4in from one end. The pitch capacitor VC1 is fitted to the smaller flange. The other flange is drilled for the two 6BA bolts mentioned, so that the wired board can be locked in place, with leads and joints clear of the metal. Connect the variable capacitor fixed plates to pin 3 on L1, and the moving plates to one MC tag, Fig. 2.

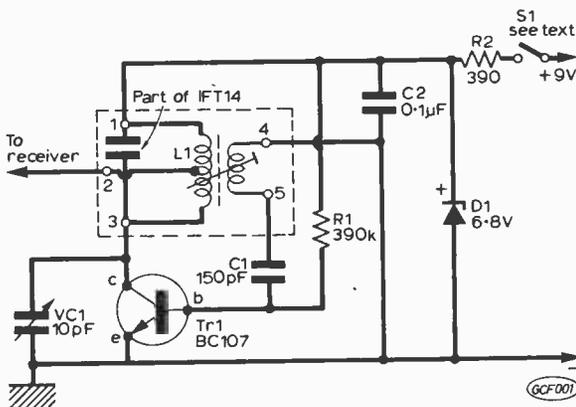


Fig. 1: Circuit of the simple beat frequency oscillator.

## ★ components list

R1	390kΩ	VC1	10pF (Jackson C804)
R2	390Ω	Tr1	BC107
C1	150pF	L1	Denco IFT14
C2	0.1μF	D1	Zener diode 6.8V

Perforated board, about 1½ x 3in. Knob. Metal case, see text. On/off switch, see text.

## TESTING THE BFO


Set VC1 half open. Tune in any AM signal on the receiver. Place an **insulated** lead from pin 2 of L1 near the IF circuitry of the receiver. Connect the BFO to the 9V supply to be used. Rotating the core of L1 with a trimming tool should result in a setting being found where an audio tone arises. Set the core to the central or zero-beat position. If the core is rotated either way from this position an audio tone will be produced, rising in pitch as the core is turned.

Rotating VC1 should now give a similar result. That is, a rising audio tone as the capacitor is rotated either way from the central or zero-beat position.

The BFO is not used for AM reception and slight re-setting of the core may be necessary after the unit is fitted in its case, if it is found that VC1 comes at the fully open or fully closed position.
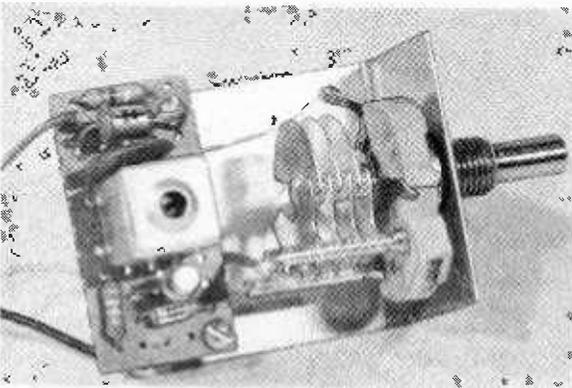
## BFO LOCATION

The BFO unit is only about 2¼x1¾x1½in so it may be fitted in almost any receiver, especially home-constructed types. A reasonably large control knob is best on VC1 and an on-off switch is necessary in the battery positive lead to the unit.



The unit itself is very small indeed so it can be fitted into a convenient corner in any receiver requiring a BFO.

It may be preferred to have the BFO as an external unit, with its own battery, when it can then be used with any receiver. To avoid troublesome hand-capacity effects, the unit must be in a metal box. A box about 6x3x2½in with a backplate fixed with self-tapping screws will be suitable. This will also take a 9V battery and switch.

## COUPLING TO RECEIVER

A short insulated lead from pin 2 of L1, placed near the receiver or near the receiver IF stages, should normally give suitable coupling which is not too critical. Much looser coupling to the earlier IF

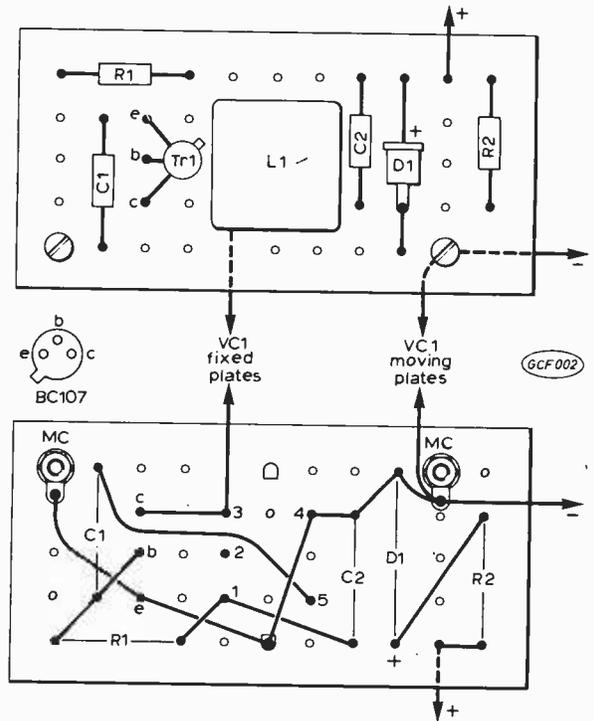


Fig. 2: Layout of components on top of the Veroboard and wiring beneath.

circuits will be required than to those at the diode end of the IF amplifier.

If coupling is too close, receiver sensitivity will fall off considerably when the BFO is switched on. Should coupling be too weak, strong SSB or CW signals will be difficult to resolve, while weak SSB or CW will be resolved easily. However, it should be an easy matter to move the lead from the BFO, or to cut it down, until results are satisfactory.

## RECEIVING CW and SSB

Morse signals should be found easily in the amateur and other bands and VC1 is simply rotated to produce a suitable audio tone. In some cases rotating VC1 one side of the zero position may be found to give better reception than the other side.

To receive SSB, first tune in an amateur SSB signal, probably on 80m, with the BFO off. Switch the BFO on and rotate VC1 slowly until intelligible speech is produced. This requires quite careful adjustment. If the signal cannot be resolved, turn VC1 the other side of the zero position. This alternative position will in any case be necessary on the HF bands, where the upper sideband is usually employed compared to the lower sideband transmitted on the LF bands.

If the receiver is fitted with RF and audio gain controls, the audio gain should be near maximum and the RF control advanced as necessary, for best results on SSB.

VC1 need not be 10pF but larger values give more critical adjustment while smaller values may not give enough range of adjustment. Where the receiver has a fine tuning control this can be used for tuning SSB or CW signals, but if the receiver tuning does not allow very critical adjustment, VC1 can be used for this purpose, after locating the wanted signals.


# SAXON

Money saving high performance audio equipment  
DIRECT FROM OUR OWN FACTORIES

## GUARANTEED TESTED HIGH PERFORMANCE MODULES—now better value than ever

<b>SA35</b> 35W RMS 25-50V 7 transistors, 7 diodes	<b>£5-45</b>	Carriage free	★ 25Hz-25kHz ★ 0.2% distortion ★ Nalae—80dB ★ 500mV into 20K $\Omega$
<b>SA50</b> 50W RMS 25-55V 7 transistors, 7 diodes	<b>£6-90</b>	Carriage free	★ 4-16 ohms ★ Simple wiring ★ Short and open circuit proof
<b>SA100</b> 100W RMS 45-70V 10 transistors, 7 diodes	<b>£12-50</b>	Carriage free	★ Continuously rated ★ Top-grade components

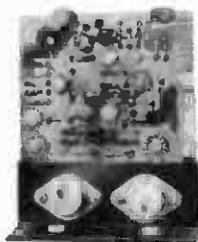120 watt module complete with built-in supply—extra heavy duty **£22-50**  
Carr. 60p



THE SA100 MODULE

## POWER SUPPLIES

### UNSTABILISED—READY WIRED

<b>PU45</b>	Suits 2 SA35 or 1 SA50 (4 ohm)	<b>£5-45</b>	Carriage 30p
<b>PU70</b>	Suits 2 SA50 (8 ohm) or 2 SA100	<b>£8-45</b>	Carriage 40p

### STABILISED

<b>PS45</b>	Suits 2 SA35 or 2 SA50 (4 ohm)	<b>£4-45</b>	Carriage free
<b>MT45</b>	Transformer for above	<b>£3-50</b>	Carriage 30p
<b>PS70</b>	Suits 2 SA100	<b>£5-45</b>	Carriage free
<b>MT70</b>	Transformer for above	<b>£4-90</b>	Carriage 40p

N.B. PS70 is not suitable for the SA50

## Mk II STEREO DISCO MIXER £22-50

This well tried unit mixes two decks, handles any ceramic cartridge, and features mic over-ride plus separate full range bass and treble controls on both mic and deck inputs. Ample headphones power is available for P.F.L. May be used for mono and is mains operated. Fitted with sturdy screening case. Controls: Mic vol, base, treble. Left/Right fade, deck volume, base, treble, h/phone select, vol. Mains. Size 17 $\frac{1}{2}$ in X 2in X 4in deep.



## DISCO MODULE £9-50

Thousands sold of this extremely popular mono version. A mic input may be fitted using the VA30 (see below). Low consumption from a 9V battery. Features the same high standards of reproduction as the Stereo version. Controls: H/phone select, vol. Left deck vol, Right deck vol, bass, treble, master vol. Size 12 $\frac{1}{2}$ in X 3in X 2in deep.



## 3-CHANNEL SOUND-LITE £22-50

Only SAXON can supply such incredible value for money. This unit features 3kW power handling, full-wave control, bass, middle, treble AND master controls. Twin loudspeaker jacks for "through" connections. It may be used free standing or will panel mount next to either of the above. Also features unique CUT-BACK Circuitry for extra wide range response. Size 12in X 3in X 2in deep. Professional standards at a price you can afford!



## SINGLE CHANNEL VERSION £7-50

Recently reduced in price due to increasing sales, handles 1kW. Full wave operation.


ADD 8% VAT TO ALL ORDERS

## MULTI-PURPOSE MIXERS

**M4HL** Carr. 50p **M6HL** Carr. 50p  
**£19-50** **£29-50**  
Featuring multiples of our VA30 module, the M4HL and M6HL fulfil the requirements of all clubs, groups, etc. where a high quality mixer is required. Each channel has one high and one low impedance input, plus volume, treble and bass controls. Input impedances may, if required, be easily changed. The M4HL has four channels, and one output, and the M6HL six channels (12 inputs) and a master control and two outputs. Either unit may be used free standing or panel mounted. These mixers will feed all types of amplifier. Recommended for their versatility and high performance, and excellent value for money.
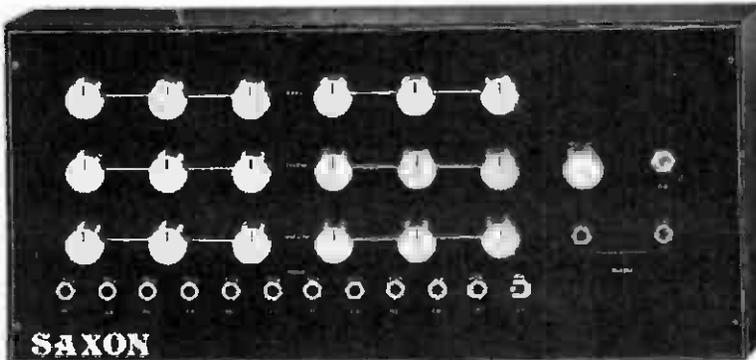
## VA30 CHANNEL MODULE £3-50


This is the basic channel module in the above mixers and may also be used for extra inputs on either the mono or stereo mixers. Fitted with volume, bass and treble controls, requires just a jack and supply (9-100V)



## SAXON CSE 100

COMPLETE AMPLIFIER  
**£34-90**  
Carr. free

100W of speech and music—Two separately controlled inputs. Wide range bass and treble controls. Sturdy and attractive vinyl case. Twin outputs. Ideal for groups, discos, etc. Fully tested and guaranteed. 50W version identical in appearance.

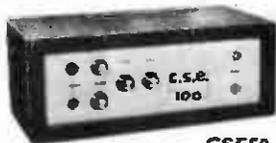

**CSE50**  
**£29-50** Carr. free



sockets. Sturdy case, and an attractive fascia make this excellent value for money. Hundreds in use by groups, discos, clubs, etc. 50W version identical in appearance.

Four individually controlled FET input stages plus wide range bass and treble controls. 120W of speech and music output. 120m twin loudspeaker

**SAXON 100**  
COMPLETE AMPLIFIER  
**£53-00**  
Carr. free

**SAXON 50**  
**£37-50**  
Carr. free

## CALLERS AND MAIL ORDER

## SAXON ENTERTAINMENTS LIMITED

327-333 WHITEHORSE ROAD · CROYDON CR0 2HS

(Please quote magazine when ordering)

SHOP HOURS: 9 a.m.—5 p.m. — LUNCH 12.30-1.30 p.m. MAIL ORDER DESK: 10 a.m.—3 p.m.  
24-HOUR ANSWER SERVICE. TEL. 01-684 6385. TECHNICAL ENQUIRIES: 01-684 0098.

SEND 10p FOR OUR 26 PAGE MANUAL—full circuits & details.

TERMS OF BUSINESS: C.W.O. C.O.D. or ACCESS (just send in card number). Send 50p for C.O.D.

Please send S.A.E. with all enquiries.

VAT @ 8% must be added to all orders including carr. charges.



### "I MADE IT MYSELF"

Imagine the thrill you'll feel! Imagine how impressed people will be when they're hearing a programme on a modern radio you made yourself.

## Now! Learn the secrets of radio and electronics by building your own modern transistor radio!

Practical lessons teach you sooner than you would dream possible.

What a wonderful way to learn—and pave the way to a new, better-paid career! No dreary ploughing through page after page of dull facts and figures. With this fascinating Technatron Course, you learn by building!

You build a modern Transistor Radio . . . a Burglar Alarm. You learn Radio and Electronics by doing actual projects you enjoy—making things with your own hands that you'll be proud to own! No wonder it's so fast and easy to learn this way. Because learning becomes a hobby! And what a profitable hobby. Because opportunities in the field of Radio and Electronics are growing faster than they can find people to fill the jobs!

**No soldering—yet you learn faster than you ever dreamed possible.**

Yes! Faster than you can imagine, you pick up the technical know-how you need. Specially prepared step-by-step lessons show you how to: read circuits—assemble components—build things—experiment. You enjoy every minute of it!

You set everything you need. Tools. Components. Even a versatile Multimeter that we teach you how to use. All included in the course. **AT NO EXTRA CHARGE!** And this is a course anyone can afford. (You can even pay for it by easy instalments).

So fast, so easy, this personalised course will teach you even if you don't know a thing today!

No matter how little you know now, no matter what your background or education, we'll teach you. Step by step, in simple, easy-to-understand language. You pick up the secrets of radio and electronics.

You become a man who makes things, not just another of the millions, who don't understand. And you could pave the way to a great new career, to add in the thrill and pride you receive when you look at what you have achieved. Within weeks you could hold in your hand your own transistor radio. And after the course you can go on to acquire highly-powered technical qualifications, because our famous courses go right up to City & Guilds levels.

**Send now for FREE 76 page book—see how easy it is—read what others say!**

Find out more now! This is the gateway to a thrilling new career, or a wonderful hobby you'll enjoy for years. Send the coupon now. There's no obligation.

**POST TODAY FOR FREE BOOK**

To: ALDERMASTON COLLEGE  
DEPT. BPW 85  
READING RG7 4PF

QH BPWBS

Yes, I'd like to know more about your course. Please send me free details—plus your big, 76-page book that tells about all your courses.

NAME

ADDRESS



BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY

# wireless?

The early days of electronics were based very largely around the topic of radio. Things like computers and calculators are very much an afterthought. AMBIT is instigating a specialist sales and service line, just for AC electricity. From 10Hz to 1000 MHz. With our association with the largest producer of coils and filters in the world, namely TOKO, we think we have got a head start. Add to this our declared commitment to linear monolithic technology, and the result is the most advanced and comprehensive service available to the amateur or industry.

In our AC line information folder, you will find the CA3090A PLL decoder, with TOKO coils and pilot tone filter, PCB and other bits for just £3.90 +VAT.

The CA3123E AM radio module, the CA3089E FM radio module, the TB810AS short circuit proof 7W audio amp module. DATA FOLDA is 25p inc pp., and contains information for all concerned with audio and wireless - GET YOURS NOW....

**ambit INTERNATIONAL**  
37a HIGH STREET  
BRENTWOOD  
ESSEX CM14 4RH  
(0277) 216029  
Telex: 995194



### for fast, easy reliable soldering

Erskin Multicore Solder contains 5 cores of non corrosive flux, instantly cleaning heavily oxidised surfaces. No extra flux is required.

### EASY-TO-USE DISPENSERS



Size 5  
Savbit alloy  
18 swg, 32p (illustrated).  
Size 19A  
60/40 alloy  
18 swg, 34p  
Size 15  
60/40 alloy  
22 swg, 36p

### IDEAL FOR HOME CONSTRUCTORS


Size 1 cartons in 40/60, 60/40 and Savbit alloys in 7 gauges 56p



Size 12 Reel for Service Engineers and Electricians.  
18 swg  
Savbit alloy £1.72




### BIB WIRE STRIPPER AND CUTTER

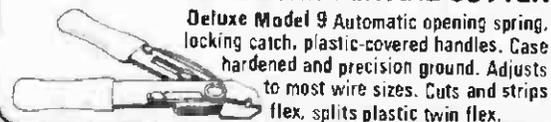

Deluxe Model 9 Automatic opening spring, locking catch, plastic-covered handles. Case hardened and precision ground. Adjusts to most wire sizes. Cuts and strips flex, splits plastic twin flex.

Prices shown are recommended retail excluding V.A.T. From Electrical and Hardware Shops. If unobtainable send 10p p&u direct to Bib Hi-Fi Accessories Limited, Hemel Hempstead, Herts HP2 7EP

# ANOTHER BATTERY SAVER!

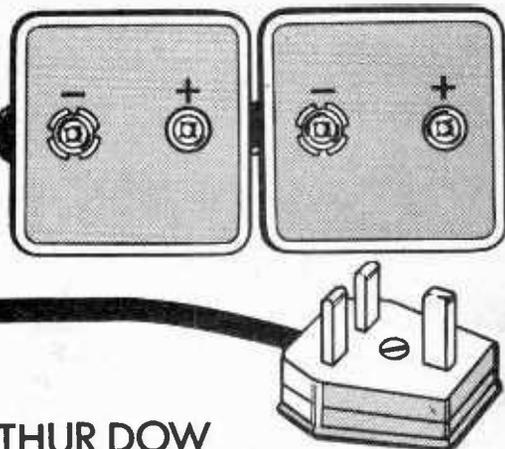

ARTHUR DOW

AS we go through the Age of Apollo with everything rocketing upwards the prices of dry batteries are no exception. The common PP7 9 volt battery, for example, costs around 33p at the moment and many transistor radios use two of these. Their useful life in a radio is very variable but one factor, above all else, determines how economical they are likely to be in the long run: the sensible use of the volume control.

Just about all transistor radios use output stages designed to operate in what is known as "Class B" conditions, where the current consumption is very low with no signal, rising as the signal input is increased so that low volume levels mean low battery consumption and longer battery life.

At 66p for a pair of PP7s it is immediately obvious that a mains operated power supply unit is going to pay for itself very quickly indeed, after which the cost of the electricity to operate the set is negligible. Taking a month as a typical life span for the batteries the cost of this power supply unit at under £3 could be written off in about four months. For our Senior Citizens and others similarly placed this is no mean saving.

## Design

While power units for radios requiring 6 or 9 volts are common enough, units to replace 2 × PP7 batteries (18 volts) seem hard to come by. In the author's case, an Ultra 6142 LW, MW and VHF

portable, it seemed logical to make up a power supply unit to fit in the same space as the batteries, so what better than to use the tin cases from a pair of defunct PP7s?

In the final circuit used, Fig. 1, one tin box carries the mains transformer T1, the 12 + 12 volts secondary windings going to the rectifier diodes D1 and D2, smoothing capacitors C1 and C2 and the zener diodes which stabilise the output voltage at 9.1 + 9.1 volts, all contained in the second box. The tops of the boxes carrying the terminals are retained and accept the original battery clips so that no alterations whatsoever need to be made to the radio set itself, a very important consideration. At any time the power unit can be slipped out of the set and normal batteries fitted back in a few seconds. In any other set a check ought to be made to with a voltmeter to ensure that the two batteries are, in fact, in series, requiring 18 volts. Otherwise, as long as the original battery polarities are adhered to, there should be universal use for this type of power unit.

## Construction

Initially, two old PP7 type batteries are dealt with as follows: Mark the tops with the + and - signs, as shown on the side of the case, against the respective terminals. Cut across the corners at the top with a pair of sidecutters and ease back the edges until the top can be lifted out complete with battery. Cut the connecting wires or thin metal strips fairly close to the terminals and throw out the battery.

A hole of about  $\frac{1}{8}$  in diameter is made in corresponding positions in each case and the two cases held together with a rubber grommet, Fig. 2, noting the polarity markings on the cases. Another hole is made for the mains lead to enter, again via a grommet. The position of this hole will be dictated by the position of the batteries in the set. In the Ultra 6142 a slot was filed at the bottom of one side of the cabinet, adjacent to the battery compartment, from which the mains lead was led out.

Next, all the components, with the exception of the transformer, are soldered on to the small piece of veroboard, Fig. 3, and lead-out wires attached. Some sort of colour coding for the wires is an advantage to avoid wiring errors. The board is

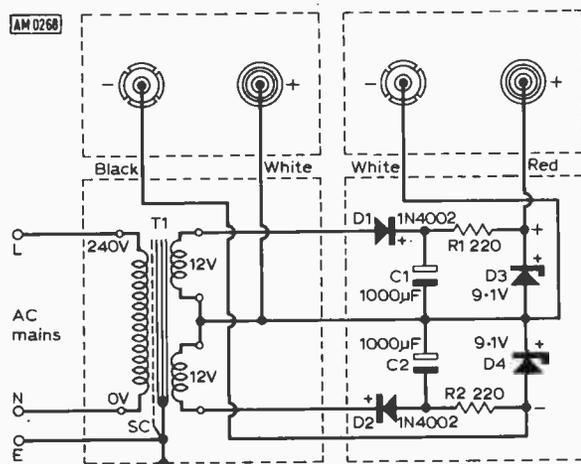


Fig. 1: Circuit of the power unit together with the connections to the terminals of the retained battery tops.

fitted across the diagonal of one box and a couple of spots of adhesive will hold it in place. Be particularly careful that the polarity of the four diodes and the smoothing capacitors is carefully observed. The wires from the board are passed through the grommet with the exception of the one white and one red wire which are soldered to the + and - terminals on one of the battery tops.

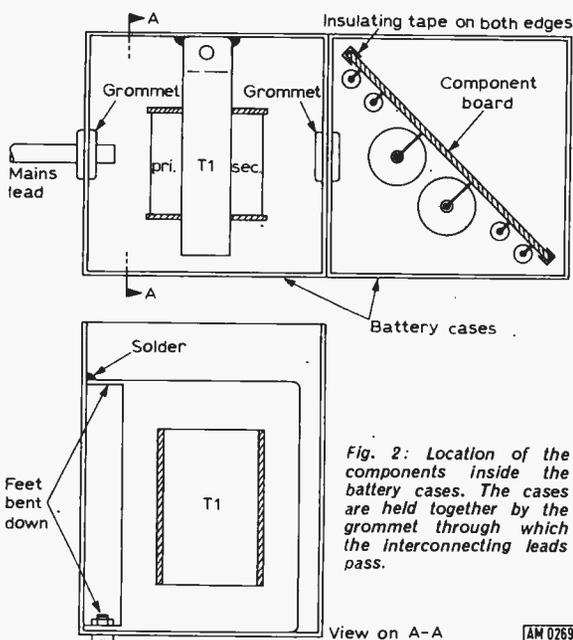


Fig. 2: Location of the components inside the battery cases. The cases are held together by the grommet through which the interconnecting leads pass.

The mains transformer has two mounting feet which must be bent down, Fig. 2, one being fixed to the bottom of the box with a 6BA nut and bolt and the other soldered to the box just below the top. But, before fixing the transformer finally, feed a few inches of the mains lead through the grommet and connect to the primary winding taking the earth lead to the transformer's "screen" connection and to the case. Put a few turns of narrow insulation tape on the end of the mains lead inside the box to prevent the lead being pulled out. This may not be the best arrangement but space is rather limited inside the box. The wires from the board may now be connected to the transformer secondary with a white wire and a black wire going to the terminals on the second battery top, again noting the correct polarity. The transformer may now be dropped into the case and finally fixed into position. Some insulation tape was stuck across the core of the transformer at the top to prevent any possibility of a short circuit of the terminals immediately above. Likewise some tape was put across the top edge of the board in the other box.

## Testing

Before replacing the tops in the cases it is a good idea to try out the power unit for correct operation. After checking the wiring again and the polarity of the various components connect a DC voltmeter across the red and black terminals. Select a voltmeter range of, say, 50 volts initially. Switch on the mains, when a reading of about 18 volts should be

## ★ components list

R1/2 220Ω 5% ½ watt  
 C1/2 1000μF 25V  
 D1/2 1N4002  
 D3/4 9-1V zener  
 (BZY88C9V1)  
 T1 Transformer 240V/12V 12V  
 (Douglas MT111CS)

Veroboard. Grommets. Battery cases. Mains lead.

obtained, with 9 volts between the white wires and either black or red.

If everything appears correct put some insulating tape over the connections to the terminals and put the tops back into the cases finally turning over the edges of the cases to hold the tops in position. If thought necessary, the unit can be checked on the radio itself before fitting the tops back, connecting the battery leads from the set on to the power unit terminals. If there is something wrong it can be attended to now instead of having to open up the cases again. As a further check, the voltage across each of the smoothing capacitors should be about 16 volts.

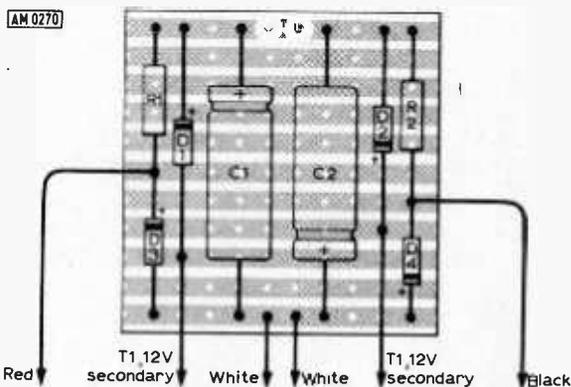


Fig. 3: Layout of components on small piece of Veroboard. Protect vertical edges and top with insulating tape or similar.

## Notes

It should be remembered that the on/off switch on the radio set itself still only controls the DC output of the power unit to the set and not the mains input. Although the set consumes very little power from the mains it is still good practice to switch off the mains side when the set is not being used. The set switch can be left on permanently and operation of the set controlled by a switch at the mains outlet point.

The miniature mains transformer specified has a secondary current rating of 250mA which is far in excess of the 20/30mA which will be drawn by the average set. However, since it costs only a matter of a few pence more than the sub-miniature transformers rated at around 30/50mA the additional safety factor was thought to be well worth while. The light loading of the transformer will also assist the output voltage regulation of the unit. ■

# If you're looking for trouble you needn't look any further.



It's not only technicians who can see the finer points of Eagle multi-meters.

Every handyman notices them too.

They're easy to read.

They're tough.

Their construction comes up to laboratory standards.

Even our inexpensive pocket sized models have features you'd usually only find on professional equipment.

Take a look through our catalogue.

You'll see over twenty models.

Specifications that would impress the most experienced technician.

And a price range that takes in amateurs as well as professionals.

We guarantee every one for two years.

With parts to service them in no time.

So you can confidently find fault in anything.

**Eagle**  
International

The name on Britain's widest range of electronic equipment.

Please send me the Eagle electronics catalogue containing the complete range of test equipment.

Name

Address

PW 3


Eagle International Precision Centre Heather Park Drive  
Wembley HA0 4SU Telephone 01-903 0144

**G. F. MILWARD, 369 Alum Rock Road, Birmingham B8 3DR.**  
Tel. 021-327 2339

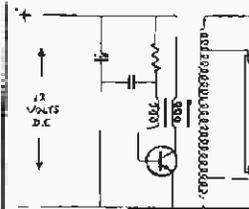**12 VOLT FLUORESCENT LIGHTING**



- INVERTER TRANSFORMERS 13/15 WATT (CIRCUIT INCLUDED) **70p**
- "CURRENT ECONOMY" TRANSISTOR (600 ma.) **50p**
- "MAXIMUM LIGHT" TRANSISTOR (1.3A) **50p**
- RESISTORS/CAPACITORS TO SUIT **15p**
- LAMP HOLDERS (LONG LEAD) **30p PAIR**
- (SHORT LEAD) **20p PAIR**
- WHITE ENAMEL CASE, 18" or 21" (Postage 30p) **70p**
- TUBE, 18"-15 WATT or 21"-13 WATT **45p**
- (NOTE:- TUBE ONLY SUPPLIED IF CASE ORDERED, TO PREVENT POSTAL DAMAGE)
- 13 WATT FITTING READY BUILT AND TESTED—INCLUDING TUBE (Postage 30p) **£3.75**
- Post/Packing 25p per order except where shown



**NEW IMPROVED CIRCUIT!**

Drives 21" 13 watt  
18" 15 watt  
or adaptable for  
2 x 12" 8 watt

**SMALL ELECTROLYTICS**

Ref. No.	Capacity	Voltage	Price
H8/3	2µF	50V	4p
H8/2A	4µF	50V	4p
H8/5	5µF	10V	4p
H8/8A	10µF	10V	4p
H8/8A	10µF	18V	4p
H8/9A	20µF	70V	4p
H8/10	22µF	50V	4p
H8/11	25µF	12V	4p
H8/12A	30µF	10V	4p
H8/13A	32µF	50V	4p
H8/14	40µF	25V	5p
H8/14A	40µF	16V	4p
H8/15A	40µF	35V	4p
H7/1A	50µF	10V	4p
H7/2A	64µF	2.5V	2p
H7/4	84µF	15V	4p
H7/9A	125µF	4V	4p
H7/10A	180µF	2.5V	2p
H7/11	100µF	25V	4p
H7/11A	150µF	16V	5p
H7/14	220µF	50V	14p
H7/14A	220µF	18V	6p
H7/15	220µF	25V	4p
H7/15A	220µF	35V	10p
H8/1A	250µF	4V	3p
H8/3A	320µF	2.5V	3p
H8/4	320µF	10V	4p
H8/5	330µF	25V	10p
H8/5A	330µF	35V	15p
H8/6A	470µF	35V	20p

POSTAGE 25p PER ORDER

**£1** 100 1/2 WATT RESISTORS  
100 CERAMIC CAPACITORS  
100 DIODES  
POSTAGE 25p

**£1** 1 VERO-BOARD CUTTER  
2 1/2 In. x 1 In. x 15 BOARDS  
30 SO. INS. "ODD PIECES"  
VERO  
POSTAGE 25p

**£1** 25 ASSORTED UNUSED  
MARKED, TESTED  
TRANSISTORS  
BC100 ETC.  
POSTAGE 25p

**£1** 8 COMPUTER PANELS  
CONTAINING MASSES OF  
DIODES, TRANSISTORS,  
INDUCTORS, RESISTORS &  
CAPACITORS  
POSTAGE 25p

**£1** 100 RESISTORS  
100 CERAMIC CAPACITORS  
100 POLYSTYRENE CAPACITORS  
POSTAGE 25p

**£1** 100 RESISTORS  
100 CERAMIC CAPACITORS  
100 MULLARD POLYESTER CAPACITORS  
POSTAGE 25p

**£1** 1 TRANSISTORISED  
SIGNAL TRACER KIT  
1 TRANSISTORISED  
SIGNAL INJECTOR KIT  
POSTAGE 25p

**£1** 100 RESISTORS  
100 CAPACITORS  
(ASSORTED TYPES)  
POSTAGE 25p

**NOTE:- ALL GOODS PLUS 8% VAT (EXCEPT OVERSEAS)**

**DISCOUNTS UP TO 60%**

- FANTASTIC OFFER**
- T-transcriber Saturn With Vestibul Arm ... **£63 95**
  - AMPLIFIERS**  
Please add £1.95 for p & p & Ins.  
Amstrad Integra 4000 MkII ... **£235.75**  
Amstrad IC2000 MkII ... **£31.95**  
Amstrad 8000 MkIII ... **£18.50**  
Eagle AA2 ... **£31.90**  
Eagle AA4 ... **£43.10**  
Metro-Sound ST20E MkII ... **£26.45**  
Metro-Sound ST40 ... **£23.35**  
Metro-Sound ST80 ... **£24.75**  
Sansul AU191 ... **P.O.A.**  
Sinclair 2000 ... **£28.95**  
Sinclair 4000 ... **£44.95**  
Teleton SA202 ... **£34.50**  
Teleton SAQ206B ... **£23.95**  
Teleton SAQ307D ... **£27.20**
  - COMBINATION UNITS**  
Please add £1.10 for p & p & Ins.  
Goodmans Compact80 (Teak) **£135.15**  
Goodmans Compact90 ... **£169.90**  
Goodmans Compact 1-10 ... **£191.00** (Teak)
  - TUNERS**  
Please add £1.05 for p & p & Ins.  
Amstrad MLX3000 ... **£26.25**  
Eagle AAB ... **£26.95**  
Eagle TST 152 ... **£32.95**  
Metro-Sound FMS 20 MkII ... **£33.35**  
Teleton T300 ... **P.O.A.**
- GARRARD SP25 MkIV**  
Pliinth & Cover  
Garrard SP25 MkIV deck, Goldring G600 Cartridge, Teak finished Pliinth/Cover (Non Hinged) All Leads  
GLOBALS PRICE £19.95  
Cart. & Ins. £1.83
- TURNABLES**  
Please add £1.05 for p & p & Ins.  
Garrard SP25 Mk IV Chassis **£12.95**  
Garrard 865B P/C Cart (Mod.) **£47.50**  
Garrard 865B Chassis ... **£22.40**  
Garrard 401 Chassis **£32.00**  
Goldring 101 MkII P/C G800 **£29.95**  
Goldring GL75 P/C G800 ... **£29.95**  
Goldring GL75 P/C G600 ... **£24.40**  
Goldring GL65 P/C ... **£23.50**  
Pioneer PL 12D ... **P.O.A.**  
Sansul SR 212 ... **P.O.A.**  
Thorens TD185 MkII ... **£72.25**  
Thorens TD185A MkII ... **£191.95**  
Thorens TD180 ABC ... **£59.95**  
Thorens TD185 ABC ... **£52.95**

- Teleton ST202 ... **£38.40**
- Sinclair 2000 Mk III ... **£23.95**
- Sinclair 4000 ... **£27.45**
- TUNER/AMPLIFIERS**  
Please add £1.21 for p & p & Ins.  
Amstrad 5000 ... **£50.95**  
Goodmans Module 80 ... **£72.50**  
Goodmans Module 90 ... **£92.90**  
Goodmans 1-10 Module ... **£108.50**
- SPEAKERS**  
Add £1.82 for p & p & Ins per Pair.  
Amstrad 1500 ... **£25.85**  
Amstrad 2500 ... **£29.75**  
Caeleion County ... **£45.25**  
Caeleion Dilton 10 MkII ... **£42.65**  
Caeleion Dilton 15 ... **£45.50**  
Caeleion Dilton 25 ... **£129.25**  
Caeleion Dilton 44 ... **£180.95**  
Caeleion Dilton 66 ... **£180.95**  
Caeleion Hadleigh ... **£180.95**  
Goodmans Dimension 8 ... **£127.95**  
Goodmans Hovant SL ... **£64.50**  
Goodmans Magleters ... **£107.75**  
Goodmans Magnum K2 SL ... **£84.85**  
Goodmans Ministar ... **£38.00**  
Goodmans Mezo 35L ... **£84.80**  
Marsden Hall 110F/C ... **£21.95**  
Marsden Hall 150F/C ... **£30.45**  
Marsden Hall 300F/C ... **£75.75**  
Wharfedale Denton 2 ... **£29.75**  
Wharfedale Ovedale ... **£77.80**  
Wharfedale Glendale ... **£52.65**
- CARTRIDGES**  
Please add 12p for p & p & Ins.  
Goldring G800 ... **£3.95**  
Goldring G800E ... **£5.20**  
Goldring G800 ... **£3.40**  
Shure V15 Type 3 ... **£28.40**  
Shure M75ED Type 2 ... **£7.90**
- Shure M75ED Type 2 ... **£9.10**
- Shure 91ED ... **£8.20**
- Shure M3D ... **£3.10**
- Sonolone 8 TACHD ... **£1.30**
- FABULOUS OFFER**
- AMSTRAD IC2000 MkII STEREO SYSTEM**  
Amstrad IC2000 MkII with increased power 25+25 watts amplifier. Complete with a pair of Amstrad Acoutra 2500 speakers, Garrard SP25 MkIV deck G800 Cart, Pliinth/Cover (Non Hinged) all leads.  
GLOBALS PRICE £80.75  
Cart. & Ins. £3.30
- STEREO HEADPHONES**  
Please add 42p for p & p & Ins.  
Koss ESP 5 ... **£47.95**  
Koss ESP 9 ... **£44.50**  
Koss K7/11 Red Devil ... **£29.90**  
Koss K8 ... **£21.70**  
Koss K6/LC ... **£32.25**  
Koss KD72E ... **£14.30**  
Koss 747 ... **£10.35**  
Koss HV1 ... **£18.95**  
Koss HV1/LC ... **£23.90**  
Koss PRO 5/LC ... **£27.15**  
Koss K7/11 Black ... **£9.90**  
Sennheiser HD414 ... **£30.75**  
Sennheiser HD 424 ... **£15.55**

**GLOBAL AUDIO**

Full 12 Month After Sales Service  
We give a FULL 12 MONTH GUARANTEE on all products purchased at any branch parts and labour absolutely FREE

**NO HIDDEN PRICES AT GLOBAL AUDIO - ALL OUR PRICES ARE SHOWN WITH VAT INCLUDED**

PERSONAL CALLERS VERY WELCOME! COMPARE OUR PRICES WITH ANY AT THE 1000 OPIA BOEAT TO SATURDAY 2.30pm - 4pm. CASH RECEIPTS ONLY OPEN UNTIL 3pm

**M.P. FACILITIES AVAILABLE FOR PERSONAL CALLERS ONLY**


MAIL ORDERS TO 24 PENTONVILLE ROAD, LONDON, N1  
Order with confidence. Send Postal Order, Cheque, Money Order, Bank Draft, Giro or Cash by Reg. Mail.

PLEASE WRITE TO: M.P. FACILITIES, Money Order, Postal Order, Bank Draft or Giro to be made payable to: M.P. FACILITIES

**MODEL  
CONTROL  
BY  
RADIO!**

**IN NEXT MONTH'S  
PRACTICAL  
WIRELESS**

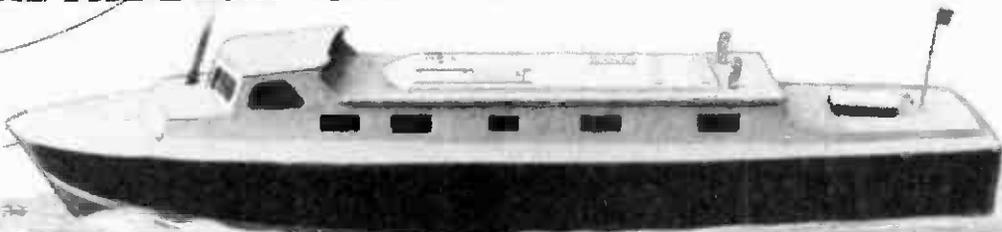**MAKE THE COMPLETE CONTROL SYSTEM YOURSELF!**




**PW** **MODEL  
CONTROLLER  
PART 1**

In this short series we shall show you how to build the transmitter, receiver and actuating mechanism required to provide radio control over a model up to around 100 yards away. No bought modules, you build everything yourself from scratch. You'll feel very pleased with yourself when it's finished and working! A special 'no-test' transmitting licence is required by law and we tell you how to get yours without any trouble. Amaze your friends as your model moves around under your complete control!

**LOW FREQUENCY AND  
MARINE  
RECEIVER**

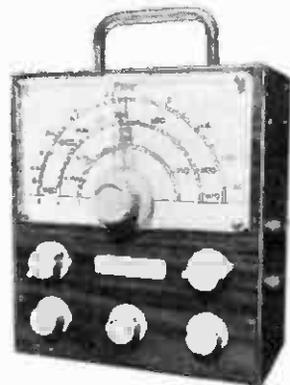This receiver covers the bands 150-1500 kHz and 1-65.5MHz and receives Marine, Broadcast and Amateur transmissions on AM, CW and SSB.



**ALSO:-**

**CONCLUDING SECTION OF PW BUYERS' GUIDE 74/5**

**MANY OTHER CONSTRUCTIONAL  
ARTICLES, SPECIAL FEATURES  
AND REGULAR COLUMNS.  
ON SALE IN DECEMBER**

**\*Special  
Pre-Publication  
Radio Book Offer**



KEITH CUMMINS & TONY

**T**HE motor car is not an ideal environment for a tape player, or indeed for any electronic apparatus. In particular the problems of power supply regulation and electrical noise are far more acute than those likely to be encountered by a domestic machine.

### ENVIRONMENT

The supply voltage, although nominally 12V, is likely to vary considerably under the loading conditions imposed by windscreen wipers and heaters, lights, etc. As a result we must produce a unit capable of working safely up to a possible maximum of around 15.5V, yet also maintaining a satisfactory performance down to 10V. For the amplifiers this is not too difficult—achieving a constant speed for the tape transport is not so straightforward.

Because a negative earth system is more or less universal on modern cars, the unit has been designed for this. Conversion to positive earth working is very simple, however, and will be described later: no change of components is required. Operation on 6V systems is not possible.

The construction of the tape-transport mechanism itself would of course be beyond the resources of the majority of our readers. It is therefore necessary to use a commercial mechanism. The one specified in the components list incorporates facilities for electronic speed control and also auto-stop and cassette ejection at the end of the tape. This feature is very necessary in a car where the machine must “look after itself” if the driver is fully occupied in manoeuvring his vehicle.

Interference from the car’s electrical system seems to be worse with the modern alternator and solid-state regulator than it was with their predecessors. Power supply filtering and comprehensive screening are essential if the tape-head output, which is less than 500µV, is not to be completely submerged in the hash.

Acoustic noise levels in the passenger compartment vary considerably from one car to another. The amplifiers used here provide over 3W rms output into 4Ω loudspeakers from a 12V supply: this should be adequate for pretty well any car.

### TAPE AMPLIFIER

The amplifier system can be conveniently divided into three parts, a low-noise preamplifier, an equalisation section and a power amplifier. Silicon transistors are used in all but the power output stages.

A stereo cassette carries four tracks recorded on a tape only 1/8in wide and running at 1 7/8in/sec. Hence the very low output level from the tape head. The amplifier input stage must therefore be designed for very low-noise performance. The technique adopted here uses complementary npn and pnp transistors, with the collector current of the first stage providing the base current of the second. The first transistor is thus operating under “starvation” conditions—a factor which greatly assists in the reduction of transistor noise.

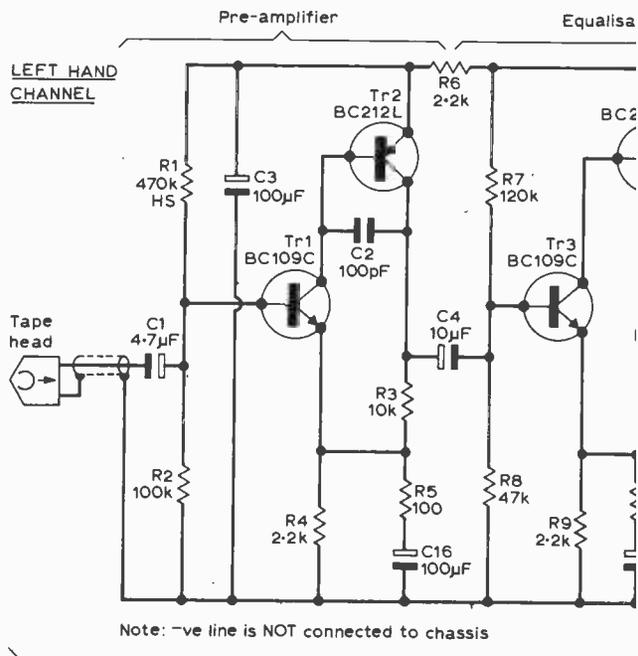


Fig. 1: Circuit of one channel of

\* Hamilton Electronics Ltd.

**PRACTICAL WIRELESS**

some may not. It is a chance that the buyer takes.

Before you solder into the circuit, make sure that you know or can obtain the correct connections for the specimen you have obtained. Do not overheat; use a small soldering iron (15 watts max.) and hold the wire being soldered with wiring pliers. If you are experimenting leave the wires long. Only shorten them when you wish to fit them in permanently or in u.f. work, where the length may be critical.

Some transistors require heat-sinks. Take care and observe instructions regarding fitting, insulating washers and position.

Transistor holders are available for many types and like i.c.s they are worth using in experimental projects, but it is always better to solder in for permanent use.

**TRANSISTOR MOUNTING PADS**

These often-neglected but very cheap little components are recommended to give some measure of protection against accidental knocks to the transistor when handling, and further provides a "seat" for the transistor to keep it clear of the component assembly board, so ensuring that the wires are properly protected and insulated.

**TRIACS**

When triggered, triacs will pass forward and reverse current; hence their use with a.c. The triggering voltage and current is important to achieve successful firing. Observe the main terminal connections m1 and m2 with respect to the gate. Note that the triac does not isolate the high secondary voltage from the low trigger voltage. If used with a.c. mains supplies it is wise to employ an isolating 1:1 transformer for the trigger signal.

**CHOOSING**

**COMPONENTS**

**CAPACITORS**

Markings usually identify the capacitance and sometimes the working voltage and/or tolerance. Colour coded capacitors can be identified by reference to the Practical Wireless Datacard No.2 which was provided in the October 1973 issue.

*Capacitance*  
microfarads shown as  $\mu\text{F}$ , mF, mfd,  
nanofarads shown as nF, n, k,  
or  $\text{kpf} = 1/1,000\mu\text{F} = 1,000\text{pF}$ ,  
picofarads shown as pF, p,  $\mu\mu\text{F}$ ,  
mmfd=one millionth of  $1\mu\text{F} = 1/1,000\text{nF}$ .

*Voltage* also known as the working voltage and shown as a number of volts d.c. (VWDC) or V d.c. or V a.c.

This value represents the maximum safe recommended voltage that should be applied to its terminals. There is no different effect in applying a lower voltage, but the stated voltage should not be exceeded.

It is quite common now for "pre-ferred value" components to be supplied as substitutes, for example  $0.47\mu\text{F}$  instead of  $0.5\mu\text{F}$  or  $0.022\mu\text{F}$  instead of  $0.02\mu\text{F}$  and so on. There is usually no detrimental effect by substituting in this way with near alternatives, as long as the specified voltage is not exceeded.

When using capacitors for a.c. mains (200 to 250V) such as for interference suppression, either a 270V (minimum) a.c. type or a 1,000V (minimum) d.c. type should be used.

*Dielectric*  
The insulating material between the metallic foil or plates gives the

**PLUGS AND SOCKETS OR CONNECTORS**




Socket (SK) plug (PL) for single core screened wire



Single plug and socket




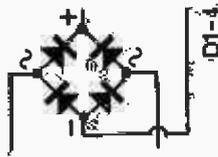Socket (SK) plug (PL) for coaxial cable (not BS)



BRIDGE RECTIFIERS

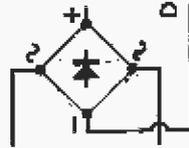Bridge rectifier. The signs may not always be shown



Simplified symbol for a bridge rectifier. The diode symbol must be shown pointing to the + terminal

**WATFORD ELECTRONICS**

35 Cardiff Road  
Watford Herts  
Tel. Watford 37774

Callers Saturday only  
Orders despatched by return of post. All components brand new and guaranteed at competitive prices. Send 10p for catalogue. *Directory entry on page 14*

**H. L. SMITH & CO. LTD.**

287/9 Edgware Rd,  
London W2 1BE

INSTRUMENT CASES  
& CHASSIS OFF THE SHELF—MANY SIZES  
Send SAE for leaflet.

01-723 5891/723 7595  
Directory Entry P43.

**CAPACITANCE CODE (BS 1852)**

Capacitors can be marked with their nominal value using figures and letters in place of the conventional colour code. The three multiplier letters in common use are:—

$p = 10^{-12}$   $n = 10^{-9}$   $\mu = 10^{-6}$   
of the capacitance in FARADS.

Nominal value	Becomes
1pF	1p0 (mult x 1)
330pF	330p ( " " )
1000pF	1n0 (mult x 1000)
4700pF	4n7 ( " " )
10000pF	10n ( " " )
1 $\mu\text{F}$	1 $\mu$ 0 (mult x 1000000)
6.8 $\mu\text{F}$	6 $\mu$ 8 ( " " )

capacitor specific properties (see text book on the subject). Generally the most suitable for r.f. applications are ceramic or silver mica types; for a.f. and h.f. use one of the plastic types; for space saving and smoothing, electrolytic types can be used, or tantalum types which, although more expensive, are more stable and reliable over long periods of use. Electrolytic capacitors break down after a few years and are number one suspect of capacitor failure symptoms. Paper types are now being superseded by plastics.

**COILS**

Ready made coils are usually designed for a specific application, hence they seldom carry any characteristic markings other than the makers code number. Unless their properties are known or can be measured accurately, there is little value in unmarked coils. If buying coil formers or bobbins for winding your own coils, check that you order or ask for all parts, especially if a brass or dust iron slug is to be used to adjust the inductance in a tuned circuit.

**DIODES**

Because of the very small size of many diodes, it is not always possible to mark them with the full type number. Some are marked with very small lettering that needs a magnifying glass to read it. One end of the diode body is usually marked with a + sign or a band of distinguishing colour, or maybe black or white; this indicates the cathode terminal.

Special types include "Varicap" or similar variable capacitance diodes. The capacitance effect changes with a change in the applied voltage. This type is now frequently used in radio and television tuners.

Zener diodes limit the applied voltage to the specified level and are very useful for regulating low voltage d.c. supplies.

**FERRITES**



Often the cause of some misunderstanding, "ferrite" is a term now loosely applied, even mistakenly, to some kinds of dust iron materials and ceramic cores. Their properties are quite specific. Ferrite beads (used for suppressing parasitic oscillation) pot cores, rods and toroids are specifically designed to be most effective over a pre-determined frequency range. For more detailed information consult manufacturers' literature. When ordering pot core assemblies make sure that you ask for all the necessary parts, which usually include two halves of the pot, the bobbin, the clamps and tag strips.

**HEATSINKS**

Heatsinks vary enormously in size and shape. If they are cast or moulded in aluminium alloy they should be painted matt black, but if electrical connection is required to the transistor casing, make sure that the contact area is free from paint. Insulation from the transistor casing must, where required, be carefully achieved with the correct insulating washer and nylon fixings. Any rough edges on drilled holes must be removed. Other heat sinks are made from copper; alternative metals are not always suitable because of inferior heat conductivity properties.

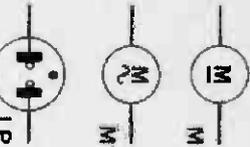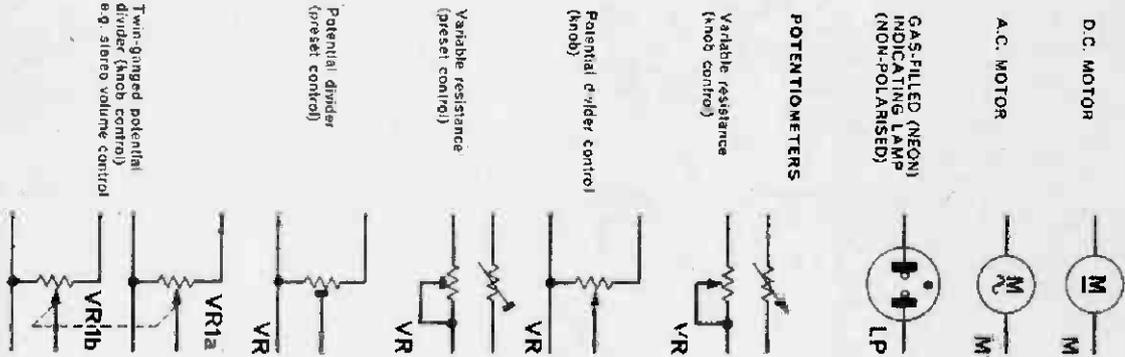**INTEGRATED CIRCUITS**

In the limited space available it is not possible to give detailed suggestions on all types available; however, here are a few hints to observe.




**POTENTIOMETERS**


Variable resistance (knob control)




Potential divider (knob control)

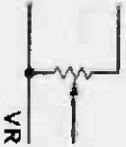

Variable resistance (preset control)

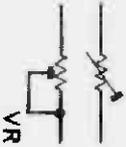

Potential divider (preset control)

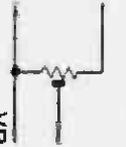

Twin-jugged potential divider (knob control) e.g. stereo volume control



high, so many thousands of transistors (and other semiconductor devices) find their way into a scrap yard or on to the open market. In spite of precautions taken to minimise the number that are released, several do slip through, sometimes with makers' names on them. However, experts can often identify the source by internal inspection.

Sub-standard devices may turn out to be very good bargains; in a lot of cases they can be used, particularly for experimenting with one-off projects, but it is unwise to spread adoption in a particular project because of the variations outside the specified characteristic range. They usually appear on the market as unmarked, re-marked or recorded types. In the latter case, a firm may have measured a batch and re-classified them, in which case you should identify the coding and obtain the correct specification from the supplier.

Unmarked devices cannot be classified unless they are measured under normal operating conditions and with a proper instrument. For the low prices often asked, the buyer can expect to have a very mixed batch; some may be usable and



SEE OUR REGULAR ADVERTISEMENT IN PRACTICAL WIRELESS

**PRACTICAL WIRELESS**

tolerance. Thyristors can be obtained at low cost and in these circumstances it is wise to measure the triggering voltage and current required to fire it. Also the "release" voltage should be measured.

**TRANSFORMERS**

Well made transformers are usually wound on chequered bobbins. Cheap versions have no cheeks and often have flying leads connected to the windings.

Satisfy yourself that the physical size is large enough to handle the current expected to be passed through the windings, otherwise saturation of the core and subsequent overheating could occur. This applies particularly to mains transformers and valve output transformers.

Mains transformers with a screen between the primary and secondary windings are recommended, to reduce problems from mains borne interference and high frequency transference. This screen must be earthed with the laminations.

**TRANSISTORS**

Many problems arising from the purchase of transistors are due to misunderstandings about their characteristics.

Transistors are made first, then measured and classified according to test measurements made on them. The result is a wide spread of characteristics, particularly on the gain (h<sub>FE</sub>) and leakage current (I<sub>CO</sub>).

Published data often give the range of gain for a particular type number. If transistors made for that type number have characteristics outside the quoted figures, then they are either classified into another appropriate type number or rejected. The reject rate is fairly

To be reasonably certain of getting a good specimen look for the manufacturer's official trade mark as well as type number. Some specimens may not carry all this information so you are entitled to ask for a full specification. Some sub-standard or "out-of-spec." items do appear and in many cases are usable. However, it does happen that a fault may be present on one of the pin connections. If it is otherwise functional it could be used if the fault does not interfere with your application. For example, you may buy a 7400 quad gate i.c. This device was designed to contain four gates, but if one gate is faulty you may still be able to use the other three.

It can sometimes occur that an assumed first grade i.c. may have an intermittent or faulty internal connection. If the device has been properly used in the circuit then the buyer could expect the supplier to replace it, unless it was declared as faulty at the time of purchase.

However, a problem arises immediately if the device has been soldered and there is no way of proving that the fault could have been there before it was soldered in or may have resulted from clumsy or overheated soldering. It is always wise to use i.c. holders for this reason and to make removal of the i.c. from the board easier. You cannot expect the supplier to replace a faulty i.c. if it has not been operated as recommended by the manufacturer.

Unmarked i.c.s or unidentifiable i.c.s are seldom worth having unless the supplier can offer some clue to the originally intended function. Even with test equipment it is almost impossible to ascertain the properties of such devices.

Whatever i.c.s you buy always ask for a data sheet or obtain a copy

**PANEL METERS**



Ammeter (current)



Voltmeter (voltage)



Wattmeter (power)



Frequency meter



Ohmmeter (resistance)



Galvanometer or centre-zero balance meter



SINGLE-POLE ON-OFF MICROSWITCH OR LIMIT SWITCH



MORSE KEY

**KEEP  
UP-TO-DATE**

**ON  
TECHNICAL  
DEVELOPMENTS**

**IN TV  
AT HOME  
AND ABROAD**

**READ  
TELEVISION**

**EVERY  
MONTH**

**A  
COMPANION  
MAGAZINE  
TO  
PRACTICAL  
WIRELESS**

from the manufacturers or distributors. This is most valuable for pin connection identification as well as giving the expected specification.

A golden rule is never to solder in, until you are satisfied that you have the correct device in the correct position; i.c.s can be very costly and difficult to replace.

**PRINTED CIRCUIT BOARDS**

P.C.B.s are mainly of two kinds: glass fibre board and s.r.b.p.

Glass fibre board is more expensive but is superior to s.r.b.p. board, being more rigid and stable. Slight bending or flexing of any board can lead to the copper cracking, especially where it is in narrow strips. Small soldering irons (15 watt maximum) should be used; larger irons can melt the copper away.

Most unetched board is unprinted and not tinned so the copper must be thoroughly cleaned before etching and again before soldering. A washing-up scouring pad or powder can be used with care. When cutting the board always use a fine toothed hacksaw. Glass fibre tends to blunt the blade more rapidly than s.r.b.p.

Double-sided board is sometimes used where it is important to have a "ground-plane". The copper on one side is etched to suit the circuit and, on the other (ground-plane) side, the copper can be carefully etched or peeled away from holes to avoid short-circuits. All components should be mounted just clear of the copper on the "ground-plane" side to avoid short circuits. Kits are available for etching p.c.b.s yourself. Read and follow the instructions carefully and do not leave the bottle of solution open. Some component suppliers do arrange to supply ready-etched boards for specific purposes and some are able to supply etched

boards to individual design requirements.

Magazines usually publish the printed circuit patterns for their projects where applicable so that constructors can etch their own boards. Adequate copper must be allowed where holes are required to ensure a satisfactory soldered connection. Any modifications to the board after etching can easily be done by either peeling away copper carefully with a sharp pen-knife or adding link wires as necessary.

**POTENTIOMETERS**

Potentiometers are made in various styles: Apart from the overall resistance value, the other properties to quote are: carbon track or wirewound; logarithmic or linear track resistance. Skeleton preset types have open unprotected carbon tracks and can be obtained for vertical or horizontal mounting on p.c.b.s. Log types are most commonly used for volume controls. The maximum power rating of all potentiometers determines the current that can be safely handled, and in particular with d.c. voltage control, this rating should never be exceeded.

**RESISTORS**

A look at the directory classification will show many different groups. The following information should be provided when ordering:

- (a) Construction material e.g. carbon film, etc.
- (b) Resistance in ohms, kilohms ( $\Omega \times 1,000$ ) or megohms ( $\Omega \times 100$ ).
- (c) The tolerance, e.g. 1%, 2%, etc.
- (d) The power rating, e.g.  $\frac{1}{2}$  watt etc.

*continued on p33*

Some of the high stability types are more expensive and are used where low thermal noise and close tolerance are important factors to the application. The power rating quoted is an indication of the maximum current that can be handled by the resistor in conjunction with the applied voltage, and should be adequate for the application.

**SWITCHES**

Wafer switch assemblies are obtainable in kit form and it is essential to ask for every part down to the last nut. The wafer specifies the switching mode, which is described later. Common abbreviations used for switches are:

**SP** = single pole (one switch).  
**DP** = double pole (two switches operated simultaneously).

**3-pole** = three switches operated simultaneously, etc.

**ST** = single throw or on-off function.

**DT** = double throw or change-over function.  
**4-pole, 3-way** four switches each having three outlets and operated simultaneously, usually on a wafer.

**CO** = changeover.  
**MB** = make before break.  
**BM** = break before make.

Centre-off applies where a toggle or lever switch has two outlets and a central neutral position.

**THYRISTORS & TRIACS**

Thyristors can behave in various ways if they are not up to manufacturers' published specification. In some applications such low cost specimens may appear to function, but in others they may be unreliable. The most common defect is the triggering level which may be outside the manufacturer's quoted

**MARKING OF CAPACITORS (pF) AND RESISTORS ( $\Omega$ )**

**PREFERRED VALUES.** The common range of twelve values is known as the E12 Series:—  
 1.0-1.2-1.5-1.8-2.2-2.7-3.3-3.9-4.7-5.6-6.8-8.2 together with their decades such as 47 470 4700 47000 etc.  
 The E24 Series can be expanded to the E24 Series by adding the following intermediate values:—  
 1.1-1.3-1.6-2.0-2.4-3.0-3.6-4.3-5.1-6.2-7.5-9.1 and their decades.

**RESISTANCE CODE (BS 1852)**

Increasing use is being made of the British Standards (BS 1852) method of marking resistors with their value and tolerance using figures and letters only instead of a colour code. The multiplier is represented by a single letter:—  
 R =  $\times 1$  K =  $\times 1000$  M =  $\times 1000000$

which replaces the decimal point when indicating the value of the resistor, thus:—  
 150 15R (multiplier =  $\times 1$ )  
 330K 330R ( " " )  
 56K 56 (multiplier =  $\times 1000$ )  
 47K 47K (multiplier =  $\times 1000$ )  
 1.2M  $\Omega$  1M2 (multiplier =  $\times 1000000$ )  
 18M  $\Omega$  18M (multiplier =  $\times 1000000$ )

**TOLERANCE.** The marking indicating the nominal value of the resistor has a single letter added to it representing the tolerance figure:—  
 F =  $\pm 1\%$  G =  $\pm 2\%$  J =  $\pm 5\%$   
 K =  $\pm 10\%$  M =  $\pm 20\%$

**Examples:—**

- 2M2F signifies 2.2M  $\Omega$  1%
- 1K8G " 1.8K  $\Omega$  2%
- 120KJ " 120K  $\Omega$  5%
- 158R " 150  $\Omega$  10%
- 6R8M " 6.8  $\Omega$  20%

# CASSETTE

# LAYER

ANCIS\*




Transistor gain will vary from sample to sample and will also change with the supply voltage. To overcome these problems, negative feedback is used to stabilise the gain of the preamplifier.

The preamplifier has now raised the signal from the tape to a more reasonable level, but it still has a "Velocity characteristic"—that is, for every doubling of the recorded frequency the output level also doubles. This is because the tape head output level is proportional to the rate of change of magnetic flux due to the tape moving past the head. For a constant recorded amplitude, an increase in pitch of one octave (doubling of frequency) will cause the flux to change at twice the rate, and hence the output doubles also. It continues to double with each octave rise until tape head losses become significant at the higher frequencies.

At the time of recording, the higher frequencies are pre-emphasised or boosted relative to the low and middle frequencies. This means that the signal-to-noise ratio of the tape is improved, since tape noise is predominantly at high frequencies.

From the foregoing it is obvious why we need to have an equalisation amplifier. This has a characteristic which is the inverse or "dual" of the overall tape curve. The output of this section has a flat frequency response over the audio range.

At this point the signal is suitable for feeding into the power amplifier, which uses a conventional complementary-symmetry circuit. The output voltage can swing between the two supply rails, less the residual voltage drop across each output transistor, say about  $12 - 2 = 10V$ . The rms equivalent of this peak-to-peak voltage is approximately  $3.6V$  which will produce about  $3.25W$  using a  $4\Omega$  loudspeaker.

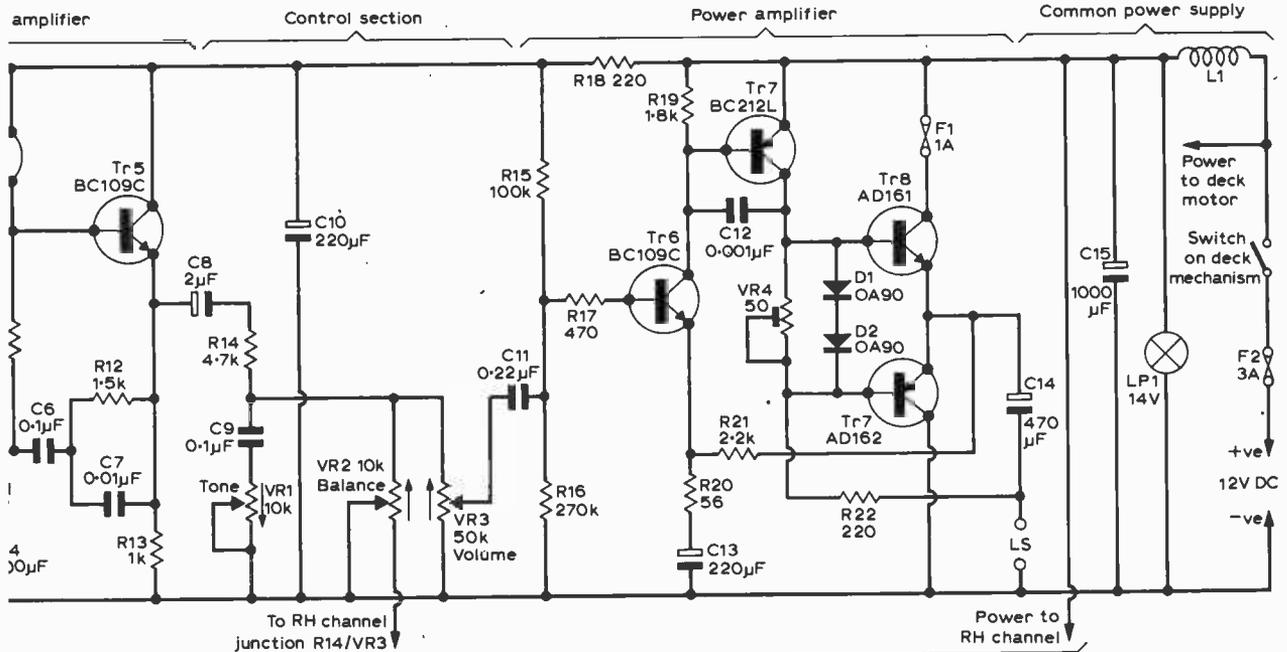

Right hand channel is identical to left hand channel. This diagram shows the right hand channel amplifier board, plus common power supply. NOTE.—The AD162 should be Tr 9.

AM0247

## ★ components list

### AMPLIFIERS

#### Resistors

R1 470kΩ	R9 2.2kΩ	R17 470Ω
R2 100kΩ	R10 10kΩ	R18 220Ω
R3 10kΩ	R11 47Ω	R19 1.8kΩ
R4 2.2kΩ	R12 1.5kΩ	R20 56Ω
R5 100Ω	R13 1kΩ	R21 2.2kΩ
R6 2.2kΩ	R14 4.7kΩ	R22 220Ω
R7 120kΩ	R15 100kΩ	
R8 47kΩ	R16 270kΩ	

R1 is  $\frac{1}{2}$ W High Stability. R22 is 1W 5%. Remainder are  $\frac{1}{4}$ W 5% carbon.

#### Potentiometers

VR1 10kΩ log (ganged with other channel)
VR2 10kΩ lin.
VR3 50kΩ log (ganged with other channel)
VR4 50Ω horizontal preset

#### Capacitors

C1 4.7μF 6V Tant.	C9 0.1μF Cer.
C2 100pF Cer.	C10 220μF 16V
C3 100μF 16V	C11 0.22μF 10V Tant.
C4 10μF 10V	C12 0.001μF Cer.
C5 100μF 6V	C13 220μF 10V
C6 0.1μF Poly.	C14 470μF 16V
C7 0.01μF Poly.	C15 1000μF 16V
C8 2μF 10V	C16 100μF 6V

Tant — Tantalum bead Cer — Disc ceramic  
Poly — Polyester Remainder electrolytic

#### Semiconductors

Tr1, Tr3, Tr5, Tr6	Tr8 AD161	} matched pair
BC109c	Tr9 AD162	
Tr2, Tr4, Tr7	BC212L	D1, D2 OA 90

NOTE—The above components are for one channel only. All except C15 and VR2 are duplicated for the second channel.

#### Miscellaneous

L1 2A suppressor choke; LP1 14V lamp;  
F1 1A fuse with chassis-mounting holder (two required);  
F2 3A fuse with in-line holder;  
Cassette mechanism, Lenco FFR, Stereo with D.C. motor;  
Veroboard 6.75 x 2.5in, 0.1in pitch; DIN connectors for loudspeaker outputs; 4Ω loudspeakers; metal case; mounting kits for Tr8, Tr9; knobs, etc.

### MOTOR CONTROL BOARD

#### Resistors

R51 2.2kΩ	R56 15Ω	R61 100kΩ
R52 6.8kΩ	R57 820Ω	R62 2.7kΩ
R53 8.2kΩ	R58 560Ω	R63 680Ω
R54 1.5kΩ	R59 680Ω	R64 120Ω
R55 3.9Ω	R60 4.7kΩ	

R55, R56 are  $\frac{1}{2}$ W, remainder  $\frac{1}{4}$ W  $\pm 5\%$   
VR51 1kΩ miniature preset.

#### Capacitors

C51, C52 22μF 25V Electrolytic

#### Semiconductors

D51—D53 BA100  
Tr51, Tr54 BC109 Tr52 AD162 Tr53 AC128

#### Miscellaneous

Mounting kit for Tr52; pcb.

The use of class B output with output transformers could, with correct design, yield 10 watts per channel if needed. However, we have to consider the size, weight and economics of the machine, as well as the problems of obtaining specialised components. The complementary output stage produces as much power as is likely to be needed for practical purposes, and all components are easily obtainable.

## PREAMPLIFIER

The circuit of the complete unit is shown in Fig. 1. It will be seen that the signal from the tape head is coupled to the base of transistor Tr1 via capacitor C1. The biasing of Tr1 base is set by R1 and R2. Resistor should be R1, a low-noise, high-stability type, but R2, the lower leg of the bias divider is effectively by-passed by the low impedance of the head so far as audio is concerned, and is a normal carbon type.

The collector of Tr1 connects directly to the base of the complementary pnp transistor, Tr2. The base current of Tr2 and the collector current of Tr1 are therefore the same.

We can now consider the DC stabilising action of the circuit. If the current in Tr1 increases, so does the base current of Tr2. This change is amplified by Tr2 so that its collector current increases. Thus, more current flows through R3, which in turn connects to R4. The voltage drop across R4 is almost entirely due to the current flow via R3, rather than current in Tr1 which is operating under "starvation" conditions. An increase in the collector current of Tr2 therefore causes the emitter of Tr1 to move positively towards the supply rail. This is equivalent to a negative shift of its base bias and the collector current of Tr1 is so reduced. The change is amplified by Tr2 and this heavy DC feedback action stabilises the working point of the complete preamplifier.

We do not need such heavy AC feedback—in fact appreciable AC gain is required. By decoupling R4 completely, a very high gain could be obtained, but it would be unpredictable and unstable. By introducing R5, the gain of the stage is set at about 100 by the ratio R3:R5 and is almost independent of voltage, temperature and transistor variations. The output from the preamplifier is therefore about 50mV. The supply to the preamp is decoupled by R6 and C3, and the output is coupled to the equalisation amplifier via capacitor C4.

## EQUALISATION

The biasing method and stabilisation technique is the same as that employed in the preamplifier. However, an extra emitter-follower output stage is added which feeds both the Tone and Volume controls and the equalisation network comprising R11, C6, R12 and C7. The basic amplifier without equalisation would provide a gain determined by the ratio R10:R11, in this case, 200.

It is essential that the feedback network, which operates into the low impedance R11, should be fed from a low impedance source. If this were not the case, the response correction would be hopelessly inaccurate, as the network loads the source.

It will now be seen why Tr5, the emitter-follower stage, is included. It is DC coupled to Tr4 and provides a low impedance output. Basic correction for the velocity characteristic of the tape is provided by R12 and C6; C7 provides extra feedback to compensate for the tape pre-emphasis.

The equalised signal, which has now been amplified to around the 250mV level, is conveyed via C8 to R14 which is included to increase the impedance "seen" by the tone and balance networks. Resistor R14 forms the upper leg of a divider network, whose lower leg is formed by the Balance control VR2. This control operates differentially upon the two stereo channels, so that increased attenuation of one simultaneously results in an increase of output from the other. The tone control network consists of C9 and VR1. This is a simple "top cut" network which is adequate for use in the car.

Finally we come to the Volume control, VR3, which taps off the required output to drive the power amplifier.

## POWER AMPLIFIER

The power amplifier consists of four transistors, Tr6, Tr7, Tr8 and Tr9. The latter two are complementary output transistors mounted on the backplate of the machine, which serves as a heat sink.

The action of the driver stage is similar to that of the previous amplifier. Transistor Tr6 has its base level set by R15 and R16. In this case, the level set is approximately half-way between the .12V rail and earth. Capacitor C12 is included to prevent RF instability, as is R17. The collector of Tr7 feeds the base of Tr8 directly, and the base of Tr9 via D1 and D2 and VR4, before reaching the collector load resistor R22.

Potentiometer VR4 sets the forward bias applied to the output transistors. In order to compensate for changes in temperature, diodes D1 and D2 are shunted across VR4. As the output transistors are germanium types, germanium diodes are used. When

the temperature increases (a condition which would cause increased conduction in Tr8 and Tr9) the impedance of the diodes falls, so decreasing the forward bias and stabilising the working conditions.


The emitters of Tr8 and Tr9 are connected via R21 to the emitter of Tr6, giving overall stabilisation of the DC working point of the amplifier. The emitter of Tr6 is decoupled by C13, and R20 is included to provide AC feedback in the ratio R21:R20, so stabilising the gain at around 40. If we consider a level of 200mV coming in from the volume control, this means we are just inside the overload point of the amplifier. The audio signal is coupled to the speaker via C14.

The loudspeaker also completes the DC return for R22. The audio output signal is in phase with that at the collector of Tr7 and hence there is positive feedback. This raises the input impedance of the output stage and enables the small transistor Tr7 to drive the output pair fully. This technique is known as "boot-strapping."

The output pair operate in class B. Forward bias is needed to prevent cross-over distortion, and VR4 is set up to provide a 10mA quiescent current measured at the fuse-holder. The fuse is connected in series with the collector of Tr8, to protect the output stage from conditions of gross overload.

The incoming supply from the vehicle is filtered by L1 and decoupled by C15. Power to the deck motor and panel light are also fed from this part of the circuit. The on-off switch is included as part of the tape deck mechanism.

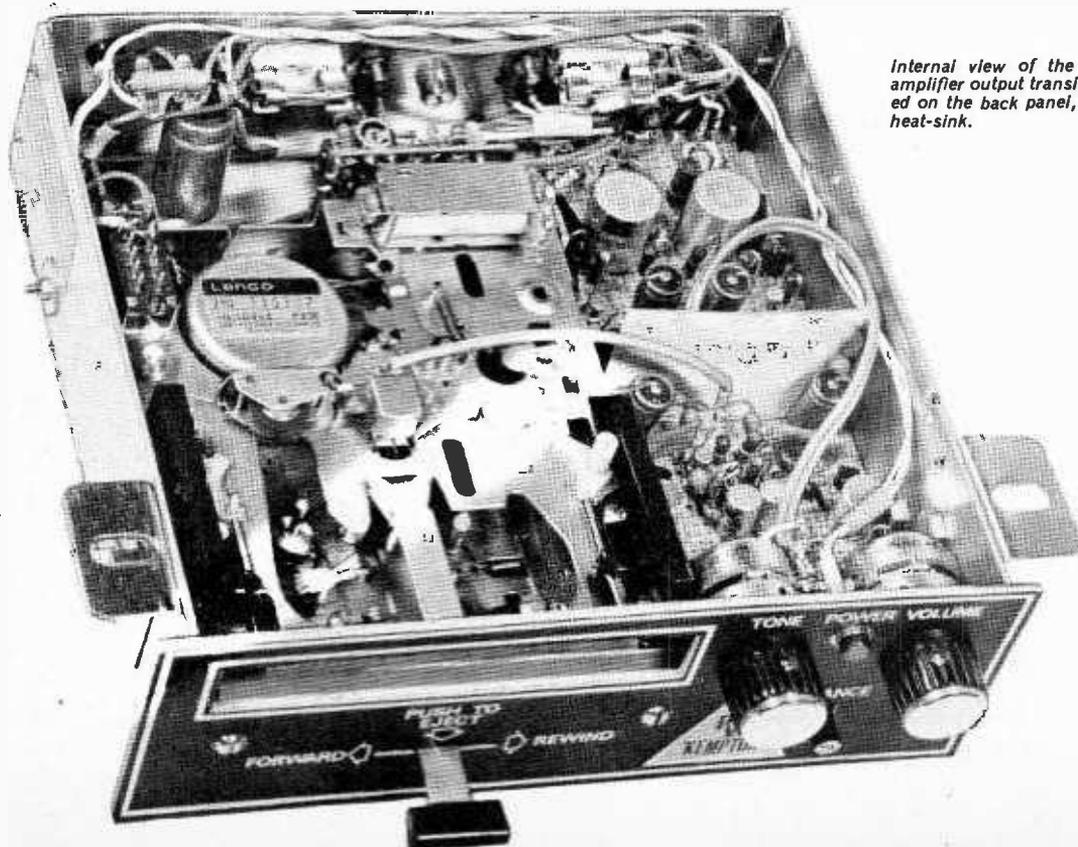The second part of the article describes the motor control circuitry and construction of the circuit boards.



*Internal view of the prototype. The amplifier output transistors are mounted on the back panel, which acts as a heat-sink.*

Now - two fascinating ways to enjoy saving money!

# NEW! Sinclair Scientific kit **£19.95** (INC. VAT)

## Britain's most original calculator now in kit form

The Sinclair Scientific is an altogether remarkable calculator.

It offers logs, trig, and true scientific notation over a 200-decade range — features normally found only on calculators costing around £100 or more.

Yet even ready-built, the Sinclair Scientific costs a mere £32.35 (including VAT).

And as a kit it costs under £20!

## Forget slide rules and four-figure tables!

With the functions available on the Scientific keyboard, you can handle directly

- sin and arcsin,
- cos and arccos,
- tan and arctan,
- automatic squaring and doubling
- $\log_{10}$ , antilog<sub>10</sub>, giving quick access to  $x^y$  (including square and other roots),
- plus, of course, addition, subtraction, multiplication, division, and any calculations based on them.

In fact, virtually all complex scientific or mathematical calculations can be handled with ease.

## So is the Scientific difficult to assemble?

No. Powerful though it is, the Sinclair Scientific is a model of tidy engineering.


All parts are supplied — all you need provide is a soldering iron and a pair of cutters. Complete step-by-step instructions are provided, and our Service Department will back you throughout if you've any queries or problems.

Of course, we'll happily supply the Scientific or the Cambridge already built, if you prefer — they're still exceptional value. Use the order form.

## Components for Scientific Kit (illustrated)


1. Coil
2. LSI chip
3. Interface chips
4. Case mouldings, with buttons, windows and light-up display in position
5. Printed circuit board
6. Keyboard panel
7. Electronic components pack (diodes, resistors, capacitors, etc.)
8. Battery assembly and on/off switch
9. Soft carrying wallet
10. Comprehensive instructions for use

Assembly time is about 3 hours.

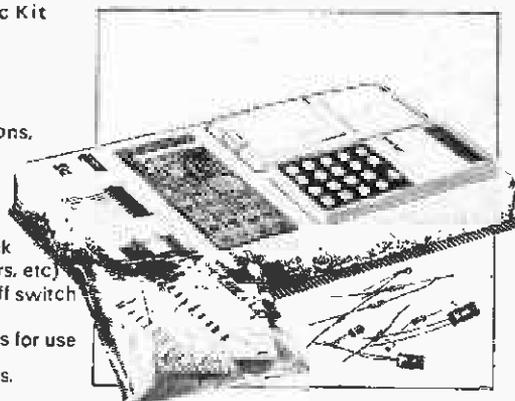
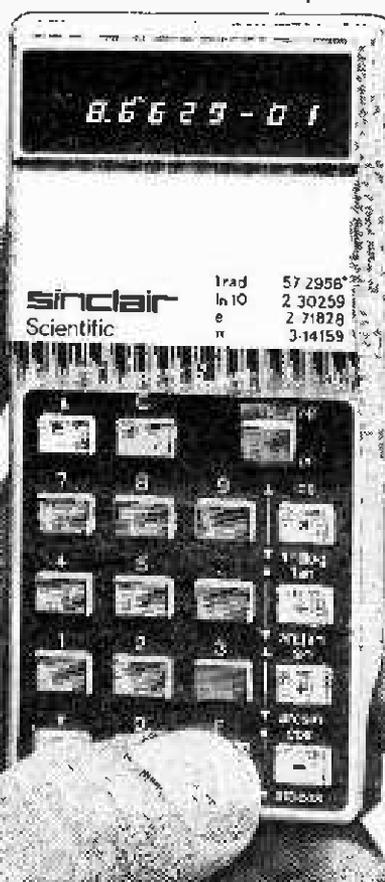
## Features of the Sinclair Scientific

- 12 functions on simple keyboard. Basic logs and trig functions (and their inverses), all from a keyboard as simple as a normal arithmetic calculator's. Upper and lower case operation means basic arithmetic keys each have two extra functions.
- Scientific notation. Display shows 5-digit mantissa, 2-digit exponent, both signable.
- 200-decade range  $10^{99}$  to  $10^{-99}$ .
- Reverse Polish logic. Post-fixed operators allow chain calculations of unlimited length — eliminate need for an = button.
- 25-hour battery life. 4 AAA manganese alkaline batteries (e.g. MN2400) give 25 hours continuous use. Complete independence from external power.
- Genuinely pocketable.  $4\frac{1}{3}'' \times 2'' \times 1\frac{1}{16}''$ . Weight 4 oz. Attractively styled in grey, blue and white.





A series of simple transistor projects, using not more than twenty components.

ONCE again we turn to that very useful integrated circuit, the SN7400, for a low-cost novel application, acting as the sensing circuitry for a photo detector. There are innumerable applications for this type of circuit. This particular one will operate in a multitude of roles without change to circuit layout or component values and possible uses range from burglar alarms to process control and object counters.

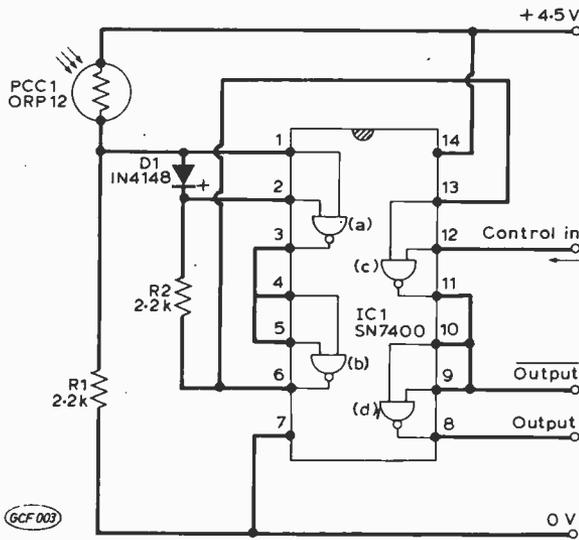


Fig. 1: Circuit of the photo trigger using an SN7400.

## Photo detector

The photo detector itself is a photo-conductive cell, PCC1, which forms part of a potential divider circuit with R1. When the cell is illuminated the potential at the junction of these two components rises to some positive level, the actual level depending on the degree of illumination and on the value of R1. As long as this potential exceeds +3V, with the power supply of 4.5V the circuit will work satisfactorily. To achieve this level it is necessary to use a reasonable level of light such as the focussed beam of a small torch. In the absence of illumination PCC1 becomes a very high resistance and the potential referred to falls towards zero.

The potential is applied to the input of a trigger circuit comprising IC1 (a) and (b). Positive feedback is achieved by R2 in conjunction with D1. Even though the controlling potential may rise slowly the regenerative feedback action causes the output of gate (b) to change rapidly and the change occurs as the input voltage moves around the +2.5V level. There is a certain amount of hysteresis built in and this is set by the value of R2.

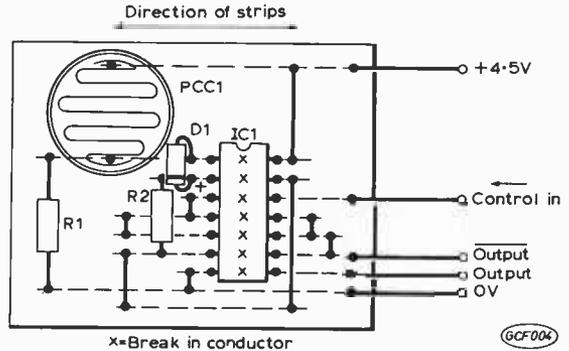


Fig. 2: Simple layout of the circuit using Veroboard.

The sense of the signal at the output of gate (b), pin 6 of the integrated circuit, is such that it rises to +5V when the cell is illuminated and falls to zero volts when the cell is obscured. We could have left the circuit at that stage and have said that the output was at pin 6; however we can make use of the other two gates within the integrated circuit to make the device more versatile.

## Control operation

Firstly we introduce a control operation by means of gate (c). The control signal should come from a source impedance of 2kΩ or less and should be a DC level of either 0V or +4.5V. A control signal of 0V will hold the output of gate (c) at +4.5V irrespective of what the photo detector might be sensing. We call the output signal at pin 11 the OUTPUT (NOT 'output') and use the final gate in the package (d) to invert this, thus, for the conditions stated, when the control signal is at 0V the final output at pin 8 will be 0V irrespective of the illuminating conditions. If the control signal is switched to +4.5V the output at pin 8 will be +4.5V when the cell is illuminated and 0V when it is obscured. The OUTPUT signal at pin 11 will be the opposite of this.

## Audio square wave


If desired, the control signal could be an audio frequency square wave. When the cell is in darkness the output at pin 8 will be zero volts but when illuminated the audio frequency will appear at the output. Should the control facility not be required pin 12 can be permanently wired to the positive supply rail. An advantage of having the complementary pair of outputs is that one can select the "bias" of the system; this is particularly useful if the output signals are to drive relays which may be required to be biased either "ON" or "OFF".

# f. m. stereo tuner

## CONTROL PANEL

The layout of the prototype control panel is shown in the photographs. Since all functions are DC controlled the layout is not critical and can be altered to suit your own requirements. Also, as mentioned earlier, any features which you do not require may be omitted.


The manual tuning drive was constructed on a framework built mainly of aluminium angle, as shown in Fig. 8a. Details of the drive-cord arrangements are given in Fig. 8b.

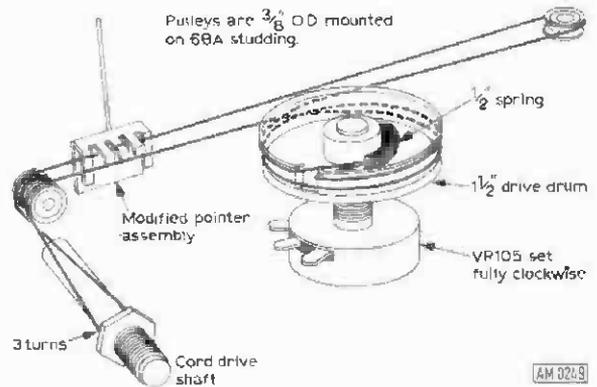

AM 0249

Front panel  $9\frac{3}{4} \times 4\frac{1}{2} \times 16$ swg aluminium

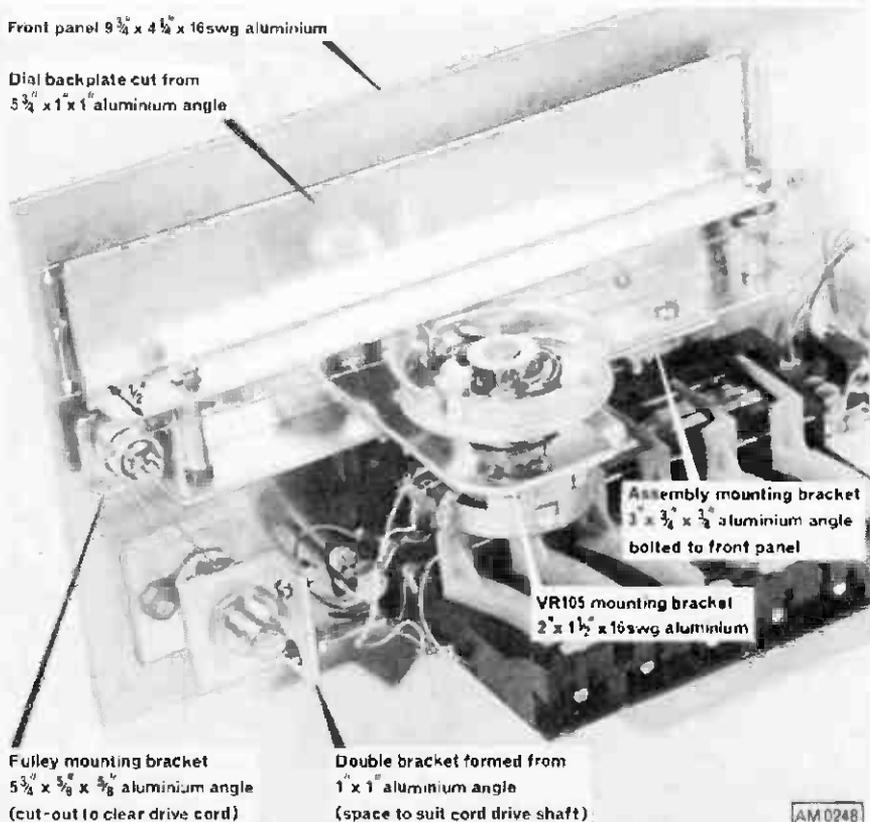Dial backplate cut from  $5\frac{3}{4} \times 1 \times 1$  aluminium angle



Assembly mounting bracket  
 $1 \times \frac{3}{4} \times \frac{3}{8}$  aluminium angle  
bolted to front panel

VR105 mounting bracket  
 $2 \times 1\frac{1}{2} \times 16$ swg aluminium

Fuley mounting bracket  
 $5\frac{3}{8} \times \frac{3}{8} \times \frac{3}{8}$  aluminium angle  
(cut-out to clear drive cord)

Double bracket formed from  
 $1 \times 1$  aluminium angle  
(space to suit cord drive shaft)

AM 0248

▲  
Fig. 8b: Drive cord stringing arrangements. The pointer assembly is modified by trimming the ends of the carriage to clear the pulley mountings and also inverting the pointer on the carriage.

Fig. 8a: Construction of the prototype tuning and dial drive.

**TABLE 2**  
Voltage analysis

Meter 20k $\Omega$ /Vdc—negative lead to 0V rail, all readings in volts. No aerial connected.

H.T. Supply at C303 13V.

**Transistors**

	s*	g1	g2	d		e	b	c
Tr 101	0.1	0	4.5	13	Tr 103	7.2	6.5	0
Tr 102	0.4	0	1.4	13	Tr 201	7.2	6.5	0.9
					Tr 202	5.8	6.5	12.1

\* Subject to wide variations between transistors.

**Integrated circuits**

	Pin	Reading		Pin	Reading
IC 201	1, 2, 3	1.9	IC 202	1	2.3
	6	5.5		6	2.1
	10	5.8		9, 10	6.4
	13	1		12	13
	15	4.5			

† See Table 4.

## INITIAL TESTING AND SETTING UP

Before any RF adjustments are made it is wise to check the DC conditions at each stage in turn. A construction error or a faulty component is likely to produce an incorrect voltage in an associated part of the circuit. Table 2 shows the voltages to be expected at important points in the circuit when measured with a 20,000 ohms per volt meter, on the range most appropriate to the voltage to be measured.

Switch on and check the voltages appearing in the front end and oscillator stages. If they are correct connect the meter, on its 2.5V or 3V range, to the positive end of VR104 which should be adjusted until a reading of 2.0V is obtained with VR105 at minimum and S101 switched to Manual.

Now solder in R205 to apply power to the IF section and check the voltages against Table 2. Follow the same procedure with the demodulator and stereo decoder integrated circuits to complete the initial testing. The voltage appearing at pin 15 of IC201 indicates the strength of the signal at its input. A high reading here could indicate that a programme is being received or that there is some instability in the IF section. If rocking the tuning control does not reduce this voltage to the correct level, check that all the IC201 decoupling capacitors and the link joining the top and bottom earth planes are in place.

## ALIGNMENT

When all the DC tests have been completed satisfactorily you are ready to move on to the final stage of construction, aligning the receiver. Connect two lengths of screened wire to the Left and Right audio output pads ready for attachment to the output socket. Remove the temporary earth wire and mount the receiver in the die-cast box. The earth connection is now made via the mounting stud in the power supply section of the pcb.

Connect a short length of wire from the centre pin of the aerial socket to L101, as shown in Fig. 7, and

solder the audio output leads to the 5-pin DIN socket (Fig. 9). If your audio amplifier is earthed via its mains plug, avoid hum loops by breaking the earth connection between the tuner and the amplifier (which is made by the screen of the audio connecting lead) at a convenient point.

## RF/IF ALIGNMENT

The method of alignment adopted depends on the facilities available to the constructor. Two methods are therefore proposed; the first requires the use of a VHF signal generator but the second needs only another, aligned, FM tuner.

## FIRST METHOD

Short out the oscillator coil, L106, with a crocodile clip and connect the signal generator to the 'hot' end of L104. The output level of the generator should be set to about 1mV and the frequency set to the nominal centre frequency of the particular ceramic filter used. The filters are graded into batches of varying centre frequency, each frequency being identified by different colours. Table 3 lists the frequencies and their corresponding colours.

If a signal strength meter is not included a high impedance multimeter should be connected to pin 13 of IC201. By varying the frequency of the generator slightly about the nominal value it should be possible to detect a deflection on the signal strength meter or the multimeter. Once this has been found the core of the mixer load coil, L105, should be adjusted until maximum deflection is obtained. This circuit has a low Q so the peak is very broad.

Leaving the generator frequency unchanged remove the dustcore of L202. The tuning meter should now show only a slight deviation from the null position. Screwing in the core will make the tuning meter give a large deflection to the right, pass through the null position and deflect to the left before returning to the null.

This demonstrates the S-shaped curve of the detector, the correct position for the core being that which resulted in the null between the two large deflections. Slight variation of the generator frequency on either side of the null should now produce deflections of the tuning meter to the left and right.

To align the front end, first remove the clip from the oscillator coil and set the tuning voltage to the low end of its range. Sweep the generator frequency slowly over the range 80-100MHz when a deflection should be observed on the tuning meter or multimeter. Once this has been located, set the generator to 88MHz and separate or push together the turns on the oscillator coil to produce a maximum deflection again. Then transfer the signal generator to the tuner input and maximise the deflection by adjusting L101, 102, 104. As the signal strength reading increases, the output of the signal generator should be backed off to avoid overloading or oscillator pulling.


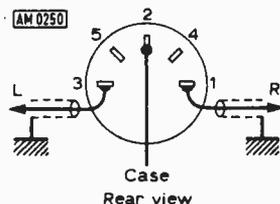


Fig. 9: Audio output connections to match DIN Standard amplifier input socket.

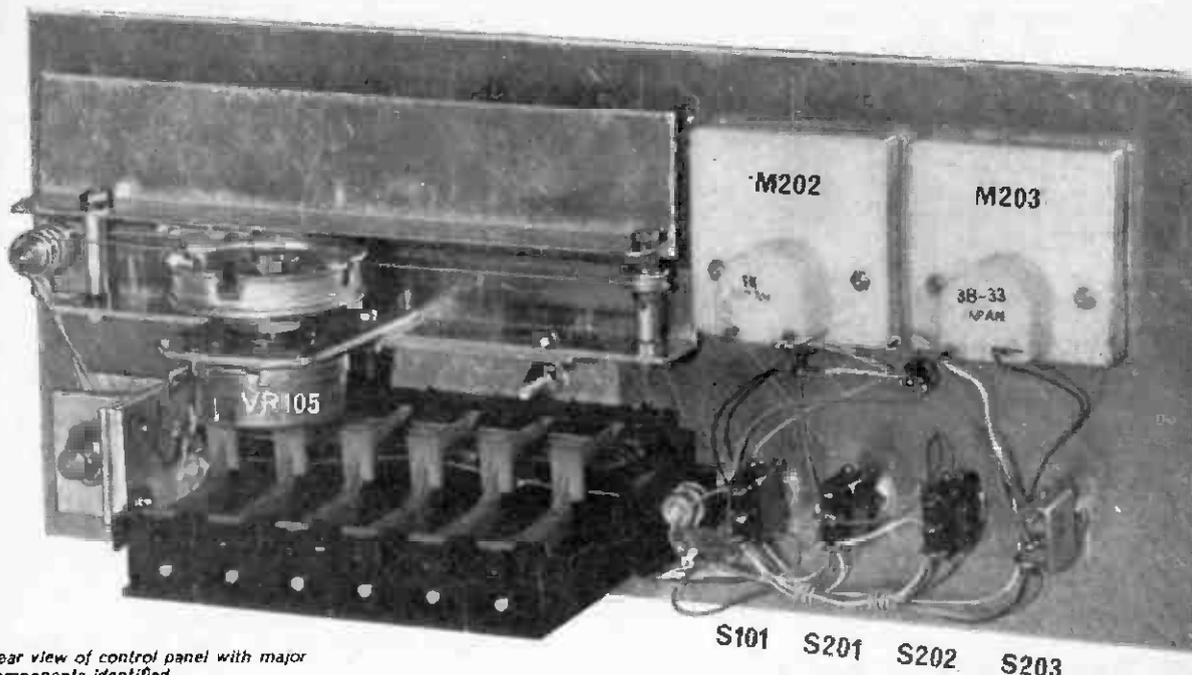

Rear view of control panel with major components identified.

Next change the tuning voltage to maximum, increase the generator frequency to 105MHz and restore its output to 1mV. Vary the generator frequency about 105MHz until a signal strength meter deflection is obtained and bring this to a peak at this frequency by adjustment of VR101-103. The alignment at the bottom end of the scale does not have to be altered as the two adjustments do not interact when done in the manner described.

## SECOND METHOD

This method may be used by those who do not have access to an RF signal generator. A second FM tuner, which must have an IF of 10.7MHz and a tuning meter, is used both as a signal generator and as a monitor to check the frequency of the local oscillator of the tuner which is being aligned. Connect a loop of wire to the aerial input of the second tuner and place it in the proximity of the oscillator of the first. Set VR105 to its low-voltage end and adjust L106 until the local oscillator appears as a carrier at 98.7MHz on the scale of the second tuner.

Now reverse the situation with the wire loop feeding the first tuner and the second tuner set to 88MHz. Adjust the tuning control of the first tuner until the tuning meter (or a multimeter connected as in the previous section) gives a deflection, indicating that the local oscillator of the second tuner is being received. L105 is now adjusted to maximise the response and L202 is adjusted as described in the previous section.

It now remains to align the RF circuits. Disconnect the wire loop and connect a good FM aerial. The sensitivity of the tuner is such that some stations will be received even if the RF stages are not correctly aligned. Set VR101-103 to maximum voltage and tune in a signal near the bottom of the band (the local Radio 2 transmitter will usually be the most suitable). Now adjust L101, 102, 104 to produce maximum response on the signal strength meter.

Adjust the presets VR101-103 with a signal towards the top of the band, a local radio station for example.

## DECODER ADJUSTMENTS

The alignment of the stereo decoder is very simple and requires no special equipment. With the receiver tuned to a stereo transmission the core of L203 is screwed in until the stereo indicator illuminates. The lamp will now remain illuminated over a range of several turns of the core and the correct setting is at the middle of this range.


The precision of this setting may be increased by use of the BBC test tone transmissions on Radio 3 each evening after the end of normal broadcasting. These transmissions include a tone in one channel only. With the tuner connected to an amplifier and speakers, the speaker of the channel with the tone should be disconnected and the setting of L203 varied to give minimum signal in the other channel.

## USING THE TUNER

We would like to conclude this series of articles with a description of the tuner in use so that constructors can check the operation of their receivers and get the best use out of them.

The operation of the tuning meter is straightforward. The centre-zero meter should give a slight deflection to the left (low frequency) with no signal present. As the receiver is tuned through a transmission from the low frequency side the meter will deflect strongly to the left, pass through zero and then deflect to the right. The correct tuning point is at the central zero. For maximum accuracy, tuning should be carried out with the AFC off.

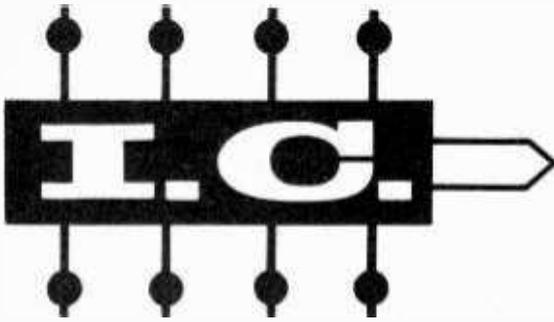If the centre-zero tuning meter is omitted from the tuner the signal strength meter may be used as a tuning indicator by simply tuning for the maximum deflection. This method is, however, not as accurate. Table 4 shows the voltage at pin 13 of



# OF THE MONTH

## Number 49      SGS TBA 790 AUDIO POWER AMPLIFIER

**T**HE TBA 790 is an audio power amplifier integrated circuit available in various forms which have absolute maximum voltage ratings of 12, 15 and 18V and respectively providing maximum output powers of 1.2, 2.2 and 3.45W into an 8 ohm loudspeaker.

### The TBA 790KSD

In this article we will discuss the TBA 790KSD device which has an 18V, 3.45W rating, having the type of encapsulation shown in Fig. 1. The bracket is permanently attached to the back of the device, acting as a small heat sink. The bracket contains two holes, tapped 6BA, by which it can be fastened to a larger additional heat sink. For most applications at normal room temperatures the additional heat sink is not required. However, the constructor will often find it convenient to bolt the device to a sheet of metal and this will help to cool it.

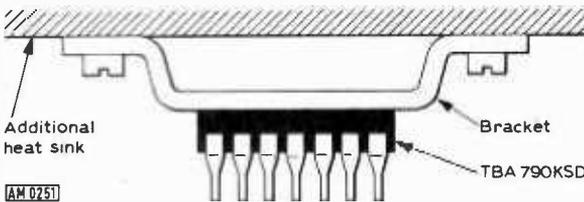


Fig. 1. The integral bracket of the IC provides the normal heat sink for the TBA 790 series.

The pins of this IC are in the quad-in-line configuration, the connections being shown in Fig. 2. Constructors are advised to solder directly to these pins, partly because sockets for quad-in-line devices are not easily obtainable and partly because the use of a socket renders spurious feedback more likely.

### Circuit

A simple circuit for the use of the TBA 790 is shown in Fig. 3. The input impedance of the device itself is very high, typically 50 MΩ, and the circuit input impedance is therefore normally determined by R1. The high input impedance enables the circuit to be used with ceramic record player cartridges.

As the value of R2 is reduced, the amount of negative feedback decreases and the gain rises, being equal to  $8000/R2$ . Thus if R2 is 100 ohms, the voltage gain is 80 or 38dB. R2 should not be less than about 39 ohms where the voltage gain is 200

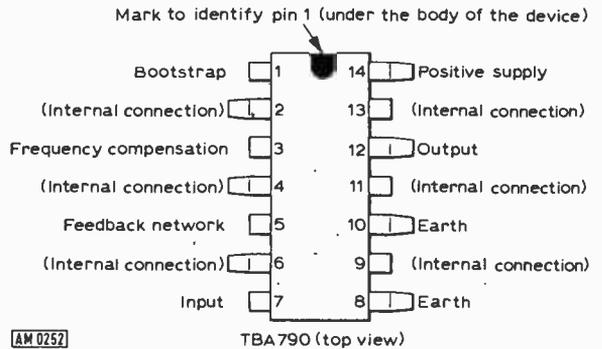


Fig. 2: Pin connections for the TBA 790. The heat sink is omitted for clarity.

or 46dB, since instability is likely at very high gain. The value of R2 should not, generally, be greater than about 200 ohms.

### Frequency compensation

The components C2 and C3 provide frequency compensation. Ideally their values should be chosen according to the graph of Fig. 4, although these values are by no means critical. One should therefore estimate the gain required and then ascertain the value of R2 in Fig. 3. The value of C3 can then be read from the left hand side of Fig. 4 and the value of C2 from the right hand side of Fig. 4.

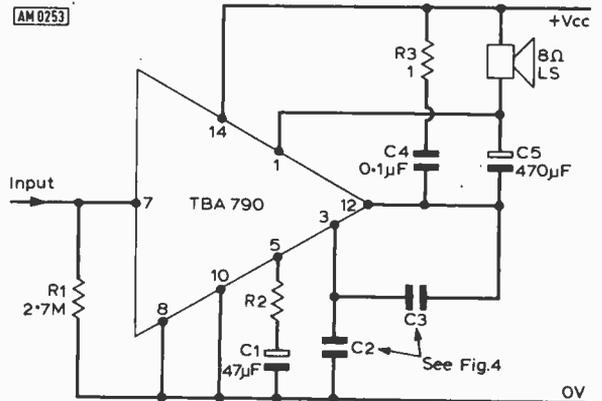


Fig. 3: Basic circuit of the TBA 790 as an audio amplifier.


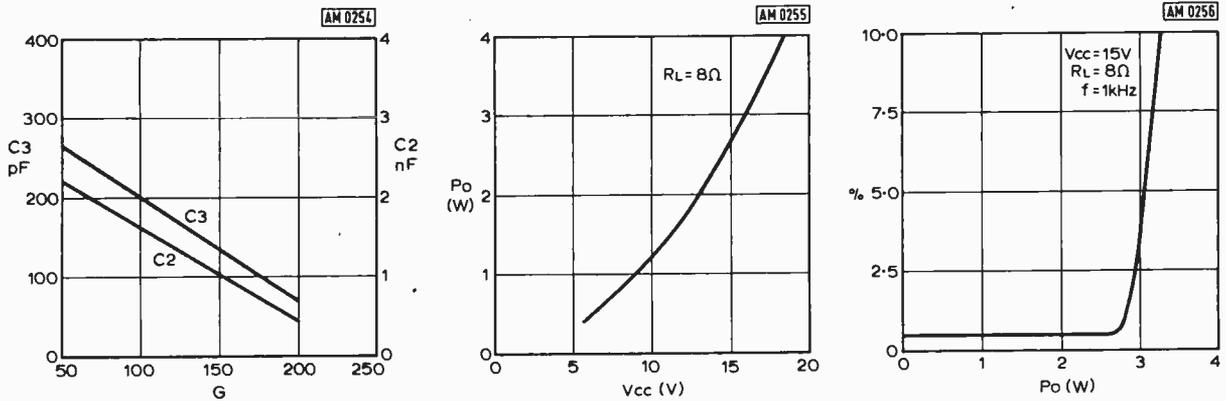


Fig. 4: above, graph for selecting values of C2 and C3 in Fig. 3. Fig. 5: centre, output power related to supply voltage. Fig. 6: right, distortion level at various output levels. Fig. 7: below, is a practical circuit of a radio receiver using the TBA 790KSD and a ZN414.

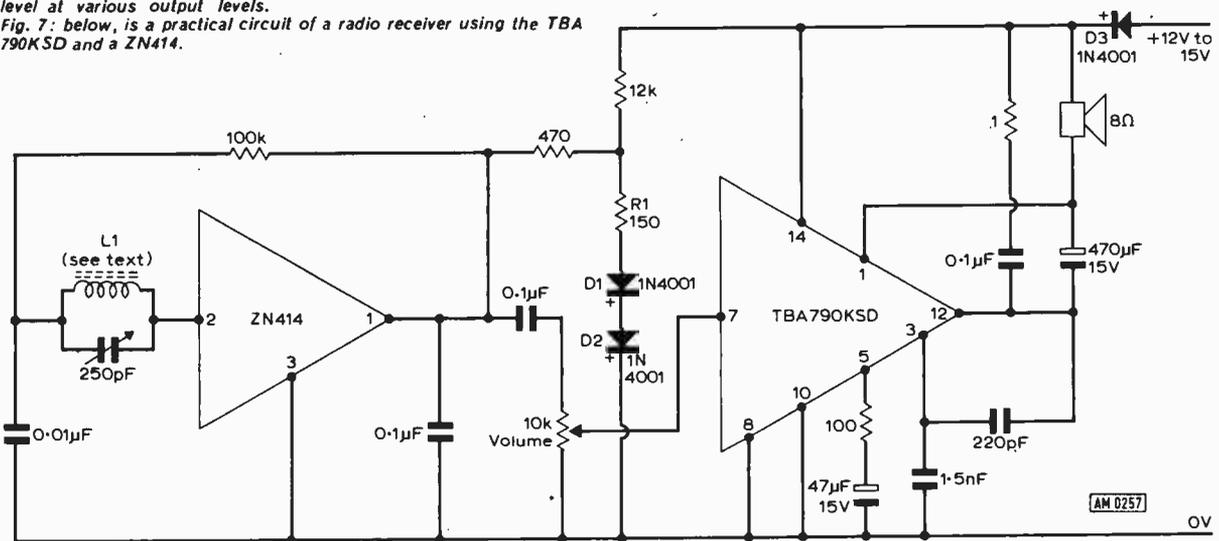

## Power supply

The maximum output power which can be obtained from the TBA 790KSD at various supply voltages is shown in Fig. 5 where an 8 ohm loud-speaker is employed. In general it is wise to regard the maximum power supply voltage as about 16V to allow a small margin of safety.

It can be seen that an output of just under 2W can be obtained when the device is used in a 12V car radio, although more than 2W should be obtainable when the battery is being charged.

The quiescent current is only about 10mA at 15V or 7mA at 10V, but it will rise to around 1 to 3A when 3W is being delivered to an 8 ohm speaker. The efficiency (output power/input power) is typically 65 per cent at the 2.7W level.

The circuit shown has a frequency response which is 3dB down at about 70Hz and at about 12kHz. The use of a capacitor of larger value for C5 of Fig. 3 will extend the bass response, whilst the high frequency response can be altered by changing the value of C2 or C3.

The components R3 and C4 of Fig. 3 compensate for the speaker inductance.

The total harmonic distortion is plotted as a percentage against the output power in Fig. 6 for a 15V supply and an 8 ohm speaker. It can be seen that the total harmonic distortion is fairly constant

at a fraction of a per cent until the power exceeds about 2.6W. It then rises rapidly with the onset of clipping to about 10 per cent at 3.4W.

## Typical use

The writer has used the TBA 790KSD as the output stage of a very simple radio receiver employing the well known Ferranti ZN414. The circuit is shown in Fig. 7. The voltage gain of the audio amplifier has been set at about 80 which has been found to provide good volume. The two diodes D1 and D2 are forward-biased silicon diodes which stabilise the ZN414 supply voltage. If these diodes are replaced by a resistor, the receiver will not function satisfactorily over a range of supply voltages. The gain of the ZN414 circuit can be adjusted by altering R1, reducing it in value or removing it altogether if the ZN414 stage oscillates.

The diode D3 in the supply lead is included to prevent the destruction of the TBA 790 if the power supply is accidentally connected with the wrong polarity. It may be omitted if desired.

The coil L1 consisted of about 80 turns of 28 SWG enamelled copper wire close wound on a 4in. long ferrite rod. A long-wave coil of around 220 turns of much finer wire could be placed at the other end of the rod and switched into circuit to replace L1 if long wave reception is required.

# EXPERIMENTAL WORKSHOP

M. J. HUGHES M.A.

## LEARNING BY PRACTICAL PROJECT STEPS

### PART 13—PHASE SHIFT CIRCUITS

**T**HERE is more to a top cut filter than an attenuation factor, as described last month. Apart from the potential divider effect of the resistor and total circuit impedance on the input voltage, the circuit introduces what is called **Phase delay**. This means that when a sine wave signal is applied to the input we will see an attenuated sine-wave at the output but the peaks and troughs of the wave will not occur at the same instances of time. To confuse the issue, the time discrepancy between input and output depends on the frequency of the signal we apply. This is not an easy feature to demonstrate without an oscilloscope but we hope the following experiment, coupled with a bit of thought, might clarify the situation a little.

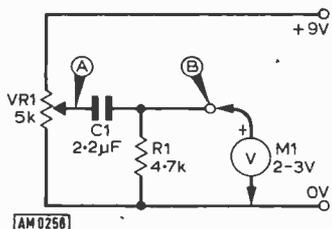


Fig. 90: Experiment to show phase shift in a top cut filter.

In Fig. 90 we shall simulate an AC input signal by moving the wiper of VR1. Because we are limited to slow movements (low frequencies) we shall have to use a suitable high value capacitor for C1 so that useful signals can be measured on the meter M1. This meter must be sensitive, 20,000 ohms per volt, and switched to a low DC voltage range, about 2 or 3 volts. The voltage at "A" will be set by the potentiometer and can be anything in the range of 0 to +9V. We can, with a bit of manual dexterity, make this voltage follow a near sinusoidal pattern; to do this, start with the wiper at minimum voltage and rotate it, slowly at first, reaching a maximum speed of rotation at the half way point, then start to slow down gently until you reach the top end of its track. You should aim to slow down progressively, so that you don't suddenly stop when you reach the top. Having reached the top, peak positive voltage, immediately start turning the knob the other way, slowly at first, speeding up to the halfway point and

then slowing down as you reach the bottom end, again without an abrupt stop. This needs a bit of practice but it is not as difficult as it might at first appear. If you manage to do this satisfactorily the voltage at the wiper should approximate to a sine wave and if repeated over and over again should produce a waveform something like that shown in Fig. 91.

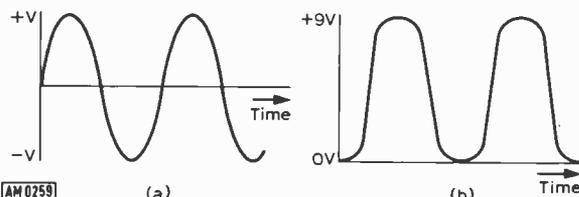


Fig. 91: (a) Ideal sine wave oscillating about zero volts. (b) Approximate waveform from Fig. 90, oscillating between zero and +9V.

The thing to do now is to monitor the voltage at point "B" on the circuit as you go through the "sine wave" cycle. Initially make the cycle stretch over about two seconds and watch the meter stretch closely. During the slow portion of the rising waveform the meter will read virtually nothing but as you speed up at the halfway point the meter voltage will rise. As you pass the halfway point and slow up towards maximum you should see that the meter voltage

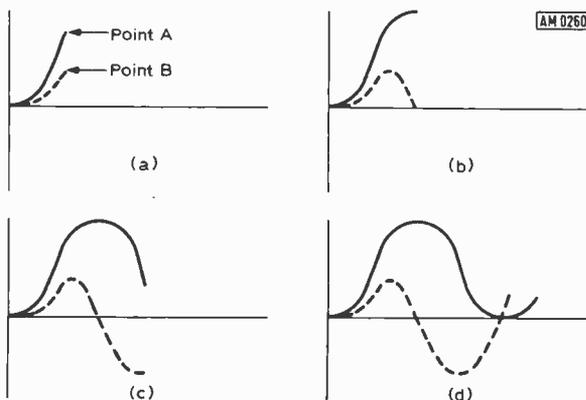


Fig. 92: Progressive construction of waveform obtained in Fig. 91 (b).

starts to fall back to zero and reaches zero just as you reach maximum voltage. The voltage you see on the meter should be proportional to the rate at which the input signal was changing. If you had an oscilloscope the output voltage would trace out the line shown in the progressives of Fig. 92.

When you turn the potentiometer in the opposite direction, describing the negative half of the input sine wave, the meter will try and read backwards so reverse its leads and you will find that a similar effect is produced in a negative direction. If you repeat this cycle many times you can imagine that the voltage at point B has the same sinusoidal shape as that at A but it is reduced in amplitude (attenuation by top cut filter action) and it reaches a positive peak as the input voltage is going through the centre part, the fast moving part, of its positive going swing. The voltage at B is zero when A is peak positive, maximum negative when A is moving in a negative direction and zero again when A is at its peak negative, zero volts, level. The final trace in Fig. 92 clearly shows that the voltages at B are out of step with those at A by a quarter of a wavelength.

Because a complete wavelength of a sinewave is a cyclic event we sometimes say it corresponds to a  $360^\circ$  cycle hence we can say a quarter of a wavelength is  $90^\circ$ . Using this nomenclature we can say there is a  $90^\circ$  phase shift between the input and output signals for this circuit, at the low frequencies we are considering.

If you had a signal generator instead of a potentiometer as an input signal and a double-beam oscilloscope monitoring the voltages at A and B you would see this more clearly. You would also see that if the frequency of the input signal were increased the amplitude of the output would increase but the phase shift would also start to reduce. As the input signal frequency becomes very high the phase difference approaches zero and the output becomes an almost exact replica of the input, both in phase and amplitude.

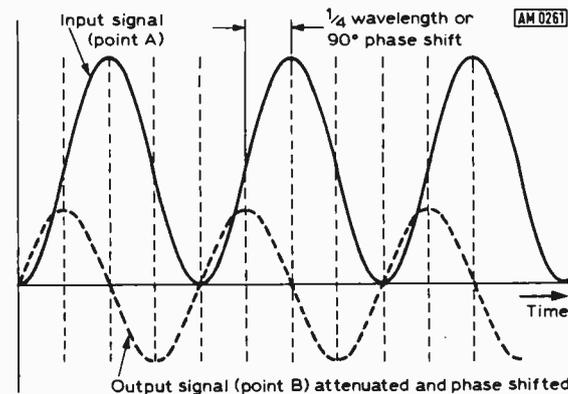


Fig. 93: Curves showing  $90^\circ$  phase shift of LF signal through top cut filter.


We can thus say for a top cut filter:—

1. At very low frequencies we get  $90^\circ$  phase shift and heavy attenuation, Fig. 93.
2. At very high frequencies we get no phase shift and little attenuation.
3. At intermediate frequencies we get a graded scale of phase shift (between  $0^\circ$  and  $90^\circ$ ) and graded attenuation, depending on the frequency we choose, and, of course, on the values of the components in the filter.

This phase shift effect can be put to good service in certain types of oscillators. To obtain oscillation all we need is an amplifier with frequency selective positive feedback. This means that we have to take the output of the amplifier and at a certain frequency feed it back to the input with a phase relationship that enhances the output.

We have seen several examples of the opposite effect in amplifier stages, previously described in this series. Negative feedback was achieved by feeding the signal from the collector of a transistor back to its base. A single transistor stage, in grounded emitter configuration, has  $180^\circ$  phase shift between its input and output, when the input moves positive the output moves negative and vice versa. To get positive feedback we must arrange to feed back a signal that is in phase (i.e. having zero or  $360^\circ$  or any multiple of  $360^\circ$  phase shift).

One simple way of doing this is to use two transistor stages, one cascaded into the next. The output of the second stage will be  $360^\circ$  out of phase with the input to the first and this is equivalent to there being no overall phase shift. If we feed the output signal back to the input the circuit will oscillate at a frequency set by any frequency dependent components, capacitors or inductors, that form part of the loop, from input to output and back to the input again. If there are no such frequency sensitive devices and the amplifier is DC coupled then the oscillator becomes locked in one or two possible states (it tries to oscillate at zero frequency!!). This circuit is, in effect a bistable which has been described in a previous part.

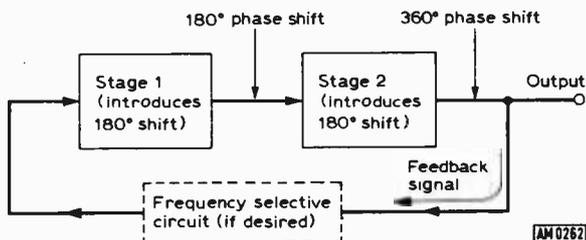

This block diagram shows concept of an oscillator, producing zero phase shift, gain and frequency selective feedback.

For regenerative feedback to occur, a pre-requisite for oscillation, it is necessary for the gain of the amplifier to equal or exceed any signal losses in the feedback path. Positive feedback alone is not sufficient. We can turn the two transistor stage into a free running oscillator as shown in Fig. 94. The capacitors determine the frequency and, if looked at from a different view point, this circuit is very similar to a free running (astable) multivibrator. Changing the value of the capacitor in the feedback loop changes the frequency of oscillation; you can try this and, with the values given, the frequencies should be in the mid-audio range. Layout shown in Fig. 95.

If we accept that we can get  $90^\circ$  phase shift from a simple RC filter it might seem that two such filters cascaded into one another Fig. 96(a) would give us  $180^\circ$  phase shift. This would be true of signals of zero frequency but, apart from zero frequency being a rather impracticable concept when dealing with oscillators, the attenuation would be infinite and no measurable signal would be seen at the output. If, however, we extend the logic a little and consider three such filters connected together (Fig. 96(b)) there will be a specific frequency that undergoes  $60^\circ$

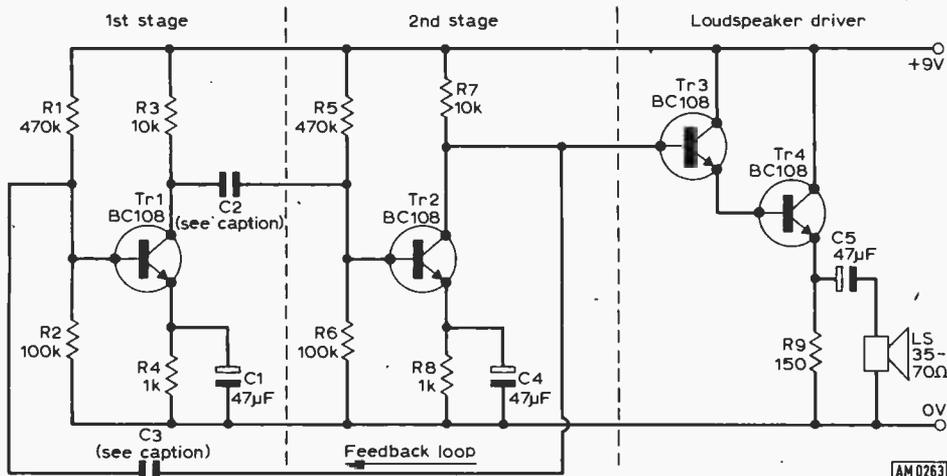


Fig. 94: Two stage amplifier converted to an oscillator, frequency being determined mainly by C2 and C3.

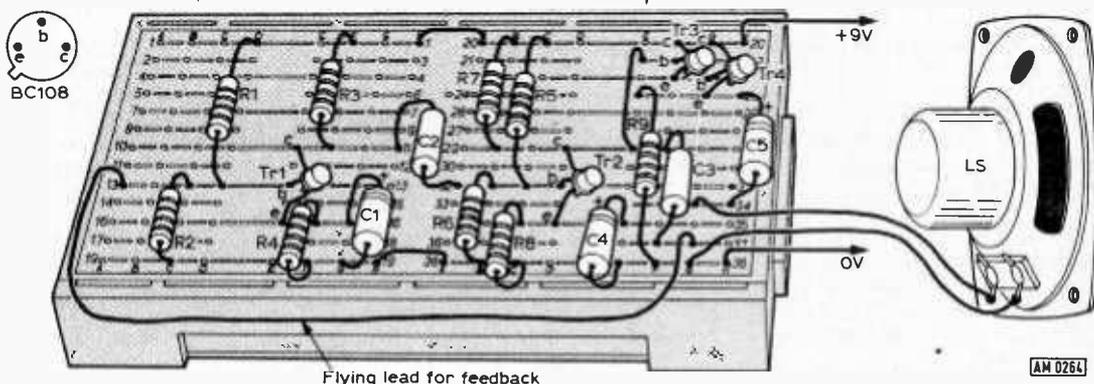


Fig. 95: Layout for Fig. 94. Try values of 1000pF to 0.47µF for C2 and C3 in any combination.

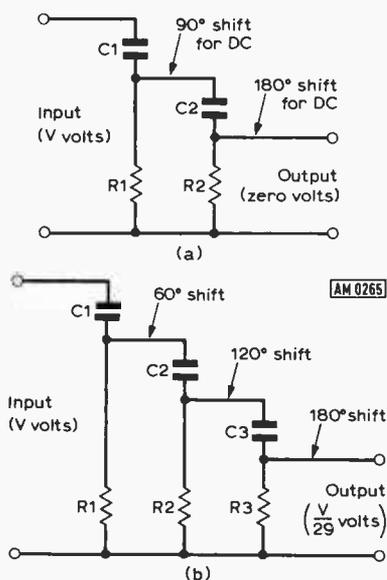


Fig. 96: (a) Two stages cascaded as shown will give theoretical 180° phase shift at zero frequency. (b) With three stages each stage will give 60° shift at a certain frequency giving 180° shift overall.

phase shift through each of the three stages. Three lots of 60° shift give 180° shift overall but this time we are no longer dealing with zero frequency; it will be a finite frequency and although there will be considerable attenuation it will certainly not be infinite and we can guarantee at least some measurable signal at the output for this particular frequency.

It can be shown that if each of the resistors in the three stage filter have values R (in ohms) and the capacitors are of equal value C (in farads) the frequency that is subjected to 180° phase shift is given by:—

$$f = \frac{1}{2.7CR\sqrt{6}}$$

Because of the inter-relationships of impedance, reactance and frequency the attenuation for this circuit at this particular frequency is always a factor of 29.

We can now conceive using this network to replace the second transistor in our experimental circuit, to give 180° phase shift instead of the second transistor and simultaneously determine the frequency at which this phase shift occurs. By using this network in the feedback path of a single transistor stage we should be able to get regenerative feedback at a predetermined frequency provided that the voltage gain of


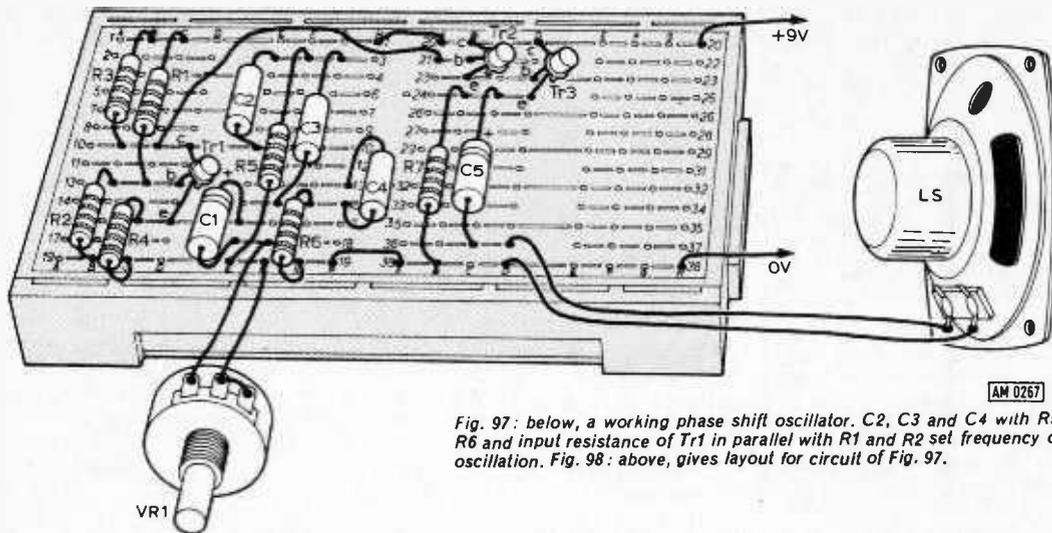


Fig. 97: below, a working phase shift oscillator. C2, C3 and C4 with R5, R6 and input resistance of Tr1 in parallel with R1 and R2 set frequency of oscillation. Fig. 98: above, gives layout for circuit of Fig. 97.

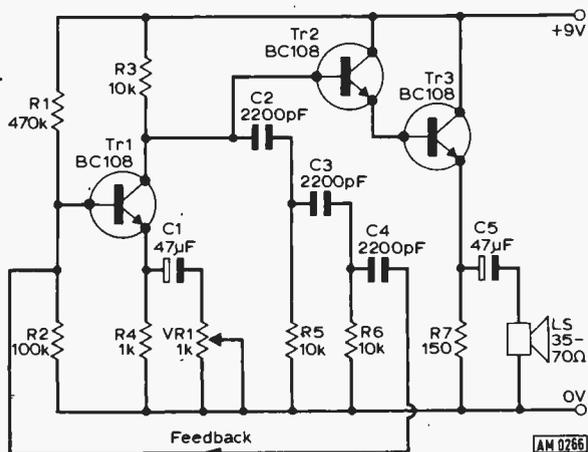

the single transistor stage exceeds 29. Ideally the gain of the amplifier should be greater than, but as near to 29 as possible, otherwise clipping will occur and providing the gain is just right the oscillator will produce a very pure sinusoidal output waveform. VR1 introduces a controllable amount of negative feedback and thus sets the gain of the amplifier, Fig. 97. Start with this set to maximum resistance and no oscillations will be heard in the loudspeaker; as it is reduced in value a pure note will be heard and reducing its value to zero will provide zero negative feedback, maximum gain, and some distortion might be heard in the loudspeaker as clipping starts to occur. The latter effect will depend on the transistor latent gain. Layout is given in Fig. 98.

This is a very useful and simply made oscillator for audio and sub-audio frequencies and is sometimes used for generating low frequency vibrato signals in electronic organs as it has a comparatively pure signal content. The only problems are that the gain of the amplifier needs setting carefully for optimum performance and that it is rather difficult to change its frequency of operation with a variable control. Small changes in frequency can be provided by varying the value of one or two of the resistors in the feedback loop by small amounts. The best way of setting the frequency to a predetermined value is

to leave the resistors fixed and substitute different sets of capacitors in the feedback circuit.

Phase shift has many other useful applications in electronics and it can be obtained in other ways. Under some circumstances it can be detrimental and is sometimes encountered unexpectedly in audio amplifiers giving rise to undesirable spurious oscillations.

**Next month: Some more applications of positive feedback.**

**P.W. SANDOWN**—continued from page 735

IC201 measured for various signal strengths for a typical tuner. This information may be used to calibrate the signal strength meter if required, although quite wide variations can be expected between tuners.

With the muting or squelch switched off there is considerable inter-station noise and the usual distorted output as the signal enters the edge of the tuner passband. With the squelch in operation the background should be silent until a noise-free signal is received. It should normally be left on unless a weak signal is being received.

TABLE 3 Filter centre frequencies		TABLE 4 Signal strength meter indication	
Colour code	Centre frequency (MHz)	Voltage at Pin 13, IC201 (v)	Approx. signal level at aerial socket
Orange	10.625	0.15-0.3	0
Yellow	10.665	0.4	1μV
Green	10.700	1.3	10μV
Blue	10.735	2.0	100μV
Violet	10.775	3.0	1mV
		4.6	10mV

The stereo defeat facility automatically inhibits the decoder when the signal falls below the level required for noise-free stereo. Alternatively the tuner can be held in the mono or the stereo mode independent of the signal level by moving the mode switch R203 to the appropriate position.

# PRODUCTION LINES

colin riches

## EKCO ZU540

Sound Project ZU540 from Ekco is a tuner-amplifier/turntable/Dolby cassette tape recorder unit.

The Dolby noise reduction system operates on both record and play-back. The v.h.f. varicap tuner employs 4 push-button pre-selectors plus free tuning and a built-in stereo decoder with beacon indicator.

The transcription-type 2-speed record player uses a Philips GP400 magneto-dynamic cartridge with a 15 micron diamond stylus.

There is a facility for using chrome dioxide tapes on the recorder and there is an automatic level control with a manual override.

An electronic tape-end auto stop allows for automatic 'pop-up' disengagement of the cassette keys.

Output power is quoted as 20W per channel into 4Ω.

I have tried out this unit and found it to give excellent quality reproduction through the DX181 speakers which come with the system.

I cannot give full details of the impressive specification in the limited space I have here but please write to Pye Limited, P.O. Box 49, Cambridge if you would like further details.

## BANISH THE IRON!

Banish the soldering iron—that's what Radio and TV Components have done with their latest car radio kit.

All the electrical connections are made through colour-coded press-on tags and R and TV Ltd. claim that a complete novice can build it in under two hours.

The "Tourist TT" has five push-buttons which can be tuned to any pre-selected station. Four operate on m.w. and one on l.w.

This new radio kit developed from the firm's very successful and efficient "Tourist" radio, utilises an i.c. and a p.c. board allied to tested sub-assemblies. Constructing the kit is simply a matter of fixing the

various component assemblies to the chassis using the screws provided.

The kit features permeability tuning and long-wave coils to ensure good sensitivity and selectivity on both bands. The r.f. sensitivity at 1MHz is said to be better than 15μV and power output into a 3Ω speaker is claimed to be better than 4W.


Both the tuner and the i.f. module are pre-aligned and the kit is suitable for 12V positive or negative operation.

The kit comes complete with step-by-step assembly instructions and instructions for installing the radio into the car itself.

This excellent kit is available by post or direct from Radio and TV Components Ltd., 21 High Street, Acton, London, W.3. The price is £7 plus VAT. Postage and packing cost 55p.

Extras available are a speaker with baffle and fitting strips, at £1.65 (post and packing 23p) and a retractable, matched locking aerial for £1.37 (20p postage and packing).

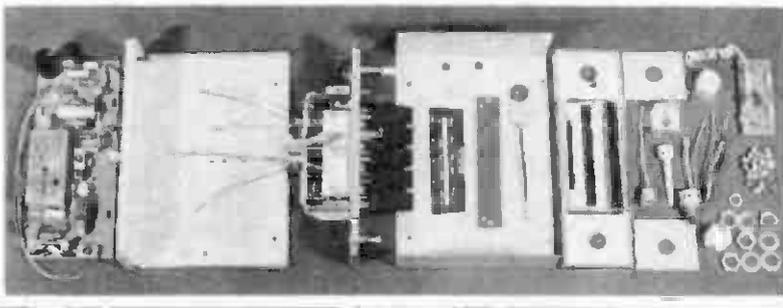We are publishing a Special Product Report on the "Tourist TT" car radio on page 704 of this issue of Practical Wireless.



## COMDEL SPEECH PROCESSOR

The Comdel CSP 11 is a communication aid designed for any system using a microphone for voice transmission. Its prime feature is the achievement of peak limiting without distortion which is the very undesirable by-product of conventional speech clippers. Therefore the average or 'talk power' gain obtained is more effective.

Features of the CSP 11 are: instantaneous limiting action; no appreciable distortion; talk power gain greater than 10dB; optimum frequency response for voice; installs in microphone lead; all silicon solid-state circuitry. The unit costs £55 (including VAT and postage and is available from Interface International, 29 Market Street, Crewkerne, Somerset.

# Henry's

**CASH & CARRY  
PRICES**  
FOR CALLERS or BY POST

G.B. Carr/Pack 15p per item.

- | Ref. No. | Description   | Price           |
|----------|---|-----------------|
| 1        | D1203 Telephone Amplifier—Suction                               | £4.95           |
| 2        | D1201 Telephone Amplifier—Cradle                                | £7.50           |
| 4        | T1206 2 Station Intercomm                                       | £4.95           |
| 5        | T1306 3 Station Intercomm                                       | £9.95           |
| 5        | T1406 4 Station Intercomm                                       | £12.50          |
| 6        | TA1A 2 Station Telephones Intercomm                             | £13.50          |
| 7        | W1.2 2 Station Wireless Intercomm                               | £18.20          |
| 8        | DP303 Door Phone Intercomm                                      | £7.00           |
| 9        | PK3 ETCM your own printed circuits                              | £2.25           |
| 9        | EAC1 Reverberation amplifier                                    | £11.75          |
| 11       | US50 Ultrasonic switch  | £12.75          |
| 12       | XP4002 Photoelectric alarm system                               | £13.50          |
| 13       | Solid state tachometer  | £3.75           |
| 14       | Power dash transistor assisted ignition                         | £13.50          |
| 15       | Car auto lock   | £4.85           |
| 16       | 4 amp 6.12 volt battery charger                                 | £4.50           |
| 17       | FF21 Car radio/tape quad adaptor                                | £4.50           |
| 18       | Fully disappearing car aerial                                   | £2.00           |
| 19       | Electric disappearing car aerial                                | £7.80           |
| 20       | ET (F1009) Morse Code Key/Buzzer                                | £1.70           |
| 21       | VH105 aircraft band converter                                   | £12.95          |
| 22       | LN300 50K Disc mic  | £3.75           |
| 23       | DE50B 50K Communications mic.                                   | £3.75           |
| 24       | Car lighter plug 12v voltage adaptors 300mA (state 5/74/9 volt) | £1.95 ea.       |
| 25       | STC time delay module   | £1.50           |
| 26       | Gravenre 911A photo electric unit (with data)                   | £3.50           |
| 27       | 3 ch. 3 x 1000 watt sound to light                              | £21.50          |
| 28       | 3 ch. 3 x 1000 watt sound to light plus override                | £41.25          |
| 29       | 150 w. light display projector with wheel                       | £23.50          |
| 30       | MM1 (B2005) 4 channel 9 volt mixer                              | £4.20           |
| 31       | MX100 deluxe 4 channel mixer                                    | £6.78           |
| 32       | H57 (G120) Stereo headphone amplifier                           | £10.50          |
| 33       | MP12 6-CH. Slider control mixer                                 | £27.95          |
| 34       | RE 208 stereo phone adaptor                                     | £2.25           |
| 35       | MO802 stereo phones   | £2.20           |
| 36       | CIS200 stereo phones  | £2.75           |
| 37       | CIS 250 stereo phones   | £6.50           |
| 38       | IC1301 and IC1305 stereo phone controls                         | £2.95           |
| 39       | Car stereo speakers in Pods. Special offer                      | £2.95 pr. £0.60 |
| 40       | Crystal lapel microphone  | £1.00           |
| 41       | IO52 car speakers front/rear fader                              | £1.76           |
| 42       | Bib Groove Clean (Ref. No. 42)                                  | £2.20           |
| 43       | Bib Record care kit (Ref. No. 43)                               | £2.20           |
| 44       | Bib cassette recorder care kit (Ref. No. 26A)                   | £1.96           |
| 45       | Bib cassette Tape splicing kit (Ref. No. 24)                    | £1.64           |
| 46       | BA5F reel-reel Hobby Box  | £2.40           |
| 47       | 3000 OHM Headphones   | £1.35           |
| 48       | 4000 OHM Headphones   | £1.35           |
| 49       | Cassette Recorder Mic. (2 x 3mm Plug)                           | £1.85           |
| 50       | 420 ES Microscope   | £5.70           |
| 51       | UP050 Low cost 9 volt eliminator                                | £2.35           |
| 52       | RE 527K Tape Head Demagnetiser                                  | £1.70           |
| 53       | Cambridge pocket calculator                                     | £16.95          |
| 54       | BC808 % Pocket calculator                                       | £21.95          |
| 55       | BC817 Memory Pocket calculator                                  | £20.95          |
| 56       | BCM 850 % and memory calculator                                 | £33.25          |
| 57       | Sinclair scientific calculator                                  | £26.95          |
| 57A      | Sinclair Cambridge Memory                                       | £23.50          |
| 58       | Antax soldering iron kit (SK)                                   | £3.30           |
| 59       | Bib record care kit (Ref. No. 59)                               | £1.17           |
| 60       | Sp Chassis punch kits   | £5.50           |
| 61       | Longs desoldering tool  | £5.50           |
| 62       | 1 amp line mains suppressors                                    | £2.50           |
| 63       | B551 (E1013) 7 way stereo speaker switch                        | £2.20           |
| 64       | Weller B2000-PK expert 2 in 1                                   | £6.20           |
| 65       | 'S' Dec breadboard  | £1.98           |
| 66       | 'D' Dec breadboard  | £4.29           |
| 67       | 'M' Dec breadboard  | £7.50           |
| 68       | 'T' Dec breadboard  | £1.65           |
| 69       | Instant heat soldering gun                                      | £2.30           |
| 70       | 40 watt soldering iron  | £1.90           |

**TRANSISTORS, VALVES AND SEMI-CONDUCTOR DEVICES - ANY QUANTITIES**  
UK'S LARGEST STOCKISTS

**FREE NEW '74/75 SEMI-CONDUCTOR AND VALVE LISTS**  
Ref No. 36  
on request

## ELECTRONIC COMPONENTS

(Post/Packing 15p Per 1-6 items GB unless stated)

- Ceramic Filters**  
Miniature 10.7 MHz filters 40p pair.  
**IC IF Unit**  
CA3089 10.7 MHz IC £2.94  
Sinclair 6 w. IC IC12 with data and PC board £2.10  
**Radio IC Chip**  
ZNA14 Radio IC with circuit £1.20  
**Stereo Cassette Tape Head Replacement** for most recorders £2.20  
**Scrobe Tubes**  
ZFT8A (limi. lar to 4A) £4.00  
ZFT12A £5.00  
7 segment indicator a 3015F with data £1.78 ea  
Spring delay units  
HR42 9" twin spring £3.30  
pp 20P HR16 5" twin spring £6.95 pp 25p  
**IC Clock**  
MM 531 single chip clock with CCT £9.00  
**Ultrasonic transducers** with data/circuits £3.90 pr

- Fibre optics**  
0.01" diam. mono filament £5.50 per 100 metres  
0.13" diam. 64 fibres £1 per metre  
15m diam mares tails £10.50 each  
**Radio Control XTALS**  
Matched pair for 465 KHZ IF £2.00 pr. for all supernet trans. RX's  
**Handsets**  
Lightweight telephone handsets brand new complete with diagrams for intercomms £3.00 pr.  
**MARROT TAPE HEADS**  
'17' High Impedance £2.50  
'18' Med. Impedance £3.50  
'36' Med. Impedance £3.00  
'63' 2 track mono. High Imp. £1.75  
**Erase Head for '17' '18' and '36'** 75p  
'43' Erase Head for '63' 75p  
**Stereo Cassette Head** £1.20  
**Bosen UK290 Erase** £1.50  
(Post. etc. 15p any quantity)

## TEST EQUIPMENT MULTI-METERS

- (Carr./packing 35p)  
U4324, 20kV with £12.50  
steel case £9.25  
U435, 20kV with £8.75  
steel case  
U4313, 20kV with steel case £12.50  
U4317, 20kV with case £14.50  
U4319, 33kV + transistor tester steel case £10.50  
Accessories  
U4323, 20kV plus 1KHZ OSC with case £7.70  
ITL-20kV/V slim type £5.95  
TP55N, 20kV (Case £2.00) £8.25  
TP105 2kV/V £6.25  
TW205 20kV/V £10.00  
TW50K 50kV/V £11.25  
EP10K 10kV/V £9.95  
AF105 50kV/V Deluxe (case £1.90) £9.95  
S100TR 100kV/V Plus trans. tester £22.50



- General Test Equipment**  
(1 carr./pack 50p. \*c/p 30p unless stated)  
**New Revolutionary Supermeter 680R**  
680R Multi-meter £19.50  
Accessories  
Transistor tester £11.00  
Electronic volt. £18.00  
Ampclamp £11.95  
Temp. probe £11.95  
Gauss meter £11.95  
Signal injector £5.95  
Phase Sequence £5.95  
EHT Probe £5.95  
Shunts 25/50/10A £4.50  
3100 IMA Stripchart recorder £44.00  
TE40 AC Multi voltmeter £19.75  
TE15 Grid dip meter 440KHZ-20MHz £19.95  
TE65 28 Range valve voltmeter £22.50  
TK26D RF Generator 120-KHZ 500MHz £14.95  
TK220 AF Gen 20MHz-200KHZ £19.95  
\*HM35 In circuit transistor tester £19.50  
\*C3025 Deluxe meter 1-300 MHz £40.95  
\*TT145 Composite transistor tester £14.75  
TC1-36 R/C osc. 2MHz-200 KHZ £19.75  
\*C3042 SWR Meter £3.75  
\*SE350A Deluxe signal tracer £12.95  
\*SE400 Mini-lab all in one tester £15.50  
C1-5 Scope 500,000 KHZ (carr. £1) £41.00  
\*C3043 5 CH F/A meter 1-100 MHz £5.75  
Resistance sub box / Post. etc. / £2.40  
Capacitor 20p £2.10  
2 amp var. transformers (carr. £1) £6.35  
Radio activity counter 0-10 (carr. £1) £6.95



## QUALITY CASSETTE TAPES

- "Living Sound" made specially for Henry's by EMI Tapes Ltd.  
5 screw type with library case Post paid (GB)  
C60 3 for £1.10 6 for £2.00 10 for £3.15 25 for £7.50  
C90 £1.47 £2.85 £4.65 £11.37  
C120 £1.83 £3.54 £5.60 £14.00



## SPECIAL OFFER CASSETTE STORAGE

- Rotating unit up to 32 cassettes stackable £3.60 pp 15p  
Car unit with bracket for 10 cassettes £2.00 pp 10p

## ELECTRONIC COMPONENTS & EQUIPMENT

(Please enclose large SAE)

More selection - bigger stocks of electronic components and equipment for supply purpose. Let us quote for your requirements with all enquiries

## BUILD IT YOURSELF

- MW/LW Portable radio ET-98 pp 12p  
MW/LW Radio tuner £5.25 pp 20p  
9 volt regulated power supply £2.15 pp 15p  
15 watt inverter £5.20 pp 30p  
40 watt inverter £6.40 pp 40p  
Sinclair micromatic radio £3.25 pp 15p  
Sinclair Cambridge Calculator £13.84 post paid

## MULTI-KITS

- Ready to use and use again. Educational and practical. All transistor circuits with full handbooks.  
10 in 1, 10 projects £5.95 Post 20p  
50 in 1, 50 projects £13.95 Post 25p  
150 in 1, 150 projects £21.50 Post 30p  
Radicnic X 20, 20 (Elec.) Projects £4.95 Post 20p  
Radicnic X 40 40 (Radio) Projects £9.45 Post 20p


## AMTRON KITS

- 310 Radio control receiver £3.25  
300 4-channel R/C trans £6.61  
345 Superhet R/C receiver £6.61  
65 Simple transistor tester £1.66  
115 Bwatt amplifier £4.50  
120 12 watt amp £4.73  
125 Stereo control unit £6.61  
127 Noise reduction unit £9.55  
157 Private TV loop Trans. £4.95  
130 Mono control unit £4.16  
605 Power Supply for 115 £5.31  
610 Power supply for 120 £5.31



- 615 Power supply for 2 x 120 £6.64  
230 AM/FM aerial amplifier £3.29  
240 Auto packing light £6.90  
275 Mic. preamp £6.99  
525C 120-160 MHz VHF tuner £11.31  
5705 LF Generator 10Hz-1MHz £21.45  
5755 Sq. wave generator 20Hz-20KHz £19.77  
590 SWR meter £9.47  
610 STAB Power supply 6.12v 0.25-0.1A £9.24  
690 DC motor speed Gov. £3.31  
700 Electronic Chaffinch £7.92  
707 Windscreen wiper timer £7.97  
760 Acoustic switch £12.57  
780 Metal Detector (electronics only) £10.91

- 790 Capacitive Burglar alarm £7.92  
835 Guitar preamp £4.99  
840 Delay car alarm £5.99  
875 CAP. Discharge ignition for car engine-Ve Earth) £13.19  
80 Scope Calibrator £2.65  
255 Level indicator £6.98  
525 120-160MHz VHF timer £11.31  
715 Photo cell switch £8.97  
795 Electronic continuity tester £4.97  
860 Photo timer £15.51  
235 Acoustic Alarm for driver £8.61  
465 Quartz XTAL checker £9.90  
220 Signal injector £2.45  
390 VDX £13.62  
432 Testkit £21.83  
670 Battery Charger £7.59

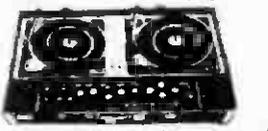

Without doubt UK's best range of modular and complete equipment, lighting, mixing, microphones, accessories, speakers, amplifiers, lenses, etc., etc. FREE stock lists (Ref. No. 18) on request. CALL IN AND SEE FOR YOURSELF AT HENRY'S DISCO CENTRE 309 EDGWARE ROAD 01-723 6963

**8% TO BE ADDED TO ALL ORDERS (Export VAT FREE)**  
**FOR MORE ELECTRONICS SEE BACK PAGE**


# Henry's RADIO

EDGWARE ROAD, W2

**Electronic Centres**  
404-406 Electronic Components & Equipment 01-402 8381  
309 PA. Disco-Lighting High Power Sound 01-723 6963  
303 Special offers and bargains store  
All mail to 303 Edgware Road, London W2 1BW  
Prices correct at time of preparation. Subject to change without notice. E. & O.E.  
All Field Electronics Centres Open 9 am - 6 pm

# A 2 WATT AUDIO IC Amplifier

R.A.PENFOLD

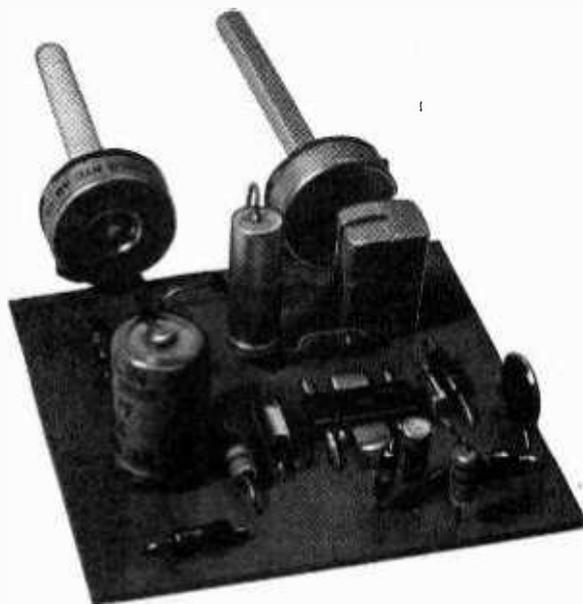

**I**N the medium power range there is now a wide variety of i.c. audio amplifiers available, with power outputs ranging from 1 to 6 watts r.m.s. As with the majority of semiconductor devices, the prices of these have dropped in recent years and most now represent very good value for money.

This article describes an amplifier based on such an i.c., the Motorola MFC9020, which gives a maximum output power of 2W r.m.s. into a 15Ω load. A peak power of about 4W is available. In the configuration used here the device has a typical distortion level of approximately 0.5% at full output at 1kHz, with an input sensitivity of 250mV r.m.s.

The prototype was made for use as a tape recorder monitor amplifier, but as the input impedance is high it is also suitable for use in simple record playing equipment in conjunction with a crystal or ceramic cartridge. With the addition of a suitable preamplifier it would of course be suitable for many other applications.

The unit has built-in volume and simple tone controls. A circuit of a simple mains power unit for the amplifier is provided.

A diagram of the internal circuit of the MFC9020 is shown in Fig. 1. Basically this is divided into two sections. The first four transistors form a differential amplifier while the other five form a fairly conventional complementary class B output stage.

Operation of the differential amplifier is quite simple. For high gain and input impedance this uses two darlington pairs. The first is used in the emitter follower mode, and the output of this stage is developed across the emitter resistor. The second darlington pair operates as a grounded base amplifier to the signals appearing across the emitter resistor. No voltage amplification is provided by the emitter follower stage which provides the circuit with a high input impedance and has a low enough output impedance to drive the grounded base stage. The grounded base stage does provide a degree of voltage amplification.

Neither an emitter follower, nor a grounded base stage provides any phase change to the signal, and so the input to pin 7 is in phase with the output at pin 5. There is a second input to the circuit at pin 8. For an input at pin 8 the second darlington pair will operate as a common emitter amplifier, with the amplified and inverted output appearing at pin 5. Thus pin 7 is a non-inverting input and pin 8 is an inverting input.

## OUTPUT STAGE

This is quite conventional, the only unusual feature being that two transistors are used in the upper section, and three in the lower, rather than the more usual two in each section. The two silicon diodes connected across the two inputs to the two sections of the output stage operate as low voltage zeners, and provide a suitable bias for the output transistors to reduce cross-over distortion to an unnoticeable level. The diodes also provide temperature stabilisation of the output stage.

Under normal operating conditions the output stage is biased to give about half the supply potential at the output (pin 3). The two upper transistors operate as another darlington pair in the emitter follower mode, providing current amplification to positive-going half cycles. The lower three transistors consist of another darlington pair, this time in the common emitter configuration, driven by a pnp common emitter amplifier. There is 100% negative feedback between pin 3 and the emitter of

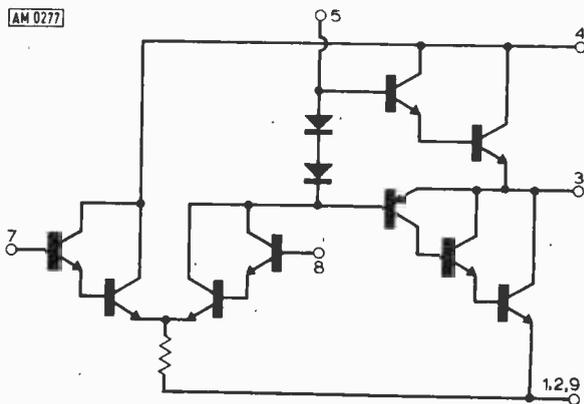


Fig. 1: Internal circuit of the MFC9020.

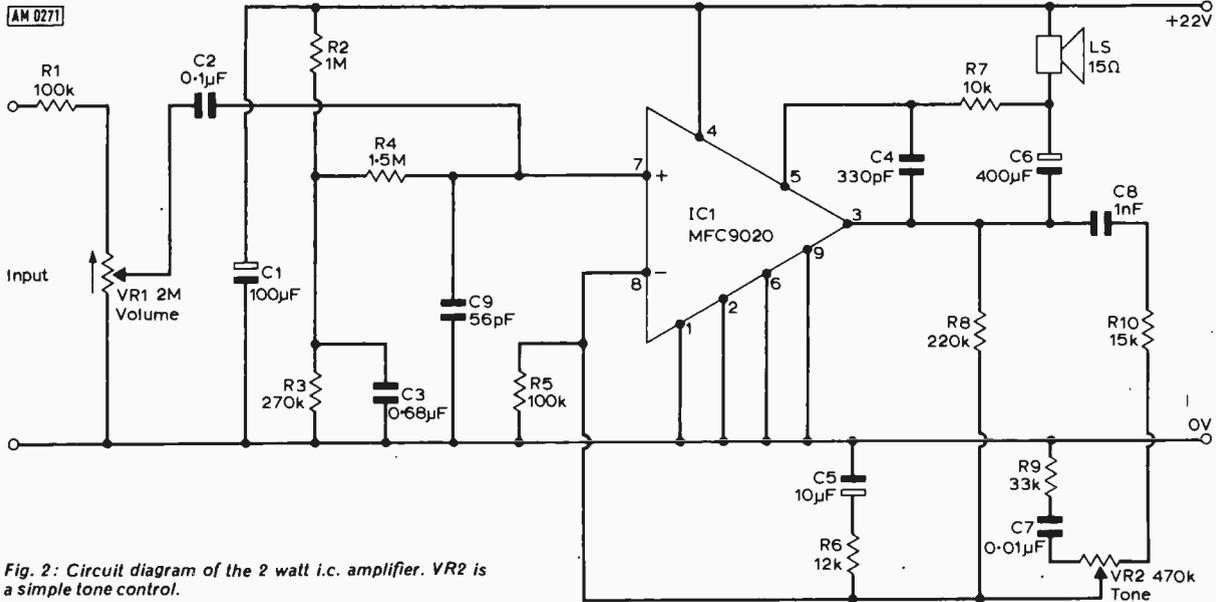


Fig. 2: Circuit diagram of the 2 watt i.c. amplifier. VR2 is a simple tone control.

the first of these three transistors, and this forms what is termed a compound amplifier. Like an emitter follower, a compound amplifier provides no voltage gain, but has a high current gain. It also has the input and output signals in phase. These three transistors amplify negative-going half cycles. Due to the high current amplification of the output stage, the output at pin 3 is at a very low impedance, and can directly drive the loudspeaker via a d.c. blocking capacitor.

## AMPLIFIER CIRCUIT

A circuit diagram of a practical amplifier using the MFC9020 is shown in Fig. 2. The input is taken via R1 to the volume control, VR1. C2 couples the signal from here to the non-inverting input of the i.c. This input is biased via R4 from a potential divider across the supply, R2-R3. C1 and C3 are decoupling capacitors.

The inverting input is biased from the output of the i.c. by the potential divider, R5-R8. This introduces negative feedback and helps to give a stable biasing arrangement, though it seriously reduces the sensitivity of the circuit. C5 and R6 are therefore used to decouple some of the a.c. feedback and so provide increased sensitivity.

A simple treble boost and cut tone control is provided in the feedback network. This consists of VR2, C7, C8, R9, and R10. With the slider of VR2 towards the right, R10 and C8 are in effect shunting R8. The impedance of R10-C8 is frequency dependent, and reduces as frequency increases. The negative feedback in the circuit will therefore increase with frequency, causing the response of the amplifier to drop at high frequencies. With VR2 in this position the circuit is given top cut.

With the slider of VR2 at the other end of the track, C8 and R10 are in effect cut out of circuit due to the high value of VR2. However, R9 and C7 are now shunted across R6 and C5. Again, the impedance of these will be frequency dependent, but as they are connected across the other section of the potential


divider, the feedback will be increased as frequency increases. This gives treble boost. R9 and R10 are required to limit the effect of VR2 to a certain extent, in the interest of good stability.

Capacitors C4 and C9 are required for good stability. C6 couples the output to the loudspeaker. R7, which is the load resistor for the differential amplifier, is connected to the positive supply via the L.S. so as to give bootstrapping to the circuit.

The input impedance of the amplifier varies with the setting of VR1, but is about 2.1MΩ at minimum sensitivity, reducing to about 700kΩ at maximum sensitivity.

## ★ components list

AMPLIFIER	
<b>Resistors, 1/4 watt, 5%</b>	
R1 100kΩ	R6 12kΩ
R2 1MΩ	R7 10kΩ
R3 270kΩ	R8 220kΩ
R4 1.5 MΩ	R9 33kΩ
R5 100kΩ	R10 15kΩ
VR1 2 MΩ log.	VR2 470kΩ lin.
<b>Capacitors</b>	
C1 100µF 25v	C5 10µF, 10V
C2 0.1µF	C6 400µF, 25V
C3 0.68µF	C7 0.01µF
C4 330pF polyester	C8 0.001µF polyester
	C9 56pF polyester
<b>Miscellaneous</b>	
Motorola MFC9020 (available from SCS Components); Materials for p.c.b., 15Ω loudspeaker, rated at 2 Watts r.m.s. or more; Wire, solder, etc.,	
<b>POWER SUPPLY</b>	
R11 390Ω, 1/4W, ±10%	C9 1000µF 50V
C10 500µF 25V	T1 MJE340 D1-D2 1N4001 D3 22V, 1W zener.
T1 Mains transformer 20-0-20V 250 mA secondary.	S1 d.p.s.t. F1 250mA.

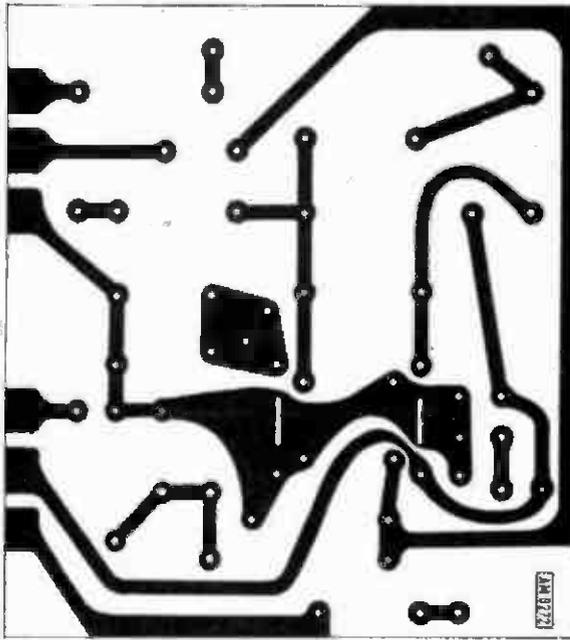

## CONSTRUCTION

A printed circuit board measuring  $3\frac{1}{4} \times 3$  in. is used and this carries all the components except the loudspeaker. Fig. 3 shows the pattern of the copper side of the p.c.b., and also the drilling points. Fig. 4 shows the component layout on the board.

The integrated circuit requires two  $\frac{1}{4}$  in. long slots in the p.c.b. into which its heat tabs fit. These are cut using a coping saw or a fret saw. Although potentiometers with pins which fit into p.c.b. mounting holes are manufactured, these would not seem to be widely available to the amateur, and this p.c.b. has therefore been designed to accept ordinary potentiometers with tag connections. The tags are taken under the edge of the p.c.b. and soldered to the copper backing.

## POWER SUPPLY

The amplifier requires a supply of approximately 20-22V. As the i.c. has a maximum supply voltage rating of 24 volts, it would be difficult to find a suitable unregulated power supply circuit considering that the amplifier has a class B output stage. This is because the supply should not rise to more than 24V under quiescent conditions, with a current con-


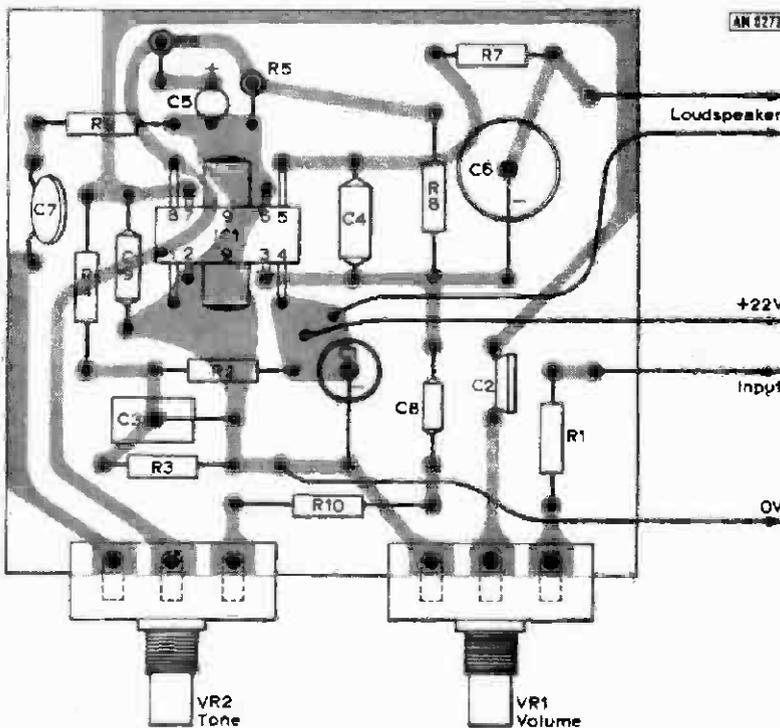


Fig. 3: above, shows the PCB layout actual size. Note that this is turned through  $90^\circ$  compared with Fig. 4.

Fig. 4: left, shows the layout of components on the PCB. The tags of VR1 and VR2 are soldered to the underside of the board.


Fig. 5: below, is a circuit of a suitable stabilised mains power supply unit for the amplifier.

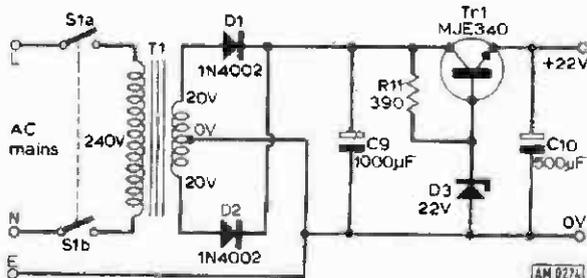

sumption of perhaps only 10mA, and yet maintain about 21 volts under full load conditions with the current consumption peaking as high as 500mA.

It is more practical to use a simple stabilised circuit as shown in Fig. 5. This is a fairly standard configuration, using a zener diode stabilisation circuit feeding an emitter follower. This uses few components, and can easily be constructed on a small tagstrip or connector block. The MJE340 can be mounted on a strip of aluminium which will act as a heat sink and can be bent to form a suitable mounting bracket for the component.

# GOING BACK...

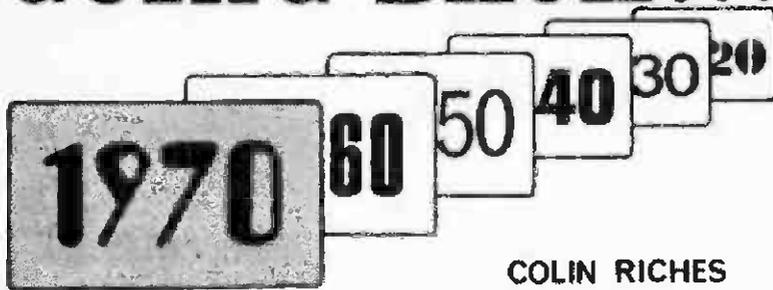

COLIN RICHES

## Story of the P.S.U.

WHILE reading through one of my favourite vintage radio reference books, the BBC Year Book of 1930, I noticed a page devoted to telling listeners about power supplies for their receivers. It certainly was intended as a serious article then but these days one cannot help but smile when one reads about a BBC warning on making a direct connection between a receiver and the mains supply. So, below are a few pointers which listeners should have taken note of in the days 10 years or so before World War II.

"No receiver can give really good quality reproduction if the power supply to it is inadequate. Since broadcast receivers first came into use by the general public there has been a tendency to gradually increase the power supply to the last stage of amplification. Electric light supply mains provide a constant and convenient source of power for wireless re-

ceivers, but in no circumstances should the mains be connected direct to the receiver without the use of an intermediary mains-unit.

A year ago, the BBC drafted a pamphlet which describes the many ways in which electric light supplies can be utilised for wireless receivers. The publication of this pamphlet has been delayed owing to the fact that a number of bodies, such as the Institution of Electrical Engineers, the British Engineering Standards Association and the Radio Manufacturers' Association, are all interested in its contents and the BBC naturally is anxious to conform with their views and wishes. It will however be published as soon as possible.

The BBC wishes to take this opportunity to warn listeners most seriously against the direct connection of their receivers to supply mains, and also strongly recommends that no listener who is unacquainted with handling power and electric light circuits


should attempt the home construction of a mains-unit. It is a far more difficult matter to build a safe and satisfactory mains-unit than it is to build a valve receiver. Owing to the danger to life if a number of improperly designed and constructed mains-units come into use by the listening public, the Institution of Electrical Engineers, in collaboration with the other bodies concerned, has drawn up a set of regulations which governs the use of electric power supplies to wireless receivers. One set of regulations, by the I.E.E. has already been published but new and more detailed regulations are now under consideration. These new regulations, if agreed, will be written in formal technical language and it is thought that many listeners will not be able to follow them conveniently. It is therefore probable that in its mains-unit pamphlet, the BBC will print an explanation written in more simple terms.

In conclusion, listeners are reminded that they are likely to have some difficulty in the future with electricity supply contractors, fire insurance authorities and other similar bodies, if they are using a mains-driven receiver which does not conform with the agreed regulations."

I suppose it is a matter of familiarity breeding contempt since electronic enthusiasts have been successfully assembling mains operated equipment and power supply units for a very long time now without any serious losses among their numbers from electric shock!

These interesting photographs show some "mint" items of vintage radio equipment kindly provided by Mr. Ken H. Rann of Lancing, Sussex.

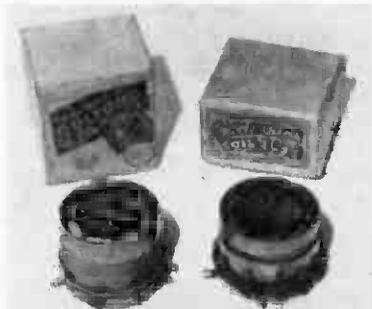It's rather unusual to locate brand new components but new items in their original boxes are interesting items indeed!





## AMATEUR BANDS

by Eric Dowdeswell G4AR

**T**HIS month I am glad to be able to give a plug for the West of Scotland Amateur Radio Society. Publicity and QSL Manager Graham Bleakley reports a thriving membership of 80 and space for many more and promises a warm welcome for SWL's, young or old. In the past the club has concentrated more on the interests of the licenced amateur so it is very good to hear that the SWL is actually being welcomed! It is an unfortunate fact that many clubs catering for the licenced chap tend to spurn the SWL who goes along once, gets the cold shoulder and then decides to drop the idea of pursuing the hobby. The fact that the SWL of today is the licenced amateur of tomorrow seems to escape notice. The SWL is also only too pleased to be a general dogsbody around the club, taking on tasks that no-one else wants to do, especially on Field Day events. SWL's in the Glasgow area are invited along to 81 Virginia Street, Glasgow every Friday evening at 8pm to sample the Morse classes, junk sales, films, library and lectures etc. More details from Secretary K. Drinkwater at that address.

Steve Blake (Aylesbury) joined the flock with a report of 40m doings including a nice collection of ZL's on SSB. Hope Steve will favour me with some details of his gear in his next log. Michael Crimes (Exeter) has forsaken VHF now that he can really hear the DX on his shiny new Yaesu FR50B coupled to 132ft of wire via an ATU. Like several other reporters he is a little 'disgusted with the antics of the Italian boys especially when a rare call pops up.

Michael Green A8088 (Northwich, Cheshire) refutes any suggestion that the 4m band only comes alive in contests and submits a long list of G's heard in one evening on his home-made converter plus CR100 and 4-element beam at only 12ft. Regular John Porter (Baslow, Derbys) is glad to have left the classroom for an OND course at Chesterfield Tech. His Trio 9R59DS was not allowed to get cold, evidenced by the list of DX from 15 to 160m. Andrew Darragh (Wetherby, Yorks) sends his first log and promises more. Last reported in 1968 it seems, getting married in the interim, now 'back on the rails' and I should jolly well think so! A Geloso converter puts signals into an AR88 from a 12AVQ trapped vertical and nine radials per band!!! He must be located in the centre of the racecourse up there!

Alan Rae (Glasgow) found a few nice calls on 20m thoughtfully omitting the lists of W's that are not of much interest to anyone. Tim Charles (Colchester) in again with six pages of notes and calls gives the impression that he never goes to sleep! His long wires suffered in the gales but one would never think so! Interesting catch was F9LC on 7MHz with two watts of SSB and over S9 at that. I'm a bit put out to hear Alan had to look up ST2 in the prefix list since yours truly was ST2AR for 15 years! Incidentally, I've just had the very great pleasure of meeting ST2AS in London. I'm glad to say that I started him off as a SWL some years ago when he was a medical student and now he is Dr. Ibrahim, ophthalmic surgeon and the only active ST2 for some years past.

Bernard Hughes (Worcester) also stuck at 20m SSB which seems a pity with a lovely FR500SDX! The other bands are quite lively too, OM! Bernard keeps a record of the number of countries heard on each band and wonders if anyone is interested in seeing a totals table in this column from time to time? Paul Barker (Sunderland) is another of the sleepless brigade! Three pages of rare ones from 15 to 80m including several on SSTV but nothing exceptional this month, he says!

Max France (Warrington, Lancs) now has an RA1 but still prefers his old R107 for sorting out the DX on 80m. Back to school means less burning of the midnight oil however, so it looks as if 20m will be favourite for some time now, with a picture rail aerial. Ought to be good for SSTV!

### Log extracts

Max France:—80m PQ0NS PZ0CJ VS6DO ZL2CB 5Z4LW 6Y5BM 20m VP8NS XV5AB XW8GV.

Paul Barker:—15m CX2AAO (1700) 20m JW5DQ KH6IAG KL7MF KX6LP VS6FB ZD3U ZK1DJ 4W1GM 20m SSTV CT1TX 16RME KILEM LU4CN.

Bernard Hughes:—20m HK0BKX KM6DZ TR8VE YK1KAS 4W1GM.

Tim Charles:—80m ZL3NC ZJ4AU 40m CE5BMN YA2KL ZL1AUL ZL2ALR ZL3PW 20m HK4SAJ HK0BKX JYSUMC KC6BL TG5YD XZ1AB 2m DC3GEC DC4JHA.

Alan Rae:—20m CR3AX HK3CKW K3CI/OE K7RSC.

John Porter:—15m EA8JP PY8RW 20m CT3AT EA9FB FY7AU KV4AD TG9VN TR8SS ZB2CH 8R1CB T12AJF.

Steve Blake:—40m EA9AI HC0HM KZ5PW M1C SVIDO TU2DO VK7GK XE3U ZL3AR ZL4GN ZL4KS 8P6AG.

Michael Crimes:—20m CR4BS DU1XK ET3USE HZ1AB ST2AY VP1MT VP2DH 4W1GM.

**Andrew Duragh:**—15m CX2XC VQ9MC VU2DK ZP5NT 7P8AQ 20m AC3PT CR3ON DU2EF FC2CD HR2JAG JY9GR KC4AAC KG4AM ST2AY TA2QR VK9XX VP8HA VS5MC ZD7SD 8R1CB.

CW stations in bold, remainder SSB. Please note that logs should be in alphabetical order for every band.

## BROADCAST BANDS

### MEDIUM WAVE BROADCASTS

by Charles Molloy

**R**OY PATRICK reports again from Derby. With his Trio 9R59DS communications receiver he has logged Dakar, Senegal on 764kHz; Amman, Jordan on 800kHz; Rio de Janeiro, Brasil on 980kHz; Cluj, Romania on 1151kHz; Tripoli, Libya on 1250kHz; Conakry, Republic of Guinea on 1403kHz. Roy sends a mobile report of reception in North Wales. The receiver is a National RF 1400 portable connected to a car aerial and his daytime reception includes BBC Radio Merseyside on 1484kHz; BBC Radio Cumbria 1457kHz; Piccadilly Radio in Manchester on 1151kHz; Manx Radio, Isle of Man on 1295kHz (good signal) and 1594kHz (weak). After dark Tunis was heard on 962kHz and the Voice of Tangiers at 2000hrs in Arabic on 1232kHz.

**M. J. Clarke** (Warley) is a self confessed local radio enthusiast. Using a Philips RL210 portable receiver he has pulled-in BBC Local Radio outlets at Blackburn on 845kHz; Stoke on 1052kHz; Derby on 1115kHz and Birmingham on 1475kHz together with IBA Capital Radio on 557kHz and Birmingham on 1151kHz.

**Timothy James** (Southampton) has been tuning around the medium waves with his Fidelity RAD16. He reports hearing Capital Radio (London) on 557kHz; Radio Solent on 998kHz; Radio Medway on 1034kHz; Radio Sweden on 1178kHz and Radio

Brighton on 1484kHz.

**Peter Kirkbride** (Kenilworth, Warwickshire) still enjoys "scanning the medium waves" with his 20 year old Bush valve receiver. He mentions reception of AFN Frankfurt on 872kHz and Munich on 1106kHz; Radio Sweden on 1178kHz; Radio Tirana, Albania on 1394kHz. Peter asks if it is possible to pick up North America using this receiver. Provided that a good outdoor aerial is used it should be possible to hear a few of the stronger trans-atlantic signals when conditions are good for reception of this area. Try after 2330hrs GMT for CJON St John's, Newfoundland on 930kHz; CBA in Moncton, New Brunswick on 1070kHz and WNEW in New York City on 1130kHz.

**Mike Larvin** (Redcar, Cleveland) has a Pye 1403D and an ITT Weekend Automatic Radio. Both are portable receivers and although neither has a socket for an external aerial for the medium waveband and external aerial 25m long and 20ft high is pressed into use by means of the following ingenious device. "I use a 6 inch ferrite slab wound with 75 turns of 20-30 SWG wire one end of which is connected to a good earth and the other to the aerial". The slab is brought near the receiver until peak signals occur, coupling being by induction between the slab and the receiver's internal aerial. Mike's log includes WKBW Buffalo NY on 1520kHz at 0230hrs GMT; BBC Relay Stations in Cyprus on 638kHz and 1322kHz; AFN stations in Germany on 872kHz (Frankfurt), 935kHz (Berlin), 1106kHz (Munich), 1142kHz Stuttgart; Budapest, Hungary on 1340kHz at 2245hrs; Norte, Portugal on 755kHz and 1061kHz. A total of 23 BBC local outlets were heard as well as London Broadcasting on 719pHz and Metropolitan Radio (Newcastle) on 1151kHz with Radio Clyde and Piccadilly Radio in the background.

**Clive Barwood** (Grimsby) is another local radio enthusiast. He uses an Ekco Mariner 6 valve domestic receiver connected to an outdoor aerial 75 ft long and 25ft high. He reports hearing Capital Radio 557kHz; IBA Birmingham 1151kHz; Metro Radio also on 1151kHz; Manx Radio 1294kHz and BBC Radios at Stoke 1502kHz; Cleveland 1546kHz and Leicester 1594kHz.

### SHORT WAVE BROADCASTS

by Derek Bell

**H**ELLO there! my name is Derek Bell and our editor has invited me to take over Malcolm Connah's Short Wave News column for a spell. May I say that I hope all readers will give me the same help and friendship that they gave Malcolm. All columnists must rely on the help of their readers, especially in this sort of column, since it could be said that the readers write the column with their contributions. I hope also that in your letters you will pop in a line or two telling me what you would like to see included in this feature.

Having said all that I will declare the meeting open with the first log. This is from another first timer, namely **David Lovatt** of Cheadle, Staffs, and he reports the following:—

5980 SBC in English at 2130  
5990 Prague in English at 2131  
6010 Budapest at 2136  
6800 Pekin S/on at 2030  
7200 Deutsche Welle at 2031  
15350 Peace and Progress at 0920

This is a shortened version of a superb log from our thirteen year old correspondent who is equipped with an Ultra domestic valved receiver and a 60 ft aerial suspended 20 feet above terra firma.

**Christopher Hall** of Birmingham has the other sort of aerial, a 4-ft telescopic one, bolted to his Bush VTR178 Multiband. Using this line-up he reports an impressive list of catches the cream of which is as follows:—

6185 R. Norway in English at 1200  
9770 R. Australia at 1600  
11955 B.B.C. Malaysia relay in English at 1500

I was interested in your comments at the end of your letter Christopher. As far as DX clubs go one must rely on the adverts they place in various magazines so "yer pays yer money and takes yer choice" in other words! Your request for the latest information on equipment for the BC stations however brings forth the information that Uganda is pressing ahead with a new SW transmitter setup that will bring the voice of Uganda blaring out loud and clear. Recently a member of Radio Nederlands staff went on record as saying that they are to increase the

power of their transmitters, another victim I fear of the "power game".

From the biggest to the smallest now, Paul Heath says his equipment "is somewhat joked about". This Heath kit (sorry about that!) is a home-built HAC one valver plugged in to various "out board motors" namely an ATU and feeding out through a transistor amplifier. Well Paul, let them laugh!, you pulled in a fine list, as is shown below:—

- 9005 Voice of Iran at 2020
- 9625 R. Jerusalem at 2000 (This is R. Israel, Paul)
- 9655 R. Damascus at 0830
- 9670 A.W.R. Portugal at 0945

You remark Paul, that you have received QSLs from only a couple of stations but that "there are more to come". Well OM, this is purely a matter of being patient. Radio Tirana, for instance, has been known to take 125 days to deliver, while Polish Radio Warsaw has taken only seventeen. Your logging of Damascus on 9655 was fortunate since Damascus is a notorious "wanderer" having been heard as far off frequency as 9630.

My final letter for this month is written by Robert Hill who hails from Hough, near Crewe, and he reports that he heard:—

- 9005 R. Tehran in English at 2015
- 9480 R. Tirana in English at 1830
- 9550 R. Finland in English at 1605.
- 11775 R. Bucharest in English at 1300

Having Crewe as a QTH seems to me to pose some unusual problems, I imagine it is possible that with all the QRM around from electric railways DXing is rather difficult. I would be interested to find out if I am right.

Well folks, that winds up my first venture into the pages of Practical Wireless. I hope that having read it you will feel that you want to write in with your logs (see address box) so I look forward to hearing from you, best 73s to you and yours.

### BROADCAST BANDS

Short Wave and VHF/FM reports by the 15th of the month to Derek Bell c/o Practical Wireless, Fleetway House, Farringdon Street, London, EC4A 4AD.

Medium Wave Logs to Charles Molloy, 132 Segars Lane, Southport, PR8 3JG.

### AMATEUR BANDS

Logs covering any amateur band/s in band/ alphabetical order by the middle of the month to Eric Dowdeswell G4AR, Silver Firs, Leatherhead Road, Ashted, Surrey, KT21 2TW.

A reprint of the P.W. Tele-Tennis series is being prepared and will be available shortly. Further details in the January 1975 issue of Practical Wireless.



## ALL PRICES INCLUDE V.A.T.

### SPEAKER BARGAINS

EMI 13" x 8" 3, 8 or 15 ohm	£
Plain	2-05
With Co-Axial Tweeter	
8 ohms only	2-20
Twin Tweeter	3-70
Type 350 8 or 15 ohm,	
20 watt	£ 64
4 1/2" 8 ohm, 10 watt	2-40
6" 8 ohm, 10 watt	2-75
12" 8 ohm, 20 watt	4-75
12" x 5" C/Mag. 5 watt	1-25
12" x 5" Dualcone	
8 ohm 10 watt	2-45

GOODMANS 6 1/2" 8 ohm	£
Dualcone	2-15
ELAC 8" 8 ohm Dualcone	2-25
ELAC 8 ohm Dualcone 10 watt	3-50
FANE 7" x 4" 3 or 8 ohm	1-00
ADASTRA 10" 8 or 15 ohm,	
10 watt	3-45
BAKER GROUP 25 12" 8 or	
15 ohm, 25 watt	7-85
5 8 ohm, C/Mag.	1-30
2 1/2" 8 ohm or 64 ohm	50
P. & P.	15

### TWEETER & CROSSOVER

EMI 3 1/2" 3 or 8 ohm C/Mag.	1-20
Cone Tweeter 8 or 15 ohm,	
10 watt	2-40
Cone Tweeter 8 ohm, 3 watt	1-45
Horn Tweeter 8 ohm, 20 watt	6-40

Dome Tweeter 8 ohm, 30 watt	5-40
Crossovers CN23 (3 ohm),	
CN28 (8 ohm), CN216 (16	
ohm)	1-20
P. & P.	10

### KIT FORM CABINETS TEAK VENEER

12 x 12 x 6 with 8" 8" x 5" or	
6 1/2" and 3 1/2" cut out.	2-45
17 x 10 x 9 with 8" or 13" x 8"	
cutout	3-50

18 x 11 x 9 with 13" x 8" cutout	
for EMI 350 ..	4-25
P. & P. ea.	45

### MICROPHONES

CM70 Planet stick metal,	
switch crystal	1-55
DM160 Dynamic omni-dir,	
ball metal	3-85
UD130 50K/600 ohm, uni-dir	
ball metal	5-95

TW209 ..	5-75
CONDENSER MIKE 600 ohm,	
uni-dir	9-35
Cassette Stick Mike with R.	
Control on/off switch	1-45
(2-5 & 3-5mm J/Pl)	20
P. & P.	

### SOLDERING IRONS

ANTEX CN240 15 watt	1-90
SK 1 Kit (15 watt iron	
2 spare Bib etc.)	3-30

X25 25 watt (low	
leakage)	1-90
P. & P.	10

### CARTRIDGES & STYLII

ACOS GP91/25C or 35C ster.	
comp.	1-00
GP93/1 or 95/1 ster.	
cryst.	1-35
GP94/1 or 96/1 ster.	
ceram.	1-75
GP101 cryst. comp.	2-80
GP104 ster. ceram.	1-65
BSR X5M or X5H cryst. comp.	1-70
SX6M or SX6H cryst.	
comp.	1-90
SC5M ster. ceram.	2-60

SONOTONE	
9TAHC or 9TAHC/G Diam.	1-80
3509 Ster. ceram. Diam.	1-90
GOLDRING G850	2-85
G800	3-85
G800E	8-90
P. & P.	10
D. Diamond Stylil for above..	1-25
G800/G850	1-95
G800E	3-85
P. & P.	04

### CALCULATORS SINCLAIR

Cambridge	19-00
-----------	-------

Scientific	29-00
------------	-------

### BATTERY ELIMINATORS

240V Input 6, 7.5 or 9 300mA	2-95
12V d.c. Input (specify output)	
	1-5

6, 7.5 or 9 d.c. output at	
300mA	2-30
P. & P.	15

TAPES Sind. LP OP	
5" 50p 65p 1-00p	
5 1/2" 65p 80p 1-40p	
7" 85p 1-10p 1-80p	

PLASTIC LIBRARY CASES	
For 5" Reels	18p
5 1/2" Reels	22p
7" Reels	25p
P. & P. 1-3, 9p ea. 4 or more, lot 30p	

### LOW NOISE CASSETTES

1-5 6-10 11-20	
C60 35p 33p 30p	
C90 45p 43p 40p	
C120 55p 52p 50p	

Cassette Cases	10p
Cassette Head Cleaner	35p
P. & P. 1-5, 3p ea. 6-10, 15p lot.	
11-20, Post Free.	

### BIB ACCESSORIES

Tape Editing Kit Ref. 23	1-35
Recording Tape	
Splicer Ref. 20	1-15
Cassette Tape, editing Ref. 24	1-50
Cassette Salvage Kit Ref. 29	45
12" Cassette Case Ref. 34	1-50
Stylus Balance Ref. 32A	1-20
Spirit Lever Ref. 46	50
Hi-Fi Stereo Test Cassette	2-10
Groove-Kleen Record Cleaner	1-90
P. & P.	10

### WHARFEDALE SPEAKER BARGAINS

Linton 2 Kit (pr)	£	P&P
Glendale 3 Kit (pr)	19-00	1-00
Dovedale 3 Kit (pr)	33-50	1-50
Denton 2 Speaker (pr)	32-00	2-00
Linton 2 Speaker (pr)	30-50	2-00
Dovedale 3 Speaker		
(each)	42-00	2-00
Glendale 3 Speaker (pr)	57-00	3-00
Kingsdale 3 Speaker		
(each)	59-95	3-00


Send 25p for COMPLETE CATALOGUE, refundable upon first order. ALL OUR MERCHANDISE IS FULLY GUARANTEED. Subject to manufacturer increase and availability.

**Riversdale Electronics**  
Mail Order Department PW1  
P.O. Box 470, Manchester M60 4BU.





**I.L.P. (Electronics) Ltd**

# SHEER SIMPLICITY!

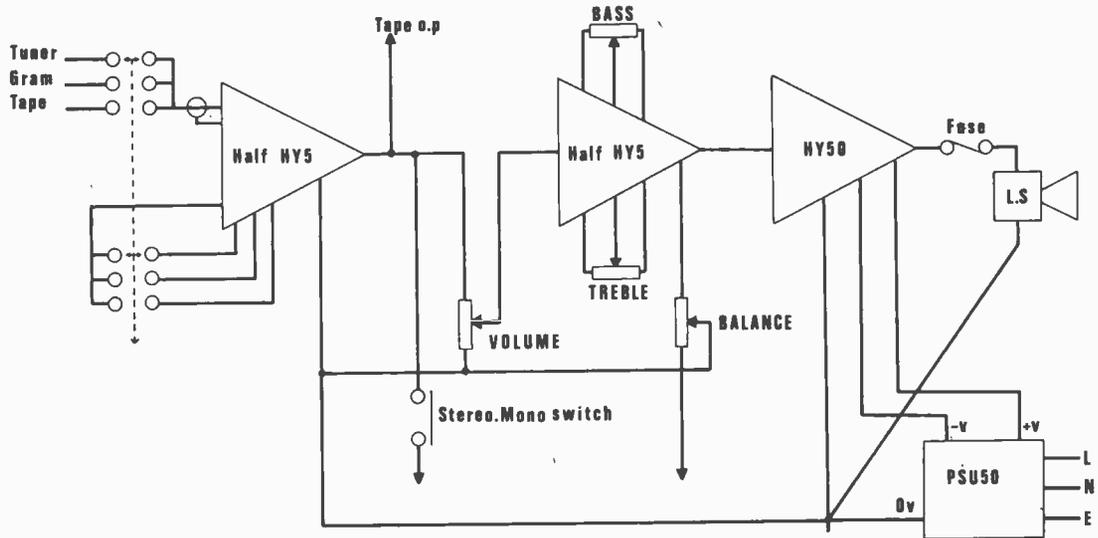

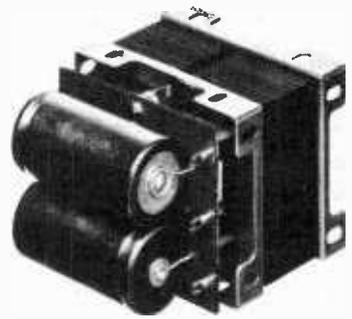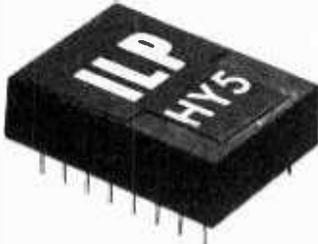**MONO ELECTRICAL CIRCUIT DIAGRAM WITH INTERCONNECTIONS FOR STEREO SHOWN**



The HY5 is a complete mono hybrid preamplifier. Ideally suited for both mono and stereo applications. Internally the device consists of two high quality amplifiers—the first contains frequency equalisation and gain correction, while the second caters for tone control and balance.

**TECHNICAL SPECIFICATION**  
 Inputs: Magnetic Pick-up 3mV RIAA; Ceramic Pick-up 30mV; Microphone 10mV; Tuner 100mV; Auxiliary 3-100mV; Input Impedance 47kΩ at 1kHz. Outputs: Tape 100mV; Main output 0db (0.775V RMS). Active Tone Controls: Treble ± 12db at 10kHz; Bass ± 12db at 10kHz; Bass ± 12db at 100Hz. Distortion: 0.5% at 1kHz. Signal/Noise Ratio: 88db. Overload Capability: 40db on most sensitive input. Supply Voltage: ± 16-25V.

**PRICE £4.50** + 36p VAT  
 P. & P. free

The HY50 is a complete solid state hybrid HI-FI amplifier incorporating its own high conductivity heatlink hermetically sealed in black epoxy resin. Only five connections are provided, input, output, power lines and earth.

**TECHNICAL SPECIFICATION**  
 Output Power: 25W RMS into 8kΩ. Load Impedance: 4-16Ω. Input Sensitivity 0db (0.775V RMS). Input Impedance: 47kΩ. Distortion: Less than 0.1% at 25V typically 0.05%. Signal/Noise Ratio: Better than 75db. Frequency Response: 10Hz-50kHz ± 3db. Supply Voltage: ± 25V. Size: 105 x 50 x 25mm.

**PRICE £5.98** + 48p VAT  
 P. & P. free

The PSU50 can be used for either mono or stereo systems.

**TECHNICAL SPECIFICATIONS**  
 Output voltage: 50V (25-0-25V). Input Voltage: 210-240V.  
 Size: L.70. D.80. H.60mm.

**PRICE £5** + 40p VAT  
 P. & P. free

## TWO YEARS' GUARANTEE ON ALL OUR PRODUCTS

**I.L.P. Electronics Ltd.**  
**Crossland House,**  
**Nackington, Canterbury**  
**Kent CT4 7AD**  
**Tel (0227) 63218**

Please supply, .....

Total Purchase price .....

I Enclose, Cheque  Postal Orders  Money Order

Please debit my Access account  Barclaycard account

Account number .....

Name & Address .....

Signature .....

# ALL OUR PRICES INCLUDE V.A.T.

## BSR HI-FI AUTOCHANGER

### STEREO AND MONO

Plays 12", 10" or 7" records  
Auto or Manual. A high  
quality unit backed by BSR  
reliability with 18 months'  
guarantee. AC 200/250v.  
Size 13 1/2 x 11 1/2 in.



Above motor board 3 1/2 in.  
Below motor board 2 1/2 in.  
With STEREO/MONO CARTRIDGE **£6.95** Post 45p.

## PORTABLE PLAYER CABINET

Modern design. Size 18" x 15" x 7" veneer  
covered. Large front grille. Hinged lid. Chrome  
fittings. Motor board cut for BSR deck.  
Few only in red. **£4.50** Post 45p.

## SOLID MAHOGANY PLINTH

With P.V.C. Cover. Cut out for most  
B.S.R. or Garrard decks.  
Size 12 1/2 x 14 1/2 x 7 1/2 in.

**£5.95**

Post 45p

## BSR JUNIOR SINGLE PLAYER

Heavy duty 4-speed motor with  
separate pick-up arm fitted  
LP/78 turnover motor. **£4.95** Post 25p




## R.C.S. DISCO DECK SINGLE RECORD PLAYER

Fitted with auto stop, stereo/mono cartridge. Base-  
plate. Size 11 1/2 x 8 1/2 in. Turntable. Size 7 in diameter. A/C  
mains. 220/250v motor has a separate winding 14 volt to  
power a small amplifier.  
3 speeds plays all size  
records. **£5.50** Post 25p
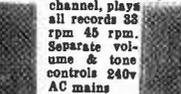
## COMPACT PORTABLE STEREO HI-FI

Two full size loudspeakers 13 1/2 x 10 x 3 1/2 in. Player  
unit clips to loudspeakers making it extremely compact.  
Overall size only 13 1/2 x 10 x 3 1/2 in. 3 watts per



channel, plays  
all records 33  
rpm 45 rpm.  
Separate vol-  
ume & tone  
controls 240v  
AC mains

Attractive  
Teak finish  
Weight 13lbs. **£25** Post 45p  
Bargain Price  
85p carriage

## SPECIAL OFFER! SMITH'S CLOCKWORK 15 AMP TIME SWITCH

### 0-60 MINUTES

Single pole two-way surface mounting  
with fixing screws. Will replace existing  
well switch to give light for return home,  
garage, automatic anti-burglar lights etc. Variable knob  
Turn on or off at full or intermediate settings.  
Fully insulated. Makers last list price £4.50. Brand new and  
fully guaranteed. **OUR PRICE £1.95** Post 25p.



## CASSETTE RECORDER MOTOR ONLY.

Will replace many type's £1.25.

BLANK ALUMINIUM CHASSIS. 18 s.w.s. 2 1/2 in sides  
6 x 4 in 45p; 8 x 6 in 55p; 10 x 7 in 65p; 12 x 8 in 85p;  
14 x 9 in 95p; 16 x 10 in 95p; 12 x 8 in 50p; 16 x 10 in 21p.

ALUMINIUM BOXES 3 x 3 x 3 in. 80p. 4 x 4 x 4 in. 70p.  
6 x 4 x 4 in. 80p. 9 x 4 x 4 in. £1.12 x 4 x 4 in. 21-30p.

ALUMINIUM PANELS 18 s.w.s. 6 x 4 in 12p; 8 x 6 in 15p;  
14 x 8 in 25p; 10 x 7 in 25p; 12 x 8 in 25p; 12 x 8 in 25p;  
16 x 8 in 34p; 14 x 8 in 40p; 12 x 8 in 47p; 16 x 10 in 60p.  
S.R.B.P. PAXOLIN PANEL 10 x 8 in 30p.

1 1/2 inch DIAMETER WAVECHANGE SWITCHES, 45p. EA.  
2 p. 2-way, or 2 p. 6-way, or 3 p. 4-way.  
1 p. 1 2-way, or 4 p. 2-way, or 4 p. 3-way.

TOGGLE SWITCHES, sp. 20p; dp. 25p; dp. dt. 30p.

## R.C.S. STABILISED POWER PACK KITS

All parts and instructions with Zener Diode. Printed Circuit  
Board Rectifiers and Double Wound Mains Transformer.  
Input 200/240v. Output voltages available 8 or 9 or 12  
or 15 or 18 or 20V d.c. at 100mA or less.  
PLEASE STATE VOLTAGE REQUIRED. **£2.20** Post  
Details S.A.E. Size 3 1/2 x 1 1/2 in. 20p

## R.C.S. GENERAL PURPOSE TRANSISTOR PRE-AMPLIFIER BRITISH MADE

Ideal for Micro, Tape 2/T, Guitar, etc. Can be used with  
Battery 9-15v. or H.T. 150-300V. D.C. operation. Size  
1 1/2 x 1 1/2 x 1 1/2 in. Response 25 c.p.s. to 25 Kc/s. 28 db gain.  
For use with valve or transistor equipment. **99p** Post  
Full instructions supplied. Details S.A.E. 10p

## NEW TUBULAR ELECTROLYTICS CAN TYPES

2/850V 14p	250/25V 14p	16 + 16 + 16/275v 45p
4/850V 14p	500/25V 20p	50 + 50/350V 50p
8/850V 18p	1000/25V 25p	32 + 32/250V 20p
16/350V 22p	1000/50V 47p	32 + 32/450V 80p
32/500V 50p	3 + 8/450V 22p	32 + 32/450V 80p
25/25V 10p	3 + 16/450V 22p	100 + 50 + 50/350V 35p
50/50V 10p	3 + 16/450V 40p	32 + 32 + 32/850 85p
100/25V 10p	32 + 32/850V 40p	500MFD/350V 65p

## LOW VOLTAGE ELECTROLYTICS

1, 2, 4, 5, 8, 16, 25, 30, 50, 100, 200mF 15V 10p.  
500mF 12V 15p; 25V 20p; 50V 30p.  
1000mF 12V 20p; 25V 25p; 50V 47p; 100V 70p.  
2000mF 6V 25p; 25V 42p; 50V 57p; 4700/83V 85p.  
2500mF 6V 25p; 3000mF 25V 47p; 50V 55p.  
5000mF 6V 25p; 10V 42p; 25V 75p; 50V 85p; 50V 95p.  
CERAMIC 1pF to 0.1mF 4p. 120 pF 4p. 1000pF, 4p.  
PAPER 350V-0.1 4p; 0.5 13p; 1mF or 2mF 150V 15p.  
500V-0.001 to 0.05 4p; 0.1 5p; 0.25 8p; 0.47 25p.  
MICRO SWITCH single pole changeover 20p  
MICRO SWITCH sub min 25p.

TWIN GANG. "0-0" 205pF + 176pF, £1.10.  
Slow motion drive +60pF + 35pF with 25pF, 25pF, 50p;  
500pF standard twin gang 75p. 120 pF twin gang 55p.  
SHORT WAVE SINGLE. 10pF, 30p; 25pF, 55p; 50pF, 55p.

ELAC 9 x 5in. HI-FI SPEAKER. TYPE 59RM. THIS  
FAMOUS AND WIDELY USED UNIT NOW AVAILABLE  
AT BARGAIN PRICE £2.95.  
10 WATT, 5 OHM. CERAMIC MAGNET.

NEON PANEL INDICATORS. 250V AC/DC Amber, 30p.  
RESISTORS. 1 w., 1/2 w., 20%, 1p; 2 w. 5p. 10 to 10M.  
HIGH STABILITY. 1/2 w. 2% 10 ohms to 6 meg., 10p.  
Ditto 5%. Preferred values 10 ohms to 10 meg., 4p.  
WIRE-WOUND RESISTORS. 5 watt, 10 watt, 15 watt,  
10 ohms to 100K, 10p each; 2w 0.5 ohm to 5.2 ohms 10p.  
TAPPE OSCILLATOR COIL. Valve type, 30p.  
FERRITE ROD 8" x 1/2" 20p; 6" x 1/2" 20p; 3" x 1/2" 10p

## MAINS TRANSFORMERS ALL POST 25p each

Eagle MT12 12-0-12v 50MA ..... 90p  
250-0-250 80 mA. 6.3 v. 3.5 a. 6.3 v. 1 a. or 5 v. 2 a. £2-50  
300-0-300 80 mA. 6.3 v. 3.5 a. 6.3 v. 1 a. or 5 v. 2 a. £2-00  
400-0-400 v. 120 mA., 6.3 v. 4 a. C.T. 6.3 v. 2 a. £4-05  
MINIATURE 200 v. 20 mA., 6.3 v. 1 a. 2 1/2 x 2 1/2 in. 75p  
MIDGET 220 v. 45 mA., 6.3 v. 2 a. 2 1/2 x 2 1/2 in. 90p  
HEATER TRANS. 6.3 v. 3 amps. £1-20 + amp. 85p  
GENERAL PURPOSE LOW VOLTAGE. Tapped outputs at  
3 amp., 6, 8, 10, 12, 15, 18, 24, 30, 36, 40, 48, 60, 24-00  
1 amp., 6, 8, 10, 12, 15, 18, 24, 30, 36, 40, 48, 60, 24-00  
2 amp., 6, 8, 10, 12, 15, 18, 24, 30, 36, 40, 48, 60, 24-00  
3 amp., 6, 8, 10, 12, 15, 18, 24, 30, 36, 40, 48, 60, 24-00  
5 amp., 6, 8, 10, 12, 15, 18, 24, 30, 36, 40, 48, 60, 24-00  
3, 5, 8, 10, 12, 15, 18, 24, 30, 36, 40, 48, 60, 24-00  
5 amp. 9 v. 1 amp. 95p. 12 v. 300 mA 75p. 12 v. 500 mA  
85p. 12 v. 750 mA 95p. 48 v. 2 amp. tapped 12 v. or 36 v.  
22-00. 20V 3 amp. £2-00.

AUTO TRANSFORMERS. 115v to 230v or 230v to 115v.  
150w. £3-00; 500w. £6-75; 750w. £13-50; 1000w. £18-50.  
CHARGER TRANSFORMERS. Input 200/250v.  
for 8 or 12v., 1 amp. £1-50; 2 amp. £1-80; 4 amp. £3  
BATTERY CHARGERS. Ready built with leads and clips  
1 1/2 amp. £2; 4 amp. £4; 8 amp. £4-50.  
FULL WAVE BRIDGE CHARGER RECTIFIERS;  
6 or 12v. outputs. 1 1/2 amp. 40p; 2 amp. 55p; 4 amp. 85p.

## MAINS ISOLATING TRANSFORMER

Primary 0-110-240v. Secondary 0-240v. 3 amps. 750  
watts. Insulated terminals. Varnish impregnated. Fully  
enclosed in steel case with fixing feet. **£12** Carr.  
Famous make. (Value £19) OUR PRICE **£12** 85p  
Suitable for outside use.

## SET OF 3 MOTORS FOR COLLARO STUDIO 115 VOLT TAPE DECK £1-50 Post 50p.

## VOLUME CONTROLS 80 Ohm Coax 5p yd.

5 K. ohms to 2 Meg. LOG or  
LIN. L/S 20p. D.P. 35p.  
STEREO L/S 55p. D.P. 75p.  
Edge SE. S.P. Transistor 25p

Wirewound controls 1 1/2 in. diam. 3 watts. 10 ohms to 100K  
British made with long spindles. Lin. dia 80p es.

DUAL CONCENTRIC POT 500k Log + 500k LIN D.P.  
switch. Inner spindle 3 1/2 in; outer spindle 2 1/2 in. 75p.

## E.M.I. 13 1/2 x 8 in. SPEAKER SALE!

With twin tweeters.  
And crossover. 10  
watt. Size 8 or 8  
or 15 ohm. As illustrated. **£4-50** Post 25p



With fired tweeter cone and ceramic  
magnet. 10 watt.  
Bass res. 45-60 cps. **£2-75**  
Flux 10,000 gauss.  
Size 8 or 8 or 15 ohm. Post 25p

## Bookshelf Cabinet 16 x 10 x 9 in. £6-60

Printed wood front Teak Veneer Post 45p

## E.M.I. 6 1/2 in. HI-FI WOOFER

8 ohm, 10 watt. Large ceramic magnet  
Special Rubber cone surround.  
Frequency response 30-12,000  
cps. Ideal P.A. Columns,  
Hi-Fi Enclosure Systems, etc.  
Suitable cabinet 12 x 8 x 6 24-00.  
Suitable Tweeter £2-00.



## ELAC CONE TWEETER

The moving coil diaphragm gives a good  
radiation pattern to the higher frequencies  
and a smooth extension of total response  
from 1,000 cps to 18,000 cps. Size 8 1/2 x  
3 1/2 x 2 in. deep. Rating 10 watt, 3 ohm.  
Crossover £1.25  
Post 25p **£1-90**

## GOODMANS 8 in. WOOFER

8 ohm 12 watt. Deep cone.  
Heavy ceramic magnet. Bass  
resonance 35 cps. Frequency  
response 30-8,000 cps.  
Ideal bass unit for **£3-75**  
Hi-Fi systems



LOUDSPEAKERS P.M. 3 OHMS. 7 x 4 in. £1-25; 6 in. £1-50;  
8 x 6 in. £1-60; 8 in. £1-75; 10 x 6 in. £1-90; 10 in. £2-00.  
SPECIAL OFFER! LOUDSPEAKERS! All Brand New.  
3 ohm, 2 1/2 in; 3 1/2 in; 5 in. 8 ohm, 2 1/2 in; 2 1/2 in x 3 in;  
5 in. 15 ohm, 3 1/2 in; 5 in; 8 x 4 in; 5 in x 3 in; 7 x 4 in; 8 x 5 in.  
25 ohm, 2 1/2 in; 3 in; 3 in; 5 x 3 in. 35 ohm, 2 in; 3 in; 5 in.  
80 ohm, 2 1/2 in; 2 1/2 in. 120 ohm, 3 in. **£1 EACH.**

## LOUDSPEAKER VOLUME CONTROL 15 ohm 10 watt

with 1 in long threaded bush for wood panel mounting 65p.

RICHARD ALLAN TWIN CONE LOUDSPEAKERS. 8 in.  
diameter 4W £2-50, 10 in. diameter 5W £2-75; Post 25p.  
12 in. diameter, 8W, £3-30; 8 or 8 or 15 ohm models.  
SPEAKER COVERING MATERIALS. Samples Letter S.A.E.  
Horn Tweeters 2-16Kc/s. 10W 8 ohm or 16 ohm £2-90.  
De Luxe Horn Tweeters 2-18 Kc/s. 15W, 8 ohm £3-50.  
TWO-WAY 2,000 c.p.s. CROSS OVERS 3, 8 or 15 ohm £1-25.  
3-WAY CROSSOVER 850 cps and 3000 cps (25 watt) £1-25.

## DECCA DOME TWEETER

18,000 cps. 25 watts. 8 ohm. Price **£3-30.**

## ELECTRO MAGNETIC PENDULUM MECHANISM

1.5v d.c. operation over 250 hrs. continuous on SP2 battery.  
fully adjustable swing and speed. Ideal displays teaching  
electro magnetism or for metronome; strobe etc. 95p. Post 20p

## R.C.S. VALVE AMPLIFIER

2 State Triode Pentode valve, 3 watts 3 ohm output. Volume  
on/off and tone controls AC mains. Complete and tested.  
With Loudspeaker. **£4-50** Post 25p.

## WEYRAD COILS

P50/1AC-80p. RAZW 85p. Twin Gang £1-10.  
P50/2CC-40p. OFTI 65p. Printed Circuit 85p.  
P50/3CC-40p. LFDT4. 65p.

COAXIAL PLUG 10p. PANEL SOCKETS 10p. LINE 15p  
OUTLET BOXES, SURFACE MOUNTING 25p.  
BALANCED TWIN RIBBON FEEDER 300 ohms, 7p yd.  
JACK SOCKET 5id. open-circuit 14, closed circuit 23p;  
Chrome Lead Socket 45p. Phone Plugs 5p. Phone Socket 5p  
JACK PLUGS 8id. Chrome 30p; 3.5mm Chrome 18p. DIN  
SOCKETS Chassis 3-pin 10p; 5-pin 10p. DIN SOCKETS  
Lead 3-pin 10p; 5-pin 15p. DIN PLUGS 3-pin 18p; 5-pin 25p.  
VALVE HOLDERS 5p; CERAMIC 10p; CAN5 5p.

## FM/VHF AERIAL FEEDER CABLE

300 ohm suitable for stereo 7p per yard.  
BRITISH FM/VHF TUNING HEART  
88 to 108 Mc/s. British made. 3 Transistors ready aligned - requires 10.7  
Mc/s IF. Complete with tuning gang.  
Connections supplied but some  
technical experience required.  
SUITABLE I.F. STRIP £4-95.  
Post 20p. **£3-95**

ALL PRICES INCLUDE VAT MINIMUM POST AND PACKING 20p. CALLERS WELCOME

# RADIO COMPONENT

Illustrated Brochure, Radio Books & Component Lists 10p. Written guarantee.

# ALL OUR PRICES INCLUDE V.A.T.

## E.M.I. WOOFER AND TWEETER KIT

**THE PAIR.** Post 25p.  
(Available separately.)  
**£5-75** Woofer 25-25; Tweeter £1-00.  
Comprising a fine example of a Woofer 10 1/2 x 6 1/2 in. with a massive Ceramic Magnet, 44oz. Gauss 13,000 lines. Aluminium Cone centre to improve middle and top response. Also the E.M.I. Tweeter 8 1/2 in. square has a special lightweight paper cone and magnet flux 10,000 lines. Crossover condenser and full instructions supplied.  
Impedance Standard 8 ohms  
Maximum power 12 watts  
Useful Response 25 to 18,000 cps  
Bass Resonance 45 cps  
**£10-50** Post 75p  
SUITABLE ENCLOSURE 20 x 13 x 9 in.  
MODERN DESIGN. TEAK WOOD FINISH.



## BAKER MAJOR 12" £8-50

Post Free  
30-14,500 c/s. 12in. double cone, woofer and tweeter cone together with a BAKER ceramic magnet assembly having a flux density of 14,000 gauss and a total flux of 145,000 Maxwells. Bass resonance 40 c/s Rated 20 watts. NOTE: 3 or 8 or 15 ohms must be stated.  
Module kit, 30-17,000 c/s with tweeter, crossover, baffle and instructions. **£10-95**  
Please state 3 or 8 or 15 ohms. Post Free

## "BIG SOUND" BAKER SPEAKERS

Robustly constructed to stand up to long periods of electronic power. As used by leading groups.  
Useful response 30-18,000 cps.  
Bass Resonance 55 cps.  
**GROUP "25"** **£7-75** Post Free  
12in. 25 watt - 3, 8 or 15 ohms.  
**GROUP "35"** **£8-50** Post Free  
12in. 35 watt - 3, 8 or 15 ohms.  
**GROUP "50"** **£17-80** Post Free  
15in. 50 watt - 8 or 15 ohms.  
**GROUP 50/12in.** **£12-95** Post Free  
50 watt 8 or 15 ohms  
Group + PA Cabinets in stock. Callers only. Send for Leaflet.

## MAJOR 100 WATT ALL PURPOSE TRANSISTOR AMPLIFIER

All purpose transistorised. Ideal for Groups, Disco and P.A. 4 inputs speech and music. 4 way mixing. Output 8/15 Ohm. a.c. Mains. Separate treble and bass controls. Guaranteed. Details SAE. **£49** Carr. £1-00  
NEW MODEL—MAJOR 50 WATT £39-95. Carr. £1.  
4 inputs 2-way mixing. 2 outputs separate treble and bass controls.



## CALLERS ONLY! DE LUXE 100 WATT VALVE AMPLIFIER CHASSIS

4 input 10 wide range controls. For Mikes, Discos, Organs, Guitars, etc. 4, 8 & 15 ohm loudspeakers matching £89-00.

## THE "INSTANT" BULK TAPE ERASER & HEAD DEMAGNETISER.

Suitable for cassettes, and all sizes of tape reels. A.C. mains 200/250V. Leaflet S.A.E. **£3-50** Post 20p



## QUALITY LOUDSPEAKER ENCLOSURE

Teak veneered 1 1/2 in thick wood cabinet. Size 18 1/2 in x 18 1/2 in x 8 1/2 in. Weight 23lbs. This cabinet features a wide mesh Silver Grill covering a separate compartment for mounting Tweeters or Mid-Range Horn. The fully sealed bass compartment is cut out for 6 1/2 inch Woofer. 27-50 Carr. 85p. Rosewood Version 28-50 Carr. 85p.

## SPECIAL OFFER 100 Ohm 20 watt Rheostat 2 1/2 in diam. Cera micFormer. Screw Terminals 1/2 in. diam. spindle.

**REVERSIBLE 4 POLE MOTOR**  
1,400 r.p.m. Reversible 42 Watt. **£2-25**  
spindle 1 1/2" x 7/32", size 3 1/2" x 3".  
As illustrated. 240v. AC mains. Post 35p

**E.M.I. TAPE MOTOR**  
4 pole, 240 v. 135 mA. Size 3 1/2 x 2 1/2 x 2 1/2 in. **£1-85**  
1200 rpm. Spindle 1/2 in diameter. Post 30p.

## BAKER HI-FI SPEAKERS HIGH QUALITY -- BRITISH MADE


### REGENT 12in. 15 watts

An inexpensive unit for the beginner in high fidelity and for general purposes. May be used with Hi-Fi or Television receiver.  
Bass Resonance 45cps  
Flux Density 12,000Gauss  
Useful response 45-13,000cps  
3 or 8 or 15 ohm models.  
**£7-75** Post Free


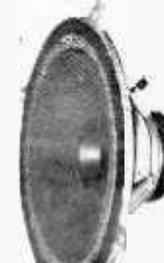
### DE-LUXE Mk II 12in 15 watts

Especially designed to provide full range reproduction at an economical cost. Suitable for use with any high fidelity system. Built-in concentric tweeter cone.  
Bass Resonance 30cps  
Flux Density 14,000Gauss  
Useful response 25-16,000cps  
8 or 15 ohms models.  
**£9-75** Post Free



### SUPERB 12in. 20 watts

A high quality loudspeaker. its remarkable low cone resonance ensures clear reproduction of the deepest bass. Fitted with a special copper drive and concentric tweeter cone resulting in full range reproduction with remarkable efficiency in the upper register.  
Bass Resonance 25cps  
Flux Density 16,500Gauss  
Useful response 20-17,000cps  
8 or 15 ohms models.  
**£13-80** Post Free



### AUDITORIUM 12in. 25 watts

A full range reproducer for high power. Electric Guitars, Public address, multi-speaker system, electric organs. Ideal for Hi-Fi and Discotheques.  
Bass Resonance 35cps  
Flux Density 15,000Gauss  
Useful response 25-16,000cps  
8 or 15 ohms models.  
**£12-95** Post Free



### AUDITORIUM 15in. 35 watts

A high wattage loudspeaker of exceptional quality with a level response to above 8,000 cps. Ideal for Public Address, Discotheques, Electronic instruments and the home Hi-Fi.  
Bass Resonance 35cps  
Flux Density 15,000Gauss  
Useful response 20-14,000cps  
8 or 15 ohms models.  
**£17-80** Post Free



Hi-Fi Enclosure Manual containing plans, designs, crossover data and cubic tables. 60p. Post Free.

## ELAC 8in. or 10 x 6in. HI-FI SPEAKER

Dual cone plasticised roll surround. Large ceramic magnet. 50-18,000 cps. Bass resonance 55 cps. 8 ohm impedance. 8in. 10 watts **£3-75**



## TEAK VENEER HI-FI SPEAKER CABINETS Fluted Wood Fronts

MODEL "A". 20 x 13 x 9 in. For 12in. dia. **£10-50** Post 75p  
MODEL "B". 16 x 10 x 9 in. For 13 x 9 in. or **£6-60** Post 75p  
MODEL "B2" ditto. Triangular corner version.  
MODEL "C". 18 x 8 x 6 in. For 8 x 5 in. **£4-95** Post 85p  
LOUDSPEAKER CABINET WADDING 18in. wide, 20p ft.



## CALLERS ONLY—HI-FI CABINET BAKER RECOMMENDED 12 inch Enclosure 4 cubic ft. Size 30 x 20 x 12in. Teak Finished Fluted Front. £18-50

## TEAKWOOD LOUDSPEAKER FRONT GRILLS

Modernise your cabinets with the Groover look. Sizes—18" x 10 1/2"—75p. 10 1/2" x 7 1/2"—45p.

## BARGAIN 4 CHANNEL TRANSISTOR MONO MIXER.

Add musical highlights and sound effects to recordings. Will mix Microphone, records, tape and tuner with separate controls into single output. 9 volt battery operated. **£4-50**  
STEREO VERSION OF ABOVE 25-95.



## BARGAIN FM TUNER. 88-108 Mc/s Six Transistor. 9 volt. Printed circuit. Calibrated slide dial tuning. Walnut Cabinet. £14

BARGAIN FM TUNER. **£10**  
As above less cabinet.  
BARGAIN 3 WATT AMPLIFIER. 4 Transistor Push-Pull Ready built with volume, treble and bass controls. 18 volt battery operated. **£3-50**



## WAFER HEATING ELEMENTS THIN

OFFERING 1001 USES for every type of heating and drying applications in the home, Garage, Greenhouse, factory (available in manufacturer quantities). Approx. size 1 1/2 x 2 1/2 x 1/4 in. Operating voltage 200/250V. a.c. 250 watts approx. Printed circuit element enclosed in asbestos fitted with connecting wires. Completely flexible providing safe Black heat. British-made for use in photocopiers and print drying equipment.  
Ideal for home handymen and experimenters. Suitable for Heating Pads, Food Warmers, Convector Heaters, etc. Must be clamped between two sheets of metal or asbestos, etc., to make efficient clothes dryers, towel rails—ideal for airing cupboards. Ideal for anti-frost device for the Garage—preventing frozen radiators or acting as oil sump heater. Use in the greenhouse for seed raising and plant protection. Invaluable aid for bird houses, incubators, etc. etc. Can be used in series for lower heat. Or in parallel for higher heat applications.

**ONLY 40p EACH (FOUR FOR £1-50)**  
ALL POST PAID—Discounts for quantity.

CUSTOMERS FREE CAR PARK

# SPECIALISTS

(Exports Remit cash and extra postage.)

OPEN 9-6. WEDNESDAY 9-1. SATURDAY 9-5. Closed for lunch 1-15—2-30

337 WHITEHORSE ROAD . CROYDON

Telephone 01-684-1665

Buses 50, 68, 159. Rail Selhurst

# FREE TRANSISTOR LEAD IDENTICHART

Inside the December issue of PRACTICAL ELECTRONICS is an invaluable 'Transistor Lead Identichart' which identifies, at a glance, the connections of more than 700 transistors.

## Get your car in tune for winter with the P.E. Dwell Meter

Make this instrument and then check the state of your distributor in one easy step.

**PRACTICAL  
ELECTRONICS**

DECEMBER ISSUE  
ON SALE FRIDAY,  
8th NOVEMBER  
25p

# SPARKRITE Mk II

## Electronic Ignition...

### Better on all points

### Because you keep your points!

The SPARKRITE MK II is a full capacitive discharge electronic system specifically designed to retain the points assembly with all the advantages and none of the disadvantages. No misuse because contact breaker bounce is eliminated electronically by a pulse suppression circuit which prevents the unit firing if the points bounce open at high rpm. Contact breaker bounce is eliminated by reducing the current to about 1/50th of normal, thus avoiding arcing. But you can still revert to normal ignition if need be in seconds. It is so easy to fit (very unlikely) you can get replacements anywhere. All these advantages.

- Fitted in 15 minutes. ● Up to 20% better fuel consumption. ● Instant all weather starting. ● Clean plugs - may last 5 times longer without attention.
- Faster acceleration. ● Faster top speeds.
- Coils and battery last longer. ● Efficient fuel burnt with less air pollution.

The kit comprises everything needed

Ready drilled scratch and rust resistant case, metalwork, cables, coil connectors, printed circuit board, top quality 5 year guaranteed transformer and components, full instructions to make positive or negative earth system, and 8 page installation instruction leaflet.

WE SAY IT IS THE BEST SYSTEM AT ANY PRICE!

#### PRICES

D.V.Y. Kit only £10.93 incl. VAT and P & P  
Ready Built Unit £13.96 incl. VAT and P & P  
(Both to fit all cars with coil distributor ignition up to 8 cylinders)

We can supply units for any type of engine vehicle (buses, motorcycles with coil contact breaker ignition).

Details on request. Call in and see us for a demonstration.

**ELECTRONICS DESIGN ASSOCIATES**

1 Dept

82 Bath Street, Walsall WS1 3DE Phone 33652



## YOUR CAREER in RADIO & ELECTRONICS ?

Big opportunities and big money await the qualified man in every field of Electronics today—both in the U.K. and throughout the world. We offer the finest home study training for all subjects in radio, television, etc., especially for the CITY & GUILDS EXAMS (Technicians' Certificates); the Grad. Brit. I.E.R. Exam.; the RADIO AMATEUR'S LICENCE; P.M.G. Certificates; the R.T.E.B. Servicing Certificates; etc. Also courses in Television; Transistors; Radar; Computers; Servo-mechanisms; Mathematics and Practical Transistor Radio course with equipment. We have OVER 20 YEARS' experience in teaching radio subjects and an unbroken record of exam. successes. We are the only privately run British home study College specialising in electronics subjects only. Full details will be gladly sent without any obligation.

To: British National Radio & Electronics School, Dept W.C. 124, P.O. Box 156, Jersey, C.I.

Please send FREE BROCHURE to

NAME ..... Block

ADDRESS ..... Caps.

..... Please

**BRITISH NATIONAL RADIO  
AND ELECTRONICS SCHOOL**

# Crescent Quality Components

**74 SERIES TTL**

7400	20p	7473	41p
7401	20p	7474	41p
7402	20p	7475	83p
7403	20p	7476	44p
7404	20p	7486	49p
7408	25p	7489	£4.75
7409	25p	7490	82p
7410	20p	7491	£1.10
7413	31p	7492	82p
7420	20p	7493	82p
7430	20p	74100	£2-37
7441	81p	74121	46p
7442	81p	74122	88p
7445	£1.20	74141	£1.10
7447	£1.45	74154	£1.82
7447A	£1.80	74192	£2.15
7448	£1.50	74193	£2.53
7470	33p	74196	£1.73



**LIGHT EMITTING DIODES**

TIL 208 (Red) With Clip	22p each
TIL 208 (Green) With Clip	38p each
TIL 209 (Yellow) With Clip	90p each
Mied 500 T092 Type	16p each

**LED READOUTS**

**Litronix**

DL707 3 Character 14 Pin DIL	£2.00
DL701 as above but ± 1	£2.00
DL747 6 Character	£2.62

**Mintron**

3015 7 Segment 16 Pin DIL	£1.18
30150 as above but ± 1	£1.18

**Clock Chip**

CT7001 MOS/LSI Digital Clock/Calendar Chip Plus full Circuits and Information leaflet **£3.95**

Circuits and Information Sheet **15p**

Lit 704 Led Display for above **£1.35**

Or 4 for **£5.25**

**WAFER SWITCHES**

1 Pole 12 Way	
2 Pole 2 Way	
2 Pole 3 Way	
2 Pole 4 Way	
2 Pole 6 Way	
3 Pole 4 Way	
4 Pole 3 Way	

£2p each



**POTENTIOMETERS**

All types 1" and less diameter

5K	Log or	Dual	5K
10K	Lin Less		10K
25K	Switch	Less	25K
50K	15p each	50K	Switch
100K		100K	45p each
250K	Double	250K	
500K	Pole	500K	
1M	Switch	1M	
2M	80p each	2M	

**PRE SETS**

Brand new Miniature Skeleton Type 0-1 Watt Horizontal Mounting 100, 250 and 500 ohm. 1k, 2.5k, 5k, 10k, 25k, 50k, 100k, 250k, 500k, and 1M ohm **6p each**

**MAINS TRANSFORMERS**

Open Type Double Wound Continuously Rated, two hole fixing clamp with colour coded flying leads, varnish impregnated. Approx. size: 1 1/2" x 1 1/2" x 1 1/2" high Fixing centres .29 1/2"

TR1	20-0-20v 100 m/a	
TR2	12-0-12 v 100 m/a	All
TR3	9-0-9 v 100 m/a	240 Volt
TR4	6-0-6 v 100 m/a	Primary
TR5	3-0-3 v 100 m/a	

Our Price £1.23 each

**200/250v MAINS RELAY**

Heavy duty contacts 2500 ohm coil. All new and unused D.P.D.T. mains relays 50p, Carr. Free. Special quantity £40 per 100 off.

**MINIATURE RELAYS**

Brand new range of British made Relays. Size 1 1/2" x 1" x 1". All two changovers with 250v 15A contacts and suitable for fitting on 1m Veroboard.

Type	Volts	Current	Ohms	
27/A	12v	17M/A	700	All
21/A	12v	28M/A	430	80p
12/A	6v	33M/A	185	each

**DOUGLAS TRANSFORMERS**

All types are standard 240 volt primary.  
MT 102 et. 0 - 19 = 25 = 33 = 40 = 50 at 500M/A

MT237cs	20-0-20 at 150M/A	£2.00 each
MT241cs	20-0-20 at 30M/A	£1.25
MT240cs	15-0-15 at 30M/A	£1.05
MT238cs	12-0-12 at 50M/A	£1.05
MT238cs	3-0-3 at 200M/A	£1.05

**POWER PACKS**

PP1 Switched 3 - 6 - 7 1/2 - 9 volt 400M/A Transistor and Zener Stabilised On/Off Switch and Polarity Reversal Switch, in a black metal case **£5.25 each**.

PP2 Switched 6 - 7 1/2 - 9 volt Battery Eliminator. Approx. size 2 1/2" x 2 1/2" x 3 1/2". Ideal for cassette recorders **£2.75 each** (philips type £3.00).

PP3 Car converter. From 12v Pos. or Neg. to = 6 - 7 1/2 - 9 volt. Easy to fit and transistor regulated **£2.50 each**



**VEROBOARD**

2 1/2 x 3 1/2	1	15	Plain 15
2 1/2 x 3 1/2	32p	24p	15p
2 1/2 x 5	24p	34p	18p
3 1/2 x 3 1/2	34p	84p	
3 1/2 x 5	39p	46p	
17 x 2 1/2	1.06p	77p	80p
17 x 3 1/2	1.45p	1.16p	75p
17 x 5	1.85p		1.10p

Pin insertion tool **75p**  
Spot face cutter **52p**  
Pkt. 36 pins (state -1 or -15) **25p**

**LOUDSPEAKERS**

2 1/2" 8 ohm	50p
2 1/2" 40 ohm	50p
2 1/2" 80 ohm	50p
5" 8 ohm	ceramic £1.25
6 1/2" 8 ohm dual cone	ceramic £2.50
10" 8 ohm dual cone	ceramic £3.75
7" x 4" 8 ohm	ceramic £1.60
8" x 5" 8 ohm Permanent Magnet	£1.60



\*EMI 13" x 8" 450 Kit **£3.75**  
3 - 8 - 15 ohm

\*EMI 13" x 8" 350 Kit 8 ohm **£7.50**

**FAVE ULTRA HIGH POWER LOUDSPEAKERS**

*Pop 25/2 30 watt 150 ohm 12"	£2.29
*Pop 55 60 watt 8/15 ohm 12"	£14.50
*Pop 50 50 watt 15 ohm 12"	£11.99
*Pop 60 60 watt 8/15 ohm 15"	£15.70
*Pop 100 100 watt 8/15 ohm 18"	£23.70

\* Carr. on L/S over 13 x 8 and 12" 60p per L/S.

**ALUMINIUM CHASSIS**

Four-sided with corner plates. All are 2 1/2" deep.

6" x 3"	42p	12" x 5"	66p
6" x 4"	45p	12" x 8"	87p
8" x 3"	48p	14" x 3"	83p
8" x 6"	57p	14" x 9"	99p
10" x 7"	70p	16" x 5"	90p
12" x 3"	57p	16" x 10"	£1.15

**ALUMINIUM BOXES**

Metal project boxes give you work a professional finish

AB7	L	2 1/2	5 1/2	1 1/2	40p
AB8	4	4	1 1/2	40p	
AB9	4	2 1/2	1 1/2	40p	
AB10	4	5 1/2	1 1/2	40p	
AB11	4	2 1/2	2	40p	
AB12	3	2	1	35p	
AB13	3	4	2	55p	
AB14	7	3	2 1/2	66p	
AB15	8	6	3	85p	
AB16	10	7	3	90p	
AB17	10	4 1/2	3	85p	
AB18	12	5	3	95p	
AB19	12	8	3	£1.26	

**ABS PLASTIC BOXES**

Handy boxes for construction Projects. Moulded extrusion rails for P.C. or chassis panels. Fitted with 1mm front panels.

1005 = 105mm x 73mm x 45mm = 51p
1006 = 150mm x 75mm x 47mm = 66p
1007 = 184mm x 124mm x 60mm = 96p
1021 = 106mm x 74mm x 46mm (sloping front) = 50p

**BARGAIN BOARDS**


Components galore for the experimenter Ex Computer boards with Resistors, Capacitors and useful Transistors - at least 4 transistors per board. Five boards **£1.00.**

**CLEAR PLASTIC PANEL METERS**

Size 59mm x 46mm x 35mm these meters require a 38mm hole for mounting.

ME6	= 0 to 50 micro amp Full Scale
ME7	= 0 to 100 micro amp Full Scale
ME8	= 0 to 500 micro amp Full Scale
ME9	= 0 to 1 mA Full Scale
ME10	= 0 to 5 mA Full Scale
ME11	= 0 to 10 mA Full Scale
ME12	= 0 to 50 mA Full Scale
ME13	= 0 to 100 mA Full Scale
ME14	= 0 to 500 mA Full Scale
ME15	= 0 to 1 amp Full Scale
ME16	= 0 to 50 volts A.C. Scale
ME17	= 0 to 300 volts A.C. Full Scale
ME18	= "S" Meter
ME19	= "VU" Meter

OUR PRICE **£3.50**

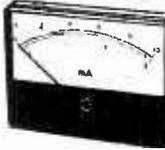

**Q-MAX SHEET METAL PUNCHES**

The easiest and quickest way of punching holes in sheet metal (up to 1.625mm Mill Steel)

DECON DALO 33PC	SIZE	PRICE	
ETCH RESIST PEN	1"	88p	Key "T" 6p
The Decon Dalo 33PC	1 1/2"	75p	
is a unique instrument	1 3/4"	83p	Key "A"
for the professional and	1 7/8"	83p	Key "B" 6p
amateur electronics engineer,	2"	88p	
enabling him to	2 1/8"	88p	
prepare in minutes a	2 1/2"	90p	
perfect printed circuit	3"	90p	Key "C" 13p
board	3 1/2"	98p	Key "B"
OUR PRICE 80p	4"	98p	Key "E"
	4 1/2"	108p	Key "C" 13p

**ADD LUXURY TO YOUR CAR**

with a motor driven car aerial

SPEC: ★ 5 section extended length 100cm  
★ Length under fender 40cm  
★ Cable length 120cm

1 1/2"	£1.05
1 7/8"	£1.10
1 3/4"	£1.25
1 7/8"	£1.43
1 3/4"	£1.50
2"	£2.05
2 1/8"	£2.30
2 1/2"	£4.10
2 1/2"	£5.25
3"	£8.10

Supplied complete with fixing bracket and control switch **£6.75**

1" SQUARE PUNCH complete with key **£2.10**

**STOP PRESS**

BHA0002	15 watt Amp Module	£2.50
N5555	Timer I.C.	78p
MC1310P	Stereo Decoder I.C.	£2.00
7905	Regulator	£1.49
TIP 29A		55p
TIP 30A		63p
BC107		10p
BC108		10p
HC109		10p



**BARGAIN TRANSFORMERS**

12-0-12 volt 500m/a

240 volt primary transformer bargain. approx size = 60mm x 40mm x 50mm fixing centres = 75mm

Our Price = **£1.20.**

18 volt 500m/a

240 volt tapped 120 volt with screen. approx size = 60mm x 40mm x 50mm fixing centres = 75mm

Our Price = **£1.00.**

**BARGAIN BOX**

Load buzzer mounted in a metal box complete with two U2 battery size holder.

Designed and can be used as a fire alarm but is ideal as a door or Morse code practice buzzer.

Approx. size - 2 1/2" x 6 1/2" x 1 1/2".

OUR PRICE - **50p.**

**U.K. POSTAGE 15p UNLESS OTHERWISE STATED**

**V.A.T. Please add 8% to all Totals**

**CRESCENT RADIO LTD.**

All mail to 11 MAYES ROAD, WOOD GREEN, LONDON N22 6TL

Phone: 01-888 3206  
Callers Welcome at  
15 Mayes Road & 13 South Mall, Edmonton N9.

If you construct You should own one.

**CRESCENT CATALOGUE**  
Price 20p.

**Wire Wound Resistors.** Our selection of mixed values. 30 for £1 50, 100 for £4.00.

**Audio Amplifier Module.** Mullard LP1173 capul power, nominal 10 watt, supply voltage +24 volt, with data and circuit. £2.50.

**Ferguson Stereogram chassis** Model 3157, all transistor, medium long, VHF, FM. 3 wails per channel S/M. with connection data, less tuning scale. £20.

**Crystals -IC6U:** 32 03333 MHz: 52 02400: 52 01667: 51 56667: 51 58330: 37 76250: 2: 75000: 12 395 8: 12 891 6: 12 70C 0: 9 458 33: 9 436 25: 9 455 55: 9 533 33: 9 531 94: 9 530 55: 9 090 62: 9 087 5: 9 096 87: 50p each.

**Electrolytics.** 32/32/32V. 325v. 2" 1 1/2" 35p: 2000V 30v. 2" 1 1/2" 25p: 2000V 30v. 2 1/2" 1" 25p: 2000V 35v 3" x 1 1/2" 30p: 470V 100v 3" 1 1/2" 25p: 2000 2000V 25v 2" 1 1/2" 35p: 30,000V 25v 4 1/2" 2 1/2" 50p: 700V 200v 3 1/2" 1 1/2" 30p: 15 16V 275v 1 1/2" 1" 20p: 40 40 20V 475v 3" 1" 20p: 4500 900 900V 30v 2 1/2" 1 1/2" 50p: 4000V 35v 3" 1" 20p: 4500V 35v 3" 1 1/2" 50p: 4000V 35v 2" 1" 20p: 470V 25v 1 1/2" 1 1/2" 15p.

**Matched pair of bookshelf speakers.** Teak finish, size 12" 8" 5", 8" 5" 8" ohms ceramic, 5 watts PMS. Complete with din leads. £11.00 pair.

**Thorn TV IF chassis.** 950 series (less valves) £1.75.

**UHF 625 transistor push button tuner** (NSF Telewiken) as used on Decca MS240C. Brand new and boxed. £3.25. Light Dependent Resistors (RCA sq3536) 30p each, 4 for £1.00.

**P-C Boards** (not computer panels) 1 off 6 transistor single wave band. 1 off 4 transistor audio. 1 off 3 transistor £1.60, three boards.

**Rank EVR Teleplayer colour transistor panels.** type and components on new panels listed as follows. £2.50, each panel. Z605-14 off BC148: 2 RCA ca3051 (ic): 1 crystal 4-433618 MHz-Z307-12 off BC148: 1 BC108: 1 BC156: 1 RCA ca3046 (ic): 1 RCA ca3045 (ic): Z608-23 off BC148: 2 BC158-Z612-12 off ME4103: 2 BC-251B: 1 BFY3C

**Mains Droppers,** 10 mixed values. £1.00.

**Edgewise Level meters,** 200uA, size 2" overall 50p.

**Chrome Plastic knots,** 3 types, 4 off each with spring clip, £1.25.

**Die Cast Boxes,** 4 1/2" 3 1/2" 3" 95p: 8 1/2" 5 1/2" 2" £1.20. 8 1/2" 5 1/2" 4" £1.70.

**Aluminium Chassis,** 7 1/2" 5 1/2" 2 1/2" 70p: 10" 7 1/2" 2 1/2" 85p: 11" 7 1/2" 2 1/2" 95p.

**BSR P128,** similar to HT70 single play, with heavy die cast turntable, less cartridge £11.00.

**Transistorised FM tuner head** with A.M. gang, slow motion drive 88-108 Mcs. with circuit diagram, £2.30.

**Mono Amp Transistorised (Mains)** ideal for electric player 8 ohms 2 watts. £3.50.

**Ferguson Stereogram Chassis.** MW/LW VHF with tuning scale 15+5 watts sine wave) 15 ohms £28.50.

ALL ITEMS INCLUDE VAT  
All items post paid in GREAT BRITAIN

**SURPLECTRONICS**  
216 LEAGRAVE ROAD,  
LUTON, LU3 1JD, BEDS.

**TRANSISTORS (p. & p. 10p.)**

All new and full spec.

BC107/8/9, BC147/8/9, BC157/8/9 all 9p  
BF190 25p, BF182/3 40p, BF184 17p,  
BF187 13p, BFW10 55p, 741 8DIL 34p,  
BF336 35p, 2N3771 £1.10, 2N3441 50p,  
BD131 40p.

**EX COMPUTER PC PANELS**

4 x 2in Packed with semiconductors and top quality resistors, capacitors, diodes etc. Guaranteed min. 35 transistors, plus data 25 boards £1 (30p)  
**DURAL EXTRUDED HEATSINKS,** 10D outline, black anodised, drilled for 4 x TO3 transistors 5 x 4 x 1 1/2 40p (15p)  
Sim. to above but for 8 x TO3 5 x 8 x 1 1/2 70p (27p)

**ELECTROLYTICS**

15,000u 30v, 68,000u 16v 65p (22p)  
30,000u 25v 65p (22p)  
4,000u 70v, 3,600u 40v 4 x 2" 55p (15p)  
5,000u 35v 40p (12p)  
20A 100 pV Si recs. 4 for £1 (12p)  
3A 100 pV Si recs. 4 for 50p (8p)  
250 mixed resistors 60p (13p)  
250 mixed capacitors 60p (11p)  
150 mixed HI-ST ABS 60p (11p)  
200 Si planar diodes 60p (8p)  
QH bulbs 12v 55w 50p (7p)  
2N3055 EQUIV 4 for £1 (10p)

Postage and packing shown in brackets  
ADD 8% VAT TO TOTAL

**KEYTRONICS**

(Mail Order only)

44 EARLS COURT ROAD  
LONDON W8. 01-478 8499

**MAINS UNITS for all types of TRANSISTOR EQUIPMENT**

**RUN YOUR TAPE RECORDER OFF AC MAINS**

Mains unit supplied complete and ready to plug into your cassette recorder. (State voltage, make and type of plug required. If in doubt send diagram of recorder socket).

ONLY £2.97

**CAR OWNERS**

Buy a British Made battery eliminator for your car. This unit enables you to run your cassette tape recorder from the car whilst travelling. It is easily fitted and comes complete with fitting instructions. Please state make of cassette, voltage and type of plug required.

ONLY £2.65

**MAINS UNIT FOR TRANSISTOR RADIO ONLY**

For single outputs, £2.42

6v or 9v

For two separate outputs, 6v + 6v. or

9v + 9v. £2.97 per unit.

(Please state outputs required).

All units are completely isolated from mains by double wound transformer ensuring 100% safety.

ALL PRICES INC VAT & P. & P

ALL BRITISH MADE

FULL REFUND IF NOT COMPLETELY SATISFIED

R.C.S. PRODUCTS (RADIO) LTD.

(Dept. P.W.D.)

31 Oliver Road, Walthamstow, London, E17

**SINCLAIR CALCULATORS**

Cambridge Assembled £15.95 (£1.55)  
Sinclair Scientific £22.45 (£2.05)  
Executive with Memory £26.25 (£2.53)  
Executive £22.75 (£2.25)

**FERRANTI ZN64**

IC radio chip with data £1.20 (22p). Also available kit of extra parts to complete a radio £2.45 (42p). Send SAE for free leaflet.

**SINCLAIR PROJECT 31**

AFU £5.95 (70p)  
Z40 £4.45 (60p)  
Z90 £3.95 (70p)  
O18 £6.75 (77p)  
P25 £4.20 (46p)  
P28 £6.85 (82p)  
P28 £6.95 (82p)  
Decoder £6.45 (75p). Trans for P28 £3.35 (50p).  
Tuner £9.95 (£3.05). Stereo £0.60 95 (£1.05).  
Project 805 £2.95 (£2.90)  
Project 805SQ £3.95 (£3.10).

**ECONOMICAL QUADRAPHONICS**

Introducing the Neopler QA10 with contained mixer, quadraphonic synthesizer. Just feed the output of any stereo system (including Project 80 or 803) into it and hook on 4 speakers to obtain the latest experience in sound. Send SAE for free leaflet. Only £15.95 (£1.10).

**SINCLAIR SUPER IC12**

6W rms Power. With 4 page booklet and printed circuit £1.90 (40p).

**NEW SINCLAIR IC20**

High power IC audio amplifier £8.45 (£1.05).

**DELUXE KIT FOR THE IC12**

Includes all parts for the printed circuit and volume, bass and treble controls needed to complete the mono version £1.70 (25p). Stereo model with balance control £3.70 (45p).

**IC12 POWER KIT**

Supplies 28V 0.5 Amps £2.77 (48p).

**LOUDSPEAKERS FOR THE IC12**

5" 8 ohm £1.20 (27p). 5" x 8" 8 ohm £1.95 (37p).

**PREAMP KITS FOR THE IC12**

Type 1 for magnetic pickups, mica and tuners. Mono model £1.40 (25p). Stereo model £2.50 (33p). Type 2 for ceramic or crystal pickups. Mono 70p (19p). Stereo £1.48 (24p).

SEND SAE FOR FREE LEAFLET ON KITS

**BATTERY ELIMINATOR BARGAINS**

The most versatile battery eliminator ever offered. Switched output of 3, 4, 6, 7, 9 and 12V at 500 mA £3.90 (70p). Other eliminators stocked:— 250mA:— 3 way switched model giving 3, 7 and 9V £2.25 (55p). 50mA:— 6V £1.95 (40p), 9V £1.95 (40p), 7.1V cassette type £2.50 (40p), Double 6V + 6V £2.50 (40p), 9V + 9V £2.50 (40p). 500mA:— Heavy duty deluxe models 6V £2.78 (55p), 7.1V £2.78 (55p), 9V £2.78 (55p).

**S-DECS AND T-DECS**


S-DeC £1.98 (31p)  
T-DeC £3.83 (47p)  
µ-DeC A £3.95 (51p)  
µ-DeC B £6.99 (81p)  
IC carriers:— 18 dit: plain kit (15p) with socket £1.77 (25p)  
10 TO3: plain 70p (15p). With socket £1.68 (24p).  
Experiment guides:— A £1.50 (26p), B £1.77 (29p), C 90p (18p), D £2.40 (35p), E £4.20 (53p).

**SWANLEY ELECTRONICS**  
PO BOX 68, SWANLEY,  
KENT BR8 8TQ.


Please add the sum shown in brackets after the price to cover the cost of Post and new VAT. Official credit orders from schools etc. welcome. No V.A.T. charged on overseas orders.
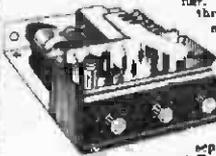
## SUPERSOUND 13 HI-FI MONO AMPLIFIER

A superb solid state audio amplifier. Brand new components throughout. 5 silicon transistors plus 2 power output transistors in push-pull. Full wave rectification. Output approx. 15 watts r.m.s. into 8 ohm. Frequency response 12Hz-30KHz  $\pm$  3dB. Fully integrated pre-amplifier stage with separate Volume, Bass Boost and Treble cut controls. Suitable for 8-15 ohm speakers. Input for ceramic or crystal cartridges. Sensitivity approx. 40mV for full output. Supplied ready built and tested, with knobs, control panel, input and output plugs. Overall size 8" high x 6" wide x 7 1/2" deep. AU 200720V. PRICE £11.50. P. & P. 50p.



## DE LUXE STEREO AMPLIFIER

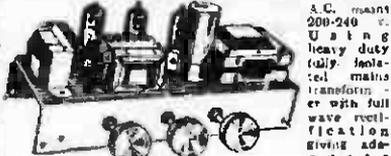

A.C. mains 200-240 V. U.S.A. & heavy duty fully isolated mains transformer with full wave rectification giving additional smoothing with negligible hum. Valve line up: 2 x ELL06 Triode Pentodes, 1 x EZ90 as rectifier. Two dual potentiometers are provided for bass and treble control, giving bass and treble boost and cut. A dual volume control is used. Balance of the left and right hand channels can be adjusted by means of a separate 'Balance' control fitted at the rear of the chassis. Input sensitivity is approximately 300mV for full peak output of 4 watts per channel (8 watts mono), into 8 ohm speakers. Full negative feedback in a carefully calculated circuit, allows high volume levels to be used with negligible distortion. Supplied complete with knobs, chassis size 11 1/2" x 4 1/2". Overall height including valves 6". Ready built & tested to a high standard. £10.25. P. & P. 50p.

**POWER SUPPLY UNIT 200720V. A.C. Input.** Four wire-bred fully smoothed D.C. outputs giving 6, 5 and 7.5, and 9v. and 12v. at 1 amp on load. Fitted insulated output terminals and pilot lamp indicator. Harmonic finish metal case overall size 6" x 3 1/2" x 2 1/2". Suitable for Transistor Radio, T9C Recorders, Amplifiers, etc. etc. Ready built and tested. **PRICE £4.90 P. & P. 35p.**

**VYNAIR & REIMS SPEAKERS & CABINET FABRICS** approx. 34 in. x 10 in. Output £1.10. Length P. & P. 15p. Per yd. (incl. 1 yd.). S.A.E. for samples.

**HARVERSON'S SUPER MONO AMPLIFIER**  
A super quality gram amplifier using a double wound fully insulated main transformer, rectifier and ELL22 triode pentode valve as audio amplifier and power output stage. Impedance 3 ohms. Output approx. 3.6 watts. Volume and tone controls. Chassis size only 7 1/2" wide x 3 1/2" deep x 4 1/2" high overall. A.C. mains 200/240V. Supplied absolutely Brand New completely wired and tested with good quality output transformer. **£3.78 P. & P. 40p. BARGAIN PRICE**

**BRAND NEW MULTI-RATIO MAINS TRANSFORMERS** Giving 13 alternatives. Primary: 0-210-240V. Secondary combinations 0-5-10-15-20-30-40-50-60V. Full wave at 1 amp. or 10-10-10, 20-20-30, 30-30-30, at 2 amps full wave. Size 3 1/2" long x 3 1/2" wide x 3 1/2" deep. Price £2.51. P. & P. 40p.

**MAINS TRANSFORMER.** For transistor power supplies. Pri. 200/240V. Sec. 0-5-9 at 500 mA. £1.10. P. & P. 25p. Pri. 200/240V. Sec. 19-0-12 at 1 amp. £1.21. P. & P. 25p. Pri. 200/240V. Sec. 10-0-10 at 2 amp. £1.28. P. & P. 35p.

**HI-GRADE COPPER LAMINATE BOARDS** 3 1/2" x 5". Five for 60p plus 30p P. & P.

See Personal callers only  
Limited number of stereo padogram chassis covering LW MW/PW bands. Mono radio and stereo gram.  
Overall size approx. 18 1/2" W. 5 1/2" H. 8" Depth.  
4 watts per channel output, only £18.20.

**GENERAL PURPOSE HIGH STABILITY TRANSISTOR PRE-AMPLIFIER**  
For P.U. Tape, Mike, Guitar, etc. and suitable for use with valve or transistor equipment. 9-18v. battery or from H.T. line 500/300V. Frequency response 10Hz-20KHz. Gain 250. Solid encapsulation size 1 1/2" x 1 1/2" x 1/2". Brand new complete with instructions. Price 98p. P. & P. 15p.

**HANDBOOK OF TRANSISTOR EQUIVALENTS AND SUBSTITUTES**  
A must for servicemen and home constructors. Including many 1000's of British, U.S.A. European and Japanese transistors. D.N.Y. 40p. Post 5p.  
References Encyclopedias for Electronic Engineers and Designers, covering between them transistor characteristics, diode and transistor equivalents. Many thousands of up to date European types listed.  
Diode Equivalents, 800r Transistor Equivalents, 90p; Transistor Characteristics, 21:15; POST FREE All three together, £2.50

**NEW ISSUE**  
Thyristor, Triac, Diac etc. encyclopedias 95p. Post Free  
6 pole 3 way 2 bank low loss Vaxley type switches 1 1/2 sections. Standard 95p. 2 switches 84p + 10p P. & P.

Open 9.30-5.30 Monday to Friday. 9.30-5 Saturday  
Closed Wednesday.  
A few minutes from South Wimbledon Tube Station.

## HARVERSONIC MAINS OPERATED SOLID STATE STEREO FM TUNER



Enjoy stereo radio at this fabulous low price!  
Designed and styled to match our 10 + 10 amplifier but will suit any other standard stereo amplifier. The design incorporates the very latest circuitry techniques with high-gain, low noise IF stages. Automatic frequency control to "lock-on" station and prevent drift. IC stereo decoder for maximum stereo separation. T.E.D. for stereo beacon indicator. Normal output of tuner 100mV. Approximate size 12" wide x 8" deep by 2 1/2" high. Supplied ready built, fully tested and fully guaranteed (not available in kit form). **Price £21.50 Post and Packing 50p.**

**STEREO-DECODER**  
SIZES 2" x 3" x 4" ready built. Pre-aligned and tested. Needs 20-500 mV for 0.1-1V neg. earth operation. Can be fitted to almost any FM VHF radio or tuner. Stereo beacon light can be fitted if required. Full details and instructions (inclusive of hints and tips) supplied. £9.00 plus 10p. P. & P. Stereo beacon light if required 40p extra.



**SPECIAL BARGAIN OFFER!**  
Limited number of BRR C123 Auto Changer De Luxe with lightweight tubular arm and stereo cartridge. **Brand new. ONLY £7.80 + p. & p. 50p.**

**PRECISION ENGINEERED PLINTER**  
Beautifully constructed in heavy gauge "Colocort" plastic coated steel. Resonance free. Designed to take Garrard 1025, 2000, 2002TC, 2500, 3000, 4500, 5100, 5225 II and III, SLS40, Arco etc. or B.B.R. C109, C120, A21 etc. Black leatherette finish. Size 12 1/2" x 14 1/2" x 3 1/2" high approx. 7 1/2" high including mild smoked acrylic cover. **NOW ONLY £4.75. P. & P. 70p.**

**LATEST ACOS 90118C mono compatible cartridge** with T/O stylus for LP/EP/78. Universal mounting bracket. £1.46. P. & P. 15p.

**SONOTONE STANC COMPATIBLE STEREO CARTRIDGE** T/O stylus Diamond Stereo LP and Rappure 78. **ONLY £2.27. P. & P. 10p.** Also available fitted with Twin Diamond T/O stylus for Stereo LP, EP, 78, 8, & P. 15p.

**LATEST T/O STEREO/COMPATIBLE CARTRIDGE** for EP/LP/EP/78. £1.50. P. & P. 15p. LATEST T/O **MONO COMPATIBLE CARTRIDGE** for playing EP/LP/78 mono or stereo records on mono equipment. Only £1.47. P. & P. 10p.

**QUALITY RECORD PLAYER AMPLIFIER ME. II**  
A top quality record player amplifier employing heavy duty double wound mains transformer, EC503, EL24, and rectifier, Brevary 8A, Treble and Volume control. Complete with output transformer matched for 3 ohm speaker. Size 7 1/2" wide x 3 1/2" deep x 6 1/2" high. Ready built and tested. **PRICE £4.61. P. & P. 50p.**  
**ALSO AVAILABLE** mounted on board with output transformer and speaker. **PRICE £4.20. P. & P. 50p.**

## HI-FI LOUSPEAKER SYSTEMS

Beautifully made leak finish enclosure with most attractive Tuxan/Vynair front. Size 16" high x 10 1/2" wide x 6" deep. Fitted with E.M.I. Ceramic Magnet 15" x 8" bass unit, two E.M.I. tweeter units and crossover. Maximum power handling 10 watts. Available 3 or 8 or 15 ohm impedance.

**OUR PRICE £9.10** Carr. 90p  
Cabinet Available Separately £4.80, Carr. 90p.  
Also available in 8 ohms with EMI 15" x 8" bass speaker with parasitic tweeter £7.80, Carr. 90p.

## LOUDSPEAKER BARGAINS

5in. 3ohm £1.25. P. & P. 10p. 7x4in. 3ohm £1.40. P. & P. 20p. 10" x 4in. 3 or 15 ohm £2.10. P. & P. 30p. E.M.I. 8" x 6in. 3ohm with high flux magnet £1.70. P. & P. 20p. E.M.I. 15" x 8in. with high flux retentive magnet with built-in tweeter 3, 8 or 15 ohm £2.50. P. & P. 30p. E.M.I. 15" x 8in. 3, 8 or 15 ohm with two built-in tweeters and crossover network £4.00. P. & P. 30p. E.M.I. tweeter. Approx. 31". Available 5 or 8 or 15 ohms. £1.25 + 20p. v. p.

**BRAND NEW** Bakers Loudspeakers at substantial discounts. 12in. MID Bakers, 8 or 15 ohms. Size with current production by well-known British maker. Now with Hifist ceramic terminal magnet assembly £7.75. Guitar models: 25w £7.75, 35w £9.50. P. & P. 45p.

18in. "VRA" TWIN CORE LOUSPEAKER. 10 watts peak handling. 3 or 8 or 15 ohm (state which) £2.70. P. & P. 35p.

"POLY PLANAR" WAFER-TYPE, WIDE RANGE ELECTRO-DYNAMIC SPEAKER  
Size 11" x 14 1/2" x 1 1/2" deep. Weight 180g. Power handling 20W rms. (40W peak). Impedance 8 ohm only. Response 40Hz-20KHz. (Can be mounted on ceiling, walls, doors, under tables, etc. and used with or without baffle. Send S.A.E. for full details. Only 60¢ each plus P. & P. 34p.

## HARVERSONIC SUPER SOUND 10 + 10 STEREO AMPLIFIER KIT




A really first-class Hi-Fi Stereo Amplifier Kit. Uses 14 transistors including Silicon Transistors in the last five stages on each channel resulting in even lower noise level, with improved sensitivity. Integrated pre-amp with Bass, Treble and two Volume Controls. Suitable for use with Ceramic or Crystal cartridges. Very simple to modify to suit magnetic cartridge—Instructions included. Output stage for any speakers from 8 to 15 ohms. Compact design. All parts supplied including drilled metalwork high quality ready drilled printed circuit board with component identification clearly marked, smart brushed anodised aluminium front panel with matching knobs, wire, solder, nuts, bolts—no extras to buy. Simple step by step instructions enable any constructor to build an amplifier to be proud of. Brief specifications: Power output: 14 watts r.m.s. per channel into 8 ohms. Frequency response:  $\pm 3dB$  12-30,000 Hz. Sensitivity: better than 80mV into 1M $\Omega$ . Full power bandwidth:  $\pm 3dB$  12-15,000 Hz. Bass boost approx. to  $\pm 12dB$ . Treble cut approx. to  $-16dB$ . Negative feedback 10dB over main amp. Power requirements 25v. at 1-0 amp. Overall Size: 12" W. x 6" D. x 2 1/2" H.

Fully detailed 7 page construction manual and parts list free with kit or send 10p plus large S.A.E.

**AMPLIFIER KIT** £11.34 P. & P. 50p  
(Magnetic input components 33p extra)  
**POWER PACK KIT** £2.46 P. & P. 40p  
**CABINET** £4.74 P. & P. 40p  
(Post Free if all units purchased at same time)

Full alter after service  
Also available ready built and tested £24.50. Post Free.

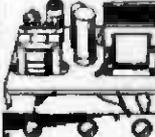Note: The above amplifier is suitable for feeding two mono sources into inputs (e.g. radio, twin record decks, etc.) and will then provide mixing and fading facilities for red-tan powered Hi-Fi Discography, etc.




**3-VALVE AUDIO AMPLIFIER HA34 MK II**  
Designed for Hi-Fi reproduction of records. A.C. Mains operation. Ready built on plated brass gang metal chassis. Size 7 1/2" x 4" x 4 1/2". Incorporates ECC83, EL84, EZ90 valves. Heavy duty, double wound mains transformer and output transformer matched for 3 ohm speaker. Separate volume control and new with improved wide range tone controls giving bass and treble lift and cut. Negative feedback line. Output 4 watts. Front panel can be detached and leads extended for remote mounting of controls. Complete with knobs, valves, etc. wired and tested for only £6.80. P. & P. 45p.

**HSL "FOUR" AMPLIFIER KIT.** Similar in appearance to HA34 above but employs entirely different and advanced circuitry. Complete set of Parts, etc £4.98 P. & P. 45p.
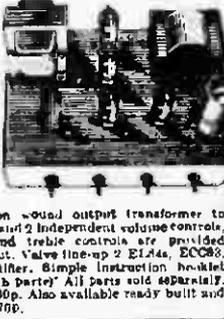
## 10/14 WATT HI-FI AMPLIFIER KIT

A stylish finished monaural amplifier with an output of 14 watts from 2 EL84s in push-pull. Super reproduction of both music and speech, with negligible hum, separate inputs for mike and gram allow records and announcements to follow each other. Fully shrouded section wound output transformer to match 3-15  $\Omega$  speaker and 2 independent volume controls, and separate bass and treble controls are provided giving deep lift and cut. Valve line-up 2 EL84s, ECC83, EF86 and EZ90 rectifier. Simple instruction booklet 10p + SAE (Free with Party) All parts sold separately. **ONLY £9.00 P. & P. 60p.** Also available ready built and tested £12.75 P. & P. 70p.



## HI-FI STEREO HEADPHONES

Adjustable headband with comfortable Bestbeam ear-muffs. Wired and fitted with standard stereo tin lock plug. Frequency response 10-15,000Hz. Matching impedance 8-16 ohms. Easily converted for Mono. **PRICE £3.24. P. & P. 25p.**

**PRICES INCLUDE VAT at 8%**

# HARVERSON SURPLUS CO. LTD.

(Deot. P.W.) 170 HIGH ST., MERTON, LONDON, S.W.19 Tel.: 01-540 3985

SEND STAMPED, ADDRESSED ENVELOPE WITH ALL ENQUIRIES

(Please write clearly)  
PLEASE NOTE: P. & P. CHARGES QUOTED APPLY TO U.K. ONLY & P. ON OVERSEAS ORDERS CHARGED EXTRA.



# RSC 100 watt DISCO SYSTEM



Units listed below  
 (a) DISCOMASTER TWIN TURNTABLE CONSOLE with integral 100W amplifier  
 (b) PAIR OF HI-FI HEAD- PHONES  
 (c) MATCHING DYNAMIC "MIKE" (attached to 1" phone)  
 (d) PAIR 50 WATT SPEAKERS Black Rexine covered Cabinets Size approx. 18" x 18" x 8"  
 (a) (b) (c) & (d) Carr. £3-00

## RSC TDI DISCO CONSOLE

Incorporating twin Garrard SP25 or BSR MP60 type turntables and Sonolone or Accos Cartridges with diamond styli. Separate Vol. controls for each turntable. Also MONITORING FACILITIES, plus Treble and Bass Controls. Separate input for 'mike' with vol. control switch. Black 'vinyl' covered Cabinet with lid, see illustration on left. Or Dep. £9-00 and 18 fortnightly pymts. £75-00 Carr. £1-50

DEP. £19-95 & 19 fortnightly payments of £7-87 (Total £169-48)

### DISCOMASTER TWIN TURNTABLE POWER CONSOLE

Garrard SP25 or McDonald MF60 turntables. Sonotone or Accos cartridges with diamond styl. Facilities as TDI Console but with built-in 100 watt Power Amplifier, complete with lid. Or Deposit £11-48 and 18 fortnightly payments £5-74 Carr. £2-50 (Total £114-80) **£99-95**

### R.S.C. COLUMN SPEAKERS

All types 15 Ohms covered in Rexine and Vynair  
**TYPE C132 30-40 WATTS** Fitted two exceptionally efficient, low feedback h/w characteristic high flux 13" x 8" 20 watt speakers. Terms: Dep. £3-95 and 8 m'thly payments £2-87 (Total £25-81) Carr. 65p. **£19-95**

**IDEAL FOR VOCALISTS AND PUBLIC ADDRESS**  
**TYPE C8/70 70 WATTS.** Fitted three 12" 25 watt Highly sensitive high flux speakers with high power voice coils. Size approx. 54" x 14" x 11". Dep. £5-11 & 8 m'thly pymts. £5-11 **£39-95** (Total £45-99) Carr. 85p

### FANE ULTRA HIGH POWER LOUDSPEAKERS

All power ratings are R.M.S. continuous. 2 YEARS' GUARANTEE High flux ceramo magnets. ALL CARRIAGE FREE.

'POP' 100	'POP' 60	'POP' 50
18" 100 Watt 14,000 Gauss 8/15Ω	15" 60 Watt 14,000 gauss 8/15Ω	12" 50 Watt 13,000 gauss 15Ω
<b>£29-95</b> Dep: £3-80 and 5 m'thly payments £3-80 (Total £24-20)	<b>£16-95</b> Dep. £2-17 and 8 m'thly payments. £2-17 (Total £19-53)	Terms for pairs Dep. £3-90 & 8 m'thly pymts £3-16 Total £29-18 PAIR SUITABLE ALL PURPOSES

### FANE POP '55' PH50 Power Tweeter

12" 60 watt 15000 gauss 8-16Ω **£15-99** 50w when used with rec. filter provides improved vocal sound **£5-95**

### FANE SPEAKERS 'POP' 25/2 12 in. 30 WATT

Dual Cone 15 Ω (for uses other than Bass Guitar or Electronic Organ). Carr. free **£8-95** CREDIT TERMS (PAIRS ONLY) Dep. £2-80 & 8 m'thly pymts. £2-80 (Total £21-20)

### GROUP EQUIPMENT PACKAGE OFFERS

F.A.L. PHASE 50 MK. III AMPLIFIER	£48-85	PACKAGE PRICE
PR. FANE POP 25/2 12" L/SPEAKERS	£17-90	
Terms: Deposit £7-35 and 8 monthly payments of £7-35 (Total £66-15)	<b>£61-85</b>	<b>£56-95</b> carr. £1-10
F.A.L. PHASE 60 MK.III AMPLIFIER	£43-95	PACKAGE PRICE
PR. FANE POP 60 L/SPEAKERS	£25-90	
Terms: Deposit £22-00 and 12 monthly payments of £4-20 (Total £78-40)	<b>£69-85</b>	<b>£63-95</b> carr. £1-10
F.A.L. PHASE 50 AMPLIFIER	£43-95	PACKAGE PRICE
PAIR 12/20 SPEKRS (in Cabinets)	£25-90	
Terms: Deposit £22-00 and 12 monthly payments £4-20 (Total £78-40)	<b>£69-85</b>	<b>£63-95</b> carr. £2-00

### HIGH QUALITY LOUDSPEAKER UNITS

ALL TWO TONE REXINE AND VYNAIR FINISH  
**L125 50 WATT Fitted pair of 12" 30 watt high flux speakers for conservative rating. Impedance 8-15 ohms. Carr. £1-50**  
 Or deposit £5-11 and 8 monthly pmts. of £5-11. Total **£45-99**  
**L12/25G 12" 25 WATT 13,000 lines 15 ohms Terms for Pairs. Dep. £3-32 & 8 m'thly pymts £3-32 £12-95** Carr. 65p.  
**L12/10-15 WATT Veneered cabinet 12" unit 8-15 ohm. Approx. 14" x 14" x 9". Carr. 65p. Terms for Pairs. Dep. £2-05 & 8 m'thly pymts £2-05 (Total £18-45).** **£7-95**

### ALL RSC PRICES INCLUDE VAT

INTEREST CHARGES REFUNDED on Credit Purchases settled in 3 months



### MINSTREL 8W GUITAR AMP.

Incorporating Tremolo and 13" x 8" or 10" Speaker. Output 8 watts R.M.S. Continuous. 3 Jack Inputs for Microphone and Instrument. Mains Neon Controls: Volume, Tone, Tremolo Speed Tremolo Intensity. Terms: Deposit £4-40 and 8 monthly payments £2-87 (Total £25-76) Carr. free **£19-95**

### FANE CRESCENDO SPEAKERS



Full range available at all BRANCHES

### FAL MAESTRO COMBINED 30W AMPLIFIER AND 18" LOUDSPEAKER

For Lead Guitar, Mic, Gram, Radio. Tap (Not for use with Bass instruments) Inc. 3 inputs and 2 vol controls plus Treble & Bass, TREMOLO with associated controls. Attractively finished in black with silver-finished fascia. Compact size. Fitted carrying handle. Terms: Deposit £5-59 and 8 monthly payments £5-59 (Total £50-81) **£43-74** Carriage free

Also RSC PHANTOM '50' Rating 50w £49-95 Carr. £1-50




### FAL PHASE 50 Mk. III AMPLIFIER 50 WATT

Solid state. 4 Separately controlled inputs Plus master vol. control. In-Bass and Treble Controls. Protective Circuitry against serious output overloading. Output for Speakers 8 to 15 ohms. Size 17" x 7" x 7 1/2". 200-250v. A.C. mains. Output 50 watts music rating. Or deposit £5-75 & 8 monthly payments £5-75. Total **£51-75.** Carr. Free **£43-95**


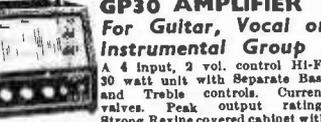
### REGENT 50X 50 WATT AMP.

A powerful high quality unit for lead, rhythm guitar, vocalists, gram, radio, tape. 50w Peak O/P rating. Not for Bass Guitar. ★ Two Fane heavy duty high flux 12in. spkrs. ★ Four Jack inputs and two "Volume Controls for instant use of up to four pick-ups or "mikes". Bass and Treble controls. Send S.A.E. for leaflet. Credit Terms. Deposit £7-98, & 18 fortnightly payments of £3-99 (Total £79-80). Carr. £2-50 **£69-95**  
**REGENT 50B** for Bass Guitar and general purposes. Or Dep. £9-18 & 18 fortnightly payments £4-59. (Total £91-80). Carr. £2-50 **£79-95**



### GP30 AMPLIFIER

For Guitar, Vocal or Instrumental Group  
 A 4 input, 2 vol. control Hi-Fi 30 watt unit with Separate Bass and Treble controls. Current valves. Peak output rating. Strong Rexine covered cabinet with handles. Attractive black/silver P.V.C. fascia. Neon indicator. For 200-250v. A.C. mains. For 8 or 15 ohm speakers. Send S.A.E. for leaflet. Terms: Deposit £5-58 and 8 monthly payments of £3-58 (Total £34-22). Carr. 75p **£29-95**

### COMPLETE PULSAR £99-95

'SOUND TO LITE' SYSTEM  
 Terms: Deposit £11-48 and 18 fortnightly payments £5-74. (Total Credit Price £114-80). Super 8L Unit. 1000 watt per channel. Manual override buttons, 2 spotlights with 6 bulbs (3 sep. colours) 5 yd and 10 yd leads, fitted plugs. Units sold sep. TRADE SUPPLIED. S.A.E. PLEASE WITH ENQUIRIES.

### DISCO LIGHTING AT KEEN PRICES

NEW BRANCHES AT  
**BOLTON, COVENTRY**  
**DONCASTER, PRESTON**  
**and STOCKPORT**

### FAL DISCO PRE-AMPLIFIER

T/Table mixing inputs. Headphone Monitoring. Mic. Jack & Tape inputs. Independent Vol. Control Std. 200-250v A.C. Mains operation **£18-50**

### TITAN 18" 100W SPEAKERS

15 ohms (List £33) Carr. 75p **£25-95**



Barclaycard and Access accepted  
 All items subject to availability. Prices correct at 14.10.74 E. & O.E.

### R.S.C. BRANCHES OPERATE A 5-DAY WEEK

OPEN ALL DAY SATURDAY  
**BRADFORD** 10 North Parade (Closed Wed.). Tel. 25349  
**BOLTON** 23 Deansgate. (Closed Wed.). Tel. 33512  
**BIRMINGHAM** 30/31 Great Western Arcade. Tel. 021-236 1279 (Closed Wed.).  
**COVENTRY** 17 Shelton Square, The Precinct. Tel. 25883  
**DERBY** 97 St. Peter's Street. (Closed Wed.). Tel. 41361  
**DARLINGTON** 19 Northgate (Closed Wed.). Tel. 68043

HI-FI CENTRES LTD.  
**DONCASTER** 3 Queensgate, Waterdale Centre. (Closed Thurs.). Tel. 63069  
**EDINBURGH** 101 Lothian Rd. (Closed Wed.). Tel. 229 9501  
**GLASGOW** 326 Argyle St. (Closed Tues.). Tel. 248 4158  
**HULL** 7 Whitefriargate (Closed Thurs.). Tel. 20305  
**LEICESTER** 32 High Street (Closed Thurs.). Tel. 56420  
**LEEDS** 5-7 County (Mecca) Arcade, Brigate. (Closed Wed.). Tel. 28252  
**LIVERPOOL** 73 Dale St. (Closed Wed.). Tel. 236 3573  
**LONDON** 238 Edware Road, W.2. (Closed Thurs.). Tel. 723 1629

MAIL ORDERS & EXPORT ENQUIRIES TO:-  
**AUDIO HOUSE, HENCONNER LANE, LEEDS, 18.** Tel: Pudsey (09788) 77881.  
 MAIL ORDER MUST NOT BE SENT TO SHOPS  
 TERMS C.W.O. or O.O.D. No O.O.D. under £1.  
 POSTAGE 40p PER ORDER OR AS QUOTED.  
 TRADE SUPPLIED.  
**MANCHESTER** 60A Oldham Street (Closed Wed.). Tel. 236 2778  
**MIDDLESBROUGH** 105 Newport Road (Closed Wed.). Tel. 47098  
**NEWCASTLE UPON TYNE** 24 Newgate Shopping Centre (Closed Wed.). Tel. 21469  
**NOTTINGHAM** 19/19A Market Street (Closed Thurs.). Tel. 48068  
**PRESTON** 41 Friargate Walk, St. Georges Shopp Prec. Tel. 51979  
**SHEFFIELD** 13 Exchange Street (Castle Mkt. Bldg.) (Closed Thurs.). Tel. 20716  
**STOCKPORT** 8 Little Underbank (Closed Thurs.). Tel. 480-0777  
**SUNDERLAND** 5 Market Sq. (Closed Wed.). Tel. 70573

# PARTRIDGE UNWRAP THEIR SUPER PACKAGE COMPLETE RADIO COMMUNICATION STATION FOR THE HOME — CAMPING — BOATING — ETC.

THE TREND LEADER, TRIO'S LATEST QR666 SOLID STATE GEN. COVERAGE RECEIVER £139.82 del. FREE (our risk), with FREE MATCHING HEADPHONES—OR—COMPLETE STATION. On the air in seconds from ANY LOCATION—DEL. FREE (our risk) £157.58.


THE SUPER PARTRIDGE PACKAGE comprises—

- QR666 Receiver, 170 kHz-30 MHz, ALL BANDS, ALL MODES, AM, SSB, CW (opt. FM) for Mains, Batteries, DC ext. supply. A TRULY BEAUTIFUL RECEIVER—EXTENDED BANDSPREAD—NO THERMAL DRIFT—MECH. AND CERAMIC FILTER—DUAL GATE MOSFETS. SINGLE AND DOUBLE CONVERSION—AND SO SIMPLE AND PLEASANT TO OPERATE.
- FREE MATCHING HEADPHONES, lightweight, comfortable, hygienic.
- World Record ALL BAND patented VFA aerial in beautiful gold stove enamel, hammer finish (7ft. 6in. long).
- Made to match, the QR666, the JOYMATCH 111B A.T.U. (also gold stove enamel).
- All necessary cables. **THE COMPLETE RADIO STATION FOR ANY LOCATION.**

JOYSTICK VFA + JOYMATCH 111B (SYSTEM "A") for modern communications receivers £29.58 del.  
 JOYSTICK VFA + JOYMATCH LO-Z500, with RF meter, transmitting 500w. PEP (SYSTEM "H") £36.27 "  
 JOYSTICK VFA + JOYMATCH LO-Z500X With no RF meter, transmitting 500w. PEP (SYSTEM "J")


JOYMATCH tuned AERIAL SYSTEM for ANY MW and SW communications or Solid State receiver .. .. £5.87 del.  
 JOYMATCH Artificial Earth for MW and SW, as used on North Sea Oil Rigs .. .. £3.39 "  
 Communications HEADPHONES, 8 ohm. Suitable most modern comm. receivers .. .. £4.75 "  
 VALVES: Complete replacement set for 9R59DS and 9R59DE .. .. £0.59 "  
 AERIAL WIRE, heavy duty 16 SWG enamelled aluminium. Per 10 metres .. .. £5.87 del.

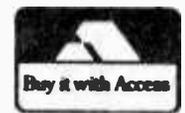Send 4p stamp for complete details of PARTRIDGE PRODUCTS AND TRIO QR666.



BOX 5 **PARTRIDGE**  
*PRODIGE STAIRS WENT ENGLAND*  
**ELECTRONIC**

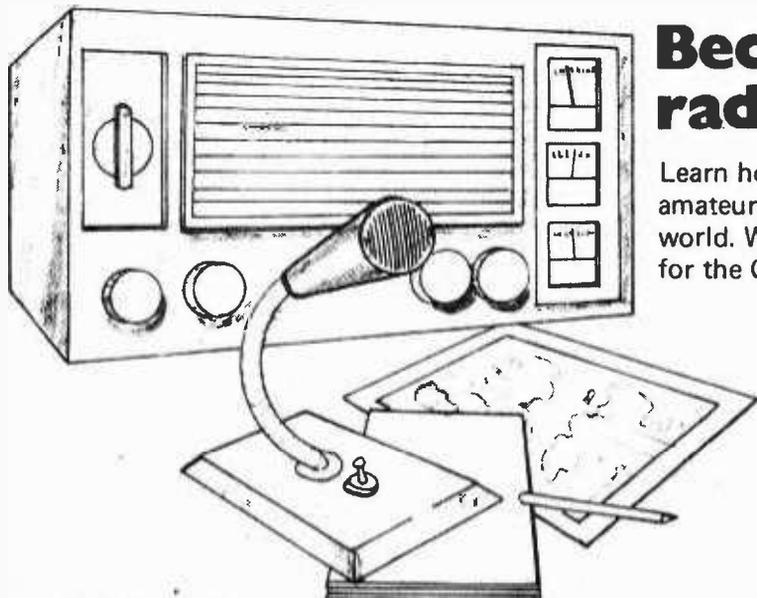G3CED — G3VFA  
 FOR EXPERT ADVICE AND INFORMATION  
 Telephone: 0843 62535 or 62839  
 evenings and weekends



## Become a radio amateur.

Learn how to become a radio-amateur in contact with the whole world. We give skilled preparation for the G.P.O. licence.

**Free!**

Brochure, without obligation to:  
**BRITISH NATIONAL RADIO & ELECTRONICS SCHOOL, Dept.,**  
 P.O. Box 156, Jersey, Channel Islands.

NAME \_\_\_\_\_

ADDRESS \_\_\_\_\_

W.B. 124

Block caps please

# C. T. ELECTRONICS

NOW AT 267 & 270 ACTON LANE, LONDON W4 5DG

Now open—our new components shop. These premises are very much larger and will enable us to have greater stocks than we already have. Having all the components under one roof will now guarantee you speedier service on the counter, and on the mail order side. We have an enormous range of components to choose from. If you are having problems getting your components then come along. We are open from 9.30 a.m. through 6.30 p.m. Monday to Saturday. The nearest underground is Chiswick Park, and there are no parking restrictions.

## SEMICONDUCTORS

AC107	35p	BCY30	40p	MJ340	55p	OC36	85p	TIP41C	95p	2N2846	£1.50
AC123	35p	BCV31	55p	MJ281	£1.25	OC42	40p	TIP42C	£1.10	2N2904	25p
AC128	25p	BC102	55p	MJ281	£1.25	OC44	20p	TIS50	40p	2N2905	25p
AC129	27p	BCY33	45p	MJ2901	£2.20	OC45	20p	ZTX107	15p	2N2906	25p
AC128	28p	BCY34	50p	MJ340	55p	OC70	15p	ZTX300	15p	2N2907	25p
AC176	27p	BCV38	85p	MJ370	75p	OC71	17p	ZTX500	18p	2N2926	12p
ACY17	55p	BCV39	£1.00	MJE371	90p	OC72	20p	ZTX501	20p	2N3025	25p
ACY18	30p	BCY55	£1.00	MJE520	£5.00	OC75	25p	ZTX504	50p	2N3054	25p
ACY19	30p	BCY70	22p	MJE2955	£1.85	OC76	25p	ZTX531	30p	2N3055	25p
ACY20	25p	BCV71	22p	MJE3055	85p	OC77	40p	ZTX550	25p	2N3232	78p
ACY29	15p	BCV72	25p	MM1813	43p	OC81	25p	IN659	8p	2N3325	95p
ACY21	30p	BD121	75p	MM1702	60p	OC83	25p	IN614	8p	2N3702	12p
AD140	80p	BD123	75p	MPF102	45p	OC84	25p	IN616	8p	2N3703	12p
AD149	85p	BD124	80p	MPF103	45p	OC139	30p	IN4001	8p	2N3704	12p
AD161	40p	BD131	75p	(2N5457)	35p	OC140	30p	IN4002	8p	2N3705	12p
AD162	40p	BD132	75p	MPF104	45p	OC170	25p	IN4003	8p	2N3706	12p
AF114	25p	BD153	75p	(2N5458)	35p	OC171	30p	IN4004	10p	2N3707	12p
AF115	25p	BD156	75p	MPF105	45p	OC200	50p	IN4005	12p	2N3708	12p
AF116	25p	BDV11	£1.40	(2N5459)	40p	OC203	15p	IN4007	15p	2N3709	12p
AF117	25p	BDV11	£1.40	MPSA06	30p	OC202	75p	IN4002	12p	2N3711	£2.45
AF118	80p	BDV19	£1.95	MPSA16	30p	TIP29A	48p	IN4148	7p	2N3772	£2.75
AF172	30p	BF152	20p	MPA556	20p	TIP29A	48p	IN696	25p	2N3773	£2.85
ASV28	30p	BF194	14p	MSUJ06	75p	TIP1A	20p	2N697	70p	2N3819	25p
AS221	40p	BF195	15p	MSUJ56	70p	TIP32A	74p	2N698	25p	2N3820	55p
BA120	33p	BFX29	30p	NKT135	35p	TIP33A	£1.05	2N706	12p	2N3886	85p
BA112	50p	BFX84	30p	NKT222	25p	TIP34A	£1.55	2N708A	15p	2N3904	22p
BA114	50p	BFX85	30p	NKT222	25p	TIP35A	£1.55	2N709	15p	2N3905	22p
BA156	15p	BFX86	30p	NKT404	80p	TIP36A	£2.05	2N730	20p	2N4059	12p
BC107	14p	BFX86	30p	NKT773	30p	TIP41A	75p	2N1132	25p	2N4059	12p
BC108	14p	BFY10	35p	NKT774	25p	TIP42A	80p	2N1302	25p	2N4060	12p
BC109	14p	BFY11	35p	OA200	10p	TIP29B	50p	2N1303	25p	2N4061	12p
BC147	12p	BFY50	25p	OA10	20p	TIP30B	66p	2N1304	25p	2N4126	17p
BC148	12p	BFY51	25p	OA47	10p	TIP31B	70p	2N1305	25p	2N4286	15p
BC149	12p	BFY52	25p	OA70	12p	TIP32B	82p	2N1306	25p	2N4287	15p
BC150	14p	BFY53	25p	OA81	10p	TIP33B	£1.12	2N1307	25p	2N4288	15p
BC157	14p	BFY54	25p	OA81	10p	TIP34B	£1.00	2N1308	25p	2N4289	15p
BC158	15p	BSW63	85p	OA90	10p	TIP35B	£2.81	2N1309	25p	2N4290	15p
BC159	15p	BSW68	85p	OA91	10p	TIP36B	£3.84	2N1613	25p	2N4444	£1.80
BC169C	14p	BSY25A	12p	OA200	10p	TIP1A	20p	IN2147	75p	2N4871	35p
BC182	14p	BSY25A	12p	OA202	10p	TIP28B	80p	IN2147	75p	2N4871	35p
BC183	14p	CS26	40p	OA210	35p	TIP29C	71p	2N2160	85p	2N5191	£1.10
BC184	14p	BY100	15p	OA211	36p	TIP30C	78p	2N2217	25p	2N5194	£1.10
BC212	14p	BY126	30p	OA16	90p	TIP31C	85p	2N2218	25p	40360	50p
BC213	14p	BY145	30p	OC10C	85p	TIP32C	85p	40361	50p	40362	50p
BC214	14p	BY164	85p	OC22	55p	TIP33C	£1.90	2N2222	20p	40362	50p
BC236	12p	IS100	15p	OC26	55p	TIP34C	£1.90	2N2224	20p		
BC239	12p	IS103	20p	OC28	85p	TIP35C	£3.20	2N2988	70p		
				OC30	60p	TIP36C	£4.10	2N2846	50p		

## S.C.R.s

CRS1/05	40p
CRS1/10	50p
CRS1/20	60p
CRS1/40	65p
CRS1/60	90p
CRS1/10	82p
CRS3/20	62p
CRS3/40	90p
CRS7/400	£1.00
CRS16/100	85p
CRS16/200	90p
CRS16/600	£1.00
CI06B	45p
CI06D	70p
40669	90p
TIC4	35p
2N444	£1.90
BT10/5004 R	90p

## TRIACS

TXL228B 8A 400V	85p
SC40D	£1.40
SC45D	£1.65
SC45E	£1.70
SC45F	£2.10
SC50D	£2.42
SC50E	£2.70
DIAC	25p

## \*\*SPECIAL OFFERS\*\*

**MINIATURE MAINS TRANSFORMER** PRI 240V, SEC. 12V, 100MA MANUF., Hinchley 51x 70 x 45 x 40mm F.C. 53mm Price 1.99p. 100-80p ea. 1,000-50p ea. 10,000-40p ea.

**3 CORE PVC INSULATED MAINS CABLE** GREY M.L.650 3x7.0mm Price 100-40p ea. 100m-£35, 10,000m-£330, 9-47met. 50V MYLAR FILM CAPACITOR Size 11x 7.5 x 0.85in P.C Mount Price 100-40p ea. 1000-35p ea.

**240V. A.C. SOLENOID** Reversible operation. twin coil. slide approx 2" x 1" x 1/4in 80p ea.

**30 unmarked OC71 transistors** £1.00

**25 UNMARKED 250W Zenerdiodes** 4.7V 5.1V 2V 7.5V 9.1V 10V Measured and tested £1.00

**Tested state voltage required**

**50 GE Grade OA4 equivalent** £1.00

**TRANSFORMER: DOUGLAS P.C. D. 115** 200, 220 SEC 25-0.25-0.6V. 2V. £4.50 - 50p ea.

**TRANSFORMER** PRI 0.115, 160, 205, 225, 245 SEC 35-0.35, 1.2A £4.50 - 50p. p.p.b.

**MULLARD TUBULAR CERAMIC UHF** RIMERS (PROFESSIONAL) 30p

**Type D2 0.8-2.2p** } Price 10p ea.

**801 0.8-2.2p** }

**99.995 DS DS-1-3p** }

**QUANTITY DISCOUNTS PLEASE TELEPHONE**

**1000PF Feedthrough capacitor** 5p ea.

**Miniature tubular P.C trimmers** 80p ea.

**4p 60V Varley 700Ω relay** 10p ea.

**50p ea.**

**TOP VOLTAGE REGULATORS**

**L036 12V 500mA** £1.00 ea.

**L037 15V 450mA** £1.00 ea.

## BRIDGE RECTIFIERS

W02 1A 200V 3p	50p
BY164 1.4A 200V 57p	50p
MDA9522	50p

## ZENER DIODES

1.5W range	25p
3-3V-33V, 5%	11p
10W range	45p
TIL209	20p
HP5082	20p
MA2082R	25p
L.D.R.	20p
ORP12	60p
NE555 Timer	90p

## LINEAR I.C.s

LM309K 5V, 1A, Volt-amp Reg.	£2.10
LM723C 2-37V, 150mA Voltage Reg.	£1.05
MFC4000 250mW Audio	80p
TBAB00 5Watt Audio	£1.50
709C Op Amp D.I.L.	45p
7099	45p
741C Op Amp 8/14 D.I.L./TO99	55p
748C Op Amp D.I.L.	75p
747C Dual Op Amp	£1.20
ZN414 Radio I.C.	£1.25
TAD100 Radio I.C. In. Filler	£1.90
CA3014	£1.55
CA3018	£1.00
CA3026	£1.20
CA3036	£1.60
CA3046	35p
CA3048	£2.35
CA3075	£1.80
CA3076	£4.85
MC1303L	£2.20
SN76023 5W Audio I.C. with circuit	£1.75

## METAL BOXES

### ALUMINIUM BOXES IDEAL FOR VEROBORD WITH BASE

AB7	2 1/2" Lx 3 1/2" Wx 1 1/2" H	50p
AB7	4 1/2" Lx 3 1/2" Wx 1 1/2" H	50p
AB7	6 1/2" Lx 3 1/2" Wx 1 1/2" H	50p
AB10	4 1/2" Lx 4 1/2" Wx 1 1/2" H	50p
AB11	4 1/2" Lx 2 1/2" Wx 1 1/2" H	60p
AB12	3 1/2" Lx 2 1/2" Wx 1 1/2" H	60p
AB13	6 1/2" Lx 4 1/2" Wx 2 1/2" H	80p
AB14	8 1/2" Lx 4 1/2" Wx 2 1/2" H	£1.00
AB16	10 1/2" Lx 4 1/2" Wx 2 1/2" H	£1.22
AB17	10 1/2" Lx 6 1/2" Wx 2 1/2" H	£1.00
AB18	12 1/2" Lx 6 1/2" Wx 2 1/2" H	£1.20
AB19	12 1/2" Lx 8 1/2" Wx 2 1/2" H	£1.60

### ALUMINIUM BOXES WITH SLOPING TOP PANEL—IDEAL FOR PRE-AMP, ETC., USING SLIDER CONTROLS

AB20	8" Long 3" Wide 3/4" High at back 2" High at front 6" Slope to front	£2.00
AB21	With P.K. Screws	£2.20
AB22	As above but 12" long	£2.40

### VAT VU METER

The VAT is calibrated -20 to +3 and 0-100% making it suitable for use as a recording level meter or as a power output indicator.

Dimensions: 130 x 40 x 29mm

### ALSO STOCKED

Electrolytic Capacitors Mullard, Sprague, Lorin etc. Polyester, polystyrene Silver Mica Capacitors, etc. Resistor Networks Potentiometers, carbon, wirewound. Preset, Rectifier, multitrans Antex Soldering Irons, switches, rotary, slide, toggle, etc. Cable, veroboard.


## DIGITAL INTEGRAL CIRCUITS

SN7400	20p	SN7428	50p	SN7473	40p	SN74107	50p	SN74166	£4.00
SN7401	20p	SN7430	50p	SN7474	40p	SN74110	80p	SN74167	£5.25
SN7402	20p	SN7432	42p	SN7475	55p	SN74118	£1.00	SN74170	£1.00
SN7403	20p	SN7433	70p	SN7476	45p	SN74119	£1.00	SN74174	£2.00
SN7404	20p	SN7437	85p	SN7478	45p	SN74122	£1.35	SN74175	£1.35
SN7405	20p	SN7438	85p	SN7479	45p	SN74123	£2.78	SN74177	£1.60
SN7406	30p	SN7440	20p	SN7482	87p	SN74141	£1.00	SN74180	£1.55
SN7407	30p	SN7441A	75p	SN7483	£1.00	SN74145	£1.50	SN74181	£7.00
SN7408	20p	SN7442	55p	SN7484	90p	SN74150	£3.35	SN74182	£2.00
SN7409	45p	SN7443	£1.65	SN7485	85p	SN74151	£1.16	SN74184	£1.50
SN7410	20p	SN7445	£2.00	SN7486	75p	SN74153	£1.35	SN74185A	£2.40
SN7411	23p	SN7446	£2.90	SN7489A	£1.00	SN74154	£2.00	SN74180	£1.95
SN7412	42p	SN7447	£1.75	SN7482	75p	SN74155	£1.55	SN74191	£1.95
SN7413	40p	SN7448	£1.75	SN7481	£1.25	SN74156	£1.55	SN74192	£2.00
SN7416	30p	SN7450	20p	SN7494	80p	SN74157	£1.80	SN74193	£2.00
SN7417	30p	SN7451	20p	SN7495	80p	SN74160	£2.00	SN74194	£2.50
SN7420	20p	SN7453	20p	SN7496	£1.00	SN74161	£2.00	SN74195	£1.85
SN7421	40p	SN7454	85p	SN7497	£1.25	SN74162	£3.40	SN74196	£1.55
SN7423	40p	SN7460	20p	SN74100	£2.50	SN74163	£3.40	SN74197	£1.50
SN7425	40p	SN7470	30p	SN74104	£1.45	SN74164	£2.75	SN74198	£4.00
SN7427	42p	SN7472	30p	SN74105	£1.45	SN74165	£4.00	SN74199	£4.00

QUANTITY DISCOUNTS—12+ 10%, 25+ 15%, 100+ 20%.

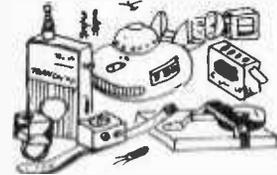
**EXPERIMENTER PRINTED CIRCUIT KIT BUILD 60 INTERESTING PROJECTS**

**CONTENTS:** (1) 2 Copper Laminate Boards 4 1/2" x 2 1/2". (2) 1 Board for Matchbox Radio. (3) 1 Board for Wristwatch Radio, etc. (4) Resistor Degreaser. (5) 16-page Booklet Printed Circuits for Amateurs. (6) 2 Miniature Radio Dials SW/MW/LW. Also free with each kit. (10) Essential Design Data Circuits, Chassis Plans, etc. for 60 TRANSISTORIZED PROJECTS. Circuits to suit everyone's requirements. Price \$1. post paid.



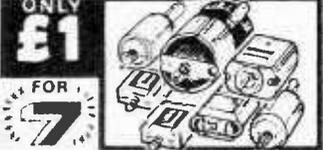**RECORD PLAYBACK HEADS (TRUVOX)**

Individual prices of these are:  
2 track record playback heads 50p each.  
4 track record playback heads 72p each.  
Erase heads are also available separately:  
2 track 35p; 4 track 55p.  
MV metal mounting shields 20p each.  
2 track-heads already fixed on heavy mounting plate with shield \$1.25.



**ELECTRIC MOTORS**

7 powerful battery motors as used in racing cars and power models. Output and types vary to make them suitable for hundreds of different projects—tools, toys, models, etc. All brand new, reversible and for 1 1/2 to 12v. Bats., wiring diagrams included. Post and VAT 30p.

**FREE** Details of how to make miniature power station.

**BSR TAPE DECK TWIN CHANNEL**  
Mounted on a wooden plinth with amplifier. Not new, but unused. Originally intended for schools teaching system. The tape deck is perfectly standard and has the usual record, playback and fast rewind controls. Limited quantity—only 25-50 plus £1 post and insurance.

**BATTERY SWITCH**  
Famous Atlas in metal case with meter. Output leads terminated by crocodile clips. For 6 or 12v charging simply by changing plug on front panel. Ready built, new and still in maker's original packing. Two models: 1 1/2 amp \$1.99 and 3-4 amp \$2.95. Please add 40p postage for one and 75p postage for two.

**TIME SWITCH**  
Smith's mains driven clock with 15 amp switch, also notes showing how you can wake up with music playing, kettle boiling or come home to a warm house, warn off burglars, keep pet warm, have your heating bills, etc. \$1.95.

**RELAY BARGAIN**  
Type 600 relay, 2 changeover one open and one closed contact. Twin 500 ohm coils make this suitable for closing off DC 6v, DC 12v, DC 24v or AC mains using resistor and rectifier. 33p each. Resistor and rectifier 20p extra.

**BATTERY ELIMINATORS**  
Kit of parts comprising mains transformer, rectifier and necessary smoothing components with instructions, showing how to make up for 6v, 9v or 12v types.  
Radio from mains \$1.90  
Cassette from mains \$1.50  
Cassette or radio from car (stabilized) \$2.10

**AMPLIFIER PANELS**

Very nice looking, polished black pre-painted with fixing holes. 6 phono sockets and changeover slide switch and is printed as sketch. Price is 30p.

**RADIO STETHOSCOPE**  
Easiest way to fault find—traces signal from aerial to speaker—when signal stops you've found the fault. Use it on Radio, TV, amplifier, anything—complete kit comprises two special transistors and all parts including probe tube and crystal earpiece. \$2.80—twin stethoet instead of earpiece 85p extra—post and ins. 20p.

**CENTRIFUGAL BLOWER**  
Miniature mains driven blower centrifugal type blower unit by Woods. Powerful but specially built for quiet running—driven by cushioned induction motor with specially built low noise bearings. Overall size 4 1/2" x 4 1/2" x 4". When mounted by flange, air is blown into the equipment but to suck air out, mount it from centre using clamp. Ideal for cooling electrical equipment or fitting into a cooker hood, film drying cabinet or for removing flux smoke when soldering, etc. etc. A real bargain at \$2.05.

**TANGENTIAL HEATER UNIT**  
This heater unit is the very latest type, most efficient, and quiet running. Is as fitted in Hoover and blower heaters. Comprises motor, insulator, 2kW. element allowing switching 1, 2kW. and with thermal safety cut-out. Can be fitted into any metal line case or cabinet. Only needs control switch. \$2.75. Don't miss this. Control Switch, 49p. P. & F. 40p.

**MULLARD UNILEX STEREO SYSTEM**  
There is no doubt that it is a good system, we believe that for the money it is without comparison. We demonstrate gladly at our Tamworth Road depot. Prices of the individual items for this—  
1 Unilex Amplifier Ref. EP.9000 \$1.40  
1 Unilex Pre-Amp Ref. EP.9001 \$1.80  
1 Unilex Power Unit Ref. EP.9002 \$2.30  
1 Control panel kit with spun aluminium faced knobs \$2.50. Or the complete outfit—\$11.90 post paid.  
Pair of 15 ohm speakers made by E.M.I. are also available if required. \$3.80 the pair. No extra postage if ordered with the above, otherwise add 25p.

**SHORTWAVE CRYSTAL SET**  
Although this uses no battery it gives really amazing results. You will receive an amazing assortment of stations over the 19.25-31.39 metre bands—Kit contains chassis front panel and all the parts. \$1.25—crystal carphone 35p.

**THIS MONTHS SNIPS**  
**AM/FM TUNER**  
Unit made by the American GEC company. 8 transistor, all-wired ready to work. Complete with tuner condenser, needs only scale and pointer. Tunes AM range 540 to 1620 KHz, FM range 88 to 108 MHz. Switches for on-off and AFC. Output for MXP or direct. Special snip price \$5 plus 30p post. Three or more post free.

**7 WATT STEREO AMPLIFIER**  
Again by the American GEC company. This has exceptionally good tone quality. Is complete with pre-amp and treble base, volume and balance controls. Also has mains smoothing circuit and rectifiers so requires only mains transformer. Output for 15 ohm speakers. Inputs for tuner pick-up, mike, etc.  
Special snip price \$6 plus 30p post. Three or more post free.

**DIGITAL DISPLAY UNIT 'DIGIVISOR'**  
A precision instrument consisting basically of a 12 volt lamp focused by a lens system to shine through a numbered scale onto a ground glass front screen, the number being selected by applying a different voltage of the coil. Overall size approx. 2 1/2" x 1 1/2" x 4 1/2". Price \$2.50.

**TAPE DECK**  
In metal case with carrying handle, heavy fly wheel and capstan drive. Tape speed 3 1/2. Mains operated on metal platform with tape head and guide. Not new but guaranteed perfect. Price \$1.95 plus 21p post and insurance.

**HORSTMANN 24-HOUR TIME SWITCH**  
With 6 position programmer when fitted to hot water systems this could programme as follows—  
Programme Hot Water Central Heating  
0 Off Off  
1 Twice Daily Off  
2 All Day Off  
3 Twice Daily Twice Daily  
4 All Day All Day  
5 Continuously Continuously

Suitable, of course, to programme other than central heating and hot water, for instance, programme upstairs and downstairs electric heating or heating and cooling or taped music and radio. In fact there is no limit to the versatility of this Programmer. Mains operated. Size 3in. x 3in. x 2in. deep. Price \$2.95 as illustrated but less case.

**WANT A CHEAP OSCILLOSCOPE**  
We offer this month a laboratory type instrument made by G.E.C. for their communications laboratory. In a steel case with carrying handle. It is mains operated and has its own internal time base and plenty of room to add another base if you wish. Probable cost of this instrument is in excess of £100. We offer this tested and in working order. \$17.50 plus 22c carriage for first 200 miles then \$1 for each 100 miles after.

**OIL PUMP**  
Driven by Redmond Motor of approx. 1/20th horse power, pump originally intended for oil fired boilers etc. with normal inlet and outlet pipes and unions. \$2.15 plus 30p post and insurance.

**TINY BATTERY MOTOR**  
Works off 1 1/2 or 3v requires no on/off switch as it will not draw current until it is spinning. Approx. 1 1/2" long, 1/2" diameter. Ideal for hand held fan, propeller driven model etc. 20p each, 10 for \$1.80.

**LUMINOUS ROCKER SWITCH ON/OFF**  
Luminous Rocker switch on/off. Panel mounting, snaps into a 1" hole. Rated at 10A 250v. 15p each or 10 for \$1.35.

**TERMS:**—  
Add 8% V.A.T.  
Send postage where quoted—other items, post free if order for these items is £6.00. otherwise add 30p.

**AUTOMATIC EMERGENCY LIGHTING**  
Power cut days will soon be upon us. Our simple kit makes any light a fail-safe light. Kit containing relay and rectifiers and data, only 65p each. 10 or more 60p each. Suitable case 40p extra.

**PORTABLE CABINET OFFER**  
A nicely made portable cabinet, soft padded black finish intended for portable stereo system. Dimensions as sketch. With motor horn cut out for Garrard SP 25. This was obviously a very costly cabinet originally made for a deluxe record player. Offered at \$1.95 plus 21c carriage free if bought with the Garrard or NRI record decks.

**LIGHT DIMMER KIT**  
For dimming up to 250w without heat sink or 750w with heat sink. This comprises, quadrate, variable control potentiometer, condenser, resistors, tag strip for mounting and data. Price \$1.50.

**MACLAREN THERMOSTAT**  
Make and break 20A a.c. with the sensor probe coupled by a 2 feet capillary covering range of 10-100°C—complete with large engraved control knob. Price 85p.

**WATERPROOF HEATING ELEMENT**  
13 yards length 35W. Self-regulating temperature control 65p post free.

**TREASURE TRACER**  
Complete Kit (except wooden battens) to make the metal detector as the circuit in Practical Wireless August issue. \$4.80 plus 20p post and insurance.

**MAINS MOTOR**  
Precision made—as used in record decks and tape recorders—ideal also for extractor fans, blower, heaters, etc. New and perfect. Snip at 85p. Postage 20p for first one then 10p for each one ordered.  
1" stackmotor 94p.  
1 1/2" stackmotor \$1.10.

**NEED A SPECIAL SWITCH**  
Double Leaf Contact. Very slight pressure closes both contacts. 5p each, 10 for 60p. Plastic pushrod suitable for operating. 6p each. 10 for 54p.

**AMPLIFIER IN CASE WITH SPEAKER**  
Marketed by British Relay under the name Luxistor. This is in a very neat looking cabinet and is ideal around the home or in the workshop for trouble shooting or for testing out a quick lash up. Size approx. 9 1/2" x 6 1/2" x 3 1/2" deep. Input is via a matching transformer and volume control and amplifier may be powered by an internal 9v battery or an external 110v source. Speaker is an R-A elliptical 6" x 3 1/4" 10,000 gauss. The amplifier proper is a Newmarket model ref. P.C.4. Price \$2.95 each. 10 for \$21.50. Post and insurance 20p.

**12 VOLT 1 1/2 AMP POWER PACK**  
This comprises double-wound 230/240V mains transformer with full wave rectifier and 2000 mfd/smoothing. Price \$2.20 + p. & p. 20p.

**Heavy Duty Mains Power Pack.** Output voltage adjustable from 15-40V in steps—maximum load 250W—that is from 6 amp at 40V to 15 amp at 15V. This really is a high power heavy duty unit with dozens of workshop uses. Output voltage adjustment is very quick—simply interchange push-on leads. Silicon rectifiers and smoothing by 3,000mF. Price \$6.33 plus 65p post.

**HEADPHONE STEREO AMP.**  
With volume, balance and tone control. Output approx. 2 watt into 22 ohm speaker but will operate with reduced output into 16 ohm or 8 ohm headphones. Power supply 14v AC (We can supply suitable transformer—80p). The amplifier has all controls mounted and is ready to slip into a simple box. Price \$2.99 plus 60p post and insurance.

**J. BULL (ELECTRICAL) LTD.**  
(Dept. PW), 102/103 TAMWORTH RD., CROYDON CRO IX.

# ELECTROVALUE

APPOINTED STOCKISTS FOR SIEMENS QUALITY PRODUCTS

Present

top quality electronic components for price-minded buyers

112 p. CATALOGUE · FREE POSTAGE (U.K.) · ATTRACTIVE DISCOUNTS · SPECS. GUARANTEED

## A 100 OF THE BEST

From our transistor stock

2N1307	47p	BC149C	14p
2N2844	51p	BC165B	15p
2N3053	26p	BC159	15p
2N3054	66p	BC167B	13p
2N3055	78p	BC168B	12p
2N3702	11p	BC169B	12p
2N3703	10p	BC169C	12p
2N3704	19p	BC179B	26p
2N3705	16p	BC182L	26p
2N3794	18p	BC184L	26p
2N3810	25p	BC212L	12p
2N4082	11p	BC214L	14p
2N4443	85p	BC257A	14p
2N5082	67p	BC259B	14p
2N5163	28p	BCY38	8p
2N5490	22p	BD130	86p
40351	45p	BD131	41p
40362	44p	BD132	42p
40622	46p	BD138	87p
40636	41p	BD139	79p
40689	41-10	BDY20	82p
AC128	17p	BF194	15p
AC181R	22p	BFR20	23p
AC150	21p	BFR79	23p
AC183K	27p	BFX29	33p
AC178	24p	BFX34	27p
AC170K	38p	BFY51	23p
AC187K	31p	BRY30	45p
AC188K	29p	BY164	51p
AD133	41-12	C106B1	62p
AD136	41-11	C106D1	62p
AD149	45p	C1408	78p
A D161	42p	MJ481	21-29
AD162	48p	MJ481	21-29
AF200U	70p	MJ2955	80p
AF230	66p	MJE371	80p
B1906	36p	MJE371	81p
BA126	21p	MJE2955	81p
BS113	24p	MJE2955	80p
BS105	34p	OA91	9p
BS109	18p	SD4	9p
BC107A	15p	TIP31A	78p
BC107B	15p	TIP32A	80p
BC108B	12p	TIP41A	80p
BC108C	16p	TIP42A	81-86
BC109B	18p	WC2	20p
BC109C	18p	ZTX300	14p
BC147A	12p	ZTX304	23p
BC147B	13p	ZTX304	14p
BC148B	12p	ZTX304	14p

100 MORE IN CATALOGUE 7

## BAXANDALL SPEAKER KIT

As designed by P. J. Baxandall and described originally in "Wireless World." Simple to assemble, fantastically good results and a greater money saver. Carries 10 watts RMS. 15 ohms impedance. Size 18in x 12in x 10in. Complete kit including pack-flat cabinet. £14.99.

The size and weight of this product oblige us to charge 70p post cost of cart. in U.K. Equivalents Assembly. £2.30.

Loudspeaker Unit 50R100. £2.45. Cabinet kit to Baxandall design, £10.45. Cross-over choke for additional weight to above. £1.50.

## DISCOUNTS

Available on all items except those shown with NETT PRICES 10% on orders from £5 to £14.99, 15% on orders £15 and over.

## FREE POSTAGE

In U.K. for pre-paid mail orders. For mail orders for £2 list value and under there is an additional handling charge of 10p. Overseas orders - carriage charged at cost. Give A/C No.

26/671/449Z

## RESISTORS

Code	Watts	Ohms	1 to 9	10 to 99	100 up
(see note below)					
C	1/3	4-7-470K	1-3	1-1	0-3 nett
C	1/2	a-7-10M	1-1	1-1	0-9 nett
C	3/4	4-7-10M	1-5	1-2	0-87 nett
C	1	4-7-10M	2-2	2-5	1-62 nett
MO	1/2	10-1M	4	3-3	2-3 nett
WW	1	0-25-3-90	11	10	0
*WW	3	1-10K	1	3	6
*WW	7	1-10K	11	10	6

\* Add 40% for values under £20.

## Codes:

C - carbon film, high stability, low noise.  
MO - metal oxide. Electrical TR5 ultra low noise.  
WW - wire wound, Precision.

Values: All E12 except C 1W, C 1W and MO 1W.  
E12: 10, 12, 15, 18, 22, 27, 33, 39, 47, 56, 68, 82 and their decades.  
E24: as E12 plus 11, 13, 16, 20, 24, 30, 36, 43, 51, 62, 75, 91 and their decades.

## Tolerances:

5% except WW 10% ± 0.05% below 10Ω and 1W MO 2%.

Prices are in pence each for quantities of the same ohmic value and power rating. NOT mixed values. (Ignore fractions of one penny on total value of resistor order). Prices for 100 up in units of 100 only.

## POTENTIOMETERS

### ROTARY, CARBON TRACK.

Double wipers for good contact and long working life.

P.20 SINGLE linear 100 ohms to 4-7 megohms. each 14p

P.20 SINGLE log. 4-7 Kohms to 2-2 megohms. each 14p

JP.20 DUAL GANG lin. 4-7 Kohms to 2-2 megohms. each 48p

JP.20 DUAL GANG log. 4-7 Kohms to 2-2 megohms. each 48p

JP.20 DUAL GANG Logarithmic 10K, 22K, 47K, 1 megohm only. each 48p

JP.20 DUAL GANG audio 10K only 48p

2A DP mains switch for any of above 14p extra.

Decades of 10, 22 and 47 only available in ranges above.

Stereo Carbon Presets. Type PR, horizontal or vertical 6p each.

## SLIDER

Linear or log mono 4-7K to 1 meg. in all popular values each 28p

STEREO, matched tracks. lin. or log in all popular values from 4-7K to 1 meg 48p

Eucalypton plates, mono, black, white or light grey. each 18p

Control knobs, blk/whit/red/yel/brn/blk/blue/dk. grey/lt. grey. each 3p

## ELECTROLYTIC CAPACITORS

Axial Lead	2V	6.3V	10V	16V	25V	40V	63V	100V
0.47	—	—	—	—	—	—	—	—
1.0	—	—	—	—	—	—	—	—
2.2	—	—	—	—	—	—	—	—
4.7	—	—	—	—	—	—	—	—
10	—	—	—	—	—	—	—	—
22	—	—	—	—	—	—	—	—
47	3p	—	—	—	—	—	—	—
100	5p	8p	—	—	—	—	—	—
220	8p	12p	—	—	—	—	—	—
470	12p	18p	—	—	—	—	—	—
1,000	18p	27p	—	—	—	—	—	—
2,200	27p	47p	—	—	—	—	—	—
4,700	47p	82p	—	—	—	—	—	—
10,000	82p	150p	—	—	—	—	—	—

## MINITRON DIGITAL INDICATORS

2015F Seven segment filament compatible with standard logic modules. 0-9 and decimal point. 9mm characters in 18 lead DIL.

Suitable BCD decoder driver 7447 £1.15  
2015G showing + or - & 1/4 dec. pt. £1.20

LED'S (Light Emitting Diodes) 25p  
Photo Cells, each 40p

## ANTEX Soldering Irons

CN840	£2.15	Spare bits	32p
CCN240	£2.70	Spare bits	40p

## DESOLDER BRAID

8 ft grip 75p  
WAVECHANGE SWITCHES

1 pole 12 way; 2 pole 6 way each 23p  
3 pole 4 way; 4 pole 3 way each 23p  
T.C. STRIP 25 way 11p

## NUTS, SCREWS, etc.

In lots of 100 each  
45A NUTS 25p; 68A NUTS 25p  
4B Screws 25p; 66A Screws 24p  
Threaded pillars 68A; 7" hexagonal 21-92

Plain spacers 7" round £1.12  
Other sizes available

## ENAMEL COPPER

### WIRE IN 2 ounce reels

16, 18, 20, 22 SWG 34p  
24, 26, 28, 30 SWG 40p  
22, 34 48p; 26, 28, 30 45p

## DIN CONNECTORS

1 way loudspeaker	10p	12p
2 way audio	18p	12p
3 way audio	18p	15p
5 way audio	24p	12p
6 way audio	18p	15p

## EV CATALOGUE 7

2nd printing - Green and yellow covers

512 pages, thousands of items; illustrations; diagrams; much useful technical information. The 2nd printing has been updated as much as possible on prices. It costs only 25p post free including refund voucher for 25p for spending when ordering goods net value £5 or more.

## QUALITY GUARANTEE

All goods are sold on the understanding that they conform to manufacturer's specifications and satisfaction is guaranteed as such - no rejects, 'seconds' or sub-standard merchandise is offered for sale.

Prices quoted do not include V.A.T. for which 8% must be added to total net value of order. Every effort is made to ensure the correctness of information and prices at time of going to press. Prices subject to alteration without notice.

# ELECTROVALUE LTD

All postal communications, mail orders etc. to Head Office at Egham address, Dept. PW12. S.A.E. with enquiries requiring answers.

28, ST. JUDES ROAD, ENGLEFIELD GREEN, EGHAM, SURREY TW20 6HS  
Telephone Egham 3683 Telex 264475 Shop hours 9-5.30 daily: Sat. 9-1 p.m.

NORTHERN BRANCH: 680, Burnage Lane, Burnage, Manchester M19 1NA  
Telephone (061) 432 4945 Shop hours 9-1 p.m. 2-5.30 daily: Sat. 9-1 p.m.

U.S.A. CUSTOMERS are invited to contact ELECTROVALUE AMERICA, P.O. Box 27, Swarthmore PA 19081.

# Marshall's

A. Marshall & Son (London) Limited Dept. PW  
42 Cricklewood Broadway London NW2 3HD Tel: 01-452 016  
& 85 West Regent Street Glasgow G2 0D Tel: 041-332 4133

Everything you need is in our new catalogue available now price 20p

Trade and export enquiries welcome

## TELE TENNIS KIT

This exciting new game is now available in kit form. Due to popular demand we are now able to offer a fantastic saving on list prices. Ideal game for whole family. No need to modify your TV set, just plug in to aerial socket. Parts list as follows:

A Resistor Pack	£1.00 p.p. 20p
B Potentiometer Pack	£1.25 p.p. 20p
C Capacitor Pack	£3.10 p.p. 20p
D Semiconductor Pack	£14.50 p.p. 20p
E IC Sockets	£4.00 p.p. 20p
F Transformer	£1.15 p.p. 25p
G PCB's	£7.50 p.p. 20p
H Switches	£4.50 p.p. 20p
I UHF Modulator Kit (pre-assembled)	£7.20 p.p. 20p

Special Prices—complete kit £42.00 p.p. 50p. Sections A-F incl. £23.50 plus 30p. Assembly instructions with complete kit or 30p on request.

SN7400 16p	SN7420 16p	SN7453 16p	SN7491 41.10
SN7401 16p	SN7423 37p	SN7454 16p	SN7492 72p
SN7401AN 38p	SN7425 37p	SN7460 16p	SN7493 65p
SN7402 16p	SN7427 45p	SN7470 30p	SN7494 85p
SN7403 16p	SN7430 16p	SN7472 38p	SN7495 80p
SN7404 24p	SN7432 45p	SN7473 44p	SN7496 £1.00
SN7405 24p	SN7437 35p	SN7474 48p	SN74100 £2.16
SN7406 45p	SN7438 35p	SN7475 59p	SN74107 43p
SN7407 45p	SN7440 16p	SN7478 45p	SN74118 £1.00
SN7408 45p	SN7441 85p	SN7480 75p	SN74119 £1.02
SN7409 33p	SN7442 85p	SN7481 £1.23	SN74121 57p
SN7410 16p	SN7445 £1.59	SN7482 87p	SN74122 80p
SN7411 25p	SN7446 £2.80	SN7483 £1.20	SN74123 72p
SN7412 38p	SN7447 £1.30	SN7484 55p	SN74141 £1.00
SN7413 50p	SN7448 £1.59	SN7485 £1.58	SN74150 £1.44
SN7416 45p	SN7450 16p	SN7486 45p	SN74190 £1.93
SN7417 30p	SN7451 16p	SN7490 65p	

## OUR NEW GLASGOW SHOP IS NOW OPEN

Prices correct at August 1974, but all exclusive of V.A.T.  
Post and Package 20p postage and package charges

### Popular Semi-conductors

2N696	22p	2N3707	13p	AD142	50p	BC309	10p	LM709	48p
2N697	16p	2N3708	70p	AD143	45p	BC237	21p	T0 99	38p
2N698	16p	2N3715	£1.50	AD161	45p	BC238	19p	80UL	38p
2N699	45p	2N3716	£1.80	AD162	45p	BCV70	17p	140IL	35p
2N1302	19p	2N3771	£2.20	AO161	pr	BCV71	22p	LM723C	90p
2N1303	19p	2N3772	£2.80	AD162	£4.05	BCV72	13p	LM741	40p
2N1304	24p	2N3773	£2.65	AF109A	40p	BD123	33p	T 0 99	40p
2N1305	34p	2N3815	37p	AF178	24p	BD131	40p	BD1L	40p
2N1306	31p	2N3820	38p	AF124	30p	BD112	50p	140IL	14p
2N1307	21p	2N3823	£1.42	AF125	30p	BD135	42p	LM747	£1.00
2N1308	23p	2N3904	27p	AF126	28p	BD136	49p	LM7805	£2.00
2N1309	36p	2N3905	24p	AF127	28p	BD137	55p	MCI310	£2.91
2N1671	£1.44	2N4036	63p	AF139	39p	BD138	63p	M460	90p
2N1671A	£1.54	2N4037	42p	AF179	55p	BD139	71p	M481	£1.16
2N1671B	£1.72	2N4126	20p	AF179	65p	BD140	87p	M490	96p
2N1671C	£4.12	2N4289	34p	AF180	59p	BF115	25p	M491	£1.38
2N2102	50p	2N4921	73p	AF239	54p	BF116	23p	MJE340	45p
2N2147	70p	2N4922	84p	AF240	72p	BF117	43p	MJE2955	£1.12
2N2148	94p	2N4923	83p	AF279	54p	BF154	32p	MJE3055	68p
2N2160	60p	2N5150	92p	AF280	54p	BF163	32p	NE555Y	70p
2N2181A	22p	2N5191	95p	BC107	16p	BF180	35p	OC28	76p
2N2219	24p	2N5192	£1.24	BC108	15p	BF181	30p	OC71	13p
2N2219A	26p	2N5195	£1.46	BC109	19p	BF184	30p	OC72	13p
2N2221	18p	2N5245	43p	BC147	12p	BF194	12p	SC35D	£1.68
2N2221A	21p	2N5457	49p	BC148	13p	BF195	12p	SC36D	£1.46
2N2222	20p	2N5458	49p	BC149	12p	BF196	13p	SC40D	£1.89
2N2222A	25p	2N5459	49p	BC167B	13p	BF197	15p	SC41D	£1.23
2N2646	55p	40361	48p	BC168B	13p	BF198	18p	SC45D	£1.89
2N2904	22p	40362	50p	BC168C	11p	BF200	40p	SC46D	£1.96
2N2904A	24p	40363	88p	BC169B	13p	BF237	23p	SC50D	£2.40
2N2905	24p	40406	44p	BC169C	13p	BF238	22p	SC51D	£2.39
2N2905A	26p	40407	49p	BC149	12p	BF239	30p	SL414A	£1.80
2N2906	19p	40408	50p	BC182L	13p	BF240	23p	TA243	£1.00
2N2906A	21p	40409	52p	BC183	09p	BFX84	14p	TBA800	£1.50
2N2907	28p	40410	52p	BC183L	09p	BFX85	30p	TBA810	£1.50
2N2907A	24p	40411	2.25	BC184	11p	BFX87	28p	TIP29A	48p
2N2926	11p	40602	46p	BC184L	11p	BFX88	25p	TIP30A	58p
2N3053	32p	40604	56p	BC212K	10p	BFX89	45p	TIP31A	62p
2N3054	60p	40609	1.00	BC212L	16p	BFY19	52p	TIP32A	74p
2N3055	75p	AC17	20p	BC214L	11p	BFY51	21p	TIP34A	£1.01
2N3441	97p	AC126	20p	BC237	09p	BFY52	21p	TIP34A	£1.51
2N3442	£1.69	AC127	20p	BC238	09p	BFY90	60p	TIP35A	£2.90
2N3415	10p	AC128	20p	BC239	09p	BRV39	48p	TIP36A	£3.70
2N3416	15p	AC151V	25p	BC257	09p	IC1060	65p	TIP41A	79p
2N3417	21p	AC152	17p	BC258	09p	CA3102A	1.00	TIP42A	80p
2N3702	11p	AC153K	25p	BC259	13p	CA31045	70p	TIP295	93p
2N3703	12p	AC176	18p	BC300	£2.12	CA31048	£3.11	TIP305S	60p
2N3704	14p	AC176K	25p	BC301	14p	CA31089E	£1.96	TX300	12p
2N3705	12p	AC187K	23p	BC307	10p	CA31090E	£2.23	TX302	20p
2N3706	9p	AC188K	23p	BC308	09p	LM301A	46p	ZTX500	15p

## TECHNOMATIC LTD.

54 SANDHURST ROAD, LONDON, NW9

AC126 11p	JC184 11p	TIP295 70p	RECTIFIERS
AC127 11p	JC221 11p	TI844 25p	1N4001 5p
AC128 11p	BC213 10p	ZTK108 10p	1N4004 6p
AC176 11p	BC214 12p	2N706 15p	1N4007 7p
AC187 12p	BD131 40p	2N820 18p	BY127 12p
AC188 11p	BD132 40p	2N9640 88p	
AD149 45p	BFY80 10p	2N9906 15p	SIGNAL DIODES
AD181 85p	BFY81 15p	2N9928 8p	1N974 4p
AD180 85p	BFX99 18p	2N9963 18p	1N4148 4p
AF115 18p	MFF103 31p	2N3005 40p	OA70 6p
AF117 13p	MFF104 31p	2N3702 11p	OA81/85 6p
BC107 9p	MFF106 31p	2N3703 11p	OA200 6p
DC168 9p	OC28 47p	2N3704 11p	
DC109 10p	OC28 49p	2N3705 10p	ZENERS
DE188 11p	OC85 45p	2N3706 10p	400mW 8p
BC182 10p	OC44 11p	2N3707 11p	1.5W 18p
BC183 10p	OC71 21p	2N5819 20p	

TGS GAS SENSOR Semiconductor .. £2.00

(As illustrated in P.E. Sept./Oct issues)

RECTIFIER BRIDGES				SCR-THYRISTORS				TRIAC		
1 A	20p	81p	23p	25p	1 A	48p	48p	60p	78p	3A
2 A	30p	85p	46p	43p	3 A	48p	50p	78p	80p	400V
4 A	40p	48p	60p	70p	7 A	—	60p	64p	110p	80p
6 A	—	58p	76p	88p	10 A	—	78p	86p	—	

LINEAR ICs			TTL Series				
885	55p	561	£2.00	7400	24p	7472	80p
798	82p	562	£2.90	7404	18p	7473	88p
710	55p	MC1803	£1.00	7408	80p	7474	84p
723	55p	MC1307	£1.80	7410	18p	7475	52p
741	88p	MC1310	£2.70	7413	38p	7476	37p
747	70p	MFC4000	40p	7418	38p	7480	41p
748	38p	MC1312	£2.25	7420	16p	7489	£8.58
7600	£1.40	TBA800	£1.00	7480	16p	7490	52p
538	82p	TBA810	£1.25	7481	75p	7493	83p
580	£2.90	TBA820	80p	7417	48p	74107	45p
		ZN414	£1.10	7470	30p	74121	54p
						74141	85p

Data Sheets on I.C.s 10 each

For more selection, please refer to our advertisements in P.R. and W.W.

We also supply at competitive prices complete semi-conductor kits for various projects published in P.W., P.E., W.W., TV.

eg. our price for Tele-Tennis semi-conductor kit (P.W. Jan) complete with I.C. DIL sockets £16 + V.A.T.

Please send S.A.E. for prices specifying the Projects.

Minimum Order £21 P. A. 10p for orders below £5.

All prices exclusive of V.A.T.

Trade, OEM, Colleges inquiries welcome.

# Train for television

Course commences 8th January, 1975

This is your opportunity to train as a television and radio engineer on our full-time Two-Year College Diploma Course specially designed to cover the examinations of the City and Guilds' Radio, Television and Electronics Technicians' Certificate. Full theoretical and practical instruction on all types of modern receivers—including the latest colour sets. Minimum entrance requirements are Senior Cambridge or 'O' Level, or equivalent in Mathematics and English.

Please send free prospectus to:

Name

Address

## THE PEMBRIDGE COLLEGE OF ELECTRONICS

(Dept. PW7 34a Hereford Rd., London W2 5AJ

# BI-PRE-PAK

SUPPLIERS OF SEMI-CONDUCTORS TO THE WORLD



## Telephone Corner

COMPLETE TELEPHONES

Normal Household Type

EX. G.P.O.

only **99p** P & P 45p each

## TELEPHONE DIALS

Standard Post Office type. Guaranteed in working order.

only **25p** POST & PACKING 15p

## Tested and Guaranteed Paks



- |     |     |   |     |
|-----|-----|---|-----|
| B79 | 4   | IN4007 Sil. Rec. diodes                                     | 50p |
|     |     | 1,000 PIV lamp plastic                                      |     |
| B81 | 10  | Reed Switches, 1" long, 1/2" dia. High Speed P.O. type      | 50p |
| M25 | 100 | Mixed Diodes, Germ. Gold bonded, etc. Marked and Unmarked   | 50p |
| M34 | 30  | Short lead Transistors, NPN Silicon Planar types            | 50p |
| M39 | 6   | Integrated Circuits, 4 Gates BMC 962, 2 Flip Flops BMC 945  | 50p |
| M41 | 2   | Sil Power Transistors comp pair BO131/132                   | 50p |
| M63 | 4   | 2N3055 type NPN Sil. power transistors. Below spec. devices | 50p |
| M64 | 4   | 3A19 N Channel FETs 2N3619 in plastic case                  | 50p |



## Unmarked Untested Paks

- |     |     |   |     |
|-----|-----|---|-----|
| B31 | 50  | Germanium Transistors PNP, AF and RF                        | 50p |
| M65 | 150 | Germanium Diodes Min. glass type                            | 50p |
| B13 | 200 | Transistors, manufacturer's rejects, AF, RF, Sil. and Germ. | 50p |
| B34 | 100 | Silicon Diodes DO-7 glass equiv. to OA200, OA202            | 50p |
| B16 | 100 | Sil. Diodes sub. min. IN914 and IN916 types                 | 50p |
| M34 | 15  | Power Transistors, PNP, Germ. NPN Silicon TO-3 Can.         | 50p |
| M67 | 10  | 3B19N Channel FETs plastic case type                        | 50p |

## Lenco cassette tape recorder mechanisms

Type FFH for the PW, Kempton car stereo cassette player

£21.50 30p p&p

## Electronic Transistor Ignition £6.00

Complete kit p. & p. 11p

Now in kit form, we offer this "up-to-the-minute" electronic ignition system. Simple to make, full instructions supplied with these outstanding features. Transistor and conventional switchability, burglar proof lock-up and automatic alarm, negative and positive compatibility.

## Extension Telephones

Ideal for childrens toys 70p each P. & P. 25p

## New X Hatch

Our new vastly improved Mark Two Cross Hatch Generator is now available

Will align the colour guns on a colour T.V. receiver

Featuring plug in IC's and a more sensitive sync. pick-up circuit. The case is virtually unbreakable—ideal for the engineer's tool box—and only measures 3" x 3 1/2" x 3".

Ready built unit only **£9.95** Complete kit **£7.95**

(includes p. & p. but no batteries)



## LM380 AUDIO IC

We have just received a large consignment of LM380 IC's. These are specially selected to a higher grade and are marked with the number SL60745.

This fantastic little 3 watt audio IC only requires two capacitors and two potentiometers to make an amplifier with volume and tone control. The quality is good and has to be heard to be believed.

Our special price **£1.00** ea complete with data and projects book

## Over 1,000,000 Transistors in stock

We hold a very large range of fully marked, tested and guaranteed transistors, power transistors, diodes and rectifiers at very competitive prices. Please send for free catalogue.

## Our very popular 4p transistors

TYPE "A" PNP Silicon alloy, TO-5 can  
TYPE "B" PNP Silicon, plastic encapsulation  
TYPE "E" PNP Germanium AF or RF  
TYPE "F" NPN Silicon plastic encapsulation  
TYPE "G" NPN Silicon similar ZTX 300 range  
TYPE "H" PNP silicon similar ZTX 300 range

8 RELAYS FOR VARIOUS TYPES P & P 27p **£1.00p**

## UHF TV Tuner Units

Brand new by a famous manufacturer

Data supplied **£2.50**

## Plastic Power Transistors



NOW IN TWO RANGES

These are 40W and 90W Silicon Plastic Power Transistors of the very latest design, available in NPN or PNP at the most shockingly low prices of all time. We have been selling these successfully in quantity to all parts of the world and we are proud to offer them under our Tested and Guaranteed terms.

Range 1. VCE. Min. 15. HFE Min 15.  
1-12 15-25 25-50  
40 Watt 25p 13p 18p  
90 Watt 24p 23p 20p

Range 2. VCE. Min. 40. HFE Min 40.  
1-12 15-25 25-50  
40 Watt 30p 25p 25p  
90 Watt 35p 33p 30p  
Please state NPN or PNP on order.

## HIGH SPEED MAGNETIC COUNTERS

4 Digit (non-reset) 4 x 1 x 1 in ex G.P.O. 38p

## INTEGRATED CIRCUITS

We stock a large range of I.C.s at very competitive prices (from 18p each). These are all listed in our FREE Catalogue, see coupon below.

METRICATION CHARTS now available. This fantastically detailed conversion calculator carries thousands of classified references between metric and British (and U.S.A.) measurements of length, area, volume, liquid measure, weights etc.  
Pocket Size 15p Wall Chart 18p

## LOW COST DUEL IN LINE I.C. SOCKETS

14 pin type at 15p each } Now new low profile 16 pin type at 17p each } type

## BOOKS

We have a large selection of Reference and Technical Books in stock. Details are in our latest Catalogue. Send for it TODAY, using the coupon below. N.B. Books are void of V.A.T.  
Send for lists of publications

## Our famous P1 Pak is still leading in value

Full of Short Lead Semiconductors & Electronic Components, approx. 470. We guarantee at least 30 really high quality factory marked Transistors PNP & NPN, and a host of Diodes & Rectifiers mounted on Printed Circuit Panels. Identification Chart supplied to give some information on the Transistors.

Please ask for Pak P.1. only **50p**

Please send me one FREE BI-PRE-PAK Catalogue (enclose large SAE with 5p stamp)

NAME .....  
ADDRESS .....

Please add VAT current rate  
MINIMUM ORDER 50p. CASH WITH ORDER PLEASE. Add 15p post and packing on all orders OVERSEAS ADD EXTRA FOR POSTAGE  
**BUY THESE GOODS WITH ACCESS**

BI-PRE-PAK LTD

Dept. D. 222-224 WEST ROAD, WESTCLIFF-ON-SEA, ESSEX.  
TELEPHONE: SOUTHDEN (0702) 46344.

Co Reg. No 62089

# Guest Speaker

## The Castle 8.RS.DD.



A highly sensitive, full range eight inch unit designed for use in the recommended cabinet, or one of similar dimension.

Suitable for use with good quality stereo installations, tape recorders, car radios, public address and background music systems, it has a frequency range of 50 to 20,000kHz - the lower limit variable with increases in cabinet volume. Recommended retail price is £9.00 excluding VAT.

*Aluminium Voice Coil  
High Flux 14,000 Oersteds Ceramic Magnet  
Roll Surround  
Double Diaphragm  
8" Die-cast Chassis  
8 ohms Impedance  
15 Watt DIN Power Handling*

# Castle Acoustics Limited

Park Mill, Shortbank Road,  
Skipton, Yorks. Tel: Skipton 5333.



- ★ ELECTRONIC PIANO KIT
- ★ SYNTHESISER KIT
- ★ ELECTRONIC ORGAN KITS



*There are five superb Electronic Organ kits specially designed for the D-I-Y enthusiast. With the extreme flexibility allowed in design, you can build an organ to your requirements, which will compare with an organ commercially built costing double the price.*

★ Portable organ with 4 octave keyboard. £145.29. ★ Console organ with 5 octave keyboard. £269.90. ★ Console organ with 2 x 4 octave keyboards and 13 note pedal board. £470.65. ★ Console organ with 2 x 5 octave keyboards and 32 note pedal board. £655. ★ Console organ with 3 x 5 octave keyboards and 32 note pedal board. £770. ★ W/W Sound Synthesiser Kit. £130. ★ W/W Touch Sensitive Electronic Piano. £100.

All components can be purchased separately, i.e., semi-conductor devices, M.O.S. master oscillators, coils, keyboards, pedal boards, stop tabs, draw bars, key-contacts, etc. Send 50p for catalogue which includes 5 x 10p vouchers or send your own parts list, enclosing S.A.E. for quotation.

## ELVINS

ELECTRONIC MUSICAL INSTRUMENTS

Designers and component suppliers to the musical industry  
12 Brett Road, Hackney, London, E8 1JP. Tel. 01-986 8455

AMBIT FOR CLOCK CHIPS: CT 7001 £10.00

*Ambit the PLL people:*

NE560B £3.19  
NE561B £3.19  
NE562B £3.19  
NE565A £2.75  
NE566V £2.55  
NE567V £2.75

*Ambit for radio ICs:*

CA3123E £1.40  
CA3089E £1.90  
TBA651 £1.82  
uA753 £0.99

*Ambit for displays:*

(All LED 7 seg types)

SLA1 .33" red £1.50  
SLA11 .33" green £1.50  
SLA21 .33" yellow £1.50  
SLA7 .33" red £1.25  
plus many others

*Ambit for TOKO COILS*

CFT 455/470-B/C 0.45  
CFU 470C 0.50  
MFH 41/71T 1.35  
CFS10.7 0.40  
KACSK586HM 0.30

many others available

*Ambit for Larholt and TOKO FM modules:*

FM Tunerset - the high quality RF/IF module with features of £60 tuners £20.00  
TOKO EF5603 ultra quality varicap head £8.40

*Ambit for TTL:*

7400 19p 7402 19p 7413 44p  
7446 £1.50 7447 £1.45  
7448 £1.50 7490 65p  
74121 55p 74192 £1.45

*Ambit for lots more besides*

Our catalogue is gaining momentum, and contains much of interest to any technologically minded persons - we have devices for most occasions.

All our devices are BRAND NEW GUARANTEED TYPES available in OEM quantities. We do not sell any seconds. Catalogue 25p - now refundable with £5+ worth of purchases. Don't forget that we are here to talk about applications - and have a wealth of experience in all that we sell. (Plus several hundredweight of data at your disposal - through our datacopy service.) All prices exclude VAT. Post and packing 15p.

# ambit international

37 HIGH STREET  
BRENTWOOD  
ESSEX CM14 4RH  
Tel: (0277) 216029  
Telex: 995194

# YATES ELECTRONICS

(FLITWICK) LTD.

DEPT PW, ELSTOW STORAGE DEPOT  
KEMPSTON HARDWICK  
BEDFORD

C.W.O. PLEASE. POST AND PACKING  
PLEASE ADD 10p TO ORDERS UNDER £2.

Catalogue sent free on request, 10p stamp  
appreciated.

PLEASE ADD 8% VAT

## RESISTORS

¼W and ½W P.IHER.  
¼W 2% ELECTROSIL.

Power watts	Tolerance	Range	Values available	1-99	Price	100+
½	5%	4.7 Ω-2.2M Ω	E24	1-3p	1-1p	1-1p
½	10%	3.3M Ω-10M Ω	E12	1-3p	1-1p	1-1p
½	2%	10 Ω-1M Ω	E24	3-5p	3p	3p
½	10%	1 Ω-3.9 Ω	E12	1-3p	1-1p	1-1p
½	5%	4.7 Ω-1M Ω	E12	1-3p	1-1p	1-1p
½	10%	1 Ω-10 Ω	E12	8p	7p	7p

Quantity price applies for any selection. Ignore fractions on total order.

## DEVELOPMENT PACK

0-5 watt 5% P.Iher resistors 5 off each value 4.7 Ω to 1M Ω.  
E12 pack 325 resistors £2.40, E24 pack 650 resistors £4.70.

## POTENTIOMETERS

Carbon track 5k Ω to 2M Ω, log or linear (log ¼W, lin ½W).  
Single, 14p. Dual (stereo), 49p. Single D.P. switch, 49p.

## SKELTON PRESET POTENTIOMETERS

Linear: 100, 250, 500Ω and decades to 5MΩ. Horizontal or vertical P.C.  
mounting (0.1 matrix).  
Sub-miniature 0.1WV, 6p each. Miniature 0.25WV, 7p each.

## TRANSISTORS

AC107	16p	BC109	14p	BD115	75p	BF377	46p	ZTX300	10p
AC126	19p	BC115	16p	BD116	60p	BFY50	22p	ZTX302	20p
AC127	18p	BC116	15p	BD124	81p	BFY51	23p	ZTX341	18p
AC128	18p	BC117	23p	BD131	60p	BFY52	23p	ZTX500	18p
AC141K	22p	BC125	15p	BD132	64p	BRV39	41p	ZTX503	25p
AC142	25p	BC142	24p	BD140	66p	MJE340	47p	2N2646	60p
AC165	20p	BC143	21p	BDY32	57p	MJE370	69p	2N2904	25p
AD161	42p	BC147	12p	BF115	32p	OC76	90p	2N2905	32p
AC187	18p	BC148	12p	BF158	22p	OC28	90p	2N2926	13p
AC188	22p	BC149	12p	BF159	22p	OC35	90p	2N3053	31p
AC193K	28p	BC153	10p	BF160	23p	OC42	16p	2N2054	60p
AD140	53p	BC154	18p	BF161	22p	OC44	12p	2N3055	60p
AD143	73p	BC157	15p	BF164	22p	OC45	12p	2N3702	15p
AD149	70p	BC158	15p	BF173	28p	OC70	12p	2N3703	14p
AD161	42p	BC159	14p	BF177	29p	OC71	12p	2N3704	20p
AD162	42p	BC169	15p	BF178	43p	OC72	12p	2N3705	20p
AF114	25p	BC171	13p	BF179	41p	OC75	12p	2N3706	19p
AF115	25p	BC172	22p	BF180	42p	OC81	12p	2N3707	20p
AF116	25p	BC177	20p	BF181	32p	OC82	12p	2N3708	20p
AF117	25p	BC182	15p	BF182	41p	OC97	35p	2N3709	19p
AF118	50p	BC182L	16p	BF183	43p	ORP12	65p	2N3710	19p
AF121	50p	BC183	15p	BF184	32p	TIP29A	49p	2N3713	19p
AF126	50p	BC183L	16p	BF185	32p	TIP30A	58p	2N3819	32p
AF127	50p	BC184	18p	BF194	14p	TIP31A	62p	2N4062	25p
AF139	53p	BC186	25p	BF195	17p	TIP32A	74p	40360	43p
AF178	48p	BC187	25p	BF196	15p	TIP33A	98p	40361	43p
AF180	49p	BC192	13p	BF197	16p	TIP24A	140p	40362	45p
AF186	39p	BC212L	15p	BF200	40p	TIP41A	79p	40363	88p
AF239	48p	BC214L	19p	BF259	25p	TIP42A	90p	40406	44p
BC107	11p	BCY70	21p	BF262	26p	TIP43	35p	40486	90p
BC108	11p	BD112	52p	BF263	26p	ZTX108	18p		

## ZENER DIODES

400mW 5% 3.3V to 30V, 12p.

## WIRE WOUND POTS. 3W, 50p.

25, 50Ω and decades to 100kΩ, 10p.

## DIODES

### RECTIFIER

BY127	1250V	1A	12p
IN4001	50V	1A	7p
IN4002	100V	1A	8p
IN4004	400V	1A	8p
IN4006	800V	1A	10p
IN4007	1000V	1A	10p

### SIGNAL

OA85	7p
OA90	5p
OA91	5p
OA202	7p
IN4148	5p
BA114	8p

## SLIDER POTENTIOMETERS

86mm x 9mm x 16mm, length of track 59mm.  
SINGLE 10K, 25K, 100K log or lin, 50p.  
DUAL GANG, 10K + 10K etc. log or lin, 50p.  
KNOB FOR ABOVE, 12p.  
FRONT PANEL, 90p.

## BRUSHED ALUMINIUM PANELS

12in x 6in 37p.  
12in x 24in, 14p.  
9in x 2in, 12p.

18 Gauge panel 12in x 4in with slots cut for use  
with slider pots. Grey or black finish complete  
with fixings for 4 pots.

## THYRISTORS

2N5060	50V 0.8A	65p	105F	50V 5A	55p
2N5064	200V 0.8A	80p	105D	200V 5A	80p

## HEATSINKS—REPOINT

2W	24p	4W	45p	TO5 Clip	5p	TO1 Single	5p
3W	36p	6W	60p	TO18 Clip	5p	TO1 Double	8p

## TRANSFORMERS All have 240V Primary

MT30/2	0.12-15-20-24-30V	2A	£3.85
MT50/4	0.19-25-33-40-50V	1A	£2.50
MT50/2	0.19-25-33-40-50V	1A	£3.15
MT50/2	0.19-25-33-40-50V	2A	£4.20
MT60/4	0.24-30-40-48-60V	1A	£3.30
MT60/2	0.24-30-40-48-60V	1A	£4.80
MT60/2	0.24-30-40-48-60V	2A	£6.50

## MULLARD POLYESTER CAPACITORS C280 SERIES

250V P.C. Mounting: 0.01µF, 0.015µF, 0.022µF, 0.033µF, 0.047µF, 3.3p, 0.068µF 4p.  
0.1µF 4p, 0.15µF 5p, 0.22µF 5p, 0.33µF 7p, 0.47µF 9p, 0.68µF 12p, 1.0µF 14p,  
1.5µF 22p, 2.2µF 28p.

## MYLAR FILM CAPACITORS 100V

0.001µF, 0.002µF, 0.005µF, 0.01µF, 0.02µF,  
3p, 0.04µF, 0.05µF, 0.068µF, 0.1µF, 6p.

## CERAMIC DISC CAPACITORS

100pF to 10,000pF, 2p each.  
3p, 0.04µF, 0.05µF, 0.068µF, 0.1µF, 6p.

## ELECTROLYTIC CAPACITORS

(µF/V) 1/63, 1-5/63, 2-2/63, 3-3/63, 4-7/63, 6-8/40, 6-8/63, 10/25, 10/63, 15/16, 15/40,  
15/63, 22/10, 22/25, 22/63, 33/6-3, 33/16, 33/40, 47/4, 47/10, 47/25, 47/40, 68/6-3,  
68/16, 100/4, 100/10, 100/25, 150/6-3, 150/16, 220/4, 220/6-3, 220/16, 330/1, 3p, 47/63,  
100/40, 150/25, 220/25, 330/10, 470/6-3, 7p, 68/63, 150/40, 220/40, 330/16, 100/4, 10p,  
470/40, 680/25, 1000/16, 1500/10, 2200/6-3, 18p, 330/63, 680/40, 1000/25, 1500/16,  
2200/10, 3300/6-3, 4700/4, 21p.

## SOLID TANTALUM BEAD CAPACITORS

0.1µF 35V	2.2µF 35V	22µF 16V	12p
0.22µF 35V	4.7µF 35V	33µF 10V	
0.47µF 35V	6.8µF 25V	47µF 6.3V	
1.0µF 35V	10µF 25V	100µF 3V	

## VEROBOARD

2½ x 3½	0.1	0.15	26p	28p
2½ x 5	28p	30p	32p	34p
3½ x 3½	28p	30p	32p	34p
3½ x 5	34p	36p	38p	40p
17 x 2½	95p	77p		
17 x 3½	130p	108p		
17 x 3½ (plain)	86	72p		
17 x 2½ (plain)	—	51p		
2½ x 5 (plain)	—	18p		
2½ x 3½ (plain)	—	15p		
Pin insertion tool	62p	62p		
Spot face cutter	52p	52p		
Pkt. 50 pins	20p	20p		

## JACK PLUGS AND SOCKETS

Standard screened	32p	2.5mm insulated	13p
Standard insulated	18p	3.5mm insulated	13p
Stereo screened	44p	3.5mm screened	22p
Standard socket	15p	2.5mm socket	14p
Stereo socket	22p	3.5mm socket	14p

## D.I.N. PLUGS AND SOCKETS

2 pin, 3 pin, 5 pin 180°, 5 pin 240°, 6 pin  
Plus 12p. Socket 8p.  
2½ x 5 (plain) — 18p  
4 way screened cable, 26p/metre.  
2½ x 3½ (plain) — 15p  
6 way screened cable, 32p/metre.

## BATTERY ELIMINATOR

9V mains power supply. Same size as PP9 battery. £1-70

## HIGH VOLTAGE TUBULAR CAPACITORS—1,000 VOLT

0.01µF 12p	0.047µF 16p	0.22µF 25p
0.022µF 14p	0.1µF 20p	0.47µF 36p

## POLYSTYRENE CAPACITORS 160V 2½%

10pF to 1,000pF E12 Series Values, 4p each.

## SMOKE AND COMBUSTIBLE GAS DETECTOR—GDI

The GDI is the world's first semiconductor that can convert a concentration of gas  
or smoke into an electrical signal. The sensor decreases its electrical resistance when  
it absorbs oxidizing or combustible gases such as hydrogen, carbon monoxide,  
methane, propane, alcohol, North Sea gas, as well as carbon-dust containing air or  
smoke. This decrease is usually large enough to be utilized without amplification. Full  
details and circuits are supplied with each detector. Detector GDI £3. Smoke and Gas  
Detector Kits, mains operated with audible alarm £5.60. Mains operated Meter  
Indicator £7.90. Mains/Battery Gas Leak Detector £12.60, 12/24V Battery operated  
£8.40. 12V Battery operated Two Remote Sensors £12.80. NOTE: The battery operated  
kits incorporate our patented circuit to minimise battery drain. Typically 120mA for 12V.  
These kits contain all parts required with the exception of case. Suitable case mains  
operated kit £1.60. Battery operated kits £5.

## PRINTED BOARD MARKER

Draw the planned circuit onto a copper laminate board with the P.C. Pen, allow to  
dry, and immerse the board in the etchant. On removal the circuit remains in high  
relief. 97p

## METERS

2" Scale, 500µA, 1mA, 10mA, 100mA £3-30

## BULGIN MAINS CONNECTORS

3 Pin 1½A	Chassis Plug	18p	3 Pin 1½A	Chassis Socket	30p
	Line Plug	22p		Line Plug	24p
3 Pin 3A	Chassis Plug	24p	3 Pin 3A	Chassis Socket	34p
	Line Socket	28p		Line Plug	40p
3 Pin 5A	Chassis Plug	24p	2 Pin 5A	Line Plug	20p
	Line Socket	32p			

## THERMISTORS

VA1005	15p
VA1026	15p
VA1033	15p
VA1055S	15p
VA1066S	15p
VA1077	15p
R53	£1.25

## ROTARY MAINS SWITCH

D.P. 2A 35p

## LINEAR IC's

709	14 pin DIL	40p
741	8 pin DIL	40p
741	14 pin DIL	38p
723	14 pin DIL	95p
747	14 pin DIL	85p
748	8 pin DIL	45p

## WAVECHANGE SWITCH 33p

1p 12W, 3p 4W, 2p 2W, 2p 6W,  
4p 3W

DIL Sockets 14 pin and 16 pin 16p

**HOMER 1 STATION KE550** £3.95  
**INTERCOM**  
**HILLS HIQIVSM STEREO HEADPHONE WITH VOLUME CONTROLS 30-18,000Hz 8Ω** £4.50  
**JB3 HEADPHONE JUNCTION BOX** £1.37  
**CAR STEREO SPEAKERS 8Ω** £4.50  
 15ft Coiled Headphone ext. cable £1.45  
 20ft Coiled Guitar ext cable £1.50  
**VYNIAR SPEAKER CLOTH**  
 Black or Black & Silver  
 Sizes 18in x 25in 60p  
 36in x 25in £1.10  
 36in x 50in £2.20

**SOLDERING IRONS**  
**CCN240** 15watt £2.08  
**X25** 25watt £1.08  
 Replacement Elements £1.14  
 Replacement Bits 40p  
 ST3 Stand 75p

**CARTRIDGES**  
 Acos GP91-35C Mono Crystal Compat. 95p  
 GP93-1 Stereo Crystal £1.30  
 GP96-1 Stereo Ceramic £1.70  
 Sonotone 9TAHC Diam. £1.95

**CASSETTE TAPE RECORDER**  
**DYNAMIC MICROPHONE** £1.50  
 Telephone Pickup Coil 45p  
 Small Crystal Lapel Microphone 55p

**DIN PLUGS**  
 1, 2, 4, 5, 180°, 5, 240°, 6, 7, Pin 12p each  
 STD Jack Plug Plastic Mono 11p  
 STD Jack Plug Plastic Stereo 20p  
 3.5mm Jack Plug Plastic 8p

Visit our Warehouse for your requirements of Resistors, Capacitors, Transistors, SCRs, Speakers, Metal Boxes, Headphones, Intercoms, Meters, Audio Cables, Cartridges, Microphones, Wide range of Plugs and Sockets, etc.

All prices include V.A.T.  
 Please add 10% for P.P. Min. Order £1

**HILLS COMPONENTS LTD**  
 DEPT. RW1 UNIT Nos. 4  
 MELBURN INDUSTRIAL ESTATE  
 BRIXTON RD., WATFORD, Herts.  
 WD3 1SL Tel. Watford 3701

**H.A.C. SHORT-WAVE KITS**  
**WORLD-WIDE RECEPTION**




Famous for over 36 years for Short-Wave Equipment of quality, "H.A.C." were the Original suppliers of Short-Wave Receiver Kits for the amateur constructor. Over 10,000 satisfied customers—including Technical Colleges, Hospitals, Public Schools, R.A.F., Army, Home, etc.

**1974 "DX" RECEIVER**  
 Complete kit—Price £4.50 (incl. p. & p. & V.A.T.). Customer write: "Australia, India and America at loud volume."—"I have now heard over 300 stations including many Amateurs. I have received 32 Q.S.L. verified reports—from all continents. An amazing one-writer."  
 This kit contains all genuine short-wave components, drilled chassis, valve, accessories and full instructions. Ready in assembly and of course, as all our products—fully guaranteed. Full range of other S.W. kits, including the famous model "K plus" illustrated above. All orders despatched by return. Send stamped addressed envelope for descriptive catalogue of kits & components, also test report and details of evolving competition for Short-Wave listeners.

"H.A.C." SHORT-WAVE PRODUCTS  
 P.O. BOX No. 16, EAST GRINSTEAD,  
 SUSSEX RM19 3SN

**VEROBOARD**

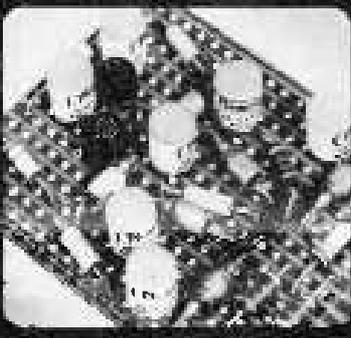

**VEROBOARDS GIVE A PROFESSIONAL FINISH TO YOUR WORK**  
 0.1 and 0.75 pitch, plain and copper clad universal circuit boards.  
 All boards are made to order.  
 (Printed in U.K. by the author of the VeroBoard)

**VERO**

4400 ELECTRONICS LTD  
 Dept. 10, The Old Mill, 1000  
 1000, The Old Mill, 1000

**BUILD A PROFESSIONAL TELEVISION CAMERA**

Complete kits available as designed by "Mullard" Includes a comprehensive construction manual, lens tube and lens at £60.00 + VAT. Lens and tubes also available from stock. UHF Modulator Kits at £7.19 including P. & P. & VAT. Allows standard domestic TV to be used as monitor (Modulator also suitable for TV Tennis and other similar games).

Send 5p stamp for illustrative brochure and price sheet.

**CROFTON ELECTRONICS**  
 124 Colne Road, Twickenham, Middlesex TW2 6QS.  
 Tel. 01-898-1569

**ENGINEERS**

**FREE**

**YOURSELF FOR A BETTER JOB WITH MORE PAY!**

Do you want promotion, a better job, higher pay? "New Opportunities" shows you how to get them through a low-cost home study course. There are no books to buy and you can pay-as-you-learn.

This helpful guide to success should be read by every ambitious engineer. Send for this helpful 76 page FREE book now. No obligation and nobody will call on you. It could be the best thing you ever did.

**CUT OUT THIS COUPON**  
 CHOOSE A BRAND NEW FUTURE HERE!  
 Tick or state subject of interest. Post to the address below

**POST NOW**

Build As-You-Learn PRACTICAL RADIO AND ELECTRONICS (with kit) <input type="checkbox"/>	Electronic Engineering <input type="checkbox"/>	CITY AND GUILDS Installations and Wiring <input type="checkbox"/>
Electrical Engineering <input type="checkbox"/>	Computer Electronics <input type="checkbox"/>	CITY AND GUILDS Electrical Technicians <input type="checkbox"/>
Electrical Installations and wiring <input type="checkbox"/>	Computer Programming <input type="checkbox"/>	CITY AND GUILDS Telecommunications <input type="checkbox"/>
Electrical Draughtsmanship <input type="checkbox"/>	General Radio and TV Engineering <input type="checkbox"/>	Radio Amateurs' Exam etc. etc. <input type="checkbox"/>
Electrical Mathematics <input type="checkbox"/>	Radio Servicing, Maintenance and Repairs <input type="checkbox"/>	
	Transistor Technology <input type="checkbox"/>	

To ALDERMASTON COLLEGE Dept. BPW95, Reading RG7 4PF **BPW 95**

NAME (Block Capitals Please) \_\_\_\_\_  
 ADDRESS \_\_\_\_\_

Other subjects \_\_\_\_\_ Age \_\_\_\_\_

Accredited by C.A.G.C. Member I.A.B.C.

**BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY**





# Practical Wireless Classified Advertisements

The pre-paid rate for classified advertisements is 12p per word (minimum 12 words), box number 30p extra. Semi-displayed setting £10.00 per single column inch. All cheques, postal orders, etc., to be made payable to PRACTICAL WIRELESS and crossed "Lloyds Bank Ltd." Treasury notes should always be sent *registered post*. Advertisements, together with remittance, should be sent to the Classified Advertisement Manager, PRACTICAL WIRELESS, IPC Magazines Ltd. Fleetway House, Farringdon Street, London, EC4A 4AD for insertion in the next available issue.

## Aerials

**GENUINE FULL SIZE**  
**18 element TV aerial**  
 as used by leading TV companies

ITV, BBC1 & 2, 4 & Colour Guaranteed  
 Perfect Pictures  
 Save ££s. We supply this genuine U.H.F. aerial for only £2.20, can be fitted outside or inside. Quality made technically advanced design. Precision grid/reflector eliminates ghosting. Complete with clamp, instructions advice. Money Back Refund. Wall/Caravan Bracket 25p. Best Cable 12p per yard. Plug 100p & FREE with order maps & channel reference of Radio & TV Transmitters. SEND DIRECT TO DEPT. PW15 219 Mansfield Rd. Nottingham.

**FOR ONLY £2.20**  
 +43P CARR

**IMPERIAL TRADING BRADFIELD LTD.**  
 The Quality Aerial Specialists

**J. & A. TWEEDY LTD.** Incorporating R. Baines  
 Prices include VAT and Postage  
**Multibeams:** MBM 30 £5.20, MBM 46 £8.35, MBM 70 £14.25.  
**Parabeams:** PBM 12 £4.95, PBM 18 £5.15, Log-Periodic £7.20.  
**Stereobeams:** SBM 1 £2.65, SBM 2 £3.66, SBM 3 £5.30, SBM 4 £5.80, SBM 6 £8.75.  
**Masthead Amplifiers** UHF or FM VHF £10.00, Seiback £3.50.  
 We are stockists of AMTRON KITS and BIB ACCESSORIES.  
 VHF Co-ax 8p/m, Low Loss 12p/m.  
 Open Tuesday to Saturday 0900-1730.  
 79 Chatsworth Road, Chesterfield S44 2AP.

## Wanted

**TOP PRICES PAID FOR NEW VALVES and TRANSISTORS**  
 popular T.V. and Radio types.  
**KENSINGTON SUPPLIES (C),**  
 367 Kensington Street, Bradford 8, Yorkshire.

**WE BUY** New Valves, Transistors and clean new components, large or small quantities, all details, quotation by return. **WALTON'S,** 55 Worcester Street, Wolverhampton.

**EARLY WIRELESS** receivers, components and magazines, details to Johnson Raffles, Haverbreaks, Lancaster.

**VINTAGE RADIO MART** urgently wants to buy all types of pre-war radios, literature, components, particularly pre-1927. Box No. 116.

**WANTED.** One of each, new or good S/H, PEN20, H20, SP20 valves. John Benson, 258 Portland Road, South Norwood, London SE25.

**AVO. 7 & 8** any condition. Any quantity. Huggett's, 2 Pawsons Road, W. Croydon.

**WANTED.** Volumes 1-7 Practical Electronics and volumes 40-46 Practical Wireless in perfect condition. Box 117.

**HEATHKIT** Hi-Fi MA-12 Power Amplifier and USC-1 Stereo Control Unit. Amberley 2237.

**URGENTLY** required Service Sheet for "Sound" tape recorder Model 555 all expenses paid. Box No. 119.

## For Sale

### COPPER CLAD LAMINATE FOR PRINTED CIRCUITS

Single sided 1/16" paper base—1.0p/sq. inch.  
 Single sided 1/16" glass-epoxy—1.5p/sq. inch.  
 Any rectangular sizes cut to your requirements.  
 Please send cash with order.  
 Price includes postage and packing.  
 From: **SIMTECH ENGINEERING LTD**  
**VOLUNTARY PLACE**  
**WANSTEAD**  
**LONDON E.11. 01-530-4240.**

**SEEN MY CAT?** 5,000 Items. Mechanical & Electrical Gear, and materials. S.A.E. K. R. WHISTON, Dept. PW, NEW MILLS, Stockport.

**PVC ADHESIVE TAPES** 5/8 in x 11 yds Black, some colours. £5 per 100. £40 1,000, samples. £1. North, 1 Elloughton Grove, Cottingham, Yorks. Tel: Hull 847208.

**MICROPHONES:** AKG D109, £12.65; AKG D202EI, £43.45; AKG D190C, £18.70; AKG D190E, £20; AKG D224 £55; Sennheiser MD211N, £49.50; Sennheiser MD413N, £29.70. All brand new and boxed. Send CWO to J. J. Francis, (Wood Green) Ltd., Manwood House, Matching Green, Harlow, Essex. Tel: Matching 476.

**VALVES, VALVES & MORE VALVES.** Large stocks 1930-1974, many obsolete. Also available many types of transistors and styl. Price lists available, 15p. Cox Radio, The Parade, East Wittering, Sussex. West Wittering 2023.

**SOUND TO LIGHT CONVERTORS** 3-channel, 1.5 kW £18, 3 kW £25, single channel £9; Sequencer £93; Strobes from £19; Projectors from £24; etc. Call or mail Aarvak Electronics, 98A West Green Road (Side Door), London N15 5NS. 01-800 8656.

**CONNOISSEURS.** I have attic-rescued back numbers Wireless Weekly (later Wireless), seven issued in 1924, two issued 1925, nine issued 1926; Wireless World, six issued 1925, thirty-seven issued 1926, three issued 1927; and miscellaneous same dates. Offers to Box 118.

## Books and Publications

### Technical Books — Radio & Electronics

Handbook of Tested Transistor Circuits.....	£0-40
Radio Servicing for Amateurs.....	£0-20
Boys Book of Crystal Sets & Simple Circuits.....	£0-25
Television Timebase Circuits.....	£1-00
How to Solve Solid State Circuit Troubles.....	£1-75
How to get the best out of your Tape Recorder.....	£1-50
Transistor Circuits Manual No. 2.....	£0-15
Jack Darr's Service Clinic.....	£1-35
Transistor Circuits for Modern Test Equipment.....	£0-60
Rad & Electr Colour Codes and Data Chart.....	£0-15
Hndbk of Transistor Equiv. and Substitutes.....	£0-40
Hi Fi, PA & Disco Amplifier Design Hndbk.....	£0-75
Radio Servicing Problems.....	£0-45
Electronic Circuits for the Amat Photographer.....	£0-60
Handbook of Simple Transistor Circuits.....	£0-35
How to build Solid State Audio Circuits.....	£1-75
Sound and Loudspeaker Manual.....	£0-50
TV Technicians Bench Manual.....	£2-50
Radio Amateur Operator's Handbook.....	£0-70
Audio Amplifiers.....	£0-53
Television Servicing Vol. No 1.....	£0-85
Television Servicing Vol. No. 2.....	£0-60
Television Servicing Vol. No. 3.....	£0-85
Radio Technicians Bench Manual.....	£3-00
Servicing Transistor Radio Receivers.....	£0-75
1st Book of Hi Fi Loudspeaker Enclosures.....	£0-60
2nd Book of Hi Fi Loudspeaker Enclosures.....	£0-60
Manual of Electronic Circuits for the Home.....	£0-50
Modern Crystal Set Circuits for Beginners.....	£0-35
Electronic Novelties for the Motorist.....	£0-50
2nd Book of Transistor Equiv. & Substitutes.....	£0-85
Handbook of Electronic Musical Novelties.....	£0-50
Transistorised Novelties for Hi Fi Enthusiast.....	£0-35
Fault Location Exercises in Rad. & TV Vol. 1.....	£0-80
Fault Location Exercises in Rad. & TV Vol. 2.....	£1-35
Colour TV Picture Faults.....	£2-50
Practical Transistor Novelty Circuits.....	£0-40
Boys Book of Practical Radio & Electronics.....	£0-60
Radio Receiver Construction using ICs & Transis.....	£0-60
ICs & Transistor Gadgets Construction Handb'k.....	£0-80
Integrated Circuits Equiv. & Substitutes Hbk.....	£0-75

**FREE!** \*\*\*\*\*  
 \* A Resistor Colour Code Disc Calculator \*  
 (Invaluable to the keen radio constructor!)  
 \* OFFERED FREE ON REQUEST FOR ORDERS £3 AND OVER \*  
 \* PLEASE ADD 10% FOR POSTAGE & PACKING \*  
**RADIO BOOK SERVICE**  
 40 Elwill Way, Beckenham BR3 2RZ

**UFO CHARTS.**—Wave Prediction, 49p; Daily Flight Pattern, 44p; Map, 44p; TV UFO Detection, 2 Optical Circuits, 55p; Propulsion Theory, 55p; Gravity Theories, 55p. Circuits: Transistor Optical, 66p; Radiation/Optical, 40p; Microdetector with memory, LSI, 75p. R. & E., Highlands, Needham, Suffolk.

## Service Sheets

**SERVICE SHEETS** for over 6,000 models of Televisions, Radios, Transistors, Stereo, Tape Recorders, Record Players, etc., at only 30p plus SAE with free Fault-Finding Guide. Over 50,000 sheets in stock for 10,000 models. SAE enquiries. Catalogue 20p plus SAE. Hamilton Radio, 47 Bohemia Road, St. Leonards, Sussex. Telephone Hastings 429066.

**SERVICE SHEETS.** Radio, TV etc., 8,000 models. Catalogue 20p. S.A.E. enquiries. Telray, 11 Maudland Bank, Preston.

## LARGE SUPPLIER OF SERVICE SHEETS

(T.V., RADIO, TAPE RECORDERS,  
RECORD PLAYERS, TRANSISTORS,  
STEREOGRAMS, RADIOGRAMS,  
CAR RADIOS)  
ALL AT 40p EACH

"PLEASE ENCLOSE LARGE S.A.E.  
WITH ALL ENQUIRIES & ORDERS"

Otherwise cannot be attended to  
(Uncrossed P.O.'s please, original  
returned if service sheets not available.)

### PLEASE NOTE

We operate a "by return of post" service. Any  
claims for non-delivery should be made within  
7-days of posting your order.

## C. CARANNA

71 BEAUFORT PARK  
LONDON, N.W.11 6BX

We have the largest supplies of Service  
Sheets (strictly by return of post). Please  
state make and model number alternative.  
Free TV fault tracing chart or TV list on  
request with order.

Mail order or phone 01-458 4882

## Educational

## TELEVISION TRAINING

16 MONTHS' full-time practical and  
theoretical training course in Radio  
and TV Servicing (Mono and Colour)  
for beginners.

13 WEEKS' full-time Colour TV  
Servicing course. Includes 100 hours  
practical training. Mono revision if  
necessary. Good electronics back-  
ground essential.

Next session commences on Janu-  
ary 2nd.

Prospectus from: London Elec-  
tronics College, Department A12,  
20 Penywern Road, London  
SW5 9SU. Tel. 01-373 8721.

## C AND E EXAM

Make sure you succeed with an ICS home  
study course for C and E Electrical Installa-  
tion Work & Technicians, Radio/TV/Elec-  
tronics Technicians, Telecomms Technicians  
and Radio Amateurs.

## COLOUR TV SERVICING

Make the most of the current boom! Learn  
the techniques of servicing Colour and Mono  
TV sets through new home study courses,  
approved by leading manufacturers.

## TECHNICAL TRAINING

Home study courses in Electronics and  
Electrical Engineering, Maintenance, Radio,  
TV, Audio, Computer Engineering and Pro-  
gramming. Also self-build radio kits.

Get the qualifications you need to succeed.  
Free details from: International Correspondence  
Schools, Dept. 732B, Intertex House, London  
SW8 4UJ. Or phone 01-622 9911.

GO TO SEA as a Radio Officer. Write.  
Principal, Nautical College, Broad-  
water, Fleetwood FY7 8JZ.

## Situations Vacant



Jobs Galore? Tens of thousands of  
new computer personnel needed over  
the next few years alone. With  
our revolutionary, direct-from-  
America, course, you train as a  
Computer Operator in only 4 weeks!  
Pay prospects? £3500 + p.a.  
After training, our exclusive ap-  
pointments bureau—one of the  
world's leaders of its kind—intro-  
duces you FREE to world-wide  
opportunities. Write or phone  
TODAY, without obligation.

London  
Computer Operators  
Training Centre

773, Oxford House

9-15, Oxford Street, W.1.  
Telephone: 01-734 2874

## Receivers and Components

### ALLARD ELECTRONICS Brand Components—Full Specification

TRANSISTORS	SCR's	Price	DIODES	Price
ea.	ea.	ea.	ea.	ea.
AC125/6/7/8	CR81/05	0-30	1N4011	0-05
AD140/149	CR81/10	0-50	1N4001/2/3/4/0-06	
AD161/162	CR81/20	0-80		
AF114/5/6/7	CR81/40	0-45		
AF119	CR83/40	0-55		
BC107/8/9	CR87/400	0-85		
BC147/8/9	CR818/100	0-85		
BC182/3/4	CR816/200	0-88		
BC212/3/4	CR816/600	1-50		
BCY70/71/72/0-15	IC's			
BD131/132	TBA800	1-35		
BF194/5/6	free data			
BFY50/51/52/53				
BY127	SPECIAL OFFER			
MJE370	ZN414			
MJE371	RADIO 1/C			
MJE370	£1 Free Circuit			
OC28	ZENERS			
OC35	0-50 BZ788	0-10		
OC83	0-20 All voltages			
TIL209	0-22 HZX61 series			
2N2218	0-19 1-3 wait	0-17		
2N2906	0-13			
2N2926 all	0-11			
2N3053	0-15			
2N3054	0-20			
2N3055	0-44			
2N3702/3/4	0-10	100v 0-24	0-39	0-54
2N3705/6	0-10	200v 0-27	0-44	0-58
2N3707/8/9	0-10	400v	—	0-40
2N3819	0-29	600v 0-29	—	0-74

299/301 BALLAROS LANE  
LONDON N12 8NP

MAIL ORDER ONLY Telephone enquiries:  
01-445 5188  
Cash with order. Add V.A.T.  
Orders under £2 plus 12p P. & P.

### NEW MOSEL V.H.F. KIT MK2

Our latest kit. Improved design and performance  
plus extra amplifier stage, receiver, aircraft,  
amateurs, mobile, radio 2, 3, 4, etc., this novel  
little set will give you endless hours of pleasure  
and can be built in one evening. Powered by 9 volt  
battery, complete with easy to follow instruction  
and built in jack socket for use with earphones or  
amplifier.

Only £4-00 + p&p 20p U.K. only.

Illustrated catalogue of selected kits and com-  
ponents, 20p inc. VAT. P & P free.

ALL PRICES PLUS 8% VAT

Galleon Trading Co,  
12, Burra Way,  
Corringham,  
Stanford-Le-Hope,  
Essex. SS17 9DE

### CRATA F.M. TUNER

- |         |                     |       |
|---------|---------------------|-------|
| Pack 1. | Resistors           | 36p   |
| 2.      | Capacitors          | £1-70 |
| 3.      | Semi Conductors     | £5-85 |
| 4.      | Inductors & filters | £7-00 |
| 5.      | Chassis & hardware  | £5-00 |
| 6/7.    | A.M. Parts          | £3-65 |

### TEXAN 20 + 20W AMP.

- |         |                 |       |
|---------|-----------------|-------|
| Pack 1. | Resistors       | 80p   |
| 2/3.    | Capacitors      | £3-65 |
| 5.      | Switches        | £1-00 |
| 6.      | Potentiometers  | £1-45 |
| 7.      | Semi Conductors | £8-25 |
| 8.      | Transformer     | £6-95 |
| 9.      | Printed Circuit | £2-50 |
| 10.     | Chassis         | £3-00 |
| 11.     | Cables          | 40p   |

V.A.T. EXTRA

add 20p p/p etc. except transformer  
(35p)

S.A.E. for lists

**TELERADIO ELECTRONICS,**  
325-7 Fore Street, Edmonton,  
London N9 0PE 01-807-3719  
Closed Thursdays

## Precision Polycarbonate Capacitors

All High Stability—Extremely Low Leakage

440V AC ( $\pm 10\%$ )	63V Range	$\pm 1\%$	$\pm 2\%$	$\pm 5\%$
0-1 $\mu$ F (11" x 1")	50p	0-47 $\mu$ F	50p	46p
0-22 $\mu$ F (11" x 1")	50p	1-0 $\mu$ F	50p	46p
0-25 $\mu$ F (11" x 1")	82p	2-2 $\mu$ F	80p	65p
0-47 $\mu$ F (11" x 1")	71p	4-7 $\mu$ F	£1-30	£1-05
0-8 $\mu$ F (11" x 1")	75p	6-8 $\mu$ F	£1-64	£1-29
0-68 $\mu$ F (2" x 1")	80p	10-0 $\mu$ F	£2-00	£1-60
1-0 $\mu$ F (2" x 1")	81p	15-0 $\mu$ F	£2-75	£2-15
2-0 $\mu$ F (2" x 1")	£1-22			£1-40

**TANTALUM BEAD CAPACITORS**—Values available:  
0-1, 0-22, 0-47, 1-0, 2-2, 4-7, 6-8 $\mu$ F at 15V/25V or 35V;  
10-0 $\mu$ F at 15V/20V or 25V; 22-0 $\mu$ F at 6V/10V or 15V;  
33-0 $\mu$ F at 6V or 10V; 47-0 $\mu$ F at 5V or 6V; 100-0 $\mu$ F at 3V.  
ALL at 10p each, 10 for 95p, 50 for £4.

**TRANSISTORS**—BC183/183L 11p BFY50 80p  
BC107/8/9 8p BC184/184L 12p BFY51 20p  
BC114 12p BC212/212L 14p BFY52 20p  
BC147/8/9 10p BC547/558A 12p AF178 30p  
BC153/7/8 12p BF194 12p OC71 12p  
BC182/182L 11p BF197 12p 2N3055 50p

**POPULAR DIODES**—1N914 6p, 8 for 45p, 18 for 90p;  
1N916 8p, 6 for 45p, 14 for 90p; 1844 5p, 11 for 50p,  
24 for £1-00, 1N4148 5p, 6 for 27p, 12 for 48p; 1N4001  
5p; 002 6p; 003 6p; 004 7p; 005 7p; 006 8p; 007 8p.  
**LOW PRICE ZENER DIODES**—400mW, Tol.  $\pm 5\%$  at  
5mA. Values available: 3V, 3-6V, 4-7V, 5-1V, 5-6V, 6-2V,  
6-8V, 7-8V, 8-2V, 9-1V, 10V, 11V, 12V, 13V, 13-5V, 15V,  
16V, 18V, 20V, 22V, 24V, 27V, 30V. All at 7p each.  
6 for 35p, 14 for 85p. SPECIAL OFFER: 100 Zeners  
for £5-50.

**RESISTORS**—High stability, low noise carbon film 5%  
1W at 40°C. 1/4W at 70°C. E12 series only—from 2-2 $\Omega$  to  
2-2M $\Omega$ . ALL at 1p each, 8p for 10 of any one value, 70p  
for 100 of any one value. SPECIAL PACK: 10 of each  
value 2-2 $\Omega$  to 2-2M $\Omega$  (730 resistors) £5.

**SILICON PLASTIC RECTIFIERS**—1-5 amp, brand new  
wire ended DO27: 100 P.I.V. 7p (4 for 28p); 400 P.I.V. 8p  
(4 for 30p); 800 P.I.V. 11p (4 for 42p).

**BRIDGE RECTIFIERS**—2 1/2 amp; 200V 40p; 350V 45p;  
600V 55p.

**SUBMINIATURE VERTICAL PRESETS**—0-1W only:  
ALL at 5p each; 50 $\Omega$ , 100 $\Omega$ , 220 $\Omega$ , 470 $\Omega$ , 680 $\Omega$ ,  
2-5M $\Omega$ , 5M $\Omega$ , 1k $\Omega$ , 2-2k $\Omega$ , 4-7k $\Omega$ , 6-8k $\Omega$ , 10k $\Omega$ , 15k $\Omega$ ,  
22k $\Omega$ , 47k $\Omega$ , 100k $\Omega$ , 250k $\Omega$ , 500k $\Omega$ , 1M $\Omega$ .

PLEASE ADD 10p POST AND PACKING ON ALL  
ORDERS BELOW £5. ALL EXPORT ORDERS ADD  
COST OF SEA/AIRMAIL.

PLEASE ADD 8% V.A.T. TO ORDERS.  
Send S.A.E. for lists of additional ex-stock items.  
Wholesale price lists available to bona fide companies.

**MARCO TRADING (Dept. W12),**  
The Old School, Edstaston, Nr. Wem, Shropshire.  
Tel: Whixall 464 (STD 094 872)  
(Proprietor: Minicost Trading Ltd.)

### INCOMPARABLE V.H.F. KIT

CV2—unique triple-purpose (Converter,  
Receiver, Tuner—Feeder) kit for the amateur  
enthusiast. Fantastic transistorised perfor-  
mance, World Wide Sales. Complete kit of top  
grade parts covers 80-180 MHz with easy  
build diagrams only £5 direct from makers or  
S.A.E. for free literature.

**JOHNSONS (RADIO) EST. 1943**  
SHAW ST., WORCESTER WR1 3QQ.

## BETA DEVICES

FOR BETTER PRICES

ITEM NO.	DESCRIPTION	PRICE	ITEM NO.	DESCRIPTION	PRICE
AC107/118	700C TO 99	0-30	IN914		0-04
PR.	709C D.L.L.	0-30	IN4145		0-06
BC107	723C TO 99	0-30	IN127		0-11
BC108	743C D.L.L.	0-30	IN4501/2		0-08
BC109C	711C D.L.L.	0-40	IN4003/4/5		0-08
BC147/8/9	747C D.L.L.	0-30	IN4005/7		0-08
MO70/71/72/218	748C D.L.L.	0-30	BRIDGE		
BYX08/7/68			W01 1A		
RF755	5 Watt Audio I.C.		100V		0-30
RF751/62	723C TO 99	0-30	W04 1A		
OC98	Data line with		800V		0-30
OC98	848		ZENER8		
2F2640	0-30	D.L.L. SOCKETS	32Y55 3-3-		
2N5090	0-24	8-Pin	0-12		
2N5088	0-28	14-Pin	0-18	1 Watt 5-8-	
2N5442	0-30	16-Pin	0-18	200V 5%	0-16
2N771	42-20		L.E.D.		
71P41A	0-74	All prices	200-Red		0-17
40585	01-00	include V.A.T.	L.E.D. Clip		0-24

C.W.O. PLUS P.P. 10p TO BETA DEVICES.

201 THE RIDGEWAY, ENFIELD, MIDD.

250mA Cartridge Fuses 1", 90p per 100.  
Unassd Carbon Resistors. 100 different 45p  
your choice 70p per 100  
Unassd W/W Resistors—100 assorted £1-10.  
150 Assorted Capacitor Mixture, 15p.  
11p. 8 to 2BA Nut & Bolt mixture Brass 32p Steel  
24 p.  
23 Assorted Potentiometers Unassd £1-15.  
Ex Government Standard Jack Plugs 4 for 55p.  
New 6 volt 36 watt SBC Bulbs 70p per doz.  
Earphones Ex. Govt. 70p per pair.  
Modulator Speech Amplifier Unit for Transmitters.  
New & Boxed 16" x 8" x 9", 8 valves.  
Meter, Carbon & Dynamic Mike Inputs. £4-50  
(All postage included in price)

**SOUND SYSTEMS OF SUFFOLK**  
678 Foxhall Rd., Ipswich, Suffolk IP1 1NQ

## TAPE HEADS

For valve and transistorized recorders from £2 ea

Send stamp for lists.  
**R.D.I. Ltd.**  
Chilton Works.  
Garden Rd.,  
Richmond,  
Surrey,  
TW9 4NS

Super Constructor Pack. Why not relock your workshop with our latest bargain pack containing:  
Two 6" ext shafts. Two couplers. Two 2" ext shafts with couplers attached. 50 assorted spacers. One foot each of 2-4 and 5BA brass studs. 370 20 lvs strips. Two "T" type trimmer converters. 100 mixed self-tapping screws. Plus extra components free in every pack. All the above items are brand new components. Only £1-65p Post paid.  
Electro-Mech Products, 7 Chantry Avenue, Bideford, Devon. Tel. 6820.

**BRAND NEW COMPONENTS** by return. Electrolytics, 15V, 25V, 50V 0-47, 1, 2-2, 4-7, 10 Mids.—4p, 22, 47—4-2p (50V—5p), 100—5-2p (50V—7p), 220—6p (50V—9p). Subminiature bead-type tantalums 0-1/35V, 0-22/35V, 0-47/35V, 1/35V, 2-2/35V, 4-7/35V, 10/16V, 22/16V, 47/6V, 100/3V—9p. Mylar Film 100V 0-001, 0-002, 0-005, 0-01, 0-02—2-2p, 0-04, 0-045—3p. Mullard Tubular Polyester 400V E6 series. 0-001-0-022—3p, 0-033-0-1—4p. Mullard miniature C333 ceramics E12 series 2% 1-8pf-47pf—2-2p, 56pf-330pf—3p. Polystyrene 63V, E12 series 10pf-1,000pf—2-2p, 1,200pf-10,000pf—3-2p. Miniature Highstab Carbon Film Resistors 1/2W E12 series 5% 1N-10M (10% over 1 Megohm)—1p. Postage 8p. Prices VAT inclusive. The C.R. Supply Co., 127 Chesterfield Road, Sheffield S8.

**COMPONENTS GALORE.** Pack of 500 mixed components manufacturers surplus plus once used. Pack includes resistors, carbon and W.W., capacitors various, transistors, diodes, trimmers, potentiometers etc. Send £1+10p p.p. C.W.O. To: Caledonian Components, Strathore Road, Thornton, Fife.

**NEW COMPONENTS** Post Free, 8% VAT included. 2N3702, 2N3704, 12p. Guest UPM 050 1/2W Carbon Film resistors 1p each. Seven segment common anode LED displays. 0.3in DL707 £2-19, 0-6in DL747 £2-89. Siemens B32540 250V Polycarbonate 0-01, 0-015, 0-022, 0-833, 0-047, 4p; 0-068, 0-1, 5p. Triac TAG 250 400V/8A, 75p. D52 diac 25p. 300W Light Dimmer, £2-75. Delivery from stock or your money returned. **GREENBANK ELECTRONICS**, 94 New Chester Road, Wirral, Merseyside L62 5AG.

**MULLARD UNIVERSAL AUDIO PRE-AMPLIFIER** ready built and tested, £9-70. For complete data send SAE to Quantec, Mile Road, Widdington, Morpeth, Northumberland

**GAS SENSOR TGS 105** with circuits £1-90 post free. Baron Electronics, 176 Brookhurst Ave, Bromborough, Wirral, Merseyside L63 0PF.

**LEDs.** Red, green, yellow. Sizes: 0.1in, 0.125in, 0.16in, 0.2in. Mixed bags all sizes and colours. 50—£5, 100—£9 including postage, VAT. CWO. Individual types and larger quantities by negotiation. Industrial Electronic Supplies (Stockport) Ltd., 181a Bramhall Lane, Davenport, Stockport, Cheshire.

## Ladders

**LADDERS 'Special Offer'** Unvarnished triples. 9ft 7in closed—23ft 1in extd. £18-52 delivered, Home Sales Ladder Centre (WLS2) Haldane (North) Halesfield (1) Telford, Shropshire. Tel: 0952-586644 and pay at the door.

## Miscellaneous

### PSYCHEDELICATESSEN

is the only way to describe the zodiac of Freaky Gear now available from Boffin. Look!

ITEMS	PRICE
No Licence Exam Transmitter/Receiver	£8 00
Variable rate Bright Flash, Pocket Mini-Strobe	£2 40
<b>READY-MADE MODULES</b>	
Mini-Volt Spark Generator (4 inch spark), 15,000 Volts	£5 31
Experimental Mini DNM-Lab-oratory	£3 30
Sensitive 'non-anatomical' electronic Stethoscope	£2 20
Electronic 'Voice-Thruster'	£2 20
Ghost Hunting Aid	£2 20
People Detector	£2 20
Experimental Water-Fonz	£4 40
Psychedelic Meditation Aid	£2 20
Bird-Walkers Remote Monitor	£12 20
Psychological Cross-Eyed Ears Device	£4 41
Super Sound-Catcher	£2 21

(All prices include VAT, packing & postage)

Send remittance to:

**BOFFIN PROJECTS**  
4 Cunliffe Road, Stoneleigh  
Ewell, Surrey  
(Mail order U.K. only)

Or for more details, send 20p for lists. Plus free design, prot shield

### GADGETS GALORE!!

Alarms — Test Gear — Musical Instruments  
Timers — Audio — Discs — Sound Effects

★ READY BUILT + TESTED ★

Sample prices: Signal Injector £3-95  
Signal Tracer £2-65

Prices include U.K. Postage and Batteries  
—Mail Order Only—S.A.E. list to:

**G.K. SERVICES,**  
43 Westdale Road, London SE18 3BQ

## MORE RANGES FOR LESS MONEY!

AC/DC Multimeter type U4324  
A-DC 0-08-3A — 8 Ranges  
A-AC 0-3-3A — 6 Ranges  
V-DC 0-5-100V — 9 Ranges  
V-AC 3-300V — 8 Ranges  
Frec. In the range of 45 to 20kHz  
Resistance, 500 Ohm to 5 Mohm  
9 Ranges Decibel —10 to +12dB  
Accuracy ± 2.5% DC, ± 4% AC  
Dimensions: 167 x 98 x 83 mm.



Only £8.85



**SUPERTESTER 808R ICE**  
10 Fields — 80 Ranges! Plus a lot of accessories for measurements of 500A-AC 100 A/DC — Temperature —50C to +200C — Magnetic fields up to 15 Gauss — Phase indicator — EHT 25kV Electronic Volt Ohm — meter. Transistor: Diode Tester etc.

Dimensions: 128 x 92 x 32 mm  
300 grams—200Ohm/V Accuracy £18-50  
1% DC. Ask for free catalogue  
Accessories Extra

## ALPHANUMERIC NIXIE TUBES B7071

The Alpha numeric NIXIE tube has the ability to display all the letters of the alphabet, numerals 0 thru 9 and special characters in a single tube. From the standpoint of both readability and electrical characteristics, the Alphnumeric NIXIE tube provides many unique benefits including ★ All DC operation ★ Uniform, continuous line characters of equal height ★ Memory with ample solid state drive circuits ★ Readability in high ambient light—200 foot-lamberts brightness ★ Long life with no loss of brightness ★ Character height 2 1/2 in.

Price only 99p each plus 10p P/P

## SPECIAL OFFER

**The Sinclair Scientific.**  
Logs, trig and arithmetic. All at the touch of a button.

At last there's a pocket calculator which gives you log and trig functions instantly.

Fuji 12 function machine. With the functions available on the Scientific keyboard, you can handle directly logs, anti logs, sin and arcsin, cos and arccos, tan and arctan, automatic squaring, automatic doubling, xy (including square and other roots), plus of course, addition, subtraction, multiplication, division and any calculations based on them. 7-digit scientific notation, 200-decade range, Reverse Polish logic and 25 hour battery life. Send for further information **£27-50**

Add 8% VAT to all items + 35p P & F  
**ELECTRONIC BROKERS LTD.**  
49-53 Pancras Road, London NW1 2QB  
Tel: 01-837 7781

## Synthesiser "Sounds Supreme" by Dewtron (VAT extra.)

Famous kits, e.g. was-was complete kit £3-50, fuzz kit £3-50, P&F 25p under £10. Ring Modulator modules £9 "Mister Baseman" Bass Pedal Units and whole range of Synthesiser modules, musical novelties, etc. Catalogue 15p from D.E.W. Ltd., 254 Rinkwood Road, Farnham, Dorset.

**CRYSTAL EARPIECES:** Bargain 30p delivered. Partridge Electronics Ltd., Broadstairs, Kent.

### TREASURE TRACER MK III Metal Locator



- Varicap tuning
- Britain's best selling metal locator kit
- Weights only 22oz.
- Speaker and earphone operation
- Knocks down to only 17in.
- Prebuilt search coil assembly
- As seen on BBC1 and BBC2 TV
- You only need soldering iron, screwdriver, pliers and snipe
- Five transistor circuit

Send s.a.e. for leaflet

Complete Kit **£9.80** Built, tested and guaranteed **£13.75**  
 P & P 45p + 75p VAT P & P 45p + £1.19 VAT

MINIKITS ELECTRONICS, 354 LANGLEY DRIVE, (Mail Order Only) LONDON E11 2LN

### Hi-Fi Console

JUST SEND YOUR ADDRESS TO

Widens your STEREO S.P.A. from only **£8.95**  
 takes AUDIO UNITS BOOKS & RECORDS

Elegant **WHITE/TEAK MELAMINE**  
 70 pounds of SOLID VALUE

**FREE COLOUR**

WHITE Illustr. **£29.50** carr. 1.90

LEISURE TIME Ltd. Dept. V, CROZIER RD PLYMOUTH

**SUPER SPACER PACKS** containing 150 assorted spacers 1/4-3/8 at 1/2 long, 4 at 6BA clearance types plus 150 mixed 4 at 6BA screws, nuts, and washers to fit. 600 brand new top quality components for only £2.50 plus 20p postage. Lists 7p. Electro-Mech Products, 7 Chantry Avenue, Bideford, Devon.

**AERIAL WIRE.** High quality PVC covered multi-strand copper, 50ft 60p (10p), 75ft 86p (13p), 100ft £1.19 (15p), 150ft £1.77 (24p), 200ft £2.36 (26p), 250ft £2.95 (28p), 300ft £3.54 (31p). Egg insulators 12p pair (6p). P&P in brackets. S.A.E. all enquiries. A.I. Radio Components, 14 The Borough, Canterbury, Kent CT1 2DR.

**LOW COST I.C. MOUNTING.** Lengths of 100 I.C. pin sockets, 60p (p & p 5p). Quantity rates, SAE details & sample. L.E.D. (MLED500), 20p each. (post paid). P.K.G. Electronics, "Oak Lodge", Tansley, Derbyshire.

**JOYMATCH A/B:** Better than Big Set performance from your transistor radio! "Non-existent" stations come in like local. Big saving in battery costs. Quality greatly improved. High rise flat problem solved. Refund if not delighted £5-71. Partridge Electronics Ltd., Broadstairs, Kent.

**AUDIOSCAN,** the "do-it-yourself" speaker mail-order specialists. High fidelity speaker kits, chassis units, sound absorbent, grille fabric and much more. Send 7p in stamps for bargain list to: Audioscan, Dept. PW-7 4 Princes Square, Harrogate, Yorks.

**LOWEST COST IC SOCKETS.** Use Soldercon IC socket pins for 8 to 40 pin DILs. Make 8 pin sockets for 4p, 14 pin for 7p (at 300 pin price). In strips of 100 pins: 100+ pins 70p, 300+ 50p, 1,000+ 40p. Instructions supplied. 10p p&p for orders under £2. Add 8% VAT. SINTEL, 53n Aston Street, Oxford.

### FLUORESCENT LIGHT KIT

12v 8w

You can build this reverse polarity proof light for use in homes, garages, caravans, for camping, or emergency lighting. Everything is supplied, the 100w, white enamelled metalwork, first quality components. P.C.B., instructions, etc.

Price only **£3-19** Inc. V.A.T. post & packing  
 Ready built **£3-78**  
 Diffuser only 59p extra

### ALUMINIUM BOXES

Prices include lid, screws, and V.A.T. Post and packing 10p extra on all orders

7	5 1/2"	by	2 1/2"	by	1 1/2"	high	100p
8	5 1/2"	by	2 1/2"	by	1 1/2"	high	100p
9	5 1/2"	by	2 1/2"	by	1 1/2"	high	100p
10	5 1/2"	by	2 1/2"	by	1 1/2"	high	100p
11	5 1/2"	by	2 1/2"	by	1 1/2"	high	100p
12	5 1/2"	by	2 1/2"	by	1 1/2"	high	100p
13	5 1/2"	by	2 1/2"	by	1 1/2"	high	100p
14	5 1/2"	by	2 1/2"	by	1 1/2"	high	100p
15	5 1/2"	by	2 1/2"	by	1 1/2"	high	100p
16	5 1/2"	by	2 1/2"	by	1 1/2"	high	100p
17	5 1/2"	by	2 1/2"	by	1 1/2"	high	100p
18	5 1/2"	by	2 1/2"	by	1 1/2"	high	100p
19	5 1/2"	by	2 1/2"	by	1 1/2"	high	100p
20	5 1/2"	by	2 1/2"	by	1 1/2"	high	100p

Order now to —

ELECTRONICS DESIGN ASSOCIATES DEPT. PW 62 Bath St. Walsall, WS1 3DE. Phone 33652

**AIRCRAFT TYPE** servo position indicator and transmitter. Can be used for aerial direction indication. £1 (40p) per set. S.A.E. for details and list of ex-equipment components. Eldun Electronics, 16 Raven Road, Timperley, Cheshire.

**PRINTED CIRCUIT MANUFACTURERS** offer P.W. Project P.C.B.'s, 70p each. Also, Production, Design, Artwork, Photography, Electroplating, Screen-printing, Tinning, Undertaken. Estimates by return or phone W.K.F. Electronics, Welbeck St., Whitwell, Worksop, Notts. Tel. 695.

**SUPERB INSTRUMENT CASES** by Bazelli, manufactured from heavy duty PVC faced steel, choice of 212 types, send for free list. Bazelli Instrument Cases, Dept 25, St. Wilfrids, Lane, Halton LA2 6LT, Nr. Lancaster.

**HARDWARE SUPPLIES.** Sheet aluminium individual sizes or standard packs, drilled to spec. Screws, nuts, washers etc. Fascia panels in aluminium individual requirements. Printed circuit boards, one-off or small runs. Printed circuit drafting tapes etc. 7p for list. Ramar Constructor Services, 29 Shelbourne Road, Stratford on Avon. Warwks. CV37 9JP.

**MULLARD 10W RMS AUDIO AMPLIFIER MODULES.** Brand new, for 24 volt 4 ohm operation. Tremendous offer, absolutely no extra components or hardware required. Supplied with circuit and full data for simple operation. £2.65 INCLUSIVE. LTE, 46 Minehead Road, South Harrow, Middx. Mail order only.

**ENERGY CRISIS?** The distant Radio Station powers your World's first DX-CRYSTAL SET; general coverage, with Aerial and Earpiece £3.56. Costs nothing to run. Partridge Electronics Ltd., Broadstairs, Kent.

P.W. TENNIS. 12.NE555. 16.7400 24.IN914. 2.BC108. £11 inclusive. Island Devices, P.O. Box 11, Margate, Kent CT9 1QX.

**ANTIQUE WIRELESS ENTHUSIASTS.** For all your requirements in radio, pre-1945, contact Tudor Rees's Antique Wireless Service. Retail shop now open at 64 Broad Street, Staple Hill, Bristol. Tel: 0272 565472.

### AERIAL BOOSTERS £3.30

We make three types of Aerial Boosters: B45-UHF 625, B12-VHF 405, B11-VHF, RADIO

### VALVE BARGAINS

Any 5—50p, 10—75p, 50—£3.30 —  
 ECC82, ECL80, EB91, EBF89, EF80, EF85, EF183, EF184, EY86, PCC84, PCC89, PCC189, PC97, PCF80, PCF86, PCF805, PCF808, PCL82, PCL83, PCL84, PCL85, PFC200, PL36, PL81, PL504, PY33, PY82, PY800, PY801, 30L15, EH90, PC88, PC86.

### TV COLOUR VALVES

PL508, PL509, PY5001A, 25p EACH.  
 Press Button U.H.F. Tuners—£2.50.  
 Rotary U.H.F. Tuners—£2.00.

### PLUGS—SOCKETS

Price per item, in brackets for ten  
**CO-AX PLUGS** 6p (50p) Socket surface 7p (60p), Connectors 4p (35p).  
**D.I.N. PLUGS**  
 2 pin, 3 pin and 5 pin 20p (£1.65).  
**JACK PLUGS.** Standard 18p (£1.50), 3.5 mm 10p (80p), 2.5 mm 10p (80p).  
 All prices include V.A.T. P. & p. 10p per order. Money back refund. S.A.E. for leaflet

### ELECTRONIC MAILORDER (BURY) LTD.

62 Bridge St., Ramsbottom, Bury, Lancs. Tel. Rams 3036.

### BUILD THE STEREO FM TUNER

# PW SANDOWN LOOK

- PCB & Cmpnts Inc. TR & BOX — £26.32
- Push Button Unit. 6 Position — £2.97
- METERS. Tuning & Level — each £1.50
- Subminiature Switches — set of 4 £2.62
- Cabinets & Front Panels — — to order
- VAT INCLUSIVE PRICES P & P 25p

S.A.E. for further details

FW ELECTRONICS. 40 TUDENHAM RD. IPSWICH. SUFFOLK IP4 2SL. Mail Order only

### MINI ACCUMULATORS

2 volt MULTI-USE Sealed Lead Acid Rechargeable Cells.

Size L450—1.4" x 1.1" x .44". 3 for £1.50 Inc. P. & P.

Size GA2—1.7" x 1.3" x .5". 3 for £1.95 Inc. P. & P.

GARFIELDS, 269 Rye Lane, London. S.E.15



# TRAMPUS ELECTRONICS LTD

58-60 GROVE ROAD,  
WINDSOR, BERKS.

MONEY BACK IF NOT SATISFIED.  
LARGE STOCKS. LOW PRICES.  
ALL BRAND NEW TOP GRADE FULL  
SPEC DEVICES. CALLERS WELCOME.

FAST SERVICE.

SEND C.K.O. ADD VAT TO ALL PRICES IN U.K. P&P 15P. EUROPE 25P. OVERSEAS 65P.

CATALOGUE/LIST FREE SEND S.A.S.

## Digital Displays



MINIIRON 5015F  
0-9DP £1.15 ea  
LED 0.3" dia:  
0-9DP £1.49 ea  
JUMBO LED 0.6"  
0-9DP £2.25 ea  
LIQUID CRYSTAL  
6 digit £18

702 OPA 69p  
703 REF/IF 28p  
709 T099 21p  
709 DIL 14 29p  
710 DIL 14 36p  
720 Radio £1.39  
723 Regulator 67p  
741 T099 29p  
741 D118 31p  
741 D114 31p  
747 Dual 741 89p  
748 DIL 8 36p  
1505 IC A/D  
Converter £7

MFC4000 2V AF 35p  
MFC4050 54p  
MFC6030 52p  
MFC6040 90p  
MFC6010 £1.10  
MFC6040 £1  
NES31 35V/50 £2  
NES36 FET OPA12  
NES40 Driver £1  
NES46 AM Ref 1.50  
NES50 2v ref 79p  
NES55 TIMER 67p  
NES56 Dual 11.50  
NES60 PLL £3.15  
NES61 PLL £3.15  
NES62 PLL £3.19  
NES65 PLL £2.69  
NES66 Gen £2.49  
NES67 code £2.69  
SN7209 709 29p  
SN7274 741 31p  
SN7274 748 36p  
SN76131 11.20  
SN76660 FMIF £1  
SN76611 IF £1.25  
TAD 100 & IF £2  
2N4006 £3  
2N402T £1.75  
2N405 Servot 2.50  
2N419 AN Ref 1.09

### SPECIAL OFFERS

741 29p MFC4000 35p  
555 67p 2N411 £1.09  
BC107, BC108, BC109 9p ea  
2N3055 39p Three for £1  
115W/T03 or 90W plastic  
2N3819E 16p 2N3053 17p  
RF550/51/52/53 all 18p  
1A50Vrect 4p ea 1N914 4p

### Price each:-

AC127/128 16p  
AC187/188 19p  
AD161/162 35p  
BC107/8/9 9p  
BC132/4/7 18p  
BC147/8/9 10p  
BC157/6/9 12p  
BC167/8/9 12p  
BC177/8/9 18p  
BC182/3/4 11p  
BC212/3/4 12p  
"A or L"  
BC270/1/2 15p  
BU151/2 39p  
BFY50/1/2 18p  
BFY53 17p  
BX90 12p  
NIE2955 95p  
HJE3055 62p  
MUI151put 49p  
DA91 8p  
TIP29A 48p  
TIP30A 57p  
TIP31A 61p  
TIP32A 73p  
TIP31A 78p  
TIP42A 89p  
TIP2955 90p  
TIP3055 55p  
TIP315 9p  
TIP32 20p  
GAS SENSOR £2  
GAS "KIT" £3

## vero

VERO PINX36 25p  
COPPER CLAD VEROBOARD 0.1"  
21x31" 27p, 31x31" 24p, 31x31" 27p  
31x35" 29p, 31x11" 11.50  
DIL IC'S BOARDS 6x11" £1.50  
24 way edge connector 60p  
36way 90p. PLAIN 31"x17" £1  
FACE CUTTER 43p. REC ETCHANT

PRINTED CIRCUIT BOARD-AT £11.69  
COPPER BOARD 6x4" 40p.  
DESOLDER BRAID reel 59p  
HEATSINKS  
51/T05 & 181/T018 5p ea.  
TV4 12p. TV3/T03 16p. AV1/T03 29p.

CAPACITORS  
22pf to 0.1uf 3p ea. ELECTROLYTIC  
25V 2/10/50/100uf ep. 1000uf 20p  
PNESETS VERT: 5p. RESISTORS 55¢ 11p

POTS AB or EGIN  
ROTARY: 12p. SWITCH 13p. DUAL 38p.  
SLIDERS: SINGLE 26p. DOUBLE 48p.  
SWITCHES: SPST 18p. DPDT 25p.  
MINI 1": SPST 39p. PUSH 39p.  
BENCH POWER SUPPLY 3-12V 5S.  
DIN PLUGS all 15p ea. Sockets 9p  
TRANSFORMERS 1A 6/12V £1.34  
BIA 0002 MODULE 15WATT 4VP £5  
BA1000 1W AF MODULE £2.49  
BW/12V FLUORESCENT LIGHT 53p.

Oil sockets  
PROFESSIONAL  
GOLD PLATED  
4 GREY NYLON.  
8 & 16 PIN  
ONLY 15p each.

## LEDS 14P.

MINI PIN SOURCE OR RED DIFFUSE  
LEDS. 209 STYLE. NO CLIP. 14p ea  
TIL209 RED LED & CLIP 17p ea  
BIG 1" RED LED & CLIP 18p ea  
ORANGE & GREEN LEDS:  
NIX1 25p ea. BIG & CLIP 33p ea  
INPRA RED LED £1.2N5777 33p.  
PS12 PHOTO IC/amp/switch £1.

## DIGITAL CLOCK

HOS INTEGRATED CIRCUITS.  
AY51224 a DIGIT CLOCK supplied  
with 14pin socket & data £4.25  
MMS311/14 a DIGIT CLOCK with  
28 pin socket & date 17.50  
SDIGIT BW4 AY55500 £7.50  
2DIGIT COUNTER/DRIVER £7.50

## CASSETTE mechanics £12.50

STEREO CASSETTE MECHANISM.  
As used in imported types  
costing £100. Only requires  
a case & electronics heads  
supplied. Send for data 15p.

CA3046 69p  
L4501 OPA 49p  
L4507 OPA 49p  
L4508 1100pa 95p  
L4509K Reg. £2.29  
LM371 REF/IF £2  
LM372M AF/IF £2  
LM373 £3  
LM377 2x29 £2.69  
LM380 2V AF 99p  
LM382 2V AF £2  
LM382 amp £2  
LM3900 4x20A 89p

7400 etc gates 16p  
7413 Schmitt 31p  
7447 driver 11.09  
7470/72 32p  
7473/74/76 39p  
7475 48p  
7490 Counter 61p  
7492 Counter 69p  
74121 none 45p  
74141 driver 83p

## 7400 TTL

Full range in Cat.

## INDEX TO ADVERTISERS

Adeola	678
Allard Electronics	772
Ambit International	720, 766
A.S.P. Ltd.	769
Barrie Electronics	687
Bentley Acoustics	688
Beta Devices	773
B.H. Component Factors Ltd.	682
Bi-Pak Semiconductors	694-695
Bi-Pre-Pak Ltd.	765
Boffin Projects	773
British Institute of Engineering Techno-logy	720, 768, cover iii
British National Radio & Electronics	699, 754, 760
Bull. J. (Electrical) Ltd.	762
Caranna. C.	772
Castle Acoustics Ltd.	766
Chilmead Ltd.	700
Chromasonic Electronics	693
C.J.L. Ltd.	678
Codar	712
Colomar (Electronics) Ltd.	776
Crescent Radio Ltd.	735
Crofton Electronics	768
C.T. Electronics	761
Custom Cabinets	697
Dabar Electronic Products	698, 712
D.E.W. Ltd.	773
Doram Electronics Ltd.	711
Eagle International	723
Electra-Mech	773
Electronics Brokers	773
Electronic Design Assoc.	754, 774
Electronic Mail Order Ltd.	774
Electrospares	698
Electro-Tech	700
Electrovalve Ltd.	763
Elvins	766
E.T.E.H.	687

Felstead Electronics	769
Fairline Supplies	682
Foulsham-Tab Ltd.	678
F.W. Electronics	774
Galleon Trading	772
Garfields	774
G.K. Electronics	773
Global Audio	724
Greenwold Electronics	698
H.A.C. (Shortwave) Products	768
Harverson Surplus Co. Ltd.	757
Heath (Gloucester) Ltd.	715
Henry's Radio Ltd.	743, cover iv
Hills Components Ltd.	768
I.C.S.	772
I.L.P. (Electronics) Ltd.	751
Imperial Trading	771
Integrex Ltd.	692
Johnsons (Radio)	772
Kensington Supplies	771
Keytronics	756
Laskys	679, 600, 681
Leisure Time	774
Lewis Radio	712
Linear Products Ltd.	692
London Computer Operators Training Centre	772
London Electronic College	772
Maplin Electronic Supplies	701
Marco Trading	772
Marshall, A.	764
Milward, G. F.	724
Minkies Electronics	774
Multicore Solders	720
Newmart Electronics	683

Partridge Electronic Ltd.	760
Pembridge College of Electronics	764
Purnell Book Services	690-691
Radio Book Services	771
Radio Components Specialists	752-753
Radio Exchange Ltd.	cover ii
R.C.S. Products Ltd.	756
R.D.I.	773
RSC (Hi-Fi) Centre Ltd.	758-759
RST Valve Mail Order Co.	696
R & TV Components Ltd.	684, 685, 686
Riversdale Electronics	750
Saxon Entertainments Ltd.	719
Selray Book Co.	697
Shoptonics Ltd.	688
Simtech	771
Sinclair (Cambridge) Ltd.	730-731
Sound Systems of Suffolk	773
Studio Electronics	682
Supratronics	756
Swanley Electronics	756
Technomatic Ltd.	764
Teleradio	772
Thacker, A. H.	700
Trampus Electronics Ltd.	775
Trannies Ltd.	716
Tweedy, Ltd. (J. A.)	771
Vero Electronics Ltd.	768
Viking Books Ltd.	689
Watford Electronics	770
Wilmslow Audio	689
Xeroza Radio	770
Yates Electronics	767
Z & Aero Services	776


Head Office and Warehouse  
44A WESTBOURNE GROVE  
LONDON W2 5SF  
Tel: 727 5441/2/3

# Z & I AERO SERVICES LTD.

Please send all correspondence and Mail-Orders to Head Office  
When sending cash with order, please include 0.15 in £ for postage and handling.  
MINIMUM CHARGE 15p. No C.O.D. orders accepted

Retail Shop  
85 TOTTENHAM COURT ROAD  
LONDON W1  
Tel: 500 8403  
Open all day Saturday

## AC/DC MULTIMETER TYPE U432A

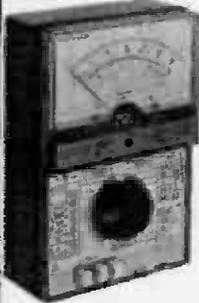

33 ranges up to  
3 Amps AC/DC;  
1200V DC, 900V  
AC, 500kΩ, +12  
db.

Sensitivity: 20kΩ/V DC;  
4kΩ/V AC

Accuracy:  
±2.5% DC;  
±4% AC

Movement is protected by silicon diodes.

Dimensions 187x98x83 mm. Weight: 1.5lb.

PRICE: complete with test leads, instruction manual and fibre-board storage case £9.25. Packing & carr. £0.50.

## MULTIMETER TYPE U4323

Sensitivity: 20,000Ω/V.




7 D.C. Voltage ranges 0.5-1000V  
6 A.C. Voltage ranges 2.5-1000V  
5 D.C. Current ranges 0.05-500mA  
4 Resistance ranges 1kΩ-1MΩ  
Built-in oscillator providing AF output of 1kHz and I.F. output of 465kHz with an amplitude of 1 volt minimum.

Dimensions: 140x87x40 mm. Weight 0.5kg

PRICE complete with leads and plastic storage case £7.70. Packing & postage £0.50

## AC/DC MULTIMETER TYPE U4313

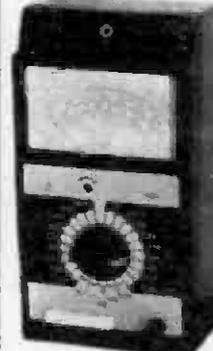

39 ranges:  
600μA to 1.5A  
AC  
60μA to 1.5A DC  
75mV to 800V  
DC  
1.5V to 600V AC  
1MΩ, 0.5μF, 12db

Accuracy: 1-5%  
DC; 2-5% AC

Sensitivity: 20k  
Ω/V DC; 2kΩ/V  
AC

Mirror scale 86mm long.

Dimensions: 115x215x90 mm, Weight 3.3lb.

PRICE, complete with test leads, service manual and steel carrying case £12.50. Packing & carriage £0.50.

ALL THE ABOVE INSTRUMENTS FEATURE TAUT SUSPENSION MOVEMENTS  
PRICES ARE EXCLUSIVE OF V.A.T.

## Fully guaranteed Individually packed VALVES

A1065	£1.25	ECL80	50p	GX24	70p	PT80	40p
A82	55p	ECL82	25p	G237	£1.00	PT81	40p
ATP4	80p	ECL88	70p	KT66	£2.50	PT82	40p
R12H	£2.00	EPL88	40p	KT98	£2.00	PT83	40p
CV31	80p	EP28	50p	MH4	75p	PT84	40p
DAF88	50p	EP37A	50p	M15	65p	PT800	£1.00
DP28	50p	EP37A	50p	OA2	45p	PT800	45p
DK98	70p	EP40	75p	OS2	45p	PT801	50p
D102	40p	EP41	60p	PAB200	40p	QV05-10	
D106	50p	EP60	30p	PO37	60p	QV05-10	£1.40
DY86/87	40p	EP68	£1.25	PC900	50p	QV06-60A	
		EP85	25p	PC924	40p	QV05	50p
DT802	45p	EP96	25p	PC928	40p	QV05-12	
ES8CX/01	£1.20	EP99	30p	PC938	40p	QV05-11	£1.16
		EP91	45p	PC939	50p	R19	40p
E1800C	70p	EP92	50p	PC9180	60p	BCL/400	
E1830C	70p	EP90	40p	PC980	40p	£2.00	
		EP183	35p	PCF82	40p	BCL/600	
EAS6	40p	EP184	35p	PCF84	60p	U26	75p
EAB20	40p	EP1200	70p	PCF86	60p	U181	75p
EAP34	75p	EL33	£2.50	PCP260	75p	U801	75p
EA91	25p	EL24	70p	PCP201	75p	UAB200	
EBC33	£1.00	EL36	60p	PCP801	55p		
EBC41	75p	EL37	£1.30	PCY502	50p		
EBF50	40p	EL41	80p	PCY505	50p		
EBF49	50p	EL82	55p	PCY508	60p		
EC2	35p	EL84	30p	PCY820	50p		
EC31	40p	EL85	60p	PCY81	35p		
EC32	35p	EL86	45p	PCY82	40p		
EC33	35p	EL90	45p	PCY80	40p		
EC34	35p	EL94	50p	PCY84	45p		
EC35	40p	EM31	60p	PCY86	50p		
EC36	50p	EM50	45p	PCY808	50p		
EC38	50p	EM54	45p	PF1200	70p		
EC318	70p	EM27	£1.00	PLF62	75p		
ECY60	40p	EY01	45p	PL81	60p		
ECY82	40p	EY11	45p	PL82	45p		
ECY901	70p	EY88	40p	PL83	45p		
ECY33	£1.40	EZ40	70p	PL84	45p		
ECY83	40p	EZ41	75p	PL84	45p		
ECH1	25p	EZ48	80p	PL85	£1.15		
ECH3	40p	EZ81	30p	PL902	65p		
ECH54	45p	EZ81	75p	PT23	60p		

A lot of these valves are imported and prices vary for each delivery, we reserve the right to change prices for new stock when unavoidable.

## TRANSISTORS, DIODES etc.

AC 113	AP 139	BSY 27	OA 272	OC 200	2N 3033
AC 128	AP 178	BSY 28	OA2 200	OC 205	2N 3034
AC 129	AP 186	BSY 55A	OC 22	EX 751	2N 3053
AC 176	AF 12	BZ 16	OC 25	EX 11	2N 3300
AC 178	AF 21	CR8 1/15	OC 26	ZR 21	2N 3301
AC 19	AST 27	CR8 1/20	OC 28	1N 23A	2N 3730
AC 19	AST 28	CR8 1/30	OC 29	1N 23	2N 3731
AC 20	BC 108	CR8 1/40	OC 30	1N 32A	2N 3819
AC 25	BC 115	CR8 3/10	OC 36	1N 38A	2N 4038
AC 29	BC 119	CR8 3/20	OC 42	1N 43	2N 4065
AC 40	BC 136	CR8 3/30	OC 44	1N 70	2N 4061
AD 149	BC 137	CR8 3/40	O 46	1E 277	2N 4795
AD 161	BC 149A	CR8 26/23	OC 70	1N 418C	2N 5205
AD 162	BC 172	GBT 115	OC 75	1N 4148	1N 125
ADZ 11	BC 172A	GBT 116	OC 78	2N 454A	2N 154
ADZ 13	BC 215A	EX 66	OC 78D	2N 706	2N 159
AP 114	BCY 31	NKT 222	OC 81	2N 918	2N 3030
AP 115	BCY 32	OA 5	OC 82	2N 1304	404
AP 116	BCY 72	OA 47	OC 82D	2N 1305	2082
AP 117	BF 115	OA 70	OC 82DM	2N 1307	40230
AP 118	BF 187	OA 71	OC 85	2N 1309	40231
AP 124	BF 188	OA 72	OC 180	2N 2062	6668
AP 125	BPT 51	OA 79	OC 140	2N 2162	
AP 126	BPT 52	OA 91	OC 170	2N 2411	
AP 127	BPT 90	OA 200	OC 172	2N 2989	

V.A.T.  
Please add 8%  
to all orders

IF95	45p	1B5	40p	5BQ90	80p	1626	80p
IF99	50p	1B4	30p	5B4	55p	64WA	
UL41	70p	1T4	30p	6BQ74	80p	£1.25	
UL44	40p	1X24	60p	6BR7	£1.00	£1.25	
UY41	45p	1X29	75p	6C4	50p	£1.25	
UY85	40p	2D21	50p	6C5	50p	£1.25	
VR105/30	2E23	2E25	£0.90	6C6	50p	£1.25	
	2A4	2A4	50p	6C8	50p	£1.25	
	2E27	2E27	£0.90	6C9	50p	£1.25	
	2E28	2E28	£0.90	6C9B	50p	£1.25	
	2E29	2E29	£0.90	6C9C	50p	£1.25	
	2E30	2E30	£0.90	6C9D	50p	£1.25	
	2E31	2E31	£0.90	6C9E	50p	£1.25	
	2E32	2E32	£0.90	6C9F	50p	£1.25	
	2E33	2E33	£0.90	6C9G	50p	£1.25	
	2E34	2E34	£0.90	6C9H	50p	£1.25	
	2E35	2E35	£0.90	6C9I	50p	£1.25	
	2E36	2E36	£0.90	6C9J	50p	£1.25	
	2E37	2E37	£0.90	6C9K	50p	£1.25	
	2E38	2E38	£0.90	6C9L	50p	£1.25	
	2E39	2E39	£0.90	6C9M	50p	£1.25	
	2E40	2E40	£0.90	6C9N	50p	£1.25	
	2E41	2E41	£0.90	6C9O	50p	£1.25	
	2E42	2E42	£0.90	6C9P	50p	£1.25	
	2E43	2E43	£0.90	6C9Q	50p	£1.25	
	2E44	2E44	£0.90	6C9R	50p	£1.25	
	2E45	2E45	£0.90	6C9S	50p	£1.25	
	2E46	2E46	£0.90	6C9T	50p	£1.25	
	2E47	2E47	£0.90	6C9U	50p	£1.25	
	2E48	2E48	£0.90	6C9V	50p	£1.25	
	2E49	2E49	£0.90	6C9W	50p	£1.25	
	2E50	2E50	£0.90	6C9X	50p	£1.25	
	2E51	2E51	£0.90	6C9Y	50p	£1.25	
	2E52	2E52	£0.90	6C9Z	50p	£1.25	

MINIMUM POSTAL ORDER IS PERSONAL CALLERS WELCOME.  
MANY OTHERS IN STOCK include Cathode Ray Tubes and Special Valves, U.K.  
Postage: Up to £2.15p, £1-£3 22p, Over £3 post free, C.O.D. 25p extra.

24HOUR. ORDERS each consisting of 1oz. 24. 1oz. dia. tubular screw-in sections. 11/2 (8-section) solid aerial with adaptor to fit the 7in. rod, insulated base, stay plate and stay assemblies, pegs, reamer, hammer, etc. Absolutely brand new and complete ready to erect, in carrying bag. £7.99 new £4.99 slightly used. Carriage £1.50.

## Colomor ALL valves guaranteed

68C70T	60p	20P4	£1.10	6060	70p
68C77	60p	23L6GT	70p	6084	60p
68C78	55p	28CL5	£1.00	6085	£1.00
68C79T	50p	80C17	£1.00	6087	70p
68K7	60p	80C19	90p	6090	£2.50
68L70T	50p	20P5	£1.00	6146	£2.25
68M70T	50p	20P11	£1.00	6148	£2.25
68Q7	50p	20P12	£1.00	6020	£2.00
6V6Q	150p	30P14	£1.10	9001	£2.00
6V6T	150p	30P15	£1.00	9002	50p
6X4	40p	30P16	£1.00	9003	75p
6X50	40p	20L17	85p	9004	15p
6X5GT	60p	20P12	£1.00	9006	£2.00
6Y6G	80p	20P19	£1.00		
6Z4	85p	20P11	90p		
6Z4L2	90p	20P13	90p		
7B7	80p				
7E4	80p	20P14	£1.10		
9D6	40p	25L6GT	75p		
11E2	£0.90	35W4	50p		
12A6	55p	35Z4GT	70p		
12A7	45p	50Z5	60p		
12A7	40p	60C90C			
12A7T	35p		£1.10		
12A8	50p	25	£1.00		
12A9	45p	30P14	£1.10		
12AX1	25p	70C1	75p		
12E6	45p	75	75p		
12E8	45p	78	70p		
12E9	45p	78	70p		
12E10	45p	78	70p		
12E11	45p	78	70p		
12E12	45p	78	70p		
12E13	45p	78	70p		
12E14	45p	78	70p		
12E15	45p	78	70p		
12E16	45p	78	70p		
12E17	45p	78	70p		
12E18	45p	78	70p		
12E19	45p	78	70p		
12E20	45p	78	70p		
12E21	45p	78	70p		
12E22	45p	78	70p		
12E23	45p	78	70p		
12E24	45p	78	70p		
12E25	45p	78	70p		
12E26	45p	78	70p		
12E27	45p	78	70p		
12E28	45p	78	70p		
12E29	45p	78	70p		
12E30	45p	78	70p		
12E31	45p	78	70p		
12E32	45p	78	70p		
12E33	45p	78	70p		
12E34	45p	78	70p		



# Henry's

SO MUCH MORE - AND YOU PAY LESS VAT WITH HENRY'S LOW PRICES

UK's No. 1 for Electronics and Hi Fi

## You can build the Texan and Stereo FM Tuner

TEXAN 20 + 20 WATT IC STEREO AMPLIFIERS

Features glass fibre PC board, Gardners low field transformer, 6-ICs, 10-transistors plus diodes, etc. Designed by Texas Instruments engineers for Henry's and, P.W. 1972. Supplied with full chassis with detailed construction handbook and all necessary parts. Full input and control facilities. Stabilised supply. Overall size 15 1/2" x 2 1/2" x 6 1/2" mains operated. Free teak sleeve with every kit. £28.50 (GB post paid). (also built and tested £35)



**STEREO FM TUNER** Features capacity diode tuning, lead and tuning meter indicators, stabilised power supply—mains operated. High performance and sensitivity with unique station indication IC stereo decoder. Overall size in teak sleeve 8" x 2 1/2" x 6 1/2". Complete kit with teak sleeve £21.00 (GB post paid). (also built and tested £24.95)

### JOIN THE LARGE BAND OF HAPPY CONSTRUCTORS!

#### JOSTY KITS IN STOCK

(Post etc. 15p each)

AF20	Mono Transistor Amp.	5.61
AF25	Mixer	3.30
AF30	Mono Trans. Pre-amp.	1.20
AF35	Emitter Amplifier	2.43
AF60	Small 5W Amplifier for Microphone	4.86
AF305	Intercom	7.68
AF310/2	Mono Amplifier (for Stereo use two)	7.56
M160	Multivibrator	2.19
M1302	Transistor Tester	8.34
M191	Vu-Meter	5.37
M192	Stereo Balance Meter	5.94
LF380	Quadrophonic Device	8.43
AT60	Psychedelic Light Control, Single Ch.	10.82
AT65	Psychedelic Light Control, 3 Chan.	16.53
AT25	Window Wiper Robot	5.82
AT30	Photo Cell Switching Unit	6.69
AT50	400w Triac Light Dimmer Sp. Cont.	5.19
AT56	2-300w Triac Light Dimmer Sp. Cont.	6.75
ATS	Automatic Lt. Cont.	3.75
GU330	Tremolo Unit for Guitars, ecc.	8.10
HF61	Diode Detector	3.87
HF65	Frequency Modulated FM Transmitter	3.21
HF75	FM Transist. Receiver	3.66
HF310	FM Tuner Unit	16.31
HF325	De-luxe FM Tuner Unit	26.34
HF330	Stereo Decoder for use with HF310/25	10.56
GP310	Stereo Pre-amp (for use with 2 AF310)	22.98
GP312	Basis Circuit Board	10.02
GP304	Basit Circuit Board	5.33
HF380	Aerial Amp. for LW or VHF	6.03
HF395	Broadband Aerial Amp. 2-10	10.56
NT10	Power Supply 0.60mA 9V Stab. & 12V Unstable	6.27
NT300	Professional Stab. Power Supply	13.17
NT310	Power Pack 2 x 15 volt	5.64
NT305	Voltage Converter	5.64
NT330	Power Pack AF310/ GP304	6.27
NT315	PS 240V ac to 4-5-15V dc. 500mA	12.06
AE1	Output Stage 100mW	1.56
AE2	Pre-amplifier	1.32
AE3	Diode-receiver	2.05
AE4	Flasher	1.26
AE5	A stable Multivibrator	1.14
AE6	Monostable Multivibrator	1.11
AE7	R.C. Generator	1.08
AE8	Basiffiter	1.06
AE9	Treblefilter	1.06
AE10	CCIR-filter	1.06

#### TRANSISTORISED MODULES

<b>Tuners - Power Suppliers - Amplifiers</b>		
<b>AMPLIFIERS (All single channel unless stated)</b>		
4-300	9 volt 300 MW O/P 3-8 OHM, 1-10 MV I/P Special Offer	£ 0
2004	9 volt 250 MW O/P 3-8 OHM, 10-100M V I/P	1.75
104	9 volt 1 watt O/P 8-16 OHM, 10 MV I/P	2.70
304	9 volt 3 watt O/P 4-8 OHM, 10 MV I/P	3.95
555	12 volt 3 watt O/P 8-16 OHM, 150 MV I/P	4.10
555ST	12 volt 1 1/2 + 1 1/2 watt O/P 8 OHM, 150 MV I/P Stereo module	5.95
E1208	12 volt 5 watt O/P 4-16 OHM, 25-60 MV I/P	5.10
608	24 volt 10 watt O/P 4-8 OHM, 30-50 MV I/P	4.95
410	28 volt 10 watt O/P 8 OHM, 160 MV I/P	4.95
620	45 volt 30 watt O/P 4-8 OHM, 150 MV I/P	9.95
Z40	30/35 volt 15 watt O/P 4-8 OHM, 100 MV I/P	5.45
Z60	45/50 volt 25 watt O/P 4-8 OHM, 100-250 MV I/P	6.95
SA6817	24 volt 6 + 6 O/P 8 OHM 100 MV I/P Stereo module	10.20
<b>AMPLIFIERS with controls</b>		
E1210	12 volt 2 1/2 + 2 1/2 watts 8 ohms, Stereo	8.25
R 500	Mains 5 watts 4-16 ohms, Mono	6.30
SAC14	Mains 7 + 7 watts 8 ohms, Stereo	11.75
SAC30	Mains 15 + 15 watts 8 ohms, Stereo	14.95
CAO38	9 volt 1 1/2 + 1 1/2 watts 8 ohms, Stereo	6.95
CAO68	12 volt 3 + 3 watts 8 ohms, Stereo	10.50

<b>FM Modules</b>		
Mullard LP 1185	FM tuner (front end) with data 10.7 MHz O/P	4.85
Mullard LP 1185	10.7 MHz IF unit with data	4.50
Gorler	Permeability FM tuner (front end) 10.7 MHz O/P	4.20
<b>FM and AM tuners and decoders</b>		
FM 5231	(cu 2) 6 volt fm tuner	7.95
TU3	12 volt version (FM use with Decoder)	7.95
SD4912	Stereo Decoder for Tu 3, 12 volt	7.95
SP62H	6 volt stereo FM tuner	4.80
A10C7	9 volt MW-AM tuner	11.95
Sinclair	12.45 volt FM tuner stereo recorder for above	7.45
A1018	9 volt FM tuner in cabinet	13.95
A1005M	(S) 9-12 volt Stereo decoder FM for above	7.50
1062	12 volt Stereo decoder general purpose	6.50
<b>PRE-AMPLIFIERS</b>		
Sinclair	Stereo 60 Pre-amplifier with controls	6.75
I1300	Carti Tape/Mic Inputs 9 volt Module	2.85
E1310	Stereo 3-30 mV mat cart 9 volt	4.75
FF3	Stereo 3 mV tape head 9 volt	4.95
EC2	Stereo 5-20 mV Mat. cart. mains	5.95
EC2S	Mono 3-250 mV Tape, Carti/Play 9 volt	5.95
<b>Power Supplies</b>		
470C	6.75/9V 300 MA with/rdrs 2-25 *P1081 45V 0.9A	7.80
P500	9 volt 500 MA	3.20
HC244R	3.6/7.5/9v. 400 MA	3.20
stabilised		12.75
*P11	24v, 1 amp, 1-30	3.30
*P15	28V, 1 amp, 1-30	3.30
*P1080	12V 1A 4-70	7.80

<b>SINCLAIR MODULES &amp; KITS</b>	
<b>SINCLAIR PROJECT 80</b>	
ST80 Stereo pre-amplifier	11.95
Audio Filter Unit	6.95
Z40 15 Watt Amplifier	5.45
Z60 25 Watt Amplifier	6.95
P25 Power Supplies for	4.98
P26 Power Supplies (5 Tab) for 1 or 2 Z40	7.98
P28 Power Supplies (5 Tab) for 1 or 2 Z60	7.98
TRANSFORMER FOR P28 FM TUNER	3.95
STEREO DECODER IC20 power amp kit	11.95
PZ20 power supply for 1 or 2 IC20	7.95
TRANSISTORS/SEMICONDUCTORS	5-45

UK's largest stockists of branded guaranteed devices at low prices. EXTRA DISCOUNTS Any one type. Extra 10% for 12 | 15 | 25 | 200 | 100 |. The above also applies to mixed S/N74 series IC. Get Your free stock list now—new '74-'75 edition now available (Ref. No. 36).

#### EXCLUSIVE DECCA KELLY SPEAKERS

12 watt speaker / tweeter systems 8 in. bass/midrange. Mattex domed HF radiator plus crossover. Built into veneered cabinets size 16 1/2 x 6 1/2 in. PRICE £19.50 pair (carr., ecc. £1.00)

#### EMI SPEAKERS SPECIAL PURCHASE

13 in x 8 in chassis speakers (carr., packing 30p each or 50p pr) \*150 TC 10 watts 8 ohms twin cone £2.20 \*450 10 watts 4, 6, 15 ohm with twin tweeters and crossover £3.85 each EW 15 watt 8 ohm with tweeter £5.25 350 20 watt 8, 15 ohm with tweeter £7.80 ea. \* Polished wood cabinet £4.80 carr., ecc. 35p each or 50p pair.

#### PHILIPS 8 WATT FLUORESCENT UNIT EXCLUSIVE PURCHASE

Brand new Philips 12 volt operated 8 watt fluorescent tube units for standby lighting. Complete with tube and instructions. Price £3.50 p & p 25p.

#### EXCLUSIVE 5 WATT IC AMPLIFIERS

Special purchase 5 watt output 8-16 ohm load, 30 volt max. DC operation, complete with data. Price £1.50 each or 2 for £2.85. Printed Circuit Panels. 50p

#### UHF TV TUNERS

625 line receiver UHF transistorised tuner FM UK operation. Brand new. (Postpacking 25p each) TYPE C variable tuning £2.50 TYPE B 4-button push-button (adjustable) £3.50

#### HENRY'S HOME ENTERTAINMENT CENTRES

London  
354/6 Edgware Rd. W2 01-402 5854  
376/8 Edgware Rd. W2 01-723 2564  
372 Edgware Rd. W2 01-402 8140  
120 Shaftesbury Ave. W1 01-437 9692  
230 Tottenham Court Rd. W1 01-580 1785  
144 Burnt Oak B'way, Burnt Oak, Edgware 01-952 7402  
190/4 Station Rd., Harrow, Middlesex 01-863 7788  
Out of Town  
256 Banbury Rd., Summerdown, Oxford (0865) 53072  
55 Gloucester Rd., Bristol 7 (0272) 45791

#### FREE STOCK LISTS

No. 36 Transistors/valves/semiconductors  
No. 18 Disc-lighting—high power sound  
No. 17 Hi-Fi TV-Tape Equipment  
Send large stamped address to envelope with all enquiries

### SUPPLIERS OF ELECTRONICS FOR OVER 30 YEARS 6% VAT TO BE ADDED TO ALL ORDERS VAT-UK ONLY

# Henry's RADIO

EDGWARE ROAD, W2

Electronic Centres  
404-406 Electronic Components & Equipment 01-402 8381  
309 PA-Disco-Lighting High Power Sound 01-723 6963  
303 Special offers and bargains store  
All mail to 303 Edgware Road, London W2 1BW  
Prices correct at time of preparation. Subject to change without notice. E.&O.E

Hi Fi and Electronics Centres Open 9 am - 6 pm