
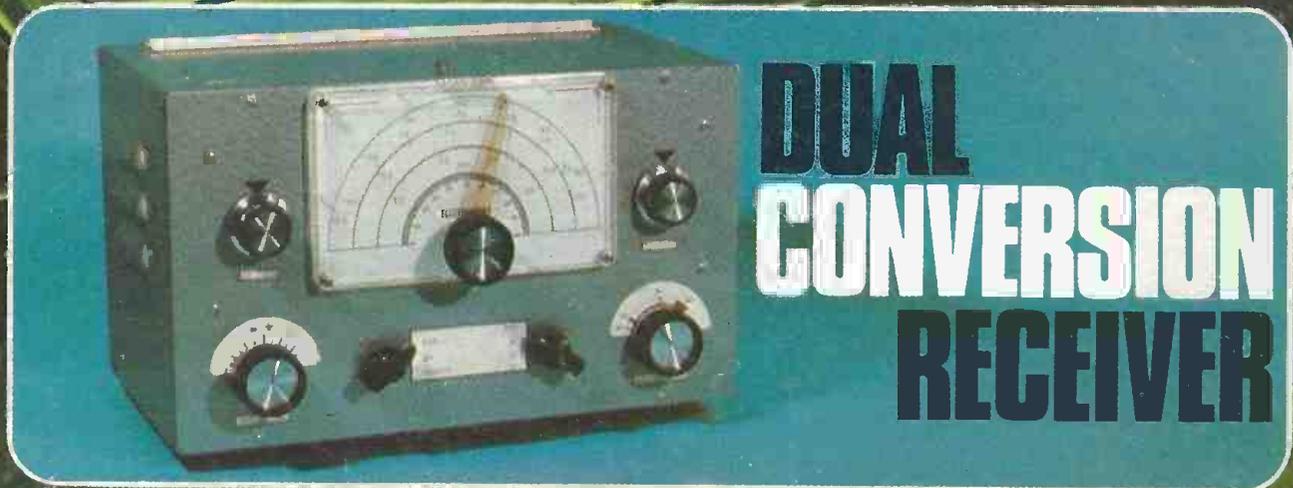


# PRACTICAL WIRELESS

AUGUST  
1975

30p

## **Pw** car Radio

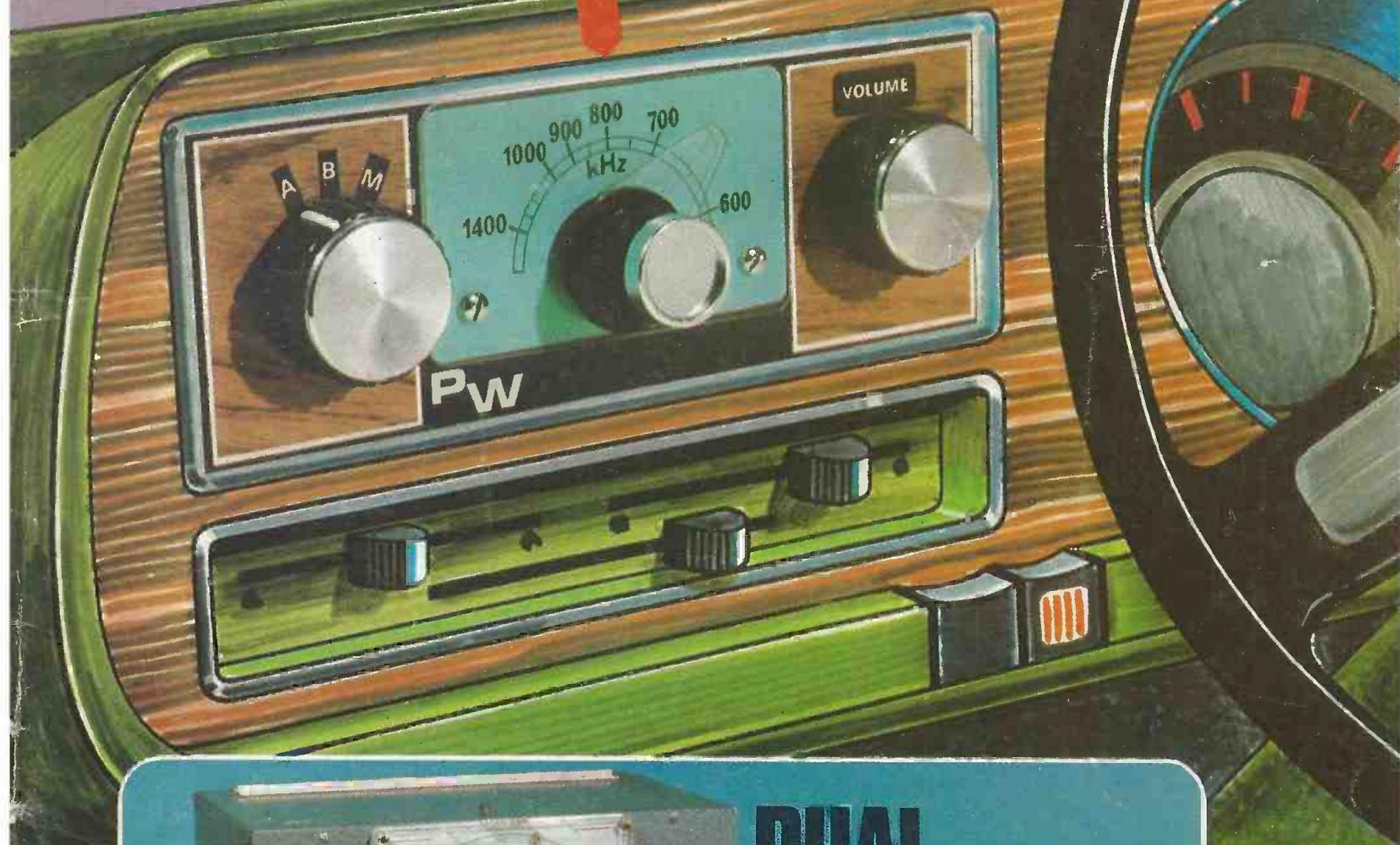

### DUAL CONVERSION RECEIVER

+ USING THE TDA2020 HIGH POWER AUDIO IC

**ALL MAIL ORDER BY  
RETURN. C.O.D. SERVICE  
WELCOME**

# C. T. ELECTRONICS

Tel: 01-994 6275

**V.A.T.**  
Unless otherwise stated all prices are exclusive of VAT. Please check whether the goods you are ordering are 25% or 8%. Carriage orders under £5 please add 33p. Order over £10 post free in U.K. only. This to be at our discretion.

All mail order and enquiries to 270 Acton Lane, Chiswick, London W4 5DG

## SEMICONDUCTORS

AAZ12	25p	BC214	14p	IS100	15p
AC107	35p	BC214L	15p	IS103	15p
AC125	25p	BC238	15p	MJ481	95p
AC126	25p	BC239	15p	MJ481	95p
AC127	25p	BC300	30p	MJ2801	£1.25
AC128	25p	BC301	30p	MJ2801	£1.95
AC176	25p	BC302	30p	MJE340	50p
AC187	27p	BC303	35p	MJE370	75p
AC188	27p	BCY31	35p	MJE371	90p
ACY17	25p	BCY32	95p	MJE520	65p
ACY18	25p	BCY33	60p	MJ2955	£1.20
ACY19	25p	BCY34	65p	MJE3055	75p
ACY20	25p	BCY38	65p	MM1613	45p
ACY21	25p	BCY39	95p	MM1712	60p
AD140	60p	BCY50	£1.50	MPP102	45p
AD142	60p	BCY70	20p	MPP103	35p
AD161	45p	BCY71	20p	(2N5457)	35p
AD162	45p	BCY72	20p	MPF10.4	
AF114	25p	BD121	75p	(2N5458)	35p
AF115	25p	BD123	85p	MPF105	
AF117	25p	BD124	70p	(2N5459)	40p
AF118	25p	BD131	40p	OA47	10p
AF119	25p	BD132	50p	OA70	10p
AF124	30p	BD135	50p	OA79	10p
AF239	60p	BD136	50p	OA81	10p
BA102	30p	BD139	75p	OA90	10p
BA112	50p	BD140	87p	OA91	10p
BA114	16p	BD153	80p	OA200	10p
BA155	16p	BDY17	£1.50	OA202	10p
BA156	16p	BDY17	£1.50	OA210	35p
BC107	13p	BDY18	£1.75	OA211	35p
BC108	12p	BDY19	£1.90	OC19	85p
BC109	14p	BDY20	£1.20	OC22	55p
BC109c	16p	BF152	20p	OC26	65p
BC113	13p	BF156	30p	OC28	60p
BC114	13p	BF178	35p	OC35	60p
BC115	15p	BF180	35p	OC36	65p
BC116	15p	BF194	16p	OC42	40p
BC117	20p	BF195	16p	OC44	20p
BC118	15p	BF196	16p	OC45	25p
BC119	30p	BF197	16p	OC70	15p
BC143	25p	BF200	35p	OC71	12p
BC147	12p	BF224	18p	OC72	20p
BC148	12p	BF244J	18p	OC75	25p
BC149	12p	BF245	45p	OC76	25p
BC149c	14p	BF259	55p	OC77	40p
BC157	14p	BFX29	30p	OC81	25p
BC158	14p	BFX34	30p	OC83	25p
BC159	15p	BFX85	30p	OC84	25p
BC167	14p	BFX86	30p	OC139	30p
BC168	14p	BFX88	30p	OC170	25p
BC169	14p	BFY10	35p	OC171	30p
BC169c	15p	BFY44	50p	OC200	60p
BC172	13p	BFY50	25p	OC201	60p
BC182	12p	BFY51	25p	OC202	75p
BC182L	12p	BFY52	25p	TIP29A	45p
BC183	12p	BFY53	25p	TIP30	55p
BC183L	12p	BFY90	65p	TIP31A	57p
BC184	12p	BSV63	75p	TIP32A	69p
BC184L	12p	BSW63	85p	TIP33A	£1.00
BC185	35p	BSW68	80p	TIP34A	£1.40
BC186	27p	BSX19	15p	TIP35A	£3.20
BC212	12p	BSX20	15p	TIP36A	£3.50
BC212L	14p	BSX21	25p	TIP41A	70p
BC213	12p	BY127	20p	TIP42A	85p
BC213L	12p	BY164	65p		

QTY. DISCOUNTS: 12+ 10%; 25+ 15%; 100+ 20%

## TTL (full stocks available)

SN7400	18p	SN7411	23p	SN7430	20p
SN7401	18p	SN7412	22p	SN7432	42p
SN7402	20p	SN7413	40p	SN7433	70p
SN7403	20p	SN7416	30p	SN7437	50p
SN7404	20p	SN7417	30p	SN7438	50p
SN7405	20p	SN7420	20p	SN7440	20p
SN7406	30p	SN7422	38p	SN7441 AN75	
SN7407	30p	SN7423	38p	SN7442	75p
SN7408	20p	SN7425	38p	SN7443	£1.00
SN7409	40p	SN7427	42p	SN7445	£1.70
SN7410	18p	SN7428	50p	SN7446	£2.00

SN7447	£1.50	SN7481	£1.25
SN7448	£1.75	SN7482	87p
SN7450	20p	SN7483	£1.00
SN7451	20p	SN7484	90p
SN7452	20p	SN7486	45p
SN7454	20p	SN7490	75p
SN7460	20p	SN7491AN	
SN7470	30p		£1.00
SN7472	30p	SN7492	75p
SN7473	40p	SN7493	75p
SN7474	40p	SN7494	80p
SN7475	55p	SN7495	80p
SN7476	45p	SN7496	£1.00
SN7480	80p	SN7497	£2.25

## S.C.R.s

CRS1/05	40p	2N2369A	50p
CRS1/10	56p	2N2477	30p
CRS1/20	60p	2N2646	50p
CRS1/40	65p	2N2846	£1.50
CRS1/60	90p	2N4904	25p
CRS3/10	62p	2N2905	30p
CRS3/20	62p	2N2906	25p
CRS3/40	90p	2N2907	25p
CRS7/400	£1.00	2N2926	13p
CRS16/100	85p	2N3053	25p
CRS16/200	90p	2N3055	50p
CRS16/600	£1.60	2N3232	£1.35
C106B	45p	2N3525	£1.10
C106D	70p	2N3643	30p
40669	90p	2N3702	12p
TIC44	35p	2N3703	12p
2N4444	£1.90	2N3704	12p
BT10/500A	90p	2N3705	12p
		2N3706	12p
		2N3707	12p
		2N3708	14p
		2N3709	14p
		2N3771	£1.50
		2N3772	£1.60
		2N3792	£1.80
		2N3794	30p
		2N3819	35p
		2N3820	55p
		2N3823	70p
		2N3866	85p
		2N3904	22p
		2N3905	25p
		2N3906	25p
		2N4014	80p
		2N4036	62p
		2N4037	44p
		2N4058	14p
		2N4059	14p
		2N4060	12p
		2N4061	12p
		2N4062	12p
		2N4126	18p
		2N4286	25p
		2N4287	27p
		2N4288	27p
		2N4289	30p
		2N4290	25p
		2N4291	32p
		2N4302	45p
		2N4444	£1.90
		2N4871	35p
		2N4903	£1.30
		2N4919	90p

## BRIDGE RECTIFIERS

W02 1A 200V	35p
BY164 1.4A 200V	57p
MDA952/2 6A 100V	80p

## ZENER DIODES

BZY88 Series	400mW
3.3V-33V, 5%	11p
1.5W range	25p
10W range	45p

## L.E.D.

TIL209	38p
HP5082	28p
MA2082R	20p

## L.D.R.

ORP12	60p
NE555 Timer	80p

## TO3 VOLTAGE REGULATORS

L005 5V 650mA	£1.60 ea.
L036 12V 600mA	
L037 15V 450mA	

## VEROBOARD

0.1	0.15
2 1/2 x 3 1/2	32p
2 1/2 x 5	35p
3 1/2 x 3 1/2	35p
3 1/2 x 5	40p
17 x 2 1/2	£1.05
17 x 3 1/2	£1.43
17 x 5	£1.84
PIN INS. TOOL	72p
S.P.F. CUTTER	52p
100 PINS SS	30p
100 PINS DS	30p
500 PINS SS	£1.55
500 PINS DS	£1.55

## BNC PLUGS at 35p each

UHF (N) PLUGS at 50p each.

U.H.F. V.S.W.R. probes ex U.H.F. transmitters £5 each + 8% VAT  
All the above are new in original packets. Please add 8% VAT P & P 30p.

## POTENTIOMETERS

Linear or Log	Single	Double
Rotary Pots	17p	45p
Rotary Switched	25p	—

## TRIACS

TXL228B 8A 400V	85p
SC40D	£1.40
SC40E	£1.65
SC45D	£1.70
SC45E	£2.10
SC50D	£2.42
SC50E	£2.70
DIAC	25p

## LINEAR I.C.s

LM304 Neg Voltage Reg.	£2.10
LM309K 5V, 1A. Voltage Reg.	£2.10
LM723C 2.37V, 150mA Voltage Reg.	75p
MFC4000 250mW Audio	75p
TBA800 5 Watt Audio	99p
709C Op Amp D.I.L./TO99	45p
741C Op Amp 8/14 D.I.L./TO99	35p
747C Dual Op Amp	£1.20
748C Op Amp D.I.L.	75p
ZN414 Radio I.C.	£1.25
TAD100 Radio I.C. inc. Filter	£1.90
CA3014	£1.55
CA3018	£1.00
CA3028	£1.20
CA3036	£1.00
CA3046	95p
CA3048	£2.35
CA3075	£1.60
CA3089E	£1.90
CA3090Q	£4.85
MC1303L	£2.20
MC1310P	£2.80
SN76660 EQ	60p
TBA120	65p

## ★★SPECIAL OFFERS★★

**MINIATURE MAINS TRANSFORMER.**  
PRI 240V. SEC. 12V. 100Ma Manuf.: Hinchley  
Size: 36 x 45 x 40mm. F.C. 53mm.  
Price 1.65p. 100.60p ea. 1,000 50p ea. 10,000 40p ea. 8% VAT.

**MINIATURE MAINS TRANSFORMER.**  
Primary 115/240V Sec. 18v/250 Ma at 80p ea.  
+ VAT & postage 33p. 8% VAT.

**MULLARD POT CORE TYPE FX2241** at 60p ea. + 33p p.p. 8% VAT.

**24V D.C. SOLENOID** by MAGNETIC DEVICES 60p each. 2 1/2" long x 1 1/2" x 1 1/2". + 8% VAT.

**240V A.C. SOLENOID.** Reversible operation; twin coil. Size approx. 2 1/2" x 1 1/2" x 1 1/2". 90p.

30 unmarked OC71 transistors £1.00  
25 Unmarked 250mW Zener diodes, 4-7V, 5-1V, 6-2V, 7-5V, 9-1V, 10V, Measured and tested £1.00

Please state voltage required.  
50 GE Diode OA47 equivalent. £1.00

8µF 600V WKG PAPER CAPACITORS, ideal for Strobe Constructors £1.50 each + 8% VAT + 33p post.

Many other values of PAPER CAPACITORS in stock. Phone for details.

**JACKSON AIRSPACED CAPACITORS** to suit 1in. spindle:

100pF Two Gang at 55p + 25% VAT  
500pF Two Gang at 75p + 25% VAT

**MULLARD TUBULAR CERAMIC UHF TRIMMERS (PROFESSIONAL)**

Type 092 0.8-2.2p } Price 10p ea.  
801 0.8-2.2p }  
991 0.5-1.3p }

**QUANTITY DISCOUNTS PLEASE TELEPHONE**

1000pF Feedthrough capacitor 5p ea.  
Miniature tubular P.C. trimmers  
3-5-13pF  
6-30pF 10p ea.  
4p c/o Varley 700Ω relay 50p ea.

**Gold Flashed professional TRANSISTOR SOCKETS.** To suit small signal TO18, etc. 30 for £1.00 + 8% VAT.

**W. WOUND POTS** 1Ω-100KΩ at 30p each  
Covern or Reliance styles + 25% VAT

**VERO EDGE CONNECTOR** 24 way 1" pitch 30p each + 8% VAT. All the other sizes in stock.

**SIEMENS VARLEY RELAY** 4P C/O 700Ω 24V 50p each.

**PLESSEY RELAY** 2 P C/O 6V operation 40p each.

**MODERN DISC CERAMICS** £1.00 a hundred, £8.00 a thousand + 25% VAT. Phone or write for list.

**ACCESSORIES**  
DIL SOCKETS, 8 pin 14p, 14 pin 14p, 16 pin 14p. Mica Washers + 2 Bushes (TO3 or TO66) 4p.

## METAL BOXES

**ALUMINIUM BOXES IDEAL FOR VERO-BOARD WITH BASE & P.K. SCREWS**

AB7	2 1/2" Long	5 1/2" Wide	1 1/2" High	55p
AB8	4"	4"	1 1/2"	55p
AB9	4"	2 1/2"	1 1/2"	55p
AB10	4"	5 1/2"	1 1/2"	55p
AB11	4"	2 1/2"	2"	65p
AB12	3"			

# PRACTICAL WIRELESS

VOL. 51 NO. 4

ISSUE 822

AUGUST 1975

BRITAIN'S PREMIER MAGAZINE FOR THE DO-IT-YOURSELF RADIO AND ELECTRONICS CONSTRUCTOR

## EDITOR

Lionel E. Howes, G3AYA

## ASSISTANT EDITOR

Eric Dowdeswell, G4AR

## ART EDITOR

Peter Metalli

## TECHNICAL EDITOR

Sam Lewis B.Sc. (Eng.)

## PRODUCTION & NEWS EDITOR

Colin R. Riches

## TECHNICAL SUB-EDITOR

Bill Tull

## TECHNICAL ARTIST

Alan Martin

## SECRETARIAL

Jenny Maunder  
Susan King

## ADVERTS MANAGER

01-634 4293 Roy Smith

## CLASSIFIED ADVERTS

01-634 4301 Colin R. Brown

Published by IPC Magazines Ltd.,  
Fleetway House, Farringdon Street,  
London EC4A 4AD. Tel. 01-634 4444

## SUBSCRIPTIONS

Publisher's Subscription Rate for one year to the UK is £5.00 and to the rest of the world £5.00 (\$13.50 USA/CAN) including postage. Enquiries to Subscription Department, IPC Magazines Ltd., Carlton House, 68 Gt. Queen Street, London, WC2 5DD. Phone 01-242 4477. International Giro facilities Account No. 5122007. Please state reason for payment "message to payee".

Binders (£1.90) and indexes 30p (inc. VAT) can be supplied by the Binders Dept at the same address.

## BACK NUMBERS

We regret that we are unable to supply back numbers of Practical Wireless. Readers are recommended to enquire at a public library to see copies. Requests for specific back numbers of Practical Wireless and Television only can be published in our CQ Column.

## ● NEWS & COMMENT

- 286 TECHNOLOGICAL POVERTY—Editor's comment
- 287 NEWS . . . NEWS . . . NEWS . . .
- 303 NEXT MONTH IN PRACTICAL WIRELESS
- 310 LETTERS—Readers comment
- 311 PRODUCTION LINES by *Colin Riches*
- 318 TELEVISION—coming in the next issue
- 323 HOTLINES on recent developments by *Ginsberg*
- 324 PRACTICAL WIRELESS BINDERS
- 324 BOOK REVIEW—A Guide to Amateur Radio—*RSGB*
- 326 ON THE AIR
- 326 Amateur Bands—*Eric Dowdeswell, G4AR*
- 329 Broadcast Bands—Short Waves—*Derek Bell*
- 330 Broadcast Bands—Medium Waves—*Charles Molloy*

## ● CONSTRUCTIONAL

- 288 DUAL CONVERSION RECEIVER—Part 1—*F. G. Rayer*
- 297 P.W. 'APOLLO' Series—Part 4—Varicap AM/FM Stereo Tuner—construction and setting-up—*W. Poel*
- 304 P.W. CAR RADIO—*Charles Heath*
- 314 A DRAIN DIP OSCILLATOR—*F. G. Rayer*
- 319 DIGITAL WAVEFORM GENERATOR—Part 3—*John Smith*

## ● OTHER FEATURES

- 309 TECHNICROSS—No 10
- 312 I.C. OF THE MONTH—SGS-ATES TDA2020 Power Amplifier
- 316 CQ! CQ! CQ! CQ! CQ!
- 317 GOING BACK—Earlier days of Wireless—*Colin Riches*
- 330 POINTS ARISING—notes on the 'ASCOT'

## COPYRIGHT AND QUERIES

© IPC Magazines Limited 1975. Copyright in all drawings, photographs and articles published in "Practical Wireless" is fully protected and reproduction or imitation in whole or in part is expressly forbidden. All reasonable precautions are taken by "Practical Wireless" to ensure that the advice and data given to readers are reliable. We cannot, however, guarantee it and we cannot accept legal responsibility for it. Prices are those current as we go to press.

We regret that we cannot answer technical queries by telephone nor can we provide information or advice on manufacturers' products other than that given in the magazine. We will endeavour to assist readers who have queries relating to articles published but we cannot offer advice on modifications to our published designs. All correspondents expecting a reply should enclose a stamped addressed envelope.

## IMPROVE PETROL CONSUMPTION

Fit the Brilliant New P.E. Scorpio Mk II "Dual Polarity" Capacitive Discharge Electronic Ignition System



- ★ Genuine improvement in overall petrol consumption (independent report claims at least 8%—10%)
  - ★ Much easier cold weather starting, less strain on your battery
  - ★ Less use of choke—increases engine life
  - ★ Smoother running at lower revs—makes your four cylinder car feel like a six cylinder
- Together with the following 'Scorpio Mk II' plus features not previously available with other makes:—
- ★ Only one model used for both positive (+) and negative (—) earth vehicles—if you change your car, you can certainly transfer your 'Scorpio'.
  - ★ Retains your original contact breaker points, which last their mechanical life—no points burn
  - ★ Will drive electronic tachometers.


Send a stamped addressed envelope for our free interesting brochure, "Electronic Ignition—How it Works", containing circuit and itemised price list. Price for complete kit of parts, with easy to follow, comprehensive instructions, connecting wire, etc. **ONLY £19.95**, including V.A.T. and postage and packing. Ready made unit, fully tested, for immediate installation with easy to follow instructions, all leads, etc., **ONLY £13.85**, including V.A.T. and postage and packing.

**THOUSANDS ALREADY IN USE—FULLY GUARANTEED.**

**ELECTRO SPARES, 288 ECCLESALL ROAD, SHEFFIELD S11 8PE**

*Please allow 14 days minimum for delivery, for postal delays, cheque clearance, etc.*
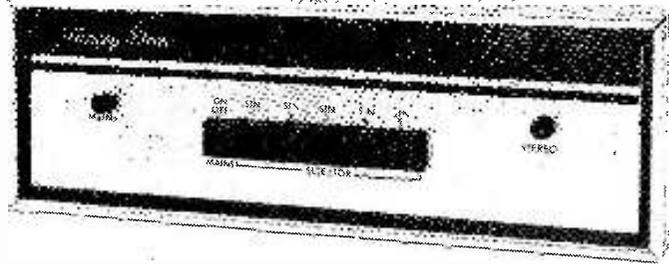
## P.E. 'VARICAP' STEREO PUSH BUTTON F.M. TUNER



The P.E. 'Varicap' Stereo Tuner uses the latest Mullard modules for R.F. and I.F. circuits—highly sensitive and pre-aligned for ease of construction. This superb kit has everything to enable you to construct this highly sensitive F.M. Stereo Tuner, with instant push button station selection, self contained regulated

power supply, stereo decoder, etc. etc. Easy to construct, highest quality reproduction. Price only **£34.50** including V.A.T. and postage and packing. Please send stamped addressed envelope for our free brochure on the Varicap, which gives performance figures, detailed description, etc., etc.

## P.E. 'GEMINI' STEREO AMPLIFIER

Output genuine 30W R.M.S. per channel! Distortion 0.01% (Maximum)! Frequency response —3dB, 20Hz to 100 kHz into 8 ohms! Fully comprehensive inputs, disc, tape, MIC etc.!

Yes, we are still supplying all components for this superb Stereo Amplifier, since we have not yet found a better one!

Fully comprehensive constructional booklet available, containing full specification, performance graphs, step-by-step, assembly instructions, photographs, fault finding guide, etc. etc. Price 55 pence plus 9 pence postage and packing.

For itemised price list only please forward stamped addressed envelope.

# Train for television

Course commences September 8th 1975

This is your opportunity to train as a television and radio engineer on our full-time Two-Year College Diploma Course specially designed to cover the examinations of the City and Guilds Radio, Television and Electronics Technicians' Certificate. Full theoretical and practical instruction on all types of modern receivers—including the latest colour sets.

Minimum entrance requirements are Senior Cambridge or 'O' Level, or equivalent in Mathematics and English.

Please send free prospectus to:

Name \_\_\_\_\_

Address \_\_\_\_\_  
 \_\_\_\_\_  
 \_\_\_\_\_

**THE PEMBRIDGE COLLEGE OF ELECTRONICS**

(Dept PW 5) 34a Hereford Rd., London W2 5AJ



4½ in × 3½ in **METER.** 30µA, 50µA or 100µA, £3.85. P. & P. 13p.

**TAPE RECORDER LEVEL METER**

500µA, 80p  
P. & P. 10p.



**CARDIODYNAMIC MICROPHONE**

Model UD-130. Frequency response 50–15,000c/s. Impedance Dual 50K and 600 ohms, £7.40. P. & P. 13p.




42 × 42mm **METERS** 100µA, 500µA, 1mA, 500mA £2.76, 11p P. & P.

60 × 45mm **METERS** 50µA, 100µA, 500µA and 1mA **VU METER** £2.92, 11p P. & P.

**EDGEWISE METERS**, 90mm × 34mm, 1mA £3.40, 13p P. & P.

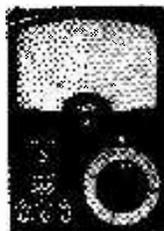**MULTI-METER**

Model ITI-2  
20,000 ohm/volt, £6.90.  
P.&P. 16½p.



**3 WATT STEREO AMPLIFIER**

1½W PER CHANNEL  
£4.30. P. & P. 12½p.



All above prices include V.A.T. LARGE S.A.E. for List No. 12. Special prices for quantity quoted on request.

**M. DZIUBAS**

158 Bradshawgate · Bolton · Lancs. BL2 1BA

# RSC 100 watt DISCO SYSTEM

**50 WATT SPEAKER**    **50 WATT SPEAKER**

**TWIN TURNTABLE WITH PRE-AMP. and POWER AMPLIFIER**

**Complete with lid**

**HEADPHONES MICROPHONE**

*AT FANTASTIC LOW PRICES!*

Units listed below

(a) DISCOMASTER TWIN TURNTABLE CONSOLE with integral 100W amplifier

(b) PAIR OF HI-FI HEAD PHONES

(c) MATCHING DYNAMIC 'MIKE' (attached to h'phone)

(d) PAIR 50 WATT SPEAKERS Black Rexine covered Cabinets Size approx. 18" x 18" x 8"

(a) (b) (c) & (d) Carr. £3-00

**£169-99**

## RSC TDI DISCO CONSOLE

Incorporating twin BSR MP60 type turntables and Sonotone or Acoas Cartridges with diamond styl. Separate Vol. controls for each turntable. Also MONITORING FACILITIES, plus Treble and Bass Controls; Separate input for 'mike' with vol. control switch. Black Vynide covered Cabinet with lid, see illustration on left. Or DEP. £9-95 and 18 fortnightly pymts. £5-11 (Total £101-98) Carr. £1-50

**£89-95**

**DEP. £19-99 & 18 fortnightly payments of £9-75 (Total £195-49).**

**STEREO VERSION**

Above System Or DEPOSIT £34-95 and 18 fortnightly pymts. £11-19 (Total £286-87) Carr. £3-50

**£209-95**

**TD2S STEREO VERSION OF ABOVE**

Terms DEPOSIT £80 and 18 fortnightly payments £6-71 (Total £140-78) Carr. £1-60

**£125-00**

### DISCOMASTER TWIN TURNTABLE POWER CONSOLE £119-95

Twin McDonald MP60 type turntables, Sonotone or Acoas cartridges with diamond styl. Facilities as TDI Console but with built-in 100 watt Power Amplifier, complete with lid. Or Deposit £13-95 and 18 fortnightly payments £6-78 (Total £135-99)

Carr. £2-50

**STEREO VERSION £155** or DEPOSIT £25 and 18 fortnightly pymts £8-30 (Total £174-40). Carr. £3

### FANE ULTRA HIGH POWER SPEAKERS & KITS

All power ratings are R.M.S. continuous. 2 YEARS' GUARANTEE High flux ceramic magnets. ALL CARRIAGE FREE.

'POP' 100	'POP' 60	'POP' 50
18" 100 Watt 14,000 gauss 8/15Ω	15" 60 Watt 14,000 gauss 8/15Ω	12" 50 Watt 13,000 gauss 15Ω
<b>£35-95</b>	<b>£18-95</b>	<b>£13-95</b>
Dep. £7-95 and 8 mthly payments £4-00 (Total £39-95)	Dep. £4-17 and 8 mthly payments. £2-17 (Total £21-53)	Terms for pairs Dep £5-90 & 8 mthly pymts £3-16 Total £81-48

FOR BASS GUITAR, ELECT. ORGAN, ETC.

### R.S.C. COLUMN SPEAKERS

All types 15 Ohms covered in Vynide & Vynair

**TYPE C132 40-50 WATTS £27-95**

Incorporating two exceptionally efficient 13" x 8" speaker units. Dep. £3-95 and 8 monthly payments £3-50 (Total £31-95) Carr. 65p

**IDEAL FOR VOCALISTS AND PUBLIC ADDRESS**

**TYPE C370 70 WATTS. Fitted three 12" 25 watt Highly sensitive high flux speakers with high power voice colls. Size approx. 54" x 14" x 11". Dep. £5-11 & 8 mthly pymts. £5-11 £39-95 (Total £45-99) Carr. 85p**

### ALL RSC PRICES INCLUDE VAT

**INTEREST on Credit Purchases REFUNDED settled in 3 months**

**SUPER MINSTREL 10 W GUITAR AMP.**

Incorporating Tremolo and 10" Speaker. Output 10 watts R.M.S. Continuous. 3 Jack Inputs for Microphone and Instrument. Mains Neon Controls: Volume, Tone, Tremolo, Speed Tremolo Intensity.

Terms: DEPOSIT £7-78 and 8 monthly payments £3-40 (Total £34-98) Carr. free

**£29-99**

**FANE CRESCENDO SPEAKERS**

FULL RANGE AVAILABLE AT ALL BRANCHES

**'POP' 25/T 12" 25W**

Dual cone. 15 ohm Imp. (Not for Bass Guitar use)

Terms for Pairs: Deposit £3-90 and 8 mthly payments of £2-75 (Total £25-90).

**£10-99**

**PH50 HIGH POWER TWEETER**

Response 3KHz-20KHz with 2 to 4 mid. Non elect. filter available 55p.

Rating 50 Watt Imp 8 Ω

**£6.65**

### FAL MAESTRO COMBINED 30W AMP. AND 12" SPEAKER £56-25

For Lead Guitar, Mic, Gram, Radio, Tape (Not for use with Bass Instruments) Inc. 3 inputs and 2 vol controls plus Treble & Bass, TREMOLO with associated controls. Attractively finished in black with silver-finished fascia. Compact size Fitted carrying handle. Deposit £9-25 and 8 mthly payments £6-76 (Total £68-33)

Carr. Free

**RSC 'PHANTOM 50'**

Rating 50 watts, 3 inputs, 2 vol. controls. Bass, Treble, Presence

Dep. £7-95 & 8 mthly. pymts. £7-48 (Total £67-79).

**£59-95** Carr. £1-50

### D40 50 WATT DISCO KIT

ALL PURPOSE FULL RANGE

Consisting of 12" 13,000 Gauss Bass Unit, HPX1 Cross over and PH50 Tweeter. Imp 8Ω (Bass Guitar requires pair in one cabinet). Terms: Dep. £3 x 8 mthly. pymts. £2-75 (Total £25)

Carr. Free

**£21-50**

### FAL PHASE 50 Mk. III AMPLIFIER 50 WATT

Solid state. 4 Sep. controlled inputs Plus master vol. control. Ind. Bass and Treble Controls. Protection against serious o/p overloading. O/p for spkrs. 8 to 15 ohms. Size 17" x 7" x 7". 200-250v. A.C. mains. O/p 50w Music. Deposit £8-60 & 8 mthly. payments. £5-75. Total £24-60

Carr. Free. **£48-60**

**JINGLE MACHINES I.S.E. CA127 £79-95** DEPOSIT £9 and 18 fortnightly payments £4-61. Total £91-98

### TITAN GROUP/DISCO SPEAKERS

as advertised elsewhere in this issue Send S.A.E. for leaflet

**FULL RANGE AT DISCOUNT PRICES**

### REGENT 50X 50 WATT AMP.

A powerful high quality unit for lead, rhythm guitar, vocalists, gram, radio, tape. 50w Peak O/P rating. Not for Bass Guitar.

★ Two Fane heavy duty high flux 12in. spkrs.

★ Four Jack inputs and two Volume Controls for instant use of up to four pick-ups or "mikes". Bass and Treble controls.

Send S.A.E. for leaflet. Credit Terms: Deposit £9-95 & 18 fortnightly payments of £4-15 (Total £284-65).

**£74-95**

Carr. £2-50

**REGENT 50B** for Bass Guitar and general purposes. Or Dep. £8-00 & 18 fortnightly payments £4-61. (Total £91-98). Carr. £2-50

**£79-95**

### HIGH QUALITY LOUDSPEAKER UNITS

ALL 2-TONE VYNIDE & VYNAIR FINISH

L12/2 50 WATT Fitted pair of 12" 30 watt high flux speakers. Imp. 8-15 ohms. Carr. £1-50

Terms: Dep. £5-11 and 8 monthly payts. of £5-11. Total £45-99

L12/50 12" 50 WATT 13,000 lines 15 ohms

Terms Dep: £3-95 & 8 monthly payments £3-37 (Total £30-91) Carr. 55p.

**£25.95**

### FAL DISCO PRE-AMPLIFIER

T/Table mixing inputs. Headphone Monitoring. Mic. Jack & Tape inputs. Independent Vol. Control. Std. 200-250v A.C. Mains operation

**£18-50**

### LIQUID WHEEL from PROJECTORS £24-75

**'SOUND TO LITE' SYSTEM**

**PULSAR** special price complete kit **£99-95**

Dep. £11-48 and 18 fortnightly payts. £5-74. (Total £114-80). Super SL Unit. 1000 watt per channel. Manual override buttons, 2 spotbanks with 6 bulbs (3 sep. colours) 5 yd. and 10 yd. leads, fitted plugs. Units sold sep.

**FAL SOUND-TO-LITE UNIT £21-60**

**" 3-WAY SPOT BANK** Excluding Bulbs Each **£16-20**

**COMPLETE SYSTEM** Incl. 2 Spotbanks and bulbs. Carr. £1-50 **£55**

## NEW BRANCHES AT BOLTON, DONCASTER, and PRESTON

OPEN ALL DAY SATURDAYS (5 Day Week)

**BRADFORD** 10 North Parade (Closed Wed.). Tel. 25349

**BOLTON** 23 Deansgate. (Closed Wed.). Tel. 33512

**BIRMINGHAM** 30/31 Great Western Arcade. Tel. 021-236 1279 (Closed Wed.).

**COVENTRY** 17 Shelton Square, The Precinct. Tel. 25983

**DERBY** 97 St. Peter's Street. (Closed Wed.). Tel. 41361

**DARLINGTON** 19 Northgate (Closed Wed.). Tel. 68043

**MANCHESTER** 60A Oldham Street (Closed Wed.). Tel. 238 2778

**MIDDLESBROUGH** 108 Newport Road (Closed Wed.). Tel. 47096

**NEWCASTLE UPON TYNE** 24 Newgate Shopping Centre (Closed Wed.). Tel. 21469

**NOTTINGHAM** 19/19A Market Street (Closed Thurs.). Tel. 48088

**PRESTON** 41 Friargate Walk, St. Georges Shoppg Prec. Tel. 51979

**SHEFFIELD** 13 Exchange Street (Castle Mkt. Bldg.).

**STOCKPORT** (Closed Thurs.). Tel. 20716

**SUNDERLAND** 5 Market Sq. (Closed Wed.). Tel. 70573

**LIVERPOOL** 73 Dale St. (Closed Wed.). Tel. 236 3573

**LONDON** 238 Edgware Road, W.2. (Closed Thurs.). Tel. 723 1629

**LEICESTER** 32 High Street (Closed Thurs.). Tel. 56420

**LEEDS** 5-7 County (Mecca) Arcade, Briggate (Closed Wed.). Tel. 458252

**HULL** 7 Whitefriargate (Closed Thurs.). Tel. 20505

**GLASGOW** 326 Argyle St. (Closed Tues.). Tel. 229 9501

**EDINBURGH** (Closed Thurs.). Tel. 63069

**DONCASTER** 3 Queensgate, Waterdale Centre. (Closed Thurs.). Tel. 63069

**101 Lothian Rd. (Closed Wed.). Tel. 229 9501**

**HI-FI CENTRES LTD.**

Barclaycard and Access accepted

All items subject to availability. Prices correct at 17.6.75 E. & O.E.

# Marshall's

A. Marshall & Son (London) Limited Dept. PW  
42 Crickwood Broadway London NW9 3HD Tel: 01-452 0161  
& 85 West Regent Street Glasgow G22 QD Tel: 041-332 4133

Everything you need is in our new 1975 catalogue. Available now price 25p

Trade and export enquiries welcome

Our range covers over 7,000 items. The largest selection in Britain

## Top 200 IC's TTL, CMOS & Linears

CA3018A 85p	CD4043 £1.80	NE565 £4.48	SN7448 90p	SN74157 95p
CA3020A £1.80	CD4044 £1.80	SL414 £1.80	SN7450 16p	SN74160 £1.10
CA3028A 79p	CD4045 £2.65	SL610C £1.70	SN7451 16p	SN74161 £1.10
CA3035 £1.37	CD4046 £1.65	SL611C £1.70	SN7453 16p	SN74162 £1.10
CA3048 70p	CD4047 £1.65	SL612C £1.70	SN7454 16p	SN74163 £1.10
CA3052 £2.11	CD4049 81p	SK620C £2.60	SN7460 16p	SN74164 £2.01
CA3052 £1.62	CD4050 66p	SL621C £2.60	SN7470 33p	SN74165 £2.01
CA3085E £1.94	LM301A 48p	SL623C £2.59	SN7472 26p	SN74167 £4.10
CA3090Q £4.23	LM308 £2.50	SL640C £3.10	SN7473 36p	SN74174 £1.25
CD4000 36p	LM308 £2.50	SN7400 16p	SN7474 36p	SN74175 90p
CD4001 36p	LM380 £1.10	SN7401 16p	SN7475 50p	SN74180 £1.40
CD4002 36p	LM381 £2.20	SN7401 AN38p	SN7476 35p	SN74181 £1.95
CD4006 £1.58	LM702C 75p	SN7402 16p	SN7480 50p	SN74180 £1.40
CD4007 36p	LM709 35p	SN7403 16p	SN7481 £1.25	SN74181 £1.95
CD4008 £1.63	8DIL 48p	SN7404 19p	SN7482 75p	SN74190 £2.30
CD4009 £1.18	14DIL 40p	SN7405 19p	SN7483 95p	SN74191 £2.30
CD4010 £1.18	14DIL 40p	SN7406 45p	SN7484 95p	SN74192 £1.15
CD4011 36p	LM723C 90p	SN7407 45p	SN7485 £1.25	SN74193 £1.15
CD4012 36p	LM741C 32p	SN7408 19p	SN7486 32p	SN74196 £1.60
CD4013 66p	8DIL 40p	SN7409 22p	SN7490 45p	SN74197 £1.58
CD4014 £1.72	14DIL 38p	SN7410 16p	SN7491 85p	SN74198 £2.25
CD4015 £1.72	LM747 £1.05	SN7411 25p	SN7492 45p	SN74199 £2.25
CD4016 66p	LM748 60p	SN7412 28p	SN7493 45p	SN76003N £2.92
CD4017 £1.72	14DIL 73p	SN7413 35p	SN7494 82p	SN76013N £1.95
CD4018 £2.55	LM3900 70p	SN7416 35p	SN7495 72p	SN76023N £1.60
CD4019 85p	LM7805 £2.00	SN7417 16p	SN7496 75p	SN76033N £2.92
CD4020 £1.91	LM7812 £2.50	SN7420 16p	SN74100 £1.25	TAA263 £1.10
CD4021 £1.72	LM7815 £2.50	SN7423 29p	SN74107 36p	TAA300 £1.80
CD4022 £1.66	LM7824 £2.50	SN7425 29p	SN74118 £1.92	TAA350A £2.10
CD4023 36p	MC1303L £1.50	SN7427 29p	SN74119 £1.92	TAA550 60p
CD4024 £1.24	MC1318P £2.59	SN7430 16p	SN74121 37p	TAA611C £2.18
CD4025 32p	MC1330P 90p	SN7432 28p	SN74122 50p	TAA621 £2.03
CD4026 43p	MC1351P 80p	SN7437 35p	SN74123 60p	TAA661B £1.32
CD4028 £1.50	MC1352P 80p	SN7438 35p	SN74141 85p	TAA641B £2.25
CD4029 £3.50	MC1466L £3.50	SN7440 16p	SN74145 90p	TBA651 £1.69
CD4030 87p	MC1469R £2.75	SN7441 AN85p	SN74150 £1.50	TBA800 £1.40
CD4031 £5.19	NE555V 70p	SN7442 65p	SN74151 85p	TBA810 £1.40
CD4037 £1.93	NE556 £1.30	SN7446 95p	SN74153 85p	TBA810 £1.40
CD4041 £1.86	NE560 £4.48	SN7447 95p	SN84154 £1.50	TBA820 £1.15

PW TELENNIS KIT £42.50 + VAT Reprint 75p  
TRY OUR GLASGOW SHOP

## POPULAR SEMICONDUCTORS

2N696 22p	2N3906 27p	AF139 65p	BD139 71p	MPSA56 31p
2N697 16p	2N4037 42p	AF239 65p	BD140 87p	OC28 76p
2N698 82p	2N4036 67p	AF240 90p	BF115 36p	OC35 60p
2N699 59p	2N4058 18p	AF279 70p	BF117 55p	OC42 50p
2N706 14p	2N4062 15p	AF280 79p	BF154 20p	OC45 32p
2N708 17p	2N4289 34p	AL102 £1.00	BF159 27p	TIP29A 49p
2N916 28p	2N4920 £1.10	BC107 14p	BF180 35p	TIP29C 58p
2N918 32p	2N4921 83p	BC108 14p	BF181 36p	TIP31A 62p
2N1302 18p	2N4923 £1.00	BC109 14p	BF184 30p	TIP32A 74p
2N1304 26p	2N5245 47p	BC147B 14p	BF194 12p	TIP33A £1.01
2N1306 31p	2N5294 48p	BC148B 15p	BF195 12p	TIP34A £1.51
2N1308 47p	2N5296 48p	BC149B 15p	BF196 13p	TIP35A £2.90
2N1711 45p	2N5457 49p	BC157A 16p	BF197 15p	TIP36A £3.70
2N2102 60p	2N5458 46p	BC158A 16p	BF198 18p	TIP42A £0.90
2N2147 78p	2N5459 49p	BC167B 15p	BF244 21p	TIP2955 98p
2N2148 94p	2N6027 45p	BC168B 15p	BF257 47p	TIP3055 50p
2N2218A 22p	3N128 73p	BC169B 15p	BF258 53p	TIS43 28p
2N2219A 26p	3N140 £1.00	BC182 12p	BF259 55p	ZTX300 13p
2N2220 25p	3N141 81p	BC182L 12p	BF561 27p	ZTX301 13p
2N2221 18p	3N200 £2.49	BC183 12p	BF598 25p	ZTX500 15p
2N2222 20p	40361 40p	BC183L 12p	BFR39 24p	ZTX501 13p
2N2369 20p	40362 45p	BC184 13p	BFR79 24p	ZTX502 18p
2N2646 55p	40406 44p	BC184L 13p	BFX29 30p	IN914 7p
2N2904 22p	40407 35p	BC212A 16p	BFX30 27p	IN3754 15p
2N2905 25p	40408 50p	BC212LA 16p	BFX84 24p	IN4007 10p
2N2906 19p	40409 52p	BC213LA 15p	BFX85 30p	IN4148 7p
2N2907 22p	40410 52p	BC214LB 18p	BFX88 25p	IN5404 22p
2N2924 20p	40411 £2.00	BC237B 16p	BFY50 22p	IN5408 30p
2N2926G 12p	40594 74p	BC238C 15p	BFY51 23p	AA119 8p
2N3053 25p	40595 84p	BC239C 15p	BFY52 20p	BA102 25p
2N3054 60p	40636 £1.10	BC257A 16p	BRY39 48p	BA145 18p
2N3055 75p	40673 73p	BC258B 16p	ME0402 20p	BA154 12p
2N3391 28p	AC162 20p	BC259B 17p	ME0412 18p	BA155 12p
2N3392 15p	AC127 20p	BC301 34p	ME4102 11p	BB103B 23p
2N3393 15p	AC128 20p	BC307B 17p	MJ480 95p	BB104B 45p
2N3440 59p	AC151 27p	BC308A 15p	MJ481 £1.20	BY126 12p
2N3442 £1.40	AC152 49p	BC309C 20p	MJ490 £1.05	BY127 15p
2N3638 15p	AC153 35p	BC327 23p	MJ491 1.45	BYZ11 51p
2N3702 12p	AC176 30p	BC328 22p	MJ2955 £1.00	BYZ12 51p
2N3703 13p	AC187K 35p	BCY70 17p	MJE340 48p	OA47 6p
2N3704 15p	AC188K 40p	BCY71 22p	MJE370 65p	OA81 18p
2N3706 15p	AD143 68p	BCY72 15p	MJE371 75p	OA90 6p
2N3708 14p	AD161 50p	BD121 £1.00	MJE520 60p	OA91 6p
2N3714 £1.38	AD162 50p	BD123 82p	MJE521 70p	WO21A200 32p
2N3716 £1.80	AF106 40p	BD124 67p	MJE2955 £1.20	BY164 37p
2M3771 £2.20	AF109 40p	BD131 40p	MJE3055 75p	ST2diac 20p
2N3773 £2.65	AF115 35p	BD132 50p	MP8113 47p	40669 £1.00
2N3789 £2.06	AF116 35p	BD135 43p	MPP102 39p	TIC44 29p
2N3819 37p	AF117 35p	BD136 47p	MPSA05 25p	CI06D 65p
2N3820 64p	AF118 35p	BD137 55p	MPSA06 31p	ORP12 60p
2N3904 27p	AF124 30p	BD138 63p	MPSA55 31p	

Prices correct at July 1975, but all exclusive of VAT. P. & P. 25p.

# ELECTROVALUE

The best of all!

## CATALOGUE 7 ISSUE 3

with 25p refund voucher

Up-dated Price & Product Information

112 pages plus cover As comprehensive and up-to-the-minute as possible. Thousands of items from vast ranges of semi-conductors including I.C.s to components, tools, accessories, technical information and diagrams are included as well as a refund voucher worth 25p for spending on orders list value £5 or more SEND NOW FOR YOUR COPY BY RETURN 30p post it's an investment in practical money-saving and reliability!

PRICES as shown in Catalogue 7, issue 3 have remained unchanged from January to July, although our policy is to review prices at 3 monthly intervals. This is instead of making day-to-day price changes. Next price review is due Oct. 1st.

DISCOUNTS apply on all items except the few where prices are shown NETT. 5% on orders from £5 to £14.99; 10% on orders list value £15 or more.

FREE POST AND PACKING in U.K. for pre-paid mail orders over £2 (except Baxandall cabinets). If under there is an additional handling charge of 10p.

QUALITY GUARANTEE. All goods are sold on the understanding that they conform to maker's specification. No rejects, seconds or sub-standard merchandise.

## ELECTROVALUE LTD

All communications to Section 2.5, 28, ST. JUDES RD, ENGLEFIELD GREEN, EGHAM, SURREY TW20 0HB. Telephone Egham 3603, Telex 264475. Shop hours: 9-5.30 daily, 9-1 pm Sats.

NORTHERN BRANCH: 680, Burnage Lane, Burnage, Manchester M19 1NA. Telephone (061) 432 4945. Shop hours: Daily 9-5.30 pm; 9-1 pm Sats.

# YOUR CAREER in RADIO & ELECTRONICS ?

Big opportunities and big money await the qualified man in every field of Electronics today—both in the U.K. and throughout the world. We offer the finest home study training for all subjects in radio, television, etc., especially for the CITY & GUILDS EXAMS (Technicians' Certificates); the Grad. Brit. I.E.R. Exam.; the RADIO AMATEUR'S LICENCE; P.M.G. Certificates; the R.T.E.B. Servicing Certificates; etc. Also courses in Television; Transistors; Radar; Computers; Servo-mechanisms; Mathematics and Practical Transistor Radio course with equipment. We have OVER 20 YEARS' experience in teaching radio subjects and an unbroken record of exam. successes. We are the only privately run British home study College specialising in electronics subjects only. Full details will be gladly sent without any obligation.

To: British National Radio & Electronics School, Dept W.C. 85 P.O. Box 156, Jersey, C.I.

Please send FREE BROCHURE to

NAME ..... Block

ADDRESS ..... Caps.

..... Please

## BRITISH NATIONAL RADIO AND ELECTRONICS SCHOOL

# More than just a catalogue!

## PROJECTS FOR YOU TO BUILD

4-digit clock, 6-digit clock, 10W high quality power amp., High quality stereo pre-amp., Stereo Tuner, F.M. Stereo decoder, etc., etc.

CIRCUITS . . . Frequency Doublers, Oscillators, Timers, Voltmeters, Power Supplies, Amplifiers, Capacitance Multiplier, etc., etc. . . .

Full details and pictures of our wide range of components, e.g. capacitors, cases, knobs, veroboards, edge connectors, plugs and sockets, lamps and lampholders, audio leads, adaptor plugs, rotary and slide potentiometers, presets, relays, resistors (even 1% types!), switches, interlocking pushbutton switches, pot cores, transformers, cable and wire, panel meters, nuts and bolts, tools, organ components, keyboards, L.E.D.'s, 7-segment displays, heatsinks, transistors, diodes, integrated circuits, etc., etc. . . .


Really good value for money at just 40p.



## The 3600 SYNTHESISER


The 3600 synthesiser includes the most popular features of the 4600 model, but is simpler. Faster to operate, it has a switch patching system rather than the matrix patchboard of the larger unit and is particularly suitable for live performance and portable use.

Please send S.A.E. for our price list.

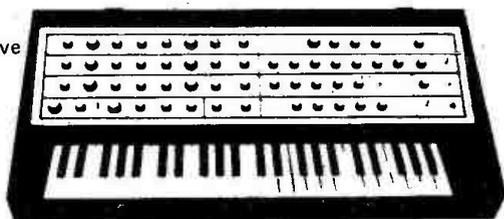

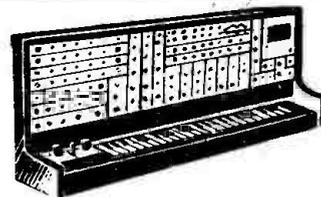
## The 4600 SYNTHESISER

We stock all the parts for this brilliantly designed synthesiser, including all the PCB's, metalwork and a drilled and printed front panel, giving a superb professional finish. Opinions of authority agree the ETI International Synthesiser is technically superior to most of today's models. Complete construction details available shortly in our booklet price £1.50, or S.A.E. please for specification


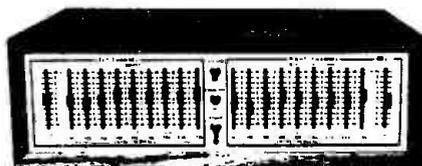
## GRAPHIC EQUALIZER

A really superior high quality stereo graphic equaliser as described in Jan. 1975 issue of ETI. We stock all parts (except woodwork) including all the metal work drilled and printed as required to suit our components and PCB's. S.A.E. for price list or complete reprint of article - price 15p.



## ELECTRONIC ORGAN

Build yourself an exciting Electronic Organ. Our leaflet MES51, price 15p, deals with the basic theory of electronic organs and describes the construction of a simple 49-note instrument with a single keyboard and a limited number of stops. Leaflet MES52, price 15p, describes the extension of the organ to two keyboards each with five voices and the extension by an octave of the organ's range. Solid-state switching and new footages along with a pedal board and a further extension of the organ's range are shown in leaflet MES53, also priced at 15p.



## NO MORE DOUBTS ABOUT PRICES

Now our prices are GUARANTEED (changes in VAT excluded) for two month periods. We'll tell you about price changes in advance for just 30p a year (refunded on purchases). If you already have our catalogue send us an s.a.e. and we'll send you our latest list of GUARANTEED prices. Send us 30p and we'll put you on our mailing list - you'll receive immediately our latest price list then every two months from the starting date shown on that list you'll receive details of our prices for the next GUARANTEED period before the prices are implemented! - plus details of any new lines, special offers, interesting projects - and coupons to spend on components to repay your 30p

NOTE: The price list is based on the Order Codes shown in our catalogue so an investment in our super catalogue is an essential first step.

Call in at our shop, 284 London Road, Westcliff-on-Sea, Essex. Please address all mail to



**MAPLIN ELECTRONIC SUPPLIES**  
P.O. Box 3 Rayleigh Essex SS6 8LR.

I enclose Cheque/P.O. value \_\_\_\_\_ PW  
For \_\_\_\_\_ copy/copies of your Catalogue  
Name \_\_\_\_\_  
Address \_\_\_\_\_

**MAPLIN ELECTRONIC SUPPLIES** P.O. Box 3 Rayleigh Essex SS6 8LR.

# 12 inch MODELS

Guaranteed for 5 years

## T12/35 Rated Power 35 WATTS

Centre Pole Diam. 1 1/2" Imp. 8-15 Ω  
Twin Cone. Range: 50-17000Hz  
Ceramic Magnet  
Weight: 600 Gms


Rec. Price **£13.00**



## T12/60 Rated Power 60 WATTS

Centre Pole Diam. 2" Imp. 8-15 Ω  
Range: 60-9000Hz  
Ceramic Magnet  
Weight 1150 Gms.


Rec. Price **£20.00**

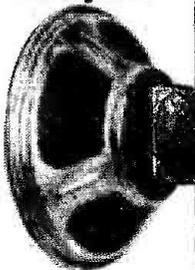

## T12/100 Rated Power 100 WATTS

Centre Pole Diam. 3" Imp 8-15 Ω  
Range: 40-5000Hz  
Ceramic Magnet  
Weight: 1250 Gms

Rec. Price **£37.00**

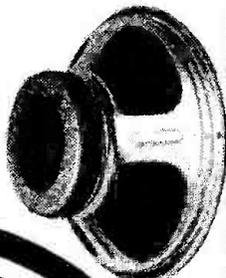

**FOR THE MUSIC INDUSTRY** **ULTRA HIGH POWER**

Power Ratings R.M.S. Continuous

All Rec. Prices inc. VAT

# 15 inch MODELS

Guaranteed for 5 years

## T15/70 Rated Power 70 WATTS

Centre Pole Diam. 2" Imp 8-15 Ω  
Ceramic Magnet  
Weight: 1150 Gms  
Range: 50-4000Hz


Rec. Price **£27.00**



## T15/100 Rated Power 100 WATTS

Centre Pole Diam. 3" Imp. 8-15 Ω  
Ceramic Magnet  
Weight: 1250 Gms.  
Range: 50-4000Hz

Rec. Price **£38.50**

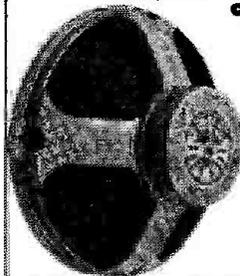


# 18 inch MODEL

## T18/100 Rated Power 100 WATTS

Centre Pole Diam. 3" Imp. 8-15 Ω  
Ceramic Magnet  
Weight: 1250 Gms.  
Range: 35-4000Hz

Rec. Price **£42.00**

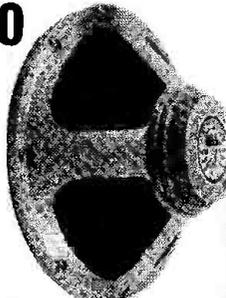

Manufacturers, Wholesale, Retail and Export enquiries to sole Distributors:-

**AUDIO EQUIPMENT LTD.**  
102 Henconner Lane, Leeds 13


S.A.E. please for trade terms or leaflet  
Prices correct at June 16, 1975

# QUALITY STEREO SOUND.

ALMOST 1/2 PRICE OFFER!

SOLENT AUDIO SYSTEM

**£5.95 down**

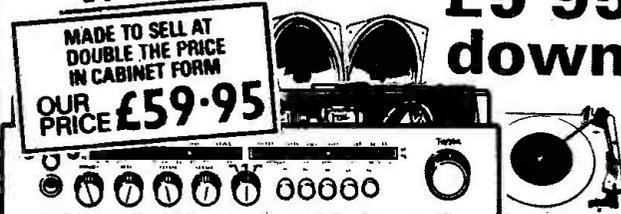

MADE TO SELL AT DOUBLE THE PRICE IN CABINET FORM  
**OUR PRICE £59.95**

\*Stereo Tuner Amplifier chassis with AM/FM radio covering long medium short and Stereo FM wavebands. Separate Base and Treble controls. 30 watts total power output (frequency response 25-20,00 Hz) Tape record and playback facilities. Dimensions 18" x 8 1/2" x 3 1/4". The very latest BSR automatic record deck with cue and pause control. Two matching elliptical speaker units.

Order early limited stocks available cash price £59.95. Credit Sale £5.95 deposit 9 monthly payments of £7.00 (Total Credit price £68.95). P. & P. £3.00. Send £8.95 today.

Chassis only available for cash at £42.00.

Full 12 months Guarantee.

CALLERS WELCOME.

Stereo headphones supplied with every complete order.

**LEWIS radio** PW/8/75 100 CHASE SIDE SOUTHGATE  
LONDON N14 5PL Telephones: 01-882-1644



# become a RADIO-AMATEUR!

learn how to become a radio-amateur in contact with the whole world. We give skilled preparation for the G.P.O. licence

**free!** Brochure, without obligation to:

**BRITISH NATIONAL RADIO & ELECTRONICS SCHOOL** Dept. WB85, P.O. Box 156, JERSEY


NAME : \_\_\_\_\_  
ADDRESS : \_\_\_\_\_

BLOCK CAPS please





I.L.P. (Electronics) Ltd

# SHEER SIMPLICITY!

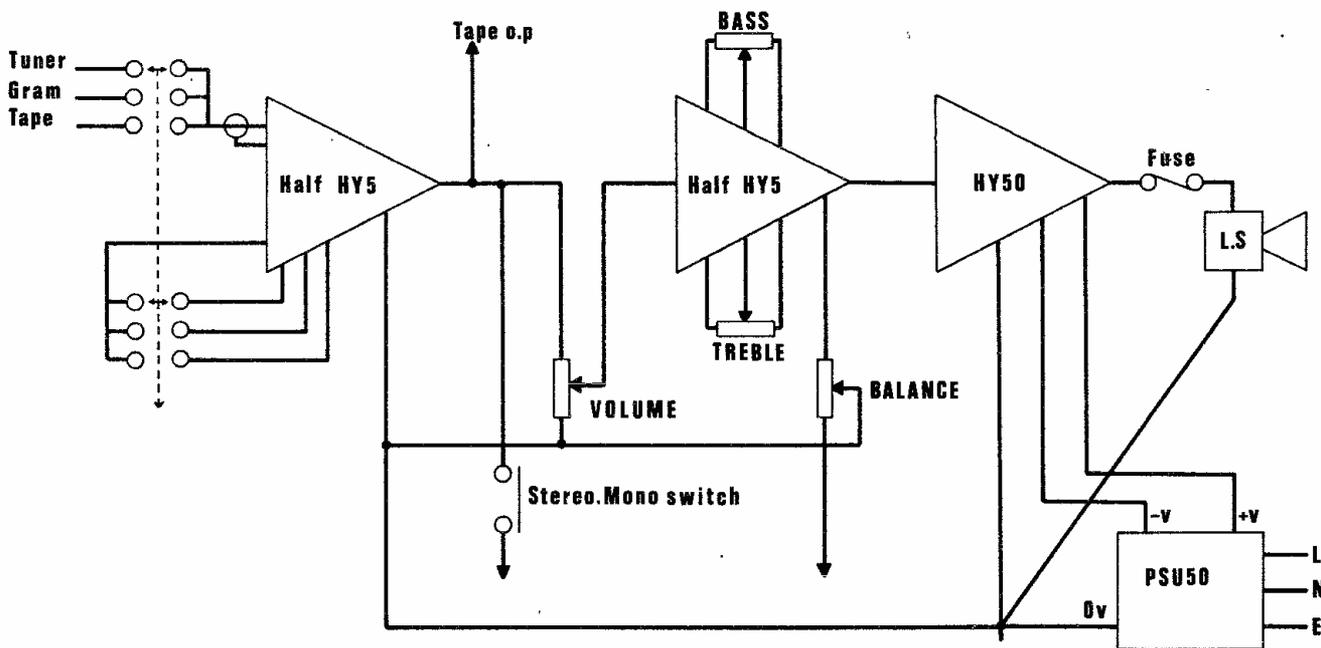

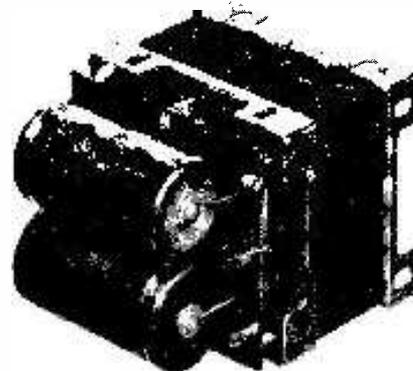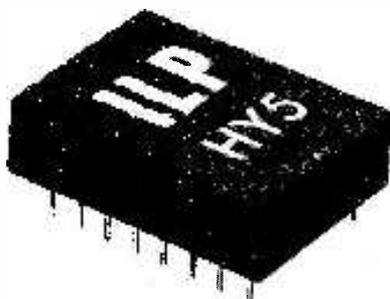MONO ELECTRICAL CIRCUIT DIAGRAM WITH INTERCONNECTIONS FOR STEREO SHOWN



The HY5 is a complete mono hybrid preamplifier, ideally suited for both mono and stereo applications. Internally the device consists of two high quality amplifiers—the first contains frequency equalisation and gain correction, while the second caters for tone control and balance.

**TECHNICAL SPECIFICATION**  
Inputs: Magnetic Pick-up 3mV RIAA; Ceramic Pick-up 30mV; Microphone 10mV; Tuner 100mV; Auxillary 3-100mV; Input Impedance 47kΩ at 1kHz. Outputs: Tape 100mV; Main output 0db (0.775V RMS). Active Tone Controls: Treble ± 12db at 10kHz; Bass ± 12db at 100Hz. Distortion: 0.5% at 1kHz. Signal/Noise Ratio: 68db. Overload Capability: 40db on most sensitive input. Supply Voltage: ± 16-25V.

**PRICE £4.50** + 36p VAT  
P. & P. free

The HY50 is a complete, solid state hybrid Hi-Fi amplifier incorporating its own high conductivity heatsink hermetically sealed in black epoxy resin. Only five connections are provided, input, output, power lines and earth.

**TECHNICAL SPECIFICATION**  
Output Power: 25W RMS into 8Ω. Load Impedance: 4-16Ω. Input Sensitivity 0db (0.775V RMS). Input Impedance: 47kΩ. Distortion: Less than 0.1% at 25W typically 0.05%. Signal/Noise Ratio: Better than 75db. Frequency Response: 10Hz-50kHz ± 3db. Supply Voltage: ± 25V. Size: 105 x 50 x 25mm.

**PRICE £5.98** + 48p VAT  
P. & P. free

The PSU50 incorporates a specially designed transformer and can be used for either mono or stereo systems.

**TECHNICAL SPECIFICATIONS**  
Output voltage: 50V (25-0-25V). Input Voltage: 210-240V. Size: L.70. D.90. H.60mm.

**PRICE £6** + 48p VAT  
P. & P. free

## TWO YEARS' GUARANTEE ON ALL OUR PRODUCTS

I.L.P. Electronics Ltd.  
Crossland House,  
Nackington, Canterbury  
Kent CT4 7AD

Tel (0227) 63218

Regd. V.A.T. No. 202141535

Please supply, .....  
Total Purchase price .....  
I Enclose, Cheque  Postal Orders  Money Order   
Please debit my Access account  Barclaycard account   
Account number .....  
Name & Address .....

Signature .....

# TRANSFORMERS

## POWER UNIT Type A126

Supplying 6, 7.5 or 9 Volt DC at 200 mA.

In moulded case forming a 2 pin 5A mains plug.

2 metre output lead with 4-way multiplex giving 2-1 and 2-5 mm sockets and 3-5 mm plugs.

Price £2.30. Post 10p.



## 2" and 4" PANEL METERS

SIZE: 60mm Wide x 45mm High x 40mm Deep. Movement I.R. Ohms

SIZE: 60mm Wide x 45mm High x 40mm Deep. Movement I.R. Ohms	SIZE: 110mm Wide x 82mm High x 43mm Deep. Movement I.R. Ohms
0-50 micro A. 1250	0-50 micro A. 1400
0-100 micro A. 580	0-100 micro A. 730
0-500 micro A. 170	0-500 micro A. 200
0-1 mA. 170	0-1 mA. 200
0-5 mA. 170	0-5 mA. 200
0-10 mA. 8	0-10 mA. 6
0-50 mA. 0.5	0-50 mA. 0.5
0-100 mA. 0.5	0-100 mA. 0.5
0-500 mA. 0.5	0-500 mA. 0.5
0-1 AMP. 0.5	0-1 AMP. 0.5
0-2 AMP. 0.5	0-2 AMP. 0.5
0-25 Volt. 15K	0-25 Volt. 15K
0-50 Volt. 30K	0-50 Volt. 30K
0-300 Volt. 300K	0-300 Volt. 300K
"k" Meter. 170	"g" Meter. 200
VU Meter. 5250	VU Meter. 5250

VU Meters are complete with detectors. Modern wide view. Price 2" £3.20 Post 10p. Price 4" £4.00 Post 10p. Lamps 60p per set.

## 1/4 watt CARBON FILM RESISTORS

1/4 watt at 70°C E 12 range 10Ω-1MΩ 5% tol above 470 KΩ 10% tol at 96p per 100.

## C1000 MULTIMETER

Special Offer Compact General Purpose Mini Multimeter. Input Resistance 1000 ohms per volt

Ranges:  
AC Volts 0-15, 50, 250, 1000 V  
DC Volts 0-10, 50, 250, 1000 V  
DC Current 0-1 mA, 0-100mA  
Resistance 0-150K ohms  
Size 80 x 24 x 90 mm  
Complete with Batteries, Test Prods, Instructions. Special price £3.80 Post 25p.



## C1001 MULTIMETER

Input Resistance 20,000 ohms per volt. Overload protection 150 μA movement, clear scale Ranges—AC Volts 0-10, 50, 250, 1000V DC Volts 0-5, 25, 125, 500, 2500V DC Current 0-50 mA Resistance 0-60 Kohms, 0-6 Mohms Decibels -20 to +22 dB. Carrying Case, Test Prods and Batteries included. Size: 11.5 x 8.3 x 2.7 cm. Price £9.85. Post 20p.

## CASED TRANSFORMERS

Housed in smart resin-coated steel cases, with 3-core power cable and outlet socket, fused primary winding. Isolation types are fitted with 3-pin outlet sockets, and are available with 110 volt or 240 volt output. (Please state). Auto types are fitted with 2-pin flat style sockets up to 500 VA. 3-pin sockets from 750 to 3000 VA. See Auto and Isolation sections for prices.

## SAFETY ISOLATING

Prim. 120/240V. Sec. 120/240V. Centre Tap with Screen.

VA	Ref. No.	Price Cased	Price Plugs 2 Pin + 1 Earth	Price Open	Post
60	149	8.35	0.88	4.37	0.56
100	150	9.15	0.88	4.90	0.64
200	151	11.45	0.88	8.14	0.80
250	152	12.90	0.88	9.80	0.88
350	153	15.50	0.88	11.88	0.95
500	154	17.25	0.88	13.82	1.13
750	155	27.10	1.10	20.59	O.A.
1000	156	35.40	1.10	29.15	O.A.
1500	157	42.00	1.10	33.37	O.A.
2000	158	49.75	0.84	37.10	O.A.
3000	159	73.15	2.84	58.55	O.A.

## 12 & 24 Volts Prim. 200-240V.

Amps	Ref. No.	Price	Post
12V	24V		
0.3	0-15	2.42	1.58 0.34
0.5	0-25	1.11	1.38 0.34
1	0.5	2.13	1.74 0.47
2	1	2.71	2.30 0.47
4	2	3.18	2.96 0.56
6	3	3.70	4.18 0.56
8	4	4.08	4.56 0.64
10	5	4.72	5.20 0.72
12	6	5.16	5.51 0.72
16	8	5.17	7.00 0.80
20	10	11.5	10.42 0.88
30	15	18.7	13.25 1.01
40	20	23.2	14.85 O.A.
60	30	22.6	16.83 O.A.

## 30 Volts

Prim. 200-240V. Amps	Ref. No.	Price	Post
0-5	112	1.90	0.47
1	79	2.40	0.56
2	3	3.50	0.56
3	20	4.50	0.64
4	21	5.15	0.72
5	51	6.40	0.72
6	117	7.16	0.88
8	88	9.55	0.95
10	89	9.67	0.95

## AUTO TRANSFORMERS

VA	Ref. No.	Price Cased	Price Plugs 2 & 3 pin	Price Open	Post
Tapped at 115, 220, 240 Volts	113	3.85	0.20	1.71	0.47
Tapped at 115, 200, 220, 240 Volts	150	4	0.38	0.20	4.12 0.56
	200	65	7.04	0.20	4.95 0.64
	300	66	8.00	0.20	5.81 0.72
	500	67	10.99	0.20	8.85 0.88
	750	83	13.32	0.85	10.80 0.95
	1000	84	17.27	0.85	13.68 1.13
	1500	93	21.87	0.85	18.31 O.A.
	2000	95	33.11	1.60	24.25 O.A.
	3000	73	47.94	2.10	35.10 O.A.

## 50 Volts

Prim. 200-240V. Sec. 19, 25, 33, 40, 50V. Amps	Ref. No.	Price	Post
0.5	102	2.58	0.47
1	103	3.48	0.56
2	104	5.03	0.64
3	105	5.81	0.72
4	106	7.58	0.88
6	107	12.30	0.95
8	118	13.20	1.13
10	119	17.02	O.A.

## 60 Volts

Prim. 230-240V. Sec. 24, 30, 40, 43, 60V. Amps	Ref. No.	Price	Post
0.5	124	2.30	0.56
1	126	3.41	0.56
2	127	5.09	0.72
3	125	7.52	0.80
4	123	8.75	0.95
5	40	9.75	0.95
6	120	11.80	1.01
8	121	15.00	1.19
10	122	18.80	O.A.
12	189	18.50	O.A.

## MINIATURE AND EQUIPMENT

Prim. 240V with screen. Sec. 1 Volts	Sec. 2	Milliamps	Ref. No.	Price	Post
3-0-3	---	200	238	1.50	0.25
0-6	0-6	500	234	1.88	0.25
0-6	0-6	1000	212	1.90	0.47
0-9-9	---	100	13	1.40	0.25
0-9-9	0-9	330	235	1.50	0.25
0-8-9	0-8-9	500	207	1.92	0.34
0-8-9	0-8-9	1000	208	2.75	0.47
15-0-15	---	40	---	2.40	1.35
0-15	0-15	200	206	2.36	1.38
20-0-20	---	30	---	2.41	1.35
0-20	0-20	150	237	1.38	0.25
0-15-20	0-15-20	500	500	2.05	0.56
0-20	0-20	300	300	2.14	1.93
0-20	---	3500	NO SCREEN	1116	3.30
20-12-0-12-20	---	700 (11/C)	---	2.21	2.20
0-15-20	0-15-20	1000	1000	2.06	3.50
0-15-27	0-15-27	500	500	2.03	3.00
0-15-27	0-15-27	1000	1000	2.04	3.85

## PLASTIC CASED SILICON BRIDGE RECTIFIERS

One Amp	Two Amp	Four Amp	Six Amp
50 P.I.V. 20p	50 P.I.V. 35p	100 P.I.V. 55p	50 P.I.V. 65p
100 P.I.V. 25p	100 P.I.V. 40p	200 P.I.V. 59p	100 P.I.V. 70p
200 P.I.V. 28p	200 P.I.V. 45p	400 P.I.V. 65p	200 P.I.V. 80p
600 P.I.V. 30p	400 P.I.V. 50p	600 P.I.V. 75p	400 P.I.V. 90p

ADD 10p P & P PER ORDER



PLEASE ADD VAT

## POWER UNIT Type CC 12-05

Output switched 3, 4.5, 6, 7.5 9 and 12 volts at 500 mA D.C. Operates from 240 V mains, suitable for Radios, Tape Recorders, Record Players etc Size 7.5 x 5.0 x 14.0cm. Price £3.95. Post 25p.



## MINIATURE NEONS

6mm dia., 12mm length leads length approx. 26mm. Recommended ballast resistor 150K ohms for 240 Volt operation Price: Packet of 10 for 60p. Postage 15p.

# A.S.P. LTD.

DEPT PW8, SIMMONDS ROAD, WINCHEAP, CANTERBURY, KENT. Tel: (0227) 52436

**SEND NOW!**  
**YOUR SINGLE SOURCE FOR THE EASY-BUILD ORGAN**

We are the only manufacturers supplying the easy-build organ complete. Full after sales advice given.

**Studio Electronics**

LTD

PO BOX 18 HARLOW CM18 6SH ESSEX

Tel: HARLOW (STD 0279) 416771

New catalogue now available on receipt of S.A.E.

## INVERTORS

240v-50Hz. from your 12v car battery.  
25 watt—£2.90 + 30p p & p.  
40 watt—£6.80 + 55p p & p.  
75 watt—£9.96 + 75p p & p.  
150 watt—£18.30 + 80p p & p.  
300 watt (12v)—£26.80 + £1.05 p & p.  
300 watt (24v)—£22.70 + £1.05 p & p  
All above invertors are in kit form but may be purchased built up & ready for use. Price list sent on receipt of stamped addressed envelope.

## P.W. AUTOMATIC EMERGENCY SUPPLY

250v-50Hz-150 watt inverter with built in battery charger. In event of power failure switches over automatically from battery charging to inverter operation. Cct. as appeared in Dec. 73 P.W. Complete kit of parts (excluding meter) £22.50 + £1.10 p & p.

## COMPLETE FLUORESCENT LIGHT INVERTOR KIT

8 watt-12v-Fluorescent light, suitable for tents, caravans, houses, boats and secondary lighting for, factories, hotels etc. 12"-8 watt £2.90 + 25p p & p. 21"-13 watt. £3.30 + 30p p & p.

## TRANSFORMERS & COILS

Both high volume & small order capacity available for Mains, R.F., & I.F. Transformers. Before you buy elsewhere let us quote you and see what you save.

V.A.T. at 8% included.

TRADE & EXPORT ENQUIRIES WELCOMED

ASTRO ELECTRONICS, 10A SPRINGBANK RD., CHESTERFIELD, DERBYSHIRE

# BI-PRE-PAK

Bargains in Semi-Conductors, components, modules & equipment.

## Bargains from our FREE Catalogue

20 large pages, filled with real bargains in transistors, I.Cs, components, equipment, etc. Send large S.A.E. with 6p stamp for your FREE copy of 6th Edition by return. Meanwhile, for prompt delivery order from this month's ad. NOW.

### TRANSISTOR PACKS ALL AT 50p EACH TESTED & GUARANTEED

<b>B79</b>	<b>4</b>	IN4007 Sil. Rec. diodes. 1,000PIV 1 amp. plastic	<b>H39</b>	<b>6</b>	Integrated circuits 4 gates BMC 962. 2 flip flops BMC945
<b>B81</b>	<b>10</b>	Reed Switches. 1 long 1/2" dia. High-speed P.O. type	<b>H41</b>	<b>2</b>	BD131/BD132 Complementary Plastic Transistors. 40361 Type NPN Sil. Transistors TO-5 can comp. to H66
<b>H35</b>	<b>100</b>	Mixed Diodes. Germ. Gold bonded, etc. Marked and Unmarked.	<b>H65</b>	<b>4</b>	40362. Type PNP Sil. Transistors TO-5 can comp. to H65
<b>H38</b>	<b>30</b>	Short lead, NPN Silicon Planar Ex Equipment.			

### UNMARKED & UNTESTED

<b>B1</b>	<b>50</b>	Germanium Transistors PNP, AF and RF	<b>H6</b>	<b>40</b>	250mV zener diodes. At least 20 good.
<b>B66</b>	<b>150</b>	Germanium Diodes Min. glass type	<b>H15</b>	<b>30</b>	Silicon rectifiers 750mA assorted. Top-hat type.
<b>H68</b>	<b>10</b>	Experimenter's pack of I.Cs, D.T.L. and T.T.L. (some marked)	<b>H34</b>	<b>15</b>	Power Transistors, PNP, Germ. NPN Silicon TO-3 Can
<b>B86</b>	<b>100</b>	Sil. Diodes sub. min. IN914 and IN916 types	<b>H67</b>	<b>10</b>	3819N Channel FET's plastic case type

### PLASTIC POWER TRANSISTORS

40 WATT SILICON					
Type	Polarity	Gain	VCE	Price	
40N1	NPN	15	15	20p	
40N2	NPN	40	40	30p	
40P1	PNP	15	15	20p	
40P2	PNP	40	40	30p	

90 WATT SILICON					
Type	Polarity	Gain	VCE	Price	
90N1	NPN	15	15	25p	
90N2	NPN	40	40	35p	
90P1	PNP	15	15	25p	
90P2	PNP	40	40	35p	

### NEW X-HATCH GENERATOR Mk. 2



Essential for Colour T.V. alignment of 4 patterns. Featuring plug in IC's and a more sensitive sync. pick-up circuit. The case is virtually unbreakable—ideal for the engineer's toolbox—only measures 3" x 5 1/2" x 3". Operates from 3 U.2 type batteries (extra).

P/P add Complete kit **£7-93\*** Ready built unit only **£9-93\***

### TO CLEAR

Hundreds of various portable transistor radio chassis with FM & AM tuning. Ideal for experimenters. All electronic components in good order, but no instructions or tuning drives. A cheap way to make a portable. Each £1

### SUNDRY

Capacitor Discharge Ignition Kit **£7-50** (8). 8 assorted relays **£1-00** (8). Rev counter device (for cars) **£1-00**. U.H.F./TV Tuner Units **£2-50**. LM.389 Audio I.C. **£1-00**. Technical books of all kinds (no VAT).

### TERMS OF BUSINESS

V.A.T. Prices shown do not include V.A.T. This must be added to total value of your order including postage at 25% except for prices marked \* or (8%) when only 8% V.A.T. is required. No V.A.T. on overseas orders.

POSTAGE Except where stated, add 20p for postage & packing in U.K. Overseas—add £1, any difference being charged or refunded.

PAYMENT Cash with order, Cheque or money order. Minimum order value £1. You can also pay by ACCESS.

IMPORTANT—Every effort is made to ensure accuracy of prices and description at time of preparing this advertisement and going to press. Prices are subject to alteration without notice.

## BI-PRE-PAK LTD

Co Reg No A270109

222 224 WEST ROAD, WESTCLIFF-ON-SEA, ESSEX SSO 9DF.

TELEPHONE: SOUTHEND (0702) 46344.

WRITE ORDER SEPARATELY AND ATTACH COUPON IF REQUIRED



challenging values!

## Stirling Sound

STIRLING SOUND AUDIO MODULES come to you as basic units assembled on P.C.Bs enabling you to add required components in layouts of your own choice. Modules are tested and boxed before despatched and include well printed instructions.

### PRE-AMP TONE CONTROLS

Pre-amplifiers; tone control

<b>SS.100</b>	Active tone control unit to provide bass, treble, balance and volume controls	<b>£1-60</b>
<b>SS.101</b>	Pre-amp for ceramic cartridge, tape and radio	<b>£1-60</b>
<b>SS.102</b>	Pre-amp for low output magnetic cartridge, tape and radio. With R.I.A.A. correction $\pm 1\text{dB}$ at 1K	<b>£2-25</b>

### POWER AMPLIFIERS

<b>SS.103</b>	Compact I.C. amp. with 3 watts R.M.S. output. Operating voltage 10-20v. Size 3 1/2" x 2"	<b>£1-75</b>
<b>SS.103-3</b>	Stereo version of above using one I.C. on each channel	<b>£3-25</b>
<b>SS.105 MK2</b>	New improved all-purpose power amp which will run excellently on a 12V supply. With 5 watt output, two make a good stereo amp. Size 3 1/2" x 2"	<b>£2-25</b>
<b>SS.110 MK2</b>	Similar in size to SS.103 but with a 10 watt output. Ideal for many domestic and small-size P.A. applications. Operates from 26 to 32V.	<b>£2-75</b>
<b>SS.140</b>	Excellent designed 40 watt R.M.S. (into 4 ohms) hi-fi amplifier. S/N ratio better than 75dB. THD better than 0.2%. Power requirements—45V. d.c. With 0.15" centre edge connections. Two can be bridged to give 80 watts R.M.S. into 8 ohms	<b>£3-60</b>

### BUILD A STEREO FM TUNER!

<b>SS.201</b>	Ganged tuning condenser with accurately engineered slow-motion drive in rugged housing. Excellent sensitivity. Tunes 88-108MHz. With A.F.C. facility. Operates from 6-16V	<b>£6-25</b>
<b>SS.202</b>	I.F. stage (with I.C.) Pre-tuned. A.F.C. connection. Operates from 4.5 to 14V	<b>£5-25</b>
<b>SS.203</b>	Stereo Decoder. Designed essentially for use with SS.201 and 2, this module can also be used in most mono FM tuners. A LED may be attached. Operating voltage 9-16V. d.c.	<b>£5-62</b>

### SPECIAL £5 MONEY SAVING OFFER

Buy all three modules for building a stereo FM Tuner (Total list £17-21) and you pay only **£12-12**

### POWER SUPPLY STABILIZER

<b>SS.300</b>	Add this to an unregulated supply (say typically 45V output) to obtain a steady powerful working output adjustable from 12 to 60V. Essential on your audio and special systems as well as test bench. Money saving and very reliable	<b>£3-25</b>
---------------	--	--------------

### MAINS TRANSFORMERS FOR ABOVE

Add 35p per transformer for P/P	
Type A 18V/1A (Suit SS.103)	<b>£1-50</b>
Type B 25V/2A (Suit SS.110)	<b>£2-00</b>
Type C 30V/2A (Suit SS.140)	<b>£4-50</b>
Bridge Rectifiers—Type A 27p. Types B & C 38p	

Founded 1959

To BI-PRE-PAK, 224-226 WEST RD., WESTCLIFF-ON-SEA, ESSEX

Please send .....

for which I enclose ..... inc. V.A.T.

Name .....

Address .....

PW 8

# RTVC\*

**NEW!**

## VISCOUNT IV STEREO SYSTEM

System 1a. £65.00

The new 20+20 watt Stereo Amplifier incorporating the latest silicon transistor solid state circuitry, the RT-VC VISCOUNT IV gives you a powerful 20 watts RMS per channel into 8 ohms. Superb teak-finished cabinet, with anodised fascia to harmonise with any decor. Polished trim and knobs.

The VISCOUNT IV has a comprehensive range of controls — volume, bass, treble, balance, mono/stereo, mode selector, and scratch filter.

Front panel socket for stereo headphones. And a host of sockets at the rear — for left and right speakers, tape recorder, auxiliary, tuner, disc and microphone.

**SPECIFICATION:** 20 watts RMS per channel 40 watts peak. Suitable 8-15 ohms speakers. Total distortion @ 10 watts better than 0.2%. Six switched inputs: 1. Magnetic P.U. — 3 millivolts @ 47 K ohms (R.I.A.A.); 2. Crystal/ceramic P.U. — 50 millivolts @ 50 K ohms (R.I.A.A.); 3, 4, 6. Tape Tuner/Aux. — 140 millivolts @ 50 K ohms (flat frequency response); 5. Microphone — 3 millivolts @ 50 K ohms (flat frequency response).

**CONTROLS:** Push button ON/OFF, stereo/mono, scratch filter, 6 position rotary selector. Individual rotary controls for treble, bass, balance and volume. Headphone socket, tape out socket. Aux. mains output. Frequency response: 25 Hz to 25 KHz @ full rated output. Signal to noise ratio: better than -50 dB on all inputs. Tone control range: Bass ±15 dB @ 50 Hz; Treble ±12 dB @ 10 KHz. Power requirements: 200-250V A.C. mains @ 60 watts. Approx. size: 15¼" × 3" × 10".

MP60 type deck with magnetic cartridge, de luxe plinth and cover.

Two Duo Type Ila matched speakers — Enclosure size approx. 19½" × 10½" × 7½" in simulated teak. Drive unit 13" × 8" with 3" tweeter. 15 watts handling, 30 watts peak.

Complete System with these speakers £69.00 +£6.50 p & p.

### System 2. £81.00

Viscount IV amplifier (As System 1a)  
MP60 type deck (As System 1a)

Two Duo Type III matched speakers

— Enclosure size approx. 27" × 13" × 11½". Finished in teak simulate. Drive units 13" × 8" bass driver, and two 3" (approx.) tweeters. 20 watts RMS. 8 ohms frequency range — 20 Hz to 18,000 Hz.

Complete System with these speakers £85.00 +£7.60 p & p.

#### PRICES: SYSTEM 1a

Viscount IV R103 amplifier £25.00 +£1.90 p & p.

2 Duo Type Ila speakers £30.00 +£6.50 p & p.

MP60 type deck with Mag. cartridge de luxe plinth and cover £20.00 +£3.30 p & p.

Total if purchased separately: £75.00

Available complete for only: £65.00 +£6.50 p & p.

#### PRICES: SYSTEM 2

Viscount IV R103 amplifier £25.00 +£1.90 p & p.

2 Duo Type III speakers £46.00 +£7.50 p & p.

MP60 type deck with Mag. cartridge de luxe plinth and cover £20.00 +£3.30 p & p.


Total if purchased separately: £91.00

Available complete for only: £81.00 +£7.60 p & p.



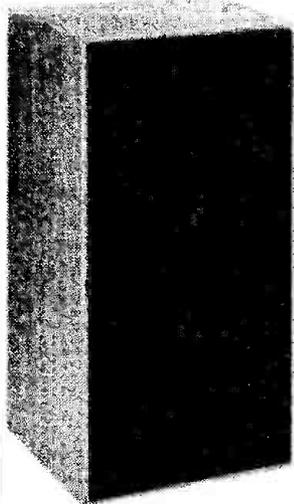**20x20 SYSTEM**

Scotland P & P Surcharge  
System 1a £1.75 System 2 £3.50



## EMI SPEAKERS AT FANTASTIC REDUCTIONS

### LE-4 SPEAKERS

Superb performance and beautifully finished in selected teak veneers. A professional standard four-way speaker system giving 25 watts RMS power handling. Bass unit is 14" × 9" with 8" × 5" unit for mid-range and twin 3" high frequency units to give monitor type quality and performance.

**Specification** — Size 33" × 14" × 16" approx. Impedance 8 ohms. Power handling 25W RMS. (Peak 50 watts.) Frequency range 35 Hz—20 KHz.

**Our Price £34.00**


(normally £66.00) +£5.80 p & p.

### EASY TO BUILD SPEAKER KITS

These superb simulated teak-finished speaker kits have been specially designed by RT-VC for the cost-conscious hi-fi enthusiast who wants top quality speakers but doesn't want to spend the earth. Built to EMI's exacting specification, these new RT-VC speaker kits (350 type kit) incorporate 13" × 8" woofer, 3½" tweeter and matching crossover.

Easily put together with just a few basic tools.

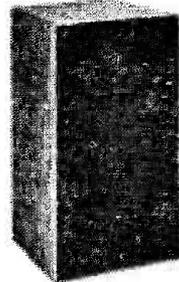**Specification (each speaker):** Impedance 8 ohms. Power handling 15 watts RMS (30 watts peak). Response 20—20,000 Hz. Size 20" × 11" × 9½" approx. Comparable built units (EMI LE3) sold elsewhere for over £45 pair.



**£22.00 pair complete**

+£5.20 p & p. Complete with crossover Components and circuit diagram



### EMI 350 KIT

System consists of a 13" × 8" approx. woofer with a 3" tweeter, crossover components and circuit diagram. Frequency response: 20 Hz to 20 KHz. Power handling 15 watts RMS into 8 ohms. (Peak 30 watts.)


**£6.50** +£1.20 p & p.

Complete with crossover Components and circuit diagram

## DECCA STEREO AMPLIFIER CHASSIS

**Specification:** 4+4 watts into 8 ohms. Input Sensitivity 4mV into 47K (for magnetic cartridges). AC Mains only 240V. Controls — volume, bass, treble, on/off, mono/stereo switch. Chassis size 11" × 5½" × 3¼" approx.

**£6.90** +£1.20 p & p.

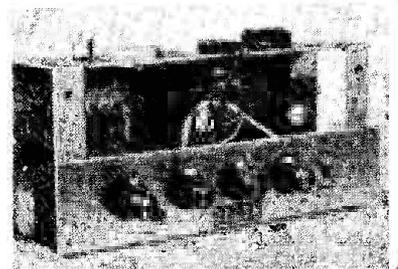

# PUSH BUTTON CAR RADIO KIT— THE TOURIST TT\*



## NOW BUILD YOUR OWN PUSH BUTTON CAR RADIO

Easy to assemble construction kit comprising fully completed and tested printed circuit board on which no soldering is required. All connections are simple push fit type making for easy assembly. Fine tuning push button mechanism is fully built and tested to mate with printed circuit board.

**TECHNICAL SPECIFICATION:** (1) Output 4 watts RMS output. For 12 volt operation on negative or positive earth. (2) Integrated circuit output stage, pre-built three stage IF Module.

Controls volume manual tuning and five push buttons for station selection, illuminated tuning scale covering full, medium and long wave bands. Size chassis 7" wide 2" high and 4 3/4" deep approx. **£9.50** +£1.05 p & p. Speaker including baffle and fixing strip **£2.00** +45p p & p. Car Aerial Recommended — fully retractable **£1.60** +40p p & p.

The Tourist I Kit For the experienced constructor. If you can solder on a printed circuit board you can build this model. Same technical specification as Tourist TT. **Price £8.20** +£1.05 p & p.

**NO SOLDERING REQUIRED**

# \*STEREO 21 QUALITY SOUND FOR LESS THAN £24.00



Stereo 21, easy to assemble audio system kit. No soldering required.

The unit is finished in white P.V.C. and the acrylic top presents an unusually interesting variation on the modern deck plinth.

Includes — BSR 3 speed deck, automatic, manual facilities together with stereo cartridge.

Two speakers with cabinets. Amplifier module. Ready built with control panel, speaker leads and full, easy to follow assembly instructions.


**Specifications** — For the technically minded: Input sensitivity 600mV. Aux. input sensitivity 120mV. Power output 2.7 watts per channel. Output impedance 8—15 ohms. Stereo headphone socket with automatic speaker cutout. Provision for auxiliary inputs — radio, tape, etc., and outputs for taping discs.

**Overall Dimensions.** Speakers approx 15 1/2" x 8" x 4". Complete deck and cover in closed position approx. 15 1/2" x 12" x 6".

**Complete only £23.20** +£3.00 p & p.

Extras if required. Optional Diamond Stylus **£1.60**. Specially selected pair of stereo headphones with individual level controls and padded earpieces to give optimum performance **£5.80**.

# \*DISCO AMPLIFIER

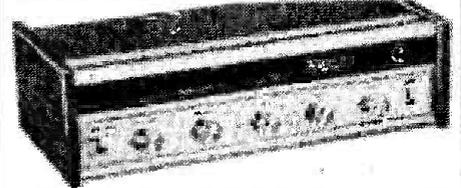

Reliant Mk IV Mono Amplifier, ideal for the small disco or house parties. Output 20 watts RMS into 8 ohms (suitable for 15 ohms).

Inputs \* 4 electrically mixed inputs. \* 3 individual mixing controls. \* Separate bass and treble controls common to all 4 inputs. \* Mixer employing F.E.T. (Field Effect Transistors). \* Solid State circuitry. \* Attractive styling.


**INPUT SENSITIVITIES** — Input — 1). Crystal mic. guitar or moving coil mic, 2 and 10mV. (Selector switch for desired sensitivity.) — Inputs — 2), 3), 4). Medium output equipment — ceramic cartridge, tuner, tape recorder, organs, etc. — all 250mV sensitivity. AC Mains. 240V operation. Size approx: 12 1/2" x 6" x 3 1/2". **£20.00** +£1.35 p & p.

# \*8 TRACK HOME CARTRIDGE PLAYER



Elegant self selector push button player for use with your stereo system. Compatible with Viscount IV system, Unisound module and the Stereo 21. Technical specification Mains input, 240V. Output sensitivity 125mV. Comparable unit sold elsewhere at **£24.00** approx. Yours for only

**£16.20** +£1.70 p & p.

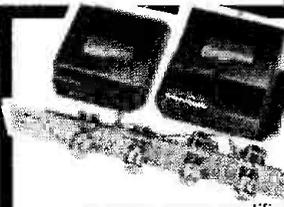


# BUILD YOUR OWN \*STEREO AMPLIFIER

For the man who wants to design his own stereo — here's your chance to start, with Unisound — pre-amp, power amplifier and control panel. No soldering — just simply screw together. 4 watts per channel into 8 ohms. Inputs: 120mV (for ceramic cartridge). The heart of Unisound is high efficiency I.C. monolithic power chips which ensure very low distortion over the audio spectrum. 240V. AC only.

Also available with 2 speakers (7" x 4") **£10** +£1.75 p & p. **£8.95** +£1.05 p & p.
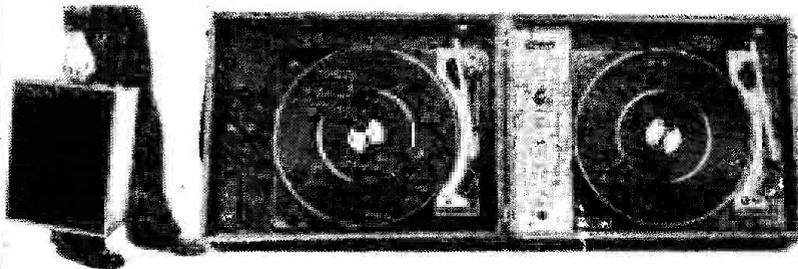
# PORTABLE DISCO CONSOLE\*

**INCORPORATES:** Pre-Amp with full mixing facilities, including switched input for mic with volume control, switched input for auxiliary with volume control, bass and treble controls, Volume control and blend control for turntables. Two B.S.R. MP60 type single play professional series decks, fitted with crystal cartridges.



**TECHNICAL SPECIFICATION:**  
Pre-amp — Output — 200mV.  
Auxiliary inputs — 200mV and 750mV into 1 meg. Mic input — 6mV into 100K. 240 volt operation.  
Turntables capacity — 7", 10" or 12" records. Rumble, wow and flutter Rumble Better than —35dB. Wow Better than 0.2%. Flutter Better than 0.06% (Gaugmont kalee meter).  
**Finish** — Satin black mainplate with black turntable mat inlaid with brushed aluminium trim. Tonearm and controls in black and brushed aluminium.

**Console size** —  
Unit Closed — 17 3/4" x 13 3/4" x 8 1/4" (app.)  
Unit Open — 35 3/4" x 13 3/4" x 4 1/4" (app.)  
This disco console is ideally matched for the Reliant IV and Disco 50 or any other quality amplifier.  
The unit is finished in black PVC with contrasting simulated teak edging, diamond spun control knobs with matching control panel.

**Yours for only £57.00** +£6.50 p & p.



**DO NOT SEND CARD**  
Just write your order giving your credit card number

Mail orders to Acton. Terms C.W.D. All enquiries stamped addressed envelope. Goods not despatched outside U.K.

Leaflets available for all items listed thus \* Send stamped addressed envelope. All items subject to availability. Prices correct at 1st June 1975 and subject to change without notice.  
**All prices include V.A.T. at 25% rate.**



21C HIGH STREET, ACTON, LONDON W3 6NG  
323 EDWARE ROAD, LONDON W2

Personal Shoppers EDWARE RD: 9 a.m.—5.30p.m. Half day Thurs.  
ACTON: 9.30a.m.—5p.m. Closed all day Wed.

# TRAMPUS

**Electronics Ltd.**

WINDSOR, BERKS  
58/60 GROVE RD;  
SEND C.V.O. ADD VAT TO ALL PRICES IN U.K. P&P 15p. EXPORTS 80p

MONEY BACK IF NOT SATISFIED.  
LARGE STOCKS. LOW PRICES.  
ALL BRAND NEW TOP GRADE FULL  
SPEC. DEVICES. CALLERS WELCOME.  
CATALOGUE/LIST FREE SEND SAE  
BARCLAYCARD & ACCESS A POST.  
COPPER CLAD VEROBORD 0.1"

## Digital Displays



SLA7 RED LED 0.3"  
DIGIT 0-9DP 89p ea  
GREEN&YELLOW £1.40  
JUMBO LED 0.6" 747  
DISPLAY £2.25 ea.  
3015F 0-9DP £1 ea.  
ZENON FLASH TUBE  
£4. Data 15p.

## LEDS red 13p

LEDS 209 STYLE ONLY 13p ea  
TIL 209 WITH CLIP RED 15p ea  
TIL 211 & CLIP GREEN 29p ea  
LARGE 0.2" & CLIP RED 17p ea  
LARGE 0.2" CLIP GREEN 30p ea  
209 STYLE OR .2"ORANGE 29p ea  
INFRA RED LED £1.2N5777 33p.

## PHOTO IC 81p

TEC12 PHOTO AMP/SCMITT/RELAY  
DRIVER or LED TTL INTERFACE 81p



FLUORESCENT LIGHTS 12V MADE IN UK  
8 WATT 13" £3. 13W 22" £3.50

## DIGITAL CLOCK

IC AY51224 4 DIGIT CLOCK £3.75  
MM5311/4 6 DIGIT CLOCK £7

## CASSETTE mechanics £13.75

NEW 8tk CARTRIDGE MECHANISM £8  
STEREO CASSETTE MECHANISM £13.75  
Suitable for 'PW ASCOT' recorder  
with heads etc. SEND 15p for DATA

## INTEGRATED CIRCUITS

709 DIL14	29p	LM377 2x2Wt2.87
555 TIMER	54p	LM380 2W AF 89p
703 RF/IF	28p	LM381 2xPre £2
709 T099	23p	LM3900 4xOPA69p
709 DIL 14	28p	MC1303 £1.20
710 DIL 14	34p	MC1306 49p
723 Reg.	54p	MC1310&LEDr2.65
741 DIL 8	27p	MC1312 SQ £2.10
741 DIL 14	29p	MC1330 69p
741 T099	29p	MC1339 2xPre £1
747 2x741	70p	MC1350 55p
748 DIL 8	33p	NE536 fetOPA £2
7805 5V	£1.40	NE540 Driver £1
7812 & 15	£1.40	NE550 2xRef 79p
76013 6W AF	£1	NE555 Timer 55p
8038 SIG GEN	£3	NE556 2x" £1.20
CA3028	£1	NE560 PLL £3.15
CA3046	55p	NE561 PLL £3.15
CA3048	£2	NE562 PLL £3.19
CA3052	£1.50	NE565 PLL £2.69
CA3054	£1	SN72709 709 28p
LM300 2-20V	£2	SN72741 741 26p
LM301 OPA	45p	SN72748 748 33p
LM304 0-40V	£3	SN76660 IF £1
LM307 OPA	49p	SN76611 IF£1.25
LM308 HiRo	95p	TAD110 & IF £2
LM309K 5V	£1.48	TBA810 7WAF 99p
LM372 IF	£1.80	ZN414 RX £1.09

### SPECIAL OFFERS

2N3055 FULL HIGH SPEC 115W 37p  
741C SPIN DIL 27p. MFC4000B 33p  
NE555 TIMER 55p. ZN414 RX £1.09  
BC109 9p. 2N3819e 16p. BFY51 15p



## 7400 TTL

7400 GATES	13p	7473/74/76	29p
7404 INVERT	17p	7475	45p
7401/2/10etc	14p	7490	52p
7413 SCMITT	31p	7491/2/3/4	59p
7440 BUFFER	14p	74100 74175	£1
7447 DRIVER	89p	74121	32p
7470 & 7472	29p	74123	59p
		74141(&7441)73p	

## TRANSISTORS & DIODES

Price each		MATCHING	16p
AC127 & 128	16p	INS. BUSH SET	10p
AC187 & 188	19p	TIP 41	70p
AD149	43p	TIP 42	88p
AD161 & 162	33p	TIP 2955	90p
BC107 & 108	9p	TIP 3055	55p
BC109	10p	TIS43 <del>see 2N2646</del>	
BC147/8/9	10p	2TX109&301	13p
BC157/8/9	12p	1N4001	4p
BC167/8/9	12p	1N4004 & 7	7p
BC177/8/9	18p	1N4148 & 914	4p
BC182/3/4A&L10p		2N697	14p
BC212/3/4A&L11p		2N706&8	11p
BCY70/1/2	17p	2N2646 UJT	32p
BD131 & 132	39p	2N2904 & 5	20p
BFR51		2N2926royg	9p
BFR50/51	23p	2N3053	17p
BFR50/51	23p	2N3055 115W	37p
BFR88 250V	29p	2N3563 & 64	16p
BFY50/1/2	15p	2N3614	49p
BSX19/20/21	16p	2N3702 & 3	9p
MJE2955	90p	2N3704 & 5	10p
MJE3055	65p	2N3706 & 7	9p
MPU131 PUT	49p	2N3708 & 9	8p
OA91 OA81	6p	2N3710 & 11	10p
OA81 & OA91	6p	2N3819E FET	16p
TIP 29 & 30	52p	2N3823E FET	17p
TIP 31 & 32	69p	2N3904/5/6	15p

FULL SELECTION IN OUR FREE LISTS.

### NEW TRAMPUS FULL SPEC PAKS

PAK A	10 RED LEDS our choice	£1
PAK B	4 741 OP AMP "	£1
PAK C	4 2N3055 £1.D 12 BC109	£1
PAK E	10 BC182 £1.F 11 2N3704	£1
PAK G	8 BFY51 £1.H 9 2N3819e	£1
PAK J	9 2N3053 £1.K 40 1N914	£1

BZY88 400mW	1A/50V SCR	36p
ZENER DIODES 9p	TAG1/400	55p
	C106 & 7 SCR D1	
BRIDGE RECT	4A/400V	53p
1A 50V	SC146D TRIAC	
BR100 DIAC 25p	10A 400V	75p

## vero

VERO PINSx36 28p.  
COPPER CLAD VEROBORD 0.1"  
2 1/2"x5" 29p 2 1/2"x3 1/2" 26p. 3 1/2"x3 1/2" 31p.  
3 1/2"x5" 31p 3 1/2"x 17" £1.50

DIL IC'S BOARDS 6x4 1/2" £1.50  
24 way edge connector 60p.  
36 way 90p. PLAIN 3 1/2"x17" £1.  
FACE CUTTER 45p. FEC ETCH PAK 50p

## DALOpen69p

PRINTED CIRCUIT BOARD KIT £1.69  
DECON NO MESS ETCH PAK NEW 69p  
DECON DESOLDER BRAID REEL 59p

## HEATSINKS

5F/T05 & 18F/T018 5p ea. TV4 15p.  
TV3/T03 16p. EXTRUDED 4" 4Y1 29p.  
TGS308 GAS DETECTOR £1.80 ea.  
LOGIC PROBE TTL TESTER PEN £5

## CAPACITORS

CERAMIC 22pf to 0.1uf 50v 5p.  
ELECTROLYTIC: 10/50/100 uf in  
10v 5p. 25v 6p. 50v 8p. 2uf/10v 5p.  
1000 uf/25v 18p. 200/500 25v 9p.

## POTENTIOMETERS (POTS) AB or EGIN


LN or LOG ROTARY 13p. SWITCH 14p  
DUAL 45p. SLIDERS 29p. STEREO 57p  
KNOBS 7p. PRESETS 6p. RESISTORS 14p  
SWITCHES: SPST 18p. DPDT 25p

DIN PLUGS ALL 12p. SOCKETS 10p.  
ALI CASES AB5/AB7 50p. AB13 65p.  
TRANSFORMERS 1A 6v6v or 12v12v  
Only £1.34. 100mA type CT 75p.

## OIL sockets

TEXAS GOLD ea  
LOW PROFILE ea  
8, 14, & 16 PIN 13p  
SOLDERCON STRIPS-  
100 PINS 50p. 1K £3.

# LOWE ELECTRONICS

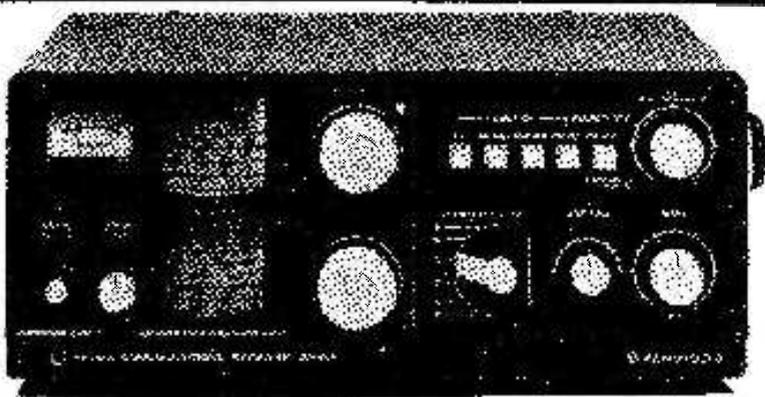

## TRIO QR666

**SPECIFICATION 170-410**  
Frequency coverage 170-410kHz, 525-1250kHz, 1.25-3.0MHz,  
3-7.5MHz, 7.5-18MHz, 18-30MHz (Dual conversion)  
Bandspread 3-5.4MHz, 7-7.5MHz, 14-14.6MHz, 21-21.5MHz  
(Dual conversion), 28-30MHz (Dual conversion)  
Modes AM, USB, LSB, CW  
Selectivity 2 position wide/narrow  
Antenna 50-100Ω  
Sensitivity 1µV for 10dB SIN (SSB/CW)  
AF Output More than 1.5W into 8Ω. Internal speaker fitted  
Power supply 100/117/220/240V ac 50/60Hz, External 12V dc.  
Internal 12V batteries, Automatic changeover to  
internal supply in the event of mains failure  
Dimensions (mm) 362 wide x 163 high x 322 deep  
Weight 7.3kg (16.09 lbs)  
Options 500kHz marker QR6MK, FM broadcast tuner  
QR6FM

An all new receiver from the TRIO company providing general coverage reception 170kHz to 30MHz with calibrated bandspread for the amateur bands. Dual-gate MOSFETS for RF and mixer stages ensure high gain, good selectivity and first class A.G.C. characteristics.

Dual position selectivity gives two bandwidths to cater for all band conditions.

Use the QR666 at home, in the car or boat or truly portable; all catered for by the exclusive 3-way power supply. **PRICE £130 (VAT excl)**

We stock a great many products apart from those advertised month by month—everything in fact for the radio amateur operator. If you need more information, our complete catalogues are available free to callers. If you require them sending by mail, postal charges being what they are today, please send us 20p in stamps because that's what it costs to send them to you!

**HEAD OFFICE** 119 Cavendish Road, Matlock, Derbyshire. Tel. 2817 or 2430 9 a.m. to 9 p.m.

**BRANCH OFFICES** Goring Road, Steyning, Sussex. Tel. Steyning 814466  
Soho House, 362-4 Soho Road, Handsworth, Birmingham. Tel. 021-554 0708

**AGENTS** Alan GW3YSA, 35 Pen-Y-Waun, Efail Isaf, Nr. Pontypridd. Tel. Newton Llantwit 3809  
John G3JYG, 16 Harvard Road, Ringmer, Lewes, Sussex. Tel. Ringmer 812071  
Sim GM3SAN, 19 Ellismuir Road, Baillieston, Nr. Glasgow. Tel. 041-771 0364

**OPENING HOURS: 9-5.30 TUESDAY TO SATURDAY INCLUSIVE**


**73 from BILL G3UBO/VE8DP, ALAN G3MME, JOHN G3PCY/5N2AAC, IAN G3ZYC**

## SUPERSOUND 13 HI-FI MONO AMPLIFIER



A superb solid state audio amplifier. Brand new components throughout. 6 silicon transistors plus 2 power output transistors in push-pull. Full wave rectification. Output approx. 13 watts r.m.s. into 8 ohms. Frequency response 12Hz 30KHz  $\pm$  3db. Fully integrated pre-amplifier stage with separate Volume, Bass boost and Treble cut controls. Suitable for 8-15 ohm speakers. Input for ceramic or crystal cartridge. Sensitivity approx. 40mV for full output. Supplied ready built and tested, with knobs, escutcheon panel, input and output plugs. Overall size 3" high  $\times$  6" wide  $\times$  7 1/2" deep. AC 200/250V. PRICE £15-00. P. & P. 65p.

## DE LUXE STEREO AMPLIFIER

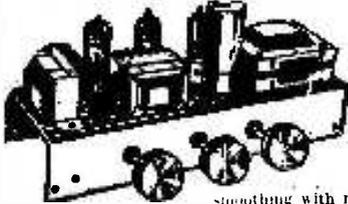

A.C. mains 200-240 v. Using heavy duty fully isolated mains transformer with full wave rectification giving adequate smoothing with negligible hum.

Value line output: 2 ECL86 Triode Pentodes, 1  $\times$  EZ80 as rectifier. Two dual potentiometers are provided for bass and treble control, giving bass and treble boost and cut. A dual volume control is used. Balance of the left and right hand channels can be adjusted by means of a separate 'Balance' control fitted at the rear of the chassis. Input sensitivity is approximately 300mV for full peak output of 4 watts per channel (8 watts mono), into 8 ohm speakers. Full negative feedback in a carefully calculated circuit, allows high volume levels to be used with negligible distortion. Supplied complete with knobs, chassis size 11" w  $\times$  4" d. Overall height including valves 5". Ready built & tested to a high standard. £12-50. P.&P. 85p.

**ALL-PURPOSE POWER SUPPLY UNIT** 200/240v. A.C. Input. Four switched fully smoothed D.C. outputs giving 6v. and 7.5v. and 9v. and 12v. at 1 amp on lead. Fitted insulated output terminals and pilot lamp indicator. Hammer finish metal case overall size 6"  $\times$  3 1/2"  $\times$  2 1/2". Ready built and tested. PRICE £5-35 P. & P. 55p.

**VYNAIR & REXINE SPEAKERS & CABINET FABRICS** app. 54 in. wide. Our price £1.30 yd. length. P. & P. 30p per yd. (min. 1 yd.). S.A.E. for samples.

### HARVERSON'S SUPER MONO AMPLIFIER

A super quality gram amplifier using a double wound fully isolated mains transformer, rectifier and ECL82 triode pentode valve as audio amplifier and power output stage. Impedance 3 ohms. Output approx. 3-5 watts. Volume and tone controls. Chassis size only 7in. wide  $\times$  3in. deep  $\times$  6in. high overall. AC mains 200/240v. Supplied absolutely Brand New completely wired and tested with good quality output transformer. P. & P. 60p BARGAIN PRICE £5-00

### FEW ONLY!

High grade mains transformer with grain orientated lamination. Primary 200/240 Secondary 18-5 volts at 0-6 amps and 4-6 volts at 0-3 amps. Size 2"  $\times$  1 1/2" w  $\times$  2" d overall. £1-40 plus 35p P. & P.

**BRAND NEW MULTI-RATIO MAINS TRANSFORMERS.** Giving 13 alternatives. Primary: 0-210-240v. Secondary combinations 0-5-10-15-20-25-30-35-40-60v. half wave at 1 amp. or 10-0-10, 20-0-20, 30-0-30v. at 2 amps full wave. Size 3in. long  $\times$  3 1/2in. wide  $\times$  3in. deep. Price £2-75 P. & P. 65p.

**MAINS TRANSFORMER.** For power supplies. Pri. 200/240v. Sec. 9-0-9 at 500 mA. £1-35. P. & P. 30p. Pri. 200/240v. Sec. 12-0-12 at 1 amp. £1-50. P. & P. 30p. Pri. 200/240v. Sec. 10-0-10 at 2 amp. £2-20. P. & P. 40p.

### 3 VOLT RELAY

100 mA single pole normally closed. 2 for 60p + 15p P. & P.

### GENERAL PURPOSE HIGH STABILITY TRANSISTOR PRE-AMPLIFIER

For P.U. Tape, Mike, Guitar, etc. and suitable for use with valve or transistor equipment. 9-18v. battery or from H.T. line 200/300v. Frequency response 15Hz-25KHz. Gain 26dB. Solid encapsulation size 1 1/2"  $\times$  1 1/2"  $\times$  1/2". Brand new complete with instructions. Price 1-36p. P. & P. 15p.

### HANDBOOK OF TRANSISTOR EQUIVALENTS AND SUBSTITUTES

A must for servicemen and home constructors. Including many 1000's of British, U.S.A. European and Japanese transistors. ONLY 40p. Post 7p.

8 Reference Encyclopedias for Electronic Engineers and Designers, covering between them transistor characteristics, diode and transistor equivalents. Many thousands of up to date European types listed. Diode Equivalents, £1-00; Transistor Equivalents, £1-20; Transistor Characteristics, £1-40; POST FREE All three together, £3-20

### NEW ISSUE

Thyristor, Triac, Diac etc. encyclopedias £1-70, Post Free 8 pole 3 way 2 bank low loss Yaxley type switches 1 1/2" sections. Standard spindle. 2 switches 75p - 15p P. & P.

Open 9.30-5.30 Monday to Friday. 9.30-5 Saturday Closed Wednesday.

All prices and specifications correct at time of press and subject to alteration without notice.

## HARVERSONIC MAINS OPERATED SOLID STATE STEREO FM TUNER



Enjoy fabulous stereo radio at this fabulous low introductory price!

Designed and styled to match our 10 + 10 amplifier but will suit any other standard stereo amplifier. The design incorporates the very latest circuitry techniques with high-grain, low noise IF stages. Automatic frequency control to "lock-on" station and prevent drift. I.C. stereo decoder for maximum stereo separation. L.E.D. for stereo beacon indicator. Nominal output of tuner 100mV. Approximate size 12 1/2" wide  $\times$  8" deep by 2 1/2" high. Supplied ready built, fully tested and fully guaranteed (not available in kit form). Price £27-50 Post and Packing £1-00.

### STEREO-DECODER

SIZE 2"  $\times$  3"  $\times$  1/2" ready built. Pre-aligned and tested. Sens. 20-560 mV for 9-16V neg. earth operation. Can be fitted to almost any FM VHF radio or tuner. Stereo beacon light can be fitted if required. Full details and instructions (inclusive of hints and tips) supplied. £6-25 plus 15p. P. & P. Stereo beacon light if required 45p extra.



### SPECIAL BARGAIN OFFER!

Limited number of BSR C123 Auto Changer De Luxe with lightweight tubular arm and stereo cartridge. Brand new. ONLY £9-50 + p. & p. 80p.

**LATEST HI Sensitivity Uni-directional slim-line condenser microphone** as used by many professionals. Very low acoustic feedback. Available hi impedance or low impedance. State which required. £16-25 plus 25p P. & P.

**LATEST ACOS GP91/15C mono compatible cartridge** with T/O stylus for LP/EP/78. Universal mounting bracket. £1-75. P. & P. 15p.

**CERAMIC STEREO CARTRIDGE.** Universal Mounting brackets and turnover stylus. 70mV per channel output. ONLY £2-06 + 15p P. & P.

**SONOTONE STARC COMPATIBLE STEREO CARTRIDGE** T/O stylus Diamond Stereo LP and Sapphire 78. ONLY £2-62 P. & P. 10p. Also available fitted with twin Diamond T/O stylus for Stereo LP. £3-18. P. & P. 15p.

**LATEST BONETTE T/O STEREO / COMPATIBLE CARTRIDGE** for EP/LP/Stereo/78. £1-88 P. & P. 15p.

**LATEST T/O MONO COMPATIBLE CARTRIDGE** for playing EP/LP/78 mono or stereo records on mono equipment. Only £1-75. P. & P. 15p.

**QUALITY RECORD PLAYER AMPLIFIER MK. II** A top quality record player amplifier employing heavy duty double wound mains transformer, ECC83, EL84, and rectifier. Separate Bass, Treble and Volume controls. Complete with output transformer matched for 3 ohm speaker. Size 7in. wide  $\times$  3in. deep  $\times$  6in. high. Ready built and tested. PRICE £6-50, P. & P. 75p.

ALSO AVAILABLE mounted on board with output transformer and speaker. PRICE £7-75. P. & P. 75p.

### HI-FI LOUDSPEAKER SYSTEM MK II

Beautifully made, simulated teak finish enclosure with attractive slatted front. Size 16 1/2" high  $\times$  10 1/2" wide  $\times$  9" deep (approx.). Fitted with E.M.I. Ceramic Magnet 13"  $\times$  8" bass unit, H.F. tweeter unit and crossover. AVAILABLE IN NOMINAL 4 Ohm, 8 Ohm or 16 Ohm impedance (state which).

**OUR PRICE £11-25** each Carr. £1-25.

Cabinet Available Separately £6-25, Carr. £1-10. Also available in 8 ohms with EMI 13"  $\times$  8" bass speaker with parasitic tweeter £10-00, Carr. £1-25.

### LOUDSPEAKER BARGAINS

5in. 3 ohm £1-45, P. & P. 15p. 7  $\times$  4in. 3 ohm £1-60, P. & P. 25p. 10  $\times$  6in. 3 or 15 ohm £2-50, P. & P. 35p. E.M.I. 8  $\times$  5in. 3 ohm with high flux magnet £2-06, P. & P. 25p. E.M.I. 13 1/2  $\times$  8in. with high flux ceramic magnet with parasitic tweeter 3, 8 or 15 ohm £4-12, P. & P. 35p. E.M.I. 18  $\times$  8in. 3, 8 or 15 ohm with inbuilt tweeter and crossover network £5-50, P. & P. 35p. E.M.I. tweeter. Approx. 3 1/2". Available 3 or 8 or 15 ohms, £2-00 + 25p. P. & P.


**BRAND NEW Bakers Loudspeakers** at substantial discounts. 12in. 15w. H/D Speakers, 3, 8 or 15 ohms. State which. Current production by well-known British maker. Now with Hifix ceramic ferrobar magnet assembly £9-50. Guitar models: 25w £9-50, 35w £11-50, P. & P. 75p.

### "POLY PLANAR" WAFER-TYPE, WIDE RANGE ELECTRO-DYNAMIC SPEAKER

Size 11 1/2"  $\times$  14 1/2"  $\times$  1 1/2" deep. Weight 19oz. Power handling 20W r.m.s. (40W peak). Impedance 8 ohm only. Response 40Hz-20KHz. Can be mounted on ceilings, walls, doors, under tables, etc., and used with or without baffle. Send S.A.E. for full details. Only £7-68 each. P. & P. 60p.

**NOW ALSO AVAILABLE:** 8", 10 watts, r.m.s. 20 watt peak 40Hz-20,000Hz. Overall depth 1". Ideal for Hi-Fi or for use in cars. £5-18 + 40p P. and P.
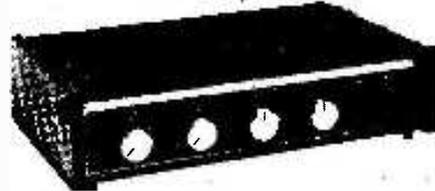
## HARVERSONIC SUPER SOUND 10 + 10 STEREO AMPLIFIER KIT



A really first-class Hi-Fi Stereo Amplifier Kit. Uses 14 transistors including Silicon Transistors in the first five stages on each channel resulting in even lower noise, level with improved sensitivity. Integrated pre-amp with Bass, Treble and two Volume Controls. Suitable for use with Ceramic or Crystal cartridges. Very simple to modify to suit magnetic cartridge—instructions included. Output stage for any speakers from 8 to 16 ohms. Compact design, all parts supplied including drilled metalwork high quality ready drilled printed circuit board with component identification clearly marked, smart brushed anodised aluminium front panel with matching knobs, wire, solder, nuts, bolts—no extras to buy. Simple step by step instructions enable any constructor to build an amplifier to be proud of. Brief specification; Power output: 14 watts r.m.s. per channel into 5 ohms. Frequency response  $\pm$  3dB 12-30,000 Hz Sensitivity: better than 80mV into 1M $\Omega$ . Full power bandwidth:  $\pm$  3dB 12-15,000 Hz. Bass boost approx. to  $\pm$  12dB. Treble cut approx. to -16dB. Negative feedback 18dB over main amp. Power requirements 35v. at 1-0 amp. Overall Size 12" w.  $\times$  8" d.  $\times$  2 1/2" h.

Fully detailed 7 page construction manual and parts list free with kit or send 25p plus large S.A.E.

**AMPLIFIER KIT** £15-00 P. & P. 50p (Magnetic input components 33p extra)

**POWER PACK KIT** £5-35 P. & P. 55p  
**CABINET** £5-35 P. & P. 55p

(Post Free if all units purchased at same time)

Full after sales service

Also available ready built and tested £32-50. Post Free.

Note: The above amplifier is suitable for feeding two mono sources into inputs (e.g. mike, radio, twin record decks, etc.) and will then provide mixing and fading facilities for medium powered Hi-Fi Discotheque use, etc.




### 3-VALVE AUDIO AMPLIFIER HA34 MK II

Designed for Hi-Fi reproduction of records. A.C. Mains operation. Ready built on plated heavy gauge metal chassis, size 7 1/2" w.  $\times$  4" d.  $\times$  4 1/2" h. Incorporates ECC83, EL84, E280 valves. Heavy duty double wound mains transformer and output transformer matched for 3 ohm speaker. Separate volume control and now with improved wide range tone controls giving bass and treble lift and cut. Negative feedback line. Output 4 1/2 watts. Front panel can be detached and leads extended for remote mounting of controls. Complete with knobs, valves, etc., wired and tested for only £7-75. P. & P. 70p.

**HSL "FOUR" AMPLIFIER KIT.** Similar in appearance to HA34 above but employs entirely different and advanced circuitry. Complete set of parts, etc £8-50 P. & P. 70p.
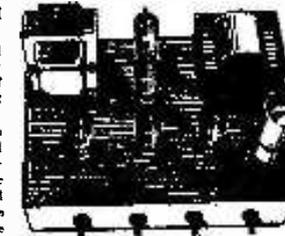
### 10/14 WATT HI-FI AMPLIFIER KIT

A stylishly finished monaural amplifier with an output of 14 watts from 2 EL84s in push-pull Super reproduction of both music and speech, with negligible hum. Separate inputs for mike and gram allow records and announcements to follow each other. Fully shrouded section wound output transformer to match 8-15  $\Omega$  speaker and 2 independent volume controls, and separate bass and treble controls are provided giving good lift and cut. Valve line-up 2 EL84s, ECC83, EF86 and E280 rectifier. Simple instruction booklet 25p + SAE (Free with parts) All parts sold separately. ONLY £12-00 P. & P. £1-00. Also available ready built and tested £18-50 P. & P. £1-00.



### HI-FI STEREO HEADPHONES

Adjustable headband with comfortable flexifoam ear-muffs. Wired and fitted with standard stereo  $\phi$ in jack plug. Frequency response 30-15,000Hz. Matching impedance 8-16 ohms. Easily converted for Mono. PRICE £4-05, P. & P. 25p.

**PRICES INCLUDE VAT @ 25%**

(Please write clearly)

PLEASE NOTE: P. & P. CHARGES QUOTED APPLY TO U.K. ONLY. P. & P. ON OVERSEAS ORDERS CHARGED EXTRA.

## HARVERSON SURPLUS CO. LTD.

(Dept. P.W.) 170 HIGH ST., MERTON, LONDON, S.W.19 Tel.: 01-540 3985

A few minutes from South Wimbledon Tube Station.

SEND STAMPED ADDRESSED ENVELOPE WITH ALL ENQUIRIES

# Don't miss your copy of HENRY'S NEW 1975 CATALOGUE

only  
50p  
Plus 15p  
P&P



- ★ OVER 5,000 ITEMS – largest UK range of electronic components for home constructors.
- ★ 200 PAGES – every aspect of electronics and components for amateurs and hobbyists – kits, projects, test gear.
- ★ DOZENS of new lines and new ranges.
- ★ MANY price reductions throughout the new Catalogue.
- ★ A Discount Voucher with every copy, worth 50p.

**FREE** TO EDUCATIONAL ESTABLISHMENTS when ordered on official notepaper.

Write now for your copy, enclosing 65p remittance.

Now Open Supermarket,  
Browse Round The New  
Supermarket at 404 Edgware  
Road.  
**ALL PRICES INCLUSIVE OF VAT**

# HENRY'S

Electronic Centres  
404-406 Electronic Components & Equipment 01-402 8381  
309 PA-Disco. Lighting High Power Sound 01-723 6963  
303 Special offers and bargains store  
All mail to 303 Edgware Road, London W2 1BW

Hi Fi and  
Electronics  
Centres Open  
9 am - 6 pm

Prices correct at time of preparation. Subject to change without notice. E & O E

## ELECTRONIC FOOTBALL & TENNIS WITH THE FABULOUS VIDEO SPORT

### ON YOUR OWN TV

Play three exciting electronic ball games. FOOTBALL, TENNIS, HOLE IN THE WALL on your own TV! Just plug Video Sport into the aerial socket of your TV and away you go. Completely safe for you, your children and your TV. Mains operated.



OUR INCREDIBLE PRICE **£35.00**  
DEMONSTRATIONS NOW IN  
ALL HI, FI CENTRES!

## NEW SPECIAL PURCHASE

Mullard type LP1179 and LP1171  
AM/FM tuner modules  
These two modules together form a high quality AM/FM tuner covering the long, medium and VHF broadcast bands. Requires only 16 resistors and capacitors and a switch to complete. Supplied with circuits and spec. data.

**LP1179**  
FM Coverage 87-108 MHz  
Bandwidth 300 KHz  
Audio output 75mV  
with built in tuning gang

**LP1171**  
AM Coverage mW-1W  
Supply 6V negative earth  
LP1179 and LP1171 **£4.60** each or **£8.63** pr.  
Suitable Ferrite aerial **£4.60** ea. or **£8.63** pr.



## UHF TV TUNERS

625 line receiver UHF transistorised tuners UK operation.  
Brand new. (Post/packing 25p each).  
TYPE A var. tun. slow motion drive **£3.50**.  
TYPE C variable tuning **£2.90**.  
TYPE B 4-button push button (adj.) **£4.60**.  
TYPE D 6-button UHF/VHF tuner **£5.15**.

You can build the Texan and Stereo FM Tuner  
TEXAN 20 - 20 WATT IC STEREO AMPLIFIERS

Features glass fibre PC board, Gardners low field transformer 6-IC's, 10-transistors plus diodes etc. Designed by Texas instruments engineers for Henry's and P.W.1972. Overall size 15 1/2" x 22" x 6 1/2" mains operated. Free teak sleeve with every kit. **£38.75** (CARRIAGE 50p).  
(also built and tested £46.87).



## HENELEC STEREO FM TUNER

Features capacity diode tuning, lead and tuning meter indicators, mains operated. High performance and sensitivity.  
Overall size in teak sleeve 8" x 22" x 6 1/2". Complete kit with teak sleeve. **£26.25** (Carriage 50p).  
(also built and tested £31.20).

JOIN THE LARGE BAND OF  
CONSTRUCTORS!

**FREE:**  
SEND NOW FOR OUR  
FREE LIST NO. 36 FOR  
OUR COMPLETE RANGE  
OF OVER 10,000 SEMI-  
CONDUCTOR DEVICES  
AT NEW LOW PRICES.




## EXTRA DISCOUNTS

Semiconductors—Any one type or mixed  
SN74 Series 'IC' 12-extra 10%; 25-extra  
15%; 100-extra 20%.

## TRANSISTORS & INTEGRATED I/C's

TTL "7400-series" IC's from 18p each  
Cosmos "4000-series" IC's from 28p each  
Linear Op-Amps from 43p each  
Signetics Phase Lock IC's; RCA Linear  
IC's; TO3 Power Devices in PNP and NPN;  
BC107 and "BC range" from 13p each  
Range of OC Types 20p  
Plastic Power Devices, Rectifiers, Zener,  
Power Regulator IC's and many others.  
Diodes up to 10 watts.

# VEROBOARD

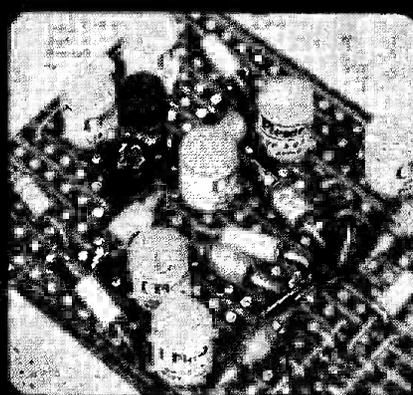

VEROBOARDS GIVE A PROFESSIONAL  
FINISH TO YOUR WORK

0.1" and 0.15" pitch, plain and copper  
clad universal circuit boards.  
AVAILABLE FROM YOUR LOCAL RETAILER

TRADE DISTRIBUTOR: N. Rose Electrical Ltd., London W.C.1



VERO ELECTRONICS LTD.  
Industrial Estate, Chandler's Ford,  
SO5 3ZR Tel: Chandler's Ford 2552

# GREENBANK ELECTRONICS

Tel:—051-645 3391

## FREE!

Data and circuit diagram for Digital Clock Chip AY-5-1224, Digital Alarm Clock Chip MK 50253, also data sheet for DL-704/707 and DL-750/747 LED displays. (A stamped addressed envelope with enquiries would be a great help to us, but is not essential.)

## CLOCK CHIPS (Add 8% VAT)

AY-5-1224, 4 digit, 12/24 hr., 50/60 Hz, TTL compatible, zero reset, easy display interface, 16 pin DIL package: **£3.66**  
MK 50253, 4/6 digit alarm clock chip, 50 Hz, 12/24 hr., AM/PM and activity indication, 'snooze' feature, intensity control, simple time setting, 28 pin DIL package: **£5.50**

## LED DISPLAYS (Add 8% VAT)

DL-704E 0-3" LED 7 Seg. Display C. Cathode: **85p**  
DL-707E 0-3" LED 7 Seg. Display C. Anode: **£1.70**  
DL-750 0-6" LED 7 Seg. Display C. Cathode: **£2.25**  
DL-747E 0-6" LED 7 Seg. Display C. Anode: **£2.04**

## CLOCK KITS (Add 8% VAT)

SOK/1 Many parts for 4 x 0-6" LED Clock: **£14.95**  
SOK/2 Many parts for 4 x 0-3" LED Alarm Clock: **£13.50**  
Add VAT to all prices. (If in doubt, ask for a quotation or send 25% VAT and we will refund any excess.) Post etc. 10p + 8% VAT per order.

# GREENBANK ELECTRONICS

(Dept. W8P), 94 New Chester Road,  
New Ferry, Wirral, Merseyside. L62 5AG

# CENTURION

## INSTRUMENT

## CASES



Model Nos. 119 and 121 two part aluminium construction base front and back unit finished in white gloss, hooded cover finished in blue hammer stove enamel.

Model	D	W	H	Price
119	152mm	127mm	89mm	£1.80 ea
121	152mm	203mm	76mm	£2.25 ea

Model Nos. 221F and 222F flat packs. Front & Rear panels aluminium case mild steel front panel finished in white gloss other parts finished in blue hammer stove enamel.

221F	152mm	203mm	152mm	£3.05 ea
222F	197mm	254mm	159mm	£3.65 ea

Model No 321F flat pack front panel aluminium, rear panel and case mild steel, front panel finished in white gloss other parts finished black, textured finish supplied with aluminium top and bottom trim.

321F	203mm	406mm	165mm	£6.20 ea
------	-------	-------	-------	----------

Prices include P & P U.K.

Add 8% V.A.T. U.K. only.

Send S.A.E. for full range brochure.

Manufactured by

## Arbour Electronics Limited

Unit 13 East Hanningfield Ind. Est  
Nr. Chelmsford, Essex CM3 5BG  
Tel. Chelmsford (0245) 400700.

Sheet metal work wiring assembly service available.



# ALL OUR PRICES INCLUDE V.A.T.

## BSR HI-FI AUTOCHANGER

### STEREO AND MONO

Plays 12", 10" or 7" records Auto or Manual. A high quality unit backed by BSR reliability with 12 months' guarantee. AC 200/250v. Size 13 1/2" x 11 1/2". Above motor board 8 1/2". Below motor board 2 1/2". With STEREO/MONO CARTRIDGE



£9.25 Post 45p.

## PORTABLE PLAYER CABINET

Modern design. Size 16" x 15" x 7" roxine covered. Large front grille. Hinged Lid. Chrome fittings. Motor board out for Garrard deck. Post 45p. Few only, in red and black.

£5.25

## SOLID MAHOGANY PLINTH

With P.V.O. Cover. Cut out for most B.S.R. or Garrard decks. Size 12 1/2" x 14 1/2" x 7 1/2".

£7.50



Post 45p

## BSR JUNIOR SINGLE PLAYER

Heavy duty 4-speed motor with separate pick-up arm fitted LP/78 turnover mono compatible cartridge.

£5.25

Post 45p

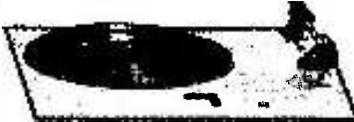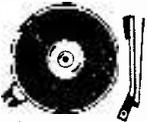

## R.C.S. DISCO DECK SINGLE RECORD PLAYER

Fitted with auto stop, stereo/compat. cartridge. Base-plate. Size 11 1/2" x 8 1/2". Turntable. Size 7 1/2" diameter. A/C mains. 220/250V motor has a separate winding 14 volt to power a small amplifier. 3 speeds plays all records.

£6.95

Post 45p

## COMPLETE STEREO SYSTEM

Two full size loudspeakers 13 1/2" x 10" x 3 1/2". Player unit clips to loudspeakers making it extremely compact. Overall size only 13 1/2" x 10" x 3 1/2". 3 watts per channel, plays all records 33 rpm 45 rpm. Separate volume & tone controls 240v AC mains



Attractive Teak finish Weight 13lbs.

Bargain Price £29

85p carriage

## SPECIAL OFFER! SMITH'S CLOCKWORK 15 AMP TIME SWITCH 0-60 MINUTES

Single pole two-way surface mounting with fixing screws. Will replace existing wall switch to give light for return home, garage, automatic anti-burglar lights etc. Variable knob Turn on or off at full or intermediate settings. Fully insulated. Makers last list price £4.50. Brand new and fully guaranteed. OUR PRICE £2.50 Post 35p.



CASSETTE RECORDER MOTOR ONLY. 6 Volt. Will replace many types. Ideal for models. £1.25.

BLANK ALUMINIUM CHASSIS. 18 s.w.g. 2 1/2" sides 6 x 4 1/2" 45p; 8 x 6 1/2" 55p; 10 x 7 1/2" 65p; 12 x 8 1/2" 85p; 14 x 9 1/2" 90p; 16 x 10 1/2" 90p; 18 x 11 1/2" 100p; 20 x 12 1/2" 105p.

ALUMINIUM PANELS 18 s.w.g. 6 x 4 1/2" 12p; 8 x 6 1/2" 14p; 10 x 7 1/2" 16p; 12 x 8 1/2" 18p; 14 x 9 1/2" 20p; 16 x 10 1/2" 22p; 18 x 11 1/2" 24p; 20 x 12 1/2" 26p.

1 1/2" DIAMETER WAVECHANGE SWITCHES 45p. EA. 2 p. 2-way, or 2 p. 6-way, or 3 p. 4-way, 1 p. 1 2-way, or 4 p. 2-way, or 4 p. 3-way.

TOGGLE SWITCHES, sp. 20p; dp. 25p; dp. dt. 30p.

## R.C.S. GENERAL PURPOSE TRANSISTOR PRE-AMPLIFIER BRITISH MADE

Ideal for Mike, Tape P.U., Guitar, etc. Can be used with Battery 9-12v. or H.T. Line 200-300V. D.C. operation. Size 1 1/2" x 1 1/2" x 1". Response 25 c.p.s. to 25 Kc/s, 26 db gain. For use with valve or transistor equipment. £1.45 Post Full instructions supplied. Details S.A.E. 20p

### NEW TUBULAR ELECTROLYTICS

			CAN TYPES
2/350V	14p	250/25V	14p
4/350V	14p	500/25V	20p
8/350V	18p	100+100/275v	65p
16/350V	22p	150+200/275v	70p
32/500V	50p	8+8/450V	22p
25/25V	10p	8+16/450V	25p
50/50V	10p	16+16/450V	40p
100/25V	10p	32+32/850V	40p
			4700/68V
			95p

### LOW VOLTAGE ELECTROLYTICS.

22, 25, 50, 68, 150, 470, 500, 680, 1500, 2200, 3300, mfd all 6 volt 10p. ea.  
22, 25, 68, 100, 150, 200, 220, 330, 470, 680, 1000, 1500, 2200, mfd all 10 volt 10p. ea.  
220, 330, 1000, 4700, mfd all 4v. 10p. ea.  
1. 2. 4. 5. 8. 16. 25. 30. 50. 100. 200mF 15V 10p.  
500mF 12V 15p; 25V 20p; 50V 30p.  
1000mF 12V 20p; 25V 35p; 50V 47p; 100V 70p.  
2000mF 4V 25p; 25V 42p; 50V 57p; 4700/68V 95p.  
2500mF 50V 62p; 3000mF 25V 47p; 50V 65p.  
5000mF 6V 25p; 12V 42p; 25V 75p; 35V 85p; 50V 95p.  
500V-0-001 to 0-05 4p; 0-1 10p; 0-25 12p; 0-47 25p.  
CERAMIC 1pF to 0-01mF, 4p. Silver Mica 2 to 5000pF, 4p.  
PAPER 350V-0-1 7p; 0-5 15p; 1mF or 2mF 150V 15p.  
MICRO SWITCH single pole changeover 20p  
MICRO SWITCH sub min 25p  
TWIN GANG. "0-0" 208pF +176pF. £1.10.  
Slow motion drive 365pF + 365pF with 25pF + 25pF, 50p;  
500pF standard twin gang 75p. 120 PF twin gang 50p.

ELAC 9 x 5in. HI-FI SPEAKER. TYPE 59RM. THIS FAMOUS AND WIDELY USED UNIT NOW AVAILABLE AT BARGAIN PRICE 10 WATT, 8 OHM. CERAMIC MAGNET. £3.45

NEON PANEL INDICATORS. 250V AC/DC Amber, 30p RESISTORS. 1 w., 1/2 w., 20%, 1p; 2 w. 5p. 10 Ohm to 10M. HIGH STABILITY. 1/2 w. 2% 10 ohms to 6 meg., 10p. Dhto 5%. Preferred values 10 ohms to 10 meg., 4p. WIRE-WOUND RESISTORS. 5 watt, 10 watt, 15 watt, 10 ohms to 100k, 10p each; 2w 0-5 ohm to 8-2 ohms 10p. TAPE OSCILLATOR COIL. Valve type, 35p. FERRITE ROD 8" x 1/2" 20p; 6" x 1/2" 20p; 3" x 1/2" 10p.

## MAINS TRANSFORMERS ALL POST 40p EACH

250-0-250V 50MA. 6-3.2A £2.95.  
250-0-250 80 mA. 6.3 v. 3.5 A. 6.3 v. 1 A. or 5 v. 2 A. £4.60  
250-0-350 80 mA. 6.3 v. 3.5 A. 6.3 v. 1 A. or 5 v. 2 A. £5.80  
300-0-300 v. 120 mA. 6.3 v. 4 A. C.T. 6.3 v. 2 A. £7.00  
MINIATURE 200 v. 20 mA. 6.3 v. 1 A. 2 1/2 x 2 1/2 x 2 1/2. 95p  
MIDGET 220 v. 45 mA. 6.3 v. 2 A. 2 1/2 x 2 1/2 x 2 1/2. £1.20  
HEATER TRANS. 6.3 v. 3 amp. £1.45 1 amp. 95p  
GENERAL PURPOSE LOW VOLTAGE. Tapped outputs at 2 amp., 3, 4, 5, 6, 8, 9, 10, 12, 15, 18, 24 and 30 v. £4.60  
1 amp., 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60 £4.60  
2 amp., 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60 £7.00  
3 amp., 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60 £8.70  
5 amp., 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60 £11.25  
5, 8, 10, 16 v. 1 A £2.6-0-6 v. 500 mA 90p. 9 v. 1 amp. 95p.  
12 v. 300 mA 75p. 12 v. 500 mA 85p. 12 v. 750 mA 95p.  
40 v. 2 amp. tapped 10 v. or 30 v. £2.50. 20V 3 amp. £2.40V 3 A. £2.50. 22V 4 A. £3.  
AUTO TRANSFORMERS. 115v to 230v or 230v to 115v. 150w. £4.60; 500w. £8.70; 750w. £17.50; 1000w. £21.00.  
CHARGER TRANSFORMERS. Input 200/250v. for 6 or 15v. 1 1/2 amp. £1.50; 2 amp. £1.80; 4 amp. £3.  
BATTERY CHARGERS. Ready built with leads and clips 4 amp. £4.5; 5 amp. £4.50.  
FULL WAVE BRIDGE CHARGER RECTIFIERS: 6 or 12v. outputs. 1 1/2 amp. 40p; 2 amp. 65p; 4 amp. 85p.

## MAINS ISOLATING TRANSFORMER

Primary 0-110-240v. Secondary 0-240v. 3 amps. 720 watts. Insulated terminals. Varnish impregnated. Fully enclosed in steel case with fixing test. Famous make. (Value £19) OUR PRICE £13.50 Carr. 85p Suitable for outside use.

## R.C.S. 3 WAY CROSSOVER

Complete with 12 ft. twin lead fitted with din speaker plug. Ready assembled with leads for speakers, bass, mid and tweeter. Crossover frequencies—950 cps and 3,000 cps. £2.20

## VOLUME CONTROLS 80 Ohm Coax 5p yd.

5 K. ohms to 2 Meg. LOG or LIN. L/S 20p. D.P. 35p. STEREO L/S 55p. D.P. 75p. Edge 5K. S.P. Transistor 25p  
BRITISH AERIALITE AERAXIAL-AIR SPACED 40 yd. £2; 60 yd. £3.  
FRINGE LOW LOSS 10p per yd Ideal 625 and colour.

Wirewound controls 1 1/2 in. diam. 3 watts. 10 ohms to 100K British made with long spindles 1/2 in. dia 80p ea.

DUAL CONCENTRIC POT 500k LOG + 500k LIN D.P. switch. Inner spindle 3 1/2 in; outer spindle 2 1/2 in. 75p.

## E.M.I. 13 1/2 x 8 in. SPEAKER SALE!

With tweeter. £5.25  
And crossover. 10 watt. State 3 or 8 or 15 ohm. As illustrated. Post 35p



With flared tweeter cone and ceramic magnet. 10 watt. Bass res. 45-60 cps. Flux 10,000 gauss. State 3 or 8 or 15 ohm. Post 35p

£3.45

## Bookshelf Cabinet

Fluted wood front 16 x 10 x 7 1/2 in. Teak Veneer Post 45p

£6.60

## GOODMANS 6 1/2 in. HI-FI SPEAKER

8 ohm, 10 watt. Large ceramic magnet Special Rubber cone surround. Frequency response 30-15,000 cps. Ideal P.A. Columns, HI-FI Enclosure Systems, etc. Suitable cabinet 12 x 8 x 6 1/2 in. Suitable Tweeter £2.30.

£4.60



## ELAC CONE TWEETER

The moving coil diaphragm gives a good radiation pattern to the higher frequencies and a smooth extension of total response from 1,000 cps to 18,000 cps. Size 5 1/2 x 3 1/2 x 2 1/2 in. deep. Rating 10 watt, 8 ohm. Crossover £1.90 Post 20p

£2.25



## GOODMANS 8 in. WOOFER

8 ohm 12 watt. Deep cone. Heavy ceramic magnet. Bass resonance 35 cps. Frequency response 30-3,000 cps. Ideal bass unit for Hi-Fi systems

£4.35



LOUDSPEAKERS P.M. 3 OHMS. 7 x 4 in. £1.25; 6 1/2 in. £1.60; 8 x 5 in. £1.60; 8 in. £1.75; 10 x 6 in. £1.90; 10 in. £2.00. SPECIAL OFFER! LOUDSPEAKERS! All Brand New: 3 ohm, 2 1/2 in; 3 1/2 in; 5 in. 8 ohm, 2 1/2 in; 5 in. 3 ohm, 2 1/2 in; 5 in; 6 x 4 in; 6 in x 3 in; 7 x 4 in; 8 x 5 in. 25 ohm, 2 1/2 in; 3 in; 3 in; 5 x 3 in; 5 in. 36 ohm; 5 in; 5 in. 80 ohm, 2 1/2 in; 2 1/2 in. 120 ohm, 3 in.

£1.25 EACH

LOUDSPEAKER VOLUME CONTROL 15 ohm 10 watt with lin long threaded bush for wood panel mounting 75p.

RICHARD ALLAN TWIN CONE LOUDSPEAKERS. 8 in. diameter 4W £2.50, 10 in. diameter 5W £2.95; Post 25p. 12 in. diameter, 6W, £3.50; 3 or 8 or 15 ohm models. SPEAKER COVERING MATERIALS. Samples Large S.A.E. Horn Tweeters 2-16Kc/s. 10W 8 ohm or 16 ohm £2.60. De Luxe Horn Tweeters 2-18 Kc/s, 15W, 8 ohm £4.00. TWO-WAY 3,000 c.p.s. CROSS OVERS 3, 8 or 15 ohm £1.60. 3-WAY CROSSOVER 850 cps and 3000 cps (25 watt) £2.20.

GOODMANS CONE TWEETER 18,000 cps, 25 watts, 8 ohm. Price £3.60.

## ELECTRO MAGNETIC PENDULUM MECHANISM

1.5v d.c. operation over 250 hrs. continuous on SP2 battery. fully adjustable swing and speed. Ideal displays teaching electro magnetism or for metronome: strobe etc. 95p. Post 20p

## R.C.S. VALVE AMPLIFIER

2 Stage Triode Pentode valve. 3 watts 3 ohm output. Volume on/off and tone controls AC mains. Complete and tested. With Loudspeaker. £4.50 Post 35p.

## WEYRAD COILS

P50/1A0-60p. RA2W 85p. Twin Gang £1.10.  
P50/2C0-40p. OPTL 65p. Printed Circuit 85p.  
P50/3C0-40p. LFDTA. 65p.

COAXIAL PLUG 10p. PANEL SOCKETS 10p. LINE 18p OUTLET BOXES. SURFACE MOUNTING 25p. BALANCED TWIN RIBBON FEEDER 300 ohms, 7p yd. JACK SOCKET Std. open-circuit 15p, closed circuit 25p; Chrome Lead Socket 45p. Phone Plugs 10p. Phone Socket Sp JACK PLUGS Std. Chrome 20p; 3-5mm Chrome 15p. DIN SOCKETS Chassis 3-pin 10p; 5-pin 10p. DIN SOCKETS Lead 3-pin 18p; 5-pin 15p. DIN PLUGS 3-pin 15p; 5-pin 25p. VALVE HOLDERS 5p; CERAMIC 10p; Glass 5p.

## FM/VHF AERIAL FEEDER CABLE

300 ohm suitable for stereo 7p per yard.

## BRITISH FM/VHF TUNING HEART

88 to 108 Mc/s British made. 2 Transistors ready aligned—requires 10.7 Mc/s IF. Complete with tuning gang. Connections supplied but some technical experience required. SUITABLE I.F. STRIP 24.95. Our Price £3.95 Post 20p.

ALL PRICES INCLUDE VAT MINIMUM POST AND PACKING 30p. CALLERS WELCOME

# RADIO COMPONENT

Illustrated Brochure, Radio Books & Component Lists 10p. Written guarantee.

# ALL OUR PRICES INCLUDE V.A.T.

## E.M.I. WOOFER AND TWEETER KIT

**£6.75** THE PAIR. Post 45p. (Available separately. Woofer £4.25; Tweeter £1.90).

Post 45p  
Comprising a fine example of a Woofer 10 1/2 x 6 1/2 in. with a massive Ceramic Magnet. 44oz. Gauss 13,000 lines. Aluminum Cone centre to improve middle and top response. Also the E.M.I. Tweeter 3 1/2 in. square has a special lightweight paper cone and magnet flux 16,000 lines. Crossover condenser and full instructions supplied.  
Impedance Standard 8 ohms  
Maximum power 12 watts  
Useful Response 25 to 18,000 cps  
Bass Resonance 45 cps



**£14.50**  
SUITABLE ENCLOSURE 20 x 18 x 12 in.  
MODERN DESIGN. TEAK WOOD FINISH. Post 75p

## ELAC 8 in. or 10 x 6 in. HI-FI SPEAKER



Dual cone plasticized roll surround. Large ceramic magnet. 50-18,000 cps. Bass resonance 55 cps. 8 ohm impedance. 8 in. 10 watts **£4.35**

## TEAK VENEER HI-FI SPEAKER CABINETS Fluted Wood Fronts

MODEL "A". 20 x 18 x 12 in. For 12 in. dia. **£14.50** Post 10 in. speaker. 75p

MODEL "B". 18 x 10 x 7 in. For 18 x 8 in. or **£7.60** Post 8 in. speaker. 45p



LOUDSPEAKER CABINET  
WADDING 18 in. wide, 20p ft.

BAKER RECOMMENDED 12 inch Enclosure 4 cubic ft. HI-FI CABINET #21-50. Carr. £2 each. Few only. Size 30 x 20 x 12 in. Teak Finished Fluted Front.

TEAKWOOD LOUDSPEAKER FRONT GRILLS  
Modernise your cabinets with the Grooved look. Sizes—18 1/2" x 10 1/2"—75p. 10 1/2" x 7 1/2"—45p.

BARGAIN 4 CHANNEL TRANSISTOR MONO MIXER. Add musical highlights and sound effects to recordings. Will mix Microphone, records, tape and tuner with separate controls into single output. 9 volt battery operated. **£5.20**  
STEREO VERSION OF ABOVE #6 85.



## R.C.S. STEREO FM TUNER BRITISH MADE



This completely cased mains powered Hi-Fi Tuner with brushed aluminium fascia is British made using the latest circuitry. Barga in **£30** Post 45p.

BARGAIN 3 WATT AMPLIFIER. 4 Transistor Push-Pull Ready built with volume, treble and bass controls. 18 volt battery operated. **£4.50**

## WAFER HEATING ELEMENTS THIN

OFFERING 1001 USES for every type of heating and drying applications in the home, garage, greenhouse, factory (available in manufacturing quantities). Approx. size 1 1/2 x 8 1/2 x 1/2 in. Operating voltage 200/250V. a.c. 250 watts approx. Printed circuit element enclosed in asbestos fitted with connecting wires. Completely flexible providing safe Black heat. British-made for use in photo-copiers and print drying equipment.  
Ideal for home handymen and experimenters. Suitable for Heating Pads, Food Warmers, Convector Heaters, etc. Must be clamped between two sheets of metal or asbestos, etc., to make efficient clothes dryers, towel rails—ideal for airing cupboards. Ideal for anti-frost device for the garage—preventing frozen radiators or acting as oil sump heater. Use in the greenhouse for seed raising and plant protection. Invaluable aid for bird houses, incubators, etc., etc. Can be used in series for lower heat. Or in parallel for higher heat applications.

**ONLY 40p EACH (FOUR FOR £1.50)**

ALL POST PAID—Discounts for quantity.

## BAKER MAJOR 12" £11.50



Post 40p  
30-14,500 c/s. 12 in. double cone, woofer and tweeter cone together with a BAKER ceramic magnet assembly having a flux density of 14,000 gauss and a total flux of 145,000 Maxwells. Bass resonance 40 c/s Rated 20 watts. NOTE: 8 or 8 or 15 ohms must be stated.

Module kit, 30-17,000 c/s with tweeter, crossover, baffle and instructions. **£14.50**

Please state 8 or 8 or 15 ohms. Post 45p

## "BIG SOUND" BAKER SPEAKERS

Robustly constructed to stand up to long periods of electronic power. As used by leading groups and discos

Useful response 30-18,000 cps.

Bass Resonance 55 cps.

GROUP "25"

12 in. 25 watt  
3, 8 or 15 ohms.

**£8.95**

Post 40p

GROUP "35"

12 in. 35 watt

3, 8 or 15 ohms.

**£10.50**

Post 40p

GROUP "50"

15 in. 50 watt

8 or 15 ohms.

**£19.50**

Post 50p

GROUP 50/12 in.

50 watt 8 or 15 ohms

**£14.50**

Post 50p

Group + PA Cabinets in stock

Send for Leaflet.



## MAJOR 100 WATT ALL PURPOSE TRANSISTOR AMPLIFIER

All purpose transistorised. Ideal for Groups, Disco and P.A. 4 inputs speech and music. 4 way mixing. Output 8/15 ohm. a.c. Mains. Separate treble and bass controls. Guaranteed. Details SAE. De Luxe Model in wood case £89.



**£59** Carr. £1.00

NEW MODEL—MAJOR 50 WATT **£49.95** Carr. £1.

4 inputs 2-way mixing. 2 outputs separate treble and bass controls. Ideal disco or p.a. amp.

## DE LUXE 100 WATT VALVE AMPLIFIER CHASSIS

4 input 10 wide range controls. For Mikes, Discos, Organs, Guitars, etc. 4, 8 & 15 ohm loudspeakers matching £92.00.

THE "INSTANT" BULK TAPE ERASER & HEAD DEMAGNETISER. Suitable for cassettes, and all sizes of tape reels. A.C. mains 200/250V. Leaflet S.A.E. **£4.35** Post 30p



## QUALITY LOUDSPEAKER ENCLOSURE

Teak veneered 1/2 in thick wood cabinet. Size 18 1/2 in x 18 1/2 in x 8 1/2 in. Weight 23 lbs. This cabinet features a wide mesh Silver Grill covering a separate compartment for mounting Tweeters or Mid-Range Horn. The fully sealed bass compartment is cut out for 6 1/2 in Woofer. £8.50 Carr. 85p. Rosewood Version £9.50 Carr. 85p. Baffle could be cut to take larger speaker.



## SPECIAL OFFERS

100 Ohm 20 watt Rheostat 2 1/2 in diam. Ceramic Former. Screw Terminals 1/2 in. diam. spindle. 95p. Post 25p. AC mains relay 3 pole change over 75p.

E.M.I. GRAM MOTOR  
120v. or 240v. A.C. 2,400 rpm. 2-pole  
70mA. Size 2 1/2 x 2 1/2 x 2 1/2 in. **£1.25** Post 30p.

E.M.I. TAPE MOTOR  
4 pole, 240 v. 135 mA. Size 3 1/2 x 2 1/2 x 2 1/2 in. 1200 rpm. Spindle 1/2 in diameter. 120v version £1. **£2.00** Post 30p

## BAKER HI-FI SPEAKERS HIGH QUALITY — BRITISH MADE

### REGENT 12 in. 15 watts

An inexpensive unit for the beginner in high fidelity and for general purposes. May be used to improve any Radio, Amplifier, Hi-Fi or Television receiver.

Bass Resonance 45cps  
Flux Density 12,000gauss  
Useful response 45-18,000cps  
3 or 8 or 15 ohm models.


**£9.50** Post 40p



### DE-LUXE Mk II 12 in 15 watts

Especially designed to provide full range reproduction at an economical cost. Suitable for use with any high fidelity system. Built-in concentric tweeter cone.  
Bass Resonance 30cps  
Flux Density 14,000gauss  
Useful response 25-18,000cps  
8 or 15 ohms models.

**£12.50** Post 40p

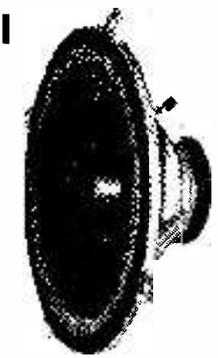


### SUPERB 12 in. 20 watts

A high quality loudspeaker, its remarkable low cone resonance ensures clear reproduction of the deepest bass. Fitted with a special copper drive and concentric tweeter cone resulting in full range reproduction with remarkable efficiency in the upper register.

Bass Resonance 25cps  
Flux Density 16,500gauss  
Useful response 20-17,000cps  
8 or 15 ohms models.

**£17.00** Post 50p

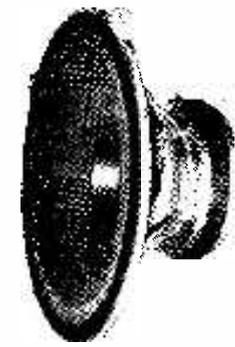


### AUDITORIUM 12 in. 25 watts

A full range reproducer for high power. Electric Guitars, public address, multi-speaker systems, electric organs. Ideal for Hi-Fi and Discoteques.

Bass Resonance 35cps  
Flux Density 15,000gauss  
Useful response 25-18,000cps  
8 or 15 ohms models.

**£14.50** Post 50p

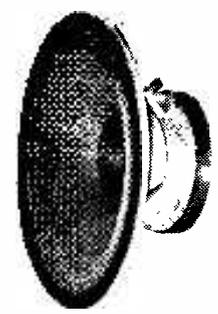

### AUDITORIUM 15 in. 35 watts

A high wattage loudspeaker of exceptional quality with a level response to above 8,000 cps. Ideal for Public Address, Discotheques, Electronic instruments and the home HI-FI.

Bass Resonance 35cps  
Flux Density 15,000gauss  
Useful response 20-14,000cps  
8 or 15 ohms models.

**£19.50** Post 50p



Hi-Fi Enclosure Manual containing plans, designs, crossover data and cubic tables. 60p. Post 3p.

CUSTOMERS FREE CAR PARK

# SPECIALISTS

(Exports Remit cash and extra postage.)

Practical Wireless, August 1975

OPEN 9-6. WEDNESDAY 9-1. SATURDAY 9-5. Closed for lunch 1-15-2-30


337 WHITEHORSE ROAD . GROVDON

Buses 50, 68, 159. Rail Selhurst

Telephone 01-684-1665

# The Shop Window for the Very Best...

# CPC

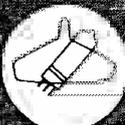

**COMBINED  
PRECISION  
COMPONENTS  
(PRESTON)LTD**

Department PW  
194-200 North Rd.  
Preston PR1 1YP  
Tel: 55034  
Telex: 677122.

### TOSHIBA VALVES

| Type   | Price (p) | Type   | Price Each (p) |
|--------|-----------|--------|----------------|
| DY87   | 30.0      | AD149  | 40             |
| DY802  | 30.0      | AD161  | 38             |
| ECC82  | 28.0      | AD162  | 38             |
| EF80   | 29.5      | AF114  | 24             |
| EF183  | 34.5      | AF115  | 21             |
| EF184  | 34.5      | AF116  | 22             |
| EH90   | 35.5      | AF117  | 19             |
| PC900  | 24.5      | AF118  | 50             |
| PCC59  | 40.0      | AF1J9  | 35             |
| PCC189 | 41.0      | AF178  | 45             |
| PCF80  | 31.5      | AF180  | 45             |
| PCF86  | 39.0      | AF181  | 45             |
| PCF801 | 42.0      | AF239  | 40             |
| PCF802 | 40.0      | AF240  | 60             |
| PCL82  | 39.0      | BC107  | 11             |
| PCL84  | 39.0      | BC108  | 10             |
| PCL85  | 44.5      | BC108C | 14             |
| PCL86  | 41.0      | BC113  | 13             |
| PFL200 | 59.5      | BC116A | 19             |
| PL36   | 55.5      | BC117  | 14             |
| PL84   | 25.0      | BC125B | 15             |
| PL504  | 64.5      | BC132  | 25             |
| PL508  | 67.0      | BC135  | 15             |
| PL519  | £1.50     | BC137  | 19             |
| PY88   | 35.5      | BC138  | 26             |
| PY800  | 33.0      | BC142  | 23             |
| PY500A | 85.0      | BC143  | 25             |

### SEMI CONDUCTORS

| Type   | Price Each (p) | Type   | Price Each (p) |
|--------|----------------|--------|----------------|
| AC127  | 17             | BC147A | 11             |
| AC128  | 13             | BC148  | 10             |
| AC141K | 25             | BC149  | 15             |
| AC142K | 25             | BC154  | 15             |
| AC151  | 20             | BC157  | 14             |
| AC154  | 18             | BC158  | 10             |
| AC155  | 18             | BC159  | 11             |
| AC156  | 20             | BC173  | 18             |
| AC176  | 22             | BC178B | 20             |
| AC187  | 19             | BC182L | 12             |
| AC187K | 24             | BC183L | 12             |
| AC188  | 17             | BC187  | 25             |
| AC188K | 26             | BC214L | 15             |
| AD142  | 45             | BC328  | 28             |
|        |                | BC337  | 19             |

### DIODES

| Type     | Price Each (p) | Type     | Price Each (p) |
|----------|----------------|----------|----------------|
| BD124    | 75             | BF173    | 20             |
| BD131    | 45             | BF178    | 35             |
| BD132    | 39             | BF179    | 40             |
| BD160    | £1.39          | BF180    | 31             |
| BD235    | 49             | BF181    | 32             |
| BD237    | 52             | BF184    | 25             |
| BDX32    | £2.40          | BF185    | 25             |
| BF115    | 20             | BF194    | 9              |
| BF160    | 15             | BF195    | 8              |
| BF167    | 20             | BF196    | 10             |
| BF173    | 20             | BF197    | 12             |
| BF178    | 35             | BF198    | 23             |
| BF179    | 40             | BF200    | 25             |
| BF180    | 31             | BF218    | 30             |
| BF181    | 32             | BF224    | 23             |
| BF184    | 25             | BF258    | 34             |
| BF185    | 25             | BF336    | 28             |
| BF194    | 9              | BF337    | 35             |
| BF195    | 8              | BF356    | 54             |
| BF196    | 10             | BFX86    | 28             |
| BF197    | 12             | BFY50    | 19             |
| BF198    | 23             | BFY52    | 20             |
| BF200    | 25             | BSY52    | 35             |
| BF218    | 30             | BT106    | £1.20          |
| BF224    | 23             | BU105/02 | £1.96          |
| BF258    | 34             | BU108    | £2.10          |
| BF336    | 28             | BU208    | £2.95          |
| BF337    | 35             | E1222    | 30             |
| BF356    | 54             | MJE340   | 45             |
| BFX86    | 28             | OC71     | 15             |
| BFY50    | 19             | OC72     | 16             |
| BFY52    | 20             | RZ008B   | £2.00          |
| BSY52    | 35             | RZ010B   | £2.00          |
| BT106    | £1.20          | RCA16334 | 80             |
| BU105/02 | £1.96          | RCA16335 | 80             |
| BU108    | £2.10          |          |                |
| BU208    | £2.95          |          |                |
| E1222    | 30             |          |                |
| MJE340   | 45             |          |                |
| OC71     | 15             |          |                |
| OC72     | 16             |          |                |
| RZ008B   | £2.00          |          |                |
| RZ010B   | £2.00          |          |                |
| RCA16334 | 80             |          |                |
| RCA16335 | 80             |          |                |

### INTEGRATED CIRCUITS

| Type      | Price Each | Type     | Price Each |
|-----------|------------|----------|------------|
| BA115     | 7          | TAA550   | 49p        |
| BA145     | 14         | TAA700   | £2.95      |
| BA148     | 19         | TBA120AS | £1.00      |
| BA154/201 | 11         | TBA460Q  | £1.40      |
| BY126     | 11         | TBA520Q  | £2.35      |
| BY127     | 12         | TBA530Q  | £1.75      |
| BY199     | 27         | TBA540Q  | £1.75      |
| BY206     | 21         | TBA560CO | £2.40      |
| BY238     | 25         | TBA800   | £1.50      |
| OA90      | 6          | TBA920Q  | £2.90      |
| OA202     | 7.5        | TBA990Q  | £2.90      |
| IN60/OA91 | 5          | TCA270Q  | £2.90      |

### NEW TOSHIBA TUBES

|              |        |
|--------------|--------|
| 19" A49/191X | £48.95 |
| 20" 5100JB22 | £50.75 |
| 22" A56/120X | £54.25 |

### EHT MULTIPLIERS MONOCHROME (BRC)

| Type                  | Price Each |
|-----------------------|------------|
| 2HD 950MK1.960        | £1.70      |
| 2TO 950MK2.1400       | £1.85      |
| 2DAK 1500 (17" & 19") | £1.85      |
| 2TAK 1500 (23" & 24") | £2.00      |

### EHT MULTIPLIERS - COLOUR

|                        |       |
|------------------------|-------|
| 11TAO ITT CVCI. 2 & 3  | £4.50 |
| 11N GEC/Sobell         | £4.50 |
| 11TAZ GEC 2110         | £4.85 |
| 11TAM Philips G8       | £4.50 |
| 11TBD Philips G5       | £4.50 |
| 3TCW Pve 951/693       | £3.50 |
| 11H Decca 30 Series    | £4.50 |
| 11TAO Decca 'Bradford' | £4.50 |
| 3TCU Thorn 3000/3500   | £5.00 |
| 11HAA Thorn 8500       | £1.90 |
| 11HAB Thorn 8500       | £4.25 |


PRICES SUBJECT TO 25% V.A.T.  
All goods subject to settlement  
discount of 5% 7 days and 2%  
monthly.  
No postage charges or minimum  
order values.  
Write or phone for full details now.

## ...In Prices, Quality and Service.

LISTEN TO **CODAR**®

THE WORLD!

# ★CR70A

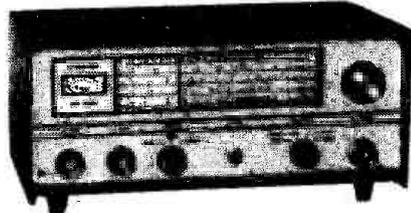

**COMMUNICATION RECEIVER**

The CODAR CR70A is an outstanding general coverage communication receiver, ideal for the keen S.W.L. It tunes from 540 metres medium through to 10 metres with no gaps. Covers shipping, coastguard and distress frequencies, all six amateur bands 160-10 metres, International broadcast, Met. stations etc. etc. giving world-wide reception. Exclusive features include Air-spaced CODAR-COIL Hi-"Q" Aerial input, illuminated Meter and Slide Rule Scale, Two Speed vernier tuning. Switched B.F.O. for CW/SSB signals. Separate output for Tape recorder. Ready to plug in to 200/240 volts A.C. it only needs your aerial and a 2/3 ohm loudspeaker to bring the world to your finger tips. 12 months full guarantee.

### ★ IMPORTANT NOTE

This fine receiver is not a mass produced item, but each set is hand built to your order, individually checked and air tested. Please allow for this when ordering—your delivery date will be shown on your receipt, sent by return.

\* Special discounts for Educational Authorities and Senior Citizens.




"Free Gift!! Claim your Codar ball-point pen free with your next order!!"

**VALCON WORKS · BURRELL BUILDINGS · CHURCHILL INDUSTRIAL ESTATE · LANCING · SUSSEX**  
WORLD-WIDE MAIL ORDER—EXPORT QUOTES FREE.



★MADE TO ORDER!


**£36.00! (carr. free)**  
+ VAT £9.00

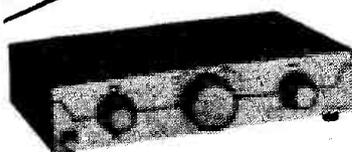

**£11.00! (carr. free)**  
+ VAT £2.75

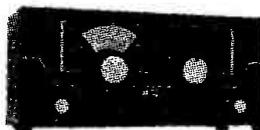**R.F. PRESELECTOR**

The PR40 R.F. Preselector is the solid state version of the world famous PR30 which it now supersedes. It employs Silicon "N" Channel FET (Field Effect Transistor) front end followed by silicon NPN Broad Band R.F. Amp., and will substantially improve receiver performance over the range 1.5 to 35 MHz, providing a considerable increase in gain up to an overall average of 30dB, with improved image rejection and noise ratio. Supplied complete with co-ax plug (less standard 9 volt PP6 Battery). 12 months Guarantee...



# MULTIBAND-6★

**SHORT WAVE RECEIVER KIT**  
**£16.56! (carr. free)**  
+ VAT £4.14

All transistor T.I.F. Receiver tunes 550 KHz to 30 MHz (540 to 10 metres) complete coverage—no gaps. Medium waves—Trawlers—Ship/Shore Telephone—All Six Amateur Bands 160-10 metres—International Broadcast from Australia, Far East, Russia, USA etc. using 4 miniature plug in Coils. Hi-Gain FET Regen. Det./AF/AF Module giving full loudspeaker output to any external 2/3 ohm speaker. Receives AM/CW/SSB. Separate Electrical Bandsread, Calibrated Main Tuning. A Quality CODAR-KIT with 12 months Guarantee. No technical knowledge required, simple to build, printed circuit and Pictorial Instruction Manual. fully detailed step by step. Complete Kit with 4 Coils (less standard PP6 battery).

ILLUSTRATED LEAFLETS FREE ON REQUEST (STAMP APPRECIATED)

# CODAR

**NEW! AVAILABLE SOON!!**  
THE MINI-CLIPPER STARTER KIT. ALL SOLID STATE SHORT WAVE RECEIVER, ALSO SUPER HI-"Q" A.T.U.

Tel: LANCING 61901

BN15 - 8TZ

## NEW ITEMS THIS MONTH

The bargains in this column are just some of the items which appeared in the April supplement to our catalogue. You can receive this catalogue and the next 12 supplements by sending £1.

**Telephone cords.** 4 core, curly cords as fitted to telephone handsets, made for the GPO so obviously very good quality. Standard length, 25p each. VAT & Post 15p each.

**Fire alarm switches.** In red cast iron case with break glass panel. These are engraved "In case of fire break glass" and have a hinged lid and second safety switch for testing purposes. £1.75 each. VAT & Post 45p each.

**Tacho-motors.** A precision motor made by Muirhead, when driven at 1000 rpm it generates 3V so it is the basis of a tacho-meter. It is a battery operated motor which can be used for precision work and within limits its speed can be brought to that desired by choosing the right voltage. Ex-equipment but fully guaranteed by us. 50p. VAT & Post 15p each.

**Mains motor.** Heavy duty made by Smiths with special long bearings for extra quiet running. This is a powerful (1 1/2") stack motor; good quality of these available at the price of £1.25 each. VAT & Post 30p each.

**Crouzet motor.** With gear box, mains input. final speed 12 revs per hour, fitted on mounting plate with on-off switch. £1.50 each. VAT & Post 30p.

**2 1/2 r.p.m. mains motor.** With gear box, ideal for driving colour wheels, etc. 95p each. VAT & Post 20p.

**Battery motor.** With gear box. Extremely well-made motor and gear box which with a 4 volt battery will rotate at 1 r.p.m. Speeds easily adjustable up and down (within limits) by changing the battery volts. Price £3 each. VAT & Post 60p.

**Multi-purpose relay.** Work with coil volts from 6v to 24v or from the mains through diode and 15w lamp or equivalent resistor. It has two sets of normal change-over contacts and a further two sets of change-overs which make before break. Supplied complete with mounting bracket. Price 50p. VAT & Post

**24v power pack.** Normal mains input, with a thermal safety device in primary of mains transformer and 4000 mfd of smoothing with full wave rectifier; completely enclosed in plastic box and with flex for mains, and terminal block for output. Price £1.75 + VAT & Post 95p.

**Pointer knob.** With brushed aluminium embellishers, for 3/16 spindle. 10 for £1 + 40p VAT & Post.

**500K Edgeways control.** 1 1/2" diameter made by Morganite s/og, ideal for light dimmer control or similar. 10 for £1 + 40p VAT & Post.

**Battery charger.** For nickel cadmium cells intended or small 1" diameter cells but suitable for other sizes using adaptors or external leads. This pushes straight into a 2-pin razor socket and is completely enclosed. 35p each + 20p VAT & Post.

**Permeability tuners.** Two stage ideal for use with ZN414 or similar circuit. Price 15p each + 15p VAT & Post.

**47 of 400v condensers by Eris.** 10 for 50p + 25p VAT & Post.

**8 switch disco lamp controller.** This is a mains motor driving a rotating drum on which are 8 adjustable segments. These segments operate individual changeover 10 amp switches, so a total of 8 x 20 amps of lighting can be controlled enabling an unlimited variety of lighting effects to be achieved and changed with the minimum of effort. This is a real snip at £8.50 + 95p VAT & Post.

**Wire ended neons.** For incorporating in random lighting effects or simply as mains indicators, with long leads and resistors for working directly off mains. 10 for £1 + 20p VAT & Post.

**Oven thermostat.** Made by the famous Diamond H Company, this has a sensor joined by a capillary to a variable control and when fitted with a knob is ideal for many ovens or processes. 50p each + 25p VAT & Post.

**150w auto transformer.** 230-240v in, 115-150v out, very well made and dip sealed for quiet running, upright mounting with fixing legs. £2.20 each + 75p VAT & Post.

**Immersion heaters.** Standard screw-in fitting for normal tanks 23" 4KW - £2.50; 21" 3KW - £2.25; 10" 2KW - £2. Rod thermostats to suit. £1 each. Postage 40p per heater. VAT 8%.

**Mains transformer.** 25v-0-25v 2 amps and 110v 100mA secondaries normal tapped primary. Price £2.50 + £2 VAT & Post.

**Instrument mains transformer.** With 140v secondary tapped at 130, 120, 80 and 5v at 1 amp rating. Price £2 + 56p VAT & Post.

**Panel lamps.** With plastic lens, push through circular hole for 6v operation, 20p. Ditto for 12v operation 20p. Ditto for 24v operation 20p. + 10p each VAT & Post.

**2 pole 3 way wave change switch.** Standard length 1 1/2" spindle. 20p + 15p VAT & Post.

**Panel meter.** 2 1/2" 0-500mA, flush mounting. Price £1.50 + 56p VAT & Post.

**Mercury batteries.** Tube of 7 batteries connected together to give 10-7 volts offered some time ago at 6p per tube or £1 per carton of 25 tubes. A further large purchase of these enables us to offer at an even better price - 10 cartons making a total of 250 x 10-7 volt batteries for only £7.50 + £1.85 VAT & Postage per 10 cartons.

**EHT transformer.** American made, sealed in a steel case measuring 6 1/2" x 6" x 5 1/2" high with large porcelain stand-off insulators; it is extremely well-made, looks good enough to give 10 kv at 1 amp, intended for American mains, its primary would have to be fed through a variac or similar. With 90v input EHT output is 6-5v. Price £15 each + carriage and VAT £3.

## MULLARD UNILEX STEREO SYSTEM

There is no doubt that it is a good system, we believe that for the money it is without comparison. We demonstrate gladly at our Tamworth Road depot. Prices of the individual items for th is:

|   |              |       |
|---|--------------|-------|
| 1 Unilex Amplifier                                  | Ref. EP.9000 | £1.60 |
| 1 Unilex Amplifier                                  | Ref. EP.9000 | £1.60 |
| 1 Unilex Pre-Amp                                    | Ref. EP.9001 | £1.98 |
| 1 Unilex Power Unit                                 | Ref. EP.9002 | £2.53 |
| 1 Control panel kit with spun aluminium faced knobs |              | £3.80 |

Pair of 15 ohm speakers made by Goodmans are also available if required, price £3.30 the pair. No extra postage if ordered with the above, otherwise add 25p.


ALL SUBJECT TO 25% VAT

## SMITHS CENTRAL HEATING CONTROLLER



Push button gives 10 variations as follows:-(1) continuous hot water and continuous central heating (2) continuous hot water but central heating off at night (3) continuous hot water but central heating on only for 2 periods during the day (4) hot water and central heating both on but day time only (5) hot water all day but central heating only for 2 periods during the day (6) hot water and central heating on for 2 periods during the day time only—then for summer time use with central heating off (7) hot water continuous (8) hot water day time only (9) hot water twice daily (10) everything off. A handsome looking unit with 24 hour movement and the switches and other parts necessary to select the desired programme of heating. Supplied complete with wiring diagram. Originally sold, we believe, at over £15—we offer these, while stocks last, at £5.95 each, VAT & Postage 85p each.

## WALL THERMOSTATS

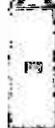

Wall mounting and in a handsome plastic case. (Cream and beige). Adjustable by slider (lockable) and may be set to control temperatures from around freezing through to 50°C. The slide panel is engraved and indicates (frost), (warm), (very warm), etc. The thermostat will control heaters, etc., up to 15 amp at normal mains voltage and is ideal for living room, bedroom and greenhouse, etc. Price £1.95, VAT & Postage 30p. Don't miss this.

## THIS MONTH'S SNIP

**High power battery motor,** 12v operated, strong enough to power a motor mower, go-cart or similar. Speed easily variable. These motors can also be used as a brake for any rotating machine, simply by coupling the spindle to the machine and short-circuiting the windings by a variable resistance, price £2.50, VAT & Postage 64p.


Even more powerful 6/12 volt model £3.50, VAT & Postage 92p.

## BREAK-DOWN UNIT

Contains a whole range of most useful parts some of which are as follows—66 silicon diodes equivalent OA91, 68 resistors, mostly 1/2 watt 5% covering a wide range of values. 4 x 1 mfd 400v condensers. 5 x .01 mfd 100v condensers. 2 RF chokes. 8 x B9 valve holders. 1 x 4H choke. 1 x 115v transformer. 1 boxed unit containing 4 delay lines. Tag panels, trimmer condensers, suppressors, all mounted up on a useful chassis sized approx. 9" x 5" x 7". Offered at only 75p—the 66 diodes would cost at least 10 times this amount, so this is obviously a snip not to be missed. VAT & Postage 70p.
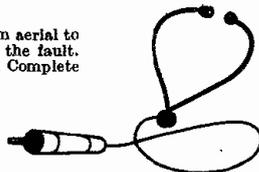
## RADIO STETHOSCOPE

Easiest way to fault find, traces-signal from aerial to speaker, when signal stops you've found the fault. Use it on Radio, TV, amplifier, anything. Complete kit comprises two special transistors and all parts including probe tube and crystal earpiece, £2.20 twin stetho-set instead of earpiece 85p, VAT & Postage 45p.



## DISTRIBUTION PANELS



Just what you need for work bench or lab. 4 x 13 amp sockets in metal box to take standard 13 amp fused plugs and on/off switch with neon warning light. Supplied complete with 6 feet of flex cable. Wired up ready to work. £2.75, VAT & Postage 85p.

## ISA ELECTRICAL PROGRAMMER



Learn in your sleep: Have radio playing and kettle boiling as you awake—switch on lights to ward off intruders—have a warm house to come home to. All these and many other things you can do if you invest in an electrical programmer. Clock by famous maker with 15 amp. on/off switch. Switch-on time can be set anywhere to stay on up to 6 hours. Independent 60 minute memory jogger. A beautiful unit. Price £2.30, VAT & Postage 60p, or with glass front, chrome bezel, £1.00 extra.

## SHORTWAVE CRYSTAL SET

Although this uses no battery it gives really amazing results. You will receive an amazing assortment of stations over the 19, 25, 31, 39 metre bands—Kit contains chassis front panel and all the parts, £1.50—crystal ear-piece 55p, VAT & Postage 75p.



## INSTANT START FLUORESCENT LIGHTING BARGAINS

Starterless control gear, complete with tube ends and tube clips for window lighting, signs, fascias, etc. 4 ft. 40 w. £1.50; 5 ft. 65w. £1.60; 6 ft. 80w. £1.75; 8 ft. 100w. £1.95; and for pairs as follows:—twin 2 ft. 20w. £2.55; twin 3 ft. 30w. £2.75; twin 4 ft. 40w. £2.95; twin 5 ft. 65w. £3.25; twin 5 ft. 80w. £3.95; twin 8 ft. 125w. £4.50. These are about one half of maker's current prices and can't be repeated once stocks are cleared. Please add 30p per piece to cover postage or carriage and 8% VAT.


# J. BULL (ELECTRICAL) LTD.

(Dept. P.W.), 103 TAMWORTH ROAD, CROYDON CRO 1XX

## MAINS TRANSFORMERS

|                                      |                 |       |
|--------------------------------------|-----------------|-------|
| All standard 230-250 volt primaries. |                 | £     |
| 1v                                   | 1 amp (special) | 1.75  |
| 2-4v                                 | 5 amp           | .85   |
| 6-3v                                 | 2 amp           | 1.00  |
| 6-3v                                 | 3 amp           | 1.50  |
| 9v                                   | 1 amp           | .95   |
| 9v                                   | 3-5 amp         | 1.95  |
| 12v                                  | 1 1/2 amp       | 1.50  |
| 12v                                  | 1 amp           | 1.00  |
| 6-5v-0-6-5v                          | 1 amp           | 1.85  |
| 18v                                  | 1 amp           | 1.25  |
| 20v                                  | 4 amp           | 1.00  |
| 24v                                  | 1 amp           | 1.50  |
| 24v                                  | 3 amp           | 3.50  |
| 12-0-12v                             | 50mA            | 1.20  |
| 6-0-6v                               | 50mA            | 1.20  |
| 8-0-8v                               | 4 amp           | 1.25  |
| 18-0-18v                             | 2 amps          | 3.50  |
| 25v                                  | 1 1/2 amp       | 1.95  |
| 50v 2 amp & 6-3v                     | 1 amp           | 4.50  |
| 60v 5 amp & 5v                       | 1 amp           | 7.50  |
| 27v                                  | 8 amp           | 4.50  |
| 30v                                  | 37 amp          | 22.00 |
| 80v tapped 75v & 70v                 | 4 amp           | 5.50  |
| 230v-60mA & 6-3v                     | 1.5 amps        | 1.75  |
| 275-0-275v at 90mA & 6-4v            | 3 amps          | 2.25  |
| EHT Transformer 5000v                | (intermittent)  | 5.50  |
| 23mA                                 |                 |       |
| Charger Transformers                 |                 |       |
| 6v and 12v                           | 2 amps          | 1.25  |
| 6v and 12v                           | 3 amps          | 2.25  |
| 6v and 12v                           | 5 amps          | 3.50  |

## ONLY £1 FOR SEVEN ELECTRIC MOTORS

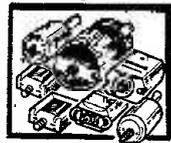

7 powerful batt. motors as used in racing cars & power models. Output & types vary for use in hundreds of different projects—Tools, toys, models, etc. All brand new reversible & for 1 1/2-12v. batts. Wiring diag. inc. VAT & Post 40p. FREE plan for min. power station.

## RELAY BARGAIN

Type 600 relay, 2 changeover one open and one closed contact. Twin 500 ohm coils make this suitable or closing off DC 6v, DC 12v, DC 24v or AC mains using resistor and rectifier. 33p each. Resistor and rectifier 20p extra. Post and VAT 80p.

## BLACK LIGHT

As used in discotheques and for stage effects, etc. Virtually no white light appears until the rays impinge on luminous paint or white shirts, etc. We offer 9" 6w tubes complete with starter, choke, lamp-holders and starter-holder. Price £2.75 + 30p post. Tubes only £2. Post & VAT 50p.


## TAPE DECK

In metal case with carrying handle, heavy fly wheel and capstan drive. Tape speed 31. Mains operated on metal platform with tape head and guide. Not new but guaranteed good working order. Price £1.50 plus VAT and Postage £1.50.


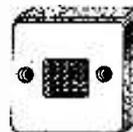
## LIGHT SWITCH

Automatically switches onlights at dusk and off at dawn. Can also be used where light and dark is a convenient way to stop and start an operation. Requires only a pair of wires to the normal switch. In bakelite box, normal switch-plate size. 1 amp model £2.95. VAT and Postage 50p.



## MAINS TRANSISTOR PACK

Designed to operate transistor sets and amplifiers. Adjustable output 6v., 9v., 12 volts for up to 500mA (class B working). Takes the place of any of the following batteries: PPI, PP3, PP4, PP6, PP7, PP9 and others. Kit comprises: main transformer rectifier, smoothing and load resistor, condensers and instructions. Real snip at only £1.50. VAT & Postage 60p.

## SOUND TO LIGHT UNIT

Add colour or white light to your amplifier. Will operate 1, 2 or 3 lamps (maximum 400w). Unit in Box all ready to work. £7.95 plus 95p VAT and postage.




## MAINS MOTOR


Precision made—as used in record decks and tape recorders—ideal also for extractor fans, blower, heaters, etc. New and perfect. Snip at 75p Postage 20p for first one then 10p for each one ordered. 1" stackmotor £1.04. 1 1/2" stackmotor £1.20. VAT 8%.
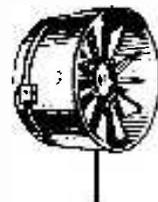
## EXTRACTOR FAN

Cleans the air at the rate of 10,000 cubic ft. per hour. Suitable for kitchens, bathrooms, factories, changing rooms, etc., it's so quiet it can hardly be heard. Compact, 5 1/2" casing with 5 1/2" fan blades. Kit comprises motor, fan blades sheet steel casing, pull switch, mains connector and fixing brackets. £3.75 VAT & Postage £1.25.


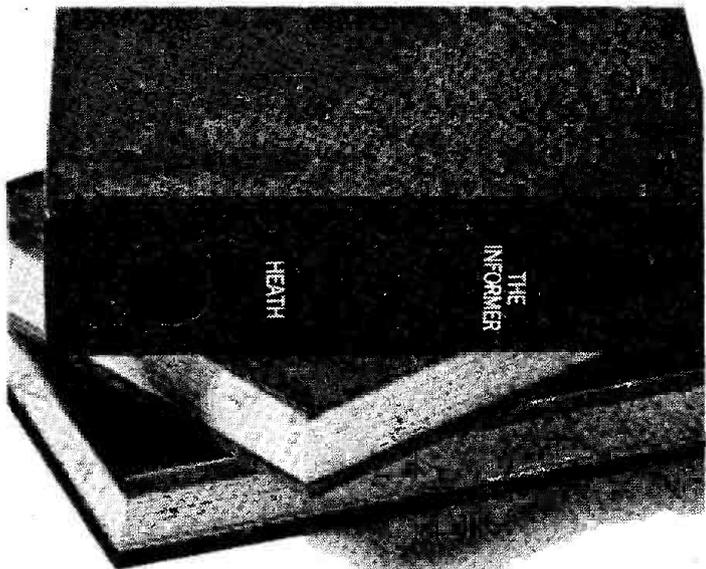
# Enough books are written about crime, this one stops it.



Outside it's a book. Inside it's an ingenious ultrasonic burglar alarm from Heathkit. The GD-39.

A complete kit that can be assembled in only a few enjoyable hours, with the help of a very easy to follow instruction manual.

The GD-39 works by transmitting a silent, ultrasonic signal throughout the room. And continuously monitoring it. Any movement made by an intruder in the room will then automatically produce a change in the signal. Which triggers off a lamp and, thirty seconds later, a remote buzzer, that just you hear, or a loud bell.

Enough to scare the living daylight out of a burglar.

For more details, and a bookful of other ideas, just post the coupon now for your free Heathkit catalogue.

Or, if you're in London or Gloucester, call in and see us. The London Heathkit Centre is at 233 Tottenham Court Road. The Gloucester showroom is next to our factory in Bristol Road.

Heath (Gloucester) Limited,  
Dept. PW-85, Bristol Road,  
Gloucester GL2 6EE.  
Tel: (0452) 29451.



## The GD-39 Ultrasonic Burglar Alarm

To: Heath (Gloucester) Limited, Dept. PW-85, Gloucester GL2 6EE. Please send me a free Heathkit catalogue.



Name \_\_\_\_\_  
Address \_\_\_\_\_  
Postcode \_\_\_\_\_

Remember easy terms are available with the Heathkit Monthly Budget Plan.



# TRANSFORMERS

## MAINS ISOLATING PRI 120/240v SEC 120/240v CENTRE TAPPED AND SCREENED

| Ref. No. | VA (Watts) | £     | p & p |
|----------|------------|-------|-------|
| 07       | 20         | 2.80  | 38    |
| 149      | 60         | 4.37  | 45    |
| 150      | 100        | 4.89  | 45    |
| 151      | 200        | 8.13  | 53    |
| 152      | 250        | 9.83  | 73    |
| 153      | 350        | 11.88 | 73    |
| 154      | 500        | 13.65 | 91    |
| 155      | 750        | 20.51 | BRS   |
| 156      | 1000       | 29.15 | BRS   |
| 157      | 1500       | 33.23 | BRS   |
| 158      | 2000       | 37.07 | BRS   |

## 12 and or 24 Volt PRIMARY 240-250 VOLTS

| Ref. No. | 12v | Amps | 24v | £     | p & p |
|----------|-----|------|-----|-------|-------|
| 111      | 0.5 | 0.25 |     | 1.35  | 23    |
| 213      | 1.0 | 0.5  |     | 1.74  | 30    |
| 71       | 2   | 1    |     | 2.29  | 38    |
| 18       | 4   | 2    |     | 2.86  | 38    |
| 70       | 6   | 3    |     | 4.12  | 45    |
| 108      | 8   | 4    |     | 4.56  | 45    |
| 72       | 10  | 5    |     | 5.14  | 53    |
| 116      | 12  | 6    |     | 5.52  | 53    |
| 17       | 16  | 8    |     | 7.28  | 60    |
| 115      | 20  | 10   |     | 10.39 | 73    |
| 187      | 30  | 15   |     | 13.59 | 83    |
| 226      | 60  | 30   |     | 16.83 | BRS   |

## 30 VOLT RANGE SECONDARY TAPS 0-12-15-20-25-30

| Ref. No. | Amps | £    | p & p |
|----------|------|------|-------|
| 112      | 0.5  | 1.81 | 30    |
| 79       | 1.0  | 2.40 | 38    |
| 3        | 2.0  | 3.49 | 38    |
| 20       | 3.0  | 4.53 | 45    |
| 21       | 4.0  | 5.13 | 53    |
| 51       | 5.0  | 6.41 | 53    |
| 117      | 6.0  | 7.16 | 60    |
| 88       | 8.0  | 9.87 | 67    |
| 89       | 10.0 | 9.90 | 73    |

## 50 VOLT RANGE SECONDARY TAPS 0-19-25-33-40-50

| Ref. No. | Amps | £     | p & p |
|----------|------|-------|-------|
| 102      | 0.5  | 2.58  | 30    |
| 103      | 1.0  | 3.38  | 38    |
| 104      | 2.0  | 4.68  | 45    |
| 105      | 3.0  | 5.81  | 53    |
| 106      | 4.0  | 7.60  | 67    |
| 107      | 6.0  | 12.10 | 67    |
| 118      | 8.0  | 12.98 | 85    |
| 119      | 10.0 | 16.99 | BRS   |

## 60 VOLT RANGE SECONDARY TAPS 0-24-30-40-48-60

| Ref. No. | Amps | £     | p & p |
|----------|------|-------|-------|
| 124      | 0.5  | 2.33  | 38    |
| 126      | 1.0  | 3.41  | 38    |
| 127      | 2.0  | 5.08  | 45    |
| 125      | 3.0  | 7.52  | 60    |
| 123      | 4.0  | 8.75  | 67    |
| 40       | 5.0  | 9.75  | 73    |
| 120      | 6.0  | 11.30 | 85    |
| 121      | 8.0  | 15.00 | BRS   |
| 122      | 10.0 | 17.52 | BRS   |
| 189      | 12.0 | 19.98 | BRS   |

## AUTO TRANSFORMERS

| Ref. No. | VA (Watts) | Auto Taps         | £     | p & p |
|----------|------------|-------------------|-------|-------|
| 113      | 20         | 0-115-210-240     | 1.67  | 30    |
| 64       | 75         | 0-115-210-240     | 2.90  | 38    |
| 4        | 150        | 0-115-210-220-240 | 4.12  | 45    |
| 66       | 300        | "                 | 5.82  | 53    |
| 67       | 500        | "                 | 8.82  | 67    |
| 84       | 1000       | "                 | 13.68 | 91    |
| 93       | 1500       | "                 | 18.11 | BRS   |
| 95       | 2000       | "                 | 24.20 | BRS   |
| 73       | 3000       | "                 | 35.09 | BRS   |

## CASED AUTO TRANSFORMERS

240V mains lead input and USA 2 pin outlets 20VA £3.23 p & p 38p.  
500 VA £10.45 p & p 80p  
1000 VA £17.51 BRS

## HIGH VOLTAGE

| Mains Isolating        | Ref. No. | VA       | £    | p & p |
|------------------------|----------|----------|------|-------|
| PRI 200/220 OR 400/440 | 200      | 200      | 1.54 | 10    |
| SEC 100/120 OR 200/240 | 1A       | 1A       | 1.84 | 30    |
|                        | 13       | 100      | 1.41 | 13    |
|                        | 235      | 330, 330 | 1.56 | 19    |
|                        | 207      | 500, 500 | 1.92 | 30    |
|                        | 208      | 1A, 1A   | 3.30 | 38    |
|                        | 236      | 200, 200 | 1.43 | 19    |
|                        | 214      | 300, 300 | 1.93 | 30    |
|                        | 221      | 700(DC)  | 2.17 | 38    |
|                        | 206      | 1A, 1A   | 3.46 | 38    |
|                        | 1000     | MT250    | 3.00 | 38    |
|                        | 2000     | MT252    | 3.85 | 38    |

## MINIATURE TRANSFORMERS WITH SCREENS

| Ref. No. | MA       | Volts            | £    | p & p |
|----------|----------|------------------|------|-------|
| 238      | 200      | 3-0-3            | 1.54 | 10    |
| 212      | 1A, 1A   | 0-6, 0-6         | 1.84 | 30    |
| 13       | 100      | 9-0-9            | 1.41 | 13    |
| 235      | 330, 330 | 0-9, 0-9         | 1.56 | 19    |
| 207      | 500, 500 | 0-8-9, 0-8-9     | 1.92 | 30    |
| 208      | 1A, 1A   | 0-8-9, 0-8-9     | 3.30 | 38    |
| 236      | 200, 200 | 0-15, 0-15       | 1.43 | 19    |
| 214      | 300, 300 | 0-20, 0-20       | 1.93 | 30    |
| 221      | 700(DC)  | 20-12-0-12-20    | 2.17 | 38    |
| 206      | 1A, 1A   | 0-15-20, 0-15-20 | 3.46 | 38    |
| 1000     | MT250    | 0-15-27, 0-15-27 | 3.00 | 38    |
| 2000     | MT252    | 0-15-27, 0-15-27 | 3.85 | 38    |

## BRIDGE RECTIFIERS

| VA        | Ref. | £     | p & p |
|-----------|------|-------|-------|
| 50v       | 2A   | 30p   |       |
| 100v      | 2A   | 35p   |       |
| 200v      | 1A   | 40p   |       |
| 400v      | 4A   | 60p   |       |
| 600v      | 2A   | 45p   |       |
| PM7A6     |      | £2.35 |       |
| P & P 15p |      |       |       |

## POWER UNITS

A125 6-9v at 200mA in moulded case forming a 2 pin 5A plug £2.45 P & P 25p.  
CC12-05 Output Switched 3-4-5-6-7-5-9-12V at 500mA £4.08 P & P 30p.

## METERS

|                                     |        |
|-------------------------------------|--------|
| AVO 8 Mk 5                          | £50.80 |
| AVO 72                              | £19.75 |
| U4313*                              | £11.80 |
| U4315*                              | £13.85 |
| * (USSR) Inc. Steel Case P & P 95p. |        |

## CARBON FILM RESISTORS

±V 10 ohm-1 Mohm 90p per 100, inc. P & P.

## CAPACITORS

MINIATURE CERAMICS 22pf-0.047mfd 30p per doz.  
PAPER (Metal cased) 0.01-0.025-0.05-0.1mfd 85p per doz. P & P 15p

## MAINS KEYNECTORS

£3.25. P & P 25p.

## PLEASE ADD 25+ VAT

INCLUDING P & P.

## MAINS TIMER

Delay 1-30 minutes (Adjustable) £5.95. P & P 25p.

## ELECTROSIL AND

SEMICONDUCTOR STOCKIST

SEND STAMP FOR CAT.

# Barrie Electronics Ltd.

3, THE MINORIES, LONDON EC3N 1BJ

TELEPHONE: 01-488 3316/8

NEAREST TUBE STATIONS: ALDGATE & LIVERPOOL ST.

# SAXON

Money saving high performance audio equipment DIRECT FROM OUR OWN FACTORIES

## GUARANTEED TESTED HIGH PERFORMANCE MODULES—now better value than ever

**SA35 £6-60** Carriage free

35W RMS 25-50V  
7 transistors, 7 diodes


**SA50 £8-50** Carriage free

50W RMS 25-65V  
7 transistors, 7 diodes

**SA100 £12-50** Carriage free

100W RMS 45-70V  
10 transistors, 7 diodes

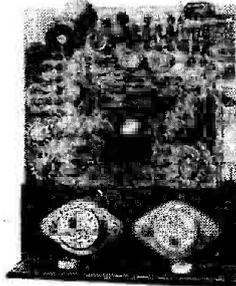- ★ 25Hz-25kHz
- ★ 0-2% distortion
- ★ Noise—80dB
- ★ 500mV into 20K
- ★ 4-16 ohms
- ★ Simple wiring
- ★ Short and open circuit proof
- ★ Continuously rated
- ★ Top-grade components



THE SA100 MODULE

## POWER SUPPLIES

### UNSTABILISED—READY WIRED & FUSED

**PU45** Suits 2 SA35 or 1 SA50 (4 ohm) **£6-50** Carriage 50p

**PU70** Suits 2 SA50 (8 ohm) or 2 SA100 **£9-50** Carriage 60p

### STABILISED

**PS45** Suits 2 SA35 or 2 SA50 (4 ohm) **£5-50** Carriage free

**MT45** Transformer for above **£3-90** Carriage 50p

**PS70** Suits 2 SA100 **£6-50** Carriage free

**MT70** Transformer or above **£5-50** Carriage 60p

N.B. PS70 is not suitable for the SA50

## Mk II STEREO DISCO MIXER £29-50

Carr. 60p

This well tried unit mixes two decks, handles any ceramic cartridge, and features mic over-ride plus separate full range bass and treble controls on both mic and deck inputs. Ample headphone power is available for P.F.L. May be used for mono and is mains operated. Fitted with sturdy screening case. Controls: Mic vol, base, treble. Left/Right fade, deck volume, bass, treble, h/phone select. vol, Mains. Size 17½in X 3in X 4in deep.



## DISCO MODULE £12-50

Carr. 50p

Thousands sold of this extremely popular mono version. A mic input may be fitted using the VA30 (see below). Low consumption from a 9V battery. Features the same high standards of reproduction as the Stereo version. Controls: H/phone select, vol, Left deck vol, Right deck vol, bass, treble, master vol. Size 12½in X 3in X 2in deep.



## 3-CHANNEL SOUND-LITE £24-75

Carr. 50p

Only SAXON can supply such incredible value for money. This unit features 3kW power handling, full-wave control, bass, middle, treble AND master controls. Twin loudspeaker jacks for "through" connections. It may be used free standing or will panel mount next to either of the above. Also features unique CUT-BACK circuitry for extra wide range response. Size 12in X 3in X 2½in deep. Professional standards at a price you can afford!



## SINGLE CHANNEL VERSION

£7-90

Carr. free

NOTE: ONLY 8% VAT TO BE ADDED TO ORDER VALUE

## MULTI-PURPOSE MIXERS


**M4HL**

£25-00 Carr. 60p

Featuring multiples of our VA30 module, the M4HL and M6HL fulfil the requirements of all clubs, groups, etc. where a high quality mixer is required. Each channel has one high and one low impedance input, plus volume, treble and bass controls. Input impedances may, if required, be easily changed. The M4HL has four channels, and one output, and the M6HL six channels (12 inputs) and a master control and two outputs. Either unit may be used free-standing or panel mounted. These mixers will feed all types of amplifier. Recommended for their versatility and high performance, and excellent value for money.

**M6HL**

£35-00 Carr. 60p

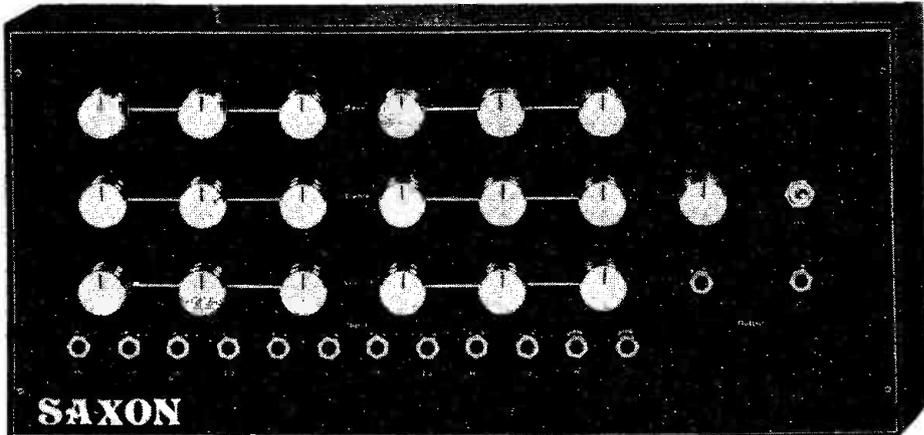

## VA30 CHANNEL MODULE £3-90

Carr. free

This is the basic channel module in the above mixers and may also be used for extra inputs on either the mono or stereo mixers. Fitted with volume, bass and treble controls, requires just a jack and supply (9-100V)


## SAXON CSE 100

COMPLETE AMPLIFIER

£39-90

Carr. 60p

100W of speech and music—two separately controlled inputs. Wide range bass and treble controls. Sturdy and attractive vinyl case. Twin outputs. Ideal for groups, discos, etc. Fully tested and guaranteed. 50W version identical in appearance

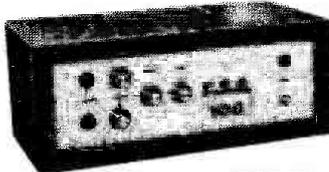

CSE50

£33-00 Carr. 60p

## NEW !!

**SAXON MULTIMIX 100 £57-00** carr. £1-00

100W rms four inputs slider controls plus master slider. Wide range bass and treble controls. Fantastic value, ideal for complete disco's, groups, clubs etc.

**SAXON MULTIMIX 50**—Exactly as above but 50W rms. £45-00

## CALLERS AND MAIL ORDER

# SAXON ENTERTAINMENTS LIMITED

327-331 WHITEHORSE ROAD · CROYDON CR0 2HS

(Please quote magazine when ordering)

SHOP HOURS: 9 a.m.-5 p.m. — LUNCH 12.30-1.30 p.m. MAIL ORDER DESK: 10 a.m.-3 p.m. 24-HOUR ANSWER SERVICE. TEL. 01-684 6385. TECHNICAL ENQUIRIES: 01-684 0098.

SEND 10p FOR OUR 26 PAGE MANUAL—full circuits & details.

TERMS OF BUSINESS: C.W.O. C.O.D. or ACCESS (just send in card number). Send 50p for C.O.D.

Please send S.A.E. with all enquiries.

VAT @ 8% must be added to all orders including carr. charges.

# Technological Poverty

**T**HE radio and electronic technician is expected to spend some years of his life in training and study to become qualified. He usually joins a professional society, such as The Society of Electronic and Radio Technicians, and continually updates his knowledge of radio and electronic science. He does this for love.

Compared to members of powerful trade unions, workers in all branches of technology have lost not only their salary differential above these workers but are in the majority of cases substantially *below* what these workers earn. A look at recent advertisements for technicians in this magazine tells the story: Wireless technician £40 to £46 pw, Laboratory technician grade 5 £42 to £49, Prototype wiremen £45 including overtime. Recent news items draw the comparison; to Chryslers workers £54.77 is a pittance, they want £70 per week, seamen *reject* 30% giving them £70 for their rather long week, dockers basic rises to £55 and average earnings will be £60 to £70 per week, and now the miners are talking about £100 per week in 1976.

Is it really so difficult to bolt bits of car together? To labour on a ship? To hump containers or coal? The results are beginning to show; hands up any prototype wiremen who are **not** self-employed. This is the only way these skilled electronic workers are able to make a decent living, supervised by technicians who are paid less. There is a chronic shortage of technicians which is not corrected by the law of supply and demand, because the professionally qualified engineers, physicists and chemists are in a similar position. Car builders, dockers and miners have caught them up and, in many cases, overtaken them. Low professional salaries hold the technicians back.

How has this situation come about? Firstly, integrated circuits have streamlined the design and subsequent maintenance of electronic equipment; secondly, lack of industrial investment has slowed the growth of automation and instrumentation; thirdly, the powerful unions insist on high manning levels and prevent investment in technology. All of this reduces the need for technological staff, and has given rise to a surplus at the professional level. By standing still British industry is rapidly becoming underdeveloped; nations with underdeveloped industry have little need for advanced technology. It comes as no surprise to technicians that universities, technical colleges and teachers training colleges are beginning to find a shortage of technical students.

What can the individual do about it? Some technicians have, like the prototype wiremen, become self-employed to gain extra money, tax relief on their cars and relief on travel to work. Some have come under the umbrella of powerful unions in printing works and similar establishments. Some have found employment in the EEC, USA, Canada, South Africa, Gulf States, Australia and New Zealand who all provide a much higher standard of living for technicians of all grades. Many 'moonlight' but the vast majority just put up with it and hope for better things in the future.

Those of us who are already qualified have a message for all the students about to study technology; in Britain today your certificate, diploma or degree in technology is a passport to poverty.

LIONEL E. HOWES—*Editor*

## NEWS...

### Radar Lights

**A**T the Mullard Research Laboratories, radars have been designed which can detect whether moving objects are advancing or receding. One of these has been applied to the control of portable traffic lights in a way which, at reasonable cost, gives the performance required by the Department of the Environment.

The radars are fitted to a pair of traffic lights and are interfaced with a control unit; they respond to traffic movement but not to irrelevant objects such as moving branches of trees.

The advantages of this system over conventional timed lights is that traffic is not held at 'stop' when no traffic is approaching from the other direction. At times when traffic is approaching from each direction the control unit shares the cycle time; the system ensures a steady flow of traffic at all times.

The system is now at the pre-production stage and production is planned to start very soon.

### Cramer Electronics

**M**OTOROLA has appointed Cramer Electronics to be a UK franchised distributor for its range of products.

Cramer has established its UK headquarters at Ealing (16 Uxbridge Road, Ealing, London W.5. Telephone No. 01-579 3001) with office and warehouse facilities. A complete range of Motorola products is available from stock and products manufactured by any of the more than 100 other top companies for which Cramer Electronics in the USA is franchised can be obtained. All products stocked in the USA are available in the UK within 48 hours, so Cramer inform us.

### "Radio Exchange"

Due to a printing error, the above advertiser's full-page advertisement space which appeared in the July issue, is incorrect. Prices quoted were at the old VAT rate. We apologise to all our readers for any inconvenience caused.

**PUBLISHER'S ANNOUNCEMENT**

THE content of PRACTICAL WIRELESS is fully protected by international copyright and reproduction of it in any form is prohibited without our consent. With effect from this announcement any application for permission to reproduce, or use our material in any way or part of, must be made to the Editor. Under no circumstances will permission be given to reproduce material in a similar or competitive publication, without payment. No application need be made in the case of a private constructor, constructing one item for his/her own enjoyment and interest.

**INTERFACE '75—TEXAS SEMINAR**

THURSDAY, 5th June, saw the 1975 Texas Instruments Ltd. Seminar at South Bank in London. The day started at 10.00 a.m. with a talk on Technology Trends in Integrated Circuits. This was followed by an updating on advanced digital circuits entitled New I.C. Products and their Applications.

The next very informative lecture was entitled Semiconductor Memories—it was a comparison of memory products in different systems; their reliability and system interface requirements; the reliability of programmable read-only memory (PROM); fusible links using the PROM in random logic applications, etc. New concepts in power devices were then discussed; high-speed Darlington transistors and their operation and the benefits of fast, slow-recovery high voltage rectifiers.

The following talk entitled Power Control discussed new Darlington transistors in deflection circuits for VDUs, economical switching regulated power supplies with multiple outputs and power control with triacs and thyristors in "touch-switching circuits".

The afternoon lectures started with a discussion on Scientific Calculator Developments—a review of advances in calculator techniques and the development from an initial 4-function chip to that of the latest complex scientific and statistical machines.

J-FETs and MOSFETs was the title of the next lecture and subjects covered were: low-noise J-FETs in audio and other applications, dual gate MOSFETs in tuner front ends and in a digital frequency display and FETs for switching circuits.

What makes a VLED bright? That was the question posed for a discussion entitled Operating Techniques with Visible Light Emitting Diodes. The physiological aspects of VLED brightness were covered together with various techniques used to optimise their efficiency and circuit considerations necessary to maximise visual response.

The last in the series of lectures was Microprocessor Units—an introduction to various MPU architectures. Trade-offs in technology versus complexity and performance were covered together with Schottky microprocessors and an I<sup>2</sup>L expandable 4-bit-slice MPU, MOS single and multi-chip microprocessors. Delegates were also shown how to build a 16-bit mini-computer from standard products.

All in all, this was yet another very successful and extremely well-attended Texas Instruments seminar. Exceedingly good value at the £16 plus VAT charge, for a good lunch was included together with wads of useful reference data and a copy of Semiconductor Circuit Design (which, by itself, costs £5). If you would like to know more about Texas Instruments components or be interested in attending next year's Seminar, please contact Richard Mann at Texas Instruments Limited, Manton Lane, Bedford, MK41 7PA.

**Bulk Buying**

ABOUT five years ago a buying group was formed among the small electronic component retailers. The main object was, and still is, to buy goods at cheaper rates by bulk buying.

The membership at present is 25 but for obvious reasons it would be better to enlarge it. There are not sufficient funds to advertise the group as total revenue is derived from a modest £6 a year subscription.

It's possible that there are other component retailers who may like to join this group and help us all by keeping the prices of components down.

Would those who may be interested please write to Alan Sproston, c/o Home Radio (Components) Ltd., 240 London Road, Mitcham, Surrey, CR4 3HD. Telephone 01-648 8422.

**Books received**

**Elements of Transistor Pulse Circuits**

By T. D. Towers

Expanded and updated coverage on digital microcircuits readily commercially available.

Price: £3.50

Butterworth & Company, 88 Kingsway, London, WC2B 6AB.

**Radio Servicing Pocket Book**

By Vivian Capel

A practical book for the radio service man. A lot of space is devoted to workshop planning and practice, test equipment, repair techniques and hints as well as fault diagnosis and quick economical repair etc.

Price: £1.95

Newnes-Butterworth, the Butterworth Group, 88 Kingsway, London, WC2B 6AB

**Television**

By K. Wicks

Shows basic principles of converting light into electricity, scanning and sound systems, the organisation of a TV studio. Shows developments and processes of TV which result in pictures.

McDonald Educational, St. Giles House, 49-50 Poland Street, London, W1A 2LG.

# DUAL CONVERSION receiver

PART: 1


F.G. RAYER

**T**O reduce second channel interference, it is necessary either to increase selectivity before the mixer or frequency-changer, or to use a higher intermediate frequency. If an RF stage is used to increase selectivity, the need for a number of coils, with switching and ganged tuning, is introduced. On the other hand, the high IF alone does not result in better selectivity.

The receiver described here seeks to avoid these difficulties by double conversion. It has a first IF of 5.5MHz to reduce second channel interference, followed by conversion to 465kHz, for improved selectivity. The choice of a first IF around 5.5MHz, combined with the fact that the oscillator may be above or below the received signal frequency, allows four amateur bands to be tuned, without any need for oscillator coil switching. This considerably simplifies construction.
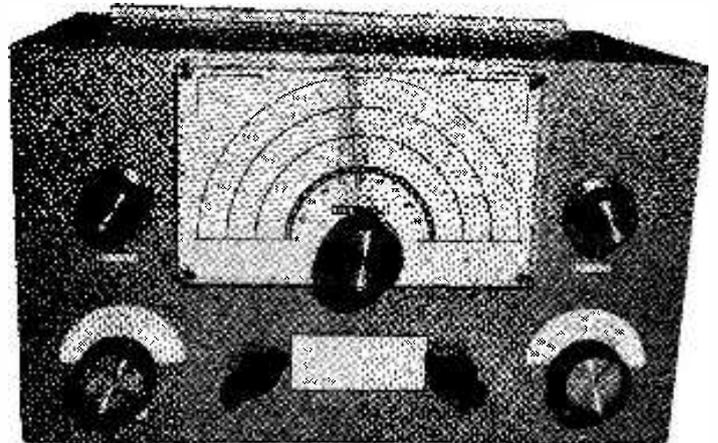
## AERIAL TUNING

The variable tuned circuits of the receiver are shown in Fig. 1. S1 to S4 are sections of the 4-way bandswitch. Only two aerial coils are required. L1 tunes 160m and 80m, while L2 covers 40m and 20m. Variable capacitor VC1 is the aerial tuning control which is peaked for best reception. There is no ganged tuning in the receiver.



Aerial socket A1 is for normal aerials, S1 switching to the required primary of L1 or L2. Socket A2 is for a short aerial, which is useful, as even a short indoor wire or rod will provide a considerable number of signals. The 5.5MHz trap is optional and can be added later. It is only needed in those circumstances where breakthrough around 5.5MHz is troublesome.

A small 365pF capacitor is used for VC1 but only about 250pF is required here. However, this capacitor, and similar midget ganged capacitors for transistor portables, can be easily obtained.

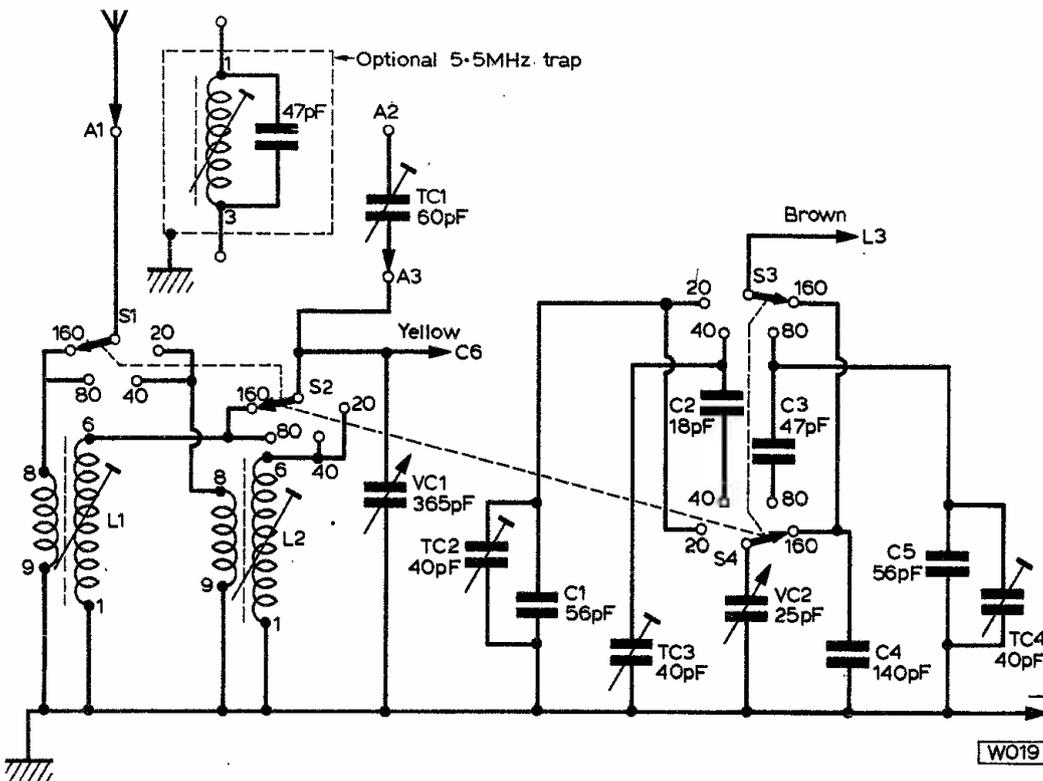


Fig. 1: Circuit of aerial and 500Hz tuned circuits.

# ★ components list

## Resistors

|     |       |     |       |
|-----|-------|-----|-------|
| R1  | 100kΩ | R18 | 2.2MΩ |
| R2  | 2.2kΩ | R19 | 8.2kΩ |
| R3  | 100kΩ | R20 | 2.7kΩ |
| R4  | 2.7kΩ | R21 | 1.2kΩ |
| R5  | 1MΩ   | R22 | 3.9kΩ |
| R6  | 5.6kΩ | R23 | 100Ω  |
| R7  | 1kΩ   | R24 | 56Ω   |
| R8  | 15kΩ  | R25 | 680Ω  |
| R9  | 2.7kΩ | R26 | 390Ω  |
| R10 | 120kΩ | R27 | 5.6Ω  |
| R11 | 47kΩ  | R28 | 5.6Ω  |
| R12 | 33kΩ  | R29 | 2.2kΩ |
| R13 | 330kΩ | R30 | 22kΩ  |
| R14 | 27kΩ  | R31 | 4.7kΩ |
| R15 | 390Ω  | R32 | 1kΩ   |
| R16 | 1.5kΩ | R33 | 2.7kΩ |
| R17 | 2.7kΩ |     |       |

All resistors are  $\frac{1}{4}$  or  $\frac{1}{2}$ W 10%  
 VR1 5kΩ linear potentiometer  
 VR2 10kΩ log. potentiometer

## Capacitors

|     |          |     |             |
|-----|----------|-----|-------------|
| C1  | 56pF*    | C17 | 6μF (6V)    |
| C2  | 18pF*    | C18 | 0.1μF       |
| C3  | 47pF*    | C19 | 0.01μF      |
| C4  | 140pF*   | C20 | 220μF (10V) |
| C5  | 56pF*    | C21 | 0.1μF       |
| C6  | 150pF    | C22 | 0.02μF      |
| C7  | 0.01μF   | C23 | 0.25μF      |
| C8  | 10pF     | C24 | 100μF (10V) |
| C9  | 5000pF   | C25 | 10μF (6V)   |
| C10 | 100pF    | C26 | 320μF (6V)  |
| C11 | 0.1μF    | C27 | 22μF (6V)   |
| C12 | 100pF 2% | C28 | 320μF (6V)  |
| C13 | 100pF 2% | C29 | 22μF (10V)  |
| C14 | 0.04μF   | C30 | 0.01μF      |
| C15 | 0.02μF   | C31 | 0.01μF      |
| C16 | 330pF 2% | C32 | 0.01μF      |

TC1 60pF compression trimmer  
 TC2 40pF ceramic or beehive trimmer  
 TC3 40pF ceramic or beehive trimmer  
 TC4 40pF ceramic or beehive trimmer  
 VC1 35pF variable (Jackson 01)  
 VC2 35pF variable (Jackson C804)  
 VC3 15pF variable (Jackson C804)  
 \* C1-C5 are 2% silver mica.

## Semiconductors

|     |        |      |       |
|-----|--------|------|-------|
| Tr1 | 40673  | Tr6  | BC107 |
| Tr2 | MPF102 | Tr7  | AC128 |
| Tr3 | BF194  | Tr8  | AC141 |
| Tr4 | BF195  | Tr9  | AC142 |
| Tr5 | BF195  | Tr10 | BC107 |
| D1  | OA91   |      |       |

## Miscellaneous

Aerial coils L1 and L2, Denco valve type 'Blue' Range 3 and 4 respectively. Oscillator coil L3, Denco valve type 'Red' Range 4. L4, Denco 'Red' range 4T. BFO coil L5, Denco IFT14. IFT1, Denco IFT15. IFT2, Denco IFT18/455. IFT3, Denco IFT18/465. IFT4, Denco IFT14. Optional 5.5MHz trap, Denco valve type 'White' Range 3 with 47pF silver mica capacitor. S1/S2/S3/S4, 4-pole 4-way rotary switch, single or double wiper. S5/S6, 2-pole 3-way switch. 3.5mm jack socket. 1st mixer and osc. board, plain perforated board 0.15in. matrix 51 x 57mm (2 x 2 $\frac{1}{4}$ in.). 2nd mixer and IF board, plain perforated board 0.15in. matrix 135 x 45mm (5 $\frac{1}{2}$  x 1 $\frac{1}{2}$ in.). Audio amplifier board, plain perforated board 0.15in. matrix 83 x 52mm (3 $\frac{1}{4}$  x 2in.). BFO board plain perforated board 0.15in. matrix 75 x 32mm (3 x 1 $\frac{1}{4}$ in.) Type W case 305 x 178 x 118mm (12 x 7 x 7in.) available from H. L. Smith & Co. Ltd. Chassis, four sided 254 x 152 x 31mm (10 x 6 x 2in.). Pair of panel brackets 102 x 100mm (4 x 4in.) Dial and drive, Type DL6 Home Radio.

## OSCILLATOR TUNING

VC2 tunes the oscillator coil L3 and is operated by a two-speed ball drive. For 160m C4 is across VC2 while on 80m C5 and TC4 are in use, with C3 in series with VC2. For the 40m band TC3 is across L1 with C2 in series with VC2. For 20m C1 and TC2 are in parallel with VC2 and L3.

The oscillator is HF of the signal frequency for 160, 80 and 40m, and LF of the signal frequency for 20m. With a 5.5MHz IF, the oscillator frequency coverage is as follows:

| Aerial Circuit       | Oscillator     |
|----------------------|----------------|
| 1.65—2.05MHz (160m)  | 7.15—7.55MHz   |
| 3.45—3.90MHz (80m)   | 8.95—9.40MHz   |
| 6.70—7.60MHz (40m)   | 12.20—13.10MHz |
| 13.90—14.60MHz (20m) | 8.40—9.10MHz   |

It is not necessary, of course, that the first IF is exactly 5.5MHz. When adjustment of the oscillator coil and trimmers is to be made, 160m is dealt with first, as C4 is fixed. With the bandswitch at 160m, L3 is adjusted until the swing of VC2 gives Top Band reception 1.8-2.0MHz. The switch is then set to 80m and TC4 adjusted to bring this band into the tuning range. In a similar way, TC3 is adjusted to bring in 40m, and TC2 for 20m.

## 1st MIXER/OSCILLATOR

The circuit of the 1st mixer and oscillator is shown in Fig. 2. When assembled, this board has flying leads and a chassis return, for connecting to the bandswitch, etc.

As Tr1 is a gate-protected device, assembly is straightforward. The oscillator coil L3 is on the board, and the same coil is used for the four bands,

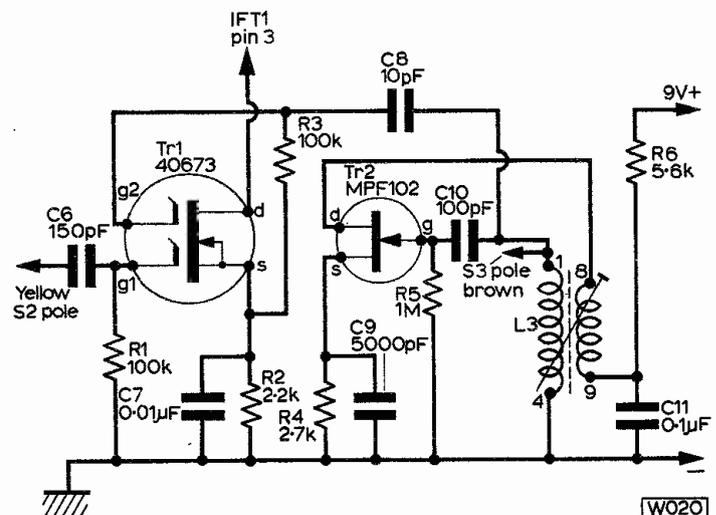


Fig. 2: First mixer and oscillator stages.

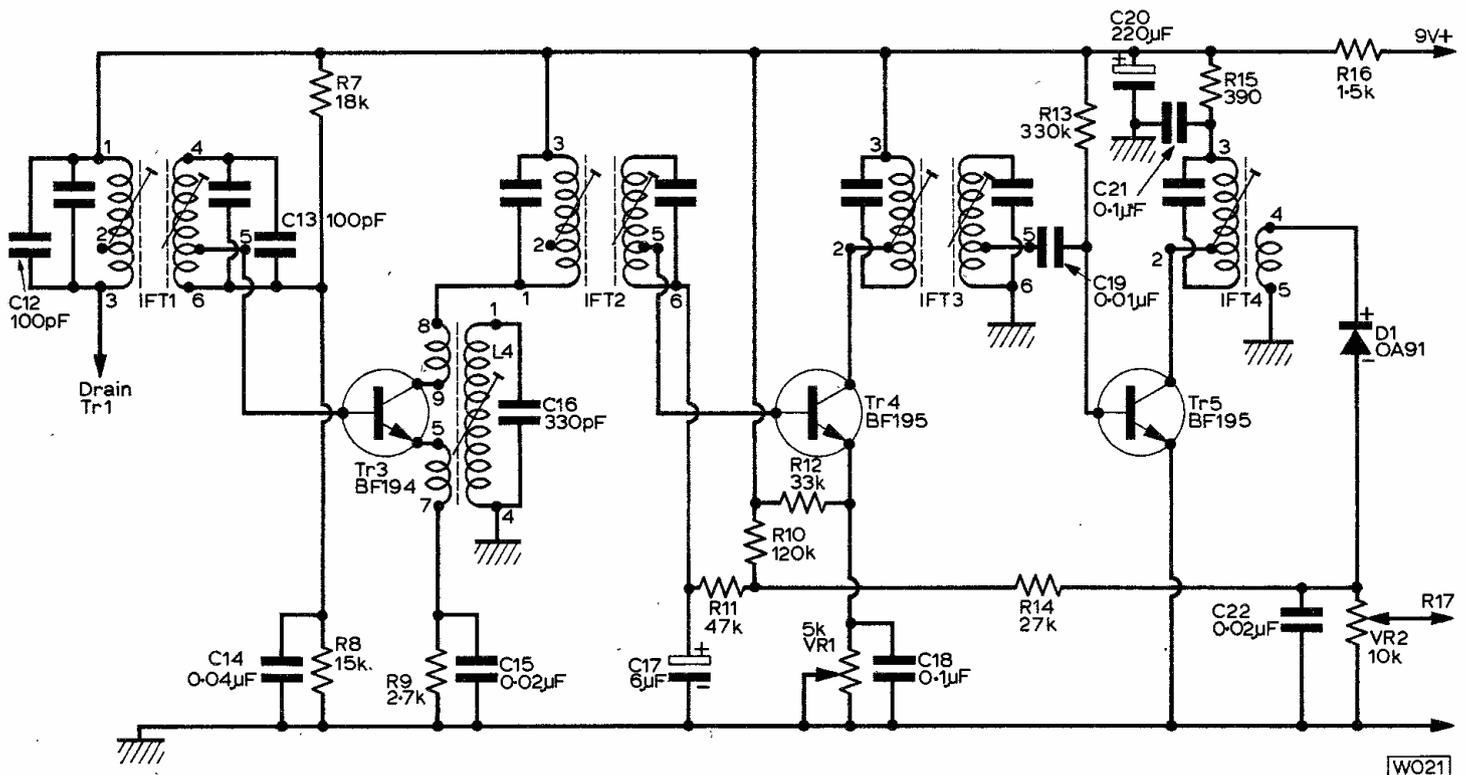


Fig. 3: Circuit diagram of the 5.5MHz IFT input circuit, 2nd mixer/oscillator, and 465kHz amplifier.

as described. The drain circuit of Tr1 passes to the primary of the 5.5MHz IF transformer mounted on the next board.

### 2nd MIXER AND IF

Fig. 3 shows this part of the receiver. IFT1 is a 10.7MHz IF transformer, loaded by C12 and C13 so that it can be tuned to 5.5MHz. As the extra capacitance needed here depends on the internal capacitors, different values might be necessary with other 10.7MHz IFT's. There are thus two circuits operating at 5.5MHz and the small screened transformer was found to be ideal here.

Tr3 is a self-oscillating mixer, with oscillator coil L4 and C16 in parallel. When L4 is correctly tuned, a 465kHz signal is fed for IFT2. Diode D1 provides

automatic gain control bias in the usual way, through R14. The gain of Tr4 is also controlled manually by VR1. This is essential, as strong signals will overload later stages, while the signal level will be too great for satisfactory SSB or CW operation.

The board for this section of the circuit also has flying leads and a pin for the positive connection. All components in Fig. 3, except VR1 and the volume control VR2, are present on this board.

### AUDIO AMPLIFIER

The amplifier is shown in Fig. 4, and is a transformerless circuit giving excellent gain and output. An IC or equivalent audio amplifier could no doubt be used, but the transistors are inexpensive and

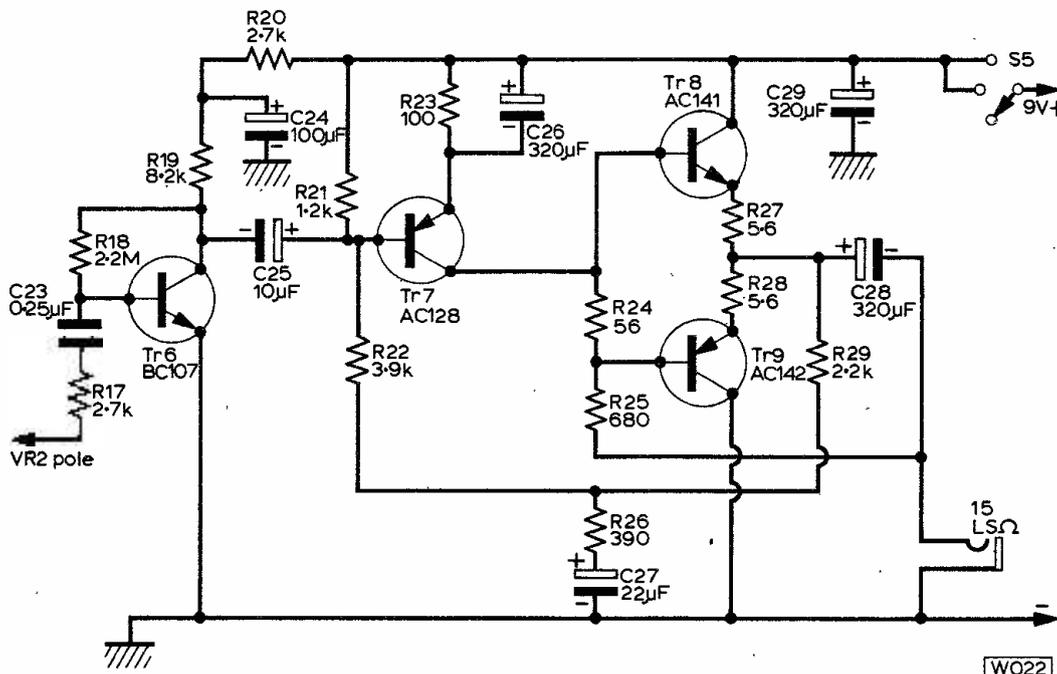



Fig. 4: Circuit of the four transistor audio amplifier. The loudspeaker impedance should be around 15Ω.

# New **BIGGER! BETTER!** DORAM
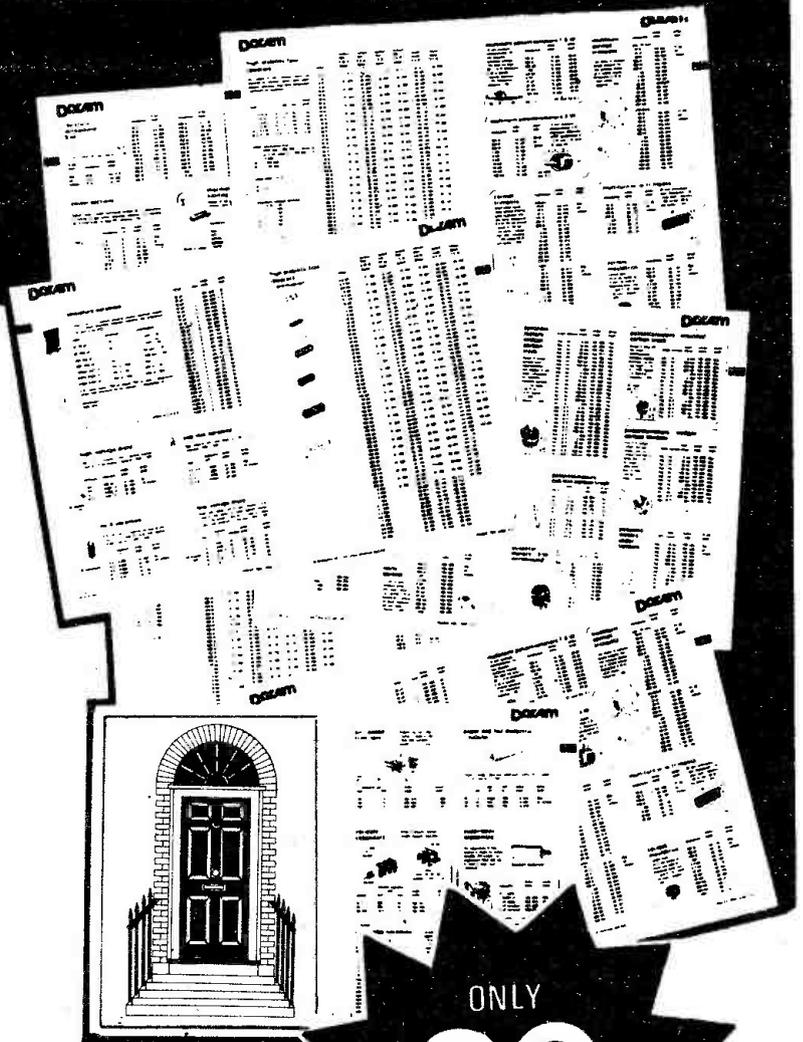
## CATALOGUE 2nd Edition

SPECIFICALLY DESIGNED FOR THE AMATEUR RADIO, ELECTRONICS AND HI-FI ENTHUSIAST.

- \* MUCH, MUCH BIGGER RANGE OF QUALITY ELECTRONIC COMPONENTS AND AUDIO ACCESSORIES FROM TRUSTED BIG NAME MANUFACTURERS
- \* THOUSANDS UPON THOUSANDS OF COMPONENTS – ILLUSTRATED, INDIVIDUALLY CODED AND PRICED. MANY NEW COMPONENTS ADDED FROM CUSTOMER REQUESTS
- \* 16 EXTRA PAGE DATA SECTION
- \* UNIQUE FREE UP-DATE PRODUCT INFORMATION SERVICE DURING LIFE SPAN OF CATALOGUE
- \* ALL COMPONENT REQUIREMENTS SENT BY RETURN POST
- \* POST AND PACKING FREE (only applies for Great Britain, N. Ireland plus B.F.P.O. Nos. – overseas orders F.O.B.)
- \* NO-QUIBBLE REPLACEMENT PART SERVICE



ONLY  
**60p**  
Inc. Post and Packing

*All this and more - so don't delay*

*send for  
your new  
catalogue  
TODAY!*

The doorway to amateur electronics

### DORAM

DORAM ELECTRONICS LIMITED  
P. O. Box TR8  
Leeds LS12 2UF

I enclose 60p. Please send me by return my new Doram Catalogue. (Overseas orders except for N. Ireland, please add 30p for post and packing surface only).

PLEASE PRINT BLOCK CAPITALS

PW8

NAME \_\_\_\_\_

ADDRESS \_\_\_\_\_  
\_\_\_\_\_  
\_\_\_\_\_

Post Code \_\_\_\_\_



# WILMSLOW AUDIO

**THE Firm for speakers!**

## SPEAKERS

|   |        |
|---|--------|
| Baker Group 25 3, 8 or 15 ohm             | £8.64  |
| Baker Group 35 3, 8 or 15 ohm             | £10.25 |
| Baker Group 50/12 8 or 15 ohm             | £14.00 |
| Baker Deluxe 12" d/cone                   | £13.75 |
| Baker Major "                             | £11.87 |
| Baker Regent "                            | £10.00 |
| Baker Superb "                            | £18.12 |
| Baker Auditorium 12                       | £16.25 |
| Celestion MH1000 horn, 8 or 15 ohm        | £10.95 |
| Celestion PS3 for Uniex                   | £3.75  |
| Celestion G12M 8 or 15 ohm                | £12.00 |
| Celestion G12H 8 or 15 ohm                | £15.00 |
| Celestion G15C 8 or 15 ohm                | £24.00 |
| Celestion G18C 8 or 15 ohm                | £33.00 |
| EMI 13 x 8" 150 d/c 8 ohm                 | £2.94  |
| EMI 13 x 8" type 350 8 or 15 ohm          | £9.56  |
| EMI 13 x 8" 20 watt base                  | £7.69  |
| EMI 6 1/2" 93850 4 or 8 ohm               | £4.37  |
| EMI 8 x 5 d/cone, roll surr 10 watt       | £3.44  |
| EMI 2 1/2" tweeter 97492AT                | .77    |
| Eagle DT33 30 watt tweeter                | £6.31  |
| Eagle HT15 horn tweeter                   | £4.40  |
| Eagle CT5 cone tweeter                    | £2.06  |
| Eagle CT10 tweeter 8 or 16 ohm            | £3.00  |
| Eagle MHT10 horn tweeter                  | £4.44  |
| Eagle crossover CN23, CN28, CN216         | £1.75  |
| Eagle FR4                                 | £6.12  |
| Eagle FR65                                | £9.12  |
| Eagle FR8                                 | £12.31 |
| Eiac 9 x 5, 59RM109 15 ohm, 59RM114 8 ohm | £3.44  |
| Eiac 6 1/2" 6RM171 d/c roll surr.         | £4.08  |
| Eiac 6 1/2" 6RM220 d/cone                 | £3.12  |
| Eiac 4" tweeter TW4                       | £1.75  |
| Eiac 10" d/cone 10RM239 8 ohm             | £3.12  |
| Eiac 8" 8CS175 3 ohm                      | £2.87  |
| Fane Pop 15 watt 12"                      | £5.25  |
| Fane Pop 25/2 25 watt 12"                 | £7.50  |
| Fane Pop 50 watt 12"                      | £12.00 |
| Fane Pop 55 60 watt 12"                   | £12.95 |
| Fane Pop 60 watt 15"                      | £13.75 |
| Fane Pop 100 watt 18"                     | £25.95 |
| Fane Crescendo 12A 100 watt 12"           | £34.50 |
| Fane Crescendo 12B bass                   | £36.50 |
| Fane Crescendo 100 watt 15"               | £47.50 |
| Fane Crescendo 150 watt 18"               | £62.95 |
| Fane 801T 8" d/c roll surr.               | £8.12  |
| Fane 807T 8" d/c roll surr.               | £4.62  |
| Fane 808T 8" d/c                          | £3.44  |
| Fane 701 twin ribbon horn                 | £40.00 |
| Fane 910 horn                             | £14.95 |
| Fane 920 horn                             | £33.95 |
| Goodmans 8P 8" or 15 ohm                  | £5.50  |
| Goodmans 10P 8 or 15 ohm                  | £5.80  |
| Goodmans 12P 8 or 15 ohm                  | £13.95 |
| Goodmans 12P-D 8 or 15 ohm                | £16.95 |

|  |        |
|--|--------|
| Goodmans 12P-G 8 or 15 ohm             | £15.95 |
| Goodmans Audiomax 12AX 100 watt        | £36.50 |
| Goodmans Audiomax 15AX                 | £40.25 |
| Goodmans 15P 8 or 15 ohm               | £21.00 |
| Goodmans 18P 8 or 15 ohm               | £36.00 |
| Goodmans Hidax 750                     | £16.00 |
| Goodmans Axent 100 tweeter             | £3.44  |
| Goodmans Audiom 100 12"                | £13.90 |
| Goodmans Axiom 401 12"                 | £20.00 |
| Goodmans Twinaxiom 8                   | £10.14 |
| Goodmans Twinaxiom 10                  | £10.75 |
| Kef T27                                | £6.06  |
| Kef T15                                | £6.94  |
| Kef B110                               | £8.37  |
| Kef B200                               | £9.50  |
| Kef B139                               | £16.50 |
| Kef DN8                                | £2.31  |
| Kef DN12                               | £5.75  |
| Kef DN13                               | £3.87  |
| STC4001G super tweeter                 | £6.56  |
| Richard Allan CG8T 8" d/c r/surr.      | £7.37  |
| 2 1/2" 64 ohm, 70mm 80 ohm, 70mm 8 ohm | .77    |
| 2 1/2" 75 ohm                          | .55    |
| 7" x 4" 3 or 8 ohm                     | £1.65  |
| 8" x 5" 3 or 8 ohm                     | £1.75  |
| 10" x 6" 3, 8 or 15 ohm                | £2.69  |

## SPEAKER KITS

|                            |             |
|----------------------------|-------------|
| Baker Major Module         | each £13.44 |
| Goodmans Mezzo Twinkit     | pair £47.19 |
| Goodmans DIN 20            | each £13.44 |
| Helme XLK 25               | pair £25.44 |
| Helme XLK 30               | pair £17.19 |
| Helme XLK 50               | pair £46.25 |
| Kefit 1                    | pair £48.44 |
| Kefit 3                    | each £42.50 |
| Richard Allan Twinkit      | each £10.37 |
| Richard Allan Triple 8     | each £15.94 |
| Richard Allan Triple 12    | each £23.15 |
| Richard Allan Super Triple | each £27.50 |
| Wharfedale Linton 2 kit    | pair £23.12 |
| Wharfedale Glendale 3 kit  | pair £40.60 |
| Wharfedale Dovedale 3 kit  | pair £63.12 |

## PA/DISCO AMPLIFIERS

|                       |        |
|-----------------------|--------|
| (carr. and ins. £1)   |        |
| Baker Major 100 watt  | £57.25 |
| Linear 30/40          | £30.00 |
| Linear 40/60          | £35.00 |
| Linear 80/100         | £58.95 |
| Linear 100 watt slave | £44.00 |

Eagle PA range in stock—ask for catalogue.

**Free with speaker orders over £7—**

"Hi-Fi Loudspeaker Enclosures" book. All units guaranteed new and perfect. Prompt despatch. Carriage and packing: speakers 38p each, 12" and up 50p each. Speaker kits 75p each (£1.50 pair) tweeters and crossovers 25p.

Including V.A.T. 25% on Hi Fi, 8% on PRO and PA

## WILMSLOW AUDIO (Dept. PW)

Loudspeakers: Swan Works, Bank Square, Wilmslow, Cheshire. SK9 1HF  
Discount Radio, PA, Hi-Fi: 10 Swan Street, Wilmslow  
Send stamp for free booklet "Choosing a Speaker"



## Cassettes

The best buy!

Agfa Low Noise Cassettes  
AT LESS THAN  
HALF PRICE!

AGFA HIGH DYNAMIC  
SUPER

AGFA STEREO-CHROM  
CHROMIUM DIOXIDE

|       | 1     | 5     | 10     |
|-------|-------|-------|--------|
| C60   | 40p   | £2.00 | £3.98  |
| C90   | 54p   | £2.70 | £5.38  |
| C120  | 75p   | £3.70 | £7.38  |
| C60+6 | 54p   | £2.70 | £5.35  |
| C90+6 | 70p   | £3.50 | £6.75  |
| C120  | 99p   | £4.95 | £9.85  |
| C60   | 90p   | £4.50 | £8.75  |
| C90   | £1.10 | £5.50 | £10.90 |

SAME DAY DESPATCH. P. & P. 15p per order

## WILMSLOW AUDIO

(DEPT. PW)  
10 SWAN STREET, WILMSLOW,  
CHESHIRE, SK9 1HF

Cut-price prerecorded cassettes—send stamp for list

## NEW SINCLAIR

# IC20

IC20 10+10W stereo amp  
lifer with free booklet and  
printed circuit £6.59  
(£1.99)  
PZ20 power supply kit for  
above £4.45 (£1.46)  
VP20 stereo volume, tone  
control and preamp kit  
£4.95 (£1.61)

## AMPLIFIERS

SEND SAE FOR FREE DATA BOOKLET

## SINCLAIR CALCULATORS

Scientific calculator assembled £15.61 (£1.57)  
Cambridge calculator assembled £10.97 (£1.13)  
Cambridge memory assembled £13.96 (£1.44)  
Oxford 100 £10.50 (£1.20), Oxford 200 £15.95  
(£1.70), Oxford 300 £23.95 (£2.40).

## CALCULATOR POWER SUPPLIES

Mains adaptor for Oxford series £2.65 (£1.04)  
Mains power unit for Cambridge, Cambridge Mem.  
and Scientific calcs £3.60 (£1.30)

## FERRANTI ZN414

IC radio chip with data £1.20 (49p). Also available  
kit of extra parts to complete a radio £2.55 (83p)  
Send sae for free leaflet

## SINCLAIR PROJECT 80

AFU £6.38 (£1.93)  
Z40 £4.97 (£1.58)  
Z60 £6.38 (£1.93)  
Q16 £6.70 (£2.17)  
PZ5 £4.62 (£1.59)  
PZ6 £7.41 (£2.28)  
PZ8 £7.25 (£2.20)  
Decoder £7.46 (£2.23). Trans for PZ8 £3.75  
(£1.41). Tuner £11.43 (£3.48). Stereo 80 £11.43  
(£3.48). Project 805 £29.95 (£8.27). Project 805SQ  
£36.95 (£9.70). Project 80 SQ Quad Decoder  
£16.50 (£4.47)  
Stereo 80/2 Z40/PZ5 £24.40 (£6.69)  
Stereo 80/2 Z40/PZ6 £26.70 (£7.37)  
Stereo 80/2 Z60/PZ8 £28.66 (£7.91)



## SINCLAIR IC12

With 44 page  
booklet and printed  
circuit £3 (£1.08)  
Special offer—  
Only £2.30 (90p) if  
ordered with de-  
luxe kit!



## DELUXE KIT FOR THE IC12

Includes all parts for the printed circuit and  
volume, bass and treble controls needed to  
complete the mono version £1.80 (64p). Stereo  
model with balance control £3.90 (£1.16).

## IC12 POWER KIT

Supplies 28V 0.5 Amps £3.27 (£1.44).

## PREAMP KITS FOR THE IC12

Type 1 for magnetic pickups, mics and tuners.  
Mono model £1.50 (57p). Stereo model £2.70 (86p)  
Type 2 for ceramic or crystal pickups. Mono 80p  
(39p). Stereo £1.60 (59p).

SEND SAE FOR FREE LEAFLET ON KITS


## BATTERY ELIMINATOR BARGAINS

The most versatile battery  
eliminator ever offered. Switched  
output of 3, 4 1/2, 6, 7 1/2, 9 and  
12V at 500 mA £3.90 (£1.55)  
Other eliminators stocked—  
2.50mA—3 way switched  
model 6/7 1/2/9V £2.50 (£1.05)  
50mA—6V £2.75 (£1.11), 9V £2.75 (£1.11), 7 1/2V  
cassette type £3.35 (£1.26), Double 4 1/2+4 1/2V  
£3.20 (£1.23), 6+6V £3.20 (£1.23), 9+9V £3.20  
(£1.23).  
500mA— Heavy duty models 6V £3.60 (£1.30),  
7 1/2V £3.60 (£1.30), 9V £3.60 (£1.30).


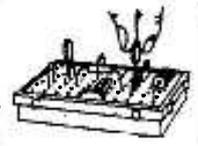
## S-DECS AND T-DECS


S-DeC £1.98 (36p)  
T-DeC £3.63 (52p)  
H-DeC A £3.99 (56p)  
H-DeC B £6.99 (86p)  
IC carriers—  
16 dill: plain 99p (19p)  
With socket £1.92 (28p)  
10 TO5: plain 90p (19p)  
With socket £1.80 (28p)


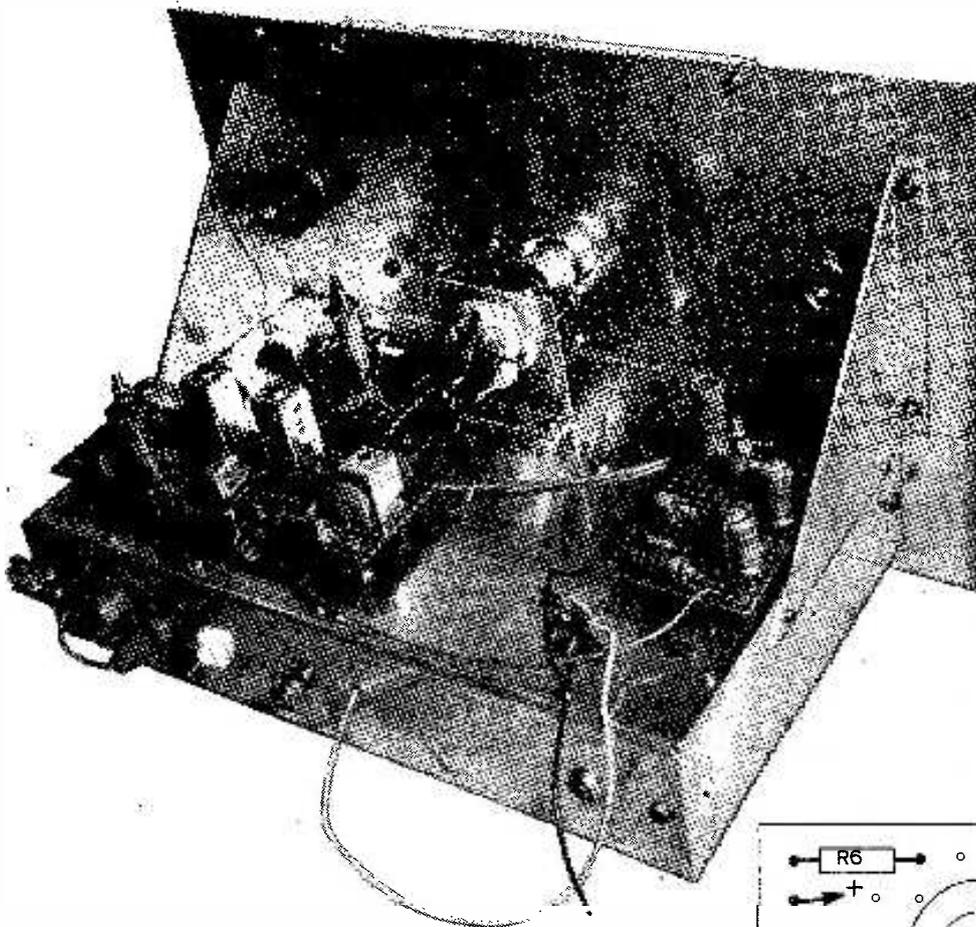
## SWANLEY ELECTRONICS

PO BOX 68, SWANLEY,  
KENT BR8 8TQ.

Please add the sum shown in brackets after the  
price to cover the cost of post and VAT.  
Official credit orders from schools etc welcome.  
No VAT charged on overseas orders.  
All prices are special offers ending 14th August.



Rear view photograph of the receiver, showing the layout of the boards, the mounting for the tuning capacitor and the various aerial sockets.

Fig. 5: below, drawing showing both sides of the first mixer and oscillator board.

easily obtained and the circuit perfectly straightforward. Tr6 gives high gain with low noise, while Tr7 and the output pair are directly coupled to stabilise DC conditions, with selective feedback through R29 and R22.



### FIRST MIXER BOARD

The method of wiring here is followed in the other circuit boards of the receiver. Plain perforated board, 0.15in. matrix, is used, approximately 51 x 57mm (2 x 2 1/4in). Fig. 5 shows both sides of the board.

Drill two holes for the 6BA bolts MC. The metal chassis can also be drilled at the same time, through these holes, so that no fitting difficulty arises later. Each bolt is 12.5mm (1/2in) long and has a tag forming the chassis return. When the board is finished, extra nuts hold it about 6mm (1/4in) clear of the chassis and nuts under the chassis lock it in position.

Holes are drilled for the pins of the oscillator coil L3 which is then fixed with adhesive. The resistors and capacitors are added as in Fig. 5. Bend the wire ends over, cut as needed and solder, keeping all connections and joints near the board so that there is no possibility of contact with the chassis. Insulated sleeving is put on wires which cross other leads.

As it is difficult to check the leads of Tr1 and Tr2 when these are fitted, short lengths of coloured insulated sleeving are put on these wires first. Brown is used for source, yellow for gate 1 of Tr1 with white for gate 2, and drain leads left bare. The devices are then positioned as in Fig. 5. Tr1 is gate-

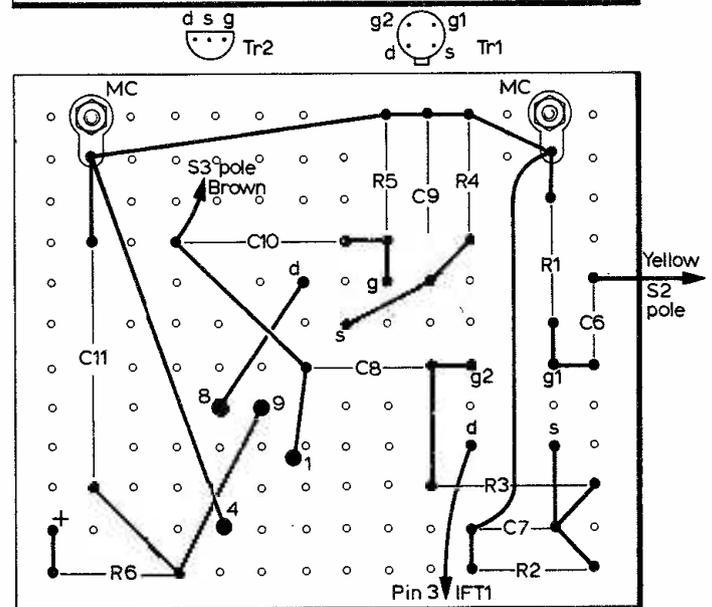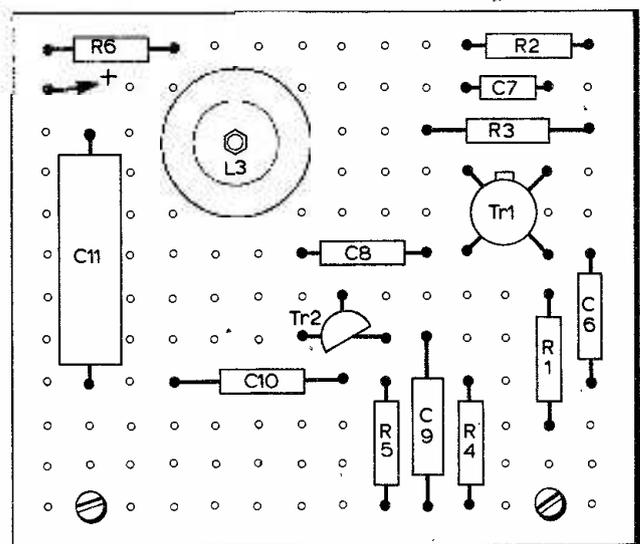

WO23

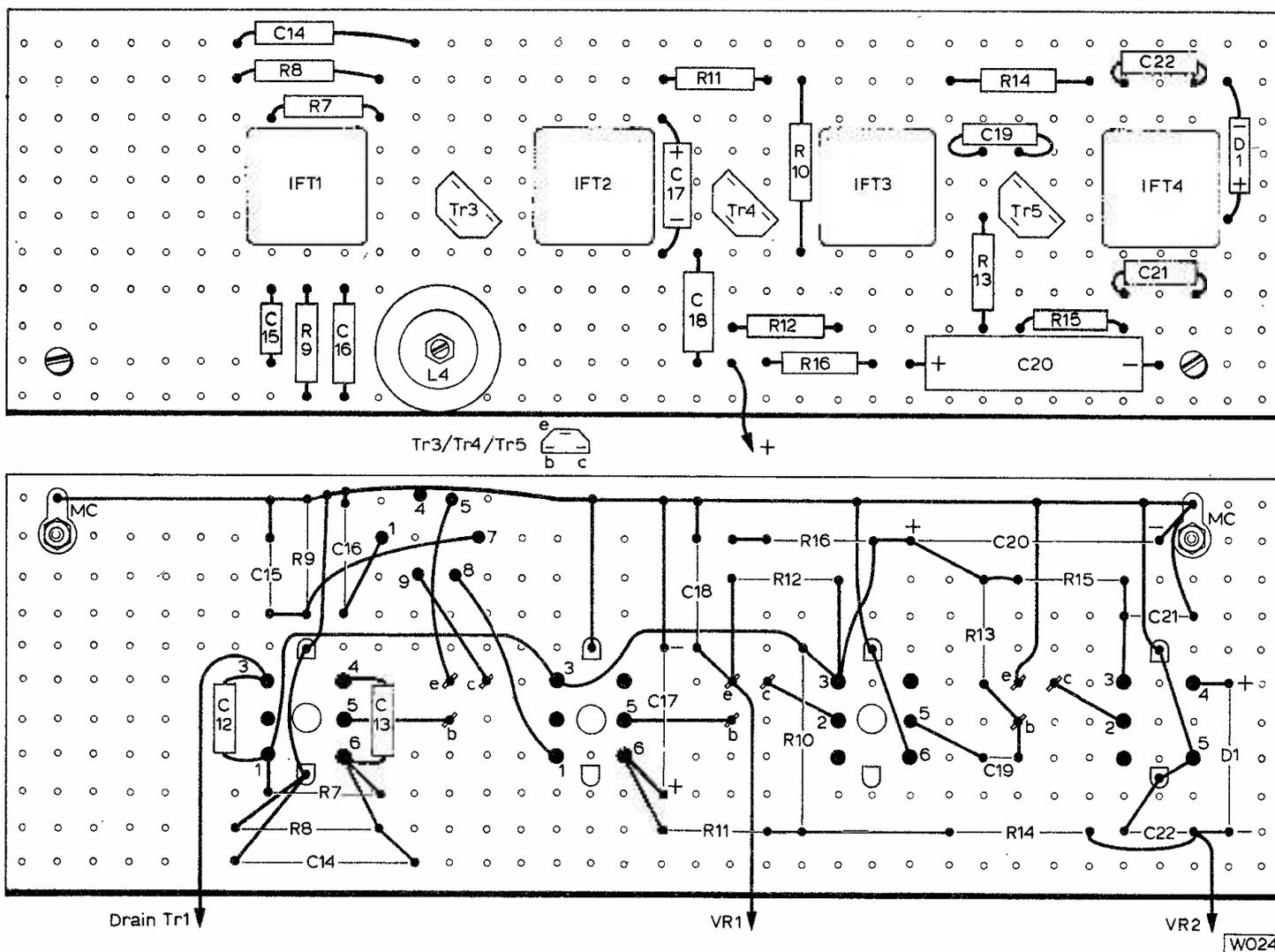


Fig. 6: Topside and underside views of the 2nd mixer/oscillator and 465kHz IF board.

protected, so that no special care is necessary when soldering, except for the usual caution to avoid lengthy and unnecessary heating.

A pin or flying lead is provided from R6, for the battery positive circuit. A wire (Yellow in Fig. 5) runs from C6, down through the chassis to the bandswitch together with a brown wire from pin 1 and C8 which is for oscillator tuning. On top of the chassis, a wire runs from D of Tr1, to pin 3 of IFT1. The chassis return is via the bolts mentioned.

If desired, this board can be tested by connecting up a 9V supply and using a receiver to note that the oscillator carrier can be found with the receiver on any of the oscillator frequencies mentioned.

## 2nd MIXER-IF BOARD


Fig. 6 shows both sides of this board. It is prepared by drilling for the four IFT's, bolts MC and second oscillator coil L4. Central holes are necessary under IFT1, 2 and 3 for trimming purposes. A very small round file may be helpful when making the holes as the IFT's and coil should fit without any strain on the pins.

All the IFT screening cans are connected to the chassis while C12 and C13 are directly across the windings of IFT1, below the board, as in Fig. 6.

Leave a pin or projecting wire of R16 for the positive supply as this is a junction point for other leads later. Flying leads are left for VR1 (from C18) and for VR2 (from C22). When the board is finished, the drain wire from Tr1 can be cut to a suitable length and soldered to pin 3, IFT1. Correctly positioned holes for the bolts MC are made by placing the board on the chassis before wiring it. Chassis holes are drilled to reach the cores of IFT1/2 and 3.

If desired, this board can be tested before fitting. To do this, leave pin 3 of IFT1 (drain) off, connect VR1 and VR2 and a 9V supply. The audio signal from VR2 can be taken to the audio amplifier or to phones via an isolating capacitor. As the 465kHz IFT's are pre-aligned, little or no adjustment should be necessary at this stage. A signal generator tuned to 5.5MHz can be temporarily coupled to pin 3 of IFT1, and L4 tuned until this is heard. The two cores of IFT1 can then be peaked up for best volume.

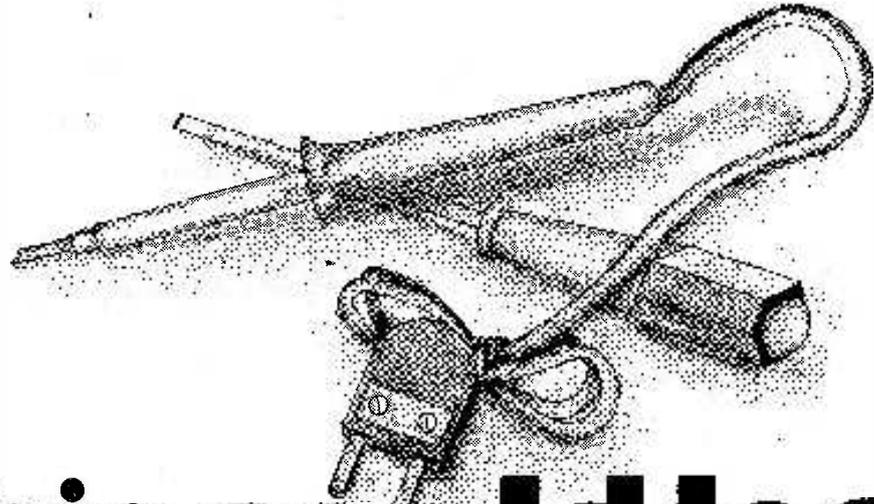**PART 2 NEXT MONTH GIVES FURTHER DETAILS OF THE BOARDS, GENERAL CONSTRUCTION OF THE CABINET, THE WIRING OF THE BAND-SWITCH AND THE ALIGNMENT PROCEDURE.**



# This could lead to something big.

A soldering iron and a screw driver. If you know how to use them, or at least know one end from the other, you know enough to enrol in our unique home electronics course.

This new style course will enable anyone to have a real understanding of electronics by a modern, practical and visual method. No previous knowledge is required, no maths, and an absolute minimum of theory.


You build, see and learn as, step by step, we take you through all the fundamentals of electronics and show you

how easily the subject can be mastered and add a new dimension not only to your hobby but also to your earning capacity.

This course is accepted by and used in a large number of schools and colleges and forms an invaluable grounding for professional training in the subject. All the training is planned to be carried out in the comfort of your own home and work in your own time. You send them in when you are ready and not before. These culminate in a final test and a certificate of success.

**1**

## Build an oscilloscope.

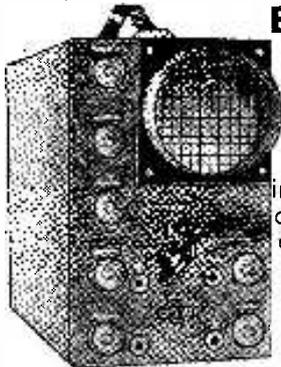

As the first stage of your training, you actually build your own Cathode ray oscilloscope! This is no toy, but a professional test instrument that you will need not only for the course's practical experiments, but also later if you decide to develop your knowledge and enter the profession. It remains your property and represents a very large saving over buying a similar piece of essential equipment.

**2**


## Read, draw and understand circuit diagrams.



In a short time you will be able to read and draw circuit diagrams, understand the very fundamentals of television, radio, computers and countless other electronic devices and their servicing procedures.

**3**
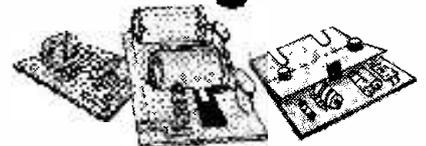
## Carry out over 40 experiments on basic circuits.



We show you how to conduct experiments on a wide variety of different circuits and turn the information gained into a working knowledge of testing, servicing and maintaining all types of electronic equipment, radio, t.v. etc.

**PLUS**



## FREE GIFT!

ALL STUDENTS ENROLLING IN OUR COURSES RECEIVE A FREE CIRCUIT BOARD ORIGINATING FROM A COMPUTER AND CONTAINING MANY DIFFERENT COMPONENTS THAT CAN BE USED IN EXPERIMENTS AND PROVIDE AN EXCELLENT EXAMPLE OF CURRENT ELECTRONIC PRACTICE

To find out more about how to learn electronics in a new, exciting and absorbing way, just clip the coupon for a free colour brochure and full details of enrolment.

Brochure without obligation to:

**BRITISH NATIONAL RADIO & ELECTRONICS SCHOOL, Dept WL/85**

**P.O. Box 156, Jersey, Channel Islands.**

NAME.....

ADDRESS.....

(Block caps please)



GIRO NO. 331 7056. Access accepted.  
C.W.O. only P. & P. 15p on orders below £5  
Discount: £10-10% (except net items)  
Export Order enquiries welcome (VAT free)

Official Orders accepted from  
Educational & Government Departments  
ALL PRICES INCLUDE VAT AT 8%

PLEASE ADD AN EXTRA 15% VAT EXCEPT ON TEST METERS, AND VEROBOARD  
SPECIAL RESISTOR KITS (Prices include post & packing)

10E12 ½W KIT: 10 of each E12 value, 22 ohms—1M, a total of 570 (CARBON FILM 5%), £3.85 net  
25E12 ½W KIT: 25 of each E12 value, 22 ohms—1M, a total of 1425 (CARBON FILM 5%), £9.00 net

Due to current world shortages, resistor kits may contain some wattage and value substitutions.

**MULLARD POLYESTER CAPACITORS C280 SERIES**  
250V P.C. Mounting: 0.01µF, 0.015µF, 0.022µF, 0.033µF, 0.047µF, 3½p, 0.068µF, 0.1µF, 4½p, 0.15µF, 5p, 0.22µF, 6p, 0.33µF, 8p, 0.47µF, 10p, 0.68µF, 13p, 1µF, 16p, 1.5µF, 24p, 2.2µF, 27p.

**MULLARD POLYESTER CAPACITORS C296 SERIES**  
400V: 0.001µF, 0.0015µF, 0.0022µF, 0.0033µF, 0.0047µF, 3p, 0.0068µF, 0.01µF, 0.015µF, 0.022µF, 0.033µF, 3½p, 0.047µF, 0.068µF, 0.1µF, 4½p, 0.15µF, 7p, 0.22µF, 9p, 0.33µF, 13p, 0.47µF, 15p.  
160V: 0.01µF, 0.15µF, 0.022µF 3½p, 0.047µF, 0.068µF, 4p, 0.1µF, 4½p, 0.15µF, 5½p, 0.22µF, 6p, 0.33µF, 7p, 0.47µF, 9p, 0.68µF, 13p, 1µF, 15p.

**MINIATURE CERAMIC PLATE CAPACITORS**  
50V: (pF) 22, 27, 33, 39, 47, 56, 68, 82, 100, 120, 150, 180, 220, 270, 330, 390, 470, 560, 680, 820, 1K, 1K5, 2K2, 3K3, 4K7, 6K8, (µF) 0.01, 0.015, 0.022, 0.033, 0.047, 2½p, each, 0.1, 30V, 5p.

**POLYSTYRENE CAPACITORS 160V 5%**  
(pF) 10, 15, 22, 33, 47, 68, 100, 150, 220, 330, 470, 680, 1000, 1500, 2200, 3300  
4700, 6800, 10,000, 4½p.

**RESISTORS**

| W. Type | Range  | 1-99 | 100-499 | 500-999 | 1000+ | Size mm  |
|---------|--------|------|---------|---------|-------|----------|
| CF      | 22-1M  | 1    | 0.80    | 0.65    | 0.60  | 2.4x7.5  |
| CF      | 22-2M2 | 1    | 0.80    | 0.65    | 0.60  | 3.9x10.5 |
| CF      | 22-1M  | 1    | 0.80    | 0.65    | 0.60  | 5.5x16   |
| MF      | 10-2M7 | 2    | 1.7     | 1.4     | 1.1   | 4.2x10.8 |
| MF      | 10-2M2 | 2    | 1.6     | 1.3     | 1.1   | 3x7      |
| MF      | 10-10M | 3    | 1.98    | 1.81    | 1.65  | 6.6x13   |
| MF      | 10-10M | 4.5  | 3.52    | 3.08    | 2.75  | 8x17.5   |

(Price in pence each).

VALUES AVAILABLE—E12 Series only. (Net prices above 100.)

**PRESET SKELETON POTENTIOMETERS**

MINIATURE 0.25W Vertical or horizontal 7p each 1K, 2K2, 4K7, 10K, etc. up to 1M Ω  
SUB-MIN 0.05W Vertical, 100 Ω to 220K Ω 7p each.



**B. H. COMPONENT FACTORS LTD.**

(P.W.) LEIGHTON ELECTRONICS CENTRE,  
59 NORTH ST., LEIGHTON BUZZARD, BEDS.  
Tel.: LEIGHTON BUZZARD 2316 (STD. Code 05253)  
CATALOGUE No. 4 20p

**Miniature Mullard Electrolytics**

|           |     |             |     |
|-----------|-----|-------------|-----|
| 1.0µF 63V | 7p  | 100µF 25V   | 7p  |
| 1.5µF 63V | 7p  | 100µF 63V   | 17p |
| 2.2µF 63V | 7p  | 150µF 16V   | 7p  |
| 3.3µF 63V | 7p  | 150µF 63V   | 17p |
| 4.0µF 40V | 7p  | 220µF 6.4V  | 7p  |
| 4.7µF 63V | 7p  | 220µF 10V   | 7p  |
| 6.8µF 63V | 7p  | 220µF 16V   | 8p  |
| 10µF 25V  | 7p  | 220µF 63V   | 25p |
| 10µF 63V  | 7p  | 330µF 16V   | 14p |
| 15µF 16V  | 7p  | 330µF 63V   | 28p |
| 15µF 63V  | 7p  | 470µF 6.4   | 25p |
| 16µF 40V  | 7p  | 470µF 40V   | 25p |
| 22µF 25V  | 7p  | 680µF 16V   | 17p |
| 22µF 63V  | 7p  | 680µF 40V   | 28p |
| 32µF 10V  | 7p  | 1000µF 16V  | 25p |
| 33µF 16V  | 7p  | 1000µF 25V  | 28p |
| 33µF 40V  | 7p  | 1500µF 6.4V | 17p |
| 47µF 10V  | 7p  | 1500µF 16V  | 28p |
| 47µF 25V  | 7p  | 2200µF 10V  | 28p |
| 47µF 63V  | 8p  | 3300µF 6.4V | 28p |
| 68µF 16V  | 7p  |             |     |
| 68µF 63V  | 14p |             |     |
| 100µF 10V | 7p  |             |     |

**VEROBOARD 0.1 0.15**

|                  |         |
|------------------|---------|
| 2½ x 5"          | 36p 36p |
| 2½ x 3½"         | 33p 25p |
| 3½ x 5"          | 42p 26p |
| 3½ x 3½"         | 36p 36p |
| 2½ x 1"          | 10p 9p  |
| 2½ x 5" (Plain)  | — 19p   |
| 2½ x 3½" (Plain) | — 16p   |
| 5 x 3½" (Plain)  | — 29p   |
| Insertion tool   | 73p 73p |
| Track Cutter     | 56p 56p |
| Pins, Pkt. 50    | 22p 22p |

**TRANSISTORS**

|        |     |        |     |
|--------|-----|--------|-----|
| AC127  | 21p | BC212L | 13p |
| AC128  | 22p | BC213L | 13p |
| BC107  | 12p | BC214L | 18p |
| BC108  | 12p | OC44   | 19p |
| BC109  | 13p | OC71   | 13p |
| BC148  | 13p | OC81   | 17p |
| BC149  | 13p | OC170  | 29p |
| BC182L | 13p | 2N2926 | 13p |
| BC183L | 13p | 2N3702 | 14p |
| BC184L | 14p |        |     |

**POTENTIOMETERS**

Carbon Track 5K Ω to 2M Ω, log or lin (and 1K lin). Single, 17p Dual Gang 48p. Log single with switch 28p. Slider Pots. 10K, 100K, 500K, semi log 30mm, 34p, 45mm, 47p, 60mm, 55p.

**DIODES**

|        |     |                |     |
|--------|-----|----------------|-----|
| IN4001 | 6p  | DIN 2 Pin      | 12p |
| IN4002 | 7p  | 3 Pin          | 13p |
| IN4003 | 9p  | 5 Pin 180°     | 16p |
| IN4004 | 90p | Std. Jack      | 20p |
| IN4005 | 12p | 2.5mm jack     | 13p |
| IN4006 | 14p | Phono          | 7p  |
| IN914  | 7p  | <b>SOCKETS</b> |     |
| IN916  | 7p  | DIN 2 Pin      | 10p |
| BA100  | 10p | 3 Pin          | 10p |
| OA5    | 42p | 5 Pin 180°     | 12p |
| OA47   | 9p  | Std. Jack      | 18p |
| OA81   | 11p | 2.5mm jack     | 13p |
| OA200  | 8p  | Phono          | 7p  |

**PLUGS**

|            |     |
|------------|-----|
| DIN 2 Pin  | 12p |
| 3 Pin      | 13p |
| 5 Pin 180° | 16p |
| Std. Jack  | 20p |
| 2.5mm jack | 13p |
| Phono      | 7p  |

**ELECTROLYTIC CAPACITORS. Tubular & Large Cans**

(µF/V): 1/25, 2/25, 4/25, 4.7/10, 5/25, 8/25, 10/10, 10/50, 16/25, 22/63, 25/25, 25/50, 32/25, 50/25, 100/10, 100/25, 7p, 50/50, 8p, 100/50, 200/25, 10p, 250/50, 18p, 500/10, 8p, 500/25, 17p, 500/50, 25p, 1000/10, 17p, 1000/25, 25p, 1000/50, 40p, 2000/10, 20p, 1000/100, £1.10, 2000/25, 35p, 2000/100, £1.20, 2500/25, 38p, 2500/50, 68p, 5000/25, 69p, 5000/50, £1.20.  
**HI-VOLT:** 4/350, 20p, 8/350, 23p, 100/100 27p, 16/350, 35p, 100/100, 27p, 100/250, 40p.  
**METALLISED PAPER CAPACITORS**  
250V: 0.05µF, 0.1µF, 6p, 0.25, 6p, 0.5µF, 7½p, 1µF, 9p, 500V: 0.025, 0.05, 6p, 0.1, 6p, 0.25, 7½p, 0.5, 9p, 1000V: 0.01, 12p, 0.022, 13p, 0.047, 0.1, 19p, 0.22, 28p, 0.47, 36p.

**PLEASE NOTE OUR NEW ADDRESS**  
Our new Electronics Centre is now open in Leighton Buzzard and all callers are welcome. As well as our normal stock of over 2000 product lines, we have a large range of surplus equipment, Bargains, Calculators, etc. **OPEN 6 DAYS 9 to 5 (shut 12.30 to 1.30).**

**NEW KIT**  
5E12 ½W Metal Film.  
5 each value 10Ω-1M,  
total of 305 £3.75 net.

**MULTIMETER U4323**  
22 Ranges plus AF/IF Oscillator 20,000Ω/Volt.  
Vdc—0.5—1000V in 7 ranges  
Vac—2.5—1000V in 6 ranges  
Idc—0.05—500mA in 5 ranges  
Resistance—5Ω—1MΩ in 4 ranges.  
Accuracy—5% of F.S.D.  
**OSCILLATOR**—1 KHz and 465 KHz (A, M.) at approx. 1 Volt.  
Size—160 x 97 x 40mm.  
Supplied complete with carrying case, test leads and battery.  
PRICE £8.64 net p & p 50p.



U4323

**MULTIMETER U4341**  
27 Ranges plus Transistor Tester. 16,700Ω/Volt. Overload protected.  
Vdc—0.3—900V in 8 ranges.  
Vac—1.5—750V in 6 ranges.  
Idc—0.06—600mA in 5 ranges.  
Iac—0.3—300mA in 4 ranges.  
Resistance—2KΩ—2MΩ in 4 ranges.  
Accuracy—dc—2½%, ac—4% of F.S.D.  
hfe—10—350 in 2 ranges.  
Size—115 x 215 x 90mm.  
Complete with steel carrying case, test leads, and battery.  
PRICE £11.88 net p & p 50p.



U4341

**MULTIMETER U4324**  
34 Ranges. High sensitivity. 20,000Ω/Volt. Overload protected.  
Vdc—0.6—1200V in 9 ranges.  
Vac—3—900V in 8 ranges.  
Idc—0.06—3A in 6 ranges.  
Iac—0.3—3A in 5 ranges.  
Resistance—25Ω—5MΩ in 5 ranges.  
Accuracy—dc and R—2½% of F.S.D. ac and db—4% of F.S.D.  
Size—167 x 98 x 63mm.  
Supplied complete with storage case, test leads, spare diode, and battery.  
PRICE £10.64 net p & p 50p.



U4324

**MULTIMETER U4313**  
33 ranges. Knife edge with mirror scale. 20,000Ω/Volt. High accuracy. mVdc—75mV  
Vdc—1.5—600V in 9 ranges.  
Vac—1.5—600V in 9 ranges.  
Idc—60—120 microamps in 2  
Idc—0.6—1500mA in 6 ranges.  
Iac—0.6—1500mA in 6 ranges.  
Resistance—1KΩ—1MΩ in 4 ranges.  
db scale—10 to + 12db.  
Accuracy—dc—1½%, ac—2½%  
Size—115 x 215 x 90mm.  
Complete with steel carrying case, test leads, and battery.  
PRICE £14.90 net p & p 50p.



U4313

**HAVE YOU GOT YOURS**

66 PAGES  
3000 ITEMS  
600 PICTURES

YOUR COMPLETE ELECTRONIC STORES, MAIL ORDER AND SHOP

★ DISCOUNTS  
★ ALL NEW STOCK  
★ SATISFACTION GUARANTEE  
★ DEPENDABLE SERVICE

CATALOGUE NO. 4  
NEW CONVENIENT SIZE, AND FULLY ILLUSTRATED.

CONTAINS MANY HARD TO GET ITEMS

20p

PAYS FOR ITSELF WITH DISCOUNT VOUCHERS WORTH 20p

**VALVE BARGAINS**  
Any 5 64p, 10 99p, 50 £4.15,  
Your choice from the following list:  
ECC82, ECL80, EB91, EF80, EF183, EF184, PC86, PC88, PC97, PC900, PCC84, PCC89, PCC189, PCF80, PCF802, PCF805, PCL82, PCL84, PCL85, PCL805, PCL86, PFL200, PL38, PL504, PY33, PY81, PY800, PY88, EH90, 30FL1, 30FL2, 30PL14  
**Colour Valves 30p each**  
PL508, PL509, PY500/A  
**Press 4 Button UHF Tuners £2.90.**  
Prices include V.A.T. P. & P. under £1/15p, £1 to £3/20p over £3/25p.  
**ELECTRONIC MAILORDER LTD., 62 Bridge Street, Ramsbottom, Bury, Lancs 1.**

**AERIAL BOOSTERS**  
We make three types of Aerial Boosters all for set top fitting, with Co-ax Plugs and Sockets.  
**B11—For Stereo and Standard VHF Radio**  
**B12—For the older VHF Television, please state BBC1 & ITV Channels.**  
**B45—For mon. or colour this covers the complete UHF band.**  
All Boosters are complete with Battery and take only minutes to fit.  
**Price £3.90 each**

**ELECTRONI-KIT**

"... educational kits of exceptional quality"  
(AUDIO mag. Dec. 1974)

**BUILD AND REBUILD ANY NUMBER OF TIMES:**  
Radios, microphones, burglar alarms, inter-comms, ferrite detectors, solar cell, photoelectric cell, voice relay, electronic cats, birds, guns, organs, illuminometers, voltmeters, meters of all types, etc., etc., plus your own circuit designs.  
**COMPLETELY SAFE**—suitable for all, from beginners on. 30 different projects £10.45, 100 different projects £20.45, over 150 £33.95. Add-on kits, spares, available too.  
Prices include Manuals, Battery, p & p, VAT, etc. Cheque/PO (or 11p for catalogues) to DEPT. PW:

Satisfaction guaranteed.  
**ELECTRONI-KIT LTD, 408 St. John's Street, London, EC1. (01-278 4579)**

# Pw APOLLO series

## Part 4

# VARICAP AM/FM STEREO TUNER (CONSTRUCTION & ALIGNMENT)

W. POEL\*

**I**N THIS, the final part of the P.W. Apollo series, we will look at the construction of the AM/FM Varicap Tuner which was discussed theoretically in Part 3.

### CONSTRUCTION

Whenever making a project that employs an integrated circuit, it is always advisable to familiarise oneself with the device from the manufacturer's data sheet. So much has been published on the CA3089E and the stereo decoder that a great deal of knowledge and experience is readily available on their usage.

Integrated circuits need printed circuit boards for radio frequency applications. Veroboard and the like will not suffice for best results, so follow precisely the etching patterns shown in this article or obtain p.c.b.s ready-made before starting the project.

The base board layout allows simple construction practice so follow details for each module and the final assembly will present no difficulties.

### THE TUNERHEAD

The tunerhead is available pre-aligned and tested. The resources for manufacturing such an item are generally beyond the average constructor. The only point to note is that the tuning bias supply is externally decoupled with an additional electrolytic capacitor of approximately  $10\mu\text{F}$  and that this capacitor is soldered to the lugs as shown in Fig. 4.8.

### THE FM IF AMPLIFIER

Again, since it was felt that the construction of an FM IF strip with only 0.1 per cent THD may be beyond the technical resources of the average constructor a standard unit that is also available ready-built was chosen. However, for the more experienced constructor a kit is also available.

The IF linear phase blocks are pre-aligned and require only a minimum of trimming to ensure best

results and this should be no more than a single turn of the input and output transformer cores.

The p.c.b. pattern is shown ready for copying (Fig. 4.1) and also with the components superimposed for positioning (Fig. 4.2). The leadout from the module is taken via some p.c.b. pins to the mother board but there are also some minor modifications to accommodate the switch for the muting circuit so that this function can be defeated when searching around for a weak station.

With the EC3302U tunerhead the a.g.c. facility is not operational though if a tunerhead such as the Larsholt 8319/8321 or the Toko EF5600K were used, this could then be employed by making the appropriate connection. However, the a.g.c. is not a facility that will be missed much in most locations in Britain. Modern limiting amplifiers, especially when preceded by an eight pole filter, will not be adversely affected by its omission.

When soldering always use an iron of adequate heat capacity and remember that more faults occur through "under soldering" than through components damaged by too much heat. Even the IC will not be affected by the amount of heat it takes to leave a really complete smooth and shiny soldered joint.

The pins that are used to fit the module to the mother board can be made from 20 s.w.g. tinned copper wire if desired. Just bend the top across to prevent the pins from dropping through whilst being soldered. The quadrature detector coil can be either single or double tuned as previously mentioned. Provision is made on the board for the use of a single KACSK 586HM, and this transformer can then be aligned without anything more complex than a voltmeter. Full details are given in the section on testing and alignment.

### THE STEREO DECODER

The KB4400 requires little in the way of external circuitry and there are few points to note during the construction that are not supplied by reference to the circuit and layout diagrams (Figs. 4.3 and 4.4.)

The decoder is once again mounted to the base board via pins.

\* Ambit International.

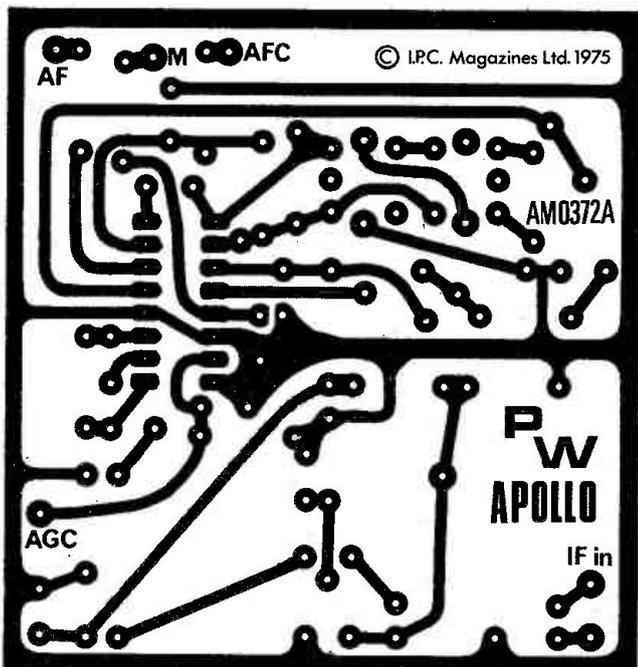


Fig. 4.1: Printed circuit board master for the FM/IF Board shown full size.

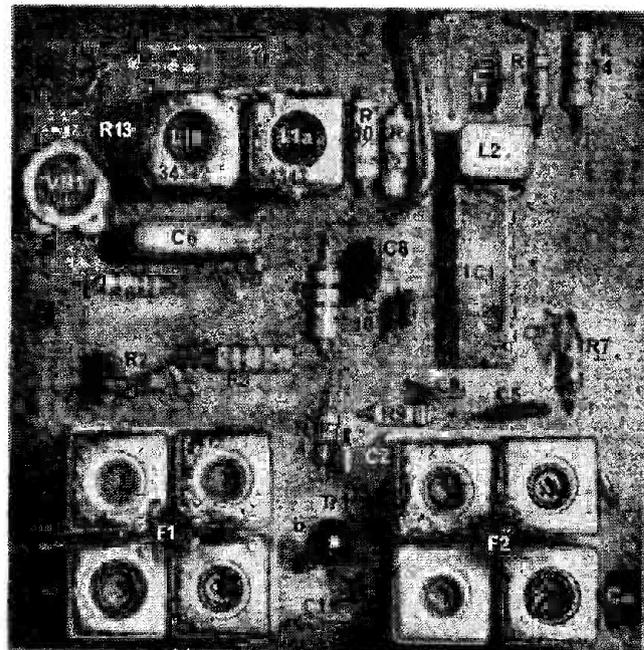


Fig. 4.2: Layout of the components on the FM/IF Board. If a single tuned circuit is to be used instead of the double tuned circuit shown then a KACSK586HM should replace L1a.

## THE AM RADIO MODULE

The AM tuner module has been fully documented in Part 1 of the Apollo series. It is quite possible that readers will have constructed such a module and wish to incorporate it in this design, but, if not, the layout and p.c.b. patterns are shown in Figs. 4.5 and 4.6. There have been one or two minor routing changes in the p.c.b. layout to keep the tracks from the tuning diode to the aerial socket away from the output of the RF stage. It is never a good idea to place inputs and outputs in close proximity especially in RF layouts where the mutual coupling is far greater than in audio. A trimmer has also been included across the RF stage in the new layout.

The net results of the improvements is that the positioning and alignment of the ferrite rod aerial is not as critical as previously.

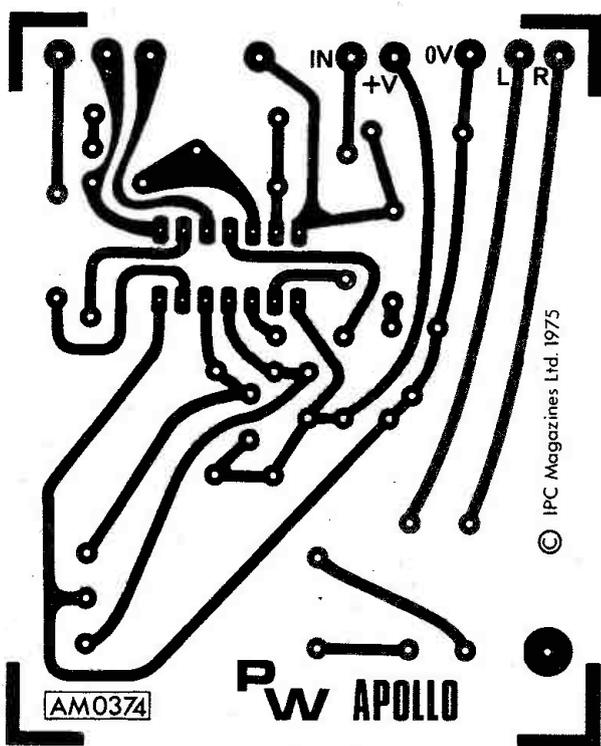


Fig. 4.3: Printed circuit master of the Stereo Decoder Board shown full size.

The overall component layout and the pins to and from the AM radio module remain unchanged apart from the alterations mentioned above.

The new coil for the RF stage is the Toko 6A6371 which is electrically the same as the 6A6408 but with the pin connections revised according to the changes in the layout.

## THE POWER SUPPLY

A standard Douglas mains transformer can be used in the power supply or maybe the MTC "do-it-yourself" transformer with ready wound primary would be suitable. In any case, remember that the two windings must be separate and that a centre-tapped 40V winding will certainly not be suitable.

The voltage regulator devices are the 78 series fixed voltage regulators but by placing a Zener diode in the earth lead as shown in Fig. 3.4 the output voltage can be increased by the amount of the Zener voltage. This method is a simple means of adapting any 78 regulator in place of the 30V source.

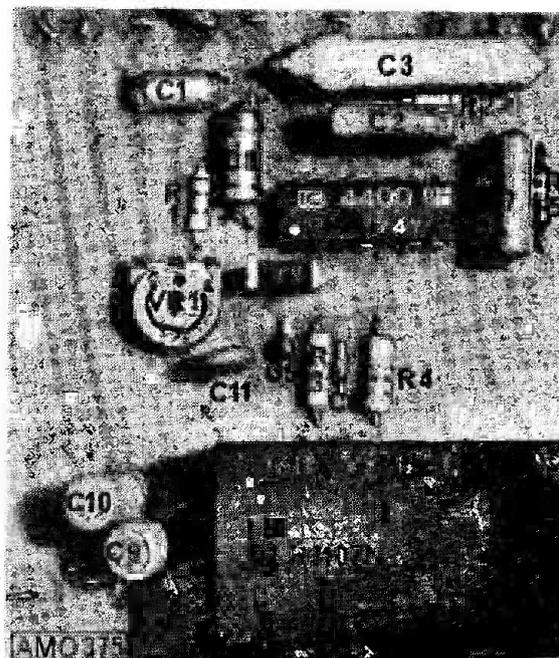


Fig. 4.4: Layout of the components on the Stereo Decoder Board.

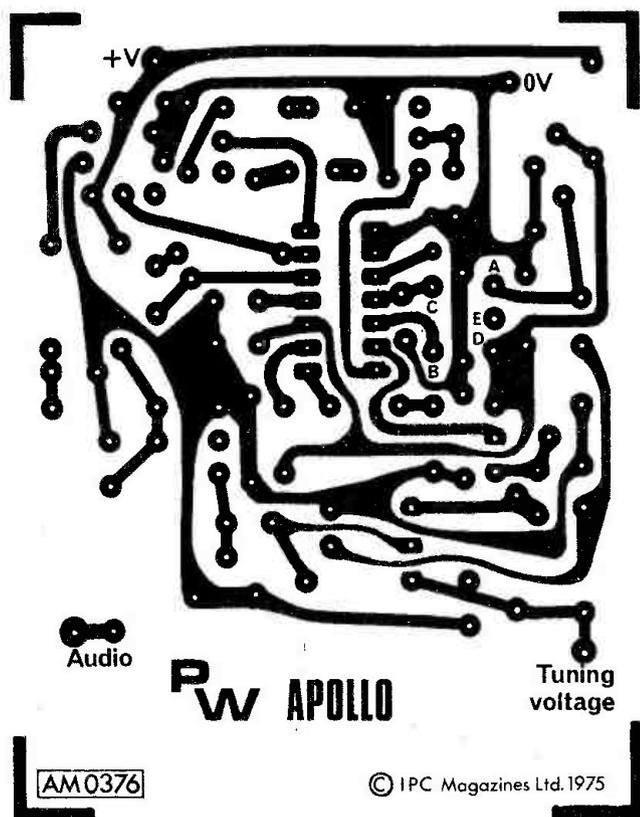


Fig. 4.5: Full size printed circuit master for the AM Module.

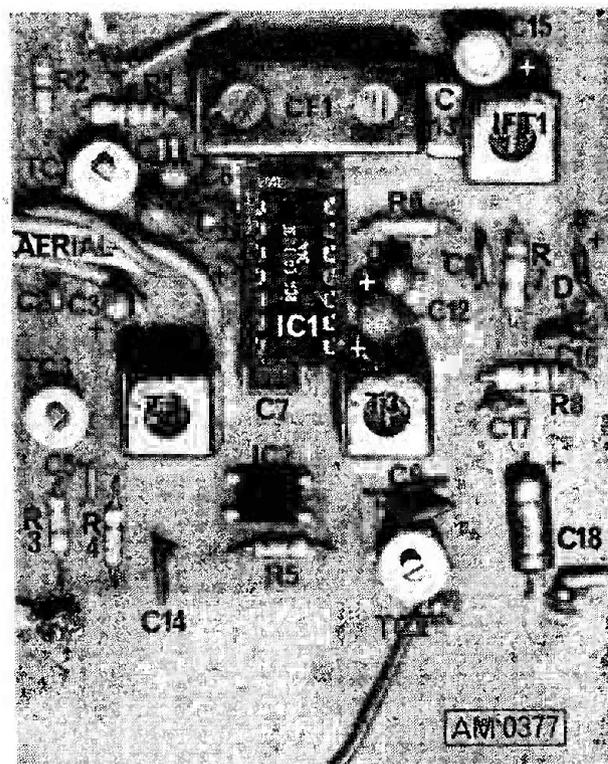


Fig. 4.6: Layout of the components on the AM Module. Note that there is another trimmer capacitor (TC3) on this board, otherwise all components are the same as given in Part 1 of the series, except the RF coil which is now a 6A6371.

## TEST PROCEDURES

Before attaching any of the modules to the base board, it is advisable to test them first.

The tunerhead is supplied ready built and tested but if the FM/IF section has been home made then it is advisable to ascertain that the unit is functioning by connecting the units up with an audio amplifier and the output from the tunerhead.

Begin by rotating the muting control (VR1) fully anticlockwise, in order to defeat the muting function, and apply the supply to the unit. The meter need not be connected for this test as it is simply intended to provide a go/no go indication.

The tunerhead can be simply connected up via the edge connector terminations to provide an input to the IF.

Some white noise should be heard in the audio amplifier (the output from the IF board is approximately 330mV), and by tuning the front end, a signal should be heard without too much difficulty. The actual degree of success will depend on the strength of the FM signals in each particular location and reference to the BBC FM transmitter area coverage will reveal the relative strength in any particular area.

Provided some recognisable sound is forthcoming, adjust the quadrature detector stage coil (L1) which is assumed to be the KACSK 586HM since the double tuned variety, the TKACS 34342/3, requires a wobulator for alignment and persons possessing such equipment will not require comment on its application.

The core should be rotated for best audio which is also liable to coincide with maximum off station noise. (Remember that the mute preset has been left untouched in the mute defeat position.) When confident of the functioning of the IF affix to the base board.

## POWER SUPPLY UNIT

The power supply is relatively simple in terms of components, but before applying any of its outputs directly to the tunerhead/IF ensure that the voltages are in fact correct. If possible the d.c. line should be examined on an oscilloscope to make certain that there is no hum present.

Check that the operation of the AM/FM switch reverses the tuning voltage in the correct sense.

## STEREO DECODER


The stereo decoder requires only the adjustment of the preset to align it though before attempting alignment make certain that the tuner is, in fact, tuned to a stereo broadcast (see *Radio Times*) and that the mono/stereo switch is in the stereo position. Alignment is completed when the stereo broadcast beacon LED lights up. Note where the LED extinguishes in the rotation of the preset (VR1) and return the preset to the centre of its travel during the period of the illumination of the LED to set the VCO in the phase locked loop as close to 19kHz as possible.

## AM MODULE

The AM module has been described previously (May 1975) but there are a couple of points which should be mentioned here since the demand for the triple diode (MVAM1) has outstripped the capacity that Motorola had set aside for its manufacture.

The two section diode, the MVAM2 has been made in larger quantities and it is possible to employ it in place of the MVAM1 on the Apollo tuner board.

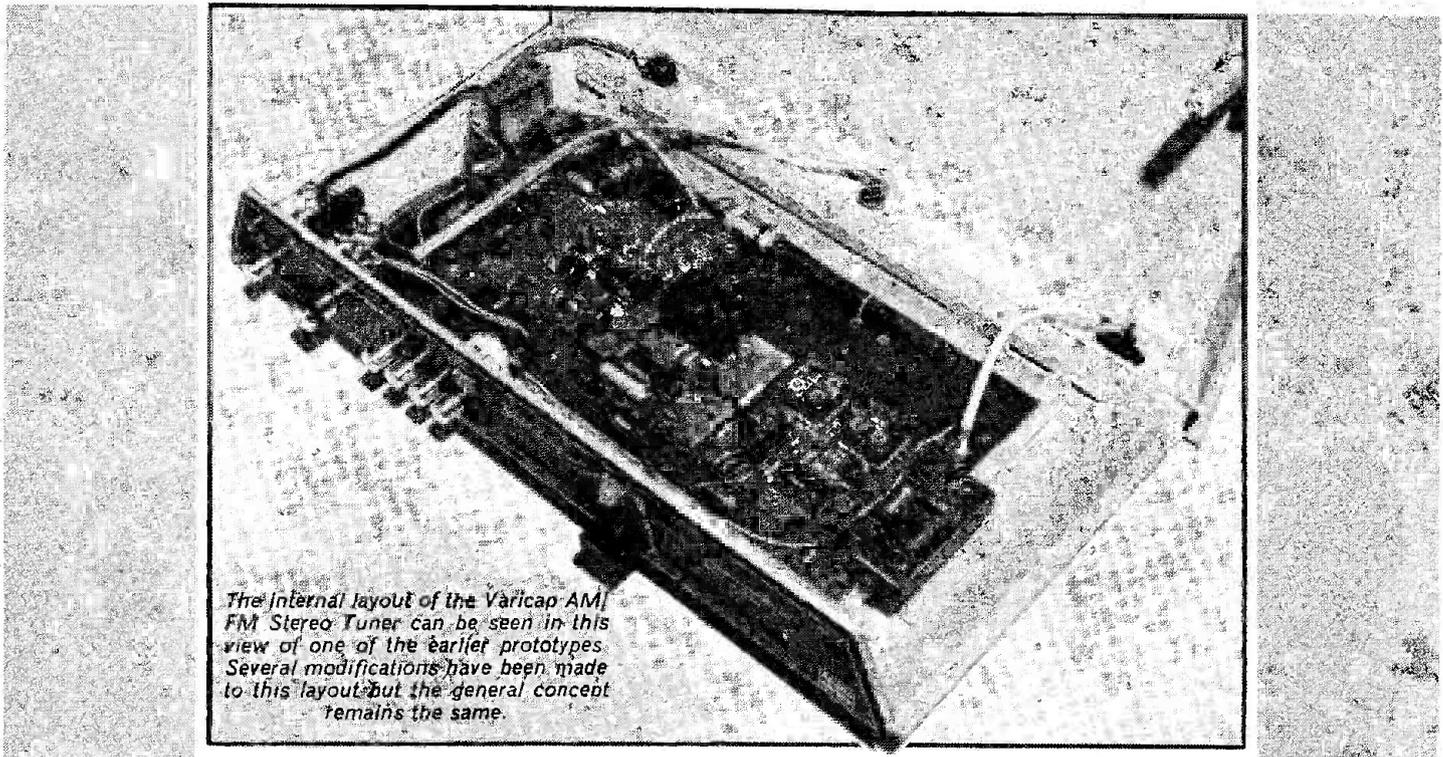Two MVAM2 are required: one to control the RF and aerial section coils and half the other MVAM2 for the oscillator tuning control. This means that the tracking of the signal frequency circuits will be



largely independent of the dissimilarities which may occur between two different examples of the MVAM2.

In practice, the MVAM2 tend to be quite closely matched between samples from the same batch and the results are indistinguishable from those obtained using the more expensive MVAM1 device.

By the time of publication the supply may have caught up with the demand for the MVAM1 but,

as stated, this substitution provides the basis for a lower cost alternative.

### FINAL TESTING

When satisfied that the power supply is providing the correct voltages and all sections are soldered down onto the base board, together with the additional components and the various links (see Figs.

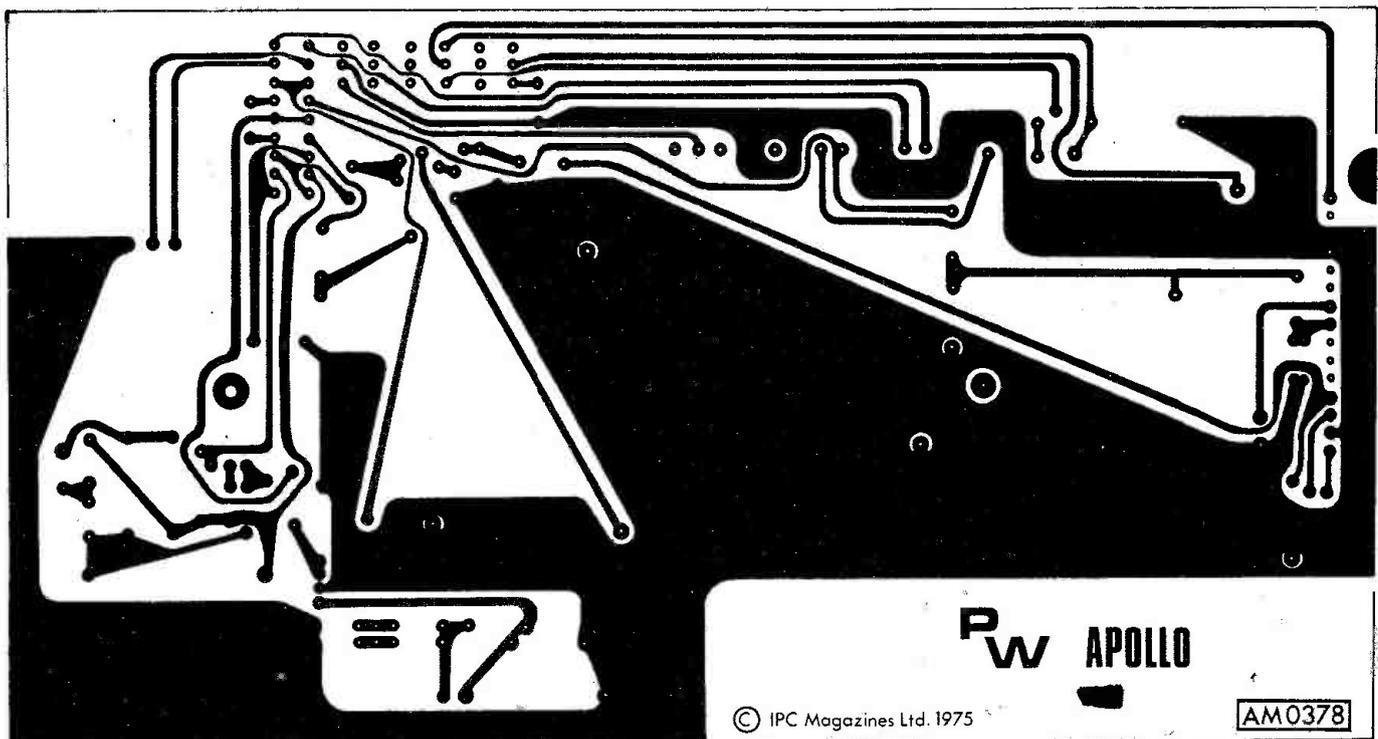


Fig. 4.7: Half scale printed circuit master of the mother board. The three smaller boards and the tunerhead are mounted on this board.


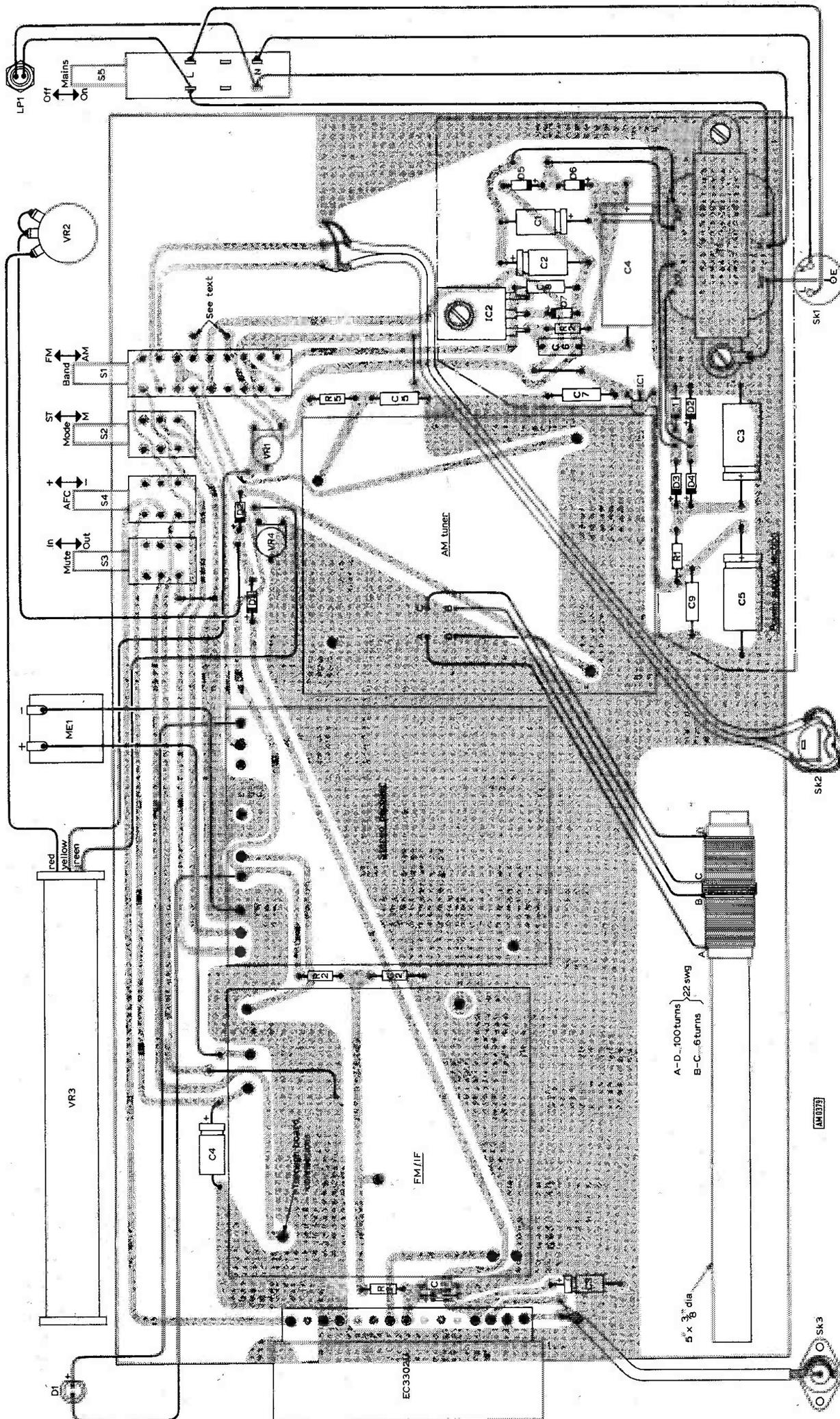


Fig. 4.8: Layout of the three small boards, the tunerhead and the other components on the main board. The interwiring to the front and rear panels is also shown on this diagram. The four leads to the ferrite rod aerial go to the four corresponding points on the AM Board. Note the link from the main board on to the FM/I/F Board, and the capacitor mounted on the tunerhead.

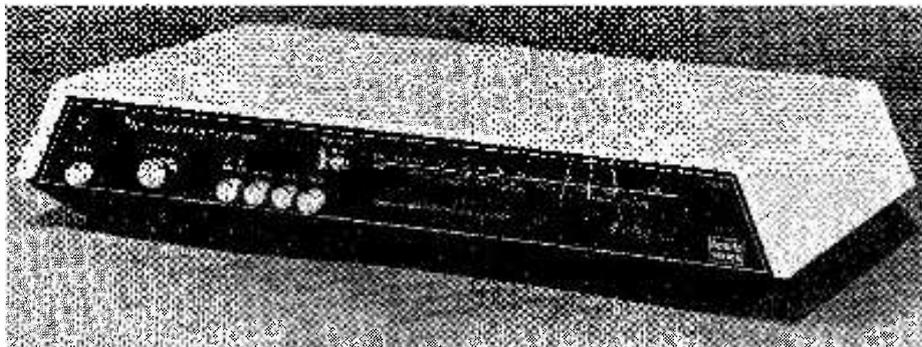The completed tuner. The case was specially designed for this project and has overall dimensions of 420 x 230 x 90mm (16½ x 9 x 3½in).



4.7 and 4.8), switch to FM stereo and turn on the mains.

With an aerial at the rear tune around for a station and peak up using the signal strength meter as a guide.

Slowly rotate the cores in the IF filter—NO MORE THAN HALF A TURN EACH, until the maximum peaking is achieved. In most cases such adjustment will bring about no improvement since the filters are accurately prealigned before despatch.

With the signal strength and fine tune control peaked adjust the detector coil for maximum audio. (Defeat a.f.c. for this operation.)

The IF strip is now aligned and the decoder should be checked for accurate stereo indication.

## MEDIUM WAVE RECEPTION

With the AM/FM switch in the AM position and the ferrite rod connected, check that reception of the medium wave is satisfactory. To align the scale rotate the preset at the end of the tuning potentiometer until -27V is present. Adjust the core in the oscillator of the AM section for coverage of 190 to 550 metres from one end of its travel to the other. The simplest means of checking this is to calibrate against existing broadcast stations though a signal generator will naturally be a great help.

Mark the scale on a piece of paper and keep for reference when marking the final scale.

## FM ALIGNMENT

FM alignment can be carried out in much the same way. With such a high tuning voltage it may be necessary to reduce the FM range by placing a resistor in the lead from the AM/FM tuning voltage changeover switch to reduce the maximum tuning bias on FM to about 20V otherwise the coverage will extend into the aircraft band to approximately 115MHz.

## CONCLUSION

The remainder of the exercise will largely depend on the individual's experience. Fault finding can be a lengthy process to the inexperienced and the only advice is to employ a systematic approach and work back from the audio amplifier stages to determine the section in which the fault lies. Once isolated the modular approach allows for easy breakdown.

A refinement of preset tuning can be added via a six-way pushbutton unit as described in Part 1 of the Apollo series. Perhaps this could be mounted via a 3-pin DIN or similar socket at the front or rear of the tuner cabinet and thus also include a remote tuning facility.

## AMENDMENTS

In Part 3, several modifications have been made and now incorporated into the main circuit board. In Fig. 3.1:

Capacitor C3 has been reduced to 4.7µF.

Resistor R3 has been eliminated and replaced by a link.

Resistor R4 has been replaced by a 4.7kΩ preset potentiometer (horizontal skeleton type) which will be referred to as VR4.

Potentiometer VR1 has been moved to be directly in series with VR3 i.e. between VR3 and S1.

Switch S1d has been replaced by two diodes (D2 and D3 Fig. 4.8). The unused switch position has been used to provide outputs which may be used to operate lamps to indicate FM or AM mode.

In Fig. 3.2:

Resistor R1 has been eliminated.

Resistor R15 has been replaced by a wire link on the circuit board.

In Fig. 3.4, resistor R1 has been reduced to 47Ω. 0.1µF capacitor has been placed in parallel with C5. This will be referred to as C9.

Capacitor C6 should be connected to the junction of R2 and IC2 rather than to D7.

In Fig. 3.1 S2 is shown in the "stereo defeat" position and S3 in the "mute" position. S1 is in the "FM" position and S4 in the "AFC on" position.

## PRINTED CIRCUIT BOARD

Due to lack of space it is not possible to show the main printed circuit board full size. For constructors wishing to make their own printed circuit board a full-size paper drawing of the main board only is available from:

**Practical Wireless  
Fleetway House  
Farringdon Street  
London EC4A 4AD,**

Mark the envelope "Varicap Tuner."

A cheque or Postal Order for 20p made out to Practical Wireless and a 10 x 8in s.a.e. must be enclosed. Do not enclose any other correspondence or queries.

NOTE In Part 1 (May 1975), Fig. 1.4 capacitor C19 should be shown connected to Pin 6 of IC3 whilst pin 2 is unused. Fig. 1.7 is correct in this respect except that the capacitor marked C1 should be marked C19.

The ferrite rod should be 3/8in diameter and about 5in long. 22 s.w.g. wire is suitable for the coils.

PW

Yes! to the PW

IN NEXT MONTH'S

**PRACTICAL  
WIRELESS**

**EASYBUILD  
ELECTRONIC**

**CLOCK!**

**+ 4-RANGE TIMER**

PHOTOGRAPHIC USE \*

BIO-MEDICAL TIMER \*

DESK CLOCK \*



Simple to build, the PW Easybuild Electronic Clock can also function as a 4-range electronic timer, with timing cycles of 12 and 24 minutes or 12 and 24 hours. Timer may be reset to zero or allowed to record integrated time intervals. Three small printed circuit boards assure easy assembly and first time operation. The clock is just 120 x 75 x 50mm (4 3/4 x 3 x 2 in.) while the optional timer control box is 75 x 50 x 25mm (3 x 2 x 1 in.) approximately.

Also~

**TELE-TENNIS-Electronic Scoring Unit  
Miniaturised Equipment for the 2m band-Part 1**



# car radio

A car radio providing pre-set reception of two local stations in addition to manual tuning, is very convenient and the receiver described here is of this type. Though intended for operation from the 12V vehicle supply, the circuit allows satisfactory working from dry batteries.

Fig. 1 is the circuit. The 3-way switch S1/2 provides for manual tuning, or two pre-selected stations. With S1/S2 at A, C1 with TC3 tunes the aerial circuit L2, while TC6 tunes the oscillator coil. The values in use are for 200kHz on long waves, but in some areas LW reception is not wanted, and the capacitors can be modified for an additional pre-set MW station. With the switch at B, TC2 and TC5 provide a pre-selected MW programme. The remaining position is for manual tuning, with the ganged capacitor VC1/VC2. This allows MW coverage, which is useful for alternative programmes, or when driving outside the area for which positions A and B have been set.

Coverage obtained in the aerial circuit with various pre-sets in the TC2 position is approximately as follows:

|             |              |
|-------------|--------------|
| 7 to 60pF   | 1600-1000kHz |
| 30 to 140pF | 1350-750kHz  |
| 40 to 250pF | 1200-600kHz  |

The smaller values will not of course tune to the LF end of the MW band, but the larger values cannot always be fitted as their relatively high minimum capacitance prevents tuning to the HF end of the band. However, there should be no difficulty in fitting one of these three values, to suit stations wanted, or local circumstances. Should position A be for an additional MW station, C1 is omitted, and the required value is used for TC3.

In the oscillator section, the padder C4 is necessary for ganged tuning, but is not present in positions A or B. Here, TC5 can be as follows:

|             |             |
|-------------|-------------|
| 7 to 60pF   | 1600-700kHz |
| 30 to 140pF | 1450-550kHz |

Again, if 200kHz LW is not required, the 450pF trimmer TC6 in Fig. 1 can be replaced by one of the

smaller capacitors, as needed. L2 and the oscillator coil are easily obtained for use as a pair and as the receiver is fully screened, L1 is added for aerial coupling. Cascaded IF amplifiers, one double-tuned and one single-tuned IFTs, give a good degree of sensitivity and reasonable selectivity. Mixer and IF stages run from a 6.2V line, stabilised by D1.


Audio signals from the volume control VR1 pass to a high gain IC amplifier with push-pull output. In the case of a car radio with a large Class A output stage, current drain is too heavy for dry battery working. This is not so with the circuit here, which can be run in this way from a 9V or higher voltage supply, with economy equal to that of a battery portable. Dry battery working may be adopted if it is not wished to make the required connections for a permanent installation, or when testing the circuit, or using it where no accumulator supply is available.

## POLARITY AND SUPPLY


The emitter or negative line is isolated from the chassis so that a positive or negative earth is possible. L1 tuning capacitor and trimmers return to the receiver metal case. With a positive earth, C12 provides the RF circuit for these components. With a negative earth, as in Fig. 1, chassis and negative line are connected so C12 is not necessary and may be omitted.

No difficulty will arise if the negative or emitter line is isolated as described, as either positive or negative supply leads can then be connected to the metal case, with no change in results. This isolation

AM 0359

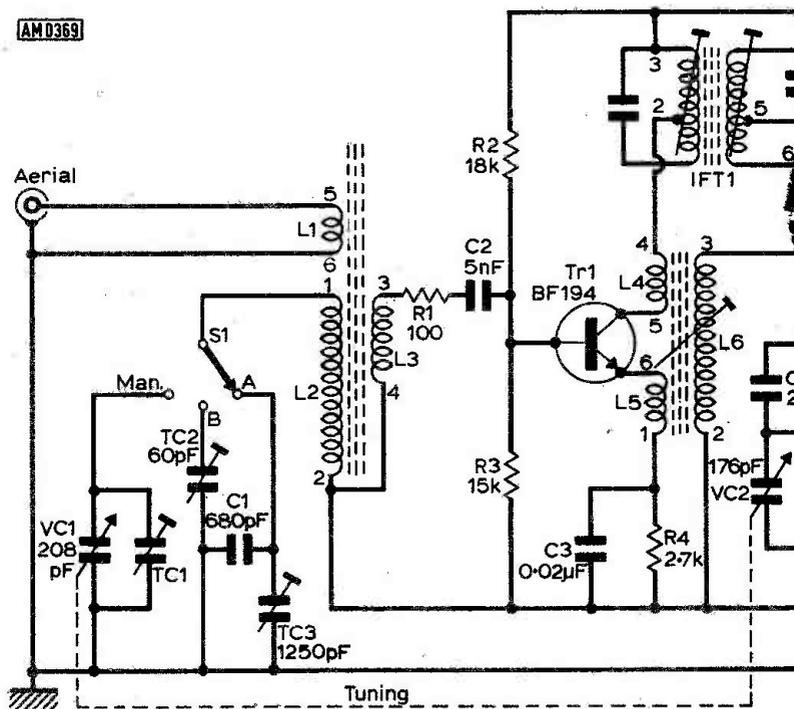


AM10353

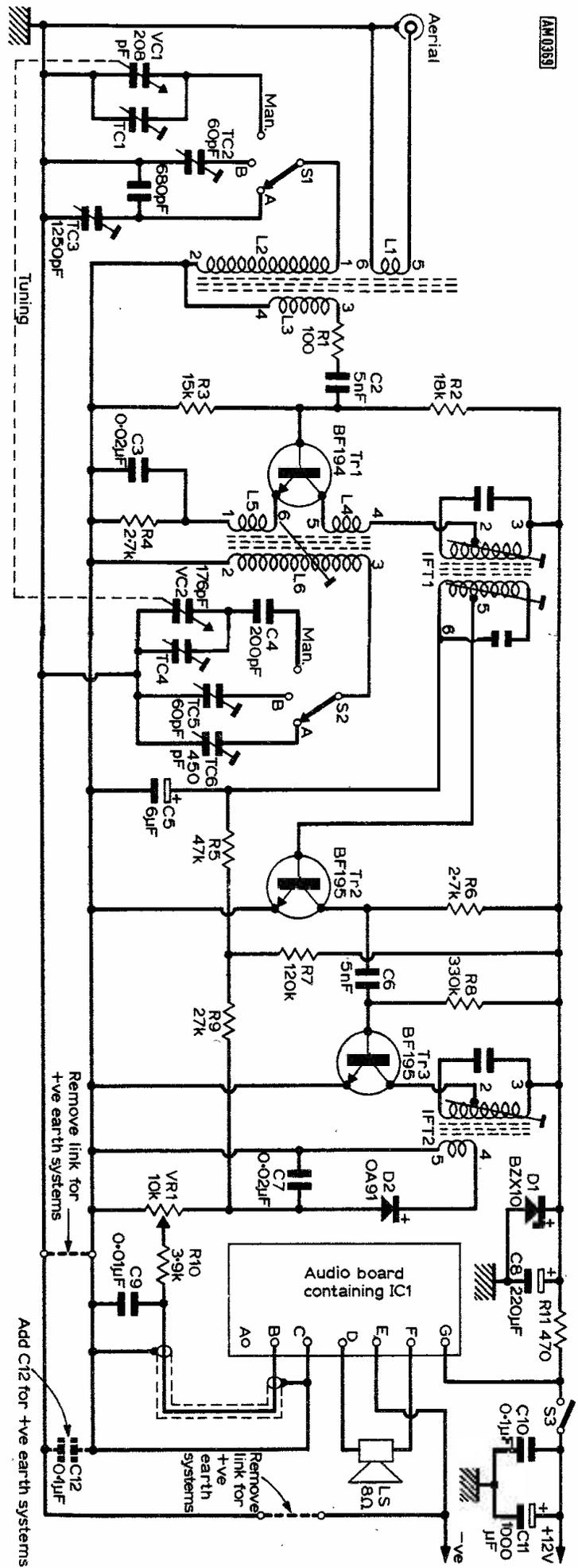

# Radio

**CHARLES HEATH**

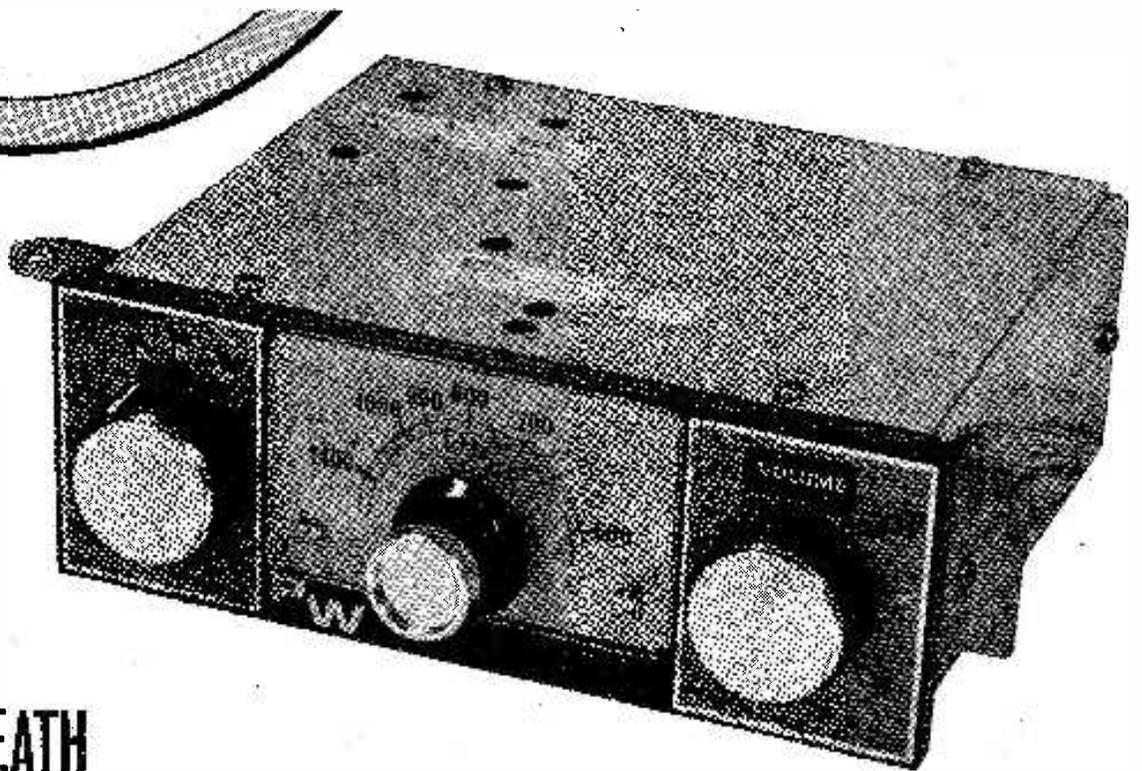

is of course carried through to include the AF amplifier.

In the vehicle installation used with the receiver, it was found that C10 and C11, with the addition of a 220 $\mu$ F 25V capacitor between positive supply point, and chassis, was enough to avoid interference, even with the engine running. Some car receivers also employ small chokes in the supply. Should interference prove troublesome when first testing the receiver in a vehicle, it is worth trying an alternative and sound return from receiver case to vehicle chassis, especially if this is not done by mounting brackets or other direct contact from case to metal parts. Should interference cease or be much reduced with the aerial unplugged, check its earthing and that it is not unnecessarily close to vehicle wiring, plugs, generator, etc. On the other hand, if interference ceases when temporarily connecting a dry battery, it is introduced through the battery supply,

and more suppression is necessary. It is assumed that the vehicle itself has the usual suppressors.

No interference was found to be introduced through the speaker leads. D or F cannot be earthed directly, but could be by-passed by 0.1 $\mu$ F or similar capacitor. Should permanent operation from a 9V dry battery be envisaged a little current can be saved by omitting D1, which is then unnecessary.

## SPEAKER AND AERIAL

The speaker may be from 3 to 15 ohms, but around 8 ohms is recommended. A little more power is available however, with a 3 ohm unit, but at increased current drain, whereas a 15 ohm unit will give some extra economy for dry-battery running.

When the metal case is closed, an external aerial becomes necessary, and various car aeri-

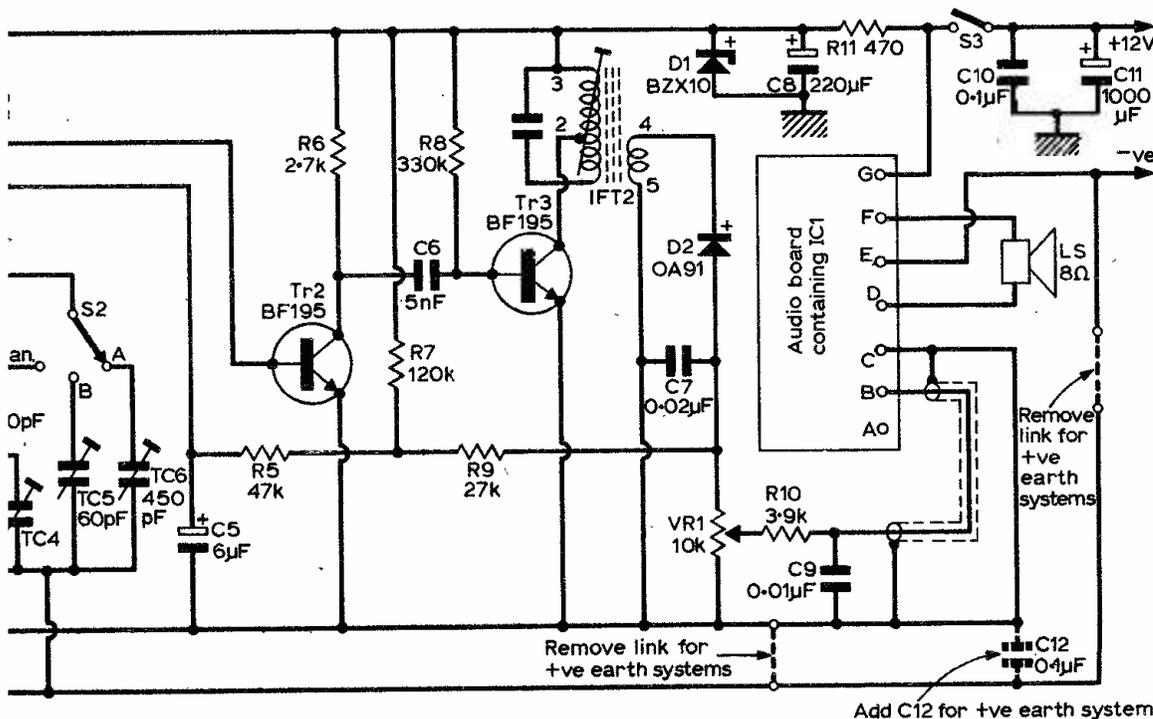


Fig. 3. Circuit diagram for the complete car radio, shown here connected for negative earth systems. Circuit details for the audio amplifier board are shown in Fig. 5.

## ★ components list

| Resistors   |                            |
|---|----------------------------|
| R1 100Ω   | R7 100Ω                    |
| R2 18kΩ   | R8 330kΩ                   |
| R3 15kΩ   | R9 27kΩ                    |
| R4 2.7kΩ  | R10 3.9kΩ                  |
| R5 47kΩ   | R11 470Ω                   |
| R6 2.7kΩ  | VR1 10kΩ log pot (with S3) |
| All resistors 5% 1W   |                            |
| Capacitors  |                            |
| C1 680pF  | C7 0.02μF                  |
| C2 5nF  | C8 220μF (10V)             |
| C3 0.02μF   | C9 0.01μF                  |
| C4 200pF  | C10 0.1μF                  |
| C5 5μF (4V)   | C11 1000μF (18V)           |
| C6 5nF  | C12 0.1μF                  |
| VC1/VC2 Jackson 00, 203 175pF slow motion with trimmers (TC1 and TC4) |                            |
| TC2 and TC5 7-60pF (Home Radio VC29LC)                                |                            |
| TC3 400-1250pF (Home Radio VC29SA)                                    |                            |
| TC6 50-450pF (Home Radio VC29R)                                       |                            |
| Semiconductors  |                            |
| Tr1 BF194   | D1 BZX10 (6.2V 400mW)      |
| Tr2 BF195   | D2 OA91                    |
| Tr3 BF195   |                            |
| Miscellaneous   |                            |
| L1, 30 turns 34SWG L2/L3, Denco MW ferrite rod                        |                            |
| aerial L4/L5/L6, Denco TDC1, IFT1, Denco IFT18,                       |                            |
| 485 IFT2, Denco IFT14, S1/S2, 2-pole 3-way rotary                     |                            |
| switch, Metal case, 127 x 153 x 51mm (5 x 6 x 2in)                    |                            |
| universal chassis and extra 127 x 153mm (5 x 6in)                     |                            |
| plate (Home Radio), Mixer IF board 121 x 32mm                         |                            |
| (4 1/2 x 1 1/2in) 0.15in plain veroboard, Trimmer board,              |                            |
| 51 x 57mm (2 x 2 1/2in), 3 control knobs, plywood and                 |                            |
| perspex dial and pointer.   |                            |

## ★ components list

| Audio amplifier board (Sinclair Super IC12)     |                   |
|---|-------------------|
| Resistors                                       |                   |
| R1 270kΩ  | R4 100Ω           |
| R2 150kΩ  | R5 27kΩ           |
| R3 18Ω  |                   |
| All resistors 5% 1W                             |                   |
| Capacitors                                      |                   |
| C1 0.1μF  | C6 1nF            |
| C2 100pF  | C7 470pF or 500pF |
| C3 10μF (15V)                                   | C8 0.01μF         |
| C4 100μF (15V)                                  | C9 500μF (15V)    |
| C5 100μF (30V)                                  |                   |
| Integrated Circuit                              |                   |
| IC1 Sinclair Super IC12 (Swanley Electronics)   |                   |
| Miscellaneous                                   |                   |
| Printed circuit board as supplied with the IC12 |                   |
| 77 x 68mm (3 x 2 1/2in)                         |                   |



ceiver allow trimmers to be reached, so that a final alignment of these can be undertaken after the radio is fitted and the aerial connected.

## CASE PREPARATION

The case (a) is 127 x 152 x 51mm (5 x 6 x 2in) made up from two 127 x 51mm (5 x 2in) and two 152 x 51mm (6 x 2in) universal chassis flanged members (b and c), and two 127 x 152mm (5 x 6in) flat plates (d). Cut one end flange off each 'b' member. Assemble the box, with the 'c' items inside the 'b' sides. The cut-off ends of the latter are at the front. The 'd' plates are then drilled so that the bottom can be fixed with 6BA bolts, and the top with self-tapping screws. Check that the box is square.

The 'b' front is removed and drilled or punched for

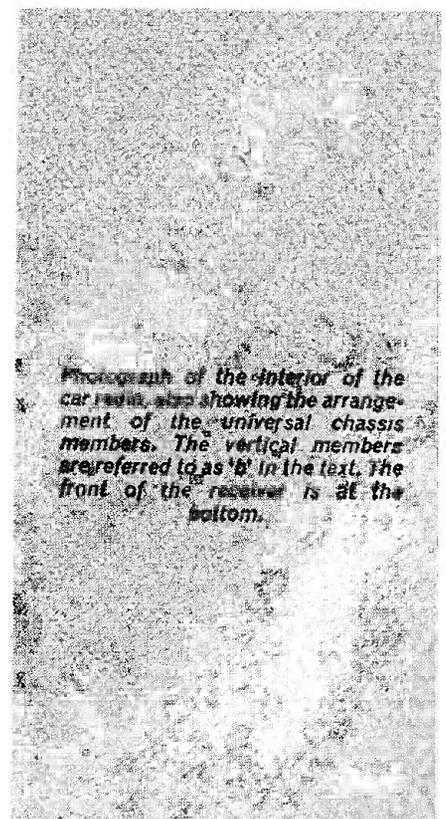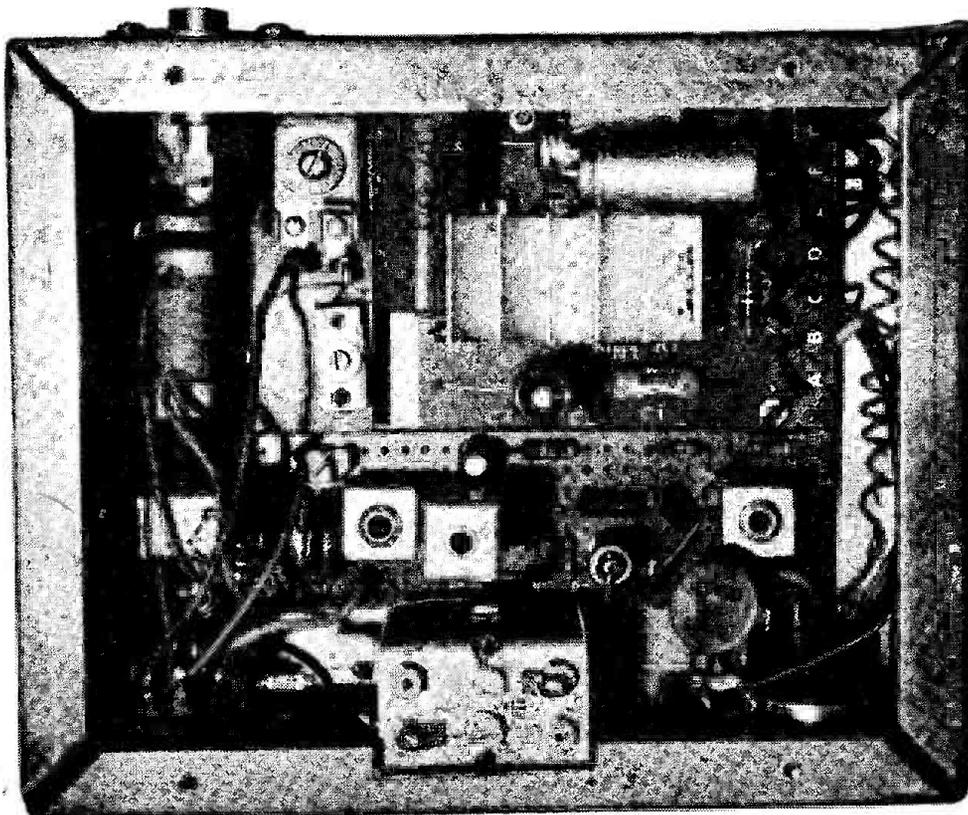able, including some which avoid any need to drill holes in the vehicle. It will be found that the aerial loading has some effect on tuning. Holes in the re-



Photograph of the interior of the car radio, also showing the arrangement of the universal chassis members. The vertical members are referred to as 'b' in the text. The front of the receiver is at the bottom.

VR1, the switch and ganged capacitor. The latter is fixed with three 4BA bolts. Do not overlook that these must be cut or filed short, or washers put between gang and front, in order to prevent the screws from projecting inside the gang and bending its plates. Cut the top flange so that the trimmers can be reached, and then bolt the front and bottom plate together. Sides and back are left off until construction is otherwise finished.

Fit the back with a co-axial socket as shown. Speaker leads run from the IC board through a grommet or they can go to a pair of insulated sockets. Power connections can be to a 2-pin non-reversible plug as used for battery connecting, twin insulated leads, or a single lead and chassis as required. To improve the front appearance, a piece of varnished 3-ply approximately 159 x 54mm (6<sup>1</sup>/<sub>4</sub> x 2<sup>1</sup>/<sub>8</sub>in) is fixed to the front by two chrome 6BA bolts. These also hold a piece of 1.5mm (1/16in) perspex about 45 x 76mm (1<sup>3</sup>/<sub>4</sub> x 3in) which protects a card scale of similar size. The latter is marked for MW tuning. Later, 6mm (1/4in) holes are punched in the top plate, to allow the six trimmers and oscillator coil to be reached with a suitable insulated adjusting tool.

## MIXER-IF BOARD

This board is approximately 127 x 32mm (5 x 1<sup>1</sup>/<sub>4</sub>in), Fig. 2 and is fitted so that its front edge is 26mm (1in) from the front of the case. Drill the board and bottom to take 6BA bolts for mounting it about 6mm (1/4in) clear of the bottom. The board is cut as in Fig. 2 to clear the vanes of the tuning capacitor. Holes now have to be drilled for the oscillator coil and IFTs, with a central hole under IFT1, to reach the

lower core. If final IF alignment is done after fitting the board, a matching hole is necessary in the case bottom.


The chassis, as previously mentioned, is isolated from the negative line. If therefore a negative earth is always to be used, C12 can be omitted and the adjacent negative pin wired to the tag MC. Pins or projecting leads are fitted for subsequent connections to R1, negative line, pin 3 of oscillator coil, R11, VR1 and negative adjacent to C8.

## AERIAL COIL

No alignment problems can arise with the two pre-set frequencies. But the manual tuning alignment requires the correct ganged capacitor, and the aerial inductance which is intended for use with the oscillator coil. For this reason, L2 is a MW portable receiver winding, with the ferrite rod reduced to about 76mm (3in). The rod can be snapped by gripping it with a vice or tool at the wanted point, and sharply tapping the projecting end. A 9mm (3/8in) hole is drilled in a block of hardwood or other insulated material, to take the end of the rod, which is then glued and mounted at a centre height of 26mm (1in) from the metal case bottom.

L3 which consists of a few turns on L2 is placed towards the receiver front. Join adjacent ends of L2 and L3, points 4 and 2, and take to the pin in Fig. 2. The free end of L3 goes to R1, and the free end of L2 will go to S1.

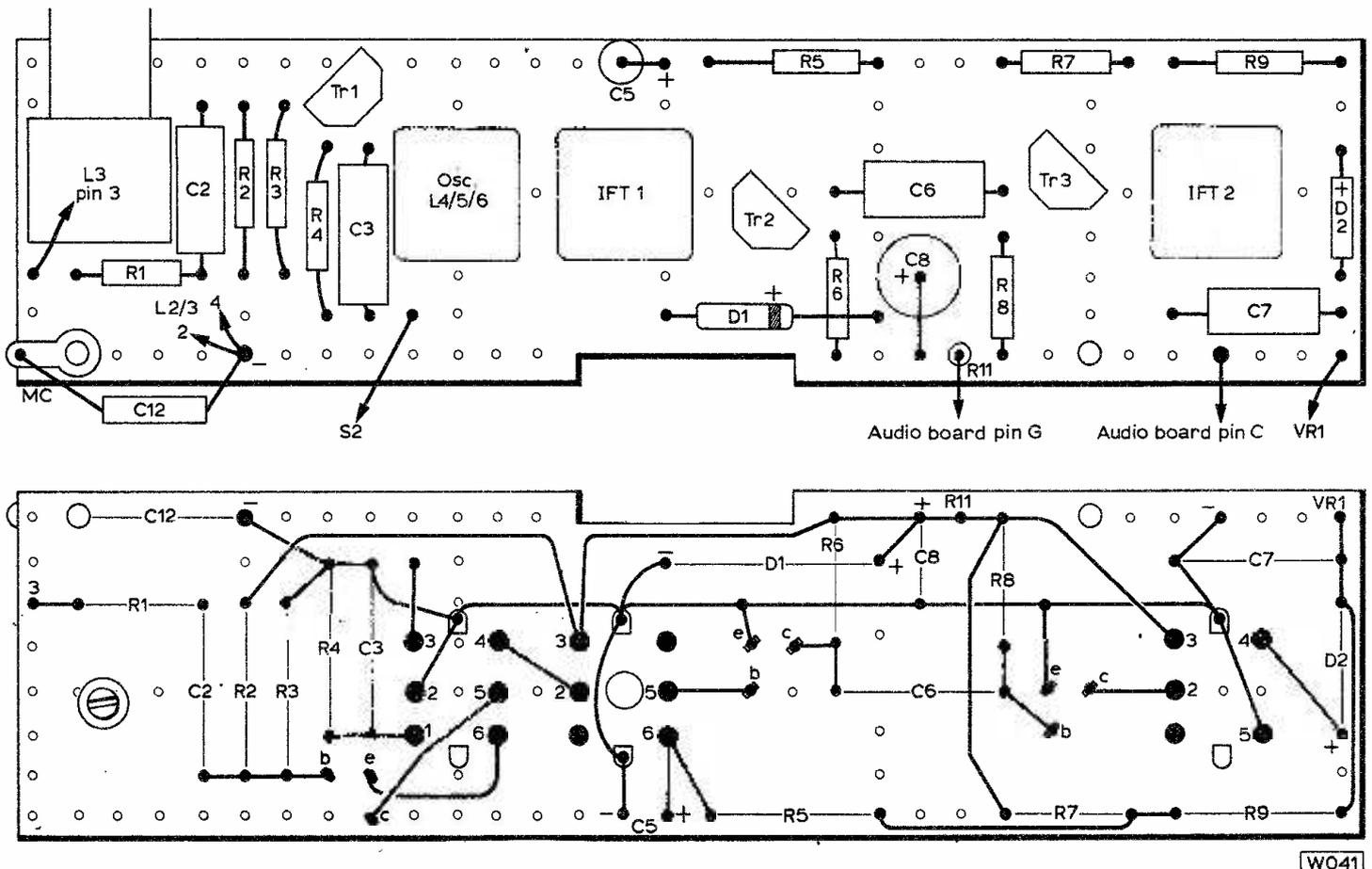L1 is 30 turns of 34SWG enamelled or other thin wire, wound on a paper strip around the free end of the rod. It is later connected to inner and outer (case) of the co-axial socket.



W041

Fig. 2: Mixer/IF board, showing both component side and wiring side. The board is cut away in the centre to accommodate the tuning capacitor.

## IF ALIGNMENT

As the IFT's are aligned by the maker, unnecessary adjustment of the cores should be avoided. A final slight re-adjustment may be necessary after wiring, and if this is so, a correctly fitting tool must be used, as a wedge-shaped blade may break the cores so that they jam. If necessary, a suitable tool can be obtained from the IFT maker.

Adjustment can be made with a weak but stable signal tuned in. Each core is slightly adjusted either way, as necessary for best volume. A signal generator can of course be used, and is more convenient. With a modulated signal of this type, the cores can be adjusted for maximum battery current with the audio amplifier working. The signal generator input being reduced to give a current of 30-40mA or so maximum, with VR1 well advanced. Once each of the three IFT cores has been set for best results, no further adjustment is needed here.

## TRIMMER BOARD

This is paxolin, about 51 x 57mm (2 x 2 1/4 in) in size, fitted as in Fig. 3. Holes take the tags of TC2 and TC5, and the adjusting screws of all trimmers. Two fixing bolts with extra nuts raise the board a little from the metal, and one forms the MC or return connection, as shown.

Connections to the switch are as in Fig. 4. Trimmers TC1 and TC4 are integral with the ganged capacitor. Should a component without trimmers be used, a trimmer must be connected to each section of the gang.

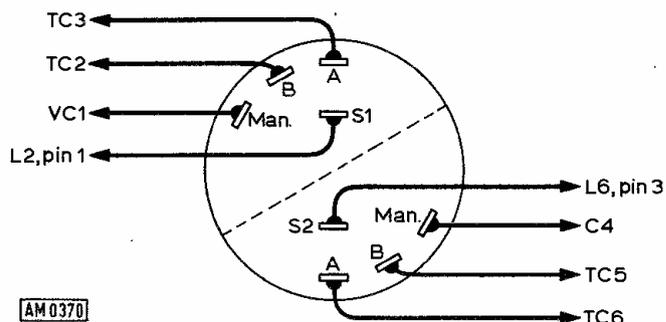


Fig. 4: Connections for the manual/pre-select waveband switch, S1/S2.

## AUDIO AMPLIFIER

The Sinclair Super IC12 is a multi-transistor integrated circuit with finned heat sink, providing high gain and adequate audio output from 12V. The associated circuit and component values are shown in Fig. 5. It is assumed that the Sinclair PCB which is drilled with component positions printed on the top side will be used. Assembly then merely consists of forming the wire ends of resistors and capacitors to suit the holes so that they can be soldered in position, and any excess snipped off. It will be noticed that C5 is rated at 30V, as the module is intended for use with up to 28V. In this case, however, 28V will not be reached and C5 can be of a lower rating. It is also advantageous to use a larger

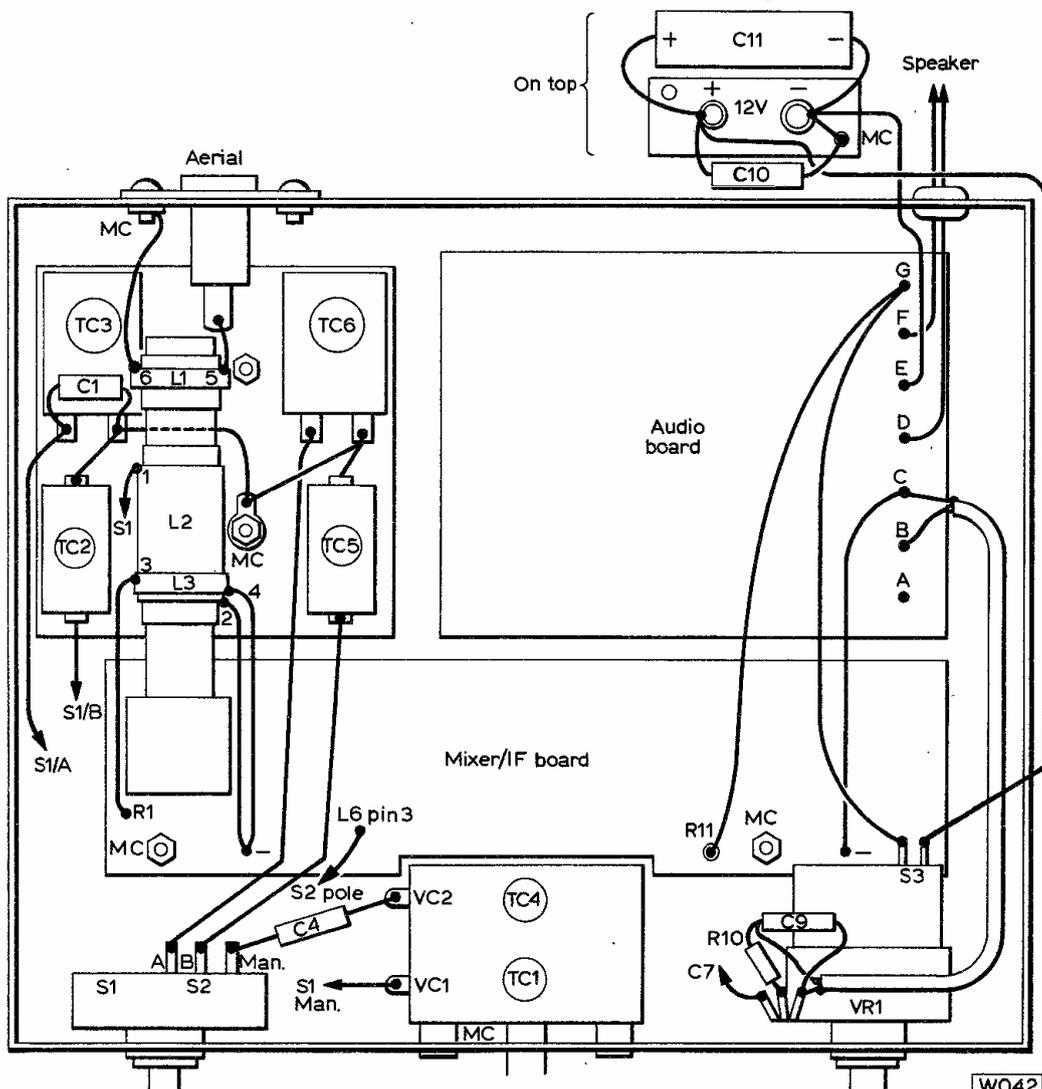


Fig. 3: General layout, showing positioning of the three boards, ferrite rod and controls. The view is from above.

capacitance here and C5 may be 250 $\mu$ F, 500 $\mu$ F or larger.

Referring to Fig. 3. B runs via the screened lead to C9 and R10. The braid is returned to C. A lead also runs from C to negative on the IF board. D and F are for the speaker. E is for the negative power supply. G is for positive, via S3, supplying also R11. Connections are arranged in the way shown to avoid feedback loops in the negative line.

If a positive earth is to be used, remember that the negative line must be disconnected at the supply socket, and must not be completed to the metal case

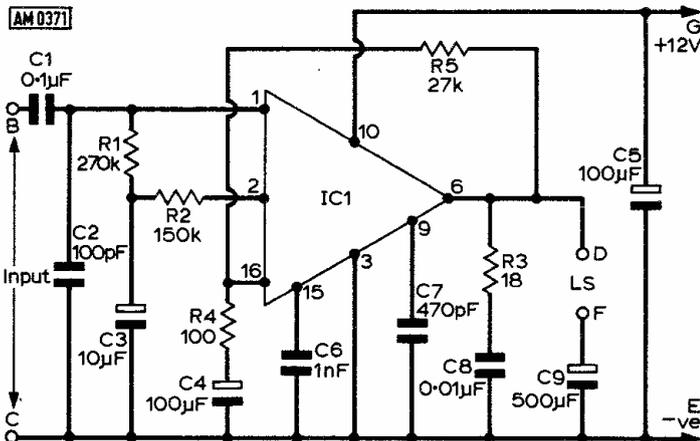


Fig. 5: Audio amplifier circuit using the Sinclair Super IC12 and associated PCB. The audio output is approximately 5W into an 8 $\Omega$  speaker.

at any point. If the receiver is not to be run from an accessory fuse-way, an in-line fuseholder should be included in the live power lead, to avoid any possible power short in the receiver causing damage or interrupting the supply to other items. The power supply can be a permanently fitted insulated lead and case return, or two such leads, as mentioned. For plug-in connections, the plug should be shrouded or secured with a screw, or pins should be on the receiver end, and sockets on the lead end, to avoid any possible short to metal parts should the plug come out of place.

### ALIGNMENT

With the switch at manual tuning, adjustments should be made to obtain a band coverage of about 1500-550kHz. Adjust TC1 and TC4 at the HF end of the band and L2 and the oscillator coil at the LF end of the band. Repeat these adjustments until no further improvement is obtained. The switch can then be set at B and TC5 adjusted to bring in the wanted transmission, TC2 being set for best volume. Now with the switch at A adjust TC6 and TC3.

When the case lid is fitted and the aerial connected slight re-adjustment of trimming will be required for optimum results. As movement of L2 is not feasible, a very slight re-setting of L6 can be made, while rocking VC1/VC2 to tune in a signal near the LF end of the band. Trimmers TC1 to TC6 can then be checked TC4 being left untouched. R1 is to prevent unwanted oscillation which may begin near the HF end of the band, especially with the aerial disconnected. If no such trouble arises with the aerial connected, R1 may be left as shown. Otherwise it can be increased to 150 or 220 $\Omega$  or so, depending on the actual gain of Tr1. However in most cases values as given should be suitable. **PW**

# PW TECHNICAL CROSS PUZZLE No. 10


### ACROSS

- 3 It's high on the list with earpieces? (9)
- 8 Slough not making solid-state? (4)
- 9 But succumb to pencil for printed circuits? (6, 3)
- 10 A natural problem in voice reproduction (4)
- 12 Valve case needed in this bloody channel! (4)
- 14 It's just bordering on the picture . . . (5)
- 15 . . . which contains quite a story! (4)
- 17 A world link for good reception (5)
- 19 Dawn's way with a set repair? (4)
- 21 Row in with bus-bar guesswork? (5)
- 22 Good turnover with this sound part? (4)
- 26 Cape shape example of 1 Down? (4)
- 27 Girl with a bike that's a MHz? (9)
- 28 Set for a smile? (4)
- 29 Powerless without them? Not in the main! (9)

### DOWN

- 1 A speaker against noise abatement (9)
- 2 Within a whisker of receiving from them? (8)
- 4 Mild alloy in some Ekco components (4)
- 5 Bad home reception led him to it? (5)
- 6 Nut tea around to get the right wavelength! (6)
- 7 A pointed piece in broken components (4)
- 11 This charge may not be electrical (3)
- 12 Over-selectivity cuts out the poetry! (5)
- 13 Protecting your coils from interference? (9)
- 16 You need brass for this amateur lay-out? (8)
- 18 He's got a swine of a call-sign! (3)
- 20 Play this unschooled art nut's oscillator! (6)
- 23 Relay distortion by and egg-producer! (5)
- 24 Second-rate transistor value? (4)
- 25 Kept on the air, we hear, from a chimney (4)
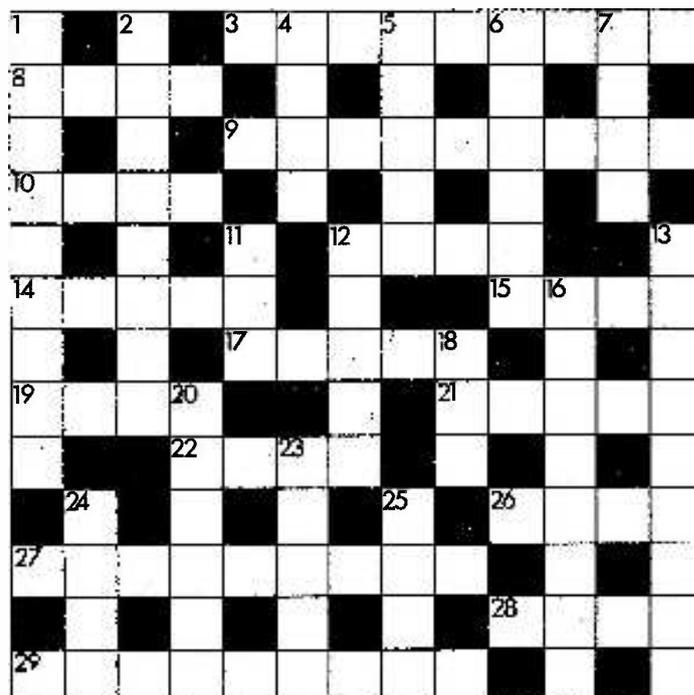
### FOR AMUSEMENT ONLY ANSWERS NEXT MONTH





## British Justice?

The Editorial—**Thou shalt not listen**—in the March issue of P.W. is interesting. I believe that a Licence for the operation of a Sound only, Broadcast receiver is no longer necessary.

On the back of a Television Broadcast Receiving Licence, section 4 of the Schedule says that if any message is received:—other than that which the apparatus is authorised to receive—unintentionally—the message shall NOT be communicated to anyone—Except to specified authorised persons.

As Section 1 of the Schedule and the accompanying Notes refer specifically to—apparatus for wireless telegraphy—there would appear to be some discrepancy between the terms of the receiving licence and the information which formed the basis of your Editorial.

If, as stated in the editorial, it is an offence to listen, one would be admitting an offence if one passed information which ought to be passed on, to the appropriate authority. The offence would be one of illegal listening. This seems to me to be a travesty of British Justice.

General Coverage Communications receivers are usually capable of receiving many transmissions which are privileged in one respect or another; a standard FM receiver is not difficult to modify, to receive aircraft and public service bands: short of Big Brother, it would be impossible to prevent such transmissions from being listened to.

It is also illegal with certain exceptions, such as Ansaphone, to tape record telephone conversations, yet the same type of induc-

tive coil is used in some T.V. Hi-Fi adaptors.

It would seem that whilst those with criminal intent, could not only listen, but make what use they pleased, of what they heard: a comparatively innocent licensed operator could get done in every sense of the word.

A somewhat difficult field to control, is that of the purchase of the various types of transmitter, including those of the Walkie-Talkie type being used by people who have no knowledge of how to use them. I am not, nor am I likely to be a licensed operator, but the havoc which these sets, in inexperienced hands, can cause, both to licensed operators and the various other authorised users of transmission equipment, is something which I feel strongly about.—A. D. Crossland (Portsmouth).

## It's free!

I have several good pre-war radio chassis in good condition, together with a workable Grundig tape-recorder (TK2) which I am happy to give away free to any group of under-privileged boys or youth club which would appreciate the equipment. This would have to be collected from Purley, of course.

If you can kindly provide a "link" in this matter, I shall be grateful.—A. Lorand (23 Banstead Road, Purley, Surrey).

## Unjust VAT

*The following is an extract of a letter sent to Mr Sproxtton's MP—Mr Bruce Douglas.*

I represent a group of 25 business men, though there are many more, who retail electronic components. Our customers, besides the general public are Universities, teaching hospitals, schools, polytechnics, and Government Departments. Although most of us own our businesses we work very long hours, for extremely modest rewards. Our main consolation is the fact that we are interested in what we are doing. We have always co-operated with the Government whatever its colour, and try to be law-abiding citizens.

When VAT was introduced, in spite of difficulties, we made it

work. Now, ignoring all the warnings from responsible bodies against bringing in a multiple VAT system, Mr Healey is trying to enforce it. What is the reason for it? Please do not tell me it is to raise revenue. Far more money can be raised far more easily, by simply increasing VAT to 10% or 12%. Was it a sop to the Left Wing, who imagine they are soaking the rich? If so, who are the rich? The medical student building electronic apparatus? The wireless amateur trying to build his experimental transmitter? Was this legislation demanded by the Civil Service, who wanted a valid reason for increasing their ever-proliferating numbers? Whatever the reason, they have produced a scheme that is completely un-workable!

We stock over 6000 different small electronic components, which now carry three different rates of VAT!! In addition to that, on many items we cannot even get a reliable definition of what rate of VAT they carry. Some of us recently had a meeting with Senior Customs and Excise Officials and already many of the rulings they gave us have been turned upside down. When one of our members asked them if we could assume that, if we were charged 25% VAT by our suppliers, that this was a reliable indication of what we charged our customers, we were told "no it has nothing to do with it, you must make up your own mind what you charge"!

To try and work this ludicrous scheme we would need far more staff, at a time when we are hard put to it, to pay the wages of the ones we already employ. Even with unlimited staff we would still have to say to the Customs and Excise, when they ask for their money, "come an examine our stock (all 6000 items) and then give us a written definition of the VAT rate on each one".

It seems to me that Governments, whatever their persuasions are determined to stamp out the small business (and in the case of your own Party, to take over all the big ones) but there are two million of us giving employment to a further four million and patient though we are, we have been needlessly provoked long enough. We are now preparing to fight back. Please bear this in mind.—A. Sproxtton (Home Radio Ltd).

# PRODUCTION LINES

colin riches

## HEATSINKS

Conventional high performance heat-sinks are large and heavy, but where size and weight are of importance, the Redline series of heatsinks provides an efficient economical alternative. They comprise an assembly of twisted vane surfaces mounted on a tubular heat pipe thereby combining the advantages of both.

Typical of the series is the L2220 heatsink which is 200mm by 60mm and weighs 60gm. It accepts two TO-3 devices and has a thermal performance equal to that of a conventional heatsink three times its weight. Information is available from *Redpoint Associates Limited, Lynton Road, Cheney Manor, Swindon, Wilts SN2 2QN.*

## TOROIDAL CORES

TMP Electronic Supplies inform me that they can supply a complete range of toroidal cores for making your own transformers.

All toroidal inductors are highly self shielding, most of the flux lines are contained within the toroidal form thereby keeping the flux density essentially uniform over its entire magnetic path. Stray magnetic fields have little or no effect on toroids. It is seldom necessary to enclose toroids in a screened can to prevent feedback etc, hence multistage filters and amplifiers can be built using them without the worry of coupling between them.

These cores lend themselves easily to use on broadband RF transformers, winding primary and secondary bifilar or trifilar, thereby obtaining an impedance ratio transformation and are particularly effective in interstage applications. The ordinary slug tuned coil can be used in conjunction with a toroid by connecting them both in series, this way the high "Q" of the toroid coil and the convenience of the slug tuned coil are combined.

Further information and prices may be obtained from *TMP Electronic Supplies, 3 Bryn Clyd, Leeswood, Mold, Clwyd, CH7 4RU, North Wales.*

*Practical Wireless, August 1975*

## DATAMATH II


In case you thought the write-up on the Texas Instruments calculator seemed a bit strange, the photograph showed the sophisticated model SR-50 while the text described the T1-2500 II. In addition, the address we gave was of the Bedford plant. *The European Calculator Division is based at 165 Bath Road, Slough SL1 4AD, Berks. Our apologies . . .*



## ORGAN KITS


*A. Marshall and Son (London) Limited (Dept. P.W.) of 42 Cricklewood Broadway, London, NW2 3HD* tell us that they are now able to supply kits of parts (less cabinet) for the P.W. Easybuild Organ. Send a stamped addressed envelope to them for full details.


## HIGH-OUTPUT CASSETTES FROM 3M

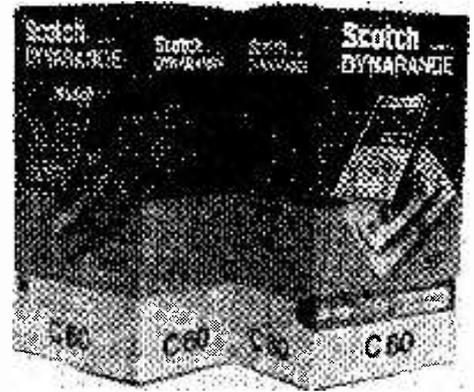

A new range of medium-priced low-noise, high-output cassettes from 3M is claimed to give an improvement of up to 9dB in high frequency response over standard cassettes. Scotch New High Energy cassettes feature a completely new gamma-ferric oxide tape, not a cobalt tape as employed in previous Scotch High Energy cassettes. The uniformity and size of the acicular (needle-like) crystals is very accurately controlled during the manufacturing process, and this, together with binder improvements, has enabled a high density coating to be produced with optimum surface finish, resulting in extended high frequency response.

The cassettes, available in C45, C60 and C90 versions, have 3M's exclusive Posi-Trak back coating for smooth, even winding and improved speed regulation (less wow and flutter). They are manufactured under clean-room conditions and are ultrasonically sealed to exclude dust and other frequency-robbing contaminants. Ultrasonic welding, says 3M, assures virtually stress-free construction, and this technique, coupled with Posi-Trak treatment, produces cassettes which are highly resistant to jamming under normal play or rewind conditions. *3M Ltd., 380-384, Harrow Road, London, W9 2HU.*

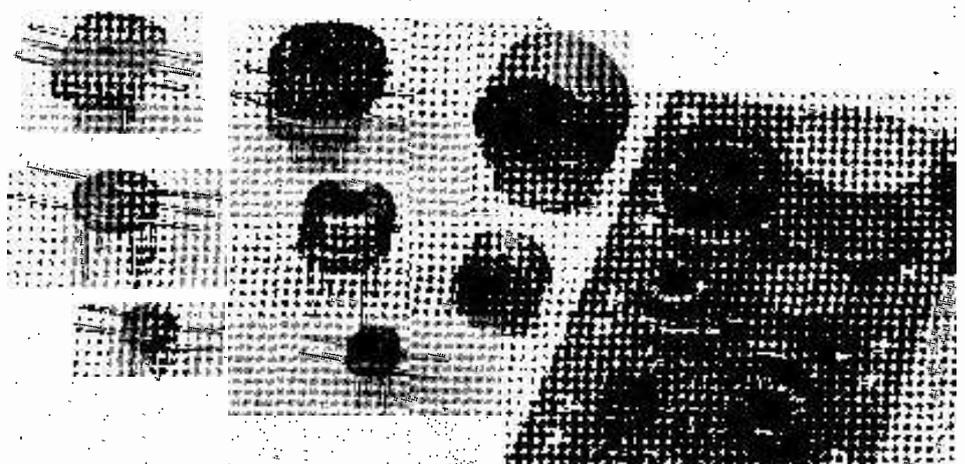

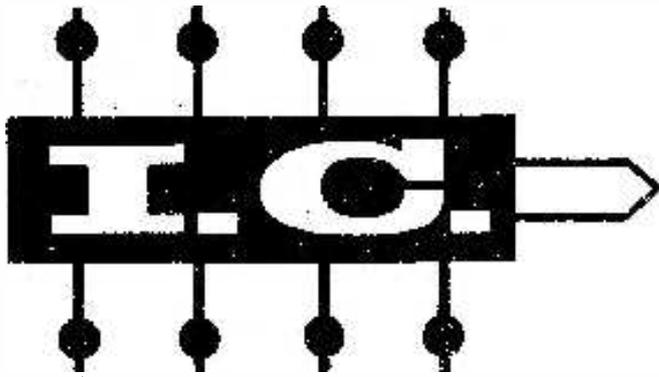

# OF THE MONTH

Number 52

## SGS-Ates TDA2020 POWER AMPLIFIER

IT is only a few years since the first IC audio power amplifiers were introduced, yet now we have quite a wide variety of types and devices becoming available which will handle higher power levels. The TDA2020 device from SGS-Ates is thought to handle more power than any other IC audio amplifier, having a rating of about 20W into a 4Ω load. However, it is not only the high power handling capability which renders the TDA2020 especially attractive. The device incorporates a new type of short circuit protection which automatically limits the dissipated power so as to keep the working point of the output transistors within their safe operating area. Without this protection, any accidental shorting of the loudspeaker leads could destroy the device.

In addition, a thermal shutdown system is included which limits the maximum junction temperature to 135°C. Therefore a large margin of safety in the size of the heat sink is not required, as the risk of thermal runaway, which is found in discrete power amplifiers, does not exist. Special attention has also been given to reducing the 'thump' noise at switch-on and to eliminating cross-over distortion.

### PACKAGE AND HEAT SINK

The TDA2020 is encapsulated in a normal 14-pin quad-in-line package, with a copper insert fitted into the back. This insert must be clamped so that it is in good thermal contact with an external heat sink. Heat transfer is best assisted by means of a thin layer of silicone grease or preferably one of the special heat conducting mixtures containing a silicone grease and a metal oxide.

A plastic spacer is supplied with the TDA2020 for spacing the bolts which attach the external heat sink. Various forms of heat sink are possible, but if maximum power is required, the thermal resistance of the heat sink should not exceed 6°C/W. The thermal resistance between the chip and the copper insert is less than 3°C/W, so if the power being dissipated in the device is 10W, the temperature of the chip is  $9 \times 10 = 90^\circ\text{C}$  above the ambient temperature. On a hot day this may be around 30°C, so the chip temperature is then about 120°C, fairly near to the maximum value of 135°C.

The copper insert is connected electrically to the

silicon substrate and care must be taken to ensure that the heat sink in contact with the copper does not touch any point of the circuit other than the negative supply line.

### CIRCUIT

The TDA2020, like other IC power amplifiers, is basically an operational amplifier, as shown in Fig. 1. The input signal is fed to the non-inverting input of pin 7, negative feedback being taken from the output at pin 14, through R3 to the inverting input at pin 8. Gain is determined by the ratio of R3 to R2 and the HF response by the value of the compensating capacitor C5.

Unlike the circuits employed with most audio power amplifiers, the recommended circuits for the TDA2020 do not employ a capacitor between the output terminal of the device and the loudspeaker. The absence of any large capacitor, therefore, enables a much more compact unit to be built. The omission of this capacitor, however, makes it necessary to arrange that the quiescent potential at the

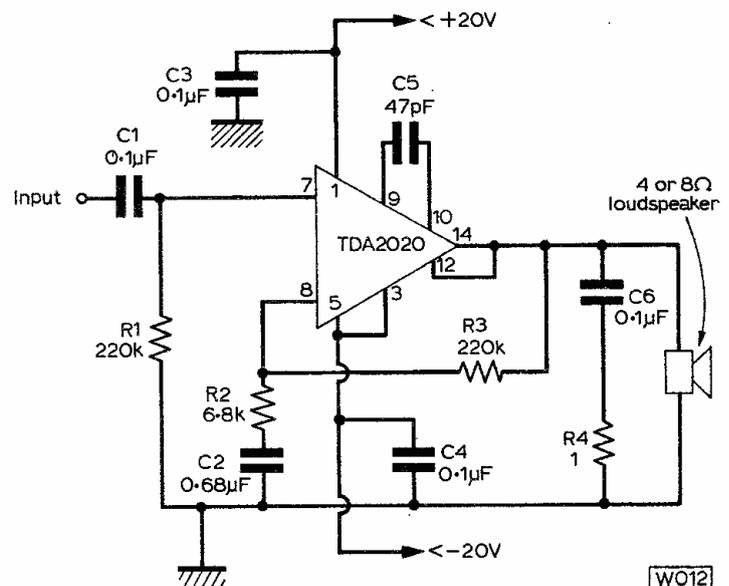


Fig. 1: Circuit configuration for a single channel high power amplifier, utilising the TDA2020.

output (pin 14) is at earth potential, or a steady current would pass through the loudspeaker. Therefore, in the circuit shown, balanced positive and negative supplies are employed, since the quiescent output voltage is mid-way between the power supply lines.

The absolute maximum voltage rating of the TDA2020 is  $\pm 20V$ . Although higher voltages are likely to damage the IC, it will operate quite correctly from supply voltages down to  $\pm 5V$ . The variation of the maximum output power obtainable from a typical device with the supply voltage is shown in Fig. 2. A stabilised supply of  $\pm 17V$  is used to

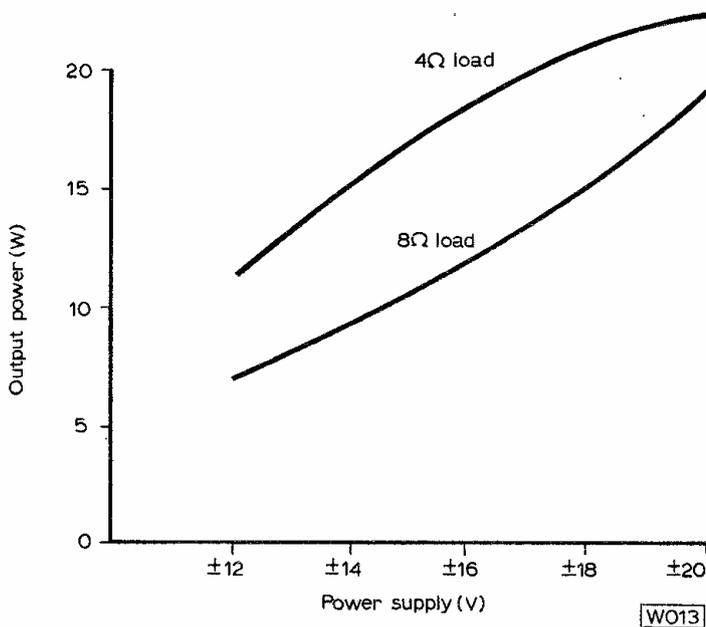


Fig. 2: Graph of maximum output power plotted against supply voltage for the TDA2020.

obtain 20W RMS into a 4Ω loudspeaker at 1% THD (even if the input is a sine wave). Alternatively, 13W RMS into an 8Ω load can be obtained by using a smaller heat sink and the higher impedance speaker.

If a  $\pm 15V$  supply is employed, every TDA2020 device is guaranteed to deliver 15W RMS into a 4Ω load at 1% THD. At lower power levels, less than about 8W, the distortion does not exceed about 0.2% and at most frequencies is about 0.1%.

## STEREO OR QUADRAPHONY

Two of the amplifier circuits shown in Fig. 1 can be employed in a stereo system, but R2 and C2 of the two channels should be replaced by the network shown in Fig. 3 to form a balance control. If desired,

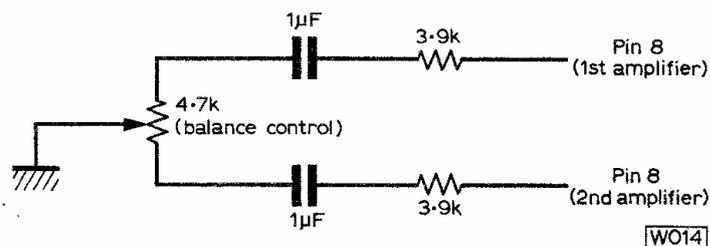


Fig. 3: A stereo amplifier can be made using two of the circuits shown in Fig. 1 with the pin 8 connections replaced with the above network. The feedback resistor R3 remains connected to pin 8.

a common heat sink may be used for both of the devices.

Four TDA2020s can also be utilised in a quadraphonic system, thereby taking full advantage of the circuit simplicity. The only electrolytic capacitors required are those in the power supplies. A common heat sink may be employed for all four channels, although it must obviously have a smaller thermal resistance than the heat sink required for a single channel amplifier.

## 36W CIRCUIT

A single channel 36W circuit employing an 8Ω loudspeaker is shown in Fig. 4. This type of circuit is known as a 'bridge' or push-pull amplifier and requires two TDA2020 devices. The input signal is fed to the inverting input of the left-hand amplifier and to the non-inverting input of the right-hand amplifier. Thus, as the output voltage of one device rises, the other falls, and one obtains twice the voltage swing across the loudspeaker, than would have been obtained with a single device.

Available from Chromasonic Electronics (for £3.90 inc. VAT and p/p) and other distributors.


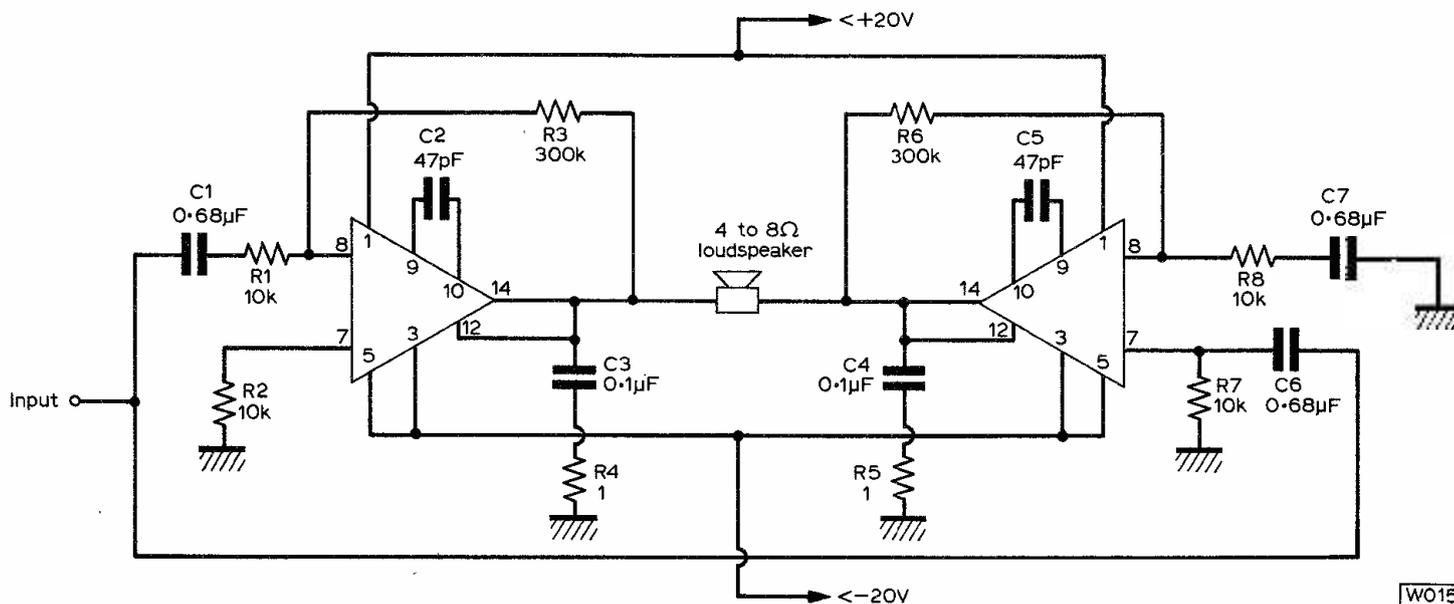


Fig. 4: Circuit diagram of a 36W single channel amplifier using two TDA2020 devices in a bridge circuit.

# A DRAIN-DIP OSCILLATOR

F.G. RAYER G3OGR

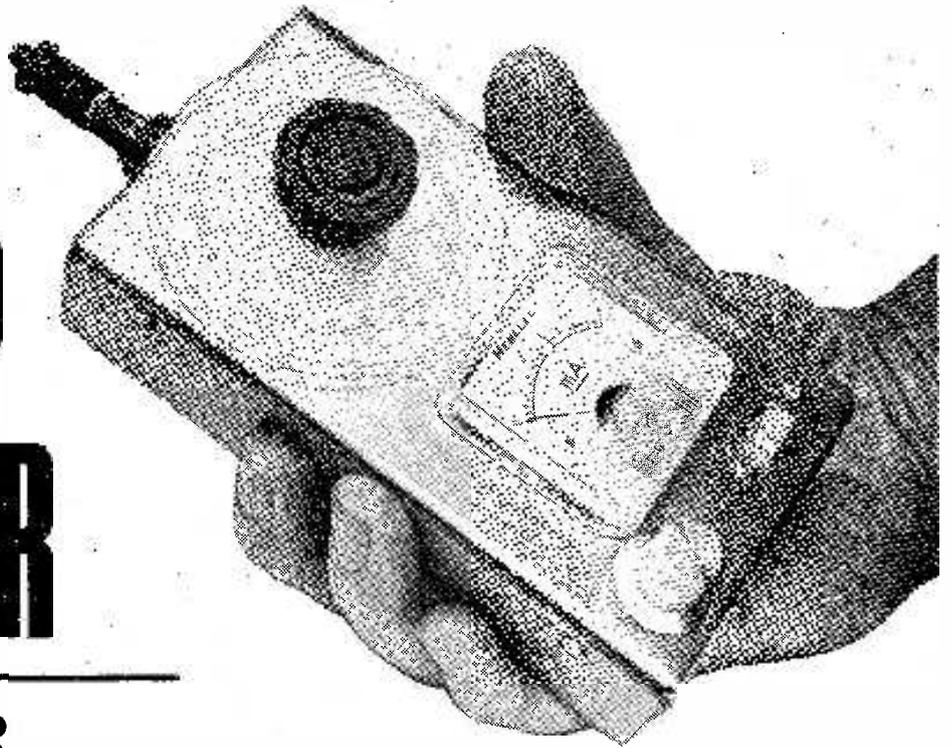

THIS DDO serves the same purposes as the usual type of grid dip oscillator. Its principle usage is in determining the resonant frequency of a tuned circuit but it can also be used to find unknown values of inductance and capacitance. It employs plug-in coils, having four ranges which cover from 3MHz to 50MHz. This includes frequencies for which a DDO will usually be needed, such as checking multiplier stages and other amateur transmitter circuits, or the resonant frequency of aerials, etc.

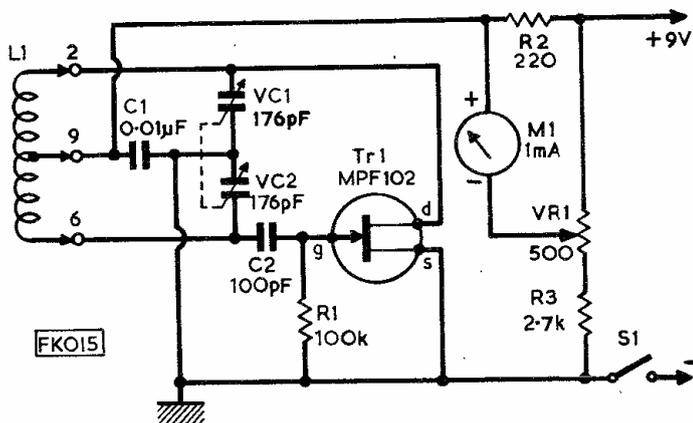


Fig. 1: Schematic diagram of the drain-dip oscillator.

The circuit is shown in Fig. 1, and by using centre-tapped coils it is possible to dispense with the need for any RF choke, which may cause dead spots or reduce efficiency on some frequencies in certain circuits. In fact the upper limit at which the circuit will continue to function depends largely on Tr1; in this case it was near 100MHz. However, at VHF VC1/2 becomes rather large and if there is much need for these frequencies it is better to employ a VHF dip oscillator.

## SENSITIVITY

The circuit is designed to give a generous meter indication. The meter is employed in a bridge circuit with Tr1 and R2 in one side and VR1 and R3

in the other side. It was felt that this provides adequate sensitivity without calling for a microammeter as the indicating instrument or a meter amplifier. In operation, VR1 is adjusted so that the meter reads about half-scale. The instrument is held so that L1 is coupled to the resonant circuit of the equipment. Coupling is tight when L1 and the equipment inductor are side by side or end to end on the same axis, and falls as L1 is moved away, or turned at an angle. With L1 near the equipment inductor, the dip indicated can move the meter completely to the zero stop. However, such tight coupling is normally avoided as the accuracy of frequency readings is then reduced.

The usual procedure is to find approximate resonance by putting L1 quite near the inductor then moving the DDO away a little. Readings also depend on the Q or loading of the circuit under test, the frequency, type of coil and other factors. In the case of inaccessible coils, it may be better to make a link with a few turns each end, placing one loop near L1 and the other on or near the equipment coil.

## INDUCTORS

Each coil is centre tapped and wound as in Fig. 2. The windings are as follows:

- (1) 50-20MHz. 10 turns of 24SWG enamelled wire.
- (2) 32-12MHz. 20 turns of 24SWG enamelled wire.
- (3) 12-5MHz. 50 turns of 34SWG enamelled wire.
- (4) 8-3MHz. 90 turns of 38SWG enamelled wire.

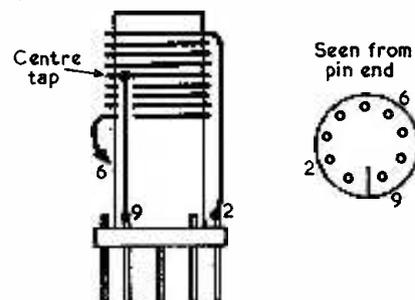


Fig. 2: Each of the four coils required is wound as shown here.

There is no need to employ these exact gauges of wire. It will be noted that three coils will enable the 3-30MHz range to be covered, if this is adequate coverage.

Turns are close wound beginning as near as possible to the threaded end of the formers. The ends can be secured with adhesive or cotton and may run down outside, as in Fig. 2. Alternatively, small holes can be drilled in the formers, so that the leads pass down inside, emerging through further holes near the appropriate pins. The coil formers must be fitted in a holder when soldering to the pins and should be left in it until the pins are cool.

## CONSTRUCTION

The case is made by taking a single 8×3in. flanged universal chassis member and clipping out 90 degree sections from each flange, 1¼in. from the

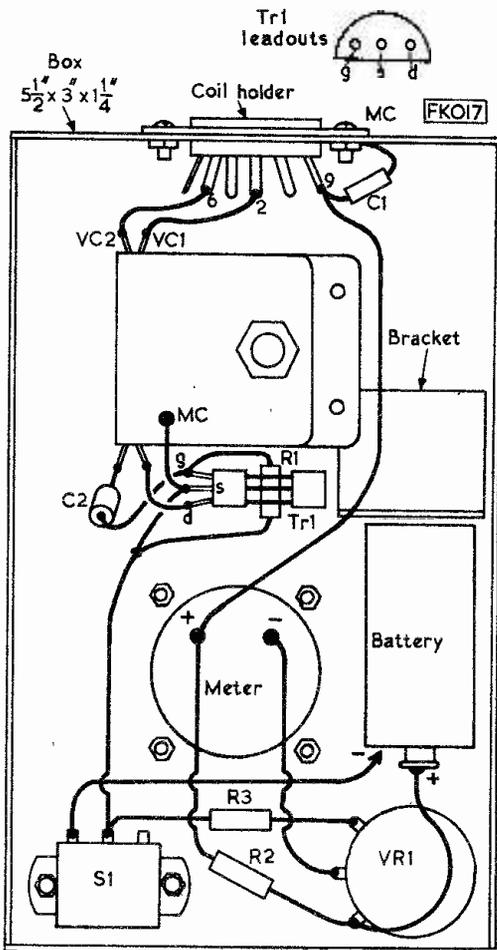


Fig. 3: Layout of components on the front of the case. A corresponding photograph of the oscillator is shown at the right.

ends. The member is then bent across here, to form a flanged, open box 5½×3×1¼in. in size. A sharp bend is obtained by gripping the metal along the required bending line between pieces of wood in a vice.

The ganged capacitor, meter, S1 and VR1 are positioned as in Fig. 3. The capacitor is fixed with three 4BA bolts. One holds the bracket shown, which keeps the battery in position. Ordinary washers or washers cut from the same thickness metal are put under the capacitor at the other fixing positions. Slide switch S1 occupies a slot and is held with two bolts. A separate switch is more convenient than incorporating one with VR1.


Practical Wireless, August 1975

A 3-lead transistor holder was used, mainly as a simple means of trying alternative transistors. The MPF102 seemed most generally suitable but the MFP105 and 2N5459 were found to be satisfactory. The Source tag is soldered to VC1, or has a very short lead here, and this secures the holder. Solder C2 and R1 to the Gate tag and connect the Drain tag to VC1 as in Fig. 3.

The battery should fit between the meter and flange, with VR1 and the bracket at the ends, as in Fig. 3, and its connectors must not be able to touch the metal.
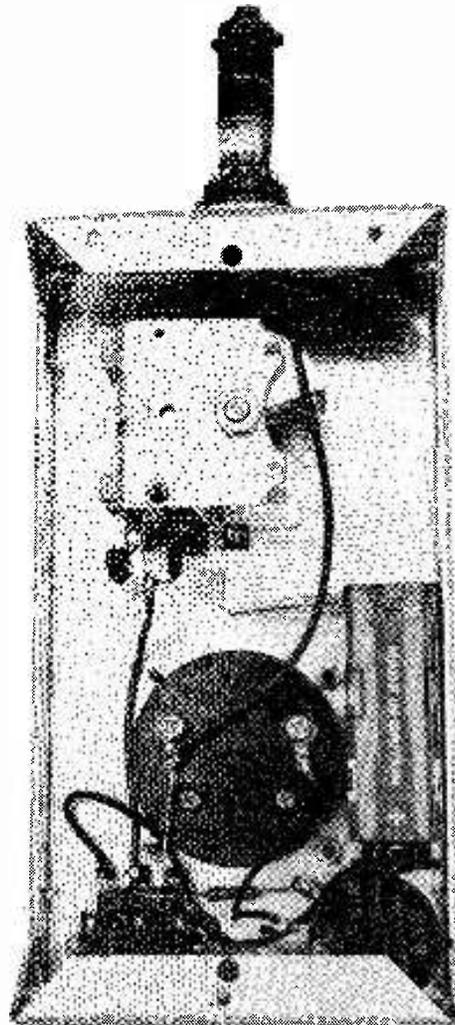
## CALIBRATION

The dial with four scales is fixed with adhesive and a 3in. diameter disc of thin Perspex was prepared with a washer or tank cutter, scribed with a line, and fixed to the control knob with three screws.




## ★ components list

|                                   |                   |                        |
|-----------------------------------|-------------------|------------------------|
| R1 100kΩ                          | } ½ or ¼W.<br>10% | C1 0.01μF disc ceramic |
| R2 220Ω                           |                   | C2 100pF tub. ceramic  |
| R3 2.7kΩ                          |                   | VR1 500Ω linear pot.   |
| VC1/2 176+176pF (Jackson type 00) |                   |                        |
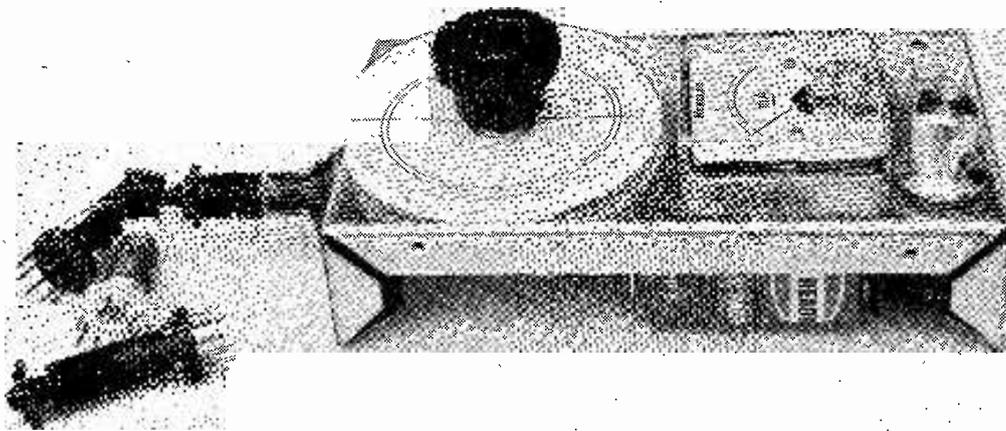
### Miscellaneous

Tr1, MPF102, with socket. M1, 1mA meter. S1, on/off switch. Knobs (2) and dial (see text). Aluminum box approx. 5½ x 3 x 1¼in. Coil formers (4), miniature 9 pin, without cores (Denco). B9A valveholder. Wire for coils.



Finished oscillator with set of coils covering 3 to 50MHz. No cores are fitted to the coil formers. If any adjustment is found necessary to the number or spacing of the turns on a coil this must be made symmetrically about the centre tap.

If VR1 is set for about half scale on the meter, this should do for most of the band. Readings will tend to fall off near the extreme HF end of the coverage provided. When a short wave receiver covering up to 30MHz is available, place the DDO near a wire attached to the aerial socket and tune it to various frequencies, as indicated by the receiver S-meter, or BFO. These frequencies can then be marked on the DDO scales. If necessary, tune up and down to make sure a harmonic response is not being obtained with the receiver. A calibrated absorption wavemeter may also be used for calibration. There will be no ambiguity in frequency readings due to harmonics with this form of wavemeter.

When checking the frequency of a circuit, avoid unnecessarily tight coupling. This will pull the frequency of the DDO, so that a less accurate reading is obtained. Where transmitter multiplier stages or other circuits are tuned up with no power applied, bandswitches must be in the appropriate position because the resonant frequency will be influenced by stray capacitances thrown across the circuit.

If the design of equipment results in the DDO coil being very near metal parts and inductors other than that being checked, so that no definite indication is readily obtained, it is better to employ a coupling link, as described.

## FINDING INDUCTANCE

It may be necessary to check the inductance of unknown short wave coils, or to wind coils to some wanted inductance. The inductance of a winding can be found with reasonable accuracy by connecting a known capacitance across the winding and determining the resonant frequency of the combination with the DDO.

A 100pF 1% silver mica capacitor can be used, and the inductance  $L$  in  $\mu\text{H}$  can then be found from the following:

$$L = \frac{25330}{100 \times F^2}$$

$F$  is the frequency in MHz, as found with the DDO. For example, assume resonance arises at 10MHz. Then  $25330/100 \times 10 \times 10 = 2.53\mu\text{H}$ .

## FINDING CAPACITANCE

By placing the unknown capacitor across a known inductance, the same method can be used to determine the capacitor value. This may be useful with capacitors with obliterated markings, or to find the value of variable capacitors or trimmers.

A  $5\mu\text{H}$  inductor is convenient and can be wound on a 1in. diameter former using 24SWG enamelled wire. Wind six turns closewound leave a space of  $\frac{1}{8}$ in., and wind a further six turns. The ends are each 1in. long. If maximum accuracy is required, the inductance can be modified slightly by increasing or reducing the space, checking resonant frequency by the formula given.

The value of the unknown capacitor  $C$  in pF can now be found from:

$$C = \frac{25330}{5 \times F^2}$$

$F$  is the frequency in MHz, as before. For example, suppose resonance arises at 10MHz. From this,  $25330/5 \times 10 \times 10 = 50.6\text{pF}$ .

A check by these means will show the value of a capacitor or inductor with enough accuracy for most purposes. For maximum accuracy, the capacitor or inductor forming the standard should be of close tolerance and the resonant frequency checked with a finely calibrated receiver, tuned to the DDO.

PW

# CQ! CQ! CQ! CQ!

## INFORMATION WANTED

...service manual or circuit diagram for a Grundig Prima Boy. Will refund postage after I've photo-copied it.—Eugene De Mello, P.O. Box 295, Zanzibar.

...circuits to build a VLF 3-30kHz LF 30-300kHz converter.—C. Mahoney, 37 Camp Place, Callander, Perthshire, Scotland.

...buy or borrow circuit details of Bendix RA10, P.W. September 58, R101-B (ARN-6); source for PU head Cosmocord GP19 or similar; surplus conversion manuals Nos. 2 and 3.—A.D. Besford, G3NHU, 49 Blake Road, Gt. Yarmouth Norfolk.

...loan or purchase handbook for Lafayette HA-600A receiver.—B. Harvey, 114 St. Nicholas Drive, Wybers Wood, Grimsby, South Humberside.

...article on DX'ers Processing Unit from P. W. July 1972.—W. E. Philpott, Russell House, East Cliff, Rye, Sussex, TN31 7LP.


...information and circuit diagrams on modified No. 19 set and B44 Mk. 3.—J. Apollo-Oluoch, Comm. Dept. E.A.P.L., Box 151, Kisumu, Kenya.

...buy or borrow any info. on Avo electronic CT38, especially opv valve.—P. Saunders, 13 Pulteney Gardens, Bath.

...circuit or info on micro voltmeter model No. 10B serial No. 503 (U.S.A.)—F. Higgins, 4 Rural Cottages, Shrawardine, Shrewsbury.

...gen required on manufacturer/importer of Sonora tape recorder. Also cct. diagram required.—K. D. Halliday, 145 Wenlock Road, South Shields, Tyne and Wear.

# GOING BACK...

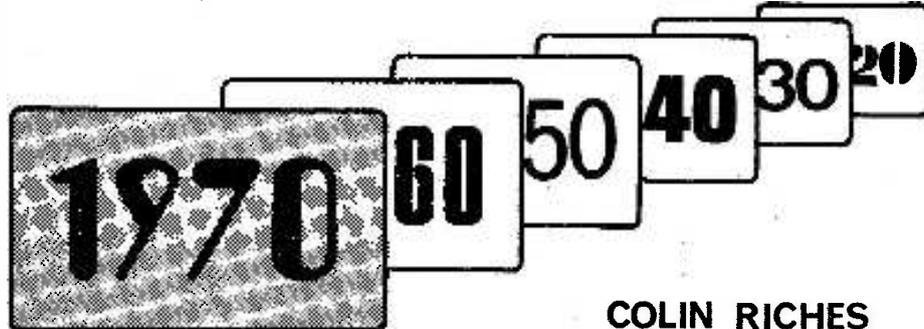

## The Fultograph

FIRST, I would like to say a sincere "thank you" to all those readers who have written to me with information on the "Fultograph". I am at present compiling an article on this fascinating machine and hope to publish it in the near future.

## A shop for us

I RECENTLY received a copy of the Tudor Rees (Vintage Services) catalogue and was pleasantly surprised on opening it to find vast lists of vintage radio books, service manuals, magazines and equipment offered for sale.

If you are keen on renovating vintage receivers, buying spare parts or complete models, then this is the catalogue for you.

Tudor Rees has a shop at 64 Broad Street, Staple Hill, Bristol BS16 5NL, and as you can see from the photograph it's pretty well stocked.

## COLIN RICHES

Tudor tells me that he has always been interested in radio and electronics from his school-days (he's now 31) so was brought up on valves and the early days of transistors (yours truly can remember paying £1 for a "red-spot" type). He was an apprentice at the local aircraft factory and worked there with "things electronic". After leaving that, he spent approximately seven years at the Bristol University as an electronics technician—but with transistor technology becoming "integrated circuit" technology, he realised he was fast becoming bored with the work as it was, to him, more maths than electronics and all the "mystery and mystic" had gone.

Owning a vintage car (1937 Chevrolet) and belonging to various vintage clubs, Tudor was often asked by people to repair old car radios (valve/vibrator jobs). After the first one, he became hooked—valves and components he could see! Marvellous! His repairs to vintage sets soon

moved into the domestic field and he did jobs from his home until demand became so great he opened his shop.

The business is now in its third year and Tudor says he's "touching wood" that it will continue to flourish. He comments, "There are easier ways of making a living, but not so many that are so interesting! Every day there is something new and the old designs were so clever!"

He tells me that it really is a form of nostalgia to him. Nostalgia from the days when as a boy he built radios on wooden bases using old *Practical Wireless* circuits and using 2 volt battery triodes, etc. (bring back the PM2!). It's also nostalgia from the golden days of radio, when British wireless sets were British made—and good.

Personally, Tudor Rees now collects early American wireless sets of about the 1930s, the Scott, McMurdo, etc.

His shop stocks most equipment from 1920-1950. He literally gets asked for almost anything from this period and says that there is quite a demand for the early 1930's mains radios. Also, almost everybody he speaks to asks for crystal sets.

## Catalogue

The catalogue gives a good insight into the kind of gear for sale in Mr. Rees's shop and he tells me it is his intention to offer a full service to the vintage radio collector and enthusiast.

If you would like to have a copy of the catalogue send 40p plus 7p to the above-mentioned address. If you wish to contact the shop by telephone, the number is Bristol (0272) 565472.

## Did you know?

I N 1926 an Aberdeen court imposed fines of £2 each on two wireless "pirates."

The Sheriff, or magistrate, was told by the prosecution that fines of £10 had been imposed for similar offences "south of the border."

The Sheriff replied that heavier fines might be required to bring Englishmen to their senses but he hoped the Scotsmen, with their appreciation of the value of money, would come to their senses through the imposition of a much smaller fine!



Mr. Rees' 'Aladdin's Cave' of vintage radio equipment.

next month  
in  
the new style..

# Television

AUGUST 1975

ON SALE 21st. JULY

40p

## ● VIDEOTAPE RECORDING

Videotape recorders intended for the domestic and educational markets are now available. To handle such machines it is necessary to understand the specialised circuit techniques used and the mechanical arrangements. This is the first part of a new series.

## ● THORN 9000 CHASSIS


Thorn's new 9000 chassis, built around the PIL colour tube, employs much novel circuitry including the Syclops combined line-output/power supply circuit. How this and the rest of the circuit works will be explained.

## ● OVER-VOLTAGE PROTECTION

With the advent of solid-state chassis using stabilised power supplies came the need for over-voltage protection, to prevent the h.t. or e.h.t. rising excessively in the event of a fault in the regulator circuit. This guide covers many different circuit techniques.
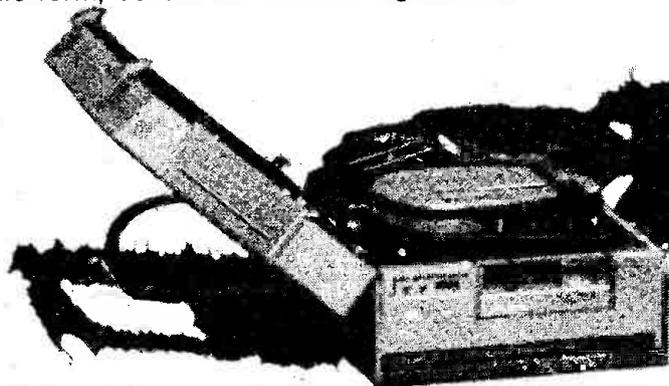
## ● ELECTRONIC LOGIC

Many will already have come across logic circuitry; those now plunging into the peculiarities of Ceefax/Oracle decoding will shortly have to do so. Our guide, mainly in diagrammatic form, covers the various logic elements.



# DIGITAL WAVEFORM GENERATOR

John Smith C. Eng PART THREE

READERS not having access to the instrumentation described in Part 2, may nevertheless wish to build a function generator. These readers can make a number of simplifications to the design, without impairing the performance more than their lack of instrumentation dictates.

Consider the circuit diagrams shown in Part 1. The decade switching is unnecessary because calibration inaccuracies make S3 and S4 virtually ineffective. Therefore the first simplification made is to dispense with these two decade switches and employ the coarse steps given by S1 only.

Secondly, it is unnecessary to have two separate banks of resistors. Without instrumentation to select these resistors the up and down strokes of the triangular waveform cannot be made symmetrical. Therefore pins 4 and 5 of the 8038 are linked together and a single-gang nine-way switch is employed instead of the more expensive twin gang unit.

If desired a "fine" adjustment may be incorporated using a 5kΩ potentiometer (VR6) in series with the switch (see the simplified function generator diagram, Figs. 10 and 11).

Thirdly, the removal of the decade switches means that the LED indicators are unnecessary, and these are dispensed with.

Finally, the sine purity potentiometers VR1 and VR2 may be omitted as they have very little effect on the waveform. The rest of the circuitry remains the same, but as a consequence of the simplifications outlined, a very much smaller case may be used to house the instrument.

In the simplified circuit diagram shown in Fig. 10, capacitors C1 to C7 have the design values shown in the early components list, but the front panel should be differently marked. As there are no LEDs to indicate the decimal places, the range switch must be marked thus: Range 1: ×1 second; Range 2: ×100mSec; Range 3: ×10mSec; Range 4: ×1mSec; Range 5: ×100μSec; Range 6: ×10μSec; Range 7: ×1μSec.

Of course range seven is no more accurate in this design than it is in the earlier model.

## COMPONENTS

Where marked with the same component number the same component as shown in the first components

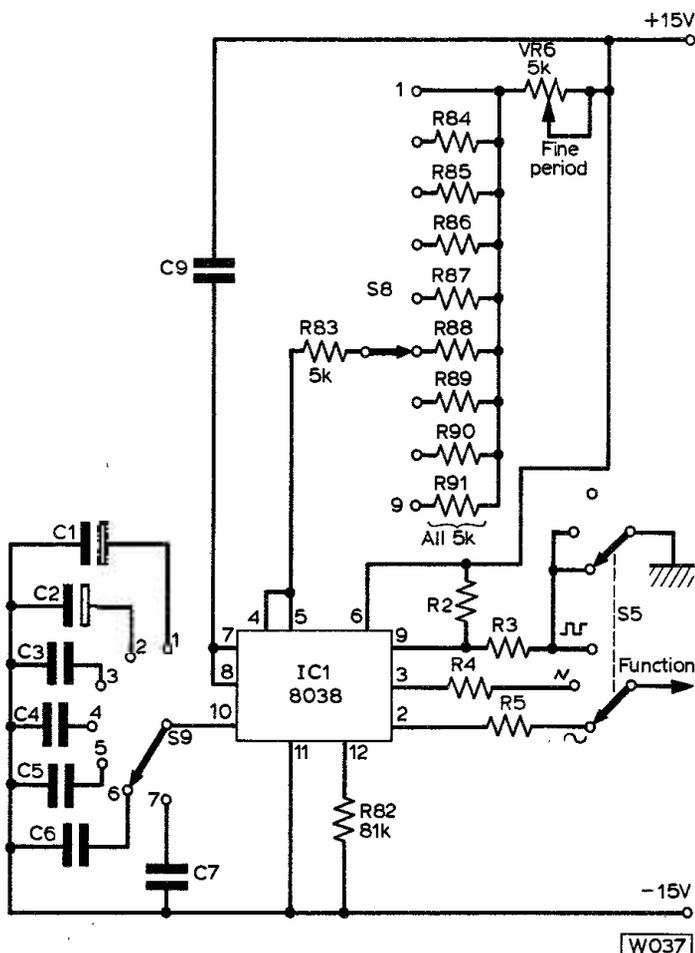


Fig. 10: Circuit diagram of the main generator section of the simplified Digital Waveform Generator.

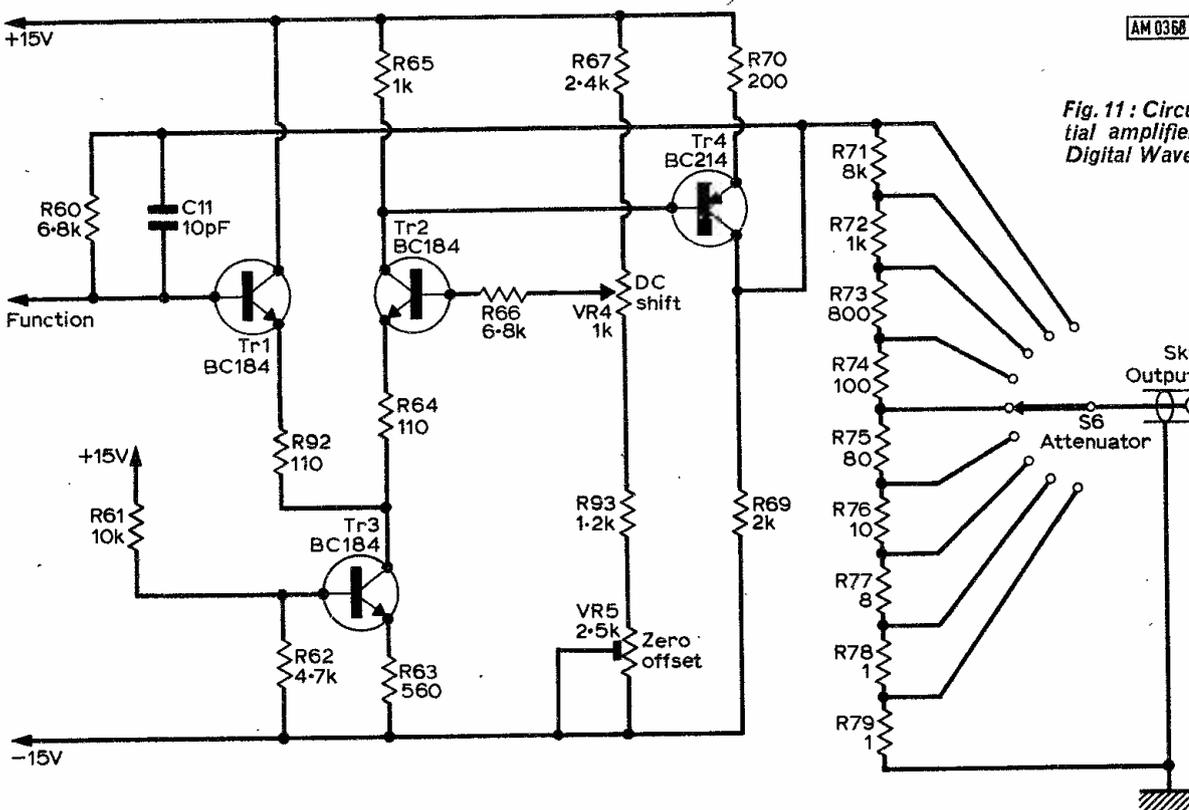


Fig. 11: Circuit diagram of the Differential amplifier used in the simplified Digital Waveform Generator.

list is used. The components which differ or are added are:

- S8 Single-pole nine-way switch.
- S9 Single-pole seven-way switch.
- R82 81kΩ
- R83-R91 5kΩ resistors (10kΩ + 10kΩ in parallel).
- R92 110Ω
- R93 1.2kΩ.
- VR5 2.5kΩ.
- VR6 5kΩ.

The unnecessary components are: R1, R6 to R59, R68, VR1, VR2, VR3, S1, S2, S3, S4, C12, D1, D2, D3.

## PERIOD VERSUS FREQUENCY

This simplified signal generator design is calibrated for *period* in the same manner as the more accurate instrument described in Part 2. However, some readers constructing the simplified instrument may prefer to have switched *frequencies* as an alternative to period calibration. The changes required are quite simple. First the range switch must be marked thus: Range 1: ×0.1Hz; Range 2: ×1Hz; Range 3: ×10Hz; Range 4: ×100Hz; Range 5: ×1kHz; Range 6: ×10kHz; Range 7: ×100kHz.

Switch S8 now becomes a multiplier giving 100, 200, 300, 400Hz etc. up to 900Hz. VR6 cannot be used in this arrangement and must be replaced by a link. Secondly the multiplier switch S8 must be wired with different values of resistor as shown in Fig. 12 to give the preselected frequencies. As with the previous design use of the 8038BC will give much higher accuracy and better waveforms than the cheaper CC model.

## USING THE FUNCTION GENERATOR

When using the function generator it may be convenient to convert from period measurement to frequency. The relationship between period (p) and frequency (f) is given simply by  $f=1/p$ .

Table 1 gives this relationship for the first two significant decades in the form of a four figure num-

ber. To use the table find the row given by the first decade and the column given by the second decade and multiply the four figure number by the appropriate factor.

For example, if the decade switches are set to 3, 6, 0 on range 4 (3.6mSec) the frequency is 277.8Hz (divide the number appearing in row 3, P1, column 6, P2, by 10).

Alternatively if a particular frequency is required, 1.8kHz for example, look for the nearest frequency given in the table; 1818 in this case. 1.818kHz is obtainable on Range 5 with the decade switches set to 550. To produce a frequency nearer to 1.8kHz the third decade switch must be used. In this case it gives steps of  $3.2 (1818 - 1786)/10$ , therefore five or six steps on this third decade are necessary to obtain 1.8kHz.

It must be remembered that the third decade *lowers* the frequency set by the first two switches.

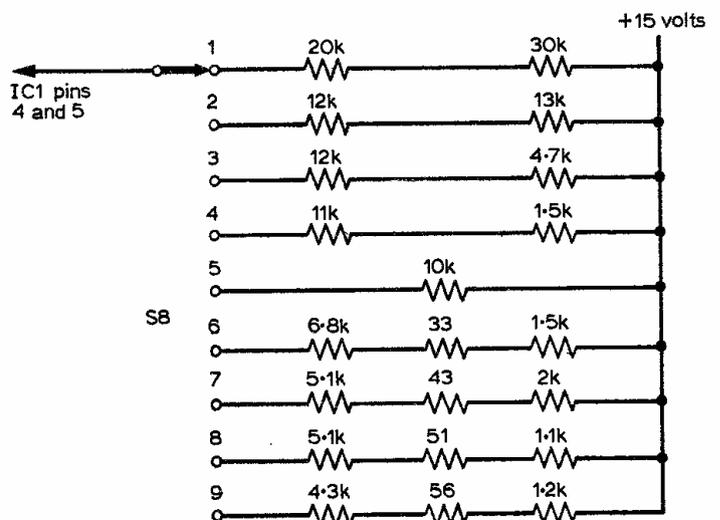


Fig. 12: Values of resistors to be wired to the multiplier switch S8 are shown here.

TABLE I

| P1 | P2    |      |      |      |      |      |      |      |      |      |
|----|-------|------|------|------|------|------|------|------|------|------|
|    | 0     | 1    | 2    | 3    | 4    | 5    | 6    | 7    | 8    | 9    |
| 1  | 10000 | 9091 | 8333 | 7692 | 7143 | 6667 | 6250 | 5882 | 5556 | 5263 |
| 2  | 5000  | 4762 | 4546 | 4348 | 4167 | 4000 | 3846 | 3704 | 3571 | 3448 |
| 3  | 3333  | 3226 | 3125 | 3030 | 2941 | 2857 | 2778 | 2703 | 2632 | 2564 |
| 4  | 2500  | 2439 | 2381 | 2316 | 2273 | 2222 | 2174 | 2128 | 2083 | 2041 |
| 5  | 2000  | 1961 | 1923 | 1887 | 1852 | 1818 | 1786 | 1754 | 1724 | 1695 |
| 6  | 1667  | 1639 | 1613 | 1587 | 1563 | 1539 | 1515 | 1493 | 1471 | 1449 |
| 7  | 1429  | 1408 | 1389 | 1370 | 1351 | 1333 | 1316 | 1299 | 1282 | 1266 |
| 8  | 1250  | 1235 | 1220 | 1205 | 1190 | 1176 | 1163 | 1149 | 1136 | 1124 |
| 9  | 1111  | 1099 | 1087 | 1075 | 1064 | 1053 | 1042 | 1031 | 1020 | 1010 |

Range 1:  $\div 10,000$  to give Hz  
 Range 2:  $\div 1,000$  to give Hz  
 Range 3:  $\div 100$  to give Hz  
 Range 4:  $\div 10$  to give Hz  
 Range 5:  $\div 1,000$  to give kHz  
 Range 6:  $\div 100$  to give kHz  
 Range 7:  $\div 10$  to give kHz

P3 The third decade lowers the frequency in roughly equal steps. For example, at P1 and P2 setting of 18, P3 reduces frequency in the steps 1019, 1018, 1017, etc.

With a little practice the use of the table for converting period to frequency or frequency to period settings is quick and accurate.

### USING SINE WAVES

Apart from their use as a signal source in the development of circuits, sine waves are invaluable for gain-frequency plots of amplifiers. In the case of an audio amplifier a set of characteristics may be plotted showing level response, maximum bass/treble response and minimum bass/treble response.

The fine adjustments possible using the three decade switches makes the generator admirably suited to plotting the characteristics of scratch filters, or indeed any other kind of filter working in the 0.1Hz to 100kHz range.

A further use is in the gain-phase analysis of general feedback amplifier design for stability.

### USING TRIANGULAR WAVES

The triangular waveform can be very useful in the investigation of trigger levels for devices like Schmitt trigger circuits, logic circuits, pulse generators, etc. At low frequencies it provides a slowly rising ramp where time and voltage are related. Such a waveform can often be most useful in general circuit design where linearity is important.

The triangular waveform can be used for investigating intermodulation distortion. When examining an amplifier with sine waves, deviation from linearity does not show up very well and with square waves not at all. However, providing there is no distortion due to frequency limitations, deviations from linearity shows itself most clearly on triangular waveforms.

It is well known that non-linear characteristics, such as a diode, can be used for demodulation or frequency changing simply by applying two signals and using the resulting sum and difference frequencies generated. Similarly, if a multiplicity of frequencies are applied to an amplifier which has non-linear characteristics sum and difference (intermodulation) components are produced. This is why some inferior amplifiers can pick up interference from powerful radio stations.

Great care must be exercised in testing to ensure that frequency limitations are not causing distortion, a factor of at least 20 to 25 must be allowed for faithfully reproducing the harmonics.

For example an amplifier of 10Hz to 100kHz bandwidth should be tested with a triangular waveform of less than 4 to 5kHz, 500Hz to 1kHz would be ideal.

In the case of class B output stages any crossover or unbalance in the output amplifiers is immediately apparent when the triangular waveshape is applied. With these tests it is desirable to use a double beam oscilloscope to compare input directly with output signal, however, if this facility is not available the linearity of the generator is good enough to obtain useful results from a single beam instrument.

### SQUARE WAVE TESTING

The square wave signal is used as a source for testing digital circuits such as counters, logic, digital frequency meters, etc., but is also used increasingly by hi-fi specialists for testing audio amplifiers.

Gain frequency plotting and linearity checks with sine and triangular waveforms tell little about the transient response of amplifiers. Square wave tests are capable of showing unwanted resonances which can spoil an amplifier's ability to reproduce transients, (sharply changing waveforms such as cymbals).

A well-shaped square wave signal consists of the fundamental frequency plus a large number of harmonics, which are necessary to form a precise square wave signal. Therefore when a square wave is applied to an amplifier it is, in effect, producing a whole band of frequencies. This means that when the square wave output is viewed on an oscilloscope its shape is determined by the characteristics of the amplifier.

The characteristics of an amplifier are investigated by connecting it to a resistive load and applying a small amplitude square wave signal to the input. It is essential in this test to ensure that the input signal is small enough to prevent saturation of any stage in the amplifier.


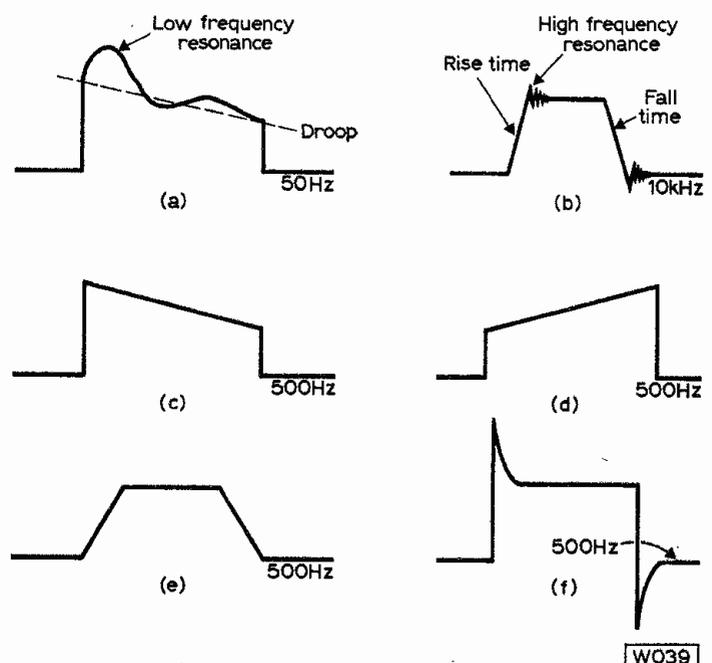


Fig. 13: Typical square wave responses. (a) Pulse with droop and low frequency resonance. (b) Pulse with low rise and fall times and high frequency resonance (c) Effect of bass cut (d) Effect of bass boost (e) Effect of treble cut (f) Effect of treble boost.

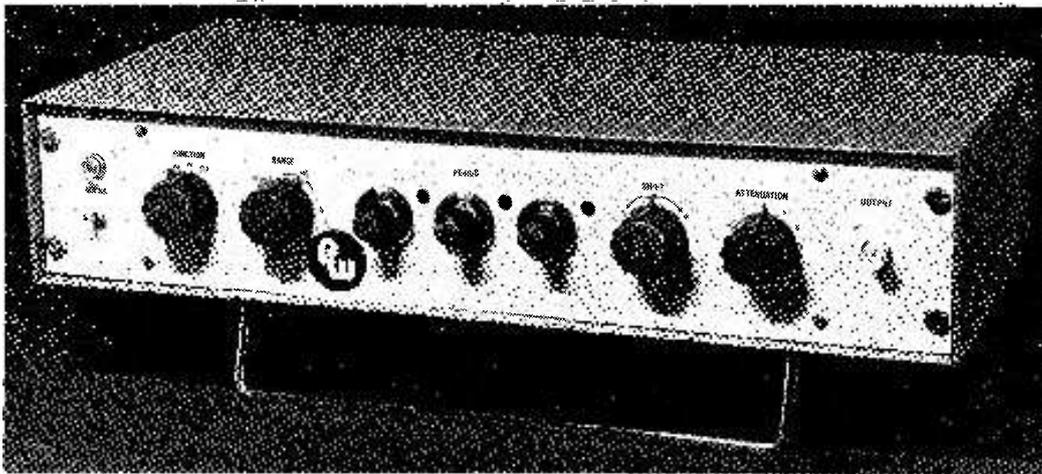

The completed Digital Waveform Generator.

## SQUARE WAVE RESPONSES

The output signal will not be perfect, Figs. 13a and 13b show the possible responses to low and higher frequency square waves. Fig. 13a shows a pulse with droop and a low frequency resonance, such a resonance could be concerned with the low frequency phase-gain characteristics of the amplifier.

Low frequency resonance is not common, but the pulse will droop in any capacitively coupled amplifier, as it is related to the low frequency 3dB point. Strictly speaking it is difficult to relate droop to the 3dB point in an amplifier, because the rate at which the amplifier response falls towards cut off influences the droop. However, many writers assume a single time constant (6dB per octave) and estimate the 3dB point from the droop that this single time constant causes. Droop is also caused by the bass cut control and may be used to evaluate the operation of the bass tone circuits.

Fig. 13b shows the response to a high frequency square wave. Here the rise and fall times are related to the high frequency response and may be used to calculate this response if the 6dB per octave time constant is assumed. The figure also shows some high frequency resonance which may be caused by the overall gain-phase response, alternatively it may be caused by a single faulty stage in the amplifier. Whatever the cause, such resonances must be eliminated.

## TONE CONTROLS

Figs. 13c, d, e, and f show the effects on a 500Hz signal of the bass cut, bass boost, treble cut and treble boost controls respectively.

The bass cut control increases the droop (c), whilst the bass boost control gives a rising response (d). However, if a very low frequency signal is used the cut off characteristics of the amplifier causes droop which no amount of bass boost can compensate.

In waveform (e) it is apparent that treble cut gives rise to a slowly rising response. (Most of the high frequencies are concentrated in the leading edge of the pulse). Treble boost, on the other hand increases the amplitude of the high frequency components giving rise to the spikes shown in (f). In practice the low frequency characteristics show up better at low square wave frequencies (50 to 100Hz), whilst the high frequency effects are more apparent at the higher frequencies. (1 to 4kHz).

The testing of loudspeaker enclosure damping can also be carried out with the aid of square waves. In this test the square wave generator must drive a powerful amplifier coupled to the loudspeaker through a high resistance. A resistance some ten times that of the loudspeaker will be necessary using an amplifier capable of operating without its loudspeaker load. The amplifier must also be capable of operating at frequencies below that of the speaker resonance under test, and capable of producing satisfactory square waves at 20 to 30Hz.

Fig. 14 shows the test circuit arrangement. A high gain oscilloscope is necessary to see the type of response shown. This response represents an underdamped system where the box or loudspeaker is resonating.

This method provides a means of investigating the effect of various cavities and baffles using a variety of loudspeakers. Removing or omitting the high resistance will cause the amplifier to damp the loudspeaker system (a highly desirable characteristic in practice) which will mask the effects of acoustic damping in the loudspeaker system.

These suggestions represent just a few uses for the function generator, there are many more. Readers constructing the instrument will find that it is an invaluable signal source for testing their various constructional projects.

**ERROR** In the circuit of Fig. 4, Part 1, the resistor in the bias chain of Tr3 (R61) was shown connected to earth. It should in fact be connected to the +15V line as indicated in the board layout in Fig. 6 Part 2.

PW

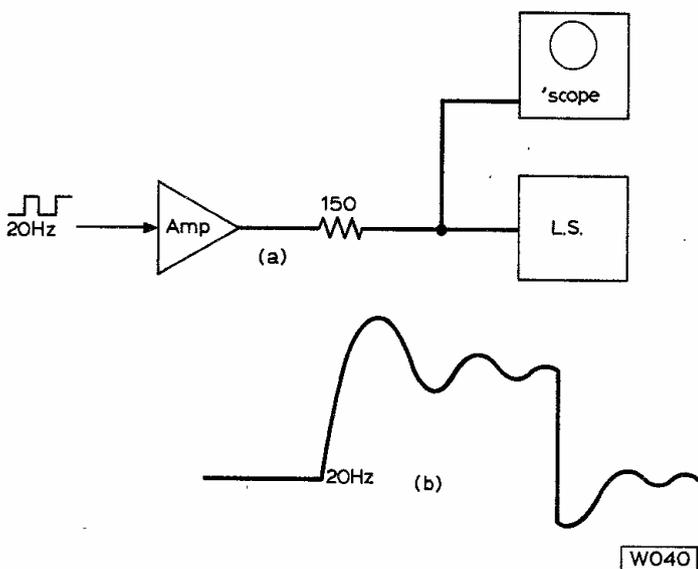


Fig. 14: (a) Test set-up for producing the characteristics of a loudspeaker in its enclosure (b) The response of an underdamped system.

# HOT LINES

ON RECENT DEVELOPMENTS

## RACING ELECTRONICS

**W**HEN a racing car goes out on to the track, a great number of estimates have to be made. For example, how long the fuel will last. If you pull the car in for refuelling too quickly, you will lose valuable time. If you leave it too late, it may run out of petrol and you'll lose the race altogether.

At Indianapolis, Indiana, the Gatorade-McLaren racing car is different—it cuts out all the guesswork. Under the bonnet sits an engine plus a radio transmitter. The input of the transmitter accepts signals from various sensors strategically placed, and the output is radioed back to a computer in the pits. A printout or a visual display tells the pit mechanics and engineers exactly what the state of the car is—and the information is never more than one second old! The sensors are scanned 100 times every second by the computer.

A tiny propeller in the fuel lead tells the computer exactly how much fuel is being used and the computer can then display exactly how much is left. It can also time the car each lap.

Some 14 of the car's functions are monitored. These include the "ride height" of each wheel, the oil and water temperature and their pressures, forward and sideways acceleration, manifold pressure, air inlet temperature etc.

Perhaps the ultimate will be where the driver sits on the side of the track and "drives" the car by looking at a tv screen which shows the track immediately in front of the radio-steered car via a small tv camera. Possible, but remote.

## OPTICAL COAX?

Have you ever looked at a piece of coaxial cable and thought how much material and effort goes into producing it? All that copper. Now think of the larger coaxial cables used in professional telephone cable systems etc. It could well be that the coax cable will be replaced, gradually, by plastic fibres.

A laser beam can be shone down a plastic light fibre (like the "mare's tail" displays) and the single beam can carry some six different tv channels or a very large number of

telephone conversations. Good thing about plastic fibre is that it doesn't rot or corrode, it's light in weight and the system isn't prone to electromagnetic or electrostatic interference.

At the University of London, one experiment has been to pass signals down a light fibre (just one) and it is possible to "tap" off the signal anywhere along the fibre without breaking the plastic. A sensor—so tiny that it can be mounted on the inside edges of a small clothes peg, is simply clipped anywhere along the fibre and the signal can be heard via the tap.

It is interesting to note that two of the large connector manufacturers—Amphenol and ITT Cannon, already offer connectors not for connecting things electrically, but optically. Amphenol has a small "coaxial type" plug and socket, while ITT Cannon has a multi "pin" plug and socket.

## 20% EFFICIENCY CELL

Another thing not to be taken lightly is the new approach to photo-cells by Bell Labs. A 5 micron thick gallium arsenide coating is one of the secrets which, it is claimed, assists in the making of a cell which will have nearly 20% efficiency. While 20% may not sound very high to some, it is quite an achievement when comparing it with the 8% efficiency of the current silicon cell.

## GIVE US A TUNE!

The world of computers seems to be a place where the smaller and smaller gets ever more complex. We've reached the stage of mini-computers which seem to have amazing versatility when coupled to certain other items. For example I hear of one application where a minicomputer was programmed and coupled to a suitably "voiced" oscillator and tone forming circuits. The net result and point to it all was that the computer played the second instrument in a Beethoven clarinet duet and listeners were unable to tell which was the computer and which was the real man plus proper clarinet.

Perhaps schoolboys will be programming their more advanced pocket calculators to sing Good King

Wenceslas outside your door at Christmas thereby allowing them to concentrate on the more important task of collecting and counting the money.

## DIAMONDS ARE . . .

Diamonds are supposed to be a girl's best friend so perhaps sapphire could do something for the men? It's certainly doing something for the giant US company Hughes Aircraft. This company had been making liquid crystal displays by placing same on a bulk silicon substrate. This same substrate also contained the addressing and switching circuitry. Now, Hughes is building the display but using a sapphire substrate. Better yield and isolation between elements plus simpler processing are some of the advantages. A 10,000 element display has been fabricated using this type of substrate and it measures only one inch square. Rumour has it that Hughes is now working on a 2 inch square device.

I would think that viewing a single element on the sapphire substrate one would see precious little.

## TIE-PIN TELLY?

Some time back I commented on a minute calculator which fitted on the wrist. I note that the Optel Corp. in America has just launched a wrist-watch which is also a calculator—the whole lot in a single wristwatch case. Prices quoted are between 500 dollars and 1,000 dollars and the watches/calculators have eight digit readouts and employ liquid crystal displays. The batteries are disposable types and should last for a least one year.

About time we saw the tie-pin television isn't it?

## BUG-FINDER

In the June issue we referred to the EMI wide-band receiver as the Bloodhound. This should have read 'Bug-hound.' Our apologies.



# NEW BOOKS

## A GUIDE TO AMATEUR RADIO (Sixteenth Edition)

By Pat Hawker G3VA

Published by the Radio Society of Great Britain,

35 Doughty Street, London WC1N 2AE

112 pages 9½ × 7½ in. (248 × 184mm)

Price 98p (£1.10 inc. p/p)

**A**S compiler of the Amateur Bands feature every month I receive many letters from would-be listeners to the short wave bands. One question pops up more frequently than any other, "where can I get a book that explains all the jargon I hear and read about concerning the SW bands?" "What's a QSL card?" is another favourite.

Having enjoyed the privileges of a licensed radio amateur for more years than I care to remember I usually try to steer a newcomer's interest towards the amateur bands! I see no point in listening to broadcast stations, frequently using very high power, when I can be talking to another amateur thousands of miles away on gear that I have built myself. One cannot achieve this overnight but it should be the natural target of any short wave listener. It is at this point that I always advise newcomers to write to the RSGB for the Guide!

In reviewing a book it is all too easy to list material that one feels ought to have been included in the interests of completeness. In the Guide this seems to me to be quite impossible! It's all there, page after page of solid information, all the hieroglyphics and jargon carefully explained in much detail. However, since this is the sixteenth edition it is inevitable that much of the material used was already set and the consequent saving in production costs is reflected in the very low cover price.

For year after year the Council of the RSGB has dodged the issue of revising the Guide and the longer it is left the costlier will be the work involved but it will have to be done. Reading the Guide a newcomer could be forgiven for thinking that a new term "Mc/s" had been invented, replacing MHz! Even in the new material it has been persisted with. A note to explain why it occurs at all would not have been out of place on the first page.

There are many other inconsistencies which could be cleared up such as the use of K, ohms, m/ohms and KΩ for resistance instead of Ω, kΩ, MΩ, etc. "Condenser" instead of "capacitor" in places, reference to component suppliers no longer in business, use of metric and Imperial measurements on one diagram!

Chapter One (This is Amateur Radio) answers some of the simpler questions, "what types of licences are available in the UK?", "how much do they cost?", "are the exams difficult to pass?" and perhaps more pertinent "how much does an amateur station cost?". Chapter Two (Getting Started) looks at log-keeping, discusses the characteristics of the amateur bands from 1.8MHz to above 1215MHz, advises on the sending of reports, and reviews amateur equipment in a general way. Although the PA circuit in Fig. 17 is not intended to be a practical one, a blocking capacitor in the anode circuit would not have come amiss! Chapter Three (Communications Receivers) gets down to details on requirements, leading to practical designs for a high stability converter, a Q multiplier and the now famous RSGB Transistor Four simple superhet.

Chapter Four (Amateur Transmitters) discusses the usual types of oscillators found in amateur transmitting

equipment, leading on to power amplifier design and the problems of harmonics and parasitics, a much-beloved subject of the Radio Amateurs Examination! CW and telephony operation is followed by aërials, frequency measurement and the RSGB Noviset, a low power transmitter for telephony or CW on the 160/80m bands.

Chapter Five (The Licence Examinations) is perhaps the most important chapter in the Guide! Details of the RAE syllabus, which is very frightening and daunting to the prospective candidate but need not be, a typical exam paper, a summary of licence conditions and a table of frequencies available to the UK amateur. Finally, preparing and passing the RAE, some very useful advice indeed if only candidates would heed it!

Having got a ticket Chapter Six (Operating an Amateur Station) will assume a new significance with notes on the Morse code, RST code, International Q code and Amateur Abbreviations, and, very useful indeed, the list of callsign prefixes. Chapter Seven (Workshop Practice) should convince the newcomer that making one's own equipment is not so very difficult after all, and, very significantly, that it's very much cheaper and certainly much more satisfying. For some strange reason a 3.5MHz direct-conversion receiver design is included in this chapter.

Chapter Eight (Amateur Radio Equipment) is completely new in the Guide and quite invaluable to the would-be purchaser of any amateur gear. A review of receivers from the 30s to the present day runs on to transmitters and transceivers and is followed by an extremely useful listing of equipment, by make, with basic technical data. Finally, Chapter Nine (The RSGB and the Radio Amateur) outlines the work of the Society and the advantages of being a member.

Don't worry about my trivial criticisms! It's still a wonderful publication and worth every penny!

*Eric Dowdeswell G4AR*

**BINDERS FOR PW**

Keep your copies together  
Keep them clean  
with the  
PW Easi-Binder

*The Easi-Binder is attractively bound with the title blocked in gold on the spine with the current (or last) volume number and year. For any previous volume numbers please advise year and volume and a separate set of gold transfer figures will be supplied.*

**£1.90 inclusive of VAT, post and packing from:**  
Post Sales (Binders) IPC Magazines Ltd.,  
Carlton House, 68 Great Queen Street,  
London WC2

# BENTLEY ACOUSTIC CORPORATION LTD.

7a GLOUCESTER ROAD, LITTLEHAMPTON, SUSSEX  
All prices inclusive of V.A.T. at 25% Telephone 6743

|        |      |       |       |        |      |        |      |          |       |         |       |
|--------|------|-------|-------|--------|------|--------|------|----------|-------|---------|-------|
| OB2    | -47  | 6BA6  | -41   | 6L1    | 2-34 | 12J7GT | -70  | 35D5     | -88   | DK40    | -82   |
| OZ4    | -55  | 6BC8  | -70   | 6L6GC  | -88  | 12K5   | -117 | 35L6GT   | -88   | DK92    | -82   |
| 1A3    | -53  | 6BE6  | -41   | 6L7    | -59  | 12K7GT | -59  | 35W4     | -59   | DK96    | -70   |
| 1A5GT  | -59  | 6BH6  | -70   | 6L18   | -84  | 12Q7GT | -53  | 35Z3     | -88   | DL96    | -84   |
| 1A7GT  | -76  | 6BJ6  | -64   | 6L19   | 2-34 | 12SC7  | -59  | 35Z4GT   | -82   | DM70    | -70   |
| 1B3GT  | -59  | 6BK7A | -70   | 6LD20  | -88  | 12SG7  | -47  | 35Z5GT   | -88   | DM71    | -76   |
| 1B5GT  | -70  | 6BQ7A | -64   | 6N7GT  | -70  | 12SH7  | -41  | 42       | -59   | DY87/6  | -41   |
| 1L4    | -33  | 6BR7  | -117  | 6Q7G   | -59  | 12SJ7  | -52  | 43       | -117  | DY80Z   | -41   |
| 1N5GT  | -76  | 6BR8  | -117  | 6Q7GT  | -59  | 12SQ7  | -76  | 50B5     | -117  | E80C    | -2-57 |
| 1R5    | -53  | 6BS7  | -1-64 | 6R7(M) | -64  | 12SR7  | -88  | 50C5     | -70   | E80F    | -1-64 |
| 1B4    | -39  | 6BW6  | -94   | 6R7G   | -70  | 14H7   | -64  | 50CD6G   | -59   | E80G    | -88   |
| 1U4    | -70  | 6BW7  | -82   | 6R7(M) | -88  | 14S7   | -94  | -1-46    | -1-46 | E92C    | -70   |
| 1U5    | -88  | 6BZ6  | -57   | 6SA7   | -59  | 19A6   | -59  | 50EH5    | -76   | E180F   | -117  |
| 2D21   | -53  | 6C4   | -47   | 6SC7GT | -88  | 19G6   | 7-02 | 50L6GT   | -76   | E182CC  | 1-46  |
| 2GK5   | -64  | 6C5G  | -59   | 6SG7   | -52  | 20D1   | -70  | 85A2     | -70   | E1148   | -62   |
| 2X2    | -70  | 6C6   | -47   | 6SH7   | -52  | 20P2   | -88  | 85A3     | -70   | E1A50   | -62   |
| 3A4    | -59  | 6C9   | -117  | 6SJ7   | -94  | 20L1   | 1-29 | 90AG     | -2-93 | E1A76   | -117  |
| 3D6    | -47  | 6CD6G | -1-46 | 6SK7GT | -52  | 20P3   | -94  | 90C1     | -88   | E1ABC80 | -45   |
| 3Q4    | -70  | 6CG8A | -88   | 6SQ7GT | -53  | 20P4   | 1-17 | 90C2     | -88   | E1AC91  | -88   |
| 3Q5GT  | -64  | 6CL6  | -76   | 6V6G   | -59  | 20P5   | 1-52 | 150B2    | -88   | E1AF42  | -88   |
| 3S4    | -47  | 6CL8A | -94   | 6V6GT  | -53  | 25A6G  | -70  | 2158G    | -59   | E1AF301 | -88   |
| 3V4    | -82  | 6CM7  | -88   | 6X4    | -47  | 25L6G  | -70  | 807      | -117  | E1B34   | -2-9  |
| 4CB6   | -64  | 6C6U5 | -88   | 6X5GT  | -53  | 25Y6G  | -82  | 5702     | -117  | E1B91   | -88   |
| 5CC8   | -64  | 6CW4  | -117  | 7B6    | -88  | 25Z4G  | -47  | 5763     | -117  | E1BC41  | -88   |
| 5R4GY  | -94  | 6DE7  | -88   | 7B7    | -82  | 25Z6   | -94  | 6067     | -117  | E1BC81  | -41   |
| 5U4G   | -47  | 6DT6A | -88   | 7B7    | -88  | 25Z6G  | -82  | 6068     | -117  | E1BF80  | -46   |
| 5V4G   | -59  | 6EW6  | -88   | 7B7    | -94  | 28D7   | 1-17 | 6067     | -117  | E1BF89  | -59   |
| 5Y3GT  | -53  | 6E5   | -117  | 7Y4    | -88  | 30A5   | -76  | 7193     | -62   | E1BL21  | 2-34  |
| 5Z3    | -88  | 6E1   | -88   | 7Z4    | -94  | 30C15  | -82  | 9002     | -59   | E1C86   | -82   |
| 5Z4G   | -53  | 6F6G  | -59   | 9D7    | -76  | 30C17  | -94  | 9006     | -35   | E1C86   | -82   |
| 5Z4GT  | -53  | 6F13  | -82   | 10C2   | -76  | 30C18  | -82  | ACPEN    | -117  | E1C88   | -59   |
| 6/30L2 | -70  | 6F14  | -88   | 10DE7  | -88  | 30F5   | -88  | AC2/PEN/ | -117  | E1C92   | -59   |
| 6A8G   | 1-46 | 6F15  | -76   | 10F1   | -88  | 30FL1  | -78  | DD       | -117  | E1C93   | -117  |
| 6AC7   | -57  | 6F18  | -84   | 10F9   | -76  | 30FL2  | -78  | AC6PEN   | -70   | E1C98   | -111  |
| 6AG5   | -32  | 6F23  | -82   | 10F18  | -64  | 30FL12 | 1-05 | AC/TH1   | -117  | E1C99   | -117  |
| 6AH6   | -70  | 6F24  | -1-00 | 10LD11 | -82  | 30FL13 | -64  | AL60     | 1-17  | E1C98   | -117  |
| 6AJ5   | -78  | 6F25  | -117  | 10P13  | -88  | 30FL14 | -82  | ATP4     | -59   | E1C98   | -39   |
| 6AK5   | -47  | 6F28  | -78   | 10P14  | 2-34 | 30L15  | -82  | AZ1      | -29   | E1C84   | -41   |
| 6AK6   | -70  | 6F32  | -59   | 12A6   | -75  | 30L17  | -76  | AC       | -70   | E1C85   | -47   |
| 6AM8A  | -64  | 6G6G  | -59   | 12AC6  | -82  | 30P4MR | -76  | AZ31     | -70   | E1C85   | -41   |
| 6AN8   | -82  | 6G8A  | -88   | 12AD6  | -76  | AZ41   | -29  | E1C88    | -1-00 | E1C88   | -59   |
| 6AQ5   | -53  | 6GK5  | -76   | 12AE6  | -76  | 30P12  | -76  | BL63     | 2-34  | E1C88   | -59   |
| 6AR5   | -70  | 6G7   | -88   | 12AT6  | -67  | 30P19  | -76  | CL33     | -1-87 | E1C88   | -59   |
| 6AS7   | 1-17 | 6H6GT | -89   | 12AU6  | -53  | 30P4   | -88  | CY1C     | 1-17  | E1C87   | -1-41 |
| 6AT6   | -53  | 6J5GT | -53   | 12AV6  | -59  | 30PLL  | 1-00 | CY81     | -59   | E1C80   | -53   |
| 6AU6   | -35  | 6J6   | -85   | 12BA6  | -53  | 30PLL3 | 1-11 | DAF91    | -35   | E1C82   | -58   |
| 6AV6   | -53  | 6J7G  | -85   | 12BB6  | -59  | 30PLL4 | 1-29 | DAF96    | -59   | E1C86   | -88   |
| 6AW8A  | 1-11 | 6JU8A | -88   | 12BH7  | -59  | 30PLL5 | -94  | DC90     | -70   | E1C804  | 2-34  |
| 6AX4   | -88  | 6K7G  | -35   | 12BY7  | -88  | 35A3   | -76  | DF91     | -35   | E1C81   | 2-34  |
| 6B8G   | -85  | 6K8G  | -58   | 12E1   | 8-51 | 35C5   | -88  | DF96     | -59   | E1C85   | 1-46  |

|       |      |        |      |           |      |         |      |        |      |       |     |        |     |
|-------|------|--------|------|-----------|------|---------|------|--------|------|-------|-----|--------|-----|
| ECH49 | -82  | EY81   | -47  | PCF84     | -69  | QS95/10 |      | VP41   | -88  | AC177 | -36 | BF181  | -52 |
| ECH81 | -39  | EY83   | -63  | PCF86     | -56  | VR105   | -59  | VR105  | -59  | AC177 | -36 | BF185  | -52 |
| ECH83 | -52  | EY84   | -82  | PCF200    | 1-17 | VU111   | -94  | VU111  | -94  | ACV18 | -26 | BF194  | -20 |
| ECH84 | -52  | EY87/6 | -89  | PCF201    | 1-17 | VU120   | 1-17 | VU120  | 1-17 | ACV19 | -25 | BFY50  | -89 |
| ECL80 | -47  | EY88   | -47  | PCF501    | -59  | R19     | -70  | R19    | -70  | ACV20 | -23 | BFY51  | -85 |
| ECL82 | -40  | EY91   | -68  | PCF802    | -59  | TH233   | 1-17 | TH233  | 1-17 | ACV21 | -25 | BFY52  | -86 |
| ECL83 | -82  | EZ40   | -69  | PCF806    | -59  | TP2620  | 1-17 | TP2620 | 1-17 | ACV22 | -20 | BY100  | -33 |
| ECL84 | -70  | EZ41   | -84  | PCH200    |      | UABC80  | 4-7  | UABC80 | 4-7  | ACV28 | -30 | BY114  | -23 |
| ECL85 | -70  | EZ80   | -88  |           |      | UAF42   | -70  | UAF42  | -70  | AD140 | -47 | BY126  | -80 |
| ECL86 | -47  | EZ81   | -84  | PCL82     | -45  | UBC41   | -70  | UBC41  | -70  | AD149 | -64 | BY127  | -83 |
| E22   | -76  | GY501  | -82  | PCL83     | -53  | UBC81   | -63  | UBC81  | -63  | AD161 | -59 | BY210  | -33 |
| EP40  | -88  | GZ32   | -82  | PCL84     | -47  | UBF80   | -47  | UBF80  | -47  | AD162 | -59 | BY211  | -33 |
| EP41  | -82  | GZ33   | 1-46 | PCL86     | -55  | UBF89   | -47  | UBF89  | -47  | AF114 | -83 | BY212  | -33 |
| EP42  | -82  | GZ34   | -70  | PCL805    | -64  | UBL21   | 2-84 | UBL21  | 2-84 | AF115 | -80 | BY213  | -33 |
| EP73  | 1-76 | GZ37   | 1-17 | PEN45     | -94  | UC92    | -53  | UC92   | -53  | AF117 | -25 | F5Y11A | -29 |
| EP80  | -89  | HABC80 |      | PEN45DD   |      | UC94    | -88  | UC94   | -88  | AF121 | -39 | F5Y41A | -29 |
| EP83  | 1-17 | HL23DD | -70  | PRN46     | -59  | UCF80   | -53  | UCF80  | -53  | AF124 | -33 | OA9    | -16 |
| EP85  | -35  | HL41DD | -88  | PEN453DD  | 2-34 | UCH21   | 2-84 | UCH21  | 2-84 | AF125 | -22 | OA10   | -55 |
| EP86  | -53  | HL42DD | -88  | PENDD     |      | UCH81   | -47  | UCH81  | -47  | AF126 | -33 | OA47   | -18 |
| EP89  | -35  | HL42DD | -88  | 4020      | 2-34 | UCL42   | -65  | UCL42  | -65  | AF180 | -62 | OA70   | -20 |
| EP91  | -43  | HN309  | 1-76 | PFL200    | -82  | UCL83   | -64  | UCL83  | -64  | AF186 | -71 | OA73   | -20 |
| EP92  | -59  | HVR2   | 1-17 | PL33      | -59  | UF41    | -82  | UF41   | -82  | BA115 | -18 | OA79   | -13 |
| EP97  | -94  | HVR2A  | 1-17 | PL36      | -70  | UF42    | -88  | UF42   | -88  | BA116 | -23 | OA81   | -12 |
| EP98  | -94  | KTW61  | 1-76 | PL81      | -53  | UF80    | -41  | UF80   | -41  | BA129 | -16 | OA85   | -12 |
| EP98  | -94  | KTW62  | 1-76 | PL81A     | -53  | UF85    | -62  | UF85   | -62  | BA130 | -13 | OA90   | -16 |
| EP98  | -94  | KTW63  | 1-17 | PL81B     | -53  | UF89    | -47  | UF89   | -47  | BA153 | -20 | OA91   | -12 |
| EL30  | -59  | KTW63  | 1-17 | PL82      | -47  | UL41    | -70  | UL41   | -70  | BC107 | -16 | OA95   | -13 |
| EL32  | -59  | KTW63  | 1-17 | PL83      | -47  | UL42    | -49  | UL42   | -49  | BC108 | -16 | OA200  | -13 |
| EL34  | 1-17 | KT81   | 2-84 | PL84      | -47  | UL84    | -49  | UL84   | -49  | BC109 | -16 | OA202  | -13 |
| EL35  | 2-93 | KTW61  | 1-76 | PL504/500 |      | UM80    | -59  | UM80   | -59  | BC115 | -20 | OC45   | -14 |
| EL37  | 2-93 | KTW62  | 1-76 | UY41      | -82  | UY41    | -82  | UY41   | -82  | BC116 | -32 | OC46   | -90 |
| EL41  | -59  | KTW63  | 1-17 | UY85      | -41  | UY85    | -41  | UY85   | -41  | BC118 | -29 | OC70   | -16 |
| EL81  | -70  | MHLD6  | 1-17 | PL508     | 1-05 | U10     | -117 | U10    | -117 | BCY10 | -59 | OC71   | -14 |
| EL83  | -64  | P61    | -59  | PL509     | 1-70 | U12/12  | 1-17 | U12/12 | 1-17 | BCY12 | -64 | OC72   | -14 |
| EL84  | -36  | P61    | -59  | PY33/2    | -53  | U19     | 2-93 | U19    | 2-93 | AC128 | -26 | OC74   | -29 |
| EL85  | -52  | PABC80 | -45  | PY81      | -41  | U25     | -70  | U25    | -70  | AC132 | -26 | OC75   | -14 |
| EL86  | -45  | PC86   | -70  | PY82      | -35  | U26     | -77  | U26    | -77  | AC134 | -33 | OC76   | -20 |
| EL86  | -45  | PC86   | -70  | PY83      | -45  | U33     | 1-76 | U33    | 1-76 | AC156 | -26 | OC77   | -35 |
| EL86  | -45  | PC86   | -70  | PY84      | -35  | U36     | -77  | U36    | -77  | AC157 | -33 | OC78   | -20 |
| EL86  | -45  | PC86   | -70  | PY85      | -45  | U37     | 1-76 | U37    | 1-76 | AC158 | -33 | OC78D  | -20 |
| EL86  | -45  | PC86   | -70  | PY86      | -47  | U38     | -77  | U38    | -77  | AC166 | -33 | OC81   | -14 |
| EL86  | -45  | PC86   | -70  | PY87      | -47  | U39     | -77  | U39    | -77  | AC168 | -49 | OC81D  | -14 |
| EL86  | -45  | PC86   | -70  | PY88      | -47  | U40     | -88  | U40    | -88  | AC176 | -71 | OC82   | -14 |
| EL86  | -45  | PC86   | -70  | PY89      | -47  | U41     | -89  | U41    | -89  |       |     |        |     |
| EL86  | -45  | PC86   | -70  | PY90      | -47  | U42     | -89  | U42    | -89  |       |     |        |     |
| EL86  | -45  | PC86   | -70  | PY91      | -47  | U43     | -89  | U43    | -89  |       |     |        |     |
| EL86  | -45  | PC86   | -70  | PY92      | -47  | U44     | -89  | U44    | -89  |       |     |        |     |
| EL86  | -45  | PC86   | -70  | PY93      | -47  | U45     | -89  | U45    | -89  |       |     |        |     |
| EL86  | -45  | PC86   | -70  | PY94      | -47  | U46     | -89  | U46    | -89  |       |     |        |     |
| EL86  | -45  | PC86   | -70  | PY95      | -47  | U47     | -89  | U47    | -89  |       |     |        |     |
| EL86  | -45  | PC86   | -70  | PY96      | -47  | U48     | -89  | U48    | -89  |       |     |        |     |
| EL86  | -45  | PC86   | -70  | PY97      | -47  | U49     | -89  | U49    | -89  |       |     |        |     |
| EL86  | -45  | PC86   | -70  | PY98      | -47  | U50     | -89  | U50    | -89  |       |     |        |     |
| EL86  | -45  | PC86   | -70  | PY99      | -47  | U51     | -89  | U51    | -89  |       |     |        |     |
| EL86  | -45  | PC86   | -70  | PY100     | -47  | U52     | -89  | U52    | -89  |       |     |        |     |
| EL86  | -45  | PC86   | -70  | PY101     | -47  | U53     | -89  | U53    | -89  |       |     |        |     |
| EL86  | -45  | PC86   | -70  | PY102     | -47  | U54     | -89  | U54    | -89  |       |     |        |     |
| EL86  | -45  | PC86   | -70  | PY103     | -47  | U55     | -89  | U55    | -89  |       |     |        |     |
| EL86  | -45  | PC86   | -70  | PY104     | -47  | U56     | -89  | U56    | -89  |       |     |        |     |
| EL86  | -45  | PC86   | -70  | PY105     | -47  | U57     | -89  | U57    | -89  |       |     |        |     |
| EL86  | -45  | PC86   | -70  | PY106     | -47  | U58     | -89  | U58    | -89  |       |     |        |     |
| EL86  | -45  | PC86   | -70  | PY107     | -47  | U59     | -89  | U59    | -89  |       |     |        |     |
| EL86  | -45  | PC86   | -70  | PY108     | -47  | U60     | -89  | U60    | -89  |       |     |        |     |
| EL86  | -45  | PC86   | -70  | PY109     | -47  | U61     | -89  | U61    | -89  |       |     |        |     |
| EL86  | -45  | PC86   | -70  | PY110     | -47  | U62     | -89  | U62    | -89  |       |     |        |     |
| EL86  | -45  | PC86   | -70  | PY111     | -47  | U       |      |        |      |       |     |        |     |



## AMATEUR BANDS

by Eric Dowdeswell G4AR

**R**EPORTS from readers continue to arrive in spite of the competition from many other summer activities. Perhaps I ought to put summer in quotes as snow falls to a depth of several inches in the North! That'll keep the lads glued to their sets! Incidentally, because of changes to our printing schedules you can now hold your reports to me until the end of the month. This ought to get your reports into print a bit sooner after you part with them and generally make the news a bit more up-to-date.

Among the regular publications that come my way is *TARS TALK*, journal of the Torbay Amateur Radio Society, and one that I enjoy reading very much. The Society obviously has a solid core of hard-working members resulting in a healthy membership. Apart from regular meetings the Society organises coach trips from time to time in which wives, girl-friends and children take part, thus showing that radio amateurs do have a human facet, for a short time, anyway! Those interested and lucky enough to live in the Torbay area should contact M. Yates, G3UIQ, 23 Waverley Road, Newton Abbot, Devon, secretary of TARS.

There are dozens of similar societies up and down the country so if you are unattached radio-society-wise (ugh!) why not ask the Radio Society of Great Britain at 35 Doughty Street, London WC1, for the address of your local society? In the larger towns there may well be two or three from which you can choose. While you are at it, why not consider getting a copy of the Society's *Guide to Amateur Radio* (16th Edition) which is a give-away at £1.10 p/p. Hopefully, my review of the Guide should appear elsewhere in this issue.

**Tim Charles** (Colchester) grabbed the far end of his 132ft aerial wire and pulled it round to form a half wave loop on 80m, and, parallel tuned with 500pF, was delighted to find it tuned to all the HF bands. I feel it must have been mis-matched at times but full marks Tim for experimenting! On 2m Tim now has a Microwave Module converter feeding his CR70A on 2 to 4MHz. He mentions some very low power work by G8EWC on 2m, heard by Tim when the power was just 10mW, that's milliwatts not megawatts! Distance was only one and a half miles but the 8-element Yagi at EWC must have helped.

**Paul Barker** (Sunderland) doesn't intend to wear out his bandswitch! He stuck to 20m SSB and SSTV and found CN8HD on the latter mode. Paul praises the conditions into the Middle East and Africa of late on 20m, no doubt due to the change towards summer propagation paths. **Stephen Budd** A8713 (Worthing) also preferred 20m where he found KG6, KS6 and 9N1 for comparatively rare ones. I must say it is nice to see some people getting away from the bedlam on 80m for the relative quiet of 20m! It was always my favourite band and could usually be relied upon to produce something new from time to time.

**Colin Fawcett** (Oldham) reports back on to the bands after a three-year lapse, starting off again with an Eddystone 840 to which he hopes to add an SSTV monitor before long. We look forward to your reports in this field OM. In spite of several logs from **M. C. P. Bennett** (Slough) I still don't know his first name! Come along OM and reveal all to us! He's now got a Trio JR310 and keeps his CR70A for 160m only. Just to prove he doesn't sleep he reports ZL's on 40m at 0200, VK's on 20m at 0600 but 15m not waking up until around 1400GMT, M.C.P. mentions the activities of one or two DXpeditions but I'm afraid they will have been and gone by the time you read this in print. Finally, he reckons that KC4AF, HS5ABD and ZA3PC are the work of a single phoney operator.

**Peter Walton** A9002 (Llanfair PG, Gwynedd) has an Eddystone 358X and 87ft of wire plus a 15ft vertical, with an ATU in between and he concentrated on 20m mainly. I often get requests for data on ATU's and as I still have a few copies of the *PW Aerial Data Chart* stashed away anyone interested can send me a SAE, not less than 8 x 6in.

An appeal from **Mark Hill** A9008 (114 Green Lane, Castle Bromwich, Birmingham) to others of similar age group to correspond with him. He has an RA-1 receiver fed from a Microwave Modules converter at 28/30MHz for 2m work, the aerial being the halo type. Other gear includes a Collins TCS8 and Codar T28 together with a G5RV aerial plus a 20m dipole and a base-loaded whip. All that's missing are some of my log sheets and those are already in the post! Welcome to the column, Mark. **Stephen Terry** (Banbury) BRS35669 produced a useful list of things heard but complained of QRM caused by moving his QTH. For the time being he is using 100ft of wire and hopes to get back into the groove very soon. Another enthusiast intent on getting the best aerials he can is **Andrew Swiffin** (Cheadle) who is in the process of erecting dipoles for 10 to 80m. One aim is to get them as far away as possible from his neighbour's colour TV installation and the line time base QRM he is suffering at the moment.

no extras

FREE delivery



ALL ITEMS SUBJECT TO MANUFACTURERS INCREASE AND AVAILABILITY  
Personal Callers are Welcome!



High Quality Construction Kits, stocked at all branches. Send for catalogue!

PLEASE ADD VAT AT CURRENT RATE

AMPLIFIERS

|               |        |
|---------------|--------|
| Rotel RA211   | £43.95 |
| RA311         | £54.95 |
| Sansui AU2200 | £49.00 |
| AU4400        | £75.00 |
| Sinclair 4000 | £50.00 |

TUNERS & RECEIVERS

|                      |        |
|----------------------|--------|
| Sinclair 4000 Tuner  | £43.95 |
| Rotel RT222          | £45.30 |
| Pioneer SX434        | £97.80 |
| SX300                | £75.15 |
| Rotel 152            | £71.45 |
| Sansui 441 AM/FM/MPX | £79.95 |

RECORD DECKS (Ins. 50p)

|                                 |        |
|---------------------------------|--------|
| Garrard SP25 MkIV               | £14.75 |
| BSR MP60                        | £12.75 |
| Garrard SP25 MkIV P & C         | £25.45 |
| Goldring GL78 P & C/Connoisseur | £56.00 |
| BDI Kit                         | £13.25 |
| BD2 Chassis/SAU2                | £34.15 |
| SAU Arm                         | £14.25 |
| SCUI Cartridge                  | £5.95  |
| Pioneer PL12D                   | £46.59 |

TAPE DECKS (Insurance 2.00)

|                                |         |
|--------------------------------|---------|
| Akai GXC36D                    | £85.00  |
| GXC38D                         | £107.95 |
| Akai CR81D 8-track Rec. player | £85.95  |
| GXC82D                         | £95.95  |

SPEAKERS

|  |           |
|--|-----------|
| Chassis Speakers                                   |           |
| EMI (Plain) 13in x 8in, Bass unit                  | £2.50     |
| with Single Tweeter (only 8 ohm)                   | £2.75     |
| with Tweeter and Cross-over 3, 8 or 15 ohm         | £4.25     |
| Type 350 Kit 15 watt 8 ohm                         | £8.25     |
| 13in x 8in Bass unit 15 watt 8 ohm or 15 ohm       | £5.45     |
| 8in x 5in 5 watt 3, 8 or 15 ohm                    | £1.70     |
| 8in x 5in 10 watt Dualcone 8 ohm                   | £2.95     |
| 6 1/2" 10 watt 8 ohm                               | £2.65     |
| 8in 10 watt 8 ohm                                  | £4.50     |
| 8in 4 or 15 ohm                                    | £2.25     |
| 7in x 4in 3 or 8 ohm                               | £1.30     |
| Elac 6 1/2" 8 ohm Dualcone                         | £2.65     |
| Elac 8in 8 ohm Dualcone                            | £2.70     |
| Elac 10in 8 ohm Dualcone                           | £3.75     |
| Baker Group 25 12in 8 or 15 ohm                    | £12.00    |
| Adastra 'Top 20' 12in 25 watt 8 or 15 ohm          | £8.25     |
| Adastra 'Hi-Ten' 10in 10 watt 8 or 15 ohm          | £3.75     |
| Also 5in 8 ohm speaker 2 1/2in 8 or 64 ohm speaker | £0.95 60p |

WHARFEDALE SPEAKER BARGAINS

|                |        |
|----------------|--------|
| Denton 1 pr.   | £25.35 |
| Denton 2 pr.   | £32.00 |
| Denton 3 pr.   | £34.20 |
| Linton 3 pr.   | £47.60 |
| Glendale 3 pr. | £63.88 |
| Dovedale 3 ea. | £44.25 |

KITS

|                |        |
|----------------|--------|
| Linton 2 pr.   | £20.95 |
| Glendale 3 pr. | £35.95 |
| Dovedale 3     | £58.50 |

SPEAKER CABINETS IN KIT FORM (Teak Veneer)

|   |       |
|---|-------|
| (Ins. 50p. per pair)                                    |       |
| 12in x 8in x 4 1/2in (8 x 5 or 7 x 4 cutout)            | £3.75 |
| 12in x 12in x 7 1/2in (10", 8 x 5, 8", 6 1/2" & 3 1/4") | £5.25 |
| 18in x 11in x 7 1/2in (8" x 4" or 13 x 8)               | £6.56 |
| 22in x 14in x 7 1/2in (12" & 3" or 13 x 8)              | £7.96 |

TWEETERS & CROSSOVERS

|  |       |
|--|-------|
| Cone Tweeter 10 watt 8 or 15 ohm (K2006) | £2.95 |
| Cone Tweeter 3 watt 8 ohm (K2003)        | £1.55 |
| Horn Tweeter 8 ohm (K2007)               | £6.50 |
| Dome Tweeter 8 ohm (K2011)               | £5.75 |
| 2-way Crossovers (CN23, CN28, CN216)     | £1.40 |
| 3-way Crossover (CN38)                   | £2.85 |

CARTRIDGES & STYLII

|                                   | Cart. £ | D/D Styli £ |
|-----------------------------------|---------|-------------|
| ACOS GP91/25C or 3CS (ster. comp) | 1.10    | 1.25        |
| GP93/1 or 95/1 ster. cryst.       | 1.35    | 1.25        |
| GP94/1 or 96/1 ster. ceram.       | 1.75    | 1.25        |
| GP101 cryst. comp.                | 90      | —           |
| GP104 ster. ceram.                | 1.95    | 1.25        |
| BSR X5M or X5H cryst. comp.       | 1.95    | 1.25        |
| SX6M or SX6H cryst. ster.         | 2.10    | 1.25        |
| SC5M ster. ceram.                 | 2.85    | 1.25        |
| SONOTONE 9TAHC or 9TAHC/G (Diam.) | 1.95    | 1.25        |
| 3509 Magnetic                     | 1.95    | 1.25        |
| AUDIO TECNICA AT55                | 1.95    | —           |
| EMPIRE 999 REX                    | 3.95    | —           |
| GOLDRING G850                     | 3.10    | 1.95        |
| G800                              | 4.25    | 1.95        |
| G800H                             | 4.25    | 1.95        |
| G800E                             | 7.25    | 3.95        |

SHURE CARTRIDGES & STYLII

|              |       |      |
|--------------|-------|------|
| M44G         | 4.95  | 3.95 |
| M55E         | 6.25  | 4.95 |
| M75ED Type 2 | 11.75 | 8.25 |
| MJ5EJ Type 2 | 9.75  | 6.25 |
| V15 Type 3   | 32.25 | —    |

MICROPHONES

|   |       |
|---|-------|
| UD130 50K/600 ohm uni-dir. ball metal           | £6.75 |
| UD147   | £9.25 |
| Condenser Mic. 600 ohm uni-dir                  | £9.50 |
| Cassette Stick Mic. with R/Control              | £1.65 |
| Cass. Stick Mic. with R. control (Philips type) | £2.00 |
| TW209   | £5.90 |

HEADPHONES

|  |             |
|--|-------------|
| Rotel RH430  | £4.75       |
| RH 630   | £7.75       |
| RH 700   | £11.50      |
| Koss K711  | £11.65      |
| KRD711   | £11.65      |
| K6   | £13.00      |
| K6LC   | £14.88      |
| KO727B   | £15.95      |
| KO747  | £21.95      |
| HVI  | £24.75      |
| PRO4AA   | £29.40      |
| PRO5LC   | £32.20      |
| K6LCCQ   | £27.06      |
| Sansui SS10  | £16.75      |
| *Headphone adaptor (junction box) extension lead 2ft curly | £2.75 £1.50 |

CLOCK RADIOS

|                         |        |
|-------------------------|--------|
| Bush CR128 LW/MW        | £15.50 |
| Bush CR232 MW/VHF       | £24.95 |
| Murphy MV5600 MW/VHF    | £22.95 |
| Vega Signal 2 wave band | £9.95  |

CASSETTE RECORDERS

|                         |        |
|-------------------------|--------|
| Bush TP66 M/Batt        | £25.75 |
| Murphy BA200 M/Batt     | £22.75 |
| Bush BT8504 (miniature) | £25.50 |
| Mains Battery Cass.     | £15.50 |

RADIO CASSETTES

|                     |        |
|---------------------|--------|
| (Mains/Batt.)       |        |
| Murphy BA209 MW/VHF | £33.50 |

STEREO RECORD PLAYER & SYSTEM

|   |         |
|---|---------|
| Hanimex HRC5060 8-track AM/FM/MPX+Speaker | £116.95 |
|---|---------|

CAR AUDIO

|  |        |
|--|--------|
| Hitachi Car Radio WM702R LW/MW                     | £16.50 |
| KM1510 LW/MW/VHF                                   | £32.50 |
| Battery Eliminators 240 in 6, 7.5 or 9 volt output | £3.10  |

SINCLAIR PROJECT 80

|                          |        |
|--------------------------|--------|
| Stereo Pre-amp.          | £12.95 |
| Active Filter Unit       | £7.25  |
| Z40 15 watt Amp          | £5.75  |
| Z60 25 watt Amp          | £7.25  |
| P25 Power Supply for 240 | £5.45  |
| P26 Power Supply for 240 | £8.45  |
| P28 Power Supply for 260 | £8.25  |
| FM Tuner                 | £12.95 |
| Stereo Decoder           | £8.45  |
| Q16 Speaker              | £7.75  |
| IC20 Stereo Amp. Kit     | £7.45  |
| PZ20 Power Kit           | £5.25  |

PORTABLE RADIOS

|                                     |        |
|-------------------------------------|--------|
| Meridian Mk. II                     | £12.25 |
| Vega Sapphire                       | £8.75  |
| Vega VEF206                         | £15.50 |
| Selena LM/MW/FM/55W                 | £22.50 |
| Murphy B833 MW/VHF                  | £9.95  |
| BA838 LW/MW/VHF M/Batt              | £18.50 |
| MA5003 Head Set Radio LW            | £7.95  |
| Bush VTR165 LW/MW/VHF               | £22.00 |
| VTR127 LW/MW/VHF                    | £15.50 |
| VTR 175 LW/MW/VHF                   | £13.95 |
| VTR188 LW/MW/VHF/2SW M/Batt         | £31.95 |
| BY5661 LW/MW/VHF                    | £14.95 |
| Selga 2 wave band with leather case | £5.50  |

CASSETTES

|                                      |                   |
|--------------------------------------|-------------------|
| C40 C60 C90 C120                     |                   |
| BASF Super SM                        | — 95p 122p 170p   |
| Low Noise                            | — 35p 45p 55p     |
| Philips                              | — 55p 75p 110p    |
| Memorex                              | 65p 79p 110p 155p |
| Ampex (360)                          | 45p 55p 75p 99p   |
| Ampex (20-20+)                       | 59p 65p 99p 135p  |
| Chromium Dioxide                     | — 99p 140p —      |
| Cassette Head Cleaner                | 45p               |
| Ampex Head Cleaner                   | Damage £1.65      |
| BIB Stereo Test Cassette             | £2.15             |
| Cassette Racks (hold 6)              | £0.45             |
| Cassette Rotating Racks (hold 20)    | £3.50             |
| Cassette Carrying Case (hold 18)     | £1.95             |
| 8-Track Cartridge Blanks C40 C64 C80 | 80p 95p £1.10     |
| Ampex 8-track H/Cleaner              | £1.90             |
| Demagnetiser                         | £1.90             |
| 8-track Carrying Cases (BIB)         | £1.65             |

TAPES

|                      |          |        |         |           |
|----------------------|----------|--------|---------|-----------|
| 5"                   | Stnd 55p | LP 65p | DP 1.00 | Cases 20p |
| 5 1/2"               | 65p      | 86p    | 1.35    | 25p       |
| 7"                   | 80p      | 110p   | 1.85    | 30p       |
| High frequency Ampex |          |        |         |           |
| 5"                   | —        | 1.40p  | 1.55p   |           |
| 7"                   | —        | 1.90p  | 2.95p   |           |
| AKAI Metal Reel 7"   |          |        |         | £2.10     |

CALCULATORS

|                                |        |
|--------------------------------|--------|
| Sinclair Cambridge Build       | £12.95 |
| Sinclair Cambridge with memory | £17.95 |
| Scientific                     | £19.95 |

ALL MERCHANDISE FULLY GUARANTEED

NEWMART ELECTRONICS

Mail Order Dept PWJ/8  
Belmont St, Monton,  
Eccles, Manchester.  
Tel: 061-789 5268

Manchester  
30-32 Shudehill. tel 061-832 7710  
Leeds  
4 New Market St tel 0532 42708  
Liverpool  
15 Whitechapel tel 051-236 0738

Please bring this advertisement to obtain the benefit of these special prices



## "I MADE IT MYSELF"

Imagine the thrill you'll feel! Imagine how impressed people will be when they're hearing a programme on a modern radio you made yourself.

# Now! Learn the secrets of radio and electronics by building your own modern transistor radio!

Practical lessons teach you sooner than you would dream possible.

What a wonderful way to learn—and pave the way to a new, better-paid career! No dreary ploughing through page after page of dull facts and figures. With this fascinating Technatron Course, you learn by building!

You build a modern Transistor Radio . . . a Burglar Alarm. You learn Radio and Electronics by doing actual projects you enjoy—making things with your own hands that you'll be proud to own! No wonder it's so fast and easy to learn this way. Because learning becomes a hobby! And what a profitable hobby. Because opportunities in the field of Radio and Electronics are growing faster than they can find people to fill the jobs!

### No soldering—yet you learn faster than you ever dreamed possible.

Yes! Faster than you can imagine, you pick up the technical know how you need. Specially prepared step-by-step lessons show you how to: read circuits—assemble components—build things—experiment. You enjoy every minute of it!

You get everything you need. Tools. Components. Even a versatile Multimeter that we teach you how to use. All included in the course. **AT NO EXTRA CHARGE!** And this is a course anyone can afford. (You can even pay for it by easy instalments).

### So fast, so easy, this personalised course will teach you even if you don't know a thing today!

No matter how little you know now, no matter what your background or education, we'll teach you. Step by step, in simple easy-to-understand language, you pick up the secrets of radio and electronics.

You become a man who makes things, not just another of the millions, who don't understand. And you could pave the way to a great new career, to add to the thrill and pride you receive when you look at what you have achieved. Within weeks you could hold in your hand your own transistor radio. And after the course you can go on to acquire highpowered technical qualifications, because our famous courses go right up to City & Guilds levels.

### Send now for FREE 76 page book—see how easy it is—read what others say!

Find out more now! This is the gateway to a thrilling new career, or a wonderful hobby you'll enjoy for years. Send the coupon now. There's no obligation.

**POST TODAY FOR FREE BOOK**

To: ALDERMASTON COLLEGE  
DEPT. CPW 08, READING RG7 4PF CPW08

Also at our London Advisory Office, 4 Fore Street Avenue, Moorgate, London, EC2Y 5EJ Tel: 01-628 2721  
Yes, I'd like to know more about your course. Please send me free details—plus your big, 76-page book that tells about all your courses.

Name .....

Address .....

POST CODE.....



HOMI OF BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY

## ★ ELECTRONIC PIANO KIT ★ SYNTHESISER KIT ★ ELECTRONIC ORGAN KITS



There are five superb Electronic Organ kits specially designed for the D-I-Y enthusiast. With the extreme flexibility allowed in design, you can build an organ to your requirements, which will compare with an organ commercially built costing double the price.

★ Portable organ with 4 octave keyboard, £145-29. ★ Console organ with 5 octave keyboard, £250-93. ★ Console organ with 2 x 4 octave keyboards and 13 note pedal board, £470-65. ★ Console organ with 2 x 5 octave keyboards and 32 note pedal board, £680. ★ Console organ with 3 x 5 octave keyboards and 32 note pedal board, £960. ★ W/W Sound Synthesiser Kit, £149. ★ W/W Touch Sensitive Electronic Piano, £110.


All components can be purchased separately, i.e., semiconductor devices, M.O.S. master oscillators, coils, keyboards, pedal boards, stop tabs, draw bars, key-contacts, etc. Lesley type speaker units from £50. Send 50p for catalogue which includes 5 x 10p vouchers or send your own parts list, enclosing S.A.E. for quotation.

## Elvins Electronic Musical Instruments

12 Brett Road, Hackney, London E8 1JP (Tel. 01-986 8455);  
8 Putney Bridge Road, London SW18 1HU (Tel. 01-870 4949);  
40a/42a Dalston Lane, Dalston Junction, London E8 (Tel 01-249 5624).

Business hours: Open 10 a.m. to 7 p.m. Monday to Saturday. Closed all day Thursday. Open 10 a.m. to 1 p.m. Sunday.

## CARBON SLIDE POTENTIOMETERS

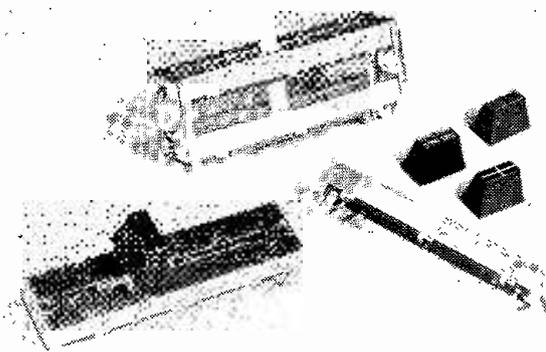

60mm Single Track including Black Knob 50p (inc. V.A.T.), 60mm Twin Track including Black Knob 60p (inc. V.A.T.), 60mm Quad Slide Potentiometers—Prices upon application. 1K, 5K, 10K, 25K, 50K, 100K, 500K ohms Log, Lin, Antilog. Metal Case. 3-2db Matched Track. 15mV Nominal Noise (B.S. 2122). Life Exceeds 20,000 cycles. Fixing Holes 2 x M3 on 80mm Centres.

Designed, Manufactured and Supplied by:—

## RIVLIN INSTRUMENTS LTD

DOMAN ROAD, CAMBERLEY, SURREY GU15 3DJ

Send cash with order to above address. Postage and packing 15p per order. Trade enquiries invited.



### Log extracts

**T. Charles:**— 80m PJ9EE TI9DX TR8DG VP2DM 40m EA9FD HI8FGP HK4DEG OA4AHV ZL1AUA ZL2FM 20m FG7AE JR6QZD (Ryukyu Is. Box 377 Tokyo) 8R1AK 2m I5ARS OE4MFA SMOERR SP9EGM 2m via Oscar VII W2LV W3OMU W4FJ

**P. Barker:**— 20m A6XR (G4CHP) C5AR (G3LQP) OE5CA/YK 5L2DT 8SK2AT (Sweden) 20m SSTV CN8HD DL3PN HA5KFU


**S. Budd:**— 20m A4XVF KG6JAR KS6SFA 9N1MM 9X5PT 15m VS9MB 9M2CJ

**M. Bennett:**— 80m KP4AN PY3CIQ 40m ZL4KF 20m DU7DP KL7USA ST2AY 5U7AB 7X5AB 15m CX5BK VQ9SS/C (Diego Garcia) ZP5DE 6W8DY

**P. Walton:**— 80m 4Z4KB 20m VQ9P VS9MAS

**S. Terry:**— 20m KH6GDR KL7IEU VP2LBR VQ9P (Mahe Is.) ZD7SD 9M8VLC

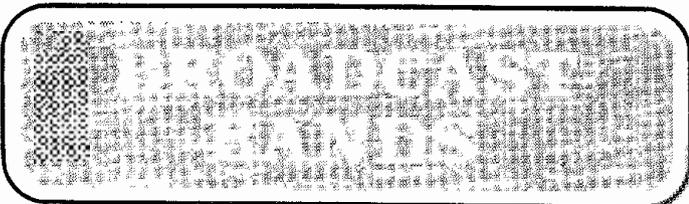**A. Swiffin:**— 80m 9M2FX 20m AC3PT FR7ZW VP2LBR VS5MC VU7GV (Andaman Is.) 4W1ED 9M1MM



### SHORT WAVE BROADCASTS

by *Derek Bell*

FROM somewhere in Ireland Cpl. D. Hardman writes to this column requesting the times and freqs. of the Singapore radio stations. These are as follows: 5010, 5052, 6000, 6155, 7170, 7250, 9653, 11940kHz. The service runs 24 hours a day and includes a VHF system. It is, however, very seasonal here in Europe, depending on the darkness path. To while away the hours Cpl. Hardman has an HAC one-valver. To show what can be done with this set, Christopher Midgley of Cleckheaton has logged:—

Radio Jordan at 1700 on 9560  
Radio Baghdad at 1930 on 9745  
NHK Tokyo at 0800 on 17855

Christopher had added 90 feet of aerial wire and an ATU to the basic set and says the QSL cards are rolling in thick and fast, numbering 52 at the time of writing.

Moving over the Irish border to Drogheda, Tomas O'Donoghille writes for information on his Koyo KTR. Tomas says that when tuning up and down the bands the set "oscillates". My first thought is that these are heterodynes caused by signals on adjacent stations interfering with each other. This type of interference is sometimes called "adjacent channel" interference and the clue to it is that when the tuning is moved from side to side the pitch of the interference changes. The only way out is to have the set checked by an expert. If it is the same on all signals then the IF stages could be unstable.

Two readers write asking for more details of the abbreviations used in our radio hobby so I will deal with them separately if I may. Martin Chapple of

Leamington Spa asks for some frequencies:—

Adventist World Radio is 9670

Radio Berlin International is 7260 and 1151

These, of course, are in English and both have many other slots for transmissions in other tongues.

B. W. Cowie of Telford is the other letter writer and for both a short list is offered:—see box

Barry Clayton from Bristol writes a welcome letter to tell us of a competition being run by Radio RSA in which the listener has to log and report on RSA transmissions on all the freqs. they use up to Nov.1st 1975. These are:— 3995, 5980, 7270, 9525, 9695, 11900, 11970, 15155, 15220, 15175, 17780 and 21535kHz. A formidable task you will agree but if you do manage it send the results to: Contest 75, Radio RSA, Box 4559, Johannesburg, South Africa.

Barry also takes this column to task regarding the amount of attention given to newcomers to the hobby. I can only say that a large percentage of letters come from newcomers and they do deserve help since they are the ones that ensure that the hobby flourishes.

David Lovatt from Stoke-on-Trent is awarded this column's 'Honorary gold tuning knob'! This thirteen-year-old won first prize in Radio Sofia's recent New Year competition, and deserves our congratulations. David writes appealing to us to "save the English transmission of Radio Finland". This is in danger of being dropped in favour of a German language broadcast. If readers care to write to Radio Finland by all means do so but, whether German or English, Radio Finland will still be there to be heard!

Now that the summer schedules frequency changes have taken place and things have settled down we can have an update on the week's DX 'Show list' recently featured in this column. These are provided by Gary Stevens from London and the changes to shows noted in the previous item are as follows:—

Tues. Hungary now 2130 on 6025 and 7175  
Thurs. Holland now 1830 on 6045  
Sats. Israel now 2000 on 12025 and 9009  
Canada now 2102 on 15325 and 11855

Continuing "across the pond" the summer schedules from Radio Canada have been received by this column and they show a coverage from 0600 to 0800 and from 1715 to 1900 then from 2005 to 2159 on the frequencies 5995, 6100, 7235, 7290, 9685, 11855, 15325 and 17820kHz. It is interesting to hear

|     |                        |     |              |
|-----|------------------------|-----|--------------|
| BC  | broadcast              | kW  | kilowatt     |
| DX  | long distance          | MHz | megahertz    |
| GMT | Greenwich Mean Time    | Net | network      |
| ID  | station identification | m.  | metre (band) |
| kHz | kilohertz (frequency)  | Tx  | transmitter  |

Some groups of the International Q Code have been taken over by short wave listeners and amateurs and their meanings adapted:—

|     |                                     |     |                     |
|-----|-------------------------------------|-----|---------------------|
| QRG | Frequency                           | QRV | Ready               |
| QRK | Signal strength                     | QRX | Stand by            |
| QRM | Interference (by other stations)    | QSB | Fading              |
| QRN | Interference (atmospheric/electr'l) | QSL | Verification card   |
| QRT | Shut down                           | QSO | Radio contact       |
|     |                                     | QSY | Frequency change    |
|     |                                     | QTH | Location or address |

A good source of information for both SWLs and listeners to the amateur bands is *A Guide to Amateur Radio* by Pat Hawker G3VA from the RSGB at £1.10 inc.



from overseas since it shows just how far your column voyages and how this hobby of ours is truly international.

Time to wrap up now I am afraid. The post this month was exceptionally heavy so apologies to all who were left out and best wishes to you and yours.

## MEDIUM WAVE DX

by **CHARLES MOLLOY**

**R**ADIO South Africa is back on the medium waves following a public protest at the suspension of broadcasting on this band last year. Programmes in Afrikaans/English are transmitted from Johannesburg on 575kHz/638kHz, from Port Elizabeth on 1043kHz/1178kHz, and from Cape Town on 557kHz/656kHz. Listen between midnight and sunrise for the All-Night Service which is broadcast on all frequencies.

A number of West African broadcasters are audible in the UK after dark at this time of year. Enugu in Nigeria can be found on 1320kHz with a programme in English at 2300 while Conakry in the Republic of Guinea is a regular on 1403kHz after the French stations on this frequency sign-off at 2300. Radio Senegal in Dakar shares 764kHz with Sotton in Switzerland but the two are easily separated with a medium wave loop aerial. The RNE outlet at Tenerife in the Canary Islands can be heard with Spanish programming after Belgium clears the frequency. Radio Kinshasa, Zaire is on 692kHz all night and is sometimes found clear of the East German station on that channel.

Glyn Morgan (Tredegar) returns to the medium waves after a long absence due to illness. He is using a Lafayette HA230 connected to a 12ft down lead from an attic TV aerial. His first late night session brought an unidentified Russian on 1070kHz (Ust Kamenogorsk in Kazakhstan signs-on at 0000). A MW loop is now under construction. Welcome back to the band Glyn, hope to hear from you again before long. Fourteen year old Peter Bouger (Kettering) uses a very old Bush radio with an aerial tuning unit and a 150ft long outdoor aerial 25ft above ground level. He reports hearing the AFN low power outlet at Heidelberg on 1304kHz and a programme in English from Sweden on 1178kHz at 2250. Radio Sweden carries "Sweden Calling DXers" on this frequency at approximately 2300 every Tuesday while "DX Circle" is broadcast by Deutschlandfunk, West Germany, on alternate Wednesdays at 1900 on 1268kHz. "DX Circle" can only be heard on the medium waves.

N. Taylor (Sunbury-on-Thames) has a PW Medium Wave Loop but is having some difficulty using it with his Pioneer SX737 receiver which has its own internal aerial. A method tried by the writer is to attach the receiver to the centre of the loop so that the nulls of the loop and an internal aerial coincide, i.e., point in the same direction. The loop and the receiver are then rotated together to null out unwanted stations, coupling between the two being by induction.

Harold Emblem writes again from Mirfield in Yorkshire. With his Eddystone 730 and MW loop he has heard CJON in St. John's in Newfoundland on 930kHz, WCBS in New York City on 880kHz, Arkhangelsk with local identification and sign-on at 0200 and Tashkent in Uzbekistan with sign-on at 0300, both stations on 908kHz. Harold mentions that if reception towards the east is good then Arkhangelsk will not be heard, a good pointer to conditions. Three of the Greek Armed Forces (Yened) low power stations have been heard recently by the writer during the evenings. Kavala on 1355kHz was logged at 2115 with news in English with unidentified parallel outlets on 1301kHz (Serrae off frequency?) and on 1291kHz. The transmission on 1301kHz was heard until sign-off at 2200 GMT.

### BROADCAST BANDS

Short Wave Reports by the 15th of the month to Derek Bell, c/o Practical Wireless, Fleetway House, Faringdon Street, London, EC4A 4AD. Medium Wave Logs to Charles Molloy, 132 Segars Lane, Southport, PR5 3JG.

### AMATEUR BANDS

Logs covering any amateur bands in band/alphabetical order by the end of the month to Eric Dowdall G4AR, Silver Pine, Leatherhead Road, Ashford, Surrey, KT21 3TW.

# points arising...

ASCOT STEREO CASSETTE DECK, FEB/MARCH/APRIL 1975

Some minor points have arisen:-

- p819 Recording Amplifier second para, VR6 should read VR5. Fig. 4 R23 should be between C12 and R21.
- p820 Component List C30 is electrolytic. C30 is tantalum. S8 is SPDT. Add S8 DPDT. Add F3, 250mA cartridge fuse and holder. C32 one off only.
- p891 Fig. 5. R36 should be between Tr13(e) and C32.
- p892 Fig. 7. add resistor 15kΩ in series with pause switch, between RH end of R63 and + line.
- p893 Fig. 8. add 15kΩ between A26 and rail A.
- p1057 Fig. 10. S2 should read S4.
- p1088 Fig. 11. Unmarked resistor below Tr12 is R38. C26 above Tr9 should read R26. C21, left of Tr7, should read R21.
- p1090 Fig. 12. L2 should read L1.
- p1093 In Note:- Fig. 3 Part 2 'collector' should read 'emitter'.

UHF WAVEMETER, JULY 1975

- p241 Fig. 4. Resistor 'k' should be marked 1kΩ.

# Sinclair Scientific kit

**Britain's most original calculator – now in kit form**

The Sinclair Scientific is an amazing calculator. It offers logs, trig, and true scientific notation over a 200-decade range – features normally found on calculators costing around £50 or more.

Yet even ready-built, it costs a mere £21.55 (including VAT).


And as a kit it costs under £15!

**Forget slide rules and four-figure tables**

On the Scientific, you can handle *directly* all three trig functions, their inverses,  $\log_{10}$ ,  $\text{antilog}_{10}$ , giving quick access to  $x^y$  (including square and other roots),

plus, of course, the four arithmetic functions and any calculation based on them.

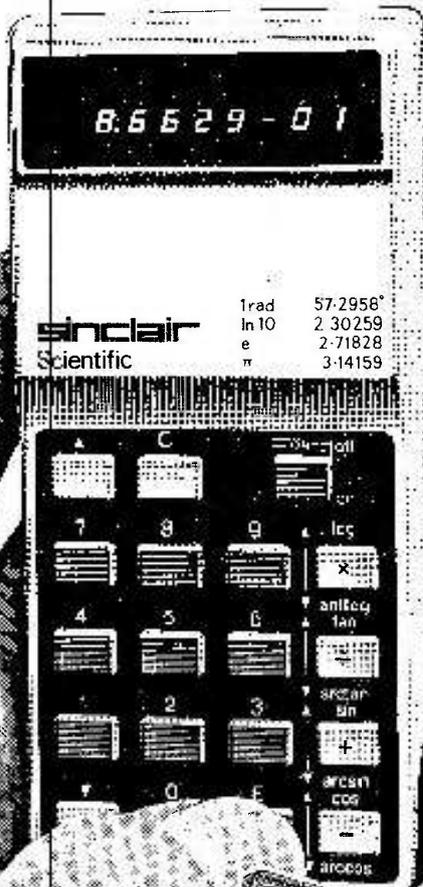In fact, virtually all complex scientific or mathematical calculations can be handled with ease.



**Now only  
£14.95  
(inc. VAT)**

**So is the Scientific difficult to assemble?**

No. Powerful though it is, the Sinclair Scientific is a model of tidy engineering. All parts are supplied – all you need provide is a soldering iron and pair of cutters. Complete step-by-step instructions are provided, and our Service Department will back you throughout if you've any queries or problems.

Of course, we'll happily supply the Scientific or the Cambridge already built, if you prefer – they're still exceptional value. Use the order form.

**Features of the Scientific**

- 12 functions on a simple keyboard
- Scientific notation
- 200-decade range
- Reverse Polish logic
- 25-hour battery life
- Genuinely pocketable

# Sinclair Cambridge kit

At its new low price, the Sinclair Cambridge kit remains unbeatable value.

The Cambridge is now Britain's most popular pocket calculator. And it's not surprising. Check the features – then ask yourself what other calculator offers such a powerful package at such a reasonable price.

**Take advantage of this money-back no-risk offer today**

The Sinclair Cambridge and Scientific kits are fully guaranteed. Return either kit within 10 days, and we'll refund your money without question. All parts are tested and checked before despatch – and we guarantee any correctly-assembled calculator for a year. This guarantee also applies to calculators supplied in built form.

Simply fill in the preferential order form below and post it – today!

**Now only  
£9.95  
(inc. VAT)**



**Features of the Cambridge**

- Only  $4\frac{1}{8}'' \times 2'' \times \frac{1}{16}''$ . Weight  $3\frac{1}{2}$  oz.
- Fully-floating decimal point.
- Algebraic logic.
- Constant on all four functions (+ - × ÷).
- Constant and algebraic logic combine to act as limited memory.
  - Clear, bright 8-digit display.
  - Operates for weeks on 4 AAA batteries.

To: Sinclair Radionics Ltd, FREEPOST, St Ives, Huntingdon, Cambs., PE17 4BR.

Please send me

Scientific kit – £14.95 inc. VAT

Scientific built – £21.55 inc. VAT

Cambridge kit – £9.95 inc. VAT

Cambridge built – £13.99 inc. VAT

\*I enclose a cheque for ..... made out to Sinclair Radionics Ltd, crossed.

\*Please debit my \*Access/Barclaycard account number: \_\_\_\_\_

\*Delete as required

Signed \_\_\_\_\_ Name \_\_\_\_\_

Address \_\_\_\_\_

Please print. FREEPOST – no stamp required.

Sinclair Radionics Ltd,  
London Road, St Ives, Huntingdon, Cambs., PE17 4JH. Tel: St Ives (0480) 64646  
Reg. no: 699483 England. VAT Reg. no: 213 8170 83



ENGINEERS

**FREE**

**YOURSELF FOR A BETTER JOB WITH MORE PAY!**

Do you want promotion, a better job, higher pay? "New Opportunities" shows you how to get them through a low-cost home study course. There are no books to buy and you can pay-as-you-learn.



This helpful guide to success should be read by every ambitious engineer. Send for this helpful 76 page FREE book now. No obligation and nobody will call on you. It could be the best thing you ever did.

**CUT OUT THIS COUPON**  
**CHOOSE A BRAND NEW FUTURE HERE!**  
 Tick or state subject of interest. Post to the address below.

|  |   |   |
|--|---|---|
| Build-As-You-Learn PRACTICAL RADIO AND ELECTRONICS (with kit) <input type="checkbox"/> | Electrical Mathematics <input type="checkbox"/>                   | Transistor Technology <input type="checkbox"/>                  |
| Electrical Engineering <input type="checkbox"/>  | Electronic Engineering <input type="checkbox"/>                   | CITY AND GUILDS <input type="checkbox"/>                        |
| Electrical Installations and wiring <input type="checkbox"/>                           | Computer Electronics <input type="checkbox"/>                     | Installations and Wiring <input type="checkbox"/>               |
| Electrical Draughtsmanship <input type="checkbox"/>                                    | Computer Programming <input type="checkbox"/>                     | CITY AND GUILDS Electrical Technicians <input type="checkbox"/> |
|  | General Radio and TV Engineering <input type="checkbox"/>         | CITY AND GUILDS Telecommunications <input type="checkbox"/>     |
|  | Radio Servicing, Maintenance and Repairs <input type="checkbox"/> | Radio Amateurs' Exam etc. etc. <input type="checkbox"/>         |

To ALDERMASTON COLLEGE Dept. EPW-06, Reading RG7 4PF **EPW 06**  
 Also at our London Advisory Office, 4 Fore Street Avenue, Moorgate London, EC2Y 5EJ Tel: 01-828 2721

NAME (Block Capitals Please) \_\_\_\_\_  
 ADDRESS \_\_\_\_\_ POST CODE \_\_\_\_\_  
 Other subjects \_\_\_\_\_ Age \_\_\_\_\_  
 Accredited by C.A.C.C. Member of A.B.C.C.

**HOME OF BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY**

**TONER ELECTRONICS**

FOR

(Components, Transistors, Valves, Hi-Fi, all accessories, leads, etc., stocked. Speakers, Cartridges, Microphones, Tapes.)

Send 15p for price lists and our bargain page (Callers Welcome).

38 MORGAN ST., WATERFORD, IRELAND  
 Phone: 051-32300

**PUBLISHER'S ANNOUNCEMENT**




The contents of *Practical Wireless* is fully protected by international copyright and reproduction of it in any

form is prohibited without our consent.

With effect from this announcement for permission to reproduce, or use our material in any way or part of, must be made to the Editor. Under no circumstances will permission be given to reproduce material in a similar or competitive publication, without payment. No application need be made in the case of a private constructor, constructing one item for his/her own enjoyment and interest.

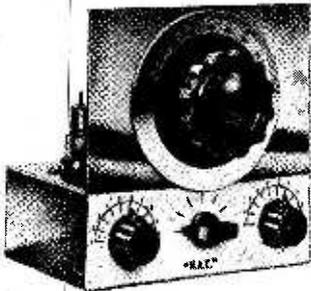**H.A.C. SHORT-WAVE KITS**  
**WORLD-WIDE RECEPTION**



Famous for over 35 years for Short-Wave Equipment of quality. "H.A.C." were the Original suppliers of Short-Wave Receiver Kits for the amateur constructor. Over 10,000 satisfied customers—including Technical Colleges, Hospitals, Public Schools, R.A.F., Army, Hams, etc.

**1975 "DX" RECEIVER**  
 Complete kit—Price £5-50 (incl. p. & p. & V.A.T.). Customer writes: "Australia, India and America at loud volume." "I have now heard over 800 stations including many Amateurs. I have received 82 Q.S.L. verified reports—from all continents. An amazing one-valver."  
 This kit contains all genuine short-wave components, drilled chassis, valve, accessories and full instructions. Ready to assemble, and of course, as all our products—fully guaranteed. Full range of other S.W. kits, including the famous model "K plus" (illustrated above). All orders despatched within 7 days. Send now for free descriptive catalogue of kits and components.  
 Send stamped envelope for details.

**"H.A.C." SHORT-WAVE PRODUCTS**  
 P.O. BOX No. 16, EAST GRINSTEAD, SUSSEX RH19 3SN

250w Light Dimmers £2-70 (15p)  
**SEMICONDUCTORS** (p. & p. 10p).  
 All new and full spec.  
 BC107/8/9, BC147/8/9, BC157/8/9 all 9p  
 BF180 25p, BF182/3 40p, BF184 17p,  
 BF187 13p, BW10 55p, 741 8DIL 28p,  
 BF336 35p, 2N3771 £1-10, 2N3441 50p,  
 BD131, 40p, 2N3055 45p, NE555 50p.  
 2N 3819E 20p, BFY51 20p.

**EX COMPUTER PC PANELS**  
 4 x 2in packed with semiconductors and top quality resistors, capacitors, diodes etc. Guaranteed min. 35 transistors, plus data 25 boards £1 (35p)

**ELECTROLYTICS**  
 2,200µ 63v 35p (11p)  
 2,000µ 50v with clip 35p (11p)  
 15,000µ 30v, 68,000µ 16v 65p (32p)  
 30,000µ 25v 65p (32p)  
 3,600µ 40v 4 x 2" 55p (32p)  
 5,000µ 35v 40p (15p)  
 20A 100 p1v Si recs 4 for £1 (13p)  
 250 mixed resistors 60p (15p)  
 250 mixed capacitors 60p (15p)  
 150 mixed HI-STABS 60p (13p)  
 QH bulbs 12v 55w 50p (8p)  
 2N3055 EQUIV 4 for £1 (12p)  
 Sub Min Co-Ax connectors 4 prs. 70p (8p).

**SMALL ELECTROLYTICS**  
 2-2µ 10/16v, 10µ 35v, 50µ 40v, 100µ 40v,  
 100µ 6v, 150µ 10v, 64µ 10v 12 for 45p (7p).  
**PRESETS 100mW "PIHER"**  
 220Ω 470Ω 4k7 10k 100k 12 for 50p (7p).  
 Postage and packing shown in brackets  
**ADD 25% VAT to TOTAL**

**KEYTRONICS**  
 (Mail Order only)  
**44 EARLS COURT ROAD**  
**LONDON W8. 01-478 8499**

# NEW MULLARD & MAZDA VALVES

All individually boxed and guaranteed. Full trade discounts to bona fide companies. Price and availability lists on application.

## EXPRESS POSTAGE

10p for 1 Valve.  
Each additional Valve add 2p in UK

|        |      |        |      |        |      |            |      |            |      |
|--------|------|--------|------|--------|------|------------|------|------------|------|
| DM70   | 0-61 | ECL83  | 0-88 | PC86   | 0-95 | PL82       | 0-48 | 30C1/PCF80 |      |
| DY51   | 0-80 | ECL86  | 0-84 | PC88   | 0-95 | PL83       | 1-04 | 30C15/     | 0-54 |
| DY86/7 | 0-41 | EF80   | 0-42 | PC97   | 0-42 | PL84       | 0-68 | PCF800     | 1-01 |
| DY802  | 0-46 | EF83   | 0-98 | PC900  | 0-47 | PL504      | 0-90 | 30C17      | 1-01 |
| EABC80 | 1-08 | EF85   | 0-92 | PC984  | 0-54 | PL508      | 1-24 | 30C18/     |      |
| EB91   | 0-64 | EF86   | 1-16 | PC985  | 0-80 | PL509      | 1-56 | PCF805     | 1-00 |
| EBC81  | 0-79 | EF89   | 1-14 | PC988  | 0-86 | PL802      | 1-40 | 30F5/EF818 |      |
| EBF80  | 0-58 | EF91   | 1-00 | PC989  | 0-64 | PY33       | 0-65 |            | 1-03 |
| EBF83  | 0-59 | EF92   | 1-37 | PC989  | 0-80 | PY81/800   | 0-49 | 30FL1/     |      |
| EBF89  | 0-58 | EF95   | 1-47 | PC989  | 0-80 | PY82       | 0-67 | PCF800     | 1-00 |
| EC86   | 0-78 | EF182  | 0-83 | PCF80  | 0-54 | PY88       | 0-56 | 30FL2      | 0-80 |
| EC88   | 0-76 | EF184  | 0-83 | PCF82  | 1-22 | PY500A     | 1-02 | 30FL12     | 1-13 |
| EC90   | 0-86 | EB90   | 0-85 | PCF86  | 0-64 | PY800      | 0-49 | 30FL14     | 1-00 |
| EC97   | 0-80 | EL34   | 0-92 | PCF200 | 1-00 | PY801      | 0-49 | 30L1/PC084 |      |
| ECC81  | 0-47 | EL36   | 1-01 | PCF201 | 1-00 | U26        | 0-88 |            | 0-54 |
| ECC82  | 0-44 | EL81   | 0-85 | PCF802 | 0-70 | U191       | 0-88 | 30L15/     |      |
| ECC83  | 0-47 | EL84   | 0-47 | PCF806 | 0-64 | U193       | 0-54 | PCC805     | 1-03 |
| ECC84  | 0-58 | EL85   | 0-85 | PCH200 | 1-15 | UABC80     | 0-90 | 30L17      | 0-89 |
| ECC85  | 0-71 | EL86   | 0-92 | PCF801 | 0-64 | UBC81      | 0-71 | 30P4MR     | 1-27 |
| ECC88  | 0-84 | EL91   | 0-00 | PCL82  | 0-56 | UUC85      | 0-59 | PC012/     |      |
| ECC189 | 0-68 | EL95   | 0-72 | PCL84  | 0-61 | UCH81      | 1-12 | PC801      | 1-01 |
| ECF80  | 0-60 | ELL80  | 2-50 | PCL85  | 0-64 | UCL82      | 0-72 | PC019/     |      |
| ECF86  | 0-88 | EY51   | 0-78 | PCL86  | 0-64 | UCL83      | 0-72 | PC802      | 0-89 |
| ECH81  | 1-18 | EY86/7 | 0-40 | PD500  | 1-88 | UF89       | 0-80 | 30PL1/     |      |
| ECH83  | 0-94 | EY88   | 0-72 | PDL200 | 0-83 | UL84       | 0-92 | 30L801     | 1-00 |
| ECH84  | 1-00 | EZ80   | 0-54 | PL36   | 0-90 | UY85       | 0-54 | 30PL13/    |      |
| ECL80  | 0-67 | EZ81   | 0-88 | PL81   | 0-77 | 6/30L2/    |      | PCL800     | 1-15 |
| ECL82  | 0-64 |        |      | PL81A  | 0-90 | ECC804     | 0-98 | 30PL14/    |      |
|        |      |        |      |        |      | 6F23/EF812 | 1-03 | PCL88      | 1-35 |
|        |      |        |      |        |      |            |      | 30PL15     | 1-13 |

# NEW VALVES

Individually boxed and guaranteed but of European or other origin at greatly reduced prices. Quotations for any valve not listed. Send SAE for lists.

|         |      |            |      |       |      |           |      |         |       |
|---------|------|------------|------|-------|------|-----------|------|---------|-------|
| AZ1     | 0-75 | EF39       | 1-25 | KTW61 | 1-50 | PY88      | 0-58 | 6F28    | 0-75  |
| AZ31    | 0-60 | EF80       | 0-35 | MU14  | 1-00 | PY88      | 0-58 | 6J5M    | 0-65  |
| CB131   | 1-40 | EF85       | 0-45 | N78   | 3-50 | PY600     | 1-10 | 6J5G    | 0-45  |
| CL33    | 1-50 | EF86       | 0-50 | OA2   | 0-45 | PY81/800  | 0-50 | 6J6     | 0-85  |
| CY31    | 0-60 | EF89       | 0-95 | OB2   | 0-45 | SP41      | 3-00 | 6J7G    | 0-30  |
| DAF91   | 0-40 | EF91       | 0-40 | PC86  | 0-65 | SP61      | 0-85 | 6K6GT   | 0-80  |
| DAF96   | 0-60 | EF92       | 0-50 | PC88  | 0-65 | T41       | 1-00 | 6K7G    | 0-85  |
| DC90    | 1-85 | EF95       | 0-45 | PC97  | 0-55 | U14       | 0-75 | 6K7M    | 0-45  |
| DF91    | 0-40 | EF98       | 0-50 | PC900 | 0-55 | U25       | 1-00 | 6K8G    | 0-45  |
| DF96    | 0-60 | EF183      | 0-40 | PC984 | 0-54 | U26       | 0-85 | 6K8M    | 0-70  |
| DK91    | 0-50 | EF184      | 0-40 | PC985 | 0-80 | U191      | 0-75 | 6K25    | 1-00  |
| DK92    | 1-00 | EL32       | 0-80 | PC988 | 0-86 | UABC80    | 0-40 | 6L6G    | 0-55  |
| DL96    | 0-75 | EL33       | 2-50 | PC989 | 0-64 | UAF42     | 0-75 | 6Q7G    | 0-40  |
| DL92    | 0-50 | EL34       | 0-70 | PC989 | 0-80 | UBC41     | 0-60 | 6Q7M    | 0-80  |
| DL94    | 0-48 | EL36       | 0-90 | PC989 | 0-80 | UBC81     | 0-50 | 68L7GT  | 0-85  |
| DL96    | 0-55 | EL37       | 2-50 | PC989 | 0-80 | UBF80     | 0-50 | 68N7GT  | 0-85  |
| DY87    | 0-45 | EL41       | 0-90 | PC989 | 0-80 | UBF89     | 0-50 | 68Q7GT  | 0-40  |
| DY802   | 0-47 | EL42       | 1-85 | PC989 | 0-80 | UCC85     | 0-50 | 6U5G    | 1-50  |
| EABC80  | 0-38 | EL84       | 0-35 | PC989 | 0-80 | UCH81     | 0-80 | 6V6G    | 0-30  |
| EAF42   | 0-70 | EL95       | 0-60 | PC989 | 0-80 | UCH81     | 0-80 | 6V6GT   | 0-30  |
| EB91    | 0-25 | ELL80      | 2-00 | PC989 | 0-80 | UCL82     | 0-40 | 6X4     | 0-45  |
| EBC33   | 1-00 | EM80       | 0-55 | PC989 | 0-80 | UCL83     | 0-70 | 6X5G    | 0-45  |
| EBC34   | 0-75 | EM81       | 0-60 | PC989 | 0-80 | UF41      | 0-75 | 6X5GT   | 0-55  |
| EBC81   | 0-40 | EM84       | 0-40 | PC989 | 0-80 | UF89      | 0-50 | 7B6     | 0-80  |
| EBF80   | 0-40 | EM85       | 1-00 | PC989 | 0-80 | UL41      | 0-85 | 7B7     | 0-80  |
| EBF83   | 0-40 | EM87       | 1-00 | PC989 | 0-80 | UL84      | 0-85 | 7C5     | 1-80  |
| EBF89   | 0-32 | EY51       | 0-45 | PC989 | 0-80 | UY41      | 0-55 | 7C6     | 1-00  |
| EBL31   | 2-00 | EY86       | 0-45 | PC989 | 0-80 | UY85      | 0-45 | 7H7     | 0-80  |
| ECC81   | 0-45 | EZ40       | 0-60 | PC989 | 0-80 | VR105/30  | 0-40 | 7R7     | 0-80  |
| ECC82   | 0-88 | EZ41       | 0-75 | PC989 | 0-80 | VR150/30  | 0-45 | 787     | 2-25  |
| ECC83   | 0-88 | EZ80       | 0-30 | PC989 | 0-80 | IR5       | 0-50 | 7Y4     | 0-80  |
| ECC84   | 0-85 | EZ81       | 0-81 | PC989 | 0-80 | 185       | 0-40 | 12AT6   | 0-45  |
| ECC85   | 0-45 | GY501      | 0-90 | PC989 | 0-80 | 1T4       | 0-40 | 12AT7   | 0-45  |
| ECC88   | 1-50 | GZ30       | 0-65 | PC989 | 0-80 | 384       | 0-50 | 12AU6   | 0-50  |
| ECH35   | 0-50 | GZ32       | 0-65 | PC989 | 0-80 | 3V4       | 0-85 | 12AU7   | 0-38  |
| ECH42   | 0-85 | GZ34       | 0-75 | PC989 | 0-80 | 5R4GY     | 1-00 | 12AX7   | 0-38  |
| ECH81   | 0-35 | GZ37       | 1-25 | PC989 | 0-80 | 5U4G      | 0-55 | 12BA6   | 0-50  |
| ECH83   | 0-50 | HN309      | 1-50 | PC989 | 0-80 | 5Y3GT     | 0-85 | 12BR6   | 0-60  |
| ECL80   | 0-60 | KT61       | 2-50 | PC989 | 0-80 | PCL82     | 0-45 | 30C1    | 0-40  |
| ECL82   | 0-48 | KT66       | 2-95 | PC989 | 0-80 | PCL83     | 0-70 | 30C15   | 1-00  |
| ECL83   | 0-75 | KT81 (7C5) |      | PC989 | 0-80 | PCL84     | 0-50 | 30C17   | 1-00  |
| ECL86   | 0-55 |            |      | PC989 | 0-80 | PCL85     | 0-60 | 30C18   | 0-90  |
| ECLL800 | 3-50 | KT81       | 1-75 | PC989 | 0-80 | PCL86     | 0-50 | 30F5    | 1-00  |
| EF37A   | 1-20 | KT88       | 3-25 | PC989 | 0-80 | PCL805/85 |      | 30FL1   | 1-00  |
|         |      |            |      | PC989 | 0-80 | PD500     | 1-50 | 30FL2   | 0-75  |
|         |      |            |      | PC989 | 0-80 | PEN45     | 0-85 | 30FL14  | 1-00  |
|         |      |            |      | PC989 | 0-80 | PL36      | 0-88 | 30L15   | 0-95  |
|         |      |            |      | PC989 | 0-80 | PL81      | 0-55 | 30L17   | 0-95  |
|         |      |            |      | PC989 | 0-80 | PL82      | 0-50 | 30P4MR  | 1-30  |
|         |      |            |      | PC989 | 0-80 | PL83      | 0-50 | 30P12   | 1-00  |
|         |      |            |      | PC989 | 0-80 | PL84      | 0-50 | 30P19   | 0-95  |
|         |      |            |      | PC989 | 0-80 | PL504     | 0-85 | 30PL1   | 0-95  |
|         |      |            |      | PC989 | 0-80 | PL508     | 0-90 | 30PL13  | 1-10  |
|         |      |            |      | PC989 | 0-80 | PL509     | 1-55 | 30PL14  | 1-10  |
|         |      |            |      | PC989 | 0-80 | PL802     | 1-00 | 35W4    | 0-60  |
|         |      |            |      | PC989 | 0-80 | PX25      | 3-50 | 85ZAGT  | 0-70  |
|         |      |            |      | PC989 | 0-80 | PY33      | 0-68 | 60CD6G  | 1-20  |
|         |      |            |      | PC989 | 0-80 | PY81      | 0-50 | 60C7    | 1-00  |
|         |      |            |      | PC989 | 0-80 | PY82      | 0-45 | 813TTT  | 14-00 |
|         |      |            |      | PC989 | 0-80 | 6F23      | 0-80 | 813USSR | 6-00  |
|         |      |            |      | PC989 | 0-80 | 6F25      | 1-00 | 866A    | 1-20  |

# TRANSISTORS-INTEGRATED CIRCUITS

## EXPRESS POSTAGE

10p per order in UK

All transistors, I.C.'s offered are new and branded. Manufactured by Mullard, Texas, RCA, Ferranti, Motorola, ITT, Fairchild, Lucas, etc. Quantity discounts on application. Send SAE for full lists.

|        |      |              |      |              |      |         |      |         |      |
|--------|------|--------------|------|--------------|------|---------|------|---------|------|
| AA119  | 0-07 | BD124        | 0-65 | OA200        | 0-08 | ZTX501  | 0-15 | 2N2904A | 0-25 |
| AAZ13  | 0-12 | BD131        | 0-42 | OA202        | 0-08 | ZTX503  | 0-16 | 2N2905  | 0-25 |
| AAZ15  | 0-10 | BD132        | 0-50 | OC16         | 1-00 | ZTX531  | 0-25 | 2N2905A | 0-25 |
| AC107  | 0-51 | BF115        | 0-20 | OC20         | 2-00 | ZTX550  | 0-18 | 2N2906  | 0-20 |
| AC126  | 0-25 | BF167        | 0-25 | OC23         | 1-25 | LN914   | 0-08 | 2N2926  | 0-12 |
| AC127  | 0-25 | BF173        | 0-28 | OC25         | 0-40 | IN4001  | 0-08 | 2N3053  | 0-18 |
| AC128  | 0-15 | BF179        | 0-33 | OC28         | 0-65 | IN4002  | 0-07 | 2N3055  | 0-45 |
| AC176  | 0-25 | BF180        | 0-38 | OC35         | 0-65 | IN4003  | 0-08 | 2N3525  | 0-45 |
| AC187  | 0-21 | BF181        | 0-35 | OC36         | 0-60 | UN4004  | 0-08 | 2N3614  | 0-65 |
| AC188  | 0-20 | BF194        | 0-10 | OC42         | 0-40 | UN4005  | 0-10 | 2N3615  | 0-65 |
| AC191  | 0-22 | BF195        | 0-13 | OC44         | 0-20 | UN4006  | 0-18 | 2N3702  | 0-11 |
| AC192  | 0-22 | BF196        | 0-13 | OC45         | 0-20 | UN4007  | 0-12 | 2N3703  | 0-12 |
| AC193  | 0-22 | BF197        | 0-15 | OC71         | 0-18 | UN4009  | 0-08 | 2N3704  | 0-14 |
| AD140  | 0-80 | BF200        | 0-32 | OC72         | 0-23 | LN4148  | 0-06 | 2N3705  | 0-15 |
| AD149  | 0-50 | BF261        | 0-25 | OC76         | 0-80 | IS921   | 0-07 | 2N3706  | 0-11 |
| AD161  | 0-44 | BF268        | 0-25 | OC77         | 0-50 | IS9233  | 0-20 | 2N3707  | 0-18 |
| AD162  | 0-44 | BF270        | 0-28 | OC81         | 0-28 | IS2061A | 0-20 | 2N3709  | 0-10 |
| AD165  | 0-25 | BF279        | 0-28 | OC81D series | 0-28 | IS2100A | 0-20 | 2N3710  | 0-11 |
| AF115  | 0-25 | BF280        | 0-24 | OC81Z        | 0-45 | IS3010  | 0-25 | 2N3710  | 0-11 |
| AF116  | 0-25 | BF288        | 0-24 | OC83         | 0-27 | IN2696  | 0-16 | 2N3711  | 0-11 |
| AF117  | 0-24 | BF289        | 0-20 | OC140        | 1-14 | 2N697   | 0-16 | 2N3819  | 0-28 |
| AF186  | 0-48 | BFY51        | 0-20 | OC170        | 0-30 | 2N706   | 0-10 | 2N3820  | 0-50 |
| AF239  | 0-44 | BFY52        | 0-20 | OC200        | 0-55 | 2N1131  | 0-28 | 2N3823  | 0-50 |
| ASY27  | 0-83 | BY100        | 0-27 | OC201        | 1-00 | 2N1132  | 0-24 | 2N3825  | 0-15 |
| BA102  | 0-25 | BY126        | 0-14 | OC202        | 0-90 | 2N1302  | 0-18 | 2N3805  | 0-25 |
| BA115  | 0-15 | BY127        | 0-15 | OC203        | 0-65 | 2N1303  | 0-18 | 2N3806  | 0-25 |
| BC107  | 0-14 | BZX61 series | 0-20 | OC207        | 1-20 | 2N1804  | 0-28 | 2N4058  | 0-10 |
| BC108  | 0-13 | BZY88 series | 0-10 | OC210        | 0-50 | 2N1805  | 0-28 | 2N4060  | 0-13 |
| BC109  | 0-12 | CR81-05      | 0-35 | OC171        | 0-30 | 2N706A  | 0-28 | 2N4061  | 0-13 |
| BC113  | 0-25 | CR81-40      | 0-60 | OC172        | 0-30 | 2N706A  | 0-28 | 2N4062  | 0-14 |
| BC117  | 0-21 | CR83-05      | 0-40 | OC200        | 0-55 | 2N1131  | 0-28 | 2N4062  | 0-14 |
| BC143  | 0-80 | CR83-40      | 0-65 | OC201        | 1-00 | 2N1132  | 0-24 | 2N4289  | 0-30 |
| BC147  | 0-10 | MJE340       | 0-47 | OC202        | 0-90 | 2N1302  | 0-18 | 3N120   | 1-75 |
| BC148  | 0-08 | MJE370       | 0-68 | OC203        | 0-65 | 2N1303  | 0-18 | 3N120   | 1-75 |
| BC169C | 0-15 | MJE520       | 0-65 | OC210        | 0-50 | 2N1804  | 0-28 | 3N120   | 1-75 |
| BC182  | 0-18 | MJE2955      | 1-27 | ORP12        | 0-60 | 2N1305  | 0-28 | 3N120   | 1-75 |
| BC182L | 0-12 | MJE3055      | 0-75 |              |      |         |      |         |      |

# S.W.Ls! A GOOD TRANSMITTING AERIAL is also A GOOD RECEIVING AERIAL!!

**ZL1ASY** worked GC3EML on 20m with \*"JOYSTICK LYING ON FLOOR OF SHACK"  
**G2BAH** (ex G4CJN) Kendal, "I happened to be listening on 80m and heard someone in Manchester testing, we established a strength 8 QSO each way. He had a \*VFA laying on his kitchen table and was making tests to see if it would load up etc. An old timer, a G2 and 2 letters, so he knew what he was doing."  
**G3ZDR** worked a W3 on 20m using a \*VFA and 5 watts.  
**G3VFA** worked W1TW on 20m using a \*VFA and 750mw.  
**W6TYP** worked WA6JPR over hundreds of miles on 40m using a \*VFA & MICROWATTS "equivalent to ONE MILLION!!! miles per watt of input power" (so says the WORLD RECORD certificate).  
 P.W. "ON THE AIR" feature reports "Terry Gilbert sends a logging of a VERY RARELY reported station, Radio Afghanistan on 15195 at 1130. This goodie was pulled in via a Codar CR70A and JOYSTICK"  
 (\*VFA). \*These are VFA USERS' claims, and remember SWLs—A GOOD TRANSMITTING AERIAL IS A GOOD RECEIVING AERIAL ALSO. (You sure can't work 'em if you can't hear 'em!)

Here is YOUR complete World Record Aerial System for 160, 80, 40, 20, 15 & 10m plus all SW BC, bands and everything between—FOR ANY LOCATION—HOWEVER RESTRICTED.

**SYSTEM "A"** for modern Communications RX's and QRP work £32.76  
**SYSTEM "D"** for other SW & MW receivers £24.43  
**SYSTEM "J"** for TX's & XCVR's up to 500w PEP 160 thru 10m £40.72

All prices DELIVERED—including packing & insurance.

Send stamp for FULL LIST including the PARTRIDGE SUPER PACKAGE COMPLETE GENERAL COVERAGE LISTENING STATION FOR ANY LOCATION.

(Prices subject to alteration without notice)



Phone 0843 62535  
 or 62839  
 After office hours  
 G3CED G3VFA



## B. BAMBER ELECTRONICS

5 STATION ROAD, LITTLEPORT, CAMBS., CB6 1QE

Telephone: ELY (0353) 860185 (2 lines) Tuesday-Saturday

TV plugs, metal type, 6 for 50p.  
 TV sockets, metal type, 5 for 50p.  
 TV line connectors (back-to-back socket), 5 for 50p.

TO3 transistor insulator sets, 10 for 50p.  
 Mixed electrolytics, large bag, £1.  
 PC board withdrawal handles, mixed cols., 8 for 50p.  
 Solder, 20SWG, 60/40 alloy, approx. 9yds, 25p.

OA81 diodes, 15 for 25p.  
 OC200 transistors, 8 for 50p.  
 Perspex coil formers, 1 1/2in x 1/2in dia., 5 for 25p.

Turret tags, 1/2in dia., 25p pack.  
 Rotary switches, min. 4 pole 2-way, 2 for 50p.

Telephone type earpiece insert, 50p.  
 Reeds (for reed relays) single-pole make, 5 for 30p.

Mullard tubular ceramic trimmers, 1-18uF, 6 for 50p (as featured in Red. Comm. Jan. p. 25).

I.C.s, some coded, 14DIL type, untested, mixed, 20 for 25p.  
 IF cans 1/2in square, suitable for rewind, 6 for 30p.

Small neons, 6 for 25p.  
 24V min. read relays, encapsulated single-pole make, 2 for 50p.

24V 2-8W lamps, MES type, 6 for 20p.  
 Chassis tags, 25p pack.  
 Cable clips, for railing cable, 15p pack.  
 Miniature slider switches, 2 pole, 2-way, 5 for 50p.

BSY95A transistors, 6 for 50p.  
 6-3V 0-3A capless lamps, 10 for 25p.  
 PNP audio type TO5 transistors, 12 for 25p.  
 Black plastic knobs, 1/2in dia., 1/2in spindle, 4 for 50p.

Ring magnets, 7mm outside dia., 20 for 50p.  
 Large box of P.C. Boards, containing transistors, I.C.s, trimpots, resistors, capacitors, etc. (not unknown computer rubbish), £3 per box.

1 1/2in polythene chassis mounting fuse-holders, 6 for 30p.  
 LES Lamps, 24V 1-2W, 10 for 40p.

**MAINS TRANSFORMERS**  
 All 240V input, voltages quoted approx. RMS. (Please quote type no. only when ordering)

TYPE 10/2, 10-0-10V at 2A, £1.50 each.  
 TYPE 18/2, 18V at 2A, £1.65 each.  
 TYPE 18/6, 18V at 6A + 45V at 100mA, £4.  
 TYPE 28/4, 28V at 4A + 125V at 500mA, £4.  
 TYPE 63/1, 6-3V at 1A, 85p each or 2 for £1.50.

TYPE 129, 400V at 20mA + 200V at 10mA + 6-3V at 500mA, £1.25.  
 TYPE 72703, 400V at 10mA + 200V at 5mA + 6-3V at 400mA, £1.25.  
 TYPE 70462, 250-0-250V at 80mA + 6-3V at 2A, £1.75.

**RADIO SPARES 500W AUTO TRANSFORMERS**, 100-110-130-200-220-240-250V tapped input, and output, step-up or step-down facility, ex-new equip, £8.

**CURLY LEADS**, 4 core telephone type, 2 for 20p.

**TRANSISTOR HEATSINKS**, to take 2 x TO18 transistors, screw in clamps, block size 1 x 1/2 x 1/2in, with holes for mounting, 3 for 50p.

**VARIABLE STABILISED PSU**, solid-state 240V a.c. input, output 0-24V d.c. at 500mA, +32V d.c. at approx. 50mA. Voltage controlled by external 5kΩ pot. Size 7 1/2 x 4 x 2 1/2in (less 5kΩ pot), £5 each.

**THREE-TURN WIRE-WOUND POTS**, 5kΩ, for above, 75p each.

**LARGE DIE CAST BOXES** (brand new ITT) 10 1/2 x 6 1/2 x 2 1/2in, £2 each.  
**25-way ISEP PLUGS AND SOCKETS**, 40p each (1 plug + 1 socket).

**DIN SPEAKER SOCKETS** (2-pin) 4 for 30p.  
**HIGH QUALITY SPEAKERS**, 8 1/2 x 6in elliptical, only 2in deep, inverse magnet, 4 ohms, rated up to 10W, £1.50 each, or 2 for £2.75 (qty. discount available).

Rotary switches 9-way 4-pole (separate wafers, plastic) 1/2in spindle, 40p each.  
**Heatsinks** (Approx. 3in x 4in x 2in high), 12 fins (drilled for 1 x TO3 transistor) brand new, 45p each.

## D. J. ELECTRICAL SERVICES

81A Grays Inn Rd., London WC1 01-405-5118  
 DISCOUNT:—15% off for 12+20% off for 50, 25% off for 100+

**MAIL ORDERS ONLY**

**CASH WITH ORDER**

Add 10p p & p for orders under £3.00

All Prices inclusive of VAT.

All top branded makes and guaranteed.

|        |     |         |       |         |       |               |       |               |       |
|--------|-----|---------|-------|---------|-------|---------------|-------|---------------|-------|
| AC126  | 13p | BCY42   | 27p   | 2N698   | 28p   | 2N3054        | 42p   | 40310         | 48p   |
| AC127  | 13p | BCY43   | 25p   | 2N699   | 30p   | 2N3055        | 44p   | 40311         | 32p   |
| AC128  | 13p | BCY58   | 16p   | 2N706A  | 11p   | 2N3302        | 35p   | 40312         | 50p   |
| AC154  | 19p | BCY59   | 16p   | 2N708   | 13p   | 2N3440        | 50p   | 40314         | 32p   |
| AC187  | 12p | BF154   | 16p   | 2N914   | 16p   | 2N3525        | 80p   | 40315         | 32p   |
| AC188  | 12p | BF177   | 27p   | 2N916   | 24p   | 2N3614        | 60p   | 40316         | 48p   |
| ACY17  | 28p | BF182   | 33p   | 2N918   | 30p   | 2N2615        | 63p   | 40317         | 32p   |
| ACY20  | 19p | BF183   | 33p   | 2N920   | 45p   | 2N3663        | 12p   | 40319         | 39p   |
| ACY21  | 20p | BF185   | 20p   | 2N929   | 18p   | 2N3702        | 10p   | 40320         | 32p   |
| ACY22  | 15p | BF195   | 20p   | 2N961   | 55p   | 2N3703        | 10p   | 2S026         | £8.00 |
| ACY40  | 21p | BF196   | 11p   | 2N1131  | 20p   | 2N3704        | 11p   | TIP33C        | 80p   |
| ACY41  | 25p | BF200   | 31p   | 2N1132  | 20p   | 2N3705        | 10p   | TIP35         | £2.00 |
| ACY44  | 36p | BF274   | 18p   | 2N1302  | 16p   | 2N3707        | 10p   | TIP36         | £3.80 |
| AD149  | 45p | BFW88   | 19p   | 2N1303  | 16p   | 2N3708        | 5p    |               |       |
| AD161  | 35p | BFW89   | 18p   | 2N1304  | 16p   | 2N3709        | 7p    | <b>DIODES</b> |       |
| AD162  | 35p | BFW91   | 17p   | 2N1305  | 23p   | 2N3710        | 11p   | <b>STUD</b>   |       |
| AD162  | 35p | BFX29   | 25p   | 2N1306  | 23p   | 2N3711        | 11p   | 6amp          | 28p   |
| AF114  | 13p | BFX38   | 30p   | 2N1307  | 23p   | 2N3730        | 90p   | 15amp         | 45p   |
| AF117  | 13p | BFX85   | 25p   | 2N1308  | 27p   | 2N3771        | £1.10 |               |       |
| AF125  | 24p | BFX87   | 23p   | SN1309  | 27p   | 2N3773        | £2.25 | <b>BRIDGE</b> |       |
| AF139  | 32p | BFX88   | 21p   | 2N1671  | 90p   | 2N3791        | £2.25 | <b>REC.</b>   |       |
| AF178  | 49p | BFY11   | 20p   | 2N1671A | 95p   | 2N3819        | 25p   | 1amp 50v      | 24p   |
| BC107  | 10p | BFY18   | 47p   | 2N1671B | £1.00 | 2N3866        | 70p   | 2amp 600v     | 48p   |
| BC107B | 10p | BFY19   | 54p   | 2N2160  | 60p   | 2N3903        | 14p   | 4amp 200v     | 50p   |
| BC108  | 10p | BFY50   | 19p   | 2N2217  | 21p   | 2N3904        | 14p   | 6amp 100v     | 15p   |
| BC109  | 10p | BFY51   | 19p   | 2N2218  | 20p   | 2N3905        | 15p   |               |       |
| BC109B | 11p | BFY64   | 33p   | 2N2220  | 18p   | 2N3906        | 15p   | <b>SCR</b>    |       |
| BC113  | 13p | BFY90   | 72p   | 2N2297  | 27p   | 2N4061        | 12p   | 1/05          | 30p   |
| BC114  | 14p | BSW70   | 15p   | 2N2303  | 75p   | 2N5458        | 27p   | 1/10          | 35p   |
| BC115  | 13p | BSX26   | 22p   | 2N2369  | 13p   | OA81          | 15p   | 1/20          | 40p   |
| BC116  | 13p | BSX67   | 26p   | 2N2369A | 15p   | OA94          | 4p    | 16/400        | 80p   |
| BC116A | 14p | BY127   | 11p   | 2N2411  | 50p   | OC20          | £1.00 | 16/800        | £1.20 |
| BC117  | 13p | BU105   | £1.00 | 2N2646  | 44p   | OC28          | 50p   |               |       |
| BC118  | 12p | MEF103  | 35p   | 2N2846  | 70p   | OC29          | 50p   | <b>TRIACS</b> |       |
| BC119  | 22p | MJ480   | 75p   | 2N2894  | 35p   | OC35          | 48p   | SC40D         | £1.05 |
| BC134  | 12p | MJ481   | 95p   | 2N2904A | 45p   | OC36          | 50p   | SC45D         | £1.30 |
| BC136  | 16p | MJ490   | 85p   | 2N2905  | 22p   | OC71          | 30p   | SC45E         | £1.45 |
| BC137  | 16p | MJE371  | 60p   | 2N2906  | 14p   | OC83          | 25p   | SC50D         | £1.50 |
| BC138  | 16p | MJE2801 | £1.15 | 2N2906A | 16p   | OCP71         | 75p   |               |       |
| BC153  | 17p | MJE2955 | £1.00 | 2N2907A | 16p   | ZTX107        | 8p    | <b>I.C.s.</b> |       |
| BC154  | 17p | MJE3055 | 85p   | 2N2925  | 14p   |               |       | 741           | 30p   |
| BC167B | 12p | MFP102  | 30p   | 2N2926  | 9p    | <b>R.C.A.</b> |       | 1310          | £2.40 |
| BC183L | 19p | 2N697   | 14p   | 2N3053  | 18p   | 40309         | 30p   |               |       |

Many Radio & TV Spares in stock. Please ring.

# Everest Instruments Ltd.

34, Shakespeare St., Nottingham.  
Tel. (0602) 45466

All prices quoted include p. & p., & VAT, min. order, £1, CWO only. 12 x 10 SAE for full lists.

| Transformers  |            | P.C. Board              |                                 |
|---|------------|-------------------------|---------------------------------|
| All 240V 50Hz primaries                               |            | Single sided fibre 6-70 |                                 |
| Volts   | Amps       | £ p                     | glass 9c ft                     |
| 6-3   | 1-5        | 1-83                    | Double sided fibre 1-90         |
| 6-3   | 3-0        | 1-83                    | glass sq ft                     |
| 9-0   | 1-0        | 1-83                    | cut in multiples of 6" i.e.     |
| 12-0  | 0-5        | 1-83                    | 6 x 6, 6 x 12, 12 x 12, 12 x 18 |
| 12-0  | 1-5        | 2-09                    | etc.                            |
| 12-0  | 3-0        | 3-02                    | Circuit etchant 250ml 0-55      |
| 8-0-5   | 0-5        | 1-96                    | 1 lb ferric chloride 0-50       |
| 0-5-0   | 0-8        | 1-96                    | 250ml plastic bottles 0-16      |
| 8-0-9   | 1-0        | 2-09                    |                                 |
| 10-0-10   | 2-0        | 3-06                    |                                 |
| 12-0-12   | 2-0        | 2-23                    |                                 |
| 12-0-12   | 2-0        | 3-13                    |                                 |
| 12-0-12   | 3-0        | 4-32                    |                                 |
| 15-0-15   | 1-0        | 2-88                    |                                 |
| 18-0-18   | 2-0        | 4-32                    |                                 |
| 20-0-20   | 2-0        | 4-32                    |                                 |
| 30-0-30   | 1-0        | 4-32                    |                                 |
| 0-10-12-14-16-18                                      | 4-0        | 4-58                    |                                 |
| 0-12-15-20-24-30                                      | 2-0        | 6-45                    |                                 |
| 0-5-20-30-40-60                                       | 2-0        | 6-54                    |                                 |
| Battery charger transformers 6 & 12V                  |            |                         |                                 |
|   | 1-0        | 2-35                    |                                 |
|   | 2-0        | 3-27                    |                                 |
|   | 4-0        | 4-32                    |                                 |
| 240/110 autos   | 30 watts   | 2-88                    |                                 |
|   | 50 watts   | 3-66                    |                                 |
|   | 100 watts  | 5-23                    |                                 |
|   | 150 watts  | 6-33                    |                                 |
|   | 200 watts  | 8-36                    |                                 |
|   | 400 watts  | 13-14                   |                                 |
|   | 800 watts  | 15-54                   |                                 |
|   | 1000 watts | 23-67                   |                                 |
| Bulk tape eraser                                      |            |                         |                                 |
| 15-5-3 ohm 12 watt matching                           |            | 1-71                    |                                 |
| Transistor driver 4:1+1                               |            |                         |                                 |
|   |            | 6-27                    |                                 |
| Speakers  |            |                         |                                 |
| 3" Goodman tweeter 8 ohm 51CDA                        |            | 1-47                    |                                 |
| 3" Audax tweeter 8 ohm 6-5TWB18                       |            | 1-60                    |                                 |
| 5" Audax 8 ohm bass HIF13E8                           |            | 3-23                    |                                 |
| 6 1/2" EMI d/cone 8 ohm 10 watt                       |            | 3-59                    |                                 |
| 6 1/2" Audax 8 ohm 8" Celestion 8 ohm d/cone PS8 9858 |            | 2-76                    |                                 |
| 10 x 8 EMI 8 ohm midrange                             |            | 4-18                    |                                 |
| 10 x 6 EMI 8 ohm 20 watt                              |            | 7-36                    |                                 |
| 13 x 8 EMI 8 ohm 20 watt                              |            | 6-75                    |                                 |
| 13 x 8 EMI 8 ohm 25 watt                              |            | 7-84                    |                                 |

Electrolytics. Tubular with axial leads except where stated.

| Mfd.                    | Volts | Pence |
|-------------------------|-------|-------|
| 47                      | 4     | 7     |
| 330                     | 4     | 7     |
| 68                      | 6-3   | 7     |
| 470                     | 6-3   | 9     |
| 1000                    | 6     | 11    |
| 25                      | 10    | 7     |
| 47                      | 10    | 7     |
| 220                     | 10    | 7     |
| 330                     | 10    | 9     |
| 15                      | 16    | 7     |
| 33                      | 16    | 7     |
| 68                      | 16    | 9     |
| 220                     | 16    | 9     |
| 330                     | 16    | 12    |
| 1000                    | 16    | 15    |
| 10                      | 25    | 7     |
| 22                      | 25    | 7     |
| 47                      | 25    | 7     |
| 100                     | 25    | 7     |
| 150                     | 25    | 9     |
| 200                     | 25    | 11    |
| 1250                    | 25    | 24    |
| 5000                    | 25    | 55    |
| 1000+1000               | 30    | 32    |
| 2500                    | 30    | 40    |
|                         | 6-8   | 7     |
|                         | 16    | 7     |
|                         | 100   | 40    |
|                         | 1000  | 50    |
|                         | 1     | 63    |
|                         | 4-7   | 63    |
|                         | 10    | 63    |
|                         | 800   | 63    |
|                         | 2500  | 63    |
|                         | 4700  | 83    |
| Oddments to clear       |       |       |
| 50mfd @ 50V tubes       |       | 6     |
| 250mfd @ 60V cans       |       | 10    |
| 300mfd @ 10V p/c        |       | 5     |
| 60+250mfd @ 350V cans   |       | 30    |
| 0-03mfd @ 200V tantalum |       | 5     |

# TELEVISION CAMERA KITS

Complete kits are available for both "Mullard" and "P.E." design. Each kit includes a comprehensive construction manual, and a completely FREE technical back up service to ensure your success. VHF and UHF Modulator kits also available to allow standard domestic T.V. to be used as monitor.

All parts available separately, including a wide range of lenses, vidicon tubes and focus/scan coil assemblies. Ready built cameras also available. Complete kits available for P.W. tele-tennis game. Send 5" x 7" S.A.E. for full details, or come along for a demonstration and a chat with our technical staff.

## CROFTON ELECTRONICS

124 Colne Road, Twickenham, Middlesex, TW2 6QS

Telex: 01-898 1569

Telex 934642

Cadanac LDN



## 4-STATION INTERCOM




£16.15

Solve your communication problems with this 4-Station Transistor Intercom system (1 master and 3 Slaves), in robust plastic cabinets for desk or wall mounting. Call/talk/listen from Master to Slaves and Slaves to Master. Ideally suitable for Business, Surgery, Schools, Hospitals and Office. Operates on one 9V battery. On/off switch. Volume control. Complete with 3 connecting wires each 66ft. and other accessories. P. & P. 65p.

## MAINS INTERCOM NEW MODEL

No batteries—no wires. Just plug in the mains for instant two-way, loud and clear communication. On off switch and volume control. Price £25.91 per pair P. & P. 65p.
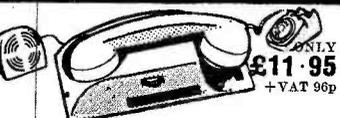
## NEW! AMERICAN TYPE CRADLE TELEPHONE AMPLIFIER



£11.95

+VAT 96p

Latest transistorised Telephone Amplifier with detached plug-in speaker. Placing the receiver on to the cradle activates a switch for immediate two-way conversation without holding the handset. Many people can listen at a time. Increase efficiency in office, shop, workshop. Perfect for "conference" calls! Leaves the user's hands free to make notes, consult files. No long waiting, saves time with long-distance calls. On/Off switch, volume. Direct tape recording model at £12.95 + VAT £1.04 P. & P. 65p. 10-day price refund guarantee.

WEST LONDON DIRECT SUPPLIES (FWS)  
169 KENSINGTON HIGH STREET, LONDON, W8

Wire Wound Resistors. Our selection of mixed values. 30 for £1.40, 100 for £3.50.

Audio Amplifier Module. Mullard LP1173, output power, nominal 10 watt, supply voltage +24 volt, with data and circuit, £2-30 + post.

Ferguson Stereogram chassis Model 3357, all transistor, medium long, VHF/FM. 3 watts per channel S/M. with connection data, less tuning scale, £18.00. Post paid.

Crystals HC6U: 52-03333 MHz: 52-02500: 52-01667: 51-56667: 51-58330: 37-76250: 37-75000: 12-895-8: 12-891-6: 12-700-0: 9-456-25: 9-455-55: 9-533-33: 9-531-94: 9-530-55: 9-090-62: 9-087-5 50p each.

Electrolytics. 32/32/μF, 325v. 2" x 1 1/4" 35p: 80μF 150v 1 1/4" x 1" 20p: 2000μF 30v, 2 1/4" x 1" 25p: 2000μF 35v 3" x 1" 30p: 470μF 100v 3" x 1 1/4" 25p: 2000/2000μF 25v 2" x 1 1/4" 35p: 700μF 200v 3 1/2" x 1 1/4" 30p: 16/16μF 275v 1 1/4" x 1" 20p: 40/40/20μF 275v 3" x 1" 20p: 900/900/900μF 30v 2 1/4" x 1 1/4" 50p: 2500μF 40v 2 1/4" x 1 1/4" 40p: 470μF 25v 1 1/4" x 1 1/4" 15p: 4,000μF 25v 3" x 1 1/4" 40p. 32μF 450v 1 1/4" x 1" 30p: 8μF/16μF 450v 1 1/4" x 2" 30p: 1000μF 12v 1 1/4" x 1 1/4" 15p. Try our parcel of small capacitors 20 mixed values £1.50 + post.

Matched pair of bookshelf speakers. Teak finish, size 12" x 8" x 5". 8 x 5 8" ohms ceramic, 5 watts RMS. Complete with din leads. £10.00 pair + post.

Thorn TV IF chassis, 950 series (less valves). £1.60 + post.

UHF 625 transistor push button tuner (NSF Telefunken) as used on Decca MS2400. Brand new and boxed, circuit diagram supplied £3.00 + post.

P.C. Boards (not computer panels) 1 off 6 transistor single wave band. 1 off 4 transistor audio. 1 off 3 transistor £1.40 + post, three boards.

Repanco Transformers AF1, AF2, TT45, 46, 47, 49, 53. 20p each + post. L/M. M/W. VHF Tuner 5 transistor in kit form, complete with full assembly instructions. 9vt supply, positive earth. O/p ut 100mw. Built-in A.M. aerial. 88-108 Mcs. £5.25 + post.

Stereo Decoder using MC1310. Fully assembled, can be used with our tuner kit. With data. £3.90 + post.

Mains Droppers, 10 mixed values, £1.00 + post.

Edgewise Level meters, 200μA, size 3 1/2" overall. 50p + post.

Chrome Plastic knobs, 3 types, 4 off each with spring clip. £1.25 + post.

Aluminium Chassis, 7 1/4" x 5 1/4" x 2 1/4" 65p + post: 10" x 7 1/4" x 2 1/4" 75p + post. 11" x 7 1/4" x 2 1/4" 85p + post.

BSR P128, similar to HT70 single play, with heavy die cast turntable, less cartridge, £10.00 + post.

Ferguson Stereogram Chassis. MW/LW/VHF with tuning scale (5+5 watts sine wave) 15 ohms £26.25. Post paid 15 ASSORTED SWITCHES £1.90 + post. 50—3 way to 7 way TAG STRIPS, £1.15 + post, ALMA REED RELAY TYPE DRH. 3 VOLTS 50p + post.

REPANCO & DENCO COILS, NEW/BOXED OUR SELECTION—5 FOR £1.15 + post.

Please add 10% post and packing. Add 25% VAT to total order. Gram Chassis free postage. No goods despatched outside U.K.

## SURPLECTRONICS

216 LEAGRAVE ROAD, LUTON, LU3 1JD, BEDS.

**Fully guaranteed  
Individually packed  
VALVES**

|          |       |        |       |        |       |           |       |
|----------|-------|--------|-------|--------|-------|-----------|-------|
| A1065    | 21-25 | ECL80  | 55p   | GZ34   | 70p   | PY81      | 40p   |
| ARS      | 55p   | ECL82  | 35p   | GZ37   | £1.08 | PY82      | 40p   |
| ATP4     | 50p   | ECL83  | 70p   | KT66   | £2.50 | PY83      | 40p   |
| R12H     | 23-09 | ECL86  | 50p   | KT68   | £2.20 | PY88      | 45p   |
| CY31     | 50p   | EF36   | 65p   | MH4    | 75p   | PY500     | £1.00 |
| D4F96    | 55p   | EF37A  |       | ML6    | 65p   | ACY 39    |       |
| DF96     | 55p   | EF38   | £1.20 | OC 42  | 65p   | ACY 40    |       |
| DK96     | 70p   | EF40   | 75p   | OB2    | 45p   | ACY 50    |       |
| DL92     | 40p   | EF41   | 85p   | PAB080 | 40p   | QY003-10  |       |
| DL96     | 60p   | EF80   | 30p   | PC97   | 50p   |           | £1.40 |
| DY86/87  |       | EF83   | £1.25 | PC90   | 50p   | QQV06-40A |       |
|          |       | EF85   | 35p   | PC84   | 40p   |           | £2.00 |
| DY802    | 45p   | EF86   | 35p   | PC85   | 40p   | E19       | 75p   |
| E88CC(1) |       | EF89   | 30p   | PC89   | 45p   | £3.00     |       |
| E180CC   | £1.20 | EF92   | 50p   | PC189  | 50p   |           |       |
| E182CC   |       | EF95   | 40p   | PCF80  | 40p   | SCL100    |       |
|          |       | EF188  | 35p   | PCF82  | 40p   | SP61      | £5.00 |
|          |       | EF184  | 35p   | PCF84  | 40p   | TT21      | £5.00 |
| EAS0     | 40p   | EFL200 | 75p   | PCF86  | 80p   | U26       | 85p   |
| EAB30    | 40p   | EL33   | £2.50 | PCF200 | 75p   | U25       | 75p   |
| EAF49    | 75p   | EL34   | 70p   | PCF301 | 75p   | U27       | 85p   |
| EB91     | 30p   | EL36   | 60p   | PCF801 | 45p   | U191      | 75p   |
| EBC83    | £1.00 | EL37   | £1.80 | PCF802 | 50p   | U801      | 75p   |
| EBC41    | 75p   | EL41   | 80p   | PCF805 | 90p   | UAB080    |       |
| EBF80    | 40p   | EL41   | 80p   | PCF806 | 75p   | UAF42     | 40p   |
| EBF83    | 50p   | EL42   | 55p   | PCF808 | 90p   | UAF44     | 40p   |
| EBF89    | 40p   | EL43   | 30p   | PCF200 | 80p   | UBC41     | 60p   |
| EC32     | 35p   | EL44   | 30p   | PCF809 | 40p   | UBF80     | 40p   |
| ECC81    | 40p   | EL45   | 60p   | PCF82  | 40p   | UBF80     | 40p   |
| ECC82    | 35p   | EL46   | 45p   | PCF83  | 65p   | UBL1      | 70p   |
| ECC83    | 35p   | EL49   | 45p   | PCF84  | 45p   | UCC85     | 50p   |
| ECC84    | 35p   | EL50   | 45p   | PCF86  | 50p   | UCF80     | 75p   |
| ECC85    | 40p   | EM1    | 60p   | PCF805 | 60p   | UCH42     | 75p   |
| ECC86    | 90p   | EM80   | 55p   | PCL806 | 60p   | UCH41     | 45p   |
| ECC88    | 50p   | EM84   | 40p   | PCL807 | 70p   | UCL82     | 45p   |
| ECC189   | 70p   | EM87   | £1.00 | PL180  | 50p   | UCL83     | 65p   |
| ECC80    | 40p   | EY51   | 45p   | PL82   | 45p   | UF41      | 70p   |
| ECC82    | 40p   | EY81   | 45p   | PL83   | 45p   | UF80      | 85p   |
| ECC83    | 40p   | EY88   | 40p   | PL84   | 45p   |           |       |
| ECC85    | 40p   | EZ40   | 70p   | PL804  | 80p   |           |       |
| ECH2     | £1.40 | EZ40   | 70p   | PL508  | £1.00 |           |       |
| ECH42    | 80p   | EZ41   | 75p   | PI-509 | £1.35 |           |       |
| ECH81    | 35p   | EZ80   | 30p   | PL802  | £1.25 |           |       |
| ECH83    | 45p   | EZ81   | 30p   | PY83   | 60p   |           |       |
| ECH84    | 45p   | GY501  | 75p   | PY80   | 40p   |           |       |

A lot of these valves are imported and prices vary for each delivery, so we reserve the right to change prices for new stock when unavoidable.

**TRANSISTORS, DIODES etc.**

|        |         |           |        |         |         |
|--------|---------|-----------|--------|---------|---------|
| AC 113 | AF 178  | BSY 86    | OAZ 22 | OC 206  | 2N 3054 |
| AC 126 | AF 186  | BSY 95A   | OC 22  | SK 754  | 2N 3055 |
| AC 127 | AFZ 12  | BYZ 76    | OC 25  | ZR 11   | 2N 3391 |
| AC 128 | ASV 26  | CRS 1/10  | OC 26  | ZR 21   | 2N 3730 |
| AC 176 | ASV 27  | CRS 1/20  | OC 28  | 1N 25A  | 2N 3819 |
| AC 178 | ASV 28  | CRS 1/30  | OC 29  | 1N 25B  | 2N 4058 |
| AC 19  | BC 108  | CRS 1/40  | OC 35  | 1N 32A  | 2N 4058 |
| AC 20  | BC 118  | CRS 1/10  | OC 36  | 1N 36A  | 2N 4061 |
| AC 29  | BC 119  | CRS 2/20  | OC 42  | 1N 43   | 2N 4785 |
| AC 38  | BC 136  | CRS 3/30  | OC 44  | 1N 70   | 2N 5295 |
| AC 40  | BC 137  | CRS 3/40  | OC 47  | 1N 275  | 3N 128  |
| AD 148 | BC 145A | CRS 25/25 | OC 78  | 1N 415G | 3N 154  |
| AD 161 | BC 172  | GET 115   | OC 78  | 1N 4148 | 3N 159  |
| AD 162 | BC 172A | GET 116   | OC 78  | 2N 456A | 28 305  |
| ADZ 11 | BC 212A | GEX 66    | OC 78D | 2N 708  | 404     |
| ADZ 12 | BCY 31  | NKT 222   | OC 81  | 2N 918  | 2082    |
| AF 114 | BCY 32  | OC 82     | OC 82  | 2N 1304 | 40250   |
| AF 115 | BCY 33  | OC 82M    | OC 82M | 2N 1306 | 40261   |
| AF 116 | BF 115  | OC 83     | OC 83  | 2N 1307 | 40317   |
| AF 117 | BF 167  | OC 83     | OC 83  | 2N 1309 | 40668   |
| AF 118 | BF 185  | OC 139    | OC 139 | 2N 2062 |         |
| AF 125 | BFY 51  | OC 140    | OC 140 | 2N 2147 |         |
| AF 126 | BFY 52  | OC 170    | OC 170 | 2N 2411 |         |
| AF 127 | BFY 90  | OC 172    | OC 172 | 2N 2989 |         |
| AF 138 | BSY 27  | OC 200    | OC 200 | 2N 3053 |         |

**Colomor** ALL valves guaranteed

|         |        |        |       |       |       |
|---------|--------|--------|-------|-------|-------|
| 68CTGT  | 40p    | 25LGT  | 70p   | 6064  | 60p   |
| 68G7    | 50p    | 30C17  | £1.00 | 6065  | £1.00 |
| 68J7    | 55p    | 30C17  | £1.00 | 6067  | 70p   |
| 68J7GT  | 55p    | 30C18  | 90p   | 6080  | £2.20 |
| 68K7    | 55p    | 30F9   | £1.00 | 6146  | £2.35 |
| 68LGT   | 55p    | 30P11  | £1.00 | 6146B | £2.35 |
| 68N7GT  | 50p    | 30PL12 |       | 8020  | £2.00 |
| 68Q7    | 55p    |        |       | 9001  | £5.00 |
| 6V6GT   | 50p    | 30PL14 | 90p   | 9002  | 50p   |
| 6X4     | 40p    | 30L16  | 85p   | 9003  | 70p   |
| 6X5GT   | 40p    | 30L17  | 85p   | 9004  | 35p   |
| 6Y8G    | 50p    | 30F12  | £1.00 | 9006  | 35p   |
| 6Z4     | 85p    | 30FL1  | 85p   |       |       |
| 6-30L2  | 90p    | 30FL13 |       |       |       |
| 7B7     | 80p    |        | £1.10 |       |       |
| 7Y4     | 80p    | 30P14  | £1.10 |       |       |
| 93F6    | 40p    | 35L6GT | 75p   |       |       |
| 11E2    | £6.00  | 35V4   | 50p   |       |       |
| 12A6    | 55p    | 35Z4GT | 70p   |       |       |
| 12AT6   | 45p    | 50C5   | 60p   |       |       |
| 12AT7   | 40p    | 50CDB  |       |       |       |
| 12AT7   | 35p    |        | £1.10 |       |       |
| 12AV6   | 50p    |        | £1.00 |       |       |
| 12AX7   | 35p    | 75C1   | 75p   |       |       |
| 12BA6   | 45p    |        | 75p   |       |       |
| 12BE6   | 50p    |        | 78p   |       |       |
| 12BH7   | 50p    |        | 75p   |       |       |
| 12C8    | 55p    | 85A2   | 75p   |       |       |
| 12E1    | £3.50  | 723A/b | £2.00 |       |       |
| 12K5    | £1.10  | 808    | £2.00 |       |       |
| 12KGT   | £2.00  | 805    | £1.00 |       |       |
| 12KSGT  | 70p    | 807    | 85p   |       |       |
| 12Q7GT  | 70p    | 813    | 25p   |       |       |
| 12SA7GT |        | 866A   | £1.20 |       |       |
|         |        | 931A   | £2.00 |       |       |
| 128G7   | 55p    | 954    | 60p   |       |       |
| 12S7    | 55p    | 955    | 60p   |       |       |
| 12Y4    | 40p    | 966    | 50p   |       |       |
| 14S7    | £1.00  | 957    | 80p   |       |       |
| 19AQ5   | 65p    | 1305   | 80p   |       |       |
| 19G3    | 88p    | 1629   | 70p   |       |       |
| 19G6    | £2.60  | 2051   | £1.00 |       |       |
| 19H5    | £14.00 | 5838   | £2.00 |       |       |
| 20F9    | 60p    | 6957   | 75p   |       |       |
| 20T4    | £1.10  | 6960   | 70p   |       |       |

C.R. Tubes  
DG7-5  
DG13-2  
MW13-85  
MW15-85  
VCR139A

**V.A.T.**  
Please add 25% to all orders

|       |       |        |       |
|-------|-------|--------|-------|
| 6B6G  | 90p   | 6H6    | 85p   |
| 6B7G  | 65p   | 6J4WA  |       |
| 6BQ7A | 60p   |        | £1.25 |
| 6BR7  | £1.20 | 6J5    | 65p   |
| 6BW6  | £1.00 | 6J9T   | 50p   |
| 6C4   | 40p   | 6J6    | 30p   |
| 6C5   | 50p   | 6J7    | 50p   |
| 6C6   | 50p   | 6J7G   | 40p   |
| 6C6B  | 50p   | 6K6GT  | 80p   |
| 6C6E  | £1.45 | 6K7    | 55p   |
| 6C6L  | 75p   | 6K7GT  | 50p   |
| 6D6   | 55p   | 6L6GT  | 60p   |
| 6EAS  | 85p   | 6R25   | £1.00 |
| 6F7   | £1.10 | 6L8    | 90p   |
| 6F8G  | 75p   | 6L6C   | 60p   |
| 6F23  | 90p   | 6L7G   | 40p   |
| 6F32  | 75p   | 6S7A   | 50p   |
| 6F33  | £2.60 | 6SA7GT | 40p   |

MINIMUM POSTAL ORDER £1. PERSONAL CALLERS WELCOME.  
MANY OTHERS IN STOCK include Cathode Ray Tubes and Special Valves, U.K.  
UK Postage £1-22 17p, £2-22 30p, £3-24 40p, Over £5 free. C.O.D. 50p extra.

29/41FT. AERIALS each consisting of ten 3ft., 1/4in. dia. tubular screw-in sections, 11ft. (6-section) whip aerial with adaptor to fit the 7in. rod, insul'd base, stay plate and stay assemblies, pegs, reamer, hammer, etc. Absolutely brand new and complete ready to erect, in canvas bag. £7-50 new. Carriage £1-50.

**Colomor (Electronics) Ltd.**  
170 GOLDHAWK ROAD, LONDON W12.  
Open 9-12.30, 1.30-5.30 p.m. Thursday 9-1 p.m.

**TOROIDAL TRANSFORMERS FOR THE TEXAN II**

Designed by S.I.G.A. ELECTRONICS in conjunction with Texas Instruments for uprating Texan 20+20 Amplifiers. Pri. 220-240V; 50Hz; Screen; Sec. 25-20-0-20-25V, 1-5A. Fully impregnated; flying lead connections.

Ref. T1295 Price £6-70 + 25% VAT post 50p.  
Ref. T1295/F with resin filled centre, 2BA clear hole. Price £7-10 + 25% VAT post 50p.

Toroidal transformers suitable for Audio Power Supplies Pri. 240V 50Hz; Screen; fully impregnated; flying leads

| REF | SECONDARIES       | O.D. (cms) | HT. | Price  | Post  |
|-----|-------------------|------------|-----|--------|-------|
| 315 | (a) 33-0-33V 2A   | 12-0       | 4-4 | £8-50  | £0-89 |
|     | (b) 25-0-25V 0-1A |            |     |        |       |
| 291 | (a) 33-0-33V 4A   | 13-0       | 5-7 | £10-69 | £0-78 |
|     | (b) 25-0-25V 0-2A |            |     |        |       |
| 271 | 24-0-24V 1A       | 8-6        | 4-1 | £5-07  | £0-50 |
| 061 | 20-0-20V 1A       | 8-5        | 4-0 | £4-87  | £0-50 |
| 285 | 25-0-25V 2A       | 10-8       | 5-1 | £6-37  | £0-60 |
| 284 | 0-45V 1A          | 9-5        | 4-4 | £5-15  | £0-60 |
| 000 | 0-45V 2A          | 12-0       | 4-4 | £6-64  | £0-69 |

Terms: Cash with order, please add 25% VAT to goods only. Quantity discounts available on request.

Dept. PW 02  
**S.I.G.A. (ELECTRONICS) LIMITED**  
Sunderland Road, Sandy, Beds  
SG19 1QY

**RELAY UNIT**  
Smart steel case 12 x 7 x 4 1/2" with 22 PO Type relays, most with at least 3 sets c/o contacts; 4 reed relays+coils, 2 pots, resistors, capacitors, 12BH valve, various diodes, tag board etc. Only £3-50

**PC ETCHING KIT MK II**  
Contains 1lb Ferric Chloride, 100 sq ins copper clad board, DALO etch resist pen, abrasive cleaner etching dish and instructions. Now also includes 2 miniature drill bits. £3-50

**FERRIC CHLORIDE**  
Anhydrous technical quality in 1lb double sealed pack. 1lb 89p; 3lb £1-80; 10lb £4-65; 100lb £25.

**COMPUTER PANELS**  
Large quantity always available. 3lb asstd £1-80; 7lb £2-85; 56lb £15. Pack with about 500 components inc. at least 50 transistors £1.

**7lb BARGAIN PARCELS**  
Hundreds of new components—pots, resistors, capacitors, switches, + PC boards with transistors and diodes also loads of odds and ends. Contents always changing. Only £3-00.

**POWER SUPPLY UNIT**  
G101: Mains transformer, 2A thermal cut-out, bridge rect., will give 1-7-10-5V output with 2 extra capacitors provided. With data, only £1-30

**TRANSFORMERS**  
All mains primaries. 6-0-6V @ 100mA 99p; 9-0-9V 100mA £1-92; 12-0-12V 100mA £1-08; 24-0-24V 50mA £2-20; 1A multitapped to give 3, 4, 5, 6, 8, 9, 10, 12, 15, 18, 20, 24 or 30V, also 12-0-12 or 15-0-15 £3-00. 2A version £4-40. 6-5-0-6-5V 50mA £1-45; 17V 1A £2; 9V 10A £3-00; sub-miniature 12-0-12V @ 50mA 80p.

**UK POSTAGE**  
All prices include UK postage VAT @ 8% or 25% as appropriate. SAE list, enquiries. Surplus components wanted for cash.

**GREENWELD (PW8)**  
51 Shirley Park Road, Southampton, SO1 4FX.  
Tel: (0783) 772501.  
Also callers welcome at 21 Deptford Bdy SE8 01-692 2009, & 38 Lower Addiscombe Rd, Croydon 01-688 2950

**BARGAIN PACKS**  
12 BC107 £1-20 25 1N4001 £1-20  
12 BC108 £1-20 22 1N4002 £1-20  
12 BC109 £1-20 20 1N4003 £1-20  
15 BC148 £1-20 18 1N4004 £1-20  
12 BC149 £1-20 10 1N4005 £1-20  
12 BC151 £1-20 14 1N4006 £1-20  
12 BC158 £1-20 12 1N4007 £1-20  
12 BC159 £1-20 40 1N4148 £1-20  
2 2N2646 £1-20 3 2N3055 £1-20  
10 BC326 £1-20 12 BC548 £1-20  
12 BF194 £1-20 12 BF195 £1-20  
7 BF173 £1-20 5 BF181 £1-20  
All full spec marked components.

**5 PIN DIL 741's**  
10+30p; 25+25p; 100+24p; 250+23p

**555 TIMERS**  
3+ 60p; 10+ 50p; 25+ 46p; 100+ 43p

**RESISTORS AND CAPACITORS**  
400 asstd carbon resistors £1-49  
250 Hi-stabs 1, 2, 5, 1, 1W £1-35  
100 Wirewounds, 2W to 15W £2-00  
200 ceramic, mica etc caps £1-10  
100 C230 polyesters, .01-.47 £1-30  
200 min electrolytics, but mainly unmarked, so only £1-35.  
15 alspaced & compression trimmers up to 1250F £1-10.  
JUMBO PACK—1 each of the above, £9-60 value for only £7-50!!!

**VEROBAND**  
100 sq ins, about 8 places asstd sizes and pitches £1-15

**MISCELLANEOUS**  
9 pole 6 way Yaxley switches 55p;  
SPCO microswitch, 5A 12p; 15 asstd pots 75p; plug in relay, 25000C2 c/o 25p; 4 x 80V 10A rect on heat sink, 100mA charge. SW7600N £1.  
Good range choice tolerance resistors—SAE list 96KHz crystal £1.

**PUSH BUTTON BANK**  
8 interlocking buttons, each 4 pole changeover, only 4 x 2 1/2" x 1". £1.

**TRANSISTOR PACKS**  
Large quantity of mainly unmarked out of spec. transistors just arrived. Sample tests show 75% OK. Sold in mixed packs with PNP, NPN, RF, AF, plastic, metal can, small signal and power devices. At least 200 for £1-50; 500 for £2-50; 1000 for £6-00. Out-of-spec 2N3055's 8 for £1-10. 25 untested BFY51 type transistors £1-10. 25 untested BC108 £1; 100 £3-00.

**ENGINEERS**

**FREE**

**YOURSELF FOR A BETTER JOB WITH MORE PAY!**



Do you want promotion, a better job, higher pay? "New opportunities" shows you how to get them through a low-cost, Home Study Course. There are no books to buy and you can pay as you learn.

This easy to follow GUIDE TO SUCCESS should be read by every ambitious engineer. Send for this helpful 76-page free book NOW! No obligation, nobody will call on you. It could be the best thing you ever did.

**CHOOSE A BRAND NEW FUTURE HERE**

**CUT OUT THIS COUPON**

Tick or state subject of interest. Post to address below.

- |   |   |   |
|---|---|---|
| <input type="checkbox"/> <b>ELECTRICAL ENGINEERING</b><br>City & Guilds Wiring and Installations<br><input type="checkbox"/> C. G. Electrical Tech-Primary<br><input type="checkbox"/> Gen. Electrical Eng.   | <input type="checkbox"/> <b>RADIO &amp; TV</b><br>Gen. Radio and TV Eng.<br><input type="checkbox"/> Radio Servicing, Maintenance and Repairs<br><input type="checkbox"/> Practical Radio & Electronics (with self-build kit)<br><input type="checkbox"/> Radio Amateurs' Exam  | <input type="checkbox"/> <b>DRAUGHTSMANSHIP</b><br>Institute of Engineering Draughtsmen & Designers<br><input type="checkbox"/> General Draughtsmanship<br><input type="checkbox"/> Architectural Draughtsmanship<br><input type="checkbox"/> Technical Drawing   |
| <input type="checkbox"/> <b>AERONAUTICAL ENGINEERING</b><br>Air Registration Board Certificates<br><input type="checkbox"/> Gen. Aero Engineering   | <input type="checkbox"/> <b>ELECTRONIC ENGINEERING</b><br>Gen. Electronic Eng.<br><input type="checkbox"/> Practical Electronics (with kit)   | <input type="checkbox"/> <b>CONSTRUCTION &amp; BUILDING</b><br>Institute of Building<br><input type="checkbox"/> Construction Surveyor's Inst.<br><input type="checkbox"/> Clerk of Works Diploma<br><input type="checkbox"/> C. & G. Building Quantities<br><input type="checkbox"/> General Building<br><input type="checkbox"/> General Civil Eng.<br><input type="checkbox"/> Heating, Ventilation & Air Conditioning<br><input type="checkbox"/> Carpentry & Joinery |
| <input type="checkbox"/> <b>AUTO ENGINEERING</b><br>City & Guilds Auto Engineering Practice<br><input type="checkbox"/> Inst. Motor Industry<br><input type="checkbox"/> M.A.A./I.M.I. Management Diploma<br><input type="checkbox"/> Gen. Auto Engineering<br><input type="checkbox"/> Auto Diesel Maintenance<br><input type="checkbox"/> Motor Mechanics<br><input type="checkbox"/> Service Station and Garage Management | <input type="checkbox"/> <b>AGRICULTURAL ENGINEERING</b>  | <input type="checkbox"/> <b>REFRIGERATOR SERVICING</b>  |
| <input type="checkbox"/> <b>TELECOMMUNICATIONS</b><br>City & Guilds Telecommunications  | <input type="checkbox"/> <b>MECHANICAL ENGINEERING</b><br>Society of Engineers<br><input type="checkbox"/> Inst. Engineers and Technicians<br><input type="checkbox"/> General Mechanical Eng.<br><input type="checkbox"/> Welding<br><input type="checkbox"/> Maintenance Eng.<br><input type="checkbox"/> General Diesel Eng. | <input type="checkbox"/> <b>PAINTING &amp; DECORATING</b><br><input type="checkbox"/> Plumbers<br><input type="checkbox"/> C.E.I. (Part 1)<br><input type="checkbox"/> Inst. Cost & Management<br><input type="checkbox"/> Accountants<br><input type="checkbox"/> Works Management etc. etc.   |



**G.C.E.**  
—58 'O' & 'A' Level Subjects  
—over 10,000 Group Passes!

**Aldermaston College**

Dept. TPW08, Reading RG7 4PF.

also at our London Advisory Office, 4 Fore Street Avenue, Moorgate, London EC2Y 5EJ. Tel. 01-628 2721.

NAME (Block Capitals) .....

ADDRESS .....


Postcode.....

Other subjects of interest..... Age.....

Accredited by C.A.C.C. Member of A.B.C.C.

**HOME OF BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY**

**BIG Discounts**

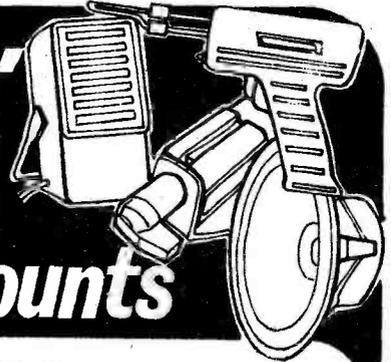

|                               |      |                                |       |
|-------------------------------|------|--------------------------------|-------|
| <b>SPEAKER BARGAINS</b>       | £    |                                | £     |
| P. & P. 40p per speaker       |      |                                |       |
| EMI 13" x 8" 3 or 8 ohm Plain | 2-20 | ELAC 6 1/2" 8 ohm Dualcone ..  | 2-25  |
| With Co-Axial Tweeter         |      | ELAC 8" 8 ohm Dualcone ..      | 2-50  |
| 8 ohms only ..                | 2-30 | ELAC 10" 8 ohm Dualcone        | 3-50  |
| Tweeter & Crossover 3, 8      |      | 10 watt ..                     |       |
| or 15 ohm ..                  | 3-95 | ADASTRA 10" 8 or 15 ohm,       | 3-55  |
| Type 350 8 or 15 ohm, 20 watt | 7-95 | 10 watt ..                     |       |
| 6 1/2" 8 ohm, 10 watt         | 2-60 | BAKER GROUP 25 12" 8 or        | 11-60 |
| 8" 8 ohm, 10 watt             | 4-50 | 15 ohm, 25 watt ..             |       |
| 8" x 5" C/Mag. 3, 8 or        |      | Following speakers 15p P. & P. |       |
| 15 ohm 5 watt                 | 1-40 | 2 1/2" 8 ohm or 64 ohm ..      | .55   |
| 8" x 5" Dualcone              |      | 5" 8 ohm, c/mag. ..            | .85   |
| 8 ohm, 10 watt                | 2-55 | 7" x 4" 3 or 8 ohm ..          | 1-20  |

|                                |      |                          |      |
|--------------------------------|------|--------------------------|------|
| <b>TWEETER &amp; CROSSOVER</b> |      |                          |      |
| Cone Tweeter 8 or 15 ohm,      |      | Crossovers CN29 (3 ohm), |      |
| 10 watt ..                     | 2-80 | CN28 (8 ohm), CN216 (16  |      |
| Cone Tweeter 8 ohm, 3 watt     | 1-45 | ohm) ..                  | 1-30 |
| Horn Tweeter 8 ohm, 20 watt    | 6-40 | P. & P. ..               | .15  |
| Dome Tweeter 8 ohm, 30 watt    | 5-60 |                          |      |

|                                      |      |                                 |      |
|--------------------------------------|------|---------------------------------|------|
| <b>KIT FORM CABINETS TEAK VENEER</b> |      |                                 |      |
| 12 x 12 x 6 with 8" 8" x 5" or       |      | 18 x 11 x 7 1/2 with 8" x 3" or |      |
| 6 1/2" and 3 1/2" cut out ..         | 4-00 | 13" x 8 1/2" cutout for EMI 350 | 6-00 |
| 17 x 10 x 7 1/2 with 8" or 13" x 8"  |      | P. & P. ea. ..                  | .50  |
| cutout ..                            | 6-00 |                                 |      |

|                            |      |                             |      |
|----------------------------|------|-----------------------------|------|
| <b>MICROPHONES</b>         |      |                             |      |
| CM70 Planet stick metal,   |      | TW209 ..                    | 5-75 |
| switch crystal ..          | 1-55 | CONDENSER MIKE 600 ohm,     | 9-35 |
| DM160 Dynamic omni-dir.    |      | uni-dir                     |      |
| ball metal ..              | 4-90 | Cassette Stick Mike with R. |      |
| UD130 50K/600 ohm, uni-dir |      | Control on/off switch       |      |
| ball metal ..              | 6-40 | (2-5 & 3-5mm J/Ply)         | 1-50 |
|                            |      | P. & P. ..                  | .30  |

|                        |      |                  |      |
|------------------------|------|------------------|------|
| <b>SOLDERING IRONS</b> |      |                  |      |
| ANTEX CN240 15 watt .. | 2-10 | X25 25 watt (low |      |
| SK 1 Kit (15 watt iron |      | leakage) ..      | 2-10 |
| 2 spare Bib etc.) ..   | 3-40 | P. & P. ..       | .15  |

|                                |      |                                |      |
|--------------------------------|------|--------------------------------|------|
| <b>CARTRIDGES &amp; STYLII</b> |      | <b>SONOTONE</b>                |      |
| ACOS GP91/2SC or 3SC ster.     | 1-00 | 9TAHC or 9TAHC/G Diam. 2-00    |      |
| comp. ..                       |      | 3509 Ster. ceram. Diam. ..     | 2-00 |
| GP93/1 or 95/1 ster.           |      | GOLDRING G850 ..               | 3-25 |
| cryst. ..                      | 1-50 | G800 ..                        | 4-10 |
| GP94/1 or 96/1 ster.           |      | G800E ..                       | 7-10 |
| ceram. ..                      | 1-85 | P. & P. ..                     | .15  |
| GP101 cryst. comp. ..          | 0-80 | D. Diamond Stylil for above .. | 1-25 |
| GP104 ster. ceram. ..          | 1-95 | G800/G850 ..                   | 1-95 |
| BSR X9M or X5H cryst. comp.    | 1-80 | G800E ..                       | 4-10 |
| SX6M or SX6H cryst.            |      | P. & P. ..                     | .05  |
| comp. ..                       | 2-00 |                                |      |
| SC5M ster. ceram. ..           | 2-75 |                                |      |

|                             |       |                  |       |
|-----------------------------|-------|------------------|-------|
| <b>CALCULATORS SINCLAIR</b> |       |                  |       |
| Cambridge ..                | 12-95 | Scientific ..    | 19-95 |
| Cambridge with memory       | 17-95 | V.A.T. inclusive |       |

|                            |      |                                      |      |
|----------------------------|------|--------------------------------------|------|
| <b>BATTERY ELIMINATORS</b> |      |                                      |      |
| 240v Input 6, 7-5 or 9     | 2-95 | 12v input, 6, 7 1/2, 9 output, 1 amp | 4-25 |
|                            |      | P. & P. ..                           | .15  |

|              |       |       |  |
|--------------|-------|-------|--|
| <b>TAPES</b> |       |       |  |
| 5" LP        | 65p   | 1-00p |  |
| 5 1/2" 80p   | 1-40p | 1-80p |  |
| 7" 80p       | 1-10p | 1-30p |  |

|                                       |     |
|---------------------------------------|-----|
| <b>PLASTIC LIBRARY CASES</b>          |     |
| For 5" Reels ..                       | 18p |
| 5 1/2" Reels ..                       | 22p |
| 7" Reels ..                           | 25p |
| P. & P. 1-3, 9p ea. 4 or more lot 35p |     |

|                                   |     |     |     |
|-----------------------------------|-----|-----|-----|
| <b>LOW NOISE CASSETTES</b>        |     |     |     |
| C60                               | 35p | 33p | 30p |
| C90                               | 45p | 43p | 40p |
| C120                              | 55p | 52p | 50p |
| Cassette Cases                    |     |     | 10p |
| Cassette Head Cleaner             |     |     | 40p |
| P. & P. 1-5, 5p ea. 6-10, 20p lot |     |     |     |
| 11-20, Post Free.                 |     |     |     |

|                                |      |  |  |
|--------------------------------|------|--|--|
| <b>BIB ACCESSORIES</b>         |      |  |  |
| Tape Editing Kit Ref. 23       | 1-35 |  |  |
| Recording Tape                 |      |  |  |
| Splicer .. Ref. 20             | 1-15 |  |  |
| Cassette Tape, editing Ref. 24 | 1-50 |  |  |
| Cassette Salvage Kit Ref. 29   | .45  |  |  |
| Stylus Balance Ref. 32A        | 1-20 |  |  |
| Spirit Level .. Ref. 46        | .50  |  |  |
| Hi-Fi Stereo Test Cassette     | 2-10 |  |  |
| Groove-Kleen Record Cleaner    | 1-90 |  |  |
| P. & P. ..                     | .15p |  |  |

|                                    |       |      |
|------------------------------------|-------|------|
| <b>WHARFEDALE SPEAKER BARGAINS</b> | £     | P&P  |
| Linton 2 Kit (pr)                  | 19-95 | 1-50 |
| Glendale 3 Kit (pr)                | 33-50 | 2-00 |
| Dovedale 3 Kit (pr)                | 52-00 | 2-00 |
| Denton 2 Speaker (pr)              | 30-00 | 2-50 |
| Linton 2 Speaker (pr)              | 39-50 | 2-50 |
| Dovedale 3 Speaker                 |       |      |
| (each) ..                          | 42-00 | 2-50 |
| Glendale 3 Speaker (pr)            | 57-00 | 3-50 |
| Kingsdale 3 Speaker                |       |      |
| (each) ..                          | 59-95 | 4-00 |

Send 25p for COMPLETE CATALOGUE, refundable upon first order. ALL OUR MERCHANDISE IS FULLY GUARANTEED. Subject to manufacturer increase and availability. PLEASE ADD V.A.T. AT 25% UNLESS OTHERWISE STATED

**Riversdale Electronics**

Mail Order Department **PWB**

P.O. Box 470, Manchester M60 4BU.

# Practical Wireless Classified Advertisements

The pre-paid rate for classified advertisements is 12p per word (minimum 12 words), box number 30p extra. Semi-displayed setting £10.00 per single column inch. All cheques, postal orders, etc., to be made payable to PRACTICAL WIRELESS and crossed "Lloyds Bank Ltd." Treasury notes should always be sent registered post. Advertisements, together with remittance, should be sent to the Classified Advertisement Manager, PRACTICAL WIRELESS, IPC Magazines Ltd. Fleetway House, Farrington Street, London, EC4A 4AD for insertion in the next available issue. (01-634 4451).

## Receivers and Components

### BETA DEVICES MANUFACTURERS BRANDED PRODUCTS

| TRANSISTORS      | DIODES & RECT.   | BRIDGE RECT.     |
|------------------|------------------|------------------|
| AC187/8 PR 0-40  | IN914 0-04       | 1A 100V W010-20  |
| BC107/8/9 0-09   | IN4148 0-04      | 1A 200V W020-22  |
| BC109C 0-11      | BY127 0-14       | 1A 200V W060-30  |
| BC147/8 0-10     | IN4001/2 0-05    | 25A 200V £2-00   |
| BCY70/71/72/0-13 | IN4003/4/5 0-08  | ZENERS           |
| BFX88 0-20       | IN4006/7 0-08    | BZY88c 3-3-      |
| BFY50 0-18       | IN5401 0-11      | 33V 5% 0-09      |
| BFY51/52 0-12    |                  | 1 watt 6-8-      |
| 2N1132 0-25      | 555 Timer 0-50   | 200V 5% 0-15     |
| 2N1711 0-25      | 556 Dual Tr 1-00 | L.E.D.           |
| 2N2646 0-30      | TBA500 1-50      | 209-RED 0-17     |
| 2N2905A 0-21     | TBA810 1-60      | LED CLIP 0-02    |
| 2N3053 0-14      |                  | OP. AMP. IC's    |
| 2N3055 0-38      | D.I.L. SOCKETS   | 709C T099 0-30   |
| OC28 0-45        | 8 Pin 0-12       | 709C D.I.L. 0-30 |
| OC35 0-35        | 14 Pin 0-12      | 741C T099 0-36   |
| TIP29A 0-49      | 16 Pin 0-14      | 741C D.I.L. 0-36 |
| TIP31A 0-61      |                  | 723C D.I.L. 0-30 |
| TIP41A 0-74      |                  | 747C D.I.L. 0-35 |
| TIP42A 0-90      |                  | 748C D.I.L. 0-36 |
|                  | ADD 17% V.A.T.   |                  |
| 7400N 0-16       | 74 SERIES TTL    | 74121N 0-50      |
| 7404N 0-18       | 7447N            | 74123N 1-26      |
| 7410N 0-18       | 7474N            | 74141N 1-13      |

ALUMINIUM ELECTROLYTIC CAPACITORS  
10µF 22µF 47µF 100µF 220µF 470µF 1,000µF  
16V 0-07 0-07 0-07 0-10 0-12 0-14 0-22  
25V 0-07 0-07 0-08 0-10 0-13 0-16 0-26

C.W.O. PLUS P.P. 15p TO BETA DEVICES, 4, Highbridge Street, Waltham Abbey, Essex.

COMPONENTS GALORE. Pack of 500 mixed components manufacturers surplus plus once used. Pack includes resistors, carbon and W.W., capacitors various, transistors, diodes, trimmers, potentiometers etc. Send £1+10p p&p. C.W.O. To: Caledonian Components, P.O. Box 3, Glenrothes, Fife.

### NEW MODEL V.H.F. KIT MK2

Our latest kit. Improved design and performance plus extra amplifier stage, receives aircraft, amateurs, mobile, radio 2, 3, 4, etc., this novel little set will give you endless hours of pleasure and can be built in one evening. Powered by 9 volt battery, complete with easy to follow instruction and built in jack socket for use with earphones or amplifier.

Only £4.50 + p&p 30p U.K. only.

Illustrated catalogue of selected kits and components, 35p inc. VAT. P&P free.

ALL PRICES PLUS 25% VAT  
Galleon Trading Co.  
12, Burra Way,  
Corringham,  
Stanford-Le-Hope,  
Essex. SS17 9DE

COMMUNICATIONS RECEIVER modules. Small superhet circuit boards requiring only controls and tuned circuits. 9 volt. Mosfet mixer, IC IF, BFO, Prod. Det. Excellent AM/CW/SSB results reported by delighted users. From £11.50. SAE details. PR Goldedge Electronics, Millend, Stonehouse, Glos.

### ELECTROLYTICS 6½p DESPATCH BY RETURN.

2,2µF, 4,7µF - 63V. 10µF, 22µF, 47µF, 100µF - 25V.  
ALL 6.5P (Inc. Vat) + 10P p&p  
Discount: 10% on totals over  
£3, 15% over £6. C.W.O.  
BUG SOUND ELECTRONICS, THE SHOP  
BLACKMORE END, BRAINTREE, ESSEX

## Precision Polycarbonate Capacitors

All High Stability - Extremely Low Leakage

| 440V AO (±10%)     | 50p   | 63V Range | ±1%   | ±2%   | ±5%   |
|--------------------|-------|-----------|-------|-------|-------|
| 0.1µF (1½" x 1½")  | 50p   | 0.47µF    | 50p   | 45p   | 35p   |
| 0.22µF (1½" x 1½") | 50p   | 1.0µF     | 60p   | 50p   | 40p   |
| 0.25µF (1½" x 1½") | 62p   | 2.2µF     | 80p   | 65p   | 55p   |
| 0.47µF (1½" x 1½") | 71p   | 4.7µF     | £1.80 | £1.05 | 85p   |
| 0.5µF (1½" x 1½")  | 75p   | 6.8µF     | £1.84 | £1.20 | £1.00 |
| 0.68µF (2" x 1½")  | 80p   | 10.0µF    | £2.00 | £1.60 | £1.40 |
| 1.0µF (2" x 1½")   | 91p   | 15.0µF    | £2.75 | £2.15 | £1.90 |
| 2.0µF (2" x 1½")   | £1.22 |           |       |       |       |

TANTALUM BEAD CAPACITORS—Values available: 0.1, 0.22, 0.47, 1.0, 2.2, 4.7, 6.8µF at 16V/25V or 35V; 10.0µF at 16V/20V or 25V; 22.0µF at 6V/10V or 16V; 33.0µF at 6V or 10V; 47.0µF at 3V or 6V; 100.0µF at 3V. ATL at 10p each, 10 for 95p. 60 for 54.

| TRANSISTORS:   | BC183/183L 11p | BFY50 20p  |
|----------------|----------------|------------|
| BC107/8/9 8p   | BC184/184L 12p | BFY51 20p  |
| BC114 13p      | BC212/212L 14p | BFY52 20p  |
| BC147/8/9 10p  | BC547/558A 12p | AF178 30p  |
| BC153/7/8 12p  | BF194 12p      | OC71 12p   |
| BC182/182L 11p | BF197 18p      | 2N3055 50p |

POPULAR DIODES—1N914 5p, 8 for 45p, 18 for 90p; 1N916 8p, 6 for 45p, 14 for 90p; 1844 5p, 11 for 50p, 24 for £1.00, 1N4148 5p, 6 for 27p, 12 for 45p; 1N4001 5p; 002 6p; 003 8p; 004 7p; 005 7p; 006 8p; 007 8p. LOW PRICE ZENER DIODES—400mW, Tol. ±5% at 5mA. Values available: 3V, 3.3V, 3.6V, 4.7V, 5.1V, 5.6V, 6.2V, 6.8V, 7.5V, 8.2V, 9.1V, 10V, 11V, 12V, 18V, 13.6V, 15V, 16V, 18V, 20V, 22V, 24V, 27V, 30V, 33V. All at 7p each, 6 for 30p, 14 for 84p. SPECIAL OFFER: 100 Zeners for £5.60.

RESISTORS—High stability, low noise carbon film 5%, ¼W at 40°C, ½W at 70°C. E12 series only—from 2.2Ω to 2.2MΩ. ALL at 1p each, 8p for 10 of any one value, 70p for 100 of any one value. SPECIAL PACK: 10 of each value 2.2Ω to 2.2MΩ (730 resistors) £5.

SILICON PLASTIC RECTIFIERS—1.5 amp, brand new wirewound D027: 100 P.I.V. 7p (4 for 26p); 400 P.I.V. 8p (4 for 30p).

BRIDGE RECTIFIERS—2½ amp: 200V 40p; 350V 45p; 600V 55p.

SUBMINIATURE VERTICAL PRESETS—0.1W only: ATL at 5p each; 50Ω, 100Ω, 220Ω, 470Ω, 680Ω, 1kΩ, 2.2kΩ, 4.7kΩ, 6.8kΩ, 10kΩ, 15kΩ, 22kΩ, 47kΩ, 100kΩ, 250kΩ, 880kΩ, 1MΩ, 2.5MΩ, 5MΩ.

PLEASE ADD 15p POST AND PACKING ON ALL ORDERS BELOW £5. ALL EXPORT ORDERS ADD COST OF SEA/AIRMAIL.

PLEASE ADD 25% V.A.T. TO ORDERS. Send S.A.E. for lists of additional ex-stock items. Wholesale price lists available to bona fide companies.

MARCO TRADING (Dept. W8),  
The Old School, Edgerton, Nr. Wem, Shropshire.  
Tel: Whical 464/465 (STD 094 872)  
(Propra. Minicost Trading Ltd.)

## TAPE HEADS

Send stamp for lists.

R.D.I. Ltd.  
Chilton Works,  
Garden Rd.,  
Richmond,  
Surrey,  
TW9 4NS

For valve and transistorized recorders from £2 ea.

BRAND NEW COMPONENTS BY RETURN: Electrolytics—16V, 25V, 50V—0.47, 1.0, 2.2, 4.7, 10 mfd.—5p, 22, 47—5.2p. (50V—6p) 100—7p. (50V—8p), 220—8p. (50V—10p), 500—11p. (50V—16p), 1000/25V—18p. Subminiature bead-type tantalums—0.1/35V, 0.22/35V, 0.47/35V, 1.0/35V, 2.2/35V, 4.7/35V, 10/20V, 22/16V, 47/6V, 100/3V.—11p. Mylar Film 100V.—0.001, 0.002, 0.005, 0.01, 0.02.—3p. 0.04, 0.05—3.2p. Mullard tubular polyester 400V E6 series 0.001-0.022—3.2p. 0.033-0.1—4.2p. Mullard miniature C333 ceramics 63V E12 series 2%, 1.8 pf.—47 pf.—3p. 56 pf.—330 pf.—3.2p. Polystyrene 63V E12 series 10 pf.—1000 pf.—3p. 1200 pf.—10,000 pf.—4p. Miniature Highstab. carbon film resistors ½W E12 series 5% 10-10MΩ. (10% over 1MΩ) 1.2p. Postage 10p. Prices VAT Inclusive. The C.R. Supply Co., 127, Chesterfield Road, Sheffield S8.

UNBELIEVABLE SPEAKER BAR-GAINS! 8Ω Acoustic Suspension, teak/sculptured foam front, 6 watt £5.30; 12 watt £6.50; 16 watt (8in woofer, 3in tweeter) £7.90. (Lists 20p.) Satisfaction guaranteed (10% p&p). Gregg Electronics, 105 Grange Road, London SE25.

## BULK OFFERS

ALL GOODS FULL SPEC. AND MARKED

|              |              |                |
|--------------|--------------|----------------|
| 1N4001 £2.50 | BC147 £8.00  | BF195 £6.00    |
| 1N4002 £2.80 | BC149 £6.00  | BSY95A £6.00   |
| 1N4003 £3.20 | BC157 £5.00  | 2G302 £4.00    |
| 1N4004 £3.60 | BC158 £6.00  | 2N2646 £34.00  |
| 1N4005 £4.30 | BC159 £3.00  | 2N3055 £28.00  |
| 1N4006 £4.70 | BC161 £10.00 | NE555V £38.00  |
| 1N4007 £5.00 | BC267 £5.00  | 709C £16.00    |
| 1N4148 £2.50 | BC328 £10.00 | 741C £19.00    |
| BC107 £7.00  | BC548 £6.00  |                |
| BC108 £7.00  | BF173 £14.00 | All prices per |
| BC116A £8.00 | BF181 £20.00 | min. quantity  |
|              | BF194 £6.00  | 100.           |

Ferric Chloride £30 per 100 lb bags (8% VAT). Miniature mains transformers, 100mA sec: 6-0-6V £5/10; 9-0-9V £5.50/10; 12-0-12V £6/10; subminiature 6-0-6V 100mA £6/10; 12-0-12V 50mA £6/10 £50/100.

Assorted small value capacitors—ceramic, mica, poly, etc., £26/10,000. Assorted C290 polyesters £26/10,000; 10µF 25V PC £2/100; 47µF 40V Axial lead £4/100.

MINIMUM ORDER £5; CARR. FREE. Add VAT at the appropriate rate (25%). S.A.E. enquiries

JUNIPER ELECTRONICS (PW4)  
PO BOX 61, SOUTHAMPTON SO9 7EE

## Aerials

GENUINE FULL SIZE 18 element TV aerial as used by leading TV companies

FOR ONLY £2.55 incl. VAT

ITV BBC1 & 2B/W & Colour Perfect Pictures. Save ££s. We supply this genuine U.H.F. aerial for only £2.55, can be fitted outside or inside. Quality made technically advanced design. Precision grid reflector eliminates ghosting. Complete with clamp, instructions, advice. Money Back Refund. Wall/Caravan Bracket, 25p. Best Cable 12p per yard. Plug TOP & FREE with order maps & channel reference of Radio & TV Transmitters. Send direct to Dept. PW 10 219 Mansfield Rd. Nottingham

IMPERIAL TRADING (AERIALS) LTD.  
the quality Aerial Specialists

STOCKISTS of Jaybeam Stereobeams, Antiference Mush Killers, Rotars, coax cable, masts and fittings. Send stamp for full lists competitive prices. Alan Turner Services, 26 Chapel Garth, Skipsea, Driffield.

J. & A. TWEEDY (Electronic Supplies) LTD.  
VAT at 25% and Carriage paid to the mainland only. Terms are C.W.O. We welcome ACCESS. Multibeams—Highgain aerials by Jaybeam MBM 28 £5-80 MBM 48 £9-20 MBM 70 Group B £10-00. Stereobeam FM Aerials SBM 4 £8-00 SBM 6 £9-58 FM05 £20-00. Aerial Rotators AR 30 £31-25 AR 40 £37-50. Masthead amplifiers 18db gain complete with power supply £12-00. Low loss co-ax 12p/m. Standard 3 p/m. Cassettes C60 30p. C90 50p. Co-ax plugs 12p. Couplers 20p. We keep a good stock of components at the Chesterfield Branch. Tues to Sat 9 till 5 p.m. 79 Chatsworth Road, Chesterfield, Derbyshire S40 2AP. Telephones: Chesterfield 34982-363755 6-8p.m.

## NEW HIGH GAIN 4 ELEMENT VHF/FM RADIO AERIAL

**Stereo or mono!**

Increase volume, quality and sensitivity of any VHF/FM

Radio or Hi-Fi, stereo or mono, with this genuine aerial. It's a necessity if you want the best out of your equipment, whether a small radio or expensive stereo. Don't put up with poor reception any longer. Send now, hear for yourself. Ideal for the do-it-yourself enthusiast. Supplied with clamp, instructions and advice. Use inside or out. FREE with order maps and channel reference of all Radio and TV Transmitters! Money Back Refund. Send Direct to Dept. HS10 219 Mansfield Rd., Nottingham.

**ONLY**  
**£4.49**  
Inc VAT  
+65p P&P

Best Cable 12p yd

**IMPERIAL TRADING (AERIALS) LTD.**  
the quality Aerial Specialists.

### Service Sheets

**SERVICE SHEETS** for Radio, TV, etc., 50p and SAE. Catalogue 20p and SAE. Hamilton Radio, 47 Bohemia Road, St. Leonards, Sussex.

### LARGE SUPPLIER OF SERVICE SHEETS

(T.V., RADIO, TAPE RECORDERS, RECORD PLAYERS, TRANSISTORS, STEREOGRAMS, RADIOGRAMS, CAR RADIOS)  
ALL AT 50p EACH

**"PLEASE ENCLOSE LARGE S.A.E. WITH ALL ENQUIRIES & ORDERS"**

Otherwise cannot be attended to

(Uncrossed P.O.'s please, original returned if service sheets not available.)

#### PLEASE NOTE

We operate a "by return of post" service. Any claims for non-delivery should be made within 7-days of posting your order.

### C. CARANNA

71 BEAUFORT PARK  
LONDON, N.W.11 6BX

We have the largest supplies of Service Sheets (strictly by return of post). Please state make and model number alternative. Free TV fault tracing chart or TV list on request with order.

Mail order or phone 01-458 4882

**NO OVERSEAS MAIL PLEASE**

**SERVICE SHEETS**, radio, TV etc. 10,000 models. Catalogue 24p, plus SAE with orders, enquiries. Telray, 154 Brook Street, Preston PR1 7HP.

**AERIAL MAIL ORDER** business. Complete stock of 500 aerial material to clear, £250. 90 Ewhurst Road, Crawley 23885 Sussex.

**VARIOUS** new and perfect Heathkit test instruments, including oscilloscope. Expert-built. List. Toms, 6 St. Mary Road, London E17. 01-734 1361.

**EDDYSTONE RECEIVERS** for sale, EC10 Mk. 1, £45; EB37, Mk. 2, £55. All general coverage. Hatton, Parklands, Charmouth, Dorset. Charmouth 225.

*Practical Wireless, August 1975*

## Situations Vacant

# ELECTRONIC CRAFTSMEN

Is your present job routine and uninteresting?

We are a research establishment and our craftsmen are engaged on a wide variety of work in the fields of prototype and small batch wiring and assembly, test and inspection, maintenance fault finding and repair. Why not join us and enjoy working in first-class conditions in the country.

Earnings are good and our rates of pay are currently under review. We can offer good housing at low rental (for applicants who live outside the radius of our Assisted Travel Area) together with 3 weeks paid holiday with holiday bonus, free pension and excellent sick benefit scheme.

Applicants who should have served a recognised apprenticeship or have had equivalent training together with experience in one of the fields detailed should 'phone Padley 4111 (STD 073 56 4111) Ext 5230, or write to:

**Industrial Recruitment Officer**  
**(PA/86/PW) Procurement Executive**  
**Ministry of Defence**  
**AWRE Aldermaston**  
**Reading, Berks**  
**RG7 4PR**

## MEN! £90 p.w. can be yours

Tens of thousands of new computer personnel needed over the next few years alone. With our revolutionary, direct-from-America, course, you train as a Computer Operator in only 4 weeks!

It can pay around £35 p.w. as a starter and can reach over £90 p.w.

After training, our executive appointments bureau—one of the world's leaders of its kind—introduces you FREE to world-wide opportunities. Write or 'phone TODAY, without obligation.

**London Computer Operators Training Centre**

Y26, Oxford Hse.,  
9-15 Oxford St. W1. Tel: 01-734 2874

### Ladders

**LADDERS**, timber and aluminium.  
Tel: Telford 586644 for brochure.

### Wanted

**TOP PRICES PAID for NEW VALVES and TRANSISTORS**

popular T.V. and Radio types.

**KENSINGTON SUPPLIES (C)**,  
367 Kensington Street, Bradford 8,  
Yorkshire.

**WE BUY** New Valves, Transistors and clean new components, large or small quantities, all details, quotation by return. **WALTON'S**, 55 Worcester Street, Wolverhampton.

### For Sale

**HEATHKIT GR78**. Very little used. Aligned and tested by Heathkit, £60. Apply Box No. 125.

#### COPPER CLAD LAMINATE FOR PRINTED CIRCUITS

Single sided 1/16" paper base—1.0p/sq. inch. Single sided 1/16" glass-epoxy—1.5p/sq. inch. Any rectangular sizes cut to your requirements. Please send cash with order. Price includes postage and packing.  
From: **SIMTECH ENGINEERING LTD**  
Voluntary Place  
**WANSTEAD, LONDON E11 2RP**  
01-530 4240

**SOUNDLIGHT CONVERTERS** 3-channel: 1.5kW, £17; 3kW, £25. Strobes: 1-joule, £21; 4J, £27; 15J, £45. Chasers from £27. Rainbows, Projectors. Bumper catalogue: Aarvak Electronics, 98a(P) West Green Road, N15 5NS. 01-800 8656.

**MICROPHONES**: AKG D202EI, £45.00; AKG D190C or E, £20.00; AKG D224, £60.00; Sennheiser MD211N, £45.00. All brand new and boxed. Please add 25% for VAT. All other AKG and Sennheiser mikes, SAE for quote. J. J. Francis (Wood Green), Ltd., Manwood House, Matching Green, Harlow, Essex. Tel: Matching 476.

## Educational

### C AND G EXAMS

Study for success with ICS. An ICS homestudy course will ensure that you pass your C. & G. exams. Special courses for: Telecons, Technicians', Electrical Installations, Radio, TV & Electronics Technicians', Radio Amateurs'. Full details from ICS School of Electronics, Dept. 320, Intertext House, London, SW8 4UJ. Tel: 01-622 9911 (all hours).

### TECHNICAL TRAINING

Get the training you need to move up into a higher paid job. Take the first step now—write or phone ICS for details of ICS specialist homestudy courses on Radio, TV, Audio Eng. and Servicing, Electronics, Computers; also self-build radio kits. Full details from ICS School of Electronics, Dept. 321, Intertext House, London, SW8 4UJ. Tel: 01-622 9911 (all hours).

### COLOUR TV SERVICING

Learn the techniques of servicing Colour TV sets through new home study course approved by leading manufacturer. Covers principles, practice and alignment with numerous illustrations and diagrams. Other courses for radio and audio servicing. Full details from ICS School of Electronics, Dept. 322, Intertext House, London SW8 4UJ. Tel: 01-622 9911 (all hours).

## Books and Publications

### Technical Books — Radio & Electronics

|   |       |
|---|-------|
| World's Radio & TV Stations (International Edit)..... | £0.68 |
| Audio Amplifiers.....                                 | £0.70 |
| Boys Book of Crystal Sets & Simple Circuits.....      | £0.33 |
| Television Timebase Circuits.....                     | £1.15 |
| Radio TV and Industrial Tube & Valve Equip.....       | £0.68 |
| How to get the best out of your Tape Recorder.....    | £1.67 |
| Practical Electronic Science Projects.....            | £0.85 |
| Jack Darr's Service Clinic.....                       | £1.55 |
| Transistor Circuits for Modern Test Equipment.....    | £0.68 |
| Rad & Electr Colour Codes and Data Chart.....         | £0.20 |
| Handbk of Transistor Equip and Substitutes.....       | £0.48 |
| Hi Fi, PA & Disco Amplifier Design Hndbk.....         | £0.87 |
| Radio Servicing Problems.....                         | £0.75 |
| Electronic Circuits for the Amat Photographer.....    | £0.68 |
| Handbook of Simple Transistor Circuits.....           | £0.40 |
| TV Fault Finding.....                                 | £1.10 |
| Sound and Loudspeaker Manual.....                     | £0.60 |
| Practical Stereo & Quadrophony Handbook.....          | £0.85 |
| Radio Amateur Operator's Handbook.....                | £0.85 |
| Coil Design & Construction Manual.....                | £0.58 |
| Radio TV & Electronics Data Book.....                 | £0.68 |
| 79 Electronic Novelty Circuits.....                   | £0.80 |
| Receiving Pal Colour Television.....                  | £5.35 |
| Radio Technicians Bench Manual.....                   | £3.30 |
| Servicing Transistor Radio Receivers.....             | £0.90 |
| 1st Book of Hi Fi Loudspeaker Enclosures.....         | £0.68 |
| 2nd Book of Hi Fi Loudspeaker Enclosures.....         | £0.68 |
| Manual of Electronic Circuits for the Home.....       | £0.60 |
| Modern Crystal Set Circuits for Beginners.....        | £0.40 |
| Electronic Novelties for the Motorist.....            | £0.58 |
| 2nd Book of Transistor Equip. & Substitutes.....      | £1.07 |
| Handbook of Electronic Musical Novelties.....         | £0.58 |
| Transistorised Novelties for Hi Fi Enthusiast.....    | £0.40 |
| Fault Location Exercises in Rad. & TV Vol.1.....      | £0.95 |
| Fault Location Exercises in Rad. & TV Vol.2.....      | £1.55 |
| Colour TV Picture Faults.....                         | £2.70 |
| Practical Transistor Novelty Circuits.....            | £0.48 |
| Boys Book of Practical Radio & Electronics.....       | £0.68 |
| Radio Receiver Construction using ICs & Transis.....  | £0.68 |
| ICs & Transistor Gadgets Construction Handbk.....     | £0.68 |
| Integrated Circuits Equip. & Substitutes Hbk.....     | £0.85 |
| Audio Technicians Bench Manual.....                   | £3.30 |
| Improving your Hi-Fi.....                             | £3.30 |
| Guide to Printed Circuits.....                        | £2.80 |
| HOW TO LISTEN TO THE WORLD, 9th EDIT.....             | £2.65 |
| WORLD RADIO TV HANDBOOK 1975.....                     | £3.80 |

All prices include Postage & Packing

**RADIO BOOK SERVICE**  
40 Elwill Way, Beckenham BR3 2RZ

GO TO SEA as a Radio Officer. Write: Principal, Nautical College, Broadwater, Fleetwood FY7 8JZ.

## TELEVISION TRAINING

**16 MONTHS'** full-time practical and theoretical training course in Radio and TV Servicing (Mono and Colour) for beginners.

**13 WEEKS'** full-time Colour TV Servicing course. Includes 100 hours practical training. Mono revision if necessary. Good electronics background essential.

NEXT SESSION commences on Sept. 15th.

Prospectus from: **London Electronics College, Department B8, 20 Penywern Road, London SW5 9SU. Tel. 01-373 8721.**

## Miscellaneous

**LOW COST IC MOUNTING.** 100 IC pin sockets, 50p. Quantity rates. SAE details and sample. 7 and 8 hole plastic supports 5p/pair (P&P 8p/order). LED (MLED500), 20p each, post free (quantity rates). PKG Electronics, Oak Lodge, Tansley, Derbyshire DE4 5FE.

**175cc.P.C.B. INK !!**  
**£ 1-50 post & vat free**  
**Mawson Associates**  
**64, Brookbank Road,**  
**London SE13.**

**GLASS FIBRE PCBs** for all projects. Drilled and tinned. Send master and 30p per board plus 5p per square inch. Electro Circuits, 4 Highcliffe Way, Wickford, Essex.

**P.W. CRATA F.M. TUNER.** Set of five P.C. boards £3, p&p 20p. Other components available. S.A.E. for lists. Teleradio, 325 Fore Street, Edmonton, London N9 0PE.

### H. M. ELECTRONICS

275a FULWOOD RD., BROOMHILL,  
SHEFFIELD S10. 3BD.



Be proud of your work and build it in a BEC (Book End Chassis) 5 Standard sizes

Please send 15p (Refundable) for folder of leaflets

**DIGITAL CLOCK CHIP, AY-5-1224,** with data & circuit diagram, £3.66 + VAT, Jumbo' LED digits (16mm high) economy type DL-747, only £2.04 each + VAT, post free.—Greenbank Electronics, 94 New Chester Road, Wirral, Merseyside, L62 5AG.

## A BETTER FT.101

G3LLL's RF Clipper + "VK BLOB" (double balanced mixer module) makes old FT.101's better than new on both send and receive. Full gen. + useful free modification leaflet.

**G3LLL, HOLDINGS LTD.,**  
39/41 Mincing Lane, Blackburn BB2 2AF  
Tel: 59595/6

**ELECTRONIC ORGAN and Piano constructors.** Teach yourself musical harmony with The Instachord Method. New, simple, only £1.60 complete. Or send SAE for illustrated details. Hawkins Associates, PO Box 8, Newbury, Berks. RG13 4QJ.

**VALVES:** 1920 to 1955, large stocks at realistic prices, send SAE for free list, or 40p for our full "Antique Wireless Catalogue". Tudor Rees, 64 Broad Street, Staple Hill, Bristol. Tel: 0272-565472.

**PRINTED CIRCUIT COPPER CLAD.** Single Sided. Quality material. Flame retardant to N.E.M.A. Spec. Paper Base (FR2) 1/4 x 7 x 5, 3 for £1. Epoxy Glass (FR4) 1/4 x 7 x 5, 2 for £1

Also panels cut to your requirements, quotation by return.

Prices include P. & P. Cash with Order.

**P. G. OLIVER & CO.**

4 Hearsall Lane,  
COVENTRY CV5 6HH.

**HARDWARE.** Comprehensive range of screws, nuts, washers, etc. in small quantities, and many useful Constructors' items. Sheet aluminium to individual requirements, punched, drilled, etc. Fascia panels, dials, nameplates in etched aluminium. Printed circuit boards for this magazine and other individual requirements, one-offs and small runs. Machine engraving in metals and plastics, contour milling. Send 2 x 4 1/2 p stamps for catalogue. Ramar Constructor Services, Masons Road, Stratford on Avon, Warwick., CV37 9NF.

## Synthesiser "Sounds Supreme"

by **Dewtron** (25% VAT extra.)

Famous kits, e.g. vaa-waa complete kit £3.50; Fuzz Kit £5.50. P & P 25p under £10. Ring Modulator modules £9. "Mister Bassman" Bass Pedal Units and whole range of synthesiser modules, musical novelties, etc. Catalogue 20p from D.E.W. Ltd., 254 Ringwood Road, Ferndown, Dorset.

**LOWEST COST IC SOCKETS.** Use Soldercon IC socket pins for 8 to 40 pin DIL's. Make 8 pin sockets for 4p, 14 pin for 7p (at 300 pin price), 7p for strip of 100 pins, £1.50 for 3 x 100. £4 for 1000. 10p p&p for orders under £2. Add 8% VAT. Instructions supplied—send sae for sample. SINTEL, 53n Aston Street, Oxford. Tel: 0865 43203.

Practical Wireless, August 1975

**SUPERB INSTRUMENT CASE** by Bazelli, manufactured from heavy duty PVC faced steel. Hundreds of Radio, Electronic, Hi-Fi enthusiasts, and Industrial users are choosing the cases they require from our range. Make your VAT go further with our competitive prices which begin at a low 75p. Examples: Width, Depth, Height 7" X 7" X 5" £2.65, 8" X 10" X 6" £3.60, 12" X 8" X 7" £4, 12" X 12" X 7" £4.40. Over 200 Models to choose from. Prompt despatch, Free literature (Stamp would be appreciated) Bazelli Dept No 25, St. Wilfrids, Foundry Lane, Halton, Lancaster LA2 6LT.

**P.W. EASIBUILD ORGAN**

- Set of two P.C.B.'s ... .. £6-80
- Set of thirteen MOS ics ... .. £23-65
- Set of all semiconductors ... .. £29-80
- Set of all semiconductors plus the P.C.B.'s ... .. £34-90

All include V.A.T. and P. & P.

**FORESIGHT ELECTRONICS**

62 High Street,  
Croydon,  
Surrey.

MAIL ORDER ONLY. ALLOW 14 DAYS DELIVERY.

**UFO CHARTS:** Wave Prediction, 54p; Daily Flight Pattern, 50p; TV Doppler Detection, 63p; Propulsion Theory, 55p; "Anti-Gravity", 55p. Map 50p. Circuits: Transistor Optical Detector, 66p; Radiation/Optical, 44p; Crystal Radiation Counter/Timer/Stopclock, 85p. R. & E. Highlands, Needham Market, Suffolk.

**12 VOLT** 21" 13 Watt Fluorescent Lighting (by Thor/AEL) with diffuser & on/off switch. Ideal caravan, boat, emergency lighting, etc. Guaranteed.



£5.50 inc. VAT & Post. List price £7.02 inc. VAT  
**SALOP ELECTRONICS** 23 Wyle Cop, Shrewsbury, Shropshire Tel. 53208

**RANDOM NUMBER SELECTOR**

Minicomp 6L: New! Electronic Dice, range 1-6. Jumbo. 0.6in LED display. 4 ICs. Kit £14.75; built and tested £16.90. Minicomp 10L: Two ranges 1-6 and 0-9. Kit £17.75, built and tested £19.90. Minicomp 100: Four ranges 1-6, 0-36 (Roulette), 0-59 (Pools) and 0-99. Nixie display, 6 ICs. Built and tested £29.50. Terms: CWO, Mail Order only. Prices inclusive. 1 year guarantee.

**MICROELECTRONICS**

51 Mexfield Road, London SW15 2RG

**TRIACS** (plastic) 10A/400V 67p (3+64p), Diac 19p, NE555V 55p (3+50p), 2N6027 PUT 30p, Ferrite Rods 1 1/4 in X 3/4 in dia. 10p, Plastic Lightdimmer Frontplate 20p, with 3/8 in dia hole 22p. P&P 15p. Add VAT. T.K. Electronics, 106 Studley Grange Road, London W7 2LX.

**SINTEL**

Add 10p P. & P. for orders under £2. Data, and circuits where appropriate supplied with orders or available separately (send 9in x 4in S.A.E.) **ADD VAT at 8%.**

- MK1-6-Kit 6 digit Alarm Clock Kit (complete less case, transformer, switches, LS) £16-55
- MK1-4-Kit 4 digit Alarm Clock Kit £14-75
- MK50250N Alarm Clock IC with Snooze £5-60
- Xtal plus CMOS to provide 50 c.p.s. £5-84
- DL704E Red 0.3in LED 7 seg display C. Cath. 85p
- MAN3M Red 0.12in LED 7 seg display C. Cath. 48p
- SOLDERCOM I.C. Socket Pins** 50p per 100 pins Send s.a.e. for pin sample 1000 pins for £4.00
- RCA 1975 CMOS Databook £2.30 (No VAT)+37p P&P
- Other displays, IC's, etc. are available; also RCA CMOS. Phone or send s.a.e. for Price List 6.
- ADD VAT at 8%**—new 25% rate does not apply to any of these goods.

**SINTEL, 53N ASTON STREET, OXFORD**  
Tel. (0865) 43203

**TREASURE TRACER MK III Metal Locator**

- Varicap tuning
- Britain's best selling metal locator kit
- Weighs only 22oz. Fitted with Faraday shield.
- Speaker and earphone operation
- Knocks down to only 17in.
- Prebuilt search coil assembly
- Thoroughly professional finish
- As seen on BBC1 and BBC2 TV
- You only need soldering iron, screwdriver, pliers and snips
- Five transistor circuit

Send stamped, addressed envelope for leaflet

Complete Kit £10-90 Built & tested £15-25  
Post 63p 78p VAT(8%) Post 60p 1 £12.27 VAT(8%)

**MINIKITS ELECTRONICS,**  
62 CLEVELAND ROAD,  
LONDON, E18 2AN (Mail order only)

**VALVES.** Radio, TV, transmitting, industrial. 1930 to 1975. Many obsolete. 2,000 types stocked. List 20p. We wish to purchase new and boxed valves. Cox Radio (Sussex) Ltd., The Parade, East Wittering, Sussex. West Wittering 2023.

**BUILD YOUR OWN**

You are invited to send S.A.E. for lists of our very extensive range of high quality amplifier, pre-amps, F.M. tuners, instruments. Radiocontrol ignition units and many other kits.

**TELERADIO ELECTRONICS,**  
325 FORE STREET, EDMONTON,  
LONDON N9

**PCB MANUFACTURER'S OFFER.** IPC approved full spec, fully drilled ready to assemble PCBs for: "PW" Easy-build Organ, £5.70 (2 PCBs); Tricolour, £1.37; Tele-Tennis (6 PCBs), £3.70; Add-on Sound Effects, £1.10; Telephone Exchange, £1.10; Ferret Metal Locator, 78p; Derby, 85p; Audio/Mixer, 40p; Tone & Rumble, 65p; "PE" CCTV, £2 (2 PCBs); Orion with printed layout on PCB, £1.20; Power Slaves, £1.60 (3 PCBs); Scorpio 2, 70p; Gas Detectors, £1.20; Pulse Generator, £1.10. CWO. Prices totally inclusive. Many others available. SAE for lists. Production space for PCB production, Electroplating, Screen Printing, Tinting, plus all Graphic/Art & Photographic and Design facilities and supplies. Estimates by return or Phone WKF Electronics, Welbeck Street, Whitwell, Worksop, Notts. S80 4TW. Tel: Whitwell 695 (Derbys.). Callers to 1-3 Station Road.

**DON'T LOOK**

unless you can resist the temptation to get these super 'attention-getters':

- ★ Pocket-sized **MAXI-VOLT** Big 1/2 inch Spark Generator (instant 15,000 volts!). Ready-made, needs no batteries. Carry it around anywhere. Only weighs about 3 oz. (89g.) send £2.45 for your Maxi-Volt now!
- ★ Unique **TRANSMITTER/RECEIVER** Kit. No licence examinations or tests required to operate this transistorised equipment. Easy to build. Get transmitting. Send £7.95 for yours now!
- ★ Psychedelic **MINI-STROBE** Kit. Take a pocket-sized lightning storm to Disco's & parties. 'Brain-freeze' 'em with vari-speed stop-motion flashes. Includes super case too. Send £3.50 now! (all prices include V.A.T., packing & postage.)

Send remittance to:

**BOFFIN PROJECTS,**  
4 CUNLIFF ROAD,  
STONELEIGH, EWELL, SURREY  
(Mail order U.K. only)

Or for more details, send 20p for lists

**FANTASTIC NEW MICROTEST 80**

**MEASURES ONLY**


90 X 70 X 18 mm  
ELECTRONIC ZERO Ω

Amazing Value at **£11.95**

8 fields of measurement and 40 ranges

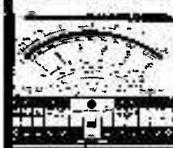**PRINTED CIRCUIT BOARD IS REMOVABLE WITHOUT SOLDERING**

- Volts D.C. 6 ranges: 100mV - 2V. - 10V. - 50V. - 200V. - 1000V. (20kΩ/V) £2% precision on DC and AC
- Volts A.C. 5 ranges: 1.5V. - 10V. - 50V. - 250V. - 1000V. (4kΩ/V)
- Amp. D.C. 6 ranges: 50μA - 500μA - 5mA - 50mA - 500mA - 5A
- Amp. A.C. 5 ranges: 250μA - 2.5mA - 25mA - 250mA - 2.5A
- Ohms 4 ranges: Low Ω - Ω x 1 - Ω x 10 - Ω x 100 from 1/10 dl Ω until 5 Mega Ω
- V Output 5 ranges: 1.5V. - 10V. - 50V. - 250V. - 1000V.
- Decibels 5 ranges: + 6dB, +22dB, +36dB, +50dB, +62dB
- Capacity 4 ranges: 25μF - 250μF - 2500μF - 25,000μF



**SUPERTESTER 680R ICE**

20,000 Ohm per Volt/sensitivity  
● Fully screened against external magnetic fields  
● Scale width and small case dimensions (128 x 95 x 32mm)  
● Accuracy and stability (1% in D.C., 2% in A.C.) of indicated reading  
● Simplicity and ease of use and readability  
● Full ranges of accessories  
● 1000 times overload  
● Printed circuit board is removable without de-soldering  
● More ranges than any other meter. Ask for free catalogue

**£18.50**

Accessories (extra) available to convert Microtest 80 & SuperTester 680R into following: LIGHT-METER GAUSS METER, ELECTRONIC VOLT-METER, AMPERCLAMP, TRANSISTOR TESTER, TEMPERATURE PROBE, PHASE SEQUENCE INDICATOR, Ω x 100K Multiplier, SIGNAL INJECTOR—Send for details.

**MORE RANGES FOR LESS MONEY!**

AC/DC Multimeter type U4324

- A-DC 0-08-3A - 6 Ranges.
- A-AC 0-3-3A - 5 Ranges.
- V-DC 0-6-1200 V - 9 Ranges.
- V-AC 3-900 V - 8 Ranges.

Freq.: in the range of 45 to 20kHz, Resistance: 500 Ohm to 5 Mohm - 5 Ranges. Decibel: -10 to +12dB. Accuracy: ± 2.5% DC, ± 4% AC. Dimensions: 167 x 98 x 63 mm.

Only **£9.25**

**ALPHANUMERIC NIXIE TUBES B7971**

The Alphanumeric NIXIE tube has the ability to display all the letters of the alphabet, numerals 0 thru 9 and special characters in a single tube. From the standpoint of both readability and electrical characteristics, the Alphanumeric NIXIE tube provides many unique benefits including ★ 170v-21mA ★ All d.c. operation ★ Uniform, continuous line characters of equal height ★ Memory with simple solid state drive circuits ★ Readability in high ambient light ... 200 footcandle brightness ★ Long life with no loss of brightness ★ Character height 2 1/2 in.

Price only **99p** each plus 16p P/P. Bases for above 60p each.

**JUST ARRIVED !!**

**NUMERIC INDICATOR TUBES**

Ultra-long life, high quality, 0-9 and 2 independent decimal points. Supply voltage 200V D.C. Current 14mA. Pulse duration 100μs. Character height 0.51, overall size 1.4. Brand new, guaranteed. Surplus to manufacturers requirements. Type B5853st

1-25 £1. 1000+ price on application 8% VAT to all items + 35p P & P

**ELECTRONIC BROKERS LTD.**  
49-53 Pancras Road, London NW1 2QB  
Tel: 01-837 7871

# WATFORD ELECTRONICS

35 CARDIFF ROAD, WATFORD, HERTS, ENGLAND  
MAIL ORDER. CALLERS SATURDAYS ONLY

OUR NEW LOW PRICES MEANS YOU PAY LESS VAT.

| TRANSISTORS (less 10% for 25+ of one type) |            |             |            |             |             |  |  |  |  |
|--|------------|-------------|------------|-------------|-------------|--|--|--|--|
| AC125 13p                                  | BC148 7p   | BF177 26p   | OC71 11p   | 1S920 7p    | 2N2926Y 8p  |  |  |  |  |
| AC126 11p                                  | BC149 9p   | BF178 28p   | OC72 11p   | 1S921 7p    | 2N3053 18p  |  |  |  |  |
| AC127 11p                                  | BC154 18p  | BF179 33p   | OC74 28p   | 1S922 8p    | 2N3054 42p  |  |  |  |  |
| AC128 11p                                  | BC157 13p  | BF180 33p   | OC81 12p   | 1S923 10p   | 2N3055 45p  |  |  |  |  |
| AC141 20p                                  | BC158 12p  | BF181 33p   | OC82 12p   | 2N696 15p   | 2N3614 59p  |  |  |  |  |
| AC142 15p                                  | BC159 13p  | BF184 22p   | OC83 28p   | 2N697 13p   | 2N3615 85p  |  |  |  |  |
| AC176 11p                                  | BC167 12p  | BF185 22p   | OC140 100p | 2N698 30p   | 2N3702 12p  |  |  |  |  |
| AC187 12p                                  | BC168 12p  | BF194 10p   | OC201 70p  | 2N706 11p   | 2N3703 12p  |  |  |  |  |
| AC188 11p                                  | BC169 12p  | BF195 10p   | OC202 80p  | 2N708 16p   | 2N3704 12p  |  |  |  |  |
| ACY17 35p                                  | BC170 11p  | BF196 12p   | TIC44 30p  | 2N918 40p   | 2N3705 12p  |  |  |  |  |
| ACY19 25p                                  | BC171 11p  | BF197 12p   | TIP29 43p  | 2N930 18p   | 2N3706 10p  |  |  |  |  |
| ACY20 24p                                  | BC172 11p  | BF257 32p   | TIP30 45p  | 2N1131 20p  | 2N3707 10p  |  |  |  |  |
| ACY21 29p                                  | BC177 18p  | BF595 18p   | TIP39 48p  | 2N1132 20p  | 2N3708 8p   |  |  |  |  |
| ACY22 16p                                  | BC178 16p  | BF596 18p   | TIP30A 54p | 2N1301 20p  | 2N3709 8p   |  |  |  |  |
| AD140 48p                                  | BC179 18p  | BF598 22p   | TIP31 54p  | 2N1302 17p  | 2N3710 9p   |  |  |  |  |
| AD149 45p                                  | BC182 10p  | BFY50 15p   | TIP32 64p  | 2N1303 20p  | 2N3771 140p |  |  |  |  |
| AD161 34p                                  | BC183 10p  | BFY51 15p   | TIP33 95p  | 2N1304 24p  | 2N3772 160p |  |  |  |  |
| AD162 34p                                  | BC184 11p  | BFY52 15p   | TIP34 130p | 2N1305 24p  | 2N3773 200p |  |  |  |  |
| AF114 13p                                  | BC184L 11p | BFY53 17p   | TIP41A 68p | 2N1306 24p  | 2N3819 20p  |  |  |  |  |
| AF115 13p                                  | BC212 12p  | BSX20 16p   | TIP42A 74p | 2N1307 24p  | 2N3820 47p  |  |  |  |  |
| AF116 13p                                  | BC212L 12p | RU105 22.2p | TIS43 26p  | 2N1893 30p  | 2N3823 60p  |  |  |  |  |
| AF117 13p                                  | CC213 10p  | MJE370 63p  | TIS44 17p  | 2N1890 45p  | 2N3824 50p  |  |  |  |  |
| AF118 40p                                  | CC214 13p  | MJE371 78p  | ZTX107 10p | 2N2166 62p  | 2N3804 15p  |  |  |  |  |
| AF121 33p                                  | CCY42 28p  | MJE520 62p  | ZTX108 8p  | 2N2217 23p  | 2N3905 17p  |  |  |  |  |
| AF124 30p                                  | CCY43 25p  | MFP102 30p  | ZTX109 12p | 2N2219 20p  | 2N3906 17p  |  |  |  |  |
| AF125 30p                                  | CCY58 18p  | MFP103 30p  | ZTX300 12p | 2N2221 20p  | 2N4037 35p  |  |  |  |  |
| AF126 30p                                  | CCY59 18p  | MFP104 30p  | ZTX301 14p | 2N2222 20p  | 2N4058 15p  |  |  |  |  |
| AF127 30p                                  | CCY70 15p  | MFP105 30p  | ZTX302 18p | 2N2303 25p  | 2N4061 13p  |  |  |  |  |
| AF139 33p                                  | CCY71 18p  | OC23 144p   | ZTX304 22p | 2N2369A 14p | 2N4062 14p  |  |  |  |  |
| AF181 45p                                  | CCY72 12p  | OC26 48p    | ZTX311 10p | 2N2483 30p  | 2N4871 31p  |  |  |  |  |
| AF186 48p                                  | BD124 75p  | OC28 48p    | ZTX341 19p | 2N2646 38p  | 2N5457 30p  |  |  |  |  |
| AF209 38p                                  | BD131 40p  | OC35 48p    | ZTX500 15p | 2N2904 20p  | 2N5458 30p  |  |  |  |  |
| BC137 9p                                   | BD132 40p  | OC36 52p    | ZTX501 13p | 2N2906 15p  | 2N5459 30p  |  |  |  |  |
| BC108 9p                                   | BD137 45p  | OC41 15p    | ZTX502 18p | 2N2907 18p  | 3N140 85p   |  |  |  |  |
| BC108B 12p                                 | BD145 55p  | OC42 15p    | ZTX504 42p | 2N2908 15p  | 3N141 85p   |  |  |  |  |
| BC109 8p                                   | BDY80 75p  | OC44 12p    | ZTX531 23p | 2N2925G 10p | 40361 40p   |  |  |  |  |
| BC109C 12p                                 | BDY61 65p  | OC45 12p    | ZTX550 18p | 2N2925E 8p  | 40362 40p   |  |  |  |  |
| BC147 7p                                   | BF115 22p  | OC70 11p    | 1S44 5p    | 2N2925R 8p  | 40673 58p   |  |  |  |  |

ALL DEVICES BRAND NEW AND FULLY GUARANTEED. ORDERS DESPATCHED BY RETURN OF POST. TERMS OF BUSINESS: CASH/CHEQUE/P.O. OR BANKERS DRAFT WITH ORDER. GOVERNMENT AND EDUCATIONAL INSTITUTIONS OFFICIAL ORDERS ACCEPTED. TRADE AND EXPORT INQUIRY WELCOME. P & P ADD 20p TO ALL ORDERS UNDER £10.00. OVERSEAS ORDERS POSTAGE AT COST, AIR/SURFACE.

## PRICES EXCLUSIVE OF VAT

Send 15p postage for our comprehensive catalogue

**POLYESTER CAPACITORS:** Axial lead type. (Values are in  $\mu$ F).  
400V: 0-001, 0-0012, 0-0015, 0-0018, 0-0022, 0-0033, 0-0047 3p; 0-0068, 0-01, 0-015, 0-022, 0-033, 0-047, 0-068, 0-1 4p; 0-15, 0-22, 7p; 0-33, 10p; 0-47, 13p; 160V: 0-1, 0-15, 4p; 0-22 5p; 0-33 6p; 0-47 9p; 0-68 10p; 1-0 15p. 250V: 0-22 8p; 0-33 8p; 0-68 12p; 0-47 9p; 2-2 18p.

**POLYESTER RADIAL LEAD P.C. TYPE** (Values are in  $\mu$ F). **FEED THROUGH CAPACITORS**  
250V: 0-01, 0-015, 0-022, 0-033, 0-047 3p; 0-068, 0-1 4p; 0-15 4p; 0-22 5p; 0-33 7p; 0-47 9p; 0-68 10p; 1-0 14p; 1-5 22p; 2-2 24p. 1000pF/350V 8p

**ELECTROLYTIC CAPACITORS.** Axial lead type (Values are in  $\mu$ F)  
63V: 0-47, 1-0, 1-5, 2-2, 3-3, 4, 4-7, 6-8, 10, 15, 20, 22, 47, 68, 6p. 100, 12p. 40V 100, 6p  
50V: 1000, 42p. 30V: 3500, 41p. 25V: 10, 68, 150, 6p; 220, 11p; 470, 13p; 680, 18p; 1000, 24p; 2200, 34p. 3000, 39p; 4700, 47p. 18V: 40, 125, 250, 6p. 16V: 1000, 1500, 18p. 10V: 4, 100, 5p; 640, 10p; 1000, 14p; 2200, 18p.

**POTENTIOMETERS (AB)** Carbon Track, 0-25W Log & 0-5W Linear values  
1K  $\Omega$ -2M  $\Omega$  single gang 14p  
5K  $\Omega$ -2M  $\Omega$  single gang D/P switch 32p  
2K  $\Omega$ -2M  $\Omega$  dual gang stereo 45p

**SLIDER POTENTIOMETERS**  
0-25W log and linear values  
5K  $\Omega$ -500K  $\Omega$  single gang 35p  
10K  $\Omega$ -500K  $\Omega$  Dual gang 50p  
KNOBS for above Black or Silvered 8p

**PRESET POTENTIOMETERS**  
0-1W 50  $\Omega$ -1M  $\Omega$  Vertical only 5p  
0-25W 100  $\Omega$ -2-2M  $\Omega$  Horizontal 6p  
0-25W 1K  $\Omega$ -2-2M  $\Omega$  Vertical 6p

**TANTALUM BEAD CAPACITORS**  
25V: 0-1  $\mu$ F, 0-2, 0-47, 1-0, 2-2, 4-7, 6-8 3p  
30V: 0-1  $\mu$ F, 0-2, 0-47, 1-0, 2-2, 4-7 2p  
25V: 10  $\mu$ F, 16V: 22  $\mu$ F, 10V: 33  $\mu$ F, 22  $\mu$ F, 6V: 33  $\mu$ F, 47  $\mu$ F; 3V: 47  $\mu$ F, 100  $\mu$ F. Price: 10p each.

**MYLAR FILM CAPACITORS**  
100V: 0-001, 0-002, 0-005, 0-01  $\mu$ F 3p  
0-015, 0-02, 0-04, 0-05  $\mu$ F, 0-1  $\mu$ F 4p  
0-15, 0-2 50V: 0-47  $\mu$ F 6p

**CERAMIC CAPACITORS**  
50V d.c. Plaquette body 25mm leads.  
Range: 5p-10,000pF  
0-015  $\mu$ F, 0-022  $\mu$ F, 0-033  $\mu$ F, 0-047  $\mu$ F 3p

### TTL 74 DIGITAL ICs

| IC   | Price | IC   | Price | IC    | Price |
|------|-------|------|-------|-------|-------|
| 7400 | 14p   | 7428 | 35p   | 7473  | 33p   |
| 7401 | 14p   | 7430 | 15p   | 7474  | 32p   |
| 7402 | 15p   | 7432 | 25p   | 7475  | 32p   |
| 7403 | 15p   | 7433 | 36p   | 7476  | 32p   |
| 7404 | 18p   | 7437 | 27p   | 7480  | 44p   |
| 7405 | 18p   | 7438 | 27p   | 7481  | 99p   |
| 7406 | 38p   | 7440 | 15p   | 7482  | 75p   |
| 7407 | 38p   | 7441 | 65p   | 7483  | 83p   |
| 7408 | 15p   | 7442 | 65p   | 7484  | 90p   |
| 7409 | 15p   | 7443 | 120p  | 7485  | 125p  |
| 7410 | 15p   | 7444 | 105p  | 7489  | 275p  |
| 7411 | 20p   | 7445 | 88p   | 7490  | 40p   |
| 7412 | 20p   | 7446 | 105p  | 7491  | 80p   |
| 7413 | 35p   | 7447 | 100p  | 7492  | 48p   |
| 7414 | 60p   | 7448 | 70p   | 7493  | 39p   |
| 7416 | 35p   | 7450 | 15p   | 7495  | 63p   |
| 7417 | 35p   | 7451 | 15p   | 7496  | 72p   |
| 7420 | 15p   | 7453 | 15p   | 74121 | 32p   |
| 7422 | 24p   | 7454 | 15p   | 74122 | 45p   |
| 7423 | 27p   | 7460 | 15p   | 74141 | 65p   |
| 7425 | 27p   | 7470 | 30p   | 74190 | 160p  |
| 7426 | 27p   | 4772 | 26p   | 74191 | 160p  |

### DIODES

| Diode    | Price | Diode    | Price |
|----------|-------|----------|-------|
| AA120    | 10p   | BY127    | 11p   |
| BY100    | 18p   | BYZ11    | 25p   |
| BY127    | 11p   | OA5      | 38p   |
| BYZ11    | 25p   | OA9      | 9p    |
| OA5      | 38p   | OA10     | 36p   |
| OA9      | 9p    | OA79     | 8p    |
| OA10     | 36p   | OA81     | 8p    |
| OA79     | 8p    | OA85     | 10p   |
| OA81     | 8p    | OA90     | 6p    |
| OA85     | 10p   | OA91     | 6p    |
| OA90     | 6p    | OA100    | 10p   |
| OA91     | 6p    | OA200    | 6p    |
| OA100    | 10p   | OA202    | 6p    |
| OA200    | 6p    | 1N914    | 4p    |
| OA202    | 6p    | 1N4001/2 | 5p    |
| 1N914    | 4p    | 1N4003   | 5p    |
| 1N4001/2 | 5p    | 1N4004/5 | 6p    |
| 1N4003   | 5p    | 1N4006/7 | 6p    |
| 1N4004/5 | 6p    | 1N4148   | 5p    |
| 1N4006/7 | 6p    | 1S920    | 6p    |
| 1N4148   | 5p    | 1S921    | 6p    |

### SPECIAL OFFER

Beat the VAT Man.  
LED 0-2" diameter, Red 12p  
Green, Yellow, Amber & White 17p  
7 Seg Display DL707 £1.25  
DL747 £1.85  
741C 23p  
748C 25p  
7447TTL 70p  
NE555 42p  
TBA800 88p  
ZN414 88p

### EARPHONES

With Cord and Jack  
Plug Magnetic  
2-5 mm plug 15p  
3-5 mm plug 15p  
Crystal  
3-5 mm plug 28p

### LINEAR IC'S

| IC              | Price | IC       | Price |
|-----------------|-------|----------|-------|
| 709C 14 pin     | 29p   | LM304H   | 170p  |
| 741C            | 26p   | LM305    | 170p  |
| 747C            | 70p   | LM380    | 90p   |
| 748C            | 28p   | LM381    | 160p  |
| AY-1-0212 5-50p |       | LH3900   | 75p   |
| AY-1-5051 1-15p |       | MC724P   | 55p   |
| CA3018          | 72p   | MC1303L  | 130p  |
| CA3020          | 145p  | MC1304P  | 160p  |
| CA3035          | 135p  | MC1310P  | 220p  |
| CA3036          | 90p   | MC1710CG | 55p   |
| CA3046          | 55p   | MFC4000B | 54p   |
| CA3048          | 220p  | MFC6040  | 90p   |
| CA3075          | 150p  | MLM309K  | 158p  |
| CA3081          | 150p  | NE555    | 55p   |
| CA3089E         | 195p  | NE556DB  | 99p   |
| CA3090AQ        | 250p  | NE561    | 304p  |
| CA3123          | 140p  | NE562    | 315p  |
| LM300H          | 170p  | NE567    | 249p  |
| LM301           | 42p   | SL403D   | 150p  |
|                 |       | SL414A   | 150p  |

### BRIDGE RECTIFIERS

| Rectifier | Price | Rectifier | Price |
|-----------|-------|-----------|-------|
| SN78033   | 250p  | 2A100V    | 20p   |
| SN78115   | 200p  | 1A100V    | 20p   |
| TAD100    | 130p  | 1A200V    | 24p   |
| TBA800    | 110p  | 1A400V    | 21p   |
| TBA810    | 150p  | 1A600V    | 22p   |
| ZN414     | 110p  | 1A800V    | 25p   |
|           |       | 2A50V     | 30p   |
|           |       | 3A100V    | 43p   |
|           |       | 3A200V    | 55p   |
|           |       | 3A400V    | 74p   |
|           |       | 3A600V    | 91p   |
|           |       | 5A400V    | 90p   |
|           |       | 7A400V    | 85p   |
|           |       | 7A600V    | 108p  |
|           |       | C106B     | 37p   |
|           |       | TIC44     | 29p   |
|           |       | 2N3525    | 30p   |
|           |       | 2N4444    | 191p  |

### REGULATOR

| Regulator  | Price |
|------------|-------|
| 723C       | 45p   |
| 7805 (TO3) | 150p  |
| 7815 (TO3) | 175p  |
| LM309K     | 185p  |
| MVR12      | 170p  |

### ZENER DIODES

| Zener    | Price |
|----------|-------|
| 2-7V-33V | 315p  |
| 400mW    | 9p    |
| 3-3V-33V | 17p   |
| 1-3V     | 17p   |

### SCR (Thyristors)

| SCR     | Price |
|---------|-------|
| 1A 50V  | 38p   |
| 1A 100V | 42p   |
| 1A 200V | 47p   |
| 1A 400V | 52p   |
| 1A 600V | 70p   |
| 3A 50V  | 38p   |
| 3A 100V | 43p   |
| 3A 200V | 55p   |
| 3A 400V | 74p   |
| 3A 600V | 91p   |
| 5A 400V | 90p   |
| 7A 400V | 85p   |
| 7A 600V | 108p  |
| C106B   | 37p   |
| TIC44   | 29p   |
| 2N3525  | 30p   |
| 2N4444  | 191p  |

### THERMISTORS

| Thermistor | Price |
|------------|-------|
| TBH11      | 135p  |
| TBH12      | 135p  |

### DENCO COILS

Miniature Dual purpose  
Rng. 1-5 B,Y,R,W 60p  
6-7 B,Y,R 58p  
1-5 Green 65p  
MAXI-Q Coil Aerial  
Coil. Range 2-T. Blue 60p  
Transistor Tuning coils  
Rng. 1-5 B,Y,R,W 70p  
IFT 13/14/15 65p each  
IFT 18/465 75p  
TOC 1 70p  
MW F.R. Aerial 70p

### ENAMEL COPPER WIRE

(2oz reel)  
16, 18, 20, 22 SWG 32p P & P  
24, 26, 28, 30 SWG 39p 5p per reel  
32, 34, 36, 40 SWG 48p

### OPTO ELECTRONICS

LED TIL209 (red) with socket 16p  
MINITRON 3015F 7-seg display 100p  
OCP70 40p LED larger 0-2" diam.  
OCP71 85p diam.  
ORP12 58p Red  
ORP61 46p Green, Yellow, Amber & White.  
2N5777 41p only 19p

### FUSES AND HOLDERS

20mm 150mA-5A 3p  
1 1/2" 500mA-15A 3p  
Anti-surge 20mm 100, 250, 500, 800mA, 1A, 1-6, 2, 2.5, 3-15, 5A 7p each

### ALUM. BOXES

with lid  
2 1/2x5 1/2x1 1/2 50p  
4x4x1 1/2 50p  
4x2 1/2x1 1/2 50p  
4x5 1/2x1 1/2 58p  
4x2 1/2x2 50p  
3x2x1 40p  
6x4x2 78p  
7x5x2 1/2 84p  
8x6x3 106p  
10x7x3 122p  
10x4 1/2x3 119p  
12x5x3 129p

### SPEAKERS


# SPARKRITE MK 2

## CAPACITIVE DISCHARGE ELECTRONIC IGNITION KIT

"Sparkrite MK 2" is a high performance, high quality, capacitive discharge, electronic ignition system. Sparkrite completely eliminates problems of the contact breaker. Misfire due to contact breaker bounce is electronically eliminated, contact breaker burn is eliminated, the condition of the contacts is not relevant to the performance of the ignition, and the system is no longer dependent on the dwell period for recharging. Sparkrite will give you: Up to 20% better fuel consumption, instant all weather starting, cleaner plugs—they last up to five times longer without attention; faster acceleration, higher top speed, longer coil and battery life, efficient fuel burning and less air pollution, smoother running, continual peak performance. The Kit comprises everything needed: Ready drilled pressed steel case coated in matt black epoxy resin, ready drilled base and heatsink top quality 5 year guaranteed transformer and components, cables, coil connectors, printed circuit board, nuts, bolts, silicon grease, full instructions to make the kit negative or positive earth, and 10 page installation instructions. WE SAY IT IS THE BEST SYSTEM AT ANY PRICE

Voted best of 8 ignition systems tested by a leading Motoring Magazine

Prices: D.I.Y. assembly kit £10-93 including VAT post and packing. Ready built unit £13-86 including VAT post and packing. (Both to fit all vehicles with coil/distributor ignition up to 3 cylinders.) Switch for instant changeover from "Sparkrite" ignition to conventional ignition £2-79 including VAT post and packing. R.P.M. limiting control £2-42 including VAT post and packing. (Fitted in case on ready built unit dashboard mounting on kit.) We can supply units for any petrol-engined vehicle (boat, motorcycle, etc.) with coil/contact breaker ignition. Details on request. CALL IN AND SEE US FOR A DEMONSTRATION

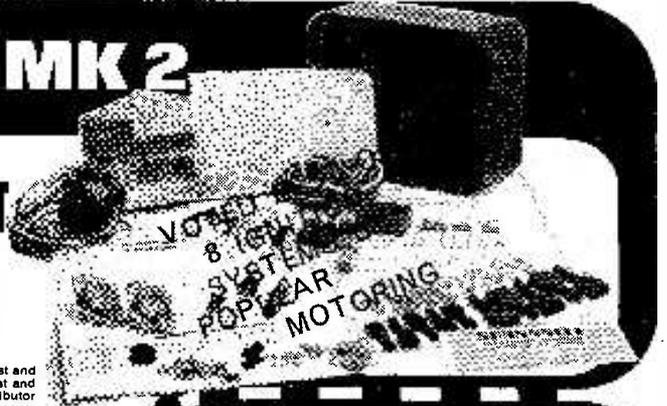

## ORDER NOW

To: Electronics Design Associates Dept. PW1  
82 Bath Street, Walsall, WS1 3DE. Phone 33652

From: Name

Address

Quantity Please Supply

Sparkrite Mk. 2 D.I.Y. Assembly kits at £10-93  
Sparkrite Mk. 2 Ready Built Negative earth at £13-86  
Sparkrite Mk. 2 Ready Built Positive earth at £13-86  
Ignition changeover switches at £2-79  
R.P.M. Limit systems in the above units at £2-42  
Fluorescent light assembly kits at £3-46  
Fluorescent light built units at £4-10  
Diffusers for the above at 59p

of number — aluminium boxes at  
of number — aluminium boxes at  
of number — aluminium boxes at

I enclose cheque/P.O.s for £..... Cheque No.....  
(Send S.A.E. if brochure only required)

## ELECTRONICS DESIGN ASSOCIATES of WALSALL

### ALUMINIUM BOXES

Prices include lids, screws and VAT (at 8%). 18p should be added to the total order value for postage and packing.

|        |              |              |              |               |               |               |               |               |               |
|--------|--------------|--------------|--------------|---------------|---------------|---------------|---------------|---------------|---------------|
| No.    | 7            | 8            | 9            | 10            | 11            | 12            | 13            | 14            | 15            |
| Size   | 7" x 4" x 2" | 8" x 4" x 2" | 9" x 4" x 2" | 10" x 4" x 2" | 11" x 4" x 2" | 12" x 4" x 2" | 13" x 4" x 2" | 14" x 4" x 2" | 15" x 4" x 2" |
| Height | high         | high         | high         | high          | high          | high          | high          | high          | high          |
| Price  | 47p          | 48p          | 49p          | 49p           | 48p           | 38p           | 56p           | 75p           | 93p           |

### FLUORESCENT LIGHT KIT

You can build this reverse polarity protected 12V 8W fluorescent light. Everything needed is supplied: white enamelled drilled metalwork, ready drilled heatsink, printed circuit board, high quality components and transformer, end caps, cable, the fluorescent tube, nuts, bolts, washers and simple assembly and operating instructions. When complete the light has many uses: workshop and workbench illumination, garage lighting, emergency lighting, lighting for camping, and boating, as an inspection lamp and many more.  
Prices: Assembly kit £3-46 inc. VAT post and packing; Ready built £4-10 inc. VAT post and packing. Diffuser 59p inc. VAT post and packing.

## INDEX TO ADVERTISERS

Amib International ... cover iv  
Arbour Electronics Ltd. ... 278  
A.S.P. Ltd. ... 272  
Astro Electronics Ltd. ... 272  
Audio Equipment ... 270  
A.W.R.E. (Ministry of Defence) ... 339

Bamber, B. ... 334  
Barrie Electronics ... 284  
Bentley Acoustic Ltd. ... 325  
Beta Devices ... 338  
B.H. Component Factors Ltd. ... 296  
Bi-Pre-Pak Ltd. ... 273  
Bofin Projects ... 341  
British Institute of Engineering Technology ... 328, 332, 337  
British National Radio & Electronics School ... 268, 270, 295  
J. Bull (Electrical) Ltd. ... 283  
Bug Sound Electronics ... 338

C. Caranna ... 339  
Chromasonic Electronics ... 279  
Codar ... 282  
Colomor (Electronics) Ltd. ... 336  
Combined Precision Equipment ... 282  
Crofton Electronics ... 335  
C.T. Electronics ... cover ii

D.E.W. Ltd. ... 340  
D.J. Electronics ... 334  
Doram Electronics Ltd. ... 291  
Dziubas, M. ... 266

Electroni-Kit ... 296  
Electronic Brokers ... 341  
Electronic Design Associates ... 343  
Electronic Mail Order Ltd. ... 296  
Electrospares ... 266  
Electrovalue Ltd. ... 268  
Elvins ... 328

Everest ... 335  
Foresight Electronics ... 341  
Galleon Trading ... 338  
Greenbank Electronics ... 278  
Greenweld Electronics ... 336

H.A.C. Short-wave Products ... 332  
Harversons Surplus Co. Ltd. ... 277  
Heath (Gloucester) Ltd. ... 284  
Henry's Radio Ltd. ... 278  
H.M. Electronics ... 340  
Holdings Ltd. ... 340

I.L.P. Electronics Ltd. ... 271  
Imperial Trading ... 338 & 339  
Intertext (I.C.S.) ... 340

Juniper Electronics ... 338

Kensington Supplies ... 339  
Keytronics ... 332

Lewis Radio ... 270  
Linear Products Ltd. ... 325  
London Computer Operators Training Centre ... 339  
London Electronic College ... 346  
Lowe Electronics ... 276

Maplin Electronic Supplies ... 269  
Marco Trading ... 338  
Mawson Associates ... 340  
Microelectronics ... 341  
Marshall, A. & Son ... 268  
Minikits Electronics ... 341

Newmart Electronics ... 327

Oliver (P. G.) ... 340

Partridge Electronics Ltd. ... 334  
Pembroke College of Electronics ... 266

RDI Ltd. ... 338  
Radio Book Services ... 340  
Radio Components Specialists ... 280-281  
Radio Exchange Ltd. ... cover iii  
Rivlin Instruments Ltd. ... 328  
R.S.C. (Hi-Fi) Centre Ltd. ... 267  
R.S.T. Valve Mail Order Co. ... 333  
R & TV Components Ltd. ... 274-275  
Riversdale Electronics ... 337

Salop Electronics ... 341  
Saxon Entertainments Ltd. ... 285  
S.I.G.A. Electronics Ltd. ... 336  
Simtech Engineering Ltd. ... 339  
Sinclair Radionics Ltd. ... 331  
Sintel ... 341  
Studio Electronics ... 272  
Surpletronics ... 335  
Swanley Electronics ... 292

Technomatic Ltd. ... 344  
Teleradio Electronics ... 341  
Toner Electronics ... 332  
Trampus Electronics Ltd. ... 276  
Tweedy (J. & A.) ... 338

Vero Electronics ... 278

Watford Electronics ... 342  
West London Direct Supplies ... 335  
Wilmslow Audio ... 292

Z & I Aero Services ... 344


Head Office and Warehouse  
44A WESTBOURNE GROVE  
LONDON W2 5SF  
Tel: 727 5641/2/3

# Z & I AERO SERVICES LTD.

Retail Shop  
85 TOTTENHAM COURT ROAD  
LONDON W1  
Tel: 580 8403  
Open all day Saturday


Please send all correspondence and Mail-Orders to Head Office

## MULTIMETERS

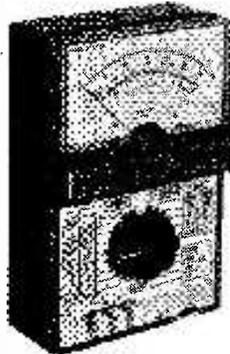

**AC/DC MULTIMETER TYPE U4324**  
33 ranges covering  
D.C. current  
60µA to 3A;  
AC current  
300µA—3A;  
DC voltage: 0.6—  
1200V  
AC voltage: 3—  
900V  
Resistance:  
500Ω—500kΩ  
Level: -10 to  
+12db  
Sensitivity:  
20,000 o.p.v. DC.  
4,000 o.p.v. A.C.

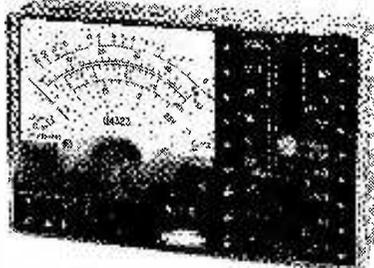Instrument is powered by re-chargeable nickel cadmium batteries.  
**PRICE £9.85\***



**AC/DC MULTIMETER TYPE U4323**  
Apart from usual multimeter facilities the instrument incorporates fixed frequency Audio (1kHz) and I.F. (465kHz) Oscillators. 22 ranges covering AC Voltage 2.5-1000V; D.C. Voltage 0.5-1000V; D.C. current 50µA to 500µA and resistance 0 to 1MΩ. Sensitivity 20,000 o.p.v. Oscillator output voltage—1V minimum.  
**PRICE: £8.00**

## LINEAR INTEGRATED CIRCUITS

— Please note reductions in prices —

**Mullard TAA263.** Direct coupled three stage low level amplifier for use from DC to 600 kc/s. Supply voltage 6-8v. Typical power gain 77 db into 150Ω load. Output power 10mW. TO72 four-lead encapsulation **£0.65\***

**Mullard TAA293.** Medium frequency amplifier with frequency response of 600kc/s. Nominal supply voltage 6v. Typical power gain 89db. Maximum power dissipation 160 mW. Power output 10 mW into 150Ω load. TO74 ten lead-encapsulation **£0.65\***

**Mullard TAA320.** Metal oxide silicon low frequency pre-amplifier consisting of a MOST stage followed by a bi-polar transistor. Gate to source voltage 9-14v. Total power dissipation 200 mW. Drain current 1 µA. Output conductance 0.65 mmho. TO18 3-lead encapsulation **£0.60\***

**Type 741 Operational Amplifiers,** 8-dual-in-line encapsulation **£0.30\***


## L.E.D. TYPE HP5082/4850

Red Light GASP Light Emitting Diodes giving bright diffused light of 0.8 mcd at forward voltage of 1.6V and DC current of 20 mA. Plastic wide angle lens 0.200in. diameter. Ideal for panel lights, etc.  
Price for 12 pieces **£1.75** incl. VAT and p.&p

OUR NEW 1975 ILLUSTRATED CATALOGUE/PRICE LIST covering VALVES, TUBES, SEMICONDUCTORS, PASSIVE COMPONENTS AND TEST EQUIPMENT IS NOW READY. PLEASE SEND **£0.20** FOR YOUR COPY.

\* ALL PRICES EXCLUSIVE OF V.A.T. WHEN REMITTING CASH WITH ORDER PLEASE ADD **£0.50** PER MULTIMETER AND **£0.15** IN £ FOR OTHER ITEMS—SUBJECT TO A MINIMUM CHARGE OF **£0.20**—TO COVER HANDLING AND POSTAGE. NO C.O.D. ORDERS ACCEPTED.

|  |   |   |   |   |  |   |  |  |
|--|---|---|---|---|--|---|--|--|
| 7400 13p<br>7401 14p<br>7402 14p<br>7403 16p<br>7404 16p<br>7405 14p<br>7406 36p<br>7407 36p<br>7408 16p<br>7409 16p<br>7410 13p<br>7411 20p<br>7412 20p<br>7413 32p<br>7414 60p<br>7416 30p<br>7420 14p<br>7422 25p<br>7423 27p<br>7425 30p<br>7427 37p<br>7430 14p<br>7432 25p<br>7437 27p<br>7440 16p<br>7441 65p<br>7442 65p<br>7447 75p<br>7448 70p               | 7450 15p<br>7451 16p<br>7453 16p<br>7454 22p<br>7460 15p<br>7470 30p<br>7472 25p<br>7473 32p<br>7474 32p<br>7475 45p<br>7476 32p<br>7480 65p<br>7481 84p<br>7482 76p<br>7483 84p<br>7484 90p<br>7485 120p<br>7486 34p<br>7489 270p<br>7490 40p<br>7491 80p<br>7492 50p<br>7493 40p<br>7494 75p<br>7495 64p<br>7496 72p<br>74107 35p<br>74121 30p          | 74122 45p<br>74123 68p<br>74141 85p<br>74145 95p<br>74151 72p<br>74153 76p<br>74154 150p<br>74155 72p<br>74156 72p<br>74160 99p<br>74161 99p<br>74162 99p<br>74163 99p<br>74164 120p<br>74165 120p<br>74174 120p<br>74175 85p<br>74180 100p<br>74181 300p<br>74182 82p<br>74185 135p<br>74190 155p<br>74191 155p<br>74192 120p<br>74193 120p<br>74195 75p<br>74198 200p<br>74199 190p | <b>LINEAR I.C.'s</b><br>CA3048 Transistor Array 50p<br>CA3048 4 Independent Amplifiers 230p<br>ICL8038CC VCO Fun. Gen. 14 pin DIL 275p<br>ICL8038BC VCO Fun. Gen. 14 pin DIL 5.50p<br>LM301A Op. Amp. with ext. comp. 36p<br>LM380 Audio Amplifier 90p<br>LM381 Stereo Pre Amp. 150p<br>LM3900 Quad Op. Amp. 70p<br>MC1310 Colless FM Stereo Dec. 225p<br>MC1312 SQ Quadraphonic Dec. 1130p<br>MC1314 1W Audio Amp. 57p<br>MFC4000 Electronic Attenuator 90p<br>NE536 FET Op. Amp. 250p | NE555 Timer 8 pin DIL 45p<br>NE556 Dual 555/14 Pin DIL 100p<br>NE560 PLL 16 Pin DIL 325p<br>NE561 PLL with AM Demod. 16 Pin 325p<br>NE562 PLL with VCO 16 Pin 325p<br>NE563 PLL FM/IF Demod. 16 Pin DIL 300p<br>NE565 PLL 14 Pin DIL 325p<br>NE566 Fun. Gen. 8 Pin DIL 220p<br>NE567 PLL Tone Decoder 8 Pin DIL 250p<br>TBA570 AM/FM Radio receiver 160p<br>TBA800 5 Watt Audio Amp. 90p<br>TBA810 7 Watt Audio Amp. 100p<br>TBA820 2 Watt Audio Amp. 80p<br>ZN414 TRF Radio Receiver 110p<br>Data sheets on above I.C.'s 10p each. | <b>Popular Op Amps</b><br>709 ext. comp. 8/14 pin DIL 30p<br>710 Diff. Comp. 14 pin DIL 45p<br>741 int. comp. 8 pin DIL 25p<br>747 Dual 741 14 pin DIL 70p<br>748 ext. comp. 8 pin DIL 38p<br>5001 12 Digit Calculator Chip 28 pin DIL 485p<br>PC Keyboard 0-9, decimal, 4 function, C, K, keys. Size: 2-36" x 3-76" x 0-45" 400p<br><b>DIL SOCKETS BY TEXAS.</b><br>8 pin 13p, 14 pin 14p, 16 pin 15p |   |  |  |
| 7400 13p<br>7401 14p<br>7402 14p<br>7403 16p<br>7404 16p<br>7405 14p<br>7406 36p<br>7407 36p<br>7408 16p<br>7409 16p<br>7410 13p<br>7411 20p<br>7412 20p<br>7413 32p<br>7414 60p<br>7416 30p<br>7420 14p<br>7422 25p<br>7423 27p<br>7425 30p<br>7427 37p<br>7430 14p<br>7432 25p<br>7437 27p<br>7440 16p<br>7441 65p<br>7442 65p<br>7447 75p<br>7448 70p               | 7450 15p<br>7451 16p<br>7453 16p<br>7454 22p<br>7460 15p<br>7470 30p<br>7472 25p<br>7473 32p<br>7474 32p<br>7475 45p<br>7476 32p<br>7480 65p<br>7481 84p<br>7482 76p<br>7483 84p<br>7484 90p<br>7485 120p<br>7486 34p<br>7489 270p<br>7490 40p<br>7491 80p<br>7492 50p<br>7493 40p<br>7494 75p<br>7495 64p<br>7496 72p<br>74107 35p<br>74121 30p          | 74122 45p<br>74123 68p<br>74141 85p<br>74145 95p<br>74151 72p<br>74153 76p<br>74154 150p<br>74155 72p<br>74156 72p<br>74160 99p<br>74161 99p<br>74162 99p<br>74163 99p<br>74164 120p<br>74165 120p<br>74174 120p<br>74175 85p<br>74180 100p<br>74181 300p<br>74182 82p<br>74185 135p<br>74190 155p<br>74191 155p<br>74192 120p<br>74193 120p<br>74195 75p<br>74198 200p<br>74199 190p | <b>VOLTAGE REGULATORS (PLASTIC)</b><br>723 1amp +Ve -Ve<br>5v 7805 140p 7905 250p<br>12v 7812 140p 7912 250p<br>15v 7815 140p 7915 250p<br>18v 7818 140p 7918 250p<br>24v 7824 140p 7924 250p<br>Data Sheets on Vol. Regs. 10p each   | <b>SCR-THYRISTORS</b><br>50v 100v 400v 600v<br>1A 40p 42p 50p 70p<br>3A 43p 49p 75p 100p<br>7A — 80p 84p —<br>16A — 160p 190p —<br>Other<br>BT106 140p, C106D 55p, MCR101 25p<br>BR100 BI-DIRECTIONAL TRIGGER FOR SCR's and TRIACS ... 21p  | <b>Other</b><br>2N3225 91p<br>2N4444 185p<br>2N5060 40p<br>2N5062 45p<br>2N5064 50p<br><b>TRIACS</b><br>100V 400V 500V<br>3A 85p 95p 120p<br>6A 88p 120p 150p<br>10A 109p 154p 165p<br>15A 145p 180p 205p<br>Other<br>40430 90p, 40486 98p, 40669 95p  |   |  |  |
| Transistors<br>AC126/7 11p<br>AC128 11p<br>AC176 11p<br>AC187 12p<br>AC188 11p<br>AD149 43p<br>AD161 36p<br>AD162 36p<br>AF114/5 13p<br>AF116/7 13p<br>AF139 33p<br>AF239 40p<br>BC107/8 9p<br>BC109 10p<br>BC109C 12p<br>BC147/8 7p<br>BC149 9p<br>BC157 10p<br>BC158 8p<br>BC159 9p<br>BC169C 12p<br>BC177 18p<br>BE178 17p<br>BC179 18p<br>BC182/3 10p<br>BC184 11p | BC212 11p<br>BC213 10p<br>BC214 13p<br>BD115 55p<br>BD124 75p<br>BD131 42p<br>BD132 45p<br>BF115 25p<br>BF167 25p<br>BF173 25p<br>BF184 22p<br>BF194 11p<br>BF195 12p<br>BF198 14p<br>BF197 12p<br>BFR39/7 28p<br>BFR29/30 30p<br>BFX84/5 25p<br>BFX87/8 24p<br>BFY50/1/2<br>BRY39 34p<br>MJE340 45p<br>MJE295 99p<br>MJE305 88p<br>MPS06 58p<br>OC26 47p | OC28 55p<br>OC35 48p<br>OC36 52p<br>OC41/2 15p<br>OC44/5 11p<br>OC70/1/2 11p<br>OC81/2 12p<br>OC83/4 28p<br>TIP295 75p<br>TIP41A 65p<br>TIP42A 75p<br>ZTX300 15p<br>ZTX500 15p<br>2N697 11p<br>2N698 30p<br>2N706 12p<br>2N708 12p<br>2N930 15p<br>2N1131/2 17p<br>2N1302/3 17p<br>2N1304/5 21p<br>2N1306/7 28p<br>2N1308/9 28p<br>2N1613 20p<br>2N1711 20p<br>2N1893 27p             | 2N2219 20p<br>2N2221/2 20p<br>2N2369 14p<br>2N2484 30p<br>2N2904 20p<br>2N2905 18p<br>2N2926RB 8p<br>2N2926O 8p<br>2N2926Y 8p<br>2N3053 18p<br>2N3054 45p<br>2N3055 50p<br>2N3442 140p<br>2N3702/3 11p<br>2N3704/5 11p<br>2N3706/7 11p<br>2N3708/9 9p<br>2N3772 161p<br>2N3773 220p<br>2N3903/4 15p<br>2N3905/6 15p<br>2N4058 15p<br>2N4060 13p<br>2N4289 18p<br>40361 43p<br>40362 45p   | 40594 75p<br>40595 85p<br><b>UJTS</b><br>TIS43 27p<br>2N2160 70p<br>2N2646 37p<br>2N4781 30p<br><b>FETS</b><br>BF244 36p<br>MPF102/3 30p<br>MPF104/5 30p<br>2N3819 22p<br>2N3820 57p<br>2N3823 50p<br>2N5457 30p<br>2N5458 30p<br>2N5459 30p<br><b>MOSFETS</b><br>40603 58p<br>40673 58p<br>3N128 75p<br>3N140 85p<br>3N141 75p   | <b>DIODES</b><br>BY100 15p<br>BY126 12p<br>BY127 12p<br>OA47 7p<br>OA70 8p<br>OA79 7p<br>OA81 7p<br>OA85 8p<br>OA90 6p<br>OA91 6p<br>OA95 7p<br>OA200 6p<br>OA202 7p<br>IN914 4p<br>IN4001 5p<br>IN4004 5p<br>IN4007 7p<br>IN4148 4p   | <b>ZENERS</b><br>3-3V to 33V<br>400mW — 9p<br>1W — 18p<br><b>Tunnel</b><br>AEEY11 50p<br><b>Varicap</b><br>BB105 30p<br><b>Noise</b><br>ZIJ 90p<br>Mica + 2 bushes for TO3 & TO6 5p | <b>C-MOS I-C's</b><br>CD4000AE 18p<br>CD4001AE 19p<br>CD4002AE 19p<br>CD4009AE 67p<br>CD4011AE 21p<br>CD4013AE 63p<br>CD4016AE 63p<br>CD4017AE 163p<br>CD4018AE 229p<br>CD4022AE 168p<br>CD4023AE 21p<br>CD4024AE 116p<br>CD4027AE 91p<br>CD4028AE 140p<br>CD4029AE 196p<br>CD4046AE 202p<br>CD4047AE 137p<br>CD4049AE 63p<br>CD4054AE 196p<br>CD4055AE 196p<br>CD4060AE 229p<br>CD4071AE 26p<br>CD4081AE 26p<br>CD4510AE 120p<br>CD4511AE 250p<br>CD4528AE 120p | <b>OPTO-ELECTRONICS</b><br>ORP12 50p OCP70 30p<br>ORP60 80p OCP71 90p<br>ORP61 60p 2N5777 40p<br><b>LEDS</b><br>TIL209 Red 16p<br>TIL211 Green 35p<br><b>SEVEN SEGMENT DISPLAYS</b><br>3015F 0-35 in DIL 120p<br>LIT704 0-33 in DIL 130p<br>LIT707 0-33 in DIL 135p<br>LIT747 0-63 in DIL 210p<br><b>MAN-3M</b><br>0-127 in 100p<br>MAN-4 0-19 in DIL 180p |
| Minimum order £2. P & P 20p. MAIL ORDER ONLY<br>Please add VAT as shown Govt., Colleges, etc, orders welcome   |   | <b>TECHNOMATIC LTD.</b>   |   | 54 SANDHURST ROAD,<br>LONDON, NW9<br>Tel. 01-204 4333   |  |   |  |  |

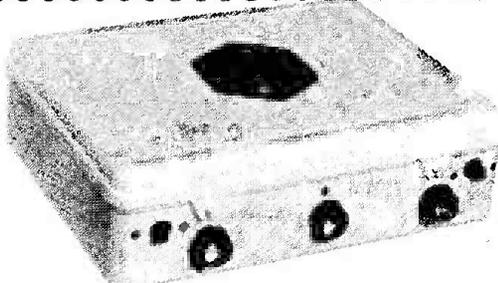

# NEW EDU-KIT MAJOR

Completely Solderless Electronic Construction Kit  
Build these projects without soldering iron or solder

- ★ 4 Transistor Earpiece Radio.
- ★ Signal Tracer.
- ★ Signal Injector
- ★ Transistor Tester NPN-PNP.
- ★ 4 Transistor Push Pull Amplifier.
- ★ 5 Transistor Push Pull Amplifier.
- ★ 7 Transistor Loudspeaker Radio MW/LW.
- ★ 5 Transistor Short Wave Radio.
- ★ Electronic Metronome.
- ★ Electronic Noise Generator.
- ★ Batteryless Crystal Radio.
- ★ One Transistor Radio.
- ★ 2 Transistor Regenerative Radio.
- ★ 3 Transistor Regenerative Radio.
- ★ Audible Continuity Tester
- ★ Sensitive Pre-Amplifier.


## Total Building Costs

**£7-23** PP Ins. 45p  
(Overseas Seamail P & P £2-35)  
(+25% VAT £1-80)

Components Include: 24 Resistors ● 21 Capacitors ● 10 Transistors ● 3 1/2" Loudspeaker ● Ear-piece ● Mica Baseboard ● 3 12-way connectors ● 2 Volume controls ● 2 Slider Switches ● 1 Tuning Condenser ● 3 Knobs ● Ready Wound MW/LW/SW Coils ● Ferrite Rod ● 6 1/2 yards of wire ● 1 Yard of sleeving etc. ● Parts Price List and Plans 55p free with parts.

## NEW ROAMER NINE

WITH V.H.F. INCLUDING AIRCRAFT

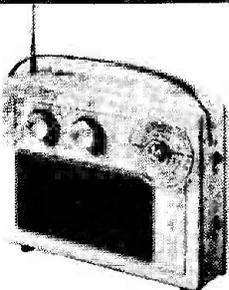


Nine Transistors, 9 Tuneable wavebands as Roamer Ten. Built in ferrite rod aerial for MW/LW. Retractable chrome-plated telescopic aerial for VHF and SW. Push Pull output using 600 mW transistors. 9 Transistors and 3 diodes, tuning condenser with V.H.F. section, separate coil for aircraft, moving coil loudspeaker, volume ON/OFF and wavechange controls. Attractive all white case with red grille and carrying strap. Size 9 1/2" x 7" x 2 1/2" approx. Parts Price List and Plans free with parts.

**Total Building Costs £6-95** PP & Ins. 44p  
(Overseas Seamail P & P £2-35)  
(+25% VAT £1-75)
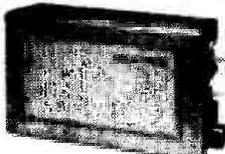
## POCKET FIVE

NOW WITH 3" LOUD-SPEAKER

3 Tunable wavebands, M.W., L.W. and Trawler Band, 7 stages, 5 transistors and 2 diodes; supersensitive ferrite rod aerial, attractive black and gold case. Size 5 1/2" x 1 1/2" x 3 1/2" approx. Plans and Parts Price List free with parts.



**Total Building Costs £2-50** PP & Ins. 36p  
(Overseas Seamail P & P £1-70)  
(+25% VAT 62p)



## TRANSONA FIVE NOW WITH 3" LOUDSPEAKER


Wavebands, transistors and speaker as Pocket Five. Larger Case with Red Speaker Grille and Tuning Dial. Plans and Parts Price List free with parts.

**Total Building Costs £3-20** PP & Ins. 36p  
(Overseas Seamail P & P £1-70)  
(+25% VAT 80p)
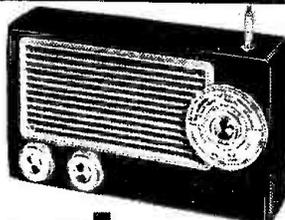
## TRANS EIGHT 8 TRANSISTORS and 3 DIODES

6 Tuneable Wavebands: MW, LW, SW1, SW2, SW3 and Trawler Band. Sensitive ferrite rod aerial for M.W. and L.W. Telescopic aerial for Short Waves. 3in. Speaker. 8 improved type transistors plus 3 diodes. Attractive case in black with red grille, dial and black knobs with polished metal inserts. Size 9 x 5 1/2 x 2 1/2 in. approx. Push pull output. Battery economiser switch for extended battery life. Ample power to drive a larger speaker. Parts price list and plans free with parts.

**Total building costs £4-78** PP & Ins. 40p  
(Overseas Seamail P & P £2-00)  
(+25% VAT £1-20)



## ROAMER SIX

CASE AND LOOKS AS TRANS-EIGHT

6 Tuneable Wavebands: MW, LW, SW1, SW2, SW3 and Trawler Band plus an extra Medium waveband for easier tuning of Luxembourg, etc. Sensitive ferrite rod aerial and telescopic aerial for Short Waves. 3in. Speaker. 8 stages—6 transistors and 2 diodes. Attractive black case with red grille, dial and black knobs with polished metal inserts. Size 9 x 5 1/2 x 2 1/2 in. approx. Plans and parts price list free with parts.

**Total building costs £4-38** (Overseas Seamail P & P £2-00)  
(+25% VAT £1-10)

## NEW Everyday Series

Build this exciting New series of designs

E.V.5. 5 Transistors and 2 diodes. MW/LW. Powered by 4 1/2 volt Battery. Ferrite rod aerial, tuning condenser, volume control, and now with 3" loudspeaker. Attractive case with red speaker grille. Size 9" x 5 1/2" x 2 1/2" approx. Parts Price List and Plans free with parts.

**Total Building Costs £3-40** PP & Ins. 36p  
(Overseas Seamail P & P £1-70)  
(+25% VAT 85p)

E.V.6. Case and looks as above. 6 Transistors and 3 diodes. Powered by 9 volt battery. Ferrite rod aerial, 3" loudspeaker, etc., MW/LW coverage. Push Pull output. Parts Price List and Plans free with parts.

**Total Building Costs £3-60** PP & Ins. 36p  
(Overseas Seamail P & P £1-70)  
(+25% VAT £1-00)

E.V.7. Case and looks as above. 7 Transistors and 3 diodes. Six wavebands. MW/LW, Trawler Band, SW1, SW2, SW3, powered by 9 volt battery. Push Pull output. Telescopic aerial for short waves. 3" Loudspeaker. Parts Price List and Easy Build Plans free with parts.


**Total Building Costs £4-48** PP & Ins. 38p  
(Overseas Seamail P & P £2-00)  
(+25% VAT £1-12)

## ROAMER EIGHT Mk I

NOW WITH VARIABLE TONE CONTROL

7 Tuneable Wavebands: MW1, MW2, LW, SW1, SW2, SW3 and Trawler Band. Built in Ferrite Rod Aerial for MW and LW. Chrome plated Telescopic aerial can be angled and rotated for peak short wave listening. Push pull output using 800mW transistors. Car aerial and Tape record sockets. Selectivity switch. 8 transistors plus 3 diodes. Latest 4" 2 watt ferrite magnet loudspeaker. Air spaced ganged tuning condenser. Volume/on/off, tuning wave change and tone controls. Attractive case in rich chestnut shade with gold blocking. Size 9 x 7 x 4in. approx. Easy to follow instructions and diagrams. Parts price list and plans free with parts.

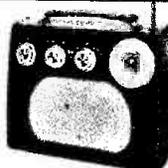**Total building costs £6-98** PP & Ins. 65p  
(Overseas Seamail P & P £3-50)  
(+25% VAT £1-75)




## ROAMER TEN Mk 2

WITH VHF INCLUDING AIRCRAFT

Now with free earpiece and switched socket. 10 Transistors. Latest 4" 2 watt Ferrite Magnet Loudspeaker. 9 Tuneable Wavebands, MW1, MW2, LW, SW1, SW2, SW3, Trawler Band, VHF and Local Stations also Aircraft Band.

Built in Ferrite Rod Aerial for MW/LW. Chrome plated 6 section Telescopic Aerial, can be angled and rotated for peak short wave and VHF listening. Push Pull output using 800mW Transistors. Car Aerial and Tape Record Sockets. 10 Transistors plus 3 Diodes. Ganged Tuning Condenser with VHF section. Separate coil for Aircraft Band. Volume on/off. Wave Change and tone Controls. Attractive Case in black with silver blocking. Size 9" x 7" x 4". Easy to follow instructions and diagrams. Parts price list and plans 50p free with parts.

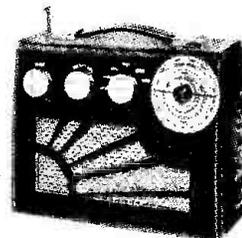**(Total building costs Overseas Seamail P & P £9-50)** PP & Ins. 65p  
(+25% VAT £2-37)



## "EDU-KIT"

Build Radios, Amplifiers, etc. from easy stage diagrams.

Five units including master unit to construct

Components include:

Tuning Condenser: 2 Volume Controls: 2 Slider Switches: Fine Tone 3" Moving Coil Speaker: Terminal Strip: Ferrite Rod Aerial: Battery Clips: 4 Tag Boards: 10 Transistors: 4 Diodes: Resistors: Capacitors: Three 1/2" Knobs. Units once constructed are detachable from Master Unit, enabling them to be stored for future use. Ideal for Schools, Educational Authorities and all those interested in radio construction. Parts price list and plans free with parts.

**Total building costs £5-50** PP & Ins. 35p  
(Overseas Seamail P & P £2-35)  
(+25% VAT £1-37)

★ Callers side entrance "Lavells" shop.  
★ Open 10-1, 2.30-4.30, Mon.-Fri. 9-12 Sat.

To RADIO EXCHANGE CO., 61a HIGH STREET, BEOFORD, MK40 1SA  
Tel.: 0234 52367. Reg. No. 788372.

I enclose £..... for .....

Name .....

Address .....

(Dept. PW8.)

# the wireless tecknowledgedgy page

Pure Wireless has been the Cinderella of electronic component supplies for some time now. Things like coils, ceramic and mechanical filters, linear phase arrays, complete IF systems and tuners haven't been available from a single source until now. We call it the Ambit 'One stop Wireless Service'.

## Join the Wireless Set with ambit.

### Apollo / The All electric Wireless Set

Ambit carries all the parts for the Apollo project, please send an SAE for free list of components. Components and PCB for complete AM module as described in part one of the series £8.00.  
 Rivlin WS150 long slider potentiometer £3.00  
 IMI 6 button preset bank for varicaps £3.40  
 MVAM1 £2.75, MVAM2 £1.05, CA3123EE1.40- see price list for other items.

91200 - Double linear phase filter FM IF strip with muting, meter output etc. £9.00 (built) or £6.20 in kit form.

91310 - Stereo decoder module with pilot tone filter and LED beacon. £5.10 (built) £4.40 (kit)

EC3302 - Varicap tunerhead with AFC £5.00 to suit the CA3089E/TDA1200/HA1137 IF system.

EF5603 - The top quality varicap tunerhead, with 5 tuned circuits, double varicaps, fully moulded VHF coils, MOSFET RF stage. £8.80.

7252 - Larsholt Electronics varicap tuned FM radio receiver module - antenna to audio, with mute, meter drive, AGC, AFC, double varicap front end. Built, tested. £20.00.

7254 - A new tunerset, combining a four stage varicap tuned head, with an IF and PLL stereo decoder. The features include muting, AFC, meter drive, beacon drive. Built and tested £24.00.

EC720 - A new varicap tuned MW radio module, with built in audio stage, and positive bias tuning. Built and tested £10.50. Kit price £8.00.

### Meters for wireless and audio equipment:

We supply meters scaled for frequency, and relative signal amplitude; mostly low cost edgewise types.

### Components for wireless/consumer electronics.

In order to manufacture our wide range of wireless and audio products, we use many types of top quality ICs, coils, filters, transistors etc. So when you buy from AMBIT, you are assured of the experience of a user, not just a seller. It also means that our catalogue contains more useful applications ideas and hints than most. Get yours now. Please note that we sell no seconds, all our ICs are branded types, tested by the manufacturers.

*We are prepared to undertake custom projects, and also modification to our existing range to suit particular customer requirements. But please note that the minimum project fee, payable in advance, is £25.00.*

Please note that we cannot deal with any enquiries unless accompanied with a stamped addressed envelope of adequate dimensions. Thankyou.

EF5603 £8.40



A major aspect of our 'one stop' wireless facility revolves around Ambit's association with TOKO - the world's largest coil and filter manufacturer.

*As the major source of TOKO information and products in the UK and European consumer electronics market: AMBIT is also pleased to supply and advise professional and OEM buyers. Please ensure that your enquiry is directed to the 'OEM Division'.*



Illustrated here are various TOKO items, ranging from delay lines, through the famous MFH mechanical filters to the varicap tuner-heads, EF5603, EC3302.



EC3302 £5.00




RET delay line POA




7BA choke  
1µH to 1mH 15p



Variable capacitors

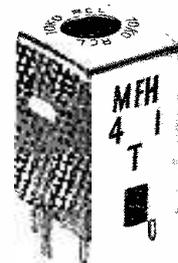

MFH £1.45

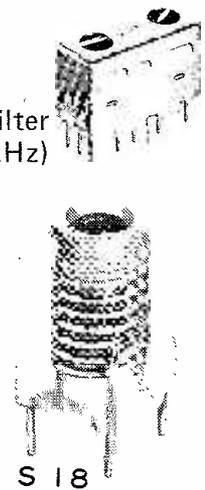

CFT AM ceramic filter  
45p (455 or 470 kHz)

# ambit international

CWO please. Prices Exclude VAT. P&P now 20p. Min.order £1.00. Min Invoice £7.50. Catalogue 40p shortform price list free with SAE

37 High Street, Brentwood, Essex. CM14 4RH. tel. 216029 tlx. 995194