

PRACTICAL WIRELESS

SEPTEMBER
1975


30p

pw
'Easybuild'

also: TELE-TENNIS:-
Electronic Scoring Unit

Miniaturised Equipment
for the 2m band
Part-1

ELECTRONIC
CLOCK

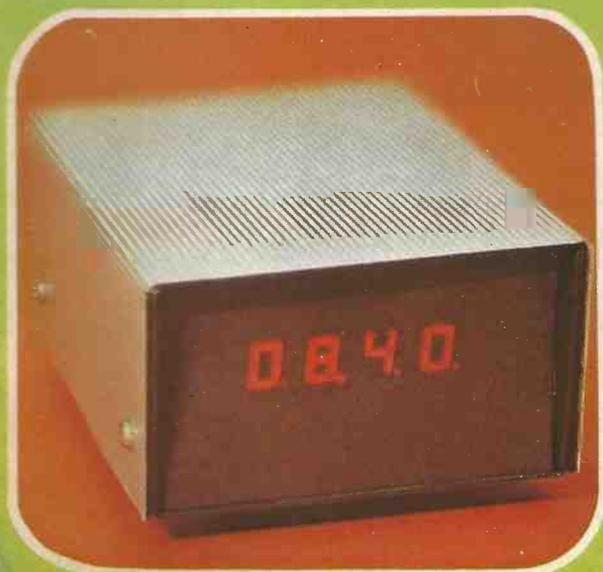

WITH OPTIONAL 4-RANGE TIMER

CHROMASONIC electronics

Dept 3 56, Fortis Green Road,
Muswell Hill, London, N10 3HN.
telephone: 01-883 3705

C-MOS

74 TTL

LINEAR I.C.'s

| C-MOS | | | 74 TTL | | | LINEAR I.C.'s | | | | | | | | | |
|----------|-------|--------|--------|-------|-------|---------------|-------|----------------------|-------|----------------------|-------|-----------------|-------|---------------------|-------|
| 1-24 | 25-99 | 100up | 1-24 | 25-99 | 100+ | | | | | | | | | | |
| CD4000AE | 23p | 19p | 15p | 7400 | 14p | 12p | 10p | 555 (8 pin dip) V | 55p | 7824UC (TO-220) | £1.72 | MC1303L | £1.84 | SN76003S | £3.30 |
| CD4001AE | 23p | 19p | 15p | 7401 | 14p | 12p | 10p | 555 (TO-99) T | 81p | ICL8038 | £3.52 | MC1306P | 80p | SN76013N | £1.88 |
| CD4002AE | 23p | 19p | 15p | 7402 | 14p | 12p | 10p | 556 (14 pin dip) | £1.29 | AY-1-0212 | £6.93 | MC1310P | £2.38 | SN76023N | £1.98 |
| CD4006AE | £1.59 | £1.33 | £1.06 | 7403 | 15p | 12p | 10p | 703 (RF/IF Amp) | £1.33 | AY-1-5051 | £1.44 | MC1314 | £4.13 | SN76227N (MC1327) | £1.89 |
| CD4007AE | 23p | 19p | 15p | 7404 | 16p | 13p | 11p | 708 (8 pin dip) | 38p | AY-5-1224 | £3.95 | MC1315 | £4.62 | SN76532N | £1.88 |
| CD4008AE | £1.75 | £1.46 | £1.17 | 7408 | 16p | 13p | 11p | 709 (TO-99) | 45p | AY-5-3507 | £6.59 | MC1327 | £1.12 | SN76544N | £1.81 |
| CD4009AE | Use | CD4049 | | 7409 | 16p | 13p | 11p | 709 (14 pin dip) | 45p | AY-5-4007 | £7.94 | MC1330P | £1.52 | SN76550-2 (TAAS550) | 89p |
| CD4010AE | Use | CD4050 | | 7410 | 16p | 13p | 11p | 710 (8 pin dip) | 39p | BHA0002 | £3.01 | MC1350 | 64p | SN76552-2 | 81p |
| CD4011AE | 23p | 19p | 15p | 7413 | 27p | 24p | 20p | 710 (TO-99) | 45p | CA2111 | £1.19 | MC1351 | 88p | SN76660N (TBA120) | 75p |
| CD4012AE | 23p | 19p | 15p | 7417 | 27p | 22p | 20p | 710 (14 pin dip) | 44p | CA3045 | £1.69 | MC1352 | 98p | SN76660N (CA3065) | £1.12 |
| CD4013AE | 69p | 58p | 46p | 7420 | 16p | 13p | 11p | 711 (TO-99) | 51p | CA3046 | 85p | MC1357 | £1.52 | TAA263 | £1.50 |
| CD4014AE | £1.75 | £1.46 | £1.17 | 7427 | 27p | 22p | 18p | 711 (14 pin dip) | 44p | CA3053 | 59p | MC1358 (CA3065) | £1.16 | TAA300 | £2.16 |
| CD4015AE | £1.75 | £1.46 | £1.17 | 7430 | 16p | 13p | 11p | 720 (A.M. Radio) | 72p | CA3065 | £1.60 | MC1375 | £1.82 | TAA310A | £1.87 |
| CD4016AE | 69p | 58p | 46p | 7432 | 27p | 22p | 18p | 723 (TO-99) | £1.76 | CA3075 | £1.64 | MC1455 (555T) | 62p | TAA320 | £1.44 |
| CD4017AE | £1.75 | £1.46 | £1.17 | 7437 | 27p | 22p | 18p | 741 (8 pin dip) | 36p | CA3078 | £1.26 | MC1456G | £1.65 | TAA330 | £2.43 |
| CD4018AE | £2.51 | £2.09 | £1.67 | 7441 | 75p | 62p | 50p | 741 (14 pin dip) | £1.04 | CA3089 | 59p | MC1458CPI | 84p | TAA350 | £3.40 |
| CD4019AE | 80p | 66p | 53p | 7442 | 75p | 62p | 50p | 742 (8 pin dip) | 74p | CA3081 | £1.86 | MC1468CPI | £2.18 | TAA370 | £3.40 |
| CD4020AE | £1.97 | £1.64 | £1.31 | 7445 | 85p | 71p | 57p | 741 (TO-99) | 43p | CA3082 | £1.86 | MC1495L | £4.24 | TAA550 | 75p |
| CD4021AE | £1.75 | £1.46 | £1.17 | 7447 | 95p | 83p | 67p | 741 (14 pin dip) | £1.04 | CA3089E (TDA1200) | £1.43 | MC1496G | 96p | TAA570 | 72p |
| CD4022AE | £1.83 | £1.53 | £1.22 | 7447A | 95p | 83p | 67p | 742 (8 pin dip) | 42p | CA3097E | £2.43 | MC1502P | £1.50 | TAA700 | £5.03 |
| CD4023AE | 23p | 19p | 15p | 7448 | 85p | 71p | 57p | 748 (8 pin dip) | 42p | CA3123E | £1.76 | MC3401P | 74p | TBA1205 | £1.25 |
| CD4024AE | £1.26 | £1.05 | 84p | 7470 | 30p | 25p | 20p | 748 (TO-99) | 51p | CA3401E (LM3900) | £5.34 | MFC4000B | 87p | TBA231 | £1.02 |
| CD4025AE | £2.79 | £2.33 | 19p | 7472 | 25p | 21p | 17p | 748 (14 pin dip) | £1.08 | CA3600E | £1.44 | MFC4060A | 79p | TBA281 (723) | £2.52 |
| CD4026AE | £2.79 | £2.33 | 19p | 7473 | 25p | 21p | 17p | 753 (F.M. 1st. I.F.) | £1.39 | CA397E | £1.63 | MFC6030A | 79p | TBA500Q | £3.16 |
| CD4027AE | 98p | 82p | 65p | 7474 | 35p | 29p | 21p | 75491 | 88p | CA3989 | 59p | MFC6040 | £1.86 | TBA520Q | £3.85 |
| CD4028AE | £1.53 | £1.28 | £1.02 | 7475 | 47p | 39p | 31p | 75492 | £1.10 | LO05T1 (TO-3) | £1.46 | MMS314 | £4.80 | TBA540Q | £3.72 |
| CD4029AE | £1.12 | £1.76 | £1.41 | 7476 | 32p | 26p | 21p | Regulators 100mA | | LO36T1 (TO-3) | £1.46 | MMS316 | £9.99 | TGA550Q | £5.29 |
| CD4030AE | 71p | 59p | 47p | 7482 | 75p | 62p | 50p | 78105WC (TO-92) | 60p | LO37T1 (TO-3) | £1.46 | MVR5V (TO-3) | £1.45 | TBA560CQ | £5.29 |
| CD4035AE | £1.75 | £1.46 | £1.17 | 7485 | £1.30 | £1.09 | 87p | 78L12WC (TO-92) | 60p | L129 (SOT-32) | 85p | MVR12V (TO-3) | £1.45 | TBA625A | £1.03 |
| CD4040AE | £2.01 | £1.68 | £1.34 | 7486 | 32p | 26p | 21p | 78L15WC (TO-92) | 60p | L130 (SOT-32) | 85p | MVR15V (TO-3) | £1.45 | TBA625B | £1.03 |
| CD4042AE | £1.49 | £1.24 | 99p | 7489 | £3.56 | £2.80 | £2.10 | Regulators 100mA | 60p | L131 (SOT-32) | 85p | NE540 | £1.46 | TBA625C | £1.03 |
| CD4045AE | 69p | 58p | 46p | 7490 | 49p | 40p | 32p | 78L15WC (TO-92) | 60p | LM301T (TO-99) | 65p | NE540B | £1.25 | TBA651 | £1.87 |
| CD4050AE | 69p | 58p | 46p | 7491 | 65p | 55p | 45p | Regulators 500mA | 60p | LM301S (8 pin dip) | 59p | NE546A | £1.16 | TBA750Q | £2.79 |
| CD4051AE | £2.78 | £2.32 | £1.85 | 7492 | 57p | 46p | 36p | 78M05HC | £1.35 | LM301T (TO-99) | 67p | NE555V | 73p | TBA800 | £1.11 |
| CD4052AE | £2.78 | £2.32 | £1.85 | 7493 | 49p | 40p | 32p | 78M12HC | £1.35 | LM301A (TO-99) | 59p | NE555 | £1.29 | TBA810S | £1.24 |
| CD4056AE | £2.12 | £1.76 | £1.41 | 7495 | 67p | 55p | 45p | 78M12HC (TBA625B) | 90p | LM301A S (8 pin dip) | 59p | NE560B | £5.06 | TBA810AS | £1.24 |
| CD4060AE | £2.51 | £2.09 | £1.67 | 74100 | £1.08 | 89p | 72p | 78M15AHC (TBA625C) | 90p | LM301A S (8 pin dip) | 59p | NE561B | £5.06 | TBA820S | £1.80 |
| CD4066AE | £1.13 | 94p | 75p | 74107 | 35p | 28p | 22p | Regulators 500mA | 60p | LM307 T (TO-99) | 59p | NE562B | £5.06 | TBA920Q | £4.71 |
| CD4068AE | 28p | 24p | 19p | 74121 | 34p | 28p | 22p | 78M05HC | £1.35 | LM307 T (TO-99) | 59p | NE563 | £2.63 | TBA990Q | £4.71 |
| CD4069AE | 28p | 24p | 19p | 74122 | 47p | 39p | 31p | 78M12HC | £1.35 | LM307 S (8 pin dip) | 59p | NE565N | £2.63 | TCA270Q | £5.24 |
| CD4070AE | 28p | 24p | 19p | 74141 | 78p | 63p | 53p | 78M12HC | £1.35 | LM307 S (8 pin dip) | 59p | NE566V | £1.87 | TCA760 | £2.16 |
| CD4071AE | 28p | 24p | 19p | 74154 | £1.75 | £1.48 | 88p | 78M15HC | £1.35 | LM308 T (TO-99) | 57p | NE567 | £2.63 | TCA800Q | £2.24 |
| CD4077AE | 71p | 59p | 47p | 74174 | £1.00 | 89p | 67p | 78M18HC | £1.35 | LM308 T (TO-99) | 57p | SL414A | £2.75 | TCA830S | £1.04 |
| CD4081AE | 28p | 24p | 19p | 74180 | £1.06 | 89p | 71p | 78M24HC | £1.35 | LM308 S (8 pin dip) | 99p | SL415A | £2.75 | TCA940 | £2.25 |
| CD4082AE | 28p | 24p | 19p | 74181 | £3.20 | £2.50 | £1.50 | Regulators 1A | | LM308 S (8 pin dip) | 99p | SL437D | £7.50 | TD1054 | £1.50 |
| CO4085AE | £1.28 | £1.04 | 85p | 74192 | £1.35 | £1.14 | 90p | 7805KC (TO-3) | £2.09 | LM308A T (TO-99) | 99p | SL440 | £2.84 | TD1200 | £2.43 |
| CO4086AE | £1.28 | £1.06 | 85p | 74193 | £1.35 | £1.14 | 90p | 7812KC (TO-3) | £2.09 | LM308A T (TO-99) | 99p | SL610C | £2.03 | TD1405 | £1.50 |
| CO493AE | £1.56 | £1.20 | £1.04 | 74196 | £1.64 | £1.34 | 99p | 7815KC (TO-3) | £2.09 | LM308A S (8 pin dip) | 99p | SL612C | £2.03 | TD1412 | 80p |
| CD4099AE | £2.95 | £2.46 | £1.96 | 74196 | £1.64 | £1.34 | 99p | 7818KC (TO-3) | £2.09 | LM309K | £2.34 | SL613C | £4.31 | TD1415 | 80p |

SIEMENS LCD's

LINE-O-LIGHT

LIQUID CRYSTAL DISPLAY complete with socket and removable reflective backing; Ref AN4132R 13mm character height. Can be directly driven by National Semiconductors Alarm Clock chip MMS316. £13.99




NEW LED Linear Cursors each device contains 10 light emitting diodes in a 20pin dual-in-line package. Ideal for solid state analogue meters or dials. Type 101 RED. £2.26




PHOTO-DARLINGTON

SPECIAL PURCHASE

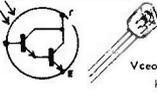
2N5777 Vceo, Vcbo 25v; Vcbo Bv Vceo, Vcbo 25v; VEB0 Bv Ife 2500; Ic 250 mA **35p.**



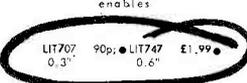
enables LIT707 90p; LIT747 £1.99 0.3" 0.6"



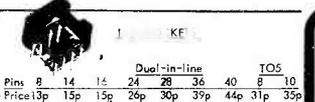Dual-in-line TO5 Pins 8 14 16 24 28 36 40 8 10 Price 13p 15p 26p 30p 39p 44p 31p 35p



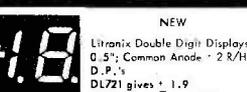NEW Litronix Double Digit Displays 0.5" Common Anode - 2 R/H D.P. L. DL721 gives 1.9 DL727 gives 0.0 to 9.9 Suitable for Clocks; Instruments; T.V. Channel Indicator Our Price £4.75 each



L.E.D.'s

NOTICE

Free snap-on plastic retainer

| 0.125" dia. lens (TIL209) | 0.16" dia. lens | 0.2" dia. lens (MLED 650) |
|---------------------------|-----------------|---------------------------|
| 1+ 10+ 100+ | 1+ 10+ 100+ | 1+ 10+ 100+ |
| Red 15p 13p 27p | 27p 24p 22p | 18p 16p 14p |
| Green 27p 24p 22p | 33p 30p 27p | 30p 27p 25p |
| Orange 27p 24p 22p | 33p 30p 27p | 30p 27p 25p |
| Yellow 34p 31p 29p | 35p 32p 29p | 35p 33p 30p |

Low Cost Red Caps Motorola MLED 500 in a 1092 package. 15p

NEW Opto-isolators (I1 4N25 or TIL114) 6 pin industry standard package. 2.5KV isolation £1.00

With the recent increase in postal charges and a continuing increase in packaging costs we have been forced to review our policy. Henceforward:

- Orders valued at £5 or more will be post free.
- All U.K. "small package" orders will go first class mail.
- Minimum postage & packing charge will increase to 70p.

SEVEN SEGMENT DISPLAYS

| litronix Xciton Monsanto | COMMON ANODE R/H | | COMMON ANODE L/H | | COMMON CATHODE | | Our Price |
|--------------------------|------------------|---------|------------------|---------|----------------|-------|-----------|
| | Dec. Pt. | DL707P | Dec. Pt. | DL701 | Dec. Pt. | DL704 | |
| 0.3" | GREEN | MAN51 | MAN52 | MAN53 | MAN54 | £1.82 | |
| | RED | MAN71 | MAN72 | MAN73 | MAN74 | £1.82 | |
| | YELLOW | MAN81 | MAN82 | MAN83 | MAN84 | £1.82 | |
| | ORANGE | MAN9510 | MAN9620 | MAN9630 | MAN9640 | £1.82 | |
| 0.4" | GREEN | XAN51 | XAN52 | XAN54 | £1.49 | | |
| | RED | XAN71 | XAN72 | XAN74 | £1.49 | | |
| | YELLOW | XAN81 | XAN82 | XAN84 | £1.49 | | |
| | GREEN | MAN4510 | MAN4520 | MAN4530 | MAN4540 | £2.32 | |
| 0.6" | RED | MAN4710 | MAN4720 | MAN4730 | MAN4740 | £2.32 | |
| | YELLOW | MAN4810 | MAN4820 | MAN4830 | MAN4840 | £2.32 | |
| | ORANGE | MAN4910 | MAN4920 | MAN4930 | MAN4940 | £2.32 | |
| | C.A. L/H | DL747 | C.A. L/H | DL746 | C.C. L/H | DL745 | £2.42 |

NOTE: MAN4000 series pinouts are 14 pin dill the same as MAN5070 & 80 series.

MINITRON

Minitron Filament Display bi-directional 0.36" 3015G ± 0.9 L/H d.p.t. 3015G ± 0.1 £1.08



PRACTICAL WIRELESS

VOL. 51 NO. 5

ISSUE 823

SEPTEMBER 1975

BRITAIN'S PREMIER MAGAZINE FOR THE DO-IT-YOURSELF RADIO AND ELECTRONICS CONSTRUCTOR

EDITOR

Lionel E. Howes, G3AYA

ASSISTANT EDITOR

Eric Dowdeswell, G4AR

ART EDITOR

Peter Metalli

TECHNICAL EDITOR

Sam Lewis B.Sc. (Eng.)

PRODUCTION & NEWS EDITOR

Colin R. Riches

TECHNICAL SUB-EDITOR

Bill Tull

TECHNICAL ARTIST

Alan Martin

SECRETARIAL

Jenny Maunder
Susan King

ADVERTS MANAGER

01-634 4293 Roy Smith

CLASSIFIED ADVERTS

01-634 4301 Colin R. Brown

Published by IPC Magazines Ltd.,
Fleetway House, Farringdon Street,
London EC4A 4AD. Tel. 01-634 4444

Binders (£1.90) and indexes 30p (inc.
VAT) can be supplied by the Binders
Dept at the same address.

BACK NUMBERS

We regret that we are unable to supply
back numbers of Practical Wireless.
Readers are recommended to enquire
at a public library to see copies. Re-
quests for specific back numbers of
Practical Wireless and *Television* only
can be published in our CQ Column.

COPYRIGHT AND QUERIES

© IPC Magazines Limited 1975. Copyright in all drawings, photographs and articles published in "Practical Wireless" is fully protected and reproduction or imitation in whole or in part is expressly forbidden. All reasonable precautions are taken by "Practical Wireless" to ensure that the advice and data given to readers are reliable. We cannot, however, guarantee it and we cannot accept legal responsibility for it. Prices are those current as we go to press.

We regret that we cannot answer technical queries by telephone nor can we provide information or advice on manufacturers' products other than that given in the magazine. We will endeavour to assist readers who have queries relating to articles published but we cannot offer advice on modifications to our published designs. All correspondents expecting a reply should enclose a stamped addressed envelope.

Practical Wireless, September 1975

● NEWS & COMMENT

- 364 CAUSE FOR ALARM!—Editor's comment
- 365 NEWS . . . NEWS . . . NEWS
- 387 NEXT MONTH IN PRACTICAL WIRELESS
- 402 LETTERS—Readers comment
- 409 HOTLINES on recent developments by *Ginsberg*
- 410 ON THE AIR—
- 410 Amateur Bands—*Eric Dowdeswell, G4AR*
- 413 SW Bands—*Derek Bell*
- 414 MW Bands—*Charles Molloy*

● CONSTRUCTIONAL

- 366 ON-SCREEN SCORING for TELE-TENNIS—*E. A. Parr, B.Sc., C.Eng., MIEE*
- 372 MINIATURE 2m EQUIPMENT—Part 1: Converter—*W. H. Bond, F.R.C.S., G3XGP*
- 377 EXPERIMENTAL WORKSHOP—TRF Radio Receivers—*M. J. Hughes, M.A., C.Eng., MIERE*
- 385 TAKE 20 No. 71—Motor Speed Controller—*David Andrews*
- 388 PW 'EASYBUILD' ELECTRONIC CLOCK—*M. J. Hughes, M.A., C.Eng., MIERE*
- 395 DUAL CONVERSION RECEIVER—Part 2—*F. G. Rayer*
- 399 SHORT WAVE PRE-AMPLIFIER—*Steve Money, G3FZX*

● OTHER FEATURES

- 386 TECHNICROSS No. 10—Solution
- 406 IC OF THE MONTH No. 53—TAA930 FM Detector

BENTLEY ACOUSTIC CORPORATION LTD.

7a GLOUCESTER ROAD, LITTLEHAMPTON, SUSSEX
All prices inclusive of V.A.T. at 25% Telephone 6743

| | | | | | | | | | | | |
|--------|-----|-------|-----|--------|-----|--------|------|----------|-------|--------|-----|
| OB2 | 47 | 6BA6 | 41 | 6L1 | 234 | 12J7GT | 70 | 35D5 | 88 | DK40 | 88 |
| OZ4 | 55 | 6BC8 | 70 | 6L6GC | 88 | 12K3 | 117 | 35L6GT | 88 | DK92 | 88 |
| LA3 | 58 | 6B18 | 41 | 6L7 | 58 | 12K7GT | 88 | 35W4 | 59 | DK98 | 70 |
| 1A6GT | 59 | 6B16 | 70 | 6L18 | 64 | 12Q7GT | 53 | 35Z3 | 88 | DL96 | 64 |
| 1A7GT | 76 | 6B36 | 64 | 6L19 | 234 | 128C7 | 59 | 35Z4GT | 82 | DM70 | 70 |
| 1B3GT | 59 | 6BK7A | 70 | 6LD20 | 88 | 128G7 | 47 | 35Z5GT | 88 | DM71 | 176 |
| 1H5GT | 70 | 6BQ7A | 64 | 6N7GT | 70 | 128H7 | 41 | 42 | 59 | DY87/8 | 41 |
| LL4 | 33 | 6BR7 | 117 | 6Q7G | 59 | 128J7 | 52 | 43 | 177 | DY90Z | 41 |
| 1N5GT | 76 | 6BR8 | 176 | 6Q7GT | 59 | 128K7 | 59 | 50R5 | 100 | 8Y0CC | 287 |
| 1R5 | 58 | 6B87 | 164 | 6Q7M | 64 | 128R7 | 88 | 50C5 | 70 | E80F | 164 |
| 1R4 | 59 | 6B97 | 94 | 6R7G | 70 | 141H7 | 64 | 50CD60 | 88 | E88CC | 88 |
| 1U4 | 70 | 6B7W | 82 | 6R7M | 88 | 1487 | 94 | 50E5H | 88 | E180F | 117 |
| 1U5 | 58 | 6B24 | 57 | 68A7 | 52 | 19A06 | 70 | 50L6GT | 70 | E162CC | 146 |
| 2D21 | 63 | 6C4 | 47 | 68C7GT | 39 | 19C36 | 70 | 50P1 | 70 | E148 | 69 |
| 2GK5 | 64 | 6C6G | 59 | 68G7 | 52 | 20D1 | 70 | 50P2 | 88 | EA50 | 38 |
| 2K2 | 70 | 6C9 | 47 | 68H7 | 52 | 20P2 | 88 | 50P2 | 88 | EA50 | 38 |
| 2K3 | 70 | 6C9 | 117 | 68J7 | 84 | 20L1 | 189 | 90AG | 298 | EA76 | 117 |
| 3D6 | 47 | 6CD6G | 146 | 68K7GT | 53 | 20P3 | 94 | 90C1 | 88 | EABC80 | 45 |
| 3Q4 | 70 | 6C88A | 88 | 68Q7GT | 53 | 20P4 | 117 | 90C2 | 88 | EAC91 | 88 |
| 3Q5GT | 64 | 6C1A | 76 | 6V6G | 20 | 20P5 | 158 | 180B2 | 88 | EAF42 | 88 |
| 384 | 47 | 6CL8A | 64 | 6V6GT | 53 | 25A6G | 70 | 25B6G | 59 | EAF501 | 88 |
| 3V4 | 52 | 6CM7 | 88 | 6X4 | 47 | 25L6G | 70 | 807 | 117 | EB34 | 29 |
| 4C6 | 64 | 6CG | 88 | 6X5GT | 53 | 25Y6G | 82 | 5702 | 117 | EB91 | 28 |
| 6C8G | 64 | 6COW4 | 117 | 7B6 | 88 | 25Z4G | 47 | 5783 | 176 | EB41 | 88 |
| 6B4GY | 64 | 6DE7 | 88 | 7B7 | 82 | 25Z5 | 84 | 6057 | 117 | EB81 | 41 |
| 5U4G | 47 | 6DT6A | 88 | 7H7 | 88 | 25Z6G | 82 | 6090 | 117 | EBF90 | 40 |
| 6V4G | 39 | 6E9W | 88 | 7H7 | 94 | 28D7 | 117 | 6067 | 117 | EBF83 | 50 |
| 6Z3 | 58 | 6E1 | 117 | 7Y4 | 88 | 30A5 | 74 | 7193 | 62 | EBF89 | 38 |
| 6Z4G | 58 | 6F5G | 89 | 9D7 | 76 | 30C17 | 94 | 9008 | 35 | EC86 | 82 |
| 6Z4GT | 58 | 6F13 | 88 | 10C2 | 76 | 30C18 | 82 | ACPEN1 | 117 | EC88 | 82 |
| 6/30L2 | 70 | 6F14 | 88 | 10DE7 | 88 | 30P9 | 88 | AC2/PEN1 | EC92 | 82 | |
| 6A8G | 146 | 6F15 | 76 | 10F1 | 88 | 30P11 | 78 | DD | 117 | BCC33 | 176 |
| 6AC7 | 57 | 6F18 | 88 | 10F9 | 76 | 30P12 | 78 | ACPEN7 | 70 | EC835 | 111 |
| 6AG5 | 35 | 6F33 | 82 | 10F18 | 64 | 30P12 | 105 | AC/TH1 | EC840 | 117 | |
| 6A8E | 70 | 6F24 | 100 | 10LD11 | 82 | 30P13 | 64 | 117 | EC881 | 40 | |
| 6AJ5 | 76 | 6F25 | 117 | 10P13 | 88 | 30P14 | 82 | AL60 | 117 | EC882 | 39 |
| 6AK5 | 47 | 6F28 | 76 | 10P14 | 234 | 30L15 | 82 | ATP4 | 59 | EC888 | 39 |
| 6AK6 | 70 | 6F82 | 89 | 12A6 | 75 | 30L17 | 78 | AZ1 | 29 | EC884 | 41 |
| 6AM8A | 64 | 6G6G | 59 | 12AC8 | 82 | 30P4R | 88 | AZ1 | 29 | EC885 | 47 |
| 6AN8 | 89 | 6G85A | 88 | 12AD6 | 76 | 117 | AZ41 | 29 | EC888 | 100 | |
| 6AQ5 | 58 | 6GK6 | 76 | 12AE6 | 76 | 30P15 | 94 | BL63 | 234 | EC888 | 58 |
| 6AR5 | 70 | 6G7U | 88 | 12AT6 | 47 | 30P19 | 88 | CL33 | 187 | ECC189 | 76 |
| 6AS7 | 117 | 6HG6T | 89 | 12AU6 | 53 | 30P4 | 88 | CV1C | 117 | ECC807 | 141 |
| 6AT6 | 58 | 6J5GT | 88 | 12AV6 | 88 | 30P11 | 100 | CY81 | 59 | ECF80 | 53 |
| 6AT6 | 86 | 6J3 | 85 | 12BC8 | 83 | 30P15 | 111 | DAF91 | 35 | ECF82 | 53 |
| 6AV6 | 85 | 6J7G | 85 | 12BE6 | 59 | 30P14 | 129 | DAF96 | 59 | ECF86 | 88 |
| 6AW8A | 111 | 6JUSA | 88 | 12BH7 | 59 | 30P15 | 94 | DC90 | 70 | ECF804 | 283 |
| 6AX4 | 88 | 6K7G | 35 | 12BY7 | 88 | 35A3 | 88 | DF91 | 35 | ECH21 | 234 |
| 6B8G | 85 | 6K8G | 58 | 12E1 | 81 | 35C5 | 88 | DF96 | 59 | ECH35 | 146 |

| | | | | | | | | | | | | | | |
|-------|-----|--------|---------|---------|-------|--------|--------|-------------|--------|-------|-------|--------|------|----|
| ECH42 | 82 | BY34 | 68 | PCF801 | 59 | TP2820 | 117 | W729 | 117 | AD161 | 69 | BYZ13 | 83 | |
| ECH81 | 89 | EY87/6 | 89 | PCF802 | 59 | UBA80 | 47 | X65 | 146 | AD103 | 69 | BYZ13 | 83 | |
| ECH83 | 62 | EY88 | 47 | PCF806 | 59 | UAF42 | 70 | X66 | 146 | AF114 | 88 | F8Y11A | 89 | |
| ECH84 | 52 | EY91 | 68 | PCB200 | 59 | URC41 | 70 | X101 | 234 | AF110 | 80 | F8Y41A | 89 | |
| ECL80 | 47 | EZ40 | 59 | 100 | UBC81 | 58 | Z789 | 88 | 88 | AF117 | 85 | OA9 | 18 | |
| ECL82 | 40 | EZ41 | 64 | PCL82 | 45 | UBF90 | 47 | Transistors | | AF121 | 89 | OA19 | 66 | |
| ECL83 | 58 | EZ60 | 88 | PCL85 | 58 | UBF89 | 47 | & Diodes | | AF125 | 82 | OA70 | 80 | |
| ECL84 | 70 | EZ81 | 94 | PCL84 | 47 | UBL21 | 234 | 1N4744 | 18 | AF126 | 82 | OA73 | 80 | |
| ECL85 | 70 | GZ501 | 82 | PCL86 | 55 | UC92 | 88 | 2N404 | 28 | AF180 | 82 | OA79 | 18 | |
| ECL86 | 47 | GZ33 | 59 | PCL805 | 64 | UCC84 | 28 | 2N2965 | 68 | AF186 | 71 | OA81 | 12 | |
| EF22 | 176 | GZ33 | 146 | PEN45 | 94 | UC95 | 63 | 2N2966 | 68 | AF187 | 71 | OA85 | 18 | |
| EF40 | 88 | GZ44 | 70 | PEN45DD | UC96 | 82 | 2N3176 | 94 | 2N3177 | 94 | AF188 | 71 | OA86 | 18 |
| EF41 | 88 | GZ27 | 117 | UCH21 | 234 | 234 | 2N3177 | 94 | 2N3178 | 94 | AF189 | 71 | OA89 | 18 |
| EF42 | 82 | HAB80 | 80 | PEN46 | 59 | UCH42 | 88 | 2N3257 | 89 | BA129 | 16 | OA91 | 12 | |
| EF73 | 176 | 70 | PEN45DD | UCH81 | 47 | 234 | 2N3259 | 89 | BA130 | 18 | OA96 | 18 | | |
| EF80 | 29 | HL23DD | 234 | UCL82 | 45 | 2N3053 | 82 | BA153 | 80 | OA200 | 12 | | | |
| EF83 | 117 | 88 | PENDD | UCL83 | 64 | 2N3121 | 322 | BC107 | 16 | OA202 | 12 | | | |
| EF85 | 85 | HL41DD | 4020 | 234 | UF41 | 88 | 2N3703 | 25 | BC108 | 16 | OC44 | 18 | | |
| EF86 | 50 | 234 | PFL200 | 82 | UF42 | 88 | 2N3709 | 22 | BC109 | 18 | OC45 | 14 | | |
| EF89 | 35 | HL42DD | PL38 | 59 | UF80 | 41 | AA119 | 20 | BC113 | 83 | OC46 | 20 | | |
| EF92 | 69 | HN309 | 178 | PL81 | 58 | UF89 | 53 | AA120 | 20 | BC115 | 80 | OC70 | 16 | |
| EF97 | 94 | RVR2 | 117 | PL81A | 58 | UL41 | 70 | AA123 | 20 | BC118 | 29 | OC72 | 14 | |
| EF184 | 41 | KT41 | 117 | PL82 | 43 | UL84 | 40 | AZ107 | 39 | BOY10 | 69 | OC74 | 29 | |
| EF804 | 148 | KT66 | 238 | PL83 | 47 | UM90 | 88 | AC113 | 23 | BOY12 | 64 | OC75 | 14 | |
| EF92 | 69 | KT66 | 238 | PL84 | 47 | UY41 | 58 | AC126 | 16 | BOY33 | 29 | OC76 | 20 | |
| EL32 | 59 | KT61 | 176 | PL84 | 47 | UY85 | 41 | AC127 | 23 | BOY34 | 29 | OC77 | 20 | |
| EL34 | 117 | KTW62 | 176 | PL85 | 170 | UY12 | 117 | AC128 | 28 | BOY39 | 29 | OC78 | 20 | |
| EL35 | 208 | KTW63 | 117 | PL86 | 170 | UY25 | 70 | AC154 | 83 | BF128 | 83 | OC81 | 14 | |
| EL37 | 288 | MHL26 | 117 | PL87 | 176 | UY35 | 41 | AC156 | 83 | BF163 | 29 | OC82 | 14 | |
| EL41 | 58 | P61 | 117 | PL88 | 176 | UY35 | 41 | AC165 | 83 | BF173 | 49 | OC82D | 14 | |
| EL43 | 64 | PABCR0 | 45 | PL89 | 176 | UY35 | 41 | AC166 | 83 | BF180 | 39 | OC83 | 20 | |
| EL45 | 62 | PC88 | 70 | PL90 | 176 | UY35 | 41 | AC178 | 71 | BF185 | 82 | OC84 | 20 | |
| EL46 | 45 | PC88 | 70 | PL91 | 176 | UY35 | 41 | AC177 | 71 | BF189 | 82 | OC89 | 20 | |
| EL48 | 64 | PC88 | 70 | PL92 | 176 | UY35 | 41 | AC178 | 71 | BF190 | 82 | OC92 | 20 | |
| EL50 | 63 | PC88 | 70 | PL93 | 176 | UY35 | 41 | AC179 | 71 | BF191 | 82 | OC93 | 20 | |
| EL51 | 63 | PC88 | 70 | PL94 | 176 | UY35 | 41 | AC180 | 71 | BF192 | 82 | OC94 | 20 | |
| EL52 | 63 | PC88 | 70 | PL95 | 176 | UY35 | 41 | AC181 | 71 | BF193 | 82 | OC95 | 20 | |
| EL53 | 63 | PC88 | 70 | PL96 | 176 | UY35 | 41 | AC182 | 71 | BF194 | 82 | OC96 | 20 | |
| EL54 | 63 | PC88 | 70 | PL97 | 176 | UY35 | 41 | AC183 | 71 | BF195 | 82 | OC97 | 20 | |
| EL55 | 63 | PC88 | 70 | PL98 | 176 | UY35 | 41 | AC184 | 71 | BF196 | 82 | OC98 | 20 | |
| EL56 | 63 | PC88 | 70 | PL99 | 176 | UY35 | 41 | AC185 | 71 | BF197 | 82 | OC99 | 20 | |
| EL57 | 63 | PC88 | 70 | PL100 | 176 | UY35 | 41 | AC186 | 71 | BF198 | 82 | OC100 | 20 | |
| EL58 | 63 | PC88 | 70 | PL101 | 176 | UY35 | 41 | AC187 | 71 | BF199 | 82 | OC101 | 20 | |
| EL59 | 63 | PC88 | 70 | PL102 | 176 | UY35 | 41 | AC188 | 71 | BF200 | 82 | OC102 | 20 | |
| EL60 | 63 | PC88 | 70 | PL103 | 176 | UY35 | 41 | AC189 | 71 | BF201 | 82 | OC103 | 20 | |
| EL61 | 63 | PC88 | 70 | PL104 | 176 | UY35 | 41 | AC190 | 71 | BF202 | 82 | OC104 | 20 | |
| EL62 | 63 | PC88 | 70 | PL105 | 176 | UY35 | 41 | AC191 | 71 | BF203 | 82 | OC105 | 20 | |
| EL63 | 63 | PC88 | 70 | PL106 | 176 | UY35 | 41 | AC192 | 71 | BF204 | 82 | OC106 | 20 | |
| EL64 | 63 | PC88 | 70 | PL107 | 176 | UY35 | 41 | AC193 | 71 | BF205 | 82 | OC107 | 20 | |
| EL65 | 63 | PC88 | 70 | PL108 | 176 | UY35 | 41 | AC194 | 71 | BF206 | 82 | OC108 | 20 | |
| EL66 | 63 | PC88 | 70 | PL109 | 176 | UY35 | 41 | AC195 | 71 | BF207 | 82 | OC109 | 20 | |
| EL67 | 63 | PC88 | 70 | PL110 | 176 | UY35 | 41 | AC196 | 71 | BF208 | 82 | OC110 | 20 | |
| EL68 | 63 | PC88 | 70 | PL111 | 176 | UY35 | 41 | AC197 | 71 | BF209 | 82 | OC111 | 20 | |
| EL69 | 63 | PC88 | 70 | PL112 | 176 | UY35 | 41 | AC198 | 71 | BF210 | 82 | OC112 | 20 | |
| EL70 | 63 | PC88 | 70 | PL113 | 176 | UY35 | 41 | AC199 | 71 | BF211 | 82 | OC113 | 20 | |
| EL71 | 63 | PC88 | 70 | PL114 | 176 | UY35 | 41 | AC200 | 71 | BF212 | 82 | OC114 | 20 | |
| EL72 | 63 | PC88 | 70 | PL115 | 176 | UY35 | 41 | AC201 | 71 | BF213 | 82 | OC115 | 20 | |
| EL73 | 63 | PC88 | 70 | PL116 | 176 | UY35 | 41 | AC202 | 71 | BF214 | 82 | OC116 | 20 | |
| EL74 | 63 | PC88 | 70 | PL117 | 176 | UY35 | 41 | AC203 | 71 | BF215 | 82 | OC117 | 20 | |
| EL75 | 63 | PC88 | 70 | PL118 | 176 | UY35 | 41 | AC204 | 71 | BF216 | 82 | OC118 | 20 | |
| EL76 | 63 | PC88 | 70 | PL119 | 176 | UY35 | 41 | AC205 | 71 | BF217 | 82 | | | |

RSC 100 watt DISCO SYSTEM

50 WATT SPEAKER 50 WATT SPEAKER
TWIN TURNTABLE WITH PRE-AMP. and POWER AMPLIFIER

AT FANTASTIC LOW PRICES!

Complete with lid HEADPHONES MICROPHONE

RSC TDI DISCO CONSOLE

Incorporating twin BBR MP60 type turntables and Sonotone or Acos Cartridges with diamond styl. Separate Vol. controls for each turntable. Also MONITORING FACILITIES, plus Treble and Bass Controls. Separate input for 'mike' with vol. control. Black Vynide covered Cabinet with lid, see illustration on left. Or DEP. £8-95 and 18 fortnightly payments of £1-01. (Total £101.95) Carr. £1-50

Units listed below
(a) DISCOMASTER TWIN TURNTABLE CONSOLE with integral 100W amplifier
(b) PAIR OF HI-FI HEAD PHONES
(c) MATCHING DYNAMIC 'MIKE' (attached to h'phone)
(d) PAIR 50 WATT SPEAKERS Black Vynide covered Cabinets Size approx. 18" x 18" x 8" £169-99
(a) (b) (c) & (d) Carr. £3-00

DEP. £19-99 & 18 fortnightly payments of £9-75 (Total £195-49).

STEREO VERSION of Above System Or DEPOSIT £24-95 and 18 fortnightly pymts. £11-19 (Total £258-87) Carr. £3-50

TD2S STEREO VERSION OF ABOVE Terms DEPOSIT £20 £125-00 and 18 fortnightly payments £8-71 (Total £140-78) Carr. £1-00

DISCOMASTER TWIN TURNTABLE POWER CONSOLE £119-95

Twin McDonald MP60 type turntables. Sonotone or Acos cartridges with diamond styl. Facilities as TDI Console but with built-in 100 watt Power Amplifier, complete with lid. Or Deposit £18-95 and 18 fortnightly payments £6-78 (Total £185-99) Carr. £2-50

STEREO VERSION £155 or DEPOSIT £25 and 18 fortnightly pymts £8-30 (Total £174-40). Carr. £3

R.S.C. COLUMN SPEAKERS IDEAL FOR VOCALISTS AND PUBLIC ADDRESS

All types 15 Ohms covered in Vynide & Vynair

TYPE C132 40-50 WATTS £27-95
Incorporating two exceptionally efficient 13" x 8" speaker units. Dep. £9-95 and 8 monthly payments £3-50 (Total £31-95) Carr. 65p

TYPE C37/70 70 WATTS. Fitted three 12" 25 watt Highly sensitive high flux speakers with high power voice coils. Size approx. 54" x 14" x 11". Dep. £5-11 & 8 mthly pymts. £5-11 £39-95 (Total £45-99) Carr. 85p

FANE ULTRA HIGH POWER SPEAKERS & KITS

All power ratings are R.M.S. continuous, 2 YEARS' GUARANTEE High flux ceramic magnets. ALL CARRIAGE FREE.

| 'POP' 100 | 'POP' 60 | 'POP' 50 |
|---------------------------------------|--------------------------------------|------------------------------------|
| 18" 100 Watt 14,000 gauss 8/15Ω | 15" 60 Watt 14,000 gauss 8/15Ω | 12" 50 Watt 13,000 Gauss 15Ω |
| £35-95 | £18-95 | £13-95 |

Dep. £7-95 and 8 mthly payments £4-00 (Total £29-95)

Dep. £4-17 and 8 monthly payments. £2-17 (Total £21-53)

Terms for pairs Dep £8-90 & 8 mthly pymts £3-10 Total £31-18 PAIR SUITABLE ALL PURPOSES

FOR BASS GUITAR, ELECT. ORGAN, ETC.

ALL RSC PRICES INCLUDE VAT

INTEREST ON Credit Purchases REFUNDED settled in 3 months

SUPER MINSTREL 10 W GUITAR AMP.

Incorporating Tremolo and 10" Speaker. Output 10 watts R.M.S. Continuous. 3 Jack Inputs for Microphone and Instrument. Mains Neon Controls: Volume, Tone, Tremolo, Speed Tremolo Intensity. Terms: DEPOSIT £7-78 and 8 monthly payments £3-40 (Total £34-98) Carr. free £29-99

'POP' 25/T 12" 25W HIGH POWER TWEETER PH50

Dual cone. 15 ohm Imp. (Not for Bass Guitar use) Terms for Pairs: Deposit £8-90 and 8 mthly payments. of £2-75 (Total £25-90)

Response 3KHz-20KHz with 2 to 4 mid. Non elect. filter available 55p. Rating 50 Watt £6.65 Imp 8Ω

FAL MAESTRO COMBINED 80W AMP. AND 12" SPEAKER £55-95 Carr. Free

For Lead Guitar, Mic, Gram, Radio, Tape (Not for use with Bass instruments) Inc. 3 inputs and 2 vol controls plus Treble & Bass, TREMOLO with associated controls. Attractively finished in black with silver-finished fascia. Compact size Fitted carrying handle. Deposit £9-25 and 8 mthly payments £6-78 (Total £68-38)

RSC 'PHANTOM 50' Rating 50 watts, 3 inputs, 2 vol. controls, Bass, Treble, Presence £59-95 Carr. £1-50 Dep. £7-95 & 8 mthly. pymts. £7-48 (Total £27-78).

D40 50 WATT DISCO KIT £21-50

ALL PURPOSE FULL RANGE Consisting of 12" 13,000 Gauss Bass Unit. HPX1 Cross over and PH50 Tweeter. Imp 8/15Ω (Bass Guitar requires pair in one cabinet). Terms: Dep. £3 x 8 mthly. pyts. £2/75 (Total £25)

TITAN GROUP/DISCO SPEAKERS

Send S.A.E. for leaflet

FAL PHASE 50 Mk. III AMPLIFIER 50 WATT

Solid state. 4 Sep. controlled inputs Plus master vol. control. Ind. Protection against serious o/p overloading. O/p for spkrs. 8 to 15 ohms. Size 17" x 7" x 7". 200-250v. A.C. mains. O/p 50w Music. Deposit £8-00 & 8 mthly. payments. £5-75. Total £41-60 Carr. Free. £48-60

JINGLE MACHINES I.S.E. CA127 £79-95 DEPOSIT £9 and 18 fortnightly payments £4-61. Total £91-98

HIGH QUALITY LOUDSPEAKER UNITS

ALL 2-TONE VYNIDE & VYNAIR FINISH L12/2 50 WATT Fitted pair of 12" £39-95 30 watt high flux speakers. Imp. 8-15 ohms. Carr. £1-50 Terms: Dep. £5-11 and 8 monthly payments. of £5-11. Total £45-99 L12/50 12" 50 WATT 13,000 lines 15 ohms Terms: Dep. £3-95 & 8 monthly payments £3-37 (Total £30-91) Carr. 55p. £25-95

REGENT 50X 50 WATT AMP.

A powerful high quality unit for lead, rhythm guitar, vocalists, gram, radio, tape. 50w Peak O/P Rating. Not for Bass Guitar.
★ Two Fane heavy duty high flux 12in. spkrs.
★ Four Jack inputs and two Volume Controls for instant use of up to four pick-ups or "mikes". Bass and Treble controls. Send S.A.E. for leaflet. Credit Terms: Deposit £9-95 & 18 fortnightly payments of £4-15 (Total £34-45) £74-95 Carr. £2-50

REGENT 50B for Bass Guitar and general purposes. Or Dep. £9-00 & 18 fortnightly payments £4-61. (Total £21-68) Carr. £2-50

GP30 AMPLIFIER

For Guitar, Vocal or Instr. Group, Gram, Radio or Page. 4 inputs. 2 Vol. Controls. Current Valves. Peak o/p rating. Strong Vynide covered cabinet with carrying handles. Black/Silver Facia. Neon Indicator. For 200-250v A.C. For 2 or 15Ω speakers. Send SAE for leaflet. Terms: Dep. £5-58 & 8 mthly pymts £3-58 (Total £29-52) Carr. 75p £29-95

LIQUID WHEEL from PROJECTORS £24-75

'SOUND TO LIFE' SYSTEM PULSAR special price complete kit £99-95 Dep. £11-48 and 18 fortnightly payts. £5-74 (Total £114-80). Super SL Unit. 1000 watt per channel. Manual override buttons, 2 spotbanks with 6 bulbs (3 sep. colours) 6 vd. and 10 yd. leads, fitted plugs. Units sold sep.

FAL SOUND-TO-LIFE UNIT £21-60

3-WAY SPOT BANK Excluding Bulbs Each £16-20 COMPLETE SYSTEM Incl. 2 Spotbanks and bulbs. Carr. £1-50 £55

FAL DISCO PRE-AMPLIFIER

T/2 Table mixing inputs Headphone Monitoring, Mic, Jack & Tape inputs. Independent Vol. Control. Std. 200-250v A.C. Mains operation £18-50

REGENT '50' AMPLIFIER

As supplied with Regent 60x or 50B. Terms: Dep. £5-11 & 8 mthly pymts £5-11 (Total £45-99) Carr. £1 £39-95

NEW BRANCHES AT BOLTON, DONCASTER, and PRESTON

OPEN ALL DAY SATURDAYS (5 Day Week)

BRADFORD 10 North Parade (Closed Wed.). Tel. 25349
 BOLTON 23 Deansgate. (Closed Wed.). Tel. 33512
 BIRMINGHAM 30/31 Great Western Arcade. Tel. 021-236 1279 (Closed Wed.).
 COVENTRY 17 Shelton Square, The Precinct. Tel. 25983
 DERBY 97 St. Peter's Street. (Closed Wed.). Tel. 41361
 DARLINGTON 19 Northgate (Closed Wed.). Tel. 88043
 DONCASTER 3 Queensgate, Waterdale Centre. (Closed Thurs). Tel. 63069


Barclaycard and Access accepted

All items subject to availability. Prices correct at 21.7.75 E. & O.E.


HI-FI CENTRES LTD.

EDINBURGH 101 Lothian Rd. (Closed Wed.). Tel. 229 8501
 GLASGOW 326 Argyle St. (Cl'd Tues). Tel. 248 4158
 HULL 7 Whitefriargate (Closed Thurs). Tel. 20505
 LEICESTER 32 High Street (Closed Thurs.). Tel. 56420
 LEEDS 5-7 County (Mecca) Arcade, Briggate (Closed Wed.). Tel. 458252
 LIVERPOOL 73 Dale St. (Closed Wed.). Tel. 236 3573
 LONDON 238 Edgware Road. W.2. (Closed Thurs.). Tel. 723 1629
 MANCHESTER 60A Oldham Street (Closed Wed.). Tel. 236 2778

MIDDLESBROUGH 108 Newport Road (Closed Wed.). Tel. 47096
 NEWCASTLE UPON TYNE 24 Newgate Shopping Centre (Closed Wed.). Tel. 21488
 NOTTINGHAM 19/19A Market Street (Closed Thurs.). Tel. 48088
 PRESTON 41 Friargate Walk. St. George's Shoppo Prec. Tel. 51679
 SHEFFIELD 13 Exchange Street (Castle Mkt. Bldg.) (Closed Thurs.). Tel. 20719
 STOCKPORT 8 Little Underbank (Closed Thurs.). Tel. 480-0777
 SUNDERLAND 5 Market Sq. (Closed Wed.). Tel. 70573

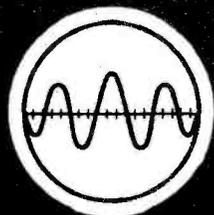


TUAC

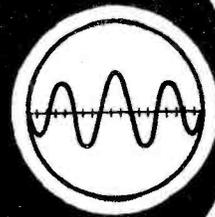

TRANSISTOR UNIVERSAL AMPLIFICATION CO. LTD.
163 MITCHAM RD. LONDON SW17 9PG 01-672 3137/9080

TUAC POWER MODULES offering more power and quality than ever before

- 125 watts RMS continuous sine wave output

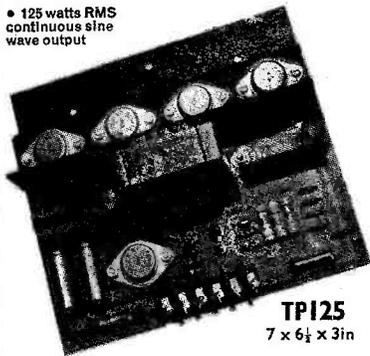


TP125
7 x 6½ x 3in
£19-50


- 4 R.C.A. 150 watt 15 amp output transistors

- Rugged layer wound driver transformer
- Short—Open—and Thermal overload protection
- Only 6 connections

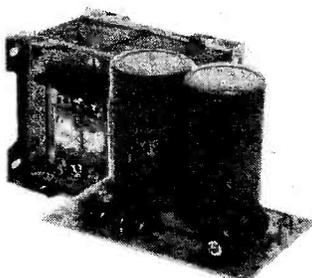Power supplies vacuum impregnated Transformers with supply board incorporating pre-amp supply.



PS 125 ± 45 volts for TP125 **£12-25**
PS 100 ± 43 volts for TL100 **£11-25**
PS 60 ± 38 volts for TL60 **£10-00**
PS 30 ± 25 volts for TL30 **£5-90**
PSU 2 for supplying disco mixer **£4-75**

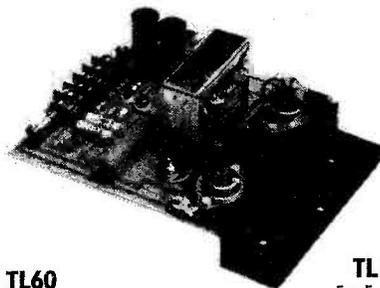

TL60

5 x 5 x 3in

- 60 watts R.M.S. continuous sine wave output
- 2 R.C.A. 110 watt 15 amp transistors

£12-50

TL100

5 x 5 x 3in

- 100 watts R.M.S. continuous sine wave output
- 2 R.C.A. 150 watt 15 amp transistors

£15-00

Specification on all power modules. All output power ratings ± 0.5dB; Output impedance 8-15 ohms; THD at full power 2% typically 1%; input sensitivity 60mV into 10kΩ; Frequency response 20Hz-20kHz ±2dB; Hum and noise better than -70dB.

TUAC DISCOTHEQUE MIXER WITH AUTO FADE



£31-50

Designed for the discerning D.J. of professional standard. Offering a vast variety of functions. Controls: Mic Vol; Tone, over-ride depth; auto/Manual Sw; Tape Vol; L & R Deck Faders; Deck Volume; Treble and Bass; H. Phon Vol Selector; Master Vol On/Off Sw. Max output 1V RMS.

Specification: Deck Inputs—50mV into 1MΩ; Deck Tone Controls—treble +20 -10dB at 12kHz; Bass +22 -15dB at 40Hz; Mic Input—200 ohms upwards, 2mV into 10kΩ; Mic Tone Control—Total Variation Treble 15dB, Total Variation Bass 10dB; Tape Input—30mV into 47kΩ; Power Requirements—30-50 volts at 50mA.

PANEL SIZE
18 x 4½in.
DEPTH 3in.

HOW TO ORDER BY POST


Make cheques/P.O.s payable to TUAC LTD (PW5)
or quote Access/Barclay Card No.
and post to TUAC LTD (PW/5)
163 Mitcham Road, London, SW17 9PG
We accept phone orders against
Access/Barclay Card Holders
Phone: 01-672 3137/9080

STOCKISTS—CALLERS ONLY


Arthur Sallis Ltd., 28 Gardner Street. Tel. Brighton 65806
Bristol Disco Centre, 86 Stokes Croft. Tel. Bristol 41666
Socodi, 9 The Friars. Tel. Canterbury 60948
Cookies, 132 West Street. Tel. Crewe 4739
Calbarrie Audio, 88 Wellington Street. Tel. Luton 411733
Al Music Centre, 88 Oxford Street. Tel. Manchester 236 0340
Damon Electronics, 99 Carrington Street. Tel. Nottingham 53880
Electra Centre, 58 Lancaster Road. Tel. Preston 58488
Mitchell Electronics, 64 Winchester Street. Tel. Salisbury 23689
Wec Lighting, 10 Commercial Road. Tel. Southampton 28102

ALL PRICES INCLUDE V.A.T. (8%) AND POSTAGE AND PACKING

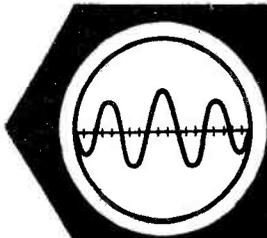ACCESS & BARCLAY CARDS ACCEPTED JUST SEND OR PHONE US YOUR NUMBER H.P. ENQUIRIES INVITED.




TUAC

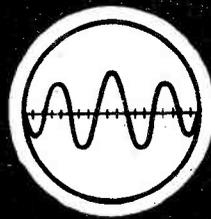

TRANSISTOR UNIVERSAL AMPLIFICATION CO. LTD.
163 MITCHAM RD. LONDON SW17 9PG 01-672 3137/9080

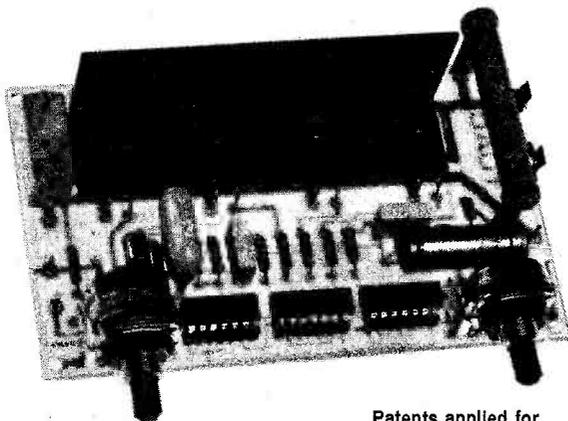NEW !!! 4 CHANNEL SOUND TO LIGHT SEQUENCER—4LSMI



- R.C.A. 8 amp Triacs
- 1000W per channel
- Fully suppressed and fused
- Switched master control for sound operation from 1/2W to 125W
- Speed control for fixed rate sequence from 8 per minute to 50 per second
- Full logic integrated circuitry with optical isolation for amplifier protection
- Full wave control
- 13 easy connections

Patents applied for


£22.00

3 CHANNEL LIGHT MODULATOR


- R.C.A. 8 amp Triacs
- 1000W per channel
- Each channel fully suppressed and fused
- Master control to operate from 1W to 100W
- Full wave control
- 12 easy connections.

Single Channel Version 1500 watts **£7.25**

£15.50

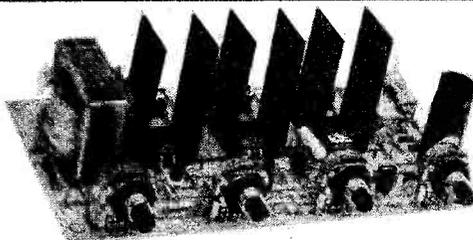

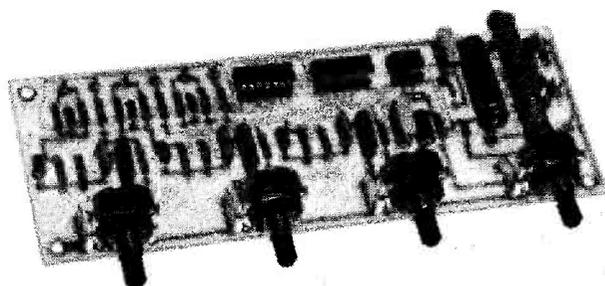
ADD SEQUENCE AND DIMMING EFFECTS TO YOUR TUAC 3 CHANNEL LIGHT MODULATOR



SEQUENCE DIMMER MODULE—3SDMI

Speed Control 3 per min. to 10 per sec.
Full logic integrated circuitry
Dimmer control to each channel
9 easy connections

£9.50

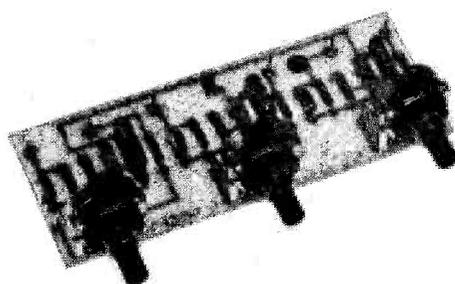

DIMMER MODULE—LMDI

Dimmer control for each channel
7 easy connections

£4.25

MANUFACTURERS OF ELECTRONIC AND AMPLIFICATION EQUIPMENT
SPECIALISTS IN QUALITY TRANSISTOR EQUIPMENT OPEN 6 DAYS A WEEK 9.30 am 6.00pm

TRANSFORMERS

MAINS ISOLATING

PRI 120/240V SEC 120/240V
CENTRE TAPPED AND
SCREENED

| Ref. | VA (Watts) | £ | p & p |
|------|---------------|-------|-------|
| No. | | | |
| 07 | 20 | 2-80 | 38 |
| 149 | 60 | 4-37 | 45 |
| 150 | 100 | 4-89 | 45 |
| 151 | 200 | 8-13 | 53 |
| 152 | 250 | 9-83 | 73 |
| 153 | 350 | 11-88 | 73 |
| 154 | 500 | 13-65 | 91 |
| 155 | 750 | 20-51 | BRS |
| 156 | 1000 | 29-15 | BRS |
| 157 | 1500 | 33-23 | BRS |
| 158 | 2000 | 37-07 | BRS |

12 and or 24 Volt

PRIMARY 240-250 VOLTS

| Ref. | 12v | 24v | £ | p & p |
|------|-----|------|-------|-------|
| No. | | | | |
| 111 | 0-5 | 0-25 | 1-35 | 30 |
| 213 | 1-0 | 0-5 | 1-74 | 30 |
| 71 | 2 | 1 | 2-29 | 38 |
| 18 | 4 | 2 | 2-86 | 38 |
| 70 | 6 | 3 | 4-12 | 45 |
| 108 | 8 | 4 | 4-56 | 45 |
| 72 | 10 | 5 | 5-14 | 53 |
| 116 | 12 | 6 | 5-52 | 53 |
| 17 | 16 | 8 | 7-28 | 60 |
| 115 | 20 | 10 | 10-39 | 73 |
| 187 | 30 | 15 | 13-59 | 83 |
| 226 | 60 | 30 | 16-83 | BRS |

30 VOLT RANGE

SECONDARY TAPS
0-12-15-20-25-30

| Ref. | No. | Amps | £ | p & p |
|------|------|------|------|-------|
| 112 | 0-5 | | 1-81 | 30 |
| 79 | 1-0 | | 2-40 | 38 |
| 3 | 2-0 | | 3-49 | 38 |
| 20 | 3-0 | | 4-53 | 45 |
| 21 | 4-0 | | 5-13 | 53 |
| 51 | 5-0 | | 6-41 | 53 |
| 117 | 6-0 | | 7-16 | 60 |
| 88 | 8-0 | | 9-87 | 67 |
| 89 | 10-0 | | 9-90 | 73 |

50 VOLT RANGE

SECONDARY TAPS
0-19-25-33-40-50

| Ref. | No. | Amps | £ | p & p |
|------|------|------|-------|-------|
| 102 | 0-5 | | 2-58 | 30 |
| 103 | 1-0 | | 3-38 | 38 |
| 104 | 2-0 | | 4-68 | 45 |
| 105 | 3-0 | | 5-81 | 53 |
| 106 | 4-0 | | 7-60 | 67 |
| 107 | 6-0 | | 12-10 | 67 |
| 118 | 8-0 | | 12-98 | 85 |
| 119 | 10-0 | | 16-99 | BRS |

60 VOLT RANGE

SECONDARY TAPS
0-24-30-40-48-60

| Ref. | No. | Amps | £ | p & p |
|------|------|------|-------|-------|
| 124 | 0-5 | | 2-33 | 38 |
| 126 | 1-0 | | 3-41 | 38 |
| 127 | 2-0 | | 5-08 | 45 |
| 125 | 3-0 | | 7-52 | 60 |
| 123 | 4-0 | | 8-75 | 67 |
| 40 | 5-0 | | 9-75 | 73 |
| 120 | 6-0 | | 11-30 | 85 |
| 122 | 8-0 | | 15-00 | BRS |
| 122 | 10-0 | | 17-52 | BRS |
| 189 | 12-0 | | 19-98 | BRS |

AUTO TRANSFORMERS

Ref VA Auto Taps

| Ref. | VA | Auto Taps | £ | p & p |
|------|------|-------------------|-------|-------|
| 113 | 20 | 0-115-210-240 | 1-67 | 30 |
| 64 | 75 | 0-115-210-240 | 2-90 | 38 |
| 4 | 150 | 0-115-210-220-240 | 4-12 | 45 |
| 66 | 300 | " | 5-82 | 53 |
| 67 | 500 | " | 8-82 | 67 |
| 84 | 1000 | " | 13-68 | 91 |
| 93 | 1500 | " | 18-11 | BRS |
| 95 | 2000 | " | 24-20 | BRS |
| 73 | 3000 | " | 35-09 | BRS |

CASED AUTO TRANSFORMERS

240V mains lead input and USA 2 pin
outlets 20VA £3-23 p & p 38p.
500 VA £10-45 p & p 80p
1000 VA £17-51 BRS

HIGH VOLTAGE

Mains Isolating

| PRI | SEC | VA | Ref. | £ | p & p |
|------------|-------|-------|------|---|-------|
| 200/220 OR | | | | | |
| 400/440 | | | | | |
| 100/120 OR | | | | | |
| 200/240 | | | | | |
| 60 | MT247 | 4-37 | 63 | | |
| 350 | MT247 | 10-41 | 95 | | |
| 1000 | MT250 | 27-06 | BRS | | |
| 2000 | MT252 | 41-07 | BRS | | |

MINIATURE TRANSFORMERS

WITH SCREENS

| Ref | MA | Volts | £ | p & p |
|-----|----------|------------------|------|-------|
| 238 | 200 | 3-0-3 | 1-54 | 10 |
| 212 | 1A, 1A | 0-6, 0-6 | 1-84 | 30 |
| 13 | 100 | 9-0-9 | 1-41 | 13 |
| 235 | 330, 330 | 0-9, 0-9 | 1-56 | 19 |
| 207 | 500, 500 | 0-8-9, 0-8-9 | 1-92 | 30 |
| 208 | 1A, 1A | 0-8-9, 0-8-9 | 3-30 | 38 |
| 236 | 200, 200 | 0-15, 0-15 | 1-43 | 19 |
| 214 | 300, 300 | 0-20, 0-20 | 1-93 | 30 |
| 221 | 700(DC) | 20-12-0-12-20 | 2-17 | 38 |
| 206 | 1A, 1A | 0-15-20, 0-15-20 | 3-46 | 38 |
| 203 | 500, 500 | 0-15-27, 0-15-27 | 3-00 | 38 |
| 204 | 1A, 1A | 0-15-27, 0-15-27 | 3-85 | 38 |

BRIDGE RECTIFIERS

| 50v | 100v | 200v | 400v | 600v | PM7A6 | £2-35 |
|-----|------|------|------|------|-------|-------|
| 2A | 2A | 1A | 4A | 2A | | |
| | | | | | | |
| | | | | | | |
| | | | | | | |
| | | | | | | |
| | | | | | | |

POWER UNITS

AI25 6-9v at 200mA in moulded
case forming a 2 pin 5A plug
£2-48 P & P 25p.
CC12-05 Output Switched
3-4-5-6-7 5-9-12V at 500mA
£4-08 P & P 30p.

CARBON FILM RESISTORS

1/2W 10 ohm-1 Mohm
90p per 100, inc. P & P.

CAPACITORS

MINIATURE CERAMICS
22pF-0-047mfd 30p per doz.
PAPER (Metal case)
0-01-0-025-0-05-0-1mfd
85p per doz. P & P 15p

METERS

| AVO 8 Mk 5 | AVO 72 | U4313* | U4315* | £ |
|------------|--------|--------|--------|-------|
| | | | | 50-80 |
| | | | | 19-75 |
| | | | | 11-80 |
| | | | | 13-85 |

MAINS KEYNECTORS

£3-25. P & P 25p.

PLEASE ADD 25+ VAT

INCLUDING P & P.

MAINS TIMER

Delay 1-30 minutes
(Adjustable)
£5-95. P & P 25p.

ELECTROSIL AND

SEMICONDUCTOR STOCKIST
SEND STAMP FOR CAT.

Barrie Electronics Ltd.

3, THE MINORIES, LONDON EC3N 1BJ

TELEPHONE: 01-488 3316/8

NEAREST TUBE STATIONS: ALDGATE & LIVERPOOL ST.



4 1/2 in x 3 1/2 in METER. 30µA,
50µA or 100µA, £3-85. P. & P. 13p.

**TAPE
RECORDER
LEVEL
METER**

500µA, 80p
P. & P. 10p.



**CARDIOID
DYNAMIC
MICROPHONE**

Model UD-130. Fre-
quency response 50-
15,000c/s. Impedance
50K and 600 ohms,
£7-40. P. & P. 13p.

42 x 42mm METERS 1mA,
10mA, 100mA, 500mA, £2-76,
11p P. & P.
60 x 45mm METERS 50µA,
100µA, 500µA and 1mA VU
METER £2-92, 11p P. & P.

**EDGEWISE METERS, 90mm x
34mm, 1mA £3-40, 13p P. & P.**

**MULTI-
METER**

Model IIT-2
20,000 ohm/
volt, £6-90.
P.&P. 16 1/2p.



3 WATT STEREO AMPLIFIER

Dual 50K and 600 ohms,
1 1/2W PER CHANNEL
£4-30. P. & P. 12 1/2p.

All above prices include V.A.T. LARGE S.A.E. for List No. 12.
Special prices for quantity quoted on request.

M. DZIUBAS

158 Bradshawgate · Bolton · Lancs. BL2 1BA

CLOCK COMPONENTS

PW Clock Constructors—
See starred ★ items

DISPLAYS

★ DL704E 0-3 Red CC LED—Pin-for-pin direct replacement
for MAN3640
★ MAN3M 0-13" Red CC LED 48p FNF500 0-5" Red CC LED £2-20
★ CRYSTAL TIMEBASE—suitable for any digital clock
32.768 kHz min. Xtal: High accuracy/stability—can be used
with CMOS divider & logic to provide stable 50 cps
(circuit provided, CMOS & PCB available—details in price list) £3-60

IC's

MK50253 4 or 6 digit, 12 or 24 hr format, alarm clock... £5-60
(PCBs, Kits available for alarm clock with 8no.2s,
intensity control, 4/6 digits—all in our Price List)

★ AY51224

4digit clock £4-25

★ SOLDERCON IC PIN SOCKETS

The sensible method for lowest cost sockets for ICs, displays, CMOS, TTL
(nylon supports available if required. Samples encl. with any pin order)
Strip of 100 for 50p 400 for £2 1000 for £4 3000 for £10-50

CMOS CMOS CMOS CMOS CMOS

Widest stock range in UK—from RCA, Motorola, National,
Siltek only

| | | | | | | | | | |
|--------|------|--------|------|--------|-------|--------|-------|---------|------|
| CD4000 | 0-21 | CD4021 | 1-63 | CD4040 | 1-86 | CD4059 | 16-60 | CD4085 | 1-17 |
| CD4001 | 0-21 | CD4022 | 1-69 | CD4041 | 2-02 | CD4060 | 2-29 | CD4086 | 1-17 |
| CD4002 | 0-21 | CD4023 | 0-21 | CD4042 | 1-37 | CD4061 | 20-63 | CD4083 | 1-43 |
| CD4006 | 1-47 | CD4024 | 1-16 | CD4043 | 2-02 | CD4062 | 7-33 | CD4085 | 1-82 |
| CD4007 | 0-21 | CD4025 | 2-01 | CD4044 | 2-02 | CD4063 | 2-22 | CD4089 | 2-73 |
| CD4008 | 1-63 | CD4026 | 1-96 | CD4045 | 2-29 | CD4066 | 1-05 | MC14501 | 0-32 |
| CD4009 | 0-67 | CD4027 | 0-81 | CD4046 | 2-02 | CD4068 | 0-28 | MC14502 | 0-85 |
| CD4010 | 0-87 | CD4028 | 1-40 | CD4047 | 1-37 | CD4069 | 0-26 | MC14508 | 4-20 |
| CD4011 | 0-21 | CD4029 | 1-96 | CD4048 | 0-78 | CD4070 | 0-26 | MC14510 | 1-26 |
| CD4012 | 0-21 | CD4030 | 0-65 | CD4049 | 0-62 | CD4071 | 0-26 | MC14511 | 1-95 |
| CD4013 | 0-63 | CD4031 | 4-05 | CD4050 | 0-62 | CD4072 | 0-26 | MC14518 | 1-87 |
| CD4014 | 1-62 | CD4032 | 1-77 | CD4051 | 2-57 | CD4073 | 0-26 | MC14520 | 1-87 |
| CD4015 | 1-62 | CD4033 | 2-48 | CD4052 | 2-57 | CD4075 | 0-26 | MC14528 | 0-87 |
| CD4016 | 0-67 | CD4034 | 8-28 | CD4053 | 2-57 | CD4076 | 1-63 | MC14553 | 4-07 |
| CD4017 | 1-63 | CD4035 | 1-63 | CD4054 | 1-96 | CD4077 | 0-65 | MC14553 | 4-07 |
| CD4018 | 2-29 | CD4036 | 7-88 | CD4055 | 1-96 | CD4078 | 0-26 | MC14566 | 1-21 |
| CD4019 | 0-73 | CD4037 | 1-83 | CD4056 | 1-96 | CD4081 | 0-26 | MC14585 | 1-45 |
| CD4020 | 1-82 | CD4038 | 1-80 | CD4057 | 24-30 | CD4082 | 0-26 | MM74C14 | 1-16 |

RCA 1975 CMOS Databook: Pin-Outs, 400 pages of data, 200 pages of
circuits, applications and use £2-30 (No VAT) + 37p p & p.

ADD VAT at 8% (higher rate does not apply to any of above) 10p p & p on
orders under £2—Despatch is 1st Class Post BY RETURN! Price List sent
FREE with any order, or on request (an s.a.e helps) Official orders welcomed
(written or phoned)—Univs, Polys, Govt, Cos. etc. Export orders: No VAT,
Add 35p (Europe) 70p (overseas) for Air Mail p & p

SINTEL, 53n Aston Street, Oxford. Tel: 0865 43203

**ADD APPROPRIATE
V.A.T. P. & P. &
INSURANCE EXTRA.**



**ALL ITEMS SUBJECT TO
MANUFACTURERS INCREASE
AND AVAILABILITY**
**Personal
Callers are
Welcome!**

**High Quality
Construction
Kits, stocked at
all branches
Send for
catalogue!**

AMPLIFIERS
P. & P. 95p, Ins. £1-00
Sansui AU2200 £49-00
AU4400 £75-00
Sinclair 4000 £50-00
Pioneer SA5300 £45-60
Bush Arina A220 £37-95

TUNERS & RECEIVERS
P. & P. 95p, Ins. £1-00
Sinclair 4000 Tuner £43-95
Rotel RT222 £45-30
Pioneer SX434 £97-80
SX400 £75-15
Rotel 152 £71-45
Rotel RX202 £81-09
Sansui
441 AM/FM/MPX £79-95
TU 4400 £75-00
Bush Arina BH4000 £84-65

RECORD DECKS (Ins. 50p)
P. & P. 85p
Garrard SP25 MkIV £14-75
BSR MP60 £12-75
Garrard
SP25 MkIV P & C £25-45
Goldring GL78 P & C/Connoisseur £56-00

TAPE DECKS (Insurance 2-00)
P. & P. 95p
Akai CR81D 8-track Rec. player £85-95
GXCR2D £95-95
Akai 4000DS Reel to Reel £103-05
Akai CS33D £84-00
Sansui SC 737 £114-65
Sansui SC 636 £99-70
Wharfedale 20D £72-10

SPEAKERS
P. & P. 45p, Ins. £1-00
Chassis Speakers
EMI (Plain) 13in x 8in, Bass unit with Single Tweeter (only 8 ohm) £2-50
with Tweeter and Crossover 3, 8 or 15 ohm £2-75
Type 350 Kit 15 watt 8 ohm £4-25
13in x 8in Bass unit 15 watt, 8 ohm or 15 ohm £8-25
8 ohm or 15 ohm £5-45
8in x 5in 5 watt 3, 8 or 15 ohm £1-70
8in x 5in 10 watt Dualcone 8 ohm £2-95
6 1/2" 10 watt 8 ohm £2-65
8in 10 watt 8 ohm £4-50
8in 4 or 15 ohm £2-25
7in x 4in 3 or 8 ohm £1-30
Elac 6 1/2" 8 ohm Dualcone £2-65
Elac 8in 8 ohm Dualcone £2-70
Elac 10in 8 ohm Dualcone £3-75
Baker Group 25 12in 8 or 15 ohm £12-00
Aadstra "Top 20" 12in 25 watt 8 or 15 ohm £8-25
Aadstra "Hi-Ten" 10in 10 watt 8 or 15 ohm £3-75
Global 8 ohm 5 watt £7-95 pr.
Also 5in 8 ohm speaker £0-95
2 1/2in 8 or 64 ohm speaker 60p

WHARFEDALE SPEAKER BARGAINS
P. & P. 85p, Ins. £1-00
Denton 1 pr. £25-35
Denton 2 pr. £32-00
Denton 3 pr. £34-20
Linton 3 pr. £47-60

KITS
Linton 2 pr. £20-95
Glendale 3 pr. £35-95

SPEAKER CABINETS IN KIT FORM (Teak Veneer)
P. & P. 85p (Ins. £1-00 per pr.)
12in x 8in x 4 1/2in (8 x 5 or 7 x 4 cutout) £3-75
12in x 12in x 7 1/2in (10", 8 x 5, 8", 6 1/2" & 3 1/2") £5-25
18in x 11in x 7 1/2in (8" x 2 1/2" or 13 x 8) £6-56
22in x 14in x 7 1/2in (12" & 2 1/2" or 13 x 8) £7-96

TWEETERS & CROSSOVERS
P. & P. 25p
Cone Tweeter 10 watt 8 or 15 ohm (K2006) £2-95
Cone Tweeter 3 watt 8 ohm (K2003) £1-55
Horn Tweeter 8 ohm (K2007) £6-50
Dome Tweeter 8 ohm (K2011) £5-75
2-way Crossovers (CN23, CN28, CN216) £1-40
3-way Crossover (CN38) £2-85

CARTRIDGES & STYLII
P. & P. 25p
ACOS
GP91/25C or 3CS (ster. comp) 1-10 1-25
GP93/1 or 95/1 ster. cryst. 1-35 1-25
GP94/1 or 96/1 ster. ceram. 1-75 1-25
GP101 cryst. comp. 90 —
GP104 ster. ceram. 1-95 1-25
BSR
X5M or X5H cryst. comp. 1-95 1-25
SX6M or SX6H cryst. ster. 2-10 1-25
SC5M ster. ceram. 2-85 1-25
SONOTONE
9TAHC or 9TAHC/G (Diam.) 1-95 1-25
3509 Magnetic AUDIO TECNICA AT55 1-95 —
EMPIRE 999 REX 3-95 —
GOLDRING
GB50 3-10 1-95
GB00 4-25 1-95
GB00H 4-25 1-95
GB00E 7-25 3-95

SHURE CARTRIDGES & STYLII
M44G 4-95 3-95
M55E 6-25 4-95
M75ED Type 2 11-75 8-25
MJ5EJ Type 2 9-75 6-25
V15 Type 3 32-25 —

MICROPHONES
P. & P. 25p
UDI30 50K/600 ohm uni-dir. ball metal £6-75
UDI47 £9-25
Condenser Mic. 600 ohm uni-dir. £9-50
Cassette Stick Mic. with R/Control £1-65
Cass. Stick Mic. with R. control (Philips type) £2-00
TW209 £5-90

HEADPHONES P. & P. 25p
Rotel
RH430 £4-75
RH 630 £7-75
RH 700 £11-50
Koss
K711 £11-65
KRD711 £11-65
K6 £13-00
K6LC £14-88
KO727B £15-95
KO747 £21-95
HVI £24-75
PRO4AA £29-40
PROSLC £32-20
K6LCQ £27-06
Sansui SS10 £16-75
*Headphone adaptor (Junction box) £2-75
extension lead 2ft curly £1-50

CLOCK RADIOS P. & P. 45p
Bush CR12B LW/MW £15-50
Bush CR232 MW/VHF £24-95
Murphy MV5600 MW/VHF £22-95
Vega Signal 2 wave band £9-95

CASSETTE RECORDERS
P. & P. 45p
Bush TP66 M/Batt £25-75
Murphy BA200 M/Batt £22-75
Bush BT8504 (miniature) £25-50
Mains Battery Cass. £15-50

RADIO CASSETTES
P. & P. 25p
(Mains/Batt.)
Murphy BA209 MW/VHF £33-50

STEREO RECORD PLAYER & SYSTEM P. & P. 25p
Hanimec HRC5060 8-track AM/FM/MPX+Speaker £116-95

CAR AUDIO P. & P. 25p
Hitachi Car Radio WM702R LW/MW £16-50
KM1510 LW/MW/VHF £32-50
Battery Eliminators 240 in 6, 7.5 or 9 volt output £3-10

SINCLAIR PROJECT 80
P. & P. 45p
Stereo Pre-amp. £12-95
Active Filter Unit £7-25
Z40 15 watt Amp £5-75
Z60 25 watt Amp £7-25
P25 Power Supply for 240 £5-45
P26 Power Supply for 240 £8-45
P28 Power Supply for 260 £8-25
FM Tuner £12-95
Stereo Decoder £8-45
Q16 Speaker £7-75
IC20 Stereo Amp. Kit £7-45
PZ20 Power Kit £5-25

PORTABLE RADIOS
P. & P. 45p
Meridian Mk. II £12-25
Vega Sapphire £8-75
Vega VEF206 £15-50
Selena LM/MW/FM/SSW £22-50
Murphy
B833 MW/VHF £9-95
BA838 LW/MW/VHF M/Batt £18-50
MA5003 Head Set Radio LW £7-95

Bush
VTR165 LW/MW/VHF £22-00
VTR127 LW/MW/VHF £15-50
VTR 175 LW/MW/VHF £13-95
VTR188 LW/MW/VHF 25W M/Batt £31-95
BY5661 LW/MW/VHF £14-95
Selga 2 wave band with leather case £5-50

CASSETTES P. & P. 25p
C40 C60 C90 C120
BASF
Scotch Dyna 65p, 83p, £1-20
Super SM — 95p 122p 170p
Low Noise — 35p 45p 55p
Philips — 55p 75p 110p
Memorex 65p 79p 110p 155p
Amplex (360) 45p 55p 75p 99p
Amplex (20-20+) 59p 65p 99p 135p
Chromium Dioxide — 99p 140p —

Cassette Head Cleaner 45p
Amplex Head Cleaner Demag £1-65
BIB Stereo Test Cassette £2-15
Cassette Racks (hold 6) £0-45
Cassette Rotating Racks (hold 20) £3-50
Cassette Carrying Case (hold 18) £1-95
8-Track Cartridge Blanks
C40 C64 C80 80p 95p £1-10
Amplex
8-track H/Cleaner Demagnetiser £1-90
8-track Carrying Cases (BIB) £1-65

TAPES P. & P. 25p
Cases
5" 55p 65p 1-00 20p
5 1/2" 65p 86p 1-35 25p
7" 80p 110p 1-85 30p
High frequency Amplex
5" — 1-40p 1-55p
7" — 1-90p 2-95p

AKAI Metal Reel 7" £2-10
CALCULATORS P. & P. 25p
VAT INCLUDED
Sinclair Cambridge Build £12-95
Sinclair Cambridge with memory £17-95
Scientific £19-95

ALL MERCHANDISE FULLY GUARANTEED

**NEWMART
ELECTRONICS**

Mail Order Dept PW/9
**Belmont St, Monton,
Eccles, Manchester.**
Tel: 061-789 5268

Manchester
30-32 Shudehill, tel 061-832 7710
Leeds
4 New Market St tel 0532 42708
Liverpool
15 Whitechapel tel 051-236 0738

Please bring this advertisement to obtain the benefit of these special prices



GIRO NO. 331 7056. Access accepted.
C.W.O. only. P. & P. 15p on orders below £5
Discount: £10-10%, (except net items)
Export Order enquiries welcome (VAT free)

Official Orders accepted from
Educational & Government Departments
ALL PRICES INCLUDE VAT at 8%

PLEASE ADD AN EXTRA 15% VAT EXCEPT ON TEST METERS, AND VEROBOARD
SPECIAL RESISTOR KITS (Prices include post & packing)

10E12 1/2W KIT: 10 of each E12 value, 22 ohms—1M, a total of 570 (CARBON FILM 5%), £3.85 net
25E12 1/2W KIT: 25 of each E12 value, 22 ohms—1M, a total of 1425 (CARBON FILM 5%), £9.00 net

Due to current world shortages, resistor kits may contain some wattage and value substitutions.

MULLARD POLYESTER CAPACITORS C280 SERIES
250V P.C. Mounting: 0-0.1µF, 0-0.15µF, 0-0.22µF, 0-0.33µF, 0-0.47µF, 3/4p, 0-0.68µF, 1p, 0-1µF, 4p, 0-1.5µF, 5p, 0-2.2µF, 6p, 0-3.3µF, 8p, 0-4.7µF, 10p, 0-6.8µF, 13p, 1µF, 16p, 1-5µF, 24p, 2-2µF, 27p.

MULLARD POLYESTER CAPACITORS C296 SERIES
400V: 0-0.01µF, 0-0.015µF, 0-0.022µF, 0-0.033µF, 0-0.047µF, 3p, 0-0.068µF, 0-0.1µF, 0-0.15µF, 0-0.22µF, 0-0.33µF, 3/4p, 0-0.47µF, 0-0.68µF, 0-1µF, 4/4p, 0-1.5µF, 7p, 0-2.2µF, 9p, 0-3.3µF, 13p, 0-4.7µF, 15p.
160V: 0-0.01µF, 0-0.15µF, 0-0.22µF, 3/4p, 0-0.47µF, 0-0.68µF, 4p, 0-1µF, 4/4p, 0-1.5µF, 5/4p, 0-2.2µF, 6p, 0-3.3µF, 7p, 0-4.7µF, 9p, 0-6.8µF, 13p, 1µF, 15p.

MINIATURE CERAMIC PLATE CAPACITORS
50V: (pF) 22, 27, 33, 39, 47, 56, 68, 82, 100, 120, 150, 180, 220, 270, 330, 390, 470, 560, 680, 820, 1K, 1K5, 2K2, 3K3, 4K7, 6K8, (µF) 0-0.01, 0-0.015, 0-0.022, 0-0.033, 0-0.047, 2/4p, each, 0-1, 30V, 5p.

POLYSTYRENE CAPACITORS 160V 5%
(pF) 10, 15, 22, 33, 47, 68, 100, 150, 220, 330, 470, 680, 1000, 1500, 2200, 3300, 4700, 6800, 10,000, 4/4p.

RESISTORS
CF—High Stab Carbon Film, 5% MF—High Stab Metal Film, 5%

| W. Type | Range | 1-99 | 100-499 | 500-999 | 1000+ | Size mm |
|---------|--------|------|---------|---------|-------|----------|
| CF | 22-1M | 1 | 0-80 | 0-65 | 0-60 | 2-4x7-5 |
| CF | 22-2M2 | 1 | 0-80 | 0-65 | 0-60 | 3-9x10-5 |
| CF | 22-1M | 1 | 0-80 | 0-65 | 0-60 | 5-5x16 |
| MF | 10-2M7 | 2 | 1-7 | 1-4 | 1-2 | 3x7 |
| MF | 10-2M2 | 2 | 1-6 | 1-3 | 1-1 | 4-2x10-8 |
| MF | 10-10M | 3 | 1-98 | 1-81 | 1-65 | 6-6x13 |
| MF | 10-10M | 4-5 | 3-52 | 3-08 | 2-75 | 8x17-5 |

(Price in pence each).

VALUES AVAILABLE—E12 Series only. (Net prices above 100.)

PRESET SKELETON POTENTIOMETERS
MINIATURE 0-25W Vertical or horizontal 7p each 1K, 2K2, 4K7, 10K, etc. up to 1M Ω
SUB-MIN 0-05W Vertical, 100 Ω to 220K Ω 7p each.



B. H. COMPONENT FACTORS LTD.

(P.W.) LEIGHTON ELECTRONICS CENTRE,
59 NORTH ST., LEIGHTON BUZZARD, BEDS.
Tel.: LEIGHTON BUZZARD 2316 (STD. Code 05253)
CATALOGUE No. 4 20p

Miniature Mullard Electrolytics

| | | | |
|-----------|-----|-------------|-----|
| 1-0µF 63V | 7p | 100µF 25V | 7p |
| 1-5µF 63V | 7p | 100µF 63V | 17p |
| 2-2µF 63V | 7p | 150µF 16V | 7p |
| 3-3µF 63V | 7p | 150µF 63V | 17p |
| 4-0µF 63V | 7p | 220µF 6-4V | 7p |
| 4-7µF 63V | 7p | 220µF 10V | 7p |
| 6-8µF 63V | 7p | 220µF 16V | 8p |
| 10µF 63V | 7p | 220µF 63V | 25p |
| 10µF 63V | 7p | 330µF 16V | 14p |
| 15µF 16V | 7p | 330µF 63V | 28p |
| 15µF 63V | 7p | 470µF 6-4 | 28p |
| 22µF 40V | 7p | 470µF 40V | 28p |
| 22µF 25V | 7p | 680µF 16V | 17p |
| 22µF 63V | 7p | 680µF 40V | 28p |
| 30µF 10V | 7p | 1000µF 16V | 25p |
| 33µF 16V | 7p | 1000µF 25V | 28p |
| 33µF 63V | 7p | 1500µF 6-4V | 17p |
| 47µF 10V | 7p | 1500µF 16V | 28p |
| 47µF 25V | 7p | 2200µF 10V | 28p |
| 47µF 63V | 8p | 3300µF 6-4V | 28p |
| 68µF 16V | 7p | | |
| 68µF 63V | 14p | | |
| 100µF 10V | 7p | | |

VEROBOARD 0-1 0-15

| | |
|------------------------|-------|
| 2 1/2 x 5" | 36p |
| 2 1/2 x 3 1/2" | 33p |
| 3 1/2 x 3 1/2" | 42p |
| 3 1/2 x 3 1/2" | 36p |
| 2 1/2 x 3 1/2" | 10p |
| 2 1/2 x 5" (Plain) | — 19p |
| 2 1/2 x 3 1/2" (Plain) | — 16p |
| 5 x 3 1/2" (Plain) | — 29p |
| Insertion tool | 73p |
| Track Cutter | 36p |
| Fins, Pckt. 50 | 22p |

POTENTIOMETERS
Carbon Track 5K Ω to 2M Ω, log or lin (and 1K lin). Single, 17p Dual Gang 48p. Log single with switch 28p. Slider Pots. 10K, 100K, 500K, semi log 30mm. 34p, 45mm, 47p, 60mm, 55p.

DIODES

| | | |
|------------|------------|-----|
| IN4001 61p | DIN 2 Pin | 12p |
| IN4002 71p | 3 Pin | 13p |
| IN4003 9p | 5 Pin 180° | 16p |
| IN4004 90p | Std. Jack | 20p |
| IN4005 12p | 2.5mm jack | 13p |
| IN4006 14p | Phono | 7p |
| IN914 7p | | |
| IN916 7p | DIN 2 Pin | 10p |
| BA100 10p | 3 Pin | 10p |
| OA5 42p | 5 Pin 180° | 12p |
| OA47 9p | Std. Jack | 13p |
| OA81 11p | 2.5mm jack | 13p |
| OA200 8p | Phono | 7p |

ELECTROLYTIC CAPACITORS. Tubular & Large Cans
(µF/V): 1/25, 2/25, 4/25, 4-7/10, 5/25, 8/25, 10/10, 10/50, 16/25, 22/63, 25/25, 25/50, 32/25, 50/25, 100/10, 100/25, 7p, 50/50, 8p, 100/50, 200/25, 10p, 250/50, 18p, 500/10, 8p, 500/25, 17p, 500/50, 25p, 1000/10, 17p, 1000/25, 25p, 1000/50, 40p, 2000/10, 20p, 1000/100, £11.6, 2000/25, 35p, 2000/100, £12.0, 2500/25, 38p, 2500/50, 68p, 5000/25, 69p, 5000/50, £1.20.

HI-VOLT: 4/350, 20p, 8/350, 23p, 100/100 27p, 16/350, 35p, 100/100, 27p, 100/250, 40p.

METALLISED PAPER CAPACITORS
250V: 0-0.05µF, 0-1µF, 6p, 0-25, 6p, 0-5µF, 7/4p, 1µF, 9p, 500V: 0-0.25, 0-0.5, 6p, 0-1, 6p, 0-1, 6p, 0-25, 7/4p, 0-5, 9p, 1000V: 0-0.1, 12p, 0-0.22, 13p, 0-0.47, 0-1, 19p, 0-22, 28p, 0-47, 36p.

MULTIMETER U4323
22 Ranges plus AF/IF Oscillator, 20,000Ω/Volt.
Vdc—0-3—1000V in 7 ranges
Vac—2-5—1000V in 6 ranges
Idc—0-05—300mA in 5 ranges
Resistance—5Ω—1MΩ in 4 ranges.
Accuracy—5% of F.S.D.
OSCILLATOR—1 KHz and 465 KHz (A. M.) at approx. Volt.
Size—160 x 97 x 40mm.
Supplied complete with carrying case, test leads and battery.
PRICE £8-64 net p & p 50p.



U4323

MULTIMETER U4341
27 Ranges plus Transistor Tester, 16,700Ω/Volt. Overload protected.
Vdc—0-3—900V in 8 ranges.
Vac—1-5—750V in 6 ranges.
Idc—0-06—600mA in 5 ranges.
Iac—0-3—300mA in 4 ranges.
Resistance—2KΩ—2MΩ in 4 ranges.
Accuracy—dc—2.5%, ac—4% of F.S.D.
Hfe—10—350 in 2 ranges.
Size—115 x 215 x 90mm.
Complete with steel carrying case, test leads, and battery.
PRICE £11-88 net p & p 50p.



U4341

MULTIMETER U4324
34 Ranges. High sensitivity, 20,000Ω/Volt. Overload protected.
Vdc—0-6—1200V in 9 ranges.
Vac—3—900V in 8 ranges.
Idc—0-06—3A in 6 ranges.
Iac—0-3—3A in 5 ranges.
Resistance—25Ω—5MΩ in 5 ranges.
Accuracy—dc and R—2% of F.S.D., ac and db—4% of F.S.D.
Size—167 x 98 x 63mm.
Supplied complete with storage case, test leads, spare diode, and battery.
PRICE £10-64 net p & p 50p.



U4324

MULTIMETER U4313
33 ranges. Knife edge with mirror scale, 20,000Ω/Volt. High accuracy, mVdc—75mV
Vdc—1-5—600V in 9 ranges.
Vac—1-5—600V in 9 ranges.
Idc—60—120 microamps in 2
Idc—0-6—1500mA in 6 ranges.
Iac—0-6—1500mA in 6 ranges.
Resistance—1KΩ—1MΩ in 4 ranges.
db scale—10 to +12db.
Accuracy—dc—1%, ac—2%
Size—115 x 215 x 90mm.
Complete with steel carrying case, test leads, and battery.
PRICE £14-90 net p & p 50p.



U4313

PAYS FOR ITSELF WITH DISCOUNT VOUCHERS WORTH 20p

66 PAGES
3000 ITEMS
600 PICTURES

YOUR COMPLETE ELECTRONIC STORES. MAIL ORDER AND SHOP

HAVE YOU GOT YOUR CATALOGUE NO. 4 NEW CONVENIENT SIZE, AND FULLY ILLUSTRATED.

CONTAINS MANY HARD TO GET ITEMS

20p

★ DISCOUNTS
★ ALL NEW STOCK
★ SATISFACTION GUARANTEE
★ DEPENDABLE SERVICE

poly-planar
20-Watt Full Range Speaker

Completely replaces the conventional cone speaker
Super-thin construction permits new installation ideas.

Power capability: 40 watts peak. Frequency range: 40 Hz-20 KHz
Sensitivity: 85 dB/M for 1 watt electrical input. Input Impedance: 8 ohms. Operating temperature range: -20°F to +175°F. Size (WxDxL): 1-7/16" x 1-3/4" x 1-4/16". Weight: 19 ounces.

£8.50 each Stereo pair £16.50
INCLUSIVE OF VAT AND POSTAGE

web europa
P.O. Box 9, Ruthin Clwyd

it is new! it's News!

mti
Pocket size medium wave signal generator. Can align, trim and tune I.F.s and M.W. bands. Variable frequency. Can also be used as SIGNAL INJECTOR. Price £ 3.50 by post parcel. Send bank draft with order.

Pen sized, fully transistorised handy signal injector.
Covers 1000 Hz. with harmonics upto 30 MHz.
Helps trouble-shoot any tube or transistor audio, I.F. and R.F. circuitry. Price £ 3.00

WHOLESALE ENQUIRIES WELCOME
CENTRAL IMPORTS & EXPORTS
68, MOUNT PLEASANT, WEMBLEY MIDDx (U.K.)


QUALITY* STEREO SOUND.

ALMOST **1/2 PRICE OFFER!** SOLENT AUDIO SYSTEM

£5.95 down

MADE TO SELL AT DOUBLE THE PRICE IN CABINET FORM

OUR PRICE £59.95

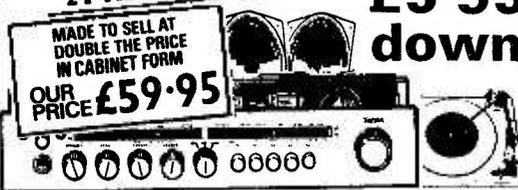

*Stereo Tuner Amplifier chassis with AM/FM radio covering long medium short and Stereo FM wavebands. Separate Base and Treble controls. 30 watts total power output (frequency response 25-20,00 Hz) Tape record and playback facilities. Dimensions 18" x 8 1/2" x 3 1/4". The very latest BSR automatic record deck with cue and pause control. Two matching elliptical speaker units.

Order early limited stocks available cash price £59.95. Credit Sale £5.95 deposit 9 monthly payments of £7.00 (Total Credit price £68.95). P. & P. £3.00. Send £8.95 today.

Chassis only available for cash at £42.00.

Full 12 months Guarantee.

CALLERS WELCOME.

Stereo headphones supplied with every complete order.

LEWIS Radio PW/9/75 100 CHASE SIDE SOUTHGATE LONDON N14 5PL Telephones: 01-882-1644

YOUR CAREER in RADIO & ELECTRONICS ?

Big opportunities and big money await the qualified man in every field of Electronics today—both in the U.K. and throughout the world. We offer the finest home study training for all subjects in radio, television, etc., especially for the **CITY & GUILDS EXAMS** (Technicians' Certificates); the Grad. Brit. I.E.R. Exam.; the **RADIO AMATEUR'S LICENCE**; P.M.G. Certificates; the R.T.E.B. Servicing Certificates; etc. Also courses in Television; Transistors; Radar; Computers; Servo-mechanisms; Mathematics and Practical Transistor Radio course with equipment. We have **OVER 20 YEARS'** experience in teaching radio subjects and an unbroken record of exam. successes. We are the only privately run British home study College specialising in electronics subjects only. Full details will be gladly sent without any obligation.

To: **British National Radio & Electronics School, Dept W.C. 95 P.O. Box 156, Jersey, C.I.**
Please send FREE BROCHURE to

NAME Block
ADDRESS Caps.
..... Please

**BRITISH NATIONAL RADIO
AND ELECTRONICS SCHOOL**


Lenco stereo cassette mechanisms from Goldring.

Lenco cassette mechanisms, as recommended by Practical Wireless for the Kempton and Ascot car stereo players, have major appeal for the enthusiast.

Both units are based on the famous STAAR designs, and the robust construction and precision engineering make these units ideal for use in car stereo players, Hi-fi systems, industrial and many other applications.



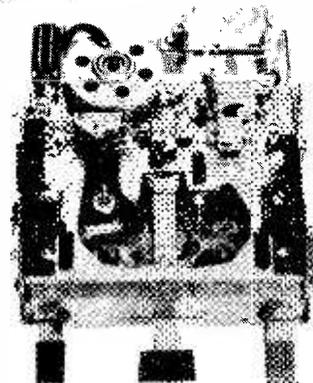Lenco CRV (as specified for the PW Ascot model). High quality unit, manufactured to hi-fi standards, with full facilities for both recording and playback. Features include fast forward, fast rewind, pause control, erase, auto stop and cassette ejection. £23.12 including packing, carriage and VAT.



Lenco FFR (as specified for the PW Kempton model). Cassette player with fast forward and rewind mechanism, auto stop and cassette ejection. £21.88 including packing, carriage and VAT.

To: Goldring Ltd., 10 Bayford Street, Hackney, London E8 3SE.

Please send me: Lenco FFR at £21.88

Lenco CRV at £23.12

I enclose PO, cheque for £ _____

NAME _____

ADDRESS _____

Goldring

To order, complete coupon and enclose Cheque or Postal Order made out to Goldring Ltd. Please cross out on coupon unit not required.

ERSIN

Multicore
5 CORE SOLDER

for fast easy reliable soldering
EASY TO USE DISPENSERS AND REELS
IDEAL FOR HOME CONSTRUCTORS

Ersin Multicore Solder contains 5 cores of non-corrosive flux. Instantly cleaning heavily oxidised surfaces. No extra flux is required.

SAVBIT handy solder dispenser



A coil of Ersin Multicore Savbit Solder in a dispenser 7 1/2 in of 18 s.w.g. (2.2 metres of 1.22mm). The Solder that reduces the wear of soldering iron bits.

Size 5 32p

SAVBIT solder for general purpose work

A handy plastic reel of SAVBIT alloy, 63ft of 18 s.w.g. (19.2 metres of 1.22mm)

Size 12 £1.80



ALU-SOL for soldering aluminium

New Multicore Alu-sol flux-cored solder in 16 s.w.g. No extra flux needed. Plastic reel holds 36ft. Supplied with full instructions. Also available in solder dispenser.

Size 4 £2.32



Fine gauge solder for soldering small components

Fine gauge solder for soldering small components 138ft of 22 s.w.g. (42.0 metres of 0.71mm) Ersin Multicore 5 core solder wound on a plastic reel. Suitable for intricate work and small components.

Size 10 £1.44



For soldering fine joints

Dispensers of Ersin Multicore Solder make those small jobs easier. 21ft of 22 s.w.g. (6.4 metres of 0.71mm) solder, specially suitable for soldering fine wires, small components and for repairing printed circuits.

Size 15 40p

Or size 19A for kit wiring or Radio and T.V. repairs 7ft. (2.1 metres) of 18 s.w.g. (1.22mm) Ersin Multicore Solder.

Size 19A 34p

NEW BIB WIRE STRIPPER & CUTTER



Fitted with unique 8 gauge selector with handle locking device and easy grip handles. Spring incorporated for automatic opening. Strips insulation from flex and cables in seconds and can also be used as a cutter. Model 8B. 80p

NEW SOLDER WICK



Absorbs solder instantly, from tags and printed circuits. Only needs 40 to 50 Watt soldering iron. Quick and easy to use. Does not need flux and is non-corrosive.

Size 18 90p

Bib Hi-Fi Accessories Limited,

Sole U.K. Sales Concessionaires, P.O. Box 78, Hemel Hempstead, Herts. HP2 4RH

Prices shown are recommended retail excluding VAT. From Electrical and Hardware Shops. If unavailable, send 20p P & P. Prices VAT at 8% in the U.K. Prices and specifications subject to change without notice.

Fully guaranteed Individually packed VALVES

| | | | | | | | |
|----------|-------|-------|-------|--------|-------|-----------|-------|
| A.1065 | 21-25 | ECL30 | 55p | GZ34 | 70p | PY81 | 40p |
| ARS | 55p | ECL32 | 35p | GZ37 | 21-90 | PY82 | 40p |
| ATP4 | 50p | ECL33 | 70p | KT86 | 42-50 | PY83 | 40p |
| B.12H | 22-00 | ECL36 | 50p | KT88 | 22-20 | PY88 | 45p |
| CY32 | 50p | EP36 | 85p | MH4 | 75p | PY600 | £1.00 |
| DAF96 | 50p | EP37A | | ML6 | 65p | PY80 | 45p |
| DF96 | 55p | | £1.20 | OA2 | 45p | PY81 | 50p |
| DK96 | 70p | EF40 | 75p | OS2 | | QQY03-10 | |
| DL92 | 40p | EF41 | 65p | PAB080 | 40p | QQY06-40A | |
| DI98 | 60p | EF80 | 30p | PC97 | 50p | | £1.40 |
| DY98/87 | 40p | EF83 | £1.25 | PC900 | 50p | | £8.00 |
| | 45p | EF86 | 35p | PC884 | 40p | R19 | 75p |
| DY802 | 45p | EF86 | 35p | PC885 | 40p | SCL400 | |
| E8800/01 | £1.80 | EF89 | 30p | PC889 | 50p | | £2.00 |
| E1800CC | 70p | EF92 | 50p | PC889 | 50p | SCL600 | |
| E182CC | £1.85 | EF96 | 45p | PC890 | 40p | | £5.00 |
| | | EF183 | 35p | PCF82 | 40p | SP61 | 75p |
| EA60 | 40p | EF184 | 35p | PCF84 | 40p | TT21 | £5.00 |
| EAB080 | 40p | EF190 | 75p | PCF86 | 80p | U26 | 85p |
| EAF42 | 75p | EL33 | £2.50 | PCF200 | 75p | U36 | 75p |
| EB91 | 30p | EL34 | 70p | PCF201 | 75p | U27 | 65p |
| EBC33 | £1.00 | EL36 | 60p | PCF802 | 50p | U901 | 75p |
| EBC41 | 75p | EL37 | £1.80 | PCF805 | 70p | U801 | 75p |
| EBF80 | 40p | EL41 | 80p | PCF806 | 75p | UAC80 | |
| EBF83 | 50p | EL42 | 55p | PCF808 | 80p | UAR42 | 65p |
| EBF89 | 40p | EL64 | 80p | PCF800 | 80p | UBC41 | 80p |
| EC92 | 35p | EL68 | 40p | PCF81 | 65p | UC65 | 45p |
| ECC31 | 40p | EL86 | 60p | PCL82 | 40p | UC85 | 45p |
| ECC82 | 35p | EL95 | 45p | PCF83 | 65p | UB89 | 40p |
| ECC83 | 35p | EL90 | 45p | PCL84 | 45p | UB11 | £1.00 |
| ECC84 | 35p | EL94 | 50p | PCL86 | 50p | UB21 | 70p |
| ECC85 | 40p | EM80 | 55p | PCL86 | 50p | UC85 | 45p |
| ECC86 | 50p | EM84 | 40p | PFL200 | 70p | UCF80 | 75p |
| ECC88 | 50p | EM84 | 40p | PL36 | 60p | UCH42 | 75p |
| ECC189 | 70p | EY67 | £1.00 | PL81 | 50p | UC851 | 45p |
| ECF80 | 40p | EY61 | 45p | PL82 | 45p | UCL82 | 45p |
| ECF82 | 40p | EY61 | 45p | PL83 | 45p | UCL83 | 45p |
| ECF801 | 75p | EY86 | 40p | PL84 | 45p | UC81 | 70p |
| ECH83 | 45p | EY88 | 50p | PL804 | 30p | UF80 | 35p |
| ECH84 | £1.40 | EZ40 | 70p | PL508 | 81.85 | | |
| ECH42 | 80p | EZ41 | 75p | PL509 | 81.85 | | |
| ECH81 | 35p | EZ80 | 30p | PL802 | £1.25 | | |
| ECH82 | 45p | EZ81 | 30p | PY33 | 60p | | |
| ECH84 | 45p | GY501 | 75p | PY80 | 40p | | |

TRANSISTORS, DIODES etc.

| | | | | | |
|--------|---------|------------|---------|---------|---------|
| AC 113 | AF 178 | BSY 38 | OAZ 200 | OC 206 | 2N 3054 |
| AC 126 | AF 186 | BSY 95A | OC 22 | SX 754 | 2N 3055 |
| AC 127 | AFZ 12 | BVZ 18 | OC 25 | ZR 11 | 2N 3391 |
| AC 128 | ASV 26 | CRS 1/10 | OC 26 | ZR 21 | 2N 3730 |
| AC 176 | ASV 27 | CRS 1/20 | OC 28 | IN 23A | 2N 3819 |
| ACY 18 | ASV 28 | CRS 1/50 | OC 29 | IN 26 | 2N 4028 |
| BC 108 | ACV 19 | CRS 1/40 | OC 35 | IN 32A | 2N 4028 |
| BC 118 | ACV 20 | CRS 3/10 | OC 38 | IN 38A | 2N 4061 |
| BC 119 | ACV 39 | CRS 3/20 | OC 42 | IN 43 | 2N 4785 |
| ACY 40 | ACY 40 | CRS 3/30 | OC 44 | IN 70 | 2N 6295 |
| AD 149 | AD 149 | CRS 3/40 | OC 45 | IN 277 | 2N 6296 |
| AD 161 | BC 148A | CRS 25/025 | OC 70 | IN 415C | 2N 154 |
| AD 162 | BC 172 | GET 115 | OC 73 | IN 4148 | 2N 159 |
| AD 163 | BC 172A | GXT 116 | OC 78 | 2N 466A | 2S 303 |
| ADZ 12 | BC 212A | GEX 66 | OC 81D | 2N 708 | 404 |
| AF 114 | BOY 31 | NKT 222 | OC 82 | 2N 918 | 2082 |
| AF 116 | BOY 33 | OA 5 | OC 82 | 2N 1304 | 40280 |
| AF 117 | BOY 72 | OA 47 | OC 82D | 2N 1305 | 40281 |
| AF 118 | BF 115 | OA 70 | OC 82MD | 2N 1307 | 40310 |
| AF 119 | BF 167 | OA 71 | OC 83 | 2N 1309 | 40668 |
| AF 124 | BF 185 | OA 73 | OC 139 | 2N 2062 | |
| AF 125 | BFY 51 | OA 79 | OC 140 | 2N 2147 | |
| AF 126 | BFY 62 | OA 81 | OC 170 | 2N 2411 | |
| AF 127 | BSY 90 | OA 900 | OC 172 | 2N 2989 | |
| AF 139 | BSV 27 | OA 202 | OC 200 | 2N 3053 | |

-V.A.T.-

Please add 25% to all orders

| | | | | | | | |
|----------|-------|---------|------|--------|-------|---------|-------|
| UF85 | 45p | IR5 | 40p | 6BG6G | 90p | 6H6 | 40p |
| UF89 | 50p | IR4 | 30p | 6BJ6 | 65p | 6JAWA | £1.25 |
| UL41 | 70p | IT4 | 30p | 6C7A | 60p | 6J5 | 65p |
| UL64 | 40p | IX3A | 75p | 6BR7 | £1.20 | 6J5 | 65p |
| UY41 | 45p | IX3B | 75p | 6BW6 | £1.00 | 6J59T | 50p |
| UY85 | 40p | 2D21 | 50p | 6BW7 | £1.00 | 6J6 | 80p |
| VR105/30 | 2K25 | 2K25 | 2K25 | 6C4 | 40p | 6J7 | 60p |
| | 45p | 2A4 | 60p | 6C5 | 50p | 6J7G | 60p |
| VR150/30 | 3D6 | 40p | 3Z4T | 6C6 | 50p | 6K6GT | 80p |
| | 45p | 384 | 40p | 6C7B | 50p | 6K6GT | 80p |
| X61M | £1.40 | 3V4 | 85p | 6C8 | 50p | 6K7 | 55p |
| X66 | 65p | 6B/254M | | 6C8B | 50p | 6K7G | 55p |
| Z800U | | 24-50 | | 6C8C | 50p | 6K7G | 55p |
| Z801U | 22-70 | 5B255M | | 6C8E | 50p | 6K8 | 55p |
| Z900T | £1.30 | 5R4GY | 90p | 6C8G | 50p | 6K8T | 55p |
| IAS | 55p | 5U4G | 50p | 6C8H | £1.45 | 6K7 | 55p |
| IL4 | 25p | 5V4G | 55p | 6C8J | 75p | 6K7G | 55p |
| | | 6A8X | 70p | 6C8K | 55p | 6K8GT | 50p |
| | | 6AK5 | 40p | 6C8L | 85p | 6K25 | £1.00 |
| | | 6AK8 | 40p | 6AX5GT | £1.10 | 6L6 | 40p |
| | | 6AL5 | 30p | 6B | £1.00 | 6L6 | 40p |
| | | 6ALW | 55p | 6B7 | 75p | 6L7G | 40p |
| | | 6AM6 | 60p | 6B8 | 90p | 6L7G | 40p |
| | | 6AN8 | 45p | 6BA8 | 35p | 6E8A7 | 50p |
| | | 6AN8 | 45p | 6BE6 | 40p | 6E83 | £2.50 |
| | | | | | | 6E8A7GT | 40p |

MINIMUM POSTAL ORDER IS PERSONAL CALLERS WELCOME. MANY OTHERS IN STOCK include Cathode Ray Tubes and Special Valves. U.K. UK Postage £1-22 17p, £2-23 30p, £3-24 40p, Over £5 free. C.O.D. 50p extra.

COLORMOR

ALL valves guaranteed

| | | | | | |
|--------|--------|---------|-------|------------|---------|
| 68C7GT | 40p | 25L6GT | 70p | 6064 | 60p |
| 68G7 | 50p | 30C15 | £1.00 | 6065 | £1.00 |
| 68J7 | 55p | 30C17 | £1.00 | 6067 | 70p |
| 68K7GT | 55p | 30C18 | 70p | 6080 | £2.30 |
| 68K7 | 55p | 30F8 | £1.00 | 6146 | £2.35 |
| 68N7GT | 50p | 30FL1 | £1.00 | 6146B | £2.35 |
| 68Q7 | 55p | 30FL2 | | 8020 | 25.00 |
| 6V6GT | 55p | 30FL4 | 95p | 9001 | 25.00 |
| 6X4 | 40p | 30F5 | 95p | 9002 | 50p |
| 6X6 | 40p | 30L17 | 95p | 9003 | 70p |
| 6X5GT | 50p | 30P12 | £1.00 | 9004 | 35p |
| 6Y6G | 90p | 30P19 | £1.00 | 9006 | 35p |
| 6Z4 | 65p | 30PL1 | 95p | | |
| 6-30L2 | 90p | 30PL13 | | | |
| 7B7 | 30p | | | | |
| 7Y4 | 30p | 30P14 | £1.10 | C.R. Tubes | |
| 9D6 | 40p | 30P14 | £1.10 | DG7-5 | |
| 12A7 | 40p | 35L6GT | 75p | | £12.00 |
| 12A7G | 40p | 50C6 | 60p | DG13-2 | |
| 12A7V | 35p | 50C6D6G | | MW13-35 | |
| 12B2 | 28-00 | 5W4 | 50p | | £25.00 |
| 12BE | 28-00 | 5W4GT | 70p | | |
| 12AT6 | 45p | 50C6 | 60p | | |
| 12AT7 | 40p | 50C6D6G | | | |
| 12AU7 | 35p | | | | |
| 12AV6 | 50p | 75 | £1.00 | | 28.00 |
| 12AX7 | 35p | 7501 | 75p | 3BP1 | 24.50 |
| 12BA6 | 45p | 76 | 75p | 88D | 29.00 |
| 12BE6 | 50p | 78 | 75p | 88J | 29.00 |
| 12BH7 | 55p | 80 | 75p | 88L | 29.00 |
| 12B1 | 29-50 | 80 | 75p | | |
| 12BR7 | 55p | 82A | 75p | | |
| 12K5 | £1.10 | 803 | £2.00 | Special | |
| 12K7GT | 50p | 805 | £1.00 | Valves | |
| 12K8GT | 70p | 807 | 75p | CV239 | |
| 12Q7GT | 70p | 807 | 75p | | £45.00 |
| 12R7GT | 70p | 866A | £1.20 | M503-2742 | |
| 12S7 | 55p | 807 | 75p | | £42.00 |
| 12S7G | 55p | 954 | 50p | X301 | 27.00 |
| 12S7J | 55p | 955 | 50p | KIN2A | |
| 12Y4 | 40p | 966 | 60p | | 26.00 |
| 1457 | £1.00 | 957 | 50p | OY4-350 | |
| 19A4Q5 | 65p | 1305 | 50p | | £13.00 |
| 19G3 | 28-00 | 1829 | 70p | TY4-500 | |
| 19G6 | 26-00 | 2051 | £1.00 | | 220.00 |
| 19E15 | £14.00 | 5933 | 28.00 | 726A | 228.00 |
| 20P3 | 80p | 8097 | 75p | 27/192 | |
| 20P4 | £1.10 | 6080 | 70p | | £140.00 |

VALVES AND TRANSISTORS Telephone enquiries for valves, transistors, etc., retail 749 3994; trade and export 743 0899.

Colomor (Electronics) Ltd.
170 GOLDHAWK ROAD, LONDON W12.

A lot of these valves are imported and prices vary for each delivery, so we reserve the right to change prices for new stock when unavoidable.

Personal Callers 9-12.30, 1.30-5.30 closed Saturdays

29

RTVC*

NEW!

VISCOUNT IV STEREO SYSTEM

System 1a. **£65.00**

The new 20+20 watt Stereo Amplifier incorporating the latest silicon transistor solid state circuitry, the RT-VC VISCOUNT IV gives you a powerful 20 watts RMS per channel into 8 ohms. Superb teak-finished cabinet, with anodised fascia to harmonise with any decor. Polished trim and knobs.

The VISCOUNT IV has a comprehensive range of controls - volume, bass, treble, balance, mono/stereo, mode selector, and scratch filter.

Front panel socket for stereo headphones. And a host of sockets at the rear - for left and right speakers, tape recorder, auxiliary, tuner, disc and microphone.

SPECIFICATION: 20 watts RMS per channel 40 watts peak. Suitable 8-15 ohms speakers. Total distortion @ 10 watts better than 0.2%. Six switched inputs: 1. Magnetic P.U. - 3 millivolts @ 47 K ohms (R.I.A.A.); 2. Crystal/ceramic P.U. - 50 millivolts @ 50 K ohms (R.I.A.A.); 3, 4, 6. Tape Tuner/Aux. - 140 millivolts @ 50 K ohms (flat frequency response); 5. Microphone - 3 millivolts @ 50 K ohms (flat frequency response).

CONTROLS: Push button ON/OFF, stereo/mono, scratch filter, 6 position rotary selector. Individual rotary controls for treble, bass, balance and volume. Headphone socket, tape out socket. Aux. mains output. Frequency response: 25 Hz to 25 KHz @ full rated output. Signal to noise ratio: better than -50 dB on all inputs. **Tone control range:** Bass ± 15 dB @ 50 Hz; Treble ± 12 dB @ 10 KHz.

Power requirements: 200-250V A.C. mains @ 60 watts. **Approx. size:** 15½" x 3" x 10".

MP60 type deck with magnetic cartridge, de luxe plinth and cover.

Two Duo Type IIa matched speakers - Enclosure size approx. 19½" x 10½" x 7½" in simulated teak. Drive unit 13" x 8" with 3" tweeter. 15 watts handling, 30 watts peak.

Complete System with these speakers £69.00 + £6.50 p & p.

System 2. **£81.00**

Viscount IV amplifier (As System 1a)
MP60 type deck (As System 1a)

Two Duo Type III matched speakers

- Enclosure size approx. 27" x 13" x 11½". Finished in teak simulate.

Drive units 13" x 8" bass driver, and two 3" (approx.) tweeters. 20 watts RMS, 8 ohms frequency range - 20 Hz to 18,000 Hz.

Complete System with these speakers £85.00 + £7.60 p & p.

PRICES: SYSTEM 1a

Viscount IV R103 amplifier £25.00 + £1.90 p & p.

2 Duo Type IIa speakers £30.00 + £6.50 p & p.

MP60 type deck with Mag. cartridge de luxe plinth and cover £20.00 + £3.30 p & p.

Total if purchased separately: £75.00

Available complete for only: **£65.00** + £6.50 p & p.

PRICES: SYSTEM 2

Viscount IV R103 amplifier £25.00 + £1.90 p & p.

2 Duo Type III speakers £46.00 + £7.50 p & p.

MP60 type deck with Mag. cartridge de luxe plinth and cover £20.00 + £3.30 p & p.

Total if purchased separately: £91.00

Available complete for only: **£81.00** + £7.60 p & p.



20x20 SYSTEM

Scotland and the Orkneys P & P Surcharge
System 1a £17.75 System 2 £3.50

EMI SPEAKERS AT FANTASTIC REDUCTIONS

LE-4 SPEAKERS

Superb performance and beautifully finished in selected teak veneers. A professional standard four-way speaker system giving 25 watts RMS power handling. Bass unit is 14" x 9" with 8" x 5" unit for mid-range and twin 3" high frequency units to give monitor type quality and performance.

Specification - Size 33" x 14" x 16" approx. Impedance 8 ohms. Power handling 25W RMS. (Peak 50 watts.) Frequency range 35 Hz-20 KHz.

Our Price £34.00 each

(normally £66.00) + £5.80 p & p.


Scotland and the Orkneys P & P Surcharge £3.50

EASY TO BUILD SPEAKER KITS

These superb simulated teak-finished speaker kits have been specially designed by RT-VC for the cost-conscious hi-fi enthusiast who wants top quality speakers but doesn't want to spend the earth. Built to EMI's exacting specification, these new RT-VC speaker kits (350 type kit) incorporate 13" x 8" woofer, 3½" tweeter and matching crossover.

Easily put together with just a few basic tools.

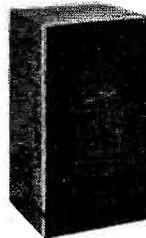Specification (each speaker): Impedance 8 ohms. Power handling 15 watts RMS (30 watts peak). Response 20-20,000 Hz. Size 20" x 11" x 9½" approx. Comparable built units (EMI LE3) sold elsewhere for over £45 pair.



£22.00 pair complete

+£5.20 p & p. Complete with crossover Components and circuit diagram

EMI 350 KIT

System consists of a 13" x 8" approx. woofer with a 3" tweeter, crossover components and circuit diagram. Frequency response: 20 Hz to 20 KHz. Power handling 15 watts RMS into 8 ohms. (Peak 30 watts.)

£6.50 + £1.20 p & p.


Complete with crossover Components and circuit diagram




DECCA STEREO AMPLIFIER CHASSIS

Specification: 4+4 watts into 8 ohms. Input Sensitivity 4mV into 47K (for magnetic cartridges). AC Mains only 240V. Controls - volume, bass, treble, on/off, mono/stereo switch. Chassis size 11" x 5½" x 3½" approx.

£6.90 + £1.20 p & p.

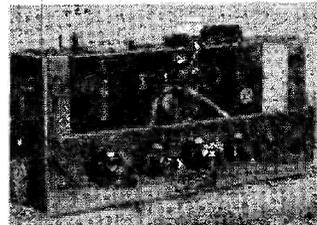

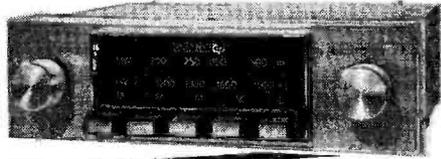PUSH BUTTON CAR RADIO KIT— THE TOURIST TT*




NO SOLDERING REQUIRED

NOW BUILD YOUR OWN PUSH BUTTON CAR RADIO

Easy to assemble construction kit comprising fully completed and tested printed circuit board on which no soldering is required. All connections are simple push fit type making for easy assembly. Fine tuning push button mechanism is fully built and tested to mate with printed circuit board. **TECHNICAL SPECIFICATION:** (1) Output 4 watts RMS output. For 12 volt operation on negative or positive earth. (2) Integrated circuit output stage, pre-built three stage IF Module.

Controls volume manual tuning and five push buttons for station selection. Illuminated tuning scale covering full, medium and long wave bands. Size chassis 7" wide 2" high and 4½" deep approx. **£9.50** +£1.05 p & p. Speaker including baffle and fixing strip **£2.00** +45p p & p. Car Aerial Recommended — fully retractable **£1.60** +40p p & p. The Tourist I Kit For the experienced constructor. If you can solder on a printed circuit board you can build this model. Same technical specification as Tourist TT. **Price £8.20** +£1.05 p & p.

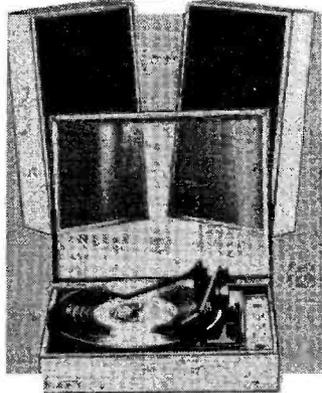*STEREO 21 QUALITY SOUND FOR LESS THAN £24.00




Stereo 21, easy to assemble audio system kit. No soldering required. The unit is finished in white P.V.C. and the acrylic top presents an unusually interesting variation on the modern deck plinth. Includes — BSR 3 speed deck, automatic, manual facilities together with stereo cartridge. Two speakers with cabinets. Amplifier module. Ready built with control panel, speaker leads and full, easy to follow assembly instructions. **Specifications** — For the technically minded: Input sensitivity 600mV. Aux. input sensitivity 120mV. Power output 2.7 watts per channel. Output impedance 8–15 ohms. Stereo headphone socket with automatic speaker cutout. Provision for auxiliary inputs — radio, tape, etc., and outputs for taping discs. Overall Dimensions. Speakers approx 15½" x 8" x 4". Complete deck and cover in closed position approx. 15½" x 12" x 6"

Complete only £23.20 +£3.00 p & p.

Extras if required. Optional Diamond Stylus **£1.60**. Specially selected pair of stereo headphones with individual level controls and padded earpieces to give optimum performance **£5.80**.

*DISCO AMPLIFIER

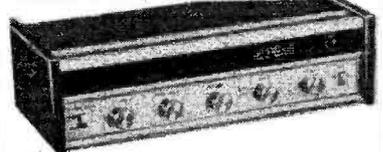


Reliant Mk IV Mono Amplifier, ideal for the small disco or house parties. Output 20 watts RMS into 8 ohms (suitable for 15 ohms). Inputs *4 electrically mixed inputs. *3 individual mixing controls. *Separate bass and treble controls common to all 4 inputs. *Mixer employing F.E.T. (Field Effect Transistors). *Solid State circuitry. *Attractive styling. **INPUT SENSITIVITIES** — Input — 1) Crystal mic. guitar or moving coil mic, 2 and 10mV. (Selector switch for desired sensitivity.) — Inputs — 2), 3), 4). Medium output equipment — ceramic cartridge, tuner, tape recorder, organs, etc. — all 250mV sensitivity. AC Mains, 240V operation. Size approx: 12½" x 6" x 3½". **£20.00** +£1.35 p & p.

*8 TRACK HOME CARTRIDGE PLAYER



Elegant self selector push button player for use with your stereo system. Compatible with Viscount IV system, Unisound module and the Stereo 21. Technical specification Mains input. 240V. Output sensitivity 125mV. Comparable unit sold elsewhere at £24.00 approx. Yours for only

£16.20 +£1.70 p & p.

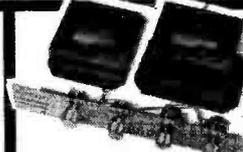


BUILD YOUR OWN *STEREO AMPLIFIER

For the man who wants to design his own stereo — here's your chance to start. With Unisound — pre-amp, power amplifier and control panel. No soldering — just simply screw together. 4 watts per channel into 8 ohms. Inputs: 120mV (for ceramic cartridge). The heart of Unisound is high efficiency I.C. monolithic power chips which ensure very low distortion over the audio spectrum. 240V. AC only.

Also available with 2 speakers (7" x 4") **£10** +£1.75 p & p. **£8.95** +£1.05 p & p.

PORTABLE DISCO CONSOLE*

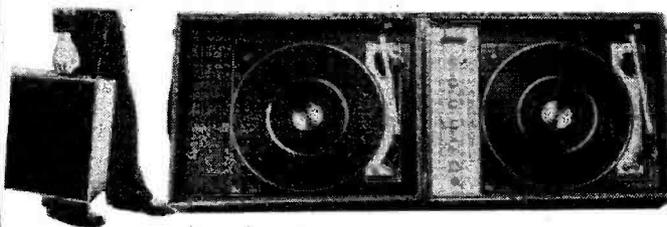

INCORPORATES: Pre-Amp with full mixing facilities, including switched input for mic with volume control, switched input for auxiliary with volume control, bass and treble controls, volume control and blend control for turntables. Two B.S.R. MP60 type single play professional series decks, fitted with crystal cartridges.

TECHNICAL SPECIFICATION:
Pre-amp — Output — 200mV.
Auxiliary inputs — 200mV and 750mV into 1 meg. Mic input — 6mV into 100K. 240 volt operation.
Turntables capacity — 7", 10" or 12" records. Rumble, wow and flutter Rumble Better than —35dB. Wow Better than 0.2%. Flutter Better than 0.06% (Gaumont kalee meter).
Finish — Satin black mainplate with black turntable mat inlaid with brushed aluminium trim. Tonearm and controls in black and brushed aluminium.

Console size — Unit Closed — 17½" x 13½" x 8½" (app.) Unit Open — 35½" x 13½" x 4½" (app.) This disco console is ideally matched for the Reliant IV and Disco 50 or any other quality amplifier. The unit is finished in black PVC with contrasting simulated teak edging, diamond spun control knobs with matching control panel.

Yours for only £49.00 +£6.50 p & p.



DO NOT SEND CARD
Just write your order giving your credit card number

Mail orders to Acton. Terms C.W.O. All enquiries stamped addressed envelope. Goods not despatched outside U.K. Leaflets available for all items listed thus* Send stamped addressed envelope. All items subject to availability. Prices correct at 1st July 1975 and subject to change without notice. All prices include V.A.T. at current rates



21C HIGH STREET, ACTON, LONDON W3 6NG
323 EDGWARE ROAD, LONDON W2

Personal Shoppers EDGWARE RD: 9 a.m.—5.30p.m. Half day Thurs. ACTON: 9.30a.m.—5p.m. Closed all day Wed.

Everest Instruments Ltd.

34, Shakespear St., Nottingham.
Tel. (0602) 45466

All prices quoted include p. & p., & VAT, min. order £1, CWO only.

| Transformers | | 10 x 6 EMI | | |
|--|------------|------------------|------------------------|--|
| All 240v 50hz primaries | | 8 ohm 20 watt | 7-36 | |
| | | 13 x 8 EMI | | |
| | | 8 ohm 20 watt | 6-75 | |
| | | 13 x 8 EMI | | |
| | | 8 ohm 25 watt | 7-84 | |
| Semiconductors | | Diodes | | |
| Volts | Amps | IN4001 | 8p | |
| 6-3 | 1-5 | IN4002 | 74p | |
| 6-3 | 3-0 | IN4003 | 95p | |
| 9-0 | 1-0 | IN4004 | 92p | |
| 12-0 | 0-5 | IN4006 | 13p | |
| 12-0 | 1-5 | IN4007 | 13p | |
| 12-0 | 3-0 | OA70 | 8p | |
| 6-0-6 | 0-5 | OA81 | 75p | |
| 9-0-9 | 0-5 | OA90 | 6p | |
| 9-0-9 | 1-0 | OA91 | 6p | |
| 10-0-10 | 2-0 | OA202 | 74p | |
| 12-0-12 | 1-0 | BA154 | 95p | |
| 12-0-12 | 2-0 | BA156 | 15p | |
| 15-0-15 | 1-0 | IN914 | 4p | |
| 15-0-15 | 2-0 | | | |
| 18-0-18 | 2-0 | | | |
| 20-0-20 | 1-0 | | | |
| 20-0-20 | 2-0 | | | |
| 30-0-30 | 1-0 | | | |
| 0-10-12-14- | | 400mw zeners | | |
| 16-18 | 4-0 | 3v to 33v | 10p | |
| 0-12-15-20- | | | | |
| 24-30 | 2-0 | | | |
| 0-5-20-30- | | Silicone bridge | | |
| 40-60 | 2-0 | rectifiers | | |
| | | 2a 50v rms | 40p | |
| | | 2a 100v rms | 47p | |
| Bulk tape eraser | | Thyristors | | |
| 15-8-3 ohm 12 watt | | 1a 100v piv | 30p | |
| matching | 1-71 | 1a 400v piv | 45p | |
| Transistor driver | | 3a 400v piv | 57p | |
| 4:1+1 | 0-27 | | | |
| P.C. Board | | Triacs | | |
| Single sided fibre | | 2a 400v piv | 86p | |
| glass | 0-70 sq ft | 6a 400v piv | 85p | |
| Double sided fibre | | 10a 400v piv | 122p | |
| glass | 1-00 sq ft | Diac | 25p | |
| Cut in multiples of 6" | | | | |
| i.e. 6 x 6, 6 x 12, 12 x 12, | | Linear I.C.'s | | |
| 12 x 18, etc. | | 709P 8p D.I.L. | 30p | |
| Circuit etchant 250ml | 0-55 | 741P 8p D.I.L. | 42p | |
| 1 lb ferric chloride | 0-50 | 748P 8p D.I.L. | 45p | |
| 250ml plastic bottles | 0-16 | | | |
| Speakers | | 74 series T.T.L. | | |
| 3" Goodman tweeter | | 7400 | 15p | |
| 8 ohm 51CD4 | 1-47 | 7402 | 15p | |
| 3" Audax tweeter | | 7404 | 15p | |
| 8 ohm 15 watt | 1-60 | 7413 | 40p | |
| 5" Audax bass | | 7447 | 123p | |
| 8 ohm 10 watt | 3-23 | 7473 | 46p | |
| | | 7475 | 58p | |
| 6 1/2" Audax 8 ohm | | 7490 | 69p | |
| 15 watt | 2-95 | | | |
| 6 1/2" EMI d/cone | | 7 segment led | | |
| 8 ohm 10 watt | 3-59 | numeral display | | |
| | | 16p D.I.L. | 115p | |
| 3 x 5 EMI d/cone | | | | |
| 8 ohm 10 watt | 3-67 | D.I.L. sockets | | |
| 8" Celestion d/cone | | 8 pin | 15p | |
| 8 ohm 10 watt | 2-76 | 14 pin | 18p | |
| | | 16 pin | 16p | |
| Electrolytics. Tubular with axial leads except where stated. | | | | |
| Mfd. | Volts | Pence | | |
| 47 | 4 | 7 | | |
| 330 | 4 | 7 | | |
| 68 | 6-3 | 7 | | |
| 470 | 6-3 | 9 | | |
| 1000 | 6 | 11 | single end p/c fitting | |
| 25 | 10 | 7 | | |
| 47 | 10 | 7 | | |
| 220 | 10 | 7 | | |
| 330 | 10 | 9 | | |
| 15 | 16 | 7 | | |
| 33 | 16 | 7 | | |
| 68 | 16 | 7 | | |
| 220 | 16 | 9 | | |
| 220 | 16 | 9 | single end p/c fitting | |
| 330 | 16 | 12 | | |
| 1000 | 16 | 20 | | |
| 10 | 25 | 7 | | |
| 22 | 25 | 7 | | |
| 47 | 25 | 7 | | |
| 100 | 25 | 7 | | |
| 150 | 25 | 9 | | |
| 200 | 25 | 11 | | |
| 1250 | 25 | 24 | single end can | |
| 5000 | 25 | 55 | single end can | |
| 1000+1000 | 30 | 32 | single end can | |
| 2500 | 30 | 40 | single end can | |
| | 6-8 | 40 | | |
| | 16 | 40 | | |
| | 100 | 40 | | |
| | 1000 | 50 | single end can | |
| | 1 | 63 | | |
| | 4-7 | 63 | | |
| | 10 | 63 | | |
| | 32 | 63 | | |
| | 800 | 63 | 32 single end can | |
| | 2500 | 63 | 80 single end can | |
| | 4700 | 63 | 140 single end can | |

RECHARGEABLE BATTERIES

CAN SAVE YOU A FORTUNE!
Bush & Meissner's two purpose-built battery chargers for economy minded enthusiasts:

The "KESTREL-DOWN" Charger .. £11-31 for Alkaline rechargeable batteries, no-load voltage of 1.5-volts per cell, for the following sizes ALKALINE (All prices ex-VAT)

| Equivalent to | Type | Capacity | PRICE |
|------------------|---------|----------|--------|
| U2 size | SA-13D | 2Ah | £1-73 |
| U11 size | SA-14C | 1Ah | £1-13 |
| U7 size (pencil) | SA-15AA | 0.3Ah | £0-56p |

NICKEL-CADMIUM (All prices ex-VAT)
The "DAIMON" Charger .. £9-76 for Nickel-Cadmium batteries, no-load voltage of 1.25 volts per cell, for the following sizes:

| Type | Capacity | PRICE |
|--------|----------|-------|
| NCC400 | 4Ah | £3-64 |
| NCC200 | 2Ah | £2-48 |
| NCC50 | 0.5Ah | £1-45 |

Charger designed to give optimum results with a specific type of cell. Never be without power, day or night.

*Note, under no circumstances must Alkaline batteries be used with the Daimon charger.

S.A.E. brings full details



Bush & Meissner

Importers & Distributors
Dept LS260
275 West End Lane,
London NW6 1QS
01-794-9611

FREE Brochure on New KITS



Whether professional, student, teacher or amateur, the field of electronics can open up a new world for you.

CROFTON don't just sell kits, we offer you a technical back up service to ensure your success

The following is a selection of some of the more popular kits -

- ★ Mullard CCTV Camera
- ★ PE CCTV Camera
- ★ PE Rondo Quadraphonic Four Channel Sound (Designer Approved)
- ★ Electronic Ignition
- ★ Electronic Flash
- ★ P.W. Tele-Tennis Game
- ★ U.H.F. Modulator
- ★ Bench Power Supply
- ★ Wobulator
- ★ All ETI Top Projects
- ★ Many of the Elektor Projects

NOTE PCB's for most published projects available to order

CROFTON ELECTRONICS LTD
Dept B 124 Colne Road Twickenham Middx. O1 898 1569

Wire Wound Resistors. Our selection of mixed values. 30 for £1.40. 100 for £3.50.

Audio Amplifier Module. Mullard LP1173, output power, nominal 10 watt, supply voltage +24 volt, with data and circuit, £2-30 + post.

Ferguson Stereogram chassis Model 3357, all transistor, medium long, VHF/FM. 3 watts per channel S/M. with connection data, less tuning scale, £18-00. Post paid.

Crystals HC6U: 52-03333 MHz: 52-02500: 52-01667: 51-56667: 51-56330: 37-76250: 37-75000: 12-895-8: 12-891-6: 12-700-0: 9-456-25: 9-455-55: 9-533-33: 9-531-94: 9-530-55: 9-090-62: 9-087-5 50p each.

Electrolytics. 32/32/32µF 325v. 2" x 1 1/2" 35p: 80µF 150v 1 1/2" x 1" 20p: 2000µF 30v, 2 1/2" x 1" 25p: 2000µF 35v 3" x 1" 30p: 470µF 100v 3" x 1 1/2" 25p: 2000/2000µF 25v 2" x 1 1/2" 35p: 700µF 200v 3 1/2" x 1 1/2" 30p: 16/16µF 275v 1 1/2" x 1" 20p: 40/40/20µF 275v 3" x 1" 20p: 4500/900/900µF 30v 2 1/2" x 1 1/2" 50p: 2500µF 40v 2 1/2" x 1 1/2" 40p: 470µF 25v 1 1/2" x 1 1/2" 15p: 4,000µF 25v 3" x 1 1/2" 40p. 32µF 450v 1 1/2" x 1" 30p: 8µF/16µF 450v 1 1/2" x 1 1/2" 30p: 1000µF 12v 1 1/2" x 1 1/2" 15p.

Try our parcel of small capacitors 20 mixed valves £1-50 + post.

Matched pair of bookshelf speakers. Teak finish, size 12" x 8" x 5". 8 x 5 8" ohms ceramic, 5 watts RMS. Complete with din leads. £10-00 pair + post.

Thorn TV IF chassis, 950 series (less valves). £1-60 + post.

UHF 625 transistor push button tuner (NSF Telefunken) as used on Decca MS2400. Brand new and boxed, circuit diagram supplied £3-00 + post.

P-C Boards (not computer panels) 1 off 6 transistor single wave band. 1 off 4 transistor audio. 1 off 3 transistor £1-40 + post, three boards.

Repanco Transformers AF1, AF2, TT45, 46, 47, 49, 53. 20p each + post.

L/W, M/W, VHF Tuner 5 transistor in kit form, complete with full assembly instructions. 9vt supply, positive earth. O/pout 100mw. Built-in A.M. aerial. 88-108 Mcs. £5-25 + post.

Stereo Decoder using MC1310. Fully assembled, can be used with our tuner kit. With data. £3-90 + post.

Mains Droppers, 10 mixed values, £1-00 + post.

Edgewise Level meters, 200µA, size 3" overall. 50p + post.

Chrome Plastic knobs, 3 types, 4 off each with spring clip, £1-25 + post.

Aluminium Chassis, 7 1/2" x 5 1/2" x 2 1/2" 65p + post: 10" x 7 1/2" x 2 1/2" 75p + post. 11" x 7 1/2" x 2 1/2" 85p + post.

BSR P128, similar to HT70 single play, with heavy die cast turntable, less cartridge, £10-00 + post.

Ferguson Stereogram Chassis. MW/LW/VHF with tuning scale (5+5 watts sine wave) 15 ohms £26-25. Post paid

15 ASSORTED SWITCHES £1-90 + post. 50-3 way to 7 way TAG STRIPS. £1-15 + post, ALMA REED RELAY TYPE DRH. 3 VOLTS 50p + post.

REPANCO & DENCO COILS. NEW/BOXED OUR SELECTION-5 FOR £1-15 + post.

Please add 10% post and packing. Add 25% VAT to total order. Gram Chassis free postage. No goods despatched outside U.K.

SURPLECTRONICS

216 LEAGRAVE ROAD,
LUTON, LU3 1JD, BEDS.

SAXON

Money saving high performance audio equipment
DIRECT FROM OUR OWN FACTORIES

GUARANTEED TESTED HIGH PERFORMANCE MODULES—now better value than ever

SA35 £6.60 Carriage free

35W RMS 25-50V
7 transistors, 7 diodes


SA50 £8.50 Carriage free

50W RMS 25-65V
7 transistors, 7 diodes

SA100 £12.50 Carriage free

100W RMS 45-70V
10 transistors, 7 diodes

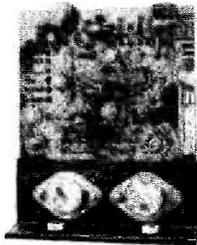- ★ 25Hz-25kHz
- ★ 0.2% distortion
- ★ Noise—80dB
- ★ 500mV into 20K
- ★ 4-16 ohms
- ★ Simple wiring
- ★ Short and open circuit proof
- ★ Continuously rated
- ★ Top-grade components



THE SA100 MODULE

POWER SUPPLIES

UNSTABILISED—READY WIRED & FUSED

PU45 Suits 2 SA35 or 1 SA50 (4 ohm) **£6.50** Carriage 50p

PU70 Suits 2 SA50 (8 ohm) or 2 SA100 **£9.50** Carriage 60p

STABILISED

PS45 Suits 2 SA35 or 2 SA50 (4 ohm) **£5.50** Carriage free

MT45 Transformer for above **£3.90** Carriage 50p

PS70 Suits 2 SA100 **£6.50** Carriage free


MT70 Transformer or above **£5.50** Carriage 60p

N.B. PS70 is not suitable for the SA50

Mk II STEREO DISCO MIXER £29.50

Carr. 60p

This well tried unit mixes two decks, handles any ceramic cartridge, and features mic over-ride plus separate full range bass and treble controls on both mic and deck inputs. Ample headphone power is available for P.F.L. May be used for mono and is mains operated. Fitted with sturdy screening case. Controls: Mic vol, base, treble. Left/Right fade, deck volume, bass, treble, h/phone select. vol, Mains. Size 17½in x 3in x 4in deep.

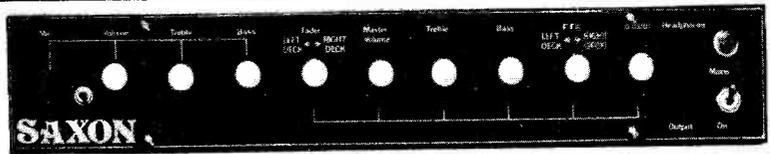

DISCO MODULE £12.50

Carr. 50p

Thousands sold of this extremely popular mono version. A mic input may be fitted using the VA30 (see below). Low consumption from a 9V battery. Features the same high standards of reproduction as the Stereo version. Controls: h/phone select. vol, Left deck vol. Right deck vol, bass, treble, master vol. Size 12½in x 3in x 2in deep.



3-CHANNEL SOUND-LITE £24.75

Carr. 50p

Only SAXON can supply such incredible value for money. This unit features 3kW power handling, full-wave control, bass, middle, treble AND master controls. Twin loudspeaker jacks for "through" connections. It may be used free standing or will panel mount next to either of the above. Also features unique CUT-BACK circuitry for extra wide range response. Size 12in x 3in x 2½in deep. Professional standards at a price you can afford!



SINGLE CHANNEL VERSION £7.90
Carr. free

NOTE: ONLY 8% VAT TO BE ADDED TO ORDER VALUE

MULTI-PURPOSE MIXERS

M4HL

£25.00 Carr. 60p

M6HL


£35.00 Carr. 60p

Featuring multiples of our VA30 module, the M4HL and M6HL fulfil the requirements of all clubs, groups, etc. where a high quality mixer is required. Each channel has one high and one low impedance input, plus volume, treble and bass controls. Input impedances may, if required, be easily changed. The M4HL has four channels, and one output, and the M6HL six channels (12 inputs) and a master control and two outputs. Either unit may be used free-standing or panel mounted. These mixers will feed all types of amplifier. Recommended for their versatility and high performance, and excellent value for money.

VA30 CHANNEL MODULE £3.90

Carr. free

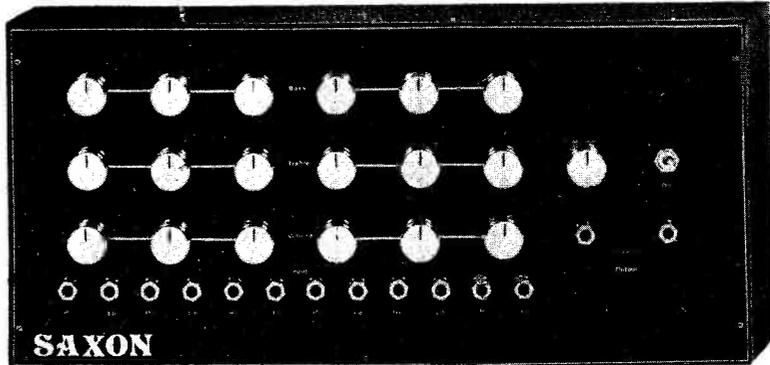This is the basic channel module in the above mixers and may also be used for extra inputs on either the mono or stereo mixers. Fitted with volume, bass and treble controls, requires just a jack and supply (9-100V)




SAXON CSE 100

COMPLETE AMPLIFIER

£39.90
Carr. 60p

100W of speech and music—Two separately controlled inputs. Wide range bass and treble controls. Sturdy and attractive vynide case. Twin outputs. Ideal for groups, discos, etc. Fully tested and guaranteed. 50W version identical in appearance

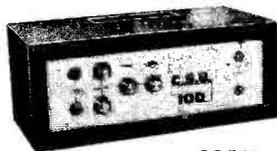

CSE50
£33.00 Carr. 60p

NEW !!

SAXON MULTIMIX 100 £57.00 carr. £1.00

100W rms four inputs slider controls plus master slider. Wide range bass and treble controls. Fantastic value, ideal for complete disco's, groups, clubs etc. **SAXON MULTIMIX 50**—Exactly as above but 50W rms. **£45.00**

CALLERS AND MAIL ORDER

SAXON ENTERTAINMENTS LIMITED

327-331 WHITEHORSE ROAD · CROYDON CR0 2HS

(Please quote magazine when ordering)

SHOP HOURS: 9 a.m.—5 p.m. — LUNCH 12.30-1.30 p.m. MAIL ORDER DESK: 10 a.m.—3 p.m.
24-HOUR ANSWER SERVICE. TEL. 01-684 6385. TECHNICAL ENQUIRIES: 01-684 0098.


SEND 10p FOR OUR 26 PAGE MANUAL—full circuits & details.

TERMS OF BUSINESS: C.W.O. C.O.D. or ACCESS (just send in card number). Send 50p for C.O.D.

Please send S.A.E. with all enquiries.

VAT @ 8% must be added to all orders including carr. charges.

INVERTORS

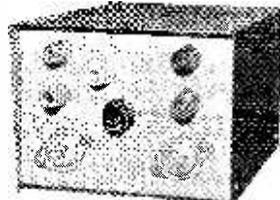

240v-50Hz from your 12v car battery.

25 watt—£4.20 150 watt—£19.10
40 watt—£7.35 300 watt (12v)—£29.85
75 watt—£10.71 300 watt (24v)—£23.75

All above invertors are in kit form but may be purchased built up in metal case & ready for use. Price list sent on receipt of s.a.e. Prices include post & packing.

P.W. AUTOMATIC EMERGENCY SUPPLY

240v-50Hz-150 watt inverter with built in battery charger. In event of power failure switches over automatically from battery charging to inverter operation. Cct. as appeared in Dec. 72 P.W. Complete kit of parts (excluding meter) £22.50+£1.10 p. & p.

FLUORESCENT LIGHT INVERTOR KIT
8 watt-12v-Fluorescent light, suitable for tents, caravans, houses, boats & secondary lighting for factories, hotels, etc.

12"-8 watt—£2.99+25p p. & p. Built up £4+25p.
21"-13 watt—£3.39+30p p. & p. Built up—£4.59+30p.

TRANSFORMERS & COILS

Both high volume & small order capacity available.

Special offer. Miniature mains transformer 12-0-12v-6V.A.—85p plus 10p p. & p.

TRADE & EXPORT ENQUIRIES WELCOMED

ORION STEREO AMPLIFIER




20 + 20 Watts r.m.s. into 8 ohm load. Distortion less than 0.01% 100Hz-10kHz. Frequency response ± 1 dB 20 Hz to 20 kHz. Hum level virtually nil with vol. full on.

This is a power amplifier of superb quality incorporating the very latest design features. Professional hi-fi enthusiasts have classed it as fantastic and real value for money. The CCT incorporates a low flux transformer and inputs for disc. tape, tuner etc.

Complete kit of parts including slim line bookend case, silk screened front panel & knobs. £43 incl. VAT & p. & p.

The bookend case, I.C.s & semiconductors, P.C. board, Transformer, etc. may be purchased separately if desired. Send S.A.E. for further information

ASTRO IGNITION

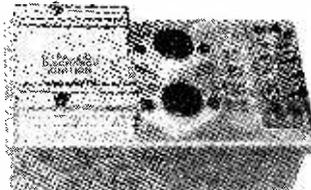

ASTRO IGNITION SYSTEM

Complete kit of parts for this proven and tested system £9.50 incl VAT. Ready built with only two connections to alter £12.50 incl. VAT.

Thousands have used this system both home and abroad. Consider these *advantages* more power, faster acceleration, fuel economy, excellent cold starting, smoother running, no contact breaker-burning. Also because of the high energy spark, the fuel mixture can be made weaker giving further economy and fewer plug problems. Fitting time when built 5 minutes approx. Please state whether positive or negative earth. Trade and export enquiries welcomed.

ASTRO ELECTRONICS,
Spring Bank Rd., West Park,
Chesterfield.

VALVE BARGAINS

Any 5 64p, 10 99p, 50 £4. Your choice from the following list: ECH84, ECC82, ECL80, EF80, EF183, EF184, PC86, PC88, PCF80, PCF802, PCL82, PCL84, PCL85, PCL805, PCL86, PFL200, PL36, PL504, PY33, PY81, PY800, PY88, EH90, 30FL1, 30FL2, 30PL14.

Colour Valves 25p each
PL508 PL509, PY500/A

Press 4 Button Transistor UHF Tuners £2.50

AERIAL BOOSTERS

We make three types of Aerial Boosters all for set top fitting, with Co-ax Plugs and Sockets.

B11—For Stereo and Standard VHF Radio
B12—For the older VHF Television, please state BBC1 and ITV Channels.

B45—For mon. or colour this covers the complete UHF band.

All Boosters are complete with Battery and take only minutes to fit.

Price £3.90 each

BARGAIN PACKS

All Components in the Bargain Packs are unused and marked.

Pack 1—Polyester (C280) Axial Leads Capacitors—250V/W & 400V/W, very good mixed selection from 0.01 UF to 2.2 UF. Price 100 £1.25, 1000 £10.00 (our choice).

Pack 2—50 AC128 untested but marked Transistors. Price 50 £1.50.

Pack 3—Plugs Plastic Insulated Type. (Prices in brackets for ten).

Co-Ax Plug—8p (70p).

Jack Plugs—Standard 17p (£1.50), 2.5mm 10p (85p), 3.5mm 10p (85p).

Din Plugs—2 Pin 12p (£1.00), 3 Pin 14p (£1.20), 5 Pin 18p (£1.50).

Prices include V.A.T. P. & P. under £1/10p, £1 to £3/15p, above £3/20p. Overseas at cost. Money back guarantee on all orders.

ELECTRONIC MAILORDER LTD., 62 BRIDGE ST., RAMSBOTTOM, BURY, LANCS. Tel. Rams. 3036.

TOROIDAL TRANSFORMERS FOR THE TEXAN II

Designed by S.I.G.A. ELECTRONICS in conjunction with Texas Instruments for uprating Texan 20+20 Amplifiers. Pri. 220-240V; 50Hz; Screen; Sec. 25-20-0-20-25V, 1.5A. Fully impregnated; flying lead connections. Ref. T1295

Price £6.70 + 25% VAT post 50p.

Ref. T1295/F with resin filled centre, 2BA clear hole.

Price £7.10 + 25% VAT post 50p.

Toroidal transformers suitable for Audio Power Supplies Pri. 240V 50Hz; Screen; fully impregnated; flying leads

| REF | SECONDARIES | O.D. (cms) | HT. | Price | Post |
|-----|-------------------|------------|-------|--------|-------|
| 315 | (a) 33-0-33V 2A | 12.0 | × 4.4 | £8.50 | £0.69 |
| | (b) 25-0-25V 0.1A | | | | |
| 291 | (a) 33-0-33V 4A | 13.0 | × 5.7 | £10.69 | £0.78 |
| | (b) 25-0-25V 0.2A | | | | |
| 061 | 20-0-20V 1A | 8.5 | × 4.0 | £4.87 | £0.50 |
| 360 | 25-0-25V 1.5A | 7.7 | × 4.5 | £6.26 | £0.50 |
| 285 | 25-0-25V 2A | 10.8 | × 5.1 | £6.37 | £0.60 |
| 284 | 0-45V 1A | 9.5 | × 4.4 | £5.15 | £0.60 |
| 000 | 0-45V 2A | 12.0 | × 4.4 | £6.64 | £0.69 |

Terms: Cash with order, please add 25% VAT to goods only. Quantity discounts available on request.

Dept. PW 03

S.I.G.A. (ELECTRONICS) LIMITED
Sunderland Road, Sandy, Beds
SG19 1QY

HIGH POWER BATTERY MOTOR

12v operated, strong enough to power a motor mower, go-cart or similar. Speed easily variable. These motors can also be used as a brake for any rotating machine, simply by coupling the spindle to the machine and short-circuiting the windings by a variable resistance, price £2-50+post and V.A.T. 74p. *DITTO* but 6/12v even more powerful as it's larger and is series wound £3-50+85p post and V.A.T.



FIRE ALARM SWITCHES



In cast iron case with break glass panel. These are red and engraved "Fire break glass", they have hinges and a second safety switch for testing purposes. Limited quantity, £1-75 each+post and VAT 46p.

DC HIGH CURRENT PANEL METERS

3 1/2" wound wide angle 240u movement meters, flush mounting fitted with external shunts, made by Crompton Parkinson brand new, still in maker's cartons. These are a real bargain at £5-50 each. Reasonable quantities available in the following ranges: 0-10 amps, 0-20 amps, 0-30amps, 0-40 amps, 0-50 amps. Post and VAT 80p each.



EDGE MOUNTING MOVING COIL METER



Size 2 1/2" x 1" by Weston, 100uA movement sealed DE, unused still in original maker's cartons. £3-50 each + post and VAT 60p.

PERMEABILITY TUNERS



M.W. two stage ideal for use with ZN414 or similar circuit. Price 15p each + post and VAT 15p.

OVEN THERMOSTAT

Made by the famous Diamond H Company, this has a sensor joined by a capillary to a variable control and when fitted with a knob is ideal for many ovens or processes. 50p each + post and VAT 15p.



NUMICATOR TUBES

For digital instruments, counters, timers, clocks, etc. Hi-vac XNII Price 90p each, 20p Post and VAT



WINDSCREEN WIPER CONTROL

Vary speed of your wiper to suit conditions. All parts and instructions to make. £2-25 £1-00 post and VAT.



PORTABLE CABINET OFFER

A nicely made portable cabinet, soft padded black finish intended for portable stereo system. Dimensions as sketch. With motor board cut out for Garrard SP 25. This was obviously a very costly cabinet originally made for a de-luxe record player. Offered at £1-95+£1-50 post and VAT, carriage free if bought with the Garrard or BSR record decks.



HIGHLY SENSITIVE MOVING COIL RELAY



panel mounting with glass window, this measures approx. 5 1/2" x 4" x 3", triggering current can be varied from a fraction of a milliamp to 5 milliamps by removing the front and adjusting the setting level. Price £3 each + post and VAT 95p.

SOUND TO LIGHT UNIT



Add colour or white light to your amplifier. Will operate 1, 2 or 3 lamps (maximum 450w). Unit in Box all ready to work. £2-25 plus 80p VAT and postage.

AUDIO AMPLIFIER

Part of the famous Reddittone background music system, secondhand, but believed in good order. However, no guarantee; we are selling for spares value only. These are 6 valve amplifiers, the output valves are 2x BL 84 in push/pull, complete with mains transformer, rectifier and ample smoothing equipment. The mains transformer alone, today would cost at least £4. Size is 9 1/2" x 5 1/2" x 4 1/2". Price only £2-00+postage and VAT £1.50.



BREAK-DOWN UNIT

Contains hundreds of useful parts some of which are as follows—66 silicon diodes equivalent OA 91. 68 resistors mostly 1/2 watt 5% covering a wide range of values. 4x1 mfd. 400v mfd. condensers. 15x.01 mfd. 100v condensers. 2 RF 1x115v transformer. 1 boxed unit containing 4 delay lines also tag panels, trimmer condensers, suppressors, etc., on a useful chassis sized approx. 9" x 6" x 7". Only 75p (the 66 diodes would cost at least 10 times this amount). This is a snip not to be missed. Post and + VAT 75p.



GPO PUSH BUTTON DIALLING UNIT

Will take the place of the normal rotating dial, has 10 numbered keys, so suitable for other digital systems. A desk mounting unit with rubber feet, this is a very intricate and expensive piece of apparatus. New and unused—our price only 49 each+£1.38 post and VAT.




24V POWER PACK



Normal mains input with a thermal safety device, 800 mA output, 4000 mfd of smoothing and full wave rectification, completely enclosed in plastic box and with flex for mains and terminal block for output Price £1-75+£1 post and VAT.

8-SWITCH DISCO LAMP CONTROLLER

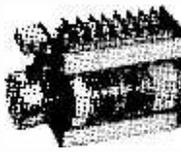Mains motor driving a drum with adjustable trips operating 8 changeover 10 amp switches, so a total of 40KW of lighting can be controlled enabling an unlimited variety of effects to be achieved and changed with the minimum of effort. This is a real snip a £7-50+£1.15 post and VAT.



HONEYWELL PROGRAMMER

This is a drum type timing device, the drum being calibrated to equal divisions for switch-setting purposes with trips which are infinitely adjustable for position. They are also arranged to allow 2 operations per switch per rotation. There are 15 changeover micro switches each of 10 amp type operated by the trips, thus 15 circuits may be changed per revolution. Drive motor is mains operated 5 revs per min. Some of the many uses of this timer are Machinery control, Boiler firing, Dispensing and Vending machines, Display lighting animated and signs, Signalling, etc. Price from makers probably £20 each. Special snip price £2-95 £1-00 Post and VAT. Don't miss this terrific bargain.



HORSTMANN 24-HOUR TIME SWITCH

With 6 position programmer. When fitted to hot water systems this could programme as follows:

| Programme | Hot Water | Central Heating |
|-----------|--------------|-----------------|
| 0 | Off | Off |
| 1 | Twice Daily | Off |
| 2 | All Day | Off |
| 3 | Twice Daily | Twice Daily |
| 4 | All Day | All Day |
| 5 | Continuously | Continuously |

Suitable, of course, to programme other than central heating and hot water, for instance, programme upstairs and downstairs electric heating or heating and cooling or taped music and radio. In fact, there is no limit to the versatility of this Programmer. Mains operated. Size 3in x 3in x 2in deep. Price £2-50. 30p Post and VAT, as illustrated but less case.



CENTRIFUGAL BLOWER

Miniature mains driven blower centrifugal type blower unit by Woods. Powerful but specially built for quick running—driven by cushioned induction motor with specially built low noise bearings. Overall size 4 1/2" x 4 1/2" x 4". When mounted by flange, air is blown into the equipment but to suck air out, mount it from centre using clamp. Ideal for cooling electrical equipment or fitting into a cooker hood, film drying cabinet or for removing fume smoke when soldering, etc. etc. A real bargain at £2-50p. 55p Post and VAT.



SHORTWAVE CRYSTAL SET

Although this uses no battery it gives really amazing results. You will receive an amazing assortment of stations over the 19, 25, 31, 39 metre bands—Kit contains chassis front panel and all the parts. £1-25—crystal earphone 50p. 60p Post and VAT.



TERMS:

Where order is under £5 please add 30p surcharge to offset packing expenses.

NEW ITEMS THIS MONTH

EHT transformer. American made, sealed in a steel case measuring 8 1/2" x 6" x 5 1/2" high with large porcelain stand-off insulators; it is extremely well-made, looks good enough to give 10 kv at 1 amp, intended for American mains, its primary would have to be fed through a variac or similar. With 90v input EHT output is 6.5v. Price £15 each+carriage and VAT 23.

Sticker strip inter-phone. This is 4 copper wires mounted on an adhesive tape intended for telephone extensions, can also be used for 230v AC, etc. It is invisible under thick wallpaper and of course carpet or other floor coverings. Price 25 per 100' reel+postage and VAT 60p.

2 1/2" panel meter, 0-9 amps, flush mounting. These were made for military applications, probably measurements of RF power. They work on the hot wire principle so they are suitable for AC or DC measurements. These instruments have a considerable interest in schools and colleges over these days. Consequently they are very suitable for school labs, museums and exhibitions. Price £1-50 each+post and VAT 40p.

Instrument Mains Transformer, 6.3v at 1 amp and 115v at 100mA. This is an upright mounting open construction, small size (2 1/2" x 2 1/2" x 2 1/2"). Price £1-40+postage and VAT 60p. **DJFTO, 6.3v at 1 amp and 150v at 200 mA.** This is a fully shrouded upright mounting transformer, size approx. 2 1/2" x 3" x 3". Price £1-95+post and VAT 85p.

Instrument power supply mounted on a chassis size 9" x 2 1/2" x 4 1/2". This is suitable for instruments which use valves and has AC output of 6.3v at 1 amp and a fully smoothed DC outputs of 150v and 200v. Price £2-50+post and VAT 74p.

FM Band amplifier. This is a 4 valve amplifier tunable to cover FM frequencies. Tuning is by locking in fully screened compartments and the whole is mounted on a heavy metal chassis size 9" x 2 1/2" x 2 1/2". This requires a separate power supply of 150v DC at 100 mA and 6.3V at 1 amp. Price £3-75+post and VAT £1-58.

Instrument case, grey steel finish size 9 1/2" x 3 1/2" x 2 1/2". These cases are not secondhand but come from partly assembled equipment so the front panel has a few holes already punched through. However, these are very suitable for toggle switches, etc. There are no really big holes, 50p each+post and VAT 36p.

Instrument case, size 9" x 9" x 5 1/2", made from sheet steel grey hammer finish. No holes in these 75p+post and VAT 49p.

Holidays are coming, don't forget you can fool the thieves with our completely automatic daytime off, nighttime on switch; it is simplicity itself to fit—just put in parallel with landing light switch. Price this month and September is only 23+post and VAT 60p; after this the price has to up, probably to 24-50 owing to increased costs to us.

Pilot lamp bargain. Box of 10 x 24v .05 amp tubular MBS lamps made by Philips, the selling price of which is 25p each—our price only 50p per box.

Last chance for this wire bargain. Heavy duty 3 core waterproof flex 1.5 mm (8-10 amp) very heavy insulation, ideal for running down the garden, will take a heater as well as power tools; would cost 30p per metre in your local shop—our price, 100 meter coil only £7-50+£2.00 carriage and VAT per coil.

Micro Switches. Standard size and type made by Honeywell, Burgess, Frye, Plessey or similar famous makers, two tag type normally open. 15p each less usual quantity discount which makes them 8p each if you buy 1,000 or over. **DITTO,** change over switching. 15p each or 10p for 1,000 or over.

Relay by STC—8 pin octal base, plug-in with perspex cover over contacts, an expensive and well-made relay for 24 volt working. £1 each+VAT & post 10p.

0-1 mA panel meter, Eagle 1 1/2" square full vision, perspex cover, standard price over £3 each—sale price £2-30+post & VAT 80p.

Solenoid 230v mains operated. A small (1 1/2" x 1 1/2" x 1") solenoid metal encased with plunger. Sale price 40p each+post & V.A.T. 15p.

Reversible motor with gear box which rotates a splined shaft causing a carrier to travel backwards and forwards along same shaft; limit switches fitted at each end stop the motor. It is an extremely well-made device which could be used for opening and closing a door remotely, or similar. We have one only and the price is £25+carriage and V.A.T. £4.

Instrument motor with electro brake made by Evershed & Vigantiles Ltd. This is described as a hysteresis motor, maker's ref. FBX 25 CO30; the electro brake is easily removed. Sale price £4-50 each+post & V.A.T. 100p.

6 switch disco lamp controller. This is a mains motor driving a rotating drum made up of discs with cut-outs. As the cut-outs engage on the switch levers, contact is made via 10 amp switches. A large variety of lighting effects can be obtained. A real bargain at £2-75+post & V.A.T. 9" x 4" loudspeaker ceramic magnet 12 ohm coil so suitable for 8-15 ohm outputs, a good performer. Sale £1+post & V.A.T. 80p.

Microswitches 10 amp changeover, ex GPO equipment, but little used and any not received in perfect order would be exchanged. Price, 10 for 75p+post & V.A.T. 18p.

Clock switch for Tricity cooker, made by Smiths and probably a replacement in many of the two cookers. This has clock in the centre and the two control switches on the right-hand side. The top control switch sets the on-off times and is infinitely adjustable over the 12 hours; the lower switch selects manual or automatic. No glass front, but you could take this off your existing clock. Price £1-76 each+post & V.A.T. 36p.

J. BULL (ELECTRICAL) LTD.
(Dept. PW), 103 TAMWORTH RD.
CROYDON CRO IXX

BIPAK

SEMICONDUCTORS

TRANSISTORS

BRAND NEW FULLY GUARANTEED

| Type | Price | Type | Price | Type | Price | Type | Price |
|--------|-------|-------------------|-------|-------|-------|--------|-------|
| AC107 | 0.20 | BSY40 | 0.29 | AF118 | 0.31 | ORP61 | 0.41* |
| AC113 | 0.19 | BSY41 | 0.29 | AF124 | 0.36 | P20 | 0.51* |
| AC115 | 0.20 | BSY55 | 0.19 | AF125 | 0.31 | P20 | 0.51* |
| AC117 | 0.20 | BSY56A | 0.19 | AF127 | 0.29 | P346A | 0.20 |
| AC122 | 0.12 | BU105 | 0.24 | AF128 | 0.29 | P397 | 0.43 |
| AC125 | 0.18 | CL11E | 0.51 | AF129 | 0.29 | SP140 | 0.18 |
| AC126 | 0.18 | C400 | 0.51 | AF130 | 0.51 | ST141 | 0.18 |
| AC127 | 0.19 | C407 | 0.26 | AF131 | 0.51 | TIP29 | 0.44 |
| AC128 | 0.19 | C424 | 0.26 | AF132 | 0.51 | TIP30 | 0.52 |
| AC132 | 0.15 | C425 | 0.51 | AF133 | 0.51 | TIP31A | 0.56 |
| AC134 | 0.15 | C426 | 0.36 | AF134 | 0.51 | TIP32A | 0.58 |
| AC137 | 0.15 | C428 | 0.20 | AF135 | 0.51 | TIP33 | 0.58 |
| AC141 | 0.19 | C441 | 0.31 | AF136 | 0.51 | TIP34 | 0.58 |
| AC141K | 0.30 | C442 | 0.31 | AF137 | 0.51 | TIP35 | 0.58 |
| AC142 | 0.19 | C444 | 0.36 | AF138 | 0.51 | TIP36 | 0.58 |
| AC142K | 0.26 | C445 | 0.22 | AF139 | 0.51 | TIP37 | 0.58 |
| AC151 | 0.16 | MAT100 | 0.19 | AF140 | 0.51 | TIP38 | 0.58 |
| AC154 | 0.20 | MAT101 | 0.20 | AF141 | 0.51 | TIP39 | 0.58 |
| AC155 | 0.20 | MAT120 | 0.19 | AF142 | 0.51 | TIP40 | 0.58 |
| AC156 | 0.20 | MAT121 | 0.20 | AF143 | 0.51 | TIP41 | 0.58 |
| AC157 | 0.25 | MJE521 | 0.56 | AF144 | 0.51 | TIP42 | 0.58 |
| AC165 | 0.20 | MJE2955 | 0.88 | AF145 | 0.51 | TIP43 | 0.58 |
| AC166 | 0.20 | MJE3055 | 0.57 | AF146 | 0.51 | TIP44 | 0.58 |
| AC167 | 0.20 | MJE3440 | 0.51 | AF147 | 0.51 | TIP45 | 0.58 |
| AC168 | 0.25 | MPP102 | 0.45 | AF148 | 0.51 | TIP46 | 0.58 |
| AC169 | 0.15 | MPP104 | 0.38 | AF149 | 0.51 | TIP47 | 0.58 |
| AC176 | 0.20 | MPP105 | 0.38 | AF150 | 0.51 | TIP48 | 0.58 |
| AC177 | 0.25 | OC19 | 0.36 | AF151 | 0.51 | TIP49 | 0.58 |
| AC178 | 0.29 | OC20 | 0.45 | AF152 | 0.51 | TIP50 | 0.58 |
| AC179 | 0.29 | OC22 | 0.47 | AF153 | 0.51 | TIP51 | 0.58 |
| AC180 | 0.29 | OC23 | 0.49 | AF154 | 0.51 | TIP52 | 0.58 |
| AC180K | 0.30 | OC24 | 0.57 | AF155 | 0.51 | TIP53 | 0.58 |
| AC181 | 0.20 | OC25 | 0.39 | AF156 | 0.51 | TIP54 | 0.58 |
| AC181K | 0.30 | OC26 | 0.30 | AF157 | 0.51 | TIP55 | 0.58 |
| AC187 | 0.22 | OC28 | 0.51 | AF158 | 0.51 | TIP56 | 0.58 |
| AC187K | 0.23 | OC29 | 0.51 | AF159 | 0.51 | TIP57 | 0.58 |
| AC188 | 0.23 | OC30 | 0.45 | AF160 | 0.51 | TIP58 | 0.58 |
| AC188K | 0.23 | OC36 | 0.51 | AF161 | 0.51 | TIP59 | 0.58 |
| ACY17 | 0.26 | OC41 | 0.20 | AF162 | 0.51 | TIP60 | 0.58 |
| ACY18 | 0.20 | OC42 | 0.25 | AF163 | 0.51 | TIP61 | 0.58 |
| ACY19 | 0.20 | 2N918 | 0.31 | AF164 | 0.51 | TIP62 | 0.58 |
| ACY20 | 0.20 | 2N929 | 0.21 | AF165 | 0.51 | TIP63 | 0.58 |
| ACY21 | 0.20 | 2N930 | 0.21 | AF166 | 0.51 | TIP64 | 0.58 |
| ACY22 | 0.17 | 2N1131 | 0.20 | AF167 | 0.51 | TIP65 | 0.58 |
| ACY27 | 0.19 | 2N1132 | 0.22 | AF168 | 0.51 | TIP66 | 0.58 |
| ACY28 | 0.19 | 2N1302 | 0.15 | AF169 | 0.51 | TIP67 | 0.58 |
| ACY29 | 0.36 | 2N1303 | 0.15 | AF170 | 0.51 | TIP68 | 0.58 |
| ACY30 | 0.29 | 2N1304 | 0.18 | AF171 | 0.51 | TIP69 | 0.58 |
| ACY31 | 0.29 | 2N1305 | 0.18 | AF172 | 0.51 | TIP70 | 0.58 |
| ACY34 | 0.21 | 2N1306 | 0.21 | AF173 | 0.51 | TIP71 | 0.58 |
| BG173 | 0.15 | 2N1307 | 0.21 | AF174 | 0.51 | TIP72 | 0.58 |
| BC174 | 0.15 | 2N1308 | 0.24 | AF175 | 0.51 | TIP73 | 0.58 |
| BC175 | 0.22 | 2N1309 | 0.24 | AF176 | 0.51 | TIP74 | 0.58 |
| BC177 | 0.19 | 2N1613 | 0.20 | AF177 | 0.51 | TIP75 | 0.58 |
| BC178 | 0.19 | 2N1711 | 0.20 | AF178 | 0.51 | TIP76 | 0.58 |
| BC179 | 0.19 | 2N1839 | 0.32 | AF179 | 0.51 | TIP77 | 0.58 |
| BC180 | 0.25 | 2N1840 | 0.45 | AF180 | 0.51 | TIP78 | 0.58 |
| BC181 | 0.25 | 2N1893 | 0.38 | AF181 | 0.51 | TIP79 | 0.58 |
| BC182 | 0.15 | 2N2147 | 0.73 | AF182 | 0.51 | TIP80 | 0.58 |
| BC182L | 0.15 | 2N2148 | 0.58 | AF183 | 0.51 | TIP81 | 0.58 |
| BC183 | 0.15 | 2N2192 | 0.36 | AF184 | 0.51 | TIP82 | 0.58 |
| BC183L | 0.15 | 2N2193 | 0.36 | AF185 | 0.51 | TIP83 | 0.58 |
| BC184 | 0.26 | 2N2194 | 0.36 | AF186 | 0.51 | TIP84 | 0.58 |
| BC184L | 0.20 | 2N2217 | 0.32 | AF187 | 0.51 | TIP85 | 0.58 |
| BC186 | 0.29 | 2N2218 | 0.20 | AF188 | 0.51 | TIP86 | 0.58 |
| BC187 | 0.29 | 2N2219 | 0.20 | AF189 | 0.51 | TIP87 | 0.58 |
| BC207 | 0.11 | 2N2220 | 0.22 | AF190 | 0.51 | TIP88 | 0.58 |
| BC208 | 0.11 | 2N2221 | 0.20 | AF191 | 0.51 | TIP89 | 0.58 |
| BC209 | 0.25 | 2N2222 | 0.20 | AF192 | 0.51 | TIP90 | 0.58 |
| BC212L | 0.13 | 2N2368 | 0.15 | AF193 | 0.51 | TIP91 | 0.58 |
| BC213L | 0.13 | 2N2369 | 0.15 | AF194 | 0.51 | TIP92 | 0.58 |
| BC214L | 0.17 | 2N2369A | 0.15 | AF195 | 0.51 | TIP93 | 0.58 |
| BC225 | 0.28 | 2N2411 | 0.25 | AF196 | 0.51 | TIP94 | 0.58 |
| BC226 | 0.36 | 2N2412 | 0.25 | AF197 | 0.51 | TIP95 | 0.58 |
| BC291 | 0.28 | 2N2346 | 0.45 | AF198 | 0.51 | TIP96 | 0.58 |
| BC302 | 0.25 | 2N2711 | 0.22 | AF199 | 0.51 | TIP97 | 0.58 |
| BC303 | 0.21 | 2N2712 | 0.21 | AF200 | 0.51 | TIP98 | 0.58 |
| BC304 | 0.37 | 2N2714 | 0.21 | AF201 | 0.51 | TIP99 | 0.58 |
| BC440 | 0.31 | 2N2904 | 0.18 | AF202 | 0.51 | TIP100 | 0.58 |
| BC460 | 0.37 | 2N2904A | 0.21 | AF203 | 0.51 | TIP101 | 0.58 |
| BCY30 | 0.25 | 2N2905 | 0.21 | AF204 | 0.51 | TIP102 | 0.58 |
| BCY31 | 0.27 | 2N2905A | 0.21 | AF205 | 0.51 | TIP103 | 0.58 |
| BCY32 | 0.31 | 2N2906 | 0.16 | AF206 | 0.51 | TIP104 | 0.58 |
| BCY33 | 0.22 | 2N2906A | 0.19 | AF207 | 0.51 | TIP105 | 0.58 |
| BCY34 | 0.28 | 2N2907 | 0.20 | AF208 | 0.51 | TIP106 | 0.58 |
| BCY70 | 0.15 | 2N2907A | 0.22 | AF209 | 0.51 | TIP107 | 0.58 |
| BCY71 | 0.20 | 2N2923 | 0.15 | AF210 | 0.51 | TIP108 | 0.58 |
| BCY72 | 0.15 | 2N2924 | 0.15 | AF211 | 0.51 | TIP109 | 0.58 |
| BCZ10 | 0.20 | 2N2925 | 0.15 | AF212 | 0.51 | TIP110 | 0.58 |
| BCZ11 | 0.28 | ACY35 | 0.21 | AF213 | 0.51 | TIP111 | 0.58 |
| BCZ12 | 0.28 | ACY36 | 0.29 | AF214 | 0.51 | TIP112 | 0.58 |
| BD115 | 0.43 | ACY40 | 0.13 | AF215 | 0.51 | TIP113 | 0.58 |
| BD116 | 0.81 | ACY41 | 0.19 | AF216 | 0.51 | TIP114 | 0.58 |
| BD121 | 0.61 | ACY44 | 0.36 | AF217 | 0.51 | TIP115 | 0.58 |
| BD122 | 0.45 | AD120 | 0.49 | AF218 | 0.51 | TIP116 | 0.58 |
| BD124 | 0.70 | AD140 | 0.49 | AF219 | 0.51 | TIP117 | 0.58 |
| BD131 | 0.51 | AD142 | 0.49 | AF220 | 0.51 | TIP118 | 0.58 |
| BD132 | 0.61 | AD143 | 0.89 | AF221 | 0.51 | TIP119 | 0.58 |
| BD133 | 0.87 | AD149 | 0.51 | AF222 | 0.51 | TIP120 | 0.58 |
| BDY35 | 0.41 | AD161 | 0.86 | AF223 | 0.51 | TIP121 | 0.58 |
| BFY10 | 0.18 | AD162 | 0.86 | AF224 | 0.51 | TIP122 | 0.58 |
| BSX19 | 0.18 | AD161 & AD162(MF) | 0.86 | AF225 | 0.51 | TIP123 | 0.58 |
| BSX20 | 0.18 | AD161 & AD162(MF) | 0.86 | AF226 | 0.51 | TIP124 | 0.58 |
| BSY25 | 0.16 | ADY140 | 0.51 | AF227 | 0.51 | TIP125 | 0.58 |
| BSY27 | 0.16 | AF114 | 0.25 | AF228 | 0.51 | TIP126 | 0.58 |
| BSY28 | 0.16 | AF115 | 0.25 | AF229 | 0.51 | TIP127 | 0.58 |
| BSY29 | 0.16 | AF116 | 0.25 | AF230 | 0.51 | TIP128 | 0.58 |
| BSY32 | 0.17 | AF117 | 0.25 | AF231 | 0.51 | TIP129 | 0.58 |
| BSY39 | 0.19 | AF117 | 0.25 | AF232 | 0.51 | TIP130 | 0.58 |

* 74 SERIES T.T.L. I.C.'s

BI-PAK STILL LOWEST IN PRICE. FULL SPECIFICATION GUARANTEED. ALL FAMOUS MANUFACTURERS.

| Type | Quantities | Type | Quantities | Type | Quantities | | | | | | |
|------|------------|------|------------|------|------------|------|------|-------|------|------|------|
| 1 | 25 | 100+ | 1 | 25 | 100+ | | | | | | |
| 7420 | 0.14 | 0.13 | 0.12 | 7448 | 1.00 | 0.99 | 0.97 | 7412E | 0.05 | 0.03 | 0.00 |
| 7407 | 0.14 | 0.13 | 0.12 | 7450 | 0.14 | 0.13 | 0.12 | 7413E | 0.08 | 0.06 | 0.05 |
| 7409 | 0.14 | 0.13 | 0.12 | 7451 | 0.14 | 0.13 | 0.12 | 7414E | 0.07 | 0.06 | 0.05 |
| 7405 | 0.14 | 0.13 | 0.12 | 7452 | 0.14 | 0.13 | 0.12 | 7415E | 0.10 | 0.08 | 0.07 |
| 7404 | 0.14 | 0.13 | 0.12 | 7453 | 0.14 | 0.13 | 0.12 | 7416E | 0.10 | 0.08 | 0.07 |
| 7403 | 0.14 | 0.13 | 0.12 | 7454 | 0.14 | 0.13 | 0.12 | 7417E | 0.10 | 0.08 | 0.07 |
| 7402 | 0.14 | 0.13 | 0.12 | 7455 | 0.14 | 0.13 | 0.12 | 7418E | 0.10 | 0.08 | 0.07 |
| 7401 | 0.14 | 0.13 | 0.12 | 7456 | 0.14 | 0.13 | 0.12 | 7419E | 0.10 | 0.08 | 0.07 |
| 7400 | 0.14 | 0.13 | 0.12 | 7457 | 0.14 | 0.13 | 0.12 | 7420E | 0.10 | 0.08 | 0.07 |
| 7400 | 0.14 | 0.13 | 0.12 | 7458 | 0.14 | 0.13 | 0.12 | 7421E | 0.10 | 0.08 | 0.07 |
| 7400 | 0.14 | 0.13 | 0.12 | 7459 | 0.14 | 0.13 | 0.12 | 7422E | 0.10 | 0.08 | 0.07 |
| 7400 | 0.14 | 0.13 | 0.12 | 7460 | 0.14 | 0.13 | 0.12 | 7423E | 0.10 | 0.08 | 0.07 |
| 7400 | 0.14 | 0.13 | 0.12 | 7461 | 0.14 | 0.13 | 0.12 | 7424E | 0.10 | 0.08 | 0.07 |
| 7400 | 0.14 | 0.13 | 0.12 | 7462 | 0.14 | 0.13 | 0.12 | 7425E | 0.10 | 0.08 | 0.07 |
| 7400 | 0.14 | 0.13 | 0.12 | 7463 | 0.14 | 0.13 | 0.12 | 7426E | 0.10 | 0.08 | 0.07 |
| 7400 | 0.14 | 0.13 | 0.12 | 7464 | 0.14 | 0.13 | 0.12 | 7427E | 0.10 | 0.08 | 0.07 |
| 7400 | 0.14 | 0.13 | 0.12 | 7465 | 0.14 | 0.13 | 0.12 | 7428E | 0.10 | 0.08 | 0.07 |
| 7400 | 0.14 | 0.13 | 0.12 | 7466 | 0.14 | 0.13 | 0.12 | 7429E | 0.10 | 0.08 | 0.07 |
| 7400 | 0.14 | 0.13 | 0.12 | 7467 | 0.14 | 0.13 | 0.12 | 7430E | 0.10 | 0.08 | 0.07 |
| 7400 | 0.14 | 0.13 | 0.12 | 7468 | 0.14 | 0.13 | 0.12 | 7431E | 0.10 | 0.08 | 0.07 |
| 7400 | 0.14 | 0.13 | 0.12 | 7469 | 0.14 | 0.13 | 0.12 | 7432E | 0.10 | 0.08 | 0.07 |
| 7400 | 0.14 | 0.13 | 0.12 | 7470 | 0.14 | 0.13 | 0.12 | 7433E | 0.10 | 0.08 | 0.07 |
| 7400 | 0.14 | 0.13 | 0.12 | 7471 | 0.14 | 0.13 | 0.12 | 7434E | 0.10 | 0.08 | 0.07 |
| 7400 | 0.14 | 0.13 | 0.12 | 7472 | 0.14 | 0.13 | 0.12 | 7435E | 0.10 | 0.08 | 0.07 |
| 7400 | 0.14 | 0.13 | 0.12 | 7473 | 0.14 | 0.13 | 0.12 | 7436E | 0.10 | 0.08 | 0.07 |
| 7400 | 0.14 | 0.13 | 0.12 | 7474 | 0.14 | 0.13 | 0.12 | 7437E | 0.10 | 0.08 | 0.07 |
| 7400 | 0.14 | 0.13 | 0.12 | 7475 | 0.14 | 0.13 | 0.12 | 7438E | 0.10 | 0.08 | 0.07 |
| 7400 | 0.14 | 0.13 | 0.12 | 7476 | 0.14 | 0.13 | 0.12 | 7439E | 0.10 | 0.08 | 0.07 |
| 7400 | 0.14 | 0.13 | 0.12 | 7477 | 0.14 | 0.13 | 0.12 | 7440E | 0.10 | 0.08 | 0.07 |
| 7400 | 0.14 | 0.13 | 0.12 | 7478 | 0.14 | 0.13 | 0.12 | 7441E | 0.10 | 0.08 | 0.07 |
| 7400 | 0.14 | 0.13 | 0.12 | 7479 | | | | | | | |

PO BOX 6 WARE HERTS

SUPER UNTESTED PAKS

| Pak No. | Description | Sp | Price |
|---------|---|-----|--------|
| U 1 | 120 Glass Sub-min. General purpose Germ. diodes | ... | 0-60 |
| U 2 | 50 Mixed Germanium transistors AF/RF | ... | 0-60 |
| U 3 | 75 Germanium gold bonded sub-min. like OA5, OA47 | ... | 0-60 |
| U 4 | 30 Germanium transistors like OC31, AC128 | ... | 0-60 |
| U 5 | 60 200mA sub-min. silicon diodes | ... | 0-60 |
| U 6 | 30 Sil. Planar trans. NPN like B5Y95A, 2N706 | ... | 0-60 |
| U 7 | 16 Sil. rect. TOP-HAT 750mA VLTG. RANGE up to 100 | ... | 0-60 |
| U 8 | 50 Sil. planar diodes DO-7 glass 250mA like OA200/202 | ... | 0-60 |
| U 9 | 20 Mixed voltages, 1 Watt Zener Diodes | ... | 0-60 |
| U10 | 20 BAY50 charge storage diodes DO-7 glass | ... | 0-60 |
| U11 | 20 NPN Sil. planar trans. TO-5 like 2N1132, 2N2904 | ... | 0-60 |
| U13 | 30 PNP-NPN Sil. transistors OC200 & 2S104 | ... | 0-60 |
| U14 | 150 Mixed silicon and germanium diodes | ... | 0-60 |
| U15 | 20 NPN Sil. planar trans. TO-5 like 2N695, 2N697 | ... | 0-60 |
| U16 | 10 3Amp sil. rectifiers stud type up to 1000 PIV | ... | 0-60 |
| U17 | 30 Germanium PNP AF transistors TO-5 like ACY 17-22 | ... | 0-60 |
| U18 | 8 6 Amp sil. rectifiers BZY12 type up to 600 PIV | ... | 0-60 |
| U19 | 20 Silicon NPN transistors like BC 108 | ... | 0-60 |
| U20 | 12 1-5 Amp sil. rectifiers top hat up to 1000 PIV | ... | 0-60 |
| U21 | 30 AF. Germ. alloy transistors 2G300 series & OC71 | ... | 0-60 |
| U23 | 25 MADT's like MHz series PNP transistors | ... | 0-60 |
| U24 | 20 Germ. 1 Amp rectifiers GJM series up to 300 PIV | ... | 0-60 |
| U25 | 25 300 MHz NPN silicon transistors 2N705, B5Y27 | ... | 0-60 |
| U26 | 20 Fast switching silicon diodes like 1N914 Micro-Min | ... | 0-60 |
| U29 | 10 1 Amp SCR's TO-5 can. up to 600 PIV CRS1/25-600 | ... | £1-20* |
| U32 | 25 Zener diodes 400 mW DO-7 case 3-33 volts mixed | ... | 0-60 |
| U33 | 15 Plastic case 1 Amp sil. rectifiers 1N4009 series | ... | 0-60 |
| U34 | 30 Silicon PNP alloy trans. TO-5 BCY26 88902/4 | ... | 0-60 |
| U35 | 25 Silicon planar transistors PNP TO-18 2N2906 | ... | 0-60 |
| U36 | 20 Silicon planar NPN transistors TO-5 BFY50/51/52 | ... | 0-60 |
| U37 | 30 Silicon alloy transistors SO-2 PNP OC300, S2322 | ... | 0-60 |
| U38 | 20 Fast switching silicon trans. NPN 400 MHz 2N3011 | ... | 0-60 |
| U39 | 30 RF. Ger. PNP transistors 2N1303/5 TO-5 | ... | 0-60 |
| U40 | 10 Dual transistors 6 lead TO-5 2N2060 | ... | 0-60 |
| U43 | 25 Silicon trans. plastic TO-18 A.F. BC113/114 | ... | 0-60 |
| U44 | 20 Silicon trans. plastic TO-5 BC115 | ... | 0-60 |
| U45 | 7 3A SCR. TO66 up to 600 PIV | ... | £1-20* |
| U46 | 20 Unijunction transistors similar to T1843 | ... | 0-60* |
| U47 | 10 TO220AB plastic triacs 50V 6A | ... | £1-20* |
| U48 | 9 NPN Sil. power transistors like 2N3055 | ... | £1-20* |
| U49 | 12 NPN Sil. plastic power trans. 60W like 2N294/2996 | ... | £1-20 |

Code No's mentioned above are given as a guide, to the type of device in the pak. The devices themselves are normally unmarked.

QUALITY TESTED PAKS

| Pak No. | Quality Tested Paks | Price |
|---------|--|--------|
| Q 1 | 20 Red spot transistors PNP | 0-60 |
| Q 2 | 16 White spot R.F. transistors PNP | 0-60 |
| Q 3 | 4 OC 77 type transistors | 0-60 |
| Q 4 | 6 Matched transistors OC44/45/81/81D | 0-60 |
| Q 5 | 4 OC 75 transistors | 0-60 |
| Q 6 | 5 OC 72 transistors | 0-60 |
| Q 7 | 4 AC 128 transistors PNP high gain | 0-60 |
| Q 8 | 4 AC 126 transistors PNP | 0-60 |
| Q 9 | 7 OC 81 type transistors | 0-60 |
| Q 10 | 7 OC 71 type transistors | 0-60 |
| Q11 | 2 AC 127/128 Complementary pairs PNP/NPN | 0-60 |
| Q12 | 3 AF 116 type transistors | 0-60 |
| Q13 | 3 AF 117 type transistors | 0-60 |
| Q14 | 3 OC 171 H.F. type transistors | 0-60 |
| Q15 | 7 2N2926 Sil. Epoxy transistors mixed colours | 0-60 |
| Q17 | 5 NPN 2 x ST.141. & 3 x ST.140 | 0-60 |
| Q18 | 4 MADT'S 2 x MAT 100 & 2 x MAT 120 | 0-60 |
| Q19 | 3 MADT'S 2 x MAT 101 & 1 x MAT 121 | 0-60 |
| Q20 | 4 OC 44 Germanium transistors A.F. | 0-60 |
| Q21 | 4 AC 127 NPN Germanium transistors | 0-60 |
| Q22 | 20 NKT transistors A.F. R.F. coded | 0-60 |
| Q23 | 10 OA 202 Silicon diodes sub-min | 0-60 |
| Q24 | 8 OA 81 diodes | 0-60 |
| Q25 | 15 IN 914 Silicon diodes 75PIV 75mA | 0-60 |
| Q26 | 8 OA95 Germanium diodes sub-min-IN69 | 0-60 |
| Q27 | 2 10A 600 PIV Silicon rectifiers IS425B | 0-60* |
| Q28 | 2 Silicon power rectifiers BZY 13 | 0-60 |
| Q29 | 4 Sil. transistors 2 x 2N696, 1 x 2N697, 1 x 2N698 | 0-60 |
| Q30 | 7 Silicon switch transistors 2N706 NPN | 0-60 |
| Q31 | 6 Silicon switch transistors 2N705 NPN | 0-60 |
| Q32 | 3 PNP Sil. trans. 2 x 2N131, 1 x 2N132 | 0-60 |
| Q33 | 3 Silicon NPN transistors 2N1711 | 0-60 |
| Q34 | 7 Sil. NPN trans. 2N2369, 500MHz (code P397) | 0-60 |
| Q35 | 3 Silicon PNP TO-5 2 x 2N2904 & 1 x 2N2095 | 0-60 |
| Q36 | 7 2N3646 TO-18 plastic 300 MHz NPN | 0-60 |
| Q37 | 3 2N3053 NPN Silicon transistors | 0-60 |
| Q38 | 5 PNP transistors 3 x 2N3703, 2 x 2N3702 | 0-60 |
| Q39 | 5 NPN transistors 3 x 2N3704, 2 x 2N3705 | 0-60 |
| Q40 | 5 NPN transistors 3 x 2N3707, 2 x 2N3708 | 0-60 |
| Q41 | 3 Plastic NPN TO18 2N3904 | 0-60 |
| Q43 | 5 BC 107 NPN transistors | 0-60 |
| Q44 | 5 NPN transistors 3 x BC 102, 2 x BC 109 | 0-60 |
| Q45 | 3 BC 113 NPN TO-18 transistors | 0-60 |
| Q46 | 3 BC 115 NPN TO-5 transistors | 0-60 |
| Q47 | 4 NPN high gain transistors 2 x BC 157, 2 x BC 168 | 0-60 |
| Q48 | 3 BCY 70 PNP transistors TO-18 | 0-60 |
| Q49 | 3 NPN transistors 2 x BFY 51, 1 x BFY 52 | 0-60 |
| Q50 | 7 B5Y 95 NPN switch transistors TO-18 | 0-60 |
| Q51 | 7 B5Y 95A NPN transistors 300MHz | 0-60 |
| Q52 | 8 BD 100 type silicon rectifiers | 0-60 |
| Q53 | 25 Sil. & Germ. trans. mixed all marked new | £1-50 |
| Q54 | 6 TIL 209 Red LED | £1-20* |

MAMMOTH I.C. PAK

APPROX. 200 PIECES
Assorted fall-out integrated circuits, including: Logic, 74 series, Linear, Audio and D.T.L. Many coded devices but some unmarked—you to identify.
OUR SPECIAL PRICE £1.20p

WORLD SCOOP

JUMBO SEMICONDUCTOR PAK
Transistors—Germ. and Silicon. Rectifiers—Diodes—Triacs—Thyristors—I.C.'s and Zeners. ALL NEW AND CODED
APPROX 100 PIECES
Offering the amateur a fantastic bargain PAK and an enormous saving—identification and data sheet in every pak.
ONLY £1.85p

UNTESTED LIN PAKS

Manufacturers 'Fall Outs' which include Functional and part Functional Units. These are classed as 'out-of-spec' from the makers' very rigid specifications, but are ideal for learning about I.C.'s and experimental work.

| Pak No. | Contents | Price |
|---------|------------|-------|
| ULIC709 | = 10 x 710 | 0-60 |
| ULIC710 | = 7 x 710 | 0-60 |
| ULIC741 | = 7 x 741 | 0-60 |
| ULIC747 | = 5 x 747 | 0-60 |
| ULIC748 | = 7 x 748 | 0-60 |

C280 CAPACITOR PAK

Containing 75 of the C280 range of capacitors assorted in values ranging from .01uF to 2.2uF. Complete with identification chart.
FANTASTIC VALUE ONLY £1.20p

SIL. G.P. DIODES

300 mW 40 PIV (min) SUB-MIN FULLY TESTED
Ideal for Organ builders
30 for 50p, 100 for £1.50, 500 for £5, 1000 for £8.

G.P. SWITCHING TRANS

TO18 SIM. TO 2N706/8 B5Y27/28/95A
All usable devices. No open and shorts. ALSO AVAILABLE IN NPN similar to 2N2906, BCY 70 20 for 50p, 50 for £1, 100 for £1.30, 500 for £8, 1000 for £14.
When ordering please state NPN or PNP

G.P. 100

30 WATT GERMANIUM TO8 METAL CASE
Vceo 80V, Vceo 50V, IC 10A, Hfe 30-170 replaces the majority of Germanium power Transistors in the OC, AD NKT range.

| | 1-24 44p | 25-99 41p | 100+ 37p |
|--|-------------|--------------|-------------|
|--|-------------|--------------|-------------|

G.P. 300

115 WATT SILICON TO8 METAL CASE
Vceo 100V, Vceo 60V, IC 15A, Hfe, 20-100 suitable replacement for 2N3055, BDY11 or BDY20

| | 1-24 50p | 25-99 48p | 100+ 40p |
|--|-------------|--------------|-------------|
|--|-------------|--------------|-------------|

INDICATORS

3015F Minitor 7 Segment Indicator £1.11p**
MAN 3M L.E.D. 7 SEGMENT DISPLAY O.127" High Characters £1.76p**

ZENER DIODES

FULL RANGE IN STOCK
VOLTAGE RANGE 2-33V

| 400 mw 8p | 1-5 w 17p | 10 w** 80p |
|--------------|--------------|---------------|
|--------------|--------------|---------------|

EXCLUDE VAT AT 25% TO ALL
***ADD 8% NO VAT**
add 20p overseas
Minimum order 75p

VOLTAGE REGULATORS

To.3 Plastic Encapsulation
u.A.7808/L129 5V (Eqiv. to MVR5V) £1-25p
u.A.7812/L120 12V (Eqiv. to MVR12V) £1-25p
u.A.7815/L131 15V (Eqiv. to MVR15V) £1-25p
u.A.7818 18V (Eqiv. to MVR18V) £1-25p

THYRISTORS

| PIV | 0-6A | 0-8A | 1A | 3A | 5A | 5A | 7A | 10A | 16A | 30A |
|-----|------|------|------|------|------|------|------|------|-------|-------------|
| | TO18 | TO92 | TO5 | TO66 | TO66 | TO64 | TO48 | TO48 | TO48 | TO48 |
| 10 | 0-15 | 0-15 | — | — | — | — | — | — | — | — |
| 20 | 0-15 | 0-15 | — | — | — | — | — | — | — | — |
| 30 | 0-19 | 0-22 | — | — | — | — | — | — | — | — |
| 50 | 0-22 | 0-28 | 0-20 | 0-25 | 0-36 | 0-36 | 0-48 | 0-51 | 0-54 | £1-18 |
| 100 | 0-25 | 0-30 | 0-25 | 0-25 | 0-48 | 0-48 | 0-61 | 0-57 | 0-58 | £1-43 |
| 150 | 0-31 | 0-38 | — | — | — | — | — | — | — | — |
| 200 | 0-38 | 0-44 | 0-25 | 0-30 | 0-50 | 0-50 | 0-57 | 0-62 | 0-62 | £1-63 |
| 400 | — | — | 0-30 | 0-39 | 0-55 | 0-57 | 0-71 | 0-77 | 0-77 | £1-79 |
| 600 | — | — | 0-35 | 0-43 | 0-69 | 0-69 | 0-78 | 0-99 | 0-99 | £1-60 |
| 800 | — | — | 0-38 | 0-48 | 0-65 | 0-65 | 0-81 | 0-82 | £1-22 | £1-39 £4-07 |

DIODES

| Type | Price | Type | Price | Type | Price | Type | Price |
|-------|-------|--------------|-------|--------------|-------|--------|-------|
| AA119 | 0-08 | BY101 | 0-12 | BZY216 | 0-41 | OA85 | 0-09 |
| AA120 | 0-08 | BY105 | 0-12 | BZY217 | 0-36 | OA90 | 0-07 |
| AA129 | 0-08 | BY114 | 0-12 | BZY218 | 0-36 | OA81 | 0-07 |
| AA330 | 0-09 | BY124 | 0-12 | BZY219 | 0-28 | OA95 | 0-07 |
| AAZ13 | 0-10 | BY126 | 0-15 | CG82 | — | OA200 | 0-07 |
| BA100 | 0-10 | BY127 | 0-16 | (OA91Eq) | 0-06 | OA202 | 0-07 |
| BA116 | 0-21 | BY128 | 0-16 | CG851 (OA70) | — | SD10 | 0-06 |
| BA126 | 0-22 | BY130 | 0-17 | OA79 | 0-07 | SD19 | 0-07 |
| BA148 | 0-15 | BY133 | 0-21 | OA5 Short | — | IN34 | 0-07 |
| BA154 | 0-12 | BY164 | 0-51 | Lead. | 0-01 | IN34A | 0-07 |
| BA155 | 0-15 | BX338/300-43 | — | OA10 | 0-14 | IN914 | 0-06 |
| BA156 | 0-14 | BZY10 | 0-36 | OA47 | 0-07 | IN916 | 0-06 |
| BA173 | 0-15 | BZY11 | 0-31 | OA70 | 0-07 | IN4148 | 0-06 |
| BB104 | 0-16 | BZY12 | 0-31 | OA79 | 0-07 | 18021 | 0-10 |
| BY100 | 0-16 | BZY13 | 0-26 | OA81 | 0-07 | 18951 | 0-70 |

UNTESTED T.L. PAKS

Manufacturers 'Fall Outs' which include Functional and part Functional Units. These are classed as 'out-of-spec' from the makers' very rigid specifications, but are ideal for learning about I.C.'s and experimental work.

| Pak No. | Contents | Price | Pak No. | Contents | Price |
|---------|-------------|-------|-------------------------|-------------|-------|
| UIC00 | = 12 x 7400 | 0-60 | UIC72 | = 8 x 7472 | 0-60 |
| UIC01 | = 12 x 7401 | 0-60 | UIC73 | = 8 x 7473 | 0-60 |
| UIC02 | = 12 x 7402 | 0-60 | UIC74 | = 8 x 7474 | 0-60 |
| UIC03 | = 12 x 7403 | 0-60 | UIC75 | = 8 x 7475 | 0-60 |
| UIC04 | = 12 x 7404 | 0-60 | UIC76 | = 8 x 7476 | 0-60 |
| UIC05 | = 12 x 7405 | 0-60 | UIC80 | = 5 x 7480 | 0-60 |
| UIC06 | = 8 x 7406 | 0-60 | UIC81 | = 5 x 7481 | 0-60 |
| UIC07 | = 8 x 7407 | 0-60 | UIC82 | = 5 x 7482 | 0-60 |
| UIC10 | = 12 x 7410 | 0-60 | UIC83 | = 5 x 7483 | 0-60 |
| UIC13 | = 8 x 7413 | 0-60 | UIC86 | = 5 x 7486 | 0-60 |
| UIC20 | = 12 x 7420 | 0-60 | UIC90 | = 5 x 7490 | 0-60 |
| UIC30 | = 12 x 7430 | 0-60 | UIC91 | = 5 x 7491 | 0-60 |
| UIC40 | = 12 x 7440 | 0-60 | UIC92 | = 5 x 7492 | 0-60 |
| UIC41 | = 5 x 7441 | 0-60 | UIC93 | = 5 x 7493 | 0-60 |
| UIC42 | = 5 x 7442 | 0-60 | UIC94 | = 5 x 7494 | 0-60 |
| UIC43 | = 5 x 7443 | 0-60 | UIC95 | = 5 x 7495 | 0-60 |
| UIC44 | = 5 x 7444 | 0-60 | UIC96 | = 5 x 7496 | 0-60 |
| UIC45 | = 5 x 7445 | 0-60 | UIC99 | = 5 x 7499 | 0-60 |
| UIC46 | = 5 x 7446 | 0-60 | UIC100 | = 5 x 74100 | 0-60 |
| UIC47 | = 5 x 7447 | 0-60 | UIC121 | = 5 x 74121 | 0-60 |
| UIC48 | = 5 x 7448 | 0-60 | UIC141 | = 5 x 74141 | 0-60 |
| UIC50 | = 5 x 7450 | 0-60 | UIC151 | = 5 x 74151 | 0-60 |
| UIC51 | = 12 x 7451 | 0-60 | UIC154 | = 5 x 74154 | 0-60 |
| UIC53 | = 12 x 7453 | 0-60 | UIC193 | = 5 x 74193 | 0-60 |
| UIC54 | = 12 x 7454 | 0-60 | UIC199 | = 5 x 74199 | 0-60 |
| UIC60 | = 12 x 7460 | 0-60 | UIC X1 25 Assorted 74's | £1-50 | |
| UIC70 | = 8 x 7470 | 0-60 | | | |

CAUSE FOR ALARM!

AT a recent press conference *New Scientist* magazine demonstrated just how easy it is to bug an MP's private conversation within the House of Commons. A simple bugging device (miniature radio transmitter) was planted in the MP's office, without his knowledge, by a member of the staff of *New Scientist*. His conversation was not only bugged but recorded in another office within the House of Commons and outside the House, on Westminster Bridge!

It appears that the sole purpose of the *New Scientist* exercise* was to publicly demonstrate just how easy it is to bug any building or person, and that even strict security is not a defence against bugging. The alarming extent to which the magazine was proven right was confirmed by photographs and tape recordings of the House of Commons bugging operation.

It will surely come as a surprise to many of our readers that the only offence that appears to have been committed was contravention of the Wireless Telegraphy Acts—operating a radio transmitter without a licence! There is no doubt whatsoever that the Radio Regulatory Department of the Home Office would certainly not have issued a licence for the operation of this device, which operated within the 88-108 MHz FM broadcast band.

Anti-bugging equipment is used in the House of Commons for the detection of bugging devices, but with its vast number of rooms and also the large daily influx of thousands of people, it would therefore be quite easy for an individual or organisation to plant one or more bugging devices, which could go undetected indefinitely. The bugging/electronic surveillance industry both in this country and abroad produces some highly sophisticated devices, many operating on frequencies and principles which make their detection by current anti-bugging equipment virtually impossible. There certainly appears to be a recent proliferation by companies in the UK, of electronic surveillance devices.

Advertisements offering micro or miniature VHF transmitters to all and sundry appear regularly in newspapers and periodicals. Anyone can purchase these devices by post and there is no doubt whatsoever that they are certainly in widespread use as bugging or surveillance devices not only in the UK but also in other countries. No boardroom, office, laboratory, workshop, vehicle or person for that matter, is free from the threat of electronic bugging.

The next time you go out for your "evening pint at the local," beware of what you say. Someone up to several hundred yards away may be "tuned-in" to you!

Think about it.

* "How we bugged the Commons"—*New Scientist* 10th July 1975

LIONEL E. HOWES—*Editor*

NEWS...

CMOS book

MOTOROLA have just published a comprehensive 48-page new CMOS brochure which is available free of charge to all electronics engineers. The brochure lists the entire Motorola CMOS family and is complete with a full set of logic diagrams and family technical data. Advanced information is given on nearly 40 new CMOS devices that will be introduced by Motorola during 1975, including some functions that have never been available before in integrated circuit form.

Of particular value is the section devoted to equivalents of Motorola CMOS devices. This includes an 'other manufacturers' to Motorola interchangeability guide, a complex function (MC14500 family) equivalents chart listing devices from ten different manufacturers, and a list of TTL/CMOS functional equivalents.

The brochure also includes a CMOS interface guide, design hints and a bibliography of applications notes and technical articles. *Motorola Ltd., Semiconductor Products Division, York House, Empire Way, Wembley, Middlesex.*

Low-cost solar cells

BELL Telephone Laboratories have announced two new electronic devices which may provide a cheap means of providing electrical power from the sun's energy.

Should it be possible for the new devices to be manufactured using thin-film techniques—like those employed for making integrated circuits—they should be much cheaper to manufacture than silicon solar cells.

The new devices are an offshoot of studies involving the finding of new photodetectors for converting light into electrical signals. One of them has an efficiency of 12.5% in converting sunlight into electricity. This compares with the efficiency of the silicon solar cells used in space vehicles and satellites.

Osmor coils

OSMOR Limited tell us that they still receive numerous requests from constructors all over the world for coils. The Company ceased production of RF coils some 7 years ago to concentrate on their main products, reed relays.

Error

Due to an error, the Linear I.C. section of the Chromasonic Electronics advert in the July 1975 issue of Practical Wireless, was incorrectly priced. The magazine apologizes for any inconvenience caused to readers.

Sir Edward Fennessy

THE Council is pleased to announce that Sir Edward Fennessy has accepted an invitation to become a Vice President of the Society of Electrical and Radio Technicians.

Sir Edward's career in electronics goes back to 1934 when he joined Standard Telephones & Cables Limited development laboratories after graduating from London University. In 1938 he moved to the Air Ministry research establishment at Bawdsey where he joined the team working on the development of radar. In 1940 he entered the Royal Air Force where he was immediately involved in the planning and construction of radar defences. When he left the RAF in 1945, he was a group captain and chief engineer of No. 60 Group. He joined the Board of Decca Navigator Company and between 1946 and 1949 established the system as an international marine aid to navigation. His next appointment was Managing Director of Decca Radar, a position which he held for fifteen years. He became Managing Director of Plessey Company Electronics Group in 1965.

He joined the Post Office as Managing Director Telecommunications and a member of the Board in 1969. In 1973 he was appointed additionally as Board

Design guide

A 36-PAGE GUIDE to the range of digital products available has been produced by Semicomps Ltd., and is obtainable free of charge. The guide covers not only the main general purpose logic families but also the large area of MOS memories, shift registers and special purpose LSI circuits. Products from leading manufacturers such as Motorola, R.C.A., Signetics, G.I.M., Mostek and Ferranti are included to make this one of the most comprehensive aids available for the digital designer. *Semicomps Ltd., 5c Northfield Industrial Estate, Beresford Avenue, Wembley, Middlesex HA0 1SD.*

Richard Arbib

RICHARD ARBIB, who has died aged 65, was Chairman of Kelsey Industries Ltd. He was also Chairman of Multicore Solders Limited since that Company started in 1939. He built Multicore up into the largest manufacturer of flux-cored solder wires in the world and the Company was one of the first winners of the Queen's Award to Industry for outstanding export achievement in 1966.

In recent years he made a considerable contribution in establishing BIB Hi-Fi Accessories Limited, the manufacturers of Europe's largest range of hi-fi accessories for audio equipment, and many products within the range were his own invention.

Mr. Arbib served on the Radio Industry's Council and the Council of the Radio and Electronic Component Manufacturers Federation for over 30 years and was been closely associated with the electronics industry during his whole career.

member for data processing and was reappointed Managing Director Telecommunications for a further three years.

He received a knighthood in the New Year's Honours List and became Deputy Chairman of the Post Office in March of this year.

Books received

World Radio/TV Handbook

A complete directory of international radio and television. Contains details of every short-wave station around the world, frequencies used by each country, foreign broadcasts, long and medium wave stations together with domestic programming.

Price £3.50 (soft cover)

£5.00 (hard cover)

Billboard Limited, 7 Carnaby Street, London, W1V 1PG. Telephone: 01-437 8090.

Ernie and 'Irene'

THAT machine which selects Premium Bond numbers up at Lytham St. Annes, namely ERNIE (Electronic Random Number Indicator Equipment) now has a sister.

Plessey Telecommunications is producing for the Central Bank of the Philippines a sister installation which has been christened IRENE. (Indicating Random Electronic Numbering Equipment).

IRENE is a complex of electronic units controlled by a computer. Winning numbers are generated at random and stored in the computer memory for checking and subsequent transfer to magnetic tape machines.

RAE Course

THE City of Bath Technical College, Avon St. Bath, will be offering a course of instruction to prepare for the May 1976 City & Guilds Radio Amateurs Exam.

The tutor is P. A. Bubb G3UWJ.

Further details and enrolment at the College 11th and 12th September.

A RADIO Amateur Course will be held at the North East Essex Technical College, Sheepen Road, Colchester, Essex. For further information please contact D. Mason, Electrical Engineering Department, at the College, Sheepen Road, Colchester, Essex, CO3 3LL or telephone Colchester 70271 ext. 66.

ON-SCREEN SCORING

40305

for

TELE-TENNIS

E.A. PARR B.Sc., C. Eng., M.I.E.E.

THE P.W. Tele Tennis game is an excellent starting point for anyone wishing to experiment with TV games. Most games require some form of scoring and this article describes a method similar to the commercial version seen in arcades where the score is displayed on the screen itself.

MODIFICATIONS TO CIRCUITRY

As originally described there are no signals inside the game which indicate which player has won or lost. These signals are provided by new serve/lose logic on Board G which replaces the serve/lose logic on Board D of the original game. (To avoid confusion with existing boards and components, all items in the modifications are numbered sequentially from the existing game.)

The logic of Board G is shown on Fig. 1.

This is very similar to the original logic on Board D except that a "lose" signal is generated and stored separately for left and right players. The score counter counts on a negative-going (1 to 0) edge.

Suppose the left hand player misses the ball. A coincidence between "ball" and "left base" will be detected by IC34a and its output will go to 0. This will set the bistable formed by IC33a and IC33b, the output of IC33b going to 0. This blanks the ball, and at the same time the 1 to 0 edge is used to step the counter. This output is therefore labelled "count right". (As the left hand player lost, the right hand player's score is incremented.)

The ball, meanwhile, is still bouncing around the court even though it is blanked, so detection of a miss must be prevented on the right hand side. The "count right" output, which is still at 0 is taken to IC34c to inhibit the detection of the coincidence of the ball and right base. The blanked ball can now bounce round the court indefinitely without further effect on the count outputs.

The sequence of events if the right player misses the ball is similar. The bistable formed by IC33c and IC33d is set, the ball is blanked and IC34a inhibited by "count left".

The serve logic is also similar to that on Board D. The two serve buttons are gated with (right base

+ right bat) and (left base + left bat) signals and the resulting 0 output from IC32b or IC32a used to reset both of the "lose" bistables. The ball is unblanked and the game starts. The normally closed contacts on each serve button inhibit the "miss" that could be generated at the moment the ball is served.

GAME IN PROGRESS

The on-screen display circuit requires a signal indicating that a game is in progress to turn off the display during a game. This is provided by IC35a which gives a 0 out when both "count right" and "count left" are at 1. This will occur when both "lose" states are reset, i.e., a game is being played.

The modifications required on Board D are quite straightforward. First, ICs 28 and 29 are removed. If sockets have been used on Board D these ICs can be reclaimed for use elsewhere.

Next the two signals "left bat or left base" and "right bat or right base" are brought out. This is best done by connecting to the wire links on Board D as shown in Fig. 7.

The serve button connections are transferred or linked to Board G. Note that the two normally closed contacts are now used independently.

Finally on Board D, the "ball" and "blanked ball" pins are linked to the same pins on Board G.

The other signals required by Board G are "left base" and "right base". These are already provided on Board B.

These interconnections are summarised on Fig. 2.

When Board G is connected to Board D the game can be played as before; it is not necessary to complete the display circuits at the same time.

SERVE INDICATOR

Board G also contains logic to indicate which player is to serve. Tele Tennis is usually played to a rough adaptation of table tennis, i.e., first to 21 wins.

In table tennis, the players change serves after


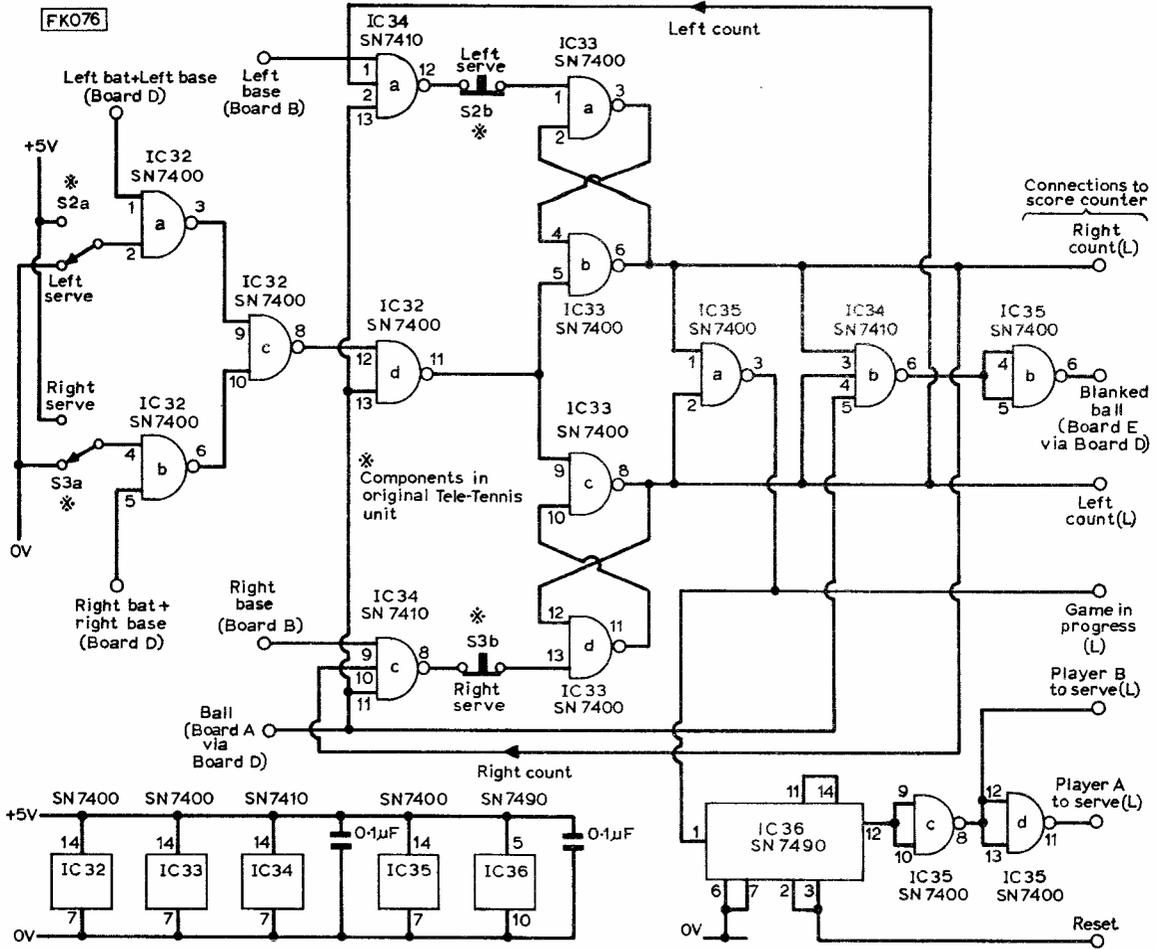


Fig. 1: Logic diagram of Board G which contains the new Serve/Lose logic. The (L) after some of the signals indicates negative logic (logic 1 = 0V).
 Fig. 2: below, Summary of connections to Board G from the original Tele Tennis Boards B and modified Board D (see Fig. 7).

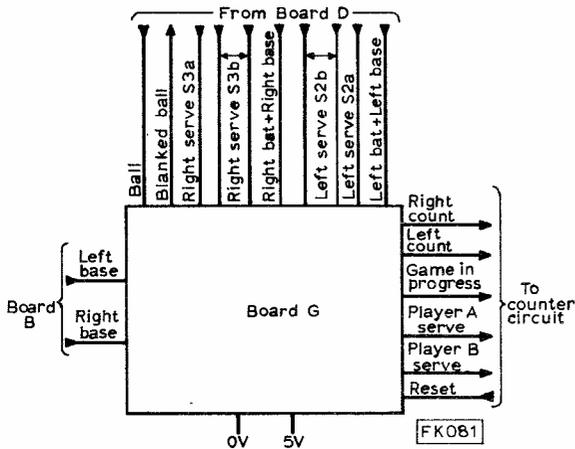

five serves. A counter is included on Board G to count serves and indicate which player is to serve next.

The counter used is IC36, a 7490 decade counter which conveniently consists of a ÷5 counter and an independent ÷2 counter.

The ÷5 counter counts the serves from the "game in progress" signal and after five serves the ÷2

counter changes state indicating that the service passes to the other player. After another five serves the ÷2 counter changes back. The serve indicators are displayed on the screen itself.

The serve counter is reset by the button used to reset the score counters.

If it is required to add the serve indicators only without the scoring, a suitable signal exists within Board D. The output of IC27d goes from 1 to 0 on each serve, and this signal can be used to step the 7490.

The format of the on-screen display is shown in Fig. 3. As can be seen, the numbers are formed from seven segments identical to a conventional seven-segment display.

As in the original game, generation of the ball, bats and base lines is a question of timing to give a bright-up on the screen at the correct time.

The timing of the character generation is shown on Fig. 4. Delay Q1 is fired by the line sync pulse, and Delay Q4 by the field sync pulse. These determine horizontal and vertical position of the characters respectively.

Delay Q1 starts an oscillator consisting of two delays Q2 and Q3. These determine the width and separation of the characters respectively.

Delay Q4 fires Delay Q5 which on completion of its delay fires Delay Q6. These determine the height

★ components list

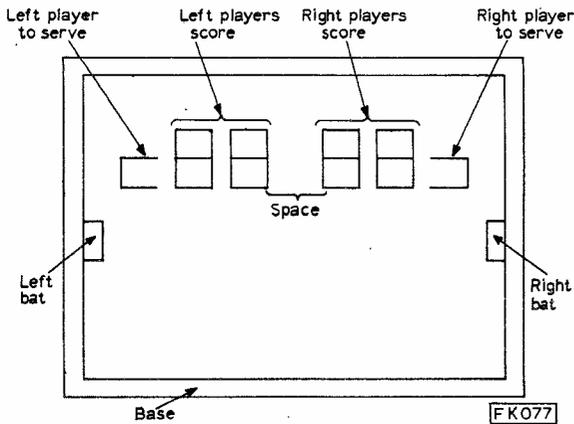


Fig. 3: Format of the scoring display on the TV screen. Only one of the serve indicators will appear at a time and the whole display is blanked during the course of a game.

of the top and bottom halves of the character respectively.

At the end of delays Q2 to Q6 a narrow strobe pulse is generated. These strobe pulses are labelled SP2 to SP6 and determine the width of the lines in the character.

It can be seen that

- Segment a occurs at (SP2 OR Q2) AND SP4
- Segment b occurs at (SP5 OR Q5) AND SP2
- Segment c occurs at (SP6 OR Q6) AND SP2
- Segment d occurs at (SP2 OR Q2) AND SP6
- Segment e occurs at (SP6 OR Q6) AND SP3
- Segment f occurs at (SP5 OR Q5) AND SP3
- Segment g occurs at (SP2 OR Q2) AND SP5

In practice, segments b and f do not occur alone, and these can be simplified to (Q5 AND SP2) for segment b and (Q5 AND SP3) for segment f.

The circuit diagram for the timing is shown in Fig. 6. This is quite straightforward and needs little examination. Note that the line sync pulse clears Q2 and Q3, stopping the oscillator. This allows Q1 to start the oscillator again via IC55a at the same point in each line.

GATING

Having obtained the timing waveforms we must now gate the characters with them.

The order in which the characters are displayed is:

1. L.H. player to serve.
2. L.H. player most significant digit.
3. L.H. player least significant digit.
4. Space.
5. R.H. player most significant digit.
6. R.H. player least significant digit.
7. R.H. player to serve.

These signals are gated in turn to the character generation by a counter triggered by the oscillator Q2 and Q3. The circuit of the score counting, gating and character generation is shown in Fig. 5.

SCORE COUNTERS

The score is counted on the four decade counters IC37 to IC40 giving a two decade count for each player.

The outputs from each decade counter are gated in turn along with the serve indicators and the middle space to the seven segment decoder (IC46)

BOARD G SERVE/LOSE LOGIC

Integrated Circuits

| | |
|------|---------|
| IC32 | SN7410N |
| IC33 | SN7400N |
| IC34 | SN7410N |
| IC35 | SN7400N |
| IC36 | SN7490N |

BOARD H CHARACTER GENERATION

Resistors

| | |
|-----|------|
| R69 | 1kΩ |
| R70 | 1kΩ |
| R71 | 100Ω |
| R72 | 100Ω |
| R73 | 1kΩ |

Switch

S5 Single pole biased changeover

Integrated Circuits

| | |
|-----------|--------------------|
| IC37-IC40 | SN7490N (4 off) |
| IC41-IC44 | SN75151N (4 off) |
| IC45 | SN7493N |
| IC46 | SN7448N (not 7447) |
| IC47-IC49 | SN7412N (3 off) |
| IC50 | SN7404N |
| IC51 | SN7400N |

BOARD J TIMING

Resistors

| | |
|---------|--------------|
| R74-R84 | 1kΩ (11 off) |
| R85 | 2-2kΩ |
| R86 | 1kΩ |
| R87 | 2-2kΩ |
| R88 | 1kΩ |
| R89 | 2-2kΩ |

VR15-VR17 10kΩ (3 off) } skeleton
VR18-VR20 100kΩ (3 off) } presets

Capacitors

| | | | |
|-----|--------|-----|--------|
| C41 | 2200pF | C47 | 470pF |
| C42 | 1000pF | C48 | 470pF |
| C43 | 1000pF | C49 | 0-33μF |
| C44 | 0-22μF | C50 | 0-33μF |
| C45 | 0-1μF | C51 | 0-33μF |
| C46 | 0-1μF | | |

Diodes

D29-D39 1N914 (11 off)

Integrated Circuits

| | | | |
|-----------|----------|-----------|---------|
| IC52-IC54 | SN74123N | IC55-IC57 | SN7400N |
|-----------|----------|-----------|---------|

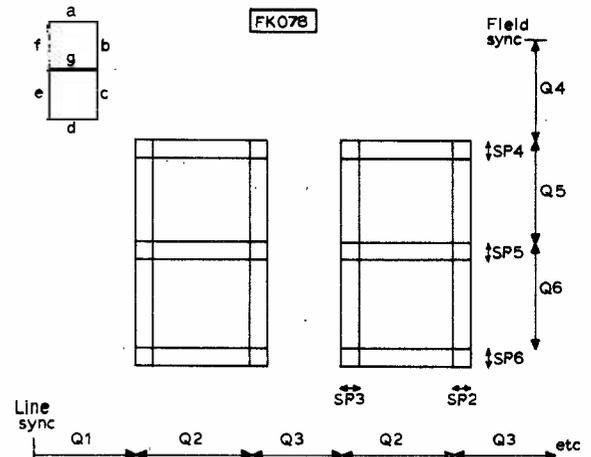


Fig. 4: An enlarged section of the score display which shows the timing of the various segments which go to make up the characters. The smaller character at top left shows the segment designation referred to in the text.

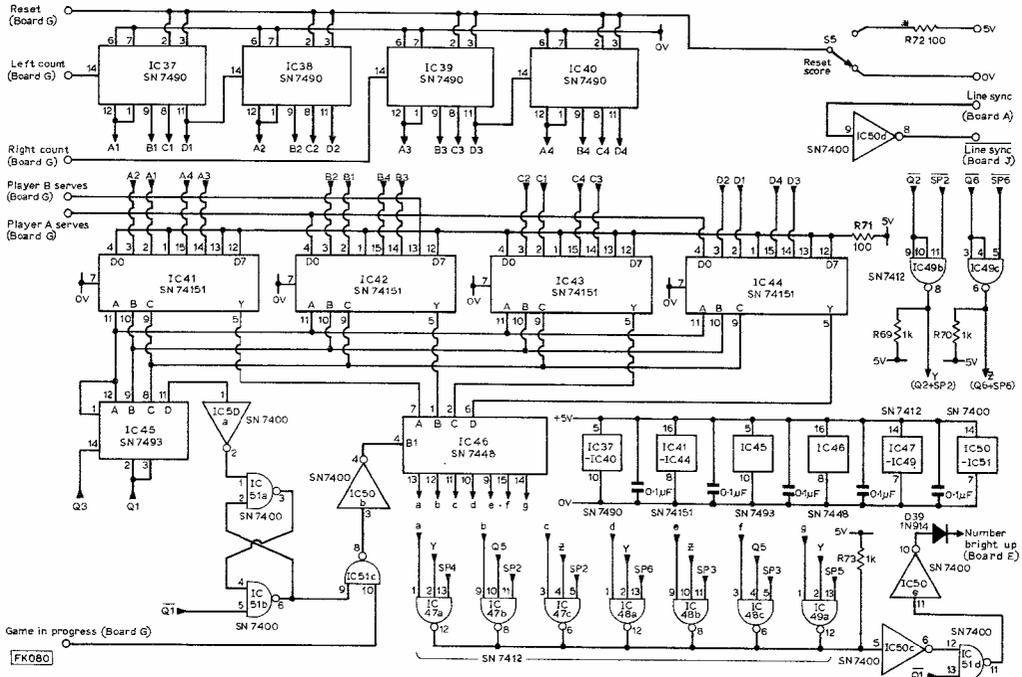


Fig. 5: Logic diagram of Board H, the character generation board. S5 is a new component which can be mounted on the front panel.

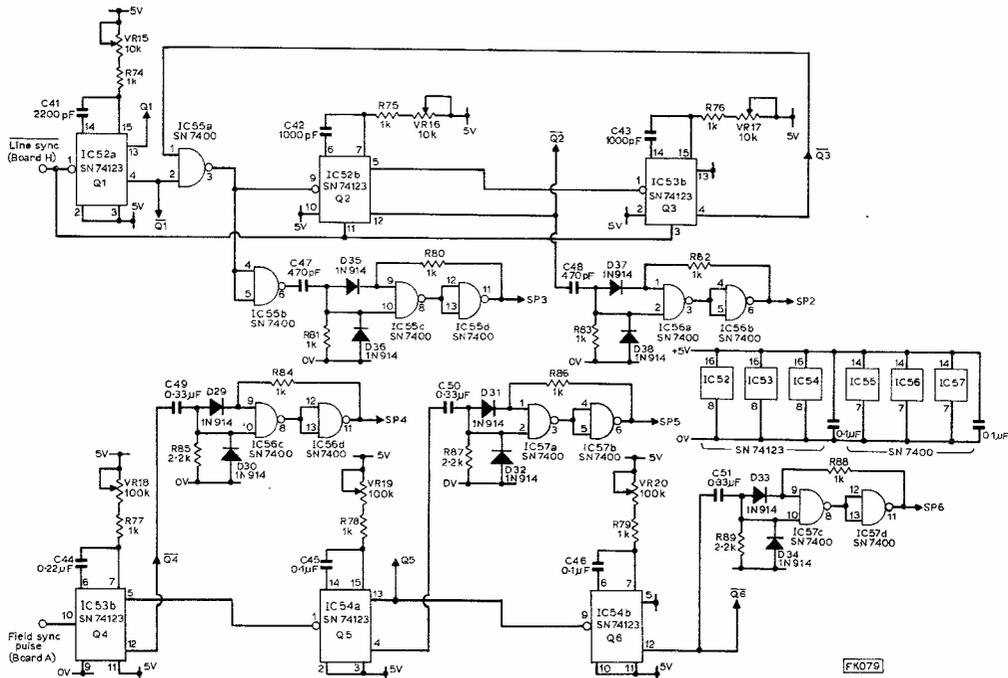


Fig. 6: Logic diagram of Board J which contains the timing logic.

by the four multiplexer circuits IC41 to IC44. The operation of the multiplexer circuits as follows.

Each IC has eight data inputs, labelled D0 to D7, three gate inputs labelled A, B and C, and two outputs labelled W and Y. The IC simply takes the binary address on A, B and C and gates the data on the corresponding input in true and complement forms to the outputs Y and W respectively.

Thus, for example, if A, B, and C are at 110 (binary 3, A being the least significant digit) the data on D3 will appear on output Y and its complement on output W.

If ABC are fed from a binary counter, each of the inputs in turn will be selected as the counter counts from 000 to 111.

In this application, four multiplexers are used to gate the four binary coded outputs from each decade counter to the seven segment decode matrix IC46. The sequencing is done by the four bit binary counter IC45. Only the first three digits are used for the selection, the fourth being used for display blanking as described later.

The counter is stepped at the end of Delay Q3, and is reset to zero at the start of each line by Delay Q1.

There are therefore seven segments for each character appearing in turn at the outputs of IC46.

All that is necessary now is to gate these with the timing pulses as described earlier.

The outputs from IC46 are positive going (unlike the conventional seven segment decoder) and can be gated by NAND gates. The gating is done by the open collector NANDs IC47, IC48 and IC49. The gating signals (Q2 or SP2) and (Q6 or SP6) required for segments a, c, d, e, and g are generated by IC49b and c. The picture will bright up if any of the seven outputs from the NAND goes to a 0. These are Wired-ORed together and the resulting signal inverted by IC50c to be fed to Board E for mixing with the other video signals.

CHARACTER SIZE

If the characters on the screen are made fairly small it is possible for the binary counter IC45 to reach full count and start again, giving a second score at the right hand side of the screen. To prevent this, after eight counts the bistable constructed of IC51a and b is set. This is used to inhibit the seven segment decoder via its blanking input. This bistable is reset at the start of each line by Q1.

Unfortunately the characters have to be displayed quite large in order to avoid the inherent flicker of horizontal lines on a random interlace system.

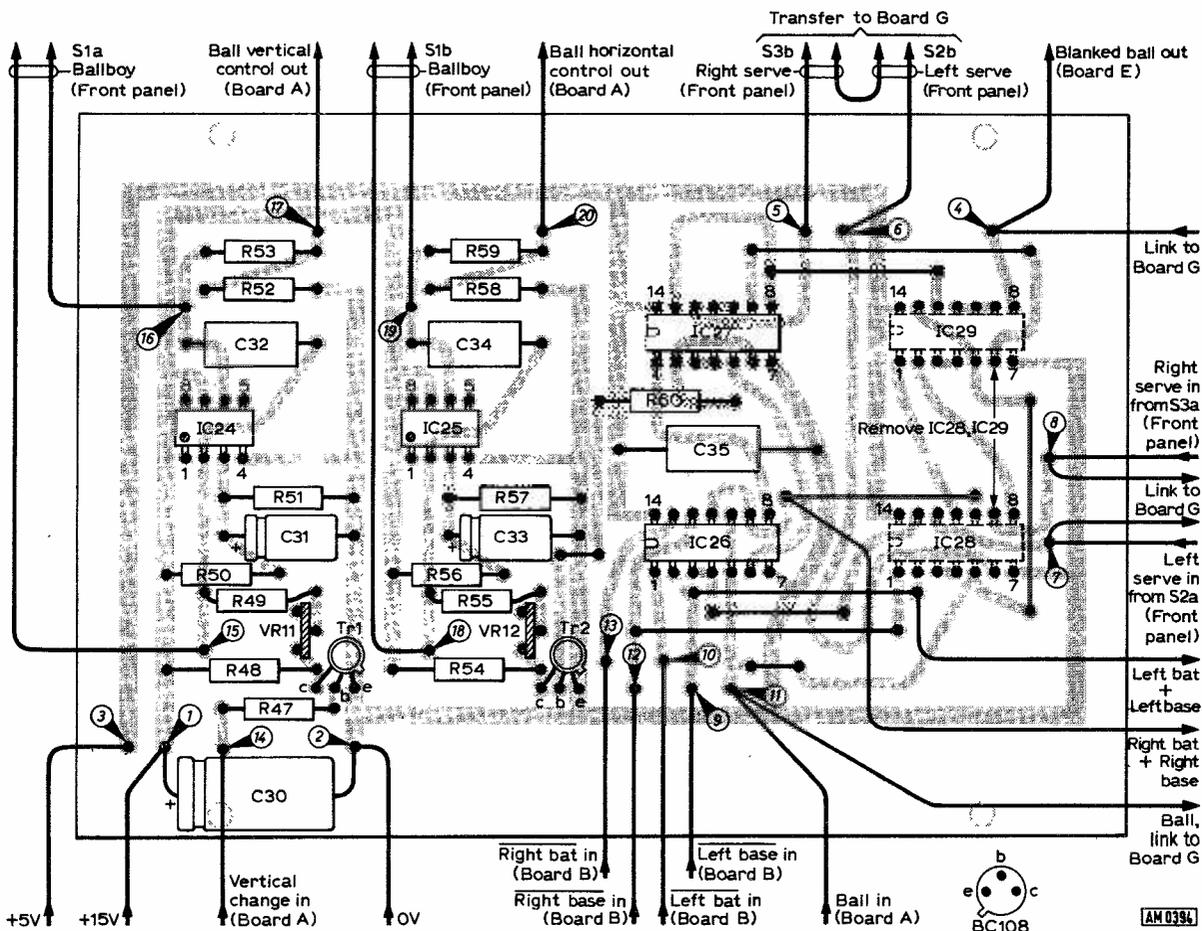


Fig. 7: Modifications to be made to the Board D in the original Tele Tennis unit.

This means that if the characters were left on during a game the screen would be rather cluttered. The "game in progress" signal on Board G is therefore used to blank the displays during the game.

Invalid codes are used to generate the serve indicators and the space between the two scores.

Decimal 10 (1010) generates the "left hand player to serve" signal in position D0; decimal 11 (1011) generates the "right hand player to serve", signal in position D6; decimal 15 (1111) generates a space in position D3 and in position D0 and D6 when the serve indicators are not lit.

The score counter is reset by the reset button. This also initialises the serve counter.

Because all the gates on Board J are utilised, the inversion of the line sync pulse required to fire Delay Q1 and clear Delays Q2 and Q3 on Board J is done by inverter IC50d on Board H.

SETTING UP

The interconnections between Boards H and J are straightforward and self-explanatory, as are the connections from Boards G and A to H and J.

The bright-up signal from Board H has to be or'ed with the other signals coming to Board E. This is done by adding an additional diode to D17-D23.

The additional diode (D39) is mounted on Board H, and is connected to the common junction of D17-D23. This is best done by removing R61, putting through pins in its two mounting holes and reconnecting R61 to the through pins. The lead from Board H can then be soldered neatly to the through pin at the junction of R61 and the diodes.

Setting up the displays is done as follows:

- (1) Set trim pots VR15-20 to mid positions.
- (2) Turn on the game. Press the reset score button.
- (3) Somewhere on the screen there should be a "player A to serve" and two zero symbols although they will probably be distorted and may even run off the sides of the screen.
- (4) Adjust VR15 (horizontal) and VR18 (vertical) to bring the display roughly to the middle.
- (5) Adjust VR16 and VR17 to give the required character width and gap respectively.
- (6) Serve the ball until one character shows the symbol for 2. Adjust VR19 and VR20 to give the required heights for the top and bottom halves.
- (7) Adjust VR15 and VR18 again to position the display as required.
- (8) Try playing the game. The display should go off during a game and come on when a player loses. After five serves the serve indicator should change sides.

The sizes of the lines that make up the characters are determined by C47 and C48 for the two vertical lines and C49, C50 and C51 for the three horizontal lines. The sizes of the lines can be increased or decreased by increasing or decreasing the size of the corresponding capacitor.

POWER SUPPLIES

The Tele Tennis game obtains its 5V supply from a 7805 regulator. This is rated at 600mA, and is not capable of driving both the game and the scoring. It is therefore necessary to improve this supply, add

another separate supply for the scoring or add a completely separate supply to drive both the game and the scoring.

Having two separate supplies for the game and the scoring logic is not good practice. Because logic signals pass between them there is a danger that some integrated circuits could be damaged if the two supplies differed by more than about 0.5V. The 7805 regulator has a tolerance of 0.25V so there could be 0.5V difference between two regulators. This difference could be increased during turn-off and turn-on as the supplies ramp up and down. It is not recommended that two supplies are used.

RS have recently introduced an uprated version of their MVR5V regulator. This is the RS309K which is rated at 1.2A. This is capable of supplying the needs of both the game and the scoring.

Fortunately this is pin compatible with the 7805 regulator although the heatsink originally fitted is not adequate. The recommended heatsink needs a thermal resistance of about 4°C/W. The regulator should therefore be mounted on to a suitable heatsink on the cabinet, and leads extended to it from Board F.

The transformer now needs to supply 12-15V at 1A. If a 0.5A transformer was fitted this will need changing.

The rectifier diodes D25-D28 are rated at 1A and are theoretically capable of handling the current needed. The author has had nasty experiences with rectifier diodes and likes to see them loaded at no more than half their rated current. Pessimists like myself should change them for 3A diodes such as 1N5401.

If it is intended to add any more modifications to the Tele Tennis, adding a substantial five volt supply to power the game should be considered now. This could be done either by using a higher power regulator such as the RS HPV regulator which will supply 2A or even purchasing a commercial fixed voltage power supply.

People who wish to design their own power supplies should be careful. You have probably spent a significant amount of money on TTL integrated circuits and commercial supplies have over-voltage protection and other features to look after your investment. Failures of logic power supplies can be very expensive.

It is recommended that at least one 0.1µF capacitor be used for decoupling every three integrated circuits.

PW


AVAILABLE NOW!
REPRINT OF PW's
TELE-TENNIS SERIES
July-November 74

Send 75p + 7p (post & packing) to: Chief Cashier
(PW Tele-Tennis), IPC Magazines, Tower House,
Southampton St., London, WC2E 9QX.

Miniature 2m EQUIPMENT

part 1: converter

W. H. Bond F.R.C.S. G3XGP

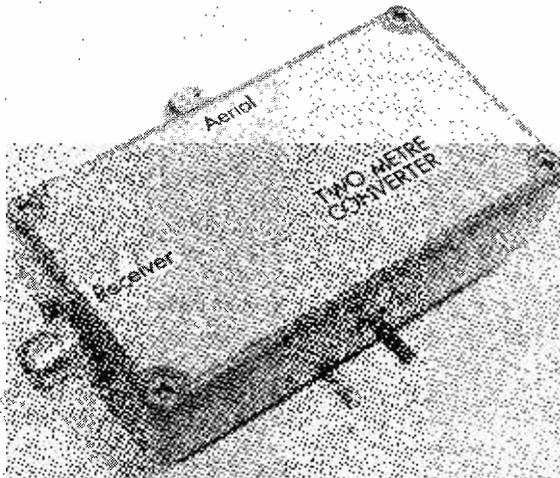

THIS 2m CONVERTER IS INTENDED TO BE USED WITH AN EXISTING HF BANDS RECEIVER. LATER WE SHALL DESCRIBE AN RF AMPLIFIER TO GO WITH IT, FOLLOWED BY A LOW POWER FM TRANSMITTER. ALL THREE UNITS ARE HOUSED IN SIMILAR SMALL DIECAST ALUMINIUM BOXES TO MAKE UP A COMPLETE STATION FOR THE 2m BAND.

THIS miniature converter is designed to complement the small transmitter to be described in PW, and has an output of 28-30MHz. This IF is chosen because of the peace and quiet on that band, requiring no input filter, and although the gain of most receivers falls at this frequency, the lack of breakthrough ensures a quiet band and a good S/N ratio. Construction is considerably eased

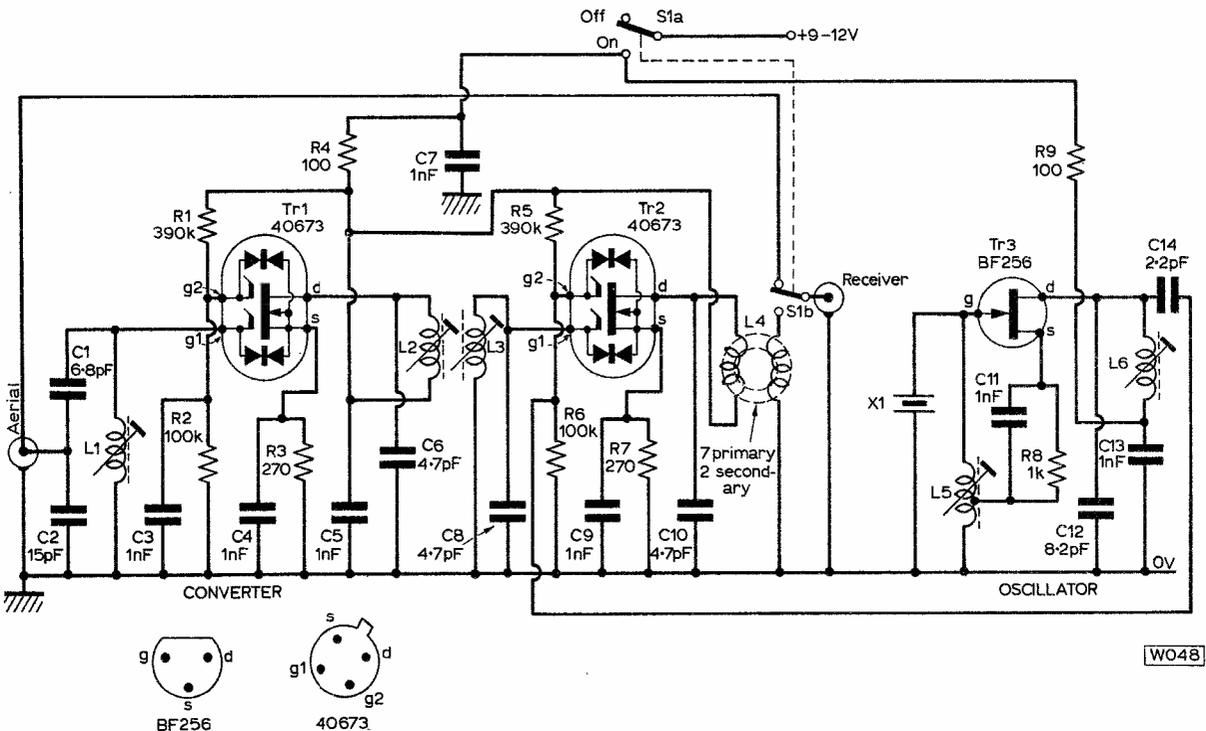


Fig. 1: The complete circuit diagram of the converter. The oscillator circuit uses a crystal on 116MHz for easy calibration, while the output from the converter is via a wideband toroidal transformer.

by the use of commercial coils of high Q and excellent stability; gate-protected MOSFETS simplify construction and the risk of damage in use is largely eliminated.

The crystal oscillator is unconventional and is the only part of the circuitry requiring any care in setting up. Results are comparable with other converters, the S/N ratio is good and it can be optimised by the adjustment of two resistors.

THE CIRCUIT

The circuit Fig. 1, follows modern popular practice, Tr1 being a gate-protected MOSFET which has internal zener diodes to protect against static from handling and from any excessive RF applied during use. The double channels isolate input and output circuits to give excellent separation so that neutralization is not required. These circuits are tuned by L1 and L2 respectively. To avoid the need for a tap on the input coil L1, C1 and C2 provide a match for a 50 to 75Ω aerial. Further tuning is



Fig. 2: Full size drawing of the printed circuit board viewed from the underside. Owing to its small size, considerable care should be taken in the drawing and etching of this board.

achieved by the slug in L1. L1 also provides a DC return for gate 1 of Tr1, forward bias for the second gate being provided by R1 and R2, decoupled by C3.

The channel current of Tr1 is controlled by R3 with C4 as bypass, and since the channel current varies the S/N ratio, R3 may be varied to suit the characteristics of the particular MOSFET employed. The drain load of Tr1 is L2 and C6, the whole of the RF input stage being decoupled by R4 and C5. L2 is inductively coupled to L3 and C8, while L3 provides a DC return for gate 1 of Tr2. Gate 2 of Tr2 is forward biased by R5 and R6 and receives the oscillator injection voltage via C14 at 116MHz. This gives the required mixer product of 28-30MHz from the drain load of L4, broadly tuned to these frequencies by C10. The channel current of Tr2 is controlled by R7, bypassed by C9 and some control of mixer noise is available by variation in the value of R7. C7 serves to decouple the whole circuit.

OSCILLATOR

The oscillator circuit is unusual, in as much as the high frequency crystal employed requires an inductance to tune out the capacity of the crystal and its mounting. This same inductance, connected in parallel with the coil, is employed in a Hartley circuit to supply the necessary feedback to maintain oscillation. The crystal is connected between earth

★ components list

| Resistors | |
|-----------|----------------------|
| R1 390kΩ | R6 100kΩ |
| R2 100kΩ | R7 270Ω |
| R3 270kΩ | R8 1kΩ |
| R4 100Ω | R9 100Ω |
| R5 390kΩ | All resistors 10% ½W |

| Capacitors | |
|------------|-----------|
| C1 6.8pF | C8 4.7pF |
| C2 15pF | C9 1nF |
| C3 1nF | C10 4.7pF |
| C4 1nF | C11 1nF |
| C5 1nF | C12 8.2pF |
| C6 4.7pF | C13 1nF |
| C7 1nF | C14 2.2pF |

| Semiconductors | |
|----------------|-----------|
| Tr1 40673 | Tr3 BF256 |
| Tr2 40673 | |

| Miscellaneous | |
|--|--|
| L1, L2, L3 and L6, MC6S Toko coils, type 503HS 04BY5A (4½ turns). L5, S18 Toko coil 4½ turns tapped at 2½ turns. L4, Toroid core type CR0718A. Coils and core available from Ambient International, 37 High St., Brentwood, Essex, CM14 4RH. Eddy-stone diecast box 115 x 64 x 32mm (4½ x 2½ x 1¼ in.) type 7134P. 2 Coax sockets. Stand-off bushes. DPDT switch. 116MHz crystal, type HC18/U, available from PM Electronic Services, 7A Arrows Park Road, Upton, Wirral, Merseyside L49 0JB. Fibre glass PCB, 41 x 34mm (1½ x 1¼ in.) | |


and gate of Tr3, which is in parallel with L5 tapped to provide feedback from the emitter. R8 limits current flow through the oscillator, by-passed by C11 with neutralization of the crystal capacity obtained by careful adjustment of L5. The output from the oscillator is taken from the drain, the load being L6 tuned by C12 and the slug in the coil. C12 also decouples to earth, with the output being passed to the second gate of the mixer through C14.

The circuit is designed for operation between 9 and 12V without zener stabilization. These circuit facts, together with the additional capacity across the crystal, result in slightly inaccurate frequencies although the error should not be more than 15kHz. For average amateur use such an error is immaterial.

CONSTRUCTION

The circuit is made on a printed circuit board and the technique of preparation is worth repeating. Using Fig. 2, make a tracing, stick it to a suitable piece of single sided copperclad board and dot punch each of the component mounting holes. Drill each point with a No. 60 drill and file off the burrs on each side. Following Fig. 2, link the holes using either a Dalo pen or a Staedtler Permawriter making the gaps between the copper lands as narrow as possible. Etch in ferric chloride or ammonium persulphate and common salt (much cleaner), both slightly warmed. When completed, remove the etch resistant with Brillo or steel wool. Examine with a magnifying glass and remove any excess copper remaining between lands.

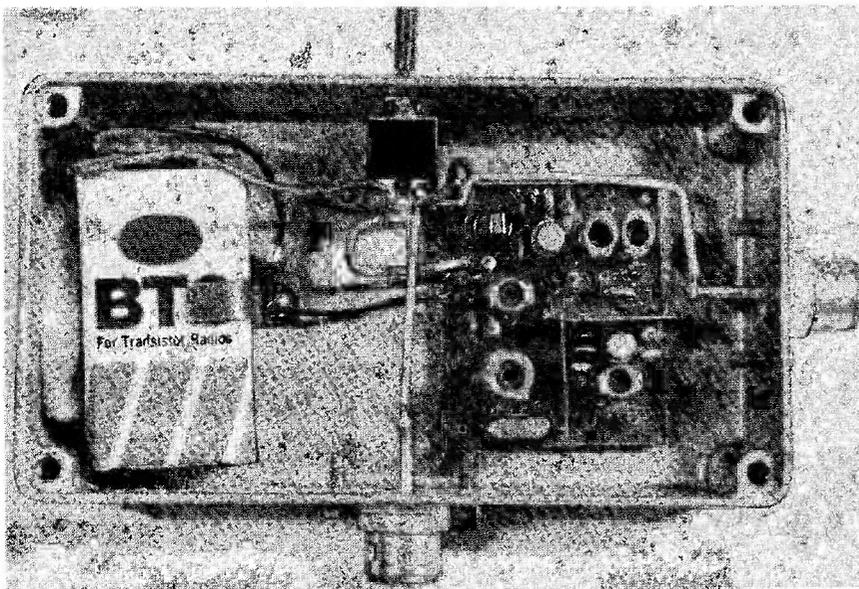
Construction is considerably simplified by the use of suitable Toko coils and only the output toroid need be wound, (7 turns primary, 2 turns secondary



Interior view of the unit, showing position of PCB in relation to the coaxial sockets and double pole switch. Notice the screening around the input stage of the converter. This can be constructed from 20SWG tinplate and soldered to pins in the board and earthed.

of about 22SWG copper wire), taking care the windings terminate over the PCB connections. Because of the small spacing of components on the recommended circuit board, start at the centre and work outwards making all component leads as short as possible and mounting the coils and screen last of all. Omit R9 until the oscillator has been placed on frequency.

10mA. Adjust L3 and L2 for maximum current. Connect the aerial to the input, or, alternatively, supply a 144-146MHz signal from a signal generator, and adjust L1. Meanwhile, feed the output into a receiver tuned to 28-30MHz, looking for maximum gain, and readjusting all three coils approximately. After acquaintance with the unit it is worth while altering the values of R3 and R7 to obtain the best signal-to-noise ratio.

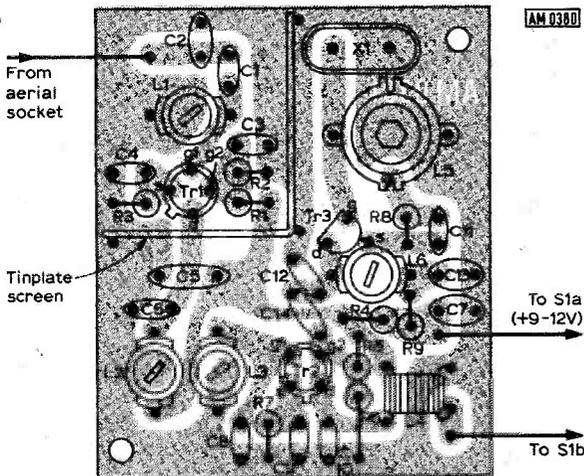

Component side view of the PCB, shown approximately 1½ times actual size. For components to fit the hole spacings correctly, the leads should be kept as short as possible.

SETTING UP

The omission of R9 allows the oscillator to be put on to frequency without energizing the converter. Give the oscillator a power supply by temporarily connecting 9 to 12V via a milliammeter to the C12 end of R9, and adjust L5 and L6 for minimum current. A frequency meter makes this adjustment easy, but failing this an RF 'sniffer' placed near L6 will show maximum output and the milliammeter minimum current, when the coils are correctly adjusted. Now insert R9 and connect power to the correct point; the consumption should be

CONCLUSIONS

As a straightforward converter to 28-30MHz this very small unit gives excellent results with a 9 to 12V supply, the optimum behaviour depending on adjustment of the voltage supply or the two emitter resistors R3 and R7.


Although this converter contains an expensive crystal it is easy to construct and adjust, and is further enhanced by the quiet IF selected and the certainty that, using commercial coils, only minor adjustment is required for satisfactory operation.

THE SECOND ARTICLE IN THIS SERIES WILL BE PUBLISHED IN THE OCTOBER ISSUE AND WILL DESCRIBE THE CONSTRUCTION OF A 2m PRE-AMPLIFIER.

points arising...

PW TEXAN II AMPLIFIER JULY 1975

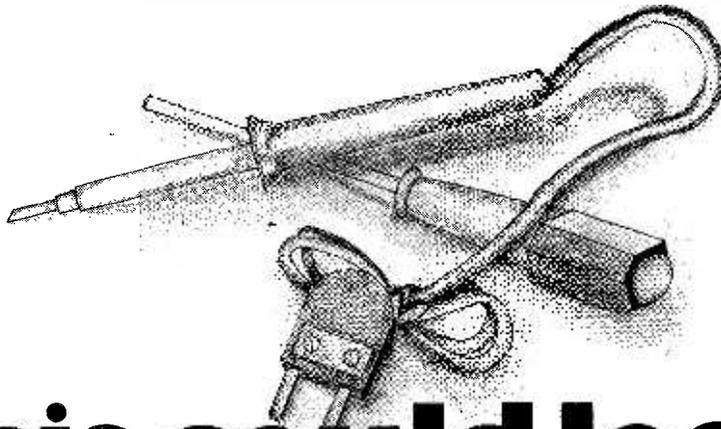p202. In Fig. 10, R41 should be R42 and R42 should be R41. Accordingly in the components list R41 should be 15kΩ and R42 should be 100kΩ. The changes apply to the other channel resistors as well. The buffer stages will work but not as well as intended. Briefly, for those who have made the modifications, change over the 15kΩ and 100kΩ resistors.



This could lead to something big.

A soldering iron and a screw driver. If you know how to use them, or at least know one end from the other, you know enough to enrol in our unique home electronics course.

This new style course will enable anyone to have a real understanding of electronics by a modern, practical and visual method. No previous knowledge is required, no maths, and an absolute minimum of theory.


You build, see and learn as, step by step, we take you through all the fundamentals of electronics and show you

how easily the subject can be mastered and add a new dimension not only to your hobby but also to your earning capacity.

This course is accepted by and used in a large number of schools and colleges and forms an invaluable grounding for professional training in the subject. All the training is planned to be carried out in the comfort of your own home and work in your own time. You send them in when you are ready and not before. These culminate in a final test and a certificate of success.

1

Build an oscilloscope.

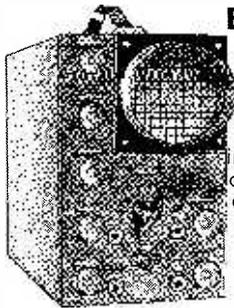

As the first stage of your training, you actually build your own Cathode ray oscilloscope! This is no toy, but a professional test instrument that you will need not only for the course's practical experiments, but also later if you decide to develop your knowledge and enter the profession. It remains your property and represents a very large saving over buying a similar piece of essential equipment.

2



Read, draw and understand circuit diagrams.

In a short time you will be able to read and draw circuit diagrams, understand the very fundamentals of television, radio, computers and countless other electronic devices and their servicing procedures.

3



Carry out over 40 experiments on basic circuits.

We show you how to conduct experiments on a wide variety of different circuits and turn the information gained into a working knowledge of testing, servicing and maintaining all types of electronic equipment, radio, t.v. etc.

PLUS



FREE GIFT!

ALL STUDENTS ENROLLING IN OUR COURSES RECEIVE A FREE CIRCUIT BOARD ORIGINATING FROM A COMPUTER AND CONTAINING MANY DIFFERENT COMPONENTS THAT CAN BE USED IN EXPERIMENTS AND PROVIDE AN EXCELLENT EXAMPLE OF CURRENT ELECTRONIC PRACTICE


To find out more about how to learn electronics in a new, exciting and absorbing way, just clip the coupon for a free colour brochure and full details of enrolment.

Brochure without obligation to:
BRITISH NATIONAL RADIO & ELECTRONICS SCHOOL, Dept WL/95
P.O. Box 156, Jersey, Channel Islands.

NAME.....

ADDRESS.....

(Block caps please)

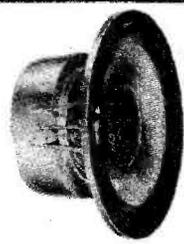

WILMSLOW AUDIO

THE Firm for speakers!

SPEAKERS

| | |
|---|--------|
| Baker Group 25 3, 8 or 15 ohm | £8-64 |
| Baker Group 35 3, 8 or 15 ohm | £10-25 |
| Baker Group 50/12 8 or 15 ohm | £14-00 |
| Baker Deluxe 12" d/cone | £13-75 |
| Baker Major | £11-87 |
| Baker Repeat | £10-00 |
| Baker Superb | £8-12 |
| Baker Auditorium 12 | £16-25 |
| Celestion MH1000 horn, 8 or 15 ohm | £10-95 |
| Celestion PS6 for Unilux | £3-75 |
| Celestion G12M 8 or 15 ohm | £12-00 |
| Celestion G12H 8 or 15 ohm | £15-00 |
| Celestion G15C 8 or 15 ohm | £24-00 |
| Celestion G18C 8 or 15 ohm | £33-00 |
| EMI 13 x 8" 150 d/c 8 ohm | £2-84 |
| EMI 13 x 8" type 350 8 or 15 ohm | £9-55 |
| EMI 13 x 8" 20 watt base | £7-69 |
| EMI 6 1/2" 83850 4 or 8 ohm | £4-37 |
| EMI 8 x 5 d/cone, roll surr 10 watt | £3-44 |
| EMI 2 1/2" tweeter 97492AT | £7-77 |
| Eagle DT33 30 watt tweeter | £6-31 |
| Eagle CT15 horn tweeter | £4-49 |
| Eagle CT5 cone tweeter | £2-06 |
| Eagle CT10 tweeter 8 or 16 ohm | £3-00 |
| Eagle MHT10 horn tweeter | £4-44 |
| Eagle crossover CN23, CN28, CN216 | £1-75 |
| Eagle FR4 | £6-12 |
| Eagle FR5 | £9-12 |
| Eagle FR9 | £12-31 |
| Eiac 9 x 5, 59RM109 15 ohm, 59RM114 8 ohm | £3-44 |
| Eiac 6 1/2" 6RM171 d/c roll surr. | £4-08 |
| Eiac 6 1/2" 6RM220 d/cone | £3-12 |
| Eiac 4" tweeter TV4 | £1-75 |
| Eiac 10" d/cone 10RM239 8 ohm | £3-12 |
| Eiac 8" 8CS175 3 ohm | £2-87 |
| Fane Pop 15 watt 12" | £5-25 |
| Fane Pop 25/25 watt 12" | £7-50 |
| Fane Pop 50 watt 12" | £12-00 |
| Fane Pop 55 60 watt 12" | £12-95 |
| Fane Pop 60 watt 15" | £13-75 |
| Fane Pop 100 watt 18" | £25-95 |
| Fane Crescendo 12A 100 watt 12" | £34-50 |
| Fane Crescendo 12B bass | £36-50 |
| Fane Crescendo 100 watt 15" | £47-50 |
| Fane Crescendo 150 watt 18" | £62-95 |
| Fane 801T 8" d/c roll surr. | £8-12 |
| Fane 807T 8" d/c roll surr. | £4-62 |
| Fane 808T 8" d/c | £3-44 |
| Fane 701 twin ribbon horn | £40-00 |
| Fane 910 horn | £14-95 |
| Fane 920 horn | £33-95 |
| Goodmans 8P 8" or 15 ohm | £5-50 |
| Goodmans 10P 8 or 15 ohm | £5-80 |
| Goodmans 12P 8 or 15 ohm | £13-95 |
| Goodmans 12P-D 8 or 15 ohm | £16-95 |

| | |
|--|--------|
| Goodmans 12P-G 8 or 15 ohm | £15-95 |
| Goodmans Audiomax 12AX 100 watt | £36-90 |
| Goodmans Audiomax 15AX | £49-25 |
| Goodmans 15P 8 or 15 ohm | £21-00 |
| Goodmans 18P 8 or 15 ohm | £36-00 |
| Goodmans Hixax 750 | £16-00 |
| Goodmans Axent 100 tweeter | £3-44 |
| Goodmans Audiom 100 12" | £13-90 |
| Goodmans Axiom 401 12" | £20-00 |
| Goodmans Twinaxiom 8" | £10-14 |
| Goodmans Twinaxiom 10" | £10-75 |
| Kef T27 | £6-06 |
| Kef T15 | £6-94 |
| Kef B110 | £8-37 |
| Kef B200 | £9-50 |
| Kef B139 | £16-50 |
| Kef DN8 | £2-31 |
| Kef DN12 | £5-75 |
| Kef DN13 | £3-87 |
| STC4001G super tweeter | £6-56 |
| Richard Allan CG8T 8" d/c r/surr. | £7-37 |
| 2 1/2" 64 ohm, 70mm 80 ohm, 70mm 8 ohm | 77 |
| 2 1/2" 75 ohm | 55 |
| 7" x 4" 3 or 8 ohm | £1-65 |
| 8" x 5" 3 or 8 ohm | £1-75 |
| 10" x 6" 3, 8 or 15 ohm | £2-69 |

SPEAKER KITS

| | |
|----------------------------|-------------|
| Baker Major Module | each £13-44 |
| Goodmans Mezo Twinkit | pair £47-19 |
| Goodmans DIN 20 | each £13-44 |
| Helme XLK 25 | pair £25-44 |
| Helme XLK 30 | pair £17-19 |
| Helme XLK 50 | pair £46-25 |
| Kem 1 | pair £48-44 |
| Kem 1 1/2 | each £42-50 |
| Richard Allan Twinkit | each £10-37 |
| Richard Allan Triple 8 | each £15-94 |
| Richard Allan Triple 12 | each £23-15 |
| Richard Allan Super Triple | each £27-50 |
| Wharfedale Linton 2 kit | pair £23-12 |
| Wharfedale Glendale 3 kit | pair £40-60 |
| Wharfedale Dovedale 3 kit | pair £53-12 |

PA/DISCO AMPLIFIERS

| | |
|-----------------------|--------|
| (carr. and ins. £1) | |
| Baker Major 100 watt | £87-25 |
| Linear 30/40 | £30-00 |
| Linear 40/60 | £35-00 |
| Linear 80/100 | £58-95 |
| Linear 100 watt slave | £44-00 |

Eagle PA range in stock—ask for catalogue.

Free with speaker orders over £7—

"Hi-Fi Loudspeaker Enclosures" book. All units guaranteed new and perfect. Prompt despatch. Carriage and packing: speakers 38p each, 12" and up 50p each. Speaker kits 75p each (£1.50 pair) tweeters and crossovers 25p.

Including V.A.T. 25% on Hi Fi, 8% on PRO and PA

WILMSLOW AUDIO (Dept. PW)

Loudspeakers: Swan Works, Bank Square, Wilmslow, Cheshire. SK9 1HF
Discount Radio, PA, Hi-Fi: 10 Swan Street, Wilmslow
Send stamp for free booklet "Choosing a Speaker"



Agfa Cassettes

The best buy!

| | |
|---|----------------------|
| Agfa Low Noise Cassettes | |
| AT LESS THAN HALF PRICE! | |
| C80 | 1 40p £2-00 £3-88 |
| C90 | 1 44p £2-70 £5-38 |
| C120 | 1 75p £3-70 £7-38 |
| AGFA HIGH DYNAMIC SUPER | |
| C80+6 | 1 54p £2-70 £6-35 |
| C90+6 | 1 70p £3-50 £7-35 |
| C120 | 1 89p £4-95 £9-85 |
| AGFA STEREO-CHROM CHROMIUM DIOXIDE | |
| C80 | 1 90p £4-50 £8-75 |
| C90 | 1 £1-10 £5-50 £10-90 |

SAME DAY DESPATCH. P. & P. 15p per order

WILMSLOW AUDIO
(DEPT. PW)
10 SWAN STREET, WILMSLOW,
CHESHIRE, SK9 1HF

Cut-price prerecorded cassettes—send stamp for list

SINCLAIR

IC20

IC20 10+10W stereo amplifier with free booklet and printed circuit £6-59 (£1-90)
PZ20 power supply kit for above £4-45 (£1-46)
VP20 stereo volume, tone control and preamp kit £4-95 (£1-81)

AMPLIFIERS

SEND SAE FOR FREE DATA BOOKLET

SINCLAIR CALCULATORS



Scientific calculator assembled £15-44 (£1-51)
Cambridge calculator assembled £10-07 (£1-13)
Cambridge memory assembled £10-81 (£1-14)
Oxford 100 £10-50 (£1-20), Oxford 200 £15-95 (£1-70), Oxford 300 £23-95 (£2-40)
CALCULATOR POWER SUPPLIES
Mains adaptor for Oxford series £2-65 (£1-04)
Mains power unit for Cambridge, Cambridge Mem. and Scientific calcs £3-60 (£1-30)

FERRANTI ZN414

IC radio chip with data £1-20 (49p). Also available kit of extra parts to complete a radio £2-55 (83p) Send see for free leaflet

SINCLAIR PROJECT 80

A FU £6-38 (£1-93)
Z40 £4-97 (£1-58)
Z60 £6-38 (£1-93)
Q16 £5-70 (£2-17)
PZ5 £4-82 (£1-59)
PZ6 £7-41 (£2-28)
PZ8 £7-25 (£2-20)
Decoder £7-46 (£2-23), Trans for PZ8 £3-75 (£1-41), Tuner £11-43 (£3-48), Stereo 80 £11-43 (£3-48), Project 805 £29-95 (£8-27), Project 805SQ £38-95 (£9-70), Project 80 SQ Quad Decoder £16-50 (£4-47), Stereo 80/2 Z40/PZ5 £24-40 (£6-69), Stereo 80/2 Z40/PZ6 £26-70 (£7-37), Stereo 80/2 Z60/PZ8 £28-66 (£7-91)



SINCLAIR IC12

With 44 page booklet and printed circuit £3 (£1-08)



DELUXE KIT FOR THE IC12

Includes all parts for the printed circuit and volume, bass and treble controls needed to complete the mono version £1-80 (64p), Stereo model with balance control £3-90 (£1-16).

IC12 POWER KIT

Supplies 28V 0.5 Amps £3-27 (£1-44).

PREAMP KITS FOR THE IC12

Type 1 for magnetic pickups, mics and tuners. Mono model £1-50 (57p), Stereo model £2-70 (86p)
Type 2 for ceramic or crystal pickups. Mono 80p (39p), Stereo £1-60 (59p).

SEND SAE FOR FREE LEAFLET ON KITS

BATTERY ELIMINATOR BARGAINS

The most versatile battery eliminator ever offered. Switched output of 3, 4, 5, 7, 9 and 12V at 500 mA £3-90 (£1-55)
Other eliminators stocked:—
250mA—3 way switched model 6/7/9V £2-50 (£1-05)
500mA—8V £2-75 (£1-11), 9V £2-75 (£1-11), 7.1V cassette type £3-35 (£1-28), Double 4+4.1V £3-20 (£1-23), 6+6V £3-20 (£1-23), 9+9V £3-20 (£1-23),
500mA:— Heavy duty models 6V £3-60 (£1-30), 7.1V £3-60 (£1-30), 9V £3-60 (£1-30).




S-DECS AND T-DECS

S-DeC £1-98 (36p)
T-DeC £3-63 (52p)
M-DeC A £3-99 (58p)
M-DeC B £6-99 (86p)

IC carriers—

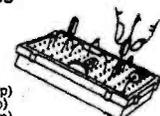16 dit: plain 99p (19p)
With socket £1-82 (26p)
10 TO5: plain 99p (19p)
With socket £1-80 (26p)



SWANLEY ELECTRONICS

PO BOX 68, SWANLEY,
KENT BR8 8TQ.

Please add the sum shown in brackets after the price to cover the cost of post and V.A.T. Official credit orders from schools etc welcome. No V.A.T. charged on overseas orders. All prices are special offers ending 14th Sept.

EXPERIMENTAL WORKSHOP

M. J. HUGHES
M.A., C.Eng., MIERE.

LEARNING BY PRACTICAL PROJECT STEPS

PART 16—TRF RADIO RECEIVERS

WHEN a radio signal is transmitted it comprises what is called a "carrier" on which is superimposed the audio signals we wish to receive. The carrier can be one of a vast range of frequencies which cover the radio frequency spectrum from a hundred kilohertz to several hundred megahertz. The audio frequency signals are superimposed on the carrier by a process known as "modulation" and there are several forms. The oldest form is AMPLITUDE MODULATION (AM). As its name suggests the audio frequencies are used to make the carrier's amplitude vary in exact relationship to the amplitude of the audio signal, as shown in Fig. 112.

All frequencies are suitable for amplitude modulation but generally speaking we think of the long, medium and short waves as being the primary domain for AM. Within the same bands there are other modes of modulation which are used for specific commercial or technical reasons. For example, most amateurs using telephony now operate on SSB (single sideband) as this enables them to radiate power more efficiently while, at the same time, using only half the bandwidth. However, SSB is still only another form of AM.

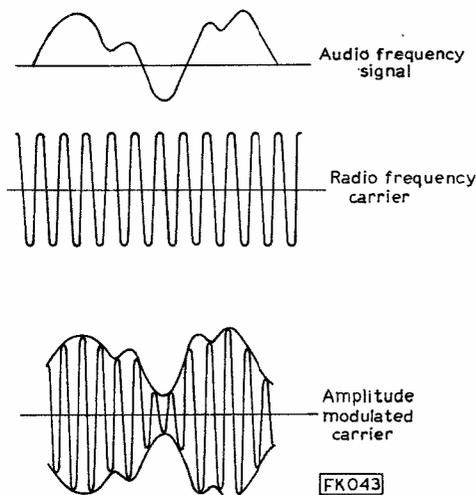


Fig. 112: Formation of an amplitude modulated (AM) signal from audio and RF sources.

Facsimile transmission of photographs and weather maps is carried out on the short waves using a process resembling FREQUENCY MODULATION (FM) although not in its normal form. We normally associate FM with the VHF bands, ranging from about 80MHz and upwards in frequency. With frequency modulation the carrier is modulated by shifting its frequency up and down in proportion to the amplitude of the audio signal impressed upon it. It should be clear that when frequency modulation is applied to a carrier the receiver has got to be capable of receiving a range of frequencies when it is tuned in, the maximum positive and negative-going excursions of the frequency being set by the maximum amplitude of the audio signals. Therefore the receiver has to have a certain bandwidth centred on the nominal frequency of the carrier. Although this seems obvious for FM signals the same argument applies to the reception of amplitude modulated signals, but the reason is not quite so obvious.

When a signal is amplitude modulated the carrier is modified to become (1) sum of the carrier plus the frequency of the audio signal and (2) difference between the carrier and the audio frequency, plus (3) carrier frequency. Thus if a carrier frequency of 1,000,000Hz is used to carry an audio tone of 1,000Hz the frequencies transmitted would be 1,001,000Hz and 999,000Hz, plus the original carrier. These extra signals are called the upper and lower sidebands. The frequencies of the sidebands depend on the frequencies of the audio signals but one can limit the excursion of these sidebands by preventing audio signals greater than a certain frequency reaching the modulator.

On the medium waveband the width of the sidebands becomes critical in so far as they might cause one station to overlap another, so the more one limits the frequency range of the audio signal the more stations, theoretically, can be accommodated in a particular waveband. This is one of the reasons why one does not expect the same high-frequency response from a station received on the medium waveband as one received on FM at VHF where, at present, there is less problem with station crowding and a wider bandwidth can be used.

We can experiment with a straightforward medium wave transistor portable radio to experience the presence of the sidebands. Try tuning in a station,

making sure to obtain the best setting of the dial to give a good quality signal. Now very gently offset the tuning upscale and downscale. Notice that the sound quality becomes more shrill as it loses its bass frequencies. This is simply moving the tuning of the receiver to pick up the higher frequency sidebands, at the expense of the lower frequencies which are nearer to the carrier and consequently move out of the bandwidth of the radio.

Clearly a radio receiver MUST have a bandwidth that allows the reception of the carrier as well as the maximum excursions of the sidebands, for every setting of the dial, if we wish to get the best quality signal. A receiver having too narrow a pass-band will cause high frequency audio signals to be lost, even on tune but, on the other hand, a receiver having too wide a pass-band will suffer from interference from stations on adjacent channels.

We have dived into the deep end of this kind of explanation although all we are going to describe are a few experiments on T-Dec. The answer is, simply, that the bandwidth of tuned circuits is most important and we hope to instil a better appreciation of how good quality tuned circuits and good matching can make or mar a radio receiver.

We shall limit ourselves to receiving amplitude modulated signals on the medium waveband, approximately 525kHz to 1.605MHz. The signal transmitted from the broadcasting station is broadly described as an electromagnetic wave. To be more precise, there are two signals radiated by a transmitter, one is rather like a magnetic field which can induce small currents in coils wound on ferrite rod aeriels and the other is an electrostatic field which needs a long wire aerial or a dipole for reception. One signal always goes with the other but the range of the electrostatic signal is usually greater.

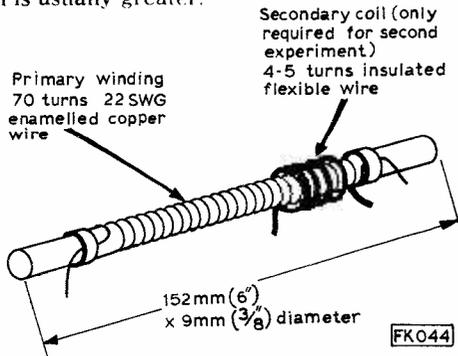


Fig. 113: Construction of aerial coil on ferrite rod, used in experiments shown here.

In practice most modern transistor radios embody ferrite rod aeriels and operate by picking up the magnetic field; usually we are only interested in receiving local stations on the medium waves. Because of this we shall use a ferrite rod, Fig. 113, aerial for all our experiments this month. When winding this make sure that the turns are tight and try to separate one turn from the next by about the thickness of the wire. Sellotape can be used to hold the ends of the wire in place.

If this coil is placed with its axis perpendicular to the line between the receiver and a transmitter the radiated magnetic field, oscillating at the carrier frequency, will induce small voltages across the windings, just like a transformer in which the secondary has been moved away from the primary.

Obviously the induced voltages are going to be very small indeed, in reality a microvolt or two. More important is the fact that ANY radio stations lying on the right line will induce voltages irrespective of the frequency. A transformer will operate, in theory, with any frequency of input voltage if one ignores problems involving power dissipation. Off the perpendicular line the induced voltages will be lower.

If we place a capacitor in parallel with the coil we alter the state of affairs significantly by making a frequency selective, or tuned, circuit. The impedance of the parallel circuit becomes low for all except one particular frequency, the resonant frequency, given by $f = \frac{1}{2\pi\sqrt{LC}}$. The impedance of the circuit rises to a maximum value depending on

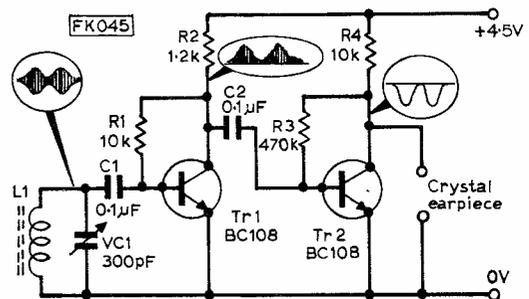


Fig. 114: First experiment, demonstrating effect of loading on coil Q.

the Q, or efficiency, of the coil. The higher the Q the sharper will be this tuning.

There are two main factors which control the Q of a coil. One, which we can do very little about, is the internal resistance of the coil itself. This should be as low as possible for maximum Q, hence the use of reasonably thick 22 SWG wire. The second factor is the effect of parallel resistance across the tuned circuit, which is directly influenced by connecting into another stage. This latter effect is something we definitely can control.

The first two experiments demonstrate very effectively the effect of loading on the Q of the tuned circuit. Use the coil to make up the circuit of Fig. 114 on T-Dec, Fig. 115. The tuned circuit is connected via C1 to the relatively low input impedance stage of Tr1 which is operating as a detect-


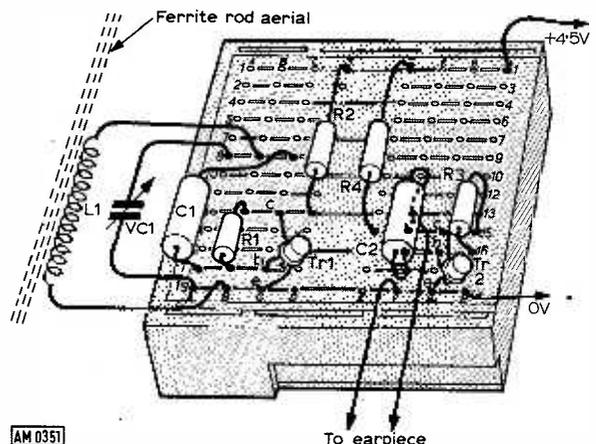
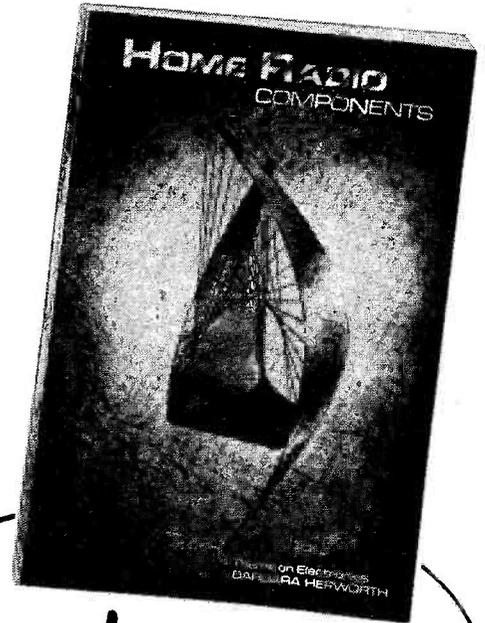


Fig. 115: Arrangement of Fig. 114 on T-Dec.

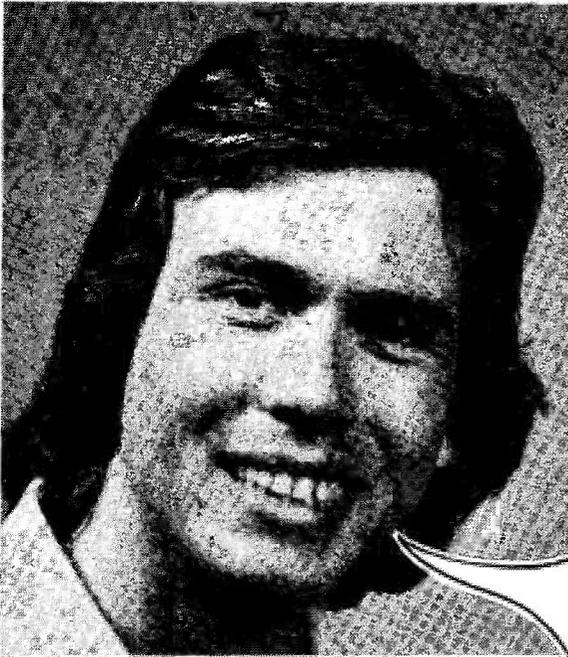

*It's the
LONG LIFE!
Catalogue.*

You have heard of "Long Life" batteries, milk and beer, so why not a "Long Life" catalogue? The thought struck me the other night when I visited a friend to chat about a joint project we were building. We needed a few bits and pieces, so he went to a drawer and pulled out a catalogue. Yes, it was the famous Home Radio Components catalogue alright, but at first I didn't recognise it. "Gracious! How old is it?" I exclaimed. "Oh" he said, "about 5 or 6 years". Fascinated, I said "Can you still use it? Surely, it's years out of date?". "No, not really" he said, "you see many basic things like plugs, sockets, resistors, capacitors, switches, don't change much. Only the prices change, and Home Radio were wise enough to take all prices out of their catalogue many years ago and put them on a separate list. What's more, they were far sighted enough not to change their catalogue numbers, so all I have to do is to write or phone them occasionally and 'hey presto' along comes an up to date price list. Not a penny extra to pay!" "You really believe in getting your money's worth out of a catalogue" I said. "Sure thing" he replied, "but I might have bought four or five catalogues and still not ordered any more goods. These catalogues must cost Home Radio a bomb to produce, so I imagine they are quite pleased if one of their catalogues produces business for say two years or more. However I must admit it's about time I got myself a new one". This conversation set me thinking, Home Radio Components

really do produce a catalogue that will last and last, and a service to back it up. So if you are keen to save the pennies, send for a copy today. You may still be using it in 1977. On the other hand, if you really like to keep up with the latest developments, Home Radio will be happy to sell you a new one. Each year they spend at least 5 or 6 months revising it in order to bring the latest trends to your notice. Either way you cannot lose. Especially when you bear in mind, that although the initial cost is 65p plus 33p postage and packing, they enclose 14 vouchers each worth 5p if used as directed. Add to that the fact you could easily make it last two or three years . . . well, to borrow a phrase, "You never had it so good". Don't wait, send off the coupon today with your cheque or P.O. for 98 pence.

65p. plus 33p POST AND PACKING

POST THIS COUPON
with cheque or P.O. for 98p.

The price of 98p applies only to customers in the U.K. and to BFPO Addresses.

Please write your Name and Address in block capitals

NAME

ADDRESS

.....

.....

HOME RADIO (Components) LTD., Dept. PW,
234-240 London Road, Mitcham, Surrey CR4 3HD



(Regn. No.
London 912966)

HOME RADIO (Components) LTD. Dept. PW, 234-240 London Road, Mitcham, CR4 3HD. Phone 01-648 8422

POWER UNIT Type A126

Supplying 6, 7.5 or 9 Volt DC at 200 mA. In moulded case forming a 2 pin 5A main-plug.



3 metre output lead with 4-way multiplex giving 2-1 and 2-3 mm sockets and 3-5 mm plugs. Price £2.30. Post 10p.

2" and 4" PANEL METERS

| 2" | | 4" | |
|--|---------------|---|---------------|
| SIZE: 60mm Wide x 45mm High x 40mm Deep. | I.R. Movement | SIZE: 110mm Wide x 82mm High x 43mm Deep. | I.R. Movement |
| 0-50 micro A. | 1250 Ohms | 0-50 micro A. | 1400 Ohms |
| 0-100 micro A. | 580 Ohms | 0-100 micro A. | 730 Ohms |
| 0-300 micro A. | 170 Ohms | 0-500 micro A. | 200 Ohms |
| 0-1 mA | 170 Ohms | 0-1 mA | 200 Ohms |
| 0-5 mA | 170 Ohms | 0-5 mA | 200 Ohms |
| 0-10 mA | 6 Ohms | 0-10 mA | 6 Ohms |
| 0-50 mA | 0.5 Ohms | 0-50 mA | 0.5 Ohms |
| 0-100 mA | 0.5 Ohms | 0-100 mA | 0.5 Ohms |
| 0-500 mA | 0.5 Ohms | 0-500 mA | 0.5 Ohms |
| 0-1 AMP | 0.5 Ohms | 0-1 AMP | 0.5 Ohms |
| 0-2 AMP | 0.5 Ohms | 0-2 AMP | 0.5 Ohms |
| 0-25 Volt | 15K | 0-25 Volt | 15K |
| 0-50 Volt | 50K | 0-50 Volt | 50K |
| 0-300 Volt | 300K | 0-300 Volt | 300K |
| "g" Meter | 170 | "g" Meter | 200 |
| VU Meter | 5250 | VU Meter | 5250 |

VU Meters are complete with detectors. Modern wide view. Prices 2" £2.20 Post 10p. Price 4" £4.00 Post 10p. Lamps 60p per set.

1/2 watt CARBON FILM RESISTORS
1/2 watt at 70°C E 12 range 10Ω-1MΩ 5% tol above 470 KΩ 10% tol at 95p per 100.

C1000 MULTIMETER

Special Offer
Compact General Purpose Mini Multimeter. Input Resistance 1000 ohms per volt



Ranges:
AC Volts 0-15, 50, 250, 1000 V
DC Volts 0-10, 50, 250, 1000 V
DC Current 0-1 mA, 0-100mA, 0-1000mA
Resistance 0-150K ohms
Size 60 x 24 x 90 mm
Complete with Batteries, Test Prods, Instructions. Special price £2.30 Post 25p.

C1001 MULTIMETER

Input Resistance 20,000 ohms per volt
Overload protection
150 μA movement, clear scale
Ranges—AC Volts 0-10, 50, 250, 1000V
DC Volts 0-5, 25, 125, 500, 2500V
DC Current 0-50 mA
Resistance 0-60 Kohms, 0-6 Mohms
Decibels -20 to +22 dB.
Carrying Case, Test Prods and Batteries included.
Size: 11.5 x 8.3 x 2.7 cm.
Price £2.85. Post 20p.

TRANSFORMERS

CASED TRANSFORMERS

Housed in smart resin-coated steel cases, with 3-core power cable and outlet socket, fused primary winding. Isolation types are fitted with 3-pin outlet sockets, and are available with 110 volt or 240 volt output. (Please state). Auto types are fitted with 2-pin flat style sockets up to 500 VA. 3-pin sockets from 750 to 3000 VA. See Auto and Isolation sections for prices.

SAFETY ISOLATING

Prim. 120/240V. Sec. 120/240V. Centre Tap with Screen.

| VA (watts) | Ref. No. | Price Cased | Price Isolated | Price Open | Post |
|------------|----------|-------------|----------------|------------|------|
| 60 | 149 | 8.85 | 8.85 | 4.87 | 0.56 |
| 100 | 150 | 9.15 | 8.85 | 4.90 | 0.64 |
| 200 | 151 | 11.45 | 8.85 | 8.14 | 0.80 |
| 250 | 152 | 13.90 | 8.85 | 9.80 | 0.88 |
| 350 | 153 | 15.50 | 8.85 | 11.88 | 0.95 |
| 500 | 154 | 17.25 | 8.85 | 13.82 | 1.13 |
| 750 | 155 | 27.10 | 1.10 | 20.59 | O.A. |
| 1000 | 156 | 35.40 | 1.10 | 29.15 | O.A. |
| 1500 | 157 | 43.00 | 1.10 | 33.87 | O.A. |
| 2000 | 158 | 49.75 | 2.64 | 37.10 | O.A. |
| 3000 | 159 | 72.15 | 2.64 | 58.55 | O.A. |

12 & 24 Volts Prim. 200-240V.

| Amps | Ref. No. | Price | Post |
|---------|----------|-------|-------|
| 12V 0.3 | 0-15 | 2.42 | 1.58 |
| 0.5 | 0-25 | 1.11 | 1.38 |
| 1 | 0-5 | 2.13 | 1.74 |
| 2 | 1 | 71 | 2.30 |
| 4 | 2 | 18 | 2.98 |
| 6 | 3 | 70 | 4.18 |
| 8 | 4 | 108 | 4.55 |
| 10 | 5 | 72 | 5.20 |
| 12 | 6 | 116 | 5.51 |
| 18 | 8 | 17 | 7.00 |
| 20 | 10 | 115 | 10.42 |
| 30 | 15 | 187 | 12.25 |
| 40 | 20 | 282 | 14.85 |
| 60 | 30 | 226 | 16.88 |

30 Volts

Prim. 200-240V. Sec. 12, 15, 20, 24, 30V.

| Amps | Ref. No. | Price | Post |
|------|----------|-------|------|
| 0-5 | 112 | 1.90 | 0.47 |
| 1 | 79 | 2.40 | 0.56 |
| 2 | 8 | 3.50 | 0.56 |
| 3 | 20 | 4.50 | 0.64 |
| 4 | 21 | 5.15 | 0.72 |
| 5 | 51 | 6.40 | 0.72 |
| 6 | 117 | 7.16 | 0.88 |
| 8 | 88 | 9.55 | 0.95 |
| 10 | 89 | 9.67 | 0.95 |

AUTO TRANSFORMERS

| VA | Ref. No. | Price Cased | Price Plugs | Price Open | Post |
|------------------------------------|----------|-------------|-------------|------------|------|
| Tapped at 115, 220, 240 Volts | | | | | |
| 20 | 113 | 3.85 | 0.20 | 1.71 | 0.47 |
| Tapped at 115, 200, 220, 240 Volts | | | | | |
| 150 | 4 | 6.88 | 0.20 | 4.12 | 0.56 |
| 200 | 65 | 7.04 | 0.20 | 4.85 | 0.64 |
| 300 | 95 | 8.00 | 0.20 | 5.72 | 0.72 |
| 500 | 67 | 10.99 | 0.20 | 8.85 | 0.88 |
| 750 | 83 | 13.82 | 0.85 | 10.80 | 0.95 |
| 1000 | 84 | 17.27 | 0.85 | 13.68 | 1.13 |
| 1500 | 93 | 21.87 | 0.85 | 18.31 | O.A. |
| 2000 | 95 | 33.11 | 1.80 | 24.25 | O.A. |
| 3000 | 73 | 47.94 | 2.10 | 35.10 | O.A. |

50 Volts

Prim. 200-240V. Sec. 19, 25, 33, 40, 50V.

| Amps | Ref. No. | Price | Post |
|------|----------|-------|------|
| 0-5 | 102 | 2.53 | 0.47 |
| 1 | 103 | 3.48 | 0.56 |
| 2 | 104 | 5.03 | 0.64 |
| 3 | 105 | 5.81 | 0.72 |
| 4 | 106 | 7.58 | 0.88 |
| 6 | 107 | 12.30 | 0.95 |
| 8 | 118 | 13.20 | 1.13 |
| 10 | 119 | 17.62 | O.A. |

60 Volts

Prim. 230-240V. Sec. 24, 30, 40, 48, 60V.

| Amps | Ref. No. | Price | Post |
|------|----------|-------|------|
| 0-5 | 124 | 2.30 | 0.56 |
| 1 | 126 | 3.41 | 0.56 |
| 2 | 127 | 5.09 | 0.72 |
| 3 | 125 | 7.52 | 0.80 |
| 4 | 123 | 8.75 | 0.85 |
| 5 | 40 | 9.75 | 0.95 |
| 6 | 120 | 11.20 | 1.01 |
| 8 | 121 | 15.00 | 1.19 |
| 10 | 122 | 18.20 | O.A. |
| 12 | 189 | 18.50 | O.A. |

MINIATURE AND EQUIPMENT

Prim. 240V with screen.

| Sec. 1 | Sec. 2 | Milliamps | Ref. No. | Price | Post |
|---------------|---------|-----------|-----------|-------|------|
| 3-0-3 | — | 200 | — | 238 | 1.50 |
| 0-6 | 0-6 | 500 | 500 | 234 | 1.88 |
| 0-6 | 0-6 | 1000 | 1000 | 212 | 1.90 |
| 0-9-9 | — | 100 | — | 18 | 1.40 |
| 0-9 | 0-9 | 330 | 330 | 235 | 1.50 |
| 0-9-9 | — | 500 | — | 207 | 1.93 |
| 0-9-9 | 0-9-9 | 1000 | 1000 | 208 | 2.75 |
| 15-0-15 | — | 40 | — | 240 | 1.85 |
| 0-15 | 0-15 | 200 | 200 | 236 | 1.88 |
| 20-0-20 | — | 30 | — | 241 | 1.85 |
| 0-20 | 0-20 | 150 | 150 | 237 | 1.88 |
| 0-15-20 | 0-15-20 | 500 | 500 | 205 | 2.75 |
| 0-20 | 0-20 | 300 | 300 | 214 | 1.98 |
| 0-20 | — | 3500 | NO SCREEN | 1116 | 3.30 |
| 20-12-0-12-20 | — | 700 (D/C) | — | 221 | 2.20 |
| 0-15-20 | 0-15-20 | 1000 | 1000 | 206 | 3.50 |
| 0-15-27 | 0-15-27 | 500 | 500 | 203 | 3.00 |
| 0-15-27 | 0-15-27 | 1000 | 1000 | 204 | 3.85 |

PLASTIC CASED SILICON BRIDGE RECTIFIERS

| One Amp | Two Amp | Four Amp | Six Amp |
|----------------|----------------|----------------|----------------|
| 50 P.I.V. 20p | 50 P.I.V. 35p | 100 P.I.V. 55p | 50 P.I.V. 65p |
| 100 P.I.V. 25p | 100 P.I.V. 40p | 200 P.I.V. 60p | 100 P.I.V. 70p |
| 200 P.I.V. 25p | 200 P.I.V. 45p | 400 P.I.V. 65p | 200 P.I.V. 80p |
| 600 P.I.V. 30p | 400 P.I.V. 50p | 600 P.I.V. 75p | 400 P.I.V. 90p |

ADD 10p P & P PER ORDER

PLEASE
ADD
VAT

POWER UNIT Type CC 12-05

Output switched 3, 4.5, 6, 7.5, 9 and 12 volts at 500 mA D.C., Operates from 240 V mains, suitable for Radio, Tape Recorders, Record Players etc. Size 7.5 x 5.0 x 14.0cm. Price £3.95. Post 25p.



MINIATURE NEONS

6mm dia. 12mm length leads length approx. 20mm. Recommended ballast resistor 150K ohms for 240 Volt operation. Price: Packet of 10 for 60p. Postage 10p.

A.S.P. LTD.

DEPT PW9, SIMMONDS ROAD, WINCHEAP, CANTERBURY, KENT. Tel: (0227) 52436

Send 25p for Catalogue

ELECTRONI-KIT

"... kits of exceptional quality" (AUDIO mag. Dec. 1974)

"... These kits are very good" (P.W. mag. June 1975)

BUILD AND REBUILD AND DESIGN YOUR OWN WORKING PROJECTS—NO SOLDERING

Radios, microphones, burglar alarms, inter-comms, ferrite detectors, solar cell, photoelectric cell, voice relay, electronic cats, birds, guns, organs, illuminometers, voltmeters, meters of all types, etc., etc., plus your own circuit designs.

COMPLETELY SAFE—suitable for all, from beginners on. 30 different projects £10-45, 100 different projects £20-45, over 150 £33-95. Add-on kits, spares, available too.

Prices Include Valuable Manuals, Battery, p. & p. VAT etc.

Cheque/P.O./Cash (or 11p for literature) to DEPT. PW

Satisfaction guaranteed


ELECTRONI-KIT LTD, 408 St. John's Street, London, EC1. (01-278 4579)

Newest, neatest system ever devised for storing small parts and components: resistors, capacitors, diodes, transistors, etc. Rigid plastic units interlock together in vertical and horizontal combinations. Transparent plastic drawers have label slots. ID have space dividers. Build up any size cabinet for wall, bench or table top.

INTER-LOCKING PLASTIC STORAGE DRAWERS

NEAT! HANDY! TIDY!

DISCOUNT PRICES

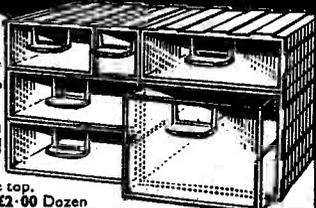

SINGLE UNITS (5" x 2 1/2" x 2 1/2") £2.00 Dozen

DOUBLE UNITS £3.50 Dozen. TREBLE (3D) £3.50 for 8

DOUBLE TREBLE £4.90 for 8.

EXTRA LARGE SIZE (6D) £4.50 for 8.

Carriage 50p. Orders over £10 please add 10% carr.

QUANTITY DISCOUNTS 1% in £1 for orders over £20

7 1/2% for orders over £60. Quotations for large quantities.

PLEASE ADD 8% VAT to TOTAL REMITTANCE.

(Dept. PW7), 124 CRICKLEWOOD BROADWAY LONDON N.W.2 01-450 4844

FLAIDLINE SUPPLIES

ing amplifier. It is biased into almost complete conduction so that when positive going excursions of any applied AC appear at its base the transistor finds it hard to go any further into conduction and there will be little negative going signal at its collector. On the other hand negative going excursions will find it easier to take the transistor slightly out of conduction and amplified positive signals will appear at the collector. These positive signals should be at the carrier frequency but will be varying in amplitude in sympathy with the audio frequency. It is necessary to "detect" the signal by cutting off the negative going portion otherwise we shall be unable to regain any audio information as the average signal level would have been zero. The detected signal, still at radio frequency, is then fed to a second, more conventional, grounded-emitter amplifier where its level is increased. The signal at the collector of Tr2 is fed to a crystal earpiece the capacitance of which effectively shunts out the radio frequency component

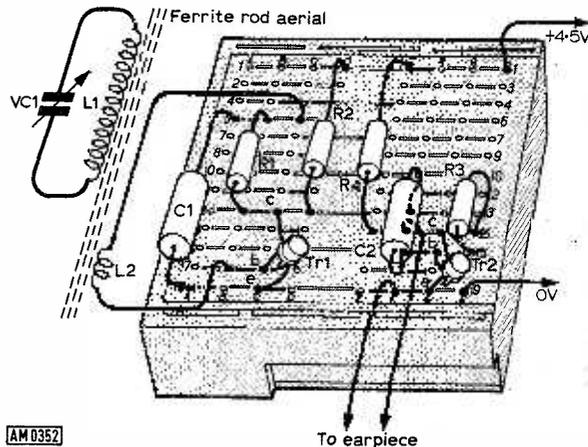


Fig. 117: Layout of circuit of Fig. 116.

coil has a much lower output impedance and while the voltages developed across it will be less than the main coil there is a greater current drive ability. We have made, in effect, a simple transformer which allows the current sensitive input stage of Tr1 to draw the current it wishes without reflecting its impedance across the main tuned circuit. If this theory is correct the Q of the main tuned circuit should not be so adversely effected. Make up the circuit Fig. 117 and you should be pleasantly surprised by the vast improvement in signal level obtained as well as the improved ability to separate the stations, or selectivity.

We should, perhaps, add a note of sympathy for those who live in the more remote parts of the country because, although we imply good reception

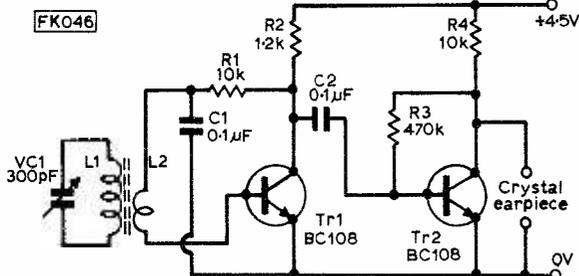


Fig. 116: Circuit modification to retain high Q of tuned circuit.

of the signal leaving only the audio frequency "envelope" which should be heard as an audio signal in the earpiece.

You will be fortunate if you can hear anything very much with this circuit until VC1 is set to its minimum capacitance, i.e. the vanes are fully open, and then you should hear a conglomeration of local stations all on top of each other. The signals will be weak and almost impossible to separate from one another. The reason for this is that the input impedance of Tr1 is very low and has lowered the Q of the tuned circuit, as well as being so low that we are getting anything but optimum power coupling between the two stages.

To prove the point use the same components in the slightly different circuit shown in Fig. 116. Notice that you need to put about four turns of flexible insulated wire on the ferrite rod over the top and at the end of the basic 70 turn coil. This secondary



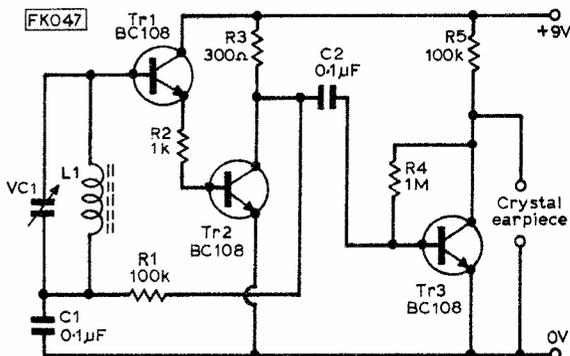


Fig. 118: above, shows addition of emitter follower stage to provide feedback.

Fig. 119: below, practical layout of circuit of Fig. 118.

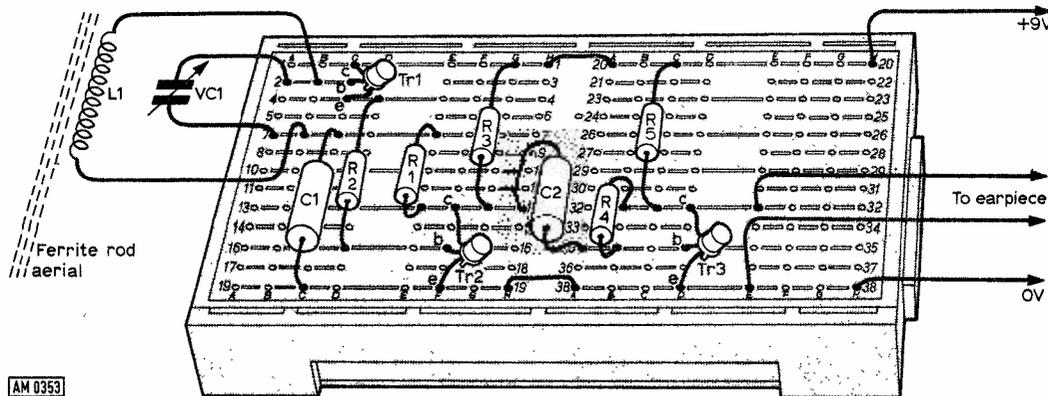


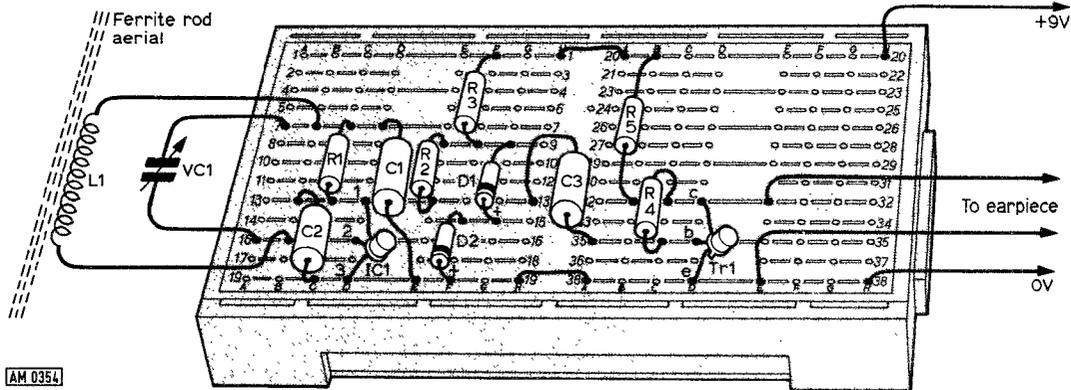

AM 0354

Fig. 121: above, suggested arrangement for Fig. 120.

Fig. 120: below, alternative TRF circuit arrangement using the ZN414 integrated circuit.

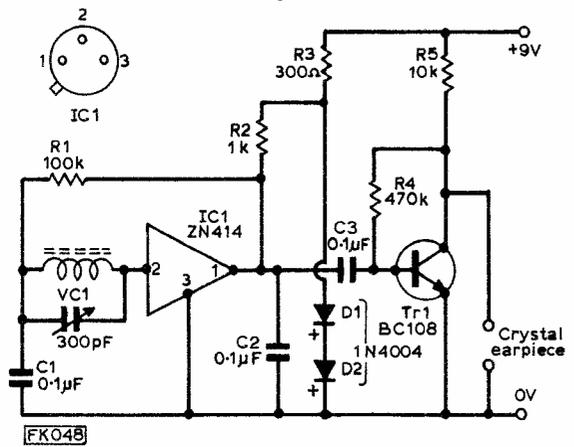

FK048

from this circuit, it would be fairer to add that it is only suitable for reception of stations within a fifty to hundred mile radius!

For those who do not like having to wind an extra coil on the aerial there are other ways of improving the Q. If the output impedance of the tuned circuit cannot be reduced than the alternative is to increase the input impedance of the subsequent amplifiers. The circuit of Fig. 118, layout in Fig. 119, shows how this can be done by using an emitter follower. This has a very high input impedance and is biased into conduction by the 100k resistor, R1, feeding its base through the coil. The bias current is obtained by negative feedback from the collector of Tr2 and C2 bypasses any radio frequency signals to earth. Tr2 acts as an amplifying detector just as before and Tr3 provides a greater degree of amplification. Note the high value of collector load for Tr3, which is necessary to prevent instability. You can reduce this value down to about 10kΩ in easy stages but at some point you might find that the circuit starts to oscillate.

While this latter circuit does work we have included it to demonstrate, in a simple way, the principle of operation of a very well known integrated circuit which, these days, is by far the best way of making a TRF radio. It is the ZN414, well worth the investment of about a £1, if nothing else, for the satisfaction of getting a radio to work when outside the range of the preceding experiments! The integrated circuit, Fig. 120, contains a very high input impedance amplifier which is biased in much the same way as our preceding experiment, with R1.

The IC contains a much higher degree of amplification than we could possibly obtain with conventional components without instability creeping in and as a bonus contains the detector and a degree of automatic gain control as well.

Apart from the obvious advantages of the extra gain and added refinement of AGC there is little difference between the principle of operation of this device and the preceding circuits. Resistor R2 corresponds to the collector load which goes to the positive rail. In the case of the ZN414 it only needs 1.2V to drive it and we have obtained this by using the forward voltage drop across two diodes, D1 and D2, in series with R3. C2 acts, in place of the internal capacitance of the earpiece, to filter out the RF carrier and we have added a conventional audio amplifier stage to bring up the level for comfortable listening. When using this little radio note the high degree of selectivity given by its high input impedance. The layout is given in Fig. 121.

Finally, a brief point about having too narrow a bandwidth which would limit high frequency audio response. This problem did not crop up at all in our experiments, apart from the earlier reference to it. The reason is that normally the Q of simple tuned radio frequency circuits is never likely to give too narrow a bandwidth, consequently a TRF receiver such as the one described, will give as high a quality output as is possible when operating on medium waves. The only drawbacks which would force one to more sophisticated circuits are the lack of sensitivity and the problems of overcrowding on the waveband which necessitate narrower bandwidth receivers giving poorer quality associated with narrow bandwidth.

This is the concluding part of the present series of Experimental Workshop.


points arising . . .

REACTION TIMER

April 1975. In the circuit diagram Fig. 1 page 1098, R3 should be shown as 27kΩ and R4 as 47kΩ. The component list is correct.

BENCH STABILISED POWER SUPPLY

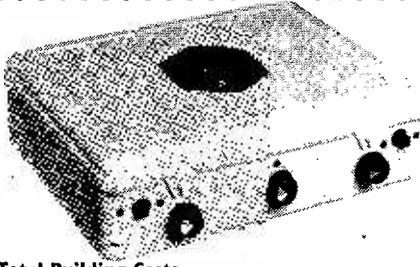February 1974. In use a fault developed giving a permanent output of over 30V. This was found to be caused by a short circuit inside Tr1, a 2N3053. This was replaced by a Texas Instruments BFT39 which has proved satisfactory.



NEW EDU-KIT MAJOR

Completely Solderless Electronic Construction Kit
Build these projects without soldering iron or solder

- ★ 4 Transistor Earpiece Radio.
- ★ 5 Transistor Push Pull Amplifier.
- ★ Batteryless Crystal Radio.
- ★ Signal Tracer.
- ★ 7 Transistor Loudspeaker Radio MW/LW.
- ★ One Transistor Radio.
- ★ Signal Injector
- ★ 5 Transistor Short Wave Radio.
- ★ 2 Transistor Regenerative Radio.
- ★ Transistor Tester NPN-PNP.
- ★ Electronic Metronome.
- ★ 3 Transistor Regenerative Radio.
- ★ 4 Transistor Push Pull Amplifier.
- ★ Electronic Noise Generator.
- ★ Audible Continuity Tester
- ★ Sensitive Pre-Amplifier.


Total Building Costs

£9.03 PP Ins. 44p
(Overseas Seamail P & P £2.35)

Components include: 24 Resistors ● 21 Capacitors ● 10 Transistors ● 3 1/4" Loudspeaker ● Earpiece ● Mica Baseboard ● 3 12-way connectors ● 2 Volume controls ● 2 Slider Switches ● 1 Tuning Condenser ● 3 Knobs ● Ready Wound MW/LW/SW Coils ● Ferrite Rod ● 6 1/2 yards of wire ● 1 Yard of sleeving etc. ● Parts Price List and Plans 55p free with parts.

NEW ROAMER NINE


WITH V.H.F. INCLUDING AIRCRAFT

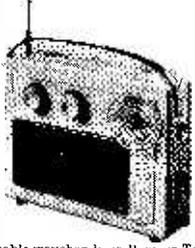

Nine Transistors, 9 Tunable wavebands as Roamer Ten. Built in ferrite rod aerial for MW/LW. Retractable chrome-plated telescopic aerial for VHF and SW. Push Pull output using 600 mW Transistors. 9 Transistors and 3 diodes, tuning condenser with V.H.F. section, separate coil for aircraft, moving coil loudspeaker, volume ON/OFF and wavechange controls. Attractive all white case with red grille and carrying strap. Size 9 1/2" x 7" x 2 1/4" approx. Parts Price List and Plans free with parts.

Total Building Costs £8.70 PP & Ins. 44p
(Overseas Seamail P & P £2.35)

NEW Everyday Series

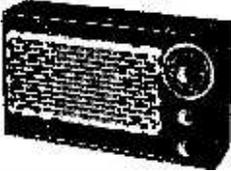

Build this exciting New series of designs
E.V.5. 5 Transistors and 2 diodes. MW/LW. Powered by 4 1/2 volt Battery. Ferrite rod aerial, tuning condenser, volume control, and now with 3" loudspeaker. Attractive case with red speaker grille. Size 9" x 5 1/4" x 2 1/4" approx. Parts Price List and Plans free with parts.

Total Building Costs £4.25 PP & Ins. 36p
(Overseas Seamail P & P £1.70)

E.V.6. Case and looks as above. 6 Transistors and 3 diodes. Powered by 9 volt battery. Ferrite rod aerial, 3" loudspeaker, etc. MW/LW coverage. Push Pull output. Parts Price List and Plans free with parts.

Total Building Costs £4.98 PP & Ins. 36p
(Overseas Seamail P & P £1.70)

E.V.7. Case and looks as above. 7 Transistors and 3 diodes. Six wavebands. MW/LW, Trawler Band, SW1, SW2, SW3, powered by 9 volt battery. Push Pull output. Telescopic aerial for short waves. 3" Loudspeaker. Parts Price List and Easy Build Plans free with parts.

Total Building Costs £5.60 PP & Ins. 38p
(Overseas Seamail P & P £2.00)

ROAMER EIGHT Mk I

NOW WITH VARIABLE TONE CONTROL



7 Tunable Wavebands: MW1, MW2, LW, SW1, SW2, SW3 and Trawler Band. Built in Ferrite Rod Aerial for MW and LW. Chrome plated Telescopic aerial can be angled and rotated for peak short wave listening. Push pull output using 600mW transistors. Car aerial and Tape record sockets. Selectivity switch. 8 transistors plus 3 diodes. Latest 4" 2 watt ferrite magnet loudspeaker. Air spaced ganged tuning condenser. Volume/on/off, tuning wave change and tone controls. Attractive case in rich chestnut shade with gold blocking. Size 9 x 7 x 4in. approx. Easy to follow instructions and diagrams. Parts price list and plans free with parts.

Total building costs £8.73 PP & Ins. 65p
(Overseas Seamail P & P £3.50)

POCKET FIVE

NOW WITH 3" LOUD-SPEAKER



3 Tunable wavebands. M.W. L.W. and Trawler Band. 7 stages, 5 transistors and 2 diodes, supersensitive ferrite rod aerial, attractive black and gold case. Size 5 1/2" x 1 1/2" x 3 1/4" approx. Plans and Parts Price List free with parts.

Total Building Costs £2.50 PP & Ins. 36p
(+ 25% VAT 62p)
(Overseas Seamail P & P £1.70)



TRANSONA

FIVE NOW WITH 3" LOUDSPEAKER

Wavebands, transistors and speaker as Pocket Five. Larger Case with Red Speaker Grille and Tuning Dial. Plans and Parts Price List free with parts.

Total Building Costs £3.20 PP & Ins. 36p
(+ 25% VAT 80p)
(Overseas Seamail P & P £1.70)


TRANS EIGHT

8 TRANSISTORS and 3 DIODES

6 Tunable Wavebands: MW, LW, SW1 SW2, SW3 and Trawler Band. Sensitive ferrite rod aerial for M.W. and L.W. Telescopic aerial for Short Waves. 3in. Speaker. 8 improved type transistors plus 3 diodes. Attractive case in black with red grille, dial and black knobs with polished metal inserts Size 9 x 5 1/4 x 2 1/4 in. approx. Push pull output. Battery economiser switch for extended battery life. Ample power to drive a larger speaker. Parts price list and plans free with parts.

Total building costs £5.98 PP & Ins. 40p

(Overseas Seamail P & P £2.00)

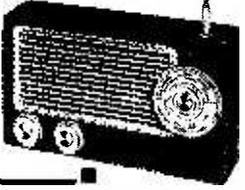

ROAMER SIX

CASE AND LOOKS AS TRANS-EIGHT

6 Tunable Wavebands: MW, LW, SW1 SW2 etc. Sensitive ferrite rod aerial and telescopic aerial for Short Waves. 3in. Speaker 8 stages—6 transistors and 2 diodes. Attractive black case with red grille, dial and black knobs with polished metal inserts. Total building costs

£5.48 PP & Ins. 40p

(Overseas Seamail P & P £2.00)

ROAMER TEN Mk 2

WITH VHF INCLUDING AIRCRAFT



Now with free earpiece and switched socket. 10 Transistors. Latest 4" 2 watt Ferrite Magnet Loudspeaker. 9 Tunable Wavebands, MW1, MW2, LW, SW1, SW2, SW3, Trawler Band, VHF and Local Stations also Aircraft Band. Built in Ferrite Rod Aerial for MW/LW. Chrome plated 6 section Telescopic Aerial, can be angled and rotated for peak short wave and VHF listening. Push Pull output using 600mW Transistors. Car Aerial and Tape Record Sockets. 10 Transistors plus 3 Diodes. Ganged Tuning Condenser with VHF section. Separate coil for Aircraft Band. Volume on/off, Wave Change and tone Controls. Attractive Case in black with silver blocking. Size 9" x 7" x 4". Easy to follow instructions and diagrams. Parts price list and plans 50p free with parts.

Total building costs £11.87 PP & Ins. 65p
(Overseas Seamail P & P £3.50)

(Total building costs £11.87 PP & Ins. 65p)

"EDU-KIT"



Build Radios, Amplifiers, etc. from easy stage diagrams.

Components include:
Tuning Condenser: 2 Volume Controls: 2 Slider Switches: Fine Tone 3" Moving Coil Speaker: Terminal Strip: Ferrite Rod Aerial: Battery Clips: 4 Tag Boards: 10 Transistors: 4 Diodes: Resistors: Capacitors: Three 1/2" Knobs. Units once constructed are detachable from Master Unit, enabling them to be stored for future use. Ideal for Schools, Educational Authorities and all those interested in radio construction. Parts price list and plans free with parts.

Total building costs £6.87 PP & Ins. 35p
(Overseas Seamail P & P £2.35)

"ALL PRICES NOW INCLUSIVE VAT"

RADIO EXCHANGE LTD

★ Callers side entrance "Lavelle" shop.
★ Open 10-1, 2.30-4.30, Mon.-Fri. 9-12 Sat.

To RADIO EXCHANGE CO., 61a HIGH STREET, BEDFORD, MK40 1SA
Tel. : 0234 52367, Reg. No. 788372.

I enclose £..... for

Name.....

Address

(Dept. PW9.)

ESSENTIAL BOOKS FOR RADIO AMATEURS

NEW (16th) EDITION

A GUIDE TO AMATEUR RADIO

by Pat Hawker, G3VA

For over 40 years the many editions of the *Guide* have helped successive generations of amateurs to learn about amateur radio and to obtain transmitting licences.

The new edition has been extensively revised and enlarged. Chapters include: (1) This is amateur radio; (2) Getting started; (3) Communication receivers; (4) Amateur transmitters; (5) Licence examinations; (6) Operating an amateur station; (7) Workshop practice, and (8) Amateur equipment.

An entirely new chapter on popular equipment includes facts on over 160 well-known models—receivers, transmitters, transceivers. Full constructional details are given of two simple receivers and a phone/cw transmitter.

This edition reflects current interest in ssb, vhf, transistor and valve equipment, Class A and Class B licences. It describes how licences are obtained and provides guidance on both home-built and factory-made equipment.

Almost 100,000 copies of all editions sold

112 pages, fully illustrated

Price £1.10 post paid

NBFM MANUAL

by R. S. Hewes, G3TDR, and G. R. Jessop, G6JP

The relative freedom from interference to television, radio and audio equipment and the excellent rejection of impulse noise makes narrow band frequency modulation attractive and economic. This manual presents complete coverage of the subject and is invaluable to any amateur wishing to use the mode.

60 pages

Price £1.10 post paid

RAE MANUAL

by G. L. Benbow, G3HB

The standard work for all would-be licensed radio amateurs studying for the Radio Amateurs' Examination. This revised edition meets the present syllabus requirements.

96 pages

Price £1 post paid

Also by the same author: **RAE REVISION NOTES**, price 45p post paid

These are just a few of a complete range of technical publications, log books and maps for the radio amateur. Send a large stamped self-addressed envelope for the complete list.

The **RSGB** is the national society representing all UK radio amateurs. Membership is open to all interested in the hobby: write to the membership section and ask for full details.



RADIO SOCIETY OF GREAT BRITAIN

35 DOUGHTY STREET, LONDON, WC1N 2AE TEL: 01-837 8688

ELECTROVALUE

The best of all!

CATALOGUE 7 ISSUE 3

with 25p refund voucher

Up-dated Price & Product Information

112 pages plus cover. As comprehensive and up-to-the-minute as possible. Thousands of items from vast ranges of semi-conductors including ICs to components, tools, accessories, technical information and diagrams are included as well as a refund voucher worth 25p for spending on orders list value £5 or more **SEND NOW FOR YOUR COPY BY RETURN 30p** post it's an investment in practical money-saving and reliability!

PRICES—Electrovalue policy is to review prices every three months rather than try to keep up with day by day changes as they occur. We have, in fact, held our prices for two such periods (Jan. 1st–July 1st) and our next price review is due October 1st.

DISCOUNTS apply on all items except the few where prices are shown NETT. 5% on orders from £5 to £14.99; 10% on orders list value £15 or more.

FREE POST AND PACKING in U.K. for pre-paid mail orders over £2 (except Baxandall cabinets). If under there is an additional handling charge of 10p.

QUALITY GUARANTEE. All goods are sold on the understanding that they conform to maker's specification. No rejects, seconds or sub-standard merchandise.

ELECTROVALUE LTD

All communications to Section 2/5, 28, ST. JUDES RD, ENGLEFIELD GREEN, EGHAM, SURREY TW20 0HB. Telephone Egham 3603, Telex 264475. Shop hours: 9-5.30 daily, 9-1 pm Sats.

NORTHERN BRANCH: 680, Burnage Lane, Burnage, Manchester M19 1NA. Telephone (061) 432 4945. Shop hours: Daily 9-5.30 pm; 9-1 pm Sats.

RELAY UNIT

Smart steel case 12 x 7 x 4 1/2" with 22 PC Type relays, most with at least 3 sets c/o contacts; 4 reed relays+coils, 2 pots, resistors, capacitors, 12BH7 valve, various diodes, tag board etc etc. Only £3.50

PC ETCHING KIT MK II

Contains 1lb Ferric Chloride, 100 sq ins copper clad board, DIALO etch resist pen, abrasive cleaner etching dish and instructions. Now also includes 2 miniature drill bits. £3.50

FERRIC CHLORIDE

Anhydrous technical quality in 1lb double sealed packs. 1lb 80p; 3lb £1.80; 10lb £4.65; 100lb £35

COMPUTER PANELS

Large quantity always available. 3lb asstd £1.60; 7lb £2.85; 56lb £15.

Pack with about 500 components inc. at least 50 transistors £1.

71b BARGAIN PARCELS

Hundreds of new components—pots, resistors, capacitors, switches, + PC boards with transistors and diodes also loads of odds and ends. Contents always changing. Only £3.00

POWER SUPPLY UNIT

G101: Mains transformer, 2A thermal cut-out, bridge rect., will give 1.7-10.5V output with 2 extra capacitors (provided). With data, only £1.30

TRANSFORMERS

All mains primaries, 0-0-5V @ 100mA 80p; 0-0-9V 100mA £1.02; 12-0-12V 100mA £1.08. 24-0-24V 500mA £2.20 1A multitapped to give 3, 4, 5, 6, 8, 9, 10, 12, 15, 18, 20, 24 or 30V. Also 12-0-12 or 15-0-15 £3.00. 2A version £4.40. 6-5-0-6-5V 500mA £1.45; 17V 1A £2; 0V 10A £3.00; sub-miniature 12-0-12V @ 50mA 80p.

Send 10p Stamp for Illustrated Multimeter Catalogue (Free with orders over £3).

All prices include UK postage VAT @ 8% or 25% as appropriate. SAE list, enquiries. Surplus components wanted for cash.

GREENWELD (PW9)

51 Shirley Park Road, Southampton, SO1 4FX. Tel: (0703) 772581. Also callers welcome at 21 Deptford Bdy SE8 01-692 2009, & 38 Lower Addiscombe Rd, Croydon 01-688 2950

BARGAIN PACKS

| | |
|----------------|-----------------|
| 12 BC107 £1.20 | 25 1N4001 £1.20 |
| 14 BC108 £1.20 | 22 1N4002 £1.20 |
| 12 BC109 £1.20 | 20 1N4003 £1.20 |
| 15 BC148 £1.20 | 18 1N4004 £1.20 |
| 13 BC149 £3.20 | 16 1N4005 £1.20 |
| 12 BC157 £1.20 | 14 1N4006 £1.20 |
| 12 BC158 £1.20 | 12 1N4007 £1.20 |
| 12 BC159 £1.20 | 40 1N4148 £1.20 |
| 2 2N2646 £1.20 | 3 2N3055 £1.20 |
| 10 BC328 £1.20 | 12 BC548 £1.20 |
| 12 BF194 £1.20 | 12 BF195 £1.20 |
| 7 BF173 £1.20 | 5 BF181 £1.20 |

All full spec marked components.

8 PIN DIL 741's

10+26p; 25+23p; 100+21p; 250+20p

555 TIMERS

3+ 60p; 10+ 30p; 25+ 46p; 100+ 43p

RESISTORS AND CAPACITORS

400 asstd carbon resistors £1.40
250 Hi-stabs 1, 2, 5%, 1/2, 1W £1.35
100 Wirewounds, 2W to 15W £1.80
200 ceramic, mica etc caps £1.10
100 C280 polyesters. 01-47 £1.30
200 min electrolytics, but mainly unmarked, so only £1.35.
15 airspaced & compression trimmers up to 1250pF £1.10.

JUMBO PACK—1 each of the above, £9.40 value for only £7.50!!!

VEROBOARD

100 sq ins, about 8 pieces asstd sizes and pitches £1.15

MISCELLANEOUS

SPCO microswitch, 5A 12p; 15 asstd pots 75p; plug in relay, 2500V 4 c/o 25p; 4 x 30V 10A rectx on heat sink, ideal batt. charger, £1.20 SN76680N £1. Good range close tolerance resistors—SAE 11st 96kHz crystal £1.

PUSH BUTTON BANK

8 interlocking buttons, each 4 pole changeover, only 4 x 21 x 2 1/2" £1.

TRANSISTOR PACKS

Large quantity of mainly unmarked out of spec. transistors just arrived. Sample tests show 75% OK. Sold in mixed packs with PNP, NPN, RF, AF, plastic, metal can, small signal and power devices. At least 200 for £1.50; 500 for £3.50; 1000 for £8.00. Out-of-spec 2N3055's 8 for £1.10. 25 untested BFY51 type transistors £1.10. 25 untested BC108 £1; 100 £3.00.

TAKE 20

DAVID ANDREWS

No. 71 MOTOR SPEED CONTROLLER

A series of simple transistor projects, using not more than twenty components.

BEFORE describing this project, a word of warning. Although exceedingly simple and easy to make, this device operates directly from the mains and has its components connected to the live mains without isolation from a transformer. This circuit is probably not suitable for less experienced constructors. The project should definitely **NOT** be made unless the constructor is prepared to go all the way and make a **fully insulated and earthed metal case** similar to that which will be described.

Speed control

The circuit makes possible the speed control of series wound brush electric motors as found in small portable electric drills such as the Black and Decker D520 and D720 series. When the device is in circuit speed control is effective from about 20 r.p.m. to half the drill's normal speed and at low speeds very little of the normal torque is lost; this constant torque effect is produced by making use of a feedback signal developed across the windings of the electric motor during the portion of the mains cycle when the thyristor is not conducting. Because the non-conducting cycle is necessary it is not possible to insert a triac instead of a thyristor to obtain speed control up to maximum speed. Almost any thyristor having minimum ratings of 3 amp and 400V breakdown can be used in the circuit.

Thyristor operation

To make the thyristor conduct it is necessary to pass a current between the gate and the cathode while a potential difference exists across the anode and cathode of the device. This trigger current is produced when the gate is made positive with respect to the cathode.

Referring to Fig. 1, R1 in conjunction with VR1 and D1 form a potential divider and rectifier across the mains so that the signal at the wiper of VR1 is a positive going half wave signal, the amplitude of which can be varied with VR1. If there was a

★ components list

R1 10kΩ 5W
VR1 2kΩ 2W wirewound
D1 1N4004
D2 1N4004
CSR1 CRS3/40 or similar 3A, 400V thyristor
Metal case, MK socket, terminal blocks, cable clamp, wide bezel knob, bracket for thyristor, good quality insulating board, stand off spacers, Rubber grommet for mains lead

normal resistive load across the output instead of a drill motor, the signal at the gate of the thyristor would rise in a positive direction in exact phase with the rise of the mains across the normally switched off device.

When the gate current so produced reaches its trigger threshold the thyristor will turn on and hold on for the duration of that positive mains cycle—the power being dissipated in the load. At the end of the mains cycle the thyristor switches off because its "holding current" falls to zero. During the negative half cycle which follows, the thyristor will not turn on but at the same moment in the next positive half cycle the first conduction cycle will be repeated.

Motor action

This explanation assumes a resistive load which guarantees that at the start of each positive half cycle the potential at the cathode of the thyristor is zero with respect to the gate, hence it is not difficult for the potential of the triggering voltage—set by VR1—to drive sufficient trigger current into the gate.

If, however, a drill motor is connected across the output, the drill will start to rotate as soon as the first positive half cycle is applied, but at the end of the cycle—when the thyristor switches off—the motor will "coast" on without extra power being applied.

During this coasting action the armature of the motor behaves like a generator and produces a positive voltage at the cathode of the thyristor so when the next conducting cycle begins the potential at the gate has to reach a higher absolute value before the trigger current flows. This occurs later on in the cycle so consequently less energy is applied to the motor and it will not receive such a great "kick" of power. The effect is that the motor slows up slightly.

This operation will, of course, occur repetitively over consecutive cycles and after a small period of time the system reaches equilibrium and the motor runs at a speed set by the potential at the wiper of VR1.

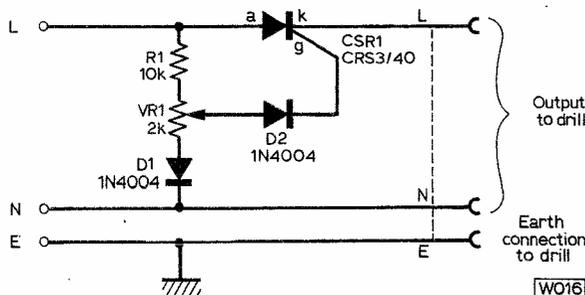


Fig. 1: Circuit diagram of the Motor Speed Controller.

If torque is applied to the motor it will naturally try to slow down during the negative half cycles so a lower reverse voltage will be generated and the "kick" of the next positive cycle will be greater, thus maintaining the near constant torque.

At slow speeds when no load is applied to the motor the speed may hunt up and down—a process known as "skip cycling" because the coasting action of the motor may prevent a further power kick over several cycles; as soon as torque is applied, however, the skip cycling effect stops.

Assembly

When assembling the device take great care over insulation—sleeve the leads of all the components which should be mounted on a good quality insulated board, see Fig. 2.

Remember that all connections are live to mains voltages **INCLUDING** the bracket for the thyristor and its mounting screw on the reverse side of the board. Because of this the board should be mounted on a metal front panel with stand-off spacers (Fig. 3), and the metal panel must be earthed.

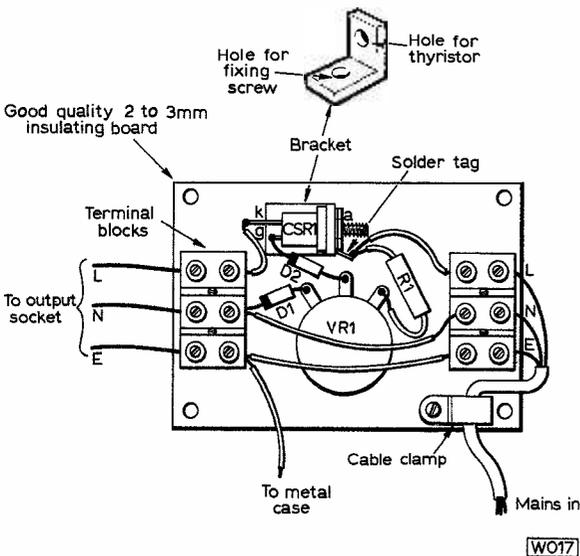


Fig. 2: Layout of the components in the Motor Speed Controller. Note that the bracket holding the thyristor will be live.

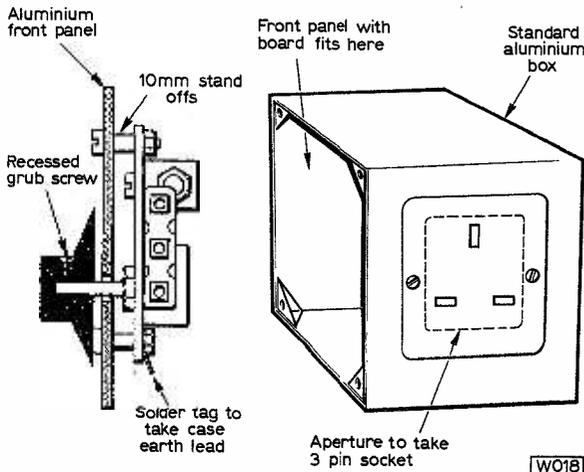


Fig. 3: Suggested "safe" method of housing the Motor Speed Controller.

Do not rely on the insulation of the spindle of the potentiometer. Use flush knobs which are either collet fixing or have a deeply recessed grub screw. Input and output leads are taken to standard electrical terminal blocks screwed to the board and the mains input lead should be anchored securely with a cable clamp.

The output can be connected from within the earthed case to a standard flush mounting MK wall socket which is screwed to the outside of the case if a suitably sized aperture is cut to take the terminations of the socket. **DO NOT FORGET THE EARTH CONNECTION TO THIS SOCKET.**

Note that R1 must be a five watt device and VR1 a two watt wirewound potentiometer.

PW TECHNICROSS PUZZLE No.10

presented last month



AVAILABLE NOW!

**REPRINT OF PW's
TELE-TENNIS SERIES**



July-November 74

Send 75p + 7p (post and packing) to:
Chief Cashier (PW Tele-Tennis), IPC Magazines,
Tower House, Southampton Street,
London, WC2E 9QX

IN NEXT MONTH'S PRACTICAL WIRELESS

EXTRA INSIDE 8-PAGE SUPPLEMENT No. 1 SIMPLE HOME PROJECTS

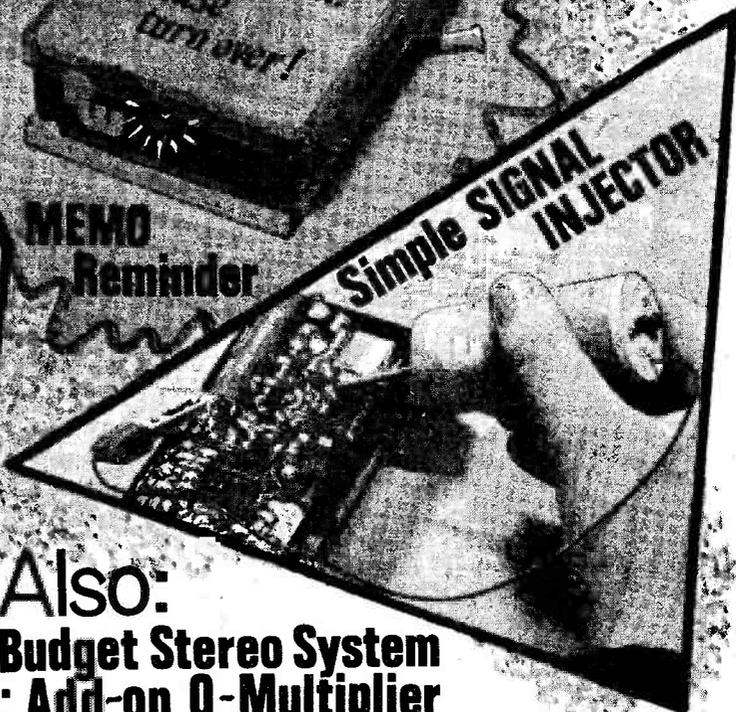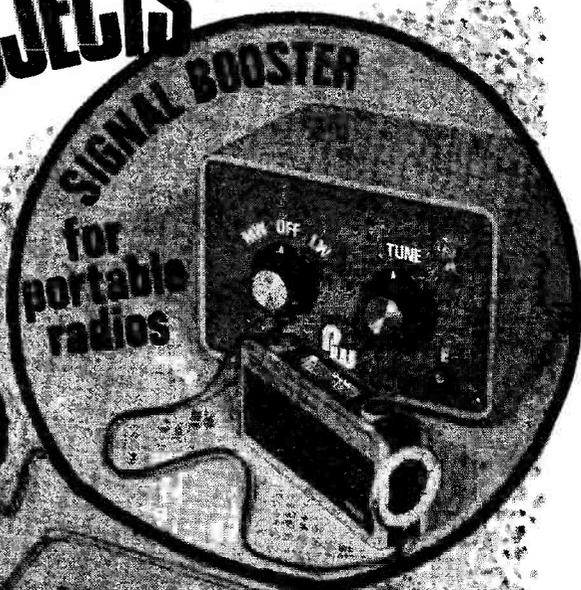Something for everybody! A Rain Warning device to protect Mum's washing, a Tuner for Dad's hi-fi, a Signal Injector for your own servicing work, a Signal Booster for the family radio and a Memo Reminder for everyone.



Also:
starting: Improve your Budget Stereo System
; Add-on Q-Multiplier

ON SALE IN SEPTEMBER



pw
'Easybuild' ELECT
WITH OPTIONAL

M. J. HUGHES M.A., C. Eng., MIERE

THIS project is a wonderful example of how modern technology can bring what was a super-sophisticated project into the realms of anyone who is reasonably competent at wielding a soldering iron. At the same time mass production of the complex integrated circuit used has brought down the cost to an amazingly low figure. Some people might complain that the introduction of modern large scale integrated circuit technology takes all the fun out of amateur electronic construction. This may, perhaps, be the case in some instances but there are many constructors who may not have the time to embark on lengthy projects and who like to get down to a job and see it through in one or two sittings.

It should not take the experienced constructor more than an hour or two to put this project together. Because of the simplicity of the electronic assembly it could, perhaps, be considered more as an exercise in neatness of construction and, for the real enthusiast, could be a useful exercise in producing a "do-it-yourself" printed circuit board.

PERFORMANCE

Having sounded the fanfare perhaps we had better say a few things about the end product itself. On the face of it the device is "yet another" digital clock but there are a few significant differences. For a start, use is made of the popular General Instru-


ment Microelectronics device the AY-5-1224. This is one of the lowest priced digital clock IC's on the market, readily available from several advertisers in this magazine. Being a 16 pin DIL (dual-in-line) package there is not the usual high cost of a specialised socket. The small number of output pins clearly implies that there are no fancy options such as alarm or six digit capabilities. By clever design the manufacturers have made amazing use of the few pins by giving them duplex functions from a strobe signal.

For example, by adding a few diodes to the external circuitry one has the option of 12 or 24 hour display (in the 12 hour mode the higher significant zeros of the hours presentation are blanked). The internal dividers can be pre-selected to operate from 50Hz or 60Hz inputs. In this project we have limited the design to 50Hz operation from 240V mains. The clock can be set to display minutes and seconds instead of hours and minutes, by the introduction of a further diode. There is a very unusual feature in the "reset to zero" facility which resets the display to "All Zeros" whether counting in the 12 or 24 hour mode, in hours and minutes or minutes and seconds. This reset clears the early stages of the counter chains completely giving a true zero. An extra diode in the circuitry will give a BCD output instead of the seven segment output (we shall not make use of this facility in this project) and, if desired, the segment drive outputs can be complemented by means of a single diode operating from the strobe line.

For those who have not come across the device before we show the typical general purpose application circuit in Fig. 1. We have deliberately left out component values on this drawing to avoid confusion with the circuit we shall be adopting for the project. A big attraction of the device is that it requires so few external components to get it to function. Its supply voltage is comparatively flexible, between 12 and 18V, and this means one does not have to make use of a sophisticated power supply. A half wave rectified supply is adequate. This means that with a carefully designed printed circuit layout the whole clock can be made very compact without introducing too many constructional problems. The mechanical construction is rather novel, using three printed circuit boards in a "bedstead" structure. Pins are used to route connections from one board to the next and there is the absolute minimum amount of free wiring.

Because of the "reset to zero" facility of the IC it seemed a pity to miss the obvious application of using the device as a stop clock (it will operate in "start/stop/reset" mode when counting in hours and minutes or minutes and seconds). Rather than include the necessary push buttons and switches in the basic clock it was felt wiser to offer this facility

DINIC CLOCK ~ RANGE TIMER

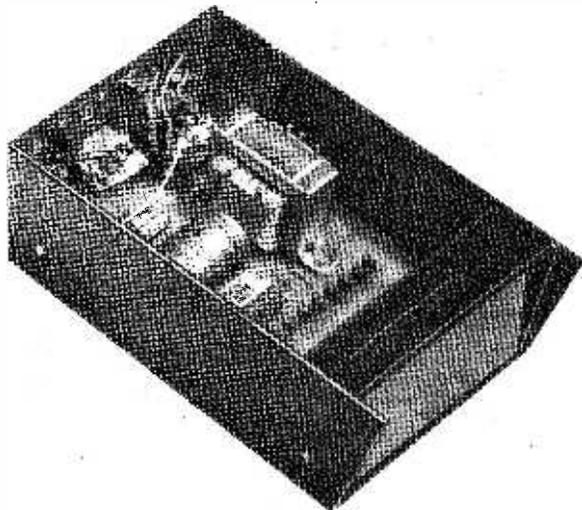

with an external plug-in control. This means that those who just wish to make a simple clock can omit the extra components. Having the external control means that the user has remote control of the clock and this in itself could be a very useful feature for some applications.

A very important application, which seems to have been missed out on in previous clock designs, is that in a photographic darkroom. What better than a red

Practical Wireless, September 1975

★ components list

Resistors

| | | |
|------------------|-------------------|-------------------|
| R1 470k Ω | R6 2.2k Ω | R11 1k Ω |
| R2 1k Ω | R7 1.5k Ω | R12 1.5k Ω |
| R3 2.2k Ω | R8 1.5k Ω | R13 1.5k Ω |
| R4 2.2k Ω | R9 1.5k Ω | R14 1.5k Ω |
| R5 2.2k Ω | R10 1.5k Ω | R15 1k Ω |

All $\frac{1}{4}$ or $\frac{1}{2}$ W 5%

Capacitors

| | |
|---------------------|----------------------------|
| C1 1000 μ F 25V | C2 0.022 μ F polyester |
| C3 1000pF polyester | |

Semiconductors

| | |
|----------------------|--------------------------|
| D1 1N4001 | D2/3/4 1N4148 |
| LED1/2/3/4 MAN3640 | LED5 General purpose LED |
| Tr1 to 11 inc ZTX108 | |
| IC1 AY-5-1224 | |

All available from PW advertisers

Miscellaneous

T1, Transformer 240V/12V 100mA, see text. SK1/PLG1, 5 pin DIN plug and socket. S3, SP on/off slide switch. S4, 2P changeover pushbutton unit. S5, SP push-to-make switch. 3-way mains lead with grommet and clamp. Cabinet material. Feet, plastic or rubber. Set of PCB's (3). Timer control box, 75 x 50 x 25mm (3 x 2 x 1in.) with lid. Veroboard pins, 0.1in. (18). Sockets for LED's and IC1, see text.

A specially wound transformer is available from Foresight Electronics, 62 High Street, Croydon, Surrey for £1.54 inc. VAT/pp. The same firm can supply the three PCB's for £2.04 inc. VAT/pp.

LED display in a darkroom when printing on black and white paper? More will be said about stop clock applications when the control unit is described. Another advantage of keeping the extra stop clock components outside the main clock is that the overall size can be kept down.

For the same reason it was felt desirable to keep the current drain of the clock to a minimum, allowing use of a small transformer, and to this end, high efficiency seven segment LED displays are used. These are MAN3640 manufactured by Monsanto. Other types that have the correct pin configuration could be used but they will not give as much illumination.

FINAL CIRCUIT

The circuit for the complete clock, including the switch and DIN socket for the stop clock facility, is shown in Fig. 2. Notice that only three external diodes are used in association with the strobe line of the IC. These allow fast setting of hours and minutes at pins 1 and 16 respectively when the specific switch is closed. The diode going to pin 13 selects a 24 hour display. If a 12 hour display is required this diode should be left out.

The 1000pF capacitor between pin 3 and earth sets the multiplexing frequency and the 50Hz reference signal is fed to the input of the clock (pin 4) via a 470k Ω and a 1k Ω resistor. The junction of these resistors is taken to the DIN output socket so that an external switch can earth the signal at this point thus stopping the clock. In order to reset the clock to zero, from the remote unit, it is necessary to take an output from the strobe line and pin 15 to the

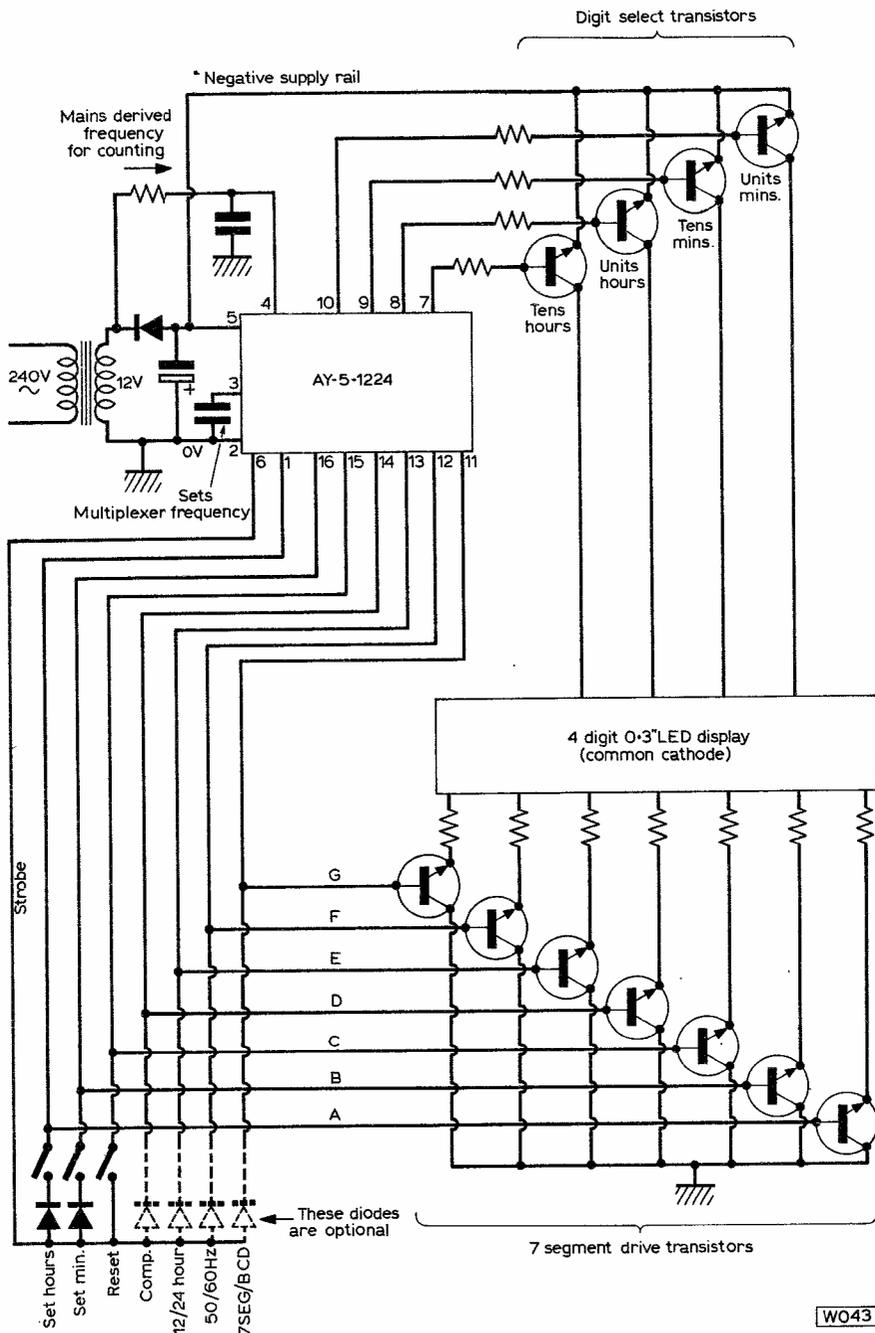


Fig. 1: General application circuit for the AY-5-1224 integrated circuit, emphasizing the few components needed externally.

DIN socket. The rest of the circuitry is associated with the LED display.

ZTX108 transistors are used for digit select and segment drive. With the component values given the maximum current per segment is 10mA thus the common cathode digit select transistor never has to carry more than 70mA, well within the capabilities of the ZTX108. As the digits are multiplexed 70mA represents the total display current apart from the decimal point (a further 15mA). Note that to get a balance in illumination level it is necessary to

drive the decimal point of the units of hours digit through 1kΩ while the rest of the digit segments are driven through 1.5kΩ. The IC itself draws 10mA. This gives a MAXIMUM current for the whole circuit of 95mA hence the transformer has to be rated at 10mA at 12V rms to be on the safe side.

Unfortunately there are transformers and transformers! There are several types available on the market which will serve the purpose but they are either large and will not fit the circuit board or they are rather optimistically rated and tend to get hot

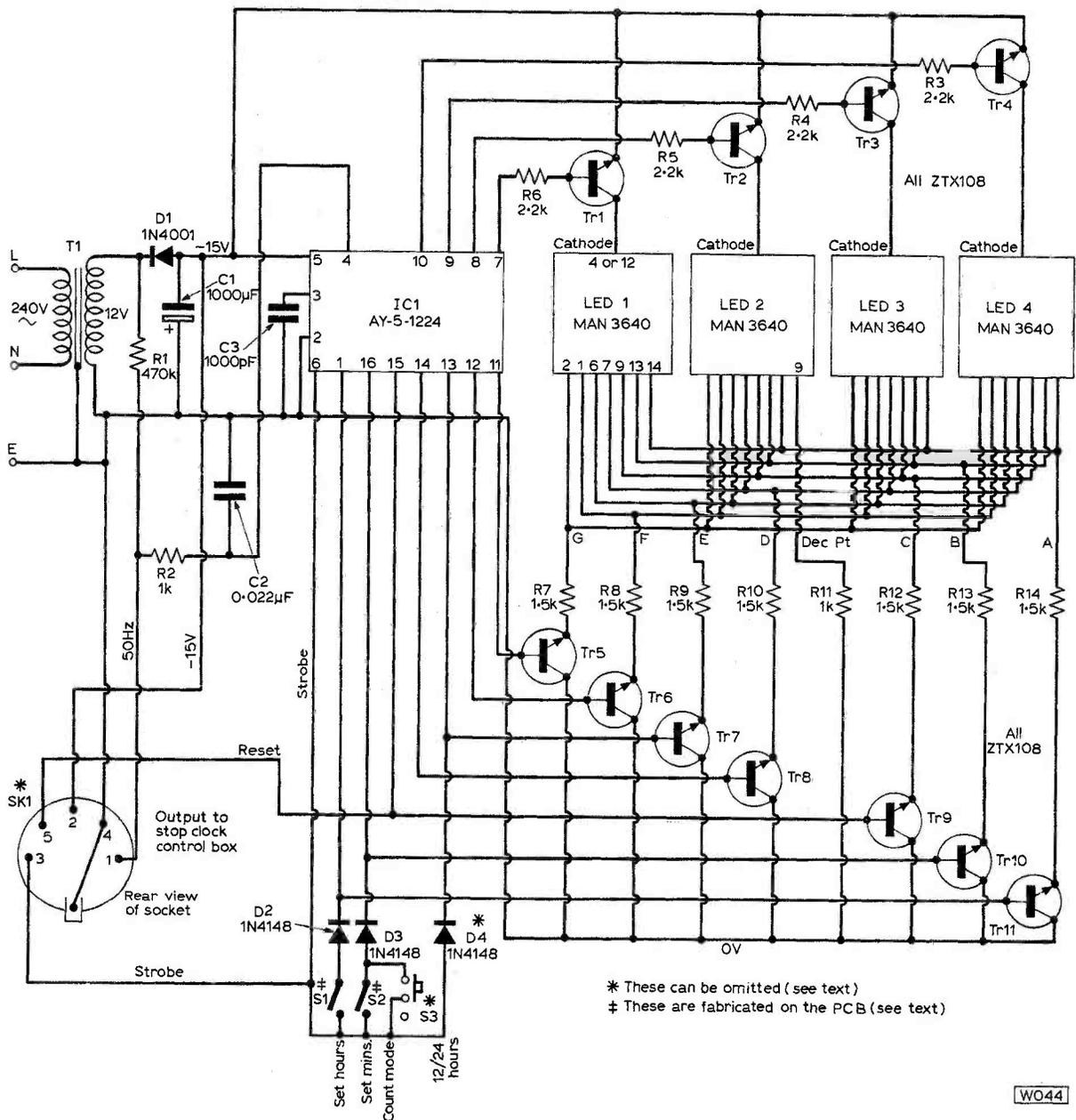


Fig. 2: Circuit of the clock described in the article, including the switch and socket required for the stop-clock facility.

when operating continuously at the full circuit current. It is for this reason that we have arranged for a special transformer to be wound. It can be operated at the maximum current in the unventilated cabinet without overheating and has been specially designed to plug directly into our printed board layout. Before using other 100mA rated transformers check their temperature rise when operated over a period of half an hour or more at full load.

CONSTRUCTION

The circuit is built on three printed circuit boards which are designated:—the front panel, Fig. 3, which carries the LED displays; the rear panel Fig. 4, carry-

ing the external connecting socket and switches; and the main board Fig. 5, which embodies the rest of the circuitry. At an early stage the constructor must decide whether or not he wants to use the stop clock option. If this is not necessary and only a desk or mantelpiece clock is required items SK1 and S3 can be omitted. At the same time it is not necessary to cut the fixing holes for them in the rear panel. If it is decided to keep the option open, drill out the fixing holes for these components and drill and file the small slot for S3. The fixing holes and slot are marked in the printed circuit layout for the rear panel. Make sure that the two holes between the copper lands near the top of the rear panel are


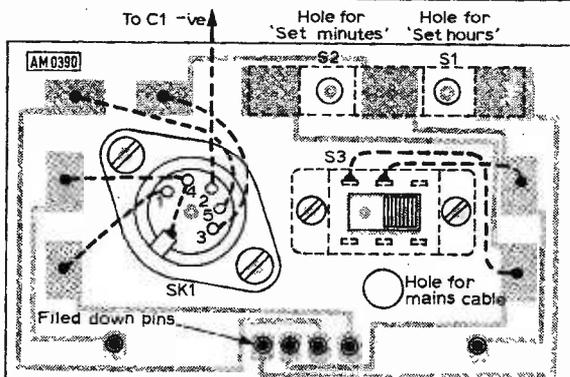
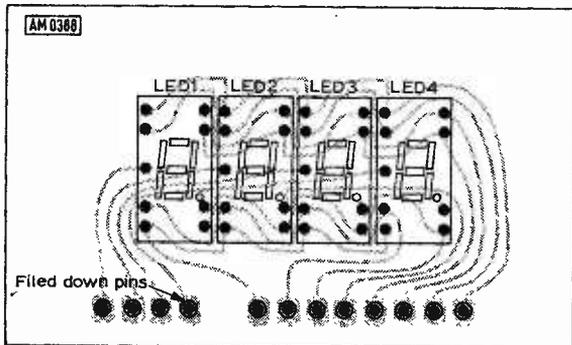
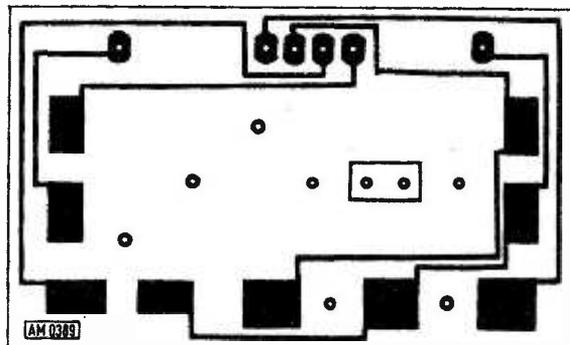
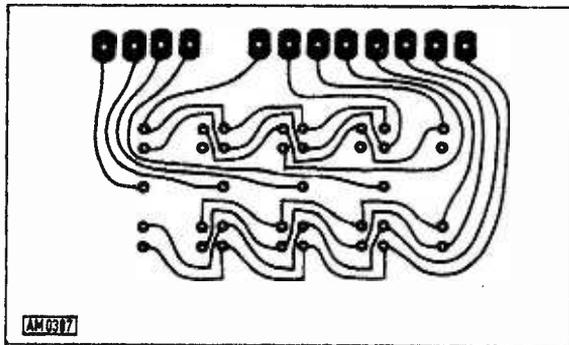


Fig. 3 left, and Fig. 4 above, show the end PCB's actual size and component layout. Fig. 4a below, shows the details of the two switches S1 and S2, constructed from phosphor bronze strip.

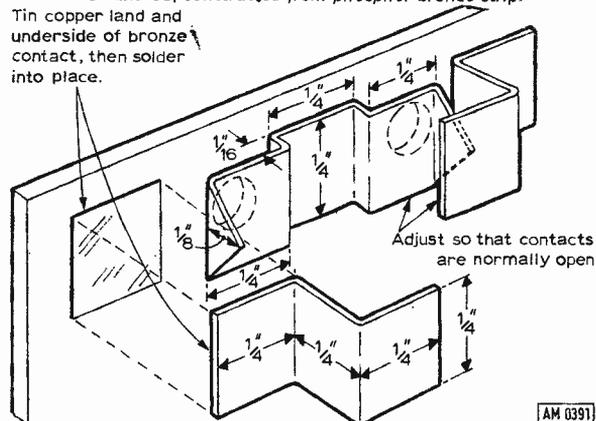Tin copper land and underside of bronze contact, then solder into place.



Insert and bolt into place SK1 and S3 then connect their tags to the copper lands of the board as shown in Fig. 4. With reference to Fig. 4a, cut and bend springy phosphor bronze (a piece of draught excluder strip will do nicely) into the shape of the contacts for S1 and S2. These contacts should be soldered on their respective copper lands having first tinned the underside of each contact where it comes into contact with the land. Now proceed to assemble the main board.

When installing the transformer make sure to cut the spills off short after they have been soldered into place, to prevent any possibility of them shorting against the bottom of the case on final assembly. Now decide on whether 12 or 24 hour display is required. For stop clock operation it might be best to go for 24 hour display so that one can time up to 23 minutes 59 seconds when switched to time in minutes and seconds mode. For a 24 hour display insert D4 but this diode can be omitted if a 12 hour

drilled out to about $\frac{1}{8}$ inch (enough for a matchstick to slide through). These holes are to facilitate operation of the hours and minutes set switches S1 and S2.

Once all the holes are drilled start assembly by inserting all the Veroboard pins into their holes on the front and rear panels. Pins for 0.1in veroboard were used in the prototype and these require a suitable hole to ensure a tight fit. They should be inserted from the COPPER side of the board and pressed gently into place until they are firmly gripped in their holes. DO NOT SOLDER THEM IN AT THIS STAGE. If improvised pins are used trim off any excess which protrudes on the top side, with a pair of strong side cutters or a fine hacksaw blade, and then carefully file the cut end flush with the board. Try not to make file marks on the board surface.

Finish off the top side (non copper side) of the front and rear panels by painting with a matt black paint.

When the paint is dry insert and solder the LED sockets into place. The LEDs themselves are inserted later. Notice that only 9 of the 14 possible locations are drilled for each socket. This is to allow space on the foil side of the board for the large number of conductors. Because of this remove, or bend flat, the pins of the socket which are not required. Be very careful with the soldering because the lands are not very large and it is very easy to get a blob of solder bridging across the narrowly spaced conductors. Note that the spacing between socket locations has been set with the Texas Instruments "Low Profile" DIL socket in mind. Other types of sockets might be too wide in which case it might be necessary to file material off the sides of each socket until the four fit neatly together. Put the front panel aside and start assembly of the rear panel.

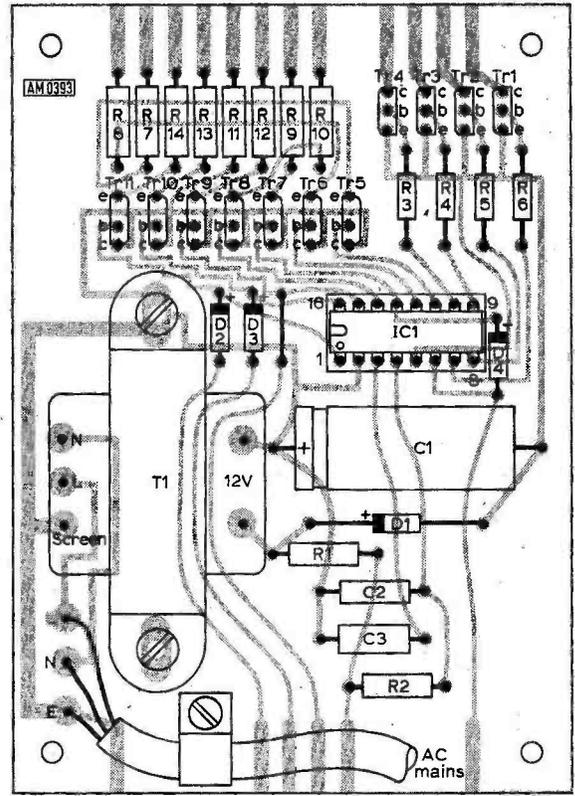
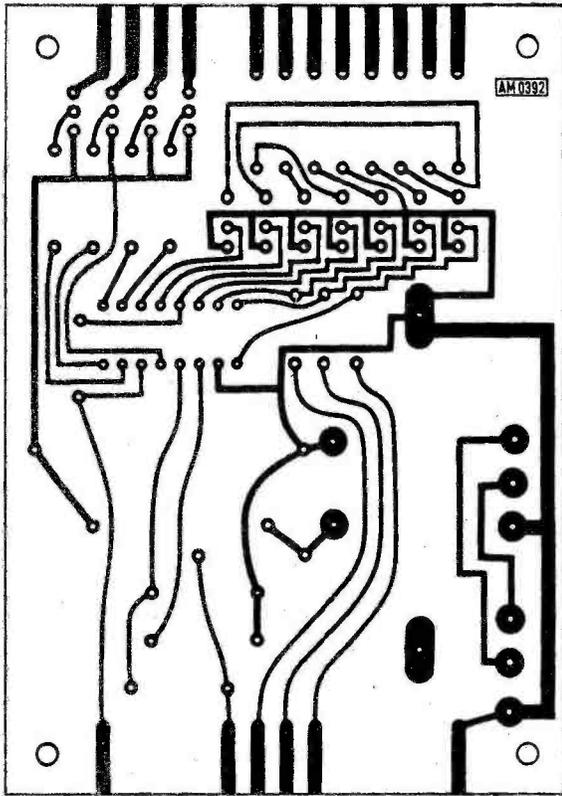


Fig. 5: Main PCB, left, actual size and component layout, right.

version is required, with preceding zeros ripple blanked.

Be careful about the polarity of the small diodes and in particular make sure that the transistors are connected correctly. It should be noted that the four digit select transistors, which are on their own, are orientated differently from the rest of the transistors! Ideally, use a 16 pin socket to carry IC1 otherwise one may invalidate any manufacturer's guarantee. If it is decided to solder it into place take all the necessary precautions to prevent damage from static charges. When installing IC1 be especially careful that it is inserted the correct way round! See Fig. 5. As already said, take care not to allow any solder to bridge the gaps between the narrowly spaced conductors in the vicinity of the transistors. Do not solder the mains cable into place just yet.



It is now necessary to join the three boards together. The three boards should be brought together by supporting on books so that the pins on the front and rear panels register exactly with the lands on the main board, see photograph. Make sure that the end panels are at right angles to the main board and then apply a generous amount of solder to each pin, ensuring that the pad on the end panel is wetted at the same time as the length of the pin is soldered to the main board. This operation should be done very carefully as the pins carry the electronic signals

round the corner on to the end panels as well as providing mechanical support to the main board.

It only remains to fix the mains cable into place with the cable clamp and solder the three cores into their respective holes on the main board. Use the smallest diameter three core cable available and make sure that the inlet hole is suitably grommetted. Apart from testing and assembly into the final case the clock itself is now finished. Plug in IC1 and the four LED displays, taking very great care that they are the right way round. If in doubt make sure that that the decimal point can be seen at the bottom right hand corner of the device when viewed from the front.

Apply power and the LEDs should display a group of digits. If S3 is switched to count in minutes and seconds the right hand digit should immediately start counting at second intervals. If this is the case put S3 into Hours and Minutes display mode and the rapid counting should stop and the right hand digit should change once a minute. Try the 'hours' and 'minutes' set switches by pushing a matchstick into each hole in turn until the respective contacts are brought together. Check that the connections going to SK1 are functioning correctly. Firstly set S3 to count minutes and seconds and then using a short piece of wire short pins 3 and 5 (of SK1) together; the display should reset to "All Zeros". Remove this shorting link and then short pins 1 and 4;

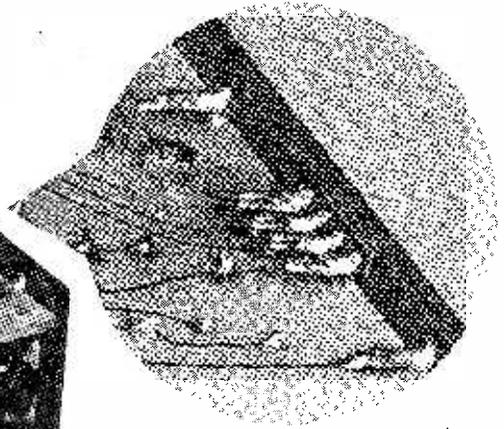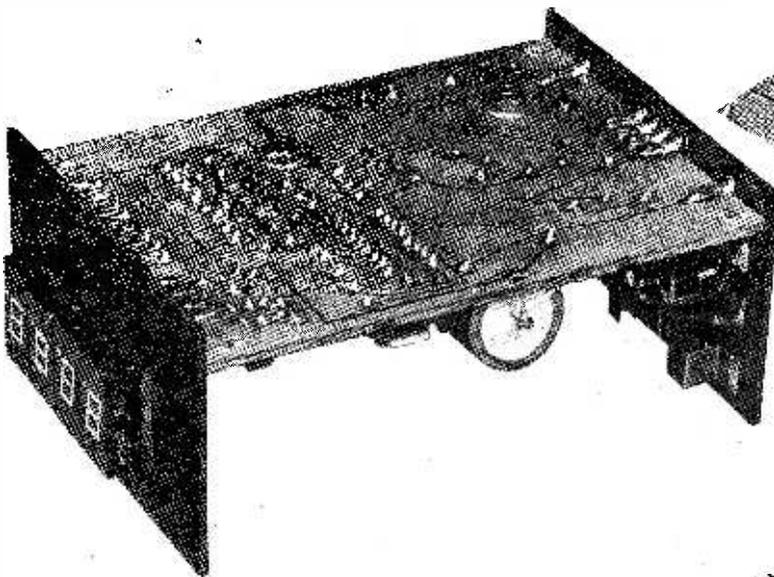
Photograph of the underside of the electronic clock with an enlargement to show how the printed circuit board lands are soldered to the pins in the end boards.



The illustration below is of the two simple shapes forming the cabinet for the clock. Inside dimensions are given for the inner lower part, the upper outer part being made to fit. In this prototype the metal used was 16SWG aluminium.

this should stop the counting as the 50Hz input is effectively earthed.

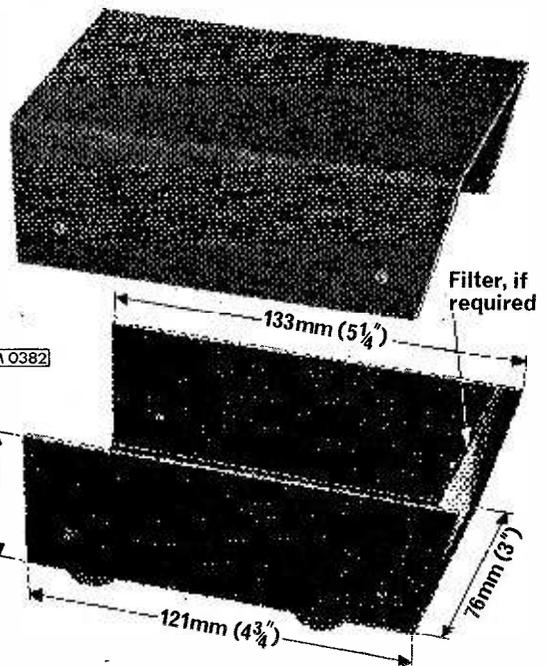There is the option of using the fifth terminal (No. 2), and in the prototype this was connected, via a short wire, to the negative rail of the clock (the negative lead of C1) as it was felt that a small current in the remote control unit could be used to light an LED showing that all was well and that the clock was working.



THE CABINET

The cabinet is made from two pieces of folded aluminium which slide over each other and held in place with self-tapping screws. A piece of red perspex is Araldited in a vertical position at the front end of the narrower channel to form the front "window". This should be so positioned that the LED displays just touch it when the rear panel of the clock is JUST inside the back end of the channel. The assembled "bedstead" chassis should be fixed into position with self-tapping screws but do not forget the earthing solder tag which has to be connected with a flexible lead to the point where the mains inlet cable is connected on the underside of the board. This earthing of the case is MOST IMPORTANT because it is metal and we suggest that in some applications one could be in a photographic darkroom where there is always a certain amount of dampness present!

TIMER OPERATION

As a photographic enlarger timer, the mode switch should be set to count in minutes and seconds when the clock can be stopped or started with a remote switch across pins 1 and 4 of the DIN socket. A simple single-contact push switch connected across pins 3 and 5 will reset to zero. It would be very

simple to use a ganged switch to start and stop the clock which would also switch the enlarger lamp on and off. One can use a spare contact on the simple remote control unit, Fig. 6, to switch an LED on and off. When it is on it reminds the operator that the clock is timing. This is where the -15V source came in useful. It is quite conceivable that one could use this same current source to operate a relay. But be careful, do not draw more than 10 or 20mA from the supply. This should be intermittent with a duty cycle of about 50/50 to avoid overheating the transformer.

The clock could prove very useful in school

continued on page 414

Practical Wireless, September 1975

DUAL CONVERSION receiver

PART:2

F. G. RAYER

AUDIO BOARD

Fig. 7 shows both sides of this board, which is prepared and wired in a similar way to the earlier boards already described. Solder a red flexible lead from C29 for battery positive and a lead from C28 negative for the speaker the other side being returned to chassis. A jack socket is fitted to allow a speaker or phones to be plugged in. A 15Ω speaker is most suitable, being attached to a baffle or enclosed within the cabinet.

The amplifier is tested by connecting C23 to an audio signal, or VR2. The unit has considerable gain so that it is easy to overload with strong signals. This is useful for weak signals, but naturally means that VR2 **must** be turned well back for stronger transmissions. The amplifier alone will draw about 10 to 12mA with no signal, rising to 25 to 50mA with full volume. The quiescent current can be adjusted by changing R24, for a 39Ω resistor with a 100Ω pre-set in series, if particular transistors should require this sort of adjustment.


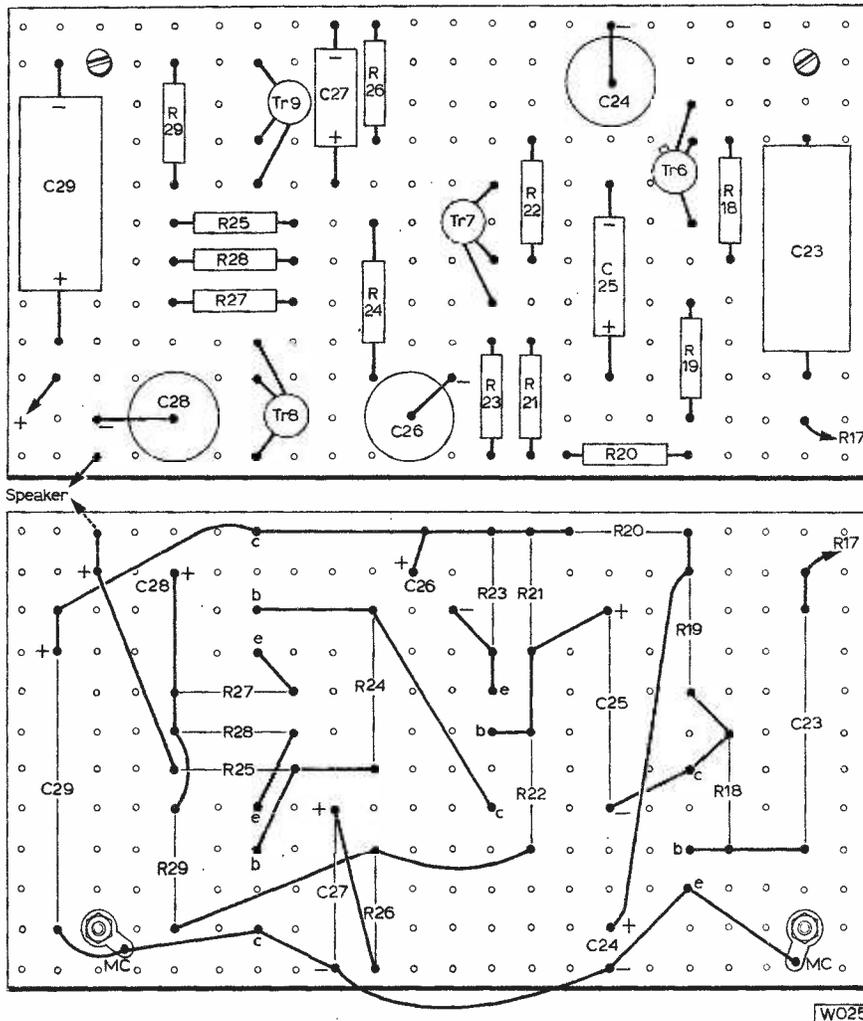


Fig. 7: Audio amplifier board, showing both component side and wiring side. Recommended speaker impedance for this circuit is 15Ω, although a jack socket is provided for headphones should they be preferred.

Fig. 8: Topside view of the chassis, giving positions of boards in relation to VR1, VR2 and VC2. Holes for the front dial are made by following the paper template supplied by the dial manufacturer.

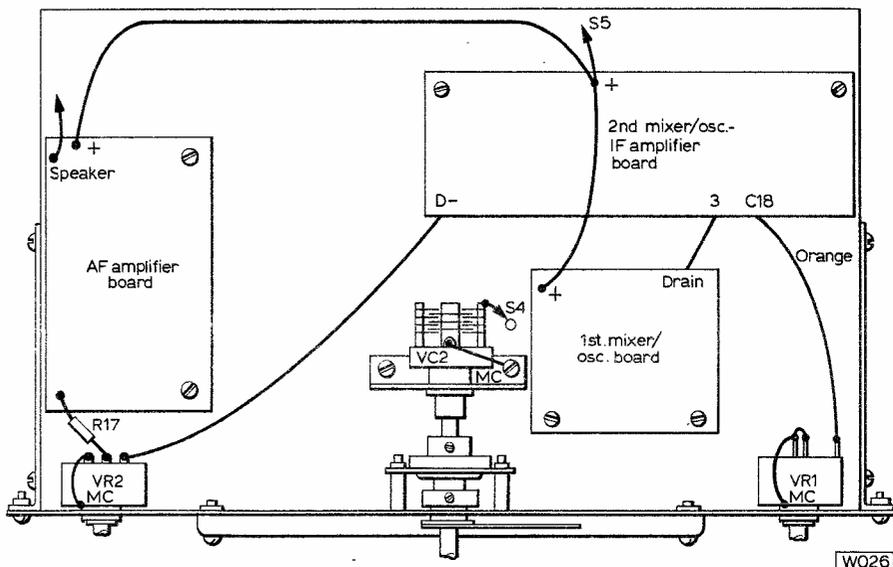

GENERAL CONSTRUCTION

For a rigid assembly, panel and chassis are fixed together with side brackets, as in Fig. 8. This also shows the position of the circuit boards. Holes for the dial are made by following the paper template provided. VC2 is supported on a strong bracket to avoid any movement and it should line up correctly with the drive. If necessary, a little adjustment to the position of the spindle can be obtained by making the bracket hole larger than necessary and placing a washer each side the bracket. The dial cursor is fixed to a collar which can be moved. This and the shaft are locked with the cursor at zero on the dial and VC2 fully closed.

Connect all board positive leads as shown and run a lead down, (Fig. 9), to S5 which has 3 positions,

CW/SSB, AM and OFF. S6 is wired so that the circuit to R33 is completed in the second "on" position only. The receiver can be tested on AM reception only with the BFO and VC3 omitted.

Fig. 9 shows the layout and connections under the chassis. Check that VC1 is mounted just clear of the side and that the fixing nuts of the aerial coils are only done up finger tight. The pins should be cleaned if necessary, and not 'cooked' with the iron when soldering connections to them.

Ceramic pre-sets are used for the oscillator circuit and mounted with 8BA bolts. The beehive air-spaced type of trimmers would probably be better as several turns are needed to move them from maximum to minimum value. As each trimmer proved to be set near half value, 30pF, 50pF or 60pF trimmers would also appear to be suitable.

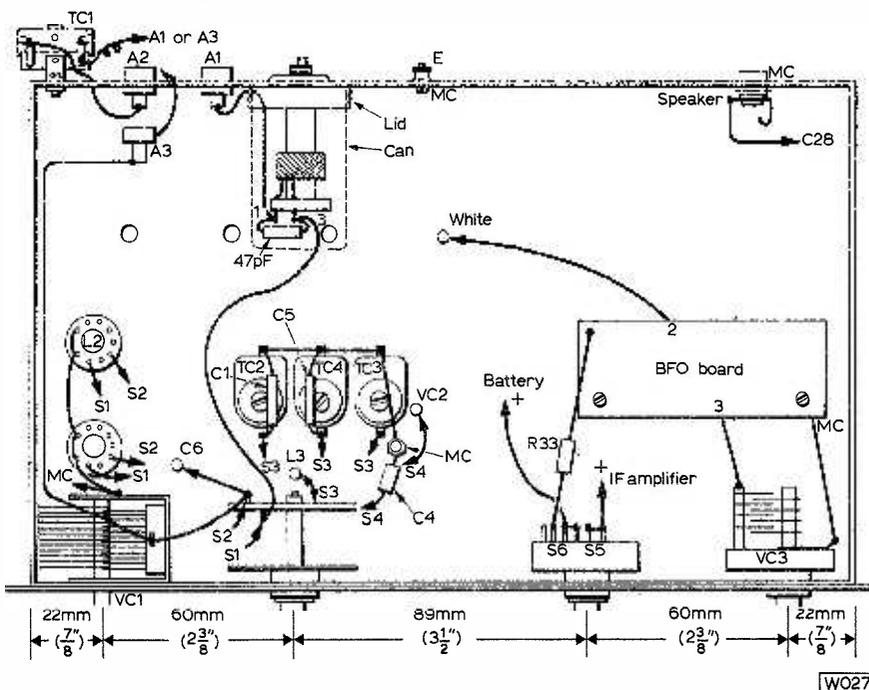


Fig. 9: Aerial tune (VC1), BFO pitch (VC2) and trimmers viewed from underneath. The diagram also shows the positioning of the BFO board and the three alternate aerial sockets, A1, A2 and A3.

BANDSWITCH

The bandswitch is of a type in which contacts are fitted both sides of an insulated wafer. Switch connections are shown in Fig. 10, contacts S1 and S4 are separated from S2 and S3, for clarity.

If reference is also made to Fig. 1, no error should arise here as, with this type of switch, contacts can be easily seen. Somewhat similar rotary switches with hidden contacts are also available, and with these a check should be made with a meter.

If a fully-insulated speaker jack is used the outer or sleeve tag must be connected to the chassis or negative on the audio amplifier.

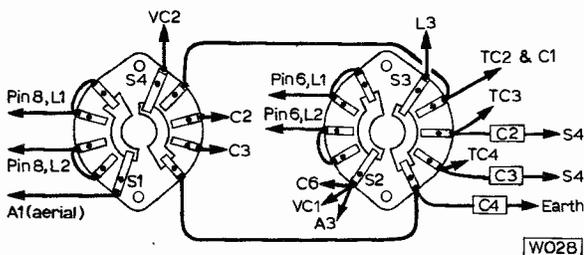


Fig. 10: Bandswitching for the Dual Conversion receiver is achieved with the wafer switch shown above. In the prototype only one wafer was used with contacts mounted both sides.

ALIGNMENT

A signal generator or accurately calibrated receiver will prove useful when adjusting the various circuits, but satisfactory alignment is possible without either.

465kHz IF. If a generator is available, couple it loosely to Tr3, placing an insulated lead near Tr3 should be sufficient. Adjust the five cores of IFT2, IFT3 and IFT4 for best results. Each core should have a definite peak and need little movement. A correctly shaped tool, such as that available from the IFT maker, should be used, as a wedge-shaped metal blade would probably crack the cores and upset the adjustments.

If no generator is available, wait until some signal can be accurately tuned in, then peak up the cores for best results. The signal should be relatively weak, with VR1 turned back and VR2 well towards maximum, so that adjustments are not masked by the AGC action.

Second Mixer. Rotate the core of L4 until the oscillator carrier is found at about 6MHz with a receiver. Alternatively, set the core with about 6mm ($\frac{1}{4}$ in) of thread projecting. Now peak both cores of IFT1 for best volume with a 5.5MHz signal from the generator loosely coupled to pin 3, slightly adjusting L4 as necessary to peak up the signal.

If no generator or receiver is available tune in any signal and adjust IFT1 and L4. Do this a little at a time to peak the signal, meanwhile rocking the tuning control from side to side if necessary. Should no signals be received, temporarily connect an aerial through a 100pF capacitor to pin 3 of IFT1. Breakthrough is almost certain to arise, and the signal can be peaked up by adjusting IFT1 and L4. Subsequently, shift each core slightly to avoid this unwanted signal and later peak up these cores when signals can be tuned in.

First Oscillator. If a receiver is available, it is easy to set the core of L3, on 160m first, as described. The trimmers can then be adjusted to give the coverages listed. Alternatively, adjust the core of L3 until some Top Band signal is received. When L3 and L4 are suitably adjusted lock each with a fixing nut. The other trimmers are then adjusted, with the bandswitch in the appropriate position, until the other amateur bands are found.

Aerial Circuit. This is peaked with VC1 for best volume. If necessary, adjust L1 or L2 until both bands fall within the swing of VC1. It will be apparent that it is possible to obtain four other bands by deliberately tuning the aerial circuit to the second channel, or image frequencies. The second channel is IF x 2 from the wanted signal, that is 11MHz, if the IF is 5.5MHz. For example, the oscillator tunes 7.15 to 7.55MHz for Top Band so the second channel for this range is 12.65 to 13.05MHz, which is remote from the wanted frequencies but which may provide some signals if VC1 is deliberately set to minimum capacitance. A similar effect is observed with some commercial equipment using this method of tuning but it does not indicate a fault.

IFT1 is actually set to some frequency near 5.5MHz, which avoids interference, and L4 adjusted to convert this to 465kHz. Such adjustments are easily made a little at a time when the receiver is working and it should be clear that the operation of the receiver does not depend on IFT1 being tuned to exactly 5.5MHz.

Dial calibration is best made with a crystal marker or similar after finishing alignment adjustments. The scale is marked 0 to 100 will be useful when first checking the band coverage.

BFO CIRCUIT

Fig. 11 shows the circuit of the BFO with Tr10 an oscillator working on approximately 465kHz, the frequency being adjusted by the BFO pitch control VC3. Switch S6 brings the BFO into operation in its last position only, for CW (Morse) and SSB (single sideband) reception. The value of VC3 is not too critical as long as sufficient shift of the BFO frequency is possible. Note that connections to 4 and 5 must be as shown, for the circuit to operate.

If, however, the circuit of the BFO appears not to be oscillating, evidenced by the lack of a beat note on AM or CW signals or inability to resolve SSB signals, the connections to pins 4 and 5 on the coil should be reversed.

ASSEMBLY AND ADJUSTMENT

The BFO is assembled as in Fig. 12. A lead from the MC tag is provided for the moving plates tag of VC3 and the lead coded brown is for the fixed plates.

The lead coded white runs up through a hole, near IFT3. Coupling or injection is to the base of Tr5 so that the BFO level is raised for diode D1.

Coupling was found to be suitable when the thin insulated lead from the BFO looped around the body of C19. Coupling is not in any way critical. However, if coupling is too tight, sensitivity to all signals is unnecessarily reduced. On the other hand, if coupling is very small, strong SSB signals will sound like

badly over-modulated AM, or will not be resolved at all. If VR2 is near maximum and VR1 is turned back to obtain reasonable volume, and SSB and CW signals are then received well, the amount of coupling to the base circuit of Tr5 is optimum.

To obtain a satisfactory frequency range for VC3 it is necessary to adjust the core of the BFO inductor which can be done by tuning in an AM signal,

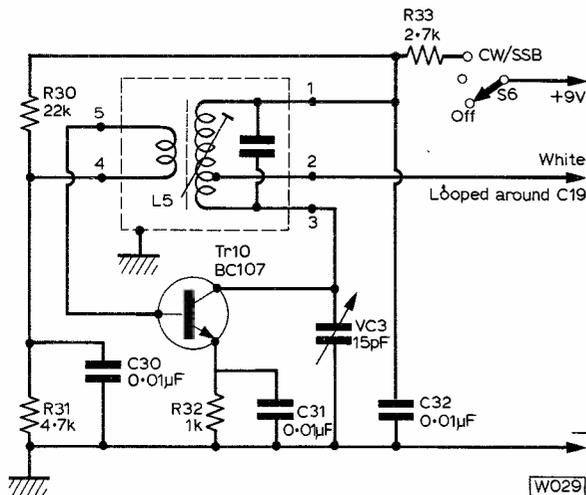


Fig. 11: Complete circuit of the BFO. The oscillator transistor Tr10 works at approximately 465kHz, frequency being varied by VC3, after rough adjustment of the core in L5.

with VC3 half open, and adjusting the BFO coil until a loud heterodyne whistle is heard. The correct position is the zero-beat or middle setting. An audio tone, rising in pitch, is then obtained if VC3 is rotated either way. Check with one or two other signals to make sure that a harmonic of the BFO, reaching the aerial circuit, is not responsible.

When receiving CW, adjust VC3 to the position


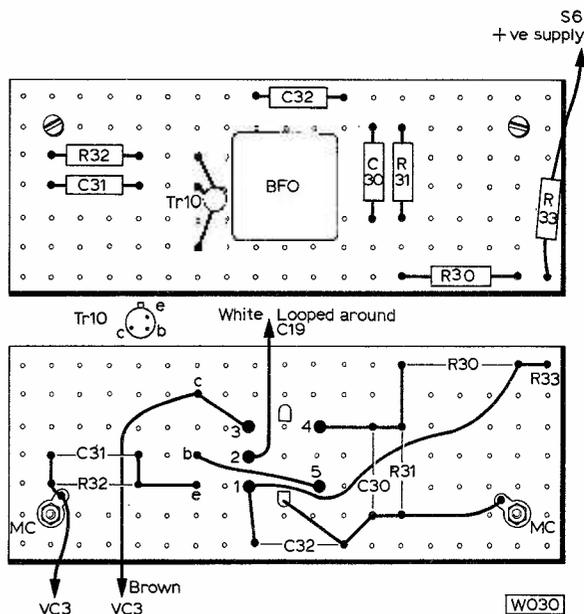


Fig. 12: Underside and topside of BFO board. The output signal is taken via an insulated lead, looped around C19.

giving best reception, which may prove to be either side of the zero position. To receive SSB it is essential to adjust VC3 carefully, and to the required side of its zero position. The off-set used for 20m is the opposite to that on 40, 80 and 160m. The way in which this control operates will soon become clear in use. Remember that for all but weak signals it is essential to reduce gain prior to the detector, by turning back VR1.

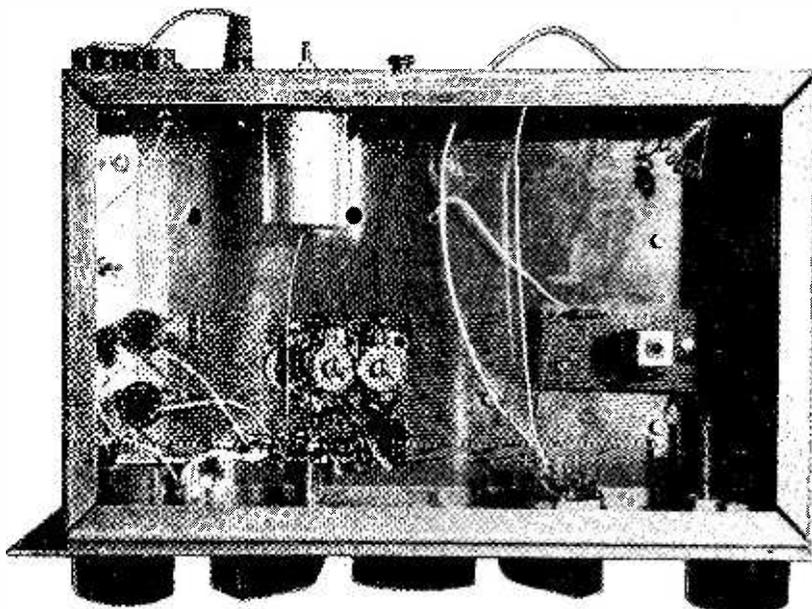5.5MHz TRAP

This is an optional item which can be added at any time. Its purpose is to reduce the strength of any unwanted signals which may be using frequencies near to that of the first IF, and which are



Underside photograph showing details of the universal chassis used and the 5.5MHz trap, situated on the rear drop of the receiver.

continued on page 403


SW Pre-Amplifier

STEVE MONEY G3FZX

IN the less expensive versions of the communications type receiver the more commonly met deficiencies in short wave performance are lack of sensitivity and poor front-end selectivity on the higher frequency bands. With such a receiver the bands above about 12MHz may well appear to be completely dead at a time when a more expensive receiver can still produce a lively selection of signals. As a result the listener using the cheaper receiver may be failing to hear many stations simply because of the poor performance of his receiving equipment.

SELECTIVITY


In the simpler receivers the selectivity of the main IF amplifier is generally adequate for the separation of signals on adjacent channels, but the selectivity of the tuned circuits ahead of the mixer stage often leaves a lot to be desired. Since this type of receiver is usually a single conversion superheterodyne having an IF of around 465kHz, the effect of poor HF selectivity will be severe second channel or "image" interference on the high frequency bands. Thus, on the 14MHz amateur band severe breakthrough from broadcast stations operating in the 15MHz band is frequently experienced. On the other bands, reception may be marred by CW or teleprinter interference from stations operating roughly 1MHz, or twice the IF, above the frequency of the

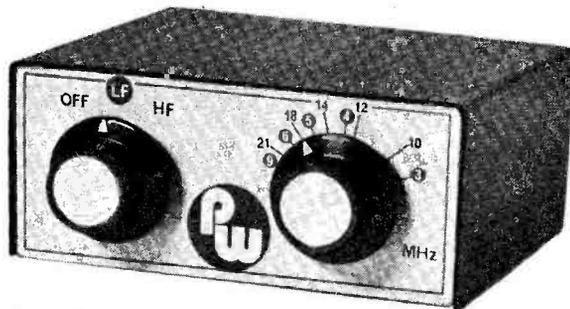

desired station. This assumes that the receiver follows the usual practice in which the local oscillator for the mixer stage is operated at a frequency above that of the signal.

The problem of lack of receiver sensitivity on the higher frequencies can be readily solved by merely adding a pre-amplifier stage to the main receiver. However, this solution is likely to aggravate the second channel interference problem unless some additional selectivity is provided in the pre-amplifier unit. This add-on unit would then effectively become a preselector amplifier and, with its aid, the performance of the receiver, in terms of both its sensitivity and selectivity, can be greatly improved.

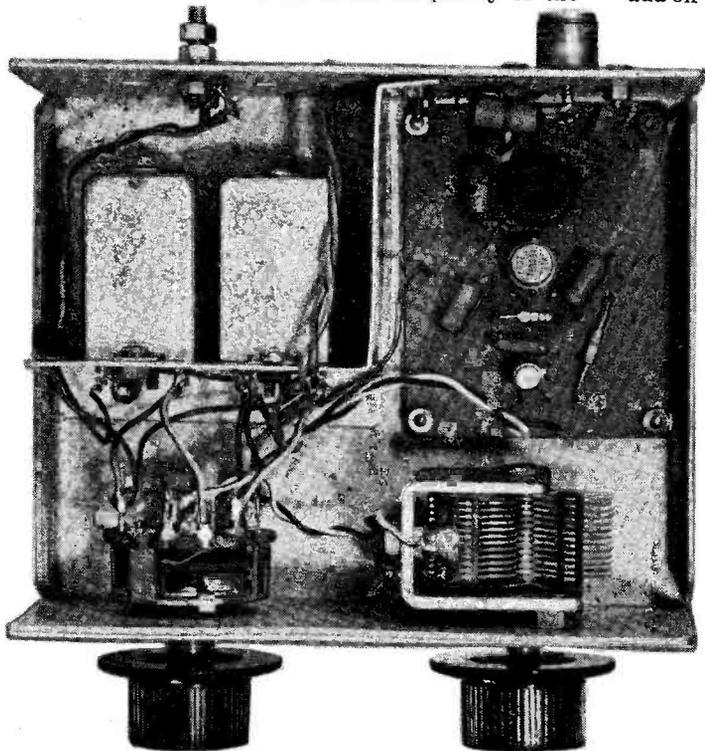For the relatively small cost of making a suitable add-on unit the user of a simple inexpensive receiver,



Interior view from above, of the 'U' shaped chassis, showing details of the PCB, coils and switch layout. The two coils, L1/L2 are mounted on a small screen with their bases towards the front panel to facilitate short wiring.

is able to compete on rather more favourable terms with other listeners fortunate enough to have more expensive equipment.

INTEGRATED AMPLIFIER

In this article a pre-amplifier unit is described which makes use of an integrated circuit amplifier to provide the additional gain. This gives the advantage of simplicity in construction since few external components are needed with the IC. A Fairchild type μ A703 RF/IF amplifier was chosen for this purpose since it is inexpensive and is readily obtainable.

Basically the μ A703, which has six lead wires, is a single stage two transistor amplifier of the emitter-coupled type. A third transistor provides the constant-current feed for the emitters of the differential amplifier stage. The chip also incorporates resistors and diodes to provide the correct bias for the amplifier and allow the supply to be decoupled. Since it is difficult to fabricate large value capacitors on an IC chip, the decoupling capacitors have to be wired externally.

The type of amplifier circuit used and its small physical size ensure that the feedback of signals from output to input, inside the amplifier, is extremely small. This means that stable operation of the circuit is readily achieved without the need for any form of neutralisation. The μ A703 has a forward transconductance of some 30 mmhos at the frequencies in use, so there is no lack of available gain.

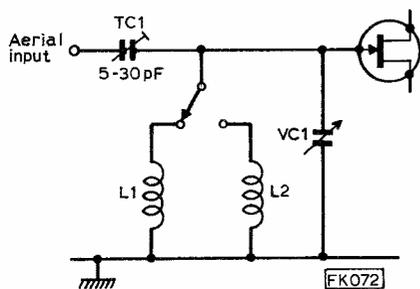


Fig. 1: Alternative aerial coupling circuit to that used in the prototype, but of a simpler design.

MATCHING STAGE

For the short wave bands, the input impedance of the μ A703 amplifier is about 15000 Ω . If this impedance were connected directly across the input tuned circuit, it would cause severe shunt loading, reducing the effective Q and hence the selectivity of the input tuned circuit.

The effects of loading on the tuned circuit can be reduced by using a coupling winding on the tuning coil to feed the amplifier input. It then becomes possible to provide a rough impedance match over most of the tuning range, although there will be a reduction in the signal voltage fed to the amplifier because of the step-down transformer action of the coupling winding. Also the need to switch the extra winding on the coils makes band changing arrangements more complicated.

An alternative impedance matching technique makes use of a field-effect transistor as a source follower stage between the tuned circuit and the amplifier input. This stage will have a very high input impedance and a low output impedance thus providing the required buffering action between the

tuned circuit and the amplifier. Since the gain of the source follower is nearly unity almost all of the signal is passed to the amplifier. The source follower has an input impedance of more than 1M Ω . It will therefore produce virtually no loading effect on the input tuned circuit, permitting maximum operating Q and hence high selectivity to be maintained.

To ensure that the correct bias conditions are maintained within the 703 amplifier, it is recom-

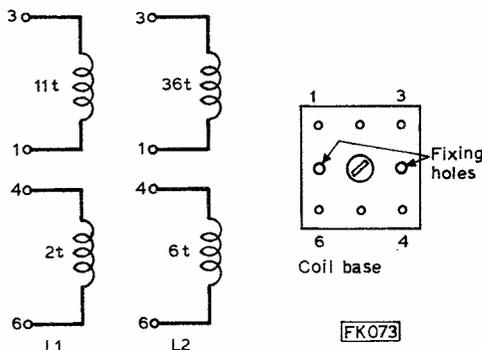


Fig. 2: L1/L2 coil winding details and pin configuration.

mended that the DC resistance of the external circuit connected between the input terminals of the 703 should be less than 1000 Ω . This is achieved here by connecting a 470 Ω resistor across the 703 input terminals.

If the output of the source follower transistor were connected directly to the input of the 703 some of the current from the transistor would flow into the amplifier input circuit and upset the internal biasing conditions. To avoid this, the source follower output is coupled through a capacitor to the 703 input. Although the 470 Ω resistor providing the bias path for the 703 is effectively shunted across the output of the source follower, it has little effect upon the signal level fed to the 703 amplifier.

INPUT TUNING

For most SW listeners the more interesting of the bands lie within the range 3MHz to 25MHz. This range can be covered using only two switched coils. The first coil is used to tune from 3MHz to 10MHz whilst the second covers frequencies from say 9MHz up to about 27MHz. For frequencies below about 3MHz it is likely that the performance of the receiver will be quite adequate without the need for a pre-amplifier. If it is desired to include the 28 to 30MHz amateur band, this should be possible by readjustment of the two tuning ranges. This may, however, involve some loss of coverage at the lower frequency end of the range.

Tuning is carried out by means of a single gang 365pF air spaced variable capacitor. In the present climate of component shortages it may be difficult to obtain the particular type of tuning capacitor specified. As an alternative almost any air spaced variable capacitor of small physical size and with a maximum capacitance of 350 to 500pF should be suitable. A 208+176pF dual gang transistor radio type could be used with the two sections connected in parallel to give 384pF. Although the tuning is fairly sharp at the higher frequencies it should not be necessary to fit a slow motion drive to the capacitor.

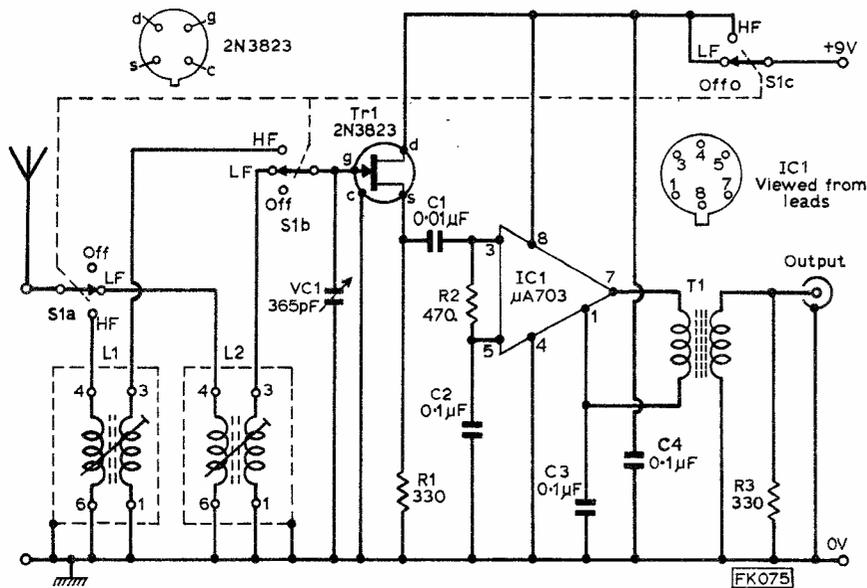


Fig. 3: Complete circuit diagram of the SW Pre-amplifier giving details of IC1 (μ A703) and Tr1 (2N3823) base connections.

The signal from the aerial is coupled to the tuned circuit through a link winding on each of the tuning coils. These windings are switched at the same time as the main tuning coil when the frequency range is selected. An alternative and simpler approach to coupling the aerial circuit is to feed the signal through a capacitor in series between the aerial terminal and the gate of the transistor, as shown in Fig. 1. This simple arrangement however is not as effective as the use of separate switched link windings.

Each of the tuning coils is wound, together with its aerial coupling winding, on to a 6mm diameter coil former. The formers used are Neosid types on a square base as used for the IF strips of older television receivers. The coil former is 35mm long and is mounted inside an aluminium screening can to reduce stray pick-up. Tuning coverage is adjusted by an iron dust core.

For the lower frequency range a tuning inductance of about $6.4\mu\text{H}$ is required, obtained by a winding of 36 turns of 28SWG enamelled wire close wound. The aerial coupling link consists of 6 turns of the

same wire wound on top of the main winding at the end near the coil former base.

The coil used for the high frequency range is wound with 24SWG enamelled wire and consists of 11 turns wound to form a single layer coil about 12.5mm ($\frac{1}{2}$ in) long. This means that the turns will be spaced out roughly one wire diameter apart. For this coil the required inductance of $0.8\mu\text{H}$ will be obtained when the iron dust core is inserted. The link winding is 2 turns of 24SWG wire, wound between the turns of the main coil at the base end of the coil former. Figure 2 gives details of the coil windings and also the pin connections on the coil bases. In Fig. 3 the complete circuit of the pre-amplifier unit is shown.

OUTPUT TRANSFORMER

Rather than use a second tuned circuit ganged to the input circuit, a broadband untuned transformer is used to couple the output from the pre-amplifier to the main receiver input. This simplifies range switching and reduces the possibility of amplifier instability.

To produce an efficient broadband RF transformer the toroidal type of construction is employed. In this, the core of the transformer takes the form of a doughnut shaped ring of powdered iron material. The windings are wound on the core by looping the turns through the central hole as shown in Fig. 4.

A T-50-2 type core is used for the transformer in

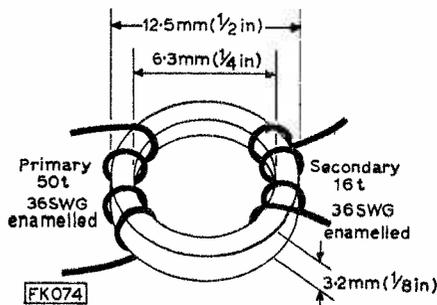


Fig. 4: Transformer T1, is of toroidal construction, efficient for broadband RF applications.

★ components list

| | |
|--|---------------------------|
| Resistors | |
| R1 330 Ω | R3 330 Ω |
| R2 470 Ω | All resistors 10% \pm W |
| Capacitors | |
| C1 0.01 μF | C3 0.1 μF |
| C2 0.1 μF | C4 0.1 μF |
| VC1 365pF air spaced variable | |
| Semiconductors | |
| Tr1 2N3823 (FET) | |
| IC1 μ A703 or equivalent | |
| Miscellaneous | |
| L1, L2 see text. S1, 3-pole 3-way wavechange switch. T1, toroidal core type T-50-2 Carbonyl 'E', available from TMP (Electronic Supplies), 3 Bryn Clyd, Leeswood, Mold, Clwyd, CH7 4RU. Equivalent cores (up to 30MHz) also available from other distributors. | |



10 + 0 = 20?

I would advise Sinclair Scientific owners to be careful if they use Mr. McBriar's "clear last entry" system (Letters, June) as this can give some very surprising results. I suggest they try the following key sequence to illustrate the point: 1,E,1,+ ,1,E,-, 9,9,+ . This gives the answer 2.0000 01 or, in effect, $10 + 0 = 20!$

This incorrect result is caused by an anomaly in the calculator's logic, but it can be avoided by limiting numbers to the range 10^{-50} to 10^{50} . — R. T. Russell (Kent).

So now you know!

I have been reading the various letters over the past few months concerning the reception of public service broadcasts and was particularly interested in the selection appearing in the June edition.

I have, for a long time, been concerned about this aspect of the law and, since I am employed in the legal profession, I have been able to go into the matter at some depth.

My first encounter was when I was about to purchase a communications receiver and the typical footnote on the ads. warned that for reception of certain broadcasts a licence "not generally available to the public" was required. Appreciating that a C.R. would cover trawlers, etc., I contacted the, then, Ministry of Posts & Telecommunications to find out about this licence. I was quite surprised to receive a reply stating "I should point out . . . that it is an offence contrary to the Wireless Telegraphy Act 1949 . . . to listen intentionally to broadcasts from . . . police, fire-

brigade, etc., and no licence can be issued . . ." (emphasis marks my own). The letter went on to state that the maximum fine for a first offence was £50, and £100 thereafter.

I, like D. H. Myers, could not accept that merely to listen intentionally was an offence and I buried myself in the statute books to read the Wireless Telegraphy Acts 1949 and 1967, the Marine, etc., Broadcasting (Offences) Act 1967 and the Post Office Act 1969. There was nothing I could find to support the view that to listen intentionally was, in itself, an offence. I was continually bothered by references to "authorised broadcasting stations". Could this, I thought, mean that we could not listen to Hilversum?

Determined to prove that Big Brother was NOT going to tell me what I could or could not listen to, I wrote back to the Ministry quoting what I had read and adding, with some relish, that even the dreaded Marine Broadcasting Offences Act did not prohibit LISTENING to such stations!

The Ministry took considerable trouble with their detailed reply:

(1) An authorised broadcasting station is defined (Statutory Instrument 1970 No. 548. The Wireless Telegraphy (Broadcast Licence Changes and Exemption Regulations 1970)) as "a station for the time being authorised to conduct a broadcasting service pursuant to the International Radiocommunications Regulations for the time being in force".

(2) "Broadcasting service" is defined in those Regulations as "a radiocommunication service . . . where the transmissions are intended for direct reception by the general public".

(3) Section 5(b)(1) of the Wireless Telegraphy Act 1949 makes clear that it is an offence . . . to use . . . any . . . apparatus with intent to obtain information as to the contents, sender or addressee of any message which . . . the person using the apparatus is (not) authorised by the Minister . . . to receive.

Surely, I thought, this had proved my very point—there **had** to be intent to obtain information! I stopped my correspondence with the Ministry at that point feeling somewhat pleased with myself.

A little later, in a legal journal, I found a decision of the High Court which was to shatter this. The case in question was "Paul

v Ministry of Posts". The Court had dismissed an appeal, holding that a man who listened to firebrigade messages without authority was guilty of an offence under Section 5(b)(1), although there was no intention to use this information for an improper use. (Anyone who has access to a copy of "The Times" for 6th March, 1973, can read the full facts for himself). It does, though, seem clear from this decision that merely to listen is to intend to "obtain information, etc." and is therefore an offence in itself! Of course, merely to tune to a public service by accident is specifically exempted by the same section but, those who continue to listen do so at their peril! Remembering that ignorance of the law is no excuse.

I STILL find this piece of law totally unacceptable and the day it is repealed will be a day to rejoice. As to whether freedom of choice is being curtailed is a matter of personal belief. I myself think it is. But, to criticise the, now, Home Office for seeking to uphold the law is not, in my opinion, at all fair. Whether the law is just or unjust, it must be accepted to be the law. The Home Office has been given the job of operating this sphere of law and they, like me, have to do their job whether they like it or not. Those of us who do not approve must take all proper steps to change the law not sit back damning a government department which has the unenviable task of operating the law.—(Name and address supplied).

Single handed

I recently built the PW Tele-Tennis by M. J. Hughes, and found it to be a great time-passer. However, one draw-back to the game is that it requires two players. For this reason, I cut the copper track of the OV line, feeding IC23 (NE555). A switch was then inserted, and mounted on the outside panel.

The outcome of this modification, is that the right-hand bat loses height, and provides a wall to bounce the ball off. Also, readers may like to know that it is impossible to beat the machine, when wired in this manner!—A. O'Brian (Sunderland).

Calculating danger

The paragraph in "Production lines" about the "Mickey Math" calculator has prompted me to put pen to paper about calculators in general.

As a sixth form student I have so far resisted the temptation to invest in a calculator for two main reasons:

(a) Financial—no elucidation needed!

(b) Not only do I consider that I don't need a calculator—I think that, as far as I, and others in school are concerned, it would be a positively bad thing.

After several years of handling "A" level equations I have acquired a sort of mental agility which is useful, not only in tedious calculations, but also in quick estimations of everyday problems. For example, I never multiply by 5, I divide by 2 and move the decimal point one place to the right. Then there's the old trick of finding whether a number is divisible by 9, by adding the digits—I have recently found this works with 3 as well.

If one used a calculator, these little tricks would not be necessary, which perhaps would detract

from one's understanding of the ideas involved. Also, calculators are not allowed in exams, so it's useful to have the practice in calculation before.

To be fair, I do make extensive use of slide rules, logs and other tables, but there are tricks to be learnt or invented with these as well.

Teaching a child to use a calculator certainly isn't teaching it maths. Although children learn processes for addition, multiplication, etc., they do not necessarily understand exactly what they are doing, until years later, after a lot of experience working with numbers. It is only comparatively recently that I realised precisely why, when dividing vulgar fractions, you "turn the second one upside down and multiply."

Will children soon be leaving Junior School who do not really understand what is meant by addition, subtraction, etc., and cannot multiply or divide without their calculators?

Agreed, the pocket calculator is a good thing for the housewife, checking bills, or the businessman or university student; but with programmable calculators (i.e., pocket computers) becoming

cheaply available, as I am sure will happen, the range of functions available on calculators will extend to embrace more complex algebraic ideas, even perhaps integral and differential calculus.

Shall we soon see students leaving sixth form college for University who cannot solve a simple quadratic equation without their "Acme Pocket Comput-o-matic"?
—Jonathan Gebbie (Hants)

Why bother!?

How right you are, dear Editor, in your editorial on Technological Poverty (August). The daughter, aged 24, of a colleague is a temporary shorthand typist with a bank in the City of London and although she admits that 'she is not all that good' has been offered a permanent position in the bank at £70 a week or £3,640 a year! She's 'thinking' about it because it means starting at 9am instead of at 9.30am!

After a lifetime in electronics and communications my present salary as a senior executive on a national monthly electronics magazine is £3,875! I feel like throwing myself into the river! (Name and address supplied.)

DUAL CONVERSION RECEIVER—contd from page 398

introduced into the receiver through the aerial circuit. If interference of this type is present, it can be easily identified as it is not influenced by tuning.

Whether or not such interference arises depends on the actual aerial and other circumstances. The most likely cause of trouble would be with a long, random length end-connected aerial. The use of some form of resonant amateur band aerial, or aerial tuner, will reduce chances of 5.5MHz breakthrough. Direct pick-up is also largely avoided by using a metal cabinet, while the frequency of the first IF can be shifted one way or the other, if necessary, to avoid a strong transmission.

TRAP CONSTRUCTION

The trap comprises a 13.6 μ H slug tuned coil, with a 47pF silver mica capacitor in parallel. The Denco "White" Range 3 (valve type) miniature coil is suitable and the maker's can is used for screening. The capacitor is connected across pins 1 and 3, Fig. 9. Pin 1 goes to the aerial or an aerial trimmer if the aerial is very long, and pin 3 is connected to S1. Drill the can lid to take the coil mounting bush. Drill a small hole for a lead high on the side of the lid and cut off a little of the can threaded portion so that the can does not cover the hole when screwed in place. Also drill a small hole in the middle of the bottom of the can.

Use the coil to fix the lid inside the back runner of the chassis, near the aerial socket, and run a lead from pin 1 through the hole to the socket. Solder

a lead to pin 3, pass it through the hole in the can bottom, and screw the can in place. The lid must make contact with the chassis runner, so the paper coil identification label should be removed.

The trap can be set by coupling the signal generator to the aerial, tuned to 5.5MHz, and then rotating the core for minimum volume. Alternatively, set the core for minimum interference from any unwanted signal around this frequency.

AERIAL

Many signals should be heard with an indoor wire, or quite short outdoor aerial. For extreme distance reception, an efficient external aerial will be essential. With aerials of medium length, TC1 is unscrewed to reduce loading of the tuned circuit, while with long aerials, TC1 or another series capacitor can with advantage be plugged into socket A1. Though many transmissions can be received without an earth, better reception of weak and difficult signals can be expected when this is provided.

It is necessary to provide holes in the back of the case so that the aerial sockets etc. can be reached. These can be made with a chassis punch, or small holes can be drilled to take a saw blade so that a suitable aperture can be cut. An opening lid was formed in the prototype by cutting out a piece 254×127mm (10×5in) with a saw, and hinging this at the back. When closed, the lid rests on strips bolted to the case top each side. This lid is not essential.

DW

the pre-amplifier unit. This type of core has an outside diameter of 12.5mm (1/2in) and is 3.2mm (1/8in) thick with a central hole of 6.3mm (1/4in) diameter. Thus the core is roughly 3.2mm (1/8in) square cross section. These cores are colour coded to indicate the type of material used. In the case of the T-50-2 the colour code is red and the material is effective up to a frequency of at least 30MHz.

A primary winding of 50 turns is wound on the core using 36SWG enamelled wire, each turn being threaded through the central hole in the ring core. Try to wind the turns in an even layer but do not pull the turns too tight otherwise the enamel coating on the wire may be damaged. Make sure that turns do not cross or overlap one another since this can greatly reduce the efficiency of the transformer. When the winding is complete, twist the free ends loosely together to hold the winding in place on the core.

In the remaining space on the core between the ends of the primary winding 16 turns of the same gauge wire are wound on to the core to form the secondary of the transformer. Once more check that there are no crossed turns and that the primary and secondary windings do not overlap. When complete, the windings will be slightly loose on the core but there is no need to worry about this. It is not advisable to cement the windings with coil cement since this can increase the capacitance of the windings and reduce the efficiency of the transformer.


When the unit is connected to a receiver the load impedance presented to it by the receiver input circuits will vary considerably over the tuning range. If the load has a high impedance, and is reactive, it is possible that the 703 amplifier can become unstable at the higher frequencies. To avoid this, and to even out the gain over the complete range, a shunt damping resistor (R3) is connected across the secondary of the output transformer.

One advantage of using the toroidal type transformer is that the magnetic field of the transformer is confined almost entirely to the ring core. This results in very little stray RF field, which makes screening unnecessary.

CONSTRUCTION

The components of the amplifier circuit are mounted on a small printed circuit board measuring 50mm (2in) by 62.5mm (2 1/2in). A suitable layout for the PCB is given in Fig. 5. The output transformer T1 is simply held down on the board by its four wires. If desired the core can be fixed with a nylon or tufnol screw, but NOT a metal one.

A simple inverted "U" shape chassis 125mm (5in) wide, 100mm (4in) deep and 50mm (2in) high is used to carry the tuning components and the PCB. For the cover, another "U" shaped piece of aluminium can be used and is fixed to the main chassis with self-tapping screws. Note that the two tuning coils are mounted on a small aluminium screen with their bases facing the front panel to give short wiring runs to the switch and tuning capacitor. Aerial and earth input sockets, and the output coaxial socket for the feed to the receiver are mounted on the back of the chassis. It is important that the PCB should be spaced from the chassis to reduce stray capacitance to earth from the copper tracks.

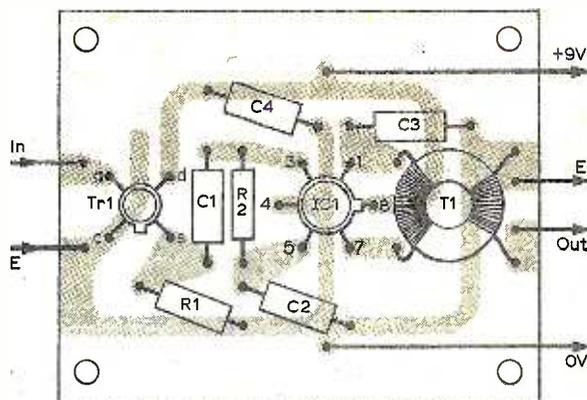

AM 0367

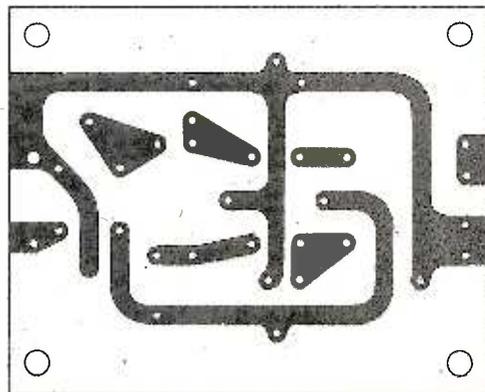


Fig. 5: PCB, full size, showing the component layout above and foil side below.

PERFORMANCE

A gain of some 20 to 30dB in signal level can be expected over the tuning range of the unit. This is equal to about 3 or 4 "S" points in signal strength. The output of the unit is connected to the aerial and earth terminals of the main receiver via the shortest length of coaxial cable possible. Alternatively a twisted pair or balanced twin feeder cable could be used, but the advantage of a screened cable is that there is less possibility of direct pick-up of strong signals on the cable.

Current consumption of the unit is approximately 10mA at 9V. A PP6 type 9V battery can be used to power the unit which should give good battery life. Alternatively a small mains-driven power unit can be used.

OPERATION

Using the pre-amplifier is quite straightforward. First tune the main receiver to the desired frequency band and select the appropriate range on the pre-amplifier. Adjust the unit's tuning capacitor until maximum signal or noise is obtained. In some cases it may be found that there are apparently two signal peaks in the pre-amplifier tuning. One will occur when the pre-amplifier is tuned to the main receiver image frequency. Usually the correct tuning point for the pre-amplifier will be at the lower frequency peak.

Once the unit is tuned for the band it should be possible to operate throughout the band with no further adjustment of the unit's tuning, since the peak is fairly flat over a band of some 200 to 300kHz on the higher frequency bands.

PrW

BI-PRE-PAK

The people for component bargains




Makers of Stirling Sound audio equipment

ORIGINATORS OF PRE-PACKED COMPONENTS IN BRITAIN — AND STILL LEADING!


AUDIO MODULES — today's most challenging values!

POWER AMPS

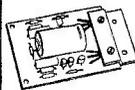


SS103
Compact I.C. amp. 3 watts R.M.S. Single channel (mono). On P.C.B. size 3 1/4" x 2". Needs 10-20V supply. **£1.75**

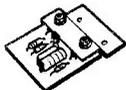SS103-3
Stereo version of above. (Two I.Cs.) **£3.25**



NEW! SS105 Mk. 2
A compact all-purpose power amp. Can be run from 12V car battery. Size 3 1/4" x 2". Useful 5W output (mono) into 3Ω using 12V. Excellent value. **£2.25**

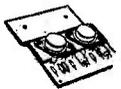SS110 Mk. 2
Similar in size to SS105 but will give 10W output into 4Ω using 24V (mono). Two in stereo give first-class results, suitable for many domestic applications. **£2.75**



SS140*
Beautifully designed. Will give up to 40W R.M.S. into 4Ω. Excellent S.N.R. and transient response. Fine for P.A., disco use, etc. Operates from 45V D.C. Two in bridge formation will give 80W R.M.S. into 8Ω. **£3.60**

PRE-AMP/CONTROL MODULES

SS100
Active tone control unit to provide Bass and Treble facilities (stereo). **£1.60**

SS101
Pre-amp for stereo ceramic cartridges, radio and tape. **£1.60**

SS102
Pre-amp for low-output stereo magnetic cartridges, radio and tape. **£2.25**




BUILD A STEREO F.M. TUNER

SS201
Front End assembly. Ganged tuning with well engineered slow-motion geared drive in robust housing. A.F.C. facility. Requires 6-16V. Excellent sensitivity. 88-108MHz. **£6.25**

SS202
I.F. Stage (with I.C.). Designed to use with SS201 uses I.C. Carefully checked before despatch. **£5.25**

SS203
Stereo Decoder. Designed essentially for use with SS201 and SS202, this excellent decoder can also make a stereo tuner of almost any single channel FM tuner. Supplied ready aligned. A.L.E.D. can easily be fitted. **£5.62**

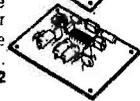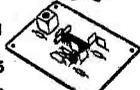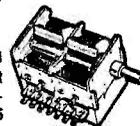Above 3 units together special price **£12.12**



3 SPECIAL OFFERS

LM 380 AUDIO IC
(Marked SL60745). Brand new and to spec. 3 watts R.M.S. out. With data. **£1.00**

2X SN7490. Brand new I.C. to spec. decade counters. **£1.00***

3XSN 7400 Quad 2 input Nan gate I.Cs. **50p***

SUNDRY

P.I PAK—Approx. 170 short-lead semi-conductors and components. PNP, NPN, diodes, rectifiers, etc. on PCBs. At least 30% factory marked. Some data supplied. **50p**

UHF 625 line tuner, rotary. **£2.50**

Rev Counter (for cars). **£1.00***

Books by Bernard's Publications. Newnes-Butterworth's etc. No VAT.

THE FREE CATALOGUE

New edition better than ever. It's yours for free and well worth getting—only please send large S.A.E. with 10p stamp if we have to post it to you.

TERMS OF BUSINESS:

VAT at 25% must be added to total value of order except for items marked * or (0%), when VAT is to be added at 1%. No VAT on overseas orders. P.O.S.T. & PACKING add 2p for UK orders unless marked otherwise. Minimum mail order acceptable—£1. Overseas orders, add £1 for postage. Any difference will be credited or charged. PRICES subject to alteration without notice. AVAILABILITY All items available at time of going to press when every effort is made to ensure correctness of information.

NEW RANGE TRANSISTOR & COMPONENT PACKS

TP SELECTION

TP5 20 Transistors. PNP Germanium, Red Spot A.F.

TP6 20 Transistors. PNP Germanium, White spot RF.

TP7 1 2N174 150w 50Vce Power Transistor, with mounting assembly.

TP19 100 diodes, mixed Germanium, Gold-bonded, etc. Marked/Unmarked.

TP23 Twenty NPN Silicon uncoded T05. Similar to BFY50/2, 2N696, 2N1613, etc. Complementary to TP24.

TP24 Twenty PNP Silicon, uncoded T05. Similar to BFY64, 2N2904/5

TP28 8 power diodes 400V, 1-25A Silicon FCT 3/4.

ALL ABOVE PACKS—50p EACH.

UT SELECTION

UT1 50 PNP's Germanium, AF & RF.

UT2 150 Germanium diodes, min. glass.

UT4 100 Silicon diodes, min. glass, similar to IN914, IN916.

UT5 40 250mW Zener diodes OAZ24 range; average 50% good.

UT7 30 Silicon rectifiers 750mA, mixed voltages, Top Hats, etc.

UT9 40 NPN Silicon planers. Similar to 2N3707-11 range. Low noise amps.

UT12 25 2N3702/3 Transistors, PNP Silicon, Plastic to 92.

CP SELECTION

CP1 Mixed bag of capacitors—Electrolytic, Paper, Silver Mica (Approx. 150—sold by weight).

CP2 200 (approx.) Resistors, various types, values, watts. (Sold by weight.)

CP3 40 Wire wound resistors, mixed.

CP4 12 pots—pre-set, w/wound, carbon, dual, with/without switches—all mixed.

CP7 Heat sinks, assorted. To fit SO-Z (OC72) TO-1 (AC128), etc.

CP7 Heat sinks, assorted. To fit SO-Z (OC72) TO-1 (AC128), etc.

CAPACITOR DISCHARGE IGNITION KIT

Simple to assemble and fit. Improves car performance, saves on fuel. P&P 30p. **£7.50***

BI-PRE-PAK X-HATCH GENERATOR Mk.2

Four-pattern selector switch **£9.93**

3" x 5 1/2" x 3" Ready-built and tested **£7.93**

In kit form **£7.93**

Please add 35p for postage and packing

Is invaluable to industrial and home user alike. Improved circuitry assures reliability and still better accuracy. Very compact, self-contained. Robustly built. Widely used by TV rental and other engineers. With reinforced fibreglass case, instructions, but less batteries. (Three U2 type required.)

TV SIGNAL STRENGTH METER

Complete kit as described in "Television" **£19.50** plus 40p for P&P plus VAT at current rate.

SS300 POWER SUPPLY STABILISER

Add this to your unregulated supply to obtain a steady working voltage from 16 to 60V for your audio system, workbench etc. Money saving and very reliable. **£3.25***

PLASTIC POWER TRANSISTORS

40 WATT SILICON*

| Type | Polarity | Gain | VCE | Price |
|------|----------|------|-----|-------|
| 40N1 | NPN | 15 | 15 | 20p |
| 40N2 | NPN | 40 | 40 | 30p |
| 40P1 | PNP | 15 | 15 | 20p |
| 40P2 | PNP | 40 | 40 | 30p |

90 WATT SILICON

| Type | Polarity | Gain | VCE | Price |
|------|----------|------|-----|-------|
| 90N1 | NPN | 15 | 15 | 25p |
| 90N2 | NPN | 40 | 40 | 35p |
| 90P1 | PNP | 15 | 15 | 25p |
| 90P2 | PNP | 40 | 40 | 35p |

If you prefer not to cut coupon out, please mention ET1P2 when writing

To BI-PRE-PAK, 224-226 WEST RD., WEST CLIFF-ON-SEA, ESSEX

Please send

for which I enclose Inc. V.A.T.

Name

Address

PW9


BI-PRE-PAK LTD

Co. Reg. No. R21199

222 224 WEST ROAD, WEST CLIFF-ON-SEA, ESSEX SSO 9DF.

TELEPHONE: SOUTHEND (0702) 46344.

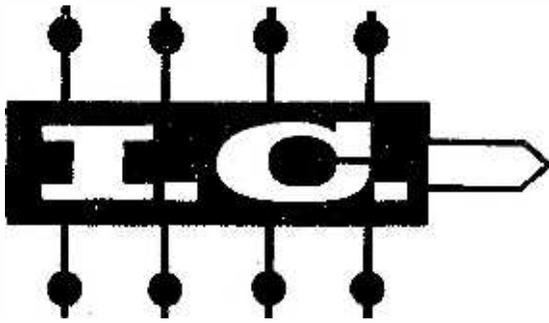WRITE ORDER SEPARATELY AND ATTACH COUPON IF REQUIRED



OF THE MONTH

Number 53

TAA930 IF/FM DETECTOR

THE TAA930 is a linear integrated circuit containing a four stage IF amplifier-limiter, a balanced coincidence FM detector and a voltage regulator in a single encapsulation. In circuits using this Sescosem device, demodulator tuning requires only one coil with a single winding.

The TAA930 has been specially designed for use in the sound system of television receivers. It is available in two different 14-pin plastic encapsulations. The TAA930A is a dual-in-line device, whilst the TAA930B has its connecting pins bent into the quad-in-line configuration. Electrically the two are identical.

TYPICAL CIRCUIT

A typical circuit for the use of the TAA930 in a television sound section is shown in Fig. 1. The coil L1 consists of 46 turns of enamelled wire (about 22 s.w.g.) with a tapping six turns from the earthed end of the coil. This coil can be tuned with a ferrite slug. The coil L2 consists of 32 turns of the same wire in a close wound coil.

CHARACTERISTICS

The limiting action will commence when the input voltage is only about 50 μ V; the input resistance is 15 kilohm. When a signal modulated to the ± 50 kHz deviation level is applied at an amplitude of 10mV, the audio output signal is about 1.4V when a 12V power supply line is used, or about 0.75V r.m.s. with a 9V supply.

The output is taken from an internal emitter follower. The output impedance is about 100 ohms with a 12V supply or 150 ohms with a 9V supply. The minimum recommended load is two kilohm.

The absolute maximum permissible supply voltage is 15V, but the device normally operates from a 9V or a 12V supply line. The power supply current is typically 12 to 17mA.

The AM rejection ratio of the TAA 930 is plotted against the input voltage in Fig. 2. It can be seen that the rejection is over 50dB at normal input levels.

The TAA 930A is available from Phoenix Electronics (Portsmouth) Ltd., 139-141 Havant Rd., Drayton, Portsmouth, PO6 2AA at £1.42 plus 20p postage and packing (V.A.T. included).

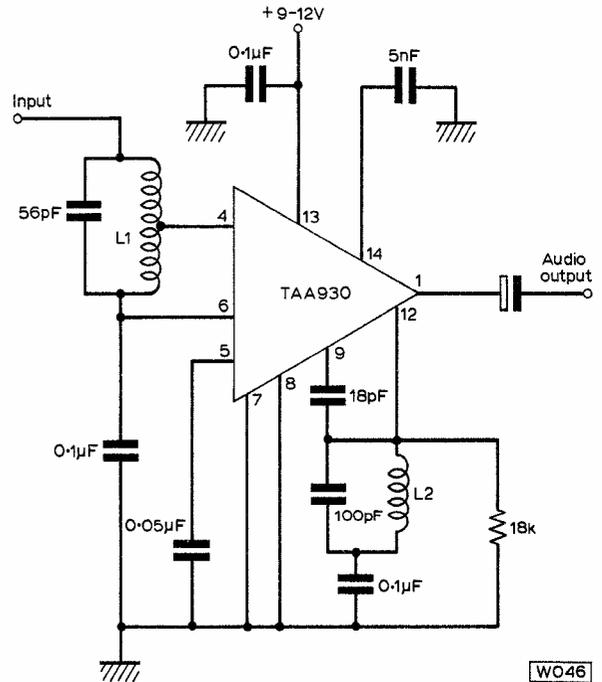


Fig. 1: A typical circuit using the TAA930 integrated circuit in a television sound system.

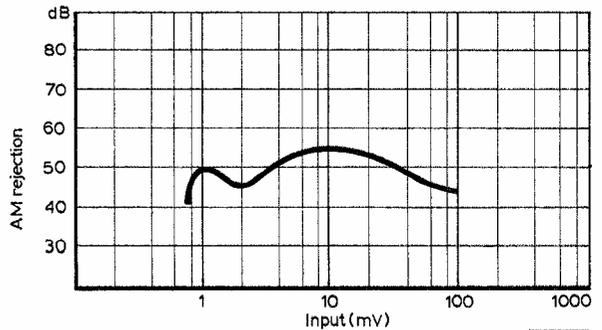


Fig. 2: AM rejection plotted against input voltage.

Practical Wireless, September 1975



"I MADE IT MYSELF"

Imagine the thrill you'll feel! Imagine how impressed people will be when they're hearing a programme on a modern radio you made yourself.

Now! Learn the secrets of radio and electronics by building your own modern transistor radio!

Practical lessons teach you sooner than you would dream possible.

What a wonderful way to learn—and pave the way to a new, better-paid career! No dreary ploughing through page after page of dull facts and figures. With this fascinating Technatron Course, you learn by building!

You build a modern Transistor Radio . . . a Burglar Alarm. You learn Radio and Electronics by doing actual projects you enjoy—making things with your own hands that you'll be proud to own! No wonder it's so fast and easy to learn this way. Because learning becomes a hobby! And what a profitable hobby. Because opportunities in the field of Radio and Electronics are growing faster than they can find people to fill the jobs!

No soldering—yet you learn faster than you ever dreamed possible.

Yes! Faster than you can imagine, you pick up the technical know how you need. Specially prepared step-by-step lessons show you how to: read circuits—assemble components—build things—experiment. You enjoy every minute of it!

You get everything you need. Tools. Components. Even a versatile Multimeter that we teach you how to use. All included in the course. **AT NO EXTRA CHARGE!** And this is a course anyone can afford. (You can even pay for it by easy instalments).

So fast, so easy, this personalised course will teach you even if you don't know a thing today!


No matter how little you know now, no matter what your background or education, we'll teach you. Step by step, in simple easy-to-understand language, you pick up the secrets of radio and electronics.

You become a man who makes things, not just another of the millions, who don't understand. And you could pave the way to a great new career, to add to the thrill and pride you receive when you look at what you have achieved. Within weeks you could hold in your hand your own transistor radio. And after the course you can go on to acquire highpowered technical qualifications, because our famous courses go right up to City & Guilds levels.

Send now for FREE 76 page book—see how easy it is—read what others say!

Find out more now! This is the gateway to a thrilling new career, or a wonderful hobby you'll enjoy for years. Send the coupon now. There's no obligation.

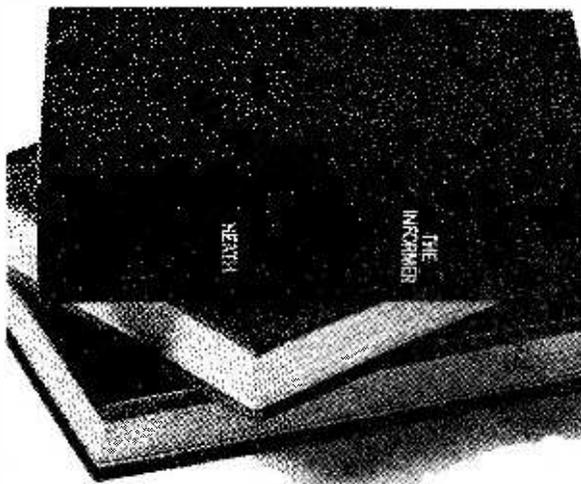Enough books are written about crime, this one stops it.



Outside it's a book. Inside it's an ingenious ultrasonic burglar alarm from Heathkit. The GD-39.

A complete kit that can be assembled in only a few enjoyable hours, with the help of a very easy to follow instruction manual.

The GD-39 works by transmitting a silent, ultrasonic signal throughout the room. And continuously monitoring it. Any movement made by an intruder in the room will then automatically produce a change in the signal. Which triggers off a lamp and, thirty seconds later, a remote buzzer, that just you hear, or a loud bell.

Enough to scare the living daylights out of a burglar. For more details, and a bookful of other ideas, just post the coupon now for your free Heathkit catalogue.

Or, if you're in London or Gloucester, call in and see us. The London Heathkit Centre is at 233 Tottenham Court Road. The Gloucester showroom is next to our factory on Bristol Road.

Heath (Gloucester) Limited,
Dept. PW-95, Bristol Road,
Gloucester GL2 6EE.
Tel: (0452) 29451.



The GD-39 Ultrasonic Burglar Alarm

To: Heath (Gloucester) Limited, Dept. PW-95 Gloucester GL2 6EE. Please send me a free Heathkit catalogue.

 Name _____
 Address _____

 Postcode _____
 Remember easy terms are available with the Heathkit Monthly Budget Plan.

POST TODAY FOR FREE BOOK
 To: ALDERMASTON COLLEGE DEPT. CPW 09, READING RG7 4PF CPW09
 Also at our London Advisory Office, 4 Fore Street Avenue, Moorgate, London, EC2Y 5EJ Tel: 01-628 2721
 Yes, I'd like to know more about your course. Please send me free details—plus your big, 76-page book that tells about all your courses.
 Name _____
 Address _____
 POST CODE _____

 HOME OF BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY

KITS FOR THE CONNOISSEUR



Apollo III Tuner

High Quality FM/AM Tuner as Featured in the July and August Issues of Practical Wireless
 Complete Kit Order as TTS/1000/S £35.00 Circuit Board only Order as TTS/1375/S £5.00
 Kit less Cabinet Order as TTS/1001/S £46.00 Built and Tested Order as TTS/A/BT £68.50
 Complete Kit less Part I Order as TTS/1003/S £45.50

Scorpio Tuner FM/AM Varicap Tuner

Similar in appearance to the Apollo III.
 This more complex kit builds into a high performance tuner with special features such as the EC5603U tuner head, the 3089 IF IC, 1310 stereo decoder and BR2007N pilot tune notch filter. Also has remote tuning facilities and adjustable output.
 Complete Kit Order as TTS/1005/A £48.50 Remote Control Unit Order as RC/1005/A £5.20
 Built and Tested Order as TTS/SC/BT £60.50 Cabinet and Metal work only Order as TTS/CM/O £13.00
 All prices quoted are exclusive of VAT—please add 25%.

Capricorn Amplifier

Matching amplifier to the above tuners. Features an active cross-over unit and separate bass and treble amplifiers, tape to tape and provision for quadraphonic add-on unit. Details on request.

Aquarius Tape Unit

A matching cassette tape unit to all the above units. Fitted with slimline front loading cassette deck, twin level meters and adjustable output. Details on request.

Taurus Quadraphonic Add-on Unit

Styled to match the other units in the range. Further details on request.

All kits include all parts necessary to complete the particular kit, together with full constructional information.

Please send a stamped self-addressed envelope with all enquiries.

WE DESIGN AND MANUFACTURE A COMPLETE RANGE OF DOMESTIC AUDIO EQUIPMENT

INCLUDING MUSIC CENTRES, QUADPHONIC UNITS AND TUNER AMPLIFIERS

TRADE ENQUIRIES WELCOME.

TAPE TRAINING SERVICES LTD 7 West Road, Westcliff-on-Sea, Essex.

ONLY THE ANTENNA WAS ON THE FLOOR!!

* These are VFA USERS' claims, and remember, SWL's, A GOOD TRANSMITTING AERIAL IS AN EQUALLY GOOD Receiving AERIAL—You sure can't work 'em if you can't hear 'em

ZL1ASY worked GC3EML on the 20m. band with **JOYSTICK lying ON FLOOR OF SHACK!!

G2BAH (ex G4CJN), Kendal, reports: "I happened to be listening on 80m. and heard someone in Manchester testing. We established a strength 8 qso each way. He had a *VFA laying on his kitchen table and was making tests to see if it would load up, etc. An old timer, a G2 and 2 letters, so he knew what he was doing".

G3ZDR worked a W3 on 20m. using a *VFA and a PM3A with 2 watts.

G3VFA worked WITW on 20m. using a *VFA and 750mW.

W6TYP worked WA6JPR over hundreds of miles on 40m. using *VFA and microwatts "equivalent to ONE MILLION !!! miles per watt of input power" (So says his WORLD RECORD achievement certificate).

Here is YOUR Complete WORLD RECORD AERIAL SYSTEM for 160, 80, 40, 20, 15 and 10m. plus all SW BC bands and everything between FOR ANY LOCATION—

SYSTEM "A" for modern communications RX's and QRP xcvr's. £32.76

SYSTEM "D" for other SW and MW receivers £24.43

SYSTEM "J" for TX's and XCVR's up to 500w. PEP 160 thru 10m. £40.72

JOYMATCH 111B A.T.U. low impedance aerial input receivers £15.97

JOYMATCH LO-Z 500 X including external RF meter £22.12

JOYMATCH Triple Purpose A.T.U. (Short Wave coverage only) KIT £7.26

JOYMATCH Triple Purpose A.T.U. (Short & Medium Wave Bands) KIT £7.26

Either KIT assembled ready for use with easy to follow instructions £8.77

JOYMATCH Artificial Earth (Ground) Matches Short-Medium wave £7.26

JOYMATCH Aerial Bandswitch (Aerial & A.T.U. for Domestic Receivers £7.26

DX-CRYSTAL SET Mk 2 (World's first Short Wave & Medium Wave Crystal Set) £4.73

Communications Headphones 8 ohm. Suitable for modern communications £4.82

VALVES, Complete replacement set incl. OA2 for 9R59DE & 9R59DS £6.12

ALL PRICES DELIVERED (incl. insurance)

Send STAMP for full list of PARTRIDGE PRODUCTS including **PARTRIDGE SUPER PACKAGE COMPLETE STATION FOR ANY LOCATION.** Comprising: QR666 TRIO G.C. Rx, 111B A.T.U., World Record VFA, matching headphones, outdoor insulators, feeder, connecting cables. Delivered **£185.00.**

(PRICES SUBJECT TO ALTERATION WITHOUT NOTICE)

BOX 5



Phone 0843 62535
 or 62839
 After office hours
 G3CED G3VFA



HOTLINES

ON RECENT DEVELOPMENTS

PROJECTION TELE.

TELEVISION tyros will remember the old projection television sets. A long, cylindrical projection "tube" was used to project the image on to a screen. A problem at the time was the use of very high voltages to run the tube. This idea fell out of favour and never really caught on in the home. It may therefore come as a surprise to learn that a company is manufacturing not just a projection tube, but the whole system, including screen; and suitable for colour. Designated the Videobeam, it will receive colour television transmissions (all u.h.f. channels 21-68) and it will also accept video tape input or a signal direct from a suitable camera. A further input accepts computer data where the system would prove useful for giving direct viewing of a printout in alpha numeric form.

The 1.75m. wide image is projected onto a special screen which is curved. The sound is also "projected" at the screen and is reflected back to the audience. The manufacturers claim that some 40 people can view the screen in comfort.

WATCH THE CALCULATIONS

A few Ginsbergs ago I mentioned a wristwatch/calculator (electronic, of course). Having now seen just what they look like I can only comment, "fascinating". The same remarks apply to the price—about \$400. But hope is not lost if you aspire to owning one and haven't got too many pennies. A plastics specialist manufacturer has mentioned that he can see the price dropping to \$20! He argues that a huge part of the cost of these miniature marvels lies in the expensive, bespoke metal cases. His answer is to simply switch to special, tough, plastic cases which can be modelled/moulded into some very attractive shapes.

The "buttons" on the watch/calculator are depressed using the point of, say, a ballpoint pen. The proposed plastic cases and keyboards measure 40 x 35 x 3mm. deep. The keys themselves are only 3mm. in diameter. In the basic design of the plastic case, up to seven functions could be accommodated

which includes a memory. Readout of the watch I have seen is a liquid crystal type but doubtless LED versions are around too. Not available over this side of the pond—yet.

S.A. TV

Changing channels, back to television, I see that the long awaited South African television transmissions are finding their way into the ether. The official inauguration of these transmissions was back in the early part of this year. One hour test programmes are the order of the day so far with a promise of daily broadcasts from 1800-2300 to follow.

The licence fee is around £25, and the cost of a 26in. colour (PAL) receiver is about £700. Despite this high price it is estimated that some 175,000 sets will be sold this year and that colour receivers will account for 75% of this figure.

I²L

For the semiconductor enthusiasts, keep a sharp lookout for the new I²L (injection logic) which seems to be creeping in quietly. Fairchild has recently introduced a 4,096-bit RAM (random access memory) with an access time of only 100ns. Another giant, Texas Instruments, is also working hard on I²L products although it is playing its cards very close to the chest with not too many details available at present. Philips has already used I²L in an in-house motor control requirement. I predict that injection logic will have quite an impact once it gets started in a big way.

SWL's NOTE

People who, listen in the radio spectrum from 2-30MHz will be pleased to hear of new equipment just launched on to the market (but not so pleased to hear the price!). Radio signals in this sector rely on reflection from the various ionised layers high above the earth. There are different layers which can affect the signal. At times a signal will just fade, sometimes a band is "open" working well and full of signals. Later, the same band can be almost dead and void of any radio life at all.

Which band do you choose, and how long will it stay "open"?

The new equipment tells all. The unit has a c.r.t. display which shows two sets of data. One is a barograph display which shows intensity of the received signals (in dBs) and shows which signals in the spectrum are strongest at a glance. Beneath this display is another which shows via which path these signals are reaching the receiver and taking into account single and multiple path transmissions. Part of the system is a sounder transmitter which sweeps the band over a five minute period.

The band is divided up into various data channels. Another part of the equipment makes seven duplicates of each channel and these are transmitted as a package of tones. These are transmitted and received by the receiver which can then calculate to allow for things like short-term fading, static bursts etc. Just for the record, a sounder transmitter/receiver system costs in the region of 100,000 dollars—then, of course, you may want to purchase the modern unit. . . .

SIG. GENNY

It seems that in the dim distant Ginsberg past, memories of having two small signal generators marked a.f. and r.f. respectively come to light. A separate "box" was required for each job. This seems a far cry from one new signal generator just released which covers, in a single box, from 15Hz to over 1GHz. Needless to say it doesn't end there. The unit has both analog and digital readout, has an a.f. voltmeter built in and does numerous things quite automatically. Accuracy is almost frightening and mention is made of "four options". Grudgingly I must give it best over the ubiquitous BC221 which was the pride and prestige symbol of many a ham station.





by Eric Dowdeswell G4AR

ON several occasions in the past I have mentioned the possibility of running a small contest for readers of this page, with a couple of prizes thrown in. Very briefly the idea is to ask you to submit a cassette recording of the best DX that you hear over a period of, say, a month, on any amateur band. The "best" recording will take into account the band, time, mode, clarity of signal etc. If you have a cassette recorder it ought to be alongside your receiver anyway, always ready to record a choice bit of DX, so why not fix up a permanent lead out of your set to take immediate advantage of the recording facility?

Full details next month, I hope, so start practising and don't forget to make an entry in your log at the same time as the recording or you will be wasting your time! Better still, use the microphone to put the details of date, time etc., on the tape immediately after the recording.

Pete Dawson (Westward Ho! N. Devon) may wonder why he hasn't heard from me in reply to his first letter. Unfortunately Pete, you did not give your full address. For those willing to lose a few hours sleep Pete listed quite a few Central American prefixes heard between about midnight and 0400 on 3.5 and 14MHz. His "very ordinary" equipment is an old R107 with a Delta loop (for 14MHz?) and an inverted Vee about 50ft at the top. Pete has 246 countries to his credit and naturally has trouble in finding a new one these days, although he has been looking for the HK0AA and CE0A DXpeditions without success. I suggest Geoff Watts' DX News Sheet is the best and latest source of info on such matters. See July column.

Another first-timer is **Peter Allen** A8677 (Taunton) using a Trio 9R59DS and a G5RV aerial plus a G8AEV converter for 2m aided by an eight element horizontal beam and a five element vertical "for mobiles and repeaters". Not a bad idea, Pete! With the benefit of hindsight it now seems a pity that the early workers on 2m did not go for vertical polarisation in the first place! I have sent my condolences to **Mike Conolly** A8796 (Yeovil) who has had to move from the village of Odcombe to a "terrace house in the centre of Yeovil", losing the lovely countryside and its DX potentialities! However, Pete has had his 2m halo fixed on a TV mast at 45ft plus a pulley for the eventual long-wire. Good thinking!

Neil Whiteside A8859 (Hitchin, Herts) has only been watching the SW bands for a few months with his 50ft wire feeding a CR100/8 and Codar PR40 preselector. He deplores the selfish attitude of amateurs who seem to choose 3.6MHz for tuning up their rigs on a Sunday morning thus QRM'ing the RSGB News Bulletin. Although you are not too far from Chelmsford, I think one of the other transmissions might be better for you, Neil. Try the first one from G2MI in Bromley, Kent. Neil hopes to take his RAE in December plus the Code exam and to get his G4+3 right away. Very wise of you, OM. Top Band enthusiast **Tim Charles** (Colchester) bemoans the usual summer fade out of that band and seems to have gone to the other extreme by concentrating on 2m. Recent lift conditions on 2m have enabled Tim to listen to Europeans working through the GB3BC repeater. In fact, Tim has copied nine repeaters so far, including PA0ALK, DB0SM, DB0WW and DB0ZO.

Andrew Swiffin A8603 (Cheadle) couldn't leave radio alone when he went camping near Ullswater, taking along a transistorised set and loaded whip aerial. He was pleased with VP1PF and several W's on 80m plus some GDX on 160m in daylight. **Colin Fawcett** (Oldham) gets back on the bands after five years' absence but so far has not fixed up a decent aerial for his Eddystone 840C. **Paul Barker** (Sunderland) got back into the SSTV groove again finding plenty of activity from Europe on 20m plus his first-ever reception of SSTV signals on 10m, from three DLs.

"**M. C. P. Bennett**" reveals that he is Michael, at long last! At Slough he found some nice ones on 15m including three VP8s. Attention, all those in Aberdeen! **Stan Sutherland** GM4BKV, secretary of the Aberdeen ARS, tells me of RAE courses starting at the local Tech College in September but he's short of candidates at the moment. Anyone contemplating taking the RAE next May and living around Aberdeen should write to Stan at 67 Greenfern Road, Aberdeen AB2 6TP. Even if next May seems too soon it is still worth looking into. **John Bennett** (Bristol) is yet another newcomer to the amateur bands and he has a Codar CR70A and a 35ft wire. He has already joined the Western-Super-Mare Radio Club which is a very good way of sorting out the mysteries of our hobby!

I was glad to note that **John Porter** (Baslow Derbys) had a look at the CW end of 15 and 20m for a change. Quite a few countries and prefixes can often be heard for new ones down at the LF end of the bands so why not try it out sometime? There are fast ones and slow ones with straight keys and electronic wonders so the newcomer to code need not fear that he won't be able to copy anything at all, even if it is only call-signs.

NEW MULLARD & MAZDA VALVES

All individually boxed and guaranteed. Full trade discounts to bona fide companies. Price and availability lists on application.

EXPRESS POSTAGE

10p for 1 Valve.
Each additional Valve add 2p in UK

| | | | | | | | | | |
|--------|------|--------|------|----------|------|------------|------|------------|------|
| DM70 | 0-61 | ECL83 | 0-66 | GY501 | 1-18 | PL82 | 0-48 | 30C1/PCF80 | |
| DY51 | 0-80 | EOL86 | 0-64 | GZ34 | 0-80 | PL83 | 1-04 | 30C15/ | 0-54 |
| DY86/7 | 0-41 | EF80 | 0-62 | PC86 | 0-95 | PL84 | 0-88 | 30C15/ | 0-54 |
| DY802 | 0-46 | EF83 | 0-98 | PC87 | 0-42 | PL504 | 0-90 | PCF800 | 1-01 |
| EABC80 | 0-48 | EF85 | 0-42 | PC80 | 0-57 | PL508 | 0-84 | 30C17/ | 1-01 |
| EB1 | 0-64 | EF86 | 0-12 | PC84 | 0-54 | PL509 | 1-56 | PCF805 | 1-00 |
| EB31 | 0-79 | EF89 | 1-14 | PC88 | 0-86 | PL802 | 1-40 | 30F5/PF818 | |
| EBF80 | 0-56 | EF91 | 1-00 | PC89 | 0-84 | PY33 | 0-65 | | 1-08 |
| EBF83 | 0-59 | EF92 | 1-37 | PC8189 | 0-80 | PY81/800 | 0-49 | 30FL1/ | |
| EBF89 | 0-58 | EF95 | 0-83 | PC866 | 0-64 | PY82 | 0-57 | PCF800 | 1-00 |
| EC86 | 0-78 | EF184 | 0-63 | PC878 | 1-22 | PY83 | 0-82 | 30FL2 | 1-13 |
| EC88 | 0-76 | EH90 | 0-85 | PC878 | 0-64 | PY80 | 0-49 | 30FL4 | 1-00 |
| EC90 | 0-86 | EL34 | 0-98 | PCF200 | 1-00 | UY81 | 0-49 | 30L1/PCC84 | |
| EC97 | 0-80 | EL36 | 1-01 | PCF201 | 1-00 | U26 | 0-88 | | 0-54 |
| EC98 | 0-47 | EL61 | 0-85 | PCF801 | 0-64 | U193 | 0-54 | PC805 | 1-03 |
| EC99 | 0-44 | EL81 | 0-85 | PC802 | 0-70 | U198 | 0-54 | PC805 | 1-03 |
| EC998 | 0-47 | EL84 | 0-47 | PC820 | 1-15 | UC1380 | 0-78 | PC805 | 0-89 |
| EC994 | 0-58 | EL85 | 0-85 | PC822 | 0-58 | UBF89 | 0-58 | 30P4MR | 1-27 |
| EC995 | 0-71 | EL86 | 0-92 | PC83 | 0-64 | UC825 | 0-59 | 30P12/ | |
| EC998 | 0-84 | EL91 | 1-00 | PC84 | 0-61 | UC861 | 1-12 | PC801 | 1-01 |
| EC998 | 0-88 | EL91 | 1-00 | PC85 | 0-64 | UC82 | 0-72 | 30P19/ | |
| EC998 | 0-88 | EL93 | 0-72 | PC86 | 0-64 | UC83 | 0-78 | PC805 | 0-89 |
| EC998 | 0-88 | EL95 | 0-50 | PC805/85 | | UF89 | 0-58 | 30P11/ | |
| EC998 | 0-88 | EV81 | 0-79 | | 0-64 | UL84 | 0-92 | PC801 | 1-00 |
| EC998 | 1-16 | EV86/7 | 0-40 | PD500 | 1-88 | UY85 | 0-54 | PC8L13/ | |
| EC998 | 1-00 | EV98 | 0-72 | PF1200 | 0-83 | 30L2/ | 0-80 | PC8L80 | 1-15 |
| EC998 | 0-87 | EZ30 | 0-54 | PL31 | 0-90 | EC804 | 0-98 | 30P14/ | 1-35 |
| EC998 | 0-64 | EZ31 | 0-38 | PL31A | 0-90 | 6P29/EF812 | 1-03 | 30P15 | 1-13 |

NEW VALVES

Individually boxed and guaranteed but of European or other origin at greatly reduced prices. Quotations for any valve not listed. Send SAE for lists.

| | | | |
|----------|------|---------|-------|
| PY83 | 0-50 | 6P28 | 0-75 |
| PY88 | 0-56 | 6J5M | 0-65 |
| PY800 | 1-10 | 6J5G | 0-45 |
| PY801 | 0-55 | 6J5H | 0-35 |
| SP41 | 3-00 | 6J7M | 0-65 |
| SP61 | 0-85 | 6K6GT | 0-80 |
| T41 | 1-00 | 6K7G | 0-35 |
| U14 | 0-75 | 6K7M | 0-45 |
| U26 | 1-00 | 6K8G | 0-45 |
| U26 | 0-85 | 6K8M | 0-70 |
| U191 | 0-75 | 6K8S | 1-00 |
| UABC80 | 0-40 | 6L6G | 0-55 |
| UAF42 | 0-75 | 6Q7G | 0-40 |
| UBC41 | 0-60 | 6Q7M | 0-60 |
| UBC81 | 0-60 | 6SL7GT | 0-55 |
| UBF80 | 0-60 | 6SN7GT | 0-55 |
| UBF89 | 0-60 | 6S7GT | 0-40 |
| UC88 | 0-60 | 6V6G | 1-50 |
| UC81 | 0-50 | 7C8 | 1-80 |
| UC82 | 0-40 | 6X4 | 0-45 |
| UC83 | 0-70 | 6X5G | 0-45 |
| UR41 | 0-75 | 6X6GT | 0-55 |
| URF89 | 0-60 | 7B6 | 0-80 |
| UL41 | 0-80 | 7B7 | 0-80 |
| UY41 | 0-55 | 7C8 | 1-00 |
| UY85 | 0-45 | 7E7 | 0-80 |
| VR105/30 | 0-40 | 7E7 | 0-80 |
| VR160/30 | 0-45 | 7E7 | 2-25 |
| 1E5 | 0-50 | 7Y4 | 0-80 |
| 1T4 | 0-40 | 12A7E | 0-45 |
| 1T4 | 0-40 | 12A7T | 0-45 |
| 3B4 | 0-50 | 12A9G | 0-50 |
| 3V4 | 0-88 | 12A9T | 0-88 |
| 3U4G | 0-55 | 12B4A | 0-60 |
| 3Y3GT | 0-60 | 12B6G | 0-60 |
| 6A4C | 0-85 | 8C1 | 0-40 |
| 6/30L2 | 0-90 | 30C15 | 1-15 |
| 6AK5 | 0-45 | 30C17 | 1-00 |
| 6AM5 | 1-00 | 30C18 | 0-90 |
| 6AQ5 | 0-50 | 30F5 | 1-00 |
| 6AS7G | 1-00 | 30FL1 | 1-00 |
| 6AT6 | 0-60 | 30FL2 | 0-75 |
| 6AU6 | 0-40 | 30FL4 | 1-00 |
| 6BA6 | 0-35 | 30L15 | 0-95 |
| 6BE6 | 0-48 | 30L17 | 0-95 |
| 6BH6 | 0-75 | 30P4MR | 1-30 |
| 6BJ6 | 0-75 | 30P12 | 1-00 |
| 6BQ7A | 0-55 | 30P19 | 0-95 |
| 6BR7 | 1-20 | 30P11 | 0-95 |
| 6C7G | 0-40 | 30P13 | 1-10 |
| 6BW6 | 1-00 | 30P14 | 1-00 |
| 6BWW | 1-00 | 35W4 | 0-60 |
| 6C4 | 0-40 | 35Z4GT | 0-70 |
| 6CD6G | 1-80 | 50CD6G | 1-20 |
| 6CH6 | 1-50 | 807 | 1-00 |
| 6CW4 | 1-00 | 813TT | 14-00 |
| 6E25 | 0-60 | 813FSSR | 6-00 |
| 6E25 | 1-00 | 86A | 1-20 |

| | | | | | |
|--------|------|------------|------|-----------|------|
| AZ1 | 0-75 | EF39 | 1-25 | KTW61 | 1-50 |
| AZ31 | 0-60 | EF80 | 0-35 | MU14 | 1-00 |
| CBL31 | 1-40 | EF85 | 0-45 | N78 | 3-50 |
| CL33 | 1-50 | EF86 | 0-50 | OA2 | 0-45 |
| CT81 | 0-80 | EF89 | 0-35 | OC8 | 0-45 |
| DAF91 | 0-40 | EF184 | 0-60 | PC36 | 0-85 |
| DAF96 | 0-60 | EF92 | 0-50 | PC88 | 0-85 |
| DC990 | 1-85 | EF95 | 0-45 | PC97 | 0-65 |
| DP91 | 0-40 | EF98 | 0-80 | PC900 | 0-55 |
| DP96 | 0-60 | EP183 | 0-40 | PC984 | 0-45 |
| DK91 | 0-50 | EP184 | 0-45 | PC988 | 0-82 |
| DK92 | 1-00 | EL23 | 0-80 | PC989 | 0-55 |
| DK96 | 0-75 | EL33 | 2-50 | PCF189 | 0-85 |
| DL92 | 0-50 | EL34 | 0-70 | PCF80 | 0-40 |
| DL94 | 0-48 | EL36 | 0-60 | PCF82 | 0-42 |
| DL96 | 0-65 | EL37 | 2-50 | PCF86 | 0-65 |
| DY86 | 0-45 | EL41 | 0-80 | PCF801 | 0-60 |
| DY87 | 0-45 | EL42 | 1-65 | PCF802 | 0-56 |
| DY802 | 0-47 | EL84 | 0-25 | PCF805 | 0-80 |
| EABC80 | 0-38 | EL95 | 0-85 | PCF806 | 0-80 |
| EAF42 | 0-70 | ELL80 | 2-00 | PCF808 | 1-00 |
| EB91 | 0-25 | EM80 | 0-55 | PCF82 | 0-46 |
| EB93 | 1-00 | EM81 | 0-60 | PCF83 | 0-70 |
| EB94 | 0-40 | EM84 | 0-40 | PCL84 | 0-60 |
| EBF80 | 0-40 | EM85 | 1-00 | PCL85 | 0-60 |
| EBF83 | 0-40 | EM87 | 1-00 | PCL86 | 0-50 |
| EBF89 | 0-32 | EV86 | 0-45 | PCF805/85 | |
| EBL31 | 2-00 | EZ40 | 0-60 | PD500 | 1-80 |
| EC991 | 0-45 | EZ41 | 0-75 | PEN46 | 0-85 |
| EC992 | 0-35 | EZ80 | 0-30 | PL36 | 0-82 |
| EC993 | 0-35 | EZ81 | 0-31 | PL81 | 0-55 |
| EC995 | 0-45 | GY501 | 0-90 | PL82 | 0-60 |
| EC998 | 0-50 | GZ30 | 0-65 | PL83 | 0-50 |
| EC998 | 1-50 | GZ32 | 0-65 | PL84 | 0-50 |
| EC998 | 0-85 | GZ34 | 0-75 | PL500 | 0-85 |
| EC998 | 0-85 | GZ37 | 1-25 | PL504 | 0-85 |
| EC998 | 0-50 | HN309 | 1-50 | PL508 | 0-90 |
| EC998 | 0-60 | KT61 | 2-50 | PL509 | 1-25 |
| EC998 | 0-42 | KT66 | 2-95 | PL802 | 1-55 |
| EC998 | 0-75 | KT81 (7C5) | | EX25 | 3-50 |
| EC998 | 0-65 | KT81 | 1-80 | FY33 | 0-60 |
| EC998 | 3-50 | KT81 | 1-75 | FY81 | 1-00 |
| EC998 | 1-20 | KT88 | 3-25 | FY82 | 0-45 |

TRANSISTORS-INTEGRATED CIRCUITS

EXPRESS POSTAGE

10p per order in UK

All transistors, I.C.'s offered are new and branded. Manufactured by Mullard, Texas, RCA, Ferranti, Motorola, ITT, Fairchild, Lucas, etc. Quantity discounts on application. Send SAE for full lists.

| | | | | | | | | | |
|--------|------|--------------|------|---------|------|--------|------|---------|------|
| AA119 | 0-07 | BD124 | 0-65 | QA200 | 0-08 | ZTX501 | 0-15 | 2N2904A | 0-25 |
| AA213 | 0-12 | BD131 | 0-48 | QA202 | 0-08 | ZTX502 | 0-15 | 2N2905 | 0-25 |
| AAZ15 | 0-10 | BD132 | 0-60 | QA203 | 0-08 | ZTX503 | 0-15 | 2N2905A | 0-25 |
| AC107 | 0-10 | BF115 | 0-30 | OC16 | 1-00 | ZTX550 | 0-18 | 2N2906 | 0-25 |
| AC126 | 0-25 | BF167 | 0-25 | OC23 | 1-25 | 1N914 | 0-08 | 2N2906 | 0-18 |
| AC127 | 0-25 | BF173 | 0-25 | OC25 | 0-40 | 1N4001 | 0-06 | 2N3053 | 0-13 |
| AC128 | 0-15 | BF179 | 0-38 | OC28 | 0-08 | 1N4002 | 0-07 | 2N3055 | 0-05 |
| AC176 | 0-25 | BF180 | 0-38 | OC28 | 0-08 | 1N4003 | 0-08 | 2N3525 | 0-41 |
| AC187 | 0-21 | BF181 | 0-35 | OC28 | 0-08 | 1N4004 | 0-08 | 2N3614 | 0-65 |
| AC188 | 0-20 | BF184 | 0-10 | OC28 | 0-08 | 1N4005 | 0-10 | 2N3615 | 0-65 |
| AC191 | 0-22 | BF195 | 0-13 | OC29 | 0-40 | 1N4006 | 0-10 | 2N3702 | 0-11 |
| AC192 | 0-25 | BF197 | 0-15 | OC29 | 1-25 | 1N914 | 0-08 | 2N3703 | 0-13 |
| AD140 | 0-40 | BF200 | 0-38 | OC29 | 0-40 | 1N4001 | 0-06 | 2N3704 | 0-14 |
| AD149 | 0-50 | BF261 | 0-25 | OC28 | 0-08 | 1N4002 | 0-07 | 2N3705 | 0-15 |
| AD161 | 0-44 | BF289 | 0-25 | OC28 | 0-08 | 1N4003 | 0-08 | 2N3706 | 0-11 |
| AD162 | 0-44 | BFW10 | 0-61 | OC28 | 0-08 | 1N4004 | 0-08 | 2N3707 | 0-18 |
| AF115 | 0-25 | BFX38 | 0-54 | OC42 | 0-40 | 1N4005 | 0-10 | 2N3708 | 0-07 |
| AF116 | 0-25 | BFY60 | 0-20 | OC45 | 0-20 | 1N4007 | 0-12 | 2N3709 | 0-13 |
| AF117 | 0-24 | BFY61 | 0-20 | OC71 | 0-18 | 1N4009 | 0-06 | 2N3704 | 0-14 |
| AF186 | 0-48 | BFY62 | 0-20 | OC72 | 0-28 | 1N4148 | 0-08 | 2N3705 | 0-15 |
| AF239 | 0-44 | BFY60 | 0-27 | OC76 | 0-20 | 18921 | 0-07 | 2N3706 | 0-11 |
| AS737 | 0-33 | BY126 | 0-14 | OC77 | 0-65 | 18933 | 0-20 | 2N3707 | 0-18 |
| AS728 | 0-25 | BY127 | 0-15 | OC81 | 0-28 | 18210A | 0-25 | 2N3708 | 0-07 |
| BA102 | 0-25 | BZX61 series | | OC81D | 0-28 | 18210A | 0-25 | 2N3709 | 0-13 |
| BA115 | 0-10 | | 0-20 | OC81Z | 0-45 | 183010 | 0-25 | 2N3710 | 0-11 |
| BA107 | 0-14 | BZY88 series | | OC83 | 0-27 | 2N696 | 0-15 | 2N3711 | 0-11 |
| BC109 | 0-12 | | 0-10 | OC140 | 1-14 | 2N697 | 0-16 | 2N3819 | 0-88 |
| BC112 | 0-15 | CR81-05 | 0-30 | OC170 | 0-30 | 2N706 | 0-10 | 2N4050 | 0-70 |
| BC117 | 0-21 | CR81-40 | 0-60 | OC200 | 0-20 | 2N709A | 0-12 | 2N4053 | 0-60 |
| BC143 | 0-80 | CR88-40 | 0-50 | OC201 | 0-25 | 1N1131 | 0-25 | 2N4055 | 0-15 |
| BC147 | 0-10 | MJE340 | 0-47 | OC202 | 0-20 | 1N1392 | 0-20 | 2N4056 | 0-20 |
| BC148 | 0-08 | MJE370 | 0-68 | OC203 | 0-50 | 1N1302 | 0-18 | 2N4055 | 0-25 |
| BC1890 | 0-15 | MJE520 | 0-65 | OC205 | 0-85 | 1N1803 | 0-13 | 2N4056 | 0-25 |
| BC189 | 0-12 | MJE2985 | 0-27 | OC271 | 1-20 | 2N1804 | 0-22 | 2N4058 | 0-15 |
| BC189 | 0-12 | MJE2985 | 0-27 | ORP12 | 0-60 | 2N1805 | 0-22 | 2N4059 | 0-15 |
| BC184L | 0-18 | MPP109 | 0-40 | ORP60 | 0-55 | 2N1806 | 0-22 | 2N4060 | 0-18 |
| BC238 | 0-15 | MPP103 | 0-38 | TIG44 | 0-28 | 18210A | 0-25 | 2N4061 | 0-13 |
| BCY82 | 0-35 | MPP104 | 0-35 | TIC226D | 1-50 | 2N1808 | 0-22 | 2N4062 | 0-14 |
| BCY83 | 0-38 | MPP105 | 0-38 | TIL209 | 0-20 | 2N1809 | 0-20 | 2N4289 | 0-30 |
| BOY24 | 0-45 | NKT404 | 0-68 | ZTX107 | 0-12 | 2N1613 | 0-21 | 2N1825 | 1-75 |
| BOY70 | 0-15 | OA5 | 0-72 | ZTX108 | 0-08 | 2N1614 | 0-45 | 2N141 | 0-81 |
| BOY71 | 0-22 | OA6 | 0-72 | ZTX300 | 0-13 | 2N1617 | 0-78 | 40380 | 0-40 |

Don't miss your copy of HENRY'S NEW 1975 CATALOGUE



only 50p
Plus 20p P&P

- ★ OVER 5,000 ITEMS - largest UK range of electronic components for home constructors.
- ★ 200 PAGES - every aspect of electronics and components for amateurs and hobbyists - kits, projects, test gear.
- ★ DOZENS of new lines and new ranges.
- ★ MANY price reductions throughout the new Catalogue.
- ★ A Discount Voucher with every copy, worth 50p.

ALL HENRY'S PRICES INCLUSIVE OF VAT

Write now for your copy, enclosing 70p remittance.

Now Open Supermarket,
Browse Round The New
Supermarket at 404 Edgware
Road.

Henry's

Electronic Centras
404-406 Electronic Components & Equipment 01 402 8381
354 PA Disco Lighting High Power Sound 01-402 8554
303 Special offers and bargains store
All mail to 303 Edgware Road London W2 1BW

Hi-Fi and
Electronics
Centres Open
9am - 6pm

Prices correct at time of preparation. Subject to change without notice. E & O E

ELECTRONIC FOOTBALL & TENNIS

WITH THE FABULOUS VIDEO SPORT

ON YOUR OWN TV

Play three exciting electronic ball games. FOOTBALL, TENNIS. HOLE IN THE WALL on your own TV! Just plug Video Sport into the aerial socket of your TV and away you go. Completely safe for you, your children and your TV. Mains operated.



OUR INCREDIBLE PRICE £29.50

Inc. VAT

DEMONSTRATIONS NOW IN ALL CENTRES!

AM/FM MODULES LP1179 LP1171

Combined AM/FM tuner modules, together with a small number of R.C.'s Ferrite aerials, make up a sensitive FM/MW/LW tuner.

6 volts Supply, supplied with data and circuit sheets.

LP1171 COMBINED IF STRIP £4.60

LP1179. FM FRONT END AND AM GANG £4.60.

£8.62 THE PAIR.

Suitable Ferrite aerial 87p.



UHF TV TUNERS

625 line receiver UHF transistorised tuners UK operation.

Brand new. (Post/packing 25p each).

TYPE A var. tun. slow motion drive £3.50.

TYPE C variable tuning £2.90.

TYPE B 4-button push button (adj.) £4.60.

TYPE D 6-button UHF/VHF tuner £5.20.

Build the Texan & FM Tuner TEXAN 20 + 20 W STEREO AMP

Features glass fibre PC board, Gardners low field transformer 6-IC's 10-transistors plus diodes etc. Designed by Texas Instruments engineers for Henry's and P.W. 1972. Overall size 15 1/2" x 2 1/2" x 6 1/2" mains operated. Free teak sleeve with every kit.

£29.95 (CARRIAGE 50p)

(also built and tested £39.95)

HENELEC STEREO FM TUNER

Features capacity diode tuning, lead and tuning meter indicators, mains operated. High performance and sensitivity. Overall size in teak sleeves 8" x 2 1/2" x 6 1/2". Complete kit with teak sleeve.

£26.25 (Carriage 50p).

(also built and tested £31.20).

JOIN THE LARGE BAND OF CONSTRUCTORS!

SPECIAL OFFER GARRARD CT4 STEREO CASSETTE TRANSPORT MECHANISM

Features

- Stereo Heads
- Built in Motor Stabiliser
- Auto Stop + Eject
- Pause Control
- 12V DC Operation



Robust, precision engineered mechanism based on the "STARR" patented design, ideal for use in Car stereo cassette players. Hi-Fi stereo cassette recorders, industrial and many other applications. Suitable for the 'PW' Ascot Stereo Cassette Deck.

£13.50 inc. VAT p & p 35p

FREE: SEND NOW FOR OUR FREE LIST NO. 36 FOR OUR COMPLETE RANGE OF OVER 10,000 SEMI-CONDUCTOR DEVICES AT NEW LOW PRICES.



TRAMPUS

Electronics Ltd.

WINDSOR, BERKS
58/60 GROVE RD;
SEND C.V.O. ADD VAT TO ALL PRICES IN U.K. P&P 15p. EXPORTS 50p.

Digital Displays


SLA7 RED LED 0.3" DIGIT 0-9DP 89p ea
GREEN&YELLOW £1.40
JUMBO LED 0.6" 747 DISPLAY £2.25 ea.
3015F 0-9DP £1 ea.
ZENON FLASH TUBE £4. Data 15p.

LEDS red 13p

LEDS 209 STYLE ONLY 13p ea
TTL 209 WITH CLIP RED 15p ea
TTL 211 & CLIP GREEN 29p ea
LARGE 0.2" & CLIP RED 17p ea
LARGE 0.2" CLIP GREEN 30p ea
209 STYLE OR .2"ORANGE 39p ea
INFRA RED LED £1.2N5777 33p.

PHOTO IC 81p

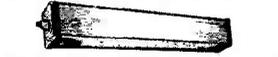TEC12 PHOTO AMP/SCMITT/RELAY DRIVER or LED TTL INTERFACE 81p



FLUORESCENT LIGHTS 12V MADE IN UK
8 WATT 13" £3. 13W 22" £3.50

DIGITAL CLOCK

IC AY51224 4 DIGIT CLOCK £3.75
MM5311/4 8 DIGIT CLOCK £7

CASSETTE mechanics £13.75

NEW 8tk CARTRIDGE MECHANISM £8
STEREO CASSETTE MECHANISM £13.75
Suitable for 'PW ASCOT' recorder with heads etc. SEND 15p for DATA

INTEGRATED CIRCUITS

| | |
|-----------------|------------------|
| 709 D114 28p | LM377 2x2Wt 87p |
| 555 TIMER 34p | LM380 2W AF 89p |
| 703 RF/IF 28p | LM381 2xPre £2 |
| 709 T099 23p | LM3900 4xOPA89p |
| 709 D1L 14 28p | MC1303 £1.20 |
| 710 D1L 14 34p | MC1306 49p |
| 723 Reg. 54p | MC1310&LEDt 65p |
| 741 D1L 8 27p | MC1312 SQ £2.10 |
| 741 D1L 14 29p | MC1330 69p |
| 741 T099 29p | MC1339 2xPre £1 |
| 747 2x741 70p | MC1350 55p |
| 748 D1L 8 33p | NE536 fetOPA £2 |
| 7805 5V £1.40 | NE540 Driver £1 |
| 7812 & 15 £1.40 | NE550 2Wref 79p |
| 76013 6W AF £1 | NE555 Timer 55p |
| 8038 SIG GEN £3 | NE556 2x" £1.20 |
| CA3028 £1 | NE560 PLL £3.15 |
| CA3046 55p | NE561 PLL £3.15 |
| CA3048 £2 | NE562 PLL £3.19 |
| CA3052 £1.50 | NE565 PLL £2.69 |
| CA3054 £1 | SN72709 709 28p |
| LM300 2-20V £2 | SN72741 741 26p |
| LM301 OPA 45p | SN72748 748 33p |
| LM304 OPA 45p | SN76660 IP £1 |
| LM307 OPA 49p | SN76611 IP £1.25 |
| LM308 HiBo 95p | TAD110 AIF £2 |
| LM309K 5V £1.48 | TR810 7WAF 99p |
| LM372 IF £1.80 | ZN414 RX £1.09 |

SPECIAL OFFERS

2N3055 FULL HIGH SPEC 115W 37p
741C 8PIN DIL 27p.MPC4000B 33p
NE555 TIMER 55p.ZN414 RX £1.09
BC109 9p.2N3819e 16p.BF751 15p

749 TTL

| | |
|-----------------|-----------------|
| 7490 GATES 13p | 7473/74/76 29p |
| 7494 INVERT 17p | 7475 45p |
| 7491/2/10etc14p | 7490 52p |
| 7413 SCMITT 31p | 7491/2/3/4 59p |
| 7440 BUFFER 14p | 74100 74175 £1 |
| 7447 DRIVER 89p | 74121 32p |
| 7470 & 7472 29p | 74123 59p |
| | 74141(&7441)73p |

TRANSISTORS & DIODES

| | | |
|-----------------|------------------|-----|
| Price each | MATCHING | 16p |
| AC127 & 128 16p | INS. BUSH SET10p | |
| AC187 & 188 19p | TIP 41 | 70p |
| AD149 43p | TIP 42 | 88p |
| AD161 & 162 33p | TIP 2955 | 90p |
| BC107 & 108 9p | TIP 3055 | 55p |
| BC109 10p | TS143 3x3x17mm | 43p |
| BC147/8/9 10p | ZTX109K301 | 13p |
| BC157/8/9 12p | 1N4001 | 4p |
| BC177/8/9 18p | 1N4004 & 7 | 7p |
| BC182/3/4&4L10p | 1N4148 & 914 | 49p |
| BC212/3/4&4L11p | 2N697 | 14p |
| BC270/1/2 17p | 2N706&8 | 11p |
| BD131 & 132 39p | 2N2646 UJT | 32p |
| BF851 | 2N2904 & 5 | 20p |
| BF850/51 23p | 2N2926royg | 9p |
| BF850/51 23p | 2N3053 | 17p |
| BF888 250V 29p | 2N3055 115W | 37p |
| BFY50/1/2 15p | 2N3563 & 64 | 16p |
| | 2N3614 | 49p |
| | 2N3702 & 3 | 9p |
| | 2N3704 & 7 | 9p |
| | MJE2955 | 65p |
| | 2N3706 & 8 | 9p |
| | 2N3708 & 9 | 8p |
| | 2N3710 & 11 | 10p |
| | 2N3819E FET | 16p |
| | 2N3823E FET | 17p |
| | 2N3904/5/6 15p | |

NEW TRAMPUS FULL SPEC PAKS

| | |
|--------------------------------|----|
| PAK A 10 RED LEDS our choice | £1 |
| PAK B 4 741 OP AMP " | £1 |
| PAK C 4 2N3055 £1. D 12 BC109 | £1 |
| PAK E 10 BC182 £1. F 11 2N3704 | £1 |
| PAK G 8 BFY51 £1. H 9 2N3819E | £1 |
| PAK J 9 2N3053 £1. K 40 1N914 | £1 |

| | | |
|-----------------|-----------------|-----|
| BZ88 400mW | 1A/50V SCR | 39p |
| ZENER DIODES 9p | TAG1/400 | 55p |
| BRIDGE RECT | C108 & 7 SCR D1 | 53p |
| 1A 50V | 4A/400V | 53p |
| BR100 DIAC | SC146D TRIAC | 75p |
| | 10A 400V | 75p |

vero NEW LOW PRICES!

VERO PINSx36 28p.
COPPER CLAD VEROBORD 4" 1"
2 1/2"x5" 29p 2 1/2"x3 1/2" 26p 3 1/2"x3 1/2" 31p.
3 1/2"x5" 31p 3 1/2" 17" £1.50
DIL IC'S BOARDS 6x4 1/2" £1.50
24 way edge connector 60p.
36 way 90p. PLAIN 3 1/2"x17" £1.
FACE CUTTER 45p. FEC ETC PAK 50p

DALopen69p

PRINTED CIRCUIT BOARD KIT £1.69
DECON NO MESS ETC PAK NEW 69p
DECON DESOLDER BRAID REEL 59p

HEATSINKS

5F/T05 & 18F/T018 5p ea. TV4 15p.
TV3/T03 16p. EXTRUDED 4" 4Y1 29p.
TG5308 GAS DETECTOR £1.80 ea.
LOGIC PROBE TTL TESTER PEN £5

CAPACITORS

CERAMIC 22pf to 0.1uf 50v 5p.
ELECTROLYTIC: 0.50/100 uf 1n 9p
10v 5p. 25v 6p. 50v 8p. 2uf/10v 5p.
1000 uf/25v 18p. 200/500 25v 9p.

POTENTIOMETERS (POTS) AB or BGIN

LIN or LOG ROTARY 13p. SWITCH 14p
DUAL 45p. SLIDERS 29p. STEREO 57p
KNOBS 7p. PRESETS 6p. RESISTORS 11p
SWITCHES: SPST 18p. DPDT 25p.

DIN PLUGS ALL 12p. SOCKETS 10p.

ALI CASES AB5/AB7 50p. AB13 65p.
TRANSFORMERS 1A 6v8v or 12v12v
Only £1.34. 100mA type CT 75p.

Oil sockets

TEXAS GOLD ea
LOW PROFILE 8, 14, & 16 PIN 13p
SOLDERCON STRIPS: 100 PINS 50p. 1K £3.





Log extracts

J. Porter:— 15m JA4HG/MM PY2ELV 20m CE6DT FG7AQ KA2AD KV4AAR YS1GW 5L2FH (Liberia) 8P6FU

P. Dawson:— 80m CP1AT EA9FC HP1GD VP2ABC (Barbuda) VP2VBG (Virgin Is) ZP5AL 20m CE1FA CP1AT FG7AR HR1LM KZ5RT TG9CQ VP1IL VS5MC 9N1MM 9Y4NB

P. Allen:— 20m A4XFX VQ9R 9X5PT

T. Charles:— 80m VP2AYL 8P6CP 40m HC2JN HK2DBK VK5QQ ZL4AW 20m FG7XE FP8CH HC2IK HP2BF OA2BJ VQ9MC YS1JWD 15m CE3RC VQ9SS/C (Chagos) ZS2JL 2m DR2NO (FM) via DB0SM GC8FBO OZ2BB


M. Connolly:— 80m CE6DP FP8DH JY3ZA PJ8HS 20m A4XVG C5AG C31LO KZ5JM VE8DC VP2SV 9X5SM

A. Swiffin:— 80m PJ8HS VP1PF 20m C5AM M1D 5L5F 10m OJ0MA

P. Barker:— 20m SSTV DJ7IC DL2AE HB9AQU 11MSV K1LEM YZ2CDS 20m KD4ITU OY8KH ZP5PT 15m SSTV ON5TB 15m ZD7FT ZD8RD 10m SSTV DK4NA DL1WX DL7HT 10m 8SK2AT

M. Bennett:— 80m 7X4MD 20m M1D TI2MEF 3B8DO (Mauritius) 15m M1C TU2FD VP8JC VP8NK VP8ML ZP5VO 7Q7RM 7X0WW

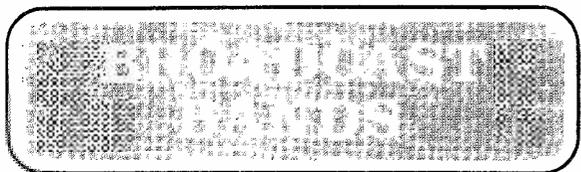All stations are SSB except those in bold which are CW.



SHORT WAVE BROADCASTS

by Derek Bell

A letter arrived "chez Bell" recently from a writer in London, who wishes to remain anonymous, asking "is it really a must to have an expensive communications set to pull in stations like Radio Nacional de Brasil?" On the face of it OM, no, but, and it's that little word that is the crux of the matter, while many SWLs (Short Wave Listeners) and DXers are content with their Astrads and VEFs there are a good many who, after a while, yearn to move on to bigger and better sets. They find that they would like a product detector or that they need the finer tuning that only a more expensive set can give. While we are now in a sunspot minimum and the more far-flung stations are beyond our reach, there will come a time when, as solar activity rises, the transistor portable sets will tend to become cluttered with signals and the AR88, or Trio or Codar with their better sensitivity, selectivity and suchlike refinements will come into their own. A lot of the present licensed amateur operators of today started out as SWLs and decided to seek something a little more complicated. So it seems that if a transistor portable fills your needs then stick with it, but if you seek to probe the far reaches of the bands then a communications receiver is a must.

After having indulged in a little philosophising Fred Tagg from Nottingham writes to show us a new wrinkle on DXing. He has hooked his PYE PM128 into a Celestion Ditton speaker and says that it really sounds good. His chimneys look like Jodrell Bank, says Fred, and his logbook has items like:—

- Radio Kuwait on 11940 at 1800
- Radio Israel on 12025 at 2030
- Ghana on 21545 at 1525

Fred also says that being an ex "met" man his main interest is CW transmissions of weather reports and wonders if anyone else has the same interest. Ian McLean of Port Glasgow in Scotland has come up against the bane of the SWL, TV timebase interference. Although he is using screened coax cable for his aerial he still gets a "buzzing sound". Ian, I am afraid that there is little that can be done to cure this. In continental countries the TV sets are lined with foil to reduce this nuisance but here in the UK manufacturers do not seem to bother.

Colour TV sets are the worst offenders and they can radiate over several hundred yards. I personally have a "gremlin" that I suspect is a thyristor in a nearby factory, which, on occasions, ruins my medium wave listening with a similar "buzzing sound". Ian says that while in Canada he got a Citizens Band licence and wonders why we cannot have a similar set-up here. Ah! why not, passed to you, Lord Annan.

More "gen" has been sent in regarding the summer changes to schedules. Geoff. Thompson from Lincoln reports that Radio Budapest is now airing its DX show on Tuesdays and Fridays at 1515 on 1340, 6025, 7175, 9585, 9833, 11910, 15125 and 17780. This same writer also has logged Radio Argentina al Exterio on 11710 at 2300 using a ITT Euromarine dangling on the end of 12 metres of wire.

Radio Canada International seem to be taking a close look at their mailing list as they are writing to every one of their members asking them to renew for a two-year period. They were kind enough to send a copy of the latest schedule which is as follows:—

- 0600 to 0800 on 7290 6100 in English, French and German.
- 1715 to 1800 on 17820, 15325, 7235, 5995 in German.
- 2005 to 2159 on 15325, 11855, 9685 in French and English.

These details apply to the European target area but the station also has a service for the USSR, Eastern Europe and Africa. I think the DXer here in the UK will be lucky to hear these since the aerial system at Sackville, New Brunswick will not be set to favour us. The World DX Club reports that Radio Pakistan is now asking for reports to be mailed to World Service P.O. Box 443 Karachi. This station runs two 1000 kilowatters at Islamabad and can be heard in English on 15115, 15325, 17700, 17830 and 21730 at various times during the day. They are also noted for dictation speed news broadcasts in English which I think must be unique on the short waves.

"I have also heard Radio Baghdad but I am not sure of the frequency except that it was in the 31m band." These words were penned by John Higginbotham of Holyhead and express the feelings of us all. Radio Baghdad is one of the most notorious "floaters" in the short wave spectrum. They were recently reported on 9735 in English at 1955 but their official frequency was announced as 9745 for



the English transmission at this time. On another occasion they were logged on 3240 at 1947 while for this time the announced freq. was 9745.

Jon Seddon joins us now, having just built himself a crystal set and fitted it with an ATU. Jon admits that the freqs. he logs are prone to be a little wayward as he only has a "crude tuning scale". He has, however, managed to get some accurate frequencies and these were marked on the dial and the dial then sub-divided with a pair of compasses to give a better readout. I hope, Jon, that you manage to build a more sensitive set, and that we 539kHz, Riyadh in Saudi Arabia on 587kHz with that I will draw the curtain now and wish you and yours best 73s.

MEDIUM WAVE DX by CHARLES MOLLOY

BABYLON, in Iraq, is the most recent addition to the growing number of megawatt broadcasters on the medium waves. Operating on 1038kHz with a power of 2000kW it beams towards North Africa and can be heard in the UK during the evening between European channels 1034kHz (Milan) and 1043kHz (Dresden). Other high power outlets to search for are Kuwait with 1500kW on 539kHz, Riyadh in Saudi Arabia on 587kHz with 1200kW, Istanbul on 1016kHz with 1200kW and two Libyan stations, El Beida on 1124kHz and Tripoli on 1250kHz each with 1000kW.

The Iberian peninsula is an interesting hunting ground for the medium wave DXer. In Spain there are chains of low power commercial stations spread across the country. Well over 100 of them transmit on 1106kHz, 1133kHz, 1394kHz, 1412kHz, 1430kHz, 1520kHz and 1570kHz and many of them sign-off between 2330 and midnight GMT. The DXer who listens on a single channel at this time can often hear one station after another become dominant only to be replaced after sign-off by a weaker companion. Use a loop to reduce QRM and listen on 1133kHz for ECS8 Sevilla, EFJ19 Castellon, EFJ46 Zaragoza; 1412kHz for EAJ16 Granada, EAJ17 Murcia, EAJ25 Tarrasa, EAJ64 Segovia; 1430kHz for EAK5 Valencia, EAK11 Malaga; 1475kHz for EAJ19 Asturias, EAJ59 Cadiz, EAJ60 Almeria, EAJ72 Zamora; 1570kHz for EFE10 Alava, ECS10 Mancha.

Mark Reddie of Edinburgh, who has been tuning round the medium waves with his Bang and Olufsen 600 receiver, reports hearing Radio Tirana at Durres in Albania on 1457kHz. Mark is building a MW loop aerial and hopes soon to own a communications receiver. **P. Bookbinder** (Shepherds Hill) is astonished to see the results achieved by DXers in reports to this column. He would now like to build a medium wave loop aerial and he wonders where he can obtain plans of one. Articles on loop construction have appeared in *Practical Wireless* issues April 1973 and November 1966. Although these issues are out of print, bound volumes of *Practical Wireless* are usually available in main libraries throughout the

UK. A medium wave loop is an indoor aerial that is tunable and directional. It is usually constructed in the shape of a square with a 40in side and has a main winding of seven turns tuned by a 500pF variable capacitor and there is a one-turn coupling winding which is connected to the aerial and earth terminals of the receiver. The windings are supported on a wooden frame. Maximum pick-up is along the plane of the windings and there are two nulls, directions of minimum pick-up, which are at right angles to the windings. When using a loop, peak up the signal with the loop tuning control and rotate the loop for optimum results.

Radio Andorra on 701kHz 300kW broadcasts in French, Spanish and in English (m'nt-0200) and Sud Radio Andorra 818kHz 900kW can be heard in French during the evening. Each station will send a QSL card in return for a correct reception report (and return postage in the form of an International Reply Coupon which is obtainable at main post offices). Andorra, which is a tiny republic in the Pyrenees located between France and Spain does not have a short wave service and the DXer who would like to add this "country" to his verification list will have to turn to the medium waves. The address of both stations is Andorra-la-Vielle, Andorra.

BROADCAST BANDS

Short Wave Reports by the 15th of the month to Derek Bell, c/o Practical Wireless, Fleetway House, Farringdon Street, London, EC4A 4AD. Medium Wave Logs to Charles Molloy, 132 Segars Lane, Southport, PR8 3JG.

'EASYBUILD' ELECTRONIC CLOCK

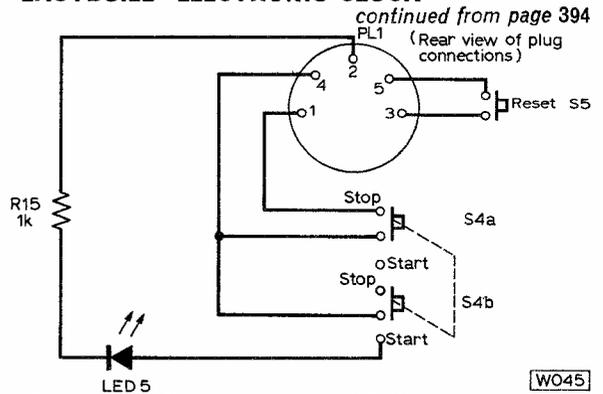


Fig. 6: Circuit of the remote control unit for the stop-clock facility. [W045]

physics laboratories for pendulum timing and other applications where timing to the nearest second is sufficient. It could also prove very useful for controlling circuit training activities for athletes and when switched to the Hours and Minutes display mode the stop/start function still operates. Thus the stop clock is perhaps unique in that it allows a stop/start facility over a 23 hour 59 minute period and this could be very useful in biological and bio-medical applications. Finally, the beauty is that by simply unplugging the remote control lead the device reverts to a very smart miniature desk clock to impress other executives, an attractive mantelpiece clock to impress your neighbours or a lovely bedroom clock to impress your wife! [PW]

LASKYS FOR CHOICE

SEW PANEL METERS

STOCKED AT
481 Oxford Street 311 Edgware Road
42 Tottenham Court Rd. 3 Lisle Street
branches or by mail order.

USED EXTENSIVELY BY
INDUSTRY, GOVERNMENT
DEPARTMENTS, EDUCATIONAL
AUTHORITIES ETC.

Over 200 ranges in stocked—other ranges to
order. Quantity discounts available. Send
for fully illustrated brochure.

CLEAR PLASTIC MODEL SD640

Size: 85 x 84mm

| | | | |
|--------------|-------|----------|-------|
| 50uA | £4.20 | | |
| 100uA | £4.10 | | |
| 200uA | £4.10 | | |
| 500uA | £4.05 | | |
| 50-0-500uA | £4.15 | | |
| 100-0-1000uA | £4.10 | | |
| 1mA | £4.05 | | |
| 5mA | £4.05 | | |
| 10mA | £4.05 | | |
| 50mA | £4.05 | | |
| 100mA | £4.05 | | |
| 500mA | £4.05 | | |
| 1A DC | £4.05 | 10V DC | £4.05 |
| 5A DC | £4.05 | 20V DC | £4.05 |
| 10A DC | £4.05 | 25V DC | £4.05 |
| 5V DC | £4.05 | 50V DC | £4.05 |
| | | 300V DC | £4.05 |
| | | VU Meter | £4.95 |

CLEAR PLASTIC MODEL SW180

Size: 100 x 80mm

| | | | |
|--------------|-------|----------|-------|
| 50uA | £5.05 | | |
| 100uA | £4.95 | | |
| 500uA | £4.75 | | |
| 50-0-500uA | £4.95 | | |
| 100-0-1000uA | £4.90 | | |
| 1mA | £4.75 | | |
| 1A DC | £4.75 | | |
| 5A DC | £4.75 | | |
| 20V DC | £4.75 | 150V AC | £4.90 |
| 50V DC | £4.75 | 300V AC | £4.90 |
| 300V DC | £4.75 | VU Meter | £6.25 |

MODEL ED107 EDUCATIONAL METER

Size: 100 x 90 x 150mm including terminals

A range of high quality moving coil instruments ideal for school experiments and other bench applications. 3" mirror scale. The meter movement is easily accessible to demonstrate internal working.

| | | | |
|------------|-------|-------------|-------|
| 50uA | £9.35 | | |
| 100uA | £9.70 | | |
| 50-0-500uA | £9.70 | | |
| 1mA | £9.40 | | |
| 1-0-1mA | £9.40 | | |
| 1A DC | £9.40 | 20V DC | £9.40 |
| 5A DC | £9.40 | 300V DC | £9.40 |
| 5V DC | £9.40 | 500mA 5A DC | £9.50 |
| 10V DC | £9.40 | 5V 50V DC | £9.50 |
| 15V DC | £9.40 | 5V 15V DC | £9.50 |
| | | 1A/15A DC | £9.50 |

CLEAR PLASTIC MODEL SD460

Size: 59 x 46mm

| | | | |
|--------------|-------|----------|-------|
| 50uA | £3.85 | | |
| 100uA | £3.80 | | |
| 200uA | £3.75 | | |
| 500uA | £3.70 | | |
| 50-0-500uA | £3.80 | | |
| 100-0-1000uA | £3.75 | | |
| 1mA | £3.65 | | |
| 5mA | £3.65 | 5V DC | £3.85 |
| 10mA | £3.65 | 10V DC | £3.85 |
| 50mA | £3.65 | 20V DC | £3.85 |
| 100mA | £3.65 | 50V DC | £3.85 |
| 500mA | £3.65 | 300V DC | £3.85 |
| 1A DC | £3.65 | 15V AC | £3.80 |
| 5A DC | £3.65 | 300V AC | £3.80 |
| 10A DC | £3.65 | VU Meter | £4.85 |

*Items with asterisk are Moving Iron type, all others are Moving Coil

CLEAR PLASTIC MODEL SD830

Size: 110 x 83mm

| | | | |
|--------------|-------|----------|-------|
| 50uA | £4.75 | | |
| 100uA | £4.65 | | |
| 200uA | £4.60 | | |
| 500uA | £4.55 | | |
| 50-0-500uA | £4.65 | | |
| 100-0-1000uA | £4.60 | | |
| 1mA | £4.50 | | |
| 5mA | £4.50 | | |
| 10mA | £4.60 | | |
| 50mA | £4.50 | | |
| 100mA | £4.50 | | |
| 500mA | £4.50 | | |
| 1A DC | £4.50 | 10V DC | £4.50 |
| 5A DC | £4.50 | 20V DC | £4.50 |
| 10A DC | £4.50 | 50V DC | £4.50 |
| 5V DC | £4.50 | 300V DC | £4.50 |
| | | 15V DC | £4.50 |
| | | 300V AC | £4.60 |
| | | VU Meter | £5.60 |

CLEAR PLASTIC MODEL MR 45P

Size: 50 x 50mm

| | | | |
|--------------|-------|-------------|--------|
| 50uA | £3.55 | | |
| 100uA | £3.50 | | |
| 200uA | £3.45 | | |
| 500uA | £3.30 | | |
| 50-0-500uA | £3.50 | | |
| 100-0-1000uA | £3.45 | | |
| 500-0-5000uA | £3.25 | | |
| 1mA | £3.25 | | |
| 5mA | £3.25 | | |
| 50mA | £3.25 | | |
| 100mA | £3.25 | | |
| 500mA | £3.25 | | |
| 1A DC | £3.25 | 15V AC | £3.40 |
| 5A DC | £3.25 | 30V AC | £3.40 |
| 10V DC | £3.25 | 5 Meter 1mA | £3.75 |
| 20V DC | £3.25 | VU Meter | £4.30 |
| 50V DC | £3.25 | 1A AC | £3.25 |
| 300V DC | £3.25 | 5A AC | £3.25* |
| | | 10A AC | £3.25* |
| | | 20A AC | £3.25* |
| | | 30A AC | £3.25* |

CLEAR PLASTIC MODEL MR 38P

Size: 42 x 42mm

| | | | |
|--------------|-------|-------------|-------|
| 50uA | £3.45 | | |
| 100uA | £3.40 | | |
| 200uA | £3.30 | | |
| 500uA | £3.10 | | |
| 50-0-500uA | £3.40 | | |
| 100-0-1000uA | £3.30 | | |
| 500-0-5000uA | £3.05 | | |
| 1mA | £3.05 | | |
| 1-0-1mA | £3.05 | | |
| 2mA | £3.05 | | |
| 5mA | £3.05 | | |
| 10mA | £3.05 | 10V DC | £3.05 |
| 20mA | £3.05 | 15V DC | £3.05 |
| 50mA | £3.05 | 20V DC | £3.05 |
| 100mA | £3.05 | 50V DC | £3.05 |
| 150mA | £3.05 | 100V DC | £3.05 |
| 200mA | £3.05 | 150V DC | £3.10 |
| 300mA | £3.05 | 300V DC | £3.10 |
| 500mA | £3.05 | 500V DC | £3.15 |
| 750mA | £3.05 | 750V DC | £3.15 |
| 1A DC | £3.05 | 15V AC | £3.15 |
| 5A DC | £3.05 | 50V AC | £3.15 |
| 10A DC | £3.05 | 150V AC | £3.15 |
| 1A DC | £3.05 | 300V AC | £3.15 |
| 5A DC | £3.05 | 500V AC | £3.30 |
| 10A DC | £3.05 | 5 Meter 1mA | £3.50 |
| 3V DC | £3.05 | VU Meter | £4.10 |

CLEAR PLASTIC MODEL MR 85P

Size: 120 x 110mm

| | | | |
|--------------|-------|---------|--------|
| 50uA | £6.00 | | |
| 100uA | £5.95 | | |
| 200uA | £5.90 | | |
| 500uA | £5.80 | | |
| 50-0-500uA | £5.95 | | |
| 100-0-1000uA | £5.90 | | |
| 500-0-5000uA | £6.65 | | |
| 1mA | £5.75 | | |
| 1-0-1mA | £5.75 | | |
| 5mA | £5.75 | | |
| 10mA | £5.75 | | |
| 50mA | £5.75 | | |
| 100mA | £5.75 | | |
| 500mA | £5.75 | | |
| 1A DC | £5.75 | 50V DC | £5.75 |
| 5A DC | £5.75 | 150V DC | £5.75 |
| 10A DC | £5.75 | 300V DC | £5.75 |
| 5A DC | £5.75 | 15V AC | £5.85 |
| 10A DC | £5.75 | 50V AC | £5.85 |
| 20V DC | £5.75 | 100V AC | £5.75* |
| 10V DC | £5.75 | 20A AC | £5.75* |
| 20V DC | £5.75 | 30A AC | £5.75* |

EDGWISE MODEL PE70

Size: 90 x 34mm

| | | | |
|--------------|-------|--|--|
| 50uA | £4.55 | | |
| 100uA | £4.50 | | |
| 200uA | £4.45 | | |
| 500uA | £4.30 | | |
| 50-0-500uA | £4.50 | | |
| 100-0-1000uA | £4.45 | | |
| 1mA | £4.25 | | |
| 10V DC | £4.25 | | |
| 300V DC | £4.25 | | |
| VU Meter | £5.50 | | |

BAKELITE MODEL S80 Enlarged Window

Size: 80 x 80mm

| | | | |
|--------------|-------|--|--|
| 50uA | £4.95 | | |
| 100uA | £4.80 | | |
| 500uA | £4.60 | | |
| 50-0-500uA | £4.80 | | |
| 100-0-1000uA | £4.85 | | |
| 1mA | £4.60 | | |
| 1A DC | £4.60 | | |
| 5A DC | £4.60 | | |
| 20V DC | £4.60 | | |
| 50V DC | £4.60 | | |
| 300V DC | £4.60 | | |
| 300V AC | £4.75 | | |
| VU Meter | £5.95 | | |

CLEAR PLASTIC MODEL MR 52P

Size: 60 x 60mm

| | | | |
|--------------|-------|-------------|--------|
| 50uA | £4.10 | | |
| 100uA | £3.85 | | |
| 500uA | £3.70 | | |
| 50-0-500uA | £3.85 | | |
| 100-0-1000uA | £3.70 | | |
| 1mA | £3.65 | | |
| 5mA | £3.65 | | |
| 10mA | £3.65 | | |
| 50mA | £3.65 | | |
| 100mA | £3.65 | | |
| 500mA | £3.65 | | |
| 1A DC | £3.65 | 5 Meter 1mA | £4.20 |
| 5A DC | £3.65 | VU Meter | £4.85 |
| 10V DC | £3.65 | 1A AC | £3.65* |
| 20V DC | £3.65 | 5A AC | £3.65* |
| 30V DC | £3.65 | 10A AC | £3.65* |
| 300V DC | £3.65 | 20A AC | £3.65* |
| 15V AC | £3.75 | 30A AC | £3.65* |
| 300V AC | £3.75 | | |

BAKELITE MODEL MR 65 Size: 80 x 80mm

| | | | |
|--------------|-------|----------|--------|
| 25uA | £5.80 | | |
| 50uA | £4.40 | | |
| 100uA | £4.35 | | |
| 500uA | £4.05 | | |
| 50-0-500uA | £4.35 | | |
| 100-0-1000uA | £4.30 | | |
| 500-0-5000uA | £3.95 | | |
| 1mA | £3.95 | | |
| 1-0-1mA | £3.95 | | |
| 5mA | £3.95 | | |
| 10mA | £3.95 | | |
| 50mA | £3.95 | | |
| 100mA | £3.95 | | |
| 500mA | £3.95 | | |
| 1A DC | £3.95 | | |
| 2A DC | £3.95 | | |
| 5A DC | £3.95 | | |
| 10A DC | £3.95 | | |
| 15A DC | £3.95 | | |
| 30A DC | £3.95 | | |
| 50A DC | £3.95 | | |
| 5V DC | £3.95 | | |
| 10V DC | £3.95 | | |
| 15V DC | £3.95 | | |
| 50V DC | £3.95 | | |
| 50V DC | £3.95 | | |
| 150V DC | £3.95 | | |
| | | 300V DC | £3.95 |
| | | 30V AC | £3.95* |
| | | 50V AC | £3.95* |
| | | 150V AC | £3.95* |
| | | 300V AC | £3.95* |
| | | 500V AC | £3.95* |
| | | VU Meter | £5.20 |
| | | 5A AC | £3.95* |
| | | 10A AC | £3.95* |
| | | 20A AC | £3.95* |
| | | 30A AC | £3.95* |
| | | 50A AC | £3.95* |
| | | 50mV DC | £4.15 |
| | | 100mV DC | £4.15 |

CLEAR PLASTIC MODEL MR 65P

Size: 86 x 78mm

| | | | |
|--------------|-------|-------------|--------|
| 50uA | £4.35 | | |
| 100uA | £4.25 | | |
| 200uA | £4.20 | | |
| 500uA | £4.15 | | |
| 50-0-500uA | £4.25 | | |
| 100-0-1000uA | £4.20 | | |
| 1mA | £4.10 | | |
| 1-0-1mA | £4.10 | | |
| 5mA | £4.10 | | |
| 10mA | £4.10 | | |
| 50mA | £4.10 | | |
| 100mA | £4.10 | | |
| 500mA | £4.10 | | |
| 1A DC | £4.10 | | |
| 5A DC | £4.10 | | |
| 10A DC | £4.10 | | |
| 15A DC | £4.10 | | |
| 20A DC | £4.10 | | |
| 30A DC | £4.25 | | |
| 50A DC | £4.10 | | |
| 5V DC | £4.10 | | |
| 10A DC | £4.10 | | |
| 15A DC | £4.10 | | |
| 15V DC | £4.10 | | |
| 20V DC | £4.10 | | |
| 50V DC | £4.10 | | |
| 150V DC | £4.10 | | |
| | | 300V DC | £4.10 |
| | | 16V DC | £4.20 |
| | | 50V AC | £4.20 |
| | | 150V AC | £4.20 |
| | | 300V AC | £4.20 |
| | | 500V AC | £4.20 |
| | | 5 Meter 1mA | £4.30 |
| | | VU Meter | £5.20 |
| | | 1A AC | £4.10* |
| | | 5A AC | £4.10* |
| | | 10A AC | £4.10* |
| | | 20A AC | £4.10* |
| | | 30A AC | £4.10* |
| | | 50A AC | £4.10* |
| | | 50mV DC | £4.10* |
| | | 100mV DC | £4.10* |
| | | 500mV DC | £4.10* |
| | | 1000mV DC | £4.10* |

240° Wide Angle 1mA METERS

| | |
|---------------------|--|
| MW1-6.60 x 60 mm | |
| £7.00 P/P & Ins 15p | |
| MW1-8.80 x 80mm | |
| £7.45 P & P Ins 15p | |


ALL PRICES INCLUDE VAT

BATTERY/LEVEL PANEL INDICATOR

18mm
18mm Panel mounting.

OUR PRICE
95p P/P

* & Ins 15p/Discounts for quantity.


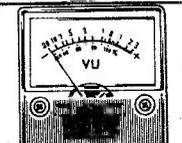


VU METER TYPE 3
250uA Size: 33mm x 20mm.
£1.55 P/P & Ins 15p

REDUCED TO CLEAR

YAMABISHI VARIABLE VOLTAGE TRANSFORMERS
Excellent quality

T MAKES SENSE TO
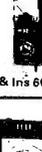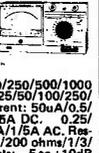
| | | | | |
|--|---|--|---|--|
| <p>HIOKI 730X 30,000 opv. Overload protection. 6/30/60/300/600/1200V DC. 12/60/120/600/1200V AC. 60/μA/30mA/300mA. 2K/200k. 2 Meg Ohm. -10 to +83 dB. OUR PRICE £8.10 P/P & Ins 30p</p>  | <p>U4312 MULTIMETER extremely sturdy instrument for general electrical use. 367 opv. 0/3/1.5/5/30/60/150/300/600/900V DC & 75mV. 0/3/15/12/120/60/150/300/600/900V AC. 0/300mA/1.5/6/15/150/60/600mA/1.5/6A DC. 0/1/5/16/15/60/150/600mA. 1.5/6A AC. 0/2/30k/30k ohms. DC accuracy 1%. AC 1.5%. Knife edge pointer, mirror scale. Complete with sturdy metal carrying case, leads and instructions. OUR PRICE £11.60 P/P & Ins 60p</p>  | <p>MODEL AS.100D VOM 100,000 opv. Mirror scale. Built-in meter protection. 0/3/12/60/120/300/600/1200V DC. 0/6/30/120/300/600V AC. 0/10μA/6/60/300mA/12 Amp. 0/2k/200k/2M/200 Meg Ohm. -20 to -17 dB. OUR PRICE £18.90 P/P & Ins 60p</p>  | <p>KAMODEN HM720B FET VOM Input impedance 10 Megohms. Ranges: 0/2.5/12/50/100V DC. 0/2.5/10/50/250/1000V AC. 0/25μA/2.5/25/250 mA DC. 0/5k/50k/500k/5 M 500 Megohms. OUR PRICE £24.30 P/P & Ins 60p</p>  | <p>RUSSIAN C116 Double Beam OSCILLOSCOPE 5 MHz pass band. Separate Y1 and Y2 amplifiers. Rectangular 5" x 4" CRT. Calibrated triggered sweep from 0.2μsec. to 100 milli-sec/cm. Free running time base. 50Hz-1MHz. Built-in time base. Calibrator and amplitude. Supplied complete with all accessories and instruction manual. OUR PRICE £93.95 P/P & Ins £2.00</p>  |
| <p>U4323 MULTIMETER 20,000 opv. Simple unit with audio/IF oscillator. Suitable for general receiver tuning. Ranges: 0.5/2.5/10/60/250/500/1000V DC. 0.5/2.5/10/15/250/500/1000V AC. 0.05/0.5/5/50/500mA DC. Resistance: x1, x10, x100, x1,000, x10,000 (50Ω). 60kΩ centre scale. Frequency operation. Size: 160 x 97 x 40mm. Supplied in carrying case complete with test leads. OUR PRICE £8.60 P/P & Ins 60p</p>  | <p>HIOKI 750X VOLT-OHM-MILLIAMETER 43 ranges: 0-0.3/0.6/2.5/10/15/250/500/1000V AC. 0.05/0.5/5/50/500mA DC. Resistance: x1, x10, x100, x1,000, x10,000 (50Ω). 60kΩ centre scale. Frequency operation. Size: 160 x 97 x 40mm. Supplied in carrying case complete with test leads. OUR PRICE £8.60 P/P & Ins 60p</p>  | <p>KAMODEN 360 MULTIMETER High sensitivity. DC 100kΩ/V AC 10kΩ/mV 5" mirror scale. overload protection. Ranges: 0.5/2.5/10/50/100/1000V DC. 5/10/50/250/1000V AC. Current: 0.01mA/0.5/5/50/500mA/10A. Resistance: 0.1/1/10/100 ohms. DC accuracy: 1%. AC 1%. 10/100 ohms. Decibels -20 to +62dB. Battery operated. Size: 180 x 140 x 80mm. Supplied complete with test leads etc. OUR PRICE £18.90 P/P & Ins 60p</p>  | <p>SWR METER Model SWR3 Handy SWR meter for transmitter antenna alignment, with built-in field strength meter. Accuracy 5%. Impedance 52Ω. Full scale 5 section collapsible antenna. Size: 145 x 50 x 60mm. OUR PRICE £4.55 P/P & Ins 60p</p>  | <p>MODEL TE15 GRID DIP METER Transistorised. Operates as Grid Dip, Oscillator, Absorption Wave Meter and Oscillating Detector. Frequency range 440kHz-20MHz in six coils. 500mA meter. 9V battery operation. Size: 180 x 80 x 40mm. OUR PRICE £18.90 P/P & Ins 30p</p>  |
| <p>TMK 200 MULTIMETER KIT Build yourself a quality 20000 opv multimeter and save money. Complete kit with meter scale, movement and rotary range selector ready mounted in cabinet. All parts, batteries, test prods and instructions. Ranges: 0/0.6/6/30/120/600/1200V DC. 0/6/30/120/600/600mA AC. Current: 0/0.6/6/80/600mA. Resistance: 0/10/100k/1/10 Meg ohms. Decibels: -20 to +83 dB. Size: 90 x 150 x 35mm OUR PRICE £9.65 P/P & Ins 30p</p>  | <p>TMK MODEL TW50K 46 ranges, mirror scale. 50kΩ DC 50kΩ AC. DC Volts: 0.125/0.25/1.25/2.5/5/10/25/50/125/250/1000V AC. DC current 25/50mA. 2.5/5/25/50/250/500mA. 10A. Resistance: 10k/100k/1 Meg. 10 Meg ohms. -20 to +81.5dB. OUR PRICE £13.50 P/P & Ins 60p</p>  | <p>Model HT100B4 MULTIMETER Overload protected, shock proof circuits. 9.5uA Meter with mirror scale. Sensitivity: 100kV. Polarity change switch. Ranges: 0.5/2.5/1.5/10/250/500/1,000 Volts DC. 2.5/10/50/250/1,000 Volts AC. DC resistance: 0-20/200k/2/20 Meg. ohms. DC current: 10/250uA/2.5/25/250 mA/10A. AC current: 0-10μA, -20 to +62dB. Operates from 2 x 1.5V batteries. Size: 180 x 134 x 79mm. OUR PRICE £21.50 P/P & Ins 60p</p>  | <p>U4341 Multimeter & Transistor Tester 27 ranges. 16,700 opv. Overload protected. Ranges: 0.3/1.5/5/30/60/150/300/600V DC. 1.5/5/30/150/300/600mA AC. Current: 0.05/0.6/6/60/600mA DC. 0.3/3/30/300mA AC. Resistance: 0.05/0.6/6/60/600mA DC. 0.6/2/6/20/60/200k ohms/2 Mohms. Battery operated. Supplied complete with probes, leads and steel carrying case. Size: 115 x 215 x 90mm. OUR PRICE £11.85 P/P & Ins 60p</p>  | <p>SINCLAIR DM2 DIGITAL MULTIMETER Will measure AC and DC volts, AC and DC current, and resistance in a total of 20 ranges. The large light emitting diode display will read up to 1999 and automatically indicate polarity. Indication of positive and negative overload is also provided. The instrument is fitted with a combined carrying handle and bench stand and sockets are provided for the connection of an external power supply. RANGES: DC VOLTS: 1v, 10, 100v, 1000v. AC VOLTS: 1v, 10v, 100v, 1000v. DC CURRENT: 1mA, 10mA, 100mA, 1000mA. AC CURRENT: 1mA, 10mA, 100mA, 1000mA. RESISTANCE: 1k, 10k, 100k, 1000k OUR PRICE £63.70 P/P & Ins 50p</p>  |
| <p>MODEL C7208FM 30,000 opv DC. 15,000 opv AC. 6/3/15/60/300/600/1200V DC. 6/30/120/600/1200V AC. DC Resistance x1, x10, x100, x1000 (50Ω centre scale) DC Current 30uA/3/30/300mA. -20 to +83dB. OUR PRICE £9.65 P/P & Ins 30p</p>  | <p>MODEL AF.105 VOM 50,000 opv. Mirror scale. Meter protection. 0/3/3/12/60/120/300/600/1200V DC. 0/6/30/120/600/1200V AC. 0/30uA/6/60/300mA/12 Amp. 0/10k/1m/10m/100 Meg Ohms. -20 to -17 dB. OUR PRICE £13.50 P/P & Ins 60p</p>  | <p>370WR MULTIMETER Features AC current ranges: 20,000 opv. 0/2.5/10/50/100/250/500/1000V DC. 0/2.5/10/50/250/500/1000V AC. 0/50uA/1/10/100 mA/1/10A DC. 0/100mA/1/10A AC. 0/5k/50k/500k/5 Meg/50 Meg. Decibels: -20 to +62dB. OUR PRICE £21.50 P/P & Ins 60p</p>  | <p>KAMODEN TT35 TRANSISTOR TESTER High quality instrument to test reverse leak current and DC current. Indication factor of NPN, PNP, diodes, transistors, 0.1's etc. 4" square clear scale meter. Operates from internal batteries. Complete with instructions, leads carrying handle. OUR PRICE £18.90 P/P & Ins 60p</p>  | <p>TRANSISTORISED L.C.R. A.C. BR/8 MEASURING BRIDGE A new portable bridge offering excellent range and accuracy at low cost. Resistance: 6 ranges: 0.1 ohm-11.1 megohm \pm 1% inductance: 6 ranges: 1 microhenry-111 henries \pm 2% Capacity: 6 ranges: 10pF-110 nF \pm 2% Turns Ratio: 6 ranges: 1:1/1000:1/11100:1 \pm 1% Bridge Voltage at 1.000cps. Operated from 9-volt battery, 100 micro-amp meter indication. Size 7 1/2" x 5" x 2" OUR PRICE £29.70 P/P & Ins 60p</p>  |
| <p>U4324 MULTIMETER High sensitivity. 20,000 opv. Ranges: 0.5/1.2/3/12/30/60/120/600/1200V DC. 3/6/15/60/150/300/600/900V AC. Current: 0.05/0.6/6/60/600mA/3A DC. 0.3/3/30/300mA AC. Resistance: 25/500 ohms/0.5/5/50/500k ohms/5 Mohms. Decibels: -10 to +12dB. Size 167 x 98 x 63mm. Complete with test leads, spare diode and instructions. OUR PRICE £10.60 P/P & Ins 60p</p>  | <p>MODEL 500 30,000 opv with overload protection. Mirror scale. 0/0.5/2.5/10/25/100/250/500/1000V DC. 0/2.5/10/25/100/250/500/1000V AC. 0/50uA/5/50/500mA/12A DC. 0/50k/6 meg/60 megohms. OUR PRICE £15.05 P/P & Ins 60p</p>  | <p>MODEL C7080EN Giant 6" mirror scale. 20,000 opv. 0/0.25/1.2/5/10/50/250/1000V DC. 0/2.5/10/50/250/1000V AC. 0/50uA/1/10/100/500mA/10A DC. 0/2k/200k/20 Meg. -20 to +50dB. OUR PRICE £21.50 P/P & Ins 60p</p>  | <p>LB4 TRANSISTOR TESTER Tests PNP or NPN transistors. Audio indication. Operates on two 1.5V batteries. Complete with instructions etc. OUR PRICE £4.85 P/P & Ins 20p</p>  | <p>TE-200 RF SIGNAL GENERATOR Accurate wide range signal generator covering 120 kHz-600 MHz on 6 bands. Directly calibrated. Variable RF attenuator audio output. Xtal socket for calibration 220/240V a.c. Brand new with instructions. Size 140mm x 215mm x 170mm. OUR PRICE £24.30 P/P & Ins 60p</p>  |
| <p>U91 Clamp VOLT AMMETER For measuring AC voltage and current without breaking circuit. Ranges: 300/600V AC. Current: 10/25/100/250/500A. Accuracy 4%. Size 283 x 54 x 36mm. Complete with carrying case, leads and fuses. OUR PRICE £15.10 P/P & Ins 60p</p>  | <p>U4317 MULTIMETER High sensitivity instrument for field and laboratory work. Knife edge pointer, 36mm mirror scale. Overload protection. Ranges: 100mV/0.5/2.5/10/25/50/100/250/500/1000V DC. 0.5/2.5/10/25/50/100/250/500/1000V AC. Current: 50uA/0.5/1/5/10/50/250mA/1/5A DC. 0.25/1.5/15/150/250mA/1/5A AC. Resistance: 0.5/10/100/200 ohms/1/3/30/300k ohms. Decibels: -5 to +10dB. Battery operated. Size: 210 x 115 x 63mm. Supplied in carrying case complete with leads. OUR PRICE £18.35 P/P & Ins 60p</p>  | <p>KAMODEN 72.200 Multitester High sensitivity meter. 200,000 opv. Overload protected. Mirror scale. Ranges: 0/0.06/3/30/300/1200V DC. 0/3/12/60/300/1200V AC. 0/5uA/0.5/5/50/500mA/12A DC. 0/2k/200k/2 Meg/200 Megohms. OUR PRICE £24.30 P/P & Ins 60p</p>  | <p>CIS PULSE OSCILLOSCOPE For display of pulsed and periodic waveforms in electronic circuits. VERT. G.M.P. Bandwidth: 10MHz. Sensitivity at 100kHz V/Div/mm: 0.1-25. HOR. AMP. Bandwidth: 500kHz. Sensitivity at 100kHz V/Div/mm: 0.3-25. Preset triggered sweep 1-300μsec. Free running 20-200 kHz. In mine expansion. Size: 220 x 360 x 430mm. 115-230V AC. OUR PRICE £47.50 P/P & Ins £1.50</p>  | <p>ALL PRICES INCLUDE VAT</p> |



a service that makes sense!

EXPORT Personal exports arranged for overseas visitors. Goods especially packed, insured and despatched to all parts of the world at minimum cost exclusive of VAT. Payment by bank transfer, certified cheque, postal order or money order in any currency.

CUSTOMER SERVICES Our Customer Services Division at Head Office will answer all your enquiries - just ring 01-2001321

BUY AT LASKYS

ALL PRICES INCLUDE VAT

TE22 SINE SQUARE WAVE AUDIO GENERATOR
Sine 20cps to 200kHz on 4 bands. Square 20 cps to 30 kHz. Output impedance 500 Ohms. 200/250V AC operation. Supplied brand new guaranteed, with instruction manual and leads.
OUR PRICE £26.90 P/P & Ins 60p



HANIMEX HDC 1900 DIGITAL ALARM CLOCK
240V operation with large clear numbers, night light and 'snooze' switch. Attractively finished in white and silver.
OUR PRICE £8.10 P/P & Ins £1.00



T.T.C. SPRITE STEREO HEADPHONES
Feather weight (5 oz) Dynamic stereo headphones providing high quality reproduction at a budget price. Soft removable ear pads and adjustable headband. Speaker Size: 28mm. Impedance: 8 Ohms. Frequency response: 30 - 13000 Hz.
OUR PRICE £2.40 P/P & Ins 30p



SAVE £9.35
ELIZABETHAN DCR26 DIGITAL CLOCK RADIO
A smaller than usual digital clock AM/FM radio, measuring only 8 1/2" x 3 1/4" d x 4" h. The DCR is finished in simulated teak veneer and is fitted with a pre-set sleep timer switch that will turn on the radio at the precise time chosen (Mains operated) List Price £24.25
OUR PRICE £14.90 P/P & Ins. £1.35



HIGH QUALITY CONSTRUCTION KITS
ALL PRICES REDUCED TO CLEAR
LIMITED STOCKS AT Oxford Street, 42 & 287 Tottenham Court Road, 1-2 Fleet Street, 311 Edgware Road, CROYDON BIRMINGHAM KINGSTON LEICESTER NORTHAMPTON SOUTHEND TUNBRIDGEWELLS WOLVERHAMPTON branches, or by Mail Order.
All kits are complete with comprehensive easy to follow instructions and covered by full guarantee. Post and Packing Ins. 15p per kit.

ARF 300 AF/RF SIGNAL GENERATOR
All transistorised compact fully portable. AF sine wave 18Hz to 220 kHz. AF square wave 18Hz to 100k Hz. Output Square/Sine wave 10V. P-P AF 100kHz to 200MHz. Output TV maximum 220/240V AC operation. Complete with instructions and leads.
OUR PRICE £40.50 P/P & Ins 60p



NEW GOLDRING G102 KIT
Belt-drive 2-speed turntable in kit form complete with pick up arm and head shell. P/P & Ins.
OUR PRICE £21.15 Ins £1.00



WALKIE TALKIES SKYFON NV7
Super low cost transmitter/receivers. 100MW with call buzzer and on/off volume control. 7 transistors. Telescopic rod antenna.
OUR PRICE £43.60 per PAIR P/P & Ins 50p
NOT LICENSABLE IN THE U.K.



SAVE £14.00
ELIZABETHAN 8/LZ-1
8-Track Stereo Player. Home 8-Track player with automatic and manual programme change and illuminated channel indicators for use with your hi fi system. Size 7 1/2" w x 12" D x 2 1/2" h. List Price £28.90.
OUR PRICE £14.90 P/P & Ins. £1.35



| | |
|--|--------|
| AF20 Mono amplifier..... | £5.05 |
| AF25 Mixer..... | £2.90 |
| AF30 Mono pre-amplifier..... | £3.40 |
| AF35 Emitter amplifier..... | £2.55 |
| AF80 0.5W mic. amplifier..... | £5.10 |
| AF305 Intercom..... | £8.45 |
| AF310/2 Mono Amplifier..... | £7.95 |
| M160 Multi-vibrator..... | £3.95 |
| M1302 Transistor tester..... | £7.05 |
| M131 VU Meter..... | £5.45 |
| M192 Stereo balance meter..... | £7.10 |
| LF380 Quadraphonic device..... | £11.45 |
| ATS Automatic light control..... | £17.55 |
| AT30 Photo cell switch unit..... | £5.65 |
| AT50 400W triac light dimmer/speed control..... | £24.35 |
| AT56 2,200W triac light dimmer/speed control..... | £10.82 |
| AT60 1 channel light control..... | £8.65 |
| AT65 3 channel light control..... | £4.05 |
| GU330 Tremolo unit..... | £3.40 |
| HF61 Diode detector..... | £3.85 |
| HF65 FM transmitter..... | £17.30 |
| HF75 FM receiver..... | £27.95 |
| HF10 FM tuner..... | £11.15 |
| HF325 Deluxe FM tuner..... | £6.35 |
| HF330 Decoder (HF310/325)..... | £2.20 |
| GP310 Stereo amplifier..... | £8.90 |
| GP312 Circuit board..... | £2.25 |
| GP304 Circuit board..... | £6.85 |
| HF380 Iw/vhi aerial amplifier..... | £5.95 |
| HF395 broadband aerial amp..... | £5.25 |
| NT10 Stabilised power supply 100mA, 9V..... | £8.80 |
| NT300 Stabilised p. supply..... | £13.95 |
| NT310 Power Supply 240 V AC 2 x 18 V D.C. at 2 amps..... | £5.95 |
| NT305 Voltage converter..... | £5.95 |
| NT315 Power supply 240V AC to 4.5/15V DC, 500mA..... | £12.75 |

MODEL TE20 RF SIGNAL GENERATOR
Six bands. 120kHz - 200MHz. Dual output RF terminals. Separate variable audio output. Accuracy ± 2%. Audio output to 8V. Power requirements: 105 - 125V, 220 - 240V AC. Size: 13 x 26.5 x 150mm. Complete with test leads etc.
OUR PRICE £20.45 P/P & Ins 60p



SUPERB QUALITY LOW PRICES
AUDIOTRONIC DIGITAL CLOCK RADIOS
ADC22 24-hour clock radio, covering MW/FM wavebands. 180-minute sleep timer. Choice of Gray or White cabinet. P/P & Ins.
OUR PRICE £17.50 Ins £1.00



SINCLAIR Project 80 Modules
240 Power Amp. £5.80 P/P & Ins. 15p
280 Power Amp. £8.95 P/P & Ins. 15p
Stereo 80 Pre-Amp. £13.10 P/P & Ins. 15p
Active Filter Unit. £7.40 P/P & Ins. 15p
FM Tuner. £13.10 P/P & Ins. 15p
Stereo Decoder. £8.40 P/P & Ins. 15p
P25 Power Supply. £4.65 P/P & Ins. 30p
P26 Power Supply. £7.30 P/P & Ins. 30p
P28 Power Supply. £7.30 P/P & Ins. 30p
Transformer for P25 £5.10 P/P & Ins. 30p

SAVE £14.00
ELIZABETHAN 8/LZ-1
8-Track Stereo Player. Home 8-Track player with automatic and manual programme change and illuminated channel indicators for use with your hi fi system. Size 7 1/2" w x 12" D x 2 1/2" h. List Price £28.90.
OUR PRICE £14.90 P/P & Ins. £1.35



LASKYS make sense of Hi-Fi

ADC33 Deluxe 24-hour clock radio covering MW/FM wavebands. 180-minute sleep timer. Buzzer alarm. Tone control. P/P & Ins.
OUR PRICE £19.95 Ins £1.00



AUDIOTRONIC AHA101 Stereo Headphone Amplifier
All silicon transistor amplifier operates from magnetic, ceramic or tuner inputs with twin stereo headphone outputs and separate volume controls for each channel. Operates from 9V battery. INPUTS: 5mV and 100mV. OUTPUT: 50mV per channel.
OUR PRICE £10.65 P/P & Ins 30p



FREE CATALOGUE
LASKYS 32 PAGE CATALOGUE AND PRICE LIST - absolutely free and available from all stores or by post (see coupon below). This exciting catalogue provides a comprehensive selection from the largest Hi-Fi Retailer in Europe - a MUST for every Hi-Fi and electronics specialist.

Amateur Electronics by Josty-Kit, the professional books for the amateur - covers the subject from basic principals to advanced electronic techniques. Complete with circuit board for AE1 to AE10 listed below.
OUR PRICE £3.30 (No VAT)

| | |
|------------------------------------|-------|
| AE1 100mW output stage..... | £1.60 |
| AE2 Pre-amplifier..... | £1.40 |
| AE3 Diode receiver..... | £2.15 |
| AE4 18 V D.C. at 2 amps..... | £1.30 |
| AE5 Astable multi-vibrator..... | £1.15 |
| AE6 Monostable multi-vibrator..... | £1.10 |
| AE7 RC generator..... | £1.10 |
| AE8 Bass filter..... | £1.10 |
| AE9 Treble filter..... | £1.10 |
| AE10 CCIR filter..... | £1.10 |

AUDIOTRONIC HEADPHONES
LSH20 Individual volume controls. Mono/stereo switch. 40-19,000 Hz. 8 Ohms.
OUR PRICE £6.25 P/P & Ins 50p



MINIATURE ORGAN MUSIC MASTER AM100
Spanning nearly two octaves, including semi-tones. This instrument will give hours of enjoyment to all the family. Beautifully finished. The Keyboard range can be adjusted to be in tune with any instrument. Operates from internal 9V battery. Fitted with on/off switch, vibrate switch, earphone socket and external 9V D.C. socket. Size 229mm x 127mm x 64mm.
OUR PRICE £9.95 P/P & Ins 60p



RANK AUDIO RA 210T STEREO AMPLIFIER
7 1/2 - 7 1/2 watts rms. Inputs for magnetic phono, tuner, tape and aux. Separate base, treble, balance and volume controls. Headphone socket. Teak case. Unrepeatable offer. P/P & Ins.
OUR PRICE £21.85 Ins £1.00



LSH30 Individual tone and volume controls. Mono/stereo switch. 30-20,000 Hz. 8 Ohms.
OUR PRICE £8.95 P/P & Ins 30p



LSH40 Two-way speaker system. Individual volume controls. 20-20,000 Hz. 8 Ohms.
OUR PRICE £11.75 P/P & Ins 30p



your nearest store

| | | | |
|--------------------------------|--------------|---|----------|
| CENTRAL LONDON | (01) | LEICESTER 45 Market Pl. | 537678 |
| 481 Oxford Street, W1 | 493 8641 | NORTHAMPTON | |
| 10 Tottenham Court Rd. W1 | 637 2232 | 78 Abington Street | 35753 |
| 33 Tottenham Court Rd. W1 | 636 2605 | NOTTINGHAM | |
| 42/45 Tottenham Ct. Rd. W1 | 636 0849 | 5-7 Lower Parliament St | 48987 |
| 257/8 Tottenham Ct. Rd. W1 | 380 0670 | OXFORD 16 Westgate Centre | 722870 |
| 3 Lisle Street, WC2 | 437 8204 | RICHMOND 32 Hill Street | 948 1441 |
| 118 Edgware Road, W2 | 723 9789 | ROMFORD 85 South Street | 20218 |
| 193 Edgware Road, W2 | 723 6211 | SOUTHEND | |
| 207 Edgware Road, W2 | 723 3271 | 205/206 Churchill West | 612241 |
| 311 Edgware Road, W2 | 262 0387 | TUNBRIDGE WELLS | |
| 345 Edgware Road, W2 | 723 4453 | 53/57 Camden Road | 23242 |
| 382 Edgware Road, W2 | 723 4194 | WOLVERHAMPTON | |
| 109 Fleet Street, EC4 | 353 5812 | 30 Wulfrun Way | 23384 |
| 152/3 Fleet Street, EC4 | 353 2833 | NEW BRANCH AT READING | |
| BIRMINGHAM | | OPENING AUGUST | |
| 116 Corporation Street | 021-236 3503 | All prices correct at 16/8/75 but subject to change without notice E. & O. E. | |
| BRISTOL | | ALL PRICES INCLUDE VAT. | |
| 16-18-20 Penn Street | 20421 | | |
| CROYDON | | | |
| 1046 Whitgift Centre | 681 3027 | | |
| KINGSTON 38/40 Eden St. | 546 1271 | | |

TO LASKYS CUSTOMER SERVICES DIVISION Audiotronic House, The Hyde, London NW9 6JJ. Tel: 01-200 1321

Please send me the following items

Name _____

Address _____

Signature _____

TOTAL PURCHASE PRICE _____ (inc. P/P & Ins.)

Please send me your Free 32-page Hi-Fi catalogue price list I enclose cheque postal order money order

I wish to pay by Barclaycard/Access and my number is _____

Registered in England No. 347947 at 12 Lower Grosvenor Place, London SW1 0EX **PW9**

CRYSTAL CALIBRATOR CT432 mains operated unit giving O/ps at 100Kc, 1 Mc/s and 10 Mc/s these 3 O/Ps are obtained from 3 separate crystals, also as provision for feeding in ext freq to give beat freq using phones supplied with copy of H/B, a fuller disc of these very neat units on our list **£19.**

AIRCRAFT H.F. Rx type R4187 and Control Box these are a crystal controlled Rx intended for remote control and will provide up to 24 channels in the range 2.8 to 18Mc/s the Rx is a dual conversion type with 2 RF stages, I.F. filters of 3Kc and 500c/s, BFO, N.L. AVC. O/P stage, uses 16 B7g valves, 1st IF 2.15Mc/s 2nd IF 100Kc. Normal power 1/P 24 and 19v DC (or 200v HT and 19v DC) crystals required are HC6/u tube not supplied, supplied with control box and manual **£16.20.**

SIGNAL GENERATORS type TF144G made by Marconi standard radio type covers 85Kc to 25 Mc/s in 8 ranges, O/P variable from 1Uv to 1 volt, int mod var up to 70% at 400c/s fitted meter to read RF and Mod levels provision for ext mod. Supplied tested for use on 200/250v mains with circ, inst, leads **£25.**

ROLLER COASTERS coil 5 x 1 1/2" dia 36 turns silver plated fittings and carbon brush **£3.30.**

SPECTRUM FILTERS contain 10 type LA2 pot cores, 10 neons and 10 1% conds, consists of 10 tuned circs in the 20 to 100Kc range **£2.40.**

CRYSTALS type FT243 in range 5-6 to 8.3Mc/s new 5 different for **£1.20.**

TAPE HEADS for use on 8 chan units low impedance new **£1.20.**

STRIPPER UNITS function not known contains DC motor 24v 1/8th HP 8000 RPM, also gears, clutches, solenoids, etc. **£8.50.**

FLUORESCENT LIGHTING CHOKES as follows type A for 2 x 12" 8w tubes **£1.20.** B for 5ft 65w tube **£1.40** and C for 8ft 125w tube **£1.90.**

RELAYS moving coil type very sensitive coil 200 Ua 100 and 47 ohm 1p c/o with base **£1.** Micropositioner relay precision polar relay 2 x 3.5K coils, 1p c/o, high speed, octal base new **£1.50.** Sealed type 12v on B7g base 1p c/o low current coil 2k size 1 1/2 x 1 1/2" new **50p.**

T.V. FILTER units made to fit in Ae lead fully screened all box size 4 1/2 x 1 1/2 x 1 1/2" fitted standard coax plug and sk, okay for Ae pre amp new 3 for **£1.** R.F. O/P Indicator consists of 100 watt dummy load 70 ohm with RF meter 0 to 2 amps in neat case, for use up to 20Mc/s new cond **£4.**

SPEAKERS small 3 1/2" sq 15 ohm coil new **£1.30.**
HANDSETS GPO style black with inserts new **£1.50** or less cord **£1.25.**

SMALL WOODEN BOXES ext size 10 1/2 x 7 x 6" with hinged lid and int fittings 4 for **£3.**

YAXLEY SWTS all new 2p 11w 2b 40p. 4p 11w 4b 75p. 8p 5w 4b 65p. 2p 6w 1b 360° rotation plus dummy wafers 55p. 6p 2w 3b 45p.

CRYSTAL OVENS with heater and thermostat for 24v DC also contain 12 type HC6/u holders these can be removed **90p.**

SMALL BLOWER motors double ended type for use on 6 to 28v DC overall size 6 x 3 1/2" new boxed **£3.20.**
TRIMMERS small air spaced type 20pf ceramic base new. 10 for **70p.** Circs and Manuals available.

Above prices inc Carr and VAT. SAE for list No. 12/1 or enquiry. Goods ex equipment unless stated otherwise.

A. H. SUPPLIES

57 MAIN RD., SHEFFIELD S9 5HL. 444278 (0742)

Marshall's

A. Marshall (London) Ltd Dept: PW
42 Cricklewood Broadway London NW2 3ET Tel: 01-452 0161/2
Telex: 21492
& 85 West Regent St Glasgow G2 2QD Tel: 041-332 4133
& 1 Straits Parade Fishponds Bristol BS16 2LX
Tel: 0272 654201/2
& 27 Rue Danton Issy Les Moulineaux Paris 92 Tel: 642 2985
Catalogue price 25p Trade and export enquiries welcome

Our range covers over 7,000 items. The largest selection in Britain

Top 200 IC's TTL, CMOS & Linears

| | | | | | | | | | |
|---------|-------|---------|-------|----------|-------|---------|-------|----------|-------|
| CA3018A | 85p | CD4043 | £1.80 | NE565 | £4.48 | SN7448 | 90p | SN74157 | 95p |
| CA3020A | £1.80 | CD4044 | £1.80 | SL1414 | £1.80 | SN7450 | 16p | SN74160 | £1.10 |
| CA3028A | 79p | CD4045 | £2.65 | SL610C | £1.70 | SN7451 | 16p | SN74161 | £1.10 |
| CA3035 | £1.37 | CD4046 | £2.84 | SL611C | £1.70 | SN7453 | 16p | SN74162 | £1.10 |
| CA3046 | 70p | CD4047 | £1.65 | SL612C | £1.70 | SN7454 | 16p | SN74163 | £1.10 |
| CA3048 | £2.11 | CD4049 | 81p | SK620C | £2.70 | SN7460 | 16p | SN74164 | £2.01 |
| CA3052 | £1.62 | CD4050 | 66p | SL621C | £2.60 | SN7470 | 33p | SN74165 | £2.01 |
| CA3089E | £1.96 | LM301A | 49p | SL623C | £4.59 | SN7472 | 26p | SN74167 | £4.10 |
| CA3090Q | £4.23 | LM380 | £2.50 | SL640C | £3.10 | SN7473 | 36p | SN74174 | £1.25 |
| CD4000 | 36p | L005TL | £1.80 | SN7400 | 16p | SN7474 | 36p | SN74175 | 90p |
| CD4001 | 36p | LM390 | £1.10 | SN7401 | 16p | SN7475 | 50p | SN74176 | £1.44 |
| CD4002 | 36p | LM381 | £2.20 | SN7401AN | 38p | SN7476 | 35p | SN74177 | £1.40 |
| CD4006 | £1.58 | LM702C | 75p | SN7402 | 16p | SN7480 | 50p | SN74181 | £1.95 |
| CD4007 | 36p | LM709 | 35p | SN7403 | 16p | SN7481 | £1.25 | SN74181 | £1.95 |
| CD4008 | £1.63 | BDIL | 49p | SN7404 | 19p | SN7482 | 75p | SN74190 | £2.30 |
| CD4009 | £1.18 | 14DIL | 40p | SN7405 | 19p | SN7483 | 95p | SN74191 | £2.30 |
| CD4010 | £1.18 | LM710 | 47p | SN7406 | 45p | SN7484 | 95p | SN74192 | £1.15 |
| CD4011 | 36p | LM723C | 90p | SN7407 | 47p | SN7485 | £1.25 | SN74193 | £1.15 |
| CD4012 | 36p | LM741C | 40p | SN7408 | 19p | SN7486 | 32p | SN74196 | £1.60 |
| CD4013 | 66p | BDIL | 40p | SN7409 | 22p | SN7490 | 45p | SN74197 | £1.58 |
| CD4014 | £1.72 | 14DIL | 38p | SN7410 | 16p | SN7491 | 85p | SN74198 | £2.25 |
| CD4015 | £1.72 | LM747 | £1.05 | SN7411 | 25p | SN7492 | 45p | SN74199 | £2.25 |
| CD4016 | 66p | LM748 | 60p | SN7412 | 28p | SN7493 | 45p | SN76003N | £2.92 |
| CD4017 | £1.72 | 14DIL | 75p | SN7413 | 35p | SN7494 | 82p | SN76013N | £1.95 |
| CD4018 | £2.55 | LM3900 | 70p | SN7414 | 72p | SN7495 | 75p | SN76023N | £1.60 |
| CD4019 | 86p | LM7805 | £2.50 | SN7417 | 35p | SN7496 | 75p | SN76033N | £2.92 |
| CD4020 | £1.91 | LM7812 | £2.50 | SN7420 | 16p | SN74100 | £1.25 | SN76033N | £2.92 |
| CD4021 | £1.72 | LM7815 | £2.50 | SN7423 | 29p | SN74107 | 36p | TAA263 | £1.10 |
| CD4022 | £1.66 | LM7824 | £2.50 | SN7425 | 29p | SN74118 | £1.00 | TAA300 | £1.10 |
| CD4023 | 36p | MCI303L | £1.50 | SN7427 | 29p | SN74119 | 19¢ | TAA550 | 60p |
| CD4024 | £1.24 | MCI318P | £2.59 | SN7430 | 16p | SN74121 | 37p | TAA611C | £2.18 |
| CD4025 | 32p | MCI330P | 90p | SN7432 | 28p | SN74122 | 50p | TAA621 | £2.03 |
| CD4027 | 43p | MCI351P | 80p | SN7437 | 35p | SN74123 | 60p | TAA661B | £1.32 |
| CD4028 | £1.50 | MCI352P | 80p | SN7438 | 35p | SN74141 | 85p | TAA661B | £1.32 |
| CD4029 | £3.50 | MCI466L | £3.50 | SN7440 | 16p | SN74145 | 90p | TBA651 | £1.69 |
| CD4030 | 87p | MCI469R | £2.75 | SN7441AN | 85p | SN74150 | £1.50 | TBA800 | £1.40 |
| CD4031 | £5.19 | NE555V | 70p | SN7442 | 65p | SN74151 | 85p | TBA810 | £1.40 |
| CD4037 | £1.93 | NE560 | £4.48 | SN7444 | 95p | SN74153 | 85p | TBA810 | £1.40 |
| CD4041 | £1.86 | NE560 | £4.48 | SN7449 | 95p | SN84154 | £1.50 | TBA820 | £1.15 |

BRISTOL 10% discount for callers at our new shop at 1 Straits Parade, Fishponds, Bristol, BS16 2LX DURING AUGUST. Tel: 0272 654201/2

POPULAR SEMICONDUCTORS

| | | | | | | | | | |
|---------|---------|--------|-------|---------|-------|---------|---------|----------|-------|
| 2N696 | 22p | 2N3906 | 27p | AF139 | 65p | BD139 | 71p | MPSA56 | 31p |
| 2N697 | 12p | 2N4037 | 42p | AF239 | 65p | BD140 | 87p | OC28 | 76p |
| 2N698 | 82p | 2N4036 | 67p | AF240 | 90p | BF115 | 80p | OC35 | 60p |
| 2N699 | 59p | 2N4058 | 18p | AF279 | 70p | BF117 | 55p | OC42 | 50p |
| 2N700 | 14p | 2N4289 | 34p | AJ280 | 79p | BF134 | 20p | TAAC45 | 32p |
| 2N708 | 17p | 2N4289 | 34p | AI102 | £1.00 | BF159 | 27p | TIP29A | 90p |
| 2N916 | 28p | 2N4920 | £1.10 | BC107 | 14p | BF180 | 35p | TIP29C | 58p |
| 2N918 | 32p | 2N4921 | 83p | BC108 | 14p | BF181 | 36p | TIP31A | 62p |
| 2N1302 | 18 1/2p | 2N4923 | £1.00 | BC109 | 14p | BF184 | 40p | TIP32A | 74p |
| 2N1304 | 26p | 2N5245 | 47p | BC147B | 14p | BF194 | 12p | TIP33A | £1.01 |
| 2N1306 | 31p | 2N5246 | 49p | BC148B | 15p | BF195 | 12p | TIP34A | £1.51 |
| 2N1308 | 47p | 2N5296 | 48p | BC149B | 15p | BF196 | 13p | TIP35A | £2.90 |
| 2N1711 | 45p | 2N5457 | 49p | BC157A | 16p | BF197 | 15p | TIP36A | £3.70 |
| 2N2102 | 60p | 2N5458 | 46p | BC158A | 16p | BF198 | 18p | TIP42A | £0.90 |
| 2N2147 | 78p | 2N5459 | 49p | BC167B | 15p | BF244 | 21p | TIP295 | 90p |
| 2N2148 | 94p | 2N6027 | 45p | BC168B | 15p | BF257 | 47p | TIP305S | 50p |
| 2N218A | 22p | 3N128 | 73p | BC169B | 15p | BF258 | 53p | TIS43 | 28p |
| 2N219A | 26p | 3N140 | £1.00 | BC192 | 12p | BF259 | 55p | ZTX300 | 13p |
| 2N2220 | 25p | 3N141 | 81p | BC182L | 12p | BF561 | 27p | ZTX301 | 8p |
| 2N2221 | 18p | 3N200 | £2.49 | BC183 | 12p | BF598 | 25p | ZTX500 | 15p |
| 2N2222 | 20p | 40361 | 40p | BC183L | 12p | BFR39 | 24p | ZTX501 | 13p |
| 2N2369 | 20p | 40362 | 45p | BC184 | 13p | BFR79 | 24p | ZTX502 | 18p |
| 2N2646 | 55p | 40406 | 44p | BC184L | 13p | BFX29 | 30p | IN914 | 7p |
| 2N2904 | 22p | 40407 | 35p | BC212A | 16p | BFX30 | 27p | IN375A | 15p |
| 2N2905 | 25p | 40408 | 50p | BC212LA | 16p | BFX84 | 24p | IN4007 | 10p |
| 2N2906 | 19p | 40409 | 52p | BC213LA | 15p | BFX85 | 30p | IN4148 | 7p |
| 2N2907 | 22p | 40410 | 52p | BC214LB | 18p | BFX88 | 25p | IN5404 | 22p |
| 2N2924 | 20p | 40411 | £2.00 | BC237B | 16p | BFY50 | 22 1/2p | IN5408 | 30p |
| 2N2926G | 12p | 40594 | 74p | BC238C | 15p | BFY51 | 23p | AA119 | 8p |
| 2N3053 | 25p | 40595 | 84p | BC239P | 15p | BFY52 | 20 1/2p | BA102 | 25p |
| 2N3054 | 60p | 40596 | £1.10 | BC257A | 16p | BFY59 | 46p | BA145 | 18p |
| 2N3055 | 75p | 40603 | 73p | BC258B | 16p | ME0402 | 20p | BA154 | 12p |
| 2N3391 | 28p | AC162 | 20p | BC259B | 17p | ME0412 | 18p | BA155 | 12p |
| 2N3392 | 15p | AC127 | 20p | BC301 | 34p | ME4102 | 11p | BB103B | 23p |
| 2N3393 | 15p | AC128 | 20p | BC307B | 17p | M1480 | 95p | BB104B | 45p |
| 2N3440 | 59p | AC151 | 27p | BC308A | 15p | M1481 | £1.20 | BY126 | 12p |
| 2N3442 | £1.48 | AC152 | 49p | BC309C | 20p | M1490 | £1.05 | BY127 | 12p |
| 2N3638 | 15p | AC156 | 35p | BC134 | 23p | M1952 | 70p | BYZ11 | 51p |
| 2N3702 | 12p | AC176 | 30p | BC328 | 22p | M12955 | £1.00 | BYZ12 | 51p |
| 2N3703 | 13p | AC187K | 35p | BCY70 | 17p | MJE340 | 48p | OA47 | 6p |
| 2N3704 | 15p | AC188K | 40p | BCY71 | 22p | MJE370 | 65p | OA81 | 18p |
| 2N3706 | 15p | AD143 | 68p | BCY72 | 15p | MJE371 | 75p | OA90 | 6p |
| 2N3708 | 14p | AD161 | 30p | BD121 | £1.00 | MJE920 | 60p | OA91 | 6p |
| 2N3714 | £1.38 | AD162 | 59p | BD123 | 82p | MJE921 | 70p | WO21A200 | 18p |
| 2N3716 | £1.80 | AF106 | 40p | BD134 | 23p | MJE255 | £1.20 | BY164 | 32p |
| 2N3773 | £2.65 | AF109 | 40p | BD131 | 40p | MJE3055 | 75p | ST2diac | 20p |
| 2N3789 | £2.06 | AF116 | 35p | BD132 | 50p | MPF102 | 39p | 40669 | £1.00 |
| 2N3819 | 37p | AF117 | 35p | BD136 | 47p | MPSA05 | 25p | TIC44 | 29p |
| 2N3820 | 64p | AF118 | 35p | BD137 | 55p | MPSA06 | 31p | CI06D | 65p |
| 2N3904 | 27p | AF124 | 30p | BD138 | 63p | MPSA55 | 31p | ORP12 | 60p |

Prices correct at August 1975, but all exclusive of

SPARKRITE MK 2

CAPACITIVE DISCHARGE ELECTRONIC IGNITION KIT

Sparkrite Mk. 2 is a high performance, high quality, capacitive discharge, electronic ignition system. Because of the superb design of the Sparkrite circuit it completely eliminates problems of the contact breaker. There is no misfire because contact breaker bounce is eliminated electronically by a pulse suppression circuit which prevents the unit firing if the points bounce open at high R.P.M. Contact breaker burn is eliminated by reducing the current to about 1/50th of the norm. It will perform equally well with new, old, or even badly pitted points and is not dependent upon the dwell time of the contact breaker for recharging the system.

Sparkrite incorporates a short circuit protected inverter which eliminates the problems of SCR lock on and therefore eliminates the possibility of blowing the transistors or the SCR. (Many capacitive discharge ignitions are not completely foolproof in this respect.)


Sparkrite can therefore give you: up to 20% better fuel consumption, instant all weather starting, cleaner plugs—they last up to 5 times longer without attention, faster acceleration, higher top speeds, longer coil and battery life, efficient fuel burning and less air pollution, smoother running, continual peak performance.

NOTE—FUEL CONSUMPTION:
The fitting of a Sparkrite Mk. 2 should reduce fuel consumption although the amount of the reduction will vary. A fair estimate of the savings which could be expected, based on reports by customers and upon our own experience, are as follows:

- any 4-cylinder vehicle, 10% improvement
- any 6-cylinder vehicle, 15% improvement
- any 8-cylinder vehicle, 20% improvement


It is worth remembering that while fuel saving is important there are other advantages to be gained from fitting a Sparkrite ignition system.

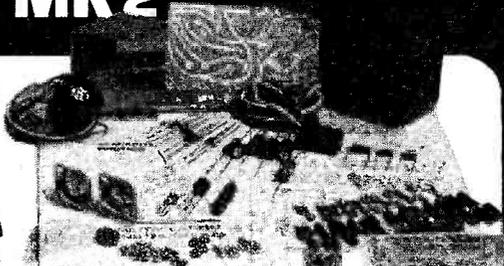*Voted best of 8
ignition systems
tested by **Leading**
Motoring Magazine*



THE KIT COMPRISES EVERYTHING NEEDED: Ready drilled pressed steel case coated in matt black epoxy resin, ready drilled base and heatsink, top quality 5-year guaranteed transformer and components, cables, coil connectors, printed circuit board, nuts, bolts, silicon grease, full instructions to make the kit negative or positive earth, and 10 page installation instructions.

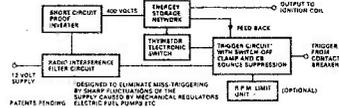WE SAY IT IS THE BEST SYSTEM AT ANY PRICE.



OPTIONAL EXTRAS
Electronic R.P.M. limitation
This can be included in the unit to prevent over revving, an advantage to most companies, hire firms, high performance drivers, etc.
Electronic/conventional ignition switch.
Gives instant changeover from 'Sparkrite' ignition to conventional ignition for performance comparisons, static timing, etc. and will also switch the ignition off completely as a security device, includes switch, connectors, mounting bracket and instructions. Cables excluded.

PRICES: D.I.Y. assembly kit £10-93*; Ready built unit £13-86* (both to fit all vehicles with coil/distributor ignition up to 8-cylinders).
Switch for instant changeover from 'Sparkrite' ignition to conventional ignition £2-79*; R.P.M. limiting control £2-42* (fitted in case on ready built unit, dashboard mounting on kit).
* including VAT, post and packing.
We can supply units for any petrol-engined vehicle (boat, motorcycle, etc.) with coil/contact breaker ignition. Details on request.
CALL IN AND SEE US FOR A DEMONSTRATION.

ELECTRONICS DESIGN ASSOCIATES of WALSALL

ALUMINIUM BOXES

These project boxes are manufactured from 18-gauge aluminium and come complete with lids and screws.
The prices shown include VAT (at 8%) but 18p should be added to the total order value for postage and packing.

| Order No. | Length (in) | Width (in) | Height (in) | Price (inc. VAT) |
|-----------|-------------|------------|-------------|------------------|
| 7 | 5 1/2 | 2 1/2 | 1 1/2 | 48p |
| 8 | 4 | 2 1/2 | 1 1/2 | 46p |
| 9 | 4 | 2 1/2 | 1 1/2 | 46p |
| 10 | 5 1/2 | 4 | 1 1/2 | 48p |
| 11 | 4 | 2 1/2 | 2 | 46p |
| 12 | 3 | 2 | 1 | 38p |
| 13 | 6 | 4 | 2 | 52p |
| 14 | 7 | 5 | 2 1/2 | 75p |
| 15 | 8 | 6 | 3 | 93p |
| 16 | 10 | 7 | 3 | £1-14 |

Boxes can be made to any size but the minimum order for special sizes is 500. General trade enquiries welcome.

FLUORESCENT LIGHT KIT

You can build this reverse polarity protected 12 volt, 8 watt, fluorescent light. Everything needed is supplied: white enamelled drilled metalwork, ready drilled heatsink, printed circuit board, high quality components and transformer, and caps, cable, the fluorescent tube, nuts, bolts, washers, and simple assembly and operating instructions.

When complete the light has many uses: workshop and workbench illumination, garage lighting, emergency as an inspection lamp and many more.

If you can't spare 30our to put the light together then we will supply it ready built (FOR A FEW EXTRA PENCE)

PRICES:
Assembly kit £3-46 inc. VAT post and packing
Ready built £4-10 inc. VAT post and packing.
Diffuser 59p inc. VAT post and packing.

ORDER NOW

To: ELECTRONICS DESIGN ASSOCIATES DEPT. PW9
82 Bath Street, Walsall WS1 3DE. Phone 33652

From Name
Address

Please Supply

| Quantity | |
|----------|--|
| | SPARKRITE Mk. 2 DIY assembly kits at £10-93 |
| | SPARKRITE Mk. 2 ready built negative earth at £13-86 |
| | SPARKRITE Mk. 2 ready built positive earth at £13-86 |
| | Ignition changeover switches at £2-79 |
| | R.P.M. Limit systems in the above units at £2-42 |
| | Fluorescent light assembly kits at £3-46 |
| | Fluorescent light built units at £4-10 |
| | Diffusers for the above at 59p |
| | of number alum. boxes at |
| | of number alum. boxes at |
| | of number alum. boxes at |

I enclose cheque/P.O. for £..... Cheque No
(Send S.A.E. if brochure only required)

MASSIVE CLEARANCE BARGAINS

Bargain component parcels contain Resistors, Capacitors, Potentiometers, Knobs, Tag Strips, Coil Formers, Wire, Grommets, Magnets, Transistor Panels, etc. Save yourself £'s on these well selected parcels, 6lb net weight £1-00, p.p. 70p.

Brand New Wire-wound Resistors 1-7 watts, mostly Plessey GWS-1-3-5-7. Good selection. 100 for £1-00, p.p. 35p.

Mullard Ferrite Cores LA3 50p, LA4 75p, LA2100 50p.

SPECIAL OFFER. Metallised Polyester Capacitors by Erie, Mullard, etc. Values include .01/160V, .01/250V, .015/160V, .022/160, .033/160, .047/160V, .068/160V, .1/160-250V, .22/160V, etc. This is a bargain not to be missed. 100 for £1-50, p.p. 35p.

Assorted Capacitors, Silver Mica, Tubular and Disc Ceramics, Polystyrene, Tremendously good selection. 300 for £1, p.p. 35p.

Please add 25% V.A.T. to total amount

Mail Order Only.

XEROZA RADIO,
1, EAST STREET, BISHOPS TAWTON, DEVON.

SEND NOW! YOUR SINGLE SOURCE FOR THE EASY-BUILD ORGAN

We are the only manufacturers supplying the easy-build organ complete. Full after sales advice given.

Studio Electronics

LTD

PO BOX 18 HARLOW CM18 6SH ESSEX
Tel: HARLOW (STD 0279) 416771

New catalogue now available on receipt of S.A.E.

Greenbank Electronics

FREE!

Data and circuit diagram for Digital Clock Chip AY-5-1224, Digital Alarm Clock Chip MK 50253, also data sheets for Economy LED displays.

(A stamped addressed envelope with enquiries would be a great help to us, but is not essential).

CLOCK CHIPS

AY-5-1224, 4 digit, 12/24 hr., 50/60 Hz, TTL compatible, zero reset, easy display interface, 16 pin package £3.66
MK 50253, 4/6 digit alarm clock chip, 50 Hz, 12/24 hr., AM/PM and activity indication, 'snooze' feature, intensity control, simple time setting, 28 pin package. £5.50

L.E.D. DISPLAYS

DL-747E 15mm (0.6") high, common anode, economy type £1.70
DL-704E 8mm (0.3") high, common cathode, economy type 85p

Add VAT at the appropriate rate to all prices, post, etc. 10p + VAT per order

GREENBANK ELECTRONICS
(Dept. W9P),

94 New Chester Road, New Ferry,
Wirral, Merseyside L62 5AG
Tel. 051-645 3391

4-STATION INTERCOM



£16.15

Solve your communication problems with this 4-Station Transistor Intercom system (1 master and 3 Subs), in robust plastic cabinets for desk or wall mounting. Call/talk/listen from Master to Subs and Subs to Master. Ideally suitable for Business, Surgery, Schools, Hospitals and Office. Operates on one 9V battery. On/off switch. Volume control. Complete with 3 connecting wires each 66ft. and other accessories. P. & P. 65p.

MAINS INTERCOM NEW MODEL
No batteries—no wires. Just plug in the mains for instant two-way, loud and clear communication. On off switch and volume control. Price £29.99 per pair P. & P. 65p.

NEW! AMERICAN TYPE CRADLE TELEPHONE AMPLIFIER



£11.95


+VAT 96p

Latest transistorised Telephone Amplifier with detached plug-in speaker. Placing the receiver on to the cradle activates a switch for immediate two-way conversation without holding the handset. Many people can listen at a time. Increase efficiency in office, shop, workshop. Perfect for "conference" calls: leaves the user's hands free to make notes, consult files. No long waiting, saves time with long-distance calls. On/Off switch, volume. Direct tape recording model at £12.95 + VAT £1.04 P. & P. 65p, 10-day price refund guarantee.

WEST LONDON DIRECT SUPPLIES (PW9)
189 KENSINGTON HIGH STREET, LONDON, W8

H.A.C. SHORT-WAVE KITS

WORLD-WIDE RECEPTION

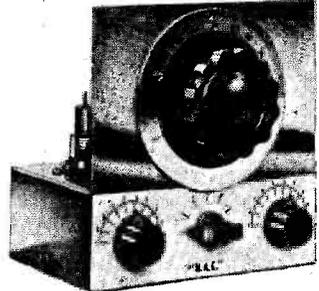

Famous for over 35 years for Short-Wave Equipment of quality. "H.A.C." were the Original suppliers of Short-Wave Receiver Kits for the amateur constructor. Over 10,000 satisfied customers—including Technical Colleges, Hospitals, Public Schools, R.A.F. Army, Hams, etc.


1975 "DX" RECEIVER

Complete kit—Price £5.50 (incl. p. & p. & V.A.T.). Customer writes: "Australia, India and America at loud volume."—"I have now heard over 300 stations including many Amateurs. I have received 32 Q.S.L. verified reports—from all continents. An amazing one-valver."

This kit contains all genuine short-wave components, drilled chassis, valve, accessories and full instructions. Ready to assemble, and of course, as all our products—fully guaranteed. Full range of other S.W. kits, including the famous model "K plus" (illustrated above). All orders despatched within 7 days. Send now for free descriptive catalogue of kits and components.

Send stamped envelope for details.

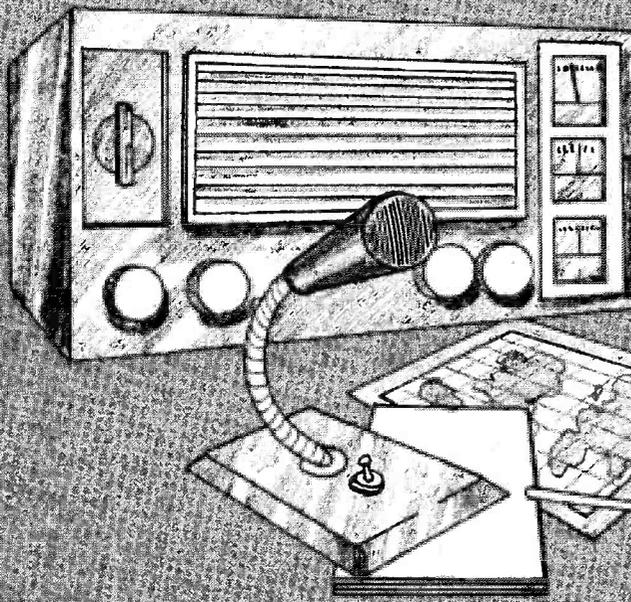"H.A.C." SHORT-WAVE PRODUCTS
P.O. BOX No. 16, EAST GRINSTEAD,
SUSSEX RH19 3SN



Become a radio amateur.

Learn how to become a radio amateur in contact with the whole world. We give skilled preparation for the G.P.O. licence...

Brochure, without obligation to:

To: **BRITISH NATIONAL RADIO & ELECTRONICS SCHOOL, Dept. w.B. 95**
P.O. Box 156, Jersey, Channel Islands.

NAME _____

ADDRESS _____


Block caps please

Free!





I.L.P. (Electronics) Ltd

SHEER SIMPLICITY!

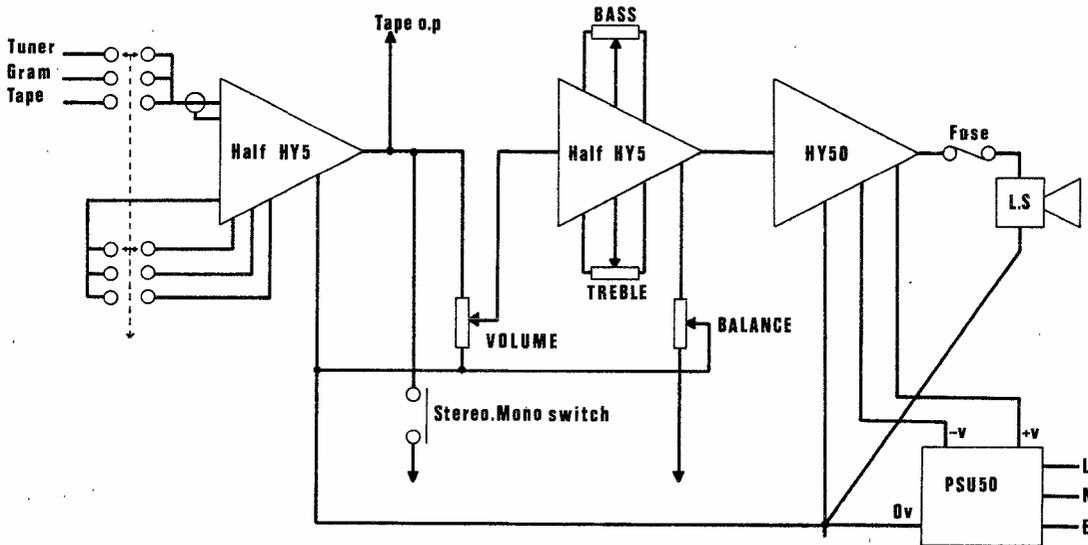

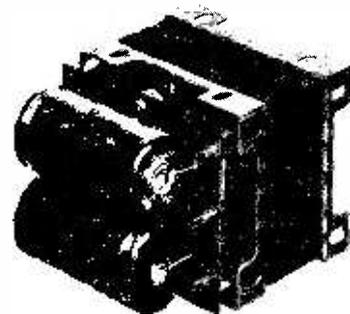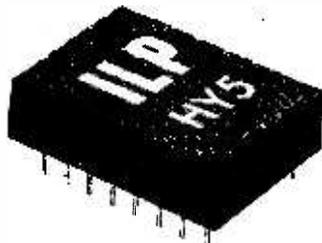MONO ELECTRICAL CIRCUIT DIAGRAM WITH INTERCONNECTIONS FOR STEREO SHOWN



The HY5 is a complete mono hybrid preamplifier, ideally suited for both mono and stereo applications. Internally the device consists of two high quality amplifiers—the first contains frequency equalisation and gain correction, while the second caters for tone control and balance.

TECHNICAL SPECIFICATION

Inputs: Magnetic Pick-up 3mV RIAA; Ceramic Pick-up 30mV; Microphone 10mV; Tuner 100mV; Auxiliary 2-100mV; **Input Impedance:** 47kΩ at 1kHz. **Outputs:** Tape 100mV; Main output 0db (0-775V RMS). **Active Tone Controls:** Treble ± 12db at 10kHz; Bass ± 12db at 100Hz. **Distortion:** 0-5% at 1kHz. **Signal/Noise Ratio:** 68db. **Overload Capability:** 40db on most sensitive input. **Supply Voltage:** ± 16-25V.

PRICE £4.50 + 36p VAT
P. & P. free

The HY50 is a complete solid state hybrid HI-FI amplifier incorporating its own high conductivity heatsink hermetically sealed in black epoxy resin. Only five connections are provided, input, output, power lines and earth.

TECHNICAL SPECIFICATION

Output Power: 25W RMS into 8Ω. **Load Impedance:** 4-16Ω. **Input Sensitivity:** 0db (0-775V RMS). **Input Impedance:** 47kΩ. **Distortion:** Less than 0-1% at 25W typically 0-05%. **Signal/Noise Ratio:** Better than 75db. **Frequency Response:** 10Hz-50kHz ± 3db. **Supply Voltage:** ± 25V. **Size:** 105 x 50 x 25mm.

PRICE £5.98 + 48p VAT
P. & P. free

The PSU50 incorporates a specially designed transformer and can be used for either mono or stereo systems.

TECHNICAL SPECIFICATIONS

Output voltage: 50V (25-0-25V). **Input Voltage:** 210-240V. **Size:** L.70. D.90. H.60mm.

PRICE £6 + 48p VAT
P. & P. free

TWO YEARS' GUARANTEE ON ALL OUR PRODUCTS

I.L.P. Electronics Ltd.
Crossland House,
Nackington, Canterbury
Kent CT4 7AD

Tel (0227) 63218

Regd. V.A.T. No. 202141535


Please supply,
Total Purchase price
I Enclose, Cheque Postal Orders Money Order
Please debit my Access account Barclaycard account
Account number
Name & Address
Signature

LISTEN TO

CODAR®

THE WORLD!

★ **CR70A**

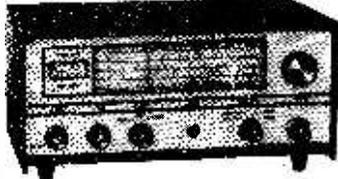

COMMUNICATION RECEIVER

★ **MADE TO ORDER!**
£39.00! (carr. free)
+ VAT £9.75

The CODAR CR70A is an outstanding general coverage communication receiver, ideal for the keen S.W.L. It tunes from 540 metres medium through to 10 metres with no gaps. Covers shipping, coastguard and distress frequencies, all six amateur bands 160-10 metres, international broadcast, Met. stations etc. etc. giving world-wide reception. Exclusive features include Air-spaced CODAR-COIL Hi-"Q" Aerial input, illuminated Meter and Slide Rule Scale, Two Speed vernier tuning, Switched B.F.O. for CW/SSB signals. Separate output for Tape recorder. Ready to plug in to 200/240 volts A.C. it only needs your aerial and a 2/3 ohm loudspeaker to bring the world to your finger tips. 12 months full guarantee.

★ **IMPORTANT NOTE**

This fine receiver is not a mass produced item, but each set is hand built to your order, individually checked and air tested. Please allow for this when ordering—your delivery date will be shown on your receipt, sent by return.

* Special discounts for Educational Authorities and Senior Citizens.



"Free Gift!! Claim your Codar ball-point pen free with your next order!!"

ILLUSTRATED LEAFLETS FREE ON REQUEST (STAMP APPRECIATED)

CODAR®

VALCON WORKS · BURRELL BUILDINGS · CHURCHILL INDUSTRIAL ESTATE · LANCING · SUSSEX

WORLD-WIDE MAIL ORDER—EXPORT QUOTES FREE.



★ **P.R.40** ★

£11.00! (carr. free)
+ VAT £2.75

R.F. PRESELECTOR

The PR40 R.F. Preselector is the solid state version of the world famous PR30 which it now supersedes. It employs Silicon "N" Channel FET (Field Effect Transistor) front end followed by silicon NPN Broad Band R.F. Amp., and will substantially improve receiver performance over the range 1.5 to 35 MHz, providing a considerable increase in gain up to an overall average of 30dB, with improved image rejection and noise ratio. Supplied complete with co-ax plug (less standard 9 volt PP6 Battery). 12 months Guarantee . . .



★ **MULTIBAND-6** ★

SHORT WAVE RECEIVER KIT

£16.56! (carr. free)
+ VAT £4.14

All transistor T.I.L.F. Receiver tunes 550 KHz to 30 MHz (540 to 10 metres) complete coverage—no gaps. Medium waves—Trawlers—Ship / Shore Telephone—All Six Amateur Bands 160-10 metres—International Broadcast from Australia, Far East, Russia, USA etc. using 4 miniature plug in Coils. Hi-Gain FET Regen, Det.(AF/AF Module giving full loudspeaker output to any external 2/3 ohm speaker. Receives AM/CW/SSB. Separate Electrical Bandspeed, Calibrated Main Tuning. A Quality CODAR-KIT with 12 months Guarantee. No technical knowledge required, simple to build, printed circuit and Pictorial Instruction Manual, fully detailed step by step. Complete Kit with 4 Coils (less standard PP6 battery).

NEW! AVAILABLE SOON!!

THE MINICLIPPER STARTER KIT, ALL SOLID STATE SHORT WAVE RECEIVER, ALSO SUPER HI-"Q" A.T.U.

Tel: LANCING 61901

BN15 - 8TZ

B. BAMBER ELECTRONICS

5 STATION ROAD, LITTLEPORT, CAMBS. CB6 1QE

Telephone: ELY 40353 850186 (2 lines) Tuesday-Saturday

- TV plugs, metal type, 6 for 50p.
- TV sockets, metal type, 5 for 50p.
- TV line connectors (back-to-back socket), 5 for 50p.
- T03 transistor insulator sets, 10 for 50p.
- Mixed electrolytics, large bag, £1.
- PC board withdrawal handles, mixed coils, 8 for 50p.
- Solder, 20SWG, 60/40 alloy, approx. 9yds, 25p.
- OC200 transistors, 6 for 50p.
- Perspex coil formers, 1 1/4" x 1/4" dia., 5 for 25p.
- Turret tags, 1/4" dia., 25p pack.
- Rotary switches, min. 4 pole 2-way, 2 for 50p.
- Telephone type earpiece insert, 50p.
- Reeds (for reed relays) single-pole make, 5 for 30p.
- Mullard tubular ceramic trimmers, 1-18pF, 6 for 50p (as featured in Rad. Comm. Jan. p. 25).
- I.C.s. some coded, 14DIL type, untested, mixed, 20 for 25p.
- IF cans 3/4" square, suitable for rewind, 6 for 30p.
- 24V min. reed relays, encapsulated single-pole make, 2 for 50p.
- 24V 2-8W lamps, MES type, 6 for 20p.
- Chassis tags, 25p pack.
- Cable clips, for nailing cable, 15p pack.
- Miniature slider switches, 2 pole, 2-way, 5 for 50p.
- BSY95A transistors, 6 for 50p.
- PNP audio type T03 transistors, 12 for 25p.
- Black plastic knobs, 3/4" dia., 3/4" spindle, 4 for 50p.
- Ring magnets, 7mm outside dia., 20 for 50p.
- Large box of P.C. Boards, containing transistors, I.C.s, trim pots, resistors, capacitors, etc. (not unknown computer rubbish), £3 per box.
- 1/4" polythene chassis mounting fuseholders, 6 for 30p.
- LES Lamps, 24V 1-2W, 10 for 40p.
- Three-switch push-button units, 3 x 2 pole, 2-way min. push-push switches, 3/4" dia., buttons mounted on one unit, 40p.

- MAINS TRANSFORMERS**
- All 240V input, voltages quoted approx. RMS. (Please quote type no. only when ordering)
- TYPE 10/2, 10-0-10V at 2A, £1-50 each.
- TYPE 10/2, 18V at 2A, £1-65 each.
- TYPE 16/6, 18V at 6A + 45V at 100mA, £4.
- TYPE 28/4, 28V at 4A + 125V at 500mA, £4.
- TYPE 63/1, 6-3V at 1A, 85p each or 2 for £1-50.
- TYPE 129, 400V at 20mA + 200V at 10mA + 6-3V at 500mA, £1-25.
- TYPE 72/03, 400V at 10mA + 200V at 5mA + 6-3V at 400mA, £1-25.
- TYPE 70462, 250-0-250V at 80mA + 6-3V at 2A, £1-75.
- RADIOSPARES** 500W AUTO TRANSFORMERS, 100-110-130-200-220-240-250V tapped input and output, step-up or step-down facility, ex-new equip. £6.
- CURLY LEADS**, 4 core telephone type 2 for 20p.
- TRANSISTOR HEATSINKS**, to take 2 x T03 transistors, screw in clamp, block size 1 x 1 x 3/4" in, with holes for mounting, 3 for 50p.
- VARIABLE STABILISED PSU**, solid-state 240V a.c. input, output 0-24V d.c. at 500mA, +32V d.c. at approx. 50mA. Voltage controlled by external 5kΩ pot. Size 7 1/2 x 4 x 2 1/4" (less 5kΩ pot), £5 each.
- THREE-TURN WIRE-WOUND POTS**, 5kΩ for above, 75p each.
- LARGE DIE CAST BOXES** (brand new ITT) 10 1/2 x 6 1/2 x 2 1/2", £2 each.
- 25-way ISEP PLUGS AND SOCKETS**, 40p each (plug + 1 set).
- DIN SPEAKER SOCKETS** (2-pin) 4 for 30p.
- HIGH QUALITY SPEAKERS**, 8 1/2 x 6 1/2" elliptical, only 2in deep, inverse magnet, 5 ohms, rated up to 10W, £1-50 each, or 2 for £2-75 (qty. discount available).
- Rotary switches 9-way 4-pole (separate wafers, plastic) 3/4" spindle, 40p each.
- Heatsinks (Approx. 3 1/4" x 4 1/4" x 2 1/4" high), 12 fins (drilled for 1 x T03 transistor) brand new, 45p each.

TERMS OF BUSINESS: CASH WITH ORDER (minimum order £1) POST FREE (UK ONLY), PLEASE ADD 25% VAT.

Export enquiries welcome. Callers welcome. Tues. to Sat. Please enclose S.A.E. with ALL enquiries.

N.S.E. PROFESSIONAL STANDARD KITS

The first two of a range of kits to appeal to both the novice & the experienced assembler. Branded devices & high quality components used throughout.

**3 CHANNEL SOUND TO LIGHT UNIT
1000 WATTS PER CHANNEL
FIBREGLASS P.C. BOARD**

High sensitivity up-to-date design giving scintillating performance. Kit includes all components inc. mains transformer, transistors & triacs. Step-by-step instructions are provided. All you need is a soldering iron etc. No technical knowledge required. In the unlikely event of you being unable to get the unit operational it may be returned to us for correction. Professional quality at the unbeatable price of **£11.90**. Carr. 50p

**5 WATT GUITAR PRACTICE
AMPLIFIER WITH TREMOLO
FIBREGLASS P.C. BOARD**

High quality unit with bass & treble controls plus tremolo speed & depth controls—Kit includes mains transformer etc. as above. Get it going service. Another N.S.E. first at only **£11.90**. Carr. 50p.

NOTE — PRICES INCLUDE VAT!

Send Cheque/P.O. or Access Number (Cash in registered envelope only) to:

N.S.E. KITS, 333, White Horse Road, Croydon, Surrey. Tel.: 01-689-3685

Shop open Mon/Sat 9.30 am—5.00 pm.
Please quote magazine when ordering.

Crescent Quality Components

BARGAIN CAPACITOR 2,000MFD at 50v. DC wkg. Size = 2" x 1 1/2" diameter. Tag ended. All new and unused. Our Price 35p. +8%

BARGAIN PROJECT BOX
A plastic box with moulded extrusion rails for PC or Chassis panels with metal front plate fitted with four screws (all supplied).
An ideal box to give a small project a professional finish. SIZE (internal) 81mm x 51mm x 28mm. OUR PRICE 40p. +8%

JB11D STEREO JUNCTION BOX
The most popular stereo junction box. Facility for two pairs of headphones and two speakers. 3 position switch selects headphones, loud-speakers or both. A bargain at £2.50 +25%



LIGHT EMITTING DIODES +8%

| | RED | GREEN | YELLOW | AMBER |
|------------|-----|-------|--------|-------|
| 0.2 inch | 17p | 27p | 29p | 27p |
| 0.16 inch | 24p | 29p | 30p | 29p |
| 0.125 inch | 15p | 25p | 30p | 25p |

For orders of 10 and more LEDs 10% discount. (All LEDs supplied with free plastic mounting clip).

LOW COST SEVEN SEGMENT DISPLAYS -3 INCH +8%

| Model | Color | Connection | Direction | Price |
|-------|--------|--------------|------------|-------|
| CR72R | Red | Com. Anode | Left Dec. | £1.35 |
| CR82G | Green | Com. Anode | Left Dec. | £1.35 |
| CR83Y | Yellow | Com. Anode | Left Dec. | £1.35 |
| CR74R | Red | Com. Cathode | Right Dec. | £1.35 |
| CR84G | Green | Com. Cathode | Right Dec. | £1.35 |
| CR84Y | Yellow | Com. Cathode | Right Dec. | £1.35 |

For full information on low cost displays please send 15p.

Clock Chip +8%
CT7001 MOS/LSI Digital Clock/Calendar Chip Plus full Circuits and Information leaflet £4.95
Circuits and Information Sheet 15p
Lit 704 Led Display for above £1.10
Or 4 for £4.20

WAFER SWITCHES

- 1 Pole 12 Way
 - 2 Pole 2 Way
 - 2 Pole 3 Way
 - 2 Pole 4 Way
 - 2 Pole 6 Way
 - 3 Pole 4 Way
 - 4 Pole 3 Way
- 22p each +8%



POTENTIOMETERS

All types 1" and less diameter

| Value | Single | Dual | Price |
|-------|----------|------|----------|
| 5K | Log or | 5K | 15p |
| 10K | Lin Less | 10K | 15p |
| 25K | Switch | 25K | 15p |
| 50K | 17p each | 50K | 25p each |
| 100K | | 100K | 53p each |
| 250K | Double | 250K | +25% |
| 500K | Pole | 500K | |
| 1M | Switch | 1M | |
| 2M | 37p each | 2M | |

FERRIC CHLORIDE

Anhydrous ferric chloride in double sealed one pound poly packs.
Our Price 50p + P/P + VAT @8% per lb.

MAINS TRANSFORMERS

Open Type Double Wound Continuously Rated, two hole fixing clamp with colour coded flying leads, varnish impregnated. Approx. size: 1 1/2" x 1 1/2" x 1 1/2" high
Fixing centres: 2 1/2"

| | | |
|-----|-------------------|----------|
| TR1 | 20-0-20v 100 m/a | All |
| TR2 | 12-0-12 v 100 m/a | 240 Volt |
| TR3 | 9-0-9 v 100 m/a | Primary |
| TR4 | 6-0-6 v 100 m/a | |
| TR5 | 3-0-3 v 100 m/a | |

Our Price £1.28 each +8%

MONO/STEREO MICROPHONE MIXER
9 volt. High impedance input. Gold finish with four black plastic chrome tipped level control knobs. On/Off switch and stereo/mono switch. 4 Input sockets.
SPECIFICATIONS:-
Input Imp = For XTAL Mics etc.
(Gain = Approx 3.D.B.)
Max Input Sig = 1 volt
Max Output Sig. = 1.3 volt
Noise Ratio = -60DB
Supply = 9 volt
OUR PRICE = £5.25p +25%

POWER SUPPLY UNITS
PP1 switched 3, 4, 6, 7, 9 and 12 volts at 500 m/a, with on/off switch and pilot light. Size: 130mm x 55mm x 75mm. ONLY £4.00.
PP2 Switched 6-71-9 volt Battery Eliminator. Approx. size 2 1/2" x 2 1/2" x 3 1/2". Ideal for cassette recorders £3.25
PP3 Car converter. From 12v Pos. or Neg. to 6-71-9 volt. Easy to fit and transistor regulated £3.90 +8%



NEW VEROBORD PRICES

| Size | Price | Plain | Price |
|---------------|-------|-------|-------|
| 2 1/2 x 3 1/2 | 38p | 15 | 18p |
| 2 1/2 x 5 | 41p | 15 | 20p |
| 3 1/2 x 3 1/2 | 41p | 15 | 20p |
| 3 1/2 x 5 | 47p | 15 | 24p |
| 1 7/8 x 2 1/2 | 1.24p | 8p | 8p |
| 1 7/8 x 3 1/2 | 1.69p | 1.32p | 97p |
| 1 7/8 x 5 | 2.18p | 1.37p | 81p |

Pin insertion tool Spot face cutter 81p
Fxt 36 pins (estate 1 or 15) 30p

LOUDSPEAKERS +25%

| | |
|------------------------|-----------------------|
| 2 1/2" 8 ohm | 50p |
| 2 1/2" 40 ohm | 50p |
| 2 1/2" 80 ohm | 60p |
| 5" 8 ohm | ceramic £1.25 |
| 6 1/2" 8 ohm dual cone | ceramic £2.50 |
| 10" 8 ohm dual cone | ceramic £3.75 |
| 7" x 4" 8 ohm | ceramic £1.60 |
| 8" x 5" 8 ohm | Perman's Magnet £1.60 |

*EMI 13" x 8" 450 Kit £4.10 + 50p Carr
3-8-15 ohm £2.50 + 50p Carr.
*EMI 13" x 8" 350 Kit 8 ohm £2.50 + 50p Carr.



10 inch DUAL CONE L/S
Manufactured by "ELAC" to a very high standard these loudspeakers are a real bargain.
SPEC:- Size=10" Dual Cone.
Power=10 Watts
Frequency=40-12000Hz
+25% Our Price = £3.75p each

MAINS KEYNECTOR
Keynector connects any Electrical Equipment to the mains supply in seconds. Ideal for bench, garage demonstrations, etc. Multi connections can be made (max. load 13A fused).
£3.25p. +8%



ALUMINIUM BOXES +8%

Metal project boxes give your work a professional finish

| Model | Price | Price | Price | |
|-------|-------|-------|-------|-------|
| AB7 | 2 1/2 | 5 1/2 | 1 1/2 | 54p |
| AB8 | 4 | 4 | 1 1/2 | 68p |
| AB9 | 4 | 2 1/2 | 1 1/2 | 54p |
| AB10 | 4 | 5 1/2 | 1 1/2 | 68p |
| AB11 | 4 | 2 1/2 | 2 | 54p |
| AB12 | 3 | 2 | 1 | 45p |
| AB13 | 6 | 4 | 2 | 69p |
| AB14 | 7 | 5 | 2 1/2 | 84p |
| AB16 | 8 | 6 | 3 | 89p |
| AB16 | 10 | 7 | 3 | £1.85 |
| AB17 | 10 | 4 1/2 | 3 | £1.02 |
| AB16 | 12 | 5 | 3 | £1.80 |
| AB19 | 12 | 8 | 3 | £1.50 |


ABS PLASTIC BOXES +8%
Handy boxes for construction projects. Moulded extrusion rails for P.C. or chassis panels. Fitted with 1mm front panels.

| | |
|--|-------|
| 1005 = 105mm x 73mm x 45mm | = 61p |
| 1006 = 100mm x 75mm x 47mm | = 66p |
| 1007 = 184mm x 124mm x 60mm | = 96p |
| 1021 = 106mm x 74mm x 45mm (sloping front) | = 60p |

TELESCOPIC AERIAL
Nine section fully swivelling telescopic aerial with 4BA single bolt fixing or two hole fixing bracket.
Fully extended = 43"
Fully closed = 7"
Our Price 50p + P/P + VAT @ 25%

CLEAR PLASTIC PANEL METERS
Size 59mm x 46mm x 35mm these meters require a 38mm hole for mounting.

- ME6 = 0 to 50 micro amp Full Scale
 - ME7 = 0 to 100 micro amp Full Scale
 - ME8 = 0 to 500 micro amp Full Scale
 - ME9 = 0 to 1 m/a Full Scale
 - ME10 = 0 to 5 m/a Full Scale
 - ME11 = 0 to 10 m/a Full Scale
 - ME12 = 0 to 50 m/a Full Scale
 - ME13 = 0 to 100 m/a Full Scale
 - ME14 = 0 to 500 m/a Full Scale
 - ME15 = 0 to 1 amp Full Scale
 - ME16 = 0 to 50 volts
 - ME17 = 0 to 300 volts
 - ME18 = "S" Meter
 - ME19 = "VU" Meter
- OUR PRICE £3.00 +8%

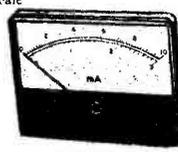

200/250v MAINS RELAY
Heavy duty contacts 2-500 ohm coil All new and unused D.F.D.T. mains relays 50p. Carr. Free. Special quantity £40 per 100 off.

DECON DALO 33PU ETCH RESIST PEN
The Decon Dalo 33PU is a unique instrument for the professional and amateur electronics engineer, enabling him to prepare in minutes a perfect printed circuit board.
OUR PRICE 80p +8%

MINIATURE RELAYS
Brand new range of British made Relays. Size 1 1/2" x 1 1/2" x 3/4". All two changeovers with 250v 1.5A contacts and suitable for fitting on 1mm Veroboard.

WIRE WOUND +8% VOLUME CONTROL
250ohm Only 25p EACH. Approx 1" Diameter. Long standard spindle.

CABLE LESS SOLDERING IRON WAHL "ISO-TIP"

- ★ Completely Portable
 - ★ Heats in 5 seconds
 - ★ Solders up to 150 joints or more per charge
 - ★ Recharges automatically in its own stand
 - ★ No AC leakage or induced current to damage delicate components
 - ★ Heats to 700 deg. F
 - ★ Fine Tip for delicate and general purpose soldering
 - ★ Only 8" long and weighs just 6 ozs.
- OUR PRICE £9.75 +8% (spare bits are available)

STOP PRESS +25%

- BHA0002 15 watt Amp Module £2.50
- NE555 Timer I.C. 75p
- MC1310P Stereo Decoder J.C. £8.00
- 7805 Regulator £1.49
- TIP 29A 55p
- TIP 30A 65p
- BC107 10p
- BC108 10p
- BC109 10p

I.C. SOCKETS +8%
D.I.L.
8 pin=18p 24 pin=24p
14 pin=14p 28 pin=29p
16 pin=14p 36 pin=36p

BARGAIN TRANSFORMERS

12-0-12 volt 500m/a
240 volt primary transformer bargain. approx size = 60mm x 40mm x 50mm fixing centres=75mm
Our Price = £1.20 +8%

P.C. ETCHING KIT

This kit contains all that the constructor will need to etch the circuits of his own design
Contents:- Plastic etching dish.
Sample copper clad board.
Laminar Cutter.
1 lb Ferric Chloride.
Large Plastic Spoon.
Etch Resist Pen.
Full Etching Instructions.

Complete and Big Kit Value at £3.75p +8%

LOW NOISE LOW PRICE CASSETTES +8%

Good quality tape in well made screw type cassettes. Presented in single plastic cases.
C60=31p C90=42p C120=53p
10% Discount on ten or more cassettes of one type

U.K. POSTAGE 20p UNLESS OTHERWISE STATED

VAT—All prices are excluding VAT. Please add to each item the VAT rate indicated.

CRESCENT RADIO LTD. P.W.

All mail to No. 1 ST. MICHAELS TERRACE
WOOD GREEN, LONDON N22 4SJ.
Phone: 01-888 3206

Callers Welcome at
15 Mayes Road & 13 South Mall, Edmonton N9.

If you construct You should own one.

CRESCENT CATALOGUE
Price 30p.

ENGINEERS
FREE
YOURSELF FOR A BETTER JOB



Do you want promotion, a better job, higher pay? "New opportunities" shows you how to get them through a low-cost, Home Study Course. There are no books to buy and you can pay as you learn.

This easy to follow GUIDE TO SUCCESS should be read by every ambitious engineer. Send for this helpful 76-page free book NOW! No obligation, nobody will call on you. It could be the best thing you ever did.

CHOOSE A BRAND NEW FUTURE HERE

CUT OUT THIS COUPON
Tick or state subject of interest. Post to address below.

- | | | |
|---|--|---|
| <input type="checkbox"/> ELECTRICAL ENGINEERING City & Guilds Wiring and Installations C. G. Electrical Tech-Primary Gen. Electrical Eng. | <input type="checkbox"/> RADIO & TV Colour TV Servicing C & G Radio, TV & Electronic Mechanics Gen. Radio and TV Eng. Radio Servicing, Maintenance and Repairs Practical Radio & Electronics (with self-build kit) Radio Amateurs' Exam | <input type="checkbox"/> DRAUGHTSMANSHIP Institute of Engineering Draughtsmen & Designers General Draughtsmanship Architectural Draughtsmanship Technical Drawing |
| <input type="checkbox"/> AERONAUTICAL ENGINEERING Air Registration Board Certificates Gen. Aero Engineering | <input type="checkbox"/> ELECTRONIC ENGINEERING Gen. Electronic Eng. Practical Electronics (with kit) | <input type="checkbox"/> CONSTRUCTION & BUILDING Institute of Building Construction Surveyor's Inst. Clerk of Works Diploma C. & G. Building Quantities General Building General Civil Eng. Heating, Ventilating & Air Conditioning Carpentry & Joinery Painting & Decorating Plumbing C.E.I. (Part 1) Inst. Cost & Management Accountants Works Management etc. etc. |
| <input type="checkbox"/> AUTO ENGINEERING City & Guilds Auto Engineering Practice Inst. Motor Industry M.A.A./I.M.I. Management Diploma Gen. Auto Engineering Auto Diesel Maintenance Motor Mechanics Service Station and Garage Management | <input type="checkbox"/> AGRICULTURAL ENGINEERING REFRIGERATOR SERVICING MECHANICAL ENGINEERING Society of Engineers Inst. Engineers and Technicians General Mechanical Eng. Welding Maintenance Eng. General Diesel Eng. | <input type="checkbox"/> TELECOM-MUNICATIONS City & Guilds Telecommunications |



G.C.E.
—58 'O' & 'A' Level Subjects
—over 10,000 Group Passes!

Aldermaston College

Dept. TPW08, Reading RG7 4PF.

also at our London Advisory Office, 4 Fore Street Avenue, Moorgate, London EC2Y 5ET. Tel. 628 2721.

NAME (Block Capitals)

ADDRESS

..... Postcode.....

Other subjects of interest..... Age.....

Accredited by C.A.C.C. Member of A.B.C.C.


HOME OF BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY

NEW PRACTICAL PAPERBACKS FROM FOULSHAM-TAB

- INDEXED GUIDE TO MODERN ELECTRONIC CIRCUITS by Robert L. Goodman £1.90
- MODEL SAIL AND POWER BOATING . . . by remote control by George Siposs £1.80
- RF AND DIGITAL TEST EQUIPMENT YOU CAN BUILD edited by Wayne Green £1.95
- AMATEUR FM CONVERSION & CONSTRUCTION PROJECTS by Ken Sessions, Jnr. £2.10
- CAR STEREO SERVICE & INSTALLATION by Paul Dorweiler & Harry Hansen £1.95
- COLOUR TV TROUBLES (FACTBOOK) by The Editors of Electronic Technician/Dealer £2.30
- ELECTRONIC TEST EQUIPMENT—and how to use it by Joe Risse £1.85
- ELECTRONICS UNRAVELLED—A new commonsense approach by James Kyle £1.90
- SIMPLIFIED COMPUTER PROGRAMMING—The easy RPG way by Kelton Carson £1.95
- INSTALLING TV & FM ANTENNAS by Leo G. Sands £1.75
- JAPANESE CONSUMER ELECTRONICS SCHEMATIC/SERVICING MANUAL by TAB Editorial Staff £2.50
- MODERN GUIDE TO CAR TUNE-UP AND EMISSION CONTROL SERVICING by Paul Dempsey £1.95

FOULSHAM-TAB LTD.
YEovil ROAD, SLOUGH, BERKS

CARBON SLIDE POTENTIOMETERS

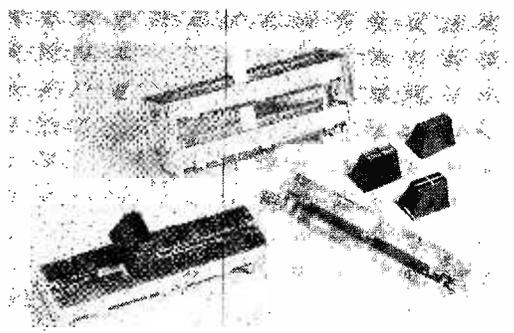

60mm Single Track including Black Knob 50p (inc. V.A.T.), 60mm Twin Track including Black Knob 60p (inc. V.A.T.), 60mm Quad Slide Potentiometers—Prices upon application. 1K, 5K, 10K, 25K, 50K, 100K, 500K ohms Log, Lin; Antilog. Metal Case. 3-2db Matched Track. 15mV Nominal Noise (B.S. 2122). Life Exceeds 20,000 cycles. Fixing Holes 2 x M3 on 80mm Centres.

Designed, Manufactured and Supplied by:—
RIVLIN INSTRUMENTS LTD
DOMAN ROAD, CAMBERLEY, SURREY GU15 3DJ
Send cash with order to above address. Postage and packing 15p per order. Trade enquiries invited.

Practical Wireless Classified Advertisements

The pre-paid rate for classified advertisements is 14p per word (minimum 12 words), box number 35p extra. Semi-displayed setting £12.00 per single column inch. All cheques, postal orders, etc., to be made payable to PRACTICAL WIRELESS and crossed "Lloyds Bank Ltd." Treasury notes should always be sent *registered post*. Advertisements, together with remittance, should be sent to the Classified Advertisement Manager, PRACTICAL WIRELESS, IPC Magazines Ltd. Fleetway House, Farringdon Street, London, EC4A 4AD for insertion in the next available issue. (01-634 4451).

Receivers and Components

NEW MODEL V.H.F. KIT MK2

Our latest kit. Improved design and performance plus extra amplifier stage, receives aircraft, amateurs, mobile, radio 2, 3, 4, etc., this novel little set will give you endless hours of pleasure and can be built in one evening. Powered by 9 volt battery, complete with easy to follow instruction and built in jack socket for use with earphones or amplifier.

Only £4.50 + p&p 30p U.K. only.

Illustrated catalogue of selected kits and components, 35p inc. VAT. P&P free.

ALL PRICES PLUS 25% VAT

Gaffoon Trading Co,
12, Burns Way,
Corintham,
Stanford-Le-Hope,
Essex. SS17 9DE

CLEARING DISTRIBUTOR STOCKS. transistors, diodes, components, etc.. Sample pack 65p incl. postage or send stamp for list. Redhawk Sales Ltd., 10 Maple Lodge Close, Rickmansworth, Herts. Mail Order Only.

BETA DEVICES

MANUFACTURERS BRANDED PRODUCTS

| TRANSISTORS | DIODES & RECT. | TRIMMERS | RELAYS |
|--|---------------------|----------|---------------------------|
| AC187/8 PR 0-40 | IN14 | 0-04 | 1A 100v W01 0-50 |
| BC107/8/9 | 0-09 IN4148 | 0-04 | 1A 200v W02 0-22 |
| BC108C | 0-11 IN427 | 0-14 | 1A 600v W06 0-30 |
| BC147/8 | 0-10 IN4001/2 | 0-05 | 25A 200v 22-00 |
| BC170/71/720-13 | IN4003/4/5 | 0-08 | ZENERS |
| BFY38 | 0-20 IN4006/7 | 0-05 | BZY55c 3-5 |
| BFY50 | 0-18 IN5401 | 0-11 | 33v 5% 0-09 |
| BFY51/52 | 0-12 | | 1 watt 6% 0-15 |
| 2N1182 | 0-25 555 Timer | 0-50 | 200v 5% 0-15 |
| 2N1711 | 0-25 555 Dual Tr | 1-00 | L.E.D. |
| 2N2046 | 0-30 TBA800 | 1-50 | 200-RED 0-17 |
| 2N2905A | 0-21 TBA810 | 1-80 | LED CLIP 0-08 |
| 2N3053 | 0-14 | | OP. AMP. 10's |
| 2N3055 | 0-38 D.L.L. SOCKETS | | 709C T099 0-30 |
| OC28 | 0-45 8 Pin | 0-12 | 709C D.L.L. 0-30 |
| OC85 | 0-35 14 Pin | 0-12 | 741C T099 0-38 |
| TIP29A | 0-49 16 Pin | 0-14 | 741C D.L.L. 0-38 |
| TIP31A | 0-61 | | 723C D.L.L. 0-80 |
| TIP41A | 0-74 | | 747C D.L.L. 0-85 |
| TIP42A | 0-90 | | 748C D.L.L. 0-88 |
| 7400N | 0-16 | | 74 SERIES TTL 74121N 0-50 |
| 7404N | 0-18 | | 7474N 1-90 74123N 1-28 |
| 7410N | 0-18 | | 7474N 0-87 74141N 1-18 |
| ALUMINIUM ELECTROLYTIC CAPACITORS | | | |
| 10µF 22µF | 47µF | 100µF | 220µF 470µF 1,000µF |
| 16v 0-07 0-07 0-07 | 0-10 0-12 0-14 0-22 | | |
| 25v 0-07 0-07 0-08 | 0-10 0-13 0-16 0-26 | | |

C.W.O. PLUS P.P. 15p TO

BETA DEVICES,

4, Highbridge Street,
Waltham Abbey, Essex.

BRAND NEW COMPONENTS BY

RETURN: Electrolytics—16V, 25V, 50V—0.47, 1.0, 2.2, 4.7, 10 mfd.—5p. 22, 47—5.2p. (50V—6p) 100—7p (50V—8p), 220—8p. (50V—10p), 500—11p. (50V—16p), 1000/25V—18p. Subminiature bead-type tantalums—0.1/35V, 0.22/35V, 0.47/35V, 1.0/35V, 2.2/35V, 4.7/35V, 10/20V, 22/16V, 47/6V, 100/3V.—11p. Mylar Film 10V—0.001, 0.002, 0.005, 0.01, 0.02.—3p. 0.04, 0.05—3.2p. Mullard tubular polyester 400V E6 series 0.001-0.022—3.2p. 0.033-0.1—4.2p. Mullard miniature C33 ceramics 63V E12 series 2%, 1.8 pf.—47 pf.—3p. 56 pf.—330 pf.—3.2p. Polystyrene 63V E12 series 10 pf.—1000 pf.—3p. 1200 pf.—10,000 pf.—4p. Miniature Highstab. carbon film resistors 1/2 W E12 series 5% 10-10MΩ. (10% over 1MΩ) 1-2p. Postage 10p. Prices VAT Inclusive. The C.R. Supply Co., 127, Chesterfield Road, Sheffield S8.

COMMUNICATIONS RECEIVER modules. Small superhet circuit boards requiring only controls and tuned circuits. 9 volt. Mosfet mixer, IC IF, BFO, Prod. Det. Excellent AM/CW/SSB results reported by delighted users. From £11.50. SAE details. PR Gold-ledge Electronics, Millend, Stonehouse, Glos.

Precision Polycarbonate Capacitors

All High Stability—Extremely Low Leakage

| 440V AC (±10%) | 50p | 63V Range | ±1% | ±2% | ±5% |
|------------------|------|-----------|-------|-------|-------|
| 0.1µF (1" × 1") | 50p | 0.47µF | 50p | 48p | 25p |
| 0.22µF (1" × 1") | 50p | 1.0µF | 65p | 55p | 40p |
| 0.25µF (1" × 1") | 60p | 2.2µF | 80p | 65p | 55p |
| 0.47µF (1" × 1") | 71p | 4.7µF | 80p | 65p | 55p |
| 0.6µF (1" × 1") | 75p | 6.8µF | 21-04 | 21-29 | 21-09 |
| 0.8µF (2" × 1") | 80p | 10.0µF | 22-00 | 21-00 | 21-40 |
| 1.0µF (2" × 1") | 91p | 15.0µF | 22-75 | 22-75 | 21-80 |
| 2.0µF (2" × 1") | 112p | 10.0µF | 22-75 | 22-75 | 21-80 |

TANTALUM BEAD CAPACITORS—Values available: 0.1, 0.22, 0.47, 1.0, 2.2, 4.7, 6.8µF at 15V/25V or 35V; 10.0µF at 16V/20V or 25V; 22.0µF at 6V/10V or 16V; 33.0µF at 6V or 10V; 47.0µF at 8V or 6V; 100.0µF at 8V. ALL at 10p each, 10 for 95p, 50 for £4.

| TRANSISTORS: | BC188/183L | 11p | BFV50 | 20p | |
|--------------|------------|------------|-------|--------|-----|
| BC107/8/9 | 8p | BC184/184L | 12p | BFY51 | 20p |
| BC114 | 18p | BC212/212L | 14p | BFY62 | 20p |
| BC147/8/9 | 10p | BC847/808A | 12p | AF178 | 30p |
| BC188/7/8 | 12p | BF194 | 12p | OC71 | 12p |
| BC182/182L | 11p | BF197 | 13p | 2N3055 | 50p |

POPULAR DIODES—1N914 5p, 8 for 45p, 18 for 90p; 1N916 5p, 6 for 45p, 14 for 90p; 1S44 5p, 11 for 50p, 24 for £1.00, 1N4148 5p, 8 for 27p, 12 for 48p; 1N4001 8p; 002 6p; 005 6p; 004 7p; 005 7p; 006 8p; 007 8p. **LOW PRICED ZENER DIODES**—400mW. Tol. ±5%. 4.5mA. Values available: 3V, 3.3V, 3.6V, 4.7V, 5.1V, 5.6V, 6.2V, 6.8V, 7.5V, 8.2V, 9.1V, 10V, 11V, 12V, 13V, 13.5V, 15V, 16V, 18V, 20V, 22V, 24V, 27V, 30V, 33V. All at 7p each, 8 for 50p, 14 for 84p. SPECIAL OFFER: 100 Zeners for £5.60.

RESISTORS—High stability, low noise carbon film 1%, 1/2W at 40°C, 1/4W at 70°C. E12 series only—from 2.2Ω to 2.2MΩ. ALL at 1p each, 5p for 10 of any one value, 70p for 100 of any one value. SPECIAL PACK: 10 of each val. at 2.2Ω to 2.2MΩ (730 resistors) £5.

SILICON PLASTIC RECTIFIERS—1.5 amp, brand new improved DO27: 100 P.I.V. 7p (4 for 28p); 400 P.I.V. 8p (4 for 30p).

BRIDGE RECTIFIERS—24 amp: 200V 40p; 350V 45p; 500V 55p.

SEMICONDUCTOR VERTICAL PRESETS—0.1W only: All at 5p each: 50Ω, 100Ω, 220Ω, 470Ω, 430Ω, 1kΩ, 1.2kΩ, 4.7kΩ, 6.8kΩ, 10kΩ, 15kΩ, 22kΩ, 47kΩ, 100kΩ, 250kΩ, 500kΩ, 1MΩ, 2.5MΩ, 5MΩ.

PLEASE ADD 15p POST AND PACKING ON ALL ORDERS BELOW £5. ALL EXPORT ORDERS ADD COST OF S.F.A./I.R.M.AIL.

PLEASE ADD 25% V.A.T. TO ORDERS. Send S.A.E. for lists of additional ex-stock items. Wholesale price lists available to bona fide companies.

MARCO TRADING (Dept. W9). The Old School, Edinston, Nr. Wem, Shropshire. Tel: Whizzall 464/465 (TEL 094 872) (Proprs. Minicoat Trading Ltd.)

COMPONENTS GALORE, pack of 500 assorted Radio, TV and Electronic components, a real bargain at a realistic price. Send only £1.50 c.w.o. This applies only to United Kingdom and Ireland. Overseas prices by arrangement. Caledonian Components. PO Box 3, Glenrothes, Fife, Scotland.

5lb parcels surplus electronic components resistors, capacitors, switches, pots etc. £1.20 p & p. 80p.

Wirewound resistors 2W and upwards mixed values 30 for £1, p & p 20p.

Lights bulbs mixed voltage & wattage eg. 2.5v, 5v, 12v etc. from 0.5 watt upwards, including panel lights and vehicle bulbs 30 for £1.

R. A. Stobbs, 933 Manchester Rd., Cowlesley, Huddersfield, Yorks HD4 5TA.

INTERSIL ICL 8038CC £3.70; ICL 8058 BC £6.18; TIL 209 equivalent LEDs 11p; 741C 31p; common anode 7 segment LED displays, DIN compatible with DL707 etc £1.08 each, 10 for £8.64; CT7001 digital clock chip £6.75; LM301A 62p; SN7400 14p; SN7413 32p; SN7490 49; Sinclair Cambridge Calculator £15.99; Sinclair Cambridge Memory Calculator £18.36; Sinclair Scientific Calculator £21.55. Catalogue 10p. All prices include VAT. Mail order only to: G. Newman, 12 Francis Avenue, St. Albans, AL3 6B.

UNBELIEVABLE SPEAKER BARGAINS! 8Ω Acoustic Suspension, teak/sculptured foam front, 6 watt £5.30; 12 watt £6.50; 16 watt (8in woofer, 3in tweeter) £7.90. (Lists 20p.) Satisfaction guaranteed (10% p&p). Gregg Electronics, 105 Grange Road, London SE25.

Service Sheets

SERVICE SHEETS, radio, TV etc. 10,000 models. Catalogue 24p, plus SAE with orders, enquiries. Telray, 154 Brook Street, Preston PR1 7HP.

LARGE SUPPLIER OF SERVICE SHEETS

(T.V., RADIO, TAPE RECORDERS, RECORD PLAYERS, TRANSISTORS, STEREOGRAMS, RADIOGRAMS, CAR RADIOS) ALL AT 50p EACH

"PLEASE ENCLOSE LARGE S.A.E WITH ALL ENQUIRIES & ORDERS"

Otherwise cannot be attended to (Uncrossed P.O.s please, original returned if service sheets not available.)

PLEASE NOTE We operate a "by return of post" service. Any claims for non-delivery should be made within 7-days of posting your order.

C. CARANNA

71 BEAUFORT PARK LONDON, N.W.11 6BX

We have the largest supplies of Service Sheets (strictly by return of post). Please state make and model number alternative. Free TV fault tracing chart or TV list on request with order.

Mail order or phone 01-458 4882

NO OVERSEAS MAIL PLEASE

SERVICE SHEETS for Radio, TV, Tape Recorders, Stereo, etc., with free fault-finding guide, 50p and SAE, Hamilton Radio, 47 Bohemia Road, St. Leonards, Sussex.

Educational

GO TO SEA as a Radio Officer. Write: Principal, Nautical College, Broadwater, Fleetwood FY7 8JZ.

Situations Vacant

**MEN!
£90 p.w.
can be yours**

Tens of thousands of new computer personnel needed over the next few years alone. With our revolutionary, direct-from-America, course, you train as a Computer Operator in only 4 weeks!

It can pay around £35 p.w. as a starter and can reach over £90 p.w.

After training, our executive appointments bureau—one of the world's leaders of its kind—introduces you FREE to world-wide opportunities. Write or phone TODAY, without obligation.

London Computer Operators Training Centre

Y27, Oxford Hse.,
9-15 Oxford St. W1. Tel: 01-734 2874

Official Appointments

AUSTRALIA EXPERIENCED SERVICEMAN REQUIRED

We require a person to take charge of our expanding consumer electronics service department. Formal qualifications are not necessary, however, wide experience in servicing transistor radios, tape recorders, car tape players, car radios, Hi-fi amps and turntables of both European and Japanese origin is a necessity. Please do not apply if you have not had at least two years experience in this field.

Pay will depend on experience and would include a good monthly bonus. We envisage the successful applicant earning in the vicinity of £6,000-00 P.A. We would require a person who could come to Australia immediately and we would be willing to pay the air fare providing the applicant stays with us for at least 18 months.

The weather is great, our winter is like your summer, the beaches fabulous. The future unlimited so please write to the personnel manager (airmail of course!) giving a brief life story.

DICK SMITH ELECTRONICS PTY LTD.
162 Pacific Highway, Gore Hill, SYDNEY,
N.S.W. 2065, AUSTRALIA

For Sale

MICROPHONES: AKG D202EI, £45-00; AKG D190C or E, £20-00; AKG D224, £60-00; Sennheiser MD211N, £45-00. All brand new and boxed. Please add 25% for VAT. All other AKG and Sennheiser mikes, SAE for quote. J. J. Francis (Wood Green), Ltd., Manwood House, Matching Green, Harlow, Essex. Tel: Matching 476.

SOUNDLIGHT CONVERTERS 3-channel: 1-5kW, £17; 3kW, £25. Strobes: 1-joule, £21; 4J, £27; 15J, £45. Chasers from £27. Rainbows, Projectors. Bumper catalogue: Aarvak Electronics, 88a(P) West Green Road, N15 5NS. 01-800 8656.

COPPER CLAD LAMINATE FOR PRINTED CIRCUITS

Single sided 1/16" paper base—1-0p/sq. inch.
Single sided 1/16" glass-epoxy—1-5p/sq. inch.
Any rectangular sizes cut to your requirements.
Please send cash with order.
Price includes postage and packing.
From: **SIMTECH ENGINEERING LTD**
Voluntary Place
WANSTEAD, LONDON E11 2RP
01-530 4240

AERIAL MAIL ORDER business. Complete stock of 500 aerial material to clear, £250. 90 Ewhurst Road, Crawley 23885 Sussex.

COMPONENTS CLEAR-OUT SALE. Ridiculous Prices. SAE: Briggs, 12a Bruce Grove, London N17 6RA.

LAMINATE OFF-CUTS FOR PRINTED CIRCUITS. Copper clad 1/16in single/double sided EPOXY GLASS IN ASSORTED SIZES (average 5in x 10in) £1-00 per lb (approx 200 sq.in) Minimum order £1-00. Cash with order please to:—Midland Circuits Limited, 76 Cato Street North, Birmingham B7 5AN.

Wanted

TOP PRICES PAID for NEW VALVES and TRANSISTORS

popular T.V. and Radio types.

KENSINGTON SUPPLIES (C),
367 Kensington Street, Bradford 8,
Yorkshire.

WE BUY New Valves, Transistors and clean new components, large or small quantities, all details, quotation by return. **WALTON'S, 55 Worcester Street, Wolverhampton.**

WANTED, H.R.O. Communication receiver, in good condition. A Worthington, 66 Cross Street, Arnold, Nottingham.

Aerials

NEW HIGH GAIN 4 ELEMENT VHF/FM RADIO AERIAL

Stereo or mono!

Increase volume, quality and sensitivity of any VHF/FM

Radio or Hi-Fi, stereo or mono with this genuine aerial. It's a necessity if you want the best out of your equipment, whether a small radio or expensive stereo. Don't put up with poor reception any longer. Send now, hear for yourself. Ideal for the do-it-yourself enthusiast. Supplied with clamp, instructions and advice. Use inside or out. FREE with order maps and channel reference of all Radio and TV Transmitters! Money Back Refund. Send Direct to Dept. HS10 219 Mansfield Rd., Nottingham.

**ONLY
£4.49
inc VAT
+£0.00 P & P**

IMPERIAL TRADING & SERVICES LTD.
the quality Aerial Specialists.

STOCKISTS of Jaybeam Stereobeams, Antiference Mush Killers, Rotars, coax cable, masts and fittings. Send stamp for full lists competitive prices. Alan Turner Services, 26 Chapel Garth, Skipsea, Driffeld.

GENUINE FULL SIZE 18 element TV aerial as used by leading TV companies

ITV BBC1
£28/W & Colour
Guaranteed
Perfect Pictures.
Save EEs. We supply
this genuine U.H.F. aerial
for only £2.55. can be fitted
outside or inside. Quality made
technically advanced design. Precision
ion grid reflector eliminates ghosting.
Complete with clamp, instructions, advice.
Money Back Refund. Wall/Caravan Bracket
25p. Best Cable 12p per yard. Plug 10P &
FREE with order maps & channel reference of
Radio & TV Transmitters. Send direct to
Dept. PW to 219 Mansfield Rd, Nottingham

IMPERIAL TRADING & SERVICES LTD.
the quality Aerial Specialists

Books and Publications

UFO CHARTS: Wave Prediction 56p; Daily Flight Pattern 50p; TV Detection 66p; Propulsion Theory 57p; "Anti-Gravity" 57p; Map 52p; Circuits: Transistor Optical Detector 68p; Radiation/Optical 46p; Crystal Radiation Counter 85p; Sighting Recorder 55p; 22-Range Multimeter Digital 95p. R & E, Highlands, Needham Market, Suffolk.

Technical Books - Radio & Electronics

| | |
|---|-------|
| World's Radio & TV Stations (International Edit)..... | £0.68 |
| Audio Amplifiers..... | £0.70 |
| Boys Book of Crystal Sets & Simple Circuits..... | £0.33 |
| Television Timebase Circuits..... | £1.15 |
| Radio TV and Industrial Tube & Valve Equip..... | £0.68 |
| How to get the best out of your Tape Recorder..... | £1.67 |
| Practical Electronic Science Projects..... | £0.85 |
| Jack Darr's Service Clinic..... | £1.55 |
| Transistor Circuits for Modern Test Equipment..... | £0.68 |
| Rad & Electr Colour Codes and Data Chart..... | £0.20 |
| Handbk of Transistor Equip & Substitutes..... | £0.48 |
| Hi Fi, PA & Disco Amplifier Design Hndbk..... | £0.87 |
| Radio Servicing Problems..... | £0.75 |
| Electronic Circuits for the Amat Photographer..... | £0.68 |
| Handbook of Simple Transistor Circuits..... | £0.40 |
| TV Fault Finding..... | £1.10 |
| Sound and Loudspeaker Manual..... | £0.60 |
| Practical Stereo & Quadraphony Handbook..... | £0.85 |
| Radio Amateur Operator's Handbook..... | £0.85 |
| Coil Design & Construction Manual..... | £0.58 |
| Radio TV & Electronics Data Book..... | £0.68 |
| 79 Electronic Novelty Circuits..... | £0.80 |
| Receiving Pal Colour Television..... | £5-35 |
| Radio Technicians Bench Manual..... | £3.30 |
| Servicing Transistor Radio Receivers..... | £0.90 |
| 1st Book of Hi Fi Loudspeaker Enclosures..... | £0.68 |
| 2nd Book of Hi Fi Loudspeaker Enclosures..... | £0.68 |
| Manual of Electronic Circuits for the Home..... | £0.60 |
| Modern Crystal Set Circuits for Beginners..... | £0.40 |
| Electronic Novelties for the Motorist..... | £0.58 |
| 2nd Book of Transistor Equip & Substitutes..... | £1.07 |
| Handbook of Electronic Musical Novelties..... | £0.58 |
| Transistorised Novelties for Hi Fi Enthusiast..... | £0.40 |
| Fault Location Exercises in Rad. & TV Vol.1..... | £0.95 |
| Fault Location Exercises in Rad. & TV Vol.2..... | £1.55 |
| Colour TV Picture Faults..... | £2.70 |
| Practical Transistor Novelty Circuits..... | £0.48 |
| Boys Book of Practical Radio & Electronics..... | £0.68 |
| Radio Receiver Construction using ICs & Transis..... | £0.68 |
| ICs & Transistor Gadgets Construction Handbk..... | £0.68 |
| Integrated Circuits Equip & Substitutes Hbk..... | £0.85 |
| Audio Technicians Bench Manual..... | £3.30 |
| Improving your Hi-Fi..... | £2.80 |
| Guide to Printed Circuits..... | £2.80 |
| Towers International Transistor Selector..... | £3.30 |
| WORLD RADIO TV HANDBOOK 1975..... | £3.80 |

All prices include Postage & Packing

RADIO BOOK SERVICE

40 Elwill Way, Beckenham BR3 2RZ

"UNDERSTANDING SOLID-STATE ELECTRONICS" is the simplest, easiest-to-follow book yet on the subject. Includes 12-lesson self-teaching course with "quizzes". 242 pages. technical glossary with each chapter. And only £1-20 post paid. Send a cheque/P.O. for your copy now to: **MS21/WW1, Book Sales, Texas Instruments Ltd., Manton Lane, Bedford MK41 7PA.**

Miscellaneous

P.W. EASI BUILD ORGAN

Set of two P.C.Bs £6.80
Set of all semiconductors plus two P.C.Bs £34.90

DIGI-CLOCK COMPONENTS

AY-5-1224 £4.15 ea.
3½ Digits MAN3640 £5.96 set
All include V.A.T. and P. & P.

FORESIGHT ELECTRONICS

62, HIGH ST.,
CROYDON

Mail Order only Allow 14 days

HARDWARE. Comprehensive range of screws, nuts, washers, etc. in small quantities, and many useful Constructors' items. Sheet aluminium to individual requirements, punched, drilled, etc. Fascia panels, dials, nameplates in etched aluminium. Printed circuit boards for this magazine and other individual requirements, one-offs and small runs. Machine engraving in metals and plastics, contour milling. Send 2 x 4½p stamps for catalogue. Ramar Constructor Services, Masons Road, Stratford on Avon, Warwicks., CV37 9NF.

ALUMINIUM PROJECT BOXES

lids and screws included

| Box No. | Length" | Width" | Height" | Price |
|---------|---------|--------|---------|-------|
| 7 | 5½ | 2½ | 1½ | 47p |
| 8 | 4 | 4 | 1½ | 48p |
| 9 | 4 | 2½ | 1½ | 46p |
| 10 | 5½ | 4 | 1½ | 49p |
| 11 | 4 | 2½ | 2 | 46p |
| 12 | 3 | 2 | 1 | 38p |
| 13 | 6 | 4 | 2 | 58p |
| 14 | 7 | 5 | 2½ | 75p |
| 15 | 8 | 6 | 3 | 93p |
| 16 | 10 | 7 | 3 | £1.14 |

Prices include VAT (at 8%) but 18p should be added to the total order value for postage and packing.
8 WATT 12 VOLT FLUORESCENT LIGHT KIT Complete Kit including all components, heatsink, channel, tube, etc.
ONLY £3.49 inc. VAT p & p
Ready Built £4.10 inc. VAT, p & p
Diffuser 39p extra inc. VAT, p & p
Send Cheques or P.O.'s with your order direct to—
ELECTRONICS DESIGN ASSOCIATES
(Dept. PW9), 82 Bath Street, Walsall WS1 3DE
Phone: Walsall 38552

SUPERB INSTRUMENT CASE by Bazelli, manufactured from heavy duty PVC faced steel. Hundreds of Radio, Electronic, Hi-Fi enthusiasts, and Industrial users are choosing the cases they require from our range. Make your VAT go further with our competitive prices which begin at a low 75p. Examples: Width, Depth, Height 7" X 7" X 5" £2.65, 8" X 10" X 6" £3.60, 12" X 8" X 7" £4, 12" X 12" X 7" £4.40. Over 200 Models to choose from, Prompt despatch. Free literature (Stamp would be appreciated) Bazelli Dept No 25, St. Wilfrids, Foundry Lane, Halton, Lancaster LA2 6LT.

PHOTOTECH (EUROPE)

New optoelectronic detectors

- Type 1** Photodiode
2 pin configuration
Photosensitive area 0.85 x 10⁻³ square inches
- Type 2** Photoswitch
4 pin configuration 20v-30v supply
Switching threshold set by external R-C
- Type 3** Photoswitch with automatic threshold adjustment
8 pin configuration 20v-30v supply
Data and operating notes sent with each order
Prices (including VAT, pkg & carr.)
Type 1: 75p each
Type 2: £1.08 each
Type 3: £1.58 each

Please send two to: Phototech (Europe)
22a Upper Elmers End Rd
Beckenham Kent

PCB MANUFACTURER'S OFFER. IPC approved full spec., fully drilled ready to assemble PCBs for: "PW"; Easy-build Organ, £5.70 (2 PCBs); Tricolour, £1.37; Tele-Tennis (6 PCBs), £3.70; Add-on Sound Effects, £1.10; Telephone Exchange, £1.10; Ferret Metal Locator, 78p; Derby, 85p; Audio/Mixer, 40p; Tone & Rumble, 65p; "PE" CCTV, £2 (2 PCBs); Orion with printed layout on PCB, £1.20; Power Slaves, £1.60 (3 PCBs); Scorpio 2, 70p; Gas Detectors, £1.20; Pulse Generator, £1.10. CWO. Prices totally inclusive. Many others available. SAE for lists. Production space for PCB production. Electroplating, Screen Printing, Tinning, plus all Graphic/Art & Photographic and Design facilities and supplies. Estimates by return or Phone WKF Electronics, Welbeck Street, Whitwell, Worksop, Notts. S80 4TW. Tel: Whitwell 695 (Derbys.). Callers to 1-3 Station Road.

Smiths molaysyn position indicator and transmitter, with or without modification will work as an aerial or wind direction monitor, £1.70p. No. 7 Moving Coil hand mike, 75p. Vero board 0.1 matrix 3-3/4" sq. 22p. LED Red or Green with clips 18p. Ex-calcraft mic. meter, 1mA. FSD. Scaled 0-110% (with coloured sectors) 3" dia. £2.75p. Min. order 25p. Prices include P & P. SAE for list.

Eidun Electronics, 16, Raven Road, Timperley, Cheshire.

TRIACS (plastic) 10A/400V 67p (3+64p), Diac 19p, NE555V 55p (3+50p), 2N6027 PUT 30p, Ferrite Rods 1¼ in x ¾ in dia. 10p, Plastic Lightdimmer Frontplate 20p, with ¾ in dia hole 22p. P&P 15p. Add VAT. T.K. Electronics, 106 Studley Grange Road, London W7 2LX.

JAYBEE FOR KITS

AMTROM, JOSTYKIT, ETC.

Send S.A.E. for full information

JAYBEE ELECTRONICS, Sarum Farm Est.
SARUM ROAD, WINCHESTER, HANTS
Telephone 0962-81886

BUILD YOUR OWN

You are invited to send S.A.E. for lists of our very extensive range of high quality amplifier, pre-amps, F.M. tuners, Instruments, Radiocontrol Ignition units and many other kits.

TELERADIO ELECTRONICS,
325 FORE STREET, EDMONTON,
LONDON N9

DIGITAL CLOCK CHIP, AY-5-1224, with data & circuit diagram, £3.66 + VAT, Jumbo LED digits (16mm high) economy type DL-747, only £2.04 each + VAT, post free.—Greenbank Electronics, 94 New Chester Road, Wirral, Merseyside, L62 5AG.

THE SCIENTIFIC WIRE CO

Copper - Nickel Chrome - Eureka - Manganin Wires.

Enamelled - Silk - Cotton - Tinned Coverings. No minimum charges or quantities.

Trade and Export enquiries welcome.

S.A.E. Brings List.

P.O. BOX 38, LONDON, E4 9BW

ELECTRONIC BARGAINS list No. 10. Send 8p. Grimsby Electronics, Lambert Road, Humberside.

FANTASTIC NEW MICROTEST 80

MEASURES ONLY
90 X 70 X 18 mm
ELECTRONIC ZERO !!



Amazing Value at £11.95
8 fields of measurement and 40 ranges

PRINTED CIRCUIT BOARD IS REMOVABLE WITHOUT SOLDERING

Volts D.C. 8 ranges: 100mV - 2V - 10V - 30V - 200V - 1000V (20kΩ/V) .2% precision on DC and AC
Volts A.C. 5 ranges: 1.5V - 10V - 50V - 250V - 1000V (4kΩ/V)
Amp. D.C. 6 ranges: 50μA - 500μA - 5mA - 50mA - 500mA - 5A
Amp. A.C. 5 ranges: 250μA - 2.5mA - 25mA - 250mA - 2.5A
Ohms: ranges: Low Ω - 0 x 1 - 0 x 10 - 0 x 100 from 1/10 Ω until 5 Mega Ω
V Output 5 ranges: 1.5V - 10V - 50V - 250V - 1000V
Decibels 5 ranges: + 6dB, + 22dB, + 36dB, + 50dB, + 62dB
Capacity 4 ranges: 25μF - 250μF - 2500μF - 25,000μF



SUPERTESTER 680R ICE

20,000 Ohm per Volt/sensitivity • Fully screened against external magnetic fields • Scale width and small case dimensions (128 x 95 x 32mm) • Accuracy and stability (1% in D.C., 2% in A.C.) of indicated reading • Simplicity and ease of use and readability • Full ranges of accessories • 1000 times overload • Printed circuit board is removable without de-soldering

More ranges than any other meter. Ask for free catalogue **£18.50**

Accessories (extra) available to convert Microtest 80 & Super Tester 680R into following: LIGHT-METER GAUSS METER, ELECTRONIC VOLTMETER, AMPERCLAMP, TRANSISTOR TESTER, TEMPERATURE PROBE, PHASE SEQUENCE INDICATOR, Ω x 100k Multiplier, SIGNAL INJECTOR—Send for details.

MORE RANGES FOR LESS MONEY!

AC/DC Multimeter type U4324

A-DC 0-99-3A - 8 Ranges.

A-AC 0-3-3A - 5 Ranges.

V-DC 0-6-1200V - 9 Ranges.

V-AC 3-900V - 8 Ranges.

Freq.: In the range of 45 to 20kHz

Resistance: 600 Ohm to 5 MOhm

B Ranges, Decibel: -10 to +12dB

Accuracy: ± 2.5% DC, ± 4% AC

Dimensions: 167 x 98 x 63 mm.

Only **£9.25**

ALPHANUMERIC NIXIE TUBES 87971

The Alpha-numeric NIXIE tube has the ability to display all the letters of the alphabet, numerals 0 thru 9 and special characters in a single tube. From the stand point of both readability and electrical characteristics, the Alphanumeric NIXIE tube provides many unique benefits including: 170v-21mA • All d.c. operation • Uniform, continuous line characters of equal height • Memory with simple solid state drive circuits • Readability in high ambient light • 200 footcandle brightness • Long life with no loss of brightness • Character height 2½ in.



Price only **99p** each plus 18p P/P. Bases for above 60p each.

JUST ARRIVED !!

NUMERIC INDICATOR TUBES

Ultra-long life, high quality, 0-9 and 2 independent decimal points. Supply voltage 200V D.C. (Current 14mA, Pulse duration 100μs. Character height 0.51, overall size 1.4. Brand new, guaranteed. Surplus to manufacturers requirements. Type B5853st 1-25 £1. 25 + 90p 100 + 80p 1000+ price on application

8% VAT to all items + 35p P & P

ELECTRONIC BROKERS LTD.

49-53 Pancras Road, London NW1 2QB

Tel: 01-837 7781

Synthesiser "Sounds Supreme"

by Dewtron (25% VAT extra.)

Famous kits, e.g. waa-waa complete kit £4.50; Fuzz kit £6.50. P&P 25p under £10. Ring Modulator modules £11. "Mister Bassman" Bass Pedal Units and whole range of synthesiser modules, musical novelties, etc. Catalogue 20p from D.E.W. Ltd., 254 Ringwood Road, Ferndown, Dorset.

TEXAN AMPLIFIER 20 + 20 Watt Complete Kit £32.00 (Tax extra)

Pack 1. Res. 30p. Pack 2/3. Capacitors £3.65. Pack 5. Switches £1.50. Pack 6. Pots. Pack 7. Semi Cond. £3.25. Pack 9 P.C.B. £3.00. Pack 10. Chassis £3.00 Case £3.50.

Toroidal Transf. £6.00 P.P. + Tax extra £2. (Toroidal Transf. for 28W £6.10 + tax & post £2)

TELERADIO ELECTRONICS

325 Fore St., Edmonton, London N9

STEREO DECODERS £4.50. Suitable for most tuners and receivers. SAE details:— Walker, 13, Greenhill Road, Halesowen, West Midlands.

12 VOLT 21" 13 Watt Fluorescent Lighting

(by Thorn/AE) with diffuser & on/off switch. Ideal caravan, boat, emergency lighting, etc. Guaranteed.



£5.50 inc. VAT & Post. List price £7.02 inc. VAT

SALOP ELECTRONICS

23 Wyle Cop, Shrewsbury, Shropshire Tel. 53266

RANDOM NUMBER SELECTOR

Minicomp 6L: New! Electronic Dice, range 1-6. Jumbo. 0.6in LED display. 4 ICs. Kit £14.75; built and tested £16.90. Minicomp 10L: Two ranges 1-6 and 0-9. Kit £17.75, built and tested £19.90. Minicomp 100: Four ranges 1-6, 0-36 (Roulette), 0-59 (Pools) and 0-99. Nixie display, 6 ICs. Built and tested £29.50. Terms: CWO, Mail Order only. Prices inclusive. 1 year guarantee.

MICROELECTRONICS

51 Mexfield Road, London SW15 2RG

FORESIGHT ELECTRONICS

92 High Street, Croydon

COMPLETE P.W. DIGITAL CLOCK KIT

£18.00

inc. V.A.T. and P.P.
Mail Order Only Allow 14 days

DON'T LOOK

unless you can resist the temptation to get these super 'attention-getters':

- ★ Pocket-sized **MAXI-VOLT** Big 4inch Spark Generator (instant 15,000 volts!). Ready-made, needs no batteries. Carry it around anywhere. Only weighs about 3 oz. (89g.) send £2.45 for your Maxi-Volt now!
- ★ Unique **TRANSMITTER/RECEIVER** Kit. No licence examinations or tests required to operate this transistorised equipment. Easy to build. Get transmitting. Send £7.95 for yours now!
- ★ Psychedelic **MINI-STROBE** Kit. Take a pocket-sized lightning storm to Disco's & parties. "Brain-freeze" 'em with vari-speed stop-motion flashes. Includes super case too. Send £3.50 now! (all prices include V.A.T., packing & postage.)

Send remittance to:

BOFFIN PROJECTS,

4 CUNLIFFE ROAD,
STONELEIGH, EWELL, SURREY

(Mail order U.K. only)
Or for more details, send 20p for lists

TREASURE TRACER MK III Metal Locator



- Variable tuning
- Britain's best selling metal locator kit
- Weighs only 22oz. Fitted with Faraday shield.
- Speaker and earphone operation
- Knocks down to only 17in.
- Prebuilt search coil assembly
- Thoroughly professional finish
- As seen on BBC1 and BBC2 TV
- You only need soldering iron, screwdriver, pliers and snips
- Five transistor circuit

Send stamped, addressed envelope for leaflet

Complete £10.90 Built & tested £15.25
Post 50p (25p VAT/BEC) Post 90p £1.21 VAT 20p

MINIKITS ELECTRONICS

63 CLEVELAND ROAD,
LONDON, E8 2AN (Mail order only)

USEFUL screws, nuts and washers. Send SAE for details. Clive Brittain, The Bungalow, Old Titness, Buckhurst Lane, Sunninghill, Ascot, Berks. SL5 7QB.

VALVES, RADIO-TV-TRANSMITTING-INDUSTRIAL 1930 to 1975. 2200 types stocked. Many obsolete. SAE for quotation. List 20p Postal Export Service. We purchase new and boxed valves. Cox Radio (Sussex) Ltd., The Parade, East Wittering, Sussex. West Wittering 2023.

H. M. ELECTRONICS

275a FULWOOD RD., BROOMHILL,
SHEFFIELD S18, 3BD

BEC CABINETS



Be proud of your work and build it in a BEC (Book End Chassis) 5 Standard sizes

Please send 15p (Refundable) for folder of leaflets

Ladders

LADDERS, timber and aluminium.
Tel: Telford 586644 for brochure.

ORDER FORM PLEASE WRITE IN BLOCK CAPITALS

Please insert the advertisement below in the next available issue of Practical Wireless for insertions. I enclose Cheque/P.O. for £..... (Cheques and Postal Orders should be crossed Lloyds Bank Ltd. and made payable to Practical Wireless).

| | | | |
|--|--|--|--|
| | | | |
| | | | |
| | | | |
| | | | |
| | | | |
| | | | |
| | | | |
| | | | |

NAME

ADDRESS

.....

Send to: Classified Advertisement Manager
PRACTICAL WIRELESS, Flatway House,
Farringdon Street, London EC4A 4AD
Telephone 01-634 4451

Rate
14p per word, minimum 12 words. Box No. 35p extra.

Company registered in England. Registered No. 53626. Registered office: Tower House, 8/14 Southampton Street, London WC2E 9QX.

WATFORD ELECTRONICS

35 CARDIFF ROAD, WATFORD, HERTS, ENGLAND
MAIL ORDER: CALLERS SATURDAYS ONLY

OUR NEW LOW PRICES MEANS YOU PAY LESS VAT.

| TRANSISTORS (less 10% for 25+ of one type) | | | | | | | | | |
|--|------------|-------------|------------|------------|-------------|--|--|--|--|
| AC125 13p | BC148 7p | BF177 26p | OC70 11p | 1S44 5p | 2N2926Y 8p | | | | |
| AC128 11p | BC149 9p | BF178 26p | OC71 11p | 1S920 7p | 2N3053 8p | | | | |
| AC127 11p | BC154 16p | BF179 33p | OC72 11p | 1S921 7p | 2N3054 42p | | | | |
| AC128 11p | BC157 13p | BF180 33p | OC74 28p | 1S922 8p | 2N3055 45p | | | | |
| AC141 20p | BC158 12p | BF181 33p | OC81 12p | 1S923 10p | 2N3014 59p | | | | |
| AC142 20p | BC159 13p | BF184 22p | OC82 12p | 2N696 15p | 2N3015 59p | | | | |
| AC176 11p | BC167 12p | BF190 10p | OC83 28p | 2N697 13p | 2N3020 12p | | | | |
| AC187 11p | BC168 12p | BF194 10p | OC140 100p | 2N698 30p | 2N3703 12p | | | | |
| AC188 11p | BC169 12p | BF195 10p | OC201 70p | 2N706 11p | 2N3704 12p | | | | |
| AC197 35p | BC170 11p | BF196 12p | OC202 80p | 2N708 16p | 2N3705 12p | | | | |
| AC198 11p | BC171 11p | BF197 12p | TIC44 30p | 2N718 40p | 2N3706 10p | | | | |
| AC199 25p | BC172 11p | BF257 32p | TIP29 43p | 2N930 18p | 2N3707 10p | | | | |
| AC20 24p | BC177 16p | BF256 39p | TIP29A 45p | 2N1191 20p | 2N3708 10p | | | | |
| AC21 29p | BC178 16p | BF259 18p | TIP30 54p | 2N1192 20p | 2N3709 8p | | | | |
| AC22 18p | BC179 16p | BF260 21p | TIP30A 54p | 2N1301 20p | 2N3710 9p | | | | |
| AD140 48p | BC182 10p | BF261 21p | TIP31 54p | 2N1302 17p | 2N3711 140p | | | | |
| AD149 45p | BC183 10p | BF262 21p | TIP32 64p | 2N1303 20p | 2N3772 160p | | | | |
| AD161 34p | BC184 11p | BFY50 15p | TIP33 95p | 2N1304 24p | 2N3773 240p | | | | |
| AD162 34p | BC184 11p | BFY51 15p | TIP34 130p | 2N1305 24p | 2N3819 22p | | | | |
| AF114 13p | BC182L 12p | BFY52 15p | TIP35 140p | 2N1306 24p | 2N3820 60p | | | | |
| AF115 13p | BC212L 12p | BU105 £2.20 | TIS44 26p | 2N1893 30p | 2N3824 50p | | | | |
| AF116 13p | BC213 12p | MUE370 65p | TIS44 26p | 2N1890 45p | 2N3904 15p | | | | |
| AF117 13p | BC214 13p | MUE371 78p | ZTX107 10p | 2N2160 62p | 2N3905 17p | | | | |
| AF118 40p | BCY42 28p | MUE520 62p | ZTX108 8p | 2N2217 23p | 2N3906 17p | | | | |
| AF124 30p | BCY45 18p | MFP102 30p | ZTX109 12p | 2N2219 20p | 2N4037 35p | | | | |
| AF125 30p | BCY59 18p | MFP103 30p | ZTX300 12p | 2N2220 20p | 2N4038 15p | | | | |
| AF127 30p | BCY70 18p | MFP104 30p | ZTX301 14p | 2N2222 20p | 2N4061 13p | | | | |
| AF139 30p | BCY71 18p | MFP105 30p | ZTX302 18p | 2N2303 25p | 2N4062 14p | | | | |
| AF181 45p | BCY72 12p | OC23 144p | ZTX304 22p | 2N2369 14p | 2N4871 31p | | | | |
| AF186 48p | BD124 75p | OC26 40p | ZTX311 10p | 2N2483 30p | 2N5457 30p | | | | |
| AF239 38p | BD131 40p | OC28 48p | ZTX341 19p | 2N2646 38p | 2N5458 30p | | | | |
| BC107 9p | BD132 40p | OC35 48p | ZTX500 15p | 2N2904 20p | 2N5459 30p | | | | |
| BC108 9p | BD137 45p | OC36 48p | ZTX501 15p | 2N2905 15p | 3N140 85p | | | | |
| BC109 12p | BDY61 75p | OC41 15p | ZTX502 18p | 2N2907 18p | 3N141 85p | | | | |
| BC109C 9p | BDY61 75p | OC42 15p | ZTX504 42p | 2N2926G10p | 40381 40p | | | | |
| BC109C 12p | BDY61 75p | OC44 12p | ZTX531 23p | 2N2926G 8p | 40382 40p | | | | |
| BC147 7p | BF115 22p | OC45 12p | ZTX550 18p | 2N2926R 8p | 40673 58p | | | | |

| TTL 74s | | | |
|-------------|-----------------|------------------|-------|
| DIGITAL ICs | Less 5% for 15+ | Less 10% for 25+ | mixed |
| 7400 14p | 7430 15p | 7475 32p | |
| 7401 14p | 7432 25p | 7476 32p | |
| 7402 15p | 7433 36p | 7480 44p | |
| 7403 15p | 7437 27p | 7481 99p | |
| 7404 15p | 7438 27p | 7482 75p | |
| 7405 15p | 7440 15p | 7484 90p | |
| 7406 38p | 7441 65p | 7485 125p | |
| 7407 38p | 7442 65p | 7489 275p | |
| 7408 15p | 7443 120p | 7490 40p | |
| 7409 15p | 7444 105p | 7491 80p | |
| 7410 15p | 7445 85p | 7492 48p | |
| 7411 20p | 7446 105p | 7493 39p | |
| 7412 20p | 7447 100p | 7494 83p | |
| 7413 35p | 7448 70p | 7495 72p | |
| 7414 60p | 7450 15p | 7496 72p | |
| 7416 35p | 7451 15p | 7497 83p | |
| 7417 35p | 7453 15p | 7498 83p | |
| 7420 15p | 7454 15p | 7499 83p | |
| 7421 20p | 7455 15p | 7500 83p | |
| 7422 20p | 7456 15p | 7501 83p | |
| 7423 27p | 7470 30p | 7502 83p | |
| 7425 27p | 7472 26p | 7503 83p | |
| 7426 27p | 7473 33p | 7504 83p | |
| 7428 38p | 7474 32p | 7505 83p | |

| DIODES | | VIDEO SPORT | |
|-------------|-------------|--|--|
| BY100 18p | BY127 11p | Play the three exciting games, TENNIS, FOOTBALL & HOLE IN THE WALL on your own TV Screen. Just plug the Video Sport to the aerial socket and play the Tele Sport at the touch of the button. | |
| OA5 38p | OA9 9p | Only £30.00 (+8% VAT) p & p 50p | |
| OA10 36p | OA17 8p | | |
| OA70 8p | OA79 8p | | |
| OA85 10p | OA91 6p | | |
| OA90 6p | OA100 10p | | |
| OA91 6p | OA200 6p | | |
| OA92 6p | OA202 6p | | |
| IN91 4p | IN91A 2p | | |
| IN4001/2 8p | IN4002 8p | | |
| IN4003 5p | IN4004 5p | | |
| IN4005 5p | IN4006/7 6p | | |
| IN4148 5p | IS920 8p | | |
| IS921 8p | IS922 8p | | |

| LINEAR ICs | | | |
|-----------------|--------------|--------------|-------------------|
| 709C 14 pin 28p | LM304H 170p | SN76023 160p | SCRs (Thyristors) |
| 709C 20p | LM305 170p | SN76115 200p | 1A 50V 38p |
| 747C 78p | LM305 95p | TAD100 130p | 1A 100V 42p |
| 748C 78p | LM380 160p | TBA800 95p | 1A 200V 47p |
| AY-1-0212 5 50p | LM381 160p | TBA801 150p | 1A 400V 27p |
| AY-1-5051 1 15p | LH9900 5p | ZN414 95p | 1A 600V 70p |
| AY-5-1224 365p | MC124P 148p | | 3A 50V 38p |
| AY-5-3500 615p | MC1304 360p | | 3A 100V 43p |
| AY-5-3507 615p | MC1305 360p | | 3A 200V 55p |
| AY-5-4007 615p | MC1306 360p | | 3A 400V 74p |
| CA3018 72p | MC1310 320p | | 3A 600V 99p |
| CA3020 145p | MC1710CC 35p | | 5A 400V 90p |
| CA3035 135p | MFC4000S 54p | | 7A 400V 108p |
| CA3036 90p | MFC6040 82p | | C106B 37p |
| CA3048 50p | MLM309K 158p | | MCR101 29p |
| CA3048 220p | NE555 48p | | TIC44 29p |
| CA3075 150p | NE556DB 99p | | 2N4444 191p |
| CA3081 150p | NE565 304p | | |
| CA3089E 195p | NE562 315p | | |
| CA3090AQ 250p | NE567 249p | | |
| CA3123 140p | NE568 249p | | |
| LM300H 140p | SL403D 160p | | |
| LM301 42p | SL414A 160p | | |

| REGULATOR | | ZENER DIODES | |
|-----------------|-----------------|--------------|----------|
| 723C 45p | 7805 (TO3) 150p | 2V-33V 39p | 5V 48p |
| 7815 (TO3) 160p | 7815 (TO3) 160p | 10V 48p | 15V 48p |
| LM309K 185p | MVR12 144p | 20V 48p | 30V 48p |
| | | 40V 48p | 50V 48p |
| | | 60V 48p | 75V 48p |
| | | 100V 48p | 150V 48p |
| | | 200V 48p | 300V 48p |
| | | 400V 48p | 500V 48p |
| | | 600V 48p | 800V 48p |
| | | 1000V 48p | |

| DENCO COILS | | ENAMEL COPPER WIRE (2oz reel) | |
|-------------------------|-----|-------------------------------|-----|
| Miniature Dual purpose | | 16, 18, 20, 22 SWG | 32p |
| Rns. 1-5 B,Y,R,W | 60p | 24, 26, 28, 30 SWG | 39p |
| 6-7 B,Y,R | 58p | 32, 34, 36, 40 SWG | 48p |
| 1-5 Green | 65p | | |
| MAXI-Q Aerial Coil | | | |
| Range 2-T. Blue | 60p | | |
| Transistor Tuning coils | | | |
| Rng. 1-5 B,Y,R,W | 70p | | |
| IFT 13/14/15 65p each | | | |
| IFT 18/465 | 75p | | |
| TOC 1 | 70p | | |
| MW F.R. Aerial | 70p | | |

| OPTO ELECTRONICS | | ALUM. BOXES with lid | |
|-----------------------------------|------|----------------------|------|
| LED TIL 209 (red) with socket | 18p | 2 1/2 x 3 1/2 | 50p |
| LED Larger 0-2" diam. Red | 15p | 4 x 4 x 1 1/2 | 50p |
| 7 Seg Display MINITRON 3015F | 19p | 4 x 2 x 1 1/2 | 50p |
| 7 Seg Display MAN 3640 | 170p | 4 x 5 x 1 1/2 | 58p |
| OC P 7 40p ORP 12 58p 2N 5777 41p | | 4 x 2 x 3/2 | 30p |
| | | 3 x 2 x 1 1/2 | 44p |
| | | 6 x 4 x 2 1/2 | 78p |
| | | 7 x 5 x 2 1/2 | 84p |
| | | 8 x 6 x 3 | 106p |
| | | 10 x 7 x 3 | 122p |
| | | 10 x 4 x 3 1/2 | 110p |
| | | 12 x 5 x 3 1/2 | 120p |

ALL DEVICES BRAND NEW AND FULLY GUARANTEED. ORDERS DESPATCHED BY RETURN OF POST. TERMS OF BUSINESS: CASH/CHEQUE/P.O. OR BANKERS DRAFT WITH ORDER. GOVERNMENT AND EDUCATIONAL INSTITUTIONS OFFICIAL ORDERS ACCEPTED. TRADE AND EXPORT INQUIRY WELCOME. P & P ADD 20p TO ALL ORDERS UNDER £10.00. OVERSEAS ORDERS POSTAGE AT COST, AIR/SURFACE.

VAT Applicable to U.K. Customers only. All prices are exclusive of VAT. Please add 8% to devices marked * To the rest add 25%.
Send 15p postage for our comprehensive catalogue

| POLYESTER CAPACITORS: | | FEED THROUGH CAPACITORS | |
|---|--|--|----------------|
| Axial lead type. (Values are in µF). | | 250V: 0.01, 0.015, 0.022, 0.033 3p; 0.047, 0.068, 0.1 4p; 0.15 6p; 0.22, 0.33 7p; 0.47, 0.68 8p; 1.0, 1.5, 2.2, 3.3, 4.7, 6.8, 10, 15, 20, 22, 47, 68, 100, 12p. 40V 100, 6p | 1000PF/350V 8p |
| 400V: 0.001, 0.0012, 0.0015, 0.0018, 0.0022, 0.0033 3p; 0.0047, 0.0068, 0.01, 0.015, 0.022 4p; 0.033, 0.047, 0.068, 0.1, 0.15, 0.22, 7p; 0.33, 13p; 0.47, 17p; 160V: 0.1, 0.15, 4p; 0.22 5p; 0.33 6p; 0.47 9p; 0.68 13p; 1.0 18p. | | | |

| ELECTROLYTIC CAPACITORS: | | TANTALUM BEAD CAPACITORS | |
|---|--|---------------------------------|-------------------------------|
| Axial lead type (Values are in µF) | | 0.25W Log & 0.5W Linear values | 0.2, 0.47, 1.0, 2.2, 4.7, 6.8 |
| 63V: 0.47, 1.0, 1.5, 2.2, 3.3, 4.7, 6.8, 10, 15, 20, 22, 47, 68, 100, 12p. 40V 100, 6p | | 1KΩ-2MΩ single gang | 14p |
| 50V: 1000, 42p, 30V: 3500, 41p, 25V: 10, 68, 150, 6p; 220, 11p; 470, 13p; 680, 18p; 1000, 24p; 2200, 34p, 3000, 39p; 4700, 47p, 16V: 40, 125, 250, 6p, 18V: 1000, 1500, 18p, 10V: 4, 100, 5p; 540, 10p; 1000, 14p; 2200, 18p. | | 5KΩ-10KΩ single gang D/P switch | 32p |
| | | 2KΩ-2MΩ dual gang stereo | 45p |

| SLIDER POTENTIOMETERS | | PRESSET POTENTIOMETERS | |
|-----------------------------------|-----|----------------------------|----|
| 0-25W log and linear values | | 0-1W 50Ω-1MΩ Vertical only | 5p |
| 1KΩ-500KΩ single gang | 35p | 0-1W 50Ω-2MΩ Horizontal | 6p |
| 5KΩ-100KΩ Dual gang | 50p | 0-25W 1KΩ-2MΩ Vertical | 6p |
| KNObS for above Black or Silvered | 8p | | |

| QUALITY RESISTORS. ERIE MAKE | | JACKSONS VARIABLE CAPACITORS | |
|--|-------|------------------------------|---------------|
| Carbon, Miniature, High Stability, Low Noise | | Dielectric | 02-2x365 240p |
| POWER Tol. RANGE Val. 1-99 100+ | PRICE | 100pF | 80p |
| 0-25W 5% 2-2Ω-4-7M E24 1p 0-8p | | 300pF | 85p |
| 0-5W 5% 2-2Ω-4-7M E12 1p 0-8p | | 500pF | 98p |
| 1W 5% 2-2Ω-10M E12 2-5p 2p | | | |

| JACK PLUGS | | SOCKETS | | PANEL METERS | |
|-----------------|--------------|------------|--------------------|-----------------------|---------------------|
| Screened chrome | Plastic body | Open metal | Moulded with break | 60mm x 48mm x 35mm | require 1 1/2" hole |
| 10p | 8p | 8p | 8p | FULL SCALE | |
| 14p | 10p | 13p | 13p | ME 6 | 0-100µA |
| 19p | 13p | 15p | 15p | ME 7 | 0-1000µA |
| 32p | 18p | 15p | 20p | ME 9 | 0-1mA |
| | | | | ME 10 | 0-5mA |
| | | | | ME 11 | 0-10mA |
| | | | | ME 12 | 0-50mA |
| | | | | ME 13 | 0-100mA |
| | | | | ME 14 | 0-500mA |
| | | | | ME 15 | 0-1 amp |
| | | | | ME 16 | 0-50V DC |
| | | | | ME 17 | 0-300V AC |
| | | | | ME 18 | "S" Meter |
| | | | | ME 19 | "VU" Meter |
| | | | | Price £2-75 p & p 10p | |

| DIN 2PIN LOUDSPEAKER | | CO-AXIAL (TV) | |
|----------------------|--|---------------|--|
|----------------------|--|---------------|--|

IMPROVE PETROL CONSUMPTION

Fit the Brilliant
New P.E. Scorpio Mk II
"Dual Polarity"
Capacitive Discharge
Electronic Ignition
System



- ★ Genuine improvement in overall petrol consumption (independent report claims at least 8%—10%)
 - ★ Much easier cold weather starting, less strain on your battery
 - ★ Less use of choke—increases engine life
 - ★ Smoother running at lower revs—makes your four cylinder car feel like a six cylinder
- Together with the following 'Scorpio Mk II' plus features not previously available with other makes:—
- ★ Only one model used for both positive (+) and negative (—) earth vehicles—if you change your car, you can certainly transfer your 'Scorpio'.
 - ★ Retains your original contact breaker points, which last their mechanical life—no points burn
 - ★ Will drive electronic tachometers.

Send a stamped addressed envelope for our free interesting brochure, "Electronic Ignition—How it Works", containing circuit and itemised price list. Price for complete kit of parts, with easy to follow, comprehensive instructions, connecting wire, etc. ONLY £15.50, including V.A.T. and postage and packing. Ready made unit, fully tested, for immediate installation with easy to follow instructions, all leads, etc., ONLY £17.50, including V.A.T. and postage and packing.

THOUSANDS ALREADY IN USE—FULLY GUARANTEED.

ELECTRO SPARES, 288 ECCLESALL ROAD, SHEFFIELD S11 8PE
Tel: Sheffield (0742) 668888

Please allow 14 days minimum for delivery, for postal delays, cheque clearance, etc.

P.E. 'VARICAP' STEREO PUSH BUTTON F.M. TUNER



The P.E. 'Varicap' Stereo Tuner uses the latest Mullard modules for R.F. and I.F. circuits—highly sensitive and pre-aligned for ease of construction. This superb kit has everything to enable you to construct this highly sensitive F.M. Stereo Tuner, with instant push button station selection, self contained regulated

power supply, stereo decoder, etc. etc. Easy to construct, highest quality reproduction. Price only £34.50 including V.A.T. and postage and packing. Please send stamped addressed envelope for our free brochure on the Varicap, which gives performance figures, detailed description, etc., etc.

P.E. 'GEMINI' STEREO AMPLIFIER

Output genuine 30W R.M.S. per channel! Distortion 0.01% (Maximum)! Frequency response —3dB, 20Hz to 100 kHz into 8 ohms! Fully comprehensive inputs, disc, tape, MIC etc.!

Yes, we are still supplying all components for this superb Stereo Amplifier, since we have not yet found a better one!

Fully comprehensive constructional booklet available, containing full specification, performance graphs, step-by-step, assembly instructions, photographs, fault finding guide, etc. etc. Price 55 pence plus 9 pence postage and packing.

For itemised price list only please forward stamped addressed envelope.

INDEX TO ADVERTISERS

A. H. Supplies 418
Ambit International cover iv
Arrow Electronics 425
A. S. P. Ltd. 380
Astro Electronics Ltd. 360

Bamber, B. 422
Barrie Electronics Ltd. 350
Bently Acoustic Ltd. 346
Beta Devices 426
B.H. Component Factors Ltd. 352
Bib Hi-Fi Ltd. 354
Bi-Pak Ltd. 362-363
Bi-Pre-Pak Ltd. 405
Birkett, J. 346
Boffin Projects 429
British Institute of Engineering Technology 346, 407, 424
British National Radio & Electronics School 353, 375, 420
J. Bull (Electrical) Ltd. 361
Bush & Meissner 358

C. Caranna 426
Central Imports & Exports 352
Chromasonic Electronics cover ii
Codar 422
Colomar (Electronics) Ltd. 354
Crescent Radio Ltd. 423
Crofton Electronics 358

D. E.W. Ltd. 429
Dick Smith Electronics Ltd. 427
Dziudas, M. 350

Eldon Electronics 428
Electroni-Kit 380
Electronic Brokers 428
Electronics Design Associates 428, 419

Electronic Mail Order Ltd. 360
Electrospares 431
Electrovalve Ltd. 384
Everest Instruments Ltd. 358

Flairline Supplies 380
Foresight Electronics 428-429
Foulsham, W. 424

Galleon Trading 426
Goldring Ltd. 353
Greenbank Electronics 420
Greenweld Electronics 384

H.A.C. Short-Wave Supplies 420
Heath (Gloucester) Ltd. 407
Henry's Radio Ltd. 412
H.M. Electronics 429
Home Radio Ltd. 379

I.L.P. Electronics Ltd. 421
Imperial Trading 427

Jaybee Electronics 428

Kensington Supplies 427

Lasky's Ltd. 415-416-417
Lewis Radio 353
London Computer Operators Training Centre 427
Lowe Electronics 425

Maplin Electronic Supplies cover iii
Marco Trading 426
Microelectronics 429
Marshall, A. & Son 418
Minikits Electronics 429

Newmart Electronics 351
N.S.E. Kits 422

Partridge Electronics Ltd. 408
Photo-Tech (Europe) 428

Radio Book Services 427
Radio Component Specialists 355
Radio Exchange Ltd. 383
Radio Society of Great Britain 384
Rivlin Instruments Ltd. 424
R.S.C. (Hi-Fi) Centre Ltd. 347
R.S.T. Valve Mail Order Co. 411
R & TV Components Ltd. 356-357

Salop Electronics 429
Saxon Entertainments Ltd. 359
Scientific Wire Company, The 428
S.I.G.A. Electronics Ltd. 360
Simtech Engineering Ltd. 427
Sintel 350
Stobbs, R. A. 426
Studio Electronics 419
Surpletronics 358
Swanley Electronics 376

Technomatic Ltd. 432
Teleradio Electronics 428-429
Texas Instruments 427
Trampus Electronics Ltd. 412
T.T.S. Ltd. 408
T.U.A.C. 348-349

Watford Electronics 430
Web Europa 352
West London Direct Supplies 420
Wilmslow Audio 376

Xeroza Radio 419

Z & I Aero Services 432

Head Office and Warehouse
 44A WESTBOURNE GROVE
 LONDON W2 5SF
 Tel: 727 5641/2/3

Z & I AERO SERVICES LTD.

Retail Shop
 85 TOTTENHAM COURT ROAD
 LONDON W1
 Tel: 580 8403
 Open all day Saturday

Please send all correspondence and Mail-Orders to Head Office

| FULLY GUARANTEED | |
|------------------|--------------|
| 0A2 | 0-45 6AJS |
| 0A3 | 0-55 6AK5 |
| 0B2 | 0-45 6AK6 |
| 0C3 | 0-45 6AL5 |
| 0D3 | 0-45 6AM6 |
| 1A3 | 0-55 6AQ5 |
| 1A7 | 0-60 6AR5 |
| 1AD4 | 1-20 6AS6 |
| 1B3GT | 0-55 6AS11 |
| 1R4 | 0-70 6ALS |
| 1R5 | 0-55 6A18A |
| 1S4 | 0-40 6AU6GTA |
| 1S5 | 0-55 6B1 |
| 1T4 | 0-40 6AU5GT |
| 1U4 | 0-70 6AV6 |
| 1U5 | 0-60 6AV6GT |
| 1V2 | 0-70 6AV6 |
| 1XB7 | 0-75 6AW8A |
| 2D21 | 0-55 6AX5GT |
| 2X2 | 0-75 6BA4 |
| 3A3 | 0-80 6B8 |
| 3A4 | 0-60 6BC8 |
| 3A5 | 1-00 6BE6 |
| 3A8GT | 0-85 6B7 |
| 3B4 | 0-60 6BF6 |
| 3D6 | 0-40 6BH6 |
| 3Q4 | 0-75 6BJ6 |
| 3Q5 | 0-60 6BK4B |
| 3V4 | 0-50 6BK7B |
| 3V4 | 0-80 6BN6 |
| 3V4 | 1-00 6BN8 |
| 4G4G | 0-55 6BT7 |
| 5R8 | 0-75 6BR7 |
| 5V4G | 0-65 6BR8 |
| 5W4GT | 0-65 6BS7 |
| 5X4G | 0-80 6BU8A |
| 5Y2GT | 0-65 6BV6 |
| 6Z4G | 0-60 6B17 |
| 6/30L2 | 0-90 6BX7GT |
| 6BA4 | 0-50 6B26 |
| 6AC7 | 0-60 6B27 |
| 6AG5 | 0-35 6CA |
| 6AG7 | 0-60 6C5GT |
| 6AH6 | 0-70 6C85A |
| 65G7 | 0-50 6CG6 |
| 65G7 | 0-50 6CD6GA |
| 65G7 | 0-50 6CE7 |
| 65G7 | 0-75 6CFL |
| 65G7 | 0-60 6CL8A |
| 65G7 | 0-85 6CS7 |
| 65G7 | 1-00 6CU5 |
| 65G7 | 1-00 6CX8 |
| 65G7 | 1-00 6CY5 |
| 65G7 | 0-60 6D1 |
| 65G7 | 0-60 6DK6 |
| 65G7 | 1-00 6D6B |
| 65G7 | 0-80 6DT6A |
| 65G7 | 0-80 6DT8 |
| 65G7 | 0-80 6E8 |
| 65G7 | 0-75 6E85 |
| 65G7 | 0-80 6E86 |
| 65G7 | 0-80 6E87 |
| 65G7 | 0-80 6E88 |
| 65G7 | 0-80 6E89 |
| 65G7 | 0-80 6E90 |
| 65G7 | 0-80 6E91 |
| 65G7 | 0-80 6E92 |
| 65G7 | 0-80 6E93 |
| 65G7 | 0-80 6E94 |
| 65G7 | 0-80 6E95 |
| 65G7 | 0-80 6E96 |
| 65G7 | 0-80 6E97 |
| 65G7 | 0-80 6E98 |
| 65G7 | 0-80 6E99 |
| 65G7 | 0-80 6E00 |
| 65G7 | 0-80 6E01 |
| 65G7 | 0-80 6E02 |
| 65G7 | 0-80 6E03 |
| 65G7 | 0-80 6E04 |
| 65G7 | 0-80 6E05 |
| 65G7 | 0-80 6E06 |
| 65G7 | 0-80 6E07 |
| 65G7 | 0-80 6E08 |
| 65G7 | 0-80 6E09 |
| 65G7 | 0-80 6E10 |
| 65G7 | 0-80 6E11 |
| 65G7 | 0-80 6E12 |
| 65G7 | 0-80 6E99 |
| 65G7 | 0-80 6E00 |
| 65G7 | 0-80 6E01 |
| 65G7 | 0-80 6E02 |
| 65G7 | 0-80 6E03 |
| 65G7 | 0-80 6E04 |
| 65G7 | 0-80 6E05 |
| 65G7 | 0-80 6E06 |
| 65G7 | 0-80 6E07 |
| 65G7 | 0-80 6E08 |
| 65G7 | 0-80 6E09 |
| 65G7 | 0-80 6E10 |
| 65G7 | 0-80 6E11 |
| 65G7 | 0-80 6E12 |
| 65G7 | 0-80 6E99 |
| 65G7 | 0-80 6E00 |
| 65G7 | 0-80 6E01 |
| 65G7 | 0-80 6E02 |
| 65G7 | 0-80 6E03 |
| 65G7 | 0-80 6E04 |
| 65G7 | 0-80 6E05 |
| 65G7 | 0-80 6E06 |
| 65G7 | 0-80 6E07 |
| 65G7 | 0-80 6E08 |
| 65G7 | 0-80 6E09 |
| 65G7 | 0-80 6E10 |
| 65G7 | 0-80 6E11 |
| 65G7 | 0-80 6E12 |
| 65G7 | 0-80 6E99 |
| 65G7 | 0-80 6E00 |
| 65G7 | 0-80 6E01 |
| 65G7 | 0-80 6E02 |
| 65G7 | 0-80 6E03 |
| 65G7 | 0-80 6E04 |
| 65G7 | 0-80 6E05 |
| 65G7 | 0-80 6E06 |
| 65G7 | 0-80 6E07 |
| 65G7 | 0-80 6E08 |
| 65G7 | 0-80 6E09 |
| 65G7 | 0-80 6E10 |
| 65G7 | 0-80 6E11 |
| 65G7 | 0-80 6E12 |
| 65G7 | 0-80 6E13 |
| 65G7 | 0-80 6E14 |
| 65G7 | 0-80 6E15 |
| 65G7 | 0-80 6E16 |
| 65G7 | 0-80 6E17 |
| 65G7 | 0-80 6E18 |
| 65G7 | 0-80 6E19 |
| 65G7 | 0-80 6E20 |
| 65G7 | 0-80 6E21 |
| 65G7 | 0-80 6E22 |
| 65G7 | 0-80 6E23 |
| 65G7 | 0-80 6E24 |
| 65G7 | 0-80 6E25 |
| 65G7 | 0-80 6E26 |
| 65G7 | 0-80 6E27 |
| 65G7 | 0-80 6E28 |
| 65G7 | 0-80 6E29 |
| 65G7 | 0-80 6E30 |
| 65G7 | 0-80 6E31 |
| 65G7 | 0-80 6E32 |
| 65G7 | 0-80 6E33 |
| 65G7 | 0-80 6E34 |
| 65G7 | 0-80 6E35 |
| 65G7 | 0-80 6E36 |
| 65G7 | 0-80 6E37 |
| 65G7 | 0-80 6E38 |
| 65G7 | 0-80 6E39 |
| 65G7 | 0-80 6E40 |
| 65G7 | 0-80 6E41 |
| 65G7 | 0-80 6E42 |
| 65G7 | 0-80 6E43 |
| 65G7 | 0-80 6E44 |
| 65G7 | 0-80 6E45 |
| 65G7 | 0-80 6E46 |
| 65G7 | 0-80 6E47 |
| 65G7 | 0-80 6E48 |
| 65G7 | 0-80 6E49 |
| 65G7 | 0-80 6E50 |
| 65G7 | 0-80 6E51 |
| 65G7 | 0-80 6E52 |
| 65G7 | 0-80 6E53 |
| 65G7 | 0-80 6E54 |
| 65G7 | 0-80 6E55 |
| 65G7 | 0-80 6E56 |
| 65G7 | 0-80 6E57 |
| 65G7 | 0-80 6E58 |
| 65G7 | |

More than just a catalogue!

PROJECTS FOR YOU TO BUILD

4-digit clock, 6-digit clock, 10W high quality power amp., High quality stereo pre-amp., Stereo Tuner, F.M. Stereo decoder, etc., etc.

CIRCUITS . . . Frequency Doublers, Oscillators, Timers, Voltmeters, Power Supplies, Amplifiers, Capacitance Multiplier, etc., etc. . . .

Full details and pictures of our wide range of components, e.g. capacitors, cases, knobs, veroboards, edge connectors, plugs and sockets, lamps and lampholders, audio leads, adaptor plugs, rotary and slide potentiometers, presets, relays, resistors (even 1% types!), switches, interlocking pushbutton switches, pot cores, transformers, cable and wire, panel meters, nuts and bolts, tools, organ components, keyboards, L.E.D.'s, 7-segment displays, heatsinks, transistors, diodes, integrated circuits, etc., etc., etc. . . .


Really good value for money at just 40p.




The 3600 SYNTHESISER

The 3600 synthesiser includes the most popular features of the 4600 model, but is simpler. Faster to operate, it has a switch patching system rather than the matrix patchboard of the larger unit and is particularly suitable for live performance and portable use.

Please send S.A.E. for our price list.

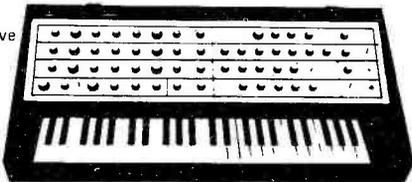


The 4600 SYNTHESISER

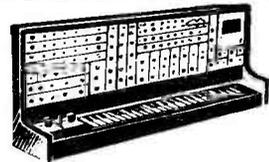

We stock all the parts for this brilliantly designed synthesiser, including all the PCB's, metalwork and a drilled and printed front panel, giving a superb professional finish. Opinions of authority agree the ETI International Synthesiser is technically superior to most of today's models. Complete construction details available shortly in our booklet price £1.50, or S.A.E. please for specification

GRAPHIC EQUALIZER

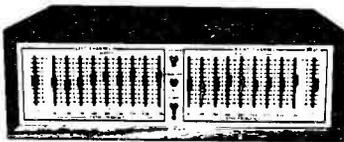A really superior high quality stereo graphic equaliser as described in Jan. 1975 issue of ETI. We stock all parts (except woodwork) including all the metal work drilled and printed as required to suit our components and PCB's. S.A.E. for price list or complete reprint of article - price 15p.



ELECTRONIC ORGAN

Build yourself an exciting Electronic Organ. Our leaflet MESS1, price 15p, deals with the basic theory of electronic organs and describes the construction of a simple 49-note instrument with a single keyboard and a limited number of stops. Leaflet MESS2, price 15p, describes the extension of the organ to two keyboards each with five voices and the extension by an octave of the organ's range. Solid-state switching and new footages along with a pedal board and a further extension of the organ's range are shown in leaflet MESS3, also priced at 15p.



NO MORE DOUBTS ABOUT PRICES

Now our prices are GUARANTEED (changes in VAT excluded) for two month periods. We'll tell you about price changes in advance for just 30p a year (refunded on purchases). If you already have our catalogue send us an s.a.e. and we'll send you our latest list of GUARANTEED prices. Send us 30p and we'll put you on our mailing list - you'll receive immediately our latest price list then every two months from the starting date shown on that list you'll receive details of our prices for the next GUARANTEED period before the prices are implemented! - plus details of any new lines, special offers, interesting projects - and coupons to spend on components to repay your 30p

NOTE: The price list is based on the Order Codes shown in our catalogue so an investment in our super catalogue is an essential first step.

Call in at our shop, 284 London Road, Westcliff-on-Sea, Essex. Please address all mail to


MAPLIN ELECTRONIC SUPPLIES
P.O. Box 3 Rayleigh Essex SS6 8LR.

I enclose Cheque/P.O. value _____ PW
For copy/copies of your Catalogue
Name _____
Address _____

MAPLIN ELECTRONIC SUPPLIES P.O. Box 3 Rayleigh Essex SS6 8LR

Illustrated below are some of the products that TOKO make for wireless manufacture. These and other TOKO products are available from Ambit, together with many linear and discrete semiconductor devices specializing in radio and audio applications. Full catalogue 40p.

wireless tecknowledgy from TOKO

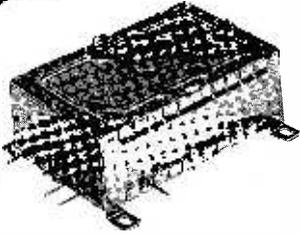

Varicap FM tunerhead:

The EF5603 represents the top of the range in TOKO FM tuner modules. With 5 double varicap tuned circuits, and dg MOSFET RF stage, the performance is really excellent. (12v supply) 1-24 £9.05 each



Coils for VHF RX/TX's

S18 are fully moulded coils, complete with cores. A wide range of custom types with up to two taps is available - standard types for VHF are available ES. 1-24 18p each




Ceramic IF filters

Similar to Murata and Vernitron types, these ceramic filters are the easiest way to achieve FM IF selectivity. Two per set are required. 1-24 40p each



6 pole linear phase filter

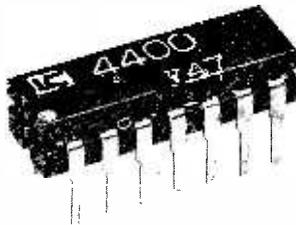Centered on 10.7MHz, this linear phase filter offers all the necessary selectivity for the construction of a Hi Fi FM stereo tuner. 1-24 £2.25 each



ICs for IF, decoder

The popular 1310, and 3089 types for FM MPX. 1310/4400 1-24 2.20 each 3089/4402 1-24 1.94 each



19 & 38 kHz notch filter

BLR3107 filters will remove the interference that causes annoyance when listening to or recording from MPX transmissions on FM. 1-24 £1.60ea




7BA Low cost RF choke

Miniature chokes 1uH to 1mH. Useful for all low power decoupling applications in RF circuits, logic circuits, filter circuits etc. Stock values 1, 4.7 and multiples through to 1mH. Custom orders 1000 min. for other values 1-24 15p ea



10K coils for HF/VHF

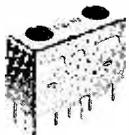The ideal coil for all FM and TV IF applications. Excellent stability - available from a very broad 'shelf stock' range, and also to exact custom specs., where a min. of 1000 pcs applies. With or without an internal capacitor. 1-24 30p ea



CFT ceramic series AM IF filters

Low cost filters for use with IC or discrete circuits. Each unit includes an input/output matching transformer. For 455 and 470 kHz BW 6kHz. CFT 1-24 50p each, or slightly larger with higher Q: CFU050 (470 kHz only) 1-24 55p each.



MFH mechanical 455kHz IF filters

Bandwidth 4 or 7 kHz, for IC and discrete IF strips. Includes input/output IFT for matching 5k/800 ohms. 1-24 £1.45 each



7P min MF/HF coils

Only 7mm square base area makes the 7P ideal for all miniature receiver circuits. Available as IFs and osc. for AM/FM. (AM IFTs are available ES.) 1-24 30p each



10E coils for AM/FM

The 10E is available in the broadest range of stock types of all TOKO coils, covering applications in MF/HF radio and FM IFTs. Base area 10mm square. 1-24 27p each

Please address all enquiries and orders for 1000 pcs or less to the distributor, AMBIT international.

AMBIT international
37 High Street
Brentwood
Essex, CM14 4RH
tel 216029 tlx 995194

Please note TOKO UK have moved to larger premises at:

Ward Royal Parade
Alma Road
Windsor, Berks. SL4 3HR
tel 54057 tlx 848095

Terms: Min CWO £1.00, VAT extra
Post 20p per order (CWO)
Min invoice £7.50 pp 50p.