
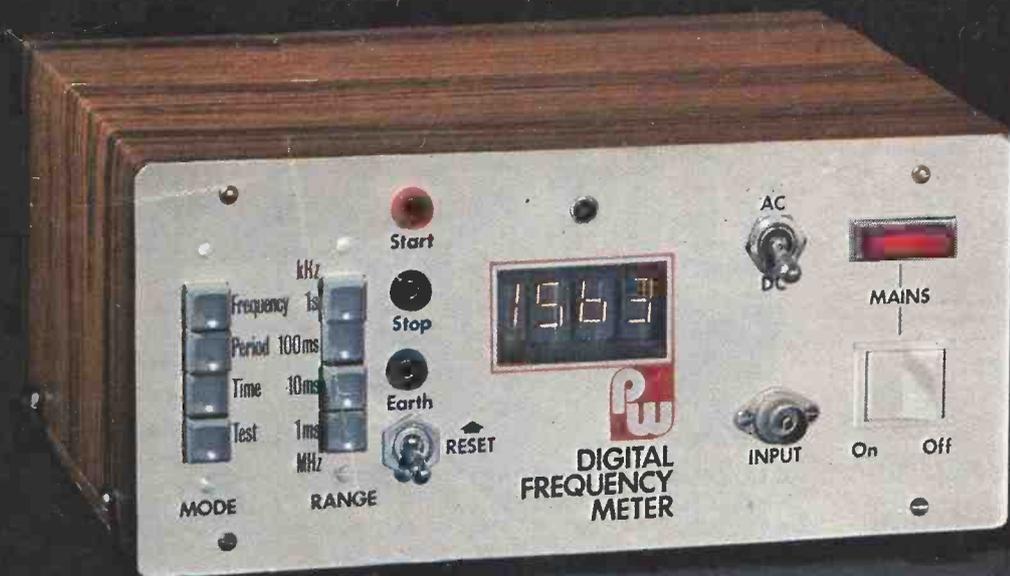


PRACTICAL WIRELESS

JUNE
1976

35p

Pw Digital Frequency Meter

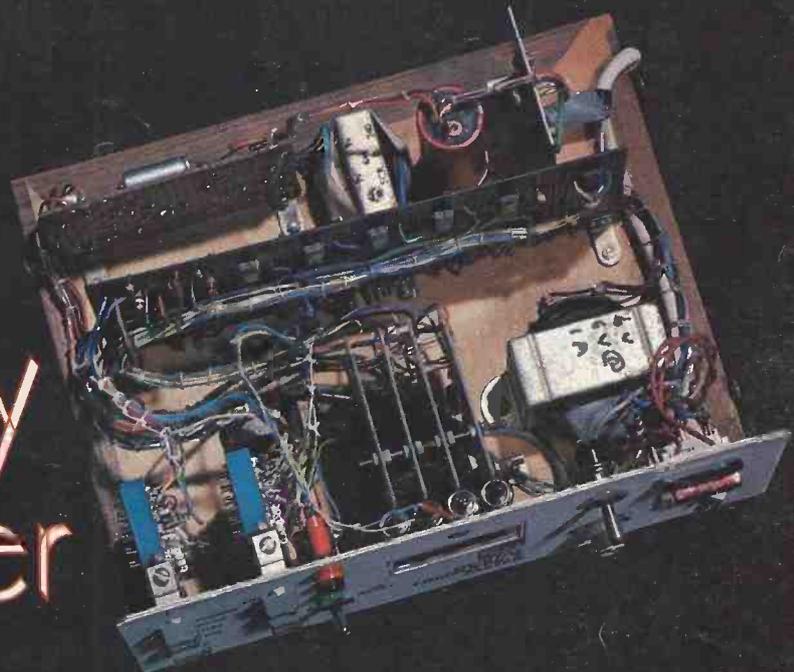

ALSO: TALKING TRANSISTORS
RECEIVER CALIBRATION AID
FAULT-FINDING GUIDE Continued



TRATIPUS ELECTRONICS LTD

58-60 GROVE RD.,
WINDSOR, BERKS.
SL4 1HS.
TEL. 54525.

ADD 8% VAT TO PRICES MARKED *
ADD 33% VAT TO ALL OTHER PRICES
ON 30 CURRENT VAT LEGISLATION.
SEND C.W.D. (EXCEPT GOV'T DEPT)
POST & PACKING 20P FOR THE UK.
BARCLAYCARD ACCESS BY POST
OR 45 MIN ON TELEPHONE ORDERS
CATALOGUE LIST FREE SEND 54P
MONEY BACK IF NOT SATISFIED.

YOU WON'T BELIEVE OUR PRICES


FAST FAST SERVICE

NORMALLY 24 HOURS
ON EX STOCK ITEMS.

QUALITY PRODUCT

FULL SPEC. DEVICES,
NO REMARKS REJECTS,
OR FLOORSWEEPINGS.

ADD VAT
TO PRICES

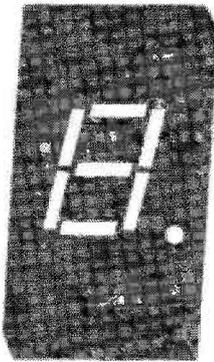

OPTO ELECTRONICS

ALL FULL SPECIFICATION LED
DL707 LITRONIX COM ANODE &
DL704 LITRONIX COM CATHODE
0.3" 0-9 & DEC POINT 89p ea *
DL747 JUMBO DISPLAY 0.6"
LED 0-9 DP.COM ANODE £1.25 *
3015F FILAMENT DISPLAY £1.25 *
DISCO ETC STROBE TUBE 55. ea *

RED LEDS 1/2"

209 STYLE OR 0.2" NO CLIP 11p *
TIL209 OR 0.2" RED & CLIP 13p *
GREEN LED LARGE OR SMALL 22p *
ORANGE LARGE OR SMALL 22p *
ORP12 57p * 2N5777 33p *
TCM12 IC PHOTODETECTOR 81p *

CROS LOGIC

NEW MOTOROLA

CD4000	15p *	CD4028	73p *
CD4001	16p *	CD4046	£1 *
CD4002	16p *	CD4077	73p *
CD4009	45p *	CD4049	45p *
CD4011	17p *	CD4054	94p *
CD4013	45p *	CD4055	£1 *
CD4016	45p *	CD4060	90p *
CD4017	82p *	CD4071	17p *
CD4018	82p *	CD4081	17p *
CD4022	77p *	CD4510	£1.19 *
CD4023	16p *	CD4511	£1.90 *
CD4024	63p *	CD4528	£1.10 *
CD4027	45p *	CD4558	£2.35 *

DIGITAL CLOCKS MM5314 £3.39*

MM5316 ALARM £5+MM5311 £5.00*

AY51224 4DIGIT £3.49+PCB £1.*

LED DISPLAY PCB 4DIGIT 75p *

vero

36PINS 28p*FACE CUTTER49p*

COPPERCLAD 0.1 PITCH VERO

24"x5" 32p * 24"x31" 29p *

31"x5" 37p * 31"x31" 32p *

31"x17" £1.70 *

31"x17" PLAIN 0.1" £1.06 *

DIL BREADBOARD 6x4" £2 *

DALO 69P pen

DALO ETCH RESIST PEN 69p *

FEC ETCH PAK 500gm 89p *

6x4" COPPER BOARD 50p *

PCB KIT 3 ITEMS £2 *

CASSETTE MECHANISM

FEW AVAILABLE TOP LOAD £15

TELEPHONE 54525



7400 series TTL IC's

7400N	9p *	7450/3/4	12p *	7491	60p *	74155	65p *
7401	10p *	7460	12p *	7492	43p *	74157	90p *
7402/3	11p *	7470	26p *	7493	38p *	74160/1	90p *
7404	13p *	7472	22p *	7495	58p *	74162/3	95p *
7405/6/7	25p *	7473/3	26p *	7496	68p *	74164	£1.20
7408/9/10	9p *	7474	25p *	74100	£1 *	74165	£1.20
7411/12	20p *	7475	44p *	74107	30p *	74175	95p *
7413	26p *	7476	28p *	74120	£1 *	74180	£1 *
7417	27p *	7480	40p *	74121	26p *	74181	£2 *
7420/27	26p *	7481	35p *	74122	42p *	74185	£3 *
7430/32	16p *	7482	72p *	74123	58p *	74190	£1.40 *
7440	12p *	7483	80p *	74141	64p *	74193	£1.10 *
7441	64p *	7485	£1.20 *	74143	£2 *	74195	75p *
7442	59p *	7486	33p *	74147	£2 *	74196	£1 *
7445	75p *	7489	£2.70 *	74151	65p *	74197	£1 *
7447	67p *	7490	37p *	74154	£1.30 *	74198/9	£2 *



AUDIBLE WARNING BLEEPER

12VOLT 35mA, SPARKLESS £1 *

TGS GAS DETECTORS £2 ea *

LOGIC PROBE FOR TTL etc £5 *

TRANSISTOR TESTER

TTC TESTS ALPHA, BETA Ico
NPN/PNP & DIODES NOW £13 *

C1000 MULTIMETER £3.49 *

BENCH POWER SUPPLY 1076

3-12V 1A ONLY £3.99 *

ALL ANTEX SOLDERING IRONS

CAPACITORS

CERAMIC 22pF to 0.1 uf 50V 5p.

ELECTROLYTIC IN 10, 25 & 50V.

2UF/10V, 10, 50, & 100uf 25V

& 10V 7p ea. 50VOLT 10p ea.

1000 uf 25V 18p. 200/500uf 9p.

POTENTIOMETERS

LIN OR LOG 2, 2K to 1 MEG, 16p

PRESETS 50P, RESISTORS 1p, ea 1W

HEATSINKS T05/18 7p. *T03 15p *

TV4 PLASTIC POWER 16p *

T03 EXTRUDED 4" FINNED 39p *

DIN PLUGS ALL 12p. SOCKETS 9p.

ALI CASES AB5/AB7 50p * AB13 69p *

AB13 69p * AB9 59p * AB12 40p *

TRANSFORMERS 100mA 6, 9 or 12V 89p *

1A/1A 6/12 or 12/24 £2 ea *

cassettes

LOW NOISE NOT REJECTS.

C60 33p ea. TEN FOR £2.70

C90 42p ea. TEN FOR £3.65

DIODES

0A81 & 0A91 GERMANIUM 5p.

1N4001 1A50V & 1N4002 5p *

1N4004 6p * 1N4007 5p *

1N4148 & 1N914 SILICON 4p.

ZENERS BZY88 400W 9p.

ZENERS 1W 17P, 211maoe11

BRIDGE RECTIFIER 1A50 18p

1A400V 25p. 4A100V 45p

SCR's TRIACS

SCR'S TAG1/400 1A400V 40c.

1A50V 25p*1A 600V 65p

C106D 4A400V SCR-ONLY

TRIAC SC146D 10A 400L

10A 400V Int.Diac £1.25*

16A 400V DISCO TRM AC £1.75*

16A 400V Int.Diac £2.*

DIACS: BR100 25p *

BULK OFFERS PER 1000ft each.

1N4001 £2.50 * 1N4004 £3.50 *

AC128 £10 AC176 £12 *

BC107 £6.80 * BC108 £6.80 *

BC109 £7.00 * BC155 £27 *

NE555 £37 * 741C(8) £18 *

BARGAIN PAKS

£1 ea. Full spec.

PAK A 10 RED LEDS our choice £1 *

PAK B 5 741C OP AMP 8 PIN £1 *

PAK C 4 2N3055 £1 * D 12 BC109 £1 *

PAK E 10 BC182 £1 * F 11 2N3704 £1 *

PAK G 8 BFY51 £1 * H 9 2N5199 £1 *

PAK J 9 2N3053 £1 * K 40 1N914 £1 *

NEW PAK M 4 PLASTIC 3055 90W £1 *

OIL sockets

TOP QUALITY NYLON

SOCKETS, HALF PRICE

8, 14, OR 16 PIN 12p *

SOLDBERGON PINS:

100 65p * 1000 £3.50

SLIDER CLEARANCE WHILE

STOCKS LAST ALL 10p ea.

PRACTICAL WIRELESS

VOL. 52 NO. 2

ISSUE 832

JUNE 1976

BRITAIN'S PREMIER MAGAZINE FOR THE DO-IT-YOURSELF RADIO AND ELECTRONICS CONSTRUCTOR

EDITOR

Lionel E. Howes, G3AYA

ASSISTANT EDITOR

Eric Dowdeswell, G4AR

ART EDITOR Peter Metall

TECHNICAL EDITOR

Terry Carter

PRODUCTION & NEWS EDITOR

Colin Riches

TECHNICAL SUB-EDITOR

Bill Tull

TECHNICAL ARTIST

Alan Martin

SECRETARIAL Karen O'Neil

Jill Austin

ADVERTS MANAGER

01-261 6275 Roy Smith

CLASSIFIED ADVERTS

01-261 5762 Colin R. Brown

Advertisement correspondence and enquiries to the Advertisement Manager, Roy Smith, Practical Wireless, Kings Reach Tower, Stamford Street, London, SE1 9LS

Published by IPC Magazines Ltd., Fleetway House, Farringdon Street, London EC4A 4AD. Tel. 01-634 4444

BINDERS

Binders (£2.10 from May 1st) and indexes 45p (inc. VAT) can be supplied by the Post Sales Department, IPC Magazines Ltd., Lavington House, 25 Lavington Street, London, SE1 0PF.

BACK NUMBERS

We regret that we are unable to supply back numbers of Practical Wireless. Readers are recommended to enquire at a public library to see copies. Requests for specific back numbers of Practical Wireless and Television can be published in our CQ Column.

COPYRIGHT AND QUERIES

© IPC Magazines Limited 1976. Copyright in all drawings, photographs and articles published in "Practical Wireless" is fully protected and reproduction or imitation in whole or in part is expressly forbidden. All reasonable precautions are taken by "Practical Wireless" to ensure that the advice and data given to readers are reliable. We cannot, however, guarantee it and we cannot accept legal responsibility for it. Prices are those current as we go to press.

We regret that we cannot answer technical queries by telephone nor can we provide information or advice on manufacturers' products other than that given in the magazine. We will endeavour to assist readers who have queries relating to articles published but we cannot offer advice on modifications to our published designs. All correspondents expecting a reply should enclose a stamped addressed envelope.

Practical Wireless, June 1976

● NEWS & COMMENT

- 120 NEWS . . . NEWS . . . NEWS . . .
- 128 KINDLY NOTE—notes on published articles
- 142 P.W. READERS' PCB SERVICE
- 143 NEXT MONTH IN PRACTICAL WIRELESS—see what's in store!
- 158 TELEVISION—contents of our 'sister' magazine
- 160 PRODUCTION LINES—news on products of interest—*Colin Riches*
- 165 HOTLINES on recent developments—*Ginsberg*
- 169 ON THE AIR—Amateur Bands—*Eric Dowdeswell, G4AR*
Broadcast Bands SW—*Derek Bell*
Broadcast Bands MW—*Charles Molloy*
- 174 NEW BOOKS—read all about it!

● CONSTRUCTIONAL

- 122 RHYTHM GENERATOR, Part 2—*A. S. Webb, B.Sc.*
- 138 RECEIVER CALIBRATION AID—*F. G. Rayer*
- 144 DIGITAL FREQUENCY METER, Part 1—*T. J. Johnson*

● OTHER FEATURES

- 129 TALKING TRANSISTORS—*P. Matthews*
- 137 TECHNICROSS—solution to Puzzle 13
- 151 P.W. FAULT-FINDING GUIDE, continued—*Les Lawry-Johns*
- 157 SPECIAL PRODUCT REPORT—Sinclair 'Black Watch' Kit
- 166 GOING BACK—invention of the telephone—*Colin Riches*

Sinclair SCIENTIFIC KIT

ONLY
£6.50
+50p p&p



LASKYS now offer this Sinclair Scientific Calculator for a fraction of the original cost. All parts are supplied - all you need provide is a soldering iron and a pair of cutters, complete step-by-step instructions. Assembly time is about 3 hours. The Sinclair Scientific performs logs, trigs and arithmetic at the touch of a button.

FEATURES OF THE SINCLAIR SCIENTIFIC

Functions summary Four arithmetic functions: (+, -, ×, ÷). Sin and Arcsin. Cos and Arccos. Tan and Arctan. Automatic squaring. Automatic doubling. Log10 and Antilog10, giving quick access to xy (including square and other roots). Scientific notation. Display shows 5-digit mantissa and 2-digit exponent, both signable. 200 decade range. —9.9999 x 10⁻⁹⁹ to 9.9999 x 10⁹⁹. Post-fixed operators. Post-fixed operators (reverse Polish notation): allow chain calculations of unlimited length. 'Upper and lower case' operation. Basic arithmetic keys each have two extra functions. Pocket-sized. 4½" x 2" x ½". Weight: 4oz. Trim-fit plastic carrying case.



LONDON 481 Oxford Street, W1. 01-493 8641
10 Tottenham Court Road, W1. 01-637 2232
33 Tottenham Court Road, W1. 01-636 2626
42 Tottenham Court Road, W1. 01-636 0845
257 Tottenham Court Road, W1. 01-580 0670
3 Lisle Street, WC2. 01-437 8204
118 Edgware Road, W2. 01-723 9785
133 Edgware Road, W2. 01-723 8211
311 Edgware Road, W2. 01-262 0387
346 Edgware Road, W2. 01-723 4453
382 Edgware Road, W2. 01-723 4194
109 Fleet Street, EC4. 01-353 5812
152 Fleet Street, EC4. 01-353 2833
BIRMINGHAM 116 Corporation St. 236 3503
BRENT CROSS Unit D19 Brent Cross Shopping Centre. Now open
BRISTOL 16-18 20 Penn Street. 20421
CHATHAM The Pentagon Centre. 407104

CROYDON 1046 Whitgift Centre. 681 3027
COLCHESTER Unit A5 Lion Walk Shopping Centre, opening FEBRUARY
DARTFORD The Arndale Centre. 32 73481
KINGSTON 38/40 Eden Street. 546 1271
LEICESTER 45 Market Place. 537678
LEWISHAM 29 Riverside, The Centre. 318 2297
NORTHAMPTON 78 Abington St. 35783
NOTTINGHAM 5 7 Lower Parliament St. 48987
OXFORD 16 Westgate Centre. 722870
READING 6 Friars Walk, Friar St. 595459
RICHMOND 32 Hill Street. 948 1441
ROMFORD 86 South Street. 20218
SOUTHEND 205/206 Churchill West. 612241
SLOUGH 65 Queensmere Centre. 7524401
SWINDON 12 Brunel Plaza
TUNBRIDGE WELLS 53/57 Camden Rd. 23242
WOLVERHAMPTON 30 Wulfrun Way. 23384



To LASKYS CUSTOMER SERVICES DIVISION (Dept. J2)
Audiotronic House, The Hyde, London NW9 6JJ. Tel: 01-200 1321

Please send me . . . Sinclair Scientific Calculator Kits at £6.50 plus 50p p&p

NAME _____
ADDRESS _____

SIGNATURE _____
TOTAL PURCHASE PRICE _____ (inc. p/p & Ins.)

Please send me FREE Hi-Fi catalogue price list
I enclose cheque postal order money order
I wish to pay by Barclaycard/Access/Diners Club and my number is _____

Registered in England No. 347947 at Lower Grosvenor Place, London SW1 0EX



DISOMATOR Mk. 2 POWER DISCO CONSOLE with integral Power Amp. Twin Jack output sockets. **TWIN BEB** turntables. Cartridges with Diamond Styl. Separate volume controls each t/table. **Full Headphone Monitoring Facilities.** PAIR OF 50 WATT SPEAKERS: Black Vynide covered cabinets approx. size 18" x 18" x 8". PAIR OF HI-FI HEADPHONES and MATCHING 'MIKE': STEREO VERSION £209-95
PACKAGE PRICE (including VAT) Carr. £4.
OR DEPOSIT £31-99 and 12 mthly. payments £18-48 (Total £181-75) **£159.95**

FANE DISCO 60C SPEAKER UNITS
Fabulous 'Specialist' range Speaker in heavy Vynide covered cab. fitted protective cover also. **£45 ea. PRICES INC. VAT**
A pair can be supplied in lieu of RSC Speakers with the above system for £25 extra.


MOBILE DISCO CONSOLE £59-95 Carr. £3
MIC. JACK. PHONE JACK. MONITOR VOL. CONTROL. MONITOR SELECTOR DECK (1) Vol. Control. DECK (2) Vol. control. Mic. Vol. Control. Treble Control. Bass Control. ON/OFF Switch. Neon Indicator. Twin Turntables. Terms: Dep. £7-95 and 18 fortnightly payments. £33. Total £87-89.



40W DISCO SYSTEM Inc. Mobile Disco Console with O/P stage (£79-95) & pr. 12" Speakers **£99-95**

POWER (SLAVE) AMPLIFIER 100 WATT

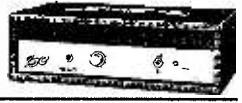Suitable for use with above or other DISCO-Consoles. Also for increasing output of lower-powered Amplifiers. Terms: Dep. £9-00 and 8 mthly payments of £5-22 (Total £50-76) carr. £1



TITAN GROUP/DISCO SPKRS GUARANTEED FOR 5 YEARS

	Rec. Price	RSC Price
T12/35 12" 35w	£14-00	£10-95
T12/60A 12" 60w	£21-00	£14-95
T12/100 12" 100w	£36-00	£23-95
T15/60 15" 60w	£27-00	£17-99
T15/70 15" 70w	£28-00	£19-95
T15/100 15" 100w	£39-50	£28-95
T18/100 18" 100w	£44-00	£29-95

SPECIAL OFFER

FOR ONE MONTH ONLY
FANE CRESCENDO
12 BASS 12" Super Bass Guitar Speaker
Our Price **£33-95**
Carr. Free
Rec. Ret. Price **£49-30**

TERMS	MONTHLY PAYMENTS DEPOSIT	TOTAL
Model T12/35	(Pp) £4-00 & 8 at £2-62	£32-86
Model T12/60A	(Pp) £6-00 & 8 at £3-37	£38-86
Model T12/100	(Ea) £4-95 & 8 at £3-00	£38-86
Model T15/60	(Ea) £3-99 & 8 at £2-25	£21-89
Model T15/70	(Ea) £4-95 & 8 at £2-37	£28-81
Model T15/100	(Ea) £6-00 & 8 at £2-37	£32-86
Model T18/100	(Ea) £6-95 & 8 at £2-37	£33-91

R.S.C. TRANSFORMERS, L.F. CHOKES & RECTIFIERS

FULLY GUARANTEED. Impregnated and Interleaved where necessary. Primaries 200-250v. 50c/a. Sorensen ALL PRICES INCLUDE VAT

MIDGET CLAMPED TYPE
250v. 60mA 6-3v. 2a. £1-75
250-0-250v. 100mA 6-3v. 2a. £1-85
250-0-250v. 60mA 6-3v. 2a. 0-5-6-3v. 2a. £2-60
250-0-250v. 100mA 6-3v. 4a. 0-5-6-3v. 3a. £4-35
300-0-300v. 130mA 6-3v. 4a. C.T. 6-3v. £5-20
1a. for Mullard 510 Amplifier. £5-20
350-0-350v. 100mA 6-3v. 4a. 0-5-6-3v. 3a. £4-35
350-0-350v. 150mA 6-3v. 4a. 0-5-6-3v. 3a. £5-20
425-0-425v. 200mA 6-3v. 4a. C.T. 6v. 3a. £5-95
425-0-425v. 200mA 6-3v. 4a. 6-3v. 4a. 5v. 3a. £10-00
450-0-450v. 250mA 6-3v. 4a. C.T. 5v. 3a. £10-45

TOP SHROUDED DROP-THROUGH TYPE
250-250v. 70mA 6-3v. 2a. 0-5-6-3v. 2a. £2-60
250-0-250v. 100mA 6-3v. 3-5a. £2-90
250-0-250v. 100mA 6-3v. 2a. 6-3v. 1a. £3-20
350-0-350v. 60mA 6-3v. 2a. 0-5-6-3v. 2a. £3-20
250-0-250v. 100mA 6-3v. 4a. 0-5-6-3v. 3a. £4-35
300-0-300v. 100mA 6-3v. 4a. 0-5-6-3v. 3a. £4-35
300-0-300v. 130mA 6-3v. 4a. 0-5-6-3v. 1a suitable for Mullard 510 Amp. £5-20
350-0-350v. 100mA 6-3v. 4a. 0-5-6-3v. 3a. £4-35
350-0-350v. 150mA 6-3v. 4a. 0-5-6-3v. 3a. £5-90

FILAMENT OR TRANSISTOR POWER PACK
Type: 12v. 1a. £1-10, 6-3v. 1-5a. £1-06, 6-3v. 2a. £1-10, 6-3v. 3a. £1-70, 6-3v. 6a. £2-60, 12v. 2a. or 24v. 1-5a. £2-60, 0-9-18v. 1½a. £2-28, 0-12-24-42v. 2a. £3-19
AUTO (STEP UP/STEP DOWN) TRANSFORMERS
0-110-120v. 200-230-250v. 50-80w. £2-90 150 watts £2-20, 250 watts £2-87, 500 watts £2-84

CHARGES TRANSFORMERS
0-9-15v. 1½a. £2-08, 2½a. £2-26, 3a. £2-32, 5a. £2-34, 6a. £2-19, 8a. £2-48

OUTPUT TRANSFORMERS
Standard Pentode 5000 to 3 ohm, or 7000 ohm to 3 ohm £11-12. Push Pull 8 watts EL34 to 3 ohm or 15 ohm £1-68; Push Pull 10-12 watts 6v, 6 to 3 ohm or 15 ohm £2-61; Push Pull 10-12 watts to match 6v, 6 to 3, 5, 8 or 15 ohm £2-72; Push Pull EL34 to 3 or 15 ohm 10-12 watts £2-61; Push Pull Ultra Linear for Mullard 510 etc. £2-35; Push Pull 15-18 watts, sectionally wound 6L6 KT66 etc. from 3 or 15 ohm. £3-71. Push Pull 20 watt high quality sectionally wound EL34 6L6 KT66 etc. to 3 or 15 ohm, fully shrouded. £2-27.


SELENIUM RECTIFIERS
F.W. (Bridge)
AIF 612 v. D.C. output. Max. A.C. input 13v. 1a 45p, 2a 57p, 3a 65p, 4a 95p, 5a 11-15.

L.F. CHOKES 150mA, 7-10H, 250 Ω £1-28; 100mA, 10H, 200 Ω £1-10; 60mA, 10H, 400 Ω £1-10.

RSC 200 WATT DISCO SYSTEM

STEREO 100 plus 100 WATT OUTPUT

AT A FANTASTIC LOW PRICE!

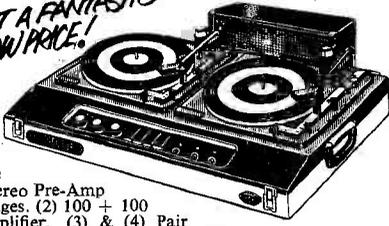

Consisting of (1) Twin T/table Console with Stereo Pre-Amp and P.U. Cartridges. (2) 100 + 100 watt Power Amplifier. (3) & (4) Pair 100 Watt Loudspeakers including Twin 12" Units

Rec. Mic. UD150 Cardioid £9.95 extra with system only

SYSTEMS UP TO 300 WATTS OUTPUT

AT UNBEATABLE PRICES Send for Catalogue

£199.95

car. £7.50

Terms: Dep. £40.00 and 12 monthly payments £15.60 (Total £227.20)

- ★ ILLUMINATED P.U. ARMS
- ★ FULL SIZE B.S.R. Turntables
- ★ SEPARATE MAINS SWITCHES for L. & R. Turntables
- ★ NEON MAINS INDICATORS for all three switches
- ★ INPUTS (Each with its own SLIDER Control) for Mic & Tape
- ★ MASTER BASS, TREBLE AND VOLUME CONTROLS
- ★ FADE IN/FADE OUT SLIDER MIXER Controls for each T/table

TDI DISCO CONSOLE

Incorporating twin BSR MP60 type turntables and Sonotone or Accos Cartridges with diamond styl. Separate Vol. controls for each turntable. Also MONITORING FACILITIES, plus Treble and Bass Controls. Separate input for 'mixer' with vol. control. Black Vynide covered Cabinet with lid. Or DEP. £14.95 and 18 fortnightly pymts. £5.47 (Total £113.41) Carr. £1.50

£99.95

TD2S STEREO VERSION OF ABOVE

Terms DEPOSIT £20 and 18 fortnightly payments £6.71 Carr. £2.00 (Total £140.78)

FANE DUO DISCO 60C SPKR UNITS

Can be supplied with 200w system in lieu of RSC spkrs. for £56 extra. Twin Fabulous specialist range Spkrs in heavy Vynide covrd pair cabinets with protective corner pieces and handles. Rating 120 watt R.M.S. each. List Price £150 Pair.

DISCOMASTER TWIN TURNTABLE POWER CONSOLE £119.95

Twin McDonald MP60 type turntables. Sonotone or Accos cartridges with Car. diamond styl. Facilities as TDI Console but with built-in 100 watt Power Amp. £2.60 pflifer, complete with lid. Or Dep. £18.95 and 18 fortnightly pymts £6.78 (Total £185.99)

STEREO VERSION £155 and 18 fortnightly pymts £8.30 (Total £174.40). Carr. £3

FANE ULTRA HIGH POWER SPEAKERS & KITS

All power ratings are R.M.S. continuous. 2 YEARS' GUARANTEE High flux ceramic magnets. ALL CARRIAGE FREE.

'POP' 100	'POP' 60	'POP' 50/2
18" 100Watt 14,000 gauss 8/15p £39.95	15" 60 Watt 14,000 gauss 8/15p £23.95	12" 50 Watt 13,000 gauss 8/15p £14.99
Dep. £6.95 and 8 monthly payments £4.60 (Total £43.75)	Dep. £5.99 and 8 monthly payments. £2.62 (Total £23.95)	Dual Cone. Terms for pairs Dep. £5.90 & 8 mthly pymts £3.00. Total £29.90 PAIR SUITABLE ALL PURPOSES

FOR BASS GUITAR, ELECT. ORGAN, ETC.

R.S.C. COLUMN SPEAKERS IDEAL FOR VOCALISTS AND PUBLIC ADDRESS

All types 15 Ohms covered in Vynide & Vynair

TYPE C132 40-50 WATTS £27.95
Highly sensitive high flux speakers with high power voice coils. Approx. size 54" x 14" x 11". Deposit £9.00 and 12 mthly. pymts. £4.00. (Total £49.95) £57.00 Carr. 85p.

TYPE C4/80 80 WATTS. Fitted four 12" highly sensitive high flux speakers with high power voice coils. Approx. size 54" x 14" x 11". Deposit £9.00 and 12 mthly. pymts. £4.00. (Total £49.95) £57.00 Carr. 85p.

ALL RSC PRICES INCLUDE VAT

INTEREST on Credit Purchases REFUNDED settled in 3 months

SUPER MINSTREL 10 W GUITAR AMP.

Incorporating Tremolo and 10" Speaker. Output 10 watts R.M.S. Continuous. 3 Jack Inputs for Microphone and Instrument. Mains Neon Controls: Volume, Tone, Tremolo Speed, Tremolo Intensity. Terms: DEPOSIT £7.75 and 8 monthly payments £3.80 (Total £34.15) Carr. free £29.99

FANE CRESCENDO SPEAKERS

FULL RANGE AVAILABLE AT ALL BRANCHES

'POP' 25/T 12" 25W HIGH POWER TWEETER PH50

Dual cone. 15 ohm Imp. £9.95 (Not for Bass Guitar use). Terms for Pairs: Deposit £3.99 and 8 mthly pymts of £2.75 (Total £25.98). Carr. free.

Response 3kHz-20kHz with 2 mjd. Non elect. filter available 55p. Rating 50 Watt 15 Ohm Imp 8

£6.65

TITAN T2H HIGH FREQUENCY UNITS

Incorporating a pair of Highly Sensitive Horns with substantially flat response to over 15 kHz. Rating 70/100 watts. Imp 8 or 16 Ω. Or Dep. £2.85 & 8 monthly payments £1.38 (Total £43.99). Carr. 55p

£39.95

RSC PHANTOM 50 COMBO AMP. £59.95

Rating 50 watts. 3 inputs, 2 vol. controls—Bass, Treble Presence. Carr. £1.50 Suitable for Lead or Rhythm Guitar, mic., Radio, Tape etc. Inc. High Flux 12" 50w Speaker. Dep. £7.95 & 8 monthly payments £7.43 (Total £67.78).

PHANTOM 50/GP

all purpose version of above. £69.95 Carr. £1.75
Extra high sensitivity. Can be used with Bass Guitar. Or Dep. £9.95 & 8 monthly payments £8.70 (Total £78.55)



FAL PHASE 50-4 AMPLIFIER 50 WATT

Solid state. 4 Sep. controlled inputs Plus master vol. control. Ind. Bass and Treble Controls. Protection against serious o/p overloading. O/p for spkrs. 8 to 15 ohms. 200-250v. A.C. mains. Output 50 watts R.M.S. cont. Deposit £8.60

& 8 mthly. payments £5.75. Total £54.60 Carr. Free.

£48.60

I.S.E. JINGLE MACHINES JINGLE 8+

Emplying Standard 8 Track Cartridge £37.95
Or Dep. £4.85 & 8 monthly pymts £4.85 (Total £43.65).

FAL PHASE 100-4 £67.95

Facilities as above. Output 100 watt MUSIC, 70W RMS

FAL PHASE 50-4 WITH L12/2 70 W TWIN SPEAKER UNIT

Vynide covered. Fitted with protective corner pieces. Carr. £2.50. £88.00
Or Dep. £10.00 & 12 monthly payments £7.67 (Total £102.04) or with L125 100 W TWIN SPKR UNIT Suitable for all purposes inc. Bass Guitar. Carr. £2.60 £94.50
Terms. Dep. £14.50 & 18 fortnightly payments £5.16 (Total £107.20)

ECHO CHAMBERS £51.95

Excellent quality units

HEAVY DUTY CABINETS

Black Vynide covered. Fitted Protective Corner Pieces. Cut for various Speaker Combinations. 18" x 18" x 9" £10.95
Carr. £1 24" x 24" x 12" £19.95
each unit. 36" x 24" x 12" £26.95
Sizes approx.: 30 1/2" x 28 1/2" x 12" £28.95

HIGH QUALITY L'SPEAKER UNITS

ALL 2-TONE VYNIDE & VYNAIR FINISH L12/2 70/100w Fitted pair of 12" 35 watt high flux speakers. Imp. £39.95
8-15 ohms. Music rating 100w. Carr. £1.50. Terms: Dep. £5.11 & 8 monthly payments of £5.11. (Total £45.99).

L12/50 12" 50 WATT 13000 lines 15 ohms. Terms: Dep. £4.95 and 8 mthly pymts. £3.37 (Total £31.91) Carr. 55p.

LIQUID WHEEL from PROJECTORS £29.95

'SOUND TO LIFE' SYSTEM PULSAR £106.95

special price complete kit
Dep. £14.95 and 18 fortnightly pymts. £5.98. (Total £121.89). Super SL Unit. 1000 watt per channel. Manual override buttons. 2 spotbanks with 6 bulbs (3 sep. colours) 5 yd. and 10 yd. leads. fitted Plugs. Units sold sep.

FAL SOUND-TO-LITE UNIT £21.60

3-WAY SOUND BANK
Extending Bulbs Each £16.20
COMPLETE SYSTEM Carr. £1.50 £55
Incl. 2 Spotbanks and bulbs.

New Branches at YORK CARLISLE, DEWSBURY LIVERPOOL, PRESTON

OPEN ALL DAY SATURDAYS (5 Day Week)

BRADFORD 10 North Parade (Closed Wed.). Tel. 25349
BOLTON 23 Deansgate. (Closed Wed.). Tel. 33512
BIRMINGHAM 30/31 Great Western Arcade. Tel. 021-236 1279 (Closed Wed.).

CARLISLE 8 English Street. (Closed Thurs.). Tel. 38744
COVENTRY 17 Shelton Sq. The Precinct. Tel. 25983
DERBY 97 St. Peter's Street. (Closed Wed.). Tel. 41361
DARLINGTON 19 Northgate (Cl. Wed.). Tel. 68043
DEWSBURY 9/11 Kingsway (Closed Tues.). Tel. 468058
DONCASTER 3 Queensgate, Waterdale Centre. (Closed Thurs.). Tel. 63069

EDINBURGH 101 Lothian Rd. (Cl. Wed.). Tel. 229 9501
GLASGOW 326 Argyle St. (Cl'd Tues.). Tel. 248 4158
HULL 7 Whitefriargate (Closed Thurs.). Tel. 20505
LEICESTER 32 High Street (Closed Thurs.). Tel. 56420
LEEDS 5-7 County (Mecca) Arcade, Briggate (Closed Wed.). Tel. 458252

LIVERPOOL 35 Dawson's Way, St. John's Shopping Centre Tel. 708 9380 (Cl. Wed.). Tel. 723 1829
LONDON 238 Edgware Road, W.2. (Closed Thurs.). Tel. 238 2778
MANCHESTER 60A Oldham Street (Closed Wed.). Tel. 238 2778
MIDDLESBROUGH 103 Linthorpe R d. Tel. 210585 (Closed Wed.)

Barclaycard and Access accepted

All items subject to availability. Prices correct at 15.4.76 E & O.E.


MAIL ORDERS & EXPORT ENQUIRIES TO:— AUDIO HOUSE, HENNONNER LANE, LEEDS. 18. Tel: Pudsey (09735) 77631. MAIL ORDERS MUST NOT BE SENT TO SHOPS TERMS O.W.O. or O.O.D. No O.O.D. under £1. POSTAGE 40p PER ORDER OR AS QUOTED. TRADE SUPPLIED. LARGE S.A.E. REQUIRED FOR FREE CATALOGUE.

NEWCASTLE UPON TYNE 24 Newgate Shopping Centre, 59 Grainger St. (Closed Wed.). Tel. 21469
NOTTINGHAM 19/19A Market Street. (Closed Thurs.). Tel. 48068
PRESTON 41 Friargate Walk, St. Georges Shopping Prec. Tel. 51978
SHEFFIELD 13 Exchange Street. (Closed Thurs.). Tel. 20716
STOCKPORT 3 Little Underbank (Closed Thurs.). Tel. 480-0777
SUNDERLAND 5 Market Sq. (Closed Wed.). Tel. 70573
YORK 5 CHURCH ST. (Closed Wed.). Tel. 34355

RTVC

ELIZABETHAN STEREO TUNER AMPLIFIER

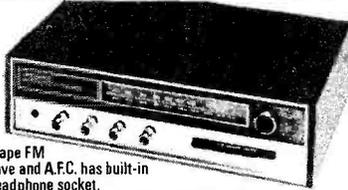This compact Tuner Amplifier gives you full medium wave and V.H.F. coverage and FM stereo. With inputs for your turntable and tape recorder. It has rotary tuning, Volume, Balance, Bass and Treble controls and push button selection switches for Phono/tape FM Stereo, FM mono, Medium wave and A.F.C. has built-in stereo beacon and switched headphone socket.



Technical Specifications 15 transistors, 11 diodes, integrated circuit. Power output 8 watts. Size of tuner amplifier: 4" x 10" x 15 1/2" approx. Finished in selected rosewood veneer with brushed aluminium front panel and matching controls. Output into 15 ohms speakers only.

£29.00
+ p&p £1.50

* STEREO 21

INCORPORATING A GARRARD DECK
Garrard 3 speed Deck automatic, manual facilities together with stereo cartridge and cueing device.



Stereo 21, easy to assemble audio system kit. No soldering required. The unit is finished in Sim Teak, and the acrylic top presents an unusually interesting variation on the modern deck plinth. Includes - 3 speed deck, automatic manual facilities together with stereo cartridge and cueing device. Two speakers with cabinets. Amplifier module. Ready built with control panel, speaker leads and full, easy to follow assembly instructions. Specifications - For the technically minded. Input sensitivity 600mV. Aux. input sensitivity 120mV. Power output 2.7 watts per channel. Output impedance 8-15 ohms. Stereo headphone socket with automatic speaker cutout. Provision for auxiliary inputs - radio, tape, etc., and outputs for taping discs. Overall Dimensions. Speakers approx 12" x 9" x 5". Complete deck and cover in closed position approx. 15 1/2" x 12" x 6". Extras if required. Optional Diamond Stylus £1.60. Specially selected pair of stereo headphones with individual level controls and padded earpieces to give optimum performance £5.00.

COMPLETE ONLY
£23.20 + p&p £4.00

BSR DECKS WITH PLINTHS AT FANTASTIC REDUCTIONS



MP 60 Type (illustrated) **£16.00**
Less Cartridge p&p £2.00

C141 (not illustrated) **£12.00**
Auto. with Cue p&p £1.50
Fitted Stereo Cartridge

All plinths finished in matching Teak veneer.

EASY TO BUILD SPEAKER KITS

These superb simulated teak-finished speaker kits have been specially designed by RT-VC for the cost-conscious hi-fi enthusiast who wants top quality speakers but doesn't want to spend the earth. Built to EMI's exacting specification, these new RT-VC speaker kits (350 type kit) incorporate 13 x 8" woofer, 3 1/2" tweeter and matching crossover. Easily put together with just a few basic tools. Specification (each speaker): Impedance 8 ohms. Power handling 15 watts RMS (30 watts peak). Response 20-20,000 Hz. Size 20" x 11" x 9 1/2" approx. Comparable built units (EMI LE3) sold elsewhere for over £45 pair.

£22.00 pair complete
+ £5.20 p&p

Complete with crossover Components and circuit diagram.



THE 'COMPACT' EASY BUILD SPEAKER KIT

A compact bookshelf speaker system giving a high electro acoustic efficiency for the low powered amplifier. The professional finish can be obtained with the minimum of tools, the infinite baffle type enclosures come ready mitred and professionally finished, and fit together with masking tape till glue dries. The cabinet measures 12" x 9" x 5" deep approx finished in simulated teak, incorporating a quality 7" x 4" elliptical speaker, power handling 4 watts, flux density 30,000 maxwells, impedance 8-15 ohms nominal, voice coil dia 3/4" magnet size 2 1/2" approx.



£6.00 + p&p £1.70
PAIR INCLUSIVE

EMI 350 KIT

£7.25 + £1.20 p & p.
Complete with crossover Components and circuit diagram

System consists of a 13" x 8" approx. woofer with a 3" tweeter, crossover components and circuit diagram. Frequency response: 20 Hz to 20 KHz. Power handling 15 watts RMS into 8 ohms. (Peak 30 watts.)

VISCOUNT IV STEREO AMP

NOW AVAILABLE IN KIT FORM!
30x30 WATTS RMS

COMPLETE 20x20 SYSTEMS
SYSTEM 1A £69.00
+ p&p £1.50

The new 20 + 20 watt Stereo Amplifier incorporating the latest silicon transistor solid state circuitry, the RT-VC VISCOUNT IV gives you a powerful 20 watts RMS per channel into 8 ohms. Superb teak-finished cabinet, with anodised fascia to harmonise with any decor. Polished trim and knobs. The VISCOUNT IV has a comprehensive range of controls - volume, bass, treble, balance mono/stereo, mode selector, and scratch filter. Front panel socket for stereo headphones. And a host of sockets at the rear - for left and right speakers, tape recorder, auxiliary, tuner, disc and microphone.

SPECIFICATION: 20 watts RMS per channel 40 watts peak. Suitable 8-15 ohms speakers. Total distortion at 10 watts better than 0.2%. Six switched inputs: 1. Magnetic PU - 3 millivolts at 47 K ohms (R.I.A.A.); 2. Crystal/ceramic PU. - 50 millivolts at 50 K ohms (R.I.A.A.); 3. 4. 6. Tape Tuner/Aux. - 140 millivolts at 50 K ohms (flat frequency response); 5. Microphone - 3 millivolts at 50 K ohms (flat frequency response).

CONTROLS: Push button ON/OFF, stereo/mono, scratch filter, 6 position rotary selector. Individual rotary controls for treble, bass, balance and volume. Headphone socket, tape out socket. Aux. mains output. Frequency response: 25 Hz to 25 kHz at full rated output. Signal to noise ratio: better than -50 dB on all inputs. Tone control range: Bass ±15 dB at 50 Hz; Treble ±12 dB at 10 KHz. Power requirements: 250V A.C. mains at 60 watts. Approx size: 15 1/2" x 3" x 10". MP60 type deck with magnetic cartridge, de luxe plinth and cover. Two Duo Type 11a matched speakers - Enclosure size approx. 19 1/2" x 10 1/2" x 7 1/2" in simulated teak. Drive unit 13" x 8" with 3" tweeter. 15 watts handling. 30 watts peak.



Complete System with these speakers
£69.00
+ £6.50 p&p.

SYSTEM 2 £85.00

Viscount IV amplifier (As System 1a)
MP60 type deck (As System 1a)
Two Duo Type III matched speakers - Enclosure size approx. 27" x 13" x 11 1/2". Finished in teak simulate. Drive units 13" x 8" bass driver, and two 3" (approx.) tweeters. 20 watts RMS, 8 ohms frequency range - 20 Hz to 18,000 Hz. Complete System with these speakers **£85.00** + £7.60 p & p.

PRICES: SYSTEM 1a
Viscount IV R103 amplifier £27.50 + £1.90 p & p.
2 Duo Type 11a speakers £30.00 + £6.50 p & p.
MP60 type deck with Mag. cartridge de luxe plinth and cover £22.00 + £3.30 p & p.
Total if purchased separately: £79.50
Available complete for only: **£69.00** + £6.50 p & p.

PRICES: SYSTEM 2
Viscount IV R103 amplifier £27.50 + £1.90 p & p.
2 Duo Type III speakers £46.00 + £7.50 p & p.
MP60 type deck with Mag. cartridge de luxe plinth and cover £22.00 + £3.30 p & p.
Total if purchased separately: £95.50
Available complete for only **£85.00** + £7.60 p & p.

Scotland and the Orkneys P & P Surcharge
System 1a £1.75 System 2 £3.50
Note: 30 x 30 kit available only as a separate item.

PUSH BUTTON CAR RADIO KIT - THE TOURIST *



* IF YOU CAN SOLDER CORRECTLY ON A PRINTED CIRCUIT BOARD YOU CAN BUILD THIS KIT CORRECTLY.

NOW YOU CAN BUILD YOUR OWN PUSH-BUTTON CAR RADIO! This construction kit comprises a fully built and aligned R.F. I.F. module; Printed circuit board, with ready mounted integrated circuit output stage and all other components. The push button tuning mechanism is fully built and tested ready to mate with the printed circuit board. (once it is assembled) **NOTE:** No test equipment is required for alignment, but remember you must have the ability to solder on a printed circuit board.

TECHNICAL SPECIFICATION:

- (1) Output 4 watts RMS output. For 12 volt operation on negative or positive earth.
- (2) Integrated circuit output stage, pre-built three stage IF Module. Controls volume

manual tuning and five push buttons for station selection, illuminated tuning scale covering full, medium and long wave bands. Size chassis 7" wide 2" high and 4 1/2" deep approx. Speaker including baffle and fixing strip £2.00 + 45p. p. & p. **Car Aerial Recommended**—fully retractable £1.60 + 40p. p. & p. **Price £8.20 + £1.05 p. & p.**

SPECIAL OFFER

The Tourist I Kit

Complete with speakers, fixing kit and fully retractable aerial. **£10.50 + p. & p. £15.00**


STEREO CASSETTE TAPE DECK KIT*

Kit comprises of ready built cassette tape transport mechanism. Featuring pause control solenoid assisted auto-stop, 3 digit tape counter, belt-driven balanced fly wheel, DC motor with electronic speed control, ready built and mounted record/replay PC board, and two VU meters, power supply, PC board, mains transformer. Input and output sockets and two level controls. Specification power source 240 AC 50Hz. Output more than 0.5v input mike -65dB, 10KΩ. DIN -47dB, 100KΩ. Track system 2 channel stereo record play-back. Tape speed, 4.8CM/SEC. Frequency response 50-12,000Hz signal to noise ratio -42dB. Recording system AC Bias. Erasing system AC erase. Bias frequency 57KHz. Size of mechanism 8" x 5" x 3 1/2" approx. unit easy to mount into your cabinet 3" required to clear base of mechanism approx.


* This is an advanced kit not suitable for those without electrical knowledge and those unable to solder.

£32.50
+ p & p £1.50
or send SAE for complete details.

NEW!

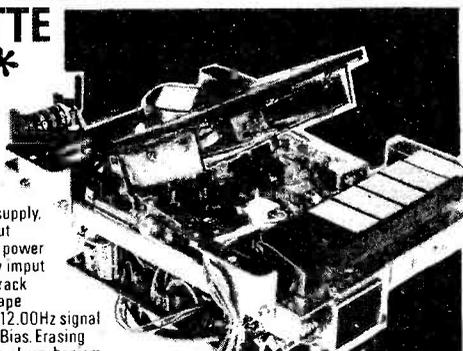

* DISCO AMPLIFIER

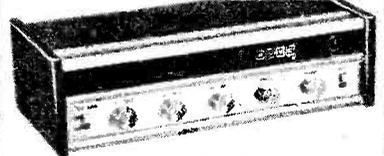


Reliant Mk IV Mono Amplifier, ideal for the small disco or house parties. Output 20 watts RMS into 8 ohms (suitable for 15 ohms). Inputs *4 electrically mixed inputs. *3 individual mixing controls. *Separate bass and treble controls common to all 4 inputs. *Mixing employing F.E.T. (Field Effect Transistors). *Solid State circuitry. *Attractive styling.

INPUT SENSITIVITIES - Input - 1). Crystal mic. guitar or moving coil mic, 2 and 10mV. (Selector switch for desired sensitivity.) - Inputs - 2), 3), 4). Medium output equipment - ceramic cartridge, tuner, tape recorder, organs, etc. - all 250mV sensitivity. AC Mains, 240V operation. Size approx: 12 1/2" x 6" x 3 1/2" **£20.00 + £1.35 p & p.**

8 TRACK HOME CARTRIDGE PLAYER

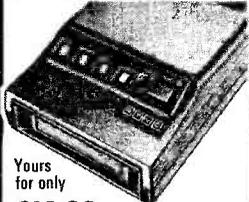Elegant self selector push button player for use with your stereo system. Compatible with Viscount IV system. Unisound module and the Stereo 21. Technical specification Mains input, 240V, Output sensitivity 125mV.



Yours for only **£14.00 + £1.70 p & p.**

SPECIAL OFFER

As above but complete with build yourself Unisound Amplifier Kit (see opposite panel) + 2 'Compact' easy to build speaker kits (see opposite page) **£25.00 + p & p £2.00**

BUILD YOUR OWN STEREO AMPLIFIER*



For the man who wants to design his own stereo - here's your chance to start, with Unisound - pre-amp, power amplifier and control panel. No soldering - just simply screw together. 4 watts per channel into 8 ohms. Inputs: 120mV (for ceramic cartridge). The heart of Unisound is high efficiency I.C. monolithic power chips which ensure very low distortion over the audio spectrum. 240V. AC only.

Also available with 2 speakers (7"x4") **£10 + £1.75 p & p. £8.95 + £1.05 p & p.**
Also available with the 'Compact' (see opposite page) easy build speaker kit **£13.50 + £2 p & p.**

INCORPORATES: Pre-Amp with full mixing facilities, including switched input for mic with volume control, switched input for auxiliary with volume control, bass and treble controls, volume control and blend control for turntables. Two B.S.R. MP60 type single play professional series decks, fitted with crystal cartridges.

PORTABLE DISCO CONSOLE*



TECHNICAL SPECIFICATION:
Pre-amp - Output 200mV.
Auxiliary inputs - 200mV and 750mV into 1 meg. Mic input - 6mV into 100K. 240 volt operation.
Turntables - capacity - 10" or 12" records. Rumble, wow and flutter Rumble Better than -35dB. Wow Better than 0.2%. Flutter Better than 0.06% (Gaugmont kalee meter).
Finish - Satin black mainplate with black turntable mat inlaid with brushed aluminium trim. Tonearm and controls in black and brushed aluminium.

Console size - Unit Closed - 17 1/2" x 13 1/2" x 8 1/2" (app.)
Unit Open - 35 1/2" x 13 1/2" x 4 1/2" (app.)
This disco console is ideally matched for the Reliant IV and Disco 50 or any other quality amplifier.
The unit is finished in black PVC with contrasting simulated teak edging, diamond spun control knobs with matching control panel.

Yours for only **£49.00 + £6.50 p & p.**

All prices include VAT at current rates

Mail orders to Acton. Terms C.W.O. All enquiries stamped addressed envelope. Goods not despatched outside U.K.

* Leaflets available for all items listed thus * Send stamped addressed envelope. All items subject to availability. Prices correct at 1st April 1976 and subject to change without notice.

Minimum order on ACCESS/BARCLAYCARD-£11.



DO NOT SEND CARD
Just write your order giving your credit card number

RTVC

21C HIGH STREET, ACTON, LONDON W3 6NG
323 EDGWARE ROAD, LONDON W2

Personal Shoppers EDGWARE RD: 9 a.m.-5.30p.m. Half day Thurs
ACTON: 9.30a.m.-5p.m. Closed all day Wed.

CLEARANCE OFFER!

SEW PANEL METERS

AT GREATLY REDUCED PRICES

BAKELITE PANEL METERS—MODEL MR 65

Dimensions: Front 80mm x 80mm square
Panel Hole: 65mm diameter
Accuracy $\pm 2.5\%$



£2.95 each


25 μ A £3.95 each
50 μ A £3.25 each
VU Meter £3.40 each
P/P + Ins. 15p

RANGES

100 μ A	5A DC	150V AC*
500 μ A	10A DC	300V AC*
50-0-50 μ A	15A DC	500V AC*
100-0-100 μ A	30A DC	1A AC*
500-0-500 μ A	50A DC	2A AC*
1mA	5V DC	10A AC*
1-0-1mA	10V DC	20A AC*
5mA	15V DC	30A AC*
10mA	20V DC	50A AC*
50mA	50V DC	300mA AC
100mA	150V DC	500V DC
500mA	300V DC	100mV DC
1A DC	30V AC*	
2A DC	50V AC*	

* Moving iron (all others are moving coil).

CLEAR PLASTIC PANEL METERS—MODEL MR 85P

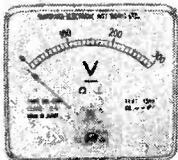

Dimensions: Front 110mm x 120mm wide
Panel Hole: 85mm
Accuracy $\pm 2.5\%$

RANGES

50 μ A	10mA	50V DC
100 μ A	50mA	150V DC
200 μ A	100mA	300V DC
500 μ A	500mA	15V DC
50-0-50 μ A	1A DC	300V AC
100-0-100 μ A	5A DC	1A AC*
500-0-500 μ A	15A DC	5A AC*
1mA	30A DC	10A AC*
1-0-1mA	10V DC	20A AC*
5mA	20V DC	30A AC*

£3.95 each

'S' Meter 1mA £4.55 each
VU Meter £4.55 each
P/P + Ins. 15p.

* Moving iron (all others are moving coil).

EDUCATIONAL METERS—MODEL ED 107

High quality moving coil meters ideal for school use and many other applications.

Housed in strong black plastic cases. Clear view front, 3" mirror scale. Fully insulated terminals will accept either spade or 4mm plug.
Dimensions: 100mm wide x 90mm deep x 105mm high overall.
Accuracy $\pm 2\%$



£5.95 each

P/P + Ins. 15p

SINGLE RANGE MODELS

50 μ A	1A DC	15V DC
100 μ A	5A DC	20V DC
50-0-50 μ A	5V DC	50V DC
1mA	10V DC	300V DC
1-0-1mA		

DUAL RANGE MODELS

500mA/5A DC	5V/15V DC
5V/50V DC	1A/15A DC

Available for personal shoppers at LASKYS



451 Oxford Street, W.1.
311 Edgware Road, W.2.
42 Tottenham Court Road, W.1.
3 Lisie Street, W.C.2

01-493 8641
01-262 0387
01-636 0845
01-437 8204

MAIL ORDERS AND ACCOUNT ENQUIRIES TO HEAD OFFICE

LASKYS, CUSTOMER SERVICES DIVISION,
DEPT. 'J' AUDIOTRONIC HOUSE, THE HYDE
HENDON, NW9 6JJ.

Telephone: Mail Order 01-200 1321 or 01-200 0037
(24 hour answerphone) Accounts: 01-200 0444

Telex: 924820

Access, Barclaycard and Diners Club accepted at all branches or by telephone at head office.

ALL PRICES INCLUDE VAT.



ELECTROLYTIC CAPACITOR OFFER

1000063 £1.88	2200/40	30p	1220/63	18p
1000050 £1.50	1000/180	63p	160/25	9p
5000/70	76p	1000/40	25p	100/40
5000/50	75p	1000/30	25p	100/12
5000/35	50p	1000/25	25p	8/450
5000/12	25p	470/63	23p	16/450
3000/25	30p	470/35	20p	50/450
2500/70	63p	330/100	30p	32+32/450
2200/63	20p	250/64	20p	50/50

Micro Switches (make or break) 8p
Cable Ties 3p
TOS Heat Sinks 13p
Pot Cores (14mm or 18mm) complete 25p
180° Plastic DIN Sockets 13p

DIGITAL I.C.S

Large range of 7400 series in stock. Prices from 18p.

INTEGRATED AUDIO POWER AMPS
20W RMS, 1 off £6.38, Stereo pair £11.95.
30W RMS, 1 off £7.95, Stereo pair £14.80.
50W RMS, 1 off £12.38, Stereo pair £22.76.
50W RMS (4 Ω) amp. kits complete with building and application details. Suitable for instruments, disco, hi-fi, etc. £8.95.

SEMICONDUCTORS

AC141	57p	BC167	14p	BD124	97p	MJ3001	£2.80	2N3053	25p
AC142	42p	BC188	14p	BD131	32p	MJ4200	25.88	2N3054	68p
AD181	82p	BC169	15p	BD132	64p	MJE2955	£1.48	2N3055	59p
AD182	82p	BC182	13p	BD135	56p	MJE3055	75p	2N3702	2.37
BC107	13p	BC212	16p	BD136	63p			2N3711	14p
BC108	12p	BC301	32p	BFY50	23p	TIP29A	69p		
BC109	16p	BC302	56p	BFY51	22p	TIP30A	85p	40361	55p
BC147	14p	BC303	37p	BFY52	24p	TIP31A	87p	40362	60p
BC148	12p	BCY70	18p	MJ481	£1.36	TIP32	99p	40406	55p
BC149	14p	BCY71	50p	MJ491	£1.52	TIP41A	72p	40407	40p
BC157	14p	BCY72	16p	MJ2500	£2.75	TIP42A	£1.27	40408	63p
BC158	12p	BD115	67p	MJ2501	£2.85	TIP2955	£1.38	40409	63p
BC159	12p	BD121	£1.48	MJ3000	£2.68	TIP3055	75p	40410	65p

P. & P. 25p on all orders. Hundreds of other types of semiconductors held in stock. S.A.E. with all inquiries.

ORDERS OVER £5-5% discount, £10-10% discount. £15-15% discount

ALL PRICES INCLUDE VAT

EBA

Elliott Blunt Audio Ltd.

40 YORK STREET, TWICKENHAM, MIDDX.

Tel. 01-891 1692

Opening hours 9.30 a.m. to 6 p.m. Tuesday-Saturday

Unbeatable VALUE

Genuine GOLDRING Stylus P. & P. 25p

G800	£2.35	G850	£1.95
G800/H	£2.35	G800/E	£4.42

MICROPHONES P. & P. 25p

UD 130—Cardioid dynamic dual Impedance 600 and 50k Ω	£5.58
ECM61—Cardioid condenser omni-directional 600 and 50k Ω	£11.99
RX20—Cardioid dynamic 600 Ω echo mike, 4 transistors, 1.5 sec reverberation time, with volume control and on-off switch	£9.93
Philips type cassette mike	£1.65
Cassette stick mike with remote control	£1.30
Gem 2 station intercom (baby alarm)	£3.85

CASSETTES (Low Noise) P. & P. 25p

C60	1-5	over 6
C90	35p	32p
C120	43p	40p
	55p	52p

SOLDERING IRONS P. & P. 25p

12V d.c. 15 watt £1.24	250V a.c. 40 watt £1.40
------------------------	-------------------------

CABINET KITS P. & P. 85p per pair

12" x 8" x 4 1/2" (8" x 5" or 7" x 4" cutout)	£2.90 each
12" x 12" x 7 1/2" (10", 8" or 8" x 5" cutout)	£4.05 each
18" x 11" x 7 1/2" (8" and 3", 8" x 5" or 8" cutout)	£5.10 each
22" x 14" x 7 1/2" (13" x 8" or 12" and 3" cutout)	£6.15 each

ALL PRICES INCLUDE VAT

Items subject to availability and manufacturers' increase. U.K. only.

Riversdale Electronics

Mail Order Department PW6

P.O. Box 470, Manchester M60 4BU

DIGITAL : CLOCKS : KITS : CALCULATORS

"ALPHA": 4 GREEN .5" HIGH DIGITS

	Alarm	Std.
Alpha Module (excl. case) Kit	13.00	10.00
Alpha Module (excl. case) Built	14.00	11.00
Alpha complete: Perspex Case Kit	15.50	12.50
Alpha Clock: Perspex Case ... Built	21.50	17.50

ALARM

- Tilt Snooze ● AM/PM ● Mains failure Ind. ●
- Auto-Control Brightness by Photocell ●

"DELTA": 4 RED .5" HIGH LEDs

	Alarm	Std.
Delta Module (excl. case) Kit	11.50	9.00
Delta Module (excl. case) Built	12.00	9.50
Delta complete: Perspex Case ... Kit	15.00	12.00
Delta Clock: Perspex Case Built	21.00	17.00
Delta complete: Teak Case Kit	15.70	12.70
Delta Clock: Teak Case Built	21.70	17.70

Perspex Case Colours: Black, White, Red, Green, Blue, Orange
Built Modules and Clocks: state 12 or 24 hour (Delta 12hr only).
Complete Clocks: 2 Year Guarantee

"NOVUS" CALCULATORS

650 Mathbox £5.40 ● 850 Mathbox £6.75
4510 Mathematician .. £16.20 ● P0120 Statistician .. £21.60

C.W.O. PULSE ELECTRONICS (PW13), 202 Shefford Road, Clifton, Shefford, Beds. SAE complete range
TELEPHONE: HITCHIN (0482) 81477

Module kits

£9:00

INCLUDING VAT, P. AND P.
SATISFACTION GUARANTEED

- Modern 2 Part Case
- Drilled P.C.B.
- 4 Digit Display 0.5 inch high
- All components included
- Even Mains lead included
- Full instructions
- Assembly Drawing
- Circuit Diagram

You supply only mains plug and standard tools — Easy!



BENTLEY ACOUSTIC CORPORATION LTD.

7a GLOUCESTER ROAD, LITTLEHAMPTON, SUSSEX
All prices inclusive of V.A.T. at 25% Telephone 6743

OB2	45	8RA6	41	6K7G	85	19E1	8.51	9E4A	76	DK96	70	ECH42	80	BY84	98	PCF2011	1.05	QS160/15		VR105	59	ACY21	85	BY127	83
OZ4	55	8BC8	80	9K8G	88	19J7G	70	9E5C	86	DL96	64	ECH81	40	EY86/7	40	PCF801	65	QV08/20	1.90	VU111	80	ACY22	80	BY210	83
IAS	85	8BE6	41	6L1	2.84	12K5	1.17	3E5D	90	DM70	80	ECH83	58	EY88	80	PCF802	50			VU120	1.17	ACY26	83	BY211	83
1ASGT	89	8BE6	75	6L6GC	88	12K7G	50	3E5DGT	88	DM71	1.76	ECH84	50	EY91	50	PCF806	60			VU120A	1.17	AD140	87	BY212	83
1A7GT	80	8BJ6	84	6L7	59	12K8	85	3E5W	80	DY87/8	41	ECL80	80	EZ40	55	PCH200				B19	75	VU133	80	AD181	59
1B3GT	89	8BK7A	85	6L18	85	12K9T	50	3E5Z	88	DY87/8	41	ECL82	45	EZ41	55	PCF808	50	UBC81	60	TH333	1.00	WI07	75	AD182	59
1B3GT	89	8BQ7A	84	6L19	2.00	12K9T	50	3E5ZGT	88	EY80C	2.57	EY80	80	EZ42	55	PCF812	45	UBC80	47	UBP80	40	Z759	5.85	AF121	89
1HG7	75	8BR7	1.20	6LD20	88	12M7	55	3E5ZGT	90	E80CF	6.00	EY80	80	EZ43	55	PCF813	50	UBC80	47	PEN45	1.00	UBF89	47	AF126	82
1NGT	76	8BR8	1.25	6N7GT	70	12M7	55	43	1.00	E80F	2.20	EY80	80	EZ44	55	PCF814	50	UBC80	47	PEN45	1.00	UBF89	47	AF126	82
IR5	50	8B87	1.64	6Q7G	60	12M7	55	43	1.00	E80F	2.20	EY80	80	EZ45	55	PCF815	50	UBC80	47	PEN45	1.00	UBF89	47	AF126	82
184	89	8BW6	1.00	6Q7GT	60	12M7	55	43	1.00	E80F	2.20	EY80	80	EZ46	55	PCF816	50	UBC80	47	PEN45	1.00	UBF89	47	AF126	82
1U4	70	8BW7	85	6Q7M	60	12M7	55	43	1.00	E80F	2.20	EY80	80	EZ47	55	PCF817	50	UBC80	47	PEN45	1.00	UBF89	47	AF126	82
1U5	88	8BZ6	87	6R7G	64	14H7	64	6DC6DG	70	E180F	1.17	EY81	50	EZ48	55	PCF818	50	UBC80	47	PEN45	1.00	UBF89	47	AF126	82
SD21	80	8C4	47	6S47	55	14S7	1.10		1.48	E180C	2.00	EY81	50	EZ49	55	PCF819	50	UBC80	47	PEN45	1.00	UBF89	47	AF126	82
2GK5	75	6CG5	59	6SC7GT	60	18A05	65	60E8H5	88	E1148	62	EY81	50	EZ50	55	PCF820	50	UBC80	47	PEN45	1.00	UBF89	47	AF126	82
2X2	70	6C6	47	6SG7	52	19G5	7.00	60L6GT	1.00	E450	40	EY81	50	EZ51	55	PCF821	50	UBC80	47	PEN45	1.00	UBF89	47	AF126	82
3A4	60	6C9	2.00	6SH7	55	20D1	80	8E42	75	E476	1.40	EY81	50	EZ52	55	PCF822	50	UBC80	47	PEN45	1.00	UBF89	47	AF126	82
3D6	47	6CB6A	47	6S47	55	20F2	85	8E43	75	E4B080	45	EY81	50	EZ53	55	PCF823	50	UBC80	47	PEN45	1.00	UBF89	47	AF126	82
3Q4	85	6CD8G	1.80	6SK7GT	52	20L1	1.20	90A4	2.98	EAC91	85	EY81	50	EZ54	55	PCF824	50	UBC80	47	PEN45	1.00	UBF89	47	AF126	82
3Q5GT	70	6CG8A	88	6S47	50	20P1	1.00	90C1	88	EAF42	68	EY81	50	EZ55	55	PCF825	50	UBC80	47	PEN45	1.00	UBF89	47	AF126	82
384	47	6CL8	78	6V6G	90	20P3	94	90Q2	81	EAF801	80	EY81	50	EZ56	55	PCF826	50	UBC80	47	PEN45	1.00	UBF89	47	AF126	82
3V4	82	6CLA	94	6V6GT	58	20P4	1.17	150B2	1.00	E434	35	EY81	50	EZ57	55	PCF827	50	UBC80	47	PEN45	1.00	UBF89	47	AF126	82
4CB6	75	6CM7	88	6X4	47	20P5	1.50	218S8	59	E434	35	EY81	50	EZ58	55	PCF828	50	UBC80	47	PEN45	1.00	UBF89	47	AF126	82
6CG8	75	6C05	88	6X5GT	50	20A8G	70	807	1.17	E4C41	88	EY81	50	EZ59	55	PCF829	50	UBC80	47	PEN45	1.00	UBF89	47	AF126	82
8R4GY	94	6CW4	1.17	7B6	88	25L60	70	8702	1.20	E4C81	88	EY81	50	EZ60	55	PCF830	50	UBC80	47	PEN45	1.00	UBF89	47	AF126	82
5U4G	80	6D3	75	7B7	82	26V6G	60	8763	1.78	E4F80	40	EY81	50	EZ61	55	PCF831	50	UBC80	47	PEN45	1.00	UBF89	47	AF126	82
5V4G	89	6D7	88	7B7	88	28Z4G	50	6067	1.00	E4F80	40	EY81	50	EZ62	55	PCF832	50	UBC80	47	PEN45	1.00	UBF89	47	AF126	82
5Y3GT	85	6ED7	88	7B7	2.00	28Z6	75	6060	1.00	E4F80	40	EY81	50	EZ63	55	PCF833	50	UBC80	47	PEN45	1.00	UBF89	47	AF126	82
5Z3	88	6EW6	88	7Y4	80	28Z6G	80	6067	1.00	E4F80	40	EY81	50	EZ64	55	PCF834	50	UBC80	47	PEN45	1.00	UBF89	47	AF126	82
5Z4G	55	6E5	1.17	7Z4	80	28D7	8.00	7193	95	E4C86	80	EY81	50	EZ65	55	PCF835	50	UBC80	47	PEN45	1.00	UBF89	47	AF126	82
5Z4GT	55	6E1	80	9D7	80	30C15	80	9006	50	E4C86	80	EY81	50	EZ66	55	PCF836	50	UBC80	47	PEN45	1.00	UBF89	47	AF126	82
6A0G	80	6F8G	89	10C14	78	30C15	80	9006	50	E4C86	80	EY81	50	EZ67	55	PCF837	50	UBC80	47	PEN45	1.00	UBF89	47	AF126	82
6ACT	80	6F14	88	10F1	86	30C18	85	ACPEP	1.17	E4C86	80	EY81	50	EZ68	55	PCF838	50	UBC80	47	PEN45	1.00	UBF89	47	AF126	82
6AG5	85	6F15	78	10F9	78	30F5	75	AL60	1.17	E4C86	80	EY81	50	EZ69	55	PCF839	50	UBC80	47	PEN45	1.00	UBF89	47	AF126	82
6AH6	80	6F18	84	10F18	80	30FL1	1.10	ATP4	50	E4C86	80	EY81	50	EZ70	55	PCF840	50	UBC80	47	PEN45	1.00	UBF89	47	AF126	82
6AJ5	76	6F23	80	10LD11	82	30FL2	1.10	AZ1	50	E4C86	80	EY81	50	EZ71	55	PCF841	50	UBC80	47	PEN45	1.00	UBF89	47	AF126	82
6AK6	47	6F24	1.00	10F13	85	30F13	78	AZ21	80	E4C86	80	EY81	50	EZ72	55	PCF842	50	UBC80	47	PEN45	1.00	UBF89	47	AF126	82
6AK6	40	6F25	89	10C14	2.84	30FL14	82	AZ41	50	E4C86	80	EY81	50	EZ73	55	PCF843	50	UBC80	47	PEN45	1.00	UBF89	47	AF126	82
6AM8A	70	6F28	78	12A6	75	30L15	82	E163	2.84	E4C86	80	EY81	50	EZ74	55	PCF844	50	UBC80	47	PEN45	1.00	UBF89	47	AF126	82
6AN8	68	6F29	70	12AC6	90	30L17	76	E163	1.85	E4C86	80	EY81	50	EZ75	55	PCF845	50	UBC80	47	PEN45	1.00	UBF89	47	AF126	82
6AQ5	65	6G6G	80	12AD9	80	30F4MR		CY1C	1.00	E4C86	80	EY81	50	EZ76	55	PCF846	50	UBC80	47	PEN45	1.00	UBF89	47	AF126	82
6AR5	80	6G88A	88	12AE6	90	1.05	CY31			E4C86	80	EY81	50	EZ77	55	PCF847	50	UBC80	47	PEN45	1.00	UBF89	47	AF126	82
6AS7	1.17	6GK5	78	12AT6	47	30F13	80	DAF91	40	E4C86	80	EY81	50	EZ78	55	PCF848	50	UBC80	47	PEN45	1.00	UBF89	47	AF126	82
6AT6	88	6G77	88	12B76	58	30F13	80	DAF91	40	E4C86	80	EY81	50	EZ79	55	PCF849	50	UBC80	47	PEN45	1.00	UBF89	47	AF126	82
6AUS	40	6HGT	89	12AV8	59	30P4	88	DC90	70	E4C86	80	EY81	50	EZ80	55	PCF850	50	UBC80	47	PEN45	1.00	UBF89	47	AF126	82
6AV6	85	6JSGT	88	12BA6	85	30FL4	1.00	DF91	90	E4C86	80	EY81	50	EZ81	55	PCF851	50	UBC80	47	PEN45	1.00	UBF89	47	AF126	82
6AWA	90	6J6	85	12BE6	59	30FL13	1.20	DP96	85	E4C86	80	EY81	50	EZ82	55	PCF852	50	UBC80	47	PEN45	1.00	UBF89	47	AF126	82
6AX8A	88	6J7G	85	12BH7	59	30FL14	1.29	DK40	82	E4C86	80	EY81	50	EZ83	55	PCF853	50	UBC80	47	PEN45	1.00	UBF89	47	AF126	82
6B8G	85	6JUS8A	88	12BY7	85	30FL15	80	DK92	1.15	E4C86	80	EY81	50	EZ84	55	PCF854	50	UBC80	47	PEN45	1.00	UBF89	47	AF126	82



WILMSLOW AUDIO

THE Firm for speakers!

SPEAKERS

Baker Group 25, 3, 8 or 15 ohms £8-64
 Baker Group 35, 3, 8 or 15 ohms £10-25
 Baker Group 50/12 8 or 15 ohms £14-00
 Baker Group 50/15 8 or 15 ohms £18-62
 Baker Major 3, 8 or 15 ohms £13-75
 Baker Major 8 or 15 ohms £11-87
 Baker Superb 8 or 15 ohms £18-12
 Baker Regent 12" 8 or 15 ohms £10-00
 Baker Auditorium 12" 8 or 15 ohms £16-25
 Baker Auditorium 15" 8 or 15 ohms £21-56
 Celestion G12M 8 or 15 ohms £12-95
 Celestion G12/50 8 or 15 ohms £15-95
 Celestion G12/50TC 8 or 15 ohms £16-50
 Celestion G15C 8 or 15 ohms £26-95
 Celestion G18C 8 or 15 ohms £34-50
 Celestion HF1300 8 or 15 ohms £7-65
 Celestion HF2000 8 ohms £9-50
 Celestion MH1000 8 or 15 ohms £13-50
 Celestion C03K £4-95
 Decca London ribbon horn £32-00
 Decca London CO/1000/8 Xover £7-50
 Decca DK30 ribbon horn £19-00
 Decca CO/1/8 Xover (DK30) £3-06
 EMI 14" x 9 Bass 8 ohms 14A/770 £13-25
 EMI 8" x 5, 10 watt, d/cone, roll surr. £3-95
 EMI 6" d/cone, roll surr. 8 ohms £4-37
 EMI 8" roll surr. bass £6-37
 EMI 5" mid range £3-50
 Elac 59RM109 (15) 59RM114 (8) £3-75
 Elac 6" d/cone, roll surr. 8 ohms £4-25
 Elac 10" 9RM230 8 ohms £4-25
 Eagle Crossover 3000Hz 3, 8 or 15 ohm £1-75
 Eagle FR4 £6-12
 Eagle FR65 £9-62
 Eagle FR8 £12-31
 Eagle FR10 £15-62
 Eagle HT15 £24-40
 Eagle HT21 £6-81
 Eagle MHT10 £4-44
 Eagle FF28 multicell. horn £9-00
 Fane Pop 15, 8 or 16 ohm £5-25
 Fane Pop 25T, 8 or 16 ohm £7-50
 Fane Pop 30T, 8 or 16 ohm £9-25
 Fane Pop 50, 8 or 16 ohm £12-50
 Fane Pop 55, 8 or 16 ohm £15-50
 Fane Pop 60, 8 or 16 ohm £17-95
 Fane Pop 70, 8 or 16 ohm £18-75
 Fane Pop 100, 8 or 16 ohm £27-95
 Fane Crescendo 12A, 8 or 16 ohms £37-95
 Fane Crescendo 15B, 8 or 16 ohms £39-95
 Fane Crescendo 15/100A, 8 or 16 ohms £49-95
 Fane Crescendo 15/125, 8 or 16 ohms £59-95
 Fane Crescendo 18, 8 or 16 ohms £67-95
 Fane 910 Mk II horn £15-75
 Fane 920 Mk II horn £36-95
 Fane HPK1 crossover 200 watt £2-50
 Fane 13 x 8, 15 watt dual cone £5-50
 Fane 801T 8" d/c, roll surr. £9-95
 Goodmans Axent 100 £14-95
 Goodmans Audiom 200 8 ohm £22-00
 Goodmans Axion 402 8 or 15 ohm £10-55
 Goodmans Twinaxiom 8, 8 or 15 ohm £10-95
 Goodmans Twinaxiom 10, 8 or 15 ohm £5-95
 Goodmans 8P 8 or 15 ohm £6-25
 Goodmans 10P 8 or 15 ohm £14-95
 Goodmans 12P 8 or 15 ohm £14-95
 Goodmans 12PD 8 or 15 ohm £16-50
 Goodmans 12AX 8 or 15 ohm £16-95
 Goodmans 12AX 8 or 15 ohm £39-00

SPEAKERS

Goodmans 15AX 8 or 15 ohm £45-00
 Goodmans 15P 8 or 15 ohm £22-50
 Goodmans 18P 8 or 15 ohm £39-00
 Goodmans Hifax 750P £16-00
 Goodmans 5" midrange 8 ohm £13-75
 Gauss 12" 200 watt £11-87
 Gauss 15" 200 watt £96-00
 Gauss 18" 200 watt £129-00
 Jordan Watts Module 4, 8 or 15 ohm £17-06
 Kef T27 £5-75
 Kef T15 £6-94
 Kef B110 £7-50
 Kef B200 £8-70
 Kef B139 £16-75
 Kef DN8 £2-31
 Kef DN12 £5-99
 Kef DN13 SP1015 or SP1017 £4-50
 Lowther PM6 Mk 1 £34-00
 Lowther PM7 £36-50
 Peerless K010DT 4 or 8 ohms £8-06
 Peerless DT10HFC 8 ohms £9-18
 Peerless K040MRF 8 ohms £10-31
 Peerless MT25HFC 8 ohms £3-12
 Richard Allan Super disco 60W 12" £22-00
 Richard Allan HP85 £13-25
 Richard Allan HP88 £9-25
 Richard Allan DT20 £6-75
 Richard Allan CN8280 £18-00
 Richard Allan CN820 £3-50
 Richard Allan CA12 12" bass £18-95
 Richard Allan CG15 15" bass £30-50
 Richard Allan Super Disco 10" 50 watt £13-25
 Richard Allan Super Disco 8" 50 watt £12-95
 Radford MD9 £11-50
 Radford MD6 dome mid range £12-50
 Radford TD 2 £8-06
 Radford Crossover network £14-25
 BD25 Mk II £24-00
 STC 4001G £6-56
 Tannoy 10" HPD £75-00
 Tannoy 12" HPD £81-95
 Wharfedale Super 10 RS/DD 8 ohms £97-95
 Castle 8 RS/DD £15-00

SPEAKER KITS

Richard Allan Twin assembly each £14-95
 Richard Allan Triple 8 each £22-50
 Richard Allan Triple 12 each £27-95
 Richard Allan Super Triple each £32-50
 Richard Allan RA8 Kit pair £42-00
 Richard Allan RA82 Kit pair £66-00
 Richard Allan RA82L Kit pair £73-00
 Fane Mode One Mk2 each £11-50
 Wharfedale Linton II kit pair £23-12
 Wharfedale Glendale 3XP kit pair £53-00
 Wharfedale Dovedale III kit pair £66-00

HI-FI

ON DEMONSTRATION in our showrooms

Akai, Armstrong, Bowers and Wilkins, Castle, Celestion, Dual, Goodmans, Kef, Leak, Pioneer, Radford, Richard Allan, Rotel, Tandberg, Trio, Videotone, Wharfedale, etc. Ask for our Hi-Fi Discount Price List.

THIS MONTHS SPECIALS! Pioneer PL12D £46-95, Pioneer PL15R £57-95, Pioneer SX434 £104-95, Rotel RX202 £87-95, Videotone Minimax II £42-95.

We stock the complete Radford range of amplifiers, preamplifiers, power amplifiers, tuners, etc., and also Radford Audio Laboratory equipment, low distortion oscillator, distortion measuring set, audio noise meter, etc.

All Prices Include VAT
(Prices correct at 9.3.76)

Send stamp for Free 32 page booklet 'Choosing a Speaker'.

All units guaranteed New and Perfect. Carriage and Insurance: Speakers 50p each, 12" and up 75p each. Kits 80p each (£1-60 per pair). Tweeters and crossovers 30p each.

WILMSLOW AUDIO

Dept. PW

Loudspeakers, Mail Order and Export: Swan Works, Bank Square, Wilmslow.

Hi-Fi, Radio & TV: Swift of Wilmslow 5 Swan Street, Wilmslow, Cheshire.

PA, Hi-Fi & Accessories: Wilmslow Audio, 10 Swan Street, Wilmslow, Cheshire.

Telephone: Loudspeakers, Mail Order and Export Wilmslow 29599

Hi-Fi, Radio, etc., Wilmslow 26213

Complete kits in stock for Radford Studio 90, Radford Monitor 180, Radford Studio 270, Radford Studio 360, HiFi Answers Monitor (Rogers), HiFi New No Compromise (Frisby), Wireless World Transmission Line (Bailey), Practical HiFi and Audio Monitor (Giles), Practical HiFi and Audio Triangle (Giles), Popular HiFi (Colloms), etc.

Construction leaflets for Radford, Kef, Jordan Watts, Tannoy, Hi-Fi Answers Monitor, Free on Request.

P.A. Amplifiers, microphones etc. by Shure, Linear, Eagle, Beyer, AKG etc.

FREE with orders over £10—"HiFi Loudspeaker Enclosures" Book

BI-PAK High quality audio



OUR PRICE ONLY

£19.95

The 450 Tuner provides instant programme selection at the touch of a button ensuring accurate tuning of 4 pre-selected stations, any of which may be altered as often as you choose, by simply changing the settings of the pre-set controls. Used with your existing audio equipment or with the BI-KITS STEREO 30 or the MK60 Kit etc. Alternatively the PS12 can be used if no suitable supply is available, together with the Transformer T481. The S450 is supplied fully built, tested and aligned. The unit is easily installed using the simple instructions supplied.




STEREO FM TUNER

Fitted with Phase Lock-loop Decoder

- ★ FET Input Stage
- ★ VARI-CAP diode tuning
- ★ Switched AFC
- ★ Multi turn pre-sets
- ★ LED Stereo Indicator

Typical Specification:
Sensitivity 3µ volts
Stereo separation 30db
Supply required 20-30v
at 90 Ma max.

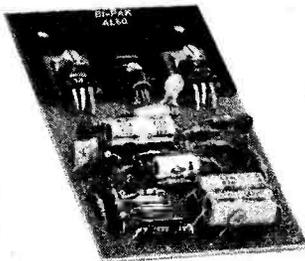

AL 60

25 Watts
(RMS)

- Max Heat Sink temp. 90C.
- Frequency response 20Hz.
- Distortion better than 0.1 at 1kHz.
- Supply voltage 15-50v.
- Thermal Feedback.
- Latest Design Improvements.
- Load—3,4,5, or 16ohms.
- Signal to noise ratio 80db.
- Overall size 63mm. 13mm.

Especially designed to a strict specification. Only the finest components have been used and the latest solid-state circuitry incorporated in this powerful little amplifier which should satisfy the most critical A.F. enthusiast.

ONLY **£3.95**

Stabilised Power Supply Type SPM80

SPM80 is especially designed to power 2 of the AL60 Amplifiers, up to 15 watts (r.m.s.) per channel simultaneously. With the addition of the Mains Transformer BMT80, the unit will provide outputs of up to 1.5A at 35V. Size: 63mm, 105mm, 30mm. Incorporating short circuit protection.

INPUT VOLTAGE	33-40V. A.C.	
OUTPUT VOLTAGE	33V. D.C. Nominal	
OUTPUT CURRENT	10mA-1.5 amps	£3.00
OVERLEAD CURRENT	1.7 amps approx.	
DIMENSIONS	105mm x 63mm x 30mm	
TRANSFORMER BMT80	£2.60 + 62p. postage	

VAT
ADD
12½%

STEREO PRE-AMPLIFIER PA 100



A top quality stereo pre-amplifier and tone control unit. The six push-button selector switch provides a choice of inputs together with two really effective filters for high and low frequencies, plus tape output.

Frequency Response + 1dB
20Hz-20KHz.
Sensitivity of inputs:
1. Tape Input 100mV into 100K ohms
2. Radio Tuner 100mV into 100K ohms
3. Magnetic P.U. 3mV into 50K ohms
P.U. input equalises to RIAA curve within 1dB from 20Hz to 20KHz. Supply 20-35V at 20mA.
Dimensions—200mm x 60mm x 35mm.

£13.50 p & p 45p


MK60 AUDIO KIT:

Comprising: 2 x AL60's 1 x SPM80, 1 x BTM80, 1 x PA100, 1 front panel and knobs. 1 Kit of parts to include on/off switch, neon indicator, stereo headphone sockets plus instruction booklet. **COMPLETE PRICE £27.55 plus 62p postage.**

TEAK 60 AUDIO KIT:

Comprising: Teak veneered cabinet size 16½" x 11½" x 3½", other parts include aluminium chassis, heatsink and front panel bracket plus back panel and appropriate sockets etc. **KIT PRICE £9.20 plus 62p postage.**

STEREO 30 COMPLETE AUDIO CHASSIS

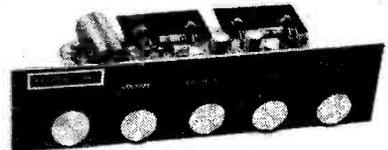

1 + 1 WATTS R.M.S.

The Stereo 30 comprises a complete stereo pre-amplifier, power amplifiers and power supply. This, with only the addition of a transformer or overwind will produce a high quality audio unit suitable for use with a wide range of inputs i.e. high quality ceramic pick-up, stereo tuner, stereo tape deck etc. Simple to install, capable of producing really first class results, this unit is supplied with full instructions, black front panel, knobs, mains switch, fuse and fuse holder and universal mounting brackets enabling it to be installed in a record plinth, cabinets of your own construction or the cabinet available. Ideal for the beginner or the advanced constructor who requires Hi-Fi performance with a minimum of installation difficulty (can be installed in 30 mins.).

TRANSFORMER **£2.45** plus 62p p & p

TEAK CASE **£3.65** plus 62p p & p.

£15.75 P & P 45p.


equipment mono and other modules for Stereo

IT'S NEW!

IT'S POWERFUL

IT'S THE AL250

125 watts
R.M.S.

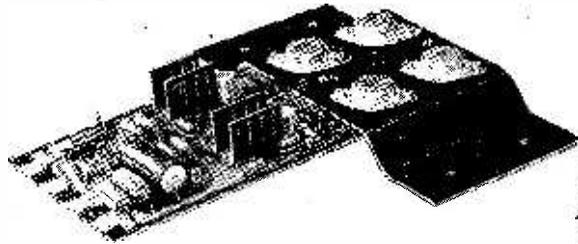

POWER AMPLIFIER

Specially designed for use in—
Disco Units, P.A. Systems, high power
Hi-Fi, Sound reinforcement systems

The module has a sensitivity of 450mV and a frequency response extending from 25Hz to 20KHz whilst distortion levels are typically below 0.1%. The use of 4, 115w transistors in the output stage makes the unit extremely rugged while damage resulting from incorrect or short-circuit loads is prevented by a four transistor protection circuit.

The unit is intended for use in many applications such as disco units, sound reinforcement systems, background music players, etc.

SPECIFICATION:

Output Power: 125 watt RMS
Continuous
Operating voltage: 50-80
Loads: 4-16 ohms
Frequency response: 25Hz-
20kHz Measured at 100 watts
Sensitivity for 100 watts output
~ at 1kHz: 450mV
Input impedance: 33Kohms

Total harmonic distortion
50 watts into 4 ohms: 0.1%
50 watts into 8 ohms: 0.06%
S/N ratio: better than 80dBs
Damping factor, 8 ohms: 65-
Semiconductor complement: 13
transistors 5 diodes
Overall size: Heatsink width
190mm, length 205mm Height
40mm

ONLY £15.95 +8% VAT

MPA 30



Enjoy the quality of a magnetic cartridge with your existing ceramic equipment using the new Bi-Pak M.P.A. 30 which is a high quality pre-amplifier enabling magnetic cartridges to be used where facilities exist for the use of ceramic cartridges only. Used in conjunction are 4 low noise, high gain silicon transistors. It is provided with a standard DIN input socket for ease of connection. Supplied with full, easy-to-follow instructions.

£2.65




POSTAGE & PACKING

Postage & Packing add 25p unless otherwise shown. Add extra for airmail. Min. £1.00

AL10-20-30

AUDIO AMPLIFIER MODULES

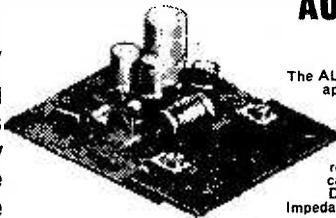

The AL10, AL20 and AL30 units are similar in their appearance and in their general specification.

However, careful selection of the plastic power devices has resulted in a range of output powers from 3 to 10 watts R.M.S.

The versatility of their design makes them ideal for use in record players, tape recorders, stereo amplifiers and cassette and cartridge tape players in the home. Harmonic Distortion: Po = 3 watts f = 0.25% Load Impedance 8-16ohm

Frequency response $\pm 3dB$ Po = 2 watts 50Hz-25KHz
Sensitivity for Rated O/P -Vs = 25v. RL = 80ohm
f = 1KHz 75mV. RMS. Size: 75mm x 63mm x 25mm.

AL10 3w
R.M.S.

£2.30

AL2: 5w
R.M.S.

£2.65

AL30 10w
R.M.S.

£2.95



PA12

£6.50

NEW PA12 Stereo Pre-Amplifier completely redesigned for use with AL10 20 30 Amplifier Modules. Features include on/off volume. Balance. Bass and Treble controls. Complete with tape output.

Frequency Response 20Hz-20KHz (-3dB)

Bass and Treble range $\pm 12dB$

Input Impedance 1 meg ohm

Input Sensitivity 300mV

Supply requirements 24v. 5mA

Size 152mm x 84mm x 33mm

PS12

Power supply for AL10/20/30, PA12, S450 etc. Input voltagr 15-20v A.C. Output voltage 22-30v D.C. Output Current 800 mA Max. Size 60mm x 43mm x 26mm.

Transformer T538 **£2.30**

£1.20

BI-PAK

P.O. BOX 6, WARE, HERTS

GREENWELD

443 Millbrook Road Southampton
SO1 0HX Tel: (0703) 772501

All mail order and callers (OPEN 9-6 MON-SAT.) to this address please
—callers only to 21 Deptford Broadway, SE8 (Tel. 01-692 2009), and 38 Lower
Addiscombe Road, Croydon (Tel. 01-688 2950).

PC ETCHING KIT Mk II
Contains 1lb Ferric Chloride, 100 sq ins copper clad board, DALO Quick Dri Etch resist pen, abrasive cleaner, 2 miniature drill bits, etching dish and instructions. £3-65

7lb BARGAIN PARCELS
Hundreds of new components—pots, resistors, capacitors, switches, PC Boards with transistors, diodes and zeners, loads of odds and ends. Only £3-25

TRANSISTOR PACKS
200 asstd. malhly out of spec. transistors, mostly unmarked—NPN PNP plastic, TO18 RF AF. Small signal and TO9 power devices. About 75% useable. £1-00. Only £1-50. 100 unmarked BC108, untested £2-10. 10 out of spec. 2N3055 £1.

COMPONENT PACKS
400 asstd. carbon resistors £1-50
250 HI-Stabs, 1, 2, 5% 1/4W £1-40
100 Wirewounds 2-15W £2-00
200 Miniature resistors, 1/4, 1/2 and 3/4W, mostly carbon film £1-10
200 poly, mica, ceramic caps £1-10
100 Polyester, .01-2.2uF £1-30
200 miniature electrolytics, but many unmarked so only £1-35
15 Useful switches, micro, toggle, rocker and rotary. £2-00
35 Crystals, mostly HC11U, at least 30 cts, freqs. 4-5MHz £1-80.
300 cable markers, sieving, etc. 30p
150 Grommets, assorted sizes 50p

COMPUTER PANELS
Large quantity always available; 3lb asstd. £1-75; 7lbs £3-65; 56lb £16. Pack with about 500 components inc. at least 50 transistors £1-00; pack with 12 High quality panels, inc. IC's, power transistors, multi-turn trim pots, hundreds of small signal transistors, resistors, zeners, capacitors, etc. Only £2-75.
7400 IC pack—20 74 series IC's on panels £1-20

PE Gas Ignitor Kit, as featured in July 75 edition. Still only £3-00.

FERRIC CHLORIDE
Anhydrous technical quality in 1lb double sealed packs. 1lb 85p; 3lbs £1-90; 10lbs £4-80; 100lbs £36-00.

VEROBOARD
100sq ins asstd. sizes and pitches, about 8 pieces (All 0-1" if requested) £1-20

DEVELOPMENT PACKS
50V ceramic plate capacitors, 5%, 10 of each value 22pF to 1000pF, total 210 caps. £3-90
Cres carbon film 1/3rd watt resistors, 5%, 10 of each value 10 ohms to 1M Total 610 resistors £7-50. Electrolytics, wire ended 25V working 10 each of: 1, 2-2, 4-7, 10, 22, 47 and 100mfd. 70 capacitors for £3-60. 400mV zeners 5%, 10 each 3V to 30V, 260 in all. Only £14-00.
C280 Polyester Caps, 10 of each, 0-01-0.47uF 110 caps for £4-50.

TRANSFORMERS
All have mains primaries, 6-0-6V 100mA £1-00; 9-0-9V 100mA £1-07; 12-0-12V 50mA 95p; 12-0-12V 100mA £1-90; 24-0-24V 50mA £2-05; Multi-tapped transformer to give 3, 4, 5, 6, 8, 9, 10, 12, 15, 18, 20, 24 or 30V, or 12-0-12, or 15-0-15V. 1A version £3-15; 2A Version £4-45; 30-0-30V 1A £3-25; 6-0-6V 1A £1-95; 12-0-12V 1A £2-15; 25V 1-7A £2-60. 25V 50mA £3-15; 12V 150mA 95p. Type LGC: 17V at 2.4A; 15-7V at 1.25A and 12V at 0.5A £2-50.

ODDS AND ENDS
975kHz FT17B Xtal 50p; 20 33k or 1-8k 1% resistors 25p; Connector blocks, 12 way 2A or 5A, both 20p; Magnets, ceramic 9mm dia. x 10mm long with 2-8mm hole through the middle. 10 for 15p; Capacitors: 2000uF 10V vert mntg, long leads 12 for £1-00; 100 + 400uF 275V 45mm dia. x 12mm long 60p; 16000uF 25V 52mm dia. x 12mm long 65p; Telephone inserts, 20 balanced armature unit 30p; 250V 2 1/2A bridge rect 50p; 50V 1A 30p; Twin Phono Socket 8p; Crystal Mic insert 1 1/2" dia 35p. 20m Hook-up Wire, solid core 10 x 2m lengths, assorted colours 20p.

SEE PRACTICAL ELECTRONICS FOR INDIVIDUAL COMPONENT PRICES
All prices quoted include VAT and UK/BFPO postage. Most orders despatched on day of receipt. SAE with enquiries or for List please. Send 10p for full time or order form on orders over £3. Official Orders accepted from Schools, etc. Export/Wholesale enquiries welcome. Surplus components always wanted.

MULTIMETERS



MODEL LT22

Probably one of the lowest priced meters featuring a mirror scale, overload protection and 20000 ohms per volt sensitivity. A modern styled meter with unusually clear scale markings. Ranges: DC Volts 0-0.5-2.5-10-50-250-1000 AC Volts 0-10-50-250-1000 DC Current 0-50, 0-25mA-250mA Resistance 0-50k-500k-5M (Mid Scale 300-3k-30k) db's 4 ranges —20db to +42db. Size 130 x 90 x 42mm. £9-00



MODEL C7071

An exceptionally sensitive meter, 100,000 ohms per volt, that will prove its worth in a very short time. It features 4 ohms ranges, measuring up to 100 megohms and has a mirror scale. Ranges: DC Volts 0-0.5-5-25-50-250-1000 AC Volts 0-10-50-250-500-1000-DC Current 0-10uA-2-5mA-25mA-500mA Resistance 0-10k-1M-10M-100M (Mid Scale 130-13k-130k-1.3M) db's —20 to +62. Size 152 x 102 x 44mm £15-30

VEROBXES & CASES

Case type 1410, 205 x 140 x 40mm £2-90
1411, 205 x 140 x 75mm £3-25
1412, 205 x 140 x 110mm £4-20

Plastic Boxes—Professional quality, two tone grey polystyrene boxes with threaded inserts for mounting PC boards.

Type 2518, 120 x 65 x 40mm £1-52;
2520, 150 x 80 x 50mm £1-75; 2522,
188 x 110 x 60mm £2-40; Sloping front
type: 220 x 174 x 100/52mm £4-20.

INTERCOM UNIT

Chassis 230 x 155mm with Celestion 3 ohm 110mm speaker, small buzzer, 3 pole 4 way switch, line matching transformer, 10 way terminal block, 100k pot, etc. £2-00.

RF UNIT

A compact tuning unit containing 2 x CV4063 and 3 x CV4014 with screening cans, and a beautifully made 5 gang tuning capacitor, twin slider type, silver plated, with padders on each section. Also numerous coils, R's C's, etc. Only £2-50.

HEAT SINK

Large finned matt black aluminium heat sink 230 x 200 x 35mm with 4 silicon power transistors, sim, to 2N3718, and 16 1 ohm 5W resistors. £3-00.

RELAYS

Miniature plug in types: 1250 ohm 4c/o 40p; 700 ohm 4c/o 50p PO 3000 type: 650 ohm 12V, with 6 heavy duty c/o contacts (Equip) 75p. 6 1/2" coil 50p. Plug in relay, BTG base. 17mm dia. x 42mm long. 10kΩ coil, 1c/o contact 40p.

SWITCHES

16A 250V on/off rocker 20p; Push-on, push-off DPCC switch, 15p; 10A 250V rocker, DPCC Bistab 25p; 4 pole 3 way rotary switch, 32mm dia, 25p; Bank of 20 open construction SPCO microswitches, overall length 225mm, useful as cheap keyboard substitute. Only £1-30.

WIREWOUND POTS

30k 50p; 200Ω 4W; 10k 3W; 1k 3W; 50Ω 3W; 80Ω 3W; 80Ω 3W; 80Ω 3W, 100k 3W. All 25p each, any 10 £2-00.

FND500 Jumbo 0-5° CC Red LED now only £1-02

ADVANCED CLOCK KIT

Complete kit including attractive slim case for 6 digit alarm clock with bleep alarm, snooze, high brightness driving of Jumbo LED displays, automatic intensity control—no extra add-ons of touch switch snooze control and crystal control/battery back-up. £26-80

P.E. CAR CLOCK with Journey Timer

6 digit clock for use in any car with 12V battery, with an independent Journey timer incorporated. Bright Jumbo LED display comes on with Ignition—automatic intensity control. Complete kit of all parts needed including case, PCB's and all components. Full Instructions. £39-50

Easy to Build E.E. DIGITAL CLOCK (Jan. issue). Kit of all components, including case etc., for this attractive clock with 12mm green display. Full instructions. £15-70

50 Hz Xtal Timebase Kit for clocks (incl. advanced kit above). £8-28

CMOS ICS	CD4029 0-84	CD4059 3-64	CD4510 1-12	Displays
RCA MOT	CD4030 0-46	CD4060 0-82	CD4511 1-28	SLT-01 5-88
ONLY	CD4031 1-82	CD4061 1-84	CD4512 2-88	DL70AE 0-75
CD4000 0-17	CD4032 0-88	CD4062 7-33	CD4515 1-56	FND500 1-02
CD4001 0-17	CD4033 1-14	CD4063 0-90	CD4516 1-22	Display Int.
CD4002 0-17	CD4034 1-56	CD4066 9-58	CD4518 1-03	SN75491 0-81
CD4006 0-97	CD4035 0-97	CD4068 2-95	CD4520 1-03	SN75492 1-02
CD4007 0-17	CD4036 1-82	CD4069 0-18	CD4527 1-30	CA3130 0-88
CD4008 0-79	CD4037 0-78	CD4069 0-18	CD4532 1-6	Flat Cable
CD4009 0-46	CD4038 0-88	CD4070 0-18	CD4555 0-74	20WAY 1M
CD4010 0-46	CD4039 2-86	CD4071 0-18	CD4566 0-74	10M for 8-50
CD4011 0-17	CD4040 0-88	CD4072 0-18	MC14528 0-86	10WAY 1M
CD4012 0-17	CD4041 0-69	CD4073 0-18	MC14534 6-04	10M for 4-80
CD4013 0-46	CD4042 0-69	CD4075 0-18	MC14553 4-07	IC Socket
CD4014 0-83	CD4043 0-83	CD4076 1-27	MC14566 1-21	Pins
CD4015 0-83	CD4044 0-77	CD4077 0-18	MCM14552	100 0-50
CD4016 0-46	CD4045 1-15	CD4078 0-18	MC14552	1000 4-00
CD4017 0-83	CD4046 1-10	CD4081 0-18	MC14552	3000 10-50
CD4018 0-83	CD4047 0-74	CD4082 0-18	MC50253 5-60	Verocases
CD4019 0-46	CD4048 0-46	CD4085 0-59	MM5314 4-44	751410J 2-64
CD4020 0-92	CD4049 0-46	CD4086 0-58	AY51224 3-66	751411D 2-94
CD4021 0-83	CD4050 0-46	CD4089 1-27	MY5122 1-21	751412K 4-00
CD4022 0-79	CD4051 0-77	CD4093 0-66	MC14875 2-67	uA78L12WC
CD4023 0-17	CD4052 0-77	CD4094 1-53	CMOS	0-60
CD4024 0-84	CD4053 0-77	CD4095 0-86	Books	
CD4025 0-17	CD4054 0-95	CD4096 0-86	NO VAT or	
CD4026 1-42	CD4055 1-08	CD4097 2-95	P & P	
CD4027 0-46	CD4056 1-88	CD4098 1-50	RCA14875 2-67	
CD4028 0-74	CD4057 20-35	CD4098 0-86	MCMS02 8-77	

ADD VAT at 8% (Higher rate does not apply to any of above).
15p P & P on orders under £3—Despatch is by 1st Class Post.
Price list and data sent FREE with an order, or on request (an SAE helps).
Official orders welcomed (written or phoned)—Univis, Polys, Gof, Cos, etc.
Export orders: no VAT, add 35p (Europe) £1 (overseas) for Airmail p & p.
(No Export outside Europe for databooks and transformers).

SINTEL, 53n Aston Street, Oxford. Tel: 0865 49791

ENGINEERS

FREE



YOURSELF FOR A

BETTER JOB WITH MORE PAY!

Do you want promotion, a better job, higher pay? "New Opportunities" shows you how to get them through a low-cost home study course. There are no books to buy and you can pay-as-you-learn.

This helpful guide to success should be read by every ambitious engineer. Send for this helpful 44 page FREE book now. No obligation and nobody will call on you. It could be the best thing you ever did.

CUT OUT THIS COUPON

CHOOSE A BRAND NEW FUTURE HERE!
Tick or state subject of interest. Post to the address below.

POST NOW

Build-As-You-Learn	Electronic Engineering	Transistor Technology
PRACTICAL RADIO AND ELECTRONICS (with kit)	Computer Electronics	CITY AND GULLDS Installations and Wiring
Electrical Engineering	Programming	CITY AND GULLDS Electrical Technicians
Electrical Installations and wiring	Colour TV Servicing	CITY AND GULLDS Telecommunications
Electrical Draughtsmanship	C&G Radio, TV & Electronic Mechanics	Radio Amateurs' Exam etc. etc.
Electrical Mathematics	General Radio and TV Engineering	
	Radio Servicing, Maintenance and Repairs	

To ALDERMASTON COLLEGE Dept. EPW-16, Reading RG7 4PF EPW 16
Also at our London Advisory Office, 4 Fore Street Avenue, Moorgate London, EC2Y 3EJ Tel: 01-628 2721

NAME (Block Capitals Please) _____
ADDRESS _____
POST CODE _____

Other subjects _____ Age _____

Accredited by C.A.C.C. Member of A.B.C.C.

HOME OF BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY

ALL PRICES INCLUDE V.A.T.



PERSONAL CALLERS ARE WELCOME!

all items subject to manufacturers increase and availability



High Quality Construction Kits, stocked at all branches. Send for catalogue!

AMPLIFIERS P&P 95p Ins. £1
 Sansui AU2200 £63.70
 AU4400 £57.50
 Pioneer SA5300 £63.00

WHARFEDALE SPEAKER BARGAINS P&P 85p Ins. 50p
 Chevin (pair) £32.00
 Denton 2 (pair) £42.50
 Linton 3 (pair) £59.50
 Linton 2 (kits) £26.18

RECORD DECKS P&P 85p Ins. 50p
 Garrard SP25 Mk. IV £23.50
 Garrard SP25 Mk. IV/G800 £36.85
 Plinth & Cover
 BSR MP60 £17.00
 Connoisseur BD1 Kit £16.56
 BD2 Chassis/SAU2 £42.68
 SAU2 Pick-up Arm £17.91
 SCUT Cartridge £7.43
 Pioneer PL12D £58.25
 Plinth-cover for Garrard or BSR £5.31

KIT FORM CABINETS
 Teak Veneer P&P 85p Ins. 50p
 12" x 8" x 4 1/2" (8 x 5 or 7 x 4 cutout) £3.34
 12" x 12" x 7 1/2" (10", 8 x 5, 8", 6 1/2" and 3 1/2") £4.75
 12" x 11" x 7 1/2" (8" x 3 1/2" or 13 x 8) £5.94
 22" x 14" x 7 1/2" (12" x 3 1/2" or 13 x 8) £7.18

TWEETERS & CROSSOVERS P&P 25p
 Cone Tweeter 8 or 15 ohm, 10 watt £3.68
 Cone Tweeter 8 ohm, 3 watt £1.93
 Horn Tweeter 8 ohm, 20 watt £8.72
 Dome Tweeter 8 ohm, 30 watt £7.18
 Crossovers CN23 (3 ohm) CN28 (8 ohm), CN126 (16 ohm) £1.75

SPEAKERS P&P 45p
 EMI 13" x 8", 3, 8 ohm plain £3.75
 6 1/2" 8 ohm, 10 watt £4.06
 8" x 5" C. Mag. 5 watt 8 or 15 ohm £2.62
 8" x 5" Dualcone 8 ohm, 10 watt £4.12
 Elac 6 1/2" 8 ohm Dualcone £3.96
 8" 8 ohm Dualcone £3.37
 Baker Group 25 12", 8 or 15 ohm £15.00
 Goodmans 8" x 5" 8 ohm £2.12
 Global 8 ohm 5 watt (pair) £9.93
 Richard Allan 12" 90 watt 8 or 15 ohm £12.95
 Richard Allan 12" Dualcone £13.95

CARTRIDGES & STYLII P&P 25p
 Acos GP91/2SC or 3SC (ster. comp) £1.60 £1.20
 GP93/1 or 95/1 ster. cryst £2.00 £1.20
 GP94/1 or 96/1 ster. ceram. £2.00 £1.20
 GP101 cryst. comp. £1.00 —
 GP104 ster. ceram. £2.15 £1.20
 BSR XM5 or H5X cryst. comp. £1.65 £1.20
 SX6M or SX6H cryst. ster. £2.25 £1.20

SC5M ster. ceram. £2.75 £1.20
Sonosone
 9TAHC or 9TAHC G (Diam) £2.25 £1.20
 3509 ster. ceram. £2.25 £1.20
 Audio Technica AT55 £2.25 —
 Empire 999 REX £4.95 —
 Goldring G850 £3.50 £1.75
 G800 £5.25 £1.75
 G800H £5.25 £1.75
 G800E £9.06 £3.50

Shure Carts & Styli
 M44G £6.18 £4.93
 M55E £7.81 £6.18
 M75ED Type 2 £14.68 £10.31
 M75EJ Type 2 £12.18 £7.81

MICROPHONES P&P 25p
 CM70 Planet stick metal, switch crystal £2.12
 DM160 Dynamic omni-dir. ball metal £6.18
 UD13050K 600 ohm, uni-dir, ball metal £7.31
 CONDENSER MIKE 600 ohm, uni-dir. £10.62
 Cassette STICK MIKE with R Control on/off switch (2.5 & 3.5 mm) J/PLY £1.56
 Cassette STICK MIKE with R/Control (Phillips Type) £1.97

BATTERY ELIMINATORS P&P 25p
 240v input 6, 7.5 or 9 volt output £2.75
 12v d.c. input (specify output 6, 7.5 or 9 d.c.) at 300mA £4.62

CASSETTES P&P 25p

Type	Low noise	Phillips	Memorex
C50	37p	59p	81p
C90	48p	81p	£1.18
C120	59p	£1.18	£1.67

CASSETTE CASES
 Cassette Head Cleaner £0.48
 B18 Stereo Test Cassette £2.32
 AMPEX Head Cleaner Demag £1.99

TAPES P&P 25p

5"	5 1/2"	7"	Stand.	LP	DP	Cases
59p	70p	82p	£1.08	£1.08	£1.08	32p
59p	70p	82p	£1.19	£1.19	£1.19	32p

SINCLAIR PROJECT 80 P&P 25p
 Stereo Pre-amp £16.18
 Active Filter Unit £9.95
 Z40 15 watt Amp. £7.18
 Z60 25 watt Amp. £9.06
 P25 Power Supply for 240 £6.81
 P26 Power Supply for 240 £10.56
 P28 Power Supply for 260 £10.31
 FM Tuner £16.18
 Q16 Speaker £9.31
 IC20 stereo amp. kit £9.37
 PZ20 Power kit £6.56

Send 25p for complete catalogue.

PLEASE BRING THIS ADVERTISEMENT TO OBTAIN THE BENEFIT OF THESE SPECIAL PRICES


ALL MERCHANDISE FULLY GUARANTEED

NEWMART ELECTRONICS

Mail Order Dept | PW6
 Belmont St, Monton,
 Eccles, Manchester.
 Tel: 061-789 5268

Manchester
 30-32 Shudehill. tel 061-832 7710
 Leeds
 4 New Market St tel 0532 42708
 Liverpool
 15 Whitechapel tel 051-236 0738

The good old days are here again

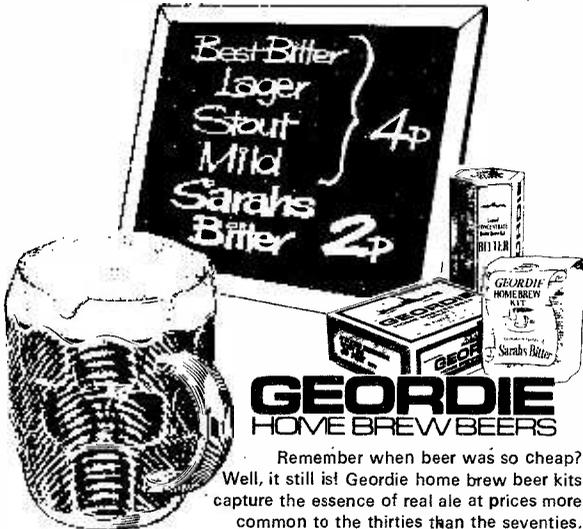


GEORDIE HOME BREW BEERS

Remember when beer was so cheap? Well, it still is! Geordie home brew beer kits capture the essence of real ale at prices more common to the thirties than the seventies. Brew your own Mild, Bitter, Lager, Stout - so easily, and so cheaply. Try Sarah Oliver's Bitter too. 40 satisfying pints for 68p - ideal for parties, as well as private enjoyment.

From most chemists, large Woolworth branches, Westons, Health/Homebrew shops or direct -


VIKING BREWS LIMITED, 28/29 CLIVE STREET, NORTH SHIELDS, TYNE & WEAR

Practical Wireless, June 1976

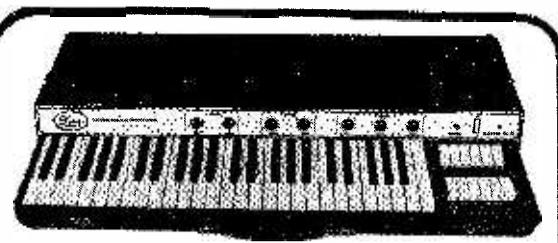

BUILD YOUR OWN DIGITAL ORGAN OR TOUCH SENSITIVE PIANO

SEND S.A.E. FOR FREE LEAFLETS

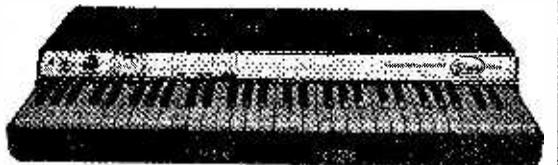

*** COMPONENTS ON SPECIAL OFFER!** 4-Octave keyboard C-C £15.50. 5-Octave keyboard C-C and F-F £20.00. Top octave tone generator complete with transpose control, GU500 £12.95. Top octave tone generator and divider unit complete with transpose control, GD500 £35.00. Construction manual for portable organ using discrete components £2.25. Catalogue 60p. Prices include VAT

ELVINS ELECTRONIC MUSICAL INSTRUMENTS

Organ Centre: 12, Brett Rd., Hackney, London, E8 1JP. 01-986 8455
 NEW ELECTRONIC COMPONENT SHOP AT DALSTON JUNCTION
 40/42a, Dalston Lane, Hackney, London, E8 2AZ. 01-249 5624.

DESIGNED BY TEXAS



Texan Amplifier as featured by PRACTICAL WIRELESS SOLE U.K. DISTRIBUTORS - HENRY'S

Build it yourself for only

£32 KIT PRICE INC. VAT + £1.00 p&p, Built and tested £42.00 inc. VAT + £1.00 p&p

Build the Texan stereo amplifier, then you can be doubly proud! For a start, you'll own a superb home entertainment unit. And have had all the pleasure of doing it yourself, with the Henry's kit.

Look at the Texan specification

Incorporating fully integrated stereo preamp and power amp, with 6 IC's, 10 transistors, 6 rectifiers and zener diodes. Plus stabilised, protected circuitry, glass fib pcb; Gardnet's low-field low-line mains transformer; all facilities and controls. Slim design, chassis 14 1/2" x 6" x 2" overall, 20 watts per channel RMS, less than 0.1% distortion at 1 kHz.

* Can be built stage by stage Ask for leaflet S.
* Everything necessarily supplied. Full after sales service and guarantees.

TEXAN FM TUNER KIT **£23.50** inc. VAT + 50p p&p

Built and tested £28.50 inc. VAT + 50p p&p.

Build the matching Texan stereo tuner! Features advanced varicap tuning. Phase lock loop decoder. Professionally designed circuit. Everything you need is in the kit. From the glass fibre pcb to the cabinet itself. Excellent spec: 2.5 uV aerial sensitivity, 500 mV output (adjustable). Tuning range 87-102 MHz. Mains powered.

THE NATURAL FOLLOW-ON

Henry's latest ELECTRONICS CATALOGUE

- * over 5000 items - many new
- * free 50p voucher inside every copy
- * virtually everything needed by amateurs and professionals
- * over 200 pages
- * easy-to-use, complete alphabetical index section
- * everything at competitive prices

FREE to Educational Establishments when ordered on official headed notepaper

VIDEO SPORT



An up-to-the-minute game. Plug into your own TV aerial socket. Switch on. And you're away! Choose your game - Football, tennis or hole-in-the-wall. Absolutely safe. For you. Your children. And your TV. Mains powered. List Price £42.50

HENRY'S PRICE **£29.50** inc. VAT + 50p p&p

* OVER 10,000 ALREADY SOLD
* IDEAL GIFT

For this latest edition, we have made hundreds of changes and additions. Features now include:

TRANSISTOR & VALVE DISCOUNT PRICE LIST over 2000 types SEND FOR YOUR FREE COPY

All mail to: Henry's Radio 303 Edgware Rd, London W2

HENRY'S RADIO

LONDON W2: 404-5 Edgware Road. Tel: 01-402 8381
LONDON W1: 231 Tottenham Ct Rd. Tel: 07-636 6681
BOTTINGHAM: 94-96 Upper Parliament St. Tel: 066021 40463
READING: BERKS: 130/131 Friar Street. Tel: 07247 583230
HARROW: 100-4 Station Road. Tel: 01-863 7783
CROYDON: 110 North End. Tel: 01-681 3310

Please Note: MAIL ORDER CUSTOMERS VAT DOWN HENRY'S WILL CREDIT ANY VAT OVERPAYMENTS

AIRCRAFT H.F. Rx type R4187 & Control box these are a crystal controlled Rx intended for remote control & will provide up to 24 channels in the range 2.8 to 18Mc/s the Rx is a dual conversion type with I.F.s of 2.15Mc/s & 100Kc. as 2 RF stages, RT & C.W. filters, BFO, N.L. O/P stage etc uses 16 B7g valves, normal power I/P 24 & 19 v DC or 200v ht & 19v uses Hc6/u crystals not supplied, with C/Bx & manual **£16.20. TAPE DECKS & AMPS** standard BSR type TD.2 tape deck with transistor amps, erase osc & mixer o/p circs, spool type deck speed 3 3/4" these units are complete except for power unit req 24v DC smoothed & mains. These are a two chan unit the O/Ps from both tracks being combined in a mixer stage & provide o/p for phones, the deck & circ boards are mounted on a plywood base size 23 x 14" units are in clean conds with circs but not tested **£9.50**, also similar unit but valve circs reqs ext 250v & 6.3v on plinth size 17 x 13" **£6.50. MAINS TRANS** all C core types 240v new L.T. type 13.4v 3a, 10v 3a & 6.3v 2a **£3.50**. H.T. types 330-0-330 at 85Ma. 6.8 3a & 6.3 1.5a **£4**. 600-0-600 250Ma. 290-0-290 66Ma & 80-0-80 60Ma twic **£5.50. POWER UNIT** sub ass 240v I/P o/p 18v DC smoothed at 500Ma **£2.50. MOTOR** 240v ex tape deck with clutch & friction drive **£1.30. CRYSTAL FILTERS** all 10.7Mc/s size 38 x 16 x 18mm 30Kc b.w. **£1.30**. 15 & 12Kc b.w. **£1.60** all new. **SIGNAL GENERATORS** for 115v 50c/s 100Kc to 120Mc/s in 10 bands, int mod & xtal check with leads circ inst book in case good cond not tested **£16. TWO CHAN AMPS** circ board 6 x 5" with transis amps ex tape rec. suitable rec or playback amps with o/p stage for phones with circ **£1. INDICATOR UNIT** with CRT 3BP1 3" green trace, 34x octal valves, 100Kc crystal unit, as 4 chan Rx tunes 1.8 to 2Mc/s with RF & 2 IF stages complete in neat case size 20 x 12 x 8" with circ, I/P 115v 400c/s **£13.50. CRYSTAL OVENS** with 12 type Hc6/u holders can be removed **£1.20. JOY STICK** control units operate 4 micro swts fully enclosed complete may need attention **£2. STRIPPER UNIT** application not known contains DC motor 28v rated 1/2 H.P. at 8800 RPM with control relay & heavy gears **£8.50. CONTROL BOX** for use with aircraft nav Rx as provision for 24 type Hc6/u crystals two per chan gives two O/p's in 30/40Mc/s range with circ & crystal data **£2.20. CABINETS** bench mounting type overhaul size 41" long 27" high 15" deep with sloping front, removable panels Ali construction store soiled otherwise okay **£15.20. CABLE** 24 core ea core screened & colour coded approx 5/8th OD new 5 meters for **£1.50**.

Above prices inc carr/postage & V.A.T. goods are ex equip unless stated new, SAE for list or enquiry. Shop open Tues to Sat.

A. H. SUPPLIES

122, HANDSWORTH RD., SHEFFIELD S9 4AE Ph. 44278 (0742)

BI-PRE-PAK

Bargains in Semi-Conductors, components, modules & equipment.

B-P-P Packs

Originated in 1959 by managing director Bernard Davis, his were the first semi-conductor and component packs to be marketed in this country, and indeed, the company's name grew out of "British Industrial Pre-Pack Components". Today, Bi-Pre-Pak continues to occupy a position of pre-eminence in the supply of packs as well as a vastly extended range of products detailed in our latest 24 page A-4 size free catalogue. Send 10p stamped large addressed envelope for your copy by return.

IT'S ALL IN OUR FREE CATALOGUE

Component Packs

- CP1 150 Capacitors, mixed bag of paper, silver mica, electrolytics, etc. Approx. quantity, counted by weight. **60p**
- CP2 200 Resistors, mixed bag of different types, values, wattages, etc. Approx. quantity, counted by weight. **60p**
- CP3 40 Wirewound resistors, mixed types, values and wattages. **60p**
- CP4 12 Potentiometers, pre-sets, w/wound, carbon, etc. Mixed types and values. **60p**
- CP5 5 Earphones, single low impedance for transistor radios, cassettes etc. Less plugs, for suitable plugs see PAKs CP9 and CP10. **60p**
- CP6 50 TO-5 mounting pads, fits between transistor and board, for that pro. finish. **60p**
- CP8 500 Cable clips for G.P.O. 1/4" dia. cable. Nylon with hardened steel pin (probably tungsten) per sealed box of 500. **60p**
- CP9 5 3.5mm plugs, miniature jack, to fit earphones in PAK CP5. **60p**
- CP10 5 2.5mm sub miniature jack plugs, to fit earphones in PAK CP5. **60p**
- CP11 6 Screwdrivers, 1 mains neon tester, 5 x grub screwdrivers. **60p**
- CP12 10 Reed relay inserts, 1" long 1/4" dia. These will operate from an external magnet or coil. For magnets see PAK CP13. **60p**
- CP13 10 Magnets of various sizes for operating reed switches in PAK CP12. Ideal for burglar alarms on doors and windows etc. **60p**
- CP14 40 Potentiometers, presets, wirewounds, carbons, dual gangs, with and without switches etc. Mixed values and wattages **£1.20**
- CP15 12 Standard crocodile clips, screw fixing, good quality. **60p**
- CP16 5 P.C. boards each containing a BF180 UHF amplifier transistor. A good basis for building a T.V. aerial pre-amp as various parts inc. **60p**
- CP17 25 Electrolytic Capacitors, various values and voltages, many useful types, from T.V. to transistor radio & Hi-Fi **60p**
- CP18 1 Light activated SCR.50 volts 1-6 amps type 13F. Ready mounted on PC board with gate resistor and leads fitted. Full data and circuit diagrams for 14 projects, includes: slave photo flash unit, burglar alarm etc. **60p**
- CP19 3 Micro switches 1 pole change over. standard model 1 1/2 x 3/4". **60p**

Semi-Conductors

TESTED AND GUARANTEED

TP4 3 SN7490 integrated circuits, 14 pin dual in line TTL type. Decade counter. Get one FREE these are 60p each in singles. **£1.20p***

ALL THE FOLLOWING ARE AT 60p EACH PACK
 TP9* 5 SN7400 integrated circuits, 14 pin dual in line TTL type. Quad 2-input NAND gate. Get one FREE, these are 15p/each.

- TP10 2 Light dependant resistors. 400 ohms light, 1 megohm dark. 1/2" dia.
- TP11 10 Transistors XB102 and XB112 equivalent to AC125, AC156, OC81/2, OC72 etc.
- TP12* 4 BY127 Silicon rectifiers 1000 pIV 1 amp. Plastic T.V. rectifier.
- TP13* 5 OC71 Light sensitive transistors.
- TP14 20 OC71 germanium PNP audio pre amp transistor, black glass type.
- TP15 20 OC81 germanium PNP audio output transistor, white glass type.
- TP16 20 OC200/1/2/3 transistors, PNP silicon TO-5, unmarked.
- TP17 20 1 watt zener diodes, mixed voltages. 6-8 to 43 volts.
- TP18 20 2N3707/8/9/10 transistors, NPN silicon plastic, unmarked.
- TP19 100 Diodes, mixture of germanium, gold bonded, silicon, etc., a useful selection of many types, marked and unmarked.
- TP20 10 Multi OC45 transistors, I.F. amp. PNP germanium.
- TP23 20 BFY50/1/2, 2N696/7, 2N1613, etc. NPN silicon IO-5 uncod. COMPLEMENTARY TO PAK TP24.
- TP24 20 BFY64, 2N2904/5, etc., PNP silicon TO-5 uncod. COMPLEMENTARY TO PAK TP23.
- TP30 20 NPN silicon planar transistors, TO-18 similar to BC108 etc. uncod.
- TP31 20 PNP silicon planar transistors. TO-18 similar to BC178 etc. uncod.

UNTESTED PACKS—60p EACH

- UT1 50 PNP germanium transistors, AF and RF. Very good yield.
- UT2 150 Germanium diodes, miniature glass type.
- UT5 40 Zener diodes, 250 mW OAZ240 range, average 50% good.
- UT6 25 Zener diodes, 1-1 1/2 watt top hat type, mixed voltages.
- UT9 40 NPN silicon planar transistors, of the 2N3707-11 range, low noise amp.
- UT10 15 PNP transistors, PNP germanium and NPN silicon, mostly TO-3 but some plastic and some marked.
- UT13 15 Integrated circuits, experimenters pak, dual in line, TO-5, TTL, DTL, marked and unmarked, some definitely good but old types.

FOR FULL RANGES—SEE CATALOGUE

BRIDGE RECTIFIERS Plastic encapsulated

- F.1.V. 50v 100v 400v
- 1 amp 25p* 35p* 45p*
- 2 amp 35p* 45p* 55p*
- 4 amp 45p* 50p* 80p*
- 6 amp 50p* 60p* 90p*
- BY164 equiv. SKB2/02 400v 1.5 amp. 45p*

FETs

- 2N3919 18p
- 2N4416 20p

MOS F.E.T.s

- 3N141/MEM616 50p

UNI-JUNCTION TRANSISTORS

- 2N2160 65p*
- 2N2946 45p*
- TIS43 31p*

PUTs

- 2N26027 50p

LEDs

- TIL209—Red 18p*
- TIL211—Green 33p*

Also Power Diodes, Thyristors, Triacs, Diac Zener Diodes, Opto-Electronics, etc.

VAT NOW 12% EXCEPT ITEMS MARKED * AT 8%.

POWER TRANSISTORS

	Vce	Watts	1c Amps	Price
40P1	15	20	3	20p*
40N2	40	40	4	30p*
40P2	40	40	4	30p*
90N1	15	45	4	25p*
90P1	15	45	4	25p*
90N2	40	90	8	35p*
90P2	40	90	8	35p*

Many other types available from 3 to 115 watts

INTEGRATED CIRCUITS

MM5314 Dual in line clock chip **£3***
 LMS380/SL60745 Dual in line 2w. audio amp. with data, etc. **75p**
 Dual in line I.C. sockets 8 pin 14p; 14 pin 15p*; 16 pin 16p*

Sundry

SIGNAL GENERATOR

For MW and IF Covers 550 KHz to 1.6 MHz for MW and 400 to 550KHz for IF. Fully portable. (p/p 40p) **£4.25***

POCKET SIGNAL INJECTOR

Fountain-pen type. Invaluable for finding faults **£2.00***

EX-G.P.O. 5" SIDECUTTERS

Not new, but in perfect order, per pair **50p***

EX-G.P.O. 6" LONG NOSE PLIERS

Not new, but in perfect order, per pair **60p***

MAINS TRANSFORMERS

MT6	6v 0.6v 100mA	£1.22*
MT12	12v 0 12v 50mA	£1.22*
SS19/1	9v 1amp	£1.67*
SS121/1	12v 1amp	£2.65*
SS118/1	18v 1amp	£2.50*
SS125/2	25v 2amp	£3.00*
SS130/2	30v 2amp	£4.25*
SS135/4	35v 4amp	£5.50*

PC EDGE CONNECTORS

Type	Size	Pitch	Price
SSEC 6 way	1 1/2"	.156"	32p
SSEC 10 "	1 1/2"	.156"	50p
SSEC 12 "	2"	.156"	60p
SSEC 16 "	2 1/2"	.156"	75p
SSEC 18 "	3"	.156"	85p
SSEC 22 "	3 1/2"	.156"	1.00

BOOKS

All free of V.A.T. We carry very large stocks of technical books by Babani & Bernard Publishers, by Newnes and Butterworth as well as reference books from the Common Market in English/German/Italian. All detailed in our catalogue.

MONEY SAVERS FOR MOTORISTS

Our new "Super Spark" Capacity Discharge Ignition unit is instantly adaptable for pos. or neg. earth; can be switched back to conventional ignition instantly and incorporates anti-burglar immobilising switching. Rev. limiting adjustment. In totally enclosed strong metal box (p/p—50p)

KIT—£7.95* READY BUILT £10.50*

"A VERY GOOD INVESTMENT

INDEED" says Practical Wireless. May issue, reviewing this unit "It worked first time. Is it a good buy? It certainly is!"

B-P-P SECURITY CHECK POINT

Write your own name and address clearly in block capital letters. **MAKE SURE YOU GET OUR NAME AND ADDRESS RIGHT**

Check that your order is correct for description, quantity and price. **WHEN ORDERING**

Don't forget V.A.T. at 25% of total value of order unless otherwise stated. **Cash (cheque, money or postal order) with your order, please.**

Terms of Business: VAT at 12 1/2% must be added to total value of order, except for items marked * or (B%) when VAT is to be added at 8%. No VAT on overseas orders. **POST & PACKING** Add 30p for UK orders except where shown otherwise. Minimum mail order acceptable—£1. Overseas orders, add £1 for postage. Any difference will be credited or charged. **PRICES** Subject to alteration without notice. **AVAILABILITY** All items available at time of going to press when every effort is made to ensure correctness of information.

V.A.T. charged at rates effective at time of despatch of goods.

To BI-PRE-PAK, 224-226 WEST RD., WESTCLIFF-ON-SEA, ESSEX

Please send

for which I enclose

Name

Address

..... PW:6A



BI-PRE-PAK LTD

222-226 WEST ROAD, WESTCLIFF-ON-SEA, ESSEX SSO 9DF.

TELEPHONE: SOUTHEND (0702) 46344.

WRITE ORDER SEPARATELY AND ATTACH COUPON IF REQUIRED

15-240 Watts!

HY5 Preamplifier

The HY5 is a mono hybrid amplifier ideally suited for all applications. All common input functions (mag Cartridge, tuner, etc) are catered for internally. The desired function is achieved either by a multi-way switch or direct connection to the appropriate pins. The internal volume and tone circuits merely require connecting to external potentiometers (not included). The HY5 is compatible with all I.L.P. power amplifiers and power supplies. To ease construction and mounting a P.C. connector is supplied with each pre-amplifier.

FEATURES: Complete pre-amplifier in single pack—Multi-function equalization—Low noise—Low distortion—High overload—Two simply combined for stereo.

APPLICATIONS: Hi-Fi—Mixers—Disco—Guitar and Organ—Public address

SPECIFICATIONS:

INPUTS: Magnetic Pick-up 3mV; Ceramic Pick-up 30mV; Tuner 100mV; Microphone 10mV;

Auxiliary 3-100mV; input impedance 4-7k Ω at 1kHz.

OUTPUTS: Tape 100mV; Main output 500mV R.M.S.

ACTIVE TONE CONTROLS: Treble \pm 12dB at 10kHz; Bass \pm at 100Hz.

DISTORTION: 0-1% at 1kHz. Signal/Noise Ratio 68dB.

OVERLOAD: 38dB on Magnetic Pick-up. **SUPPLY VOLTAGE** \pm 16-50V.

Price £4.75 + £1.19 VAT P&P free.

HY30

15 Watts
into 8 Ω

The HY30 is an exciting New kit from I.L.P. It features a virtually indestructible I.C. with short circuit and thermal protection. The kit consists of I.C., heatsink, P.C. board, 4 resistors, 6 capacitors, mounting kit, together with easy to follow construction and operating instructions. This amplifier is ideally suited to the beginner in audio who wishes to use the most up-to-date technology available.

FEATURES: Complete Kit—Low Distortion—Short, Open and Thermal Protection—Easy to Build

APPLICATIONS: Updating audio equipment—Guitar practice amplifier—Test amplifier—audio oscillator.

SPECIFICATIONS:

OUTPUT POWER 15W R.M.S. into 8 Ω ; **DISTORTION** 0-1% at 1-5W.

INPUT SENSITIVITY 500mV. **FREQUENCY RESPONSE** 10Hz-16kHz—3dB.

SUPPLY VOLTAGE \pm 18V.

Price £4.75 + £1.19 VAT P&P free.

HY50

25 Watts
into 8 Ω

The HY50 leads I.L.P.'s total integration approach to power amplifier design. The amplifier features an integral heatsink together with the simplicity of no external components. During the past three years the amplifier has been refined to the extent that it must be one of the most reliable and robust High Fidelity modules in the World.

FEATURES: Low Distortion—Integral Heatsink—Only five connections—7 amp output transistors—No external components

APPLICATIONS: Medium Power Hi-Fi systems—Low power disco—Guitar amplifier

SPECIFICATIONS: **INPUT SENSITIVITY** 500mV

OUTPUT POWER 25W RMS into 8 Ω **LOAD IMPEDANCE** 4-16 Ω **DISTORTION** 0-04% at 25W

at 1kHz

SIGNAL/NOISE RATIO 75dB **FREQUENCY RESPONSE** 10Hz-45kHz—3dB.

SUPPLY VOLTAGE \pm 25V **SIZE** 105 50 25mm.

Price £6.20 + £1.55 VAT P&P free.

HY120

60 Watts
into 8 Ω

The HY120 is the baby of I.L.P.'s new high power range. Designed to meet the most exacting requirements including load line and thermal protection this amplifier sets a new standard in modular design.

FEATURES: Very low distortion—Integral heatsink—Load line protection—Thermal protection—Five connections—No external components

APPLICATIONS: Hi-Fi—High quality disco—Public address—Monitor amplifier—Guitar and organ

SPECIFICATIONS

INPUT SENSITIVITY 500mV.

OUTPUT POWER 60W RMS into 8 Ω **LOAD IMPEDANCE** 4-16 Ω **DISTORTION** 0-04% at 60W

at 1kHz

SIGNAL/NOISE RATIO 90dB **FREQUENCY RESPONSE** 10Hz-45kHz—3dB **SUPPLY VOLTAGE**

\pm 35V

SIZE 114 50 85mm

Price £14.40 + £1.16 VAT P&P free.

HY200

120 Watts
into 8 Ω

The HY200 now improved to give an output of 120 Watts has been designed to stand the most rugged conditions such as disco or group while still retaining true Hi-Fi performance.

FEATURES: Thermal shutdown—Very low distortion—Load line protection—Integral heatsink—No external components

APPLICATIONS: Hi-Fi—Disco—Monitor—Power slave—Industrial—Public Address

SPECIFICATIONS

INPUT SENSITIVITY 500mV

OUTPUT POWER 120W RMS into 8 Ω **LOAD IMPEDANCE** 4-16 Ω **DISTORTION** 0-05% at

100W at 1kHz.

SIGNAL/NOISE RATIO 96 dB **FREQUENCY RESPONSE** 10Hz-45kHz—3dB **SUPPLY VOLTAGE**

\pm 45V

SIZE 114 100 85mm

Price £21.20 + £1.70 VAT P&P free.

HY400

240 Watts
into 4 Ω

The HY400 is I.L.P.'s "Big Daddy" of the range producing 240W into 4 Ω ! It has been designed for high power disco address applications. If the amplifier is to be used at continuous high power levels a cooling fan is recommended. The amplifier includes all the qualities of the rest of the family to lead the market as a true high power hi-fidelity power module.

FEATURES: Thermal shutdown—Very low distortion—Load line protection—No external components.

APPLICATIONS: Public address—Disco—Power slave—Industrial

SPECIFICATIONS

OUTPUT POWER 240W RMS into 4 Ω **LOAD IMPEDANCE** 4-16 Ω **DISTORTION** 0-1% at

240W at 1kHz.

SIGNAL NOISE RATIO 94dB **FREQUENCY RESPONSE** 10Hz-45kHz—3dB **SUPPLY VOLTAGE**

\pm 45V

INPUT SENSITIVITY 500mV **SIZE** 114 x 100 x 85mm

Price £29.25 + £2.34 VAT P&P free.

POWER SUPPLIES

PSU36 suitable for two HY30's £4.75 plus £1.19 VAT. P/P free.

PSU50 suitable for two HY50's £6.20 plus £1.55 VAT. P/P free.





PSU70 suitable for two HY120's £12.50 plus £1.00 VAT. P/P free.

PSU90 suitable for one HY200 £11.50 plus £0.92 VAT. P/P free.

TWO YEARS' GUARANTEE ON ALL OF OUR PRODUCTS

I.L.P. Electronics Ltd.
Crossland House
Nackington, Canterbury
Kent CT4 7AD
Tel. (0227) 63218

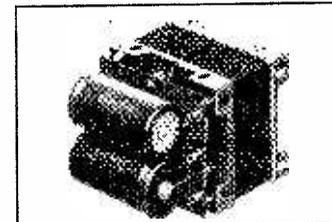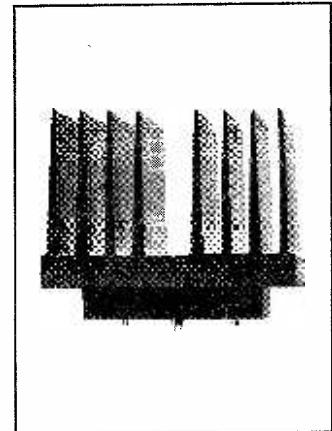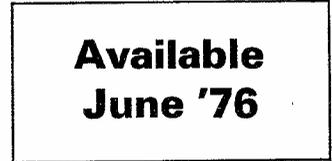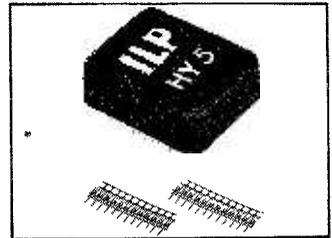Please Supply _____
Total Purchase Price _____
I Enclose Cheque Postal Orders Money Order
Please debit my Access account Barclaycard account
Account number _____
Name and Address _____
Signature _____



CRESCENT RADIO LTD.

11-15 & 17 MAYES ROAD, LONDON N22 6TL
(also) 13 SOUTH MALL, EDMONTON, N.9

MAIL ORDER DEPT.
1 ST. MICHAELS TERRACE, WOOD GREEN,
LONDON N22 4SJ Phone 888-4474

CLEAR PLASTIC PANEL METERS

Size 59mm x 46mm x 35mm these meters require a 38mm hole for mounting.
ME6 = 0 to 50 micro amp Full Scale
ME7 = 0 to 100 micro amp Full Scale
ME8 = 0 to 500 micro amp Full Scale
ME9 = 0 to 1 mA Full Scale
ME10 = 0 to 5 mA Full Scale
ME11 = 0 to 10 mA Full Scale
ME12 = 0 to 50 mA Full Scale
ME13 = 0 to 100 mA Full Scale
ME14 = 0 to 500 mA Full Scale
ME15 = 0 to 1 amp Full Scale
ME16 = 0 to 50 volts
ME17 = 0 to 300 volts
A.C. Full Scale
ME18 = "8" Meter
ME19 = "VU" Meter




OUR PRICE £3.00
+8%

BARGAIN PROJECT BOX.

A plastic box with moulded extrusion rails for PC or Chassis panels with metal front plate fitted with four screws (all supplied).

An ideal box to give a small project a professional finish
SIZE (Internal) 81mm x 51mm x 28mm.

OUR PRICE
40p. +8%

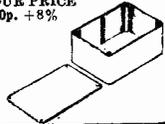

WAVER SWITCHES

- 1 Pole 12 Way
- 2 Pole 2 Way
- 2 Pole 3 Way
- 2 Pole 4 Way
- 2 Pole 6 Way
- 3 Pole 4 Way
- 4 Pole 3 Way



30p each +8%

SCOOP PURCHASE MW-LW-LM STEREO TUNER

We supply a MW-LW-LM Stereo Tuner fully wired and aligned on a 6" x 4" x 1 1/2" printed board, plus the Ferric Aerial and switch which you connect following our complete instructions.
Now you only need a 9-12 volt D.C. supply and you can feed this tuner into any Stereo Amplifier.

FANTASTIC VALUE AT £7.00+12% VAT

MINIATURE RELAYS

Brand new range of British made Relays. Size 1 1/2" x 1" x 1/2". All two changeovers with 250V 1.5A contacts and suitable for fitting on 'Im Veroboard'.

Type Volts Cur. Ohms
rent
27/A 12v 17M/A 700
21/A 12V 28M/A 430
12/A 6v 33M/A 185
All £1.30 each

POWER SUPPLY UNITS +8%



PP1 switched 3, 4, 6, 7, 9 and 12 volts at 500 mA, with on/off switch and pilot light. Size: 130mm x 55mm x 75mm.
ONLY £4.50

PP2 Switched 6-7-9 volt Battery Eliminator. Approx. size 2 1/2" x 3 1/2". Ideal for cassette recorders £3.25 PP3 Car converter. From 12v Pos. or Neg. to =6-7-9 volt. Easy to fit and transistor regulated £3.95

LOW VOLTAGE STEREO AMPLIFIER

8 Transistor Stereo Amplifier with Vol. Base, Balance and Tone Controls. Approx. 3 watts into 8 ohm per channel needs a 9/12 volt DC supply and is complete on a 2 1/2" x 7 1/2" P/F board.
Ideal for domestic record players, etc. A Bargain at £5+12% VAT.

ABS PLASTIC BOXES +8%

E handy boxes for construction projects. Moulded extrusion rails for P.C. or chassis panels. Fitted with 1mm front panels.
1005 = 105mm x 73mm x 45mm = 55p
1006 = 150mm x 75mm x 47mm = 72p
1007 = 184mm x 124mm x 80mm = £1.28
1021 = 108mm x 74mm x 45mm (sloping front) = 55p

TELESCOPIC AERIAL

Nine section fully swivelling telescopic aerial with 4BA single bolt fixing or two hole fixing bracket. Fully extended = 43". Fully closed = 7".
Our Price 50p + P/F + VAT @ 12 1/2%

LOW NOISE LOW PRICE CASSETTES +8%

Good quality tape in well made serret type cassettes. Presented in single plastic cases.
C60 = 33p C90 = 48p C120 = 60p
10% Discount on ten or more cassettes of one type

LOUDSPEAKERS +25%

2 1/2" 8 ohm 60p
2 1/2" 40 ohm 60p
2 1/2" 80 ohm 80p
5" 8 ohm ceramic £1.25



10-INCH 8 OHM DUAL CONE
Manufactured by "BLAC" to a very high standard these loudspeakers are a real bargain
SPEC: Size = 10" Dual Cone.
Power = 10 Watts
Frequency = 40-12000Hz
+12% Our Price = £3.75p each

U.K. CARRIAGE 50p UNLESS OTHERWISE STATED

VAT—All prices are excluding VAT. Please add to each item the VAT rate indicated.

TRANSFORMERS

MAINS SAFETY ISOLATING Primary 240V. Sec. 150V or 240V.
Please state which type you require.
All types are screened and Centre tapped to earth.

V.A. (watts)	OPEN TYPE		P. & P.		CASED TYPE	SOCKETS 5 amp 15 amp	CARRIAGE	PLUGS FOR CASED TYPE complete set
	£	£	£	p				
50	3-98		62					
100	4-53		70					
200	7-26		80					
250	8-80		1-10					
350	10-59		1-18					
500	12-18		1-34		23-25	1	—	O.A. 1-20
750	18-65		O.A.		30-80	1	—	O.A. 1-20
1000	26-00		O.A.		37-77	2	—	O.A. 2-40
1500	29-65		O.A.		44-30	3	—	O.A. 3-60
2000	35-00		O.A.		51-85	1	1	O.A. 2-70
3000	55-00		O.A.		75-35	3	1	O.A. 5-10

CASED TYPES These are of extremely high quality to British Standard Specification, with resettable fused primary winding, and are fitted with covered outlet sockets. Housed in steel cases with carrying handles and 3ft of 3 core cable.

12V or 24V				MINIATURE TRANSFORMERS			
Primary 240V				Primary voltage 240V			
Please state which		voltage		Sec. volts		mA	
AMPS	PRICE	P & P	PRICE	PRICE	P & P	PRICE	P & P
12V	24V	£	p	3-0-3	200	1-37	25
5	25	1-30	26	0-6 x 2	1A	1-80	45
1	5	1-58	45	0-9 x 2	330	1-34	26
2	1	2-05	45	0-9 x 2	500	1-83	45
4	3	2-52	62	0-9 x 2	1A	2-60	52
6	3	3-76	62	0-15 x 2	200	1-30	25
8	4	4-30	85	0-20 x 2	300	1-72	52
10	5	4-67	85	0-20 x 2	1A	3-08	72
12	6	4-93	98	0-15-27 x 2	1A	3-86	72
16	8	6-35	1-20				
20	10	9-27	1-20				

QUANTITY DISCOUNTS 1 to 24 off Basic Price 250 to 499 off 15% off
25 to 49 off 2 1/2% off Price 500 to 999 off 20% off
50 to 99 off 5% off Price 1,000 to 1,999 off 25% off
100 to 249 off 10% off Price 2,000 and over 30% off

We manufacture Power Transformers to customers own special requirements, please send details of any Transformer you may require custom built. All queries must be accompanied by S.A.E.

PLEASE ADD 8% V.A.T. TO TOTAL PRICE

S. G. Wright's Ltd., Bishop House Works, Rylands St.,
BURNLEY, Lancs. BB10 1RG Tel. 26934

ELECTROVALUE

the good components service

In relatively few years, Electrovalue has risen to a position of pre-eminence as mail-order (and industrial) suppliers of semi-conductors, components, accessories, etc. There are wide ranges and large stocks to choose from as well as many worthwhile advantages to enjoy when you order from Electrovalue.

CATALOGUE 8-ISSUE 2

With the first printing sold out, Issue No. 2 is up-dated on prices, etc. 144 pages. New items. Opto-electronics. Diagrams of components, applications, I.C. circuits, etc. Post free 40p, including voucher for 40p for spending on order over £5 list value.

DISCOUNTS

On all C.V.O. mail orders, except for some items marked NETT.
5% on orders list value 10% on orders list value
5% on £10 or more 10% on £15 or more

FREE POST & PACKING

On all C.V.O. mail orders in U.K. over £2 list value. If under, add 15p handling charge.

PRICE STABILIZATION POLICY

Prices are held and then reviewed over minimum periods of 3 months—Next price review due July 1st 1976.

QUALITY GUARANTEE


On everything in our Catalogue—No manufacturer's rejects, seconds or sub-standard merchandise.

ELECTROVALUE LTD

All communications to Dept. 6/1, 28, ST. JUDES ROAD, ENGLEFIELD GREEN, EGHAM, SURREY TW20 0HB. Telephone Egham 3603, Telex 284475. Shop hours 9-5.30 daily, 9-1 pm Sats.

NORTHERN BRANCH: 680, Burnage Lane, Burnage, Manchester M19 1NA. Telephone (061) 432 4945. Shop hours Daily 9-5.30 pm; 9-1pm Sats.

INVERTORS

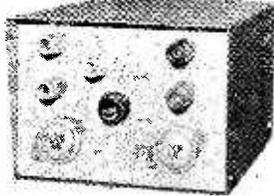

240v-50Hz from your 12v car battery
 25 watt-£4.75 300 watt (12v)-£33.08
 40 watt-£8.27 400 watt (24v)-£39.05
 75 watt-£12.03 500 watt (24v)-£48.18
 150 watt-£21.27 1 Kw (50v)-£127.80
 300 watt (24v)-£26.45 1.5 Kw (110v)-£140.80

All above Invertors are in kit form but may be purchased built up in metal case and ready for use. Price list sent on receipt of s.a.e. Prices include p. and p.

P.W. AUTOMATIC EMERGENCY SUPPLY

240v-50Hz-150 watt Inverter with built in battery charger. In event of power failure switches over automatically from battery charging to inverter operation. Cct. as appeared in Dec. 72 P.W. Complete kit of parts (excluding meter) £24.50 plus £1.70p.p.


FLUORESCENT LIGHT INVERTER KIT

8 watt-12v-Fluorescent light, suitable for tents, caravans, houses, boats and secondary lighting for factories, hotels, &c.
 12"-8 watt £3.90 + 35p p. & p. Built up £4.90 + 35p p. & p.
 21"-13 watt £4.20 + 52p p. & p. Built up £5.80 + 52p p. & p.

TRANSFORMERS AND COILS

Both high volume and small order capacity available.
 Special offer. Miniature mains transformer 12-0-12v-6v. A. 35p + 10p p. & p.

ORION STEREO AMPLIFIER

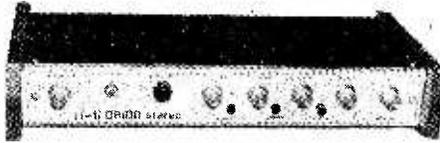

20 + 20 Watts r.m.s. into 8 ohm load. Distortion less than 0.01% 100Hz-10kHz. Frequency response \pm 1dB 20 Hz to 20kHz. Hum level virtually nil with volume full on.

This is a power amplifier of superb quality incorporating the very latest design features. Professional hi-fi enthusiasts have classed it as fantastic and real value for money. The CCT incorporates a low flux transformer and inputs for disc, tape, tuner, etc.


Complete kit of parts including slim line bookend case, silk screened front panel and knobs £47.30 inc. VAT and p. & p.

The bookend case, I.C.'s and semiconductors, P.C. board, Transformer, etc. may be purchased separately if desired. Send S.A.E. for further information.

INSTRUMENT CASES

Bookend Amplifier and attractive styled Instrument Cases available. Send S. and A. envelope for Price List.

ASTRO IGNITION

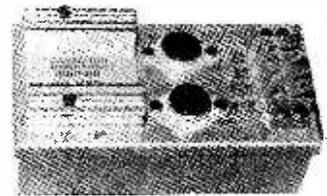

ASTRO IGNITION SYSTEM

Complete kit of parts for this proven and tested system £10.45 inc. VAT Ready built with only two connections to alter £13.75 inc. VAT. Thousands have used this system both home and abroad. Consider these advantages—more power, faster acceleration, fuel economy, excellent cold starting, smoother running, no contact breaker burning. Also because of the high energy spark the fuel mixture can be made weaker giving further economy and fewer plug problems. Fitting time when built 5 minutes approx. Please state whether positive or negative earth.

TRADE AND EXPORT ENQUIRIES WELCOMED ON ALL PRODUCTS

ASTRO ELECTRONICS
 Springbank Road, West Park
 CHESTERFIELD. 31475

MAINS TRANSFORMERS

PRI. 240v sec. 27/0/27v at 800 m/a, £2.35. P.P. 50p.
 PRI. 110/240v sec. 50v at 10 amps, £10.00. P.P. £1.50.
 PRI. 110/240v sec. 20/21/22v at 8 amp, £6.00. P.P. £1.50.
 PRI. 110/240v sec. 23/24/25v at 10 amp, £7.00. P.P. £1.50.
 PRI. 110/240v sec. 24/40v at 1½ amp, £1.90. P.P. 60p.
 PRI. 240v sec. 20/40/60v at 2 amp, £3.80. P.P. 70p.
 PRI. 240v sec. 20v at 2½ amp, £2.00. P.P. 65p.
 PRI. 240v sec. 18v at 1.5 amp and 12v at 1 amp, £2.25. P.P. 50p.
 PRI. 240v sec. 18v at 1 amp, £1.10. P.P. 35p.

12 volt MINI UNISELECTOR

11 way, 4 bank. (3 non-bridging 1 homing) £2.50. P.P. 35p.

24 volt MINI UNISELECTOR

11 way, 6 bank (5 non-bridging, 1 bridging) £2.00. P.P. 35p.

SIEMENS MINIATURE RELAYS

6v 4c/o with base, 65p ea.
 24v 2c/o with base, 50p ea.

MAINS RELAY 240v

3 c/o 10 amp contacts. £1 with base.

MINIATURE RELAYS

(1½ x 1½ x ¾) 24v. 4 c/o 40p

GARRARD PLINTH & COVER

For Zero-100, etc. Finished in brushed aluminium and black, with hinged smoke grey perspex lid, £11.00.

SCR 1 amp 400 P.I.V. 35p.
 5 amp 400 P.L.V. 40p.

EDGE CONNECTOR

54 way -1 vero size etc.
 Can easily be cut to any length 55p. P.P.10p.

CIRCUIT BOARD

P.C.B. 1/161 oz. COPPER

FORMICA

Dim. 8-4 x 7-7 in 3 pcs., 80p.
 Dim. 9-4 x 8-1 in 3 pcs., 90p.
 Dim. 10-1 x 7-9 in 3 pcs., £1.00.
 Dim. 13-1 x 9-4 in 3 pcs., £1.20.
 Dim. 17-0 x 9-0 in 2 pcs., £1.20.

} P.P. 35p

BARGAIN PACK

10 pcs. 10-1 x 7-9 in. Plus free ½lb etching Xtals, £3.10. P.P. 45p.

FIBRE GLASS P.C.B.

Dim. 6 x 6, in 50p each.
 Dim. 12 x 6 in, 75p. each.
 Dim. 12 x 12 in, £1.30 each.
 Equals less than 1p sq.in.

} P.P. 15p

RESIST COATED P.C.B. FIBRE GLASS

6 x 6 in, 65p ea.
 12 x 6 in, £1.20 ea.
 12 x 12 in, £2.00 ea.
 Post & Packing 15p per sheet.

FERRIC CHLORIDE ETCHING XTALS

1 lb makes 1 litre pack, 70p. P.P. 35p.
 5 lb makes 5 litre pack, £2.65. P.P. 65p.

PRINTED CIRCUIT KIT

The no frills all value kit. Containing 4 pcs 8 x 7 Formica laminate, 1 pcs 6 x 6 Fibre glass laminate, 1 lb Etching Crystals, 50 c.c. Resist Ink, with instructions. £2.40. P.P. 65p.

BLUE P.C.B. INK

Etch resist use with any pen. Much cheaper than ready loaded pens.
 50 c.c. 55p. P.P. 10p.

S-DECS AND T-DECS

S-DEC £1.90. T-DEC £3.60. } P.P. 25p.
 U-DEC A £4.20. U-DEC B £6.90.

FIBRE GLASS BARGAIN PACK

200 sq. in. single & double sided pieces, £1.25. P.P. 25p.

OVERLOAD CUT-OUTS

Panel mounting 800 M/A. 1.8 amp. 10 amp. 55p ea.

HIGH CAPACITY ELECTROLYTICS

2500mfd/63 volt, 20p. P.P. 8p.
 1000mfd/100 volt, 70p. P.P. 25p.
 2200mfd/100 volt, 90p. P.P. 25p.
 4700mfd/25 volt, 65p. P.P. 20p.
 6800mfd/ 16 volt, 50p. P.P. 15p.
 10,000mfd/25 volt, 75p. P.P. 25p.
 47,000mfd/40 volt, £2.00. P.P. 50p.
 100,000mfd/10 volt, £1.50. P.P. 50p.
 160,000mfd/10 volt, £2.00. P.P. 50p.

3 GANG TUNING CAPACITOR

8.5pf to 320pf, 80p. P.P. 20p.
 16.7 M.H.Z. canned I.F.s Size 1 x 1½ x 1 in, 65p. P.P. 10p.

MINIATURE METERS

500 micro-amp (level-stereo beacon, etc.), scaled half black/half red. Size 1 x 1 in, 65p. P.P. 15p.

RIBBON CABLE

8 way, 8 colours. Bonded flat side by side.
 10 Metres, £1.90.
 100 Metres, £12.50.

KINNIE COMPONENTS 10 NELMES WAY, HORNCHURCH
 ESSEX RM11 2OZ
 HORNCHURCH 45167

MAIL ORDER ONLY. PERSONAL CALLERS BY APPOINTMENT

barclay

ELECTRONICS

TECHNOLOGICAL
PRECISION PRODUCTS

DECIMO

VATMAN—SCIENTIFIC

Large green display. 8-digits, 2 exponents, 4 trig log functions $10^{\pm 99}$. Radian degrees. Exchange. Memory, π , Reciprocal, X^2 etc. Single Function keyboard, 20 hr battery life. **£25·50**



MINI-VATMAN—Similar to above but slimmer, Green display 8-digits. $\frac{1}{x}$ key. **£8·84**

MINI-VATMAN M—As above but with \sqrt{x} and full-function memory. **£10·70**

VATMAN—8-digit. $\frac{1}{x}$ key. Green display. **£8·84**

SUPER-VATMAN—Similar to above but with full-function memory, X^2 , Reciprocal, π , \sqrt{x} . **£11·58**

SINCLAIR

NEW SCIENTIFIC

Only $1\frac{1}{2}'' \times 2'' \times 1\frac{1}{4}''$. Yet has 8-digits or 5+2 exponents. Using the NEW chip, it has full algebraic logic and many more functions. Algebraic logic is constant on all four arithmetic functions.

FUNCTIONS:

C & CE key
sin ● cos
tan ● arcsin
arccos and tan ● reciprocal ● E to the X ● natural log ● antilog ● memory+ ● memory- ● memory exchange ● memory cancel ● EE exponent ● change notation ● PLUS a degree radian switch.



ONLY

£13·58

OXFORD 300—Larger version of above. **£16·69**

SCIENTIFIC PROGRAMMABLE **£27·45**

CAMBRIDGE **£7·45**

CAMBRIDGE MEMORY— **£9·99**

OXFORD 150— **£8·32**

CBM

4148R—10-digits, 2 exponents. Full log and trig functions, X^2 , Reciprocal, π , X root of Y. Polar rectangular co-ordinates. 2-store memory. Rechargeable. Mean and Standard deviation. **£30·22**



SR1800—Similar to the 4148R. Green display. Battery operated. **£25·60**

796D—8-digits, $\frac{1}{x}$ and store. **£6·27**

997R—Rechargeable $\frac{1}{x}$ and full memory. **£11·62**


including charger.

7919D—Full trig and logs, 8-digit or 5+2 exponents. Reciprocal, π , \sqrt{x} , memory. **£12·55**

ADD 8% VAT TO ALL PRICES + 55p p&p

ROCKWELL

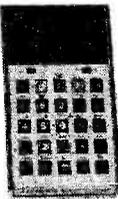61R—8-digit, 2 exponent. $10^{\pm 99}$. Memory. 2-level parenthesis. All trig and log functions. Degree radian. Factorial. Reciprocal. π , \sqrt{x} etc. Rechargeable. **£30·65**



Including recharger.

61R—Green display. 8-digits. All trig and log functions. **£20·42**

51R—8-digits. Metric and currency converter. **£20·42**

8R—Special purchase. 8-digits. $\frac{1}{x}$ key. Only **£7·50**

20R—Special purchase. 8-digits. $\frac{1}{x}$ key. Full-function memory. **£8·95**

31R—Special purchase. \sqrt{x} , Memory. Memory exchange. Reciprocal, X^2 . Rechargeable. **£14·65**

Including recharger

24RD—Green display. 8-digit. **£12·79**

24K—Stainless-steel Slimline. Green display. Beautiful leatherette wallet to hold pen, note-pad and credit cards (all included). Full memory. \sqrt{x} . Click-buttons. Rechargeable. Including recharger **£20·42**

24K—Stainless-steel Slimline. Green display. Beautiful leatherette wallet to hold pen, note-pad and credit cards (all included). Full memory. \sqrt{x} . Click-buttons. Rechargeable. Including recharger **£20·42**

24K—Stainless-steel Slimline. Green display. Beautiful leatherette wallet to hold pen, note-pad and credit cards (all included). Full memory. \sqrt{x} . Click-buttons. Rechargeable. Including recharger **£20·42**

24K—Stainless-steel Slimline. Green display. Beautiful leatherette wallet to hold pen, note-pad and credit cards (all included). Full memory. \sqrt{x} . Click-buttons. Rechargeable. Including recharger **£20·42**

NOVUS

4520—8-digit, 2 exponent. $10^{\pm 99}$. RPN Logic. Full trig and log functions. 4 Roll stack. Memory. Memory exchange. \sqrt{x} . Degree and Radian. Rechargeable **£21·15**



Including recharger

4525—Rechargeable. Programmable version of 4520. **£42·69**

Including recharger

4510—8-digits. 3 level stack. All trig and log functions. \sqrt{x} , π , Reciprocal. Memory etc. **£13·49**

4515—100-step programmable version. **£35·10**

6020—Financier. **£16·69**

6025—Rechargeable. Financier 100-step programmable. **£42·69**

Including recharger

6030—Statistician. **£16·55**

6035—100-step programmable Statistician. Rechargeable. **£42·69**

Including recharger

TEXAS

SR50A—10-digit. 2 exponent. Rechargeable. All trig and log functions. Hyperbolic. X to the root of Y. Radian and degree. Factorial. Memory etc. **£35·10**



Including recharger

SR51A—As above but with 3 independent memories. Linear regression. Mean. Variance. Standard deviation. Permutation. Random number generation + 20 basic conversions and their inverse. Rechargeable. **£46·26**

Including recharger

T1200—8-digit. $\frac{1}{x}$ key. **£7·90**

T1250—As above with Memory. **£8·95**



Digital Wrist Watches

The Barclay



WITH STRAP

3 Functions. Shows hours mins. & secs. Single button operation. Limited supplies at this low, low price. **ONLY £12·99. Gold finish £14·83**

THE SUPERB 10-FUNCTION PULSTRONIC



Shows date and month in correct order! Single button control. Display visible in pitch dark. Hrs, Mins, Secs, Date, Date + Month, Day of Week, Self-adjusting calendar. Auto hold and fade-out. A.M. setting Indicator, P.M. setting Indicator. Undoubtedly one of the most sophisticated watches available at this unbeatable price! Styled in finest solid stainless-steel satin finished with polished bevelled edges. Complete with adjustable matching stainless-steel bracelet AND a FREE presentation box.

LIMITED SUPPLIES AT ONLY £32·15

DECIMO DIGITAL CLOCK/RADIO

£33·50 OUR PRICE incl. VAT plus £1 p&p



This is the most unique clock/radio in the country today having a soft 13" high orange-glow digital readout which is completely silent and non-pulsating. In a beautiful teak style cabinet with up-to-date VHF/MW radio. You can awake to soft music or alarm—and if you want up to 10 minutes more—just press the 'Drowse' button. Automatic 80 minute 'sleep' button in case you drop off while the radio's on.

ORDER FORM

PHONE CALLS AND PERSONAL CALLERS WELCOME MONS TO THURS BETWEEN 2 & 5 p.m. 01-451 4755. SUNDAYS 10 a.m. to 1 p.m. To: BARCLAY ELECTRONICS Dept. TPW, 1115 FINCHLEY ROAD, TEMPLE FORTUNE, LONDON N.W.11

Please send me.....

with/without optional mains adaptor. I enclose cheque/money order total value £.....including 55p to cover P&P

NAME.....

ADDRESS.....

ALL ITEMS CARRY A FULL YEARS GUARANTEE

B.S.I. approved adaptor available for all non-rechargeable calculators. **ONLY £2·50**

barclay

Sparkrite mk2

Capacitive discharge electronic ignition

VOTED BEST OF 8 SYSTEMS TESTED BY 'POPULAR MOTORING' MAGAZINE



- * Smoother running
- * Instant all-weather starting
- * Continual peak performance
- * Longer coil/battery/plug life
- * Improved acceleration/top speeds
- * Up to 20% better fuel consumption

Sparkrite Mk. 2 is a high performance, high quality capacitive discharge, electronic ignition system in kit form. Tried, tested, proven, reliable and complete. It can be assembled in two or three hours and fitted in 15/30 mins.

Because of the superb design of the Sparkrite circuit it completely eliminates problems of the contact breaker. There is no mistfire due to contact breaker bounce which is eliminated electronically by a pulse suppression circuit which prevents the unit firing if the points bounce open at high R.P.M. Contact breaker burn is eliminated by reducing the current to about 1/50th of the norm. It will perform equally well with new, old, or even badly pitted points and is not dependent upon the dwell time of the contact breakers for recharging the system. Sparkrite incorporates a short circuit protected inverter which eliminates the problems of SCR lock on and, therefore, eliminates the possibility of blowing the transistors or the SCR. (Most capacitive discharge ignitions are not completely foolproof in this respect). All kits fit vehicles with coil/distributor ignition up to 8 cylinders.

THE KIT COMPRISES EVERYTHING NEEDED

Ready drilled pressed steel case coated in matt black epoxy resin, ready drilled base and heat-sink, top quality 5 year guaranteed transformer and components, cables, coil connectors, printed circuit board, nuts, bolts, silicon grease, full instructions to make the kit negative or positive earth, and 10 page installation instructions.

OPTIONAL EXTRAS

Electronic/conventional ignition switch. Gives instant changeover from "Sparkrite" ignition to conventional ignition for performance comparisons, static timing etc., and will also switch the ignition off completely as a security device, includes: switch connectors, mounting bracket and instructions. Cables excluded. Also available RPM limiting control for dashboard mounting (fitted in case on ready built unit).

CALLERS WELCOME. For Crypton tuning and fitting service - phone (0922) 33008.

PRICES INCLUDE VAT, POST AND PACKING.

Improve performance & economy NOW

POST TODAY!

Quick installation
No engine modification required

Electronics Design Associates, Dept., PW/6
82 Bath Street, Walsall, WS1 3DE. Phone: (0922) 33652

Name
Address

Mk. 2 DIY Ass. Kit @ £11.80	QUANTITY REQUIRED	for	£
Mk. 2 Ready Built Negative Earth @ £14.97		Cheque No.	
Mk. 2 Ready Built Positive Earth @ £14.97			
Ignition Changeover switches @ £4.30		Send SAE if brochure only required.	
R.P.M. Limit systems in above units @ £2.42			

J. BIRKETT

Radio Component Suppliers

25 The Strait, Lincoln, LN2 1JF

Telephone: 20767

- 50 ASSORTED TRANSISTOR ELECTROLYTICS @ 57p.
- SILICON SOLAR CELLS 0.5 Volt 15mA @ 35p.
- POWER TRANSISTORS 3 WATT MP 8112 NPN @ 15p, MP 8512 PNP @ 15p.
- FM I.C.'s like TAA 570 Untested with data @ 5 for 57p.
- 1000µf 40v.w. ELECTROLYTICS size 1 1/4 x 1/2" @ 3 for 35p.
- 20 SILICON PHOTO TRANSISTORS and PHOTO DARLINGTONS mixed @ £1.
- STACKPOLE ROCKER SWITCHES 5 amp 240 VAC @ 18p each or 4 for 60p.
- VHF DUAL GATE MOS FET's like 40673 @ 33p or 4 for £1-10.
- LINE OUTPUT POWER TRANSISTORS R2008 @ 75p, R2010 @ £1-25.
- HIGH SPEED 40 KHz STACKED SOLAR CELLS .5 volt 250 µA. 6 in x Row @ 45p.
- BATTERY CHARGER AMMETERS 2 amp, 3 amp, 4 amp, 6 amp. All at 66p ea.
- 50 ASSORTED RADIO AND TV KNOBS @ 75p.
- 10 SUB-MINIATURE 10 amp SILICON BRIDGES Untested @ £1-25.
- 100 SUB-MINIATURE CERAMIC PLATE CAPACITORS from 3.3pf to .01µf @ 57p.
- PLASTIC TRIACS 400 PIV 6 amp @ 60p each.
- 20 ASSORTED BRANDED 250mW ZENERS @ 75p.
- 20 ASSORTED BRANDED 750mA SILICON DIODES @ 50p.
- PLASTIC SCR's 50 PIV 6 amp @ 15p, 400 PIV 6 amp @ 40p.
- TAG ENDED ELECTROLYTICS 3300µf 64v.w. size 2 1/2 x 1 1/2" @ 50p, 4700µf 40v.w. size 2 1/2 x 1 1/2" @ 45p.
- POSTAGE STAMP TRIMMERS 10pf, 30pf, 50pf, 150pf, 750pf, 1000pf. All at 6p each.
- BD187 4 amp PLASTIC POWER TRANSISTORS @ 40p each. 4 for £1-40.
- GERMANIUM TRANSISTORS AC 153K, AC 176K, AC 187K, AC 188, AC 141K, AC 142K. All at 20p each.
- 35 ASSORTED PRE-SETS AND SLIDERS @ 57p.
- AC 141K, AC 142K. All at 20p each.
- 30 ASSORTED PNP TRANSISTORS 85% GOOD @ 57p.
- 30 PLASTIC PNP TRANSISTORS 85% GOOD @ 57p.
- 30 ASSORTED TUNING VARIATORS Untested @ 45p.
- 60 ASSORTED WIRE WOUND RESISTORS 1 to 10 Watt @ 57p.
- 500yd Reel of PVC 14 Strand .0048 CABLE @ £3.
- 100 ASSORTED 1/2 and 1/4 Watt RESISTORS 17 different values @ 57p.
- 50 AC 128 TRANSISTORS Branded but Untested @ 57p.
- ITT 100µf 16v.w. size 2 x 1/2" @ 6 for 35p.

Please add 20p post and packing for orders under £2

QUALITY STEREO SOUND

ALMOST 1/2 PRICE OFFER!

SOLENT AUDIO SYSTEM

£5.95 down

MADE TO SELL AT DOUBLE THE PRICE IN CABINET FORM

OUR PRICE **£59.95**

*Stereo Tuner Amplifier chassis with AM/FM radio covering long medium short and Stereo FM wavebands. Separate Base and Treble controls. 30 watts total power output (frequency response 25-20,000 Hz) AFC Switching, Tape record and playback facilities. Dimensions 18 1/2" x 9" x 3 1/2". The very latest BSR automatic record deck with cue and pause control. Two matching elliptical speaker units.

Order early limited stocks available cash price £59.95. Credit Sale £5.95 deposit 9 monthly payments of £7.00 (Total Credit price £68.95). P. & P. £3.00. Send £8.95 today.

Chassis only available for cash at £42.00.


Full 12 months Guarantee.
CALLERS WELCOME.
Access and Barclaycard
telephone orders accepted

Stereo headphones supplied with every complete order.

LEWIS radio PW/6/76 100 CHASE SIDE SOUTHGATE
LONDON N14 5PL Telephone: 01-882-1644

ELECTRONIC DIGITAL CLOCK

with alarm and snooze features

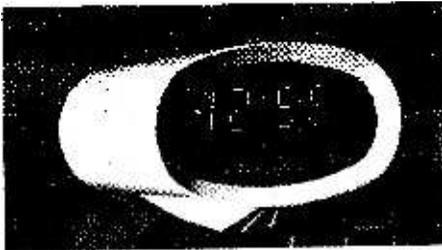

SPECIAL OFFER

£12.48

+ 99 pence VAT

FEATURES: ● 0.7 INCH HIGH DIGITS ● VARIABLE INTENSITY ● 24 HOUR ALARM ● 5 MINUTE REPEATING, SNOOZE ALARM ● ALARM SET INDICATOR ● SNOOZE INDICATOR ● PULSING SECOND INDICATOR ● POWER INTERRUPT INDICATOR ● ALARM CANCEL FEATURES — TILT OPERATION ● ALARM TONE OUTPUT ● A.M. P.M. INDICATOR

Size: 130mm x 90mm x 95mm; Weight: 10oz; Power supply 110 VAC ± 10% 60Hz 230 VAC ± 10% 5HZ

Manufactured to high standards by a major American electronics corporation this superbly styled solid-state timepiece is made available to all readers fully guaranteed.

FREE TRIAL IN YOUR HOME. TRY OUT THE CLOCK IN YOUR HOME. IF DIGITAL TIME IS NOT FOR YOU RETURN IT IN ORIGINAL CONDITION WITHIN 10 DAYS AND WE'LL REFUND YOUR MONEY WITHOUT QUESTION.

Please send electronic clocks as illustrated

I enclose cheque postal order money order £14.02 which includes 55p p & p

Name

Address

Signature

TIME MICROELECTRONICS



**BRIGHTON HILL PARADE,
BASINGSTOKE, HAMPSHIRE RG22 4EH**

T.T.L. 74 I.C.'s. Prices include Postage and V.A.T. plus BIG QUANTITY DISCOUNTS

7400 12p	7413 30p	7432 25p	7454 15p	7490 35p	74121 25p	74139 100p	74156 70p	74174 100p	74189 350p
7401 12p	7414 60p	7437 25p	7460 15p	7491 75p	74122 40p	74141 60p	74157 70p	74175 75p	74190 140p
7402 12p	7416 30p	7438 25p	7470 30p	7492 45p	74123 80p	74142 270p	74160 90p	74176 100p	74191 140p
7403 12p	7417 30p	7440 15p	7472 25p	7493 40p	74125 50p	74143 270p	74161 90p	74177 100p	74192 120p
7404 12p	7420 15p	7441 65p	7473 30p	7495 60p	74126 50p	74144 270p	74162 90p	74178 140p	74193 120p
7405 12p	7422 20p	7442 65p	7474 30p	7496 70p	74130 130p	74145 75p	74163 90p	74179 140p	74194 100p
7406 35p	7423 25p	7445 80p	7475 30p	74100 95p	74131 100p	74147 230p	74164 125p	74180 100p	74195 75p
7407 35p	7425 25p	7446 85p	7476 30p	74104 40p	74132 65p	74148 160p	74165 125p	74181 200p	74196 100p
7408 15p	7426 25p	7447 AN 75p	7483 85p	74105 40p	74135 100p	74150 120p	74166 125p	74182 75p	74197 100p
7409 15p	7427 25p	7448 70p	7485 100p	74107 30p	74136 80p	74151 65p	74167 325p	74184 150p	74198 185p
7410 13p	7428 40p	7450 15p	7486 30p	74118 90p	74137 100p	74152 120p	74170 200p	74185 150p	74199 185p
7411 20p	7430 15p	7453 15p	7489 250p	74120 90p	74138 125p	74155 70p	74173 150p	74188 350p	74199 185p

SPECIAL OFFER ALL 22 I.C.'s FOR P.W. DIGITAL FREQUENCY COUNTER FOR £7.50

POPULAR BRANDED TRANSISTORS

BC147 — BC148 — BC149 — BC157 — BC158 — BC159 — BF194 — BF195 — BF196 — BF197
7p each. 100 for £6.00. Type numbers may be mixed for quantity discount.

Bulk Purchase I.T.T. IN4148 10 for 30p, 100 for £1.50

1 Amp Diodes IN4001, IN4002, IN4003 4p each, 30 for £1.00
IN4004, IN4005, IN4006 6p each, 30 for £1.50

Zener Diodes BZY88, 400MW 3V to 33V 7p each, 100 for £6.00

NEW LOW PRICE
741 OP Amps
ANY QUANTITY 20p each
555 TIMERS
ANY QUANTITY 35p each

TRANSISTORS, etc.

AC128 12p	MTCHN PR	AF117 18p	BC148 7p	BC182L 12p	BC212L 12p	BCY72 16p	BF180 30p	BFX85 25p	2N3702 12p
AC176 12p		BC107 9p	BC149 7p	BC183 10p	BC547 12p	BD124 70p	BF182 30p	BFX87 25p	2N3704 12p
AD149 45p	AF114 18p	BC108 9p	BC157 7p	BC183L 11p	BC548 12p	BD131 35p	BF183 30p	BRY39 35p	1N914 3p
AD181 35p	AF115 18p	BC109 9p	BC159 7p	BC184 11p	BC549 12p	BD132 35p	BF200 30p	BRY56 35p	BY100 15p
AD182 35p	AF116 18p	BC147 7p	BC169 12p	BC184L 12p	BCY70 16p	BD135 50p	BF244 16p	BSX20 16p	BY126 10p
			BC182 11p	BC212 12p	BCY71 16p	BD137 40p	BFX84 25p	2N3055 50p	BY127 12p

PLEASE NOTE THAT ALL PRICES INCLUDE POSTAGE AND V.A.T. AT 8 OR 12½% AS APPROPRIATE

MAIL ORDER ONLY

XEROZA RADIO

1, EAST STREET, BISHOPS TAWTON, BARNSTAPLE, DEVON

SUBSCRIPTIONS – PRACTICAL WIRELESS AND TELEVISION MAGAZINES

WE are still receiving numerous letters requesting subscriptions to *Practical Wireless* and *Television* magazines. For those readers who are not aware, we regret that our magazines can no longer be supplied on direct subscription by IPC Limited due to escalating costs.

This action is very much regretted, but it should not mean that any reader is deprived of his/her regular copies of *Practical Wireless* or *Television*. Readers should order direct from their local newsagents. Any readers outside the UK who have difficulty in locating a supplier should write to the Editor and he will advise them of their local agent.

Soldering Catalogue

A NEW catalogue covering a wide range of soldering instruments and accessories is now available from Adcola Products Ltd. The contents include the well-established range of Invader lightweight soldering instruments for operation from either mains or low voltage

supply, the medium 'A' series range and the heavy duty 'R' series of tools. Safety stands and stations, desoldering instruments including the Remov-ic for DIP extraction and desolder braid are also featured together with solder pots, and wire cutting tools. Details of Superspeed cored solder are also featured.

Despatched with the catalogue is a separate four page technical specification covering the Unit 222 electronically switched variable temperature, thermostatically controlled soldering instrument, and a four-page price list. Details of the Bahco range of pliers for electronics use are also included in the form of a separate leaflet.

Copies of the catalogue and supplementary specifications are available free on request from *Adcola Products Ltd., Adcola House, Gauden Road, London SW4 6LH (01-622 0291)*.

Foundations

WELL-KNOWN author M. G. Scroggie whose work *Foundations of Wireless and Electronics* has just reached its 250,000 sale, is shown here being presented with a specially bound copy of his book.

The publishers, Newnes Butterworth also announced the new 9th Edition of Mr. Scroggie's book.

M. G. Scroggie, B.Sc., C.Eng. F.I.E.E. was the second radio Amateur, under the callsign 5XJ, to make two-way radio contact across the Atlantic.



Mr. Scroggie, centre, shows his specially-bound book to Fred Judd, G2BCX (right) while a Newnes-Butterworth employee looks on.

Tyneside Amateur Radio Society

THE Borough of North Tyneside is holding a Festival of Sport and Recreation during July and the Society which operates within the Borough has agreed to take part by establishing an amateur radio station. Members of the public will be invited to see the station in operation and persons interested in the hobby will be assisted wherever possible.

It is intended to go on the air from approximately 10.00 hours on Saturday, 10th July to 18.00 hours on Sunday, 11th July. They hope to be operating on all bands from Top Band to 10 metres and also on 2 metres.

Special QSL cards are now being printed using the Club callsign G3ZQN. All contacts will be sent a card and Special Certificates to be signed by the Mayor of the Borough will be sent to the furthest contact on each band. The venue of the Festival Station is the Pavilion at the Churchill Playing Fields, Monkseaton, Whitley Bay. The venue for normal Society meetings is the *Wallsend Community Centre, Vine Street, Wallsend* every Monday evening at 20.00 hours. New members will be welcome.

RADIO SHOW

SOUND and Vision 76, National Exhibition Centre, Birmingham, 28/31 May, 1976

BBC Stereo Radio from Tacolneston, Norfolk

THE BBC announced that the Radio 2 and Radio 3 VHF transmitters at Tacolneston, Norfolk broadcast in stereo from Friday, 19 March. The start of a full stereophonic service on all three VHF channels is dependent upon the completion of a new pulse code modulation (pcm) link to the station at Tacolneston. It is hoped that this will be possible within the next two years, but to provide stereo in the meantime, a rebroadcast link has been installed, and this will make it possible to provide Radio 2 and Radio 3 in stereo to about 1,100,000 people in Norfolk, Suffolk and the eastern part of Cambridgeshire. Radio 4 stereo programmes will be added to the service when the permanent pcm link has been completed.

With the present extension, BBC stereo radio will be available to approximately 88 per cent of the United Kingdom population. The start of stereo transmissions does not affect listeners using ordinary monophonic receivers, and to take advantage of the stereophonic information, a receiver having a stereo decoder is required. Advice about reception of the BBC's stereophonic service may be obtained from the *BBC's Engineering Information Department, Broadcasting House, London W1A 1AA*.

Eagle 1976 catalogue

TO mark their 25th year in electronics Eagle International have created a completely different format for the new 1976 catalogue. A comprehensive range of over 500 models including some 45 new products are featured in this absorbing 64 page full-colour publication.

For easy reference the catalogue is divided into nine broad product categories — each page carrying a colour code indicating a particular section. It contains more factual information, comprehensive specifications, frequency response graphs and many additional detail photographs. The sections cover hi-fi, tape, headphones, audio, microphones, public address equipment, intercoms, test equipment and ancillary products, plus a comprehensive index with recommended retail prices.

The section on intercoms includes a useful selection guide and the clamp meter and multi-meter guides in the test equipment section are of particular interest. A welcome addition is the connecting lead guide which shows the correct hook-up for a complete hi-fi system. As always every Eagle product line carries a two-year guarantee plus a reputable after-sales service, even after the warranty period.

The new Eagle catalogue for 1976 is available on request from *Eagle International, Precision Centre, Heather Park Drive, Wembley, HA0 1SU.*

The Budget and prices in P.W.

IN the April 6th Budget, VAT at the 25% rate was cut to 12½%. At the time of our going to press we were unable to make alterations to all of our advertisements but we would advise readers that some of the prices quoted on our pages will be different and if ordering goods, it might help to check with the advertisers concerned before purchasing.


Mullard Data Book 1976

THE 1976 edition of the Mullard Data Book is now available. It contains abridged data on the company's range of components for use in consumer applications, including valves, integrated circuits, semiconductor devices, TV picture tubes, capacitors and resistors. Equivalents and comparables are also listed.

Designed for the radio and TV dealer and his service engineers, the pocket-size book runs to 176 pages and, for easy reference, different coloured papers are used for each of the main sections: blue for semiconductors, yellow for picture tubes and receiving valves and green for capacitors and resistors.

The Mullard Data Book is obtainable for 50p direct from *Technical Press Ltd., Freeland, Oxford OX7 2AP.*

The Eagle strikes

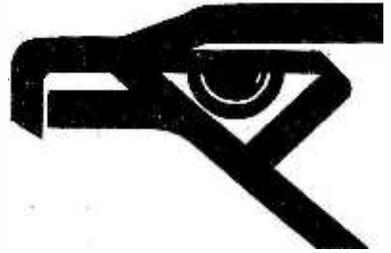

A NEW symbol has been perfected for Eagle International, which will be systematically applied to all Eagle audio and electronic products, packaging, advertising and promotional material in the coming months.

Marketing Director David Harris says, "The symbol will project an aggressive identity for Eagle and will provide an internationally recognisable image for overseas markets". The design adopted is a totemic device depicting a stylised eagle head which expresses the power and majesty of the keen sighted king of the sky.


Free offers galore!

ORCHARD Electronics Director Mr. D. M. Trueman recently sent us this picture of the firm's premises at Wallingford, Oxon. He's offering, completely free, one floor of the building to anyone interested in joining/forming an amateur radio and electronics club in the area. If any readers would like to help form something along these lines, Orchard Electronics would be pleased to hear from them.

Another offer from the firm comes in the form of a free transistor (CIL 108) it's the equivalent of the BC108 and the first 3000 readers who send a stamped, addressed envelope for the Orchard list of components will get one.

If you want a free transistor and components list or are interested in joining up with other enthusiasts to form a club, write to *Mr. D. M. Trueman, Orchard Electronics, Flint House, High Street, Wallingford, Oxon, OX10 0DE. (Telephone: Wallingford (0491) 35529 or 36588).*

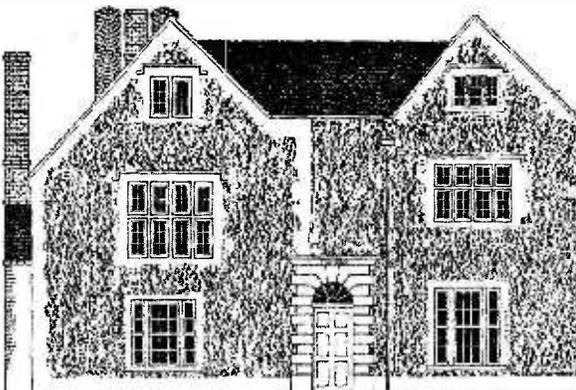The 15th century building, part of which has been offered free of charge for anyone in the Wallingford (Oxon) area wanting to join a Radio/ Electronics club.





RHYTHM GENERATOR

PART 2

A.S.WEBB B.Sc

Power supply

The power supply circuit shown in Fig. 8 is of conventional design providing the three regulated voltages required by the rhythm generator. The regulation is necessary to reduce false triggering of the twin-T oscillators which are very sensitive to supply fluctuations and to ensure that the voltage delivered to the M252 chip across pins 9 and 10 remains at $17V \pm 1V$. The total current consumption of the complete generator is very low, about 30mA when the LED is off rising to 44mA when on.


Construction

The construction of the rhythm generator is simplified by the use of three printed circuit boards, one for the snare drum, long cymbals, short cymbals, maracas, M252 chip, clock generator and down-beat indicator; the second for the bass drum, high bongos, low bongos, claves, conga drum and pre-amplifier and the third for the power supply unit. No detailed procedure for the mounting of the

components is given as this is fairly straight forward although careful soldering is required.

There is, however, one point over which **extreme care** should be taken. The M252 chip and the 4011A NAND gate ICs are manufactured using MOS technology and although various input protection components are built in they are vulnerable to high voltage static electricity. They are normally supplied packed in conductive foam or surrounded in metal foil and should not be removed until ready to be inserted into their respective sockets.

A static charge can build up on anything that is insulated from earth. Friction with modern plastics such as nylon or PVC quickly cause static to accumulate e.g. by combing one's hair or wearing synthetic fibre clothes. A plastic laminate surface on a table with rubber feet could become highly charged after polishing. The basic rule when handling these devices is that the pins should not be allowed to come into contact with anything that is not an earthed conductor. The author uses a pair of metal tweezers connected to earth which automatically earths the body thus making handling completely safe. If the ICs have to be removed from their sockets they should be placed in conductive

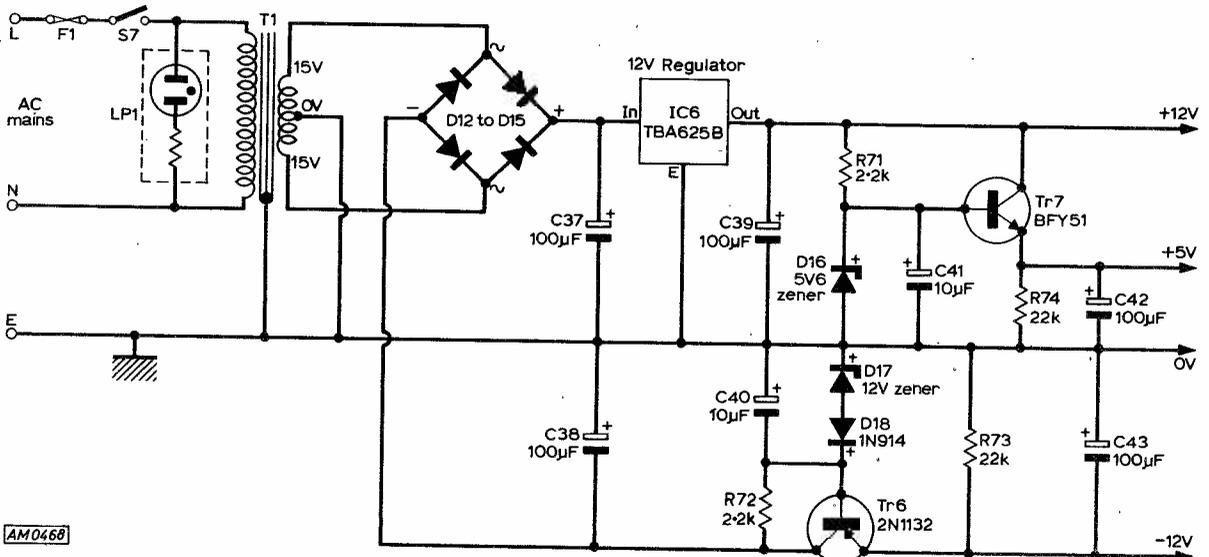

AM0468

Fig. 8: Circuit diagram of power supply giving $-12V$ and $+5V$ for IC1, $+12V$ and $-12V$ for IC5, and $+5V$, $+12V$ and $0V$ for the remaining IC's and transistors.

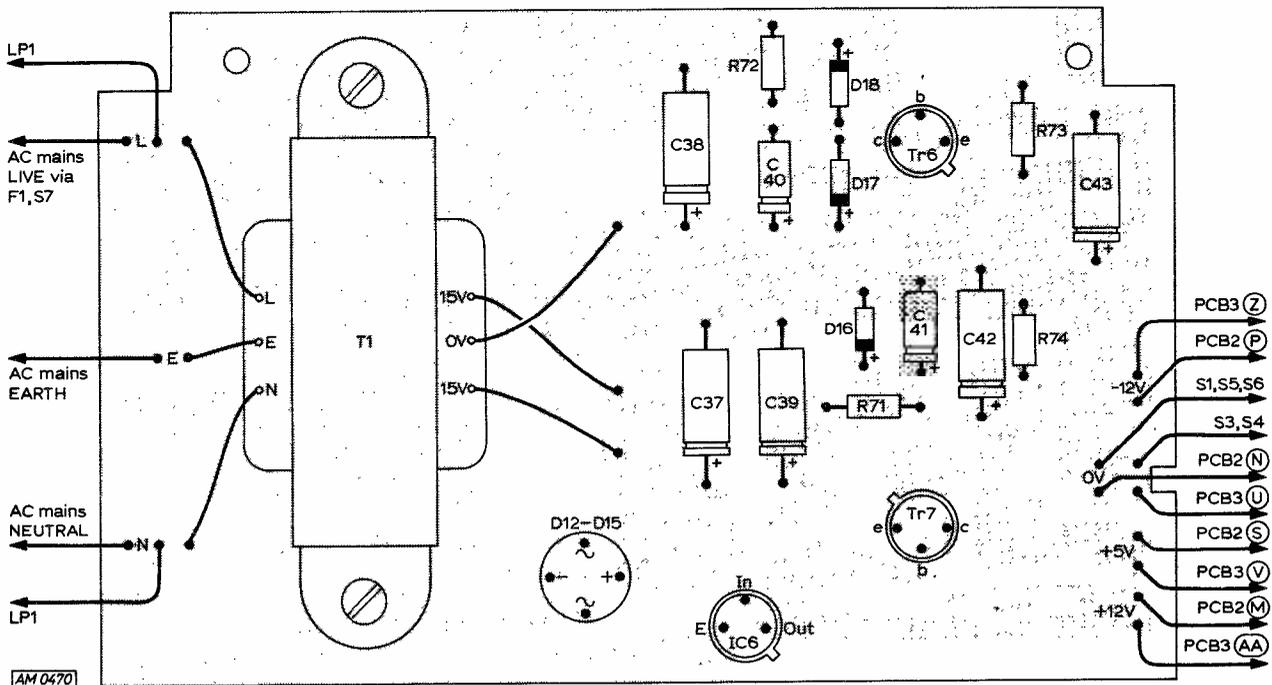
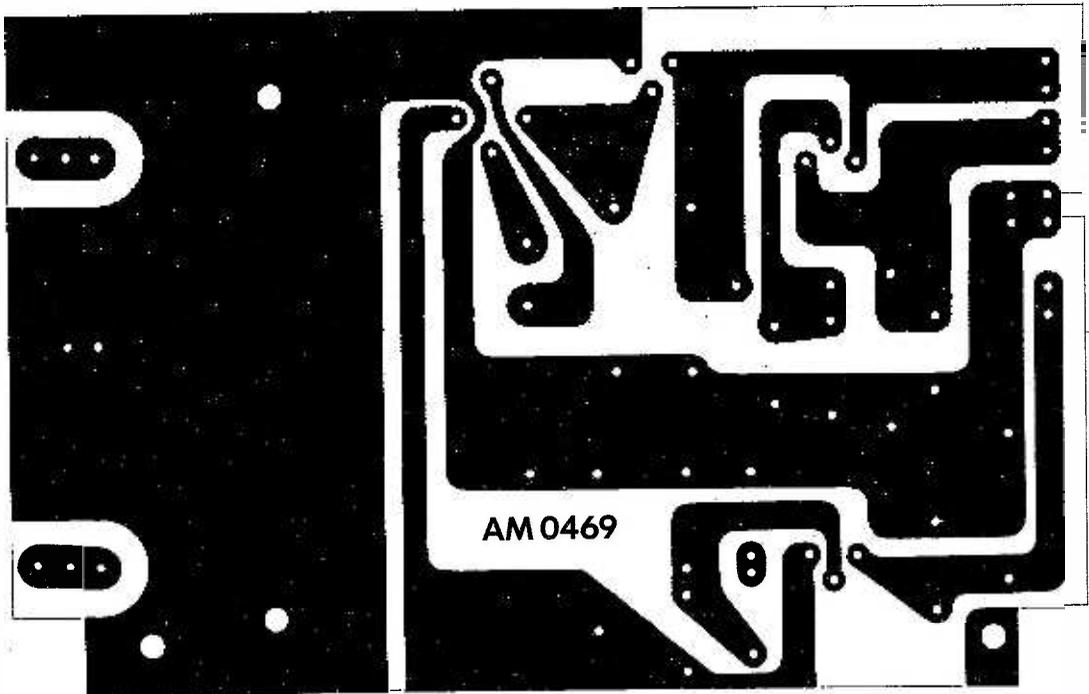



Fig. 9: Full size drawings of the power supply board showing foil side above, and component overlay below.

foam or on an earthed metal plate. No alterations should be made to the circuit with these devices in position and they should not be inserted with the power switched on. No apologies are made for stressing these points as a replacement for the M252 chip will cost over £9!

Having obtained all the necessary components the enthusiastic constructor often finds it difficult to resist the urge to put everything together as quickly

as possible. Although a lot of the complexity of the circuitry has been taken out of the hands of the constructor and built into the printed circuit boards there is nevertheless a certain amount of interwiring involved. This means that if the generator is not functioning correctly when it has been completed it may be difficult to locate and rectify any fault.

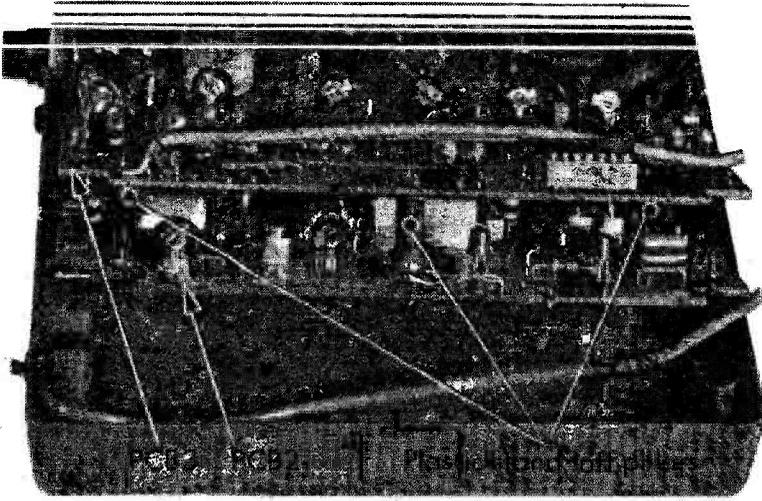For this reason it is highly recommended that all the components with the exception of the integrated



The two pcb's containing the rhythm generating sections are mounted one above the other by means of three plastic stand-off spacers.


circuits are individually checked before assembly. With an ordinary multimeter set to measure resistance, check the values of the resistors against their colour codes, check for leakage of the capacitors, the forward drop and reverse leakage of the diodes and transistors (these may be considered as two diodes connected back to back) and the continuity of the transformer windings, chokes and switches. Also carefully examine the copper track on the printed circuit boards for any hair-line cracks or for bridging caused by roller tinning smear or under-etching.

The first step is to assemble the power supply unit on PCB1 referring to the component layout given in Fig 9. Begin by inserting the Vero pins at the appropriate points, followed by the resistors, capacitors, semiconductors and finally the transformer. Having completed the board, check that the capacitors and diodes have been soldered in the right way

round. Temporarily connect the mains to the transformer and ensure that the power supply unit is functioning correctly by measuring the three voltage outputs.

If all is well, proceed to assemble the components in the same order as indicated above on PCB2 and PCB3 according to the layouts in Fig. 10 and Fig. 11. When completed check the circuit boards over for mistakes and for any solder bridging the copper tracks. It is well worth taking some time over this as mistakes are easily made and careful checking now may eliminate time-consuming and possibly expensive trouble-shooting later. Don't forget the links!

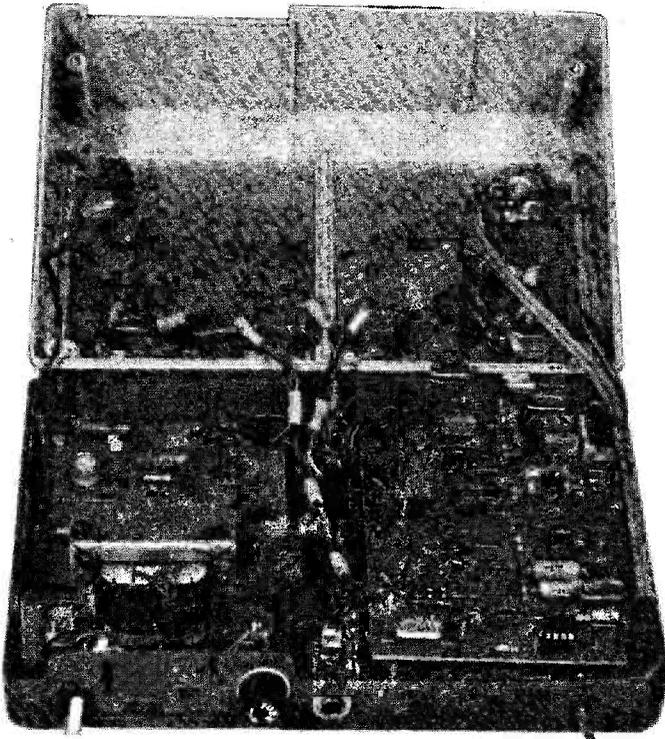The interwiring leads are then soldered to the pins on PCB2 in accordance with Fig. 10 allowing sufficient length of wire. The three stand-offs are next inserted and PCB3 pressed home on top. The wiring to this board may now be completed routing all the



Overall photograph of the complete unit, showing details of the PCB layout and positioning of the various switches.


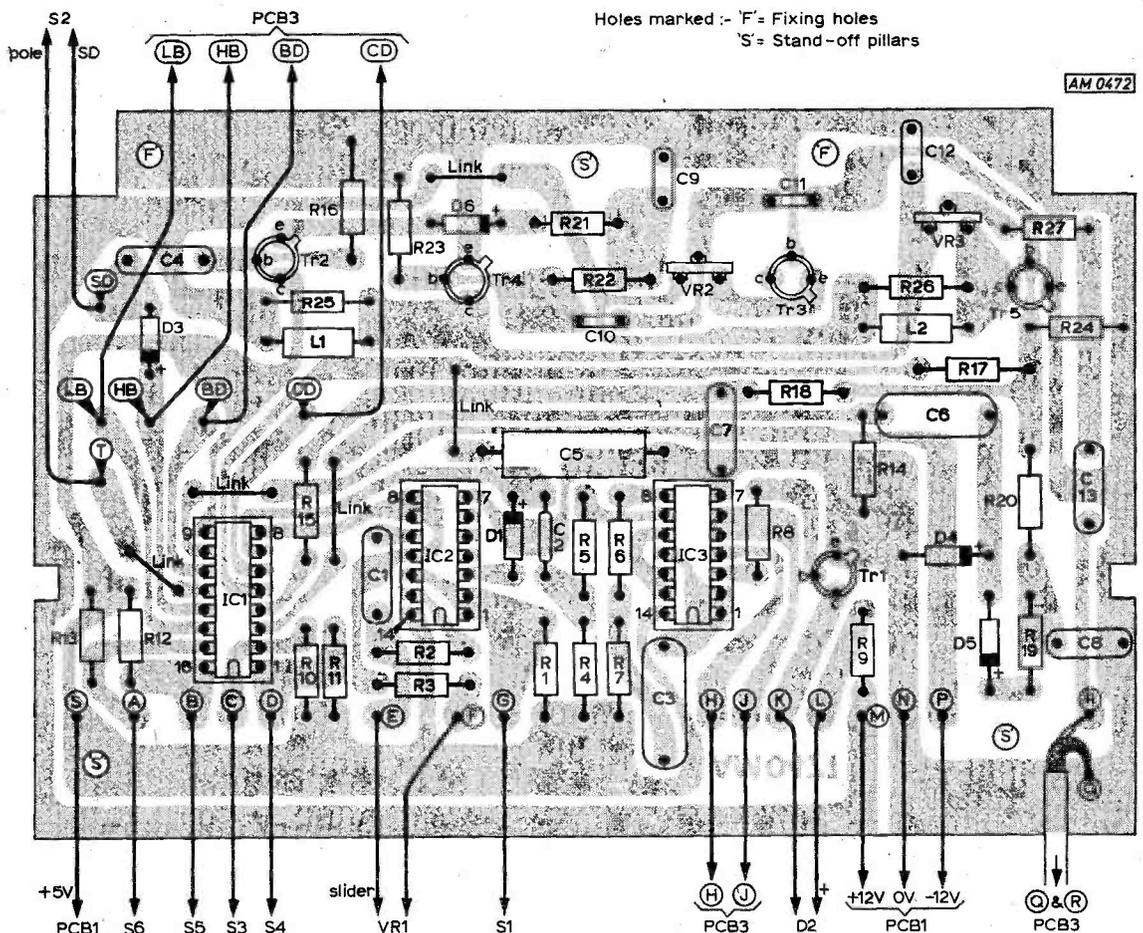
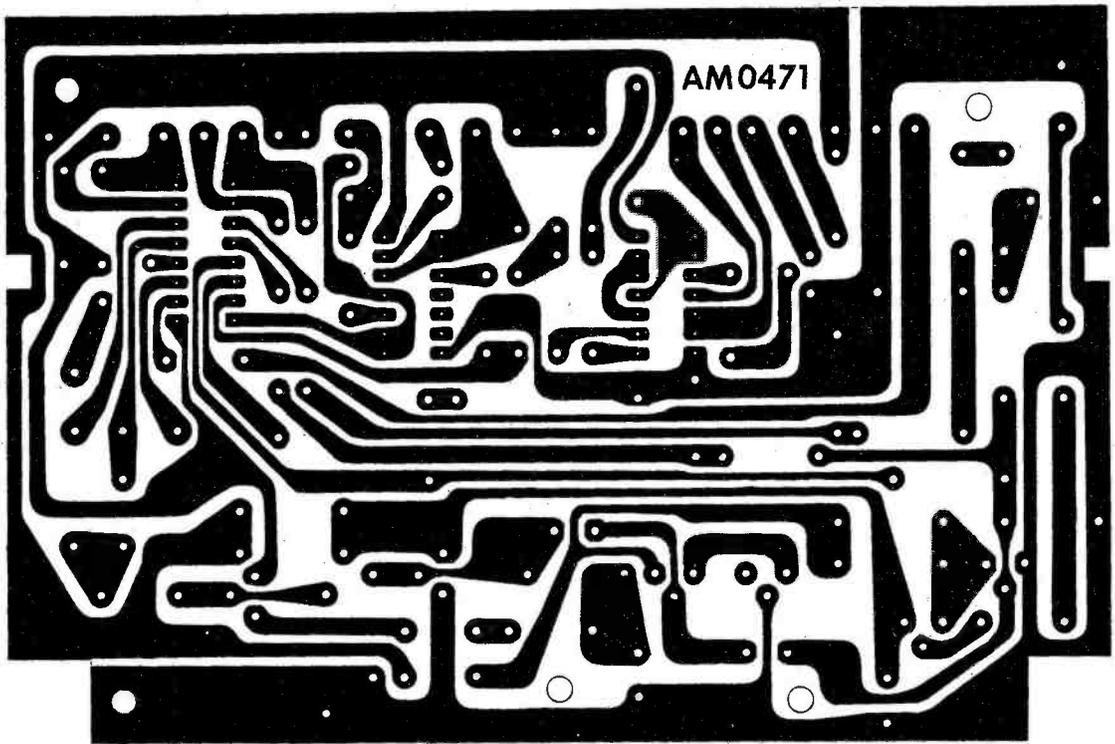


Fig. 10: PCB2 containing the master chip IC1, together with the individual circuits for clock generator, down-beat indicator, snare drum, long and short cymbals, and maracas. Board is shown full size.

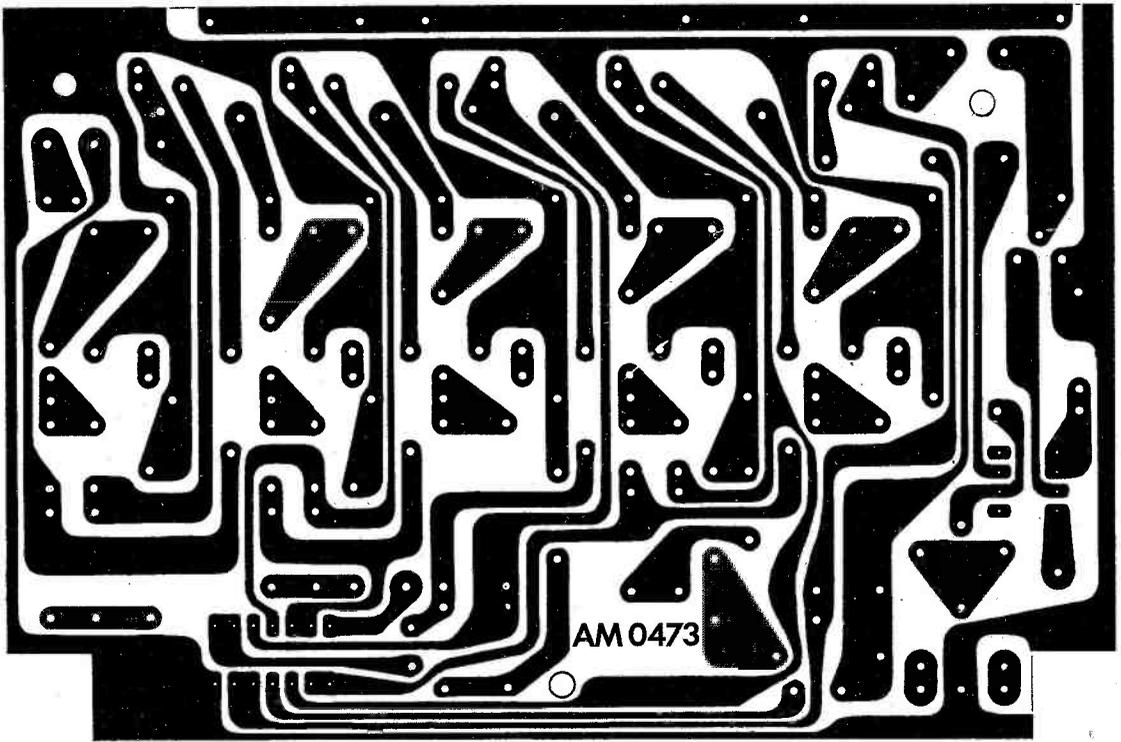

Holes marked 'S' = Stand-off pillars

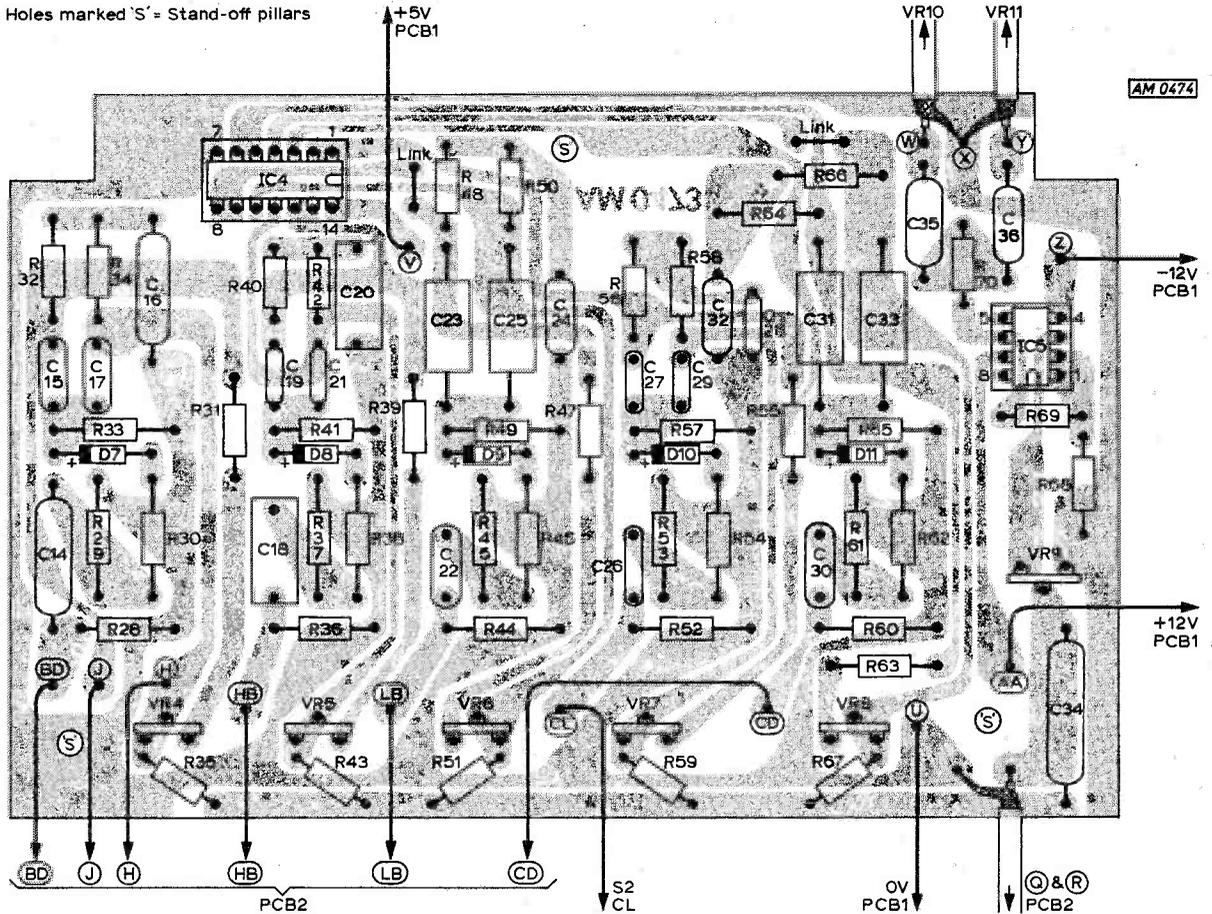


Fig. 11: PCB3, which is shown full size and contains components for the bass and conga drum, high and low bongos, claves and the pre-amplifier. The NAND gate used for the bass drum is 'borrowed' from IC3 which is situated on PCB2.

wires from the board below on the right hand side. This allows the top board to be "hinged" from the lower one when fitting and making adjustments. Note that the bass drum oscillator utilises a spare NAND gate in IC3 on the lower board.

Case assembly

The Vero plastic box type 65-2523E used in the prototype makes a small and very attractive housing. The light grey moulding is removable allowing easy access to the base. Before mounting the boards inside the case four holes must be

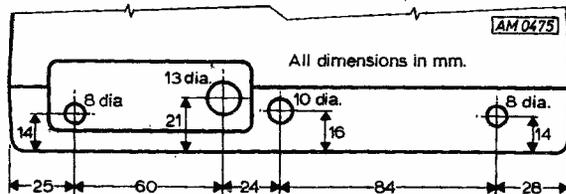


Fig. 12: Rear view of the Vero plastic box base, giving details of the drilling dimensions.

drilled in the back of the base as shown in Fig. 12 to accommodate the fuse-holder, foot switch socket, mains input and signal output leads.

The drilling layout for the front panel is shown in Fig. 13. A really professional finish may be achieved by using Letraset for the legend on the panel as in the photograph. The code table (Fig. 2) should be cut out or copied and stuck in the position indicated for easy reference. The panel will then require protection from abrasion and may be sprayed with a protective lacquer such as Letracote Gloss or alternatively covered in a sticky-backed clear film similar to "Libraseal". Both these items are obtainable from most stationers or artists supplies shops. If the film is used it will be necessary to trim it close to the sides of the panel and in the holes with a razor blade to prevent it peeling off.

The boards may now be fitted in the base with power supply unit on the right and the double board assembly alongside on the left. The base incorporates brass inserts for this purpose. These require 3mm metric screws although at a pinch 6BA could be used if the metric size proves difficult to obtain. The +12V, -12V, +5V and 0V supply lines are now connected up from the power supply to the instrument boards and the mains input lead wired in.

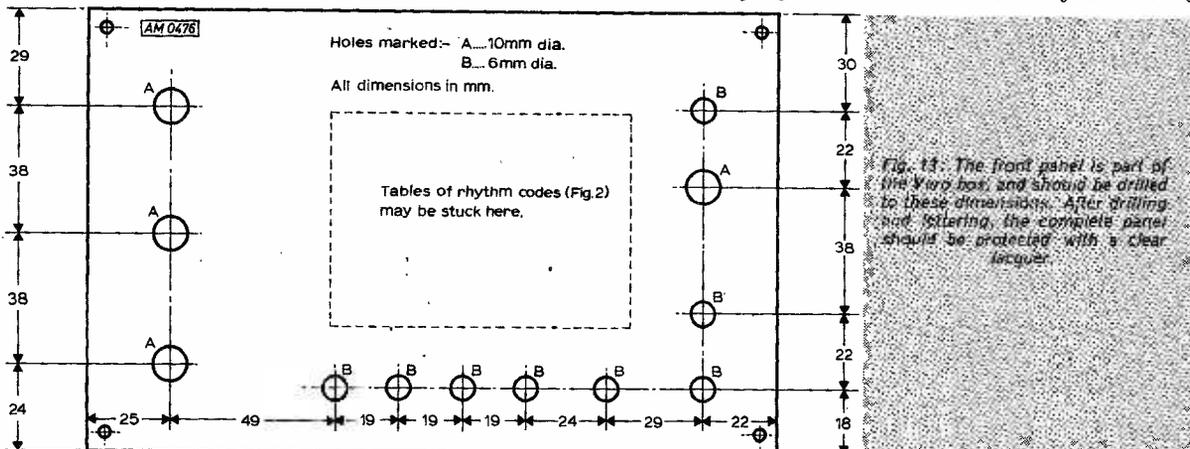


Fig. 13: The front panel is part of the Vero box and should be drilled to these dimensions. After drilling and finishing, the complete panel should be protected with a clear lacquer.

The controls are then assembled on the front panel, see Fig. 14. To preserve the neat appearance of the panel the locating lugs on the potentiometers should be filed off and any locating washers supplied with the miniature switches discarded. To prevent rotation in the absence of these, crinkle washers are fitted between the components, and the back of the panel and the nuts screwed up tightly. Note the tag under the stop switch, S1, to allow earthing of the panel.

The light grey case moulding is placed on the base and the panel controls wired in. There is a supporting strut running vertically across the opening of the box and the wiring must be routed so that wires are not trapped between this and the panel. For this reason there are two earth wires running from the code switches, one on either side.

The switches S3 and S4 are fairly close to PCB3 when the panel is screwed in position so the link wire between them should be insulated and pressed flat on the panel to prevent it touching VR4.

Final adjustments

For making the final adjustments the output of the generator is connected via a screened lead to an external amplifier and loudspeaker. The three 4011A and the 741 ICs may now be inserted. The insertion of an IC into a socket can be a bit of a problem the more so when the IC has to be handled with caution. New sockets are often very tight and a useful tip is to 'ease' the socket by repeatedly inserting and removing an old IC of the same outline until it is free. With VR9 set midway and with the volume of the amplifier at a fairly low level the preset potentiometers VR4 to VR8, should be adjusted in turn until oscillation occurs and then backed off until it just disappears. In some instances it may not be possible to achieve continuous oscillation of the bass drum circuit but this does not matter. The bass drum may be made to sound momentarily by connecting its input, i.e. the non-earthly side of R28, to the +5V supply. The potentiometer VR4 is then further adjusted to achieve the best sound. The procedure is repeated for the remaining four instruments on PCB3.

The adjustment of the instruments on PCB2 is made by varying VR2 which controls the filtered white noise level in conjunction with VR3 which balances the output from the snare drum with the rest of the instruments on this board. The instruments may again be made to sound by connecting

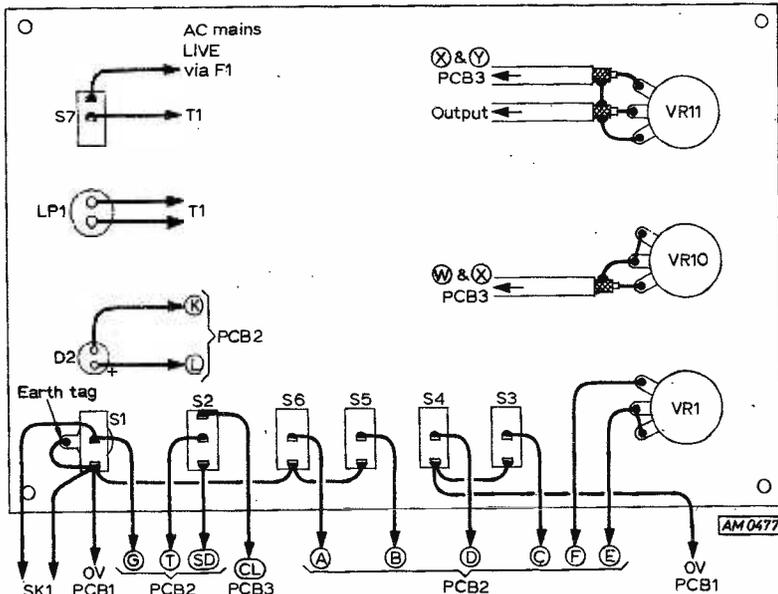


Fig. 14: Rear view of the front panel, showing controls mounted in position, with wiring from boards and power supply.

their respective inputs momentarily to +5V. The preset potentiometer VR9 controls the maximum voltage output from the Rhythm Generator and should be adjusted to suit the sensitivity of the external amplifier.

Having completed the preceding adjustments it is worthwhile checking that the voltage between pins 9 and 10 on the M252 socket is $17V \pm 1V$ with pin 9 positive. Switch off the power and carefully insert the M252 chip in its socket, the correct way round! bearing in mind the handling procedure outlined previously. Check through the fifteen rhythms (with S1 open) by entering the various codes given in Fig. 2 on switches S3 to S6. It is important that the tempo is adjusted so that the particular rhythm sounds right and that the snare drum or claves is correctly selected. Final adjustment to the instru-

ments should be made while the generator is running to correct any excessive "ringing", and to achieve the best overall balance of sound. If a foot operated switch is added it should be of the "press to break" type in order to inhibit the generator in its "off" position.

Finally, a word about loudspeakers. The Rhythm Generator by its very nature produces large transient signals especially from the bass drum circuit where, because of its low frequency, large excursions of the loudspeaker cone are required. It is therefore essential that a speaker of adequate power rating is used to avoid permanent damage.

Acknowledgements are due to SGS-ATES for some circuit details. RW

Note. R4 in the components list, Part 1, was incorrect, and should have read 220k Ω and not 22k Ω .

KINDLY NOTE!

STEREO DISCO SYSTEM

Dec 75-Jan/Feb 76

Some readers report encountering earthing problems with the stereo unit. To obviate the risk of earth loops the following earthing table should be followed. The terminal block, Fig. 14 page 849, negative side of the bridge rectifier, will be referred to as the "common earth".

Pin 23 RH amplifier	to Common earth
Pin 23 LH amplifier	to Pin 23 RH amplifier
Pin 2 LH amplifier	to Pin 2 RH amplifier
Pin 2 LH amplifier	to E tagstrip B Fig. 11
Pin 2 RH amplifier	to E tagstrip B Fig. 11
Pin 23 RH amplifier	to Neg. RH speaker socket
Pin 23 LH amplifier	to Neg. LH speaker socket
Mains earth in	to Copper plane, mains panel

Copper plane, mains panel	to Common earth
Transformer metalwork	to E on mains input socket
Pin 32 Light Modulator	to E on mains input socket
Turntable metalwork	to Common earth

All connecting leads to the speaker output sockets should be routed well clear of pre-amplifier and mixer panel. Good quality screened lead must be used for the turntable and mixer connections and the screens of these connected as shown in Fig. 11. It will be noted that all these connections are made to the mixer ONLY.

A transformer of low flux leakage must be used if hum is to be eliminated. The hum level of the prototype at maximum gain setting was virtually nil on both channels.

It is an advantage to exchange capacitors C3 and C5 i.e. C3 to be 100 μ F and C5 25 μ F. Resistor R19 should be changed to 390 Ω . On mono versions of the Disco omit the balance control and make VR9 10k Ω log.

The polarity of C6 in Fig. 6 and on the PCB supplied by the Readers PCB Service is reversed to what it should be. Reverse the capacitor if already fitted.

Before initial switch-on ensure that VR52 is set fully clockwise.

Talking TRANSISTORS

P. MATTHEWS

BEFORE the design formulae of transistors are derived, it is necessary to examine how a transistor is capable of amplification. Conduction is simply the movement of electrons in a general direction within a substance. A substance which allows electrons to flow freely through it is called a "conductor", one which does not is called a "non-conductor" or "insulator". The electrons responsible for conduction are those most loosely held by the nuclei of the atoms of the substance and lie in the outer parts of the atoms. These electrons are known as the "bonding" or "valence" electrons and there are usually two or three of these for each atom. Note that the definition of conduction does not imply that the electrons which start from one end of a conductor need be those which reach the other end, although this is usually the case with good conductors. It could happen that after an electron had been removed from an atom A, leaving a "hole" in A, it could fill up a previously existing hole in an atom B, leaving the electron from atom B to continue. This process is shown in Fig. 1. Note that this is a purely diagrammatical representation of conduction in general, and that in a good conductor all the bonding electrons are quite free from the rest of their atoms.


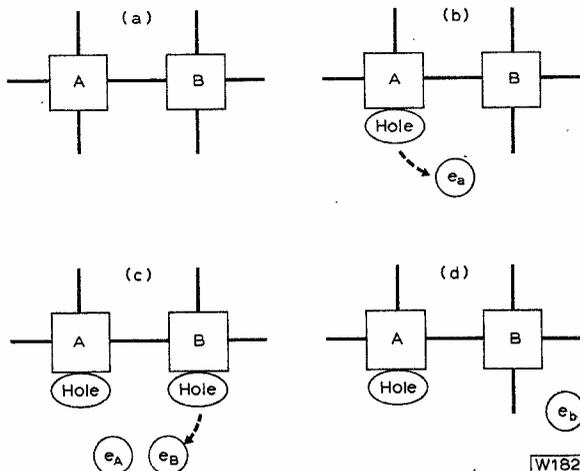


Fig. 1: Diagram to illustrate the idea of movement of electrons in a conductor.

A point worth mentioning is that electrons are considered to have unit negative charge, which is 1 electron-volt (ev) in value, and that a flow of negative electrons in one direction is denoted by a flow of positive current in the other direction. This fact is brought out in Fig. 2, which depicts a simple battery and resistance circuit. At the negative battery terminal there is available a supply of electrons

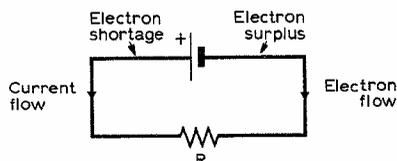which flow through the resistor to the positive terminal where there is a shortage of electrons. In fact, the battery serves just to pump electrons from its positive to its negative terminal, through the internal circuit of the battery. An electric current flows from the positive, through R, to the negative terminal.



W183

Fig. 2: The electron state in the simplest of circuits.

In summing up, it should be remembered that in conductors, including "resistances", the bonding electrons are effectively separate from the rest of the atoms, whereas they are tightly held in insulators. As a matter of interest, this can be illustrated by observing the effect of heat on conduction, through the two classes of materials. An increase in the temperature of a conductor causes a drop in conductance (and increase in resistance) because the increasing vibration of the "stationary" ions impedes the otherwise almost free flow of electrons. When an insulator is heated it remains as such until a certain high temperature when the insulator "breaks down" into a conductor because the electrons part from the atoms.

SEMICONDUCTORS

A semiconductor is a substance which falls between the general categories of conductors and non-conductors. In other words, it is a very high resistance conductor at room temperature. As an example, the resistivity of silver, a conductor, is about $10^{-6}\Omega/\text{cm}^3$, that of pure germanium, a semiconductor, about 60, and glass, an insulator, 10^{10} .

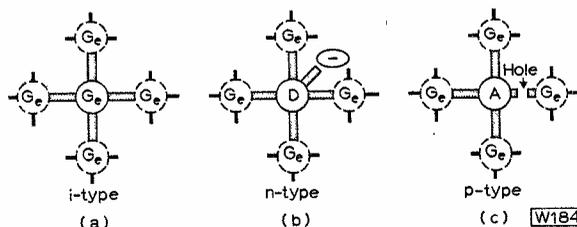


Fig. 3: Three types of germanium, the n and p types being the result of added impurities.

Semiconductors are really insulators which have a low "breakdown" temperature and they behave as insulators when cooled appreciably. Between somewhat below room temperature and about 75°C in the case of germanium (approx. 150°C for silicon) the resistivity falls very sharply until it is so low that the material acts as a conductor.

It happens that the introduction of traces of impurities into the semiconductor over this temperature range has unusual effects on the resistivity and to see why this occurs it is necessary to take a closer look at the structure of semiconductors. Germanium, an elemental semiconductor, has four bonding electrons, and forms a crystalline type of structure, with each electron teaming up with one other electron from an adjacent germanium atom. Although the bonding pairs of electrons are symmetrically arranged in three dimensions, Fig. 3 has been drawn in two dimensions for simplicity.

Suppose an impurity is introduced into the structure. In diagram Fig. 3(b) so-called "donor" impurities, such as arsenic or phosphorus, which have five bonding electrons, are fitted into the structure. It can be seen that one electron is left over because only four are required for bonding, hence the name "donor". The space electron is weakly held by the donor nucleus. Germanium modified in this way is known as n-type germanium alloy and contains large numbers of virtually free electrons.

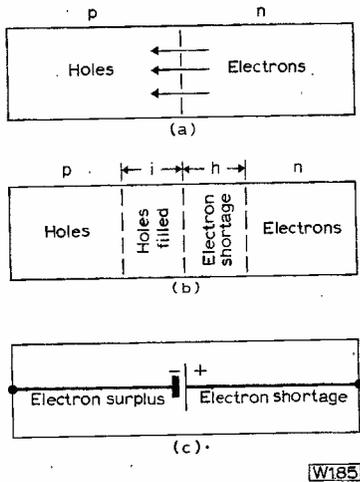


Fig. 4: Illustration of electron flow in a p-n junction.

An opposite effect occurs when "acceptor" impurities, such as aluminium, boron or indium, with three bonding electrons, are added to form p-type germanium, Fig. 3(c). One electron is needed to complete the structure so that there is a positive hole. It can be seen that this p-type germanium is conductive since electrons can be attracted away from nearby atoms to fill the hole. In this way, the passage of a negative electron from A to B corresponds to that of a positive hole from B to A.

There are, therefore, two important types of impure germanium, the n-type which has been treated with a trace of a donor impurity, and the p-type with an acceptor impurity. Electrons can move freely through both p and n alloys so they can be classed as conductors. This is contrasted with pure

or "intrinsic" i-type germanium, in which there is only limited intrinsic conduction at a given energy level.

THE P-N JUNCTION

When a strip of pure germanium is treated so that one half is of p-type and the other of n-type germanium, there is said to be a "p-n junction" in the middle. Almost as soon as the junction is formed, some loose electrons break away from the n-layer and a few of these diffuse into the p-layer to fill in the holes nearest the junction. This means that there is a

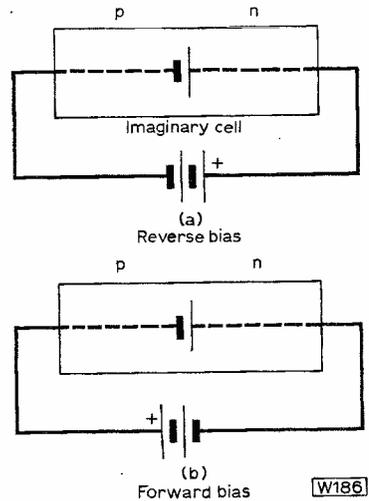


Fig. 5: The two forms of biasing applicable to a junction.

layer of intrinsic germanium on the p-side of the junction. However, i-type germanium constitutes a comparatively very high resistance and so the electron flow from n to p ceases almost immediately, an equilibrium being set up at a given temperature. This is illustrated in Fig. 4 (a) and (b). Since electrons have moved from the n layer to the p layer, there is a shortage of electrons in the n-region and a surplus in the p-region. Another way of saying this is that the n-half of the p-n junction has obtained a positive charge with respect to the p-half. This is represented diagrammatically by means of a cell in Fig. 4(c). The value of this "contact potential" is about half a volt, and it is important to remember this.

Consider what happens when an external source of EMF is applied across the junction terminals, and its polarity opposes that of the imaginary cell, as in Fig. 5(a). This is known as biasing in the reverse direction. Only a small current flows as the insulation or "depletion" region of germanium atoms in the junction is "reinforced" or widened. When the external battery is connected the other way, as in (b), the depletion region is broken down and electrons flow freely from the n-region to the p-region. This is known as biasing in the forward direction. In other words, the p-n junction acts as a rectifier provided that the applied voltage is greater than its contact potential. This simple p-n junction rectifier has found a large number of applications in industry and is currently available in a wide variety of types ranging from modern versions of the "cat's whisker"

DORAM


A PROFESSIONAL DEAL FOR AMATEURS

*ORDERS BY RETURN OF POST *NO QUIBBLE REPLACEMENT PART SERVICE
*QUALITY BRANDED PRODUCTS *FREE UP DATE INFORMATION SERVICE


TOOLS

The handy EXPO 12V d.c. drill is supplied complete with drill kit containing 4 small drills, two spare collets, two cutters, wire brush, soft buffer, grindstone and 9 various milling and reaming tools.

Drill & kit £9.50 + s
Kit only £4.75 + s

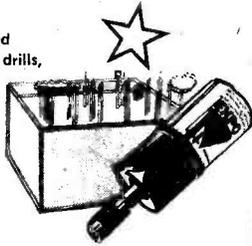

ORYX 50W SOLDERING IRON

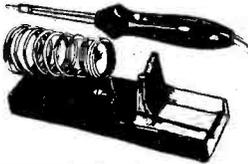

Temperature can be altered between 200-400°C.

Iron 240V £6.90 + s
Stand £2.80 + s

ISO-TIP CORDLESS IRON

Mains and 12V d.c. versions available
£11.50 + s



DE-SOLDER TOOLS

Three high-suction models available

SR2 £6.20 + s
SR3 £5.20 + s
SR3AS £4.80 + s

Spare nozzle 60p ea. + s
Please state type



NICKEL - CADMIUM RECHARGEABLE CELLS

	Sim. to dry cell	nom. capacity	charge cur. (mA)	
HP7	None	0.5Ah	50	£1.10 s
HP11	None	1.2Ah	100	£1.24 s
HP2	2.0Ah	2.0Ah	200	£1.80 s
HP2	4.0Ah	4.0Ah	400	£2.70 s

ELECTRONIC IGNITION UNIT

- * High performance
- * For 2 & 4 stroke engines
- * Improved start/running
- * 'Crisper' throttle response
- * Reduce battery drain

Neg. earth or pos. earth
£15.00 + s

Please state type required



BATTERY ELIMINATOR

Switched output 6, 7.5 or 9V at 250mA.
D.C. pos. or neg. earth
£3.15 + s



SEMI-CONDUCTOR DEVICES

RECTIFIERS

IN 4001 - 5p ea.)
IN 4002 - 6p ea.) + s
IN 4003 - 6p ea.)

1-0A bridge (400V) - 32p + H
1-6A " (200V) - 48p + H
1-6A " (800V) - 70p + H
2-0A " (200V) - 72p + H
2-0A " (600V) - 90p + H



MULLARD MODULES

LP 1173 - £6.10 + H
LP 1184/2 - £6.58 + H
LP 1185 - £4.50 + H
LP 1186 - £6.32 + H
LP 1400 - £5.15 + H



BIG PRICE REDUCTIONS

TRANSISTORS


BC 107 - 12p s
BC 108 - 11p s
BC 109 - 12p s
BFY 50 - 20p s
BFY 51 - 19p s
BFY 52 - 20p s
2N 3055 - 62p s
2N 2646 - 94p s
TIP 2955 £1.14 s
TIP 3055 61p s
BC 237B - 11p H
BC 238C - 10p H
BC 239C - 12p H
ZTX 107 - 10p H
ZTX 108 - 9p H
ZTX 109 - 12p H
ZTX 300 - 13p H
ZTX 500 - 14p H
MUE 340 - 62p H
TIP 31A - 36p H
TIP 32A - 40p H
2N 3819 - 27p H
3N 141 - 65p s
CS 715 - 18p H
10 for £1.50 H



I.C.'s
T05 Reg - £1.10 s
MVR 5 - £1.55 s
MVR 12 - £1.66 s
MVR 15 - £1.55 s
LM 309K - £1.95 s
7805 - £1.50 s
7812 - £1.50 s
7815 - £1.50 s
7824 - £1.50 s
±15V D.I.L. - £2.82 s
TBA 231 - £1.50 H
TBA 800 - £1.20 H
TBA 810S - £1.30 H
TBA 820 - £1.00 H
ZN 414 - £1.30 H
ZN 424 - £1.25 H
741 Op-amp - 36p s
747 Op-amp (Dual 741) - 95p s
748 Op-amp - 48p s
555 TIMER - 56p s
556 (dual 555) - £1.10 H
HA 1156 - £1.60 H (similar to MC1310P)
ORP12 - 72p s
8A Triac - £1.18 s
ZN 1034E - £4.70 s

'INTERNATIONAL 25'

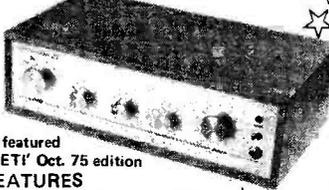Build yourself a BIG SOUND amp at a budget price



As featured in 'ETI' Oct. 75 edition

- #### FEATURES
- * Triple Op-amp pre-amplifier
 - * Power 'Darlington's'
 - * Modern styling
 - * 25W per channel into 8 ohms.

Complete kit with assembly instructions
Overseas orders £34.50
S.A.E. for full spec.


£29-95
+ £3.74 VAT

BOOKS (z)

Hi-fi hints and tips 38p ea.
Towers international transistor selector £2.95 ea.
Electronic circuit design handbook - a must for electronic enthusiasts £4.50 ea.

'SAMOS' CASES

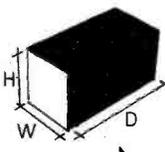Low-cost blue cover and white base PVC steel cases



S1	50W x 50H x 100D	£1.03 + s
S2	100W x 50H x 100D	£1.17 + s
S3	150W x 50H x 100D	£1.31 + s
S4	50W x 75H x 125D	£1.47 + s
S5	100W x 75H x 125D	£1.68 + s
S6	150W x 75H x 125D	£1.97 + s
S7	200W x 75H x 125D	£2.19 + s

SPECIAL OFFER!!

If catalogue ordered simultaneously with order for SAMOS cases - case price less 25%

CONDITIONS OF SALE

All prices are ex-VAT
If affixed with s add 8%
If affixed with H add 12½%
Z = Zero rated
Package & posting free
for orders over £3.00
Overseas orders add 15%
Cash with order. Cheques/Postal
Orders to Doram Electronics Limited,
P.O. Box TR8, Leeds, LS12 2UF
Small order handling charge of 40p
for orders under £3.00

DORAM'S NEW CATALOGUE - THE AMATEURS GOOD COMPANION



ONLY 60p

inc. post & packing.

Free up-date service until Aug. 1976.

DORAM "The Doorway to Amateur Electronics"

An Electrocomponents Group Company

NAME.....
ADDRESS.....
POST CODE.....

I enclose 60p. Please send me by return my Doram Catalogue.
(Overseas orders except B.F.P.O. please add 30p for post and packing surface only).

A Guide to Amateur Radio

PAT HAWKER


16th Edition

A Guide to Amateur Radio will assist the newcomer to learn about the hobby and help him to obtain a transmitting licence. It will also provide a valuable reference source for information on amateur receivers and transmitters as well as providing details of home-built equipment and new data on recent trends in equipment and simple multi-band aerials. The whole range of amateur equipment is covered—test gear, fixed, mobile and portable stations and constructional details are given of an economical h.f. receiver and a 1.8/3.5Mc/s phone/cw transmitter.

Entirely new material has been added giving useful information on international amateur radio organizations, on learning the morse code and on the international allocation of call-signs.

128 pages

£3.95

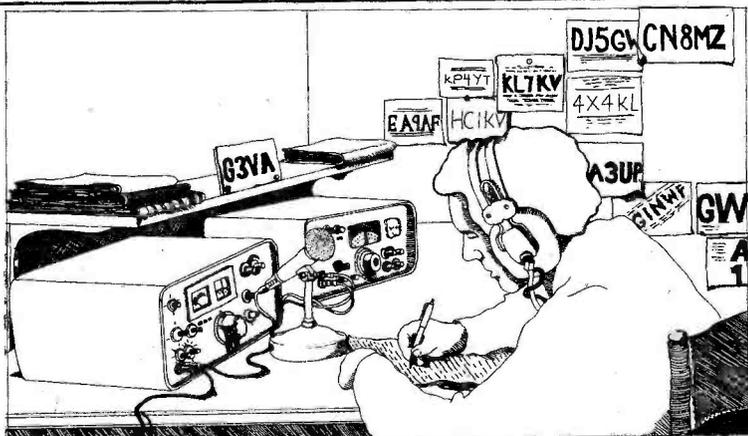

Please order from your bookseller or from:


Newnes-Butterworths
Borough Green, Sevenoaks, Kent

A.S.P. LTD
(DEPT. PW5), SIMMONDS ROAD, WINCHEAP
CANTERBURY, KENT Tel: (0227) 52436

TRANSFORMERS VAT 8%

CASED TRANSFORMERS

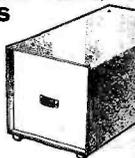Housed in smart resin coated steel cases with 3 core power cable and outlet socket, fused primary winding. Isolation types are fitted with 3-pin outlet sockets and are available with 110 volt or 240 volt output (please state). Auto types are fitted with 2-pin flat style sockets up to 500VA. 3-pin sockets from 750 to 3000VA. See Auto Isolation Sections for prices. Plugs extra.



SAFETY ISOLATING See catalogue for full range.
Prim. 120/240V. Sec. 120/240V. Centre Tap with screen.

VA (Watts)	REF. NO.	PRICE £	PLUGS CAGED 2 Pin+Earth	PRICE £	OPEN	POST £
60	140	9.48	0.98	5.02	0.72	
200	151	12.87	0.88	9.07	0.97	
250	152	14.47	0.98	10.51	1.18	

AUTO TRANSFORMERS

See catalogue for full range.

VA (Watts)	REF. NO.	PRICE £	PLUGS CAGED 2 & 3 pin	PRICE £	OPEN	POST £
1500	85	24.37	0.95	20.13	O/A	

MINIATURE & EQUIPMENT

Primary 240V with screen.		See catalogue for full range.	
VOLTS	MILLIAMPS	REF. NO.	PRICE £
3-0-3	200	238	1.75
0-6	500	500	2.34
0-6	1000	1000	2.32
9-0-9	100	13	1.75
0-9	330	330	1.75

12 & 24 VOLTS

Primary 200-240 Volts.		See catalogue for full range.	
AMPS	REF. NO.	PRICE £	POST £
12V	24V		
2	1	71	2.64
4	2	15	3.17
6	3	70	4.82
8	4	108	5.65

30 VOLTS

Primary 200/240V		Secondary 12, 15, 20, 24, 30V	
AMPS	REF. NO.	PRICE £	POST £
0.5	112	2.17	0.61
1	79	2.74	0.68
2	3	4.32	0.72
3	20	5.05	0.85
4	21	5.98	0.85
6	51	7.05	0.95
6	117	7.83	0.97
8	88	10.31	1.18
10	89	10.87	1.18

50 VOLTS

Primary 200/240V		Secondary 15, 25, 33, 40, 50V	
AMPS	REF. NO.	PRICE £	POST £
0.5	102	2.23	0.61
1	103	3.67	0.76
2	104	5.87	0.85
3	105	6.89	0.85
4	106	8.25	1.08
6	107	13.66	1.18
8	118	14.23	1.44
10	119	18.66	1.86

60 VOLTS

Primary 200/240V		Secondary 24, 30, 43, 60V	
AMPS	REF. NO.	PRICE £	POST £
0.5	124	2.72	0.72
1	126	4.08	0.72
2	127	5.63	0.85
3	125	8.20	0.97
4	123	9.45	1.18
5	40	10.73	1.18
6	129	13.00	1.36
8	121	16.43	O/A
10	122	21.99	O/A
12	189	19.24	O/A

BRIDGE RECTIFIERS

One Amp	Price	Four amp	Price
50P.I.V.	0.25	100P.I.V.	0.60
100P.I.V.	0.30	200P.I.V.	0.65
200P.I.V.	0.35	400P.I.V.	0.65
600P.I.V.	0.40	600P.I.V.	0.80

Two Amp	Price	Six Amp	Price
50P.I.V.	0.40	50P.I.V.	0.70
100P.I.V.	0.45	100P.I.V.	0.75
200P.I.V.	0.50	200P.I.V.	0.80
400P.I.V.	0.55	400P.I.V.	0.85

Add 12½% VAT on all prices.
Post 10p.

SPECIAL OFFER 2 KVA ISOLATORS

Fully impregnated & screened
2 Primary windings 110V each
2 Secondary windings 115V each
(2 matching transformers) £29.50 plus carriage
VAT 8%.

NEW! 2" and 4" PANEL METERS VAT 8%

2"	4"
Size: 60mm wide x 45mm high x 40mm deep.	Size: 110mm wide x 82mm high x 43mm deep
	I.R.
Movement	Ohms
0-5 micro A	0-50 micro A
0-100 micro A	580
0-500 micro A	170
0-1 mA	170
0-5 mA	170
0-10 mA	6
0-50 mA	0.5
0-100 mA	0.5
0-500 mA	0.5
0-1 Amp	0.5
0-2 Amp	0.5
0-25 Volt	15K
0-50 Volt	50K
0-300 Volt	300K
"S" meter	170
	"S" meter
	200

Vu meters are complete with detectors. Modern wide view. Price 2" £3.30 Post 10p. Price 4" £4.10 Post 20p. VAT 12½%. Lamps 95p per set. Plus 8% VAT.

FOR MULTI-METERS, INSTRUMENTS, RESISTORS, NEONS, TOOLS, POWER SUPPLIES, etc. Send for Catalogue.

NEW CATALOGUE 25p


NEW CATALOGUE 25p

detector to power units capable of handling hundreds of amperes.

It should be mentioned that germanium is not the only semiconductor, there being many covalently bonded crystalline compounds and a few elements which exhibit this effect. Silicon is commonly used today and, in all that has been written so far, "silicon" can be substituted for "germanium" as both elements have four bonding electrons and function in the same way.

THE JUNCTION TRANSISTOR

An ordinary junction transistor is basically a strip of semiconductor material, such as germanium or silicon, which has been processed so that it is either all n-type except for a narrow p-region in the middle (n-p-n transistor) or p-type except for a narrow n-region (p-n-p transistor). These connections are made to the strip, one to each end (emitter, collector) and one to the centre region (base). The p-n-p transistor has been very popular in Britain for many years, but n-p-n transistors are now becoming more common. The following discussion will be confined to the n-p-n transistor, although what is stated applies also to the p-n-p transistor, but with voltages reversed and "holes" in place of "electrons".

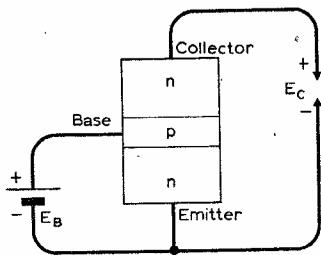

W187

Fig. 6: Polarities of voltages applied to a junction transistor, in this case an n-p-n type.

Transistors are normally biased by two external voltage sources, as shown in Fig. 6. When the base lead is disconnected, only a small leakage current flows through the transistor. If the base is given a small positive bias E_B , the emitter-base pn junction is biased in the forward direction and electrons are emitted from the emitter towards the base. Now the base region is very thin, so that a large fraction of the electrons travel on into the collector region where they are attracted by the electron shortage caused by the collector-emitter battery, E_C . This fraction, which is obviously less than unity, is given the symbol " α " and with most transistors has a value of about 0.98. The remainder of the electrons flow out through the base connection.

It has therefore been shown that a small current, I_b , flowing into the base causes a much larger current, I_c , to flow into the collector, and this is what is meant by "current amplification". The ratio, small change in I_c /corresponding change in I_b , is known as the "current gain" of the transistor of a particular working point, and it is denoted by the symbol " β ". Many transistors have a β of about 50. It will be shown later that $\beta = \alpha / 1 - \alpha$.

AMPLIFICATION

The emitter of a transistor corresponds to the cathode of a triode valve, the base to the grid and the collector to the anode. The polarities of the bias

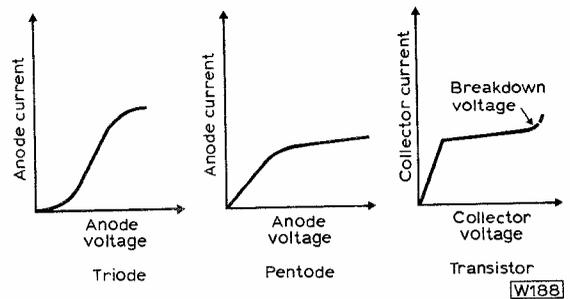


Fig. 7: Characteristics of a transistor compared to two types of thermionic valve.

voltages for an n-p-n transistor are similar to those of a triode, but those for a p-n-p type are different. It is convenient at this point to note two important differences between valve and transistor characteristics.

- (i) Transistors have a finite base current flow and consequently a low input impedance. Valves do not.
- (ii) The collector voltage/current graph of a transistor can be divided into two sections characterised by a low collector (output) impedance at low voltages, and a linear high impedance region of higher voltages. Valves show somewhat different characteristics as illustrated in Fig. 7.

Transistors can be operated in the three modes, common base, common emitter and common collector, similar to their valve counterparts, and these circuits will now be considered in greater detail.

COMMON BASE

The common base or "collector follower" amplifier circuit is used, like the common grid circuit, for VHF and UHF amplification, as well as to match low impedance to high impedance. Its theoretical and representative practical circuits are shown in Fig. 8.

The current amplification, A_I , is defined as small change in i_c /corresponding change in i_b which is equal to α . Voltage amplification A_V , is given by small change in output voltage/corresponding change in input voltage, and since, from Ohm's Law, $V = I \times R$,

this can be written as $\frac{i_c}{i_e} \times \frac{R_L}{r_{IN}}$, which is the same as $\alpha \frac{R_L}{r_{IN}}$.

The power gain, A_p , is the product of voltage and current gain which is $\alpha^2 \frac{R_L}{r_{IN}}$ or just $\alpha \cdot A_V$.

The input impedance is defined as r_{IN} = small change in e_{be} /corresponding change in i_b . However, from Ohm's Law, $V = I \times R$, so that

$$e_{be} = i_e (r_{IN} + R_S) = i_e \cdot r_{IN} + i_e R_S.$$

$$\therefore i_e r_{IN} = e_{be} - i_e R_S$$

$$\therefore r_{IN} = \frac{e_{be}}{i_e} - R_S$$

It is thus shown that the total effective R_{in} is the sum of the transistor input impedance and the source impedance, R_S , of the input. The transistor input impedance is found to vary greatly with R_L .

The output impedance, r_{out} , is small change in e_{cb} / corresponding change in i_c .

This quantity tends to increase as the source impedance, R_s , increases.

Examples

Fig. 9 depicts an impedance converter for matching a 200Ω (low impedance) moving coil microphone to a 24V transistorised amplifier with a 10kΩ input impedance. A low-noise n-p-n medium power transistor with an α of 0.990 is used. Find, approximately, (a) current (b) voltage (c) power gains of the circuit, assuming $r_{IN} = 200\Omega$.

(a) Current gain = $\alpha = 0.99$

(b) Voltage gain =

$$\alpha \frac{R_L}{r_{IN}} = \left(0.99 \times \frac{10,000}{200} \right) = 50 \text{ approx}$$

(c) Power gain = $A_I A_V = 50$ approx

Note that R_L has been made as small as possible to ensure low input impedance and that a resistor R_1 has been included in series with the input to increase the transistor output impedance, typically,

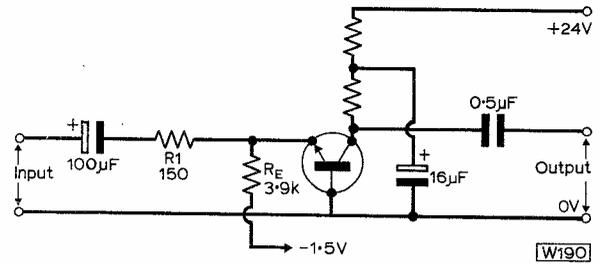


Fig. 9: Circuit using a collector-follower as an impedance matching device, the characteristics of which are discussed in the text.

to over 100kΩ. This is, of course, shunted by R_L , so that the overall output impedance is nearly 10kΩ, as required.

COMMON EMITTER

The theoretical and practical representative circuits of common emitter amplifiers are shown in Fig. 10. The common emitter circuit is widely used for AF and many lower frequency RF applications where a

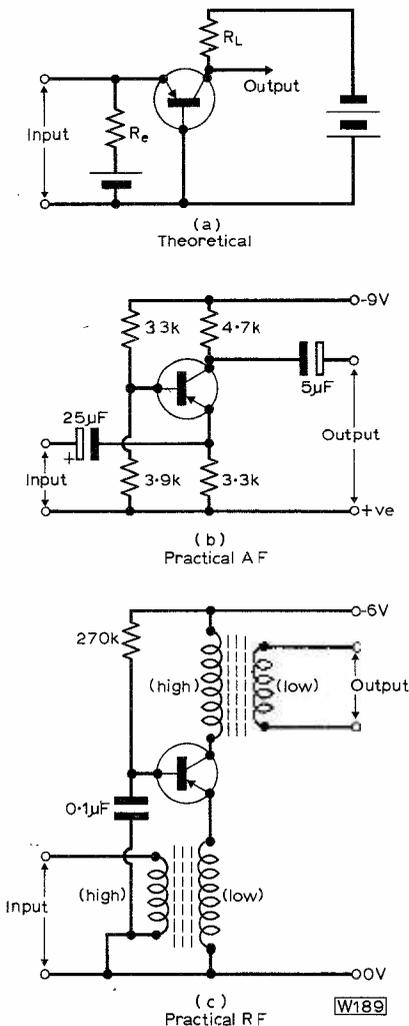


Fig. 8: Transistor in a collector-follower configuration (a) with a practical circuit for audio applications (b) and high-frequency use (c).


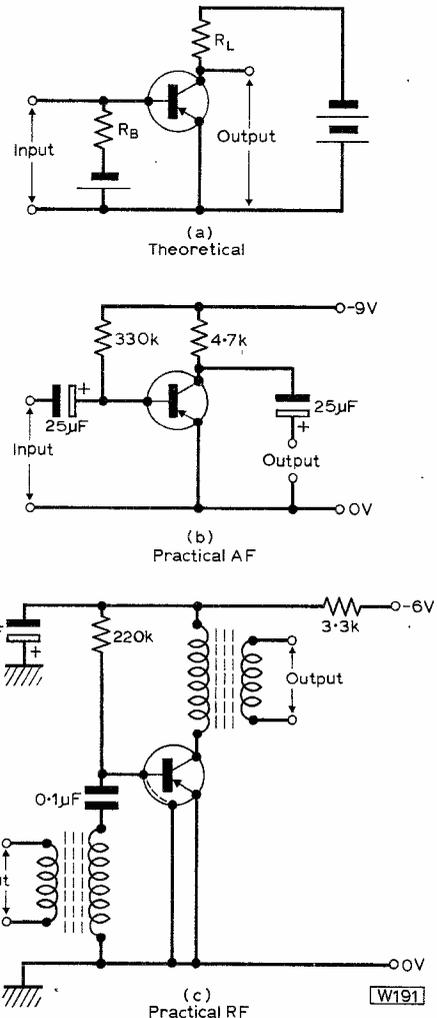


Fig. 10: Theoretical circuit (a) and two practical circuits (b) and (c) for a common-emitter high gain application.

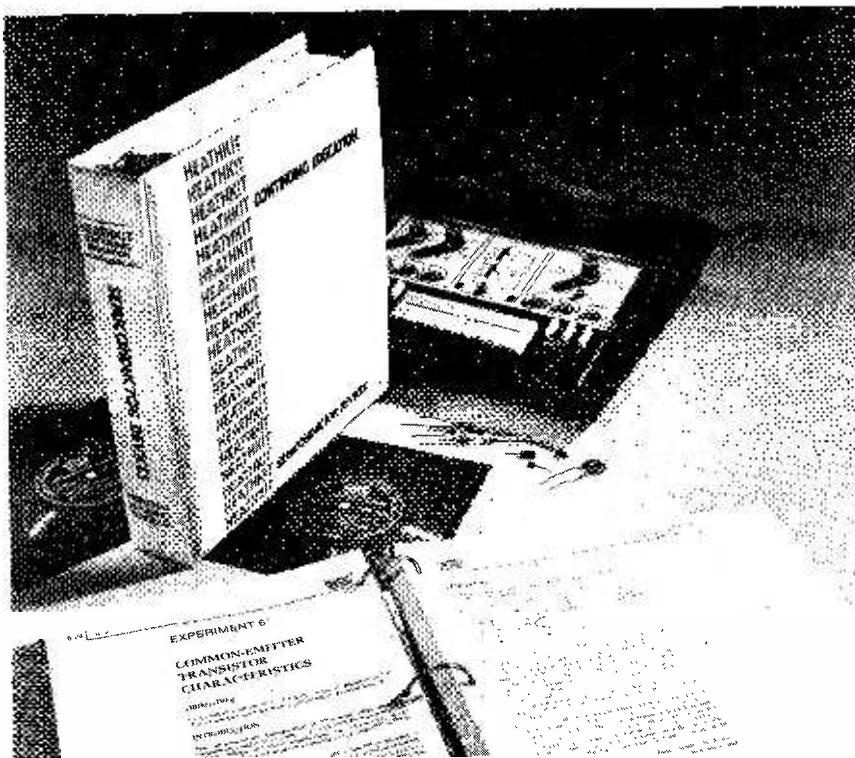You can learn quite a lot about electronics, just by building a Heathkit.



Now we can teach you even more.

Part of the satisfaction in building a Heathkit is finding out how it's made and how it operates.

And now, with the introduction of the Heathkit Continuing Education Series, you can learn even more.

There are four Heathkit Individual Learning Programmes available in this series: DC Electronics; AC Electronics; Semiconductor Devices; and Digital Technology.

Each programme is self-instructional, allowing you to study at your own pace—

repeating any section as many times as you need. The comprehensive course and kit experiments will lead you step by step to a thorough knowledge of electronics.

And, when you've finished the programme, you can also take an optional final examination.

If you'd like to learn more about the Heathkit Continuing Education Series, just post the coupon (enclosing 10p for postage). Heath (Gloucester) Limited, Dept. PW-66, Bristol Road, Gloucester, GL2 6EE.

Tel: Gloucester (0452) 29451. **HEATHKIT**

To: Heath (Gloucester) Limited, Dept. PW-66, Gloucester, GL2 6EE.

Please send me a leaflet about the Continuing Education Series.

I enclose a 10p stamp for postage.

Name _____

Address _____


Postcode _____

HEATH
Schlumberger

EASY TO USE AVAILABLE
WITH HEATHKIT FOR ANOTHER
COLOUR PLAN

tecknowledgegey in consumer ICs - and their applications

SGS Audio ICs

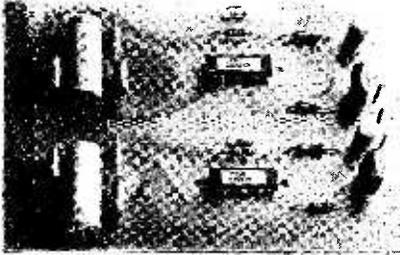

The much heralded TDA2020 is here. And just to make sure that you don't go wrong, so is the SGS application test circuit PCB for a stereo 15 + 15 (RMS) Hi Fi amplifier.

Prices :	IC	AUDIO	DISCRETES
TBA810AS	+HS 1.09	ZTX107/8/9	14p
TCA040E	+HS 1.80	ZTX413(LN)	17p
TDA2020	2.99	ZTX212/3/4	16p
FM LINEAR	ICS	BD 535 npnp	7A/60v 52p
MC1350	0.70	BD536 npnp	53p
CA3089	+QC 1.94	BD377 npnp	3A/50v 29p
TBA120	+QC 1.00	BD378 npnp	32p
MPX LINEAR	ICS	BD515 npnp	2A/45v 27p
MC1310P	+LED 2.20	BD516 npnp	30p
CA3090AQ	+LED 3.75	BD609 npnp	10A/90v 70p
		BD610 npnp	102p

We've moved

To accommodate expanded R & D facilities, AMBIT has moved sales and administration to 25 High St. Brentwood. The existing 37 High Street premises are retained for the engineering activities.

One of the first products of this move has been the development of a TV sound tuner, from an "off air" system, using its own varicap UHF TV tuner, with ICIF amplifiers and block filters by TOKO. And then one of our best ever circuits - an electronic touch tuner, with scanning mode, and facilities for 6 preset stations. The unit is suitable for use with FM, and now AM of course, and offers a complete tuner system without any moving parts. Selection is by means of touch tuning in all cases, with manual scan and preset switching automatically interlocked.

Our R&D facilities are available for general consultancy to OEMs: further details on application. Standard project estimation fee, including project evaluation comment data is £15.00 payable in advance.


Modules & Kits

New modules:

8011	Totally touch tuned varicap controller built	£14.99.
8005	Larsholt tunerset accessory unit, with pilot tone filter and audio stages, rectifier, IC stabilizer, meter driver circuits.	£4.99 (kit)
8001	55kHz low pass filter (mpx birdy filter)	£2.35 built £1.75 (kit)
2001	Stereo scratch and rumble filter, with continuously variable operating frequencies.	£5.80 (built) £4.60 (kit)
3000	Stereo control preamp - a wide dynamic range, low distortion AF preamp, with vol, bal, bass and treble controls.	kit £5.78
2020K	The TDA2020 stereo amp kit photographed on the left.	£7.85
7700	TV off air UHF sound tuner - built	£26.00 (4 preset stations)
9000 kit	AM/FM mpx tuner chassis, with mech. tuner	£17.50
7004 kit	MW/LW varicap tuner module, inc. ferrite rod	£9.95
7252	HIFI MOSFET FM tuner module by Larsholt	£24.00
7253	HIFI FET FM tuner module inc decoder	£24.00
5500	Hi Q MOSFET varicap tunerhead by TOKO	£11.25
EC3302	FET tunerhead from TOKO	£5.00

Complete FM Tuner Kits, inc case, for use with the above modules: details SAE please. Prices range from £40 - £60.

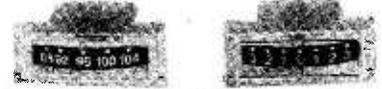Amongst our various accessories for entertainment electronics is a range of FM tuning, frequency and sig. strength meters with 12v, 50mA bulb. £2.50 ea.



ambit international
Trade Mark
25 high street, brentwood,
essex. cm14 4rh.
 tel: (0277) 216029
 tlx: 995194

Free price list with an SAE, catalogue of modules and parts 40p., including postage and VAT.

General Terms: CWO please, official bodies and companies please note min. invoice £7.50. PP for CWO orders 22p per order. (UK and Eire). Overseas customers please include sufficient for postage. VAT is not included, and must be added at 25%, in stock orders despatched within 48 hours.

JUST PUBLISHED

VHF/UHF MANUAL

(Third edition)

by

D. S. Evans, PhD, AIM, G3RPE, and G. R. Jessop, CEng, MIERE, G6JP

Everything about vhf/uhf radio techniques—in a single book

Since 1969 the RSGB VHF/UHF Manual has been a best seller around the world, as the standard textbook on techniques and equipment for amateur radio transmission and reception at frequencies over 30MHz. (You will find a copy in many a professional radio technician's bookcase as well.)

Now we are proud to announce the latest and best-ever edition.

Over 400 large-format (180 x 245mm) pages packed with ideas, information and constructional details of tried and tested equipment, each specialist topic contributed by an acknowledged expert in the field.

There are chapters on receivers, transmitters, space communications, filters, aerials, microwaves and much more. Simple amateur television is covered, and a data section provides valuable facts and figures to help the constructor. Many of the designs make use of integrated circuits, and the microwave chapter gives details of equipment for use up to 24GHz.

It is the most comprehensive and up-to-date review of vhf and uhf techniques available today. If you are seriously interested in operation at these frequencies, it is a book you must have.

Price £4-95, plus 68p postage and packing, direct from the publishers

THE RADIO SOCIETY OF GREAT BRITAIN,
35 Doughty Street, London WC1N 2AE

high gain is necessary. It is seldom found in VHF applications because common base circuits are more stable and give greater gain.

The common emitter current gain, often denoted by β , is given by $\beta = \frac{\alpha}{1 - \alpha}$, which is derived as follows:— $\alpha = i_c / i_e$. But $i_e = i_c + i_b$ (Using Kirchoff's 1st Law) (as)

$$\therefore \alpha = \frac{i_c}{i_c + i_b} \therefore \alpha (i_c + i_b) = i_c \text{ and eventually}$$

$$\frac{i_c}{i_b} = \frac{\alpha}{1 - \alpha} = \beta$$

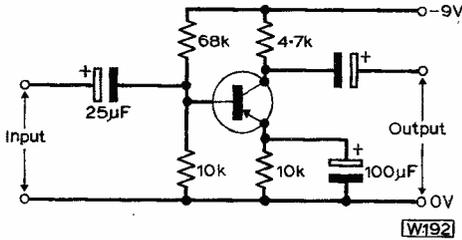


Fig. 11: Typical audio stage using the common-emitter circuit.

Thus, if for a given transistor $\alpha = 0.98$, then $\beta = \frac{0.98}{1 - 0.98} = 49$.

As for common base operation, the voltage gain is calculated from Ohm's Law:—

$$A_v = \frac{\text{small change in } e_c}{\text{corresp. change in } e_{cb}} = \frac{i_c \times R_L}{i_b \times r_{IN}} = \beta \left(\frac{R_L}{r_{IN}} \right)$$

The power amplification, being the product of voltage and current amplifications, is given by

$$\beta^2 \left(\frac{R_L}{r_{IN}} \right) \text{ or } \beta(A_v).$$

As with valves in the common cathode (normal)

configuration there is a phase change of approximately 180° between output and input.

Similarly the input impedance $r_{IN} = \left(\frac{e_{bc}}{i_b} - R_s \right)$.

This quantity is greater (about $1k\Omega$ for a small AF transistor) than in the common base mode, and decreases slightly with increasing R_L . The output impedance r_{out} is considerably lower than in the common base mode, and decreases somewhat with increasing R_s .

Fig. 11 depicts the first AF stage in a transistor radio set. Find (a) the current gain (b) the voltage gain (c) the power gain, if the transistor has an α of 0.983 and the input impedance is $1k\Omega$. Neglect the loading of the following stage.

(a) $\alpha = 0.983 \therefore \beta = \frac{\alpha}{1 - \alpha} = \frac{0.983}{0.017} = 58$ approx

(b) Voltage gain $= \beta \times \frac{R_L}{r_{IN}} = \frac{58 \times 4.7 \times 10^3}{1 \times 10^3} = 273$ approx


(c) Power gain $= \beta \times A_v = 58 \times 273 = 15834$

COMMON COLLECTOR


This third configuration, sometimes known as the "emitter follower", is used only for matching a high impedance to a low impedance. It is not commonly found elsewhere because little power gain is possible, the voltage gain being less than unity. The current gain is about the same as for common emitter operation. Input impedance is found approxi-

mately from $\frac{\beta}{R_L}$, output impedance from $\frac{R_s}{\beta}$.

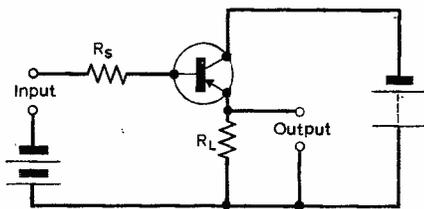Although these are only approximate it is found that accurate values are seldom needed. Fig. 12 shows theoretical and practical common collector circuits.



(a) Theoretical

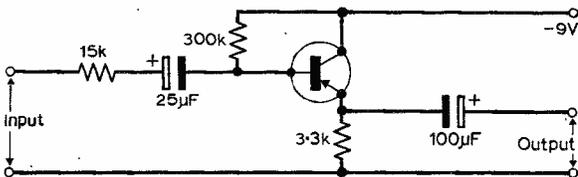

(b) Practical

Fig. 12: Theoretical and practical circuit for the emitter-follower which can be used to convert a high impedance circuit to a low one.

Practical Wireless, June 1976

PW TECHNICROSS PUZZLE

Solution to No. 13
presented last month

1	F	2	P	3	S	4	T	5	R	6	I	7	D	8	E	9	N	10	C	11	Y
12	O	13	R	14	A	15	L	16	O	17	D	18	I	19	A	20					
21	R	22	N	23	W	24	I	25	R	26	E	27	L	28	E	29	S				
30	W	31	O	32	O	33	D	34	E	35	N	36	I	37	E	38	T				
39	A	40	R	41	R	42	I	43	S	44	L	45	E	46	47	48	49	50	51	52	53
54	R	55	E	56	A	57	D	58	S	59	M	60	61	62	63	64	65	66	67	68	69
70	D	71	M	72	73	74	75	76	77	78	79	80	81	82	83	84	85	86	87	88	89
90	L	91	E	92	A	93	94	95	96	97	98	99	100	101	102	103	104	105	106	107	108
109	Y	110	111	112	113	114	115	116	117	118	119	120	121	122	123	124	125	126	127	128	129
130	131	132	133	134	135	136	137	138	139	140	141	142	143	144	145	146	147	148	149	150	151
152	153	154	155	156	157	158	159	160	161	162	163	164	165	166	167	168	169	170	171	172	173
174	175	176	177	178	179	180	181	182	183	184	185	186	187	188	189	190	191	192	193	194	195
196	197	198	199	200	201	202	203	204	205	206	207	208	209	210	211	212	213	214	215	216	217
218	219	220	221	222	223	224	225	226	227	228	229	230	231	232	233	234	235	236	237	238	239
240	241	242	243	244	245	246	247	248	249	250	251	252	253	254	255	256	257	258	259	260	261
262	263	264	265	266	267	268	269	270	271	272	273	274	275	276	277	278	279	280	281	282	283
284	285	286	287	288	289	290	291	292	293	294	295	296	297	298	299	300	301	302	303	304	305

receiver calibration AID

F.G.RAYER

IF a home-built receiver or a signal generator is to be calibrated, or a receiver with errors in calibration is to be adjusted, some accurate means of obtaining frequencies for this purpose is required. Assuming that an accurately calibrated signal generator is not available, one method is to employ a harmonic marker giving a range of known frequencies. Such a marker is generally crystal controlled and thus relatively expensive. However, it is possible to dispense with crystals and still obtain a degree of accuracy which is greater than that with which the usual tuning scale can be read visually and which is thus high enough for most purposes.

The unit described here is not crystal controlled, but provides frequencies of 100kHz, 1MHz and 5MHz, and their harmonics, and can be of enormous aid in calibrating the tuning scales of receivers covering frequencies to 30MHz or higher.

HARMONIC CALIBRATION

Fig. 1 shows some of the calibration signals obtained from the unit, and which might be marked on a receiver tuning scale. These will explain how the calibrator aid is used. One fundamental frequency provided is 100kHz, and its harmonics are multiples such as 200kHz, 300kHz, 400kHz, and so on. Scale "A" is a typical medium wave range for a receiver and the 100kHz harmonics furnish calibration points from 600kHz to 1500kHz (or 1.5MHz). If necessary, the 1000kHz mark is at once identified by the 1MHz fundamental frequency provided by the unit.


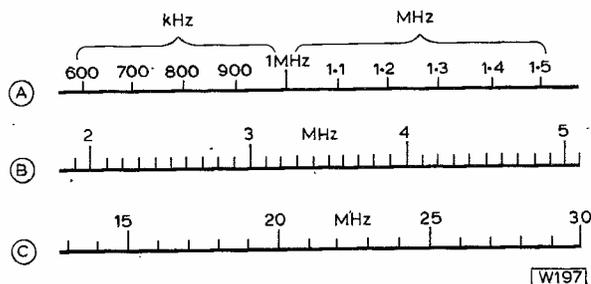


Fig. 1: Typical dial calibrations on a receiver, all of which can be checked with the calibrator.

Scale "B" is a short wave band, in this instance covering from 1.8MHz to 5.1MHz. The 2, 3, 4 and 5MHz tuning points are given by harmonics of the 1MHz frequency and the 100kHz (or 0.1MHz) harmonics fill in between these. This permits calibration for an Amateur band such as 1.8-2.0MHz or 3.5-3.8MHz to be made easily.

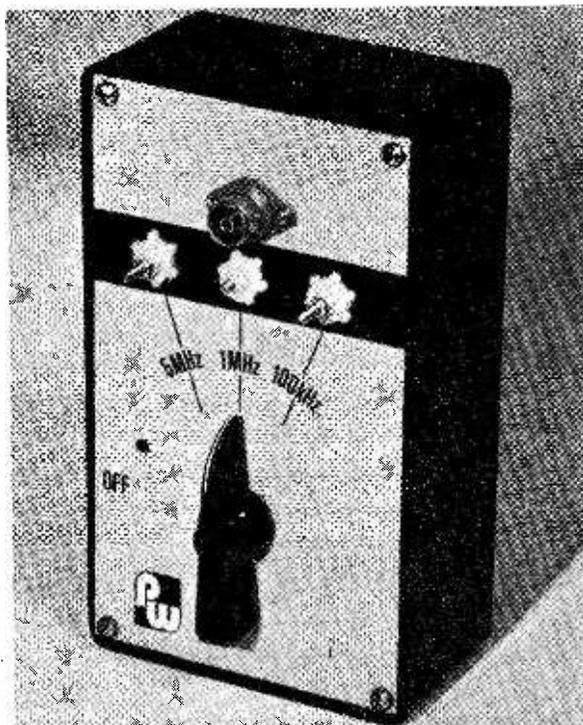Scale "C" is that of a higher frequency range with 5MHz points from 15MHz to 30MHz given by



The author's prototype built on a metal panel and fitted in a plastic box. General radiation may provide sufficient signal for most purposes but for maximum output the signal can be taken from the coaxial socket.

harmonics of the 5MHz frequency, and 1MHz intervals completed by the 1MHz signal harmonics. There is of course no need to provide only those calibration marks shown in Fig. 1. The 100kHz signal and its harmonics, the 1MHz signal and its harmonics, and the 5MHz signal and its harmonics may be used without breaks over the whole frequency range, up to the frequency limit at which they can no longer be detected.

Each range of harmonics is obtained without any indication of the order of multiplication. For example, if a MW band is dealt with (such as "A") marker signals will be heard at 100kHz intervals. To number these, it is necessary to discover what the frequency of one such mark is. Here, the 1MHz signal does this, and the scale can be counted off and numbered up and down from this point.

With a range similar to that at "B" 5MHz could be identified from the calibrator and 1MHz harmonics counted off from this. With range "C" it would be necessary to identify readings to one 5MHz point, either by reference to the expected tuning coverage of the receiver, or by finding a known band, such as the 14MHz or 21MHz Amateur band, by listening. Once any single frequency is identified, calibration points can be counted from it, and numbered.

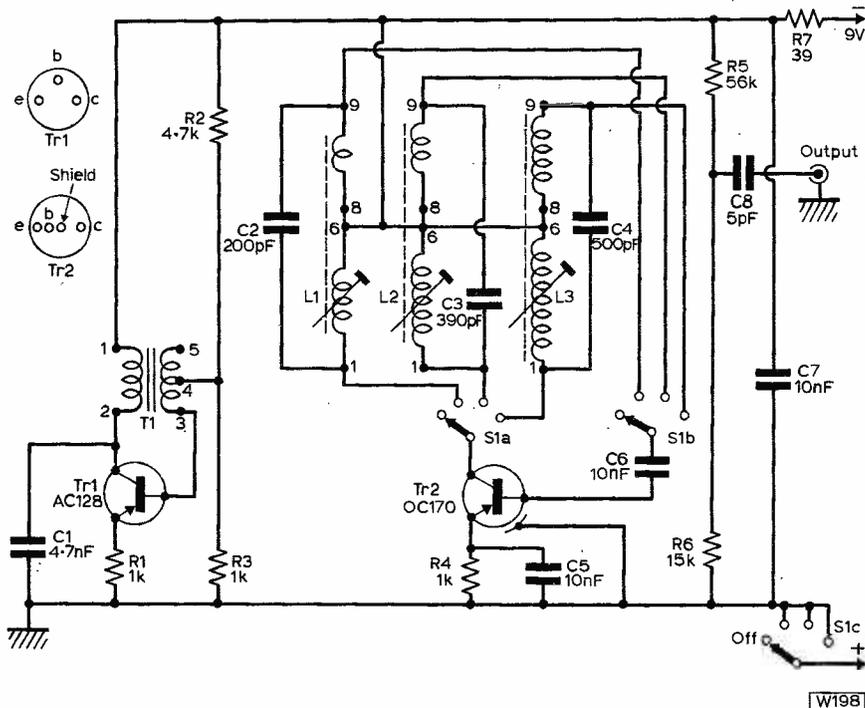


Fig. 2. Circuit of the calibration aid and transistor leadout diagrams. Modulation is obtained by means of the common load resistor R7. If the audio modulation is absent reverse ONE winding of transformer T1.

CIRCUIT

In Fig. 2, Tr1 is an audio oscillator and modulates the RF oscillator because of the common resistance R7, to allow easy identification of the marker signals. Should T1 be other than listed, it may be necessary to reverse connections to one winding to obtain oscillation, or to change C1 or R1 to secure a suitable tone.

Transistor Tr2 is the RF oscillator and the 4-way switch S1 transfers collector and base circuits to L1, L2 or L3. These inductors are tuned by capacitors C2, C3 and C4 and are set to 5MHz for L1, 1MHz for L2, and 100kHz for L3, by adjustment of the cores. Signal output is taken from the capacitor C8, but in many cases no electrical connection to the output socket is necessary. One pole of the switch breaks the battery circuit.

CONSTRUCTION

Most of the components are assembled on plain perforated Veroboard 95 x 41mm (3³/₄in x 1⁵/₈in) as in Fig. 3. A bracket cut from scrap metal is bolted to the board which allows the switch to be used to mount the board on the panel. The collector lead of Tr2 and C6 are connected directly to tags S1a and S1b of the switch. S1c has a flexible connection with a positive clip while the battery negative runs from R7. Put sleeving on all leads where necessary.

The case used has a panel 152 x 90mm (6 x 3¹/₂in) but any box of somewhat similar size would be satisfactory. The switch and assembled circuit board fit as in Fig. 4. Holes are also drilled for the three coils and for the output socket. The latter holds a bracket, fitted to retain the battery at the end of the case.

For easy soldering, the coil pins should be scraped first and lengthy heating must be avoided here or the pins may become loose in the formers. Wiring can be finished off from Fig. 4 and a check made that all is in order.

COIL ADJUSTMENT

The capacitor values are chosen so that adjustment of a coil core allows a fairly small band of frequencies around that wanted to be tuned. Before the unit can be used the cores have to be set with the aid of a radio receiver. To set L3 to 100kHz tune the receiver to the long wave programme of BBC on 200kHz. Switch the calibrator to 100kHz and turn the core of L3 until a whistle is heard on the programme. This is the second harmonic of 100kHz. A zero beat or central position will be found, which is

★ components list

Resistors

R1 1kΩ	R5 56kΩ
R2 4.7kΩ	R6 15kΩ
R3 1kΩ	R7 39Ω
R4 1kΩ	
All 1/4 or 1/2 watt 10%	

Capacitors

C1 4.7nF	C5 10nF
C2 200pF 5M	C6 10nF
C3 390pF 5M	C7 10nF
C4 500pF 5M	C8 5pF

Semiconductors

Tr1 AC128	Tr2 OC170
-----------	-----------

Miscellaneous

T1, AF driver transformer (Doram 217-668 or Home Radio TR63. L1, 'yellow' range 4, L2, 'yellow' range 3, L3, 'yellow' range 1 (Denco, valve type). S1, 3-pole 4-way wafar switch. Knob, Output socket. Case approx 152 x 90 x 50mm deep with metal panel. Plain veroboard 95 x 41mm approx. Battery and clips.



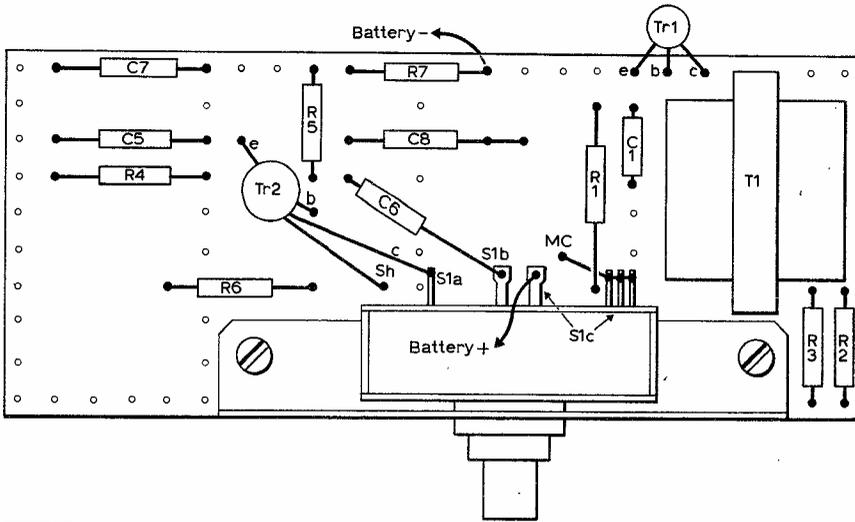


Fig. 3. Top view of the rear board on which the calibrator is constructed. A metal bracket carries the water switch. The lock nuts on the switch spindle being used to secure the unit to the panel.

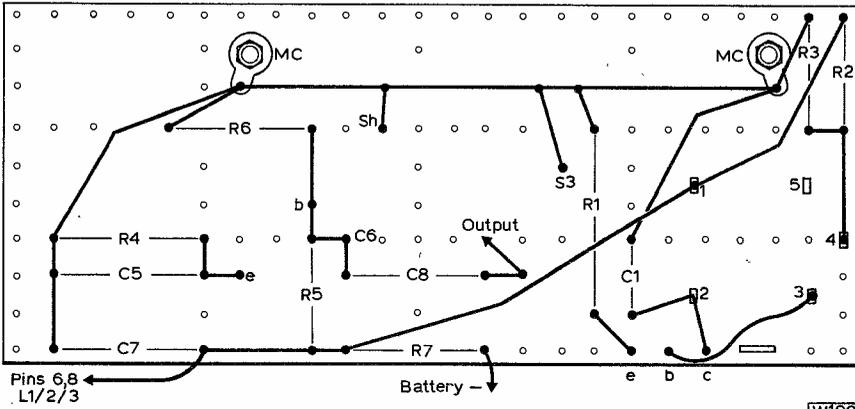

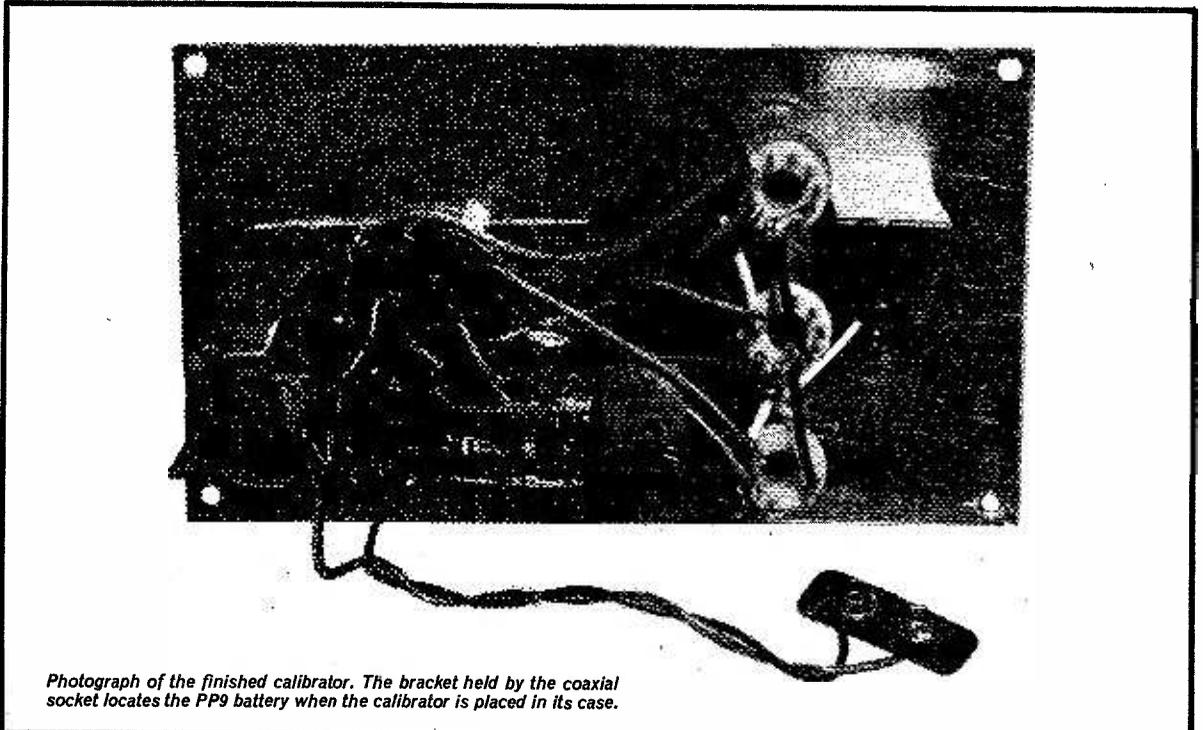The wiring under the board in most cases the component leads can be used instead of cutting them short. Unwanted pins can be soldered to the board as required and used for anchoring points.



Photograph of the finished calibrator. The bracket held by the coaxial socket locates the PP9 battery when the calibrator is placed in its case.


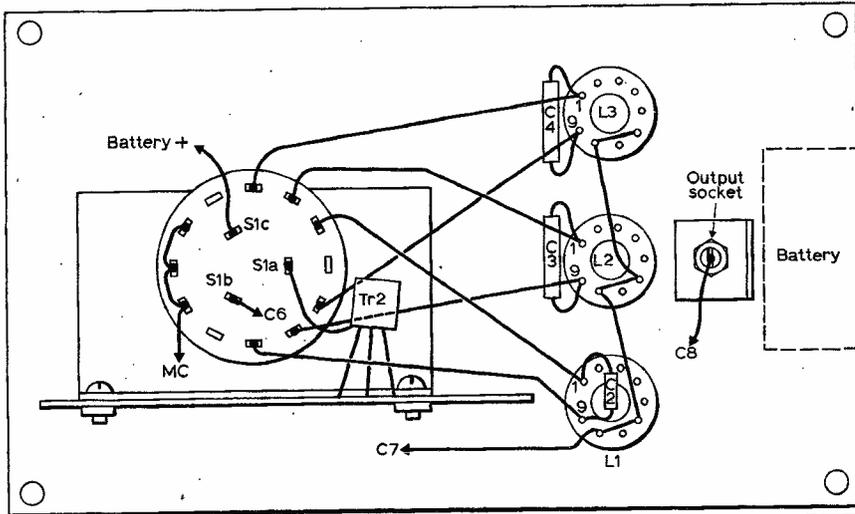


Fig. 4: Details of the wiring between the coils and the selector switch. If it is not possible to obtain the correct zero beat with a particular coil the parallel capacitor can be altered in value. Ensure the slug in the coil is moved through its entire range before changing any of these capacitors. The photograph below is another shot of the finished calibrator.

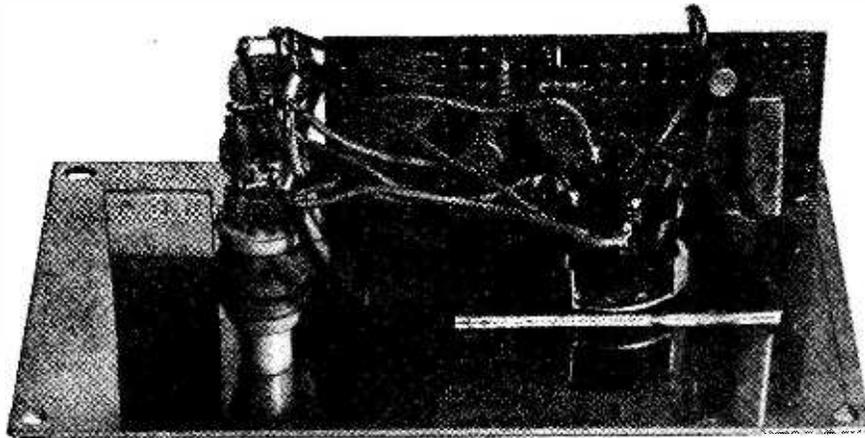

the correct position. Turning the core either way from this will result in a whistle which rises in pitch.

The core of L2 is most easily set to 1MHz by using a short wave receiver to tune in a standard frequency transmission on 5MHz and adjusting L2 for zero beat. Check that this is correct by noting that the signal comes up at 1MHz or 1000kHz on the MW band of the receiver. L1 can also be adjusted to 5MHz by this means.

One range may help provide tuning points for another. For example, when the 100kHz frequency is set using the BBC's long wave transmitter, 1000kHz can be identified on the receiver MW band and L2 can be tuned to this. Harmonics of 1MHz will then allow a fairly accurate location of 5MHz on the receiver, to find the standard frequency signal, so that L2 can be correctly set, and also L1.

Once the cores are correctly positioned, they will need only a small re-adjustment occasionally, and this can be done in a few moments with the aid of the 200kHz and 5MHz signals mentioned. The long term stability is of course not that of a crystal controlled oscillator, but if the calibration is checked before using the calibration aid, accuracy easily equals the ability to read an ordinary tuning scale.

For long and medium waves, it may be sufficient to place the unit near the receiver, especially if the latter has a ferrite rod aerial for these bands. For higher frequencies, and higher orders of harmonics,

more coupling is required. A lead from the output socket can then be placed near the receiver aerial socket or can be directly connected, as necessary. With the usual communications type receiver or reasonably efficient short wave receiver, the 1MHz and 5MHz harmonics can be heard up to 30MHz. The upper limit at which the 100kHz harmonics can be heard depends on the receiver, and these become rather difficult to detect above about 5MHz, but can be heard well beyond this with a sensitive receiver.

When preparing the scales for an actual receiver, note that the high-frequency end of a band is generally to the left, and that marking become progressively closer together. Despite this, they will have a regular appearance when counted off systematically.

To calibrate or check the calibration of a signal generator tune a receiver to various harmonics of the calibration aid and then tune the generator to zero beat and mark its scale. Where the receiver does not cover the generator frequencies completely, a harmonic of the generator signal may be used. For example, 900kHz on the receiver can be used for 450kHz on the generator, or second harmonic.

As the unit is not crystal controlled, remember to check the frequency when it is used to calibrate other equipment. The cores may be locked with 6BA nuts.

D.W.


EDITORIAL ANNOUNCEMENT

NEW!

PRACTICAL WIRELESS

PCB SERVICE FOR READERS

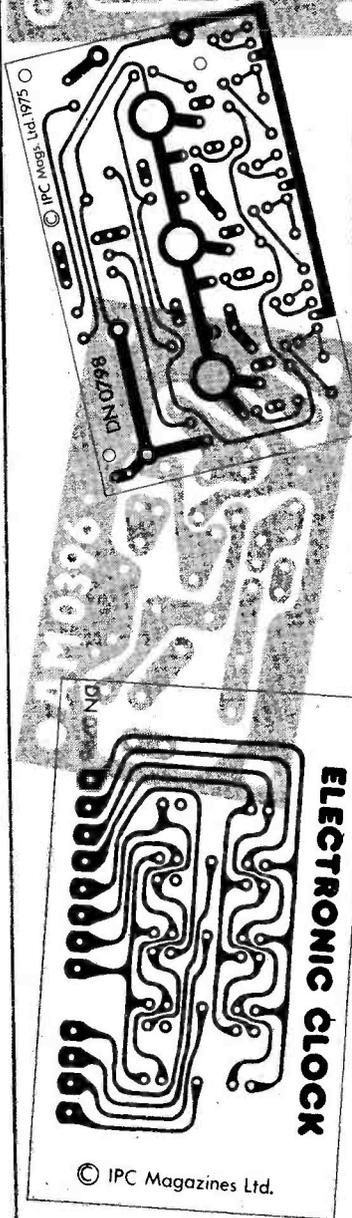Our new PCB service is well under way and we are now able to add PCBs for two popular projects published prior to December 1975. All boards, except SRBP, are epoxy glassfibre, drilled and roller-tinned.



To:- READERS PCB SERVICES LTD, PO BOX 11, WORKSOP, NOTTS

Please supply PCB/s as indicated by tick/s in box/es

Issue	Project	Ref	Price P/P	
Mar 75	Electronic Organ (set of two)	AM0315 AM0318	7.56 + 25	<input type="checkbox"/>
Sep 75	Electronic Clock (set of three)	DN0795 DN0796 DN0797	2.40 + 15	<input type="checkbox"/>
Dec 75	Radio-Pickup Link	DN0792	0.98 + 12	<input type="checkbox"/>
Dec 75	Random Number Selector	DN0793A	0.98 + 12	<input type="checkbox"/>
Dec 75	Sound-To-Light Display	DN0798	1.15 + 12	<input type="checkbox"/>
Dec 75	12V PA System	DN2/JM	0.98 + 12	<input type="checkbox"/>
Dec 75	Disco System, Amplifier (2 required)	each AM0421	3.40 + 18	<input type="checkbox"/>
Dec 75	Disco System, Light Modulator	AM0423	2.70 + 18	<input type="checkbox"/>
Jan 76	Music Box	SRBP DN1/JM	2.25 + 18	<input type="checkbox"/>
		glassfibre DN1/JM	3.00 + 18	<input type="checkbox"/>
Jan 76	Emergency Light Unit	AM0419	3.50 + 18	<input type="checkbox"/>
Mar 76	CMOS Crystal Calibrator	AM0438	1.19 + 12	<input type="checkbox"/>
Apr 76	DF Receiver (set of two)	DN4/JM DN5/JM	1.92 + 15	<input type="checkbox"/>
Apr 76	Wobblulator	AM0443	1.08 + 12	<input type="checkbox"/>
Apr 76	Auto. Slide Synchroniser	AM0441	2.33 + 15	<input type="checkbox"/>

Post and packing is for one board or set of boards. Prices include VAT.

Remittances with overseas orders must be sufficient to cover despatch by sea or air mail as required. ACCESS welcome. Send card number only.

I enclose Postal Order/Cheque No..... for £..... made payable to READERS PCB SERVICES LTD.

NAME.....

ADDRESS.....

Post Code.....

Any correspondence concerning this service must be addressed to READERS PCB SERVICES and not to the Editorial offices.

A-GAIN, A MEASURE OF SUCCESS!

What's the problem? Transistors not matched? Gain suspect? Diodes open or short circuit? Don't GUESS—FIND OUT. The bulk of your semi-conductors can be measured for their vital statistics by this easy-to-use, self-contained, ever ready, professional style test set.

A VERSATILE TRANSISTOR TESTER




Plus: VERTICAL AERIALS for 144 MHz

Fred Judd G2BCX shows how readily available materials can be assembled into vertical aerial systems giving worthwhile gain.

PREAMPLIFIER for the PW DISCO SYSTEM

Lack of bass with some ceramic cartridges can be corrected with this equalising circuit, designed for two turntables.

DON'T MISS THIS ISSUE!-ON SALE IN JUNE

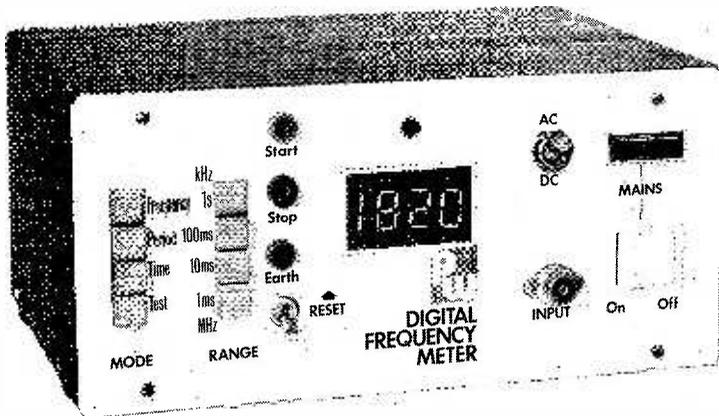

DIGITAL FREQUENCY METER

T. J. JOHNSON

Specification

Frequency range	0-15MHz
Input voltage	60mV to 10V
Input impedance	1kΩ to 10kΩ
Period	1ms to 9999s (2½ hours)
Time interval	1ms to 9999s
Gate times	100µs to 1s
Accuracy	1 part in 10 ⁵ ± 1 count
Stability	Dependent on crystal— typically 1 in 10 ⁵ @ 20°C
Input waveform	Immaterial
Display	4 digits, 7-segment filament type

WHEN first designing the counter, cost was the first consideration, since it needed to be a versatile instrument, and within the pocket of the home constructor. At the same time it needed to compete favourably with commercial designs, and for this reason the counter design has been kept as simple as possible.

One of the major considerations was in deciding the type of display to be used. Having surveyed the various types available, it was decided to use Doram filament types, as they come complete with ready made PCB's. Alternatively, LED's may be used.

CIRCUIT DESCRIPTION

The input stage centres around IC1 which has 3 functions; (a) To amplify the incoming signal (or attenuate as appropriate) suitable for operating the counter. (b) To shape the signal into a waveform for operating the counter, and (c) To provide a suitable impedance so as not to unduly load the circuit under test.

The crystal clock, provided by Tr1 and 2 operates at 100kHz, to provide a square wave to operate the counter. IC3-7 divide the clock down to the required times. The display consists of a four stage counter, IC11-IC14. Four BCD stores, IC15-IC18, and the decoder/driver, IC19-IC22, driving the display. The control logic of the counter is centred on the pulse generator, IC9 and IC10. When in the frequency mode, the signal, having been "cleaned up" is passed into the counter IC14, via the switching system and the gate of IC10, the state of which is determined by the flip flops (FF1 and 2) in IC9.

In operation a clock pulse will change the state of the second flip flop, which in turn will open the gate in IC10 and allow the signal to pass. When the clock pulse ends, the state of the flip flop is reversed, thus ending the count. At the same time a condition is passed to the pulse generator causing it to operate. This has three functions; (1) To enable the stores, thus registering the count in the displays, (2) To reset the counters to zero, (3) To set the first flip flop in IC9, thus enabling the second flip flop to operate on the next clock pulse.

In the **period** mode, the clock pulse is continually passed to the counter, and the incoming signal now operates the flip flop in IC9. In the **time** mode the same happens, except that the control signal to IC9 comes from the monostable IC2. This provides a short pulse when triggered by a logic "0" at either SK1 or SK2. In the **test** position the switching system selects a clock time of one second and a frequency of 1kHz, the counter thus has a display of 1000.

OPERATING PRINCIPLES

Referring to Fig 1, the input signal is applied to the input of a counting stage with its associated display, via a switch. Assume for the moment that the signal is a square wave of 1000Hz, and the switch is closed for exactly 1 second. In that time therefore 1000 cycles will have passed through to the counter. If the counter has 4 decades driving 4 separate dis-


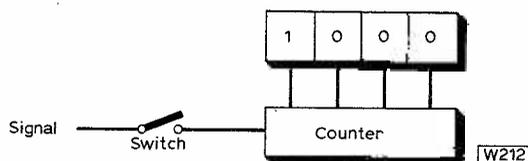


Fig. 1: Block diagram showing the path of a signal applied to the counting stage.

plays, then the number displayed will be 1000. It follows then, that the maximum frequency of the counter will be 9999Hz, ie, a maximum of 4 digits in the display.

To increase the maximum frequency of the counter, all we need to do is to shorten the time the switch is closed. Take for example a signal of

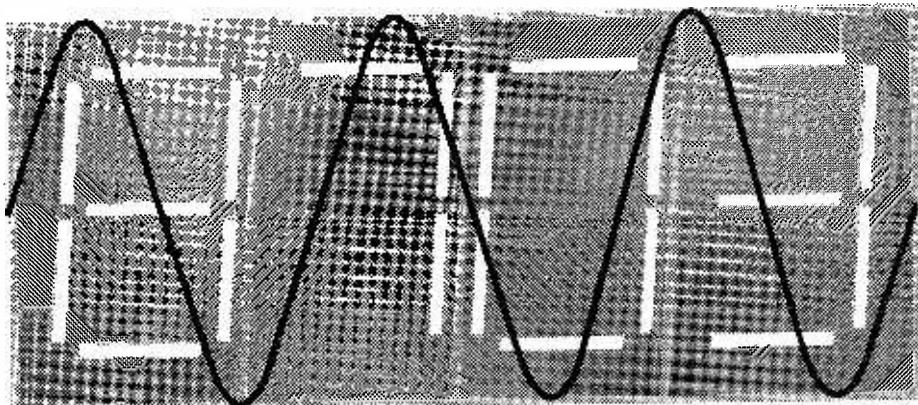

PART 1

1MHz. If we close the switch for 1/1000 of the time, then the display will again show 1000 but this time it will represent kHz. In a practical counter the switch is replaced by an electronic gate, and the time the switch is closed, is referred to as the **gate time**. The accuracy is therefore dependent on the accuracy of the gate time, and in the present design this is accomplished by using a highly stable crystal oscillator.

MODES OF OPERATION

In this design, 3 basic modes of operation have been provided for, these are detailed as follows;
Frequency

With reference to Fig. 2, the signal whose frequency is to be measured is applied to the input stage. The function of which, is to either amplify or attenuate the signal and to convert it into a square wave. The gate time is selected by S4 and applies it to the control logic, assuming the counter has

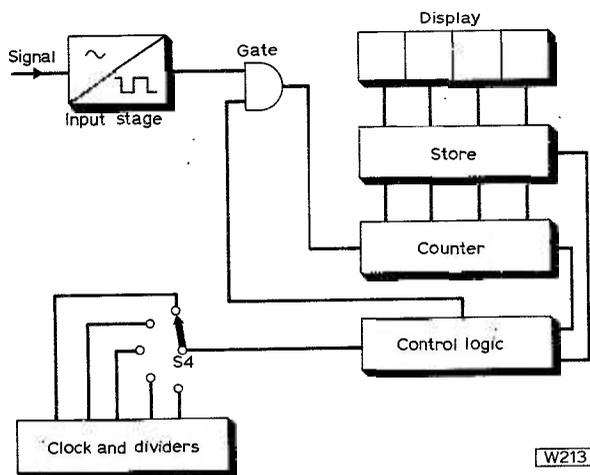


Fig. 2: The incoming signal is converted into a square wave, amplified or attenuated, and applied for one clock pulse.

been reset to zero, the operation is as follows; The gate is enabled for one period of the gate time (clock-period) which allows the square wave to pass through to the counter. At the end of this period, the control logic inhibits the gate, and provides two

Practical Wireless, June 1976

pulses. One for enabling the store thus registering the count, and the second to reset the counter. At the same time it enables the gate to open on the

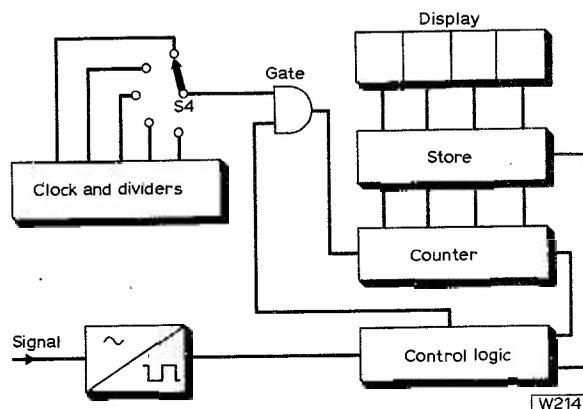


Fig. 3: In order to measure low frequencies, the roles of the clock generator and input stage are reversed.

next clock pulse, the result of which causes the display to update alternate clock pulses.

Period

The main difference between period and frequency measurement is that the roles of clock generator and input stage are reversed, as shown in Fig. 3. Instead of counting the number of input cycles during one clock period, the number of clock pulses


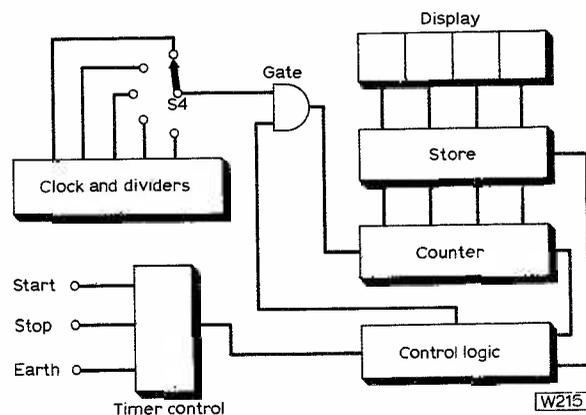


Fig. 4: Block diagram showing the method used for time measurement. In this mode, maximum time indicated is 9999s.

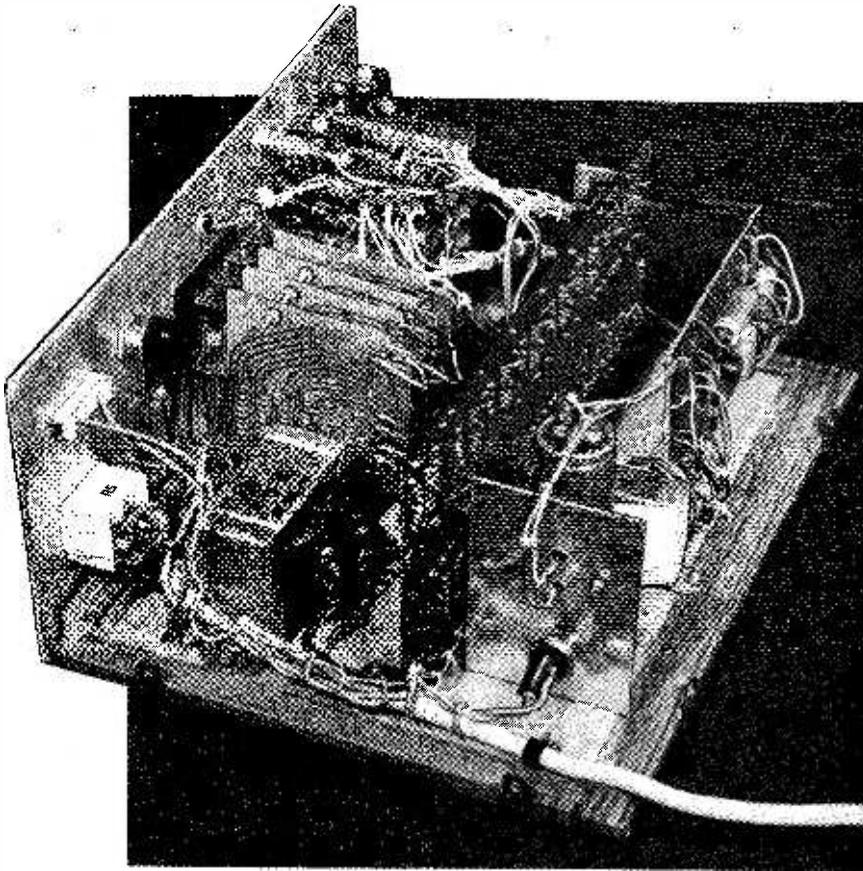

General interior photograph of the unit, showing layout of displays and their associated PCB's, function switches and main board containing all logic and transistor components.

during one input cycle is counted. The selected clock period is applied to the counter via the gate. The input waveform, after being cleaned up, is applied to the control logic. The store and reset pulses are generated in the same way but this time using the input waveform as the initiating signal. The period measurement is useful for low frequencies, such as those below 10Hz. At the same time it is more accurate.

Time

Referring to Fig. 4 it may be seen that time measurement closely resembles that of period. The major difference is that the control signal to the control logic comes from the timer control.

In operation, the time interval selected again passes to the counter and the timer control is connected to the control logic. When the start terminal is connected to 0V, the timer control produces a short pulse which operates the control circuitry to open the gate. The counter will now count in units as selected. For example, if a time interval of 10m is selected, the counter will count in units of 10ms, the display therefore will be in units of 10. A display of 875 therefore represents 8750ms or 8.75 seconds.

When it is desired to end the count the stop terminal is connected to 0V, which again produces a short pulse to close the gate and initiate the store and reset sequence. The display will now hold that count until the counter is reset.

STAGES

A block diagram of the frequency counter is shown in Fig. 5. All of the above modes have been catered for, plus an extra position for testing.

PSU: This section provides the following voltages for the various sections, +5V for the main circuit board, +5V for the display, +12V and -6V for the input stage.

Input stage. This section converts the incoming waveform to operate the TTL circuits correctly.

Timer control. This stage produces a short pulse to operate the control logic when used in the **TIME** mode.

Crystal clock. This stage operates at 100kHz and provides a square wave to operate the dividers.

Dividers. Five stages divide the standard frequency down to the times shown.

Control logic. This performs the following functions; (1) To reset the counter to zero, (2) To store the count reached, (3) To open the gate for the time selected.

Counter/store/decoder/display. These units together perform as a 4 stage counter, to count and display the frequency being measured.

Switching network. The switches incorporated in this section perform the three modes of operation as detailed above.

Referring to the power supply circuit diagram, Fig. 6. T1 provides two windings of 6.3V at 1.8A. The first winding being half wave rectified with CI

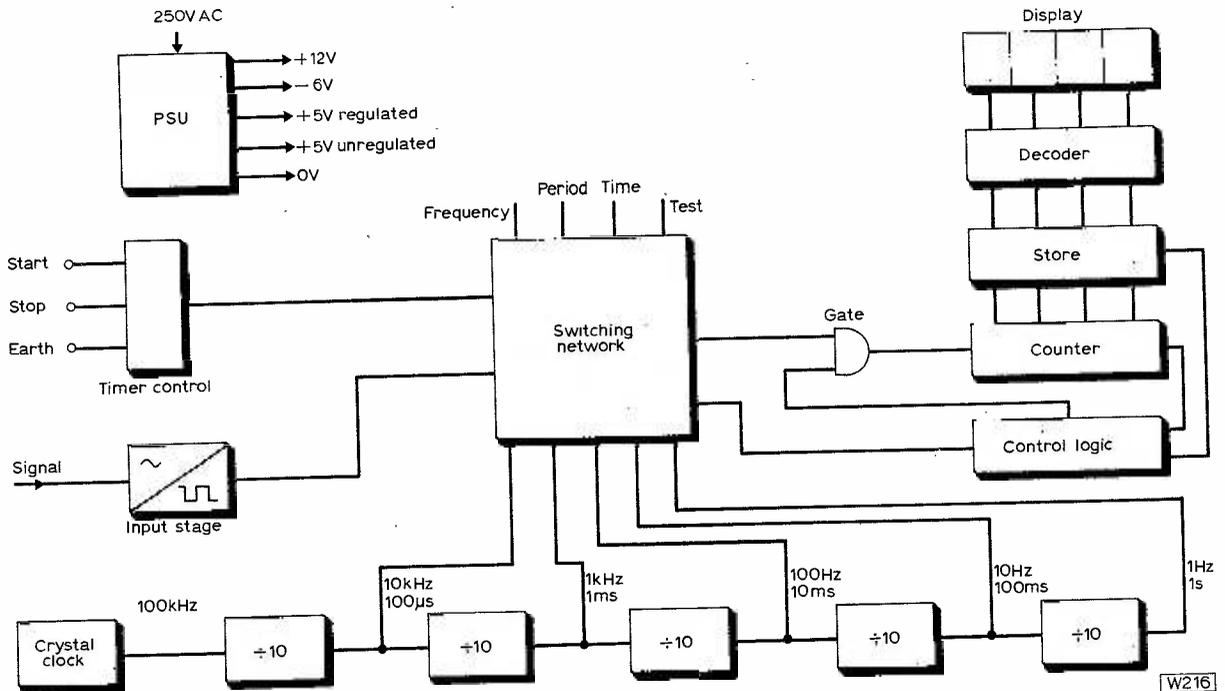


Fig. 5: Diagram showing the complete unit in block form. The crystal clock has a frequency of 100kHz, which is subdivided down to 1Hz by means of five 7490 IC's.


providing a small amount of smoothing. This is then used to power the displays. The second winding is bridge rectified by D2-D5, and smoothed by C2. A 5V regulator is used to provide the required voltage for the remaining circuit. A small amount of smoothing is provided by C3, and RF noise being decoupled by C4. The second transformer T2, supplies 18V to the bridge rectifier Br1, while the two zener diodes provide +12V and -6V for the input stage.

It will be noticed that when all the segments of the displays are on, slight dimming occurs. This is due to the rather simple nature of the supply, although in practice this is quite acceptable, since

when operating with their correct voltage, the displays can be quite dazzling.

INPUT STAGE

IC1 Fig. 7 together with its associate components form the input stage of the circuit. The 710 is a comparator and has two inputs, inverting and non-inverting, pins 4 and 3 respectively. In use if the non-inverting input goes more than 5mV positive than the inverting input, the output goes high. Conversely, if the inverting input goes more positive than the non-inverting input, then the output goes low. R5, 6 and 7 provide positive feedback to the non-inverting input, which causes the device to

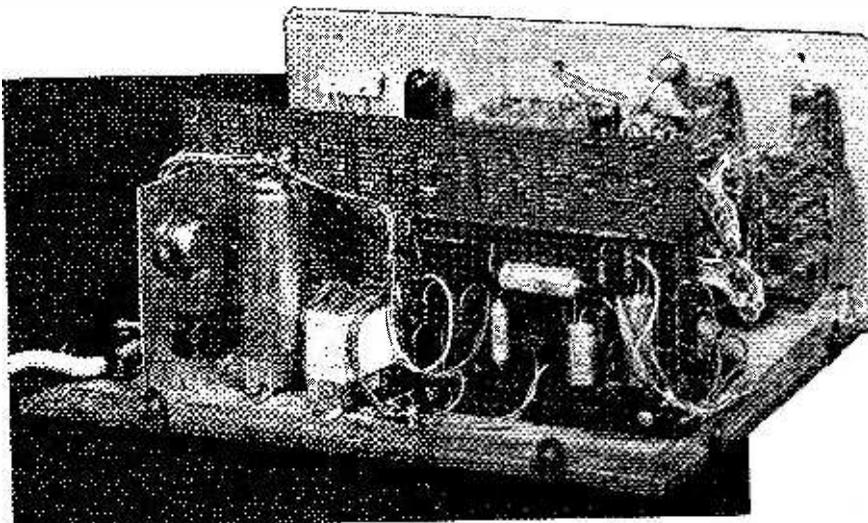

Rear view photograph giving details of the power supply board, regulator and fuse bracket, and smoothing capacitor C2.

★ components list

Resistors		ICs		Diodes	
R1 180Ω	R11 2.2kΩ	IC3 7490	D7 BZY88 6V/	D8 1N914	D9 1N914
R2 120Ω	R12 1kΩ	IC4 7490	400mA zener	D10 1N914	MVR1 5V 1.2A volt-
R3 1kΩ	R13 10kΩ	IC5 7490			age regulator
R4 10kΩ	R14 1kΩ	IC6 7490			Doram type
R5 10kΩ	R15 10kΩ	IC7 7490			305-614
R6 1kΩ	R16 1kΩ	IC8 7490			Br1 Mains recti-
R7 10Ω	R17 10kΩ	IC9 7475			fier, encaps-
R8 1.8kΩ	R18 1kΩ	IC10 7400			ulated type,
R9 220kΩ	R19 10kΩ	IC11 7490			1A rating.
R10 5.6kΩ	R20 1kΩ	IC12 7490			
All resistors 1/2W, 10% except R1 which is 1W	R21 120Ω	IC13 7490			
		IC14 7490			
		IC15 7475			
		IC16 7475			
		IC17 7475			

Capacitors		Miscellaneous	
C1 100μF 10V	C11 1nF silver mica	T1 0-6 2V, 0-6 3V 1.8A mains transformer (196-189)	T2 0-12V, 0-12V miniature mains transformer (196-302)
C2 2000μF 10V	C12 10nF polyester	S1 SPST rocker switch	S2 SPST rocker switch
C3 100μF 10V	C13 200pF silver mica	S3 and S4 four-pole change-over switches, push type in banks of four (338-635)	S5 DPDT rocker switch
C4 10nF polyester	C14 2nF polyester	Eight square opaque buttons for push switches (339-456)	Two 4 switch mounting frames with latching bar for push switches (339-254)
C5 100μF 10V	C15 10nF polyester	SK1 surface mounted, cow, socket	SK2, SK4, 4mm chassis sockets, black, red, and green
C6 100μF 10V	C16 22pF silver mica	Four 7-segment filament type tubes (530-852)	Four PCBs for filament tubes (133-906)
C7 10nF 250V DC	C17 22pF silver mica	X1 100kHz crystal socket for crystal	Piece of Veroboard 95 x 23mm, 0.1in pitch
C8 10nF polyester	C18 22pF silver mica	Place of Veroboard for power supply 95 x 23mm, 0.1in pitch	Aluminum front panel 255 x 116mm
C9 10nF polyester	C19 22pF silver mica	Aluminum regulator/fuse bracket 55 x 90mm	Wood for case, screws, fasten, rubber feet, coloured wire, Fuse holder
C10 4μF 6.3V			(Numbers in brackets indicate Doram type numbers)

Semiconductors	
T1 2N2304	IC18 7475
T2 2N2304	IC19 7447
T3 BSX20	IC20 7447
T4 BSX20	IC21 7447
T5 BSX20	IC22 7447
T6 BSX20	D1 1N4001
IC1 710	D2-D5 1N4001
IC2 74121	D6 BZY88 12V/400mA zener

operate as a schmitt trigger, and is used to shape the signal into a square wave. Input protection to the device is provided by the two diodes D8/D9, which conduct at about 0.7V thus limiting voltage excursions to the IC.

The maximum voltage which may be applied to the instrument, is mainly dependent on the dissipation of R3. In the present design this works out to approximately 14V. If the power rating of the resistor is increased, to say, 2W then the input voltage may then

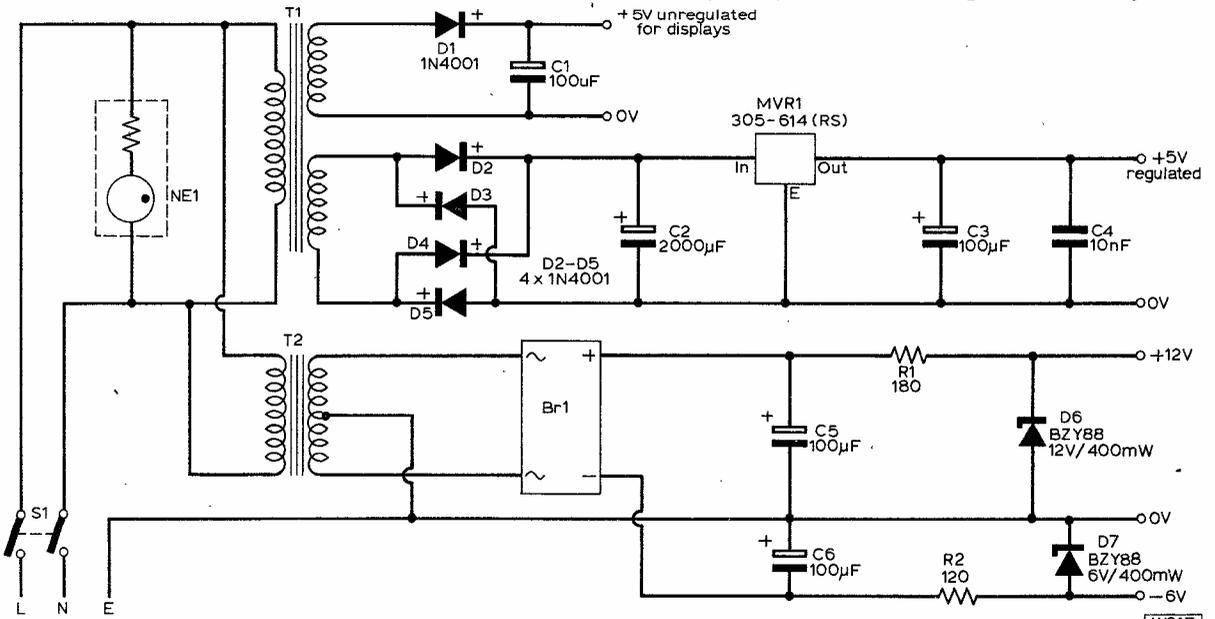


Fig. 6: Although the above power supply is of a simple form, it has to supply four separate voltages. These are +5V regulated, +5V unregulated +12V and -6V.

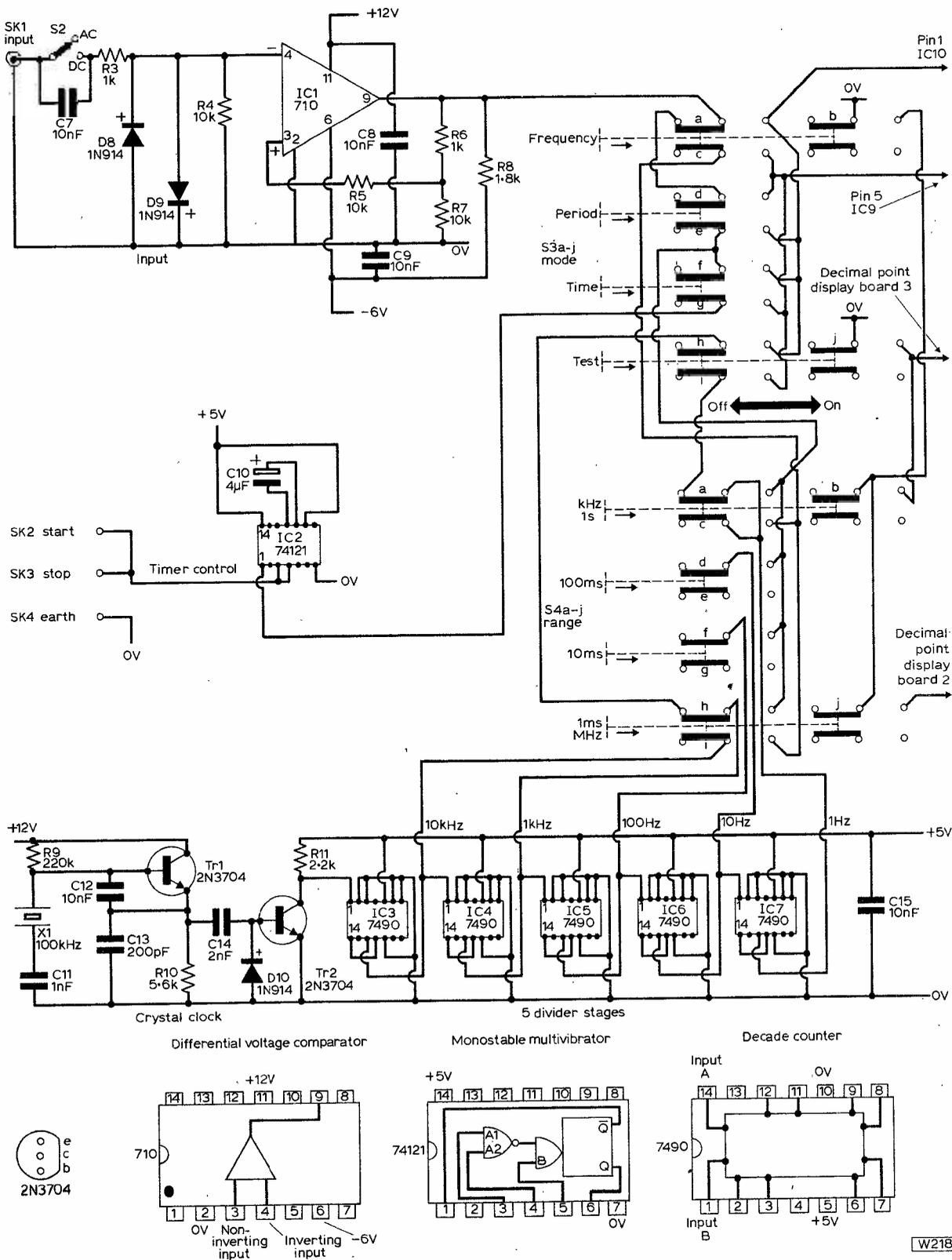


Fig. 7: Part of the complete circuit diagram showing details of the following stages:—Input stage, timer control, crystal clock, divider stages and switching network. continued on page 156

SOUND DESIGN

A PRACTICAL ELECTRONICS PUBLICATION

THE MINISONIC MK2 SOUND SYNTHESISER

An up-dated version of the published Mk 1, the Mk 2 has an integral keyboard, two 250 mW monitoring channels and loudspeakers, and facilities for amplitude, frequency and harmonic modulation.



Available
Now
£1.20
POST PAID

(Please allow at least 2 weeks for delivery)

If you do not wish to mutilate your copy of the magazine, please send your order on a separate sheet.

A SPECIAL
SELECTION
OF MUSICAL
PROJECTS
FROM PE

THE JOANNA ELECTRONIC PIANO

has realistic piano effect with touch-sensitive keyboard and additional choice of harpsichord or honky-tonk voicing.

THE ORION STEREO AMPLIFIER

A hi-fi amplifier with output of over 20+20 watts. Compact and complete in one unit, it measures only 14" x 6" x 2".

PLUS

Some great sound effects units for guitars, keyboard instruments and general recording.

To: Practical Electronics
IPC Magazines Ltd., Receiving Cashiers
Dept., King's Reach Tower,
Stamford Street, London SE1 9LS

Please send me.....copy(ies)
of "Sound Design". I enclose a Postal
Order/Cheque for £1.20 (post paid) or
(state amount for more than one copy)

(£2.35 post paid for 2 copies).

PLEASE WRITE IN BLOCK LETTERS

Name

Address

Post code

Remittances with overseas orders must be sufficient to cover despatch by sea or air mail as required.

Company registered in England. Regd. No 53626. A subsidiary of Reed International Limited.

PRACTICAL WIRELESS FAULT-FINDING GUIDE


continued from April 1976

In the first part of this Guide Les Lawry-Johns concentrated on test equipment and methods of checking transistors and components. This concluding article deals with the technique of logical fault-finding in a typical piece of equipment, a Music Centre, and on getting the maximum amount of information from observed fault symptoms.

In the first part we looked at the bare essentials as far as tools and service aids were concerned. We also looked at the basic methods of testing diodes and transistors and briefly touched upon RF and IF alignment, testing capacitors and resistors with a multimeter etc. Once it becomes known that you are a servicing man you will be expected to become a convenience for all and sundry, to perform miracles at the drop of a hat, repairing everything from hair dryers to colour TV's. Practically all these jobs will be a labour of love and you will gain little, except an ever-growing circle of "friends" that you could well do without!

You will have to develop a defence mechanism which will enable you to escape without giving offence. To be able to give an apologetic smile and say "I'd love to do it, old chap, but it's not my line. You should see old so-and-so, he's an absolute wizard with these things! I wish I was half as clever as he is but I'd probably make a mess of it. Sorry". If this is not the right line, try, "Oh yes, it's well worth spending a fiver on it, provided I can get the spares from the maker but they are very pricey you know". At the mention of a fair amount of money, the golden object becomes as tinkling brass and is not worth the trouble.

In fact this is not an excuse as spares are very expensive. Recently a plastic spool carrier for a well known tape recorder was ordered thinking it would be no more than a £1 or so. When it arrived it was £6.25 including postage and COD. We paid but we doubt if the customer is going to be pleased! In any case you will have to make up your mind just what you are going to tackle and what you are not. Make these dividing lines and stick to them.

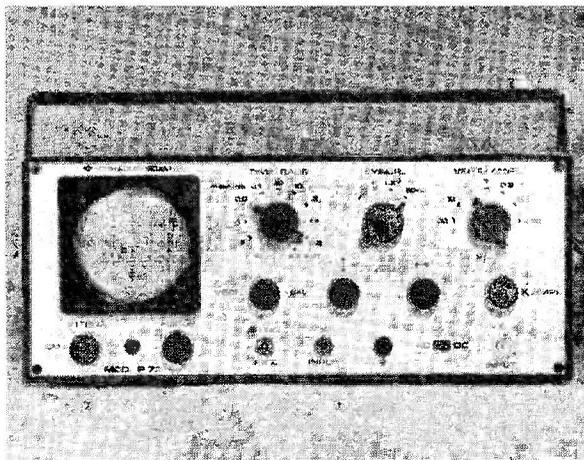

The Chinaglia Belluno P73 single trace oscilloscope has an input impedance of $1M\Omega$ and the input capacity is $45pF$. The Y amplifier response is 3dB down at 8MHz.

What's all this got to do with fault finding? Precious little but there are other matters to consider and it is as well to ponder on these as it is very difficult to earn a living at servicing alone. The one that can make a fortune at it will have to be a hard man indeed, and I don't know of him!

General servicing, such as we have in mind, will mainly concern radios and TV receivers, but the latter are adequately covered by our sister magazine *Television* and so we must concern ourselves here with the radio side, with reference to tape recorders, amplifiers and the like. Recent issues of PW have given a general idea of the methods employed in servicing car radios, unit audios and valved equipment etc. So here we are concerned with fault tracing, diagnosis and handling.

DISMANTLING

Whilst one glance is all that is required in some cases, to see how a particular set is to be dismantled, in others no amount of inspection seems to reveal how the thing comes apart. If the maker's service information is to hand this may explain all, or it may not. The best thing to do in such cases is to remove what can be removed and hope that this leads on to the next step. For example, if it is a battery operated transistor radio, the cover of the battery compartment, as well as concealing the battery, will often conceal the main fixing screw, the remaining fixings being tongue-and-groove pressings. Others may require the dial glass to be removed before the main frame screws are revealed. Quite a few require the carrying strap to be removed by a


FAULT-FINDING GUIDE

downward pressure against a spring which then reveals the side fixing screws.

Having overcome this first hazard it is often necessary to remove the panel from the main frame. Care is required here as some of the screws may be employed in securing the dial drive to the panel and these **must not** be loosened. Reassembling a dial drive can be one of the most frustrating and time-wasting exercises it is possible to imagine so it is well worthwhile assessing the exact purpose of each visible screw. In many cases the relevant screws are marked with a spot of coloured paint to identify them and these are the ones which should be removed first.

FAULT TRACING

Having gained access one can then get down to the main object of the exercise which is to find out what is wrong and ascertain what is likely to be needed to put it right. We say likely because it is often well-nigh impossible to do this without actually doing the job. This is why it is not feasible to supply an accurate estimate of cost and why, if one is pushed to supply one, the job should be turned down as gracefully as possible. What is more reasonable is a rough estimate combined with a goodly amount of mutual goodwill and trust.

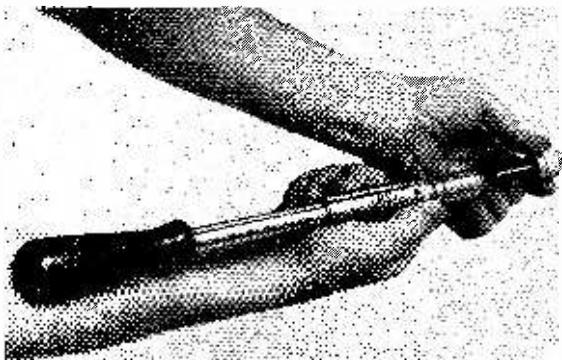

The Paramo loose drill chuck can be quickly fitted to almost any ratchet screwdriver and will take drills up to 6mm for smaller ratchets and 8mm for larger ratchets.

A fair amount of battery operated equipment fails to function purely as a result of poor contact in the battery compartment. This is often the result of batteries being left in too long, the resultant weeping of electrolyte corroding any metal which may be in the vicinity. If the battery box is a separate item, it is best to replace it, clear up any spillage from the receiver, with bicarbonate of soda, fit new cells or batteries and make sure the thing works. If there is no battery box, only a compartment, the job may be more complicated even after the spillage has been neutralised and cleaned up. Some improvisation may be necessary to replace corroded springs and this is why an old torch is never thrown away without removing the springs. Even the springs from ball-point pens have their uses when the pen is finished.

Even though there is no sign of trouble, it pays to check that all is well in the battery compartment before moving on. We have bitter memories of a Philips receiver which

used two 9V batteries. One battery read 8V and the other nothing. There was a good reason for this, since there was a dead short across it! Tracing the leads back, we found they went to the on-off switch and were shorted by the switch. It took a little time to realise that this was quite correct and that the black leads were on the wrong batteries. They had been originally taped to prevent this confusion but the tape had been removed at some time and the owner had finally made the fatal wrong connection and concluded that the set was at fault. The possibility of this happening should have been anticipated by the designer and the batteries should not have been side by side, but there it is, the set was quite old and had functioned for years before this happened.

If a short or partial short is found across the batteries the normal cause is defective output transistors or a shorted electrolytic capacitor. A fair indication can be obtained by switching the meter to the 100mA range, lifting off one of the battery connections and connecting this to one meter lead, and the other to the battery. The actual connection of course depends upon which lead is lifted. If negative, the positive probe of the meter goes to the lead, the negative to the battery. With the volume control turned down a reading of not more than 20mA can be regarded as reasonable, depending upon the receiver, the average being quite a bit less than 20mA but usually over 10mA. If the meter reads over this either the sound will be deafening where the volume was left turned up or there is indeed a short of some kind.

THE 'SHORT'!


Now let's pause here and consider the term "short". It implies that the circuit is of much lower resistance than intended and that it cannot operate correctly. This is the opposite to "open" circuit, which is the other basic fault usually of extremely high resistance. Putting it in the simplest possible terms we can say that there are only two basic faults which can happen to an electrical circuit, either an "open" circuit where nothing happens or a "short" where too much happens! The complication arises due to the degree of the condition i.e. a partial short which is a leak, or a partial open circuit which is a higher resistance than intended. Most appliances consist of not just one circuit but of a great many, so "circuitry" is the better term. The art is to locate the faulty circuit in the shortest time, recognising the nature of the fault and knowing what is needed to put it right.

The first step is to find out what does work as opposed to what doesn't. Let us consider the case of a mains operated Music Centre, consisting of a cassette recorder-player, a record player with auto changer and radio facilities with stereo VHF plus long and medium wave AM. We will assume this has been received for servicing, without loudspeakers, and with the minimum of information regarding the nature of the fault(s). Probably just a label marked, unhelpfully, "does not work"! This shouldn't be allowed to happen in the first place and more information should have been supplied, but this is an exercise, not an actual case.

A preliminary check shows that the appliance is marked at the rear with the mains input, if you are lucky, complete with lead and not just an awkward input socket with no lead! The loudspeaker terminals or sockets will be marked

FAULT-FINDING GUIDE

C	1	TC1	4	5	6	7	8	TC2	11	10	13	12	15	16
R			1	2				3	6	7	8	9		10
L	1	2	3	4					5	6			7	8

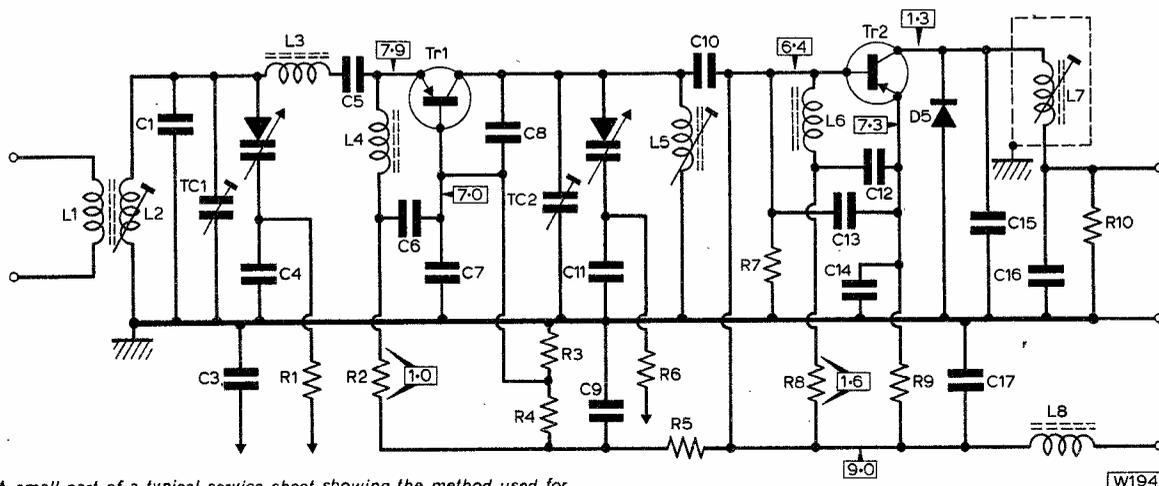

A small part of a typical service sheet showing the method used for rapidly locating a component on the circuit diagram.

with the matching impedance, probably 8Ω . Possibly 4Ω but use 8Ω if in doubt: better to underrun than risk losing the output transistors. Connect suitable speakers and if the mains input lead has a fused plug, check on this first before taking any other action. Remove the fuse and check its rating and whether it is intact. It will probably be intact but it could be too high a rating. Reduce to 3A or less. If, in fact, it has blown, check the receiver end and if there is a filter capacitor across the on-off switch suspect this and use a suitable replacement rated at least 240V AC or 1kV DC.

The method of gaining access will depend upon the unit and it must be admitted that there are a few which appear to have been designed with absolutely no regard for service at all! If there is a dust cover, carefully stow this in a safe place, ensure the record deck is locked in the transit position and the PU arm clipped. Turn the unit up on one end and make sure it cannot topple over. If there is a bottom cover, note how many screws secure it. If there are a large number in various places it probably holds some of the units and is probably not meant to be removed for normal service. If it is of light construction and is only secured around the edges it can probably be removed for inspection. If the bottom cover is not meant to be removed, it will probably have either a couple of holes to provide access to the retaining clips of the auto-changer or some screws which reach through and secure the top cover. If in doubt, the maker's service information should be consulted.

Having ensured that the speakers are connected and the mains input is intact, plug in and switch on. The mains indicator light may come on but if it does not, switch on the auto-changer to see if the turntable rotates. If nothing happens it can be assumed the set fuse in the mains

supply, somewhere around the mains transformer, has failed. The rating of this will be around 300mA surge limiting, the ones with a little spring inside. There are times when these can fail simply because they are fed up with life and a replacement will restore normal operation but a little caution is required here. First look at the fuse to see how it has failed. If it has shattered or is blackened there is no point in putting another one in, and on no account put a fuse in which has a much higher rating. The cause must be traced and rectified.

FUSES


We all get caught out with fuses sooner or later as it is difficult to carry all ratings and types at all times. A little common sense can be used however and if the original rating was say 315mA fit one of between 250mA and 500mA without too much fuss, but these limits should not be exceeded. If the blown fuse is blackened, there is probably a direct short across the supply or there is a short across the secondary of the transformer, most likely a defective bridge rectifier. The former should direct attention to any mains filter capacitor included after the fuse, rather than across the on/off switch and also to the gram motor, the winding of which may appear blackened. Not very often but it does happen. The latter fault, a bridge rectifier breakdown is quite common. The bridge may be formed by four separate diodes or one block with four lead outs. If it is (they are) defective there is usually some visual sign, a block may be bulged or individual diodes blackened. If the fault is further in, the supply fuse would not normally be the one to fail as there is a fuse included in the lower voltage supply line to the amplifiers and the cassette

FAULT-FINDING GUIDE

player etc. This fuse will usually be rated at some 2A and will fail when a short or other overload occurs in the associated circuitry. There is little doubt which fuse is which as they are marked on the panel or at least on the fuse and their situations leave little doubt, the smaller mains fuse being near the mains transformer or on/off switch, the larger rating fuse being on or near the rectifier or main electrolytic smoothing capacitor.

Now there is always the possibility that some bright spark has been there before you and has fitted a heavy fuse in the low voltage (LV) side, say 5A, and that the mains fuse has failed because of this and that the fault will, after all, be found on the amplifier panel. If this is indeed what has happened, leave out both fuses and check, both visually and with a meter, to see if the fault can be spotted or isolated. We say spotted as it is quite common to see some evidence of overheating usually in the small resistors associated with the output transistors, which immediately calls attention to the transistors, or slight discolouration around the audio chips if ICs are used. Also bear in mind the fact that dial lamps are often fed from the LV line or from the transformer secondary and that the lamps themselves can short or the holders into which they are fitted can be defective. If in doubt disconnect the supply lead(s) and check each separately. If no shorts are found, fit the correct fuses and switch on. It is possible that both fuses will hold and the set will operate for some time, say on radio. If this is so, switch over to the cassette player and see what happens. It is possible, again, that the LV fuse will now fail. If it does you then know where the enemy is hiding!

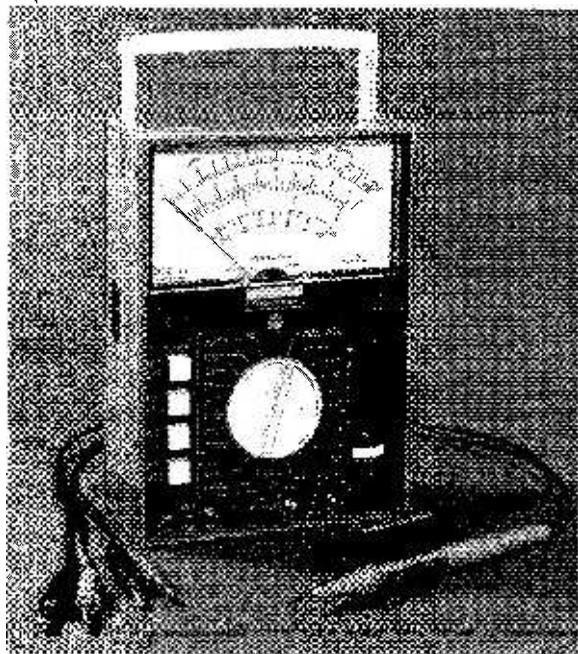If the fuses hold, it means a long soak test and possibly



The Heathkit Type 670 in-circuit tester is capable of measuring the current in a conductor on a PCB while the circuit is in operation.

a request to inspect the loudspeakers, one of which may have defective wiring. This latter check is not likely to be fruitful as a shorted speaker outlet would normally cause damage to the output transistors or chip and recovery is most unlikely, but it can happen. If the LV fuse blows on switch-on, you probably haven't conducted your investigation in the true traditions of the service so start again, isolating and testing each take off point, possibly cutting through a track or two to isolate a particular line, joining up with a lead soldered across the gap, not, repeat not, just a blob of solder which may hold for a moment and then crack. When faulty section has been located you may well kick yourself because the visible evidence was there all the time and missed it. If this is not so you can congratulate yourself for tracing it logically, even if it was only a whisker of wire across two tracks at some hidden point.

Now it is quite likely that the fuses may hold but some overheating may be taking place and a resistor or perhaps a heat sink may feel quite hot to touch. Whilst this may be due to a faulty transistor or a leaky capacitor, it is possibly due to a preset control being maladjusted, causing the output circuit to draw too much current. If the circuit is available the voltages can be checked to see if they conform or can be made to conform, otherwise the voltages on the normally working channel can be compared with the defective channel and the right conclusions drawn.

OUTPUT TRANSISTORS

Output transistors often have a smaller transistor wired across their bases with a preset control provided from collector to base, to set the conduction of this smaller transistor. The more it conducts the closer are the potentials of the bases of the output transistors and the less they conduct, and vice versa, with increased conduction producing more heat. If this causes some head shaking in some quarters because it seems hideously wrong we would point out that the reader should do his own homework, we are only concerned here with the practical results not the theory! We could say that if the small transistor were replaced by a simple resistor, the value of which determine the conduction of the output pair, the lower the resistance the less current is drawn, but such a device allows no compensation such as is provided by a transistor, properly set up.

In stubborn cases, the freezer solution aerosol and the hair dryer mentioned in the first part of this saga can be brought to bear and the results obtained by these assessed, to pin-point a certain component or small area which enables one to draw a conclusion, hopefully the right one, and the correct replacements made.


HUM

One of the most common complaints is not that the equipment does not work at all but that "it hums". The first question must be, assuming this is a stereo outfit, "which side hums, or is it both channels"? If both, the problem is a little easier and is likely to be due to a defective rectifier, probably of the bridge type, which is leaking but not enough to blow a fuse, or a faulty electrolytic capacitor where one of the end contacts is not properly made to the lead-out tab. The electrolytic could be dried up and this is what we would have gone for, once upon a

FAULT-FINDING GUIDE

time. Times change though and so do the habits of certain components. If the rectifier is not running warm and the electrolytic is not at fault it is likely that it was not the right assessment in the first place and that one channel is in fact inoperative, drawing too much current and thus impairing the smoothing. If this is so there is probably output trouble, so back to the previous paragraph!

However, hum is not all in the power supply and output transistors overheating. It can be due to poor earthing, dry joints, defective controls but less often to resistors which have gone "high". Once more, ask the questions. Is it one side only or both, does it occur on radio or gram or both, what effect does the volume control have? When those questions are answered leap into action and head straight to the source of the trouble!

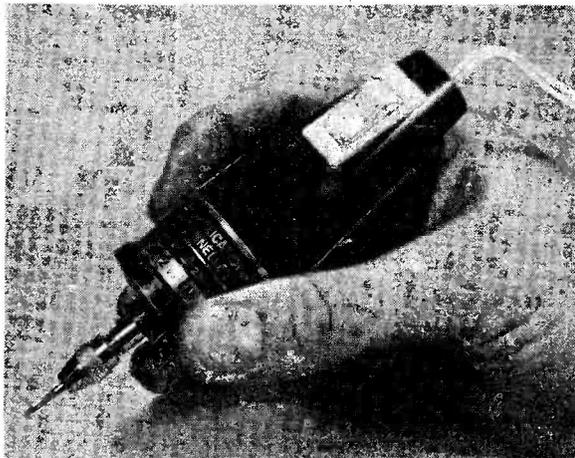

Precision Petite Ltd. produce this very useful 12V DC electric drill. A stand is also available and a kit of tools.


The radio doesn't hum but the gram does, the volume control reducing the hum. Start from the pick-up head, checking the tags first and the way the wires are secured in the tags. Often they are not soldered, merely pressed with the tag making better contact with the plastic insulation than with the actual wire. Correct this and follow through to the underside of the deck where a similar system may be employed, checking the lead-outs and terminals (or phono plugs if used) and the earthing of inner tags or outer screening, as appropriate. Follow on to the input to the amplifier and note that many units use a preamplifier stage for gram input which is not used on radio. The hum could well be occurring in such a pre-amplifier stage especially if this is a separate unit raised from the main board. These are the simple but essential lines one follows to locate hum, there is nothing complicated about it but some patience is often necessary in order to pin it down.

DISTORTION

We have mentioned this problem in several articles and do not wish to go on unnecessarily. There are all types of distortion and one's ears become trained to detect the differences between a low supply voltage (the battery's flat!), cross-over distortion where the output stage is

not being allowed to work properly, unbalance where one transistor is working and the other cannot or will not, loudspeaker rubbing where the speech coil is fouling the magnet, the strangled sound of an output valve running into grid current or the clipped noise of a high value resistor stressing the sibilants.

Sounds are very difficult to describe in words and if the ear is not educated enough to enable a short cut to be made, routine tests will have to be made, starting from the supply and working through, checking voltages and, if necessary, the current drawn, plus cold resistance tests etc. to ascertain where the readings depart from those expected. If it takes a long time, don't worry, you'll recognise that sound again and it won't take nearly so long next time.

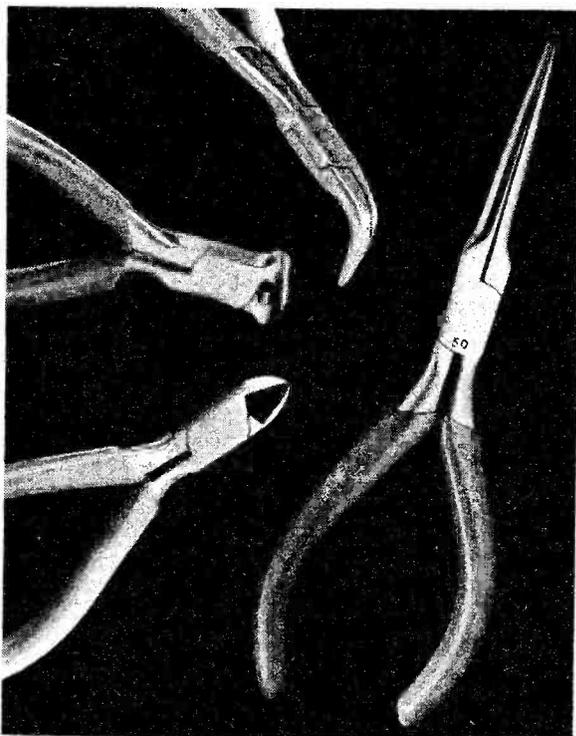

West Hyde now offer a new range of quality tools including these long-nosed pliers, curved needle-nosed pliers, side and face cutters. The long-nosed pliers have an internal spring to bias them in a normally-open position.

TAKING VOLTAGE READINGS

It is one thing to take a number of readings, it is another to review them in order to reach the right conclusion. In order to do this one needs to know, within limits, what to expect before any readings are taken. This can be gathered from service information or from previous knowledge of this or a similar circuit. As far as individual stages are concerned, divorced from the preceding and succeeding stages by capacitors or transformers, one or two readings immediately establish the conditions and enable a diagnosis to be made. For example, if a transistor is inoperative, with no emitter reading, although the base and collector

FAULT-FINDING GUIDE

voltages are about right, it does not require much thought to reach the conclusion that the transistor is likely to have an open-circuit base-emitter junction. Note that we said "likely". Now, should the reading show the emitter with a higher voltage than the base, still assuming a straightforward amplifier layout where the collector is relatively high, the emitter and base low, with the base sufficiently above the emitter to allow it to conduct, one can conclude that the transistor cannot operate and one has to find where the emitter voltage is coming from. If there is only a straightforward resistor from emitter to supply or return, it can be concluded that there is a collector to emitter leak in the transistor, which will normally show up on an ohms test.

For example, if the emitter resistor is say 470Ω , this is the minimum reading to be expected and, if there is doubt, the resistor can be lifted from the circuit at one end to ascertain the exact reading, which should be high, except in the case of one or two specialist types. Where transistors are DC coupled, as in most audio designs, voltage readings must be looked upon as a very rough guide and not as an instant fault locator. The same can be said for AGC systems where the controlled stages are dependent upon a controlling voltage derived from a source which is itself controlled. If that sounds decidedly awkward, it is.

The audio stages are less awkward since the majority of troubles are usually in the output stage and can be identified by disconnecting the suspect transistor and cold testing it (or them) and associated resistors and then working back from this point.

GENERAL

These are the general lines to follow. Note what is working and what isn't, disconnect what can be disconnected in order to narrow the field. Accept the fact that you are going to be misled by "red herrings" and write this down to experience. The man that hasn't made a mistake hasn't made anything but you don't have to make the same mistake twice. If a thing looks horribly complicated this is because one is not used to looking at it, but divided into sections there is little to fear although it is still necessary to understand the basic operating principles.

Once the fault has been localised, the rest can be ignored. Concentrate on that section, understand what it is supposed to do before trying to put it right. Get it working properly and then connect up the rest ensuring that this doesn't upset the operation. Start from the supply, get that right or see that it is right, check the output stage as this is where most of the trouble abides and then isolate sections to see which parts are functioning and which are not.

Use the tools you have to the best advantage, including the ears, eyes, nose and sense of touch. Your multi-meter, signal injector, coolants and "heatants", this unlikely last term to include your soldering iron and the hair dryer we spoke of earlier, and above all your ability to think electrically. This is half the job. P.W.

Photographs were kindly supplied by the following companies to whom all queries on the instruments illustrated should be addressed.

Heath (Gloucester) Ltd., Gloucester GL2 6EE.

Precision Petite Ltd., 119A High Street, Teddington, TW11 8HG

Chinaglia Ltd., 19 Mulberry Walk, London SW3 6DZ

Parramore Ltd., Caledonian Works, Chapelton, Sheffield S30 4WZ

West Hyde Developments Ltd., Ryefield Crescent, Northwood Hills, Northwood, Middx HA6 1NN.

be increased to 28V. However this was not thought too important, since we are generally concerned with low level signals. R8 is added to increase IC1's output current sinking ability. The supply lines are decoupled at RF by the two capacitors C8 and C9.

The input is applied to a standard coaxial socket SK1 by screened lead, and then passes to S2. The purpose of which is to short out the capacitor to allow either AC or DC signals to be measured. It is also used in the DC position when measuring low frequencies, such as those below 25Hz, and also when in the Period mode.

TIMER, CRYSTAL, CLOCK AND DIVIDERS

The monostable IC2 uses the external capacitor C10 to achieve a pulse length of about 10ms to clock FF2 of IC9. The monostable produces this pulse when pins 3 and 4 are connected temporarily to 0V. In the prototype, two sockets are used together with an earth socket to achieve this. In fact only one socket is needed, although two make the connection of external control easier.

Tr1 is connected as a Colpitts oscillator, Fig. 7 in the emitter follower mode while the crystal X1 works in the parallel mode of resonance. C11 provides series blocking, and R9 base bias. Positive feedback is achieved across the potential divider C12 and C13, the centre point being taken to the emitter. Output is developed across R10, and is then fed to the squaring amplifier Tr2, via C14. Diode D10, together with Tr2 provides symmetrical clipping of the signal, the output being developed across R11, and finally coupled to the divider stages.

IC3 to IC7 make up the divider stages and are connected in the square wave output mode. They divide the 100kHz of the oscillator down to the following gate times; 1Hz—1 second; 10Hz—100ms; 100Hz—10ms; 1kHz—1ms; 10kHz—100 μ s.

These outputs are then selected by S4 and passed to S3 where they are passed to either the counter or FF2 as appropriate.

SWITCHING NETWORK

This hardly needs explanation, since the various paths for the signals etc, may easily be followed in Fig. 7. However, a few points to notice are as follows;

Referring to the range switch S4a-j. When the test position is selected by S3 (mode) the 1kHz and 1Hz times are connected through sections h and a, it is therefore important that no range switches are depressed when in this mode. When measuring frequency, only two gate times may be selected, these are 1s (S4c) and 100 μ s (S4i), therefore pressing any other times will not operate the counter.

Referring to both switches, sections b and j. These position the decimal point in the display, eg. when in the TEST and FREQUENCY mode the decimal point will be positioned between the fourth and third digit on the left, thus indicating 1.000kHz.

Part 2 continues in the July issue, and will be covering details of the circuit, Veroboard layout, and case construction.

**SPECIAL
PRODUCT
REPORT**

SINCLAIR

'BLACK WATCH' KIT



THE Sinclair "Black Watch" is a digital wrist watch of unconventional appearance, as may be seen from the illustration. The watch is available ready-built, or in kit-form, the latter version being priced at under £15, including VAT.

The components supplied include a double-sided glass fibre printed circuit board, a flexible self-adhesive printed circuit, an LED digital display, an 18-pin IC, a quartz crystal, a trimmer, all parts for the case, two cells, a flexible insulated copper screen, a plastic strap, varnish, grease and solder. Assembly and operating instructions are also provided.

The case of the watch is moulded in black plastic material, the back fitting on the front section by "click" retaining lugs. A transparent purple window is fixed in an aperture in the front of the case so that the LED display is visible. Three flexible diaphragms are moulded into the case, two in the front and one in the back. The diaphragms have small pieces of metal foil attached and, when the watch is in use, pressure on the diaphragms causes the foil to short together pairs of contacts. The rear diaphragm is used when setting the watch to the correct time and pressure on the two front diaphragms causes the display to work.

HOW DOES IT WORK ?

The heart of the watch is a quartz crystal which oscillates at 32,768kHz divided by the IC to obtain one pulse per second, the pulses being counted into minutes and hours by circuitry in the same IC. A 4-digit LED display is connected to the IC and brought into action by shorting two pairs of contacts, as mentioned earlier. One pair is used to obtain a display of the hours and minutes held by the watch and the other displays the minutes and seconds. Thus, for a time of

12 06 42, the two displays are 12 06 and 06 42. If the contacts are shorted together briefly, the display is illuminated for about half a second, or continuously by keeping the contacts closed.

A further pair of contacts is used when setting the watch to the correct time. The hours can be made to advance at one per second until the correct hour is reached and the minutes can also be advanced similarly, while the seconds are held at "00". The only discrete components in the watch are the quartz crystal, a trimmer to allow a small variation in the frequency of the oscillator and a tantalum bead capacitor, though this is omitted from later kits. The battery consumption is only a few microamps when the display is not in use, but rises considerably when the display is operating. This is the reason why the display cannot be illuminated continuously; battery life would then be very short indeed.

ASSEMBLY

Assembly of the watch is carried out in a number of stages: preparation and assembly of the PCB; fitting of the flexible PCB; fitting of the insulated copper screen; testing and adjustment; final assembly into case.

The first step is to varnish most of the component side of the glass fibre PCB. The varnish is left to dry, about two to four hours. The ceramic trimmer is then soldered into position on the PCB. The tantalum capacitor is next, followed by the quartz crystal, the display and the IC. This stage is completed by fitting the flexible printed circuit, wrapped round the IC. The flap of the flexible printed circuit carries the two battery contacts.


The watch assembly then looks like the illustration. The total time spent so far will probably be about an hour, excluding the drying time of the varnish. The next step is to fit the insulated flexible copper screen, which is wrapped round the assembly and soldered to one pin of the IC.



TESTING AND ADJUSTMENT

Testing of the watch is carried out by setting the trimmer capacitor to mid-range and connecting the batteries by a temporary arrangement. If the two pairs of contacts on top of the IC are shorted together, the display should function. Using a radio time-signal, or the telephone clock, the display time is noted at the same time on consecutive days, to determine if the watch is gaining or losing and appropriate adjustment made to the trimmer.

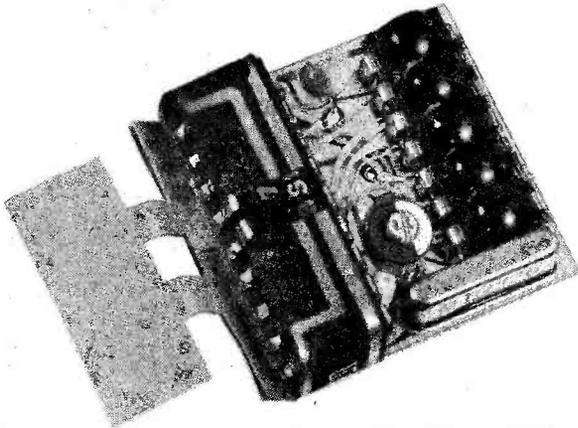Sinclair say that the watch is ultimately capable of an accuracy of about one second per week. When the accuracy is satisfactory, the watch is fitted into the case, the strap is attached, and the watch is ready to wear.



First stage of construction with components mounted on PCB and the flexible printed circuit in position round the IC at left.

For the temporary connection of batteries, Sinclair advise the use of a "Bulldog" clip, but it was very easy to short the batteries accidentally and almost impossible to hold two batteries, a flexible printed circuit and a Bulldog clip in the correct positions, all at the same time! This difficulty was aggravated by a tendency for one digit of the display to light up as soon as the batteries made contact. The instructions said that this might happen and that the remedy was to interrupt the battery supply. Then, of course, the clip, the batteries and the flexible printed circuit tended to part company once more! The problem of accidental short circuits was cured by using insulating tape on one jaw of the clip, but the operation remained very difficult to carry out.

The idea of using two wooden clothes pegs (of the spring type), two drawing pins and a piece of insulated wire solved the problem. This enabled the batteries to be fitted one at a time and made the procedure comparatively easy. The adjustment of the watch took some four days to accomplish, but was not difficult, rather a little tedious through having to wait four days before being able to complete the watch.

FITTING INTO CASE

Trying to fit the watch into the case was where the problems really started. The PCB assembly was too thick for the space available and there were two reasons for this. The impression was that the flexible copper screen had not been part of the original design; the instructions for the fitting of this screen were separate from the main assembly instructions. The two thicknesses of screen obviously reduced the front-to-back clearance between PCB assembly and case. However, the main reason for the difficulty was that the soldered joints were protruding too far from the PCB. The importance of making very small solder joints had not been emphasised sufficiently in the instructions, which merely called for the use of a fine-tipped soldering iron, and "small wire cutters capable of cropping within $\frac{1}{2}$ mm of the PCB".

Sinclair have since stated that an improved IC is now being supplied which is free from any effects due to external static. The insulated copper screen is no longer necessary.

Sinclair Radionics Ltd., St. Ives, Huntingdon, Cambs.
PE17 4BR.

TELEVISION

IN THE JUNE ISSUE

SERVICING THE DECCA 10/30 SERIES CHASSIS

The Decca Bradford chassis was first released in 1970 and is still in production. It is one of the best known hybrid colour chassis and large numbers have been sold and rented. This month we start a detailed survey of the chassis, the faults to be expected, and fault-finding procedures, dealing with both the 10 and 30 versions.

SIMPLE GREY-SCALE GENERATOR

Three 74-series TTL i.c.s. and two transistors are used to generate an eight-step wedge suitable for injection into the video or luminance stages. The circuit can be modified to match either the BBC or the IBA colour bar standards.

THYRISTOR LINE OUTPUT STAGES

All line output stages work on the same basic principle but the thyristor circuit at first glance appears to be something entirely different. Because of the characteristics of thyristors, there is added complexity, though the circuit still performs the same basic operations. We shall examine the principles, the differences between thyristor and transistor circuits, and practical arrangements.

SERVICING TELEVISION RECEIVERS

Les Lawry-Johns describes his experiences with the Pye group's 173 chassis which superseded the 169 in 1973.

VIDEOTAPE COPYING

Vivian Cape reviews various techniques currently available for producing multiple copies of videotaped material.

PLUS ALL THE REGULAR FEATURES

TO
(Name of Newsagent)

Please reserve/deliver the JUNE issue of TELEVISION (40p), on sale May 17th, and continue every month until further notice.

NAME

ADDRESS



4 1/2" x 3 1/2" METER. 30µA, 50µA or 100µA, £3-85. P. & P. 16p.

TAPE RECORDER LEVEL METER



500µA, 80p P. & P. 10p.

CARDIOID DYNAMIC MICROPHONE



Model UD-130. Frequency response 50-15,000c/s. Impedance Dual 50K and 600 ohms, £7-40. P. & P. 26p.

42 x 42mm METERS 1mA, 10mA, 100mA, 500mA. £2-76, 11p P. & P.

60 x 45mm METERS 50µA, 100µA, 500µA and 1mA VU METER £2-92, 13p P. & P.

EDGEWISE METERS, 90mm x 34mm, 1mA £3-40, 13p P. & P.

MULTI-METER



Model ITI-2 20,000 ohm/volt, £6-90. P.&P. 24p.



3 WATT STEREO AMPLIFIER
1 1/2 W PER CHANNEL
£4-30. P. & P. 13p.

All above prices include V.A.T. LARGE S.A.E. for List No. 12. Special prices for quantity quoted on request.

M. DZIUBAS

158 Bradshawgate · Bolton · Lancs. BL2 1BA

G SPRING BUSINESS BARGAIN SALE RD

- F.M. Tuners. 8-transistor chassis with Stereo-decoder and L.E.D. indicator £10-90
- Aircraft-band receiver. Just place near any radio Echo-chamber. (Endless tape). Variable delay £24-50
- Field-strength indicators. 1-250 MHz £3-30
- Stereo Amplifiers complete. 3-watt. 8-ohm £2-75
- 10-watt Amplifiers. 12 volt D.C. 3/8/15-ohm £1-50
- Cartridges. Acos GP 104. Ceramic/Diamond £2-50
- Cartridges. Acos GP 101. Crystal/Sapphire/Compatible £0-35
- Speakers. 2 1/2" 8-ohm £2-00
- Speakers. Car Stereo. 8-ohm. 5-watt. In cabinets £2-00
- Dynamic Tape Mikes with remote-control facility £0-00
- Crystal Tape Recorder Mikes £0-00
- Crystal Mike inserts with bracket £2-25
- Indicators. 12-volt L.E.D. in Chrome Bezel £2-50
- "Bargain Bags" 4lbs Caps/Resistors/Transistors/Diodes £2-50
- Controls. Volume/Pre-set (Rotary & Slider) Assorted 100 £1-00
- Transistors. 20 NPN/PNP. All new and marked £1-00
- Transistors. 100 NPN untested. £1-00
- Diodes. 100 Germanium untested £2-50
- Diodes. 100 Silicon untested £0-50
- Diodes. 100 Zener untested £1-00
- "Pack 1" 100 resistors. 100 ceramics. 100 diodes £1-00
- "Pack 2" 100 resistors. 100 ceramics. 100 polystyrene £1-00
- "Pack 3" 100 resistors. 100 S/Mica/Ceramic. 100 Polyester £1-00

ALL ABOVE ITEMS PLUS 12 1/2% VAT

- Fluorescent 12-volt Camping Lights. 21" 13-watt £4-00
- 12" 8-watt £3-90
- "Disco type 3-Channel flashing light units. Built-in mike. No connection needed to amp £17-50
- Multimeters. AC 0-1000V. DC 0-1000V. 0-100 ma. 0-150kohm £3-50
- Multimeters. AC 0-500V. (10 ranges) DC 0-500V. (12 ranges) DC Current 0-25ua to 0-10 amps (10 ranges) Resistance 0-100ohms to 0-15Mohms. (4 ranges) £11-30
- Panel Meters. 0-50ua. 2 1/2" x 1 1/2" £2-50
- Soldering Irons. 15-watt. Pencil Bit. £1-25
- Servisol Switch Cleaner (with Snorkel) £0-50
- Copper-clad Fibre Glass Board. Single-sided. Square foot £1-00
- Double-sided £1-25
- "Fotolak" Light sensitive spray for printed circuit making £0-30
- Developer for same £0-40
- Ferric Chloride for etching £0-40

ALL ABOVE ITEMS PLUS 8% VAT

G. F. MILWARD, 369 Alum Rock Road, Tel. 021-327 2339 Birmingham B8 3DR.

POSTAGE: Below £10 50p Above £10 Free

ENGINEERS

FREE



YOURSELF FOR A BETTER JOB WITH MORE PAY!

Do you want promotion, a better job, higher pay? "New opportunities" shows you how to get them through a low-cost, Home Study Course. There are no books to buy and you can pay as you learn.

This easy to follow GUIDE TO SUCCESS should be read by every ambitious engineer. Send for this helpful 44-page free book NOW! No obligation, nobody will call on you. It could be the best thing you ever did.

CHOOSE A BRAND NEW FUTURE HERE

CUT OUT THIS COUPON
Tick or state subject of interest. Post to address below.

- | | | |
|--|---|---|
| <input type="checkbox"/> ELECTRICAL & ELECTRONICS | <input type="checkbox"/> Radio, Servicing & Repairs | <input type="checkbox"/> Painting & Decorating |
| <input type="checkbox"/> Practical Radio & Electronics (with KIT) | <input type="checkbox"/> Radio Amateur's Exam. | <input type="checkbox"/> MECHANICAL A.M.S.E. (Mech.) |
| <input type="checkbox"/> Electronic Engineering Certificate | <input type="checkbox"/> AUTO & AERO Motor Mechanics | <input type="checkbox"/> General Mech. Eng. |
| <input type="checkbox"/> General Elect. Eng. Certificate | <input type="checkbox"/> C. & G. Motor V. Mechanics | <input type="checkbox"/> Inst. Engineers & Technicians |
| <input type="checkbox"/> C. & G. Elect. Installations | <input type="checkbox"/> General Auto Engineering | <input type="checkbox"/> Maintenance Engineering |
| <input type="checkbox"/> Elect. Install. & Work | <input type="checkbox"/> A.M.I.M.I. | <input type="checkbox"/> Welding |
| <input type="checkbox"/> C. & G. Elect. Technicians | <input type="checkbox"/> Air Registration Board Certs. | <input type="checkbox"/> M.A.A./I.M.I. Dip. |
| <input type="checkbox"/> RADIO & TELECOM. COMMUNICATIONS | <input type="checkbox"/> CONSTRUCTIONAL Heating, Ventilating & Air Conditioning | <input type="checkbox"/> MANAGEMENT & PRODUCTION Computer Programming |
| <input type="checkbox"/> Colour TV Servicing | <input type="checkbox"/> Architectural Draughtsmanship & Design | <input type="checkbox"/> Inst. of Cost & Managements Accts. |
| <input type="checkbox"/> C. & G. Telecoms. Technician's Cert. | <input type="checkbox"/> L.I.O.B. | <input type="checkbox"/> DRAUGHTSMANSHIP & DESIGN |
| <input type="checkbox"/> C. & G. Radio, TV & Electronics Mech. Cert. | <input type="checkbox"/> Carpentry & Joinery | <input type="checkbox"/> General Draughtsmanship |
| <input type="checkbox"/> Radio & TV Engineering Course | <input type="checkbox"/> Plumbing Technology | <input type="checkbox"/> A.M.I.E.D. |
| | <input type="checkbox"/> General Building | <input type="checkbox"/> Electrical Draughtsmanship |



G.C.E.
—58 '0' & 'A' Level Subjects
—over 10,000 Group Passes!

Aldermaston College

'Dept. TPW 18, Reading RG7 4PF.

also at our London Advisory Office, 4 Fore Street Avenue, Moorgate, London EC2Y 5ET. Tel. 628 2721.

NAME (Block Capitals)

ADDRESS

..... Postcode

Other subjects of interest..... Age.....

Accredited by C.A.C.C. Member of A.B.C.C.

HOME OF BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY

PRODUCTION LINES

colin riches

JONELLE CASSETTES

Stores in the John Lewis partnership have introduced their own brand—Jonelle—blank cassette tapes. They come supplied in the usual snap-pack cases, complete with an index card.

The cassettes are made in England using tape supplied by "a large West German manufacturer". The Jonelle C60 (30 minutes per side) costs 39p and the C90 (45 minutes per side) costs 49p. *The John Lewis Partnership (Dept. P.W.) Merchandise Information, Oxford Street, London W1A 1EX. (Telephone 01-637-3434).*



AIWA BREAK ALL THE RULES

If you ask an expert in the HiFi field, what he thinks of music centres i.e. a complete system, less speakers, housed in a single cabinet, he would probably quickly eject you from his presence and swear never to speak to you again. His loathing for this particular form of 'HiFi' was, in the past, justifiable, and could be backed up with test data from both manufacturer and independent reviewer. The fact that true HiFi could not be obtained at a reasonable cost from a system housed in a single cabinet has always been a stumbling block, but Aiwa, have shattered this long-held belief.

With their model, the AF-5080, they have brought together in a single cabinet an AM/FM stereo tuner, a Dolby cassette recorder, a 24W per channel amplifier and record turntable. The tuner section covers LW,


MW and SW on the AM band, while on the FM band, coverage is from 87.5MHz to 108MHz. Sensitivity ranges from $550\mu\text{V/m}$ (LW), through to $2.5\mu\text{V/m}$ on the FM band. The amplifier section has a rated output of 24W RMS per channel, with a THD factor at 1kHz of 0.08%. Power bandwidth is from 20Hz to 20kHz.

To satisfy the ever increasing demand for cassette recorders, Aiwa have had the good sense to incorporate a Dolby recorder into the system, which boasts a frequency response of 30Hz to 17000Hz (fe-Cr). The cassettes are front loaded, with all controls oil damped, to give precise and noiseless operation.

Moving on to the record playing section, the aluminium turntable is belt driven from a synchronous motor, giving W & F and S/N figures of 0.1% and 45dB's respectively. The lightweight tubular S-shaped arm, is fitted with an anti-skate device and magnetic cartridge, Recommended tracking force is 2gms.

Obviously there are many more parameters available than the ones discussed here, but taking into account the stylish cabinet, facilities available and price, a potential buyer would be hard pressed to better this combination, either in music centre form or as separates.

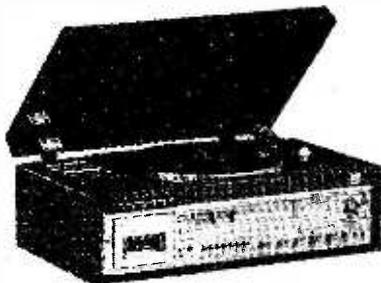Price of the AF-5080 is £288.63 inc. VAT, and it is distributed by *Johnsons of Hendon, (Dept. P.W.) 14 Priestly Way, Eldonwall Trading Estate, London NW2 7TN.*



Aiwa's AF-5080 Music Centre


GOLDRING G.900

In the item on the G.900 Cartridge in the April issue the total mass should have read 5gm and the moving mass 0.32gm. We thank Mr. Sharp of Goldring Limited for bringing these points to our notice.

CAR INTRUSION ALARM KIT

The new Heathkit GD-1157 not only protects your vehicle from tampering and theft, but it protects your entire car—engine, boot and passenger compartment—from would-be thieves by sounding your car's horn.

The alarm unit itself can be mounted almost anywhere and is connected to pushbutton switches on the doors, bonnet and boot. The entire system can be armed or disabled by a convenient underdash switch. Two controls in the alarm unit set entry and exit delay times so you can enter or leave the car without accidentally triggering the alarm. However, with the system armed the alarm sounds instantly whenever the doors, bonnet or boot are opened. The alarm sounds for approximately two minutes, then resets and repeats the two-minute alarm cycle until the reset switch on the GD-1157 is flipped or the cause of the alarm has been removed.

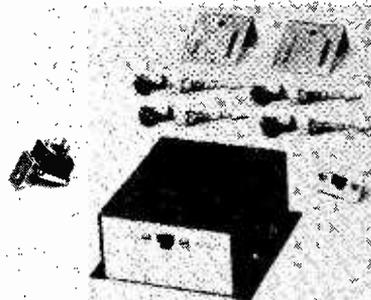


Once the alarm sounds, the underdash arm/disable switch no longer functions and the only way to disable the system is to flip the set/reset switch on the concealed alarm unit.

There is just one simple printed circuit board to wire and the manual gives complete installation instructions. The kit includes 4 pushbutton switches, mounting hardware and cables. And, to simplify installation, your car's existing courtesy light switches can double as switches for the alarm.

Prices: Kit GD-1157 £18.80 (including 8% VAT and delivery within the UK). Full details available upon request from: *Heath (Gloucester) Ltd., (Dept. P.W.) Bristol Road, Gloucester GL2 6EE or The London Heathkit Centre, 233 Tottenham Court Road, London W1P 9AE.*

BI-PAK MODULES

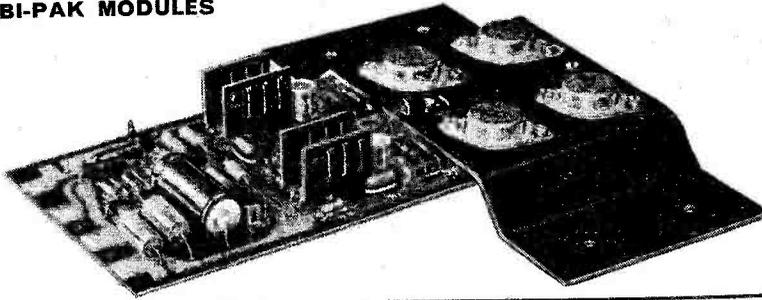

A major addition to their range of Audio Modules is announced by *Bi-Pak Semiconductors, (Dept P.W.) 63 High Street, Ware, Herts.*

The unit, designated AL250, is a power amplifier providing an output of up to 125W RMS into a 4Ω load.

The module has a sensitivity of 450mV and a frequency response extending from 25Hz to 20kHz whilst distortion levels are typically below 0.1%. The use of 4, 115W transistors in the output stage makes the unit extremely rugged while damage resulting from incorrect or short-circuit loads is prevented by a four transistor protection circuit.

The unit is intended for use in many applications such as disco units, sound re-inforcement systems, background music players etc.

Priced at only £15.95 plus V.A.T., the module is supplied with complete instructions and is fully guaranteed.

BARRIE ELECTRONICS

Barrie Electronics inform us that they market the Bi-Kit range of kits with BSR decks in addition to stocking a very large range of components, especially resistors. The firm also supplies Avo meters.

Where possible, Barrie pride themselves on their 'same day dispatch' service and say that they will be pleased to supply readers with their price lists upon receipt of a stamped, addressed envelope. *Barrie Electronics (Dept. P.W.) Ltd., 3 The Minories, London EC3N 1BS.*

DRILL CHUCK

Paramo Tools have introduced a loose drill chuck, mounted on a spiral ratchet bit. This slides into any spiral ratchet screwdriver, either Paramo or their competitors, to replace the standard screwdriver bit.



Quickly fitted, the chuck will take twist bits up to 6mm for the smaller two sizes of spiral ratchet, and up to 8mm for the 131AH. The speed of replacement of the drill chuck enables drilling and screwing operations to be speedily carried out. The high speed attainable with the spiral ratchet action, of course, makes drilling thin materials easy.

The drill chucks are priced at £3.15 plus V.A.T. for all sizes, and are available from your usual Paramo Tool stockist. *F. Parramore & Sons (Dept. P.W.) Ltd., Caledonian Works, Chapeltown, Sheffield S30 4WZ.*

LUX PD-131




Howland-West have pleasure in announcing the Lux PD-131 turntable. It comes without arm, but is fitted with bayonet type mount to take the SME arm. Features include: brushless DC servo-controlled motor (ensures excellent stability of rotational speed and offers high torque): Turntable platter—so designed as to give not only necessary inertia but possible heaviest weight in consideration of motor bearing and resonance/tension of each part of the turntable: Chassis, wooden frame and panel—aluminium die-cast chassis with sufficient strength and weight, 3mm-thick anodised aluminium panel are firmly assembled together with rubber and the wooden frame has a bumper effect which keeps this turntable immune from vibration: Acrylite case—4mm-thick (0.16in) dust cover: Insulator Compliance and control required for prevention of vibration is obtained by combination of spring, rubber and silicon grease: Unique mirror system stroboscope which permits visual identification of AC line frequency by colour in addition to indication of rotation speed by number of pulses blinking black light.

The price of the turntable, without arm, is £195.00, plus VAT, and it will be available through Lux appointed dealers only. *Howland West Ltd. (Dept. P.W.), 3-5 Eden Grove, London N7 8EQ.*



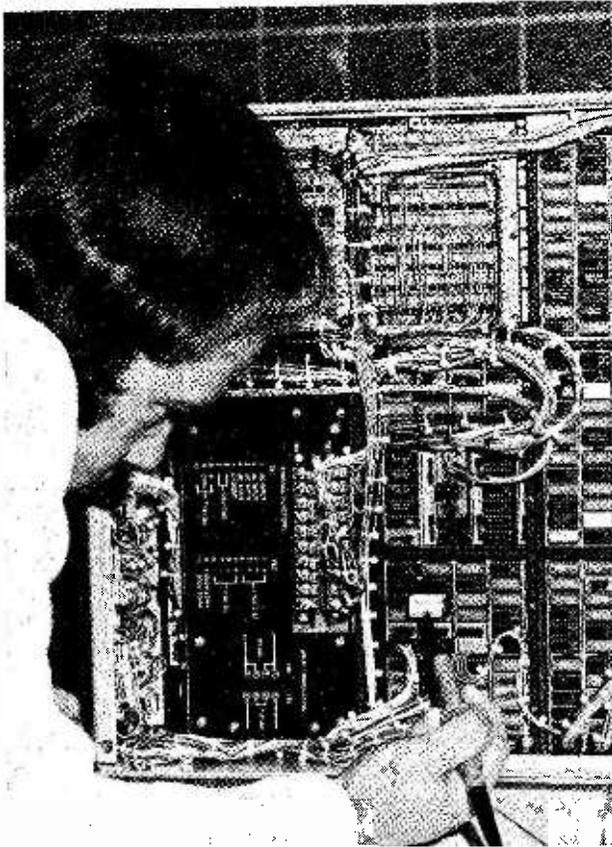Two amplifier kits and BSR deck supplied by Barrie Ltd.



This hobby brings big rewards.

A soldering iron and a screwdriver. If you know how to use them, or at least know one end from the other, you know enough to enrol in our unique home electronics course.

This new style course will enable anyone to have a real understanding of electronics by a modern, practical and visual method. No previous knowledge is required, no maths, and an absolute minimum of theory.


You build, see and learn as, step by step, we take you through all the fundamentals of electronics and show you how easily the subject can be mastered and add a new dimension not only to your hobby but also to your earning capacity.

All the training can be carried out in the comfort of your own home and at your own pace. A tutor is available to whom you can write, at any time, for advice or help during your work. A certificate is given at the end of every course.


1

Build an oscilloscope.

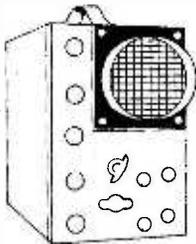As the first stage of your training, you actually build your own Cathode ray oscilloscope! This is no toy, but a test instrument that you will need not only for the course's practical experiments, but also later if you decide to develop your knowledge and enter the profession. It remains your property and represents a very large saving over buying a similar piece of essential equipment.




2

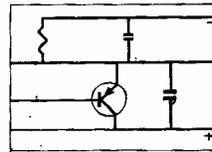

Read, draw and understand circuit diagrams.

In a short time you will be able to read and draw circuit diagrams, understand the very fundamentals of television, radio, computers and countless other electronic devices and their servicing procedures.

3

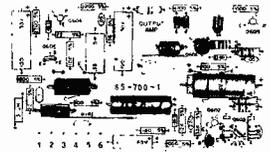

Carry out over 40 experiments on basic circuits.

We show you how to conduct experiments on a wide variety of different circuits and turn the information gained into a working knowledge of testing, servicing and maintaining all types of electronic equipment, radio, t.v. etc.

PLUS

FREE GIFT!



ALL STUDENTS ENROLLING IN OUR COURSES RECEIVE A FREE CIRCUIT BOARD ORIGINATING FROM A COMPUTER AND CONTAINING MANY DIFFERENT COMPONENTS THAT CAN BE USED IN EXPERIMENTS AND PROVIDE AN EXCELLENT EXAMPLE OF CURRENT ELECTRONIC PRACTICE

To find out more about how to learn electronics in a new, exciting and absorbing way, just clip the coupon for a free colour brochure and full details of enrolment.

Brochure without obligation to:

**BRITISH NATIONAL RADIO
& ELECTRONICS SCHOOL, Dept WL66
P.O. Box 156, Jersey, Channel Islands.**

NAME _____

ADDRESS _____

(Block caps please)

ERSIN

Multicore

5 CORE SOLDER



for fast easy reliable soldering

EASY TO USE DISPENSERS AND REELS

IDEAL FOR HOME CONSTRUCTORS

Ersin Multicore Solder contains 3 cords of non-corrosive flux. Instantly cleaning heavily oxidised surfaces. No extra flux is required.

SAVBIT handy solder dispenser



A coil of Ersin Multicore Savbit Solder in a dispenser 7ft 6in of 18 s.w.g. (2.2 metres of 1.22mm). The Solder that reduces the wear of soldering iron bits.

Size 5 32p

SAVBIT solder for general purpose work

A handy plastic reel of SAVBIT alloy. 63ft of 18 s.w.g. (19.2 metres of 1.22mm)

Size 12 £1.72



ALU-SOL for soldering aluminium

New Multicore Alu-sol flux-cored solder. In 16 s.w.g. No extra flux needed. Plastic reel holds 36ft. Supplied with full instructions. Also available in solder dispenser.

Size 4 £2.32



Fine gauge solder for soldering small components

Fine gauge solder for soldering small components 138ft of 22 s.w.g. (42.0 metres of 0.71mm) Ersin Multicore 5 core solder wound on a plastic reel. Suitable for intricate work and small components.

Size 10 £1.44



For soldering fine joints

Dispensers of Ersin Multicore Solder make those small jobs easier. 21ft of 22 s.w.g. (6.4 metres of 0.71mm) solder, specially suitable for soldering fine wires, small components and for repairing printed circuits.

Size 15 36p

Or size 19A for kit wiring or Radio and T.V. repairs 7ft. (2.1 metres) of 18 s.w.g. (1.22mm) Ersin Multicore Solder.

Size 19A 34p



NEW BIB WIRE STRIPPER & CUTTER

Fitted with unique 8 gauge selector with handle locking device and easy grip handles. Spring incorporated for automatic opening. Strips insulation from flex and cables in seconds and can also be used as a cutter.

Model 8B. 80p



NEW SOLDER WICK

Absorbs solder instantly, from tags and printed circuits. Only needs 40 to 50 Watt soldering iron. Quick and easy to use. Does not need flux and is non-corrosive.

Size 18 90p



Bib Hi-Fi Accessories Limited.

Prices shown are retail prices (net) excluding V.A.T. from Electrical and Hardware Shops. It is not possible to send 15p P&P. Prices and specifications subject to change without notice.

Sole U.K. Sales Concessionaries, P.O. Box 76 Hemel Hempstead, Herts. HP2 4RH

orchard electronics

A FEW TRANSISTORS FROM OUR LIST

AC128 25	ASV28 30	BC135* 12	BC178B 18	BC261A 16	BC559* 9
AC128 25	ASV27 30	BC136* 16	BC179B 18	BC262A 15	BCY70 15
AC127 24	ASV28 30	BC137* 18	BC182B* 11	BC267A 16	BCY71 16
AC128 25	ASV29 34	BC138 15	BC183B* 10	BC268B 13	BCY72 14
AC132 33	ASV77 70	BC139 35	BC184B* 12	BC269 19	BD115 60
AC141 20	BA145* 15	BC142 22	BC184I* 11	BC270 20	BD121 90
AC142 17	BA154 10	BC143 24	BC184J* 11	BC280 27	BD122 68
AC151 24	BA155 12	BC147* 9	BC185 25	BC291 25	BD131 26
AC153 27	BAX12 10	BC147B* 10	BC187 28	BC302 24	BD132 38
AC176 20	BAX13 4	BC148* 9	BC1204A* 18	BC303 30	BD133 65
AC188 20	BAX16 8	BC148B* 10	BC205A* 15	BC304 27	BD135* 37
AD161 42	BC107 11	BC149B* 11	BC206A* 15	BC307A* 16	BD136* 39
AD162 42	BC107A 12	BC149C* 11	BC207A* 11	BC308A* 14	BD137* 44
AF114 24	BC108 10	BC153* 18	BC208A* 11	BC309B* 16	BD138* 47
AF115 24	ECL5B 11	BC154* 18	BC209A* 12	BC317A 12	BD139* 54
AF116 24	BC109 11	BC157B* 12	BC212A* 13	BC319B* 12	BD165* 75
AF117 24	BC109B 12	BC168A* 12	BC212L* 15	BC322B 15	BD165* 34
AF118 47	BC109C 13	BC169A* 12	BC213B* 12	BC327* 20	BD232* 70
AF124 30	BC116* 15	BC167A* 11	BC213L* 14	BC328 18	BDY20 80
AF125 30	BC116* 15	BC168* 14	BC214* 15	BC327* 18	BF115 22
AF126 28	BC117* 18	BC171A* 14	BC214L* 17	BC330 18	BF154* 20
AF139 34	BC118* 10	BC172A* 15	BC287A* 16	BC461 35	BF158* 20
AF186 50	BC119 28	BC173B* 16	BC388A* 15	BC557* 9	BF159* 26
AF239 37	BC125* 14	BC177 17	BC395* 15	BC558* 9	BF160* 20

SILICON/REC. RESISTORS

50V 3A 13p	1 1/2 watt B12
100V 3A 15p	
200V 3A 15p	

1Ω-10mΩ

THYRISTORS

60V 1A 25p
100V 1A 30p
200V 1A 40p
600V 1A 60p
BT 106 120p

DIODES

IN4002 6p
IN4006 10p
IN4148 5p

IC's LINEAR

709 (8 pin Dtl) 21p*	BZX89/BC788
741 (8 pin Dtl) 33p*	3V3, 3V6, 3V9,
NE555 60p	4V2, 4V7, 5V1,
NE566 190p*	5V6, 6V2, 6V1,
NE567 270p*	7V5, 8V2, 8V1,
SN76012N 157p*	10V, 12V, 13V,
TAA550 86p*	15V, 18V, 30V,
TBB800 138p*	All at 12p* each

IC's TTL/D19

7400 15p
7401 20p
7402 15p
7403 15p
7404 25p
7405 25p
7408 40p

PLUS C I MOS

VOLTAGE REG. (TO3)

1A, 5V, 12V,
15V £1.35
1A, 5V, 12V,
15V £1.75

LED

125 Red 20p	Like TTL
125 Yel 27p	209
125 Grn 27p	0.125"
TTL 200 Red 20p	
TTL 200 Amber 27p	0.2"
TTL 200 Grn 20p	

SAE for full list of components "same day despatch to mail order customers" "Minimum order £1 p & p 25p". Callers Mon. - Sat. incl.

VAT—Items marked * add 12½%, Rest at 8%

Flint House, High Street, Wallingford, Oxon OX10 0DE
Tel. Wallingford (0491) 35529 Telex 45PWALFRD849349

Mixed Nuts, Bolts, Screws, Eyelets, Grommets, etc., 50p per lb plus postage and packing* 30p.

Fuse Holder Nylon 3p each*

Bulb Holder Nylon 3p each*

Transistor or Diode metal mounting or Cooling clip 2p each*

5 Pin Din Socket 6p each*

2 Pin Aerial Socket 6p each*

Cord Wheel 1½" dia. 2p each*

Drive Spindle for Indicator 3p each*

Plastic or Wire Indicator Bar 1p each*

Knobs 2p each*

Sleeving: Grey 8mm od x 5mm; Black 10mm od x 5mm 5p per metre*

RF - HT Choke 3p each

Electrolytic Capacitors: 400 µF 16V, 250 µF 25V, 125 µF 16V, 320 MFD 6-4V, 220 µF 25V, 400 µF 10V, 10 µF 16V, 10 µF 25V, all at 6p each.

Resistors, mainly Erie make, Mixed values, 100 at 50p, 200 at 90p, 500 at £2.00.

Mixed Capacitors: 100 at 65p, 200 at £1.10, 500 at £2.50.

Toko Coils: 20 at £1 or 6p each.

Car Radio Push Button Switch Set
Ferrite rod 15p each
Push Button Switches, Single 5p each
Triples 15p each, Fours 20p each, Sixes 25p each.

POTENTIOMETERS
Single without switch 20K and 100K Lin and log 1MO log only 15p each
Single with Switch 5K and 470K 20p each
Dual Pots without switch 20K, 100K and 470K Lin and Log 30p each
Dual Pots with switch 20K and 80K and 1MO Lin only 35p each
Slides: Dual 100K Log, Singles 1MO Lin 22K, 100K, Lin 7p each
PACKS: Mixed Potentiometers 10 at £1.00

**Aerial Coils M.W. and L.W. without Ferrite rod 5p each
10ft each with Ferrite rod 25p each**

Car Radio Transformers 20p each

Transistors: AC 127, AC 128, AC 176, all 9p each

Gang Condensers 50p each

Pre-set Skeleton 3p each

Trimmers 3p each

VHF Diode Tuner £2 each

POLYSTYRENE CAPACITORS
10, 68, 100, 130, 1080 all 5% tol 30VDC Working; 100, 200, 320, 390, 1200, 1300, 1800, 2½% Tol 30VDC Working; 200, 300, both 10% Tol 30VDC Working; 1300 2½% Tol 125 VDC Working. All at 2p each.

PLEASE NOTE: All items subject to V.A.T., please add to all items * 8%, all other 12½%, PLUS POSTAGE/PACKING 20p per £1 order except nuts and Bolts Pack. Minimum order £1.00.

TERMS: CASH WITH ORDER. REGRET MAIL ORDER ONLY.

K.K.S. TRADING COMPANY
Department R/C
38 Oakdene, Cheshunt, Herts, EN8 9JA

HOTLINES

ON RECENT DEVELOPMENTS

IT FOOLS 'EM!

If you are one of those people who enjoys dropping the odd mouthful of technical novelty—try monolithic gyrator. Ageing engineers have known about them for years but the gyrators were costly to fabricate and so did not appear on the market in any great numbers.

A Dutch company has now manufactured what many believe to be the very first monolithic gyrator. So what are they? Well, they are very small, and when you terminate them with a capacitor, they pretend to be an inductance—but without bulky coils. At present, one adds a single capacitor plus two resistors to form a frequency conscious circuit which can be extremely compact. Another rather startling fact about these gyrators is the size of coil they can fool other electronic circuits into thinking they are. For example a 1,000,000H (one million Henries) coil can be simulated—and to within 0.2% too. Just imagine a 1,000,000H coil—and the gyrator chip measures only 3.4mm x 3.4mm. Used in resonant circuit applications, a Q of between 500 and 5,000 is achievable.

A CALCULATING MOVE MATE!

The second idea (I predict) will take off very fast indeed once it becomes available. It's a pocket sized calculator in appearance—but it isn't, if you follow me. Closer examination reveals a miniature chess board engraved or screened on the face together with the necessary buttons to enter moves. The hand held unit employs a microprocessor and the unit was on show at a recent International toy fair. Not available yet but the price looks very reasonable. Just the thing you've always wanted; chess without getting board!

ELECTRONIC NOSH

With Easter now firmly behind us for another year, it allows a full twelve months to prepare ourselves to receive an electronically cooked hot cross bun. Not really so far-fetched and will be in our homes by

next Easter. Gone are the old switches and timers: In their place has come a cooker with digital readout, electronic cooking keyboard and a store of some 120 cooking programs in its own memory banks.

The housewife of the future needs only to mix ingredients as per the cooking book (supplied with the cooker) and then punch in the relevant code for perfect cooking. The grilling and baking programs can be used with hundreds of different recipes and dishes. The cooker uses two Read-Only Memories (ROMs) and a Central Processing Unit (CPU).

Fancy that; if you want to dial-a-doughnut then there's just one place to press!

CREDITABLE

It is a peculiarity of the hologram that if one tiny part of its area is examined, the whole complete holographic image can be seen. To check authenticity of any one of these cards, it is only necessary to examine a tiny part of the card and the holographic image at that point will show the whole card—as it was originally. This image, together with a direct image of the card being viewed are shown side by side in a special viewer. Any alteration can thus be immediately detected. Clearly a method that will not forge ahead!

1k CQ's

Good news for Hams and anyone else interested in producing a number of different frequencies with crystal controlled accuracy. A CMOS LSI digital chip is now on the market which will provide 1,021 output frequencies from one crystal—a truly digital v.f.o. It will operate from a 5V line and will accept input frequencies of up to 5MHz. Another bonus too, it isn't greedy on power; dissipation is only 5mW. I note that in the United States, a sample by post costs \$19.76c. It seems doubtful if the company would send one over to the UK against a remittance but the number to watch for when they become available here is HCTRO320.

Lids on the Amateur bands should note that this is not a heaven-sent device for calling CQ on 1,021 frequencies at the same time!

Bad news for the forgery profession. Alteration of credit cards and the like will soon be quite impossible if a German company gets its system accepted. The original card is photographed using a laser to form a holographic image which is then bound with the original card and sealed in.

SKINNY C's


How thin is thin? It really depends upon what one is talking about. I was impressed by the thinness of a series of capacitors called Thin-trim. These are variable types with an adjustable range from 7 to 45pF. They measure 0.2 x 0.2 x 0.05in. The manufacturers inform that they make another type with a 25pF maximum value—but of course, that's much smaller! Wonder how many puffs to the pound?

READ-OUT

Playing games with electronic calculators has been in vogue for some time. The idea is that by turning the unit upside down, it is possible to "read" a message formed by the number displayed. It seems that certain companies are taking the whole thing a few steps further—and it isn't necessary to turn the calculator upside down.

One idea shortly to be introduced allows a calculator to be used as an active terminal for a computer. In this application, it forms a substitute for a teletype terminal. With this unit, it will be possible to talk to the computer and to receive information which will then be displayed on the calculator's readout.

GOING BACK...

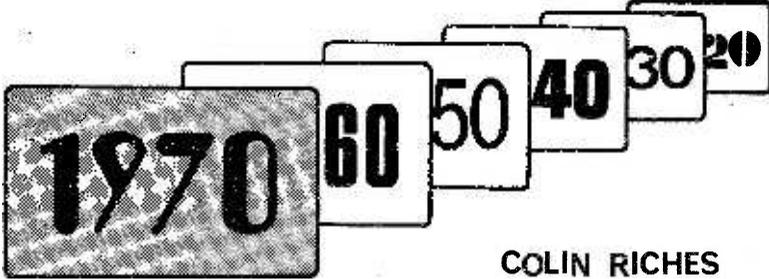

COLIN RICHES

ALLEXANDER Graham Bell was born in Edinburgh on 3 March, 1847. His father and grandfather were teachers of elocution and he used a new system of phonetic symbols, invented by his father, to teach the deaf to speak. In 1870 the family emigrated to Canada and Bell established himself in Boston as a teacher of the deaf.

Bell's telephone arose from a chance observation made in 1875 when he was working on his "harmonic telegraph". This was an instrument designed to carry several telegraph messages over a single circuit by using currents of a different frequency for each message, and detecting each signal by a tuned reed and an electromagnet. With two such instruments connected together he noticed that when one reed was twanged the corresponding reed on the other instrument vibrated in sympathy. Bell had assumed that the current generated by a vibrating reed would be too feeble to be of use. The discovery that it could set another reed in motion estab-

lished a train of thought that led to his "gallows frame" telephone (see picture). A pair of these, used as transmitter and receiver, produced sounds that were unmistakably vocal, though not intelligible.

On 7 March, 1876 Bell was granted a patent that covered the harmonic telegraph, telephones acting on the principle of the gallows-frame instrument, and also the production of a signal by varying a resistance and thereby controlling the current from a battery. He returned to his telephone experiments, now using a crude variable-resistance transmitter. On 10 March, 1876 his assistant heard the first intelligible sentence conveyed by a telephone, "Mr. Watson—Come here—I want to see you". Since then most telephones have used the variable-resistance principle in their transmitters, though Bell returned to the electromagnetic transmitter and used it to establish the telephone commercially in North America. In August 1877 he came back to Britain to promote the telephone. In January 1878 he demonstrated it to Queen Victoria and in June established The Telephone Company Limited.

Meanwhile Thomas Edison had produced a practical variable-resistance transmitter employing compressed lamp-black, which gave a much greater output than Bell's electromagnetic instrument. Edison could not use Bell's receiver because of the patent, so had to invent his own. This was an electrochemical device, the "motograph", which gave loud but poor-quality reproduction and required the user to turn a handle continuously. However, it served its purpose of strengthening Edison's commercial position, and he founded a British company in August 1879 which merged with Bell's in 1880 to

form The United Telephone Company Limited.


By 1880 commercial rivalry was less important to the telephone than its legal status. For ten years public telegraphy in Britain had been a state monopoly run by the GPO. So long as Bell confined the telephone to private wires, relations with the GPO were reasonably cordial. But from the outset he realised that the future of the telephone lay in the operation of *exchanges*, enabling any subscriber to be connected with any other, and in 1879 both the Bell and Edison Companies opened exchanges in London. The GPO realised that this new development could undermine the revenue of the telegraph service, though it was not sufficiently convinced of the



Alexander Graham Bell (1847-1922).

telephone's usefulness to wish to be committed to exploiting it. It was nonetheless able to control the development of the telephone system after obtaining a High Court judgment that the telephone was a telegraph and a telephone message was a telegram within the meaning of the Telegraph Acts. Commercial companies were licensed and though there were numerous companies in operation during the 1880's, the three largest merged in 1889 to form The National Telephone Company, which thereafter held a dominant position until its licence expired on 31 December, 1911; the GPO then took over full responsibility for the nation's telephone service.

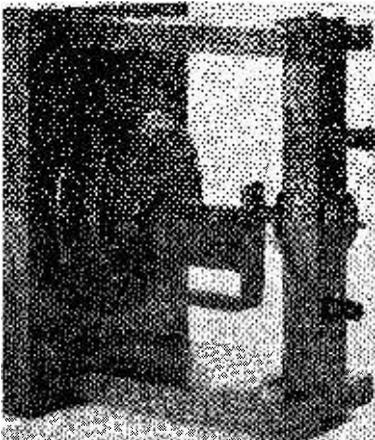We thank the Science Museum for information used in this article.



Bell's "gallows" telephone.
Science Museum picture.

SAXON ENTERTAINMENTS LTD

SYSTEM 7000


professional standards · realistic prices

SAI208D—120 WATTS RMS POWER AMP

Uses 150W 16A RCA devices

All three types include

- 10 Transistors 4 Diodes—Fibre Glass P.C.B.
- Typical Distortion—0.4%: Noise—80dB
- Short, Open Circuit proof—Load line limiting
- Only FOUR Connections—Simplicity!
- High sensitivity (240mV) suits most mixers
- 30 Hz—40kHz ± 1dB Frequency response
- Single supply line—no output capacitor needed (95V)
- Standard 8Ω output—will operate on other impedances
- Compact—6" × 3" × 1½" (15 × 8 × 4cm)
- All units individually tested and guaranteed

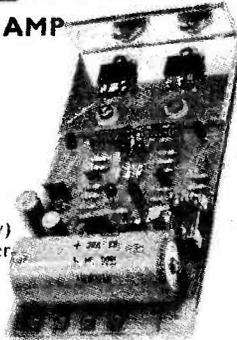

In the same series

- SA608**
60 W. RMS
into 8Ω (65V)
£12.50
- SA308**
30 W. RMS
into 8Ω (48V)
£9.50

Large SAE brings leaflet

POWER SUPPLIES

on glass-fibre P.C.B., high grade transformer, fully fused and ready to wire:

- PM120/1 for one SAI208D £11.60
- PM1202 for two SAI208D £15.30
- PM601/2 for one or two SA608 £10.50
- PM301/2 for one or two SA308 £8.80

SAI208D 120 volts R.M.S. into 8Ω £19.50

SYSTEM 7000—DISCO CONTROL UNIT

- Complete and ready to plug in
- Totally encased—no soldering at all
- Tough, bold, two tone stainless panel—for panel mounting or freestanding
- Inputs for 2 ceramic cartridges/tape/microphone
- Individual deck controls AND left/right fader
- Low noise (—80dB) 20 Hz—50kHz ± 1dB
- Suits all Saxon amplifiers and most other makes
- ½ watt headphone monitor—five position switch with mute positions



- Controls—L. to R.: Mic, Vol/Treble/Bass, Autofade depth, L/Deck Vol, R/Deck Volume, Tape Volume, Treble, Bass, Master, Monitor Volume, Monitor Selector-On-Off

MONO £34.50

STEREO £49.50

In Modular Form

Printed circuit sub-assembly version of disco control unit: All electronics included. Only plugs, socket and one switch required.

MONO £18.50 STEREO £27.50


Front panel for either version £3.50

SYSTEM 7000 LIGHTING CONTROL UNIT

- Full control of 3kW of lights (1kW/channel)
- Audio control plus sequence plus override
- Variable speed sequence with slider function control
- Stainless steel two tone panel—matches mixer
- 13 transistors 8 diodes—advanced control circuitry
- High audio sensitivity—operates from any amplifier
- Attractive Bondene case—free standing or panel mounting
- Individual tone controls plus master audio control

Inc. case and plug—ready to use

£38.00

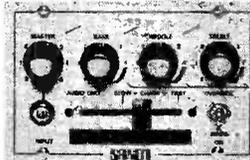

SUPERFECT MODULE

On P.C.B. requires only plug/socket/panel for mounting as desired £27.75

Soundlite 3kw Converter Module

O/P up to 1 kW/channel: Individual tone and master controls: RCA 8A triacs: Scintillating Light Display: Operates from any amplifier: Glass-fibre PCB: Unbeatable value at

£15.50

SYSTEM 7000 MODULAR MIXING


with panels as illustrated

- COMPLETELY WIRED WITH STAINLESS PANEL
- UP TO 20 CHANNELS MONO, STEREO OR MIXED
- Inputs for all sources inc. mag. cartridge
- Wide range bass and treble controls
- ½W monitor power outlet
- Modern low noise circuitry
- Echo send/return facility
- 5cm matrix—bold panel
- Send for details

- Only one mixing module required
- Feeds most amplifiers
- 20Hz—30kHz ± 1dB
- Complete—ready to plug in or solder
- Individual monitor buttons

INPUT Mono £8.50
Stereo £12.00

MIXER Mono £8.50
Stereo £12.00

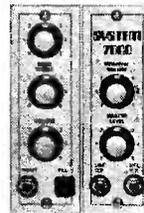

PCB MODULES

With same facilities and performance as complete units.

- Soldered or edge connections.
- IM.7001/M mono input £5.50
- IM.7001/S stereo input £9.00
- IM.7002/M mono mixing £5.50
- IM.7002/S stereo mixing £9.00



SAXON STROBES

SUPERSTROBE

- 1 flash/2 sec up to 20 flashes/sec £24.75
- Compact black Bondene case
- Ideal for the mobile disco or smaller club

PRO-STROBE

- External trigger—audio up to 240V
- Use with Soundlite for rainbow strobe effect
- Smart, tough Bondene case 8in × 8in × 5in.
- Giant 80 watt tube Discharge energy up to 6 Joules £38.50

150 WATT LIQUID WHEEL PROJECTOR

- Complete with wheel
- 150 watt tungsten lamp
- Wide range of extra effects may be attached
- Sturdy construction £29.20
- Adjustable feet

Spare wheels £4.90



Loudspeakers 12"/50W high grade chassis units: 14000 gauss: presence dome: £14.50

Cabinets Attractive range of speaker and other cabinets at our showrooms. Enquiries welcomed.

ACCESSORIES Mics: Headphones: Special Lamps.

PRICES include carriage and packing. VAT must be added to all orders at 8%. C.O.D. 65p extra. S.A.E. with all enquiries please.

Send or phone your ACCESS or BARCLAYCARD No. for prompt attention. After 5.0 p.m. leave your message on our answer-phone.

Orders by post—Please make cheques or crossed P.O.'s payable to
SAXON ENTERTAINMENTS LTD.
327-333 WHITEHORSE ROAD, CROYDON, SURREY CR0 2HS
Telephone: 01-684 0098 / 6385
Shop Hours 9am—5pm (Lunch 12.30—1.30): Sat. 9.30am—5pm.
Prices & specifications subject to alteration without notice. Mail Order desk 10am—4pm Mon—Fri.

TRADE ENQUIRIES

Send for name and address of your nearest wholesale supplier.

Wire Wound Resistors. Our selection of mixed valves. 30 for £1.40. 100 for £3.50.

Audio Amplifier Module. Mullard LP1173. Output nominal 10 watt. Supply voltage +24vt. With data and circuit. £2.30.

Varicap Control Selector. 4 way 25K. £1.50. 6 way 14.5K. £2.00.

Mains Droppers. 10 mixed values £1.00.

Edgewise Level Meters. 200mA. Size 2" overall 50p.

15 Assorted Switches. Micro, push button, etc. £1.90.

Tag Strips. 3 way to 7 way. 50 for £1.15.

Chrome Plastic Knobs. 3 Types 4 off each with spring clip. £1.25.

Repenco & Denco Coils. New boxed, our selection. 5 for £1.15.

Ferguson Stereogram Chassis. Model 3357. All transistor. Med LW. FM. 3 watts per channel S.M. With connection data. Less tuning scale. £18.00. P.P. free.

Ferguson Stereogram Chassis. MW. LW. FM. With tuning scale (5+5 watts sine wave) 15 ohms £26.25. P.P. free.

Copper Clad Laminate. 8" x 7" - 3 boards £1.00 + 8%.

Ferric Chloride. 1lb 65p + 8%.

Repenco Transformers. AF1. AF2. TT45. 46. 47. 49. 53. 20p each.

Crystals HC6U. (MHz) 12700; 12891.6; 9455.55; 9530.55; 9087.5; 9456.25; 52.01667; 52.02500; 37.7625; 51.56667; 52.03333; 9090.62; 9531.94; 9533.33, 50p each.

Transfilter. 455KC. AM. 5 for £1.00.

Electrolytics. 32.32 32µF, 325v. 2" x 1 1/2" 35p; 80µF 150v 1 1/2" x 1" 20p; 2000µF 30v, 2 1/2" x 1" 25p; 2000µF 35v 3" x 1" 30p; 470µF 100v 3" x 1 1/2" 25p; 2000 2000µF 25v 2" x 1 1/2" 35p; 700µF 200v 3 1/2" x 1 1/2" 30p; 16 16µF 275v 1 1/2" x 1" 20p; 4500/900/900µF 30v 2 1/2" x 1 1/2" 50p; 2500µF 40v 3" x 1 1/2" 40p; 470µF 25v 1 1/2" x 1 1/2" 15p; 4,000µF 25v 3" x 1 1/2" 40p; 32µF 450v 1 1/2" x 1" 30p; 8µF 16µF 450v 1 1/2" x 1 1/2" 30p; 1000µF 12v 1 1/2" x 3/4" 15p; 5000µF 50v 2" x 1 1/2" 50p; 150/200 200µF 300v 3" x 1 1/2" 50p; 16/16/16µF 350v 2" x 1" 30p; 50/30µF 500v 3 1/2" x 1 1/2" 50p; 400µF 40v 1 1/2" x 3/4" 20p.

Try our parcel of small capacitors 20 mixed valves £1.50 + post.

Miniature Presets - Selection of various values 10 for 65p.

Coil Formers. 50 mixed, £1.25.

Slider Volume Controls. 1K Lin; 100K Log; 1 Meg Log; 25K Lin; 25K Log; 10K 100K Log; 100K 100K Log; 50K Log. 35p each.

U.H.F. 625. Transistor push button tuner (NSF Telefunken), as used on Decca MS2400. Brand new and boxed. Circuit diagram supplied. £3.00.

Thorn T.V. 1F. Chassis. 950 Series (less valves) £1.60.

Aluminium Chassis. 7 1/2" x 5 1/2" x 2 1/2" 65p. 10" x 7 1/2" x 2 1/2" 75p. 11" x 7 1/2" x 2 1/2" 85p. + 8%.

500 Metres. 1/2 0148 TC. Single polythene lapped screen wire. £5.00 + 8%.

Please add 10% P.P. Unless stated free P.P. VAT 12 1/2% to be added to total order unless stated 8%. No goods despatched outside U.K.

BSS Single Play Decks with Cue-fitted stereo cartridge. P146 £11.00. P153 £12.00.

SURPLECTRONICS

216 LEAGRAVE ROAD,
LUTON, LU3 1JD, BEDS.

CF GIRO NO. 331 7056. Access and Barclaycard accepted. C.W.O. only. Terms of business as in our Catalogue. Export Order enquiries welcome (£5. min.)

Official Orders accepted from Educational and Government Departments. ALL PRICES include VAT @ 8% P. E. & O.E. SHOP HOURS 9-12.30, 1.30-5.00 5 days. CLOSED WEDNESDAY.

1976 ISSUE 66 PAGES - 3,000 ITEMS FULLY ILLUSTRATED

20p CREDIT VOUCHERS

*ALL NEW STOCK

*SATISFACTION GUARANTEED

*DISCOUNTS

*NEW PRICE LIST For Cat. 4a - S.A.E.

Boxes - Cases - PC Kits - Test Materials - Tools - Resistors - Test Meters - Capacitors - Hardware - Semiconductors - Books - Pots - Coils - Audio Accessories - Screws - Connectors - Audio Modules - Veroboard - Transformers - Knobs - Calculators - Audio Leads - Batteries - S dec Storage Units - Heatsinks, etc., etc.

20p plus 10p postage

CTRONIC COMPONENTS Catalogue 4a

CF

ORS LTD.

SPECIAL CAPACITOR KITS

C280 Kit - PC Mounting polyester 250V 5 of each value: 0-01, 0-022, 0-047, 0-1, 0-22µF, 2 of 0-47, 1µF, £1.96 net

C296 Kit - Tubular polyester, 400V, 5 of each value 0-01, 0-022, 0-047, 0-1, 0-22µF, 2 of 0-47µF, £2.67 net.

RHYTHM GENERATOR FULL KIT AVAILABLE SAE FOR LIST

SPECIAL RESISTOR KITS (CARBON FILM 5%) (Prices include post & packing) 10E12 - W or 1/2W KIT: 10 of each E12 value, 22 ohms - 1M, a total of 570 £5.25 net. 25E12 1/2W or 1/4W KIT: 25 of each E12 value, 22ohms - 1M, a total of 1425 £12.64 net.

B. H. COMPONENT FACTORS LTD.

MULTIMETER U4323

22 Ranges plus AF/IF Oscillator 20,000Ω/Volt. Vdc - 0.5 - 1000V in 7 ranges. Vac - 2.5 - 1000V in 6 ranges. Idc - 0.05 - 500mA in 5 ranges. Resistance - 5Ω - 1MΩ in 4 ranges. Accuracy - 5% of F.S.D. OSCILLATOR - 1KHz and 465KHz (A.M.) at approx. 1 Volt. Size - 160 x 97 x 40mm. Supplied complete with carrying case, test leads and battery. PRICE £9.95 net P. & P. 75p U4323

MULTIMETER U4324

34 Ranges. High sensitivity. 20,000Ω/Volt. Vdc - 0.6 - 1200V in 9 ranges. Vac - 3 - 900V in 8 ranges. Idc - 0.06 - 3A in 6 ranges. Iac - 0.3 - 3A in 5 ranges. Resistance - 25Ω - 5MΩ in 5 ranges. Accuracy - dc and R - 2 1/2% of F.S.D. ac and db - 4% of F.S.D. Size - 167 x 98 x 63mm. Supplied complete with storage case, test leads, spare diode and battery. PRICE £11.72 net P. & P. 75p U4324

MULTIMETER U4341

27 Ranges plus Transistor Tester. 16,700Ω/Volt. Vdc - 0.3 - 800V in 8 ranges. Vac - 1.5 - 750V in 6 ranges. Idc - 0.06 - 600mA in 5 ranges. Iac - 0.3 - 300mA in 4 ranges. Resistance - 2KΩ - 2MΩ in 4 ranges. Accuracy - dc - 2 1/2% ac - 4% of F.S.D. Iife - 10 - 350 in 2 ranges. Size - 115 x 215 x 90mm. Complete with carrying case, test leads, and battery. PRICE £12.10 net P. & P. 75p U4341

MULTIMETER U4313

33 ranges. Knife edge with mirror scale. 20,000Ω/Volt. High accuracy, mVdc - 75mV. Vdc - 1.5 - 500V in 9 ranges. Vac - 1.5 - 800V in 9 ranges. Idc - 60 - 120 microamps in 2. Idc - 0.6 - 1500mA in 6 ranges. Iac - 0.6 - 1500mA in 6 ranges. Resistance - 1KΩ - 1MΩ in 4 ranges. db scale - 10 to +12db. Accuracy - dc - 1%, ac - 2 1/2%. Size - 115 x 215 x 90mm. Complete with carrying case, test leads and battery. PRICE £16.09 net P. & P. 75p U4313


(P.W.), LEIGHTON ELECTRONICS CENTRE 59 North Street, Leighton Buzzard, LU7 7EG. Tel.: Leighton Buzzard 2316 (Std. Code 05253)

PRECISION PETITE LTD. (Dept. P.W.)

119A HIGH STREET, TEDDINGTON TW11 8HG

Tel. 01-977-0878

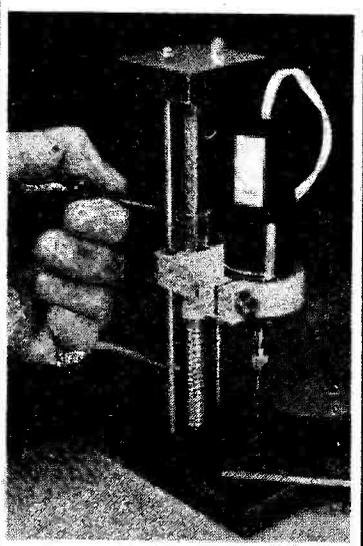INTRODUCING A MINIATURE PRECISION 12V. D.C. DRILL DESIGNED FOR THE ELECTRONIC ENGINEER



Mk II Drill only Stand

£8.00 p.p. 35p

£3.76 p.p. 35p



Complete kit as illustrated (less batts.) with a variety of 30 tools. Space for Stand and Transformer.

KIT 30 TOOLS £16.00 p.p. 75p

STAND £3.76 p.p. 35p

TRANSFORMER £5.50 p.p. 75p

S.A.E. FOR DETAILS



AMATEUR BANDS

by Eric Dowdeswell G4AR

THE author of a feature such as this is usually left with mixed feelings after completing his stint for the month. Letters from newcomers to the amateur and broadcast bands or those seeking information on our hobby raise the spirits no end, while established correspondents who write in happily to tell me that they've just passed the Radio Amateurs Examination bring despair, as I realise I've lost a reader but elation to know that a new call sign has come into being.

I believe it is important to find out just how the newcomer has got around to the SW bands. Often it is the result of casually tuning over the SW bands on a domestic receiver and wanting to do it better on a decent receiver. Sometimes it's an offshoot of listening to aircraft, police and other Public Services on the VHF bands, something to be strongly deprecated. There is much more fun on the SW broadcast and amateur bands especially when it leads to getting one's own transmitting licence and talking back to other amateurs.

At one time, when amateur band telephony was strictly double sideband and unsuppressed carrier stuff, it could be picked up and resolved on almost any domestic receiver, even if it did not cover the amateur bands! Enquiries locally usually revealed the amateur concerned but the complainant often became interested to the extent of taking up the hobby himself! Or herself, since there were ladies enjoying the hobby from the early days. However with the development and use of single sideband telephony by amateurs this method of "contact" has virtually disappeared since SSB on a domestic set is just a horrible noise. Come to think of it, it's often a horrible noise on the bands themselves! The QRM remains but the source is harder to locate, often requiring the services of the Post Office, and sometimes leading to unpleasantness all round. I often think that the coming of SSB has led to the amateur becoming more isolated from the general public.

Excellent news of **Tim Charles** A8927 of Colchester who has passed his RAE and is taking his code exam in a couple of weeks. He was one of the few readers of this column who bothered to send in logs of stations heard on CW. Let's hope the experience will pay off first time for Tim. With a

bit of luck we may get his new call sign before we go to press. So another reader bites the dust! Inevitable, I suppose! The last bit of news from Tim concerned the positive reception of JA30NB on 160m! he was 449 on 1908kHz so Tim can go out in a blaze of glory!

Ray Woodward in Colne now has an RQ80 ATU in front of his CR70A which, with 132ft of wire, albeit at only 10ft up, has greatly improved reception. He's getting some gear together for the 2m band and hopes to do well on the VHF's as he is some 700ft above sea level up there in Lancashire. **Paul Barker** BRS34898 in Sunderland had a bad month what with the flu and bands in a poor state. SSTV on 20m brought only G4BFB and I8JTU while on SSB CT4AJ proved to be a non-event being just another CT1 in reality!

Steve Cottis of Harrogate worked his way through all the bands from 80 to 10m. His best on 80 was JD1AKE while KC6AQ relieved the monotony on 20m. **Dennis Anderson** writes from Brookwood in Surrey to say that he is now BRS36591 and has joined the Farnborough and District Radio Club and "they are very helpful" which is nice to know. **Paul Flatman** (Ipswich) could only get on for a few days last month but when he did he found 20m pretty active but next to nothing on 15m. A nice one on 80m reported by Paul was K3HVG/P/HR6 on Swan Island. Paul is about to replace his old faithful HRO receiver but I hope he gets something that turns out to be at least as good. With a few mods the HRO can be turned into a pretty good receiver which will out-perform a lot of the modern sets especially in the areas of cross-modulation and inherent noise.

Stephen Budd A8713 in Worthing found 80m "unbelievably fantastic" in the early mornings but was not enthusiastic about the rest of the HF bands. He has shelved plans for a 6-element beam and rotator for 2m after seeing the "ridiculous prices". Especially, as he says, it would only be for one band. **Paul Flatman**, Ipswich, is pretty busy with other commitments, his only free time coinciding with the gap between 20m going dead and 80m coming alive!

Paul Cowburn writes from Leyland, Lancs for the first time and is full of praise for the help he is getting from local G3RFN on the many problems that beset a newcomer to the SW bands. Certainly everyone new to our hobby ought to try and contact his local amateur or radio society rather than try to steer a lonely path, often in the wrong direction. Paul has a Marconi CR300/2 but finds that its performance tends to drop off at the higher frequencies. When this happens it is not a bad idea to build a crystal controlled converter for say 20, 15 and 10m and use the main receiver as a tuneable IF around 3 to 4MHz.



Log extracts

T. Charles:- 160m JA3ONB 40m FM7AV H13HOT 20m VP2MJ ZP5AO 2m DM2BEN/P SM7CHX SP1II UR2RDR (auroral opening) via Oscar 7 VE3SAT W2BLV W90II W0EAZ 70cm PA0GDM PA0MHK

R. Woodward:- 80m CO2JA HK4DF YV4ATI 8P6FV 20m DU9FB HK6CMA VP2MEV 6W8NW

P. Barker:- 20m CT2BB VQ9R VU2HI SSTV G4BFB I8JTU


S. Cottis:- 80m JA6BSM VP9G OE6DK/YK ZL1BJ 40m ZL4ND 6W8DX 20m DU1DBT KC6AQ VP2KJ 5V7WT 9M2FR 15m CT2BB EL2T FM7AQ TU2DF 5N2ESH 10m 9J2WR

P. Flatman:- 80m K3HVG/P/HR6 KG4FU 20m DU9FB HR3JRR VK9XI VP8HZ 6W8MW 8P6FU

All SSB except those in bold which are CW.

S. Budd:- 80m A4FXE EP2SN FP8DX HR2FP KG4GG KZ5JM PJ0USA VP1DW VP2ABC VP2DM VP2KJ YN7R 5T5ZR 8P6GN 40m VK7GK ZL2AQ 20m A6XP C5AF KG6JBX TA1MB 5N2ESH 9X5SP 15m ZD7FT 2m via Oscar 7 DC2ST F6APU PA0JHM

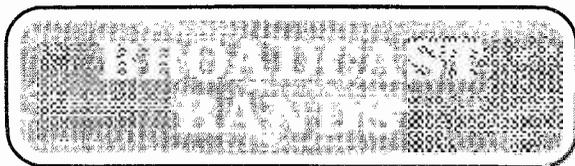P. Cowburn:- 80m CO2JA JA6BSM ZB2DK 40m VK2AVA VK5PB VK7DK YA2WJ YV6CD AD3EST (Washington, special event station, 200 years American Independence).



SHORT WAVE BROADCASTS

by Derek Bell

MANY a time and oft the controversy has been bandied about as to the stability of various SW sets. Those who run what are known as communications receivers maintain that their type of set is far and away the best and indeed the only type of set to use for DX. This point is made, often with some force and the right hand firmly round the opponents throat, in order to ensure that he sees the error of his ways! **R. Burgess** has it seems the best of both worlds in that he has recently purchased a Grundig Satellit 2000 and, though very very expensive, this set has a fair degree of portability and is fine for putting in the car. From his Haywards Heath QTH R.B. has, with the internal aerial pulled in the following:

- Radio Aparecida on 9635 at 0000
- Radio Nacional Colombia on 4955 at 2300
- Radio Abidjan on 11920 at 1940
- FEBA Seychelles on 11715 at 1700
- Radio Togo on 5047 at 2300
- Radio Grenada on 15105 at 2030

This set seems to have the advantage of pulling

in the Latin Americans an hour earlier than they are heard with a cheaper set, and as R.B. says "L.A.'s are at their best in the wee small hours". The latter item on the log, Radio Grenada, was however heard in Huntingdon, Cambs. by **Richard King** on a Russian Vega Selena, logged at 2000 and who rates the signal at nothing less than fours on the SINPO scale. Alongside this item Richard passes on the info that HCJB Quito is to build a 500kW transmitter in Indiana USA and quite pricey it sounds. One of the valves for example will cost 17000 dollars!

Another item of station news is that Indonesia is to phase out its short wave broadcasts by 1979. At present these can be heard on a wide range of freqs. from 2300 up to 17792. The transmitters are all of modest power since they are intended to serve only the home listeners but then so are the Latin Americans and these are heard here in the UK every night. I presume that the Indonesian Radio Jakarta with its overseas service will still be active and this can be heard in English on 11790 and 6045 at 2300, 0900 and 1100 with an introduction played on a Hammond organ.

To continue the theme of cheap transistor sets versus the more expensive rig, **John Baker** of Birkenhead joins in to ask this question and then on his Philips 90L goes on to log:

- Radio Nacional de Brasilia on 11780 at 2100
- Radio Australia on 9570 at 0817
- RSA on 5980 at 2133

"Do the more expensive communications sets offer better value for money than the portables?" asks John, well let's explore this question a little more. To do so we must call in our overseas reader this month **Martin Kennedy** from Christchurch, New Zealand. Martin runs a Codar CR70A hanging on the end of a 100ft long-wire. Pride of the log is the AFN "National Public Radio" from Greenville USA, this signal arrives either over the Pacific or across the pole according to which way Greenville's aerials are switched. Also featured is Radio Free China from Taiwan on 11825 at 0210, so it would seem that communications sets earn their keep wherever they are.

"What", you say "about the home built sets then" **David Wyatt** of Oswestry has built one, a seven transistor superhet with a 20ft wire. David logs on it

- Radio Pakistan on 17910 at 1100
- Voice of Turkey on 11808 at 0017

David gives the address of Voice of Turkey for QSL fans as TRT Voice of Turkey, Ankara, Turkey. He requests the address of Radio Canada, which I can supply, and that is P.O. Box 6000, Montreal, Canada, H3C 3A8.

So, what have we learned up to now?, well that both types of set fill a need but that need must depend not only on the pocket but the situation of the user.

Recently an enquiry was featured in this column for information on a certain type of Royal Navy set. An ex-member of the "Andrew" **E. J. Scudder** adds more to the gen already received. This gentleman had the job of maintaining these sets during the war and informs us that they were made by Eddy-stone. The main problem was the coil pins it seems as operators would pull the coils forward instead of up thus bending the pins and eventually breaking them off, causing much grief and no small amount

MULLARD AUDIO AMPLIFIERS

All in module form, each ready built complete with heat sinks and connection tags, data supplied.

Model 1153 500mW power output £11.10 + 40p post & VAT.

Model 1172 1W, power output £1.35 + 45p post & VAT.

Model EP9000 4 watt power output £2.40 + 50p post & VAT.

EP 9001 twin channel or stereo pre amp. £2.50 + 50p post & VAT.

TINY RADIO CASES

Intended to be adapted for the microscopic key chain radio, size approx. 23 x 21 x 11, back removable also metal flap for battery compartment, should be about right for building your own miniature radio, transmitter or bugging device. Price 40p + 10p each.

MICRO RADIO CONSTRUCTOR'S PARCEL

Not complete kit but consisting of eight matching components as follows:—(1) Wound ferrite aerial. (2) Oscillator. (3) 4 IP's of 4 Twin gang tuning condenser (4) Volume control. These last two items being fitted with control knobs. Price 80p + 20p. Post 20p + 5p.

MAINS TRANSISTOR PACK

Designed to operate transistor sets and amplifiers. Adjustable output 6v., 9v., 12 volts for up to 500mA (class B working). Takes the place of any of the following batteries: K11, PP3, PP4, PE6, PP7, PP9 and others. Kit comprises: main transformer rectifier, smoothing and load resistor condensers and inductors. Real snip at only £1.50 VAT & Postage 50p.

SOUND TO LIGHT UNIT

Add colour or white light to your amplifier. Will operate 1, 2 or 3 lamps (maximum 450w). Unit in Box all ready to work. £7.95 plus 95p VAT and postage.

MAINS MOTOR

Precision made—as used in record decks and tape recorders—ideal also for extractor fans, blowers, heaters, etc. New and perfect. Snip at 95p + VAT & Postage 30p.

1 1/2 stackmotor £1.50 + VAT & postage 35p. 1 1/4 stackmotor £2 + VAT & Postage 40p.

6 DIGIT COUNTER

Made by famous American Company, operated by 24V D.C. or mains through resistor, 1 1/2" x 1 1/2" x 2 1/2" deep. 80p Post & VAT 20p each.

MINIATURE WAFER SWITCHES

2 pole, 2 way—4 pole, 2 way—3 pole, 3 way—4 pole, 3 way—2 pole, 4 way—3 pole, 4 way—2 pole 8 way—1 pole, 12 way. All at 30p + 15p post & VAT each.

MULTI-SPEED MOTOR

Six speeds are available 500, 850 and 1,100 r.p.m. and 8,000, 12,000 and 15,500 r.p.m. Shaft is 1/4 in. diameter and approximately 1 in. long. 230/240v. Its speed may be further controlled with the use of our Thyristor controller. Very powerful and useful motor size approx. 2 in. dia. x 5 in. long. Price £1.40 + 45p post & VAT.

MERCURY BATTERIES

Each made up of 7 cells to give total of 10.7 volts, cells very easily separated for operating portable equipment. These batteries have very good shelf life. Expensive batteries normally but we are offering at an extremely low price of less than 5p per battery, namely £1 per carton of 28 batteries. VAT 8p. Post 40p + 4p.

25V 1/4 AMP INSTRUMENT MAINS TRANSFORMER

Extremely well made, intended for upright mounting and impregnated for quiet operation. Price £1.75 + 2p. Ditto but drop through chassis type with top cover. Price £2. + 16p. Post 15p + 2p.

AMMETERS

Ideal for chargers etc. 2" sq. full vision 0-8 amp 95p, 1 1/2" round 0-2 amp 55p, 0-3 amp 65p, 0-4 amp 75p. Post & VAT 25p each.

RELAY BARGAIN

Type 600 relay, 2 changeover one open and one closed contact. Twin 500 ohm coils make this suitable or closing off DC 6v, DC 12v, DC 24v or AC mains using resistor and rectifier. 40p each. Resistor or rectifier 20p extra. Post & VAT 20p.

ONLY £1.50 FOR SEVEN ELECTRIC MOTORS

7 powerful batt. motors as used in racing cars as power models. Output in types vary for use in hundreds of different projects — Tools, toys, models, etc. All brand new reversible & for 12-24v. batts. Wiring diagram, inc. VAT & Post 40p. FREE plan for mini. power station.

TWIN OUTPUT POWER PACKS

These have two separately B.C. smooth outputs so can operate two battery radios on a stereo amp without cross modulation (they will of course operate one radio-tape-cassette-calculator in full way battery appliance and will save their cost in a few months). Specs: 1. Full wave rectification, double insulated mains transformer—total enclosed in hard P.V.C. case—three core mains lead—terminal output. When ordering please state output voltage 41v, 6v, 7 1/2v, 9v, 12v or 24v. Price £3.95, post and VAT included.

LIGHT PIPE

A mains operated travelling light array. 24ft. long, it uses 130 miniature bulbs which flash in sequences to make bands of light move along the tube—The tube can be draped around a particular item or set and cannot fail to attract attention—complete kit consists of—24ft. of translucent tubing—140 miniature lamps 8 yards multicolour cable—motorised switch, taps for quick connections and full wiring instruction special introductory offer £10 for the complete kit post and V.A.T. paid.

DISTRIBUTION PANELS

Just what you need for work bench or lab. 4 x 13 amp sockets in metal box to take standard 13 amp fused plugs and on/off switch with neon warning light. Supplied complete with 6 feet of flex cable. Wired up ready to work. £2.75, VAT & postage 65p.

ISA ELECTRICAL PROGRAMMER

Learn in your sleep! Have radio playing and kettle boiling as you awake—switch on lights to ward off intruders—have a warm house to come home to. All these and many other things you can do if you invest in an electrical programmer. Clock by famous maker with 15 amp. on/off switch. Switch-on time can be set anywhere to stay on up to 6 hours. Independent 60 minute memory jogger. A beautiful unit. Price £2.95, VAT & Postage 60p, or with glass front, chrome bezel, £1.50 extra.

THIS MONTH'S SNIP

D.I.Y. BURGLAR ALARM KIT NO. 1

This is simple enough for the average householder to install and maintain. It will give protection against intruders coming in through any of four windows and two doors. Intended to frighten intruders away it will start loud ringing bell which will not stop until reset by owner. Kit consists of 6 large trigger mats, 1 loud bell, 1 relay for latching, 1 secret switch, diagram and notes. Price £14 + £1.50p. Post £1.00 + 25p.

THERMOSTAT WITH THERMOMETER

Made by Honeywell for normal air temperatures 40-80 F (5-25 C). This is a precision instrument with a differential which can be adjusted to better than 1-5 F. A mercury switch breaks on temp. rise. Elegantly styled and encased in an ivory plastic case with clear plastic windows, thermometer above and switch setting scale below—size approx. 3-8" x 3-2" x 1-4" deep—can be mounted on conduit box or directly on wall. Price £2.25 plus 50p Post & VAT.

SWITCH TRIGGER MATS

So thin is undetectable under carpet but will switch on with slightest pressure. For burglar alarms, shop doors, etc. 24in x 18in £1.99. Post & VAT 90p. 18in x 10in £1.50. Post & VAT 50p.

CENTRIFUGAL FAN

Mains operated, turbo blower type. Pressed steel housing contains motor and impeller. Motor is 1/10th h.p. giving considerable air flow but virtually no noise. Approx. dimensions 10 1/2" x 4 1/2" £2.50 plus Post & VAT.

MORE CABLE BARGAINS

All prices are very much below regular wholesalers Prices and with the price of copper going up, it will pay you to put some of this into stock, it's definitely better than money. Please if you intend to collect, telephonous (01-688-1833) if possible the day before in case we have to get supplies from out store.

Size	Amps	Type	Price 100 metres	Carriage njo 200 miles
1.5mm	16A	Single c.c.	£2.50 + 20p	80p + 6p
1.5mm	16A	Single double insulated	£3.50 + 20p	90p + 7p
1.5mm	16A	Flat twin	£2.50 + 44p	£1.25 + 10p
1.5mm	15A	Flat twin & E.	£2.50 + 52p	£1.50 + 12p
1.5mm	13A	Flat 3 core	£2.50 + 55p	£1.75 + 14p
1.5mm	13A	Flat 3 core & E.	£2.50 + 60p	£2.00 + 16p
4mm	30A	Single c.c.	£7.50 + 60p	£2.00 + 16p
4mm	30A	Single double ins.	£7.95 + 64p	£2.00 + 16p
4mm	27A	Flat twin	£12.00 + 96p	£2.00 + 16p
4mm	24A	Flat three core	£14.50 + £1.16	£2.50 + 20p
4mm	24A	Flat three core & E.	£15.50 + £1.48	£2.50 + 20p
6mm	35A	Single c.c.	£7.50 + 76p	£2.00 + 16p
6mm	35A	Flat three core	£23.00 + £1.84	£3.00 + 24p
6mm	38A	Twin & E.	£28.50 + £1.80	£3.00 + 24p
10mm	45A	Twin & E.	£35.00 + £2.80	£4.00 + 32p
16mm	64A	Twin & E.	£55.00 + £4.40	£6.00 + 40p

TERMS: Where order is under £5 please add 30p surcharge to offset packing expenses.

J. BULL (ELECTRICAL) LTD.
(Dept. P.W.), 103 TAMWORTH ROAD,
CROYDON CR0 1XX

ITS FREE!

Our monthly Advance Advertising Bargains List gives details of bargains arriving or just arrived—often bargains which sell out before our advertisement can appear—its an interesting list and its free—just send S.A.E. Below are a few of the Bargains still available from previous lists:

Spit motor with Carter gear box. Probably one of the best spit motors made. Originally intended to be used in very high priced cookers; however, this can be put to plenty of other uses, for instance your garden barbecue or to drive a colour disc for a dance or display or to drive a tumbler for stone polishing; in fact, there is no end to its uses. Normal mains operation. Special price during May and June £2.50 + 20p, post 30p + 2p.

Pulse transformer with circuit for sound to light unit. It is a very simple circuit and all parts are readily obtainable from us or you may already have them in your junk box. Price of the transformer with circuit 75p, post and VAT paid.

ORP 12 light cell. This device has been going for some years now but it has not been bettered and new applications keep being found for it. We have good stocks, price 65p + 8p.

Throat mikes. These are an ex WD item as used by air crew on their intercom, but being electromagnetic they also serve as pick-ups on musical instruments, talking to passengers on motor bike and no doubt many other use. Price 60p a pair + 15p.

12v speaker bargain, 8" round mid-range, mite for high price 12in outfit, really super, speaker, £3 + 37p, post 60p + 15p.

O.C.P. photo transistor by Mullard, very popular for circuits such as infra-red burglar alarms, smoke detectors, etc. A big buy enables us to offer at the very favourable price of 25p each — 2p, or 5 for £1 + 8p.

Component boards, mainly ex computer, these contain many useful parts and represent fantastic value at 6 for £1 + 8p. We guarantee the 5 would be different. You would receive 1Cs etc., variable controls with load leads and so on are easy to remove and re-use. Post 50p + 4p.

Microswitch bargain, made by Eyr, Honeywell, Burgess and similar first class makers originally for the Post Office, in fact they have been fitted to Post Office Equipment which was never put into use. They are a changeover microswitch with 10 amp contacts offered at the very low price of 20p for £1 + 8p. Post 40p + 3p.

Ferrite pot core (Vinko) made by Mullard, maker's ref. No. LA 1410/402K, circular, size approx. 1 1/2" x 1 1/2", a size which is the same as the one specified for the Scorpio car ignition system. Price only 50p + 4p per pair. Post 15p + 1p.

12v DC motor made by Smiths, powerful, ideal for car blower; motor size 4 1/2" long x 3" diameter, 1" spindle, 1 1/2" long, £2 + 16p. Post 30p + 8p.

Thermostat with capillary with sensor joined by approx. 1 metre of capillary covering the temperature range 0-170°C capable of switching 16 amps at 250v. Made by the famous Ranco Company with screwed thread and spindle rather like a volume control—has dozens of applications. Offered at only 75p + 6p. Post 12p + 1p.

Aerials. For medium and long wave, wound and fitted on ferrite rod, 9" long by 1/2" diameter. Price 60p + 15p Post 10p + 5p.

Dial thermometer by Rototherm, indicates from 50F to 250F, dial size 3 1/2", chrome and glass front. 75p + 6p. Post 10p + 1p.

Instrument Mains Transformer, 6.3v at 4 amp and 115v at 100mA. This is an upright mounting open construction, small size (2 1/2" x 2 1/2"). Price £1.40 + postage and VAT 60p. DITTO, 6.3v at 1 amp and 150v at 200mA. This is a fully approved upright mounting transformer, size approx. 2 1/2" x 3" x 3". Price £1.95 + post and VAT 85p.

Instrument power supply mounted on a chassis size 9 1/2" x 2 1/2" x 4 1/2". This is suitable for instruments which use Valves and its AC output of 6.3v at 1 amp and a fully smoothed DC outputs of 150v and 200v. Price £2.50 + post and VAT 74p.

FM Band amplifier. This is a 4 valve amplifier tunable to cover FM and nearby frequencies. Tuning is by lecherlines in fully screened compartments and the whole is mounted on a heavy metal chassis size 9" x 2" x 2 1/2". This requires a separate power supply of 150v DC at 100 mA and 6.3v at 1 amp. Price £3.75 + post and VAT £1.55.

Instrument case, grey steel finish size 3 1/2" x 3 1/2" x 2 1/2". These cases are not secondhand but come from factory assembled equipment, so the front panel has a few holes already punched through. However, these are very suitable for toggle switches, etc. There are no really big holes, 50p each + post and VAT 36p.

6 switch disco lamp controller. This is a mains motor driving a rotating drum made up of discs with cut-outs. As the cut-outs engage on the switch levers, contact is made via 10 amp switches. A large variety of lighting effects can be obtained. A real bargain at £2.75 + post & V.A.T. 65p.


Clock switch for Tricity cooker, made by Smiths and probably the replacement in many other cookers. This has clock in the centre and the two control switches on the right-hand side. The top control switch sets the on-off times and is infinitely adjustable over the 12 hours; the lower switch selects manual or automatic. No glass front, but you could take this off your existing clock. Price £1.75 each + post & V.A.T. 35p.

SINCLAIR IC20

IC20 10W + 10W stereo IC amplifier kit with free booklet and printed circuit £4.95
 PS20 Power supply kit for the above £3.95.
 VP20 Volume, tone-control and preamp kit £7.50.
 SP20 10W 4 ohm speaker for IC20 £2.70.
 CS20 11 x 6 x 3ins attractive case for IC20 £2.95*.
 Send sae for free leaflet.

JC12 AMPLIFIER

6W IC audio amp with free data and printed circuit £1.95*

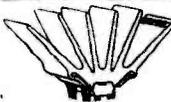**DELUXE KIT FOR JC12***

Includes extra parts for the pcb and vol. bass and treble controls for mono version £2.06. Stereo model with balance control £4.46.

JC12 POWER KIT*

Supplies 25V 1Amp £2.95.

JC12 PREAMP KITS

Type 1 for magnetic pickups, mics and tuners. Mono £1.40 Stereo £2.80. Type 2 for ceramic or crystal pickups. Mono 75p. Stereo £1.56.

LOUDSPEAKERS FOR JC12

8in x 5in 8 Ohms 5W £2.28.

SEND SAE FOR FREE LEAFLET ON KITS.

FERRANTI ZN414

IC radio chip with data £1.34. Printed circuit and extra parts for radio £3.25. Case 80p extra. Send sae for free leaflet.

SINCLAIR PROJECT 80

FM tuner £13.25. PZ5 £3.95. Q16 £10.95. PZ6 £8.70. PZ3 £3.10. Trans for PZ3 £5.40. Z40 £5.75. Stereo 80 £11.95. Project 80S £18.95. Quad decoder £14.95. Z60 discontinued but we stock 30W similar amp £10.30.

PRINTED CIRCUIT KIT £3.95*

Make your own printed circuits. Contains etching dish, 200 sq. ins. of copper clad board, 1 lb ferric chloride, etch resist pen, small drill bit, laminate cutter and instructions.

MAINS TRANSFORMERS

6.0-6V 100mA 85p. 9.0-9V 100mA 85p. 18V 1A £1.85*. 0, 12, 15, 20, 24, 30V 1A £2.95*. 12-0-12V 1A £1.95*. 0, 12, 15, 20, 24, 30V 2A £4.20*. 20V 2.5A £2.00. 6 and 9V trans are DC rated, others are AC volts.

SINCLAIR BLACK WATCH

Fully assembled with black strap £20.95*. Bracket £2*.

**SINCLAIR CALCULATORS***

Cambridge £7.95 Cambridge Memory £11.20. Scientific £8.95. Oxford 100 £6.95. Cam. Sci £14.95. Oxford 300 £16.95. Programmable scientific £25.95. Mains adaptor for programmable and Oxfords £3.19. Mains adaptor for Cambridge and Scientific £3.15.

CBM CALCULATORS*

796MD £6.45. 897D £7.60. SR1800 £23.25. 776MD 7 digit/%memory £5.95. SR7919D 8 digit/memory/trig/log/pi/powers/scientific notation £13.20. SR4148R with mains unit £34.95. Mains unit for other machines £2.95.

CASIO CALCULATORS*

Personal mini 6 + 6 digits £5.95. Pocket 8S 8 digits/%const £6.95. Memory 8R 8 digits/%memory/const £8.95. FX20 £16.95. Mains adaptor for all models £3.95.

NOVUS CALCULATORS*

750 6 digit £5.45. 835 8 digit/%const/sq. root/4 function memory £7.95. 4525 10 digit programmable scientific calculator £47.95. 4510 £13.20. 4515 £39.95. 4520 £23.45. Mains adaptor £4.20.

24 HR DIGITAL CLOCK KIT*

Includes pcb, mains power supply, attractive case, 0-9in jumbo green display, clock chip, and all other parts. Displays hours and minutes separated by a pulsating colon. Kit £12.50. Built £13.50. Send sae for free leaflet.

S-DECS AND T-DECS*

S-DeC £2.24
 T-DeC £4.95
 U-DeC A £4.45
 U-DeC B £1.45
 IC carriers:—
 16 dil: plain £1.07
 with socket £2.21
 10 TO5: plain 99p, with socket £1.95
 SST1 60p. SSU1 60p. SSN1 80p.

**BATTERY ELIMINATOR BARGAINS**

55 WAY SUPER
 New switched model. 3 to 30V in 1/2V steps. Fully stabilized. 1A output. Kit £7.95. Assembled £10.95. 2 Amp model. Kit £9.95. Built £12.95.

**6-WAY SPECIAL**

Switched output of 3 1/4V/6 7/8/9/12V at 500mA with 4-way multi-jack plug and free matching socket £3.20.

6-WAY DOUBLE RADIO MODEL £5.20

Similar to above, but with press-stud battery connectors. 3 + 3 1/4 + 4 1/8 + 6 7/8 + 7 1/2 + 9/12 + 12V at 250mA. Also gives 15/18/24V single.

3-WAY MODEL

Switched output of 6 7/8/9V at 250mA with 4-way multi-jack plug and free matching socket £2.95*.

RADIO MODELS

50mA with press-stud battery connectors for radios, etc. 6V £3.45. 9V £3.25. 4 1/2 + 4 1/2V £4.45. 6 + 6V £4.45. 9 + 9V £4.45.

CASSETTE MAINS UNITS

7 1/2V output to run cassette recorders from the mains. Complete with 5 pin DIN plug £3.45.

CAR CONVERTORS

Input 12V DC. Output 6 7/8/9V DC 1A regulated £3.95*.

BATTERY ELIMINATOR KITS

Send sae for free leaflet on range.
 100mA radio type with press stud battery terminals. 4 1/2V £1.80. 6V £1.80. 9V £1.80.
 50mA double radio type with press stud terminals. 4 1/2 + 4 1/2V £2.50. 6V + 6V £2.50. 9V + 9V £2.50.
 100mA cassette type with 5 pin DIN plug. 7 1/2V £1.80.
 Stabilized 8-way type with voltage stabilizer to give low hum. 3 1/4/6 7/8/9/12/15/18V 50mA £2.95.
 Heavy duty 12-way types 4 1/2/6 7/8/11/13/14/17/21/28/34/42V. 1Amp £3.95. 2 Amp £5.95.

SWANLEY ELECTRONICS

Dept. PW, PO Box 68, Swanley Kent

Post 30p on orders under £2, otherwise free. Prices include V.A.T. (Overseas customers deduct 7% on items marked *, otherwise 10%). Official orders from schools, government labs, etc. welcome.

A hobby that pays big salaries.

Enrol in the BNR & E School and you'll have an entertaining and fascinating hobby. Stick with it and the opportunities and the big money await you, if qualified, in every field of Electronics today. We offer the finest home study training for all subjects in radio, television, etc., especially for the CITY AND GUILDS EXAMS (Technicians' Certificates); the Grad. Brit. I.E.R. Exam; the RADIO AMATEUR'S LICENCE; P.M.G. Certificates; the R.T.E.B. Servicing Certificates; etc. Also courses in Television; Transistors; Radar; Computers; Servo-mechanisms; Mathematics and Practical Transistor Radio course with equipment. We have OVER 20 YEARS' experience in teaching radio subjects and an unbroken record of exam successes. We are the only privately run British home study College specialising in electronics subjects only. Full details will be gladly sent without any obligation.

BRITISH NATIONAL RADIO & ELECTRONICS SCHOOL, Dept WC66

P.O. Box 156, Jersey, Channel Islands.

NAME _____


ADDRESS _____

(Block caps please)

Vero Electronics Ltd, manufacture cases to give your projects a professional finish. Cases are available in plastic, extruded aluminium and PVC coated steel. A new catalogue describing these cases, Veroboard, pins, tools, card frame etc. is available (price 10p + S.A.E. 7" x 9")

vero

THE CASE OF THE PROFESSIONAL FINISH...

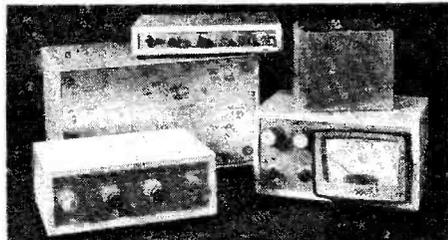


Vero Electronics Limited, Retail Dept., Industrial Estate, Chandler's Ford, Hants., SO5 3ZR
 Telephone: Chandler's Ford 2956 (STD 04125)



of Navy language to Mr. Scudder. Thus it seems the more complicated the set, the more it will cost to repair. This repair could result in having to send overseas for spares, increasing the cost and time spent without the use of the set. On the other hand cheap sets are often improved by the addition of aerial tuners and pre-selectors. **John Higginbotham** of Holyhead has written to say that the Radio N derland ATU specification sheet is once more being sent out. Readers will remember that news reached this column recently of RNI being lax in their reply to an enquiry for the plans for this handy bolt-on extra. John viewed in amazement his postbag from stations which totalled five cards and 17 calendars after the Christmas rush was over. I have recently had a card from Radio Sofia wishing me a happy Spring!

The main conclusion is that the cheap transistor radio is fine for a second or bedside set and for the person of limited budget, and that means most of us these days. While the communications set is for those who have the money to spare and the space to fit the set into. The AR88, for instance, needs a stout table just to take the weight! It is of course pointless to expect the cheaper transistor set to pull in the signals that the Grundig Satellit will or some of the American products, or even the Codar, but the use of a cheaper set may fire you to go on to bigger and better things and even aspire to the RAE.

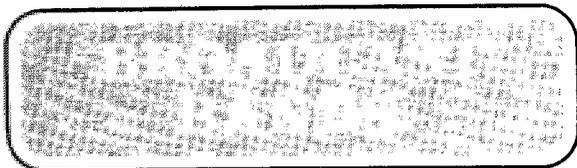So until next month I will simply say 73s to you and yours.



MEDIUM WAVE DX

by **CHARLES MOLLOY**

READER "Steve" who lives in Truro, Cornwall reports hearing CFGO in Ottawa on about 1440kHz at 0305GMT after Radio Luxemburg had closed down for the night. CFGO does operate on 1440kHz and is heard quite often in the UK. Steve uses a Philips IC326 receiver coupled to the co-ax downlead of his VHF TV aerial. The receiver is placed on top of the co-ax, the screen of which is earthed and this gives a very good boost to reception. Steve mentions hearing Radio Sweden on approx. 1151kHz as well as on 1178kHz which is the listed frequency. This effect is almost certainly due to a spurious signal generated within the receiver as a result of overloading by the pick-up from the co-ax downlead aerial. Portable receivers are normally designed to work with the comparatively low signal input from a ferrite rod aerial. Care should be taken when an external aerial is used that the coupling is not too close otherwise the increased

signal strength obtained will be accompanied by whistles and spurious signals.

Quite often the medium wave tuning scale on a receiver is not accurate enough to show the frequency to the nearest 5kHz or so. The DXer is then uncertain which one of two or even three channels he is listening to and problems with station identification can arise. A logging scale, if the receiver has one, can be used to improve matters. This scale is marked from 0 to 100 or perhaps, 0 to 1000 and is used with a sheet of graph paper to plot a curve that will enable logging scale divisions to be converted to frequency. Known local broadcasting stations can be used to mark a number of points on the graph, these points being joined with a continuous line to form a curve which is used to convert frequency to logging scale reading and vice versa.

An alternative is to use a crystal calibrator. The writer's has switched outputs of 10kHz, 50kHz and 100kHz which are found to be adequate for MW DXing. The calibrator is connected to the receiver in parallel with the aerial and it acts as a miniature transmitter to give marker points at intervals across the band. The method used by the writer is to draw up a table giving a logging scale reading for each 10kHz point on the medium waves which is very useful when DXing North Americans where the stations are on channels which are multiples of 10kHz. A more usual method is to switch-in the calibrator in place of the aerial and use the 100kHz markers to identify sections of the band and the 10kHz markers to tune to an exact channel. "Odd" frequencies between the 10kHz points can be estimated. Domestic type receivers in the UK are usually marked in metres on the tuning scale. To convert, divide 300,000 by the wavelength in metres, to get the frequency in kHz.

Roy Patrick reports from Mackworth, Derby with news of his recent broadcasts from Radio Derby on "Late Night Derby". He has been telling listeners about DXing and says it was nice to be on the other end for a change. Roy's medium wave catches made on a Trio 9R59D receiver include CJCH in Halifax, Nova Scotia on 920kHz; CJON St. John's on 930kHz; WINS in New York City on 1010kHz; WHN also in NYC on 1050kHz; CBA Moncton, New Brunswick on 1070kHz and Urumchi in China on 1525kHz at 2300GMT with a programme in Russian. Good luck with your broadcasting Roy!

When two adjacent broadcasting stations are identified by wavelength rather than by frequency it will be difficult to decide from this information whether they will interfere with each other. Only the frequency separation in kHz is of value since the bandwidth of a receiver and hence its selectivity, the ability to separate adjacent signals, is measured in kHz. On the medium and long waves in Europe the majority of channels have a separation of 9kHz. At the HF end of the MWs, channel 107 (1484kHz) corresponds to 202.2 metres while channel 106 (1475kHz) corresponds to 203.4m, the difference in wavelength being 1.2m. At the LF end of the band channel 5 (566kHz) is 530, while channel 4 (557kHz) is 539m the difference in this case being 9m. On the long waves 209kHz corresponds to 1435m and 200kHz to 1500m the difference being 65m. From an interference point of view the "distance" between the two stations in each case is the same, namely 9kHz but the wavelength separation varies between 1.2m and 35m.



The advantages of using kHz instead of metres are so obvious that the practice is now in use by DXers and broadcasting authorities in most parts of the world. In the UK, FM stations on VHF are quoted by their frequency in megahertz though the use of metres on the medium and long waves lingers on. In North America, where the separation is 10kHz the medium waves, or "Broadcast Band" extends from 540kHz to 1600kHz. Receiver manufacturers often drop the last zero, and mark the scales 54 to 160, a practice that can be seen on many imported domestic receivers on sale in the UK.

An interesting letter from Ian Rennison in Horsham, Sussex tells of a holiday spent in Richmond, Virginia, USA where he heard US radio first hand. He mentions picking-up WKBW Buffalo NY on 1520kHz on a car radio and commenting that he had clearer reception of the same station back home! WKBW is often a strong signal here in the UK just before sunrise at this time of year. Ian has been trying to pick up WRVA Richmond on 1140kHz and asks if it has been logged in this country. WRVA has been heard but not often because of the

directional aerial system in use at the transmitter. WRVA and CBI in Nova Scotia both transmit on 1140kHz and to reduce mutual interference each station has a directional aerial which has a null towards the other. The null from WRVA is towards the North East which is also the bearing of the DXer in the UK and as a result, CBI comes in well in the UK while WRVA is something of a rarity. Ian's excellent log of DX heard at Horsham on a Trio 9R59D receiver, medium wave loop and PW differential loop amplifier includes 19 Canadians (CKVO is the unidentified one on 710kHz); 20 from the US the more outstanding being WSB Atlanta, Georgia on 750kHz; WHO Des Moines on 1040kHz and KMOX St. Louis on 1120kHz, along with a number from the Caribbean area such as CMKV Radio Rebelde in Cuba on 600kHz, Radio Demerara, Guyana on 760kHz and Radio Belize on 834kHz.


BROADCAST BANDS

Short Wave reports by the 15th of the month to Derek Bell c/o Practical Wireless, Fleetway House, Farringdon Street, London, EC4A 4AD.

Medium Wave Logs to Charles Molloy, 132 Segars Lane, Southport, PR8 3JG.

AMATEUR BANDS

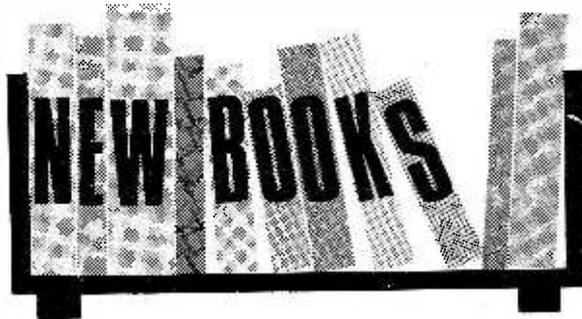Logs covering any Amateur band/s in band/ alphabetical order by the 25th of the month to Eric Dowdeswell G4AR, Silver Firs, Leatherhead Road, Ashleat, Surrey, KT21 2TW.



THE ELECTRONIC MUSICAL INSTRUMENT MANUAL

By Alan Douglas

Published by Pitman Publishing Ltd.,

39 Parker Street, London WC2B 5PB.

205 pages 25.5cms x 19.0cms

Price £7.50

In this entirely revised sixth edition, the author sets out to start the reader right at the fundamentals of sound and to progressively work up to examples of current organs. He has not, however, forgotten the owners of valve organs.

Basically this book is a comprehensive guide to the theory and design of musical instruments, with particular reference to the organ. It covers the entire field of sound theory and the function of physical sound sources and their electronic counterparts.

The author, Alan Douglas, is a well-respected expert on the design of electronic musical equipment. He is a senior member of the IEE and an Associate of the Incorporated Society of Organ Builders. Other books from his stable include "Frequency Divider Organs for the Constructor", "Electronic Music Production" and (with Sid Astley) "Transistor Electronic Organs for the Amateur".

ELECTRONIC DIAGRAMS (A Newnes Constructors Guide).

by M. A. Colwell

Published by Butterworth & Co. (Publishers) Ltd.,

88 Kingsway, London WC2B 6AB

104 pages 21.5cms x 13.5cms

Price £1.80

The reader is led through a course of learning how to understand graphical symbols of circuits. In compiling this book—with the evident aid of the British Standards Institution—the author has assumed that the reader is familiar with electrical terminology, particularly regarding components, but not a thorough knowledge of all types of circuit theory. It is suggested that this book will be an aid to studies and practical work for newcomers and a reference for those more experienced in the planning and preparation of circuit diagrams.

WORLD RADIO TV HANDBOOK 1976

Edited by J. M. Frost

Published by Billboard Publications,

7 Carnaby Street, London W1V 1PG.

500 pages 23cms x 14.5cms

Price £4.50

This 30th Anniversary Edition of the W.R. TV Handbook is, as usual, an authoritative source of information about radio and TV stations all over the world. It is really a 'must' for anyone who even thinks he/she may take up short wave listening and a veritable 'bible' for the ardent listener or TV DX enthusiast. This edition includes excellent articles on the technical planning of a short wave service, 20 best short wave receivers on the world market, tips on tapes, new aerial developments, 'pirate' stations etc. etc. in a special supplement bound in at the back of the book and entitled, "Listen to the World".

RETURN OF POST MAIL-ORDER SERVICE

JUST RELEASED

R.C.S. 100 watt VALVE AMPLIFIER



Four inputs. Four way mixing, master volume, treble and bass controls. Suits all speakers. This professional quality amplifier chassis is suitable for all groups, disco, P.A., where high quality power is required. 5 speaker outputs. A/C mains operated. Slave output. Produced by demand for a quality valve amplifier.
Suitable carrying cabinet £14. Price **£85** carr. £8-50

ANOTHER R.S.C. BARGAIN!

ELAC 9 + 5in. HI-FI SPEAKER TYPE 59RM

This famous unit now available, 10 watts, 8 ohm.

Price **£3-45** Post 40p



8" or 10" x 6" ELAC HI-FI SPEAKER

Dual cone plasticised roll surround. Large ceramic magnet. 50-18,000 cps. Bass resonance 55 cps. 8 ohm impedance. 10 watts.

£4-35

10in round £4-95.

TEAK VENEER HI-FI SPEAKER CABINETS

MODEL "A". 20 x 18 x 12in. For 12 in. dia. or **£12-50** Post 95p

MODEL "B". 16 x 10 x 9in. For 12 x 8in. or **£6-95** Post 8 in. speaker 75p

MODEL "C". 30 x 20 x 12in. Reflex cabinet will accept 1-12in. bass unit, 1-5in. mid range, 1-3in. tweeter. Teak finish. Grooved front **£21-50** Carr. 25

LOUDSPEAKER CABINET WADDING 18in. wide, 25p ft.

GOODMANS CONE TWEETER

3 1/2 in. diam. 18,000 C.P.S. 25 WATTS 8 Ω **£3-60**

BARGAIN 4 CHANNEL TRANSISTOR MONO MIXER. Add musical highlights and sound effects to recordings. Will mix Microphone, records, tape and voice with separate controls into single output. 9 volt **£5-20** battery operated.

STEREO VERSION OF ABOVE 26-85.

BARGAIN 3 WATT AMPLIFIER. 4 Transistor Push-Pull Ready built with volume, treble and bass controls. 18 volt battery operated. Mains Supply **£3-45**.

THE "INSTANT" BULK TAPE ERASER & HEAD DEMAGNETISER. Suitable for cassettes, and all sizes of tape reels. A.C. mains 200/240V. Leadst S.A.E. **£4-35** Post 40p

WAFER HEATING ELEMENTS

OFFERING 1001 USES for every type of heating and drying applications in the home, garage, greenhouse, factory (available in manufacturing quantities). Approx. size 1 1/2 x 8 1/2 x 1/2 in. Operating voltage 200/250V, a.c. 250 watts approx. Printed circuit element enclosed in asbestos fitted with connecting wires. Completely flexible providing safe Black heat. British-made for use in photo-copiers and print drying equipment.
Ideal for home hair-driers and experimenters. Suitable for Heating Pads, Food Warmers, Convector Heaters, etc. Must be clamped between two sheets of metal or asbestos, etc., to make efficient clothes driers, towel rails—ideal for airing cupboards. Ideal for anti-frost device for the garage—preventing frozen radiators or acting as oil sump heater. Use in greenhouse for seed raising and plant protection. Invaluable aid for bird houses, incubators, etc., etc. Can be used in series for lower heat. Or in parallel for higher heat applications.

ONLY 40p EACH (FOUR FOR £1-50)

ALL POST PAID—Discounts for quantity.

BAKER MAJOR 12" £11-50



Post 60p
30-14,500 c/s, 12in. double cone, woofer and tweeter cone together with a BAKER ceramic magnet assembly having a flux density of 14,000 gauss and a total flux of 145,000 Maxwells. Bass resonance 40 c/s rated 25 watts. NOTE: 3 or 8 or 15 ohms must be stated.

Module kit, 30-17,000 c/s with tweeter, crossover, baffle and instructions. **£14-50**

Please state 3 or 8 or 15 ohms. Post 50p

BAKER SPEAKERS "BIG SOUND"

Robustly constructed to stand up to long periods of electronic power. As used by leading groups. Useful response 30-13,000 cps. Bass resonance 55 cps.

GROUP "25"
12in 30 watt
3, 8 or 15 ohms.

£8-95

Post 50p

GROUP "35"
12in 40 watt
3, 8 or 15 ohms.

£10-50

Post 50p

GROUP "50/12"

12in 80 watt professional model. 8 ohms or 15 ohms.

£14-50

Post 80p

GROUP "50/15"

15in 75 watt
8 or 15 ohms.

£19-50

post 90p

MAJOR 50 WATT

ALL PURPOSE TRANSISTOR AMPLIFIER

All purpose transistorised. Ideal for Groups, Disco and P.A. 4 inputs speech and music. 2-way mixing. Output 8/15 ohm A.C. mains. Separate treble and bass controls. Guaranteed. Details S.A.E.

£49 Carr. £1-00

Latest 100 watt Model as illustrated **£68**

100 WATT DISCO AMPLIFIER CHASSIS

MADE BY JENNINGS MUSICAL INSTRUMENTS
4 speaker outputs, vol., treble, bass controls **£52**
or in cabinet 259.

QUALITY LOUDSPEAKER ENCLOSURE

Teak veneered 3/4 in thick wood cabinet. Size 18 1/2 in x 18 1/2 in x 8 1/2 in. Weight 23lb. This cabinet features a wide mesh Silver Grill covering a separate compartment for mounting Tweeters or Mid-Range Horn. The fully sealed bass compartment is cut out for 8 1/2 in Woofer. £7-50. Carr. 85p. Rosewood Version £8-50. Carr. 85p. Baffle could be cut for larger speaker.

P.W. SOUND TO LIGHT DISPLAY

Complete kit of parts with R.C.S. printed circuit. Three channels. 600 to 1,000 watt each. As featured in December Practical Wireless. Price **£12-50**
Cabinet extra 23.

8 inch PHILIPS LOUDSPEAKER

4 ohm. 4 watt. ceramic magnet **£1-95**

MAINS TRANSFORMERS

5 VOLT	1 AMP. £1-00	3 AMP. £1-40
12 VOLT	300 MA. £1-00	750 MA. £1-30
16 VOLT	1 AMP. £1-00	2 AMP. £2-00
20 VOLT	1 AMP. £1-75	1 AMP. £2-00 3AMP. £2-20

E.M.I. TAPE MOTOR

4 pole, 240 v. Size 3 1/2 x 2 1/2 in. 1200 rpm. Spindle 1/4 in. diameter. 120v version 75p. **£1-85** Post 45p

E.M.I. GRAM MOTOR

120V or 240V a.c. 2,400 rpm 2-pole. Size 2 1/2 x 2 1/2 in. **£1-25** Post 35p

BAKER DISCO SPEAKERS HIGH QUALITY—BRITISH MADE

2 x 12" CABINETS

for Disco or PA all fitted with carrying handles and corners Black finish. Other cabinets in stock.

50 WATT R.M.S. £43

70 WATT R.M.S. £46

100 WATT R.M.S. £55



1 x 15" + 1 x 12" 100 WATT CABINET
Size 36" x 24" x 15" **£63-50.**

Ideal for Disco or PA work. High quality.

SUPERB HI-FI

12in 25 watts

A high quality loudspeaker, its remarkable low cone resonance ensures clear reproduction of the deepest bass. Fitted with a special copper drive and concentric tweeter cone resulting in full range reproduction with remarkable efficiency in the upper register.
Bass Resonance 25cps
Flux Density 16,500 gauss
Useful response 20-17,000cps
8 or 15 ohms models.

£17 Post 80p

AUDITORIUM

12in. 35 watts

A full range reproducer for high power, Electric Guitars, public address, multi-speaker systems, electric organs. Ideal for Hi-Fi and Discotheques.
Bass Resonance 35cps
Flux Density 15,000 gauss
Useful response 20-14,000cps
8 or 15 ohms models.

£15-50 Post 80p

AUDITORIUM

15in. 45 watts

A high wattage loudspeaker of exceptional quality with a level response to above 8,000 cps. Ideal for Public Address, Discotheques, Electronic instruments and the home Hi-Fi.
Bass Resonance 35cps
Flux Density 15,000 gauss
Useful response 20-14,000cps
8 or 15 ohms models.

£19-50 Post 80p

Hi-Fi Enclosure Manual containing plans, designs, crossover data and cubic tables, 88p

RADIO COMPONENT SPECIALISTS 337 WHITEHOUSE ROAD, CROYDON

Minimum post 30p. Components Lists 10p. Cash price includes VAT Access & Barclay cards welcome. Rail Selhurst. Tel. 01-684 1665

VALVES

A1065	1.25	ECL80	0.60
AR8	0.60	ECL82	0.60
ARP3	0.60	ECL83	0.75
ATP4	0.60	ECL86	0.60
B12H	3.00	EF30	0.65
DAF96	0.60	EF37A	1.10
DF96	0.60	EF40	0.70
DK96	0.75	EF41	0.75
DL92	0.50	EF80	0.40
DL96	0.70	EF83	0.25
DY85/87	0.85	EF85	0.40
	0.45	EF86	0.40
DY802	3.45	EF89	0.35
E88CC/01	1.30	EF91	0.60
E180CC	1.00	EF92	0.50
E182CC	1.00	EF95	0.45
		EF93	0.40
		EF84	0.40
EA50	3.00	FL200	0.75
EABC80	0.40	EL34	0.70
		EL35	0.70
EA42	0.70	EL37	2.20
EB91	0.30	EL41	0.80
EB33	1.00	EL86	0.35
EB34	1.00	EL88	0.35
EB41	0.75	EL85	0.60
EB78	0.40	EL86	0.50
EBF83	0.45	EL90	0.50
EBF89	0.40	EL91	1.00
EC52	0.40	EL95	0.70
EC81	0.45	EL504	0.80
EC82	0.35	EL821	1.80
EC83	0.35	EL81	0.60
EC84	0.35	EM31	0.70
EC85	0.45	EM80	0.55
EC86	1.25	EM84	0.40
EC88	0.55	EM87	1.00
ECC189	0.80	EV51	0.45
		EV51	0.45
ECF80	0.45	EV86/87	0.60
ECF82	0.45		
ECF801	0.75	EY88	0.50
ECF804	2.50	EZ40	0.70
ECH42	0.85	EZ41	0.75
ECH81	0.40	EZ40	0.30
ECH84	0.60	EZ61	0.35
		PL504	0.85

A lot of these valves are imported and prices vary for each delivery, so we reserve the right to change prices for new stock when unavoidable.

PL508	0.95	U25	1.00
PL509	1.35	U26	0.80
PL802	1.85	U27	1.00
PL803	0.60	U191	0.75
PL804	0.60	U801	0.80
PL805	0.60	U802	0.80
PL806	0.60	U803	0.80
PL900	0.60	U897	0.80

TRANSISTORS

AAZ12-	BAV10	AF118	BC172	CRS3/40	OC29	OC206	2N4058
AF124	BC172A	AF125	BC212A	CRS25/025	OC35	ZR11	2N4061
AF126	BCY31	AF127	BCY33	GET115	OC36	ZR21	2N4172
AF128	BCY72	AF129	BCY72	GET116	OC42	ZR22	2N5295
AF178	BF115	AF179	BF115	GEX66	OC44	2N456A	3N1226
AF186	BF167	AF187	BF167	NKT222	OC45	2N525	3N1228
AF239	BF173	AF240	BF173	NKT304	OC70	2N696	3N154
AF212	BF185	AF213	BF185	NKT404	OC73	2N708	3N159
AF216	BF186	AF217	BF186	OA5	OC75	2N918	5X754
AF218	BF187	AF219	BF187	OA47	OC78	2N1305	2S303
AF220	BF188	AF221	BF188	OA70	OC7D	2N1307	T12082
AF222	BF189	AF223	BF189	OA71	OC81	2N1309	40235
AF224	BF190	AF225	BF190	OA73	OC82	2N1309	40236
AF226	BF191	AF227	BF191	OA75	OC82DM	2N2411	40251
AF228	BF192	AF229	BF192	OA79	OC83	2N2959	IN23A
AF230	BF193	AF231	BF193	OA81	OC83B	2N3083	IN25
AF232	BF194	AF233	BF194	OA200	OC139	2N3054	IN38A
AF234	BF195	AF235	BF195	OA202	OC140	2N3055	IN43
AF236	BF196	AF237	BF196	OA220	OC170	2N3391	IN70
AF238	BF197	AF239	BF197	CRS1/20	OC172	2N3392	IN77
AF240	BF198	AF241	BF198	CRS2/10	OC26	2N3870	IN4148
AF242	BF199	AF243	BF199	CRS3/20	OC28	2N4038	IN4785
AF244	BF200	AF245	BF200	CRS3/30	OC28	2N4038	IN4785

Please write or phone for current price of any of the transistors or diodes shown below.

AAZ12-	BAV10	AF118	BC172	CRS3/40	OC29	OC206	2N4058
AF124	BC172A	AF125	BC212A	CRS25/025	OC35	ZR11	2N4061
AF126	BCY31	AF127	BCY33	GET115	OC36	ZR21	2N4172
AF128	BCY72	AF129	BCY72	GET116	OC42	ZR22	2N5295
AF178	BF115	AF179	BF115	GEX66	OC44	2N456A	3N1226
AF186	BF167	AF187	BF167	NKT222	OC45	2N525	3N1228
AF239	BF173	AF240	BF173	NKT304	OC70	2N696	3N154
AF212	BF185	AF213	BF185	NKT404	OC73	2N708	3N159
AF216	BF186	AF217	BF186	OA5	OC75	2N918	5X754
AF218	BF187	AF219	BF187	OA47	OC78	2N1305	2S303
AF220	BF188	AF221	BF188	OA70	OC7D	2N1307	T12082
AF222	BF189	AF223	BF189	OA71	OC81	2N1309	40235
AF224	BF190	AF225	BF190	OA73	OC82	2N1309	40236
AF226	BF191	AF227	BF191	OA75	OC82DM	2N2411	40251
AF228	BF192	AF229	BF192	OA79	OC83	2N2959	IN23A
AF230	BF193	AF231	BF193	OA81	OC83B	2N3083	IN25
AF232	BF194	AF233	BF194	OA200	OC139	2N3054	IN38A
AF234	BF195	AF235	BF195	OA202	OC140	2N3055	IN43
AF236	BF196	AF237	BF196	OA220	OC170	2N3391	IN70
AF238	BF197	AF239	BF197	CRS1/20	OC172	2N3392	IN77
AF240	BF198	AF241	BF198	CRS2/10	OC26	2N3870	IN4148
AF242	BF199	AF243	BF199	CRS3/20	OC28	2N4038	IN4785
AF244	BF200	AF245	BF200	CRS3/30	OC28	2N4038	IN4785

MINIMUM POSTAL ORDER £1. PERSONAL CALLERS WELCOME. MANY OTHERS IN STOCK include Cathode Ray Tubes and Special Valves. U.K. UK Postcode £1-£2 20p, £2-£3 30p, £3-£5 40p. Over £5 free.



VIDEOCON
TUBE
Type P864B
English Elec.
£20

TEST EQUIPMENT
LARGE SELECTION
PLUBICON TUBES
Type XO 1071 Mullard £150



THE VALVE WITH A GUARANTEE

7B7	0.80	9003	0.70
7Y4	0.80	9004	0.40
9D2	0.60	9006	0.40
9D6	0.50		
11E2	6.00		
12A8	0.60		
12A76	0.45		
12A77	0.60		
12A7U	0.35		
12AX7	0.35		
12BA6	0.50		
12BE6	0.55		
12BH7	0.55		
12CB8	0.60		
12E1	3.75		
12K5	1.50		
12K7GT	0.55		
12K8GT	0.75		
12Q7GT	0.75		
12Q7GT	0.75		
12Q7GT	0.75		
12SA7GT	0.50		
12SG7	0.80		
12SJ7	0.55		
12T	0.40		
12Y7	1.00		
19AQ5	0.70		
19G3	8.00		
19G6	6.50		
19H5	15.00		
20P3	0.60		
20P4	1.10		
25L6GT	1.00		
30C15	1.00		
30C17	1.10		
30F5	1.00		
30FL1	1.10		
30FL12	1.10		
30FL15	1.00		
30L17	0.90		
30P12	1.00		
30P19	1.00		
30PL13	1.10		
30PL14	1.10		
35L6GT	0.55		
35W4	0.55		
50C5	0.65		
50C6G	0.70		
50D6G	1.20		
75C1	0.75		
76	0.75		
78	0.70		
80	0.75		
85A2	0.75		
803	6.00		
805	18.00		
807	0.75		
813	6.50		
866A	1.60		
88J	9.00		
931A	6.00		
954	0.50		
956	0.50		
957	0.50		
1629	0.70		
20			


TANGENTIAL BLOWER HEATER

240V 2KW can be switched for two speeds and 1KW Robust and efficient. Aperture 7 3/4" x 1 3/8" size overall length 10". Price £4.25 plus p. & p. 75p.



DIGITAL DISPLAY INDICATOR

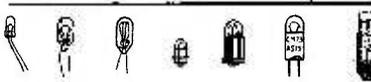by KGM. Type M4, window size 7/8" wide, 1 1/4" high, depth 1 1/2", height 3 1/2" plus front flange (3/4" top and bottom). This is an Acrylic edgelit unit illuminated by 12V flange type bulbs (as our min. lamp type D) Currently sold at £14.00 plus, our price £3.95 inc. lamps, plus p. & p. 35p.



MINIATURE LAMPS

Type	Size (Dia.)	Volt/Curr.	Type	Size (Dia.)	Volt/Curr.
A	3MM	5-6V 60 MA	D	3MM	2-5V 360 MA
B	4MM	4V 250 MA			5-6 60 MA
		5V 60 MA	E	4MM	6V 200 MA
		12V 40 MA			6-3 200 MA
		12V 100 MA	F	4MM	14V 40 MA
		14V 20 MA			2-7V 80 MA
		28V 40 MA			12V 160 MA
C	5MM	28V 40 MA			14V 80 MA

Small telephone jack type 6 or 24V
Price: Types A-F £4.00 for 25, 50 and upwards 13p each
Type G 45p each, p. & p. 20p per order.

RIBBON CABLE

4 way side by side P.V.C. 7 strand red-green-blue-yellow (miniature) 50 metre reels £4.50, 250 metres £20 P & P 70p 50 metres. £1.50 250 metres.


CENTRIFUGAL BLOWER

240V power, efficient by Universal Electric. 3,100 r.p.m. Inlet dia. 4", outlet approx. 2 3/4" x 2 3/4", overall width 5", overall dia. 5 1/2". Price £4.75 plus p. & p. 75p.



ARROW SWITCH

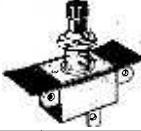Press on/press off, single hole fixing SP ST size 1 1/2" x 1 1/2" prestie extends 3". Rated 21 amps. Robust. Price for 5 (min qty.) £1.75, 10 or more 30p each, p. & p. 30p for 5.



MEM LIMIT SWITCH

Snap action 5 amps at 240/410 A.C. size base 3 1/2" x 1 1/2" x 1 1/2" plus heavy duty roller plunger 1 1/2" ext. or 1" when compressed. Very robust for tireless operation, weather proof. Price £2.20 plus p. & p. 25p.

RELAYS


Octal base 2 C/O 6 amp contacts following voltages: 12V a.c. 48V d.c. 110 d.c. 230 a.c., all £1.25 each plus base 15p postage and packing 15p. 11-pin 3 C/O 6 amp contacts, following voltages: 115 a.c. 48 d.c. 24 d.c. all at £1.50 each, base 15p plus 15p p. & p.




10 K.W. ISOLATION TRANSFORMER
Prim. 200-240V sec. 120-0-120V, size 18" x 15" x 26" high, weight approx. 250lbs. Price £110 inc. VAT delivery charge at cost.

CROUZET MICRO SWITCHES

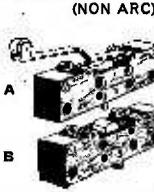Types A/B no. 83-112 n/o or n/c as desired, rating 5 a 240V, size 1 1/2" x 1 1/2" x 1 1/2" high. Can be stacked horizontally or vertically. In this mode, top switch can operate multiples. Type A has straight through plunger, whilst Type B is encased at bottom. Makers price approx. £1.40 each, our price 45p each (min. qty. 5) plus 15p per roller (as shown) plus 20p p. & p.



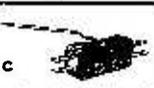Type C miniature no. 83-132, size 3/4" x 3/4" x 3/4" high, plus tags, 5 a 250V. Price 30p each (min. 5) Lever 3/8" long 19/16" long either type 8p each, plus p. & p. 20p.



Type D similar to Type C, but with tags underneath, uses same lever as Type C or can be banked horizontally and double lever (as shown) supplied at 12p. Prices as type C.



Type E no. 83-131, 10 a 250V size 1 1/2" x 3/4" x 3/4" high. 30p each (min. 5) plus lever 1 1/2" long, 8p each plus p. & p. 20p each.



NORPLX COPPERCLAD FIBREGLASS

First grade material. 1 & 2 oz. copper size 43" x 37" thickness double sided 1/32" / 1/64" 3/16" 2/32". single sided 1/32" & 3/64" all types £10 per sheet. Carriage £2 one sheet plus 50p additional sheets (G.B.).


THUMBWHEEL EDGE SWITCHES

(Plessey) ten position 0-9 (single pole ten way) modular, any number may be banked. Contact rating 2a A.C. or D.C., colour black, size overall 52-58 high x 12 wide x 49 mm deep. P.C. pitch 156. Price £1.50 per unit, end mounting cheeks £1.00 per pair, p. & p. 30p any order.




SOLENOID BY WESTOOL

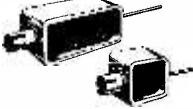240 a.c. type MM6 3lb pull. 2 1/2" x 1" x 1 1/2". Travel 1". £1.50 each, plus p. & p. 25p. 240 a.c. type MM4 2lb pull. 1 1/2" x 1 1/2" x 1". Travel 1". £1.25 each, plus p. & p. 25p.



MAINS SOLENOIDS

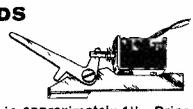This little unit gives vertical lift of approximately 1 in., through hinged "elbow". Bracket incorporates 2 fixing screws. Length of arm, 2 1/2" 240V. a.c. Pull at coil is approximately 1lb. Price £1.25 plus p. & p. 20p.



ALL PRICES INCLUDE V.A.T.

Whilst we welcome official orders from established companies and Educational Departments, it is no longer practical to invoice goods under £10. Therefore, please remit cash with orders below this amount.

MUFFIN "PANCAKE" FANS

As used in computers and other installations where silent continuous efficient cooling is needed. These fans are 115V 50Hz drawing only 14 watts 4 1/2" x 4 1/2" x 1 1/2". They can be coupled in pairs for use on 240V dropping resistor can be supplied for 50p. ONLY £6.50 plus p. & p. 50p.



SPRITE "PANCAKE" FANS

Similar to "Muffin", physically smaller, drawing only 9 watts but still giving extremely high efficiency with minimum fuss. 115V 50 Hz can be used in pairs from 240V a.c. dropping resistor supplied for 50p. Size: 3 1/2" x 3 1/2" x 1 1/2". (Large quantity available, special quotations). ONLY £4.50 plus p. & p. 50p.



6 DIGIT 24V D.C. COUNTER

Non re-set 3 watts size 1 1/2" x 1 1/2" x 1 1/2". Brand new. Plastic encased. Price £2.25 plus p. & p. 25p.




SOLDER GUN BY ETP

240V for instant heat and speedy soldering. 100 watts, built in spot lamp. Price £3.50 plus p. & p. 50p.

BENDIX MAGNETIC CLUTCH

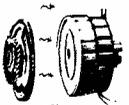A superb example of Electro-mechanics! The main body is in two sections. The coil section is fixed and has a pin sleeve. The drive section rotating on the outer perimeters. The uniting plate has pin ID bearing concentric with main section and 18-tooth cog wheel. When energized transmission is extremely powerful. 24V d.c. at 240 MA. Dur price just £2.70 plus 30p p. & p.



PROGRAMME TIMER

12 bank, cam operated micro switches, infinitely variable switching 240V. Speed 15 r.p.m. (4 secs per rev). Price £8.95 plus p. & p. 70p.




SHADED POLE GEARED MOTORS

110 r.p.m. 240 a.c., high Torque, approximate overall size 3 1/2" x 3 1/2" x 2 1/2" and spindle dia. 3/8". Price £3.50 plus p. & p. 50p.



SYLVANIA SWITCH

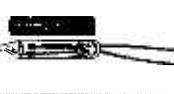Complete with magnet, normally closed, 3 amp vacuum sealed. 1 1/2" long 3/8" dia. 10 for £2.50, 50 for £11.00, 100 for £18.00 plus p. & p. 30p. for 10 to 100.



LIGHT DEPENDENT RESISTORS

Matched pairs. Pioneer type 174 similar to orp 12 resistance 1K to 40K, dia 3/8" with 3/8" flanges, £1.50 for two pairs (minimum) 10 or more pairs 50p. per pair plus p. & p. 15p.

EDGE CONNECTORS (CINCH)

Single contact sockets. 27 way 15, can be cut to various lengths. Available end mounts. 10 pieces (minimum) for £4.00 plus p. & p. 25p.

ELECTRO-TECH COMPONENTS LTD.

317 and 364 EDGWARE RD., VISIT OUR NEW BIGGER AND
LONDON, W2. BETTER SHOP—NOW OPEN
Tel: 01-723 5667 01-402 5580 AT 364 FOR A WIDE RANGE
WE ARE OPEN 9-6 MON. TO SAT. OF INTERESTING ITEMS!


FREE SUPER SOLDER BOARD WITH EVERY DEC BUILD CIRCUITS EASILY PUSH COMPONENT-IN NO SOLDERING

Designing circuits is easy with DeCs, just plug in your components. Each DeC breadboard is complete with step-by-step instructions. When circuit is designed, take components out and use them again OR plug components into SUPER SOLDER BOARDS for a perfect, finished P.C.B.

TO P. B. Electronics (Scotland) Ltd., 57 High Street, Saffron Walden, Essex. Please find enclosed P.C./Cheque value £

- ___ S-DeCs + Free Super Solder Board £1.80
- ___ T-DeCs + Free Super Solder Board £3.87
- ___ U-DeCA + Free Super Solder Board £4.31

FULL POSTAL ADDRESS

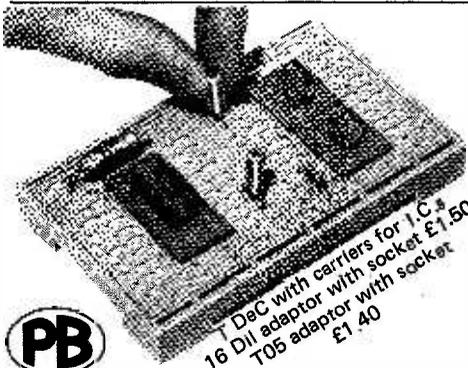

16 DeC with carriers for I.C.s
16 Dill adaptor with socket £1.50
T05 adaptor with socket £1.40



P. B. Electronics (Scotland) Ltd.,
57 High Street, Saffron Walden, Essex.
Tel: Saffron Walden (0799) 22876.

Practical Wireless, June 1976

B. BAMBER ELECTRONICS

Dept PE, 5 STATION ROAD, LITTLEPORT, CAMBS., CB6 1QE
Telephone: ELY (0353) 860185 (2 lines) Tuesday to Saturday

PLEASE ADD 8% VAT UNLESS OTHERWISE STATED

SPECIAL OFFER
FREE WELLS 25W (SP25) SOLDERING IRON (worth £2.72 inc. VAT) with all orders over £20. Limited period only. Send now.

ALU-SOL ALUMINIUM SOLDER (made by Mullerco). Soldered aluminium to itself or copper, brass, steel, nickel or Unplate. 16 s.w.g. with multicore flux, with instructions. Approx. 1 metre coil 30p pack. Large reel (approx. 12 metres) £2.75.

MIXED COMPONENT PACKS, containing resistors, capacitors, switches, pots, etc. All new (random sample bag revealed approx. 700 items), £2 per pack, while stocks last.

TUNED COILS, 2 section coils, around 1MHz, with a black smart tuning knob, which moves an internal core to vary the inductance, many uses, easily rewound, 3 for 50p.

SMALL MAINS SUPPRESSORS (small chokes, ideal for radio, Hi-Fi inputs, etc.) approx. 1/2in x 1/2in, 3 for 50p.

PERSPEX TUNER PANELS (for FM Band 2 tuners) marked 88-108 MHz and Channels 0-70, clear numbers, rear blacked out, smart modern appearance, size approx. 8 1/2in x 1 1/2in, 2 for 35p. Multiturn Pots, 10 turn, 1/2in spindle (ex-stock), following values available, 2k-50k, 50k-500k, 500k-1M, £1 each.

Lead suppressors (10k-50k) for mobile plug leads, 4 for 50p.
1mA Meters, 2 in square, plastic fronts (these have a paper case stuck over the original marked 0-1mA which is easily peeled off and an internal 18K resistor which is easily removed), £1.75 each or 2 for £3.
RIS Midgate 3 pole 4 way, rotary switches, 40p each.

HIGH QUALITY SPEAKERS, 8 1/2in x 6in elliptical, only 2in deep, inverse magnet, 4 ohms, rated up to 10W, £1.50 each or 2 for £2.75 (qty. discount available + 12% VAT).

TV PLUGS AND SOCKETS
TV Plugs (metal type), 5 for 50p.
TV Sockets (metal type), 4 for 50p.
TV Line Connectors (back-to-back sockets), 4 for 50p. Please add 12% VAT.

PLUGS AND SOCKETS
N-Type Plugs 50 ohm, 40p each, 3 for £1.50.
N-Type Sockets (4-hole chassis mounting, 50 ohms (a small coax lead type), 50p each.
PL259 Plugs (PTFE), brand new, packed with reducers, 45p or 5 for £3.
SQ230 Sockets (PTFE), brand new (4-hole fixing type), 50p each or 5 for £2.25.
25-way ISEP Plugs and Sockets, 40p set (1 plug + 1akt).

Plugs and sockets sold separately at 25p each. Bughin Round Free Sckt. 3 pin, for mains input on test equipment, etc., 25p each.

Mobile Converters, 24V DC input 13.8V at approx 3-4A DC output, fully stabilised, £3.50 each (ideal for running 12V car radio from 24V lorry battery).

Pkts. of 2BA Nuts (the self-locking ones with the nylon insert) 100 for 50p.

We now stock Spirax Tools for the electronic enthusiast. Screwdrivers, Nut Spanners, BA and Metric sizes, pop rivet guns, etc. S.A.E. for list.

I.F. Cans, 1/2in square, suitable for rewind, 6 for 30p + 12% VAT.
Miniature earphones with min. jack plug, 2 for 50p + 12% VAT.

TWIN I.F. CANS, approx. 1 1/2in x 1 1/2in high, around 3-5MHz. 2 separate transformers in 1 can, internally screened, 5 for 50p + 12% VAT.

Dubilier Electrolytics, 50µF, 450V, 2 for 50p.
Dubilier Electrolytics, 100µF, 275V, 2 for 50p.
Plessey Electrolytics, 470µF, 63V, 3 for 50p.
TCC Electrolytics, 1000µF, 30V, 3 for 60p.
Plessey Electrolytics, 1000µF, 180V, 40p each (3 for £1).

Dubilier Electrolytics, 5000µF, 35V, 50p each.
Dubilier Electrolytics, 5000µF, 50V, 60p each.
Dubilier Electrolytics, 5000µF, 70V, 65p each.
ITT Electrolytics, 6800µF, 25V, high grade, screw terminals, with mounting clips, 50p each.
Plessey Electrolytics, 10,000µF at 63V, 75p each.
Plessey Cathodry Capacitors, 0-0-4µF at 12-5KV DC, screw terminals, £1.50 each.

PLEASE ADD 12% VAT TO ALL CAPACITORS

A LARGE RANGE OF CAPACITORS AVAILABLE AT BARGAIN PRICES, S.A.E. FOR LIST.

SPECIAL OFFER!
MAINS TRANSFORMER, TYPE 14/4, 14V at 4A, £2.50.

2-6µF, 10mm circular ceramic trimmers (for VHF/UHF work) 3 pin mounting, 5 for 50p.
T03 transistor insulator sets, 10 for 50p.
PC Board Withdrawal handles, mixed cols, 8 for 50p.

Solder, 20 SWG, 60/40 alloy, approx 8 yds for 25p.
MINIATURE 2 PIN PLUGS AND SOCKETS (fit into 3in hole, pins enclosed, with covers for chassis mounting, or can be used for inline connectors). Bargain pack of 3 plugs + 3 sockets + covers, 50p.

PROGRAMMERS (magnetic devices). Contain 9 microswitches (suitable for mains operation) with 9 rotating cams, all individually adjustable, ideal for switching disco lights, displays, etc., or industrial machine programming. (Need slow motion motor to drive cams, not supplied) 8 switch version £1.50, or 15 switch version £2.
HEAVY DUTY HEATBINK BLOCKS, undrilled, base area 2 1/2in x 2in, with 8 fins, total height 2 1/2in 50p each.

RUBBER MAGNETS 1/2in square, with mounting hole, 20 for 30p.
SPERRY 7-SEGMENT P.G.D. DISPLAYS, digit height 0.3in red, with decimal pointer, 15V to 200V (nominal 150V) operation. These are high-volt industrial type and therefore brighter than normal displays. All brand new. AT THE BARGAIN PRICE OF 50p PER DIGIT, TYPE 332 (two digits in one mount) £1 each, TYPE 333 (three digits in one mount) £1.50. (Sorry, no single digit available.) Data supplied.

BSX20 (VHF Osc/Mult), 3 for 50p.
BC108 (metal can), 4 for 50p.
PBC 108 (plastic BC108), 5 for 50p.
OC200 Transistors, 6 for 50p.
BFY51 Transistors, 4 for 60p.
BCY72 Transistors, 4 for 50p.
PNP audio type 10S Transistors, 12 for 25p.
BF152 (UHF amp/mixer), 3 for 50p.
BA21 Varicap Diodes, 4 for 50p.
1N914 diodes, 10 for 25p.

1 1/2in polythene chassis mounting fuseholders, 6 for 30p.
Mullard Tubular ceramic trimmers, 1-18pF, 6 for 50p.
I.C.s, some coded, 14 DIL type, untested, mixed, 20 for 25p.

DIECAST BOXES (approx size in inches)
4.3 x 2.3 x 1.5 85p
4.8 x 2.3 x 1.5 75p
4.8 x 3.8 x 1 85p
4.8 x 3.8 x 2 £1.00
6.8 x 4.8 x 2 £1.45
4.8 x 3.8 x 3 £1.55
8.8 x 4.8 x 4 £2.25
8.8 x 5.8 x 2 £1.85
£2.25

Please add 8% VAT

WELLS SOLDERING IRONS
EXPERT. Built-in spotlight illuminates work. Pistol grip with fingertip trigger. High efficiency copper soldering tip.
EXPERT SOLDER GUN, £8.50 + VAT (54p)
EXPERT SOLDER GUN KIT (spare bits case, etc.), £9.00 + VAT (78p)

SPARE BITS, PAIR, 25p + VAT (2p)
MARKSMAN SOLDERING IRONS
SP15D 15W £2.52 + VAT (20p)
SP25D 25W £2.52 + VAT (20p)
SP25DK 25W + bits, etc, kit £3.12 + VAT (25p)
SP40D 40W £3.44 + VAT (28p)

BENCH STAND with spring for Markman Irons, £1.80 + VAT (14p)

SPARE BITS
M78 for 15W, 42p + VAT (3p).
M74 for 25W, 35p + VAT (3p)
M70 for 40W, 40p + VAT (3p)

TEMPERATURE CONTROLLED IRON. Temperature controlled iron & PSU, £18.45 + VAT (£14).

TEMPERATURE CONTROLLED IRON. Temperature controlled iron & PSU, £18.45 + VAT (£14).

SPARE BITS
Type CC single flat, Type K double flat fine tip, 90p each + VAT (8p).
ALL SPARES AVAILABLE

MULTICORE SOLDER
Size 5 Savbit 18 s.w.g. in alloy dispenser, 32p + VAT (5p).
Size C15AV18 Savbit 18 s.w.g., 56p + VAT (4p).
Size 12 SAVBIT 18 s.w.g. on plastic reel £1.80 + VAT (15p)

MINIATURE PLIERS High quality 'Crescent' made in USA £4.35 + VAT (35p).
SIDE CUTTERS, high quality 'Crescent', made in USA £5.45 + VAT (44p).

Terms of Business: CASH WITH ORDER. MINIMUM ORDER £1. ALL PRICES INCLUDE POST & PACKING (UK ONLY). SAE with ALL ENQUIRIES Please. PLEASE ADD VAT AS SHOWN. ALL GOODS IN STOCK DESPATCHED BY RETURN.

SOUTHERN VALVE COMPANY

P.O. Box 144, BARNET, Herts.

Telephone: 01-440 8641. Mail order only. Most leading makes.

ALL NEW & BOXED VALVES (Incl. tax)

AZ31	72p	EZ40/1	59p	FD500	£2.50	UL84	48p
DY88/7	40p	EZ50	38p	FL200	31p	UY35	37p
DY90/2	41p	EZ61	39p	FL25	67p	U25	80p
EB91	39p	GY101	90p	PL1	55p	U26	76p
ECC81	39p	GY20	40p	PL5A	60p	U91	80p
ECC82	37p	PC86	70p	PL82	42p	6/30L2	80p
ECC83	37p	PC88	70p	PL83	51p	6BW7	75p
ECC85	44p	PC97	44p	PL84	51p	6E22	80p
ECC88	55p	PC90	54p	PL90	38p	6E28	75p
ECC42	30p	PC94	44p	PL94	38p	6V6	52p
ECC81	40p	PC95	48p	PL98	£1.10	10F1	75p
ECC83	90p	PC98	69p	PL509	£2.00	20L1	92p
ECC84	57p	PC99	55p	PL519	£3.10	20P4	98p
ECL80	57p	PC189	58p	PL502	£2.25	30C1	44p
ECL82	51p	PC90	44p	PY33	57p	30C15	88p
ECL83	75p	PC92	55p	PY91/3	45p	30C17	88p
ECL86	46p	PC96	64p	PY88	45p	30C18	£1.35
EF80	33p	PCF200	£1.05	PY800	45p	30F5	86p
EF85	41p	PCF801	55p	PY801	45p	30FL1	£1.08
EF86	37p	PCF802	60p	PY900	£1.10	30FL2	£1.08
EF89	35p	PCF805	£1.85	PY500A	44p	30L1	44p
EF183	41p	PCF806	60p	UBF89	44p	30L15	86p
EF184	41p	PCF808	£1.25	UC88	51p	30L17	£1.10
EH90	62p	PCB200	38p	UCH42	30p	30P12	86p
EL34	90p	PCL82	41p	UCH81	46p	30P19	£1.00
EL41	64p	PCL83	55p	UCL82	46p	30PL1	£1.50
EL4	38p	PCL84	52p	UCL83	64p	30PL13	87p
EL90/1	48p	PCL85	65p	UF41	75p	30PL14	£1.30
EM84	49p	PCL805	88p	UF89	46p	30PL15	£1.30
EY51	52p	PCL86	55p	UL41	80p	30P4MR	89p
EY86/7	40p	PCL200	£1.30				

We offer return of post service. Post free over £10.00.

Most other types available.

Items in stock at time of going to press but subject to possible market fluctuations if unavoidable.

TRADE. Representative will call West Country & S. Wales, also Suffolk, Norfolk, Hunts, etc.

Enquiries s.a.e. DISCOUNT PRICES, CWO only.

One valve post 9p, each extra valve 6p (maximum 50p) LISTS s.a.e. please.

LOUDSPEAKER KITS:—8 OHMS

2 way, 8" Bass, 2 1/2" Tweeter, 15 watts £12.25

3 way, 8" Bass, 2 1/2" Midrange, 2" Tweeter, 20 watts £17.25

STEREO HEADPHONES:—8 OHMS

with Stereo/Mono switch £10.35

without switch £8.25

TELEPHONE AMPLIFIER:—

STEREO 4 CHANNEL MIXER:— £10.95

2 L.H. Channel 2 R.H. Channel £12.25

REGULATED POWER SUPPLY:—

O/P 6, 7-5, 9, 12, Volts D.C. Max. 1 amp £18.25

PRINTED CIRCUIT KIT:—

Contains everything to produce printed circuits £2.65

RESISTORS:—

1/4, 1/2, watt 5% 1p each., 10/9p; 100/80p. BC107/8/9—9p; 555 timer—

57p; 741—25p.

C.W.O. VAT included 20p P & F. Send stamp for lists or enquiries.

CLEVELAND SUPPLIES (PW)

P.O. BOX 20, REDCAR, CLEVELAND.

PLEASE MENTION
PRACTICAL WIRELESS
WHEN REPLYING TO
ADVERTISEMENTS

MOTOROLA CMOS

MC14001	QUAD 2 INPUT NOR	20p
MC14002	DUAL 4 INPUT NOR	20p
MC14007	DUAL PAIR AND INVERTER	20p
MC14009	HEX INVERTER/BUFFER	50p
MC14011	QUAD 2 INPUT NAND	20p
MC14013	DUAL D TYPE FLIP FLOP	50p
MC14015	DUAL 4 BIT STATIC SHIFT REGISTER	95p
MC14017	DECADE COUNTER/DIVIDER	95p
MC14021	8 BIT STATIC SHIFT REGISTER	95p
MC14023	TRIPLE 3 INPUT NAND	20p
MC14024	7 STATE BINARY COUNTER	£1.10
MC14025	TRIPLE 3 INPUT NOR	20p
MC14027	DUAL JK FLIP/FLOP	55p
MC14030	QUAD EXCLUSIVE OR GATE	60p
MC14042	QUAD LATCH	85p
MC14046	PHASE LOCK LOOP	£1.25
MC14049	HEX BUFFER	50p
MC14066	QUAD BILATERAL SWITCH	60p
MC14071	QUAD 2 INPUT OR GATE	20p
MC14081	QUAD 2 INPUT AND GATE	20p
MC14435	3½ DIGIT D.V.M.	£4.85
MC14501	TRIPLE GATE	35p
MC14507	D QUAD EXCLUSIVE OR GATE	60p
MC14510	BCD UP/DOWN COUNTER	£1.30
MC14511	BCD 7 SEG. LATCH/DECODER/DRIVER	£1.45
MC14518	DUAL BCD UP COUNTER	£1.95
MC14520	DUAL BINARY UP COUNTER	£1.95
MC14528	DUAL RETRIGG./RESETT. MONO/MULTI.V.	£1.10
MC14531	DUAL BIT PARITY TREE	£1.85
MC14583	DUAL SCHMITT TRIGGER	75p

TRANSISTORS

BC107	12p	BC347B	15p	BF196	10p
BC108	12p	BC348	14p	BF197	12p
BC109	12p	BC348B	15p	BFX29	25p
BC147	10p	BC349	14p	BFX48	40p
BC148	10p	BC350	15p	BFY51	20p
BC149	10p	BC351	15p	BSX20	12p
BC157	10p	BC352	15p	BSX60	60p
BC158	10p	BC516	40p	BSY27	25p
BC159	10p	BC517	40p	BSY40	43p
BC172	12p	BC547	15p	BSY95A	12p
BC237	15p	BC548	15p	BU102	£1.85
BC238	15p	BC549	15p	BSW66	35p
BC239	15p	BC558A	18p	MJ802	£3.35
BC261A	18p	BCY32	95p	MJ3701	50p
BC307	15p	BCY70	18p	MJ4502	£3.60
BC308	15p	BCY71	21p	MJE3055	50p
BC309	15p	BD115	75p	MPS3904	15p
BC317A	18p	BD121	£1.90	MPS3906	15p
BC318B	18p	BD142	85p	MPSA06	25p
BC319C	20p	BDY56	£1.85	MPSA56	25p
BC320A	20p	BF152	20p	OC28	80p
BC321A	20p	BF167	23p	TIP41A	97p
BC322B	20p	BF178	20p	TIP42A	£1.05
BC327	20p	BF181	37p	TIP2955	55p
BC328	20p	BF183	20p	TIP3055	50p
BC337	20p	BF184	25p	2N3055 (RCA)	£1.75
BC338	20p	BF194	10p		£1.05
BC347	14p	BF195	10p		£1.20

TEXAS NATIONAL

SN 7400 SERIES

SN7400	16p
SN7401	16p
SN7402	16p
SN7404	19p
SN7410	16p
SN7413	32p
SN7440	16p
SN7447A	95p
SN7472	26p
SN7473	30p
SN7474	35p
SN7475	50p
SN7483	85p
SN7490	50p
SN7493	50p
SN7495	70p
SN74121	35p
SN74122	45p
SN74123	65p
SN74136	£1.05
SN74141	85p
SN74165	£1.75
SN74175	£1.05
SN74180	£1.20

MOTOROLA POWER TRANSISTORS TO3

MJ802 (npn)	£3.35	
MJ4502 (pnp)	£3.60	
Ic (max)	BVceo	PD
30 AMP	90	200 WATT

NATIONAL

LM301A	OP-AMP	45p
LM380-8N	1 WATT AMP	£1.05
LM380N	2 WATT AMP	£1.20
LM381N	Stereo PRE-AMP	£1.85
LM723	Var. Voltage Reg.	55p
LM3900N	Quad OP-AMP	69p

DIODES

IN4001	6p
IN4002	7p
IN4003	8p
IN4004	9p
IN4005	10p
IN4006	12p
IN4007	15p
IN4148	6p


SIGNETICS VOLTAGE REGULATORS

7905	5V	} £1.60 each
7812	12V	
7815	15V	

SIGNETICS

NE555V	Timer	45p
NE556V	Dual Timer	£1.28
NE561B	PLL	£4.75

SUPERTESTER 680R ICE

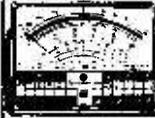

10 Fields-80 Ranges: 20,000 Ohm per Volt/sensitivity
 ● Fully screened against external magnetic fields ●
 Scale width and small case dimensions (128 x 95 x 32mm) ● Accuracy and stability (1% in D.C., 2% in A.C.) of indicated reading ● Simplicity and ease of use and readability ● Full ranges of accessories ● 1,000 times overload ● Printed circuit board is removable without desoldering ● More ranges
£19.95

AVOMETER

MODEL AVO 8 MKV.
 £69.95
 (Carr. and ins. Securicor) £3.00

ADVANCE

ALPHA II
 3-DIGIT
 DIGITAL MULTIMETER
 £64.75 + £3.00
 (Carr. and Ins. Securicor)

SPECIAL OFFER

PROFESSIONAL QUALITY LOW NOISE CASSETTES (Screw Case)
 C60 35p each, TEN for £3.00
 C90 45p each TEN for £4.00

TEXAS TRANSISTORS (Plastic Power)

TIP41A (npn)	97p
TIP42A (npn)	£1.05
TIP2955 (pnp)	55p
TIP3055 (npn)	50p

MOTOROLA

741 OP-AMPS 35p each
 8 pin dil. T±N for £3.00

MOTOROLA

MC1310P	Stereo Decoder	£2.10
MC1306P	1 Watt Amp	£1.10
MC1458	Dual OP-AMP	75p
MC1741 (8 pin DIL)	OP-AMP	35p
MC6040	Electronic Atten.	85p

ALL PRICES INCLUDE VAT

PLASTIC COMPONENT BOXES

with See Thro' Lid a must for the Tidy Bench
6 FOR £1

RELAYS

11 PIN PLUG-IN
 3 c/o 5 AMP CONTACTS
 24V D.C. 95p
 24V A.C. 95p
 240V A.C. 95p


SCR's — TRIACS

TEXAS TIC46 (SCR) 100 PIV.	45p
600md	
MOTOROLA 2N4444 (SCR)	£1.45
600 PIV. 8 amp	
R.C.A. 40689 (TRIAC) 400 PIV.	£1.45
8 amp	

OPENING SOON IN WATFORD HERTS.

MICROTEST 80

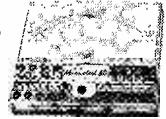Measures only 90 x 70 x 18mm
 Electronic Zero Ω
 Amazing value at
£12.90
 8 fields of measurement and 40 ranges



S'Dec	£2.14
T'Dec	£3.98
U'Dec	£4.65
U'Dec B	£7.90

SOLDERING IRONS ANTEX

CCN 240	£3.21
X25	£2.98
SK1 Kit	£4.62
SK2 Kit	£4.62
ST3 Stand	£1.21

WELLER TEMPERATURE CONTROLLED

TCPI (S. Iron)	£10.50
PUID (P.S.U.)	£8.90

0.1 ohm to 1 ohm 7 watt WIREWOUND RESISTORS

(Length 3/4" Tol. ± 5%)
 VALUES: 0.1 - 0.15 - 0.22 - 0.27
 0.33 - 0.39 - 0.47 - 0.56 - 0.82 - 1 ohm
 35p each

CARBON FILM RESISTORS

(1/3 WATT TOL. + 5%)
 4-7 ohms to 10 meg 2p each

MIN. POLYESTER FILM CAPACITORS (Radial Leads)

·01 - ·022 - ·047 7p each
 ·1 - ·22 - ·47

SOLDERCON

I.C. Pins 65p per 100

TEXAS LED'S (RED ONLY)

TIL 209 - 125"
 15p each, 7 for £1.00, 15 for £2.00

FERRANTI

ZN414 Radio Chip £1.25

R.C.A.

CA/3046 Trans/Array 80p

MACK'S ELECTRONICS

283 Edgware Road, London W2.
 Tel. 01-262 8614

Hours of business 9.30 - 6.00
 Monday to Saturday Callers welcome
 ALL PRICES INCLUDE VAT PLEASE ADD 20p P & P

ALL ITEMS BRAND NEW PRIME GRADE

"A VERY GOOD INVESTMENT INDEED"

says
P.W. May

In the course of a very thorough write-up on our product, *Practical Wireless* says: "The unit is easy to assemble and fit. It worked the first time. Is it a good buy? It certainly is! To my mind, the biggest feature is the ability to switch back to normal ignition at any time. Considering the price it is a very good investment indeed!"

Why be without when you can fit one so easily and for so little?

Capacity Discharge Ignition is not new—but the value offered by the Bi-Pre-Pak "Super-Spark" unit is. *Practical Wireless* says the P.C.B. is one of the best ever seen—it is so clearly laid out you could almost assemble it without instructions! You know the advantages of using electronic ignition—easier starting winter

and summer, reduced wear and petrol consumption, and with this unit, you can switch over instantly to the car's own ignition should you ever want. Switching arrangements enable you to immobilise and protect your car against thieves, too. Easily adapted to pos. or neg. earth, and built for years of service.

THE BI-PRE-PAK Mk. 5


Super Spark CAPACITOR DISCHARGE CAR IGNITION UNIT

DIRECT FROM THE MAKERS

Bi-Pre-Pak Ltd. 220-224 WEST ROAD, WESTCLIFF-ON-SEA, ESSEX SS0 9DF. Phone Southend (0702) 46344

FULL OF GOOD FEATURES

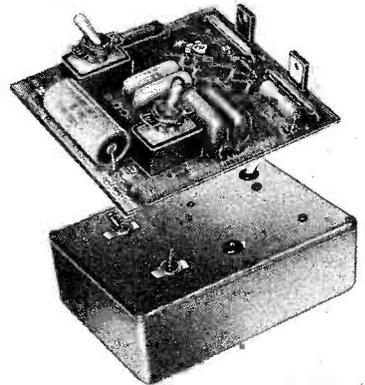- Rev. limiting adjustment
- Neon indicator
- Change over switch to normal ignition
- Immobilising switch
- Easy to connect for pos. or neg. earth
- Fully detailed information contained on P.C.B.
- Strong metal case 6½" x 4½" x 2½", sealed lid.
- Complete with transformer
- FULLY GUARANTEED



Easy to build kit— **£7.95** + 8% VAT (64p)
Ready built and tested **£10.50** + 8% VAT (64p)
Please add 50p for PIP either model.

SPECIAL CALCULATOR SALE

New Texas Instruments + Realtone

SR56—10 + 2-9 levels of brackets, 2 looping capabilities, 4 levels of subroutine, 10 date memory register @ £79.95.

SR52 @ £249.

Melcor **SCP700**, 10 memories algebraic logic programmable shortly available S.A.E. for details.
CBM4190R S.A.E. for price.

The SC60 Realtone—10-digit mantissa, 2-digit exponent, algebraic logic, 3 user addressable memories which include Sum memory, Sum of Squares memory and Index memory plus index register. It has double bracketing as well as arithmetic mean, norm (sq. root of sum of squares) STANDARD deviation, factorial, binomial, coefficient, permutation, function, normal distribution function, Gamma function, trig functions and their inverse, logs and anti logs, group operation and group controls, flexible memory control, factor reversal, degree/radian selection, error detection and display @ £46 plus £3.68 VAT. Total £49.68.

SC610 Realtone—50 functions, 65 keyboard commands. As SC60 but with 12 memories which allow memory storage for up to 10 intermediate results or 10 constants at the user's option. The extra memories may be used to store a group of variables for repeated processing of the variables. @ £60 plus VAT £4.80. Total £64.80.

SC44 Realtone—22 functions, 40 keys, 8 digit mantissa 2 digit exponent, two levels of brackets, algebraic logic works to 10 rounds to 9 Trig functions and their inverse, log and anti log, exponentiation (y^x) factorials, pi, i/x, √x (sq rt of x) degree/radian selection (trig or inverse trig) full feature memory STO, RCL, M+, exchange operation x-y automatic error detection and display. Clearing operation (CA, CE). @ £32 + VAT £2.56. Total £34.56.


All rechargeable with 220/240 adaptors. Size 6½ x 3½ x 1½. Weight 300 grams (Realtone units).

SAE for full details of our range.

All subject to availability. One year warranty.

Send to **Kramer & Co., Dept. PW, 9 October Place, Holders Hill Road, London NW4 1EJ.**
Telex 888941 ATTN KRAMER. Tel. 203 2473
p & p 65p C.W.O.

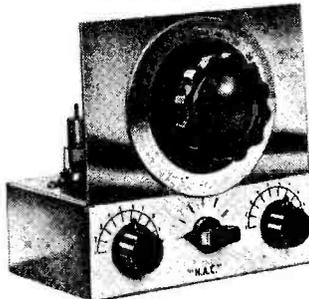H.A.C. SHORT-WAVE KITS WORLD-WIDE RECEPTION



Famous for over 35 years for Short-Wave Equipment of quality. "H.A.C." were the Original suppliers of Short-Wave Receiver Kits for the amateur constructor. Over 10,000 satisfied customers—including Technical Colleges, Hospitals, Public Schools, R.A.F., Army, Hams, etc.

1976 "DX" RECEIVER

Complete kit—Price £6.00 (incl. p. & p. & V.A.T.). Customer writes: "I think the performance is astonishing for such an inexpensive and foolproof kit. I would wholeheartedly recommend this kit to anyone, however inexperienced, as an antidote to TV-tis, and as an entry into a fascinating hobby".

This kit is ready to assemble and contains all genuine short-wave components, drilled chassis, valve, accessories and full instructions. Full range of other S.W. kits, including the famous model "K plus" (illustrated above). All orders despatched within 7 days. Send now for free descriptive catalogue of kits and components. Send stamped envelope for details.

"H.A.C." SHORT-WAVE PRODUCTS
P.O. BOX No. 16, EAST GRINSTEAD,
SUSSEX RH19 3SN

CLOCK MENU

Try the following recipe for a digital clock.

Basic Ingredients

1. **MHI CLOCK KIT.**
Comprises: clock chip, driver chip for common anode LEDs, PC board, and socket (if required).
Types: basic clock, alarm clock, alarm clock with calendar, car clock, stop-clock, up/down counter.
2. **MHI DISPLAYS KIT.**
4 or 6 digit LEDs with PC board. Sizes: 0-3" 0-5" or 0-6".
3. **MHI CASE.**
Size: 8" x 5-5" x 3" White only
4. **Transformer, resistors and transistors not supplied—all are stocked by most radio shops. With some kits we supply quartz crystals, trimmers or other components normally difficult to obtain.**

Shopping List.

MHI 5314 Basic clock	6-60
MHI 50253 Alarm clock	8-35
MHI 7001 Alarm & calendar	10-00
MHI 5378 Car clock	15-10
MHI 5309 Stop-clock	7-35
MHI 50395 UP/down counter	19-50
MHI 707/4 (digit) 0-3"	6-60
MHI 707/6 (digit) 0-3"	9-50
MHI 727/4 (digit) 0-5"	8-50
MHI 727/6 (digit) 0-5"	12-00
MHI 747/4 (digit) 0-6"	9-80
MHI 747/6 (digit) 0-6"	14-70
MHI Case 2-95 + 25p postage & packing	

Please send SAE for new catalogue.

TERMS: CWO, Access, Barclaycard (simply quote your number and sign). Credit facilities to Accredited account holders.

BYWOOD

68 Ebbwens Road, VAT: All prices
Hemel Hempstead, exclude VAT (8%)
Herts HP3 9QRA P/P: 15p
TEL: 0442 62757

Get a great deal from

Marshall's

A. Marshall (London) Ltd Dept: PW
 42 Cricklewood Broadway London NW2 3ET Tel: 01-452 0161/2
 Telex: 21492
 & 85 West Regent St Glasgow G2 2QD Tel: 041-332 4133
 & 1 Straits Parade Fishponds Bristol BS16 2LX
 Tel: 0272 654201/2
 & 27 Rue Danton Issy Les Moulineaux Paris 92 Tel: 644 2356
Catalogue price 25p Trade and export enquiries welcome



"I MADE IT MYSELF"

Imagine the thrill you'll feel! Imagine how impressed people will be when they're hearing a programme on a modern radio you made yourself.

Now! Learn the secrets of radio and electronics by building your own modern transistor radio!

Practical lessons teach you sooner than you would dream possible.

What a wonderful way to learn—and pave the way to a new, better-paid career! No dreary ploughing through page after page of dull facts and figures. With this fascinating Technatron Course, you learn by building!

You build a modern Transistor Radio . . . a Burglar Alarm. You learn Radio and Electronics by doing actual projects you enjoy—making things with your own hands that you'll be proud to own! No wonder it's so fast and easy to learn this way. Because learning becomes a hobby! And what a profitable hobby. Because opportunities in the field of Radio and Electronics are growing faster than they can find people to fill the jobs!

So fast, so easy, this personalised course will teach you even if you don't know a thing today!

No soldering—yet you learn faster than you ever dreamed possible. Yes! Faster than you can imagine, you pick up the technical know how you need. Specially Prepared step-by-step lessons show you how to: read circuits—assemble components—build things—experiment. You enjoy every minute of it!

No matter how little you know now, no matter what your background or education, we'll teach you. Step by step, in simple easy-to-understand language, you pick up the secrets of radio and electronics.

You become somebody who makes things, not just another of the millions, who don't understand. And you could pave the way to a great new career, to add to the thrill and pride you receive when you look at what you have achieved. Within weeks you could hold in your hand your own transistor radio. And after the course you can go on to acquire highpowered technical qualifications, because our famous courses go right up to City & Guilds levels.

You get everything you need. Tools. Components. Even a versatile Multimeter that we teach you how to use. All included in the course. **AT NO EXTRA CHARGE!** And this is a course anyone can afford. (You can even pay for it by easy instalments).

Send now for FREE 44 page book—see how easy it is—read what others say!

Find out more now! This is the gateway to a thrilling new career, or a wonderful hobby you'll enjoy for years. Send the coupon now. There's no obligation.

CPW18

POST TODAY FOR FREE BOOK

**To: ALDERMASTON COLLEGE
 DEPT. CPW 18, READING RG7 4PF**

Also at our London Advisory Office, 4 Fore Street Avenue, Moorgate, London, EC2Y 5EJ Tel: 01-628 2721

Yes, I'd like to know more about your course. Please send me free details—plus your big, 76-page book that tells about all your courses.

Name

Address

POST CODE



BIET

HOME OF BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY

Our range covers over 7,000 items. The largest selection in Britain

Top 200 IC's TTL, CMOS & Linears			
CA3020A	£1.80	CD4049	45p
CA3028A	75p	CD4050	35p
CA3035	£1.37	CD4510	£1.25
CA3046	70p	CD4511	£1.94
CA3048	£2.11	CD4516	£1.25
CA3052	£1.62	CD4518	£1.87
CA3089E	£1.96	CD4520	£1.87
CA3090C	£2.23	LM301A	18p
CA3133	80p	LM308	£1.17
CD4000	18p	LM309K	£1.88
CD4001	18p	LM380	98p
CD4002	18p	LM381	£2.07
CD4006	99p	LM702C	75p
CD4007	18p	LM709	38p
CD4008	80p	TO99	38p
CD4009	50p	8DIL	15p
CD4010	52p	14DIL	38p
CD4011	18p	LM710	47p
CD4012	18p	LM723C	66p
CD4013	45p	LM741C	40p
CD4014	85p	TO99	40p
CD4018	80p	8DIL	15p
CD4016	45p	14DIL	38p
CD4017	88p	LM747	£1.05
CD4018	88p	LM748	£1.05
CD4019	52p	8DIL	44p
CD4020	98p	14DIL	41p
CD4021	88p	LM740	51p
CD4022	85p	LM7805	£1.88
CD4023	18p	LM7812	£1.99
CD4024	72p	LM7815	£1.99
CD4025	19p	LM7824	£1.99
CD4027	43p	MC1303L	£1.50
CD4028	88p	MC1310P	£2.00
CD4029	£1.06	MC1300P	90p
CD4030	52p	MC1351P	80p
CD4031	£1.98	MC14553	£4.07
CD4037	78p	MC1466L	£3.50
CD4041	80p	MC1469R	£2.75
		NE555V	70p
		NE556	£1.30
		NE560	£4.48
		NE565	£4.48
		SL414	£2.35
		SL610C	£2.35
		SL611C	£2.35
		SL612C	£2.35
		SL620C	£3.50
		SL621C	£3.90
		SL623C	£5.75
		SL640C	£4.00
		SN7400	16p
		SN7401	16p
		SN7402	16p
		SN7403	16p
		SN7404	19p
		SN7405	19p
		SN7406	36p
		SN7407	30p
		SN7408	19p
		SN7409	18p
		SN7410	16p
		SN7411	20p
		SN7412	20p
		SN7413	28p
		SN7414	28p
		SN7415	28p
		SN7416	28p
		SN7417	28p
		SN7418	28p
		SN7419	28p
		SN7420	28p
		SN7421	15p
		SN7422	22p
		SN7423	28p
		SN7424	28p
		SN7425	28p
		SN7426	28p
		SN7427	28p
		SN7428	28p
		SN7429	28p
		SN7430	28p
		SN7431	28p
		SN7432	28p
		SN7433	28p
		SN7434	28p
		SN7435	28p
		SN7436	28p
		SN7437	28p
		SN7438	28p
		SN7439	28p
		SN7440	28p
		SN7441	28p
		SN7442	65p
		SN7443	65p
		SN7444	65p
		SN7445	65p
		SN7446	65p
		SN7447	80p
		SN7448	90p
		SN7450	16p
		SN7451	16p
		SN7452	16p
		SN7454	16p
		SN7456	16p
		SN7460	16p
		SN7467	25p
		SN7472	21p
		SN7473	31p
		SN7474	31p
		SN7475	45p
		SN7476	30p
		SN7480	42p
		SN7481	£1.00
		SN7482	65p
		SN7483	82p
		SN7484	95p
		SN7485	£1.00
		SN7486	29p
		SN7487	66p
		SN7489	65p
		SN7490	65p
		SN7491	10p
		SN7492	45p
		SN7493	45p
		SN7494	75p
		SN7495	66p
		SN7496	66p
		SN7497	66p
		SN7664	66p
		SN7665	

ABOVE ALL IT'S THE ANTENNA THAT MATTERS —TRANSMITTING AND RECEIVING!

"WITH 40 YEARS EXPERIENCE AS AN AMATEUR AND PROFESSIONAL OPERATOR I CAN TRUTHFULLY SAY THAT THIS IS THE ONLY MULTI-BAND ANTENNA I HAVE FOUND WHICH GIVES THE RESULTS WHICH MIGHT BE EXPECTED FROM VERTICALS TAILOR MADE FOR EACH BAND."—G6SX

U.S.A. Govt. Electronics Engr. (retd.), W70E claims "VFA 5ft below ground, same as dipole, elevated 15ft., one 'S' point UP on dipole."—AND REMEMBER THE JOYSTICK VFA MEASURES ONLY 7' 6" LONG!!

— AS SUPPLIED TO H.M. GOVT. COMMUNICATIONS H.Q. —

PRICES INCLUDE V.A.T. INSURANCE AND DELIVERY BY POST OR CARRIER

JOYSTICK V.F.A., £18-00; **JOYMATCH A.T.U.'s**— 111 (Med. wave - 30 MHz), £18-00; 111A (1.6-30 MHz), £18-00; 111B (L match, 1.6-30 MHz), £16-20; LO-Z500 (1.8 thru 30 MHz, 500w), £23-35; "RC" (pre-production prototype "impossible" location A.T.U.—S.W. bands) £9-56; **BUDGET LINE: A.T.U.** 1.6-30 MHz, £8-90; A.T.U. Medium and S.W. bands, £8-90 (both in kit form, £7-40); Aerial Bandswitch (complete aerial system, medium and SW bands), £7-40; Artificial Earth, £7-40; **DX CRYSTAL SET** (Home and World-Wide reception) ready to use, £4-86; Comm. Headphones 8 ohm, £4-90; Field Strength Meter, £2-11; Set valves 9R59DS, £6-21; Coaxial cable 50 or 75 ohms, per 10 metres, £1-55; **SYSTEM "A"**: VFA + 111B, £32-96; **SYSTEM "X"**: VFA + either 111 or 111A, £34-47; **SYSTEM "D"**: VFA + Aerial B'switch, £24-63; **SYSTEM "J"**: VFA + LO-Z500 £41-03; **SYSTEM "RC"**: VFA + "RC", £27-56.

PARTRIDGE SUPER PACKAGE

COMPLETE RADIO STATION FOR ANY LOCATION. Comprising: Trio QR666 Gen. Cov. RX, Headphones VFA., System "A", all connecting cables, del. (our risk). ASSEMBLED IN SECONDS! SAVE £14.05. **£206.93**

Send stamp for details and expert advice.

Just telephone your card number

BOX 5



Phone 0843 62535

(or 62839

after office hours)

G3CED G3VFA



RECHARGEABLE BATTERIES

CAN SAVE YOU A FORTUNE! Bush & Meissner's two purpose-built battery chargers for economy minded enthusiasts:

The "KESTREL-DOWN" Charger £10.69 & £11.77 for Alkaline rechargeable batteries, no-load voltage of 1.5 volts per cell, for the following sizes ALKALINE (All prices include VAT)
Equivalent to Type Capacity PRICE
U2 size SA-13D 2Ah £2.37
U7 size (panel) SA-15AA 0.3Ah £0.78p

NICKEL-CADMIUM (All prices include VAT)
The "DAIMON" Charger £9.98 for Nickel-Cadmium batteries, no-load voltage of 1.25 volts per cell, for the following sizes
Type Capacity PRICE
NCC400 4Ah £4.74
NCC200 2Ah £3.20
NCC50 0.5Ah £1.65
Battery containers extra 44p to 83p each

Charger designed to give optimum results with a specific type of cell. Never be without power, day or night.

Note, under no circumstances must Alkaline batteries be used with the Daimon charger.

S.A.E. brings full details

Bush & Meissner

Importers & Distributors
Dept LS260
275 West End Lane,
London
NW6 1QS
01-794-9611



GREENWAY

Radial Lead Polyesters I.T.W. *10% 100V D.C. .001 3p; .0022 3p; .0047 3p; .0068 3p; .01 3p; .015 .035p; .022 .035p; .033 .04p; .047 .04p; .068 .05p; .1 .05p; .15 .06p; .22 .065p; .33 .075p; .47 .095p; *Radial Polycarbonate 330V D.C. .33 .25p; .47 .25p; .68 .30p; 1mf. 400V .35p. *Axial Lead 10% Tolerance 200V D.C. .01mf. .185p; .022mf. .185p; .047mf. .20p; .1mf. .25p. **Dipped Tantalum Capacitors** (Bead Type) values available: 1; 15; 22; 33; 1mf. 1; 5; 2; 3; 3; 4; 7; 35V; 47; 6; 8; 10mf; 25V; 15; 22; 33; 16V; 47mf; 10V. Prices 10p each — 10 for 95p. *Electrolytic Capacitors (Axial) 1000-40V 25p; 470-16V 15p; 220-25V 12p; 100-25V 6p; 47-25V 5p; 47-10V 5p; 22-40V 5p; 10-25V 5p; 4.7-63V 5p; 2.2-63V 5p; 1 mfd-63V 5p. *Radial 2200(T20) 40V 50p each; 100-16V 25p; 470-25V 19p; 220-25V 12p; 100-25V 6p; 47-16V 5p; 33-16V 5p; 10-16V 4p; 5mf. 16V 4p; 4.7-16V 4p. *Carbon Film Resistors 3Watt RD1/3 5% (70°C) .045p each — 90p per 100. 1R-1Meg (1M2-10M 10%) Special Pack 20 popular values quarter watt — 5 of each 90p. *Polystyrene Capacitors (p) 63V & 160V 5% 10; 15; 18; 22; 33; 56; 68; 100; 120; 180; 270; 330; 390; 560; 680; 820; .03p each. 1000; 1500; 2200; 3300 .035p each. 4700; 6800; 8200 4p each. 10,000pf .05p each. **Semi-conductors** BC107/8/9 .09p; *BC147/8/9 10p; BC177/8/9 9p; BCY70 1/2 17p; BFV57 18p; SCR C106D/2P4M-400V 50p each; TIP29A .47p; TIP31A .57p; TIP32A .67p; TIP3055 41p; BU208 £2.00. **Integrated Circuits** 741 8 Pin DIL 27p; 723(T099) 57p; LM309K(TO3) 1.48p; NE555V 80p; NE558V 1.12p. *I/C Sockets (Gold) 8/14/16 15p; (Tin) 8/14/16 14p. **Minicon** £1.30 each. **Zener Diodes** 400MW 3p; 1Watt 17p. (Standard voltages). **Diodes** IN4148 .05p; BAX16 .05p. **Rectifiers** 1A IN4001 5p; IN4002 .06p; IN4003 .07p; IN4004 .08p; 3Amp 3A05(50V) .10p; 3A10(100V) 11p. **Terms** C.W.O. VAT (*) add 12½%, others 8%. P&P 25p on all orders under £5.

SPECIAL OFFER: *A.C. Capacitors 16mf. 500V A.C. £1.50 plus .42 p&p; Mains Toroidal Transformer 20V 500M.A. £1.90 plus .42 p&p.

GREENWAY ELECTRONIC COMPONENTS (EAST GRINSTEAD) LTD.

62 Maypole Road, Ashurst Wood East Grinstead, Sussex RH19 3RB

TEL: FOREST ROW 3782 (STD 034-282) 3713

FREE Brochure on New KITS



Please see us in 10c 12 15p stamp rate-coded envelope



CROFTON don't just sell kits, we offer you a technical back up service to ensure your success

The following is a selection of some of the more popular kits

- ★ Mullard CCTV Camera
- ★ PE CCTV Camera
- ★ 'Mistral' Digital Clock Kit £12.50 incl. VAT, p. & p. 50p. Made up £18.00 incl. VAT, p. & p. 50p
- ★ Electronic Ignition
- ★ Sound Operated Flash
- ★ PW Tele-Tennis Game
- ★ UHF Modulator
- ★ Bench Power Supply
- ★ Wobbulator
- ★ All ETI Top Projects
- ★ Many of the Elektor Projects

NOTE PCBs for most published projects available to order

CROFTON ELECTRONICS LTD

Dept. B, 35 Grosvenor Road, Twickenham, Middx. Tele. 01-891 1923

ELECTROTIME


ELECTRONIC DIGITAL ALARM CLOCK MODEL EC 3



- ★ LARGE 4 DIGIT DISPLAY
- ★ AM/PM INDICATOR
- ★ FLASHING SECONDS INDICATOR
- ★ 5 MINUTE REPEATING SNOOZE ALARM
- ★ 24 HOUR ALARM
- ★ BRIGHTNESS CONTROL
- ★ ATTRACTIVE WHITE CASE

COMPLETE BUILT CLOCK PRICE **£14** inc. VAT.

THE "MISTRAL" 1 DIGITAL CLOCK

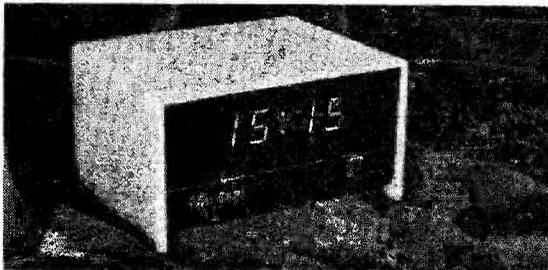

- ★ PLEASANT GREEN DISPLAY
- ★ 12/24 HOUR READOUT
- ★ FULLY ELECTRONIC
- ★ PULSATING COLON
- ★ PUSH BUTTON SETTING
- ★ BUILDING TIME 1 HOUR

COMPLETE KIT PRICE **£11.07** inc. VAT.

BUILT CLOCK PRICE **£14.95**

LCD MODEL TLC 4

CONTINUOUS READOUT UTILISING LIQUID CRYSTAL DISPLAY


WITH BACKLIGHT FOR
NIGHT READING

FEATURES—

- ★ HOURS
- ★ MINUTES
- ★ SECONDS
- ★ DATE

RHODIUM **£39.95**

GOLD **£41.50** inc VAT.

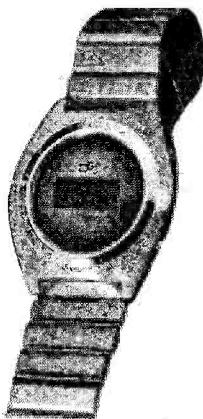

LED MODEL TLE 5

FEATURES—

- ★ HOURS
- ★ MINUTES
- ★ SECONDS
- ★ DATE
- ★ DAY OF WEEK

£29.50 inc. VAT.


GOLD OR
RHODIUM PLATED



LED MODEL TLE 3

FEATURES—

- ★ HOURS
- ★ MINUTES
- ★ SECONDS

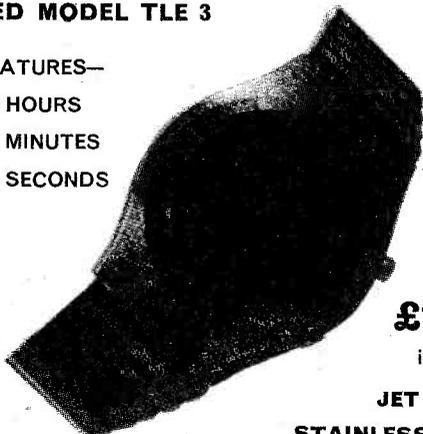

£19.95

inc. VAT.

JET BLACK
STAINLESS STEEL
CASE AND BRACELET

COME TO THE EXPERTS IN DIGITAL
TIMEKEEPING.

MONEY REFUNDED IF NOT COMPLETELY
SATISFIED

ONE YEAR GUARANTEE WITH ALL MODELS

ELECTROTIME DEPT., 3/6
111, STORFORTH LANE TRADING ESTATE,
CHESTERFIELD, DERBYSHIRE. TEL. 35804.

PLEASE SUPPLY

I ENCLOSE CHEQUE/POSTAL ORDER


NAME.....

ADDRESS.....

.....

.....

Greenbank Electronics Established 1970

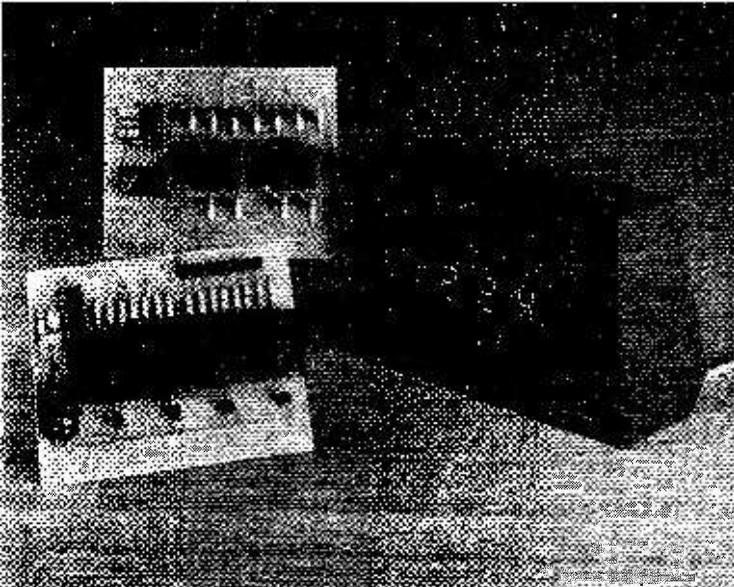

The illustration shows the two P.C.B. module kits already assembled, one has 8mm high digits, the other has 16mm high digits. Also shown is an example of a completed clock. Free on request: Data on AY-5-1224 and MK50253 clock chips, 4 and 6 digit alarm clock suggested circuits, quartz crystal timebase, and L.E.D. displays. (If you can send an S.A.E., it makes things a little easier for us).

CLOCK CHIPS

AY-5-1224A 4 digit basic clock £3.50 MK 50253 4/6 digit alarm/snooze £5.50

ECONOMY RED LED DISPLAYS ('Class II' quality, but guaranteed by us, fully returnable if not satisfied).

DL-707E/DL-704E 8mm (0.3") 70p. DL-727E/DL-728E 12mm (0.5") Double Digit £1.80. DL-747E/DL-750E 16mm (0.6") £1.50.

CMOS WITH DISCOUNTS! (Any mix: disc. 10% 25+, 25% 100+)

4000/14000	0.15	4023/14023	0.15	4043/14043	0.80	4066/14066	0.55
4001/14001	0.15	4024/14024	0.60	4044/14044	0.75	4067/	2.95
4002/14002	0.15	4025/14025	0.15	4045/	1.15	4068/14068	0.15
4006/14006	0.95	4026/	1.40	4046/14046	1.10	4069/14069	0.15
4007/14007	0.15	4027/14027	0.45	4047/	0.70	4070/14070	0.15
4008/14008	0.75	4028/14028	0.70	4048/	0.45	4071/14071	0.15
4009/14009	0.45	4029/	0.90	4049/14049	0.45	4072/14072	0.15
4010/14010	0.45	4030/14030	0.45	4050/14050	0.45	4073/14073	0.15
4011/14011	0.15	4031/	1.80	4051/14051	0.75	4075/14075	0.15
4012/14012	0.15	4032/14032	0.85	4052/14052	0.75	4076/14076	1.25
4013/14013	0.45	4033/	1.10	4053/14053	0.75	4077/14077	0.15
4014/14014	0.80	4034/14034	1.55	4054/	0.95	4078/14078	0.15
4015/14015	0.80	4035/14035	0.95	4055/	1.05	4081/14081	0.15
4016/14016	0.45	4036/	1.80	4056/	1.05	4082/14082	0.15
4017/14017	0.80	4037/	0.75	4057/	20.35	4085/	0.55
4018/	0.80	4038/14038	0.85	4059/	3.60	4086/	0.55
4019/14019	0.45	4039/	2.85	4060/	0.90	4089/	0.65
4020/14020	0.90	4040/14040	0.85	4061/	16.40	4093/14093	0.65
4021/14021	0.80	4041/	0.65	4062/	N/S	4094/	1.50
4022/14022	0.75	4042/14042	0.65	4063/	0.90	4095/	0.85

★ CA 3130 COS/MOS Operational Amplifier 75p ★

4096/	0.85	4515/4515	2.55	4543/	1.50
4097/	2.95	4516/4516	1.10	4549/	2.95
4098/14528	0.85	4517/	5.40	4552/	8.05
4099/	1.50	4518/4518	1.00	4553/	3.50
		4520/4520	1.00	4554/	1.20
		4521/	2.00	4555/4555	0.70
4700/	1.50	4522/	N/S	4556/4556	0.70
7083/	4.25	4523/	N/S	4557/	3.20
		4526/	1.50	4558/	0.90
		4527/4527	1.20	4559/	2.95
		4528/4098	0.85	4560/	1.55
14501/	0.15	4529/	1.30	4561/	0.45
14502/4502	1.00	4530/	0.65	4562/	5.25
14505/	3.30	4531/	1.25	4566/	1.20
14506/	0.35	4532/4532	1.60	4572/	0.35
14508/4508	2.35	4534/	6.00	4580/40108	6.00
14510/4510	1.10	4536/	2.85	4581/40181	3.05
14511/4511	1.25	4537/	15.25	4582/40182	1.15
14512/	1.05	4539/	1.85	4583/	0.71
14514/4514	2.55	4541/	1.00	4585/	1.45

Terms: C.W.O. Add VAT to all prices at 8%. Post etc., U.K. 10p per order, export 75p (no VAT). All orders processed on day of receipt

GREENBANK ELECTRONICS (Dept. W6P)
 94 New Chester Road, New Ferry, Wirral, Merseyside, L62 5AG, England. Tel:—051-645 3391

VALVE BARGAINS

Any 5-64p, 10-£1.10, 50-£5. Your choice from the following list: ECH84, ECC82, ECL80, EF80, EF183, EF184, PC86, PC88, PCF80, PCF802, PCL82, PCL84, PCL85, PCL805, PCL86, PFL200, PL36, PL504, PY33, PY81, PY800, PY88, EH90, 30FL1, 30FL2, 30PL14, 6F28

Colour Valves 30p each PL508, PL509, PY500/A.

Small Plastic Boxes (white) made out of high impact plastic with flick on lids, ideal for most projects. All three types one price. Prices 15p each. Ten £1.30. Size (approx.): Type 1—3½ins x 2½ins x 1½ deep. Type 2—3½ins x 2½ins x 2½ins deep. Type 3—3½ins x 3½ins x 1½ins deep.

Prices include V.A.T. P. & P. under £1.15p, £1 to £3.20p above £3.30p. Overseas at cost. Money back guarantee on all orders.

ELECTRONIC MAILORDER LTD.,
 62 BRIDGE ST., RAMSBOTTOM, BURY, LANCs. Tel. Rams. 3036

AERIAL BOOSTERS

We make three types of Aerial Boosters all for set top fitting, with Co-ax Plugs and Sockets.

B11—For Stereo and Standard VHF Radio.

B12—For the older VHF Television, please state BBC1 and ITV Channels.

B45—For mon. or colour this covers the complete UHF band.

All Boosters are complete with Battery and take only minutes to fit. Price **£3.90** each.

Capacitor Discharge IGNITION

MAXIMUM PERFORMANCE
 MAXIMUM ECONOMY,
 EASY COLD START

SYSTEM I

Professional photoelectric ignition using L.E.D. light source and reflective disc. This machined aluminium disc gives a timing accuracy far superior to other methods and is simple to fit. Unit housed in diecast box 4½" x 3¾" x 2¼" Price **£18.80** (Kit **£16.80**) State car/model/measurement across cam lobes.

SYSTEM II

Contact breaker model as above less sensor. Price **£12.80** (Kit **£10.80**) M/C Twin unit Price **£15.00**. S.A.E. for descriptive leaflet — ALL UNITS IN STOCK. Mail orders to CDI Electronic Systems Ltd, 275 Vale Road, Ash Vale, Aldershot, Hants. Demonstration/Callers to Hillside Motors, 292 Carshalton Road, Carshalton, Surrey, telephone 01-642 9973.

Do Something Useful for a Change!

Do it in your spare time. And enjoy it. And, perhaps, you'll save yourself some money. The secret is to be practical about the way you spend your spare time.

These practical magazines show you how.

Every month these six popular titles are packed with fascinating and constructive projects – full instructions for making your own furniture and fittings for the home as well as electronic gadgets for home, car or hobby.

See which 'practical' can widen your range of interests, whether in home-improvement, hi-fi or electronics – and on jobs you really could call useful.

everyday electronics

June issue : a waa waa pedal, an enlarger meter, a peak-level indicator and a continuity tester.
OUT MAY 21

30p

PRACTICAL WIRELESS

June issue : a digital frequency meter, talking transistors and a fault-finding guide.
OUT MAY 7

35p

PRACTICAL ELECTRONICS

June issue : a proportional radio-controlled system, an audio millivoltmeter and a rally milometer.
OUT MAY 14

35p

PRACTICAL HI-FI & AUDIO

June issue : 15 top pick-up cartridges compared, 12 pages of in-car entertainment and how an innocent fares on her first hi-fi shopping spree.
OUT MAY 14

30p

Television

June issue : a Decca 10/30 chassis service, a Pye 173 chassis service, a simple grey-scale generator and video-tape copying.
OUT MAY 17

40p

PRACTICAL WOOD WORKING

June issue : a pull-out booklet on hinges and fittings, a model traveller's van, a traditional-style spinster's chair and an ironing table.
OUT MAY 21

40p

Be Practical...Get a 'Practical' Today!

If you are unable to obtain a copy of any of the above titles from your newsagent, please contact :
Sales Manager, IPC Magazines Ltd., 66 Great Queen Street, London, WC2B 5DD

Practical Wireless Classified Advertisements

The pre-paid rate for classified advertisements is 14p per word (minimum 12 words), box number 35p extra. Semi-displayed setting £12.00 per single column inch. All cheques, postal orders, etc., to be made payable to PRACTICAL WIRELESS and crossed "Lloyds Bank Ltd." Treasury notes should always be sent registered post. Advertisements, together with remittance, should be sent to the GMG Classified Advertisement Manager, PRACTICAL WIRELESS, IPC Magazines Ltd., Room 2337, King's Reach Tower, Stamford Street, London SE1 9LS for insertion in the next available issue. (01-261 5846).

Receivers and Components

BRAND NEW COMPONENTS BY RETURN. Electrolytics 16V, 25V, 50V, 0.47, 1.0, 2.2, 4.7, 10mfd.—5p, 22, 47—5½p, (50V—6p); 100—7p, (50V—8p), 220—8p, (50V—10p), 500—11p, (50V—16p), 1000/25V—18p. Subminiature bead-type tantalums, 0.1/35V, 0.22/35V, 0.47/35V, 1.0/35V, 2.2/35V, 4.7/25V—11p, 10/25V, 22/16V, 47/6V, 100/5V—12p. Mylar Film 100V, 0.001, 0.002, 0.005—3p, 0.01, 0.02—3½p, 0.04, 0.05—4p. Mullard C280 series miniature polyester vertical mounting E6 series 0.01—0.1—4p, 0.15, 0.22—5p, 0.33, 0.47—8p, 1.0—15p, 1.5—20p, 2.2—24p. Mullard miniature ceramics 63V, 2%, E12 series 1.8 pf.—47 pf.—3p, 56 pf.—330 pf.—¾p. Plate ceramics 50V E12 series 22 pf.—1000 pf. E6 series 1500 pf.—47000 pf.—2p. Polystyrene 63V E12 series 10 pf.—1000 pf.—3p, 1200 pf.—10000 pf.—4p. Miniature Highstab carbon film resistors ½W E12 series 5% (10% over 1MΩ) 10—10MΩ—1p. IN4148—3p, IN4002—5p, IN4006—7p, IN4007—8p. Postage 10p. Prices VAT inclusive. The C. R. Supply Co., 127, Chesterfield Rd., Sheffield S8.

VALVES

Radio-TV Industrial Transmitting 9200 Types, 1930 to 1975, many obsolete. List 20p. S.A.E. for quotation. Postal export service. We wish to purchase all types of new and boxed valves. Wholesaler's, Dealer's, etc., stocks purchased.

COX RADIO (SUSSEX) LTD. The Parade, East Wittering, Sussex. West Wittering 223

TRIACS (Plastic) TAG250 400V/10A 67p (3+64p); Diacs 19p, 8-pin diol ICs 741 24p, 555 44p, Mini Mains Transformers 100mA 6.0-6V 85p, 12.0-12V 95p, 2N3055 36p, 300W Dimmer Kit £1.95, P&P 15p. Add 8% VAT. T. K. Electronics, 106 Studley Grange Road, London W7 2LX.

All Last Month's Advertised Products Still Available

LEDS W/CLIP 0-125"
TIL209 (Red) 17p MV5374 (Yellow) 22p
MV5174 (Orange) 22p 0.2" Red W/Clip 22p
MV5274 (Green) 22p VAT INC. P&P 20p

Catalogue now ready 15p inc. post
Data and Applications

AUDIO-OPTICS

19, Middleway, Chinnor, Oxon. Tel. 0844 52683

500 COMPONENTS. Resistors, capacitors, diodes, transistors, pots, coils, etc. Identified, formed leads, fall-out, and surplus. Good value at £1.60. All inclusive (U.K. postal rates only). CWO please to L. Penseny, PW Bankhead Farm, South Queensferry, West Lothian.

NEW COMPONENTS BY RETURN. BC109C 12p, BC182L 10p BC184L 11p, BC212L 12p, BC214L 13p, BD529 65p, BD550 65p, BDY56 £1.75, BFR39 35p, BFR79 35p, 2N5457 45p, 2N5459 45p, MPSA12 40p, MC1310P £2.70. Inclusive prices. P & P 10p. All components brand new and guaranteed. I. G. Bowman (Dept PW), 59 Fowey Avenue, Torquay, S. Devon.

COMMUNICATIONS RECEIVER models. Small superhet circuit boards requiring only controls and tuned circuits. 9 volt. Mosfet mixer, IC IF, BFO, Prod. Det. Excellent AM/CW/SSB results reported by delighted users. From £11.50. SAE details. PR Gold-ledge Electronics, Millend, Stonehouse, Glos.

COMPONENTS GALORE, pack of 500 assorted Radio, TV and Electronic components, a real bargain at a realistic price. Send only £1.50 c.w.o. This applies only to United Kingdom and Ireland. Overseas prices by arrangement. Caledonian Components. PO Box 3, Glenrothes, Fife, Scotland.

Precision Polycarbonate Capacitors

All High Stability—extremely Low Leakage			63V DC RANGE		
Value (µF)	Dimen (mm) each	Price	Value µF	±1%	±2%
0.01µF	1	1	0.01µF & 0.1µF	80p	49p
0.02µF	1	1	0.2µF; 0.33µF;	87p	50p
0.1µF	27 12.7	51p	0.47µF	67p	50p
0.15µF	27 12.7	59p	0.68µF	74p	58p
0.22µF	33 16	64p	1.0µF	82p	62p
0.25µF	33 16	67p	1.5µF	89p	71p
0.33µF	33 16	75p	2.2µF	99p	79p
0.47µF	33 19	80p	3.3µF	£1.15	82p
0.5µF	33 19	87p	4.7µF	£1.88	£1.18
0.68µF	50-8 19	98p	6.8µF	£1.96	£1.88
1.0µF	50-8 19	£1.03	10µF	£2.40	£1.95
1.5µF	60-8 26.4	£1.21	15µF	£3.28	£2.79
2.0µF	60-8 26.4	£1.44	22µF	£4.88	£3.68

TANTALUM BEAD CAPACITORS—Value available: 0.1, 0.22, 0.33, 0.47, 0.68, 1.0, 2.2, 3.3, 4.7, 6.8µF at 15V/25V or 35V; 10.0µF 16V/20V or 25V; 22.0µF at 6V/10V or 16V; 33.0µF at 6V or 10V; 47.0µF at 3V or 6V; 100.0µF at 3V. ALL at 12p* each; 10 for £11.00* or 50 for £5.00*. 100 for £9.00*.

TRANSISTORS V.L.C.'s
BC107/8/9 8p *BC212/212L 14p 2N3702/4 11p
*BC114 12p *BC213/213L 11p 2N3055 50p
*BC147/8/9 10p *BC214/214L 11p OC72 12p
*BC183/154 12p *BF194/5 12p NE555Timer 61p
*BC187/8/9 12p *BF194/5 12p 741C spin DIL 741C spin DIL
*BC183/182L 11p BFY50/1/2 20p ZN414 21.15p
*BC183/182L 11p AFY73 80p SNT6018N/2L 50p
*BC184/184L 12p AFY334 35p

POPULAR DIODES—IN914 5p, 8 for 45p, 18 for 80p; IN916 8p, 6 for 45p, 14 for 80p; 1844 5p, 11 for 60p, 24 for £1.00. IN4148 5p, 6 for 27p, 12 for 48p; IN4001 45p; 002 6p; 003 6p; 004 7p; 005 7p; 008 8p; 007 8p

LOW PRICE ZENER DIODES—400mW, Tol. ±5% at 5mA. 3V; 3V3; 3V6; 4V7; 5V1; 5V6; 6V2; 6V8; 7V5; 8V2; 8V7; 10V; 12V; 12V; 13V; 13.5V; 15V; 16V; 18V; 20V; 22V; 24V; 27V; 30V. All at 7p each, 5 for 33p, 10 for 65p. 50 for £3.12. SPECIAL OFFER: 100 Zeners (may be mixed) for £6.00.

RESISTORS—High stability, low noise carbon film 5%, ¼W at 40°C, ½W at 70°C. E12 series only—from 2.2Ω to 2.2MΩ. ALL at 1p* each, 8p* for 10 of any one value, 70p* for 100 of any one value. SPECIAL PACK: 10 of each value 2.2Ω to 2.2MΩ (730 resistors) 25*.

SILICON PLASTIC RECTIFIERS—1.5 amp, wire-ended DO27: 100 P.I.V. 7p (4 for 26p); 400 P.I.V. 8p (4 for 30p); BRIDGE RECTIFIERS—2½ amp: 200V 40p; 350V 45p; 600V 55p.

SUBMINIATURE VERTICAL PRESETS—0-1W only: All at 5p* each 50; 120; 470; 680 ohm; 1K; 2K; 4K; 6K; 10K; 15K; 22K; 47K; 100K; 250K; 500K; 1M; 2M; 5M.

PLEASE ADD 20p POST AND PACKING ON ALL ORDERS. EXPORT—ADD COST OF SFA/AIRMAIL. Add 8% VAT to all items except those marked with * which are 25%.

Send S.A.E. for additional stock lists. Wholesale price lists available to bona fide companies.

MARCO TRADING (Dept. W6).
The Old School, Edinston, Nr. Wem, Shropshire.
Tel: Whitch 464465 (STD 094 872)
(Proprs. Minicost Trading Ltd.)

METAL BOXES / INSTRUMENT CASES. Range of over 100 standard sizes with punched holes to your specification if required. B.M.S. cut to size. Components. Audio equipment, kits and complete. 2 x 6½p stamps for lists. Nottingham Audio Services, 13/15, Foxhall Road, Nottingham NG7 6NA.

3W INTEGRATED AMPLIFIER MA3

- * Po = 3W rms Built-in heatsink
- * T. harm. distortion 0.2% at 2½ W.
- * Fr. response 10Hz—100 KHz 2½ W.
- * Output into 4, 8 or 16 ohms
- * 60mm x 90mm * Data sheet
- * Supply 5/cct, thermal prot.

ONLY £2.97 (P & P 24p)

BEGINNER'S RADIO KIT

- Learn five basic trf radios
- Printed circuit construction
- Clear circuit explanations

ONLY £2.95 (P & P 27p)

NO EXTRA VAT. MAIL ORDER ONLY

HOLME ELECTRONICS

36A Front Street, ARNOLD, Notts.

For Sale

DISCOLIGHTS. Best! Cheapest! Reliable! Bumper catalogue: Aarvak Electronics, 12a(P) Bruce Grove, N17 6RA. 01-808 8923.

MICROPHONES: AKG D202EI, £45.00; AKG D190C or E, £20.00; AKG D224, £60.00; Sennheiser MD211N, £45.00. All brand new and boxed. Please add 25% for VAT. All other AKG and Sennheiser mikes, SAE for quote. J. J. Francis (Wood Green), Ltd., Manwood House, Matching Green, Harlow, Essex. Tel: Matching 476.

COPPER CLAD LAMINATE FOR PRINTED CIRCUITS

Single sided 1/16" paper base—1.5p/sq. inch. Single sided 1/16" glass-epoxy—2.0p/sq. inch. Any rectangular sizes cut to your requirements. Please send cash with order. Price includes postage and packing. From: **SIMTECH ENGINEERING LTD** Dedham Road, Ardleigh, Colchester, Essex, CO7 7QA Telephone 0206 230133

PRACTICAL WIRELESS 1966-1974. 2 missing, £5. Buyer collects. Guildford 73391.

Wanted

WE BUY NEW Valves, Transistors and clean new components, large or small quantities, all details, quotation by return. WALTON'S, 55 Worcester Street, Wolverhampton.

TOP PRICES PAID FOR NEW VALVES and TRANSISTORS

popular T.V. and Radio types.

KENSINGTON SUPPLIES (C).

367 Kensington Street, Bradford 8, Yorkshire.

WANTED LISTS. Prices of Surplus components for mail order. Distribution in Canada, Leishman, 2626 Bates, Montréal, Québec.

SERVICE SHEETS—COLOUR TV SERVICE MANUALS

LARGE SELECTION COVERING MOST MAKES—S.A.E. WITH ENQUIRIES PLEASE TO:

BELL'S TELEVISION SERVICES

190 KINGS ROAD, HARROGATE, N. YORKSHIRE TEL. (CODE 0423) 55885

We also have a large stock of Books & Magazines on Radio, TV, etc. Free lists on request

SERVICE SHEETS—COLOUR TV MANUALS

Service Sheets for Black and White TV, Radios, Record Players and Tape Recorders 50p.
Please send large Stamped Addressed Envelope.

We can supply manuals for most makes of Colour Television Receivers.

B.R.C. PYE ECKO PHILIPS ITT/KB SONY G.E.C. HITACHI BAIRD ULTRA INVICTA etc.

Please send a Stamped Addressed Envelope for a prompt reply.

G. T. TECHNICAL INFORMATION SERVICE
10 DRYDEN CHAMBERS, 119 OXFORD ST., LONDON W1R 1PA
MAIL ORDER ONLY

LARGE SUPPLIER OF SERVICE SHEETS

(T.V., RADIO, TAPE RECORDERS, RECORD PLAYERS, TRANSISTORS, STEREOGRAMS, RADIOGRAMS, CAR RADIOS)
ALL AT 50p EACH

"PLEASE ENCLOSE LARGE S.A.E WITH ALL ENQUIRIES & ORDERS"
Otherwise cannot be attended to

(Uncrossed P.O.s please, original returned if service sheets not available.)

PLEASE NOTE

We operate a "by return of post" service. Any claims for non-delivery should be made within 7-days of posting your order.

C. CARANNA
71 BEAUFORT PARK
LONDON, N.W.11 6BX

We have the largest supplies of Service Sheets (strictly by return of post). Please state make and model number alternative. Free TV fault tracing chart or TV list on request with order.

Mail order or phone 01-458 4882
Large Stocks of Colour Manuals

NO OVERSEAS MAIL PLEASE

SERVICE SHEETS, radio, TV etc. 10,000 models. Catalogue 24p, plus SAE with orders, enquiries. Telray, 154 Brook Street, Preston PR1 7HP.

BELL'S TELEVISION SERVICES for service sheets, manuals & books on radio/TV etc. Service sheets 50p plus SAE. Service sheet catalogue 25p. Back issues of magazines from April '74 onwards cover price plus 12p post. Free booklists on request. SAE with enquiries please to B.T.S., 190 Kings Road, Harrogate, Yorkshire. Telephone Harrogate (code 0423) 55885.

SERVICE SHEETS for Radio, TV, Tape Recorders, Stereo, etc., with free fault-finding guide, 50p and SAE, Hamilton Radio, 47 Bohemia Road, St. Leonards, Sussex.

Educational

TAPETALK

THE CLEVER WAY TO LEARN

TWO C60 Cassettes entitled
INTRODUCING ELECTRONICS
£5.44 plus 55p VAT/P. & P.

TAPETALK, P.O. Box 99 (PW)
Milton Keynes MK3 5BR
Tel.: Milton Keynes (0908) 77710

Educational

TELEVISION TRAINING

16 MONTHS' full-time practical and theoretical training course in Radio and TV Servicing (Mono and Colour) for beginners with GCE (or equivalent) in Maths, and English.

13 WEEKS' full-time Colour TV Servicing course. Includes 100 hours practical training. Mono revision if necessary. Good electronics background essential. NEXT SESSION commences on September 13th.

Prospectus from: London Electronics College, Department B6, 20 Penywern Road, London SW5 9SU. Tel. 01-373 8721.

GO TO SEA as a Radio Officer. Write: Principal, Nautical College, Broadwater, Fleetwood FY7 8JZ.

C AND G EXAMS

Make sure you succeed with an ICS home study course for C and G Electrical Installation Work & Technicians Radio/TV/Electronics Technicians, Telecommunications Technicians and Radio Amateurs.

COLOUR TV SERVICING

Make the most of the current boom! Learn the techniques of servicing Colour and Mono TV sets through new home study courses, approved by leading manufacturers.

TECHNICAL TRAINING

Home study courses in Electronics and Electrical Engineering, Maintenance, Radio, TV, Audio, Computer Engineering and Programming. Also self-build radio kits. Get the qualifications you need to succeed.

Free details from:

INTERNATIONAL CORRESPONDENCE SCHOOLS,
Dept. 778T, Intertext House, London SW8 4UJ.
Or Phone 01-622 9911 (All Hours)

Ladders

LADDERS. Varnished, 25½ ft extended, £24.05, carriage £1.40. Leaflet, aluminium ladders and loft stairways. Tel: Telford 586644.

Books and Publications

Technical Books—Radio & Electronics

World's Radio & TV Stations (International Edit.)	£0-70
WORLD RADIO TV HANDBOOK 1976	
(Incorporating How to listen to the World)	£5-00
Boys Book of Crystal Sets	£0-35
Resistor Selection Handbook	£0-68
Audio Hi Fi Construction Projects	£0-95
How to get the best out of your Tape Recorder	£1-70
Practical Electronic Science Projects	£0-85
Jack Darr's Service Clinic	£1-60
Transistor Circuits for Modern Test Equipment	£0-70
Modern Tape Recording Handbook	£0-85
1st Book of Transistor Equip. and Substitutes	£0-80
Hi Fi, PA & Disco Amplifier Design Handbook	£0-87
Radio Servicing Problems	£0-75
Electronic Circuits for the Amat Photographer	£0-70
52 Projects using IC 741 or Equiv	£0-85
TV Fault Finding	£1-15
Transis Circuits for Rad. Control Models	£0-50
Practical Stereo & Quadrophony Handbook	£0-85
Radio Amateur Operator's Handbook	£0-85
Coin Design & Construction Manual	£0-60
Radio TV & Electronics Data Book	£0-70
79 Electronic Novelty Circuits	£0-85
The Complete Car Radio Manual	£0-95
Radio Technicians Bench Manual	£3-40
Servicing Transistor Radio Receivers	£0-95
1st Book of Hi Fi Loudspeaker Enclosures	£0-70
2nd Book of Hi Fi Loudspeaker Enclosures	£0-70
Manual of Electronic Circuits for the Home	£0-60
Modern Crystal Set Circuits for Beginners	£0-45
Electronic Novelties for the Motorist	£0-60
2nd Book of Transistor Equip. & Substitutes	£1-10
Handbook of Electronic Musical Novelties	£0-60
Transistorised Novelties for Hi Fi Enthusiast	£0-45
Fault Location Exercises in Rad. & TV Vol. 1	£1-00
Fault Location Exercises in Rad. & TV Vol. 2	£1-60
Colour TV Picture Faults	£2-80
Practical Transistor Novelty Circuits	£0-50
Boys Book of Practical Radio & Electronics	£0-70
Radio Receiver Construction using ICs & Transis.	£0-70
ICs & Transistor Gadgets Construction Handbook	£0-70
Integrated Circuits Equip. & Substitutes Handbook	£0-85
Radio Technicians Bench Manual	£3-40
Radio Antenna Handbook for Long Dist. Receptn.	£0-90
Guide to Printed Circuits	£3-40
Diode Characteristics Equip. & Substitutes	£1-10
Electronic Gadgets & Games	£0-90
PRICES INCL. POST & PACKING	Send S.A.E. for Lists

RADIO BOOK SERVICE
40 Elwill Way, Beckenham BR3 2RZ

LOGIC. Reliable step-by-step design techniques for the non-specialist are described in a new Oxford book, "Problems and Solutions in Logic Design" by D. Zissos (1976). Over 50 problems with fully worked out solutions demonstrate the design steps. Obtainable from Booksellers £3.50 paper covers £1.75.

START YOUR OWN BUSINESS REWINDING ELECTRIC MOTORS

This unique instruction manual shows step by step how to rewind motors, working part or full time, without previous experience. Everything you need to know easily explained, including where to obtain materials, how to get all the work you need, etc. A goldmine of information and knowledge.

Only £3.65 plus 25p P&P.

Magnum Publications Dept PW5

Brinksway Trading Estate, Brinksway, Stockport SK3 0BZ.

Overseas Distributors wanted.

Courses

The Polytechnic of North London

Department of Physics B.Sc (Hons) THE PHYSICS & TECHNOLOGY OF ELECTRONICS

A sandwich course offering specialisation in Microwave Physics, or Theory and Practice of Computers, or Electrical Processes in Gases and Associated Spectroscopy.

HNC IN APPLIED PHYSICS

2-year day-release course with special topics in electronics.

CERTIFICATE OF SUPPLEMENTARY STUDY

3 one-term day-release courses (Further Electronics, Nuclear Radiation and Counting Techniques, Experimental Atomic Spectroscopy).

Details of these courses from: The Head of the Physics Dept. (Ref. PW1) THE POLYTECHNIC OF NORTH LONDON, Holloway Road, London, N7 8DB (Tel: 01-607 6767 Ext. 305).

Electrical

STYLI & CARTRIDGES. For the best at keenest prices send SAE for free illustrated list to Felstead Electronics (P/W), Longley Lane, Gatley, Ches. SK8 4EE.

Miscellaneous

PRINTED CIRCUITS and HARDWARE

Readily available supplies of Constructors' hardware, Aluminium sheet and sections. Printed circuit boards, top quality for individual or published designs. Prompt service. Send 15p for catalogue.

Ramar Constructor Services,
Masons Road, Stratford on Avon,
Warwicks. Tel. 4879

ENAMELLED COPPER WIRE

S.W.G.	1 lb reel	½ lb reel
10 to 19	2.40	1.35
20 to 29	2.45	1.40
30 to 34	2.60	1.50
35 to 40	2.85	1.60

All the above prices are inclusive of postage and packing in U.K.

COPPER SUPPLIES

102 Parrswood Road, Withington,
Manchester 20 Tel: 061-445 8753

MINI ACCUMULATORS



2 volt MULTI-USE Sealed Lead Acid Rechargeable Cells.
Size L450-1.4" X 1.1" X .44" 3 for £2.15
inc. P. & P.
Size GA2-1.7" X 1.3" X .5" 3 for £2.65
inc. P. & P.

Suits Fit-Cord
GARFIELDS, 295 Rye Lane, London, S.E.15

NICKEL CADMIUM fully sealed re-chargeable batteries. Equivalent dry cell sizes. Discount. S.A.E. brings full details by return. Charges available. Sandwell Plant Ltd., 1 Denholm Road, Sutton Coldfield, West Midlands, B73 6PP. 021-354 9764.

12 VOLT FLUORESCENTS

35% OFF
RRP

MADE BY THORN LIGHTING. Ideal for Caravan, Boat, Tent, Emergency Lighting etc. All lamps guaranteed for 12 months.

21 ins
13 watt
£4.90



12 ins
8 watt
£4.00

All lamps have On/Off Switch, Wrong Polarity Protection Device and Diffuser.

C60 CASSETTES 32p All Cassettes in Plastic Case with Index and Screwed Assembly.
C90 CASSETTES 45p

All prices include VAT. Add Postage 5p in £1.

Quantity Discounts.
10 Units 5%
50 Units 7%
100 Units 10%

SALOP ELECTRONICS
23 WYLE COP
SHREWSBURY
Tel. 53206

COLCHESTER COMPONENTS SHOP.
Now open Sunday-Thursday 12-6 p.m.
J. K. Electronics, 11 Mersea Road,
Colchester 64433.

BUILD YOUR OWN

You are invited to send S.A.E. for lists of our very extensive range of high quality amplifier, pre-amps, F.M. tuners, instruments. Radiocontrol ignition units and many other kits. Please state requirements.

TELERADIO ELECTRONICS,
325 FORE STREET, EDMONTON,
LONDON N9

Synthesiser "Sounds Supreme"

by **Dewtron** (25% VAT extra.)

Famous kits, e.g. waa-waa complete kit £4.50; Fuzz kit £6.50 P&P 25p under £10. Ring Modulator modules £11. "Mister Bassman" Bass Pedal Units and whole range of synthesiser modules, musical novelties, etc. Catalogue 20p from D.E.W. Ltd., 254 Ringwood Road, Ferndown, Dorset.

ALUMINIUM SHEET AND BOXES cut and folded to your design. Sheet: 22, 20, 18 S.W.G. 0.3p/sq inch; 16, 14 S.W.G. 1p/sq inch. Boxes: 22, 20, 18 S.W.G. 1p/sq inch; 16 S.W.G. 1.2p/sq inch; 14 S.W.G. 2p/sq inch. Maximum length of any side: 2ft. Maximum depth of box: 1 ft. Please add 8% VAT. P&P 25p per item. SAE for special quotes (UK only). Trade enquiries welcomed. Simtec Electronics (UK) Ltd., Unit 37, Faircharm Trading Estate, St. Mary's Mills, Leicester. Tel: (0533) 824380.

SUPERB INSTRUMENT CASES by Bazelli, manufactured from heavy duty PVC faced steel. Hundreds of people and industrial users are choosing the cases they require from our vast range, competitive prices start at a low 75p. Examples: width, depth, height, 8in x 5in x 3in, £1.55; 10in x 6in x 3in, £2.20; 12in x 6in x 3in, £2.70; 14in x 6in x 3in, £2.95; 10in x 8in x 3in, £2.75; 12in x 8in x 3in, £3.20; 14in x 8in x 3in, £3.60; 12in x 10in x 3in, £3.60; 8in x 4in x 4in, £1.80; 10in x 6in x 4in, £2.70; 12in x 6in x 4in, £2.85; 14in x 6in x 4in, £3.25; 12in x 8in x 4in, £3.60; 14in x 8in x 4in, £3.80; 7in x 7in x 5in, £2.65; 8in x 10in x 6in, £3.60; 12in x 8in x 7in, £4.00; 14in x 8in x 7in, £4.80; 12in x 10in x 7in, £4.25; 12in x 12in x 7in, £4.40; 14in x 10in x 7in, £5.00; 12in x 10in x 8in, £5.00; 14in x 10in x 8in, £5.30; 14in x 12in x 7in, £5.20; 12in x 12in x 8in, £5.50; 14in x 12in x 8in, £5.80. Plus 72p carriage and 8% VAT. 16in x 8in x 8in, £7.60; 16in x 10in x 8in, £8.40; 18in x 8in x 8in, £9.50; 18in x 10in x 8in, £10.30; 19.4in x 8in x 8in, £11.50; 19.4in x 10in x 8in, £12.30. Plus carriage £1.25 plus 8% VAT. Over 400 models to choose from. Prompt despatch. Free literature (stamp would be appreciated), Bazelli, Dept. No. 25, St. Wilfrid's, Foundry Lane, Hailton, Lancaster LA2 6LT.

RECORD from TV

Make **SOUND RECORDINGS** from a TV set using this

ADAPTOR

with your cassette recorder, or use it with your

Hr. Fi or headphones. Completely Safe, Fully Isolated. Leads, connectors and full instructions included. £6 inc post and VAT or write for leaflet.

CROWBOROUGH ELECTRONICS
(P/W) Eridge Road, Crowborough,
Sussex

GLASS FIBRE P.C.B.s. Send 1:1 master and 7p per square inch tinned or 9p per square inch drilled and tinned PLUS 30p per board. Send for quotation on double sided boards. Discount for quantity. **PROTO DESIGN,** 4 Highcliffe Way, Wickford, Essex SS11 8LA.

LOOKING FOR BARGAINS

Light Dimmer 500W module with knob £1.99*
LM380 2W Audio Amplifier 14 pin DIL 79p
LM555CN Timer 8 pin DIL 42p*
723 Voltage Regulator 2 - 37 Volt 44p*
CA3085E FM IF system 16 pin DIL £1.99
CA3080AQ Stereo Decoder 16 pin QIL £4.22
Please add 12½% VAT (*8%) and 15p postage or send SAE for catalogue to:-

FRASER-MANNING LTD.

26 HERVEY STREET, IPSWICH, SUFFOLK

ILB PACKS of assorted copper laminates for 60p plus p/p 30p. Cash with order to Crossley & Bradley, 248 Slater Lane, Leyland, Lancs.

HELME

DO-IT-YOURSELF
HI-FI STEREO
SPEAKER KITS

The best value around!
Send for details
HELME AUDIO PRODUCTS LTD.
Dept. P.W.
SUMMERBRIDGE
HARRGATE YORKS

Tel: Barley 279 (Std Code 0423-72)

TEXAN AMPLIFIER PARTS

Pack 1 Res. 80p, Packs 2-3 Caps. £3-50, Pack 5 Switches £1-50, Pack 6 Pots. £1-50, Pack 7 Semi Conductors. £8-25, P.C. Board £3-00, Front Panel £2-50, Chassis £3-00, Case £4-50, p.p. extra 25p except chassis 50p and case £1-00. Tax extra 25%. Send S.A.E. for details of this and other amplifiers from 1 watt-100 watt.

TELERADIO ELECTRONICS
325, FORE STREET, LONDON, N.9.
01-807-3719



TREASURE TRACER MK III Metal Locator

- Varicap tuning
- Britain's best selling metal locator kit, 4,000 sold
- Weighs only 22oz. Fitted with Faraday shield.
- Speaker and earphone operation
- Knocks down to only 17in.
- Prebuilt search coil assembly
- Thoroughly professional finish
- As seen on BBC1 and BBC2 TV
- You only need soldering iron, screwdriver, pliers and snips
- Five transistor circuit

Complete Kit **£12-50** Built & tested **£17-50**
Post 85p + £1-00 VAT 8%, Post 85p + £1-40 VAT 8%

MINIKITS ELECTRONICS,
6a CLEVELAND ROAD,
LONDON, E18 2AN (Mail order only)

LOW-COST I.C. MOUNTING for any size DIL package. 100 Soldercon sockets 60p. 7 and 8 hole plastic supports 5p/pair. Quantity rates. SAE details and sample. Trial pack 60p. (P & P 10p/order). P.K.G. Electronics, Oak Lodge, Tansley, Derbyshire DE4 5FE.

THE SCIENTIFIC WIRE CO

Copper - Nickel Chrome - Eureka - Manganin Wires.
Enamelled - Silk - Cotton - Tinned Coverings.
No minimum charges or quantities.
Trade and Export enquiries welcome.
S.A.E. Brings List.
P.O. BOX 30, LONDON, E4 9BW

TRANSMIT!

★ Unique **TRANSMITTER/RECEIVER** Kit. No licence examinations or tests required to operate this transistorised equipment. Easy to build. Get transmitting. Send **£7-95** for yours now!

★ Psychedelic **MINI-STROBE** Kit. Take a pocket-sized lightning storm to Disco's & parties. 'Brain-freeze' 'em with vari-speed stop-motion flashes. Includes super case too. Send **£3-50** now!
(all prices include V.A.T., packing & postage.)

Send remittance to:
BOFFIN PROJECTS,
4 CUNLIFFE ROAD,
STONELEIGH, EWELL, SURREY
(Mail order U.K. only)
Or for more details, send 20p for lists

RADIO. Learn from the beginning. 16 vintage circuit diagrams, receivers and transmitters with notes. £1. Allister, 58 Wavell Road, Maidenhead, Berks, SL6 5AD.

H. M. ELECTRONICS

275a FULWOOD ROAD, BROOMHILL, SHEFFIELD S10, 3BD.

REC. CABINETS (illus'd)



METAL CASES
DRY TRANSFER LETTERING
Send 15p for leaflets (Refundable)
Trade enquiries invited

VAT INCLUSIVE PRICES

Add 20p P & P - No other extras

Fully branded devices from RCA, TEXAS, MOTOROLA, MULLARD, etc.

TTLs by TEXAS

7400	13p	7484	103p
74H00	20p	7485	130p
7401	15p	7486	150p
7402	15p	7489	291p
7403	17p	7490	36p
7404	17p	7491	81p
74H04	22p	7492	48p
7405	17p	7493	43p
7406	32p	7494	81p
7407	32p	7495	80p
7408	17p	7496	84p
7409	22p	7497	291p
7410	15p	74100	116p
74H10	20p	74107	32p
7411	24p	74118	90p
7412	25p	74121	32p
7413	34p	74122	52p
7414	65p	74123	73p
7416	32p	74126	75p
7417	32p	74132	75p
7420	15p	74138	81p
7421	42p	74141	82p
7422	19p	74145	75p
7423	36p	74148	173p
7425	33p	74150	135p
7427	40p	74151	77p
7428	39p	74153	92p
7430	16p	74154	164p
7432	28p	74155	82p
7437	28p	74156	82p
7440	15p	74160	107p
7441	70p	74161	107p
7442	64p	74162	107p
7443	11p	74163	107p
7444	116p	74164	130p
7445	81p	74166	136p
7446	75p	74174	131p
7447	75p	74175	92p
7448	75p	74176	131p
7450	18p	74177	108p
7451	16p	74180	107p
7453	17p	74181	322p
7454	18p	74182	89p
7460	16p	74185	146p
7470	29p	74190	155p
7472	27p	74191	156p
7473	32p	74192	135p
7474	32p	74193	30p
7475	40p	74194	116p
7476	32p	74195	83p
7480	54p	74196	99p
7481	103p	74197	108p
7482	75p	74198	107p
7483	85p	74199	197p

TRANSISTORS

AC125	18p
AC126	18p
AC127	13p
AC128	12p
AC176	12p
AC187	14p
AC188	14p
AD148	60p
AD161	39p
AD162	39p
AF114	18p
AF115	18p
AF116	18p
AF117	18p
AF139	35p
AF139	35p
BF239	43p
BC107	10p
BC108B	10p
BC109C	11p
BC148	9p
BC149	9p
BC149	9p
BC157	11p
BC158	13p
BC159	13p
BC169C	11p
BC171	15p
BC172	15p
BC173	13p
BC177	20p
BC178	17p
BC179	20p
BC183	12p

BC184

14p	BFR30	37p	TIP30C	72p	40584	81p
32p	BFR40	37p	TIP31A	56p	40585	81p
12p	BFR70	37p	TIP31C	68p	FETs	92p
12p	BFR80	37p	TIP32A	68p	B244	45p
17p	BFR88	37p	TIP32C	85p	MPF102	37p
14p	BC337	24p	TIP33A	97p	MPF103	37p
32p	BC478	28p	TIP33C	120p	MPF104	37p
20p	BCY70	20p	TIP34A	12p	MPF105	37p
24p	BCY71	24p	TIP34C	160p	2N3819	27p
100p	BD133	100p	TIP35A	22p	2N3902	50p
39p	BD124	70p	TIP35C	290p	2N3933	50p
39p	BD131	39p	TIP36A	297p	2N5457	32p
43p	BD132	43p	TIP36C	360p	2N5458	32p
18p	BD135	54p	TIP41A	70p	2N5459	32p
55p	BD136	55p	TIP42A	76p	3N128	81p
79p	BD139	79p	TIP295	76p	3N140	92p
18p	BSX20	18p	TIP108	14p	3N141	81p
17p	BU105	17p	ZTX300	16p	40603	63p
25p	BU106	312p	ZTX500	19p	40673	54p
27p	BU173	27p	MJ2955	81p	2N697	14p
28p	MJ2955	107p	2N698	32p	2N1260	86p
30p	MJ3055	70p	2N706	13p	2N2646	38p
35p	MPSA06	37p	2N708	19p	2N4871	37p
35p	MPSA12	62p	2N918	43p	PUJT	50p
35p	MPSU06	76p	2N930	19p	2N6027	60p
24p	OC28	70p	2N1132	19p	DIODES	
24p	OC35	24p	2N1304	23p	SIGNAL	
19p	OC41	19p	2N1305	23p	OA47	9p
19p	OC42	19p	2N1306	30p	OA81	10p
19p	OC45	19p	2N1307	30p	OA85	11p
25p	OC71	25p	2N1613	22p	OA90	7p
40p	TIP29C	40p	2N1711	22p	OA91	9p
60p	TIP30A	60p	2N1933	22p	OA92	9p
			2N2219	22p	OA200	7p
			2N2220	19p	OA202	10p
			2N2221	22p	1N914	4p
			2N2222	22p	1N916	11p
			2N2369	15p	1N4148	4p
			2N2434	30p	BRIDGE	
			2N2904	22p	BY100	31p
			2N2905	22p	BY126	15p
			2N2906	22p	BY127	15p
			2N2928RB	91p	1N4001	6p
			2N2928GG	11p	1N4002	6p
			2N3053	19p	1N4004	7p
			2N3054	43p	1N4005	7p
			2N3055	54p	1N4007	8p
			2N3439	72p	ZENER	
			2N3442	151p	2-7 to 33V	
			2N3702	14p	400mW	11p
			2N3703	14p	1W	22p
			2N3704	14p	TUNNEL	
			2N3705	14p	AEY11	75p
			2N3706	12p	VARICAP	
			2N3708	11p	BB105	33p
			2N3709	11p	NOISE	
			2N3707	4p	Z5J	140p
			2N3773	240p	BRIDGE	
			2N3866	90p	RECTIFIERS	
			2N3904	22p	1A 50V	25p
			2N3905	22p	1A 100V	27p
			2N3906	22p	1A 400V	28p
			2N4058	19p	W04	28p
			2N4060	19p	2A 50V	40p
			2N4123	22p	2A 100V	56p
			2N4124	22p	2A 400V	50p
			2N4125	22p	4A 100V	75p
			2N4126	22p	6A 50V	65p
			2N4369	90p	5A 50V	70p
			2N4371	142p	TRACOR	
			2N4348	173p	Amp Voids	
			2N4401	34p	3 400	130p
			2N4403	34p	6 400	162p
			2N5089	34p	6 500	194p
			2N5401	62p	10 400	200p
			4036A	40p	50 270p	
			40381	41p	40430	108p
			40382	43p	40486	108p
			40410	59p	40669	105p
			40409	59p	DIAC	
			40411	243p	BR100	27p

OP. AMPS

301A	Ext. Comp. 8 pin DIL	40p
5367	FET Op. Amp TO 99	300p
Ext. Comp. 8/14 pin DIL	30p	
Ext. Comp. 14 pin DIL	70p	
Int. Comp. 8/14 pin DIL	25p	
Dual 741 14 pin DIL	74p	
Ext. Comp. 8 pin DIL	40p	
Prog. Op. Amp TO 99	153p	
Dual Op. Amp. 8 pin DIL	75p	
CMOS/Bipolar Mosfet	108p	
Quad. Op. Amp. 14 pin DIL	69p	

LINEAR I.C.s.

CA 302A	Diff. Cascade Amp. To 99	112p
CA 3046	5 Transistor Array 14 pin DIL	55p
CA 3048	Quad. Low Noise Amp. 16 pin DIL	250p
CA 3053	Diff. Cascade Amp. TO5/DIL	45p
CA 3089E	FM IF System 16 pin DIL	250p
CA 3090AQ	FM Stereo Decoder QIL	500p
ICL3038BC	VCO Function Generator 16 pin DIL	600p
ICL3038CC	VCO Function Generator 16 pin DIL	300p
LM 388N	2W Audio Amplifier 14 pin DIL	115p
LM 381N	Stereo Pre Amp 14 pin DIL	200p
MC1310	FM Stereo Decoder 14 pin DIL	228p
MC1498	Bal. Mod/Demod 14 DIL	100p
MFC4000B	3W Audio Amplifier PCB	135p
MFC6040	Electronic Attenuator PCB	75p
NE555V	Timer 8 pin DIL	40p
NE556	Dual 555 14 pin DIL	108p
NE561B	PLL with AM Demod 16 pin DIL	350p
NE562B	PLL with VCO 16 pin DIL	350p
NE565	PLL 14 pin DIL	200p
NE566V	PLL Function Gen 8 pin DIL	165p
NE567V	PLL Tone Decoder 8 pin DIL	200p
2567	Dual 567 15 pin DIL	400p
SN72733	Video amplifier 14 pin DIL	150p
SN7333N	Audio Pwr Amp with int HS	150p
SN76023N	Audio Pwr Amp with int HS	175p
TA5A61B	FM IF Amp Lim/Detector QIL	150p
TBA641B	Audio Amp QIL	100p
TBA800	5W Audio Amp QIL	32p
TBA810	7W Audio Amp QIL	125p
TBA820	2W Audio Amp QIL	100p
TDA2020	20W Audio Amp QIL	405p
XR2240	Prog Timer/Counter 16 pin DIL	400p
ZN414	TRF Radio Receiver TO18	140p

Basic data sheet on above ICs at 10p each + S.A.E.

OPTO-ELECTRONICS

LEDs	TIL209 Red	15p
LEDs	TIL211 Green	32p
LEDs	TIL32 Infrared	81p
OCPT70	33p	
OCPT71	120p	
OCPT77	43p	
ORs	0-2"	
ORP12	60p Red	17p
ORP60	75p Green	29p
ORP61	75p Yellow	32p

SEVEN SEGMENT DISPLAYS

3015	Minitoron 0.3"	130p
DL704	Com. Cathode 0.3"	160p
DL707	Com. Anode 0.3"	160p
DL747	Com. Anode 0.6"	250p

OPTO-ISOLATORS

Phototransistor TIL12 (IL 12)	6 Pin DIL	151p
Photodarlington ILCAS5 6 Pin DIL		270p
DRIVERS		
7549	Quad Segment Driver 14 Pin DIL	

CHOKE Miniature 100mH 80p	FOOT SWITCH* 1. Pedal £2.80	Connectors* Snap on PP3 6p Snap on PP3 9p	JACK PLUGS	SOCKETS
			Screened chrome 19p	Plastic body 3p
			Open metal 5p	Moulded with break contacts 17p
			2.5mm 14p	3.5mm 12p
			Std. MONO 15p	Std. STEREO 12p
KNOB* fits 1/4" shaft with grub screw, except K2 (push fit) & K6 (for sliders)			DIN 2 pin Loudspeaker 3, 4, 5 (180° & 240°)	Plugs 12p
K1 Black or White pointer type K2 Slim silvered aluminium K3 Black serrated. Metal top with line indicator 33mm diam. K4 As above but 25mm diam. K5 Black fluted metal top and skirt calibrated 0-10, 37mm diam. K6 PK2 as K5, pointer on skirt K7 Black, knurled, tapered. Metal top & skirt. Calib. 0-10, 30mm K8 Black or silvered for slider pot	3p 10p 20p 10p 22p 22p 8p		SOCKETS	5p (Single) 7p (Double) 10p (Triple) 7p
PANEL METERS* Full scale 59 x 46 x 35mm red, 1 1/4" hole			CO-AXIAL (TV)	10p
0-50µA 0-100mA 50µA-0-50µA 0-100µA 0-500mA 100µA-0-100µA 0-500µA 0-1 Amp 500µA-0-500µA 0-1mA 0-50V DC £3-95 each 0-3mA 0-300V DC 0-10mA "S" 0-50mA "VU"	£2.85 each Price £4.14 108 x 32.5 x 38mm red, 60mm panel hole 0-50µA; 0-100µA; 0-500µA £3-45		PHONO assorted colours Metal screened	7p 12p
TRANSFORMERS (Mains Prim. 220-240V)			BANANA 4mm 2mm	12p 7p
6-0-6V 100mA 30p 9-0-9V 100mA 30p 12-0-12V 100mA 30p 15-0-15V 100mA 195p 0-12 0-12V 150mA 160p 0-6 0-6V 280mA 170p 0-12 0-12V 500mA	237p+ 119p 119p £3-45+ 160p 170p 195p+		LAMP HOLDERS AND LAMPS*	
24-0-24V 500mA 180p 9-0-9V 1A* 198p 12-0-12V 1A* 185p 15-0-15V 1A* 198p 18-0-18V 1A* 230p 30-24-20-15-12-0 1A Multi tappings 285p+ 6-0-6V 1.5A* 180p+	ITT Pulse Transformer Miniature 110p LT44 Mini. Driver. Pri. 20K, Sec. 1K 54p LT700 Min. O/P Pri. 1.2K, Sec. 3/2.0 54p MOT Min. O/P Pri. 1.2K, Sec. 8Ω 42p		LES HOLDER Dome shaped, Red, Blue, Green, Yellow, White LES BULBS 6v and 12v MES HOLDERS Chrome cover, Red or Amber, jewelled top MES BULBS 3.5V 6V 12V NEONS Mains Sealed with Resistor. So. Top, Red or Gn, Round Top Red 21p Neon with leads. 95V AC (No resistor) 9p	14p 7p 50p 7p
			SWITCHES	SLIDE 250V:
			TOGGLE 2A, 250V	1A DP C/O 10p
			SPST 21p	1A DP C/O 15p
			DPDT 27p	1A DP 9p
			SUB-MIN TOGGLE	PUSH BUTTON
			SP changeover 45p	Spring loaded
			SPST on/off 40p	SPST on/off 55p
			DPDT 6 tag 64p	SPST C/over 65p
			DPDT Centre off 80p	DPDT 6 Tag 85p
			SWITCHES* PUSH BUTTON:	
			Miniature Non Locking	
			Push to Make	15p
			Push to Break	25p
			ROCKER (white): 10A 250V	
			SP changeover centre off	25p
			ROCKER : (black) on/off 10A 250V	20p
			ROCKER : Illuminated (white)	
			lights when on. 3A 240V	46p
			ROTARY : (ADJUSTABLE STOP) 1 pole; 2-12 way, 2p; 2-6V, 3p; 2-4V, 4p; 2-3W 22p	
			ROTARY : Mains 250V AC, 4 Amp 27p	

**TECHNICAL TRAINING IN
ELECTRONICS TELEVISION
AND RADIO SERVICING**

ICS can provide the technical knowledge that is so essential to your success, knowledge that will enable you to take advantage of the many opportunities open to the trained person. You study in your own home, in your own time and at your own pace and if you are studying for an examination ICS guarantee coaching until you are successful.

- City & Guilds Certificates:**
Telecommunications Technicians
Radio, TV, Electronics Technicians
Technical Communications
Radio Servicing Theory
Radio Amateurs
Electrical Installation Work
MPT Radio Communications Certificate

- Diploma Courses:**
Colour TV Servicing
Electronic Engineering and Maintenance
Computer Engineering and Programming
Radio, TV, Audio Engineering and Servicing
Electrical Engineering, Installation and Contracting

POST OR PHONE TODAY FOR FREE BOOKLET.

ICS To: International Correspondence Schools

Dept. No. 7777, Intertex House, LONDON SW8 4UJ or telephone 622 9911

Subject of Interest _____
 Name _____
 Address _____
 Tel: _____

INDEX TO ADVERTISERS

Alben Engineering	176
Ambit International	136
A.S.P. Ltd.	132
Astro Electronics	116
Audio-Optics	186
A.H. Supplies	110
Bamber, B.	178
Barclay Electronics	117
Barrie Electronics	112
Bell's Television Services	187
Bentley Acoustic Corp. Ltd.	104
B. H. Component Factors Ltd.	168
Bi-Pak Ltd.	106, 107
Bi-Pre-Pak Ltd.	111, 180
Birkett, J.	118
Boffin Projects	189
British Institute of Engineering Technology	108, 159
British National Radio & Electronics School	163, 172, 181
J. Bull (Electrical) Ltd.	171
Bush & Meissner	182
Butterworths	132
Bywood Electronics	180
C.D.I. Ltd.	184
Caranna, C.	187
C. J. L. Ltd.	176
Cleveland Supplies	178
Colomor (Electronics) Ltd.	176
Copper Supplies	188
Cox Radio (Sussex) Ltd.	186
Crescent Radio Ltd.	114
Crofton Electronics	182
Crowborough Electronics	188
D.E.W. Ltd.	188
Doram Electronics	131
Dziubas, M.	159
Electronics Design Associates	118
Electronics Mail Order Ltd.	184

Electro-Tech Components	177
Electro-Time	183
Electrovalue Ltd.	114
Elliott Blunt Audio	102
Elvis Electronic Musical Instruments	109
Flairline Supplies	192
Fraser-Manning Ltd.	188
G.T. Technical Information Service	187
Garfields	188
Greenbank Electronics	184
Greenwell Electronics	108
Greenway Electronics	182
H.A.C. Short-Wave Supplies	180
H.M. Electronics	189
Harversons Surplus	103
Heathkit	112, 135
Helme Audio	188
Henry's (Radio) Ltd.	110
Holme Electronics	186
I.L.P. Electronics Ltd.	113
Intertex I.C.S.	187, 191
Kensington Supplies	186
Kinnie Components	116
K.K.S. Trading	164
Kramer	180
Lasky's Radio	98, 102
Lewis Radio	118
Linear Products	162
London Electronic College	187
Lynx Electronics	162
Mack's Electronics	179
Magnum Publications	187
Manor Supplies	176
Maplin Electronic Supplies	cover iv
Marco Trading	186
Marshall, A. & Sons	181
Milward, G. F.	159
Minikits Electronics	189
Multicore Solders (Bib Hi-Fi)	164

Newmart Electronics	109
Orchard Electronics	164
Partridge Electronics Ltd.	182
P.B. Electronics	177
Polytechnic of North London	188
Pulse Electronics	104
Precision Petite	168
Radio Component Specialists	175
Radio Book Service	187
Radio Exchange Ltd.	cover iii
Ramar Construction Services	188
Radio Society of G.B.	136
R.S.C. (Hi-Fi)	98, 99
R.S.T. Valve Mail Order Co.	115
Radio & T.V. Components Ltd.	100, 101
Riversdale	102
Salop Electronics	188
Saxon Entertainments Ltd.	167
Scientific Wire Company, The	189
Simtech Engineering Ltd.	186
Sintel	108
Southern Valve Co.	178
Surplronics	168
Swanley Electronics	172
Tape Talk	187
Technomatic Ltd.	189
Teleradio Electronics	188, 189
Time-Micro Electronics	119
Trampus Electronics	cover ii
Vero Electronics	172
Viking Brews	109
Watford Electronics	190, 191
West London Direct Supplies	192
Wilmslow Audio	105
Wrights, S. G.	114
Xeroza Radio	119
Z. & I. Aero Services	192


Head Office and Warehouse
44A WESTBOURNE GROVE
LONDON W2 5SF
Tel: 727 5641/2/3

Z & I AERO SERVICES LTD.

Retail Shop
85 TOTTENHAM COURT ROAD
LONDON W1
Tel: 580 8403
Open all day Saturday

Please send all correspondence and Mail-Orders to Head Office

MULTIMETERS—MADE IN USSR

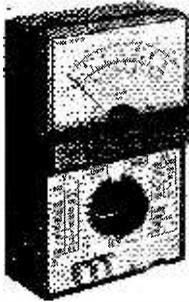

AC/DC MULTIMETER TYPE U4324
33 ranges covering
D.C. current
60μA to 3A;
AC current
300μA—3A;
DC voltage: 0·6—1200V
AC voltage: 3—900V
Resistance:
500Ω—500kΩ
Level: -10 to +12db
Sensitivity:
20,000 o.p.v. DC.
4,000 o.p.v. A.C.

Instrument is powered by re-chargeable nickel cadmium batteries.
PRICE £10·85*



AC/DC MULTIMETER TYPE U4315
42 ranges covering:
D.C. current
50μA—2·5A; A.C.
current: 500μA—2·5A; AC/DC
voltage: 1—1000V;
Resistance 300Ω—500kΩ; Capacity up
to 0·5μF; Transmission level: -15 to +2db;
Sensitivity: 20kΩ/V DC, 2kΩ/V AC.
PRICE £11·25*

TRANSISTORS FOR T.V. APPLICATIONS

R2008B	0·95	BU133	1·55
R2010B	1·65	BU208	2·00
BU126	1·55		

LINEAR I.C. AMPLIFIERS

TAA263—3 stage low level amplifier. Bandwidth DC to 600kHz. Supply voltage 6-8V. Output power 10mW 150Ω load. Typical gain 77dB. TO72 case. **£0·65**
TAA293—Med. freq. amplifier up to 600kHz. Supply voltage 6V. Output power 10mW into 150Ω. Typical gain 89dB. TO74 case. **£0·65**
TAA320—MOST stage followed by a bi-polar transistor. Gate - to - source voltage 9-14V. Drain current 1μA. Power dissipation 200mW. TO18 case. **£0·60**

HIGH GAIN DARLINGTON PAIRS

Plastic 3-lead case encapsulated DARLINGTON pair. Typical current gain 30,000. Max. collector voltage V_{CB0} 40V. Max. collector current 400mA. I_{CB0} = 10nA. BC516-PNP **£0·80**. BC517-NPN **£0·80**

Full description of the above, as well as other instruments, is available in our illustrated 126-page catalogue, which also includes price list of comprehensive range of transmitting and receiving valves, semiconductors and passive components. Please send 20p for your copy.

HANDLING AND POSTAGE CHARGES. When ordering through our Mail Order Service please add £1·00 for each instrument and 20p in £ for other items (subject to a minimum charge of 20p).

VALUE ADDED TAX: Prices are exclusive of VAT. Items marked with asterisk are at present rated at 8% and others at 25%. This percentage must be added to the total value of the order including handling charges.

4-STATION INTERCOM




£17·25

Solve your communication problems with this 4-Station Transistor Intercom system (1 Master and 3 Subs), in robust plastic cabinets for desk or wall mounting. Call/talk/listen from Master to Subs and Subs to Master. Ideally suitable for Business, Surgery, Schools, Hospitals and Office. Operates on one 9V battery. On/off switch. Volume control. Complete with 3 connecting wires each 86ft. and other accessories. P. & P. 75p.

MAINS INTERCOM NEW MODEL

No batteries—no wires. Just plug in the mains for instant two-way, loud and clear communication. On off switch and volume control. Price £31·24 per pair P. & P. 75p.

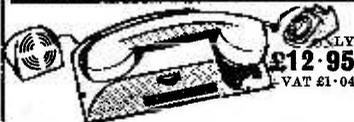NEW! AMERICAN TYPE CRADLE TELEPHONE AMPLIFIER




£12·95

VAT £1·04

Latest transistorised Telephone Amplifier with detached plug-in speaker. Placing the receiver on to the cradle activates a switch for immediate two-way conversation without holding the handset. Many people can listen at a time. Increase efficiency in office, shop, workshop. Perfect for "conference" calls: leaves the user's hands free to make notes, consult files. No long waiting, saves time with long-distance calls. On/Off switch, volume. Direct tape recording model at £13·95 + VAT £1·12 P. & P. 70p, 10-day price refund guarantee.

WEST LONDON DIRECT SUPPLIES (PW8)
169 KENSINGTON HIGH STREET, LONDON, W8

INTER-LOCKING PLASTIC STORAGE DRAWERS

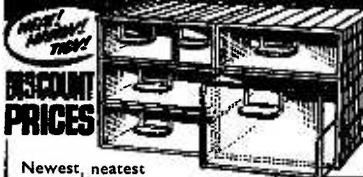

DISCOUNT PRICES

Newest, neatest system ever devised for storing small parts and components: resistors, capacitors, diodes, transistors, etc. Rigid plastic units interlock together in vertical and horizontal combinations. Transparent plastic drawers have label slots. 1D and 2D have space dividers. Build up any size cabinet for wall, bench or table top.

AS SUPPLIED TO POST OFFICE, INDUSTRY & GOVERNMENT DEPTS.

SINGLE UNITS (1D) (5ins × 2½ins × 2½ins). **£2·40 DOZEN.**
DOUBLE UNITS (2D) (5ins × 4½ins × 2½ins). **£4·20 DOZEN.**
TREBLE (3D) **£4·20 for 8.**
DOUBLE TREBLE 2 drawers, in one outer case (6D2), **£5·90 for 8.**
EXTRA LARGE SIZE (6D1) **£5·40 for 8.**

PLUS QUANTITY DISCOUNTS!
Orders over £20, less 5%.
Orders over £60, less 7½%.

PACKING/POSTAGE/CARRIAGE: Add 75p to all orders under £10. Orders £10 and over, please add 10% carriage.

QUOTATIONS FOR LARGER QUANTITIES
Please add 8% V.A.T. to total remittance

FLAIRLINE SUPPLIES

(Dept PW5)
124 Cricklewood Broadway, London NW2
Tel. 01-450 4844

AVAILABLE NOW!

REPRINT OF PW's

TELE-TENNIS SERIES

July-November 74

Send 75p + 10p (post & packing) to :-


Editor (PW Tele-Tennis),
Fleetway House,
Farringdon Street,
London, EC4A 4AD

Published on approximately the 7th of each month by IPC Magazines Limited, Fleetway House, Farringdon Street, London EC4A 4AD. Printed in England by Index Printers, Dunstable, Beds. Sole Agents for Australia and New Zealand—Gordon and Gotch (Asia) Ltd.; South Africa—Central News Agency Ltd. PRACTICAL WIRELESS is sold subject to the following conditions, namely that it shall not, without the written consent of the Publishers first having been given, be lent, resold, hired out or otherwise disposed of by way of Trade at more than the recommended selling price shown on the cover, excluding Eire where the selling price is subject to V.A.T., and that it shall not be lent, resold, hired out or otherwise disposed of in a mutilated condition or in any unauthorised cover by way of Trade or affixed to or as part of any publication or advertising, literary or pictorial matter whatsoever.

RADIO EXCHANGE LTD.

**REDUCTIONS ON ALL KITS
FOLLOWING VAT CHANGES**

NEW EDU-KIT MAJOR

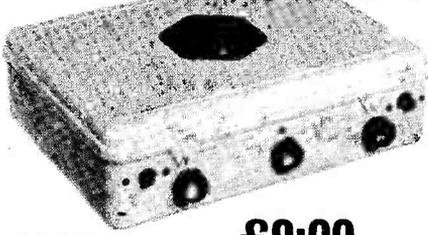

£9.00 INC. VAT
Total Building Costs P & P + Ins. 65p. (Overseas Seamail P & P £8.50)


Completely Solderless Electronic Construction Kit. Build these projects without soldering iron or solder

- ★ 4 Transistor Earpiece Radio
 - ★ Signal Tracer
 - ★ Signal Injector
 - ★ Transistor Tester NPN-PNP
 - ★ 4 Transistor Push Pull Amplifier
 - ★ 5 Transistor Push Pull Amplifier
 - ★ 7 Transistor Loudspeaker Radio MW/LW
 - ★ 2 Transistor Short Wave Radio
 - ★ 5 Transistor Short Wave Radio
 - ★ Electronic Metronome
 - ★ Electronic Noise Generator
 - ★ Batteryless Crystal Radio
 - ★ One Transistor Radio
 - ★ 2 Transistor Regenerative Radio
 - ★ 3 Transistor Regenerative Radio
 - ★ Audible Continuity Tester
 - ★ Sensitive Pre-Amplifier
 - ★ 21 Capacitors
 - ★ 10 Transistors
 - ★ 3 1/2 Volume connectors
 - ★ 3 12-way connectors
 - ★ 1 Tuning Condenser
 - ★ 3 Knobs
 - ★ 6 1/2 yards of wire
- Components include: 24 Resistors ★ 3 1/2 Loudspeakers ★ Earpiece ★ Mica Baseboard ★ 2 Volume controls ★ 2 Slider Switches ★ 1 Tuning Condenser ★ Ready Wound MW/LW/SW Coils ★ Ferrite Rod ★ 1 Yard of sleeving, etc. Complete kit of parts including construction plans.

VHF AIR CONVERTER KIT


Build this Converter Kit and receive the Aircraft Band by placing it by the side of a radio tuned to Medium Wave or the Long Wave Band and operating as shown in the instructions supplied free with all parts. Uses a retractable chrome plated telescopic aerial, Gain Control, V.H.F. Tuning Capacitor, Transistor, etc.

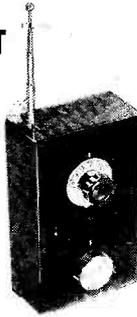All Parts including Case and Plans. **£3.95** P & P and Ins. 40p. INC. VAT



NEW Everyday Series

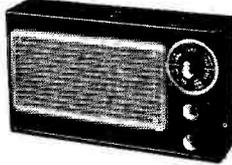Build this exciting new series of designs.



E.V. 5. 5 Transistors and 2 diodes. MW/LW. Powered by 4 1/2 volt Battery. Ferrite rod aerial, tuning condenser, volume control, and now with 3" loudspeaker. Attractive case with red speaker grille. Size 9" x 5 1/2" x 3 1/2" approx. All parts including Case and Plans.

Total Building costs **£4.30** INC. VAT P & P + Ins. 50p

E.V. 6. Case and looks as above. 6 Transistors and 3 diodes. Powered by 9 volt battery. Ferrite rod aerial, 3" loudspeaker, etc., MW/LW coverage. Push Pull output.

All parts including case and plans. Total Building costs **£4.95** INC. VAT P & P + Ins. 50p

E.V. 7. Case and looks as above. 7 Transistors and 3 diodes. Six wavebands, MW/LW, Trawler Band SW1, SW2, SW3, powered by 9 volt battery. Push Pull output. Telescopic aerial for short waves. 3" Loudspeaker.

All parts including Case and Plans. Total Building Costs **£6.35** INC. VAT P & P + Ins. 50p

ROAMER TEN MARK 2

WITH VHF INCLUDING AIRCRAFT

Now with free earpiece and switched socket. 10 transistors. Latest 5" x 3" loudspeaker. 9 tuneable wavebands, MW1, MW2, LW, SW1, SW2, SW3, trawler band, VHF and local stations, also aircraft band. Built in ferrite rod aerial for MW/LW. Chrome plated, 6 section telescopic aerial, can be angled and rotated for peak short wave and VHF listening. Push pull output using 600mW transistors. Car aerial socket. 10 transistors plus 3 diodes. Ganged tuning condenser with VHF section. Separate coil for aircraft band. Volume on/off. Wave change and tone controls. Attractive Case in rich chestnut shade with Gold Blocking. Size: 9" x 7" x 4". Easy to follow instructions and diagrams.

Total building costs **£10.68** INC. VAT P & P + Ins. 65p



POCKET FIVE

NOW WITH 3" LOUDSPEAKER
3 Tuneable wavebands. M.W., L.W., and Trawler Band. 7 stages, 5 transistors and 2 diodes, super sensitive ferrite rod aerial, attractive black and gold case. Size 5 1/2" x 1 1/2" x 3 1/2" approx.

Total Building Costs **£3.60** INC. VAT P & P + Ins. 50p.



ELECTRONIC CONSTRUCTION KITS

ECK2 Self Contained Multi-Band V.H.F. Receiver Kit. 8 Transistors and 3 Diodes. Push/Pull output. 3" Loudspeaker, Gain Control, Superb 9 section swivel ratchet and retractable chrome plated telescopic aerial, V.H.F. Tuning Capacitor, Resistors, Capacitors, Transistors, etc. Will receive T.V. Sound, Public Service Band, Aircraft, V.H.F. Local Stations, etc. Operates from a 9 Volt PP7 Battery (not supplied with kit). Complete kit of parts including construction plans

£7.15 INC. VAT P & P and Ins. 55p.



ECK4 7 Transistors, 6 tuneable wavebands, MW, LW, Trawler Band, 3 Short Wave Bands. Receiver Kit. With 5" x 3" Loudspeaker.

Push/Pull output stage, Gain Control, and Rotary Switch. 7 Transistors and 4 Diodes. 6 section chrome-plated telescopic aerial. 3" Sensitive Ready Wound Ferrite Rod Aerial. Tuning Capacitor. Resistors, Capacitors, etc. Operates from a 9 Volt PP7 Battery (not supplied with kit). Complete kit of parts including construction plans.

£6.55 INC. VAT P & P and Ins. 55p.




EDU-KIT JUNIOR

Completely Solderless Electronic Construction Kit. Build these projects without Soldering Iron or Solder.

- ★ Crystal Radio Medium Wave Coverage — No Battery necessary.
 - ★ One Transistor Radio.
 - ★ 2 Transistor Regenerative Radio.
 - ★ 3 Transistor Earpiece Radio Medium Wave Coverage.
 - ★ 4 Transistor Medium Wave Loudspeaker Radio.
 - ★ Electronic Metronome.
 - ★ 4 Transistor Push/Pull Amplifier.
- All parts including Loudspeaker, Earpiece, MW Ferrite Rod Aerial, Capacitors, Resistors, Transistors, etc. Complete kit of parts including construction plans.

£6.55 INC. VAT P & P + Ins. 55p

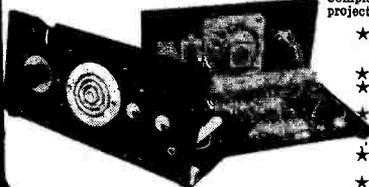

EDU-KIT

Build Radios, Amplifiers, etc. from easy stage diagrams.



Five units including master unit to construct.

Components include: Tuning Condenser; 2 Volume Controls; 2 Slider Switches; Fine tone 3" moving coil Speaker; Terminal Strip; Ferrite Rod Aerial; Battery Clips; 4 Tag Boards; 10 Transistors; 4 Diodes; Resistors; Capacitors; Three 1/2" Knobs. Units once constructed are detachable from Master Unit, enabling them to be stored for future use. Ideal for Schools, Educational Authorities and all those interested in radio construction.

All Parts including Case and Plans **£6.30** INC. VAT P & P + Ins. 55p

JIFFY TESTER

Easy to build and operate. Fits in the pocket. A quick checker for continuity of resistors, chokes, diodes, transistors, circuit wiring (not mains) and loudspeakers. Complete with earpiece, jack plug and socket resistors, capacitors, components, etc. Complete kit of parts including construction plans.



£2.85 P & P + Ins. 30p INC. VAT

TO RADIO EXCHANGE LTD.,
61A HIGH STREET, BEDFORD MK40 1SA
Tel: 0234 52367.

ALL PRICES INCLUDE VAT Reg. No. 788372

- ★ Callers side entrance "Lavelle's" Shop.
- ★ Open 10-1, 2.30-4.30. Mon-Fri. 9-12 Sat.

I enclose £.....
for
Name
Address
PW676

More than just a catalogue!

READY MADE ALARM CLOCK MODULE!

* CAN CONTROL
A RADIO, TOO!

- BRIGHT 4 DIGIT 0.5 INCH DISPLAY
- FLASHING COLDN (1Hz) SWITCH-FOR-DISPLAY SECONDS
- ALARM SET INDICATOR
- P.M. INDICATOR
- POWER FAILURE INDICATION
- SLEEP TIMER
- SNOOZE TIMER
- AUTOMATIC DISPLAY BRIGHTNESS (NEEDS CDS CELL)
- TIME CAN BE SET ACCURATELY TO WITHIN ONE SECOND
- LEADING ZERO BLANKING

ONLY
£8-60
INC. V.A.T. & P/P

Just add transformer
and switches!



This is a fully constructed and tested electronic clock module as illustrated. Data sheet supplied with module shows how simple it is to connect an audible alarm, and your battery or mains radio. A smart case will be available shortly. Data sheet available separately. Please send s.a.e. Simple Clock Kit: £9-38. Alarm Clock Kit: £10-99. Alarm Clock Kit: £11-51. (Case: £1-99 when available.) NOTE: Details not in catalogue.



Really good value for money
at just 40p.


132 Pages

100W per channel STEREO DISCO



YOU MUST
SEE OUR PRICES BEFORE YOU BUY (S.a.e. please for details)

The 4600 SYNTHESISER

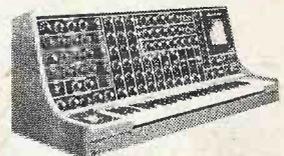

We stock all the parts for this brilliantly designed synthesiser, including all the PCB's, metalwork and a drilled and printed front panel, giving a superb professional finish. Opinions of authority agree the ETI International Synthesiser is technically superior to most of today's models. Complete construction details in our booklet now available price £1.50, or S.A.E. please for specification

GRAPHIC EQUALIZER

A really superior high quality stereo graphic equaliser as described in Jan. 1975 issue of ETI. We stock all parts (except woodwork) including all the metal work drilled and printed as required to suit our components and PCB's. Complete reprint of article—price 15p.



ELECTRONIC ORGAN

Build yourself an exciting Electronic Organ. Our leaflet MESS1, price 15p, deals with the basic theory of electronic organs and describes the construction of a simple 49-note instrument with a single keyboard and a limited number of stops. Leaflet MESS2, price 15p, describes the extension of the organ to two keyboards each with five voices and the extension by an octave of the organ's range. Solid-state switching and new footages along with a pedal board and a further extension of the organ's range are shown in leaflet MESS3, priced at 35p



NO MORE DOUBTS ABOUT PRICES

Now our prices are GUARANTEED (changes in VAT excluded) for two month periods. We'll tell you about price changes in advance for just 30p a year (refunded on purchases). If you already have our catalogue send us an s.a.e. and we'll send you our latest list of GUARANTEED prices. Send us 30p and we'll put you on our mailing list — you'll receive immediately our latest price list then every two months from the starting date shown on that list you'll receive details of our prices for the next GUARANTEED period before the prices are implemented! — plus details of any new lines, special offers, interesting projects — and coupons to spend on components to repay your 30p

NOTE: The price list is based on the Order Codes shown in our catalogue so an investment in our super catalogue is an essential first step.

Call in at our shop, 284 London Road, Westcliff-on-Sea, Essex. Please address all mail to



MAPLIN ELECTRONIC
SUPPLIES
P.O. Box 3 Rayleigh Essex SS6 8LR.

I enclose Cheque/P.O. value _____ PW
For _____ copy/copies of your Catalogue
Name _____
Address _____

MAPLIN ELECTRONIC SUPPLIES P.O. Box 3 Rayleigh Essex SS6 8LR.