

PRACTICAL WIRELESS

JUNE
1977

40p

The NEW

Pw

TELE~

TENNIS
FOOTBALL
SQUASH
PELOTA

plus

ON-SCREEN
SCORING

&

SOUND
EFFECTS



also: CW FILTER UNIT
VERSATILE AF GENERATOR

PRACTICAL WIRELESS

VOL. 53 NO. 2

ISSUE 844

JUNE 1977

BRITAIN'S PREMIER MAGAZINE FOR THE DO-IT-YOURSELF RADIO AND ELECTRONICS CONSTRUCTOR

EDITOR

Lionel E. Howes, G3AYA

ASSISTANT EDITOR

Eric Dowdeswell, G4AR

ART EDITOR

Peter Metalll

TECHNICAL EDITOR

Terry Carter

PRODUCTION & NEWS

EDITOR

Bill Tull

TECHNICAL ARTIST

Alan Martin

TECHNICAL SUB-EDITOR

Frank Ogden

SECRETARIAL

01-634 4292

Linda Walji

ADVERTISING MANAGER

01-634 4612

Roy Smith

CLASSIFIED ADVERTISING

01-261 5762

Colln R. Brown

PLEASE NOTE: We do not operate a Technical Query Service except on matters concerning constructional articles published in PW. We do not supply service sheets or information on commercial radios, TV's or electronic equipment.

All queries must be accompanied by a stamped, self-addressed envelope otherwise a reply cannot be guaranteed.

Send letters concerning advertising matters to the Advertising Manager, Roy Smith.

Send letters concerning editorial matters to the Editor, Lionel Howes.

Published by IPC Magazines Ltd., Fleetway House, Farringdon Street, London EC4A 4AD. Tel. 01-634 4444

BINDERS

Binders £2.10 and indexes 45p (inc. VAT) can be supplied by the Post Sales Department, IPC Magazines Ltd., Lavington House, 25 Lavington Street, London, SE1 0PF.

Remittances with overseas orders for binders should include 60p to cover despatch and postage.

Due to an enlarged format, shortly to be announced, there will be a delay in supplying larger sized binders for Volume 53.

● NEWS & COMMENT

- 102 LEADER ARTICLE—Comment Impossible!
- 102 TELEVISION—What's in the June issue?
- 103 NEWS . . . NEWS . . . NEWS . . .
- 111 HOTLINES—Recent Developments—Ginsberg
- 123 NEXT MONTH IN PRACTICAL WIRELESS
- 131 PW READERS PCB SERVICE
- 132 PRODUCTION LINES—Bill Tull
- 145 ON THE AIR—Amateur Bands—Eric Dowdeswell G4AR
 - Broadcast Bands SW—Derek Bell
 - Broadcast Bands MW—Charles Molloy
 - VHF—Ron Ham

● CONSTRUCTIONAL

- 104 REVERBERATION AMPLIFIER—S. C. Parsons
- 108 VERSATILE AF GENERATOR—C. Toms
- 117 THE PW SEEKIT metal locator Part 2—W. Opel
- 121 S-DeCnology—Project No 7 'MW Receiver'—David Gibson
- 124 TELE-GAMES—D. S. Coultts.
- 134 CW FILTER UNIT—A. Langton
- 136 EXTENDER FOR PW TRANSISTOR TESTER—
Ian Hickman

● OTHER FEATURES

- 107 REPORTING—The BBC's 500th World Radio Club—
Ron Ham F.R.A.S.
- 112 MONOLITHIC VOLTAGE REGULATORS Part 2—
Variable Regulators—Brian Dance M.Sc.
- 141 CIRCUITS FOR AUDIO AMPLIFIERS Part 4—
F. G. Rayer G3OGR

COPYRIGHT AND QUERIES

© IPC Magazines Limited 1977. Copyright in all drawings, photographs and articles published in "Practical Wireless" is fully protected and reproduction or imitation in whole or in part is expressly forbidden. All reasonable precautions are taken by "Practical Wireless" to ensure that the advice and data given to readers are reliable. We cannot, however, guarantee it and we cannot accept legal responsibility for it. Prices are those current as we go to press.

We regret that we cannot answer technical queries by telephone, nor can we provide information or advice on manufacturers' products other than that given in the magazine. We will endeavour to assist readers who have queries relating to articles published but we cannot offer advice on modifications to our published designs. All correspondents expecting a reply should enclose a stamped addressed envelope.

Sparkrite mk2

Capacitive discharge electronic ignition kit

VOTED BEST OF 2 SYSTEMS TESTED BY 'POPULAR MOTORING' MAGAZINE OCT 74



- * Smoother running
- * Instant all-weather starting
- * Continual peak performance
- * Longer coil/battery/plug life
- * Improved acceleration/top speeds
- * Up to 20% better fuel consumption

Sparkrite Mk. 2 is a high performance, high quality capacitive discharge, electronic ignition system in kit form. Tried, tested, proven, reliable and complete. It can be assembled in two or three hours and fitted in 15/30 mins.

Because of the superb design of the Sparkrite circuit it completely eliminates problems of the contact breaker. There is no misfire due to contact breaker bounce which is eliminated electronically by a pulse suppression circuit which prevents the unit firing if the points bounce open at high R.P.M. Contact breaker burn is eliminated by reducing the current to about 1/50th of the norm. It will perform equally well with new, old, or even badly pitted points and is not dependent upon the dwell time of the contact breakers for recharging the system. Sparkrite incorporates a short circuit protected inverter which eliminates the problems of SCR lock on and, therefore, eliminates the possibility of blowing the transistors or the SCR. (Most capacitive discharge ignitions are not completely foolproof in this respect). All kits fit vehicles with coil/distributor ignition up to 8 cylinders.

THE KIT COMPRISES EVERYTHING NEEDED

Ready drilled pressed steel case coated in matt black epoxy resin, ready drilled base and heat-sink, top quality 5 year guaranteed transformer and components, cables, coil connectors, printed circuit board, nuts, bolts, silicon grease, full instructions to make the kit negative or positive earth, and 10 page installation instructions.

OPTIONAL EXTRAS

Electronic/conventional ignition switch. Gives instant changeover from "Sparkrite" ignition to conventional ignition for performance comparisons, static timing etc., and will also switch the ignition off completely as a security device, includes: switch connectors, mounting bracket and instructions. Cables excluded. Also available RPM limiting control for dashboard mounting (fitted in case on ready built unit).

CALLERS WELCOME. For Crypton tuning and fitting service - phone (0922) 33008

PRICES INCLUDE VAT, POST AND PACKING. IMPROVE PERFORMANCE & ECONOMY NOW

Note—Vehicles with current impulse tachometers (Smiths code on dial RV1) will require a tachometer pulse slave unit. £3.35 inc. V.A.T. p & p. E.D.A. 82 BATH STREET, WALSALL, WS1 3DE.

POST TODAY!

Quick installation
No engine modification required

Electronics Design Associates, Dept., PW 6
82 Bath Street, Walsall, WS1 3DE. Phone: (0922) 33652

Name

Address

Mk. 2 DIY Ass. Kit @ £11.80

QUANTITY REQD.

Mk. 2 Ready Built Negative Earth @ £14.97

Mk. 2 Ready Built Positive Earth @ £14.97

Ignition Changeover switches @ £4.30

R.P.M. Limit systems in above units @ £2.42

I enclose cheque/PO's for £

Cheque No.

Send SAE if brochure only required.

Random FLASHER UNIT

Wired ready for use. Complete with three 100 watt coloured lamps that flash independently at random.

£18.95

TWIN BANK 6 LIGHT UNIT

(less lamps) LENGTH 14 1/2 inches

B.C. Fitting **£9.55** EACH
E.S. Fitting **£10.35** EACH

Sound to Light MASTER UNIT

600 WATTS PER CHANNEL

£30.95

INCLUDING CHANNEL OUTPUT PLUGS AND MAINS INPUT SOCKET

TYPE A SPOT

(less lamp)

B.C. Fitting **£1.95** EACH | E.S. Fitting **£2.12** EACH

TYPE B 3 BANK UNIT

(Less Lamps)

B.C. Fitting **£6.90** EACH | E.S. Fitting **£7.26** EACH

TWIN BANK 12 LIGHT UNIT

Length 31 1/2

(less lamps)
B.C. Fitting **£15.60** EACH | E.S. Fitting **£17.00** EACH

100 WATT SPOT LAMPS

RED, YELLOW, GREEN, BLUE, CLEAR

Minimum 3 lamps each **£3.90**

£1.30 each B.C. or E.S. Fitting

ACT. PRICES INCLUDE V.A.T. and POST & PACKING (where once apply to the United Kingdom only)

Send 20p for illustrated leaflet & price list.

ALBEN ENGINEERING CO. LTD.,

DEPT. PW THE CRESCENT, WORSTHORNE,
BURNLEY, LANCs. Tel Burnley 20940

DORAM kits

DORAM KITS CONTAIN EVERYTHING DOWN TO THE LAST NUT!

CMOS MORSE KEYER

£9.45 + H

Fully electronic automatic morse keyer giving perfectly spaced dots and dashes of correct duration. Sidetone or silent operation with variable speed to suit novice or expert. Very low current drain on internal battery. Single paddle operation; suitable for most transmitters with a keying facility. Give your morse that precision quality.

As featured in Sept '76 edition of RAD. COMM.

£9.45 + H VAT (Order 997-049)
Subject to availability


Overseas orders—add 15% for p & p. All items offered for sale subject to the Terms of Business as appears in Doram Edition 3 catalogue, price 60p. The Doram Kit brochure is also available, price 25p. Combined price only 70p which also entitles you to 2 x 25p vouchers each one usable on an order placed to the value of £5.00 or more (ex VAT).

DORAM ELECTRONICS LTD, P.O. BOX TR8 LEEDS LS12 2UF
An Electrocomponents Group Company

RSC 200 WATT DISCO SYSTEM

ALL RSC PRICES INCLUDE VAT

AT A FANTASTIC LOW PRICE

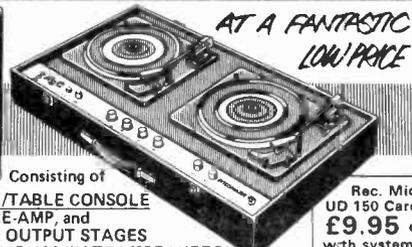

Consisting of

- (1) TWIN T/TABLE CONSOLE with PRE-AMP, and POWER OUTPUT STAGES
- (2) & (3) PAIR 100 WATT L'SPEAKERS including 12" UNITS

Rec. Mic. UD 150 Cardioid £9.95 extra with system only

Terms: Deposit £40.00 and 12 monthly payments £16.60 (Total £227.20) Carr. £7.50

Also available: 100 WATT SYSTEM £169.95 with Dynamic Stick MICROPHONE.

TDI DISCO CONSOLE

Incorporating twin BSR type turntables and Sonotone or Acoas Cartridges with diamond styl. Separate Vol. controls for each turntable. Also MONITORING FACILITIES, plus Treble and Bass Controls. Separate input for 'mixe' with vol. control. Black Vynde covered Cabinet with lid. Or DEP. £18.49 and 18 fortnightly pymts. £6.11 (Total £128.47) Carr. £3

D2S STEREO VERSION OF ABOVE

Terms DEPOSIT £20 and 18 fortnightly payments £8.99 (Total £144.02) Carr. £9.00

£199.95

40 WATT SYSTEM £99.95. 200 WATT SYSTEM £199.95 WRITE OR PHONE for Free catalogue

DISCOMAJOR/100 TWIN TURNTABLE POWER CONSOLE £129.95

Twin Full size BSR turntables, Sonotone or Acoas Cartridges with Diamond Styl. Facilities as TDI Console but with built-in 100 watt Power Amplifier complete with lid. Terms: Deposit £19.95 and 18 fortnightly pymts. £7.03 (Total £146.49) Carr. £3.00

DISCOMAJOR/200 £149.95

200 watt version of above. Terms: Dep. £29.95 and 18 fortnightly pymts £7.87 (Total £171.61)

TITAN 100W BASS BINS £99.95

High quality 15" high flux Bass Unit and J104 Horn Tweeter in folded horn type enclosure to provide amazing level of sound output. List price £144 Terms Dep. £14.95 and 18 fortnightly payments £8.88 (Total £115.39) Carr. £3.

RSC PHANTOM 50 COMBO AMP. £69.95

Rating 60 watts. 3 inputs, 2 vol. controls—Bass, Treble Presence. Carr. £1.50 Suitable for Lead or Rhythm Guitar, m.c., Radio, Tape etc. Inc. High Flux 12" 50w Speaker. Dep. £10.95 & 8 mthly pyts £8.71 (Total £89.66).

PHANTOM 50G

with twin 12" speakers £75.95

FANE HIGH POWER SPEAKERS

Power ratings R.M.S. Cont. 2 YRS GUARANTEE *Gauss 14000 Imp 8-15 ohms. CARR FREE.

- *POP 33T 12" 33w £13.95 Dual cone. Full range
- *POP 50/2 12" 50w £15.99 Dep for Pair £8.00 and 8 monthly pymts £3.54 (Total £36.32)
- *POP 60 15" 60w £25.95 Dep £7.00 & 8 monthly pymts £2.87 (Total £29.96)
- *POP 100 18" 100w £44.95 Dep £10.00 & 8 monthly pymts £5.17 (Total £51.36)

100W POWER (SLAVE) AMPLIFIER

Suitable for use with DISCO-Consoles. Also for increasing output of lower-powered Amp. Dep. £9.00 and 8 mthly pyts of £6.05 (Total £57.40) Carr. £1.50

100 + 100W MODEL £69.95 Carr. £1.50

TITAN GROUP/DISCO SPEAKERS

GUARANTEED 5 YEARS Carr. £1. under £18

	List	RBC Price
T12/45 12" 45w	£15.80	£11.95
T12/60A 12" 60w	£21.00	£13.95
T12/100 12" 100w	£26.00	£18.95
T15/60 15" 60w	£26.00	£13.95
T15/70 15" 70w	£28.00	£18.95
T15/100 15" 100w	£41.00	£29.95
T18/100 18" 100w	£47.00	£39.95

Stockists of Lighting by PULSAR Group Equipment by CARLSBRO Full range of speakers by FANE

CABINETS FOR ABOVE SPKRS

Heavy duty. fitted protective corner pieces. Various sizes and cut-outs. TE1 1 x 12" £10.95. TE2 2 x 12" £16.95. Low Deposit Terms on orders over £20

TITAN TA/50A 50W AMPLIFIER

Solid state. 3 sep. controlled inputs plus Master control. Bass, Treble & Presence Controls. Vynde covered cab. with corner protectives. List price £60. Terms: Dep. £9 & 8 monthly pymts £6.05. £49.95 (Total £57.40). Carr. £1. Matching Cabinet Spkrs. 1 x 12" £29.95 2 x 12" £49.95

TITAN TA/100C COMBO

100w R.M.S. Amp. incorporating a fabulous Fane Crescendo 12" 100 watt spkr for really superlative results with Lead Guitar £119.95 Carr. £5 Or Dep £17.95 & 18 f'tnly pays £6.69 (Total £138.37)

TITAN TA/100A 100W AMPLIFIER

TWIN CHANNEL—4 INPUTS £69.95 (NORMAL OR BRIGHT) Carr. £1.50

A De-luxe professional unit with many facilities. R.M.S. Rating. Matching 2 x 12" 120w Cabinet speaker £49.50. with above only. Carr. £1.50

INTEREST REFUNDED on Credit Purchases settled in 3 mths

TITAN 'ADD-ON' HIGH FREQUENCY HORN UNITS

MODEL T92H
Inc. Pair of highly sensitive Horns. Range 3-15 kHz Imp 16Ω. Use with 8 or 15Ω 2 x 12" or 1 x 16" or 18" Drive Unit for increased sound clarity and projection. Rating 100 watts.

MODEL T1H
with single super efficient Horn. Range 3-15 kHz. Imp 8Ω. Use with max 8Ω 2 x 12" or single 15" or 18" 8Ω Drive Unit. Maximum amplifier power output to be 100 watts.

Either model £27.95 comparable with units at twice the cost. Carr 75p. Terms: Dep £6.95 & 8 mthly pyts. £3.12 (Total £31.91)

FANE HIGH FREQUENCY HORNS 'J' SERIES

All Carr Free

MODEL J44 Imp 8Ω
Size approx 3 1/4" x 3 1/4" x 3" Rating 30-50 watts Range 2-20 kHz £7.95

MODEL J73 Imp 8Ω
Size approx 7 1/2" x 3" x 6 1/2" Rating 50 watts Range 2-20 kHz £11.95

MODEL J104 Imp 8Ω
Size approx 10 1/2" x 7 1/2" x 7 1/2" Rating 50-70 watts Range 3-15 kHz £15.50

RSC MAINS TRANSFORMERS TYPES FOR VALVE RADIOS & AMPLIFIERS (Inc. L.F. CROKES & OUTPUT TRANSFORMERS. As previously advertised still available.

FILAMENT OR TRANSISTOR POWER PACK
12v. 1a. £1.10. 6.3v. 1.5a. £1.08. 6.3v. 2a. £1.10. 6.3v. 3a. £1.70. 6.3v. 5a. £2.80. 12v. 3a. or 24v. 1.5a. £2.80. 0.9-15v. 11a. £2.20. 0.12-25.42v. 2a. £2.19. CHARGER TRANS 0.9-15v. 11a. £2.05. 21a. £2.28. 3a. £2.32. 5a. £2.84. 6a. £3.19. 8a. £3.43.

AUTO (STEP UP/STEP DOWN) TRANSFORMERS 0-110/120v 200-230-250v. 80w. £2.90; 150w. £5.20; 250w £8.37; 500w £9.84.

DISCO LIGHTING SYSTEM £58.95

Incl. 2 Spotbanks and bulbs

JINGLE MACHINES from £37.95

ECHO CHAMBERS from £53.95

COLUMN SPEAKERS from £29.95

GROUP/DISCO SPKRS £11.95

IN CABINETS from

FREE FANE HIGH POWER 'CROSS-OVER' WITH ANY OF ABOVE
Impedance or total impedance of 12", 15" or 18" Drive units must not exceed impedance of single horn or pair in series. Pair J44, Single J73 or J104 suitable for amplifier power up to 100 watts subject to above and with HP x 2 'Cross-over'

New Branches at HANLEY WOLVERHAMPTON, YORK, LIVERPOOL

Barclaycard & Access PHONE ORDERS quoting CARD NO. accepted

MAIL ORDERS & EXPORT ENQUIRIES TO:— AUDIO HOUSE, HENCONNER LANE, LEEDS, 18. Tel: 0332 377631.

MAIL ORDERS MUST NOT BE SENT TO SHOPS OR B.O.D. No G.O.D. under 48. POSTAGE 50p PER ORDER OR AS QUOTED. Phone or Write for FREE CATALOGUE.

All items subject to availability. Prices correct at 22.3.77 E. & O.E. TERMS C.W.O. or G.O.D. under 48. POSTAGE 50p PER ORDER OR AS QUOTED. Phone or Write for FREE CATALOGUE.

HANLEY, Stoke-on-Trent, 44 Piccadilly
HULL 7 Whitefriargate (Closed Thurs.). Tel. 20505
LEICESTER 32 High Street (Closed Thurs.). Tel. 56420
LEEDS 5-7 County (Mecca) Arcade, Briggate (Closed Wed.). Tel. 458252

LIVERPOOL 35 Dawson's Way, St. John's Shopping Centre Tel: 708 9380 (Cl. Wed.).
LONDON 238 Edgware Road, W.2. (Closed Thurs.). Tel. 723 1629
MANCHESTER 60A Oldham Street (Closed Wed.). Tel. 236 2778
MIDDLESBROUGH 103 Linthorpe Rd. Tel. 210585 (Closed Wed.)

NEWCASTLE UPON TYNE 59 Granger St. (Closed Wed.). Tel. 21469

NOTTINGHAM 18/19A Market Street (Closed Thurs.). Tel. 48068

PRESTON 41 Friargate Walk, St. George's Shoppg Prec. Tel. 81979

SHEFFIELD 13 Exchange Street (Castle Mkt. Bldg.) (Closed Thurs.). Tel. 20716 & Little Underbank (Closed Thurs.). Tel. 480-0777

STOCKPORT (Closed Thurs.). Tel. 20716 & Little Underbank (Closed Thurs.). Tel. 480-0777

SUNDERLAND 5 Market Sq. (Closed Wed.). Tel. 70579

WOLVERHAMPTON, 6, Wulfrun Way, Tel. 26612

YORK, 5 Church St. (Closed Wed.). Tel. 34355

GLASGOW 325 Argyle St. (Cl'd Tues.). Tel. 248 4158

EDINBURGH 101 Lothian Rd. (Cl. Wed.). Tel. 229 9501

DUNDEE 3 Queensgate. (Closed Thurs.). Tel. 63069

DARLINGTON 19 Northgate (Cl. Wed.). Tel. 68043

DEWBURY 9/11 Kingsway (Closed Tues.). Tel. 468058

COVENTRY 8 English Street. (Closed Thurs.). Tel. 38744

BIRMINGHAM 30/31 Great Western Arcade. Tel. 021-236 1279 (Closed Wed.).

BRADFORD 10 North Parade (Closed Wed.). Tel. 25349

BOLTON 23 Deansgate. (Closed Wed.). Tel. 33512

OPEN ALL DAY SATURDAYS (5 Day Week)

AUTO TRANSFORMERS

Ref	VA (Watts)	£
113	20 0-115-210-240	3.14
64	75 " " "	4.73
4	150 0-115-200-220-240	6.69
66	300 " " "	8.82
67	500 " " "	13.39
84	1000 " " "	21.12
93	1500 " " "	23.62†
95	2000 " " "	34.17†
73	3000 " " "	47.63†

CASED AUTO TRANSFORM

Ref	VA (Watts)	£
200VA	£ 5.67	Ref 113W
150VA	£ 9.30	Ref 4W
200VA	£ 11.93	Ref 65W
300VA	£ 14.32	Ref 66W
500VA	£ 16.91	Ref 67W
1000VA	£ 22.84	Ref 84W†
2000VA	£ 37.82	Ref 95W†

30 VOLT RANGE

Ref	Amps	£
112	0.5	3.45
79	1.0	4.37
3	2.0	6.21
20	3.0	7.51
21	4.0	8.61
51	5.0	9.99
117	6.0	11.50
88	8.0	14.44
89	10.0	14.85

BRIDGE RECTIFIERS

Ref	VA (Watts)	£
200V	2A	0.82
400V	2A	0.93
200V	4A	1.04
400V	4A	1.21
400V	6A	1.44
500V	10A	2.87

POWER UNITS

Ref	VA (Watts)	£
CC12-05	3-4-5-6-7-5	9-12V at 500mA £5.40
STABILISED	3-6-	7.5-9V at 400mA £7.24
3300	Fits into 13A socket	6-7.5-9V 300mA (fused) £4.30

TEST METERS

Ref	VA (Watts)	£
AVO 8 MK5		£76.33
AVO 71		£31.48
AVO 73		£42.07
AVO MM5		£42.94
AVO TT169	(in circuit transistor tester)	£32.56

MINI-MULTIMETER

Ref	VA (Watts)	£
AC/DC-1000V	1000 Ω/V	DCI-100mA. RES.-150K Ω
		£6.39

AUDIO KIT 25W

2 + 25W Amplifiers, 1 + Pre-Amp
1 + Transformer supply, 1 + Transformer
1 + Front Panel
1 + Kit of parts to include on/off switch, neon ind. Stereo headphone socket Plus Instructions book £32.86

TEAK AUDIO KIT 25W

Teak veneered cabinet
Aluminium chassis, heat sink and front panel brackets, plus back panel and sockets etc. £12.22

STEREO FM TUNER WITH PHASE-LOCK LOOP

4 Pre-selected stations supply 20-35V 90mA Max. £23.44

TRANSFORMERS

ALL EX-STOCK—SAME DAY DESPATCH

60 VOLT RANGE

Ref	VA (Watts)	£
Prim. 220-240V		
Sec. 0-24-30-40-48-60V		
Ref.	amps	£
124	0.5	4.69
126	1.0	6.02
127	2.0	8.36
125	3.0	11.47
123	4.0	13.92
120	5.0	15.24
120	6.0	17.86
121	8.0	19.56
122	10.0	24.09
189	12.0	26.57

SCREENED MINIATURES

Ref	mA	Volts	£
238	200	3-0-3	2.74
212	1A, 1A	0-6, 0-6	3.41
		0-9, 0-9	2.45
235	330, 330	0-9, 0-9	2.56
207	500, 500	0-8-9, 0-8-9	3.27
208	1A, 1A	0-8-9, 0-8-9	4.65
236	200, 200	0-15, 0-15	2.56
214	300, 300	0-20, 0-20	3.36
221	700 (DC)	20-12, 0-12-20	4.04
206	1A, 1A	0-15-20, 0-15-20	5.54
203	500, 500	0-15-27, 0-15-27	4.95
204	1A, 1A	0-15-27, 0-15-27	6.18
5112	500	12, 15, 20, 24, 30	3.45

PLUS

DECS

Solderless Bread Boarding
6 Dec 70 contacts £2.57
T Dec 208 contacts £4.35
U Dec 'A' for IC's £4.75
U Dec 'B' for IC's etc. £7.98

ELECTRONIC CONSTRUCTION KIT

10 projects (including Electronic Organ). Ideal gift at £8.74 (no soldering needed)

COMPONENT PACKS

200 Mixed value resistors (by weight)
150 Mixed value capacitors (by weight)
30 Mixed value precision resistors
15 Assorted pots and pre-sets
10 Reed switches
3 Micro switches
15 Wire wound resistors (3-14W).
1 Pack wire 50 metres, ass. colours.
STATE PACK REQ'D £1.08 PER PACK

BLOB BOARD (Pack of 3)

2.5" x 5.1" .1" or 2.5" x 5.1" .15" £1.13
3.75" x 5.1" .1" or 3.75" x 5.1" .15" £1.56
10" x 6" .1" or 10" x 6" .15" £4.51
IC Range
4.8" x 3" 2" £1.36. 4.75" x 7.5" £2.62

MAINS ISOLATING (SCREENED)

Ref	VA (Watts)	£
Prim. 120/240V		
Sec 120/240V		
PRIM & SEC CENTRE TAPPED		
Ref	VA (Watts)	£
07*	20	5.10
149	60	7.11
150	100	7.85
151	200	12.59
152	250	14.81
153	350	18.08
154	560	21.55
155	750	28.20†
156	1000	37.97†
157	1500	45.31†
158	2000	53.24†
159	3000	80.78†

*115V or 240V Sec. only.

HIGH VOLTAGE

Ref	VA (Watts)	£
Prim. 200/220 or 400/440		
Sec. 100/120 or 200/240		
VA	Ref.	£
60	243	6.86
350	247	16.59
1000	250	25.92
2000	252	54.80†

HIGH QUALITY MODULES

Ref	VA (Watts)	£
5 Watt RMS AMPLIFIER		£3.70
10 Watt RMS AMPLIFIER		£4.04
25 Watt RMS AMPLIFIER		£5.27
125W RMS AMPLIFIER		£18.50
PRE-AMP for 5-10W		£7.92
PRE-AMP for 25W		£15.90
POWER SUPPLIES 5-10W		£1.84
POWER SUPPLIES 25W		£4.60
TRANSFORMER 5-10W		£4.50
TRANSFORMER 25W		£6.43

ANTEX SOLDERING IRONS

15W £4.33 18W £4.23 25W £3.95
SOLDERING IRON KIT £3.82
STAND FOR ABOVE £2.00

12 and or 24 Volt PRIMARY 220-240V

Ref.	12V	24V	£
111	0.5	0.25	2.52
213	1.0	0.5	3.24
71	2	1	4.02
68	3	1.5	5.43
18	4	2	5.08
85	5	—	5.79
70	6	3	6.75
108	8	4	8.04
72	10	5	8.58
116	12	6	9.89
17	15	8	11.36
115	20	10	15.80
187	30	15	19.88
226	60	30	24.78†

50 VOLT RANGE

Ref.	Amps	£
Prim. 220-240V		
Sec. 0-19-25-33-40-50V		
102	0.5	4.31
103	1.0	5.55
104	2.0	7.82
105	3.0	9.86
106	4.0	12.19
107	6.0	17.56
118	8.0	19.05
119	10.0	22.04†

CARTRIDGES

Ref	VA (Watts)	£
Sonotone		£5.36
VI00		£5.95
9TAHC		£3.34
ACOS		£6.71
GP9-1		£2.83
GP96-1		£3.08
B.S.R.		£6.80
5X6M		£2.91
SC12M		£3.66
GOLDING		£6.80
GB80		£6.71
GB50		£4.94
SHURE		M75-6S
		£12.66
M55E		£14.33

Prices include VAT and P & P except † where carriage will be according to weight and distance. Save Postage—we are open 9-5pm Mon-Fri. ElectroSil Resistors, Semi-conductors, Multi-meters, wide range of Panel Meters, Audio Accessories, send stamp for lists. Prices correct at 30th March, 1977.

Barrie Electronics Ltd.

3, THE MINORIES, LONDON EC3N 1BJ

TELEPHONE: 01-488 3316/7/8

NEAREST TUBE STATIONS: ALDGATE & LIVERPOOL ST

Test Equipment

Multimeters



The Eagle range of multimeters covers every possible need of the electrical or electronic engineer. They cost from about £6 to £58 (inc V.A.T.). There's at least one which suits your job precisely.

We have a lot of other test equipment too. Send the coupon and we'll send you our complete catalogue.



Please send me details of all your test equipment.

NAME

ADDRESS

Eagle International, Precision Centre, Heather Park Drive, Wembley HA0 1SU Tel: (01)-902 8832




DORAM kits

DORAM KITS CONTAIN EVERYTHING DOWN TO THE LAST NUT!

CAR RADIO

MW/LW PUSH-BUTTON

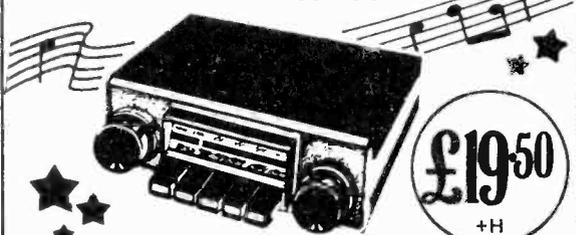


A professional standard Car Radio you can build yourself. 5 push-button selectors or manual tuning. Full 4W RMS output with tone control, illuminated tuning scale and automatic polarity selection, suitable for any 12V car. Supplied complete with full assembly instructions, fitting kit & speaker. Order code 991-962

Car Radio less speaker £16.95 + H VAT (Order code 991-978)

Overseas orders—add 15% for p & p. All items offered for sale subject to the Terms of Business as appears in Doram Edition 3 catalogue, price 60p. The Doram Kit brochure is also available, price 25p. Combined price only 70p which also entitles you to 2 x 25p vouchers each one usable on an order placed to the value of £5.00 or more (ex VAT).

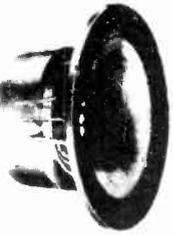DORAM ELECTRONICS LTD. P.O. BOX TR8 WELLINGTON ROAD INDUSTRIAL ESTATE LEEDS LS12 2UF
An Electrocomponents Group Company



WILMSLOW AUDIO

THE Firm for speakers!

SPEAKERS

Baker Group 25, 3, 8 or 15 ohms
 Baker Group 35, 3, 8 or 15 ohms
 Baker Group 50/12 8 or 15 ohms
 Baker Group 50/18 8 or 15 ohms
 Baker Deluxe 12" 8 or 15 ohms
 Baker Major 3, 8 or 15 ohms
 Baker Superb 8 or 15 ohms
 Baker Regent 12" 8 or 15 ohms
 Baker Auditorium 12" 8 or 15 ohms
 Baker Auditorium 15" 8 or 15 ohms
 Celestion G12M 8 or 15 ohms
 Celestion G12H 8 or 15 ohms
 Celestion G12/50 8 or 15 ohms
 Celestion G12/50TC 8 or 15 ohms
 Celestion G15C 8 or 15 ohms
 Celestion G18C 8 or 15 ohms
 Celestion HF1900 8 or 15 ohms
 Celestion HF2000 8 ohms
 Celestion MH1000 8 or 15 ohms
 Celestion CO3K
 Decca London ribbon horn
 Decca London CO/1000/8 Xover
 Decca DK30 ribbon horn
 Decca CO/1/8 Xover (DK30)
 EMI 14 x 5 Bass 8 ohms 14A770
 EMI 8 x 5, 10 watt, d/cone, roll surr.
 EMI 8" d/cone, roll surr. 8 ohms
 EMI 5" mid range
 EMI 8" roll surr. bass
 EMI 5" mid range
 Elac 59RM109 (15) 59RM114 (8)
 Elac 6 1/2" d/cone, roll surr. 8 ohms
 Elac 10" 10RM239 8 ohms
 Eagle Crossover 3000hz 3, 8 or 15 ohm
 Eagle FR4
 Eagle FR65
 Eagle FR8
 Eagle FR10
 Eagle HT15
 Eagle HT21
 Eagle MHT10
 Eagle F29 multiceil. horn
 Fane Pop 15, 8 or 16 ohm
 Fane Pop 33T, 8 or 16 ohm
 Fane Pop 50, 8 or 16 ohm
 Fane Pop 55, 8 or 16 ohm
 Fane Pop 60, 8 or 16 ohm
 Fane Pop 70, 8 or 16 ohm
 Fane Pop 100, 8 or 16 ohm
 Fane Crescendo 12A, 8 or 16 ohms
 Fane Crescendo 12BL, 8 or 16 ohms
 Fane Crescendo 15/100A, 8 or 16 ohms
 Fane Crescendo 15/125, 8 or 16 ohms
 Fane Crescendo 18, 8 or 16 ohms
 Fane 910 Mk II horn
 Fane 920 Mk II horn
 Fane HPX1 crossover 200 watt
 Fane 13 x 8, 15 watt dual cone
 Fane 80T 8" d/c, roll surr.
 Goodmans Axent 100
 Goodmans Audiom 200 8 ohm
 Goodmans Axlom 402 8 or 15 ohm
 Goodmans Twinaxiom 8, 8 or 15 ohm
 Goodmans 8P 8 or 15 ohm
 Goodmans 10P 8 or 15 ohm
 Goodmans 12P 8 or 15 ohm
 Goodmans 12PG 8 or 15 ohm
 Goodmans 12PD 8 or 15 ohm
 Goodmans 12AX 8 or 15 ohm
 Goodmans 15AX 8 or 15 ohm
 Goodmans 15P 8 or 15 ohm

SPEAKERS

£13-00
 £14-50
 £21-00
 £25-75
 £17-50
 £15-00
 £22-50
 £12-50
 £21-00
 £25-75
 £12-95
 £15-95
 £18-00
 £20-00
 £28-95
 £39-95
 £7-50
 £8-55
 £13-50
 £4-48
 £31-50
 £8-95
 £20-50
 £4-75
 £12-50
 £3-95
 £3-95
 £3-50
 £3-50
 £3-95
 £3-95
 £1-57
 £6-75
 £11-95
 £14-95
 £18-50
 £4-50
 £5-50
 £6-75
 £7-50
 £5-75
 £9-95
 £12-50
 £16-95
 £19-95
 £21-75
 £33-95
 £42-95
 £44-95
 £54-95
 £64-95
 £75-05
 £15-75
 £45-95
 £2-50
 £3-50
 £8-95
 £8-50
 £14-95
 £22-00
 £10-60
 £8-50
 £8-95
 £18-50
 £17-75
 £18-75
 £44-00
 £49-00
 £24-00

SPEAKER KITS

Goodmans 18P 8 or 15 ohm
 Goodmans Hifax 750P
 Goodmans 5" midrange 8 ohm
 Gauss 12"
 Gauss 15"
 Gauss 18"
 Jordan Watts Module 4, 8 or 15 ohm
 Kef T27
 Kef T15
 Kef B110
 Kef B200
 Kef B139
 Kef DN8
 Kef DN12
 Kef DN13 SP1015 or SP1017
 Lowther PM6
 Lowther PM6 Mk 1
 Lowther PM7
 Peerless KO10DT 4 or 8 ohms
 Peerless DT10HFC 8 ohms
 Peerless KO40MRF 8 ohms
 Peerless MT25HFC 8 ohms
 Richard Allan CA12 12" bass
 Richard Allan HP8B
 Richard Allan LP8B
 Richard Allan DT20
 Richard Allan CN8280
 Richard Allan CN820
 Richard Allan Super disc 60W 12"
 Richard Allan Super Disc 10" 50 watt
 Richard Allan Super Disc 8" 50 watt
 Radford MD9
 Radford MD6 dome mid range
 Radford TD 3
 Radford Crossover network
 BD25 Mk II
 Coles 4001 G & K
 Tannoy 10" HPD
 Tannoy 12" HPD
 Tannoy 15" HPD
 Castle 8 RS/DD

SPEAKER KITS

Fane Mode One Mk2 each £10-35
 Wharfedale Denton 2XP Kit pair £23-25
 Wharfedale Linton 3 x P Kit pair £34-25
 Wharfedale Glendale 3XP Kit pair £49-50

HI-FI

ON DEMONSTRATION in our showrooms

Akai, Armstrong, Bowers and Wilkins, Castle, Celestion, Chartwell, Dalesford, Dual, I.M.F. RAM, J. R. Formula 4, Kef, Leak, Linn Sondek, Neal, Ortofon, Pickering, Pioneer, Radford, Richard Allan, Rotel, Sansui, Stanton, Tandberg, Trio, Videotone, Wharfedale, etc. Ask for our Hi-Fi Discount Price List.

THIS MONTH'S SPECIALS! Carr.
 £2-50 Rotel RA312 £66-00. Sansui 331 £109-00. Trio KR2600 £109-00. Videotone Minimax II £46-95. Sansui SC2000/2002 £145-00. Pioneer CTF2121 £136-00. Rotel RX152II £91-00.

We stock the complete Radford range of amplifiers, preamplifiers, power amplifiers, tuners, etc., and also Radford Audio Laboratory equipment, low distortion oscillator, distortion measuring set, audio noise meter, etc.

All Prices include VAT
(Prices correct at 1.4.77)

Send stamp for Free 38 page booklet
'Choosing a Speaker'.

All units guaranteed New and Perfect.
Carriage and Insurance:

Speakers up to 12" 60p
 12" £1-00
 15" £1-75
 18" £2-50

Kits £1-00 each (£2-00 per pair)
 Tweeters & Crossovers 33p each

WILMSLOW AUDIO

Dept. PW

Loudspeakers, Mail Order and Export:
 Swan Works, Bank Square, Wilmslow.
 Hi-Fi, Radio & TV: Swift of Wilmslow
 5 Swan Street, Wilmslow, Cheshire.
 PA, Hi-Fi & Accessories: Wilmslow
 Audio, 10 Swan Street, Wilmslow,
 Cheshire.

Telephone:

Loudspeakers, Mail Order and Export
 Wilmslow 29599

Hi-Fi, Radio, etc., Wilmslow 26213
 (Access and Barclay Card orders
 accepted by phone).

Complete kits in stock for Radford Studio 90, Radford Monitor 180, Radford Studio 270, Radford Studio 360, HiFi Answers Monitor (Rogers), HiFi News No Compromise (Frisby), HiFi News State of the Art, Wireless World Transmission Line (Bailey), Practical HiFi and Audio Monitor (Giles), Practical HiFi and Audio Triangle (Giles), Popular HiFi (Colloms), etc.

Construction leaflets for Radford, Kef, Jordan Watts, Tannoy, Hi-Fi On dem. Answers Monitor, State of Art, Free on Request.

P.A. Amplifiers, microphones etc. by Shure, Linear, Eagle, Beyer, AKG etc.

FREE with orders over £10—"HiFi Loudspeaker Enclosures" Book

ENGINEERS

FREE



YOURSELF FOR A BETTER JOB WITH MORE PAY!

Do you want promotion, a better job, higher pay? "New opportunities" shows you how to get them through a low-cost, Home Study Course. There are no books to buy and you can pay as you learn.

This easy to follow GUIDE TO SUCCESS should be read by every ambitious engineer. Send for this helpful 44-page free book NOW! No obligation, nobody will call on you. It could be the best thing you ever did.

CHOOSE A BRAND NEW FUTURE HERE



CUT OUT THIS COUPON
Tick or state subject of interest.
Post to address below.

- | | | |
|--|--|---|
| <input type="checkbox"/> ELECTRICAL & ELECTRONICS | <input type="checkbox"/> Radio, Servicing & Repairs | <input type="checkbox"/> Painting & Decorating |
| <input type="checkbox"/> Practical Radio & Electronics (with KIT) | <input type="checkbox"/> Radio Amateur's Exam. | <input type="checkbox"/> MECHANICAL |
| <input type="checkbox"/> Electronic Engineering Certificate | <input type="checkbox"/> AUTO & AERO | <input type="checkbox"/> A.M.S.E. (Mech.) |
| <input type="checkbox"/> General Elect. Eng. Certificate | <input type="checkbox"/> Motor Mechanics | <input type="checkbox"/> General Mech. Eng. |
| <input type="checkbox"/> C. & G. Elect. Installations | <input type="checkbox"/> C. & G. Motor V. Mechanics | <input type="checkbox"/> Inst. Engineers & Technicians |
| <input type="checkbox"/> Elect. Install. & Work | <input type="checkbox"/> General Auto Engineering | <input type="checkbox"/> Maintenance Engineering |
| <input type="checkbox"/> C. & G. Elect. Technicians | <input type="checkbox"/> A.M.I.M.I. | <input type="checkbox"/> Welding |
| <input type="checkbox"/> RADIO & TELECOM-MUNICATIONS | <input type="checkbox"/> Air Registration Board Certs. | <input type="checkbox"/> MANAGEMENT & PRODUCTION |
| <input type="checkbox"/> Colour TV Servicing | <input type="checkbox"/> M.A.A./I.M.I. Dip. | <input type="checkbox"/> Computer Programming |
| <input type="checkbox"/> C. & G. Telecoms. Technician's Cert. | <input type="checkbox"/> CONSTRUCTIONAL | <input type="checkbox"/> Inst. of Cost & Managements Accts. |
| <input type="checkbox"/> C. & G. Radio, TV & Electronics Mech. Cert. | <input type="checkbox"/> Heating, Ventilating & Air Conditioning | <input type="checkbox"/> DRAUGHTS-MANSHIP & DESIGN |
| <input type="checkbox"/> Radio & TV Engineering Course | <input type="checkbox"/> Architectural Draughtsmanship & Design | <input type="checkbox"/> General Draughtsmanship |
| | <input type="checkbox"/> L.I.O.B. | <input type="checkbox"/> A.M.I.E.D. |
| | <input type="checkbox"/> Carpentry & Joinery | <input type="checkbox"/> Electrical Draughtsmanship |
| | <input type="checkbox"/> Plumbing Technology | |
| | <input type="checkbox"/> General Building | |



G.C.E.
—58 'O' & 'A' Level Subjects
—over 10,000 Group Passes!

Aldermaston College

Dept. TPW 22, Reading RG7 4PF.

also at our London Advisory Office, 4 Fore Street Avenue, Moorgate, London EC2Y 5ET. Tel. 628 2721.

NAME (Block Capitals)

ADDRESS

..... Postcode.....

Other subjects of interest..... Age.....

Accredited by C.A.C.C. Member of A.B.C.C.

HOME OF BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY

COMPLETE digital clock kits REAL TEAK CASE



NON ALARM £12-50 + VAT + £1-00
ALARM £15-28 + VAT + £1-22
INCLUDING P & P

TEAK OR PERSPEX CASE 6" x 2 1/2" x 3"

FEATURES: 4 Red 1/2 inch high LEDs. 12 hour display with AM/PM indication Power failure indicated by flashing display. Precise accuracy from mains frequency. Beautiful Burma Teak case or stylish Perspex (State first & second colour choice: White, Red, Blue, Green, Black). Complete kit including Teak Case £13-50 incl. Module Kit excluding case £9-50 incl.

NON ALARM ALARM EXTRAS: Pulsed alarm tone. Tilt operated "Snooze" period. Automatic brightness control. Simple setting.

ALARM: Complete kit including Teak case £16-50 incl. Module Kit excluding case £13-00 incl

PERSPEX CASES: 50p LESS than Teak

READY BUILT: Extra £1-00 on complete clocks. Extra 50p on Modules.

TIMER FACILITY: Count in seconds up to 9m 59sec. Extra 50p.



"ALPHA" £12-00 incl.
Ready Built. Non Alarm. Perspex only. 4 digits phosphorescentgreen. 1 1/2" high 12 or 24 hour display.

Discount on orders over 5 clocks or kits. Overseas: Add £2-50 for Airmail.



Send payment with order. SAE for details.

PULSE ELECTRONICS LTD
(PW 1) 6 GOWER ROAD,
ROYSTON, HERTFORDSHIRE
Phone Royston (0763) 43695

Doram kits DORAM KITS CONTAIN EVERYTHING DOWN TO THE LAST NUT!



£5.70
+ S

Dwell Meter

IDEAL FOR THE D-I-Y MOTORIST!

£5.70 + S VAT Subject to availability
(Order code 991-568)

The Dwell Meter permits easy adjustment of worn or pitted contact breakers, based on the electrical contact time and not on the mechanical distance between the points. The improved accuracy obtainable by using this self contained unit, ensures greater precision than may be obtained using Feeler Gauges.


O'seas orders—add 15% for P+P. All items offered for sale subject to the Terms of Business set out in Doram Edition 3 catalogue, price 60p. The Doram Kit brochure is also available, price 25p. Combined price only 70p which also entitles you to 2 x 25p vouchers, each one usable on any order placed to the value of £5 00 or more (ex. VAT).

DORAM ELECTRONICS LTD.
P O BOX TR8, WELLINGTON RD. IND EST., LEEDS LS12 2UF.
An Electrocomponents Group Company

30x30 WATT AMPLIFIER KIT

Specially designed by RT-VC for the experienced constructor, this kit comes complete in every detail. Same facilities as Viscount IV amplifier. Chassis is ready punched; drilled and formed Cabinet is finished in teak veneer. Silver fascia and easy-to-handle aluminium knobs. **£29.00**
Output 30+30 watts rms, 60+60 peak.


+ p & p £2.10

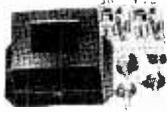

4x4 STEREO AMP

KIT £14.50 P & P £2.00

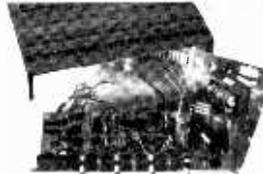For the experienced constructor who wants to design his own stereo, kit includes all necessary components including constructors manual. Plus Pair of easy to build 4 watt speakers in kit form, with teak simulate finish cabinets 12" x 9" x 5" approx



FANTASTIC SAVING.

sinclair NEW I.C. 20, 20 WATTS STEREO AMPLIFIER KIT WITH PZ 20 POWER UNIT


A build-it-yourself stereo power amplifier with latest integrated circuitry. 10W RMS per channel output, full short-circuit and overheat protection. **£5.95** OUR PRICE - p & p £1

Complete with PZ20 Power Supply LIST £14.50




35-WATT DISCO AMP

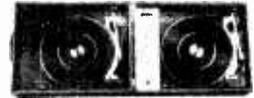Here's the mono unit you need to start off with. Gives you a good solid 35 watts rms, 70 watts peak output. Big features include two disc inputs, both for ceramic cartridges, tape input and microphone input. Level mixing controls fitted with integral push-pull switches. Independent bass and treble **£27.50** - p & p £1.50



PORTABLE DISCO CONSOLE with built-in pre-amplifiers

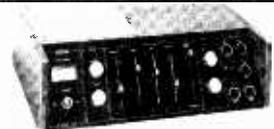Here's the big-value portable disco console from RT-VC! It features a pair of BSR MP 60 type auto-return, single-play professional series record decks. Plus all the controls and features you need to give fabulous disco performances. Simply connects into your existing slave or external amplifier. **£64.00** - p & p £6.50



70 & 100 WATT DISCO AMPS

Brightly styled for easy disco performance! Sloping fascia, so that you can use the controls without fuss or bother. Brushed aluminium fascia and rotary controls. Five smooth-acting, vertically mounted slide controls - master volume, tape level, mic level, deck level, PLUS INTER-DECK FADER for perfect graduated change from record deck No. 1 to No. 2, or vice versa. Pre-fade level control (PFL) lets YOU hear next disc before fading it in. VU meter monitors output level 70 watts rms, 140 watts peak output. All the big features as on the 70-watt disco amplifier, but with a massive 100 watts rms, 200 watts peak output power.

70 WATT **£49.00** - p & p £3.00
100 WATT **£65.00** - p & p £4

DIY SPEAKER KITS

EASY-TO-BUILD WITH ENCLOSURE

Specially designed by RT-VC for cost-conscious hi-fi enthusiasts, these kits incorporate two teak-simulate enclosures, two EMI 13" x 8" (approx.) woofers, two tweeters and a pair of matching cross-overs. Easily constructed, using a few basic tools. Supplied complete with an easy-to-follow circuit diagram, and crossover components. Input 15 watts rms. 30 watts peak, each unit. **£25.50** PER PAIR - p & p £5.50 (approx.)




15-WATT KIT IN CHASSIS FORM

When you are looking for a good speaker, why not build your own from this kit. It's the unit which we supply with the above enclosures. Size 13" x 8" (approx.) woofers, (EMI) tweeter and matching crossover. Power handling capacity 15 watts rms, 30 watts peak.

'COMPACT' FOR TOP VALUE

How about this for incredible bookshelf value from RT-VC! A pair of high efficiency units for only £7.50 - just what you need for low-power amplifiers. These infinite baffle enclosures come to you ready milled and professionally finished. Each cabinet measures 12" x 9" x 5" (approx.) deep, and is in wood simulate Complete with two 8" (approx.) speakers for max. **£7.50** per pair power handling of 7 watts. + p & p £1.70

20x20 WATT STEREO AMPLIFIER

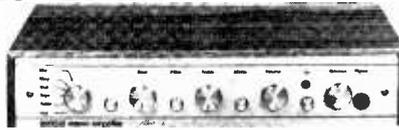

£29.90 - p & p £2.10

Superb Viscount IV unit in teak-finished cabinet. Silver fascia with aluminum rotary controls and pushbuttons, red mains indicator and stereo jack socket. Function switch for mic, magnetic and crystal pick-ups, tape, tuner, and auxiliary. Rear panel features two mains outlets, DIN speaker and input sockets, plus fuse. 20 + 20 watts rms, 40 + 40 watts peak.

HOW YOU CAN SAVE

SYSTEM 1B For only £80, you get the 20+20 watt Viscount IV amplifier, a pair of our 12-watt-rms Duo Type 1lb matched speakers; a BSR MP 60 type deck complete with magnetic cartridge, de luxe plinth **£80.00** - p & p £10.00
Carnegie surcharge to Scotland System 1B £2.50 System 2 £5.00

SYSTEM 2 Comprising our 20+20 watt Viscount IV amplifier; a pair of our large Duo Type III matching speakers which handle 20 watts rms each, and a BSR MP 60 type deck with magnetic cartridge, **£92.00** de luxe plinth and cover. - p & p £10.00

SPEAKERS Two models - Duo 1lb, teak veneer, 12 watts rms, 24 watts peak, 18 1/2" x 13 1/2" x 7 1/4" approx. **£34** PER PAIR - p & p £6.50
Duo III, 20 watts rms, 40 watts peak, 27" x 13" x 11 1/2" approx. **£52** PER PAIR - p & p £7.50



TURNTABLE Popular BSR MP 60 type, complete with magnetic cartridge, diamond stylus, and de luxe plinth and cover. **£29.00** - p & p £4.50



PYE STEREO GRAM CHASSIS

complete with circuit diagrams

Complete ready to install - Wave bands L, M, VHF STEREO, VHF MONO. Controls for tuning volume, balance, bass and treble. Power output 7 watts R.M.S. per channel 14 watts peak into 8 ohms. 2 x 8" approx. chassis speakers and BSR C141 auto record player deck. **£35.00**

CAR RADIO KIT



Complete with speaker, baffle and fixing strip. The Tourist IV for the experienced constructor only. The Tourist IV has five push buttons, four medium band and one for long wave band. The tuning scale is illuminated and attractive small aluminium control knobs are used for manual tuning and volume control.

The modern style fascia has been designed to blend with most car interiors and the finished radio will slot into a standard car radio aperture. Size approx 7" x 2" x 4". Power Supply Nominal 12 volts positive or negative earth (altered internally) Power Output 4 watts into 4 ohms **£12.50** - p & p £1.50

MOTOR TOP 10 AWARD



BSR T145 8-TRACK CARTRIDGE PLAYER MECHANISM

Requires some attention. Complete with built in pre-amp, A.C. 240V **£6.95** - p & p £1.50

SPECIAL OFFER

ALL PRICES INC. VAT. AT 12 1/2%

GOODS NOT DESPATCHED OUTSIDE UK All items subject to availability. Price correct at 1/4/77 and subject to change without notice DO NOT SEND CARD We are unable to show all our products, so please Just write your order Send stamped addressed envelope for our giving your credit card number fully descriptive catalogue and any further information.



21c HIGH STREET, ACTON, LONDON W3 6NG
323 EDGWARE ROAD, LONDON W2


Personal Shoppers EDGWARE ROAD 9am - 5.30p.m., Half day Thurs
ACTON: Mail Order only No callers

Incredible Value in Precision Test Meters

AVAILABLE FROM SELECTED STOCKISTS. WRITE OR PHONE FOR LIST

MICROTEST 80—I.C.E. 20,000 Ohms/Volt 40 RANGES

20,000 Ohms/Volt, (d.c.) 4,000 Ohms/Volt (a.c.) 2% accuracy. V d.c. 100mV to 1kV (6 Ranges). I d.c. 50µA to 5A (6 Ranges). V a.c. 1.5V to 1kV (5 Ranges) I a.c. 250µA to 2.5A (5 Ranges). Resistance, Low Ohms, Ohms×1, Ohms×10, Ohms×100. Output Level Measurements 1.5V to 1000V (5 Ranges) + 6dB to + 62dB (5 Ranges). Capacitance 25µF to 25,000 µF (4 Ranges). 1000 times overload protection (on Resistance ranges). Meter movement diode protection. Size (without case) 90×70×18mm. Automatic zero, non-parallax mirror scale. Unbreakable carrying case and probes supplied. Full After Sales Service available. Price £16.15 inc. VAT

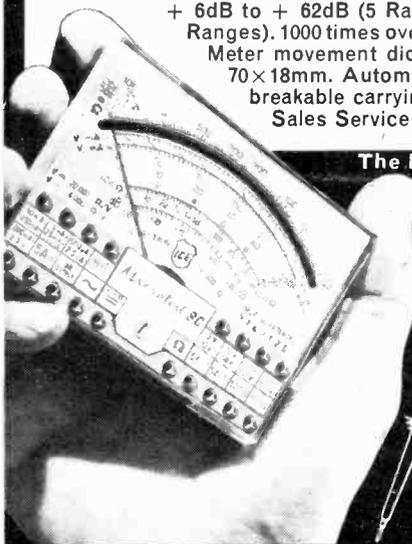


The I.C.E. Measurement System includes a comprehensive range of accessories: shunts, transformers, specialised probes, transistor-tester etc. I.C.E. High-Voltage d.c. Probe, Model 18. Input Impedance: 500M Ohm, nominal (Other values available to order). The Model 18 d.c. Probe consists of a highly insulated moulded plastic body, fitted with a hand guard-ring, containing a stable, precision 500M Ohm resistor, which may be used to extend the d.c. voltage measuring capability of analogue multi-meters or electronic voltmeters, to a maximum value of 25kV. The probe is fitted with a prod-tip for connection to the voltage source to be measured and a connecting lead terminating in a 2mm plug for insertion into the measuring instrument's d.c. voltage input socket. (4mm plug available to order). £6.42 inc. VAT

SUPER TESTER 680R—I.C.E.

20,000 Ohms/Volt 80 RANGES

20,000 Ohms/Volt 1% d.c. 4,000 Ohms/Volt a.c. 2% V d.c. 100mV to 2kV (13 ranges). V a.c. 2V to 2kV (11 Ranges). I d.c. 50µA to 10A (12 Ranges). I a.c. 250µA to 5A (10 Ranges). Resistance Ohms × 1, × 100, × 1000, × 10,000 and Low Ohms. Reactance Detector 0-10M Ohms. Freq. Measurement 0-5000 Hz (2 Ranges). Output Level 10-2000V (9 Ranges). Decibels —24+70dB (10 Ranges). Capacitance 0-500,000 pF (2 Ranges using mains supply) 0-20,000 µF (4 Ranges using internal 3 Volt battery). 1000 times overload protection on Resistance ranges and meter movement diodes protection. 10 Measurement Functions and 80 Ranges. Size 128 × 95 × 32mm. Non-parallax mirror scale. Unbreakable carrying case supplied which contains probes, mains lead, crocodile clips and shorting link. Price £27.27 inc. VAT

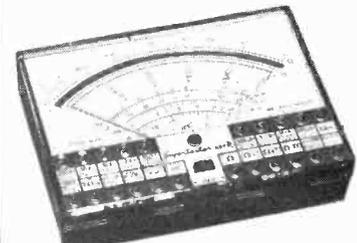

Sole Importers and Distributors

Electronic Brokers Ltd

49-53 Pancras Rd., London NW1 2QB. Tel: 01-837 7781

YES SIR 1st class post TONIGHT!
The service is available to anyone that opens an account.



HIGH SPEC components FAST!

Agents for VERO - ANTEX - BIB MULTICORE SOLDER

- Open 9am-5pm, 6 days—Phone orders 9am-4pm.
- S.A.E. for stock list including pots, presets, I.C.'s 7400 & CMOS.
- capacitors, plugs, sockets, switches, cable, valves, meters, books, etc.
- Post free envelope included for your next order.
- SUPER EXPRESS phone service—ask for details.
- Shop at keen prices 6 days per week. Late night—Fri. 7-10pm.
- Discounts £5-5%, £10-7%, £15-10%.

TRANSISTORS + 200 OTHER TYPES IN STOCK

AC125 26p	BC109B 13p	BC262A 19p	BFX29 26p	TIP41A 67p
126 26p	109C 13p	287 28p	84 22p	42A 80p
127 28p	117 18p*	300 35p	88 22p	TIS43 35p
128 20p	142 24p	301 34p	BFY50 25p	ZTX300 13p*
151 35p	143 24p	303 35p	51 25p	302 18p*
153 35p	147A 9p*	338 16p*	52 25p	55p*
176 22p	147B 10p*	557 15p*	BY164 40p	502 18p*
187 22p	148 9p*	BCY71 18p	ME0401 18p*	1N914 5p
188 20p	148B 10p*	72 14p	O411 18p*	1N4001 5p
AD149 68p	149B 11p*	BD123 90p	ME4001 10p*	4002 6p
161 52p	149C 11p*	124 90p	4101 11p*	4005 9p
162 52p	154 18p*	131 42p	MPF102 40p*	4006 10p
MCH/PR 1-24	157B 14p*	132 42p	OA47 14p	4148 35p
AF116 24p	177 17p	139 54p*	90 7p	2N2219 10p
117 28p	178B 18p	155 75p*	91 8p	2646 45p
124 30p	179B 19p	BF158 20p*	200 10p	2926O 13p*
239 46p	184B 12p*	184 25p	OC28 1-20	2926G 15p*
ALU13 1-72*	184L 11p*	185 28p	29 1-20	3053 25p
BC107 11p	187 26p	194 10p*	35 1-20	3055 60p
107A 12p	212A 13p*	196 12p*	44 45p	3702 11p*
108 10p	212L 15p*	197 12p*	71 35p	3703 14p
BC108B 11p	213B 12p*	199 15p*	ORP12 68p	3704 13p*
108C 12p	214 15p*	200 38p	TIP29A 47p*	3705 14p
109 12p	214L 17p*	328 34p	30A 56p*	3707 12p*
		BFW11 68p	31A 57p	3819E 25p*

DIODES	BRIDGES	RESISTORS 1p* each	LINEAR I/C's
50V 3A 13p	100V 1A 28p	WATT E12 (5%)	741 28p
100V 3A 15p	400V 1A 32p	1 ohm - 10m ohm	LM380 SL607451-29*
200V 3A 18p	200V 2A 98p	ZENERS (400mw) BZX83	LM390N 68p
400V 3A 21p	600V 2A 1-40	3V, 3V3, 5V1, 5V6, 7V5, 9V1, 10V, 12V, 18V, 22V, 30V. All at 12p* each.	NE555 49p
THYRISTORS		LED T11 209/0 125 0-2"	SN76013ND 1-60*
60V 1A 25p		Red 20p	SN76013N 1-75*
60V 1A 80p TAG 1 600		Red 20p	SN76023N 1-75*
400V 4A 1-40 BT106		Clps for above 3p.	TBA800 1-35*
400V 4A 65p C106D1			TBA810S 1-49*
50V 6A 1-85 BT109			TBA920 1-20*
			ZN414 1-40*

Post & Packing 25p per order. VAT please add to total * 12½%, rest 8%
ORCHARD ELECTRONICS
FLINT HOUSE, HIGH STREET, WALLINGFORD, OXON, OX10 0DE
Telephone 0491 35529

DORAM kits

DORAM KITS CONTAIN EVERYTHING DOWN TO THE LAST NUT!

ELECTRONIC CAR IGNITION

£9.95 + S



£9.95 + S VAT
(Order code 997-005) Subject to availability

Avoid difficulty in starting your car on cold mornings with the Doram C.D. Ignition Unit. The complete kit incorporates features such as single switch reversion to the standard ignition system for servicing etc. and also an immobilisation facility. Improved performance and fuel consumption, along with reduced points erosion and longer plug life makes this unit a must for any 12V neg. earth car.

O'seas orders—add 15% for P+P. All items offered for sale subject to the Terms of Business set out in Doram Edition 3 catalogue, price 60p. The Doram Kit brochure is also available, price 25p. Combined price only 70p which also entitles you to 2x25p vouchers, each one usable on any order placed to the value of £5.00 or more (ex. VAT).

DORAM ELECTRONICS LTD.
P.O. BOX TR8, WELLINGTON RD. IND. EST., LEEDS LS12 2UF.
An Electrocomponents Group Company

SAXON ENTERTAINMENTS LTD

A FULL RANGE OF MODULES & READY-TO-USE EQUIPMENT TO PROFESSIONAL STANDARDS FOR THE PROFESSIONAL
SYSTEM 7000 COMPLETE & READY-FOR-USE EQUIPMENT

POWER AMPLIFIER MODULES 30-240 WATTS



- Fully tested & guaranteed.
- Full RMS Sine Wave output.
- Distortion typically 0-2%
- 10 Transistors, 4 Diodes.
- Response 30HZ-30KHZ
- Fully short & open circuit proof
- Sensitivity suits most mixers.
- Built-in surge suppression & compensation
- Twin D.C. & output fuses.
- Top-grade components throughout.

30 Watts rms		60 Watts rms		120 Watts rms		240W rms	
SA308 30W rms/ 8 ohms £9-50	SA604 60W rms/ 4 ohms £12-50	SA608 60W rms/ 8 ohms £13-50	SA1204 120W rms/ 4 ohms £14-50	SA1208 120W rms/ 8 ohms £21-00	SA2404 240W rms/ 4 ohms £25-50		

POWER SUPPLIES FOR THE ABOVE MODULES—READY WIRED & FUSED ON GLASS FIBRE PCB

PM301 For 1/2 £9-90	PM601/4 For 1/2 £12-50	PM601/8 For 1/2 £12-50	PM1201/4 For 1 SA1204 £12-50	PM1201/8 For 1 SA1208 £12-50	PM1202/4 For 2 SA1204 £19-50	PM1202/8 For 2 SA1208 £19-50	PM2404/1 For 1 SA2404 £19-50
---------------------------	------------------------------	------------------------------	---------------------------------------	---------------------------------------	---------------------------------------	---------------------------------------	---------------------------------------

SYSTEM 7000 COMPLETE DISCO MIXERS (With Autofade)

Mono or Stereo



- Ready to plug in & use
- Automatic Mic override
- Two tone panel
- Twin deck & mic & tape inputs
- Left/Right deck fader
- 20mZ-20kHZ Noise —77 dB

The choice of the professional D.J.

Controls: Mic volume, Bass, Treble, A/Fade Depth, Tape, L/Deck, R/Deck volumes, Bass, Treble, Master, Headphone volume, Selector & On/Off.

Mono 18v £37-50 Mains £43-50 Stereo 18v £53-50 Mains 59-50

IN MODULAR FORM— All you require is front panel (see below) knobs & sockets etc. All electronics are assembled & tested.

- Specification as for complete mixer
- All Potentiometers supplied & fitted
- Low cost do it yourself with step by step easy to follow instructions.

Mono £19-50 Stereo £29-50 Panel £3-50 Supply unit £8-50

SYSTEM 7000 LIGHTING CONTROL UNIT MK II (Four channel)



Has your light unit got ?

- 4,000 W handling
- Sequence facility
- Smart 2 tone panel
- Advanced IC circuitry
- Top grade components
- All your needs in one superbly designed unit

- Integral dimmers
- Automatic audio level

OURS HAS!

ONLY £42-50

IN MODULAR FORM—THE QUADRAFACT

As with the mixers the Mk II L.C. unit may be purchased in module form with all controls, requiring only a panel, case & knobs etc. There are 13 simple connections

- 1-240w Audio
- 8A RCA tracs
- 0.5-20Hz Sequence
- Fully suppressed

CUSTOM MIXER MODULES (Complete or in printed circuit form only)

Make your own mixer, mono or stereo, up to 2 channels, with full monitoring facilities, and provision for echosend/return etc.

- Inputs for low and high 2 mic, ceramic & magnetic cartridge etc.
- Up to 20 input modules per single mixing module
- Feed most types of amplifier—accepts all inputs
- Professional low noise circuitry 20 Hz-30kHZ
- Infinitely adaptable—Extremely economical



COMPLETE MODULES With facia panel.

Knobs & sockets, Monitor buttons, Ready wired & tested

Mono Input £8-50 Mono mixing stage £8-50
 Stereo Input £12-00 Stereo mixing stage £12-00

- 0.5W headphone circuit
- Full range bass/treble controls
- Noise—80dB

PRINTED CIRCUIT MODULES With controls fitted, requires only sockets, facia & knobs

Mono Input £5-50 Mono mixing stage £5-50
 Stereo Input £9-00 Stereo mixing stage £9-00

Power supply for up to 20 channels—PPM18—£8-50.

SYSTEM 7000 SOUND—LITE (3-CHANNEL)

IN COMPLETE OR MODULAR FORM

(Modular form illustrated)

- Complete unit similar to Mk II unit above
- Long established & proven design
- 3 Channels—100W per channel
- RCA 8A Tracs—individual channel fuses
- 1-240 W Input—master audio level plus Bass/Middle/Treble



COMPLETE UNIT—Fully cased with rear terminations—just plug in & go! £24-75

MODULAR FORM Facia & knobs etc. Needs only 11 simple connections £16-50 (Panel £2-50)

CENTAUR—THE 100W RMS STEREO DISCO COMPLETE WITH SOUND-TO-LIGHT SEQUENCER & LIGHTS

ONLY £225 (+4-50 carr) or Low Interest terms Deposit £24-78 12 months at £18-77 or 24 months at £10-05

- 100W RMS stereo output
- Twin heavy duty loudspeaker
- Four channel sound lite—sequencer complete with display
- Separate mic., music bass & treble controls
- Sturdy vinylite cabinets with all leads
- Twin BSR decks with lift arm



NOW AVAILABLE
SUPER CENTAUR

200W Stereo output—other details as above £275 (carr. 4-50) or Deposit £31-00 12 months at £25-03 or 24 months at £14-20 Cut-price condenser mic & headphones £15-00 (only with complete discs)

SAXON MINI-DISCO 50W RMS £139-50 (carr. £2-50) 100W RMS £159-50


- C/W heavy output loudspeaker
- 100W version has twin speakers
- Includes mic Input & headphone monitor circuit
- Twin BSR decks with lift arm
- Tremendous value—just plug in & go
- Wide range bass & treble controls



Cut-price condenser mic & headphones £15-00 (only with complete discs)

SEND YOUR SPECIAL REQUIREMENTS FOR A CUSTOM DISCO QUOTATION

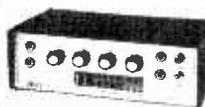SYSTEM 7000 MINOTAUR 100—All Purpose Wide Range Amplifier



- 100W rms — 1dB
- Standard 8 ohm output
- Twin mixed inputs accept a wide range of signals
- 30HZ-30KHZ ±2dB
- 23dB bass/treble

A four input, high power amplifier which will deliver up to 150 watts output. An absolute must where multiple mixing & power are required

- Four individually mixed inputs
- Wide range bass/treble + master

An extremely compact and versatile amplifier with full protection and a clean, attractive appearance. Ideal for all groups, disco's & clubs

- Vinylite covered case
- Fully short proof
- Superb value for money



£49-50

SAXON 150 HEAVY DUTY AMPLIFIER £59-00

STROBES & PROJECTORS (We stock the full Pluto range) Send for details

SUPERSTROBE £19-75

- 2-3 Joules
- 60W Tube for long life
- Compact 4" x 4" x 4"

PRO-STROBE £32-50

- 6-8 Joules
- External trigger
- Long Life tube timer circuit



150 WATT LIQUID WHEEL PROJECTOR

- Accepts all accessories
- C/w with wheel & motor plate
- Sturdy steel construction
- Remarkable value—Sold elsewhere at £39-50. Our price is only: £33-00

ACCESSORIES

Condenser mic ECM77 600 ohm £13-50
 ECM 81 Dual Impedance £14-95 Crown headphones £6-75
 Heavy duty boomstand £14-50

All prices subject to VAT @ 8% except SA308/PM301, mics. & headphones (12 1/2%) Add 50p post & packing on all orders except where already shown.
 Ordering: By Telephone—Access, Barclay Card or COD Ring (01) 684 6385/0098 By post —Send cheque or crossed P.O.'s or 60p for COD or send in your Access/Barclay card NUMBER ONLY

MAIL ORDERS & CALLERS TO: CROYDON

327-333 Whitehorse Road, Croydon Surrey CR0 2HS
 24 Hour Ansafone service (01) 684 6385

PIEZO HORNS!! UP TO 150 WATTS HANDLING. NO X-OVER REQUIRED £7-50 ea.

Exporters to 17 countries—enquiries welcomed
 Ring Sue Abegg on (01) 684 6385 for U.K. trade enquiries


BENTLEY ACOUSTIC CORPORATION LTD.

7A GLOUCESTER ROAD, LITTLEHAMPTON, SUSSEX
All prices inclusive of V.A.T. at 12½% Telephone 6743

0A2	-85	6AW8A	-84	6J7G	-85	12HA6	-80	35A3	-75	DF92	-85	ECC087	2-80	RM56	1-90	PC695	-47	PT800	-50	U403	-90	ACY17	-90	BY114	-81
0B2	-40	6AX4	-75	6JUBA	-90	12HB6	-85	35C5	-80	DF96	-80	ECC088	-50	RM57	1-10	PC698	-41	PT801	-50	U404	-75	ACY18	-83	BY126	-18
0Z4	-55	6BBG	-85	6K7G	-85	12HC7	-85	35D5	-90	DK40	-70	ECC089	-50	RM58	1-10	PC699	-49	PZ30	-50	U801	-80	ACY19	-83	BY127	-81
1A3	-80	6BA6	-40	6KR9	-80	12HY7	-85	35L8GT	-80	DK92	-100	ECC090	-50	RM59	1-10	PC700	-52	QV03/10	-50	U4020	-75	ACY20	-82	BY210	-80
1ABGT	-55	6BC8	-90	6KR8GT	-85	12IE1	3-80	35W4	-55	DK96	-70	ECC091	2-00	RY61	-45	PCF80	-45	2-00	VP23	-85	ACY21	-83	BY211	-80	
1AYGT	-60	6BE6	-40	6LI1	2-50	12J5GT	-40	35Z3	-80	DL96	-80	ECC092	1-00	RY61	-45	PCF82	-45	Q895/10	-50	VP41	-80	ACY22	-18	BY212	-80
1BGT	-55	6BH6	-70	6L6GC	-70	12J7GT	-70	35Z4GT	-80	DM70	-80	ECC093	-40	RY83	-60	PCF84	-70	1-00	VR105	-80	ACY23	-81	BY213	-80	
1HBGT	-80	6BJ6	-65	6L7	-80	12K5	-180	35Z6GT	-80	DM71	1-75	ECC094	-40	RY84	1-20	PCF86	-57	Q8150/15	-80	VT111	1-00	AD149	-42	BY214	-80
1L4	-55	6BK7A	-85	6L18	-60	12K7GT	-80	42	1-50	DY87/8	-85	ECC095	-50	RY87	-87	PCF200/1	-80	1-80	VT120	1-00	AD149	-42	BY215	-80	
1NSGT	-75	6BQ7A	-80	6L19	2-00	12K8	-75	43	1-25	DY802	-50	ECC096	-40	RY88	-55	PCF201	1-00	QV04/73	-100	VT133	1-00	AD161	-83	0A9	-14
1R5	-50	6BR7	1-00	6LD20	-80	12Q7GT	-50	50B5	-95	E800C	2-50	ECC097	-40	RY91	-55	PCF801	-49	1-19	W107	7-5	AD162	-83	0A47	-18	
1R4	-40	6BR8	1-25	6N7GT	-70	12BCT	-50	50C5	-70	E800F	5-00	ECC098	-40	RY92	-55	PCF802	-49	1-19	W107	7-5	AD162	-83	0A47	-18	
1T4	-80	6BS7	1-70	6Q7G	-50	12BCT	-50	50D5	-80	E800G	2-00	ECC099	-40	RY93	-55	PCF803	-49	1-19	W107	7-5	AD162	-83	0A47	-18	
1U4	-70	6BW6	1-70	6Q7GT	-50	12BCT	-50	50E5	-80	E800H	1-00	ECC100	-40	RY94	-55	PCF804	-49	1-19	W107	7-5	AD162	-83	0A47	-18	
1U5	-85	6BW7	-55	6Q7M	-55	12BCT	-50	50EH5	-80	E800I	1-75	ECC101	-40	RY95	-55	PCF805	-49	1-19	W107	7-5	AD162	-83	0A47	-18	
2D1	-55	6BZ6	-60	6R7G	-70	12BCT	-50	50L6GT/1	-90	E800J	1-15	ECC102	-40	RY96	-55	PCF806	-49	1-19	W107	7-5	AD162	-83	0A47	-18	
3GK3	-75	6C4	-40	68A7	-55	12BCT	-50	50M2	-75	E800K	3-00	ECC103	-40	RY97	-55	PCF807	-49	1-19	W107	7-5	AD162	-83	0A47	-18	
2X2	-70	6C5G	-60	68C7GT	-75	1A47	-75	85A3	-75	E188CC	3-00	ECC104	-40	RY98	-55	PCF808	-49	1-19	W107	7-5	AD162	-83	0A47	-18	
3A4	-55	6C6	-45	68G7	-50	1A87	-100	150B2	-80	E188CC	3-00	ECC105	-40	RY99	-55	PCF809	-49	1-19	W107	7-5	AD162	-83	0A47	-18	
3D6	-40	6C9	2-00	68H7	-55	19AQ5	-85	15B5G	-90	E188CC	2-50	ECC106	-40	RY00	-55	PCF810	-49	1-19	W107	7-5	AD162	-83	0A47	-18	
3Q4	-40	6CB6A	-50	68J7	-80	19G6	6-80	807	1-10	E1148	-60	ECC107	-40	RY01	-55	PCF811	-49	1-19	W107	7-5	AD162	-83	0A47	-18	
3Q5GT	-70	6CD6A	1-60	68KGT	-55	19H1	1-00	1825	2-50	E1A50	-40	ECC108	-40	RY02	-55	PCF812	-49	1-19	W107	7-5	AD162	-83	0A47	-18	
3B4	-55	6CG6A	-90	68Q7	-80	20P1	-70	8702	1-20	E1A78	1-00	ECC109	-40	RY03	-55	PCF813	-49	1-19	W107	7-5	AD162	-83	0A47	-18	
3V4	-80	6CH8A	-75	6V8G	-80	20P2	-85	8763	1-65	E1A80	-40	ECC110	-40	RY04	-55	PCF814	-49	1-19	W107	7-5	AD162	-83	0A47	-18	
4CB6	-75	6CLA8A	-85	6V8GT	1-00	20L1	1-20	6057	1-00	E1A81	-55	ECC111	-40	RY05	-55	PCF815	-49	1-19	W107	7-5	AD162	-83	0A47	-18	
5C08	-75	6CM7	1-00	6X4	-45	20P1	1-00	6060	1-00	E1A82	-55	ECC112	-40	RY06	-55	PCF816	-49	1-19	W107	7-5	AD162	-83	0A47	-18	
5R4GY	1-00	6C5U	-90	6X5GT	-45	20P3	1-00	6067	1-00	E1A83	-75	ECC113	-40	RY07	-55	PCF817	-49	1-19	W107	7-5	AD162	-83	0A47	-18	
5U4G	-80	6D3	-75	7B6	-80	20P4	-84	8463	-80	E1B34	-80	ECC114	-40	RY08	-55	PCF818	-49	1-19	W107	7-5	AD162	-83	0A47	-18	
5V4G	-60	6DE7	-90	7B7	-80	20P5	1-80	7025	1-50	E1B35	-80	ECC115	-40	RY09	-55	PCF819	-49	1-19	W107	7-5	AD162	-83	0A47	-18	
5Y3GT	-85	6DT6A	-85	7H7	-80	26A8G	-70	7193	-80	E1B36	-45	ECC116	-40	RY10	-55	PCF820	-49	1-19	W107	7-5	AD162	-83	0A47	-18	
5Z3	1-00	6E2W6	-85	7R7	2-00	25L6G	-70	9002	-55	E1B37	-45	ECC117	-40	RY11	-55	PCF821	-49	1-19	W107	7-5	AD162	-83	0A47	-18	
5Z4G	45	6E5	-1-00	7Y4	-80	25Y5G	-80	9008	-45	E1B38	-45	ECC118	-40	RY12	-55	PCF822	-49	1-19	W107	7-5	AD162	-83	0A47	-18	
5Z4GT	-55	6F1	-80	7Z4	-80	25Z4G	-50	ACPEN	1-20	E1B39	-45	ECC119	-40	RY13	-55	PCF823	-49	1-19	W107	7-5	AD162	-83	0A47	-18	
6B0L2	-75	6P6G	-80	8D2	-50	25Z5	-75	ACPEN	-80	E1B40	-45	ECC120	-40	RY14	-55	PCF824	-49	1-19	W107	7-5	AD162	-83	0A47	-18	
6ASG	1-40	6F13	-90	8D7	-70	25Z6G	-80	AL50	1-20	E1B41	-45	ECC121	-40	RY15	-55	PCF825	-49	1-19	W107	7-5	AD162	-83	0A47	-18	
6AC7	-55	6F14	-90	10C2	-70	28D7	2-00	ARF3	-60	E1B42	2-00	ECC122	-40	RY16	-55	PCF826	-49	1-19	W107	7-5	AD162	-83	0A47	-18	
6AC5	-65	6F15	-85	10DE7	-80	30A5	-75	ATP4	50	E1B43	-84	ECC123	-40	RY17	-55	PCF827	-49	1-19	W107	7-5	AD162	-83	0A47	-18	
6AG7	-60	6F18	-80	10P1	-87	30C15	-77	AZ1	-50	E1B44	-84	ECC124	-40	RY18	-55	PCF828	-49	1-19	W107	7-5	AD162	-83	0A47	-18	
6AE6	-70	6F23	-85	10P9	-65	30C17	-77	AZ1	-60	E1B45	-84	ECC125	-40	RY19	-55	PCF829	-49	1-19	W107	7-5	AD162	-83	0A47	-18	
6AJ5	-70	6F24	-80	10P18	-65	30F6	-70	AZ1	-60	E1B46	-84	ECC126	-40	RY20	-55	PCF830	-49	1-19	W107	7-5	AD162	-83	0A47	-18	
6AK3	-45	6F25	-1-00	10P18	-75	30L15	-75	B38	-75	E1B47	-84	ECC127	-40	RY21	-55	PCF831	-49	1-19	W107	7-5	AD162	-83	0A47	-18	
6AK6	-70	6F28	-74	10P13	-80	30L17	-70	BL63	2-00	E1B48	-84	ECC128	-40	RY22	-55	PCF832	-49	1-19	W107	7-5	AD162	-83	0A47	-18	
6AM3A	-70	6F32	-70	10P14	2-50	30P4MR	-98	CL33	1-75	E1B49	-84	ECC129	-40	RY23	-55	PCF833	-49	1-19	W107	7-5	AD162	-83	0A47	-18	
6AN8	-70	6G6G	-80	12A6	-85	30P12	-74	CY1C	1-00	E1B50	-84	ECC130	-40	RY24	-55	PCF834	-49	1-19	W107	7-5	AD162	-83	0A47	-18	
6AQ5	-88	6GH8A	-80	12AC6	-80	30P19/	-80	CY31	-70	E1B51	-84	ECC131	-40	RY25	-55	PCF835	-49	1-19	W107	7-5	AD162	-83	0A47	-18	
6AR5	-80	6GK5	-75	12AD6	-80	30P4	-90	DA1	-60	E1B52	-84	ECC132	-40	RY26	-55	PCF836	-49	1-19	W107	7-5	AD162	-83	0A47	-18	
6AS7G	1-00	6OU7	-90	12AE6	-80	30P11	1-00	DF91	-35	E1B53	-84	ECC133	-40	RY27	-55	PCF837	-49	1-19	W107	7-5	AD162	-83	0A47	-18	
6AT6	-50	6H6GT	-80	12AT6	-45	30P113	-100	DAF96	-80	E1B54	-84	ECC134	-40	RY28	-55	PCF838	-49	1-19	W107	7-5	AD162	-83	0A47	-18	
6AU6	-40	6J5GT	-80	12AU6	-60	30P114	1-80	DC90	-70	E1B55	-84	ECC135	-40	RY29	-55	PCF839	-49	1-19	W107	7-5	AD162	-83	0A47	-18	
6AV6	-80	6J6	-85	12AV6	-60	30P115	1-00	DF91	-80	E1B56	-84	ECC136	-40	RY30	-55	PCF840	-49	1-19	W107	7-5	AD162	-83	0A47	-18	

Special offer of EF50 valves, sealed, but new and tested, £1 each.

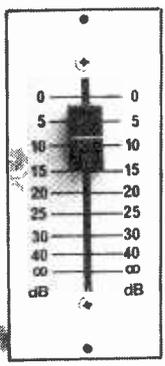All goods are unused, tested, and guaranteed. Despatch charges:—50p on all orders below £15 in value. Orders over £15 post free. Orders despatched same day as received. Any parcel insured against damage in transit for 5p per parcel extra. Terms of business available on request. Many others in stock too numerous to list. Please enclose S.A.E. for reply to any queries.



Mono or stereo 60mm track faders with anodised panels and cue switches as required.

These faders, although less than a third of the cost of our professional faders, are eminently suitable for small mixers, PA systems, disco's etc., where a consistent performance is required.

(send 8½p stamp for information sheet)

**AUDIOFAD, 46 West Way,
Bournemouth, Dorset
BH9 3EB**

PRACTICAL WIRELESS T.V. SOUND TUNER

(Nov. 75 article by A. C. Ainslie)

- IF Sub-Assembly (G8) £6-80. P & P 75p.
- Mullard ELC1043 Varicap UHF Tuner £4-20. P & P 30p.
- 3-way Station Control Unit £1-20. P & P 25p.
- 6-way Station Control Unit (Special Offer) £1-00.
- Resistors, Caps, Semiconds etc. £5-80. P & P 55p.
- Printed Circuit Board £1-00. P & P 30p.
- Mains Transformer £2-50. P & P 30p.


Add 12½% VAT to price of goods. P & P all items 85p.
Copy of original article supplied on request

Callers welcome at shop premises.

MANOR SUPPLIES

172 WEST END LANE, LONDON NW6
(Near W. Hampstead Tube Stn.) Tel. 01-794 8751

THE OPEN DOOR TO QUALITY

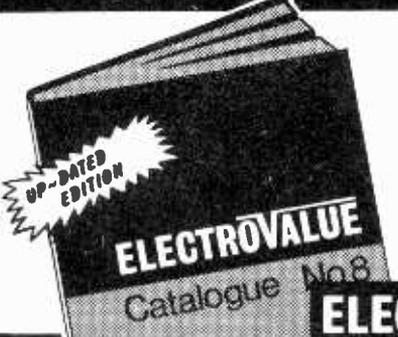

Latest revised issue (4th Edition, Cat. 8). Includes new ranges of meters and switches as well as price adjustments together with items from advanced opto-electronic components to humble (but essential) washers. Many things listed are very difficult to obtain elsewhere. The Company's own computer expedites delivery and maintains customer satisfaction. Attractive discounts are allowed on many purchases. ACCESS AND BARCLAYCARD ORDERS ACCEPTED.

144 pages
40p
POST PAID
inc. 40p Refund
Voucher

+ FREE POSTAGE on all C.W.O. mail orders in U.K. over £2-00 list value (excluding V.A.T.) If under, add 15p handling charge.

All communications to Dept. FW 5
28 ST. JUDES ROAD, ENGLEFIELD GREEN, EGHAM, SURREY
TW20 0HB. Tel Egham 3603. Telex 264476 Shop 9-5.30, 9-1 pm Sats
NORTHERN BRANCH: 680 Burnage Lane, Burnage, Manchester
M19 1NA. Tel: (061) 432 4945. Shop 9-5.30pm, 1 pm Sats.

GREENWELD

443 Millbrook Road Southampton
SO1 0HX Tel: (0703) 772501

THE GREENWELD DRAGON—GUARDIAN OF GOOD VALUE



TAPE DECKS

Reel to reel chassis, takes 7" spools. Single motor operation. Made by Telefunken. No heads or electronics, mechanics only. Diecast alloy frame 13 1/2 x 9 1/2 x 6 1/2" overall depth. Only £3-50. Data Tape Deck by D-Mac. Not much info., just arrived. Reel-to-reel, takes 3" spool. 2 heads, 12V motor. 3 position switch, 17 transistors, R's, C's, 200V 6A SCR, min 6V relay, etc. In good condition, but not new. Size 225 x 165 x 120mm high. £5-50.

BARGAIN PACKS - £1-50 EACH

K101 16 BC107
K102 17 BC108
K103 15 BC109
K104 35 1N4002
K105 30 1N4004
K106 25 1N4007
K107 50 1N4148
K135 7 741C
K136 4 555
K139 30 1/4F 25V caps

For full list of packs, see PE.

KEYBOARDS

Front half of calculator, really. Case 30 x 75mm has display window, 2 slide switches, and 25 keys. Only £1.

1 WATT AMPLIFIER

PCB 100 x 80mm with LM380 and associated components to make 1W amp operating from 9V. (Can be increased to 3W output by raising supply voltage and fitting heat sink). Complete with volume control. Connexion sheet included. Also on the board is a speed control circuit comprising 10 transistors, 2 presets, 4 pole 3 way switch, etc., but no data on this. Only £1.

POT PACKS

An overwhelming abundance of pots of all shapes and sizes, including duals, switches, sliders, etc., prompts us to make this offer: 20 asstd for £2-20, 10 for £3-50.

PO 4 DIGIT METERS

Ex-quip, 500R coil, operates on 18V only 40p, 10 for £3, 100 for £20.

RELAY UNITS

Units vary slightly, but a guaranteed minimum 20 relays, PO 3000 type, various coil resistances and contact arrangements. May be a few bent contacts, but excellent value at only £4-00. Parcel of PO 3000 type Relays—Lots of diff. types. Total 12 for £2-50.

SWITCHES

Wafer switches, 6p3w 30p. Wafer switch mechanism, 12 way. Room for 2 wafers. 15p. Wafers 1 file, 1p2w 20p, 1p 12w (few only) 40p. Bank of 5 push button switches, 4 or 6 pole c/o, Interlocking, 5th is independent dpco. No knobs 70p. Sub-min dpco slide 15p; push to make 15p; push to break 20p. 10A, 250V rocker 10p; DPCCO rocker 40p. Sub-min toggle spco 62p; dpco 74p; dpco centre off 80p. PO 1000 type lever switches, in vertical bank of 4, each 4 pole c/o, centre off. Ex-equip, 50p. Also with 4th switch bias 50p. Few horizontal banks of 10, £1-50. Push button switch (No knob) DPCCO, non-locking 12p. As above, but locking on or off, rated 250V 2A 19p. Microswitch 18 x 9 x 6mm, 5A 240V rating, has 35mm lever 19p.

TRIMMERS

2-7pf, 4-15pf, 6-25pf, 8-30pf ceramic. All 15p each. Compression types, 3-40pf 10p; 100-500pf 34p; 600-1250pf 40p.

HIGH POWER POTS

Berco preset rheostat, type SEF 28-5 ohms 3-3A, with metal cover £2-30, 11 ohm 3-4A without cover £1-50. Rotary types: 25W, 6R, 25R 114R £1-17 each; 50W, 50R, 160R 1k5 £1-44 each; 100W, 70R £1-86. Moulded Carbon High Voltage Pots, ideal for scope 3rill and focus controls, etc. Rated 3rill, 2k5, 3k, 5k, 10k, 50k, 100k, 250k, 500, 1M, 2M5, all 62p each.

71b BARGAIN PARCEL

Hundreds of new components—pots, switches, resistors, capacitors, PC Boards with semiconductors, loads of odds and ends. Amazing value at only £2-90.

COMPUTER PANELS

Large quantity always available; 31b asstd. £1-75; 71b £3-65; 561b £16. Pack with about 500 components inc. at least 50 transistors £1-90; Pack with 12 High quality panels, incl. IC's, power transistors, multitrans trim pots, hundreds of small signal transistors, resistors, zeners, capacitors, etc. Only £2-75. 7400 IC pack—20 74 series IC's on panels £1-20.

PC ETCHING KIT MKIII

Now even better value—200 sq ins copper clad board, 1lb Ferric Chloride, DALO etch resist pen, abrasive cleaner, 2 miniature drill bits, etching dish and instructions. All for £4-15.

FERRIC CHLORIDE

Anhydrous technical quality in 1lb double sealed packs, 1lb 250g 31bs £2-18; 10lbs £5-60; 100lbs £30-00.

FIBREGLASS PCB

Large quantity of offcuts, all usable 200 sq ins single sided, double sided or mixed £1-40.

DEVELOPMENT PACKS

50V ceramic plate capacitors, 5%, 10 of each value 22pF to 1000pF, total 210 caps. £2-70.

CR25 carbon film 1/3rd watt resistors, 5%, 10 of each value 10 ohms to 1M Total 610 resistors £6-00. Electrolytics, wire ended 25V working 10 each: 1, 2, 2, 4, 7, 10, £2-47 and 100uf 200 uf capacitors for £3-20. 400mV zeners 5% 10 each 3V to 30V. 260 in all. Only £14-00.

1 watt Metal Film resistors, 5% 10 of each value 27R to 10M, E12 series. Total 680 resistors £12-00. Polyurethane capacitors, 160V, 21% 10 of each value from 10pF to 10,000pF. Total 370 capacitors £12-50.

COMPONENT PACKS

400 asstd. carbon resistors £1-35
100 Wirewounds 2-15W £1-90
200 Miniature resistors, 1, 1/2, and 3W, mostly carbon film £1-20
200 poly, mica, ceramic caps £1-10
100 Polyester, .01-.2µF £1-10
200 miniature electrolytics, but many unmarked so only £1-00

RELAYS

Miniature Plug-in types: 1250 ohm 8c/o; 700 ohm 4c/o 50p. PO 3000 type 650 ohm with 6 heavy duty c/o contacts (Ex-equip) 75p; 10 for £4-00. 6 1" easily removable relays in 3580 ohm coil 50p; Plug in relay, BTG Base 17mm dia x 42mm long 10k coil 1 c/o contact 40p. Omron MK3P plug in relay, 230V AC coil, 3 sets 10A/c/o contacts. £1-25. Bases 30p. 6V PC type, SPCC contact 70p. Ex-equip on PC board, min sealed type, 22 x 20 x 10mm 200R coil (ops on 6-12V) 2 c/o contacts 40p. Ex-equip 34 x 30 x 15mm, 250R coil, ops on 6-12V 4 c/o contacts, 60p. Delay relay, 115V 20 sec coil, mains contact 60p; 230V coil 30 sec delay 21p.

CRYSTAL FILTER UNIT

Chassis 210 x 115 x 80mm containing 24 way switch, 24 HC8U tail holders, 24 beehive trimmers, + board with 4 BFl115, R's C's, etc. £3-50.

5MHz FREQUENCY SOURCE

High stability, better than 2 x 10⁻⁶ short term, better than 1 x 10⁻⁷ per month. 12-6V drive voltage, output 5MHz into 50R. £12. 4-433615MHz colour sub-carrier crystals 60p.

BOOKS

All by R. M. Marston, these titles use readily available components.
20 Solid State Projects for the Home £2. 20 Solid State Projects for the Car & Garage £2. 110 Semiconductor Projects for the Home Constructor £2-70. 110 Thyristor Projects for the Home Constructor £2-70. 110 Integrated Circuit Projects for the Home Constructor £2-70. 110 Op Amp Projects for the Home Constructor (uses 741) £2-70. 110 CosMos Digital IC Projects for the Home Constructor £2-85. 110 Electronic Alarm Projects for the Home Constructor £3-15.

VERO BOXES, CASES & BOARD



VEROBOARD

Size 0-1" 0-15" 0-1" plain
3 1/2 x 3 1/2" 44p 40p N/A
5 x 3 1/2" 50p 55p 40p
17 x 3 1/2" £1-90 £1-60 £1-30

PINS

Full or half pins, 0-1 or 0-15 35p 100.

DIY BREADBOARD

Accommodates 20 x 14 way or 16 x 16 way IC's £2-00.

OFFCUTS

Pack A, All 0-1"
Pack B, All 0-15"
Pack C, Mixed
Pack D, All 0-1" plain
Each pack contains 7 or 8 pieces with a total area of 100 sq ins. Each pack is £1-30. Also available by weight, 1lb £3-45, 10lbs £28.
We are also VERO wholesalers—Trade price list on request from Bone Fide Companies.



VEROCASES

Plastic top and bottom, ally panels front and back.
Type 1410 205 x 140 x 40mm £3-30
Type 1411 205 x 140 x 75mm £3-70
1412 205 x 140 x 110mm £4-60
1237 154 x 85 x 40mm £2-30
1238 154 x 85 x 60mm £2-80
1239 154 x 85 x 80mm £3-60

PLASTIC BOXES

Professional quality, two tone grey polystyrene with threaded inserts for mounting PC Boards.
Type 2518 120 x 65 x 40mm £2-25
2520 150 x 80 x 50mm £2-60
2522 188 x 110 x 60mm £3-50

MULTIMETER MODEL LT22

Probably one of the lowest priced meters featuring a mirror scale, overload protection and 20000 ohms per volt sensitivity. A modern styled meter with unusually clear scale markings. Ranges: DC Volts 0-0.5-2.5-10-50-250-1000 AC Volts 0-10-50-250-1000 DC Current 0-50µA-25mA-250mA Resistance 0-50k-500k-5M (Mid Scale 300-3k-30k) Ohm's 4 ranges -20db to +42db. Size 130 x 90 x 42mm. £12-70.

5V 12A REGULATED POWER SUPPLY

Brand new boxed fully stabilized PSU, complete with instruction manual. Load regulation 0-15%. Thermal & Electronic overload protection. Only £24-00.

TRANSFORMERS

All have mains primaries, secondarys as follows: 0-0-9V 100mA 95p; 0-0-9V 75mA £1-00; 12-0-12V 50mA 95p; 12-0-12V 100mA £1-10; 6.3V 1jA £1-95; 0-0-6V 1jA £2-30; 0-0-9V 1A £2-35; 12-0-12V 1A £2-85; 12V 5A £2-65; 12V 8A £4-35; 20V 55mA 90p; 22V 100mA £1-00; 20V 50mA 90p; Multitapped types, 0-12-15-20-24-30V 1A £3-50; 2A £5-00; 20-0-20V 2A £4-40; 24V 500mA £1-65.

S-DECS & T-DECS

S-DEC Breadboard £2-10
T-DEC Breadboard £3-75

SOLDERING IRONS

Antex 15W Model C £3-70
Antex 15W Model CCN £4-00
DeeGee 25W Model 3612 £2-80
Litesold 10W £2-60
EK400 40W £2-40
Instant Heat Soldering Gun with built in lighting unit and 5 spare tips £4-50.

SOLDER

Multicore small reels, size 10 22g £1-45; Size 12 15g £1-45; 500gm reels 18g £4-00; Small packs of 18 or 22g 30p.

OUR 44 page CATALOGUE FREE with orders over £2.

(Send 10p if under, or 20p stamps for just catalogue).

SURPLUS CAPACITORS

15,000µF 6V 35mm dia x 55mm PC 10p
1,250µF 16V 20 x 50mm, tags 10p
1,250µF 40V 25 x 80mm, tags 20p
800µF 40V 25 x 50mm, tags 18p
10,000µF 10V 35 x 80mm, tags 18p
6,400µF 16V 35 x 80mm, tags 20p
4,000µF 25V 35 x 80mm, tags 23p
10,000µF 16V 40 x 80mm, tags 30p
50µF 350V 25 x 50mm tags 12p
1500µF 18V 18 x 34mm FC 8p
18,000µF 25V 50 x 105mm, screws 60p
NB: Add 30p postage for any quantity
Miniature resistors, carbon film 5% 1p each, £1-00 per 100 of one value 1R to 10M. 1W metal film 21p each.

BULK OFFERS

3mm wander plugs, black only at special price of £2-20/100.
63mA 20mm quick-blow fuses, £2/100
24V 1W LES lamps £3-60/100
350mA 20mm A/S fuses £4/100

SPECIAL OFFER OF PLUG-IN MODULES

Large quantity just arrived, several diff types. Case size 77 x 50 x 50mm, either octal or 11 pin base. Send SAE for full list of types and circuits.
Type R: Contains 6A 200V SCR, 4 x 5A 300V diodes, 24V reed relay, C, R, etc. Octal base. With circuit. Only £1-00 each, 10 for £8-00. Type M: 5 BC184, C426, min. R's and C's 63p. Panel with 2 6A 400V triacs, 709C, 2N1711, 100V 1A bridge, 2 pots, 1 preset, zeners, R's, C's, etc. Only £1-50.

WHAT A BARGAIN

Probably one of the lowest priced meters featuring a mirror scale, overload protection and 20000 ohms per volt sensitivity. A modern styled meter with unusually clear scale markings. Ranges: DC Volts 0-0.5-2.5-10-50-250-1000 AC Volts 0-10-50-250-1000 DC Current 0-50µA-25mA-250mA Resistance 0-50k-500k-5M (Mid Scale 300-3k-30k) Ohm's 4 ranges -20db to +42db. Size 130 x 90 x 42mm. £12-70.

5V 12A REGULATED POWER SUPPLY

Brand new boxed fully stabilized PSU, complete with instruction manual. Load regulation 0-15%. Thermal & Electronic overload protection. Only £24-00.

TRANSFORMERS

All have mains primaries, secondarys as follows: 0-0-9V 100mA 95p; 0-0-9V 75mA £1-00; 12-0-12V 50mA 95p; 12-0-12V 100mA £1-10; 6.3V 1jA £1-95; 0-0-6V 1jA £2-30; 0-0-9V 1A £2-35; 12-0-12V 1A £2-85; 12V 5A £2-65; 12V 8A £4-35; 20V 55mA 90p; 22V 100mA £1-00; 20V 50mA 90p; Multitapped types, 0-12-15-20-24-30V 1A £3-50; 2A £5-00; 20-0-20V 2A £4-40; 24V 500mA £1-65.

OUR retail shops at 21 Deptford Broadway, London, SE8 (01-692 2099) and 30 Lower Addiscombe Road, Croydon (01-888 2959) stock some of the advertised goods for personal callers only. Ring them for details.

SEE PRACTICAL ELECTRONICS FOR INDIVIDUAL COMPONENT PRICES

All prices quoted include VAT and UK/BFPO postage. Most orders despatched on day of receipt. SAE with enquiries please. MINIMUM ORDER VALUE £1. Send 10p for Multimeter catalogue—free on request on orders over £3. Official Orders accepted from Schools, etc. (Minimum invoice charge £5). Export/Wholesale enquiries welcome. Wholesale list now available for bona-fide traders. Surplus components always wanted.

Detecknow- ledgey

Detecknowledgey? No, we haven't forgotten how to spell - a number of you thought we had during our 'Tecknowledgey' ad series last year - it is simply an expression of Ambit's specialist topic for Summer 1977: Metal Detectors. In other words, we want you to know that we know about them, not just selling them, but how they work, and why. It is surprising how few people can explain the theory and application of first principles to metal locators. Things like why a bunch of keys can sometimes fail to register, whilst a 2p piece indicates at 8-10" or why a lump of iron reacts as if it were non-ferrous. See our new publication on the subject, a concise reference work that sets out to explain from first principles the various phenomena you will encounter. £1.00 inc PP.


PW SEEKIT COMPLETE KIT

Speaking of technology - that is, the application of scientific discoveries to practical situations and every day equipment - the PW Seekit can claim to have used a few innovative features only achievable with devices that we have been largely instrumental in promoting, so it is not surprising we are able to offer complete kits, and all parts for this exciting project. The complete Seekit-kit costs £36.00 including PP AND VAT. This kit contains all electronic and plastic components (undrilled), bar things like glue, foil etc., which you are more than likely to have around the house. An SAE will bring you our new leaflet (A5 size please) with a more detailed list. Please note we can only consider service/testing on complete kits purchased from US.

BIONIC FERRET 4000

Not an electronically souped up rabbit catcher, but AMBIT's own VCD metal locator system. The £40.74 ferret, (a saving of approx. £3-529m on the human version), comes complete with drilled, and cut-plastic parts, earpiece, all electronics etc. The £40.74 includes PP and VAT at 8%. A free copy of metal Detecknowledgey with all kits.

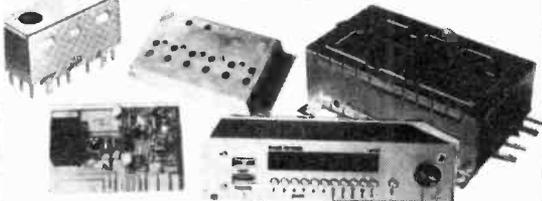Wireless COMPLETE TUNER KITS MODULES COMPONENTS etc



Linear ICs:		Transistors:			
CA3089E	1.94	7805UC*	1.55	40673 *	0.57
MC1310P	2.20	78M12*	1.20	MEM680*	0.75
TBA120	0.75	1d1412*	1.20	MEM614*	0.38
uA753	1.80	7815*	1.55	Varicaps	
HA1137W	2.20	78M20*	1.20	BA102	0.30
CA3090AQ	3.75	78M24*	1.20	BA121	0.30
HA1196	4.20	uA723C*	0.80	BB104	0.45
uA720	1.40	TAA550*	0.50	BB105	0.32
CA3123E	1.40	8038CC*	4.50	MVAM2	1.35
HA1197	1.40	NE555V*	0.70	MVAM115	0.95
TBA651	1.81	NE566/7*	2.50	MVAM125	0.90
LM380N	1.00	NE565*	2.50	Larsholt Signalmaster	
LM381N	1.81	NE560*	3.50	Mk 8 kit. Suitable for	
LM3900*	0.75	MC1312	1.50	beginners too £85.00	
TA2020	2.99	Digital ICs		Audiomaster 25W Af	
TBA810	1.09	11C90DC	14.00	kit amplifier £79.00	
TCA940	1.80				

VAT extra 12.5%, (*=8%). PP 22p per order - unless otherwise shown. Full catalogue (much new stuff since 76) 40p. SAE for free (A5) prices 37a High Street, Brentwood, Essex. CM14 4RH. (0277-216029)

ambit international

When you make your own PCB's, you need the Dalo pen!

The original etch resist marking pen that revolutionised one-off PCB drafting! Simply draw your circuit onto copper-clad board, allow ink to dry, then etch. A perfect circuit is ready in minutes.

Send in the coupon below for details of the Seno / 33 range of aids to PCB preparation

Decon Laboratories Ltd. Freepost, Portslade,
Brighton BN4 1EQ (no stamp needed)

Name: _____

Address _____

Phone 0273-414371

TECHNICAL TRAINING IN ELECTRONICS TELEVISION AND RADIO SERVICING

ICS can provide the technical knowledge that is so essential to your success, knowledge that will enable you to take advantage of the many opportunities open to the trained person. You study in your own home, in your own time and at your own pace and if you are studying for an examination ICS guarantee coaching until you are successful.

City & Guilds Certificates:
Telecommunications Technicians
Radio, TV, Electronics Technicians
Technical Communications
Radio Servicing Theory
Radio Amateurs
Electrical Installation Work
MPT Radio Communications Certificate

Diploma Courses:
Colour TV Servicing
Electronic Engineering and Maintenance
Computer Engineering and Programming
Radio, TV, Audio Engineering and Servicing
Electrical Engineering, Installation
and Contracting

POST OR PHONE TODAY FOR FREE BOOKLET

ICS To: International Correspondence Schools

Dept. No. 777G, Intertext House, LONDON
SW8 4UJ or telephone 622 9911

Subject of Interest _____

Name _____

Address _____

Tel: _____

CARAVAN/CAR CONNECTOR



The famous Clanc connectors heavy cast body enclosing the electrical socket and plug—screw together cannot be pulled out or come out with vibration. Socket screw on cover keeps out dirt when caravan is not connected. Socket £2-50. Plug £2-85p or Socket fixed to solid angle iron (ready for mounting) £3-50.

3 CORE CURLY LEAD
terminating each end with 3 pin Clang plug, length extended approx. 10ft. Price £6-00 + 75p.

12v AUTOMATIC SWITCH

It can sometimes be a problem to find your car or caravan in a big car park or caravan site after dark, so why not fit a light that will come on automatically when it gets dark. We are offering a kit for this, comprises: light sensitive switch, 12v bulb and bulb holder in tubular casing with coloured lens, with wiring diagram. Price £3-00 + 37p + 20p + 2p. Main operation switch available £3-95.



TAPE HEADS ETC.

2 track record/playback 75p.
4 track record/playback £1-10.
Erase head 2 track 50p, 4 track 80p.
Mu metal shields and holders 65p each.
1/2 track r/p head and 2 track erase head schedule and fixed on mounting plate ready for tape £1-85.

INDUCTION MOTORS

230v mains operated—precision made as used in fans—record players. Tape recorder—heaters etc. etc. £ stack (as illustrated) £1-85. £ stack £1-75. 1" stack £2-25.

MOTORISED DISCO SWITCH

With six 10 amp changeover switches. Multi adjustable switches are rated at 10 amp each so a total of 2000w's can be controlled and this would provide a magnificent display. For mains operation £4-25 post & VAT Paid. Ditto 9 switch £4-95 Post & VAT Paid. DITTO BUT 12 SWITCH £5-75 POST & VAT PAID.



DELAY SWITCH

Mains operated—delay can be accurately set with pointers knob for periods of up to 2 1/2 hrs. 2 contacts suitable to switch 10 amps—second contact opens few minutes after 1st contact 96p.

WAFER SWITCHES

8 pole 2 way 12 pole 2 way 18 pole 2 way
5 pole 3 way 10 pole 3 way 15 pole 3 way
4 pole 4 way 8 pole 4 way 12 pole 4 way
8 pole 5 way 6 pole 5 way 9 pole 5 way
2 pole 6 way 4 pole 6 way 6 pole 6 way
1 pole 10 way 4 pole 8 way 6 pole 8 way
1 pole 12 way 2 pole 9 way 6 pole 9 way
all £1-22 each all £2-11 each all £2-18 each
Multi bank switches up to 72 pole 2 way—to 12 pole 12 way quickly made to special order.

24 HOUR TIMERS

VERMEN
As illustrated with sun correction made for G.P.O. phone boxes unused and perfect £2-25 20 amp switching contacts.
SWITZER
Timer heart similar to Autotest etc. £ 13 amp on/off per 24 hrs. £4-15.
TIMAC
Module really miniature (approx 2" cube) but with 2 15 amp on/off per 24 hrs. £4-50.



UNISELECTORS

These are pulse operated switches as used in automatic telephone switchboards etc. A 24v pulse moves the switch through one switch way all we have are of the 25 switch full wiper type, the following sizes are in stock:

3 bank £4-50 + 37p
4 bank £5-94 +
8 bank £9-72 +
12 bank £12-96 +



3 bank & Homer £5-40
5 bank £7-02
10 bank £10-80

BLOWER FAN



Centrifugal type blower/fans with rectangular outlets designed to fit into trunking for heat blowing etc. will also function as extractors—three voltage motors—three sizes available small (overall size approx 4 1/2" x 4" x 4") £4-50—medium (overall size 9" x 8" x 3" approx) £6-50—large (overall size 12" x 12" x 10" approx) £13-50.

CENTRAL HEATING HEARTS

Randal (illustrated) replacement in 3060 etc £8-75.
HOBTSMAN £6-30.
SMITHS Controller 10/100 complete in wall mounting case £7-50.



THIS MONTH'S SNIP HI FI RECORD PLAYER




wooden plinth with super 10 watt amplifier. Controls are "on/off", "Tape/phone", "mono/stereo", "Bass", "Treble", "Balance", "Volume". We are offering these at price of record deck only so are a bargain not to be missed only £6-75p, post 20-00p. Note cartridge and all spares are available at low prices.

Stereo 5 watts per channel. Russian made but guaranteed repairable. Travel damaged or test line rejects, in need of attention, consist of mains operated record deck—mounts in 4" x 4" x 4" case.

MAINS TRANSFORMER BARGAINS

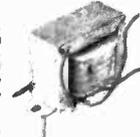20v 1 amp £1-25
18v 1 amp £1-55
6-8v 2 amp £1-39
24v 2 amp £2-00
50v 2 amp £4-50
9v 1 amp £1-25
8-8v-0-8-8v 1 amp £1-25
10v-20v-30v-40v £5-50
20 watt auto 115v £1-25
100 watt auto 115v £1-75



THERMOSTATS

Refrigeration as illustrated with 36" capillary £1-62.
Limpet Stat must be mounted in close contact calibrated 90°-190°F 15 amp contacts £1-65.
Appliance Stat fix like a volume control—15 amp contact 90°-80°F 85p.
ditto but for high temps £1-25
Over Stat—with Serson and capillary 85p




TERMS:

Cash with order—delivery same day as order received prices include VAT and carriage unless stated but orders under £6 must add 50p to offset packing etc. BULK ENQUIRIES WELCOMED.

J. BULL (ELECTRICAL) LTD
(Dept. PW), 103 TAMWORTH RD.
CROYDON CR9 1SG

WEE MEGGER A VERY SPECIAL OFFER

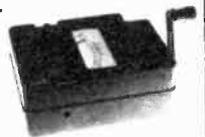Most famous testing instruments. Made by Evershed & Vignol, a must for every electrical contractor and service man. In perfect going order having been thoroughly reconditioned for the G.P.O. Price £14-00 + £1-12p. Post 80p + 6p.




LOW R.P.M. MOTORS

Made by Crouzet — Smiths — SAIWA — Venner and similar famous companies—all supplied ready for 230/240v 50hz mains working at £2-75 each. Following speeds in stock when preparing this advert:
1 rev per day 6 rev per day
1 rev per hour 12 revs per hour
1/2 rev per min 1 rev per min
2 rpm 1 1/2 rpm
5 rpm 15 rpm 20 rpm 25 rpm 30 rpm

REMEMBER 7-029

We are still able to offer the electrical equivalent of this in 100 metre coils at a very special price of £10-25p, carriage £2-50p. Our remaining stock of this is 3 core and earth, this is a little larger physically than twin and earth but if space limited then just remove the unwanted core before taking cable into small socket box.
FREE Telephone line. If you are using the above cable for taking a supply to a shed or remote point then the third core can be used as a telephone line. For lighting we can offer 1.5mm. Three core at £8-50 carriage £1-00.

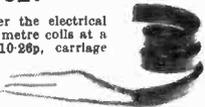

MULLARD UNILEX

A mains operated 4 + 4 stereo system. Rated one of the finest performers in the stereo field this would make a wonderful gift for almost any one in easy-to-assemble modular form and complete with a pair of Goodmans speakers this should sell at about £30—but due to a special bulk buy and as an incentive for you to buy this month we offer the system complete at only £14-00 including VAT and postage.



IT'S FREE!

Our monthly Advance Advertising Bargains list of special deals of bargains arriving or just arrived—often bargains which sell out before our advertisement can appear—It's an interesting list and it's free—just send S.A.E. Below are a few of the Bargains still available from a recent list.

Luminous Rooker Switch, suitable for 18 amps at mains voltage, these are illuminated with neon through amber panel, snap-in fitted into hole size 1 1/2" x 1 1/2". Special bargain 82p + 2p.

Chrome Plated Metal Legs, heavy duty, really good quality, made originally for an expensive Decca outfit, height 12", £1-60 per set of 4 plus post 30p.

Students Relay Parcel. 10 Multi contact 600 type relays all different coil values covering most experiments, needs. Total retail value approx. £10—yours for £3 plus 80p post.

B&E Record Auto-changer, current model of very high repute with a ceramic stereo cartridge £10-95 + £1-87. Post £1-00 + 12p.

Speaker bargain, 13" x 8" E.M.I. 10 watt speaker with twin tweeters and cross-over a really fantastic performer. Regular price over £8 each—we have a limited quantity of ohm coil £5 + 50p each post and insurance.

Motor with fan blades—if you want something to cool or if you are making a cooker hood or a blower heater etc. May be just the thing you are looking for for that portable instrument. Price £3-50 + 28p. Post 70p + 7p.

Microswitch bargain—Honeywell, brand new 10 amp 250v gold on silver contacts, standard fixing, normal operation. Price 10p + 1p—10 for £1, post & VAT paid.

Cooling Fans—heavy duty for TO5 type semi-conductors—extruded aluminium, size 4 1/2" x 3". Price 50p each.

Instrument cases—portable, about the size of portable typewriter, actually 13" x 10" x 4" thick approx. with carrying handle. Inside these boxes there is a mains transformer with two outputs 12v and 6v and two full wave rectifiers with smoothing condensers as well as many other useful components, fuse holders etc. May be just the thing you are looking for for that portable instrument. Price £3-50 + 28p. Post 70p + 7p.

Fluorescent kit for 5ft tube. This is another exceptional bargain. It comprises polyester filled almost silent running 65w choke made by GEC, starter and holder, tube ends and terry clips to hold the tube and wiring diagram etc.

THIS MONTH'S SNIP at only £1-75 + 12p the lot + 50p + 4p post and packing. Just what sort of a bargain this is will be realised when you look at the new prices for chokes only: the recommended list price of 65w is now over £3-50.

BEFORE YOU BUY AN AMPLIFIER MODULE—CHECK:

DOES IT HAVE ★ 30 A POWER TRANSISTORS ★ GLASS FIBRE P.C.B.
 ★ 3A DRIVERS (100 W UNIT) ★ INTEGRAL OUTPUT CAPACITOR
 THEN COMPARE WITH THE TAMBA RANGE—EXCELLENT VALUE—25, 50 & 100 W RMS

TAM1000 100W 4 OHMS 65V	£9.99
TAM500 50W 4 OHMS 45V	£7.50
TAM250 25W 8 OHMS 45V	£4.75
POWER SUPPLIES	
For 1 or 2 TAM250/500	£7.50
For 1 or 2 TAM1000	£9.99
(Carr. 50p on supplies)	



ALL PURPOSE MIXER/PREAMP

(WITH 50 mm SLIDER VOLUME)

- Anodised & printed facia
 - Suitable for multiple input systems
 - High & low impedance inputs
 - High sensitivity
 - Built in supply smoothing
 - 20-20,000 hz ±1dB
 - 80dB Noise level
 - Accepts a wide variety of inputs
 - Wide range bass & treble controls
- Use up to 10 preamps with 1 power

COMPLETE & TESTED assembly with Treble & Bass controls plus slider Volume Control. **£5.50**

- Suits loads 4-16 ohms
- 20-20,000 hz ±1dB
- Silicon circuitry throughout
- Glass fibre P.C.B.
- High sensitivity (100mV 10k)
- Low distortion (0.1%)
- Low profile (1" High 3½" x 3")
- 75% efficient
- Accepts most mixer/preamps
- Four simple connections

High Grade Components used throughout: Texas, Mullard, R.C.A., Plessey, etc.

You may order as follows: C.W.O. (crossed cheques, P.O.s, M.O.s, etc.) C.O.D. (60p extra). We accept Access and Barclaycard—send or telephone your number—do not send your card. Add VAT at 8% to orders for 50-100W units and at 12½% for 25W units

Hours, 9.30 a.m.—5 p.m.
 Monday—Saturday.
 Callers welcome.
 Tel: (01) 684 0098

TAMBA ELECTRONICS

BENSHAM MANOR ROAD PASSAGE, BENSHAM MANOR ROAD, THORNTON HEATH, SURREY

PHILIPS



YOU & PHILIPS HI-FI KITS

The top sellers for home assembly in Europe—now available in the U.K.

Now—read all about the Philips range of quality kits for home assembly—mixers, amplifiers, speakers, etc, etc. Send today to
 S.S.T. Distributors (Electronic Components) Ltd.,
 West Road, Tottenham, London N17 0RN

Please send me, quickly, the new colour catalogue. PW61

Name _____

Address _____

Postcode _____



free SEND TODAY!

S.S.T. Distributors is a member of the Philips Group of Companies.

THE 'METAC' DIGITAL ALARM CLOCK



- Choice of Bright Orange 12 Hour Display, or
- Soft Green 24 Hour Display ● 24 Hour Alarm
- 10 Minute Repetition ● Alarm Set indicator
- Accurate Silent Timekeeping ● British Designed and Built

SAME DAY DISPATCH orders received before 2 pm are posted same day

£12.99 + £1.04 VAT

Cash, Cheque or Postal Order or if you wish to use Barclaycard or Access, simply quote name, address and card number when ordering.

Metac-Electronics and Time Centre



DAVENTRY

67 High Street
 Daventry, Northants
 Tel. (032-72) 76545

UXBRIDGE

3 The New Arcade,
 High Street, Uxbridge,
 Middx. Tel. (0895) 56961



SEMICONDUCTORS—COMPONENTS

DIODES

Type	Price	Type	Price	Type	Price	Type	Price
AA129	£0.08	BY100	£0.16	BY211	£0.31	OA91	£0.07
AA130	£0.09	BY107	£0.12	BY212	£0.31	OA95	£0.07
AAZ13	£0.10	BY105	£0.18	BY213	£0.26	OA182	£0.07
AAZ17	£0.10	BY114	£0.12	BY216	£0.41	OA200	£0.08
BA100	£0.10	BY124	£0.12	BY217	£0.38	OA202	£0.08
BA102	£0.32	BY206	£0.15	BY218	£0.35	SD10	£0.06
BA148	£0.15	BY127	£0.16	BY219	£0.28	SD19	£0.06
BA154	£0.12	BY128	£0.16	OA10	£0.35	IN34	£0.07
BA155	£0.14	BY130	£0.17	OA47	£0.07	IN34A	£0.07
BA156	£0.14	BY133	£0.21	OA70	£0.07	IN914	£0.06
BA173	£0.15	BY164	£0.51	OA79	£0.07	IN916	£0.06
BB104	£0.15	BY178	£0.75	OA81	£0.07	IN4148	£0.06
BAX13	£0.07	BY206	£0.00	OA85	£0.09	IS44	£0.05
BAX16	£0.08	BY210	£0.36	OA90	£0.07	IS920	£0.06

SILICON RECTIFIERS

Type	Price	Type	Price	Type	Price	Type	Price
IS920	£0.06	IN4003	£0.07	IS020	£0.10	IS031	£0.25
IS921	£0.07	IN4004	£0.08	IS021	£0.11	IN5400	£0.13
IS922	£0.08	IN4005	£0.09	IS023	£0.13	IN5401	£0.15
IS923	£0.09	IN4006	£0.10	IS025	£0.14	IN5402	£0.16
IS924	£0.10	IN4007	£0.11	IS027	£0.16	IN5404	£0.17
IN4001	£0.05	IS015	£0.09	IS029	£0.20	IN5406	£0.21
IN4002	£0.06					IN5407	£0.25

TRIACS

2 AMP TO5 CASE			10 AMP TO48 CASE		
Volts	No.	Price	Volts	No.	Price
100	TR12A/100	£0.31	100	TR110A/100	£0.77
200	TR12A/200	£0.51	200	TR110A/200	£0.92
400	TR12A/400	£0.71	400	TR110A/400	£1.12

6 AMP TO66 CASE			10 AMP TO48 CASE		
Volts	No.	Price	Volts	No.	Price
100	TR16A/100	£0.51	100	TR110A/100	£0.77
200	TR16A/200	£0.61	200	TR110A/200	£0.92
400	TR16A/400	£0.77	400	TR110A/400	£1.12

THYRISTORS

600mA TO18 CASE			7 AMP TO48 CASE		
Volts	No.	Price	Volts	No.	Price
10	THY600/10	£0.13	50	THY7A/50	£0.48
20	THY600/20	£0.13	100	THY7A/100	£0.51
30	THY600/30	£0.19	200	THY7A/200	£0.57
50	THY600/50	£0.22	400	THY7A/400	£0.62
100	THY600/100	£0.25	600	THY7A/600	£0.78
200	THY600/200	£0.38	800	THY7A/800	£0.92
400	THY600/400	£0.45			

1 AMP TO5 CASE			10 AMP TO48 CASE		
Volts	No.	Price	Volts	No.	Price
50	THY1A/50	£0.26	50	THY10A/50	£0.51
100	THY1A/100	£0.27	100	THY10A/100	£0.57
200	THY1A/200	£0.28	200	THY10A/200	£0.62
400	THY1A/400	£0.36	400	THY10A/400	£0.71
600	THY1A/600	£0.38	600	THY10A/600	£0.99
800	THY1A/800	£0.58	800	THY10A/800	£1.22

3 AMP TO66 CASE			16 AMP TO48 CASE		
Volts	No.	Price	Volts	No.	Price
150	THY3A/50	£0.25	50	THY16A/50	£0.54
100	THY3A/100	£0.27	100	THY16A/100	£0.58
200	THY3A/200	£0.33	200	THY16A/200	£0.62
400	THY3A/400	£0.50	400	THY16A/400	£0.77
600	THY3A/600	£0.50	600	THY16A/600	£0.99
800	THY3A/800	£0.65	800	THY16A/800	£1.39

5 AMP TO220 CASE			30 AMP TO94 CASE		
Volts	No.	Price	Volts	No.	Price
400	THY5A/400P	£0.57	50	THY30A/50	£1.18
600	THY5A/600P	£0.69	100	THY30A/100	£1.43
800	THY5A/800P	£0.81	200	THY30A/200	£1.63
			400	THY30A/400	£1.79
			600	THY30A/600	£3.50

No.	Price
BT101/500R	£0.80
BT102/500R	£0.80
BT105	£1.25
BT107	£0.93
BT108	£0.98
2N3228	£0.70
2N3525	£0.77
BTX30/50L	£0.33
BTX30/400L	£0.46
C106/4	£0.60

ORDERING

PLEASE WORD YOUR ORDERS EXACTLY AS PRINTED, NOT FORGETTING TO INCLUDE OUR PART NUMBER

VAT

ADD 12½% TO PRICES MARKED*
ADD 8% TO OTHERS EXCEPTING
THOSE MARKED †, THESE ARE
ZERO RATED

SUPER UNTESTED PAKS

Pak No.	Qty.	Order No.	Price
U50	100	16130	£0.60
U51	150	16131	£0.60
U52	100	16132	£0.60
U53	150	16133	£0.60
U54	50	16134	£0.60
U55	20	16135	£0.60
U56	50	16136	£0.60
U57	30	16137	£0.60
U58	30	16138	£0.60
U59	25	16139	£0.60
U60	25	16140	£0.60
U61	30	16141	£0.60
U62	25	16142	£0.60
U63	30	16143	£0.60
U64	30	16144	£0.60
U65	30	16145	£0.60
U66	15	£1.20	
U67	10	£1.20	
U68	20	£1.48	
U69	10	£1.49	
U70	8	£1.20	

Code Nos. mentioned above are given as a guide to the type of device in the pak. The device themselves are normally unmarked.

COMPONENT PAKS

Pak No.	Qty.	Order No.	Price
C1	200	16164	£0.60
C2	150	16165	£0.60
C3	50	16166	£0.60
C4	80	16167	£0.60
C5	5	16168	£0.60
C6	2	16169	£0.60
C7	1	16170	£0.60
C8	10	16171	£0.60
C9	3	16172	£0.60
C10	15	16173	£0.60
C11	5	16174	£0.60
C12	30	16175	£0.60
C13	20	16176	£0.60
C14	1	16177	£0.60
C15	5	16178	£0.60
C16	20	16179	£0.60
C17	15	16180	£0.60
C18	4	16181	£0.60
C19	2	16182	£0.60
C20	1	16183	£0.60
C21	15	16184	£0.60
C22	50	16185	£0.60
C23	60	16188	£0.60
C24	25	16188	£0.60
C25	30	16187	£0.60

SLIDER PAKS

Pak No.	Qty.	Order No.	Price
S1	6	16190	£0.60
S2	6	16191	£0.60
S3	6	16192	£0.60
S4	6	16193	£0.60
S5	6	16194	£0.60
S6	6	16195	£0.60

CERAMIC PAK

Containing a range of first quality miniature ceramic capacitors. Unrepeatable value.

Pak No.	Qty.	Order No.	Price
MC1	24	16160	£0.60
MC2	24	16161	£0.60

LINEAR PAKS

Manufacturer's "Fall Outs" which include Functional and part-Functional Units. These are classed as "out of-spec" from the maker's very rigid specifications, but are ideal for learning about ICs and experimental work.

U721—30 Assorted Linear Types, 709 741, 747, 748, 710, 588, etc.
ORDER No. 16227 *£1.50

U765D FM STEREO DECODER
5 ICs 76110 equivalent to MC1310P-MA767. Data supplied with pak.
ORDER No. 16229 *£1.50

U76A AUDIO POWER OUTPUT AMPLIFIERS
8 assorted types. SL403, 76013, 76003, etc. Data supplied with pak.
ORDER No. 16228 *£1.00

74 SERIES PAKS

Manufacturer's "Fall Outs" which include Functional and part-Functional Units. These are classed as "out-of-spec" from the maker's very rigid specifications, but are ideal for learning about ICs and experimental work.

74G—100 Gates assorted 7400-01-04-10-50-60, etc.
ORDER No. 16224 *£1.20

74F—50 Flip-Flops assorted 7470-72-73-74-76-104-109, etc.
ORDER No. 16225 *£1.20

74M—30 MSI. Assorted Types. 7441-47-90-154, etc.
ORDER No. 16226 *£1.20

VEROBOARDS PAKS

V81—Approx. 30sq.in various sizes. All 0.1in matrix
ORDER No. 16199 60p

V82—Approx. 30sq.in various sizes. 0.15in matrix.
ORDER No. 16200 60p

ELECTROLYTIC PAKS

A range of paks each containing 18 first quality, mixed value miniature electrolytics.

EC1—Values from 0.47µF to 10µF.
ORDER No. 16201 *60p

EC2—Values from 10µF to 100µF.
ORDER No. 16202 *60p

EC3—Values from 100µF to 680µF.
ORDER No. 16203 *60p

C280 CAPACITOR PAK

75 Mullard C280 capacitors, mixed values ranging from 0.01µF to 2.2µF complete with identification sheet.
ORDER No. 16204 *£1.20

CARBON RESISTOR PAKS

These paks contain a range of Carbon Resistors, assorted into the following groups:

R1—60 mixed ½W 100-820 ohms.
ORDER No. 16213 *60p

R2—60 mixed ½W 1-8-2kΩ.
ORDER No. 16214 *60p

R3—60 mixed ½W 10-82kΩ.
ORDER No. 16215 *60p

R4—60 mixed ½W 100-820Ω.
ORDER No. 16216 *60p

R5—40 mixed ½W 100-820Ω.
ORDER No. 16217 *60p

R6—40 mixed ½W 1-8-2kΩ.
ORDER No. 16218 *60p

R7—40 mixed ½W 10-82kΩ.
ORDER No. 16219 *60p

R8—40 mixed ½W 100-820Ω.
ORDER No. 16220 *60p

R9—60 mixed ½W 1-10MΩ.
ORDER No. 16230 *60p

R10—40 mixed ½W 1-10MΩ.
ORDER No. 16231 *60p

WORLD SCOOP JUMBO SEMICONDUCTOR PAK

Transistors, Germ. and Silicon Rectifiers, Diodes, Triacs, Thyristors, ICs and Zeners.

ALL NEW AND CODED
Approx. 100 pieces. Offering the amateur a fantastic bargain PAK and an enormous saving—identification and data sheet in every pak.
ORDER No. 16222 *£2.25

Just a selection from our huge stocks!

SEE OUR 1977 CATALOGUE

126 pages packed with valuable information

ORDER NOW ONLY 50p plus 15p p & p

BI-PAK

Dept. P.W.6, P.O. Box 6, Ware, Herts
COMPONENTS SHOP: 18 BALDOCK STREET, WARE, HERTS

THE 'NUTS & BOLTS' OF THOSE PROJECTS

TRANSFORMERS

MINIATURE MAINS Primary 240V with two independent secondary windings

No.	Type	Price
2024	MT280 0-6V, 0-6V RMS	£1 30*
2025	MT150 0-12V, 0-12V RMS	£1 30*

MINIATURE MAINS Primary 240V

No.	Secondary	Price
2021	6V-0-6V 100mA	£1 30*
2022	9V-0-9V 100mA	£0 85*
2023	12V-0-12V 100mA	£1 30*

1 AMP MAINS Primary 240 V

No.	Secondary	Price	P & P
2026	6V-0-6V 1 amp	£2 70*	P & P 30p
2027	9V-0-9V 1 amp	£2 20*	P & P 30p
2028	12V-0-12V 1 amp	£2 60*	P & P 30p
2029	15V-0-15V 1 amp	£2 90*	P & P 30p
2030	30V-0-30V 1 amp	£3 80*	P & P 30p

STANDARD MAINS Primary 240V Multi-tapped secondary mains transformers available in 1/2 amp, 1 amp and 2 amp current rating. Secondary taps are 0-15-25-33-40-50V Voltages available by use of taps:

No.	Rating	Price	P & P
2031	1/2 amp	£3 42*	P & P 30p
2032	1 amp	£4 40*	P & P 50p
2033	2 amp	£5 45*	P & P 85p

AUDIO OUTPUT Primary 1-2kΩ, Secondary 5 ohms 200mW Dimensions 20 x 16 x 15mm

Order No.	Price
Order No. 2037	£0 25*

MINIATURE INTER/DRIVER Primary 20kΩ, Secondary 1kΩ, Ratio 5 : 1

Order No.	Price
Order No. 2038	£0 23*

LT710 MIN. INPUT Primary 100kΩ, Secondary 1kΩ, 15 x 13 x 13mm.

Order No.	Price
Order No. 3051	£0 42*

LT711 MIN. DRIVER Primary 10kΩ, Secondary 2kΩ, C.T., 15 x 13 x 13mm.

Order No.	Price
Order No. 2040	£0 35*

LT712 MIN. OUTPUT Primary 500 ohm, Secondary 8 ohms, 100mW, 15 x 13 x 13mm.

Order No.	Price
Order No. 2041	£0 28*

LT717 MIN. INPUT Primary 150kΩ, Secondary 1kΩ, 20 x 15 x 15mm.

Order No.	Price
Order No. 2042	£0 52*

LT719 MIN. INPUT Primary 20kΩ, Secondary 1kΩ, 20 x 15 x 15mm.

Order No.	Price
Order No. 2043	£0 32*

LT722 MIN. DRIVER Primary 10kΩ, Secondary 2kΩ, C.T., 20 x 15 x 15mm.

Order No.	Price
Order No. 2044	£0 32*

LT724 MIN. OUTPUT Primary 1-2kΩ C.T., Secondary 3-2 and 8 ohm, 200mW, Dimensions 20 x 15 x 15mm.

Order No.	Price
Order No. 2045	£0 38*

LT726 MIN. OUTPUT Primary 500 ohm, Secondary 3-2 and 8 ohm, 200mW, Dimensions 20 x 15 x 15mm.

Order No.	Price
Order No. 2046	£0 38*

LT728 MIN. DRIVER Primary 1kΩ C.T., Secondary 500 ohm C.T. Dimensions 25 x 20 x 20mm.

Order No.	Price
Order No. 2047	£0 43*

LT729 MIN. OUTPUT Primary 200 ohm C.T., Secondary 3-2 and 8 ohm, 400mW, Dimensions 25 x 20 x 20mm.

Order No.	Price
Order No. 2048	£0 39*

LT730 MIN. OUTPUT Primary 10 ohm C.T., Secondary 3-2 and 8 ohm, 500mW, Dimensions 25 x 20 x 20mm.

Order No.	Price
Order No. 2049	£0 42*

L.E.D.s

Type	Size	Order No.	Colour	Price
TIL209	0-125in	1501	RED	25p
TIL211	0-125in	1502	GREEN	25p
TIL213	0-125in	1503	YELLOW	25p
FLV115	0-2in	1504	RED	12p
FLV310	0-2in	1505	GREEN	25p
FLV410	0-2in	1506	YELLOW	25p

2nd Grade L.E.D.s

A pack of standard sizes and colours which fail to perform to their very ridged specification, but which are ideal for experiments.

Order No.	Price
Order No. 1507	£0 99

L.E.D. CLIPS

Pack of	Size	Order No.	Price
Pack of 5	0-125in	1508/0-125	15p
Pack of 5	0-2in	1508/0-2	30p

NUTS AND BOLTS

BA BOLTS—packs of BA threaded cadmium-plated screws, slotted cheese head. Supplied in multiples of 100

Type	No.	Price	Type	No.	Price
1in 0BA	839	£1 12	1in 4BA	845	£0 51
1in 0BA	840	£0 83	1in 4BA	846	£0 38
1in 2BA	842	£0 69	1in 4BA	847	£0 33
1in 2BA	843	£0 54	1in 6BA	848	£0 50
1in 2BA	844	£0 63	1in 6BA	849	£0 30
			1in 6BA	850	£0 33

BA NUTS—packs of cadmium-plated full nuts in multiples of 100

Type	No.	Price	Type	No.	Price
0BA	855	£0 90	4BA	857	£0 42
2BA	856	£0 60	6BA	858	£0 36

BA WASHERS—flat cadmium plated plain, stamped washers supplied in multiples of 100

Type	No.	Price	Type	No.	Price
0BA	859	£0 19	4BA	861	£0 15
2BA	860	£0 15	6BA	862	£0 12

SOLDER TAGS—hot tinned supplied in multiples of 100

Type	No.	Price	Type	No.	Price
0BA	851	£0 42	4BA	853	£0 30
2BA	852	£0 36	6BA	854	£0 30

INSTRUMENT CASES. In two sections vinyl covered top and sides, aluminium bottom, front and back.

No.	Length	Width	Height	Price
155	8in	5 1/2in	2in	£1 40*
156	11in	6in	3in	£1 80*
157	6in	4 1/2in	1 1/2in	£1 25*
158	9in	5 1/2in	2 1/2in	£1 60*

ALUMINIUM BOXES. Made from bright all., folded construction each box complete with half inch deep lid and screws.

No.	Length	Width	Height	Price
159	5 1/2in	2 1/2in	1 1/2in	62p*
160	4in	1 1/2in	1 1/2in	62p*
161	4in	2 1/2in	1 1/2in	62p*
162	5 1/2in	4in	1 1/2in	74p*
163	4in	2 1/2in	2in	64p*
164	3in	2in	1in	44p*
165	7in	5in	2 1/2in	£1 04*
166	3in	6in	3in	£1 32*
167	6in	4in	2in	86p*

BRIDGE RECTIFIERS

SILICON 1 amp

Type	Order No.	Price
50V RMS	BR1/50	£0 25
100V RMS	BR1/100	£0 28
200V RMS	BR1/200	£0 30
400V RMS	BR1/400	£0 35

SILICON 2 amp

Type	Order No.	Price
50V RMS	BR2/50	£0 40
100V RMS	BR2/100	£0 45
200V RMS	BR2/200	£0 50
400V RMS	BR2/400	£0 55
1000V RMS	BR2/1000	£0 65

FUSE HOLDERS AND FUSES

Description	Order No.	Price
20mm x 5mm chassis mounting	506	£0 07*
1 1/2in x 1 1/2in chassis mounting	507	£0 10*
1 1/2in car inline type	508	£0 20*
Panel mounting 20mm	509	£0 22
Panel mounting 1 1/2in	510	£0 24

QUICK BLOW 20mm

Type	No.	Type	No.	Type	No.
150mA	611	1A	615	3A	619
250mA	612	1.5A	616	4A	620
350mA	613	2A	617	5A	621
800mA	614	2.5A	618		All 5p each

ANTI-SURGE 20mm

Type	No.	Type	No.	Type	No.
100mA	622	1A	625	2-5A	628
250mA	623	2A	626	3-15A	629
500mA	624	1-6A	627	5A	630
		All 7p each			

QUICK BLOW 1 1/2in

Type	No.	Type	No.	Type	No.
250mA	631	500mA	632	800mA	634
		All 7p each			

Type	No.	Type	No.	Type	No.
1A	635	2-5A	638	4A	641
1-6A	636	3A	639	5A	642
2A	637	All 6p each			

Just a selection from our huge stocks!

SEE OUR 1977 CATALOGUE

126 pages packed with valuable information

ORDER NOW

ONLY 50p plus 15p p & p

SWITCHES

Description	No.	Price
DPDT miniature slide	1973	£0 10*
DPDT standard slide	1974	£0 12*
Toggle switch SPST		
1 1/2 amp 250V a.c.	1975	£0 33*
Toggle switch DPDT		
1 amp 250V a.c.	1976	£0 38*
Rotary on-off mains switch	1977	£0 42*
Push switch—Push to make	1978	£0 13*
Push switch—Push to break	1979	£0 18*

ROCKER SWITCH A range of rocker switches SPST—moulded in high insulation, Material available in a choice of colours ideal for small apparatus

Colour	No.	Price
RED	1980	£0 22*
BLACK	1981	£0 22*
WHITE	1982	£0 22*
BLUE	1983	£0 22*
YELLOW	1984	£0 22*
LUMINOUS	1985	£0 22*

Description	No.	Price
Miniature SPST toggle, 2 amp 250V a.c.	1958	£0 50*
Miniature SPST toggle, 2 amp 250V a.c.	1959	£0 55*
Miniature DPDT toggle, 2 amp 250V a.c.	1960	£0 65*
Miniature DPDT toggle, centre off, 2 amp 250V a.c.	1961	£0 85*
Push button SPST, 2 amp 250V a.c.	1962	£0 65*
Push button SPST, 2 amp 250V a.c.	1963	£0 68*
Push button DPDT, 2 amp 250V a.c.	1964	£0 80*

MIDGET WAFER SWITCHES Single-bank wafer type—suitable for switching at 250V a.c. 100mA or 150V d.c. in non-reactive loads make-before-break contacts. These switches have a spindle 0.25in dia. and 30° indexing.

Description	Order No.	Price
1 pole 12 way	1965	£0 48*
2 pole 6 way	1966	£0 48*
3 pole 4 way	1967	£0 48*
4 pole 3 way	1968	£0 48*

MICRO SWITCHES Plastic button gives simple on-off action

Rating	Order No.	Price
Rating 10 amp 250V a.c.	1969	£0 20
Button gives 1 pole change over action		
Rating 10 amp 250V a.c.	1970	£0 25

DISPLAYS

Type	Order No.	Price
BDL707 0-3in single	1510	£0 80
BDL747 0-6in single	1511	£1 50
BDL727 0-5in double	1512	£1 80

COLD CATHODE ITT 5087 ST side viewing indicator tubes. Displays 0-9 and decimal points. Wide viewing angle—operates from 180V with 16kΩ series anode resistors—character height 16-5mm pin connections supplied.

Order no. 1513 Price £0 60

VOLTAGE REGULATORS

Positive regulators TO220 case

MVR 7805 5V	£1 25	MVR 7815 15V	£1 25
MVR 7812 12V	£1 25	MVR 7824 24V	£1 25

Negative Regulators TO220 case

MVR 7905 5V	£2 00	MVR 7915 15V	£2 00
MVR 7912 12V	£2 00	MVR 7924 24V	£2 00

ORDERING

PLEASE WORD YOUR ORDERS EXACTLY AS PRINTED, NOT FORGETTING TO INCLUDE OUR PART NUMBER.

VAT

ADD 12 1/2% TO PRICES MARKED*
ADD 8% TO OTHERS EXCEPTING THOSE MARKED†. THESE ARE ZERO

BI-PAK

Dept. P.W.6, P.O. Box 6, Ware, Herts
COMPONENTS SHOP: 18 BALDOCK STREET, WARE, HERTS

Comment Impossible!

A PART from the 22,000-odd amateur radio licensees in this country there are tens of thousands of enthusiastic listeners to the amateur bands. Many of the latter are just as keen to know what is going to happen to the bands at the World Administrative Radio Conference in Geneva in 1979 as the licensed amateur.

To recap, the IARU (International Amateur Radio Union) represents just about all the national radio societies of the world and it consists of three regions. Region 1 comprises Europe and Africa, Region 2 is North and South America while Region 3 is Asia, Australia and Oceania. Believe it or not, the IARU has a plan ready for the frequency allocations it would like to see granted to the Amateur Service at the Conference. Few people can even begin to visualise the enormous amount of work that this has entailed already.

However, it is very important to remember that no national society, or even IARU itself, has a direct voice at WARC. This is a point that is frequently overlooked by those who ask 'what's the RSGB doing about protecting our bands'? National societies can only put their proposals to their own appropriate administration, the Home Office in this country. Nevertheless, if every national society throughout the world can present essentially the same proposals to its own administration there is a far greater chance of achieving success when the Conference sees such a united and massive demand. The big stumbling block is the fact that every nation at the Conference, whether it be the US or Togoland, has just one vote regardless of its standing in the field of radio communications or the number of licensed radio amateurs it has, if any!

The March issue of *Radio Communication*, journal of our own RSGB, mentions that the Home Secretary, in a written reply to an MP's question, said that although a substantial measure of consultation with users and manufacturers of radio equipment had already taken place a wider programme of consultation was desirable before the UK's proposals for the Conference were formulated. The Home Secretary added that comments from all interested bodies **and members of the public** should be sent to the Home Office, Radio Regulatory Department, Waterloo Bridge House, Waterloo Road, London SE1 8UA by 30 April 1977. (Copy, please, to RSGB).

Since the amateur band proposals represent only a very small part of the radio frequency spectrum that will be considered by the Conference it would be nice to know what all the other 'interested parties' would like to grab! It would be nothing short of a miracle if a member of the public could cast his/her eyes over the mountain of bumph involved and come up with his/her comments by 30 April!

As a matter of interest the general proposals for the HF amateur bands are for exclusive world-wide bands from 1.8 to 2.0MHz, 3.5 to 4.0MHz, 6.8 to 7.3MHz, 14.0 to 14.5MHz, 21.0 to 21.5MHz with the present allocation of 28.0 to 29.7MHz. Additional bands on the same basis are requested for 10.1 to 10.6MHz, 18.1 to 18.6MHz and 24.0 to 24.5MHz. Strangely enough, the American Amateur Radio Relay League (ARRL) and their Federal Communica-

tions Commission both agreed on the additional bands but when FCC's final proposals came out there was no mention of them. Another proposal is for a band at 160 to 200kHz, yes, kHz! But only for Regions 2 and 3 and not our Region 1. Our punishment, I suppose, for having long wave broadcasting in Europe already!

ERIC DOWDESWELL *Assistant Editor*

next month in Television

● TV SIGNAL INJECTOR

A handy tool for tracing the source of signal discontinuity in a TV receiver is a signal injector. This one, designed by Alan Willcox, provides an r.f. signal which is 100% modulated at a.f., giving a definite pattern of horizontal bars on the screen. The harmonics of this signal enable the injector to be used in every signal stage, while the a.f. component enables the audio section to be investigated. Construction is simple and the controls consist of just an on-off button and an attenuator.

● FREQUENCY SYNTHESISED TUNING

Here's another way in which i.c.s can provide a radically new approach to TV receiver design, this time revolutionising channel selection. The channel number is simply dialled up and the set then proceeds to tune in the channel itself. All that's required is a phase-locked loop and a digital counter.

● BAIRD 700 COLOUR CHASSIS

One of the earliest colour chassis to appear in the UK was the Baird 700/710 series. These sets may now look dated but can nevertheless still be made to give a very good account of themselves. E. Trundle explains how to handle them and describes the usual faults encountered.

● THE TV TELETXT DECODER

Next month we describe the operation and construction of the memory circuits.

PLUS ALL THE REGULAR FEATURES

NEWS...

NEWS...

NEWS...

Don't miss this!

THE Wessex Amateur Radio Group has organised a special programme for Friday 20th May when 'Dud' Charman BEM G6CJ will be giving his now famous lecture on 'Aerials and Propagation', PLUS Ken Alford G2DX talking on the 'Early Days of Wireless'. The venue on this occasion is the Bournemouth School, East Way, Bournemouth at 7.30pm sharp. Further information from Hon. Sec. G. Cole G4EMN, 6 St. Anthony's Road, Bournemouth.

Infocard

OUR attention has been drawn by Infocard Limited, to the fact that they have been using this name for their products for some years. On this basis they claim ownership to it. In the light of this information, we will not issue any further cards under that name.

Otley rally

ON the 22nd May the Otley Radio and Electronics Society will be holding the Northern Mobile Rally at the Victoria Park Hall, Keighley, Yorks. Amongst the exhibitions will be Trade stands, a Talk-in Station operating on FM and SSB on 2m, raffles, and a children's film show.

Further information from the Rally Manager, J. E. Annakin, G8DFZ, 25 Ashfield Place, Otley, West Yorks LS21 3JN.

Chirp . . . chirp . . .

ENTRANTS have until the end of October to record the sounds of the countryside for entry in the competition. Competition—? well it's 3M's Scotch Wildlife Sound Recording Contest and carries a top prize of £500-worth of JVC 'sound safari' recording equipment, with other

prizes amounting to a further £500.

There are several categories in which the enthusiast can enter, and these are for both experienced and novice amateur recordists—for birds, mammals, insects, and outdoor habitat recordings, with special awards for the most



original, best entry on cassette, and best entry in stereo. Naturally, entry is completely free.

All entrants will be invited to the grand prizegiving and luncheon in London (whether they are prizewinners or not), and prospective candidates should apply for rules and entry forms from R. Richmond, PR Executive, Recording Materials Division, 3M UK Ltd., 380/384 Harrow Road, London W9 2HU. Tel: 01-286 6044 Ext. 244.

... other rallies cannot reach

THE Ipswich and Mertlesham Radio Clubs are organising what they call 'The East Suffolk Wireless Revival'. It is intended, say the Clubs, to bring back the participating type of radio rally where the enthusiast or just generally interested hobbyist can find something of interest, or inspiration, as well as a chance to spend his money!

At the time of writing there

are some eleven events planned, amongst which will be a static 2m DF hunt, SSTV demonstrations, Drive-in test facility for mobiles, full 2m Talk-in using GB3PO, a home construction competition and Trade stands.

The venue will be the Civil Service Sports Ground, Straight Road, Bucklesham, Ipswich (near the Suffolk Show Ground, eastern side of Ipswich and adjacent to the A45). Opening will be from 11 am to 4 pm and will be on Sunday, May 29th.

RTTY lectures

THE British Amateur Radio Teleprinter Group invites any club which would like a lecture on amateur RTTY, given by one of the Group's team of lecturers, to write to:—The Secretary, GW3IGG, 40 Lower Quay Road, Hook, Haverfordwest, Dyfed SA62 4LR.


The BARTG will also be holding its annual convention on Saturday, May 21st, at the Village Hall, Meopham, Kent. Features of the convention include lectures, bring-and-buy stalls, a tape factory and trade stands. Doors open at 11 am, and anyone arriving at Meopham Station before 1.15 pm will be transported to the Hall.

Free chart

THE principal feature of the latest brochure to be issued by the printed circuit companies in the Nevin Group is a comprehensive fold-out wall chart. It contains a wealth of information and data of interest to people who design PCB's. Apart from metric conversions and drill sizes it gives data for conductor current ratings, recommended protective finishes, preferred relationships of hole sizes to pad diameters and other essential information. The brochure is available, free of charge, from Nevin Electric (Holdings) Ltd., 9 Arkwright Road, Poyle Trading Estate, Colnbrook, Bucks. Tel. Colnbrook (02812) 2325.

REVERBERATION amplifier

S.C. PARSONS

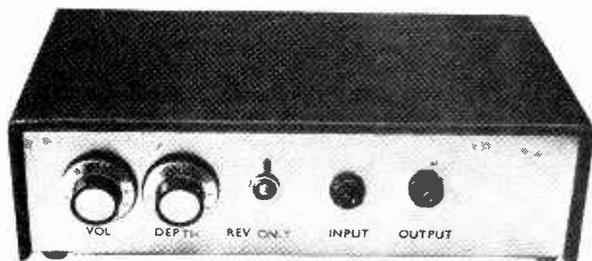

★ components list

Resistors

R1	120k Ω	R8	12 Ω
R2	22k Ω	R9	22k Ω
R3	3.3k Ω	R10	680k Ω
R4	10k Ω	R11	390k Ω
R5	15k Ω	R12	22 Ω
R6	6.8 Ω	R13	22 Ω
R7	6.8 Ω		All 10% $\frac{1}{4}$ W
VR1	1k Ω log or lin potentiometer		
VR2	2k Ω skeleton pre-set		
VR3	10k Ω log potentiometer with DPST switch		

Capacitors

C1	15 μ F 40V elect.	C5	47nF
C2	15 μ F 40V elect.	C6	15 μ F 40V elect.
C3	1nF	C7	470 μ F 40V elect.
C4	10nF	C8	470 μ F 40V elect.

Semiconductors

Tr1	BC108	D2	1N4001
Tr2	BC108	D3	1N4001
Tr3	BC108	D4	15V 1.3W zener
Tr4	BC214	D5	15V 1.3W zener
D1	1N914	IC1	741 op-amp 8 pin

Miscellaneous

Springline, HR42 available from Henry's Radio or the 'Short Spring Line' from Maplin Electronics, or Watford Electronics. PCB, 130 x 80mm available from the Readers PCB Service, page 131. T1, mains transformer. S1, SPDT switch. Two knobs with skirts. Jk 1/2, mono jack sockets. Terminal block. Aluminium box with lid approx 280 x 160 x 70mm. Mains lead, wire, stand-off pillars, fuse & holder, etc.

HOME-MADE tape recordings can often sound uninteresting even if the sound quality is very high, an impression which can usually be traced to a lack of reverberation. If tearing up the carpets in the living room doesn't appeal to you, there is another way of imitating the sound of a recording chamber and this is by using a reverberation amplifier.

Mechanical vibrations

There are several alternatives open to the amateur electronics enthusiast who wishes to build a reverberation amplifier, and the one chosen here uses a springline. This consists of a long coiled wire supported at either end in a compliant mounting. If mechanical vibrations are set up at one end by a transducer, they will travel comparatively slowly down the spring and "bounce" back, modifying on-coming waves. The output is taken from another transducer at this far end, and with correct amplification can sound very much as if heard in a large

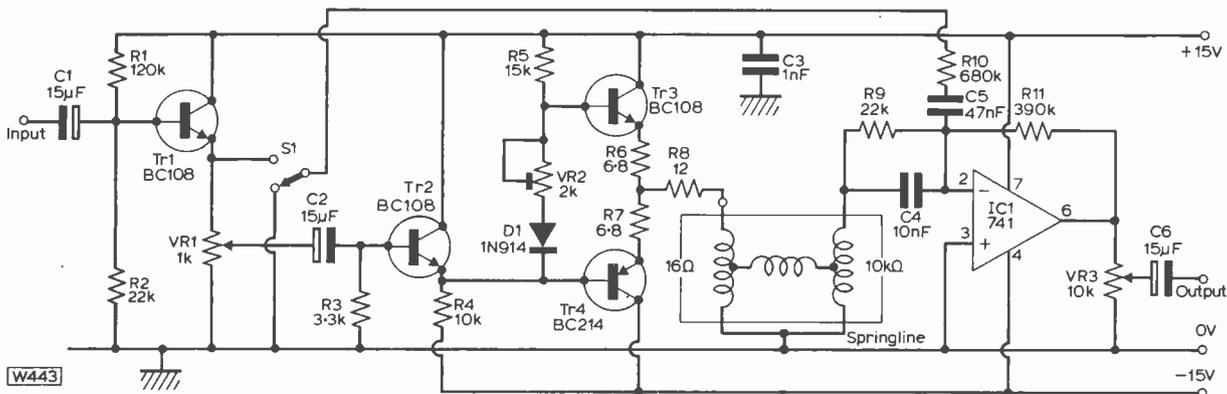


Fig. 1: Full circuit diagram of the Reverberation Unit. The mains power supply circuit is shown in Fig.4. S1 enables full reverberation to be obtained when switched to OV.

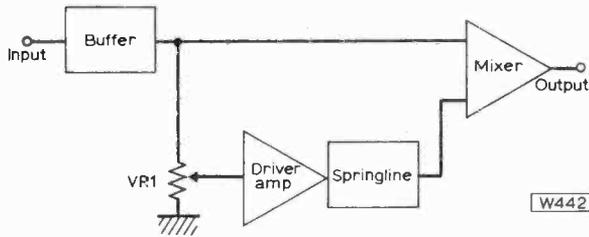


Fig.2: Block diagram showing the basic stages in the circuitry of the reverberation amplifier.


cathedral. The block diagram of the unit is shown in Fig. 2.

The input is buffered in the first stage and then

splits. Part of the signal goes directly to the mixer, and part goes via a depth control to the driver amplifier necessary to match the low input impedance of the springline. The output of the latter is then taken to the mixer so that by varying the setting of the depth control, the amount of signal passing through the springline to the mixer can be varied, and hence the depth of the reverberation effect controlled.


Circuit details


Fig. 1 shows the circuit diagram, where Tr1 and its associated components form the input buffer, and VR1 the depth control. The signal at the emitter of

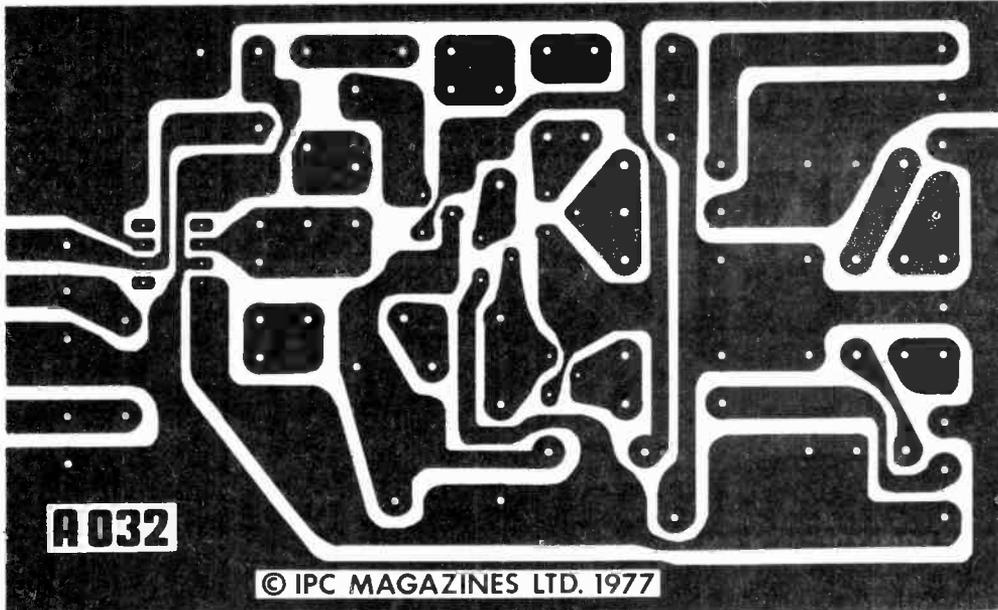

AM 0526

Fig.3: PCB designed for this project, showing the foil side above with component overlay below.

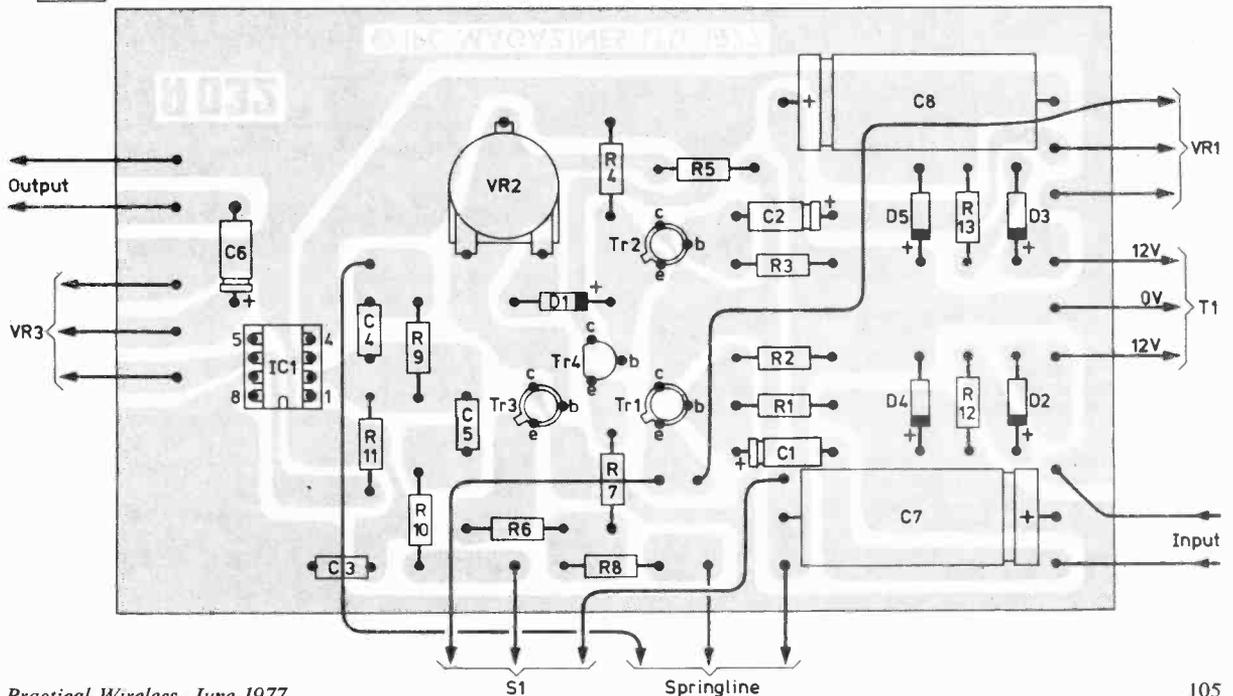

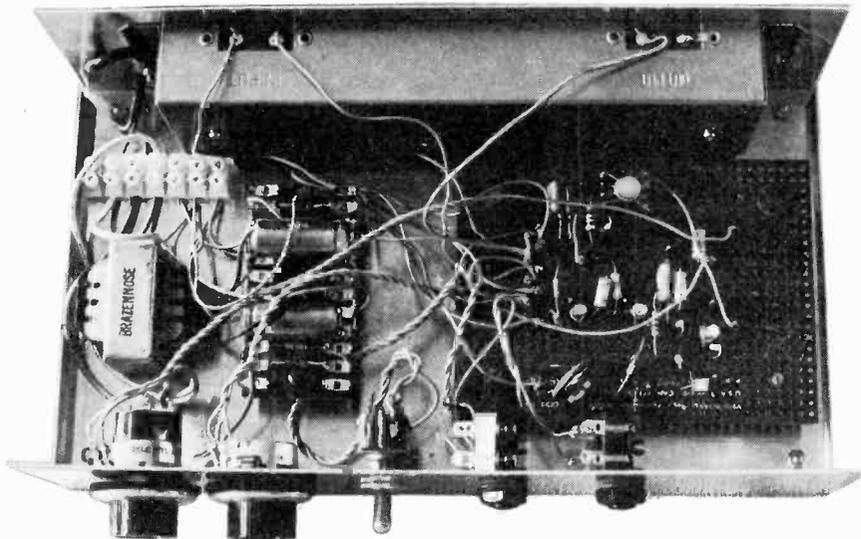

Photograph of the inside of the Reverberation amplifier showing the prototype model, using Veroboard and tag strip for component mounting.

Tr1 is unaffected by the setting of VR1 and goes via S1 direct to the mixer. Tr2, 3 and 4, form a driver amplifier which is fairly unusual in that it powers the springline directly (ie without the normal capacitor). If this were not so, the signal coming out of the springline would be almost unintelligible. Unfortunately, this method involves the use of a split power supply and some method of forcing the driver amplifier output to track the 0V line, or a heavy current will flow through the output transistors. This tracking is a secondary function of Tr2.

The mixer is a 741 op-amp, chosen because it simplifies the circuit and allows frequency compensation for the springline output (the response of the springline falls off rapidly above 4kHz, although resonances occur right up to the end of the audio range). The op-amp also provides a low output impedance, which means that a 1kΩ potentiometer

mains power supply. Although it can't supply a very heavy current it's quite suitable for this type of application.

Fig. 3 shows the PCB full size. There are no special points to be watched except the orientation of semi-conductors and electrolytic capacitors. It is quite a good idea to use an 8-pin DIL holder for IC1, and screened wire to connect the springline output to the board, to reduce the hum level from the transformer.

Alignment

Set VR2 to minimum resistance, switch on, and measure the output relative to 0v. If it is not within half a volt, switch off and check for faults. If all is OK connect an earphone or speaker with an impedance of over 14Ω and apply a signal to the input. Adjust VR2 until distortion just disappears.

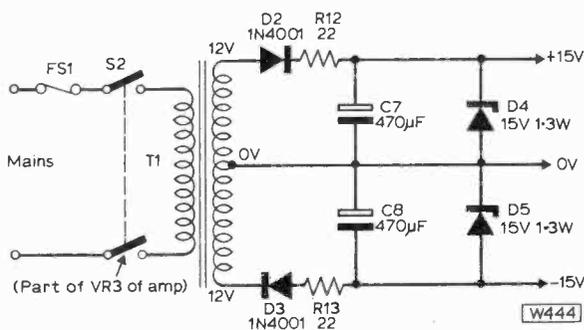


Fig. 4: Suggested circuit for the power supply, giving the twin supplies necessary for the 741, Tr2 and Tr4.

could be used for VR3 if necessary. S1 is optional and when the wiper is connected to 0V, only full reverberation is obtained. This allows the depth to be separately controlled in a synthesiser, for which the unit was designed. Alternatively the wiper could be connected to the positive end of C2 and the other contacts to the wiper of VR1 and 0V; in this way reverberation could be switched out if necessary.

Fig. 4 shows the circuit diagram of a suitable

GAS/SMOKE SENSOR ALARM April 77

Figaro Engineering (Ireland) Ltd., Shannon Airport, Co. Clare, Ireland, importers of the TGS812 sensor, have asked us to point out that this sensor has been in continuous use for more than eight years and that its life, when used in accordance with the manufacturer's recommendations, is that of a semi-conductor device. Sensors can thus be mounted directly on printed circuit boards.

PW can supply a dimensioned drawing of the TGS812 pin configuration on receipt of an SAE. Mark outer envelope 'TGS812'.

Reporting THE BBC'S 500TH. WORLD RADIO CLUB

RON HAM F.R.A.S.


WITH over 32,000 members throughout the world and a weekly audience running into millions the BBC World Service had something to celebrate on 11th February when they recorded the 500th edition of their popular programme, World Radio Club. Since it began on 1st July, 1967, the programme has provided a club atmosphere especially for the shortwave enthusiast and for those who are fascinated by the many aspects of radio communication. To achieve this, the BBC producers have used a variety of "outside" people, well known in the world of radio, to complement their regular team, and many of them were among the special guests attending the celebrations at Bush House, Home of the BBC World Service.

For the first time, and to mark this special occasion, an audience of radio enthusiasts was invited to participate in the programme and to put questions to the panel of experts chaired by regular presenter Frank Hennig G3GSW. Questions from the floor about modes of transmission, the problems of fading, amateur call signs, frequency allocation and the sunspot cycle were answered by panellists Bill Wood, Head of the BBC's Engineering Information

Department, Desmond Colling of the International Short Wave League, and of course Henry Hatch G2CBB, the programme's resident engineering personality.

The atmosphere of the recording session was alive and one could sense the enthusiasm and warmth between the BBC's staff

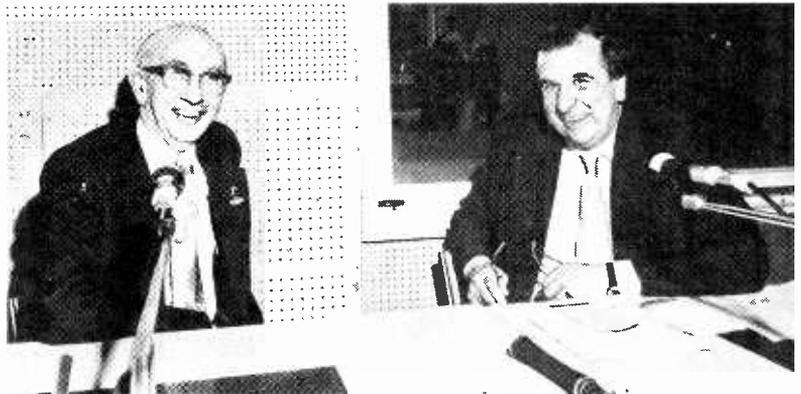Baresby, former chairman of the programme, were flying some 2000ft over the North Atlantic, in a piston aircraft, doing an interview for WRC with the RAF, showing that not all of their outside broadcasts go smoothly. Temporary producer Richard Lambley G8LAM read a letter of good



Lord Wallace of Coslany, President of the Radio Society of Great Britain (left), was interviewed by Frank Hennig during the 500th edition of the World Radio Club.

who stage-managed the affair, the panellists as they answered the questions, and the entire studio audience. It was great to hear Reg Kennedy, regular producer of WRC, relate the story of the tape recorder which suddenly emitted smoke when he and Peter

wishes from the European DX Council, and George Jessop G6JP, General Manager of the RSGB was asked to comment about radio amateurs who gave their call signs too quickly!

Another bonus for the audience was to hear the current RSGB President, Lord Wallace of Coslany, telling Frank Hennig that now he is President every one calls him 'George' and it was obvious from the smile on his face that he was thoroughly enjoying both the Presidency and his evening as a guest of the BBC. The technical press was well represented, Practical Electronics, Practical Wireless and Radio Communication just to name a few, and everyone that the writer spoke to had nothing but praise for the programme and all wish it well for the next 500. This historic meeting of the World Radio Club was preceded by a small cocktail party.



The panellists in the programme were (left to right); Desmond Colling of the International Short Wave League; Frank Hennig, the regular presenter; Henry Hatch, the programme's resident engineering personality, and Bill Wood, Head of the BBC's Engineering Information Dept.

versatile AF GENERATOR

C.TOMS

THIS article describes a versatile AF waveform/function generator based on the 8038 integrated circuit. It provides sine, square and triangular outputs selected by a front panel switch. A single capacitor C2, Fig. 1, controls output frequency while a front panel calibrated potentiometer VR1 controls the capacitor charging current; the output frequency can be varied from 20Hz to 20kHz in a single range. Since the sine wave output is derived from the non-linear characteristics of a PN junction, the junction bias conditions are critical. VR3 and 4 give precise front panel bias adjustment. A 731 high slew-rate operational amplifier acts as a low impedance buffer to avoid loading the rather high (10kΩ) output impedance of the 8038.




Waveform timing

Fig. 2 shows the phase relationships between all three output waveforms when operating with a duty cycle of both 20 and 50%. A 50% duty cycle is achieved when $R3=R4$. VR2 enables variation of the duty cycle over a 20% range allowing the symmetry of all waveforms to be adjusted. For optimum performance, the charging current through the timing capacitor C2 must be held within the range 10μA to 1mA. With pins 7 and 8 of IC1 shorted, this can be determined from the value of R3 (which has nominally the same value as R4).

$$I = \frac{V_{cc}}{5 \times R3}$$

For good thermal stability, C2 should be a high quality polystyrene or silver mica type.

Fig.1: Circuit diagram of generator and power supply. The miniature type mains transformer is mounted on the PCB.

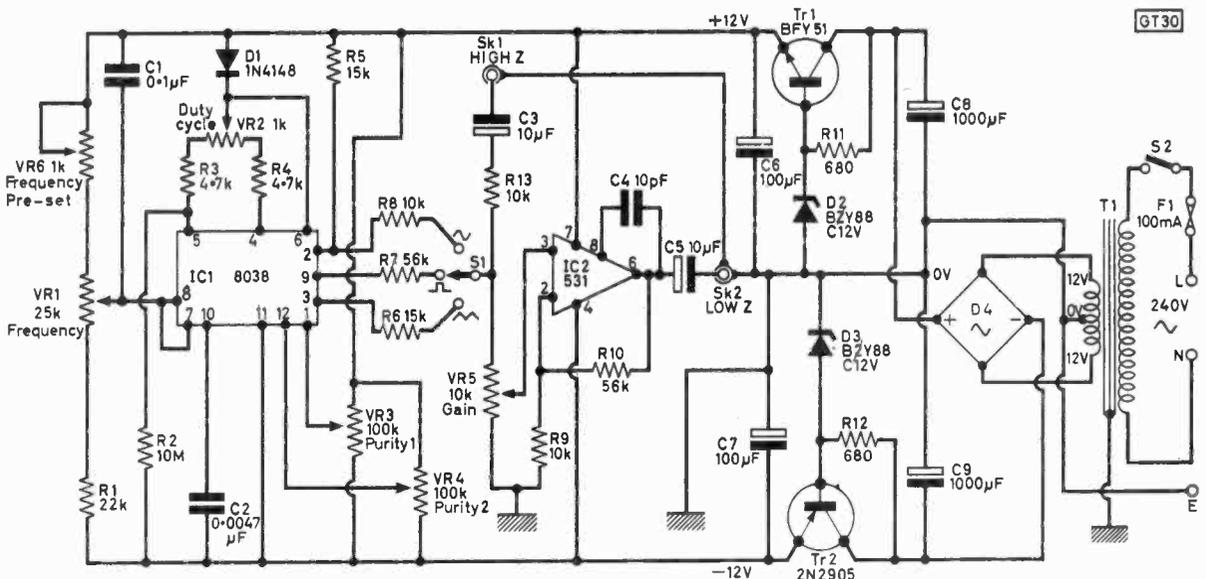

Frequency

The frequency of the oscillator is a direct function of the DC voltage existing between pin 8 on IC1 and Vcc. Originally intended by the chip manufacturer as an FM sweep facility, it provides the principal variable control but can be pre-set by VR6 for easy calibration.


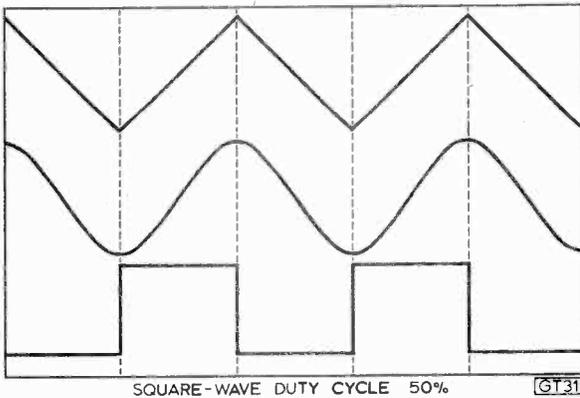
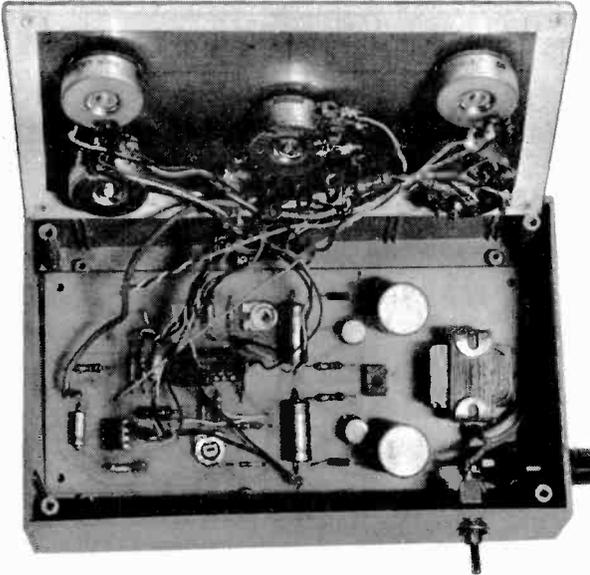


Fig.2: The upper drawing shows the various waveforms when operating with a duty cycle of 50%. The lower drawing illustrates the effect of VR2 adjustment.

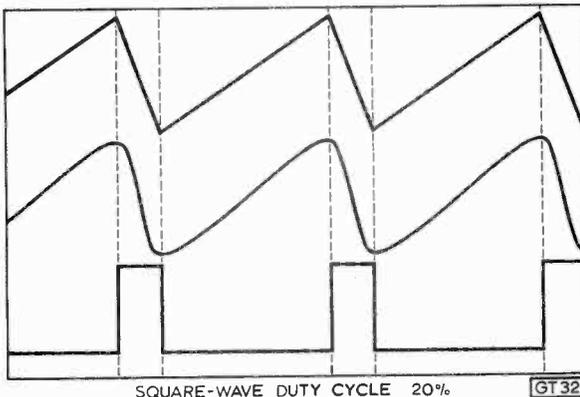

Construction

The circuit board should be assembled as shown in Fig. 3. It is probably better to assemble the power supply section first so this may be tested separately before adding the rest of the components. It should be checked between the junction of C6 and C7 and each supply rail (the top and bottom end of each capacitor respectively) for a reading of about 12V. Having established that the power supply is working, disconnect from the mains and assemble the remaining components interwiring the controls as shown in the photograph. The instrument should now be ready to test.

★ components list

Resistors

R1 22k Ω	R7 56k Ω	R13 10k Ω
R2 10M Ω	R8 10k Ω	VR1 25k Ω log
R3 4 7k Ω	R9 10k Ω	VR2 1k Ω pre-set
R4 4 7k Ω	R10 56k Ω	VR3 100k Ω lin
R5 15k Ω	R11 680 Ω	VR4 100k Ω lin
R6 15k Ω	R12 680 Ω	VR5 10k Ω lin
All 0.25W 5%		VR6 1 k Ω pre-set

Capacitors

C1 0.1 μ F ceramic disc	C6 100 μ F 25V
C2 0.0047 μ F	C7 100 μ F 25V
C3 10 μ F 25V	C8 1000 μ F 25V
C4 10pF	C9 1000 μ F 25V
C5 10 μ F 25V	

Semiconductors

D1 1N4148	IC1 8038
D2 BZY88 C12V	IC2 731
D3 BZY88 C12V	Tr1 BFY51
D4 Bridge rectifier 0.5A 50V PIV	Tr2 2N2905

Miscellaneous

T1 12-0-12V 50mA mains transformer for PCB mounting. S1 1 pole 3 way wafer switch. S2 SPST mains switch. F1 100mA fuse 20mm. Case suggested type 509737 from RS Components.

Resistors R5, 6 and 7 correct the sine, square and triangle outputs from IC1 to nominally the same amplitude. The outputs are switched by S1 to the top of the gain control VR5; the high impedance output is taken from S1 via C3 and R13. The NE531 high slew-rate operational amplifier is used in a conventional inverting configuration with frequency compensation effected by C4. The output of IC2 is taken to the low impedance output socket via C5.

Power supply

The power supply comprises a simple bridge arrangement providing both negative and positive supply rails. Each side is stabilised by a zener diode (D2 and 3) in conjunction with a series pass transistor (Tr1 and 2). The actual output voltage will be 0.5V below the nominal zener diode voltage due to the base-emitter drop in the series pass transistors.

Sinewave distortion



External purity adjustment of the sine wave is effected by VR3 and 4. After correct adjustment of these controls, less than 5% total harmonic distortion can be achieved. It also provides the facility for introducing a degree of controlled distortion which may be useful in some applications.

Testing and calibration

As a quick audible check, a 3 to 15Ω loudspeaker may be connected to the low impedance output and the instrument switched on. A tone should be heard which varies in frequency with rotation of VR1. The calibrated scale shown in the photograph can be copied but it may be very very inaccurate for individual instruments. The reason for this concerns

the resistance vs rotation for log-law pots. Correlation may be acceptable in potentiometers from an individual manufacturer but there is usually very little where the sources of supply differ. In the event, the prototype used a pointer knob on VR1 covering a 270° sweep.

Initially, select squarewave output and set the purity and duty cycle controls to mid travel. Set the frequency control to 50Hz and connect an oscilloscope

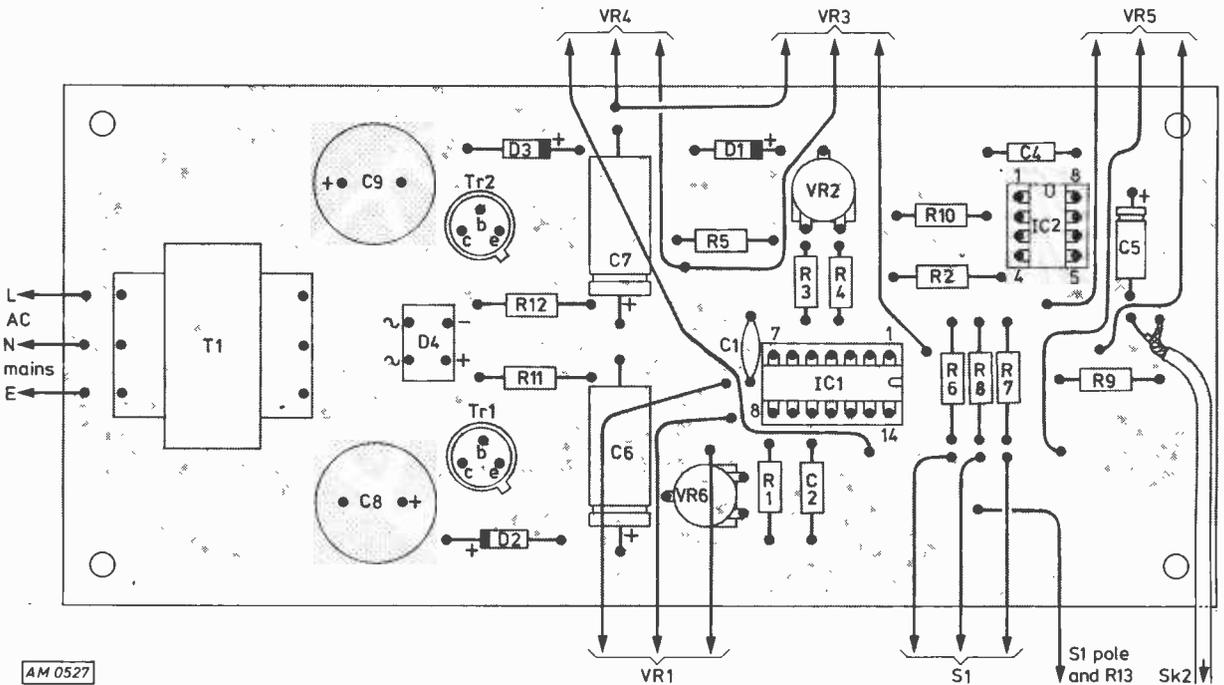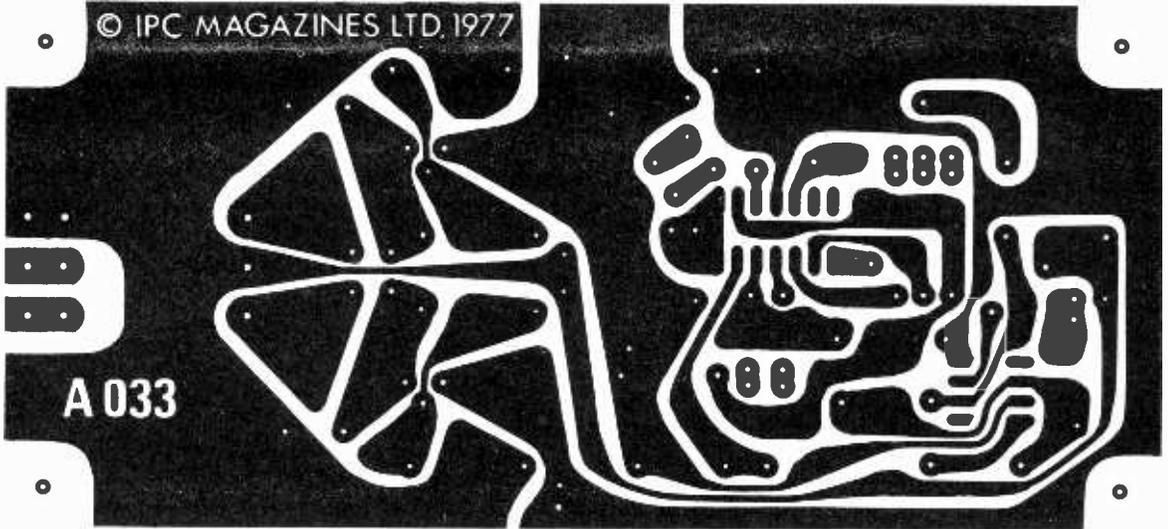

AM 0527

Fig.3: The top drawing shows the PCB copper side to actual size. Note that, when soldering the mains transformer into the board, care should be taken to avoid solder splashes around the mains input pins. The lower drawing shows the PCB reversed for component identification.

or frequency counter to the low impedance output. Adjust the frequency pre-set VR6 until the counter or 'scope display indicates a 50Hz output from the waveform generator. Adjust pre-set VR2 for a 50% duty cycle as shown in Fig. 2. Select the sinewave outputs and adjust purity controls VR3 and 4 for minimum distortion of the sinewave. Note the positions. The instrument is now ready for use. **PW**

HOTLINES

ON RECENT DEVELOPMENTS

Long life cell

Having recently reported in Hotlines about Lithium batteries, I can now announce that I actually know what they look like. The ones I've seen are about 140mm long and about 40mm in diameter. These have a 30AH capacity at a drain of 1A. One cell has a 2.8V nominal terminal voltage and an energy density of 134 watt-hours per pound. The shelf life of these devices is some five years and they will operate at -65°F . Price (in the U.S.) is put at around ten dollars but that's in very large quantities.

Still on Lithium cells, a Japanese manufacturer will soon be marketing these batteries which they will make very small, like 23mm in diameter by 2½mm thick. Such a cell will have a 2.8V nominal voltage and a current capacity of 140mA hours. In calculator applications using liquid crystal readouts, some sources believe that these batteries would last something like five years (5 years!).

Clear enough?

Projection television is back in the news. I hear that one company is about to demonstrate a 1,000-line colour television projector. I will report on this as and when news comes in, but things like single electron gun, and colour-selection diffraction grating which does not require registration are all being banded about.

Amateur radio enthusiasts (Hams) who are interested in very high frequency working will delight in the news about a new UHF transistor just about to make its debut. This device gives 40W of CW with a gain of 9dB at 2GHz (for the uninitiated we're talking about two million million cycles every second). A common manufacturing mode with higher power UHF devices has been to lay down a number of separate transistors on a single chip and to connect them all up internally to operate in parallel as one big, single transistor. The problem has been that slight differences in these

individual transistors causes each to operate slightly differently and thus incur power losses. The new devices are manufactured using ion implantation techniques to assure more uniform individual transistors which are then wired up to make the one big one. I wonder what next.

Electret relay

Relays have been with us for many years but there has been some interesting development in this field of late. First, I see there is a 3A relay now available which weighs only 0.16oz. and stands just 10mm high. These relays have 2.5mm pin spacings making them ideal for PCB mounting, and are SPDT devices able to switch their 3A DC at 24V DC.

Looking at another kind of relay makes one wonder about further developments in this field. The new one is called an electret relay. A few years ago the electret was just a laboratory curiosity. Then, electret microphones were developed and so the principle had a commercial application. Now, it seems that this electret idea is to become a new family of relays but with certain very attractive advantages. For example, they require anything up to 100,000 times less power to switch than conventional relays of the electro-magnetic ilk. The basic operation is quite simple. An electret (a piece of dielectric material that has a permanent electric polarity) is put between two plates of a shorted capacitor. This causes two electric fields (either side of the electret) and induces charges on the two plates of the capacitor. If the electret lies exactly midway between the two plates, then the fields will be equal and it will stay exactly half way between them. If, however, the electret is moved, even slightly, towards one of the plates, then it will immediately be attracted towards that plate and will switch over to it. By feeding in a pulse of the opposite polarity, the electret can then be made to switch over to the opposite plate. Thus it acts like a bistable, and the electret itself can be thought of as an electric analogue of the magnet.

Super Seekit?

Because treasure hunters are rife in Britain, any news of something different in metal detection is almost certain to arouse interest. Most PW readers will have seen circuitry for the BFO-type metal detector and will have heard about things like induction balance and crystal filter devices. Just to whet your appetite a bit further, I hear that one American laboratory has come up with an instrument called an "ultrasensitive three-axis superconducting magnetometer". If it sounds impressive, just listen to what it can do. It measures very tiny changes in magnetic and electric fields underground and it does this in three dimensions—simultaneously (sounds like some of these Yoga postures!). It can locate a geothermal-energy source when it is 30 miles (that's thirty miles) underground. Might be worth getting one to check on that old rumour about the King's treasure in the Wash area? Sorry, it's experimental at the moment and definitely not for sale.

Warm vidicons

Most people have heard of a vidicon tube, but what about a pyroelectric vidicon? These are tubes used as the sensor element in infra red TV cameras and other imaging systems. While they work very well indeed they do have one snag; they need to be at sub-zero temperatures.

Now, various companies have come up with pyroelectric vidicons which are happy to function at room temperatures and so they avoid the enormous costs associated with providing cryogenic equipment (that's the posh name given to the gear which keeps all at sub-zero temperatures). One company has recently launched a pyroelectric vidicon tube 25mm in diameter and about 150mm long. The interesting thing about this tube is its excellent resolution: for a 250 line height TV picture it has a temperature resolution to within 0.5°C .

Ginsberg

MONOLITHIC VOLTAGE REGULATORS


Brian DANCE M.Sc

Part 2:- VARIABLE REGULATORS

LAST month we saw how 3-terminal regulators can be used in very simple circuits to provide regulated fixed output voltages. Most of the variable voltage regulators to be discussed this month have more than three connections and used in slightly more complex circuits. Unlike most fixed regulators, each type of variable regulator requires a different type of circuit.

THE 723 TYPES

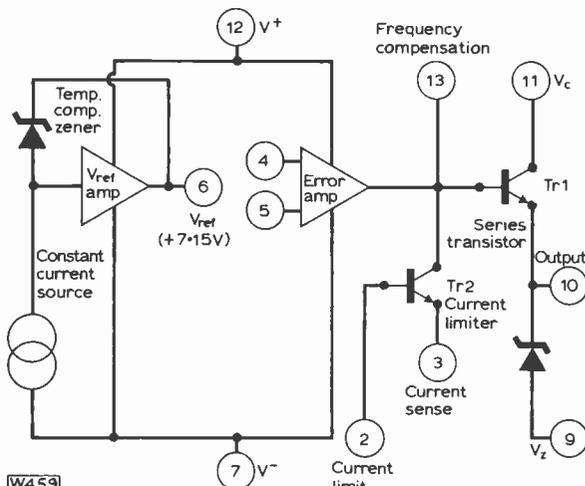The 723 type of variable regulator has become an established type which is produced by many manufacturers. This device is produced in a circular metal package and also in a 14-pin dual-in-line package under type numbers such as L123 (SGS-ATES),




W459

Fig. 10: Basic block diagram of the circuitry in the 723 type of voltage regulator.

LM723 (National Semiconductor), SF.C2723 (Thomson CSF), μ A723 (Fairchild and Signetics), MC1723 (Motorola) and SN72723 (Texas Instruments).

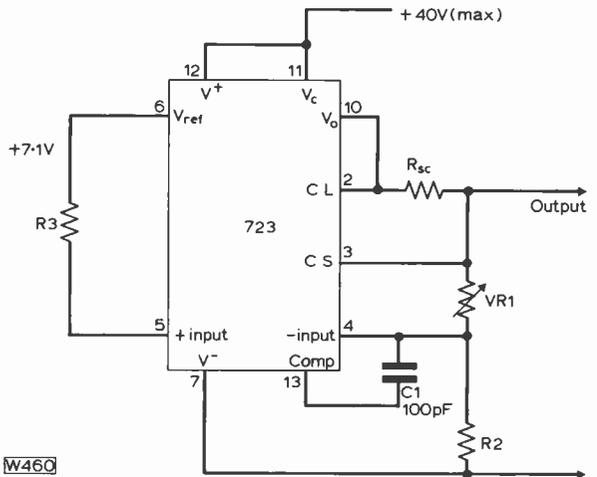The 723 device can itself deliver an output of up to 150mA over a range of 2V to 37V but the load current can be increased by the use of a more complex circuit with an external power transistor. The internal circuit is shown in block form in Fig. 10 together with the pin numbers for the 14-pin dual-in-line package. (There is no zener connection in the circular metal package.)



W460

Fig. 11: Method of using the 723 to provide a regulated output voltage of 7 to 37V.

Unlike the 3-terminal fixed regulators, the 723 should not be regarded as a completely built regulator, but rather as a versatile package which the good designer can connect up in many ways with external components to produce a wide variety of circuits. In all circuits the maximum supply voltage is 40V, but, in addition to its use as a regulator, the 723 can be used as a comparator, gated amplifier, multivibrator, etc. Space limitations enable only a few of the numerous circuits to be shown here and in all cases the pin numbering applies only to the dual-in-line version.

7 TO 37V REGULATOR

The circuit of Fig. 11 shows how the 723 can be used to provide a regulated output of 7 to 37V; it should be considered in conjunction with Fig. 10. The amplified V_{ref} from pin 6 is connected via R3 to the non-inverting input of the error amplifier (pin 5). The output from pin 10 is connected through R_{sc} to the potential divider VR1 and R2 from which feedback is taken to the inverting input of the error amplifier. The feedback action of the circuit maintains this input at the potential of V_{ref}. The output voltage is therefore equal to $V_{ref} (VR1 + R2) / R2$. For minimum temperature drift R3 should equal VR1 in parallel with R2, but R3 may be replaced by a wire link for circuit simplicity. Generally R2 may be of the order of 5k Ω . The no-load quiescent current of the 723 is only about 2.3mA and the dropout voltage about 3V.

The maximum output current is determined by the value of R_{sc}. When the output current flowing through this resistor produces a voltage drop of about 0.65V, the current limiter transistor Tr2 of

Fig.10 will conduct and will remove the base drive from Tr1 so that the output voltage falls. Thus if $R_{so}=10\Omega$ the maximum current will be set at about 65mA. This current-limiting facility not only protects the 723 (which can dissipate 1W) but can also be used to protect any devices fed by the regulated supply.

The circuit of Fig. 12 is similar to that of Fig. 11, but the transistor Tr1 boosts the maximum output current which can be taken to over 1A. If required, R_{so} can be switched in value to provide limiting at various output current levels.

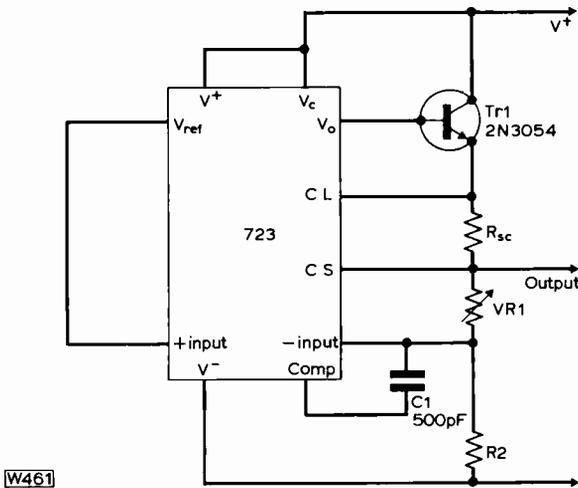


Fig. 12: Use of an external transistor to increase the maximum output current.

2 TO 7V REGULATOR

One of the main disadvantages of the 723 device is that a different circuit must be employed when the output voltage is to be less than V_{ref} . The circuit of Fig. 13 can provide outputs of 2 to 7V. The potential divider R1 and R2 reduces the V_{ref} voltage to $V_{ref} R2/(R1+R2)$ before it is applied to the non-inverting input; the output potential is equal to this latter potential. C_{ref} prevents any short-term variation in the potential of the non-inverting input. The remainder of this circuit operates in the way discussed previously.

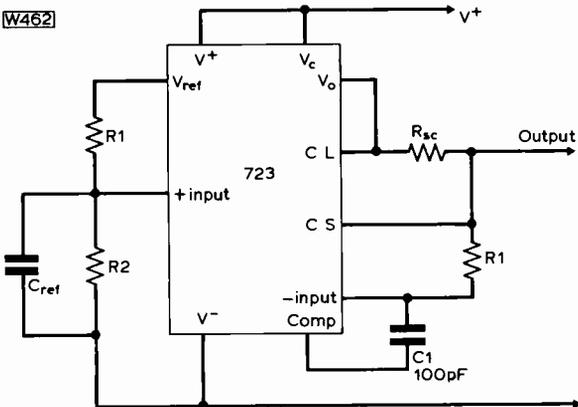


Fig. 13: In this application the output voltage, 2 to 7V, is less than the internal reference voltage.

THE CA3085

Another versatile voltage regulator device is the RCA type CA3085 (available from Electronic Component Supplies Ltd., Thames Avenue, Windsor, Berkshire). It can provide outputs of 1.8 to 26V at a maximum current of 100mA, the maximum input voltage being 30V. The device is available as an 8-pin dual-in-line package and as an 8-lead metal can package.

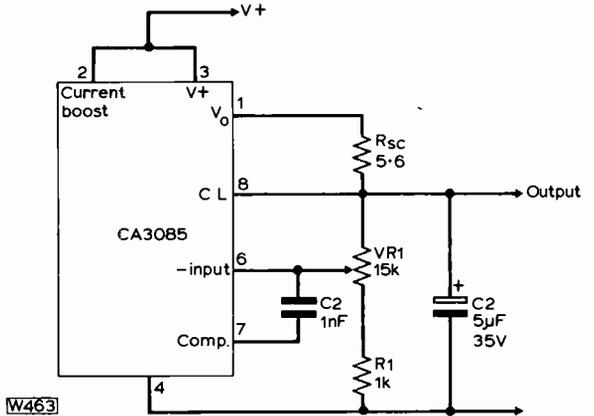


Fig. 14: Another voltage regulator circuit, this time using an RCA CA3085.

A typical CA3085 circuit is shown in Fig. 14. The 1.6V reference voltage is available at pin 5, but no connection is made to this pin in the circuit shown. A 5μF capacitor from pin 5 to negative will reduce noise at the output. An output current of 100mA will produce 0.56V across the sensing resistor R_{sc} and current limiting will commence at about this level. Similarly, if R_{so} is 22Ω limiting will start at about 25mA output current. The output voltage is $V_{ref} (VR1 + R1)/R1$. As in the case of the 723, the CA3085 can be used for many purposes, for example, as a general purpose operational amplifier.

THE μA78G AND μA78MG

A very different approach has been adopted in the Fairchild μA78G 1A regulator and in the similar μA78MG 0.5A regulator. These devices have only four connections and require a minimum of external components. Short-circuit protection and thermal overload protection are both incorporated on the chip. Indeed, the writer felt that they would be almost indestructible if operated from the correct voltages until he accidentally connected the control voltage pin to the power supply!

A typical circuit for these devices is shown in Fig. 15. The value of R1 is chosen so that the recommended current of 5mA flows through this resistor (the control pin is at a potential of 5V). The output voltage is $(R1 + VR1)/R1$ times the 5V control potential. The control pin current is about 1μA and the dropout voltage about 2V.

Various other circuits using these devices are available for high output currents, for dual tracking voltage regulators, etc. The μA78MG is available in a miniature plastic package rather like an 8-pin dual-in-line device but with only four connecting pins at each corner and with metal tabs for heat sinking in the centre of each side of the device. The μA78G 1A device is available in a plastic package with a

W464

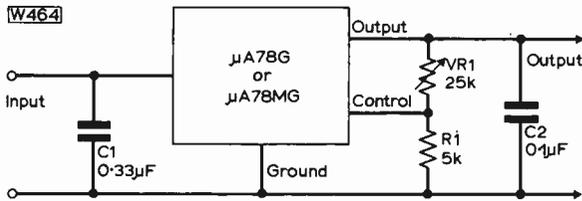



Fig. 15: In the Fairchild μ A78 type regulators only four connections are required.

metal tab for bolting to a heat sink and also in a metal case rather like a TO-3 transistor case. Similar 1A and 0.5A devices are available for negative outputs under the type numbers μ A79G and μ A79MG.

THE LM317

The LM317 is one of the most impressive regulator devices the writer has yet seen; it is the first 3-terminal variable voltage regulator and has a really excellent performance, yet can be used in simple circuits. This new device can be obtained in a TO-3 metal transistor power package (the LM317K), in a small TO-5 transistor type package (the LM317H) and in two plastic packages with tabs for bolting to a heat sink (the LM317T and the LM317P).

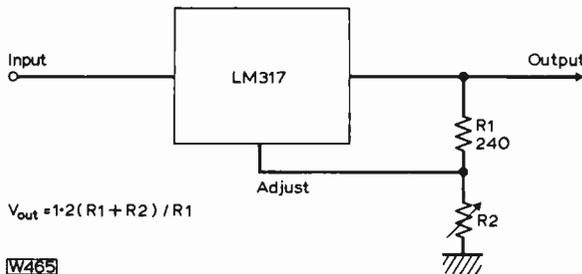The LM317K and LM317T can provide a current of at least 1.5A (typically 2.2A) at any voltage from 1.2V upwards, whilst the LM317H and LM317P can provide output currents of up to about 0.8A. The devices have current limiting (which begins at about 2.3A) and thermal shutdown circuitry (which operates at about 175°C).



W465

Fig. 16: In the LM317 series of regulators the external connections are reduced to three.

The reference voltage used in the LM317 devices is not obtained from a conventional zener regulator, but is a 1.25V source based on the band-gap energy of silicon. This not only enables the device to operate from input voltages well below the normal 7V zener reference voltage, but also provides less noise at the output than a zener circuit. Excellent hum rejection is obtainable from the LM317 (about 80dB with a 10 μ F capacitor between the adjust terminal and ground).

The LM317 devices can be used in the simple circuit of Fig. 16. The current flowing in the adjustment terminal is a constant 50 μ A and the device maintains a constant 1.2V across the resistor R1. Thus 5mA flows through R1 and R2. An optional output capacitor (about 1 μ F) will improve the transient response, whilst a 0.1 μ F input by-pass capacitor is recommended. The dropout voltage is not greater than 2.5V. The maximum permissible voltage between the input and output terminals of a LM317


device is 40V. However, the regulator itself is "floating" in the circuit shown in the sense that it is not connected to ground. Thus if R2 is large enough to ensure that the output remains within 40V of the input potential, the input voltage can have any desired value. Indeed, supplies of several hundred volts can be regulated with this circuit.

SWITCHING REGULATOR

The new Texas Instruments TL497 switching regulator in a 14-pin dual-in-line package should soon be available. This can provide outputs of up to 0.5A with power efficiencies of 60% or more. Designed to switch at 10kHz up to over 50kHz, this device contains all of the semiconductors required to build a regulator which can provide output voltages greater than the input voltage and which can invert the polarity of the input voltage. However, an inductor is required.

VARIABLE DUAL TRACKING

The Raytheon RC4194 14-pin dual-in-line device (available from Doram Electronics Ltd. Order code 306-011) can be used as a variable output voltage dual-tracking regulator for $\pm 0.05V$ to $\pm 30V$ at currents of up to 150mA. A single variable resistor adjusts both supply lines simultaneously. The device incorporates short-circuit current limiting (at about 300mA) and thermal shutdown circuitry which comes into operation at 175°C chip temperature; the maximum dissipation is 0.9W. Tracking is better than 1%.

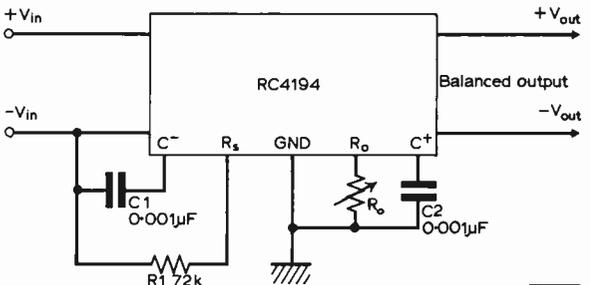

W466

Fig. 17: The Raytheon RC4194 needs only a single potentiometer to control the output of this dual-tracking regulator.

A typical circuit for the 4194 is shown in Fig. 17, each output voltage being 2.5 times the value of R_0 in kilohms. The resistor R1 may consist of 120k Ω and 180k Ω resistors in parallel. As in the case of most regulators, the output current can be greatly increased by the use of external power transistors.

Unbalanced tracking supplies can also be obtained using this device. For example, if R_0 is set to 15k Ω , this gives a $\pm 6V$ supply. If a 20k Ω resistor is now connected from the 'balance' pin to the negative line, the -6V supply will be unchanged but the positive line will be increased to +12V. Such a +12V, -6V supply is useful for feeding to 710 comparators.

HIGH CURRENT DEVICES

Variable output regulators able to deliver 10A over a range of +2 to +35V in one device and over a range of -4V to -30V in the other are available from Doram Electronics Ltd. They can dissipate up to 100W and are encapsulated in TO-3 power transistor cases.

PW

Safe, tough, efficient and versatile – that's our new miniature CX iron.

Safe because it is virtually leak-free (leakage current less than 1 μ A). Earth it if you like – three core lead. It is made to conform with B.S. 3456 and has a breakdown voltage of more than 4000V.

Tough because the handle is almost unbreakable and the ceramic shaft is covered by a stainless steel shaft.

Efficient because the element is situated right inside the soldering bit and the heat generated by its 17 watts is not wasted.

Versatile because the iron can be used for a wide variety of soldering jobs; with six easily interchangeable, slide-on bits, ranging from $\frac{1}{8}$ " right down to $\frac{1}{32}$ " (1mm). It's suitable for small, miniature and micro miniature joints.

Available for 220-250 volts or 100-120 volts. Weight – $\frac{1}{2}$ oz (40 gram). Length 7 $\frac{1}{2}$ " (19cm). Price – £3.40 fitted with standard bit $\frac{3}{32}$ " (2.3mm). Spare bits £0.45; £0.72; £0.84 exclusive of VAT.

Stocked by most of the well-known wholesalers and many retailers. Or direct from us if you are desperate.

Send for colour catalogue from:
Antex, Freepost, Plymouth PL1 1BR

Model X.25 is a general purpose soldering iron, also with two shafts for toughness and perfect insulation. Available for 220-250 volts or 100-120 volts at 25 watts and priced at £3.40 exclusive of VAT.



Standard model S.T.3 has a chromium plated steel spring, two sponges for cleaning the bits and is priced at £1.40 exclusive of VAT.



Mayflower House, Plymouth.
Telephone (0752) 67377/8 Telex 45296
Giro 2581000

Forget all you've ever read about
miniaturised soldering irons.
This is the NEW ANTEX CX.



LYNX ELECTRONICS (LONDON) LTD

92 BROAD STREET, CHESHAM, BUCKS.

Tel. (02405) 75154

P. and P. 30p — Overseas 90p — Matching 20p per pair. ACCESS
VAT 8% except for Items * which are 12½% — No VAT Overseas.

Prices correct
as at 31st March '77

THYRISTORS

PIV	1A	3A	4A	6A	8A	10A	15A	16A
	(TO5)	(ST-UD)	(C106)	(TO220)	(TO220)	(TO220)	(TO220)	(TO220)
200	0-35	0-50	0-45	0-40	0-50	0-60	0-68	1-14
400	0-40	0-60	0-50	0-45	0-87	0-88	0-98	1-40
600	0-65	0-85	0-70	—	1-09	1-19	1-26	1-80

BT106 £1-00, BT107 £1-60, BT108 £1-60, BT109 £1-00, BT116 £1-00, 2N3525 £0-50.

TRIACS—Plastic TO-220 Package Isolated Tab

	4A	6-5A	8-5A	10A	15A	
	(a)	(b)	(a)	(b)	(a)	(b)
100V	0-60	0-60	0-70	0-70	0-78	0-78
200V	0-64	0-64	0-75	0-75	0-87	0-87
400V	0-77	0-78	0-80	0-83	0-97	1-01
600V	0-96	0-99	1-01	1-10	1-21	1-26

N.B.—(a) without internal diac. (b) with internal diac.

TTL7400 Series

7400	0-18	7486	0-32	381	1-60	7488	2-02	3900	0-70
7401	0-18	7489	0-49	741	0-28	7490	0-85	748	0-45
7402	0-18	7491	0-85	748	0-45	7492	0-57	NE555	0-45
7403	0-18	7491	0-85	748	0-45	7493	0-45	NE585	0-45
7404	0-18	7492	0-57	NE555	0-45	7494	0-85	NE588	1-50
7405	0-18	7493	0-45	NE585	0-45	7495	0-85	NE567	1-50
7408	0-18	7494	0-85	NE588	1-50	7410	0-74	CA3045	0-85
7409	0-18	7495	0-85	NE567	1-50	7412	0-25	74100	1-07
7410	0-18	7496	0-82	CA3045	0-85	7413	0-40	74107	0-37
7412	0-25	74100	1-07	74107	0-37	7414	0-72	74121	0-47
7413	0-40	74107	0-37	74121	0-47	7417	0-43	74122	0-34
7414	0-72	74121	0-47	74122	0-34	7420	0-18	74123	0-65
7417	0-43	74122	0-34	74123	0-65	7425	0-30	74145	0-68
7420	0-18	74123	0-65	74145	0-68	7427	0-30	74154	1-30
7425	0-30	74145	0-68	74154	1-30	7430	0-18	4164	0-93
7427	0-30	74154	1-30	4164	0-93	7432	0-28	74185	0-93
7430	0-18	4164	0-93	74185	0-93	7437	0-28	74174	1-40
7432	0-28	74185	0-93	74174	1-40	7441	0-76	74175	0-94
7437	0-28	74174	1-40	74175	0-94	7442	0-76	74180	1-06
7441	0-76	74175	0-94	74180	1-06	7445	0-50	74186	1-25
7442	0-76	74180	1-06	74186	1-25	7447	0-81	74191	1-33
7445	0-50	74186	1-25	74191	1-33	7448	0-81	74192	1-20
7447	0-81	74191	1-33	74192	1-20	7470	0-32	74193	1-35
7448	0-81	74192	1-20	74193	1-35	7472	0-30	74194	1-20
7470	0-32	74193	1-35	74194	1-20	7473	0-30	74196	1-64
7472	0-30	74194	1-20	74196	1-64	7474	0-32	74197	1-64
7473	0-30	74196	1-64	74197	1-64	7475	0-47	Linear I.C.s	
7474	0-32	74197	1-64	74198	1-50	7476	0-36	301A	0-50
7475	0-47	74198	1-50	301A	0-50	7480	0-55	307	0-45
7476	0-36	301A	0-50	307	0-45				
7480	0-55	307	0-45						

FM TOUCH TUNER

P.W. MARCH '77
Semiconductor Pack £16-95
Resistor Pack (incl. VRS) £2-55
Capacitor Pack (exc. C1, C2, 43) £3-95
(Polyester and Electrolytic only)
ALL THREE PACKS £22-45
All prices include P. and P. and VAT

RETURN OF POST SERVICE

New Price List 20p



747	1-80	16 Pin	0-15	BZX88 Series	0-11
750	1-80	20 Pin	0-15	BZY88 Series	0-11
7805	0-45	750	1-80	OAS	0-50
7812	1-50	L.E.D.		OAS1	0-40
7815	1-50	2 Red	0-13	OAS5	0-12
7818	1-50	2 Green	0-20	OAS9	0-08
LM340-5	1-35	2 Clear	0-10	OA81	0-08
LM340-12	1-35			OA200	0-09
LM340-15	1-35			IN194	0-04*
MM5314	3-25			IN4001	0-04*
MM5316	3-85			IN4002	0-05*
AA-5-122A				IN4003	0-06*
AY-5-4007D	3-25			IN4004	0-07*
BY206	1-15			IN4005	0-08*
BY207	1-20			IN4006	0-09*
BY208	1-25			IN4007	0-10*
BY209	1-30			IN4146	0-04*
BY210	1-35				
BY211	1-40				
BY212	1-45				
BY213	1-50				
BY214	1-55				
BY215	1-60				
BY216	1-65				
BY217	1-70				
BY218	1-75				
BY219	1-80				
BY220	1-85				
BY221	1-90				
BY222	1-95				
BY223	2-00				
BY224	2-05				
BY225	2-10				
BY226	2-15				
BY227	2-20				
BY228	2-25				
BY229	2-30				
BY230	2-35				
BY231	2-40				
BY232	2-45				
BY233	2-50				
BY234	2-55				
BY235	2-60				
BY236	2-65				
BY237	2-70				
BY238	2-75				
BY239	2-80				
BY240	2-85				
BY241	2-90				
BY242	2-95				
BY243	3-00				
BY244	3-05				
BY245	3-10				
BY246	3-15				
BY247	3-20				
BY248	3-25				
BY249	3-30				
BY250	3-35				
BY251	3-40				
BY252	3-45				
BY253	3-50				
BY254	3-55				
BY255	3-60				
BY256	3-65				
BY257	3-70				
BY258	3-75				
BY259	3-80				
BY260	3-85				
BY261	3-90				
BY262	3-95				
BY263	4-00				
BY264	4-05				
BY265	4-10				
BY266	4-15				
BY267	4-20				
BY268	4-25				
BY269	4-30				
BY270	4-35				
BY271	4-40				
BY272	4-45				
BY273	4-50				
BY274	4-55				
BY275	4-60				
BY276	4-65				
BY277	4-70				
BY278	4-75				
BY279	4-80				
BY280	4-85				
BY281	4-90				
BY282	4-95				
BY283	5-00				
BY284	5-05				
BY285	5-10				
BY286	5-15				
BY287	5-20				
BY288	5-25				
BY289	5-30				
BY290	5-35				
BY291	5-40				
BY292	5-45				
BY293	5-50				
BY294	5-55				
BY295	5-60				
BY296	5-65				
BY297	5-70				
BY298	5-75				
BY299	5-80				
BY300	5-85				

Diodes cont'd

BYX38-900	18
BYX38-1200	0-21
BYX38-300	0-50
BYX38-600	0-55
BYX38-900	0-60
BXY38-1200	0-65
BZX61 Series	0-28
BZX83 Series	0-11
BZY88 Series	0-11
OAS	0-50
OA10	0-40
OA85	0-12
OA90	0-08
OA91	0-08
OA200	0-09
IN194	0-04*
IN4001	0-04*
IN4002	0-05*
IN4003	0-06*
IN4004	0-07*
IN4005	0-08*
IN4006	0-09*
IN4007	0-10*
IN4146	0-04*

SPECIAL OFFER SECTION

SG309K IAT03 5v. 0-95
TTL209 Red Led. 0-10
OC71 1-15

NPN TO-3 Power Transistors. Fully tested but unmarked. Similar to 2N3055 except: BVCEO = 50V, HFE (gain) = 20 + at VCE SAT < 1.3V at 3A 50 pps £1.00, 25 pcs £4.00, 50 pps £7.50, 100 pcs £13.00

OTL Branded Transistors. Medium Voltage, High Gain Type BSY65. Similar to

Transistors	BC148	0-09*	BD137	0-40*	BFX87	0-20	OC84	0-40	2N3702	0-10*	4024BE	0-86	
AC126	0-15	BC149	0-09*	BD138	0-48*	BFX88	0-20	OC139	1-30	2N3703	0-10*	4025BE	1-20
AC127	0-15	BC157	0-09*	BD139	0-58*	BFY11	1-10	OC140	1-30	2N3705	0-10*	4026BE	0-50
AC128	0-15	BC158	0-09*	BD144	2-20	BFY18	0-60	OC170	1-10	2N3705	0-10*	4027BE	0-62
AC128K	0-25	BC160	0-32	BD181	0-88	BFY40	0-50	TIP29A	0-44*	2N3706	0-10*	4028BE	0-91
AC141	0-22	BC161	0-38	BD18									

THE 'SEEKIT'⁶

METAL LOCATOR

W. OPEL

The circuit theory and the construction of the PCB and the search coil were given in Part 1 of this article. This month covers the Faraday shield information for the search head and the setting-up procedure.

COIL SHIELDING

To minimise the effects that wet grass or sand have on the search head the coil is almost entirely encased in a metal shield.

The simplest method of making a shield is to use strips of aluminium kitchen foil. The strips should be about 1 inch wide although the actual width isn't important, being a compromise between ease of winding a narrow strip and the fewer turns required with a wider one.

Starting at one end of the coil, commence winding the foil around the coil as if binding it. A leader of about 2 inches should be left at the start and each turn must overlap the previous one. The binding is continued to within about $\frac{1}{2}$ to 1 inch of the end of the coil. It is essential that the foil does not completely enclose the coil. The final turn is stuck in position and, to ensure that the foil doesn't move, a spiral of wire can be added followed by further adhesive tape.

Due to the difficulties of winding the aluminium strips smoothly the end product might appear a little lumpy but, since the coil won't be visible in the finished locator, it doesn't matter.

The foil leader at the beginning of the coil is connected to one wire lead-out and that connection becomes the earthy end of the assembly.

SEARCH HEAD ASSEMBLY

Before the completed coil is mounted into the head assembly the leads should be connected to the coax cable or, if changeable heads are to be used, to a coax socket. The connections must be bound with adhesive tape to ensure a sound mechanical assembly.

The coil, with its coax lead or socket, can be mounted in the moulded head shown in the photographs or into a home-made head. In either case it should be held in place initially by sticky tape. Trying to remove a defective coil after it has been fully encapsulated (or even firmly stuck) into the head can be frustrating and will almost certainly result in the destruction of the case.



PART 2

The moulded head has provision for the lead to come through the material just behind the handle fixing location. This position is also satisfactory for mounting the socket if used. When the heads are designed to be changeable this location is best. When only one head is to be used a neater result is obtained by feeding the coax lead up the handle stem and directly into the control case.

Because of the Faraday screen the head can be used under water provided the coil and the coax lead are made watertight. This can be achieved by encapsulating the head in epoxy resin (but not until testing has been completed). The depth of water which can be scanned is a function of the length of the handle and the lead since the control box isn't watertight.

The head assembly can now be connected to the control box and setting-up can commence.

SETTING-UP

The testing and setting of the unit is best carried out with the printed circuit board out of the case and the search coil held in position with adhesive tape. The main test instrument is a multimeter with a range for measuring low resistance.

The first check is on the search head assembly. For this the low ohms range is required. The resistance of 20-odd turns of 20SWG wire is not very much but it is detectable. Any reading on the meter will show that there is not a short circuit between the Faraday shield and the 'hot' end of the coil.

Having checked the coil assembly it should be plugged into the board connection. The current drawn by the circuit can now be measured. If the stabilising circuit is not used the current should be between 8mA and 12mA depending on the voltage used. If the stabiliser is used the current

drawn should be about 18mA. Significant differences indicate problems with the board construction. Generally if the current is too high look for solder bridges and if too low for unsoldered joints.

Assuming the current readings are close enough to be satisfactory there are various key voltages that should be checked. The first of these is between earth and the junction of R9, R10 and R13. This voltage depends on the setting of the core of the primary of L3 (the pink side) and it should be possible to adjust the core so that the voltage will swing above and below earth. Providing this is so, adjust the setting of the coil to give a voltage of about 0.4V positive.

The second is to ensure that the oscillator is working. Connect the meter between earth and the anode (ring end) of D3 and it should read about 1V negative. If it doesn't then check the oscillator carefully with particular care being given to the search coil connections. There is nothing to be gained by further measurements unless the oscillator is working correctly. If an oscilloscope is available the frequency of oscillation can be checked. It should be around 80kHz to 90kHz but is not critical.

Set the tuning control, VR1, to midway and the meter control, VR3, to minimum. Rotate the blue core in the detector (L3) until an audio note is heard. This will go from a very low frequency to a high howl. The meter should also indicate. The operational setting of the core will be that which gives half scale on the meter. At this setting the tone will automatically set itself to the optimum level.

If the meter reads but there is no audio tone the amplifier can be checked by applying the positive supply voltage to the junction of R22 and R23 through a 1MΩ resistor. The audio should be heard. If it is not then the components associated with the two sections of IC1 used for the amplifier must be re-examined.

10V STABILISER

The unit is designed to run on standard HP7 size batteries or on the alkaline alternatives. The alkaline types have a long life and a fairly level voltage characteristic so they provide stable operating conditions for the locator. The standard batteries, on the other hand, have a drooping voltage characteristic in addition to their shorter life. This drooping voltage causes drift in the unit and results in misleading readings or in needless corrections.

To overcome the falling voltage a stabiliser circuit, Fig.9, can be incorporated such that the electronics operate on 10V. This enables the batteries to be used down to an end voltage of about 11V and at that level they will be failing fast so the first sign of trouble will be the advice to change them.


The circuit will function equally as well on 10V as on 12V, once set, but if set for 12V it will not generally be possible to use the locator on 10V without re-adjusting L3.

The printed circuit board has provision for mounting the components for the stabiliser and the overlay pattern, (Fig.6) shows the wiring to the switches for either battery type.

To conform with the Wireless Telegraphy Act (1949) a licence is required to use the Seekit Metal Locator.

Under section 1(1) of the Act (Pipe Finder/Metal Locator Licence) frequencies between 0 and 150kHz can be used although preferably limited to 85kHz to 90kHz and 110kHz to 145kHz. The Seekit has a design frequency between 80kHz and 90kHz and has been approved by the Home Office.

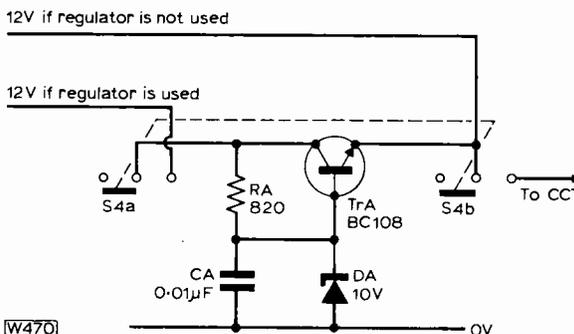A licence for five years costs £1.20 and an application form can be obtained from; The Home Office, Radio Regulatory Department, Waterloo Bridge House, Waterloo Road, London SE1. The completed form should make reference to the PW Seekit.



W470

Fig.1. The circuit of the stabiliser. Note that the drawing calls for a 10V zener and the parts for 9.1V. Either will do but 9.1V is preferred.


★ components list

Stabiliser	
RA	820Ω 10% ½W
CA	0.01µF
TrA	BC108
DA	9.1V, 400mA Zener diode

The photographs in the headings of part 1 and 2 show the unit mounted in the moulded case and search head, but, of course, the locator will work equally as well in any other suitable box and with a home-made search head. Several plastic boxes are available and size and style become a matter of personal choice provided the surface area and total volume are sufficient. Plastic conduit or waterpipe provide suitable handle material and can be bent or flattened after softening in boiling water or over a flame. If using a flame try a few practice runs first and remember to keep the pipe over the flame not in it. The search head is a little more difficult but the bottom of a plastic bucket or cake container would probably be sufficiently strong but remember to wind a coil to suit.

The moulded case and search coil housing are available from Ambit International and this company can supply a search coil and Faraday shield wound, tested and encapsulated (with light weight foam) into the search head moulding. The unit has a moulded-in coax lead of over 1 metre long included.


PW

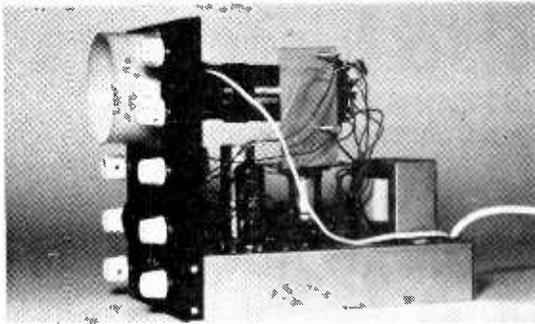

'There's only one way to master electronics... to see what is going on and learn by doing.'


1 Build an oscilloscope.

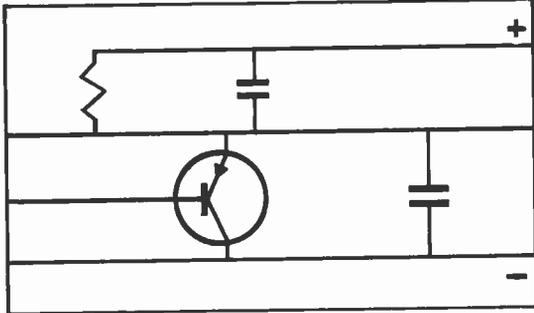As the first stage of your training, you actually build your own Cathode ray oscilloscope! This is no toy, but a test instrument that you will need not only for the course's practical experiments, but also later if you decide to develop your knowledge and enter the profession. It remains your property and represents a very large saving over buying a similar piece of essential equipment.



2 Read, draw and understand circuit diagrams.

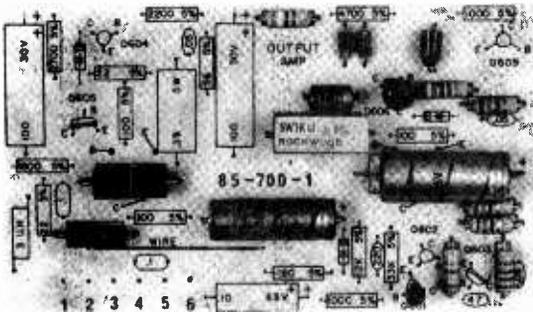In a short time you will be able to read and draw circuit diagrams, understand the very fundamentals of television, radio, computers and countless other electronic devices and their servicing procedures.



3 Carry out over 40 experiments on basic circuits.

We show you how to conduct experiments on a wide variety of different circuits and turn the information gained into a working knowledge of testing, servicing and maintaining all types of electronic equipment, radio, t.v. etc.

This new style course will enable anyone to have a real understanding of electronics by a modern, practical and visual method. No previous knowledge is required, no maths, and an absolute minimum of theory.

You learn the practical way in easy steps mastering all the essentials of your hobby or to further your career in electronics or as a self-employed electronics engineer.

All the training can be carried out in the comfort of your own home and at your own pace. A tutor is available to whom you can write, at any time, for advice or help during your work. A Certificate is given at the end of every course.



All students enrolling in our courses receive a free circuit board originating from a computer and containing many different components that can be used in experiments and provide an excellent example of current electronic practice.

To find out more about how to learn electronics in a new, exciting and absorbing way, just clip the coupon for a free colour brochure and full details of enrolment.

Write to:- British National Radio & Electronic School
P.O. Box 156, Jersey, Channel Islands.

NAME _____

ADDRESS _____

WB 6/7



Handy size Reels & Dispensers

OF THE WORLD'S FINEST CORED SOLDER TO DO A PROFESSIONAL JOB AT HOME

Ersin Multicore Solder contains 5 cores of non-corrosive flux that instantly cleans heavily oxidised surfaces and makes fast, reliable soldering easy. No extra flux is required.



SAVBIT handy solder dispenser

Contains 2.3 metres approx. of 1.22 mm Ersin Multicore Savbit Solder. Savbit increases life of copper bits by 10 times.
Size 5 49p

For soldering fine joints

Two more dispensers to simplify those smaller jobs. PC115 provides 6.4 metres approx. of 0.71 mm solder for fine wires, small components and printed circuits.
PC115 57p
Or size 19A for kit wiring or radio and TV repairs. 2.1 metres approx. of 1.22 mm solder.
Size 19A 53p



handy size reels of SAVBIT, 40/60, 60/40 & ALU-SOL solder alloys

These latest Multicore solder reels are ideal for the toolbox. Popular specifications cover all general and electrical applications, plus a major advance in soldering aluminium. Ask for a free copy of 'Hints on Soldering' containing clear instructions to make every job easy.

Ref.	Alloy	Diam. mm	Length metres approx.	Use	Price
Size 3	40/60 Tin/Lead	1.6	10.0	For economical general purpose repairs and electrical joints.	£1.79
Size 4	ALU-SOL	1.6	8.5	For aluminium repairs. Also solders aluminium to copper, brass etc.	£2.42
Size 10	60/40 Tin/Lead	0.7	39.6	For fine wires, small components and printed circuits.	£1.79
Size 12	SAVBIT	1.2	13.7	For radio, TV and similar work. Increases copper-bit life tenfold.	£1.79



BIB WIRE STRIPPER & CUTTER

Fitted with unique 8-gauge selector and handle locking device. Sprung for automatic opening. Strips flex and cable in seconds.

Pat. No.
1443913

Model 8B 86p

SOLDER- WICK



Absorbs solder instantly from tags, printed circuits etc. Only needs 40-50 Watt soldering iron. Quick and easy to use. Non-corrosive.

Size 18 97p

Sole U.K. Sales Concessionaires:

Bib Hi-Fi Accessories Limited,

Kelsey House, Wood Lane End, Hemel Hempstead, Herts. HP2 4RQ.

Prices shown are recommended retail, inc. V.A.T. From Electrical and Hardware Shops. In difficulty send direct, plus 20p P&P. Prices and specifications subject to change without notice.

If your cat is into the Average White Band



Isn't it about time you listened to them properly yourself?

The best way to achieve that is with Fidelity Fastenings—the newest, smartest way to place your speakers where they belong—on the wall. Almost undetectable when fitted they are easily adjustable and allow your speaker system to be placed in the best possible acoustical position, where they stay due to the rubber friction mounting. Fidelity Fastenings take a weight of up to 50 lb and

your speakers are easily lifted off for dusting or redecorating. Available from all good Audio and Hi-Fi shops and stores at £5.49. Look for the red and black box. If you have any difficulty in obtaining your Fidelity Fastenings, write for details of your nearest stockists to:

Fidelity fastenings

The Ridgeway, Iver, Buckinghamshire
Tel: (0753) 654222

CMOS WITH DISCOUNTS!

Any mix: Discount 10% 25+, 25% 100+, 33% 1000+

Quartz Crystals. 100kHz, 1MHz, 2.097152MHz, 3.2768MHz, 4.194304MHz, all same price £3.75. 32.768kHz, TO5 can £4.50. 50Hz Timebase kit for clocks etc., £5.91. 'DALO' Pen 75p. Liquid crystal display 4 x 0.5" digits, 40 pin, £13.95. Clock clip, 1½v battery operated, to suit our L.C.D. 40 pin DIL, 14440 £11.58. L.C.D. data free on request.


4000 0.20	4039 3.09	4081 0.24	14505 4.38	'E' LED Displays
4001 0.20	4040 1.19	4082 0.24	14506 0.57	DL-704E 0.3" 70p
4002 0.20	4041 0.93	4085 0.80	14507 0.60	DL-707E 0.3" 70p
4006 1.31	4042 0.93	4086 0.80	14508 3.08	DL-728E 2 x 0.5" 1.80
4007 0.20	4043 1.12	4089 1.74	14510 1.51	DL-727E 2 x 0.5" 1.80
4008 1.07	4044 1.04	4093 0.89	14511 1.74	DL-750E 0.6" 1.80
4009 0.60	4045 1.56	4094 2.08	14512 1.03	DL-747E 0.6" 1.50
4010 0.60	4046 1.48	4095 1.16	14514 3.47	Red LEDs
4011 0.20	4047 1.01	4096 1.16	14515 3.47	0.1" 15p
4012 0.20	4048 0.60	4097 4.15	14516 1.51	0.2" 15p
4013 0.60	4049 0.60	4098 1.22	14517 0.02	Clock Chips
4014 1.12	4050 0.60	4099 2.03	14518 1.39	AY-5-1224A 3.50
4015 1.12	4051 1.04	4101 1.76	14519 0.57	MK50253 5.50
4016 0.60	4052 1.04	4102 2.16	14520 1.39	Soldercon Pins
4017 1.12	4053 1.04	4103 2.16	14521 2.77	100 60p
4018 1.12	4054 1.29	4104 2.26	14522 2.15	1700 4.00
4019 0.60	4055 1.46	4107 0.66	14526 2.15	2500 8.75
4020 1.24	4056 1.46	4108 6.18	14527 1.39	DIL Sockets
4021 1.12	4057 29.81	4109 2.21	14528 1.22	100 15p
4022 1.07	4059 6.20	4101 4.30	14529 1.72	Timer I/C
4023 0.20	4060 1.24	4102 1.73	14530 0.95	Ne555 45p
4024 0.87	4061 25.60	4104 2.26	14531 1.74	Push Switches
4025 0.20	4062 10.10	4105 2.26	14532 1.39	Type SW9 15p
4026 1.92	4063 1.22	4700 1.75	14534 8.15	Op-Amps
4027 0.60	4068 0.89	7083 4.25	14536 4.00	CA3130
4028 1.00	4067 4.13	14160 1.18	14537 13.17	(COS/MOS) 1.00
4029 1.27	4068 0.24	14161 1.18	14539 1.24	CA3140
4030 0.60	4069 0.24	14162 1.18	14541 1.62	(BI/MOS) 95p
4031 2.46	4070 0.85	14163 1.18	14543 1.82	741 Minidlp 25p
4032 1.19	4071 0.24	14174 1.08	14549 4.10	
4033 1.55	4072 0.24	14175 1.04	14552 10.50	
4034 2.11	4073 0.24	14194 1.17	14553 4.66	
4035 1.31	4075 0.24	14490 6.51	14554 1.67	
4036 3.09	4076 1.71	14501 0.20	14555 1.01	
4037 1.06	4077 0.85	14502 1.38	14556 1.01	
4038 1.20	4078 0.24	14503 0.75	14557 4.65	

Terms: C.W.O. Add VAT to all prices at 8%. Post etc. U.K. 25p + 2p = 27p per order. All orders processed same day. Official Govt. 'Varsity, Poly etc. orders (written or telephoned) welcome.

GREENBANK ELECTRONICS (Dept. W6P)
94 New Chester Road, New Ferry, Wirral, Merseyside
L62 5AG
Tel: 051-645 3391

S-DeCnology

DAVID GIBSON

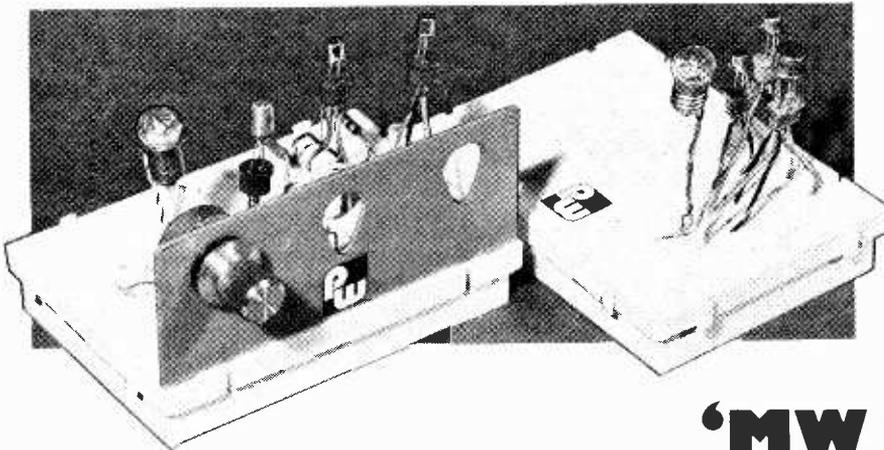

THIS MONTH

'MW Receiver'

you will need

R1	1M Ω	C3	170pF
R2	4.7k Ω	C4	100nF
R3	10k Ω	Tr1	BC108
R4	470k Ω	Tr2	AC126
VR1	50k Ω pot.	D1	OA90
C1	10pF	D2	OA90
C2	1nF	L1	ferrite slab 93 x 17 x 3mm

VC1/VC2 twin gang 500pF+500pF variable capacitor
EP1, Acos 'red spot' 1k Ω earpiece.
3V battery, S-DeC.28 SWG enamelled copper wire.
S-DeC leads with plugs. One Blob Board (if required).

THIS month's S-DeC project differs from all previous ones in this series. It is not an electronic device, but a simple two transistor receiver which gave surprisingly good results on test in Hertfordshire. Several foreign stations were received besides the more popular British medium wave transmissions. The circuitry employed attempts to extract all possible service from the first transistor Tr1, which is used as an RF amplifier and an AF amplifier. Regeneration is also used in the first stage which gives additional signal "boost" and sharpens the tuning giving improved station separation. It is ideal as a small portable receiver and it runs from only 3V.

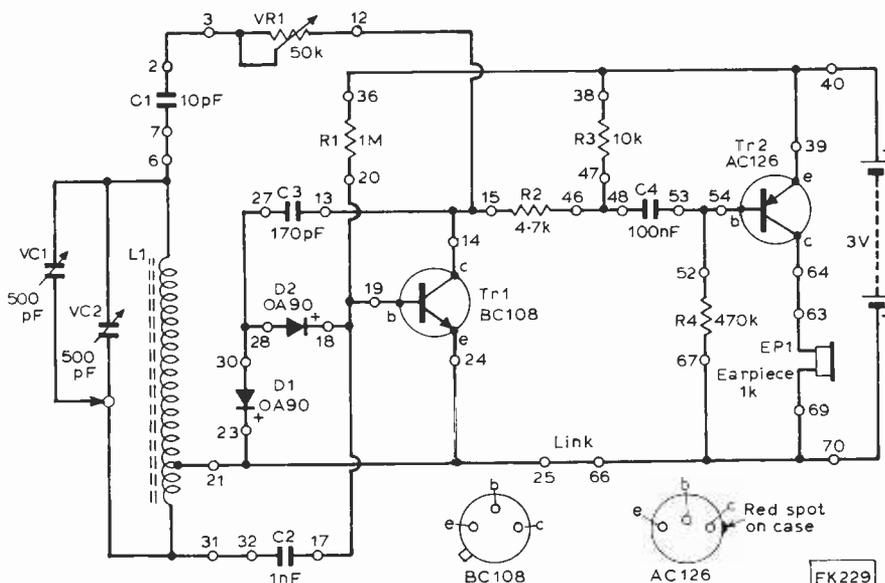


Fig. 1: Circuit diagram of this month's 2-transistor MW receiver. Note that the supply voltage is only 3V, and should not be exceeded, if optimum reception is to be achieved. Note:- An alternative aerial on a round ferrite rod is described in the text. The frame of the ganged capacitor goes to hole 6 of the S-DeC.

Lazy signals

Looking at the circuit diagram Fig. 1, the signal is first tuned by VC1/VC2 and L1, fed to the base of Tr1 and amplified at RF. This amplified signal now appears at the collector of the BC108 (Tr1) and from here it has a choice of paths. To turn sharp right into R2 means that it will immediately have to overcome $4.7k\Omega$ of resistance. It can, of course make a beeline for the $50k\Omega$ potentiometer, VR1. Its last choice is to tackle the $170pF$ capacitor, C3. Now most signals are lazy and will choose the line of least resistance. The "resistance" of the capacitor (C3) at $750kHz$ is less than 200Ω —a nice low value compared to $4.7k\Omega$ (R2) and $50k\Omega$ (VR1). In practical terms the signal, or various percentages of it, will travel all three paths but most will go through C3 where it encounters a pair of diodes. These rectify the RF signal and present a rough AF signal to the base of Tr1 via D2. Tr1 now amplifies the signal again, but this time at audio frequencies and again the amplified signal appears at the collector of Tr1. This time, things are a little different. The $170pF$ capacitor now has a "resistance" of many hundreds of thousands of ohms (to the AF signal) and so it is persuaded (or rather the bulk of it is) to develop across R2 which forms an audio load for the collector of Tr1. From here, the audio signal is fed via C4 to the base of Tr2 and amplified to feed the earpiece which forms its collector load.

Signal regeneration

So we've now persuaded two transistors to do the work of three transistors; but there's another way we can get even better performance—regeneration or reaction. Let's retrace our steps to the collector of Tr1 and let us arrive just as the amplified RF signal gets there. You remember there were three paths. Let's look at the one to the potentiometer VR1. A tiny

(very tiny) part of the signal will manage to get across VR1 and get to the capacitor C1. This $10pF$ component offers a very low "resistance" to RF (but a very high "resistance" to AF) and so this tiny part of the original RF signal goes across C1 and on through the coil L1 and back again to the base of Tr1. Here, it arrives in such a way as to reinforce the original signal which caused it, thus giving that signal an extra boost. This feedback of signal is called reaction or regeneration. Since the potentiometer is a variable resistor, we can control the amount of regeneration—too much will cause the circuit to oscillate and "howl"; too little will give only a very small (barely worthwhile) amount of boost.

Another advantage of regeneration, is that it improves the apparent "Q" of the tuned circuit—this is the thing which decides how sharply the circuit will tune in stations. One which tunes very broadly will tend to allow one signal to interfere with another. But with a higher "Q", the tuning becomes very much sharper and so station separation improves. With this receiver, station separation is excellent and sensitivity is also extremely high despite the low voltage used.

Aerial details

Construction on the S-DeC is very simple. Just plug the components into the S-DeC holes marked on the circuit diagram Fig. 1. You can also use the full size S-DeC diagram of Fig. 2. The coil was wound with 28swg enam. copper wire on a piece of flat ferrite slab which measured $93mm$ long by $17mm$ wide by $3mm$ thick. The start of the winding may be secured to the rod by a piece of plastic insulation tape (or even sellotape will do). Wind on five turns and form a big loop of wire which you should then twist until you are left with a very small loop at the end of a $25mm$ piece of twisted wire. Carry on winding another 55 turns and secure the end of the wire. Make sure to clean all the enamel off the ends

continued on page 130

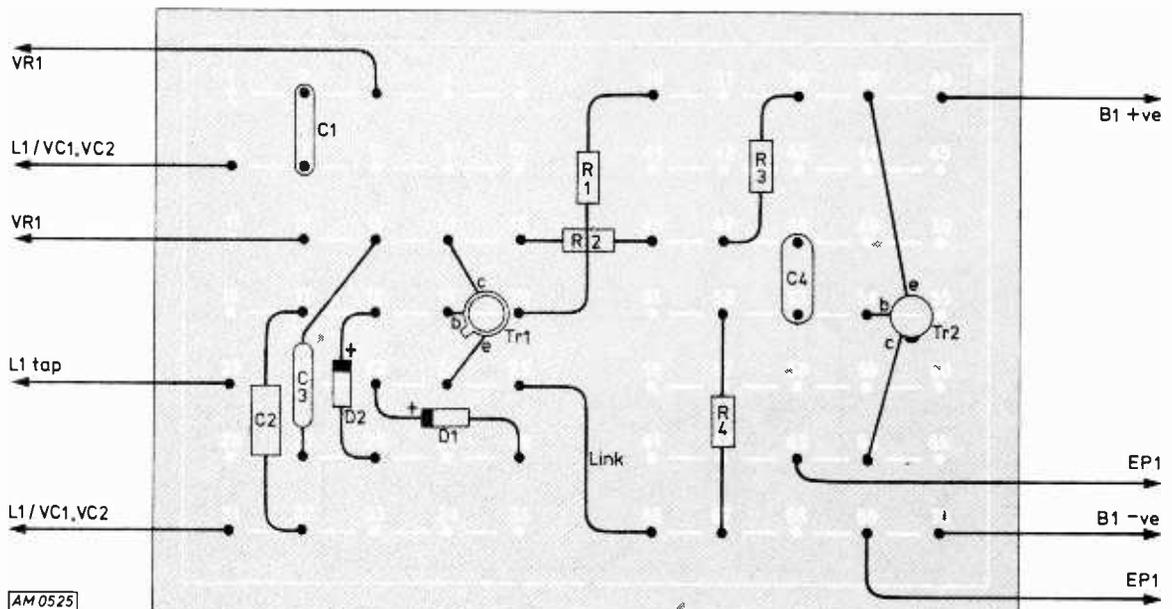



Fig. 2: Full size drawing of the S-DeC, giving component location and hole numbers. The ferrite aerial, tuning capacitor, battery, VR1 and the earphone are all connected via leads, and not on the S-DeC itself.



IN NEXT MONTH'S
PRACTICAL
WIRELESS

24-HOUR
DIGITAL
CLOCK

with **PRECISION**
TIME
SWITCH

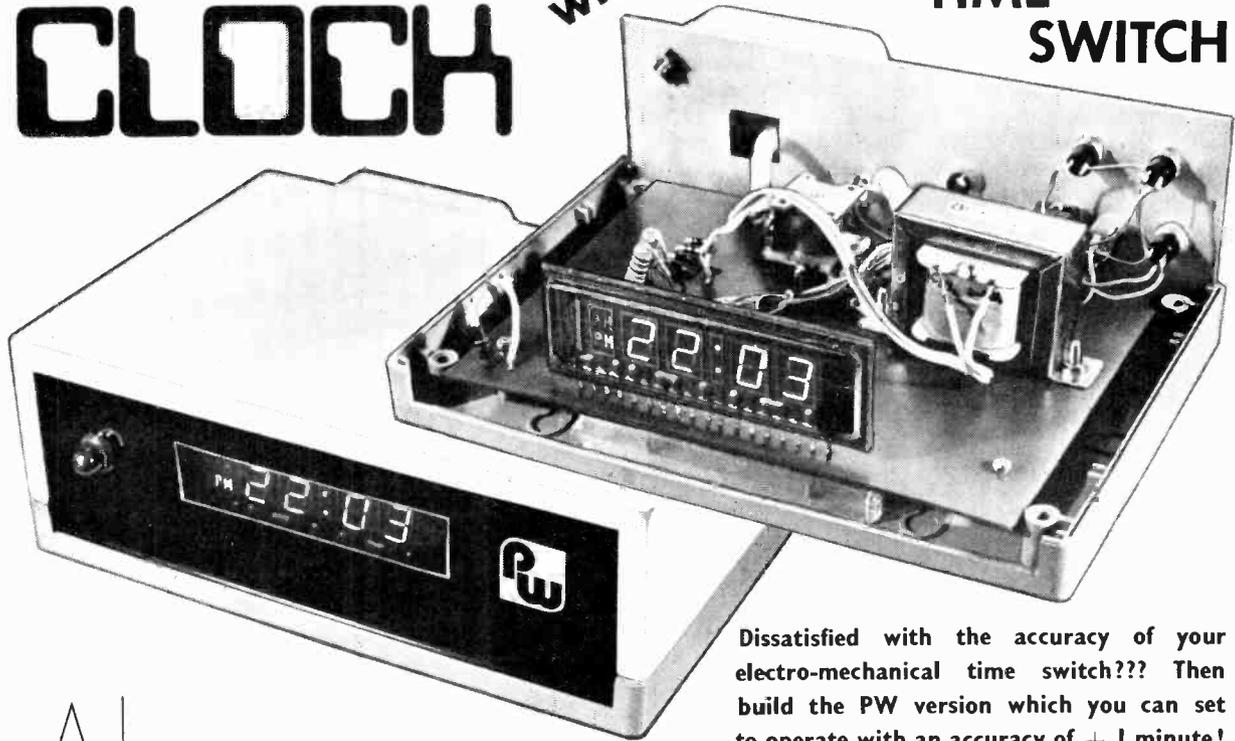

Dissatisfied with the accuracy of your electro-mechanical time switch??? Then build the PW version which you can set to operate with an accuracy of ± 1 minute! An all-electric Digital Clock PLUS a Precise Timer for an external circuit.

Also ~

Get the sporting events on our
Radio 2 TUNER

&
A 20W IC Audio
AMPLIFIER

ON SALE
3rd JUNE



TELE

plus:

ON-SCREEN SCORING & SOUND EFFECTS

TENNIS FOOTBALL SQUASH PELOTA

THE General Instruments AY-3-8500 television games integrated circuit allows a complex multigame unit to be built using very few additional components. The single device provides for 4 ball games and 2 shooting games. This article will describe a unit for the 4 ball games.

THE AY-3-8500

Before describing the construction of the unit it will be useful to give a description of the special IC. The device is in a standard 28 pin dual-in-line package with pins 1, 14, 15 and 28 not being used. Pins 2 and 4 are ground and plus 8V respectively.

★ components list

Resistors

R1	47k Ω
R2	1k Ω
R3	10k Ω
R4	2.2k Ω
R5	220 Ω
R6	220 Ω
R7	47k Ω
R8	1k Ω
R9	47k Ω
R10	47k Ω
R11	47k Ω
R12	47k Ω
R13	33k Ω
R14	47k Ω
R15	1k Ω
R16	6.8k Ω
R17	4.7k Ω
R18	1k Ω
R19	100 Ω
R20	100 Ω
VR1	10k Ω standard horizontal preset
VR2	10k Ω standard horizontal preset
VR3	1k Ω standard horizontal preset
VR4	100k Ω linear
VR5	100k Ω linear

All fixed resistors are $\frac{1}{4}$ W, 5%

Capacitors

C1	2200 μ F, 25V
C2	0.22 μ F
C3	0.22 μ F
C4	1000pF polystyrene
C5	1000pF polystyrene
C6	100pF polystyrene

Miscellaneous

T1, mains transformer, 2 secondaries each 0-12V at 250mA, fixing centres 53.5mm. FS1, fuse holder, chassis mounting, 20mm and 200mA fuse. PCB from Readers PCB Service. Speaker, miniature, 40 Ω . Former 4mm with dust core. Wire 40SWG enamel covered, 1metre long. Wire 22SWG, tinned copper, 250mm long. Case sloping top, 216mm x 130mm x 47mm (front) x 79mm (back), Watford code NJSF2 Doram code 509-608. Boxes, 2 off, 85mm x 56mm x 37mm, Watford code NJHC1 Doram code 509-636. (Note, these cases provide an attractive cover but any case of similar size can be used). SKT1, coax socket. Coax cable and 2 coax plugs. 2 grommets. Mains cable. Board pins. DIL socket (see text). Heat sink for IC2

C7	100pF polystyrene
C8	0.22 μ F
C9	0.22 μ F
C10	10 μ F, 10V
C11	1000pF disc ceramic
C12	10pF plate ceramic
C13	3.3pF plate ceramic
C14	22pF plate ceramic
C15	5.6pF plate ceramic
C16	1000pF disc ceramic, 250V
C17	1000pF disc ceramic, 250V
C18	47 μ F, 10V tantalum

Switches

S1	1 pole 6 way rotary.
S2	Single pole, biased off, miniature push
S3	S.P.S.T. miniature toggle.
S4	S.P.S.T. miniature toggle
S5	S.P.S.T. miniature toggle
S6	S.P.S.T. miniature toggle
S7	D.P.S.T. miniature toggle, mains rated

Semiconductors

Tr1	BC108
Tr2	BC108
Tr3	BC108
Tr4	BC108
Tr5	BSX20
D1	1N4001
D2	1N4001
D3	1N914
D4	1N914
IC1	AY-3-8500 G.I.
IC2	MC7808 or 78L82AWC

D.S. COUTTS

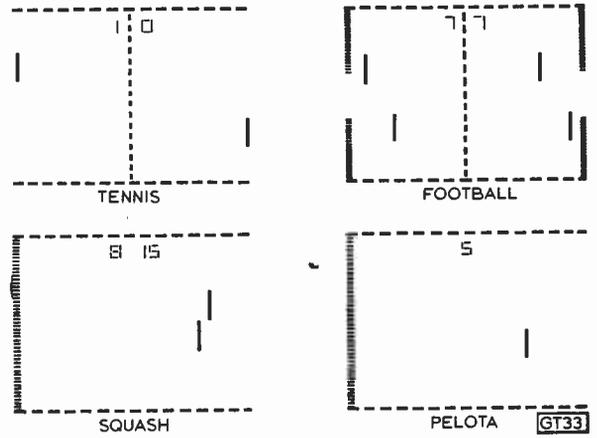
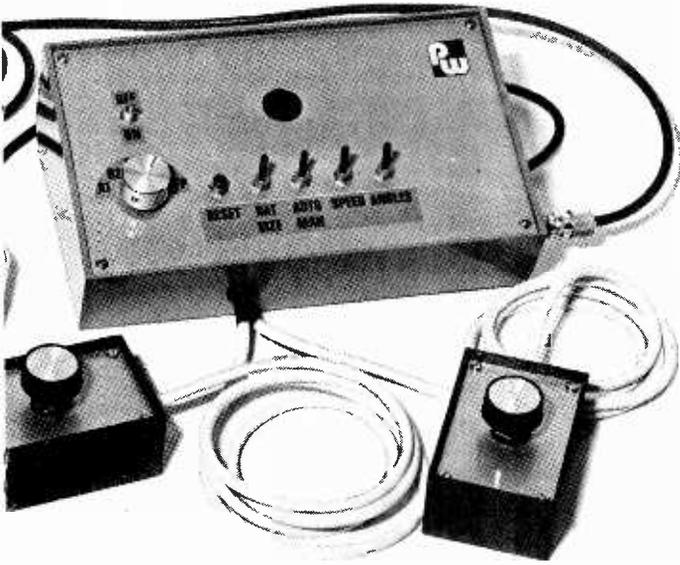


Fig.1. The outlines of the four games that can be played using this unit. The sizes of the individual dots may not be as shown due to tube distortion and sharpness of focus.

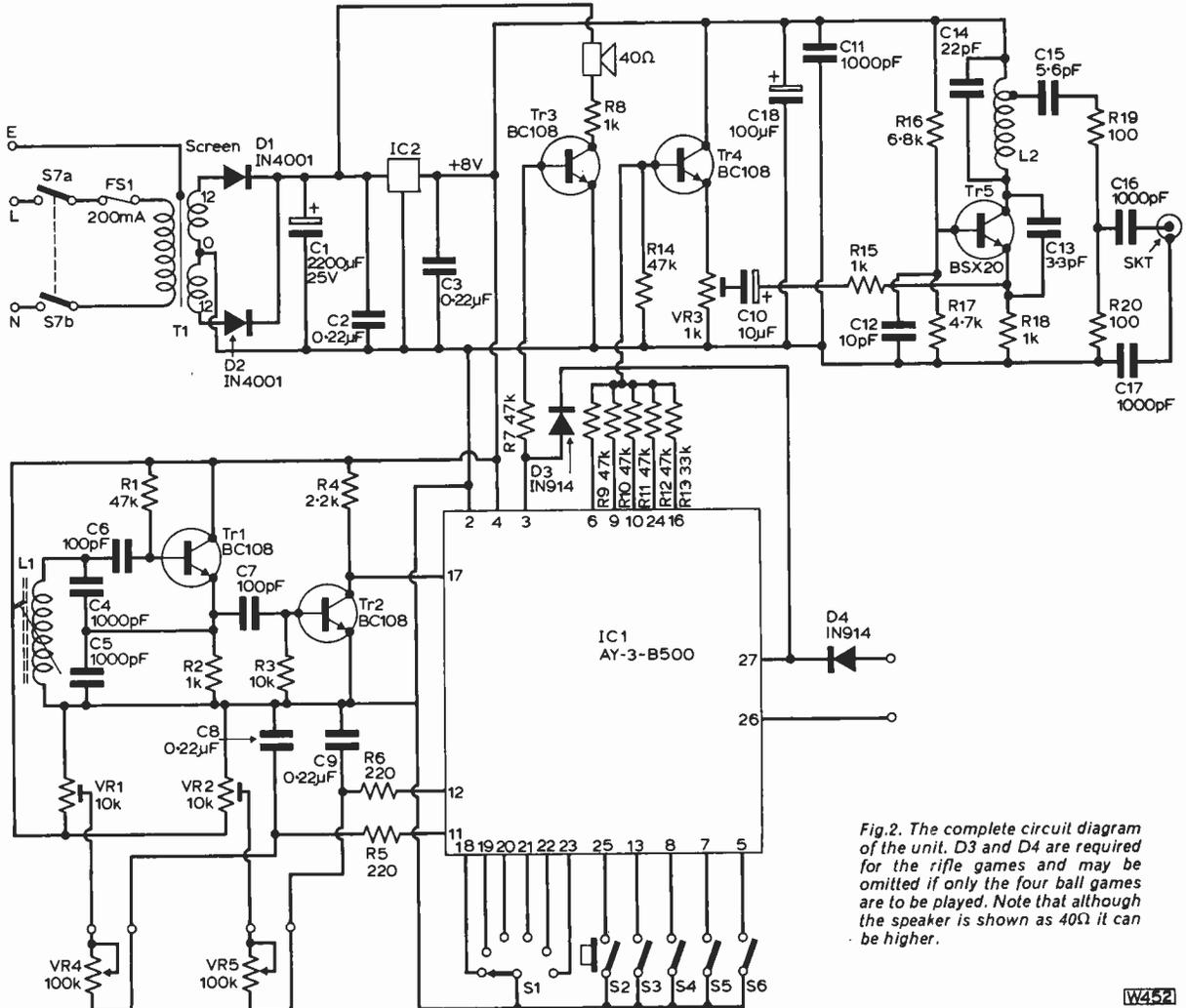


Fig.2. The complete circuit diagram of the unit. D3 and D4 are required for the rifle games and may be omitted if only the four ball games are to be played. Note that although the speaker is shown as 40Ω it can be higher.

Pin 3 gives an output of 500Hz, 1kHz or 2kHz which corresponds to the ball hitting the line, the ball hitting the bat and a scoring signal.

The ball will bounce off the correct bat at an angle determined by the condition of pin 5. When it is left open circuit the angle is constant over the whole bat except that the reflection is 'up' in the upper section of the bat and 'down' in the lower section. When pin 5 is connected to ground the bat is divided into four vertical sections. The angles in the centre two sections are as before but the outer two reflections are at steeper angles.

Pin 7 controls the ball speed. If left open circuit the ball travels slowly (suitable for beginners) if connected to ground the ball speeds up.

Automatic or manual service is selected by pin 8. If the ball leaves the court when pin 8 is open circuit it will remain off until the pin is grounded momentarily. If pin 8 is left switched to ground the ball will serve automatically, travelling in the direction that it left the ground (ie. if the right hand player scores then the ball will be served from the right hand side).

Pin 11 is the right player input and an R/C network on this pin controls the vertical position of the right bat or, in football, both right bats. Pin 12 provides similar control for the left hand player. The size of the bats is controlled by pin 13. When switched to ground the bat size is half that resulting from leaving it open circuit.

Pin 17 is the clock input and a 2MHz signal is required.

The choice of games is made by pins 18 to 23, depending which of them is grounded. The display for each of the four ball games is given in Fig. 1.

Pin 2 provides a reset facility. Switching it to ground resets the score to zero and when the ground connection is removed the ball will be served from the left. When either player scores 15 the game is finished. Both bats become transparent to the ball and the score remains static. The game is restarted by pushing and releasing the reset button.

Pins 6, 9, 10, 16 and 24 are outputs corresponding to ball, right bat, left bat, sync and field/score outputs. Their functions are explained later.

The two shooting games utilise pins 26 and 27.

CIRCUIT DESCRIPTION

The complete circuit diagram of the unit is given as Fig. 2.

The secondary of the mains transformer is given as 12-0-12V. In fact, the transformer specified has two secondaries, each of 12V. These need to be wired in series (ie, the OV of the first to the 12V of the second) and the ground connected to the junction. D1 and D2 provide full wave rectification, smoothing is by C1 and the resultant DC is regulated by IC2. High frequency decoupling is provided by C2 and C3 on the input and output of the regulator. C11 and C18 give additional decoupling to the 8V rail.

Tr1 is a 2MHz oscillator, its output being buffered by Tr2 before being fed to IC1.

VR1, VR4, R5 and C8 are the timing components for the right hand player. VR4 is the hand control and changes the charging current of C8 thus moving the vertical position of the bat. VR1 sets the voltage towards which C8 charges and alters the sweep of

the bat. R5 limits the current during the discharge period at frame flyback. The corresponding controls for the left hand player are VR2, VR5, R6 and C9.

Tr3 drives the speaker, with R8 limiting the volume. If greater volume is required the value of R8 can be reduced but, on the prototypes, it was sufficient for most domestic uses.

The video and sync outputs are summed by R9 to R13 and drive Tr4, an emitter follower. VR3 in the emitter allows the modulation level of Tr5 to be adjusted.

Tr5 is VHF oscillator operating at about 170MHz with harmonics extending into the UHF band. The output is divided by R19 and R20 and the unit is DC isolated from the display monitor by C16 and C17.

Switches S1 to S6 control the games and functions already described, (see Fig. 7 for details also).

CONSTRUCTION

Before commencing construction of the electronics it is necessary to drill the mounting holes in the case. The board can be used as a template to ensure they are in the right position. The board will ultimately sit with the modulator section at the front right and with its right hand edge about 10mm from the right side of the case. This allows the leads of C16 and C17 to be kept short. The mounting holes for the board are 6 BA.

Having drilled the base, the remaining holes can be marked out as Fig. 3. These holes will be sized to suit the grommets and the coax socket. It is also advisable to drill a series of 5mm holes in the base and in the back to assist ventilation.

Mark the top panel as Fig. 4 and drill the holes to suit the components used. A suitable hole size for the speaker is 20mm. Label the panel and mount the switches. The speaker is glued to the panel using a rapid-cure epoxy but first glue a piece of speaker fret over the hole.

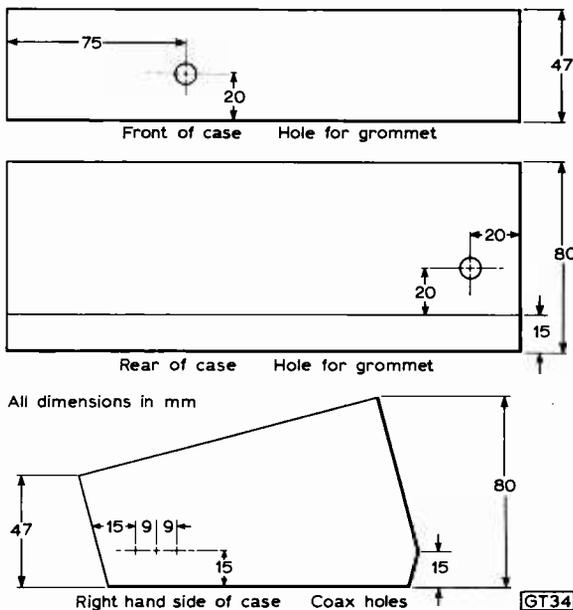


Fig. 3. Suitable drilling hole locations and sizes are shown for the box specified. The single hole in the front of the case is for both the bat control leads. It is easier to identify the bats if two holes are made, one at each end of the front.

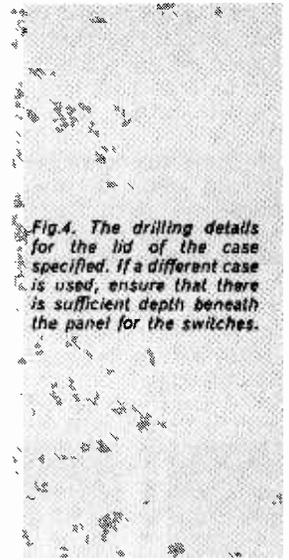
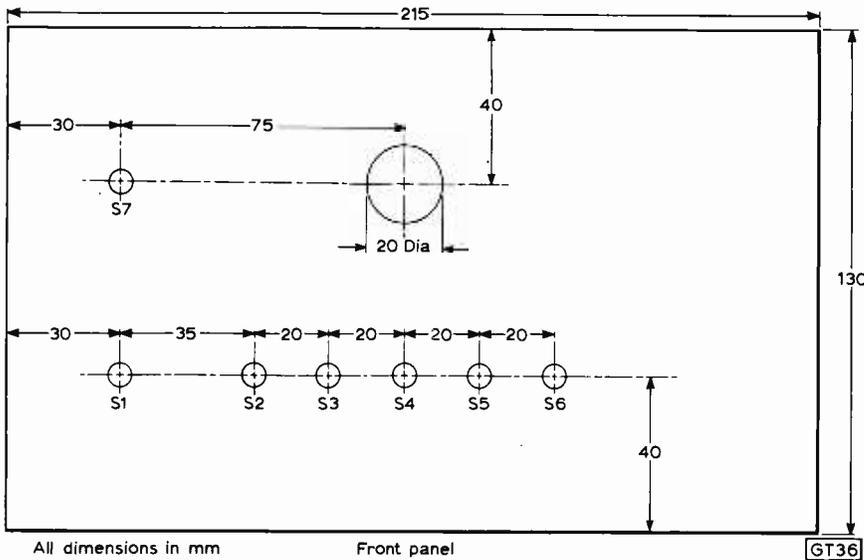


Fig.4. The drilling details for the lid of the case specified. If a different case is used, ensure that there is sufficient depth beneath the panel for the switches.

Most of the components are mounted on a single sided PCB. Fig. 5. shows the wiring pattern and Fig. 6 the component locations. The former for L1 is stuck in position, again using rapid-cure epoxy, and when the adhesive has set, 50 turns of 40 SWG are wound onto the former. After soldering the ends as shown in Fig. 6, the screening can is fitted. It is better to wind the coil after the former is fixed to the board because although it is difficult to wind it is even more difficult to hold the winding in place whilst the epoxy sets.

The remaining components, except for the coil L2 and IC1 are mounted (not forgetting the wire link). L2 is 3 complete turns of 22 SWG tinned copper wire wound on a former so that the diameter of the coil is 6mm (1/4 inch) after the former is removed. A short length of wire is soldered to the coil 3/4 of a turn from one end. The coil is mounted in position and the screen is soldered to the four pins at the

corners of the oscillator section. Leave the top of the screen off. It may be necessary to adjust the frequency. Details of the screen are given as Fig. 7.

It is strongly recommended that a socket or Solder-con pins are used for IC1. This device is of MOS construction and is liable to damage if incorrectly

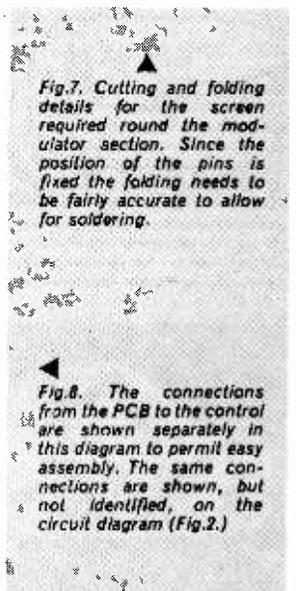
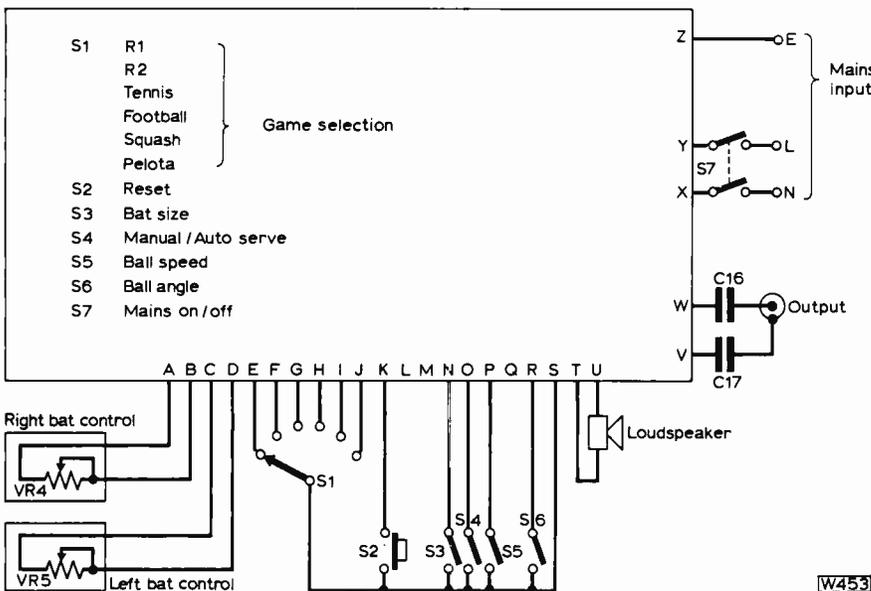
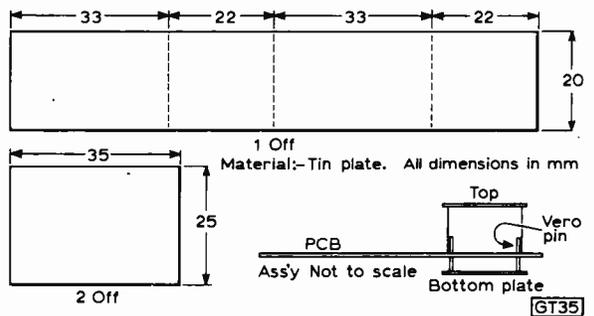


Fig.7. Cutting and folding details for the screen required round the modulator section. Since the position of the pins is fixed the folding needs to be fairly accurate to allow for soldering.

Fig.8. The connections from the PCB to the control are shown separately in this diagram to permit easy assembly. The same connections are shown, but not identified, on the circuit diagram (Fig.2.)

handled. If for any reason it is necessary to solder the IC directly into the board the soldering iron must have an earthed tip and a heat shunt should be used on the pin being soldered. The socket need only be a 24 lead type since the end pins on each side are unused. If a socket is used do not insert IC1 yet.

Recheck the board for solder bridges and for good soldered joints and then mount it in the box. The dimensions given for the box specified allow for 6mm (1/4 inch) spacers beneath the board.

Connect the off-board components to the pins as shown in Fig. 8. The leads for the bat controls should be about 1 metre long and be twin cable. The variable resistors are mounted in small boxes.

Some pins on the board are not used in this 4 game unit although S1 is shown wired for all 6 games. Pins E and F can be left unwired.

A suitable length of coaxial cable needs to be terminated at both ends and a mains cable, preferably terminated with a 13A ring main plug, completes the wiring.

Now remove the IC from its protective foam and insert it into the holder.

SETTING UP

Set the core of L1 flush with the top of the former and space L2 to approximately 7.5mm long. Set VR1, VR2 and VR3 to mid position, select football on the games unit and select auto serve. Switch the unit on, push and release the reset button S2. Tones should be heard at regular intervals from the unit as the ball hits the game boundaries etc.

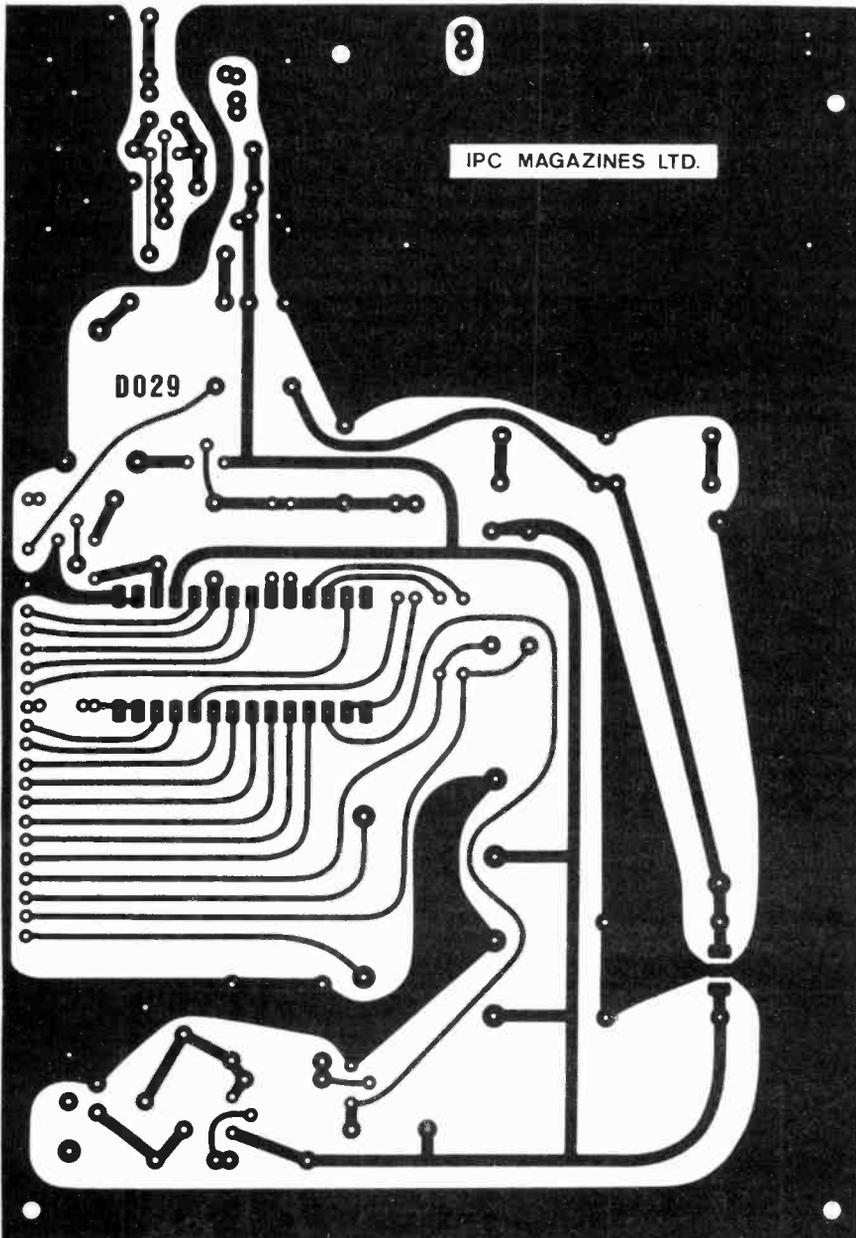


Fig.5. The wiring pattern of the printed circuit board, shown full size. For those intending to make their own boards we would stress the need for great care in laying out the IC pads and the modulator section. The earth section could be increased to conserve the etchant.

Fig.6. The component layout and orientation for the PCB. Although the outputs are not identified they conform to those shown in Fig.8. Note the tight layout of the modulator section and hence the need for careful cutting and folding of the screen.


If all is well, switch the monitor on, allow it to warm up, select a spare U.H.F. channel and plug the games unit into the aerial socket. Carefully tune the viewer until the signal from the games unit appears on the screen, it may only consist of white streaks covering the screen. Slowly screw the dust core into L1 until the streaks on the screen resolve themselves into the outline of the football pitch as shown in Fig. 1. It may be necessary to re-adjust the viewer, tuning again for a good signal. Several signals will be picked up throughout the U.H.F. band, choose the best one.

When the reset button is pushed and released the football field should appear locked solid on the


screen, if it does not adjust L1 slightly one way or the other until it locks into sync each time it is reset. When the field is stable on the screen, VR3 may be adjusted anticlockwise to increase the contrast and the brightness control on the viewer may be turned down slightly to reduce the background. (If VR3 is turned too far anticlockwise sync will be lost.)

If the signal from the unit is close to a TV station L2 may be altered in length to move the games frequency up or down the band a little, then the screening cover can be fitted.

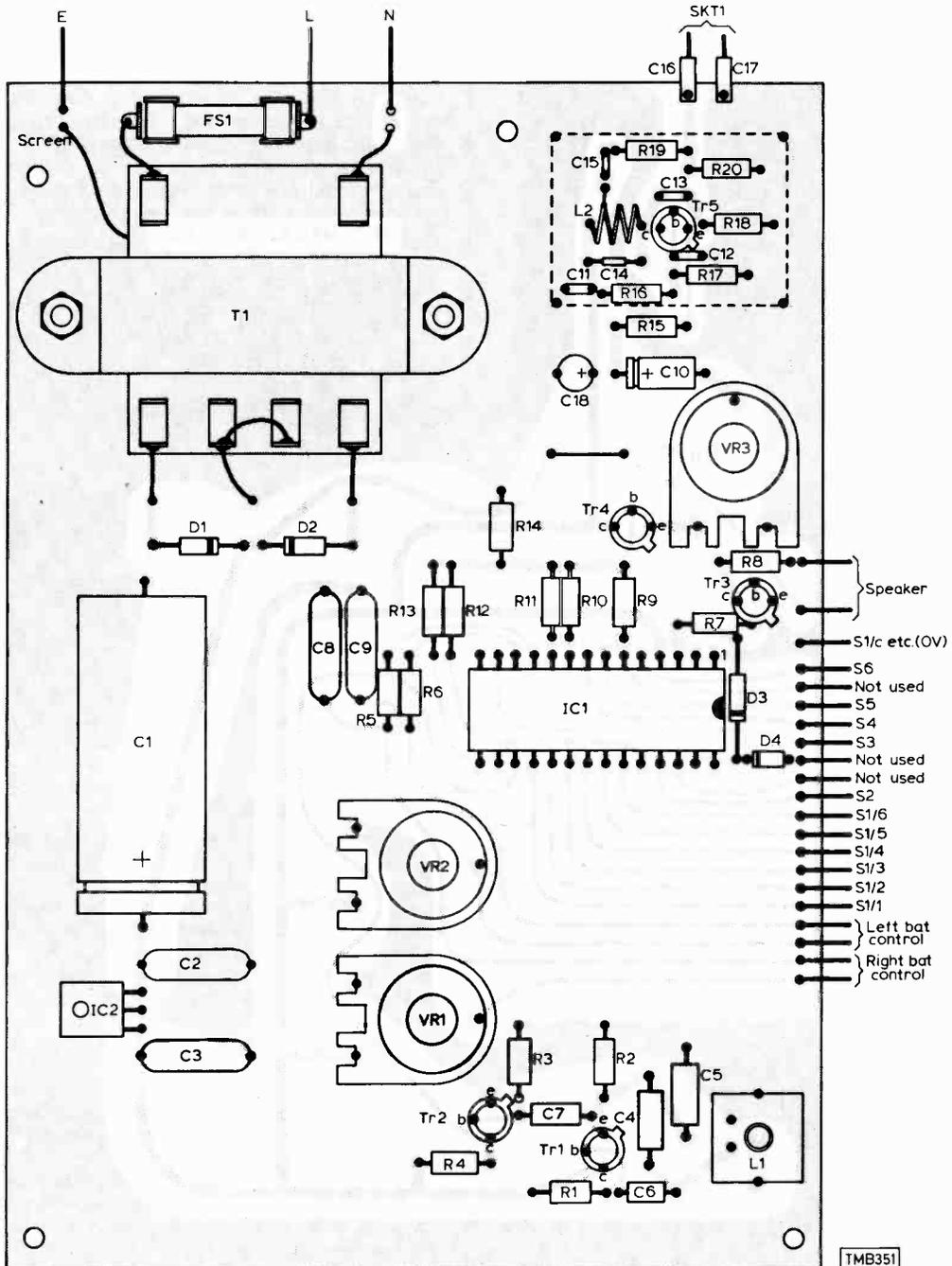Check that the bats sweep across the screen. VR1 and VR2 may be turned anticlockwise to reduce the



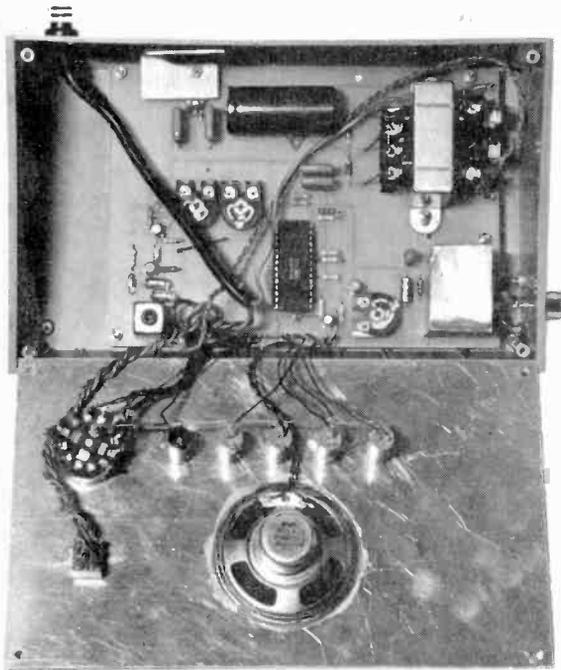sweep of the bats but if they are turned too far the bats will disappear since the ramp will not reach the I.C. trigger level. Check the other games and the various switch functions and if it all checks out, screw the lid on the case.



A general photograph of the unit with the lid removed. The retainer for the mains cable has been removed to allow the lid to be inverted. It should be positioned to avoid too much cable inside the box when re-assembled. The short leads of the capacitors coupling the board to the output socket can be identified. These two capacitors prevent any possibility of mains being fed to the unit from the television chassis if the set has its mains reversed.

FAULT FINDING

If the unit does not work, check all wiring very carefully. Check the +8 Volts supply to the I.C., modulator and the clock generator. If an oscilloscope is available, check that the oscillator is working and producing sufficient drive for the buffer, Tr2, and is approximately 2MHz.


If the I.C. has +8 Volts and a good clock signal, check the sync output. This should consist of negative going pulses $4\mu\text{s}$ wide, at $64\mu\text{s}$ intervals with an approx. $300\mu\text{s}$ frame pulse every 20 mS. If this is present, check the field and score output on pin 24, this should be a positive-going pattern repeating every 20 mS. If this is present, check that both these signals appear at the wiper of VR3. If all is well up to this point and the unit is still not working, check the modulator construction very carefully. As it is difficult to check if it is working it is possibly easiest to substitute a new transistor for Tr5.

Watford Electronics have offered to keep their special reduced price for the AY-3-8500 open to readers of Practical Wireless until the end of June 1977.

S-DeCnology—continued from page 122.

of the wire, especially the tapping loop and tin these connections before soldering on some wired S-DeC plugs. If desired, the wire from the coil itself may be plugged into the S-DeC but you will still need to use some form of single core wire from the tapping point to the S-DeC because the twisted wire, being double thickness, will not easily plug into the S-DeC and may even damage it if forced. A second ferrite aerial/coil was wound on a 125mm. length of ferrite rod, 9mm in diameter and also gave good results.

The tuning capacitor used in the prototype was a twin gang $500\text{pF} + 500\text{pF}$. There is no reason why a single capacitor of either 500pF or 350pF should not be used, but this will make some difference to the actual tuning scale covered by the receiver. The twin gang does give a useful opportunity for experiment. For example, with both sections connected in parallel—as shown in the circuit diagram of Fig. 1, one has a $1,000\text{pF}$ (or 1nF) variable tuning capacitor. By “unlinking” the two sections of VC1/VC2 to leave only one of them in circuit, one has a 500pF tuning capacitor. Again, connecting the two sections in series gives a 250pF tuning capacitor.

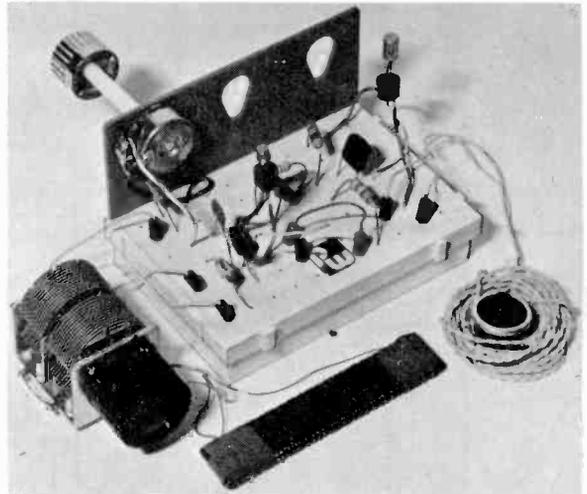

Rear view photograph showing the actual receiver, comprising S-DeC front mounted potentiometer, and external components.

Modification ideas

Experimentally minded constructors may care to try altering the coil. For example, using only 24 turns tapped at 2 turns gave all sorts of ‘funny’ foreign stations. It may even be possible to obtain good results high up in the short wave bands.

This little receiver runs from just 3V. This is the optimum voltage. If you use a higher voltage the performance will be degraded. The current drawn by the prototype (using 3V) was 1.5mA which suggests that batteries should last for a very long time indeed. It may also be possible to run the receiver from two, small rechargeable batteries which could be kept ‘topped up’ from solar cells using sunlight. Perhaps the set may be happy to work directly from solar cells?

Various component changes and modifications were tried but it's left to the constructor to experiment for himself, with different component values, to obtain the best possible results.

PW

PCB SERVICE FOR READERS

AM 03

All boards, except SRBP, are glassfibre, drilled and roller-tinned

To:- READERS PCB SERVICES LTD, PO BOX 11, WORKSOP, NOTTS

Please supply PCB/s as indicated by tick/s in box/es

Issue	Project	Ref	Price	P/P
Sep 75	Electronic Clock (set of three)	DN0795/6/7	2.40+15	<input type="checkbox"/>
Dec 75	Sound-To-Light Display	DN0798	1.15+12	<input type="checkbox"/>
Dec 75	Disco System, Amp. (2 required)	each AM0421	4.40+22	<input type="checkbox"/>
Dec 75	Disco System, Light Modulator	AM0423	3.50+22	<input type="checkbox"/>
Jan 76	Music Box	SRBP DN1/JM	2.25+18	<input type="checkbox"/>
		glassfibre DN1/JM	3.00+18	<input type="checkbox"/>
Mar 76	CMOS Crystal Calibrator	AM0438	1.19+12	<input type="checkbox"/>
Apr 76	Wobulator	AM0443	1.08+12	<input type="checkbox"/>
Apr 76	Auto. Slide Synchroniser	AM0441	2.33+15	<input type="checkbox"/>
June 76	Dig. Freq. Meter (set of 5)	A015 and 4x A004	3.17+15	<input type="checkbox"/>
July 76	Transistor Tester	A002	3.08+18	<input type="checkbox"/>
July 76	Disco Preamplifier	A003	0.65+12	<input type="checkbox"/>
Aug 76	Cassette Player Power Supply	A001	0.65+12	<input type="checkbox"/>
Sep 76	Capacitance Meter	A009	2.59+14	<input type="checkbox"/>
Oct 76	Digital Car Clock (set)	A001/2/3	2.58+12	<input type="checkbox"/>
Oct 76	Interwipe	DN8JM	0.80+12	<input type="checkbox"/>
Oct 76	Video-Writer (set)	D002/3/4/6 A007	21.44+50	<input type="checkbox"/>
Oct 76	Hazard Flasher	D005	0.76+12	<input type="checkbox"/>
Nov 76	Low Level Battery Indicator	A016	0.40+12	<input type="checkbox"/>
Nov 76	Electronic Thermostat	A017	1.30+12	<input type="checkbox"/>
Nov 76	Cirtest Probe	A018	0.48+12	<input type="checkbox"/>
Nov 76	Burglar Alarm	A019	0.50+12	<input type="checkbox"/>
Dec 76	Chromachase	A021	5.70+22	<input type="checkbox"/>
Jan 77	Oscilloscope Calibrator	A023	1.25+12	<input type="checkbox"/>
Jan 77	Icelert	A020	1.45+12	<input type="checkbox"/>
Jan 77	Polyphon, motor and main boards	A025/4	7.90+20	<input type="checkbox"/>
	Polyphon, tune disc, blank, SRBP	A008*	0.90+15	<input type="checkbox"/>
Feb 77	Transistor Checker	A026	1.18+12	<input type="checkbox"/>
Mar 77	FM Stereo Touch Tuner	D023/4/5	7.50+20	<input type="checkbox"/>
Apr 77	Tug 'o' War (set)	A029/030	2.88+12	<input type="checkbox"/>
Apr 77	Gas/Smoke Sensor Alarm	A028	0.65+12	<input type="checkbox"/>
May 77	2-Way Intercam	D019	1.28+12	<input type="checkbox"/>
May 77	Protected Battery Charger	A027	2.38+12	<input type="checkbox"/>
May 77	Seekit Metal Locator	A031	3.38+12	<input type="checkbox"/>
June 77	Reverberation Amplifier	A032	2.38+12	<input type="checkbox"/>
June 77	Versatile AF Generator	A033	2.38+12	<input type="checkbox"/>
June 77	Tele-Games	D029	3.22+18	<input type="checkbox"/>

Post and packing is for one board or set of boards. Prices include VAT
Remittances with overseas orders must be sufficient to cover despatch
by sea or air mail as required.

I enclose Postal Order/Cheque

ACCESS welcome.

No.....

Send card number only.



for £..... made payable to READERS PCB SERVICES LTD.

NAME.....

ADDRESS.....

Post Code.....

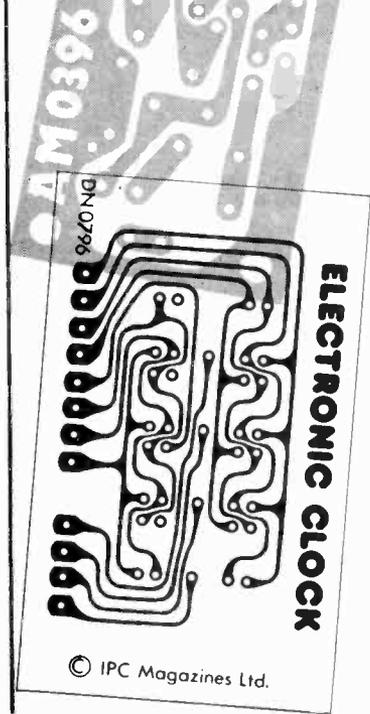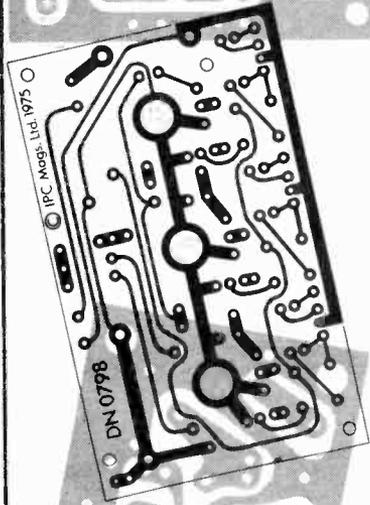Any correspondence concerning this service must be addressed to READERS
PCB SERVICES and not to the Editorial offices.



PRODUCTION LINES

bill tull


Vice time

One of the most frustrating facts of life, is that we are born with only two hands. Ever tried filing or drilling, or some kinds of soldering when you really NEED that third hand? What we all need of course, is a vice (the sort you clamp to the bench I mean!), and H. R. Holmes Ltd., are now

marketing an adjustable vice which is claimed to combine 8 tools in 1.

Called the Versa-Vice, the unit comprises an adjustable hand vice, G clamp, anvil plate and scribing pin, width and depth gauges, table vice and marking out table. Price is £4.80 plus VAT.

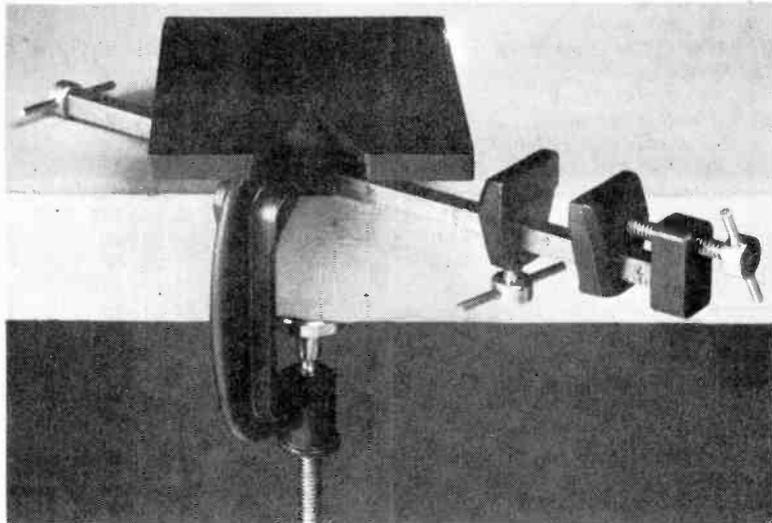*H. R. Holmes (Diecasting) & Co Ltd.,
Haldane, Halesfield 8, Telford, Salop,
TF7 4EW.*




Probe for faults

One of the most useful pieces of equipment in the Service Technicians arsenal when tracing faults in Radio, TV and HiFi, is the signal injector. These take many forms, and the one produced by Carlo Gavazzi Ltd., the Pantec Usijet, is made in the form of a pen for clipping into the pocket.

The circuit consists of two signal generators—one operating at AF and the other at RF. The waveform derived from a blocking-oscillator type circuit produces a signal with a wide range of harmonic frequencies up to 500MHz. The fundamental frequencies

Quite regular

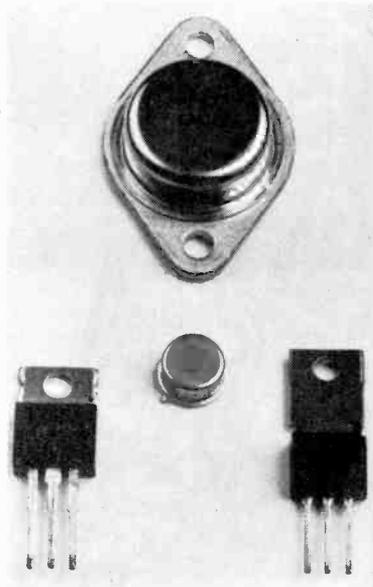A three terminal, positive voltage regulator, capable of supplying in excess of 1.5A and adjustable over an output range of 1.2V to 37V has recently been announced by Jermyn



Distributors. Requiring only 2 external resistors to set the output voltage, the LM317 has typical line and load regulation figures of 0.01% and 0.1% respectively.

Other parameters include current limiter, thermal overload, and safe area protection. Also, as this regulator sees only the input to output differential voltage, supplies of several hundred volts can be regulated providing the maximum differential of 40V is not exceeded.

A choice of TO3, TO5, TO202 and TO220 packages is available, providing a total temperature range of -55°C to +125°C.

*Jermyn Distributors, Sevenoaks,
Kent. Tel: 0732 51174.*

are 1kHz and 500kHz, with an output voltage of 20V pk. to pk. Current consumption is about 25mA from a 1.5V self-contained cell. Price is £7.50 plus VAT.

The Usijet, together with all Carlo Gavazzi products are now being distributed by Precision Instrument Labs., Instrument House, 212 Ilderton Road, London, SE15. Tel: 01-639 0155.

Tape 'Plus' tuner

Unit audio, music centres, what ever you care to call it, can be obtained almost everywhere in almost every type of combination. I say almost, because there is one combination that is comparatively rare—that is cassette recorder/amplifier/speakers and/or tuner. To fill this gap, Plustronics have launched their new combination, called the Plustron CTA 200. This unit comprises an AM/FM stereo receiver with integral cassette recorder, supplied com-

plete with matching speakers. Radio coverage on MW is 540—1600kHz, SW 6—16MHz, LW 150—350kHz and VHF 88—108MHz, while the cassette tape system boasts a wow and flutter of less than 0.35% and S/N ratio of 40dB. Power output into an 8ohm load at 1kHz is 8W.


Imported, distributed and fully guaranteed by Plustronics Ltd., the Plustron CTA 200 has, what the firm call, a 'Guide Price' of £123.49 complete.

Plustronics Ltd., Hempstalls Lane, Newcastle, Staffs, ST5 0SW. Tel: 0782-615131.

Robust amps

'Indestructable' is the term given to two new amplifier modules recently made available in the UK by Chékits Ltd.

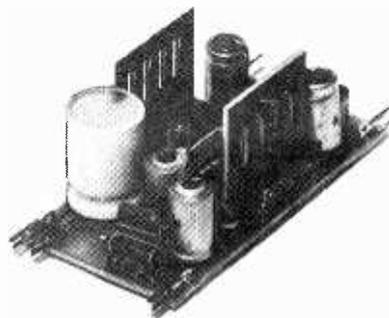
The kits are designed for the professional and constructor markets, and are based on two SGS amplifier



IC's. Although both are of similar component construction, they differ in power output and sensitivity ratings. The 75-X, which has a maximum rating of 10W into 4 ohms at 20V utilizes the TCA940 chip, while the 75-B, its less powerful brother, uses the TCA810AS and has a maximum output of 7W into 4 ohms at 16V. Both are equipped with thermal limiting circuitry, while the 75-X is short circuit protected. The quoted sensitivity figures range from 6.5mV input for 50mW output, to 90mV input for 9W output for the 75-X. For the 75-B, 6mV input gives 50mW output, and 80mV input gives 6W output. All figures quoted are into a 4 ohms load.

Both modules are constructed on 1.6mm Epoxy Glass Fibre board and measure 86 x 43 x 30mm (total dimensions with components). Price for the 75-X and 75-B is £4.50 and £3.59 inclusive respectively.

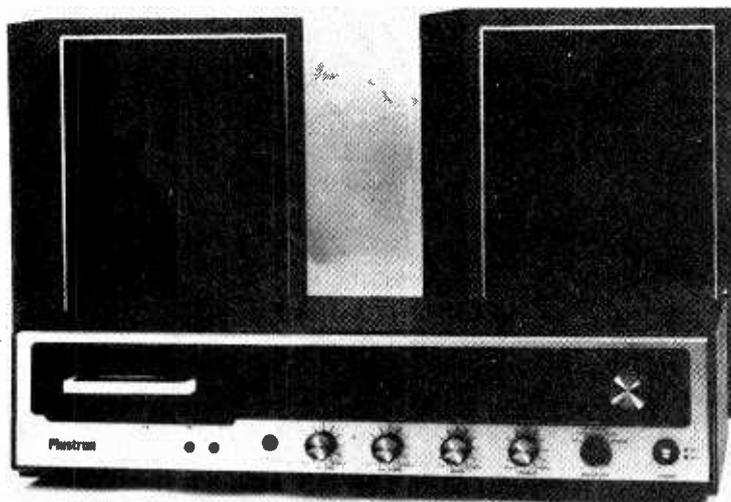Further information from *Chékits Ltd., 56 Fortis Green Road, London, N10 3HN.*



Blob board


For the past few months, PW has been publishing articles based on the S-DeC. Now, we have mentioned in these articles, that if the builder wishes to keep the project, but use the S-DeC for another project, then he should transfer the components to a Blob Board. Blob Board, do I hear you say? Well as can be seen from the photograph it is extremely simple to use—the component layout is drawn on the Board with a felt tip pen. The components are then laid over their respective drawings, and soldered in position.

All Blob Boards are roller tinned to facilitate easy and reliable soldering, while components can be re-used and re-soldered making circuit prototyping and modifications both fast and easy.

There are twelve different Blob Boards available in a variety of

patterns which, between them, are claimed to accommodate all components from discrete to IC's. The smallest board measures 3.6 x 2.4in and costs 20p.

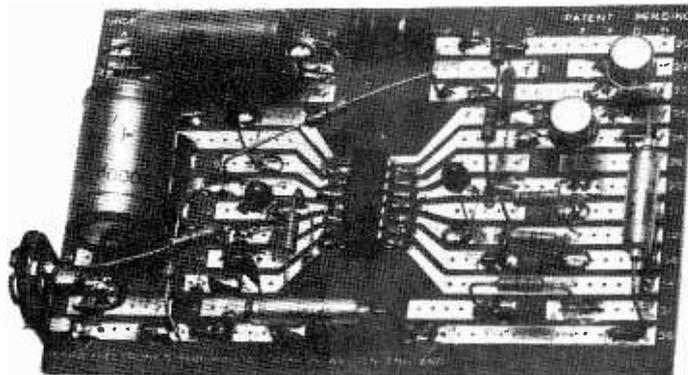P B Electronics (Scotland) Ltd., 57 High Street, Saffron Walden, Essex. Tel: 0799 22876.



CW filter unit

A. LANGTON



THIS simple bandpass filter was built to ease the reception of morse code in the presence of interference from other stations. It simulates a parallel resonant circuit with a Q of 25, the overall gain being fixed at unity. In Fig. 1 capacitor values are given for 800Hz and 1200Hz. In the prototype, soldered links select either frequency. If the Q is increased much above 25, the filter will "ring" and the keying will sound soft, making reception more difficult as the characters will begin to merge together.

Headphones of 600Ω impedance or greater can be used; blocking capacitors are not necessary at input or output as the IC2 earthing return ensures that the mean DC voltage at the input and output of the operational amplifiers is zero. The headphone socket into which this device is plugged should be isolated from high voltages by a capacitor or transformer within the receiver.

★ components list

Resistors (all 2% 1/4W)

R1 330kΩ

R2 560Ω

R3 150kΩ

Capacitors

C1 0.01 and 0.015μF } see text

C2 0.02 and 0.033μF

Semiconductors

IC1, 2 741 op amp.

Miscellaneous


S1* 3 pole 2 way wafer switch. Plug and socket to suit headphones. B1, 2 4.5 to 12V batteries. Case measuring about 17 x 9 x 7 cm.

Fig.1: Circuit diagram of filter unit.

Two sets of capacitor values are given corresponding to passband centre frequencies of 800 or 1200Hz. In the prototype either set of capacitors could be chosen by wiring in the appropriate pair with a soldered wire bridge on the circuit veroboard. Naturally, this arrangement may be replaced by a switched capacitor bank mounted on the instrument front panel. To work out other passband frequencies:

$$F \text{ varies as } \frac{1}{C}$$

Use the given circuit values to work out other values of F and C. For instance, doubling the capacitor values halves the passband frequency.

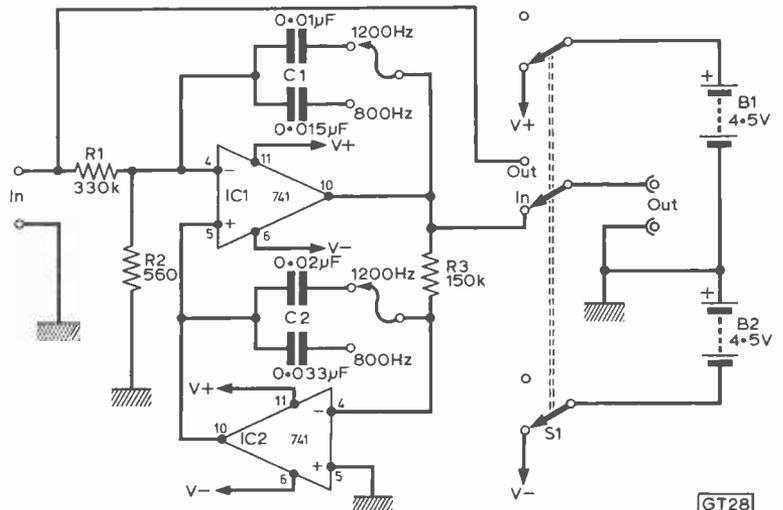

GT28

Construction

Layout is not critical, and as so few components are used, it can easily be built on a scrap of Veroboard. The Veroboard layout diagram Fig. 2 shows the positions for fitting either 14 pin or 8 pin DIL 741 IC devices. It also includes both frequency options; the desired frequency is selected by strapping two pairs of pins.

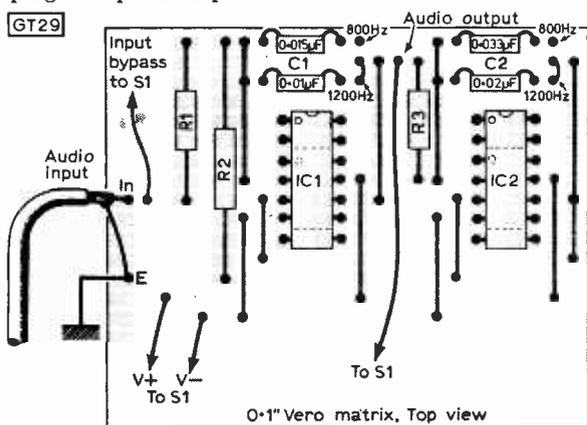


Fig. 2: Suggested veroboard layout. The dotted outline shown on IC1 and 2 indicates the position of an 8 pin mini DIP 741 in lieu of the 14 pin device shown. No other changes are necessary.


A piece of Perspex with two 6BA tapped holes is used to secure the board to the case, the Perspex being glued along one edge of the circuit board with epoxy adhesive. There are, of course, many ways the board could be secured; it is up to the individual constructor to choose the most convenient way. The battery holder is another home-made item. It might be more convenient to use 9V batteries with press stud connectors and hold them in place with a simple clip.

The case, measuring 17 x 9.5 x 7 cm, is larger than necessary, but allows plenty of room for experiments or additions to the basic design. All parts except the circuit board are permanently installed within the case, which can form a small test rig for filter ex-

periments: board replacement requires the minimum of unsoldering.

The total current consumption is about 6mA, and it will work on $\pm 4.5V$ to $\pm 12V$. The filter can be plugged into the receiver as required; a front panel switch connects the headphones either to the input or output of the filter, disconnecting the power when not required.

Other circuit values

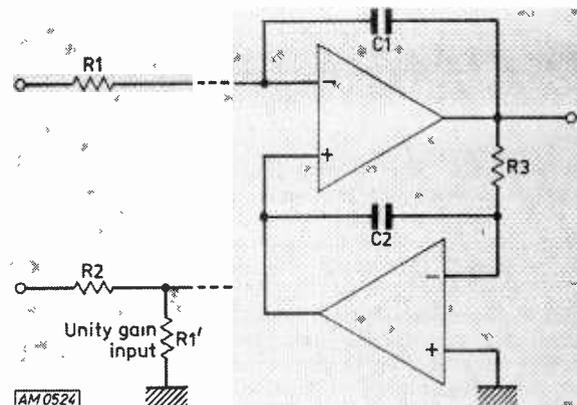

Use your pocket calculator to work out the circuit values for your own application:

F_o = passband centre frequency

R = $M\Omega$

C = μF

$$F_o = \frac{1}{2\pi \sqrt{(R_1 \cdot R_3 \cdot C_1 \cdot C_2)}}$$

To work out the 'Q' of the filter:


$$Q = \sqrt{\left(\frac{R_3 \cdot C_2}{R_1 \cdot C_1}\right)}$$

To reduce gain to unity.

$$R_2 = R_1 \cdot Q^2$$

$$\text{and } R_1' = \frac{R_1 \cdot Q^2}{Q^2 - 1}$$

PW

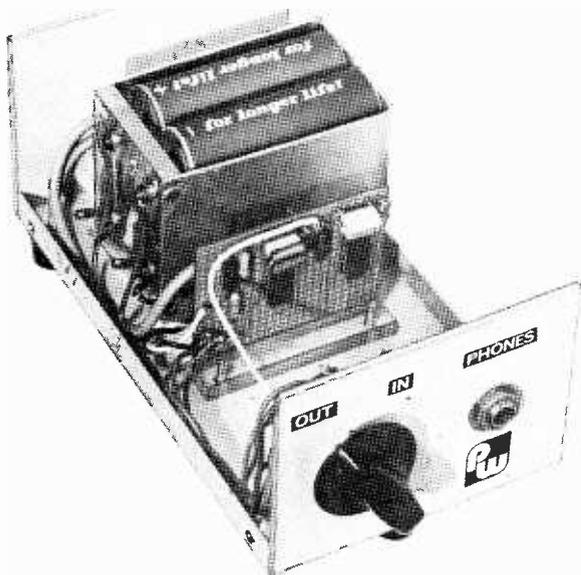

INDEXES FOR PW

Readers are asked to note that further supplies of the index for Vol. 51 (May 75-April 76) are now available. See contents page for details on obtaining indexes.

The index for Vol. 52 (May 76-April 77) was presented free in the May 77 PW and this issue can be obtained from the same address.

**PLEASE MENTION
PRACTICAL WIRELESS
WHEN REPLYING TO
ADVERTISEMENTS**

extender for PW Transistor Tester

IAN HICKMAN

WHEN the P.W. Transistor Tester was developed, the aim was to produce an instrument of simple design, yet which would enable a wide range of semiconductor devices to be tested. The result was that whilst both P and N channel J.FETs and MOSFETs (both depletion and enhancement types) could be checked for drain saturation current I_{DSS} and pinch off voltage V_p , for depletion mode FETs intermediate values of drain current versus gate voltage could not be checked. More importantly, no provision was made for dual-gate FETs.


★ components list

Resistors

R1 22Ω 5% 1W
R2 1MΩ 5% 1W
R3 39kΩ 5% 1W
VR1 500Ω
VR2 500kΩ

Miscellaneous

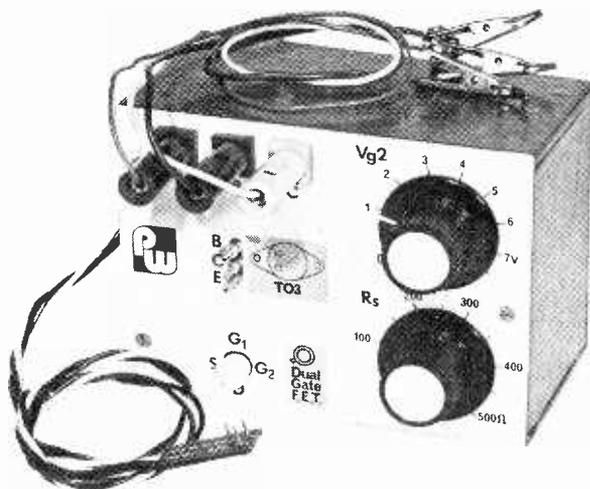Piece stripboard, 0.1" matrix, 5" × 3½". 3 off 4mm sockets and plugs to suit (preferably different colours). 2 knobs to suit variable resistors. A 4 pin socket for TO5 transistors. 3 split pins to fit TO3 output pins. Piece of springy material for case connection of TO3 can. 2 ferrite beads. Wood and hardboard for case. Cardboard for top.



This Extender Unit covers these additional uses and also incorporates a socket which accepts TO3 transistors, thus facilitating the measurement or matching of power transistors. Finally, sockets for three flying leads enable connections to be made to transistors of any case style whatever.

CIRCUIT

Fig. 1 shows the circuit diagram. The socket for TO3 transistors and the banana sockets for flying leads are self-explanatory. Via the lead labelled


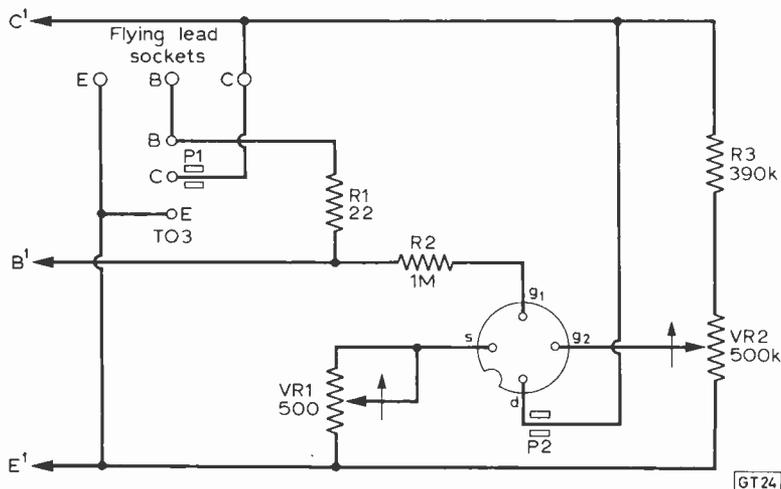


Fig. 1.
The circuit diagram for the extender. Note that power is drawn from the original test unit.

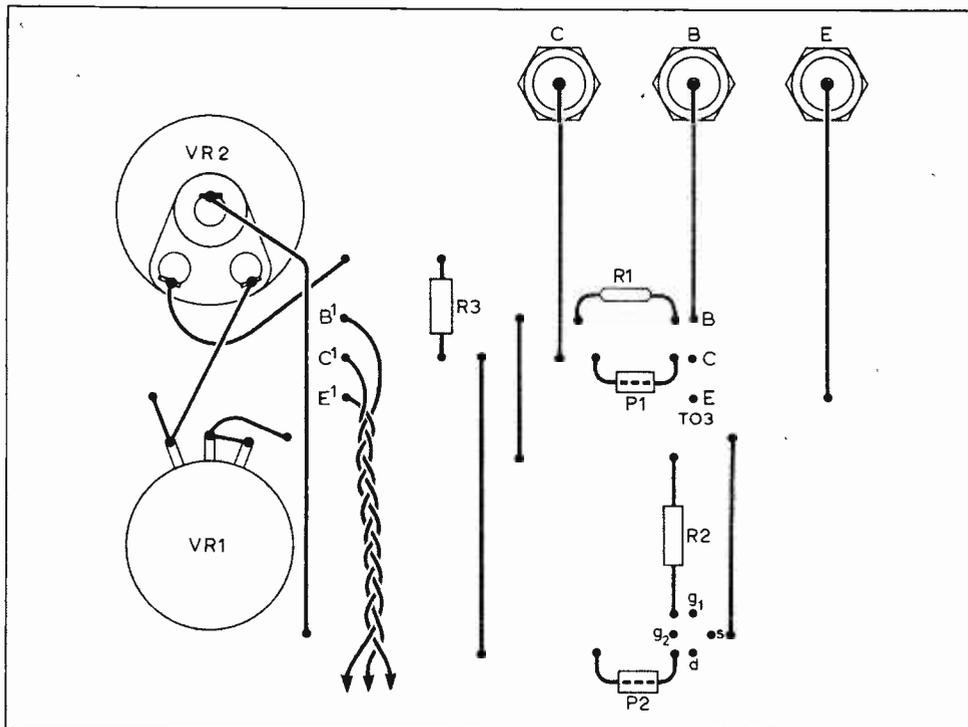

GT27

Fig. 2. The board cutting details and the components as mounted in the prototype. For a smooth top the components are soldered to the foil side and the leads do not pass through the holes.

C'B'E', which plugs into the connector panel of the P.W. Transistor Tester, they connect to transistors which cannot conveniently be plugged directly into the Transistor Tester. The four lead transistor socket is arranged to accept most TO72 type dual gate FETs, e.g. the economically priced General Instrument range including the MEM 614, as well as the popular and long-established RCA 40819 range and the earlier 40600 range (which has no gate protection diodes).

The voltage on gate 1 is controlled by the V_K control on the Transistor Tester, whilst the V_{g2} control (VR2 of the Extender Unit) controls the voltage on gate 2.

Together with source resistance control R_s (VR1 of the Extender Unit) a wide range of operating conditions and measurements can be set up and made.


Anti-parasitic ferrite beads P₁ and P₂ are included in the collector and drain connections, together with a 22 ohm stopper in the base lead of the transistor socket and 1M Ω in the gate 1 lead of the dual gate FET socket, to ensure stability.

The V_{g2} control circuit draws less than 15 μ A from the collector supply and its effect on it can therefore be ignored.

CONSTRUCTION

The unit was made up on a piece of 0.1 inch pitch strip board, 5in x 3.34in, see Fig. 2. The TO3 socket used three slotted female pins taken from an old multiway connector, the tails of which were passed through the Vero board and soldered to the copperstrips. The outer two were at 0.4 inch spacing, but as the pins of a TO3 transistor are slightly further apart than this, the holes were eased with a small file. A TO3 transistor was plugged into the pins to

A photograph of the prototype board.

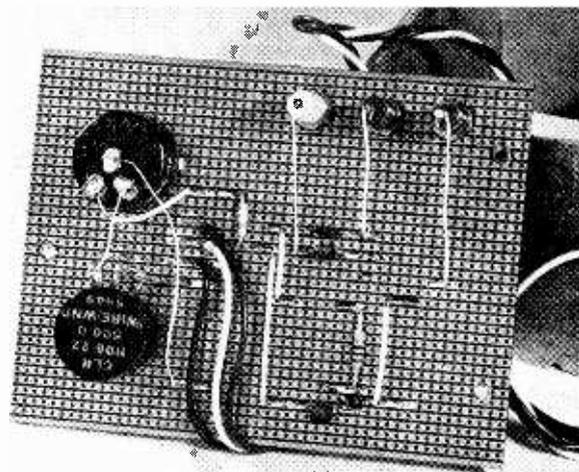

hold them whilst they were soldered. A springy connection to contact the case of the transistor was made to fit into the centre socket. It was also necessary to drill out the holes in the Vero board to take the pins of the FET socket.

A piece of white card was stuck over the top surface of the Vero board to carry the markings as shown in Fig. 3. The finished unit was mounted on wooden side pieces painted to match the original tester.

The lead connecting the Extender Unit to the Transistor Tester terminates in a small piece of strip board carrying three pins which plug into the triangular socket group. This prevents connection to the Transistor Tester the wrong way round.


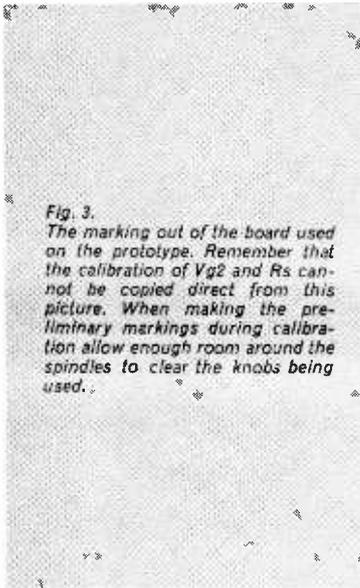


Fig. 3.
The marking out of the board used on the prototype. Remember that the calibration of V_{g2} and R_s cannot be copied direct from this picture. When making the preliminary markings during calibration allow enough room around the spindles to clear the knobs being used.

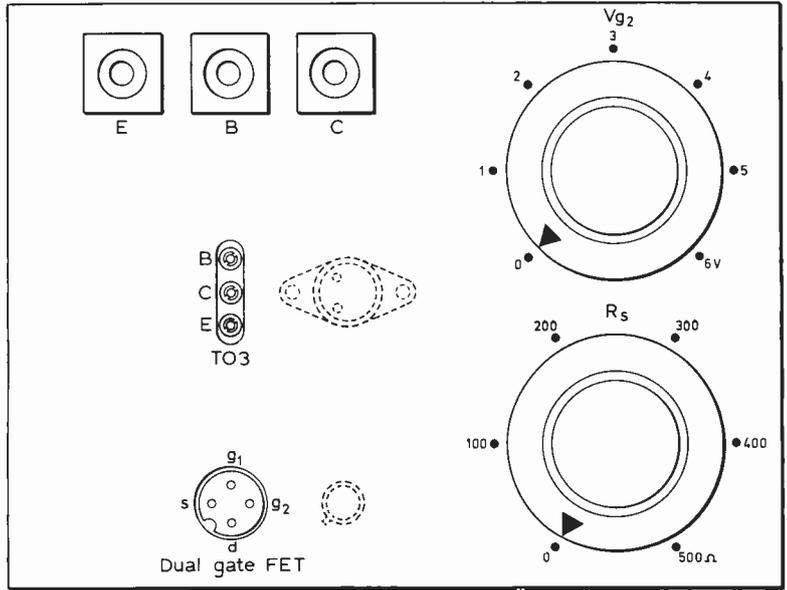

GT25

CALIBRATION

VR1, the source resistance control, can be calibrated sufficiently accurately with the aid of the ohms range of a multi-range meter, provided its batteries are fresh.

VR2 the V_{g2} control is more difficult, owing to the resistance being too high to use even a 30,000 ohm per volt meter. The best way, assuming a DVM is not available, is to connect the Extender to the Transistor Tester, switch on and set V_c to maximum. Connect the negative lead of a 0-12V power supply to E' and connect a multirange meter ($30\mu A$ or $50\mu A$ range) between the positive terminal and the slider of VR2. By setting the power supply output in 1V increments from 0 to 6V and at each step adjusting VR2 for zero reading on the meter, the calibrations can be marked in.

USE

The method of use for TO3 and other transistors is covered in the August 1976 issue of *Practical Wireless*.

For use with dual gate FETS, first check that the connections are as shown in Fig. 2. If not, the leads must be crossed as appropriate. Assuming the dual gate FET is an N channel type (most are), set the V_g/h_{FE} control of the Transistor Tester to the 0V, the V_c control to maximum, the V_{g2} control of the Extender to +4V and the R_s control to 0Ω . Switch the Transistor Tester to NPN/DIODE and the zero signal-gate voltage drain current I_{DSS} can be read. The tolerance on this is very wide, typically 1 to 20mA, and could be between 0.5 and 35mA for some types.

However, the gain of a dual gate FET is usually quoted at a fixed current, say 5mA. To achieve this, gate 1 must be slightly positive or negative to the source, as appropriate.


In a practical circuit, the drain current variation from device to device can be reduced by setting V_{g1} to +2V, V_{g2} to +6V and putting a 390 Ω resistor in the source circuit. Devices with a high

I_{DSS} will then pass somewhat more than 5mA, thus biasing themselves back at gate 1 and low I_{DSS} devices will pass somewhat less than 5mA, thus biasing themselves on harder at gate 1. The suitability of this arrangement for any particular type of dual gate FET is easily checked with this extender unit.

Note that the V_{g2} voltage is derived from the V_c supply of the Transistor Tester and this should therefore be left at maximum when testing dual gate FETS. The reduction of current through the FET resulting from decreasing the V_{g2} voltage towards zero is readily checked.

As explained in the Transistor Tester article, single gate enhancement mode FETS are readily checked, but single gate depletion mode types could only be checked for I_{DSS} and V_p . With the Extender, intermediate values of drain current can be checked by using the R_s control. If V_g is set to 0V the reverse bias on the FET gate is simply the setting of the R_s control times the collector current. When checking single gate FETS, as the V_{g2} control is not used, the effect of varying the drain voltage by means of the V_c control of the Transistor Tester can also be studied.

PW

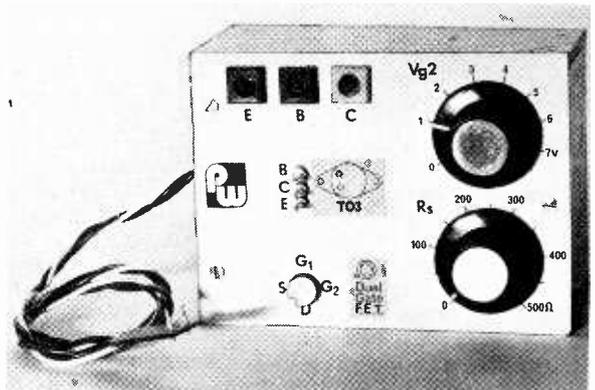

15-240 Watts!

HY5

Preamplifier

The HY5 is a mono hybrid amplifier ideally suited for all applications. All common input functions (mag Cartridge, tuner, etc) are catered for internally. The desired function is achieved either by a multi-way switch or direct connection to the appropriate pins. The internal volume and tone circuits merely require connecting to external potentiometers (not included). The HY5 is compatible with all I.L.P. power amplifiers and power supplies. To ease construction and mounting a P.C. connector is supplied with each pre-amplifier.

FEATURES: Complete pre-amplifier in single pack—Multi-function equalization—Low noise—Low distortion—High overload—Two simply combined for stereo.

APPLICATIONS: Hi-Fi—Mixers—Disco—Guitar and Organ—Public address

SPECIFICATIONS:


INPUTS: Magnetic Pick-up 3mV; Ceramic Pick-up 30mV; Tuner 100mV; Microphone 10mV; Auxiliary 3-100mV; Input impedance 4.7k Ω at 1kHz.

OUTPUTS: Tape 100mV; Main output 500mV R.M.S.

ACTIVE TONE CONTROLS: Treble \pm 12dB at 10kHz; Bass \pm at 100Hz.

DISTORTION: 0.1% at 1kHz. Signal/Noise Ratio 68dB.

OVERLOAD: 38dB on Magnetic Pick-up. **SUPPLY VOLTAGE** \pm 16-50V.

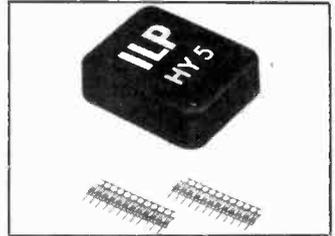

HY30

15 Watts into 8 Ω

The HY30 is an exciting New kit from I.L.P. It features a virtually indestructible I.C. with short circuit and thermal protection. The kit consists of I.C., heatsink, P.C. board, 4 resistors, 6 capacitors, mounting kit, together with easy to follow construction and operating instructions. This amplifier is ideally suited to the beginner in audio who wishes to use the most up-to-date technology available.

FEATURES: Complete Kit—Low Distortion—Short, Open and Thermal Protection—Easy to Build.

APPLICATIONS: Updating audio equipment—Guitar practice amplifier—Test amplifier—audio oscillator.

SPECIFICATIONS:

OUTPUT POWER 15W R.M.S. into 8 Ω ; **DISTORTION** 0.1% at 1.5W.

INPUT SENSITIVITY 500mV. **FREQUENCY RESPONSE** 10Hz-16kHz—3dB.

SUPPLY VOLTAGE \pm 18V.

Price £5 22 + 65p VAT P&P free.

HY50

25 Watts into 8 Ω

The HY50 leads I.L.P.'s total integration approach to power amplifier design. The amplifier features an integral heatsink together with the simplicity of no external components. During the past three years the amplifier has been refined to the extent that it must be one of the most reliable and robust High Fidelity modules in the World.

FEATURES: Low Distortion—Integral Heatsink—Only five connections—7 amp output transistors—No external components

APPLICATIONS: Medium Power Hi-Fi systems—Low power disco—Guitar amplifier

SPECIFICATIONS: **INPUT SENSITIVITY** 500mV

OUTPUT POWER 25W RMS into 8 Ω **LOAD IMPEDANCE** 4-16 Ω **DISTORTION** 0.04% at 25W at 1kHz

SIGNAL/NOISE RATIO 75dB **FREQUENCY RESPONSE** 10Hz-45kHz—3dB.

SUPPLY VOLTAGE \pm 25V **SIZE** 105 50 25mm

Price £6 82 + 85p VAT P&P free.

HY120

60 Watts into 8 Ω

The HY120 is the baby of I.L.P.'s new high power range. Designed to meet the most exacting requirements including load line and thermal protection this amplifier sets a new standard in modular design.

FEATURES: Very low distortion—Integral heatsink—Load line protection—Thermal protection—Five connections—No external components

APPLICATIONS: Hi-Fi—High quality disco—Public address—Monitor amplifier—Guitar and organ

SPECIFICATIONS:

INPUT SENSITIVITY 500mV.

OUTPUT POWER 60W RMS into 8 Ω **LOAD IMPEDANCE** 4-16 Ω **DISTORTION** 0.04% at 60W at 1kHz

SIGNAL/NOISE RATIO 90dB **FREQUENCY RESPONSE** 10Hz-45kHz—3dB **SUPPLY VOLTAGE** \pm 35V

SIZE 114 50 85mm

Price £15 84 + £1 27 VAT P&P free.

HY200

120 Watts into 8 Ω

The HY200 now improved to give an output of 120 Watts has been designed to stand the most rugged conditions such as disco or group while still retaining true Hi-Fi performance.

FEATURES: Thermal shutdown—Very low distortion—Load line protection—Integral heatsink—No external components

APPLICATIONS: Hi-Fi—Disco—Monitor—Power slave—Industrial—Public Address

SPECIFICATIONS:

INPUT SENSITIVITY 500mV

OUTPUT POWER 120W RMS into 8 Ω **LOAD IMPEDANCE** 4-16 Ω **DISTORTION** 0.05% at 100W at 1kHz.

SIGNAL/NOISE RATIO 96 dB **FREQUENCY RESPONSE** 10Hz-45kHz—3dB **SUPPLY VOLTAGE** \pm 45V

SIZE 114 100 85mm

Price £23 32 + £1 87 VAT P&P free.

HY400

240 Watts into 4 Ω

The HY400 is I.L.P.'s "Big Daddy" of the range producing 240W into 4 Ω ! It has been designed for high power disco address applications. If the amplifier is to be used at continuous high power levels a cooling fan is recommended. The amplifier includes all the qualities of the rest of the family to lead the market as a true high power hi-fidelity power module.

FEATURES: Thermal shutdown—Very low distortion—Load line protection—No external components.

APPLICATIONS: Public address—Disco—Power slave—Industrial

SPECIFICATIONS:

OUTPUT POWER 240W RMS into 4 Ω **LOAD IMPEDANCE** 4-16 Ω **DISTORTION** 0.1% at 240W at 1kHz

SIGNAL NOISE RATIO 94dB **FREQUENCY RESPONSE** 10Hz-45kHz—3dB **SUPPLY VOLTAGE** \pm 45V

INPUT SENSITIVITY 500mV. **SIZE** 114 x 100 x 85mm

Price £32 17 + £2 57 VAT P&P free.

POWER SUPPLIES

PSU36 suitable for two HY30's £5 22 plus 65p VAT. P/P free.

PSU50 suitable for two HY50's £6 82 plus 85p VAT. P/P free.



PSU70 suitable for two HY120's £13 75 plus £1 10 VAT. P/P free.

PSU90 suitable for one HY200 £12 65 plus £1 01 VAT. P/P free.

PSU180 £23 10 + £1 85 VAT.

B1 £0 48 + £0 06 VAT. **TWO YEARS' GUARANTEE ON ALL OF OUR PRODUCTS**

Available
June '76

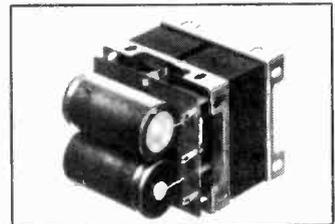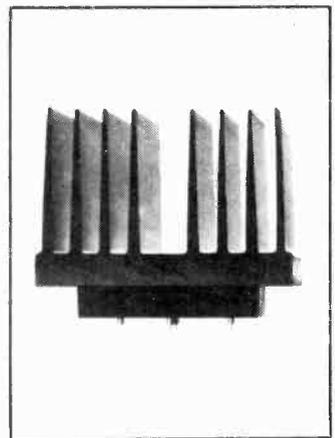

I.L.P. ELECTRONICS LTD., CROSSLAND HOUSE,
NACKINGTON, CANTERBURY, KENT, CT4 7AD

Please Supply _____

Total Purchase Price _____

I Enclose Cheque Postal Orders Money Order

Please debit my Access account Barclaycard account

Account number _____

Name and Address _____

Signature _____

Sonic

HI-FI DISCOUNT CENTRES



DISCOUNT SPEAKERS

Imp 8 or 15Ω as app.

Guarantees:
TITAN 5 years
FANE 2 years
OTHERS 1 year

ALL PRICES INC. VAT

Prices correct at 4.4.77

HI-FI TYPES	List	Sonic
5" FANE 501 Mid or Full range	Sp. Price	£44.95
8" x 5" 15w Various makes	Sp. Price	£33.35
8" A.F. Model 80 Dual Cone	Sp. Price	£55.95
8" A.F. Model 83 Dual Cone	Sp. Price	£65.95
FANE 805	Sp. Price	£55.95
FANE 804	Sp. Price	£45.95
FANE 801 Dual Cone	Sp. Price	£75.95
FANE 8" 80BT Dual Cone	Sp. Price	£35.95
FANE 8" 807TP	Sp. Price	£47.75
WH'FEDALE L'TON 3XP kit	Pr. £52.94	£34.95
10" GLENDALE XP KIT	£75.62	£52.95
8" FANE MODE ONE KIT	Sp. Price Pair	£19.75
10" ELAC Model 10RM	Sp. Price	£35.85
12" FANE 1211/SLR 20w	Sp. Price	£25.95
12" FANE 122/10 25w	Sp. Price	£9.95

GROUP/DISCO TYPES	List	Sonic
12" FANE POP 25T 25-30w	Sp. Price	£9.95
12" TITAN T12/4E 45w	£15.80	£10.95
12" TITAN T12/60A 60w	£22.50	£12.95
12" TITAN T12/100A 100w	£36.00	£22.95
12" CELESTION G12M	Sp. Price	£12.99
12" CELESTION G12H 30w	Sp. Price	£15.95
12" CELESTION G12/SO 50w	Sp. Price	£16.50
12" CELESTION G12/50TC	Sp. Price	£17.95
12" GOODMAN'S 12 PD	Sp. Price	£17.95
12" GOODMAN'S 12 PG	Sp. Price	£17.95
12" FANE 'SPECIALIST' P.A. 80	£25.95	£16.95
12" " " GUITAR 80L	£27.95	£16.95
12" " " GUITAR 80B	£26.95	£16.95
12" FANE CRESCENDO 12A	£57.35	£37.95
12" FANE " 12L	£59.95	£39.95
12" FANE " 12 BASS	£56.70	£32.95
15" TITAN T15/60 60w	£28.00	£18.95
15" TITAN T15/70 70w	£28.00	£19.95
15" TITAN T15/100 100w	£41.00	£28.95
15" FANE 'SPECIALIST' BASS 85	£37.75	£28.95
15" " " BASS 100	£39.95	£29.95
15" GOODMAN'S 15P	Sp. Price	£22.50
15" CELESTION G15C	Sp. Price	£26.95
15" FANE CRESCENDO 15/100A	£72.95	£49.95
15" FANE CRESCENDO BASS	£76.00	£49.95
15" " " 15/100LT	£74.69	£49.95
15" " " COLOSSUS 200w	£108.00	£69.95
18" TITAN T18/100 100w	£47.00	£33.95
18" GOODMAN'S 18P	Sp. Price	£38.95
18" CELESTION G18C	Sp. Price	£34.50
18" FANE CRESCENDO 18A	£101.95	£66.95
18" FANE CRESCENDO BASS	£89.95	£59.95
18" " " COLOSSUS 200w	£115.00	£69.95

HORN UNITS	List	Sonic
CELESTION MH1000 30w	Sp. Price	£13.75
FANE 910 MK II 50w	£11.75	£10.95
FANE 920 100w	£59.95	£19.95
FANE 144 30-50w	£7.95	£5.95
FANE 1104 50-70w	£16.95	£12.95

HIGH POWER 'CROSS OVERS'	List	Sonic
FANE HPX1 or HPX2	£2.99	£1.99
'ADD-ON' HIGH FREQUENCY UNITS		
F.A.L. 'Add-on'	£51.84	£35.95
TITAN TIH 70w	Sp. Price	£25.95
TITAN T52H 100w	Sp. Price	£25.95

Extra Special prices for quantities	List	Sonic
HI-FI SPEAKER SYSTEMS Carr. £1.50	Pair	
LEAK 3020	Pair	£128.56 £89.95
LEAK 3030	Pair	£175.84 £122.95
LEAK 3050	Pair	£245.80 £171.95
WH'FEDALE DENTON 2XP	Pair	£65.45 £42.95
LINTON 3XP	Pair	£91.71 £59.95
CHEVIN XP	Pair	£42.55 £28.95
DENTON 2XP	Pair	£63.34 £43.95
LINTON 3XP	Pair	£91.71 £63.95
GLENDALE 3XP	Pair	£126.67 £87.95
DOVEDALE 3XP	Pair	£217.44 £151.95

AMPS, T'ABLES, JINGLE MACHINES, DISCO CONSOLES, LIGHTING, CABINETS, (for personal callers only)

CREDIT TERMS AVAILABLE orders £20 over

Phone orders accepted from Access & Barclay card holders.

Branches at
GLASGOW
403 SAUCHIEHALL STREET
Tel: 141 332 0700
MIDDLESBROUGH
106 NEWPORT ROAD
Cleveland TS1 5JF. Tel: 0642 217402

Mail Orders & Export enquiries to Middlesbrough Branch Add 75p carr. on orders under £7. Cabinets for personal shoppers only.

TORIN ELECTRONICS

24 DARTFORD ROAD, DARTFORD, KENT. Tel. (0322) 73133/25864

All prices inclusive of V.A.T. Below are but a few of the types available. Please phone for quotation of unlisted types. S.A.E. for written replies, please. All goods brand new, boxed and guaranteed for 12 months. Postage: 12p one valve, 3p each subsequent valve. Orders over £10 free. Trade enquiries welcome. Try us first for all obsolete types.

OA2	-44	BF6	-59	20F2	-84	DF96	-59	ECL85	-69	GY501	-84	PY83	-43
OB2	-39	BF13	-89	20L1	-84	DK92	-99	ECL86	-45	GZ32	-55	PY88	-39
1B3	-54	BF14	-89	20P1	-89	DK96	-59	EF37A	1-45	GZ33	1-75	PY500A	1-15
1R5	-49	BF15	-84	20P3	-99	DL96	-69	EF39	1-45	G234	-74	PY800	-39
1S4	-39	BF18	-59	20P4	-83	DM70	-79	EF40	-77	G237	2-20	PY801	-39
1T4	-39	BF23	-64	20P5	1-48	DM71	-74	EF41	-74	KT60	3-00	QQV03/10	-99
2D21	-54	BF24	-79	25L6	-69	DY86/7	-34	EF42	-89	KZ88	6-50	QV03/10	1-95
2D21W	2-10	BF25	-99	25Z4	-49	DY802	-44	EF80	-28	KTW61	1-25	QQV03/20A	-99
3A4	-54	BF28	-73	25Z5	-74	E80CC	2-45	EF83	1-23	PABC80	1-44	QQV06/40	16-40
3Q4	-79	GG6	-59	25Z6	-79	E80CF	4-95	EF85	-35	PC86	-61	QQV06/40	-99
3Q5	-89	GH6	-29	30A5	-74	E80F	2-15	EF86	-44	PC88	61	PC88	27.00
3S4	-44	GJ5	-44	30C15	-76	E88CC	1-15	EF89	-31	PC95	-69	QS95/10	-95
8R4	-99	6J7	-34	30C17	-79	E80F	1-13	EF91	-42	PC97	-38	QV06/20	3-45
5U4	-55	6K7	-34	30C18	-89	E172CC	2-95	EF92	-49	PC900	-39	UABC90	-44
5V4	-55	6K8	-44	30F5	-69	E188CC	2-35	EF97	-89	PC884	-38	UAF42	-69
5Y3	-54	6L6	-69	30FL1	-99	EABC80	-30	EF98	-89	PC85	-46	UB 241	-49
5Z3	-99	6N7	-69	30FL2	-99	EAC91	-54	EF183	-35	PC888	-60	UF C81	-54
5Z4	-47	6Q7	-39	30L15	-74	EAF42	-69	EF184	-35	PC899	-48	UF C80	-49
6/30L2	-78	6R7	-89	30L17	-89	EB91	-19	EF804	1-79	PC189	-51	UBF99	-38
6AC7	-54	6S47	-54	30P12	-73	EC41	-79	EH90	-44	PC91	-39	UCF41	-69
6A G5	-35	6S77	-59	30P19	-89	EC81	-42	EL32	-59	PCF82	-54	UC C85	-44
6AH6	-89	6SK7	-54	30P1L	-84	EBF80	-39	EL34	-85	PCF84	-69	UCF80	-79
6AK5	-44	6SL7	-54	30P1L3	-99	EBF83	-42	EL35	2-95	PCF86	-56	UCF82	-70
6AK6	-89	6SN7	-54	30P1L4	1-08	EBF89	-34	EL37	2-95	PCF200	1-15	UC H81	-44
6AN8	-89	6SQ7	-39	30P1L5	-99	EC86	-83	EL41	-56	PCF201	-99	UC L82	-44
6AN8	-89	6V6	-29	35C5	-79	EC88	-83	EL81	-64	PCF801	-48	UC L83	-56
6AQ5	-46	6X4	-44	35L9	-79	EC92	-54	EL83	-65	PCF802	-54	UC L84	-69
6AR5	-79	6Y5	-44	35W4	-54	EC C40	-89	EL84	-33	PCF80	-52	UC F2	-79
6AS7	-99	10C2	-69	35Z4	-69	EC C81	-33	EL86	-55	PCF808	1-05	UF80	-39
6AT6	-99	10F1	-66	35Z5	-79	EC C82	-33	EL95	-65	PCH200	-99	UF85	-49
6AU6	-39	10F9	-64	50C5	-69	EC C83	-33	EL506	1-15	PCL82	-39	UF89	-44
6AV8	-49	10F18	-64	50C6	1-18	EC C84	-34	EM80	-54	PCL83	-48	UL41	-69
6BA6	-39	10LD11	-74	50L5	-99	EC C85	-38	EM81	1-10	PCL84	-45	UL84	-42
6BE6	-39	10P13	-79	55A2	-74	EC C86	-74	EM83	1-23	PCF85/805	-59	UM80	-59
6BH6	-69	10P14	2-49	90AG	3-00	EC C88	-50	EM84	-33	PFL200	-69	UY41	-49
6BJ6	-64	12AC6	-79	90C1	-90	EC C189	-79	EM85	1-15	PL36	-49	UY85	-34
6BQ7	-54	12AE8	-80	90CG	3-00	EC C807	2-70	EM87	1-05	P133	-59	U10	-99
6BR7	-99	12AT6	-44	807	1-08	EC F80	-49	EY51	-44	PL81	-48	U12	1-10
6BR8	1-24	12AU6	-48	5783	1-80	EC F82	-49	EY81	-44	PL81A	52	U14	1-10
6BS7	1-39	12AV6	-59	6057	-99	EC F86	-49	EY83	-39	PL82	-36	U19	3-83
6BW6	-99	12BA6	-49	6060	-99	EC F804	5-30	EY84	1-15	PL83	-44	U25	-70
6BW7	-64	12BE6	-54	6067	-99	ECH42	-70	EY86/7	-36	PL84	-40	U26	-55
6C4	-39	12BH7	-54	7193	-55	ECH81	-34	EY88	-54	PL504	-89	U191	-45
6C5	-59	12BY7	-84	CL33	1-73	ECH83	-49	EY91	-49	PL509	1-79	VR105/30	-45
6CB6	-48	12E1	3-40	CY31	-89	EC H84	-49	EZ40	-51	PY33	-49	VR150/30	-44
6CD6	1-59	15AQ5	-64	DAF91	-34	ECL80	-44	EZ41	-51	PY80	-49	X77	2-30
6CL6	-74	19G6	6-30	DAF96	-59	ECL82	-49	EZ80	-31	PY81	-39	X41	-99
6E6	-84	20D1	-69	DF91	-29	ECL83	-73	EZ81	-39	PY82	-39	Z750	5-80

CROFTON FOR USED VIDEO EQUIPMENT

Please send 10. 12p stamp addressed envelope

Used Video Equipment bought and sold daily. If we do not have what you want, we enter your requirements on our register and advise you when it is available. U.H.F. Modulators supplied for connecting a camera directly to a domestic T.V. or Philips V.C.R. Camera Kits for the enthusiast also in stock. Fujinon Lens available. Repairs of all types of Video equipment undertaken.

WHATEVER YOUR VIDEO REQUIREMENTS FIRST CONTACT CROFTON

CROFTON ELECTRONICS LTD
Dept. B, 35 Grosvenor Road, Twickenham, Middx. Tele. 01-891 1923

The CQ-1 by CASIO

IT'S 10.58 WEDNESDAY, 21TH
Executive Pocket Secretary
Soz. 1 1/2" H x 5 1/2" W x 2 1/2" D

DIGITAL ALARM CLOCK

Now you can be electronically reminded of up to 4 important appointments per day, perform time and date calculations, perform events timing and routine calculations—all in a lightweight (only 5oz.) pocket-sized unit... Ideal for time pressed executives, engineers and students... No more annoying wake-up calls on business trips.

STOPWATCH

Times up to 10 hours in 0.1 second increments in 3 modes elapsed time with/without pauses, and cumulative lap times. Display may be unlatched after recording.

TIME/DATE CALCULATIONS

The CQ-1's special base 60 logic allows time and date difference calculations, time conversions and a perpetual calendar. You can calculate the number of days left until a contract date or what date and day of the week a payment is due.

CALCULATOR

Performs the standard 4 functions: +, -, x, / in a full 8 digits. Also constant calculations.

DISPLAY/POWER SUPPLY

An easy to read green digitron display shows all CQ-1 time, data, stopwatch and calculator outputs. The timer circuitry is powered by 2 digital watch batteries (1 yr. life). The display is run by a standard 1.5v penlight battery (1 hr. life). When the optional AC adapter is connected a micro-switch is tripped, displaying the time constantly.

A compact Digital Clock, Calendar, Stopwatch, Calculator, Personal Alarm... £29.80
Adaptor £3.34 for continuous display

KRAMER & CO., Dept. PW4
9 October Pl, Holders Hill Rd, London NW41EJ
Tel: 888941 ATTN KRAMER. Tel. 01-203 2473

We offer all Casio LCD watches and Texas, HP, Casio, CBM and Realtime Calculators. SAE for brochures. Mail Order only. We export worldwide.

Circuits for AUDIO AMPLIFIERS

PART 4

F.G.RAYER G3OGR

"PUSH-PULL" ICs



The LM380 has alternative inputs, pin 2 being non-inverting, and pin 6 inverting. It is thus possible to combine two ICs as in Fig. 26, to obtain a higher power output. IC1 input goes to pin 2 and IC2 input to pin 6, unused input pins being earthed. Outputs are thus out of phase for the speaker. When setting up the amplifier, rotate VR2 to a central position and place a meter in series with the speaker. VR2 can be a pre-set inside the equipment and adjusted for minimum current as shown by the meter. It may be found with some ICs that VR2 gives insufficient adjustment. If so, VR2 can be 250k Ω , and R1 and R2 each 330k Ω .

Many units having an IC main amplifier will have one or more transistors as pre-amplifiers, to raise the sensitivity to that needed for a microphone or other low-level input. The various negative earth line pre-amplifiers, tone-controls and other circuits shown earlier may be incorporated, as required.

EARTH LOOPS

Power supply circuits can usually be quite simple types, designed to provide the wanted voltage over the current range expected. Trouble may arise from the manner in which pre-amplifiers, amplifiers, or other units are connected to the supply. Where equipment has substantial gain and power output,

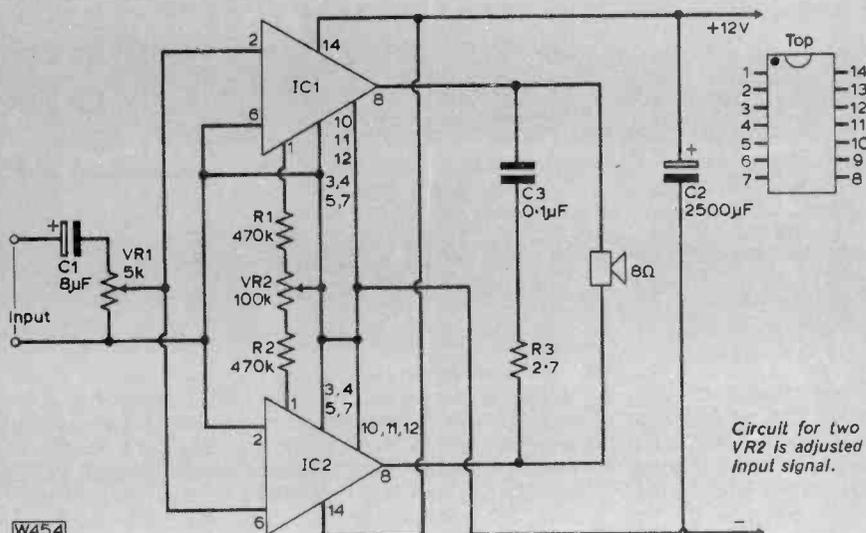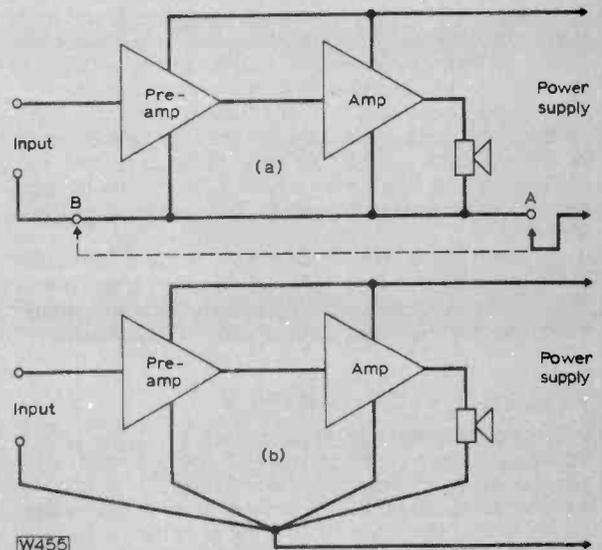incorrect earth circuits can cause problems. In Fig. 27a input currents and voltages may be extremely small, while output circuit currents may be in terms of amperes. With the power supply earth connected at point A, high currents here will not influence the input. But a connection which transferred the power supply circuit to B, for example,



27

26

Circuit for two LM380's in push-pull. Potentiometer VR2 is adjusted for minimum supply current with no input signal.

could cause instability due to the presence of high common earth return currents for the pre-amplifier. An alternative method of wiring is shown in Fig. 27b.

Electrical feedback may be by inductive or capacitive coupling from output leads (speaker) or components, or leads carrying high current (power) back into input (microphone, pick-up, tuner, pre-amplifier) circuits. It is avoided by a layout which places output components such as speaker coupling capacitors etc. away from input circuit components and by using screened leads at inputs to pre-amplifier and amplifier.

HUM PICK-UP


Hum is likely at 50Hz, 100Hz or 150Hz, these frequencies arising from the 50Hz supply. Hum at 50Hz may be caused by inductive, capacitive, or leakage coupling from mains circuits to inputs, due to the run of the wiring, or layout of power and other circuits. Screening and connectors should be checked and moving leads or pre-amplifiers around may help locate the cause. Such hum can also be caused by insufficiently smooth supplies from half-wave rectification, in which case these measures are likely to have little effect. Additional smoothing is needed, especially in early stages or pre-amplifiers.

A 100Hz hum comes from full-wave rectification, from insufficient smoothing, or circuits which result in transformer, rectifier or smoothing capacitor currents coupling into early stages. Layout should keep such circuits and components away from input circuits.

A 150Hz hum would normally be 3rd harmonic from core hysteresis, induced by the transformer into adjacent components or circuits. Layout should place the transformer clear of input components.

POLARITY OF SUPPLY

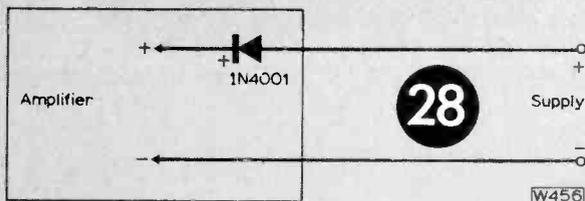
Wrong polarity can destroy transistors in circuit positions where current is not limited and non-reversible or clearly marked connectors should be used with home-built equipment. It is often worthwhile to include a protective diode in the amplifier, as in Fig. 28. The 1N4001 is suitable for currents up to 1A. Wrong supply polarity merely causes non-operation of the equipment.



POWER SUPPLIES


Fig. 29 is typical of many power supply circuits. Current is supplied via a low rating (2A or 3A) fuse and 3-core cable providing line, neutral and earth circuits. When a single pole switch is fitted it must be in the Live conductor, but the double pole switch is recommended. The earth is connected to the transformer core and secondary circuit, and is only

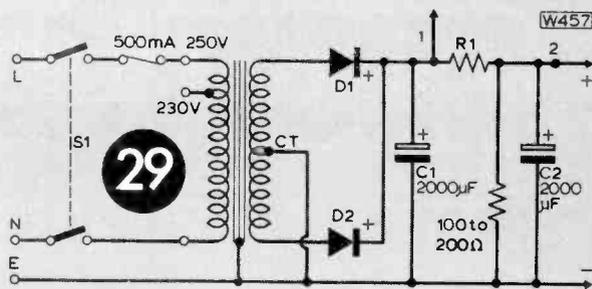properly omitted when a double-insulated transformer is used. The small fuse at the primary may be omitted in some cases and some transformers will have no optional primary tappings.



Full-wave rectification is obtained using a centre-tapped secondary winding. In many cases current is then drawn directly from the point 1, only C1 being present for smoothing. R1 and C2 are usually found in the amplifier positive line feeding earlier stages, but in some cases may be present as part of the smoothing to furnish a lower voltage with additional smoothing. As earlier stages operate Class A, with steady current, R1 may be chosen to provide the wanted voltage.

Some transformers may have a separate low voltage secondary to operate a pilot lamp. Capacitors of about 1000pF may be shunted across D1 and D2. Occasionally high working voltage capacitors (say 0.05µF) may be shunted from live and neutral to earth to eliminate mains modulation hum. By suitable choice of transformer and diodes, any wanted voltage and current is available. Peak secondary voltage is approximately 1.4 times the RMS voltage (the latter being that shown by a meter). Thus C1 can charge to this value on no load, so it must be rated to at least 1.5 times the secondary voltage. As the diodes may have to withstand this and also the peak inverse voltage they must be rated at a minimum of 2.8 times the secondary voltage. E.g., a 12V transformer for this circuit would have a 12.0-12V secondary (actually 24V overall). Thus 50V diodes will be convenient for supplies of up to about 16V to 17V or so, with 100PIV diodes for up to 35V. Suitable diodes are 1N4001 (50PIV) and 1N4002 (100PIV) for most circuits (these are rated at 1A).

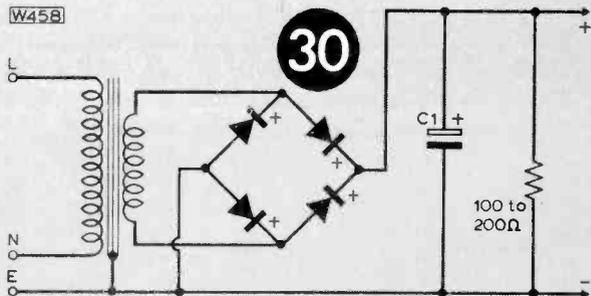

An alternative rectifier circuit, often used, is shown in Fig. 30. No secondary centre-tap is needed and the rectifier PIV is reduced. An 18V 1A secondary will provide about 24V at up to 1A, using 1A diodes. A resistor across C1 helps stabilise the voltage and is usually 100 to 200Ω, according to the current available, as transformer and rectifiers must meet this additional load.

RETURN OF POST MAIL-ORDER SERVICE

R.C.S. 100 watt MIXER/AMPLIFIER ALL VALVE CHASSIS



Four inputs. Four way mixing, master volume, treble and bass controls. Suits all speakers. This professional quality amplifier chassis is suitable for all groups, disco, P.A., where high quality power is required. 5 speaker outputs. A/C mains operated. Slave output. Produced by demand for a quality valve amplifier. Send for details. Suitable carrying cabinet £14. Price **£85** carr. 42-50

ANOTHER R.C.S. BARGAIN!

ELAC 9 + 5in. HI-FI SPEAKER TYPE 59RM
This famous unit now available, 10 watts, 8 ohm.

Price **£3.25** Post 40p



10" ELAC HI-FI SPEAKER

Large ceramic magnet.
Response: 50-18,000 cps.
Bass resonance 55 cps.
16 ohm impedance 10 watts.

Post 40p

£4.45

TEAK VENEER HI-FI SPEAKER CABINETS

MODEL "A". 20 x 13 x 12in.
For 12in. dia. or 13-50 10in. speaker
Illustrated. £1.60

MODEL "B".
For 13 x 8in. or 12 x 8in. speaker. £7.50 Post £1

R.C.S. BOOKSHELF
SPEAKERS
Size 14in. x 9in. x 6in.
Response 50 to 14,000 cps
6 watts rms 8 ohms. Post £1.30

LOUDSPEAKER CABINET
WADDING 18in. wide, 20p ft.



GOODMANS CONE TWEETER

2 1/2in. diam. 18,000 C.P.S. 25 WATTS 8 Ω **£3.25**
5in. Audax 16 watts £4-95. 6in. EMI mid range 25

BARGAIN 4 CHANNEL TRANSISTOR MONO MIXER. Add musical highlights and sound effects to recordings. Will mix Microphone, recording tape and tuner with separate controls into single output. 9 volt £5.75 battery operated.



TWO CHANNEL STEREO VERSION OF ABOVE £7.50

BARGAIN 3 WATT AMPLIFIER. 4 Transistor Push-Pull Ready built with volume, treble and bass controls. 18 volt battery operated. Mains Supply £9.95

THE "INSTANT" BULK TAPE ERASER & HEAD DEMAGNETISER. suitable for cassettes, and all sizes of tape reels. A.C. mains 200/240V. Leaflet S.A.E. **£4.50** Post 40p



WAFER THIN HEATING ELEMENTS

OFFERING 1001 USES for every type of heating and drying applications in the home, garage, greenhouse (available in manufacturing quantities). Approx. size 10 1/2 x 8 1/2 x 1/4in. Operating voltage 200/280V. a.c. 250 watts approx. Printed circuit element enclosed in asbestos fitted with connecting wires. Completely flexible providing safe Black heat. British-made for use in photocopyers and print drying equipment.

Ideal for home handyman and experimenters. Suitable for Heating Pads, Food Warmers, Convactor Heaters, etc. Must be clamped between two sheets of metal or asbestos, etc., to make efficient clothes dryers, towel rails—ideal for airing cupboards. Ideal for anti-frost device for the garage—preventing frozen radiators or acting as oil sump heater. Use in greenhouse for seed raising and plant protection. Invaluable aid for bird houses, incubators, etc., etc. Can be used in series for lower heat. Or in parallel for higher heat applications.

ONLY 40p EACH (FOUR FOR £1.50)

ALL POST PAID—Discounts for quantity.

BAKER MAJOR 12" £14.95



Post £1
30-14,500 c/s. 12in. double cone woofer and tweeter cone together with a BAKER ceramic magnet assembly having a flux density of 14,000 gauss and a total flux of 145,000 Maxwells. Bass resonance 40 c/s rated 25 watts. NOTE: 4 or 8 or 16 ohms must be stated.

Module kit, 30-17,000 c/s with tweeter, crossover, baffle and instructions. **£18.95**

Please state 4 or 8 or 16 ohms. Post £1.60

BAKER SPEAKERS "BIG SOUND"

Robustly constructed to stand up to long periods of electronic power. As used by leading groups. Useful response 30-13,000 cps. Bass resonance 55 cps.

GROUP "25"
12in 30 watt £11.95
4, 8 or 16 ohms. Post £1

GROUP "35"
12in 40 watt £13.95
4, 8 or 16 ohms. Post £1

GROUP "50/12"
12in 60 watt professional model. 3 ohms or 16 ohms. £20.95
With aluminium presence dome. Post £1.60

GROUP "50/15"
15in 75 watt £25.75
8 or 16 ohms. post £1.60



BAKER 150 WATT QUALITY TRANSISTOR MIXER/AMPLIFIER

Professional amplifier using advanced circuit design. Ideal for disco, groups, P.A. or musical instruments. 4 inputs 4 way mixing. Master treble, bass and volume controls. 3 speaker output sockets to suit various combinations of speakers. 4 to 16 ohm. Slave output. A/C mains. Guaranteed. Details S.A.E. 150W SLAVE VERSION 280 Latest 5.0 watt Model £49 **£68** Carr. £1.00




100 WATT DISCO AMPLIFIER CHASSIS
MADE BY JENNINGS MUSICAL INSTRUMENTS £52
4 speaker outputs, vol., treble, bass controls
CANNOT BE USED AS 100WATT SLAVE Carr. £1

B.S.R. SINGLE PLAYER DECK
3 speed. Plays all size records. Stereo Cartridge. Cueing device. Ideal Disco Deck. Post 75p £13.50
Autochanger Version £17.50.

QUALITY LOUDSPEAKER ENCLOSURE

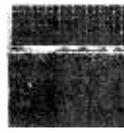Teak veneered 1/2in thick wood cabinet. Size 13 1/2in x 18 1/2in x 8 1/2in. Weight 23lb. This cabinet features a wide mesh Silver Grill covering a separate compartment for mounting Tweeters or Mid-Range Horn. The fully sealed bass compartment is cut out for 6in. Woofer 25.95. Carr. £1.00
Baffle could be cut for larger speaker.



P.W. SOUND TO LIGHT DISPLAY
Complete kit of parts with R.C.S. printed circuit. Three channels. 600 to 1,000 watts each. As featured in Practical Wireless. Price **£14.00**
Cabinet extra 43.

8 inch PHILIPS LOUDSPEAKER
4 ohm. 4 watt. ceramic magnet £1.95
General purpose replacement unit.

MAINS TRANSFORMERS Post 50p
6 VOLT 1 AMP. £1.00 3 AMP. £1.40
12 VOLT 300 MA. £1.00 750 MA. £1.30
30 VOLT 2 AMP. AND 34 VOLT 2 AMP C.T. £2.45
20 VOLT 1 AMP. £1.75 1 AMP. £2.00 3 AMP. £2.80
20-0-20 VOLT 1 AMP. £2.95 30 VOLT 1 1/2 AMP. £2.50
40 VOLT 2 AMP. £2.95. 0-20-40-80 VOLT 1 AMP. £3.50

PERIOD LOUDSPEAKER CABINETS
Two styles available, Regency and Queen Anne. Size approximately 34 x 19 x 18in. These cabinets are slightly soiled and are priced from £10 each. Callers only.


BAKER DISCO SPEAKERS HIGH QUALITY—BRITISH MADE 2 x 12" CABINETS

for Disco or PA all fitted with carrying handles and corners. Black finish. Other cabinets in stock. SAE For leaflet

50
WATT
R.M.S.
£50
Carr. 43

70
WATT
R.M.S.
£55
Carr. 43

100
WATT
R.M.S.
£69
Carr. 44

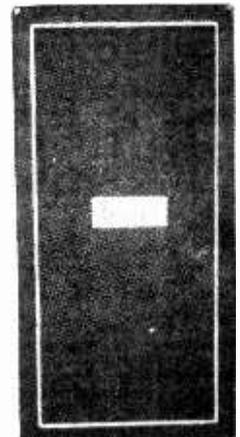

1 x 15" + 1 x 12" 100 WATT CABINET
Size 36" x 24" x 15" £75.00. Carr. £5
Ideal for Disco, Organ or PA work.
High quality. Full range.

"SUPERB HI-FI"

12in 25 watts
A high quality loudspeaker, its remarkable low cone resonance ensures clear reproduction of the deepest bass. Fitted with a special copper drive and concentric tweeter cone resulting in full range reproduction with remarkable efficiency in the upper register.
Bass Resonance 25cps
Flux Density 16,500 gauss
Useful response 20-17,000cps
8 or 16 ohms models.



£22.50 Post £1.60

"AUDITORIUM"

12in. 35 watts
A full range reproducer for high power, Electric Guitars, public address, multi-speaker systems, electric organs. Ideal for HI-FI and Discotheques.
Bass Resonance 35cps
Flux Density 15,000 gauss
Useful response 25-18,000cps
8 or 16 ohms models.



£20.95 Post £1.60

"AUDITORIUM"

15in. 45 watts
A high wattage loudspeaker of exceptional quality with a level response to above 8,000 cps. Ideal for Public Address, Discotheques, Electronic instruments and the home HI-FI.
Bass Resonance 35cps
Flux Density 15,000 gauss
Useful response 20-14,000cps
8 or 16 ohms models.



£25.75 Post £1.60

Loudspeaker Cabinet Wadding 18in wide. 20p per ft.
HI-FI Enclosure Manual containing plans, designs, crossover data and cubic tables, 68p

RADIO COMPONENT SPECIALISTS 337 WHITEHORN ROAD, CROYDON

Minimum post 30p. Components Lists 10p. Cash price includes VAT Access & Barclay cards welcome. Rail Selhurst. Tel. 01-484 1665

B. BAMBER ELECTRONICS

Dept. PW, 5 STATION ROAD, LITTLEPORT, CAMBS., CB6 1QE
Telephone: ELY (0353) 860185 (2 lines) Tuesday to Saturday

PLEASE ADD 8% VAT UNLESS OTHERWISE STATED

RED LEDs (Min. type) 5 for 70p.

VIDICON SCAN COILS (Transistor type, but no data) complete with vidicon base £8.50 each. Brand New.

FULL RANGE OF BERNARDS/BABANI ELECTRONICS BOOKS IN STOCK. S.A.E. FOR LIST.

NEW FOR THE VHF CONSTRUCTOR. A range of tuned circuits on formers with slugs and screening cans. Frequencies quoted are approximate, and range can be greatly extended by using varying capacitors in parallel.

Type S (1/4in. square, dummy type).
Type SA 20 to 30MHz (when 33pf fitted in parallel).
Type SB 35 to 50MHz (with link winding).
Type SC 70 to 100MHz (with link winding).
Type SD 135 to 175MHz (with link winding).
Type M (Min. 1/4in. square types).
Type MA 19 to 28MHz (when 33pf fitted in parallel).
Type MB 22 to 32MHz (when 33pf fitted in parallel).
Type MC 25 to 35MHz (when 33pf fitted in parallel).
Type MD 38 to 60MHz (when 33pf fitted in parallel).
Type ME 45 to 60MHz (when 33pf fitted in parallel).
Type MF 100 to 200MHz (without slug) when 0 to 30pf variable fitted in parallel.

All the above coils available in packs of five only (same type) at 80p per pack of 5.

PLASTIC PROJECT BOXES with screw on lids (in Black ABS) with brass inserts.
Type NB3 approx. 4 1/4in x 3 1/4in x 1 1/2in. 60p each. (Other sizes available shortly)

MULLARD 8542 85V STABILISER VALVES (Brand New) 70p each or 2 for £1.25.

TO3 transistor insulator sets, 10 for 50p.

2N3055 type Transistors, O.K., but unmarked. Sorry, Sold Out.

110V NEONS, SCREW-IN-TYPE, 4 for 50p.

4MHz XTAL PACKS (10 assorted xtals between 4MHz and 5MHz), our selection only. £1 Pack.

MINIATURE PLIERS. High quality "Crescent", made in USA. £4.35 + VAT (35p).

SIDE CUTTERS. High quality. £3.70 + VAT 30p.

MAINS ISOLATION TRANSFORMERS. Tapped mains input 240V at 3A, 12V at 500mA output. New. Boxed, made by Gardners. £12.

GARRARD 9V DC MINIATURE MOTORS. Type 318M, 3200 RPM governed, size approx. 1 1/4in. dia. x 1 1/2in. high, with 2mm spindle. Brand New. 60p each or 2 for £1.

SILICON HIGH VOLTAGE RECTIFIER STICKS. BY185 (new) 35kV 2.5mA £1 each. BY140 (ex-equip) 12kV 2.5mA 45p each.

VARIABLE STABILISED POWER SUPPLY. mains input, 0-24V output, stabilised and current limiting at 500mA + 32V at 50mA. Brand new by British manufacturer. Size approx. 7 1/2 x 2 1/2 x 4in. complete with external 5kΩ 3-tum pot for voltage control. Connection data supplied. £7.

14 DIL REED RELAYS. 5 to 12V DC, 450 ohm coil. Designed to work directly from TTL Logic. Single Pole Change over. Contact ratings 28V 1/2A 3W. £1.78 each.

SPECIAL OFFER ... STARPHONE HIGH BAND RF PC BOARDS, with conversion data for making into a good 2N Converter. (All that is needed: 1 xtal, 7 caps, 2 resistors, and 9V DC). PCB contains 2 Dual gate Mos Fet RF stages (3N140). Diode ring mixer, 3 stage Osc/Multiplier, all on one PCB, approx. size 6 x 1 1/2in. ext. connections, 9V DC supply, AGC (can be left fixed bias, or RF gain control) Ant. input. If output (works from a few MHz to over 30MHz). All Brand New. £6.50 each, while stocks last.

BSX20 (VHF Osc/Mult), 3 for 50p.
BC108 (metal can), 4 for 50p.
BC108 (plastic BC108), 5 for 50p.
BFY51 Transistors, 4 for 60p.
BCY72 Transistors, 4 for 50p.
PNP audio type TO5 Transistors, 12 for 25p.
BF152 (UHF amp/mixer), 3 for 50p.
2N3819 Fet, 3 for 60p.
BC148 NPN SILICON, 4 for 50p.
BC158 PNP SILICON, 4 for 50p.
BAY31 Signal Diodes, 10 for 35p.
BA121 Varicap Diodes, 4 for 80p.

SMALL MAINS SUPPRESSORS (small chokes, ideal for radio, Hi-Fi inputs, etc.), approx. 1/4in. x 1 1/4in., 3 for 50p.

PERSPEX TUNER PANELS (for FM Band 2 tuner) marked 98-108MHz and Channels 0-70, clear numbers, rest blacked out, smart modern appearance, size approx. 8 1/2in. x 1 1/2in., 2 for 35p.

PLUGS AND SOCKETS
N-Type Plugs 50 ohm, 80p each, 3 for £1.50.
PL259 Plugs (PTFE), brand new, packed with reducers, 85p or 5 for £3.
SO239 Sockets (PTFE), brand new (4-hole fixing type), 60p each or 5 for £2.25.

SOLDER SUCKERS (Plunger Type). Standard Model, £4.80. Skirted Model, £4.95. Spare Nozzles 60p each.

WELLER SOLDERING IRONS
EXPERT. Built-in-spotlight illuminates work. Pistol grip with fingertip trigger. High efficiency copper soldering.

EXPERT SOLDER GUN. £6.80 + VAT (54p).
EXPERT SOLDER GUN KIT (spare bits case, etc.), £9.80 + VAT (78p).

SPARE BITS, PAIR. 30p + VAT (23p).
MARKSMAN SOLDERING IRONS
SP15D 15W £3 + VAT (24p).
SP25D 25W £3 + VAT (24p).
SP25DK 25W + bits, etc., kit £3.85 + VAT (31p).
SP40D 40W £3.44 + VAT (28p).
BENCH STAND with spring Markman Irons, £2.22 + VAT (18p).

SPARE BITS
MT8 for 15W, 48p + VAT (4p).
MT4 for 25W, 38p + VAT (3p).
MT10 for 40W, 42p + VAT (3p).

TC2 TEMPERATURE CONTROLLED IRON. Temperature controlled iron and PSU. £27 + VAT (£2.18).

SPARE TIPS
Type K single flat, Type K double flat fine tip, Type P, very fine tip. £1 each + VAT (8p).

MOST SPARES AVAILABLE.

MOST SPARES AVAILABLE.

MULTICORE SOLDER
Size 5 Savbit 18 s.w.g. In alloy dispenser, 32p.
Size 4 Savbit 18 s.w.g., 58p + VAT (4p).
Size CISA118 Savbit 18 s.w.g., 58p + VAT (4p).
1/2kg (1-1lb) 60 x 40, 20 s.w.g. on plastic reel £3.

A LARGE RANGE OF CAPACITORS AVAILABLE AT BARGAIN PRICES, S.A.E. FOR LIST.

MIXED COMPONENT PACKS, containing resistors, capacitors, pots, etc. All new. Hundreds of items. £2 per pack, while stocks last.

ALU-SOL ALUMINUM SOLDER (made by Multicore) Solders aluminium to itself or copper, brass, steel, nickel or tinplate, 16 s.w.g. with multicore flux, with instructions. Approx. 1 metre coil 40p pack. Large reel £2.75.

VARICAP TUNERS Mullard Type ELC1043/05, Brand New. £4.40 + 12 1/2% VAT.

BARGAIN PACK OF LOW VOLTAGE ELECTROLYTIC CAPACITORS. Up to 50V working. Sestrionic Manufacture. Approx. 100. £1.50 per pack + 12 1/2% VAT.

Mobile Converters, 24V DC input 13.8V at approx. 3.4A DC output, fully stabilised. £3.80 each (ideal for running 12V car radio from 24V lorry battery).

We now stock Spiraxul Tools for the electronic enthusiast. Screwdrivers, Nut Spanners, BA and Metric sizes, pop rivet guns, etc. S.A.E. for list.

TWIN I.F. CANS, approx. 1in. x 1/2in. x 1in. high, around 3.5-5MHz, 2 separate transformers in 1 can, internally screened, 5 for 50p + 12 1/2% VAT.


Duobler Electrolytics, 500µF, 450V, 2 for 80p.
Duobler Electrolytics, 1000µF, 275V, 2 for 50p.
Plessey Electrolytics, 4700µF, 63V, 3 for 80p.
TCC Electrolytics, 1000µF, 30V, 3 for 60p.
Plessey Electrolytics, 1000µF, 180V, 40p each (3 for £1).

Duobler Electrolytics, 5000µF, 35V, 50p each.
Duobler Electrolytics, 5000µF, 50V, 60p each.
ITT Electrolytics, 8800µF, 25V, high grade, screw terminals, with mounting clips, 50p each.
Plessey Electrolytics, 10,000µF at 63V, 75p each.
Plessey Cathodray Capacitors, 0-0.4µF at 12.5kV DC. Screw terminals. £1.50 each.

PLEASE ADD 12 1/2% VAT TO ALL CAPACITORS.

TV PLUGS AND SOCKETS
TV Plugs (metal type), 5 for 50p.
TV Sockets (metal type), 4 for 50p.
TV Line Connectors (back-to-back sockets), 4 for 50p. **Please add 12 1/2% VAT.**

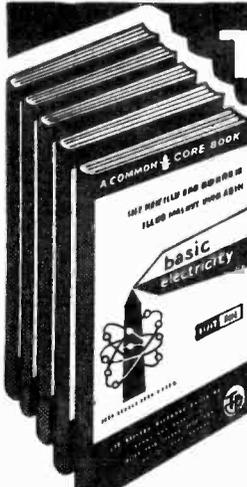Terms of Business: CASH WITH ORDER. MINIMUM ORDER £2. ALL PRICES INCLUDE POST & PACKING (UK ONLY). SAE with ALL ENQUIRIES Please. PLEASE ADD VAT AS SHOWN. ALL GOODS IN STOCK DESPATCHED BY RETURN. CALLERS WELCOME BY APPOINTMENT ONLY.



The Pictorial Method

BASIC ELECTRICITY (5vols) BASIC ELECTRONICS (6vols) BASIC TELEVISION (3vols)

You'll find it easy to learn with this outstandingly successful PICTORIAL METHOD. The essential facts are explained in the simplest language, one at a time, and each is illustrated by an accurate cartoon-type drawing. These clear and concise illustrations make study a real pleasure. The books are based on the latest research into simplified learning techniques. This easy approach-to-learning method has proved beyond doubt that acquiring knowledge can be an enjoyable experience.

YOUR 100% GUARANTEE

Should you be, in any way dissatisfied with the MANUALS your money will be refunded by return of post.

The Selray Book Co., 70 Hayes Hill, Bromley, Kent, BR2 7HP.

My blessings go with you for such splendid manuals available. P.S.J., Highgate

Thank you for a wonderful set of Books. I shall always be most grateful. S.P., Broadwater

Their simplicity is their attraction. P.J.S., Stowbridge

Your excellent manuals are the best and easiest to follow that I have come across. P.J.L., Mottingham

These manuals are away ahead of any others on the market. In one word I say 'par excellence'. 100% recommendation is my assessment of the outstanding qualities. B.W., Southampton

To The SELRAY BOOK CO., 60 HAYES HILL, HAYES, BROMLEY, KENT. BR2 7HP

Please find enclosed P.O./Cheque value £.....

BASIC ELECTRICITY 5 parts £8.00
BASIC ELECTRONICS 6 parts £9.50
BASIC TELEVISION 3 parts £5.00

Tick Set(s) required. Prices include Postage
YOUR 100% GUARANTEE. If after 10 days examination you decide to return the Manuals your money will be refunded in full.

NAME
BLOCK LETTERS

FULL POSTAL.....

ADDRESS

POST NOW FOR THIS OFFER!



AMATEUR BANDS

by Eric Dowdeswell G4AR

AN interesting letter from **Andrew Sharpe** G8MLM residing in Rowlands Gill (Tyne and Wear) who got his ticket last September at the grand old age of 15! His problem now is how to get on the air with a £1 a week pocket money! Unfortunately, Andrew has no local radio club nor local amateurs who might be able to help and it seems to me that he has been most valiant in struggling on his own thus far and passing the RAE. VHF gear can be a lot more complicated to build than for the HF bands so I have suggested to Andrew that he pass his morse code test and get on to the HF bands with a simple transmitter to start with. I am sure that all our readers will wish you well Andrew, but above all, don't give up!

On my suggestion **Eric Hill** of Bramley, Surrey, junked his pre-selector and noted 'a big decrease in noise'. He found 15m open for the States and Japan on the odd day or two and, like so many other readers, was glad to copy W6QL/VP2A on Antigua. QSLs to WA6AHF or via the Yasm Foundation, Box 2025, Castro Valley, California 94546, USA. **Don Waddell** found 80m to be the most interesting band on his FRG7 but says 'I'm too ashamed to mention my aerial!' With an FRG7 you should do as Eric Hill did and sell that pre-selector and spend the money on a decent aerial system!

The Hog's Back in Surrey was the scene of a small expedition when **Don Anderson** (Brookwood, Surrey) joined G8LVB operating there during a 144MHz competition. All this makes Don very determined to get the RAE at the first opportunity! Don belongs to the Farnborough and District Radio Society (the Hampshire one!) now happy with the call G4FRS and their first QSO was with founder member G2DX! This must be a record because they were probably the oldest and newest call signs at the time! Write to their Sec. Chris Beezley G4FEA at 152 Westheath Road, Farnborough, Hants if you want to join in the fun and games, or simply look in on the Railway Enthusiasts Club, Access Road, off Hawley Lane, Farnborough on the second and fourth Wednesday of the month around 7.30pm.

Derek Gilbert and **Ian Horwill** seem to share the same receiver in Farnham, Surrey and they were duly puzzled by the N prefix that popped up on the bands in recent times. Just our old W friends again I'm afraid. Consultation of the Geoff Watts' Prefix-Country-Zone list would have sorted that one out pretty quickly so if you send 35p to 62 Belmore Road, Norwich you too can have all the answers

at your fingertips! **BRS37901** sent in a list of DX heard on 20m sideband but omitted his QTH but would seem to be around Bournemouth. Rx is an AR88 and that's all I know!

One reader, who wishes to remain anonymous, was able to get a 9R59DS from another reader of this column and in consequence very kindly handed over his R107 to an RAIBC member in Bolton which should help an ill, 69-year-old widower to be very happy. I hope that Mr. Anon will now be able to send in some reports in future! Incidentally, anyone who feels like contacting the RAIBC should write to Sec. **Harry Boutle** G2CLP 14 Queen's Drive, Bedford. Regular **Robin Bayley** (Shifnal, Shropshire) has been experiencing QRM from a washing machine but since he's using only a few feet of wire round the shack this is hardly surprising! I think that your EC10 would benefit from a decent length of wire outside and screened feeders Robin, and thus make a good log even better. I was delighted to hear from **Albert Allnutt**, otherwise G4CQK, from Walton-on-Thames, Surrey who, seeing my review of the Heathkit HW8 QRP transceiver, reported his best DX to date with the same rig, as W4AIZ in Florida, using about 2½ watts on the 15m band. His aerial is an end-fed wire 116ft long most of which is only 25ft above the ground. Much more fun than when using 150 watts and a multi-element beam!

B. Harrison continues to mystify us from Hastings by not revealing his/her first name! Since the log is written on one of my log sheets I can't sniff it to detect any perfume! One log entry is F08GP on Clipperton Island on 80m so he/she knows a thing or two! **Paul Cowburn** is about the only correspondent who ever makes a note of stuff heard on CW. He doesn't profess to be much good at it yet but manages call signs and reports. Now this is where Paul is very clever because he records it all on tape and plays it back at leisure to see what he has missed. Full marks for ingenuity OM! I would advise any reader who normally sticks to the relatively easy job of copying SSB to have a listen round the LF end of the bands for some of the very attractive DX to be found there on CW. It's not all 25wpm by any means!

Now for a personal request. I would very much like to borrow a copy of the manual for the venerable 'Calibrator, Crystal No. 10', for statting and return immediately. Any help would be very much appreciated.

The Wessex Amateur Radio Group seems to be a well organised bunch of people judging by the excellent newsletter received from Hon. Sec. **Geoffrey Cole** G4EMN. Meetings are normally held at the Club Room, Dolphin Hotel, Holdenhurst Road, Bournemouth but Friday 20 May is going to be something special. 'Dud' Charman BEM G6CJ is giving his now famous lecture on Aerials plus Ken Alford G2DX who will talk about the early days of wireless. The meeting starts at 7.30 sharp at Bournemouth School, East Way, Bournemouth on this occasion. Knowing both of these characters quite well I can assure any potential visitors that it will be an evening to remember. The Group has a 4m FM net on 70·26MHz with several stations on permanent watch. A net operates on Sundays on 10m or 28·575MHz to be precise. Info on the many other club activities from Geoff at 6 St. Anthony's Road, Bournemouth.

Paul Barker is still trying to get an SSTV picture from Oceania to complete all continents. To date 51

countries have been 'seen' so he shouldn't be too far off achieving this ambition. Paul, in Sunderland I should add, comments on the pictures from YU3NAW which he compares to 'closed circuit stuff'. What annoys me Paul, are the appalling hand-drawn captions used by many SSTV stations. After having probably spent a lot of money and a great deal of time to get on SSTV the whole effort comes up as a scrawl with a rough paintbrush on an odd bit of card! Surely a decent bit of artwork could be prepared for the callsign and name at least.

Log Extracts

D. Hallgarten:— 15m W7AO ZP5LX ZS6BNH 20m A4XGX A6XB FR7ZL/T

P. Barker:— 20m SSTV EA5HH HA5KBM 15WC IT9DQZ K1CUW K4TGC LZ1MH OH5RM OK1JSU YU3NAW

P. Cowburn:— 20m CW FY7AS **HI8MOG** KS6GN VP2SA 8P6BU 20m HI8SRH HL9VA HV3SJ VS5MC YB0ABO 5W1AB 6W8GM 80m CO2JA CP6EL JW7FD PJ8KG SV1DL VP2DAC W6QL/VP2A ZL2BT 160m CW EA8CR **IK4AMO** PY1RO YV1OB 4X4NJ

B. Harrison:— 15m FY7BB ST2SA 20m FG7XL 9D5D 80m FM7WS HI8LC SV0WT

R. Bayley:— 15m A2GCO JA9CM W7WPR 20m TG9FRJ 7Q7BA 40m CT2AP EA9CR 80m A4XVK FP8DX HK0COP KH6PP KW6OM 9J2WR

R. Thomas:— 20m ZL2BIU ZL3QN

D. Waddell:— 15m VP9PC WB6EWH/VQ9 9X5SM 20m CW FM7AV **HI8MOG** KG4JS VP2EE VP9HT 20m C21PZ JW7FD VE8ML ZL4BX 80m JW9WT VS6DO ZD8EW

All SSB except those in bold which are CW.

BROADCAST BANDS

MEDIUM WAVE DX

by Charles Molloy

ONCE again, Transatlantic DX dominates the scene on the medium waves with reports coming in from a number of readers of some really good DX. **Michael Tallent** in Stafford heard CJCA Edmonton, Alberta on 930 kHz with a Realistic DX160 and 300ft long wire while **Harold Emblem** in Mirfield logged CFAC in Calgary on 960 at 0035 on March 3rd using his Eddystone 740 and loop. DX from the Canadian Prairies is only heard in the UK when conditions are exceptional and both stations are very fine catches indeed. The story repeats itself further south, the more exotic type of DX from the United States being reported. An outstanding log from **Gordon Darling** in Reading, who uses a Marconi AD7009 and 34in loop, includes KOMO in Seattle on 1000kHz at 0415, KFBK Sacramento, California on 1530 at 0304, WCCO Minneapolis on 830 and WSM Nashville, Tennessee on 650.

DXing on the medium waves, which is better now than it has been for over ten years is attracting the attention of enthusiasts in other branches of the

radio hobby. **Roderick Clews** (G3CDK) in Wallington, Surrey has been trying the medium waves with his newly-constructed loop and Hammarlund SP600 JX. He reports hearing 16 North Americans including KMOX in St Louis on 1120, WSB Atlanta, Georgia on 750 and KDKA Pittsburg on 1020. He mentions that the positioning of the loop appears critical to avoid mains borne QRM, a tip worth noting. Regular reporter **Derek Taylor** of Preston uses a Realistic DX160 and 48in. loop in his maisonette which is surrounded by large blocks of flats. In spite of this apparent disadvantage he pulled-in WJR Detroit on 760, WGY Schenectady on 810 (well known to old timers), WBAP Fort Worth, Texas on 820, WHAS Louisville, Kentucky 840, WWL New Orleans on 870 (close to AFN on 872), WOWO Fort Wayne, Indiana on 1190 and WOAI San Antonio, Texas on 1200. **F. A. Ainslie** in Hartlepool used his home-brew receiver to dig out WLW Cincinnati on 700, CBL Toronto 740, WLS Chicago 890 and WHO Des Moines (seldom heard in the UK) on 1040.

A home-built Aerial Tuning Unit (ATU) is used to peak-up the signal between **Clive Barwood's** 75ft long wire and an Ecko Mariner 4-valve receiver. Stations logged from his QTH in Grimsby are CBT Grand Falls on 540, WABC NY on 770, WGAR Cleveland 1220, St Pierre et Miquelon (near Newfoundland) on 1375 and WQXR NY on 1550. **Howard Hughes** writes from Crosby near Liverpool "I recently purchased a National Panasonic portable radio, which, within two days, yielded seven stations from the North American continent". These were CKVO on 710, CHNS 960, WINS 1010, WHN 1050 WNEW 1130 and inevitably, CJON on 930. Although winter is the season for North American DX it is possible to hear the east coast of Canada and the United States in mid-summer, during the hour before sunrise. QRM from Europe is minimal at this time which is a great help to the DXer who has neither a loop nor a communications receiver.

Those who are reluctant to get out of bed in the middle of the night need not abandon the medium waves, as there are a number of Africans to be heard after sunset. Listen for Gambia, with African style pop music on 648kHz after BBC Radio 3 on 647 closes down. Ougadougou in Upper Volta on 746 was logged recently by the writer at 2330 with African music and French announcements. Dakar in Senegal is generally a good signal, in French on 764kHz after Beromunster on the same channel signs off. Enugu, Nigeria on 1320 can be heard in English as a weakish signal before it goes off at 2305 and Conakry, Guinea on 1402 is usually strong after 2300, the announcements being in French. Two interesting loggings reported by **Joachim Gutschke** of Aurich-Sandhorst, West Germany are Radio Lages in the Azores on 650 and Radio Las Palmas in the Canary Islands on 953kHz.

PW reader **Siegfried Morgenrood** who lives in Cape Town uses an old domestic receiver, a Schaub Lorenz Viola, and a 10 metre long wire for DXing on the medium waves. With this set-up he heard the BBC Far East Relay in Oman on 1410kHz, Radio Antilles, Montserrat on 930, Voice of Peace, on board ship somewhere in the Red Sea, on 1540 and WCBS 880, WINS 1010, WBZ 1030. All of these can be heard in the UK, too.

The rig required by the MW DXer depends very much on the QTH. In places where interference and electrical noise are light, then a simple receiver and an outdoor aerial will give good results. The

SWL'S—YOU OWE YOUR RX A GOOD ANTENNA!

The World-famous JOYSTICK VFA (Variable Frequency Antenna) SYSTEMS continue to prove their worth in many amateur stations world-wide and in Government communication. Tunes continuously 0.5/30-00 MHz. and can be installed in any location. Comes in easily assembled form, carriage paid, VAT included. Glowing testimonials from many users on our files.

SYSTEM 'A' £36.00

SYSTEM 'J' (improved 'Q') £42.60

PARTRIDGE SUPER PACKAGES

Complete Radio Stations for any Location
All Packages feature the World Record Joystick Aerial (System 'A') with 8' feeder, all necessary cables, matching communication headphones. Deliv. Securicor our risk. ASSEMBLED IN SECONDS! BIG CASH SAVINGS!

PACKAGE No. 1 As above with R.300RX £210.55
SAVE £17.28!

PACKAGE No. 2 Is offered with the FRG7 RX. £193.11
SAVE £12.21!

PACKAGE No. 3 Here is a lower-price, high-quality package, featuring the all-solid state SMC 73 Rx., with all the Partridge extras. SAVE £154.86
£17.28!

RECEIVERS ONLY, inclusive delivery, etc.
R.300 £184.50 FRG7 £162.00 SMC73 £128.81

For further details, send 8½p stamp. You can phone your Access or Barclaycard number, ring 0843 62535 (or 62839 after office hours).

Box 5, Partridge Electronics Ltd.

Partridge House, Prospect Road, Broadstairs, CT10 1LD

G3CED (Callers by appointment) G3VFA



4½in x 3¼in METER. 30µA, 50µA or 100µA. £4.78. P. & P. 16p.

MICROPHONES FOR TAPE RECORDERS

DM228R 200 ohm with 3.5 & 2.5mm Jack Plugs £1.30

DM229R 50K with 3.5 & 2.5mm Jack Plugs £1.60

DM18D 200 ohm with 5 & 3 pin DIN plug £1.75

Postage on above microphones 11p.

CARDIOID DYNAMIC MICROPHONE

Model UD-130. Frequency response 50-15,000c/s. Impedance Dual 50K and 600 ohms. £7.55. P. & P. 26p.



42 x 42mm METERS 1mA, 10mA, 100mA, 500mA. £2.92, 11p P. & P.

60 x 45mm METERS 50µA, 100µA, 500µA and 1mA VU METER £4.13, 13p P. & P.

EDGEWISE METERS, 90mm x 34mm, 1mA £3.40, 13p P. & P.

MULTI-METER

Model ITI-2
20,000 ohm/volt, £10.05.
P.&P. 24p.



3 WATT STEREO AMPLIFIER
1½W PER CHANNEL
£4.30. P. & P. 13p.

All above prices include V.A.T. LARGE S.A.E. for NEW LIST Special prices for quantity quoted on request.

M. DZIUBAS

158 Bradshawgate · Bolton · Lancs. BL2 1BA

Your free start to a rewarding new hobby.



Heathkit make the world's largest range of electronic kits.

Including amateur radio, test equipment, educational and general interest kits.

Every one of which comes to you absolutely complete—right down

to the last nut and bolt.

You'll also get a very easy to understand instruction manual that takes you step by step through the assembly.

So, besides making an attractive, useful piece of equipment, you'll also have the makings of a satisfying, rewarding hobby.

To find out more, post the coupon and we'll send you our latest catalogue. Heath (Gloucester) Ltd., Dept. PW-67, Bristol Rd., Gloucester, GL2 6EE. Tel: Glos (0452) 29451.



HEATHKIT

BETTER BUILT BECAUSE YOU BUILD IT YOURSELF

The new Heathkit catalogue. Out now. FREE.

To: Heath (Gloucester) Ltd., Dept. PW-67, Gloucester, GL2 6EE. Please send me my Heathkit catalogue. I enclose an 11p stamp for postage.



Name _____

Address _____

Postcode _____

ACCESS AND BARCLAYCARD WELCOMED

Showrooms at 233 Tottenham Court Road, London and Bristol Road, Gloucester.



TRAMPUS ELECTRONICS LTD

58-60 GROVE RD.
WINDSOR, BERKS.
SL4 1HS.
TEL. 54525

ADD 8% VAT TO PRICES MARKED *
ADD 12% TO ALL OTHER PRICES.
OR AS CURRENT VAT LEGISLATION
SEND C.V.O. (EXCEPT GOV'T DEPT)
POST & PACKING 20P FOR THE U.K.
BARCLAYCARD & ACCESS BY POST
OR £5 MIN ON TELEPHONE ORDERS.
NEW CATALOGUE LIST FREE S.A.E.
MONEY BACK IF NOT SATISFIED.

FAST SERVICE

ON EX STOCK ITEMS
NORMALLY 24 HOURS



SEVEN SEGMENT LED DISPLAYS
BRIGHT DL707 COM ANODE &
DL704 COM CATH. 0.3" £1*
DL747 0.6" JUMBO CA £1.25*

DIGITAL CLOCK IC 51224 £4*
ZENON STROBE TUBES £4 & £7*

RED LEDS JOP.

RED LEDS 209 STYLE 0.125"
OR 0.2" DIA. NO CLIP 10p*

TIL209 RED LED & CLIP 12p*
BIG 0.2" RED LED & " 14p*
GREEN OR ORANGE LEDS 29p*
ORP12 54p*2N5777/OCF71 34p*

TRAMPUS
THE GREAT
BRITISH
DISTRIBUTOR



INDUSTRIAL, EDUCATIONAL, TRADE
& EXPORT SUPPLIED, SEND FOR
OUR FREE CATALOGUE LIST SAE
MANUFACTURERS EXCESS STOCKS
PURCHASED. DISCOUNTS 10% OFF
100 sp. 15% OFF 1000 up....

TOP DISCOUNTS.

INTEGRATED CIRCUITS

555 TIMER	34p*	LM380(60745) £1	
556 2 x 555	90p*	LM391 Preamp £2	
703 REF/IMP AMP	23p	LM3900 4XOPA 53p*	
709 T099 or DIL28p		MC1303 2xPre £2	
710 DIL14	35p*	MC1310 stereo£2	
723 Regulator	44p*	MC1312P SQ £1.70	
741 DIL 8pin	21p*	MC1330	75p
741 DIL 14pin	31p*	MC1339 Preamp£2	
741 T099	33p*	MFC4000B IW 72p*	
747 DUAL 741	60p*	MFC6030 £1	
748 DIL 8 pin	32p*	NES36 PETOPA £2	
7805 5V1A+reg£1.35*		NE540 or 550 £2*	
7812 & 7815ea£1.40*		NE555 TIMER 34p*	
78013 2W AF £1.50		NE556 2x555 90p*	
AY51224 CLOCK £4*		NE560/1/2/5/6/7/3	
CA3046	54p*	SN7241 as 741	
LM3008 Sigen £4*		SN7660 IF 74p	
LM3011	£1*	SN76611 IF £1	
LM301A DIL 8	33p*	TBA800 5W AF 84 p	
LM309K 5V reg £2*		TBA810 7W AF 94p	
LM309H T05 can £1*		ZN414 Radio £1.19	
LM318 70VuoOPA £3*		NEW 1466/69 £4	

CMOS TTL

4000 14p*	7400 12p*	7490 39p*
4001 15p*	7401 13p*	7481 75p*
4002 16p*	7402 15p*	7482/93 45p*
4007 16p*	7404 19p*	7485/96 72p*
4009 50p*	7408/10 18p*	74100 £1.25*
4011 16p*	7413 29p*	74107 32p*
4012 17p*	7440 16p*	74121 29p*
4049 50p*	7441 71p*	74123 69p*
4069	7442 72p*	74141 74p*
4501 26p*	7447 79p*	74145 85p*
4511 £1.85*	7470/72 27p*	74147 £2.50*
4528 £1*	7473/74 31p*	74151 75p*
4543 £2*	7475/36 35p*	74154 £1.40*
4553 £5*	7486 35p*	74196 £1.50*

DIL SOCKETS PROFESSIONAL QUALITY
8pin, 14pin & 16pin ALL 12p ea.*
SOLDERCONS 100 49p* 1000 £3.95*

NEW LOW PRICES.

TRANSISTORS AND DIODES

ZNS BUSH SET 5p ea*	TIP31/32 50p*		
WATCHDOG 20p Pr*	TIP31c32668p*		
AC127/8 176 15p*	TIP41/42ea 66p*		
AD161/162 ea36p*	TIP41c42c"£1.50*		
BC107	8p*	TIP2955	69p*
BC107B	13p*	TIP3055	65p*
BC108	8p*	TI843 UJT	26p
BC108B or C 13p*	IN914/4148 4p		
BC109	9p*	1N4001/2	4p*
BC109B or C 12p*	1N4004	5p*	
BC147/8/9	8p	1N4007	7p
BC157/8/9	11p	2N706/8	14p
BC167/8/9	12p	2N2646 UJT	40p*
BC177/8/9	16p	2N2904/5Pnp29p*	
BC182/3/4a/110p	2N2926 ory 7p		
BC212/3/4a/112p	2N3053 17p		
BCY70/1/2 15p*	2N3055 90W 33p*		
BD131/152ea 36p*	2N3055 115W45p*		
BFY50/51 15p*	2N3614 T03 £1*		
BFY52/53 16p*	2N3702/3/4 10p		
BSX 19/20/2119p*	2N3705/6/7 9p		
BZ788 ZENER 10p	2N3708/9 9p		
C106D SCR 54p*	2N3710/11 15p		
MJ2955 T03 95p*	2N3819 £2317p		
MJE2955 99p*	2N3820 PPET40p		
MJE3055 65p*	2N3904/5/6 15p		
OA81/91 5p	2N5457 FET 32p		
TIP29 & 30 40p*	BRIDGE1A50 20p*		

BARGAIN PAKS FULL SPEC 1ea.

PAK A: 11 RED LEDS Full spec 1*
PAK B: 5 741C 8 PIN OP AMP 1*
PAK C: 4 2N3055 £1 D 12 BC109 1*
PAK E: 11 BC182 £1 F 11 2N3704 £1
PAK G: 7 BFY51 £1* H 8 2N3819 1*
PAK J: 6 2N3053 £1* K 40x1N914 £1
PAK M: 3 T099 3055 £1* N 25 OA811*
PAK P: 20 PLASTIC BC109 TYPBnp11

10-365PF TUNER SINGLE GANG FOR
MED/SHORT WAVE, XTAL SET etc £1*
SET3/IF CANS 455/470KHZ TOKO £1*

Full spec devices

DALO pen 75p

PCB ETCH KIT 3 ITEMS £2*
ETCH RESIST PEN 2TIPS 75p*
FEC ETCH PAK TUB 600gm 1*
6x4" SRBP 45p*NYLON F/G11*

SCR AND TRIACS BR100 25p*
TAG 1A400V 50p*1A600V 63p*
1A50V 37p*.C106D 4A400 60p*
TRIACS-SCI46D 10A400V £1*
DISCO TRIAC 15A400V £2*

AUDIBLE WARNING BLEEPER
12V35mA £1, 2010 0.1" £1*
CAPACITORS 22pf - .01 5p
ELECTROLYTIC 1N 10 & 25V
1/2/10/50/100 7p 50p 10p
200/500 10p, 1000/25 20p

POTENTIOMETERS AB etc20p
PRESETS 6p WRESISTORS 2p
HEATSINKS T05 or 18 7p
T03 16p, T03 4"finned 50p
DIN-PLUGS all 15p, Sock 10p
SWITCHES SPST 20p Dpdt 29p

GAS DETECTOR Tgs 308etc4*
vero
VERO 0,1" PITCH COPPERCLAD
2 1/2"x5" 40p* 3 1/2"x5" 45p*
2 1/2"x3 1/2" 36p* 3 1/2"x3 1/2" 40p*
3 1/2"x1 7/8" £2 FACE CUTTER 65p*
DIL BREADBOARD 2"x4" £1 or
6"x4" £2, VERO PINS 36 30p*

BLACK PLASTIC CASES 42mmx.
80x60 50p*100x75 60p*99x
120 70p, DESOLDER BRAID 50p

FANE SPECIALIST RANGE SPEAKERS

Each designed to produce the individual sound
requirement for its purpose. Robust Cast Aluminium
Chassis 12" models 80w RMS Rec. Price



12" DISCO/80	Linen Cone Surround	£27.95
12" GUITAR/80L	For Lead Guitar	£25.75
12" GUITAR/80B	Prs. rec. for Bass Guitar.	£26.95
12" PA/80	For general purpose P.A.	£25.95
15" BASS/85 85w	For Bass	£39.95
15" BASS/100	For Bass Guitar	£42.00

FANE 'POP' RANGE SPEAKERS

12" POP 33T 33w	£14.95
12" POP 50/2 50w	£16.99
12" POP 55/2 65w	£22.95
15" POP 60 60w	£25.95
15" POP 70 75w	£29.95
18" POP 100 100w	£46.95

DISCO '80'

HIGH FREQUENCY HORNS

J44 Range: 2-5KHz-15KHz
Power: 50w with HPX2

HPX2 30w with HPX1
Imp: 8 ohms
Size approx 3 1/2" x 3 1/2" x 3" £7.95


J104 Range: 2KHz-15KHz
Power: 50w with HPX1
Power: 70w with HPX2

HPX1 8 ohms
Size approx 10 1/2" x 3 1/2" x 7" £16.95

HIGH POWER 'CROSS-OVERS'
HPX1 (3-5KHz)
HPX2 (5KHz) £2.99

Impedance or total impedance of
Bass Drivers not to exceed 8Ω
Otherwise use series Horns or
attenuation.
Distributors (Wholesale & Retail)

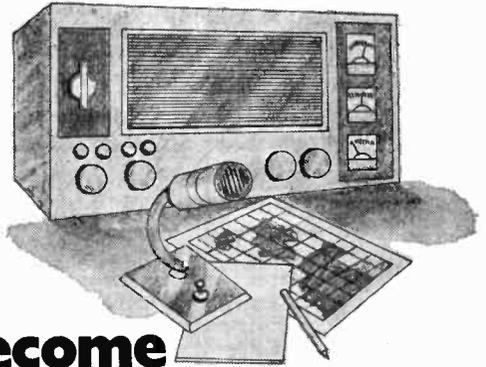LINEAR PRODUCTS LTD, ELECTRON WORKS, ARMLEY, LEEDS.
Manufacturers & Export enquiries to:-
FANE ACOUSTICS LTD, 286 BRADFORD ROAD, BATLEY, YORKS.



Become a radio amateur.

Learn how to become a radio-amateur in contact with the whole world. We give skilled preparation for the G.P.O. licence.

Free!

Brochure, without obligation to:

BRITISH NATIONAL RADIO & ELECTRONICS SCHOOL,
P.O.Box 156, Jersey, Channel Islands.

NAME _____

ADDRESS _____ (Block caps please)

DXer who lives in a country district in the north west of the UK should do well with such a set-up. The city dweller in the south however, will find it an advantage to construct a medium wave loop and to use it with a receiver which has a high degree of selectivity, such as a communications receiver.

Reports of Long wave DX seldom reach this column, which is a pity as this band, which has an attraction of its own, can produce surprises at times. That part of the spectrum between 151kHz and 281kHz is used for broadcasting by Turkey, Mongolia, Asiatic USSR, Morocco and Algeria as well as by a number of European countries. **Martin Mann** of Cambridge thinks that there may be others like himself who are attracted by the challenge of DXing on the longwaves and he reports hearing Morocco in Arabic on 209kHz, Algeria on 251 with the Voice of the Free Canary Islands, in English at 2200 and Minsk on 281. Algeria has a daily programme in English on 251 from 1900 until 2000.

Propagation on the long waves is similar to that on the medium waves. After dark the signal is refracted by the ionosphere and this is the time to look for DX. The groundwave travels much further on the LWs than on the MWs while the skywave can travel a considerable distance. Allouis in France on 164 has been heard in Australia and Europeans are heard regularly in the United States. New-comers to the longwaves might try for Reyjavik on 209 at midnight on a Saturday night when the station gives a weather report before signing-off. Others to hunt for are Ankara on 182, Oslo on 218, Lahti Finland on 254 and the out-of-band Oulu on 433kHz which is in parallel with Lahti.

Finally, a mystery station on 534kHz. Every night at 2100 a carrier comes on followed shortly afterwards by a programme of music which continues until 2120 when the transmission ends. Occasionally there is a very short announcement in an unidentified language. First reported by Ralph Newman in Reading it has been heard several times by the writer. The direction appears to be from the north of Reading and Southport!

Portuguese stations can be contacted using this dictionary.

Among the rarely logged stations that Roberto reports are the following:-

Radio Guaibia on 11795 at 2235
Radio Rio Mar on 9695 at 0100
Radio Relogio on 4905 at 0010
Radio Margarita on 1020 at 0100


It is nice to know that in this present sunspot minimum we have at least some DX to hunt. Long time readers of this column, and there are some for which I give thanks, will remember that I have always had a moan about the fact that Latin American were never keen to reply to QSL reports. This is with some justification since I have written no less than eleven letters without reply. It seems now that I may have omitted to include International Reply Coupons. **Lawrence Bennet** from Bristol has done just this and says he has had a pennant from Ecos Del Torbes logged on his Trio 9R plus 66ft long wire with ATU. Lawrence has a preference for early and bright listening getting up at around 0600 to tune the 60m band and he says that fadeout is around 0800. It seems unusual that a commercial station should only reply for an IRC but if that is the case then I might well try again. Also in the list are the following:-

Radio Bolivar on 4860 at 0600
Radio Santa Fe on 4965 at 0800
Radio Bolivar on 4770 at 2330
Radio Reloj on 4823 at 0700
Radio Continente on 5030 at 0830

There is a club just starting in the Bristol area for which Lawrence would like a mention and this column is only too pleased to oblige. The Bristol Pathfinders DX Club is one of those rare groups that asks no membership fee! Lawrence Bennet, 7 Maple Ave., Fishponds, Bristol is the address to contact although Lawrence gives no indication as to what is given from the club to the member for his free membership.

This column seems to cater for all tastes, or should I say that the radio stations reported do so. Those of us that are interested in outer space are advised to tune to the shows that are put out by Voice of America. **Peter Jones** of Abertillery, Gwent, reports that this station is giving away wall charts, photographs and decals of the American space shots. They have been conducting a quiz on the "Breakfast Show" about the space shots and ever eager to distribute information.

The new copy of WRTVH is on the market it seems, although I have not seen one. **Marcus Duncan** however has and comments that it seems unreliable. He looked for Voice of Greece on the indicated 9608 and found that they were on 9760. I will say that this massive tome is subject to the whims of the broadcasters who change freqs. in order to get the best propagation dependent on the particular year's trend. The Thornaby-on-Tees QTH of our Marcus is quite a mine of information as he reports that Radio Nacional Brasilia has changed its call sign to ZYF263 from the old PRL8 with an address reported as PO Box 04/0340, Brazilian Federal District, Brazil and its DX show to a weekly Friday session at 2115. With that I will close down and wish you and yours best 73s.

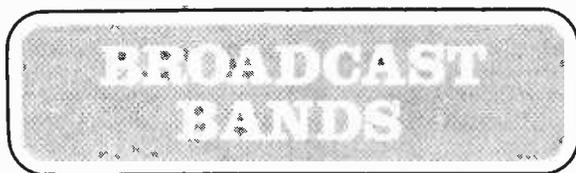


SHORT WAVE BROADCASTS

by **Derek Bell**

HANDS up all those who feel that there are gaps in their log books that could be filled by the inclusion of a few Latin American local stations! Now, hands down and grab a pen and paper. **Roberto Levinstein** of 39 Coniston Road, London N10 is offering to supply for a stamped addressed envelope a DXers guide to Brazilian stations in the form of a two-sheet A4 size English-Portuguese dictionary.

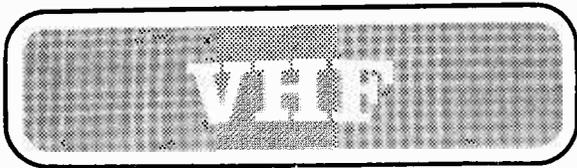This fact-packed broadsheet covers most aspects of DXing with translations of a mass of words needed when writing to Portuguese speaking countries. Alongside the technical terms is a proforma letter for a QSL and as Roberto, who is himself a Latin American, point out some African and



by Ron Ham

THERE is a great deal of enjoyment to be had and a lot of knowledge about propagation to be gained by listening in, or taking part in the RSGB VHF/UHF contests" so said your scribe in our April issue which arrived on the bookstalls as VHF enthusiasts were gathering the main ingredients for this month's feature.

Early on February 26 the atmospheric pressure went above 30·0in for the first time in three weeks and by midnight it was at 30·2in where it stayed for 24 hours, taking off again to reach 30·5in by noon on the 28th. Once the AP was around 30·2in the VHF's were vulnerable and the first report of a disturbance came from **Alan Baker**, G8LGQ, Newhaven who worked G8KCP in Coventry on 2m during the morning of the 27th and also heard stations from DJ, PA0 and ON. In the late afternoon of the 28th, **Richard Lambley**, G8LAM, London, received strong signals from the AFN stations in Brussels (100·8MHz) and SHAPE HQ (101·5MHz) using his Leak Stereofetic receiver fed by a Jaybeam JBFM9S aerial.

What goes up must come down and around 1130 on March 2, while the AP was steadily falling, Alan Baker sat in his car on Devils Dyke, Brighton, with a 5/8 λ magnetically mounted aerial on the roof and calmly worked DB5PQ, HB9MUS, HB9MYQ/P, HB9FT, and HB9BDM via the Swiss repeater (HB9F2, Pizgloria, R4) and later he worked French stations via the Paris repeater (F6AXV on R6). For most of the morning your scribe received a strong picture from Lichfield on 189MHz, several continental broadcast stations in Band II and 569 signals from the 70cm beacons GB3EM and GB3SC; in each case only a dipole was used to feed the receiver.

From midday on the 2nd until early morning on the 4th, the VHF's were "quiet" and then the AP, down at 30·1in, turned upward sharply and by midnight it was at 30·5in and, a fortunate coincidence, it began to fall around 0800 on the 5th producing a tropospheric opening which reached it's climax during the 2m contest on the 5/6! **Joost Berden**, G3RND, Isle of Wight, sent a copy of his barograph chart covering the period Feb 28 to March 6, showing that his AP trace was almost identical to mine, and so was the chart used by **George Zitterstein**, G8ITS, City of London.

For most of the week Joost noticed that signals on 2m were better than usual and during the afternoon of the 5th he observed a "lift" toward the east but the signals were very unstable; however the opening between 10-1600 on the 6th was more positive both in easterly and westerly directions. Around 2000, Joost heard the Emly Moor beacon (GB3EM) on 70cms for about an hour. **John Wilson**, G8KIS, Amersham, only contested for half an hour during the evening of the 5th and worked a portable station on Dartmoor, an ON, a GC and was amazed to work into northern G over 450ft of local hills. This whole event seemed to have a variety of effects on propagation over different areas, for instance, G8ITS said

that from his impossible VHF location he worked 126 stations during the contest and made a special point of the fact that conditions varied between the two days. His best DX came on the 6th when he worked a station on the Franco/German/Swiss border at 750km.

During the contest, G8LGQ, using SSB worked GW, HB9, ON, PA0, F, DB, DC, and Midland G, and noticed, as did G8ITS, G8KIS and your scribe, that GW stations were often strong enough to be heard off the back of the beam. G8LGQ heard from another amateurs that GI, GD, and GM had been worked from Sussex, and I heard one station say "it was a fantastic contest" and another said that some French stations had more than 1000 contest QSOs.

From late on the 5th to midday on the 7th, strong signals were received via my dipole from both GB3SC and GB3EM which was consistent with the co-channel interference on Band V TV and a report that a close neighbour of G8LAM received a solid colour picture from a West German UHF TV station. A similar theme was reported by **Des Walsh**, EI5CD, who says "In this region of south-east Ireland there is a very low density of amateur VHF/UHF activity and the terrain requires much ERP to beam over the mountains", however, things were different on the 5th and 6th when British UHF TV signals were pounding in to EI along with some Band III 819-line TV signals from France.

Nigel Golds, BR36910, West Chilmington, Sussex has been operating VHF radio equipment in the Storrington ATC Squadron and now has his own AR88D installed at home and keeping a special watch for those 10m beacons while he swots for his RAE. Although the 10m band has been dead, signals from the Cyprus beacon (5B4CY), peaking 599, were heard at 1007 on the 10th and 1027 on the 16th. On March 8, **Cmdr. Henry Hatfield**, Sevenoaks, using his spectrohelioscope, observed two active regions on the east limb of the sun and on the 9th and 10th both Henry and myself recorded solar radio noise at 136MHz. To date, the only effect from this event that we know of is the ionospheric disturbance which was reported by the BBC World Service during the early hours of the 10th. **George Zitterstein**, G8ITS found the 70cm contest on March 20 rather flat although he did manage to work 100km into Newbury using only 3 watts.

My sincere thanks for your letters and reports and I hope to meet some of you at Alexandra Palace on May 7th when, in the afternoon, I will be in the chair for Dud Charman's aerial lecture.

BROADCAST BANDS

Short Wave Reports by the 15th of the month to **Derek Bell**, 169 Max Rd., Chaddeston, Derby.
Medium Wave Logs to **Charles Molloy**, 132 Segars Lane, Southport, PR8 3JG.

AMATEUR BANDS

Logs covering any amateur band/s in band/ alphabetical order by the 25th of the month to **Eric Dowdeswell G4AR**, Silver Firs, Leatherhead Road, Ashted, Surrey, KT21 2TW.

VHF

Reports on VHF matters to **Ron Ham**, Faraday, Greyfriars, Storrington, Sussex RH20 4HE.

This is Stirling Sound's price bombshell!

NO MORE V.A.T. & POSTAGE PROBLEMS

+ NEW DIRECT FROM FACTORY DELIVERY SPEED-UP Another FIRST for Stirling Sound—B.P.P



Why worry any more about working out V.A.T. (12½% on £4.87 plus 8% on £3.39* plus 85p for p/p, or should it be 54p?) We do it for you. Just send your order with the advertised prices—we do the rest. The prices we give include V.A.T. at the appropriate rate and cost of postage and package. Buy at our shop in person and we deduct the postage charges automatically. This is not all. Now you send your orders direct to our factory (see below) where we make Stirling Sound products and send back your order from there even quicker—real time saving that! AND STIRLING SOUND PRICES REMAIN KEENLY COMPETITIVE ALL THE TIME maintaining the lead we took in 1959 by being first in the U.K. to sell bargain component packs. We've come a long way since then—with an exciting programme for the seventies we're going even further!

THE FACTORY

organised in the name of better service. Now our mail order dept. is right where the goods are made

THE SHOP

really 3 shops—audio showroom, component bargains, modules, etc. etc. Well worth a visit



YOU PAY THE PRICE YOU READ AND NOTHING MORE

subject only to (very rarely) there being a printing error or really vicious price rise in production costs. You're SAFE when you buy from Stirling Sound—the business that has grown on really understanding customers' needs and interests.

SPECIAL QUOTATIONS TO QUANTITY BUYERS.
U.K. & OVERSEAS TRADE ENQUIRIES INVITED.

BEST SELLERS IN OUR 1977 RANGE OF Q.V MODULES

The Power Amps

- SS.103 3 watt r.m.s. mono. Uses one I.C. protected against short circuit £2-33
- SS.103-3 Stereo version of above using two I.C.s £4-33
- SS.105 5 watts r.m.s. into 3 ohms, using 12V supply £3-49
- SS.110 10 watts r.m.s. using 24V and 4 ohm load £4-05
- SS.120 20 watts r.m.s. into 4 ohms, using 34V £4-61
- SS.140 Delivers 40 watts R.M.S. into 4 ohms using 45 volts supply unit such as SS.345. Ideal for small disco, P.A. etc. £4-99
- SS.1100 100 watts R.M.S. with heatsink mounting and built protection against short-circuiting £10-43
- SS.1100/H As SS.1100 but with full size heatsink £11-82
(Heatsink alone £1-39)

THE BARGAIN THEY ALL WANT!

IT'S THE SS.1100 100 WATT R.M.S. AMPLIFIER (£10-45) TOGETHER WITH SS.370 POWER UNIT (£14-63) plus full size heatsink for amp. (£1-39)

You pay **£24-25**

YOU SAVE £2-20!

(Items bought separately come to £26-45—see above)
Your chance to lay the foundations of a really powerful disco or P.A. assembly at a marvellous price. This guaranteed Stirling Sound triumph is built for real hard work, so why pay more?

8 POWER UNITS

AT VERY COMPETITIVE PRICES

Firstly, the range covers well over 65% of all constructors' needs. Secondly, with 13-15 volt take off points on all models except SS.312, you get a valuable bonus; thirdly, the stabilised models with variable outputs complete a range to suit almost all requirements.

- SS.312 12V/1A £6-35
- SS.318 18V/1A £6-54
- SS.324 24V/1A £7-27
- SS.334 34V/2A £8-31
- SS.345 45V/2A £9-98
- SS.350 50V/2A £10-35
- SS.370 70V/2A £14-63

SS.310/50 Stabilised power supply with variable output from 10V to 50V/2A. Built-in protection against shorting £16-69

SS.300 Power stabilising unit 10-50V adjustable for adding to unstabilised supplies. Built-in protection against shorting £5-02

GET MORE OUT OF YOUR CAR

with a STIRLING SOUND "SUPER SPARK" Mk5 electronic ignition unit. Adjustable for pos. or neg. earth. Simple rev. limiting control; on-off immobilising switch; switch for instant revert to normal ignition; neon indicator. In strong, totally enclosed metal box 16cm x 12cm x 10cm. 12 mchs. guarantee.

Complete kit of parts £10-28 Built & tested £12-44

Tone Control and Pre-amp Modules

- SS.100 Active stereo tone control, stereo. ±15dB on bass and on treble £3-00
- SS.101 Stereo pre-amp for ceramic cartridges, etc. Passive tone control details supplied. £2-33
- SS.102 Stereo pre-amp for low output magnetic P.U.s. R.I.A.A. corrected. With circuit for adding passive tone control £4-04

UNIT ONE

Combined pre-amp with active tone-control circuits. ±15dB at 10kHz treble and 30Hz bass. Stereo. Vol./balance/treble/bass. 200mV out for 50mV in. Operates from 10 to 16V supply. £9-00

UNIT TWO

As Unit One, but for magnetic pick-ups. For inputs 1 to 5 mV per channel. R.I.A.A. corrected. Adaptable to ceramic. Designed to genuine hi-fi standards £12-43

The F.M. Tuning Modules

- SS.201 Front end tuner, slow geared drive, two gang. A.F.C. facility. Tunes 88-108 MHz. £5-90
- SS.202 I.F. amplifier. Metering and A.F.C. facilities £3-46
- SS.203 Phase lock loop Stereo Decoder for use with the FM mono tuners. A LED may be fitted £4-19
- SS.203-1 Coil-type stereo decoder Neg. earth with I.C. £3-06 SS.203-3 Pos. earth £2-50

Every effort is made to ensure correctness of information at time of going to press

STIRLING SOUND DEPT. PW6,

37 VANGUARD WAY,
SHOEBURYNNESS, ESSEX
Telephone—Shoeburynness (0702-28) 5543

SHOP AND SHOWROOM
220-224 WEST ROAD, WESTCLIFF-ON-SEA,
ESSEX SS0 9DF
Open all day Saturday

MAIL ORDERS

Get a great deal from

Marshall's

A. Marshall (London) Ltd Dept: PW

40-42 Cricklewood Broadway London NW23ET Tel: 01-452 0161/2 Telex: 21492

& 85-West Regent St Glasgow G2 2QD Tel: 041-332 4133

& 1 Straits Parade Fishponds Bristol BS16 2LX Tel: 0272-654201/2

1977 CATALOGUE NOW IN STOCK PRICE 55p post paid (40p to callers)

Call in and see us 9-5.30 Mon-Fri 9-5.00 Sat

Our range covers over 7,000 items. The largest selection in Britain.

TOP 200 IC's TTL, CMOS & LINEARS


CA3029A	2.20LM380N	98pMC1350	75p76650N	1-10TBA700Q	1-41
CA3028A	1-01LM381A	2-45MC1351	1-2076660N	60pTBA720Q	2-30
CA3028B	1-29LM381N	1-60MC1352	97p76666N	92pTBA750	1-98
CA3030	1-24LM382N	1-25MC1357	1-45TAA310A	1-50TBA750Q	2-07
CA3080A	1-89LM384N	1-45MC1458	91pTAA320A	1-15TBA800	2-20
CA3045	1-40LM386N	80pNE555	53pTAA350A	2-48TBA810	1-16
CA3046	89pLM387N	1-08NE556	1-05TAA521	1-00TBA820	1-03
CA3048	2-23LM388N	1-00NE565	1-30TAA522	1-90TBA920	1-79
CA3049	1-66LM389N	1-00NE566	1-65TAA550	60pTBA920Q	2-99
CA3052	1-62LM702C	75pNE567	1-80TAA560	1-60TBA940	1-62
CA3053	60pLM709C	65p5A5560	2-50TAA570	2-30TCA160C	1-85
CA3080	68pLM709N	45p5A5570	2-50TAA611B	1-88TCA160B	1-61
CA3080A	1-88LM710C	60p5O42P	1-00TAA621	2-15TCA270	2-25
CA3086	51pLM710N	60p7600N	1-37TAA661B	1-32TCA280A	1-33
CA3088	1-59LM723C	85p76003N	2-55TAA700	3-91TCA290A	3-13
CA3089	2-52LM723N	75p76008K	2-50TAA930A	1-00TCA420A	1-84
CA3090	3-80LM741C	65p76013N	1-70TAA930B	1-05TCA730	3-22
CA310	94pLM741N	50p76013ND	1-57TAD100	1-95TCA740	2-76
LM301A	65pLM741-8	40p76018K	2-50TBA120	65pTCA750	2-30
LM301N	44pLM747N	90p76023N	1-70TBA400	1-50TCA760	3-18
LM304	2-45LM748-8	50p76023ND	1-37TBA500	2-21TCA800	3-13
LM307N	65pLM748N	90p76031N	1-46TBA500Q	2-30UAA170	2-00
LM308N	1-17LM1800	1-7676110N	1-87TBA510	2-21UAA180	2-00
LM309K	2-10LM1808	1-9276115N	2-06TBA510Q	2-30CD4000	20p
LM317K	3-00LM1828	1-7576116N	1-30TBA520	2-21CD4001	20p
LM318N	2-25LM3301N	85p76131N	1-94TBA520Q	2-30CD4002	20p
LM323K	6-40LM3302N	1-4076226N	1-94TBA530	1-98CD4006	1-10
LM339N	1-79LM3401N	75p76227N	1-51TBA530Q	2-07CD4007	20p
LM348N	1-91LM3900	75p76228N	1-75TBA530Q	2-07CD4008	97p
LM360N	2-75LM3905	1-6076530N	91pTBA540	2-21CD4008	97p
LM370N	3-00LM3909	68p76532N	1-50TBA540Q	2-30CD4009	37p
LM371N	2-25MC1035	1-7576533N	1-30TBA550	3-13CD4010	87p
LM372N	2-15MC1303	1-4776544N	1-44TBA550Q	3-72CD4011	20p
LM373N	2-25MC1305	1-8576545N	2-09TBA560Q	3-1CD4012	20p
LM374N	2-23MC1306	1-0076546N	1-44TBA570	1-2CD4013	87p
LM377N	1-75MC1310	1-9176550N	41pTBA570Q	1-38CD4014	1-01
LM378N	2-25MC1312	1-9876552N	65pTBA641Q	2-50CD4015	1-51
LM379S	3-95MC1327	1-8476570N	2-08TBA651	1-80CD4016	36p
LM380-8	90pMC1330	92p76620N	1-10TBA700	1-52CD4017	1-01

THIS IS JUST A SMALL SELECTION FROM OUR RANGE—PLEASE ENQUIRE FOR TYPES NOT LISTED

POPULAR SEMICONDUCTORS

2N696	35p	2N2907	21p	2N3791	3-10	2N6121	38p	BC107	15p
2N697	30p	2N2907A	22p	2N3792	3-50	2N6122	41p	BC108	15p
2N698	62p	2N2924	15p	2N3794	20p	2N6123	43p	BC109	15p
2N699	55p	2N2926	12p	2N3819	36p	2N6126	45p	BC113	17p
2N706	24p	2N3019	55p	2N3820	38p	2N6127	48p	BC116	19p
2N708	21p	2N3053	30p	2N3823	75p	40361	48p	BC118A	20p
2N709	50p	2N3054	60p	2N3904	21p	40363	48p	BC117	22p
2N718	27p	2N3055	70p	2N3908	22p	40406	58p	BC118	16p
2N718A	50p	2N3390	25p	2N4036	67p	40407	45p	BC119	30p
2N720A	80p	2N3391	25p	2N4037	55p	40408	65p	BC121	45p
2N914	35p	2N3392	16p	2N4058	20p	40409	65p	BC132	30p
2N916	30p	2N3393	15p	2N4060	20p	40410	65p	BC134	15p
2N918	38p	2N3394	15p	2N4061	17p	40411	2-85	BC135	15p
2N929	25p	2N3395	88p	2N4062	18p	40594	85p	BC136	19p
2N930	28p	2N3440	64p	2N4126	17p	40595	86p	BC137	14p
2N1131	60p	2N3441	85p	2N4289	20p	40673	73p	BC140	40p
2N1132	60p	2N3442	1-35	2N4919	65p	AC126	37p	BC141	50p
2N1613	35p	2N3638	16p	2N4920	70p	AC127	44p	BC142	30p
2N1711	37p	2N3638A	16p	2N4921	50p	AC128	37p	BC143	30p
2N1893	30p	2N3639	30p	2N4922	55p	AC151	35p	BC147	12p
2N2102	60p	2N3661	20p	2N4923	70p	AC152	50p	BC148	12p
2N2218	33p	2N3702	17p	2N5190	60p	AC153	49p	BC149	13p
2N2218A	37p	2N3703	16p	2N5192	75p	AC176	40p	BC153	27p
2N2219	30p	2N3704	15p	2N5195	90p	AC176K	60p	BC157	12p
2N2219A	32p	2N3705	16p	2N5245	35p	AC187K	55p	BC158	12p
2N2220	30p	2N3706	16p	2N5294	40p	AC188K	55p	BC159	11p
2N2221	22p	2N3707	18p	2N5295	40p	AD161	85p	BC160	50p
2N2221A	26p	2N3708	16p	2N5296	40p	AD162	85p	BC161	50p
2N2222	23p	2N3709	18p	2N5298	40p	AF106	55p	BC167	12p
2N2222A	25p	2N3710	16p	2N5447	18p	AF109	75p	BC168	12p
2N2368	25p	2N3711	18p	2N5448	15p	AF124	65p	BC169	12p
2N2369	25p	2N3712	1-20	2N5449	19p	AF125	65p	BC170	16p
2N2369A	25p	2N3713	2-30	2N5457	22p	AF126	65p	BC171	14p
2N2646	78p	2N3714	2-45	2N5458	33p	AF127	65p	BC172	12p
2N2647	1-40	2N3715	2-85	2N5459	29p	AF139	69p	BC177	20p
2N2904	36p	2N3716	2-30	2N5484	34p	AF186	30p	BC178	20p
2N2904A	37p	2N3771	1-85	2N5486	38p	AF200	70p	BC179	23p
2N2905	37p	2N3772	2-00	2N6027	33p	AF239	74p	BC182	11p
2N2905A	28p	2N3773	2-90	2N6101	65p	AF240	98p	BC182L	14p
2N2906	28p	2N3789	2-90	2N6107	42p	AF279	80p	BC183	11p
2N2806A	28p	2N3790	3-10	2N6109	42p	AF280	85p	BC183L	14p

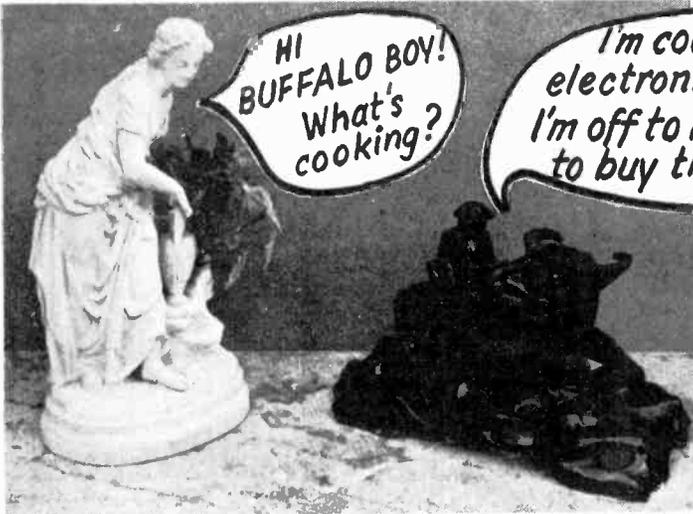"FULL RANGE OF THYRISTORS, TRIACS, DIACS, ZENERS, CAPACITORS, RESISTORS, SOLDERING IRONS, TOOLS ETC., ALWAYS IN STOCK"
Prices correct at 28th. March, 1977, but all exclusive of VAT. P. & P. 30p



I'm cooking up a new electronic masterpiece! I'm off to HOME RADIO now to buy the components.

First of course you need our catalogue—all 200 pages of it! It's so packed with good things that it's known as the constructor's 'Bible'. It costs just £1 plus 40p for post and packing. With it comes a free Bargain List showing many items at such knock-down prices that the savings can pay for the catalogue several times over. Send for a catalogue today, using the coupon on the right.

A wise move—POST THE COUPON with cheque or P.O. for £1-40



Please write your Name and Address in block capitals

NAME

ADDRESS



HOME RADIO (Components) LTD. Dept. PW
234-240 London Road, Mitcham, Surrey CR4 3HD

(Regn. No. London 912966)

Worth
30p


NEW! For the home constructor

Worth
30p



Circuit diagram to circuit board in minutes. Layout circuit plan on .1" graph paper. Select Blob Board, lay components out with leads on copper strip. Blob of solder onto lead and your circuit is complete. Blob Boards normally half price of competitive boards. Roller tinned to solder components directly. No drilling or mounting. Modifications in seconds. Blob Board is re-usable.

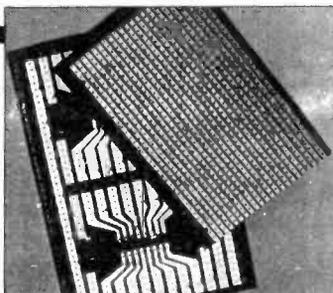Blob Boards are circuit boards designed exclusively for the home constructor and prototype engineer and are normally half the price of competitive boards. Blob Boards are roller tinned for ease of soldering, most require no cutting or breaking of contact rails. HALF PRICE AND RE-USABLE. That is NEW!



FREE BLOB BOARD!

Blob Board .1" or .15"	1 off	3 off
All approx. inch sizes		
ZB1V 2.5 x 5	£0.30	£0.75
ZB2V 2.5 x 3.75	£0.23	£0.57
ZB3V 3.75 x 5	£0.46	£1.14
ZB4V 10 x 6	£1.51	£3.78
Discrete Blob Board	1 off	3 off
ZB5D 3.6 x 2.4	£0.20	£0.51
ZB6D 2.4 x 7.3	£0.42	£1.05
ZB7D 4.9 x 7.3	£0.69	£1.75
ZB8D 9 x 7.5	£1.62	£4.05
Dip Blob Boards	1 of	3 off
ZB11C 4.5 x 3	£0.36	£0.90
ZB21C 4.8 x 3.2	£0.40	£0.96
ZB41C 4.75 x 7.5	£0.85	£2.13
ZB81C 9.5 x 7.5	£1.70	£4.26

Sample pack: 1 off ZB1V + 1 off ZB8D + 1 off ZB21C normally £2.32 only £2.00 + free Blob Board.

Many other sizes and patterns available add 30p post + 8% VAT to all orders.

S-DeC




Take an S-DeC, take a small stock of components, insert into S-DeC, no soldering, make a radio receiver, light operated switch, 3 stage amplifier. When circuit is made unplug components and use them again to make a morse practice oscillator, LC oscillator, binary counter and any other discrete circuitry. See Practical Wireless for new series of S-DeC projects. S-DeC + step by step instructions to build above projects and 3 more + which components to use + free control panel for mounting switches, lamps etc. + free Blob Board. S-DeC only £1.98 + 37p (VAT + post) send only £2.35.

If you are using IC's to build circuits use T-DeC for 1 chip circuits and U-DeC A for 2 chip circuits. Draw circuit on graph paper, plug IC into Adaptor and plug into DeC. No soldering, no bent leads, no wasted IC chip. Lines on DeC Show contact rails, plug discrete components in. Cross overs, connections are made using different coloured leads.

Circuit completed and working unplug components and use for next circuit. No soldering, no damage to components. Use your DeC and small stock of components over and over again. T-DeC send £4.30. U-DeC "A" send £4.60. Adaptor send £2.30.

T-DeC

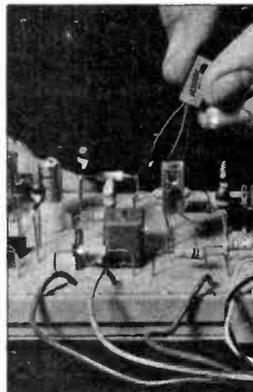

DRILL·SAW GRIND·BURR BRUSH· POLISH

PB announce a precision British built drill for the home constructor. Works better than most bigger drills and can be used for fine detailed work. Drills through any circuit board, need to break copper strip simply grind it off. 9000 RPM Drill + 20 Assorted tools £11.20 (+VAT + post) send £13.00. 9000 RPM Drill only £5.22 + post + VAT send £6.00. Multi-purpose Drill stand £10.60 + post + VAT send £12.00



For leaflets and further information please send stamped addressed envelope.

PB Electronics Scotland Ltd.
57 High Street,
Saffron Walden Essex.
CB10 1AA

Mr. Trader please exchange for 1 Blob Board ZB1V worth 30p when purchasing any of the above items.
Trade enquiries please contact Bendridge, London.
Mr. John Evans Tel: 01-228 9227

30p

CRESCENT RADIO LTD.

164-166 HIGH ROAD, LONDON N22 6EJ 888-3206
 (also) 13 SOUTH MALL, EDMONTON, N.9 803-1685
 MAIL ORDER DEPT.
 1 ST. MICHAELS TERRACE, WOOD GREEN,
 LONDON N22 4SJ Phone 888 4474

3-WAY MULTIPLE AC ADAPTOR

This compact adaptor allows a large range of battery powered equipment to be operated from A.C. mains (220-240V A.C.). Switchable for 6, 7.5 or 9 volts, current rating is 300 mA max. A polarity reversing coupler is incorporated and the lead is terminated by a four way plug offering connections by 2.1 and 2.5mm sockets, 2.5 and 3.5mm plugs. The sealed moulded unit is fitted with a 3 pin 13A mains plug and measures 70 x 50 x 42mm approx. Only £3.50 + 8%.

GOODMANS 8in. LOUDSPEAKER

Goodmans "Audion SPA" Base L/speaker, impedance 8 ohm, power handling 15W nominal. Our price £4.20 + 12½% VAT.

"0100" 100 WATT AMPLIFIER

All built and tested, mounted on a plain aluminium chassis which measures 18" x 9" x 4" and which you can mount into a cabinet of your choice. Four controlled inputs, master volume, treble, middle and bass controls. 8/6 protected output, 100 watts clean into 8ohm L/S. Ideal for disco, music groups, P.A. and clubs. A bargain at £48 + £1 cart. + 8% VAT.

P.C. ETCHING KIT

This kit contains all that the constructor will need to etch the circuits of his own design.

Contents—Plastic etching dish. Sample copper clad board. Laminate Cutter. 1 lb Ferric Chloride. Large Plastic Spoon. Etch Resist Pen. Full Etching Instructions.

Complete and Big Kit Value at £4.25 + 8% VAT.

POWER SUPPLY UNITS

+8%



PPI switched 3, 4, 6, 7, 9 and 12 volts at 500 mA, with on/off switch and pilot light. Size: 130mm x 56mm x 75mm. ONLY £5.50



M3 CONDENSER MICROPHONE

Cardioid and omni-directional 600 ohm and 50K ohm impedance. 20-18,000 Hz. On/off switch and wind shield. Complete with stand adaptor. Packed in presentation box. Price £14.50 + 12½% VAT.

HEAVY DUTY 12 VOLT POWER SUPPLY

1.5 amp at 12 volt power supply approx. size 8" x 4" x 3". Ideal for using your car entertainment in the home from domestic mains. Suitable for 8 track cartridge or 4 track cassette machines. Price £7.50 + VAT 8%.

2 WAY AND 3 WAY CROSSOVERS +12½%

NT206 2-way network for 8 ohm speakers up to 30 watts. Price £2.00.

NT206H 2-way, as above, 100 watts. Price £2.25.

NT306 3-way network for 8 ohm speakers up to 30 watts. Price £3.25.

NT306H 3-way, as above, 100 watts. Price £4.00.

TIE-CLIP CONDENSER MICROPHONE

Omnidirectional 600 ohm 40-15,000Hz. Extra long lead. Ideal for stage work, conferences, etc. Price £9.50 + 12½% VAT.

LOW NOISE LOW PRICE CASSETTES +8%

Good quality tape in well made screw type cassettes. Presented in single plastic cases. C60-40p C90-50p C120-60p

10% Discount on ten or more cassettes of one type

LOUDSPEAKERS +12½%

2½" 8 ohm 90p

2½" 40 ohm 90p

2½" 80 ohm 90p

5" 8 ohm ceramic £1.50

MULTI-METER MM12

50,000 o.p.v.



If you need a good instrument for your work/hobby and you're not prepared to settle for a small scale and poor ranges, then read the specifications for the MM12, and send for one! AC volts: 0 to 1.5, to 0/600 in 10 ranges. DC volts: 0 to 0.8, to 0/500 in 12 ranges. DC current: 0 to 25 µA, to 0/10 amps 10 ranges. Resistance: 0 to 100 ohms, to 0/16 meg ohms in 4 ranges. Decibels: -20 to +62 db in 10 ranges. Size: 6½" x 4½" x 2½". Price £9.50 + 8% VAT.

BARGAIN PROJECT BOX

A plastic box with moulded extrusion rails for PC or Chassis panels with metal front plate fitted with four screws (all supplied). SIZE (internal) 81mm x 61mm x 25mm. OUR PRICE 50p. + 8%

TT MULTI-METER



Ideal tester for everybody interested in electronics. Weighing less than 100 grammes and only 80 x 24 x 90 mm. Ranges: A.c. volts: 0-10V, 50V, 250V, 1,000V. D.c. volts: 0-10V, 50V, 250V, 1,000V. D.c. current: 0-1mA, 0-100mA. Resistance: 0-150 kohm. Price £5.50 + 8% VAT.

FERRIC CHLORIDE

Anhydrous ferric chloride in double sealed one pound poly packs. Our Price 65p + P/P + VAT @ 8% per lb.

3 KILOWATTS PSYCHDELIC LIGHT CONTROL UNIT

Three Channel Bass, Middle, Treble, Each channel has its own sensitivity control. Just connect the input of this unit to the loudspeaker terminals of an amplifier and connect three 250V up to 1000W lamps to the output terminals of the unit, and you produce a fascinating sound-light display. (All guaranteed.) £18.50 plus 75p P. & P. + 8%

BARGAIN TRANSFORMERS

12.0-12 volt 500m/a
 240 volt primary transformer bargain.
 approx size 60mm x 40mm x 50mm
 fixing centres 75mm
 Our Price £1.20 + 8%

EFFECTS PROJECTOR "150"

No Disco should be without our new effects projector, we believe that this is the most versatile machine for projecting coloured images to supplement your music. Spec:—Volts=220/240 AC 50Hz. Lamp=A1/167 150 watts. Standard Lens=60 m/m.

A sturdy metal construction and takes a range of lenses and accessories. Comes complete with 6" liquid wheel and ready to use. A bargain at £27 + VAT 8%.

ABS PLASTIC BOXES

Handy boxes for construction projects. Moulded extrusion rails for P.C. or chassis panels. Fitted with 1mm front panels.

1006-106mm x 73mm x 45mm	60p
1006-160mm x 74mm x 47mm	80p
1007-185mm x 124mm x 60mm	£1.80
1021-106mm x 74mm x 45mm (sloping front)	57p

Plus 8% VAT

U.K. CARRIAGE 50p UNLESS OTHERWISE STATED

ACCESS AND BARCLAYCARD ACCEPTED

VAT—All prices are excluding VAT. Please add to each item the VAT rate indicated.

LEKTROPACKS

17 TURNHAM GREEN TERRACE, CHISWICK, LONDON, W.4
 Tel. 01-994-2764.

MUSICAL EFFECTS EQUIPMENT . . . NEW RANGE

MC350E ECHO CHAMBER £75.00

Top quality unit with endless play tape cartridge. Stationary play heads ensure good reproduction and echo variance is achieved by changing tape speed. Input Imp. 50K and 600 ohms. 240V a.c. operation.

PS 110 MINI FAZER £27.00

Low priced "Phase Shifter" activated by on/off foot switch. 9V d.c. operation RD 10 RHYTHM MASTER £79.00
 Provides 10 Percussion Rhythms (Waltz, Foxtrot, Western, Polka, March, Rhumba, Bossanova, Cha-Cha, Mamba, Rock 1, Rock 2) as accompaniment to other instruments. Has var. speed & tempo controls. 240V a.c. operation. GP 5 GUITAR PICK-UP £4.95

Easy to fit crystal unit complete with volume control.

WF5 FUZZ WAH PEDAL £32.00

High quality professional standard unit, gives combined 'Wah Wah' and 'Fuzz' complete with 'Fuzz Adjust', Tone, Volume controls and individual effect foot switches 9V d.c. operation.

FY 2 FUZZ BOX £16.50

Low priced 'Fuzz' effect unit with variable speed and volume controls and on/off foot switch. 9V d.c. operation.

EA 45 ECHO REVERBERATION £39.00

High quality combined reverbation/mixer amplifier. Has 4 inputs and separate control for reverb. section. 240V a.c. operation.

RT 16 RESLY TONE UNIT £78.00

Basically a Tremolo/Phase Shifter/Reverb. Amp. all in one. A superb multi-effect unit from which an infinite variety of sounds can be obtained. 240V a.c. operation.

MICROPHONE MIXERS

MM2 MIXER £12.00

Mono/Stereo 4 Channel Unit. Inputs 4 x 50KΩ. Gain 3dB.

MM4 MIXER £8.00

Mono 4 Channel Unit. 4 x 50KΩ inputs. Gain 3dB.

MM3 MIXER £28.00

Stereo 4 Channel unit with 2 level control meters. 4 dual impedance (50KΩ or 600Ω) inputs. Gain 13 or 8dB.

MPX 12 MIXER £42.00

Stereo 4 channel Mixer/Pre-amp. 4 Dual Impedance (600Ω or 50KΩ) inputs; Stereo Phono (Magnetic) inputs. Output. 250mV. Mono or stereo.

MICROPHONES

Suitable for P.A., Singing, Tape Recording, Groups, Disco's, Musical Instruments, etc.

UDIS5 DYNAMIC CARDIOD £12.00

Cardioid mic. with on/off switch. Supplied complete with jack plug/lead and plastic mic. holder. Dual Imp. 50KΩ + 600Ω.

ECM 970 ELECTRET CONDENSER £18.00

Dual impedance 50KΩ + 600Ω. Detachable lead. Freq. response 20-25,000Hz ± 2dB. Uni-Directional Cardioid. Cpl. with w/shield, Mic-holder, Battery.

FLEXIBLE METAL GOOSENECKS

200mm. £2.50; 330mm. £3.50; 550mm. £5.00.

All prices include V.A.T. and U.K. postage.

YOU CANNOT SKI
 DOWN
 OUR
 SLOPES



VERO

But VERO SLOPING FRONT CASES do make attractive housings for many projects.

They are available in two sizes, made from high quality, two tone plastic, with anodised aluminium front panels. Both cases have integral circuit board fixing points in the base.



65-2523E and 75-1798K make ideal housings for test equipment, audio gear (faders, mixers, rhythm generators etc.) and control boxes.

See them at your local electronics shop and judge for yourself.

Send for our booklet which describes Veroboard, Plain board, DIP board, Pins, Tools, Plastic boxes etc. S.A.E. 7" x 9" plus 10p to -

VERO ELECTRONICS LTD. RETAIL DEPT.
 INDUSTRIAL ESTATE, CHANDLERS FORD, HANTS. SO5 3ZR.

4-STATION INTERCOM



£18.95

+ V.A.T. £1.52

Solve your communication problems with this

4-Station Transistor Intercom system (1 master and 3 Subs), in robust plastic cabinets for desk or wall mounting. Call/talk/listen from Master to Subs and Subs to Master. Ideally suitable for Business, Surgery, Schools, Hospitals and Office. Operates on one 9V battery. On/off switch. Volume control. Complete with 3 connecting wires each 66ft. and other accessories. P. & P. 90p.

MAINS INTERCOM NEW MODEL
No batteries—no wires. Just plug in the mains for instant two-way, loud and clear communication. On off switch and volume control. Price £38.74 per pair P. & P. 90p.

NEW! AMERICAN TYPE CRADLE TELEPHONE AMPLIFIER



ONLY £13.95


+ V.A.T. £1.12

Latest transistorised Telephone Amplifier with detached plug-in speaker. Placing the receiver on to the cradle activates a switch for immediate two-way conversation without holding the handset. Many people can listen at a time. Increase efficiency in office, shop, workshop. Perfect for "conference" calls: leaves the user's hands free to make notes, consult files. No long waiting, saves time with long-distance calls. On/Off switch, volume. Direct trace recording model at £18.95 + V.A.T. £1.36 P. & P. 75p, 10-day price refund guarantee.

WEST LONDON DIRECT SUPPLIES (PWS)
180 KENNINGTON HIGH STREET, LONDON, W8

H.A.C. SHORT-WAVE KITS

WORLD-WIDE RECEPTION

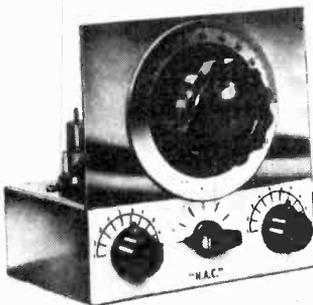

Famous for over 35 years for Short-Wave Equipment of quality. "H.A.C." were the Original suppliers of Short-Wave Receiver Kits for the amateur constructor. Special offer AR8 valves—70p each.

1977 "DX" RECEIVER

Complete kit—Price £7.20 (incl. p. & p. & V.A.T.). Customer writes: "I think the performance is astonishing for such an inexpensive and foolproof kit. I would wholeheartedly recommend this kit to anyone, however inexperienced, as an antidote to TV-titis, and as an entry into a fascinating hobby".

This kit is ready to assemble and contains all genuine short-wave components, drilled chassis, valve, accessories and full instructions. Full range of other S.W. kits, including the famous model "K plus" (illustrated above). All orders despatched within 7 days. Send now for free descriptive catalogue of kits and components. Send stamped envelope for details.

"H.A.C." SHORT-WAVE PRODUCTS
P.O. Box No. 16, 10 Windmill Lane
Lewes Road, East Grinstead, Sussex
RH19 3SN

VAT INCLUSIVE PRICES

Fully branded devices from
**RCA, TEXAS, MOTOROLA,
MULLARD, etc.**

Add 20p P & P—No other extras

TTLs by TEXAS

7400	18p	7492	55p
74H00	30p	7493	43p
7401	18p	7494	90p
7402	18p	7495	70p
7403	18p	7496	90p
7404	24p	7497	340p
74H04	30p	7498	30p
7405	25p	7404	60p
7406	43p	7405	60p
7407	43p	7407	35p
7408	22p	7409	70p
7409	22p	7410	55p
7410	18p	7411	80p
74H10	22p	7412	90p
7411	22p	7412	32p
7412	27p	7412	52p
7413	40p	7413	73p
7414	85p	7415	70p
7416	40p	7416	85p
7417	40p	7417	75p
7420	18p	7418	80p
7421	40p	7419	85p
7422	28p	7419	300p
7423	38p	7419	85p
7425	33p	7418	173p
7427	40p	7419	120p
7428	39p	7419	77p
7430	18p	7419	18p
7432	37p	7419	154p
7437	37p	7419	97p
7438	37p	7419	97p
7440	18p	7419	96p
7441	85p	7419	220p
7442	75p	7419	120p
7443	118p	7419	118p
7444	118p	7419	120p
7445	120p	7419	120p
7446	95p	7419	130p
7447	90p	7419	150p
7448	80p	7419	140p
7450	18p	7419	340p
7451	18p	7419	340p
7453	18p	7419	160p
7454	18p	7419	120p
7450	18p	7419	107p
7470	36p	7419	131p
7472	32p	7419	130p
7473	35p	7419	130p
7474	37p	7419	322p
7475	45p	7419	89p
7476	37p	7419	145p
7480	54p	7419	150p
7481	103p	7419	155p
7482	85p	7419	130p
7483	90p	7419	130p
7484	103p	7419	142p
7485	120p	7419	102p
7486	38p	7419	108p
7489	340p	7419	108p
7490	43p	7419	270p
7491	90p	7419	270p

OP. AMPS

301A	Ext. Comp. 8 pin DIL	40p
709	Ext. Comp. 8/14 pin DIL	30p
710	Diff. Comp. 14 pin DIL	45p
741	Int. Comp. 8/14 pin DIL	25p
747	Dual 741 14 pin DIL	78p
748	Ext. Comp. 8 pin DIL	200p
2007	Prop. Op. Amp TO 99	200p
1458	Dual Op. Amp. 8 pin DIL	75p
1088	CMOS/Bipolar Mosfet	108p
3140	BIMOS/FET Input 8 pin DIL	108p
3900	Quad. Op. Amp. 14 pin DIL	70p

C-MOS ICs

4029	120p
4030	50p
4042	90p
4043	100p
4046	180p
4047	110p
4049	68p
4050	50p
4052	120p
4055	120p
4056	150p
4060	120p
4069	40p
4071	29p
4072	29p
4081	18p
4082	29p
4083	140p
4084	140p
4085	140p
4086	140p
4087	140p
4088	140p
4089	140p
4090	140p
4091	140p
4092	140p
4093	140p
4094	140p
4095	140p
4096	140p
4097	140p
4098	140p
4099	140p
4100	140p

LOW PROFILE DIL SOCKETS BY TEXAS

8 pin 12p.	14 pin 13p
16 pin 14p.	24 pin 40p

VOL. REGS.

FIXED—Plastic 3 Terminals

1 Amp Positive	
5V	7805 130p
8V	7808 130p
12V	7812 130p
15V	7815 130p
24V	7824 150p
1 Amp Negative	
5V	7905 215p
12V	7912 215p
15V	7915 215p
24V	7924 215p

VARIABLE VOL. REG.

LM309K(TO3) 5V 1 Amp 150p
LM323K(TO3) 5V 3 Amp 750p
TBA625B(TO5)12V 0.5A 95p
7805(TO3) 5V 1Amp 150p
723 14 Pin DIL 45p

TRANSISTORS

BC125	20p	BC126	20p
BC127	20p	BC128	20p
BC129	20p	BC130	20p
BC131	20p	BC132	20p
BC133	20p	BC134	20p
BC135	20p	BC136	20p
BC137	20p	BC138	20p
BC139	20p	BC140	20p
BC141	20p	BC142	20p
BC143	20p	BC144	20p
BC145	20p	BC146	20p
BC147	20p	BC148	20p
BC149	20p	BC150	20p
BC151	20p	BC152	20p
BC153	20p	BC154	20p
BC155	20p	BC156	20p
BC157	20p	BC158	20p
BC159	20p	BC160	20p
BC161	20p	BC162	20p
BC163	20p	BC164	20p
BC165	20p	BC166	20p
BC167	20p	BC168	20p
BC169	20p	BC170	20p
BC171	20p	BC172	20p
BC173	20p	BC174	20p
BC175	20p	BC176	20p
BC177	20p	BC178	20p
BC179	20p	BC180	20p
BC181	20p	BC182	20p
BC183	20p	BC184	20p

LINEAR I.C.s.

301A	Ext. Comp. 8 pin DIL	40p
709	Ext. Comp. 8/14 pin DIL	30p
710	Diff. Comp. 14 pin DIL	45p
741	Int. Comp. 8/14 pin DIL	25p
747	Dual 741 14 pin DIL	78p
748	Ext. Comp. 8 pin DIL	200p
2007	Prop. Op. Amp TO 99	200p
1458	Dual Op. Amp. 8 pin DIL	75p
1088	CMOS/Bipolar Mosfet	108p
3140	BIMOS/FET Input 8 pin DIL	108p
3900	Quad. Op. Amp. 14 pin DIL	70p

OPTO-ELECTRONICS

PHOTO-TRANSISTORS

OC70	90p	LEDs	TL1209 Red	15p
OC71	140p		TL1211 Green	36p
2N577	50p		TL132 Infrared	81p
LD R8	75p		MV5025	27p
ORP61	90p			

SEVEN SEGMENT DISPLAYS

3015F	Minitron 0.3"	180p
DL704	Com. Cathode 0.3"	160p
DL707	Com. Anode 0.3"	180p
DL74	Com. Anode 0.6"	250p

TIP29C	82p	40380	43p
TIP30A	60p	40381	43p
TIP32C	72p	40382	45p
TIP31A	56p	40410	75p
TIP31C	68p	40409	75p
TIP32A	63p	40411	325p
TIP32C	85p	40594	90p
TIP33A	30p	40595	87p
TIP33C	120p		
TIP34A	120p	FETs	
TIP34C	140p	2N3744	45p
TIP35A	260p	BF256	90p
TIP35C	280p	MPF102	45p
TIP36A	270p	MPF103	40p
TIP36C	390p	MPF104	40p
TIP41A	70p	MPF105	40p
TIP41C	84p	2N3819	27p
TIP42A	76p	2N3820	80p
TIP42C	96p	2N3823	80p
TIP2955	76p	2N5457	40p
TIP3055	58p	2N5458	40p
2T1308	11p	2N5459	40p
ZX108	11p	2N5458	50p
ZX100	16p	3N128	81p
ZX500	19p	3N140	82p
ZX504	60p	3N141	81p
ZX505	25p	40673	58p

DIODES SIGNAL

2N1302	25p	0A81	15p
2N1305	25p	0A85	15p
2N1307	25p	0A81	15p
2N1613	22p	0A85	15p
2N1711	22p	0A90	90p
2N1891	32p	0A81	90p
2N2102	60p	0A95	90p
2N2129	22p	0A200	80p
2N2222	22p	0A202	10p
2N2369	15p	1N914	4p
2N2484	32p	1N916	11p
2N2904A	22p	1N4148	11p
2N2905A	22p	RECTIFIER	
2N2906A	22p	BY107	31p
2N2926B	90p	BY127	12p
2N2926G	11p	1N4001	8p
2N3053	19p	1N4002	6p
2N3054	65p	1N4004	7p
2N3055	65p	1N4005	7p
2N3439	72p	1N4007	8p
2N3442	151p	ZENER	
2N3565	34p	2.7 to 33V	22p
2N3702	14p	400mW	11p
2N3703	14p	1W	22p
2N3704	14p	NOISE	140p
2N3705	14p	Z51	140p
2N3706	14p	BRIDGE	
2N3707	14p	RECTIFIERS	
2N3708	14p	1A 50V	25p
2N3709	14p	1A 100V	27p
2N3773	320p	1A 400V	28p
2N3856	87p	1A 600V	32p
2N3900	22p	2A 50V	40p
2N3905	22p	2A 100V	48p
2N3906	22p	2A 200V	58p
2N4058	19p	3A 200V	65p
2N4060	19p	3A 800V	78p
2N4123	22p	4A 100V	90p
2N4124	22p	6A 50V	98p
2N4125	22p	6A 100V	104p
2N4126	22p	6A 400V	120p
2N4289	24p	TRIACS	
2N4403	34p	3 400V	90p
2N4427	87p	4 400V	100p
2N5089	34p	6 500V	120p
2N5296	58p	10 400V	130p
2N5401	62p	10 500V	150p
2N6107	70p	40430	130p
2N8247	200p	40669	110p
2N8254	140p	D.I.A.C	
2N8292	70p	BR100	32p

SCR THYRISTORS

1A 100V TO5	45p
1A 400V TO5	50p
3A 400V STUD	81p
7A 400V TO5 + HS	97p
6A 400V Plastic	220p
16A 600V Plastic	260p
BT106 150p	2N3525
CI06D 70p	2N4444

LP1186 MULLARD

FM Tunerhead 950p

3 1/2 DIGIT A/D CONVERTER

MC14433P 24 pin DIL £14.00 Data 50p +SAE

MEMORY ICs

2102-2 RAM	270p
2112-2 RAM	170p
RO3-2513 ROM	850p

MAIL ORDER ONLY
Govt., Colleges, etc. orders accepted

TECHNOMATIC LTD.
54 SANDHURST ROAD, LONDON, NW9
Tel. 01-294-4333, Telex 922800

BOOKS for Electronics Enthusiasts



COMING SOON—Radio, TV & Audio Technical Reference Book - S.W. Amos. The complete reference book compiled by 31 experts in all aspects of radio, TV & audio.
Spring 77. 1,200 pages

COMING SOON—Beginner's Guide to Radio—8th Edition - Gordon J. King. Completely updated and rewritten it surveys the whole field of radio.
Summer 77. 260 pages

SPECIAL SERIES FEATURE

Master Books

Authoritative yet easily understood by those with no technical knowledge whatsoever, the texts are supplemented by many highly informative illustrations. Each book is written by an expert in his own special field.

MASTER ELECTRONICS IN MUSIC T.D. Towers

Contents: Creating Musical Sounds by Electricity. Making Musical Instruments Louder. Musical Special Effects by Electronics. Electronic Keyboard Instruments. Electric Guitars. Magnetic Tape Music. The Robot Drummer. Music Synthesizers. Music by Computer. Index.
130 pages. £2.50

MASTER HI-FI INSTALLATION

Gordon J. King
Contents: How it Works. The Amplifier. Programme Signal Sources. Importance of a Good F.M. Signal. The Loudspeaker. Mono, Stereo & Quadrophonic Sound. Four-channel Techniques. Room Effects. Best Use of Controls. Terminology. Index.
150 pages. £2.50

MASTER STEREO CASSETTE RECORDING

I.R. Sinclair
Contents: Stereo Systems. Signal Sources. Controls and Facilities. Making the Recording. Replaying and Monitoring. Essential Maintenance. Aids to Better Recording. Noise Reduction Systems. Cassette Recorder and Hi-Fi.
140 pages. £2.50

STANDARD WORKS

FOUNDATIONS OF WIRELESS AND ELECTRONICS
9th Edition. M.G. Scroggie. 552 pages. £3.75

RADIO VALVE AND SEMICONDUCTOR DATA
10th Edition. A.M. Ball. 240 pages. £2.00



Newnes Technical Books

Borough Green, Sevenoaks, Kent TN15 8PH

NEWMART for all your ELECTRONICS hi-fi needs.

Stockists of: Amstrad · Teleton · Akai · Sansui · Wharfedale
Pioneer · Rotel · Garrard · Connoisseur

BATTERY ELIMINATORS P&P 25p
240v Input 6, 7-5 or 9v
output at 300mA ... £3-25
12v d.c. input (specify output 6, 7-5
or 9 d.c.) at 300mA ... £5-20

CARTRIDGES & STYLII

	D-D	RPL
P&P 25p	Cart.	Styli
Acos GP91/3CS (ster. comp)	£1-60	£1-20
GP93/1 or 95/1 ster. crst	£2-00	£1-20
GP94/1 or 96/1 ster. ceram.	£2-00	£1-20
GP101 crst. comp	£1-00	
GP104 ster. ceram	£2-60	£1-20
BSR X5M or X5H crst. comp.	£1-75	£1-20
SX6M or SX6H crst. ster.	£2-25	£1-20
SC5M ster. ceram.	£2-75	£1-20
Sonotone 9TAHC or 9TAHC/G (Diam.)	£2-60	£1-20
3509	£2-60	£1-20
Audio Technica AT55 Goldring G850	£2-25	—
G900	£3-50	£1-75
G800H	£5-25	£1-75
G800E	£9-06	£3-50

Shure Cartridges & Styli
M44G/M44C £7-70 £6-20
M55 £9-20 £7-15
M75EJ Type 2 £17-15 £12-65
M75EJ Type 2 £14-30 £8-78

SPEAKERS P&P 70p
EMI 13" x 8", 8 ohm Plain £3-40
8" x 5" C.Mag. 5 watt, 3.8 or 15 ohm ... £2-35
8" x 5" Dualcone ... £3-70
8 ohm, 10 watt ... £3-45
8" 8 ohm Dualcone ... £4-10
10" Dualcone ... £12-20
Richard Allen 30w 12" 8 or 15 ohm

MICROPHONES P&P 45p
UD 130 50K/600 ohm uni-dir. ball metal ... £7-90
Condenser Mic. 600 ohm ECM77 omni-dir ... £10-50
Cassette Stick Mic. with R/Control ... £1-65
Cass. Stick Mic. with R. Control (Phillips type) ... £1-93

CASSETTES P&P 25p
C60 C90 C120
Low Noise £0-37 £0-48 £0-75
Philips £0-79 £1-08 £1-73
Memorex £0-81 £1-38 £1-80
Cassette Head Cleaner £0-55
Bib Head Cleaner £1-99
magnetiser

RECORDS P&P £1-35
GARRARD SP25 Mk IV £20-70
GARRARD SP25 Mk IV/G800 with Plinth & Cover ... £33-20
BSR MP60 (P128R) ... £17-35
Plinth & Cover for Garrard, BSR ... £4-95
BD1 Kit ... £17-25

M.O. prices only. VAT inc. Subject to Availability & manufs. increase. Send 30p for Catalogue. Barclay/Access.
Callers Welcome at Manchester 30-32 Shudehill Tel. 061-832 7710. Leeds 4 New Market St. Tel. 0532 42708. Liverpool 15 Whitechapel. Tel. 051-236 0738

NEWMART ELECTRONICS

Mail Order Dept P.W./B
Belmont St, Monton,
Eccles, Manchester.
Tel 061-789 5268


J. BIRKETT

Radio Component Suppliers

25 The Strait, Lincoln LN2 1JF Tel: 20767

50 mm SLIDER POTS 50K Log or 100K Lin. Both 25p each or 6 for £1.
SUB-MINIATURE LOUDSPEAKERS 8 ohm Dia. 1 1/2" at 75p each.
600 MHz TRANSISTOR TYPE BF 224 at 10 for 57p.
30 CRYSTALS 10XAJ Type Assorted between 5100 to 7900 KHz for £1-10.
PLASTIC BRANDED TO92 TRANSISTORS like BC 108, BC 212 at 10 for 60p.
60 ASSORTED WIRE WOUND RESISTORS 1 to 10 Watt for 57p.
150 uf. 35v.w. TUBULAR TANTALUM CAPACITOR size 1/2" x 1/2" at 6 for 57p.
12 MICRO SWITCHES Assorted for 57p.
50 BC 107-8-9 TRANSISTORS Untested for 57p.
2 GHz DUAL TRANSISTORS in 8 Lead TO5 Can Untested 4 pair for 57p.
TEXAS R.F. PNP TRANSISTORS TYPE 2G106 at 20 for 57p.
1000uf 40v.w. ELECTROLYTICS size 1 1/2" x 1/2" at 3 for 35p.
TEXAS 800 Volt PLASTIC TO3 NPN 2 Amp TRANSISTORS @ 50p each.
TAA 570 LIMITING I.F. AMPLIFIER FM DETECTOR Untested 5 for 57p.
TBA 120S 14 Pin DIL LIMITING I.F. AMPLIFIER FM DETECTOR Untested 6 for 60p.
CRYSTALS 5 MHz 10X type @ 50p, 600 KHz 10XAJ @ 50p.
20 ASSORTED SILICON PHOTO and PHOTO DARLINGTONS Untested @ £1.
10,000uf 16v.w. ELECTROLYTICS size 3 1/2" x 1 1/2" @ 15p, 4 for 50p.
MORSE OSCILLATOR I.C. with data @ 25p.
6 to 1 FRICTION SLOW MOTION DRIVES @ 55p each.
1000pf 500v. DISC CERAMICS at 20p doz.
20 ASSORTED VARI-CAP DIODES Untested @ 45p.
-0005uf 75 K.v.w. VISCONEN CAPACITORS @ 50p each.
TO39 5 WATT NPN DARLINGTON TRANSISTORS @ 20p each.
DIVIDE BY 2 300 MHz COUNTERS with data @ 80p each.
ELECTROLYTIC CAPACITORS 47uf 450v.w., size 3 1/2" x 1" @ 20p, 75+75uf 450v.w. size 3 1/2" x 1 1/2" @ 50p, 1100+1100uf 100v.w. size 3 1/2" x 1 1/2" @ 65p, 3300uf 16v.w. size 2" x 1 1/2" @ 25p, 4700uf 16v.w. size 2" x 1" @ 25p, 7500+7500uf 16v.w. size 3 1/2" x 1 1/2" @ 55p.
10 ASSORTED MULTITURN TRIMPOTS for 60p.
SOLAR CELLS 0.5 Volt 5 mA at 35p.
Please add 20p. for post and packing on UK orders under £2. Overseas orders at cost.

INVERTORS

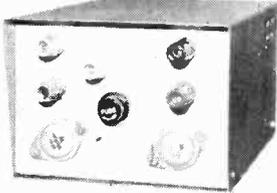

240v-50Hz from your 12v car battery
 25 watt-£4.75 300 watt (12v)-£33.08
 40 watt-£8.27 400 watt (24v)-£39.05
 75 watt-£12.03 500 watt (24v)-£48.18
 150 watt-£21.27 1 Kw (50v)-£127.00
 300 watt (24v)-£26.45 1.5 Kw (110v)-£140.80

All above invertors are in kit form but may be purchased built up in metal case and ready for use. Price list sent on receipt of S.A.E. Prices include p. and p.

P.W. AUTOMATIC EMERGENCY SUPPLY

240v-50Hz-150 watt inverter with built in battery charger. In event of power failure switches over automatically from battery charging to inverter operation. Cct. as appeared in Dec. 72 P.W. Complete kit of parts (excluding meter) £24.50 plus £1.70p.p.

DIGITAL WATCH

FOUR FUNCTION DIGITAL WATCH FOR ONLY £16 with 1 Year Guarantee HOURS . MINS. . SECONDS . DATE American Design, UK Manufacture.

TRANSFORMERS AND COILS

Both high volume and small order capacity available.
 Special offer. Miniature mains transformer 6-0-6v-6VA. 85p + 10p p. & p.

P.E. ORION STEREO AMPLIFIER & TUNER



20 + 20 Watts r.m.s. into 8 ohm load. Distortion less than 0.01% 100Hz-10kHz. Frequency response ± 1dB 20 Hz to 20kHz. Hum level virtually nil with volume full on.

This is a power amplifier of superb quality incorporating the very latest design features. Professional hi-fi enthusiasts have classed it as fantastic and real value for money. The CCT incorporates a low flux transformer and inputs for disc, tape, tuner, etc.

Complete kit of parts including slim line bookend case, silk screened front panel and knobs £48.60 inc. VAT and p. & p.

The bookend case, I.C.'s and semiconductors, P.C. board, Transformer, etc. may be purchased separately if desired. Send S.A.E. for further information.

P.E. ORION TUNER UNIT

PARTS MAY BE PURCHASED AS FULL KIT OR SEPARATE ITEMS. SEND S.A.E. FOR DETAILS.

N.B.-DELIVERIES ON ALL ITEMS MAY TAKE UP TO 28 DAYS DEPENDING ON AVAILABILITY AND DEMAND. CASH IN REGISTERED ENVELOPE OR POSTAL ORDERS CAN REDUCE TIME BY NOT HAVING TO CLEAR CHEQUES

ASTRO IGNITION



ASTRO IGNITION SYSTEM

Complete kit of parts for this proven and tested system £10.45 inc. VAT Ready built with only two connections to alter £13.75 inc. VAT. Thousands have used this system both home and abroad. Consider these advantages—more power, faster acceleration, fuel economy, excellent cold starting, smoother running, no contact breaker burning. Also because of the high energy spark the fuel mixture can be made weaker giving further economy and fewer plug problems. Fitting time when built 5 minutes approx. Please state whether positive or negative earth.

TRADE AND EXPORT ENQUIRIES WELCOMED ON ALL PRODUCTS

ASTRO ELECTRONICS
 Springfield Road, West Park
 CHESTERFIELD. 31475

VALVES

A1065	1.25	ECL80	0.60
AR8	0.60	ECL82	0.40
ARF3	0.60	ECL83	0.50
ATP4	0.50	ECL86	0.55
B12H	3.00	EF36	0.75
DAF96	0.60	EF37A	1.50
DET2212	0.55	EF39	1.00
FR8	0.60	EF40	0.70
DK95	0.80	EF41	0.75
DL92	0.50	EF80	0.35
DL96	0.70	EF81	1.50
DY86/	0.45	EF85	0.45
87	0.45	EF86	0.45
DY802	0.45	EF89	0.35
EB8C/	0.55	EF91	0.55
01	1.30	EF92	0.75
E180CC	1.30	EF95	0.45
E182CC	0.40	EF183	0.40
3.50	EF184	0.44	
EB10F	6.00	EF80A	2.00
EA50	0.45	EL200	0.75
EABC80	0.40	EH90	0.60
EA42	0.70	EL34	0.70
EB91	0.30	EL35	0.60
EBC31	1.00	EL37	3.00
EB41	0.75	EL41	0.80
EBF80	0.45	EL81	0.60
EBF83	0.45	EL82	0.60
EBF89	0.40	EL84	0.35
EC52	0.40	EL86	0.50
EC58	0.45	EL90	0.50
EC82	0.40	EL91	1.60
EC83	0.40	EL95	0.70
ECC84	0.35	EL504	0.80
ECC85	0.45	EL821	3.00
ECC86	1.25	EM31	0.75
ECC88	0.55	EM80	0.55
ECC189	0.80	EM81	0.60
ECF80	0.45	EM87	1.00
ECF82	0.45	EY51	0.45
ECF801	0.75	EY81	0.45
ECF82	0.85	EY86/87	0.45
ECH81	0.45	EM80	0.55
ECH84	0.50	EY88	0.50
		PCL86	0.60

PCL805/	0.50	QVQ06-	0.50	UBL1	1.00	Z800T	1.50	5V4G	0.65	6AX5GT	0.60	8J4WA1	0.75	6X4	0.45	
85	0.60	40A	14.00	UBL21	0.75	IA3	0.80	5Y3GT	0.65	1.00	6J5	0.75	6X5GT	0.45	6X5GT	0.55
PFL2000	0.70	QV03-	0.50	UC285	0.50	IL4	0.30	SZ1	1.00	6B7	0.75	6J5GT	0.55	6V6G	0.95	
PL36	0.60	12	1.60	UCF80	0.80	IR5	0.55	SZ4G	0.70	6BA6	0.40	6J6	0.35	6V6G	0.95	
PL81	0.55	R19	0.80	UCH42	0.80	IS4	0.40	SZ4GT	0.75	6BE6	0.45	6J7	0.70	6Z4	0.85	
PL82	0.50	S104/	0.50	UCH81	0.50	IS5	0.40	8AB7	0.60	6BG6G	1.00	6J7G	0.50	6-30L2	0.90	
GZ34	0.80	IK	2.50	UC182	0.45	IT4	0.40	8AC7	0.60	6BJ6	0.75	8K6GT	0.80	7B7	0.80	
KT37	2.00	SC17	0.50	UC183	0.70	IX2B	0.80	6A6H	0.75	6B7A	0.60	6K7	0.55	7D7	0.80	
PL504	0.85	400	4.00	UF41	0.75	2X2	0.80	6AK5	0.45	6BR7	2.30	6K7G	0.35	9D6	0.60	
PL608	0.95	SC17	0.50	UF80	0.40	2D21	0.55	6AK8	0.40	6BW6	1.30	6K8GT	0.55	9D6	0.75	
PL509	1.35	600	4.00	UF85	0.50	2K25	0.90	6AL5	0.30	6BW7	1.00	6L6M	1.90	11E3	11.00	
LM202	2.00	SP61	0.85	UF89	0.50	3A4	0.60	6ALS5W	0.65	6C4	0.40	6L6GT	0.60	12A6	0.60	
AR8	1.00	TT21	6.50	UL41	0.75	3E29	5.50	6AM5	1.60	6C8	0.55	6L7	0.65	12A6	0.60	
DK95	0.80	U25	1.00	UL84	0.50	3D6	6.00	6AM6	0.55	6CB6	0.50	6SA7	0.55	12A5L	0.70	
DL92	0.50	U26	0.85	UY41	0.55	3E4	5.50	6AN8	0.85	6CH6	3.00	6SG7	0.50	12AT6	0.45	
DL96	0.70	UY85	1.00	UY85	0.50	3V4	0.85	6AQ5	0.50	6CL6	0.75	6SJ7	0.60	12A7U	0.45	
DY86/	0.45	VR105/	0.75	VR105/	0.75	5B/	0.60	6AQ5W	0.50	6D6	0.50	6S1JGT	0.50	12A7U	0.45	
87	0.45	VR105/	0.75	VR105/	0.75	5B/	0.60	6AS6	0.80	6E7	1.10	6SL7	0.60	12A7U	0.45	
DY802	0.45	UABC80	0.50	VR150/	0.50	5B/	0.60	6AT6	0.55	6F8G	0.75	6S1JGT	0.50	12A7U	0.45	
EB8C/	0.55	UAF42	0.75	X61M	1.50	5B/	0.60	6AU6	0.40	6F12	0.65	6SNTGT	0.50	12A7U	0.45	
01	1.30	U61	0.60	X66	0.75	258M	5.50	6AV6	0.50	6F17	1.00	0.55	12C8	0.55		
E180CC	1.30	UBF80	0.50	Z800U	3.00	5R4GY	1.10	6AX4GT	0.60	6F33	4.20	6SQ7	0.65	12C8	0.55	
E182CC	0.40	UBF89	0.50	Z801U	3.50	5U4G	0.60	6AQ5W	0.50	6H6	0.45	6V6GT	0.60	DG15-2	22.00	

TRANSISTORS

AAZ12-	AF118	BC172	CRS3/40	OC29	OC206	2N4058
BAV10	AF124	BC172A	CRS25/025	OC35	ZR11	2N4061
AC113	AF125	BC212A	GET115	OC36	ZR21	2N4172
AC126	AF126	BCY31	GET116	OC42	ZR22	2N5295
AC127	AF127	BCY33	GEX66	OC44	2N456A	3N126
AC139	AF139	BCY72	NK722	OC45	2N525	3N128
AC176	AF178	BF115	NK730	OC72	2N696	3N154
ACY17	AF186	BF167	NK740A	OC73	2N708	3N159
ACY18	AF239	BF173	OA5	OC75	2N918	SX754
ACY19	AFZ12	BF185	OA7	OC78	2N1305	25303
ACY20	ASY26	BFY51	OA70	OC78D	2N1307	T12082
AD121	ASY27	BFY52	OA71	OC81	2N1309	40235
ADY40	ASY28	BSY27	OA73	OC82	2N2062	40250
AD149	BC107	BSY38	OA79	OC82DM	2N2411	40251
AD161	BC108	BSY95A	OA91	OC83	2N2989	IN23A
AD186	BC109	BY100	OA200	OC83B	2N3053	IN25
ADZ11	BC113	BYZ16	OA202	OC139	2N3054	IN38A
ADZ12	BC116	CRS1/20	QA Z200	OC140	2N3055	IN43
AF114	BC118	CRS1/30	OC22	OC170	2N3391	IN70
AF115	BC136	CRS3/10	OC25	OC172	2N3730	IN677
AF116	BC137	CRS3/20	OC26	OC200	2N3819	IN4148
AF117	BC148A	CRS3/30	OC28	OC204	2N4038	IN4785

MINIMUM POSTAL ORDER £1. PERSONAL CALLERS WELCOME. MANY OTHERS IN STOCK include Cathode Ray Tubes and Special Valves. U.K. UK Postage £1-£2 20p. £2-£3 30p. £3-£3 40p. Over £5 free.



VIDEOCON TUBE Type P84B English Elec. £20

TEST EQUIPMENT LARGE SELECTION PLUBICON TUBES Type XO 1071 Mullard £150

Please add 12 1/2% VAT

THE VALVE WITH A GUARANTEE

30L15	1.00	6146B	4.20
30L17	1.00	6350	1.60
30P12	1.00	8020	5.50
30P13	1.10	9001	0.40
30P14	1.10	9002	0.55
30P14	1.10	9003	0.70
35L6GT	0.80	9004	0.40
35W4	0.60	9006	0.40

C.R. TUBES

DG7-515	00
DG15-2	22.00
MV13-35	30.00
VCR139A	10.00
3BP1	8.00
5FP7	10.00
883	9.00
88L	9.00
CV1526	10.00

SPECIAL VALVES

BR189	250.00
M503-2342	65.00
K301	7.00
KRN2A	6.00
725A	25.00
2J/52A	75.00
CV2339	45.00
30F5	1.00
30FL12	1.20
30FL14	1.00

VALVES AND TRANSISTORS Telephone enquiries for valves, transistors, etc., retail 749 3934; trade and export 743 0899.

COLOMOR (ELECTRONICS) LTD 170 GOLDHAWK RD, LONDON W12 Open 9-12.30, 1.30-5.30 p.m. Closed Saturdays.



NOTICE TO READERS

When replying to Classified Advertisements please ensure:

- That you have clearly stated your requirements.
- That you have enclosed the right remittance.
- That your name and address is written in block capitals, and
- That your letter is correctly addressed to the advertiser.

This will assist advertisers in processing and despatching orders with the minimum of delay.

Receivers and Components

BRAND NEW COMPONENTS BY RETURN.

Electrolytic capacitors 16V, 25V, 50V.—0.47, 1.0, 2.2, 4.7 & 10mfd.—5p, 22, 47—3p. (50V—8p). 100—7p (50V—8p) 220—3p. (50V—10p) 470—11p. (50V—16p) 1000/16V—15p, 1000/25V—18p, 1000/50V—22p.

Subminiature bead tantalum electrolytics—0.1, 0.22, 0.47, 1.0, 2.2 @ 35V, 4.7/25V—11p, 10/25V—13p, 22/16V, 47/8V, & 100/3V—15p.

Multilayer miniature ceramic E12 series 2% 63V. 10p, to 47p—3p, 56p, to 330p.—4p.

Vertical mounting ceramic plate 50V. E12 series 22p—1000p. E6 series 1500p—47000p.—2p.

Polystyrene E12 series 63V horizontal mounting. 10p to 1000p—3p 1200p, to 10000p.—4p

Multilayer miniature 250V vertical mounting E6 series. 0.01 to 0.1—4p, 0.15, 0.22—5p, 0.33, 0.47—8p, 0.68—11p, 1.0—13p, 1.5—20p, 2.2—22p.

Mylar (Polyester) Film 100V vertical mounting. 0.001, 0.002, 0.005—3p, 0.01, 0.02—4p, 0.04, 0.05—41p.

Miniature resistors Highstab E12 series 5%. Carbon Film 0.25W 1Ω to 10MΩ. (10% over 1MΩ)—1p. Metal Film 0.125W, 0.25W & 0.5W 10Ω to 2MΩ.—1p. Metal Film 1W, 27Ω to 10MΩ.—2p ea.

1N4148—3p, 1N4002—5p, 1N4006—7p, 1N4007—8p, BC107/39, BC147/8/9, BF157/8/9 & BF194 & 197—9p. Fuses 20mm, glass, 13° glass & 1° ceramic. 23p. Post 10p. (Free over £4.00) Prices inclusive of VAT.

THE C. R. SUPPLY CO.,

127, Chesterfield Rd., Sheffield S8.

VHF pocket portable radio tuning 108 to 136 MHz. Very sensitive. Easily adjusted to tune 144 MHz band. £16.50 (inc post & VAT). Romak Ltd, Dept PW, 10 Hibel Road, Macclesfield, Cheshire.

SOWTER TYPE 3678

MULTI-TAP MICROPHONE TRANSFORMER
Primary windings for 600 ohm, 200 ohm and 50 ohm with Secondary loadings from 2K ohm to 10 K ohm Frequency response plus/minus ±dB 20 Hz to 26 KHz. Contained in well finished Mumetal box, 33mm diameter by 22mm high, with colour coded end leads, low distortion. Delivery (small quantities) EX STOCK, HIGHLY COMPETITIVE PRICE FULL DETAILS ON REQUEST.
E. A. SOWTER LTD., Dedham Place, Ipswich, IP4 1JP. Telephone 0473 32794

SMALL ADS

The prepaid rate for classified advertisements is 17 pence per word (minimum 12 words), box number 40p extra. Semi-display setting £14.00 per single column inch (2.5cm). All cheques, postal orders etc., to be made payable to Practical Wireless and crossed "Lloyds Bank Ltd". Treasury notes should always be sent registered post. Advertisements, together with remittance, should be sent to the Classified Advertisement Manager, Practical Wireless, Room 2337, IPC Magazines Limited, King's Reach Tower, Stamford St., London, SE1 9LS. (Telephone 01-261 5846).

CONDITIONS OF ACCEPTANCE OF CLASSIFIED ADVERTISEMENTS

- Advertisements are accepted subject to the conditions appearing on our current advertisement rate card and on the express understanding that the Advertiser warrants that the advertisement does not contravene any Act of Parliament nor is it an infringement of the British Code of Advertising Practice.
- The publishers reserve the right to refuse or withdraw any advertisement.
- Although every care is taken, the Publishers shall not be liable for clerical or printers' errors or their consequences.

SEMICONDUCTORS—1N914E 3p each, £1.80/100, £13/1,000 800V 1 amp (1N4006 equiv.) 5p each, £4/100, £35/1,000. Zeners:—2.2-36V 5p each, £4/100 (no mix), £4.50/100 (mix). G.P. Silicon Diodes:—2p each, £1.30/100, £10/1,000, OA90/91 etc 4p each, £3/100. Ltd Qty. Branded Transistors:—BC212L 9p each, ZT 212 10p each, 2N2955 £1 each, 2N3054 £0.40 each, 2N3716 £1.50 each, CZ11 Thermistor 20p each, 10 for £1.50. S.A.E. for lists. P+P 20p. Bale Electronics, "Nanock", Dalton, Lockerbie, Dumfriesshire.

BRAND NEW COMPONENTS. 0.33W 5% Hi-Stability E12 series 4.7-10M. Any selection 0.9p each, 0.8p 100+, 0.75p 1,000+. BC107/8/9 and BC147/8/9 all 8p each. Send SAE for our complete list of components. Inclusive prices. P & P 15p. C. N. Stevenson (PW) 304 Avery Hill Road, London SE9 2JN.

CARBON FILM RESISTORS. 0.33W 5% Hi-stability E12 series 4.7-10M. Any selection 0.9p each, 0.8p 100+ 0.75p 1,000+ Inclusive prices. P&P 15p. C. N. Stevenson (PW), 304 Avery Hill Road, London SE9 2JN.

Precision Polycarbonate Capacitors

440V AC RANGE		All High Stability—extremely Low Leakage		65V DC RANGE	
Value (µF)	Dimens. (mm)	Price (p)	Value (µF)	±1%	±2% ±5%
0.1µF	27 12.7 85p	0.22-0.47	1.0µF	£1.28	75p
0.15µF	27 12.7 80p	1.0µF	1.5µF	£1.32	77p
0.22µF	33 16 80p	1.5µF	2.2µF	£1.44	84p
0.25µF	33 16 92p	2.2µF	3.3µF	£1.56	81p
0.33µF	33 16 99p	3.3µF	4.7µF	£1.74	£1.16
0.47µF	33 19 11.10	4.7µF	6.8µF	£1.98	£1.33
0.5µF	33 19 11.10	6.8µF	10µF	£2.40	£1.60
0.68µF	50.8 19 11.25	10µF	15µF	£2.48	£2.32
1.0µF	50.8 19 11.87	15µF	22µF	£2.74	£2.88
1.5µF	50.8 25.4 11.64	22µF		£2.96	£2.44
2.0µF	50.8 25.4 11.95				£3.90

TANTALUM BEAD CAPACITORS—Value available: 0.1, 0.22, 0.33, 0.47, 0.68, 1.0, 2.2, 3.3, 4.7, 6.8µF at 16V/25V or 35V; 10.0µF at 16V/20V or 25V; 22.0µF at 6V/10V or 16V; 33.0µF at 6V or 10V; 47.0µF at 3V or 6V; 100.0µF at 3V. All at 12p* each, 10 for £1.10*, 50 for 45*, 100 for 80*.

TRANSISTORS & I.G.'s
 *BC107/8/9 8p *BC212/212L 12p 2N3055 60p
 *BC14 12p *BC218/213L 11p OC44/45 30p
 *BC147/8/9 10p *BC214/214L 11p OCT1/2 20p
 *BC153 16p *BF194/5 12p NE555 Timer 61p
 *BC154/7/8/9 12p BFY60/1/2 20p 741C 8 pin DIL 32p
 BC182/182L 11p AF178 40p ZN414 11.15
 *BC185/185L 11p AP239 38p 6N7601SND 11.15
 *BC184/184L 12p 2N3702/4 11p £1.50

POPULAR DIODES—1N914 6p, for 8 45p, 18 for 80p 1N918 8p 6 for 45p, 14 for 80p; 1844 5p, 11 for 50p; 26 for £1.00, 1N4148 5p, 6 for 27p, 12 for 48p; 1N4001 51p; 002 8p; 003 61p; 004 7p; 005 71p; 006 8p; 007 81p

LOW PRICE ZENER DIODES—400mW, Tol. ±5%, at 5mA: 3V; 3.3V; 3.6V; 4.7V; 5.1V; 5.6V; 6.2V; 6.8V; 7.2V; 8.2V; 9.1V; 10V; 11V; 12V; 13V; 13.6V; 15V; 16V; 18V; 20V; 22V; 24V; 27V; 30V; 33V. All at 7p each, 5 for 33p, 10 for 65p, 50 for 33.12. SPECIAL OFFER: 100 Zeners may be mixed! for 60.00.

RESISTORS—High stability, low noise carbon film 5% 1/4W at 40°C, 1/4W at 70°C. E12 series only—from 2.2Ω to 2.2MΩ. ALL at 1p each, 8p* for 10 of any one value, 70p* for 100 of any one value. SPECIAL PACK: 10 of each value 2.2Ω to 2.2MΩ (730 resistors) 25*.

SILICON PLASTIC RECTIFIERS—1.5 amp, wire-ended DO27: 100 P.I.V. 7p (4 for 26p); 400 P.I.V. 8p (4 for 30p).

BRIDGE RECTIFIERS—2 1/2 amp: 200V 40p; 350V 45p; 600V 56p.

SUBMINIATURE VERTICAL PRESETS—0.1W only: All at 5p each; 50; 100; 220; 470; 680 ohm: 1k; 2k; 4k; 7k; 10k; 15k; 22k; 47k; 100k; 320k; 680k; 1M; 2M; 5M.

PLEASE ADD 20p POST AND PACKING ON ALL ORDERS. EXPORT—ADD COST OF SEA/AIRMAIL. Add 8% VAT to all items except those marked with *

which are 12%.

Send S.A.E. for additional stock lists.

Wholesale price lists available to bona fide companies.

MARCO TRADING (Dept. P4),
The Old School, Edstaston, Wem, Shropshire.
Tel: Whixall 464/465 (Ext. 984 872).
(Proprs. Minicost Trading Ltd.)

CONTROL Knobs. Black, slightly imper-fect 5 for 50p P&P 15p. V. Laight, 14 Alexandra Road, Thames Ditton, Surrey.

TOUCH CONTROLLED LIGHTING KITS

These KITS replace conventional light switches and control 300W of lighting. No mains rewiring required. Insulated Touchplates. All with easy to follow instructions.
NEW! TS300K—TOUCHSWITCH and DIMMER combined. ONE touchplate to switch light on or off. Brightness controlled by small knob. ONLY £5.95.
TS300K—TOUCHSWITCH. TWO touchplates ON and OFF—ONLY £3.97.
TS4300K—AUTOMATIC. ONE touch plate. Light turns off after preset delay 23-87.

LD300K—LIGHTDIMMER KIT—£2.45.

LD300K (Motorola)		CMOS (Motorola)	
4000	16p	4013	51p
4001	16p	4015	91p
4002	16p	4016	31p
4007	16p	4017	91p
4011	16p	4023	17p
4012	17p	4025	17p
		4026	155p

TRIACS 400V TO220 NE555 8 pin DIL 38p
 Case isolated TAB 741 8 pin DIL 24p
 6-5A 80p 8-5A 85p 2N627 (PUT) 23p
 Diac 21p 2N3055 36p

QUANTITY DISCOUNTS ON REQUEST. ADD 8% VAT plus 25p P&P. Mail Order Only to:

T. K. ELECTRONICS (PW)

106 Sturdy Grange Road, London, W7 2LX

COMMUNICATIONS RECEIVER modules. Small superhet circuit boards requiring only controls and tuned circuits, 9 volt. Mosfet mixer, IC IF, BFO, PROD. Det. Excellent AM/CW/SSB results reported by delighted users. SAE details. PR Gollidge Electronics, Millend, Stonehouse, Glos.

AMPLIFIERS, NEW, Boxed, Guaranteed, working 1 watt audio.

AMPLIFIER PANELS with 2 speed motor controller incorporated. Uses IC Type LM380N and runs from 9 volt P/Supply. Only £1.00 each inc. VAT/P & P etc. Drawings + IC Data add extra 60p to order from:—

INDUSTRIAL RF SERVICES, 51 Deptford Broadway, London SE8 4PH. Phone 692-4284.

LED's. Mixed bags of 4 different sizes and 4 different colours, 50 at £5.25, 100 at £9.25 including VAT and post and packing. CWO, Michael Williams Electronics, 47 Vicarage Avenue, Cheadle Hulme, Cheshire SK8 7JP.

RESISTORS: AEL2 Type Carbon Film High Stab. 5% E12 Range. Sold in units of 10. 1/4W (4E7 to 2M2) 8p per 10. 1/2W (10E to 10M) 9p per 10. Also Transistors BC108/9 75p per 10. LEDs TIL/FVL 117 Red 12p, Grn & Yell. 20p SAE for more details to C.W. Electronics, Dept. PW, 10 Kingsley Path, Britwell Estate, Slough, Berkshire. (+VAT at High Rate 12½% & postage 20p).

VALVES

Radio - T.V. - Industrial - Transmitting We Dispatch Valves to all parts of the world by return of post, Air or Sea mail, 2700 Types in stock, 1930 to 1976. Obsolete types a speciality. List 20p. Quotation S.A.E. Open to callers Monday to Saturday 9.30 to 5.00 closed Wednesday 1.00. We wish to purchase all types of new and boxed Valves.

COX RADIO (SUSSEX) LTD.
Dept. P.W. The Parade, East Wittering,
Sussex PO20 8BN West Wittering
2023 (STD Code 024366)

SUPERSCOOP. Fully marked brand new semiconductors and goodies at bargain prices. Send SAE for details and prices. Dalesound, 15 Balcombe Road, Horley, Surrey RH6 7JR.

For Sale

NEW ISSUES of "Practical Wireless" available from April 1974 edition up to date. Price 55p each:— Bell's Television Services, 190 Kings Road, Harrogate, N. Yorkshire. Tel (0423) 55885.

SCOTT ALLWAVE. Collectors item. Tuner Chassis only, in working order. With original manual. Serial 325. CIRCA 1936. Offers: 0277 216175.

Wanted

WANTED NEW Valves, transistors, I.C.s, amplifiers, receivers, televisions (Anything Usefull) any quantity. Stan Willets, 37 High Street, West Bromwich. Tel: 021 553 0186.

WANTED—NEW VALVES, TRANSISTORS, I.C.s, POPULAR PRICES, popular types. Kensington Supplies (C), 367 Kensington Street, Bradford 8, Yorkshire.

Books and Publications

RADIO BOOK SERVICE

World Radio TV Handbook 1977	£3.75
The Cathode Ray Oscilloscope and its Use	£1-90
1st & 2nd Books of Transis Equip & Substitutes (Set)	£1-55
Radio Receiver Construction using I.C.s & Transistors	£0-70
Radio Antenna Handbook for Long Dist. Reception	£0-95
79 Electronic Novelty Circuits	£0-85
Audio Enthusiast Handbook	£0-95
The Complete Car Radio Manual	£0-85
Solid State Power Supply Handbook	£0-95
I.C.s & Transistor Gadgets Construction Handbook	£0-70
Integrated Circuits Equip & Substitutes Handbook	£0-95
Manual of Electronic Circuits for the Home	£0-60
Electronic Gadgets & Games	£0-95

PRICES INCL. P&P. SEND S.A.E. FOR FULL LIST. NOTE NEW ADDRESS
4 CHICHESTER COURT, WICKHAM RD, BECKENHAM KENT BR3 2QW

SIMPLIFIED TV REPAIRS. Full repair instructions individual British sets £4.50, request free circuit diagram. Stamp brings details unique TV Publications (Ausepw) 76 Church Street, Larkhall, Lanarkshire.

Ladders

LADDERS. Varnished, 20ft 9in extd. £25-33. Carr. £1-90. Leaflet. Also alloy ext. up to 62½ft. The Ladder Centre (WLS) Halesfield (1) Telford, Salop. Tel: 586644. Callers welcome.

Practical Wireless, June 1977

Service Sheets

SERVICE SHEETS — COLOUR TV SERVICE MANUALS

Service Sheets for Mono TV, Radios, Record Players and Tape Recorders 75p. Please send large Stamped Addressed Envelope.

We can supply manuals for most makes of Colour Television Receivers by return of post. B.R.C. PYE ECKO PHILIPS ITT/KB SONY G.E.C. HITACHI BAIRD ULTRA INVICTA FERUGSON H.M.V. MARCONI AND MANY MORE

Let us quote you. Please send a Stamped Addressed Envelope for a prompt reply.

Also comprehensive T.V. repair manuals by J. M. Court. S.A.E. for details.

G. T. TECHNICAL INFORMATION SERVICE

10 DRYDEN CHAMBERS, 119 OXFORD ST., LONDON W1R 1PA

MAIL ORDER ONLY

LARGE SUPPLIER OF SERVICE SHEETS

(T.V., RADIO, TAPE RECORDERS, RECORD PLAYERS, TRANSISTORS, STEREOGRAMS, RADIOGRAMS, CAR RADIOS, TUNER SHEETS)

ALL AT 75p EACH (Except colour) & CAR RADIOS Please state if Circuit will do if Service Sheet not in stock.

"PLEASE ENCLOSE LARGE S.A.E. WITH ALL ENQUIRIES & ORDERS"

Otherwise cannot be attended to

(Uncovered P.O. a please, original returned if service sheets not available.)

PLEASE NOTE

We operate a "by return of post" service. Any claims for non-delivery should be made within 7-days of posting your order.

C. CARANNA

71 BEAUFORT PARK
LONDON, N.W.11 6BX

We have the largest supplies of Service Sheets (strictly by return of post). Please state make and model number alternative. Free TV fault tracing chart or TV list on request with order.

Mail order or phone 01-458 4882
Large Stocks of Colour Manuals
NO OVERSEAS MAIL PLEASE

SERVICE SHEETS, Radio, TV, etc., 50p and s.a.e. Catalogue 20p and s.a.e. **HAMILTON RADIO,** 47 Bohemia Road, St. Leonards, Sussex.

Educational

GO TO SEA as a Radio Officer. Write: Principal, Nautical College, Broadwater Fleetwood FY78JZ.

TELEVISION TRAINING

12 MONTHS' full-time course in Radio & TV for beginners. (GCE—or equivalent—in Maths, and English).

26 WEEKS' full-time course in Mono & Colour TV. (Basic electronics knowledge essential).

13 WEEKS' full-time course in Colour TV. (Mono TV knowledge essential).

These courses incorporate a high percentage of practical training.

NEXT SESSION commences on September 12th.

Prospectus from: London Electronics College, Department B6, 20 Penywern Road, London SW5 9SU. Tel. 01-373 8721.

SERVICE SHEETS, radio, TV etc. 10,000 models. Catalogue 24p, plus SAE with orders, enquiries. Telray, 154 Brook Street, Preston PR1 7HP.

BELLS'S TELEVISION SERVICES For Service Sheets on Radio, TV, etc., 75p plus S.A.E. Colour TV Service Manuals on request. S.A.E., with enquiries to B.T.S., 190 Kings Road, Harrogate, N. Yorkshire. Tel: (0423) 55885.

Electrical

STYLI, CARTRIDGES & AUDIO LEADS etc. For the best at keenest prices send S.A.E. for free illustrated list to: Felstead Electronics (PW), Longley Lane, Gatley, Cheadle, Cheshire. SK8 4EE.

Agents Wanted

Mist Curler



MANUFACTURER AND EXPORTER
Pacific Trading Co. P.O. Box 8173 Hong Kong

Aerials

G2DYM AERIALS

TXers and S.W.L's.—Have a proper aerial system, anti-TVI, individually designed, purpose built for your particular interests. QTH and Equipment by an ex-BBC Transmitter and Aerial Engineer.

Details large S.A.E. and 3 8p stamps.

LAMBDA ANTENNA STUD FARM
WHITEBALL, WELLINGTON,
SOMERSET

Miscellaneous

GOT YOURS YET?

LOW FREQUENCY CONVERTER, 100-600 KHz, 20 dB antenna tuner, feeds 3 5-4 MHz receiver £8-80

TUNABLE AUDIO NOTCH FILTER frees OX from whistles and CW interference, powers speaker £5 30

V L F TUNER, antenna in—audio out, 10-150 KHz £9 70
Each kit includes ALL parts, coils, 1½" x 3" x 5" case, battery etc., instructions, postage, money back assurance, so SEND TODAY.

CAMBRIDGE KITS

45(P.T) Old School Lane, Milton, Cambridge

STATIC RAMS TMS4033 Equiv 2102-2 (Paster) 450NS 1024x1 PW Video writer MPUS £3-25 each 6 up £3-05 each includes data VAT, PP CWO, BSL Associates, 2 Manor Park, Richmond, Surrey.

Miscellaneous (continued)

RECHARGEABLE NICAD BATTERIES
 'AA' (HP7), £1.26; 'Sub C', £1.29; 'C' (HP11), £2.38; 'D' (HP2), £2.92. PP3, £4.98. Matching chargers, respectively, £4.48, £4.48, £5.24, £3.98. All prices include VAT. Add 10% post and package. SAE for full list, plus if wanted, 50p for 'Nickel Cadmium Power' booklet. Sandwell Plant Ltd., 1 Denholm Road, Sutton Coldfield, West Midlands B75 6PP. Tel: 021-354 9764.

MAGNETIC MICROPHONE SPEAKERS

4T Inserts. Ideal for all sound speaking and listening applications. Very rugged—d.c. resistance 20 ohms. Size: 1 1/2" dia. 1/2" deep. 48p ea. + 10p P & P. 6 for £2.20 + 20p P & P. 12 for £4.50 P & P free. S.A.E. for list of many other items. Trade enquiries welcome. B.B. Supplies, 141 Shalmford Street, Nr. CANTERBURY, Kent CT4 7QZ.

SUPERB INSTRUMENTS CASES by Bazelli, manufactured from heavy duty PVC faced steel. Hundreds of people and industrial users are choosing the cases they require from our vast range, competitive prices start at a low 82p. Examples: width, depth, height, 8in x 5in x 3in, £1.70. 10in x 6in x 3in £2.42. 10in x 8in x 3in £3.02. 12in x 10in x 3in £3.96. 8in x 4in x 4in £1.98. 10in x 6in x 4in £2.97. 12in x 8in x 4in £3.96. 7in x 7in x 5in £2.91. 8in x 10in x 6in £3.96. 12in x 8in x 7in £4.40. 12in x 12in x 7in £4.84. Plus 85p carriage and 8% VAT. Over 400 models to choose from. Prompt despatch. Free literature (stamp would be appreciated). Bazelli, Dept No. 25, St. Wilfrid's, Foundry Lane, Halton, Lancaster LA2 6LT.

ENAMELLED COPPER WIRE

swg	1 lb	8oz	4oz	2oz
14-19	2.40	1.20	.60	.50
20-29	2.45	1.60	.80	.59
30-34	2.60	1.70	.85	.64
35-40	2.85	1.90	1.04	.75

Inclusive of p&p and VAT.
 SAE brings Catalogue of copper and resistance wires in all coverings.
THE SCIENTIFIC WIRE COMPANY
 PO Box 30, London E4 9BW
 Reg. Office: 22 Coningsby Gardens,

ARMATURE & COIL WINDING ENAMELLED COPPER WIRE
 Only top quality materials supplied. All orders despatched within 24 hrs.

S.W.G.	1 lb reel	1/2 lb reel
10 to 19	£2.95	£1.80
20 to 29	£3.15	£1.80
30 to 34	£3.45	£1.90
35 to 40	£3.65	£2.10

All prices are inclusive of P. & P. in U.K.
COPPER SUPPLIES, 102 Parrwood Road, Withington, Manchester 20. Tel: 061-445 8733

LOW COST — HIGH EFFICIENCY AUDIO TEST OSCILLATOR £22



RANGE: 10Hz to 100kHz. OUTPUT: 1V, sine/sq. DISTORTION: less than 0.02%, 9V battery. Also available in Kit form at £17. Add 8% VAT. P. & P. and ins. 75p. Leaflet available, also F.M. Signal Generator, Millivoltmeter, freq. meter, THD analyser, P.S. Units. S.A.E. please for literature.
TELERADIO ELECTRONICS
 325 Fore Street, London, N9 0PE
 Tel. 01-807 3719

Musical Miracles!
 by Dewtron®

Build your own synthesiser or musical effects using some of the huge range of DEWTRON modules. Or build fuzz or waa-waa at budget prices using special kits.

Send 25p for Catalogue from—
 D.E.W. Ltd., 254 Ringwood Road, Ferndown, Dorset BH22 9AB.

GORSE'S MAIN STOCKISTS FOR GRUNDIG

Satellit 2100, 21 Wave Band Radio, TK547 and TK747 Stereo Tape Recorders, Radios, Radio/Cassette Recorders, Cassette Recorders, Microphones, etc., etc.
 Please write (send S.A.E.), phone or call for full details and prices.
42-44 CHURCH ST., BLACKBURN Tel: 51682
77 THE MALL BURNLEY Tel: 35220

ELECTRONIC BROKERS LTD

Computer parts for hobby, experimental, educational and professional use.

FRESH STOCKS OF THE POPULAR CLARE-PENDAR ASCII KEYBOARD TYPE KB6 NOW TO HAND

ASCII-Coded TTL-compatible 4-bank alphanumeric keyboards with ROM encoder chip, strobed output, two-key rollover and debounce. Standard 7-bit ASCII code (no parity) supplied complete with circuit diagrams and code chart.

SPECIFICATIONS
 Power Supply: +5VDC +/-5%, 150mA; -12VDC +/-10%, 10mA. Output Logic Levels: Data Bits 1 through 7: 0V; "0": 45V; 2.6V "1": 9.25V. Fan Out: One standard TTL load. Strobe: 2.6V "1": 5.25V; 0V "0": 46V. Fan Out: 10 standard TTL loads. Strobe signal delay 10 milliseconds nominal to allow data to stabilize.
 KB6: 96-station standard Teletype layout. AS RECOMMENDED FOR PRACTICAL WIRELESS VIDEO-WRITER PROJECT. Price £39.50 + £1 P&P + 8% VAT (send £43.74).
ALSO AVAILABLE
SPECIAL LOW COST KEYBOARD
 KBS: 3-bank alphanumeric Baudot-coded 36-station keyboard. TTL-compatible, strobed output. Price £20.00, plus £1 P&P + 8% VAT (send £22.68).
NEW ARRIVALS
FABULOUS NEW 96-STATION CRT DISPLAY KEYBOARDS. 8-bit ASCII code, upper and lower case output PLUS separate numeric pad. TTL Logic. Delayed strobe signal and two-key rollover feature. Mounted in attractive box, overall dimensions 20 1/2" x 7 1/2" x 3 1/2". Price £65.00 + £3 carriage + 8% VAT (send £73.44).
BCD-CODED 54-STATION KEYBOARD, brand new, upper and lower case outputs. Mounted on double PCB and set in attractive panel incorporating 5 indicator lamps and on/off switch. Dimensions 15 1/2" x 5 1/2" x 2 1/2". Price £39.50 + £2 P&P + 8% VAT (send £44.82). Also available. A few only of the above model WITHOUT ENCODING OR PANEL. Price £28.00 + £1.50 P&P + 8% VAT (send £28.62).
18-KEY CALCULATOR KEYBOARDS (0-9, CK + - x =). Make/break switches mounted on PCB. Overall dimensions 150 x 110 x 40mm. Price £4 plus 50p P&P + VAT (send £4.86p).
JUST RECEIVED — SPECIAL PURCHASE OF DATA DYNAMICS MODEL 390 TELETYPE TERMINALS IN BRAND NEW CONDITION.
TERMINALS — LARGE STOCKS AVAILABLE: ASR31 Teletype from £500.00. KSR33 Teletype from £325.00. ASR35 Teletype from £750.00. IBM731/0 Golfball Typewriter from £275.00.
SPECIAL OFFER
 Corsor DIDS 401.2A Visual Display Units. 13 lines x 80 characters (8 1/2 x 4 1/2" screen 64 character repertoire with detachable ASCII keyboard (Control device required). Bargain Price: £145.00. Also available Corsor DIDS 402.2A, as above but incorporating control logic. Price £295.00.
FOR IBM 360 USERS, Sanders 720 Data Display System consisting of six VDUs, control unit and communications buffer. Complete with connecting cables and technical documentation. Price £2,750.00.
MINIATURE MATRIX PROGRAMME BOARDS: Brand new X-Y Matrix boards, with 3mm grating. 3 x 10 positions (1 1/2" x 1 1/2") £4.00. P&P 40p.
MAGNETIC TAPES: Manufacturers surplus stocks, brand new in original sealed packing. 1/2" x 2400' £4.00 per reel. P&P extra.
NAB-centre metal 1" tape spools 10 1/2" dia. in plastic canister. Min. order quantity 5 for £6.25 + £2.50 P&P + 8% VAT (send £9.45).

ELECTRONIC BROKERS LTD
 49/53 Pancras Road
 London NW1 2QB
 Tel: 01-837 7781

PRINTED CIRCUITS and HARDWARE

Readily available supplies of Constructors' hardware, Aluminium sheet and sections. Printed circuit boards, top quality for individual designs. Prompt service. Send 15p for catalogue.

Ramar Constructor Services,
Masons Road, Stratford on Avon,
Warwicks. Tel. 4879

DO-IT-YOURSELF LOUDSPEAKERS for hi-fi are our speciality. Full range of components and accessories including chassis speakers, crossovers, sound absorbent, grille fabrics etc., always available. We stock the fabulous value Helme speaker kits complete with full and easy instructions, also Peerless and Wharfedale kits. Just about the lowest prices anywhere! Send 8½p stamp for bargain list to: Audioscan, Dept. PW-677, 4 Princes Square, Harrogate, North Yorkshire.

BUILD THE TREASURE TRACER MK III Metal Locator



- Varico tuning
- Britain's best selling metal locator kit: 4,000 sold
- Weighs only 22oz. Fitted with Faraday shield.
- Speaker and earphone operation
- Knocks down to only 17in.
- Prebuilt search coil assembly
- Thoroughly professional finish
- As seen on BBC1 and BBC2 TV
- You only need soldering iron, screwdriver, pliers and snips
- Five transistor circuit

Send stamped, addressed envelope for leaflet

Complete Kit £14.75 Built & tested £19.75
Post £1-00-£1-18 VAT Post £1-00-£1-38 VAT

MINIKITS ELECTRONICS,
64 CLEVELAND ROAD,
LONDON, E15 2AN (Mail order only)

MORSE CODE TUITION AIDS
Cassette 3-1-12 w.p.m. for amateur radio examination.
Cassette 5-12-24 w.p.m. for professional examination preparation.
Morse by light system available. Morse Key and Buzzer Unit for sending practice.
Prices: Cassettes (including booklets) £4; Morse Key and Buzzer £4. Prices include VAT, postage, etc., overseas £1 extra.

MHEL ELECTRONICS (PW)
12 Longshore Way, Milton,
Portsmouth PO4 8LS

LOW-COST I.C. MOUNTING for any size DIL package. 100 Soldercon sockets 65p, 7 and 8 hole plastic supports 5p/pair. Quantity rates, SAE details and sample. Trial pack 65p. (P & P 10p/order). P.K.G. Electronics, Oak Lodge, Tansley, Derbyshire DE4 5FE.

H. M. ELECTRONICS
273a FULWOOD ROAD, BROOMHILL,
SHEFFIELD S16 3SD.

BEC CABINETS (illus'd)

**METAL CASES
DRY TRANSFER LETTERING**

Send 15p for leaflets (Refundable)
Trade enquiries invited



A UNIQUE OPPORTUNITY

We can show you how to earn a lot of money working part or full time from home. We are the ONLY company in the U.K. offering this unique information. A basic interest in electrical engineering is necessary. Government Departments are making use of our system, why don't you. For complete return of post details send a large stamped addressed envelope to:-

Magnum
Dept. PW.
Brinkaway Trading Estate,
Brinkaway, Stockport.

NOTICE TO READERS

Whilst prices of goods shown in classified advertisements are correct at the time of closing for press, readers are advised to check with the advertiser both prices and availability of goods before ordering from non-current issues of the magazine.

SOUTHERN VALVE COMPANY

Upper Floor, 8 Potters Road,
New Barnet, Herts. Tel: 01-448 8641

"QUALITY" Branded Valves—90 day guarantee.
ALL NEW & BXD VALVES (incl. tax)—many makes.

AZ31	80p	PC085	44p	PY801	48p
DY36/7	37p	PC088	62p	UBF89	47p
DY802	45p	PC089	50p	UCC85	46p
EB91	18p	PC0189	53p	UCH42	80p
ECC81	35p	PCF80	40p	UCH81	42p
ECC82	35p	PCF82	45p	UCL82	42p
ECC83	34p	PCF86	62p	UCL83	58p
ECC86	40p	PCF200	95p	UF41	72p
ECC88	48p	PCF801	50p	UF89	48p
ECH42	75p	PCF802	55p	UL41	75p
ECH81	42p	PCF806	£1-45	UL84	46p
ECH83	82p	PCF806	75p	UY85	40p
ECH84	82p	PCF808	£1-45	U25	72p
ECL80	52p	PCF200	85p	U26	60p
ECL82	47p	PCL82	40p	U191	60p
ECL83	68p	PCL83	50p	6/30L2	75p
ECL86	50p	PCL84	48p	6BW7	68p
EF80	32p	PCL85	62p	6P23	60p
EF85	37p	PCL86	50p	6P28	75p
EF86	32p	PCL200	£1-40	6V6	60p
EF89	35p	PCL200	£2-70	6L6 (near	90p
EF183	38p	PFL200	73p	equiv KT66)	
EF184	38p	PL35	70p	20L1	70p
EH90	58p	PL36	70p	20P4	70p
EL34	90p	PL81	50p	80C1	40p
EL41	65p	PL81A	54p	80C15	70p
EL84	36p	PL82	38p	80C17	70p
EL909	£2-40	PL83	46p	80C18	£1-45
EM84	50p	PL84	46p	80F5	50p
EY51	47p	PL500	90p	80FL1	97p
EY86/7	38p	PL500A	£1-45	80FL2	35p
EZ40/1	53p	PL508	£1-10	80L15	60p
EZ80	38p	PL509	£2-00	80L17	70p
EZ81	38p	PL519	£2-80	80P12	60p
GY501	£1-10	PL802	£2-00	80P19	70p
GZ30	68p	PY33	52p	80P21	£1-40
PC86	63p	PY81/3	40p	80PL18	75p
PC88	63p	PY800	£1-10	80PL14	35p
PC97	67p	PY800A	£1-10	80PL15	85p
PC900	48p	PY900	48p	80P4MR	90p
PC834	36p				

We offer return of post service. Post free over £15-00. Postage: 1st valve 12p, extra valves 5p. Max. 75p. Minimum order 65p. Most types available, send see for lists. Discount Prices. All prices subject to alteration without notice due to market fluctuations etc. Telephone enquiries welcomed, see with enquiries PLEASE! C.W.O. ONLY. No C.O.D. Export enquiries welcomed. VAT invoices on request. Mail order only.

A MINIATURE POWER TOOL to speed your building

- Super 30 Kit (30 Tools) (incl. drill without stand)
£17-62 plus P. & P. 85p
- Mk. II Drill Stand
£4-40 plus P. & P. 35p
- Mk. II Drill only
£8-79 plus P. & P. 35p
- Flexible Drive Shaft
£5-46 plus P. & P. 25p
- Transformer 240V a.c./12V d.c.
£6 plus P. & P. 70p
- Variable Speed Transformer
£8-25 plus P. & P. 70p

Replacement drills, stones, burrs, etc. 40p each. Circular saw blades 50p each. £2 per set of 4 sizes. P. & P. any quantity 20p.


All VAT inclusive

PRECISION PETITE LTD.

119a High Street, Teddington, Middlesex TW11 8HG

Tel. 01-977 0878 (24 hour answering service)

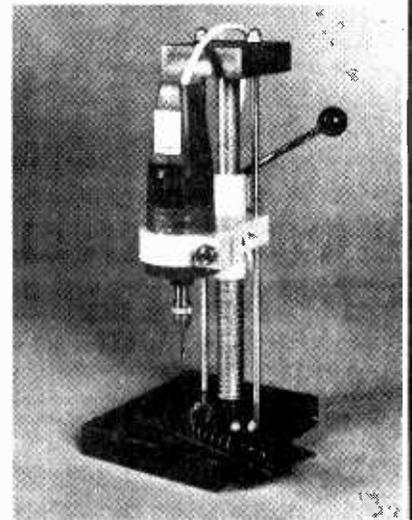9" x 4" S.A.E. please for leaflet and order form



Head Office and Warehouse
44A WESTBOURNE GROVE
LONDON W2 5SF
Tel: 727 5641/2/3

Z & I AERO SERVICES LTD.

Retail Shop
85 TOTTENHAM COURT ROAD
LONDON W1
Tel: 580 8403
Open all day Saturday

Please send all correspondence and Mail-Orders to Head Office

AC/DC TAUT SUSPENSION MULTIMETERS (Made in USSR)




TYPE U4312
Sensitivity D.C. 667 o.p.v.
Sensitivity A.C. 667 o.p.v.
D.C. Current 300 μ A-6A
A.C. Current 1.5mA-6A
D.C. Volts 75mV-900V
A.C. Volts 300mV-900V
Resistance 0-0.02-3k Ω
Capacity —
Accuracy 1% D.C.,
1.5% A.C.

U4313
20,000 o.p.v.
2,000 o.p.v.
60 μ A-1.5A
0.6mA-1.5A
75mV-600V
15V-600V
1K-1M
0.5 μ F
1.5% D.C.,
2.5% A.C.

U4315
20,000 o.p.v.
2,000 o.p.v.
50 μ A-2.5A
0.5mA-2.5A
75mV-1000V
1V-1000V
300 Ω -500k Ω
0.5 μ F
2.5% D.C.,
4% A.C.

TYPE U4341

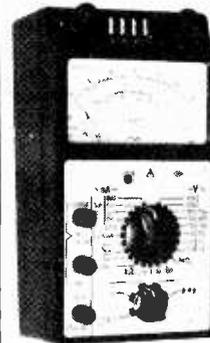


Sensitivity:
1670 Ω /V D.C.,
330 Ω /V A.C.
Ranges:
D.C. current: 0-0.8-
0.6-6-60-600mA
A.C. current 0.3-3-30-
300mA
D.C. Voltage: 0.8-1.8-
6-30-60-150-300-
900V
A.C. Voltage: 1.5-7.5-
30-150-300-750V
Resistance: 2-20-
200 Ω -2M Ω
Transistor collector
cut-off current 60 μ A
Transistor D.C. cur-
rent gain in two
ranges 10-350
Accuracy: 2.5% D.C.
4.0% A.C.
5% D.C.
current gain
Power supplies: 4.5V
battery
(Eveready 1289)

Price complete with pressed steel carrying case and test leads.

£14.50 £17.50 £14.95

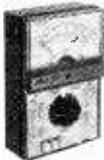TYPES U4313 & U4315 PROVIDED WITH ANTI-PARALLAX MIRROR SCALES



TYPE U4324
Sensitivity: 20,000 Ω /V D.C.
4,000 Ω /V A.C.
D.C. Current: 0.06-0.6-60-600mA-3A
A.C. Current: 0.3-3-30-300mA-3A
D.C. Voltage: 0.6-1.2-3-12-30-60-120-600-1200V
A.C. Voltage: 3-6-15-60-150-300-600-900V
Resistance: 500 Ω -5-50-500k Ω
Accuracy: D.C. 2.5%; A.C. 4% (of F.S.D.)

PRICE complete with test leads and fibreboard storage case **£14.50**

Complete with steel carrying case, test lead, battery and instruction manual **£14.50**

NO OVERLOAD PROTECTION IS INCORPORATED IN THESE INSTRUMENTS

THE ABOVE PRICES ARE EXCLUSIVE OF VAT (at present 8%) HANDLING AND POSTAGE CHARGES **£1.25 PER INSTRUMENT**

OUR NEW 1976/1977 CATALOGUE IS NOW READY AND WILL BE SENT ON RECEIPT OF REMITTANCE FOR **£0.30**



All you need for listening!

Every month 35p

PRACTICAL HI-FI & AUDIO

Listen with the complete hi-fi magazine

Published on approximately the 7th of each month by IPC Magazines Limited, Fleetway House, Farringdon Street, London EC4A 4AD. Printed in England by Index Printers, Dunstable, Beds. Sole Agents for Australia and New Zealand—Gordon and Gotch (Asia) Ltd.; South Africa—Central News Agency Ltd. PRACTICAL HI-FI & AUDIO is sold subject to the following conditions, namely that it shall not, without the written consent of the Publishers first having been given, be lent, resold, hired out or otherwise disposed of by way of Trade at more than the recommended selling price shown on the cover, excluding Hire where the selling price is subject to V.A.T., and that it shall not be lent, resold, hired out or otherwise disposed of in a mutilated condition or in any unauthorised cover by way of Trade or affixed to or as part of any publication or advertising, literary or pictorial matter whatsoever

RADIO EXCHANGE LTD.

**ALL PRICES
INCLUDE VAT**

NEW EDU-KIT MAJOR

Completely Solderless Electronic Construction Kit. Build these projects without soldering iron or solder



Total Building Costs **£9.00**

P & P + Ins. 85p.

- ★ 4 Transistor Earpiece Radio
- ★ 7 Transistor Loudspeaker Radio MW/LW
- ★ Batteryless Crystal Radio
- ★ Signal Tracer
- ★ 5 Transistor Short Wave Radio
- ★ One Transistor Radio
- ★ Signal Injector
- ★ Electronic Metronome
- ★ 2 Transistor Regenerative Radio
- ★ Transistor Tester NPN-PNP
- ★ Electronic Noise Generator
- ★ 3 Transistor Regenerative Radio
- ★ 4 Transistor Push Pull Amplifier
- ★ Sensitive Pre-Amplifier
- ★ Audible Continuity Tester
- ★ 5 Transistor Push Pull Amplifier

Components include: 24 Resistors ★ 21 Capacitors ★ 10 Transistors
 ★ 5" x 3" Loudspeaker ★ Earpiece ★ Mica Baseboard ★ 3 12-watt connectors
 ★ 2 Volume controls ★ 2 Slider Switches ★ 1 Tuning Condenser ★ 3 Knobs
 ★ Ready Wound MW/LW/SW Coils ★ Ferrite Rod ★ 6½ yards of wire
 ★ 1 Yard of sleeving, etc. Complete kit of parts including construction plans.

VHF AIR CONVERTER KIT

Build this Converter Kit and receive the Aircraft Band by placing it by the side of a radio tuned to Medium Wave or the Long Wave Band and operating as shown in the instructions supplied free with all parts. Uses a retractable chrome plated telescopic aerial, Gain Control, V.H.F. Tuning Capacitor, Transistor, etc.

All Parts including Case and Plans. **£3.95**
 P & P and Ins. 45p.




NEW ROAMER TEN MODEL R.K.3.

MULTIBAND V.H.F. AND A.M. RECEIVER
 13 TRANSISTORS AND FIVE DIODES
 QUALITY 5" x 3" LOUDSPEAKER

WITH Multiband V.H.F. section covering Mobiles, Aircraft, T.V. Sound, Public Service Band, Local V.H.F. Stations, etc. and Multiband A.M. section with Airspaced Slow Motion Drive Tuning Capacitor for easier and accurate tuning, covering M.W.1, M.W.2, L.W., Three Short Wave Bands, S.W.1, S.W.2, S.W.3, & Trawler Band. Built in Ferrite Rod Aerial for Medium Wave, Long Wave and Trawler Band, etc., Chrome Plated 7 section Telescopic Aerial, angled and rotatable for peak Short Wave and V.H.F. reception. Push Pull output using 600mw Transistors. Gain, Wave-Change and Tone Controls. Plus two Slider Switches. Negative Feedback circuit and SPECIAL POWER BOOSTER SOCKET AND RESISTOR, to virtually double gain if required. Powered by P.P.9 9 volt battery. Complete kit of parts including carrying strap. Building Instructions and Operating Manuals.

£13.99 Including Post and Packing

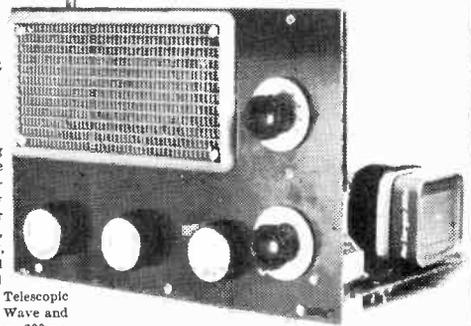Case Enclosure Kit (if required) £1.80 inc. P & P.



POCKET FIVE


NOW WITH 3" LOUDSPEAKER
 3 Tuneable wavebands, M.W., L.W., and Trawler Band, 7 stages, 5 transistors and 2 diodes, supersensitive ferrite rod aerial, attractive black and gold case. Size 5½" x 1½" x 3¼" approx.
 All Parts including Case and Plans.

Total Building Costs **£3.60**
 P & P + Ins. 60p.



NEW Everyday Series

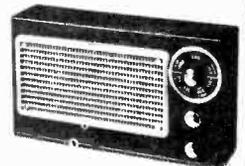Build this exciting new series of designs.



E.V.5. 5 Transistors and 2 diodes. MW/LW. Powered by 4½ volt Battery. Ferrite rod aerial, tuning condenser, volume control, and now with 3" loudspeaker. Attractive case with red speaker grille. Size 9" x 5½" x 2¼" approx. All parts including Case and Plans.

Total Building costs **£4.30** P & P + Ins. 60p.

E.V. 6. Case and looks as above. 6 Transistors and 3 diodes. Powered by 9 volt battery. Ferrite rod aerial, 3" loudspeaker, etc., MW/LW coverage. Push Pull output. All parts including Case and Plans.

Total Building costs **£4.95** P & P + Ins. 65p.


E.V. 7. Case and looks as above, 7 Transistors and 3 diodes. Six wavebands, MW/LW, Trawler Band, SW1, SW2, SW3, powered by 9 volt battery. Push Pull output. Telescopic aerial for short waves. 3" Loudspeaker. All parts including Case and Plans.

Total Building costs **£6.95** P & P + Ins. 70p.

ELECTRONIC CONSTRUCTION KITS

ECK2 Self Contained Multi-Band V.H.F. Receiver Kit. 8 Transistors and 3 Diodes. Push/Pull output. 3" Loudspeaker. Gain Control. Superb 9 section swivel ratchet and retractable chrome plated telescopic aerial. V.H.F. Tuning Capacitor. Resistors, Capacitors, Transistors, etc. Will receive T.V. Sound, Public Service Band, Aircraft, V.H.F. Local Stations, etc. Operates from a 9 Volt PP7 Battery (not supplied with kit). Complete kit of parts including construction plans.


£7.95 P & P and Ins. 70p.

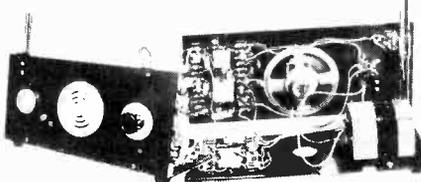

ECK4 7 Transistors, 6 tuneable wavebands, MW, LW, Trawler Band, 3 Short Wave Bands. Receiver Kit. With 5" x 3" Loudspeaker.

Push/Pull output stage, Gain Control, and Rotary Switch. 7 Transistors and 4 Diodes. 6 section chrome-plated telescopic aerial. 8" Sensitive Ready Wound Ferrite Rod Aerial. Tuning Capacitor. Resistors, Capacitors, etc. Operates from a 9 Volt PP7 Battery (not supplied with kit). Complete kit of parts including construction plans. **£7.25**


P & P and Ins. 70p.

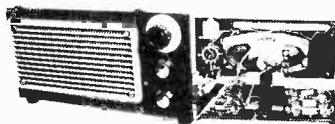

EDU-KIT JUNIOR

Completely Solderless Electronic Construction Kit. Build these projects without Soldering Iron or Solder.

- ★ Crystal Radio Medium Wave Coverage — No Battery necessary.
- ★ Electronic Metronome.
- ★ One Transistor Radio.
- ★ 4 Transistor Push/Pull Amplifier.
- ★ 2 Transistor Regenerative Radio
- ★ All parts including Loudspeaker, Earpiece, MW Ferrite Rod Aerial, Capacitors, Resistors, Transistors, etc.
- ★ 3 Transistor Earpiece Radio Medium Wave Coverage.
- ★ Complete kit of parts including construction plans.
- ★ 4 Transistor Medium Wave Loudspeaker Radio.
- ★ **£6.55** P & P + Ins. 60p.
- ★ Electronic Noise Generator

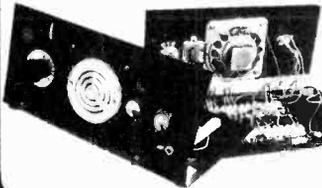

To RADIO EXCHANGE LTD
 61A HIGH STREET, BEDFORD MK40 1SA
 Tel: 0234 52367

ALL PRICES INCLUDE VAT Reg. No. 788372



- ★ Callers side entrance "Lavells" Shop.
- ★ Open 10-1, 2.30-4.30. Mon-Fri. 9-12 Sat.

I enclose £.....
 for
 Name
 Address

MAPLIN



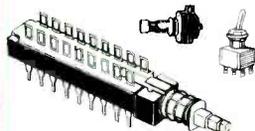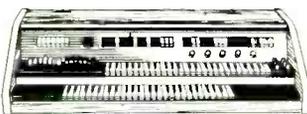
The only organ you can build in stakes and tailor to your requirements as you go along—and at each stage you'll have a fully working instrument! We haven't got the gimmicks (yet—they're coming soon), but we have got the most beautiful sounds—you won't find them on any organ less than twice our price. So get our MES50 series leaflets now! 65p buys the three available so far.



We stock a wide range of switches including a really low-priced high quality interlocking push-button switch system, which is extremely versatile. We've got toggle switches, slide switches, push switches, rotary switches—there are dozens to choose from, but it's only a tiny part of our fantastic range.



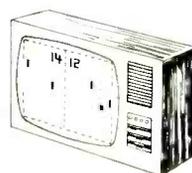A completely self-contained pedal unit. 13-note, 2-octave range. 4 organ stops. It can be added to any organ! A really unusual extra is the bass guitar stop which uses four envelope shapers to give a real bass guitar sound. A must for the solo guitarist. Full construction details in our catalogue—post the coupon below now!



Play fascinating games NOW on your own t.v. in your own living room. The kids will think it's magic when the scores pop up on the screen. Lay your bets—anyone could win—with Maplin's prices everyone can win. Get the May edition of Electronics Today International now—then get all the parts from us at a remarkably low price (I.C. alone £11.99). All prices include VAT and P & P. Complete kit £24.50. Please add 35p to kit price for copy of constructional details.



AY-3-8504. Special offer price £8.99 inc. VAT and P & P.



Our bi-monthly newsletter keeps you up to date with latest guaranteed prices — our latest special offers (they save you pounds) — details of new projects and new lines. Send 30p for the next six issues (5p discount voucher with each copy).

MAPLIN ELECTRONIC SUPPLIES

P.O. BOX 3 RAYLEIGH ESSEX SS6 8LR

Telephone: Southend (0702) 715155

Shop: 284, London Road, Westcliff-on-Sea, Essex

(Closed on Monday) Telephone: Southend (0702) 47379

IT'S A FANTASTIC BESTSELLER!

216 big (11" x 8") pages! Over a thousand illustrations!
Over 30 pages of complete projects to build!
Thousands and thousands of useful components described and illustrated! No wonder it's a bestseller!
DON'T MISS OUT! SEND 50p NOW!

POST THIS COUPON NOW FOR YOUR COPY OF OUR CATALOGUE PRICE 50p

Please rush me a copy of your 216 page catalogue by return of post. I enclose 50p, but understand that if I am not completely satisfied I may return the catalogue to you within 14 days and have my 50p refunded immediately.

NAME _____

ADDRESS _____

PWS



Rayleigh Essex