

PRACTICAL WIRELESS



JULY 1977

40p



24-HOUR DIGITAL CLOCK

with PRECISION TIME SWITCH

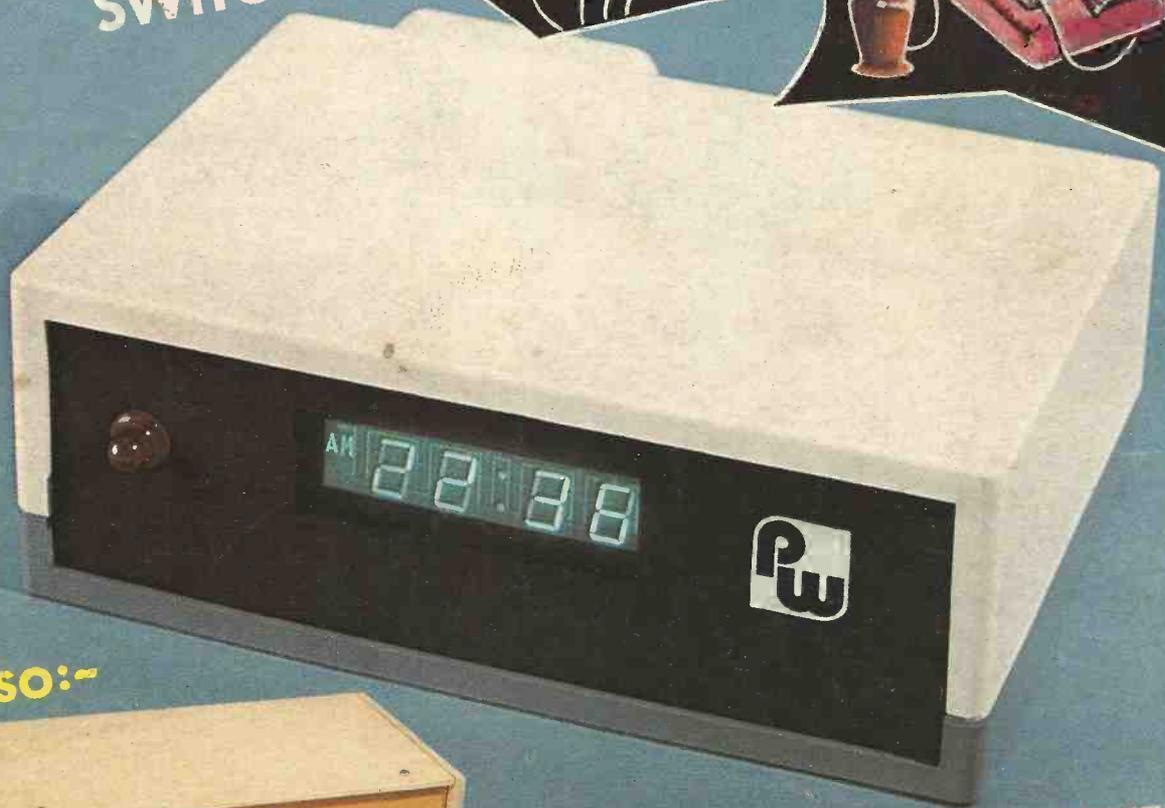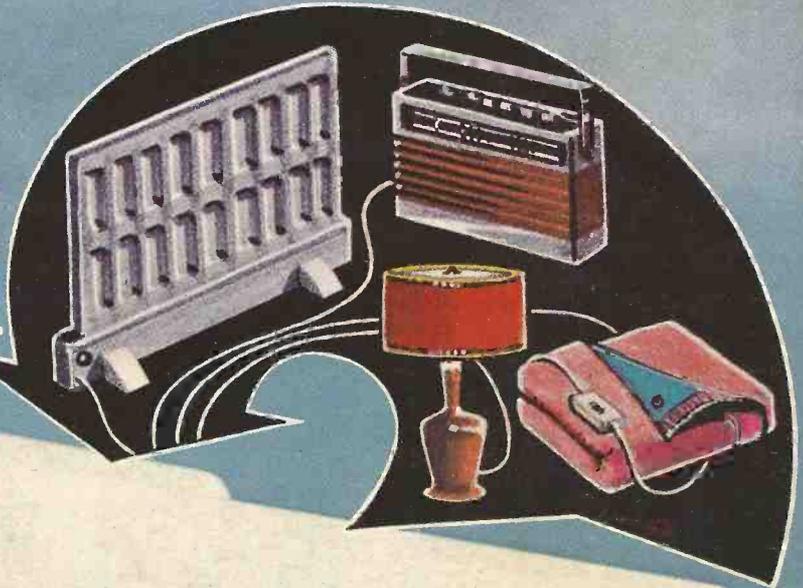

Also:-



20W IC
AUDIO AMPLIFIER



RADIO 2 TUNER
FOR YOUR
HI-FI

T.T.L. 74 I.C.'s By TEXAS, NATIONAL, I.T.T., FAIRCHILD Etc

7400	14p	7413	30p	7432	25p	7454	15p	7490	35p	74121	25p	74139	100p	74156	70p	74174	100p	74189	350p
7401	14p	7414	60p	7437	25p	7460	15p	7491	75p	74122	40p	74141	60p	74157	70p	74175	75p	74190	140p
7402	14p	7416	30p	7438	25p	7470	30p	7492	45p	74123	60p	74142	270p	74160	90p	74176	100p	74191	140p
7403	14p	7417	30p	7440	15p	7472	25p	7493	40p	74125	50p	74143	270p	74161	90p	74177	100p	74192	120p
7404	14p	7420	15p	7441	65p	7473	30p	7495	60p	74126	50p	74144	270p	74162	90p	74178	140p	74193	120p
7405	14p	7422	20p	7442	65p	7474	30p	7496	70p	74130	130p	74145	75p	74163	90p	74179	140p	74194	100p
7406	40p	7423	25p	7445	80p	7475	30p	74100	95p	74131	100p	74147	230p	74164	125p	74180	100p	74195	75p
7407	40p	7425	25p	7446	85p	7476	30p	74104	40p	74132	65p	74148	160p	74165	125p	74181	200p	74196	100p
7408	20p	7426	25p	7447	75p	7477	30p	74105	40p	74135	100p	74151	65p	74166	125p	74182	75p	74197	100p
7409	20p	7427	25p	7448	70p	7478	30p	74107	30p	74136	80p	74152	65p	74167	325p	74183	150p	74198	185p
7410	15p	7428	40p	7450	15p	7479	100p	74109	50p	74137	100p	74153	65p	74170	200p	74184	150p	74199	185p
7411	20p	7429	40p	7451	15p	7480	30p	74118	90p	74138	125p	74154	120p	74173	150p	74185	150p		
7412	20p	7430	15p	7453	15p	7489	250p	74120	90p			74155	70p	74174	150p	74188	350p		

SEMICONDUCTORS

by MULLARD, TEXAS, MOTOROLA, SIEMENS, I.T.T., R.C.A.

AA113	10p	BA138	16p	BC168B	14p	BC548C	14p	BF123	45p	BF336	35p	BY164	50p	OC140	150p	TIP35A	230p	2N1305	30p
AA144	10p	BA148	16p	BC168C	15p	BC549B	13p	BF125	45p	BF337	35p	BYX94	8p	OC171	40p	TIP35C	280p	2N1306	38p
AAZ17	30p	BA154	12p	BC169C	15p	BC549C	14p	BF127	50p	BF363	60p	C1120	30p	OC200	80p	TIP36A	350p	2N1308	50p
AC121	30p	BA157	15p	BC171	12p	BC557	13p	BF166	30p	BF594	30p	C1164	20p	ORP12	70p	TIP41A	70p	2N1711	22p
AC126	19p	BA173	15p	BC172C	12p	BCY34	80p	BF167	25p	BF598	20p	E100	42p	R1039	150p	TIP41B	75p	2N2219A	25p
AC127	19p	BA216	16p	BC178A	16p	BCY70	15p	BF173	25p	BFX29	30p	E300	47p	TIP29	45p	TIP41C	80p	2N2483	30p
AC127/01	25p	BA316	16p	BC182	10p	BCY71	20p	BF179	35p	BFX81	130p	E430	125p	TIP29A	47p	TIP42A	80p	2N2906	18p
AC128	18p	BAX13	5p	BC182L	12p	BCY72	15p	BF179C	40p	BFX84	25p	MJE340	45p	TIP29C	75p	TIP42B	85p	2N2907	20p
AC151	25p	BAX16	5p	BC183	10p	BD121	85p	BF180	30p	BFX85	30p	MPSA06	25p	TIP30	55p	TIP2955	70p	2N3053	20p
AC153K	40p	BB105A	35p	BC183L	12p	BD123	100p	BF181	35p	BFX87	25p	OA10	40p	TIP30A	58p	TIP3055	55p	2N3054	50p
AC176	20p	BB110	45p	BC184	10p	BD124	85p	BF182	30p	BFX88	25p	OA47	15p	TIP30B	65p	TI590	25p	2N3055	60p
ACY17	35p	BC107	10p	BC184L	12p	BD131	36p	BF183	30p	BFY50	20p	OA90	6p	TIP30C	80p	TI591	25p	2N3439	50p
AD149	60p	BC108	10p	BC186	24p	BD132	39p	BF186	25p	BFY51	20p	OA91	6p	TIP31	55p	IN914	5p	2N3702	11p
AD161	40p	BC109	10p	BC205	14p	BD133	45p	BF194	10p	BFY52	20p	OA202	8p	TIP31A	58p	IN3754	10p	2N3703	12p
AD162	40p	BC109C	14p	BC212	11p	BD135	40p	BF195	10p	BFY90	125p	OC23	200p	TIP31B	65p	IN4001	5p	2N3704	11p
AD161/2MP	90p	BC113	12p	BC212L	12p	BD136	40p	BF196	10p	BR101	35p	OC25	100p	TIP31C	70p	IN4002	5p	2N3705	12p
AF114	22p	BC117	19p	BC213L	12p	BD137	40p	BF197	10p	BRV39	35p	OC28	75p	TIP32	60p	IN4003	5p	2N3706	11p
AF115	22p	BC125	20p	BC214	13p	BD139	38p	BF198	25p	BRV56	35p	OC35	75p	TIP32A	65p	IN4004	5p	2N3711	12p
AF116	22p	BC126	15p	BC214L	14p	BD140	40p	BF199	25p	BSX20	20p	OC42	35p	TIP32B	85p	IN4005	5p	2N3715	300p
AF117	22p	BC146	12p	BC258	13p	BD141	40p	BF200	30p	BSY40	25p	OC43	35p	TIP32C	90p	IN4006	6p	2N3772	175p
AF118	50p	BC147	10p	BC294	35p	BD181	80p	BF224	20p	BSY95	20p	OC45	35p	TIP33	100p	IN4007	7p	2N3819	25p
AF125	25p	BC148	10p	BC303	55p	BD182	80p	BF225	20p	BT100A	80p	OC71	25p	TIP33A	105p	IN4008	4p	2N3864	95p
AF139	35p	BC149	14p	BC317	15p	BD207	70p	BF241	16p	BU133	75p	OC72	30p	TIP33B	115p	IN4148	4p	2N3904	15p
AF239	45p	BC149C	14p	BC323	60p	BD233	50p	BF244B	35p	BU208	220p	OC75	30p	TIP33C	130p	IN456A	90p	2N4062	14p
ASV26	40p	BC157	10p	BC328	13p	BD263	65p	BF257	26p	BY100	20p	OC81	30p	TIP34	115p	2N697	15p	2N4126	20p
BA114	9p	BC159	10p	BC338	12p	BDY10	100p	BF258	26p	BY126	15p	OC81D	25p	TIP34A	118p	2N929	20p	2N5061	35p
BA121	9p	BC167A	12p	BC347	12p	BDY82/01	90p	BF259	30p	BY127	15p	OC83	50p	TIP34B	145p	2N930	20p	2N5163	35p
				BC347B	13p	BF120	50p	BF274	15p	BY133	22p	OC84	50p	TIP35	225p	2N932	20p	2N6027	50p
				BC348	12p	BF121	45p	BF324	30p							2S234	50p		

BZX61	Zeners	1-3W	12V	10p	
			13V	10p	
			15V	10p	
			18V	10p	
			20V	10p	
			22V	10p	
			27V	10p	
			30V	10p	
			33V	10p	
			100 Mixed	100p	
			Zeners 850p	850p	
			Zeners 850p	850p	
			Zeners 850p	850p	
			47V	15p	
			51V	15p	
			56V	15p	
			68V	15p	
			72V	15p	
			160V	15p	
BZY88	400M.W. Zeners		LM723	14P DIL	60p
			LM741	8P DIL	75p
			LM747	14P DIL	25p
			LM748	8P DIL	30p
			NE555	8P DIL	80p
			ME556	14P DIL	45p
			TA A300		35p
			TA A350		33/40
			TA A550		0.01
			TA A570		0.0022
			TA A700		0.0033
			TAD100		0.0047
			TAD110		0.0068
			TBA120		0.01
			TBA120		0.022
			TBA120		0.033
			TBA120		0.047
			TBA120		0.075
			TBA120		0.1
			TBA120		0.15
			TBA120		0.22
			TBA120		0.33
			TBA120		0.47
			TBA120		0.75
			TBA120		1.0
			TBA120		1.5
			TBA120		2.2
			TBA120		3.3
			TBA120		4.7
			TBA120		6.8
			TBA120		10
			TBA120		15
			TBA120		20
			TBA120		30
			TBA120		40
			TBA120		720
		</			

PRACTICAL WIRELESS

VOL. 53 NO. 3

ISSUE 845

JULY 1977

BRITAIN'S PREMIER MAGAZINE FOR THE DO-IT-YOURSELF RADIO AND ELECTRONICS CONSTRUCTOR

EDITOR

Lionel E. Howes, G3AYA

ASSISTANT EDITOR

Eric Dowdeswell, G4AR

ART EDITOR

Peter Metall

PRODUCTION & NEWS

EDITOR

Bill Tull

TECHNICAL ARTIST

Alan Martin

TECHNICAL SUB-EDITOR

Frank Ogden

SECRETARIAL

01-634 4292

Linda Walji

Belinda Mould

ADVERTISING MANAGER

01-634 4612

Roy Smith

CLASSIFIED ADVERTISING

01-261 5762

Colin R. Brown

PLEASE NOTE: We do not operate a Technical Query Service except on matters concerning constructional articles published in PW. We do not supply service sheets or information on commercial radios, TV's or electronic equipment.

All queries must be accompanied by a stamped, self-addressed envelope otherwise a reply cannot be guaranteed.

Send letters concerning advertising matters to the **Advertising Manager, Roy Smith.**

Send letters concerning editorial matters to the **Editor, Lionel Howes.**

Published by IPC Magazines Ltd., Fleetway House, Farringdon Street, London EC4A 4AD. Tel. 01-634 4444

BINDERS

Binders £2.10 and indexes 45p (inc. VAT) can be supplied by the Post Sales Department, IPC Magazines Ltd., Lavington House, 25 Lavington Street, London, SE1 0PF.

Remittances with overseas orders for binders should include 60p to cover despatch and postage.

Due to an enlarged format, shortly to be announced, there will be a delay in supplying larger sized binders for Volume 53.

COPYRIGHT AND QUERIES

© IPC Magazines Limited 1977. Copyright in all drawings, photographs and articles published in "Practical Wireless" is fully protected and reproduction or imitation in whole or in part is expressly forbidden. All reasonable precautions are taken by "Practical Wireless" to ensure that the advice and data given to readers are reliable. We cannot, however, guarantee it and we cannot accept legal responsibility for it. Prices are those current as we go to press.

We regret that we cannot answer technical queries by telephone nor can we provide information or advice on manufacturers' products other than that given in the magazine. We will endeavour to assist readers who have queries relating to articles published but we cannot offer advice on modifications to our published designs. All correspondents expecting a reply should enclose a stamped addressed envelope.

Practical Wireless, July 1977

● NEWS & COMMENT

- 180 LEADER ARTICLE—Something For Nothing
- 180 NEWS . . . NEWS . . . NEWS . . .
- 190 PW READERS PCB SERVICE
- 199 TELEVISION—What's in the July issue?
- 200 LETTERS—comments from PW readers
- 202 HOTLINES—Recent Developments—*Ginsberg*
- 203 NEXT MONTH IN PRACTICAL WIRELESS
- 210 PRODUCTION LINES—*Bill Tull*
- 222 KINDLY NOTE—Tug-O-War April '77
- 225 ON THE AIR—Amateur Bands—*Eric Dowdeswell G4AR*
Broadcast Bands SW—*Derek Bell*
Broadcast Bands MW—*Charles Molloy*
VHF—*Ron Ham*

● CONSTRUCTIONAL

- 182 20W IC AUDIO AMPLIFIER—*F. G. Rayer G3OGR*
- 186 MEASURING WITH OP-AMPS—*A. Sharpe*
- 188 S-DeCNOLOGY No. 8—Ultra simple audio amplifier—
David Gibson
- 193 A 741 SIGNAL TRACER—*W. Mooney G3VZU*
- 204 24-HOUR DIGITAL CLOCK with precision time switch—
John Miller-Kirkpatrick
- 213 A RADIO 2 TUNER FOR YOUR HiFi—*R. A. Penfold*

● OTHER FEATURES

- 198 THE PARIS SHOW—A report from *David Gibson*
- 216 IC OF THE MONTH No 63—RCA CA3140 Op-Amp—
Brian Dance
- 219 HIGH FIDELITY '77 REPORT—*Richard Schofield*
- 222 RNARS MORSE PROFICIENCY TRANSMISSIONS
- 222 CQ . . . CQ . . . CQ . . .

GREENWELD

443 Millbrook Road Southampton
SO1 0HX Tel: (0703) 772501

71b BARGAIN PARCEL

Hundreds of new components—pots, switches, resistors, capacitors, PC Boards with semiconductors, loads of odds and ends. Amazing value at only £3.30.

COMPUTER PANELS

Large quantity always available; 31b asstd. £1.75; 71b £3.65; 561b £16. Pack with about 500 components inc. at least 50 transistors £1.00; Pack with 12 high quality panels, incl. IC's, power transistors, multi-turn trim pots, hundreds of small signal transistors, resistors, zeners, capacitors, etc. Only £2.75. 7400 IC pack—20 74 series IC's on panels £1.20.

PC ETCHING KIT MK III

Now contains 200 sq. ins. copper clad board, 1lb. Ferric Chloride, DALO etch-resist pen, abrasive cleaner, two miniature drill bits, etching dish and instructions. £4.15.

FERRIC CHLORIDE

Anhydrous technical quality in 1lb double sealed packs. 1lb £1.00; 3lbs £2.10; 10lbs £5.60; 100lbs £39.00.

FIBREGLASS PCB

Large quantity of offcuts, all usable pieces. 200 sq ins, single sided, double sided or mixed £1.40.

DEVELOPMENT PACKS

50V ceramic plate capacitors, 5%, 10 of each value 22pF to 1000pF, total 210 caps. £2.70.
CR25 carbon film 1/3rd watt resistors, 5%, 10 of each value 10 ohms to 1M. Total 610 resistors £6.00. Electrolytics, wire ended 25V working 10 each of: 1, 2, 4, 7, 10, 22, 47 and 100mfd. 70 capacitors for £3.20. 400mW zeners 5% 10 each 3V to 30V, 260 in all. Only £14.00.
1 watt Metal Film resistors, 5% 10 of each value 27R to 10M, E12 series. Total 680 resistors £12.00.
Polystyrene capacitors, 160V 2½% 10 of each value from 10pF to 10,000pF. Total 370 capacitors £12.50.

COMPONENT PACKS

400 asstd. carbon resistors £1.35
100 Wirewounds 2-15W £1.90
200 Miniature resistors, ½, 1 and 1½W, £1.20
200 poly, mica, ceramic caps £1.10
100 Polyester, .01-2.2µF £1.00
200 miniature electrolytics, but many unmarked so only £1.00

TAPE DECKS

Data Tape Deck by D-Mac. Reel-to-reel, takes 3" spool. 2 heads, 12V motor. 3 position switch. 17 transistors, R's, C's, 200V 6A SCR, min 6V relay, etc. In good condition, but not new. Size 225 x 165 x 120mm high. **Reduced to clear £4.**

1 WATT AMPLIFIER

PCB 100 x 80mm with LM380 and associated components to make 1W amp operating from 9V. (Can be increased to 3W output by raising supply voltage and fitting heat sink). Complete with volume control. Connexion sheet included. Also on the board is a speed control circuit comprising 10 transistors, 2 presets, 4 pole 3 way switch, etc., but no data on this. Only £1.

5V 12A REGULATED POWER SUPPLY

Brand new boxed fully stabilized PSU, complete with instruction manual. Load regulation 0-15%. Thermal & Electronic overload protection. Only £24.00.

1977 CATALOGUE NOW AVAILABLE—MUCH BIGGER AND BETTER, WITH DISCOUNT VOUCHERS. ONLY 30p + 15p POST.

Our retail shops at 21 Deptford Broadway, London, SE8 (01-692 2000) and 38 Lower Addiscombe Road, Croydon (01-882 2850) stock some of the advertised goods for personal callers only. Ring them for details. All prices quoted include VAT and UK/BFPO postage. Most orders despatched on day of receipt. SAE with enquiries please. **MINIMUM ORDER VALUE £1** Official Orders accepted from Schools, etc. (Minimum invoice charge £5). Export/Wholesale enquiries welcome. Wholesale list now available for bona-fide traders. Surplus components always wanted.



BOXES, CASES & BOARD

OFFCUTS

Pack A, All 0.1"
Pack B, All 0.15"
Pack C, Mixed
Pack D, All 0.1" plain
Each pack contains 7 or 8 pieces with a total area of 100 sq ins. Each pack is £1.30. Also available by weight, 11b £3.45, 10lbs £28.
We are also VERO wholesalers—Trade price list on request from Bone Fide Companies.

VEROCASES

Plastic top and bottom, ally panels front and back.
Type 1410 205 x 140 x 40mm £3.30
1411 205 x 140 x 75mm £3.70
1412 205 x 140 x 110mm £4.00
1237 154 x 85 x 40mm £2.30
1238 154 x 85 x 60mm £2.80
1239 154 x 85 x 80mm £3.60

PLASTIC BOXES

Professional quality, two tone grey polystyrene with threaded inserts for mounting PC Boards.
Type 2518 120 x 65 x 40mm £2.25
2520 150 x 80 x 50mm £2.60
2522 188 x 110 x 60mm £3.50



Sloping front version,
Type 2523 220 x 174 x 100/52mm £6.60
Type 1798 171 x 121 x 75/37.5mm £4.50
Gen Purpose plastic potting box 71 x 49 x 24. In black or white 40p
Hand Controller box, shaped for ease of use in the hand, 94 x 61 x 23mm 62p

S-DECS & T-DECS

S-DEC Breadboard £2.10
T-DEC Breadboard £3.75

MULTIMETER MODEL LT22



WHAT A BARGAIN

Probably one of the lowest priced meters featuring a mirror scale, overload protection and 20000 ohms per volt sensitivity. A modern styled meter with unusually clear scale markings. Ranges: DC Volts 0-0.5-2-5-10-50-250-1000 AC Volts 0-10-50-250-1000 DC Current 0-50µA-25mA-250mA Resistance 0-50k-500k-5M (Mid Scale 300-3k-30k) db's 4 ranges -20db to +42db. Size 130 x 90 x 42mm. £12.70.

TRANSFORMERS

All have mains primaries, secondaries as follows: 0-0-8V 100mA 85p; 0-0-9V 75mA £1.00; 12-0-12V 50mA 95p; 12-0-12V 100mA £1.10; 6.3V 1A £1.95; 0-0-8V 1½A £2.30; 0-0-9V 1A £2.55; 12-0-12V 1A £2.85; 12V 5A £3.45; 12V 8A £4.35; 20V 55mA 90p; 22V 100mA £1.00; 29V 50mA 85p; Multitapped types, 0-12-15-20-24-30V 1A £3.50; 2A £5.00; 20-0-20V 2A £4.40; 24V 500mA £1.65.

Random Flasher Unit

Wired ready for use
Complete with three 100 watt coloured lamps that flash independently at random.

£18.95

TWIN BANK 6 LIGHT UNIT

(less lamps) LENGTH 14 1/2 inches

BC Fitting £9.55 EACH
E.S. Fitting £10.35 EACH

Sound to Light MASTER UNIT

600 WATTS PER CHANNEL

£30.95

INCLUDING CHANNEL OUTPUT PLUGS AND MAINS INPUT SOCKET.

TYPE A SPOT

(less lamp)

BC Fitting £1.95 EACH
E.S. Fitting £2.12 EACH

TYPE B 3 BANK UNIT

(Less Lamps)

BC Fitting £6.90 EACH
E.S. Fitting £7.26 EACH

TWIN BANK 12 LIGHT UNIT

Length 31 3/4

(less lamps)
BC Fitting £15.60 EACH
E.S. Fitting £17.00 EACH

100 WATT SPOT LAMPS

RED, YELLOW, GREEN, BLUE, CLEAR

Maximum 3 lamps
£1.40 each
B.C. or E.S. Fitting

ALL PRICES INCLUDE V.A.T. and POST & PACKING (These prices apply to the United Kingdom only)
Send 20p for illustrated leaflet & price list.
ALBEN ENGINEERING CO. LTD.
DEPT. PW THE CRESCENT, WORSTHORNE,
BURNLEY, LANCs. Tel: Burnley 20940

Doram kits

DORAM KITS CONTAIN EVERYTHING DOWN TO THE LAST NUT!

CMOS MORSE KEYS

£9.45 + H

Fully electronic automatic morse keyer giving perfectly spaced dots and dashes of correct duration. Sidetone or silent operation with variable speed to suit novice or expert. Very low current drain on internal battery. Single paddle operation; suitable for most transmitters with a keying facility. Give your morse that precision quality.

As featured in Sept '76 edition of RAD. COMM.

£9.45 + H VAT (Order 997-049)
Subject to availability

Overseas orders—add 15% for p & p. All items offered for sale subject to the Terms of Business as appears in Doram Edition 3 catalogue, price 60p. The Doram Kit brochure is also available, price 25p. Combined price only 70p which also entitles you to 2 x 25p vouchers each one usable on an order placed to the value of £5.00 or more (ex VAT).

DORAM ELECTRONICS LTD P O BOX TR8 WELLINGTON
ROAD INDUSTRIAL ESTATE LEEDS LS12 2UF
An Electrocomponents Group Company

RSC 100 WATT DISCO SYSTEM ALL RSC PRICES INCLUDE VAT

AT A FANTASTIC LOW PRICE

Consisting of
 (1) TWIN T/TABLE CONSOLE with PRE-AMP, and POWER OUTPUT STAGES
 (2) & (3) PAIR 50 WATT L'SPEAKERS including 12" UNITS

Price includes High Quality Dynamic Stick Microphone and VAT

★ DISCOMAJOR POWER DISCO CONSOLE with integral Power Amplifier. Twin Jack output sockets

★ TWIN FULL SIZE B.S.R. TURNTABLES with cueing device.

★ CARTRIDGES with Diamond Styli

★ 3 SEPARATE VOLUME CONTROLS for each turntable and Microphone FULL HEADPHONE MONITORING FACILITIES CONSOLE COMPLETE WITH LID

Terms: Deposit £30.00 and 18 fortnightly pymts £9.18 (Total £195.24) Carr. £4.00

£169.95

Also available: 200 WATT SYSTEM £199.95 Carr. £3.00

TDI DISCO CONSOLE

Incorporating twin BSR type turntables and Sonotone or Acos Cartridges with diamond styl. Separate Vol. controls for each turntable. Also MONITORING FACILITIES, plus Treble and Bass Controls. Separate input for 'mike' with vol. control. Black Vynide covered Cabinet with lid. Or DEP. £18.49 and 18 fortnightly pymts. £6.11 (Total £126.47) Carr. £3

£109.95

TD2S STEREO VERSION OF ABOVE

£125.00 Carr. £3.00

40 WATT SYSTEM £99.95. 200 WATT SYSTEM £199.95 WRITE OR PHONE for Free catalogue
 OTHERS UP TO 300 WATTS AT UNBEATABLE PRICES

DISCOMAJOR/100 TWIN TURNTABLE POWER CONSOLE £129.95

Twin Full size BSR turntables. Sonotone or Acos Cartridges with Diamond Styli. Facilities as TDI Console but with built-in 100 watt Power Amplifier complete with lid. Terms: Deposit £19.95 and 18 fortnightly pymts. £7.08 (Total £148.49) Carr. £3.00

DISCOMAJOR/200 £149.95
 200 watt version of above. Terms: Dep. £29.95 and 18 fortnightly pymts £7.87 (Total £171.61)

RSC PHANTOM 50 COMBO AMP. £69.95

Rating 50 watts. 3 inputs. 2 vol. controls—Bass, Treble Presence. Carr. £1.50 Suitable for Lead or Rhythm Guitar, mic., Radio, Tape etc. Inc. High Flux 12" 50w Speaker. Dep. £10.95 & 8 mthly pymts £8.71 (Total £80.63)

PHANTOM 50G with twin 12" speakers **£75.95**

100W POWER (SLAVE) AMPLIFIER

Suitable for use with DISCO-Consoles. Also for increasing output of lower-powered Amp. Dep. £9.00 and 8 mthly pymts of £6.05 (Total £57.40) Carr. £1.50

100 + 100W MODEL £69.95 Carr. £1.50

TITAN TA/50A 50W AMPLIFIER

Solid state, 3 sep. controlled inputs plus Master control. Bass, Treble & Presence Controls. Vynide covered cab. with corner protectives. List price £60. Terms: Dep. £9 & 8 monthly pymts £6.05. **£49.95** Carr. £1. (Total £57.40)

Matching Cabinet Spkrs. 1 x 12" £29.95 2 x 12" £49.95

TITAN TA/100A 100W AMPLIFIER

TWIN CHANNEL—4 INPUTS **£69.95** (NORMAL OR BRIGHT) Carr. £1.50
 A De-luxe professional unit with many facilities. R.M.S. Rating. Matching 2 x 12" 120w Cabinet speaker £49.95. with above only. Carr. £1.50

INTEREST REFUNDED on Credit Purchases settled in 3 mths

TITAN 'ADD-ON' HIGH FREQUENCY HORN UNITS

MODEL TSEH
 Inc. Pair of highly sensitive Horns. Range 3-15 kHz Imp 16Ω. Use with 8 or 15Ω 2 x 12" or 1 x 15" or 18" Drive Unit for increased sound clarity and projection. Rating 100 watts.
 Either model **£27.95** Carr 75p. Comparable with units at twice the cost. Terms: Dep £6.95 & 8 mthly pymts. £3.12 (Total £31.91)

MODEL T1H
 With single super efficient Horn. Range 3-15 kHz. Imp 8Ω. Use with max 8Ω 2 x 12" or single 15" or 18" 8Ω Drive Units. Maximum amplifier power output to be 100 watts.

FANE HIGH FREQUENCY HORNS 'J' SERIES

MODEL J44 Imp 8Ω Size approx 3 1/2" x 3 1/2" x 3" Rating 30-50 watts Range 3-15 kHz **£7.95**

MODEL J73 Imp 8Ω Size approx 7 1/2" x 3" x 6 1/2" Rating 50 watts Range 2-20 kHz **£11.95**

MODEL J104 Imp 8Ω Size approx 10 1/2" x 3 1/2" x 7 1/2" Rating 50-70 watts Range 2-15 kHz **£15.50**

RSC MAINS TRANSFORMERS

TYPES FOR VALVE AMPLIFIERS (Inc. L.F. CHOKES & RADIOS & FILAMENT OR TRANSISTOR POWER PACK)

OUTPUT TRANSFORMERS. As previously advertised still available.

12v. 1a. £1.10, 6.3v. 1.5a. £1.05, 6.3v. 2a. £1.10, 6.3v. 3a. £1.70, 6.3v. 6a. £2.60, 12v. 3a. or 24v. 1.5a. £2.60 0-9-18v. 1.2a. £2.25, 0-12-25-42v. 2a. £2.19

CHARGE TRANS 0-9-15v. 1.2a. £2.05; 2.2a. £2.25; 3a. £2.32; 6a. £2.84. 6a. £2.19; 8a. £2.45.

AUTO (STEP UP/STEP DOWN) TRANSFORMERS 0-110/120v 200-230-250v. 80w. £2.90; 150w. £5.20; 250w £6.37; 500w £9.84.

DISCO LIGHTING SYSTEM £58.95

Incl. 2 Spotbanks and bulbs

JINGLE MACHINES from £37.95

ECHO CHAMBERS from £53.95

COLUMN SPEAKERS from £29.95

GROUP/DISCO SPKRS in CABINETS from £11.95

FREE FANE HIGH POWER 'CROSS-OVER' WITH ANY OF ABOVE
 Impedance or total impedance of 12", 15" or 18" Drive units must not exceed impedance of single horn or pair in series. Pair J44, Single J73 or J104 suitable for amplifier power up to 100 watts subject to above and with HFX2 'Cross-over'

New Branches at HANLEY WOLVERHAMPTON, YORK, LIVERPOOL

OPEN ALL DAY SATURDAYS (5 Day Week)

BRADFORD 10 North Parade (Closed Wed.). Tel. 25349

BOLTON 23 Deansgate. (Closed Wed.). Tel. 33512

BIRMINGHAM 30/31 Great Western Arcade. Tel. 021-236 1279 (Closed Wed.).

CARLISLE 8 English Street. (Closed Thurs.). Tel. 38744

COVENTRY 17 Shelton Sq., The Precinct. Tel. 25983

DERBY 97 St. Peter's Street. (Closed Wed.). Tel. 41361

DARLINGTON 18 Northgate (Cl. Wed.). Tel. 88043

DEWBURY 9/11 Kingsway (Closed Tues.). Tel. 469058

DONCASTER 3 Queensgate, Waterdale Centre. (Closed Thurs.). Tel. 63069

EDINBURGH 101 Lothian Rd. (Cl. Wed.). Tel. 229 9501

GLASGOW 325 Argyle St. (Cl'd Tues.). Tel. 248 4158

HANLEY, Stoke-on-Trent, 44 Piccadilly

HULL 7 Whitfriargate (Closed Thurs.). Tel. 29505

LEICESTER 32 High Street (Closed Thurs.). Tel. 55420

LEEDS 5-7 County (Mecca) Arcade, Briggate (Closed Wed.). Tel. 458252

LIVERPOOL 35 Dawson's Way, St. John's Shopping Centre Tel: 708 9380 (Cl. Wed.). Tel. 723 1629

LONDON 238 Edgware Road. W.2. (Closed Thurs.). Tel. 723 1629

MANCHESTER 80A Oldham Street (Closed Wed.). Tel. 238 2778

MIDDLESBROUGH 103 Linthorpe Rd. Tel. 210585 (Closed Wed.)

Barclaycard & Access PHONE ORDERS quoting CARD NO. accepted

MAIL ORDERS & EXPORT ENQUIRIES TO:— AUDIO HOUSE, HENCONNER LANE, LEEDS. 18. Tel: 0532 577631.

MAIL ORDERS MUST NOT BE SENT TO SHOPS

TERMS C.W.O. or O.O.D. No O.O.D. under £3. POSTAGE 50p PER ORDER OR AS QUOTED Phone or Write for FREE CATALOGUE.

NEWCASTLE UPON TYNE 59 Grainger St. (Closed Wed.). Tel. 21459

NOTTINGHAM 19/19A Market Street (Closed Thurs.). Tel. 48068

PRESTON 41 Friargate Walk, St. Georges Shoppg Prec. Tel. 51979

SHEFFIELD 13 Exchange Street (Castle Mkt. Bldg.) (Closed Thurs.). Tel. 20716

STOCKPORT 8 Little Underbank (Closed Thurs.). Tel. 480-0777

SUNDERLAND 5 Market Sq. (Closed Wed.). Tel. 70578

WOLVERHAMPTON, 6 Wulfrun Way (Cl'd Thurs.) Tel. 26612

YORK, 5 Church St. (Closed Wed.) Tel. 34355



MINI CONSOLES

Ideal for small desk control panels and consoles. Moulded in orange, blue, black and grey ABS. Incorporates slots for holding 1.5mm thick pcb's. Aluminium panel sits recessed into front of console and held by screws running into integral brass bushes.

MC 161 x 96 x 58mm £1.53 (1-9) £1.50 (10+)
 MC 215 x 130 x 75mm £2.20 (1-9) £2.17 (10+)
 Add 25p per £1 order value for Post & Packing

ECONOMY QUALITY LED's

50 for only £5 - 100 for only £9
 Mixed bags, all sizes, various colours

FULL SPECIFICATION LED's




Red (specify size) 75p per pack

Green, Yellow, Orange (specify size) £1.20 per pack
 (Each pack contains 5 LED's, Mounting Clips and Data)

TYPE A NEON INDICATORS

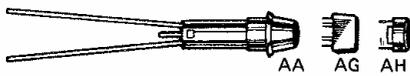Supplied with resistor for 240 Volts operation
 Held in 8mm hole by plastic bezel
 150mm wire leads




Red, Amber, Clear, Opal
 Green

AA AG AH

19p each
 28p each

12 VOLTS MINI HAND DRILL

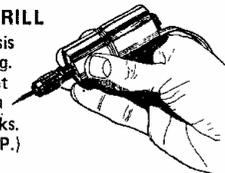Ideal for drilling pcb, chassis etc as well as model making. Supplied with 2 collets that accept tools and drills with 3/32" and .050" dia. shanks. £7.56 (Includes VAT & P.P.)



Stop wasting time soldering

The **NEW MW BREADBOARD** accepts Transistors, LED's, Diodes, Resistors, Capacitors and all DIL packages with 6 to 40 pins



Includes slot-in Component Support Bracket and has over 400 individual sockets, plus Vcc and Ground Bus Strips
 Price £9.72 (includes VAT & P.P.)

TYPE MP NEON INDICATOR

Supplied with resistor for 240 Volts operation
 150mm leads, held in 6.4mm hole by nut



Red, Amber, Clear, Opal 20p each

SEVEN SEGMENT DISPLAYS

Economy Quality
 Common Anode - 0.3" - Left Decimal
 Red, Yellow and Green @ 45p each

Full Specification
 Common Anode - 0.3" - Left Decimal
 Red @ 98p each
 Green and Yellow @ £1.35 each
 (Data supplied with Full Spec. displays only)




Quantity quotations on request

P.P. Note Unless included in price add 25p Post & Packing for orders totalling under £10. All prices include VAT and are valid in UK only for 2 months from journal issue date

Michael Williams Electronics
 47 Vicarage Av. Cheadle Hulme, Cheshire SK8 7JP

SC BOXES (square corners)

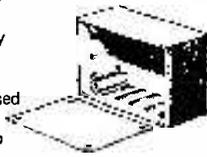
Easily drilled or punched, orange, blue, black and grey ABS. Incorporate slots for holding 1.5mm thick pcb's. Aluminium panel sits recessed into front of the box and held by screws running into integral brass bushes.



SC 85 x 56 x 35mm 80p (1-9) 77p (10+)
 SC 111 x 71 x 48mm £1.07 (1-9) £1.04 (10+)
 SC 161 x 96 x 59mm £1.49 (1-9) £1.46 (10+)
 Add 25p per £1 order value for Post & Packing

240 VOLTS MINI HAND DRILLS

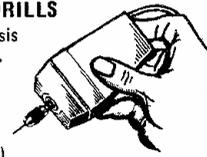Ideal for drilling pcb's, chassis etc as well as model making. Supplied with 3 collets that accept tools and drills with 1mm, 2mm and 1/8" dia shanks.



£9.72 (includes VAT & P.P.)
 Accessory tools... 5 Burrs, 1mm, 2mm, 1/8th Drills, 3/32" Collet Price £1.75 (Includes VAT & P.P.)

RC BOXES (round corners)

Easily drilled or punched, orange, blue, black and grey ABS. Incorporate slots for holding 1.5mm thick pcb's. Close fitting flanged lids held by screws running into integral brass bushes.



RC 100 x 50 x 25mm 51p (1-9) 49p (10+)
 RC 112 x 62 x 31mm 59p (1-9) 52p (10+)
 RC 120 x 65 x 40mm 68p (1-9) 62p (10+)
 RC 150 x 80 x 50mm 77p (1-9) 74p (10+)
 RC 190 x 110 x 60mm £1.33 (1-9) £1.30 (10+)

Polystyrene version

in grey only with no slots, no integral brass bushes
 RC(P) 112 x 61 x 31mm 35p (1-9) 32p (10+)
 Add 25p per £1 order value for Post & Packing

NEW FROM FAIRCHILD



£19.95 TIMEBAND TC441 LCD
 5 + 4 functions. Constant display, BATTERY HATCH, VOUCHER FOR FREE REPLACEMENT BATTERY. Chrome case, approx 3/4 x 1 inch.
 Also available with battery hatch and free voucher:-
 5 + 4 functions, round watch on strap:-
 TC411 chrome £24.95, TC410 Gold £27.95
 Oval face on integral bracket:-
 TC413 Chrome £29.95, TC412 Gold £32.95

TIMEBAND C500 DIGITAL ALARM CLOCK (Illustrated) **£14.35**
 Can be set to the exact second. Will display last minute digit and seconds. Solid state silence. Nine minute snooze and other sophisticated features. Black or White. H 3 3/4 x W 3 1/4 x D 3 3/8 inches. C611D. More sophisticated. Square £15.90 C590 (Elevating reading lamp) £23.50



£11.95 NEW SUPERBLY STYLED SIX + THREE FUNCTION LED
 Metal case, stainless steel back and s/s adjustable bracelet. At the touch of a button:- Hours, minutes and seconds. Push twice for day, date and month. Automatic 28, 30, 31 day calendar adjustment. This watch has the styling and finish of a watch costing twice or three times more. We are so impressed that we will return your money in full, if not delighted, if returned unmarked within 7 days.

Casio CQ-1. Clock, alarm, stopwatch, calculator £29.95. With AC adaptor £32.95. Ibcito quartz analogue (stepping motor) £34.50. Send 10p for our ILLUSTRATED CATALOGUE of over 50 watches, TV games etc. Prices include VAT, P & P. Credit cards, COD welcome or send cheque, P.O. to:-


TEMPUS Dept (PW), 19/21 Fitzroy Street, Cambridge CB1 1EH, Telephone 0223 312866

DORAM kits

DORAM KITS CONTAIN EVERYTHING DOWN TO THE LAST NUT!

TV Crosshatch & Pattern Generator

£19.77
 + S

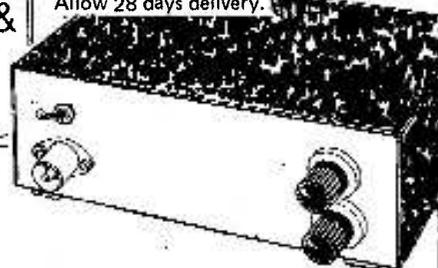

NOW AVAILABLE IN MADE-UP FORM
 PRICE £29.95 + S VAT (Built, Tested & Guaranteed - order code 997-162)
 Allow 28 days delivery.

Completely self-contained unit requiring only connection to mains and TV UHF aerial socket. Incorporates its own pulse generator giving fully interlaced scan and has unique frequency adjustment control, calibrated using visual display on TV screen to ensure correct field frequency. Choice of outputs: blank raster, dots, crosshatch and greyscale plus set frequency position. Facilitates setting of static and dynamic convergence, purity, black level, linearity, focus.

Subject to availability
 order code: 997-033

O'seas orders—add 15% for P+P. All items offered for sale subject to the Terms of Business set out in Doram Edition 3 catalogue, price 60p. The Doram Kit brochure is also available, price 25p. Combined price only 70p which also entitles you to 2x25p vouchers, each one usable on any order placed to the value of £5.00 or more (ex. VAT).
DORAM ELECTRONICS LTD. P.O. BOX TR8 WELLINGTON ROAD INDUSTRIAL ESTATE LEEDS LS12 2UF
 An Electrocomponents Group Company

DIY SPEAKER KITS

15-WATT KIT IN CHASSIS FORM

When you are looking for a good speaker, why not build your own from this kit. It's the unit which we supply with the enclosures illustrated below Size 13" x 8" (approx.) woofer (EMI), tweeter, and matching crossover components. Power handling capacity 15 watts rms. 30 watts peak.

£17.00 PER STEREO PAIR
+ P & P £3.40



EASY-TO-BUILD WITH ENCLOSURE

Specially designed by RT-VC for cost-conscious hi-fi enthusiasts, these kits incorporate two teak-simulate enclosures, two EMI 13" x 8" (approx.) woofers, two tweeters and a pair of matching crossovers. Easily constructed, using a few basic tools. Supplied complete with an easy-to-follow circuit diagram, and crossover components. Input 15 watts rms. 30 watts peak, each unit. Cabinet size 20" x 11" x 9 1/2" (approx.).

£25.50

PER STEREO PAIR
+ P & P £5.50

COMPACT FOR TOP VALUE

How about this for incredible bookshelf value from RT-VC! A pair of high efficiency units for only £7.50 - just what you need for low-power amplifiers. These infinite baffle enclosures come to you ready mitred and professionally finished. Each cabinet measures 12" x 8" x 5" (approx.) deep, and is in wood simulate. Complete with two 8" (approx.) speakers for max. power handling of 7 watts.

per stereo pair
£7.50
+ P & P
£1.70

SPEAKERS Two models - Duo IIb, teak veneer, 12 watts rms, 24 watts peak, 18 1/2" x 13 1/2" x 7 1/2" (approx.).

★ £34 PER PAIR
+ P & P £6.50

Duo III, 20 watts rms, 40 watts peak, 27" x 13" x 11 1/2" (approx.).

★ £52 PER PAIR
+ P & P £7.50

EASY TO BUILD RECORD PLAYER KIT

Ideally suited for the constructor who requires a complete stereo unit at a budget price, comprising ready assembled stereo amp, module, Garrard auto/manual deck with cueing device, pre-cut and finished cabinet work. Output 4 watts per channel, phones socket and record/replay socket

£26.95

+ P & P £4.05

CAR RADIO KIT

Complete with speaker, baffle and fixing strip. The Tourist IV for the experienced constructor only. The Tourist IV has five push buttons, four medium band and one for long wave band. The tuning scale is illuminated and attractive small aluminium control knobs are used for manual tuning and volume control. The modern style fascia has been designed to blend with most car interiors and the finished radio will slot into a standard car radio aperture. MOTOR TOP 10 AWARD

£12.50

+ P & P £1.50

PERSONAL SHOPPERS ONLY

Viscount IV 20 x 20 Amplifier as illustrated plus 1 pair of speakers finished in teak with melamine panels 8" drive unit and 3 1/2" approx tweeter. 22" x 13" x 10 1/2" size approx.

£45.00

SPECIAL OFFER

illustrated 20 x 20 WATT STEREO AMPLIFIER

Superb Viscount IV unit in teak-finished cabinet. Silver fascia with aluminium rotary controls and pushbuttons, red mains indicator and stereo jack socket. Function switch for mic, magnetic and crystal pick-ups, tape, tuner, and auxiliary Rear panel features two mains outlets. DIN speaker and input sockets, plus fuse. 20 x 20 watts rms. 40 x 40 watts peak.

★

£29.90

+ P & P £2.10

FREE "Limited Period" A Free 4 Channel Stereo Adaptor to all purchasers of the Viscount Amplifier. Available separately. + P & P £1.00

SPECIAL OFFERS

For example-

Duo speaker system II or III, Viscount Amplifier, MP60 type turntable complete

DEDUCT 10% DEDUCT 15%

★ on complete stereo systems using starred Products

PERSONAL SHOPPERS ONLY

DECCA DC1000 Stereo cassette, ready built tape deck, replay / record P.C.B. with pair record / replay heads

£3.95

AM. FM. TUNER P.C.B. with Mullard L.P. 1186, 1185, 1181 modules

£9.50

CROWN 5 push button car radio, LW, MW, 12v Pos: neg. earth 5 watts output, tone control complete with speaker and fixing kit, in dash type

£15.95

STEREO CASSETTE TAPE PLAYER Negative earth only, 3 watts per channel output

£16.50

AM. FM. STEREO MULTIPLEX CAR RADIO/cassette player in dash fixing Negative earth 5 watts output

£36.00


SONIX 'TROOPER' Boys Military style mains, battery radio

only £6.95

VISCOUNT COMBI

£65.00

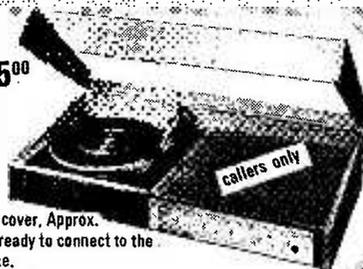For personal shoppers only, this unit comprises: The 20 x 20 Viscount amplifier BSR MP60 Type turntable housed in an attractive teak finished console with smoked acrylic cover. Approx. 30 1/2" x 14 1/2" x 7 1/2" complete ready to connect to the speaker system of your choice.



BSR TURNTABLES

BSR MP60 TYPE Single play record player (Chassis form) £15.95 less cartridge. P & P £2.00

Cartridges to suit above
ACOS MAGNETIC STEREO £4.95
CERAMIC STEREO £1.95

BSR automatic record player deck (Chassis form) with cueing device and stereo ceramic head. P & P £2.00

£9.95

TURNTABLE illus. diamond stylus, and deluxe plinth and cover. Ready wired

£29

+ P & P £4.50

30 x 30 WATT AMPLIFIER KIT

Specially designed by RT-VC for the experienced constructor, this kit comes complete in every detail. Same facilities as Viscount IV amplifier. Chassis is ready punched, drilled and formed Cabinet is finished in teak veneer. Silver fascia and easy-to-handle aluminium knobs.

Output 30 x 30 watts rms, 60 x 60 peak. P & P £2.10

£29.00

DECCA 20 WATTS STEREO SPEAKER

This matching loudspeaker system is hand made, kit comprises of two 8" diameter approx. base drive unit, with heavy die cast chassis laminated cones with rolled P.V.C. surrounds, two 3 1/2" diameter approx. domed tweeters comp with crossover networks

£20.00

+ £4.00 P & P stereo pair

PYE STEREO GRAM CHASSIS

(Complete with circuit diagrams) Complete ready to install - Wave bands LM, VHF STEREO, VHF MONO. Controls for tuning volume, balance, bass and treble. Power output 7 watts R.M.S per channel 14 watts peak 8 ohms, 2" x 8" approx chassis speakers and BSR auto record player deck. PERSONAL SHOPPERS ONLY

£35.00

Order giving your credit card number ONLY

ALL PRICES INC. VAT AT 12 1/2%
GOODS NOT DESPATCHED OUTSIDE UK
All items subject to availability. Price correct at 1st May and subject to change without notice
We are unable to show all our products, to send stamped addressed envelope for our fully descriptive catalogue and any further information.

ATVC

323 EDGWARE ROAD, LONDON W2
Personal Shoppers EDGWARE ROAD 9.30-5.00pm, Half day Thurs
21c HIGH STREET, ACTON, LONDON W3 6NG
ACTON: Mail Order only No callers

PORTABLE MONO DISCO CONSOLE



with built-in pre-amplifiers
Here's the big-value portable disco console from RT-VC! It features a pair of BSR MP 60 type auto-return, single play professional series record decks. Plus all the controls and features you need to give fabulous disco performances. Simply connects into your existing slave or external amplifier.

p & p £6.50

£64.00

35-WATT MONO DISCO AMP

£27.50

+ P & P £2.50

Size approx

13 3/8" x 5 1/2" x 6 1/2"

Here's the mono unit you need to start off with. Gives you a good solid 35 watts rms, 70 watts peak output. Big features include two disc inputs, both for ceramic cartridges, tape input and microphone input. Level mixing controls fitted with integral push-pull switches. Independent bass and treble controls and master volume.

100 WATT MONO DISCO AMP

£65.00

+ P & P £4.00

Size approx.

14" x 4" x 10 1/2"

Sloping fascia, you can use the controls without fuss or bother. Brushed aluminium fascia and rotary controls. Five smooth acting, vertically mounted slide controls - master volume, tape level, mic level, deck level, PLUS INTER-DECK FADER for perfect graduated change from record deck No. 1 to No. 2, or vice versa. Pre-fade level control (PFL) lets YOU hear next disc before fading it in. VU meter monitors output level.

£65.00

Output 100 watts RMS 200 watts peak. P & P £4.00

PRACTICE GUITAR AMPLIFIER WITH BUILT-IN SPEAKER

This budget practice amplifier, has been specially designed for the amateur, who requires a quality self-contained unit with all facilities. 2 inputs - 1 for mic or guitar, the 2nd for record player or cassette deck. It also can be used for cine-sound amplification. 2 volume controls, 1 for each input, also bass and treble controls. Power output with internal speaker, 12 watts RMS, with remote speaker (not supplied) 20 watts RMS. Size approx. 17" x 9" x 11".

£32.50

+ P & P £3.00

HOME 8 TRACK CARTRIDGE PLAYER

Automatically switches programmes monitored by indicators, with manual override track selection. This unit will match with the Unisound modules and is compatible with the Viscount IV amplifier with Sim teak cabinet, approx. 9" x 8" x 3 1/2" P & P £1.50

£14.60

4 x 4 STEREO AMP KIT

For the experienced constructor who wants to design his own stereo. Kit includes all necessary components including constructors manual. Plus Pair of easy to build 4 watt speakers in kit form, with teak simulate finish cabinets 12" x 9" x 5" approx.

£14.60

NEW FANTASTIC SAVING. sinclair

I.C. 20, 20 WATTS STEREO AMPLIFIER KIT WITH PZ 20 POWER UNIT

A build-it-yourself stereo power amplifier with latest integrated circuitry, 10W RMS per channel output, full short-circuit and overheat protection. Complete with PZ20 Power Supply

OUR PRICE

£5.95 + P & P £1.

LIST £14.50

CRESCENT RADIO LTD.

164-166 HIGH ROAD, LONDON N22 6EJ 888-3206
(also) 13 SOUTH MALL, EDMONTON, N.9 803-1685

MAIL ORDER DEPT.

1 ST. MICHAELS TERRACE, WOOD GREEN,
LONDON N22 4SJ Phone 888 4474

3-WAY MULTIPLE AC ADAPTOR

This compact adaptor allows a large range of battery powered equipment to be operated from A.C. mains (220-240V A.C.). Switchable for 6, 7.5 or 9 volts, current rating is 300 mA max. A polarity reversing coupler is incorporated and the lead is terminated by a four way plug offering connections by 2.1 and 2.5mm sockets, 2.5 and 3.5mm plugs. The sealed moulded unit is fitted with a 3 pin 13A mains plug and measures 70 x 50 x 42mm approx. Only £3.50 + 8%.

GOODMANS 8in. LOUDSPEAKER

Goodmans "Audiom 8PA" Bass L/speaker, impedance 8 ohm, power handling 15W nominal. Our price £4.53 + 12½% VAT.

"C100" 100 WATT AMPLIFIER

All built and tested, mounted on a plain aluminium chassis which measures 18" x 9½" x 4" and which you can mount into a cabinet of your choice. Four controlled inputs, master volume, treble, middle and bass controls. 8½ protected output. 100 watts clean into 8ohm L/S. Ideal for disco, music groups, P.A. and clubs. A bargain at £48 + £1 carr. + 8% VAT.

P.C. ETCHING KIT

This kit contains all that the constructor will need to etch the circuits of his own design. Contents—Plastic etching dish. Sample copper clad board. Laminated Cutter. 1 lb Ferric Chloride. Large Plastic Spoon. Etch Resist Pen. Full Etching Instructions.

Complete and Big Kit Value at £4.25 + 8% VAT.

POWER SUPPLY UNITS +8%



PP1 switched 3, 4½, 5, 7½, 9 and 12 volts at 500 mA, with on/off switch and pilot light. Size: 130mm x 55mm x 75mm. ONLY £5.50



M3 CONDENSER MICROPHONE

Cardioid and omni-directional 600 ohm and 50K ohm impedance. 20-18,000 Hz. On/off switch and wind shield. Complete with stand adaptor. Packed in presentation box. Price £14.50 + 12½% VAT.

HEAVY DUTY 12 VOLT POWER SUPPLY

1.5 amp at 12 volt power supply approx. size 6" x 4" x 3½". Ideal for using your car entertainment in the home from domestic mains. Suitable for 8 track cartridge or 4 track cassette machines. Price £7.50 + VAT 8%.

2 WAY AND 3 WAY CROSSOVERS +12½%

NT206 2-way network for 8 ohm speakers up to 30 watts. Price £2.00.

NT206H 2-way, as above, 100 watts. Price £2.25.

NT306 3-way network for 8 ohm speakers up to 30 watts. Price £3.25.

NT306H 3-way, as above, 100 watts. Price £4.00.

TIE-CLIP CONDENSER MICROPHONE

Omni-Directional 600 ohm 40-15,000Hz. Extra long lead. Ideal for stage work, conferences, etc. Price £9.50 + 12½% VAT.

LOW NOISE LOW PRICE CASSETTES +8%

Good quality tape in well made screw type cassettes. Presented in single plastic cases. C80=40p C90=50p C120=60p + 10% Discount on ten or more cassettes of one type

LOUDSPEAKERS +12½%

2½" 8 ohm 90p
2½" 40 ohm 90p
2½" 80 ohm 90p
5" 8 ohm ceramic £1.50

ABS PLASTIC BOXES

Handy boxes for construction projects. Moulded extrusion rails for P.C. or chassis panels. Fitted with 1mm front panels.
1005—105mm x 73mm x 45mm 62p
1006—150mm x 74mm x 47mm 80p
1007—185mm x 124mm x 60mm £1.80
1022—107mm x 85mm x 45mm 82p (sloping front) Plus 8% VAT

U.K. CARRIAGE 50p UNLESS OTHERWISE STATED
ACCESS AND BARCLAYCARD ACCEPTED

VAT—All prices are excluding VAT. Please add to each item the VAT rate indicated.

MULTI-METER MM12 50,000 o.p.v.



If you need a good instrument for your work/hobby and you're not prepared to settle for a small scale and poor ranges, then read the specifications for the MM12, and send for one!

AC volts: 0 to 1.5, to 0/500 in 10 ranges. DC volts: 0 to 0.5, to 0/500 in 12 ranges. DC current: 0 to 25 µA, to 0/10 amps 10 ranges. Resistance: 0 to 100 ohms, to 0/16 meg ohms in 4 ranges. Decibels: -20 to +62 db in 10 ranges. Size: 6½ x 4½ x 2½ inch. Price £19.50 + 8% VAT.

BARGAIN PROJECT BOX

A plastic box with moulded extrusion rails for PC or Chassis panels with metal front plate fitted with four screws (all supplied). SIZE (internal) 81mm x 51mm x 28mm. OUR PRICE 50p. + 8%

PIEZO ELECTRIC HORN UNITS

New high quality high power tweeter, no form of crossover network is required as low frequency voltages simply have no effect on the tweeter.

Specification:—
Frequency response: 3-8kHz to 28kHz ± 3db. (input 4V rms pink noise—output 105db). Max. continuous rms input voltage: 25V
Minimum series resistor: 10ohm at 1w
Weight: 63 gm. (2.25oz.)
Panel Cut Out: 76mm dia. (3in).
Size: 85mm x 85mm x 75mm
Rating: Depending on connections up to 100W approx.
Price: £9.00 + 8% VAT.



3 KILOWATTS PSYCHEDELIC LIGHT CONTROL UNIT

Three Channel Bass, Middle, Treble, Each channel has its own sensitivity control. Just connect the input of this unit to the loudspeaker terminals of an amplifier and connect three 250V up to 100W lamps to the output terminals of the unit, and you produce a fascinating sound-light display. (All guaranteed.) £18.50 plus 75p P. & P. + 8%



BARGAIN TRANSFORMERS 12-0-12 volt 500m/a

240 volt primary transformer bargain. approx size 60mm x 40mm x 50mm fixing centres 75mm our price £1.20 + 8%



EFFECTS PROJECTOR "150"

No Disc should be without our new effects projector, we believe that this is the most versatile machine for projecting coloured images to supplement your music. Spec:—Volts=220/240 AC 50Hz. Lamp=A1/167 150 watts. Standard Lens=60 mm.

A sturdy metal construction and takes a range of lenses and accessories. Comes complete with 6" liquid wheel and ready to use. A bargain at £27 + VAT 8%.

If your cat is into the Average White Band



Isn't it about time you listened to them properly yourself?

The best way to achieve that is with Fidelity Fastenings—the newest, smartest way to place your speakers where they belong—on the wall. Almost undetectable when fitted they are easily adjustable and allow your speaker system to be placed in the best possible acoustical position, where they stay due to the rubber friction mounting. Fidelity Fastenings take a weight of up to 50 lb and

your speakers are easily lifted off for dusting or redecorating.

Available from all good Audio and Hi-Fi shops and stores at £5.49. Look for the red and black box. If you have any difficulty in obtaining your Fidelity Fastenings, write for details of your nearest stockists to:

Fidelity Fastenings

The Ridgeway, Iver, Buckinghamshire
Tel: (0753) 654222

FANE SPECIALIST RANGE SPEAKERS

Each designed to produce the individual sound requirement for its purpose. Robust Cast Aluminium Chassis 12" models 80w RMS Rec. Price



12" DISCO/80	Fitted large Tweeter Cone	£27.95
12" GUITAR/80L	For Lead Guitar	£25.75
12" GUITAR/80B	Prs. rec. for Bass Guitar.	£26.95
12" PA/80	Dual Cone. For general purpose P.A.	£25.95
15" BASS/85 85w	For Bass	£39.95
15" BASS/100	Guitar	£42.00

'POP' RANGE SPEAKERS


12" POP 33T	33w	£14.95
12" POP 50/2	50w	£16.99
12" POP 55/2	65w	£22.95
15" POP 60	60w	£25.95
15" POP 70	75w	£29.95
18" POP 100	100w	£46.95

HIGH FREQUENCY HORNS

J44 Range: 2.5KHz-15KHz
Power: 50w with HPX2
30w with HPX1
Imp: 8 ohms
Size approx 3½" x 3½" x 3" £7.95



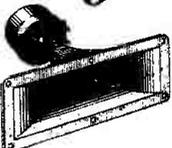J73 Range: 2.5KHz-20KHz
Power: 50w with HPX1
Imp: 8 ohms
Size approx: 7½" x 3" x 8½" Rec. Price £11.75



920/2 Range: 1KHz-18KHz
Power: 100w with HPX1
Imp: 8 ohms
Size approx 14" x 9" x 15" Rec Price £59.95

J104 Range: 2KHz-15KHz
Power: 50w with HPX1
Power: 70w with HPX2
Imp: 8 ohms
Size approx 10½" x 3½" x 7½" £16.95


HIGH POWER 'CROSS-OVERS' HPX1 (3.5KHz) HPX2 (5KHz) £2.99

Impedance or total impedance of Bass Drivers not to exceed 8Ω
Otherwise use series Horns or attenuation.


FANE SPEAKERS ARE SUPPLIED TO MOST LEADING U.K. MANUFACTURERS OF GROUP & DISCO EQUIPMENT

Rec. Prices INCLUDE VAT. 2 years guarantee on above speaker models
Distributors (Wholesale & Retail) Rec. prices shown correct at 12.5.77.
LINEAR PRODUCTS LTD, ELECTRON WORKS, ARMLEY, LEEDS.
Manufacturers & Export enquiries to:—
FANE ACOUSTICS LTD, 286 BRADFORD ROAD, BATLEY, YORKS.


DeC~IT and BLOB~IT

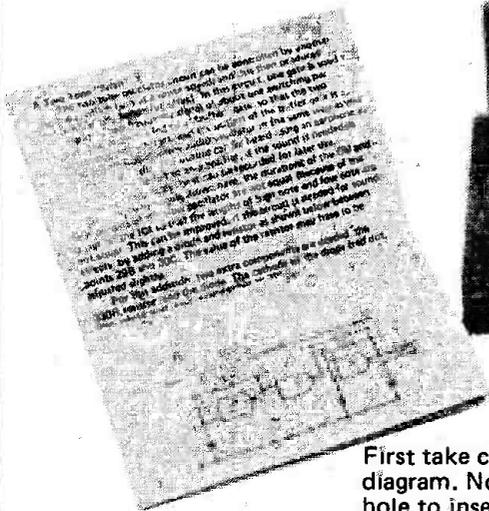

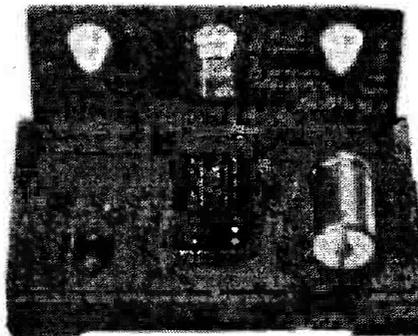
First take circuit diagram. Note, each hole to insert, component is identified by a letter number system.



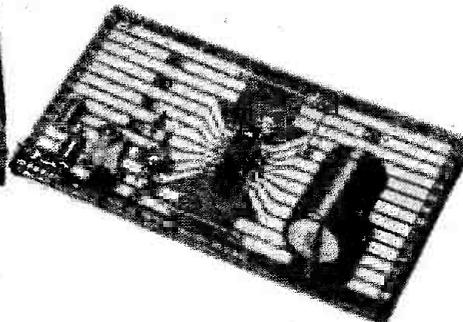Second try, test and prove the circuit on your T-DeC, no soldering.



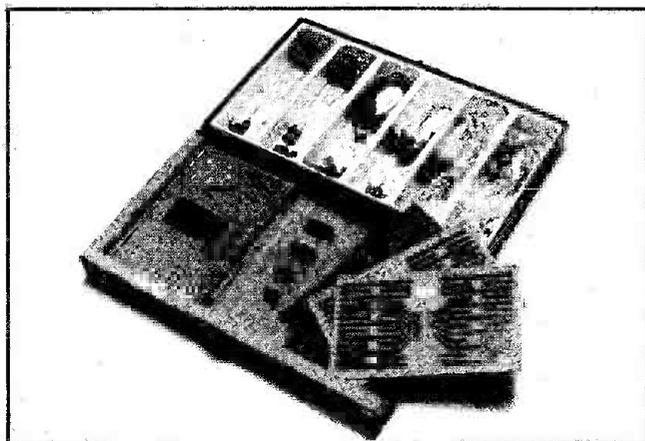
Finally when everything is working Blob onto your IC Blob-Board.



This De-K-IT contains 1 T-DeC + control panel + 1 16 DIL Carrier + 4 Blob-Boards + Components + Circuit Diagrams and step by step instructions to build Burglar Alarm – Sound Fuzz Circuit – SR Latch – Two Tone Siren.

Complete Kit with all components
£13.00 + £1.66 post and V.A.T.

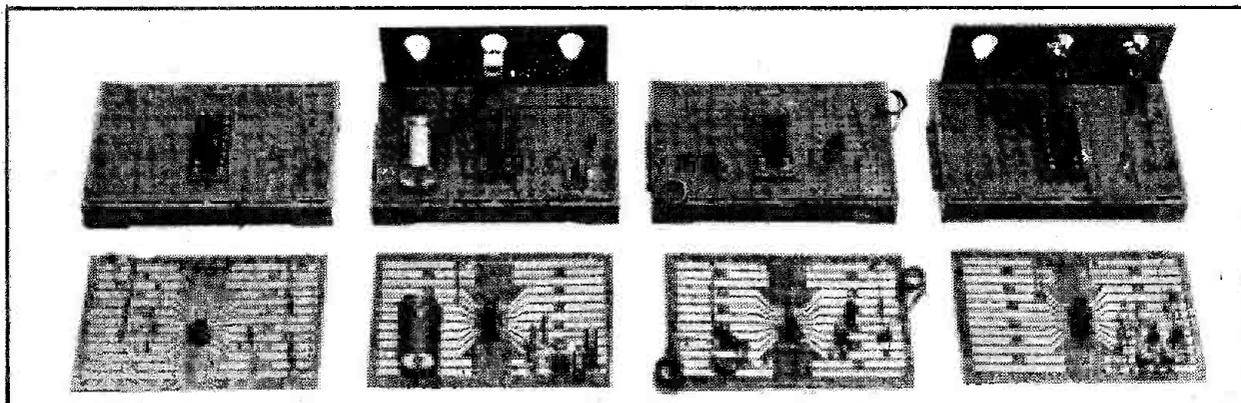Try and test each circuit on T-DeC. Prove circuit working. No soldering. Then when everything is working perfectly transfer to Blob-Board.



1
S-R Latch

2
Sound Fuzz Circuit

3
Two Tone Siren

4
Burglar Alarm




PB Electronics (Scotland) Ltd.
57, High Street, Saffron Walden, Essex. CB10 1AA

Incredible Value in Precision Test Meters

AVAILABLE FROM SELECTED STOCKISTS. WRITE OR PHONE FOR LIST

MICROTEST 80—I.C.E. 20,000 Ohms/Volt 40 RANGES

20,000 Ohms/Volt, (d.c.) 4,000 Ohms/Volt (a.c.) 2% accuracy. V d.c. 100mV to 1kV (6 Ranges). I d.c. 50 μ A to 5A (6 Ranges). V a.c. 1.5V to 1kV (5 Ranges) I a.c. 250 μ A to 2.5A (5 Ranges). Resistance, Low Ohms, Ohms \times 1, Ohms \times 10, Ohms \times 100. Output Level Measurements 1.5V to 1000V (5 Ranges) + 6dB to + 62dB (5 Ranges). Capacitance 25 μ F to 25,000 μ F (4 Ranges). 1000 times overload protection (on Resistance ranges). Meter movement diode protection. Size (without case) 90 \times 70 \times 18mm. Automatic zero, non-parallax mirror scale. Unbreakable carrying case and probes supplied. Full After Sales Service available. **Price £16.15 inc. VAT**

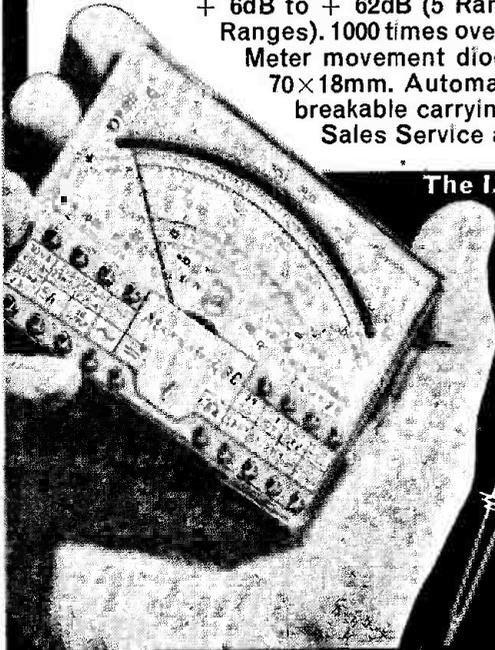


The I.C.E. Measurement System includes a comprehensive range of accessories: shunts; transformers, specialised probes, transistor-tester etc. I.C.E. High-Voltage d.c. Probe, Model 18. Input Impedance: 500M Ohm, nominal (Other values available to order). The Model 18 d.c. Probe consists of a highly insulated moulded plastic body, fitted with a hand guard-ring, containing a stable, precision 500M Ohm resistor, which may be used to extend the d.c. voltage measuring capability of analogue multi-meters or electronic voltmeters, to a maximum value of 25kV. The probe is fitted with a prod-tip for connection to the voltage source to be measured and a connecting lead terminating in a 2mm plug for insertion into the measuring instrument's d.c. voltage input socket. (4mm plug available to order). **£6.42 inc. VAT**

SUPER TESTER 680R—I.C.E.

20,000 Ohms/Volt 80 RANGES

20,000 Ohms/Volt 1% d.c. 4,000 Ohms/Volt a.c. 2% V d.c. 100mV to 2kV (13 Ranges). V a.c. 2V to 2kV (11 Ranges). I d.c. 50 μ A to 10A (12 Ranges). I a.c. 250 μ A to 5A (10 Ranges). Resistance Ohms \times 1, \times 100, \times 1000, \times 10,000 and Low Ohms. Reactance Detector 0-10M Ohms. Freq. Measurement 0-5000 Hz (2 Ranges). Output Level 10-2000V (9 Ranges). Decibels -24 to +70dB (10 Ranges). Capacitance 0-500,000 pF (2 Ranges using mains supply) 0-20,000 μ F (4 Ranges using internal 3 Volt battery). 1000 times overload protection on Resistance ranges and meter movement diode protection. 10 Measurement Functions and 80 Ranges. Size 128 \times 95 \times 32mm. Non-parallax mirror scale. Unbreakable carrying case supplied which contains probes, mains lead, crocodile clips and shorting link. **Price £27.27 inc. VAT**

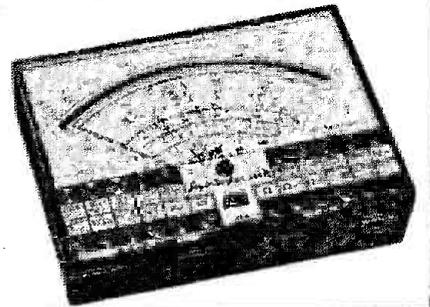

Sole Importers and Distributors

Electronic Brokers Ltd

49-53 Pancras Rd., London NW1 2QB. Tel: 01-837 7781

TAPE HEADS

FIT A BRAND NEW HEAD AND TRANSFORM THE QUALITY OF YOUR TAPE PLAYER AN EXTENSIVE RANGE ALWAYS IN STOCK ASK FOR OUR SHORT FORM CATALOGUE



SPECIAL I

STANDARD HEADS TO FIT MOST TAPE PLAYERS AT BULK DISCOUNT PRICES. ENCLOSE 15p P & P WITH ORDER

MONO CASSETTE 90p
STEREO CASSETTE £2.00
STEREO CARTRIDGES £1.00
M/S CASSETTE ERASE 60p

MONOLITH
THE MONOLITH ELECTRONICS CO. LTD.

5/7 Church Street, Crewkerne, Somerset, England.

Tel. Crewkerne 74321

PRACTICAL WIRELESS T.V. SOUND TUNER

(Nov. 75 article by A. C. Ainslie)

IF Sub-Assembly (G8) £6.80. P & P 75p.
Mullard ELC1043 Varicap UHF Tuner £4.50. P & P 35p.
3-way Station Control Unit £1.20. P & P 25p.
6-way Station Control Unit (Special Offer) £1.00.
Power Supply Printed Circuit Board £1.00, P & P 30p.
Res, Caps, Semiconds, etc. for above £5.80
Mains Transformer for above £2.50, P & P 30p.

Add 12½% VAT to price of goods. P & P all items 85p.


Copy of original article supplied on request

Callers welcome at shop premises.

MANOR SUPPLIES

172 WEST END LANE, LONDON NW6
(Near W. Hampstead Tube Stn.) Tel. 01-794 8751

THE OPEN DOOR TO QUALITY

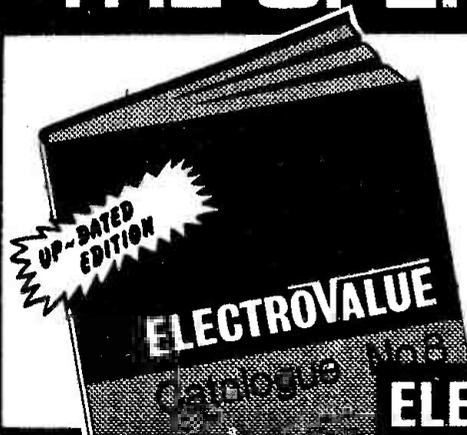

Latest revised issue (4th Edition, Cat. 8). Includes new ranges of meters and switches as well as price adjustments together with items from advanced opto-electronic components to humble (but essential) washers. Many things listed are very difficult to obtain elsewhere. The Company's own computer expedites delivery and maintains customer satisfaction. Attractive discounts are allowed on many purchases. ACCESS AND BARCLAYCARD ORDERS ACCEPTED.

144 pages

40p

POST PAID inc. 40p Refund Voucher

+ FREE POSTAGE on all C.W.O. mail orders in U.K. over £2.00 list value (excluding V.A.T.) If under, add 15p handling charge.

All communications to Dept. PW 6
88 ST. JUDES ROAD, ENGLEFIELD GREEN, EGHAM, SURREY TW20 0EB. Tel Egham 3803. Telex 884475 Shop 9-5.30, 9-1 pm Sat.
NORTHERN BRANCH: 680 Burnage Lane, Burnage, Manchester M19 1NA. Tel: (061) 492 4945. Shop 9-5.30pm, 1 pm Sat.

ELECTROVALUE LTD

SAXON ENTERTAINMENTS LTD

A FULL RANGE OF MODULES & READY-TO-USE EQUIPMENT TO PROFESSIONAL STANDARDS FOR THE PROFESSIONAL
SYSTEM 7000 COMPLETE & READY-FOR-USE EQUIPMENT

POWER AMPLIFIER MODULES 30—240 WATTS



- Fully tested & guaranteed.
- Full RMS Sine Wave output.
- Distortion typically 0-2%
- 10 Transistors, 4 Diodes.
- Response 30HZ-30KHZ
- Fully short & open circuit proof
- Sensitivity suits most mixers.
- Built-in surge suppression & compensation
- Twin D.C. & output fuses.
- Top-grade components throughout.

30 Watts rms	60 Watts rms		120 Watts rms		240W rms
SA308 30W rms/ 8 ohms £9.50	SA604 60W rms/ 4 ohms £12.50	SA608 60W rms/ 8 ohms £13.50	SA1204 120W rms/ 4 ohms £14.50	SA1208 120W rms/ 8 ohms £21.00	SA2404 240W rms/ 4 ohms £25.50

POWER SUPPLIES FOR THE ABOVE MODULES—READY WIRED & FUSED ON GLASS FIBRE PCB

PM301 For 1/2 SA308 £9.90	PM601/4 For 1/2 SA604 £12.50	PM601/8 For 1/2 SA608 £12.50	PM1201/4 For 1 SA1204 £12.50	PM1201/8 For 1 SA1208 £12.50	PM1202/4 For 2 SA1204 £19.50	PM1202/8 For 2 SA1208 £19.50	PM2404/1 For 1 SA2404 £19.50
------------------------------------	---------------------------------------	---------------------------------------	---------------------------------------	---------------------------------------	---------------------------------------	---------------------------------------	---------------------------------------

SYSTEM 7000 COMPLETE DISCO MIXERS (With Autofade)

Mono or Stereo



- Ready to plug in & use
- Automatic Mic override
- Two tone panel
- Twin deck & mic & tape inputs
- Left/Right deck fader
- 20Mhz-20kHz Noise -77 dB

The choice of the professional D.J.
 Controls: Mic volume, Bass, Treble, A/Fade Depth, Tape, L/Deck, R/Deck volumes, Bass, Treble, Master, Headphone volume, Selector & On/Off.

Mono 18v **£37.50** Mains **£43.50** Stereo 18v **£53.50** Mains **59.50**

IN MODULAR FORM—All you require is front panel (see below) knobs & sockets etc. All electronics are assembled & tested.

- Specification as for complete mixer
- All Potentiometers supplied & fitted
- Low cost do it yourself with step by step easy to follow instructions.

Mono **£19.50** Stereo **£29.50** Panel **£3.50** Supply unit **£8.50**

SYSTEM 7000 LIGHTING CONTROL UNIT MK II (Four channel)



Has your light unit got ?

- 4,000 W handling
 - Sequence facility
 - Smart 2 tone panel
 - Advanced IC circuitry
 - Top grade components
 - All your needs in one superbly designed unit
- Integral dimmers
 Automatic audio level
- OURS HAS!**

ONLY £42.50

IN MODULAR FORM—THE QUADRAFACT **£29.50** (Panel **£2.50**)

As with the mixers the Mk II L.C. unit may be purchased in module form with all controls, requiring only a panel, case & knobs etc. There are 13 simple connections

- 1-240w Audio
- 8A RCA triacs
- 0.5-20Hz Sequence
- Fully suppressed

CUSTOM MIXER MODULES (Complete or In printed circuit form only)

Make your own mixer, mono or stereo, up to 2 channels, with full monitoring facilities, and provision for echosend/return etc.

- Inputs for low and high 2 mic, ceramic & magnetic cartridge etc.
- Up to 20 input modules per single mixing module
- Feed most types of amplifier—accepts all inputs
- Professional low noise circuitry 20 Hz-30kHz
- Infinitely adaptable—Extremely economical



COMPLETE MODULES With facia panel, Knobs & sockets, Monitor buttons, Ready wired & tested

Mono input **£8.50** Mono mixing stage **£8.50**
 Stereo input **£12.00** Stereo mixing stage **£12.00**

- 0.5W headphone circuit
- Full range bass/treble controls
- Noise—80dB

PRINTED CIRCUIT MODULES With controls fitted, requires only sockets, facia & knobs

Mono input **£5.50** Mono mixing stage **£5.50**
 Stereo input **£9.00** Stereo mixing stage **£9.00**

Power supply for up to 20 channels—PPM18—**£8.50**.

SYSTEM 7000 SOUND—LITE (3-CHANNEL)

IN COMPLETE OR MODULAR FORM (Modular form illustrated)

- Complete unit similar to Mk II unit above
- Long established & proven design
- 3 Channels—100W per channel
- RCA 8A Triacs—Individual channel fuses
- 1-240 W input—master audio level plus Bass/Middle/Treble



COMPLETE UNIT—Fully cased with rear terminations—just plug in & go! **£24.75**

MODULAR FORM Facia & knobs etc. Needs only 11 simple connections **£16.50** (Panel **£2.50**)

CENTAUR—THE 100W RMS STEREO DISCO COMPLETE WITH SOUND-TO-LIGHT SEQUENCER & LIGHTS

ONLY £225 (+4.50 carr) or Low interest terms Deposit **£27.86** 12 months at **£21.18** or 24 months at **£12.01**

- 100W RMS stereo output
- Twin heavy duty loudspeaker
- Four channel sound lite—sequencer complete with display
- Separate mlc., music bass & treble controls
- Sturdy vynide cabinets with all leads
- Twin BSR decks with lift arm



NOW AVAILABLE
SUPER CENTAUR

200W Stereo output—other details as above **£275** (carr. 4.50) or Deposit **£31.86** 12 months at **£25.03** or 24 months at **£14.20**
 Cut-price condenser mic & headphones **£15.00** (only with complete discos)

SAXON MINI-DISCO 50W RMS **£139.00** (carr. **£2.50**) 100W RMS **£169.00**

- C/W heavy output loudspeaker
- 100W version has twin speakers
- Includes mic input & headphone monitor circuit
- Twin BSR decks with liftarm
- Tremendous bass—just plug in & go
- Wide range bass & treble controls



Cut-price condenser mic & headphones **£18.00** (only with complete discos)

SEND YOUR SPECIAL REQUIREMENTS FOR A CUSTOM DISCO QUOTATION

SYSTEM 7000 MINOTAUR 100—All Purpose Wide Range Amplifier



- 100W rms ± 1dB
 - Standard 8 ohm output
 - Twin mixed inputs accept a wide range of signals
 - 30HZ-30KHZ ± 2dB
 - 23dB bass/treble
- A four input, high power amplifier which will deliver up to 150 watts output. An absolute must where multiple mixing & power are required
- Four individually mixed inputs
 - Wide range bass/treble+master

An extremely compact and versatile amplifier with full protection and a clean, attractive appearance. Ideal for all groups, disco's & clubs



£49.50

- Vynide covered case
- Fully short proof
- Superb value for money

SAXON 150 HEAVY DUTY AMPLIFIER £59.00

STROBES & PROJECTORS (We stock the full Pluto range) Send for details

SUPERSTROBE **£19.75**

- 2-3 Joules
- 80W Tube for long life
- Compact 4" x 4" x 4"

PRO-STROBE **£32.50**

- 6-8 Joules
- External trigger
- Long Life tube timer circuit



150 WATT LIQUID WHEEL PROJECTOR

- Accepts all accessories
 - C/w with wheel & motor plate
 - Sturdy steel construction
- Remarkable value—Sold elsewhere at **£39.50**. Our price is only: **£33.00**

ACCESSORIES Condenser mics ECM77 600 ohm **£13.50**
 ECM 81 Dual Impedance **£14.95** Crown headphones **£8.75**
 Heavy duty boomstand **£14.50**

All prices subject to VAT @ 8% except SA308/PM301, mics. & headphones (12 1/2%)
 Add 50p post & packing on all orders except where already shown.
 Ordering: By Telephone—Access, Barclay Card or COD Ring (01) 684 6385/0098
 By post —Send cheque or crossed P.O.'s or 60p for COD
 or send in your Access/Barclay card NUMBER ONLY

327-333 Whitehorse Road, Croydon, Surrey CR0 2HS
 24 Hour Ansafone service (01) 684 6385

PIEZO HORNS!! UP TO 150 WATTS HANDLING. NO X-OVER REQUIRED **£7.50** ea.

Exporters to 17 countries—enquiries welcomed
 Ring Sue Abegg on (01) 684 6385 for U.K. trade enquiries

ESSENTIAL BOOKS for RADIO AMATEURS

VOLUME 2 completes the RADIO COMMUNICATION HANDBOOK (5th edition)

Volume 2 of this standard reference work has now been published. Its contents reflect the ever-expanding scope of amateur radio, with subjects such as fm repeaters and slow-scan television included for the first time in this edition; while a whole chapter is now given over to amateur satellites.

The major part of Volume 2, however, is devoted to the more fundamental aspects of radio communication. The 98-page chapter on hf antennas is a "book within a book", and such vital subjects as propagation, noise and interference are covered in detail in individual chapters.

Chapter titles are: Propagation; HF aeriels; VHF and uhf aeriels; Mobile and portable equipment; Noise; Power supplies; Interference; Measurements; Operating technique and station layout; Amateur satellite communication; Image communication; The RSGB and the radio amateur; and General data.

324 + xii pages

Price £8 post paid

VHF-UHF MANUAL (3rd edition)

by D. S. Evans, PhD, AIM, G3RPE,
and G. R. Jessop, CEng, MIERE, G6JP

Over 400 large-format (180 x 245mm) pages packed with ideas, information and constructional details of tried and tested equipment, each specialist topic contributed by an acknowledged expert in the field.

The most comprehensive and up-to-date review of vhf and uhf techniques available today.

Chapters on receivers, transmitters, space communications, filters, aeriels, microwaves and much more. Simple amateur television is covered and a data section provides valuable facts and figures to help the constructor. Many of the designs make use of integrated circuits, and the microwaves chapter gives details of equipment for use up to 24GHz.

404 + xii pages

Price £6.65 post paid

RSGB AMATEUR RADIO CALL BOOK 1977

Incorporates all new call signs and amendments notified between August 1975 and August 1976.

Also includes valuable operating data such as band plans, beacons, prefix list, ITU zone list, beam headings and QSL Bureau sub-managers, and lists of clubs and groups.

176 pages

Price £2.31 post paid

These are just a few of a complete range of technical publications, log books and maps for the radio amateur. Send a large stamped self-addressed envelope for the complete list.

The RSGB is the national society representing all UK radio amateurs. Membership is open to all interested in the hobby; write to the membership section and ask for full details.



Radio Society of Great Britain

35 DOUGHTY STREET, LONDON, WC1N 2AE

THE 'METAC' DIGITAL ALARM CLOCK



- Choice of Bright Orange 12 Hour Display, or
- Soft Green 24 Hour Display ● 24 Hour Alarm
- 10 Minute Repetition ● Alarm Set Indicator
- Accurate Silent Timekeeping ● British Designed and Built

SAME DAY DISPATCH orders received before 2 pm are posted same day

£13.43 + £1.07 VAT

Cash, Cheque or Postal Order or if you wish to use Barclaycard or Access, simply quote name, address and card number when ordering.

Metac-Electronics and Time Centre




DAVENTRY

67 High Street
Daventry, Northants
Tel. (032-72) 76545

UXBRIDGE

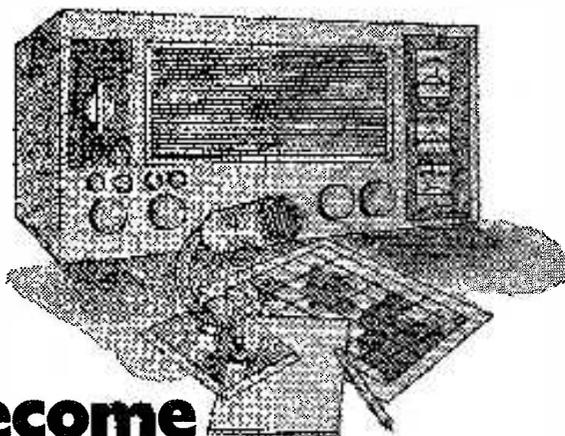3 The New Arcade,
High Street, Uxbridge,
Middx. Tel. (0895) 56961



Become a radio amateur.

Learn how to become a radio-amateur in contact with the whole world. We give skilled preparation for the G.P.O. licence.

WAA
WK67

Free!

Brochure, without obligation to:

BRITISH NATIONAL RADIO & ELECTRONICS SCHOOL,
P.O.Box 156, Jersey, Channel Islands.

NAME _____

ADDRESS _____ (Block caps please)

Stirling Sound

POWER AMPLIFIERS

at stated o/p powers ± 1 dB

SS.103 3 w. r.m.s. one I.C. protected against short circuit **£2.33**

SS.103-3 Stereo version of above using two I.C.s **£4.33**

SS.105 5 w. r.m.s. into 3 ohms, using 12V **£3.49**

SS.110 10 w. r.m.s. using 24V into 4 Ω **£4.05**

SS.120 20 w. r.m.s. into 4 Ω , using 34V **£4.61**

SS.140 40 w. r.m.s. into 4 Ω using 45V **£4.99**

SS.1100 100 w. r.m.s. into 4 Ω **£10.43**

SS.1100/H with full size heatsink **£11.82** (Heatsink alone **£1.39**)

TONE CONTROLS & PRE-AMPS

SS.100 Active tone control, stereo. ± 15 dB bass and treble **£3.00**

SS.101 Stereo pre-amp for ceramics, etc. Passive tone control details supplied. **£2.33**

SS.102 Stereo pre-amp for low output magnetic P.U.s. R.I.A.A. corrected **£4.05**

UNIT ONE

Combined pre-amp and active tone-control ± 15 dB at 10kHz treble, 30Hz bass. Stereo, Vol./Balance/treble/bass. 200mV out for 50mV in. Operates from 10 to 16V supply. **£9.00**

UNIT TWO

As Unit One, but for magnetic pick-up inputs 1 to 5mV R.I.A.A. corrected. **£12.43**

F.M. TUNERS

SS.201 Front end tuner, slow geared drive, two gang, A.F.C. facility. Tunes 88-108 MHz. **£5.90**

SS.202 I.F. amp. can take Meter & A.F.C. **£3.46**

SS.203 Phase lock loop Stereo Decoder **£4.19**

SS.203-1 Coil-type stereo decoder Neg. earth with I.C. **£3.06**

SS.203-2 Pos. earth **£2.50**

POWER SUPPLY UNITS

Complete with mains transformers, Low volt take-off points on all models except SS.300 and SS.312 off low voltage.

SS.312 12V/1A **£6.35**

SS.318 18V/1A **£6.54**

SS.324 24V/1A **£7.27**

SS.334 34V/2A **£8.31**

SS.345 45V/2A **£9.98**

SS.350 50V/2A **£10.38**

SS.370 70V/2A **£14.63**


SS.300 10-50V adjustable stabilizer to add to unstabilised supplies. Built-in protection against shorting **£5.02**

SS.310/50 Stabilised power supply. Output variable from 10V to 50V/2A. Built-in protection against shorting **£16.69**

Special terms for quantity buyers—U.K. and overseas trade enquiries invited.

PAY THE PRICE YOU READ

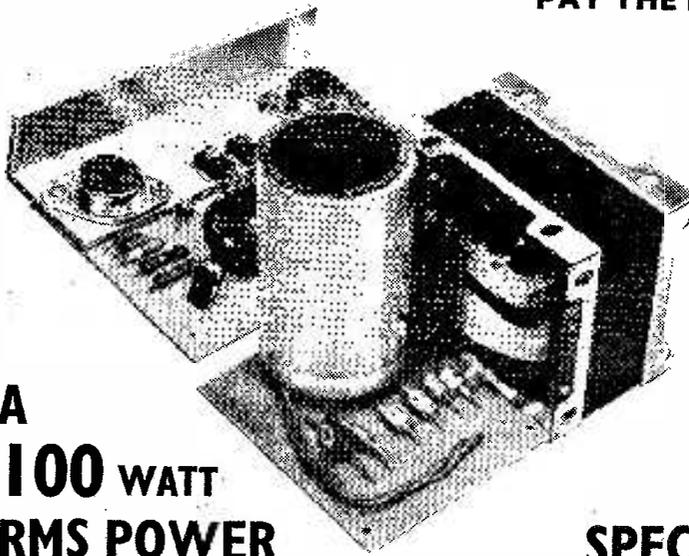All prices-shown include V.A.T. and post and packing charges so as to make ordering easy. When you buy in person from our shop, cost of p/p is deducted.



**A
100 WATT
RMS POWER
AMPLIFIER**

**A 70V/2A
SPECIAL POWER
SUPPLY UNIT**

FOR ONLY £24.25!

AND NO EXTRA FOR V.A.T. AND P. & P.

At Stirling Sound we design, make and sell our famous QV (Quality/Value) Modules ourselves in our own factory. With over 25 years of continuous selling direct to the public we know how to give value second to none. Was there ever better value than this? Look at this 100 watt R.M.S. amplifier with full size heatsink (SS.1100H) and 70 volt/2A power unit with special low volt take off point (13-15 volts) for pre-amp, etc. The assembly makes an ideal basis for a disco, a high quality P.A. system or domestic hi-fi system where low conversion factor loudspeakers are used, etc.

Bought separately, **SS.1100** costs **£10.43**, large heat sink **£1.39**, **SS.370**, **£14.63**. Total **£26.45**. Ordered together the cost is **£24.20**.

SAVES YOU £2.20!

WHEN ORDERING

Make cheques/money orders crossed, payable to Bi-Pre-Pak Ltd. Use separate sheet of paper if you prefer not to cut out coupon but quote Dept PW777. Every effort is made to ensure correctness of information at time of going to press. Prices subject to alteration without notice.

- **POWER OUTPUT**
100 watts R.M.S. into 4 ohms
- **FREQUENCY RANGE**
10Hz to 50 KHz ± 1 dB
- **SENSITIVITY**
500mV for full output
- **DISTORTION**
0.01% at half power
- **S/N RATIO**
Better than 75 dB
- **POWER REQUIREMENTS**
70 volts (i.e. SS.370)
- **SIZE (SS.1100)**
5 x 3 $\frac{1}{2}$ x 1 $\frac{1}{2}$ ins. without full size heatsink.

USE COUPON TO AVOID DELAY

STIRLING SOUND, 37 VANGUARD WAY, SHOEBURYNNESS, ESSEX

PLEASE SUPPLY

NAME

ADDRESS

for which I enclose cheque/money order £.....

Stirling Sound

Dept. PE.7
37 VANGUARD WAY
SHOEBURYNNESS, ESSEX
Telephone Shoeburyness (03708) 5543
SHOP
(open all day Saturdays) (0702) 351048
220-224 West Road,
Westcliff-on-Sea, Essex SSO 9DF
Components ● Equipment ● Hi-Fi ● Disco

BEFORE YOU BUY AN AMPLIFIER MODULE—CHECK:

DOES IT HAVE ★ 30 A POWER TRANSISTORS ★ GLASS FIBRE P.C.B.
 ★ 3A DRIVERS (100 W UNIT) ★ INTEGRAL OUTPUT CAPACITOR
 THEN COMPARE WITH THE TAMBA RANGE—EXCELLENT VALUE—25, 50 & 100 W RMS

TAM1000 100W 4 OHMS 65V	£9.80
TAM500 50W 4 OHMS 45V	£7.50
TAM250 25W 8 OHMS 45V	£4.75
POWER SUPPLIES	
For 1 or 2 TAM250/500	£7.50
For 1 or 2 TAM1000	£9.80
(Carr. 50p on supplies)	



NEW ALL PURPOSE MIXER/PREAMP
 (WITH 60 mm SLIDER VOLUME)

- Anodised & printed fascia
 - Suitable for multiple input systems
 - High & low impedance inputs
 - High sensitivity
 - Built in supply smoothing
 - 20-20,000 hz ±1dB
 - 80dB Noise level
 - Accepts a wide variety of inputs
 - Wide range bass & treble controls
- Use up to 10 preamps with 1 power

COMPLETE & TESTED assembly with Treble & Bass controls plus slider Volume Control. **£6.50**

- Suits loads 4-16 ohms
- 20-20,000 hz ±1dB
- Silicon circuitry throughout
- Glass fibre P.C.B.
- High sensitivity (100mV 10k)
- Low distortion (0.1%)
- Low profile (1" High 3½" x 3")
- 75% efficient
- Accepts most mixer/preamps
- Four simple connections

High Grade Components used throughout: Texas, Mullard, R.C.A., Plessey, etc.

You may order as follows: C.W.O. (crossed cheques, P.O.s, M.O.s, etc.) C.O.D. (60p extra). We accept Access and Barclaycard—send or telephone your number—do not send your card. Add VAT at 8% to orders for 50-100W units and at 12½% for 25W units


Hours, 9.30 a.m.-5 p.m.
 Monday—Saturday.
 Callers welcome.
 Tel: (01) 684 0098

TAMBA ELECTRONICS

BENSHAM MANOR ROAD PASSAGE, BENSHAM MANOR ROAD, THORNTON HEATH, SURREY

A MINIATURE POWER TOOL to speed your building

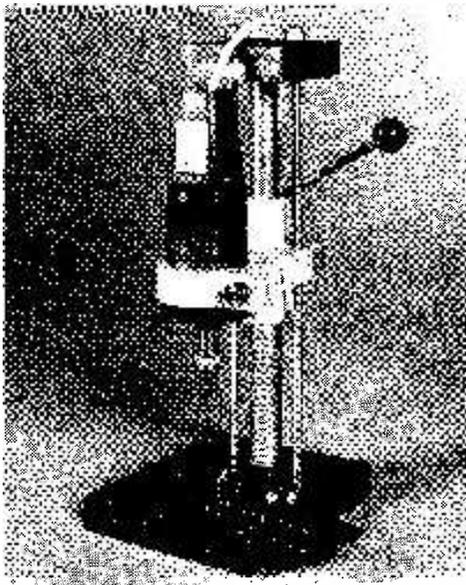- Super 30 Kit (30 Tools) (incl. drill without stand) **£19.39 plus P. & P. 85p**
- PIS Drill Stand **£5.13 plus P. & P. 35p**
- PI Drill only **£9.67 plus P. & P. 35p**
- Flexible Drive Shaft **£5.94 plus P. & P. 25p**
- Transformer 240V a.c./12V d.c. **£7.56 plus P. & P. 70p**
- Variable Speed Transformer **£9.50 plus P. & P. 70p**



Replacement drills, stones, burrs, etc. **40p** each. Circular saw blades set of 4 with arbor **£2.50**. P. & P. any quantity **20p**.

All VAT inclusive

PRECISION PETITE LTD.

119a High Street, Teddington, Middlesex TW11 8HG

Tel. 01-977 0878 (24 hour answering service)

9" x 4" S.A.E. please for leaflet and order form

INTRODUCING
 THE NEW
 CROFTON
 C1 CCTV
 CAMERA

Please send 10 x 10p
 for stamp addressed above



The C1 Camera is a completely new design offering a high specification CCTV Camera suitable for both professional and amateur use.

The design offers high sensitivity with good signal to noise ratio by incorporating an F.E.T. front end. Wide range and stable automatic sensitivity control circuit allows Camera to be operated in a wide range of lighting conditions. All controls are internal and once set remain stable over long time periods. Small size and weight make this a most versatile Camera for general usage. Special one off Retail Price including Vidicon (Less Lens) **£140.59** inclusive. Kits also available.

Send s.a.e. for information. Secondhand cameras and monitors always available.

CROFTON ELECTRONICS LTD
 Dept. B, 35 Grosvenor Road, Twickenham, Middx. Tele. 01-891 1923

SUPERSOUND 13 HI-FI MONO AMPLIFIER



A superb solid state audio amplifier. Brand new components throughout. 5 silicon transistors plus 2 power output transistors in push-pull. Full wave rectification. Output approx. 13 watts r.m.s. into 8 ohms. Frequency response 12Hz-30KHz \pm 3db. Fully integrated pre-amplifier stage with separate Volume, Bass boost and Treble cut controls. Suitable for 8-15 ohm speakers. Input for ceramic or crystal cartridge. Sensitivity approx. 40mV for full output. Supplied ready built and tested, with knobs, escutcheon panel, input and output plugs. Overall size 3" high \times 6" wide \times 7 1/2" deep. AC 200/250V. PRICE \pounds 13.75, P. & P. \pounds 10.00.

LATEST ACOS GP01/18C mono compatible cartridge with t/o stylus for LP/EP/78. Universal mounting bracket. \pounds 1.80. P. & P. 18p.


CERAMIC STEREO CARTRIDGE. Universal mounting brackets and turnover stylus 70mV per channel output. ONLY \pounds 1.80. P. & P. 18p.

SONOTONE STAHG COMPATIBLE STEREO CARTRIDGE T/O stylus Diamond Stereo LP and Sapphire 78. ONLY \pounds 2.86. P. & P. 18p. Also available fitted with twin Diamond T/O stylus for Stereo LP. \pounds 2.86. P. & P. 18p.

LATEST CRYSTAL T/O STEREO COMPATIBLE CARTRIDGE for EP/LP/Stereo 78. \pounds 1.80. P. & P. 18p.

LATEST T/O MONO COMPATIBLE CARTRIDGE for playing EP/LP/78 mono or stereo records on mono equipment. Only \pounds 1.58. P. & P. 18p.

HARVERSONIC STEREO 44

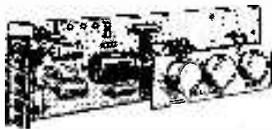

A solid state stereo amplifier chassis, with an output of 3-4 watts per channel into 8 ohm speakers.

Using the latest high technology integrated circuit amplifiers with built in short term thermal overload protection. All components including rectifier smoothing capacitor, fuse, tone control, volume controls, 2 pin din sockets & 5 pin din tape reel, plug socket are mounted on the printed circuit panel size approx. 9 1/2" \times 11" max. depth. Supplied brand new & tested, with knobs, brushed anodised aluminium 2 way escutcheon (to allow the amplifier to be mounted horizontally or vertically) at only \pounds 9.00 plus 50p P. & P. Mains transformer with an output of 17v a/c at 500mA can be supplied at \pounds 1.50 + 40p P & P if required. Full connection details supplied.

VYNAIR & REXINE SPEAKERS & CABINET FABRICS app. 64 in. wide. Our Price \pounds 1.50 yd. length. P. & P. 50p per yd. (min. 1 yd.). S.A.E. for samples.

BRAND NEW MULTI-RATIO MAINS TRANSFORMERS. Giving 13 alternatives. Primary: 0-210-240v. Secondary combinations 0-5-10-15-20-25-30-35-40-50v. half wave at 1 amp, or 10-0-10, 20-0-20, 30-0-30v. at 2 amps full wave. Size 3in. long \times 3 1/2in. wide \times 3in. deep. Price \pounds 2.90 P. & P. 90p.

MAINS TRANSFORMER. For power supplies. Pri. 200/240v. Sec. 9-0-9 at 500 mA. \pounds 1.50. P. & P. 60p. Pri. 200/240v. Sec. 12-0-12 at 1 amp. \pounds 1.85. P. & P. 60p. Pri. 200/240v. Sec. 10-0-10 at 2 amp. \pounds 2.85. P. & P. 90p. Pri. 200/240v. Sec. 23V at 1.5amp, 6V at .6 amp, 8V at 50mA. \pounds 2.00 + 65p P. & P.

ALL-PURPOSE POWER SUPPLY UNIT 200/240v. A.C. input. Four switched fully smoothed D.C. outputs giving 6v. and 7 1/2v. and 8v. and 12v. at 1 amp on load. Fitted insulated output terminals and pilot lamp indicator. Hammer finish metal case overall size 6" \times 3 1/2" \times 2 1/2". Ready built and tested Price \pounds 6.75 P. & P. 85p.


STEREO-DECODER

SIZE 2" \times 3" \times 1/2" ready built. Pre-aligned and tested. Sens. 20-560 mV for 9-16V neg. earth operation. Can be fitted to almost any FM VHF radio or tuner. Stereo beacon light can be fitted if required. Full details and instructions (inclusive of hints and tips) supplied. \pounds 5.84 plus 20p. P. & P. Stereo beacon light if required 40p extra.



QUALITY RECORD PLAYER AMPLIFIER MK. II A top quality record player amplifier employing heavy duty double wound mains transformer, ECC83, EL84, and rectifier. Separate Bass, Treble and Volume controls. Complete with output transformer matched for 8 ohm speaker. Size 7in. wide \times 3in. deep \times 6in. high. Ready built and tested. PRICE \pounds 7.00. P. & P. 90p. ALSO AVAILABLE mounted on board with output transformer and speaker. PRICE \pounds 8.00. P. & P. \pounds 1.

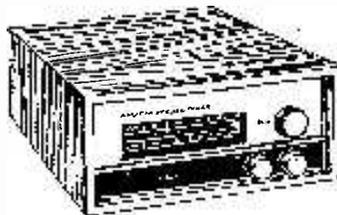MAINS OPERATED SOLID STATE AM/FM STEREO TUNER




200/240V Mains operated Solid State F/M A/M Stereo Tuner. Covering M.W. A.M. 540-1605KHz VHF/FM 88-108MHz. Built-in Ferrite rod aerial for M.W. Full AFC and AGC on AM and FM. Stereo Beacon Lamp Indicator. Built in Pre-amps with variable output voltage adjustable by pre-set control. Max o/p Voltage 600mV RMS into 20K. Simulated Teak finish cabinet. Will match almost any amplifier. Size 8 1/2" \times 4" \times 9 1/2" approx.

LIMITED NUMBER ONLY at \pounds 28.00 + \pounds 1.30 P. & P.

SPECIAL OFFERS

Mullard LP1159 R.F.-I.F. Double Tuned Amplifier Module for nominal 470 KHz. Size approx. 2 1/2" \times 1 1/2" \times 7/8" Volt + earth. Brand new pre-aligned. Full specification and connection details supplied. \pounds 2.25. P. & P. 12p

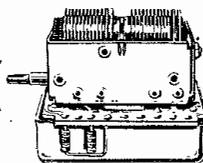Pye VHF/FM Tuner Head covering 88-108 M/Hz. 10.7 M/Hz I.F. output. 7.8 Volt + earth. Supplied pre-aligned, with full circuit diagram. Connection details supplied. Beautifully made with precision-ganged FM gang and 323P1 + 323P1 A.M. Tuning gang only \pounds 3.15 + P. & P. 35p.



PRECISION MADE

Push Button Switch bank. 8 Buttons giving 16 S/P C/O interlocked switches plus 1 Cancel Button Plus 3 d/p c/o. Overall size 5" \times 2 1/2" \times 1". Supplied complete with chrome finished switch buttons. 2 for \pounds 1.50 + 20p P & P.

HI-FI LOUDSPEAKER SYSTEM MK II

Beautifully made, simulated teak finish enclosure with attractive slatted front. Size 16 1/2" high \times 10 1/2" wide \times 9" deep (approx.). Fitted with E.M.I. Ceramic Magnet 13" \times 8" bass unit, H.F. tweeter unit and crossover. AVAILABLE IN NOMINAL 4 Ohm, 8 Ohm or 16 Ohm impedance (state which). Handling power 10 watts R.M.S.

OUR PRICE \pounds 12.80 each. Carr. \pounds 1.90 ea. Cabinet Available Separately \pounds 7.60, Carr. \pounds 1.40 each. Also available in 8 ohms with EMI 13" \times 8" bass speaker with parasitic tweeter \pounds 11.10, Carr. \pounds 1.90 ea.

LOUDSPEAKER BARGAINS

5in. 3 ohm \pounds 2.00, P. & P. 35p. 7 \times 4in. 8 ohm \pounds 2.35. P. & P. 45p. 10 \times 6in. 3 or 16 ohm \pounds 3.80, P. & P. 75p. 8 \times 6in. 8 ohm with high flux magnet \pounds 3.80. P. & P. 50p. Tweeter. Approx. 3 1/2". Available 3 or 8 or 15 ohms, \pounds 2.00 + 25p. P. & P. 2" Plastic Cone HF Tweeter 4 ohm \pounds 3.50 per matched pair + 50p P. & P.

HIGH POWER HI-FI 8 OHM DOME TWEETER. 1" voice coil, magnet size 3" dia, suitable for use in up to 50 watt systems \pounds 4.50 ea + 60p P. & P.

"POLY PLANAR" WAFER-TYPE, WIDE RANGE ELECTRO-DYNAMIC SPEAKER

Size 11 1/2" \times 14 1/2" \times 1 1/2" deep. Weight 19oz. Power handling 20W r.m.s. (40W peak). Impedance 8 ohm only. Response 40Hz-20kHz. Can be mounted on ceiling, walls, doors, under tables, etc., and used with or without baffle. Send S.A.E. for full details. Only \pounds 8.40 each + p. & p. (one 75p, two 90p).

Now also available 8" - 8 ohm 10 watts, r.m.s. 20 watt peak 40 Hz-20,000 Hz. Overall depth 1". Ideal for Hi-Fi or for use in cars \pounds 5.10 + p. & p. (one 35p, two 65p).


SPECIAL LINES OFFERED SUBJECT TO STOCK AVAILABILITY

Limited number of British manufacturer's surplus professional 100 watt RMS slave amplifiers. Special features, 2 separate power modules, 1 for Bass response and 1 for mid-range/tweeter, 5 stage LED display for power o/p indication, A/C mains i/f switchable for 110 or 240v. Can easily be converted to Stereo. AVAILABLE TO PERSONAL CALLERS ONLY, PLEASE PHONE TO CONFIRM AVAILABILITY. Brand new & tested only \pounds 33.75.

25 watt RMS Solid state power amplifier module. Fre. Resp. 35 Hz-20 KHz. Power requirements 40 volts @ 1.5 amps. Full c/d & connection details supplied. \pounds 6.20 + 30p P/P.

Prices include VAT at Current Rate

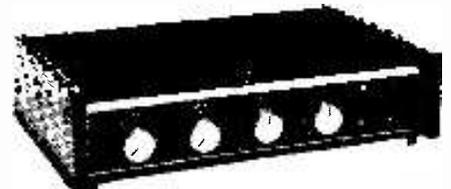HARVERSONIC SUPERSOUND 10 + 10 STEREO AMPLIFIER KIT



A really first-class Hi-Fi Stereo Amplifier Kit. Uses 14 transistors including Silicon Transistors in the first five stages on each channel resulting in even lower noise level with improved sensitivity. Integrated pre-amp with Bass, Treble and two Volume Controls. Suitable for use with Ceramic or Crystal cartridges. Very simple to modify to suit magnetic cartridge—instructions included. Output stage for any speakers from 8 to 15 ohms. Compact design, all parts supplied including drilled metalwork high quality ready drilled printed circuit board with component identification clearly marked, smart brushed anodised aluminium front panel with matching knobs, wire, solder, nuts, bolts—no extras to buy. Simple step by step instructions enable any constructor to build an amplifier to be proud of. Brief specification; Power output: 14 watts r.m.s. per channel into 5 ohms. Frequency response \pm 3dB 12-30,000 Hz Sensitivity: better than 80mV into 1M Ω . Full power bandwidth: \pm 3dB 12-15,000 Hz. Bass boost approx. to \pm 12dB. Treble cut approx. to -16dB. Negative feedback 18dB over main amp. Power requirements 35v. at 1.0 amp. Overall Size 12" \times 8" \times 2 1/2".

Fully detailed 7 page construction manual and parts list free with kit or send 25p plus large S.A.E.

AMPLIFIER KIT \pounds 13.50 P. & P. 65p (Magnetic input components 33p extra)

POWER PACK KIT \pounds 5.50 P. & P. 85p

CABINET \pounds 5.50 P. & P. 85p

SPECIAL OFFER—only \pounds 23.75 if all 3 items ordered at one time plus \pounds 1 p. & p.

Full after sales service

Also available ready built and tested \pounds 31.25. P. & P. \pounds 1.

3-VALVE AUDIO AMPLIFIER HA34 MK II




Designed for Hi-Fi reproduction of records. A.C. Mains operation. Ready built on plated heavy gauge metal chassis, size 7 1/2" \times 4" \times 4 1/2". Incorporates ECC83, EL84, E280 valves. Heavy duty, double wound mains transformer and output transformer matched for 8 ohm speaker. Separate volume control and now with improved wide range tone controls giving bass and treble lift and cut. Negative feedback line. Output 4 1/2 watts. Front panel can be detached and leads extended for remote mounting of controls. Complete with knobs, valves, etc., wired and tested for only \pounds 8.20. P. & P. \pounds 1.00.

HSL "FOUR" AMPLIFIER KIT. Similar in appearance to HA34 above but employs entirely different and advanced circuitry. Complete set of parts, etc \pounds 7.60 P. & P. \pounds 1.00.

10/14 WATT HI-FI AMPLIFIER KIT

A stylishly finished monaural amplifier with an output of 14 watts from 2 EL84s in push-pull. Super reproduction of both music and speech, with negligible hum. Separate inputs for mike and gram allow records and announcements to follow each other. Fully shrouded section wound output transformer to match 3-15 Ω speaker and 2 independent volume controls, and separate bass and treble controls are provided giving good lift and cut. Valve line-up 2 EL84s, ECC83, EF86 and E280 rectifier. Simple instruction booklet 25p + SAE (Free with parts) All parts sold separately. ONLY \pounds 12.00 P. & P. \pounds 1.35. Also available ready built and tested \pounds 16.50 P. & P. \pounds 1.35.

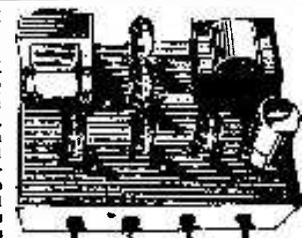

GENERAL PURPOSE HIGH STABILITY TRANSISTOR PRE-AMPLIFIER

For P.U., Tape, Mike, Guitar, etc. and suitable for use with valve or transistor equipment. 9-18v. battery or from H.T. line 200/300v. Frequency response 15Hz-25KHz. Gain 26dB. Solid encapsulation size 1 1/2" \times 1 1/2" \times 1 1/2". Brand new complete with instructions. Price \pounds 1.80 P. & P. 15p.

(Please write clearly)

PLEASE NOTE: P. & P. CHARGES QUOTED APPLY TO U.K. ONLY. P. & P. ON OVERSEAS ORDERS CHARGED EXTRA.

Open 9.30-5.30 Monday to Friday. 9.30-5 Saturday Closed Wednesday.

All prices and specifications correct at time of press and subject to alteration without notice.

HARVERSON SURPLUS CO. LTD.

(Dept. P.W.) 170 HIGH ST., MERTON, LONDON, S.W.19 Tel.: 01-540 3985

A few minutes from South Wimbledon Tube Station.

SEND STAMPED ADDRESSED ENVELOPE WITH ALL ENQUIRIES

SEMICONDUCTORS—COMPONENTS

DIODES

Type	Price	Type	Price	Type	Price	Type	Price
AA129	£0.08	BY100	£0.16	BYZ11	£0.31	OA91	£0.07
AA130	£0.09	BY107	£0.12	BYZ12	£0.31	OA95	£0.07
AA213	£0.10	BY105	£0.18	BYZ13	£0.26	OA182	£0.07
AAZ17	£0.10	BY114	£0.12	BYZ16	£0.41	OA200	£0.08
BA100	£0.10	BY124	£0.12	BYZ17	£0.36	OA202	£0.08
BA102	£0.12	BY126	£0.15	BYZ18	£0.36	SD10	£0.06
BA148	£0.15	BY127	£0.16	BYZ19	£0.28	SD19	£0.06
BA154	£0.12	BY128	£0.16	OA10	£0.35	IN34	£0.07
BA155	£0.14	BY130	£0.17	OA47	£0.07	IN34A	£0.07
BA156	£0.14	BY133	£0.21	OA70	£0.07	IN914	£0.06
BA173	£0.15	BY164	£0.31	OA79	£0.07	IN916	£0.06
BB104	£0.15	BY176	£0.75	OA81	£0.07	IN4148	£0.06
BAX13	£0.07	BY206	£0.00	OA85	£0.09	IS44	£0.05
BAX16	£0.08	BYZ10	£0.36	OA90	£0.07	IS920	£0.06

SILICON RECTIFIERS

Type	Price	Type	Price	Type	Price	Type	Price
IS920	£0.06	IN4003	£0.07	IS020	£0.10	IS031	£0.25
IS921	£0.07	IN4004	£0.08	IS021	£0.11	IN5400	£0.13
IS922	£0.08	IN4005	£0.09	IS023	£0.13	IN5401	£0.15
IS923	£0.09	IN4006	£0.10	IS025	£0.14	IN5402	£0.16
IS924	£0.10	IN4007	£0.11	IS027	£0.15	IN5404	£0.17
IN4001	£0.05	IS015	£0.09	IS029	£0.20	IN5406	£0.21
IN4002	£0.06					IN5407	£0.25

TRIACS

2 AMP TO5 CASE			10 AMP TO48 CASE		
Volts	No.	Price	Volts	No.	Price
100	TR12A/100	£0.31	100	TR110A/100	£0.77
200	TR12A/200	£0.51	200	TR110A/200	£0.92
400	TR12A/400	£0.71	400	TR110A/400	£1.12

6 AMP TO66 CASE			10 AMP TO48 CASE		
Volts	No.	Price	Volts	No.	Price
100	TR16A/100	£0.51	100	TR110A/100	£0.77
200	TR16A/200	£0.81	200	TR110A/200	£0.92
400	TR16A/400	£0.77	400	TR110A/400	£1.12

THYRISTORS

600mA TO18 CASE			7 AMP TO48 CASE		
Volts	No.	Price	Volts	No.	Price
10	THY600/10	£0.13	50	THY7A/50	£0.48
20	THY600/20	£0.13	100	THY7A/100	£0.51
30	THY600/30	£0.19	200	THY7A/200	£0.57
50	THY600/50	£0.22	400	THY7A/400	£0.62
100	THY600/100	£0.25	600	THY7A/600	£0.78
200	THY600/200	£0.38	800	THY7A/800	£0.92
400	THY600/400	£0.45			

1 AMP TO5 CASE			10 AMP TO48 CASE		
Volts	No.	Price	Volts	No.	Price
50	THY1A/50	£0.26	50	THY10A/50	£0.51
100	THY1A/100	£0.27	100	THY10A/100	£0.57
200	THY1A/200	£0.28	200	THY10A/200	£0.62
400	THY1A/400	£0.36	400	THY10A/400	£0.71
600	THY1A/600	£0.45	600	THY10A/600	£0.99
800	THY1A/800	£0.58	800	THY10A/800	£1.22

3 AMP TO66 CASE			16 AMP TO48 CASE		
Volts	No.	Price	Volts	No.	Price
50	THY3A/50	£0.25	50	THY16A/50	£0.54
100	THY3A/100	£0.27	100	THY16A/100	£0.58
200	THY3A/200	£0.33	200	THY16A/200	£0.62
400	THY3A/400	£0.42	400	THY16A/400	£0.77
600	THY3A/600	£0.50	600	THY16A/600	£0.99
800	THY3A/800	£0.65	800	THY16A/800	£1.39

5 AMP TO66 CASE			30 AMP TO94 CASE		
Volts	No.	Price	Volts	No.	Price
50	THY5A/50	£0.36	50	THY30A/50	£1.18
100	THY5A/100	£0.48	100	THY30A/100	£1.43
200	THY5A/200	£0.50	200	THY30A/200	£1.63
400	THY5A/400	£0.57	400	THY30A/400	£1.79
600	THY5A/600	£0.69	600	THY30A/600	£3.50
800	THY5A/800	£0.81			

5 AMP TO220 CASE			No.		
Volts	No.	Price	Price		
400	THY5A/400P	£0.57	BT101/500R	£0.80	
600	THY5A/600P	£0.69	BT102/500R	£0.80	
800	THY5A/800P	£0.81	BT106	£1.25	
			BT107	£0.93	
			BT108	£0.98	
			2N3228	£0.70	
			2N3525	£0.77	
			BTX30/50L	£0.33	
			BTX30/400L	£0.46	
			C106/4	£0.60	

ORDERING

PLEASE WORD YOUR ORDERS EXACTLY AS PRINTED, NOT FORGETTING TO INCLUDE OUR PART NUMBER

VAT

ADD 12½% TO PRICES MARKED*
ADD 8% TO OTHERS EXCEPTING THOSE MARKED †, THESE ARE ZERO RATED

SUPER UNTESTED PAKS

Pak No.	Qty.	Description	Order No.	Price
U50	100	Germ. gold bonded OA47 diode	16130	£0.60
U51	150	Germ. OA70/81 diode	16131	£0.60
U52	100	Silicon diodes 200mA OA200	16132	£0.60
U53	150	Diodes 75mA 1N4148	16133	£0.60
U54	50	Sil rect top hat 750mA	16134	£0.60
U55	20	Sil rect stud type 3 amp	16135	£0.60
U56	50	400mW zeners DOT case	16136	£0.60
U57	30	NPN trans BC107/8 plastic	16137	£0.60
U58	30	PNP trans BC177/178 plastic	16138	£0.60
U59	25	NPN TO39 2N697/2N1711 silicon	16139	£0.60
U60	25	PNP TO59 2N2905 silicon	16140	£0.60
U61	30	NPN TO18 2N706 silicon	16141	£0.60
U62	25	NPN BFY50/51	16142	£0.60
U63	30	NPN plastic 2N3906 silicon	16143	£0.60
U64	30	PNP plastic 2N3905 silicon	16144	£0.60
U65	30	Germ. 0071 PNP	16145	£0.60
U66	15	Plastic power 2N3055 NPN	16146	£1.20
U67	10	TO3 metal 2N3055 NPN	16147	£1.20
U68	20	Unijunction trans IIS43	16148	£0.60
U69	10	1 amp SCR TO39	16149	£1.20
U70	8	3 amp SCR TO66 case	16150	£1.20

Code Nos. mentioned above are given as a guide to the type of device in the pak. The device themselves are normally unmarked.

COMPONENT PAKS

Pak No.	Qty.	Description	Order No.	Price
C1	200	Resistor mixed value approx. (count by weight)	16164	£0.60
C2	150	Capacitors mixed value approx. (count by weight)	16165	£0.60
C3	50	Precision resistors. Mixed values	16166	£0.60
C4	80	½W resistors mixed preferred values	16167	£0.60
C5	5	Pieces assorted ferrite rods	16168	£0.60
C6	2	Tuning gangs. MW/LW VHF	16169	£0.60
C7	1	Pack wire 50 meters assorted colours single strand	16170	£0.60
C8	10	Read switches	16171	£0.60
C9	3	Micro switches	16172	£0.60
C10	15	Assorted pots	16173	£0.60
C11	5	Metal Jack sockets 3 x 3-5mm 2x standard switch types	16174	£0.60
C12	30	Paper condensers preferred types mixed values	16175	£0.60
C13	20	Electrolytics trans. types	16176	£0.60
C14	1	Pak assorted hardware—nuts/bolts, gromets, etc.	16177	£0.60
C15	5	Mains slide switches ass.	16178	£0.60
C16	20	Assorted tag strips and panels	16179	£0.60
C17	15	Assorted control knobs	16180	£0.60
C18	4	Rotary wave change switches	16181	£0.60
C19	2	Relays 6-24V operating	16182	£0.60
C20	1	Pak. copper laminate approx. 200 sq.in.	16183	£0.60
C21	15	Assorted fuses 100mA-5 amp	16184	£0.60
C22	50	Metres PVC sleeving assorted size and colour	16185	£0.60
C23	60	½ watt resistors mixed preferred values	16188	£0.60
C24	25	Presets assorted type and value	16186	£0.60
C25	30	Metres stranded wire assorted colours	16187	£0.60

SLIDER PAKS

Pak No.	Qty.	Description	Order No.	Price
S1	6	Slider potentiometers, mixed values	16190	£0.60
S2	6	Slider potentiometers, all 470 ohms	16191	£0.60
S3	6	Slider potentiometers, all 10k Ω lin	16192	£0.60
S4	6	Slider potentiometers, all 22k Ω lin	16193	£0.60
S5	6	Slider potentiometers, all 47k Ω lin	16194	£0.60
S6	6	Slider potentiometers, all 47k Ω log	16195	£0.60

CERAMIC PAK

Containing a range of first quality miniature ceramic capacitors. Unrepeatable value.

Pak No.	Qty.	Description	Order No.	Price
MC1	24	miniature ceramic capacitors, 3 of each value—22pF, 27pF, 33pF, 39pF, 47pF, 68pF, and 82pF	16160	£0.60
MC2	24	miniature ceramic capacitors, 3 of each value—100pF, 120pF, 150pF, 180pF, 220pF, 270pF, 330pF and 390pF	16161	£0.60
MC3	24	miniature ceramic capacitors, 3 of each value—470pF, 560pF, 680pF, 820pF, 1,000pF, 1,500pF, 2,200pF and 3,300pF	16162	£0.60
MCA	21	miniature ceramic capacitors, 3 of each value—4,700pF, 6,800pF, 0.01μF, 0.015μF, 0.022μF, 0.033μF and 0.047μF	16163	£0.60

LINEAR PAKS

Manufacturer's "Fall Outs" which include Functional and part-Functional Units. These are classed as "out-of-spec" from the maker's very rigid specifications, but are ideal for learning about ICs and experimental work.

U721—30 Assorted Linear Types, 709 741, 747, 748, 710, 588, etc.
ORDER No. 16227 *£1.50

U76SD FM STEREO DECODER
5 ICs 76110 equivalent to MC1310P-MA767. Data supplied with pak.
ORDER No. 16229 *£1.50

U76A AUDIO POWER OUTPUT AMPLIFIERS
8 assorted types. SL403, 76013, 76003, etc. Data supplied with pak.
ORDER No. 16228 *£1.00

74 SERIES PAKS

Manufacturer's "Fall Outs" which include Functional and part-Functional Units. These are classed as "out-of-spec" from the maker's very rigid specifications, but are ideal for learning about ICs and experimental work.

74G—100 Gates assorted 7400-01-04-10-50-60, etc.
ORDER No. 16224 *£1.20

74F—50 Flip-Flops assorted 7470-72-73-74-76-104-109, etc.
ORDER No. 16225 *£1.20

74M—30 MSI. Assorted Types. 7441-47-90-154, etc.
ORDER No. 16226 *£1.20

VEROBOARDS PAKS

VB1—Approx. 30sq.in various sizes. All 0.1in matrix.
ORDER No. 16199 60p

VB2—Approx. 30sq.in various sizes. 0.15in matrix.
ORDER No. 16200 60p

ELECTROLYTIC PAKS

A range of paks each containing 18 first quality, mixed value miniature electrolytics.

EC1—Values from 0.47μF to 10μF.
ORDER No. 16201 *60p

EC2—Values from 10μF to 100μF.
ORDER No. 16202 *60p

EC3—Values from 100μF to 680μF.
ORDER No. 16203 *60p

C280 CAPACITOR PAK

75. Mullard C280 capacitors, mixed values ranging from 0.01μF to 2.2μF complete with identification sheet.
ORDER No. 16204 *£1.20

CARBON RESISTOR PAKS

These paks contain a range of Carbon Resistors, assorted into the following groups:

R1—60 mixed ½W 100-820 ohms.
ORDER No. 16213 *60p

R2—60 mixed ½W 1-8-2k Ω.
ORDER No. 16214 *60p

R3—60 mixed ½W 10-82k Ω.
ORDER No. 16215 *60p

R4—60 mixed ½W 100-820Ω Ω.
ORDER No. 16216 *60p

R5—40 mixed ½W 100-820Ω Ω.
ORDER No. 16217 *60p

R6—40 mixed ½W 1-8-2k Ω.
ORDER No. 16218 *60p

R7—40 mixed ½W 10-82k Ω.
ORDER No. 16219 *60p

R8—40 mixed ½W 100-820k Ω.
ORDER No. 16220 *60p

R9—60 mixed ½W 1-10M Ω.
ORDER No. 16230 *60p

R10—40 mixed ½W 1-10M Ω.
ORDER No. 16231 *60p

WORLD SCOOP JUMBO SEMICONDUCTOR PAK

Transistors, Germ. and Silicon Rectifiers, Diodes, Triacs, Thyristors, ICs and Zeners.

ALL NEW AND CODED

Approx. 100 pieces. Offering the amateur a fantastic bargain PAK and an enormous saving—identification and data sheet in every pak.
ORDER No. 16222 *£2.25

Just a selection from our huge stocks!

SEE OUR 1977 CATALOGUE

1

PAKS—PARTS—AUDIO MODULES

PANEL METERS

4in RANGE

Size 4½ × 3½ × 1½in

Value	No.	Price
0-50µA	1302	£4.50
0-100µA	1303	£4.50
0-500µA	1304	£4.50
0-1mA	1305	£6.00
0-50V	1306	£6.00

2in RANGE

Size 2½ × 1½ × 1½in

Value	No.	Price
0-50µA	1307	£3.50
0-100µA	1308	£3.50
0-500µA	1309	£3.50
0-1mA	1310	£3.50
0-50V	1311	£3.50

MR2P TYPE

Size 42 × 42 × 30mm

Value	No.	Price
0-50µA	1313	£4.80
0-1mA	1315	£3.20

EDGEWISE

Size 3½ × 1½ × 2½in

Cut out 2½ × 1½in

Value	No.	Price
0-1mA	1316	£4.05
0-500µA	1317	£4.05

MINIATURE BALANCE/TUNING METER

Size 23 × 22 × 26mm

Sensitivity 100/0/100µA

No.	Price
1318	£1.95

BALANCE/TUNING

Size 45 × 22 × 34mm

Sensitivity 100/0/100µA

No.	Price
1319	£2.00

MIN. LEVEL METER

Size 23 × 22 × 26mm

Sensitivity 200µA

No.	Price
1320	£1.95

Vu METER

Size 40 × 40 × 29mm

Sensitivity 130µA

No.	Price
1321	£2.00

MINI MULTI-METER

Size 60 × 24 × 90mm

Sensitivity 1000 ohms/V

A.C. VOLTS 0-10, 50, 250 1000

D.C. VOLTS 0-10, 50, 250 1000

D.C. CURRENT 0-1 100mA Resistance 0-150kΩ

No.	Price
1322	£5.95

P & P

Postage and Packing add 25p unless otherwise shown. Add extra for airmail. Minimum order £1.

TRANSISTORS

BRAND NEW—FULLY GUARANTEED

Type	Price	Type	Price	Type	Price	Type	Price	Type	Price	Type	Price
AC126	£0.16	BC109C	£0.08	BC460	£0.38	BFX84	£0.23	TIP29C	£0.62	2N2906A	£0.19
AC127	£0.14	BC147	*£0.09	BC461	£0.38	BFX85	£0.24	TIP30A	£0.50	2N2907	£0.20
AC128	£0.12	BC148	*£0.09	BC477	£0.20	BFX86	£0.25	TIP30B	£0.60	2N2907A	£0.22
AC128K	£0.26	BC149	*£0.09	BC478	£0.19	BFX87	£0.22	TIP30C	£0.70	2N2926G	*£0.09
AC132	£0.15	BC157	*£0.12	BC479	£0.20	BFX88	£0.22	TIP31A	£0.54	2N2926V	*£0.08
AC134	£0.15	BC158	*£0.12	BC547	*£0.12	BFY90	*£0.55	TIP31B	£0.68	2N2926O	*£0.08
AC137	£0.15	BC159	*£0.12	BC548	*£0.12	BFY50	*£0.14	TIP31C	£0.68	2N2926P	*£0.08
AC141	£0.18	BC167	*£0.12	BC549	*£0.12	BFY51	*£0.14	TIP32A	£0.64	2N2926Q	*£0.08
AC141K	£0.30	BC168	*£0.12	BC550	*£0.14	BFY52	*£0.14	TIP32B	£0.76	2N2926R	*£0.08
AC142	£0.18	BC169	*£0.12	BC555	*£0.14	BIP19	£0.38	TIP32C	£0.80	2N2926S	*£0.08
AC176	£0.12	BC169C	*£0.12	BC557	*£0.13	BIP20	£0.38	TIP41A	£0.66	2N2926T	*£0.08
AC176K	£0.26			BC558	*£0.12	BIP19/20MP		TIP41B	£0.70	2N2926U	*£0.08
AC178	£0.25	BC170	*£0.10	BC559	*£0.14			TIP41C	£0.80	2N2926V	*£0.08
AC179	£0.25	BC171	*£0.10	BD115	£0.50	BRY39	£0.45	TIP42A	£0.72	2N2926W	*£0.08
AC180	£0.20	BC172	*£0.10	BD116	£0.80	BU105	£1.90	TIP42B	£0.78	2N3053	£0.16
AC180K	£0.30	BC173	*£0.12	BD121	£0.65	BU105/02		TIP42C	£0.95	2N3054	£0.40
AC181	£0.20	BC177	*£0.16	BD123	£0.65			TIP2955	£0.95	2N3055	£0.40
AC181K	£0.30	BC178	*£0.16	BD124	£0.70	BU204	£1.70	TIP3055	£0.75	2N3414	£0.16
AC187	£0.16	BC179	*£0.16	BD121	£0.35	BU205	£1.70	TIS43	£0.22	2N3415	£0.16
AC187K	£0.26	BC180	*£0.25	BD132	£0.38	BU208	£2.40	TIS90	*£0.18	2N3416	£0.29
AC188	£0.16	BC181	*£0.25	BD131/132MP		BU208/02		UT46	£0.20	2N3417	£0.28
AC188K	£0.26	BC182L		BD133	£0.80			ZTX107	*£0.10	2N3418	£0.85
AD140	£0.60			BD135	£0.36	E1222	£0.38	ZTX108	*£0.10	2N3615	£0.90
AD142	£0.85	BC183	*£0.10	BD136	£0.36	MJE2955		ZTX109	*£0.10	2N3616	£0.90
AD143	£0.75	BC183L		BD137	£0.38	MJE3055	£0.60	ZTX109	*£0.10	2N3648	£0.09
AD149	£0.60	BC184	*£0.10	BD138	£0.45	MJE3440		ZTX300	*£0.12	2N3702	£0.08
AD161	£0.36	BC184L		BD139	£0.54			ZTX300	*£0.12	2N3703	£0.08
AD162	£0.36			BD140	£0.60			ZTX500	*£0.14	2N3704	£0.07
AD161/162MP		BC207	*£0.11	BD139/140MP		MP8113	£0.45			2N3705	£0.07
		BC208	*£0.11			MPF102	£0.35	2N1613	£0.20	2N3706	£0.08
AF114	£0.20	BC209	*£0.12	BD155	£0.80	MPF104	£0.39	2N1711	£0.20	2N3707	£0.08
AF115	£0.20	BC212	*£0.11	BD175	£0.60	MPF105	£0.39	2N1889	£0.45	2N3708	£0.07
AF116	£0.20	BC212L		BD176	£0.60	MPSA05		2N1890	£0.45	2N3709	£0.07
AF117	£0.20			BD177	£0.68			2N1893	£0.30	2N3710	£0.07
AF118	£0.40	BC213	*£0.11	BD178	£0.68	MPSA06	*£0.20	2N2147	£0.75	2N3711	£0.07
AF124	£0.30	BC213L		BD179	£0.75			2N2148	£0.70	2N3712	£0.07
AF125	£0.30			BD201/202MP		MPSA55	*£0.20	2N2160	£0.80	2N3819	£0.20
AF126	£0.30	BC214	*£0.12			MPSA56	*£0.20	2N2192	£0.38	2N3820	£0.40
AF127	£0.32	BC214L		BD203	£0.80			2N2193	£0.38	2N3821	£0.60
AF139	£0.58			BD204	£0.80	OC22	£1.50	2N2194	£0.38	2N3823	£0.40
AF180	£0.58	BC237	*£0.16	BD203/204MP		OC23	£1.50	2N2217	£0.22	2N4058	*£0.12
AF181	£0.58	BC238	*£0.16	BDY20	£0.80	OC24	£1.40	2N2218	£0.22	2N4059	*£0.14
AF186	£0.58	BC251	*£0.15	BDX77	£0.90	OC25	£0.60	2N2218A		2N4060	*£0.14
AF239	£0.38	BC251A		BF457	£0.37	OC26	£0.60			2N4061	*£0.12
AL102	£0.95			BF458	£0.37	OC28	£0.90	2N2219	£0.20	2N4062	*£0.12
AL103	£0.95	BC301	*£0.30	BF459	£0.38	OC29	£1.00	2N2219A		2N4284	*£0.18
AU104	£1.00	BC302	*£0.28	BF594	*£0.15	OC35	£0.90			2N4285	*£0.18
AU110	£1.00	BC303	*£0.32	BF599	*£0.15	OC36	£0.90	2N2904	£0.18	2N4286	*£0.18
AU113	£1.00	BC304	*£0.38	BF599	*£0.15	OC70	£0.15	2N2904A		2N4287	*£0.18
BC107A	£0.08	BC327	*£0.16	BFR40	*£0.25	OC71	£0.15			2N4288	*£0.18
BC107B	£0.08	BC328	*£0.15	BFR79	*£0.28	TIC44	*£0.29	2N2905	£0.21	2N4289	*£0.18
BC107C	£0.08	BC337	*£0.15	BFR79	*£0.28	TIC45	*£0.29	2N2905A	£0.21	2N4290	*£0.18
BC108A	£0.08	BC338	*£0.15	BFX29	*£0.25	TIP29A	£0.44			2N4291	*£0.18
BC108B	£0.08	BC440	*£0.30	BFX30	£0.30	TIP29B	£0.52	2N2906	£0.16	2N4292	*£0.18
BC108C	£0.08	BC441	*£0.30								

74 SERIES TTL ICs

FULL SPECIFICATION GUARANTEED. ALL FAMOUS MANUFACTURERS

Type	Price	Type	Price	Type	Price	Type	Price	Type	Price	Type	Price
7400	£0.14	7409	£0.15	7441	£0.64	7482	£0.85	7493	£0.40	74122	£0.50
7401	£0.14	7410	£0.14	7442	£0.64	7483	£0.95	7494	£0.88	74123	£0.70
7402	£0.15	7411	£0.23	7445	£0.90	7484	£0.98	7495	£0.75	74141	£0.80
7403	£0.15	7412	£0.23	7446	£0.90	7485	£1.20	7496	£0.80	74154	£1.30
7404	£0.15	7413	£0.27	7447	£0.78	7488	£0.30	74100	£1.00	74180	£1.10
7405	£0.15	7414	£0.58	7448	£0.80	7489	£2.90	74110	£0.50	74181	£2.00
7406	£0.30	7416	£0.28	7475	£0.48	7490	£0.42	74118	£0.90	74190	£1.50
7407	£0.30	7417	£0.28	7480	£0.50	7491	£0.75	74119	£1.85	74198	£2.00
7408	£0.15	7440	£0.15	7481	£0.95	7492	£0.45	74121	£0.30	74199	£1.90

CMOS ICs

Type	Price										
CD4000	£0.14	CD4012	£0.18	CD4022	£0.95	CD4031	£2.20	CD4046	£1.30	CD4071	£0.28
CD4001	£0.18	CD4013	£0.50	CD4023	£0.16	CD4035	£1.05	CD4047	£1.10	CD4072	£0.28
CD4002	£0.18	CD4015	£0.90	CD4024	£0.72	CD4037	£0.95	CD4049	£0.55	CD4081	£0.18
CD4006	£0.98	CD4016	£0.50	CD4025	£0.98	CD4040	£0.95	CD4050	£0.55	CD4082	£0.28
CD4007	£0.18										

Something for nothing

A GREAT deal has been written in the last few years on major undertakings such as the building of the supersonic Concorde and the American space programme. While our spending on Concorde is trivial compared to the untold millions of dollars spent on space research nevertheless the lesson seems to be that we earthlings can achieve almost anything given nearly unlimited funds. But where do we draw the line? And who is going to draw it for us? Who is there big enough to say "No" to a particular project because it will mean an intolerable burden on the taxpayer? Only now is money in reasonable amounts being allocated to research on solar energy problems. It may not be too little but it may be too late!

If this matter had been tackled 20 years or so ago we might not be so beholden to overseas countries for our oil supplies. Next time you pop down the road in your car to see Auntie Flo just think about how that petrol you are using got into the tank. Someone drilled a hole in the earth, took out tons and tons of horrible, gooey, slimy sludge, put it into a boat and sent it to our shores where it was put through a complicated process of refining, adding this and that chemical, then put it back into the ground in a tank until you came along with your hard-earned lolly and bought a couple of gallons. But what did you do with it, when you had got it??? You burnt it! You sent out clouds of poisonous fumes into the air for the rest of us to breathe. Just to go to Auntie Flo's! You could have walked, anyway.

But seriously, it is all rather daft, isn't it, when there is that great ball of fire in the sky that pours more energy on to our Earth than we can ever hope to use, and all for free, relatively speaking. The Japanese, and possibly others, are already producing solar "cells" in strip form. Soon we will be able, with a bit of luck, to decide how many kilowatts of energy we need for our house and then pop out and buy the necessary length of strip from the local DIY shop! All those nasty bills that arrive each month from the electricity, coal and gas bods would disappear! Think of the money we'd save and all the nice new hi-fi gear you could buy, or that transceiver you've always wanted. All those nice people who prepared those nasty bills could do something really useful, for a change. Like building a barrage across the River Severn and taking advantage of the free energy to be got from the roaring tide.

But in the past, whatever the bonanza, be it oil or butter, the ordinary man-in-the-street never seemed to benefit from them in the form he can best appreciate—lower prices. As soon as something is given with one hand it is snatched away by another. Is it too much to hope that things might be different with solar energy when it becomes an everyday source of power?

Amateur experimenters could lead the way, as they have done in the past, by designing electronic projects using the sun as a primary source of power. Radio amateurs are already employing microwaves in the region of 10GHz (10,000MHz) for communication over quite respectable ranges, using only milliwatts of power, which could be derived from solar cells. Secondary batteries charged from the sun could provide a continuous source of power but at the moment our methods of converting solar energy are pretty crude.

No doubt space scientists have one or two useful practical ideas up their sleeves which could be adapted for use in our field of interest so we must keep our ears and eyes open. In due time it ought to be a matter of principle that we do not obtain any of our power requirements, for electronic equipment at least, from the public mains supply.

Eric Dowdeswell Assistant Editor

NEWS...

Atten-TION!

THE RNARS will be holding their annual mobile rally at HMS Mercury on Sunday, June 19th, 1977, from 1100 onwards. The site is situated on the South Downs between the villages of Clanfield and East Meon and signs are to be seen along the A3 south of Petersfield and on the A272 west of Petersfield.

In addition to trade stands for amateurs, there will be arena events from 1400 onwards, with displays by the Cowplain NTC Band, Petersfield Aero Club flying display (weather permitting), volunteer Boy Cadet Corps field gun display and a display by Kelly Squadron of HMS Mercury. A static show will be given of pre-1963 racing cars.

Refreshments will be available on site and a grand raffle will take place with the draw being made about 1530. Talk-in facilities on 2m via GB3SN, 4m and 80m (3660kHz). People are most welcome to picnic on the site, so why not make it a family day out, taking in the wonderful Hampshire scenery as well as the RNARS mobile rally.

Further details from *M. Puttick G3LIK, 21 Sandyfield Crescent, Cowplain, Portsmouth, Hants PO8 8SQ.*

Sounds tough

A NEW syllabus has been prepared for the Radio Amateurs Examination, which sets out the new Home Office requirements. It also indicates the number of questions likely to be asked on each group of topics. The first examination of this new type will be in May/June 1979, while the last in the present series will be in December 1978.

The papers will take a multiple choice format and will comprise a 1-hour Licensing Conditions and Transmitter Interference paper (765-1-01), and a 1¾-hour Operating Practice, Procedures and Theory paper (765-1-02). Both papers will be taken on the same day with a short break in be-

tween. Certificates will be issued to successful candidates of both papers, although if only one paper were failed, the candidate would be required to retake only this one at a later date, to qualify for a full certificate.

Copies of the new syllabus, together with specimen questions, will be available from the Sales Section from July 1977, price 40p.

City and Guilds of London Institute, 76 Portland Place, London WIN 4AA.

Free advice

OVER the past few months a new type of shop has sprung up in the High Streets which offer equipment and advice to the general public, that previously had only been available to professional customers.

The shops—Electronic and Time Centres, are run by a group of professional Electronics Engineers and offer electronic digital clocks, treasure tracers, TV games, electronic car ignition systems, as well as a large range of Swiss and American LED and LCD quartz watches, DIY kits and spare parts. All products are guaranteed, as

is the promise that if any orders are received by post before 2pm, dispatch will take place that same day. There are two shops open at present, one in Daventry High Street and the other in Uxbridge High Street. Further shops are now being planned for Deal, High Wycombe and Northampton.

Metac International, 16 Nightingale Close, Hazelmere, Bucks.

Show time

THE Birmingham International Ideal Homes Show is due to open at the National Exhibition Centre on Thursday, August 4th, and run through until Saturday, August 20th (excluding Sundays).

There will be hundreds of stands where some of the leading British manufacturers and retailers and many from overseas, will be displaying some of the latest goods for the home. Apart from these stands there will be a full programme of holiday features, fashion parades, cookery demonstrations, musical events, games and competitions.

The show will be open from 10 am to 10 pm. Any enquiries concerning the show should be

addressed to ITF and BPM Exhibitions Ltd. Radcliffe House, Blenheim Court, Solihull, West Midlands. Tel: 021-705 6707.

Jubilee callsigns

THE use of a special prefix GE for UK amateurs has been approved and will be effective from 4 June to 12 June inclusive ONLY. The facility is available to Class 'A' and 'B' licensees. For example, G4AR can use GE4AR, G8XYZ becomes GE8XYZ, GW4ZZZ uses GE4ZZZ. Although this means that the individual countries of the UK lose their identities for a brief period, to the chagrin of the prefix hunters, I suppose one could always add /GW etc!

Castle rally

THE 8th Elvaston Castle Mobile Radio Rally is scheduled to be held in the grounds of the castle on Sunday, the 12th June. The castle is located on the B5010, about 5 miles south-east of Derby.

Opening at 11 a.m., there will be a talk-in by G8KGC/P on 2m, G3EEO on 160m and G3ZBI/P will be on the air as an exhibition station from the site. To please the rest of the family, the organisers have arranged for a bring-and-buy stall, prize draw, refreshments, sideshows and childrens entertainments. An added attraction will be the presence of the EMI Tape hot air balloon. Entrance is free, although there is a car parking fee of 25p.

Any further information from Ian Cage G4CTZ, Nunsfield House, Boulton Lane, Alvaston, Derby DE2 0FD.

BACK NUMBER SERVICE

We are very glad to announce the re-establishment of a PW Back Numbers Service for our readers. In future back numbers dated from June 1977 only will be available from our Post Sales Department for 65p, which includes postage and packing. Cheques and Postal Orders should be made payable to IPC Magazines Ltd.

Send your orders to:—Post Sales Department, IPC Magazines Ltd., Lavington House, 25 Lavington Street, London SE1 0PF.

R T-Vc have asked us to correct some pricing errors that occurred in their advertisement on page 5 of the May 1977 issue of PW. The correct prices are:—


Sinclair IC20/PZ20 kit, £5.95.
Speakers, DuoIII, pair, £52.
Turntable, BSR MP60, £29.
Portable Disco Console, £64.

20W IC AUDIO AMPLIFIER

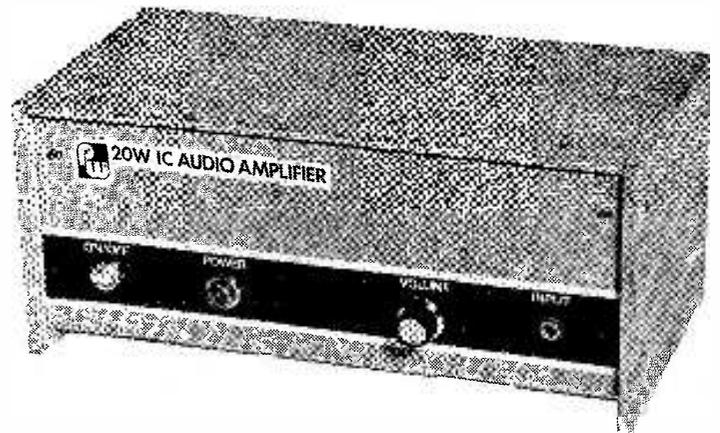F. G. RAYER G3OGR

THIS amplifier uses a single high power integrated circuit; the power supply is included for direct operation from the mains. Maximum output is up to 20W into a 4Ω speaker, or about 13.5W into an 8Ω speaker.

The use of an IC greatly simplifies construction of the amplifier section of the equipment, and comparatively few other components are necessary here. The IC features internal protection, so that no damage arises if the output (speaker) circuit is shorted. It also incorporates thermal protection. This is a valuable feature, since it avoids thermal runaway when dissipating excess power in relation to the heat sinking used. High temperatures cause the IC to shut down with normal working restored when the temperature has fallen.



CIRCUIT

Fig. 1 shows the complete circuit using the TDA2020. VR1 is the gain or volume control, and coupling is by C1 to the input pin 7. Negative feedback from the output pin 14 is by R3 to the inverting input 8, feedback also being set by R2 and C2. C3 is a frequency-compensation capacitor.

IC1 needs no speaker coupling capacitor but requires bipolar supply lines. The power supply makes provision for this.

The amplifier is assembled on its own printed circuit board which also carries the heat sink.

The mains transformer T1 has a 12-0-12V secondary; the centre tap provides the chassis line. Two of the rectifiers, with C8, give the positive supply for pin 1 of the IC. The remaining two rectifiers, with C9, produce the negative line supply for pins 3 and 5 of the IC. R6, C7 and R5 provide an auxiliary positive supply of about 12-14V for a pre-amplifier or suitable radio tuner although these may be left out if not required. C5 and C6 are HF by-pass capacitors fitted near to the IC.

The rectifiers, R5, R6, C7, C8 and C9 are assembled on a piece of tagboard adjacent to T1. R7 and the neon comprise an indicator. If a panel neon with resistor included is used, R7 will not be necessary.

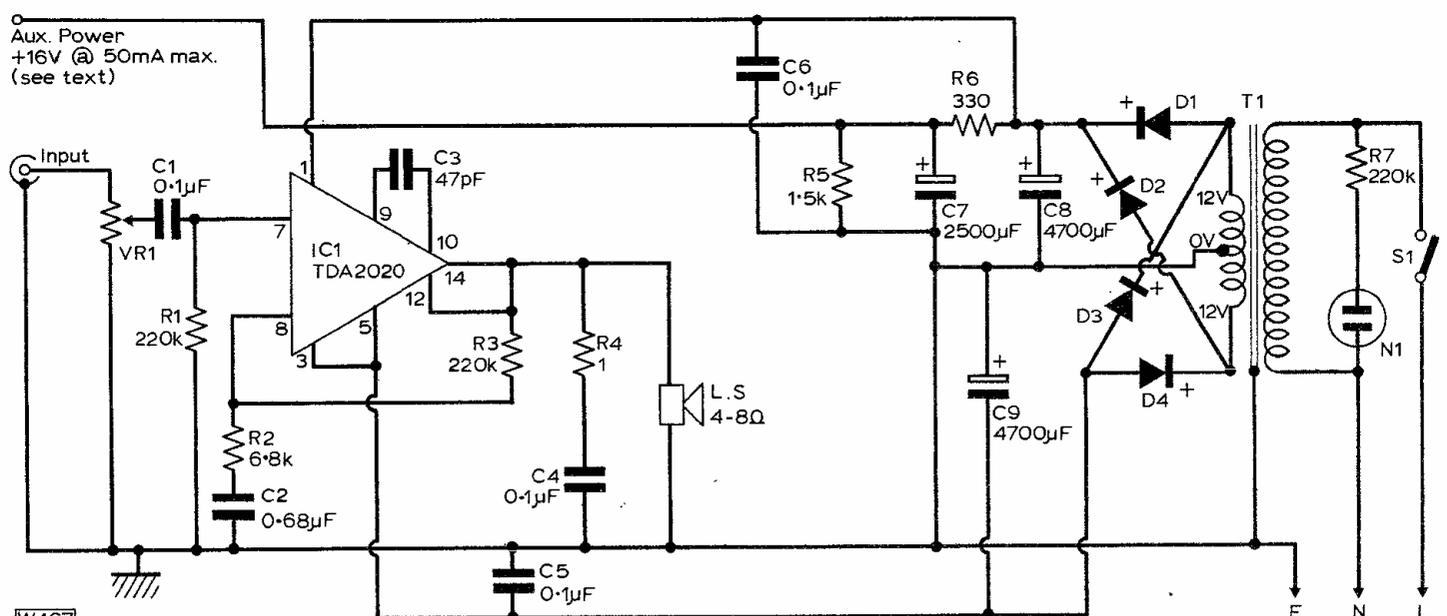


Fig. 1: Circuit diagram of amplifier and power supply. R5, R6 and C7 may be omitted (see text).

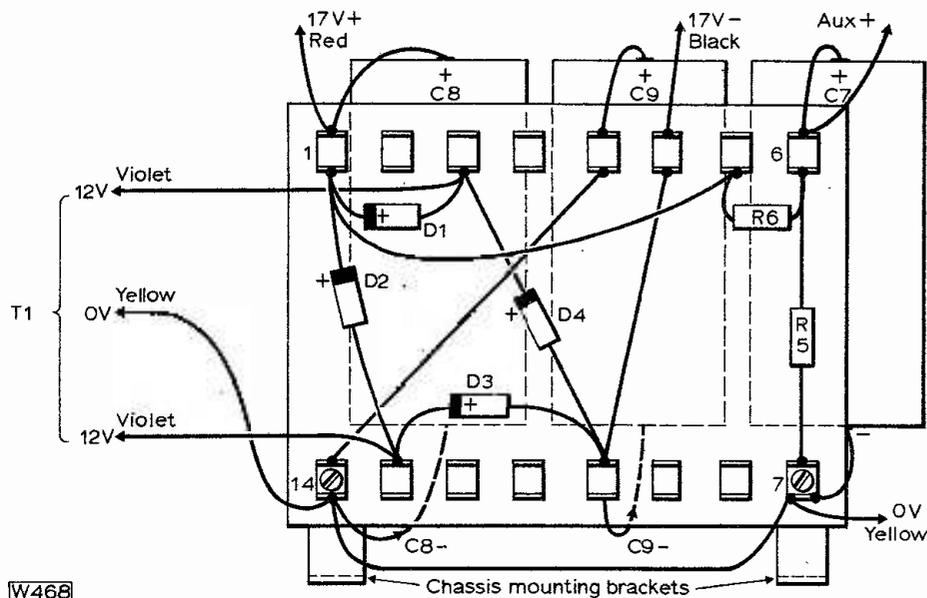


Fig. 2: Power supply tagboard layout. If tagboard cannot be obtained, the circuit may be constructed using a standard matrix pin board and printed circuit pins in which case the layout can remain the same. Alternatively, veroboard may be used with suitable rearrangement of components. C7, R6 and R5 may be left out if an auxiliary power supply (to drive a pre-amplifier or tuner, etc) is not required

W468

Fig. 2 shows wiring of the tagboard. Colour coding of the leads will be helpful here. Violet was used for the 12V leads for T1; with yellow for the centre-tap, chassis, and 0V amplifier line. Red is used for 17V positive and black for 17V negative supply.


The capacitors may be of the type with two tags one end. Two brackets mount the board vertically. These were fixed by 6BA bolts through the tags which must also be in contact with the chassis and act as earth returns and anchor points for C7 and C8. The capacitors can be held by fastening string round them looping this through holes in the board, as well as by their connections. As an alternative the power supply card may be constructed from veroboard if tagboards aren't to hand. Flexible leads run from the points shown to the amplifier board. These can be unsoldered at top tags 1 and 6 if it is wished to check current as mentioned.

The transformer fits to the left of the tagboard. Use a 3-core cord, and plug with 2A or other low rating fuse. The chassis should be earthed (Fig. 1). L and N mains conductors go to the transformer primary, with the switch in the L circuit.

POWER OUTPUT

There is latitude in both the speaker load and supply voltages when maximum power is not required. The circuit given in Fig. 1 was found to provide 17.0-17V, and with this up to 20W can be obtained with a 4Ω speaker. With 12.0-12V, output is 11.5W, rising to 15W with 14.0-14V, and 18.5W with 16.0-16V. For 8Ω speakers, ratings are 7W for 12.0-12V, 9.5W for 14.0-14V, 12W for 16.0-16V, and 13.5W for the 17.0-17V supply. The maximum supply is 20.0-20V, but this is not recommended as the IC may be damaged if higher voltages should arise, and power output is not a great deal more than with the 17.0-17V supply.

For high output while leaving some latitude for safety, the 12.0-12V rms secondary is probably best. A check across C8 and C9 should be made, and each reading should not be more than about 18V, with no signal. The tag-board is arranged so that a meter may, if wished, be placed in series with positive or negative supply lines, for an initial test; the current drawn will peak up to about 1A in each case.

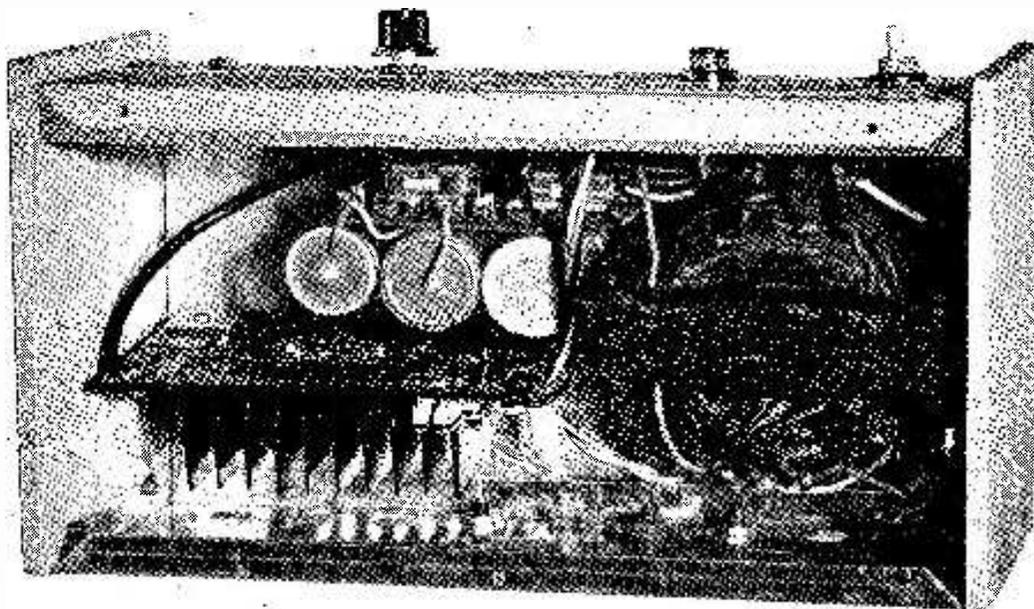

Plan view of prototype amplifier showing mains transformer (right) amplifier board/heatsink assembly and power supply tagboard. The actual layout used will depend to a large extent on the size and shape of the mains transformer used (see section of text headed POWER OUTPUT).

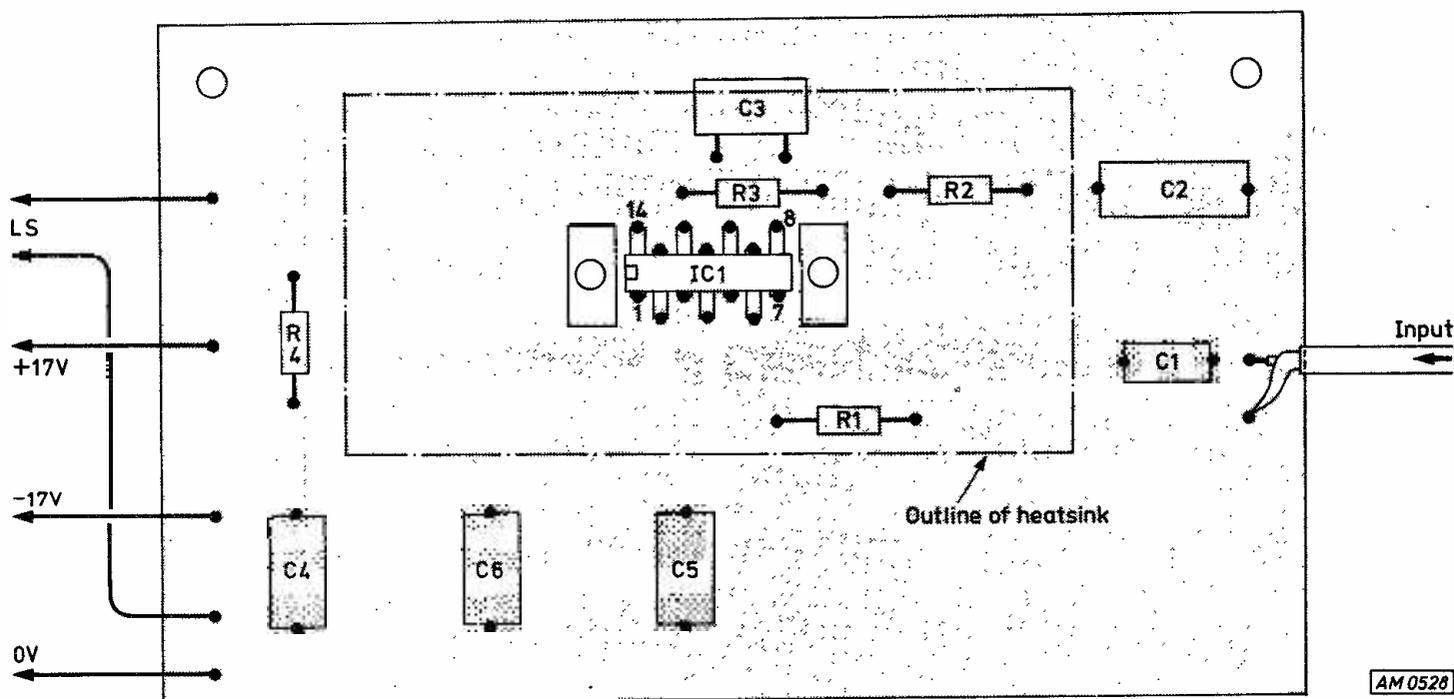
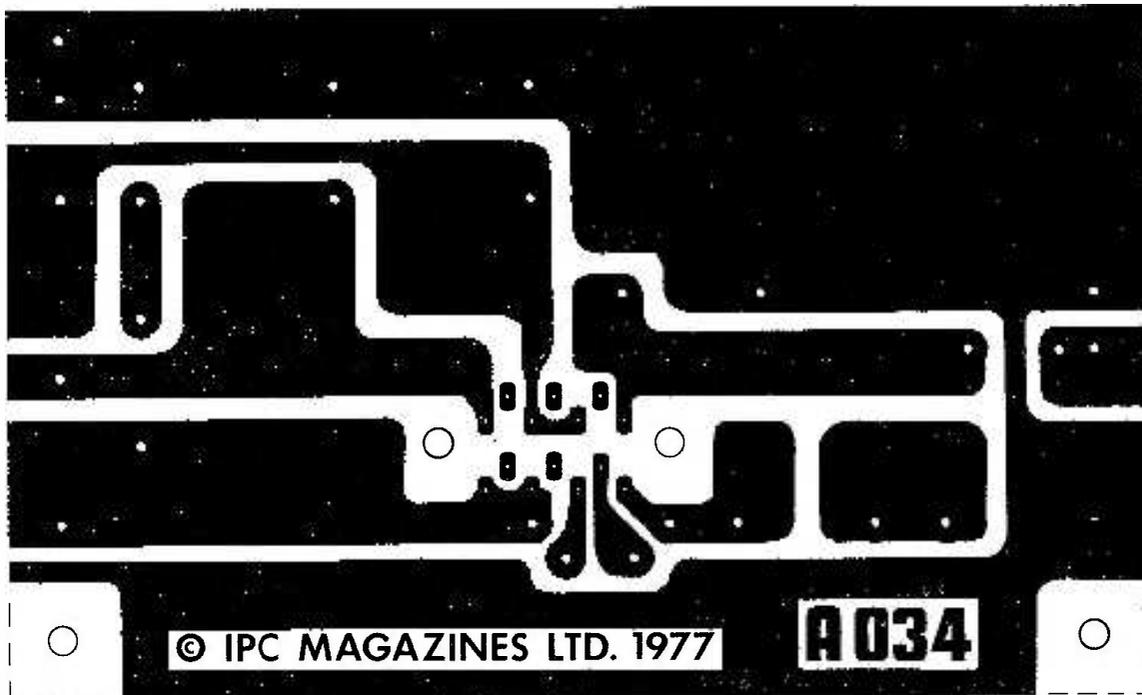


Fig. 3: (above) PCB copper side to actual size. Component side (lower) showing positions. During assembly of the board, care should be taken to ensure that components underneath the heatsink do not foul it in any way—the heatsink is electrically in contact with the substrate of the IC via the copper slug on the top of the IC.


Input is via a screened lead, which runs to C1 and the PCB 0V line, as shown in Fig. 3. Flexible leads are soldered on for the speaker connections. Also holes should be drilled so that the red, yellow and black power supply leads can be soldered to the appropriate foils as per Fig. 3.

The heat sink is 80 x 40 x 30 mm and its thermal rating is 2.75°C/W, for 20W operation. A smaller sink is available for 12W maximum. It has threaded holes to take two 6BA bolts. If other sinks are improvised, they should be of quite generous size. If the IC thermal cut-out operates, it indicates that the amplifier must be run at a lower power level, or the sink must be improved.

The IC has a mounting spacer which fits underneath it. Semiconductor mounting compound must be spread on top of the IC before fitting the sink. Be certain that the holding screws do not touch adjacent foils; insulating washers may be put under their heads if needed. The sink must not touch the

AMPLIFIER BOARD

Fig. 3 shows the underside of this, and the positions of components. The board is relatively simple, and was made from Print-A-Kit adhesive foil, but can be prepared in the usual way and etched. Alternatively, a board may be purchased from the PCB service—see p 190. It is important to note that C3 and the resistors lie under the sink, so that they may be near the IC, but that the other capacitors must be outside the area occupied by the sink.

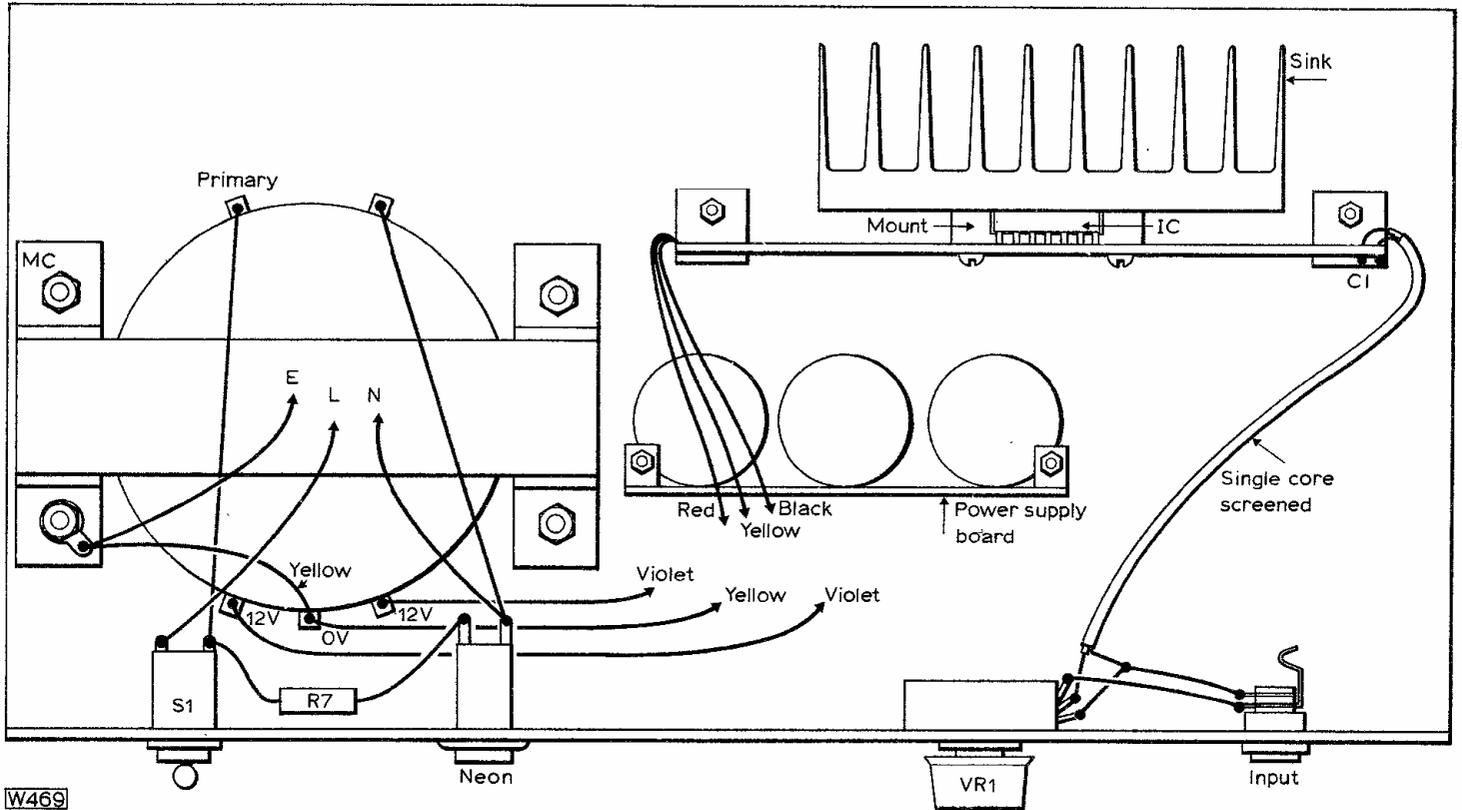

W469

Fig. 4: Detailed wiring and assembly of the amplifier. Particular attention should be paid to the mains wiring; the live tags on S1 and the panel neon are depicted unhealthily near the 12V secondary of the mains transformer. The latter should be shown slightly further back from the front panel.

case or any other metal items. Two brackets hold the board vertically, and in this position the sink fins are also vertical.

★ components list

Capacitors

- C1 0.1 μ F
- C2 0.68 μ F
- C3 47pF
- C4 0.1 μ F
- C5 0.1 μ F
- C6 0.1 μ F
- C7 2500 μ F 15v may be omitted—see text.
- C8 4700 μ F 25v
- C9 4700 μ F 25v

Resistors

- R1 220k Ω
- R2 6.8k Ω
- R3 220k Ω
- R4 1 Ω
- R5 1.5k Ω
- R6 330 Ω
- R7 220k Ω (see text). All resistors 5% 1/4W.
- VR1 10k Ω log pot

Semiconductors

- IC1 TDA2020
- D1 to D4 1N4001


Miscellaneous

- T1 12-0-12V 2A mains transformer. Indicator neon, on-off switch, 3.5mm jack socket, knob tagboard. Speaker sockets, etc. Heatsink: 3-15 E.18. Chromasonic Electronics.

ASSEMBLY

Fig. 4 shows how the transformer, tagboard and amplifier are fitted and interconnected. The yellow or 0V line is continued from the mains earth tag to transformer, capacitor assembly, and amplifier, so that reliance is not placed on chassis earth returns.

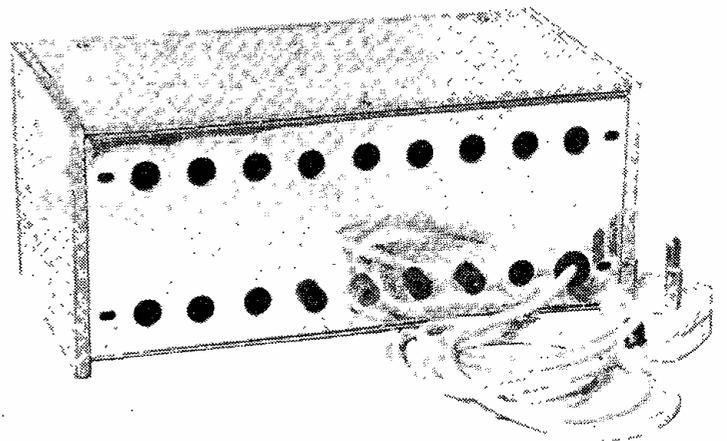It is convenient to use a metal panel and bottom, but it is not essential to have metal sides, top or



back. The least expensive assembly is to use a 25 x 10 cm (10 x 4") flanged "universal chassis" for the front, with a flat plate about 25 x 12.5 cm (10 x 5") for the bottom. The whole unit can then be completed as in Fig. 4. Subsequently, top, sides and back can be added. Appearances can be improved by making the sides of wood, large enough to give a front and bottom projection of about 1 cm ($\frac{3}{8}$ "). A number of holes, or a slot or cut-out, must be arranged near the heat sink, to allow air circulation. The back should also be fitted with sockets for the speaker, and for the 12-14V positive supply outlet, including a chassis return. Dw

Measuring with OP AMPS

A. SHARPE

AN operational amplifier is so called because it can perform specific mathematical operations such as multiplication and division; the actual parameters of the operating mode are entirely dictated by the choice of external components in the feedback loop. In the following circuits the op. amp is shown in the multiplying mode. The differential op. amp usually makes a better DC amplifier than the equivalent single ended version. To explain the reasons for this, it requires some comprehension of DC amplifier theory.

Single end

Fig. 1 shows the basic single ended circuit. It exhibits two major deficiencies: the first is that the output voltage is offset to the input voltage by a fixed value equal to the normal collector base voltage; further the collector can swing only marginally below the base.

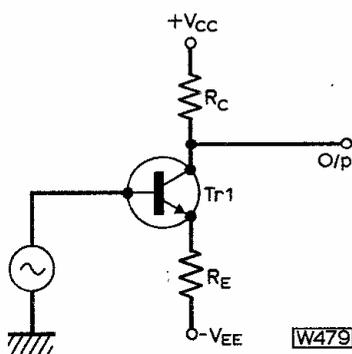


Fig. 1: A national representation of a single ended DC amplifier. It is unbalanced in every respect.

Second objection concerns the base emitter voltage which will be typically about 0.6V for a silicon transistor. The exact voltage depends on the junction temperature. Since the base emitter junction constitutes the input circuit any error in this department will be magnified by a factor proportional to the amplifier gain. In the circuit shown this relates to the ratio between R_c and R_e . For instance if $R_c=10k\Omega$ and $R_e=1k\Omega$ then the gain will be 10 providing one neglects the internal emitter resistance of the transistor. In practice, this invisible resistance would reduce the stage gain to slightly less than 10. By the same token, if the base emitter voltage changed by a hypothetical 3 units per C° then the output would change by slightly under 30 units.

Long tailed pair

Adding a further transistor produces the well known "long tailed pair" circuit shown in Fig. 2. In this

case, R_e no longer controls the amplifier gain: it simply serves to provide both transistors with current which will usually be split equally between the two.

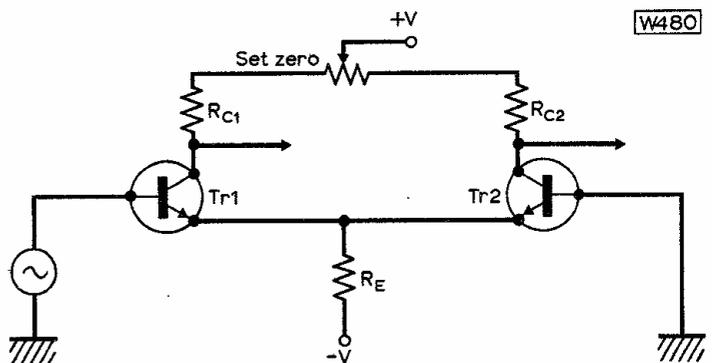


Fig. 2: Long tailed pair. The circuit primarily responds to signals applied differentially between the bases of Tr1 and 2.


The real R_e is the other transistor; the emitter output impedance of each transistor presents the emitter load to the other since both emitters are connected together. If the R_e shown in Fig. 2 were replaced by a constant current source, then the amplifier would only respond to a differing voltage between Tr1 and Tr2 bases. A voltage common to both has no effect on either output since the supply current remains equally split between the two. However if one input is held at earth potential and the other is varied, then the supply current will vary unequally between the pair although the total value will remain the same. This will result in differing voltage drops across the collector resistors.

For instance, suppose that an input signal caused a current of $10\mu A$ to flow in the base circuit of Tr1 but not Tr2. Assume that both transistors have a gain of 100. Then the emitter current of Tr1 will be 1mA higher than Tr2. Since both transistors are supplied by a source of constant current, then Tr2 will have to pass 1mA less if Tr1 is passing 1mA more. The current difference will be reflected in the voltage drops across the collector resistances: if $R_{c1}=R_{c2}=10k\Omega$ then the drop will be an extra 10V across R_{c1} and 10V less across R_{c2} , a difference of 20V total between the two collectors.

Provided that both transistors of the pair are maintained at identical temperatures then temperature error signals will be common mode (applied equally to each base) and thus not appear in the output. Integrated circuits enable easy fabrication of thermally and electrically matched long tail transistors. However the simple circuit of Fig. 2 requires a few more components to back off the standing output voltage and enable output swings below the input voltage.

The true op. amp.

Fig. 3 shows how the addition of a further transistor may be used to back off the output voltage while retaining all the benefits of a differential input. Note that, although only one collector load resistor has been used, the current is still equally split between the input pair in the quiescent state. The value of R1 is chosen so that the current flowing in the collector circuit of Tr1 produces a voltage drop across R1 proportionate to the base emitter voltage of Tr3, i.e. about 0.6V. This means that Tr3 just conducts producing an output voltage across R2. As with the last example, the amplifier will only produce an output signal in response to a differential input signal between Tr1 and Tr2. Further the output can swing from supply rail to supply rail without any fixed reference to the common mode (common to each) input voltage on Tr1 and 2.

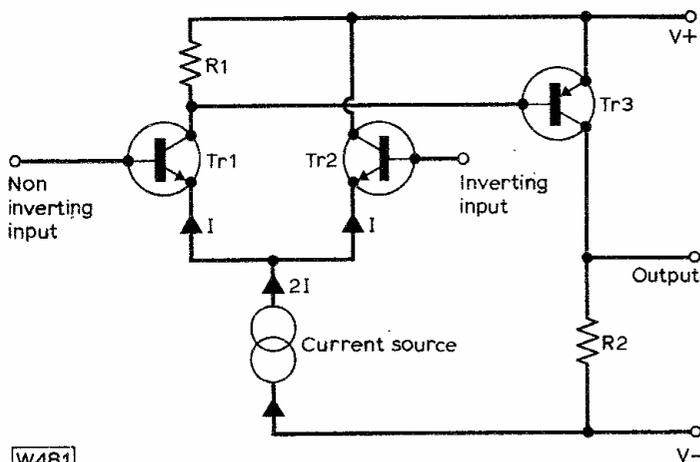

W481


Fig. 3: This circuit has all the requirements for an operational amplifier. Principally, the output can swing below the common mode input voltage.

Whereas the gain of the single sided circuit shown in Fig. 1 could be adjusted by varying the ratio of collector to emitter resistance, that cannot be done with the circuit shown in Fig. 3. The latter, having a fixed gain of over 10,000 (80dB), relies totally on the way it is connected to external components to control this parameter—a true operational amplifier.

Operational modes

The classic circuit configurations to obtain controlled gain are shown in Fig. 4. The circuit block

Fig. 4: Controlling gain in (a) the non inverting (b) the inverting and (c) the differential mode.

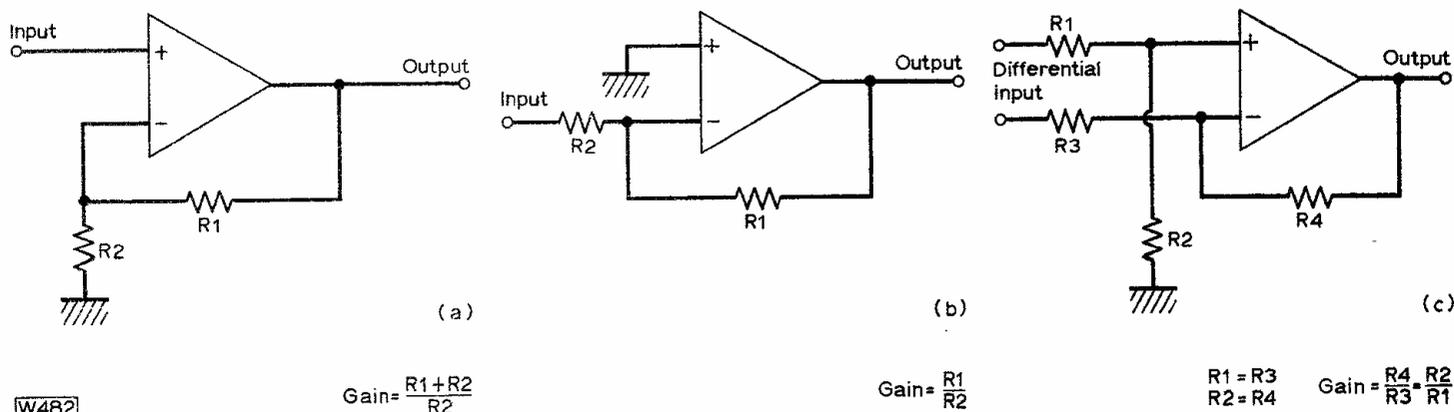

W482

of Fig. 3 has been replaced by the well known op. amp symbol. In the non-inverting mode (drawing A) the output is in phase with the input. If R1 and R2 were equal, the amplifier would exhibit a voltage gain of 2. For unity gain in the non-inverting mode, the inverting terminal of the op. amp must be connected directly to the output terminal; this arrangement is known as a voltage follower since the output signal precisely follows the input signal. However the output is at a very low impedance, a factor which usually provides the motive for implementing such a circuit.

Fig. 4(B) shows the inverting mode connection. The input impedance will approximate to the value of R2. The input and output waveforms will be out of phase by 180°. In this connection, the op. amp inverting terminal acts rather like a mechanical fulcrum of a see-saw—when one end goes up, the other comes down. Further, the gain of the circuit can be likened to the mechanical advantage obtained with a lever system; in this case, the value of the circuit resistors are analogous to the lever lengths. Because of the gain in the op. amp, very little signal is present at the inverting terminal—the output always tries to counteract the effect of the signal—hence this is known as a virtual earth point.

Fig. 4(C) is a combination of A and B circuits. This arrangement gives a true differential input, i.e. rejecting voltages which are common to both inputs, by maintaining the relationship $R2/R1 = R4/R3$. This ensures that a common mode signal will raise both the inverting and non-inverting inputs to the same level. This circuit is used extensively in electro-medicine where very small skin differential potentials need to be measured in the presence of high level mains hum and other interference.

An op. amp millivoltmeter

Fig. 5 shows a typical DC application of the well known op. amp 741 integrated circuit: a high impedance DC voltmeter. The op. amp works in the voltage follower mode in such a way as to render the resistance of the meter movement totally non-critical.

Resistors R4 to R9 provide the switchable top section of a resistive divider; R2 forms the bottom half having one end connected to earth and the other connected to the top half. The junction voltage is applied via R3 to the non-inverting terminal of the IC. Resistor R3 and diodes D1 to D4 simply serve to protect the input of the IC and the meter movement; they do not contribute in any part to the normal operation of the circuit.

S-DeCnology

DAVID GIBSON

8



THIS MONTH



Ultra Simple Audio Amplifier

THIS month's S-DeCnology project is an audio amplifier which should prove useful as an add-on unit to last month's two-transistor radio receiver. The amplifier performs efficiently from only 3V, the voltage used with the receiver.

Fig. 1 shows the complete circuit. It uses the absolute minimum number of components; excluding the microphone and loudspeaker only three transistors, one resistor and one capacitor are used. The circuit comprises three transistors wired as a Darlington triple, a configuration which exhibits a very high gain. The actual gain is a product of the gains of the individual transistors. The base of Tr1 is biased by a 2M Ω resistor R1 which also provides DC stabilisation. Input is via capacitor C1.

The circuit works very well with a crystal microphone plugged into S-Dec holes 41 and 66. The loudspeaker used in the prototype was a 75 Ω 63mm component—a larger size speaker would give more

volume. Note that the loudspeaker must be 75 to 80 Ω : lower values (such as 3, 8 or 16 Ω) should not be used.

Construction

Building the amplifier on S-Dec should present no problems—the prototype was "rebuilt" in less than 90s once circuit and values had been settled! When inserting the transistors, note that the leads are not in the sequence: emitter, base, collector (except for Tr3). This is made clear in the S-Dec layout diagram of Fig. 2.

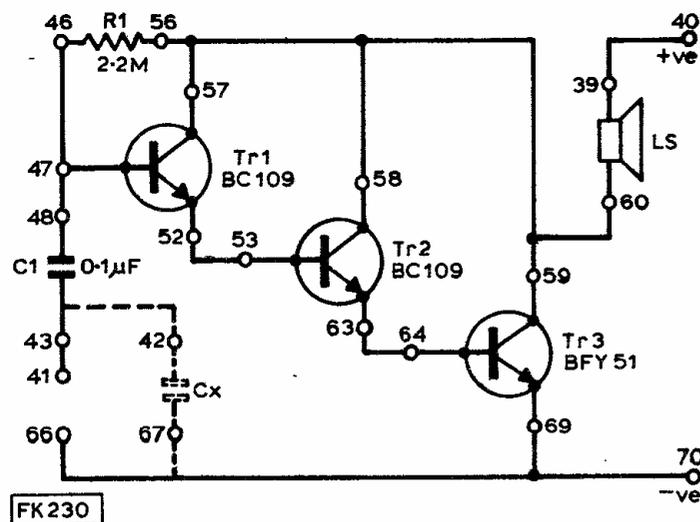


Fig. 1: Circuit diagram. Cx provides bypass for RF when used with last month's radio receiver. See section 'Radio amplifier'.

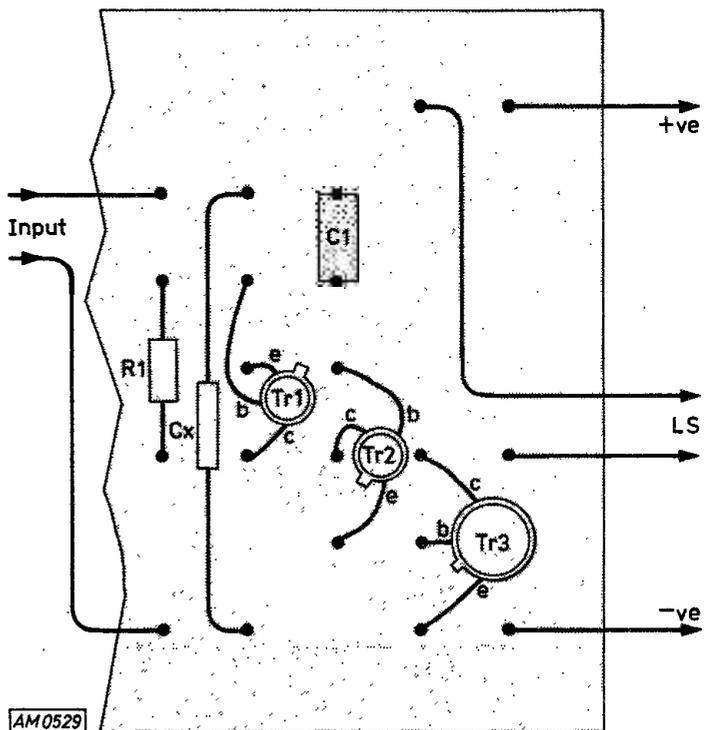


Fig. 2: Component layout. Note that Tr1 and 2 leadouts are plugged into the S-Dec out of order.

you will need

Tr1	BC109	R1	2.2M Ω
Tr2	BC109	C1	0.1 μ F
Tr3	BFY 51	LS1	75 or 80 Ω loudspeaker
One S-DeC, 3V battery, crystal microphone. Cx small value capacitor (see text).			

Supply voltage

Using a 3V battery, the amplifier draws some 16mA of current. At 4.5V, this rises to 26mA; at 6V the current drawn is around 50mA. The amplifier was left running on test where it was found that Tr3 became barely warm. If, however, the voltage was raised to 9V (current then about 86mA), Tr3 got warm quite quickly.

When used in conjunction with the radio receiver described last month, there will be ample volume at 3V. For greater sensitivity, a higher voltage may be used. In view of the experiments described above, it is suggested that 6V be considered the maximum unless intermittent operation is envisaged.

Radio amplifier

Connecting the amplifier to the S-Dec receiver presents no problems. Simply plug in a 4.7k Ω resistor in place of the earpiece on the receiver, and then connect the amplifier to the receiver as shown in Fig. 3. The circuit diagram of Fig. 1 shows a "phantom" capacitor Cx across the input (S-Dec holes 42 and 67). This prevents RF from the receiver blocking the sensitive AF amplifier. It need be used

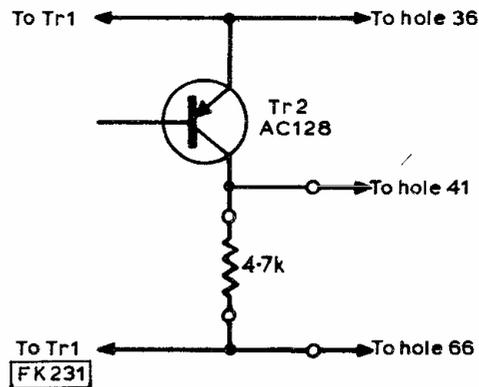


Fig. 3: Radio interface. In this drawing Tr1 and 2 refer to the transistors in last month's radio receiver.

only in this application. Its value should be between 350 and 500pF (390pF used in prototype).

Other applications

The unit can also be used as a simple record player amplifier providing the pick-up is a crystal type. A screened lead is a must here. In some applications such as this one a volume control might prove useful. For this, connect the slider of a 1M Ω potentiometer to hole 41. Connect the earth end of the pot to hole 66. The signal source is connected across the volume control.

As it stands, the unit might be used as an audio signal tracer. A 3V supply should be ample for this application. It might be prudent to connect a 0.1 μ F capacitor in series with the earth lead.

The S-Decology project for next month is another circuit which will work well from only 3V (it even functions on 1.5V). It has various applications but sufficient to say it could be used to play blind-mans bluff!

Pw

Measuring with Op. Amps.—continued from page 187.

Since the output impedance of the resistive divider is 10k Ω , any voltage measuring circuit connected to it must present an impedance many times higher than this. The voltage follower configuration of the IC typically offers an input impedance rather greater than 2M Ω and thus will not effect the voltage reading. The meter movement is connected between the output of the IC and the inverting input. A further resistor, R1, connects between the inverting terminal and earth.

The circuit shown does this by sending a current through the meter movement of exactly the right amplitude to equalise the voltage between inputs, even though this means passing extra current to counteract the effect of R1.

Since the input current to the amplifier is so small that it can be ignored, the sum total of the meter current is that which is required to reproduce the resistive divider output voltage across R1; in other words the voltage across R1 exactly mirrors that

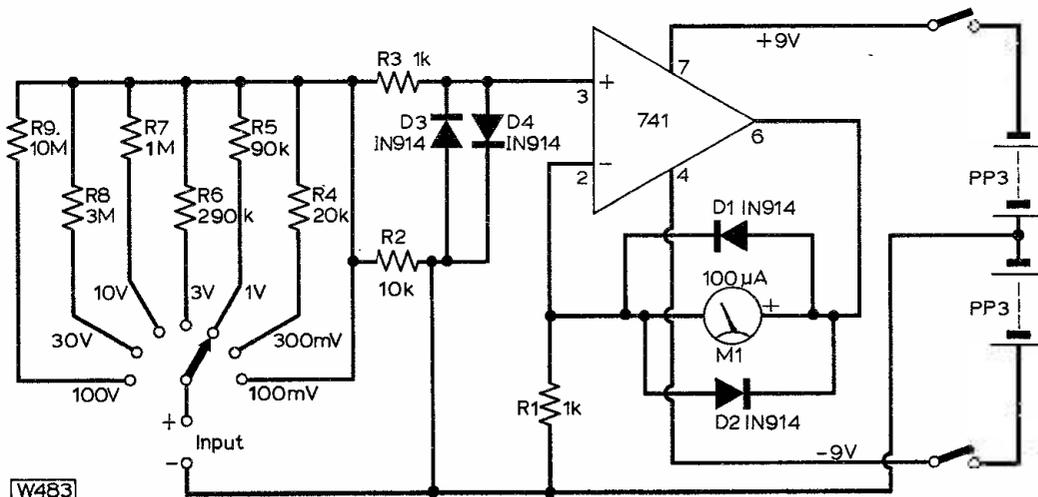


Fig. 5: Circuit diagram for a 100k Ω /Volt millivoltmeter. The diodes included in the circuit are purely intended for meter movement protection; they serve no normal operational function. Within very wide limits, the resistance of meter movement M1 has no bearing on the accuracy of the instrument. The actual sensitivity is controlled by R1; this component may be made variable for calibration purposes.

When an op. amp circuit uses negative feedback (i.e. with at least part of the output signal fed back in some manner to the inverting terminal) the actual output voltage will behave in such a way as to minimise and in most cases completely cancel out all voltages existing between the differential inputs.

across R2. This makes it very easy to work out the FSD voltage for the meter circuit. When R1=1k Ω then the voltage required to pass 100 μ A is 100mV. If the value of R1 were 500 Ω then the circuit FSD would be 100mV for a 200 μ A meter movement or 50mV for a 100 μ A meter.

Pw

PCB SERVICE FOR READERS

All boards, except SRBP, are glassfibre, drilled and roller-tinned

To:- READERS PCB SERVICES LTD, PO BOX 11, WORKSOP, NOTTS

Please supply PCB/s as indicated by tick/s in box/es

Issue	Project	Ref	Price P/P	
Dec 75	Sound-To-Light Display	DN0798	1.15+12	<input type="checkbox"/>
Dec 75	Disco System, Amp. (2 required)	each AM0421	4.40+22	<input type="checkbox"/>
Dec 75	Disco System, Light Modulator	AM0423	3.50+22	<input type="checkbox"/>
Mar 76	CMOS Crystal Calibrator	AM0438	1.19+12	<input type="checkbox"/>
Apr 76	Wobbulator	AM0443	1.08+12	<input type="checkbox"/>
Apr 76	Auto. Slide Synchroniser	AM0441	2.33+15	<input type="checkbox"/>
June 76	Dig. Freq. Meter (set of 5)	A015 and 4x A004	3.17+15	<input type="checkbox"/>
July 76	Transistor Tester	A002	3.08+18	<input type="checkbox"/>
July 76	Disco Preamplifier	A003	0.65+12	<input type="checkbox"/>
Aug 76	Cassette Player Power Supply	A001	0.65+12	<input type="checkbox"/>
Sep 76	Capacitance Meter	A009	2.59+14	<input type="checkbox"/>
Oct 76	Digital Car Clock (set)	A001/2/3	2.58+12	<input type="checkbox"/>
Oct 76	Interwipe	DN8JM	0.80+12	<input type="checkbox"/>
Oct 76	Video-Writer (set)	D002/3/4/6 A007	21.44+50	<input type="checkbox"/>
Oct 76	Hazard Flasher	D005	0.76+12	<input type="checkbox"/>
Nov 76	Low Level Battery Indicator	A016	0.40+12	<input type="checkbox"/>
Nov 76	Electronic Thermostat	A017	1.30+12	<input type="checkbox"/>
Nov 76	Cirtest Probe	A018	0.48+12	<input type="checkbox"/>
Nov 76	Burglar Alarm	A019	0.50+12	<input type="checkbox"/>
Dec 76	Chromachase	A021	5.70+22	<input type="checkbox"/>
Jan 77	Oscilloscope Calibrator	A023	1.25+12	<input type="checkbox"/>
Jan 77	Icelert	A020	1.45+12	<input type="checkbox"/>
Jan 77	Polyphon, motor and main boards	A025/4	7.90+20	<input type="checkbox"/>
	Polyphon, tune disc, blank, SRBP	A008*	0.90+15	<input type="checkbox"/>
Feb 77	Transistor Checker	A026	1.18+12	<input type="checkbox"/>
Mar 77	FM Stereo Touch Tuner	D023/4/5	7.50+20	<input type="checkbox"/>
Apr 77	Tug 'o' War (set)	A029/030	2.88+12	<input type="checkbox"/>
Apr 77	Gas/Smoke Sensor Alarm	A028	0.65+12	<input type="checkbox"/>
May 77	2-Way Intercom	D019	1.28+12	<input type="checkbox"/>
May 77	Protected Battery Charger	A027	2.38+12	<input type="checkbox"/>
May 77	Seekit Metal Locator	A031	3.38+12	<input type="checkbox"/>
June 77	Reverberation Amplifier	A032	2.38+12	<input type="checkbox"/>
June 77	Versatile AF Generator	A033	2.38+12	<input type="checkbox"/>
June 77	Tele-Games	D029	3.22+18	<input type="checkbox"/>
July 77	20W IC Amplifier	AO34	1.38+12	<input type="checkbox"/>
July 77	Radio 2 Tuner	AO35	1.68+12	<input type="checkbox"/>
July 77	Digital Clock Timer	AO36	3.28+12	<input type="checkbox"/>

Post and packing is for one board or set of boards. Prices include VAT
Remittances with overseas orders must be sufficient to cover despatch
by sea or air mail as required.

I enclose Postal Order/Cheque

ACCESS welcome.

No.....

Send card number only.


for £..... made payable to READERS PCB SERVICES LTD.

NAME.....

ADDRESS

Post Code

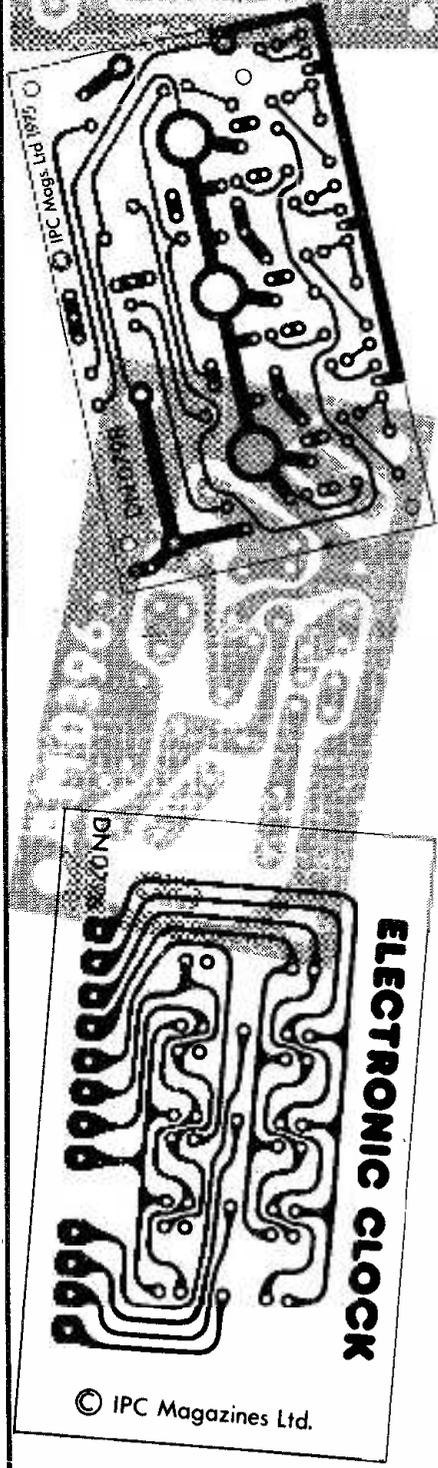Any correspondence concerning this service must be addressed to READERS
PCB SERVICES and not to the Editorial offices.



15-240 Watts!

HY5

Preamplifier

The HY5 is a mono hybrid amplifier ideally suited for all applications. All common input functions (mag Cartridge, tuner, etc) are catered for internally. The desired function is achieved either by a multi-way switch or direct connection to the appropriate pins. The internal volume and tone circuits merely require connecting to external potentiometers (not included). The HY5 is compatible with all I.L.P. power amplifiers and power supplies. To ease construction and mounting a P.C. connector is supplied with each pre-amplifier.

FEATURES: Complete pre-amplifier in single pack—Multi-function equalization—Low noise—Low distortion—High overload—Two simply combined for stereo.

APPLICATIONS: Hi-Fi—Mixers—Disco—Guitar and Organ—Public address

SPECIFICATIONS:


INPUTS. Magnetic Pick-up 3mV; Ceramic Pick-up 30mV; Tuner 100mV; Microphone 10mV; Auxiliary 3-100mV; Input impedance 4-7k Ω at 1kHz.

OUTPUTS. Tape 100mV; Main output 500mV R.M.S.

ACTIVE TONE CONTROLS. Treble \pm 12dB at 10kHz; Bass \pm at 100Hz.

DISTORTION. 0.1% at 1kHz. Signal/Noise Ratio 68dB.

OVERLOAD. 38dB on Magnetic Pick-up. SUPPLY VOLTAGE \pm 16-50V.

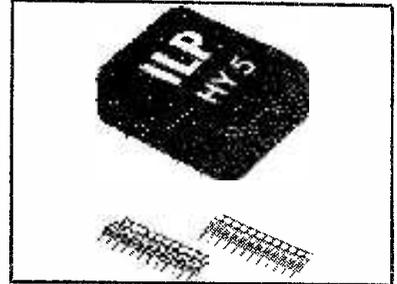

HY30

15 Watts into 8 Ω

The HY30 is an exciting New kit from I.L.P. It features a virtually indestructible I.C. with short circuit and thermal protection. The kit consists of I.C., heatsink, P.C. board, 4 resistors, 6 capacitors, mounting kit, together with easy to follow construction and operating instructions. This amplifier is ideally suited to the beginner in audio who wishes to use the most up-to-date technology available.

FEATURES: Complete Kit—Low Distortion—Short, Open and Thermal Protection—Easy to Build.

APPLICATIONS: Updating audio equipment—Guitar practice amplifier—Test amplifier—audio oscillator.

SPECIFICATIONS:

OUTPUT POWER 15W R.M.S. into 8 Ω ; DISTORTION 0.1% at 1.5W.

INPUT SENSITIVITY 500mV. FREQUENCY RESPONSE 10Hz-16kHz—3dB.

SUPPLY VOLTAGE \pm 18V.

Price \pounds 25.22 + 65p VAT P&P free.

Available
June '76

HY50

25 Watts into 8 Ω

The HY50 leads I.L.P.'s total integration approach to power amplifier design. The amplifier features an integral heatsink together with the simplicity of no external components. During the past three years the amplifier has been refined to the extent that it must be one of the most reliable and robust High Fidelity modules in the World.

FEATURES: Low Distortion—Integral Heatsink—Only five connections—7 amp output transistors—No external components

APPLICATIONS: Medium Power Hi-Fi systems—Low power disco—Guitar amplifier


SPECIFICATIONS: INPUT SENSITIVITY 500mV

OUTPUT POWER 25W RMS into 8 Ω LOAD IMPEDANCE 4-16 Ω DISTORTION 0.04% at 25W at 1kHz

SIGNAL/NOISE RATIO 75dB FREQUENCY RESPONSE 10Hz-45kHz—3dB.

SUPPLY VOLTAGE \pm 25V SIZE 105 50 25mm

Price \pounds 26.82 + 85p VAT P&P free.

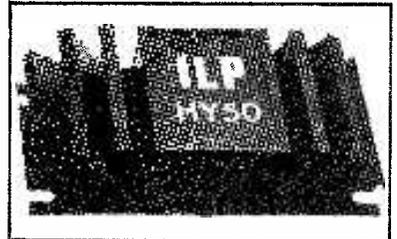

HY120

60 Watts into 8 Ω

The HY120 is the baby of I.L.P.'s new high power range. Designed to meet the most exacting requirements including load line and thermal protection this amplifier sets a new standard in modular design.

FEATURES: Very low distortion—Integral heatsink—Load line protection—Thermal protection—Five connections—No external components

APPLICATIONS: Hi-Fi—High quality disco—Public address—Monitor amplifier—Guitar and organ

SPECIFICATIONS


INPUT SENSITIVITY 500mV.

OUTPUT POWER 60W RMS into 8 Ω LOAD IMPEDANCE 4-16 Ω DISTORTION 0.04% at 60W at 1kHz

SIGNAL/NOISE RATIO 90dB FREQUENCY RESPONSE 10Hz-45kHz—3dB SUPPLY VOLTAGE \pm 35V

SIZE 114 50 85mm

Price \pounds 15.84 + \pounds 1.27 VAT P&P free.

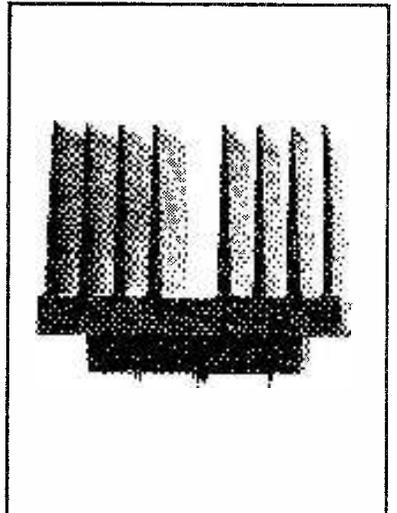

HY200

120 Watts into 8 Ω

The HY200 now improved to give an output of 120 Watts has been designed to stand the most rugged conditions such as disco or group while still retaining true Hi-Fi performance.

FEATURES: Thermal shutdown—Very low distortion—Load line protection—Integral heatsink—No external components

APPLICATIONS: Hi-Fi—Disco—Monitor—Power slave—Industrial—Public Address

SPECIFICATIONS

INPUT SENSITIVITY 500mV

OUTPUT POWER 120W RMS into 8 Ω LOAD IMPEDANCE 4-16 Ω DISTORTION 0.05% at 100W at 1kHz.

SIGNAL/NOISE RATIO 96 dB FREQUENCY RESPONSE 10Hz-45kHz—3dB SUPPLY VOLTAGE \pm 45V

SIZE 114 100 85mm

Price \pounds 23.32 + \pounds 1.87 VAT P&P free.

HY400

240 Watts into 4 Ω

The HY400 is I.L.P.'s "Big Daddy" of the range producing 240W into 4 Ω ! It has been designed for high power disco address applications. If the amplifier is to be used at continuous high power levels a cooling fan is recommended. The amplifier includes all the qualities of the rest of the family to lead the market as a true high power hi-fidelity power module.

FEATURES: Thermal shutdown—Very low distortion—Load line protection—No external components.

APPLICATIONS: Public address—Disco—Power slave—Industrial

SPECIFICATIONS

OUTPUT POWER 240W RMS into 4 Ω LOAD IMPEDANCE 4-16 Ω DISTORTION 0.1% at 240W at 1kHz

SIGNAL NOISE RATIO 94dB FREQUENCY RESPONSE 10Hz-45kHz—3dB SUPPLY VOLTAGE \pm 45V

INPUT SENSITIVITY 500mV SIZE 114 x 100 x 85mm

Price \pounds 32.17 + \pounds 2.57 VAT P&P free.

PSU36 suitable for two HY30's \pounds 25.22 plus 65p VAT, P/P free.


PSU50 suitable for two HY50's \pounds 26.82 plus 85p VAT, P/P free.

PSU70 suitable for two HY120's \pounds 13.75 plus \pounds 1.10 VAT, P/P free.

PSU90 suitable for one HY200 \pounds 12.65 plus \pounds 1.01 VAT, P/P free.

PSU180 \pounds 23.10 + \pounds 1.85 VAT.

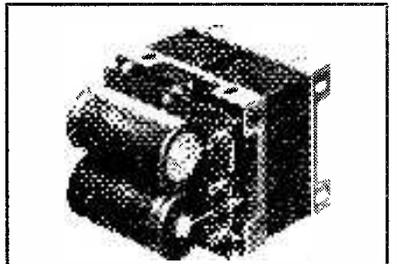B1 \pounds 20.48 + \pounds 2.06 VAT. **TWO YEARS' GUARANTEE ON ALL OF OUR PRODUCTS**



POWER SUPPLIES

I.L.P. ELECTRONICS LTD., CROSSLAND HOUSE,
NACKINGTON, CANTERBURY, KENT, CT4 7AD

Please Supply _____

Total Purchase Price _____

I Enclose Cheque Postal Orders Money Order

Please debit my Access account Barclaycard account

Account number _____

Name and Address _____

Signature _____

TTLs by TEXAS

7400	16p	74111	75p
7401	18p	74112	96p
7402	18p	74116	216p
7403	18p	74118	160p
7404	24p	74120	130p
7405	25p	74121	32p
7406	43p	74122	52p
7407	43p	74123	75p
7408	22p	74125	70p
7409	22p	74126	65p
7410	18p	74128	82p
7411	26p	74132	81p
7412	25p	74136	81p
7413	40p	74141	85p
7414	85p	74142	300p
7416	40p	74145	95p
7417	40p	74147	205p
7420	18p	74148	160p
7421	43p	74150	130p
7422	28p	74151	81p
7423	36p	74153	81p
7425	33p	74154	160p
7426	43p	74155	97p
7427	40p	74156	97p
7428	40p	74159	25p
7430	18p	74160	130p
7432	37p	74161	130p
7433	43p	74162	130p
7437	37p	74163	130p
7438	37p	74164	140p
7440	18p	74165	150p
7441	85p	74166	160p
7442	75p	74167	320p
7443	120p	74170	260p
7444	120p	74172	75p
7445	120p	74173	190p
7446	108p	74174	130p
7447	90p	74175	97p
7448	85p	74176	130p
7450	18p	74177	130p
7451	18p	74180	160p
7453	18p	74181	324p
7454	18p	74182	150p
7460	18p	74185	190p
7470	38p	74186	990p
7472	32p	74190	160p
7473	36p	74191	160p
7474	37p	74192	160p
7475	48p	74193	160p
7476	37p	74194	160p
7480	54p	74195	110p
7481	108p	74196	130p
7482	90p	74197	130p
7483	99p	74198	270p
7484	120p	74199	270p
7485	120p	74221	175p
7486	36p	74251	150p
7489	340p	74265	97p
7490	43p	74278	320p
7491	90p	74279	150p
7492	58p	74283	220p
7493	43p	74284	475p
7494	90p	74285	475p
7495	75p	74290	160p
7496	96p	74293	160p
7497	290p	74298	220p
74100	140p	74365	160p
74104	75p	74366	160p
74105	75p	74367	160p
74107	36p	74390	220p
74109	60p	74393	245p
74110	60p	74490	250p

CMOS ICs

4000	21p	4040	150p
4001	21p	4042	97p
4002	21p	4043	100p
4006	127p	4046	150p
4007	21p	4047	150p
4009	67p	4049	64p
4011	21p	4050	58p
4012	23p	4054	120p
4013	55p	4055	140p
4014	80p	4056	145p
4015	90p	4060	130p
4016	54p	4069	30p
4017	120p	4071	30p
4018	110p	4072	30p
4019	57p	4081	30p
4020	140p	4082	30p
4021	120p	4093	104p
4022	140p	4510	140p
4023	23p	4511	140p
4024	90p	4516	130p
4025	23p	4518	140p
4026	200p	4528	140p
4027	64p	14433	£14
4028	110p	14533	£50p
4029	120p	14533	£50p
4030	67p	14533	£1

LOW PROFILE DIL SOCKETS BY TEXAS

8 pin	12p	22 pin	36p
14 pin	13p	24 pin	40p
16 pin	14p	28 pin	60p
18 pin	30p	40 pin	75p

MEMORY ICs

1702A EPROM	1200p
2102-2 RAM	216p
2107 RAM	1080p
2112-2 RAM	470p
RO3-2513 ROM	850p

OP. AMPS

LM301A	40p	741	25p
LM318A	175p	747	76p
LM324A	120p	748	40p
LM339N	175p	776T	216p
NE531V	140p	MC1458	75p
709	38p	CA3130	108p
733	150p	CA3140	108p
		LM3900	70p

LINEAR I.Cs

AY-1-212	650p	NE561B	450p
CA3028A	112p	NE562B	450p
CA3046	85p	NE565	200p
CA3048	250p	NE566V	200p
CA3053	75p	NE567V	200p
CA3065	200p	SN72710N	54p
CA3080E	97p	SN76003N	275p
CA3089E	250p	SN76008	280p
CA3090AQ	425p	SN76013N	175p
ICL8038CC	400p	SN76013ND	160p
LM380N	112p	SN76018	280p
LM381N	190p	SN76023N	175p
LM389N	160p	SN76023ND	160p
M252AA	850p	SN76033N	275p
MC1310P	180p	TAA621A	310p
MC1351P	110p	TAA661B	150p
MC1495L	490p	TBA120	97p
MC1496P	112p	TBA641B	300p
MC3340P	180p	TBA651	225p
MC3360P	160p	TBA800	112p
MFC4000B	97p	TBA810S	125p
MFC6040	200p	TBA820	100p
NE540L	160p	TD A2020	405p
NE555V	40p	XR2240	400p
NE556	100p	ZN414	140p

VOLTAGE REGULATORS—Fixed

Plastic TO220-3 Terminals			
1 Amp +ve	-ve		
5V 7805	130p	7905	215p
8V 7808	130p		
12V 7812	130p	7912	215p
15V 7815	130p	7915	215p
18V 7818	150p	7918	215p
24V 7824	150p	7924	215p
100mA — TO92			
5V 78L05	70p	79L05	80p
6V 78L06	70p		
12V 78L12	70p	79L12	80p
15V 78L15	70p	79L15	80p
LM309K (TO3) 1A 5V	150p		
LM323K (TO3) 3A 5V	700p		
LM327N (16 DIL) 100mA +5 -12V		275p	
MC1468 (16 DIL) 100mA ±15V		300p	
(Adj. by Rs from ±8V to ±20V)			
TBA625B (TO5) 0-5A 12V		120p	
7805 (TO3) 1A 5V		150p	

VARIABLE

723 14 pin DIL 2V-37V 150mA	45p
LM317T TO220 1A-2V-37V	340p
TL430 TO92 100mA 2V-30V	75p

OPTO-ELECTRONICS

OCF 71 130p LEDs:	TIL209	Red	14p
ORP 12 75p	TIL211	Green	36p
ORP 60 90p	TIL32	Infrared	81p
ORP 61 90p		Red	16p
2N5777 48p		Green	20p
		Yellow	36p

DISPLAYS

3015F	Minitron	175p	
DL704	Red	160p	Green 160p
DL707	Red	160p	Green 160p
DL747	Red	250p	Green 250p

DRIVERS:

75491	84p	9368PC	216p
75492	104p		

SCR-THYRISTORS

1A 100V TO5	65p	C106D	70p
1A 400V TO5	95p	2N3525	130p
3A 400V stud	120p	2N4444	200p
7A 400V TO5	120p		
12A 400V TO220	180p		
16A 400V TO220	220p		
16A 600V TO220	270p		
BT 106 stud	150p		

TRIACS

3A 400V	85p
6A 400V 107p	
6A 500V 120p	
10A 400V 140p	
10A 500V 160p	
15A 400V 200p	
15A 500V 225p	

BRIDGE RECTIFIERS

1A 50V	25p
1A 100V	27p
1A 400V	31p
2A 50V	40p
2A 100V	45p
3A 200V	70p
3A 600V	80p
4A 100V	90p
4A 400V	90p
6A 50V	95p
6A 100V	105p
6A 400V	120p
10A 400V	270p

DIAC

BR100	30p
LP1186	£9.50

TV GAME I.C.

AY-3-8500	£7.75 inc. VAT
14433-3 1/2 DIGIT A/D CONVERTER	£14 inc. VAT

Please send SAE for detailed lists

TRANSISTORS

AC125	20p	OC42	19p
AC126	20p	OC45	19p
AC127	20p	OC71	25p
AC128	20p	R2008B	225p
AC176	20p	R2010B	225p
AC187	20p	TIP29A	60p
AC188	20p	TIP29C	62p
AD149	60p	TIP30A	60p
AD161	45p	TIP30C	72p
AD162	48p	TIP31A	56p
AF114	22p	TIP31C	68p
AF115	22p	TIP32A	63p
AF116	22p	TIP32C	85p
AF117	22p	TIP33A	97p
AF127	40p	TIP33C	120p
AF139	40p	TIP34A	124p
AF239	48p	TIP34C	160p
BC107/B	10p	TIP35A	243p
BC108/B	10p	TIP35C	290p
BC109	10p	TIP36A	297p
BC109C	11p	TIP36C	360p
BC147	9p	TIP41A	70p
BC148	9p	TIP41C	84p
BC149	10p	TIP42A	76p
BC157	11p	TIP42C	96p
BC158	13p	TIP2955	60p
BC159	13p	TIP3055	60p
BC169C	12p	TIS32	40p
BC171	15p	TIS33	28p
BC172	11p	2N687	25p
BC177	20p	2N695	43p
BC178	17p	2N706	22p
BC179	20p	2N708	22p
BC182	12p	2N718	43p
BC183	12p	2N730	19p
BC184	14p	2N1131	25p
BC187	32p	2N1132	25p
BC212	14p	2N1304	70p
BC213	14p	2N1305	70p
BC214	17p	2N1306	70p
BC461	40p	2N1307	70p
BC478	32p	2N1613	22p
BCY70	20p	2N1711	22p
BCY71	24p	2N1893	32p
BD124	1-40p	2N2102	60p
BD131	63p	2N2160	120p
BD132	67p	2N2219	22p
BD136	54p	2N2222	20p
BD139	56p	2N2369	15p
BD140	58p	2N2484	32p
BDY56	60p	2N2646	52p
BF115	2-24p	2N2804/A	22p
BF167	25p	2N2805/A	22p
BF170	25p	2N2906/A	22p
BF173	27p	2N2907/A	25p
BF177	28p	2N2926RB	9p
BF178	30p	2N2926G	11p
BF179	35p	2N3053	11p
BF180	35p	2N3054	65p
BF181	35p	2N3055	65p
BF182	24p	2N3439	72p
BF185	24p	2N3442	151p
BF195	13p	2N3565	34p
BF196	13p	2N3702	14p
BF197	17p	2N3703	14p
BF199	17p	2N3704	14p
BF200	40p	2N3705	14p
BF244B	40p	2N3706	14p
BF256B	60p	2N3708	14p
BF257	60p	2N3709	14p
BF258	39p	2N3707	14p
BF259	48p	2N3773	320p

A 741 SIGNAL TRACER

W. MOONEY G3VZU


WHEN greeted with silence from the output of a radio receiver or audio amplifier the problem of finding whether the signal is getting to the input or not and if so where it is lost can be difficult without some form of signal tracing device. Whilst a millivoltmeter is useful it only gives a voltage reading which could be noise or a highly distorted signal. Even with an oscilloscope one does not actually hear the signal. Using the tracer described here, the signal can be monitored with the aid of a small earpiece and a rough estimate made of its amplitude. The quality of the tracer amplifier is quite good, allowing noise and most common forms of distortion to be traced to a particular stage.

Design considerations

Although signal tracer designs abound there is always room for improvements or different design approaches. Many tracers are bench standing units in large cabinets housing a loudspeaker and mechanically offer a challenge to the beginner or those to whom time is at a premium. The device described here is in the form of a hand-held probe and the usual loudspeaker is therefore eliminated. No attempt has been made at miniaturisation, the size being kept reasonable to simplify construction.

The loss of the loudspeaker results in a number of advantages. The audio feedback occurring with some circuits is unlikely without the loudspeaker and the need for a fair amount of driving power is removed. The quality of the usual tracer amplifier/speaker combination is not very good mainly as a result of the speaker and its mounting. The audio heard through the earpiece is therefore at least as good as that which would be heard through a speaker-type tracer and the use of a pair of stethoscope earphones would improve matters. The lower power requirements makes probe-like construction possible and a long life can be expected from a small internal 9V PP3 battery.

The tracer should not load the circuit under examination and to this end an input impedance of $2M\Omega$ has been the aim. To cope with the wide range of signal levels likely to be encountered in practice a range of well over 60dB can be accommodated, from several volts downwards. Signals of $100\mu V$ were easily readable on the prototype and signals of only a few μV could be detected under quiet conditions. The 200kHz BBC transmission could be heard quite well using a tuned winding/ferrite rod and a simple diode detector. The requirements of high sensitivity and wide input range have therefore been met. Further requirements are that the device should be inexpensive and of reliable design, with little setting-up required. The circuit uses the cheap 741 operational amplifier IC along with a single

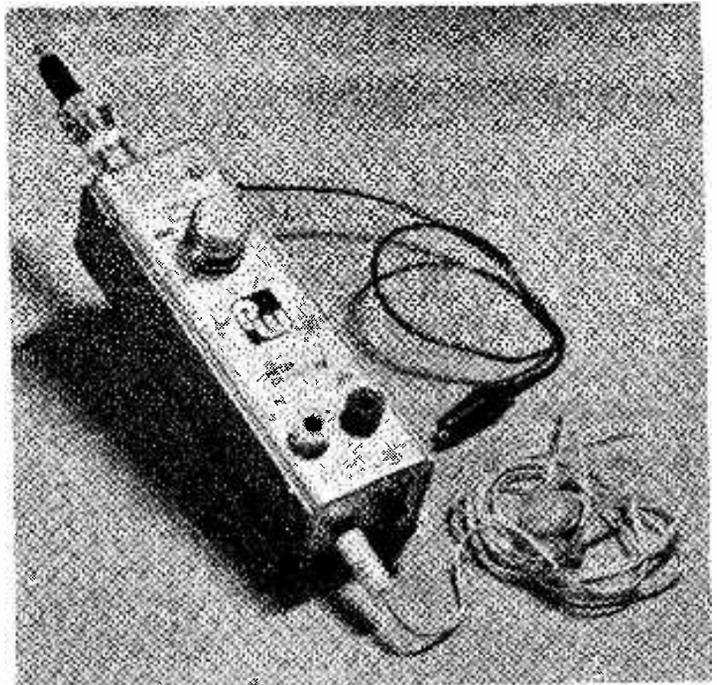

The 741 Signal Tracer ready for use. The crocodile clip earths the Tracer to the equipment under test, the audio signal being heard in the earpiece.

2N3819 FET input stage. On completion no adjustment is required other than the optional step of roughly calibrating the input attenuator.

Protection against accidental connection to a large input signal whilst the gain is set to maximum is provided by the use of a high impedance earpiece and by the limited output voltage swing of about $\pm 3V$. With a normal earpiece impedance of 500Ω the power input is about 10mW. The FET is protected by the usual back-to-back diodes across the input.

The circuit

The circuit is shown in Fig. 1, high frequency roll off and most of the gain is provided by the 741 op. amp, the output being sufficient to drive the earpiece directly. An FET input stage provides the required high input impedance and operates at a small gain of about 8dB. This input stage was necessary since an overall gain of 50dB was the aim and using the 741 alone the maximum input impedance achievable is too low unless abnormally high value feedback resistors are used. Also, at the required gain of 50dB, the bandwidth is too narrow due to the internal compensation. The prototype had a measured gain of 50dB at 1kHz. The gain is determined by the feedback and input components, C3, R5, R6 and R1 feeding the inverting input, and giving an upper frequency limit of about 10kHz in this circuit. A single supply rail is used and the non-inverting input is connected

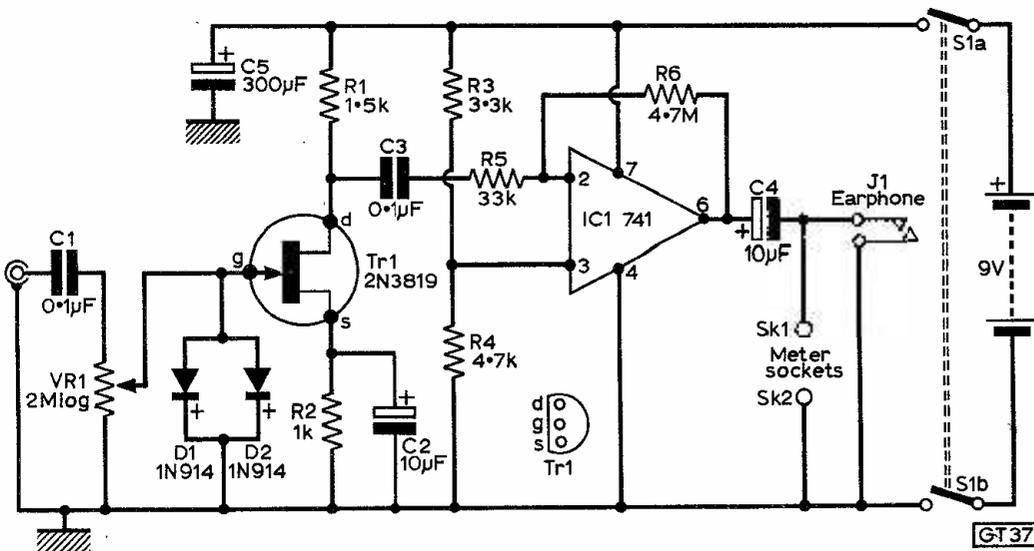


Fig. 1: Complete circuit of the Signal Tracer. The knob of the input potentiometer VR1 can be calibrated to give an indication of the signal level.

★ components list

Resistors

R1	1.5kΩ	R4	4.7kΩ	
R2	1kΩ	R5	33kΩ	all ½ or ¼W
R3	3.3kΩ	R6	4.7MΩ	5 or 10%
VR1	2MΩ log. potentiometer			

Capacitors

C1	0.1μF 250VW polyester	C4	10μF 10V
C2	10μF 10V	C5	300μF 10V
C3	0.1μF polyester		

Semiconductors

Tr1	2N3819	IC1	741 8-pin DIL	D1-D2	1N914
-----	--------	-----	---------------	-------	-------

Miscellaneous

J1, 3.5mm jack socket. S1, double pole, miniature slide switch. Coaxial socket. SK1-2, wander plug sockets. Aluminium box 135 × 70 × 40mm (5½ × 2¾ × 1½in) approx. Veroboard 44 × 22mm.

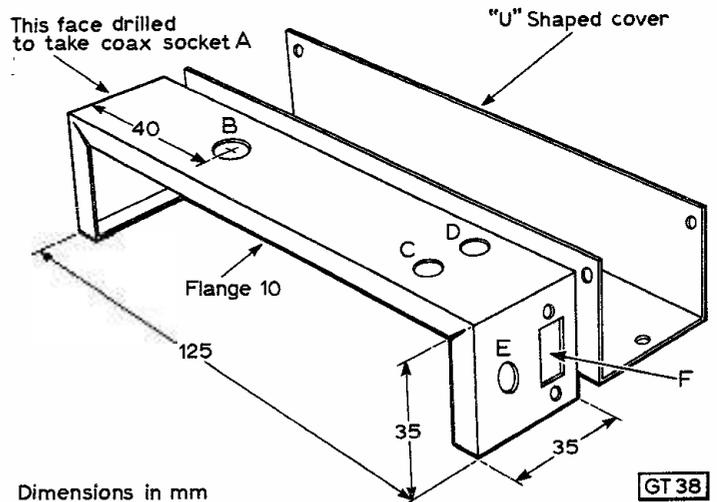


Fig. 2: Dimensions of the case as used by the author. These can be changed to suit the sizes of components actually used.

to a potential divider such that the output pin is at 5.6V. This is the middle of the range over which the output can swing. Here the voltage at the non-inverting input determines the virtual earth point into which the input and feedback operate. The output is taken through a 10μF capacitor C4. The earpiece should be a high impedance type, that used in the prototype had a measured impedance of about 500Ω at 1kHz. The output voltage at pin 6 is a little over 2V RMS at the commencement of clipping.

The FET input stage uses the readily available 2N3819 and operates at a drain current of 3mA and a gate bias of -3V. The component values represent a compromise between available gain and reasonable drain current at this rather low supply voltage of 9V. The AC voltage at the drain of the FET will be about 20mV maximum so with this method of biasing most 2N3819 samples will fall in operating range. The input impedance of the amplifier is approximately the value of the input potentiometer VR1 2MΩ. The frequency response of the unit was 50Hz to 8kHz at the -6dB points and this was considered adequate. Since the gain control is situated at the input, the amplifier is operating at constant gain and the noise generated within the amplifier is therefore present at all settings. The signal-to-noise ratio is however about 50dB and therefore this is not of any importance.

Construction

The unit is built in a small case made of light aluminium as shown in Fig. 2. A 10mm flange is bent in all around and to this is attached the "U" shaped cover using self-tapping screws. The mounting holes A, B, C and D are for the probe input socket, potentiometer and the two output wander plug sockets. The input socket is a normal protruding type coax socket. Mounting holes E and F are for the output jack socket and the slider on/off switch. Dimensions of these holes should suit the particular components used. The circuit board is held in position by a long 6BA bolt.


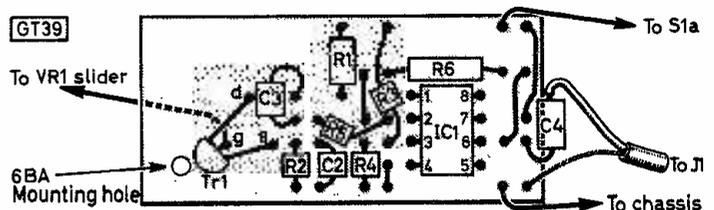



Fig. 3: Layout of components on the 17 × 8 hole Veroboard. If the horizontal holes are numbered 1 to 17 and the vertical holes lettered down A to H then the breaks in the strip are made at C14, D4, D10, D14, E6, E9, E14, F3, F5, F9, F14 and G14, looking from the components side.

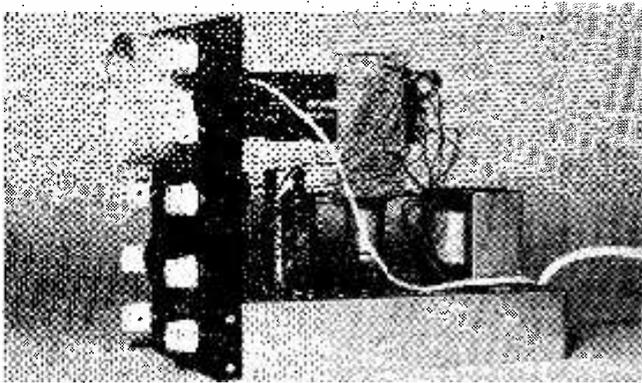

'There's only one way to master electronics... to see what is going on and learn by doing.'


1 Build an oscilloscope.

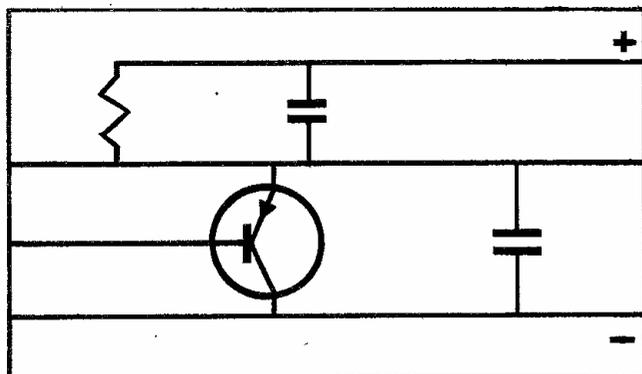As the first stage of your training, you actually build your own Cathode ray oscilloscope! This is no toy, but a test instrument that you will need not only for the course's practical experiments, but also later if you decide to develop your knowledge and enter the profession. It remains your property and represents a very large saving over buying a similar piece of essential equipment.



2 Read, draw and understand circuit diagrams.

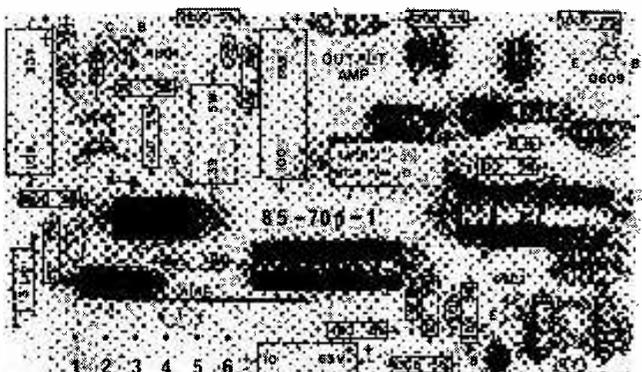In a short time you will be able to read and draw circuit diagrams, understand the very fundamentals of television, radio, computers and countless other electronic devices and their servicing procedures.



3 Carry out over 40 experiments on basic circuits.

We show you how to conduct experiments on a wide variety of different circuits and turn the information gained into a working knowledge of testing, servicing and maintaining all types of electronic equipment, radio, t.v. etc.

This new style course will enable anyone to have a real understanding of electronics by a modern, practical and visual method. No previous knowledge is required, no maths, and an absolute minimum of theory.

You learn the practical way in easy steps mastering all the essentials of your hobby or to further your career in electronics or as a self-employed electronics engineer.

All the training can be carried out in the comfort of your own home and at your own pace. A tutor is available to whom you can write, at any time, for advice or help during your work. A Certificate is given at the end of every course.



All students enrolling in our courses receive a free circuit board originating from a computer and containing many different components that can be used in experiments and provide an excellent example of current electronic practice.

To find out more about how to learn electronics in a new, exciting and absorbing way, just clip the coupon for a free colour brochure and full details of enrolment.

Write to: - British National Radio & Electronic School
P.O. Box 156, Jersey, Channel Islands.

NAME _____

ADDRESS _____

WB 6/7

AUTO TRANSFORMERS

Taps

Ref	VA (Watts)	£
113	20 0-115-210-240	3-14
64	75 " " "	4-73
4	150 0-115-200-220-240	6-89
66	300 " " "	8-82
67	500 " " "	13-39
84	1000 " " "	21-12
93	1500 " " "	23-62†
95	2000 " " "	34-17†
73	3000 " " "	47-63†

CASED AUTO TRANSFORMER

240V cable in & 115V USA 2 pin out.

Ref	VA	£
20VA	£ 5-67	Ref 113W
150VA	£ 9-30	Ref 4W
200VA	£11-93	Ref 65W
300VA	£14-32	Ref 66W
500VA	£16-91	Ref 67W
1000VA	£22-84	Ref 84W†
2000VA	£37-82	Ref 95W†

30 VOLT RANGE

Prim. 220-240V
Sec. 0-12-15-20-24-30V

Ref	Amps	£
112	0-5	3-45
79	1-0	4-37
3	2-0	6-21
20	3-0	7-51
21	4-0	8-61
51	5-0	9-99
117	6-0	11-50
88	8-0	14-44
89	10-0	14-85

BRIDGE RECTIF'S

200V	2A	0-82
400V	2A	0-93
200V	4A	1-04
400V	4A	1-21
400V	6A	1-44
500V	10A	2-87

POWER UNITS

CC12-05.3-4-5-6-7-5
-9-12V at 500mA £5-40
STABILISED 3-6
7.5-9V at 400mA £7-24
3300. Fits into 13A socket 6-7-5-9V 300-mA (fused) £4-30

TRANSFORMERS

ALL EX-STOCK—SAME DAY DESPATCH

60 VOLT RANGE

Prim. 220-240V
Sec. 0-24-30-40-48-60V

Ref.	amps	£
124	0-5	4-69
126	1-0	6-02
127	2-0	8-36
125	3-0	11-47
123	4-0	13-92
125	5-0	15-24
120	6-0	17-86
121	8-0	19-56
122	10-0	24-09
189	12-0	26-57

SCREENED MINIATURES

Ref	mA	Volts	£
238	200	3-0-3	2-74
212	1A	0-6-0-6	3-41
13	100	9-0-9	2-45
235	330	0-9-0-9	3-26
207	500	0-8-9-0-8-9	3-57
208	1A	0-8-9-0-8-9	4-65
236	200	0-15-0-15	2-56
214	300	0-20-0-20	3-36
221	700 (DC)	20-12-0-12-20	4-04
206	1A	0-15-20-0-15-20	5-54
203	500	0-15-27-0-15-27	4-95
204	1A	0-15-27-0-15-27	6-18
5112	500	12, 15, 20, 24, 30	3-45

PLUS

DECS Solderless Bread Boarding
S Dec 70 contacts £2-57
T Dec 208 contacts £4-35
U Dec 'A' for IC's £4-75
U Dec 'B' for IC's etc. £7-98

ELECTRONIC CONSTRUCTION KIT

10 projects (including Electronic Organ).
Ideal gift at £8-74 (no soldering needed)

COMPONENT PACKS

200 Mixed value resistors (by weight)
150 Mixed value capacitors (by weight)
30 Mixed value precision resistors
15 Assorted pots and pre-sets
10 Reed switches
3 Micro switches
15 Wire wound resistors (3-14W).
1 Pack wire 50 meters, ass. colours.
STATE PACK REQ'D £1-08 PER PACK

BLOB BOARD (Pack of 3)

2-5" x 5-1" -1" or 2-5" x 5-1" -15" £1-13
3-75" x 5-1" or 3-75" x 5-1" -15" £1-56
10" x 6" -1" or 10" x 6" -15" £4-51

IC Range:
4-8" x 3-2" £1-36. 4-75" x 7-5" £2-62

MAINS ISOLATING (SCREENED)

PRI. 120/240V
SEC 120/240V
PRIM & SEC CENTRE TAPPED

Ref	VA (Watts)	£
07*	20	5-10
149	60	7-11
150	100	7-85
151	200	12-59
152	250	14-81
153	350	18-08
154	560	21-55
155	750	28-20†
156	1000	37-97†
157	1500	45-51†
158	2000	53-24†
159	3000	80-78†

*115V or 240V Sec. only.

HIGH VOLTAGE

Mains Isolating (scr'ned)
Prim. 200/220 or 400/440
Sec. 100/120 or 200/240

VA	Ref.	£
60	243	6-86
350	247	16-59
1000	250	25-92
2000	252	54-80†

HIGH QUALITY MODULES

5 Watt RMS AMPLIFIER £3-70
10 Watt RMS AMPLIFIER £4-04
25 Watt RMS AMPLIFIER £5-27
125W RMS AMPLIFIER £18-50
PRE-AMP for 5-10W £7-92
PRE-AMP for 25W £15-90
POWER SUPPLIES 5-10W £1-84
POWER SUPPLIES 25W £4-60
TRANSFORMER 5-10W £4-50
TRANSFORMER 25W £6-43

ANTEX SOLDERING IRONS

15W £4-23 18W £4-23 25W £3-95
SOLDERING IRON KIT £5-82
STAND FOR ABOVE £2-00

12 and or 24 Volt PRIMARY 220-240V

amps

Ref.	12V	24V	£
111	0-5	0-25	2-52
213	1-0	0-5	3-24
71	2	1	4-02
68	3	-	5-43
18	4	2	5-08
85	5	-	5-79
70	6	3	6-75
108	8	4	8-04
72	10	5	8-58
116	12	6	9-89
17	16	8	11-36
115	20	10	15-80
187	30	15	19-88
226	60	30	24-78†

50 VOLT RANGE

Prim. 220-240V
Sec. 0-19-25-33-40-50V

Ref.	Amps	£
102	0-5	4-31
103	1-0	5-55
104	2-0	7-82
105	3-0	9-86
106	4-0	12-19
107	6-0	17-56
118	8-0	19-05
119	10-0	22-04†

CARTRIDGES

AT55 £5-36
Sonotone V100 £5-95
9TAHC £3-34
ACOS GP93-1 £2-83
GP96-1 £3-08
B.S.R. SC12M £3-66
GOLDRING G800 £6-71
G850 £4-94
SHURE M75-65 £12-66
M55E £14-33

Prices include VAT and P & P except † where carriage will be according to weight and distance. Save Postage—we are open 9-5pm Mon-Fri. Electrosl Resistors, Semi-conductors, Multi-meters, wide range of Panel Meters, Audio Accessories, send stamp for lists. Prices correct at 30th March, 1977.

Barrie Electronics Ltd.
3, THE MINORIES, LONDON EC3N 1BJ
TELEPHONE: 01-488 3316/7/8
NEAREST TUBE STATIONS: ALDGATE & LIVERPOOL ST

Get a great deal from

Marshall's

1977 CATALOGUE NOW IN STOCK PRICE 55p post paid (40p to callers)

Call in and see us 9-5.30 Mon-Fri 9-5.00 Sat

Our range covers over 7,000 items. The largest selection in Britain.

TOP 200 IC's TTL, CMOS & LINEARS

CA3020A	2-29	LM380N	98p	MCI350	75p	76650N	1-10	TBA700Q	1-61
CA3028A	1-01	LM381A	2-45	MCI351	1-20	76660N	60p	TBA720Q	2-30
CA3028B	1-29	LM381N	1-60	MCI352	97p	76666N	92p	TBA750	1-98
CA3030	1-24	LM382N	1-23	MCI357	1-45	TAA310A	1-50	TBA750Q	2-07
CA3080A	1-89	LM384N	1-45	MCI458	91p	TAA320A	1-15	TBA800	1-20
CA3045	1-40	LM386N	80p	NE555	53p	TAA350A	2-48	TBA810	1-16
CA3046	89p	LM387N	1-05	NE555E	1-05	TAA521	1-00	TBA820	1-03
CA3048	2-23	LM388N	1-00	NE565	1-30	TAA522	1-90	TBA920	1-79
CA3049	1-66	LM389N	1-00	NE566	1-80	TAA550	60p	TBA920Q	2-99
CA3052	1-62	LM702C	75p	NE567	1-80	TAA560	1-60	TBA940	1-62
CA3053	60p	LM709C	65p	SA550	2-50	TAA570	2-30	TCA160C	1-85
CA3080	68p	LM709N	45p	SA5570	1-00	TAA611B	1-85	TCA160B	1-61
CA3080A	1-88	LM710C	60p	SO42P	1-00	TAA621	2-15	TCA270	2-25
CA3086	51p	LM710N	60p	76001N	1-57	TAA661B	1-32	TCA280A	1-30
CA3088	1-59	LM723C	85p	76003N	2-50	TAA700	3-91	TCA290A	3-13
CA3089	2-52	LM723N	75p	76008K	1-70	TAA930A	1-00	TCA420A	1-84
CA3090	3-80	LM741C	65p	76013N	1-57	TAA930B	1-05	TCA730	3-22
CA3130	94p	LM741N	50p	76013ND	1-57	TAD100	1-95	TCA740	2-76
LM301A	65p	LM741-8	40p	76018K	1-92	TBA120	65p	TCA750	2-30
LM301N	44p	LM747N	90p	76023N	1-75	TBA120	1-50	TCA760	1-38
LM304	2-45	LM748-8	50p	76023ND	1-57	TBA400	2-21	TCA800	3-13
LM307N	65p	LM748N	90p	76033N	2-55	TBA500Q	2-30	TCAA170	2-00
LM308N	1-17	LM1800	1-76	76110N	1-46	TBA510	2-21	TCAA180	2-00
LM309K	2-10	LM1808	1-92	76115N	1-87	TBA510Q	2-30	TCAA400	2-00
LM317K	3-00	LM1828	1-75	76116N	2-06	TBA510Q	2-21	CD4001	20p
LM318N	2-25	LM3301N	85p	76131N	1-30	TBA520	2-30	CD4002	20p
LM323K	6-40	LM3302N	1-40	76226N	1-94	TBA520Q	1-98	CD4006	1-10
LM339N	1-75	LM3401N	75p	76227N	1-51	TBA530	2-07	CD4007	20p
LM348N	1-91	LM3900	1-50	76228N	1-75	TBA530Q	2-21	CD4008	97p
LM360N	2-75	LM3905	65p	76530N	1-50	TBA540Q	2-30	CD4009	57p
LM370N	3-00	LM3909	68p	76532N	1-30	TBA550	3-13	CD4010	57p
LM371N	2-25	MCI035	1-47	76533N	1-44	TBA550Q	3-22	CD4011	20p
LM372N	2-15	MCI303	1-85	76544N	2-09	TBA560Q	3-22	CD4012	20p
LM373N	2-25	MCI305	1-85	76545N	1-44	TBA570	1-29	CD4013	57p
LM374N	2-25	MCI306	1-00	76546N	4-1p	TBA570Q	1-38	CD4014	1-01
LM377N	1-75	MCI310	1-91	76550N	65p	TBA641Q	2-50	CD4015	50p
LM378N	2-25	MCI312	1-98	76552N	2-08	TBA651	1-80	CD4016	50p
LM379S	3-95	MCI327	1-54	76570N	1-10	TBA700N	1-52	CD4017	1-01
LM380-8	90p	MCI330	92p	76620N					

THIS IS JUST A SMALL SELECTION FROM OUR RANGE—PLEASE ENQUIRE FOR TYPES NOT LISTED

POPULAR SEMICONDUCTORS

2N696	35p	2N2907	21p	2N3791	3-10	2N6121	38p	BC107	15p
2N697	30p	2N2907A	22p	2N3792	3-50	2N6122	41p	BC108	15p
2N698	62p	2N2924	15p	2N3794	20p	2N6123	43p	BC109	15p
2N699	55p	2N2926	12p	2N3819	36p	2N6126	45p	BC113	17p
2N706	24p	2N3019	55p	2N3820	38p	40361	45p	BC115	19p
2N706A	12p	2N3053	30p	2N3823	75p	40362	48p	BC116	19p
2N708	21p	2N3054	60p	2N3904	21p	40363	1-20	BC16A	20p
2N709	50p	2N3055	70p	2N3908	22p	40406	58p	BC117	22p
2N718	27p	2N3390	25p	2N4036	67p	40407	45p	BC118	16p
2N718A	50p	2N3391	25p	2N4037	55p	40408	65p	BC119	30p
2N720A	80p	2N3391A	25p	2N4058	20p	40409	65p	BC121	45p
2N914	35p	2N3392	16p	2N4060	20p	40410	65p	BC132	30p
2N916	30p	2N3393	15p	2N4061	17p	40411	2-85	BC134	15p
2N918	38p	2N3394	15p	2N4062	16p	40594	75p	BC135	15p
2N929	25p	2N3439	88p	2N4126	17p	40595	86p	BC136	19p
2N930	28p	2N3440	64p	2N4289	20p	40673	73p	BC137	14p
2N1131	60p	2N3441	85p	2N4919	65p	AC126	37p	BC140	40p
2N1132	60p	2N3442	1-35	2N4920	70p	AC127	44p	BC141	45p
2N1613	35p	2N3638	16p	2N4921	50p	AC128	37p	BC142	30p
2N1711	37p	2N3638A	16p	2N4922	50p	AC151	35p	BC143	30p
2N1893	30p	2N3639	30p	2N4923	70p	AC152	50p	BC147	12p
2N2102	60p	2N3641	20p	2N5190	60p	AC153	49p	BC148	12p
2N2218	33p	2N3702	17p	2N5191	70p	AC153K	55p	BC149	13p
2N2218A	37p	2N3703	16p	2N5192	75p	AC176	40p	BC153	27p
2N2219	30p	2N3704							



View of the general layout of the Tracer with the cover removed. Note that C5 is wired direct to the on/off switch, and that the probes are wired across the input potentiometer.


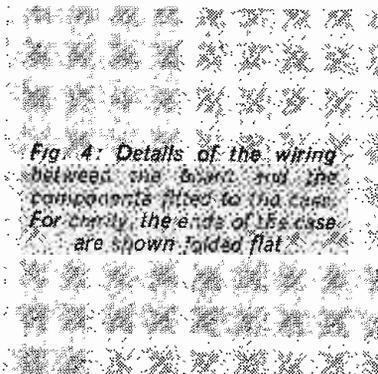


Fig. 4: Details of the wiring between the front and the components fitted to the case. For clarity, the ends of the case are shown folded flat.

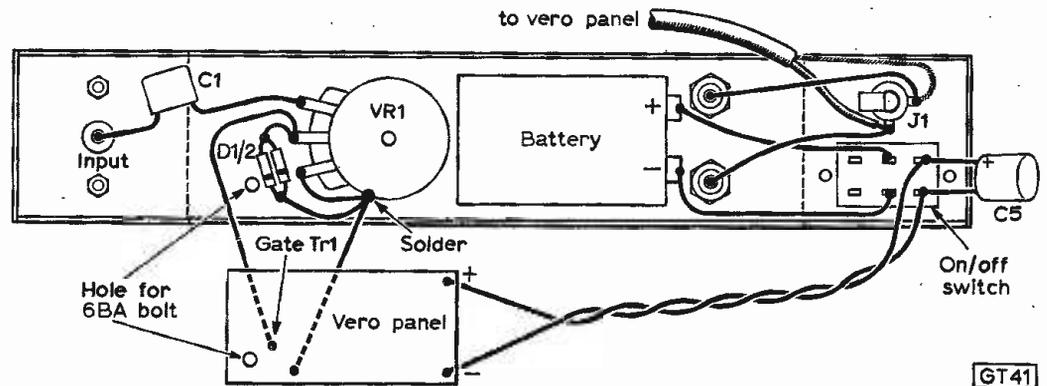


GT41

Most of the amplifier components are mounted on a piece of 0.1in Veroboard measuring 45mm by 22mm (17 holes by 8 holes), as in Fig. 3. Deviation from the layout given should not prove hazardous provided the output and input wiring is kept apart. The input capacitor C1, protection diodes D1 and 2 and the decoupling capacitor C5 are wired in point to point. If the jack is of the shorting type it should be wired so that the output is not shorted when the jack is removed as this would also short the wander plug sockets. The wiring to the output sockets should be made with a screened lead. The battery is held in position by a piece of foam rubber glued to the cover. When setting up without the cover the battery can be held to the main chassis by double-sided Sellotape, Fig. 4.

The use of a coax input socket allows a permanent connection to be made to the equipment under test

with a short length of screened lead and two miniature crocodile clips. A suitable probe may be plugged into this socket for normal tracing operations. The construction of such a probe is shown in Fig. 5. This probe is made from a good quality aluminium coax plug. Without the small tinfoil screen the mains hum pickup will be considerable due to the high impedance. The insulating sleeve is cut from a potentiometer shaft, perhaps VR1 if it is bought new. A $\frac{1}{16}$ in hole is drilled down the centre of the sleeve so that the brass contact makes a tight fit. The contact used in the original was cut from a brass welding rod, filed to a point at one end and the other end filed to a smaller diameter so as to fit down the centre of the coax plug to which it was soldered.

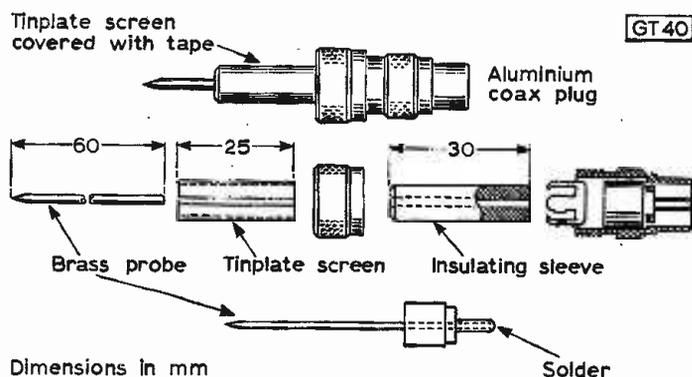

GT40

Fig. 5: One probe can be made from a coaxial cable plug as shown here.

Setting up

Before switching on for the first time a meter should be connected in series with the battery supply to check the current which should be 5 to 6mA. If everything is functioning correctly a slight hiss will be heard in the earpiece and possibly some mains hum. If possible a check on the gain should be made when an input of 3mV should give an output of 1V RMS at about 1kHz with the gain turned up fully. The input attenuator can be calibrated in several ways. A voltmeter can be connected to the output and a signal generator to the input through a suitable attenuator. The gain control then being marked in millivolts input for 1V out. The prototype was calibrated in a similar way to this except that the scale was marked 0, -20, -30, -40dB etc. for an output


continued on page 199

The PARIS SHOW

Salon International des Composants Electroniques 77

THE Exposition Park at the Porte de Versailles in Paris covers an area of 65,346m². It is the home of a major annual electronics exhibition and this year some 1,200 exhibitors displayed a diverse range of electronic goods. With 30 different countries displaying their wares, the exhibition can fairly claim to be international!

Exhibits varied from old friends seen last year, to the novel and curious. For example, one stand boasted an ionograph which might be loosely described as an electronic device which measures cleanliness! In certain areas of electronics it is necessary to know that the PCB is clean since it picks up all kinds of solvents and greases on its route through the production lines. The ionograph flushes the PCB in a fluid which then passes through a chamber, and the ionisable particles of dirt in the fluid are measured and displayed on a dial. This gives a measure of the dirtiness/cleanness of the particle content in the fluid and hence the cleanliness of the PCB. Just the thing in this modern age for checking on the state of little boys' necks (could probably be calibrated in tidesmarks).

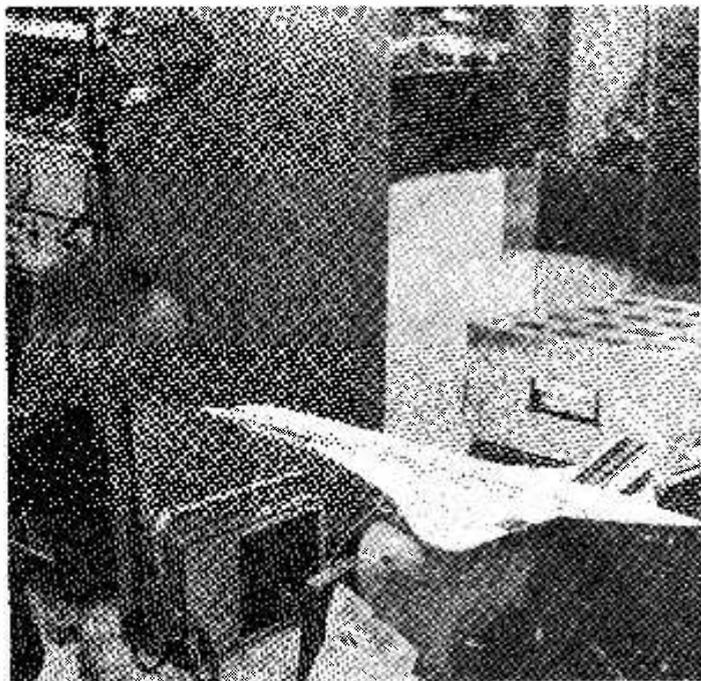


This model of Concorde looks steady enough but it's really being vibrated at varying rates on different parts of its body. A nearby stroboscope, when switched on, "freezes" the vibrating model making it appear stationary.

The cordless soldering iron has been on the market for some time, but one company has gone a stage further. They are offering a miniature drill which plugs on to the contacts of the heating element and runs from the internal rechargeable batteries in the body. The drill measures only 7.8cm x 3.2cm and weighs 65g. Definitely a hot little number! If you have \$400 under the mattress you could consider

A report from DAVID GIBSON

buying an MCP-1, a radio receiver with no tuning knob. Inside, the MCP-1 has just about everything; a microcomputer, phase-lock loop, digital frequency synthesiser, just to name a few. They combine to give a small calculator-type keyboard and a digital readout window. Touch a button and the receiver will start to scan. When it comes to the first occupied frequency it will stop. If you want that station, touch another key and the exact frequency is entered into memory. Then carry on scanning. To recall any station, merely touch in the frequency. Just a thought—the memory has sufficient capability to store 12,000 separate stations! An unusual feature is that no crystal is used; the receiver relies on phase-locked loop and digital frequency synthesiser techniques.

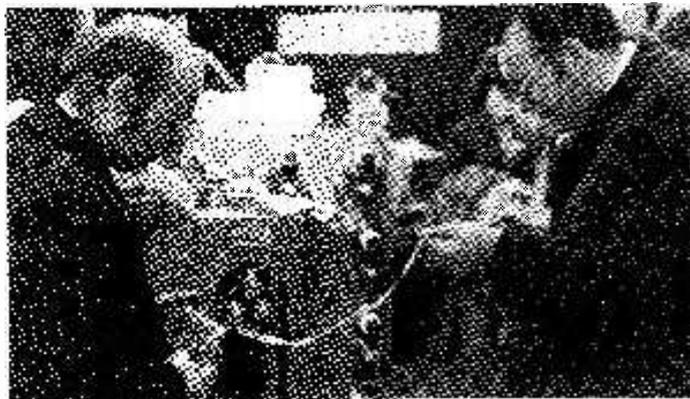

Two visitors can hardly believe it. This machine winds foil-film capacitors, and the foil is only 2 microns thick.

Some items were so new that they were only talked about in low voices. One novel IC was described as a driving circuit for analogue displays. This turned out to be a chip which has outputs suitable for driving LEDs. The novelty is the number and arrangement of these outputs. There are 10 outputs and 3 "lines" selection. Thus, if one imagines 30 LEDs arranged in three rows of ten, it is possible to address or illuminate any one (or more) LED in the matrix. Possible applications suggested were digital voltmeter where lit diodes would indicate voltage and eliminate the need for a meter. The device operates from 9V and it is possible to cater for two alarm points i.e. when (say) the voltage went above or below certain preset limits in the digital voltmeter application described above. It would seem to offer some interesting possibilities in the area of electronic games although this is not its prime function. Development samples only are available at present.

Most people have seen or heard of a teleprinter. This is a keyboard like a typewriter but which can send signals over the telephone lines which are subsequently printed out by another teleprinter at the receiving end. Trouble is that the keyboard is rather large and so invariably fixed in some office. That

was until this year's Paris show. A company called Technology Resources exhibited a pocket TTY. This measures only 25 x 75 x 155mm and comprises a complete pocket teletypewriter terminal. It allows both transmission and reception of signals and has a 36-button keyboard. Each button has two sets of characters and a small switch at the top dictates which is sent, depending upon whether this switch is set to the left or right. The standard ASCII code is used and the speed is 110 bauds. The terminal requires two power supplies: +5V at 500mA, and -12V at 100mA.

One unexpected stand was that of REF, Reseau Emetteurs Francais, the French RSGB. The Society had a station on the air using a 144MHz transceiver under the callsign F8REF. The rig was a Kenwood 2-metre all-mode transceiver with 10W of SSB, FM and CW, and 3W of AM. The society offered for sale a "Hams Interpreter" which gave equivalent phrases in most languages. While your scribe searched diligently, there was no polite phrase which could be used for those Iron Curtain T3 notes which still haunt 14MHz!

For readers who find the soldering iron has a nasty habit of burning through its own lead: good news. A Scandinavian firm which specialises in wires and cables has one which can withstand enormous temperature differentials. Available in a variety of sizes it will work over the temperature range minus 100°C up to plus 300°C.

And so the show drew to a close for another year with snippets still ringing in the visitors ears: GIM has sold eight million games chips which "play" tennis, squash, football, a sort of "four-rule" games chip; AEG Telefunken showing a 5cm rectangular flat CRT with heating power only 35mW and an accelerating voltage of 1.5kV described as suitable for pocket TV sets. With an average of over 10,000 visitors a day, the show will rest now until April 1978, when we'll find another 1,200 exhibitors showing new devices even more wonderous than this year.

A 741 SIGNAL TRACER—continued from page 197

of 0dB or 0.774V. A less accurate method is to use a low frequency input of say 200Hz and note the input level required to cause clipping as heard in the earpiece, at various gain control settings. However it should be noted that this is not intended as a measuring instrument and that any calibration can only be approximate, as the gain is to some extent dependent on the supply voltage and the frequency since the response is not perfectly flat.

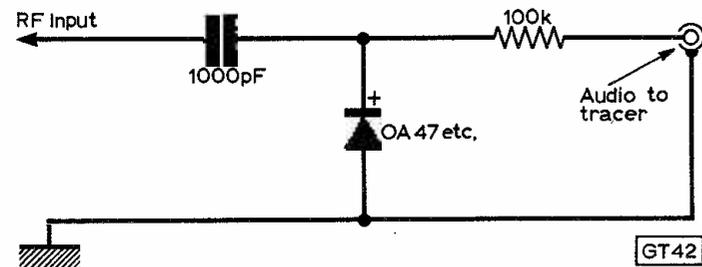


Fig. 6: For tracing modulated RF signals a probe incorporating the above circuit can be constructed.

An RF probe, as such, was not constructed for the prototype, a diode detector as in Fig. 6 being set up when required, keeping all "hot" leads as short as possible. The prototype worked well on supply voltage as low as 7V although the gain decreased. 

next month in

Television

● TV GAMES IN COLOUR

You've seen many TV games projects before — but in monochrome. This one gives you full colour display and is yet one of the simplest to build, using only four i.c.'s (including the power supply). The three games are tennis, ice-hockey and squash, and there are practice versions of the games as well. There is automatic scoring, and sound effects via the set's sound channel. Other features include automatic ball speed-up during the game and a choice of three bat sizes. The output simply feeds into the set's aerial socket. Simple to build, simple to use, and in full colour!

● SERVICING FEATURES

John Coombes writes on the widely distributed Bush/Murphy A774 monochrome chassis while James Brice describes common faults on one of the earlier up-market colour chassis, the Tandberg CTV1.

● SWITCH-MODE POWER SUPPLIES

One of the main trends in TV receiver design has been the change to the use of switch-mode power supplies. These come in many different forms to confuse us however, and require safety circuitry to suit. E. Trundle sets out the factors which determine the selection of a power supply and describes a number of recent switch-mode circuits.

PLUS ALL THE REGULAR FEATURES

ORDER YOUR COPY ON THE FORM BELOW:

TO.....
(Name of Newsagent)

Please reserve/deliver the JULY issue of TELEVISION (45p), on sale June 20th, and continue every month until further notice.

NAME.....

ADDRESS.....

.....
.....



New style R.A.E.

Candidates for the R.A.E. will probably be aware that it is intended to change the format of the examination.*

My students have taken part in a City & Guilds Protest, and if their reactions are typical there seems to be no relaxation of the standard. The multiple choice method enables the entire syllabus to be covered, probably with 150 questions. There is a sophisticated method of eliminating the chance of success by guesswork. My basic method is to subtract the wrong ones from the right ones.

Past experience in *other C. & G.* examinations having a syllabus including some Regulations, some recognition and interpretation with elementary calculations, has demonstrated to my satisfaction that the competent candidates succeed.

I have been able to monitor the performance of these students in the College and at work and I maintain that the gradings achieved reflect as accurate an assessment as any other method which does not require a display of practical, manual ability.—
Name and address supplied.

* See News Item on page 180.

Out of this world!

I write in answer to the letter by Mr. G. L. Manning, G8JBH, titled "High Power Interference" published in the May issue of *Practical Wireless*.

The transmission that is referred to is undoubtedly that of the AMSAT-OSCAR 6 command station, located at the University of Surrey, the purpose of which

is to control the satellite's periods of utilisation, hence the battery state and continued function, as a part of a world-wide command group in phase with similar stations in Hungary, New Zealand, Australia, Canada and the USA. The British section of the command network has been active for over two years and the project is now developed to a fully automatic az-el real-time computer controlled status, that has performed its part in keeping the satellite "alive" for the one thousand plus Oscar communicators around the world.

Thus, in real terms, one cannot claim that "minority groups are being given absolute priority over other groups" especially when one considers that we are dealing with some 30kHz of a band 2MHz wide. The actual bandwidth is considerably less than the 100kHz stated, although I would agree that the nature of the transmission would make it appear to be of a much wider bandwidth in many types of receivers close to the source.

The reason that the transmission is greater in its spread is in part so that any interfering signals do not accidentally command, and because it has to overcome the Doppler shift during an orbit. The selection of the particular part of the band used is because it is one of the two "all modes" sections, and also to cause the minimum possible inconvenience to other band-users, it being on a little-used section of the two metre spectrum, to which many alternatives exist. It also needs to be a frequency that is internationally available on a mutual basis for such sophisticated functions.

Our regret is that apparently this section of the band is employed in the more densely amateur populated areas, and that it would obviously be better to have the station situated at a more remote and less inhabited area, but, the considerable technical resources and cost of the installation limited its placement to the only position where the competence and allocation was available.

The periods of transmission are restricted solely to those times when Oscar 6 is in line-of-sight to the command, this being some two hours total time daily, varying from transmission times of a few minutes in the early morn-

ing and late evening hours, to a maximum of 25 minutes on overhead passes, at a rate frequency of 100 minutes. The actual times are dictated by the orbital constants, which are available from GB2RS, BARTG Teletype bulletins, CEEFAX, ORACLE, TELETEXT, AMSAT and many other sources, thus permitting those interested to know the exact times when to expect the transmission. Although AMSAT have strong links with the RSGB, the Society cannot be held responsible for the difficulties encountered by stations also using this part of the two metre band.

The particular choice of frequency of any user of the band employing it for normal QSO's is up to the user, having regard to the band-plan, and if an operator chooses to employ a section allocated for mixed modes, he still has the choice of 700kHz unaffected by the command signal, with the complete freedom to move, unrestricted by international requirement. AMSAT were not unaware of the problems being experienced by other users of the section covered, and had a valuable dialogue with G3HTP, representing the affected other users, at the last AMSAT-UK meeting at the University of Surrey, resulting in a good mutual understanding. As a result a letter explaining and outlining the problem was sent to every club Secretary of amateur radio groups within a 75 mile radius of the command station. The bandwidth was reduced, power also, to the very minimum capable of commanding the spacecraft, and azimuth control was added to reduce the groundwave signal level.

On a more optimistic note (from the point of view of those who wish to use this particular section, if not from AMSAT's) the OSCAR-6 satellite has now lost four of its Ni-Cad cells, and despite careful nursing by the command network, is unlikely to be with us for much longer. OSCAR-7 is in the main self-controlled, and is not commanded by the British section of the international network. Further, future satellites should only need short bursts of a few seconds duration to "hold" the information fed, and this only a few times per week.

On a more personal note, I do not feel that the presence of a few amateurs holding QSO's on a

particular frequency is likely to justify the continued allocation of this greatly envied spectrum at WARC in 1979. On the other hand, the knowledge and know-how of satellite operation multi-access and the development of the means of satellite command auto-control systems is an activity that is likely to be of value to those who will decide as to whether the amateur service maintains its current band availability.—**Pat Gowen G3IOR** (Norwich). Chairman and Co-ordinator AMSAT-UK.

April fool

With reference to your informative article 'Surefire' in your April 1977 issue, I must congratulate you on a most marvellous and comely piece of prose. However, when I commenced the fabrication of said circuit, in situ, I was perturbed to discover the absence, to wit the total lack, of an APR 77 transistor in my collection. Fortunately, I perchanced to recall my ownership of a multiplicity of Unitrons—of which much has been penned in your illustrious magazine.

Whereupon, on inserting said Unitron, an imaginary current was perceived to flow. Could this be the first contact with an alien universe?—Yours laboriously,
Prof. T. Pott. (Whataripoff Institute of Parapsychology, Moscow.)

A complaint

I am writing to you to complain about the lack of valve designs in your magazine. Many people have written asking for valve designs and I think you should have some. Surely, if you ignore what the readers are asking for, then people will stop buying your magazine!

After all a valve radio is simple to design; no complicated regulated power supplies are needed or heatsinks. In my opinion, people don't build radios any more. They just get a couple of integrated circuits, a ferrite rod, a printed circuit board and there you are, instant noise maker! In the old days, to build a radio was a major task. A chassis had to be punched, transformers had to be mounted. Valve holders, coils,

large variable capacitors and tag strips all had to be thought about before the soldering iron was plugged in.

I am only fifteen and I recently built a four-valve TRF to my own design using Denco coils. This had a good tone and a high output. The selectivity and sensitivity were good even though no reaction was used, and it wasn't a superhet. Valves are still in use in many TV and amplifier applications all over the country and I think you should include them in your magazine. Apart from this I find your magazine excellent!—**Andrew Redding** (Rotherham).

We would welcome such designs from readers. How about you, Andrew, submitting an article on your receiver?—Asst. Editor.

2kW from a PP3?

Having constructed my own style of Disco Unit, using some of the circuits in *Practical Wireless*, I found that I had omitted to build any form of pre-fade amp into the unit. I rushed out and purchased a small half-watt module and fitted this into the unit as a temporary fitting, powering it from a PP3 battery neatly clipped on the side of the cabinet.

A few weeks later I was booked for a party in our local public house and during the course of the evening a rather merry gent staggered up to me and asked to have a look at my 'gear'. I told him that I had built the majority of it myself and he remarked that it looked and sounded very good. He noticed the PP3 battery strapped to the side and remarked, "and it all runs off that wee battery, magic stuff" and staggered away!

I must write to a certain battery company and ask if they have found anyone else using PP3s to power a 50 watt amp, two turntables and 1800 watts of flashing lights!—**P. C. Glen** (Glasgow).

Who's he kidding?!

I am writing to you in connection with the article SUREFIRE published in the April issue of your magazine.

I would first like to agree with Mr. D. Jones theories and explanations. I would also like to point out that when VR1 is in fact acting as a Kenotron not only will all present positrons undergo adiabatic contraction, but it can also be proved that photon entering the magnetic field will actually gain energy, this energy is then converted into ultra violet light. It was also found in the atomic research laboratory that adiabatic contractions in positrons changes the charge of a given electron by exactly $1.37549865 \times 10^{-20}C.$, this was measured with an atomic operational amplifier very similar to the good 'ol 741. This amplifier can be made to detect charges as small as $10^{-12}e.$

The circuit in the article also helped to prove beyond any question the Lorentz-Fitzgerald contraction and also helped with the measurement of the time dilatation between two given events in a frame of reference travelling at twice the speed of light.

May I take this opportunity to congratulate Mr. D. Jones in the achievement of achieving Nothing.—**N. Nazoa** (London).

Look behind you!

Some time ago I constructed a 6 transistor radio for the short-wave bands in a metal case with an open "rear". A few days ago I noticed that regeneration had become somewhat "fierce" and decided to investigate as the radio is in a shack in the garden! I duly took the set out of its case and then noticed that a small spider had built a "web" around the regen-control (a variable capacitor of an open type) and as the weather was damp tiny globules of water had formed along the strands and in between the fixed and moving vanes of the capacitor and in addition there was also a web built around the volume control and I suspect shortening the life of the 9V battery, when the web became damp! So watch out boys if your equipment is in a damp or humid shack or "spidery" attic, batteries are expensive and also transistors could be damaged!—**J. Owens** (Dolgellan).

Microprocessors —new uses

Great news for Teletext/Viewdata addicts. I hear that a British company is to turn to microprocessor technology to produce what amounts to a very low cost TTV (teletext/Viewdata) module. Price quoted in the US is 20 dollars—that's around £11. The same company hopes to add another module later which will offer on-screen channel number, time, remote control, and digital tuning. This latter device will cost around 30 dollars.

Speaking of microprocessors, I hear that these components will play a major role in motor cars of the 1980s; and that's less than 3 years away. Fuel injection by electronic means has already appeared on many vehicles, but the motor manufacturers are now working on fuel management. A sensor in the exhaust system feeds back information to the electronics which in turn can control all the major adjustments possible in the engine—like fuel injection, fuel/air mixture, throttle, engine speed, etc. The electronics is so designed as to ensure that the engine is always running at maximum efficiency. One can imagine the ultimate in auto electronics—just sit in the car and say to it, "Home, James".

¹/₂ inch switch ... almost

Let's switch to a different subject—switches! Imagine a ten-way single pole switch. Quite a large affair; until Micro-Dip came along. This switch will operate over the temperature range -10° to $+60^{\circ}\text{C}$ and can switch 5V at 100mA. Its size is truly remarkable—just half a 14-pin DIL package. In inches, that's only $0.38 \times 0.4 \times 0.24$ in. The contacts are gold plated and the switch is also available in codes, such as BCD and complemented BCD. It is rotated by the blade of a small (very small!) screwdriver.

I was interested to learn of some power MOS FET devices just on the market. These give a minimum gain of

10dB at 200MHz and have a power dissipation rating of 35W. These would seem near ideal for QRP Ham rigs since not only are these devices "thermal runaway-proof", they are also immune to load mis-match burn-out too. Small quantities (in the US) are priced at around 20 dollars.

Magnetic display

Displays are always items of interest especially new ones. The latest to come to the ageing Ginsbergian eardrums (I haven't actually seen these yet) consist of little balls floating in oil. One half of each ball is white, and the other half black. The balls can be rotated by means of an applied magnetic field. Thus a pattern can be shown by simply applying the necessary magnetic fields. Quite true—not a load of balderdash.

Another display uses a liquid crystal only 10mm by 10mm. Onto this tiny cell, some 40 rows, each with 50 characters can be packed. A laser beam is scanned across this "cell" and the image projected to 10in x 10in. The speed of the system is about 20 characters per second which is very fast.

Hot car

One hears about absent-minded professors, but here's a story about a retired, but very forward-thinking one. He lives in Los Angeles and drives a small Honda motor car. Power is derived from two 3.5 horsepower electric motors. These take their power from six 6V batteries. On the roof of the car is an array of photocells which keep the battery charged. Top speed is around 25 mph with about one hours' driving time before the battery runs down and needs a recharge (free from the sun). The array of cells on the roof manages to produce around 3A/hour in sunlight and an eight-hour "exposure" gives enough battery power for at least one hours drive. But don't start eyeing your mini roof

yet; the total cost of the cells was over £1200—and the wise professor has kept the petrol engine part of the vehicle intact!

While the Citizens Band in the UK is still at the idea stage it is interesting to see the volume sales in America for CB radios—particularly from Japan. The 1976 trade figures (for the US) indicate that Japan exported 9,900,000 automobile transceivers alone! And they managed to capture 88% of the US market for this type of equipment. The actual value of these transceivers was put at well over 550 million dollars. There is currently a move afoot to restrict the imports of these equipments by putting up tariffs and setting quotas. I wonder if the UK will learn anything from all this?

Stamp collecting ... outdated?

How long before computer hobbyists emerge in Britain? Perhaps when the potential to the hobbyists/experimenters is fully understood. Take the things some people are already doing. One man generates music with his computer. He writes electronic songs by playing notes into the memory from a keyboard. These could be read out via a synthesiser to reproduce almost any instrument.

Another computer hobbyist has a wood-burning stove (which helps heat his house) coupled to the computer which has improved efficiency by some 10% on very cold days. In weather above freezing point, the efficiency has been increased by nearly 30%.


Yet another enthusiast keeps all manner of information in his computer's memory banks on things affecting his buying and selling business—could be an idea for those who play the stock market?

ON TARGET? SHOOT!

IN NEXT MONTH'S PRACTICAL WIRELESS




ON SALE 1st JULY

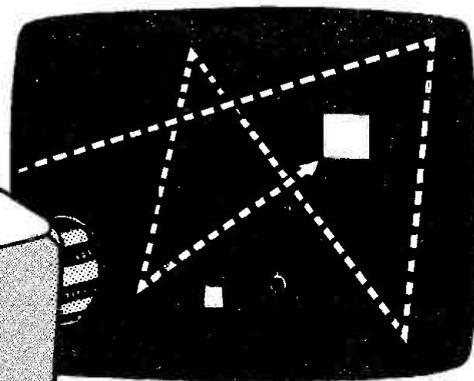

Simple add-on unit for PW's Tele-Games . . . watch for the target on the screen, aim your spot with the joystick control, press the trigger and Fire! If you are on target your score appears on the screen.



Handy-Mini POWER SUPPLY

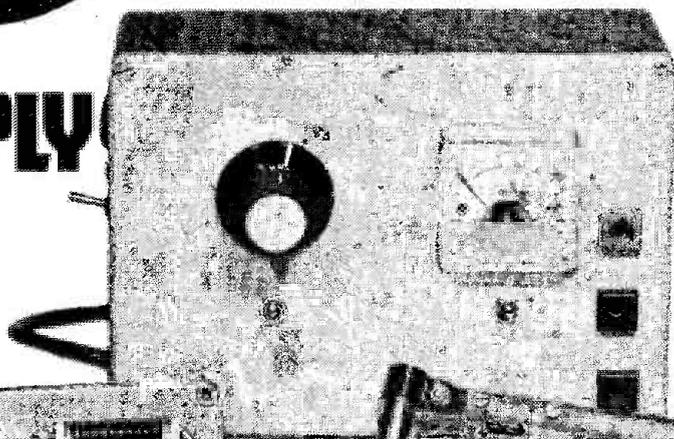No experimenter can have too many power supply units around! This one will always prove valuable, providing from 0 to 12V at 500mA or 1A as required. It incorporates overload protection and a meter to monitor the output current.



Morse Tutor

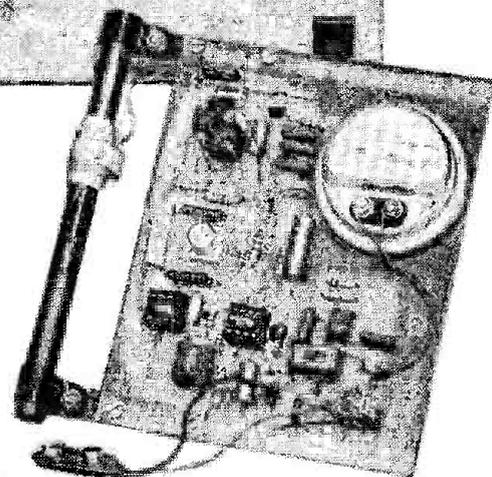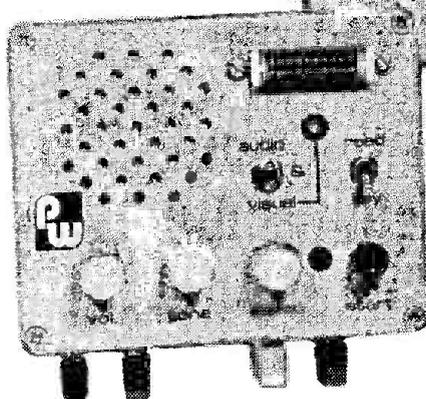Learn Morse the easy way with the PW Morse Tutor. Electronically generated Morse characters produce a perfectly keyed audio or visual signal. Code cards plug into a socket and out comes the code! Plus speed and tone controls. Invaluable for code instructions or just teach yourself.




ATOMIC Time Receiver

You won't believe it, but the period of the earth's rotation is just not constant enough these days for some purposes! Build this Atomic Time Receiver, driven from a signal from

station MSF at Rugby, and compare instantly the earth's time and atomic time.

TIME-controlled switches have been with us for many years for switching electric lighting in streets, central heating in homes and offices and in their most complex form as sequence programmers for industrial machinery and such mundane things as washing machines. The original time-switches were run by clockwork with an eight-day movement which meant that, for instance, a council employee had to tour all the streets in the area once a week to rewind all the movements. This type of switch was soon replaced with an electric movement which, although more expensive initially, soon paid for itself in the saving in manpower and in its accuracy.

Most electric time-switches used today have a synchronous motor tied to the mains frequency thus giving very accurate long term stability and requiring little in the way of servicing except after power cuts! One of the major problems left with this type of unit is the fact that the setting or repeat accuracy of the switch itself relies on a cam attached to a drive shaft which rotates once every 24 hours and contacts with switches set on the circumference of the 'dial'. As the dial has a circumference of about 250 mm at most this means that in a 24-hour cycle each hour is represented by some 10mm of movement and thus each minute is represented by something like 0.15mm. On a high quality switch these tolerances could be met and probably bettered but on a mass-produced item the resulting accuracy means that the time switch can only be set to within about 5 minutes of the required time.

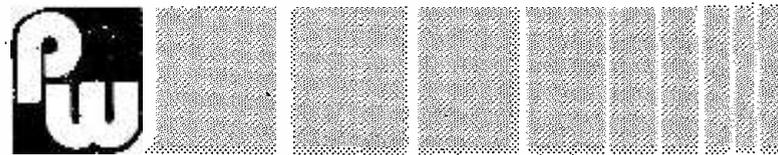

24-HOUR DIGITAL CLOCK

with
**PRECISION
TIME SWITCH**

J. MILLER-KIRKPATRICK



W475


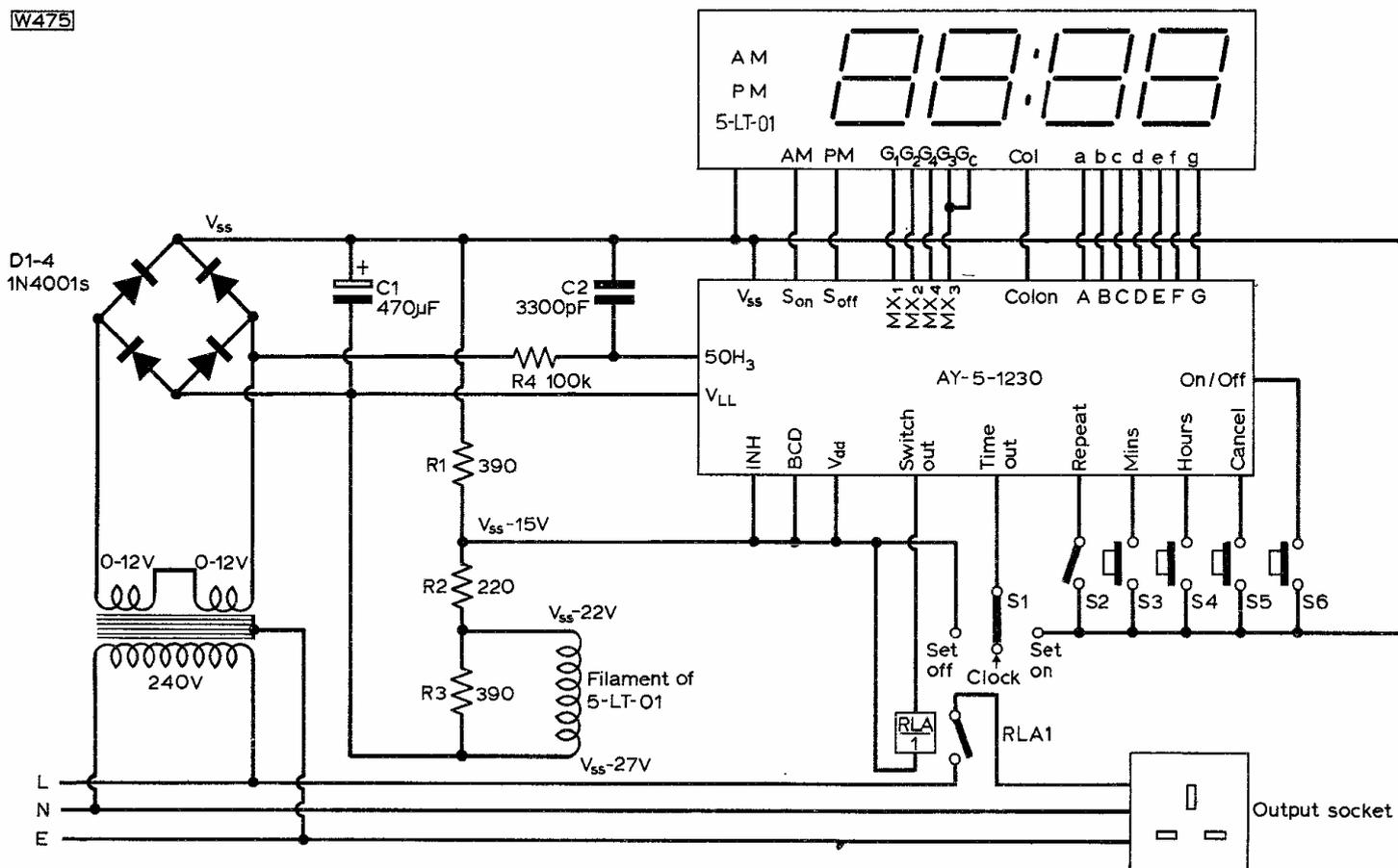


Fig. 1: Circuit diagram. The IC pinout is given on page 209.

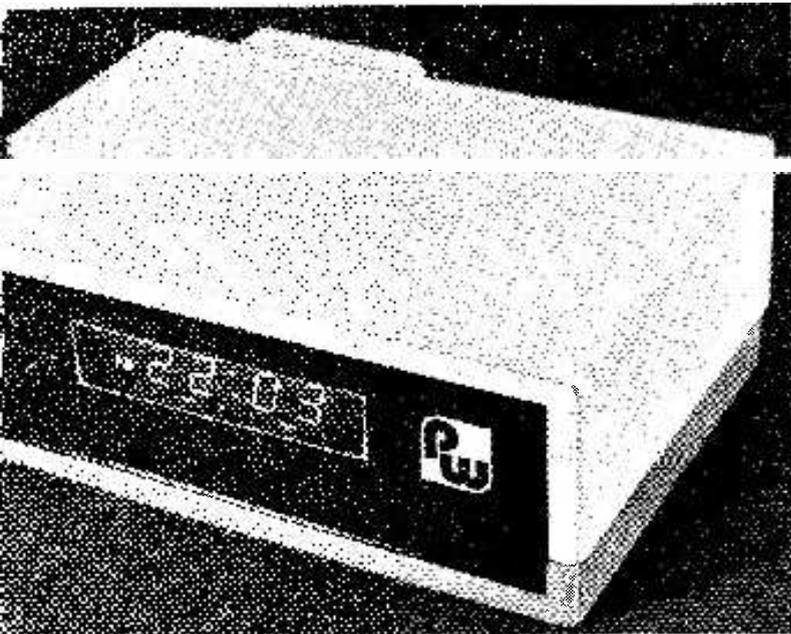This project combines an attractive digital clock with a high accuracy 24 hour timer capable of switching 500W AC. For easy construction the bright fluorescent display mounts directly on the PCB.



In industrial machinery and even in some household appliances such as washing-machines and ovens the switching of the various internal motors and other functions is controlled by dedicated TTL circuits or even microprocessors. This, coupled with quartz crystal timing if required, gives rise to equipment which can be switched on or off at any time during a 24 hour cycle (or even longer) with an accuracy of better than 1/1000th of a second. Although this sort of equipment is probably within the design ability of a lot of readers the applications and high cost would limit the interest.

With the advent of electronic digital clocks the method of timekeeping in many households has now changed from the 'quarter to two' approach to the potentially more accurate '13:43'. Some of the alarm clock chips could be modified to operate as a time-switch with an accurate "turn-on" time but, with only one alarm comparator, the "turn-off" time could not be similarly set (unless two alarm clock chips were used in parallel with the associated problems of synchronising the two chips). The CT7001 clock chip includes an alarm and an elapsed time alarm, these two functions could be linked to give an accurate turn on time and an accurate elapsed time up to a maximum of about ten hours, however, the elapsed time counter has to be set each time it is required and would not repeat in the following 24 hour cycle.

General Instruments have released the AY-5-1230 digital clock chip with a switched alarm output which comes on at the time set in the "on-time" register, goes off at the time set in the "off-time" comparator and also operates as a 24 hour, four digit, clock.

Circuit description

The circuit diagram of the unit is given as Fig. 1.

The transformer drops the mains voltage to about 24 volts which is rectified to DC by diodes D1 to D4 and smoothed by capacitor C1. The resulting voltage across C1 should be within the range 24V to 30V and capable of delivering 100mA. The positive side of C1 is referred to as Vss and all other voltages are referred to as negative with respect to Vss.

If it is assumed that the voltage on C1 is 27V then, under no load conditions, the potential divider chain R1, R2, R3 gives Vss-12V, Vss-18V and Vss-27V. When the load of the chip and the filament of the display are taken into consideration the resulting voltages are nearer Vss-15V, Vss-22V and Vss-27V.

The Vss-15V line is connected to the Vdd input of the chip and with a 50Hz signal being taken from the transformer, via limiting and shaping components C2 and R4, the chip will start to operate. An internal multiplexing oscillator starts to run and sequentially selects the data in the display registers for each digit in turn and presents that data on the segment outputs at the same time as turning on the appropriate digit drive. The data for the next digit is then selected and presented at the outputs and the next digit drive is turned on. The speed at which this happens when connected to the display is too

★ components list

Resistors

R1	390Ω 5% ½W.
R2	220Ω 5% ½W.
R3	390Ω 5% ½W.
R4	100kΩ 5% ½W.

Capacitors

C1	470μF 50V.
C2	3300pF disc ceramic.

Semiconductors

IC1	AY-5-1230 G.I. (Metac, Bi-Pak or Watford Electronics)
D1 D2 } D3 D4 }	1N4001

Switches

S1	SPDT, centre-off
S2	SPST, sub-miniature
S3 S4 } S5 S6 }	miniature push button, one pair normally open contacts, non-latching action

Display. Phosphor diode, 5-LT-01, Futaba, (Metac or Watford Electronics)

Miscellaneous.

T1, mains transformer, 24V at 250mA secondary, (MT150) fixing centres 60mm. Case 205mm × 75mm × 140mm, (8" × 3" × 5½"), Vero code 75/14112. Front plate, 198mm × 69mm × 2mm, perspex, red or clear. PCB from Readers PCB Service. Output socket to suit use.

fast for the eye to follow and a continuous four digit display is seen.

The AY-5-1230 has facilities for BCD, seven segment and blanked output. In this project the BCD and blanking (INH) inputs are connected to V_{dd} to give a seven segment output at pins a-g.

The chip is designed to allow it to interface directly with fluorescent (Phosphor-diode) displays. This type of display has a heater which acts as the cathode with the segments being the anodes. Between the two are grids connected to each digit drive.

Display

To light any one segment both the segment drive and the digit drive grid must be at least 15 volts positive to the centre voltage on the filament. In this circuit the centre voltage on the filament is V_{ss}-24.5V and the segment and digit drives switch to V_{ss} to turn on, thus the voltage differential is 24.5 volts. When in the off condition the chip outputs would normally switch to V_{dd} which is V_{ss}-15V. This would result in a voltage differential on the display of about 9 volts and could result in the segment remaining lit. For this reason the chip outputs are internally connected via resistors to a common line referred to as V_{LL} which is connected externally to the negative side of the heater. This ensures that the chip outputs switch off to V_{ss}-27V giving a display differential of zero volts and thus extinguishing the off segments.

The display includes two indicators for AM and PM which cannot be used with this chip (it does not have AM/PM outputs since they are unnecessary on a 24 hour display). The chip does have two output indicators which show that either or both ON and OFF times have been set, and, to save costs, these are connected to the AM/PM indicators on the display.

An alternative is to use two LEDs, as shown in Fig. 2, with the current limiting resistors mounted on the PCB. On the prototype provision was made for these diodes on the back panel but it would probably be more convenient to mount them on the front.

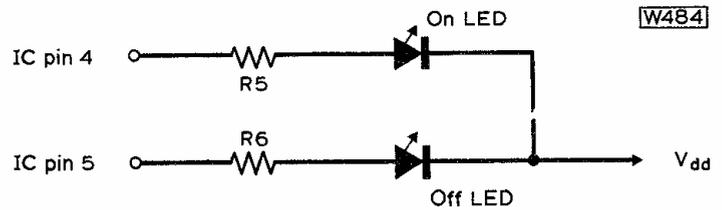


Fig. 2: Alternative alarm status indicator.

The switched output from the chip can be used to drive a relay of the type specified direct. Before using any other type of relay check that the operat-

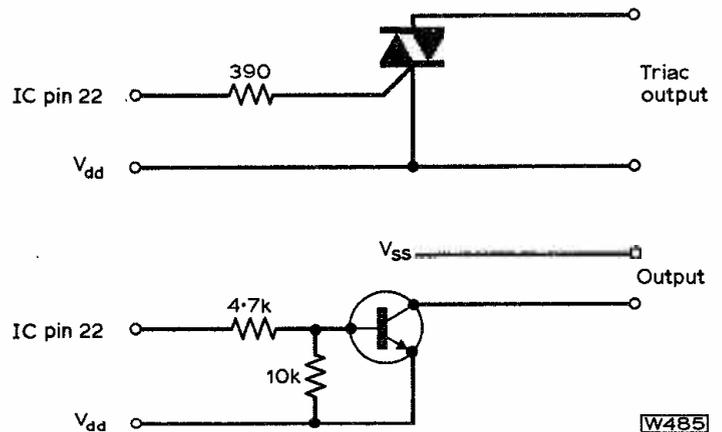


Fig. 3: Alternative alarm output circuitry.

ing current of the relay does not exceed 30mA at 15V. Other switching systems can be used as shown in Fig. 3.


Construction

Construction is reasonably straightforward but two points are worth extra attention.

First, use standard MOS handling procedures with the clock chip.

Second, beware of the mains on the board. The relay specified has its metal body connected to the centre contact of the change-over set. If the mains is being switched it will appear on the body of the

Fig. 6: Rear plate drilling details.

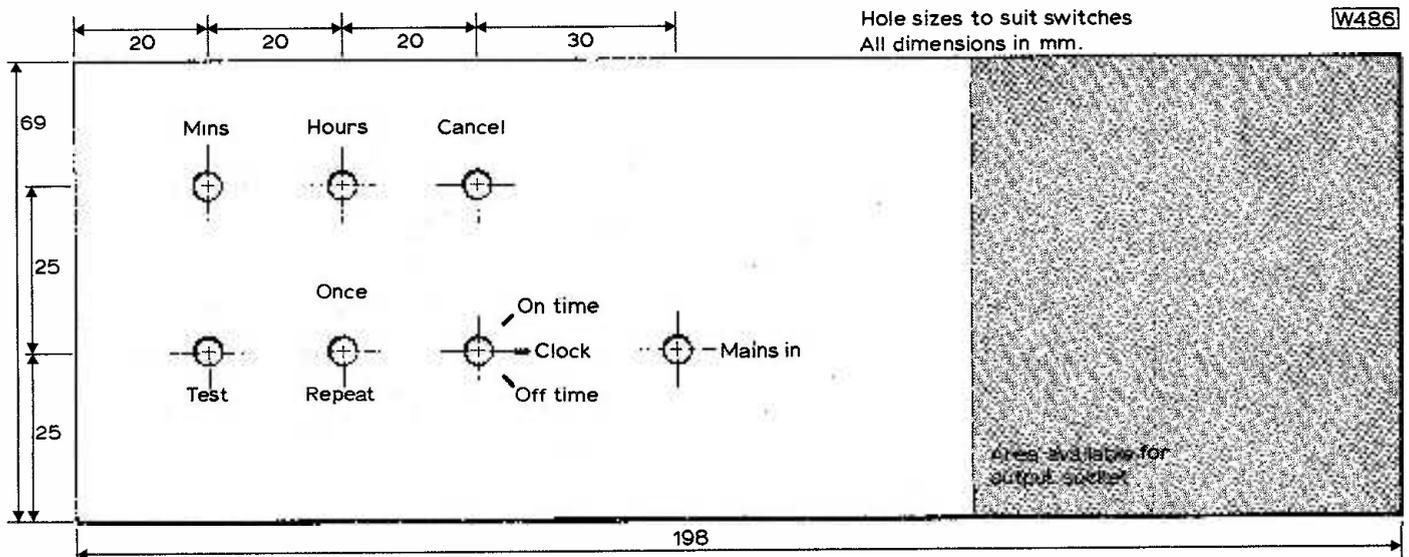

Hole sizes to suit switches
All dimensions in mm.

W486

relay. For this reason the track linking it to the mains has been broken and a link inserted. Leave the link out until the preliminary testing has been completed.

Similarly the mains is carried by tracks on the board and it would be better if these tracks are painted with enamel paint or several coats of shellac.

The single PCB used is shown as Fig. 4 and the component locations as Fig. 5. Start the assembly with the transformer, resistors R1, R2 and R3, diodes D1, D2, D3, and D4 and capacitor C1. This will allow the power supply to be checked before the more expensive components are fitted. The voltage readings should be similar to the unloaded figures given earlier.

Assuming the power is correct the remaining components can be inserted (not the link to the relay) and the switches mounted on the rear panel. (see



Fig. 6). The use of a socket for IC1 is strongly recommended. If separate LEDs are used on the front panel, leave the leads fairly long.

Do not assemble the board, front and rear panel into the box at this stage.

Testing

When switched on the display should light up and show 00:00 which is that shown after a power failure. This display will not change until the advance buttons are pressed even though the clock chip is functioning correctly. If the display is correct the remainder of this section can be ignored. If it is not correct then the following checks can be made.

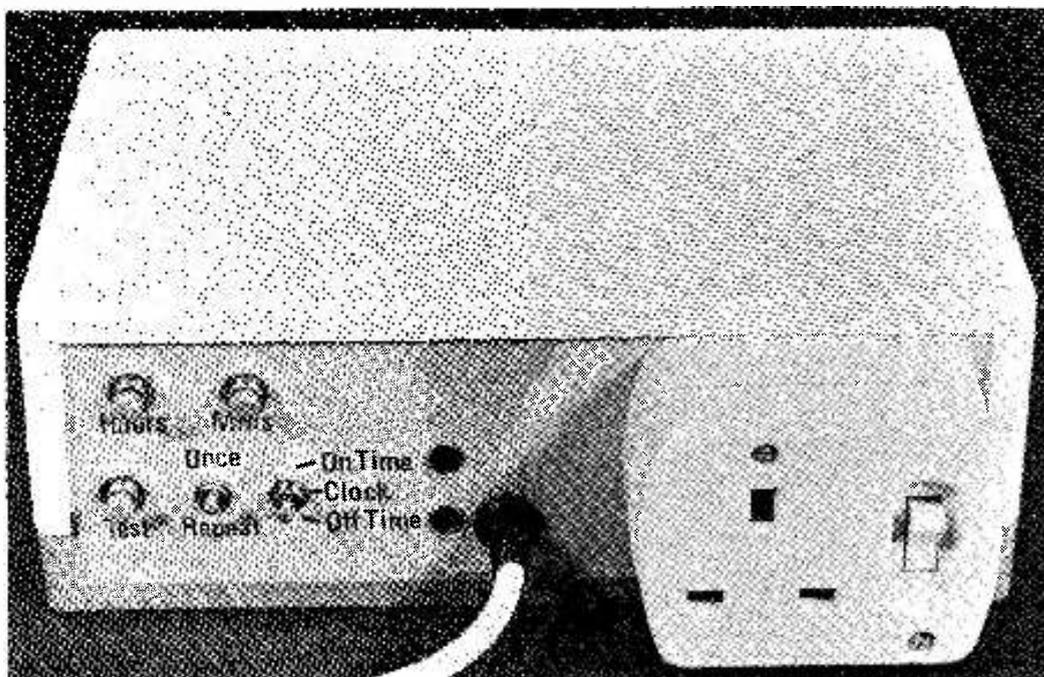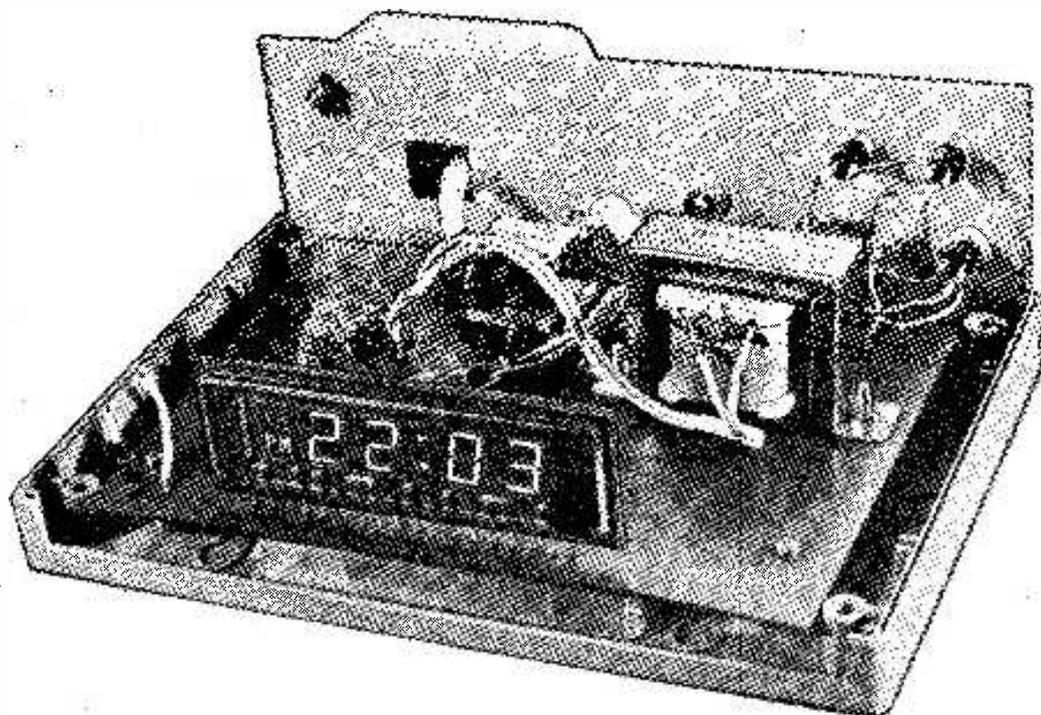The prototype was built using a single PCB for mounting all the major components. Since the board carries mains wiring, great care must be given when assembling this area. Remember to earth the frame of the mains transformer by using an external wiring strap.



Particular consideration should be given to the handling and soldering of the display strip. Prolonged and excessive heat will crack the metal/glass seal inducing terminal damage. Similarly when handling/soldering the IC, the usual anti-static precautions should be observed.

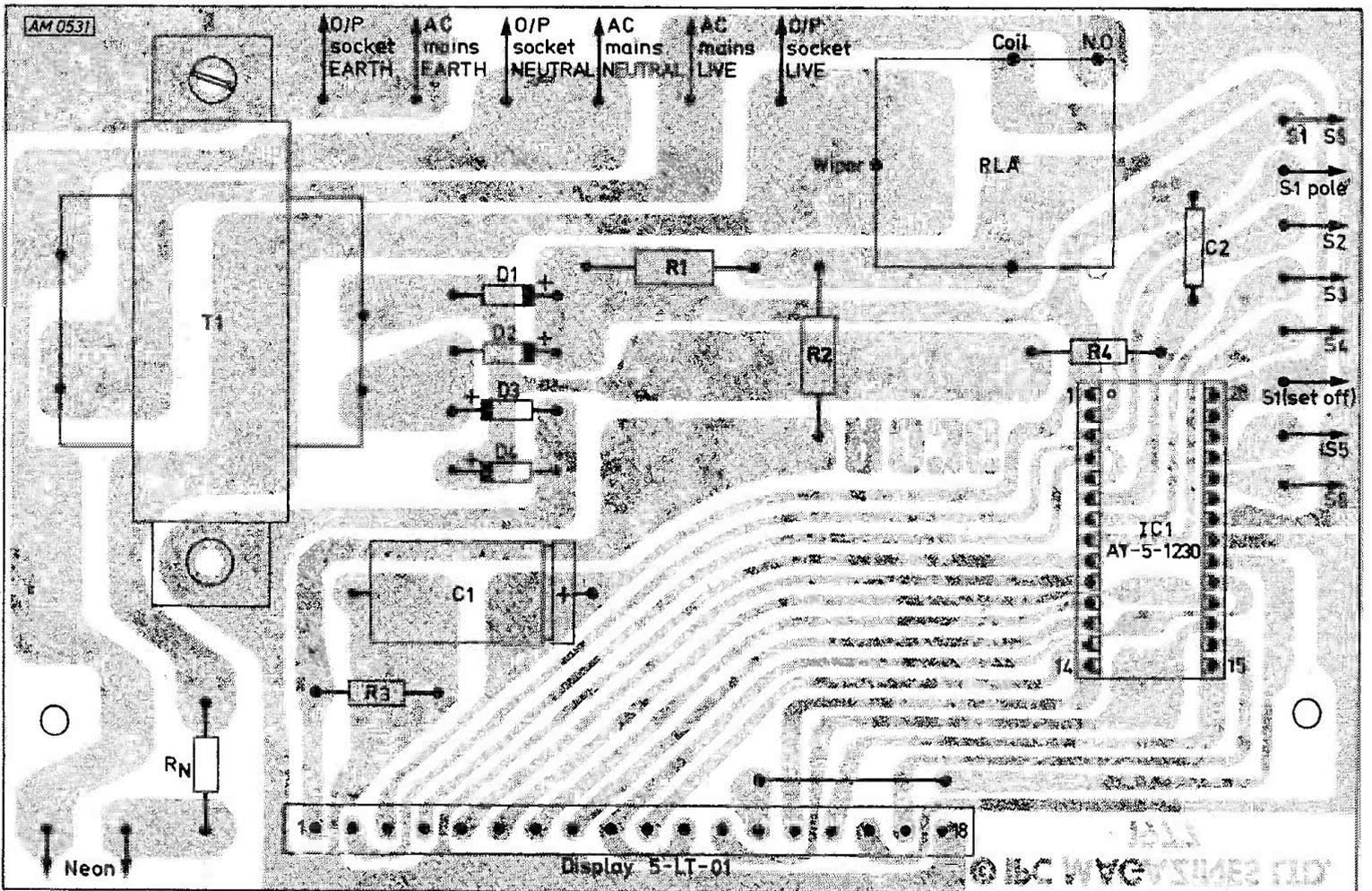
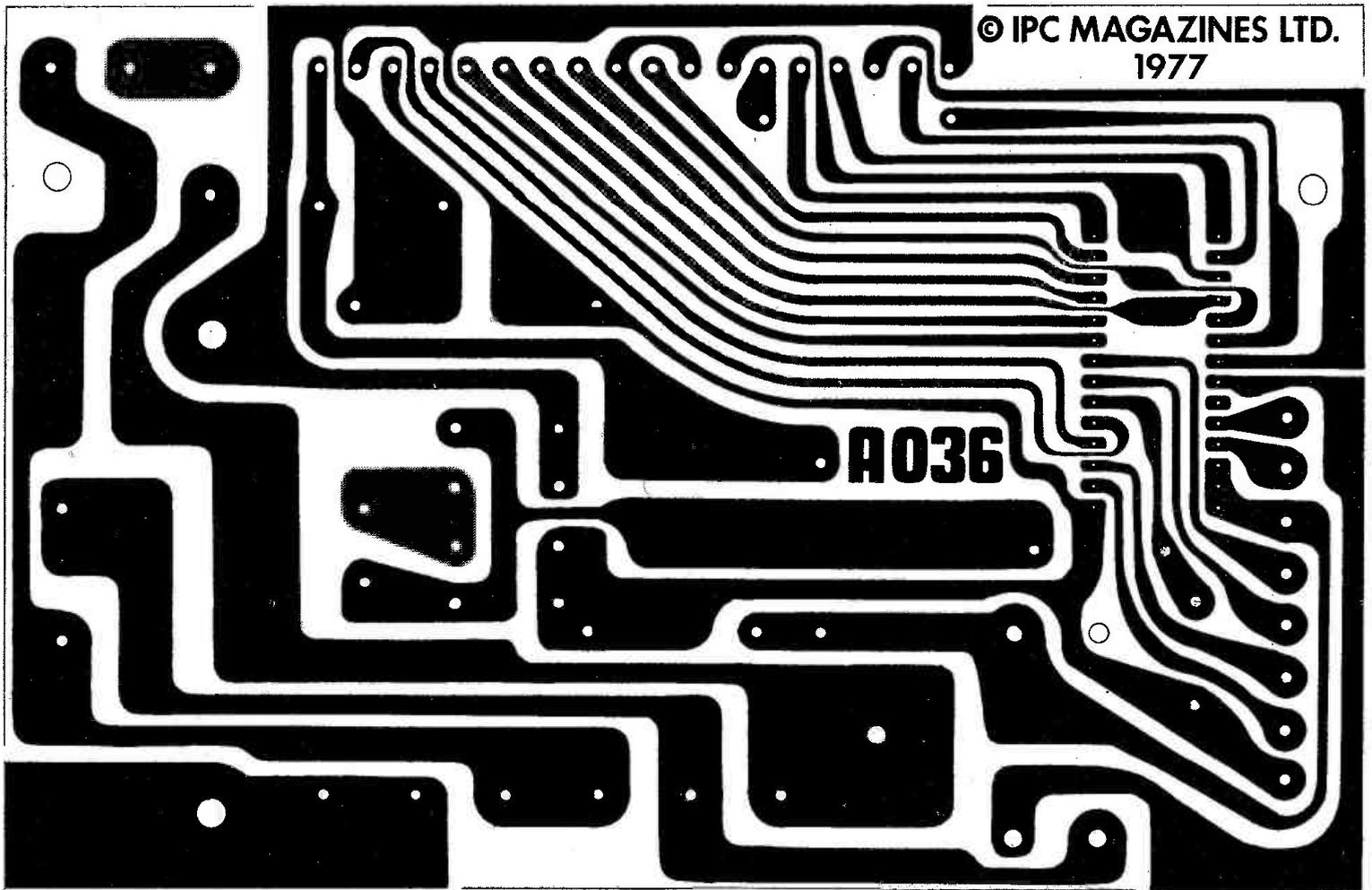


Fig. 4 (above): PCB shown actual size—copper side.
Fig. 5 (below): PCB component side showing locations and leadouts.

1. Switch off. Remove the IC from its socket (put it in its conductive foam) and switch on again. Do not attempt to remove the IC with the power on. The result is almost certain destruction of the device.

2. Measure the voltage between pins 1 and 26 on the IC socket. It should be about 15V.


3. Measure the voltage across the filament of the display. It should be about 5V.

4. Check that pin 28 is connected to Vdd.

5. Check that pin 23 is not connected.

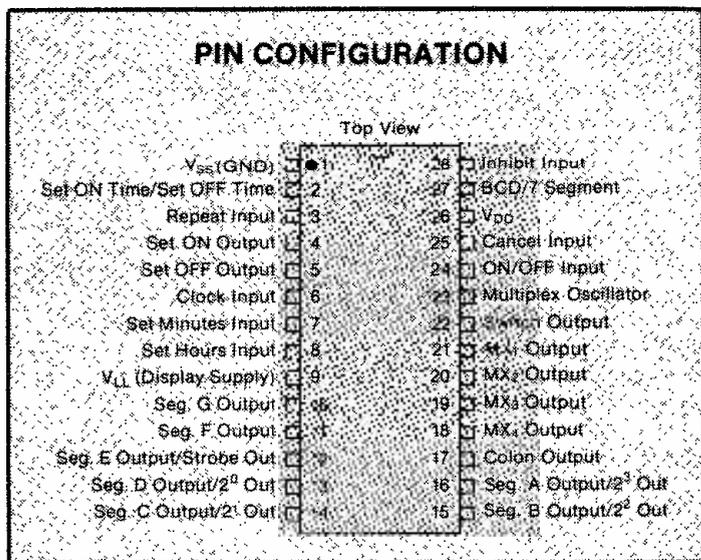6. Check the individual segments of the display as follows, connect pin 18 (the minutes digit, Mx4) and pin 10 (segment G) to Vss. The segment should light. Repeat the other segments on the minute digit, one at a time (pins 11, 12, 13, 14, 15 and 16), then repeat for the 10 minute digit, the hours and 10 hour digits.

If these tests are satisfactory the only remaining area of malfunction is the integrated circuit. Before discarding the IC try it again but ensure that it is inserted correctly. If it still doesn't work, replace it with another.



Setting up

When a suitable display has been arrived at the following procedure should be carried out.

1. Set the switch for setting the 'on' time, 'off' time and 'clock' (S1) to its middle position.

2. Push the 'hours' set button (S3) and hold closed. The hours counter should advance and the colon should start flashing. Set the hours to read 23.

3. With switch S2 set the minutes to 50. (ie. time reads 23.50).

4. Put S1 to the 'set time on' position. The display should read 00:00. The 'time on' indicator (AM or LED) should also light.

5. Use S2 and S3 to set up 23.55.

6. Switch S1 to 'time off'. The display should read 00:00 again and the 'time off' indicator should light (PM or LED).

7. Use S2 and S3 to set up 23.57.

8. Return S1 to 'clock'. The display should have moved on to something like 23.53.

9. At 23.55 the relay should close. This can be checked by observation or with a meter on Ohms.

10. The relay should open at 23.57.

11. Put S5, the 'repeat/once' switch, to the 'repeat' position and advance the clock to 23.55. The relay sequence should repeat.

12. Put S5 to 'once' and again advance the clock to 23.55. The relay should repeat its sequence but the 'set on' and 'set off' indicators should go out.

13. Advance the clock to 23.55. This time the relay should close. Push the switch a second time and the relay should open again.

15. Set any time into the 'on' and 'off' memories and then push the cancel switch, S4. The 'on' and 'off' indicators should both go out.

Having completed the tests satisfactorily the remaining items can now be added including the link to connect the relay switch to the mains input and the connections to the output socket made before final casing up. If required a neon can be connected to the relay output and mounted on the front panel of the case to show that the output circuit is operational. The current which can be taken from the output socket depends on the type of relay used but in the prototype was about 2A maximum.

Options

The basic operation of the clock is outlined in the setting up section but with the following notes:—

1. If an 'on' time is set without an 'off' time the output will stay on for ten minutes then turn off.

2. S6 will change the state of the output each time it is pressed.

3. 'Repeat' will cause the output to switch every day, 'once' will reset the logic after the first operation.

4. Cancel will reset the switch logic to 00.00 when pressed.

Options which can be added easily are a tone alarm output at turn time and display dimming con-


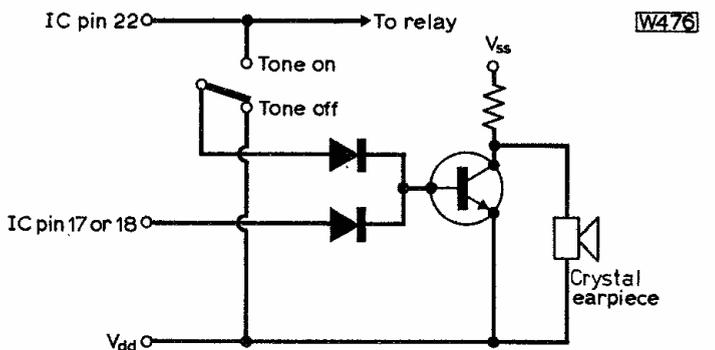


Fig. 7: Above, Fig. 8: Below.

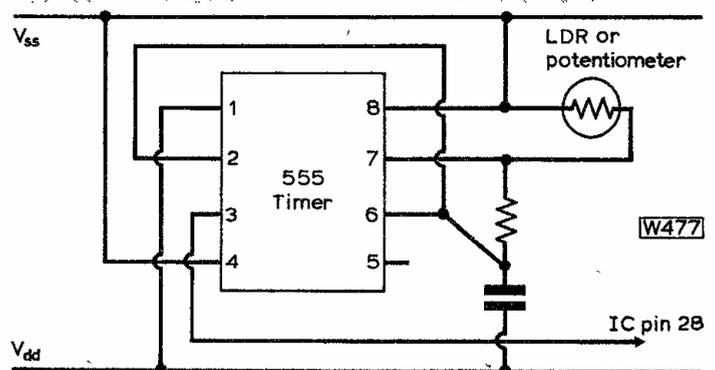

trol (Figs 7 and 8). If a battery operated device is to be switched then this unit could also include a battery eliminator.

PRODUCTION LINES

bill tull



What are the drawbacks to portable emergency lighting? Well, there are several, possibly the most important being the cost, or if we're talking about batteries, then their comparatively short shelf life which means they have to be discarded after a certain time even if they have never been used. Also few systems are completely waterproof (i.e., they can even work UNDER water), are safe to use in or around ignitable vapour, have a shelf life of around four years, and most important of all are very cheap.

Not feasible, do I hear some sceptics say? Prepare to eat your words! A US company has recently invented a device, called a "Lightstick", which tends to make all other forms of portable emergency lighting obsolete. Looking much like a candle and about 5 inches long, the lightstick is activated by bending which allows a chemical action between two liquids sealed inside the plastic tube to take place, and thereby create light.

Claims put forward by the company say that the lightstick will illuminate an average room and give sufficient light for reading, making telephone calls, repairs to equipment, or just generally finding your way about in the dark. Once activated the lightstick will emit light for 10 hours, and since it generates light without heat or

Light years ahead



flames is suitable in potentially dangerous situations where petrol or gas is concerned. The liquid can also be poured out of the tube (once the tube has been cut) and poured over an object to illuminate it. The colour of the light is a green/yellow and can be seen up to 1 mile away.

Initially supplies of Lightsticks will only be available from the sole UK distributor and usually in bulk only. However, by the late autumn of this year they should be in all the shops priced at £1.95 for a pack of three.

Tye Security Ltd., Dolphin Road North, Sunbury-on-Thames, Middlesex.

Music maker

Electronic pianos have come and gone with monotonous regularity since their birth some years ago. They have 'gone' primarily because they just don't have the sound, and more importantly, the 'feel' of a good quality conventional piano. For this reason the market has been eagerly awaiting the new chip which has been the

centre of rumours for some time now, and proposes to put an end to the inherent faults found in earlier electronic pianos.

The manufacturer to be first with this new chip is General Instruments Microelectronics, Glenrothes, whose new device—the AY-1-1320 is claimed to 'simulate the sound and touch of hammer action instruments'.

Unlike electronic organs the electronic piano incorporates circuitry which senses the key velocity as the pianist strikes each note, adjusts the output volume accordingly and

produces a note which decays in amplitude in a similar manner to a hammer action instrument. Adjustment can be made to simulate the Honky-tonk piano, Harpsicord and the Clavicord.

The AY-1-1320 incorporates 12 separate envelope generation circuits for octave tones and semitones. Thus a five octave instrument would require no more than five 40pin DIL devices of this kind.

General Instrument Microelectronics Ltd., 57/61 Mortimer Street, London, W1N 4TD.

Get kitted out

Doram Electronics, the general public's branch of RS Components, have recently announced seven new constructional kits to complement their already growing selection in this particular field.

The kits include a quadrasonic resolver to give the effect of surround sound by connecting an existing stereo system to four speakers; a 25W per channel stereo amplifier, called "The Audiomaster", and a phase-locked-loop stereo decoder. The price for these kits, which incidentally are absolutely complete down to the last nut and bolt, are




£9.95, £82.50 and £4.45 respectively plus VAT at 12½%.

Also in this new range are two test equipment kits comprising a 3½ digit multimeter (100µV to 1000V AC or DC, 100µA to 2A plus resistance) and a matching digital frequency counter which reads from 10Hz to 50MHz. Each kit is complete with case, PSU and full instructions. Both models are priced at £54.50 plus VAT at 8%.

The final two kits are of special interest to the DIY enthusiast, with an accurate ignition timing light utilising a Xenon flash and automatic polarity selection, and a transformer kit which has everything a constructor

needs to wind his own 50VA transformer. Price for these two kits is £18.95 and £4.18 respectively. Both plus 8% VAT.

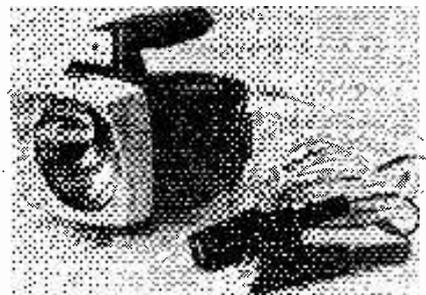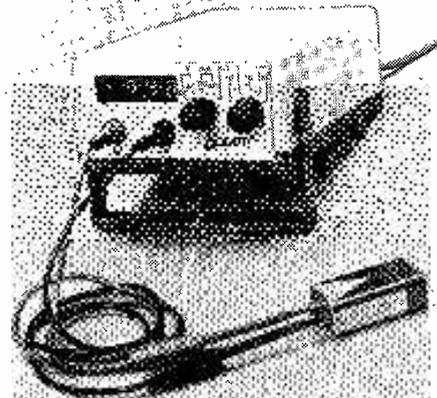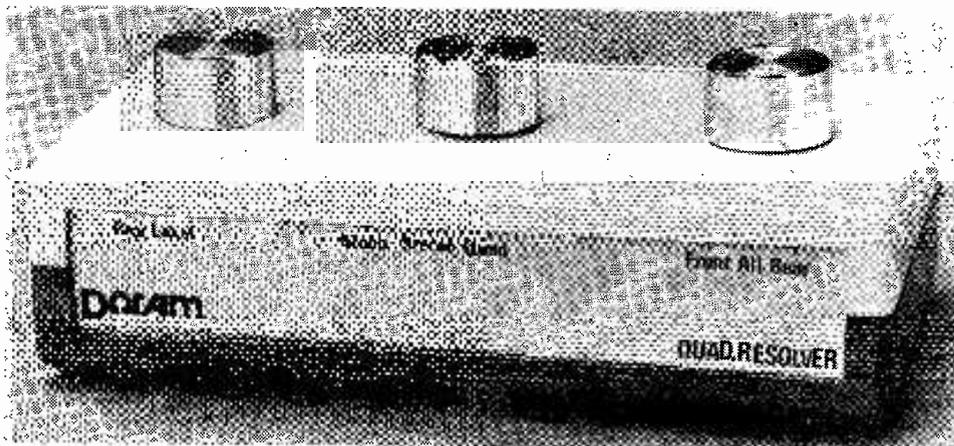Doram Electronics Ltd., PO Box TR8, Wellington Road Industrial Estate, Wellington Bridge, Leeds LS12 2UF. Tel: 0532 452548.



Morning time


Come on, be honest, who doesn't have trouble in getting up in the mornings—specially winters mornings. The answer of course is a clock radio such as the new Philips AS460, with LED display, AM/FM radio and a list of added extras as long as your arm.

One of the novel extras included is an automatic function that allows the display to dim in a darkened room, another is a "Slumber facility", which allows the set to be operated for a period of up to 59 minutes before switching off automatically. With ordinary alarm clocks, once the alarm

has been switched off, it stays off, but with the AS460 a touch sensor is used to switch the alarm off, but will automatically sound again in approximately nine minutes. This will happen up to five times, by which time Philips reckon that you'd get up just to get away from the alarm.

Aerials are built in for both AM and FM, there is a choice of either buzzer or radio to wake you up, and if there is a power failure the display flashes to indicate incorrect time.

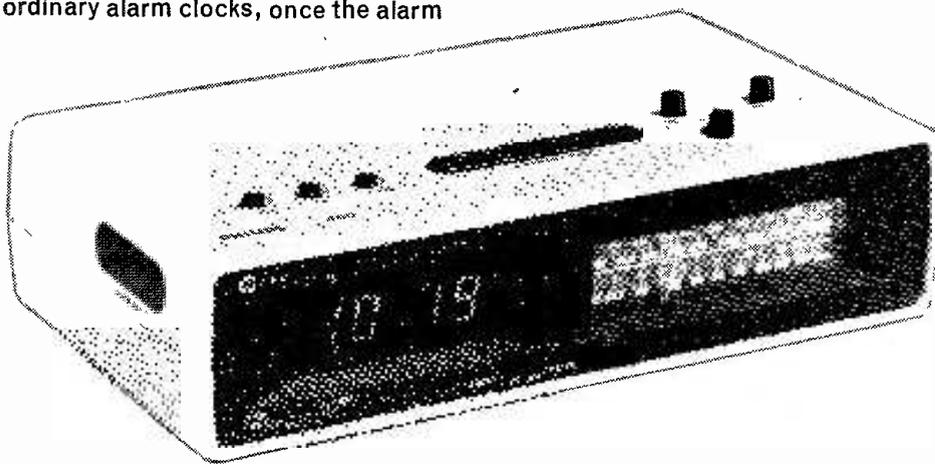Philips Electrical Ltd., Century House, Shaftsbury Ave., London, WC2H 8AS. Tel: 01-437 7777.



Practical Wireless, July 1977

Amateur chips

Two new low power IF/AF circuits designed for NBFM receiver applications, such as mobile and handheld radios have now become available from Plessey Semiconductors.


Notated the SL 664 and SL 665, each circuit is a complete IF strip and consists of a pre-amplifier, limiting amplifier, quadrature detector, carrier squelch, DC volume control and audio output stage. The SL 664 incorporates a power output stage (250mW into 8ohms), while the SL 665 has a low level audio output which drives high impedance loads (open collector output). The demodulator and audio amplifier are muted by the squelch output on the SL 664, whilst on the SL 665 the squelch output does not internally mute the demodulator, which means that it can be used for tone decoding.

Both devices are in ceramic DIL packages, but the SL 664 has 18 pins and the SL 665 has 16 pins.

Plessey Semiconductors, Cheney Manor, Swindon, Wiltshire, SN2 2QW. Tel: Swindon (0793) 36251.

Zip dip

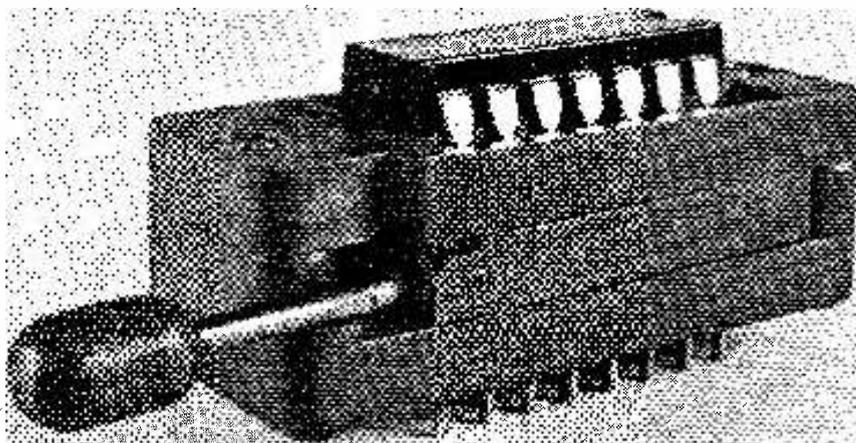A new range of integrated circuit sockets, for use in test equipment or development "breadboards", has been introduced by BFI Electronics Ltd. Called the ZIP DIP range, the sockets accept multi-lead devices with no insertion pressure, thus eliminating lead damage and distortion which often occurs when leads are forced into sockets operating on the spring contact principle.



The ZIP (Zero Insertion Pressure) DIP socket has a tiny lever at one end which is connected to an internal cam. A multi-lead device is simply dropped into the socket and the lever flicked up to positively clamp the leads inside the socket. This protects the leads from damage and ensures a good electrical connection. When the lever is released the device may be removed without force.

BFI Electronics Ltd., Sinclair House, The Avenue, West Ealing, London W13. Tel: 01-998 2113

10 watt amp.

Very often a small audio amplifier is all that is required to complete or repair a record player or radio etc. Not one that claims ultra HiFi specifications, but one that is adequate for good, clear audio reproduction and is compact in size. Module amplifiers usually satisfy this need, and the new one from Bi-Pak—the AL 30A is said to deliver 10W RMS into an 8 ohm load with a supply voltage of 28V.

The total circuit, which measures $90 \times 64 \times 27\text{mm}$, is contained on a single board with the power tran-



sistors attached to a small heatsink. The manufacturers recommend that for speech and music applications a total heatsink area of 10 sq.in. be used, and for higher power applications 15 sq.in. These figures are for mono use and should be doubled if two modules are used for stereo reproduction.


Input sensitivity is 90mV for full output, while frequency response is claimed to be from 60Hz to 25kHz. The cost, when they become available will be £3.60 each, and they can be obtained from *Bi-Pak Semiconductors, The Mallings, 63a High Street, Ware, Herts. Tel: Ware 3442.*

New chips for old

That old faithful, the 741 Op-Amp is shortly to become redundant. The successor to this device has recently been introduced by Mogul Electronics and is manufactured by Texas. Available in either single, dual, or quad BIFET modes, this new Op-Amp can be obtained in 8 pin TO99 as well as 14 pin DIL packages and is capable of operating over a temperature range of -55°C to $+125^{\circ}\text{C}$.

A few of the parameters of this new Op-Amp family, designated the TL080-4 includes an input impedance of 10^{12} ohms, supply current of 2.8mA, slew rate of $12\text{V}/\mu\text{S}$, low input bias and offset currents of down to 0.2nA and 0.1nA respectively and a frequency bandwidth of 3MHz.

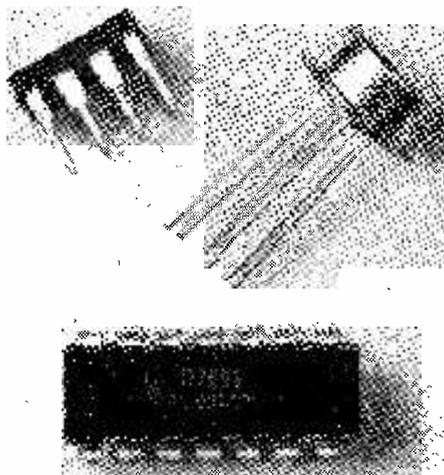Mogul Electronics Ltd., 273 High Street, Epping, Essex, CM16 4DA. Tel: 0378 77366.



Power module

Audio power Modules, made by *SANKEN*, are available in three models. Very few external components, a heatsink, and a power supply, are all that are required to complete a high quality (harmonic distortion 0.5% Max.) sound system.

Ideally suited to Hi-Fi systems, tape deck, FM tuners, record players, etc., each module has quasi-complementary class B output, and uses flip-chip transistors in a rugged, compact, lightweight package. The three modules comprise the SI-1010G (10W),

SI-1020G (20W) and the SI-1050G (50W).

Further information from *Rastra Electronics Ltd, 275-281 King Street, Hammersmith, London W6. Tel: 01-748 3143*



A Radio 2 Tuner FOR YOUR HI-FI

R.A.PENFOLD

MANY hi-fi tuners and receivers are fitted with an AM section and although this is not a source of true hi-fi signals it is a very practical facility. It removes the necessity for a separate set for listening to sports commentaries, Radio Luxembourg, and other programmes which are not available at VHF.


Unfortunately, a surprisingly large number of tuners and tuner/amplifiers do not provide coverage of the long wave band and cannot receive Radio 2 on 200kHz (1500 Metres). There are frequent occasions when such sets are unable to receive Radio 2 at all, because the Radio 1/2 VHF transmitter is devoted to Radio 1 transmissions. For instance, at the time of writing, this happens late most evenings.

The obvious solution to the problem is to construct a LW Radio 2 tuner unit to feed into an unused input of the amplifier. The author has built such a unit to feed the 'Aux' input of his Rotel RX254 tuner/amplifier and it is this simple tuner unit which forms the subject of this article. The unit can be used successfully with most amplifiers since it has an output amplitude which is adjustable from zero to about 2V peak to peak and the source impedance is fairly low at approximately 5kΩ. It is completely self-contained with an integral battery supply and ferrite rod aerial.

DESIGN

Presumably Radio 2 is the only LW station of interest, and the circuit can therefore use pre-set tuning. Since only one station at the relatively low

frequency of 200kHz is required this is one application where a superhet circuit has no advantage over a TRF one. This may at first sight seem to be an obvious place to use a circuit based on the popular ZN414 IC but reference to the appropriate data sheet shows that this device is not at its best on these frequencies. This was borne out in practice when a simple test circuit was tried. For use at the author's location the circuit lacked both sensitivity and selectivity.

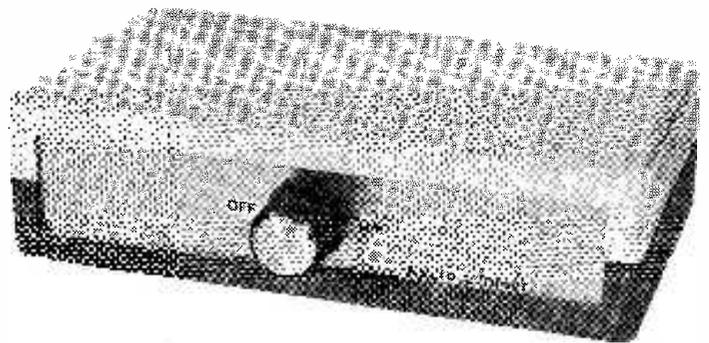

The controls on the Radio 2 Tuner are not very complicated! Just an on-off switch. The output level is adjusted by means of an internal potentiometer to suit the amplifier used with the Tuner.

The simple circuit shown in Fig. 1 was then tried and this has proved to be eminently suitable. L1 is the ferrite aerial tuned to 200kHz by means of trimmer TC1. Tr1 is used as a common source amplifier and the aerial circuit couples direct to Tr1

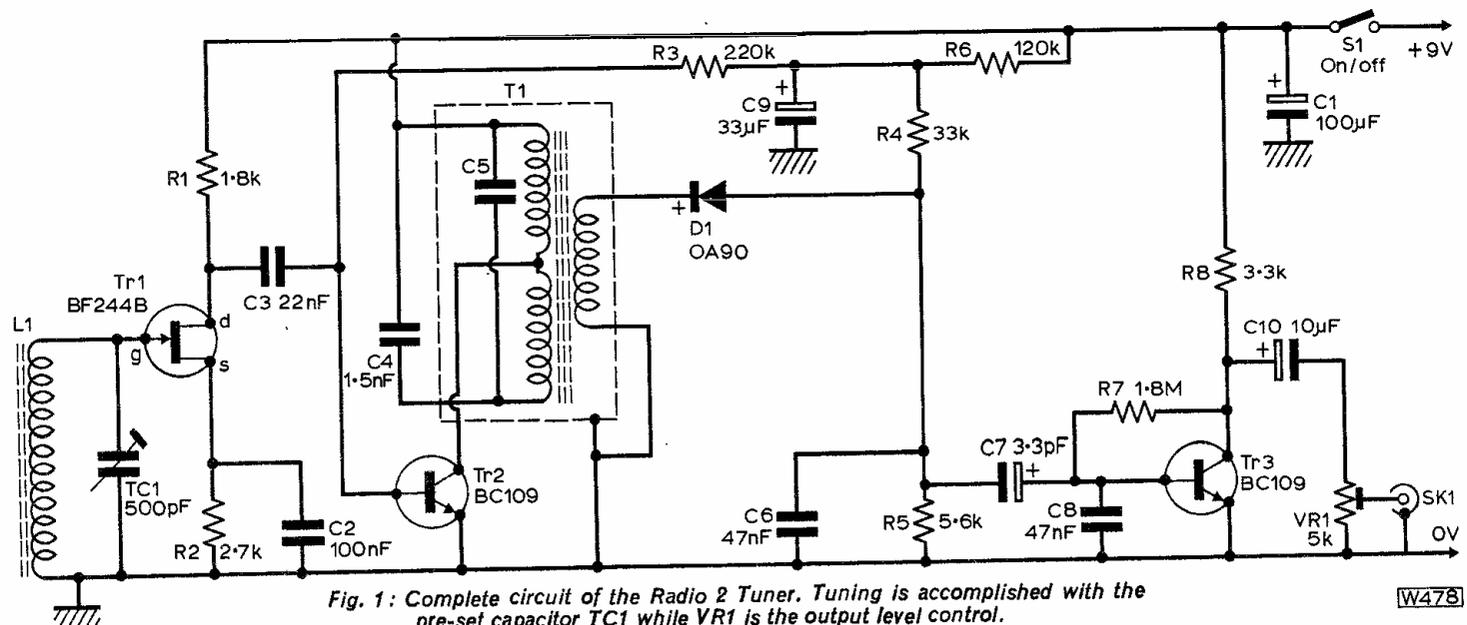


Fig. 1: Complete circuit of the Radio 2 Tuner. Tuning is accomplished with the pre-set capacitor TC1 while VR1 is the output level control.

W478


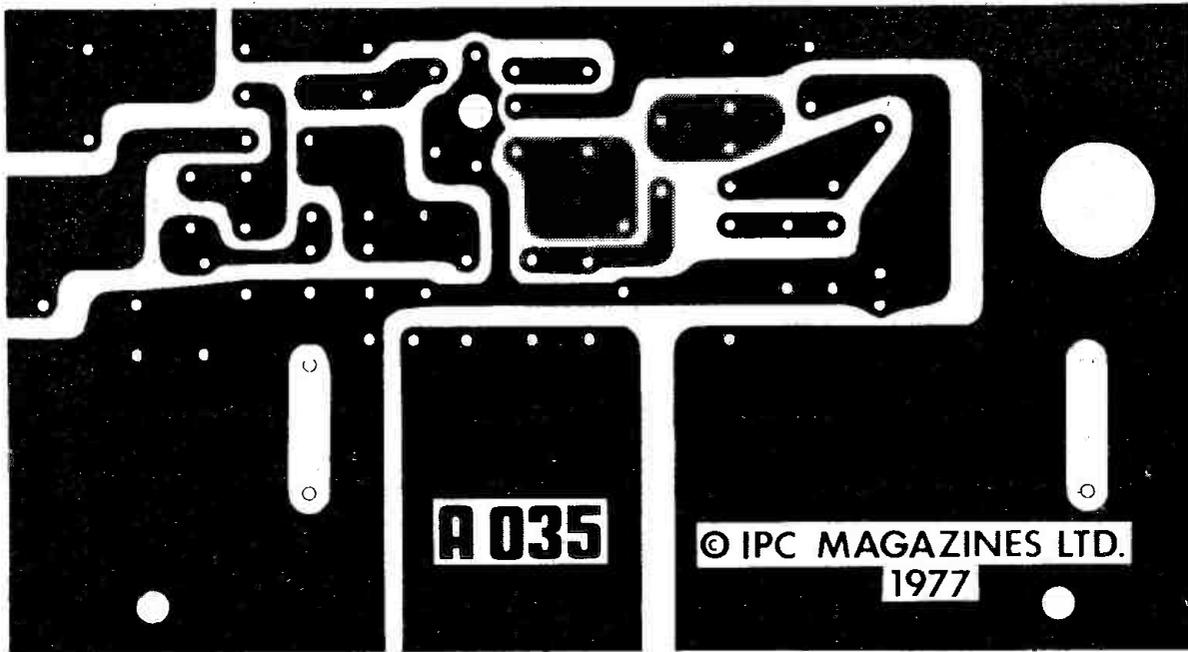


Fig. 2: Above, the printed circuit board is shown full size. Below, the PCB reversed to show the layout of the components on top of the board.

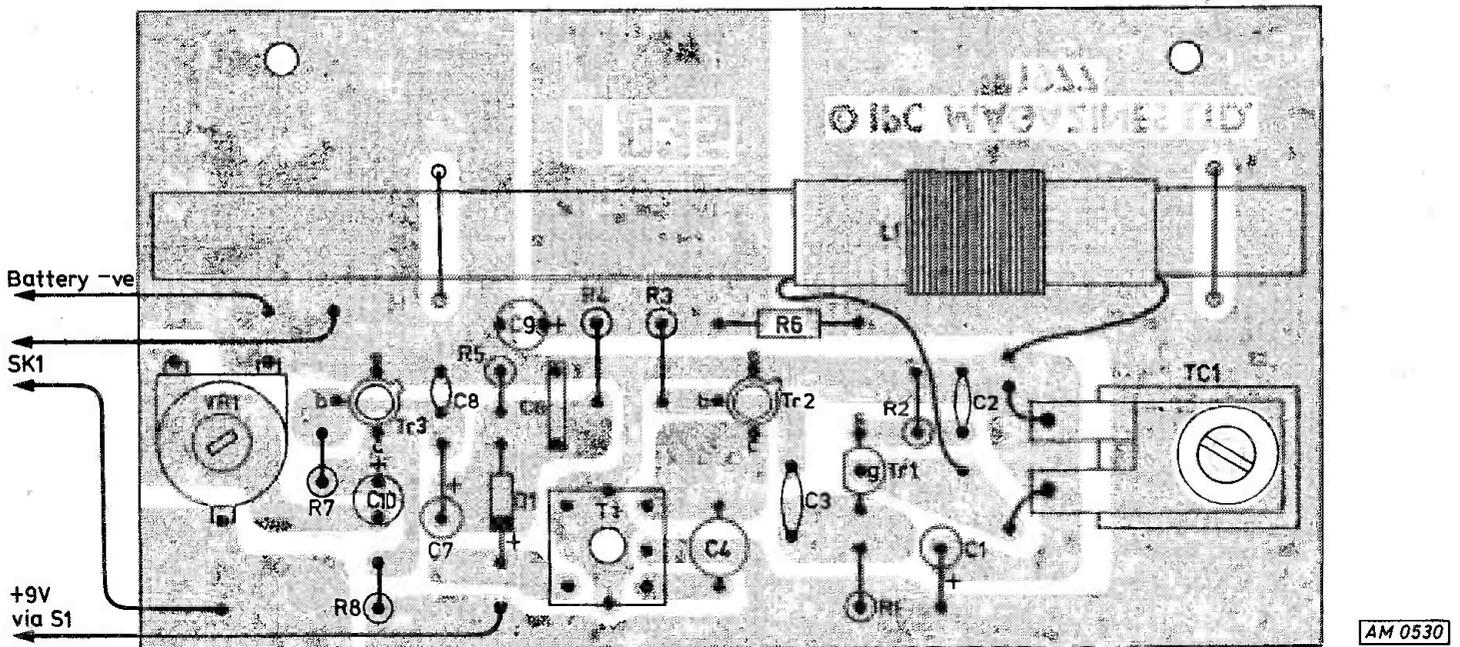


gate. This is quite acceptable as the input impedance of Tr1 is extremely high and no coupling winding on the aerial coil is necessary. R2 is the source bias resistor and C2 its bypass capacitor. The amplified output of Tr1 is developed across drain load resistor R1.

Tr2 provides a second stage of RF amplification, and used as a high gain common emitter amplifier. T1 is a 465kHz last IF transformer and C4 is connected in parallel with its internal tuning capacitor (C5) in order to reduce its operating frequency to about 200kHz. D1 is an ordinary diode detector which is fed from the secondary of T1. C6 provides RF filtering and the audio output signal plus a DC bias are produced across R5, part of a potential divider with R6 and R4, and Tr2 receives its base bias current from the junction of R4 and R6 via R3. If Radio 2 is received very strongly a comparatively

large negative bias will be produced across R5 and the voltage at the junction of R4 and R6 will therefore be reduced. This results in a reduction in the base bias current of Tr2, and in consequence its gain is reduced. This provides the tuner with a conventional automatic gain control (AGC) action, ensuring that neither the detector nor the audio stages are overloaded if the tuner is used in a strong signal area. C9 filters out the audio signal from the AGC circuitry.

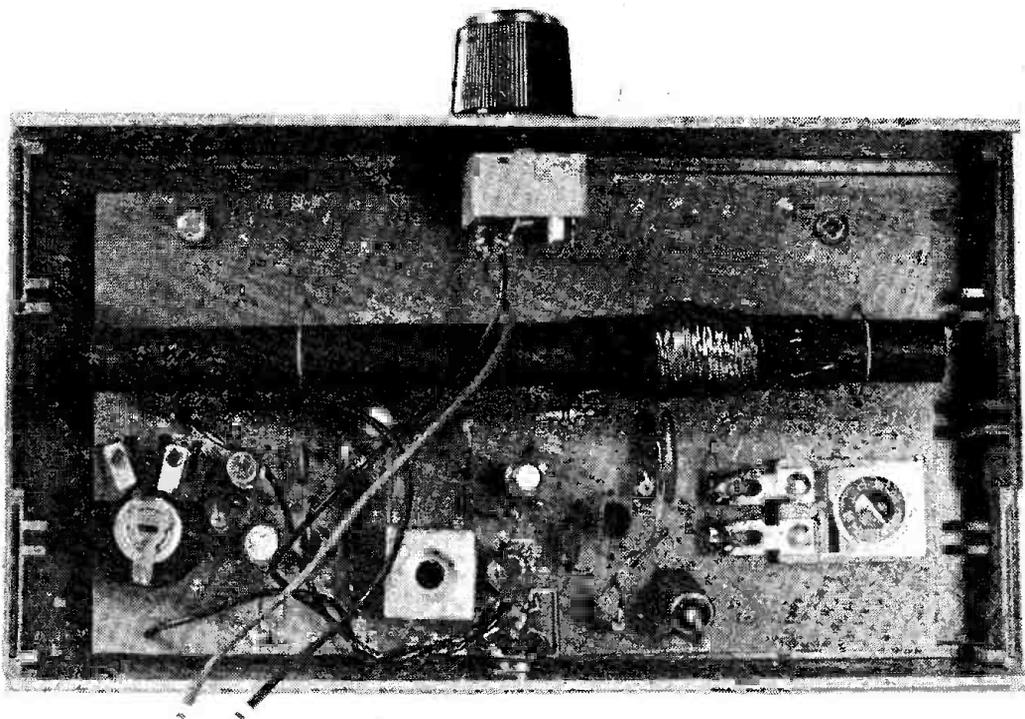Tr3 is a common emitter amplifier which is used to provide all the audio amplification. This stage has a response which hardly falls off at all at 200kHz and so it is absolutely essential that the RF signal is not allowed to enter the audio stage. Filter capacitor C8 is therefore used at the input to Tr3. Violent instability would almost certainly result if this component were to be omitted.



General view inside the Verocase which houses the Tuner. The ferrite rod aerial is held on the board with two loops of thin wire. Tuning capacitor TC1 is at the extreme right with output potentiometer VR1 at the extreme left.

The audio output level can be adjusted by means of preset potentiometer VR1. C1 is the only supply decoupling component that is required. The PP3 battery has a very long life as the current consumption of the tuner is only about 2.5mA.

CONSTRUCTION

Virtually all the components, including the ferrite aerial, are mounted on a PCB which measures 130 x 70mm illustrated actual size in Fig. 2 together with details of the ferrite rod aerial and other constructional information. Note that the holes for the pins and tags of T1 are slightly larger than for the other components, about 1.8 to 2.0mm in diameter. TC1 requires a 5mm dia. mounting hole while those for the board itself are 3.2mm in diameter.


The ferrite rod aerial is home-made and based on

a 127 x 9.5mm (5 x 3/8in.) ferrite rod. This size is readily available from Denco suppliers or direct from Denco. The winding starts 30mm from one end of the rod and consists of 225 turns of 32 SWG enamelled copper wire. Make quite sure that all the turns of the coil go in the same direction. In order to prevent the coil from unwinding, the two leadout wires are taped to the rod. The ferrite aerial is secured to the PCB by two loops of wire which are soldered in place. Try to make these loops fairly tight so that the aerial is provided with a firm mounting.


THE VEROCASE


A small Verocase is used as the housing for the prototype was designed to fit it. S1 is mounted in the centre of the front panel and must be a physically

continued on page 218

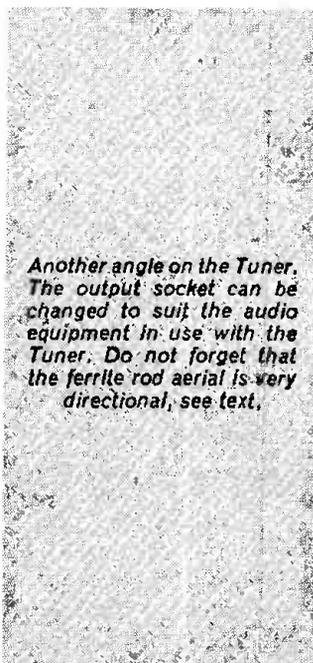

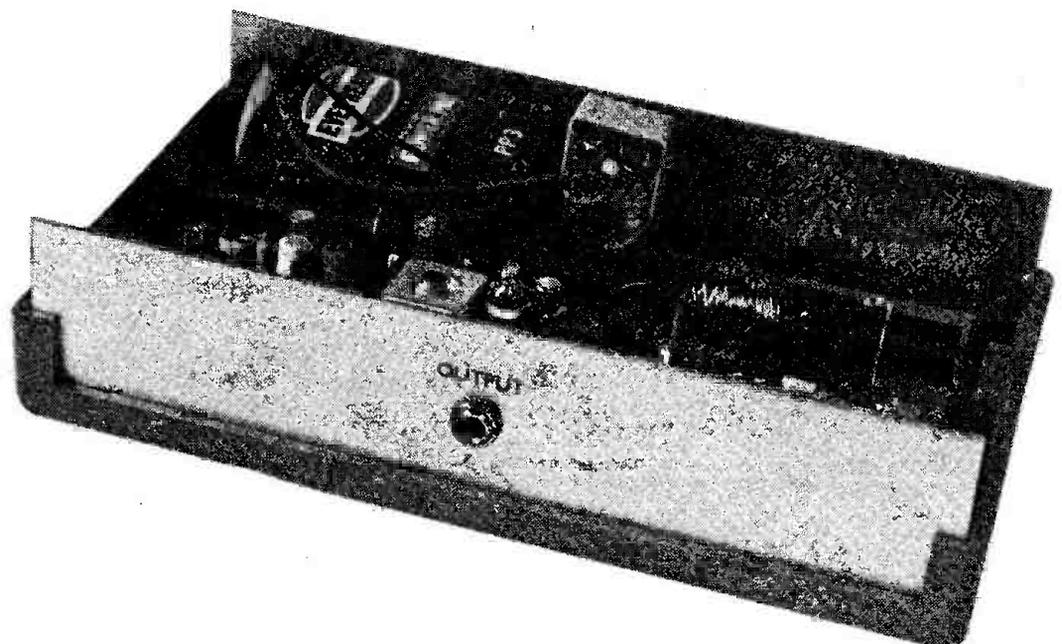Another angle on the Tuner. The output socket can be changed to suit the audio equipment in use with the Tuner. Do not forget that the ferrite rod aerial is very directional, see text.



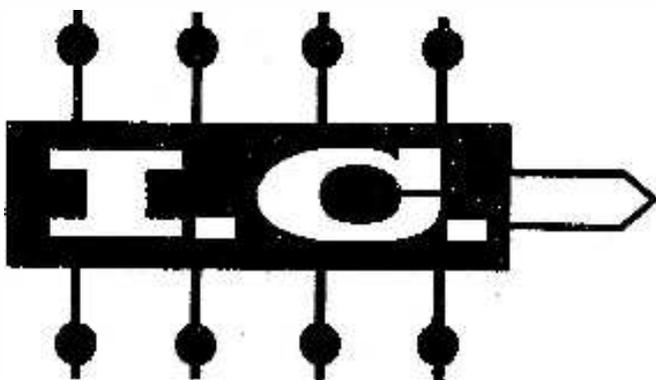

OF THE MONTH

by BRIAN DANCE

Number 63 RCA CA3140 OP. AMPLIFIER

THIS versatile and economical operational amplifier can replace the well-known 741 device in virtually all circuits, but its greatly superior specification also enables it to be used for many other purposes. The input impedance of the CA3140 device is extremely high, namely about $1.5 \times 10^{12} \Omega$ ($1\frac{1}{2}$ million megohms), so it will not impose any appreciable load on the circuit feeding it. The typical input current required by the CA3140 is only 10pA with $\pm 15V$ supplies or 2pA with $\pm 5V$ supplies.

The CA3140 is somewhat like the CA3130 (see *Practical Wireless*, April 1976), but has certain advantages which extend its range of uses. For example, the CA3140 can be operated from any power supply line voltages in the range $\pm 2V$ to $\pm 18V$ (or 4V to 36V if a single supply line is employed). In addition, the CA3140 device has an internal capacitor for frequency compensation fabricated on its silicon chip, so no additional external capacitor is needed for this purpose.

BiMOS

The so-called 'BiMOS' technique is used in the CA3140. This consists of a p-MOS input stage together with high voltage bipolar transistors integrated on the same chip. The p-MOS differential input stage provides a voltage gain of about 10 times (20dB), but the second stage provides most

of the device gain (10,000 times or 80dB). The bipolar output stage has a gain of about unity but like the 741 output stage it includes circuitry which provides built-in protection against damage from short circuiting of the output to either of the supply rails or to earth.

Although MOS transistors are used in the CA3140 input stage, these transistors are well protected with bipolar diodes. Whilst the normal precautions used in handling MOS transistors are probably unnecessary when using the CA3140, it is nevertheless good practice to ensure that soldering iron tips are well earthed, that CA3140 devices are not inserted into or removed from a circuit with the power supplies connected and that signals are not applied to the inputs when the power supply is off.

TYPES

The CA3140 is also available as the more expensive CA3140A and the considerably more expensive CA3140B; these latter 'premium' types have smaller input currents and lower input offset voltage tolerances than the standard CA3140, but the standard type is quite suitable for almost all applications. All three types are available as the CA3140T with straight leads and as the CA3140S with the leads pre-formed into the dual-in-line configuration.

CONNECTIONS

The CA3140 connections are shown in Fig. 1. It can be seen that offset nulling facilities are provided as well as on/off strobing facilities. If these facilities are not required, no connection need be made to the pins concerned. The normal non-inverting input (marked +) and inverting input (marked -) are provided in this device.

APPLICATIONS

The CA3140 can be used in most circuits for which a normal operational amplifier is required. It can also replace the CA3130 in the impedance transformer circuits discussed in our April 1976 issue, but the greater permissible power supply voltages enable much greater output voltage swings to be obtained. The applications to be discussed below are ones for which the characteristics of the CA3140 are particularly suitable.

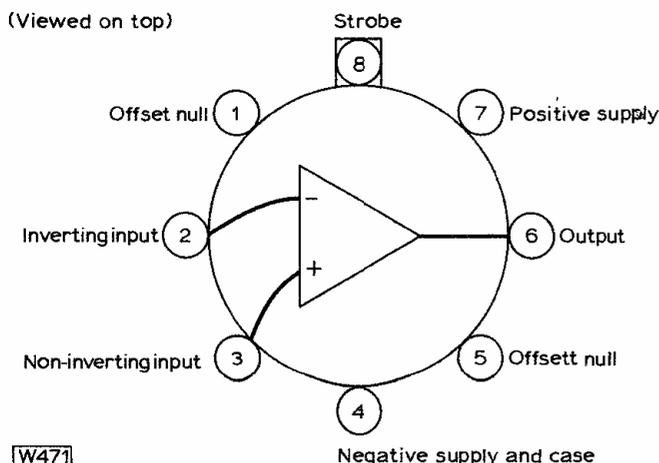


Fig. 1: Leadout connections for the CA3140 op. amplifier, viewed from the top of the device

BAXANDALL TONE CONTROL

The very high input impedance, relatively wide bandwidth, fairly high slew rate and high output voltage capability are all properties which are very useful in amplifiers used in tone control circuitry. A Baxandall type tone control circuit is shown in Fig. 2(a). It provides a gain of about unity and employs standard linear potentiometers to provide bass and treble boost or cut of $\pm 15\text{dB}$ at 100Hz and 10kHz respectively. The gain of the amplifier falls by 3dB at 70kHz relative to the gain at 1kHz in the 'flat' position of the tone controls.

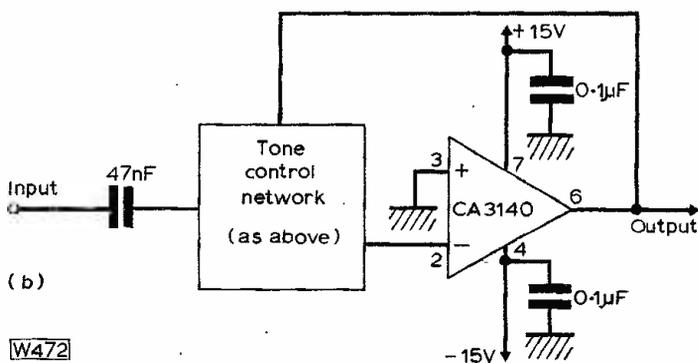
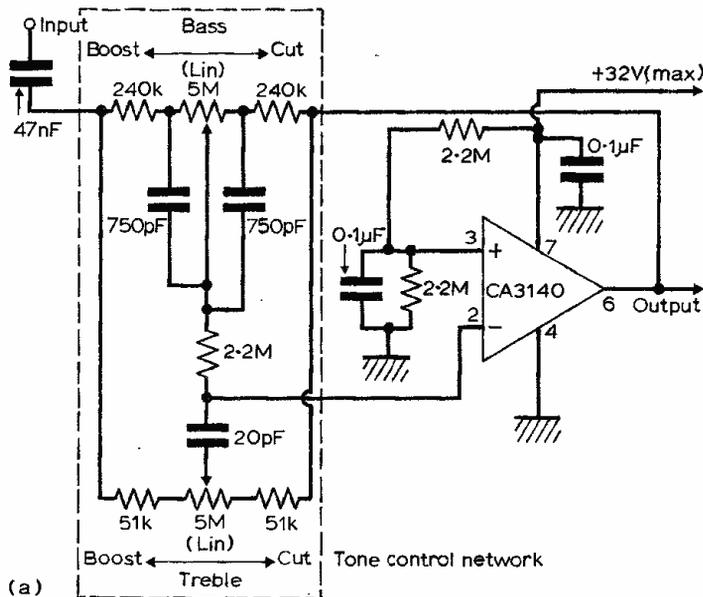


Fig. 2(a) Shows the basic Baxandall tone control circuit where the gain is approximately unity.

Fig. 2(b) is a circuit with the same performance as (a) but it uses a balanced $\pm 15\text{V}$ supply.


The high input impedance of the CA3140 device enables economical low value capacitors to be used in the tone control network. A supply voltage of 32V is shown, but smaller voltages can be used if the maximum output voltage swing required is not very great. If a 32V supply is employed, the full output voltage swings of 25V peak-to-peak are obtainable at frequencies up to more than 20kHz, since the device has a slew rate of about $9\text{V}/\mu\text{s}$ (some 15 to 20 times greater than that of a 741 device).

BALANCED SUPPLIES


The same tone control network can be employed in the circuit of Fig. 2(b) when balanced $\pm 15\text{V}$ supply lines are preferred. The performance is identical with that of Fig. 2(a) except that the out-

put quiescent potential will be almost earth potential whereas the output potential of the Fig. 2(a) circuit will be approximately half the supply line potential.

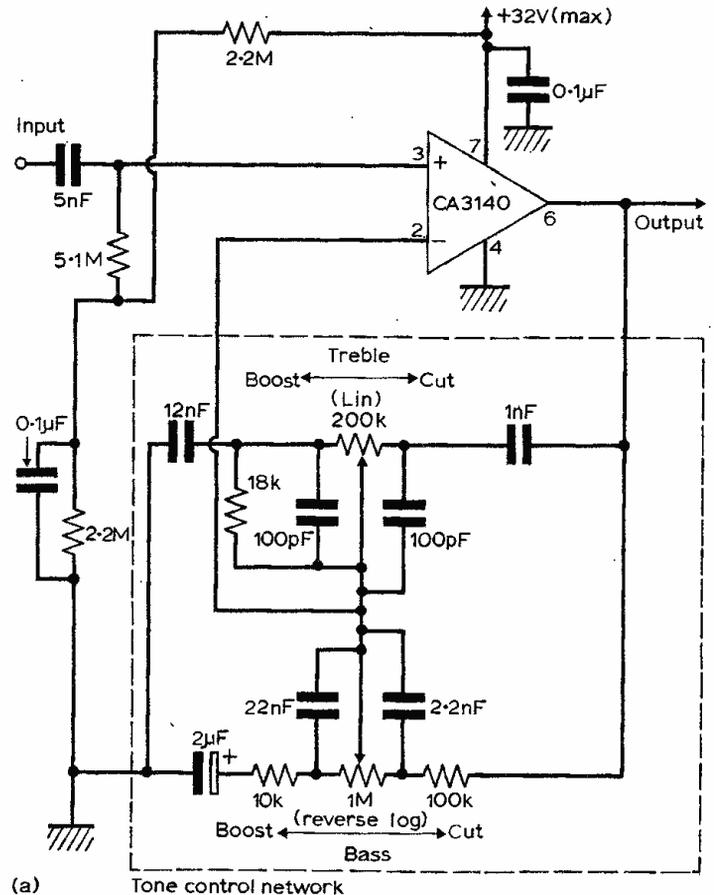The biasing components connected to the non-inverting input of Fig. 2(a) are not required when the balanced supplies of Fig. 2(b) are used. However, an additional capacitor is required to decouple the negative supply line. The typical power supply current of either circuit is only 4mA. In both circuits pins 1, 5 and 8 are left unconnected.



(a) Tone control network

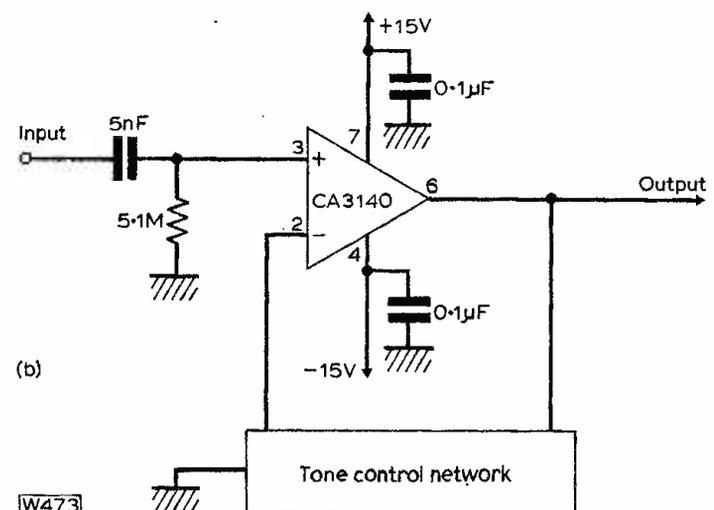

(b) W473

Fig. 3(a) This circuit has a similar performance to those in Fig. 2 but now a voltage gain of about 10 is obtained at the middle of the range.

Fig. 3(b) The circuit of (a) adapted for use with a balanced $\pm 15\text{V}$ power source.

ADDED GAIN

Another tone control circuit is shown in Fig. 3(a); this has a similar performance to that of the Fig. 2 circuits except that it provides a voltage gain of about 10 times (20dB) at mid-frequencies. The bass and treble boost or cut available to about $\pm 15\text{dB}$ at 100Hz and 10kHz respectively. Outputs of up to 25V peak-to-peak can be obtained with the supply voltage shown or smaller outputs at lower supply voltages. The gain falls by about 3dB at 24kHz relative to that at 1kHz with the controls in the 'flat' position.

The same tone control network may be used in the circuit of Fig. 3(b) in which balanced $\pm 15\text{V}$ supplies are used. The performance of the circuits of Figs. 3(a) and (b) is identical but it should not be forgotten that the output from the Fig. 3(a) circuit will be at an average of half the supply voltage, so a coupling capacitor is essential in the output circuit.

CURRENT AMPLIFIER

The circuit of Fig. 4 shows how the CA3140 device can be used as a current amplifier to amplify a very small current passing through the load so that it can easily be measured by the meter. The potential from the point A is connected to the inverting input of the CA3140 and the potential at this point will therefore always be very close to the potential of the non-inverting input.

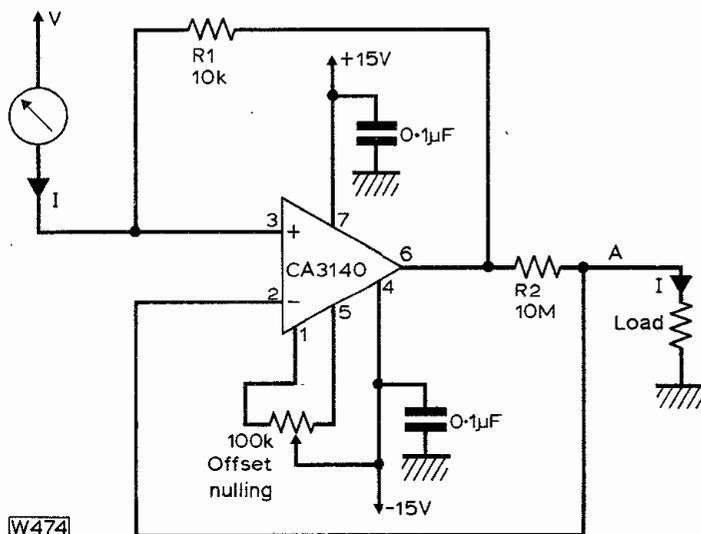


Fig. 4: Here the CA3140 is being used to amplify a very small current thus allowing a conventional meter to be used for measurement.

The voltage V drives a current I through the meter; virtually all this current flows through R_1 , since the current taken by the CA3140 input is extremely minute. Thus a voltage IR_1 appears across R_1 and this same voltage appears across R_2 (since the potentials at point A and at pin 3 are the same). The current passing through R_2 and the load is therefore IR_1/R_2 . If the values of R_1 and R_2 are as shown the current I is divided by 1000.

This current may be 100nA or even less and when amplified by about 1000 times, this current is easily measured by the meter. The potentiometer enables the offset voltage at the output to be nulled accurately and a similar offset nulling circuit can be used in other applications if desired. Pw

★ components list

Resistors

R1	1.8k Ω	R5	5.6k Ω	
R2	2.7k Ω	R6	120k Ω	All $\frac{1}{2}$ or $\frac{1}{4}$ W
R3	220k Ω	R7	1.8M Ω	5 or 10%
R4	33k Ω	R8	3.3k Ω	
VR1	5k Ω horizontal pre-set			

Capacitors

C1	100 μ F 10V	C6	47nF ceramic
C2	100nF ceramic	C7	3.3 μ F 6V
C3	22nF ceramic	C8	47nF ceramic
C4	1.5nF polystyrene	C9	33 μ F 6V
C5	Part of T1	C10	10 μ F 10V
TC1	500pF compression trimmer		

Semiconductors

T1	BF244B	T3	BC109
T2	BC109	D1	OA90

Miscellaneous

T1, IFT (Denco IFT465/14), Verobox or similar (6 \times 3 \times 1 $\frac{1}{2}$ in). Ferrite rod 5in \times $\frac{3}{8}$ in dia. 32 SWG enamelled copper wire. PP3 battery and clip. On-off switch, miniature. 3.5mm jack socket. Knob etc.

small component if it is to fit into the available space. SK1 is a 3.5mm jack socket mounted in the centre of the rear panel. All the wiring is completed before the front and rear panels are slotted into the lower case moulding and the PCB is screwed down. The latter is mounted on the two mounting pillars at the front of the case using two of the self-tapping screws provided. The battery fits into the space at the right of the on/off switch, but the lid of the case will not fit into place unless the front, right hand side mounting pillar is removed from the lid. It is easily drilled away using a 10mm diameter drill.

ADJUSTMENT

With the output of the tuner connected to the amplifier by means of a screened cable, it should be possible to tune to a few stations by adjusting the core of T1. Incidentally, a proper trimming tool such as the Denco TT5 should be used to adjust this core. A wedge shaped tool such as the blade of a miniature screwdriver could easily damage the core. Initially TC1 is adjusted for almost minimum capacitance (the plates not very compressed), and then it is adjusted to peak received signals. It should not be difficult to locate Radio 2 as it lies at about the centre of the tuning range and is stronger than the other signals. Once it has been located, tune to it as accurately as possible by adjusting the core of T1, and then set TC1 to the position which provides the best signal.

VR1 is adjusted towards maximum output (fully clockwise) at the outset. Then it is simply given a setting which provides an output level that is commensurate with those provided by the other items of ancillary equipment. Remember that the ferrite rod aerial is quite directional so turn the tuner round in the horizontal plane until the signal from Radio 2 is at a minimum and then turn at 90° to this position for maximum signal.

The case must be of plastic or wood since a metal case would act as a screen round the ferrite rod aerial. Pw

high fidelity 77 report

RICHARD SCHOFIELD



WITH no Olympia hi-fi exhibition this year, the smaller regional shows are now more important to both the trade and the public. High Fidelity 77 was held within a stone's throw of runway 01, Heathrow Airport, on the first floor of the Heathrow Hotel from April 19 to 24. The last three days were open to the public of whom over 18,000 attended. It was quite obvious that the show wasn't really geared to handle this number of people—many had to wait in the foyer in excess of an hour for a lift to the first floor exhibition area—because of strict observance of the fire regulations. As a result of this it is probable that next year's show will be trade only.

Tape


When people eventually got in, many must have been fairly disappointed with what they didn't see—the number of *interesting* new products could have been counted on one finger... perhaps a little unfair but it seemed that way. For instance, due to production problems with chrome-based cassette tape, there has been a veritable rash of new cassette tapes using 'superferrite', 'microferrite', 'gamma ferrite', etc. All these are simply brand names for highly refined ferrous-ferric oxide, Fe_3O_4 , with or without a dose of cobalt. Inevitably, all the tapes using this compound are described as being 'low noise, high output'. Similarly the publicised performance figures are measured against a nebulous norm which is different for every manufacturer.

Several new cassette decks were shown but offered no real departure from current design. With so many cassette machines offering such equitable performance the sensible thing is to choose a model by its price and other criteria such as 'does the fascia match the G-Plan?'

Elcasetts

Of greater interest were two Sony tape machines using the Elcaset format. Elcasetts operate in the same manner as standard cassettes but use a tape width of 6.25mm instead of 3.81mm; the tape speed

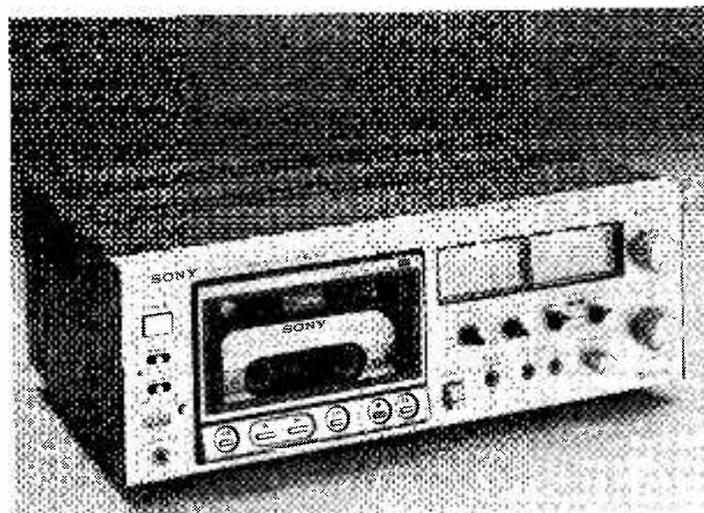is 9.5cm/s as against 4.75cm/s. Physically, Elcasetts look like overgrown compact cassettes but offer rather better performance as a result of their increased size and tape speed. Substantiated claims indicate a -20 VU frequency response of 20Hz to 20kHz±1dB; the 0 VU response is only 2dB down at 15kHz, an open reel standard of performance.




The Sony EL-5 Elcaset recorder

Similarly wow and flutter performance is improved corresponding to the closer tolerances employed within the internals of the Elcaset transport. For instance, levels below 0.1% are quite commonplace. However, nothing is free. An LC-60 (60 minutes total playing time) cassette is expected to cost about £5 or even more; there are other indications that machines to play them won't be cheap either. Sony and Teac (who are shortly to introduce an Elcaset deck) would not state a final selling price or even when the decks would be available.

Open reel

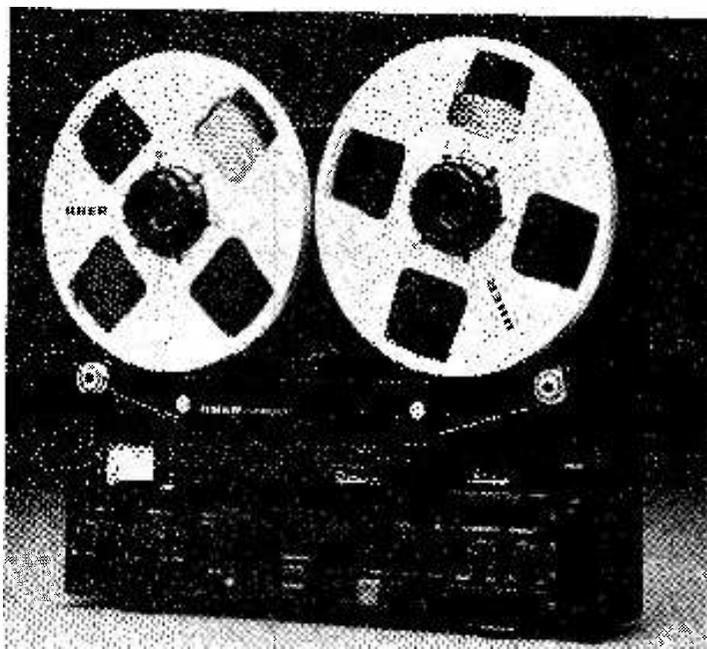One worthwhile advance was shown in respect of open reel recorders. The Uher 630SG Logic operates without the use of a capstan/pinch wheel tape drive.



Uher SG630 Logic open reel tape recorder. This machine has no pinch wheel: it uses a convoluted tape path with a capstan at the centre.

Instead, it uses an omega shaped tape loop—the tape is wrapped around a large diameter servo-controlled capstan by closely spaced roller guides—and sensor devices to maintain constant tape tension throughout a 27cm reel of tape. This system, originating from video tape recording technique, claims to significantly reduce scrape flutter while improving both short- and long-term speed stability. In both the spool and play modes, the capstan provides the prime motive force, the reel motors simply creating a 'neutral' tape tension.

Linear phase loudspeaker

Loudspeaker demos at hi-fi shows are nearly always low in objectivity and high in subjectivity for such is the nature of loudspeakers. Since the listening conditions vary from demo room to demo room (in details such as placement of speakers, size of room, choice of music, etc.) it is impossible to offer any verdict on individual units. Generalising, there was one trend in evidence: linear phase.


Current thinking suggests that phase relationships are all-important in sound image perception; in recent years, speaker manufacturers have tended to market multiple array units with separate drive units for various sections of the frequency range. Inductive/capacitor crossover networks provide the signal split for the individual drivers. The origin of linear phase is this: The initial point of origin of a radiating wave front from a driver unit is the diaphragm (cone) immediately adjacent to the speech coil. In conventional speaker systems, the speech coils of the various drive units (ie, HF, MF and LF) are not in the same vertical plane due to the varying physical dimensions. Step function transients which contains a mixture of all frequencies due to the Fourier transform, will affect all drive units. If the latter are not in vertical alignment in respect of speech coils, then the reproduced transient will no longer exhibit the same acoustic wavefront of the original. In a nutshell, linear phase means mounting the speech coils in a vertical line.

Technics introduced the first production speaker, the SB700, about two years ago. Since then several more have come on to the market. At this year's show, there were two notable additions. Rank Radio International exhibited the Leak 3030 which was about the smallest linear phase model at the show. It sounded rather bright but never-the-less produced a strong stereo image with a tight bottom end. At a discount price of about £120 a pair, it seems very good value for money. At the other end of the scale KEF were being very cagey about their wedge-shaped linear phase 105. The public weren't allowed to see this one for reasons best known only to KEF. If it sounds anything like the non-linear phase 104 which preceded it, then it will be very good indeed—and cost accordingly.

Equalisers

Manufacturers have been working hard in the room equalisation market: several graphic equalisers were on show including one from JVC which was part of a larger pre-amplifier unit. From experience, once one big Jap company goes in for a product, then all the others will follow fairly soon.

The origins of graphic equalisers are in recording studios. It is essential that producers and engineers should be able to listen to master tapes in an acoustic environment uncoloured by individual room responses. To this end, the output from the studio tape recorders is passed through a bank of filters with overlapping frequency responses enabling small sections of the frequency spectrum to be either boosted or cut. This processed signal is amplified through the studio speakers. If enough frequency

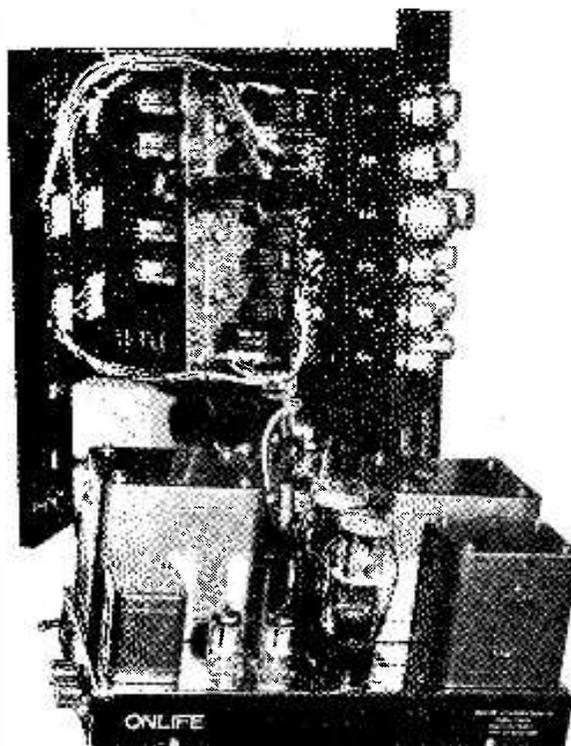

A blast from the past it is not. This is the latest product from On-life, Japan, opening up new frontiers of technology. Whether the concept of a 'valve sound' was borne of the same wave of nostalgia that resurrected Glen Miller remains to be seen.

bands are provided then the listening characteristics of the room can be cancelled out resulting in a 'flat' room without any colouration. Thus the graphic equaliser is adjusted to produce the inverse characteristic of speaker plus room. PW

How to support a SC/MP!

NEW SC/MP USERS START HERE

We make getting into microprocessors as painless as possible, with our range of SC/MP kits we can offer a start at virtually any level of experience or available finance.

SCRUMPI is our own SC/MP starter kit. It contains one SC/MP chip, two MM2112 RAM chips, two 74C173 four-bit I/O latches and a handful of other ICs, switches and LED lamps. The switches allow you to enter a program into the RAM and then execute that program, several operating modes allow for ease of testing. SCRUMPI can be extended to address up to 64K bytes and can be interfaced to ROM, PROM, RAM, EAROM or many types of I/O devices. SCRUMPI can also be used to replace a SC/MP in another circuit to give full in-circuit testing facilities. Kit contains PCB, IC sockets, cable, resistors, caps, etc. **KIT PRICE £35.56**

INTROKIT AND KBDKIT. Eurocard PCB with SC/MP chip, 256 bytes of RAM and 512 bytes of PROM containing KITBUG program, requires a TTY device as I/O. If you do not have access to a TTY then the NS KBDKIT allows you to replace the KITBUG PROM with another supplied, add a few other components (supplied) and you have a portable microprocessor. **INTROKIT £66.33 KBDKIT £66.50**

SCI SC/MP Control Card. Eurocard PCB with provision for 256 bytes of RAM and 1K bytes of PROM with basic I/O device address decoding. Similar in concept to the INTROKIT PCB but can be supplied with or without RAM or PROMs. PROMs can be supplied with any of our software programs listed below.

SCI PCB + decoding chips **£13.89*** SCI PCB + SC/MP + RAM + one PROM **£60.19***
SCI PCB + second PROM **£87.96***

LCDs. Nationals Low Cost Development Kit for SC/MP. Uses a hex keyboard and digital display or a TTY device to communicate with a 2K monitor program in ROM. The CPU application card plugs into one of the sockets on the main mother PCB. Additional PROM and RAM application cards are available to expand the system to its full 64K byte capacity. RUN/STEP/HAULT modes allow for simple debugging. **LCDs £349.30**

EXISTING USERS START HERE

VDU SYSTEM. Two Eurocards which allow for interface to a modified TV set (video not UHF) and ASCII keyboard. The TV display is in the form of 16 lines each of 64 characters (or 16 + 32 or 8 + 32 can be used), each character position can display any of 64 5 + 7 characters in black on white, black on grey, white on grey or white on black, any character set can also be flashed. Any keyboard giving parallel ASCII plus negative strobe output can be used. **VDU SYSTEM £83.34***

CASSETTE INTERFACE. Eurocard PCB with interface to audio cassette recorder in format specified by National Semiconductors. Also includes a TTY interface as found on an INTROKIT together with a relay which can be used to switch a reader/punch or cassette recorder. Requires CASSETTY or CASSIO software (or similar as published by NS). **CASS INTERFACE £16.67***

TTY INTERFACE. Convert your parallel I/O device to be TTY compatible and thus talk to your INTROKIT or LCDs (or 6800, 8080, z80, etc.). Parallel I/O is TTL or 5V CMOS compatible. **TTY INTERFACE £18.52***

4K PROM CARD. Eurocard PCB with sockets for up to eight MM5204 or MM5214 devices with address decoding for each device. Supplied with 2, 4, 6, or 8 blank or programmed PROMs from our selection below.

4K PROM CARD with 2 PROMs **£64.82*** 4K PROM CARD with 4 PROMs **£120.38***
4K PROM CARD with 6 PROMs **£160.67*** 4K PROM CARD with 8 PROMs **£208.34***

* These cards are all compatible with each other and with EYI SYSTEM 68.

P.W. CLOCK/TIMER. 5-LT-01 display **£4.60.** AY-5-1230 chip **£5.25.** 28 pin Socket 60p. Verocase & Red Screen **£3.00.** PCB. Ring for details. For full Clock & MPU Catalogue send SAE. All prices exclude 8% VAT.



BYWOOD

BYWOOD ELECTRONICS
68 Ebbens Road
Hemel Hempstead HP3 9QRW
Tel. 0442 62757

Terms. C.W.O., Access or Barclaycard. Credit facilities to accredited accounts. 15% handling charge on cancellations after despatch. All prices exclude 8% VAT. Post and packing 30p

VALVE BARGAINS

Any 5-64p, 10-£1.20, 50-£5.00. Your choice from the list below.

ECC82, EF80, EF183, EF184, EH90, PCF80, PCF802, PCL82, PCL84, PCL85, PCL86, PCL805, PL504, PY81/800, PY88, 30PL-14, 6F28.

Colour Valves—PL508, PL509, PL519, PY500/A. All tested. **35p each.**

Aerial Splitters—2 way, 75 OHMS, Inside Type, **£1.50**

Press Button UHF Tuners—4 Button Transistor—British made—**£2.50 each.**

250,000

CAPACITOR CLEARANCE SALE

All Mullard C280 and C281 range of Polyester film capacitors 250 and 400 volts working. Very good mixed selection of values from .01µf to 1.5µf.

PRICE 100-£1.50, 500-£7.00,
1,000-£12.00.

All prices include VAT. P&P 20p per order. Please send uncrossed P.O. or cheques for returning if we are out of stock of capacitor bargain packs. Exports welcome at cost.

ELECTRONIC MAILORDER LTD.

62 BRIDGE STREET, RAMSBOTTOM, BURY, LANCs.
TEL: RAMS (070 682) 3036.

AERIAL BOOSTERS

Aerial boosters can produce remarkable improvements on the picture and sound, in fringe or difficult areas.

B11 For TH stereo and standard VHF/FM radio.

B12—For the older VHF television—Please state channel numbers.

B45—For Mono or colour this covers the complete UHF Television band.

All boosters are complete with battery with Co-ax plugs & sockets. Next to the set fitting. **£3.80**

NEWMART for all your hi-fi needs.

Stockists of: Amstrad · Teleton · Akai · Sansui · Wharfedale · Pioneer · Rotel · Garrard · Connoisseur

BATTERY ELIMINATORS P&P 25p
240v input 6, 7.5 or 9v output at 300mA £3.25
12v d.c. input (specify output 6, 7.5 or 9 d.c.) at 300mA £5.20

CARTRIDGES & STYLI D—D & RPL P&P 25p
Cart. Styli

Acos GP91/3CS (ster. comp) £1.60 £1.20
GP93/1 or 95/1 ster. cryst £2.00 £1.20
GP94/1 or 96/1 ster. ceram. £2.00 £1.20
GP101 cryst. comp. £1.00 —
GP104 ster. ceram £2.60 £1.20
BSR X5M or X5H cryst. comp. £1.75 £1.20
SX6M or SX6H cryst. ster. £2.25 £1.20
SC5M ster. ceram. £2.75 £1.20
Sonotone 9TAHC or 9TAHC/G (Diam.) £2.60 £1.20
3509 £2.60 £1.20
Audio Technica AT55 £2.25 —
Goldring G850 £3.50 £1.75
G800 £5.25 £1.75
G800H £5.25 £1.75
G800E £9.06 £3.50

Shure Cartridges & Styli
M44G/M44C £7.70 £6.20
M55E £9.20 £7.15
M75ED Type 2 £17.15 £12.65
M75EJ Type 2 £14.30 £8.78

M.O. prices only. VAT inc. Subject to Availability & manufs. increase. Send 30p for Catalogue. Barclay/Access.

Callers Welcome at Manchester 30-32 Shudehill Tel. 061-832 7710. Leeds 4 New Market St. Tel. 0532 42708. Liverpool 15 Whitechapel. Tel. 051-236 0738

SPEAKERS P&P 70p
EMI 13" x 8", 8 ohm Plain £3.40
8" x 5" C.Mag. 5 watt £2.35
3,8 or 15 ohm £2.35
8" x 5" Dualcone £3.70
8 ohm, 10 watt £3.45
8" 8 ohm Dualcone £4.10
10" Dualcone £12.20
Richard Allen 30w 12" 8 or 15 ohm £12.20

MICROPHONES P&P 45p
UD 130 50K/600 ohm uni-dir. ball metal £7.90
Cassette Stick Mic. with R/Control £1.65
Cass. Stick Mic. with R. Control (Phillips type) £1.93

CASSETTES P&P 25p
C60 C90 C120
Low Noise £0.37 £0.48 £0.73
Phillips £0.79 £1.08 £1.73
Memorex £0.81 £1.38 £1.80
Cassette Head Cleaner £0.55
Bib Head Cleaner De-magnetiser £1.99

RECORD DECKS P&P £1.35
GARRARD SP25 Mk IV £20.70
GARRARD SP25 Mk IV/G800 with Plinth & Cover £33.20
BSR MP60 (P128R) £17.35
Plinth & Cover for Garrard, BSR £4.95
BD1 Kit £17.25

NEWMART ELECTRONICS

Mail Order Dept PW/7
Belmont St, Monton,
Eccles, Manchester.
Tel 061-789 5268

RNARS

morse proficiency transmissions

THE Royal Naval Amateur Radio Society runs the popular morse transmissions (QRQ runs) on the 1st Tuesday of each month on about 3520kHz, depending upon QRM, at 2000 local time (UK) from the RNARS HQ station G3BZU. Speeds are transmitted from 15 WPM to 40 WPM in increments of 5 WPM. All speeds are of a 3 minute duration and must be copied 100 per cent correct. Certificates are awarded for the 15 WPM and 20 WPM copied correctly, with endorsement stickers at all other speeds. It is necessary to obtain the basic certificate before endorsement stickers can be obtained. A charge of 30p is made for each certificate. A stamped addressed envelope is required for endorsement stickers, if not claimed with the basic certificate. The equivalent in IRC's is acceptable from outside the UK.

The initial scheme was started in December 1962 by Dave Pillely G3HLW (now VK2AYD). The 15 WPM run was only introduced to the runs in January 1975 and has since proved very popular amongst the slower morse readers. At present the manager is Michael Puttick G3LIK, who makes up the texts, operates the transmission, marks the submitted copies and issues certificates and/or stickers to successful applicants. Since the transmission began there has been a total of 859 certificates issued to amateurs from the United Kingdom and all over Europe, where the battle to read through the heavy interference is on the increase. It is not just the amateurs that use the transmissions, as large organisations use them to train their recruits to a high degree of morse capability.

The equipment used for these runs at G3BZU is the KW Viceroy transmitter and Eddystone EA12 receiver with a dipole aerial. With G3BZU sitting on top of the second highest point in Hampshire, it is not surprising that the site is such a good take-off point. Further details of the service can be obtained from Michael Puttick G3LIK, 21 Sandyfield Crescent, Cowplain, Portsmouth, Hants. PO8 8SQ.

KINDLY NOTE!

Tug 'O' War Game April 77

On PCB A030 pin 13 on IC8 should be linked across to the +9V rail. Amend Fig. 5 similarly. If the 'knot' fails to move check that pin 9 on IC6 is joined to pin 10 and that pin 11 is joined to pin 12, as shown on the PCB foil diagram.



Tech. info. wanted

.. Manual or circuit diagram with component values for Heathkit TV Alignment Generator type HFW-1.—Mike Roberts, 7 Whielden Lane, Winchmore Hill, Amersham, Bucks, HP7 0NF.

.. Any information on a Jason JTV2 VHF tuner (originally a kit).—G. Cobb, 89 Eastwick Park Ave., Great Bookham, Surrey.

.. Circuits or general information wanted on a Minimitter 10-80m amateur band converter.—T. Smithers, 15 Ferenberge Close, Farnborough, Bath.

.. Full manual or circuit details for Swanco/cse receiver type 2AR. Apply R. J. Smith, 42 Woodchurch Close, Sidcup, Kent. Tel: 01-332-0351.

.. Information required on an ex. Australian Army A510 transmitter unit. Apply Neil Braeman, 9 Millfield, Southwater, Sussex.

.. Valves VY2 and VC11 required for a 1938 German Peoples receiver. Also any surplus pre 1930 literature on radio and electrical communication. Apply C. Matthews, Museum of Communication, University of Edinburgh, Kings Buildings, Mayfield Road, Edinburgh.

.. Manual required for Heathkit 10-12U.—H. Toon, 38 Mountfield Ave., Reepham Road, Hellesdon, Norwich.

.. Circuit diagram or details of GEC Communications Receiver type BRT 400D—C. J. Gill, 95, Fosterd Road, Newbold-on-Avon, Rugby, Warwickshire.

.. Circuit diagram or any information on C. F. Lord FM3-3 Frequency meter and Elipco AC88 amplifier—W. Roebuck 16 Elizabeth St. Newsome, Huddersfield, West Yorkshire.

.. Any information on AM/FM 'Juliette' 7-band receiver—J. Pretorius, Jooste Street, 359 PO Kloofsig, Pretoria, South Africa.

.. Information on Mullard RF signal generator that used the following valves—DW2, 164V, 2286. Also copy of PW March 1976 and information on communication receiver type R1155A—W. Dibden, 13 Grizedale Road, Woodley, Cheshire.

Back issues and equipment for disposal

.. 80 issues of PW dating from 1969 for disposal if any reader would care to make an offer. C. G. Warren, 23 Chipstead Way, Woodmansterne, Banstead, Surrey.

.. Copies of PW dating back to October 1946 for sale. G. LeFlem, 11 Hillmortan Lane, Lilbourne, Nr Rugby, Warwickshire, CV23 OSS.

.. Free gift of back copies of PW to any Radio Club/Boys Club/School.—W. Ferguson, G3KMH, 9 Woodbine Terrace, Hexham, Northumberland.


Back issues and equipment wanted

.. June 1971 issue of PW.—Sidney Coles, 2 Cross Farm, Alcombe Road, Alcombe, Minehead, Somerset.

.. Morse keys for collector and overseas collector friends—G3IRM, 14 Linton Gardens, Bury St Edmunds, Suffolk, IP33 2DZ.

.. October and November 1975 copies of PW wanted.—I. R. Juniper, 28 Rabbett St, French's Forest, NSW 2086, Australia.

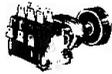HONEYWELL PUSH BUTTON PANEL MOUNTING MICRO SWITCH



1-2-3 Bank, each Bank consisting of the changeover micro switch rated at 10 amps 250 volts. Through panel fixing by 2 lock nuts complete with black 1" diameter knob. Prices:—
1 bank 40p — 2 bank 55p —
3 bank 70p.

12v AUTOMATIC SWITCH

It can sometimes be a problem to find your car or caravan in a big car park or caravan site after dark, so why not fit a light that will come on automatically when it gets dark. We are offering a kit for this, comprises: light sensitive switch, 12v bulb and bulb holder in tubular casing with coloured lens, with wiring diagram.



Price £3.00 + 37p + 20p + 2p. Main operation switch available £3.85.

TAPE HEADS ETC.




2 track record/playback 75p.
4 track record/playback £1.10.
Erase head 2 track 50p, 4 track 90p.
Mu metal shields and holders 65p each.
2 track r/p head and 2 track erase head schedule and fixed on mounting plate ready for tape £1.85.

INDUCTION MOTORS

230v mains operated—precision made as used in fans—record players. Tape recorder—heaters etc. etc. † stack (as illustrated) £1.35. ‡ stack £1.75. 1" stack £2.25.


MOTORISED DISCO SWITCH

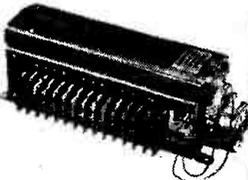With six 10 amp change-over switches. Multi adjustable switches are rated at 10 amp each so a total of 200w's can be controlled and this would provide a magnificent display. For mains operating £4.25 post & VAT. Paid Ditto 9 switch £4.95 Post & VAT Paid. **DITTO BUT 12 SWITCH £5.75 POST & VAT PAID.**



DELAY SWITCH

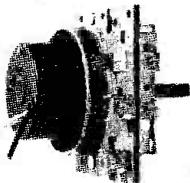Mains operated—delay can be accurately set with pointers knob for periods of up to 2 1/2 hrs. 2 contacts suitable to switch 10 amps—second contact opens few minutes after 1st contact 95p.




WAFER SWITCHES



6 pole 2 way	12 pole 2 way	18 pole 2 way
5 pole 3 way	10 pole 3 way	15 pole 3 way
4 pole 4 way	8 pole 4 way	12 pole 4 way
3 pole 5 way	6 pole 5 way	9 pole 5 way
2 pole 6 way	4 pole 6 way	6 pole 6 way
2 pole 8 way	4 pole 8 way	6 pole 8 way
1 pole 10 way	4 pole 9 way	6 pole 9 way
1 pole 12 way	2 pole 10 way	3 pole 10 way
all £1.32 each	all £2.41 each	all £3.13 each

Multi bank switches up to 72 pole 2 way—to 12 pole 12 way quickly made to special order.

24 HOUR TIMERS

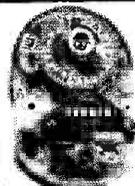

SMITHS
Timer heart similar to Autotest etc. 2 1/3 amp on/off per 24 hrs. £4.15.
TIMAC
Module really miniature (approx 2" cube) but with 2 1/5 amp on/off per 24 hrs. £4.50.

UNISELECTORS

These are pulse operated switches as used in automatic telephone switchboards etc. A 24v pulse moves the switch through one switch way all we have are of the 25 switch full wiper type, the following sizes are in stock:

3 bank	£4.80 + 37p	3 bank & Homer	£5.40
4 bank	£5.94 +	5 bank	£7.02
8 bank	£9.72 +	10 bank	£10.80
12 bank	£12.96 +		



BLOWER FAN



Centrifugal type blower/fans with rectangular outlets designed to fit into trunking for heat blowing etc. will also function as extractors main voltage motors—three sizes available small (overall size approx 4 1/2" x 4" x 4") £4.50—medium (overall size 9" x 8" x 3" approx) £6.50—large (overall size 12" x 12" x 10" approx) £13.50.

CENTRAL HEATING HEARTS

Randal (illustrated) £6.75.
HORTSMAN £6.80.
SMITHS Controller 10/100 complete in wall mounting case £7.50.



THIS MONTH'S SNIP

HI FI RECORD PLAYER



Stereo 5 watts per channel. Russian made but guaranteed repairable. Travel damaged or test line rejects, in need of attention, consist of mains operated record deck — mounted in wooden plinth with super 10 watt amplifier. Controls are "on/off", "Tape/phone", "mono/stereo", "Base", "Treble", "Balance", "Volume". We are offering these at price of record deck only so are a bargain not to be missed only £8.75p, post £2.00p. Note cartridge and all spares are available at low prices.

MAINS TRANSFORMER BARGAINS

20v † amp	£1.25
18v 1 amp	£1.55
6.3v 2 amp	£1.39
25v 1 1/2 amp	£1.75
24v 2 amp	£2.00
50v 2 amp	£4.50
9v 1 amp	£1.25
6.5v-0.8-5v † amp	£1.25
10v 20v 30v 40v	£5.50
250 watt loading	£1.25
20 watt auto 115v	£1.75
100 watt auto 115v	£1.75



THERMOSTATS



Refrigeration as illustrated with 36" capillary £1.62.
Limpet Stat must be mounted in close contact calibrated 90°-190°F 15 amp contacts £1.62.
Appliance Stat fix like a volume control—15 amp contact 30°-80°F 85p.
ditto but for high temps £1.25
Over Stat—with Berson and capillary 85p

TERMS:

Cash with order—despatched same day as order received prices includes VAT and carriage unless stated but orders under £6 must add 50p to offset packing etc. BULK ENQUIRIES WELCOMED. Phone; 01-688 1883.

J. BULL (ELECTRICAL) LTD

(Dept. PW), 103 TAMWORTH RD.
CROYDON CR9 1SG

PP3/BATTERY ELIMINATOR

Made in Japan for Sinclair Radio. This is very neat little transformer driven full wave unit totally enclosed with input mains and output leads. This power supply unit which was originally marketed by Bush at over £6 is offered as this months snip. PRICE £2.60 INCLUDING POST & VAT.

LOW R.P.M. MOTORS



Made by Crouzet — Smiths — SAIWA — Venner and similar famous companies—all supplied ready for 230/240v 50hz mains working at £2.75 each. Following speeds in stock when preparing this advert.

1 rev per day	6 rev per day
1 rev per hour	12 revs per hour
1 rev per min	1 rev per min
2 rpm	1 1/4 rpm
5 rpm	20 rpm
15 rpm	25 rpm
	30 rpm

REMEMBER 7-029

We are still able to offer the electrical equivalent of this in 100 metre coils at a very special price of £10.26p, carriage £2.50p. Our remaining stock of this is 3 core and earth, this is a little larger physically than twin and earth but if space limited then just remove the unwanted core before taking cable into small socket box.



FREE Telephone lines. If you are using the above cable for taking a supply to a shed or remote point then the third core can be used as a telephone line. For lighting we can offer 1.5mm. Three core at £6.50 carriage £1.60.

MULLARD UNILEX

A mains operated 4 + 4 stereo system. Rated one of the finest performers in the stereo field this would make a wonderful gift for almost any one in easy-to-assemble modular form and complete with a pair of Goodmans speakers this should sell at about £30—but due to a special bulk buy and as an incentive for you to buy this month we offer the system complete at only £14.00 including VAT and postage.




IT'S FREE!

Our monthly Advance Advertising Bargains List gives details of bargains arriving or just arrived—often bargains which sell out before our advertisement can appear—It's an interesting list and it's free—just send S.A.E. Below are a few of the Bargains still available from a recent list.

SHORTWAVE CRYSTAL SET

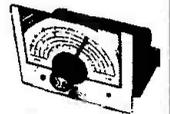Although this uses no battery it gives really amazing results. You will receive an amazing assortment of stations over the 19, 25, 31, 29 metre bands. Kit contains chassis front panel and all the parts £1.90—crystal earphone 55p including VAT and postage.



ROTARY PUMP

Self priming, portable fits drill or electric motor, pumps up to 200 gallons per hour depending upon revs. Virtually uncorrodable, use to suck water, oil, petrol, fertilizer, chemicals, anything liquid. Hose connectors each end. £2.00 Post Paid.



MULLARD AUDIO AMPLIFIERS

All in module form, each ready built complete with heat sinks and connection tags, data supplied. Model 1153 500mW power output £1.50 including Post & VAT. Model 1172 1W, power output £1.85 including Post & VAT. Model, EP9000 4 watt power output £2.90 including Post & VAT. EP 9001 twin channel or stereo pre-amp. £2.90 including Post & VAT.



SOUND TO LIGHT UNIT

Add colour or white light to your amplifier. Will operate 1, 2 or 3 lamps (maximum 450W). Unit in box all ready to work. £7.95 plus 85p VAT & Postage.



MICRO SWITCH BARGAINS

Rated at 5 amps 250 volts. Ideal to make a switch panel for a calculator and for dozens of other applications. Parcel of 10 for £1.00, VAT and post paid.



ROOM THERMOSTAT

Famous Satchwell, elegant design, intended for wall mounting. Will switch up to 20 amps at mains voltage. covers the range 0-30°C. Special snip this month £2.50, post and VAT paid.



Can YOUR Antenna do all this?

You've read our ads with their recent testimonials and user histories—so this month we thought we'd remind readers of the selling points of the

JOYSTICK VFA (World Patents)

- ★ Only 7' 6" long, comes in 3 easily assembled sections.
- ★ Tunes 5-30 MHz, no gaps.
- ★ Matching Antenna Tuner.
- ★ No harmonic resonances—means that the highest efficiency transfer of power and waveform from TX to ether takes place. In turn this ensures that TVI and other spurious emissions are just not substantially present.
- ★ Low angle radiation as an effective ground plane—that husbanded power goes on to reach destination with the least number of loss-making skips.
- ★ Gives receiver additional front end selectivity and gain—reduces cross-mod and out of band blocking.
- ★ Your installation can be "tailored" to space available. Install VFA on mast or chimney or in roof space with a long or short feeder—or SIMPLY STAND IN THE SHACK. One delighted user proved his VFA by operating FROM A BASEMENT!

ALREADY IN USE BY AMATEUR TRANSMITTING AND SWL STATIONS WORLD-WIDE AND IN GOVERNMENT COMMUNICATION.

SYSTEM 'A' £36.00
250 w. p.e.p. OR for the SWL.

SYSTEM 'J' £42.60
500 w. p.e.p. (improved 'Q' on receive).

PARTRIDGE SUPER PACKAGES

COMPLETE RADIO STATIONS FOR ANY LOCATION

All Packages feature the World Record Joystick Aerial (System 'A'), with 8' feeder, all necessary cables, matching communication headphones. Deliv. Securicor our risk. Assembled in seconds! BIG CASH SAVINGS!

PACKAGE No. 1 As above with R.300RX £210.55
SAVE £17.28!

PACKAGE No. 2 Is offered with the FRG7 RX. £193.11
SAVE £12.21!

PACKAGE No. 3 New—low priced package. £154.86

The all solid state SMC73 RX with all the Partridge extras. SAVE £17.28!

RECEIVERS ONLY, inclusive delivery, etc.
R.300 £184.50 FRG7 £162.00 SMC73 £128.81

All prices are correct at time of going to press and carry VAT current at the time and carriage.



Just telephone your card number
Phone 0843 62535
(or 62839 after office hours)



or write for details, send 8½p stamp



Box 5, Partridge House, Prospect Road, Broadstairs, CT10-1LD. (Callers by appointment).

LEKTROPACKS

17 Turnham Green Terrace, Chiswick, London W4 01-994 2784

TRANSISTORS				INTEGRATED CIRCUITS			
AC107 .60	BC153 .27	BDY20 1.10	CA3108A	MC1463R	OA91 .08		
AC126 .37	BC154 .27	BF164 .36	CA30201 .50	MC1469R	OA200 .10		
AC127 .44	BC157 .12	BF167 .38	CA3036 .90	MC1530G	OA202 .14		
AC128 .37	BC158 .11	BF179 .35	CA30482 .15		OA211 .25		
AC176 .40	BC159 .11	BF180 .40	CA30751 .50		OC16 2.50		
AC187 .45	BC167 .12	BF184 .38	CA30841 .90		OC23 2.50		
AC188 .45	BC168 .12	BF185 .35	CA3090A Q		OC25 2.50		
ACY20 .45	BC169 .12	BF194 .15			OC28 2.00		
ACY44 .75	BC171 .14	BF195 .15			OC29 2.00		
AD142 .65	BC172 .12	BF196 .15	CRS1/20	MFC6030 .80	OC42 .50		
AD161 .80	BC182 .11	BF197 .15		MJ481 1.50	OC44 .70		
AD162 .80	BC183 .11	BF198 .15	CRS1/30	MJ2801 1.50	OC45 .70		
AEY11 1.50	BC184 .12	BF200 .35		MJ2901 1.90	OC71 .45		
AF114 .65	BC212 .14	BF244B .35	CRS3/025	MJ2253 1.50	OC76 .40		
AF115 .65	BC213 .14	BF263 .68		MJE340 .58	OC77 .65		
AF116 .65	BC214 .16	BFR39 .28	CRS3/100	MJE370 .58	OC81 .75		
AF117 .65	BC237 .14	BFR79 .28		MJE371 .60	OC83 .50		
AF118 .65	BC238 .12	BFX29 .38	DL6-2100	MJE520 .45	OC84 .50		
AF139 .69	BC239 .15	BFX37 .45		MJE521 .65	OC139 1.30		
AF172 .65	BC259 .18	BFX87 .40	H8028 .15	MJE2955	OC200 1.00		
AF239 .74	BC300 .40	BFX88 .40	HT100 .15		OC202 1.50		
AF279 .80	BC301 .40	BFY50 .34	LO05 1.60	MJE3055 .85	ORP12 .80		
ASY28 1.20	BC308 .15	BFY51 .38	LO36 1.60	MM4000 .65	SC35E 1.20		
AS221 .70	BC309 .15	BFY52 .36	LO37 1.60	MM4001 .65	SC40E 1.85		
BA100 .18	BC359 .14	BFY72 .90	LM309K2 .40	MM4003 .65	SC41D 1.80		
BA102 .18	BCY31 1.00	BLX82 2.00	LM701C	MPP102 .30	SC45E 2.40		
BA112 .18	BCY32 1.70	BLY10 1.80	LM702C .75	MPP103 .35	SC50D 2.60		
BA116 .18	BCY33 1.00	BLY36L2 .00	LM709 .65	MPP104 .35	SC50E 2.90		
BA138 .25	BCY34 1.20	BRY39 .50	LM710 .65	MPP105 .40	ST2 Diac .20		
BA172 .20	BCY38 2.00	BSX20 .30	LM723 .75	MPP111 .28	ST95A .25		
BA176 .20	BCY55 3.90	BSY38 .25	LM741 .35	MFSUC1	TIP29A .50		
BA187 .10	BCY70 .25	BSY39 .25	LM747 .90	MFSU51 .50	TIP29B .63		
BC107 .15	BCY71 .25	BSY40 .25	MC724P	NE555 .60	TIP29C .75		
BC108 .15	BCY72 .24	BT1500 .95		NKT135 .50	TIP30A .60		
BC109 .15	BD121 2.00	BU105 1.50	MC817P	NKT2121 .00	TIP30B .73		
BC113 .17	BD123 2.00	BU205 2.50		NKT214 .65	TIP30C .85		
BC114 .17	BD124 2.00	BU208 3.50	MC876P	NKT222 .70	TIP31A .62		
BC115 .19	BD131 .50	BY127 .36		NKT226 .70	TIP31B .73		
BC116 .19	BD132 .54	BY164 .60	MC1303L	NKT272 .50	TIP31C .85		
BC135 .15	BD135 .37	BY238 .15		NKT4032 .00	TIP32A .75		
BC136 .19	BD136 .37	BYX22 .40	MC1310P	OA10 .50	TIP32B .87		
BC138 .40	BD156 .90	BZY59 .15		OA47 .10	TIP32C 1.00		
BC147 .12	BDX32 .60	BZY63 .15	MC1431G	OA81 .10	TIP33A 1.00		
BC148 .12	BDY11 3.00	C106B .40		OA85 .18	TIP33B 1.23		
BC149 .14	BDY17 3.00	C426 .35	MC1458 .90	OA90 .08	TIP33C 1.45		

★★★★★★★★★ 25% DISCOUNT OFF ALL ORDERS. PRICES
★ JULY OFFER! ★ INC. VAT AND UK POSTAGE. (Please add
★ 20p if under £5). Full semiconductor price list—
send s.a.e. Large range of components in stock—Callers welcome.

SINTEL FAST SERVICE SINTEL FREE CATALOGUE

P.W. ELECTRONIC CLOCK/TIME SWITCH
All major items for this month's P.W. project are available from SINTEL.

SPECIAL OFFER WHILE STOCKS LAST

AY51230 IC from G.I. (each one tested by us before despatch)
PLUS 5LT01 phosphor diode display (Futaba) at a special combination price. Order as AY51230 plus 5LT01
Special Price **£9.90**

ALL WHITE Verocase 751411D w. 205 x d. 140 x h. 75mm. £4.10
(not normal two-tone grey version)
Green perspex front window PX-G-D-14 £0.40
(fits 751411D case)

FOR BY RETURN TELEPHONE SERVICE, RING (OXFORD) 0865 49791
Minimum private telephone order £5. Official orders, no minimum.

Official and Access or Barclaycard orders very welcome.
VAT and P. & P. charges: C.W.O. add VAT at 8% + 25p p. & p. TELEPHONE
and INVOICED orders add VAT at 8% + 50p p. & p.
Premises: 209 Cowley Road, Oxford. No mail to this address.

SINTEL
P.O. BOX 75F, OXFORD

poly-planar

20-Watt Full Range Speaker

Completely replaces the conventional cone speaker
Super-thin construction permits new installation ideas.

Power capability: 40 watts peak. Frequency range: 40 Hz-20 KHz
Sensitivity: 85 dB/M for 1 watt electrical input. Input Impedance: 8 ohms. Operating temperature range: -20°F to +175°F. Size (WxDxL): 1.7/16" x 1.1/32" x 1.4-11/16". Weight: 19 ounces.


£9.50 each Stereo pair £18.50

INCLUSIVE OF VAT AND POSTAGE

web europa

PO Box 9, Bryn Goodman, Ruthin Clwyd



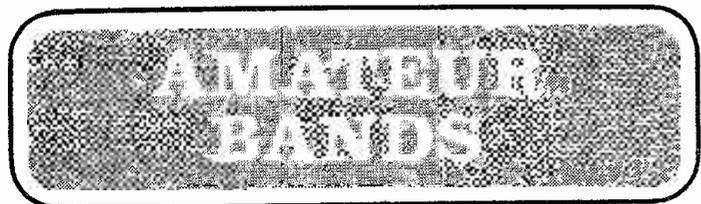

by **Eric Dowdeswell G4AR**

IT IS very nice to get a letter from **Neil Whiteside** G8MXF, formerly A8859, of Hitchin and to know that he has not forgotten the column! Wisely he is working on the code and ought to have his G4+3 in the near future. At present he is active on 2m with a Pye F27 and a Hudson FM208. Among his 700 QSO's so far has been another of our earlier contributors **Paul Turner**, now G8MWV. I hope all this will act as a spur to those of you who are thinking of taking the RAE!

Alan Doherty BRS34968 of Portrush, Co. Antrim has got back into the listening groove again after his return from New Zealand, and an Eddystone 940, newly acquired, plus a 300ft wire has put things like C21NW on Nauru Is. and HMIIV in Seoul into his log. In Harrogate **Steve Cottis** A8961 has been admiring some recently received QSLs from VP5A, 6W8FZ, WB6EWH/VQ9 and 9X5SM. He comments on the 15m band which has been producing DX from all continents.

Other readers of this column could well emulate **Paul Cowburn** in Leyland, Lancs and spend time copying the RSGB slow morse transmissions. Paul is now up to around 10wpm and mentions that past contributor to this feature **Tim Charles** G4EZA sends the slow stuff out on 2m. W4BRB/C6A in the Bahamas plus PJ8CO and FG7AR/FS7 might not seem very extraordinary unless I told you that Paul has been copying them on Top Band! Paul has joined the RSGB and started on a one-man course for the RAE. Stick to it, Paul, others have made it on their own, so why not you?

Yet another Paul reports in. **Paul Bradbeer** in Braunton, Devon is also a recruit to the RSGB and to the North Devon Radio Club. His CR70A plus RF amplifier and 33ft wire have been mainly employed on 15m with forays to 20m. If you manage to copy a lot of those Jubilee GE callsigns you might be able to qualify for the Bromsgrove and District ARS Silver Jubilee award. Copy GE3VGG the club station plus another in Bromsgrove plus 23 others and send the log to J. K. Harvey G8KLO, 22 Elm Grove, Bromsgrove, B61 0EH by 31 Dec. Send an SAE to KLO if you have any enquiries or need fuller details.

In Cambridge, **David Peck** BRS37621 complains of the QRM by CW stations on the RTTY channel 14095kHz, David's favourite spot. It is a pity but I doubt whether many op's realise it's significance and probably curse that 'QRM' on the choice bit of DX that they're after! David's FRG7 plus homemade terminal unit, Creed 7B printer and 130ft of wire seem to get him RTTY copy from most parts of the world.

If you happen to be five miles SE of Derby on Sunday 12 June you will be in the middle of the Elvaston Castle Mobile Radio Rally run by G3EEO, G3BZI, G8KGC and others for the Nunsfield House Community Assoc. Trade stands, sideshows and all the fun of the fair. Don't miss it!

The bug has bitten again for **John McFadden** in Belfast who had a Trio 9R59 a couple of years ago but sold it. Now with a 100ft of wire indoors he is active on the amateur bands again, this time with an FRG7. Nothing special to report so far but John is persisting. **Brian Harrison** of Hastings used his AR88 and ATU with a vertical to get such stations as FH8CJ in the Comoro Is. on 20m. Plans for a 300ft wire came to grief with planning permission problems. Following the note in this column **Michael Waller** in Leeds heard from several clubs and then discovered that G3WWF lived only a few streets away! So he is not alone any more.

Long-time correspondent **Robin Bayley** A9203 writes that he copies slow code from G4EYY and with his RAE course starting in September he ought to be well on his way to the RAE. He monitors all bands from 10 to 80m with his EC10 and R1475 plus a Microwaves Module converter for 2m. A warm welcome to **I. Radford** in Derby, who, in a very brief letter indeed, says he is using an Eddystone EC10 plus a whip aerial. We'd like some more info OM. **Alan Doherty**, already mentioned, would like to hear from other SWLs, DX or local. He'd really like to form a local club but the only known amateur in his area is GI3ONZ who is inactive at present. Write to Alan at 21 Romore Street, Portrush.

My thanks to **Edgar Janes** G2FWA for a copy of the Cheltenham RSGB Group newsletter, a nice blend of local news and technical tit-bits. If you happen to live in that very pleasant part of the country why not drop a line to Hon. Sec. **Derek Lively** G3KII, 26 Priors Road, Cheltenham or drop in at the Old Bakery, Chester Walk, on the first Thursday of any month at around 8pm.

The Worldwide SSTV Contest brought much joy to **Paul Barker** up in Sunderland with HC1BU and JA1PSS providing the best DX pictures. At the White Rose Rally he managed to swop his FRDX500 for a Trio JR599 which proved itself by copying all continents on 15m during one afternoon. Although he has been reading the column for some time, **Philip Ackroyd** in Peterborough at last sent in a letter and log. Glad to have you with us Peter, and I'm sure you will enjoy your membership of the Greater Peterborough ARC. Rig is an FR50B plus 60ft wire.

By the time you read this I hope to be on the air with my Pye 125 transceiver, on 80m to start with, SSB and CW reports will be welcomed.

Log Extracts

P. Bradbeer:— 20m C6AEY (Bahamas-QSL WB8HAK) HR3JJR YV0DL 15m EA8NO FG7AS PZ1DR 5Z4RG 6W8AK (QSL F6AXP) 7P8BC

P. Ackroyd:— 20m FL8GP KV4MV 15m KZ5UH

A. Doherty:— 80m HS1BG HV3SJ KA1IYO (Ogasawara Is) KA6YL KH6II PZ9AB ZP5AO 20m C21NW HM1IV 5T5DY 9D5D 15m FG7AR/FS7 FR7ZL/T

P. Barker:— 20m SSTV CN8BF FC6EFJ HC1BU JA1PSS K0ZOL LZ1MH OH5BM PY2WE W8DX 9K2DO 15m K9TQT/CP6 OA8CD ZD7SD ZP5WU 7P8BC 9J2CW 9Y4NP

I. Radford:—80m KH6IIV TY2HKY ZL3NE.

B. Harrison:—20m FH8CJ 15m TI2SAP VE3AQS/
TG9 YN4SP ZS4MZ 5N2AAV

R. Bayley:— 80m KH6PP OA8AF TG9HD 40m
AP2AD EA6BG VK2APD 20m HK0COP KH6BB
VS6DO 15m DU1DBT JA9CM TG9TY 10m JA1KSO
VK6PP 7Q7BA


J. McFadden:— 20m CT2BB VP9HY

D. Peck:— All RTTY 80m LX1JW 20m CO2FRC
FG7XT JA1ACB N4AL OH0NI WA0CKY YV7DU

P. Cowburn:— 160m W1BB W4BVV K8CCV
FG7AR/FS7 VO1KE W4BVV YV4BK 80m FM7AQ
FG7AR/FS7 HR2BLD TG9KT VP1RS VP2DAD
VS6DO ZL1AQF ZL4LM 7P8BE 9J2WR FR7ZL/T
5X5NK 40m VK7GK ZL1BIL ZL3ABN ZP5LX 20m
KG6RT KH6BB PJ8CO 9L1NP ZD8TM

S. Cottis:— 80m JY9HQ 20m HI8CDS VP2MAQ
6Y5YL 15m A4XFE AP2P CP6HB FL8KP FR7ZL/T
PJ8CO TA1ZB YB2CR 3D6BD 6W8FZ 7P8BE

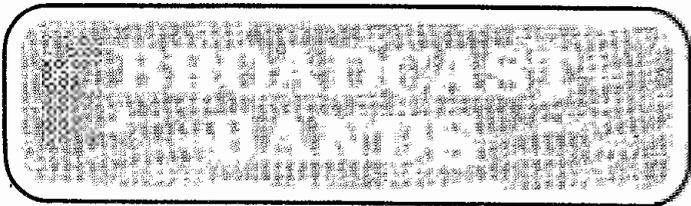All SSB except where stated otherwise, CW in bold.



MEDIUM WAVE DX

by Charles Molloy

LATIN American DX appears again, this month with a really fine log from Aurich-Sandhorst in West Germany. Joachim Gutschke, who is an old-established SW enthusiast came in contact with *Practical Wireless* and this column while on holiday in the UK and he has now been converted to the medium waves. Highlights of his log are Radio Liberacion in Havana Cuba on 640kHz, La Voz de Cuba in Camaguay on 740, Radio Demerara Guyana 760, 4VEH Cap Haitien, Haiti 840, Ondas del Pacifico Ecuador 975, Radio Commercial Santo Domingo on 1010, Radio Conquistador Puerto Rico on 1480. All were heard on a homebrew receiver and two fixed remotely tuned loops located in the loft.

A heterodyne is produced on a signal when two carrier frequencies separated by a few hundred Hz or more, enter a receiver and reach the detector stage. This heterodyne, which is equal to the frequency difference between the two signals, is rectified and heard as an audio tone similar to a tuning note. It can be distracting to the DXer and in some cases it makes reception rather difficult. The writer had experience of this effect recently when listening to the new Nigerian outlet on 945kHz which is separated by only 1kHz from the European channel on 944kHz. At the time 944 was occupied by a Russian station which was somewhat stronger than the African. The result was a strong audio note of 1kHz which made DXing almost impossible. One method of reducing this trouble is to increase the receiver selectivity until speech becomes muffled. Then detune, away from the interference, when the interfering signal and the heterodyne will both be reduced in strength and the desired station will be heard on one sideband only.

A more effective method of dealing with hetero-

dynes is to use an audio notch filter. The writer recently purchased a tunable audio notch filter from Cambridge Kits, who advertise in *Practical Wireless*. This device is connected to the receiver headphone sockets in place of the headphones, the latter being plugged in to the notch filter. The source of power is a PP3 battery and there are two controls, an on/off switch and a tuning control. The result on 945kHz was startling. When the notch filter tuning control was rotated a position was found where the heterodyne disappeared completely, leaving a nice clean signal which was now relatively easy to identify. For the technically minded the notch filter is a band stop filter with a narrow rejection band. It is tunable over the range 350Hz to 6kHz and the sharp "null" ensures that it has little effect on speech.

An interesting situation arises when two stations nominally on the same channel are in fact separated by one or two Hz. When this occurs and the two stations are of comparable strength then the 'heterodyne' becomes a beat of considerable magnitude which can be observed on the 'S' meter. Unfortunately, the receiver's AGC will respond to the beat, adjusting the receiver gain in sympathy with it and producing audio distortion which is most unpleasant to listen to. The remedy of course is to switch off the AGC.

A weak inaudible station will produce a visible beat on top of a much stronger station if there is a slight frequency difference between them, as is often the case. The effect can be very useful to the DXer. He may, as your scribe did some years ago, stay on the channel in the hope that the strong station will fade and the weak one will come up. KOMO Seattle on 1000kHz was heard this way after observing a beat on WCFL. The DXer, if he has a loop, may even take a bearing of the inaudible station by rotating the loop until the beat disappears. This too may be an indication as to whether the inaudible companion is worth waiting for.

A long and interesting letter from L. W. Spendla of Basingstoke mentions that he started DXing on the medium waves in 1925 with a one-valve receiver. By 1930 he was operating a four-valve Osram Music Magnet in Buckingham with a good, high wire aerial and a well watered earth. Best DX recorded was Pittsburg (KDKA) and Boston (WBZ). On trying this receiver again in 1975 he logged 50 continental stations plus Algiers and Oran. Dr. H. S. Brodribb from St Leonards-on-Sea writes "I am challenged to do all my DXing on vintage radio and I get good results on a 1935 Philips 745 and roof aerial". The good doctor does have a CR100 and a long wire though and with this set-up he pulled-in the 50kW WINS in New York City on 1010kHz.

The committed medium wave DXer will, when on holiday, take a receiver with him just to check out the band from a new location. In Spain, where there are several chains of low power local stations it can be an interesting exercise to try to identify some of the many locals that can be heard. A Philips jack-in car radio/portable and a copy of the *World Radio Handbook* invariably accompany yours truly when on holiday either at home or abroad. DXing Spanish locals from the UK can be an absorbing occupation during the summer months. Listen around midnight, which is sign-off time for many stations, which can be heard leaving the air one after another on some occasions. Channels to watch for local radio outlets are 1106, 1133, 1394, 1412, 1475, 1520 and 1570kHz. Stations logged recently are EFJ19 Radio



Wilmslow Audio

THE firm for speakers!

SEND 10P STAMP FOR THE WORLDS BEST CATALOGUE OF SPEAKERS, DRIVE UNITS, KITS, CROSSOVERS ETC. AND DISCOUNT PRICE LIST.

- ACT ● AUDAX ● BAKER ● BOWERS & WILKINS ● CASTLE ● CELESTION ● CHARTWELL ● COLES ● DALESFORD ● DECCA ● EMI ● EAGLE ● ELAC ● FANE ● GAUSS ● GOODMANS ● HELME ● I.M.F. ● ISOPHON ● JR ● JORDAN WATTS ● KEF ● LEAK ● LOWTHER ● MCKENZIE ● MONITOR AUDIO ● PEERLESS ● RADFORD ● RAM ● RICHARD ALLAN ● SEAS ● TANNOY ● VIDEOTONE ● WHARFEDALE

WILMSLOW AUDIO (Dept. P.W.)

SWAN WORKS, BANK SQUARE, WILMSLOW, CHESHIRE SK9 1HF

Discount HiFi Etc. at 5 Swan Street and 10 Swan Street.

TEL: WILMSLOW 29599 FOR SPEAKERS
WILMSLOW 26213 FOR HIFI.

TECHNICAL TRAINING IN ELECTRONICS TELEVISION AND RADIO SERVICING

ICS can provide the technical knowledge that is so essential to your success, knowledge that will enable you to take advantage of the many opportunities open to the trained person. You study in your own home, in your own time and at your own pace and if you are studying for an examination ICS guarantee coaching until you are successful.

City & Guilds Certificates:

- Telecommunications Technicians
- Radio, TV, Electronics Technicians
- Technical Communications
- Radio Servicing Theory
- Radio Amateurs
- Electrical Installation Work
- MPT Radio Communications Certificate

Diploma Courses:

- Colour TV Servicing
- Electronic Engineering and Maintenance
- Computer Engineering and Programming
- Radio, TV, Audio Engineering and Servicing
- Electrical Engineering, Installation and Contracting

POST OR PHONE TODAY FOR FREE BOOKLET

ICS To: International Correspondence Schools

Dept. No. 777H, Intertext House, LONDON SW8 4UJ or telephone 622 9911

Subject of Interest.....

Name

Address

Tel:

Your free start to a rewarding new hobby.



Heathkit make the world's largest range of electronic kits.

Including amateur radio, test equipment, educational and general interest kits.


Every one of which comes to you absolutely complete—right down

to the last nut and bolt.

You'll also get a very easy to understand instruction manual that takes you step by step through the assembly.

So, besides making an attractive, useful piece of equipment, you'll also have the makings of a satisfying, rewarding hobby.

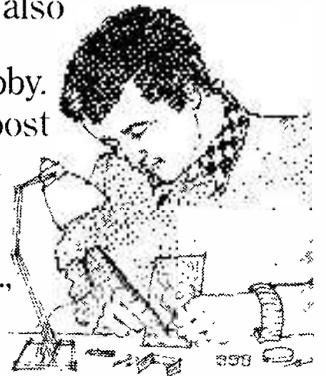To find out more, post the coupon and we'll send you our latest catalogue. Heath (Gloucester) Ltd., Dept. PW-77. Bristol Rd., Gloucester, GL2 6EE. Tel: Glos (0452) 29451



HEATHKIT

BETTER BUILT BECAUSE YOU BUILD IT YOURSELF

The new Heathkit catalogue. Out now FREE.

To: Heath (Gloucester) Ltd., Dept. PW-77. Gloucester, GL2 6EE. Please send me my Heathkit catalogue.

I enclose an 11p stamp for postage.



Name.....

Address.....

Postcode.....

ACCESS AND BARCLAYCARD WELCOMED

Showrooms at 233 Tottenham Court Road, London and Bristol Road, Gloucester.

NEW MAZDA VALVES

All individually boxed, trade discounts to bonafide companies. Prices on application.

DM70	0.69	EF83	1.10	PCC85	1.02	PL508	1.32	30C17	1.20
DY88/7	0.56	EF85	0.50	PCC88	0.98	PL509	2.16	30C18/	
DY802	0.68	EF86	1.20	PCC89	1.05	PL802	1.80	PCF8051-28	
EB91	0.72	EF89	1.73	PCC189	0.96	PY33	0.68	30F5/F818	
EBF81	0.89	EF91	1.32	PCF80	0.72	PY81/800	0.72		1.00
EBF80	0.63	EF92	1.51	PCF82	1.20	PY82	0.70	30FL1/	
EBF83	0.68	EF95	1.63	PCF86	0.92	PY86/7	0.70	PCE800	1.00
EBF89	0.50	EF183	0.64	PCF200	1.50	PY88	0.68	30FL2	1.00
EC86	0.82	EF184	0.64	PCF201	1.50	PY500A	1.36	30FL12	1.44
EC88	0.86	EH90	1.22	PCF801	1.02	PY800	0.72	30FL14	1.44
EC90	0.88	EL34	0.96	PCF802	0.72	PY801	0.72	30L1/PCCB4	
EC97	0.69	EL36	1.50	PCF806	0.97	U26	1.16		0.63
ECC81	0.70	EL84	0.70	PCH200	1.73	U191	1.17	30L1/PCE800	
ECC82	0.56	EL86	1.40	PCL82	0.68	U193	0.56		0.68
ECC83	0.56	EL95	1.02	PCL83	0.92	UBC81	0.80	30L1/5	
ECC84	0.83	EM81	1.24	PCL84	0.72	UBF89	0.85	PCC805	1.32
ECC85	0.92	EY51	0.89	PCL85	0.72	UCC85	0.66	30L17	1.32
ECC88	0.96	EY86	0.50	PCL86	0.88	UCH81	1.73	30P4	0.92
ECC189	0.77	EY86/87	0.68	PCL805/		UCL82	0.84	30P4MR	1.63
ECF80	0.80	EY88	0.81	850	0.80	UCL83	1.02	30P1Z/	
ECF82	0.88	EZ80	0.60	PD500	3.00	UL94	1.23	PCB01	1.22
ECF86	0.78	EZ81	0.60	PFL200	1.23	UY85	0.80	30P19/	
ECH81	1.00	GY501	1.32	PL36	0.92	6/30L2/		PC802	0.92
ECH83	1.06	GZ34	1.24	PL81	1.00	ECC804	1.20	30P1/	
ECH84	1.08	OC83	0.60	PL81A	1.00	6F23/EF812		PCL801	1.32
ECL80	0.80	PC86	1.08	PL82	0.84		1.32	30P13/	
ECL82	0.72	PC88	1.08	PL83	1.73	30C1/PCF80		PCL800	1.44
ECL83	0.93	PC97	0.88	PL84	0.84	0.72		30P14/	
ECL86	0.88	PCC00	0.92	PL500	0.96	30C15/		PCL88	1.68
EF80	0.68	PC884	0.68	PL504	0.96	PCF800	1.20	30PL15	1.44

MULLARD PRICES AVAILABLE ON REQUEST

NEW VALVES Individually boxed and guaranteed but of European or other origin at greatly reduced prices. Quotations for any valve not listed.

AZI	1.00	EF86 Mullard	PCC84	0.45	UCL82	0.50	6J6	0.35	
AZ31	1.10		PCC88	0.65	UCL83	1.20	6J7G	0.80	
CLB131	1.50	EF89	0.60	PCC89	0.65	UL41	1.00	6J7M	0.75
CL33	2.00	EF91	0.65	PCC189	0.55	UF89	0.50	6K6GT	0.80
CV31	1.00	EF92	0.75	PCF80	0.72	UL84	0.85	6K7G	0.85
DAF91	0.40	EF95 USSR	PCF82	0.50	UY41	0.75	6K7M	0.75	
DAF96	0.60		PCF86	0.65	UY85	0.65	6K8G	0.45	
DC90	1.85	EF95 UK	PCF801	0.55	VR105/30	0.45	6K8M	0.75	
DF91	0.40	EF98	1.25	PCF902	0.72	1R5	0.55	6L6G	2.50
DF96	1.00	EF183	0.50	PCF806	1.28	1S5	0.40	6L6GC	1.60
DK91	0.55	EF184	0.50	PCF808	0.80	1T4	0.40	6Q7G	0.40
DK92	1.10	EL32	0.75	PCF808	1.28	3S4	0.75	6Q7M	0.75
DK96	1.10	EL33	3.50	PCL82	0.50	3V4	1.00	6SL7GT	0.55
DL92	1.75	EL34	1.20	PCL83	0.92	5R4GY	1.20	6SN7GT	0.55
DL94	0.45	EL34 CH/SLO-	PCL84	0.50	5U4G	1.25	6SU7G	0.40	
DY86	0.55	YACK	PCL85	0.60	5U4GB	1.00	6U6G	2.00	
DY87	0.45	EL36	0.75	PCL86	0.55	5Y3GT	0.85	6V6GT	0.80
DY802	0.47	EL41	1.25	PCL805/85	0.80	5Z4A	0.85	6X4	0.45
EABC80	0.38	EL42	1.75	PD500	3.00	5Z4G	0.95	6X5G	0.55
EAF42	0.70	EL84	0.35	PEN45	0.85	6/30L2	0.90	7B6	0.80
EB91	0.30	EL85	0.80	PL36	0.92	6AK5 USSR		7B7	1.00
EBC33	1.00	EM80	1.10	PL81	0.55	6AK5 UK	3.30	7C5	2.00
EBC41	0.75	EM81	1.00	PL82	0.60	6AM5	2.04	7C6	1.25
EBC81	0.40	EM84	1.00	PL83	0.55	6AQ5	0.75	7H7	1.00
EBF80	0.40	EM85	1.25	PL84	0.60	6AS7G USSR		7R7	1.30
EBF83	0.40	EM87	1.50	PL804	0.86	6AS7G RCA		7S7	2.25
EBF89	0.32	EY51	0.75	PL508	1.32	6AT6	5.00	7Y4	0.75
EBL31	2.50	EY86	0.50	PL509	2.16	6AU8	0.55	12A7	0.45
ECC81	0.45	EZ40	1.25	PL802	1.80	6B6A	0.65	12AU6	0.50
ECC82	0.45	EZ41	1.25	PY33	0.68	6BA8	0.50	12AX7	0.45
ECC83	0.45	EZ80	0.30	PY81	0.50	6BE6	0.65	12BA7	0.50
ECC84	0.50	EZ81	0.35	PY82	0.45	6BH6	1.20	12BE8	0.60
ECC85	0.55	GY501	1.32	PY83	0.60	6BJ6	0.80	30C1	0.40
ECC88	0.50	GZ30	0.65	PY88	0.68	6BQ7A	0.55	30C15	1.00
ECC88 USSR	0.60	GZ32	0.75	PY500A	1.36	6BR7	3.00	30C17	1.00
ECH35	2.00	HN309	1.50	PY81/800	0.50	6BS7	4.00	30C18	1.28
ECH42	1.15	KT81	3.50	U14	0.75	6BW6	3.75	30F5	1.00
ECH81	0.50	KT66	4.00	U25	1.00	6BW7	1.12	30FL1	1.00
ECH83	0.85	KT81(7C5)2-00		U26	0.85	6C4	0.40	30FL2	1.00
ECL80	0.60	KT88	4.75	U191	0.75	6CD6GA RCA		30FL14	1.28
ECL82	0.55	KTW61	1.75	UABC80	0.50	or GE	4.00	30L15	0.95
ECL83	1.50	MU14	1.00	UAF42	0.70	6CH6	3.85	30L17	0.95
ECL86	0.65	N78	8.00	UBC41	0.75	6CW4 RCA		30P4MR	1.30
EF37A	1.60	OA2	0.45	UBC81	0.50			30P12	1.00
EF39	1.25	OB2	0.45	UBF80	0.50	F623	0.72	30P19	0.95
EF80	0.45	PC86	0.85	UBF89	0.50	F625	1.00	30P1L	0.95
EF85	0.50	PC88	0.85	UCC85	0.50	F628	0.96	30PL13	1.44
EF86 USSR	0.45	PC97	0.55	UCH42	1.00	6J5M	0.65	30PL14	1.68
		PC900	0.75	UCH81	0.50	6J5G	0.45	35W4	0.60
						35Z4GT	0.70	50CD6G	2.50
						807	1.00		
						807 USA	2.00		
						807 USSR	0.65		
						813ITT	17.50		
						813 USA	29.00		
						813USSR	6.00		
						866A UK	8.85		

● OSCILLOSCOPE TUBES
Types CV 1526,
VCR139A
All at £8.00 each, + p & p 50p
8% VAT

**EXPRESS
POSTAGE**
25p per order in UK.

VAT To be added VALVES 12 1/2%
TRANSISTORS 8%
to all orders TRANSISTORS MARKED* 12 1/2%

TERMS OF BUSINESS: C.W.O. A/c's available to approved companies
Open daily to callers 9 a.m.-5 p.m. Monday to Friday. Prices correct when
going to press. Prices on application for any types not listed.

RST VALVE MAIL ORDER CO.
Climax House
Falisbrook Road, London SW16 6ED
SPECIAL EXPRESS MAIL ORDER SERVICE

TRANSISTORS-INTEGRATED CIRCUITS

All transistors, I.C's offered are new and branded. Manufactured by Mullard, Texas, RCA, Ferranti, Motorola, ITT, etc.

AA119	0.20	BD121	1.50	NE555	0.45	1N4148	0.07	7406	0.55
AA130	0.13	BD123	1.50	OA5	0.75	1N5400	0.14	7407	0.55
AA132	0.15	BD124	1.00	OA7	0.55	1N5401	0.16	7408	0.28
AA213	0.25	BD131	0.51	OA10	0.55	1S44	0.06	7409	0.28
AA215	0.31	BD132	0.54	OA47	0.14	1S920	0.08	7410	0.20
AAZ17	0.25	*BD135	0.35	OA70	0.30	1S921	0.08	7410	0.26
AC107	0.75	*BD136	0.36	OA79	0.30	2G301	1.00	7413	0.45
AC125	0.30	*BD137	0.37	OA81	0.30	2G302	1.00	7416	0.40
AC126	0.25	*BD138	0.40	OA85	0.30	SG306	1.10	7417	0.40
AC127	0.25	*BD139	0.43	OA90	0.08	2N404	0.60	7420	0.20
AC128	0.25	*BD140	0.40	OA91	0.08	2N696	0.25	7422	0.25
AC141	0.20	BD144	2.00	OA95	0.08	2N697	0.16	7423	0.35
AC141K	0.30	BD181	1.38	OA200	0.10	2N698	0.30	7425	0.35
AC142	0.20	BD182	1.48	OA202	0.11	2N705	0.80	7427	0.35
AC142K	0.25	BD237	0.80	OA210	0.75	2N706	0.12	7428	0.50
AC176	0.25	BD238	0.85	OA211	0.75	2N708	0.21	7430	0.20
AC187	0.25	BDX10	0.75	OA2200	0.65	2N930	0.26	7432	0.36
AC188	0.25	BDX32	2.25	OA2201	0.65	2N1131	0.26	7433	0.37
AC189	0.65	BDY20	1.42	OA2206	0.65	2N1132	0.26	7437	0.42
AC189	0.65	BDY60	0.75	OA2207	0.65	2N1302	0.37	7438	0.37
AC197	0.65	BF115	0.39	OC16	1.25	2N1303	0.37	7440	0.22
AC198	0.25	BF152	0.25	OC20	2.00	2N1304	0.45	7441AN	0.92
AC199	0.65	BF153	0.25	OC22	2.50	2N1305	0.45	7442	0.78
AD149	0.70	BF154	0.25	OC23	2.75	2N1306	0.50	7447AN	1.20
AD181	0.75	BF159	0.35	OC24	3.50	2N1307	0.50	7450	0.20
AD182	0.75	BF160	0.30	OC25	0.90	2N1308	0.60	7451	0.20
AD162	0.75	BF167	0.39	OC26	0.90	2N1309	0.60	7453	0.20
AF106	0.45	BF173	0.39	OC28	2.00	2N1613	0.33	7454	0.20
AF114	0.25	BF177	0.38	OC29	2.00	2N1671	1.50	7460	0.20
AF115	0.25	BF178	0.45	OC35	2.50	2N1893	0.33	7470	0.35
AF116	0.25	BF179	0.48	OC36	1.50	2N2147	1.40	7472	0.36
AF117	0.25	BF180	0.48	OC41	0.50	2N2148	1.65	7473	0.36
AF139	0.40	BF181	0.45	OC42	0.50	2N2218	0.33	7474	0.40
AF186	1.50	BF182	0.45	OC43	1.50	2N2219	0.42	7475	0.59
AF239	0.45	BF183	0.45	OC44	0.50	2N2220	0.35	7476	0.42
AFZ11	2.75	BF184	0.39	OC45	0.50	2N2221	0.22	7480	0.60
AFZ12	2.75	BF185	0.37	OC71	0.45	2N2222	0.25	7482	0.85
AS228	0.45	*BF184	0.12	OC72	0.45	2N2223	2.75	7483	1.00
AS229	0.50	*BF195	0.11	OC73	1.00	2N2368	0.17	7484	1.00
ASZ15	1.25	*BF196	0.13	OC74	1.50</				

Juventud Murcia on 1133kHz, ECS11 Radio Centro Madrid on 1385, EAK6 Radio Popular Zaragoza on 1394, EAJ34 Radio Gijon 1412kHz. EAK9 Radio Popular Valladolid 1430, EAJ20 Radio Sabadell 1475, EAJ48 Radio Vigo 1520 and EFE25 La Voz de Catabria in 1570kHz. Spanish broadcasters are also to be heard on 809, 953, 1025, 1124, 1259, 1313 and 1358kHz.



SHORT WAVE BROADCASTS

by *Derek Bell*

LONG-TIME friends of this column will remember our recent quest for information on the oldest working short wave set. A recent letter from **Joe Owens** of Dollegellau in North Wales set me to wondering if it is possible to find the oldest reader of PW; Joe's memories go back to 1929 which is not bad since the first PW saw the light of day on 1932. However, let us hear from someone who can remember PW's first issue which was published weekly and cost 3d!

Peter Grant from Sheffield has rescued a Convair 10 set from a dustbin. After a repair to the case and several new items of electronic "innards" Peter had the set back working. Came the day when, due to an injury at work, he had time on his hands and limited mobility. This time was filled with twiddling the knobs of the set rather than his thumbs and Peter found that the DX bug had really bitten. The net result is the following:—15440 WYFR Mass, at 2050, 6480 VOA to Africa at 1930 and 1700 Radio Kiev at 1945.

Peter is a little confused since the set is calibrated in metres and he wants to know how to convert this to frequency. Well, the simple answer is to use the formula:—Frequency (kHz) = 300000/wavelength in metres. For, say, 19.34m this produces a sum of 300000/19.34 this when resolved gives 15512kHz or 15.512MHz.

More information has come in regarding the HAC problems of reader **Tony Cook**. **C. M. Lindars** of Wallington has some information that may be of help to other sufferers. It seems possible that Tony has connected the top of the top of the tuning coil to the moving vanes of the tuning capacitor instead of to the fixed vanes. I must admit that I have never had the chance to evaluate the HAC or indeed have I read any test reports so I am in no position to help **Mark Cox** of Stanford le Hope Essex whose letter is rather vague. He has logged as follows:—1178 Radio Sweden at 2300, 9605 Radio Prague at 2015 and 7260 Radio Berlin International at 1945, also on an aforementioned HAC hung on the end of a 35ft wire aerial but the problem is that Mark asks "what do I do when the set stops oscillating?" This statement is so vague that I must ask Mark to supply more details.

Ken Willis of Scarborough has supplied a few items of transmitter news. The first is that FEBC are announcing their address as PO Box 2041, Mahe,

Seychelles and not 2141 as printed in WRTH. The second also concerns a WRTH misprint, the Radio Israel DX Show is on Sundays and not Saturdays as printed. Ken seems to have been sucking in quite a few good catches in these days of low sunspot counts namely:—9585 HCJB Quito at 0715, 15120 V. of Nigeria at 0730, 15320 Radio Japan at 0800 and 11740 Radio Australia at 0800.

At the time of writing it is reported that the BBC is to seek a channel for a "Euroservice", to be grafted on to the BBC World Service to cater for the European community. I have not heard any frequencies mentioned but I suspect that it will be in the medium wave band in 'Charles Molloy' country.

A letter that dropped on the mat recently asked me to mention a new DX club that is just getting off the ground so I will therefore crave your attention for the Halstead Youth DX Club. The title does belie its name however, for its spokesman, **Matthew Phillips**, assures me that they welcome members of all ages. So contact him at 4 Nether Court, Halstead, Essex. Our QSL news is by way of **Roy Patrick** of Derby who tells me that HCJB has issued a new series of twelve cards one of which is a diorama while others feature shots of the transmitter equipment.

A happy return to DXing was experienced by **John McFadden** of Belfast recently. He had to give up DXing for some two years but the 'disease' was only dormant and recently he had the symptoms return! The itching forefinger, the twitching ear and the urge to stay awake all night. He used the event as an excuse to purchase a receiver different from his previous one and he ended up with a Yaesu FRG7. For an aerial he wound 100 feet of wire three times round the room; difficult to open the door, if I may say so! The return also brought about a rethink of John's interest and resulted in him taking an interest in the Latin American bands. As a result of this he is surprised that a 1kW station can be heard in Britain. "Is it possible, he asks, for a less powerful station to be heard in the United Kingdom?" I would think not but having said that there will be readers who can prove me wrong since this old hobby of ours is a funny thing. Very often, given the right combination of refraction from the ionosphere or perhaps the right darkness path, a very weak station can propagate with very little attenuation over fantastic distances. To prove this and to put myself well in with the many LA fans I append a handful of John's loggings:—

4800 R. Lara, Venez. at 2345
 4823 R. Reloj, Costa Rica at 0615
 4920 R. Progreso, Honduras at 0410
 4965 R. Santa Fe, Colombia at 0440

John comments that he pulled in eleven LA stations in one night and I can understand the fever that gripped him, but I will comment that he was lucky in getting so many IDs. In my experience LAs tend to let the IDs fall by the wayside.

A four-page broadsheet from Radio Finland frankly admits they can only afford one foreign language service. They announce, however, that the external service will be relayed in future from the Turku and Helsinki medium wave transmitters as well as from the main Pori station. That about wraps it up for this month so I wish you and yours 73s.

Please note that my correct address is Derek Bell, 169 Max Road, Chaddesden, Derby.

VHF

by Ron Ham

ON arrival home at 0045 on April 7th my phone was ringing and Alan Baker G8LGQ Newhaven, was shouting "aurora" in my ear and by then he had already heard a strong signal from Graham Knight GM8FFX in Aberdeen on 2m SSB, plus some tone-A CW. A quick call to Charlie Newton G2FKZ London, (RSGB auroral co-ordinator) who said that the event began around 2200 on the 6th and activity was "very patchy". By 0115 I was back on the landline to G8LGQ in time for us to compare notes, and later, for both of us to record a very clear auroral signal from GM8FFX while he worked LA8WT, SM4DLT and G8JXN. It appears that 2m was not the only band affected as **Mark Turnbull**, G4ESA, Southsea, heard auroral CW on 20m during the evening of the 6th and **Andy Mephram** G4CBZ heard the same on 80m. This aurora may well have been caused by a spray of gas and a filament seen by **Cmdr. Henry Hatfield**, Sevenoaks, through his spectrohelioscope around noon on the 3rd. Unfortunately, further visual observation of the sun before the aurora was prevented by overcast skies. However, indication of more solar activity came from the BBC World Service when they reported an ionospheric disturbance at midnight on the 4th. During the afternoon of the 6th, **Roy Bannister** G8LXR Lancing, accompanied by G8LGQ heard solar noise on 2m. Throughout the event, which for us in Sussex ended around 0200, both G8LGQ and myself found that the beam heading (due north) was critical for the auroral signals.

John Smith, Cranleigh, recorded several bursts of solar noise with his 142MHz radio-telescope between the 8th and 13th and the largest of these, during the morning of the 12th, lasted for almost an hour, which ties up nicely with a report from **Cliff Ranft**, Guildford, who was making a routine cosmic noise observation at the time with his home-brew equipment at 30MHz. Cliff recorded a sharp decline in this noise (SCNA Sudden Cosmic Noise Absorption) due to sudden absorption of signals in the D layer. This may well be the first SCNA recorded by an amateur astronomer. **Mark Bennett** G4DIX Sevenoaks is studying propagation at 21 and 28MHz and reports that during the mid-evening on the 8th it was unusual to hear strong signals from north-American stations coming through on 21MHz.

Both Henry Hatfield and John Smith reported seeing a medium size sunspot group appear on the east limb on the 11th and by the 15th Henry had counted 7 spots. On the 16th I recorded solar noise at 136MHz and on the 17th I heard on the "grape vine" that 80m was upset. This was confirmed by **Nigel Golds** BRS36910 West Chiltington, Sx, who said that signals were very funny and that the band was noisy. Nigel had a job to hear stations which are normally very strong with him.

We are always pleased to hear from readers about their special interests. For the past six months John Smith has been using his 182MHz radio telescope, comprising a 30ft dish aerial, built by Ken Tapping and himself, and a home-brew mosfet front end,

Dicke switched and all temperature stabilised for making a radio survey of the Milky-Way. To date John is very satisfied with the results.

The Blackwater Valley Group G8ARO, G8BCO and G8ECO aim to study the relationship between the prevailing weather and microwave propagation while they enjoy QSOs with other amateur stations on 10GHz. Peter Kerry G8ARO Farnham is out with the group most Sundays, subject to weather, at their P location in the Hindhead area using his home-brew wide-band FM equipment. Their best 2-way DX so far is 70km and recently Peter worked G8BDJ/P (50km) who was located on Ditchling Beacon (Nr. Brighton).

Interest in microwave activity is growing and G8ARO says that the Blackwater Valley Group would be pleased to help others get going. There are beacons on 10.1GHz situated on the Isle of Wight GB3IOW and in Romford GB2LBH and it is hoped that GB3ALN will soon be operational from Alderney in the Channel Islands, which will enable 10GHz enthusiasts to study propagation on an oversea path. Arrangements for the group's Sunday activity can be heard by listening to their SSB net at 2200 on Saturday evening on 144.33MHz. They intend to be active on June 5 with a GE call sign to celebrate the Queen's Jubilee. More reports about microwave activity would be welcome.

The Portsmouth repeater GB3PH on 70cms (RB2 Input 434.65MHz and output 433.05MHz) began operation on March 26th and so far **Constance Hall** G8LY Lee-on-Solent has worked mobile stations near Dorset, Salisbury and on the Isle of Wight plus fixed stations in Fareham, Portsmouth and Southampton via PH. More reports are wanted from users east of the repeater.

I observed the first signs of the sporadic-E "season" during the early mornings of the 12th to 19th April when strong bursts of signals from the R1 television system were heard on 49.75MHz and at 1355 on the 16th I received a 599 signal from the German beacon DLOIGI (28.195MHz). Strong Continental broadcast signals interfered with Band II BBC stations in southern England on the 4th and 5th due to a fall in the prevailing high atmospheric pressure system. The AP was just above 30" from April 6 to 14 when it rose to 30.25" and began to fall around noon on the 16th providing a variable VHF opening. During the evening on 2m G8BCO heard GC8AAZ, and G8LGQ periodically heard strong signals from northern G and GW stations. I heard several French broadcast stations in Band II and around midnight, I heard amateur stations commenting about the strange conditions on 2m.

BROADCAST BANDS

Short Wave Reports by the 15th of the month to **Derek Bell**, 169 Max Rd., Chaddesden, Derby.
Medium Wave Logs to **Charles Molloy**, 132 Segars Lane, Southport, PR8 3JG.

AMATEUR BANDS

Logs covering any amateur band/s in band/alphabetical order by the 25th of the month to **Eric Dowdeswell** G4AR, **Silver Firs**, **Leatherhead Road, Ashted, Surrey, KT21 2TW.**

VHF

Reports on VHF matters to **Ron Ham**, **Faraday**, **Greyfriars, Storrington, Sussex RH20 4HE.**

RETURN OF POST MAIL-ORDER SERVICE

**R.C.S. 100 watt MIXER/AMPLIFIER
ALL VALVE CHASSIS**



Four inputs. Four way mixing, master volume, treble and bass controls. Suits all speakers. This professional quality amplifier chassis is suitable for all groups, disco, P.A., where high quality power is required. 5 speaker outputs. A/C mains operated. Slave output. Produced by demand for a quality valve amplifier. Send for details
Suitable carrying cabinet £14. Price **£85** carr. £2-50

ANOTHER R.C.S. BARGAIN!

ELAC 9 + 5in. HI-FI SPEAKER TYPE 59RM

This famous unit now available. 10 watts, 8 ohm.

Price **£3.25** Post 40p

**10" ELAC
HI-FI SPEAKER**



Large ceramic magnet.
Response: 50-18,000 cps.
Bass resonance 55 cps.
16 ohm impedance 10 watts.

Post 40p

£4.45

TEAK VENEER HI-FI SPEAKER CABINETS

MODEL "A". 20 x 13 x 12in.
For 12in. dia. or 10in. speaker
Illustrated. Price **£14.50** Post £1-60

MODEL "B". BOOKSHELF
For 13 x 8in. or 8in. speaker.
Price **£7.50** Post £1

E.C.S. BOOKSHELF
SPEAKERS
Size 14in. x 9in. x 6in. approx.
Response 50 to 14,000 cps
6 watts rms 8 ohms.
Price **£16 pair** Post £1-30

LOUDSPEAKER CABINET
WADDING 18in. wide. 20p ft.

GOODMANS CONE TWEETER

3 1/2in. diam. 18,000 C.P.S. 25 WATTS 8Ω **£3.25**
8in. Andax 15 watts £4.95.
5in. EMI mid range £5

BARGAIN 4 CHANNEL TRANSISTOR MONO MIXER. Add musical highlights and sound effects to recordings. Will mix Microphone, records, tape and tuner with separate controls into single output. 9 volt battery operated. Price **£5.75**

TWO CHANNEL STEREO VERSION OF ABOVE **£7.50.**

BARGAIN 3 WATT AMPLIFIER. 4 Transistor Push-Pull Ready built with volume, treble and bass controls. 18 volt battery operated. Mains Supply **£2-95.**

THE "INSTANT" BULK TAPE ERASER & HEAD DEMAGNETISER. suitable for cassettes, and all sizes of tape reels. A.C. mains 200/240V. Leaflet S.A.E. Price **£4.50** Post 40p

WAFER THIN HEATING ELEMENTS

OFFERING 1001 USES for every type of heating and drying applications in the home, garage, greenhouse, factory (available in manufacturing quantities). Approx. size 10 1/2 x 8 1/2 x 1/2 in. Operating voltage 200/250V. a.c. 250 watts approx. Printed circuit element enclosed in asbestos fitted with connecting wires. Completely flexible providing safe Black heat. British-made for use in photocopyers and print drying equipment.

Ideal for home handymen and experimenters. Suitable for Heating Pads, Food Warmers, Convector Heaters, etc. Must be clamped between two sheets of metal or asbestos, etc., to make efficient clothes dryers, towel rails—ideal for airing cupboards. Ideal for anti-frost device for the garage—preventing frozen radiators or acting as oil sump heater. Use in greenhouse for seed raising and plant protection. Invaluable aid for bird houses, incubators, etc., etc. Can be used in series for lower heat. Or in parallel for higher heat applications.

ONLY **40p** EACH (FOUR FOR **£1.50**)

ALL POST PAID—Discounts for quantity.

BAKER MAJOR 12" £14.95



Post £1
30-14,500 c/s. 12in. double cone, woofer and tweeter cone together with a BAKER ceramic magnet assembly having a flux density of 14,000 gauss and a total flux of 145,000 Maxwells. Bass resonance 40 c/s rated 25 watts. NOTE: 4 or 8 or 16 ohms must be stated.

Module kit. 30-17,000 c/s with tweeter, crossover, baffle and instructions. **£18.95**

Please state 4 or 8 or 16 ohms. Post £1.60

**BAKER SPEAKERS
"BIG SOUND"**

Robustly constructed to stand up to long periods of electronic power. As used by leading groups. Useful response 30-13,000 cps. Bass resonance 55 cps.

GROUP "25"

12in 30 watt
4, 8 or 16 ohms.

£11.95

Post £1

GROUP "35"

12in 40 watt
4, 8 or 16 ohms.

£13.95

Post £1

GROUP "50/12"

12in 60 watt professional model. 8 ohms or 16 ohms. With aluminium presence dome.

£20.95

Post £1.60

GROUP "50/15"

15in 75 watt
8 or 16 ohms.

£24.95

post £1.60

Send for leaflets on Disco, P.A. and Group Gear.

**BAKER 150 WATT
QUALITY
TRANSISTOR
MIXER/AMPLIFIER**

Professional amplifier using advanced circuit design. Ideal for disco, groups, P.A. or musical instruments. 4 inputs 4 way mixing. Master treble, bass and volume controls. 3 speaker output sockets to suit various combinations of speakers. 4-8-16 ohm. Slave output. A/C mains. Guaranteed. Details S.A.E. 150w SLAVE VERSION £80
Latest 50 watt Model **£49** Carr. £1-00

100 WATT DISCO AMPLIFIER CHASSIS

MADE BY JENNINGS MUSICAL INSTRUMENTS **£52**
4 speaker outputs, vol., treble, bass controls
CAN BE USED AS 100WATT SLAVE Carr. £1

B.S.R. SINGLE PLAYER DECK

3 speed. Plays all size records. Stereo Cartridge. Cueing device. Ideal Disco Deck. Post 75p **£13.50**
Autochanger Version with balanced arm **£17.50.**

**QUALITY LOUDSPEAKER
ENCLOSURE**

Teak veneered 3/4 in thick wood cabinet. Size 18 1/2 in x 18 1/2 in x 8 1/2 in. Weight 23lb. This cabinet features a wide mesh Silver Grill covering a separate compartment for mounting Tweeters or Mid-Range Horn. The fully sealed bass compartment is cut out for 8 1/2 in. Woofer 25-95. Carr. £1-60
Baffle could be cut for larger speaker.

P.W. SOUND TO LIGHT DISPLAY

Complete kit of parts with R.C.S. printed circuit. Three channels. 600 to 1,000 watts each. As featured in Practical Wireless. Price **£14.00**
Cabinet extra £3.

8 inch PHILIPS LOUDSPEAKER

4 ohm. 4 watt. ceramic magnet **£1.95**
General purpose replacement unit.

MAINS TRANSFORMERS Post 50p

6 VOLT 1 AMP. £1.00 3 AMP. £1.40
12 VOLT 300 MA. £1.00 750 MA. £1.30
30 VOLT 5AMP. AND 34 VOLT 2AMP G.T. £3.45
20 VOLT 1 AMP. £1.75 1 AMP. £2.00 2 AMP. £2.20
20-0-20 VOLT 1AMP. £2.95 30 VOLT 1 1/2 AMP. £2.50
40 VOLT 2 AMP. £2.95. 0-20-40-80 VOLT 1 AMP. £3.50

PERIOD LOUDSPEAKER CABINETS

Two styles available, Regency and Queen Anne. Size approximately 34 x 19 x 16in. These cabinets are slightly soiled and are priced from £10 each. Callers only.

**BAKER DISCO SPEAKERS
HIGH QUALITY—BRITISH MADE**

2 x 12" CABINETS

for Disco or PA all fitted with carrying handles and corners. Black finish. Other cabinets in stock. SAE For leaflet

**50
WATT
R.M.S.
£52**

Carr. £3

**70
WATT
R.M.S.
£56**

Carr. £3

**100
WATT
R.M.S.
£69**

Carr. £4



1 x 15" + 1 x 12" 100 WATT CABINET
Size 36" x 24" x 15" **£75.00.** Carr. **£5**

Ideal for Disco, Organ or PA work. High quality. Full range.

"SUPERB HI-FI"

12in 25 watts

A high quality loudspeaker, its remarkable low cone resonance ensures clear reproduction of the deepest bass. Fitted with a special copper drive and concentric tweeter cone resulting in full range reproduction with remarkable efficiency in the upper register.
Bass Resonance 25cps
Flux Density 14,500 gauss
Useful response 20-17,000cps
8 or 16 ohms models.

£22.50 Post £1.60

"AUDITORIUM"

12in. 35 watts

A full range reproducer for high power, Electric Guitars, public address, multi-speaker systems, electric organs. Ideal for Hi-Fi and Discotheques.
Bass Resonance 35cps
Flux Density 15,000 gauss
Useful response 20-16,000cps
8 or 16 ohms models.



£20.95 Post £1.60

"AUDITORIUM"

15in. 45 watts

A high wattage loudspeaker of exceptional quality with a level response to above 8,000 cps. Ideal for Public Address, Discotheques, Electronic instruments and the home Hi-Fi.
Bass Resonance 35cps
Flux Density 15,000 gauss
Useful response 20-14,000cps
8 or 16 ohms models.

£24.95 Post £1.60

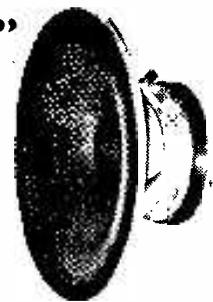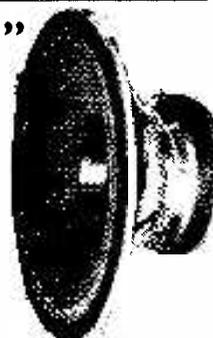

Loudspeaker Cabinet Wadding 18in wide. 20p per ft.

Hi-Fi Enclosure Manual containing plans, designs, crossover data and cubic tables, 68p

RADIO COMPONENT SPECIALISTS 337 WHITEHORSE ROAD, CROYDON
Open 9—6 Wed. 9—1 Sat. 9—5 (Closed for lunch 1.15—2.30)

Minimum post 30p. Components Lists 10p. Cash price includes VAT Access & Barclay cards welcome. Rail Selhurst. Tel. 01-684 1665

B. BAMBER ELECTRONICS

Dept. PW, 5 STATION ROAD, LITTLEPORT, CAMBS, CB6 1QE
Telephone: ELY (0353) 860185 (2 lines) Tuesday to Saturday

PLEASE ADD 8% VAT UNLESS OTHERWISE STATED

RED LEDs (Min. type) 5 for 70p.

VIDICON SCAN COILS (Transistor type, but no data) complete with vidicon base £6-50 each. Brand New.

FULL RANGE OF BERNARDS/BABANI ELECTRONICS BOOKS IN STOCK. S.A.E. FOR LIST.

NEW FOR THE VHF CONSTRUCTOR. A range of tuned circuits on formers with slugs and screening cans. Frequencies quoted are approximate, and range can be greatly extended by using varying capacitors in parallel. Type S (4in. square, dummy type). Type SA 20 to 30MHz (when 33pf fitted in parallel). Type SB 35 to 50MHz (with link winding). Type SC 70 to 100MHz (with link winding). Type SD 135 to 175MHz (with link winding). Type M (Min. 4in. square type). Type MA 19 to 28MHz (when 33pf fitted in parallel). Type MB 22 to 32MHz (when 33pf fitted in parallel). Type MC 25 to 35MHz (when 33pf fitted in parallel). Type MD 30 to 50MHz (when 33pf fitted in parallel). Type ME 45 to 60MHz (when 33pf fitted in parallel). Type MF 100 to 200MHz (without slug) when 0 to 30pf variable fitted in parallel. All the above coils available in packs of five only (same type) at 50p per pack of 5.

PLASTIC PROJECT BOXES with screw on lids (in Black ABS) with brass inserts.

TYPE N63 approx. 4 1/2in. x 3 1/2in. x 1 1/2in. 60p each. (OTHER SIZES AVAILABLE SHORTLY)

MULLARD 85A2 85V STABILISER VALVES (Brand New) 70p each or 2 for £1-20.

TO3 transistor insulator sets, 10 for 50p.

NUT SPINNER SETS - SPIRALUX Model 2210 6A sizes, 0, 1, 2, 3, 4, 5, 6, 8. £4-20. Model 2230 Metric sizes 4, 4.5, 5, 5.5, 6, 7, 8, 9, 10mm. £4-50.

110V NEONS, SCREW-IN-TYPE, 4 for 50p.

4MHz XTAL PACKS (10 assorted types between 4MHz and 5MHz), our selection only. £1 Pack.

MINIATURE PLIERS. High quality "Crescent", made in USA. £4-35 + VAT (35p).

SIDE CUTTERS. High quality. £3-70 + VAT 30p.

MAGNETIC DEVICES PROGRAMMERS. Contain 9 fully adjustable cams and 9 change over micro-switches (rated approx. 1A at 240VAC). Needs slow-motion motor to drive (not supplied). Ideal for disco lights, sequence switching, etc. ex equipment £1-50 each.

GARRARD 9V DC MINIATURE MOTORS, Type 318M, 3200 RPM governed, size approx. 1 1/2in. dia. x 1 1/2in. high, with 2mm spindle. Brand New. 60p each or 2 for £1.

SILICON HIGH VOLTAGE RECTIFIER STICKS, BY185 (new) 35kV 2.5mA £1 each, BY140 (ex-equip) 12kV 2.5mA 45p each.

VARIABLE STABILISED POWER SUPPLY, mains input, 0-24V output, stabilised and current limiting at 500mA + 32V at 50mA. Brand new by British manufacturer. Size approx. 7 1/2 x 4in. complete with external 5kΩ 3-turn pot for voltage control. Connection data supplied. £7.

14 DIL REED RELAYS, 5 to 12V DC, 450 ohm coil. Designed to work directly from TTL Logic. Single Pole Change over. Contact ratings 28V 1/4A 3W. £1-75 each.

SPECIAL OFFER ... STARPHONE HIGH BAND RF PCB BOARDS, with conversion data for making into a good 2M Converter. (All that is needed: 1 xtal, 7 caps, 2 resistors, and 9V DC.) PCB contains 2 Dual gate Mos. Fet RF stages (3N140), Diode ring mixer, 3 stage Osc/Multiplier. All on one PCB, approx size 6" x 1 1/2", ext. connections, 9V DC supply, AGC (can be left fixed bias, or RF gain control) Ant. input, IF output (works from a few MHz to over 30MHz). All Brand New. £6-50 each, while stocks last.

BSX20 (VHF Osc/Mult), 3 for 50p.
BC108 (metal can), 4 for 50p.
PBC108 (plastic BC108), 5 for 50p.
BFY51 Transistors, 4 for 60p.
BCY72 Transistors, 4 for 50p.
PNP audio type TO5 Transistors, 12 for 25p.
BF52 (UHF amp/mixer), 3 for 50p.
2N3819 Fet., 3 for 60p.
BC148 NPN SILICON, 4 for 50p.
BC158 PNP SILICON, 4 for 50p.
BAY31 Signal Diodes, 10 for 35p.
BA121 Varicap Diodes, 4 for 50p.

SMALL MAINS SUPPRESSORS (small chokes, ideal for radio, Hi-Fi inputs, etc.), approx. 1/2in. x 1 1/2in., 3 for 50p.

PERSPEX TUNER PANELS (for FM Band 2 tuner) marked 88-108MHz and Channels 0-70, clear numbers, rest blacked out, smart modern appearance, size approx. 8 1/2in. x 1 1/2in., 2 for 35p.

PLUGS AND SOCKETS
J-Type Plugs 50 ohm, 60p each, 3 for £1-50.
PL259 Plugs (PTFE), brand new, packed with reducers, 65p or 5 for £3.
SO239 Sockets (PTFE), brand new (4-hole fixing type), 50p each or 5 for £2-25.

SOLDER SUCKERS (Plunger Type), Standard Model, £4-50. Skirted Model, £4-95. Spare Nozzles 60p each.

WELLER SOLDERING IRONS
EXPERT. Built-in spotlight illuminates work. Pistol grip with fingertip trigger. High efficiency copper soldering tip.

EXPERT SOLDER GUN S100D £9-90.
EXPERT SOLDER GUN KIT (spare bits, case, etc.) £12-50.
Spare Bits 35p pair.

NEW MARKSMAN RANGE OF SOLDERING IRONS.

S115D 15W 240V £3-80.
S125D 25W 240V £3-80.
S140D 40W 240V £4-20.
S125DK 25W 240V + bits etc., KIT £4-90.
SPECIAL 12V version S125-12 25W 12V £3-80.
BENCH STAND with spring and sponge for Marksmen irons £2-38.
Spare Bits MT9 (for 15W) 50p, MT5 (for 25W) 45p, MT10 (for 40W) 50p.
ALL PRICES + 8% VAT.

TCP2 TEMPERATURE CONTROLLED IRON. Temperature controlled iron and PSU. £27 + VAT (£2-18).

SPARE TIPS
Type CC single flat. Type K double flat fine tip. Type P, very fine tip. £1 each + VAT (8p).

MOST SPARES AVAILABLE.

MULTICOE SOLDER
Size 5 Savbit 18 s.w.g. in alloy dispenser, 32p + VAT (3p).
Size C15AV18 Savbit 18 s.w.g., 56p + VAT (4p).
1/2 Kg. (1-1lb) 80 x 40, 20 s.w.g. on plastic reel £3.

A LARGE RANGE OF CAPACITORS AVAILABLE AT BARGAIN PRICES, S.A.E. FOR LIST.

MIXED COMPONENT PACKS, containing resistors, capacitors, pots, etc. All new. Hundreds of items. £2 per pack, while stocks last.

ALU-SOL ALUMINIUM SOLDER (made by Multi-core). Solders aluminium to itself or copper, brass, steel, nickel or tinplate. 16 s.w.g. with multicore flux, with instructions. Approx. 1 metre coil 40p pack. Larger reel £2-75.

VARICAP TUNERS Mullard Type ELC1043/05. Brand New. £4-40 + 12 1/2% VAT.

BARGAIN PACK OF LOW VOLTAGE ELECTROLYTIC CAPACITORS. Up to 50V working. Sastronic Manufacture. Approx. 100. £1-50 per pack + 12 1/2% VAT.

Mobile Converters, 24V DC input 13-8V at approx. 3-4A DC output, fully stabilised, £3-50 each (ideal for running 12V car radio from 24V lorry battery).

We now stock Spirulux Tools for the electronic enthusiast. Screwdrivers, Nut Spanners, BA and Metric sizes, pop rivet guns, etc. S.A.E. for list.

TWIN I.F. CANS, approx. 1in. x 1/2in. x 1in. high, around 3.5-5MHz, 2 separate transformers in 1 can, internally screened, 5 for 50p + 12 1/2% VAT.

Dubilier Electrolytics, 50µF, 450V, 2 for 50p.
Dubilier Electrolytics, 100µF, 275V, 2 for 50p.
Plessey Electrolytics, 470µF, 63V, 3 for 50p.
TCC Electrolytics, 1000µF, 30V, 3 for 50p.
Plessey Electrolytics, 1000µF, 180V, 40p each (3 for £1).

Dubilier Electrolytics, 5000µF, 35V, 50p each.
Dubilier Electrolytics, 5000µF, 50V, 60p each.
ITT Electrolytics, 800µF, 25V, high grade, screw terminals, with mounting clips, 50p each.
Plessey Electrolytics, 10,000µF at 63V, 75p each.
Plessey Cathodray Capacitors, 0-04µF at 12-5kV. DC. Screw terminals. £1-50 each.
PLEASE ADD 12 1/2% VAT TO ALL CAPACITORS.

TV PLUGS AND SOCKETS
TV Plugs (metal type), 5 for 50p.
TV Sockets (metal type), 4 for 50p.
TV Line Connectors (back-to-back sockets), 4 for 50p.
Please add 12 1/2% VAT.

Terms of Business: CASH WITH ORDER. MINIMUM ORDER £2. ALL PRICES INCLUDE POST & PACKING (UK ONLY). SAE with ALL ENQUIRIES Please. PLEASE ADD VAT AS SHOWN. ALL GOODS IN STOCK DESPATCHED BY RETURN. CALLERS WELCOME BY APPOINTMENT ONLY.

SOUTHERN VALVE COMPANY

Upper Floor, 8 Potters Road,
New Barnet, Herts. Tel: 01-440 8641

"QUALITY" Branded Valves—90 day guarantee.
ALL NEW & BXD VALVES (incl. tax)—many makes.

AZ31	80p	PC85	44p	PY801	43p
DY86/7	38p	PC88	62p	UBF89	47p
DY802	50p	PC89	50p	UC85	46p
EB91	18p	PCC189	58p	UCH42	80p
ECC81	36p	PCF80	41p	UCH81	42p
ECC82	36p	PCF82	45p	UC82	42p
ECC83	36p	PCF86	58p	UCL83	58p
ECC85	40p	PCF200	95p	UF41	47p
ECC88	48p	PCF801	50p	UF89	42p
ECH42	80p	PCF802	55p	UL41	75p
ECH81	44p	PCF805	£1-45	UL84	45p
ECH83	82p	PCF806	75p	UY85	40p
ECH84	58p	PCF808	£1-45	UZ6	72p
ECL80	52p	PCH200	85p	UZ8	60p
ECL82	48p	PCL82	40p	U91	60p
ECL83	75p	PCL83	POA	6/80L2	75p
ECL86	50p	PCL84	48p	6BW7	65p
EF80	38p	PCL85		6F23	60p
EF85	38p	PCL805	62p	6F28	75p
EF86	52p	PCL86	50p	6V6	60p
EF89	38p	PCL200	£1-40	6L6 (near 99p equiv KT86)	
EF183	38p	PD500	£3-25	20L1	70p
EF184	38p	PFL200	75p	20P4	70p
EH90	58p	PL36	70p	30C1	40p
EL34	£1-00	PL81	50p	30C15	70p
EL41	72p	PL81A	54p	30C17	75p
EL84	38p	PL82	38p	30C18	£1-45
EL509	£2-75	PL83	46p	30F5	50p
EM84	50p	PL84	48p	30FLL	
EY86/7	38p	PL500		30FL2	£1-60
EY500A	£1-60	PL504	90p	30L1	35p
EZ40/1	53p	PL508	£1-10	30L15	65p
EZ80	38p	PL509	£2-00	30L17	70p
EZ81	35p	PL519	£2-80	30P12	65p
GY501	£1-10	PL802	£2-10	30P19	95p
GZ30	75p	PY33	52p	30PLL	£1-40
PC86	63p	PY81/3	40p	30PLL3	£1-00
PC88	63p	PY88	43p	30PL14	£1-10
PC97	60p	PY500	£1-20	30PL15	85p
PC900	48p	PY500A	£1-20	30P4MR	90p
PCC84	35p	PY800	48p		

We offer return of post service. Post free over £15-00. Postage: 1st valve 12p, extra valves 6p. Max. 75p. Minimum order 65p. Most types available, send sae for lists. Discount Prices. All prices subject to alteration without notice due to market fluctuations etc. Telephone enquiries welcomed, sae with enquiries PLEASE! C.W.O. ONLY. No C.O.D. Export enquiries welcomed. VAT invoices on request. Mail order only.

Save on Calculators!

TEXAS
SR52 (mag card prog, 20 memories) @ £188
SR56 (key prog, 100 steps, 10 memories) @ £55-42
PC100A (Print Cradle for SR52/56) @ £174-10
SR51-11 (3 mem/stats, eng' notation) @ £43-00
T130 (15 levels of brackets) @ £15-88
LIBRARIES FOR SR52 @ £24-85
SR40 (Successor to SR50A) @ £24-42

HEWLETT PACKARD
21 (8 + 2, scientific) @ £60
25 (key programmable, 49 steps) @ £105
25C (continuous memory prog scien) @ £142
27 (Scientific/Management) @ £130
67 (mag card prog, 224 steps) @ £330
91 (Portable Sci. with Display and Printer) @ £236
97 (mag card + printer) @ £370

CASIO
CQ1 (Calculator, clock, alarm, stop watch) @ £29
*PRO FX1 (mag card prog, 11 mems, 127 steps) @ £125
@ £125

*FX202P (continuous memory, key prog) @ £69-90
*FX201P (11 mems, 127 steps, key prog) @ £49-86
FX2000 (6 + 2, sci/trac', LCD, 1000 hrs bat life) @ £25

FX1000 (6 + 2, sci/trac'. LCD, 11 hrs bat life) @ £19
FX21 (6 + 2) @ £13-92
FX5000EP (Scientific Printing Calculator) @ £198
We sell all Casio LCD calculators S.A.E.
We sell all Casio LCD watches S.A.E.


* Free Mains Adaptor with these items.
CQ1 Adaptor @ £3

CBM
4190R (90 functions) @ £30-40
PRO100 (8+2, key prog, 72 steps, 10 mems) S.A.E.
N60 (Navigator) M55 (Maths) S61 (Stats) S.A.E.
Sinclair Cambridge Prog. 32 Prog. Steps @ £14-92
We sell all makes of print/display calculators. S.A.E. for our prices.

We accept University/Govt/Company purchase orders by Telex or Phone. All prices include V.A.T. @ 8%. S.A.E. for brochures. All prices include P & P. Mail order only. C.W.O. to:—

KRAMER & CO., Dept. P.W.5, 9 OCTOBER PLACE, HOLDERS HILL ROAD, LONDON NW4 1EJ. Tel. 01-2032473. Telex 868941 ATTN. KRAMER. WE EXPORT WORLD-WIDE.

INTER-LOCKING PLASTIC STORAGE DRAWERS

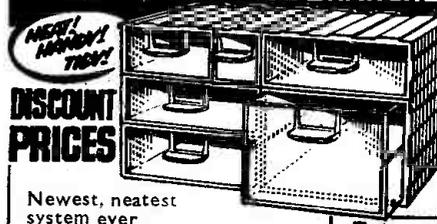

Newest, neatest system ever devised for storing small parts and components: resistors, capacitors, diodes, transistors, etc. Rigid plastic units interlock together in vertical and horizontal combinations. Transparent plastic drawers have label slots. 1D and 2D have space dividers. Build up any size cabinet for wall, bench or table top.

AS SUPPLIED TO POST OFFICE, INDUSTRY & GOVERNMENT DEPTS.

SINGLE UNITS (1D) (5ins x 2 1/2ins x 2 1/2ins). £2-90 DOZEN.
DOUBLE UNITS (2D) (5ins x 4 1/2ins x 2 1/2ins). £4-90 DOZEN.

TREBLE (3D) £4-90 for 8.
DOUBLE TREBLE 2 drawers, in one outer case (6D2), £7-25 for 8.

EXTRA LARGE SIZE (6D1) £6-25 for 8.
PLUS QUANTITY DISCOUNTS!
Orders over £20, less 5%.
Orders over £60, less 7 1/2%.

PACKING/POSTAGE/CARRIAGE: Add 75p to all orders under £10. Orders £10 and over, please add 10% carriage.

QUOTATIONS FOR LARGER QUANTITIES
Please add 8% V.A.T. to total remittance
All prices correct at time of going to press

FLAIRLINE SUPPLIES
(Dept. PW7)
124 Cricklewood Broadway, London NW2
Tel. 01-450 4844

COMPLETE *digital clock kits*
REAL TEAK CASE



"DELTA"

TEAK OR PERSPEX CASE 6" x 2 1/2" x 3"

FEATURES:

4 Red 1/4 inch high LEOS. 12 hour display with AM/PM indication. Power failure indicated by flashing display. Precise accuracy from mains frequency. Beautiful Burma Teak case or stylish Perspex (State first & second colour choice: White, Red, Blue, Green, Black).

NON ALARM:

Complete kit including Teak Case £13.50 incl. Module Kit excluding case £9.50 incl.

ALARM EXTRAS:

Pulsed alarm tone. Tilt operated "Snooze" period. Automatic brightness control. Simple setting.

ALARM:

Complete kit including Teak case £16.50 incl. Module Kit excluding case £13.00 incl.

PERSPEX CASES:

50p LESS than Teak.

READY BUILT:

Extra £1.00 on complete clocks. Extra 50p on Modules.

TIMER FACILITY:

Count in seconds up to 9m 59sec. Extra 50p.

NON ALARM **£12.50** + VAT + £1.00

ALARM **£15.28** + VAT + £1.22

INCLUDING P & P



"ALPHA" £12.00 incl.

Ready Built. Non Alarm. Perspex only. 4 digits phosphorescent green. 1/2" high 12 or 24 hour display.

Discount on orders over 5 clocks or kits. Overseas: Add £2.50 for Airmail.

Send payment with order. SAE for details.



BARON

(PW 1) 6 GOWER RD, SOUTHVIEW HOUSE,
ROYSTON, HERTFORDSHIRE
Phone Royston (0763) 43695



BOOKS for
Electronics Enthusiasts



COMING SOON—Radio, TV & Audio Technical Reference Book - S.W. Amos. The complete reference book compiled by 31 experts in all aspects of radio, TV & audio.

Spring 77. 1,200 pages

COMING SOON—Beginner's Guide to Radio—8th Edition - Gordon J. King. Completely updated and rewritten it surveys the whole field of radio.

Summer 77. 260 pages

SPECIAL SERIES FEATURE

Master Books

Authoritative yet easily understood by those with no technical knowledge whatsoever, the texts are supplemented by many highly informative illustrations. Each book is written by an expert in his own special field.

MASTER ELECTRONICS IN MUSIC

T.D. Towers

Contents: Creating Musical Sounds by Electricity. Making Musical Instruments Louder. Musical Special Effects by Electronics. Electronic Keyboard Instruments. Electric Guitars. Magnetic Tape Music. The Robot Drummer. Music Synthesizers. Music by Computer. Index.

130 pages. £2.50

MASTER HI-FI INSTALLATION

Gordon J. King

Contents: How it Works. The Amplifier. Programme Signal Sources. Importance of a Good F.M. Signal. The Loudspeaker. Mono, Stereo & Quadrophonic Sound. Four-channel Techniques. Room Effects. Best Use of Controls. Terminology. Index.

150 pages. £2.50

MASTER STEREO CASSETTE RECORDING

I.R. Sinclair

Contents: Stereo Systems. Signal Sources. Controls and Facilities. Making the Recording. Replaying and Monitoring. Essential Maintenance. Aids to Better Recording. Noise Reduction Systems. Cassette Recorder and Hi-Fi.

140 pages. £2.50

STANDARD WORKS

FOUNDATIONS OF WIRELESS AND ELECTRONICS

9th Edition. M.G. Scroggie. 552 pages. £3.75

RADIO VALVE AND SEMICONDUCTOR DATA

10th Edition. A.M. Ball. 240 pages. £2.00



Newnes Technical Books

Borough Green, Sevenoaks, Kent TN15 8PH

THIS is the Catalogue you need to solve your component buying problems!



- The finest components catalogue yet published.
- 200 A-4-size pages.
- About 5,000 items clearly listed and indexed.
- Nearly 2,000 illustrations.
- Bargain List sent free.
- At £1.40, incl. p. & p., the catalogue is a bargain.

Send the coupon below now.

POST THIS COUPON with cheque or P.O. for £1.40

Please write your Name and Address in block capitals

NAME

ADDRESS



HOME RADIO (Components) LTD., Dept. PW
234-240 London Road, Mitcham, Surrey CR4 3HD

(Regn. No
London 912966)

LYNX ELECTRONICS (LONDON) LTD

92 BROAD STREET, CHESHAM, BUCKS.

Tel. (02405) 75154

P. and P. 30p — Overseas 90p — Matching 20p per pair. ACCESS WELCOME
VAT 8% except for items * which are 12½% — No VAT Overseas.

Prices correct
as at 30th April '77

THYRISTORS

PIV	1A	3A	3A	4A	6A	8A	10A	15A	18A
(TO5) (ST-UD)	(C106)	(C220)	(C220)	(C220)	(C220)	(C220)	(C220)	(C48)	(C220)
200	0-35	0-50	0-45	0-40	0-50	0-60	0-68	1-14	—
400	0-40	0-60	0-50	0-45	0-87	0-88	0-98	1-40	—
600	0-65	0-85	0-70	—	1-09	1-19	1-26	1-80	—

BT108 £1.00, BT107 £1.60, BT108 £1.60, BT109 £1.00, BT116 £1.00, 2N3525 £0.50.

FM TOUCH TUNER

P.W. MARCH '77
Semiconductor Pack £16.95
Resistor Pack (exc. VRS) £2.55
Capacitor Pack (exc. C1 42, 43) £3.95
ALL THREE PACKS £22.45
All prices include P. and P. and VAT

RETURN OF POST SERVICE

New Price List 20p

Diodes contd

BYX36-900	0-18
BYX36-1200	0-21
BYX38-300	0-50
BYX38-600	0-55
BYX38-900	0-60
BX38-1200	0-65
BZX61 Series	0-26
BZX83 Series	0-11
BZY88 Series	0-11
OA5	0-50*
OA10	0-40
OA85	0-12
OA90	0-08
OA91	0-08
OA200	0-09
IN914	0-04*
IN4001	0-04*
IN4002	0-05*
IN4003	0-06*
IN4004	0-07*
IN4005	0-08*
IN4006	0-09*
IN4007	0-10*
IN4148	0-04*

TRIACS—Plastic TO-220 Package Isolated Tab

	4A	6-5A	8-5A	10A	15A	
	(a)	(b)	(a)	(b)	(a)	(b)
100V	0-60	0-60	0-70	0-70	0-83	0-83
200V	0-64	0-64	0-75	0-75	0-87	0-87
400V	0-77	0-78	0-80	0-83	0-97	1-01
600V	0-96	0-99	1-01	1-10	1-21	1-26

N.B.—(a) without internal diac. (b) with internal diac.

TTL7400 Series

7400	0-18	7401	0-18	7402	0-18	7403	0-18	7404	0-18	7405	0-18	7408	0-18	7409	0-18	7410	0-18	7412	0-25	7413	0-40	7414	0-72	7417	0-43	7420	0-15	7425	0-30	7427	0-30	7430	0-16	7432	0-28	7437	0-80	7441AN	0-76	7442	0-65	7445	0-90	7447AN	0-81	7448	0-81	7470	0-32	7472	0-26	7473	0-30	7474	0-32	7475	0-47	7476	0-36	7480	0-55
------	------	------	------	------	------	------	------	------	------	------	------	------	------	------	------	------	------	------	------	------	------	------	------	------	------	------	------	------	------	------	------	------	------	------	------	------	------	--------	------	------	------	------	------	--------	------	------	------	------	------	------	------	------	------	------	------	------	------	------	------	------	------

Regulators

747	1-80	750	1-80	7805	0-45	7812	1-50	7815	1-50	7818	1-50	LM340-5	1-35	LM340-12	1-35	LM340-15	1-35	LM340-18	1-35
-----	------	-----	------	------	------	------	------	------	------	------	------	---------	------	----------	------	----------	------	----------	------

L.E.D.

2 Red	0-13	2 Green	0-20	2 Clear	0-10
-------	------	---------	------	---------	------

SPECIAL OFFER SECTION

SG309K IATO3 5v. 0-95 TIL209 Red Led. 0-10
MODULE FCS8000 ££2-95
NPN TO-3 Power Transistors. Fully tested but unmarked. Similar to 2N3055 except: BVCEO = 50+ VCE (gain) = 20- at 3A VCE SAT < 1.3V at 3A
5 pcs £1.00, 25 pcs £4.00, 50 pcs £7.50, 100 pcs £13.00
ITT Branded Transistors. Medium Voltage, High Gain Ideal for Power Supplies, Inverters, etc.

Transistors

AC126	0-15	AC127	0-16	AC128	0-16	AC128K	0-25	AC141	0-22	AC141K	0-34	AC142	0-18	AC142K	0-32	AC176	0-16	AC176K	0-32	AC187	0-18	AC187K	0-36	AC188	0-18	AC188K	0-32	AD149	0-45	AD161	0-35	AD162	0-35	AF114	0-20	AF115	0-20	AF116	0-20	AF117	0-20	AF118	0-50	AF124	0-25	AF125	0-25	AF126	0-25	AF139	0-35	AF239	0-37	AL102	1-45	AL103	1-30	AU107	3-30*	AU110	1-75*	AU113	1-60*	BC107	0-12	BC107B	0-12	BC108	0-12	BC108B	0-12	BC109	0-12	BC109B	0-12	BC109C	0-15	BC117	0-19*	BC119	0-25	BC125	0-18*	BC128	0-20*	BC140	0-32	BC141	0-28	BC142	0-23	BC143	0-23	BC147	0-09*
-------	------	-------	------	-------	------	--------	------	-------	------	--------	------	-------	------	--------	------	-------	------	--------	------	-------	------	--------	------	-------	------	--------	------	-------	------	-------	------	-------	------	-------	------	-------	------	-------	------	-------	------	-------	------	-------	------	-------	------	-------	------	-------	------	-------	------	-------	------	-------	------	-------	-------	-------	-------	-------	-------	-------	------	--------	------	-------	------	--------	------	-------	------	--------	------	--------	------	-------	-------	-------	------	-------	-------	-------	-------	-------	------	-------	------	-------	------	-------	------	-------	-------

CMOS PLASTIC

4000BE	0-20	4001BE	0-20	4002BE	0-20	4006BE	1-05	4007BE	0-20	4008BE	0-93	4009BE	0-52	4010BE	0-52	4011BE	0-20	4012BE	0-20	4013BE	0-50	4014BE	1-00	4015BE	0-95	4016BE	0-54	4017BE	1-00	4018BE	1-10	4019BE	0-50	4020BE	1-12	4021BE	1-03	4022BE	0-95	4023BE	0-20	4024BE	0-86	4025BE	0-20	4026BE	1-55	4027BE	0-62	4028BE	0-91	4029BE	1-10	4030BE	0-55	4041BE	0-80	4042BE	0-83	4043BE	1-00	4044BE	0-94	4046BE	1-32	4049BE	0-54	4050BE	0-54	4069BE	0-30	4070BE	0-50	4071BE	0-26	4072BE	0-26	4081BE	0-20	4082BE	0-26	4510BE	1-42	4511BE	1-50	4516BE	1-35	4518BE	1-25	4520BE	1-20
--------	------	--------	------	--------	------	--------	------	--------	------

MEMORIES


2102A-6	3-60	2112A-4	4-75	6508	7-95	2102	2-50	2107	10-00	2112	4-50	2513	8-50	2602	2-50
---------	------	---------	------	------	------	------	------	------	-------	------	------	------	------	------	------

TO3 NPN 30 amp Transistors similar to 2N3771/2/3

Untested but no shorts or opens
1 Pcs 0-50
5 Pcs 2-00
10 Pcs 3-50
25 Pcs 7-50

H.A.C. SHORT-WAVE KITS

WORLD-WIDE RECEPTION

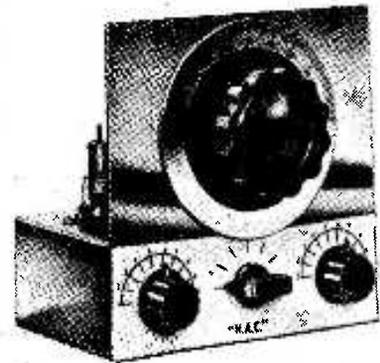

Famous for over 35 years for Short-Wave Equipment of quality. "H.A.C." were the Original suppliers of Short-Wave Receiver Kits for the amateur constructor. Special offer AR8 valves—70p each.

1977 "DX" RECEIVER

Complete kit—Price £7.20 (incl. p. & p. & V.A.T.). Customer writes: "I think the performance is outstanding for such an inexpensive and foolproof kit. I would wholeheartedly recommend this kit to anyone, however inexperienced, as an antidote to TV-titis, and as an entry into a fascinating hobby". This kit is ready to assemble and contains all genuine short-wave components, drilled chassis, valve, accessories and full instructions. Full range of other S.W. kits, including the famous model "K plus" (illustrated above). All orders despatched within 7 days. Send now for free descriptive catalogue of kits and components. Send stamped envelope for details.

"H.A.C." SHORT-WAVE PRODUCTS
P.O. Box No. 16, 10 Windmill Lane
Lewes Road, East Grinstead, Sussex
RH19 3SN

Please mention Practical Wireless when replying to Advertisements

RADIO STATION KITS for use with A510 Tx/Rx contains 2 × 8ft whip aerials, 135ft & 2 × 68ft long wire aerials, aerial tuner for use with whip, handset, head & mike set, 70 ohm twin feeder, counterpoise earth, morse key, etc all in carrying case with instructions for use in the 2 to 10Mc/s range new cond. **£13. IFF. TRANSPONDER** for use in the 1 KM/c band contains tunable tx & rx cavities, I.F. strip, blower, H.V. components, filters, & large number of misc parts, note these are less valves & ext soiled American surplus with circ **£10.80. SOLID STATE POWER SWT** fully isolated reqs I/P of 15V DC at 1 Ma to swt on will handle 3 amps at 240v or 13 amps when mounted on heatsink, opto coupled triac. okay for sound to light units **£2.40. V.H.F. POWER TRANSIS** type 2N3375 stud mt 28v 7.5w at 100Mc/s 3w at 400Mc/s new **£1.80. SPEAKER** 8 ohm size 5 × 3" new **£1.50. TEST SET** special for checking very high value res contains mains power unit, 500Ua meter, valves etc also an elec controlled stop watch cal in megs reads up to 30min with 60 sec sweep hand in transit case **£10.80. TRIMMERS** air spaced 20pf 10 for 80p, 18pf film trim 5 for 60p, 100pf film trim 3 for 60p, ceramic 3/10pf 5 for 60p, all new. **HEADPHONE LEAD** ext type with 1/4" stereo plug approx 30" open made of ends new 80p. **MERCURY SWT** size 1 × 1/2" with leads new 70p. **INTEGRATED CIRCS** type CA3014 w.b. amp & disc okay F.M. ULN2111A w.b. amp & prod det. TAA300 A.F. amp 1 watt into 8 ohm all new **85p** ea or 1 of ea **£1.80** with data. **METER UNIT X** pointer for use with RLL55 Rx as dual 115 Ua movements tested **£2.80. TRANS H.T.** pria 230v sec 1125-0-1125v at 565Ma new **£10.80. THERMOSTATS** wall mounting to control cooling fan 40/80°F rated 250v ac 5a have int thermometer req re calibration **£1.50. SWT UNIT** with 1 pole 24 way precision swt by Muirhead with qty of card res in scr box new **£2. HEAD & MIKE SET** for use with 19 set moving coil mike & headset nom 100 ohm new **£3.60. T.V. AERIAL FILTERS** high pass in scr box size 4 1/2 × 1 1/2 × 1 1/2" fitted lead with coax plug & sk new 4 for **£1.40. MISC VAR RES.** 5.5K 50 watt **£1.30**, 2.5K 3" dia **£1**, 5K & 10K both 50p ea all w.w. special 360° rotation 40K with 4 wipers at 90° 3 1/2" dia all 1/4 shafts new. **FIXED H.D.** 100 ohm 150 watt heater type **£1.30** also 4 ohm 50 watt tubular **75p** new. **AERIALS** etc ferrite rod 7" × 3/8th with long & med wave coils also 8 × 5/8th rod only both **80p** ea. Aerial telescopic chrome 36" open **95p** also aerial rods copper plated 1/4" dia × 12" will fit together 10 for **£1.30. HEADPHONE MATCHING TRANS & LEAD** will match 4k to 250 approx 5ft with standard 1/4" plug new **£1.40. REED RELAYS** for 12v ea contains 5 small reeds & two bias magnets size 1 × 1 × 1 1/4" 3 for **£1. NEONS** wire ended req 470K res for 240v new 5 for **50p. WIRE** 11 swg silver plated new **60p** per meter. **CRYSTAL OVENS** with 12 type Hc6/u holders & heaters for 24v, holders can be removed **£1.50. THE FOLLOWING ARE FOR CALLERS ONLY. SCOPES** Solartron 5" single beam DC to 15Mc/s large bench scope with circ sold as seen **£30. P.A. AMPLIFIERS** 100 watt valve type with c.u. & pre amp mains I/P **£27.** also horn speaker etc.

Above prices include carr/postage & V.A.T. carriage charges apply to mainland only, goods ex equipment unless stated new. SAE for List 17/1. or enquiry. Shop open Tues to Sat.

A. H. Supplies
122 Handsworth Road
Sheffield. S9 4AE. Phone 444278 (0742)

Practical Wireless, July 1977

Detecknow- ledgey

Detecknowledgey? No, we haven't forgotten how to spell - a number of you thought we had during our 'Tecknowledgey' ad series last year - it is simply an expression of Ambit's specialist topic for Summer 1977: Metal Detectors. In other words, we want you to know that we know about them, not just selling them, but how they work, and why. It is surprising how few people can explain the theory and application of first principles to metal locators. Things like why a bunch of keys can sometimes fail to register, whilst a 2p piece indicates at 8-10" or why a lump of iron reacts as if it were non-ferrous. See our new publication on the subject, a concise reference work that sets out to explain from first principles the various phenomena you will encounter. **£1.00 inc PP.**


PW SEEKIT COMPLETE KIT

Speaking of technology - that is, the application of scientific discoveries to practical situations and every day equipment - the PW Seekit can claim to have used a few innovative features only achievable with devices that we have been largely instrumental in promoting, so it is not surprising we are able to offer complete kits, and all parts for this exciting project. The complete Seekit-kit costs **£36.00** including PP AND VAT. This kit contains all electronic and plastic components (undrilled), bar things like glue, foil etc., which you are more than likely to have around the house. An SAE will bring you our new leaflet (A5 size please) with a more detailed list. Please note we can only consider service/testing on complete kits purchased from US.

BIONIC FERRET 4000

Not an electronically souped up rabbit catcher, but AMBIT's own VCO metal locator system. The **£40.74** ferret, (a saving of approx. **£3-529m** on the human version), comes complete with drilled, and cut-plastic parts, earpiece, all electronics etc. The **£40.74** includes PP and VAT at 8%. A free copy of metal Detecknowledgey with all kits.

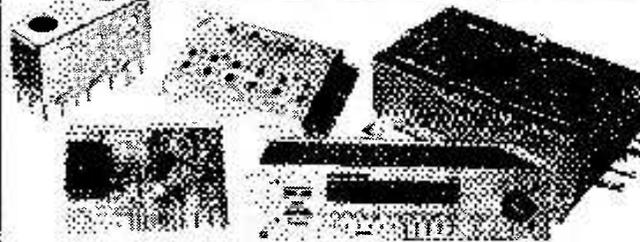Wireless COMPLETE TUNER KITS MODULES COMPONENTS etc



Linear ICs:		Transistors:					
CA3089E	1.94	7805UC*	1.55	40673 *	0.57	7253	26.50
MC1310P	2.20	78M12*	1.20	MEM680*	0.75	7252	26.50
TBA120	0.75	tda1412*	1.20	MEM614*	0.38	7020	built 6.95
uA753	1.80	7815*	1.55	Varicaps		7030	.. 10.95
HA1137W	2.20	78M20*	1.20	BA102	0.30	91196	.. 12.99
CA3090AQ	3.75	78M24*	1.20	BA121	0.30	92310	.. 6.95
HA1196	4.20	uA723CN*	0.80	BB104	0.45	7701	.. 26.50
uA720	1.40	TAA550*	0.50	BB105	0.32	71197	.. 11.35
CA3123E	1.40	8038CC*	4.50	MVAM2	1.35	Int. MkII complete	
HA1197	1.40	NE555V*	0.70	MVAM115	0.95	FM tuner kit	£65.00
TBA651	1.81	NE566/7*	2.50	MVAM125	0.90	(+£3 carriage)	
LM380N	1.00	NE565*	2.50	TUNER BITS		Larsholt Signalmaster	
LM381N	1.81	NE560*	3.50	EF5800	14.00	Mk 8 kit. Suitable for	
LM3900*	0.75	MC1312	1.50	EF5600	12.50	beginners too	£85.00
TDA2020	2.99	Digital ICs		EC3302	7.50	Audiomaster 25W Af	
TBA810	1.09	11C90DC	14.00	8319	12.00	kit amplifier	£79.00
TCA940	1.80						

VAT extra 12.5%. (*=8%). PP 22p per order - unless otherwise shown. Full catalogue (much new stuff since 76) 40p. SAE for free (A5) prices 37a High Street, Brentwood, Essex. CM14 4RH. (0277-216029)

ambit international

BENTLEY ACOUSTIC CORPORATION LTD.

7a GLOUCESTER ROAD, LITTLEHAMPTON, SUSSEX
All prices inclusive of V.A.T. at 12½% Telephone 6743

0A2	85	6AU6	40	6J5GT	81	12A7E	45	30P19	D1	50
0B2	40	6AV6	50	6J6	35	12AUG	50	30P4	DAF91	35
0Z4	55	6AW8A	84	6J7G	35	12AV6	80	30PL1	DAF96	60
1A3	80	6AX4	75	6J8A	90	12BA6	50	30PL13	DC90	70
1A5GT	55	6B8G	35	6K7G	35	12BR6	55	30PL14	DF91	30
1A7GT	80	6BA6	40	6K8G	50	12BH7	55	30PL15	DF92	25
1B3GT	55	6BC8	90	6K8GT	55	12BY7	85	35A3	DF96	80
1G6GT	1.00	6BPS	40	6L1	2.50	12E1	3.50	35C5	DK40	70
1H5GT	80	6BGGG	1.00	6L6GC	55	12J5GT	40	35D5	DK92	1.00
1L4	25	6BH6	70	6L7	1.50	12J7GT	70	38L6GT	DK96	70
1N5GT	75	6BJ6	65	6L18	80	12K5	1.50	35W4	DL96	60
1R5	50	6BK7A	85	6L19	2.00	12K7GT	50	35Z3	DM70	70
1R4	40	6BQ7A	60	6LD20	80	12K9	75	38Z4GT	DM71	75
1T4	80	6BR7	1.00	6N7GT	70	12Q7GT	50	35Z5GT	DY87/8	85
1U4	70	6BR8	1.25	6Q7G	50	12S47	75	43	DY87/8	85
1U5	85	6BS7	1.70	6Q7GT	50	12SC7	50	50B5	EB80C	5.00
2D21	55	6BV6	1.70	6Q7(M)	55	12SG7	55	50C5	EB80CF	5.00
2GK5	75	6BW7	60	6R7G	70	12SH7	50	50CD6G	EB80F	2.00
2X2	70	6BZ6	60	6SA7	55	12SJ7	60	50E1	EB80C	2.20
3A4	55	6C4	40	6SC7GT	75	12SK7	80	50EH5	EB80C	2.20
3B7	55	6C5G	40	6SG7	50	12SQ7	80	50L6GT1.00	E92CC	7.00
3D6	40	6C6	45	6SH7	55	12SR7	75	85A2	E182C	1.15
3Q4	80	6C9	2.00	6SS7	80	14S7	1.00	150B2	E182C	3.00
3Q5GT	70	6CB6A	80	6SK7GT	55	14S7	1.00	150B2	E182C	3.00
3B4	45	6CD6G	1.80	6SQ7	60	18	1.25	2158G	E188CC	2.50
3V4	80	6CG8A	90	6V6G	30	18AQ5	65	807	E1148	80
4CB6	75	6CL6	75	6V6GT	1.00	19G6	6.50	1625	E1148	80
5C88	75	6CL8A	95	6X4	45	19H1	4.00	5702	E1148	80
5R4GY	1.00	6CM7	1.00	6X5GT	85	20D1	1.00	5763	E1148	80
5U4G	80	6CU5	90	7B6	80	20F2	85	6057	E1148	80
5V4G	80	6D3	75	7B7	80	20L1	1.20	6060	E1148	80
5Y3GT	55	6E7	90	7H7	80	20P1	1.00	6067	E1148	80
5Z3	1.00	6DT6A	85	7Y4	2.00	20P3	1.00	6463	E1148	80
6Z4G	45	6EW6	85	7Y4	2.00	20P4	84	7025	E1148	80
6Z4GT	55	6E5	1.00	7Z4	80	20P5	1.50	7193	E1148	80
6/80L2	79	6F1	80	8D2	50	25A6G	70	9002	E1148	80
6A8G	1.40	6F6G	80	9BW6	80	25L6G	70	9006	E1148	80
6A7	55	6F14	90	9D7	70	25Y5G	80	ACPEN	E1148	80
6A65	35	6F15	85	10C2	70	25Z4G	80	ACPEN	E1148	80
6A7	80	6F18	80	10DE7	80	25Z5	75	AL60	E1148	80
6A85	70	6F23	65	10F1	67	25Z6G	80	ARP3	E1148	80
6A35	70	6F24	80	10F9	65	28D7	2.00	ATP4	E1148	80
6A35	45	6F25	1.00	10F18	65	30A5	75	AZ1	E1148	80
6A35	1.25	6F28	74	10D11	75	30C15	77	AZ31	E1148	80
6A35A	70	6F32	70	10P13	80	30C17	77	AZ41	E1148	80
6A35	70	6G6G	80	10P14	2.50	30F5	70	B36	E1148	80
6A35	68	6GH8A	80	12A6	65	30L15	75	BL63	E1148	80
6A35	80	6GK5	75	12AC6	80	30L17	70	CL33	E1148	80
6A35GT	1.00	6GU7	90	12AD6	80	30P4M	98	CY1C	E1148	80
6A35	60	6H6GT	30	12AE6	80	30P12	74	CY31	E1148	80

ECC84	35	EM80	55	PC97	75	PY83	50	U251	1.00	AC176	64	BY100	21
ECC85	39	EM81	60	PC900	40	PY88	60	U301	55	AC177	32	BY114	28
ECC86	125	EM83	60	PC984	39	PY500A1.35	U303	90	AC177	30	BY126	19	
ECC88	51	EM84	45	PC985	47	PY800	50	U404	75	AC178	23	BY127	20
ECC189	80	EM85	1.20	PC988	81	PY801	50	U401	80	AC179	23	BY210	30
ECC807	80	EM87	1.10	PC989	49	PZ30	50	U4020	75	AC20	21	BY211	30
ECF80	60	EM803	50	PCC189	52	QQV03/10	2.00	V23	95	AC21	30	BY212	80
ECF82	50	2.50	PCF80	40	Q895/10	1.00	V41	90	AC22	18	BY213	80	
ECF86	80	EY51	45	PCF82	45	Q8150/15	1.00	V4105	50	AC28	21	FSY11A	28
ECH21	2.00	EY81	45	PCF84	70	Q8150/15	1.00	VU111	1.00	AD140	42	FSY41A	28
ECH35	1.60	EY83	60	PCF86	57	Q8150/15	1.00	VU120	1.00	AD161	53	OA9	19
ECH42	71	EY86/7	37	PCF200	1.20	QV04/7.8	1.80	VU133	1.00	AD162	53	OA47	19
ECH81	40	EY88	55	PCF201	1.00	R19	75	W107	75	AF114	30	OA70	18
ECH88	50	EY91	50	PCF801	49	R19	75	W29	1.20	AF115	30	OA73	18
ECH84	50	EY92	50	PCF802	54	UABC80	45	X41	1.00	AF117	23	OA79	11
ECL80	45	EZ41	52	PCF806	53	UAF42	70	X66	1.00	AF121	35	OA81	11
ECL82	50	EZ40	52	PGH200	2.00	UBC41	50	Z759	5.85	AF124	36	OA85	11
ECL83	74	EZ81	40	1.00	1.00	UBC81	55	Transistors	AF180	56	OA90	14	
ECL84	65	GY501	95	PCL82	40	UBF80	50	& Diodes	AF186	64	OA91	11	
ECL85	70	GZ32	80	PCL83	48	UBF89	39	1N4744	16	BA115	18	OA95	11
ECL86	64	GZ33	1.80	PCL84	46	UBL21	2.00	2N404	21	BA116	91	OC44	12
EF22	1.00	GZ34	75	PCG86	85	UC92	50	2N966	61	BA129	14	OC45	13
EF41	75	HABC80	80	PCL805	60	UCC84	90	2N1756	58	BA130	12	OC46	18
EF73	1.75	HL23DD	68	PEN25	1.00	UCC85	45	2N1477	99	BA153	18	OC70	14
EF80	89	HL41DD	2.00	PEN45	1.00	UCF80	80	2N2297	28	BC107	14	OC71	13
EF83	1.25	1.00	1.00	PEN45DD	2.00	UCH21	90	2N2869	16	BC108	14	OC72	13
EF85	36	HL42DD	2.00	PEN453DD	2.00	UCH81	51	2N3053	38	BC109	14	OC74	26
EF86	45	1.00	1.00	UCL82	55	UCL82	55	2N3121	2.00	BC113	30	OC75	13
EF89	42	HN309	1.70	UCL85	87	UCL83	87	2N3703	23	BC115	18	OC76	18
EF91	50	HYR2	1.00	UCL88	51	UCL83	87	2N3709	23	BC116	30	OC77	32
EF92	50	HVR2A1.00	4020	1.00	1.00	UF41	70	AA119	18	BC118	26	OC78	18
EF97	90	KT41	1.00	PENDD	40	UF42	80	AA129	18	BCY10	53	OC78D	18
EF98	90	KT66	2.00	4020	1.00	UF80	40	AA129	18	BCY12	58	OC81	13
EF183	42	KT81	9.00	PL33	1.00	UF85	50	AAZ13	21	BCY33	23	OC81D	13
EF184	42	KT88	7.75	PL36	60	UF89	45	AC107	18	BCY38	26	OC82	13
EF804	1.75	KTW61	1.50	PL81	49	UL41	70	AC113	30	BCY38	26	OC82D	13
EL32	60	KTW62	1.50	PL81A	53	UL84	54	AC126	14	BF156	21	OC83	23
EL34	1.00	1.00	1.00	PL82	37	UM80	60	AC127	20	BF159	20	OC84	28
EL35	3.00	1.00	1.00	PL83	45	UY41	50	AC128	23	BF163	23	OC123	28
EL37	3.00	1.00	1.00	PL84	50	UY86	35	AC132	23	BF173	44	OC169	50
EL41	57	MHL6	90	PL504/500	90	U10	1.15	AC156	23	BF180	35	OC171	40
EL81	65	1.00	1.00	PL505	2.20	U12/14	1.15	AC157	30	BF185	47	OC200	55
EL84	34	F61	60	PL508	1.30	U25	71	AC165	30	BFY50	26	OC204	50
EL85	60	FABC80	45	PL509	2.20	U26	60	AC166	80	BFY51	23	OC205	50
EL95	67	PC38	62	PL519	2.80	U33	1.75	AC168	44	BFY52	23	OC206	1.05
EL360	1.80	PC88	62	PT4D	1.00	U35	1.75	MATCHED TRANSISTOR SETS:—					
EL506	1.20	PC92	55	PY80	50	U45	1.20	LP15 (AC113, AC154, AC157, AA120)	61p				
EL509	2.50	PC95	1.00	PY81	50	U48	80	per pack. 1/OC81D & 2/OC81, 50p.					
				PY82	40	U91	50	1/OC44 & 2/OC45, 50p; 1/OC82D &					
								2/OC82 56p. Set of 3/OC83 78p.					

Special offer of EF60 valves, soiled, but new and tested, £1 each.

All goods are unused, tested, and guaranteed. Despatch charges:—25p on all orders below £15 in value. Orders over £15 post free. Orders despatched same day as received. Any parcel insured against damage in transit for 5p per parcel extra. Terms of business available on request. Many others in stock too numerous to list. Please enclose S.A.E. for reply to any queries.

TRAMPUS ELECTRONICS LTD

58-60 GROVE RD WINDSOR, BERKS. SL4 1HS. TEL 54525

FAST SERVICE

ON EX STOCK ITEMS
NORMALLY 24 HOURS



SEVEN SEGMENT LED DISPLAYS
BRIGHT DL707 COM ANODE &
DL704 COM CATH. 0.3" £1*
DL747 0.6" JUMBO CA £1.25*

DIGITAL CLOCK IC 51224 £4*
ZENON STROBE TUBES £4 & £7*

RED LEDS 10P.

RED LEDS 209 STYLE 0.125"
OR 0.2" DIA. NO CLIP 10p*

TIL209 RED LED & CLIP 12p*
BIG 0.2" RED LED & " 14p*
GREEN OR ORANGE LEDS 29p*
ORP12 54p*2N5777/OC71 34p*

TRAMPUS THE GREAT
BRITISH
DISTRIBUTOR

INDUSTRIAL, EDUCATIONAL, TRADE &
EXPORT SUPPLIED, SEND FOR
OUR FREE CATALOGUE LIST SAE
MANUFACTURERS EXCESS STOCKS
PURCHASED, DISCOUNTS 10% OFF
100 up, 15% OFF 1000 up...

TOP DISCOUNTS.

INTEGRATED CIRCUITS

555 TIMER	34p*	LM380(60745)	£1
556 8 x 555	90p*	LM381 Preamp	£2
703 RF/IF AMP	29p	LM3900 4xOPA	53p*
709 TOPP or DIL26p		MC1303 2xPre	£2
710 DIL14	35p*	MC1310 stereo	£2
723 Regulator	44p	MC1312P SQ	£1.70
741 DIL 8pin	21p	MC1330	75p
741 DIL 14pin	31p	MC1339 Preamp	£2
741 1099	37p	MFC4000B IW	72p
747 DUAL 741	65p	MFC6030	£1
748 DIL 8 pin	38p	NE536 FETOPA	£2*
7805 5V1A+reg	£1.35*	NE540 or 550	£2*
7812 & 7815ea	£1.40*	NE55	

J. BIRKETT

Radio Component Suppliers

25 The Strait, Lincoln LN2 1JF Tel: 20767

BUTTERFLY PRE-SET MIDGET VARIABLE CAPACITORS 25 x 25pf @ 50p, 25 x 25pf Wide Spaced @ 55p, 38 x 38pf @ 60p, 38 x 38pf Wide Spaced @ 65p. Spindles easily extended.

50 AC 128 TRANSISTORS Branded but Untested @ 57p.

30 AF 117-OC 170 TRANSISTORS Untested @ 57p.

100 C 280 MULLARD CAPACITORS Assorted @ 57p.

JAPANESE 5K WITH S.P. SWITCH EDGEWISE POT @ 30p, 5 for £1.

500 + 500pf VARIABLE CAPACITOR Direct Drive @ 60p.

SILICON SOLAR CELLS 0.5 Volt 5 mA @ 35p.

10uf 50v.w. REVERSIBLE ELECTROLYTIC CAPACITORS FOR LOUDSPEAKER CROSSOVER NETWORKS 6 for 50p.

10 ASSORTED MULTI-TURN TRIMPOTS for 60p.

30 ASSORTED 10XAJ CRYSTALS from 5100 KHz to 7900 KHz @ £1.10.

20 ASSORTED VARI-CAP DIODES Untested at 45p.

200 ASSORTED 1/4, 1/2 Watt RESISTORS for 75p.

6 to 1 FRICTION DRIVES 1/2" Spindle at 55p.

1000uf 40v.w. ELECTROLYTICS. Size 1 1/2" x 1 1/2" at 3 for 35p.

250pf SOLID DIELECTRIC VARIABLE CAPACITORS at 33p each.

125 + 125pf VARIABLE CAPACITOR. Direct Drive at 55p each.

CRYSTALS 10X type 5 MHz @ 50p, 10XAJ Type 600 KHz @ 50p.

ELECTROLYTIC CAPACITORS 20 + 20uf 450v.w., size 2 1/2" x 1" @ 20p, 32 + 32uf 275v.w., size 2" x 1" @ 10p, 32 + 32uf 350v.w., size 2 1/2" x 1" @ 20p, 50 + 50uf 275v.w., size 2 1/2" x 1" @ 15p, 3300uf 40v.w., size 2 1/2" x 1 1/2" @ 50p, 4700uf 63v.w., size 4" x 1 1/2" @ 60p, 10,000uf 10v.w., size 2" x 1 1/2" @ 15p.

LARGE LED's Red @ 15p, Green @ 16p, Yellow @ 18p.

EX-GOVT. HIGH RESISTANCE HEADPHONES 1500 Ohm at £2.50 Pair.

100 POLYSTYRENE CAPACITORS. Assorted for 57p.

10 AMP S.C.R.'s 100 PIV @ 25p, 400 PIV @ 50p, 800 PIV @ 60p.

VHF DUAL GATE MOS FET's like 40673 @ 33p, 4 for £1.10.

10 x 10pf DIFFERENTIAL PRE-SET MINIATURE CAPACITORS @ 22p.

180 + 180pf VARIABLE CAPACITOR. Direct Drive @ 60p.

PLASTIC BRANDED TRANSISTORS BC 108 Type or BC 212 Type at 10 for 60p.

100 MINIATURE SILICON DIODES Assorted @ 57p.

200 + 200 + 100uf 300v.w. ELECTROLYTICS size 2 1/2" x 1 1/2" 10 for £1.80.

60 ASSORTED WIRE WOUND RESISTORS for 57p.

50 BC 107-8-9 ASSORTED TRANSISTORS Untested for 57p.

TANTALUM BEAD CAPACITORS 1uf 35v.w., 15uf 35v.w., 47uf 35v.w., 68uf 35v.w., 1uf 35v.w., 2.2uf 35v.w., 4.7uf 10v.w., 4.7uf 35v.w., 5uf 25v.w., 6.8uf 25v.w., 6.8uf 35v.w., 10uf 25v.w., 15uf 20v.w., 20uf 6v.w., 22uf 16v.w., 33uf 25v.w., 47uf 6v.w., all at 9p each.

SILICON NPN POWER TRANSISTORS Type BD 187 at 4 for £1.

2.5 GHz DUAL NPN TRANSISTORS Untested 4 Pair for 57p.

Please add 20p for post and packing on orders under £2.
Overseas orders at cost.

BURGLAR ALARM

EQUIPMENT SUPPLIES (TRADE)

Bell boxes plastic coated steel	£5.25
Magnetically operated door switch surface type	£0.65
Magnetically operated door switch flush type	£0.60
Bare magnet and reed switch	£0.25
Micro switches	£0.25
Micro switches with lever	£0.75
Vibro sensitive switch	£2.75
Pressure pads large 29" x 15" 4 wires	£1.75
Pressure pads stair tread size 4 wires	£1.50
Aluminium window foil 100ft. self adhesive	£2.00
Take off blocks for window foil per pair	£0.40
Heavy duty 6" bell 12V	£7.75
Siren 12V	£6.00
3" bell	£2.25
Key switch single pole + chrome plate	£3.00
Battery for above large HPI	£2.50
Heat detectors closed loop 135F	£3.50
Door loops	£0.75
Key blanks	£0.30
Ultra sonic heads 6-20ft. range	£45.00
Micro wave heads 6-20ft. range	£58.00
Power Pack for above in case	£15.00
Breaking glass detector 15ft. range	£20.00

CONTROL UNITS

Battery operated model	£14.00
Battery & mains model	£18.00
B.S. 4737 model battery + mains	£32.00
D.I.Y. battery model	£11.00
D.I.Y. battery & mains	£15.00

WALL AND FLOOR SAFES

2 brick size wall safe	£22.00
9 x 9 x 9 floor safe insurance approved	£27.00
9 x 12 x 15 floor safe insurance approved	£27.00
12 x 12 x 12 floor safe insurance approved	£27.00
money can be deposited while locked	£27.00

ALL PRICES + 12 1/2% VAT NO VAT EXPORTS.

ASTRO ALARMS

25 STOCKTON RD.
SUNDERLAND,
TYNE & WEAR.
ENGLAND. TEL:- 0783 77825

DISCOUNTS	
5+	10%
25+	15%
100+	20%
POST FREE	

Sparkrite Mk2

Capacitive discharge electronic ignition kit

VOTED BEST OF 8 SYSTEMS TESTED BY 'POPULAR MOTORING' MAGAZINE OCT 74



- * Smoother running
- * Instant all-weather starting
- * Continual peak performance
- * Longer coil/battery/plug life
- * Improved acceleration/top speeds
- * Optimum fuel consumption

Sparkrite Mk. 2 is a high performance, high quality capacitive discharge, electronic ignition system in kit form. Tried, tested, proven, reliable and complete. It can be assembled in two or three hours and fitted in 15/30 mins.

Because of the superb design of the Sparkrite circuit it completely eliminates problems of the contact breaker. There is no misfire due to contact breaker bounce which is eliminated electronically by a pulse suppression circuit which prevents the unit firing if the points bounce open at high R.P.M. Contact breaker burn is eliminated by reducing the current to about 1/50th of the norm. It will perform equally well with new, old, or even badly pitted points and is not dependent upon the dwell time of the contact breakers for recharging the system. Sparkrite incorporates a short circuit protected inverter which eliminates the problems of SCR lock on and, therefore, eliminates the possibility of blowing the transistors or the SCR. (Most capacitive discharge ignitions are not completely foolproof in this respect). All kits fit vehicles with coil/distributor ignition up to 8 cylinders.

THE KIT COMPRISES EVERYTHING NEEDED

Ready drilled pressed steel case coated in matt black epoxy resin, ready drilled base and heat-sink, top quality 5 year guaranteed transformer and components, cables, coil connectors, printed circuit board, nuts, bolts, silicon grease, full instructions to make the kit negative or positive earth, and 10 page installation instructions.

OPTIONAL EXTRAS

Electronic/conventional ignition switch.
Gives instant changeover from "Sparkrite" ignition to conventional ignition for performance comparisons, static timing etc., and will also switch the ignition off completely as a security device, includes: switch connectors, mounting bracket and instructions. Cables excluded. Also available RPM limiting control for dashboard mounting (fitted in case on ready built unit).

CALLERS WELCOME. For Crypton tuning and fitting service - phone (0922) 33008

PRICES INCLUDE VAT, POST AND PACKING.

IMPROVE PERFORMANCE & ECONOMY NOW

Note—Vehicles with current impulse tachometers (Smiths code on dial RV1) will require a tachometer pulse slave unit, £3.35 inc. V.A.T. p & p. E.D.A. 82 BATH STREET, WALSALL, WS1 3DE.

POST TODAY!

Quick installation
No engine modification required

Electronics Design Associates, Dept., P.W.7
82 Bath Street, Walsall, WS1 3DE. Phone: (0922) 33652

Name

Address

Mk. 2 DIY Ass. Kit @ £11.80	QUANTITY REQUIRED	I enclose cheque/PO's for £
Mk. 2 Ready Built Negative Earth @ £14.97		
Mk. 2 Ready Built Positive Earth @ £14.97		Cheque No.
Ignition Changeover switches @ £4.30		
R.P.M. Limit systems in above units @ £2.42		Send SAE if brochure only required.



SMALL ADS

The prepaid rate for classified advertisements is 17 pence per word (minimum 12 words), box number 40p extra. Semi-display setting £14.00 per single column inch (2.5cm). All cheques, postal orders etc., to be made payable to Practical Wireless and crossed "Lloyds Bank Ltd". Treasury notes should always be sent registered post. Advertisements, together with remittance, should be sent to the Classified Advertisement Manager, Practical Wireless, Room 2337, IPC Magazines Limited, King's Reach Tower, Stamford St., London, SE1 9LS. (Telephone 01-261 5846).

CONDITIONS OF ACCEPTANCE OF CLASSIFIED ADVERTISEMENTS

1. Advertisements are accepted subject to the conditions appearing on our current advertisement rate card and on the express understanding that the Advertiser warrants that the advertisement does not contravene any Act of Parliament nor is it an infringement of the British Code of Advertising Practice.
2. The publishers reserve the right to refuse or withdraw any advertisement.
3. Although every care is taken, the Publishers shall not be liable for clerical or printers' errors or their consequences.

NOTICE TO READERS

When replying to Classified Advertisements please ensure:

- (A) That you have clearly stated your requirements.
- (B) That you have enclosed the right remittance.
- (C) That your name and address is written in block capitals, and
- (D) That your letter is correctly addressed to the advertiser.

This will assist advertisers in processing and despatching orders with the minimum of delay.

Receivers and Components

TOUCH CONTROLLED LIGHTING KITS

These KITS replace conventional light switches and control 300W of lighting. No mains rewiring required. Insulated Touchplates. All with easy to follow instructions.

NEW! TSD300K—TOUCHSWITCH and DIMMER combined. ONE touchplate to switch light on or off. Brightness controlled by small knob. ONLY £5.95.

TS300K—TOUCHSWITCH. TWO touchplates ON and OFF—ONLY £3.67.

TS300K—AUTOMATIC. ONE touch plate. Light turns off after preset delay £3.67.

LD300K—LIGHTDIMMER KIT—£2.45.

CMOS (Motorola)			
4000	16p	4013	31p
4001	16p	4015	31p
4002	16p	4016	31p
4007	16p	4017	31p
4011	16p	4023	17p
4012	17p	4025	17p

TRIACS 400V TO220	NE555 8 pin DIL	36p
Case isolated TAB	741 8 pin DIL	24p
6-5A 80p 8-5A 85p	2N6027 (PUT)	34p
Diac 21p	2N3055	36p

QUANTITY DISCOUNTS ON REQUEST. ADD 8% VAT plus 25p P&P. Mail Order Only to:

T. K. ELECTRONICS (PW)

106 Studley Grange Road, London, W7 2LX

CONTROL Knobs. Black, slightly imperfect 5 for 50p P&P 15p. V. Laight, 14 Alexandra Road, Thames Ditton, Surrey.

VINTAGE RADIO
1920 to 1950

Receivers, valves, components, service data, historical research, books, magazines, repairs and restorations. A complete service for the collector and enthusiast of vintage radio.

S.a.e. with enquiries and for monthly newsheet. Full 1977 catalogue, 70p post paid.

TUDOR REES (Vintage Services), 64, Broad Street, Staple Hill, Bristol, BS16 5NL. Tel. Bristol 565472.

BRAND NEW COMPONENTS. 0.33W 5% Hi-Stability E12 series 4.7Ω-1M. Any selection 0.9p each. 0.8p 100+, 0.75p 1,000+. BC107/8/9 and BC147/8/9 all 8p each. Send SAE for our complete list of components. Inclusive prices. P & P 15p. C. N. Stevenson (PW) 304 Avery Hill Road, London SE9 2JN.

Precision Polycarbonate Capacitors

All High Stability—extremely Low Leakage					
440V AC RANGE			63V DC RANGE		
Value (μF)	Dimen- sions (mm) each	Price	Value (μF)	±1%	±2% ±5%
	L D	each			
0.1μF	27 12.7	£1.34	0.01-0.2	£1.80	£1.22 88p
0.15μF	27 12.7	£1.52	0.22-0.47	£1.82	£1.24 90p
0.22μF	33 16	£1.66	0.68μF	£2.06	£1.28 £1.00
0.25μF	33 16	£1.78	1.0μF	£2.26	£1.52 £1.08
0.33μF	33 16	£1.92	1.5μF	£2.50	£1.68 £1.20
0.47μF	33 19	£2.08	2.2μF	£2.80	£1.94 £1.42
0.5μF	33 19	£2.24	3.3μF	£3.42	£2.30 £1.84
0.68μF	50.8 22	£2.48	4.7μF	£4.00	£2.72 £2.24
1.0μF	50.8 22	£2.64	6.8μF	£4.88	£3.36 £2.66
1.5μF	50.8 25.4	£3.14	10μF	£6.94	£4.68 £3.56
2.0μF	50.8 25.4	£3.74	15μF	£9.92	£6.48 £4.96
			22μF	£13.32	£8.98 £6.80

TANTALUM BEAD CAPACITORS—0.1, 0.15, 0.22, 0.33, 0.47, 0.68, 1.0μF at 25/35V 10p*; 1.5μF/35V 11p*; 2.2μF/35V 12p*; 3.3μF/35V 13p*; 4.7μF/35V 13p*; 6.8μF/35V 17p*; 10μF 25V 17p*; 10μF 35V 21p*; 15μF/20V; 22μF/15V; 33μF/10V; 47μF/6.3V at 21p*; 68μF 3V 17p*; 100μF/8V 21p*.

TRANSISTORS & I.C.'s			
AC128	28p	BC184/212/3	18p
AC176	35p	BC214	13p
AD149	68p	BC238	17p
AF178	64p	BC267	26p
AF279	45p	BC268A	12p
BC107/8/9	12p	BC647	12p
BC114	15p	BC772	18p
BC147/8/9	10p	BD131/132	41p
BC153	16p	BF115	42p
BC157/8/9	12p	BF173	27p
BC177	18p	BF178	42p
BC182/183	12p	BF148	28p
		BF194/195	12p
		BF196/197	15p
		BF200	38p
		BF272/263	40p
		BFY50/51/52	22p
		BFX84/85	28p
		BFX86/87	31p
		BR101	41p
		GET872	15p
		OC44/OC46	40p
		OC71/72	45p
		TIP31A	55p

POPULAR DIODES—BA145 18p; BA148 18p; BA155 18p; BA156 15p; BR100 28p; BY126 15p; BY127 16p; OA47 11p; OA81 16p; OA90+91 7p; 1N914 7p; 10/88p; 1N916 8p; 10/77p 1844 7p; 10/80p 1N4148 6p; 10/55p; 1N4001 6p; 002 61p; 003 7p; 004 7p; 005 8p; 006 9p; 007 10p; TIL209 25p.

LOW PRICE ZENER DIODES—400mW, Tol. ±5% at 5mA. 3V; 3V3; 3V6; 4V7; 5V1; 5V6; 6V2; 6V8; 7V5; 8V2; 9V1; 10V; 11V; 12V; 13V; 13.5V; 15V; 16V; 18V; 20V; 22V; 24V; 27V; 33V. All at 10p each. 10/95p 50/£4.50, 100 for £8.00 (values may be mixed).

RESISTORS—High stability, low noise carbon film 5% ±W at 40°C, ±W at 70°C. E12 series only—from 2.2Ω to 2.2MΩ. ALL at 2p* each, 15p* for 10 of any one value, 95p* for 100 of any one value. SPECIAL PACK: 10 of each value 2.2Ω to 2.2MΩ (730 resistors) £6.50*.

SUBMINIATURE VERTICAL PRESETS—0.1W only: 50; 100; 220; 470; 680 ohm; 1k; 2k2; 4k7; 6k8; 10k; 15k; 22k; 47k; 100k; 320k; 680k; 1M; 2M5; 5M. All at 7p* each; 10/80p*; 100 for £5.00.

PLEASE ADD 25p POST AND PACKING ON ALL ORDERS. EXPORT—ADD COST OF SEA/AIRMAIL. Add 8% VAT to all items except those marked with * which are 12½%.

Send S.A.E. for additional stock lists. Wholesale price lists available to bona fide companies.

MARCO TRADING (Dept. P4),
The Old School, Edstaston, Wem, Shropshire.
Tel: Wirral 484/485 (STD 094 872)
(Proprs. Minicost Trading Ltd.)

SOWTER TYPE 3675
MULTITAP MICROPHONE TRANSFORMER

Primary windings for 600 ohm, 200 ohm and 60 ohm with Secondary loadings from 2K ohm to 10 K ohm Frequency response plus/minus ±dB 20 Hz to 25 KHz. Contained in well finished Mumetal box 33mm diameter by 22mm high, with colour coded end leads, low distortion. Delivery (small quantities) EX STOCK, HIGHLY COMPETITIVE PRICE FULL DETAILS ON REQUEST.

E. A. SOWTER LTD., Dedham Place, Ipswich, IP4 1JP. Telephone 0473 52794

BRAND NEW COMPONENTS BY RETURN.

Electrolytic capacitors 16V, 25V, 50V.—0.47, 1.0, 2.2, 4.7 & 10mfd.—5p. 22, 47—5½p. (50V—8p). 100—7p (50V—8p) 220—8p. (50V—10p) 470—11p. (50V—16p). 1000/16V—15p, 1000/25V—18p, 1000/50V—22p.

Subminiature bead tantalum electrolytics—0.1, 0.22, 0.47, 1.0, 2.2 @ 35V, 4.7/25V—11p. 10/25V—13p. 22/16V, 47/6V, & 100/3V—15p.

Mullard miniature ceramic E12 series 2% 63V. 10pf. to 47pf.—3p. 56pf. to 330pf.—4p.

Vertical mounting ceramic plate 50V. E12 series 22pf—1000pf. E6 series 1500pf—47000pf.—2p.

Polystyrene E12 series 63V horizontal mounting. 10pf to 1000pf—3p 1200pf. to 10000pf.—4p

Mullard polyester 250V vertical mounting E6 series. 0.01 to 0.1—4p. 0.15, 0.22—5p. 0.33, 0.47—5p. 0.68—11p. 1.0—13p. 1.5—20p. 2.2—22p.

Mylar (Polyester) Film 100V vertical mounting. 0.001, 0.002, 0.005—3p. 0.01, 0.02—4p. 0.04, 0.05—4½p.

Miniature resistors Highstab E12 series 5%. Carbon Film 0.25W 1Ω to 10MΩ. (10% over 1MΩ)—1p. Metal Film 0.125W, 0.25W & 0.5W 10Ω to 2MΩ.—1½p. Metal Film 1W, 2.7Ω to 10MΩ.—2p ea.

1N4148—3p. 1N4002—5p. 1N4006—7p. 1N4007—8p. BC107/8/9, BC147/8/9, BF157/8/9 & BF194 & 197—9p. Fuses 20mm, glass. 1½" glass & 1" ceramic. 2½p. Post 10p. (Free over £4.00) Prices inclusive of VAT.

THE C. R. SUPPLY CO.,
127, Chesterfield Rd., Sheffield S8.

VHF pocket portable radio tuning 108 to 136 MHz. Very sensitive. Easily adjusted to tune 144 MHz band. £16.50 (inc post & VAT). Romak Ltd, Dept PW, 10 Hibel Road, Macclesfield, Cheshire.

VALVES

Radio — T.V. — Industrial — Transmitting

We Dispatch Valves to all parts of the world by return of post, Air or Sea mail, 2700 Types in stock, 1930 to 1976. Obsolete types a speciality. List 20p. Quotation S.A.E. Open to callers Monday to Saturday 9.30 to 5.00 closed Wednesday 1.00. We wish to purchase all types of new and boxed Valves.

COX RADIO (SUSSEX) LTD.
Dept. P.W. The Parade, East Wittering,
Sussex PO20 8BN West Wittering
2023 (STD Code 024366)

CARBON FILM RESISTORS. 0.33W 5% Hi-stability E12 series 4.7Ω-1M. Any selection 0.9p each, 0.8p 100+, 0.75p 1,000+. Inclusive prices. P&P 15p. C. N. Stevenson (PW), 304 Avery Hill Road, London SE9 2JN.

Electrical

STYLI, CARTRIDGES & AUDIO LEADS etc. For the best at keenest prices send S.A.E. for free illustrated list to: Felstead Electronics (PW), Longley Lane, Gatley, Cheadle, Cheshire. SK8 4EE.

Service Sheets

LARGE SUPPLIERS OF SERVICE SHEETS AND COLOUR MANUALS

TV, RADIO, TUNERS, TAPE RECORDERS, RECORD PLAYERS, TRANSISTORS, STEREOGRAMS, RADIOGRAMS. ALL AT 75p EACH EXCEPT COLOUR TV & CAR RADIOS.

PLEASE STATE IF CIRCUIT WILL DO. IF SERVICE SHEET NOT IN STOCK, LARGE S.A.E. WITH ALL ENQUIRIES & ORDERS OTHERWISE CANNOT BE ATTENDED TO. UNCROSSED P.O.'s OR CROSSED P.O.'s RETURNED IF SERVICE SHEETS ARE NOT AVAILABLE. ALL SERVICE MEN, PLEASE NOTE, WE OPERATE A SAME DAY RETURN SERVICE. ALL CLAIMS OF NON-DELIVERY SHOULD BE MADE WITHIN SEVEN DAYS. NO OVERSEAS MAIL PLEASE. MAIL ORDER ONLY OR 'PHONE 01-458 4882. FREE TV FAULT TRACING CHART OR TV LIST ON REQUEST WITH ORDER.

C. CARANNA, 71 BEAUFORT PARK, LONDON, NW11 6BX.

SERVICE SHEETS, radio, TV etc. 10,000 models. Catalogue 24p, plus SAE with orders, enquiries. Telray, 154 Brook Street, Preston PR1 7HP.

SERVICE SHEETS, Radio, TV, etc., 50p and s.a.e. Catalogue 20p and s.a.e. **HAMILTON RADIO**, 47 Bohemia Road, St. Leonards, Sussex.

SERVICE SHEETS — COLOUR TV SERVICE MANUALS

Service Sheets for Mono TV, Radios, Record Players and Tape Recorders 75p.
Please send large Stamped Addressed Envelope.

We can supply manuals for most makes of Colour Television Receivers by return of post.
**B.R.C. PYE ECKO PHILIPS IIT/KB SONY G.E.C. HITACHI BAIRD ULTRA INVICTA
FERGUSON H.M.V. MARCONI AND MANY MORE**
Let us quote you. Please send a Stamped Addressed Envelope for a prompt reply.
Also comprehensive T.V. repair manuals by J. M. Court, S.A.E. for details.

G. T. TECHNICAL INFORMATION SERVICE
10 DRYDEN CHAMBERS, 119 OXFORD ST., LONDON W1R 1PA
MAIL ORDER ONLY

BELLS'S TELEVISION SERVICES For Service Sheets on Radio, TV, etc., 75p plus S.A.E. Colour TV Service Manuals on request. S.A.E., with enquiries to B.T.S., 190 Kings Road, Harrogate, N. Yorkshire. Tel: (0423) 55885.

Aerials

G2DYM PROJECTS AND AERIALS
IN ADDITION TO OUR USUAL AERIAL SERVICE FOR SWL's and the Tx Amateur we now offer a new Service:—
"THE BRITISH RADIO TECHNICAL ADVISORY SERVICE"

Full details S.A.E. and 3 x 8½p stamps. Briefly you send us details of your technical problem, we will quote you the cost of our written advice on any technical problem you have in the field of Radio Communication.

**LAMBDA ANTENNA STUD FARM
WHITEBALL, WELLINGTON, SOM.**

Books and Publications

SIMPLIFIED TV REPAIRS. Full repair instructions individual British sets £4.50, request free circuit diagram. Stamp brings details unique TV Publications (Ausepw) 76 Church Street, Larkhall, Lanarkshire.

RADIO BOOK SERVICE

World Radio TV Handbook 1977	£5-75
The Cathode Ray Oscilloscope and its Uses	£3-90
1st & 2nd Books of Transis Equiv & Substitutes (Set)	£1-55
Radio Receiver Constr'n using ICs & Transistors	£0-70
Radio Antenna H'book for Long Dist. Reception	£0-95
79 Electronic Novelty Circuits	£0-85
Audib Enthusiasts Handbook	£0-95
The Complete Car Radio Manual	£0-85
Solid State Power Supply Handbook	£0-95
ICs & Transistor Gadgets Construction Handbook	£0-70
Integrated Circuits Equiv & Substitutes Handbook	£0-95
Manual of Electronic Circuits for the Home	£0-80
Electronic Gadgets & Games	£0-95

NOTE NEW ADDRESS
3 CHILDRESFER COURT, WICKHAM RD, BECKENHAM KENT URS 20W

DATACharts: (UFOs) TV Detection; Sighting Recorder; Antigravity; Propulsion; Optical Transistor Detector; Radiation/Optical; Newsletter; each 80p. 5-Parameter (pHCapVAR) Multi-tester; Treasure-seeker (Microcircuit) £1.20 each circuit. R & E Publications, Highlands, Needham Market, Suffolk.

Wanted

WANTED NEW Valves, transistors, I.Cs, amplifiers, receivers, televisions (Anything Useful!) any quantity. Stan Willets, 37 High Street, West Bromwich. Tel: 021 553 0186.

WANTED—NEW VALVES, TRANSISTORS. TOP PRICES, popular types. Kensington Supplies (C), 367 Kensington Street, Bradford 8, Yorkshire.

For Sale

NEW ISSUES of "Practical Wireless" available from April 1974 edition up to date. Price 55p each:— Bell's Television Services, 190 Kings Road, Harrogate, N. Yorkshire. Tel (0423) 55885.

Ladders

LADDERS. Varnished. 20ft 9in extd. £25.33, Carr. £1.90. Leaflet. Also alloy ext. up to 62½ft. The Ladder Centre (WLS) Halesfield (1) Telford, Salop. Tel: 586644. Callers welcome.

Situations Vacant

APPOINTMENTS IN ELECTRONICS

Take your pick of the permanent posts in:

**MISSILES — MEDICAL
COMPUTERS — COMMS
MICROWAVE — MARINE
HARDWARE — SOFTWARE**

For expert advice and immediate action on career improvement, 'phone, or write to, Mike Gernat BSc.

Technomark
Engineering and Technical Recruitment

11 Westbourne Grove
London W2. 01-229 9239.

Educational

GO TO SEA as a Radio Officer. Write: Principal, Nautical College Broadwater, Fleetwood FY7 8JZ.

Miscellaneous

PRINTED CIRCUITS and HARDWARE

Readily available supplies of Constructors' hardware, Aluminium sheet and sections. Printed circuit boards, top quality for individual designs. Prompt service. Send 15p for catalogue.

**Ramar Constructor Services,
Masons Road, Stratford on Avon,
Warwicks. Tel. 4879**

OUTSTANDING HI-FI FM TUNER, comprises 7 transistor superhet design with Varicap tuning, AFC. Latest silicon circuitry, full coverage 88-102 MHz. Supplied built and tested with metal front, panel and instruction sheet. Only £9.95 plus 30p P&P. Gregg Electronics, 86-88 Parchmore Road, Thornton Heath, Surrey.

ALARM BUZZERS 3-12 VOLT Solid State Type AB1 £1.00 ea
MORSE PRACTICE OSCILLATORS Built-in Key Type M.P.O. 1 £2.00 ea
MINIATURE PLUG-IN RELAYS (VARLEY) 12 or 24 v. d.c. 4p, c/o, dust covers 40p ea
SPECIAL OFFER: 3 Relays for £1.00
VAT inclusive prices—please add 20p per item p & p.
BB SUPPLIES (Dept. D), 67 Westcliff Road, Ramsgate, Kent, CT11 9NP

GOLDRING CK2 BELT DRIVE TURNTABLE IN KIT FORM

Complete with SAU2 arm, template and easy-to-follow instructions.

Wow and flutter 0.15% peak, rumble weighted —60dB. Brand new in sealed cartons. 12 months guarantee. Outstanding value £19.95 + (£2 p/p & ins.). Plinth, cover, cartridge available separately, Cheque, P.O., M.O., Access, Barclaycard, American Express, Diners Club.

Lion House, 227 Tottenham Court Rd., London W.1. Tel. 01-580 7383

**ARMATURE & COIL WINDING
ENAMELLED COPPER WIRE**
Only top quality materials supplied.
All orders dispatched within 24 hrs.

S.W.G.	1 lb reel	½ lb reel
10 to 19	£2.95	£1.60
20 to 29	£3.15	£1.80
30 to 34	£3.45	£1.90
35 to 40	£3.65	£2.10

All prices are inclusive of P. & P. in U.K.
COPPER SUPPLIES, 102 Parrswood Road, Withington, Manchester 20. Tel: 061-445 8753

Musical Miracles!

by Dewtron®

Build your own synthesiser or musical effects using some of the huge range of DEWTRON modules. Or build fuzz or waa-waa at budget prices using special kits.

Send 25p for Catalogue from—

D.E.W. Ltd., 264 Ringwood Road, Ferndown Dorset BH22 9AR.

TV SOUND—kit including drilled PCB to build the Hi-Fi News TV sound isolator. Enables TV sound to be played through a hi-fi system. Only £3.75 inc. P&P. TVS Electronics, 95b Ardwell Avenue, Barkingside, Ilford, Essex.

BUILDING YOUR OWN SPEAKERS

An exponential horn will dramatically improve the realism from your moving-coil loudspeaker. Circular-section horns are difficult to make accurately—ask anyone who's tried it! But we now make a mid-range fibreglass horn that is easy to use. Build this unusual feature into your cabinet and hear the difference!

For more details and specification, send SAE to: **JAMES COOPER (ELECTRONICS) LTD.** 120 Castle Lane, Solihull, West Midlands.

A UNIQUE OPPORTUNITY

We can show you how to earn a lot of money working part or full time from home. We are the ONLY company in the U.K. offering this unique information. A basic interest in electrical engineering is necessary. Government Departments are making use of our system, why don't you. For complete return of post details send a large stamped addressed envelope to:—

Magnum
Dept. PW.
Brinkway Trading Estate,
Brinkway, Stockport.

DO-IT-YOURSELF LOUDSPEAKERS for hi-fi are our speciality. Full range of components and accessories including chassis speakers, crossovers, sound absorbent, grille fabrics etc., always available. We stock the fabulous value Helme speaker kits complete with full and easy instructions, also Peerless and Wharfedale kits. Just about the lowest prices anywhere! Send 8½p stamp for bargain list to: Audioscan, Dept. PW-777, 4 Princes Square, Harrogate, North Yorkshire.

100 RESISTORS 75p
¼w 5% C/Film 2.2Ω—2.2MΩ (E12)
10 each of any value

C60 CASSETTES 30p All Cassettes in Plastic Case with Index and
C90 CASSETTES 45p Screwed Assembly.

All prices include VAT Add Postage 10p in £1.
Quantity Discounts: **SALOP ELECTRONICS**
10 Units 5% **23 WYLE COP**
50 Units 7% **SHREWSBURY**
100 Units 10% **Tel. 53206**

BUILD THE TREASURE TRACER MK III Metal Locator



- Variable tuning
 - Britain's best selling metal locator kit; 4,000 sold
 - Weighs only 22oz. Fitted with Faraday shield.
 - Speaker and earphone operation
 - Knocks down to only 17in.
 - Prebuilt search coil assembly
 - Thoroughly professional finish
 - As seen on BBC1 and BBC2 TV
 - You only need soldering Iron, screwdriver, pliers and snips
 - Five transistor circuit
- Send stamped, addressed envelope for leaflet

Complete Kit £14.75 Built & tested £19.75
Post £1.00 + £1.18 VAT Post £1.00 + £1.58 VAT


MINIKITS ELECTRONICS,
6a CLEVELAND ROAD,
LONDON, E18 2AN (Mail order only)

AERIAL WIRE. High quality p.v.c. covered multi-strand copper, 50ft, 85p (15p); 75ft, £1.28 (17p); 100ft, £1.67 (25p); 150ft, £2.51 (34p); 200ft, £3.36 (39p); 250ft, £4.19 (46p); 300ft, £4.97 (48p); P&P in brackets. **A.1 Radio Components, 19 The Borough, Canterbury, Kent CT1 2DR.**

MORSE CODE TUITION AIDS

Cassette 3-1-12 w.p.m. for amateur radio examination.
Cassette 5-12-24 w.p.m. for professional examination preparation.
Morse by light system available. Morse Key and Buzzer Unit for sending practice.
Prices: Cassettes (including booklets) £4; Morse Key and Buzzer £4. Prices include VAT, postage, etc., overseas £1 extra.

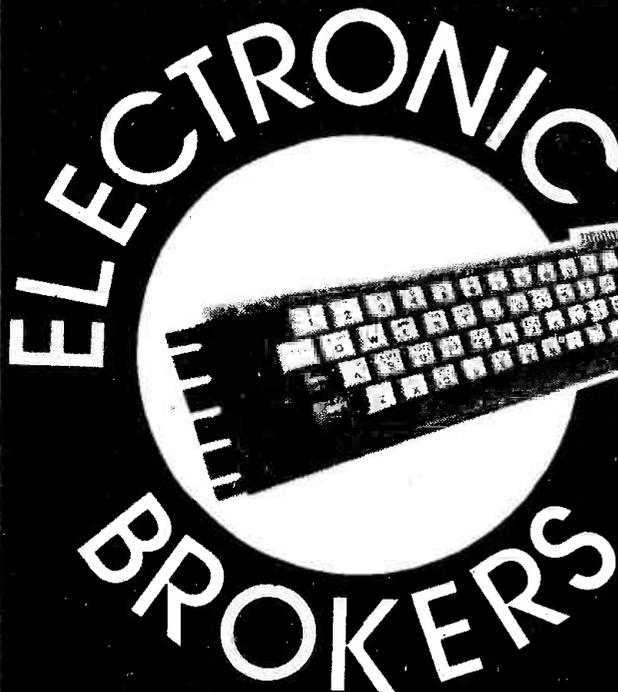MHEL ELECTRONICS (PW)
12 Longshore Way, Milton,
Portsmouth PO4 8LS



ELECTRONIC BROKERS LTD
49/53 Pancras Road
London NW1 2QB
Tel: 01-837 7781

Computer parts for hobby, experimental, educational and professional use.

FRESH STOCKS OF THE POPULAR CLARE-PENDAR ASCII KEYBOARD TYPE KB6 NOW TO HAND

ASCII-Coded TTL-compatible 4-bank alphanumeric keyboards with ROM encoder chip, strobed output, two-key rollover and debounce. Standard 7-bit ASCII code (no parity) Supplied complete with circuit diagrams and code chart.

SPECIFICATIONS

Power Supply: +5VDC +/-5% 150mA, -12VDC +/-10% 10mA. Output Logic Levels: Data Bits 1 through 7: 0V "O", 4.5V "1", 5-25V. Fan Out: One standard TTL load. Strobe: 2.6v "1", 5-25V; Ov "O", 46V. Fan Out: 10 standard TTL loads. Strobe signal delay 10 milliseconds nominal to allow data to stabilise.
KB6: 56-station standard Teletype layout, AS RECOMMENDED FOR PRACTICAL WIRELESS VIDEO-WRITER PROJECT. Price £39.50 + £1 P&P + 8% VAT (send £43.74).

NEW ARRIVALS

FABULOUS NEW 96-STATION CRT DISPLAY KEYBOARDS. 8-bit ASCII code, upper and lower case output PLUS separate numeric pad. TTL Logic. Delayed strobe signal and two-key rollover feature. Mounted in attractive box, overall dimensions 20½ x 7½ x 3¼". Price £65.00 + £3 carriage + 8% VAT (send £73.44).

BCD-CODED 54-STATION KEYBOARD, brand new, upper and lower case outputs. Mounted on double PCB and set in attractive panel incorporating 5 indicator lamps and on/off switch. Dimensions 15½ x 5½ x 2¼". Price £39.50 + £2 P&P + 8% VAT (send £44.82). Also available. A few only of the above model WITHOUT ENCODING OR PANEL. Price £25.00 + £1.50 P&P + 8% VAT (send £28.62).

18-KEY CALCULATOR KEYBOARDS (0-9, CK +, -, x, =). Make/break switches mounted on PCB. Overall dimensions 150 x 110 x 40mm. Price £4 plus 50p P&P + VAT (Send £4.86p).

JUST RECEIVED - SPECIAL PURCHASE OF DATA DYNAMICS MODEL 390 TELETYPE TERMINALS IN BRAND NEW CONDITION.

TERMINALS - LARGE STOCKS AVAILABLE. ASR33 Teletype from £625.00. KSR33 Teletype from £425.00. ASR35 Teletype from £750.00. IBM731/0 Golfball Typewriter from £275.00.

SPECIAL OFFER

Cossor DIDS 401.2A Visual Display Units. 13 lines x 80 characters (8½ x 4½" screen 64 character repertoire with detachable ASCII keyboard (Control device required). Bargain Price: £145.00. Also available Cossor DIDS 402.2A, as above but incorporating control logic. Price £295.00.

FOR IBM 360 USERS. Sanders 720 Data Display System consisting of six VDUs, control unit and communications buffer. Complete with connecting cables and technical documentation. Price £2,750.00.

MINIATURE MATRIX PROGRAMME BOARDS: Brand new X-Y Matrix boards, with 3mm grating, 3 x 10 positions (1½" x 1") £4.00. P&P 40p.

MAGNETIC TAPES. Manufacturers surplus stocks, brand new in original sealed packing. ¼" x 2400' £4.00 per reel. P&P extra.

NAB-centre metal 1" tape spools 10½" dia. in plastic canister. Min. order quantity 5 for £6.25 + £2.50 P&P + 8% VAT (Send £9.45).

ENAMELLED COPPER WIRE

SWG	1 lb	8oz	4oz	2oz
14-19	2.40	1.20	.69	.50
20-29	2.45	1.60	.82	.59
30-34	2.60	1.70	.89	.64
35-40	2.85	1.90	1.04	.75

Inclusive of p&p and VAT.
SAE brings Catalogue of copper and resistance wires in all coverings.

THE SCIENTIFIC WIRE COMPANY
PO Box 30, London E4 9BW
Reg. Office: 22 Coningsby Gardens,

RECHARGEABLE BATTERIES. 'AA' pcell (HP7) £1.26; Sub 'C' £1.29; 'C' (HP11) £2.38; 'D' (HP2) £2.92; PP3 £4.98. Matching chargers £5.91 each except PP3 charger £4.99. Charging holders for 2, 3, 4, 5 or 6 pcells 35p 'C' and 'D' holders, 4 cell only 50p. Prices include VAT. Add 10% post package and insurance orders under £20. 5% over £20. SAE for full details plus 50p for 'Nickel Cadmium Power' booklet. Mail Orders to SANDWELL PLANT LTD., 1 Denholm Road, Sutton Coldfield, West Midlands. Tel: 021-354 9764. Callers to T.L.C., 32 Craven Street, Charing Cross, London WC2.

MISSING DX?

GET RID of firing whistles and CW interference FAST, with a TUNABLE AUDIO NOTCH FILTER—between your receiver and speaker. ALL parts, 1 1/2" x 3" x 5" case, etc., instructions, money back assurance, send ONLY £5.30, now.

CAMBRIDGE KITS

45 (PU) Old School Lane, Milton, Cambridge

STATIC RAMS TMS4033 Equiv 2102-2 (Faster) 450NS 1024x1 PW Video writer MPUS £3.25 each 6 up £3.05 each includes data VAT, PP CWO, BSL Associates, 2 Manor Park, Richmond, Surrey.

MAKE YOUR OWN PRINTED CIRCUITS

RUB-ON TRANSFERS—Starter pack (5 sheets, lines, pads, i.c. pads) £1.30. Spare sheets 27p.
FERRIC CHLORIDE—1lb bags 70p (p.&p. 30p)*
SOLDERCON SOCKETS—100 65p. Quantity rates.
PLASTIC SUPPORTS—7 or 8 hole. 6p/pair.
TRANSISTOR TESTER—£7 (p.&p. 30p)*
SAE lists, samples. P.&p. 15p/order except *
P.K.G. ELECTRONICS
OAK LODGE, TANSLEY, DERBYSHIRE

1mm 9V P.C. POWER DRILL uses p.p. 9. Safe, reliable, guaranteed. 2-1mm drills supplied. £3.95 c.w.o. P.E. Ltd., Coedabew, Wrexham, Clwyd.

HIGH QUALITY TEST OSCILLATOR for AUDIO and LF. APPLICATIONS

REF. AO113

Range 10hz-100Khz in 4 switched positions. Output .01v, .1v, 1v + Attenuator. Sine-square. Rise time 1µS. Distortion below .02%. Powered by 9v battery or regulated P.S.V

PRICED AT ONLY £22.00.

(Kit £17.50). (plus UK tax 8% P.P. & insurance £1).

Also THD analyser. MVMT. F.M. sig gen. Reg'd P.S. Units. SAE for further info to

TELERADIO ELECTRONICS

325 Fore St., Edmonton, London. N9. 01-807 3719

H. M. ELECTRONICS

275a FULWOOD ROAD, BROOMHILL, SHEFFIELD S10, 3BD.

BEC CABINETS (illus'd)



METAL CASES
DRY TRANSFER LETTERING

Send 15p for leaflets (Refundable)
Trade enquiries invited

SUPERB INSTRUMENTS CASES by Bazelli, manufactured from heavy duty PVC faced steel. Hundreds of people and industrial users are choosing the cases they require from our vast range, competitive prices start at a low 82p. Examples: width, depth, height, 8in x 5in x 3in, £1.70. 10in x 6in x 3in £2.42. 10in x 8in x 3in £3.02. 12in x 10in x 3in £3.96. 8in x 4in x 4in £1.98. 10in x 6in x 4in £2.97. 12in x 8in x 4in £3.96. 7in x 7in x 5in £2.91. 8in x 10in x 6in £3.96. 12in x 8in x 7in £4.40. 12in x 12in x 7in £4.84. Plus 85p carriage and 8% VAT. Over 400 models to choose from. Prompt despatch. Free literature (stamp would be appreciated). Bazelli, Dept No. 25, St. Wilfrid's, Foundry Lane, Halton, Lancaster LA2 6LT.

NOTICE TO READERS

Whilst prices of goods shown in classified advertisements are correct at the time of closing for press, readers are advised to check with the advertiser both prices and availability of goods before ordering from non-current issues of the magazine.

4-STATION INTERCOM



£18.95

+ V.A.T. £1.52

Solve your communication problems with this 4-Station Transistor Intercom system (1 master and 3 Subs), in robust plastic cabinets for desk or wall mounting. Call/talk/listen from Master to Subs and Subs to Master. Ideally suitable for Business, Surgery, Schools, Hospitals and Office. Operates on one 9V battery. On/off switch. Volume control Complete with 3 connecting wires each 86ft. and other accessories. P. & P. 90p.

MAINS INTERCOM NEW MODEL

No batteries—no wires. Just plug in the mains for instant two-way, loud and clear communication. On off switch and volume control. Price £33.74 per pair P. & P. 90p.

NEW! AMERICAN TYPE CRADLE TELEPHONE AMPLIFIER



ONLY £14.95

+ VAT £1.20

Latest transistorised Telephone Amplifier with detached plug-in speaker. Placing the receiver on to the cradle activates a switch for immediate two-way conversation without holding the handset. Many people can listen at a time. Increase efficiency in office, shop, workshop. Perfect for "conference" calls: leaves the user's hands free to make notes, consult files. No long waiting, saves time with long-distance calls. On/Off switch, volume. Direct tape recording model at £16.95 + VAT £1.36 P. & P. 75p, 10-day price refund guarantee.

WEST LONDON DIRECT SUPPLIES (PW7)
169 KENSINGTON HIGH STREET, LONDON. W8

TV GAMES CHIP
AY-3-8500 £11.50. Printed circuit and kit of extra parts £7.95. Add on colour kit P.O.A.

NEW COMPONENTS SERVICE

Resistors 5% carbon E12 2-7Ω to 10M ±W 1p. 1W 2p. Preset pots subminiature 0-1W 100Ω to 4MΩ. Vertical 3p, horizontal 9p. Potentiometers 0-25W 4K7 to 2M2 log or lin. Single 24p. Dual 75p. Polystyrene capacitors E12 63V 25pf to 8200pf 3 1/2p. Ceramic capacitors vert. 50V E6 22pf to 47000pf 3p. Mylar capacitors 100V .001, .002, .005 4p. .01, .02, .025 4 1/2p. Polyester capacitors 250V E6 .01 to .1mf 5 1/2p. .15, .22mf 7p. .47mf 11p. Electrolytics 50V .47, 1, 2mf 5p. 25V 5, 10mf 5p. 16V 22, 47mf 6p. 100mf 7p. 220mf 9p. 470mf 11p. 1000mf 18p. Zener diodes 400mW E24 3V3 to 33V 8 1/2p.

MAINS TRANSFORMERS

6-0-6V 100mA 94p. 9-0-9V 75mA 94p. 18V 1A £1.95. 0/12/15/20/24/30V 1A £3.65. 12-0-12V 50mA 94p. 0/12/15/20/24/30V 2A £4.95. 6-3V 1 1/2A £2.10. 6-0-6V 1 1/2A £2.55. 9-0-9V 1A £2.19. 12-0-12V 1A £2.49. 15-0-15V 1A £2.69. 30-0-30V 1A £3.39.

PRINTED CIRCUIT KITS, ETC.*

Contains etching dish, 100sq ins of pc board, 1lb ferric chloride, etch resist pen, drill bit and laminate cutter £3.65. 100sq ins pc board 75p. 1lb ferric chloride 95p. Etch resist pen 75p.

S-DECS AND T-DECS*

S-DeC £1.94. T-DeC £3.61.
u-DeCA £3.97. u-DeCB £6.97.
IC carriers with sockets:-
16 dil £1.91. 10T05 £1.79.



SINCLAIR CALCULATORS, WATCHES AND POCKET TV*

Sinclair pocket TV £165. Cambridge Scientific £8.45. Cambridge Memory £5.95. Oxford Scientific £10.60. Mains adaptors (State model) £3.20.

BATTERY ELIMINATOR BARGAINS

3-WAY MODELS
With switched output and 4-way multi-jack connector. Type 1:-3/4 1/2V at 100mA £2.30. Type 2:-6/7 1/2V 300mA £2.90.

100MA RADIO MODELS
With press-stud connectors. 9V £3.45. 6V £3.45. 9V+9V £5.45. 6V+6V £5.45. 4 1/2V+4 1/2V £5.45.

CASSETTE MAINS UNIT
7 1/2V with 5 pin din plug 150mA £3.65.

FULLY STABILIZED MODEL £5.45.
Switched output of 3/6 1/2V 9V 400mA stabilized.

CAR CONVERTORS 12V INPUT
Output 9V 300mA £1.80. Output 7 1/2V 300mA £1.80.

BATTERY ELIMINATOR KITS

Send s.a.e. for free leaflet on range. 100mA radio types with press stud battery terminals. 4 1/2V £2.10. 6V £2.10. 9V £2.10. 4 1/2V+4 1/2V £2.50. 6V+6V £2.50. 9V+9V £2.50.

Cassette type 7 1/2V 100mA with din plug £2.10. Transistor stabilized 3-way type for low hum. 3/4 1/2V 9V 12V 15V 18V. 100mA £3.20. 1 Amp £6.50.

Heavy duty 13-way types 4 1/2V 6V 7 1/2V 9V 11V 13V 14V 17V 21V 25V 30V 42V. 1 Amp £4.95. 2 Amp £7.95.
Car converter kit Input 12V DC. Output 6/7 1/2V 9V DC 1A transistor stabilized £1.95.

Stabilized Laboratory power kit Switched 1 to 30V in 0-1V steps. 1 Amp £12.45. 2 Amp £14.95.

SINCLAIR PROJECT 80 AUDIO MODULES

PZ5 £4.95. Z40 £5.75.

BI-PAK AUDIO MODULES
S450 tuner £20.95. AL60 £4.60. PA100 £14.95. MK60 audio kit £31.95. Stereo 30 £15.50. SPM80 £3.65. BMT80 £3.32. Send s.a.e. for free data.

SINCLAIR IC20

IC20 10W+10W stereo integrated circuit amp kit with printed circuit and data £4.95.

PZ20 Power supply kit for above £3.65.

VP20 Volume, tone control and preamp kit £8.95. Send s.a.e. for free leaflet on the whole system.

JC12 AND JC40 AMPLIFIERS

JC12 6W IC audio amp with free data and printed circuit £1.95.

Also new JC40 20W model with pcb £3.95. Send s.a.e. for free leaflet on both models and associated power supply and preamp kits.



FERRANTI ZN414

IC radio chip £1.44. Extra parts and pcb for radio £3.85. Case £1. Send s.a.e. for free data.

SWANLEY ELECTRONICS

DEPT. PW, PO BOX 68,

32 GOLDSSEL RD., SWANLEY, KENT.

Mail order only. No callers. Send s.a.e. for free data on kits. Post 30p on orders under £4.50, otherwise free. Prices include VAT. Official orders welcome. Overseas customers deduct 7% on items marked * and 11% on others.

WATFORD ELECTRONICS

33/35, CARDIFF ROAD, WATFORD HERTS, ENGLAND
MAIL ORDER, CALLERS WELCOME. Tel. Watford 3774

ALL DEVICES BRAND NEW, FULL SPEC. AND FULLY GUARANTEED. ORDERS DESPATCHED BY RETURN OF POST. TERMS OF BUSINESS: CASH/CHEQUE/P.O.s OR BANKERS DRAFT WITH ORDER. GOVERNMENT AND EDUCATIONAL INSTITUTIONS OFFICIAL ORDERS ACCEPTED. TRADE AND EXPORT INQUIRY WELCOME. P & P ADD 25p* TO ALL ORDERS UNDER £10.00. OVERSEAS ORDERS POSTAGE AT COST, AIR/SURFACE. SEND SAE FOR OUR FREE LIST.

VAT Export orders no VAT. Applicable to U.K. Customers only. Unless stated otherwise, all prices are exclusive of VAT. Please add 8% to devices marked *. To the rest add 12½%.
We stock many more items. It pays to visit us. We are situated behind Watford Football Ground. Nearest Underground/Br. Rail Station: Watford High Street. Open Monday to Saturday. Ample Free Car Parking space available.

POLYESTER CAPACITORS: Axial lead type. (Values are in µF).
400V: 0-001, 0-0015, 0-0022, 0-0033 8p; 0-0047, 0-0068, 0-01, 0-015, 0-018 9p; 0-022, 0-033, 10p; 0-047, 0-068, 14p; 0-1, 15p; 0-15, 0-22, 22p; 0-33, 0-47 39p; 0-68 45p.
160V: 0-039, 0-15, 0-22 11p; 0-33, 0-47 19p; 0-68, 1-0 22p; 1-5 29p; 2-2 32p; 4-7 36p.
DUBILIER: 1000V: 0-01, 0-015 16p; 0-022 19p; 0-047 16p; 0-134p; 0-47 43p; 1-0, 85p.

POLYESTER RADIAL LEAD (Values in µF). 250V: 0-01, 0-015 6p; 0-022, 0-027 7p; 0-033, 0-047, 0-068, 0-1 8p; 0-15 12p; 0-22, 0-33 14p; 0-47 16p; 0-68 20p; 1-0 24p; 1-5 27p; 2-2 31p.
FEED THROUGH CAPACITORS
12p; 0-22, 0-33 14p; 0-47 16p; 0-68 20p; 1-0 24p; 1-5 27p; 2-2 31p. 1000pF/350V 8p

ELECTROLYTIC CAPACITORS: Axial lead type (Values are in µF).
250V: 100µF, 50p; 100V: 20, 33p; 0-47, 1-0, 1-5, 2-2, 2-5, 3-3, 4-7, 6-8 8, 10, 15, 22, 9p; 47, 32, 50, 12p; 63, 100, 27p; 50V: 1-0, 7p; 50, 100, 220, 25p; 470, 50p; 1000, 62p; 2200, 68p; 40V: 22, 9p; 100, 12p; 3300, 62p; 35V: 10, 33, 7p; 330, 470, 50p; 1000, 49p; 25V: 10, 22, 47, 62, 80, 100, 160, 8p; 220, 250, 13p; 470, 640, 25p; 1000, 27p; 1500, 30p; 2200, 34p; 3300, 52p; 4700, 54p; 16V: 10, 40, 47, 68, 7p; 100, 125, 8p; 470, 16p; 1000, 1500, 20p; 2200, 34p; 10V: 4, 100, 6p; 640, 100p; 1000, 14p.
TAG-END TYPE: 70V: 4700, 121p; 64V: 3300, 94p; 40V: 2500, 65p; 25V: 4700, 48p; 16V: 4500 38p; 48V: 2000+2000 95p.

TANTALUM BEAD CAPACITORS
35V: 0-1µF, 0-22, 0-33, 0-47, 0-68, 1-0, 2-2µF, 3-3, 4-7, 6-8, 25V: 1-5, 10, 20V: 1-5µF 13p each. 10V: 22µF, 33, 6V: 22µF, 47, 68, 3V: 100µF 20p each.

MYLAR FILM CAPACITORS
100V: 0-001, 0-002, 0-005, 0-01µF 5p
0-015, 0-02, 0-03, 0-04, 0-05-05µF 8p
0-1µF, 0-15, 0-2 7p. 50V: 0-47µF 10p

CERAMIC CAPACITORS 50V.
Range: 0-5pF to 10nF 3p
15nF, 22nF, 33nF, 47nF, 4p. 100nF 6p

POLYSTYRENE CAPS. Full range 6p each.

JACKSONS VARIABLE CAPS.
Dielectric 100pF 105p
500pF 125p
DILEMIN 300pF/500pF 185p
4832/2K 2 speed
Drive Unit complete with knobs and coupling 350p*
Drum 54mm 30p*
6:1 Ball Drive 4511/DAF. 107p*

SILVER MICA (pF)
3-3, 4-7, 6-8, 10, 12, 18, 22, 33, 47, 50, 88, 75, 82, 85, 100, 120, 150, 200, 250 8p each.
300, 330, 360, 390, 600 & 820pF 16p each.
1000, 2200pF 20p each.

CERAMIC TRIMMER CAPACITORS
2-7pF: 4-15pF: 6-25pF: 8-30pF 20p

MINIATURE TYPE:
2-5pF: 3-10pF: 3-30pF: 10-40pF 22p
5-25pF: 60pF: 88pF 30p

COMPRESSION
3-40pF: 8-80pF 22p
20-140pF: 50-200pF 33p
100-500pF 1250pF 36p

AUDIBLE Warning
Devices 12V 135p*

TRANSFORMERS* (Mains Prim. 220-240V)
6-0-6V 100mA 90p
9-0-9V 75mA 85p
12-0-12V 100mA 98p
15-0-15V 100mA 185p
0-12-0-12V 150mA 140p
0-6-0-6V 280mA 150p
12 012V 0-5A 240p+
15-0-15V 0-5A 220p+
20-0-20V 6V 220p+
24-0-24V 0-5A 240p+
9-0-9V 1A 245p+
0-12-0-12V 1A 245p+
30-24-20-15-12-0 1A Multi tapplings 360p+
30-24-20-15-12-0 2A multi tap 445p+
15-0-15V 1A 245p+
18-0-18V 1A 275p+
30-0-30V 1A 295p+
6-0-6V 1-5A 345p+
0-18-0-18V 1-5A 379p+
9-0-9V 2A 270p+
30-25-20-0-20-20 497p+
LT44 54p
LT700 Min. O/P Pri. 1-2K, Sec. 3-2 54p
MOT Min. O/P Pri 2A multi tap 445p+ 1-2K, Sec. 8 42p
(Please add 48p p&p charge to all prices marked +, above our normal postal charge.)

POTENTIOMETERS (AB or EGEN)
Carbon Track, 0-25W Log & 0-5W Linear values
1KΩ & 2KΩ (LIN. ONLY) Single gang 24p
5KΩ-20KΩ single gang D/P switch 24p
5KΩ-20KΩ single gang D/P switch 50p
5KΩ-20KΩ dual gang stereo 60p

SLIDER POTENTIOMETERS
0-25W log and linear values 60mm
5KΩ-500KΩ single gang 60p
10KΩ-500KΩ Dual gang 70p
Self-Silck graduated Alum. Bezels 20p

PRESET POTENTIOMETERS
0-1W 50Ω-2-2M Min. Vert. & Horiz. 8p
0-25W 100Ω-3-3MΩ Horiz. 10p
0-25W 250Ω-4-7MΩ Vert. larger 10p

RESISTORS-Erie make 5% carbon Miniature High Stability, Low Noise RANGE Val. 1-99-100+
0-25W 2-2Ω-4-7M E24 1-5p 1p
0-5W 2-2Ω-4-7M E12 2p 1-5p
1W 2-2Ω-10M E12 5p 4p
2% Metal Film 10Ω-1MΩ 6p

HEAT SINKS*
TO92 8p
TO5 8p
TO18 8p
TO88 22p
TO3 22p
TO66 22p
Special for RFC 5 (chokes) 84p
TDA2020 60p
Insulation Kit IFT 13/14/15/16/17 75p
Mica plus 1FT 18/1-6 or 465 95p
2 Bushes for TO3/TO66 or PlasticTrns5p
DIL SOCKETS*
Magnetic 2-5mm 18p
3-5mm 18p
Crystal 33p
FIGARO Gas & Smoke Detector
812 or 813 355p*
Socket 20p*

DIL SOCKETS*
Terminals Screw type Red, Black, Yellow 21p
8pin 10p
14pin 12p
16pin 13p
24pin 30p
28pin 45p
40pin 80p/PPP 10p
BATTERY CLIPS*
Polarised 3p
PPP 6p
80p/PPP 10p
SOLDERCON PINS*
100-50p; - 1000 350p

PW PROJECTS
Easibuild Organ, General Coverage Receiver, Chromachase, Smoke Sensor Alarm, Reverb Amp, Metal Detector, 20W Amplifier, 24 hrs. Digital Clock, Radio 2 Tuner, TV Games and Kit for Rifle attachment.
Send SAE plus 5p per list.

PW RHYTHM GENERATOR
We are the sole suppliers of the complete kit including the 3 re-designed circuit boards. PRICES including VAT Complete Kit £44-95. Ready Built Unit £54-95 (add £1-20 P. & P. and Insur.). Demonstration on at our shop.

TRANSISTORS		TRANSISTORS		TRANSISTORS	
AC117 35	BC154 20	BF178* 28	D MPSU02 58	TIS43 27	2N3011* 30
AC125* 22	BC157 10	BF179* 33	D MPSU05 84	TIS44 47	2N3053* 16
AC126* 18	BC158 12	BF180* 33	D MPSU06 84	TIS46 20	2N3054* 45
AC127* 18	BC159 13	BF181* 33	D MPSU05 85	TIS50 47	2N3055* 48
AC128* 18	BC160 32	BF182* 33	D MPSU55 60	TIS74 47	2N3525* 98
AC141* 22	BC167 12	BF183* 33	D MPSU56 82	TIS90 24	2N3614* 169
AC141* K38	BC168 12	BF184* 28	D MPU131* 39	TIS91 24	2N3615* 135
AC142* 20	BC169C 14	BF185* 30	D OC25* 65	ZTX107 12	2N3863 32
AC142K* 38	BC170 11	BF194 10	D OC26* 95	ZTX108 10	2N3872 11
AC176* 18	BC171 11	BF195 16	D OC28* 70	ZTX109 15	2N3703 12
AC187* 18	BC172 11	BF196 14	D OC29* 70	ZTX300 14	2N3704 11
AC188* 19	BC177* 18	BF197 15	D OC35* 70	ZTX301 14	2N3705 12
AC197 35	BC178* 16	BF198 15	D OC36* 58	ZTX302 19	2N3706 10
AC198 28	BC179* 18	BF200 37	D OC41* 17	ZTX303 22	2N3707 11
AC199 25	BC182 10	BF224A 15	D OC42* 17	ZTX304 24	2N3708 12
AC200 24	BC182L 12	BF244B 34	D OC44* 25	ZTX311 15	2N3709 12
AC212 20	BC183 10	BF256* 34	D OC45* 17	ZTX314 24	2N3710 12
AC222 16	BC183L 11	BF257* 34	D OC46* 35	ZTX341 20	2N3711 12
AC228 21	BC184 11	BF258* 38	D OC70* 25	ZTX500 17	2N3771* 164
AC239 78	BC184L 12	BF259* 48	D OC71* 23	ZTX501 15	2N3772* 175
AC240 24	BC186 22	BF294 30	D OC72* 27	ZTX502 19	2N3773* 278
AC244 30	BC187* 23	BF295 28	D OC77* 56	ZTX503 19	2N3819 22
AD149* 48	BC187* 23	BFR39 25	D OC79* 58	ZTX504 51	2N3820 44
AD161* 36	BC192 12	BFR40 25	D OC81* 24	ZTX531 28	2N3823* 49
AD162* 36	BC192L 13	BFR79 25	D OC81D* 23	ZTX550 18	2N3824* 89
AF114* 26	BC193 11	BFR80 25	D OC82* 25	2N697* 21	2N3863* 30
AF115* 29	BC213L 13	BFX18* 54	D OC82D* 35	2N698* 39	2N3865 15
AF116* 29	BC214 14	BFX29* 28	D OC83* 28	2N699* 45	2N3904 18
AF120* 20	BC214L 16	BFX38* 38	D OC84* 44	2N706A 19	2N3905 18
AF117* 23	BC307B 15	BFX53* 40	D OC84N* 44	2N707* 50	2N3906 18
AF118* 47	BC328 18	BFX55* 40	D OC123* 115	2N708 19	2N4037* 39
AF121* 39	BC441* 37	BFX64* 38	D OC139* 140	2N914 17	2N4058 15
AF124* 30	BC461* 47	BFX81* 141	D OC140* 125	2N916* 27	2N4061 13
AF125* 30	BC462* 37	BFX84* 24	D OC141* 157	2N918* 31	2N4289 24
AF126* 30	BC477* 20	BFX85* 28	D OC170* 40	2N920 54	2N4259 35
AF127* 30	BC548 20	BFX86* 28	D OC171* 42	2N930 18	2N4871 34
AF130* 40	BC549C 20	BFX87* 23	D OC201* 125	2N961* 61	2N5135 12
AF138* 70	BC557 28	BFX88* 26	D OC202* 135	2N1131* 19	2N5136 12
AF179* 70	BCY30* 55	BFY50* 17	D OC203 190	2N1132* 23	2N5138 12
AF180* 70	BCY32* 65	BFY51* 17	D OC204* 150	2N1302* 25	2N5179 60
AF181* 48	BCY34* 80	BFY52* 17	D TIP29A 43	2N1303* 27	2N5180 60
AF185* 60	BCY39* 85p	BFY65* 25	D TIP29A 43	2N1304* 45	2N5191 65
AF186* 48	BCY40* 90	BSY26* 40	D TIP29C 68	2N1305* 32	2N5305 40
AF239* 37	BCY55* 204	BSY29* 85	D TIP30 52	2N1306* 37	2N5457 35
ASV28* 40	BCY59* 18	BSY78 25	D TIP30A 56	2N1307* 37	2N5458 36
ASV29* 40	BCY70* 17	BSX20* 20	D TIP30B 64	2N1308* 48	2N5459 36
BC107* 9	BCY71* 20	BSY95A 18	D TIP30C 74	2N1613 20	2N5485 42
BC107B* 19	BCY72* 15	BU105* 168	D TIP31* 52	2N1671* 150	2N5777 56
BC108* 9	BD115 52	E5567 48	D TIP31A* 54	2N1671B 190	2N6027 35
BC108B* 12	BD121* 98	MD8001* 158	D TIP31B* 58	2N189* 27	4031* 42
BC109* 9	BD123* 95	MJ400* 90	D TIP31C* 68	2N2160* 80	40313* 114
BC109B* 12	BD124* 105	MJ491* 160	D TIP32* 63	2N2217* 40	40316* 69
BC109C* 12	BD131 36	MJ2955* 120	D TIP32A* 83	2N2218A* 25	40317* 42
BC113 20	BD132* 38	MJE340* 45	D TIP32B* 80	2N2219A* 24	40326* 42
BC114 20	BD133* 60	MJE370* 68	D TIP33* 95	2N2220A* 26	40327 48
BC115 20	BD136 45	MJE371* 80	D TIP33A* 95	2N2221A* 21	40347* 85
BC116 20	BD137 42	MJE520* 65	D TIP33B* 112	2N2222* 21	40348* 83
BC117 20	BD138 47	MJE521* 74	D TIP33C* 120	2N2303* 250	40360* 36
BC118 15	BD139 54	MJE2955* 98	D TIP34* 110	2N2369* 14	40361* 36
BC119 25	BD140 57	MJE3055* 82	D TIP34A* 115	2N2483* 30	40382* 43
BC135 13	BD142 53	MPF102 36	D TIP34B* 110	2N2484* 30	40411* 295
BC136 15	BD144 160	MPF103 36	D TIP35* 219	2N2614 54	40412* 42
BC137 15	BD145 55	MPF104 36	D TIP35A* 225	2N2646* 52	40476 170
BC138 15	BDY117 195	MPF105 36	D TIP35C* 270	2N2904A* 24	40594 90
BC140* 34	BDY60* 128	MPF106 50	D TIP35E* 220	2N2905* 20	40595 98
BC142* 24	BDY81* 147	MPF107 50	D TIP36* 346	2N2906* 18	40603 62
BC143* 24	BF115* 22	MPF108 50	D TIP41A* 66	2N2907* 20	40638* 110
BC147 7	BF154* 22	MPSA05 32	D TIP41B* 73	2N2907A* 22	40673* 55
BC148 7	BF156* 22	MPSA08 32	D TIP42A* 78	2N2926G 10	
BC149 8	BF173* 25	MPSA55 30	D TIP42B* 82	2N2926F 8	Matched Pair
BC153 25	BF177* 26	MPSA56 30	D TIP2955* 68	2N2926R 8	10p extra
		MPSA70 34	D TIP3055* 56	2N2926V 8	

TTL 74*		TTL 74*		TTL 74*	
7400 14	7474 36	74155 76	4019AE 105	7400 14	7474 36
7401 14	7475 36	74156 80	4020AE 125	7401 14	7475 36
7402 16	7476 36	74157 95	4021AE 105	7402 16	7476 36
7403 16	7480 59	74160 116	4022AE 95	7403 16	7480 59
7404 20	7481 114	74162 116	4023AE 20	7404 20	7481 114
7405 22	7482 82	74163 116	4024AE 85	7405 22	7482 82
7406 44	7483 95	74164 121	4025AE 19	7406 44	7483 95
7407 44	7484 95	74165 120	4026AE 185	7407 44	7484 95
7408 22	7485 125	74166 191	4027AE 60	7408 22	7485 125

WATFORD ELECTRONICS

(Continued from opposite side)

DIODES	*BRIDGE RECTIFIERS	SCR'S*
AA119 15p	(plastic case)	Thyristors
AAZ15 15p	1A50V 20p	1A50V 30p
AEY11 6p	1A50V 20p	1A100V 42p
BA100 10p	1A50V 20p	1A300V 47p
BA102 10p	1A50V 20p	1A500V 52p
BY100 24p	1A400V 25p	1A500V 70p
BY25 14p	1A600V 34p	1A50V 30p
BY27 14p	1A30V 35p	1A100V 45p
CA2 9p	2A100V 44p	1A200V 50p
CA47 8p	2A200V 45p	1A400V 51p
CA70 8p	2A100V 45p	1A500V 52p
CA75 12p	4A100V 72p	1A400V 52p
CA81 15p	1A200V 35p	1A400V 52p
CA85 12p	1A400V 35p	1A500V 53p
CA90 4p	1A100V 35p	1A500V 53p
CA81 4p	1A100V 35p	1A500V 53p
CA95 2p	1A200V 35p	1A500V 53p
CA300 4p	1A400V 35p	1A500V 53p
IN914 4p	BY164 56p	
IN916 5p		
IN4001/2* 5p		
IN4003* 6p		
IN4004/5* 8p		
IN4005/7* 17p		
IN4148 4p		
IS44 20p		
3A/100V* 19p		
3A/400V* 20p		
3A/600V* 27p		
3A/1000V* 30p		
6A/600V 50p		

OPTO ELECTRONICS*	VOLTAGE REGULATORS*
LEDs + Clip 7 Segment Displays	723 DIL 45p Plastic Case
TIL209 Red 13p 5-LT-01 460p	723 TO5 53p 78L82AWC 1A 8V 51p
TIL211 Grn 23p TIL312 3" C.An 125p	TBA625B 95p MC7805 1A5V 135p
TIL220 Red 20p TIL313 3" C.Cth 125p	T03 Can Type MC7812 1A 12V 135p
2" Red 17p TIL321 5" C.An 140p	1A 5V 170p MC7815 1A 15V 135p
Yellow, Green, Amber 21p DL704 3" C.Cth 99p	1A 12V 180p FT8N24 1A 24V 140p
OCPT70 49p DL707 3" C.Anod 99p	1A 15V 190p Variable Type
ORP12 68p DL747 6" An 180p	1A 18V 210p LM325N ±15V 240p
2N5777 54p MAN3610 C. An 250p	LM309K 150p LM326N ±12V 240p
ISOLATORS	LM323K 625p LM327N ±5 -12 260p
MAN3640 C. Cath 260p	MVR5 180p LM317K 20V 1.5A 350p
MINITRON 3015F 240p	MVR12 180p +1-2V to 37V 350p
	1A -5V 220p LM317H 5W 1.5A 350p
	1A -12V 220p +1-2V to 37V 320p

ALUM. BOXES with lid*	CASES:
2"x3"x1/2" 64p	NJHC1 85p
4"x4"x1/2" 64p	NJSF2 275p
4"x2"x1/2" 58p	75/1411D 380p
4"x5"x1/2" 70p	
4"x2"x2" 63p	
5"x4"x2" 85p	
6"x4"x2" 91p	
7"x5"x2" 114p	
8"x6"x3" 142p	
10"x7"x3" 150p	
10"x4"x3" 142p	
12"x5"x3" 180p	
12"x8"x3" 205p	

SPEAKERS
8Ω 0-3W 19p
2" 2 1/2" 65p
2-5, 3" 58p
64Ω 2-5" 65p
8Ω 5W 190p
7" x 4" 205p
16Ω 5W 205p
7 x 4"

COPPER CLAD BOARDS*
Fibre sing. dble/
glass sided sided
8"x6" 64p 78p
8"x12" 115p 160p


FERRIC CHLORIDE* 1lb bag
Anhydrous 65p + 30p p. & p.

DALO ETCH RESIST
PEN* + spare tip 75p

VEROBOARD* Pitch
0-1 0-15 0-15
(copper clad) (plain)
2 1/2 x 3 1/2" 29p 19p
2 1/2 x 5" 43p 39p
2 1/2 x 3 1/2" 43p 40p
2 1/2 x 5" 48p 53p
2 1/2 x 1 1/2" 134p 73p
2 1/2 x 1 1/2" 173p 143p
2 1/2 x 1 1/2" 222p 145p
Pkt of 36 pins 25p
Spot face cutter 85p
Pin insertion tool 35p

DIAC*
BT106 100p
C106D 55p
TIC44 25p
TIC45 25p
2N4444 191p

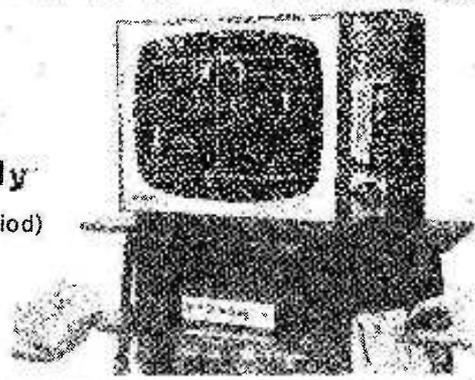It's here! . . . The "OLYMPIC" TELEVISION GAME



IC
AY-3-8500
£7.92* only
(for limited period)

This is an easy to build no compromise kit using the very latest integrated circuit only just available from the United States. Simply plug into the U.H.F. Aerial socket of any standard Television Receiver, sit back in your favourite armchair and spend countless hours with the family playing any of the six games available. The central Control Unit provides Game selection with switching for Bat size, Angle and Ball speed adjustment. The Bat position, Score reset and Serve controls being remotely connected allowing players to be many feet apart. The Unit is mains powered (no expensive batteries to buy) and incorporates the unique "Ventriloquist" audio system which produces realistic Game sounds from your Television speaker. Also included are instructions to build the "Sure Fire" rifle. A simple design which is made foolproof by the "On Target" detector incorporated in the electronics. Complete kit £27.85 incl. VAT. (P & P insured add 85p). Sure Fire Rifle Kit £9.50 incl. VAT. (Components may be ordered individually). Send SAE for details. (Demonstration on at our shop).

SWITCHES*
TOGGLE: 2A, 250V 59p
SPST 26p
DPDT 35p
4 polechangeover58p

SUB-MIN TOGGLE
SP changeover 59p
DPDT 6 tag 78p
DPDT Centre off 92p
DPDT Biased 115p

JACK PLUGS
Screened chrome 12p
3-5mm 15p
MONO 20p
STEREO 31p

SOCKETS
Open metal 3p
Moulded with break contacts 20p
12p 12p
15p 15p
24p 24p

INDEX TO ADVERTISERS

A.H. Supplies	235
Alben Engineering	166
Ambit International	235
Astro Alarms	237
Astro Electronics	244
Bamber B.	232
Barrie Electronics	196
B.B. Supplies	239
Bentley Acoustic Corp.	236
Bi-Pak Ltd.	178, 179
Bi-Pre-Pak Ltd. (Stirling Sound)	175
Birkett J.	237
British National Radio & Electronics School	174, 195
J. Bull (Electrical) Ltd.	223
Bywood	221
Cambridge Kits	241
Cannana C.	239
Copper Supplies	239
Cox Radio (Sussex) Ltd.	238
C.R. Supply Co.	238
Crescent Radio Ltd.	170
Crofton Electronics	176
D.E.W. Ltd.	240
Doram	166, 168
Electronic Design Assoc.	237
Electronic Brokers Ltd.	172, 240
Electronic Mail Order	221
Electrovalue	172
Fidelity Fastenings	170
Flairline	232

G2DYM Aerials & Project	239
Greenweld Electronics	166
G.T. Technical Information Service	239
H.A.C. Short-Wave Supplies	234
Harversons	177
H.M. Electronics	241
Heathkit Ltd.	227
Home Radio	233
I.L.P. Electronics Ltd.	191
Intertext I.C.S.	227
James Cooper (Electronics) Ltd.	240
Kramer & Company	232
Linear Products	176
Lion House	239
Lectropaks	224
Lynx Electronics	234
Manor Supplies	172
Magnum Publications	240
Maplin Electronic Supplies	cover iv
Maréo Trading	238
Marshall, A. (London) Ltd.	196
Metac Ltd.	174
Mhel Electronics	240
Minikits Electronics	240
Monolith Electronics	172
Newmart Electronics	221
Newnes-Butterworth	233
Partridge Electronics Ltd.	224
P.B. Electronics	171
P.K.G. Electronics	241

Precision Petite	176
Pulse Electronics (Baron)	233
Radio Book Services	239
Radio Components Specialists	231
Radio Exchange Ltd.	cover iii
Radio Society of Gr. Britain	174
Ramar Construction Services	239
R.S.C. (Hi-Fi)	167
R.S.T. Valve Mail Order	228
Radio & TV Components Ltd.	169
Salop Electronics	240
Saxon Entertainments	173
Scientific Wire Co., The	241
Sintel	224
Sonic Hi-Fi	192
Southern Valve Co.	232
Sowter E.A. Ltd.	238
Swanley Electronics	241
Tamba Electronics	176
Tempus	168
Technomatic Ltd.	192
Teleradio Electronics	241
Technomark	239
T.K. Electronics	238
Trampus Electronics	236
Tudor Rees (Vintage) Services	238
Watford Electronics	242, 243
Web Europa	224
West London Direct Supplies	241
Wilmslow Audio	227
Williams, Michael Electronics	168
Xeroza	cover ii
Z & I Aero Services	244

Head Office and Warehouse
44A WESTBOURNE GROVE
LONDON W2 5SF
Tel: 727 5641/2/3

Z & I AERO SERVICES LTD.

Retail Shop
85 TOTTENHAM COURT ROAD
LONDON W1
Tel: 580 8403
Open all day Saturday

Please send all correspondence and Mail-Orders to Head Office

AC/DC TAUT SUSPENSION MULTIMETERS (Made in USSR)



TYPE	U4312	U4313	U4315
Sensitivity D.C.	667 o.p.v.	20,000 o.p.v.	20,000 o.p.v.
Sensitivity A.C.	667 o.p.v.	2,000 o.p.v.	2,000 o.p.v.
D.C. Current	300 μ A-6A	60 μ A-1.5A	50 μ A-2.5A
A.C. Current	1.5mA-6A	0.6mA-1.5A	0.5mA-2.5A
D.C. Volts	75mV-900V	75mV-600V	75mV-1000V
A.C. Volts	300mV-900V	15V-600V	1V-1000V
Resistance	0.02-3k Ω	1K-1M	300 Ω -500k Ω
Capacity	—	0.5 μ F	0.5 μ F
Accuracy	1% D.C., 1.5% A.C.	1.5% D.C., 2.5% A.C.	2.5% D.C., 4% A.C.

Price complete with pressed steel carrying case and test leads.

£14.50 £17.50 £14.95

TYPES U4313 & U4315 PROVIDED WITH ANTI-PARALLAX MIRROR SCALES



TYPE U4324	
Sensitivity:	20,000 Ω /V D.C. 4,000 Ω /V A.C.
D.C. Current:	0.06-0.6-60-600mA-3A
A.C. Current:	0.3-3-30-300mA-3A
D.C. Voltage:	0.6-1.2-3-12-30-60-120-600-1200V
A.C. Voltage:	3-6-15-60-150-300-600-900V
Resistance:	500 Ω -5-50-500k Ω
Accuracy:	D.C. 2.5%; A.C. 4% (of F.S.D.)

PRICE complete with test leads and fibreboard storage case £14.50



TYPE U4341

Sensitivity:
18700 Ω /V D.C.,
3300/V A.C.

Ranges:
D.C. current: 0.06-
0.6-6-60-600mA
A.C. current 0.3-3-30-
300mA
D.C. Voltage: 0.3-1.5
-6-30-60-150-300-
900V
A.C. Voltage: 1.5-7.5-
30-150-300-750V
Resistance: 2-20-
200k Ω -2M Ω

Transistor collector
cut-off current 60 μ A
Transistor D.C. cur-
rent gain in two
ranges 10-350
Accuracy: 2.5% D.C.
4.0% A.C.
5% D.C.
current gain
Power supplies: 4.5V
battery
(Eveready 1289)


Complete with steel carrying case, test lead, battery and instruction manual £14.50

NO OVERLOAD PROTECTION IS INCORPORATED IN THESE INSTRUMENTS

THE ABOVE PRICES ARE EXCLUSIVE OF VAT (at present 8%) HANDLING AND POSTAGE CHARGES £1.25 PER INSTRUMENT

OUR NEW 1976/1977 CATALOGUE IS NOW READY AND WILL BE SENT ON RECEIPT OF REMITTANCE FOR £0.30

INVERTORS

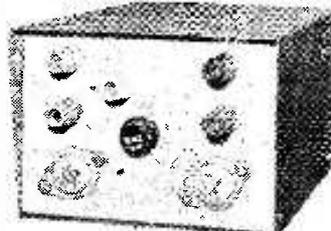

240v-50Hz from your 12v car battery

25 watt-£4.75 300 watt (12v)-£33.08
40 watt-£8.27 400 watt (24v)-£39.05
75 watt-£12.03 500 watt (24v)-£48.18
150 watt-£21.27 1 Kw (50v)-£127.00
300 watt (24v)-£26.45 1.5 Kw (110v)-£140.80

All above invertors are in kit form but may be purchased built up in metal case and ready for use. Price list sent on receipt of s.a.e. Prices include p. and p.

P.W. AUTOMATIC EMERGENCY SUPPLY

240v-50Hz-150 watt inverter with built in battery charger. In event of power failure switches over automatically from battery charging to inverter operation. Cct. as appeared in Dec. 72 P.W. Complete kit of parts (excluding meter) £24.50 plus £1.70p.p.

DIGITAL WATCH
FOUR FUNCTION DIGITAL WATCH FOR ONLY £16 with 1 Year Guarantee HOURS . MINS. . SECONDS . DATE American Design, UK Manufacture.

TRANSFORMERS AND COILS

Both high volume and small order capacity available.
Special offer. Miniature mains transformer 6.0-6v-6vA. 85p + 10p p. & p.

P.E. ORION STEREO AMPLIFIER & TUNER



20 + 20 Watts r.m.s. into 8 ohm load. Distortion less than 0.01% 100Hz-10kHz. Frequency response \pm 1dB 20 Hz to 20kHz. Hum level virtually nil with volume full on.

This is a power amplifier of superb quality incorporating the very latest design features. Professional hi-fi enthusiasts have classed it as fantastic and real value for money. The CCT incorporates a low flux transformer and inputs for disc, tape, tuner, etc.


Complete kit of parts including slim line bookend case, silk screened front panel and knobs £48.60 inc. VAT and p. & p.

The bookend case, I.C.'s and semiconductors, P.C. board, Transformer, etc. may be purchased separately if desired. Send S.A.E. for further information.

P.E. ORION TUNER UNIT
PARTS MAY BE PURCHASED AS FULL KIT OR SEPARATE ITEMS. SEND S.A.E. FOR DETAILS.

N.B.—DELIVERIES ON ALL ITEMS MAY TAKE UP TO 28 DAYS. DEPENDING ON AVAILABILITY AND DEMAND. CASH IN REGISTERED ENVELOPE OR POSTAL ORDERS CAN REDUCE TIME by NOT HAVING TO CLEAR CHEQUES

ASTRO IGNITION

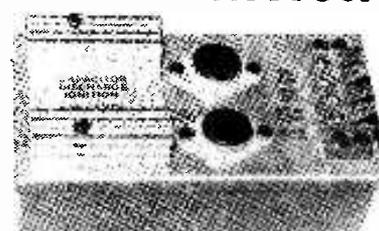

ASTRO IGNITION SYSTEM

Complete kit of parts for this proven and tested system £10.45 inc. VAT Ready built with only two connections to alter £13.75 inc. VAT. Thousands have used this system both home and abroad. Consider these advantages—more power, faster acceleration, fuel economy, excellent cold starting, smoother running, no contact breaker burning. Also because of the high energy spark the fuel mixture can be made weaker giving further economy and fewer plug problems. Fitting time when built 5 minutes approx. Please state whether positive or negative earth.

TRADE and EXPORT ENQUIRIES WELCOMED ON ALL PRODUCTS

ASTRO ELECTRONICS
Springbank Road, West Park
CHESTERFIELD. 31475

RADIO EXCHANGE LTD.

**ALL PRICES
INCLUDE VAT**

NEW EDU-KIT MAJOR

Completely Solderless Electronic Construction Kit. Build these projects without soldering iron or solder



Total Building Costs **£9.00**

P & P + Ins. £1.10

- ★ 4 Transistor Earpiece Radio
- ★ Signal Tracer
- ★ Transistor Injector
- ★ Transistor Tester NPN-PNP
- ★ 4 Transistor Push Pull Amplifier
- ★ 5 Transistor Push Pull Amplifier
- ★ 7 Transistor Loudspeaker Radio MW/LW
- ★ 5 Transistor Short Wave Radio
- ★ Electronic Metronome
- ★ Electronic Noise Generator
- ★ Batteryless Crystal Radio
- ★ One Transistor Radio
- ★ 2 Transistor Regenerative Radio
- ★ 3 Transistor Regenerative Radio
- ★ Audible Continuity Tester
- ★ Sensitive Pre-Amplifier

Components include: 24 Resistors ★ 21 Capacitors ★ 10 Transistors
 ★ 5" x 3" Loudspeaker ★ Earpiece ★ Mica Baseboard ★ 3 12-way connectors
 ★ 2 Volume controls ★ 2 Slider Switches ★ 1 Tuning Condenser ★ 3 Knobs
 ★ Ready Wound MW/LW/SW Coils ★ Ferrite Rod ★ 6½ yards of wire
 ★ 1 Yard of sleeving, etc. Complete kit of parts including construction plans.

VHF AIR CONVERTER KIT

Build this Converter Kit and receive the Aircraft Band by placing it by the side of a radio tuned to Medium Wave or the Long Wave Band and operating as shown in the instructions supplied free with all parts. Uses a retractable chrome plated telescopic aerial, Gain Control, V.H.F. Tuning Capacitor, Transistor, etc.




All Parts including Case and Plans. **£3.95**
 P & P and Ins. 60p.

NEW ROAMER TEN MODEL R.K.3.

MULTIBAND V.H.F. AND A.M. RECEIVER
 13 TRANSISTORS AND FIVE DIODES
 QUALITY 5" x 3" LOUDSPEAKER

WITH Multiband V.H.F. section covering Mobiles, Aircraft, T.V. Sound, Public Service Band, Local V.H.F. Stations, etc. and Multiband A.M. section with Airspaced Slow Motion Drive Tuning Capacitor for easier and accurate tuning, covering M.W.L.M.W.2, L.W., Three Short Wave Bands, S.W.1, S.W.2, S.W.3, & Trawler Band. Built in Ferrite Rod Aerial for Medium Wave, Long Wave and Trawler Band, etc., Chrome Plated 7 section Telescopic Aerial, angled and rotatable for peak Short Wave and V.H.F. reception. Push Pull output using 600mw Transistors. Gain, Wave-Change and Tone Controls. Plus two Slider Switches. Negative Feedback circuit and SPECIAL POWER BOOSTER SOCKET AND RESISTOR, to virtually double gain if required. Powered by P.P.9 9 volt battery. Complete kit of parts including carrying strap. Building Instructions and Operating Manuals.

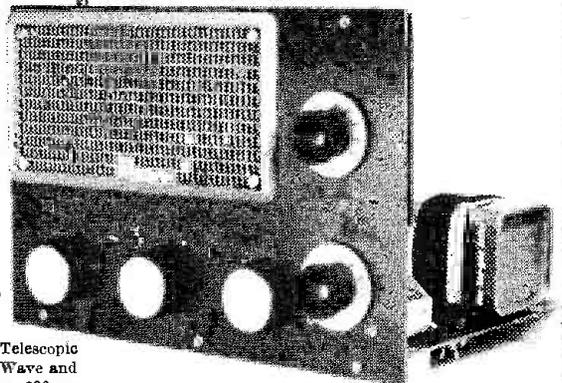

£13.99 Including Post and Packing

Case Enclosure Kit (if required) £1.90 inc. P & P.

POCKET FIVE


NOW WITH 3" LOUDSPEAKER
 3 Tuneable wavebands, M.W., L.W., and Trawler Band, 7 stages, 5 transistors and 2 diodes, supersensitive ferrite rod aerial, attractive black and gold case. Size 5½" x 1½" x 3½" approx. All Parts including Case and Plans.



Total Building Costs **£3.60**
 P & P + Ins. 85p.

NEW Everyday Series

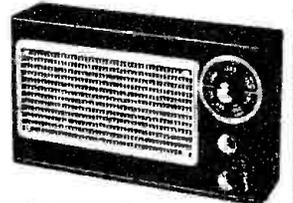Build this exciting new series of designs.



E.V.5. 5 Transistors and 2 diodes. MW/LW. Powered by 4½ volt Battery. Ferrite rod aerial, tuning condenser, volume control, and now with 3" loudspeaker. Attractive case with red speaker grille. Size 9" x 5½" x 2½" approx. All parts including Case and Plans.

Total Building costs **£4.30** P & P + Ins. 80p.

E.V. 6. Case and looks as above. 6 Transistors and 3 diodes. Powered by 9 volt battery. Ferrite rod aerial, 3" loudspeaker, etc., MW/LW coverage. Push Pull output. All parts including Case and Plans.

Total Building costs **£4.95** P & P + Ins. 90p.


E.V. 7. Case and looks as above. 7 Transistors and 3 diodes. Six wavebands, MW/LW, Trawler Band, SW1, SW2, SW3, powered by 9 volt battery. Push Pull output. Telescopic aerial for short waves. 3" Loudspeaker. All parts including Case and Plans.

Total Building costs **£6.95** P & P + Ins. 90p.

ELECTRONIC CONSTRUCTION KITS

ECK2 Self Contained Multi-Band V.H.F. Receiver Kit. 8 Transistors and 3 Diodes. Push/Pull output. 3" Loudspeaker, Gain Control. Superb 9 section swivel ratchet and retractable chrome plated telescopic aerial. V.H.F. Tuning Capacitor, Resistors, Capacitors, Transistors, etc. Will receive T.V. Sound, Public Service Band, Aircraft, V.H.F. Local Stations, etc. Operates from a 9 Volt PP7 Battery (not supplied with kit). Complete kit of parts including construction plans.


£7.95 P & P and Ins. 90p.

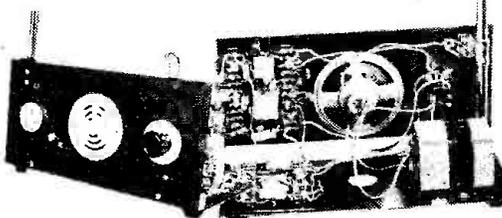

ECK4 7 Transistors, 6 tuneable wavebands, MW, LW, Trawler Band, 3 Short Wave Bands. Receiver Kit. With 5" x 3" Loudspeaker.

Push/Pull output stage, Gain Control, and Rotary Switch. 7 Transistors and 4 Diodes. 6 section chrome-plated telescopic aerial. 8" Sensitive Ready Wound Ferrite Rod Aerial. Tuning Capacitor. Resistors, Capacitors, etc. Operates from a 9 Volt PP7 Battery (not supplied with kit). Complete kit of parts including construction plans.

£7.25 P & P and Ins. 90p.

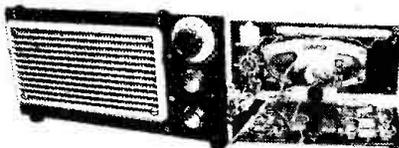


EDU-KIT JUNIOR

Completely Solderless Electronic Construction Kit. Build these projects without Soldering Iron or Solder.

- ★ Crystal Radio Medium Wave Coverage — No Battery necessary.
- ★ One Transistor Radio.
- ★ 2 Transistor Regenerative Radio
- ★ 3 Transistor Earpiece Radio Medium Wave Coverage.
- ★ 4 Transistor Medium Wave Loudspeaker Radio.
- ★ Electronic Noise Generator
- ★ Electronic Metronome.
- ★ 4 Transistor Push/Pull Amplifier.

All parts including Loudspeaker, Earpiece, MW Ferrite Rod Aerial, Capacitors, Resistors, Transistors, etc. Complete kit of parts including construction plans.

£6.55 P & P + Ins. 80p.

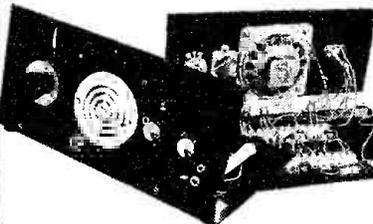

To RADIO EXCHANGE LTD
 61A HIGH STREET, BEDFORD MK40 1SA
 Tel: 0234 52367

ALL PRICES INCLUDE VAT Reg. No. 788372

- ★ Callers side entrance "Lavelis" Shop.
- ★ Open 10-1, 2.30-4.30. Mon-Fri. 9-12 Sat.

I enclose £.....
 for
 Name
 Address




PW/377

MAPLIN




ELECTRONIC ORGAN

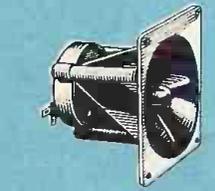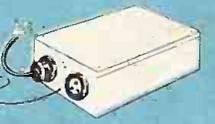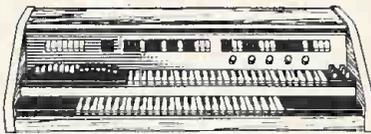The only organ you can build in stages and tailor to your requirements as you go along—and at each stage you'll have a fully working instrument! We haven't got the gimmicks (yet—they're coming soon), but we have got the most beautiful sounds—you won't find them on any organ less than twice our price. So get our MES50 series leaflets now! 65p buys the three available so far.




GRAPHIC EQUALISER

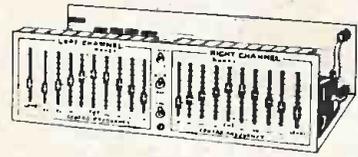

This high quality Graphic Equaliser will enhance even the most sophisticated system at a fraction of the cost of a ready-made equaliser of equal quality. You can get all the parts from us (except woodwork) including drilled and printed metalwork. Construction details in our leaflet: 15p.




TOOLS

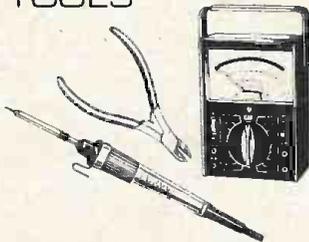


We stock an excellent range of tools especially for the electronics enthusiast. From miniature wiring tools to multimeters including soldering irons and desoldering tools, screwdrivers, cutters, pliers, strippers, miniature electric drills for p.c.b.'s, transistor tester etc. Full details on catalogue pages 167 to 176.

PEDAL UNIT


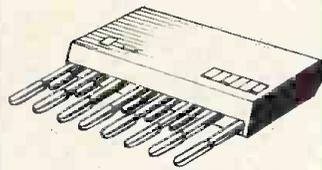


A completely self-contained pedal unit. 13-note, 2-octave range, 4 organ stops. It can be added to any organ! A really unusual extra is the bass guitar stop which uses four envelope shapers to give a real bass guitar sound. A must for the solo guitarist. Full construction details in our catalogue—post the coupon below now!

T.V. GAME

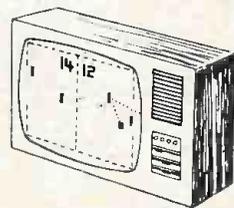

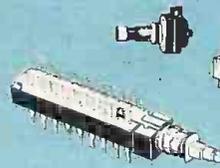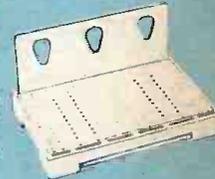Play fascinating games NOW on your own t.v. in your own living room. The kids will think it's magic when the scores pop up on the screen. Lay your bets—anyone could win—with Maplin's prices everyone can win. Complete kit to play four games only £24.50. Add 35p for copy of construction details. See our June newsletter for details of rifle kit.



Our bi-monthly newsletter keeps you up to date with latest guaranteed prices – our latest special offers (they save you pounds) – details of new projects and new lines. Send 30p for the next six issues (5p discount voucher with each copy).

MAPLIN ELECTRONIC SUPPLIES

P.O. BOX 3 RAYLEIGH ESSEX SS6 8LR

Telephone: Southend (0702) 715155

Shop: 284, London Road, Westcliff-on-Sea, Essex

(Closed on Monday) Telephone: Southend (0702) 47379

IT'S A FANTASTIC BESTSELLER!

216 big (11" x 8") pages! Over a thousand illustrations!

Over 30 pages of complete projects to build!

Thousands and thousands of useful components described and illustrated! No wonder it's a bestseller!

DON'T MISS OUT! SEND 60p NOW!

POST THIS COUPON NOW FOR YOUR COPY OF OUR CATALOGUE PRICE 60p

Please rush me a copy of your 216 page catalogue by return of post I enclose 60p, but understand that if I am not completely satisfied I may return the catalogue to you within 14 days and have my 60p refunded immediately.

NAME _____

ADDRESS _____

PW 7

