

FABULOUS PROFESSIONAL DISCO SYSTEM

F.A.L. De Luxe PROFESSIONAL Carr. CONSOLE (Powered) etc. £15

Slide Fade Controls. Autofade with Music Override on both mic. and jingle inputs. Headphone pre-fade monitor with 5 Push-button selector. Illuminated V.U. meters. Illuminated rocker switches. LED cue indicators. Tape or Jingle inputs, unity gain. Mic. channel with Bass & Treble. Slave outlet.

Treble Control (Music Channel) Output into line (Slave)
 Treble Control (Mic. Channel) Autofade Recovery
 Bass Control (Music Channel) Microphone Input.
 Bass Control (Mic. Channel) Tape/Jingle. 1/P

£399
SAVE £100

DEPOSIT £28.88

and
38 weekly payments of £9.74
 (Total £399)

TURNABLES: Garrard 125SB Belt-drive with Low-Mass 'S' arm and Magnetic Cartridge.

POWER: 120 watts continuous RMS into 4 ohms
DECK LIGHTS: Fully adjustable flexi-beams over each turntable with independent switching.
CABINET: Solidly made to withstand the rigours of transporting. Covered in heavy duty leather cloth type material in attractive colour combinations Corner cap protectors Recessed carrying handles.

INTEREST FREE CREDIT
 on this system only

List £320.76

ALL THREE UNITS PRODUCED BY BRITAIN'S LARGEST MAKERS OF DISCO EQUIPMENT



PAIR MATCHING FULL RANGE De Luxe 80w LOUDSPEAKERS

Each inc. Pair of Powerful 12" Bass units (with aluminium centre domes), and High Frequency Horn unit to extend frequency range to above 17 kHz. Normally £89.95 ea.



Make your own Console with these DISCO MODULES

CONTROL UNIT (mains powered)

Vol. (Left) Vol. (Right) Tape input and volume control. Bass, Treble, ON/OFF switch for each Table. **£25.00**
 Carr. £1

MONITOR UNIT With H/Phone Socket and Vol. Control Carr Free **£7.95**

FADER UNIT Carr Free **£7.95**

100w OUTPUT UNIT **£29.95**
 Mains powered Carr. £1.50

TITAN GROUP/DISCO SPKRS

	Value	RSC Price
T12/45R 12" 45w	£15.00	£12.95
T12/60R 12" 60w	£22.50	£14.95
T12/100 12" 100w	£36.00	£25.95
T15/60 15" 60w	£26.00	£17.95
T15/70 15" 70w	£28.00	£19.95
T15/100 15" 100w	£41.00	£29.95
T18/100 18" 100w	£51.00	£39.95

Carr. £1.20, under £18, over this add 6p per £1.




Rating RMS Imp 8-15 ohms

CABINETS FOR ABOVE Heavy duty, finished in black Vynide with Vynair fronts, protective corner pieces, various sizes cut-outs. TE1 1 x 12" £11.95. TE2 2 x 12" £16.95. Deposit Terms orders over £20.

FANTASTIC SPEAKER OFFER TWIN 12" SPEAKER CABINET PLUS PAIR 12" SPEAKERS

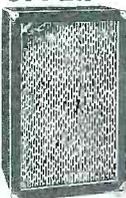of Robust vibration-proof construction. Fitted protective corner pieces. Removable Vynair covered front with silver effect trim. Sunken jack socket with escutcheon at the rear. Pair 12" 20w speakers for wiring in series and front mounting in above supplied to complete a 40 watt unit for lead guitar or P.A.




While stocks last Three items

£19.95

Carr. £2.50

RSC 100 WATT DISCO SYSTEM

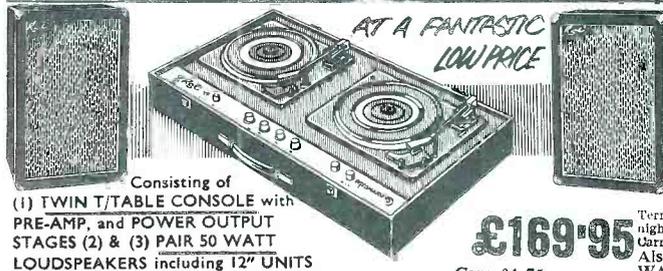

Consisting of (1) TWIN T/TABLE CONSOLE with PRE-AMP, and POWER OUTPUT STAGES (2) & (3) PAIR 50 WATT LOUDSPEAKERS including 12" UNITS

£169.95

Carr. £4.75

Terms: Deposit £30.00 and 18 fortnightly pmts, £9.80 (Total £206.40). Carr. £4.00. Also available 200 WATT SYSTEM **£199.95**

ALL RSC PRICES INCLUDE VAT

50 WATT AMPLIFIER SACRIFICE

Limited stocks of TITAN TA/50A



to be cleared to make way for a re-styled model. Solid state, 3 sep. controlled inputs plus Master control. Bass, Treble & Presence Controls. Vynide covered cabinet with corner protectives. Value £60. Terms: Dep. £7.95 & 8 monthly payments £4.72 (Total £45.71). Matching Cabinets 1 x 12" £29.95. 2 12" £49.95 Carr. £1 **£39.95**

New Branches at

★ LEEDS, ★ LIVERPOOL & ★ WOLVERHAMPTON



Barclaycard & Access PHONE ORDERS quoting CARD NUMBER accepted

MAIL ORDERS & EXPORT ENQUIRIES TO:— AUDIO HOUSE, HENCONNER LANE, LEEDS, 18. Tel: 0532 577831.

MAIL ORDERS MUST NOT BE SENT TO SHOPS TERMS C.W.O. or C.O.D. No. C.O.D. under £3. POSTAGE 60p PER ORDER OR AS QUOTED. Phone or Write for FREE CATALOGUE.

OPEN ALL DAY SATS (5 Day Week)
 BRADFORD 10 North Parade (Closed Wed.) Tel. 25349
 BIRMINGHAM 30/31 Great Western Arcade. (Closed Wed.) Tel. 021-236 1279
 CARLISLE 8 English Street (Closed Thurs.). Tel. 38744
 COVENTRY 17 Shelton Sq., The Precinct. (Closed Thurs.) Tel. 25983
 DERBY 97 St. Peter's Street (Closed Wed.) Tel. 41361
 DUNSBURY 9/11 Kingsway (Closed Tues.) Tel. 468058
 DONCASTER 3 Queensgate, Waterdale Centre. (Closed Thurs.) Tel. 63069
 EDINBURGH 101 Lothian Rd. (Closed Wed.) Tel. 229 9501

Prices correct at 11.12.78 E. & O.E. All items subject to availability
 GLASGOW 326 Argyle St. (Closed Tues.). Tel. 041-248 4158
 HULL 7 Whitefriargate (Closed Thurs.). Tel. 20505
 LEICESTER 32 High Street (Closed Thurs.). Tel. 56420
 LONDON 238 Edgware Road, W.2 (Closed Thurs.). Tel. 723 1629

★ LEEDS 16-18 County (Mecca) Arcade, Briggate (Closed Wed.). Tel. 449609
 ★ LIVERPOOL 35 Dawson Way, St. John's Precinct (Closed Wed.). Tel. 708 9380
 ★ MANCHESTER 60A Oldham Street (Closed Wed.). Tel. 236 2778

MIDDLESBROUGH 103 Linthorpe Rd. (Cl. Wed.) Tel. 247096
 ★ NEWCASTLE UPON TYNE 59 Grainger St. (Closed Wed.). Tel. 21469
 NOTTINGHAM 19/19A Market Street (Closed Thurs.). Tel. 48068
 SHEFFIELD 13 Exchange Street (Castle Mt. Bldg.) (Closed Thurs.). Tel. 20716
 ★ WOLVERHAMPTON 6 Wulfrun Way (Closed Thurs.). Tel. 26612
 ★ MUSICAL INSTRUMENTS & ACCESSORIES in stock at these branches

RADIO... ELECTRONICS... INSTRUMENTS... AUDIO...

practical WIRELESS

50p

Australia 95c
New Zealand 95c
South Africa 90c
Malaysia \$2.75

APRIL 1979

VHF MONITOR RECEIVER



Also:
THE CASSETTE TAPE MEDIUM
VHF/UHF FOLDED COLINEAR AERIAL ARRAY

TTL	★ ★	★ ★	
7401	10p	74109	25p
7402	10p	74118	75p
7403	10p	74120	80p
7404	12p	74121	25p
7405	12p	74122	35p
7406	25p	74123	40p
7407	25p	74125	35p
7408	25p	74126	35p
7409	12p	74130	120p
7410	12p	74131	90p
7411	15p	74132	45p
7412	15p	74135	90p
7413	25p	74136	80p
7414	45p	74138	100p
7415	25p	74141	50p
7416	25p	74142	180p
7417	25p	74143	270p
7418	15p	74145	55p
7419	20p	74147	100p
7420	20p	74148	90p
7421	22p	74150	65p
7422	25p	74151	45p
7423	12p	74154	70p
7424	20p	74155	45p
7425	20p	74156	45p
7426	20p	74157	55p
7427	20p	74158	55p
7428	20p	74159	55p
7429	20p	74160	60p
7430	20p	74161	60p
7431	20p	74162	60p
7432	20p	74163	60p
7433	20p	74164	60p
7434	20p	74165	60p
7435	20p	74166	60p
7436	20p	74167	60p
7437	20p	74168	60p
7438	20p	74169	60p
7439	20p	74170	100p
7440	20p	74171	80p
7441	20p	74172	80p
7442	20p	74173	80p
7443	20p	74174	80p
7444	20p	74175	60p
7445	20p	74176	60p
7446	20p	74177	60p
7447	20p	74178	60p
7448	20p	74179	60p
7449	20p	74180	60p
7450	20p	74181	60p
7451	20p	74182	60p
7452	20p	74183	60p
7453	20p	74184	60p
7454	20p	74185	60p
7455	20p	74186	60p
7456	20p	74187	60p
7457	20p	74188	60p
7458	20p	74189	60p
7459	20p	74190	60p
7460	20p	74191	60p
7461	20p	74192	60p
7462	20p	74193	60p
7463	20p	74194	60p
7464	20p	74195	60p
7465	20p	74196	60p
7466	20p	74197	60p
7467	20p	74198	60p
7468	20p	74199	60p
7469	20p	74200	60p
7470	20p	74201	60p
7471	20p	74202	60p
7472	20p	74203	60p
7473	20p	74204	60p
7474	20p	74205	60p
7475	20p	74206	60p
7476	20p	74207	60p
7477	20p	74208	60p
7478	20p	74209	60p
7479	20p	74210	60p
7480	20p	74211	60p
7481	20p	74212	60p
7482	20p	74213	60p
7483	20p	74214	60p
7484	20p	74215	60p
7485	20p	74216	60p
7486	20p	74217	60p
7487	20p	74218	60p
7488	20p	74219	60p
7489	20p	74220	60p
7490	20p	74221	60p
7491	20p	74222	60p
7492	20p	74223	60p
7493	20p	74224	60p
7494	20p	74225	60p
7495	20p	74226	60p
7496	20p	74227	60p
7497	20p	74228	60p
7498	20p	74229	60p
7499	20p	74230	60p
7500	20p	74231	60p

POWER SUPPLY CAPACITORS			
2200/16	35p	4700/63	120p
2200/63	80p	4700/70	135p
2200/100	150p	10000/10	100p
3300/30	50p	10000/25	150p
3300/63	80p	15000/15	150p
4700/25	50p	22000/25	200p
4700/40	65p		

ENQUIRIES FOR ANY OTHER TYPES

CMOS			
4000	12p	4047	80p
4001	12p	4048	50p
4002	12p	4049	25p
4006	80p	4050	25p
4007	14p	4054	100p
4009	30p	4055	130p
4011	12p	4056	120p
4012	12p	4058	100p
4013	30p	4066	35p
4015	50p	4069	12p
4016	30p	4070	12p
4017	50p	4071	12p
4018	50p	4072	12p
4019	40p	4081	12p
4020	50p	4082	12p
4022	50p	4093	70p
4023	12p	4510	60p
4024	40p	4511	70p
4025	12p	4516	65p
4026	80p	4518	65p
4027	30p	4520	65p
4028	45p	4528	80p
4029	50p	4583	70p
4030	30p		
4032	80p		
4033	100p		
4040	60p		
4043	60p		
4046	90p		

FX1593 FERRITE RINGS O/D 12mm, I/D 6mm 10 for 70p

TOGGLE SWITCHES SUB MIN Single Pole C.O. 65p Single Pole C.O. Biased 85p

RESISTORS 1/3RDW 100 of 1 type £1 00p E12 only

LINEAR			
AY3850	450p	NE556	90p
CA3039	70p	NE562B	400p
CA3046	60p	SAD1024	1500p
CA3060	225p	SL917B	65p
CA3065	200p	SN76003N	150p
CA3076	250p	SN76013N	110p
CA3080	130p	SN76013ND	125p
CA3084	250p	SN76013N	110p
CA3085	85p	SN76023ND	125p
CA3086	60p	SN76033N	150p
CA3088	190p	SN76227N	160p
CA3089	160p	SN76228N	180p
CA3090A	360p	SN7666DN	75p
CA3123E	30p	TA A300	100p
CA3130	100p	TA A350	190p
CA3140	60p	TA A550	35p
LF356	80p	TA A570	220p
LF357	80p	TA A661B	140p
LM211H	250p	TA A700	350p
LM300TR5	170p	TA D100	150p
LM301AN	20p	TA D110	130p
LM304	20p	TAD110	130p
LM307N	65p	TBA120S	60p
LM308TO5	100p	TBA120T	85p
LM308DIL	100p	TBA480Q	200p
LM309K	100p	TBA520Q	200p
LM310TO5	45p	TBA530Q	200p
LM311TO5	45p	TBA540	200p
LM317K	325p	TBA550Q	250p
LM324	70p	TBA560C	250p
LM339	60p	TBA641A12	200p
LM348N	90p	TBA700	180p
LM350	60p	TBA720Q	225p
LM381N	90p	TBA750Q	200p
LM382	90p	TBA800	80p
LM391	180p	TBA810	100p
LM555	25p	TBA820	100p
LM709C	20p	TBA920Q	100p
LM710TO5	69p	TC A270	220p
LM710DIL	65p	TC A270S	220p
LM723TO5	40p	TC A760	300p
LM723DIL	40p	TC A500A	450p
LM733	120p	TD A1034	450p
LM741	20p	TD A2020	300p
LM748	40p	TL084	120p
LM750	45p	XR220	450p
LM751	20p	XR220E	600p
LM752	20p	XR221E	650p
LM753	20p	XR256P	250p
LM754	20p	XR4136	150p
LM755	20p	XR4202	150p
LM756	20p	XR4212	150p
LM757	20p	XR4216	150p
LM758	20p	XR4218	150p
LM759	20p	XR4219	150p
LM760	20p	XR4220	150p
LM761	20p	XR4221	150p
LM762	20p	XR4222	150p
LM763	20p	XR4223	150p
LM764	20p	XR4224	150p
LM765	20p	XR4225	150p
LM766	20p	XR4226	150p
LM767	20p	XR4227	150p
LM768	20p	XR4228	150p
LM769	20p	XR4229	150p
LM770	20p	XR4230	150p
LM771	20p	XR4231	150p
LM772	20p	XR4232	150p
LM773	20p	XR4233	150p
LM774	20p	XR4234	150p
LM775	20p	XR4235	150p
LM776	20p	XR4236	150p
LM777	20p	XR4237	150p
LM778	20p	XR4238	150p
LM779	20p	XR4239	150p
LM780	20p	XR4240	150p
LM781	20p	XR4241	150p
LM782	20p	XR4242	150p
LM783	20p	XR4243	150p
LM784	20p	XR4244	150p
LM785	20p	XR4245	150p
LM786	20p	XR4246	150p
LM787	20p	XR4247	150p
LM788	20p	XR4248	150p
LM789	20p	XR4249	150p
LM790	20p	XR4250	150p
LM791	20p	XR4251	150p
LM792	20p	XR4252	150p
LM793	20p	XR4253	150p
LM794	20p	XR4254	150p
LM795	20p	XR4255	150p
LM796	20p	XR4256	150p
LM797	20p	XR4257	150p
LM798	20p	XR4258	150p
LM799	20p	XR4259	150p
LM800	20p	XR4260	150p

ELEC CAPACITORS			
0.47/25	7p	47/10	8p
1/16	7p	47/16	8p
1/25	7p	47/25	8p
1/50	7p	47/50	8p
2/25	7p	100/10	8p
2/50	7p	100/20	8p
3/25	7p	100/16	8p
4/7/10	7p	100/50	8p
4/7/16	7p	100/63	16p
4/7/25	7p	220/16	12p
4/7/50	7p	220/25	14p
6/8/25	7p	220/50	22p
10/10	7p	330/25	22p
10/16	7p	330/35	16p
10/25	7p	330/50	20p
10/50	7p	470/10	14p
22/6V3	7p	470/25	19p
22/10	7p	470/35	20p
22/16	7p	470/50	24p
22/25	7p	470/70	27p
22/35	7p	1000/16	27p
22/50	7p	1000/25	30p
33/6V3	7p	1000/35	35p
33/16	8p	1000/40	40p
33/25	8p	1000/63	50p
33/50	8p	1200/63	60p
33/50	9p	2200/10	30p

POLY CAPS			
1000 PF	5p	0.1 uF	6p
2200	5p	0.22 uF	7p
3300	5p	0.33 uF	9p
4700	5p	0.47 uF	12p
6800	5p	1.0 uF	20p
0.01 uF	5p	2.2 uF	25p
0.022 uF	5p	4.7 uF	35p
0.033 uF	5p	10 uF	40p
0.047 uF	5p	10 uF	60p

TANT. BEADS			
0.1/35V	14p	3/16V	14p
0.15/35V	14p	4/7/16V	14p
0.22/35V	14p	4/7/25V	14p
0.33/35V	14p	4/7/35V	14p
0.47/10V	14p	6/8/6V3	14p
0.47/35V	14p	1/0/35V	14p
0.68/35V	14p	1/0/35V	14p
1.0/10V	14p	22/15V	21p
1.0/35V	14p	33/16	25p
1.5/35V	14p	47/3V	20p
2.2/25V	14p	47/16V	25p
2.2/35V	14p	100/3V	25p

SPECIAL OFFER 2000uF 35v 40p 100 £30

REED INSERTS One Price 26MM Long 10 for £1 00p 50MM Long 10 for £2 60p

TRANSISTORS		
AA113	10p	BC171

practical WIRELESS

APRIL 1979
VOLUME 55
NUMBER 4
ISSUE 866

BRITAINS LEADING JOURNAL FOR THE RADIO & ELECTRONIC CONSTRUCTOR

Published by IPC Magazines Ltd., Westover House, West Quay Rd., POOLE, Dorset BH15 1JG

QUERIES

While we will always try to assist readers in difficulties with a *Practical Wireless* project, we cannot offer advice on modifications to our designs, nor on commercial radio, TV or electronic equipment. Please address your letters to the Editor, *Practical Wireless*, at the above address, giving a clear description of the problem and enclosing a stamped self-addressed envelope. Only one project per letter please.

Components are usually available from advertisers. A source will be suggested for difficult items.

SUBSCRIPTIONS

Subscriptions are available to both home and overseas addresses at £10.60 per annum, from "**Practical Wireless**" Subscription Department, Oakfield House, Perrymount Road, Haywards Heath, West Sussex RH16 3DH.

BACK NUMBERS AND BINDERS

Limited stocks of some recent issues of *PW* are available at 75p each, including post and packing to addresses at home and overseas.

Binders are available (Price £2.85 to UK addresses or £3.45 overseas, including post and packing) each accommodating one volume of *PW*. Please state year and volume number for which the binder is required.

Send your orders to **Post Sales Department, IPC Magazines Ltd., Lavington House, 25 Lavington Street, London SE1 0PF.**

All prices include VAT where appropriate. Please make cheques, postal orders, etc., payable to IPC Magazines Limited.

COPYRIGHT

© IPC Magazines Limited 1979. Copyright in all drawings, photographs and articles published in *Practical Wireless* is fully protected and reproduction or imitation in whole or in part is expressly forbidden.

All reasonable precautions are taken by *Practical Wireless* to ensure that the advice and data given to readers are reliable. We cannot however guarantee it and we cannot accept legal responsibility for it. Prices are those current as we go to press.

NEWS & VIEWS

- 20 Editorial**
Citizens' Band—Yes or No?
- 20 PW Personality**
Peter Metalli
- 21 Citizens' Band Association**
A Letter to the Prime Minister
- 24 News . . . 4**
- 29 Letters**
Comments from *PW* readers
- 31 Kindly Note**
PW "Hythe" Marine Band Receiver, February 1979
PW "Wimborne" Music Centre
- 51 Production Lines** *Alan Martin*
Information on the latest products
- 55 Hotlines** *Ginsberg*
Recent developments in electronics
- 78 RAE Reprint Announcement**

FOR OUR CONSTRUCTORS

- 22 VHF/UHF Folded Colinear Aerial Array** *Fred Judd*
A simple design giving 3dB gain over a dipole
- 32 Follow-up to the PW "Sandbanks"** *P. J. Wales*
Modified search-coil designs
- 34 VHF Monitor Receiver** *James M. Bryant*
A miniature high-performance design for n.b.f.m.
- 42 PW "Winton" Stereo Amplifier—2** *E. A. Rule*
Beginning constructional details
- 52 Logical Noughts and Crosses—1** *J. D. Mitchell*
Pit your wits against the machine
- 62 FM Multitester** *D. Whitfield & M. Tooley*
A comprehensive test—test for the v.h.f. enthusiast

GENERAL INTEREST

- 26 The Cassette Tape Medium** *Gordon J. King*
The development of the Compact Cassette system
- 30 Simple Audio Filter Design** *S. Skepper*
An introduction to filter calculations
- 39 Wireless went to War** *Ron Ham*
Recollections of military communications up to 1939
- 56 Stereo Decoders—Devices & Circuits—1** *M. J. Darby*
A survey of current i.c.s and their application
- 68 On the Air**
Amateur Bands *Eric Dowdeswell*
MW Broadcast Bands *Charles Molloy*
SW Broadcast Bands *Charles Molloy*
VHF Bands, including What do the VHF's
have to offer?—3 *Ron Ham*
VHF Personality—Guy Stanbury *Ron Ham*

Our May issue will be published on 6 April
(for details see page 33)

The latest kit innovation!

from Sparkrite

Sparkrite was featured by Shaw Taylor in "DRIVE IN"

the quickest fitting
CLIP ON
capacitive discharge
electronic ignition
in KIT FORM



- Smoother running
- Instant all-weather starting
- Continual peak performance
- Longer coil/battery/plug life
- Improved acceleration/top speeds
- Optimum fuel consumption

Sparkrite X4 is a high performance, high quality capacitive discharge, electronic ignition system in kit form. Tried, tested, proven, reliable and complete. It can be assembled in two or three hours and fitted in 1-3 mins. Because of the superb design of the Sparkrite circuit it completely eliminates problems of the contact breaker. There is no misfire due to contact breaker bounce which is eliminated electronically by a pulse suppression circuit which prevents the unit firing if the points bounce open at high R.P.M. Contact breaker burn is eliminated by reducing the current to about 1/50th of the norm. It will perform equally well with new, old, or even badly pitted points and is not dependent upon the dwell time of the contact breakers for recharging the system. Sparkrite incorporates a short circuit protected inverter which eliminates the problems of SCR lock on and, therefore, eliminates the possibility of blowing the transistors or the SCR. (Most capacitive discharge ignitions are not completely foolproof in this respect). The circuit incorporates a voltage regulated output for greatly improved cold starting. The circuit includes built in static timing light, systems function light, and security changeover switch. All kits fit vehicles with coil distributor ignition up to 8 cylinders.

THE KIT COMPRISES EVERYTHING NEEDED

Die pressed epoxy coated case, Ready drilled, aluminium extruded base and heat sink, coil mounting clips, and accessories. Top quality 5 year guaranteed transformer and components, cables, connectors, P.C.B.'s, nuts, bolts and silicon grease. Full instructions to assemble kit neg. or pcs. earth and fully illustrated installation instructions.

NOTE - Vehicles with current impulse tachometers (Smiths code on dial RV1) will require a tachometer pulse slave unit. Price £3.85 inc. VAT, post & packing. U.K. only.

Electronic Design Associates, 82 Bath Street, Walsall, WS1 3DE

Electronics Design Associates, Dept. PW4
82 Bath Street, Walsall, WS1 3DE. Phone: (9) 614791

Name

Address

Phone your order with Access or Barclaycard

Inc. VAT and P.P.

QUANTITY REQD.

Send SAE if brochure only required.

X4 KIT £16.65

TACHOPULSE SLAVE UNIT £3.85

I enclose cheque/P.O.'s for

£

Cheque No

Please state polarity pos. or neg. earth
Access or Barclaycard No.

VALVES		PC800	1.25	SP61	0.85	3E29	5.50	6H6	4.20	12SJ7	0.55
A1065	1.25	EF80	0.40	TT21	7.50	S34	0.50	6J7	0.75	12SD7	0.55
AR8	0.60	EF83	1.50	PC889	0.55	U25	1.00	3V4	0.85	6J5	0.75
APP3	0.60	EF85	0.55	PC889	0.55	U26	0.85	5B/2544M6.50	6J5GT	0.55	1306
ATP4	3.00	EF91	0.65	PC889	0.55	U27	1.00	5B/255M	6.50	6J6	0.50
B12H	3.00	EF91	0.65	PCF82	0.40	U191	0.75	5B/258M	6.50	6J7	0.75
CY31	0.50	EF92	0.75	PCF84	0.65	U281	0.50	5R4G7	1.10	6J7G	0.50
DAF96	0.60	EF95	0.45	PCF86	0.65	U301	0.50	5V4G	0.65	6K7G	0.70
DET22	19.50	EF183	0.65	PCF200	0.90	U801	0.80	5Y3GT	0.65	6K8GT	0.55
DF96	0.60	EF184	1.60	PCF201	0.90	U801	0.80	5Z3T	1.00	6L6M	1.95
DH75	0.40	EF804	2.00	PCF201	0.90	U801	0.80	5Z4G	0.70	6L6GT	0.90
OK96	0.80	EFL200	0.75	PCF802	1.65	U8F29	0.50	5Z4GT	0.70	6L6GT	0.90
OL92	0.50	EH90	0.60	PCF805	1.65	U8F29	0.50	5Z4GT	0.70	6L6GT	0.90
OY86/87	0.55	EL32	0.90	PCF806	0.85	U8L1	1.00	5Z4GT	0.70	6L6GT	0.90
OY802	0.55	EL34	2.20	PCF808	1.80	U8L21	0.75	5Z4GT	0.70	6L6GT	0.90
E55L	7.50	EL37	3.00	PCF808	1.80	U8L21	0.75	5Z4GT	0.70	6L6GT	0.90
E88 CC/011	1.30	EL41	1.60	PCF808	1.80	U8L21	0.75	5Z4GT	0.70	6L6GT	0.90
E180CC	1.30	EL81	1.05	PCF808	1.80	U8L21	0.75	5Z4GT	0.70	6L6GT	0.90
E180E	6.00	EL82	0.60	PCF808	1.80	U8L21	0.75	5Z4GT	0.70	6L6GT	0.90
E182CC	3.50	EL84	0.60	PCF808	1.80	U8L21	0.75	5Z4GT	0.70	6L6GT	0.90
E476	2.00	EL86	0.95	PCF808	1.80	U8L21	0.75	5Z4GT	0.70	6L6GT	0.90
E48C80	0.50	EL90	1.30	PCF808	1.80	U8L21	0.75	5Z4GT	0.70	6L6GT	0.90
EB91	0.40	EL91	1.60	PCF808	1.80	U8L21	0.75	5Z4GT	0.70	6L6GT	0.90
EB33	1.00	EL95	0.70	PCF808	1.80	U8L21	0.75	5Z4GT	0.70	6L6GT	0.90
EBF80	0.50	EL504	0.80	PCF808	1.80	U8L21	0.75	5Z4GT	0.70	6L6GT	0.90
EBF83	0.50	EL802	1.50	PCF808	1.80	U8L21	0.75	5Z4GT	0.70	6L6GT	0.90
EBF89	0.50	EL822	3.00	PCF808	1.80	U8L21	0.75	5Z4GT	0.70	6L6GT	0.90
EC52	0.40	EM31	0.75	PCF808	1.80	U8L21	0.75	5Z4GT	0.70	6L6GT	0.90
EC81	0.55	EM80	0.60	PCF808	1.80	U8L21	0.75	5Z4GT	0.70	6L6GT	0.90
EC82	0.50	EM81	0.60	PCF808	1.80	U8L21	0.75	5Z4GT	0.70	6L6GT	0.90
EC83	1.15	EM84	0.40	PCF808	1.80	U8L21	0.75	5Z4GT	0.70	6L6GT	0.90
EC84	0.45	EM87	1.00	PCF808	1.80	U8L21	0.75	5Z4GT	0.70	6L6GT	0.90
EC85	0.50	EV51	0.45	PCF808	1.80	U8L21	0.75	5Z4GT	0.70	6L6GT	0.90
EC86	1.25	EV80	0.45	PCF808	1.80	U8L21	0.75	5Z4GT	0.70	6L6GT	0.90
EC88	0.60	EV86/87	0.55	PCF808	1.80	U8L21	0.75	5Z4GT	0.70	6L6GT	0.90
EC89	0.80	EV88	0.55	PCF808	1.80	U8L21	0.75	5Z4GT	0.70	6L6GT	0.90
ECF80	0.50	EZ80	0.45	PCF808	1.80	U8L21	0.75	5Z4GT	0.70	6L6GT	0.90
ECF82	0.45	EZ81	0.60	PCF808	1.80	U8L21	0.75	5Z4GT	0.70	6L6GT	0.90
ECF801	0.75	GY501	0.60	PCF808	1.80	U8L21	0.75	5Z4GT	0.70	6L6GT	0.90
ECF802	0.45	EZ82	0.65	PCF808	1.80	U8L21	0.75	5Z4GT	0.70	6L6GT	0.90
ECF803	0.95	EZ82	0.65	PCF808	1.80	U8L21	0.75	5Z4GT	0.70	6L6GT	0.90
ECF83	1.50	EZ33	3.50	PCF808	1.80	U8L21	0.75	5Z4GT	0.70	6L6GT	0.90
ECF84	0.85	EZ34	2.00	PCF808	1.80	U8L21	0.75	5Z4GT	0.70	6L6GT	0.90
ECF85	0.45	EZ37	2.50	PCF808	1.80	U8L21	0.75	5Z4GT	0.70	6L6GT	0.90
ECF84	0.95	KT66	4.00	PCF808	1.80	U8L21	0.75	5Z4GT	0.70	6L6GT	0.90
ECL80	0.60	KT88	5.75	PCF808	1.80	U8L21	0.75	5Z4GT	0.70	6L6GT	0.90
ECL82	0.55	MH4	1.00	PCF808	1.80	U8L21	0.75	5Z4GT	0.70	6L6GT	0.90
ECL83	1.20	ML6	1.00	PCF808	1.80	U8L21	0.75	5Z4GT	0.70	6L6GT	0.90
ECL85	0.65	OA2	0.55	PCF808	1.80	U8L21	0.75	5Z4GT	0.70	6L6GT	0.90
ECL86	0.55	OB2	0.60	PCF808	1.80	U8L21	0.75	5Z4GT	0.70	6L6GT	0.90
EF37A	1.50	PBC80	0.40	PCF808	1.80	U8L21	0.75	5Z4GT	0.70	6L6GT	0.90
FF39	2.90	PC85	0.50	PCF808	1.80	U8L21	0.75	5Z4GT	0.70	6L6GT	0.90
FF40	0.70	PC86	0.95	PCF808	1.80	U8L21	0.75	5Z4GT	0.70	6L6GT	0.90
FF41	0.75	PC88	0.75	PCF808	1.80	U8L21	0.75	5Z4GT	0.70	6L6GT	0.90


Add 12 1/2% for V.A.T.

POSTAGE: £1-£2 20p; £2-£3 30p; £3-£5 40p; £5-£10 60p; over £10 free, minimum order £1.
A lot of these valves are imported and prices vary for each delivery, so we reserve the right to change prices for new stock when unavoidable.

VALVES AND TRANSISTORS
Telephone enquiries for valves, transistors, etc.; retail 749 3934, trade and export 743 0899.

CELOMOR 907353/ London
(ELECTRONICS) LTD.
170 Goldhawk Rd., London W.12
Tel. 01-743 0899
Open Monday to Friday
9-12.30, 1.30-5.30 p.m.

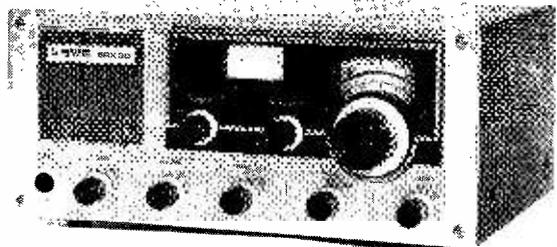OPEN UP THE EXCITING WORLD OF SHORT WAVE LISTENING



SRX-30

For the advanced, keen short wave listener, the choice of receiver has usually been between cheap and nasty or very good but very expensive equipment. We think that the SRX-30 will provide that listener with excellent performance at a reasonable cost and is the answer to this eternal problem. The SRX-30 is based on an advanced drift cancelling loop system which gives spot on dial accuracy at any frequency between 500 KHz and 30 MHz together with easy to understand frequency readout. Suitable for all users from raw beginners, thanks to its simplicity of operation; to experienced listeners and amateur operators thanks to its advanced technology, the SRX-30 is the best communications receiver available in its price range today.

Completely self contained, including operation from mains or 12 volts dc, the SRX-30 is at home on broadcast or amateur bands. All mode reception of AM, CW, USB, and LSB is provided and receiver selectivity is automatically switched to give optimum performance on any mode. Send for full details today or give us a ring and we'll tell you all about the SRX-30. Price £175 inc. vat. Carriage by Securicor £3.

NEW. Bellsonic power supply giving fully regulated 12 V dc output at 3 amps continuous rating and 5 amps peak rating from 220-240 V ac mains input. Automatic over current trip for safety. Multitude of uses for the amateur experimenter or professional user. Incredibly low price £17.28 inc. vat. P & P 86p.

NEW. CL22 aerial tuner which will match almost any receiver to almost any aerial at any frequency between 1.5 and 30 MHz. Six switching ranges with fully tunable receiver and aerial matching capacitors. A worthwhile addition to any SWL station and an instant improvement in aerial matching problems. Price £15.75 inc. vat. P & P 66p.

NEW. Transform your TRIO 9R 59D, DE or DS with our digital readout unit giving direct readout of operating frequency. Complete with fitting instructions. £38.88 inc. vat. P & P 28p.

We also stock the RAK Listener 3 aerial system for the man who demands the best and has the room for it. Double dipole system complete with H/D alloy wire, insulators, coaxial feeder, centre connector etc. in an overall length of 75 feet covering the frequency range up to 30 MHz. Price £18. inc. vat. P & P 86p.

Also available is the Listener 1 loaded end fed single wire aerial system for restricted space situations. Overall length only 15 feet due to use of loading coil and element folding. Ideal aerial for any user of short wave bands. Price £7.50 inc. vat. P & P 86p. If you need professional oscilloscopes at reasonable prices, please contact us for details of terrific TRIO range. Full range of other test equipment stocked.

For all that's good in Amateur Radio, contact: **LOWE ELECTRONICS LTD.,** 119 Cavendish Road, Matlock, Derbyshire. Tel: 0629 2430 or 2817. For full catalogue, simply send 45p in stamps and request catalogue CPW.

B. BAMBER ELECTRONICS

Dept. P.W.5 STATION ROAD, LITTLEPORT, CAMBS, CB6 1QE
Telephone: ELY (0353) 860185 (2 lines) Tuesday to Saturday

OSMOR 10V REED RELAY COILS 1k ohm coil to fit $\frac{1}{2}$ " reeds (not supplied) 2 for 50p.
HF CHOKES wound on $\frac{1}{2}$ " x 1" long ferrites. 4 for 50p.
VHF CHOKES wound on 6-hole tubular ferrites. 5 for 40p.
DUAL TO18 HEATSINKS 1" x $\frac{1}{2}$ " x $\frac{1}{2}$ " with screw-in clamps. 3 for 50p.
MAINS TESTER SCREWDRIVERS 100 to 500V. Standard size 50p. Large 70p.
RADIO PLIERS 6 $\frac{1}{2}$ " £1-80. 8 $\frac{1}{2}$ " £2-00.
SMALL SIDE CUTTERS (with wire holding device) £4.50.

HIGH QUALITY RELAYS, 4 pole C/O, 3A contacts. 12V DC coil, 150 ohm. Size approx. 1" x $\frac{1}{2}$ " x 1 $\frac{1}{2}$ ". with plastic covers. 80p each or 2 for £1-50.

LARGE ELECTROLYTIC PACKS. Contain range of large electrolytic capacitors, low and high voltage types, over 40 pieces. £3-00 per pack (+ 12 $\frac{1}{2}$ % VAT).

Slider Switches. 2 pole make and break (or can be used as 1 pole change-over by linking the two centre pins). 4 for 50p.

DUE TO A CHANGE OF SUPPLIER, OUR STOCK ALUMINIUM BOXES AND VINYL COVERED EQUIPMENT CASES WILL BE AS FOLLOWS

Aluminium boxes with lids	
AL1	3" x 2" x 1" 60p
AL2	4" x 3" x 1 $\frac{1}{2}$ " 70p
AL3	4" x 3" x 2" 80p
AL4	6" x 4" x 2" 90p
AL5	6" x 4" x 3" £1-25
AL6	8" x 6" x 2" £1-50
AL7	8" x 6" x 3" £1-75

Vinyl Equipment Cases
Blue Vinyl covered steel tops with plain aluminium lower sections.

BC0	6" x 2 $\frac{1}{2}$ " x 2 $\frac{1}{2}$ "	£1-00
BC1	6" x 4 $\frac{1}{2}$ " x 2"	£2-00
BC2	6" x 4" x 3 $\frac{1}{2}$ "	£2-25
BC3	8" x 5 $\frac{1}{2}$ " x 2"	£2-50
BC4	10" x 6 $\frac{1}{2}$ " x 3"	£3-00
BC7	12" x 6 $\frac{1}{2}$ " x 5"	£3-25

MAINS TRANSFORMERS. Type 15/300 240V input. 15V at 300mA output. £1-50 each.
MAINS TRANSFORMERS. Type 45/100, 240, 220, 110. 0V input. 45V output. £1-50 each.

PLEASE ADD 8% VAT UNLESS OTHERWISE STATED

CELESTION 8" x 5" ELLIPTICAL SPEAKERS, 20 ohm, 3 watts rated. £1-50 each + 12 $\frac{1}{2}$ % VAT.

IC AUDIO AMP PCB. Output 2 watts into 3 ohm speaker, 12V DC supply, size approx. 5 $\frac{1}{2}$ " x 1 $\frac{1}{2}$ " x 1" high, with integral heatsink, complete with circuits. £2-00 each.

NICAD CONVERTER PCB. (Low power inverter). Size approx. 4" x 1 $\frac{1}{2}$ " x 1" high, 12V DC supply. 60V DC output, through pot on pcb, for charging Nicads, etc. (ideal for charging portable batteries from mobile supply). Only needs one BFY50/51/52 or similar transistor, which can be mounted direct on the pcb pins on board, fitted with a star-type heatsink (Not Supplied). £2-00 each.

THE NEW EAGLE INTERNATIONAL CATALOGUE IS AVAILABLE ON REQUEST containing Audio, In-car, and test equipment, etc.

DECIMAL KEYBOARDS, pressure sensitive type, when pressed contacts go from O/C to approx. 25 ohms. Switches only, no encoders. Size approx. 3" x 3", with large square touch plates, O-9+Clear, A, B, Dual Watch, and spare. Few only. £2-00 while stocks last.

TYPE 8079 FULL RANGE SPEAKER, 10" dia, 15 ohm. £5-00 each (or 2 for £9-00) + 12 $\frac{1}{2}$ % VAT.

SEMICONDUCTORS
BSX20 (VHF Osc/Mult). 3 for 50p.
BC108 (metal can), 4 for 50p.
PBC108 (plastic BC108), 5 for 50p.
BFY51 Transistors, 4 for 60p.
BCY72 Transistors, 4 for 50p.

PNP audio type T05 Transistors. 12 for 25p.
BF152 (UHF amp/mixer). 3 for 50p.

2N3919 Fet. 3 for 50p.
BC148 NPN SILICON, 4 for 50p.
BC158 PNP SILICON, 4 for 50p.
BAY 31 Signal Diodes, 10 for 35p.
IN 4148 (IN914) 10 for 25p.
BC107 (Metal can) 4 for 50p.
SCRs 400V at 3A, stud type, 2 for £1-00.

Tip2955 Silicon PNP power transistor, 60V at 15A, 90 Watts. Flat pack type, 2 for £1-50.
GERMANIUM DIODES approx 30 for 30p.
741 CG op amps by RCA 4 for £1.

RED LEDs (min. type) 5 for 70p.
T03 transistor insulator sets 10 for 50p.

SPECIAL OFFER FOR COMPUTER BUILDERS, ETC.
19 way ribbon cable, decimal coded, 4 metres for 1.25.
13 way heavy duty ribbon cable, decimal coded, (ideal for PSU runs) 3 metres for £1.50.

CLAREED REED RELAYS, complete with reeds, TYPE 1. Size approx. 2 $\frac{1}{2}$ " x $\frac{1}{2}$ " x $\frac{1}{2}$ " 1 pole make, 9V 400 ohm coil, 35p each. TYPE 2. Size approx. 2 $\frac{1}{2}$ " x 1 $\frac{1}{2}$ " x $\frac{1}{2}$ ". 2 pole make + 2 pole break, 2 x 9V 200 ohm coils, 60p each.

VIDICON SCAN COILS (Transistor type, but no data) complete with vidicon base £6-50 each. Brand New.

IC TEST CLIPS, clip over IC while still soldered to pcb or in socket, Gold-plated pins, ideal for experimenters or service engineers. 28 pin DIL £1-75. 40 pin DIL £2-00. Or save by buying one of each for £3-50.

GLASS BEAD FEEDTHROUGH INSULATORS. Solder-in type, overall dia. approx. 5mm. Pack of approx. 50 for 50p.

PLASTIC PROJECT BOXES with screw on lids (in black ABS) with brass inserts.
Type NBI approx. 3 $\frac{1}{2}$ " x 2 $\frac{1}{2}$ " x 1 $\frac{1}{2}$ " 45p each
Type NB2 approx. 4" x 3" x 1 $\frac{1}{2}$ " 55p each
Type NB3 approx. 4 $\frac{1}{2}$ " x 3 $\frac{1}{2}$ " x 1 $\frac{1}{2}$ " 65p each
Type NB4 approx. 6 $\frac{1}{2}$ " x 5 $\frac{1}{2}$ " x 3 $\frac{1}{2}$ " £1-50.

DIE/CAST ALUMINIUM BOXES
Send for Latest Price List.

PLUGS AND SOCKETS
BNC Plugs, new 50p each.
N-Type Plugs 50 ohm, 60p each. 3 for £1-50.
PL259 Plugs (PTFE) brand new, packed with reducers. 75p each.
SO239 Sockets (PTFE), brand new (4-hole fixing type). 60p each.

SOLDER SUCKERS (Plunger type) Standard Model. £5-50. Skirted Model. £6. Spare Nozzles 60p each.

NEW MARKSMAN RANGE OF SOLDERING IRONS.
S1400 40W 240V £4-50.
S125DK 25W 240V + bits etc. KIT £5-50.
BENCH STAND with spring and sponge for Marksmen Irons £2-70.

Spare bits MT9 (for 15W) 60p, MT5 (for 25W) 50p, MT10 (for 40W) 55p.
ALL PRICES + 8% VAT.

TCP2 TEMPERATURE CONTROLLED IRON.

Temperature controlled iron and PSU. £30 + VAT (£2-40).

SPARE TIPS
Type CC single flat. Type K double flat fine tip. Type P, very fine tip £1-50 each + VAT (8p). MOST SPARES AVAILABLE.

WELLER SOLDERING IRONS EXPERT. Built-in-spotlight illuminates work. Pistol grip with fingertip trigger. High efficiency copper soldering tip.
EXPERT SOLDER GUN S1000 £12-00.
EXPERT SOLDER GUN KIT (spare bits, case, etc.) £15-00. Spare bits 40p pair.

MIXED COMPONENT PACKS, containing resistors, capacitors, pots, etc. All new. Hundreds of items. £2 per pack, while stocks last.

BSR AUTOCHARGE RECORD PLAYER DECKS with cue device, 33-45-78 RPM, for 7", 10", 12" records. Fitted with SC12M Stereo Ceramic cartridge and styli. Brand new £14-00 + 12 $\frac{1}{2}$ % VAT.

GARRARD AUTOCHARGE RECORD PLAYER DECKS, Model 6-300, with cue device, 33-45-78 r.p.m., for 7", 10", 12" records. Fitted with KS418 Stereo Ceramic cartridge and styli. Brand new £16-00 + 12 $\frac{1}{2}$ % VAT. Please note, record decks sent by Roadline, allow 14 days for delivery.

FULL RANGE OF BERNARDS/BABANI ELECTRONICS BOOKS IN STOCK. S.A.E. FOR LIST.


VARICAP TUNERS Mullard type ELC1043/05. Brand New. £5-00 + 12 $\frac{1}{2}$ % VAT.

BARGAIN PACK OF LOW VOLTAGE ELECTROLYTIC CAPACITORS. Up to 50V working. Seatronic Manufacture. Approx 100. £1-50 per pack + 12 $\frac{1}{2}$ % VAT.


DuBilier Electrolytics, 50 F, 450V, 2 for 50p.
DuBilier Electrolytics, 100 μ F, 275V, 2 for 50p.
Plessey Electrolytics, 470 F, 63V, 3 for 50p.
TCC Electrolytics, 1000 F, 30V, 3 for 60p.
DuBilier Electrolytics, 5000 F, 35 V, 50p each.
DuBilier Electrolytics, 5000 F, 50V, 60p each.
ITT Electrolytics, 8800 F, 25V, high grade screw terminals, with mounting clips. 50p each.
PLEASE ADD 12 $\frac{1}{2}$ % VAT TO ALL CAPACITORS.

Terms of Business: CASH WITH ORDER, MINIMUM ORDER £2. ALL PRICES INCLUDE POST & PACKING (UK ONLY). SAE with ALL ENQUIRIES
Please: PLEASE ADD VAT AS SHOWN. ALL GOODS IN STOCK DESPATCHED BY RETURN. CALLERS WELCOME BY APPOINTMENT ONLY.

The professional scopes you've always needed.

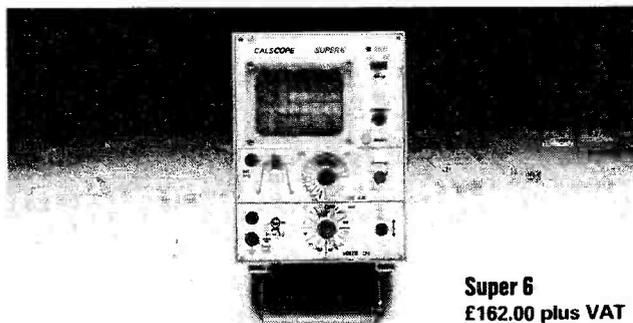

Super 6
£162.00 plus VAT

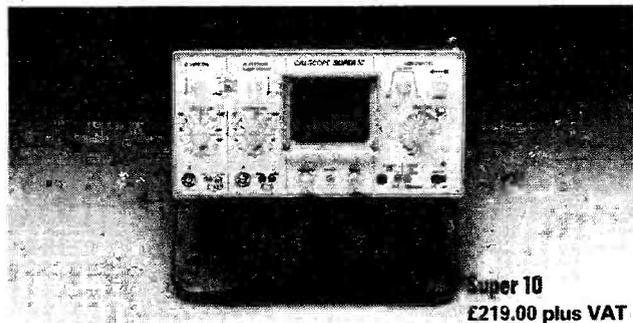

Super 10
£219.00 plus VAT

When it comes to oscilloscopes, you'll have to go a long way to equal the reliability and performance of Calscope.

Calscope set new standards in their products, as you'll discover when you compare specification and price against the competition.

The Calscope Super 10, dual trace 10 MHz has probably the highest standard anywhere for a low cost general purpose oscilloscope. A 3% accuracy is obtained by the use of stabilised power supplies which cope with mains fluctuations.

The price £219 plus VAT.

The Super 6 is a portable 6MHz single beam model with easy to use controls and has a time base range of 1 μ s to 100ms/cm with 10mV sensitivity. Price £162 plus VAT.

Prices correct at time of going to press.

CALSCOPE DISTRIBUTED BY
Marshall's Electronic Components,
Kingsgate House,
Kingsgate Place,
London, N.W.6.

Audio Electronics,
301 Edgware Road, London W.2.
Tel: 01-724 3564
Access and Barclay card facilities
(Personal Shoppers)

Maplin Electronics Supplies Ltd.
P.O. Box 3
Rayleigh, Essex.
Tel: 0702 715 155
Mail Order

CALSCOPE

Practical Wireless, April 1979

RADIO EXCHANGE LIMITED

NEW ELECTRONIC MASTER KIT



With special V.H.F. Tuner Module to construct. A completely Solderless Electronic Construction Kit, with ready drilled Bakelite Panels, Nuts, Bolts, Wood Screws, etc. Also in the kit: Transistors, Capacitors, Resistors, Pots, Switches, Wire, Sleeving, Knobs, Dials, 5" x 3" Loudspeaker and Speaker Case, Crystal Earpiece, etc. Also ready wound Coils and Ferrite Rod Aerial. These are the Projects you can build with the components supplied with the kit, together with comprehensive Instruction Manual Pictorial and Circuit Diagrams.

Projects:

V.H.F. Tuner Module ★ A.M. Tuner Module ★ M.W. L.W. Diode Radio ★ Six Transistor V.H.F. Earpiece Radio ★ One Transistor M.W. L.W. Radio ★ Two Transistor Metronome with variable beat control ★ Three Transistor and Diode Radio M.W. L.W. ★ Four Transistor Push Pull Amplifier ★ Eight Transistor V.H.F. Loudspeaker Receiver ★ Variable A.F. Oscillator ★ Jiffy MultiTester ★ Four Transistor and Diode M.W. L.W. Radio ★ A.F. R.F. Signal Injector ★ Five Transistor Push Pull Amplifier ★ Sensitive Hearing Aid Amplifier ★ Three Transistor and Diode Short Wave Radio ★ Signal Tracer ★ Three Transistor Push Pull Amplifier ★ One Transistor Class A Output Stage to drive Loudspeaker ★ Sensitive Transistor Pre-Amp ★ Transistor Tester ★ Sensitive Three Transistor Regenerative Radio ★ Four Transistor M.W. L.W. and Diode Tuner ★ Five Transistor M.W. L.W. Trawler Band Regenerative Radio ★ Five Transistor V.H.F. Tuner ★ Three Transistor Code Practice Oscillator ★ Five Transistor Regenerative Short Wave Radio ★ Four Transistor and two Diodes M.W. L.W. Loudspeaker Radio ★ Seven Transistor M.W. L.W. Radio with Loudspeaker Push Pull output ★ One Transistor Home Broadcaster.

£14.99 + P & P £1.10


V.H.F. AIR CONVERTER KIT



Build this converter kit and receive the aircraft band by placing it by the side of a radio tuned to medium wave or the VHF band and operating as shown in the instructions supplied free with all parts. Uses a retractable chrome-plated telescopic aerial, gain control, V.H.F. tuning capacitor, transistor, etc. Size 5½" x 1½" x 3½". All parts including case and plans.

£4.95 + P & P and Ins. 60p

ELECTRONIC CONSTRUCTION KIT E.C.K. 2

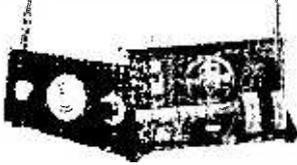


Self Contained Multi-Band V.H.F. Receiver Kit.

8 transistors and 3 diodes. Push pull output. 3 in. loudspeaker, gain control, 7 section chrome-plated telescopic aerial, V.H.F. tuning capacitor, resistors, capacitors, transistors, etc. Will receive T.V. sound, public service band, aircraft, V.H.F. local stations, etc. Operates from a 9 volt P.P.7 battery (not supplied with kit). Complete kit of parts

£7.95 + P & P and Ins. 90p


NEW MODEL R.K.1.

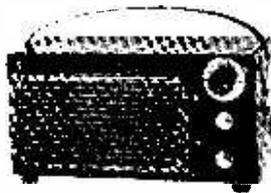

MultiBand A.M. Receiver. M.W.L.W. Trawler Band and Three Short Wave Bands. Seven Transistors and Four Diodes. Push Pull Output stage. 5" x 3" Loudspeaker. Internal Ferrite Rod Aerial. Kit includes all parts to build it up including Carrying Strap, Rubber Feet and ready-drilled Panels. Comprehensive Instruction Manual for stage by stage construction. Uses P.P.9 Nine Volt Battery.

£8.99 + P & P 90p

EDU KIT JUNIOR

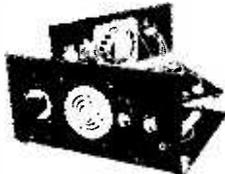


Completely Solderless Electronic Construction Kit. Build these projects without Soldering Iron or Solder

- ★ Crystal Radio Medium Wave Coverage—No Battery necessary
- ★ One Transistor Radio
- ★ 2 Transistor Regenerative Radio
- ★ 3 Transistor Earpiece Radio Medium Wave Coverage
- ★ 4 Transistor Medium Wave Loudspeaker Radio
- ★ Electronic Noise Generator
- ★ Electronic Metronome
- ★ 4 Transistor Push/Pull Amplifier

All parts including Loudspeaker, Earpiece, M.W. Ferrite Rod Aerial, Capacitors, Resistors, Transistors, etc. Complete kit of parts including construction plans.

£6.95 + P & P and Ins. 90p

NEW ROAMER TEN MODEL R.K.3.

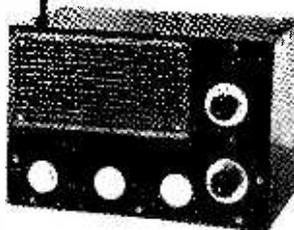

Multiband V.H.F. and A.M. Receiver. 13 Transistors and Six Diodes. Quality 6" x 3" Loudspeaker

With Multiband V.H.F. section covering Mobiles, Aircraft, T.V. Sound, Public Service Band, Local V.H.F. Stations, etc. and Multiband A.M. section with Aircapped Tuning Capacitor for easier and accurate tuning, covering M.W.1, M.W.2, L.W. Three Short Wave Bands S.W.1, S.W.2, S.W.3 and Trawler Band. Built-in Ferrite Rod Aerial for Medium Wave, Long Wave and Trawler Band, etc., Chrome-plated 7 section Telescopic Aerial, angled and rotatable for peak Short Wave and V.H.F. reception. Push-Pull output using 600mW Transistors. Gain. Wave-Change and Tone Controls. Plus two Slider Switches. Powered by P.P.9—9 volt Battery.

Complete kit of parts including carrying strap. Building Instructions and operating Manuals.

£14.79 + P & P £1.10


E.V.6 PLUS ONE



Build this exciting new design. Now with 7 Transistors and 4 diodes. MW/LW. Powered by 9V battery. Ferrite rod aerial, tuning condenser, volume control, and now with 3in. loudspeaker. Attractive case with red speaker grille. Size 9in. x 5½in. x 2½in. approx. All parts including Case and Plans.

Total Building Costs: **£6.95** + P & P and Ins. 90p

EDU-KIT MAJOR

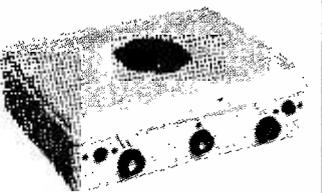

Completely solderless Electronic Construction Kit. Build fifteen projects including:—

- Signal Injector
- Transistor Tester NPN-PNP
- 7 Transistor Loudspeaker Radio MW/LW
- 5 Transistor Short Wave Radio.

Components include:

- 24 Resistors
 - 21 Capacitors
 - 10 Transistors
 - 5" x 3" Loudspeaker
 - Earpiece
 - Mica Base-board
 - 3 12-way Connectors
 - 2 Volume Controls
 - 2 Slider Switches
 - 1 Tuning Condenser
 - 3 Knobs
 - Ready Wound MW/LW/SW Coils
 - Ferrite Rod
 - 6½ yards of wire
 - 1 yard of sleeving, etc.
- Complete kit of parts including construction plans.

Total building costs:

£9.99 + P & P and Ins. £1.10

RADIO CONSTRUCTION KIT Q7



A compact small radio kit covering Medium Wave and Long Wave bands. Rugged Micanite construction and simple square design allows for easy carrying and positioning. Ideal for the Garage, Workroom, Kitchen, etc., has seven Transistors and four Diodes, quality Loudspeaker, ready wound Ferrite Rod Aerial and Carrying Strap. Size 4½" x 4½" x 4½". All parts and plans excluding 9v PP7 Battery.

£6.25 + P & P and Ins. 75p

POCKET FIVE



NOW WITH 2½" LOUDSPEAKER 3 Tuneable wavebands. M.W., L.W., and Trawler Band, 7 stages, 5 transistors and 2 diodes, supersensitive ferrite rod aerial, attractive black and gold case. Size 5½" x 1½" x 3½" approx. All Parts including Case and Plans.

Total Building Costs **£4.95** + P & P and Ins. 80p

To: RADIO EXCHANGE LTD

61A High Street, Bedford MK40 ISA

Tel.: 0234 52367

- Callers side entrance "Lavelis" Shop.
- Open 10-1, 2.30-4.30 Mon.-Fri. 9-12 Sat.

Reg. No. 788372

I enclose £.....for.....

Name

Address

PW479


all prices include VAT

BENTLEY ACOUSTIC CORPORATION LTD.

7a GLOUCESTER ROAD, LITTLEHAMPTON, SUSSEX
All prices inclusive of V.A.T. at 12½% Telephone 6743

OA2 1-20	6AM8A -70	6F24 1-00	7F8 2-00	12SR7 1-00	35Z4GT 70
OB2 -50	6A05 -85	6E25 1-00	7H7 1-00	13P8 2-00	35Z5GT 1-00
OC3 -50	6A08 -85	6E26 -50	7H7 1-00	14F1 1-00	
OZ4 -75	6A08 -50	6E28 1-00	7V7 2-00	1457 1-00	50B5 1-00
IA3 -60	6AR5 -105	6F32 1-00	7Y4 -80	18 2-00	50C5 -75
IA5GT -55	6AT7G 1-50	6GG6 1-00	7Z4 -80	19A55 -65	50CD6G 4-00
IA7GT 1-00	6AT7E -75	6GH8A -80	8D2 -50	19B6G6	
IB3GT -65	6AU6 -62	6GK5 -75	8D8 -55	1-00	50EH5 -85
IC2 1-00	6AV6 -75	6GK6 2-00	9BW6 1-00	19G6 6-00	50L6GT 1-00
ID3 1-00	6AWSA1-15	6GU7 1-00	9D7 1-00	19H1 4-00	66KU 1-00
IG6GT 1-00	6AX4 1-00	6H6GT 1-00	9U8 -45	19Y3 -50	72 -75
IHSGT 1-00	6B28 -75	6J5GT -80	10C2 1-00	20D1 -70	77 -75
IL4 1-00	6BA6 -65	6J6 -50	10C14 -65	20D4 2-50	85A2 1-75
ILD5 1-00	6BC8 1-00	6J7G -50	10D1 1-00	20F2 -85	85A3 2-00
LN5 1-00	6BE6 1-00	6J7M -75	10DE7 1-50	20L1 1-20	90C1 1-50
INSGT 1-00	6BGG 1-00	6JUSA 1-00	10F1 1-40	20L2 1-00	108C1 -50
IR5 1-50	6BH6 1-10	6K7G -50	10F9 1-00	20P3 1-00	150C2 1-20
IS4 -40	6BJ6 1-10	6K8G -50	10F18 -75	20P4 1-00	21SSG 1-00
IS5 -40	6BK7A 1-00	6K8GT -55	10L14 -55	20P5 1-50	807 1-10
IT4 -40	6BN8 1-50	6L1 2-50	10LD11 1-00	25A6G 1-50	956 -55
IU4 -70	6BQ5 -50	6L7 1-00	10LD12 6-00	25L6G 1-00	1625 2-50
IU5 -85	6BQ7A 1-40	6L12 1-50	10LP12 7-5	25Y3 1-00	1871 1-50
2GK5 1-00	6BR7 2-00	6L18 -70	10IP13 3-00	25Y6G 1-00	5687 2-00
2X2 1-00	6BR8 1-25	6L19 2-00	10IP14 3-00	25Z4G -75	50T2 1-20
3A4 -60	6BW6 3-75	6LD12 -50	12A6 1-00	25Z5 1-00	5763 3-65
3B7 1-00	6BW7 1-00	6LD20 1-00	12AC6 -80	25Z6G 1-00	6057 2-00
3D6 -40	6BX6 -45	6L21 1-00	12AC7 -80	2607 2-00	6060 2-00
3Q4 -80	6BY7 -50	6PL12 -60	12AE6 -85	30A5 1-50	6067 2-00
3Q5GT 1-00	6BZ6 1-50	6P15 -50	12AT6 -50	30C1 -80	6146 4-70
3S4 -65	6CA -50	6Q7G -75	12A77 -52	30C15 1-00	6211 2-00
3V4 1-00	6C6 -50	6Q7GT -75	12AU6 -30	30C17 1-00	6463 2-00
4CB6 1-00	6C9 2-00	6Q7M -75	12AU7 -62	30C18 2-25	6550A 6-75
4C8 1-00	6C10 1-00	6R7G 1-00	12AD6 -80	30D7 2-00	6060 2-00
5CG8 1-00	6CB6A -65	6S47 -75	12AX7 -72	30F12 1-20	7193 -60
5R4GY 1-20	6C12 -55	6SCTG1 -00	12BA6 -60	30L1 -40	7475 2-00
5T4 2-00	6CD6G 4-00	6S7 -80	12BE6 -85	30L15 1-00	9002 -75
5U4G 1-00	6CG8A -90	6SH7 -80	12BH7 -75	30L17 1-00	9006 -75
5V4G 1-00	6CL6 -75	6S7 -80	12E1 3-50	30P4MR 1-50	A3042 6-00
5Y3GT -65	6CL8A 1-00	6S7G 1-00	12J5GT -45	1-50	ACPEN2 1-00
5Z3 1-50	6CM7 1-00	6SK7GT -70	12J7GT -75	30P12 1-00	ACPEN1 1-50
5Z4G 1-50	6CS6 -75	6L7G 2-00	12K5 -1-50	30P19 1-00	ACPEN2 -50
5Z4GT 1-00	6CJ5 1-00	6SN7G 2-00	12K7GT -60	30P4 1-00	DD -50
6/30L2 1-00	6D3 1-00	6S07 -80	12K8 -75	30P16 -50	ACPEN1 1-00
6A8G 1-40	6DE7 1-00	6U4GT 1-00	12Q7 -60	30P18 -65	AC/P4 1-50
6AC7 -85	6DT6A -85	6U7G 1-00	12SA7 -75	30P1 2-20	AC/P4 -50
6AG5 -65	6EW6 -85	6U8 -55	12S7 -55	30P12 1-65	AC/P4 1-50
6AG7 -80	6ES 2-00	6V6G -60	12SG7 -50	30P13 1-30	ACTH11-50
6AH6 1-00	6F1 1-00	6X4 -95	12SH7 -1-50	30P14 1-50	ALGO 2-00
6AJ5 -70	6F6G -80	6XS7G -60	12SI7 -60	30P15 1-30	ARP3 -60
6AJ8 -55	6F7 -75	6Y6G 1-00	12S7 -60	35A3 1-00	ATP4 -50
6AK5 -55	6F14 1-00	6Y7G 2-00	12SN7G -60	35C1 -80	AZ1 1-00
6AK6 1-50	6F15 -85	7A7 1-50	2-00	35D5 1-00	AZ31 1-10
6AK8 -50	6F16 1-00	7B6 1-50	12SQ7 -80	35L6GT -85	AZ41 -60
6AL5 -40	6F18 1-00	7B7 1-00	12SQ7GT -80	35W4 -60	B36 2-00
6AM6 -70	6F23 1-00	7D6 2-00	-80	35Z3 1-00	B719 -50

B729 1-00	EB34 -50	EF92 -75	HL42DD 1-00	PEN45 1-50	UF41 1-10	AA120 -18	BF180 -35
BL63 2-00	EB91 -40	EF93 -65	HN309 2-00	PEN45DD 1-50	UF80 -50	AA129 -18	BF181 -47
CL33 2-00	EB41 1-50	EF94 -62	HVR2 1-00	PEN46 1-00	UF85 -50	AAZ13 -21	BF185 -47
CV6 -60	EB80 1-00	EF95 -55	HVR2A 1-00	PEN453DD 1-00	UF89 -55	AC107 -18	BF550 -26
CV63 1-00	EB90 -75	EF97 -90	KT2 1-00	PEN453DD 1-00	UL41 1-00	AC113 -30	BF551 -23
CV988 -25	EB91 -75	EF98 -90	KT7 1-00	PEN453DD 1-00	UL84 -90	AC126 1-14	BF552 -23
CY1C 1-00	EBF80 1-00	EF183 -55	KT71 1-00	PEN453DD 1-00	UL84 -90	AC127 -20	BY100 -21
CY31 1-00	EBF83 1-00	EF184 -55	KT82 1-00	PEN453DD 1-00	UL84 -90	AC128 -30	BY114 -21
D1 -50	EBF89 -50	EF804 6-25	KT41 1-50	PFL2001-35	UL91 1-00	AC132 -23	BY126 -18
D63 -50	EBL21 2-00	EH90 -75	KT44 2-50	PL33 1-50	UL12 -50	AC154 -30	BY127 -21
DAC32 1-00	EC52 1-00	EK90 -70	KT63 -80	PL36 1-00	UY41 -75	AC156 -30	BY128 -21
DAP 1-00	EC53 1-50	EL32 1-00	KT66 3-50	PL81 -65	UY42 -75	AC157 -30	BY129 -30
DAP6 1-00	EC54 1-50	EL34 2-50	KT78 3-00	PL81A -75	UY85 -70	AC158 -30	BY130 -30
DC90 1-00	EC86 1-00	EL37 3-00	KT81 2-50	PL82 -50	U10 1-50	AC166 -30	BY131 -30
DD4 1-00	EC88 1-00	EL41 1-00	KT88 6-75	PL83 -50	U114/14 1-50	AC168 -44	BY132 -30
DF33 1-00	EC90 -50	EL81 1-00	L63 -80	PL84 -65	U18 2-50	AC176 -64	FSY11A -26
DP91 -40	EC92 1-00	EL83 1-00	LN119 -75	PL95 1-00	U19 4-00	AC177 -32	FSY41A -26
DP92 -30	EC97 1-00	EL84 -50	LN309 2-00	PL504/500	U25 1-00	AC178 -35	OA9 -14
DL96 1-00	EC32 1-00	EL86 -80	LZ319 -80	PL505 3-10	U33 2-00	AC179 -35	OA9 -14
DH63 -75	EC33 2-00	EL90 -85	M8136 2-00	PL508 1-85	U35 2-00	AC180 -35	OA9 -14
DH76 -50	EC35 2-00	EL95 -95	M8162 2-00	PL509 3-10	U37 2-00	AC181 -35	OA9 -14
DH77 -75	EC40 1-25	EL360 2-50	M8195 3-00	PL519 3-75	U81 1-00	AC182 -35	OA9 -14
DH81 1-50	EC81 -52	EL506 2-50	MHL4 1-50	PT4D 1-50	U91 -50	AD150 -50	OA9 -14
DK32 1-00	EC82 -62	EL509 2-50	MHL6 1-00	PY33/2	U92 -50	AD161 -53	OA9 -14
DK40 1-50	EC83 -62	EM80 1-00	MHL6 1-00	1-50	U93 -50	AD161 -53	OA9 -14
DK41 1-00	EC84 -50	EM81 1-00	MHL6 1-00	1-50	U93 -50	AD161 -53	OA9 -14
DK92 1-00	EC85 -50	EM83 1-00	MX40 1-00	PY80 -50	U403 1-50	AF115 30	OA9 -14
DL33 1-00	EC86 2-00	EM84 1-00	N150 1-00	PY81 -60	U404 -75	AF117 -23	OA9 -14
DK96 1-00	EC88 -72	EM85 1-00	N308 1-50	PY82 -50	U801 1-00	AF121 -35	OA9 -14
DL63 1-00	EC91 -50	EM87 1-45	N709 -50	PY83 -60	U4020 1-00	AF124 -36	OA9 -14
DL82 1-50	EC93 1-00	EMM803	P61 -75	PY88 -12	V223 1-00	AF180 -36	OC44 -35
DL92 -65	EC94 1-00	EMM803	P61 -75	PY88 -12	V223 1-00	AF180 -36	OC44 -35
DL94 1-00	EC97 2-80	EY51 -80	PC86 -80	PC86 -80	PC86 -80	PC86 -80	PC86 -80
DL96 1-00	ECF80 -65	EY81 1-50	PC88 -80	PC88 -80	PC88 -80	PC88 -80	PC88 -80
DM70 1-50	ECF82 -55	EY83 1-50	PC92 -85	PC92 -85	PC92 -85	PC92 -85	PC92 -85
DM71 1-75	ECF86 -80	EY87 -50	PC95 1-00	PC95 1-00	PC95 1-00	PC95 1-00	PC95 1-00
DM72 1-50	ECF89 -80	EY91 -80	PC97 -80	PC97 -80	PC97 -80	PC97 -80	PC97 -80
DY5 2-00	EC42 1-00	EY91 1-00	PC900 -75	PC900 -75	PC900 -75	PC900 -75	PC900 -75
DY87/6 -55	EC81 -55	EY90 1-45	PC884 -40	PC884 -40	PC884 -40	PC884 -40	PC884 -40
DY802 -55	EC83 -50	EZ35 -60	PC88 -55	PC88 -55	PC88 -55	PC88 -55	PC88 -55
DY80C 4-75	EC84 -80	EZ40 1-00	PC88 -55	PC88 -55	PC88 -55	PC88 -55	PC88 -55
E80CF 6-00	ECL80 -60	EZ41 1-00	PC88 -55	PC88 -55	PC88 -55	PC88 -55	PC88 -55
E80F 5-50	ECL82 1-00	EZ80 -50	PC88 -55	PC88 -55	PC88 -55	PC88 -55	PC88 -55
E81CC 2-00	ECL83 1-50	EZ81 -50	PC88 -55	PC88 -55	PC88 -55	PC88 -55	PC88 -55
E82C 2-00	ECL85 1-00	EZ90 -95	PC88 -55	PC88 -55	PC88 -55	PC88 -55	PC88 -55
E83F 3-50	ECL86 -70	FC4 1-50	PC88 -55	PC88 -55	PC88 -55	PC88 -55	PC88 -55
E88CC 1-20	ECL88 1-00	GY501 1-40	PC88 -55	PC88 -55	PC88 -55	PC88 -55	PC88 -55
E92CC 4-50	ECL89 1-00	GY501 1-40	PC88 -55	PC88 -55	PC88 -55	PC88 -55	PC88 -55
E93CC 1-00	ECL90 1-00	GY501 1-40	PC88 -55	PC88 -55	PC88 -55	PC88 -55	PC88 -55
E98CC 1-00	ECL91 1-00	GY501 1-40	PC88 -55	PC88 -55	PC88 -55	PC88 -55	PC88 -55
E98CC 1-00	ECL92 1-00	GY501 1-40	PC88 -55	PC88 -55	PC88 -55	PC88 -55	PC88 -55
E98CC 1-00	ECL93 1-00	GY501 1-40	PC88 -55	PC88 -55	PC88 -55	PC88 -55	PC88 -55
E98CC 1-00	ECL94 1-00	GY501 1-40	PC88 -55	PC88 -55	PC88 -55	PC88 -55	PC88 -55
E98CC 1-00	ECL95 1-00	GY501 1-40	PC88 -55	PC88 -55	PC88 -55	PC88 -55	PC88 -55
E98CC 1-00	ECL96 1-00	GY501 1-40	PC88 -55	PC88 -55	PC88 -55	PC88 -55	PC88 -55
E98CC 1-00	ECL97 1-00	GY501 1-40	PC88 -55	PC88 -55	PC88 -55	PC88 -55	PC88 -55
E98CC 1-00	ECL98 1-00	GY501 1-40	PC88 -55	PC88 -55	PC88 -55	PC88 -55	PC88 -55
E98CC 1-00	ECL99 1-00	GY501 1-40	PC88 -55	PC88 -55	PC88 -55	PC88 -55	PC88 -55
E98CC 1-00	ECL100 1-00	GY501 1-40	PC88 -55	PC88 -55	PC88 -55	PC88 -55	PC88 -55
E98CC 1-00	ECL101 1-00	GY501 1-40	PC88 -55	PC88 -55	PC88 -55	PC88 -55	PC88 -55
E98CC 1-00	ECL102 1-00	GY501 1-40	PC88 -55	PC88 -55	PC88 -55	PC88 -55	PC88 -55
E98CC 1-00	ECL103 1-00	GY501 1-40	PC88 -55	PC88 -55	PC88 -55	PC88 -55	PC88 -55
E98CC 1-00	ECL104 1-00	GY501 1-40	PC88 -55	PC88 -55	PC88 -55	PC88 -55	PC88 -55
E98CC 1-00	ECL105 1-00	GY501 1-40	PC88 -55	PC88 -55	PC88 -55	PC88 -55	PC88 -55
E98CC 1-00	ECL106 1-00	GY501 1-40	PC88 -55	PC88 -55	PC88 -55	PC88 -55	PC88 -55
E98CC 1-00	ECL107 1-00	GY501 1-40	PC88 -55	PC88 -55	PC88 -55		

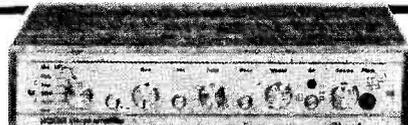

20 x 20 WATT STEREO AMPLIFIER

Viscount IV unit in teak simulate cabinet. Silver finish rotary controls and pushbuttons with matching fascia, red mains indicator and stereo jack socket. Functions switch for mic, magnetic and crystal pickups, tape tuner and auxiliary. Rear panel features two mains outlets DIN speaker and input sockets plus fuse 20x20 watts RMS 40x40 watts peak. For use with 8 to 15 ohm speakers.

£29.90
£2.50 p&p

SPECIAL OFFER

FOR PERSONAL SHOPPERS ONLY

FREE 4 dimensional stereo sound adaptor, when purchasing the 20x20 Viscount amplifier

30x30 WATT AMPLIFIER IN KIT FORM

For the experienced constructor complete in every detail, same facilities as Viscount IV, but with 30x30 output 60x60 watts peak. For use with 4, 15 ohms speakers.

£29.00 £2.50



SPECIAL OFFER

30x30 WATT AMPLIFIER IN KIT WITH SPEAKERS

2 Goodman compact 12" bass woofers with cropped size 14,000 Gauss magnet. 30 watt RMS handling + 3/4" approx. tweeters and crossovers.

£49.00

+ p&p £4.00

BUILT AND READY TO PLAY

39.00

+ p&p £2.50

30x30 Viscount. Available fully built and tested.

EMI SPEAKER BARGAIN

Stereo pair 350 kit. System consists of 13" x 8" approx. woofer with rolled surround, 2 1/2" approx. Audax tweeter, crossover components and circuit diagram. Frequency response 20 Hz to 20 KHz. Power handling 15 watts RMS. 20 watts max. 8 ohm impedance.

£14.95

Per stereo pair + £3.40 p&p



BSR P200


Belt drive chassis turntable unit semi automatic, cueing device.

£24.95

p&p £2.55

A.D.C. QLM 30 Mk III Magnetic Cartridge to suit.

£7.75

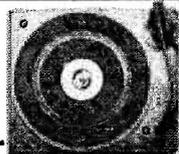

BSR Manual single play record deck with auto return and cueing lever. Fitted with stereo ceramic cartridge 2 speeds with 45 r.p.m. spindle adaptor ideally suited from home or disco use.

£10.95 p&p £2.55


GARRARD DECK MODEL CC 10A

Record changer with cueing device fitted with stereo ceramic cartridge ready to fit into your own plinth.

£7.95

p&p £2.00


Size 12" x 8 1/2"

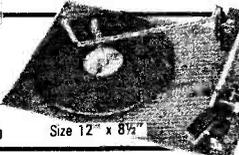

SANYO Nic/cad. battery, with mains charger equivalent in size and replaces 4 SP11 type batts. Size 3 1/4" x 1 1/4" x 2" approx.

£7.50

p&p £1.50p

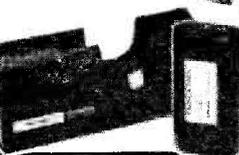

AM/FM STEREO TUNER AMPLIFIER CHASSIS COMPLETE WITH DECODER

Ready built. Designed in a slim form for compact, modern installation. Rotary Controls Vol On/Off, Bass, Treble, Balance. Push Buttons for Gram, Tape, VHF, MW, LW

Power Output 5 watts per channel Sine at 2% THD into 15 Ohm 7 watts speech and music.

Tape Sensitivity Playback 400mV/30K OHM for max output Record 200mV/50K output available from 25KHz. (150mV/100K) deviation

FM signal Frequency Range (Audio) 50Hz to 17KHz within ± 13B

Radio FM sensitivity for 3dB below limiting better than 10 uV

AM sensitivity for 20dB S/N MW 350 uV/Metre LW 1mV/Metre

Size approx length 16" x height 2 3/4" x depth 4 1/4"

240 Volts AC Complete with tuning dial Circuit diagram.

£19.95 p&p £2.25

Mullard

AUDIO MODULES IN BARGAIN PACKS

CURRENT CATALOGUE


PRICE & AT OVER **25** PER PACK

SEE OUR PRICES

1 PACK 1. 2 x LP1173 10w. RMS output power audio amp modules, + 1 LP1182/2 Stereo pre amp for ceramic and auxiliary input. OUR PRICE **£4.95** p+p £1.00

2 PACK 2. 2 x LP1173 10w. RMS output power audio amp modules + 1 LP1184/2 Stereo pre amp for magnetic, ceramic and auxiliary inputs. **illus.** OUR PRICE **£7.45** p+p £1.00

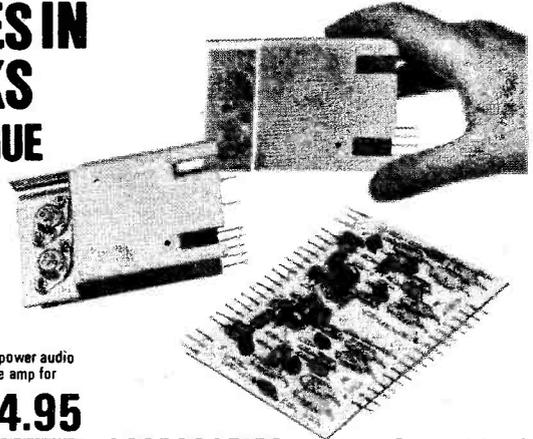ACCESSORIES ARE ONLY AVAILABLE TO THOSE CUSTOMERS WHEN BUYING OUR BARGAIN PACKS.



ACCESSORIES

Suitable power supply parts including mains transformer, rectifier, smoothing capacitors

Recommended set of rotary stereo controls comprising BASS, TREBLE, VOLUME and BALANCE.


£1.00 p+p £1.95

p+p 50p **95p**

10 + 10 AMPLIFIER KIT

An opportunity to buy a 10 watts per channel stereo amplifier kit which is suitable for use with a ceramic cartridge. The amplifier utilises proven Mullard modules and is available at a very competitive price. The amplifier kit comes complete with instructions and includes: a Mullard LP1183 stereo preamplifier module, two LP1173 power amplifiers with integral heatsinks, a power supply, Zobel networks, front and back mounting panels, a finished fascia panel, all control potentiometers (bass, treble, volume and balance), switches, input, output and headphone sockets, wire, and an easily assembled wrap around cabinet to house the finished unit.

p&p £2.05 **£11.95**

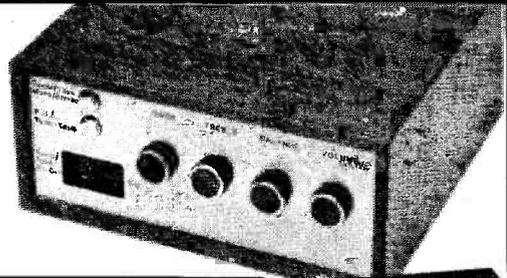

BARGAINS FOR PERSONAL SHOPPERS

LED 5 function men's digital watch stainless steel finish

£5.95

LCD 5 function men's digital watch stainless steel finish

£6.95

LCD 8 Function CHRONOGRAPH men's digital watch, stainless steel finish

£12.95

POCKET CALCULATOR. With LED display, memory and percentage key.

£2.95

AM/FM DIGITAL CLOCK

RADIO Accurate 4 Digit Electronic Clock with 1/2" LED display. Buzzer and snooze timer.

£11.95



125 Watt Power Amp Module

£13.95

Mains power supply for above unit.

£3.50

MULLARD Built power supply

£1.50

DECCA 20w Stereo speaker kit comprising 2 8" approx. bass units + 2 3/4" approx. tweeter inc. crossovers

£20.00

VIDEOMASTER Super Score TV Game with pistol mains operation

£14.95

PORTABLE RADIO/CASSETTE RECORDER, AM/FM with clock. LW, MW, SW, VHF mains/battery operation.

£41.95

VIDEOMASTER COLOUR SHOT TV GAME

Choice of three games—Football, Tennis and Squash. Ready to play—one or two players. MAINS OPERATED.

OPPORTUNITY AT **£9.95 ONLY**



50 WATT MONO DISCO AMP

£29.95

P&P £2.50

Size approx. 13 1/2" x 5 1/4" x 6 1/4"

50 watts rms. 100 watts peak output. Big features include two disc inputs, both for ceramic cartridges, tape input and microphone input. Level mixing controls fitted with integral push-pull switches. Independent bass and treble controls and master volume.

SPECIAL OFFER. The above 50 watt amp plus 4 Goodmans Type 8P, 8" speakers. Package price **£45.00 + £4.00 P&P.**



70 & 100 WATT MONO DISCO AMP

Size approx. 14" x 4" x 10 1/4"

Brushed aluminium fascia and rotary controls.

Five vertical slide controls, master volume, tape level, mic level, deck level, PLUS INTER DECK FADER for perfect graduated change from record deck No. 1 to No. 2, or vice versa. Pre fade level control (PFL) lets YOU hear next disc before fading it in. VU meter monitors output level.

Output 100 watts RMS 200 watts peak.



70 watt

140 watt peak

p&p £4.00

100 watt

£57

£65

DUO II SPEAKERS


Attractive teak finish, modern design, incorporating 2 speaker units—8"

approx. woofer and 2 1/2" approx. tweeter. 45 to 1800 Hz. Impedance 8 ohms. Power 15 watts RMS.

20 watts max. Per stereo pair

£17.00

£6.50 p&p

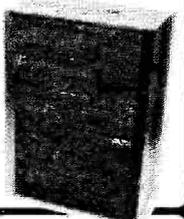

FOR PERSONAL SHOPPERS ONLY

TANNOY 15" Lancaster corner cabinets, traditional design.

£20.95 each

NOTE DUE TO INDUSTRIAL UNREST, PLEASE ALLOW EXTRA TIME FOR YOUR ORDER TO REACH YOU.



323 EDGWARE ROAD, LONDON W2
21C HIGH STREET, ACTON W3 6NG

ACTON: Mail Order only. No callers

ALL PRICES INCLUDE VAT AT 12 1/2%

All items subject to availability. Price correct at 30 January and subject to change without notice.

Personal Shoppers EDGWARE ROAD LONDON W2 Tel: 01-723 8432. 9.30am-5.30pm. Half day Thursday.

ACTON: Mail Order only. No callers GOODS NOT DESPATCHED OUTSIDE UK



Handy size reels and dispensers

of the world's finest cored solder to do a professional job at home



SAVBIT

handy solder dispenser
Contains 2.3 metres approx. of 1.22mm Ersin Multicore Savbit Solder. Savbit increases life of copper bits by 10 times.
Size 5 58p inc. VAT

For soldering fine joints

Two more dispensers to simplify those smaller jobs. PC115 provides 6.4 metres approx. of 0.71mm solder for fine wires, small components and printed circuits.
69p inc. VAT

Or size 19A for kit wiring of radio and TV repairs. 2.1 metres approx. of 1.22 mm solder.
Size 19A 63p inc. VAT



Ersin Multicore Solder contains 5 cores of non-corrosive flux that instantly cleans heavily oxidised surfaces and makes fast, reliable soldering easy. No extra flux is required.

handy size reels of

SAVBIT, 40/60, 60/40 and ALU-SOL solder alloys

These latest Multicore solder reels are ideal for the toolbox. Popular specifications cover all general and electrical applications, plus a major advance in soldering aluminium. Ask for a free copy of 'Hintson Soldering' containing clear instructions to make every job easy.

Ref.	Alloy	Diam. (mm)	Length metres approx.	Use	Price inc. VAT
Size 3	40/60 Tin/Lead	1.6	10.0	For economical general purpose repairs and electrical joints.	£2.16
Size 4	ALU-SOL	1.6	8.5	For aluminium repairs. Also solders aluminium to copper, brass etc.	£2.46
Size 10	60/40 Tin/Lead	0.7	39.6	For fine wires, small components and printed circuits.	£2.38
Size 12	SAVBIT	1.2	13.7	For radio, TV and similar work. Increases copper-bit life tenfold.	£2.29

See U.K. Sales Concessionaires
Bib Hi-Fi Accessories Limited.
Kelsey House, Wood Lane End
Hemel Hempstead, Herts. HP2 4RQ

Prices shown are recommended retail inc. VAT.
From electrical and hardware shops. Inflationary and other factors may cause prices to change without notice.

SOLDERING FLUX PASTES

'ERSIN' A non-corrosive, rosin based flux for general and electrical soldering in conjunction with 'Ersin' Multicore solders.
Ref RF10 48p inc. VAT

'ARAX' For general metal joining in conjunction with 'Arax' Multicore solders.
Ref AF14 48p inc. VAT

BIB WIRE STRIPPER and CUTTER

Fitted with unique 8-gauge selector and handle locking device. Sprung for automatic opening. Strips flex and cable in seconds.
Model 8B 97p inc. VAT
Pat. No. 144913

EMERGENCY SOLDER

Self-fluxing, tin/lead solder tape that melts with a match. For electrical and non-electrical applications.
Size ES36 39p inc. VAT

MULTICORE DESOLDERING WICK

Absorbs solder instantly from tags, printed circuits, etc. Only needs 40-50 watt soldering iron. Quick and easy to use.
Non-corrosive. Size AB10 97p inc. VAT

ECONOPAK

A reel of 1.2mm 'Ersin' Multicore solder for general electrical use.
Size 13A £2.59 inc. VAT

A reel of 3mm 'Arax' Multicore solder for general non electrical use.
Size 16A £2.59 inc. VAT

TTLS BY TEXAS				LINEAR I.C.s				TRANSISTORS				DIODES									
7400	13p	7497	130p	74221	160p	74LS192	140p	74C157	250p	LMC1496	100p	AC12/7/8	20p	BFY51/2	22p	TIP42A	70p	*2N3866	90p	*BY127	12p
7401	14p	74100	130p	74251	140p	74LS193	140p	74C160	155p	*MC1496	100p	AD149	70p	BFY56	33p	TIP42C	82p	*2N3903/4	18p	*OA47	5p
7402	14p	74104	65p	74259	250p	74LS195	140p	74C161	155p	*AY1-1313	680p	AD161/2	45p	BFV90	90p	TIP295	78p	*2N4036	65p	*OA15	15p
7403	14p	74105	65p	74265	90p	74LS196	120p	74C162	155p	*AY1-1315	212p	BC107/8	12p	BRV39	45p	TIP305	70p	*2N4058/9	12p	*OA85	15p
7404	17p	74107	34p	74273	140p	74LS240	175p	74C164	120p	*AY5-1317	636p	BC109	11p	BSX19/20	20p	*TIS43	34p	*2N4060	12p	*OA90	9p
7405	18p	74109	65p	74283	190p	74LS241	175p	74C173	120p	*AY5-1320	320p	BC147/8	9p	*BU105	190p	*TIS93	30p	*2N4061/2	18p	*OA91	9p
7406	32p	74110	55p	74284	400p	74LS242	175p	74C174	160p	*CA5019	80p	*BC159	10p	*BU108	250p	*TIS99	30p	*2N4123/4	22p	*OA95	9p
7407	32p	74111	70p	74285	400p	74LS243	175p	74C175	210p	*CA5046	70p	*BC159	10p	*BU205	250p	*TIS99	30p	*2N4283	20p	*OA99	9p
7408	19p	74116	200p	74290	150p	74LS244	175p	74C192	150p	*CA3048	225p	*BC172	12p	*BU205	250p	*TIS99	30p	*2N4401/3	27p	*OA99	9p
7409	19p	74118	150p	74293	150p	74LS245	175p	74C193	150p	*CA3080E	72p	*BC177/8	12p	*BU205	250p	*TIS99	30p	*2N4402	10p	*OA99	9p
7410	15p	74119	210p	74298	200p	74LS257	120p	74C194	220p	*CA3080E	72p	*BC179	10p	*BU306	145p	*TIS99	30p	*2N4403/3	27p	*OA99	9p
7411	24p	74120	210p	74300	200p	74LS258	175p	74C195	110p	*CA3090A	375p	*BC179	10p	*BU306	145p	*TIS99	30p	*2N4427	90p	*OA99	9p
7412	20p	74121	28p	74305	150p	74LS259	249p	74C221	175p	*CA3090A	375p	*BC182/3	10p	*BU306	145p	*TIS99	30p	*2N4427	90p	*OA99	9p
7413	30p	74122	48p	74366	150p	74LS298	249p	4000 SERIES		CA3130S	100p	*BC182/3	10p	*BU306	145p	*TIS99	30p	*2N4427	90p	*OA99	9p
7414	60p	74123	55p	74367	150p	74LS373	200p	CA3140E	70p	CA3140E	70p	*BC182/3	10p	*BU306	145p	*TIS99	30p	*2N4427	90p	*OA99	9p
7415	27p	74125	55p	74368	150p	74LS374	195p	CA3160E	75p	CA3160E	75p	*BC182/3	10p	*BU306	145p	*TIS99	30p	*2N4427	90p	*OA99	9p
7416	27p	74126	60p	74390	200p	81LS95	120p	CA3160E	75p	CA3160E	75p	*BC182/3	10p	*BU306	145p	*TIS99	30p	*2N4427	90p	*OA99	9p
7417	27p	74128	60p	74390	200p	81LS96	160p	CA3160E	75p	CA3160E	75p	*BC182/3	10p	*BU306	145p	*TIS99	30p	*2N4427	90p	*OA99	9p
7418	27p	74129	75p	74393	200p	81LS97	120p	CA3160E	75p	CA3160E	75p	*BC182/3	10p	*BU306	145p	*TIS99	30p	*2N4427	90p	*OA99	9p
7419	40p	74132	75p	74490	225p	81LS98	160p	CA3160E	75p	CA3160E	75p	*BC182/3	10p	*BU306	145p	*TIS99	30p	*2N4427	90p	*OA99	9p
7422	22p	74136	75p	74LS SERIES		81LS98	160p	CA3160E	75p	CA3160E	75p	*BC182/3	10p	*BU306	145p	*TIS99	30p	*2N4427	90p	*OA99	9p
7423	34p	74141	70p	74LS300	18p	81LS98	160p	CA3160E	75p	CA3160E	75p	*BC182/3	10p	*BU306	145p	*TIS99	30p	*2N4427	90p	*OA99	9p
7425	30p	74142	200p	74LS301	18p	81LS98	160p	CA3160E	75p	CA3160E	75p	*BC182/3	10p	*BU306	145p	*TIS99	30p	*2N4427	90p	*OA99	9p
7426	40p	74145	80p	74LS302	18p	81LS98	160p	CA3160E	75p	CA3160E	75p	*BC182/3	10p	*BU306	145p	*TIS99	30p	*2N4427	90p	*OA99	9p
7427	34p	74147	190p	74LS304	20p	81LS98	160p	CA3160E	75p	CA3160E	75p	*BC182/3	10p	*BU306	145p	*TIS99	30p	*2N4427	90p	*OA99	9p
7428	36p	74148	150p	74LS308	22p	81LS98	160p	CA3160E	75p	CA3160E	75p	*BC182/3	10p	*BU306	145p	*TIS99	30p	*2N4427	90p	*OA99	9p
7430	17p	74150	100p	74LS310	20p	81LS98	160p	CA3160E	75p	CA3160E	75p	*BC182/3	10p	*BU306	145p	*TIS99	30p	*2N4427	90p	*OA99	9p
7432	30p	74151A	70p	74LS313	30p	81LS98	160p	CA3160E	75p	CA3160E	75p	*BC182/3	10p	*BU306	145p	*TIS99	30p	*2N4427	90p	*OA99	9p
7433	40p	74153	70p	74LS314	30p	81LS98	160p	CA3160E	75p	CA3160E	75p	*BC182/3	10p	*BU306	145p	*TIS99	30p	*2N4427	90p	*OA99	9p
7437	35p	74154	80p	74LS320	22p	81LS98	160p	CA3160E	75p	CA3160E	75p	*BC182/3	10p	*BU306	145p	*TIS99	30p	*2N4427	90p	*OA99	9p
7438	35p	74155	90p	74LS322	28p	81LS98	160p	CA3160E	75p	CA3160E	75p	*BC182/3	10p	*BU306	145p	*TIS99	30p	*2N4427	90p	*OA99	9p
7440	17p	74156	90p	74LS327	38p	81LS98	160p	CA3160E	75p	CA3160E	75p	*BC182/3	10p	*BU306	145p	*TIS99	30p	*2N4427	90p	*OA99	9p
7441	70p	74157	70p	74LS330	22p	81LS98	160p	CA3160E	75p	CA3160E	75p	*BC182/3	10p	*BU306	145p	*TIS99	30p	*2N4427	90p	*OA99	9p
7442A	70p	74159	190p	74LS347	90p	81LS98	160p	CA3160E	75p	CA3160E	75p	*BC182/3	10p	*BU306	145p	*TIS99	30p	*2N4427	90p	*OA99	9p
7443	112p	74160	100p	74LS355	30p	81LS98	160p	CA3160E	75p	CA3160E	75p	*BC182/3	10p	*BU306	145p	*TIS99	30p	*2N4427	90p	*OA99	9p
7444	112p	74161	100p	74LS373	50p	81LS98	160p	CA3160E	75p	CA3160E	75p	*BC182/3	10p	*BU306	145p	*TIS99	30p	*2N4427	90p	*OA99	9p
7445	100p	74162	100p	74LS374	40p	81LS98	160p	CA3160E	75p	CA3160E	75p	*BC182/3	10p	*BU306	145p	*TIS99	30p	*2N4427	90p	*OA99	9p
7446A	83p	74163	100p	74LS375	50p	81LS98	160p	CA3160E	75p	CA3160E	75p	*BC182/3	10p	*BU306	145p	*TIS99	30p	*2N4427	90p	*OA99	9p
7447A	70p	74164	120p	74LS383	110p	81LS98	160p	CA3160E	75p	CA3160E	75p	*BC182/3	10p	*BU306	145p	*TIS99	30p	*2N4427	90p	*OA99	9p
7448	80p	74165	130p	74LS385	100p	81LS98	160p	CA3160E	75p	CA3160E	75p	*BC182/3	10p	*BU306	145p	*TIS99	30p	*2N4427	90p	*OA99	9p
7450	17p	74166	140p	74LS386	40p	81LS98	160p	CA3160E	75p	CA3160E	75p	*BC182/3	10p	*BU306	145p	*TIS99	30p	*2N4427	90p	*OA99	9p
7451	17p	74167	200p	74LS390	60p	81LS98	160p	CA3160E	75p	CA3160E	75p	*BC182/3	10p	*BU306	145p	*TIS99	30p	*2N4427	90p	*OA99	9p
7453	17p	74170	200p	74LS392	60p	81LS98	160p	CA3160E	75p	CA3160E	75p	*BC182/3	10p	*BU306	145p	*TIS99	30p	*2N4427	90p	*OA99	9p
7454	17p	74172	720p	74LS107	45p	81LS98	160p	CA3160E	75p	CA3160E	75p	*BC182/3	10p	*BU306	145p	*TIS99	30p	*2N4427	90p	*OA99	9p
7460	17p	74173	120p	74LS112	90p	81LS98	160p	CA3160E	75p	CA3160E	75p	*BC182/3	10p	*BU306	145p	*TIS99	30p	*2N4427	90p	*OA99	9p
7470	36p	74174	93p	74LS123	75p	81LS98	160p	CA3160E	75p	CA3160E	75p	*BC182/3	10p	*BU306	145p	*TIS99	30p	*2N4427	90p	*OA99	9p
7472	30p	74175	85p	74LS132	900p	81LS98	160p	CA3160E	75p	CA3160E	75p	*BC182/3	10p	*BU306	145p	*TIS99	30p	*2N4427	90p	*OA99	9p
7473	34p	74176	90p	74LS133	80p	81LS98</															

LOOK!

Here's how you master electronics.

... the practical way.

This new style course will enable anyone to have a real understanding by a modern, practical and visual method. No previous knowledge is required, no maths, and an absolute minimum of theory.

You learn the practical way in easy steps mastering all the essentials of your hobby or to further your career in electronics or as a self-employed electronics engineer.

All the training can be carried out in the comfort of your own home and at your own pace. A tutor is available to whom you can write, at any time, for advice or help during your work. A Certificate is given at the end of every course.

1. Build an oscilloscope.

As the first stage of your training, you actually build your own Cathode ray oscilloscope! This is no toy, but a test instrument that you will need not only for the course's practical experiments, but also later if you decide to develop your knowledge and enter the profession. It remains your property and represents a very large saving over buying a similar piece of essential equipment.

2. Read, draw and understand circuit diagrams.


In a short time you will be able to read and draw circuit diagrams, understand the very fundamentals of television, radio, computers and countless other electronic devices and their servicing procedures.

3. Carry out over 40 experiments on basic circuits.

We show you how to conduct experiments on a wide variety of different circuits and turn the information gained into a working knowledge of testing, servicing and maintaining all types of electronic equipment, radio, t.v. etc.

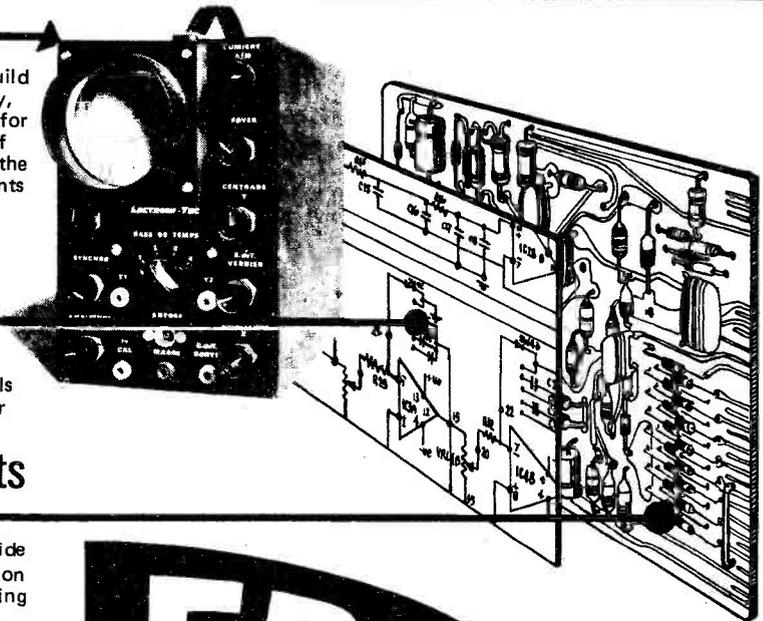4. Free Gift.

All students enrolling in our courses receive a free circuit board originating from a computer and containing many different components that can be used in experiments and provide an excellent example of current electronic practice.



FREE

Post now, without obligation, to:-

BRITISH NATIONAL RADIO & ELECTRONICS SCHOOL


P.O. Box 156, Jersey, Channel Islands.

NAME _____

ADDRESS _____

Block caps please

WB4/79

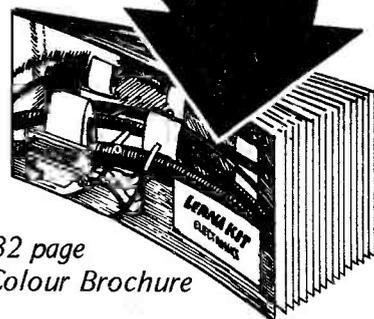

32 page
Colour Brochure

U.K. RETURN OF POST MAIL-ORDER SERVICE ALSO WORLD WIDE EXPORT SERVICE

R.C.S. LOUDSPEAKER BARGAINS

3 ohm. 6 x 4in. £1-50. 7 x 4in. £1-50. 8 x 5in. £2-50. 5in. £1-50.
6 1/2in. £1-80. 8in. £2-60. 10in. £3. 12in. £4.
8 ohm. 2 1/2in. £1-50. 3in. £1-50. 5in. £1-50. 10in. £3. 12in. £4.
16 ohm. 6 x 4in. £1-50. 7 x 4in. £1-50. 5in. £1-50. 8in. £2-60.
10in. £3. 12in. £4.

THE "INSTANT" BULK TAP ERASER


Suitable for cassettes, and all sizes of tape reels.
A.C. mains 200/249V.
Leaflet S.A.E. **£5-50** Post 50p



HEAD DEMAGNETISER PROBE £4-75

A.C. ELECTRIC MOTORS

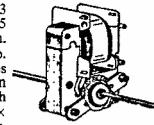2 Pole, 240V. 2 Amp Spindle — 1.43
x 0-212in. £1-75. 2 pole, 240V. 15
Amp. Double spindle — 1.75 x 0-16in.
Each £1-50. 2 Pole, 120V. 5 Amp
Spindle — 0.75 x 0-2in. Two in series
— 240V. 75p each. Brush Motor. From
a Food Mixer 240V. 3 Amp. High
Speed and Powerful. Spindle — 0.5 x
0-25in. £2-95 post 50p each



BLANK ALUMINIUM CHASSIS, 18 s.w.g. 2 1/2in. sides, 6 x 4in.
95p; 8 x 6in. £1-40; 10 x 7in. £1-55; 14 x 9in. £1-90; 16 x 6in.
£1-85; 12 x 3in. £1-20; 16 x 10in. £2-20; 12 x 8in. £1-70.

ALUMINIUM PANELS, 18 s.w.g. 6 x 4in. 24p; 8 x 6in. 38p; 10 x
7in. 54p; 12 x 5in. 46p; 12 x 8in. 70p; 16 x 6in. 70p; 14 x 9in. 94p;
12 x 12in. £1; 16 x 10in. £1-16.

ALUMINIUM ANGLE BRACKET 6 x 1/2 x 1/2in. 15p.

ALUMINIUM BOXES, MANY SIZES IN STOCK.

4 x 2 x 2in. 86p; 3 x 2 x 1in. 60p; 6 x 4 x 2in. £1; 8 x 6 x 3in.
£1-90; 12 x 5 x 3in. £2; 6 x 4 x 4in. £1-30.

DE LUXE BSR HI-FI AUTOCHANGER

Plays 12in. 10in. or 7in. records
Auto or Manual. A high quality
unit backed by BSR, reliability
with 12 months guarantee. A.C.
200/250V. Size 13 1/2 x 11 1/2in.
Above motor board 3 1/2in.
Below motor board 2 1/2in.



£17-50
All Post
£1.

With CERAMIC STEREO CARTRIDGE

BSR Budget Autochanger stereo ceramic cartridge. **£14-95**

Garrard 5300. Autochanger with ceramic cartridge. **£14-95**

Garrard Minichanger. Plays all size records.
Ceramic cartridge. Stereo. **£8-95**

BSR. P182. Snake arm, flared Aluminium Turntable
Stereo ceramic cartridge. Latest model. **£22-50**

BSR. Disco Single Player
Cueing Device 1 in. Turntable. Budget price **£19-50**

BAKER 150 WATT QUALITY TRANSISTOR MIXER/AMPLIFIER



Professional amplifier using advanced circuit design. Ideal for
disco, groups, P.A. or musical instruments. 4 inputs 4 way mixing.
Master treble, bases and volume controls. 3 speaker output sockets
to suit various combinations of speakers.
4-8-16 ohm. Slave output. Guaranteed. **£79** Carr. £1-50
Details S.A.E. A/C mains 120v. and 240v.

BAKER 50 Watt AMPLIFIER 2 inputs £59.

DRILL SPEED CONTROLLER/LIGHT DIMMER KIT. Easy to
build kit. Controls up to 480 watts A.C. mains. **£3-25**
Post 35p

STEREO PRE-AMP KIT. All parts to build this pre-amp. 3 inputs
for high medium or low gain per channel, with volume control
and P.C. Board. Can be ganged to make
multi-way stereo mixers. **£2-95**
Post 85p

R.C.S. SOUND TO LIGHT DISPLAY MK 2

Complete kit of parts with R.C.S. printed circuit. Three
channels. Up to 1,000 watts each. Will operate from 200MV
to 100 watts signal source. Suitable for home Hi-Fi
and all Disco Amplifiers. Cabinet extra £4. **£17**

200 Watt Rear Reflecting White Light Bubs. Ideal for Disco
Lights. Edison Screw 75p each or 6 for £4. or 12 for £7-50.

MAINS TRANSFORMERS

6 VOLT 1 AMP. £1-00 3 AMP. £1-95 9 VOLT 3 AMP. £2-75
12 VOLT 300 MA. £1-00 750 MA. £1-30 20 VOLT 2 AMP. £2-50
30 VOLT 5 AMP. AND 34 VOLT 2 AMP. C.T. £3-45
20 VOLT 1 AMP. £2-00 20-0-20 VOLT 1 AMP. £2-95
30 VOLT 1 1/2 AMP. £2-75 40 VOLT 2 AMP. £2-95 30V 2 AMP. £3
0-20-40-60 VOLT 1 AMP. £3-50 2 x 18 VOLT 6 AMP. £9.
Low Voltage 0-20-12V. 3 AMP. £3.

GENERAL PURPOSE LOW VOLTAGE. Voltages available at


2A, 3, 4, 5, 6, 8, 9, 10, 12, 15, 18, 24 and 30V **£5-80**
1A, 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60 **£5-80**
2A, 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60 **£8-50**
3A, 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60 **£11-00**
5A, 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60 **£14-50**

R.C.S. TEAK

COMPACT SPEAKERS

13 x 10 x 6in.
50 to 14,000 cps.
12 watts rms. 8 ohms

£19 pair Post £1-50

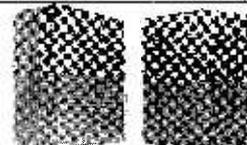

BAKER SPEAKERS "BIG SOUND"

Robustly constructed to stand up to long
periods of electronic power.
Useful response 30-13,000 cps.
Bass resonance 55 cps.

GROUP "35" **£14-00**

12in. 40 watt
4, 8 or 16 ohms.

GROUP "50/12" **£21-00**

12in. 60 watt professional
model. 4, 8 or 16 ohms.

Response 30 — 16,000 cps.
With aluminium presence dome.

GROUP "50/15" **£33-00**

15in. 75 watt
8 or 16 ohms.

Send for leaflets on Disco, P.A. and Group Gear.



E.M.I. 13 1/2 x 8in SPEAKER SALE!

With tweeter. And crossover.

10W. State 3 or 8 ohm.

£8-95

Post 45p

15W model **£10-50**

8 ohms. Post 65p

GOODMANS 20W Woofer

Size 12 x 10in. 4 ohms.

Rubber cone surround.

Hi-Fi Bass unit. **£9-95**

Post 65p

GOODMANS 20W Full Range

8in. 8 ohm Hi-Fi Twin Cone
Special unit **£5.**



R.C.S. MINI MODULE HI-FI KIT

15 x 8 1/2in 3-way Loudspeaker

System, EMI 5in, Bass 5in, Middle

5in, Tweeter with 3-way Crossover

and Ready Cut Baffle. Full assembly

instructions supplied. Response =

60 to 20 000cps 12 watt RMS.

8 ohm. £10-95 per kit. Two kits £20.

Postage 75p. One or two kits.

RADIO COMPONENT SPECIALISTS 337 WHITEHORSE ROAD, CROYDON

Minimum post 30p. Components List 20p. Phone orders. Access & Barclay VISA only. Open 9-6 Sat. 9-5 (Closed all day Wednesday) Tel. 01-684 1665

Catronics Offer!

2 Metre MONITOR RECEIVER

(as featured in this issue)

Complete kit for only **£52** less crystal

We also have available a multi-channel version of the PCB, allowing up to 7 crystals to be fitted. Kit less crystals—£53-60

Components also available separately:
PCB (single channel) £4-50; (multi-channel) £5-35;
SL6640. £3-85; Crystal filter, £24-85

40w 2m POWER AMPLIFIER

Kit for boosting output power of 2m transmitters including 'AVON'

A simple-to-build, easily-aligned Class C PA suitable for CW and FM amplification at 2 metres from a nominal 13-5V (-ve earth) supply (7amps at full power). T/R 'switching' is performed by diodes and 1/2 wave lines. A power input of 10 watts is required for the nominal 40 watts output power. £19-50 + 65p P & P.

NEW PLASTIC IC's from PLESSEY

New low cost version of the famous SL600 series communication ic's are now available. The plastic versions, designated SL1600 series, are in DIL8 or DIL14 packaging according to type.

	METAL	PLASTIC
R.F. Amplifier	SL1600	£2-05
R.F. Amplifier	SL1610	£2-65
R.F. Amplifier	SL1612	£2-05
Limiting Amp	SL1613	£2-65
VOGAD	SL1620	£4-00
AGC Generator	SL1621	£4-00
AF/VOGAD/Sidetone	SL1622	£9-85
AM/AGC/SSB	SL1623	£7-30
Multimode Det.	SL1624	£3-70
AF/VOGAD	SL1626	£2-75
A.F. Amplifier	SL1630	£1-82
Double Bal. Mod.	SL1640	£2-13
Receive Mixer	SL1641	£2-13

All prices INCLUDE VAT at current rates
Please note our minimum U.K. post and packing charge, except where indicated, is 30p. EXPORT ORDERS welcomed.

CATRONICS LTD., COMMUNICATIONS HOUSE
DEPT 984, 20 WALLINGTON SQUARE
WALLINGTON, SURREY SM6 8RG
Tel. 01-669 6700 (9 a.m. to 5.30 p.m. Sat. 1 p.m.)

Printed Circuit Coils

(Pat. App. For)

For the P.W. Sandbanks, only available from the designer of the detector. By reducing the coil capacitance, vast improvements in sensitivity to gold and silver can be achieved and only four resistors need to be changed for maximum sensitivity. A complete kit including the PC coil to fit the Ambit International moulding, the four resistors required, and instructions for only £2-50 are available from:

PLESSIS ELECTRONICS,
Castle House, Old Road, Leighton Buzzard, Beds.
Callers by appointment only

SINCLAIR PRODUCTS microvision tv uk model £89-95. PDM35 £27-25. mains adaptor £3-24. case £3-25. DM350 £67-80. DM450 £96-50. DM235 £49-45. rechargeable batts £7-50. mains adaptor £3-70. enterprise prog calculator £21-95. cambridge prog calculator £13-13. prog library £3-45. mains adaptor £3-20.

COMPONENTS send sae for full list. 1lb FeCl £1 05. dalo pen 73p. 60 sq in pcb 55p. laminate cutter 75p. small drill 20p. zn414 £1 05. pcb and extra parts for radio £3-85. case £1. IN4148 1-4p. IN4002 2-9p. 723 29p. 741 15p. NE555 23p. bc182b, bc183b, bc184b, bc212b, bc213b, bc214c 4-5p. plastic equiv bc107 4-8p. 1W 5% £12 resistors 10R to 10M 1p. 0-8p for 50-0 of one value. electrolytics 6v 5/12/5/10/22mf 5p. 100mf 6p. 1000mf 10p. 1500mf (PC) 3-4p. 10v 2mf 1-7p. 1000mf 5-1p. 2200mf 6p. polyesters 250v 0-15. 068. 1mf 1 1/2p. ceramics 50V E6 22pf to 47n 2p. polystyrenes 63v E12 10pf to 10n 3p. zeners 400mW E24 2v7 to 33v 7p.

TV GAMES send sae for data. AY-3-8500 + kit £8-95. rifle kit £4-95. AY-3-8600 + kit £12-50. stunt cycle chip + kit £10-90. racing cars chip + kit £17-90.

TRANSFORMERS 6-0-6v 100ma 74p. 1 1/2a £2-35. 6-3v 1 1/2a £1-89. 9-0-9v 75ma 74p. 1a £2-60. 12-0-12v 100ma 90p. 1a £2-49.

IC AUDIO AMPS with pcb. JC12 6W £1-60. JC20 10W £2-95. send sae for data.

BATTERY ELIMINATORS 3-way type 6/7 1/2v 300ma £2-95. 100ma radio type with press-studs 9v £3-35. 9+9v £4-50. stabilized type 3/6 7/8 9v 400ma £5-30. 12v car converters 3/4 6/7 9v 800ma £2-50.

BATTERY ELIMINATOR KITS send sae for data. 100ma radio types with press-studs 4 1/2v £1-40. 6v £1-40. 9v £1-40. 4 1/2+4 1/2v £1-80. 6+6v £1-80. 9+9v £1-80. stabilized 8-way types 3/4 6/7 9/12/15/18v 100ma £2-80. 1Amp £6-40. stabilized power kits 2-18v 100ma £3-60. 2-30v 1A £6-95. 2-30v 2a £10-95. 12v car converter 6/7 1/2v 1a £1-35.

T-DEC AND CSC BREADBOARDS s-dec £3-17. t-dec £4-02. U-deca £4-40. u-decb £6-73. 16 dil adaptor £2-14. exp300 £6-21. exp350 £3-40. exp650 £3-89. exp4b £2-48.

BI-PAK AUDIO MODULES s45 £23-51. AL60 £4-86. pa100 £15-58 spm80 £4-47. bmt80 £5-95. stereo 30 £20-12.

SWANLEY ELECTRONICS (Dept. PW)
32 Goldslee Rd., Swanley, Kent.
Post 30p extra. prices include VAT

+ BATTERY FLUORESCENT LIGHTING —

Type "A"
(12 in. or 21 in.)




Type "C"
(18 in.)



Type "B"
(21 in.)



Type "D"
(12 in.)

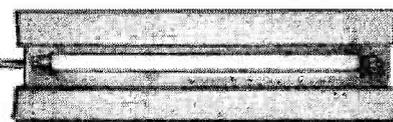

White Enamel cases as shown above, including lampholders. Type "A" or "B" £1.50. Case only, £1.00. Plastic Lampholders to suit 50p pair. Ceramic (adaptable) 40p pair. Tubes to fit (21 in.) £1.00. (These can only be supplied when cases are ordered due to risk of postal damage.) Case type "C" (18 in.) or Case type "D" (12 in.) including lampholders £1.25.

INVERTER TRANSFORMERS, special design for maximum efficiency £1.00 each
 Transistor, Heat Sink, Circuit board cut to size, Resistor, Capacitors etc £1.00 pack
 21 in. Fittings built and tested Type "A" With Tube £4.95
 12 in. ditto (Batten type) Type "A" ditto £4.95

THIS IS ABOUT HALF THE PRICE THAT A SIMILAR FITTING WOULD COST YOU ELSEWHERE!!!!
 WHY NOT DO AS MANY OTHERS ARE DOING, BUILD THEM AND SELL THEM TO YOUR CAMPING FRIENDS?

PRINTED CIRCUITS. WHY NOT MAKE YOUR OWN WITH FOTOLAK POSITIVE LIGHT SENSITIVE LACQUER

Now you can produce perfect printed circuits in minutes! Method: Spray cleaned board lightly with lacquer. When dry, place positive master of required circuit on now sensitised surface. Expose to daylight, develop and etch. Any number of exact copies can of course be made from one master. Widely used in industry for prototype work.

FOTOLAK Aerosol.....	£1.50	Pre-coated 1/16" Fibre-glass board:	£1.50	Plain Copper-clad Fibre-glass	Single-sided	Double
Developer.....	30	204mm x 114mm.....	£3.00	Approx. 3.18mm thick sq. ft.....	£1.25	£1.50
Ferric Chloride.....	40	204mm x 228mm.....	£8.00	Approx. 2.00mm thick sq. ft.....	£2.00	£2.25
Clear Acetate Sheet.....	12	408mm x 228mm.....	£8.00	Approx. 1.00mm thick sq. ft.....	£1.50	£1.75
Daylo Pens.....	98	467mm x 305mm.....	£9.00	Approx. .79mm thick sq. ft.....	£1.25	£1.50
				Single-sided Copper-clad paxolin.		
				Pack of 10 sheets each 245mm x 150mm.....	£2.50	

Giant packs of unused mixed components! Weight 4lbs., these contain an assortment of resistors (carbon and wire-wound), capacitors, electrolytic, paper, silver-mica, polyester and polystyrene; transistors, diodes, volume and pre-set controls and hosts of other 'bits and pieces'. No two bags are the same, but all contain a jolly good mixture of parts. Ideal for the odds and ends box!!! Per bag £3.00

Brand new printed circuit boards containing I.C.'s., transistors, diodes, resistors, capacitors etc. etc. It is quite impossible to list these so we are selling by weight at £1.00 per lb. This could include upwards of 100 integrated circuits! Send as many £1's as you wish, we will weigh as varied a parcel as possible and refund your change!

SPECIAL OFFER! Few only 3-channel (each 750 watts) Sound-to-light units. Fantastic value for money! Plug into any loudspeaker socket and create your own disco-type light show! Any mains lamps may be used ... £17.95

PLEASE NOTE: All lighting and printed-circuit materials plus 8% VAT. Other goods 12½%. No VAT on overseas orders. Postage INLAND 65p per order. Overseas include extra to cover. We will refund any excess paid. Any enquiries for further details MUST include stamped addressed envelope!

G. F. MILWARD (ELECTRONIC COMPONENTS LTD.), 369 Alum Rock Road, B'Ham B8 3DR. 021-327 2339

PROGRESSIVE RADIO

31 CHEAPSIDE, LIVERPOOL L2 2DY

MICROPHONES: EM506 Electret Dual Imp (50K + 600Ω) Imp Stick Mic, with Battery £11.00. Electret Model ECM105 Pencil Hand Mics (KΩ impedance, with standard jack £2.85. EM104 Tie Clip, Electret supplied with battery 1K imp £4.95. UD130 Dual Imp (50K + 600Ω) moving coil dynamic mic, cardioid response £8.25p.

BUZZERS, GPO open type 3-6V 30p. Large plastic domed type loud note 6 or 12 volts 50p. Solid state buzzers, miniature, 6-9-12-24 volt 15ma 75p each.

MAINS TRANSFORMERS, all 240V AC primary, postage shown in brackets per transformer: 6-0-6 100ma, 9-0-9 75ma 75p each (15p). 0-4-6-9 150ma no mounting bracket, 65p (20p). 12-0-12 100ma 95p (15p). 12V 500ma 95p (22p). 12V 2 amp £2.25 (45p). 12V 4 amp £2.75 (54p). 15-0-15V 1 amp £2.10 (45p). 30-0-30V 1 amp £2.75 (54p). 0-12-15-20-24-30V tapped at 2 amp £4.50 (54p). 20-0-20V 2 amp £3.50 (54p). 25V 1.5 amp £1.45 (45p). 18V 1.5 amp rectified £2.00 (45p). 35V 2 amp, 2-5V 2 amp Toroid £2.95 (45p). 20V 2.5 amp, £2.20 (54p). Murata MA401L 40KHz rec/send transducers £3.25 pair.

SMITHS TRANSISTORISED AUDIBLE WARNING DEVICE, 6-12V. 30p.

BOARDS SURPLUS. Reed Board with 14 12V Reed S.P. make RLAS £1.75. LM309K 5v Regulator Panel 65p.

NEW LOW COST MULTIMETERS. KRT100, 1000Ω. F.V. 1kV AC/DC., 150mA DC current. 0-100KΩ res. mirror scale, switched range selector. £4.65.

KRT101, same as KRT100 but range selection is by prod insertion. £3.50.

TAPE HEADS Mono Cassette £1.30. Stereo version £3.00.


SOLDER SUCKER, high suction eye protection shield £4.95.

PROJECT BOXES, black plastic ABS with lid 75 x 56 x 35 44p; 95 x 71 x 35, 52p 115 x 95 x 36 60p.

TERMS: cash with order, (for official orders from colleges etc). Postage 30p unless otherwise shown, overseas post at cost. VAT inclusive prices. New Illustrated Catalogue now ready. S.A.E. please.

Progressive Radio, 31 Cheapside, Liverpool L2 2DY. Tel: 051 236 0982.

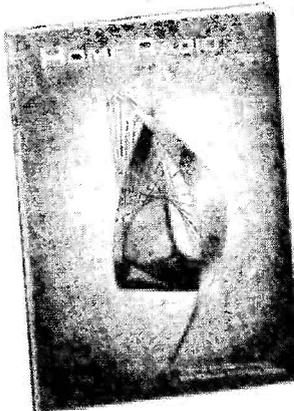SOLVE your component buying problems with this famous Catalogue



- The finest components catalogue yet published.
- 128 A-4-size pages.
- About 2,500 items clearly listed and indexed.
- Profusely illustrated.
- Bargain List sent free.
- At £1.25, incl. p. & p., the catalogue is a bargain.

Send the coupon below now.
HOME RADIO (Components) LTD.,
 Dept. P.W., 234-240 London Road,
 Mitcham, Surrey CR4 3HD

STERNWAY ELECTRICAL LIMITED

3 BRIDE COURT, LONDON EC4Y 8DU

(OFF FLEET STREET)
 01 353 8530

SPECIAL OFFERS—

555 28p each or 10 for £2.10,
 556 55p each,
 ZN414 65p each,
 ORP12 80p each,
 741 25p each or 10 for £2.00.

Above prices include V.A.T., please add 40p post and packing for orders under £10.

LOUDSPEAKER OFFERS—
 2½" 8 ohm, 2½" 25 ohm, 3" 8 ohm, 3" 35 ohm, 3½" 15 ohm, 3½" 80 ohm, 5" 5 ohm, all at £1.75 each including postage and V.A.T.

RESISTANCE SUBSTITUTION BOXES—
 A neat swivelling disc provides close tolerance substitution of 36 preferred value resistors from 5 ohms to 1 megohm. Simply fix clips into circuit and swivel until optimum result is achieved. £3.95 each including postage and V.A.T.

CAPACITANCE SUBSTITUTION BOXES—
 Similar to resistance box, covering .0001 to .22 mfd. £3.95 each including postage and V.A.T.

PLEASE SEND S.A.E. FOR SPECIAL OFFER LISTS.

POST THIS COUPON
 with cheque or P.O. for £1.25

Please write your Name and Address in block capitals

NAME.....

ADDRESS.....



HOME RADIO (Components) LTD., Dept.
 P.W., 234-240 London Road, Mitcham, Surrey
 CR4 3HD.

(Regn No
 London 912966)

Marshall's Electronics

A. Marshall (London) Ltd., Dept: PW Head Office mail order: Kingsgate House, Kingsgate Place, NW6 4TA. Tel: 01-624 0805 Retail Sales
 London: 40-42 Cricklewood Broadway, NW2 3ET. Tel: 01-452 0161/2. Telex: 21492. London: 325 Edgware Road, W2. Tel: 01-723 4242.
 Glasgow: 85 West Regent Street, G2 2QD. Tel: 041-332 4133. Bristol: 1 Straits Parade, Fishponds Road, B516 2LX. Tel: 0272 654201.

TRANSISTORS				T.T.L.				TRIACS																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																				
2N2219	0-38	2N2122	0-44	BC147	0-13	BD241C	0-65	SN7400N	0-17	SN7414AN	-80	SN7442N	0-45	SN7475N	0-80	SN7494N	0-90	SN74145N	0-85	2N2219	0-38	2N2122	0-44	BC147	0-13	BD241C	0-65	SN7400N	0-17	SN7414AN	-80	SN7442N	0-45	SN7475N	0-80	SN7494N	0-90	SN74145N	0-85	2N2219A	0-38	2N2123	0-44	BC148	0-13	BD242A	0-65	SN7401N	0-17	SN7415N	0-25	SN7446AN	0-80	SN7476N	0-80	SN7495N	0-78	SN74146N	1-35	2N2221A	0-25	2N2128	0-44	BC149	0-15	BD242C	0-62	SN7402N	0-17	SN7417N	0-22	SN7447AN	0-55	SN7477N	0-80	SN7496N	0-54	SN74150N	0-80	2N2222	0-25	2N140	1-10	BC160	0-38	BDX14	1-32	SN7403N	0-17	SN7422N	0-25	SN7448AN	0-55	SN7478N	1-00	SN7497N	1-95	SN74151N	0-76	2N2269	0-27	2N200	2-85	BC167	0-13	BDX18	1-90	SN7404AN	0-15	SN7423N	0-22	SN7448N	0-60	SN7478N	0-80	SN7498N	0-80	SN74152N	0-80	2N2369A	0-27	40361	0-55	BC168	0-13	BFX30	0-34	SN7405N	0-22	SN7425N	0-22	SN7449AN	0-55	SN7479N	1-05	SN7499N	1-20	SN74154N	1-20	2N2464	1-70	40362	0-55	BC169	0-13	BFX30	0-34	SN7406N	0-39	SN7426N	0-22	SN7451N	0-22	SN7484AN	1-20	SN74118N	0-95	SN74155N	0-78	2N2903	1-80	40406	0-73	BC177	0-22	BFY50	0-235	SN7407N	0-39	SN7427N	0-22	SN7453N	0-20	SN7485N	0-80	SN74119N	1-40	SN74157N	0-78	2N2904	0-31	40407	0-57	BC178	0-22	BFY51	0-25	SN7408N	0-22	SN7430N	0-22	SN7454AN	0-20	SN7486N	0-36	SN74121N	0-28	Also stocked 74C.	2N2905	0-31	40408	0-82	BC179	0-22	BFY50	1-35	SN7409N	0-22	SN7432N	0-22	SN7486N	0-36	SN74122N	0-55	74H, 74S, 74LS	2N2905A	0-31	40409	0-82	BC182	0-12	BFY39	0-55	SN7410N	0-20	SN7437N	0-24	SN7470N	0-30	SN7490AN	0-36	SN74123N	0-55	40576	2N2906	0-25	40594	0-87	BC182L	0-12	BU208	2-70	SN7411N	0-20	SN7438N	0-24	SN7470N	0-30	SN7491AN	0-36	SN74124N	1-20	40688	2N2907	0-25	40595	0-98	BC183	0-12	1300	0-37	SN7412N	0-20	SN7440N	0-18	SN7473N	0-36	SN7492N	0-36	SN74125N	0-45	2N4444	2N2926	0-17	40836	1-37	BC183L	0-12	1310	0-84	SN7413N	0-20	SN7441AN	0-59	SN7474N	0-26	SN7493N	0-36	SN74141N	0-56	2N4444	2N3053	0-25	40873	1-30	BC184	0-12	MJ480	1-49	SN7408N	0-22	SN7430N	0-22	SN7454AN	0-20	SN7486N	0-36	SN74121N	0-28	See catalogue	2N3054	0-72	40878	1-37	BC184L	0-12	MJ480	1-49	SN7409N	0-22	SN7432N	0-22	SN7454AN	0-20	SN7486N	0-36	SN74121N	0-28	for full range	2N3055	0-25	40873	1-30	BC184	0-12	MJ480	1-49	SN7407N	0-39	SN7427N	0-22	SN7453N	0-20	SN7485N	0-80	SN74119N	1-40	See catalogue	2N3054	0-72	40878	1-37	BC184L	0-12	MJ480	1-49	SN7408N	0-22	SN7430N	0-22	SN7454AN	0-20	SN7486N	0-36	SN74121N	0-28	for full range	2N3055	0-25	40873	1-30	BC184	0-12	MJ480	1-49	SN7409N	0-22	SN7432N	0-22	SN7454AN	0-20	SN7486N	0-36	SN74121N	0-28	for full range	2N3054	0-72	40878	1-37	BC184L	0-12	MJ480	1-49	SN7409N	0-22	SN7432N	0-22	SN7454AN	0-20	SN7486N	0-36	SN74121N	0-28	for full range	2N3055	0-25	40873	1-30	BC184	0-12	MJ480	1-49	SN7407N	0-39	SN7427N	0-22	SN7453N	0-20	SN7485N	0-80	SN74119N	1-40	See catalogue	2N3054	0-72	40878	1-37	BC184L	0-12	MJ480	1-49	SN7408N	0-22	SN7430N	0-22	SN7454AN	0-20	SN7486N	0-36	SN74121N	0-28	for full range	2N3055	0-25	40873	1-30	BC184	0-12	MJ480	1-49	SN7409N	0-22	SN7432N	0-22	SN7454AN	0-20	SN7486N	0-36	SN74121N	0-28	for full range	2N3054	0-72	40878	1-37	BC184L	0-12	MJ480	1-49	SN7409N	0-22	SN7432N	0-22	SN7454AN	0-20	SN7486N	0-36	SN74121N	0-28	for full range	2N3055	0-25	40873	1-30	BC184	0-12	MJ480	1-49	SN7407N	0-39	SN7427N	0-22	SN7453N	0-20	SN7485N	0-80	SN74119N	1-40	See catalogue	2N3054	0-72	40878	1-37	BC184L	0-12	MJ480	1-49	SN7408N	0-22	SN7430N	0-22	SN7454AN	0-20	SN7486N	0-36	SN74121N	0-28	for full range	2N3055	0-25	40873	1-30	BC184	0-12	MJ480	1-49	SN7409N	0-22	SN7432N	0-22	SN7454AN	0-20	SN7486N	0-36	SN74121N	0-28	for full range	2N3054	0-72	40878	1-37	BC184L	0-12	MJ480	1-49	SN7409N	0-22	SN7432N	0-22	SN7454AN	0-20	SN7486N	0-36	SN74121N	0-28	for full range	2N3055	0-25	40873	1-30	BC184	0-12	MJ480	1-49	SN7407N	0-39	SN7427N	0-22	SN7453N	0-20	SN7485N	0-80	SN74119N	1-40	See catalogue	2N3054	0-72	40878	1-37	BC184L	0-12	MJ480	1-49	SN7408N	0-22	SN7430N	0-22	SN7454AN	0-20	SN7486N	0-36	SN74121N	0-28	for full range	2N3055	0-25	40873	1-30	BC184	0-12	MJ480	1-49	SN7409N	0-22	SN7432N	0-22	SN7454AN	0-20	SN7486N	0-36	SN74121N	0-28	for full range	2N3054	0-72	40878	1-37	BC184L	0-12	MJ480	1-49	SN7409N	0-22	SN7432N	0-22	SN7454AN	0-20	SN7486N	0-36	SN74121N	0-28	for full range	2N3055	0-25	40873	1-30	BC184	0-12	MJ480	1-49	SN7407N	0-39	SN7427N	0-22	SN7453N	0-20	SN7485N	0-80	SN74119N	1-40	See catalogue	2N3054	0-72	40878	1-37	BC184L	0-12	MJ480	1-49	SN7408N	0-22	SN7430N	0-22	SN7454AN	0-20	SN7486N	0-36	SN74121N	0-28	for full range	2N3055	0-25	40873	1-30	BC184	0-12	MJ480	1-49	SN7409N	0-22	SN7432N	0-22	SN7454AN	0-20	SN7486N	0-36	SN74121N	0-28	for full range	2N3054	0-72	40878	1-37	BC184L	0-12	MJ480	1-49	SN7409N	0-22	SN7432N	0-22	SN7454AN	0-20	SN7486N	0-36	SN74121N	0-28	for full range	2N3055	0-25	40873	1-30	BC184	0-12	MJ480	1-49	SN7407N	0-39	SN7427N	0-22	SN7453N	0-20	SN7485N	0-80	SN74119N	1-40	See catalogue	2N3054	0-72	40878	1-37	BC184L	0-12	MJ480	1-49	SN7408N	0-22	SN7430N	0-22	SN7454AN	0-20	SN7486N	0-36	SN74121N	0-28	for full range	2N3055	0-25	40873	1-30	BC184	0-12	MJ480	1-49	SN7409N	0-22	SN7432N	0-22	SN7454AN	0-20	SN7486N	0-36	SN74121N	0-28	for full range	2N3054	0-72	40878	1-37	BC184L	0-12	MJ480	1-49	SN7409N	0-22	SN7432N	0-22	SN7454AN	0-20	SN7486N	0-36	SN74121N	0-28	for full range	2N3055	0-25	40873	1-30	BC184	0-12	MJ480	1-49	SN7407N	0-39	SN7427N	0-22	SN7453N	0-20	SN7485N	0-80	SN74119N	1-40	See catalogue	2N3054	0-72	40878	1-37	BC184L	0-12	MJ480	1-49	SN7408N	0-22	SN7430N	0-22	SN7454AN	0-20	SN7486N	0-36	SN74121N	0-28	for full range	2N3055	0-25	40873	1-30	BC184	0-12	MJ480	1-49	SN7409N	0-22	SN7432N	0-22	SN7454AN	0-20	SN7486N	0-36	SN74121N	0-28	for full range	2N3054	0-72	40878	1-37	BC184L	0-12	MJ480	1-49	SN7409N	0-22	SN7432N	0-22	SN7454AN	0-20	SN7486N	0-36	SN74121N	0-28	for full range	2N3055	0-25	40873	1-30	BC184	0-12	MJ480	1-49	SN7407N	0-39	SN7427N	0-22	SN7453N	0-20	SN7485N	0-80	SN74119N	1-40	See catalogue	2N3054	0-72	40878	1-37	BC184L	0-12	MJ480	1-49	SN7408N	0-22	SN7430N	0-22	SN7454AN	0-20	SN7486N	0-36	SN74121N	0-28	for full range	2N3055	0-25	40873	1-30	BC184	0-12	MJ480	1-49	SN7409N	0-22	SN7432N	0-22	SN7454AN	0-20	SN7486N	0-36	SN74121N	0-28	for full range	2N3054	0-72	40878	1-37	BC184L	0-12	MJ480	1-49	SN7409N	0-22	SN7432N	0-22	SN7454AN	0-20	SN7486N	0-36	SN74121N	0-28	for full range	2N3055	0-25	40873	1-30	BC184	0-12	MJ480	1-49	SN7407N	0-39	SN7427N	0-22	SN7453N	0-20	SN7485N	0-80	SN74119N	1-40	See catalogue	2N3054	0-72	40878	1-37	BC184L	0-12	MJ480	1-49	SN7408N	0-22	SN7430N	0-22	SN7454AN	0-20	SN7486N	0-36	SN74121N	0-28	for full range	2N3055	0-25	40873	1-30	BC184	0-12	MJ480	1-49	SN7409N	0-22	SN7432N	0-22	SN7454AN	0-20	SN7486N	0-36	SN74121N	0-28	for full range	2N3054	0-72	40878	1-37	BC184L	0-12	MJ480	1-49	SN7409N	0-22	SN7432N	0-22	SN7454AN	0-20	SN7486N	0-36	SN74121N	0-28	for full range	2N3055	0-25	40873	1-30	BC184	0-12	MJ480	1-49	SN7407N	0-39	SN7427N	0-22	SN7453N	0-20	SN7485N	0-80	SN74119N	1-40	See catalogue	2N3054	0-72	40878	1-37	BC184L	0-12	MJ480	1-49	SN7408N	0-22	SN7430N	0-22	SN7454AN	0-20	SN7486N	0-36	SN74121N	0-28	for full range	2N3055	0-25	40873	1-30	BC184	0-12	MJ480	1-49	SN7409N	0-22	SN7432N	0-22	SN7454AN	0-20	SN7486N	0-36	SN74121N	0-28	for full range	2N3054	0-72	40878	1-37	BC184L	0-12	MJ480	1-49	SN7409N	0-22	SN7432N	0-22	SN7454AN	0-20	SN7486N	0-36	SN74121N	0-28	for full range	2N3055	0-25	40873	1-30	BC184	0-12	MJ480	1-49	SN7407N	0-39	SN7427N	0-22	SN7453N	0-20	SN7485N	0-80	SN74119N	1-40	See catalogue	2N3054	0-72	40878	1-37	BC184L	0-12	MJ480	1-49	SN7408N	0-22	SN7430N	0-22	SN7454AN	0-20	SN7486N	0-36	SN74121N	0-28	for full range	2N3055	0-25	40873	1-30	BC184	0-12	MJ480	1-49	SN7409N	0-22	SN7432N	0-22	SN7454AN	0-20	SN7486N	0-36	SN74121N	0-28	for full range	2N3054	0-72	40878	1-37	BC184L	0-12	MJ480	1-49	SN7409N	0-22	SN7432N	0-22	SN7454AN	0-20	SN7486N	0-36	SN74121N	0-28	for full range	2N3055	0-25	40873	1-30	BC184	0-12	MJ480	1-49	SN7407N	0-39	SN7427N	0-22	SN7453N	0-20	SN7485N	0-80	SN74119N	1-40	See catalogue	2N3054	0-72	40878	1-37	BC184L	0-12	MJ480	1-49	SN7408N	0-22	SN7430N	0-2

15-240 Watts!

HY5 Preamplifier

The HY5 is a mono hybrid amplifier ideally suited for all applications. All common input functions (mag Cartridge, tuner, etc) are catered for internally. The desired function is achieved either by a multi-way switch or direct connection to the appropriate pins. The internal volume and tone circuits merely require connecting to external potentiometers (not included). The HY5 is compatible with all I.L.P. power amplifiers and power supplies. To ease construction and mounting a P.C. connector is supplied with each pre-amplifier.

FEATURES: Complete pre-amplifier in single pack—Multi-function equalization—Low noise—Low distortion—High overload—Two simply combined for stereo.

APPLICATIONS: Hi-Fi—Mixers—Disco—Guitar and Organ—Public address

SPECIFICATIONS:

INPUTS: Magnetic Pick-up 3mV; Ceramic Pick-up 30mV; Tuner 100mV; Microphone 10mV; Auxiliary 3-100mV; input impedance 4.7kΩ at 1kHz.


OUTPUTS: Tape 100mV; Main output 500mV R.M.S.

ACTIVE TONE CONTROLS: Treble ± 12dB at 10kHz; Bass ± at 100Hz.

DISTORTION: 0.1% at 1kHz, Signal/Noise Ratio 68dB.

OVERLOAD: 38dB on Magnetic Pick-up, SUPPLY VOLTAGE ± 16-50V.

Price £6.27 + 78p VAT P&P free.

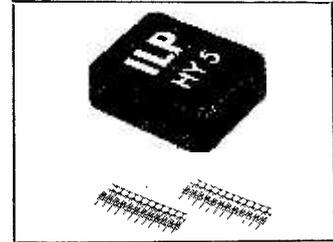

HY30 15 Watts into 8Ω

The HY30 is an exciting New kit from I.L.P. It features a virtually indestructible I.C. with short circuit and thermal protection. The kit consists of I.C., heatsink, P.C. board, 4 resistors, 6 capacitors, mounting kit, together with easy to follow construction and operating instructions. This amplifier is ideally suited to the beginner in audio who wishes to use the most up-to-date technology available.

FEATURES: Complete Kit—Low Distortion—Short, Open and Thermal Protection—Easy to Build.

APPLICATIONS: Updating audio equipment—Guitar practice amplifier—Test amplifier—audio oscillator.


SPECIFICATIONS:

OUTPUT POWER 15W R.M.S. into 8Ω; **DISTORTION** 0.1% at 1.5W.

INPUT SENSITIVITY 500mV. **FREQUENCY RESPONSE** 10Hz-16kHz—3dB.

SUPPLY VOLTAGE ± 18V.

Price £6.27 + 78p VAT P&P free.

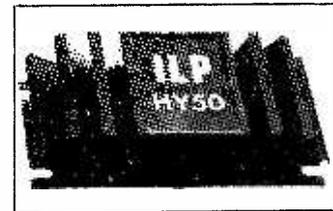

HY50 25 Watts into 8Ω

The HY50 leads I.L.P.'s total integration approach to power amplifier design. The amplifier features an integral heatsink together with the simplicity of no external components. During the past three years the amplifier has been refined to the extent that it must be one of the most reliable and robust High Fidelity modules in the World.

FEATURES: Low Distortion—Integral Heatsink—Only five connections—7 amp output transistors—No external components

APPLICATIONS: Medium Power Hi-Fi systems—Low power disco—Guitar amplifier

SPECIFICATIONS: INPUT SENSITIVITY 500mV


OUTPUT POWER 25W RMS into 8Ω **LOAD IMPEDANCE** 4-16Ω **DISTORTION** 0.04% at 25W

at 1kHz

SIGNAL/NOISE RATIO 75dB **FREQUENCY RESPONSE** 10Hz-45kHz—3dB.

SUPPLY VOLTAGE ± 25V **SIZE** 105 50 25mm

Price £8.18 + £1.02 VAT P&P free

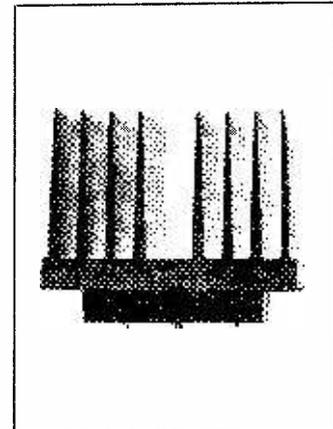

HY120 60 Watts into 8Ω

The HY120 is the baby of I.L.P.'s new high power range. Designed to meet the most exacting requirements including load line and thermal protection this amplifier sets a new standard in modular design.

FEATURES: Very low distortion—Integral heatsink—Load line protection—Thermal protection—Five connections—No external components

APPLICATIONS: Hi-Fi—High quality disco—Public address—Monitor amplifier—Guitar and organ

SPECIFICATIONS

INPUT SENSITIVITY 500mV.

OUTPUT POWER 60W RMS into 8Ω **LOAD IMPEDANCE** 4-16Ω **DISTORTION** 0.04% at 60W

at 1kHz

SIGNAL/NOISE RATIO 90dB **FREQUENCY RESPONSE** 10Hz-45kHz—3dB **SUPPLY VOLTAGE**

± 35V

SIZE 114 50 85mm

Price £19.01 + £1.52 VAT P&P free.

HY200 120 Watts into 8Ω

The HY200 now improved to give an output of 120 Watts has been designed to stand the most rugged conditions such as disco or group while still retaining true Hi-Fi performance.

FEATURES: Thermal shutdown—Very low distortion—Load line protection—Integral heatsink—No external components

APPLICATIONS: Hi-Fi—Disco—Monitor—Power slave—Industrial—Public Address

SPECIFICATIONS

INPUT SENSITIVITY 500mV

OUTPUT POWER 120W RMS into 8Ω **LOAD IMPEDANCE** 4-16Ω **DISTORTION** 0.05% at 100W

at 1kHz

SIGNAL/NOISE RATIO 96dB **FREQUENCY RESPONSE** 10Hz-45kHz—3dB **SUPPLY VOLTAGE**

± 45V

SIZE 114 50 85mm

Price £27.99 + £2.24 VAT P&P free.

HY400 240 Watts into 4Ω

The HY400 is I.L.P.'s "Big Daddy" of the range producing 240W into 4Ω! It has been designed for high power disco address applications. If the amplifier is to be used at continuous high power levels a cooling fan is recommended. The amplifier includes all the qualities of the rest of the family to lead the market as a true high power hi-fidelity power module.

FEATURES: Thermal shutdown—Very low distortion—Load line protection—No external components.

APPLICATIONS: Public address—Disco—Power slave—Industrial

SPECIFICATIONS

OUTPUT POWER 240W RMS into 4Ω **LOAD IMPEDANCE** 4-16Ω **DISTORTION** 0.1% at 240W


at 1kHz

SIGNAL NOISE RATIO 94dB **FREQUENCY RESPONSE** 10Hz-45kHz—3dB **SUPPLY VOLTAGE**

± 45V

INPUT SENSITIVITY 500mV **SIZE** 114 100 85mm

Price £38.61 + £3.09 VAT P&P free.

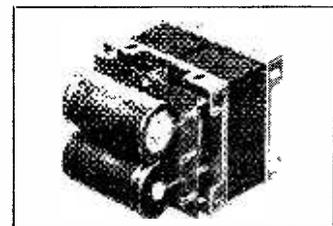

POWER SUPPLIES

PSU36 suitable for two HY30's £6.44 plus 81p VAT. P/P free.
 PSU50 suitable for two HY50's £8.18 plus £1.02 VAT. P/P free.
 PSU70 suitable for two HY120's £14.98 plus £1.17 VAT. P/P free.
 PSU90 suitable for one HY200 £15.19 plus £1.21 VAT. P/P free.
 PSU180 £25.42 + £2.03 VAT.
 B1 £0.48 + £0.06 VAT.

TWO YEARS' GUARANTEE ON ALL OUR PRODUCTS

I.L.P. ELECTRONICS LTD., CROSSLAND HOUSE, NACKINGTON CANTERBURY, KENT, CT4 7AD.

I.L.P. ELECTRONICS LTD.,
GRAHAM BELL HOUSE, ROPER CLOSE,
CANTERBURY, KENT, CT2 7EP.

Tel: (0227) 54778.

Regd No. 1032630.

Please Supply _____
 Total Purchase Price _____
 Enclose Cheque Postal Orders Money Order
 Please debit my Access account Barclaycard account
 Account number _____
 Name and Address _____
 Signature _____

EVEN LOWER PRICES!!

FROM TIMETRON Recommended by TEMPUS

A well known consumer magazine has published a report on digital watches which supports our conviction that CASIO and SEIKO are probably the best watches in the world, with CASIO offering unbeatable value for money. All CASIO watches have a calendar display, night illumination, mineral glass and stainless steel cases, water resistant to 100 ft (except sports watches—66)

SPORTS WATCHES



F-100
Left. 9-45mm was £29.95.

£19.95

52QS-14B
Right 8mm was £44.95

£27.95

Up to 25 functions. Net. lap and first and second place times to 1/100th sec. F-100. Resin case, strap 52QS-14B. S/S encased version and S/S bracelet.



50QS-17B 4 digit watch. Identical case to 52QS-14B but with 3 push buttons RRP £24.95 **£19.95**

4 DIGIT WATCHES display hours, minutes, ten seconds, seconds by flash, am/pm; And with day, date and month. 1 second to 13 hours stopwatch. Dual time facility.

31QR-20B

Left. 8.5mm 4 digit. Was £35.95

£22.95

54QS-16B

Right. 7.5mm 6 digit. Was £49.95

£29.95



Not illustrated:

51QR-19B 6 digit. Round face. Was £44.95

£24.95

51QR-18B 6 digit. Round face. Was £49.95

£26.95

6 DIGIT WATCHES (Not Sports) Hours, minutes, seconds and day of week. Model 54QS has an optional display of hrs, min, day, date, ten seconds, seconds by flash; And day, date, month, year calendar. Selectable 12 hour (with am/pm) or 24 hour clock.

CHRONOGRAPH AND ALARM CHRONOGRAPH



45CS-22B
Left. Chrono
Was £69.95

£39.95

46CS-27B
Right. A/C. 7-8mm
Was £89.95

£74.95

CHRONOGRAPH. 6 digits as above, with stopwatch measuring net, lap and 1st and 2nd place times from 1/100 sec to 6 hrs. Dual time facility.

ALARM CHRONO. As Chrono above but without dual time. 24 hour alarm with optional hourly chime facility.



60QS-20B Chronograph. Details available on request. RRP £44.95 **£34.95**

CALCULATING ALARM CLOCKS (LCD)

AQ-2000 With stopwatch and calendar. **£24.95**

MQ-10 As above.

1 1/2 x 4 1/4 ins. **£35.95**

MQ-11 As above.

1 1/2 x 2 1/4 x 3 1/4 ins. **£29.95**

CQ-82



6 digit LC Display of time, with night light. Four alarms, one with snooze facility. Calculator with %, ., K. One year battery. 1 1/2 x 5 1/2 x 2 1/2 ins. **£19.95**



LCD calculators with full memory, %, ., K. Most have battery saving APO (Automatic Power-Off). LC-79 Sensor touch Mini Card with APO. A very rigid 1 1/2 x 2 1/4 x 3 1/4 ins. Beautifully styled. Pouch £15.95.

LC-841 APO. Rigid 1 1/2 x 2 1/4 x 4 1/4 ins. Pouch £12.95.

NEW HL series. Two AA batteries (last 6,000-10,000 hours).

HL-801 8 digits £9.95. HL-101 (10) £12.95. HL-121. £19.95.

LCd Scientific Calculators. FX-48 £19.95. FX-2500 £21.95.

FX-3100 £25.95. FX-8000 £29.95.

Most CASIO products in stock. Send 15p for brochures.

Prices include VAT, P & P. Send cheque, P.O. or phone your Access or B'card number to:—

Dept. P.W., Beaumont
Suite 164-167 East Road
Cambridge CB1 1DB
Telephone 0223 67503

TIMETRON

Callers welcome by appointment

THE SINCLAIR PDM35 Digital Multimeter

Now a digital multimeter at an analogue price and look at the spec!

D.C. VOLTS 1mv-1000v (1% — 1 count) 10mΩ input.
A.C. VOLTS 1v-500v, 40Hz-5kHz (1% + 2 counts)

D.C. CURRENT 1mA-200mA (1% count)

RESISTANCE 1Ω-20MΩ (1.5% + 1 count) **£29.80**

1 in A-200mA C.W.O. or £30.95 company or govt. purchase order
Adaptor £3.20 Padded case £3.20 30kV probe £18.92

New DM 350 3 1/2 digit multimeter @ £69.90. SAE for details

New DM 450 @ £96. SAE for details



SINCLAIR DM235

Portable 3 1/2 digit 6 function Multimeter

DC volts 1mv to 1000V AC volts 1mv to 750V AC & DC current 1μA to 1A Resistance 1Ω to 20MΩ Diode test 0.1mA to 1mA 10mΩ input DC acc 1.0% AC acc 1.5% 30Hz-10kHz

inc. VAT Cash with order Case £8.80. Adaptor £3.75 C.W.O

£23.95 + 86p postage.

THE SINCLAIR MICROVISION

The amazing pocket TV that will pick up programs throughout the world, complete with rechargeable batteries. International model

£149.95 inc VAT UK model £99 inc VAT Adaptors £6.00. Battery £1.16. Sae (for detailed Brochure ex-stock)

Portable 3 1/2 digit 6 function Multimeter

DC volts 1mv to 1000V AC volts 1mv to 750V AC & DC current 1μA to 1A Resistance 1Ω to 20MΩ Diode test 0.1mA to 1mA 10mΩ input DC acc 1.0% AC acc 1.5% 30Hz-10kHz

Rech. Batts. £8.95

SINCLAIR ENTERPRISE


75 step programmable calculator (Trigonometric functions, logs etc.) has seven independent memories which can be used under program control. Forward or backward stepping facility for examining the stored programme and conditional branching under program control. We have thrown in a case, mains adaptor, alkaline battery and a three-volume software library containing 316 programs and an instruction manual

£23.95 + 86p postage.



KRAMER & CO

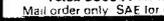We will match any lower advertised price on a cash with order basis if competitor has goods in stock
9 October Place, Hammers Hill Road, London, NW14 1EJ
Tel: 88841 Adms. Kramer K7, Tel: 01-203 2473
Mail order only. SAE for data sheets. Export enquiries welcome



£23.95 + 86p postage.

OSMABET LTD

We make transformers amongst other things

LOW VOLTAGE TRANSFORMERS: Prim 240V ac.

6.3V 1.5A £2.95; 3A £3.60; 6A CT £6.85; 12V 1.5A £3.35; 3A CT £2.85; 6A CT £3.50; 15V 0.5A £2.75; 18V 1.5A CT £6.85; 24V 1.5A £8.85; 3A CT £3.50; 12V 1.5A £2.50; 8A CT £26.75; 12A CT £35.00; 40V 3A CT £12.25.

TWIN SEC TRANSFORMERS: Prim 240V ac.

6V 0.6A + 6V 0.6A; 9V 0.4A + 9V 0.4A; 12V 0.3A + 12V 0.3A; 20V 0.15A + 20V 0.15A; all at £3.65 each; 15V 0.75A + 15V 0.75A £8.65; 18V 1.5A + 18V 1.5A £7.75; 18V 1A + 18V 1A £8.85; 18V 1.5A + 18V 1.5A £8.50; 20V 1.5A + 20V 1.5A £8.50; 12V 4A + 12V 4A £10.50; 25V 2A + 25V 2A £10.50.

MIDGET RECTIFIER TRANSFORMERS: Prim 240V ac.

5.0-6V 1.5A or 3-0.3V 1A £2.00; 12V 0.12V 1A or 0.20V 0.20V 0.75A £3.75 each; 9-0-9V 0.3A or 12V 0-12V 0.25A or 20V 0-20V 0.15A £2.85 each.

LT TRANSFORMERS TAPPED SEC. prim 240V ac.

0-10-12-14-16-18-18V 2A £6.50; 4A £8.25; 0-12-15-20-24-30V 2A £7.35; 4A £10.50; 0-20-30-40V 1.5A £7.75; 2A £10.50; 0-40-50-60-80-100-110V 1A £10.50.

MAINS TRANSFORMERS SPECIAL OFFER:

prim 240V ac. 250-0-250V 80Ma. 6.3V 1A £2.00; 250V 100Ma. 6.3V 2A £2.00; 9V 3A £2.50; 25V 0.3A £1.00.

LOUDSPEAKERS

2 1/2 in 8Ω, 2 1/2 in 8 or 25Ω, 2 1/2 in 8Ω, 3 in 35Ω, 3 1/2 in 8, 8, 16 or 8Ω, all at 1.25 each; 5 x 3 in 4, 8, 15 or 25Ω, £1.50; 7 x 4 in 4, 8, 16, 25 or 8Ω, £1.75; 8 x 5 in 4, 8 or 25Ω, £3.00; Bin 8Ω, £2.50

"INSTANT" BULK CASSETTE/TAPE ERASER

Instant erasure of cassettes, and any diameter of tape spools, demagnetises tape heads, 200/240V ac. £6.00.

POWER SUPPLY, TWIN OUTPUT: Prim 240V ac.

New, British manufacture, smoothed d.c. output 20V 1.5A, plus stabilised output of 15V 100Ma, plus 12V ac 0.5A output, complete with diagram, £3.50.

EDGEWILE LEVEL METER FSD 200/1A

Size 19 x 18 x 20mm 800Ω £1.10.

CHARGING METERS 1 1/2 ins diameter

2A or 3A £1.25 each; 5A or 10A £1.80 each.

SYNCHRONOUS GEARED MOTORS, 240V ac.

Brand new, built in gear box, 1 or 20 R.P.M., £1.25 each.

O/P TRANSFORMERS FOR VALVE AMPLIFIERS

P.P. sec tapped 3-8-15Ω, A-A 6K, 30W £15.25; A-A 3K, 50W £22.75; 100W (EL31, KT88, etc.) £31.25.

G.E.C. MANUAL OF POWER AMPLIFIERS

Covers valve amplifiers 20V to 400V, £1.00.

MULTIWAY SCREENED CABLE, PVC COVERED

36 way £1.00; 25 way 75p; 14 way 50p; 6 way 25p; 4 way 20p; 2 way 10p; 1 way 8p; 4 way individually screened 25p per metre, fig B twin stereo do screened 15p, metre.

MAINS CABLE

4 way, 3A 30p metre; fig for loudspeakers etc. £5.00 100 metres.

CONDENSERS

Electrolytic, 400/400V 75p; 2000/30V 30p; 1200/75 50p; 2200/40V 40p; Paper tubular, W/E 4/160V, 6/160V, 2/150V, 0.1/2000V 25p each.

CARRIAGE EXTRA ON ALL ORDERS

ALL PRICES INCLUDE V.A.T.


Callers by appointment only. S.A.E. Enquiries, Lists.

46, Kenilworth Road, Edgware, Middx.

HAB 8YG. Tel: 01-958 9314

Sonic

HI-FI DISCOUNT CENTRES

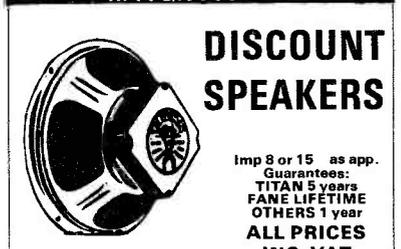

DISCOUNT SPEAKERS

Imp 8 or 15 as app.
Guarantees:
TITAN 5 yrs
FANE LIFETIME
OTHERS 1 year
ALL PRICES INC. VAT

Prices correct at 23.1.79

HI-FI TYPES	List/Value	Sonic Price
5" FANE 501 Mid or Full range	Sp. Price	£4.95
8" A.F. Model 80 Dual Cone	Sp. Price	£4.95
8" A.F. Model 83 Dual Cone	Sp. Price	£6.95
FANE 8" 808T Dual Cone	Sp. Price	£3.95
WH FEDALE L/TON 3XP kit Pr.	Sp. Price	£60.70
10" DENTON 2XP KIT Pr.	Sp. Price	£21.95
10" GLENDALE 3XP KIT	Sp. Price	£58.95
A.F. FRI 8" SPKR KIT	Sp. Price Pair	£14.95
8" FANE MODE ONE KIT	Sp. Price Pair	£19.99
10" ELAC Model 10RM 10-15W	Sp. Price	£2.50

CABINETS (TEAK VENEERED)

20" x 11 1/2" x 9 1/2" Suitable for Mode 1 or FRI Kits and Models 80, 83 or 808T Spkrs.

Limited Number **£6.95** ea.

GROUP/DISCO TYPES	List/Value	Sonic Price
12" TITAN T12/45R	£15.00	£12.95
12" TITAN T12/60R	£22.50	£14.95
12" TITAN T12/100A 100w	£26.00	£19.95
12" CELESTION G12M	£16.50	£11.95
12" CELESTION G12H 30w	£22.00	£14.95
12" CELESTION G12/50 50w	£25.75	£18.95
12" GOODMANS 12 PD	Sp. Price	£21.95
12" GOODMANS 12 PG	Sp. Price	£18.95
12" FANE 'SPECIALIST' P.A. 80	£29.95	£19.95
12" " DISCO 80	£29.95	£19.95
12" " DISCO 100	£31.95	£21.95
12" " GUITAR 80L	£28.95	£18.95
12" " GUITAR 100L	£31.95	£19.95
12" " GUITAR 80B	£29.95	£19.95
12" FANE CRESCENDO 80	£44.95	£29.95
12" " 80LT	£49.95	£34.95
12" " 12A	£64.45	£41.95
12" " 12L	£67.67	£39.95
12" " 12 BASS	£63.95	£39.95
15" TITAN T15/70 70w	£28.00	£19.95
15" TITAN T15/100 100w	£41.00	£29.95
15" FANE 'SPECIALIST' BASS 85	£41.95	£29.95
15" " BASS 100	£44.50	£31.50
15" GOODMANS 15P	Sp. Price	£23.95
15" FANE CRESCENDO/15	£82.66	£51.95
15" " BASS	£85.95	£51.95
15" " 15/100LT	£74.69	£51.95
15" " 15/160 160w	£107.23	£72.95
15" " COLOSSUS 200w	£121.91	£72.95
18" TITAN T18/100 100w	£51.00	£39.95
18" GOODMANS 18P	Sp. Price	£39.95
18" CELESTION G18C	£53.00	£41.95
18" FANE CRESCENDO 18A	£114.97	£72.95
18" " BASS	£101.86	£59.95
18" " COLOSSUS 200w	£129.81	£75.00

PLEASE STATE IMPEDANCE.

HORN UNITS	(Carr. 85p)	List/Value	Sonic Price
CELESTION NH1000 25w		£17.00	£13.75
FANE 919 MK II 50w		£19.00	£10.95
" 920 100w		£62.95	£44.50
" J44 30 25w		£7.95	£4.95
" J73 50w		£11.75	£7.95
" J104 50-70w		£16.95	£10.95

HIGH POWER 'CROSS-OVERS'

FANE HPx1R or HPx2R Carr. 35p **£3.65** **£2.25**

ADD-ON HIGH FREQUENCY UNITS

F.A.L. 'Add-on' Carr. £1	List/Value	Sonic Price
TITAN T1H 70w Carr. £1	£33.00	£19.95
TITAN T2H 100w Carr. £1	£33.00	£23.95
TITAN T2H Carr. £1	£39.00	£26.95

BIG

A breadboard as big as your ideas.

EXPERIMENTOR 325 £2.54

The ideal Breadboard for 1 chip circuits. Accepts 8, 14, 16 and up to 22 pin IC's. Has 130 contact points including two 10-point bus-bars.



EXPERIMENTOR 600 £6.30

The Breadboard for quick construction of Microprocessors and other circuits. EXP 600 has 550 contacts including two 40-point bus-bars with 0.6" centres.

EXPERIMENTOR 650 £3.60

Perfect for checking out Microprocessors. EXP 650 has 270 contacts including two 20-point bus-bars with 0.6" centres.

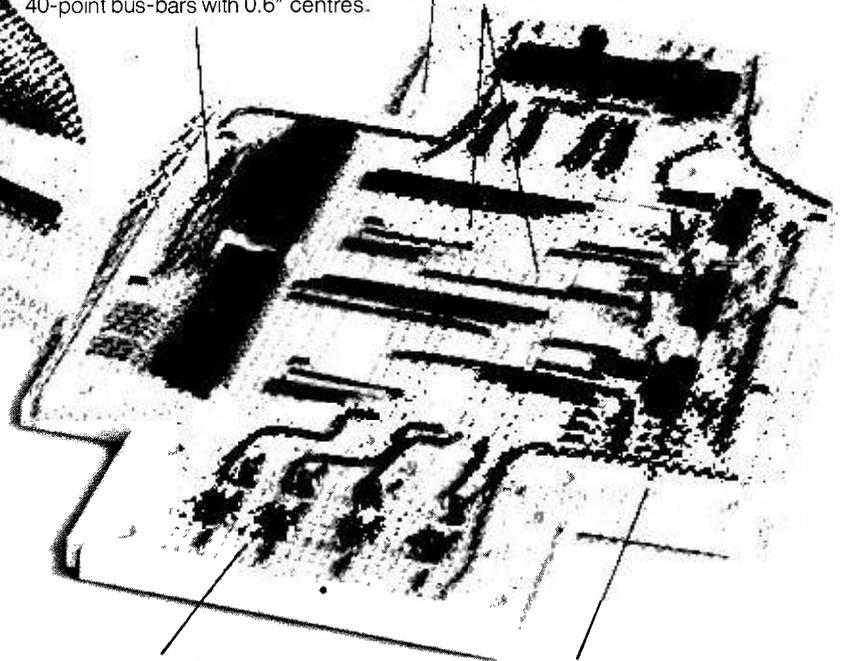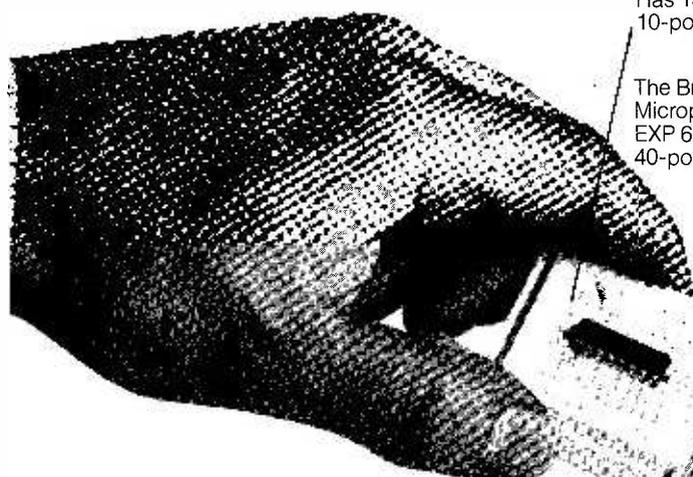EXPERIMENTOR QUAD BUS STRIP £2.30 Need more bus-bars, clip on an EXP 4B and you have four 40-point bus-strips with 8-, 12- and 16-line address, create data-buses by combining EXP 4B, Bus Strips.



No soldering simply plug all standard components in and out, nickel-silver contacts allow Breadboard and components to be used over and over again without damage.

Adaptable accepts any component without adaptors or jumper leads, use 22-30 gauge solid wire for jumper leads.

Mix and Match large and small chips in the same circuit. Use 300 series for smaller and 0.3" pitch DIP's. 600 series for Microprocessors with 0.6" centre channel for full fan-out with larger chips.

Smallest to Biggest, remember CSC's Breadboards "snap-lock" together so you can start with a small idea and expand your ideas to as Big a Breadboarding area as you like.

Easy Permanent Mounting, using four screws from front or six self-tappers from rear. Vinyl-insulated backing lets you fasten to any surface.

Pick any project that you want to build, or any part of a project that you want to test or modify. Count up the number of IC's you need for the project. Then simply look up in the box opposite the Breadboard you require. If you need more than two bus-bars simply add the correct number of Quad-Bus Strips. GET STARTED NOW FOR AS LITTLE AS £2.54.

EXPERIMENTOR 350 £3.15

EXP 350, specifically designed for the hobbyist working with up to 3 x 14 DIP IC's. With 270 contact points including two 20-point bus-bars the EXP 350 accepts any size DIP with 0.3" spacing.

Marked Contact Points transfer component by component from letter/number position on Breadboard to finished P.C. Board or Wiring Table.

Ruggedly built of abrasion-resistant materials that withstand 100°C.

EXPERIMENTOR 300 £5.75

The hobbyists ideal Breadboard, accepts 6 x 14 DIP or 5 x 16 DIP, has 550 contact points including two 40-point bus-bars, accepts any size DIP with 0.3" spacing.

Tailor-Made Breadboards e.g. a project requires up to 5 x 14 DIP chips and needs up to six bus-bars. Which to buy? Easy from the table below select an EXP 300 plus an EXP 4B, total cost £10.58.

MODEL NO.	NUMBER OF CONTACT HOLES	ICCAPACITY (14-pin DIP's)	UNIT PRICE (includes Post & VAT)
EXP 300	550	6	£7.29
EXP 600	550	use with 0.6" PITCH DIP's	£7.88
EXP 350	270	3	£4.21
EXP 650	270	use with 0.6" PITCH DIP's	£4.70
EXP 325	130	1	£2.54
EXP 4B	FOUR 40-point Bus-Bars	—	£3.29

How to order. Telephone 0799 21682 and give your Access, American Express or Barclaycard number, and your order will be in the post that night. Or send your order, enclosing cheque, postal order, or stating credit card number and expiry date. For full catalogue showing all CSC products for the engineer and hobbyist send large S.A.E.

CONTINENTAL SPECIALTIES CORPORATION



Europe, Africa, Mid-East: **CSC UK LTD. Dept. M62**
Shire Hill Industrial Estate, Units 1 and 2
Saffron Walden, Essex CB11 3AQ
Telephone Number: SAFFRON WALDEN 21682
TLX 817477

**TO ALL TRADERS, MAIL ORDER HOUSES
CONTACT MRS TINA KNIGHT FOR "PROFIT-PACKAGE" DETAILS**

SUPERSOUND 13 HI-FI MONO AMPLIFIER

A superb solid state audio amplifier. Brand new components throughout. 5 silicon transistors plus 2 power output transistors in push-pull. Full wave rectification. Output approx. 13 watts r.m.s. into 8 ohms. Frequency response 12Hz-20KHz \pm 3db. Fully integrated pre-amplifier stage with

separate Volume, Bass boost and Treble cut controls. Suitable for 8-15 ohm speakers. Input for ceramic or crystal cartridge. Sensitivity approx. 40mV for full output. Supplied ready built and tested, with knobs, escutcheon panel, input and output plugs. Overall size 3" high x 6" wide x 7 1/2" deep. AC 200/250V. **PRICE £16-00, P. & P. £1-20.**

HARVERSON MODEL P.A. TWO ZERO

An advanced solid state general purpose mono amplifier suitable for Public Address system, Disco, Guitar, Gram, etc. Features 3 individually controlled inputs (each input has a separate 2 stage pre-amp). Input 1, 15mv into 47k. Input 2, 15mv into 47k. (suitable for use with mic, or guitar etc.). Input 3 200mv into 1 meg, suitable for gram, tuner, or tape etc. Full mixing facilities with full range bass & treble controls. All inputs plug into standard jack sockets on front panel. Output socket on rear of chassis for an 8 ohm or 16 ohm speaker. Output in excess of 20 watts R.M.S. Very attractively finished purpose built cabinet made from black vinyl covered steel, with a brushed anodised aluminium front escutcheon. For ac mains operation 200/240V. Size approx. 12 1/2" w. x 5" h. x 7 1/4" d. Special introductory Price £28-00 - £2-50 carr. & pkg.



"POLY PLANAR" WAFER-TYPE, WIDE RANGE ELECTRO-DYNAMIC SPEAKER

Size 11 1/2" x 14 1/2" x 1 1/2" deep. Weight 19oz. Power handling 20W r.m.s. (40W peak). Impedance 8 ohm only. Response 40Hz-20KHz. Can be mounted on ceilings, walls, doors, under tables, etc., and used with or without baffle. Send S.A.E. for full details. Only £8-40 each + p. & p. (one 90p, two £1-10). Now available in either 8" round version or 4 1/2" x 8 1/2" rectangular. 10 watts RMS 60Hz-20KHz £5-25 + P. & P. (one 65p, two 75p).

STEREO MAGNETIC PRE-AMP. Sens. 3mV for 100mV out. 15 to 35V neg. earth. Equ. \pm 1dB from 20Hz to 20KHz. Input impedance 47K. Size 1 1/2" x 2 1/2" x 5 1/2" H. £2-60 + 20p P. & P.

2" PLASTIC CONE HF TWEETER 4 ohm, £3-50 per matched pair + 50p P. & P.

MAINS OPERATED SOLID STATE AM/FM STEREO TUNER



200/240V Mains operated Solid State FM AM Stereo Tuner. Covering M.W. A.M. 540-1605 KHz VHF/FM 88-108 MHz. Built-in Ferrite rod aerial for M.W. Full AFC and AGC on AM and FM. Stereo Beacon Lamp

Indicator. Built in Pre-amps with variable output voltage adjustable by pre-set control. Max o/p Voltage 600mV RMS into 20K. Simulated Teak finish cabinet. Will match almost any amplifier. Size 8 1/2" w x 4" h x 9 1/4" d approx. **LIMITED NUMBER ONLY at £28-00 - £1-50 P. & P.**

10/14 WATT HI-FI AMPLIFIER KIT

A stylishly finished monaural amplifier with an output of 14 watts from 2 EL84s in push-pull. Super reproduction of both music and speech with negligible hum. Separate inputs for mike and gram allow records and announcements to follow each other. Fully shrouded section wound output transformer to match 3-15 Ω speaker and 2 independent volume controls, and separate bass and treble controls are provided giving good lift and cut. Valve line-up 2 EL84s, ECC83, EF86 and EZ80 rectifier. Simple instruction booklet 25p + SAE (Free with parts). All parts sold separately. **ONLY £15-50, P. & P. £1-40.** Also available ready built and tested £20-00, P. & P. £1-40.

STEREO DECODER

SIZE 2" x 3" x 1" ready built. Pre-aligned and tested for 9-16V neg. earth operation. Can be fitted to almost any FM VHF radio or tuner. Stereo Beacon light can be fitted if required. Full details and instructions (inclusive of hints and tips) supplied. £6-00 plus 20p. P. & P. Stereo Beacon light if required 40p extra.

SPECIAL OFFER

Slightly shop soiled radios by well-known manufacturer for AC Mains or battery use. MW and FM bands. Dynamic M/coil speakers, telescopic aerial and internal ferrite aerial. Earpiece socket for personal listening. Finished in attractive simulated leatherette. Size 7 1/2" x 9 1/2" W x 4" D approx. Fully guaranteed. Bargain price of only £10-00 - £1-30 p. & p.

MODEL FL4
Few only similar to above, but battery operation only and fitted with twin speakers. Four wave bands. MW, FM and two VHF bands for reception of aircraft and some public services. **ONLY £9-50 - £1-30 p. & p.**

VYNAIR & REXINE SPEAKERS & CABINET FABRICS app. 54 in. wide. Our price £2-00 yd. length. P. & P. 50p per yd. (min. 1 yd.). S.A.E. for samples.

HARVERSONIC SUPERSOUND 10 - 10 STEREO AMPLIFIER KIT

A really first-class Hi-Fi Stereo Amplifier Kit. Uses 14 transistors including Silicon Transistors in the first five stages on each channel resulting in even lower noise level with improved sensitivity. Integral pre-amp with Bass, Treble and two Volume Controls. Suitable for use with Ceramic or Crystal cartridges. Very simple to modify to suit magnetic cartridge—instructions included. Output stage for any speakers from 8 to 15 ohms. Compact design, all parts supplied including drilled metalwork, high quality ready drilled printed circuit board with component identification clearly marked, smart brushed anodised aluminium front panel with matching knobs, wire, solder, nuts, bolts—no extras to buy. Simple step by step instructions enable any constructor to build an amplifier to be proud of. Brief specification: Power output: 14 watts r.m.s. per channel into 5 ohms. Frequency response: \pm 3dB 12-30,000 Hz Sensitivity: better than 80mV into 1M Ω . Full power bandwidth: \pm 3dB 12-15,000 Hz. Bass boost approx. to \pm 12dB. Treble cut approx. to -16dB. Negative feedback 18dB over main amp. Power requirements 35v. at 1-0 amp. Overall Size 12" w. x 8" d. x 2 1/4" h. Fully detailed 7 page construction manual and parts list free with kit or send 25p plus large S.A.E. **AMPLIFIER KIT £14-50 P. & P. 80p** (Magnetic input components 33p extra) **POWER PACK KIT £6-00 P. & P. 95p** **CABINET £6-00 P. & P. 95p** **SPECIAL OFFER—only £25-00 if all 3 items ordered at one time plus £1-25 p. & p.** Full after sales service **Also avail. ready built and tested £31-25, P. & P. £1-50.**

HARVERSONIC STEREO 44

A solid state stereo amplifier chassis, with an output of 3-4 watts per channel into 8 ohm speakers. Using the latest high technology integrated circuit amplifiers with built in short term thermal overload protection. All components including rectifier smoothing capacitor, fuse, tone control, volume controls, 2 pin din speaker sockets & 5 pin din tape rec./play socket are mounted on the printed circuit panel, size approx. 9 1/2" x 2 1/2" x 1" max. depth. Supplied brand new & tested, with knobs, brushed anodised aluminium 2 way escutcheon (to allow the amplifier to be mounted horizontally or vertically) at only £10-00 plus 50p P. & P. Mains transformer with an output of 17v a/c at 500mA can be supplied at £2-00 + 40p P & P if required. Full connection details supplied.

All prices and specifications correct at time of press and subject to alteration without notice.

PLEASE NOTE: P. & P. CHARGES QUOTED APPLY TO U.K. ONLY. SEND SAE WITH ALL ENQUIRIES.

HARVERSON SURPLUS CO. LTD. (Dept. P.W.) 170 MERTON HIGH ST., LONDON, S.W.19. Tel.: 01-540 3985
A few minutes from South Wimbledon Tube Station. **Open 9.30-5.30 Mon. to Fri. 9.30-5 Sat. Closed Wed.**

Electronics. Make a job of it....

Enrol in the BNR & E School and you'll have an entertaining and fascinating hobby. Stick with it and the opportunities and the big money await you, if qualified, in every field of Electronics today. We offer the finest home study training for all subjects in radio, television, etc., especially for the CITY AND GUILDS EXAMS (Technicians' Certificates); the Grad. Brit. I.E.R. Exam; the RADIO AMATEUR'S LICENCE; P.M.G. Certificates; the R.T.E.B. Servicing Certificates; etc. Also courses in Television; Transistors; Radar; Computers; Servo-mechanisms; Mathematics and Practical Transistor Radio course with equipment. We have OVER 20 YEARS' experience in teaching radio subjects and an unbroken record of exam successes. We are the only privately run British home study College specialising in electronics subjects only. Full details will be gladly sent without any obligation.



Become a Radio Amateur.

Learn how to become a radio-amateur in contact with the whole world. We give skilled preparation for the G.P.O. licence.

Free!

Brochure without obligation to:

British National Radio & Electronic School


P.O. Box 156, Jersey, Channel Islands.

NAME _____
ADDRESS _____

Block caps please

ANNOUNCING

THE NEW EUROREADBOARD

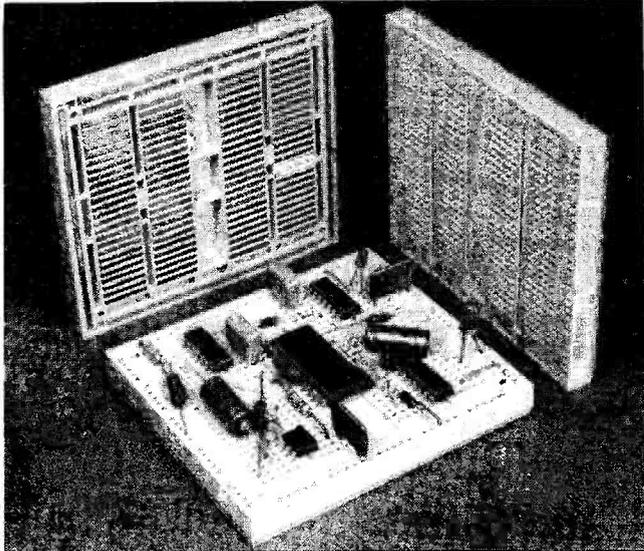

Logically laid out to accept both 0.3" and 0.6" pitch DIL packages as well as Capacitors, Resistors, LED's, Transistors and components with leads up to .85mm dia.

500 individual connections in the central breadboarding area, spaced to accept all sizes of DIL package without running out of connection points.

4 Integral Power Bus Strips around all edges for minimum inter-connection lengths.

Double-sided, nickel silver contacts for long life (10K insertions) and low contact resistance (< 10m.ohms)

Easily removable, non-slip rubber backing allows damaged contacts to be rapidly replaced.

What other breadboarding system has as many individual contacts, offers all these features and only costs £5.80 inclusive of VAT and P.P. - NONE.

At £5.80 each The EuroBreadBoard is unique value for money. At £11 for 2 The EuroBreadBoard is an indispensable design aid.

Snip out and Post
David George Sales, r/o 74 Crayford High St., Crayford, Kent, DA1 4EF

David George Sales
r/o 74 Crayford High Street,
Crayford, Kent, DA1 4EF.

Please send me 1 EuroBreadBoard @ £5.80 Please
or 2 EuroBreadBoards @ £11.00 Tick

(All prices include VAT and P.P., but add 15% for overseas orders).

Name

Company

Address

.....

.....

Tel. No. PW479

Please make cheque/P.O.'s payable to David George Sales

Technical Training in Radio, Television and Electronics

ICS have helped thousands of ambitious people to move up into higher paid, more secure jobs in the field of electronics—now it can be your turn. Whether you are a newcomer to the field or are already working in the industry, ICS can provide you with the specialised training so essential to success.

Personal Tuition and Guaranteed Success

The expert and personal guidance by fully qualified tutors, backed by the ICS guarantee of tuition until successful is the key to our outstanding record in the technical training field. You study at the time and pace that suits you best and in your own home. In the words of one of our many successful students: "Since starting my course, my salary has trebled and I am expecting a further increase when my course is completed."

City and Guilds Certificates

Excellent job prospects await those who hold one of these recognised certificates. ICS can coach you for:

- Telecommunications Technicians
- Radio, TV Electronics Technicians
- Technical Communications
- Radio Servicing Theory
- Radio Amateurs
- Electrical Installation Work
- Also MPT Radio Communications Certificate

Diploma Courses

- Colour TV Servicing
- Electronic Engineering and Maintenance
- Computer Engineering and Programming
- Radio, TV and Audio, Engineering and Servicing
- Electrical Engineering, Installations and Contracting

Qualify for a New Career

Home study courses for leading professional examinations and diploma courses for business and technical subjects:—

- | | | |
|--------------|-------------|--------------|
| G.C.E. | Engineering | Purchasing |
| 60 subjects | Farming | Sales |
| at "O" & | Heating | Storekeeping |
| "A" levels | Industrial | Work Study |
| Accountancy | Management | |
| Air | Mechanical | |
| Conditioning | | |
| Building | | |

POST OR PHONE TODAY FOR FREE BOOKLET.

ICS To: International Correspondence Schools

SINCE 1890
Dept F276 Intertext House, London
SW8 4UJ or telephone 622 9911

Subject of Interest

Name

Address

.....

Telephone Number

Quality audio modules and accessories for

S450

STEREO FM TUNER
Fitted with phase lock-loop
£23.24
+ 48p p&p
+ 12½% VAT



FREQUENCY RANGE	88-108 Mhz
SENSITIVITY	3.0 µV
BANDWIDTH	250 kHz
SPURIOUS REJECTION	50 dB
SELECTIVITY ± 400 KHZ	55 dB
AUDIO OUTPUT (22.5 kHz deviation)	100 mV
STEREO SEPARATION	30 dB
SUPPLY REQUIREMENTS	20 to 30V (90mA max)
AERIAL IMPEDANCE	75 ohms
DIMENSIONS	240mm x 110mm x 32mm

The S450 Tuner provides instant programme selection at the touch of a button ensuring accurate tuning of 4 pre-selected stations. Any of which may be altered as often as you choose, simply by changing the settings of the pre-set controls. Features include FET input stage. Vari-Cap diode tuning. Switched AFC LED Stereo Indicator.

Stereo 30

COMPLETE AUDIO CHASSIS
£19.18
+ 66p p&p
+ 12½% VAT



OUTPUT POWER	7 Watts RMS
LOAD IMPEDANCE	8 ohms
TOTAL HARMONIC DISTORTION	Less than .5% (Typically .3%)
FREQUENCY RESPONSE	50 Hz to 20 kHz ± 3dB
tone control range	± 12 dBs at 100Hz and 10kHz
SENSITIVITY	190 mV for full output
INPUT IMPEDANCE	1 M ohms
TRANSFORMER REQUIREMENTS	22 V. A.C. rated at 1A
DIMENSIONS (Less controls and panel)	200mm x 130mm x 33mm

The Stereo 30 comprises a complete stereo pre-amplifier, power amplifiers and power supply. This, with only the addition of a transformer or overwind will produce a high quality audio unit suitable for use with a wide range of inputs i.e. high quality ceramic pick-up, stereo tuner, stereo tape deck etc. Simple to install, capable of producing really first class results, this unit is supplied with full instructions, black front panel, knobs, main switch, fuse and fuse holder and universal mounting brackets.

AL60

AUDIO AMPLIFIER MODULE
25 Watts RMS
£4.69
+ 35p p&p
+ 12½% VAT



OUTPUT POWER	25 Watts RMS
SUPPLY	30-50 V
LOAD IMPEDANCE	8-16 ohms
TOTAL HARMONIC DISTORTION	Less than .1% (Typically .06%)
FREQUENCY RESPONSE	20 Hz to 30 kHz x 2 dBs
SENSITIVITY	280 mV for full output
MAX. HEAT SINK TEMPERATURE	90°C
DIMENSIONS	103mm x 64mm x 15mm

This high quality audio amplifier module is for use in audio equipment and stereo amplifiers and provides output powers up to 25 RMS with distortion levels below 0.1%.

AL80

AUDIO AMPLIFIER MODULE
35W R.M.S.
£7.34*
+ 35p p&p
+ 8% VAT



OUTPUT POWER	35 Watts RMS
SUPPLY	40-60 V
LOAD IMPEDANCE	8-16 ohms
TOTAL HARMONIC DISTORTION	Less than .1% (Typically .06%)
FREQUENCY RESPONSE	20 Hz to 30 kHz x 2 dBs
SENSITIVITY	280 mV for full output
MAX. HEAT SINK TEMPERATURE	90°C
DIMENSIONS	103mm x 64mm x 15mm

The AL80 is similar in design to the AL60 above and is of the same high quality but provides output powers up to 35W with distortion levels below 0.1%.

AL250

POWER AMPLIFIER
125W R.M.S.
£17.82*
+ 66p p&p
+ 8% VAT



OUTPUT POWER	125 Watts RMS continuous
OPERATING VOLTAGE	50-80 V
LOADS	4-16 ohms
FREQUENCY RESPONSE	25 Hz to 20 kHz measured at 100 Watts
SENSITIVITY FOR 100 WATTS	450 mV
O/P AT 1 kHz	33 K ohms
INPUT IMPEDANCE	33 K ohms
TOTAL HARMONIC DISTORTION	0.1% 50 WATTS into 4 ohms 0.06% 50 WATTS into 8 ohms

This unit, designated AL250, is a power amplifier providing an output of up to 125W RMS, into a 4 ohm load.

AL30A

AUDIO AMPLIFIER MODULES
10W R.M.S.
£3.79
+ 35p p&p
+ 12½% VAT



MAXIMUM SUPPLY VOLTAGE	30 V
POWER OUTPUT for 2% THD	10 Watts RMS
TOTAL HARMONIC DISTORTION	Less than .25%
LOAD IMPEDANCE	8-16 ohms
INPUT IMPEDANCE	100 K ohms
FREQUENCY RESPONSE	50 Hz-25 kHz ± 3 dBs
SENSITIVITY	75 mV for full output
DIMENSIONS	74mm x 63mm x 28mm

These low cost 10 watt modules offer the utmost in reliability and performance, whilst being compact in size.

SPM80

STABILISED POWER SUPPLY
£4.40
+ 35p p&p
+ 12½% VAT



INPUT A.C. VOLTAGE	33-40V
OUTPUT D.C. VOLTAGE	33 V nominal
OUTPUT CURRENT	10 mA-1.5 amps
OVERLOAD CURRENT	1.7 amps approx.
DIMENSIONS	105mm x 63mm x 30mm

Designed to power two AL60s at 15 Watts per channel simultaneously. Circuit Techniques include full short circuit protection.

PA100

STEREO PRE-AMPLIFIER
£16.05
+ 40p p&p
+ 12½% VAT



FREQUENCY RESPONSE	20 Hz to 20 kHz x 1 dB
TOTAL HARMONIC DISTORTION	Less than .1% (Typically .07%)
SENSITIVITY	1. TAPE 100 mV/100 K ohms 2. RADIO TUNER 100 mV/100 K ohms 3. MAGNETIC P.U. 3.5 mV/50 K ohms 250 mV
EQUALISATION	Within ± 1 dB from 20 Hz to 20 kHz
BASS CONTROL RANGE	± 15 dBs at 75 Hz
TREBLE CONTROL RANGE	+ 10-20 dBs at 15 kHz
SIGNAL/NOISE RATIO	Better than 65 dBs (All inputs)
INPUT OVERLOAD	Better than 26 dBs (All inputs)
SUPPLY	20 to 40 V
DIMENSIONS	300 x 90 x 33mm (less controls)

A top quality stereo pre-amplifier and tone control unit, the PA100 provides a comprehensive solution to the front end requirements of stereo amplifiers or audio units. The six push button selector switch gives a choice of inputs together with two filters for high and low frequencies.

MPA30

MAGNETIC CARTRIDGE PRE-AMPLIFIER



Enjoy the quality of a magnetic cartridge with your existing ceramic equipment using the MPA 30 which is a high quality pre-amplifier enabling magnetic cartridges to be used where facilities exist for the use of ceramic cartridges only.
£2.98
+ 35p p&p
+ 12½% VAT

SENSITIVITY	3-5 mV for 100 mV output
EQUALISATION	Within ± 1 dB from 20 Hz to 20 kHz
INPUT IMPEDANCE	50 K ohms
SUPPLY	18 to 30 V-re earth
DIMENSIONS	110 x 50 x 25mm (inc DIN socket)

PA12

STEREO PRE-AMPLIFIER



The PA12 Stereo Pre-Amplifier chassis is designed and recommended for use with the AL 20/30 Audio Amplifier Modules, the PS12 power supply and the T538 Transformer. Features include on/off volume, Balance, Bass and Treble controls. Complete with tape output.
£7.78
+ 35p p&p
+ 12½% VAT

FREQUENCY RESPONSE	20 Hz-20 kHz (-3dB)
BASS CONTROL	± 12 dB at 60 Hz
TREBLE CONTROL	± 14 dB at 10 kHz
INPUT IMPEDANCE	1 Meg. ohm
INPUT SENSITIVITY	300 mV
CROSSTALK	-60 dB
SIGNAL/NOISE RATIO	-65 dB
OVERLOAD FACTOR	± 20 dB
TAPE OUTPUT IMPEDANCE	25 K ohms
DIMENSIONS	152mm x 84mm x 25mm

PS12 POWER SUPPLY MODULE

Power supply for AL20A-30A, PA12, S450 etc. Transformer T538.

Input A.C. Voltage 15-20V. Output D.C. Voltage 22-30V approx. (Dependent upon input.) Output Current 800mA maximum. Dimensions 60 x 43 x 26mm.



£1.90
+ 12½% VAT + 35p p&p.

BP124 SIREN ALARM MODULE

American Police sreamer powered from any 12 volt supply into 4 or 8 ohm speaker. Ideal for car burglar alarm, freezer break-down, and other security purposes.



ONLY £3.50
+ 8% VAT + 35p p&p. 5 WATTS

MA60 HI-FI AMPLIFIER KIT

Build your own top quality amplifier, save yourself pounds. The MA60 kit comprises the following Bi-Kits modules, 2 x AL60 amps, 1 x PA100 pre-amp, 1 x SPM80 stab. power supply, 1 x BMT80 trans. giving 15 watts RMS per channel STEREO. All modules covered by the BI-PAK satisfaction or money back guarantee. Details of the above modules are in this ad. Price £32.00 + 12½% VAT + 82p p&p.

TC60 KIT

A beautifully designed genuine TEAK WOOD veneered cabinet to put the professional touches to your home built amplifier. Full set of parts incl. Front & Back Panels, Knobs, Chassis, Fuses, Sockets, Noen, etc. Ideal for the MA60. Size: 425mm x 290mm x 95mm. Price £19.95 + 12½% VAT + 86p p&p

TRANSFORMERS

T538 For use with S.450 AL30A MPA30 Order No. 2036 Price: £3.20 + 55p p&p + 12½% VAT
T2050 For use with Stereo 30 Order No. 2050 Price: £3.25 + 55p p&p + 12½% VAT
BMT80 For use with AL60 SPM80 Order No. 2034 Price: £5.40 + 86p p&p + 12½% VAT
BMT250 For use with AL250 Order No. 2035 Price: £6.35 + £1.10 p&p + 12½% VAT
2040. For use with AL60 Order No. 2040 Price: £5.20 + 80p p&p + 12½% V.A.T.
2041. For use with AL80, AL120 and AL250 Order No. 2041. Price: £6.30 + 86p p&p + 12½% V.A.T.

CASES

TEAK 30. 32 x 23 x 8cm. designed mainly for use with our stereo 30 Audio System but has proved very helpful to home constructors. Fitted with solid uncut front and back. o/n 139. £5.95. + 12½% V.A.T. p&p 70p.
TEAK 60. 42 x 29 x 9cm. for use with AL60/MK60 Audio Kit. Useful for the home constructor requiring an amplifier sleeve - has no front or back panel. o/n 140. £7.00. + 12½% V.A.T. p&p 85p.


Professionals and Enthusiasts from BI-PAK

AL120

AUDIO AMPLIFIER
(With integral heat sink and short-circuit protection).

£11.95

+ 8% V.A.T. P. & P. 35p

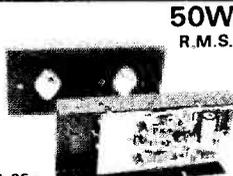

50W R.M.S.

Introduced to fulfill the demand for a fully protected power amp. capable of driving high quality speaker systems at up to 50watts, with distortion levels below 05%. Ideal for domestic use, Discos, P.A. systems, electronic organs etc. The generously rated components ensure continuous operation at high output levels.

OUTPUT POWER	50 Watts R.M.S.
SUPPLY	70 Watts
LOAD IMPEDANCE	8-16 ohms
TOTAL HARMONIC DISTORTION	05% Max. (Typically 02%)
FREQUENCY RESPONSE	25Hz-20KHz
SENSITIVITY	500mV
MAX HEAT SINK TEMP.	45 deg. C
DIMENSIONS	192 x 89 x 49 mm

ADAPTORS

AC-DC enables a large range of battery powered radios, recorders, calculators to be run off the mains. (220-240V AC) Switchable for 6, 7.5 or 9 volts. Current rating 2.500mA. Polarity reversing switch. Universal plug incorporated. **o/n 137 £3.80**, + 12 1/2% V.A.T. p&p 35p.

DC-DC for use in all cars, boats etc., with pos. or neg. earth for a regulated output of 6, 2.5 or 9 volts DC at 1A max. For radios, recorders etc. **o/n 138. £2.80**, + 12 1/2% V.A.T. p&p 35p.

CROSSOVER NETWORKS

2-WAY channels for high and low frequencies to correct speakers - high to tweeters, low to woofers. Complete with instructions. Frequency: 3,000Hz. **o/n 190A. £1.10**, + 12 1/2% V.A.T. p&p 35p.

2-WAY for 8 ohm speakers up to 30 watts. Frequency: .3KHz. **o/n 190S. £1.65**, + 12 1/2% V.A.T. p&p 35p.

3-WAY for 8 ohms speakers up to 30 watts. Frequency: 800Hz and 4.5KHz. **o/n 190E. £2.95**, + 12 1/2% V.A.T. p&p 35p.

MICROPHONES

DYNAMIC CASSETTE
For equipment requiring a high quality microphone. Sturdy, solid mounted body with 1 1/2" battery with neat chrome surround. Pick-up pattern omnidirectional. On/Off switch, 1 metre of tough lead with floating 2.5 and 3.5mm plugs. Matching moulded stud. Impedance: 200 ohms. Sensitivity: 90dB. Frequency: 90-10,000Hz. Size: 20mm dia x 120mm. **o/n 132E. £1.60** + 12 1/2% V.A.T. p&p 35p.

DYNAMIC MICROPHONE
Superior quality portable cassette recorder mike with built-in remote control switch and lead fitted with 5-pin 240° DIN plug (remote switch) and 3-pin DIN plug (microphone). Provides a direct replacement for those supplied with recorders. With detachable stand. Omnidirectional. Impedance: 200 ohms. Freq. response: 100 to 10,000Hz. Sensitivity: 79dB at 1,000Hz. **o/n 132T. £2.65**, + 12 1/2% V.A.T. p&p 35p.

RE - 317: DYNAMIC MICROPHONE
Highly sensitive, high-grade desk or hand mike suitable for use with many popular cassette decks. Incorporates On/Off switch and 1 metre lead with moulded standard jack plug. Complete with desk stand. Omnidirectional. Impedance: 5,000 ohms. Freq. response: 100 to 12,000Hz. Sensitivity: (-7dB at 1,000Hz). **o/n 133E. £4.00**, + 12 1/2% V.A.T. p&p 35p.

OMNIDIRECTIONAL CARDIOID
Powered by a 1 1/2" battery located within the aluminium body. Satin silver finish with front disk protection to the diaphragm housing. On/Off switch. Also with 'Busby' type windshield. "U" bracket and stem and extremely supple cable. Consumption: 0.2mA from 1 1/2" battery providing approx. 8-10,000 hours continuous life. Impedance: 600 ohms. Sensitivity: 70dB. Frequency: 30-16,000Hz. Size: 23mm dia x 267mm. **o/n 132B. £12.80**, 12 1/2% V.A.T. p&p 35p.

UNIDIRECTIONAL CARDIOID
Dual imp. 600 and 50,000 ohms. Response 50 to 14,000Hz. Sensitivity 54dB at 50K/ohms. Size: 1 1/2" dia x 6 1/2" long. Weight approx. 190gm. **o/n 132B. £10.95**, + 12 1/2% V.A.T. p&p 35p.

STANDS

GOOSENECK CHROME FLEXIBLE HOLDERS
Length 320mm. **o/n 133X. £2.40**, + 12 1/2% V.A.T. p&p 35p.
Length 515mm. **o/n 133A. £3.40**, + 12 1/2% V.A.T. p&p 35p.

FLOOR STAND Heavy chrome. Stow-away feet with rubber ends for maximum stability. Draws to a height of 5' maximum. **o/n 133S. £9.50**, 12 1/2% V.A.T. p&p 85p.

BOOM ARM for use with the above stand. Heavy chromed metal. It gives 30" reach from the stand. **o/n 133T. £9.20**, + 12 1/2% V.A.T. p&p 70p.

WINDSHIELD COVERS

o/n 1331 Medium per pair **£1.20**, + 12 1/2% V.A.T. p&p 35p. **o/n 1332 Large** per pair **£1.80**, + 12 1/2% V.A.T. p&p 35p.

SPM120

STABILISED POWER SUPPLIES

SPM120/45
SPM120/55
SPM120/65

£5-80

+ 12 1/2% V.A.T. P. & P. 35p



SPM120 is a fixed voltage stabiliser available with an output voltage of either 45v, 55v, or 65v. Designed primarily for use in audio applications, the stabiliser which provides output currents up to 2.5A., operates direct from a mains transformer requiring only the addition of 2 Electrolytic capacitors to complete the s/c protection.

AC INPUTS	
SPM120/45	40-48v
SPM120/55	50-55v
SPM120/65	60-65v
OUTPUT CURRENT	2.5A
RIPPLE	1A 100mV 2A 150mV

GE100 Mk2.

10 CHANNEL MONOGRAPHIC EQUALISER

£20.00

+ 12 1/2% V.A.T. P. & P. 35p



Only 155mm x 65mm x 50mm including the 10 x 10K 1in slider potentiometers and knobs which are mounted on a board positioned above the circuitry. In the frequency range of 31Hz to 20KHz you can cut and boost ± 12 dB with the 10 sliders, each of which has its frequency marked on the circuit board. The GE100 has numerous uses including mixers, P.A. systems and discos. It will also greatly improve the sound reproduction of your existing audio equipment. Power Supply for GE100. **o/d SG30 £3.80**.

Control Range	± 12 dB
Dynamic Range	110dB
Maximum Output	+15dB
Frequency Response	30Hz-20KHz (± 1 dB)
Power Supply	15-0-15v.
Voltage Handling Input	3v R.M.S.
T.H.D.	005%

VPS30

REGULATED VARIABLE STABILISED POWER SUPPLY

£7.60

+ 8% V.A.T. P. & P. 35p



This new versatile Regulated Variable Stabilised Power Supply with short circuit protection and current limiting, is a must for all electronics enthusiasts. It incorporates adjustable voltage from 2V-30V, with a current limiting range of 0-2A. With this module there is no need to build a separate power supply for each of your projects, with the simple addition of a transformer (o/d 2033). 0-1ma (o/d 1310 or 1305), plus a suitable shunt, a voltmeter (o/d 1311 or 1306), a 470ohm pot (o/d 1896), a 4K7 pot (o/d 1899), it can be used again and again as a self-contained bench, power supply, eliminating the use of batteries and thus saving EC's!

AC Input Maximum	25v
Voltage Regulation	2-30v
Regulated Current	0-2A
Incorporating short circuit protection	

PA200

STEREO PRE-AMPLIFIER

£16.55

+ 12 1/2% V.A.T. P. & P. 40p



The PA200 is basically our popular PA100. Modifications have been made to make it compatible with the higher output AL120 and AL250 amplifiers.

FREQUENCY RESPONSE	20Hz to 20kHz x 1dB
TOTAL HARMONIC DISTORTION	Less than 1% (Typically .70%)
SENSITIVITY	1. TAPE 100mV/100 K ohms For an INPUTS 2. RADIO TUNER 100mV/100 K ohms output 3. MAGNETIC P.U. 3.5mV/50 K ohms 500mV
EQUALISATION	Within ± 1 dB from 20Hz to 20KHz
BASS CONTROL RANGE	± 15 dBs at 75Hz
TREBLE CONTROL RANGE	+ 10-20dBs at 15kHz
SIGNAL/NOISE RATIO	Better than 65dBs (All inputs)
INPUT OVERLOAD	Better than 2dBs (All inputs)
SUPPLY	35 to 706v
DIMENSIONS	300 x 90 x 33mm (less controls)

HEADPHONES

A top quality headphone with cushioned earpads and headband. Separate balance/volume controls. Stereo or Mono switch. Impedance: 8 ohms. Frequency: 30-18,000Hz. **o/n 884. £8.70**, + 12 1/2% V.A.T. p&p 70p.

A brilliant compromise between price and performance. Superb stereo reproduction for the newcomer to Hi-Fi. Impedance 8 ohms. Frequency: 30-15,000Hz. **o/n 885. £4.40**, + 12 1/2% V.A.T. p&p 50p.

BIB HI-FI ACCESSORIES

Parallel Tracking GROOV KLEEN
The very latest in automatic record cleaning. Designed to suit all modern single play decks. Simple to fit, it is extremely efficient. Complete with two types of base and three height extensions. **o/n 8101. £3.68**, + 8% V.A.T. p&p 35p.

Cassette Tape Editing Kit
Enables cassette tapes to be edited and joined easily, quickly and accurately. Kit comprises: Tape Splicer #13 (2mm), 2 Precision Tape Cutters, Tape Piercer, 9 Self-adhesive Labels, Reel of Splicing Tape, 3 Winders and removers and instructions, all in a handy wallet. **o/n 811. £2.40**, + V.A.T. p&p 35p.

GROOV-STAT
The BIB Groov-Stat static reducer neutralises the static charge on records and other plastic surfaces. **o/n 8103. £5.45**, + 8% V.A.T. p&p 35p.

Cassette Head Cleaner
Essential for cleaning of tape heads, capstans and rollers. Pack contains Tape Head Applicator and tape head polisher tools. Plus bottle of special formula cleaning fluid and full instructions. **o/n 832. £0.64**, + 12 1/2% V.A.T. p&p 35p.

METERS

Miniature Balance & Tuning Meter
Miniature moving-coil meter for stereo balance indicator, tuning indicator for FM or similar application. Pointer at centre indicates zero or null position. Robust construction. Sensitivity: 100-0-100mA. Dimensions: 23 x 22 x 26mm. **o/n 1318. £1.95** + 8% V.A.T. p&p 35p.



Balance and Tuning Meter
Clear view edgeview meter. Centre zero application. Sensitivity: 100-0-100UA. Dimensions: 45 x 22 x 34mm. **o/n 1319. £2.00**, + 8% V.A.T. p&p 35p.



Miniature Level Meter
Moving coil, for accurate level indication for tape recorders, amplifiers etc. Neat design, rugged construction - will withstand five times rated value. Sensitivity: FSD: 200UA. OdB: 130UA. Dimensions: 23 x 22 x 26mm. **o/n 1320. £2.80**, + 8% V.A.T. p&p 35p.



Vu Meter
Calibrated -20 to +3 and 0-100%, making it suitable for use as a recording level meter or as a power output indicator. Sensitivity: 130UA. Dimensions: 40 x 29mm. **o/n 1321. £2.00**, + 8% V.A.T. p&p 35p.



AUDIO LEADS

- 107 FM Indoor Ribbon Aerial **£0.60**
 - 113 3.5mm Jack plug to 3.5mm jack plug. Length 1.5m **£0.75**
 - 114 5 pin DIN plug to 3.5mm Jack connected to pins 3&5. Length 1.5m **£0.85**
 - 115 5 pin DIN plug to 3.5mm. Jack connected to pins 1&4. Length 1.5m **£0.85**
 - 116 Car aerial extension. Screened insulated lead. Fixed plug & skt. **£1.10**
 - 117 AC mains connecting lead for cassette recorders & radios. 2 metres **£0.68**
 - 118 5 pin DIN phono plug to stereo headphone jack socket **£1.05**
 - 119 2 x 2 pin DIN plugs to stereo jack socket with attenuation network for stereo headphones. Length 0.2m **£0.90**
 - 120 Car stereo connector. Variable geometry plug to fit most car cassette. 8 track cartridge & combination units. Supplied with inline fused power lead and instructions. **£0.60**
 - 123 6.6m Coiled Guitar Lead Mono Jack Plug to Mono Jack Plug BLACK **£1.50**
 - 124 3 pin DIN plug to 3 pin DIN plug. Length 1.5m **£0.75**
 - 125 5 pin DIN plug to 5 pin DIN plug. Length 1.5m **£0.75**
 - 126 5 pin DIN plug to Tinned open end. Length 1.5m **£0.75**
 - 127 5 pin DIN plug to 4 Phono Plugs. All colour coded. Length 1.5m **£1.30**
 - 128 5 pin DIN plug to 5 pin DIN socket. Length 1.5m **£0.80**
 - 129 5 pin DIN plug to 5 pin DIN plug mirror image. Length 1.5m **£1.05**
 - 130 2 pin DIN plug to 2 pin DIN inline socket. Length 5m **£0.68**
 - 131 5 pin DIN plug to 3 pin DIN plug 1&4 and 3&5. Length 1.5m **£0.83**
 - 132 2 pin DIN plug to 2 pin DIN socket. Length 10m **£0.98**
 - 133 5 pin DIN plug to 2 phono plugs. Connected pins 3&5. Length 1.5m **£0.75**
 - 134 5 pin DIN plug to 2 phono sockets. Connected pins 3&5. Length 23cm **£0.68**
 - 135 5 pin DIN socket to 2 phono plugs. Connected pins 3&5. Length 23cm **£0.68**
 - 136 Coiled stereo headphone extension lead. Black. Length 6m **£1.75**
 - 178 AC mains lead for calculators etc. **£0.45**
- Please add 12 1/2% V.A.T. to all the above leads.

BI-PAK
DEPT. PW4, P.O. Box 6, Ware, Herts.

EDITOR

Geoffrey C. Arnold

ASSISTANT EDITOR

Dick Ganderton C. Eng., MIERE

ART EDITOR

Peter Metalli

TECHNICAL EDITOR

Ted Parratt, BA

NEWS & PRODUCTION EDITOR

Alan Martin

TECHNICAL SUB-EDITOR

Peter Preston

TECHNICAL ARTIST

Rob Mackie

ASSISTANT ART EDITOR

Keith Woodruff

SECRETARIAL

Sylvia Barrett
Debbie Chapman

EDITORIAL OFFICES

Westover House,
West Quay Road,
POOLE, Dorset BH15 1JG
Telephone: Poole 71191

ADVERTISEMENT MANAGER

Telephone: 01-261 6671 Roy Smith

REPRESENTATIVE

Telephone: 01-261 6636 Dennis Brough

CLASSIFIED ADVERTISEMENTS

Telephone: 01-261 5762 Colin R. Brown

MAKE UP & COPY DEPARTMENT

Telephone: 01-261 6570 Dave Kerindi

ADVERTISEMENT OFFICES

Kings Reach Tower, Stamford St.,
London, SE1 9LS
TELEX: 915748 MAGDIV-G

Citizen's Band—Yes or No?

THE mention of a Citizens' Band for the UK can be relied upon to generate strong feelings, one way or another, among people with any interest in radio.

This is evident from the letters received in response to J. S Goodier's proposals published in our December issue. A selection of these letters appears on page 29.

On the right, we print the text of a letter sent recently to the Prime Minister by the Citizens Band Association, urging the introduction of a UK CB service on a v.h.f. band. The Association's comments on four arguments against CB, while certainly valid in themselves, leave several questions unanswered. The adoption of a band other than 27MHz has undoubted advantages from the point of view of reducing interference and illegal long-distance working, and providing a boost for the UK electronics industry. But what would be the price of these sophisticated v.h.f. sets? If it's anything like that of hand-portable transceivers operating in the marine or private-mobile v.h.f. and u.h.f. bands, it seems unlikely that many would be sold to private individuals.

If 27MHz equipment continued to be imported and used, then little would have been gained. It is alleged that several thousand 27MHz sets are presently operating regularly in a net in north London, but apart from an occasional prosecution there is little that the Home Office can do to control them. How would that situation be changed by introducing a legal service in parallel, on another band? And no doubt many would plead for the quoted 15 000 existing users to be allowed to continue to operate their sets, though this figure does rather pale into insignificance against the current 66 000 licensed users of radio model control and the numerous radio-paging systems having a long-standing legal right to the 27MHz band in the UK. At the very least, the government would need to introduce legislation banning further imports of 27MHz CB equipment.

Though the Association quotes several US authorities as now backing the use of CB as an aid to road safety, there have in the past been numerous published reports of CB channels being swamped, leaving broken-down road users and others unable to contact assistance. With the present growing contempt for law and order in some sections of the community, it seems unlikely that we would be spared the interfering carriers, high-powered transmitters, obscene language or continuous music which have plagued CB in other countries.

There is no simple answer to these problems, and little use is served by claiming that there is. Whatever solution may be adopted is going to be unpopular with a lot of people.



Peter Metalli—Art Editor

From art school, Peter began his career in a newspaper feature agency in Fleet Street, receiving a solid grounding in drawing and publication methods. He remained there for 17 years, interrupted by four years (1943-47), in which he served in the RAF as a Flight Engineer.

In 1955 Peter joined "George Newnes" (incorporated now within IPC) working in the general art department "servicing" the "Practical Group"

magazines, and from there graduated to his present position in *PW*.

Peter, Gwen his wife, and daughter Angela, have all settled happily in Bournemouth after their move from Essex, following the company's relocation from London to Poole, Dorset.

Married son, Peter, and wife Alice, still back in Essex, have recently made him a proud grandfather.

Interests are model cars and aircraft, stamps, DIY and gardening.

Citizens Band Association



The Rt. Hon. Mr J. Callaghan, MP, PC,
The House of Commons,
London SW1
January 12th, 1979

Dear Prime Minister,

I am writing to you to ask you to reconsider your Government's opposition to the introduction of Citizens Band Radio in this country.

Ireland and ourselves are the only countries left in Europe which do not allow private citizens some form of short range radio communication. While care must be exercised to license a system which offers efficiency without interrupting other services, is it not somewhat repressive to deny the private citizen any access to short range communication in his everyday affairs?

In the past four main arguments have been advanced against CB:

- (i) It may be used by criminals and for undesirable purposes;
- (ii) The administration required to control it would be prohibitively complex;
- (iii) No frequencies exist which might be used for such a purpose; and
- (iv) Those countries which have it wish they did not.

I should like to comment on these objections in order:

- (i) At present any criminals who use CB equipment are unlikely to be heard. As soon as CB is legal, however, the presence of large numbers of CB users ensures that criminals using CB are heard and quite probably located and arrested. In the USA any criminal who is fool enough to try to use CB is almost invariably detected.
- (ii) Modern "silicon chip" technology makes it not only possible but simple to fit every CB set sold, at the factory, with a unique identifying signal which cannot be tampered with without the resources of a microelectronics factory and without which the CB set will not transmit. The extra cost of such identification would be under 50p per set. Such a device makes the identification of CB sets simple and reduces the

administrative costs of a CB service to a low level. It also increases the impracticality of the criminal or anti-social use of CB.

(iii) Although there are no unallocated frequencies available for CB there are many MHz of spectrum throughout the v.h.f. and u.h.f. region which, though allocated, are thoroughly under-used. In particular the 220-240MHz range has unused sectors (some never used since 1944), there is space around 900MHz, and the v.h.f. television channels are now so unused that spectrum there might well become available in the near future. Very little spectrum is needed for a Citizens Band—0.5 to 1MHz would be ample and even 200kHz could provide a reasonable service—and given political will it could be found.

(iv) This last reason is the weakest of all, though frequently advanced in official circles. In the USA it is Federal policy to encourage the use of CB radio because of its contribution to road safety, as a recent memorandum from the Secretary of the Department of Transportation, the Chairman of the Interstate Commerce Commission and the Chairman of the Federal Communications Commission makes plain. Over thirty countries, including a number not noted for their liberal regimes, now have CB and although there are inevitably some problems the benefits so far outweigh them that none regret introducing it.

However, I am not writing to you now to rehearse a dialogue which is some years old. There is at present a real danger of a less satisfactory form of CB being adopted in Britain in the future if action is not taken soon to define a better alternative.


In the past year three organisations, the National Electronics Council, the British Radio Equipment Manufacturers Association and the Electronic Engineering Association, have prepared reports on Citizens Band Radio in Britain. All are agreed that the Government should introduce CB and all are agreed that the American 27MHz a.m. standard used in most countries having CB is unsuitable for a

small, densely-populated island like our own on various grounds including television interference, the probability of the market being swamped by equipment built in the Far East for the American market and the availability of equipment, legitimately manufactured for the 10 metre Amateur service, which can boost 27MHz transmitters to illegally high powers. Instead they (and the Citizens Band Association) propose v.h.f. and frequency modulation (f.m.). Such a system offers many advantages including local manufacture (four British manufacturers are already prepared to manufacture such sets should CB be legalised), minimal interference and higher quality.

However, many people, angered by the continued illegality of CB in Britain, are now importing American and European equipment and using it illegally. The Citizens Band Association estimates that there are now some 15 000 illegal users in this country and that their number is growing by about 1000 per month. If this continues your own or some future Government will be forced, as happened in Australia, to legalise what is being done. There will then be no possibility of introducing a more sophisticated system or such controls as the automatic identification mentioned above—it will be necessary to legalise another American-style system with most of the American problems. The CBA would prefer such a system to none at all but we feel that we would have missed a golden opportunity of leading the World into a new generation of Citizens Band Radio.

I therefore most earnestly urge you to reconsider your Government's opposition to CB and legalise a sophisticated v.h.f. system, with whatever controls you or your advisers may consider necessary, before you or your successors are forced, by pressure of illegal use, to permit the use of American 27MHz equipment.

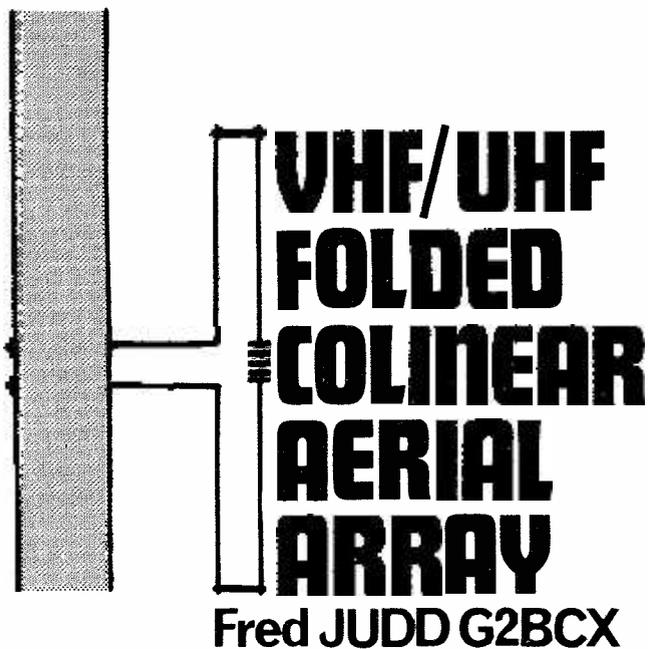Yours sincerely,
James M. Bryant,
President, Citizens Band Association



VHF/UHF FOLDED COLINEAR AERIAL ARRAY

Fred JUDD G2BCX

This aerial is a two-element colinear design for vertically polarised (omni-directional) radiation. It may be constructed for use on either the 2m or 70cm amateur bands and is a development of the very successful "Slim Jim", published in April 1978.

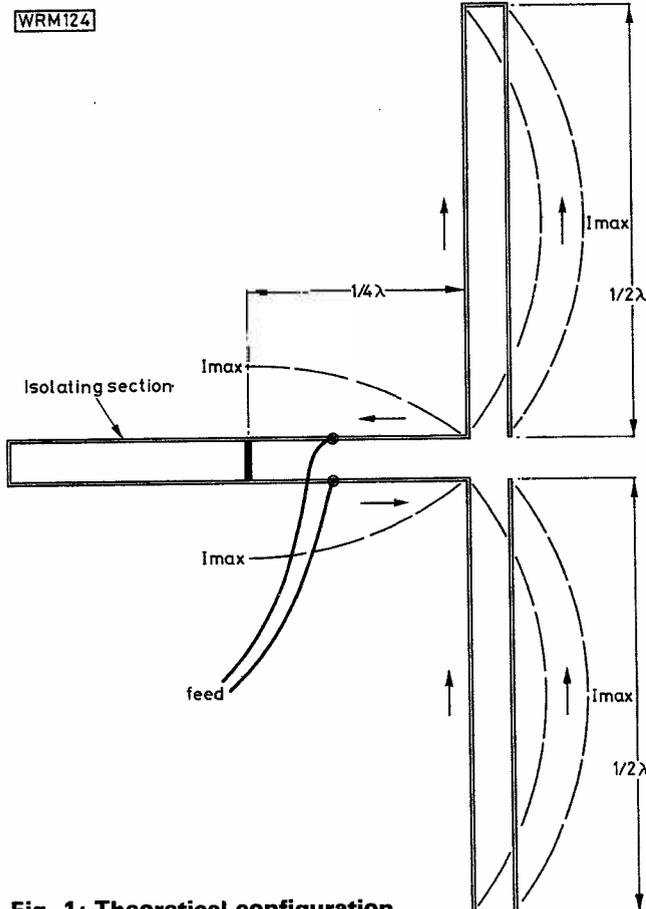


Fig. 1: Theoretical configuration of the colinear array

Two folded half-wave elements driven in phase from a quarter-wave stub constitute the active parts of the device, originally built for use on the Norwich 70cm repeater. The requirement called for a pair of aerials with at least 3dB gain which could be mounted on a mast without undue effect on their omni-directional properties—i.e. with minimal distortion of the otherwise circular radiation pattern.

The theoretical configuration is shown in Fig. 1. Experimentation indicated that the minimum tolerable distance from a metal mast producing the least effect on radiation was 0.625λ . Accordingly, a long stub section is employed which also serves as a supporting mount for the aerial.

The folded radiating elements are voltage driven from a quarter-wave section of the whole stub, the current distribution being indicated by the arrows. The increase in gain over a conventional two-element colinear (gain normally around 1.8dB) is obtained by the use of the folded elements, which contribute an additional 1.6dB. This aerial therefore has a total gain of 3dB over a dipole. Note the break between the return sections, necessary to create a standing wave.

Construction

The diagram of Fig. 2 should provide enough information to enable this aerial to be constructed for either 70cm or 2m, detailed dimensions being given in Table 1. For u.h.f. the aerial will self-support but for v.h.f. some form of boom at right-angles to the mast may be necessary to take the weight of the stub and elements—which are, of course appreciably longer than their u.h.f. counterparts. This could be constructed from wood, and reach at least as far as the quarter-wave section shorting bar. An alternative would be the use of larger diameter tubing for the elements and stubs, say 12.7mm ($\frac{1}{2}$ in).

Connections to the feed point must be protected from rain and the prototype used an oblong plastic box with tight-fitting lid for this purpose. The insulator linking the two folded element sections should be of high quality material, such as ptfе, which is drilled to fit over the ends.

A piece of aluminium about 10mm square may be used for the quarter-wave shorting bar, drilled to take the stub lines and tapped for the 4BA screws which lock the bar to the lines. Element dimensions are given for both versions, the velocity factor having been taken into account.

Adjustment

When the aerial has been completed it should be set up in fairly clear surroundings, approximately 2 metres above ground, with the full length of feeder cable attached. Adjust the feed tapping points and quarter-wave point (shorting bar) for maximum power and v.s.w.r. All v.h.f. aerials operate most efficiently when high up and clear of rooftops or other obstacles, such as tall trees. This is particularly true in the case of colinears with zero-angle radiation. Sizeable trees in full leaf can attenuate v.h.f. and u.h.f. signals by as much as 20dB when placed in the path of radiation, even in dry weather. Brickwork can reduce signals by 10dB or more.

The vertical angle polar pattern of Fig. 3 was taken from the Author's display unit and clearly shows the radiation characteristics of the u.h.f. prototype.

Fig. 2: Constructional details


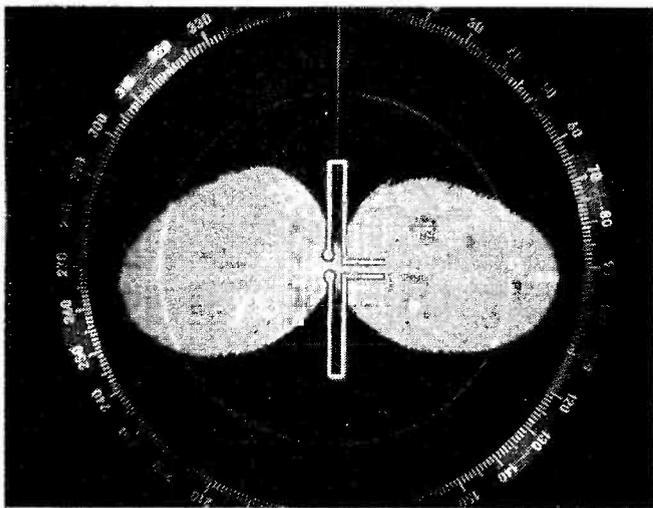


Fig. 3: Vertical polar pattern of the 70cm prototype

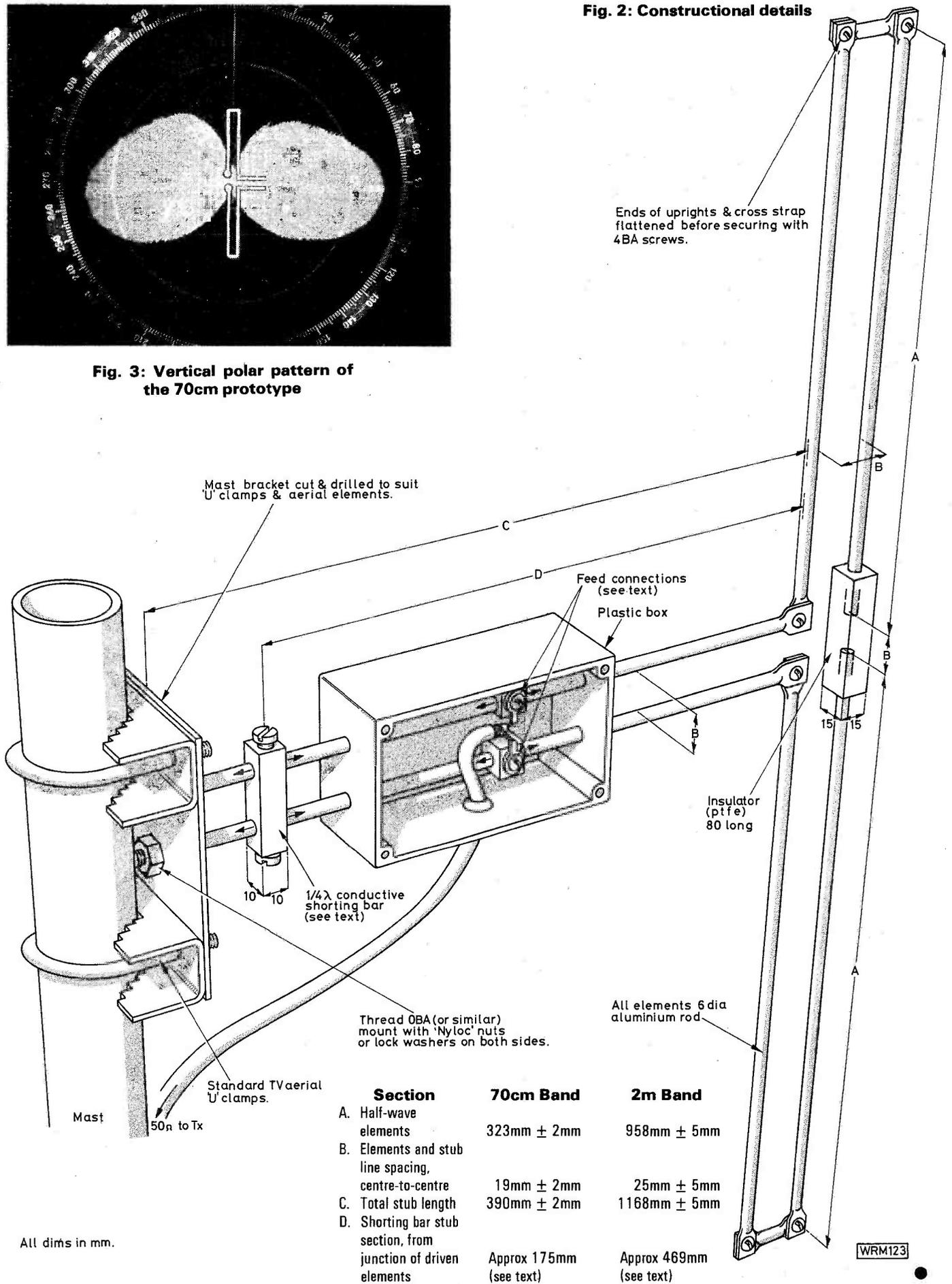

MPU evaluation kit

Now available on an off-the-shelf basis from DISTRONIC are two low-cost microprocessor development systems for the RCA CDP1800 COSMAC m.p.u. family. Costing £100 (plus VAT), the CDP18S020 evaluation kit is a complete kit of components for building an evaluation board for the CDP1802 COSMAC m.p.u., while the CDP18S021 Microterminal, which costs only £70 (plus VAT), is a low-cost, hand-held, non-hard-copy alternative to a teletypewriter data terminal.

The two systems are ideally suited to combined operation. The evaluation kit represents a valuable first step in the development of COSMAC programs and prototype systems, and incorporates on-board utility read-only memory for terminal control. The Microterminal provides a convenient means of controlling a COSMAC system, reading and modifying memory, and providing hexadecimal input/output capability. *DISTRONIC Ltd., 50-51 Burnt Mill, Elizabeth Way, Harlow, Essex. Tel: (0279) 32947/39701.*

On Station

For those interested in the whole spectrum of broadcasting, two recent publications are relevant. The 1979 "World Radio and TV Handbook", according to its Assistant Editor, contains comprehensive information on the world's transmitters (including recent frequency changes) and details of operating times, languages, DX clubs, time signal broadcasts, and even religious broadcasting organisations. The book is available at a cost of £8.50 from *Billboard Publications, via Argus Books Ltd., 14 St. James Rd., Watford, Herts, at your bookshop.*

"Radio Stations Guide", by B. B. Babani and M. Jay, has been considerably up-dated, and contains basic information on the world's radio broadcast transmitters, with a special supplement covering the changes in long- and medium-wave transmissions in the United Kingdom. This guide is available at a cost of £1.45 direct from the publisher: *Bernard Babani (publishing) Ltd., The Grampians, Shepherd's Bush Rd., London W6 7NF.*

Rally date

The North Midlands Mobile Rally organised by The Midland Amateur Radio Society and The Stoke-on-Trent Amateur Radio Society, will take place on Sunday, 29 April 1979, at Drayton Manor Park near Tamworth, Staffordshire. The Park is located on the A4091, which is within easy reach of the M1, M5 and M6 motorways.

The rally will open at 11.30am and visitors will be made very welcome. There will be a talk-in on 2 metres and 70 centimetres. For further details contact: *Norman Gutteridge G8BHE, 68 Max Road, Quinton, Birmingham B32 1LB. Tel: 021-422 9787.*

Testing m.p.u.s

Programme details and synopses of papers for "Microtest", the Symposium on the testing, maintenance and reliability of microprocessor-based equipment, being held at the University of Sussex, from 4pm on Monday, 2 April 1979, until midday on Thursday, 5 April 1979, have now been finalised.

The papers being presented are from Industry, the Universities, Government Departments, and the Post Office.

The Symposium is being organised by the Society of Electronic and Radio Technicians in association with the IERE and the Microprocessor Application Group of the IEE.

The Symposium will open with a Keynote Address given by Colin Crook, Managing Director of Rank Precision Industries Ltd. on the evening of 2 April.

Further information and registration forms are available from: *The Symposium Secretary (MS), SERT, Faraday House, 8-10 Charing Cross Road, London WC2H 0HP. Tel: 01-240 1152.*

New catalogues

Tirro Electronics, the mail order division of "Ritro" has issued a new, combined, catalogue/price-list/order form, available from them free of charge.

Products listed include a whole range of components from the AMI-COS m.p.u. system, to resistors, diodes and capacitors. Other useful items included are transformers, i.c.s, aerials, tools, books, etc.

Each item is clearly priced (VAT included), with discounts for quantity orders. *Tirro Electronics, Grenfell Place, Maidenhead, Berkshire. Tel: (0628) 36229.*

Chloride Exide have just issued an updated list of their dry batteries and torches.

In twelve A4 pages plus covers, it gives all necessary information about high-power batteries; transistor equipment batteries; calculator batteries; extra power transistor batteries; low and high tension batteries; torch, lamp and special purpose batteries. It also includes an equivalents list, dry battery terminal diagrams and coloured illustrations of the top ten popular types.

Available on request from: *Chloride Automotive Batteries Ltd., Chequers Lane, Dagenham, Essex RM9 6PX.*

Home Radio

Due to a massive rise in the rent asked for their current premises, Home Radio (Components) Ltd., of Mitcham, Surrey are moving to new offices at the end of March. Because of this, they will be unable to maintain their retail counter facilities, and will in future trade by mail order only.

To dispose of some surplus stock items, there will be lots of bargains available **to callers only** in a clearance sale from 24-31 March at the existing address, 9am-5pm daily (close 1pm on Wednesday).

The new postal address for mail order will be notified as soon as possible. For the present, customers should continue to write to: *Home Radio (Components) Ltd., Dept. PW, 234-240 London Road, Mitcham, Surrey CR4 3HD.*

Can I Help You!

Are you the secretary, organiser or general dog's body of your local radio club or any other group whose functions may interest readers of *PW*. If so, let me know and I will endeavour to publicise your rally, get-together whatever, through this column. Remember though, we compile the magazine some time ahead of publication day (e.g. this note was written in mid-January), so, the earlier I can have details, the better.

Alan Martin

J. BIRKETT

Radio Component Suppliers

25 The Strait, Lincoln LN2 1JF. Tel: 20767

400mW ZENERS Unmarked Good 3-6, 6-8, 10, 11, 12, 13, 16, 18, 24, 30, 33, 36v. All at 10 for 40p.
ERIE RED CAP .01uf 100v.w. SUB-MINIATURE CAPACITORS @ 5p each.
BD187 4 Amp NPN PLASTIC POWER NPN TRANSISTORS @ 5 for £1.
MURATA 10-7MHZ CERAMIC FILTERS @ 27p, **VERNITRON FM4 10-7MHZ FILTER** @ 50p, **MURATA 455KHz BFB FILTER** @ 30p.
10 Amp S.C.R.s 100 PIV @ 25p, 400 PIV @ 50p, 800 PIV @ 60p.
DAU TRIMMERS 2 to 3pf @ 10p, 6 to 45pf @ 10p, 0 to 125pf @ 12p, 8 to 140pf @ 15p, **TETTER VHF TRIMMERS** 10pf @ 18p.
VHF POWER TRANSISTORS unmarked Good 2N 3375 @ £1, 2N 3866 @ 3 for 75p, 2N 3853 @ 3 for £1.10.
ELECTROLYTIC CAPACITORS 1000uf 100v.w. @ 50p, 2200uf 100v.w. @ 60p, 3300uf 64v.w. @ 60p, 3300uf 40v.w. @ 50p.
HCGU CRYSTALS 38MHz, 40MHz, 44-3MHz, 45-9MHz, 46-5MHz, 46-7MHz, 48-3MHz, 50-1MHz, All at 50p each.
3 PIN PLUG AND SOCKET like R.S. European Type with Two Metres of Cable @ 75p pair.
10 ASSORTED PUSH BUTTON BANKS less knobs for £1.30.
SUB-MINIATURE TANTALUM 4-7uf 10v.w. @ 5p, 6 for 25p.
50 2 Watt ZENERS assorted untested @ 57p.
DISC CERAMICS .01uf 50v.w. @ 20p doz., 1uf 18v.w. @ 25p doz.
100 MINIATURE DIODES CV 9637 pre-formed leads @ 57p.
VHF FETS 40673T @ 33p, E304 @ 25p, J310 @ 20p, MFE 131 @ 60p, BF 256 @ 25p, 2N 3819T @ 20p.
MINIATURE BUTTERFLY PRE-SET VARIABLE CAPACITORS spindles easily extended 25 x 25pf @ 50p, 38 x 38pf @ 60p, 38 x 38pf Wide Spaced @ 65p.
50 VARI-CAP DIODES LIKE BA 102 untested @ 57p.
200 1/2 Watt RESISTORS assorted for 75p.
MULLARD VARIABLE CAPACITORS Solid Dielectric 195 + 80pf @ 40p.
30 ASSORTED 10XAJ CRYSTALS @ £1.10, **20 FT 243 CRYSTALS** assorted @ £1.50, **20 FT 241A CRYSTALS** assorted @ £1.10.
50 10X CRYSTALS assorted @ £1.50 (P. & P. £1.50).
TRANSISTORS BC 548 @ 10p, 6 for 50p, BC 549 @ 10p, 6 for 50p.
PLASTIC TRIACS 400 PIV 6 Amp @ 60p each.
COIL FORMERS 3/4" Dia. with core at 6 for 25p.
McMURDO 8 PIN PLUGS @ 20p, **8 PIN SOCKETS** @ 20p, **COVERS** @ 15p.
600MHZ FREQUENCY 8 DIGIT COUNTERS HFC600 @ £115.
2 GHz STRIPLINE NPN TRANSISTORS @ £1 each.
100uf 100v.w. WIRE ENDED ELECTROLYTICS 10p, 5 for 35p.
MC 3340 ELECTRONIC ATTENUATOR I.C. with data @ 50p.
1uf 25v.w. ELECTROLYTICS at 6 for 25p.
20 PHOTO TRANSISTORS AND DARLINGTONS assorted untested @ £1.
SOLDER-IN FEED THRU's 6-8pf, 1000pf all 20p doz.
MULLARD T PACK 600MHZ TRANSISTORS BF 362 @ 25p.
CRYSTALS 10X 8010KHz @ 40p, 10XAJ 7010KHz @ 30p.
VARIABLE CAPACITORS 25 x 25 + 25pf 1/2" Spindle direct drive @ 75p.
ELECTRET MICROPHONE INSERTS with FET Pre-amp @ £1.85.
 Please add 20p for post and packing, unless otherwise stated, on U.K. orders under £2. Overseas post at cost.

P.C.B'S FOR

PRACTICAL WIRELESS PROJECTS

Nov. 78.	Sarum Q. Meter	R030	Price £3.30 & 20 pence p & p.
Nov. 78.	Standard Charge Timer	AD212	Price £2.80 & 20 pence p & p.
Nov. 78.	Porch Light Timer	AD222	Price £0.60 & 12 pence p & p.
Nov. 78.	Battery Indicator	AD225	Price £0.60 & 12 pence p & p.
Dec. 78.	Car Radio L.W. Converter	R034	Price £2.35 & 15 pence p & p.
Dec. 78.	Digital Door Chimes	R017	Price £3.78 & 25 pence p & p.
Dec. 78.	Car Radio L.W. Converter	R032	Price £2.62 & 20 pence p & p.
Jan. 79.	Acoustic Delay Line	R018	Price £3.53 & 20 pence p & p.
Jan. 79.	Dorchester	R033	Price £10.80 & 30 pence p & p.
Feb. 79.	Hythe Receiver	WR037	Price £5.94 & 20 pence p & p.
March 79.	Hythe Receiver	WR038	Price £2.70 & 20 pence p & p.
March 79.	Soundlite Converter	WK001	Price £5.98 & 20 pence p & p.
March 79.	Tone Burst Generator	R023	Price £1.60 & 15 pence p & p.
March 79.	Wide Band Noise Souce	WR036	Price £0.70 & 12 pence p & p.

Send order to:

C. BOWES & CO. LTD.,

**4, WOOD STREET,
CHEADLE,
CHESHIRE SK8 1AQ.
Tel. 061-428-4497.**

Please state type number and enclose cheque or postal order.

Can YOUR Antenna do all this?

A SMALL SELECTION FROM OUR HUGE FILE OF TESTIMONIAL LETTERS ON THE JOYSTICK VARIABLE FREQUENCY ANTENNA (1.5-30MHz).

Carl V. Guest, Mount Vernon, Ohio, writes—"I set the Joystick antenna on the floor of my operating room which is at street level. On 40 meter CW I worked out to a distance of 700 miles in the afternoon."

"CQ" Magazine—"If you are high enough the antenna will operate (especially at 15-20) as well as the well-known 3-element beam with which we compared it. The tests were 'operational, not theoretical!' We find that if we can hear 'em we can work 'em—and in most cases with a 100 watts input."

K6MDJ—"Early results are astounding. I've been using a trap dipole for 40-20-15. This JOYSTICK out-performs the dipole 2 x 1."

G3UGB—"Extremely good reports on 160 meters and 80 meters."

W5CJV—"Do I like the JOYSTICK? I guess so! I took five antennae down and now use the Joystick alone?"

IN USE BY AMATEUR TRANSMITTING AND SWL STATIONS WORLD-WIDE AND IN GOVERNMENT COMMUNICATION

JOYSTICK ANTENNAS

SYSTEM "A" £41.00

200 w. p.e.p. OR for the SWL

SYSTEM "J" £47.95

500 w. p.e.p. (Improved "Q" on receive)

"PACKAGE DEALS"

COMPLETE RADIO STATIONS FOR ANY LOCATION

All packages include the JOYSTICK VFA (System "A") 8ft feeder, all necessary cables, matching communication headphones. Delivery Securicor our risk. ASSEMBLED IN SECONDS. You SAVE £14.15 on each PACKAGE DEAL!

PACKAGE No. 1. Features R.300 Rx. **£222.00**

PACKAGE No. 2. Features FRG7 Rx. **£237.45**

PACKAGE No. 3. Features SRX30 Rx. **£212.45**

PACKAGE No. 4. Our "Rolls"—Rx. FRG7000. **£402.00**

RECEIVERS ONLY

R.300	£184.50	FRG7	£199.95
SRX 30	£174.95	FRG 7000	£364.50

All prices are correct at time of going to press and include VAT at 12 1/2% and carriage.




Just telephone
your card number
Phone 0843 62535 (ext. 5)
(or 62839 after
office hours)




or write for details, send 9p stamp



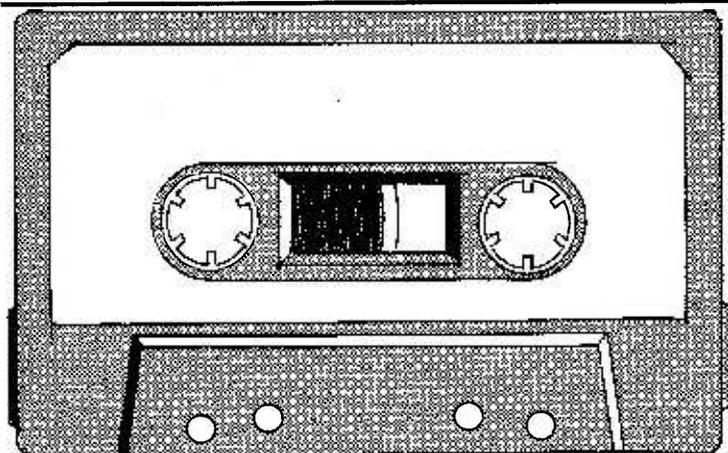5, Partridge House, Prospect Road, Broadstairs, CT10-1LD. (Callers by appointment).



THE CASSETTE TAPE MEDIUM

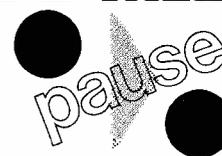

Part 1

Gordon J.KING

Having in mind the minuscule 0.6mm tracks of the Compact Cassette, and the low tape/head velocity of a mere 4.75cm/s, it seems incredible that the medium is currently capable of high quality recording and replay up to frequencies approaching 20kHz, and it is still improving. When the Compact Cassette system was launched by Philips way back in the Fifties the quality by today's hi-fi standards was, frankly, abysmal. The noise floor was little more than 40dB below signal peaks of some 5 per cent distortion, the upper-frequency response commenced rolling-off around 7 to 8kHz, and the wow and flutter figures could easily reach 0.5 per cent or more!

Assisted by the recent noise reduction systems, notably Dolby B, and the new pseudo-chrome (*Cr*) and pure *Cr* tapes, a noise floor as low as 65dB (CCIR/ARM-weighted) relative to an output of 3 per cent 3rd-order distortion threshold is readily achievable at middle frequencies, which is virtually as good as can be expected from the best gramophone records. At the recording levels likely to be experienced in the treble regions by the vast majority of home recordists, the response holds well to frequencies of 15kHz or more (which is the upper limit of most gramophone records and f.m. radio), while dramatic improvements to tape transport mechanisms have decreased the wow and flutter to less than 0.1 per cent DIN-weighted peak.

With these sort of performance figures, therefore, it is little wonder that more audiophiles and music lovers are turning to the cassette deck as a primary source of programme signal, which is regarded as having the edge on the record deck in terms of its recording attribute, if not in absolute music quality.

If a recording is made of a top quality gramophone record or stereo radio programme with a contemporary hi-fi deck using good tape, it is often difficult to determine conclusively whether one is hearing the original or the recording. Yes, the state-of-art is to this standard. Indeed, there are people who claim that the recording sometimes auditions more favourably than the original, which would appear to have significance, in that the replay distortion is "disguising" some of the less palatable distortion plaguing the original programme signal, but this is a different story!

So far as pre-recorded cassettes (e.g., Musicassettes) are concerned, the quality of the equivalent gramophone records is generally better. It is also more convenient to locate a particular track on a disc than on a cassette record, but even this cassette shortfall is being resolved by the microprocessor chip, such as found in the Optonica up-market cassette decks, for quickly locating a required

section of music for replay, without the frustration of having to make experimental fast winds and rewinds.

Cassette Shortcomings

So far, then, it might be supposed that the compact cassette medium no longer has any shortcomings and that all the problems have been resolved. This is certainly not true. For example, the medium cannot yet compete with wider-track reel-to-reel tape running at higher speed. However, with some of the latest tapes the performance can currently exceed that of reel-to-reel tape running at 9.5cm/s, which is a truly remarkably achievement.

When the pure metal particle tapes are more readily available, along with machines to do them full justice, then the improvement will be even more dramatic, and we shall probably be able to obtain the existing cassette performance with a tape speed half that of the existing cassette tape speed! Conversely, by retaining the existing cassette speed, the performance will be lifted virtually to match that of most domestic type reel-to-reel machines running at high speed.

The biggest shortcoming of the cassette medium can be described with one word—compression. A tape can assimilate only a certain amount of magnetism depending on its magnetic properties. If the magnetising force is increased by passing an increasing current through the winding of the recording head, the magnetic flux density of the tape will increase until it can accept no more magnetism. At this point no matter how much more the force is increased there will be no further increase in tape flux. This means that the tape is fully saturated since all the available magnetic domains are then in alignment.

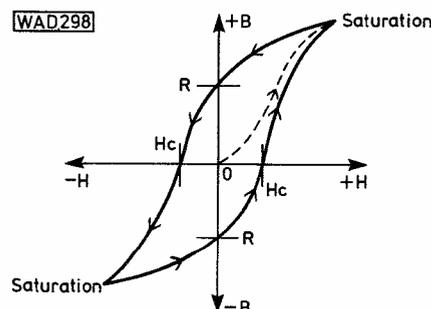


Fig. 1: Hysteresis loop of magnetisation. See text for description

The hysteresis loop in Fig. 1 describes the path taken by flux (B) as the magnetising force (H) is increased first in one direction, decreased, and then increased in the opposite direction. Initially, the flux follows the broken-line up to saturation; it then falls back from saturation as the force is reduced to zero, and rises to saturation in the opposite direction as the force is increased in the opposite direction. The loop shows that after the tape has been magnetised and the force is reduced to zero a flux remains on the tape of value (R) which is, in fact, the magnetism which has been imparted to the tape and retained by it. Points (R) on the loop are called the remanent points and thus signify the remanent magnetism remaining on the tape after the force has been removed.

The loop also shows that once the tape has been magnetised, an opposite field of force H_c is required to pull the remanent flux down to zero again, and hence to demagnetise the tape. This is called the coercive force, so the greater the coercivity of the tape, the better it holds its magnetism and the harder it is to demagnetise, which can be useful, particularly for recording high frequencies.

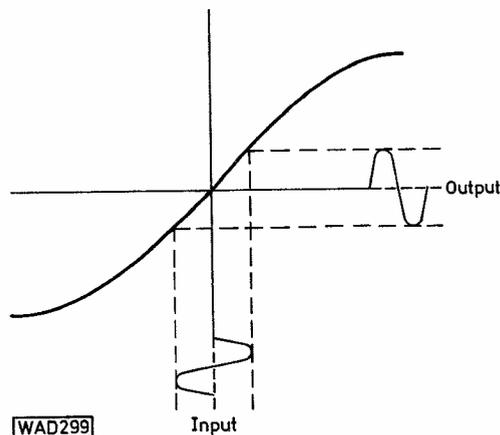


Fig. 2: Transfer characteristic of magnetic tape showing non-linearity of odd-order terms, which is responsible for odd-order distortion on the output signal. The curve takes account of the correction provided by the h.f. bias

Transfer Non-Linearity

To combat the severe non-linearity at low values of magnetising force, the signal for recording is superimposed on a high-frequency sinewave of around 100kHz. This caused the magnetic force, resulting from the signal, to swing on the upper reaches of the two halves of the BH curve, which are more linear than the lower reaches. Even so, the resulting transfer characteristic is still not very linear, particularly as the signal pushes the tape towards saturation, which means that in spite of the recording signal being of very low distortion, the replay signal is bound to carry a greater level of distortion, especially at high recording levels.

The nature of the transfer characteristic, after the improvement by the h.f. biasing has been taken into account, is shown in Fig. 2. As this type of curve contains odd-order terms, most of the distortion is odd-harmonic, such as 3rd, 5th, 7th, etc., harmonic, with the 3rd harmonic predominating. Moreover, because the curve goes more non-linear as the tape approaches saturation, so the 3rd harmonic distortion increases. If the signal being recorded is so strong as to push the tape into saturation, then there can be just as much 3rd- and odd-order distortion as there is fundamental! Hence the reason why cassette recordings sound abysmally poor when they are over-recorded on signal peaks.

The maximum output level (MOL) of a tape refers to the level of flux that it can accommodate up to a specified level of distortion—usually 3 per cent. In the SI units, magnetic flux density is expressed in webers per metre (Wb/m), but as tape flux is so small the expression nWb/m is used, where n is the nano or 10^{-9} multiplying factor. Some idea of the flux level on a tape can be gleaned from the fact that the majority of Japanese cassette decks show +3VU on their meters when the recorded tape flux corresponds to about 200nWb/m which, incidentally, is the Dolby noise reduction reference level. This means, then, that at 0VU the tape flux is about 141.5nWb/m (e.g., 3dB down from 200nWb/m, which is 200×0.707).

The curves in Fig. 3 give some indication of how the 3rd harmonic distortion increases with increasing tape flux, based on the average of five different tapes as used in domestic cassette decks at low, middle and high frequencies. It should be noted that different machines and tapes of different samples might well result in a different distribution. For convenience, lines have been drawn to

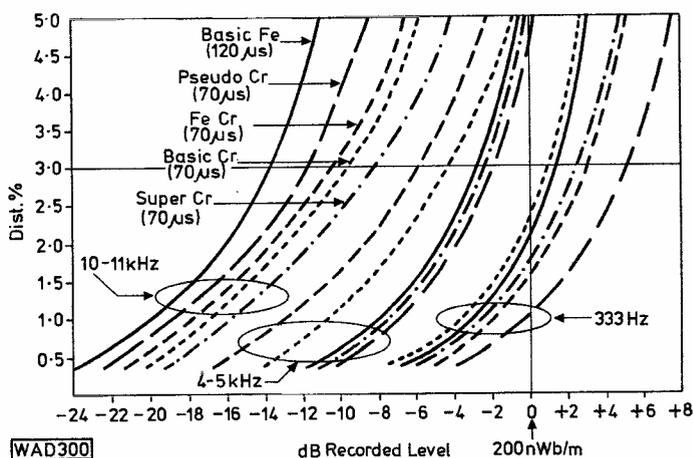


Fig. 3: Curves showing how the distortion increases at three different frequencies as the recorded level and hence the tape flux is increased. The results represent the averages of a number of samples and batches of the tape types indicated, when used with domestic cassette decks

indicate the 0dB 200nWb/m point on the horizontal scale and the 3 per cent distortion point on the vertical scale.

The curves show that with this particular combination the pseudo-Cr tape (such as Maxell UDXL II, TDK SA, etc.) is capable of the greatest flux at the low frequency of 333Hz where, to the 3 per cent distortion point, a flux of +5dB (corresponding to about 356nWb/m) can be accommodated. The basic Fe will only yield about +1dB, basic Cr a trifle less, Cr Super (a recent BASF formulation) about +2.5 (depending on bias), and ferrous-chrome (FeCr) about +3dB. Clearly, then, the pseudo-Cr is a clear winner so far as sheer flux is concerned at l.f.

Although a good deal of music energy and peaks reside at low and middle frequencies, this is not the whole story because high quality music can undoubtedly contain quite high-amplitude transients at much higher frequencies. Looking at the curves applicable to 10–11kHz, it will be seen that the distribution has altered somewhat, for now

the greatest flux is yielded by the Super *Cr* to 3 per cent distortion at about -8dB (80nWb/m). The pseudo-*Cr* is down to about -12dB (50nWb/m), while the basic *Fe* is at the bottom at about -14dB (40nWb/m). The basic *Cr* is quite respectable at -10dB (63nWb/m) and the *FeCr* is not bad at -11dB (56nWb/m). These curves, then, indicate that *Cr* and *FeCr* are good upper-frequency performers.

The middle-frequency curves fail to reveal the upper-frequency attribute of the *Cr* and *FeCr* tapes, since the pseudo-*Cr* is still showing the highest flux at -2dB (159nWb/m). Nevertheless, the Super *Cr* is not far behind, nor is the basic *Cr*. The lowest output is given by the *FeCr* at -6dB (100nWb/m).

These curves, then, signify that as the frequency of the recorded signal increases, so the tape arrives at the beginning of saturation at decreasing levels of flux. If we were to record a tape at a constant level over the frequency spectrum, starting at, say, 200nWb/m at 333Hz , on replay we would find that the flux carried by the tape would gradually decrease with increasing frequency, as shown in Fig. 4. The upper-frequency roll-off of the curve is caused by the progressively increasing compression (that is, the inability of the tape to retain a given high level of magnetic flux as the frequency is increased).

This is the result of self-demagnetisation of the high-frequency, short-wavelength magnetic domains recorded on the tape oxide. For each half-cycle of recording signal the equivalent of a minuscule bar magnet is produced on the oxide, and because the poles get closer together as the frequency of the signal is raised, the ability of the magnet to sustain its strength is diminished.

The recorded wavelength is equal to the tape velocity divided by the frequency in Hz. Thus, at 15kHz and at the cassette speed of 4.75cm/s , the wavelength is a mere $3.16\mu\text{m}$, so each magnet has a length of $1.58\mu\text{m}$. Little wonder, then, that there is a strong tendency towards demagnetisation! It is noteworthy that the length of the gap of the replay head must be of a similar small order fully to define the high-frequency components of the signal.

During recording, pre-emphasis is applied to the signal current fed to the head to help combat the h.f. loss. However, if excessive magnetic force is applied to the tape, the tape tends to demagnetise while it is actually being recorded, which can further worsen the compression distortion at h.f. Tapes which give the best h.f. performance with the least compression and hence h.f. distortion, are those of relatively high coercivity, such as the recent *Cr*, *FeCr* and the latest high-energy *Fe* and pseudo-*Cr* formulations, the first mentioned particularly including the BASF *Cr* Super if the programme material warrants the extra price and the machine can do full justice to the tape.

Although there are more factors involved in tape choice, the performance at h.f. cannot be over-stressed for the adequate recording of high quality material, from microphone channels direct, from electronic music-making devices, and from synthesisers where the peaks and energy at h.f. are likely to be relatively high. For dubbing from gramophone records and f.m. stereo radio, tape choice is less exacting (but it is desirable always to use the best that can be afforded and never cheap non-proprietary brands which can quickly shed their oxide and clog up the head gaps) because of the limited high-frequency energy and signal peaks of this nature of signal.

Although the curve in Fig. 4 is interesting, more useful are those curves which refer a given level of distortion to tape flux over the lower, middle and upper parts of the frequency spectrum. Since odd-order distortion

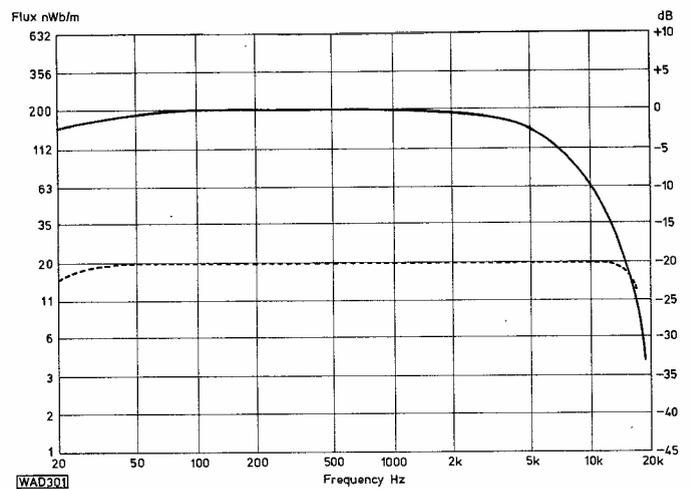


Fig. 4: Compression curve. The magnetic flux assimilated by a tape recorded at high level corresponding to 200nWb/m at 333Hz falls off with frequency as shown. To avoid the effect of compression, the frequency response is taken at a recording level at least 20dB below 200nWb/m , a curve shown by the broken-line is then achieved provided the bias and equalisation are set to suit the tape. If the bias is too low the upper frequencies will tend to show a boost, while if too high the upper frequencies will tend towards early roll-off

predominates (particularly 3rd-order), the distortion measured is 3rd harmonic at l.f. (around 333Hz) and 3rd-order intermodulation distortion at upper-middle ($4\text{--}5\text{kHz}$) and h.f. ($10\text{--}11\text{kHz}$).

There is no difficulty in measuring 3rd harmonic at l.f., for at 333Hz it falls at 999Hz , which is well within the passband of the system. At upper-middle and particularly h.f., the 3rd harmonic is likely to fall outside the passband and be affected by the replay equalisation. To avoid this, two-tone driving signals are used of f_1 and f_2 and the 3rd-order IM products of $2f_1 - f_2$ and $2f_2 - f_1$ measured in ratio to the driving signals. Since there is a mathematical relationship between 3rd harmonic and 3rd-order distortion, perfect correlation is achieved provided due attention is taken of the difference between the crest factors of the single-tone and two-tone signals.

For hi-fi applications, an upper limit distortion threshold of 3 per cent would appear to be appropriate, so the plan, then, is to find the flux assimilation of the tape when used with a specific domestic machine (or batch of such machines—taking the average) over the spectrum for 3 per cent distortion threshold.

NEXT MONTH
Spectral distortion, bias and equalisation, head problems, noise floor and dynamic range

Letters

The Editor,
PRACTICAL WIRELESS,
*Westover House,
West Quay Road, Poole,
Dorset BH15 1JG*

The letter from J. S. Goodier regarding Citizen's Band in the UK, which appeared in our December 1978 issue, provoked a flood of letters from readers. These were fairly evenly divided between "for" and "against" CB. Several writers took violent exception to Mr Goodier's suggestion that part of the 2 metre band should be allocated for novice use, as a substitute for a Citizen's Band in the UK. We print here a selection of the letters received.

Sir: I have recently returned from Australia, where Citizen's Band radio has been legal for just over a year. I feel, however, that the Australian service follows too closely the American service. I also feel that the biggest problem with these two services is that a licence is far too easily obtained, and that a bad frequency band and emission type have been employed. A CB service could be introduced in this country, with heavy modifications to the American system of licensing.

I think that the following would greatly reduce the problems of such a service:

1. Correct radio procedure should be used, with proper station identification at the beginning and end of each transmission; only normal speech should be allowed, such as would be used on the telephone, with no "10-codes", which seem to make up the total vocabulary of many CBers.
2. The 11 metre h.f. band should be maintained, but the frequencies used changed to, say, 26MHz-27MHz (11.538m-11.111m), thus avoiding any overseas contacts. This band can be used in its entirety, perhaps utilising v.f.o. controlled transceivers, and allowing plenty of space for everyone.
3. Emission should be s.s.b. only, avoiding a.m. heterodyning and giving less overcrowding and more signal clarity.
4. A maximum output of 15W p.e.p. to be allowed, with no directional or gain antennas of the beam or quad type.
5. Licensees would be required to undergo an examination on regulations, including possible interference problems and remedies, a procedural test, and show a basic knowledge of antennas for the frequencies used and their alignment.
6. A licence fee of £7 to £10 should be charged and a call-sign allocated once the examination had been passed. A call-sign could take the form SD123W, etc., where SD indicates the county, 123 is the licence number, and W is the initial of the town in which the licensee lives.

I feel that the "Toms, Dicks and Harrys" could be greatly reduced by the initial pre-licensing exam. There is obviously a demand for a service in the UK, so with the appropriate licensing conditions there is no valid reason for such a service to be denied to us.

Gerald Yates
Watcombe
Torquay

Sir: I do not think that Mr Goodier's idea of a novices' amateur band on 144.5-145.0MHz would be accepted by present 2m users. The code-free facility of the present G8-type licence should not be beyond the capability of any interested enthusiasts, and any lowering of the licensing requirements would certainly make channelised f.m. on 2m sound like CB.

Anyhow, quite a lot of the 144.5MHz region and upwards is used for s.s.b. contacts, and 144.90-145.0MHz is used for beacon facilities. As one amateur using s.s.b. on 2m and trying for beacons here in Ireland (both their reception from distant places and their establishment here too), I would not welcome private communication type facilities in the band.

We here in EI (Eire) have just been given the facility of a code-free v.h.f. licence, so we welcome the increased use of 2m throughout the country. Only a small percentage of present amateurs are active on v.h.f. here—the silence has to be heard to be believed.

Perhaps the supporters of a novice type band could try for additional frequency allocations in the v.h.f. spectrum, say, 100-105MHz, 220-225MHz, 400MHz, or some other unused band. Enthusiasm for private communications should be directed positively towards a technical service with technical requirements for operation, and also giving the home electronics industries a chance to manufacture the equipment. Re-crystalling of expensive imported 2m f.m. equipment should be made very, very difficult. CB on 27MHz has caused havoc in the USA, not only from the TV interference aspect but also by upsetting the balance of trade. A novices' v.h.f. band is a possibility for the UK.

Des Walsh EI5CD
Carrick on Suir
Co Tipperary

Sir: Why is it every now and then some crank wants to do something with 2m below 145MHz? First G3RKL wanted to put repeaters and channels for s.s.b. Letters in *Radio Communication* told him where to put them! Now a reader in Stockport wants it for CB.

The 2m band from 145MHz down is for amateur use—true amateur—with DX, RTTY, SSTV and all modes. If our reader gets a good 2m receiver and antenna, he will be able to hear these signals.

The only people we want on the air in G-land are those who have passed the RAE.

John Tye
Dereham
Norfolk

Sir: Your correspondent J. S. Goodier suggests that if a Citizen's Band was permitted in the UK "they will come in their millions".


We must assume more than, say 1 million—perhaps as many as 5 million. If we take the price for an average 2 metre transceiver equipment, let's say £200, then the total market for 5 million sets will be worth £1000 million. On this will be charged 8 per cent VAT, which comes to £80 million. Good grief, man, what is the Chancellor of the Exchequer waiting for?

Who is fooling who? Cut the b*****t and legalise what other sensible countries have already done.

J. Acton
Iver
Bucks

continued on page 67

SIMPLE AUDIO FILTER DESIGN

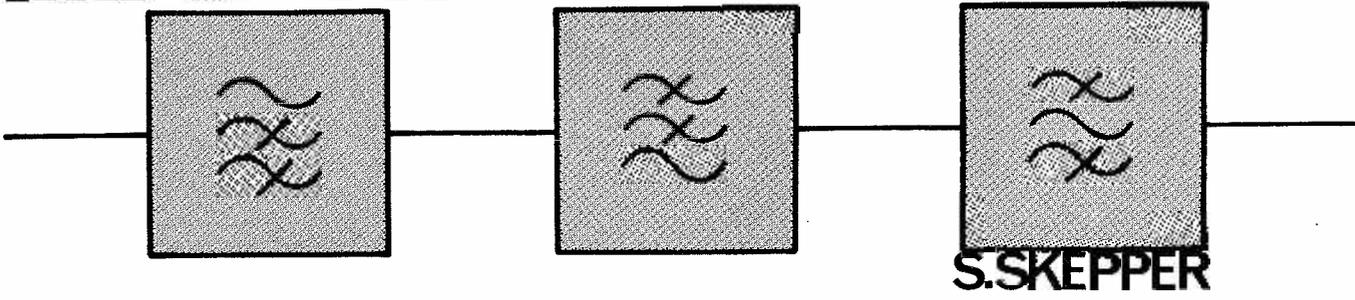

Knowing how to design a filter for a pre-amp or mixer is a very handy thing if you do a lot of playing with audio circuits, but can be uphill work if your knowledge of maths does not extend a great deal beyond Ohm's Law. If you fit into this category then despair no more! To design passable (if you will pardon the pun) filter circuits, all one needs is a (modified) version of Ohm's Law (a pocket calculator helps, too!).

The simplest type of filter is the CR filter, so called because it uses only capacitors and resistors. Fig. 1(a) shows a low-pass filter, and Fig. 1(b) a high-pass filter.

Low Pass

The low-pass filter works like this: at low frequencies, the reactance (a.c. resistance) of C is much larger than the resistance of R, so the circuit functions as a voltage divider. Because the reactance of C (called X_c) is so much larger than R, the voltage dropped across R is very small, and the output is very nearly the same as the input. As the input frequency rises, the reactance C drops until, at a certain frequency called the cut-off frequency (abbreviated F_c), X_c equals R.

If we have a voltage divider composed of two equal resistors, then the output is exactly half the input. This is the frequency that gives the filter its name, e.g., we talk of a "10kHz low-pass filter", meaning it halves a 10kHz signal and rejects all frequencies above, because as the input signal rises above the cut-off frequency, X_c gets smaller and smaller and the output drops off correspondingly. When we design a filter, we have to take into account the input impedance of the amplifier or pre-amp, Z in the circuits.

Now let's design a filter. The three things we may know or may not know are C, R and F_c , so the three formulae for calculating them are shown below:

$$F_c = \frac{1}{6.28 \times R \times C}$$

$$R = \frac{1}{6.28 \times F_c \times C}$$

$$C = \frac{1}{6.28 \times F_c \times R}$$

1. Design a scratch filter for an amplifier with an input Z of 100kΩ.

Scratch filters reject at about 15kHz, so we know F_c approximately. As a general rule, at F_c , R should equal Z, so we now know R; 100kΩ. All that leaves is C. From the above equation we get:

C in μF
R in kΩ
 F_c in kHz

$$C = \frac{1}{6.28 \times 15 \times 100}$$

$$= \frac{1}{9420}$$

$$= 0.0001 \text{ or } 100\text{pF}$$

To check, work out the other two equations;

$$R = \frac{1}{6.28 \times 15 \times 0.0001}$$

$$= \frac{1}{0.0094}$$

$$= 106\text{k}\Omega$$

$$F_c = \frac{1}{6.28 \times 100 \times 0.0001}$$

$$= \frac{1}{0.0628}$$

$$= 15.9\text{kHz}$$

Both results are near enough, considering we are only working to four decimal places.

High Pass

The high-pass filter (Fig. 1(b)), in the same way as the low-pass filter, has a point where the output is half the input: the cut-off frequency. Because the capacitor and resistor are inverted, the output rises as the frequency rises and so the circuit rejects frequencies below F_c . The equations for calculating C, R, and F_c are the same as for the low-pass filter.

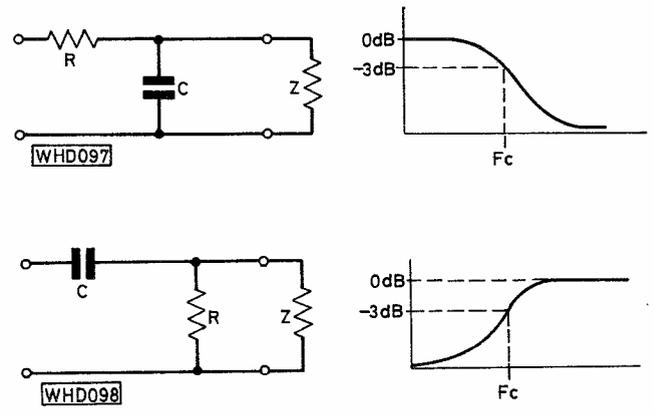


Fig. 1: Basic filter circuits and their response curves: (a) (Top) Low-pass. (b) (Bottom) High-pass

2. Design a rumble filter for a pre-amp with an input Z of $250\text{k}\Omega$. Rumble is mechanical noise from a record deck motor, and occurs at frequencies below about 25Hz , so we know F_c (25Hz) and R ($250\text{k}\Omega$);

$$C = \frac{1}{6.28 \times 0.025 \times 250}$$

$$= 0.025\mu\text{F}$$

Band Pass

Finally, let us look at band-pass filters. The simplest form of band-pass filter is shown in Fig. 2. It is simply a combination of Fig. 1(a) and 1(b). Band-pass filters are used for a variety of things, such as "middle" channel separation in tone controls, or combined rumble and scratch filters. The only limitation of this circuit is that the upper cut-off frequency, F_h , must be at least ten times the lower cut-off frequency, F_l , or interaction between the two circuits will occur, and the filter will not have a smooth response curve. Only two equations are given, as $R = Z$, and Z is usually known. Units are in kHz , $\text{k}\Omega$ and μF .

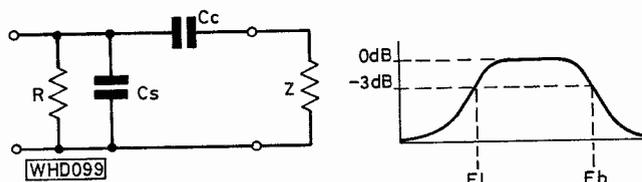


Fig. 2: A band-pass filter circuit and response

C_s determines F_h :

$$C_s = \frac{R + Z}{6.28 \times F_h \times R \times Z}$$

C_c determines F_l :

$$C_c = \frac{1}{6.28 \times F_l \times (R + Z)}$$

3. Calculate a combined rumble and scratch filter for an amplifier with an input Z of $50\text{k}\Omega$. $R = Z = 50\text{k}\Omega$. F_h wants to be, say 12kHz , and F_l about 40Hz .

$$C_s = \frac{50 + 50}{6.28 \times 12 \times 50 \times 50}$$

$$= \frac{100}{188\,400}$$

$$= 0.0005\mu\text{F} \text{ or } 500\text{pF}$$

$$C_c = \frac{1}{6.28 \times 0.04 \times (50 + 50)}$$

$$= \frac{1}{25.12}$$

$$= 0.03\mu\text{F}$$

Phase Shift

The output signal from a CR network will always differ in phase (to a greater or lesser degree) from the input signal. Whether this is important depends on the application. In this introductory article, the effects of phase shift have been ignored. ●

KINDLY NOTE!

PW "Hythe" Receiver, February 1979.

IFT1 is Denco type IFT18/465.

IFT2 is filter type CFT455 from Ambit.

IFT4 is Denco type IFT13.

Referring to the circuit diagram Fig. 2, presets VR4 and VR5 appear on the overlay (Fig. 4) as VR1 and VR2 respectively.

In Fig. 2, L2 (collector of Tr3) is unmarked. The BZY88/C6V2 diode from the junction of R17/L2 to ground should be shown at D1 (not D3).

The following may help those who are having difficulty locating specialised components:

The Denco coils are available from Maplin or Watford Electronics; C. Bowes & Co. Ltd., 4 Wood Street, Cheadle, Cheshire (Tel: 061 428 4497) supply the p.c.b. Front panels may be obtained from D. J. Pattle, "Juniper", Hillbury Road, Alderholt, Fordingbridge, Hants (Tel: 0425 52081). The vernier drive is Home Radio Type DL66—it is necessary to re-calibrate the scale. Suitable knobs are available from Marshalls or West Hyde Developments. Instrument case Type BC2121 is from West Hyde Developments. The signal-strength meter is RS Components Type 259-561 from Ace Mailtronics. Where no address is shown, see index to advertisers.

Wimborne Music Centre, October 1978.

The 2N6133 power transistors are incorrectly shown as "2N6103". RCA type BRC6103 is suitable, but alternative complementary pairs may be fitted where supplies are short, TIP41A/TIP42A being an example.

**PLEASE MENTION
PRACTICAL WIRELESS
WHEN REPLYING
TO ADVERTISEMENTS**

Follow-up to

PW Sandbanks

METAL DETECTOR

P. J. WALES

The more experienced constructor, having built his "Sandbanks", may wish to increase its performance, and these notes are a guide as to how that may be achieved.

The locator works by transmitting a heavy magnetic field over the find (which we shall call the subject) and comparing the decay of that field in the subject, to the decay in the coil. Hence, if the rate of decay in the subject is faster than that in the coil, the subject will not be detected. Thus the first item to evaluate is the coil.

Energy Storage

To detect small and fast-conducting objects such as gold, silver or copper, the energy stored in the coil must be as low as possible. The energy is stored in three ways. First the magnetism, which we want as large as possible, secondly the inductance, which is very low in an air-cored inductor, and thirdly and most importantly, the capacitance, which has no effect other than to slow down the rate of decay of the magnetic field. The capacitance is produced by the proximity of the conductors in the coil, and they are only separated by the thickness of the insulating varnish, so a significant improvement can be obtained by insulating the wire used for the coil with a pvc sleeve. Greater gains can be obtained by winding the coil, with the extra insulation, in a neat manner so that the inside turns are as far away from the outside turns as possible. This leads us on to a flat coil which has about two-thirds of the capacitance of the wire bundle coil. However, it is very difficult to wind, but if you succeed, then Araldite the coil before potting it or the turns may move in the potting compound. By far the best solution is to use a printed circuit coil, as designed by the author and available from Plessis Electronics, Castle house, Old Road, Leighton Buzzard, Beds, which has a capacitance of about half that of a wire bundle.

Coil Shape and Size

The next stage in the coil design is to alter the size of the coil. Generally speaking, to maintain the same parameters within the machine, it is necessary to increase the number of turns when reducing the diameter of the coil. A small coil will locate objects very accurately, but its range is reduced. For greater range, the coil can be increased in diameter, and as a rough guide, doubling the coil size will double the range, within limits.

Square coils also have a lot to offer, because the range on a square coil is greater than that on a round coil of a similar size. Even greater range can be obtained by using a rectangular coil, and the optimum ratio of the sides is 4:1. One manufacturer of machines using the Pulse Induction principle offers a coil 1.83 x 0.48m (72 x 18in) as a standard with one of his detectors.

Modifications

Experimenting with coils for enormous range is very easy, but finding nails 3m under hard ground is not very rewarding, so stay within reason. In order to take maximum advantage of any reduction in coil capacitance achieved, it is necessary to reduce the time between the transmit pulse and the sample pulse, called the delay time. The shorter the delay time, the more sensitive the detector is to gold. The delay time in the PW "Sandbanks" is altered by changing the value of R31 and R32. It is easiest to replace these two with 47kΩ presets during tests, putting in suitable resistors when a satisfactory performance has been reached. It is best to check the delay time using a double-beam oscilloscope, but lacking one of these, the control VR2 should be set to its midpoint and VR1 adjusted to ensure that the output of the 709 is at 0V. Then reducing the added presets until the speaker just starts clicking ensures the optimum delay time.

Internal Delays

It may be argued that the internal circuits produce their own delays and this is certainly true, but the circuit has a fall time of 3 microseconds and this is quite fast enough. No improvement was obtained with a £4.50 r.f. power transistor and low-capacitance diodes. The capacitance at the coil connections was measured as 231pF and an ordinary coil as 681pF. Reducing the 100Ω resistor R7 will reduce the decay time but it will also reduce the current in the coil and its damping effect will alter, so leave it alone.

When you have wound the coil that meets with your requirements, do not forget to waterproof it and make it rigid. If it is left loose, the machine will drift all over the places as the coil capacitance changes when the coil moves.


NEXT MONTH IN...

practical

WIRELESS

ON SALE 6TH. APRIL

FREE

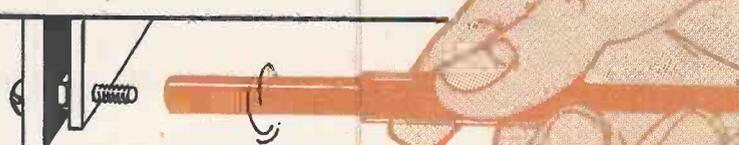

Nut Runner

One of the most useful little tools we've ever come across. Firmly grips nuts of 4 and 6BA and nearby sizes while you "start" them in inaccessible places

get into radio

WITH THE



IMP



The PW Imp is a simple beginners radio intended as an introduction to the delights of listening to radio stations around the world. The novice should find this set ideal as a starter project

VSWR problems at

VHF

Fred Judd seeks to dispel some of the misunderstanding among radio enthusiasts about what v.s.w.r. really is, and what it means.

Car Test-Probe

Checks live, open-circuit or earthed wires, ignition timing, and battery voltage rise on charge. Build one and keep it in your car, ready for an electrical breakdown

This article describes the construction of a miniature, high-performance v.h.f. receiver for narrow-band frequency modulation, based on the Plessey SL6640 integrated circuit. The SL6640 is a complete i.f. strip, detector and audio system for n.b.f.m., requiring the minimum of external components. It consumes only 3.5mA of current in the standby mode and can produce 200mW of audio.

The receiver is so simple that it may be built even by the relatively inexperienced, and yet it gives a professional account of itself

with a sensitivity better than 0.4 μ V for a 20dB signal-to-noise ratio. Physically, the module is only 46 x 82mm (1.8 x 3.2in) and although the details given are for operation within the 144MHz (2m) amateur band, the receiver will easily tune to marine v.h.f. channels, and could be used to keep a watch on, say, channel 16, the distress and calling frequency. In this respect it would be a useful project for the yachtsman or small boat-owner, and is licensable for use on board such vessels.

VHF



MONITOR RECEIVER

*James M. BRYANT B Sc

The circuit diagram of the complete receiver is given in Fig. 1. It can be seen to consist of a double-tuned input arrangement feeding a dual-gate m.o.s.f.e.t. amplifier with a gain of 18dB. Another double-tuned circuit couples the amplifier to a second dual-gate m.o.s.f.e.t. which acts as a

mixer whose conversion gain falls around 12dB. The local oscillator uses a *pnp* v.h.f. transistor in an overtone configuration.

A crystal filter, specially designed by Cathodeon, filters the 10.7MHz signal and then passes it directly to the

* Applications Manager, Radio Communications Group, Plessey Semiconductors, Cheney Manor, Swindon Wilts

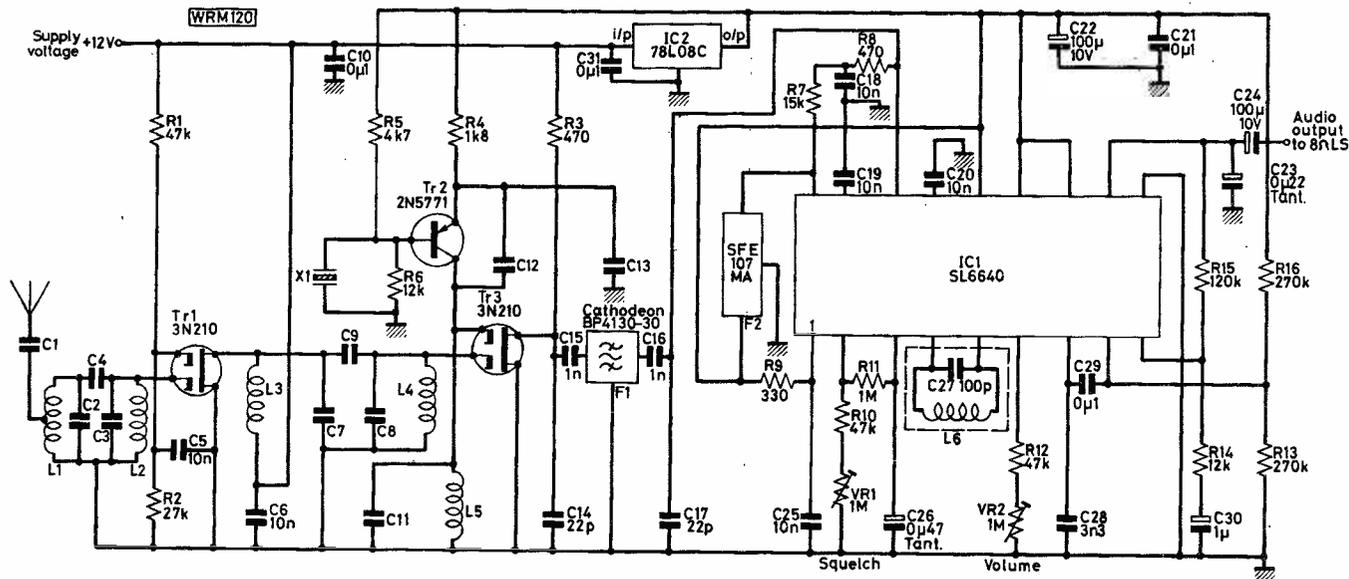


Fig. 1: Complete circuit diagram of the single-channel version of the receiver

SL6640, which performs the functions of i.f. pre-amplifier, main i.f. limiting amplifier, quadrature detector, squelch and audio output stages.

Dual-gate m.o.s.f.e.t. devices were selected on the grounds of their good noise (about 4–6dB) and intermodulation performance. They will cope with large off-channel signals with the minimum of intermodulation distortion. Prototypes used the 3N210 in a plastic encapsulation, but 3N211, 3N201 or 40673 devices in the metal TO-72 packages will fit the board and work equally well.

Only five components, in addition to the capacitors and inductors of the tuned circuits, are employed in the r.f. amplifier: the m.o.s.f.e.t., two resistors to bias gate 2 of the m.o.s.f.e.t. and two decoupling capacitors. Standard Toko coils are used throughout, and the small ceramic capacitors are of ITW manufacture. At 2m, C2 is 12pF, C3–6.8pF, C7–8.2pF and C8–6.8pF. *Note that C4 and C9 are not "real" components, but represent stray capacitance.*

A 2N5771 *pn*p transistor has been chosen for the local oscillator. This reduces the number of devices necessary in the circuit, as the collector load coil is at d.c. ground potential and hence no coupling or bias components are needed for the second gate of the mixer m.o.s.f.e.t.

The oscillator is very simple and reliable, using only nine components. Any additional expense incurred by the selection of overtone crystals is easily justified against the increased complexity and power consumption of multiplier stages.

In the case of a 2m receiver, C12 may have to be omitted or may be found to be as large as 1.8pF, a certain amount of experimentation being necessary to determine the optimum value. Capacitor C13 will not usually be required; C11 is 6.8pF and L5 a Toko S18/301–SN-0300.

Using 7th or 9th overtone crystals can lead to oscillator starting problems, but this circuit has been rigorously tested and found to be completely reliable, provided the

supply voltage remains stable. Crystal frequencies are calculated from the formula:




$$\text{Crystal frequency} = \text{Carrier frequency minus } 10.7\text{MHz}$$

If the receiver is required to work on more than one channel, some sort of d.c. switching will have to be evolved, as long leads are not permissible. Such techniques will be found to complement the use of scanners. A suitable method is shown in Fig. 2, where the diodes should exhibit low-capacitance characteristics, such as the 1N4313.

The mixer consists of another dual-gate m.o.s.f.e.t. with both gates at d.c. ground. Signals are applied to gate 1, whilst gate 2 is connected to the oscillator tank circuit, which drives it with about 2 volts r.m.s. of r.f. Better conversion gain and a lower local oscillator could be achieved by biasing gate 2 between 2.5 and 4.5 volts, but this would degrade the strong-signal performance of the front-end.

Two signals of 100mV, one 50kHz and the other 100kHz off-channel, could be tolerated by the prototypes without receiving an intermodulation product. Nevertheless, an even better performance may be obtained by sacrificing some front-end gain—and therefore sensitivity.

The mixer drives a crystal filter, designed specifically by Cathodeon for this receiver, which has a relatively low terminating impedance of 470Ω at 25pF—eminently suited to the output of the dual-gate m.o.s.f.e.t. and the input of the SL6640. Other filters, some appreciably cheaper, are acknowledged as being available, but will almost certainly present the constructor with problems, due to their different terminating impedances. Although C14 and C17 may be changed if necessary, it is not possible to increase the value of R3 and R8 above 820Ω without upsetting the operation of both Tr3 and IC1. A reduction of their values, on the other hand, will cause the gain to deteriorate.

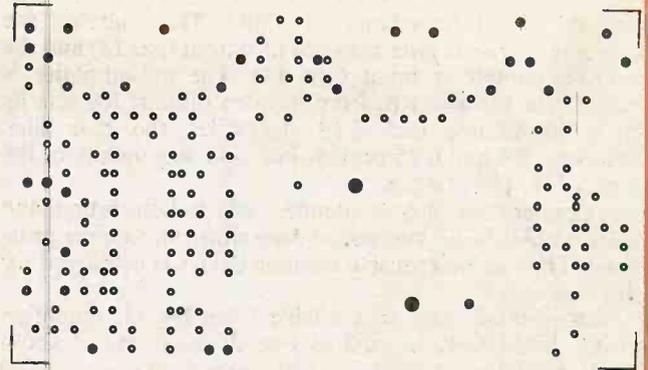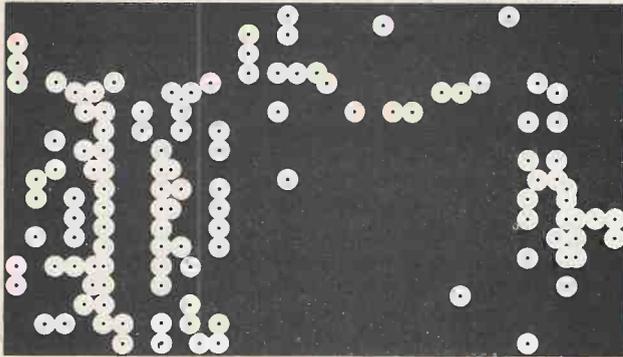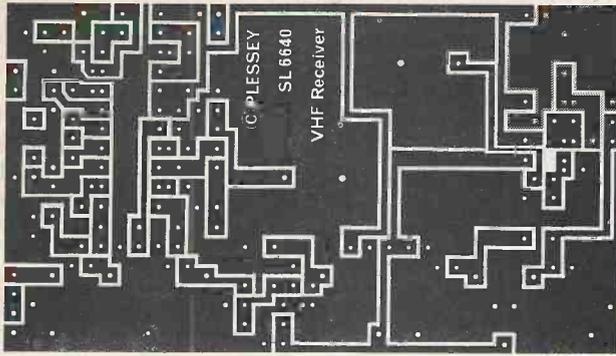


○ 0.7mm Dia ● 1mm Dia ● 3.2mm Dia WRM125

Fig. 4 (left): Full-size track patterns for the p.c.b. showing non-component side (top) and component side (bottom)

Fig. 5 (above): Drilling drawing for the p.c.b.

Fig. 6 (below): Component layout. The ground-plane pattern on the component side of the board is shown in orange tone

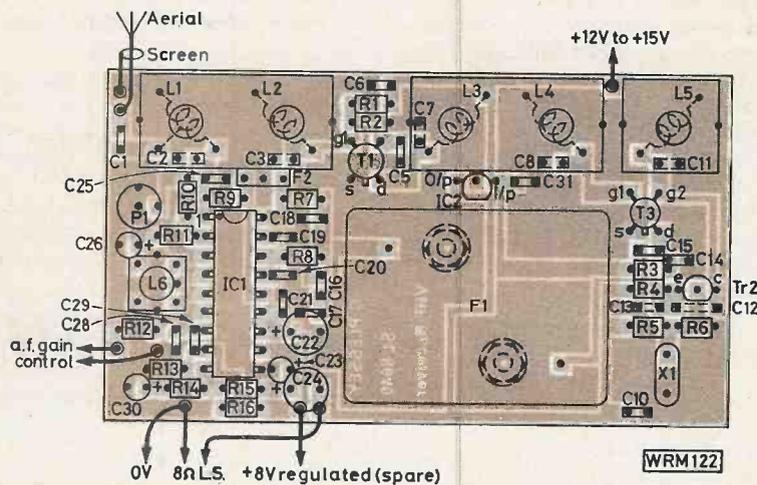

Feed a 10.7MHz frequency-modulated signal to the input side of the crystal filter. Now, with full audio gain and minimum setting of the squelch resistor, tune the quadrature coil for minimum distortion at the output. If clipping occurs, back off the audio gain slightly.

Adjustment without instrumentation is, of course, somewhat less precise. Never-the-less, acceptable results can be obtained and lack of test equipment should not deter the constructor from building this project.

With the presence of a strong v.h.f. signal, tune the local oscillator coil L5 until it is heard at maximum volume and

minimum distortion. Having done this, turn the power on and off several times to ensure that the oscillator will always start.

Next, set the quadrature coil for minimum apparent distortion with the squelch potentiometer at minimum resistance. Then reduce the strength of the alignment signal, perhaps by using progressively smaller aerial lengths, tuning L1, L2, L3 and L4 at each stage for the best signal-to-noise ratio.

Finally, the squelch control is set so that muting occurs when the signal-to-noise ratio becomes unacceptably low.

★ components

Resistors

$\frac{1}{8}$ watt carbon

330Ω	1	R9
470Ω	2	R3, 8
1.8kΩ	1	R4
4.7kΩ	1	R5
12kΩ	2	R6, 14
15kΩ	1	R7
27kΩ	1	R2
47kΩ	3	R1, 10, 12
120kΩ	1	R15
270kΩ	2	R13, 16
1MΩ	1	R11

Potentiometers

*Miniature, round, linear law preset. Plessey type 416

1MΩ	1	VR1 mute threshold
-----	---	--------------------

Miniature log law, panel mounting

1MΩ	1	VR2
-----	---	-----

Capacitors

**ITW type M2 monolithic

22pF	2	C14, 17 (but see text)
1nF	3	C1, 15, 16
3.3nF	1	C28
10nF	7	C5, 6, 10, 18, 19, 20, 25

Ceramic Plate

0.1μF	3	C21, 29, 31
-------	---	-------------

Tantalum Bead

0.22μF	1	C23 35V type
0.47μF	1	C26 35V type
1μF	1	C30 35V type
100μF	1	C24 6V type
100μF	1	C22 10V type

Note: C2-4, 7-9, 11-13 see text C27 is part of coil assembly.

Filters

***BP4130-30	1	F1
SFE10.7	1	F2 (Ambit)

Semiconductors

Transistors

3N210	2	Tr1, 3 (or 3N201, 3N211, 40673)
2N5771	1	Tr2

Integrated Circuits

***SL6640	1	IC1
μA78L08C	1	IC2

Crystal(s)

*****7th overtone, Type WW239

Inductors

Toko S18/301		
-SN-032	1	L1 (Ambit)
Toko S18/301		
-SN-0300	4	L2-5 (Ambit)
Toko 85-4402SEJ	1	L6 (Ambit)

Printed Circuit Board

The special p.c.b. for this project is available from Ambit International. Kelan Engineering Ltd., 27-29 Leadhall Lane, Harrogate, Yorkshire HG2 9NJ. Tel: 0423 879126, are also able to offer a multi-channel option, using 3rd overtone crystals.

Hardware

Two double coil screening cans are required for L2-L3, L4-L5 and a single can for L1. These are obtainable from Ambit International.

COMPONENT SOURCES

*Preset available from Ambit International.

**ITW capacitors available from ITW Electronics, Darville Ho., 4 Oxford Road East, Windsor, Berks and Ambit International.

***SL6640 available from Catronics or Ambit International.

****BP4130-30 available from Cathodeon Crystals Ltd, Linton, Cambridge CB1 6JU. Tel: 0223 891501.

*****7th overtone crystals available from Webster Electronics, Rose Mills, Hort Bridge, Ilminster, Somerset TA19 9PS. Important: specify crystal Type WW239 with channel (carrier) frequency and crystal frequency (carrier minus 10.7) when placing order.

With a calibrated signal generator, this point should be between 0.15 and 0.5μV—however, it is preferable to set the squelch to a signal-to-noise ratio, rather than to an absolute input voltage.


No instrument case or mechanical details are given for this project, but the receiver is a complete module, requiring only the addition of a battery, volume control, squelch control and small loudspeaker as external components. It could therefore easily be constructed within an existing receiver, using the incoming v.h.f. signal to mute and over-ride the normal programme. For example, the marine version on channel 16 could mute an m.f. signal, or indeed another v.h.f. signal, thus giving priority to channel 16 traffic. On the other hand, it could easily be a self-contained unit.

Multi-channel Conversion

If coverage of more than one channel is necessary, then the circuit of Fig. 2 can be regarded as a working basis, and could probably be accommodated on a small sub-assembly. If a multi-channel facility is decided on at the outset, a small extension could possibly be made to the printed circuit board.

The 7th overtone WW239 crystals are relatively expensive, but on the other hand the end-product will hold its own with many professional receivers of its type. The original design work for this project was carried out for a specific professional application, and the specification of this version has in no way been degraded.

Wireless went to War

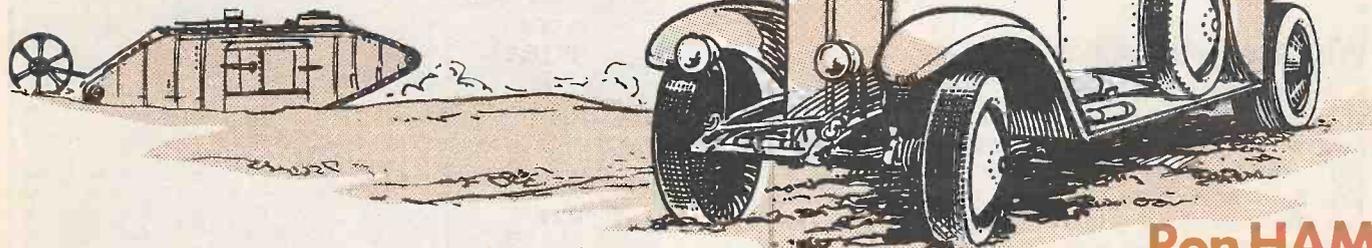

Ron HAM

In the 1830s, Samuel B. Morse invented a code which was used by signallers to convey military information along thousands of miles of telegraph lines during the American Civil War (1861–1865) and, some 40 years later, Alexander Graham Bell's telephone was extensively used by both sides throughout World War I.

To find out more about communications during that war, the author spoke to several old-timers who were there. One, Bert Knight, now 90 years old, a veteran of the Rifle Brigade, remembers seeing telephone cables at Ypres being laid from a large drum, mounted on a limber drawn by a team of horses, and signalmen in dugouts wearing headphones. However, this means of communications had its drawbacks because, the cables, whether overhead or underground, were vulnerable to secret tapping by enemy signalmen, calculated cutting of the wires, and being totally destroyed by artillery bombardment.

During the last decade of the 19th century, men like Edouard Branly, Oliver Lodge (later knighted), and Guglielmo Marconi, to name a few, were pioneering a means of transmitting both the Morse code and the human voice over great distances without wires. Before their ideas were fifty years old, wire-less communications (later called radio) was used during two world wars on land, sea and in the air.

The Great War

Wireless during the 1914/18 war rested mainly with the electric spark transmitter and receivers, using a coherer or catswhisker and crystal detectors and, for amplification, a limited range of bright-emitter (triode) valves, so called because their high filament current produced a lot of light.

Wireless installations were also vulnerable to enemy action, mainly because the high aerials required gave away the position of a signals unit to enemy spotters. Also, the noise from the transmitter spark gap and the receiver tuning buzzer could be heard for some distance on a quiet night.

The late Bill Longmire, G3TKL, joined the signals section of the 26th Canadian Battalion in 1914 and after three months training had to pass in Morse at 12 w.p.m. with buzzer, lamp and heliograph, and in semaphore and flags. "Serving in France in 1915," said Bill, "I found that war was a bloody business and that communications (by land-line) were not only most important but also dangerous." He used a "D3" telephone set, phone and Morse, with a single-strand wire and an earth return.

Later, Bill transferred to the Canadian Corps wireless section to learn the basic facts of radio and then was selected for a special, three week, training course in London. At the end of the course, a team of three could erect an aerial consisting of a 100ft long wire on two 24ft masts, with guys, earth rods and counterpoise, in under five minutes. On returning to France, Bill saw action at Vimy Ridge, and was told to set up a wireless station on a front where shell fire kept land lines out of action. For such an advanced post Bill said: "An NCO and two men with a 24-hour watch and frequent checks with headquarters station, were required. Usually we had a 2–3 week stretch in the line if the enemy was not too active."

The trench set illustrated in Fig. 1 consists of a spark transmitter, spark-gap and coil at bottom right, and a crystal detector receiver on top, with its tuning buzzer on front left. The output meter, stud-type aerial matching switch and Morse key are mounted on the top panel, all beautifully engineered and housed in a mahogany cabinet. Bill said that this type of set, plus six 6 volt storage batteries, aerial masts and earth mat was the equipment used in an advanced station. When possible, they tried to select a site for the station which was concealed from the enemy and had easy access from the rear for delivery, by carrying party or mules, of their food and replacement batteries.

Most messages were passed in cypher, code words and call signs being changed daily, their lighting was by candle and heating by coke. Around midnight, the news could be

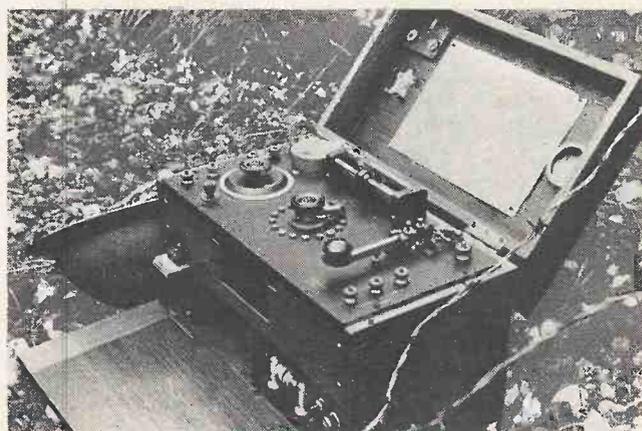


Fig. 1: 50 watt Trench set made by the Marconi Company

copied from Poldhu, Cornwall; Eiffel Tower, Paris; or Naum, Germany. "The extra copy taken to the local infantry or artillery cook-house was always good for a handout," said Bill, but Passchendaele was an exception. "Ten days in, four operators and self, one killed, four wounded, but station was able to handle all traffic in spite of the antenna being shot down eight times."

Wireless in the Air

Mark Denny, G6DN, said: "Before the war many amateurs became proficient in Morse by following a programme which started with a session of listening to the Eiffel Tower news bulletin, which was sent at 12 w.p.m. with a T1 note. Then followed a period of receiving the news from a German station at about 15 w.p.m. The final achievement was the ability to copy Cleethorpes Naval Station weather report sent at 10pm each day. This was initially at 20 w.p.m. and repeated at 25 w.p.m." At that time the Navy required aspirants for entry to their W/T branch to copy, for five minutes, without error, a message in clear at 25 w.p.m.

In 1914, Mark entered the Royal Navy as a Wireless Telegraphist and in 1915 was commissioned in the (Army) Royal Flying Corps, later the RAF. While in the RN he was posted to a Naval Airship Station and along with a group of W/T matelots had to unpack and assemble the wireless equipment for airships, which consisted of a "Stirling" spark coil and a Marconi crystal receiver plus a hand-operated winch containing over 300ft of wire, with a lead weight attached, for the aerial. Mark said: "We were ordered to install the apparatus in the airships and to assemble a ground station without delay. Our difficulty was that, whilst every material item necessary was provided, no written instructions or wiring diagrams were available. This is where our amateur, pre-knowledge of radio helped and we were on the air to the C/O's satisfaction."

The author showed Mark Denny a photograph of the Marconi transmitter in Fig. 2 and he recognised it as the type he used in the RNAS airships and in the RFC and said: "I used to feel rather apprehensive when adjusting the tuning clips on the helix, considering the thousands of cubic feet of hydrogen gas just above your head."

Their best DX from air to ground was a QSO with Malta Naval Station from the English Channel, using a half-inch spark coil. Sending Morse messages by spark, situated only a few feet below a gas bag, was one of the hazards of life in those days.

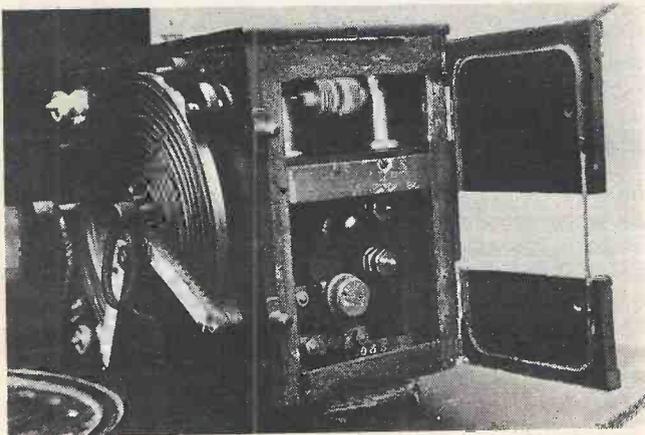


Fig. 2: Marconi spark transmitter from World War I



Fig. 3: Short-wave Tuner, Mark III made by Johnson and Philips

Aerial Installation

As a wireless officer in the RFC, Mark saw active service in France. At one stage he was supplied with portable sets, especially flown out from England for the use of certain gentlemen who were deposited over the lines, and later he listened to their transmissions. Soon after he established listening posts in "No Mans Land" and still has his pass permitting him to advance in front of the front line. Like Bill Longmire with his 24ft masts, Mark also had aerial problems to solve. While in France, they used steel rods which were a loose fit in their rifle barrels, and marched down a village street firing these rods with cords attached over opposite houses. On joining the cords with aerial wire, they soon had an excellent antenna.

Later, back in England, Mark put up the first ground-to-air telephony stations for the Air Defence of Great Britain, which involved getting up in the early hours, before the traffic was about, because one antenna was across Horse Guards Parade, from the Foreign Office to the Horse Guards building in Whitehall, and from the Horse Guards to the War Office, just over the road in Whitehall.

The late John Clarricoats, G6CL, referring to the RFC in the *T & R Bulletin* (then the journal of the RSGB), December, 1939, wrote: "The chief job of the 1915-1918 wireless operator was to act as "the ears" between a roving plane and the battery to which he was attached; his equipment was primitive (usually a Mark III tuner) and his only means of communication with the observing machine was by means of "white" ground strips which, sad to relate, seldom lived up to their name." Mark Denny also remembers the Mark III tuner, as the set supplied to them

on the Western Front, and used by RFC wireless operators in their dugouts in conjunction with the Royal Artillery batteries.

The Wireless Reserves

In the 21 years which elapsed between the two world wars, radio made fantastic strides both in broadcasting and short-wave communications around the world, and it is well-known that amateur radio enthusiasts played their full part in both fields.

With the war clouds gathering again in the early 1930s, the authorities, knowing there would be a need for trained wireless operators if war came, once more called upon the amateur radio enthusiasts for assistance. On August 26, 1932, *Wireless World* commented: "At last British wireless amateurs are to be given the opportunity to assist His Majesty's Forces"; when they reported that: "The Secretary of the Admiralty announces the institution of a Royal Naval Wireless Auxiliary Reserve (RNWAR) in Great Britain and Northern Ireland, to be recruited largely from Wireless Amateurs owning transmitting sets." One of the objects of the RNWAR was, "to provide a reserve of operators trained in Naval procedure, for Naval service afloat or ashore in war or emergency."

The setting up of this organisation was the result of careful work by officials of the Admiralty and the Radio Society of Great Britain, as was the establishment, by the Air Ministry, in September, 1938, of the Royal Air Force Civilian Wireless Reserve (RAFCWR). The announcement, by the Air Ministry, reported in *Wireless World*, December 29, 1938, made it clear that the CWR was to "consist largely of amateur experimenters which would, if the need arose, provide a reserve of personnel experienced in the operating procedure of the RAF." Both the

JANUARY 26th, 1939. Wireless
World

NATIONAL WIRELESS REGISTER

THE MINISTRY OF LABOUR is issuing a booklet giving the details of various services which are essential for the defence of our country, and is asking members of the public to volunteer their services so that the whole efforts of the country may be rightly directed. Every individual can then be put to that task for which he is most fitted by previous training. A large percentage of readers of "THE WIRELESS WORLD" possess technical qualifications which in many cases have been acquired from years of training and practical experience. In the event of a state of emergency arising, the defence services of the country will have a great need of wireless operators, teletypewriter operators, and technical personnel capable of caring for and repairing wireless and light electrical apparatus. During the Great War the needs of the Services for operators were largely met, especially during the early stages by the voluntary enlistment of trained Post Office operators, but as Morse is no longer used in the Post Office, this possible source of supply is rapidly dwindling. It is therefore imperative that all our readers who have at least a good working knowledge of Morse or have other qualifications such as ability to service and repair wireless and electrical apparatus, should apply to help fill the vacancies which now exist in the R.N.V.(W.)R., the Royal Corps of Signals, T.A., and the R.A.F.C.W.R.

Such applications will enable much valuable time to be saved and will facilitate volunteers being in their right position at the right moment if the necessity arises.

Readers who are not at present in a position to volunteer in the above-mentioned Services are asked to complete the Questionnaire which is reproduced below, and post it without delay. From the answers to this Questionnaire a register of wireless experts who are willing to serve their country should an emergency arise will be compiled in conjunction with the Wireless Telegraphy Board. This Register will be regarded as confidential and the information contained therein will only be made available to the Defence Services.

1. Name in full (in capitals)
2. Permanent address
3. Age
4. State whether British by
 - (1) Birth
 - (2) Naturalised
 (If naturalised, state former nationality and date of naturalisation.)
5. Give particulars of any technical degrees or other recognised qualifications
6. In which of the following categories would you place your qualifications:—
 - (1) Research and design of wireless apparatus
 - (2) Servicing and tracing faults
 - (3) Construction of apparatus from blueprints and designs
 - (4) Wireless operating. State number of words per minute
 - (5) Teletypewriter operating
7. Have you a sound knowledge of wireless theory and the ability to read circuit diagrams?
8. Have you had war experience, if so, give brief details
9. Are you already liable for service with any Force or Organisation? (If so, state particulars)
10. Have you any preference for service in either the Navy, Army or Air Force?
11. Are you physically fit?
12. Present occupation

Fig. 4: National Wireless Register, published in *Wireless World* on 26 January, 1939

RNWAR and the RAFCWR attracted several thousand radio enthusiasts from all walks of life. They divided the United Kingdom into areas where small groups could train to the required military standard. Experimental sections were manned by experienced radio amateurs who dealt with the design of transmitters and receivers to meet a particular section's needs; and all in harmony with the signals branch of their respective service.

National Wireless Register

Both the RSGB, through their journal, *The T & R Bulletin*, and *Wireless World* frequently reported the progress of the Wireless Reserves and, furthermore, *Wireless World* did much to find out what radio skills were available among their readers that would be of use to the armed forces in the event of war.

In their editorial on January 26, 1939, *Wireless World* comments: "In the event of an emergency which would require everyone to put himself at the service of the Country, the moment will arise when every individual will ask where he can offer his services so that such qualifications as he may possess will be of greatest value." As a pull-out in the same and some subsequent issues, *WW* enclosed a printed OHMS form, addressed on one side to... Secretary, Wireless Telegraphy Board, c/o Admiralty, Whitehall SW1, and with a general and technical ability questionnaire on the other. This document, Fig. 4, was

continued on page 60

BINDERS FOR PW

Keep your copies together
Keep them clean
with the
PW Easi-Binder

The Easi-Binder is attractively bound with the title blocked in gold on the spine with the current (or last) volume number and year. For any previous volume numbers please advise year and volume and a separate set of gold transfer figures will be supplied.

£2.85 inclusive of VAT and post and packaging from: Post Sales Department, IPC Magazines Ltd., Lavington House, 25 Lavington Street, London, SE1 0PF.
(Overseas orders please add 60p).

THE **PW** 'WINTON' Stereo Amplifier

Part 2
E.A.RULE

As the p.c.b. must be mounted into the chassis before the other parts, we will start construction by assembling the components onto the boards.

The leads of the components should be preformed and inserted into the holes, as shown in the component overlay Fig. 7. Turn the p.c.b. over so that it rests on a sponge or foam mat, which will then hold the components in close contact with the p.c.b. while they are soldered into place.

Coils

Before assembling the main p.c.b., the two coils L1a and L1b should be made up as shown in Fig. 6. Each coil consists of 30 turns of 18 s.w.g. insulated wire wound in three layers of ten turns each. The internal diameter of the first layer is 8mm. If masking tape is wound over each layer after winding, the turns will stay in place while the next layer is wound. When the coil is completed the 1W 10 Ω resistor is fed through the centre of the coil and the leads soldered to the coil as shown. The coil ends are then opened out to a spacing of 22.5mm to fit the p.c.b. It will, of course, be necessary to scrape the insulation from the coil ends before soldering.

Assembly should start with the terminal pins, which will be a tight fit and can be tapped into place with a light hammer, but you must support the p.c.b. from behind when doing this. Insert them from the top of the p.c.b. and then turn the board over and solder the pins to the track.

Once the pins are in place, the suggested order of assembly is resistors, small capacitors, transistors, electrolytics, switches, etc.

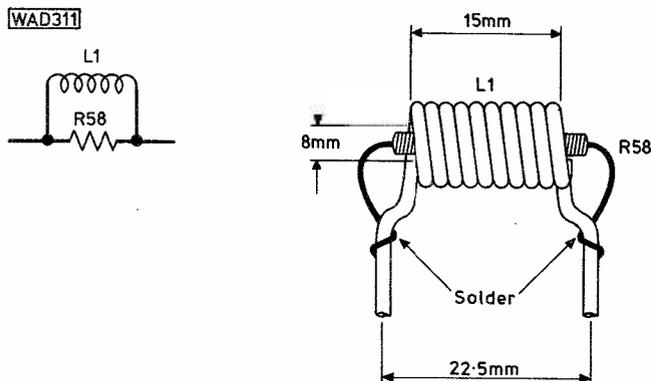


Fig. 6: Winding details of the two coils L1. Internal diameter 8mm; Length 15mm; 3 layers of 10 turns each (Total 30 turns) 18 s.w.g. enamel copper wire. R58 is 10 Ω 1W carbon resistor

Switches

Be sure to mount all electrolytics the correct way round as indicated on the overlay. This also applies to diodes and i.c.s. When fitting the push-button unit to the p.c.b., first make sure that all the pins are straight, then "walk" the pins into the holes by starting at one end of the switch with the switch at a slight angle to the p.c.b. and gradually lower the switch pins into the holes as the switch is levelled out. Make sure that the switch is parallel to, and in close contact with, the top of the p.c.b. before soldering the pins to the track, otherwise the push-buttons will not align with the front panel holes.

Use only the components specified as only then will the specification, of which the Winton is capable, be achieved.

Chassis

The main chassis is made in the form of an inverted "U" from aluminium sheet and the overall size required, before bending, is 462 \times 298mm + twice the bend allowance for the thickness of metal used, i.e., 462 \times 300mm when using 1.2mm thick (18 s.w.g.) aluminium. Most d.i.y. suppliers will cut aluminium to size for a small charge, and it is well worth having this done as it will save work and ensure a "square sided" chassis. The author used aluminium of 2mm (16 s.w.g.) thickness for the main chassis but has access to a bender capable of folding this thickness. Unless a suitable bender is available, the 1.2mm material will be found easier to work with and will still provide adequate strength.

Mark out the chassis as shown in the drawing (Fig. 14), not forgetting to scribe two lines to allow for the thickness of metal used when bending.

The centre height of the push-button holes must be 20mm above the inside edge of the bent-up chassis, and this is the reason for scribing two lines. If the bottom line is used as the guide line in the bender the holes should be correctly positioned after bending.

Cut-outs

After drilling, all the holes should be deburred. The four large rectangular cut-outs in the chassis are provided so that the underside of the p.c.b. can be reached, as it would be almost impossible to remove and/or test the p.c.b. otherwise. These cut-outs are made using an Abraflex blade fitted to a standard hacksaw, any burrs being removed with a suitable file.

When all the holes and cut-outs have been made the chassis can be bent up. Make sure you bend it the correct way!!



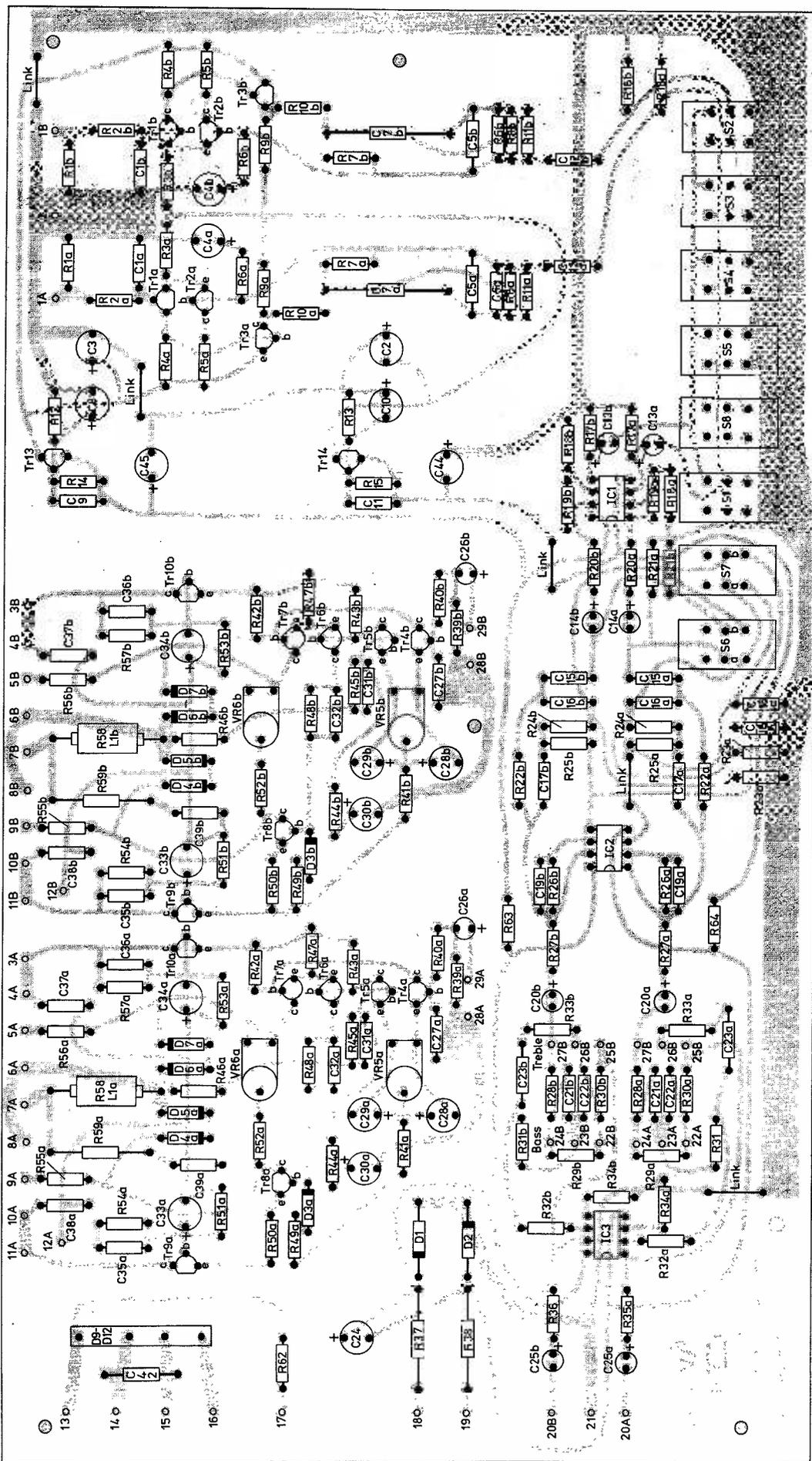
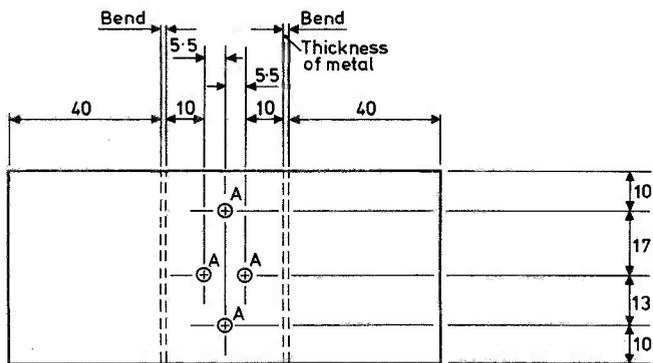


Fig. 7: Component layout for the PW Winton amplifier. This is shown slightly reduced in size

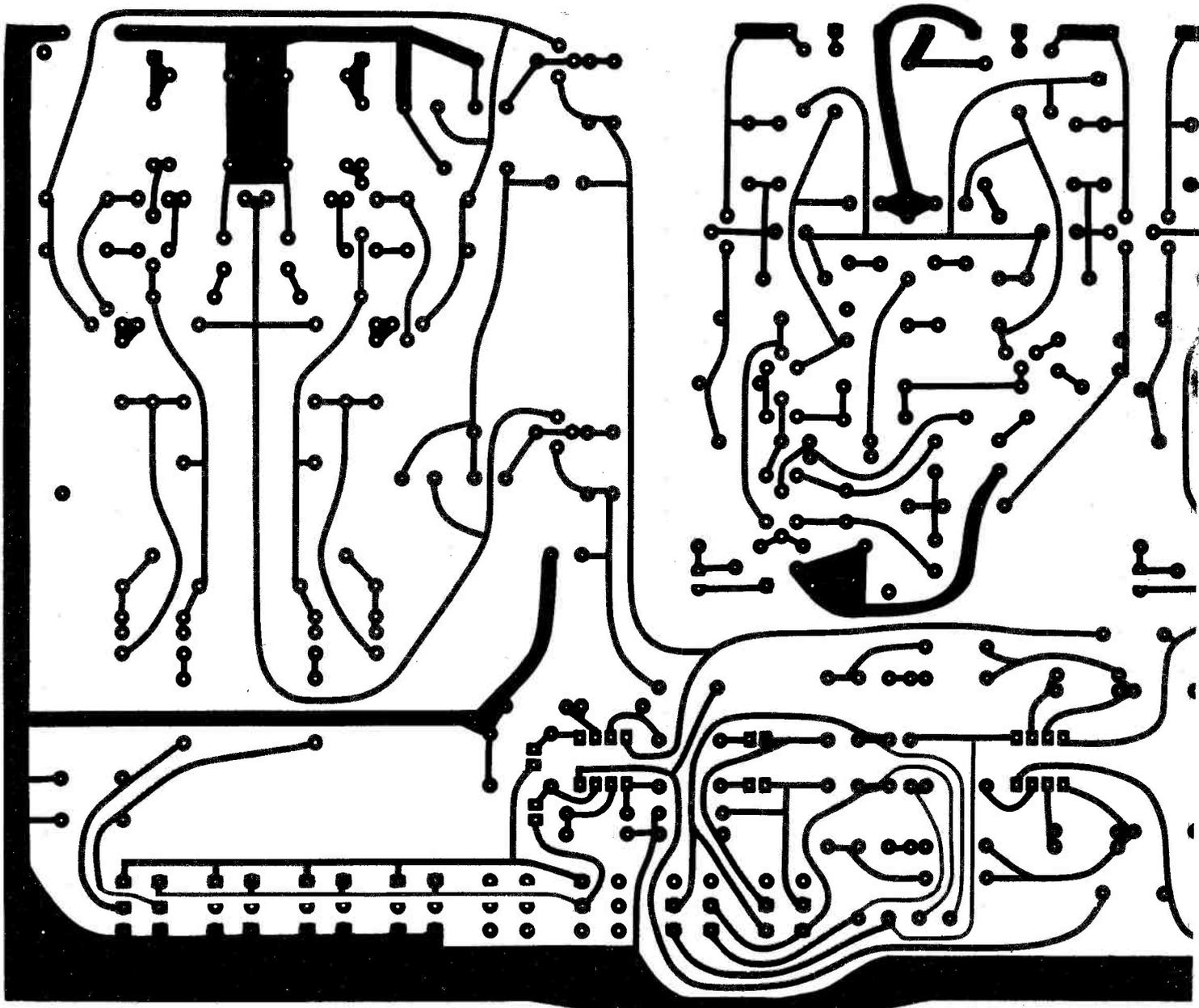

Hole sizes
A 4mm Dia.

WAD308

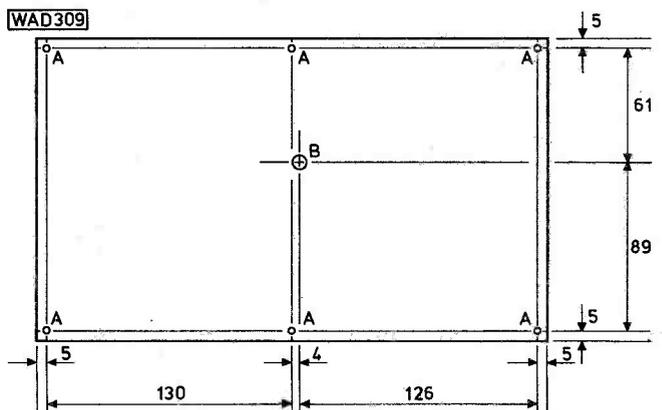

Hole sizes
A 4mm Dia.
B 8mm Dia.


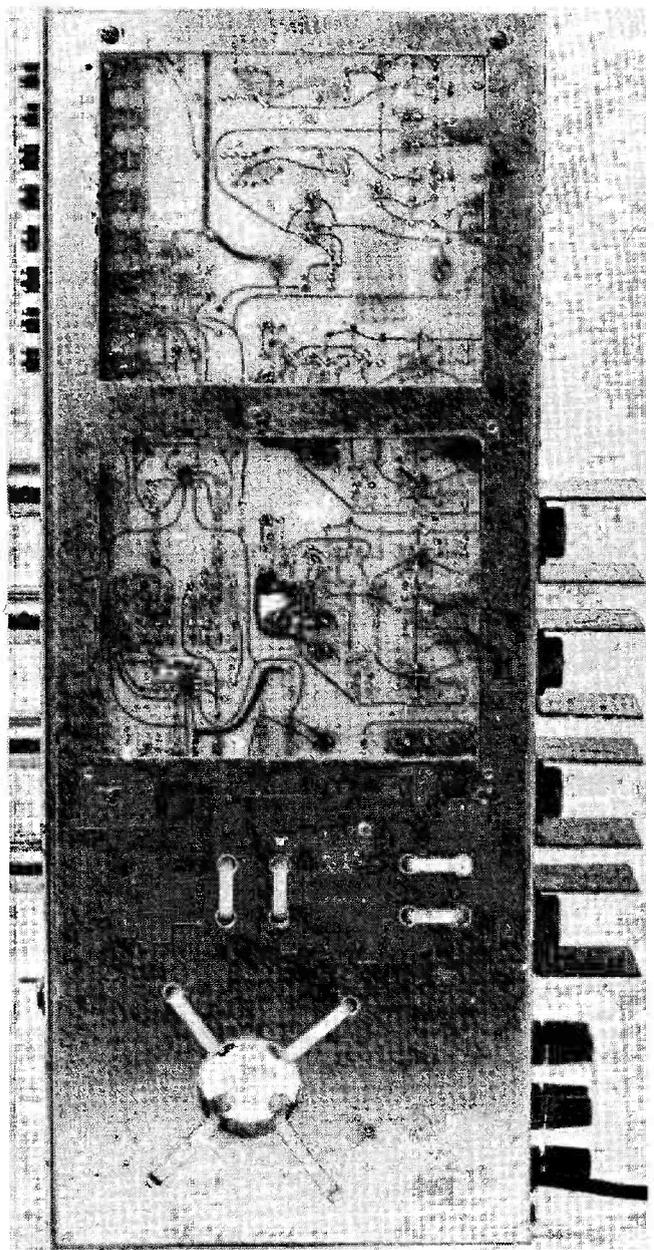
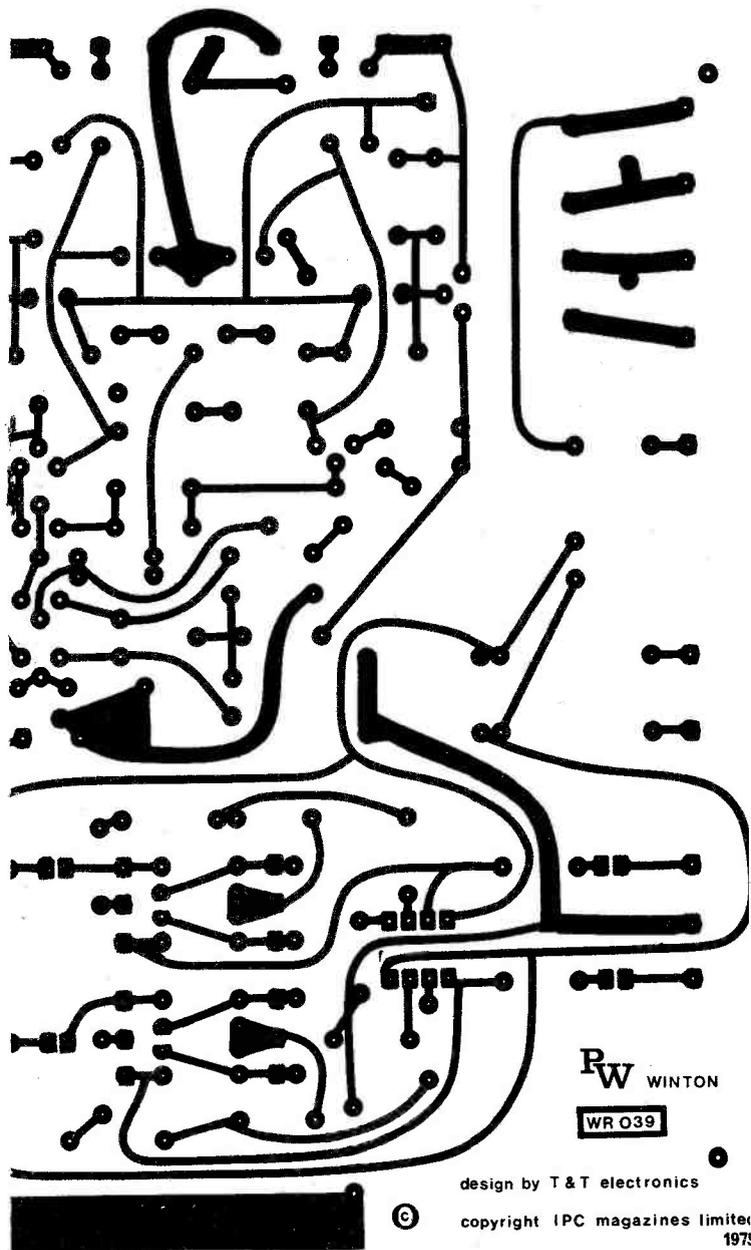



Fig. 8: Above left, the full size copper track pattern of the PW Winton printed circuit board

Fig. 9: Far left, details of the output transistor heat-sinks. Four of these are needed made from 1.2mm thick aluminium sheet with all burrs removed and the mounting surfaces absolutely flat. Paint matt black when completed

Fig. 10: Centre, the baseplate which covers the cut-outs in the aluminium chassis. Only one is needed from 1.2mm thick aluminium

Fig. 11: Left, details of the earth terminal assembly

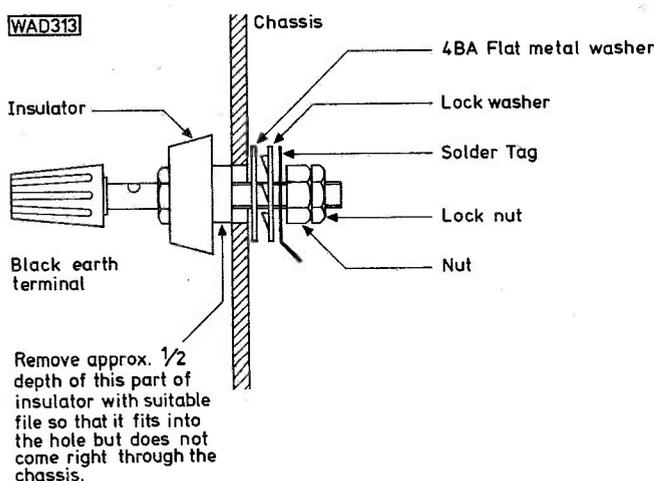

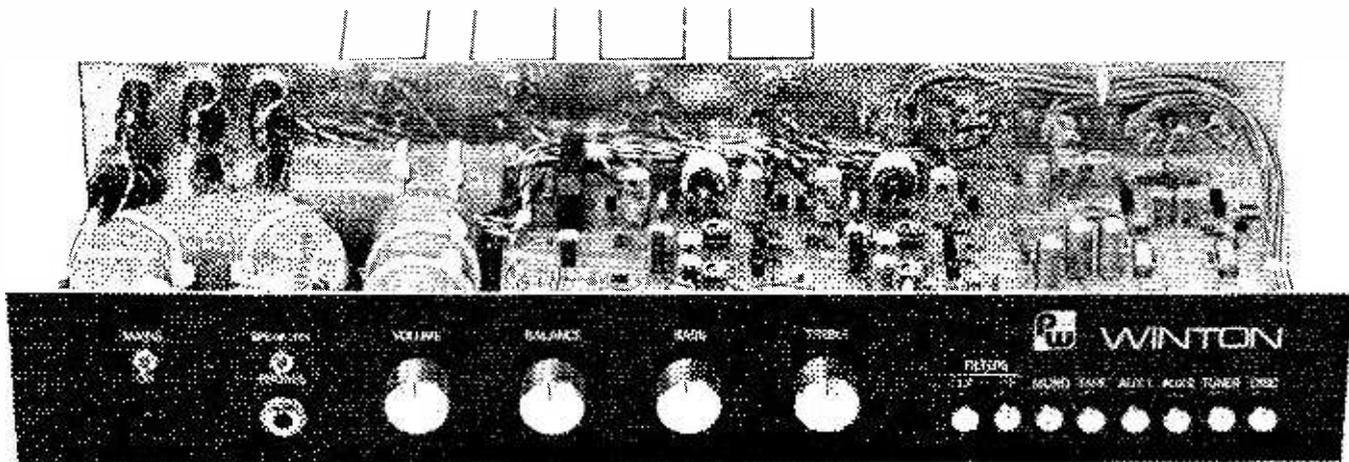

Heat Sinks

The four heat sinks can be made from the aluminium removed from the four rectangular cut-outs and should be made up as shown in Fig. 9. It is very important that the holes on the heat sinks are completely free from burrs, also the part in the centre should be flat and any high spots removed with a suitable file. The power f.e.t.s must be mounted on a perfectly flat surface and the parts used for this must be filed flat and freed of burrs.

Once the p.c.b. is fully assembled it should be very carefully checked for any errors. If possible get someone else to check your work for you. When you are satisfied that it is correct, it can be assembled into the main chassis.

First, fix the five p.c.b. pillars onto the chassis. These are held in place with No. 6 self-tapping screws approximately 9mm long. The p.c.b. can then be mounted onto the pillars by lowering the push-button end so that the buttons line up with and project through the front panel holes. Then press the p.c.b. firmly onto the pillars. Check the action of the push-button switches, which must all be free to move without catching on the chassis. The use of a small file may prove helpful if problems exist but if the chassis has been made correctly, all should be well.

The other components can now be fitted to the chassis in the position shown in the drawings and photographs. Note that the volume, balance and tone controls are assembled onto their mounting bracket (Fig. 15), before the whole assembly is fitted to the chassis.

Control Spindles

First cut the control spindles to a length of 22mm. Do not strain the control when doing this. Clamp the unwanted part of the spindle in a vice and hold the potentiometer end to steady it, while cutting the spindle with a small hacksaw. Then remove any burrs.

Assemble the controls into their respective positions on the mounting bracket and tighten all nuts firmly but do not overtighten. The bracket is fixed to the chassis front with countersunk 6BA screws, approximately 12mm long, and spaced from it with two 6BA nuts. Finally it is held in place with another 6BA nut and lock washer.

When fitting the socket for the headphones, the tags come up either side of the phone/speaker switch and should be bent slightly outwards.

When the heat sinks are satisfactory, they should be painted *mat* black and left to dry thoroughly before using.

Finally, make up the chassis base plate and the control mounting bracket as shown in Figs. 10 and 12.



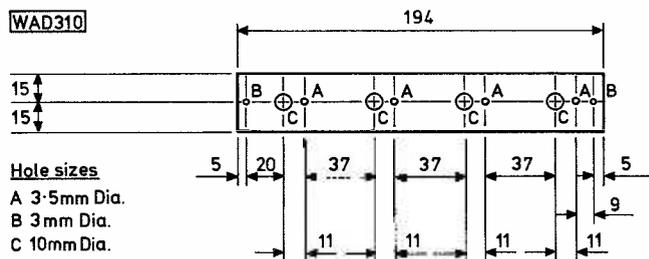


Fig. 12: Above, details of the control mounting bracket which is made from 1.2mm thick aluminium

Fig. 13: Below, the mounting details of the power f.e.t.s and heat sinks

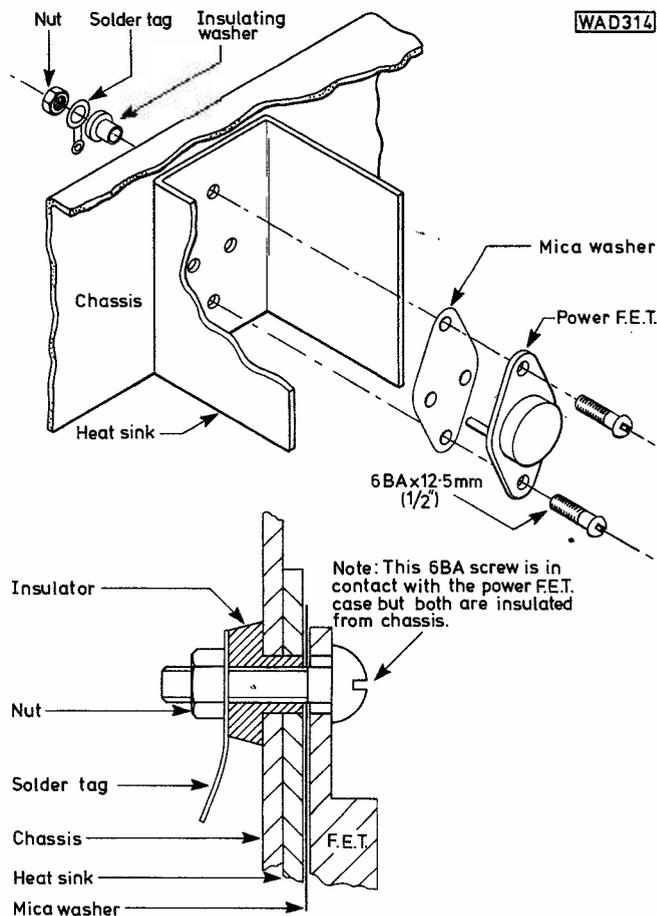

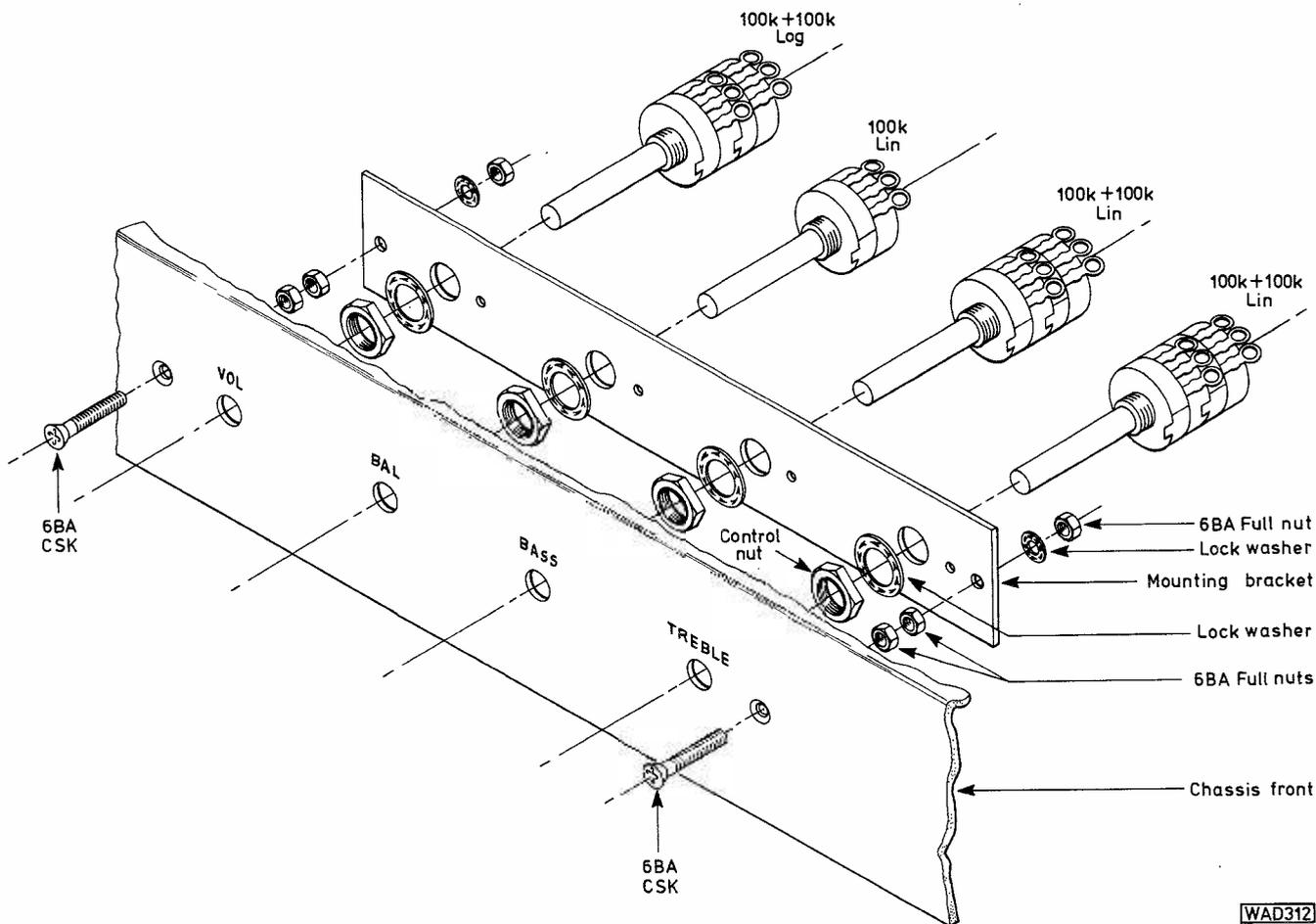

WAD312

Fig. 15: Method of mounting the control potentiometers using the pot mounting bracket


The black earth terminal on the rear of the chassis is mounted without its rear insulating washer to ensure a good electrical contact with the chassis (Fig. 11).


The output power f.e.t.s should be assembled onto the heat sinks and chassis as shown in Fig. 13, but it is very important to make sure that the pins do not touch the sides of the holes, and that the mica washers are not damaged. The use of a heat sink compound helps here. After assembly, a multimeter may be used to check for shorts between pins and chassis.

Both the 4700 μ F reservoir capacitors are held in place with plastic cable ties. Four large plastic cable ties are used to hold the special toroidal mains transformer and should be firm but not over tightened, otherwise they may distort

the chassis. A piece of foam is placed between the transformer and chassis to reduce vibration. This method of fastening the transformer to the chassis has been used instead of the bolt and plastic centre method as it has proved to be considerably cheaper and is just as easy and reliable. Do not be tempted to use metal ties, wire, or a bolt and clamp bar through the centre of the transformer, any of these methods can create a shorted turn, overloading the transformer. The i.e.d. used as an "on" indicator is a firm push fit into the hole provided.

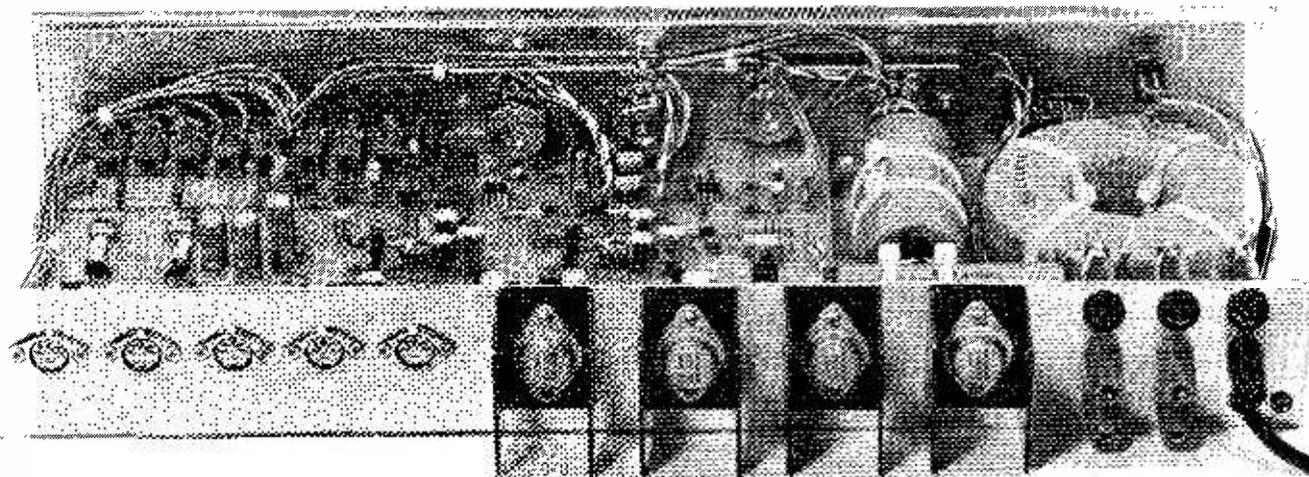Next month finishes the wiring of the amplifier and covers testing and setting-up procedures



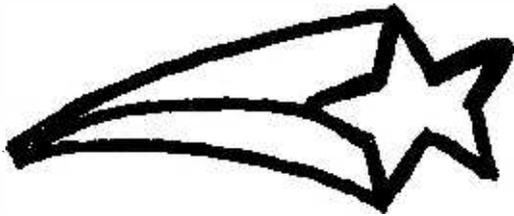

A NEW STAR ON THE WORLD'S HI-FI HORIZON.

PW
WINTON

PW and T. & T.

HAVE COLLABORATED TO BRING TO PW's READERS A WORLD FIRST ON THE HOME CONSTRUCTOR HI-FI KIT SCENE.

Ted Rule, a member of the design team of T. & T. Electronics was commissioned by P.W. to design a High Fidelity Stereophonic Amplifier in a form suitable for the Home Constructor which would supersede the now ageing "Texan".

This, bearing in mind the phenomenal success story of the Texan was a daunting brief for any design team, but we are both delighted and proud to announce that Ted as well as achieving his original design brief, has far exceeded it.

Ted, (who has 30 years experience in Hi Fi design) has excelled himself in producing the P.W. WINTON amplifier, which we sincerely believe to BETTER SIGNIFICANTLY ANYTHING CURRENTLY AVAILABLE TO THE HOME CONSTRUCTOR IN THIS POWER RANGE.

The almost unbelievable specification for this design (published in full in the WINTON article) was achieved by utilising the latest "state of the art" devices available including the revolutionary POWER MOS-FETS developed by HITACHI Ltd., and BI-FET Op Amps from TEXAS.

The HITACHI research has we feel rendered the use of Bi-Polar Power Output Transistors obsolete in any design which has any pretensions towards true HIGH FIDELITY.

Because we are so excited at the performance obtainable, and to avoid disappointment caused by the use of sub-standard components, we have decided to market a complete kit of parts to ensure that the Home Constructor can achieve the same superb results.

As with Rolls-Royce quality doesn't come cheaply, and we make no apologies at all for the fact that our kit costs a bit more than the average Bi-Polar design, we firmly believe that the standard of reproduction obtainable is a reflection in part of the quality of the components used in the kit, and that discerning Audiophiles the world over will recognise the inescapable truth that today you usually get just what you pay for.

The WINTON Kit is available in the following form:-

	Price Inc. V.A.T. & carriage.
Pack (A) Capacitors & Fixed Value Resistors	£21.45
Pack (B) Switches, Potentiometers, Pre-Sets & Knobs	£13.26
Pack (C) Printed Circuit Board, and Terminal Pins	£8.10
Pack (D) Hardware Pack, consisting of Chassis, Heat Sinks, Cabinet, Screws, Wire, Fuseholders etc., and a Brushed Aluminium Fascia Front Panel.	£32.99
Pack (E) Semiconductors (including HITACHI MOS Power Fets)	£30.53
Pack (F) Toroidal Mains Transformer	£17.22
Complete Kit of all parts necessary to build the WINTON	£120.00

ORDER WITH COMPLETE CONFIDENCE (Cash with order please) FROM:-

T. & T. ELECTRONICS. GREEN HAYES, SURLINGHAM LANE, ROCKLAND ST. MARY, NORWICH, NORFOLK. NR14 7HH. PLEASE ALLOW 28 DAYS FOR DELIVERY.

SCOOP THIS EXTRA!

40 PAGE KITS AND COMPONENTS GUIDE

Don't miss the new **Maplin** 40-page bound-in illustrated guide and price list in our **April issue!**

plus these projects:

- "Autoranging Multimeter" – 5-function autoranging AC/DC instrument for measuring voltages, current and resistance.
- "Phaser" – guitar sound effects unit with 6 phase-shift networks. Creates superb "atmospheric whooshing"!

and

- Electronic Door Bell
 - Bubble Memories
- progress with

PRACTICAL ELECTRONICS

April issue

MAINS TRANSFORMERS

All these have 230/240v 50Hz
All these have 230/240v 50Hz Primary

Voltage	Our Ref.	Price	Post
1v	2 amp TM 1	£1.94	40p
2-4v	2 amp TM 2	£1.62	45p
4v	7 amp TM 32	£2.70	60p
6v	1 amp TM 3	85p	40p
6.5v	1 amp TM 37	85p	40p
6.5v	200 mA TM 21	£1.62	40p
6.5v-0-6.5v	100 mA TM 21	£1.62	40p
6.5v-0-6.5v	750 mA TM 7	£2.16	45p
6.3-0-6.3v	100 mA TM 33	£1.62	40p
6.3v	2 amp TM 4	£1.89	50p
8-5v	1 amp TM 12	£1.62	40p
8-5+8-5v sep. winding	1 amp TM 12	£1.62	40p
9v	1 amp TM 5	£1.62	45p
9v	3 1/2 amp TM 11	£2.70	50p
9v	5 amp TM 38	£3.24	60p
10v	25 amp TM 15	£4.86	£1.25
10v-0-10v	4 amp TM 50	£3.78	£1.25
10v-0-10v	12 1/2 amp TM 15	£4.86	£1.25
12v	1 amp TM 9	£1.05	50p
13v	100 mA TM 21	£1.62	40p
13v	3 amp TM 7	£2.16	50p
12v	1 amp TM 10	£1.89	50p
12v-0-12v	50 mA TM 19	£1.62	40p
12v-0-12v	1 amp TM 41	£3.24	50p
15v tapped 9v	2 amp TM 11	£2.70	50p
17v	1 amp TM 12	£1.62	50p
18v	1 amp TM 13	£1.90	50p
20v	1 amp TM 14	£1.62	50p
20v (with 6v 1/2 amp)	2 amp TM 50	£3.78	£1.25
20v	6 amp TM 46	£4.32	£1.25
20v	12 1/2 amp TM 15	£4.86	£1.25
20v-0-20v	6 amp TM 15	£4.86	£1.25
24v	1 1/2 amp TM 16	£2.12	60p
24v	2 amp TM 17	£2.70	60p
24v+2v 7 amp	2 amp TM 39	£2.97	70p
24v	4 amp TM 40	£3.78	80p
25v	1 1/2 amp TM 18	£2.43	60p
26v	2 amp TM 39	£2.98	60p
30v	8 amp TM 15	£4.86	£1.25
37v	37 amp TM 34	£31.86	enquire
40v	3 amp TM 46	£4.32	£1.25
40v	6 amp TM 15	£4.86	£1.25
40v	8 amp TM 15	£4.86	£1.25
40v-0-40v	2 1/2 amp TM 48	£5.02	£1.25
50 & 8-3v	2 amp TM 22	£4.86	£1.25
50v	8 amp TM 29	£11.65	£1.75
60v tapped 40v & 20v	2 amp TM 46	£4.32	£1.25
70v	4-5 amp TM 24	£7.02	£2.50
75v and 63v	3 amp TM 23	£8.10	£2.00
75v	4 1/2 amp TM 24	£7.02	£2.50
80v tapped 70v & 75v	4 amp TM 24	£7.02	£2.50
80v centre tapped	2 1/2 amp TM 48	£5.02	£1.25
100v	1 amp TM 25	£7.02	£1.75
100v-0-100v	1 amp TM 25	£7.02	£1.75
200v	1 amp TM 25	£7.02	£1.75
250v-0-250v & 6-3v	50 mA TM 36	£3.78	£1.00
000v	100 mA TM 36	£3.78	£1.00
500v	50 mA TM 36	£3.78	£1.00
260v	60 mA TM 26	£3.24	£1.00
1000v	60 mA TM 43	£6.80	£2.00
4 kv	5 mA TM 49	£4.05	70p
5 kv	5 mA TM 30	£7.02	£1.00
8 kv	5 mA TM 45	£4.05	£1.00
8-5 kv	10 mA TM 31	£10.26	£2.00

Full range of Mains to 120v Auto transformers available.
Pot Cores. We have now received our delivery of Ferro pot cores. These are ex unused equipment. They contain the bobbins but of course these have to be wound and you would have to unwind. Three pairs available.

Diameter	Thickness	Price	
FX 2243	4.5 cm	81	per pair
FX 2242	4.5 cm	70	
FX 2240	2.5 cm	1-6 cm	60

Quantity discounts apply.
Component Panel Ref. 3055. Taken from unused P.S.U.'s, these contain 4 x 2N 3055 power transistors with mica insulators all on heat sink and 4 variable pots, preset type with spindle locks. Real bargain at £1.08 each.

Component Board 421. Again from unused equipment, major items on these are two power silicon transistors, Motor Rola ref. SJ 5433 mounted on a heat sink with mica insulators, also behind the panel are two power rectifiers ST NS 1008. Price 95p.

E.H.T. Mains Transformer. With inductance control, normal primary and output voltage approx. 4kv 3mA. Voltage can be varied by applying DC to lower bobbin. Unused, ex P.S.U.'s Price £4.32.

Music Centre Dust Cover. Size 12" x 10" x 1 1/2" with attachments for hinging. Price £2.95. Callers only.

Telephone Answering Machines. Used, but apparently complete and being in working order. However, we are allowed to supply these only for breaking up, they should be very suitable for conversion to open reel tape recorder, background music machine, echo chamber, etc. All untested but we guarantee to replace any major item in the machine should it be faulty. Machines less over case £7.50, case slightly broken but substantially whole £10.26. Unbroken cases £12.45, and finally with new looking cases £14.50. Post £2.50 per machine. Many accessories available for these machines. Please enquire.

Wall Mounting Thermostat. The Satchwell room stat. Mains 20 amp settable over normal air temperatures between 30-80°F, suitable also for greenhouse control. Nicely finished in white enamel. Price £3.25.

10 r.p.m. Motor with 230v mains coil, not like the usual of these geared motors this has a good length of 1" shaft. Price £2.50 + 20p.

Rigonda Intermeezo 10 + 10 hi-fi amplifier with belt driven record deck with speed control and strobe check. The best hi-fi offered by Rigonda original selling price was in excess of £125. We have approx. 50 of these unused but with various faults. Untested, believed complete except for cartridge and speakers. Offered at £33.50, less than the price of the very high quality deck incorporated. If cannot collect add £3.00 to cover the special packing and carriage charge.

MINI-MULTI TESTER
Amazing, deluxe pocket size precision moving coil instrument—jewelled bearings—1000 opv—mirrored scale.

11 instant ranges measure—
DC volts 10, 50, 250, 1000,
AC volts 10, 50, 150, 1000,
DC amps 0-1 mA and 0-100 mA,
Continuity and resistance 0-150K Ohms.
Complete with insulated probes, leads, battery, circuit diagram and instructions.
Unbelievable value only £6.50 + 50p post and insurance.

MULLARD UNILEX

A mains operated 4+4 stereo system. Rated one of the finest performers in the stereo field this would make a wonderful gift for almost anyone in easy-to-assemble modular form and complete with a pair of Plessey speakers this should sell at about £30—but due to a special bulk buy and as an incentive for you to buy this month we offer the system complete at only £16 including VAT and postage.



As illustrated with sun correction made for G.P.O. phone boxes used perfect £2.95 20 amp switching contacts.

24 HOUR TIMERS VENNER

SHORTWAVE CRYSTAL SET

Although this uses no battery it gives really amazing results. You will receive an amazing assortment of stations over the 19, 25, 29, 31 metre bands. Kit contains chassis front panel and all the parts £1.94—crystal earphone 55p including VAT and postage.



SOUND TO LIGHT UNIT

Add colour or white light to your amplifier. Will operate 1, 2 or 3 lamps (maximum 450W). Unit in box ready to work. £9.95.



BREAKDOWN PARCEL

Four unused, made for computer units containing most useful components, and these components unlike those from most computer panels, have wire ends of usable length. The transistors for instance have leads over 1" long—the diodes have approx. 3/4" leads.



List of the major components is as follows:—17 assorted transistors—38 assorted diodes—60 assorted resistors and condensers—4 gold plated plugs in units which can serve as multipin plugs or as hook up boards for experimental or quickly changed circuits (note we can supply the socket boards which we made to receive these units). The price of this four unit parcel is £1 including VAT and post (considerably less than value of the transistors or diodes alone). DON'T MISS THIS SPLENDID OFFER.

TANGENTIAL HEATER UNIT

A most efficient and quiet running blower-heater by Solatron—same type as is fitted to many famous name heaters—Comprises mains induction motor—long turbo fan—split 2 kw heating element—and thermostatic safety trip—simply connect to the mains for immediate heat—mount in a simple wooden or metal case or mount direct onto base of say kitchen unit—price £4.95 post £1.50 control switch to give 2kw, 1kw, cold blow or off available 60p extra.




3KW MODEL £5.95 + £1.50 P & P

2 kw. model made in metal case with control switch £12.00


MOTORISED DISCO SWITCH

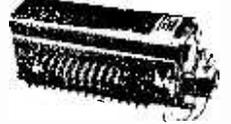With 10 amp changeover switches. Multi adjustable switches are rated at 10 amps. This would provide a magnificent display. For mains operation 8 switch model £5.25, 10 switch model £5.75, 12 switch model £6.75.



FLUORESCENT TUBE INVERTOR

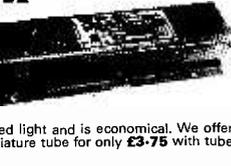For camping — car repairing — emergency lighting — from a 12v battery you can't beat fluorescent lighting. It will offer plenty of well distributed light and is economical. We offer inverter for 2' 13 watt miniature tube for only £3.75 with tube and tube holders as well.



RELAYS

12 volt 2 10 amp changeover plug in 95p.
12v three 10 amp changeover plug in £1.28.
12v two changeover miniature wire ended 95p.
12v open single screw fixing two 10 amp changeover 85p.
12 volt open three 10 amp changeovers £1.25. Latching relay mains operated 2 c/o contacts £2.11. Mains operated three 10 amp changeovers open type one screw fixing £1.25. Many other types with different coil voltages and contact arrangements are in stock, enquiries invited.



Terms: Prices include Post & VAT. But orders under £6.00 please add 50p to offset packing. Bulk enquiries—Please Phone for Generous Discounts 688 1833.

Access and Barclaycard accepted
J. BULL (ELECTRICAL) LTD
(Dept. E. E.), 103 TAMWORTH RD., CROYDON CR8 1SG

IT'S FREE

Our monthly Advance Advertising Bargains List gives details of bargains arriving or just arrived—often bargains which sell out before our advertisement can appear—it's an interesting list and it's free—just send S.A.E. Below are a few of the Bargains still available from previous lines.

FM Tuner and decoder. 2 very well made (Japan) units, nice clear dial, excellent reproduction. £11.20 the pair.

12 Volt Heavy Duty Relay. plug in tape has three pairs of 10 amp changeover contacts. A transparent dust cover. Price £1.08 suitable 1 1/2 pin base 45.

4 Changeover Relay. upright mounting 4 sets of 10 amps changeover contacts, mains voltage coil £1.72.

12 Volt Pump. Designed we believe as a bilge pump, this is 12 volt AC/DC motor coupled by a long enclosed shaft to a submersible pump. Suitable for water or most any fluids. Price £12.50.

High Load 24 Hour Clock Switch. made by the famous Smiths Company for normal mains but with clockwork reserve has load capacity of 80 amps at 240V 50HZ. Therefore suitable for dealing with large loads of say shop lighting, water heating, storage heaters, etc., etc. Has triggers for on and off once per 24 hours but extra triggers will be available. Price £1.50 per pair, totally encased. Price £9.50.

Enclosed 24 Hour Clock with contacts for breaking 10-12 amps at 240 volts. This one has two sets of on/off per 24 hours, price £7.00.

Light Dimmer. our timer module with small mods makes an excellent light dimmer. Contains a 4 amp 400V SCR so it should be suitable for loads approaching 1KW. Price of module and instructions £2.25.

Push Pull Solenoids. mains operated solenoids which will push as well as or instead of pull. Very heavy duty, estimate this at 20lbs push or pull 1 1/2" x 3 1/2" 4" made Magnetic Devices Co. £7.50.

Flashing Lights. chasing lights, random finishes, strobe effects etc., etc., can easily be achieved using our 240v AC/DC switches for mains working. To get some idea of loading number, each switch is 10 amp. For the light pipe or Catherine Wheel effect order the 12 switch model with light pipe data model, interconnecting the switches to give fastest speed, 6 Switch model £5.9 Switch model £9.75. 12 Switch model £8.20.

Reed Switches. standard 60 watt glass type. Normal open contacts glass lengths 2" diameter 3/16", 10 for £1, 100 for £8, 1000 for £70.

Flat Reed Switches. for stacking, greater quantity in confined space. Price £50p.

Ceramic Magnets. suitable for operating Reed switches, central fixing hole, 10 for £1.

Music Centre Transformer 12-0-12 at 1 amp and 9 volt at 1/2 amp. Normal primary, uprighting, impregnated and varnished for quiet operation. Price £3.50.

'W' Shaped Fluorescent Tubes for porch light, box signs or where you want light evenly spaced over a confined area of approx. 10" x 10", 20 watts made by Philips, price £2.24.

Extension Speakers. 8 ohm 4-5 watts handling power. We have 5 or 6 different models in stock, cheapest being the Partytime at £3.95 each, again only really a bargain for callers as postage is £1.50 per speaker.

Auto Transformers for working American tools and equipment, completely enclosed in sheet metal case with American type flat output socket made for computer so obviously first class 500 watts. With kang handle, offered at about half price only £15. These may be a bit soiled but are fully guaranteed. Similar but 1000 watt for £25.00.

Car Starter Charge Kit. New version. We supply two 10 amp rectifiers, 250v transformer and the start charge switch with instructions. Price £9.75. This is probably one of the most useful pieces of equipment you can have in your garage. Sooner or later you or someone will leave something on and you will have a flat battery, this starter will get you away usually in less than 5 minutes.

Resetter Counter. by Vedroot Company, 230/240v mains operated, intended for surface mounting has a fixing flange at the bottom. Price £2.16.

12V Drip proof Relay. Specially designed for going under the bonnet of a car, made by one of our big manufacturers, this really has a removable semi-hard rubber cover. Contacts lock suitably for up to 10 amps so this could be the right one. If you are thinking about making an anti-theft device. Price £1 + 8p.

High Speed Unilexector. As many customers know, we have a very comprehensive stock of unilexectors as used in automatic telephone exchanges, light flashing device etc., etc. Just arrived however is a high speed model made by famous Plessey, this is 2 pole 22 watt make before break wipers, overall size approx. 4" x 3" x 2 1/2", price £3.50 + 28p.

Pneumatic Ram for lifting, thrusting, pulling etc., has 2 1/2" travel, looks large enough to open doors, lift, staircase, ventilators, etc. Price £7.00.

Solder Gun Bargain. The ETP, this is 100 watt solder gun, a very well made tool with lamp to illuminate work has double insulated mains transformer and is built into the shock proof thermoplastic case. Comes complete with spare tips. Mains operated of course. Price £4.50.

Interested in Tape Control. American made tape punches, really beautiful units made of sophisticated parts, designed we believe to automatically operate typewriters and they can of course be used to operate other punch tape controlled machines. Reference number is NCR Class 461-2 reference 205 H8 R56. We believe these are 8 bit paper tape punches, powered from 115V 50HZ in very good condition with tape £16.00, carriage is £3.20.

Resettable Fuses (thermal trips). Two new types have come in, one made by ETA is a 6 amp model which is mounted through a single hole rather like a volume control. This is suitable for 250 volt AC or 4 volts DC. Price 54p. **4.5 Amp Model** made by AEG is held by two screws thus a bank of these could be mounted between metal straps. Price 54p.

Disc Motor. mains operated. This is very thin in fact less than 1/2" thick and only approx 2" dia. Spindle revolves at 2500 rpm and the spindle which is approx. 1/32" dia. pushes through so motor could be used to drive clockwork or anti-clockwork. The spindle being a friction fit can be pushed completely out and replaced by your own spindle, a knitting needle for instance. Price only 38p.

75 rpm Mains Induction Motor with gearbox. This motor is quite powerful and has 1 1/2" stack and the final 75 rpm drive shaft is 1 1/2" long by 3/8" dia. The motor also has a spindle coming from the opposite end to which could be fitted another pulley. Overall size approx. 3" x 5" x 2 1/4" + spindles. Price £3.35.

24 Hour Motor. beautifully made by Sangamo. This is 200-240v mains driven motor with gearbox together in one housing, size approx. 1 1/2" dia. by 1 1/2" deep. If you are contemplating making a 24 hour switch with a lot of on/off's, then this is obviously the motor. Price £1.89.

PRODUCTION LINES

alan martin

If you please


Would readers kindly mention "Production Lines", when applying to manufacturers or suppliers featured on this page.

Pattle's panels

We all know the problems of making a really good front panel for our projects. Dymo tape and typed sticky labels are no substitute for a photographically reproduced anodised aluminium panel. Several of our recent projects have featured front panels professionally made by D. J. Pattle to our designs. These panels are available to readers and come in a variety of styles, colours and thicknesses.

The thin type is available, self-adhesive backed, ready to be cut out and mounted on to a sub-panel. A full thickness aluminium version is available which also acts as the front panel.

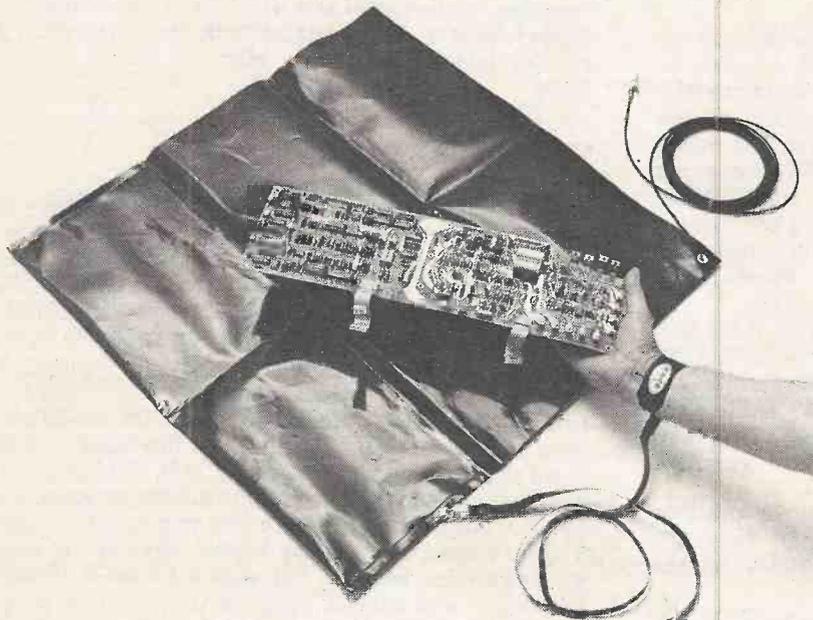If you want to add a touch of class to your shack, then the aluminium RSGB badge with your callsign across the centre, is available to order from Pattle. Full details and prices from: *D. J. Pattle, Juniper, Hillbury Road, Alderholt, Dorset. Tel: Fordingbridge 52081.*




Battery holder

Most small equipment enclosures on the market today make no provision for battery housing and dismantling a complete instrument in order to replace an exhausted battery is both tedious and time consuming.

Vero Electronics Ltd. now make available an injection-moulded battery housing of simple clip-in design offering access for battery changing from outside the instrument.

The holder accepts a 9V battery and may be easily fitted to a panel or enclosure with a thickness of 1.5 to 3mm. All that is required for fitting is a rectangular cut-out into which the holder is pressed home.

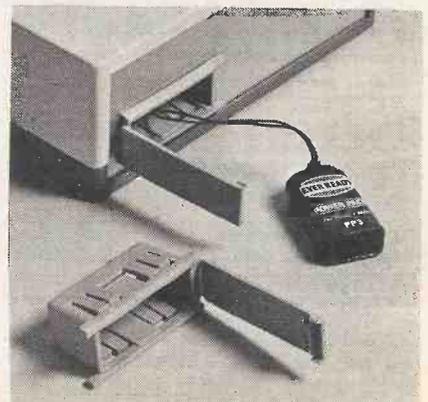Supplied as a kit, the battery holder comes complete with connector and lead for less than £1. Further details from: *Vero Electronics Ltd., Industrial Estate, Chandler's Ford, Eastleigh, Hants SO5 3ZR. Tel: (042 15) 69911.*



Grounded

A portable field service kit which can prevent electrostatic charge from damaging sensitive electronic components during construction or servicing operations is now available from 3M UK Ltd.

This is the "Velostat" 8005 Field Service Grounding Kit, which provides an effective method of draining electrostatic charge from the individual to ground before it can damage or destroy sophisticated components, such as MOS, bi-polar devices and micro-processors.

Research has shown that thousands of volts of electrostatic charge can be


generated and stored in a technician's body by simply walking across floors and sliding on and off stools. When the individual then handles a p.c.b., the electrostatic charge flows from him through the circuitry, literally blowing components.

The kit consists of a "Velostat" Table Top (614mm square), a conductive wrist strap and a ground cord. The Table Top has convenient storage pockets and can be rolled or folded to fit neatly in tool cases.

For details of price and availability contact: *3M United Kingdom Ltd., 380-384 Harrow Road, London W9 2HU. Tel: 01-286 6044.*

LOGICAL NOUGHTS & CROSSES

J.D. MITCHELL PART I

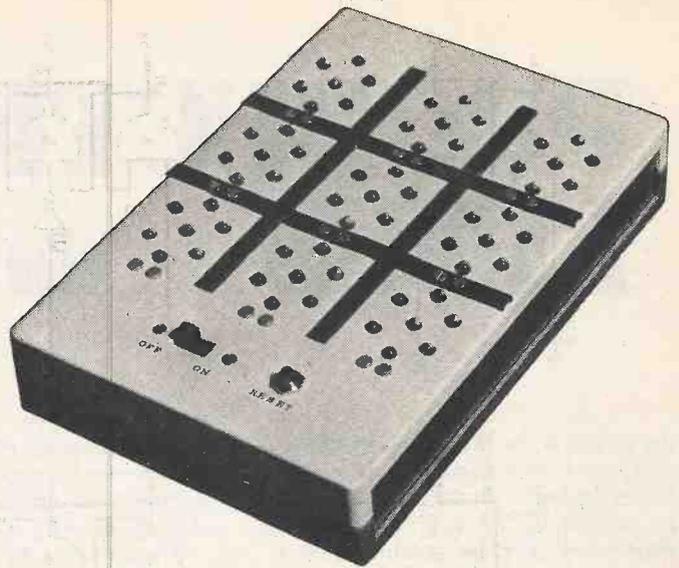

The game of Noughts and Crosses presented here is a less ambitious development than the automated opponents currently advertised, but has proved itself a source of great interest to friends and offspring alike. Babysitters particularly appreciate trying to beat the "computer" after the television closedown.

The game uses TTL integrated circuits, directly driven i.e.d. displays, and inputs are made by touch-switches or alternatively with a simple prod. The circuit automatically remembers the first input and sets its program for the remainder of the game. With the advantage of first move, the player may win 126 or 16 of the 945 different possible games as explained later. This facility was added at the cost of a few extra gates. The programming could have been wired to win or draw only, but there is little interest in competing against an infallible opponent. Mis-switches cannot override previously lit noughts and crosses.

Identifying the board squares as in Fig. 1(a), if the first input is to any outer square the reply is to 5. Should the first move be to square 5, the reply is to 1. The first reply is directly gated, but this is not possible for subsequent replies and a 9-bit event latch is used to set a program. The programs set by the first input made in each game are identified as in Fig. 1(b).

Figure 2 details the event latch, gating for the first reply, input latches which store the momentary Logic 0's from the touch-switches or probe, and display latches which directly drive the i.e.d. displays.

Six input latches are contained in IC13, type SN74118. The other three are cross-coupled 2-input NAND gates type SN7400. Capacitor C1 connected to the reset input prevents the discrete latches setting in the opposite polarity to those in IC13 on powering the circuit. All other capacitors shown are for decoupling.

Display latches

The display latches operate differently to the usual set-reset of the input latches. Initially, both inputs are at Logic 0. When one input is switched to Logic 1, both inputs to one gate are then at 1 and its output is at 0. The display in that square is thus lit.

Display gating for squares 2, 4, 6 and 8, Fig. 2(b) are modified forms of the above latches. If a nought or cross input is made first, the display will be lit accordingly. If the third (inhibit) input is made first, a nought cannot then be

displayed although a subsequent cross can. Five 3-input NAND gates are also used in the gating. Outputs from these are connected to the inhibit inputs of the latches. Two are spare type SN7410 as used in the 3-input display latches. The other three are type SN7412 (o/c collector) so that two may be connected as a wired-OR to the inhibit input of display latch 4. These latches with their associated gates prevent replies being made after the player has won a game.

Wired-OR gates

The 9-bit event latch comprises IC10 and square 5's input and display latches. IC10 is a dual 4-bit latch with clear inputs, type SN74116. Each 4-bit latch also has two enable inputs, which are connected as two pairs on PCB 1. All outputs from IC10 are connected as a wired-OR gate into one pair of enable inputs. The other enable inputs are connected to the \bar{Q} output from square 5's input latch. When either pair of enable inputs is switched from Logic 0 to 1, all eight latch outputs are held in the condition they were in previous to the switch. If the first input switched is 5, all outputs from IC10 are held at 0. Display latch output 5x is enabled, and inverted to enable program E. Output E is inverted again to enable display latch output Io. The inverters buffer display latch 5. Should any other input be switched first (say 3x), output 3 from IC10 switches to Logic 1 and enables program C. The other programs remain disabled by the output of the wired-OR gate, whilst display latch output 50 is enabled.

The nine outputs from the event latch circuit are taken to PCB 2 where they are connected with eight of the Input latch \bar{Q} outputs in a gated matrix. Input latch 5 is not re-

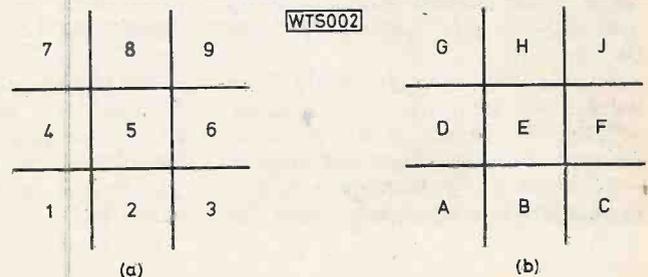


Fig. 1: The identification of the squares on the board

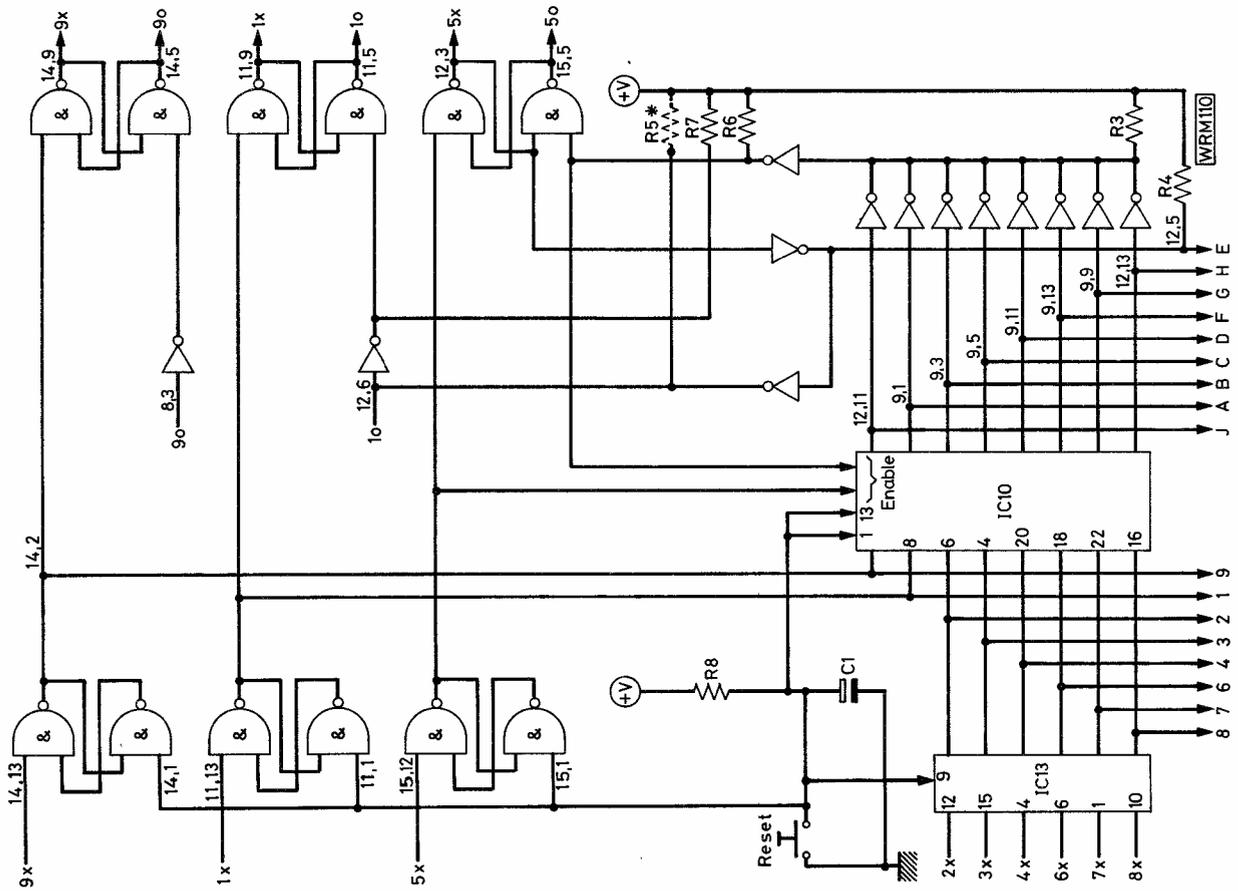


Fig. 2(a): The input latches are contained in IC13, an SN74118. The 9-bit event latch is made up from IC10 (SN74116) and square 5 input and display latches. C1 is to prevent the discrete latches from setting in the opposite polarity to those in IC13 when power is applied



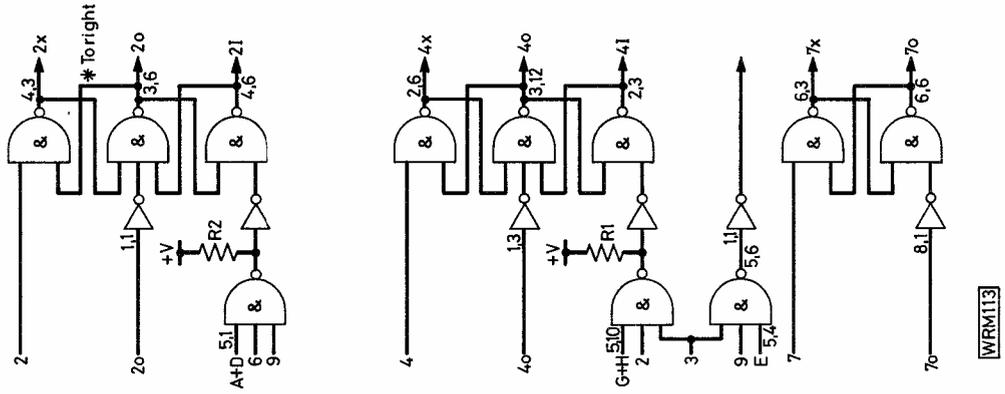


Fig. 2(b): The display gating for squares 2, 4, 6 and 8 are shown in this drawing. These gates ensure that the correct symbol is displayed in the appropriate square

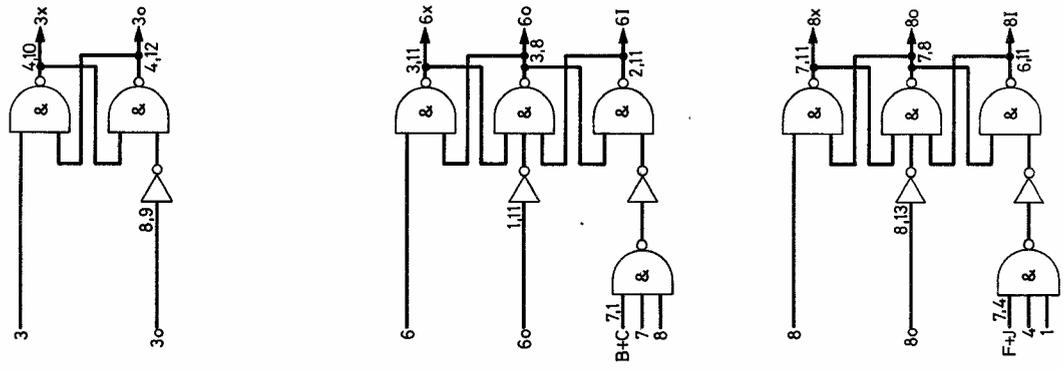

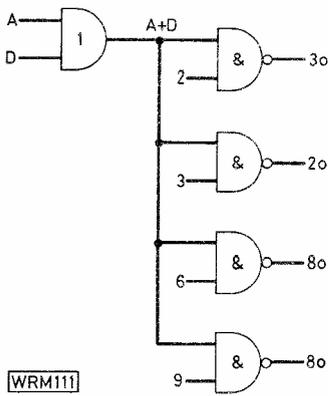

Wired prog. o/p connections to nought display latches													
Inputs	A	B	C	D	E	F	G	H	J	A+D	B+C	G+H	F+J
1	-	3	2	7	-	-	-	-	-	-	-	4	2
2	-	-	1	-	8	1	-	-	4	3	-	6	-
3	-	1	-	-	7	9	-	-	6	2	-	6	-
4	7	7	8	-	6	-	-	-	-	-	-	1	2
5	-	-	-	-	-	-	-	-	-	-	-	-	-
6	-	-	-	-	4	-	2	3	3	8	9	-	-
7	4	-	-	1	3	-	-	9	-	-	4	-	8
8	6	-	-	9	2	-	9	-	-	-	4	-	7
9	-	-	-	-	7	3	8	7	-	8	6	-	-

Fig. 3: Circuit board 2 connects the nine event latches to eight of the input latch \bar{Q} outputs in a gated matrix. All outputs with the same numbers are 'wired-OR' connected to the appropriate resistor on Board 2 and then to Nought inputs of display latches on Board 1

★ components

Resistors

$\frac{1}{2}W$ 2% metal oxide

270 Ω	9	Display
1k Ω	10	R8 and input switching
1.2k Ω	2	R3, 9
1.5k Ω	1	R14
1.6k Ω	5	R10, 11, 12, 13, 15
2k Ω	1	R16
2.2k Ω	9	Input switching
4.7k Ω	2	R1, 4
7.5k Ω	1	R6
9.1k Ω	3	R2, 5, 7

Capacitors

Disc Ceramic

0.01 μF	7	Decoupling
--------------	---	------------

Tantalum bead

22 μF 6V	1	C1
---------------	---	----

Semiconductors

Diodes

1N4001	1	D1
Red i.e.d.	63	Display

Transistors

BC108C	18	
--------	----	--

Integrated circuits

SN7400	6	IC2, 4, 6, 11, 14, 15
SN7403	12	IC17, 18, 19, 20, 21, 22, 23, 24, 25, 26, 27, 28
SN7404	2	IC1, 8
SN7405	2	IC9, 12
SN7410	2	IC3, 7
SN7412	1	IC5
SN7432	1	IC16
SN74116	1	IC10
SN74118	1	IC13

Miscellaneous

Push-to-make switch (1), miniature slide switch (1), Battery holder B203 (1), Verocase 205 x 140 x 40mm (1), Veropins, nuts, bolts, washers, printed circuit boards (set of 4).

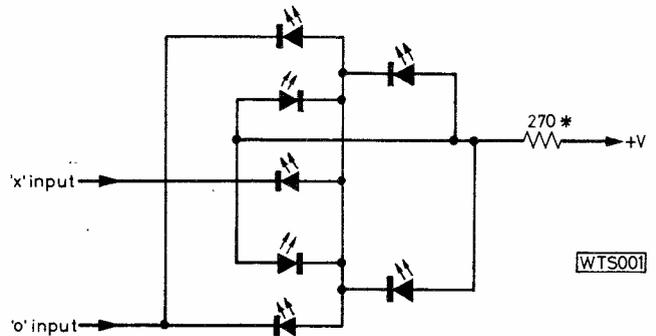


Fig. 4: Circuit diagram of one i.e.d. display. This forms the display for one square and nine of these are required for the complete game. The 270 Ω resistor is the approximate value needed to limit total current to 10mA

quired because of the direct gating used for the first reply. 2-input o/c collector NAND gates type SN7403 are used for the matrix, their outputs connected as wired-OR gates—see Fig. 3. To reduce the number of gates in the matrix, four 2-input-OR gates type SN7432 are used to provide outputs A + D, B + C, F + J and G + H. The NAND gate outputs are connected back to inverters on PCB 1 and then to the nought inputs of the display latches.

Outputs

Outputs from the display latches are connected directly to the display i.e.d.s, which are interconnected and positioned as shown in Fig. 4. Initially, both outputs of a latch are at Logic 1. If the "X" input to a display is switched to 0V, current flow is from the positive rail via the four corner-mounted i.e.d.s, through the centre i.e.d. into the gate, displaying a cross in the appropriate square. If a "O" input to a display is switched low, current flow is via the corner i.e.d.s and through the top and bottom i.e.d.s to show a nought. The resistor is selected to limit current to 10–15mA.

PART 2 will cover the construction of this interesting project together with the circuit diagrams and printed circuit board layouts

HOTLINES

A REVIEW OF RECENT DEVELOPMENTS

In general, the author does not have any more information on products than appears in the article.

Lasers Again

Readers may remember the fuss over using lasers as part of London's Christmas decorations last year. Apparently some thought the beams would constitute a hazard.

In the American town of Atlanta they've been using lasers for some time to control traffic lights. Before anyone sees "red", the health hazard is virtually nil and the system has been given a fond, approving kiss by the US Bureau of Radiological Health Standards as being "safe for eyes".

Previously, the digital computer that controls the city's traffic lights was coupled to the lights via telephone lines, or by dedicated cables. The system can control up to 500 separate road junctions. At each set of lights is an optical transceiver that faces its neighbour at another junction.

Sensors, in the road, monitor the traffic density and this information is fed back along the laser chain to the computer. The digital computer "computes" all this information and, having computed sends a master command signal to the relevant traffic lights.

Tests on the laser's range showed reliable operation at distances of well over $\frac{1}{4}$ mile even in the very worst weather conditions (such as heavy fog, etc). In a good, clear, typical English summer's day (singular!) type weather, the range approaches 10 miles.

Peak power outputs of the GaAs laser diodes used are around 10W, and these are pulsed at 2kHz.

A shining example to traffic light manufacturers everywhere.

Thermometers

For those with an interest in electronic thermometers, keep an eye open for the magic number AD590. It's a completely self-contained temperature transducer with an accuracy of $\pm 0.5^\circ\text{C}$ over the temperature range -55°C to $+150^\circ\text{C}$. And it's only "transistor size" being housed in a standard TO-52 can. Better still, there are only two leadout wires.

During manufacture, the resistive elements are precision laser trimmed to precise values. The result is a sensor that is linear over the range. So much so that you can plug in different ones without any need to recalibrate. For the technical buffs, the output is $298.2\mu\text{A}$ at 298.2K (that's 25°C) and any tem-

perature change up or down gives a $1\mu\text{A/K}$ variation.

The cheapest version costs barely the equivalent of a single British quid. A miniature, ceramic flat pack version is also available. Note that these are the prices for 100 off, though!

Stronger yet Faster

High gain-bandwidth product and high collector-emitter breakdown voltage are two conflicting ideals according to many bipolar transistors. These comments are particularly pertinent in the field of switching applications.

The Japanese think they've found an answer, and it's quite a clever one. They've combined a field-effect transistor gate structure with a standard bipolar transistor. One of the beneficial effects observed is that, assuming the same base width, where a particular conventional transistor had a breakdown voltage of say 20V, the new hybrid would make this figure 200V.

Not only does the new structure give a ten times increase in breakdown voltage, but it also offers a four times increase in gain-bandwidth product. One set of figures quotes 80MHz/500V.

Midget Supplies

Ever since the advent of switching power supplies, these items seem to have shrunk ever smaller. An American company began one power supply development programme by asking itself a question. "As digital panel meters get smaller and smaller, how will they be able to keep the useful feature of being operable from d.c. supplies and mains?" Pointless to have a beautiful, small d.p.m. only to find a dirty great power supply (by comparison) is required to power it.

Since many miniature d.p.m.s use c.m.o.s. and require only small currents and voltages, their power needs are not great, never-the-less with mains one side and a d.c. voltage the other, something very small has to go in the middle.

The result is the $\mu\text{S-A}$ series power supplies. They measure only 12.5mm cube and will supply from 1.5 to 15V d.c. from a 120 or 240V a.c. mains supply. They don't mind if the frequency of that supply is anywhere be-

tween 47Hz and 440Hz. The one-off price in the US is about the equivalent of £4 sterling. But the 100 off price plummets to just over £1.

Tiny Switch

Always well worth watching is the International Electron Devices Meeting. Among the many fascinating papers that caught my eye was one which described a small electro-mechanical switch. And when I say small, I really do mean small with a very little "s". This intriguing device is built using semiconductor technology. The switching cantilever is just 76 micrometres long. It is fabricated from a very thin layer of metal coated on a membrane of silicon dioxide. The membrane itself certainly isn't very thick, either; only 3500 Ångströms! Switching takes place by electrostatic action on the membrane. Switching time is around 40 millionths of a second using a "switching" voltage of 60V. The author claims the higher voltages give even shorter switching time—but one then starts to get contact bounce.

An important aspect of this new device is that the switch (or switches) could be fabricated on the same chip as the active devices.

A parting shot. It is thought that, after development, these tiny switches could be made to function at switching times to the order of 10 μs using 30V max. and with a current carrying capability exceeding 100mA.

Although obviously in its infancy, the idea seems to be promising when one examines the prototype test figures. Some of the switches under test in the laboratory have exhibited lifetimes of over 2 million switching operations while switching current densities of 5×10^4 amperes per square centimetre.

It might be as well for readers who are avid constructors to purchase a powerful watchmakers glass as a precautionary aid to future projects!

Ginsberg

DEVICES & CIRCUITS

PART 1

M. J. DARBY

In previous articles we have seen how a basic f.m. receiver functions, and have also considered front-end devices and circuits in detail.

However, many f.m. transmissions carry stereo information, and this part of the series deals with the essentials of the stereo decoder.

The Multiplex Signal

The audio output from the demodulator of a stereo receiver consists of both audio frequencies and ultrasonic frequencies which carry the required information for both the left and right hand channels. These two channels are said to be "multiplexed" so that they can be present as a single signal. It would obviously be very uneconomical to employ two separate transmitters for the left and right hand signals.

The multiplex signal from the output of the receiver demodulator circuit contains a number of parts which are illustrated in Fig. 1 and listed below.

1. The audio frequency band from about 30Hz up to 15kHz contains the required audio signal and constitutes the sum of the signals in the left and right hand channels. In a monaural receiver, only this part of the signal will provide the output in the loudspeaker.

The transmitted signal is thus "compatible", which means that the one signal can be used to operate both monaural and stereo radio receivers.

2. A 19kHz pilot tone which is transmitted at a relatively low signal level. This pilot tone is required for the operation of the stereo decoder circuit; if the tone is not present in any signal (or not present at an adequate amplitude), the stereo decoder circuit will switch to the monaural mode and the same signal (left-plus-right) will be fed to the two speakers.

3. A left-minus-right signal which is modulated onto a 38kHz sub-carrier signal. The sub-carrier itself is suppressed so that there is a small gap of about 60Hz in

width at 38kHz. The left-minus-right signal covers a frequency band of about 30Hz to 15kHz. The sub-carrier modulation process generates signals of $38\text{kHz} \pm$ (left-minus-right frequency); this means that the lower sideband of the sub-carrier extends from $38 - 15 = 23\text{kHz}$ up to within 30Hz of the 38kHz frequency, whilst the upper sideband extends from 30Hz above 38kHz up to $38 + 15 = 53\text{kHz}$. The upper and lower sidebands are shown in Fig. 1. The 38kHz sub-carrier itself has an amplitude which does not normally exceed 1% of the total signal amplitude.

It is obvious from Fig. 1 that the stereo multiplex signal has a much wider bandwidth than the monaural signal which extends up to only 15kHz. This wide bandwidth inevitably results in more noise being present in a stereo signal than in the same signal in the monaural mode. In practice the degradation in signal-to-noise ratio is some 20dB, so a much better aerial is required for good, low noise stereo reception than is necessary for good reception of the same signal in the monaural mode.

When a broadcast is to be monaural for a period of more than a few minutes, the pilot tone at the 19kHz frequency may be switched off so that stereo receivers are switched to the monaural mode. This automatically ensures that the optimum signal-to-noise ratio is obtained when only a monaural signal is being transmitted. Similarly, if the signal level falls below that required for good quality stereo reception, most stereo decoders will automatically switch to the monaural mode so that a better signal-to-noise ratio is automatically obtained without the listener having to take any action.

Decoder Types

Some of the earlier forms of stereo decoder circuits are of the so-called switching type. In such circuits the 19kHz pilot tone is extracted from the multiplexed signal using a tuned circuit and is doubled in frequency to re-generate the 38kHz sub-carrier frequency. This latter signal is used to switch the multiplexed input to the decoder between the left and right hand channels.

Switching circuits of this type are not at all easy to set up and to align. In addition, they have the disadvantage that they do not provide the optimum separation between the left and right hand channel signals and require ferrite cored inductors (which are always difficult to design effectively).

All modern circuits employ phase-locked loops in the stereo decoder circuit. The frequency of oscillation of the voltage controlled oscillator of the phase-locked loop automatically locks on to a harmonic of the pilot tone frequency and the loop will remain locked to this latter frequency until the pilot tone is switched off. Any normal

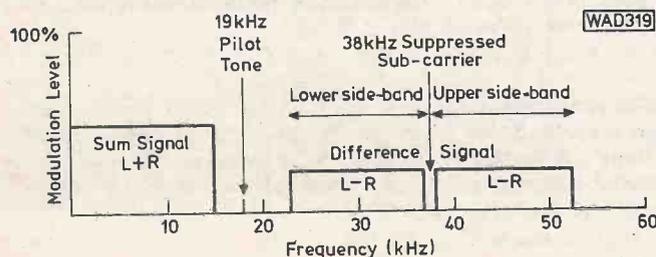


Fig. 1: Spectrum of the stereo multiplexed signal

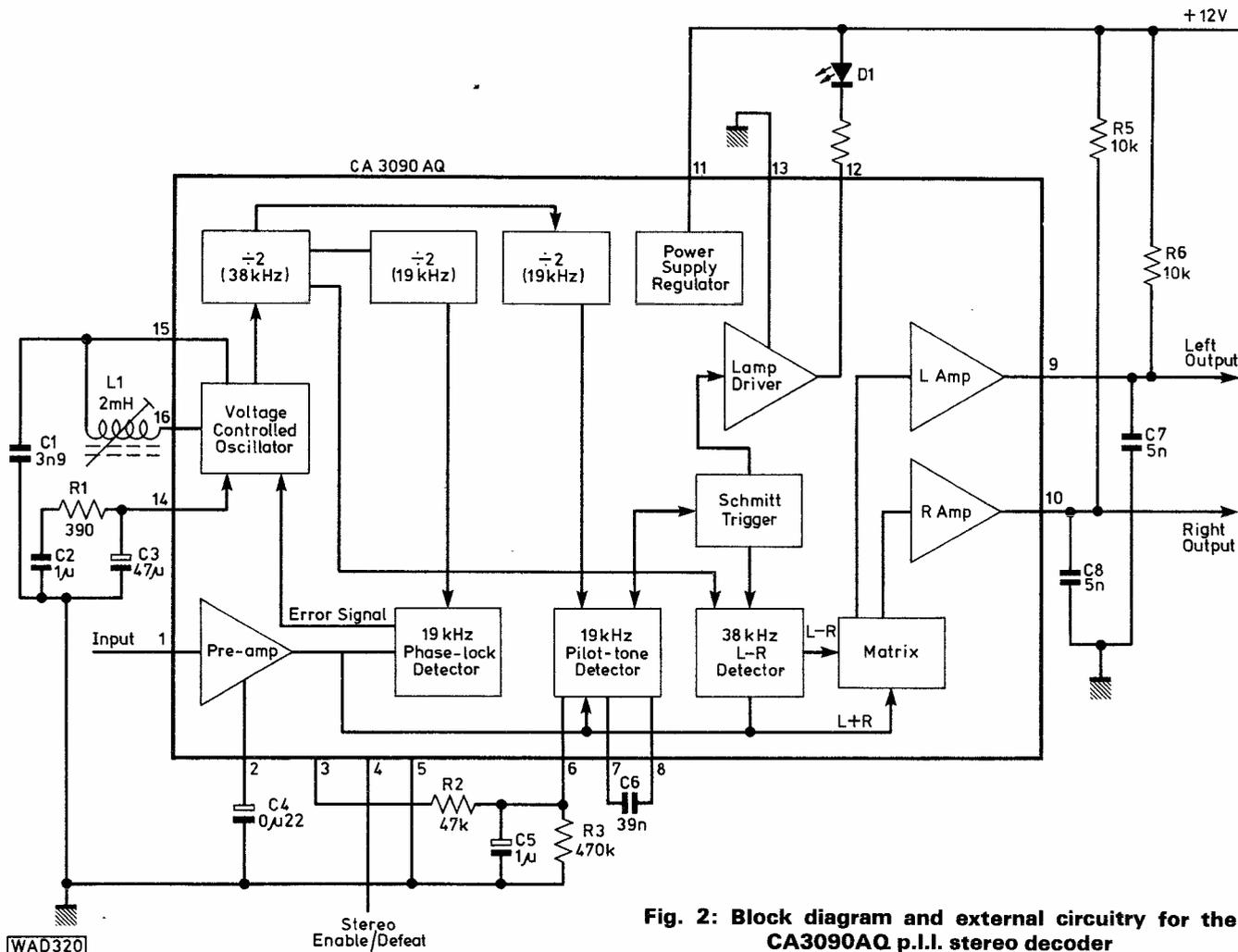


Fig. 2: Block diagram and external circuitry for the CA3090AQ p.i.l. stereo decoder

variation of the component values with temperature or normal ageing will not affect the performance of the circuit, so no critical component values are required in phase-locked loop decoders. In addition, this type of decoder is easy to set up, a simple adjustment of the loop free-running frequency being all that is required. Circuits employing a phase-locked loop for stereo decoding can provide excellent separation of the two channels, the interference between the channels normally being at least 40dB below the signal level.

Special integrated circuits for the phase-locked loop decoding of stereo signals are readily available. We will now discuss the principles of operation of a phase-locked loop stereo decoder and look at some typical circuits. It is much simpler to use a monolithic device than to try to make a stereo decoder from discrete components.

The RCA CA3090AQ

The first integrated circuit phase-locked loop stereo decoder to become available was the RCA Type CA3090Q in 1971, but this has been replaced by the CA3090AQ which is an improved version of the device, and provides an excellent performance. It has the disadvantage that the phase-locked loop is tuned by means of an inductor, whereas the other devices are tuned by a variable resistor; however, the thermal stability of the CA3090AQ is reputed to be better than that of other devices.

The internal circuit of the CA3090AQ is shown in block form in Fig. 2 together with a typical external circuit. This device is encapsulated in a 16 pin dual-in-line package and requires a supply of around 21mA from a +12V line. It can be seen that the internal circuit of the device is relatively complex, but the external circuit is quite simple and easy to construct.

A demodulated multiplexed stereo signal with a frequency spectrum like that shown in Fig. 1 is applied to pin 1 of the CA3090AQ; the input impedance at this pin is fairly high (about 50kΩ), so there is very little loading on the demodulator circuit which feeds pin 1. The signal is first amplified by a low-distortion pre-amplifier circuit inside the CA3090AQ and is then fed to both a 19kHz phase-locked detector and to a 38kHz detector of a similar type. In addition, the amplified signal is fed to a 19kHz pilot tone detector, the output of which determines the state of a Schmitt trigger circuit which controls the mode of operation (monaural or stereo).

The voltage controlled oscillator in the CA3090AQ operates at the fourth harmonic of the pilot tone frequency, namely $4 \times 19 = 76\text{kHz}$, this 76kHz signal being locked in frequency to the harmonic of the pilot tone. However, the 2mH external inductance connected to pin 16 must be adjusted so that the free-running frequency of this voltage controlled oscillator is fairly close to 76kHz; when the pilot tone is applied with the signal to pin 1, locking is then automatic.

The 76kHz voltage controlled oscillator signal is divided in frequency by a factor of two to produce a

38kHz signal exactly at the frequency of the suppressed sub-carrier; this 38kHz signal is fed to the L-R (left-minus-right) signal detector. The 76kHz signal is also divided in frequency by other circuits which produce two 19kHz signals in phase quadrature (that is, 90° out of phase with one another). One of these 19kHz signals is passed to the 19kHz phase-lock detector which generates the error signal which keeps the loop in lock, whilst the other 19kHz signal is required by the pilot tone detector.

The amplified multiplex signal and the output from the 38kHz L-R detector are applied to a matrix circuit which produces the left and right hand audio signals. These signals are amplified internally before appearing at pins 9 and 10. The 5nF capacitor and the 10kΩ resistor in each of these output circuits provide the required de-emphasis time constant.

If the pilot tone is absent or at such a low amplitude that the signal could not provide good stereo reception, the pilot tone detector does not switch the Schmitt trigger circuit to the stereo mode. The circuit therefore, operates in the monaural mode and the left-plus-right sum signal appears at both of the outputs so that both speakers produce a monaural output.

The signal from the Schmitt trigger also operates a lamp driver circuit. The latter causes the light emitting diode D1 to glow when the circuit is operating in the stereo mode. If no 19kHz pilot tone is present at the input or if the pilot tone is too weak to cause the circuit to operate in the stereo mode, the light emitting diode does not glow. A light emitting diode consumes less current than a tungsten filament lamp and also has the advantage that it is more reliable (since filaments tend to break after much use!). Nevertheless, the light emitting diode and its series resistor R4 in Fig. 2 can be replaced by a suitable small tungsten filament lamp which requires not more than about 100mA.

The Coil

The Toko coil type YXNS 30450NK has been especially designed for use with the CA3090AQ device; it has 270 turns on a ferrite core and a blue colour coded core adjuster. The use of this miniature coil (available from Ambit International) is much more convenient than trying to wind a suitable coil oneself.

In order to adjust the core, a stereo signal should be fed to the circuit of Fig. 2. The core of the coil should be rotated first in one direction and then in the other to find the points at which the circuit switches from the stereo to the monaural mode (as indicated by the light emitting diode, D1). The core should be set about half way between these two points. The centre frequency of the voltage controlled oscillator is then quite close to 76kHz, but the setting is not very critical, as the capture range of the phase-locked loop circuit is some ±10% of the centre frequency.

The mode of operation (stereo or monaural) can be controlled by the application of a suitable potential to pin 4 of Fig. 2. At potentials of more than about +1.2V, the circuit is switched to the stereo mode, whilst at voltages of less than about +1V the circuit operates monaurally. If this mode switching facility is not required, pin 4 should be directly grounded.

The CA3090AQ provides a channel separation better than 25dB, the typical value being about 40dB. The 2nd harmonic distortion in each of the outputs is some 0.2% typical, but higher order harmonics are less than 0.1% of the output amplitude.

The CA3090AQ is readily available from Arrow Electronics Ltd., Coptfold Road, Brentwood CM14 4BN,

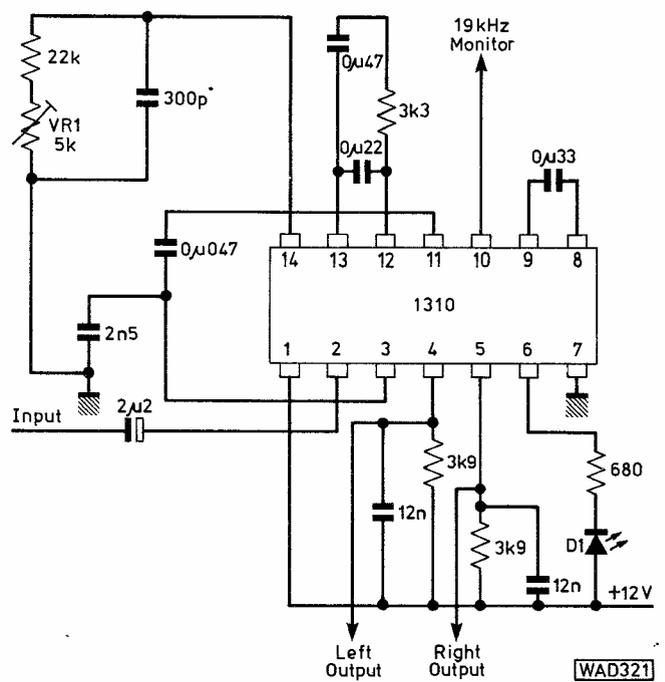


Fig. 3: External circuitry required for the MC1310

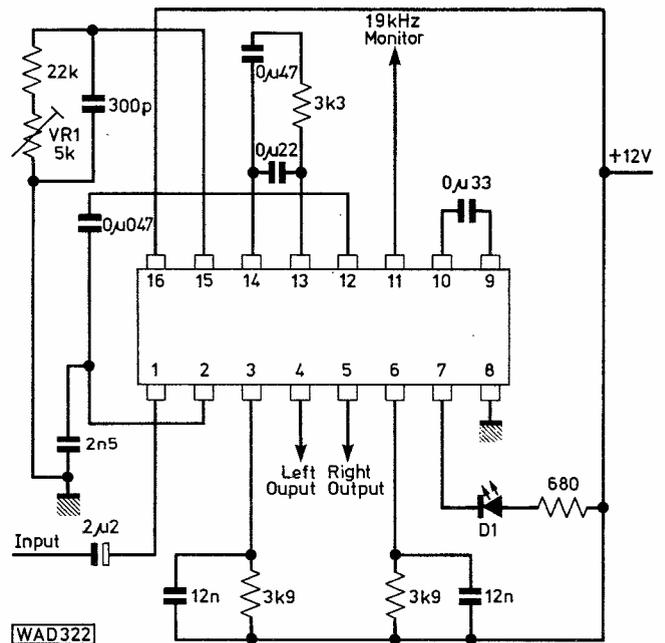


Fig. 4: External circuitry for the National LM1310E

the current price being £2.96 including VAT, but 25p is required for p&p on orders under £5.

The 1310 Types

The Motorola MC1310P first appeared on the market in 1972, but is now an "industry standard" type of device which is second sourced by many other manufacturers. For example, National Semiconductor market it as their LM1310, Signetics as the MC1310, RCA as their CA1310E, Texas Instruments as their SN76115N, Sprague as their ULN-2210 and Exar as their XR1310.

All of these devices can be used in the circuit shown in Fig. 3, although there may be minor differences between the various types, such as the exact supply voltage range over which they operate satisfactorily.

The circuit of Fig. 3 operates on very similar principles to that of Fig. 2, but the free-running frequency of the voltage controlled oscillator is set by the adjustment of VR1 instead of by the adjustment of the core of a coil. The adjustment can be made by connecting pin 10 to a frequency counter and adjusting VR1 with no input signal until the frequency at pin 10 is 19kHz. The amplitude of the signal at pin 10 is about 3V peak. However, it is usually far easier to adjust VR1 with a small stereo input signal so that it is set at about the centre of the range over which the light emitting diode D1 remains illuminated.

The value of the capacitor employed between pins 8 and 9 determines the stereo-monaural mode switching delay. The time constant for this switching is equal to the value of this capacitor multiplied by about 53kΩ. If pin 8 is connected to ground, the circuit will operate only in the monaural mode.

The capture range in the circuit of Fig. 3 is less than that in the case of the CA3090AQ, being typically about ±3%. However, it can be increased by reducing the capacitance between pin 14 and ground and increasing the resistors in parallel with this capacitor in proportion; nevertheless, care must be taken to ensure these changes do not result in increased beat note distortion at high signal levels due to oscillator phase jitter.


The MC1310P is available from Arrow Electronics Ltd., at £3.14 including VAT.

Emitter Follower Outputs

A number of other devices, such as the National Semiconductor LM1310E, are available in 16 pin dual-in-line packages. They are similar to the MC1310P, but include an emitter follower in each output circuit to provide low impedance outputs. A circuit for the use of the LM1310E is shown in Fig. 4. It can be seen that the de-emphasis components in the pin 3 and pin 6 circuits are not connected to the output pins themselves, but rather in the base circuits of the internal emitter followers. In general the remarks made about the MC1310P also apply to the versions with emitter followers (with a change of pin number), but the emitter follower device circuits will not be discussed further, as they have been largely replaced by a rather better device.


The industry standard Types LM1800, CA758E, SN76116N, MC1311, μA758 and ULN-2244 are similar to the LM1310E, but in addition to their emitter follower outputs, they incorporate a circuit which provides some 45dB of power supply ripple rejection. In other words, they can give the lowest possible hum level. These devices are encapsulated in 16 pin dual-in-line packages and can be used in the circuit of Fig. 4. They are adjusted in the way already described and the remarks about the 1310 type of device also apply to these devices except for pin number changes.

It should be noted that the total harmonic distortion from devices of this type increases with increasing input signal level, as shown in Fig. 5. However, a low signal level will give rise to a poor signal-to-noise ratio. A suitable compromise between distortion level and signal-to-noise ratio must therefore be reached. The output typically consists of the wanted signal plus a second harmonic component at -52dB down together with a 19kHz pilot tone at -37dB down, the 38kHz suppressed carrier at -40dB down and the sidebands of this sub-carrier at about -28dB down. The channel separation in dB at

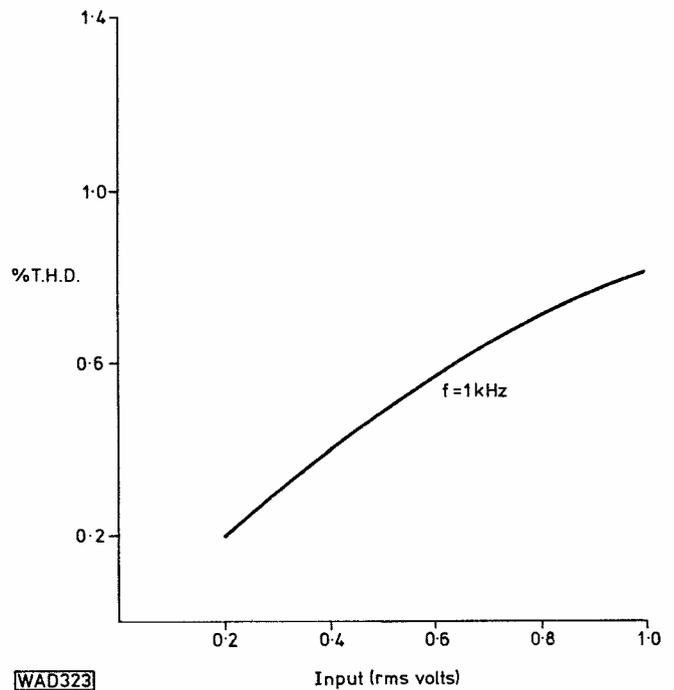

WAD323

Fig. 5: Relationship between total harmonic distortion and input signal level

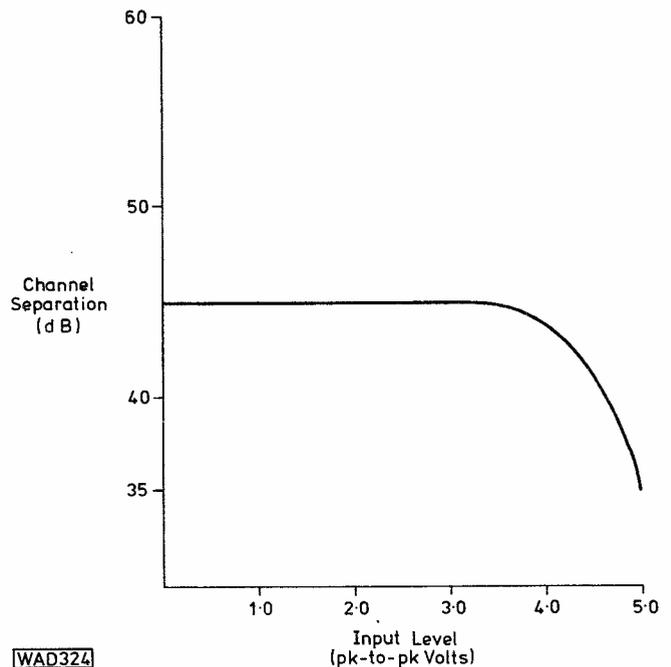

WAD324


Fig. 6: Channel separation plotted against input signal level

various levels is shown in Fig. 6 for a typical device of this type.

The Sprague ULN-2244 device is available from Phoenix Electronics Ltd., 139 Havant Road, Drayton, Portsmouth PO6 2AA at £3.38 (including VAT) plus 20p p&p at the time of writing.


The TDA1005

The Mullard/Signetics TDA1005 phase-locked loop stereo decoder device has been designed so that it can provide an output which is very low in unwanted signal levels. The device was originally designed for use with an

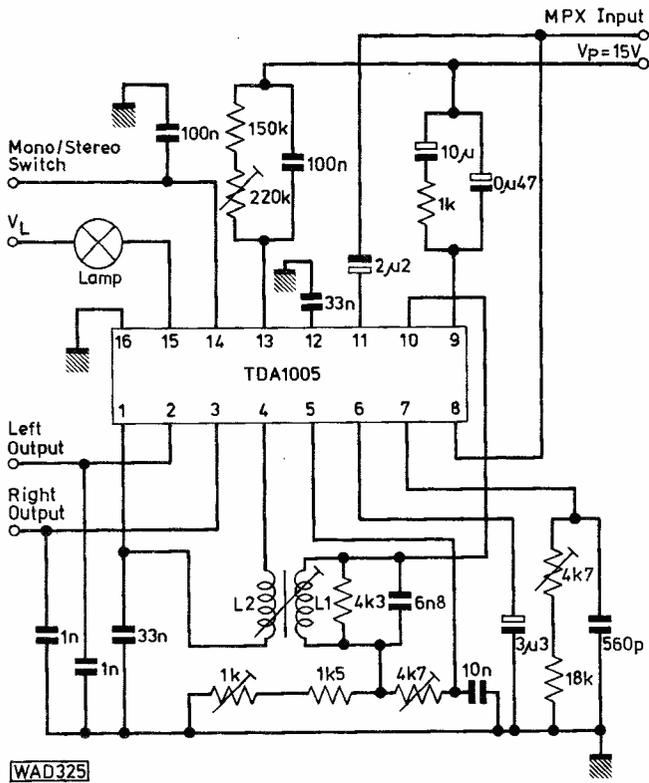

WAD325

Fig. 7: External circuitry for the TDA1005 in the frequency multiplex mode

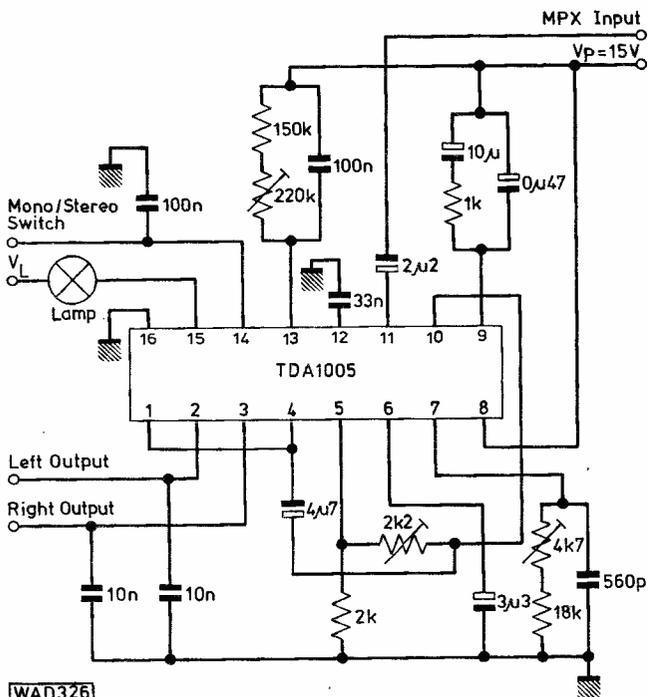

WAD326

Fig. 8: External circuitry for the TDA1005 operating in the time multiplex mode

inductor in a frequency multiplex decoder, but can also be used without any inductor in the so-called time multiplex circuit. Typical circuits of these types are shown in Figs. 7 and 8 respectively.

CONTINUED NEXT MONTH

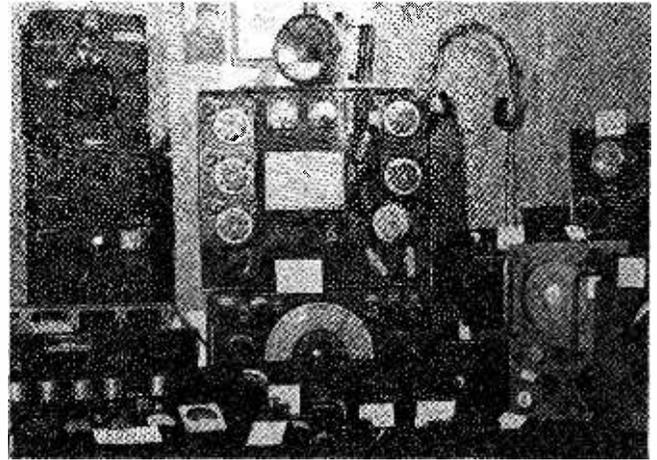


Fig. 5: Now museum pieces, the R1155/T1154 stands proudly in the centre with three sets from the Heinkel 111 on the left and a piece of wartime RADAR on the right

called the National Wireless Register, and readers were invited to complete the form so that they might be classified into technical groups which would be useful to the authorities, and avoid the real danger that the ability of wireless men might be lost through individuals being hastily drafted into non-wireless categories.

The form itself states: "During the Great War the needs of the Services for operators were largely met, especially during the early stages, by the voluntary enlistment of trained Post Office operators, but as Morse is no longer used in the Post Office, this possible source of supply is rapidly dwindling. It is therefore imperative that all our readers who have at least a good working knowledge of Morse, or have other qualifications such as ability to service and repair wireless and electrical apparatus, should apply to help fill the vacancies which now exist in the RNV(W)R, the Royal Corps of Signals, TA, and the RAFCWR."

Less than a year later, Great Britain was at war and in the early days a party of 55 ex-Civilian Wireless Reservists went to the Maginot Line and were christened the "Early Birds" by the amateur radio fraternity. According to the RSGB journal, September, 1942, some 2500 of their members had joined the forces. By the end of the war, thousands of people from the radio fraternity had served their Country in one of the many branches of radio communications in the armed forces. Ex-service personnel still talk with affection about such famous pieces of equipment as the Army's Wireless Sets, Nos 18, 19, 38 and 46, the Navy's CR100, the RAF's R1155/T1154 combination, the AR88 and the B2 and MCR-1 Clandestine sets, all of which are now collectors' items and stand silent in various museums representing a period of time when Wireless and thousands of its enthusiasts went to war.

ACKNOWLEDGMENTS

We are indebted to the Editor of *Wireless World* for permission to reproduce Fig. 4 and other extracts from that journal, and to the RSGB for permission to quote from the *T & R Bulletin*.

The sets in the photographs are from the author's collection and are on display at The Chalk, Pits Museum, Houghton, Sussex.

★ BARGAIN BUYS ★

All prices include VAT—Just add 25p post

from **GREENWELD**

443B Millbrook Road Southampton SO1 0HX
Tel: (0703) 772501/783740

SN76110 Stereo decoder **75p**; 25/£15 100/£45.

BC184 Prepared for T05 spacing 100/£4.50 1000/£30.

BC213L straight leads 100/£5 1000/£33.

2N5060 0-8A SCR 30V. Ig 200uA 10/£2 100/£15 1000/£120.

1N4148, bandoliered 1000/£15 2500/£32 10,000/£90. Loose, boxes of 10K/£75.

741 8DIL 10/£1.80 100/£14.50.

555 8DIL 10/£2.40 100/£19.50.

1N4003 100/£2.90 1000/£24.

1N4007 100/£4.90 1000/£44.

Electrolytics: 10u40V PC mntg 25/£1.25 100/£3; 4.7u/63V V.PC mntg. 1u/63V H.PC mntg same price.

1250u/25V can 10/£1.60 100/£10.

1500u/40V can 10/£2.20 100/£15.

800u/250V can 10/£5.50 100/£44.

400u/400V can 10/£8 100/£58.

200u/350V. 100 + 100 + 50/300V (all in one can) 10/£5 100/£36.

Pots - 10k lin std bush & spindle 1" long 10/£1 100/£7.50 1000/£50.

Slider 1.8k lin 60mm long prices as above.

Dual 100k lin PC or chassis mntg, min type 18 x 13 x 17mm 0.125" spindle supplied with smart knob 40p 10/£3.50 100/£30.

Compression trimmer, 10-100pF 10 for £1.20 100/£8.50.

Resistors - 1/2W 5% carbon film, these values only: 220R 470R 1k 3k9 4k7 33k 47k 220k 18R. All @ 1000/£4 (min qty of one value) or £35 per 10,000 any mix.

NIXIE TUBES

ITT type GNP7AH. Supplied with data 60p each.

7-seg display, wire ended tube NEC type LD8012 1/2" high, with data 65p.

7-seg display, (as above) Futaba type DG-10Q1 0.3" char. 70p with data.

Audible Warning device - solid state circuit drives high efficiency transducer to give high output. Voltage req'd 6-18V. Can also be driven direct from TTL or CMOS. Module size 45 x 21 x 12mm. Comprehensive data supplied £1.20. VU meters - 2 meters 40 x 40mm + driver board supplied with full data and circuit £3.50.

OSCILLOSCOPES

We have available from stock the following SCOPEX models: 4D10A - DC-10MHz; 10mV sensitivity; Stab Power supplies; Dual beam; 3% accuracy; Excellent value at £214 inc VAT and Carr. 4S6 - DC-6MHz; 10mV sensitivity. Ideal portable scope. Solid state circuitry. All for £150 inc VAT and Carr.

RESISTOR PACK

Carbon Film 5% mostly 1/2W, few 1/4W resistors. Brand new, but have preformed leads, ideal for PC mntg. Wide range of mixed popular values at the unrepeatable price of £2.50 per 1000; £11 per 5000.

1979 CATALOGUE

64 big pages with 50p discount vouchers and qty prices for bulk buyers + reply paid envelope—All this for just 45p inc. post.

Relays, push button banks and variable caps. Switches, component packs etc, etc, all in our latest Bargain List — send SAE for your free copy.

Prices in this ad include VAT and are valid until 30.4.79. Add 25p UK/BFPO postage. We buy surplus electronic components for cash.

ELECTROVALUE

FOR A GOOD DEAL BETTER THAN MOST

WE PAY POSTAGE on C.W.O. orders in U.K. over £5.00 list value. If under, add 27p handling charge.

WE GIVE DISCOUNTS on U.K. C.W.O. orders—5% for list value over £10.00; 10% for list value over £25.00.

WE GUARANTEE all goods are brand new, clean and to specification—no seconds, no surplus.

WE GIVE SERVICE to all orders large or small—to help we microfilm orders, use computer processing and double check all orders by personal supervision.

Specialist Mail Order Suppliers Since 1964

THIS MONTH'S SPECIAL OFFERS ELECTROVALUABLES

'Electrovaluables' are our own overstock items offered from time to time at greatly reduced prices. Orders should quote 'Electrovaluables' and state description and price as advertised. PRICES ARE NET AND V.A.T. MUST BE ADDED @ 8% or 12% where prices show ●

Integrated Circuits
7450 9p, 7470 16p, 7480 25p,
74190 55p, 709 (metal) 30p,
TAA991D 65p, TAA2781A 45p

Transistors
2N4906 1, ACY 30p AD161
10 for £5. BC183, BC238C,
BC157A, any 10 for 60p.

BC328, BC338 any 10 for 80p.
BD130 (=2N3055) 10 for £4.
BF194, BF195 any 10 for £1.
OC83, OC84 any 10 for £4.

Diodes
AA113, AA116, AA117, AA118,
BA133F any 10 for 60p

Rectifier diodes
B0680 any 10 for 80p

Bridge rectifiers
B1906 5 for £1.20

Thyristors
B0140, B0226 any 5 for £1.25

Potentiometers Carbon track
P20: + switch 470K 1M log 4 for £1
JP20 47K 1 in, short spindle 4 for £1

2M2 1 in, long spindle 4 for £1
100K log, 2M2 log 4 for £1

1M log, rev log short-spindle: 4 for £1

PG58, slides
1M 1 in, 10K log, 47K log, 100K log, 220K log, 1M log, any 6 for £1

Potentiometers wire wound
Colvern 505K: 100, 150, 1K5, 5K, 15K, 25K, 50K: any 2: £1

PR15 presets
Horiz: 220, 1K, 2K2, 47K, 470K, 4M7 any 10 for 40p

PR140 Presets
10M horiz, 100Kvert any 10 for 60p

Plessey MPWT moulded track
47K, 220, 47K, 220K, 1M any 4 for £1

Magneto resistor
FP30 L100E 5 for £2.50

Thermistors 500Ω disc 5 for 40p

WE ARE NATIONAL DISTRIBUTORS FOR



MICROCOMPUTER KITS

Full ranges stocked including ancillary items. £165 Nett + V.A.T. Brochure on application.

MOTOROLA D.2 MICROPROCESSOR EVALUATION KIT
(for the M.680 Microcomputer — £175.87 net + V.A.T.)

FREE FOR THE ASKING CATALOGUE 9

Two depots to serve you One North, One South
All communications, orders etc., to Englefield Green address, Dept. PW4.

Completely revised and up-dated. 120 pages. Semi-conductors, I.Cs, Opto-electronics, Rs, Cs, materials, etc. etc. And you'll be delighted with our competitive three-month stabilised price list.



ELECTROVALUE LTD

28, ST. JUDES ROAD, ENGLEFIELD GREEN, EGHAM, SURREY TW20 0HB
Telephone Egham 3603 Telex 264475
Northern Branch - 680, BURNAGE LANE, BURNAGE, MANCHESTER M19 1NA(061)432 4945
Shop hours 9-5.30: 1.00 pm Sat.

Meet 'Uncle Tom'. He's on your wavelength.



Tom Beaumont - a radio enthusiast for 25 years - sells radio equipment for love! And he particularly loves Lowe - Trio for quality, value and reliability.

Tom is the sole authorised Lowe - Trio distributor for Yorkshire and North East England, and he offers the best before-and-after-sales service around on units like the top-value SRX-30 receiver illustrated.

THE LOWE SRX-30

All the facilities of a top-class communications receiver in one top-quality, economically priced unit. Covers 500 KHz to 30 MHz with excellent dial readout and re-set accuracy. AM, CW, SSB reception. The SRX-30 is equally at home in broadcast or amateur bands.

Other features include RF gain, fine tuning selectable sidebands, built-in loudspeaker, AC mains or 12V DC operation and rugged construction at an attractive price - just £175.00 inc. VAT.

BUY BY POST OR CALL IN
For speedy delivery on your SRX-30, please send cheque/P.O. made out to Leeds Amateur Radio for £178.00 which includes £3.00 carriage and packing. We will deal with your order by return.

Alternatively, call in for a chat at 'Uncle Tom's Cabin'. The shop is just 10 minutes from Leeds City Station, and there's easy parking if you travel by car. ●Instant H.P. for Licenced Amateurs. ●Extended Credit Terms Available. ●Send 50p for Catalogue and Price List.

LOWE TRIO DISTRIBUTOR



Leeds Amateur Radio are area distributors for Jay Beams, Antenna specialists and Hilomast products.



LEEDS AMATEUR RADIO Reliability in Radio

Leeds Amateur Radio, 27 Cookridge Street, Leeds 2, West Yorkshire. Tel. Leeds 452657.


FM MULTITESTER

D. WHITFIELD & M. TOOLEY

This multimeter was originally evolved as a constructional project for members of the UK F.M. Group in London, where several such instruments were very successfully built. Together with a suitable wavemeter, it forms the basic test equipment necessary to carry out performance checks on frequency-modulated v.h.f. equipment and meets Home Office requirements in this respect.

The majority of people owning commercial apparatus will possess basic test equipment but are unlikely to have the sophistication of r.f. power meters, deviation meters and so on. The unit to be described was developed as a means of carrying out rapid assessments of performance and offers an accuracy, after initial calibration, which is quite adequate for amateur use.

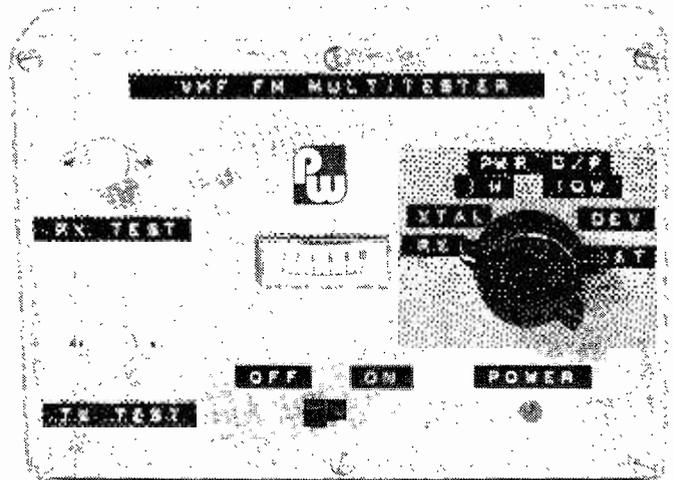Receiver check, crystal test, power output (1W and 10W) and frequency deviation are the four functions provided, together with a battery status indication. The instrument and battery pack is built into a small, diecast box, which makes it rugged and readily portable.



Functions

Function 1 selects the crystal oscillator, which puts out a low-level signal on a pre-determined frequency within the 2m band. The choice of crystal is left to the constructor but perhaps the most useful channel to use would be S20 (145.500MHz), the UK calling frequency.

The oscillator operates at the fundamental frequency of the crystal — which falls in the 8MHz range — the output frequency being achieved by a stage of multiplication. The facility may be used for checking receiver gain, S-meter calibration and alignment.

Function 2 provides a crystal test, and devices within the range 4–24MHz may be checked for performance. The internal crystal is removed and that to be tested plugged into its socket. If the constructor foresees regular use of this facility, it may be worthwhile bringing the socket to the outside of the unit — possibly putting several different types in parallel.

The measurement of r.f. power, to a maximum of 1 watt, may be carried out using Function 3 and the internal 50Ω dummy load, at a typical v.s.w.r. of 1.1:1. Although the power scales are non-linear, it is possible to draw up a calibration chart for the instrument by reference to a commercial power meter.

Measurements of up to 10 watts may be made by selecting Function 4. The internal dummy load will handle these levels only for a short period however — typically 30 seconds.

Function 5 measures the deviation of an f.m. signal on a pre-calibrated scale of 0–10kHz. The signal applied should be at a power level of between 500mW and 10W and must be of the same frequency as that used for the receiver check (Function 1).

A check on the carrier frequency is also possible using Function 5. If the internal oscillator is accurately adjusted by means of a frequency meter or against a communications receiver with crystal calibrator, the meter will

Table 1

Voltages		
(Multimeter switched to range 2, Crystal Check)		
Tr1 (with crystal fitted)	c	12V
	b	5.1V
	e	8.5V
Tr1 (crystal removed)	c	12V
	b	5.8V
	e	5.2V
Tr2 (with crystal fitted)	c	12V
	b	1.7V
	e	2.5V
Tr2 (crystal removed)	c	12V
	b	0V
	e	0V
IC1	pin 2	6V
	pin 3	6V
	pin 6	6V
	pin 7	12V

The above voltages were measured with a 10MΩ resistance d.c. voltmeter and a 1MΩ probe.

The r.f. voltages at various points are:

Tr1	emitter	1.5V r.m.s.
Tr2	base	1.4V r.m.s.
Tr2	collector	0.15V r.m.s.
D6	cathode	0.05V r.m.s.

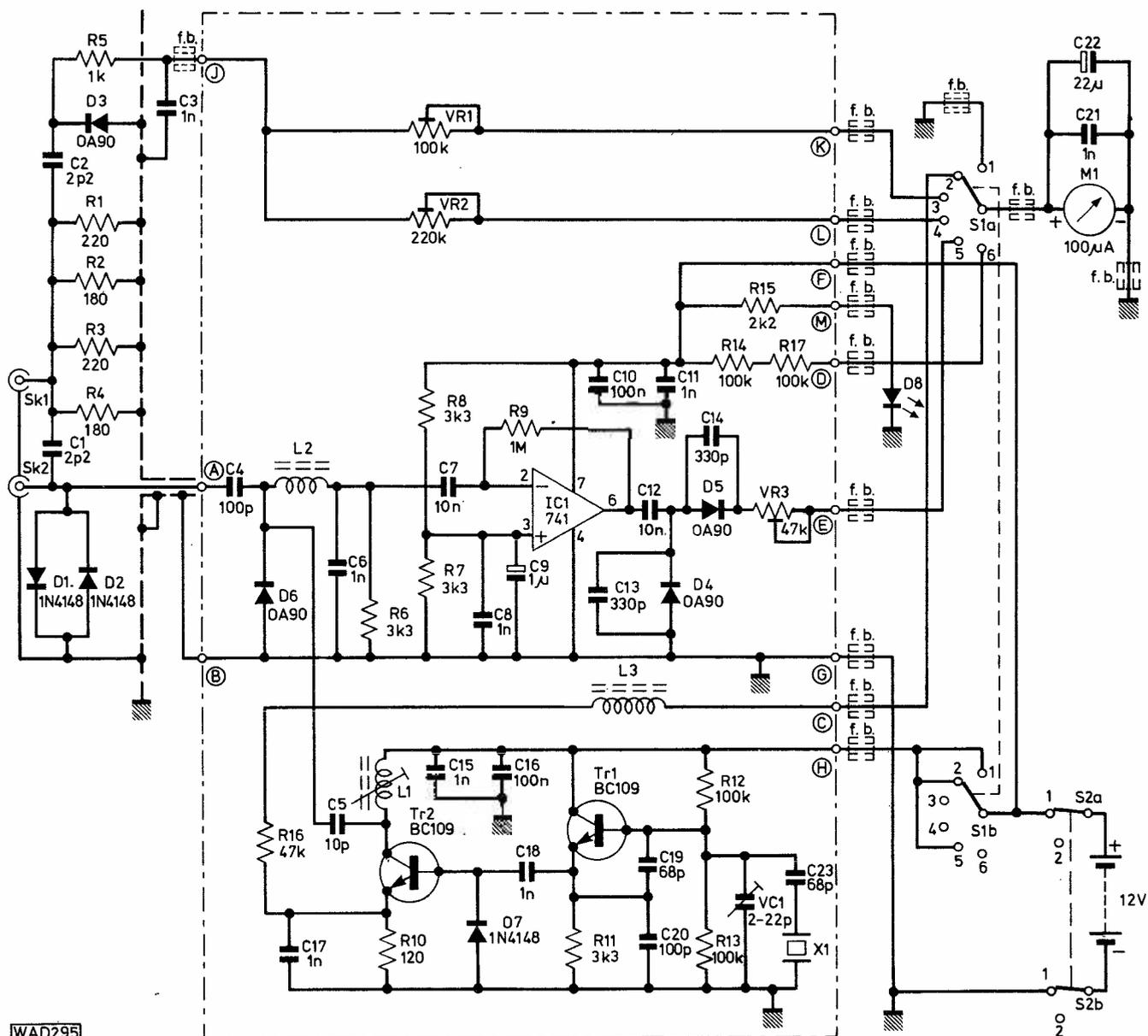


Fig. 1: Circuit of the Multitester


indicate a standing reading corresponding to the error, in kilohertz. For example, a reading of 4 in the absence of modulation would indicate that the transmitter is 4kHz off channel. Hence, the instrument can be used for checking both the receive and transmit frequencies once correctly calibrated.

The final function serves to test the internal batteries. Here the meter operates as a voltmeter with a full-scale deflection of 20 volts.

Circuit Description

Transistor Tr1 functions as a conventional Colpitt's oscillator, the frequency being adjusted by trimmer TC1, whilst Tr2 acts as a multiplier and amplifier, the diode D7 improving the harmonic content of the signal at its base.

With suitable crystals, Tr1 will readily oscillate at any frequency between 4 and 24MHz. However, the circuit is optimised for operation at 8MHz and when a crystal for

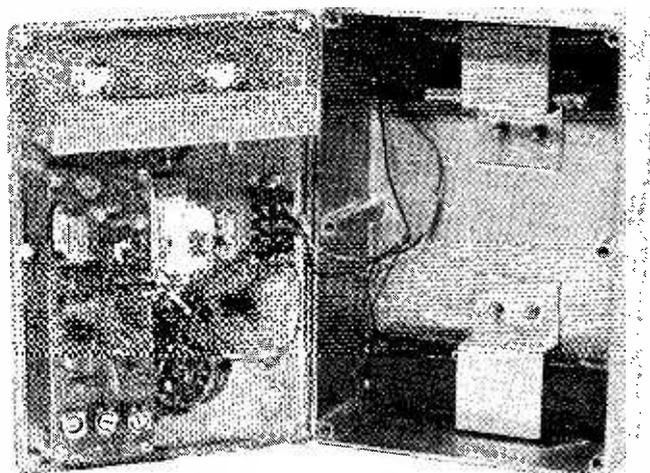

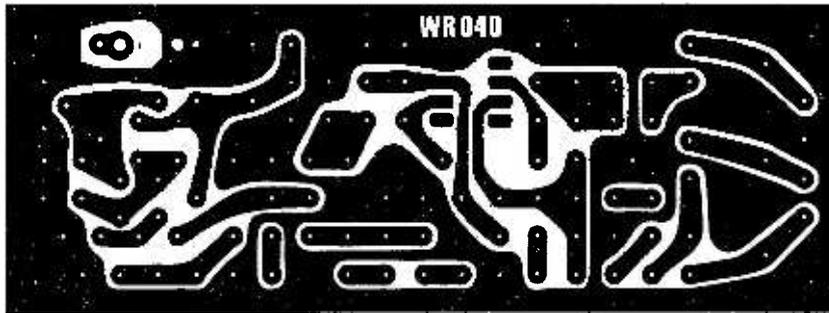


Fig. 2: Layout of the p.c.b. (shown full-size)

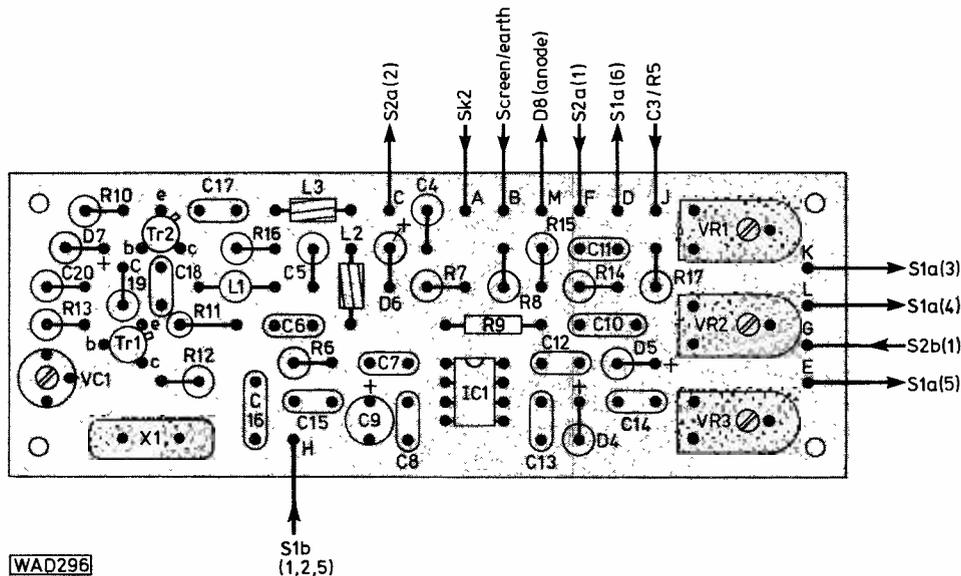


Fig. 3: Component layout

this frequency is used (8.08333MHz for 145.5MHz, for instance), Tr2 multiplies 18 times, L1, together with the stray and internal capacitance of Tr2, resonating at approximately 145.000MHz.

The integrated circuit IC1 is arranged to operate as a very high gain audio-frequency amplifier and requires only a very small input voltage to achieve full limiting of its output. This means that a small sine-wave input is converted to a 6 volt peak square-wave output of the same frequency. Diodes D4 and D5, together with C12, form a charge-pump arrangement. Thus, the current through VR3 and the meter will depend on the frequency of the signal applied to IC1 and not on its amplitude. The relationship between the input signal frequency at C7 and the meter current is substantially linear.

Potentiometer VR3 is used to calibrate the instrument. Diode D6 acts as a simple, but effective, mixer, the output of which passes through an r.f. filter formed by L2 and C6 and is the frequency difference between the output signal at Tr2 and the input from SK1. This is subsequently passed to IC1 and the circuit previously described. The diodes D1 and D2 form a limiting circuit to prevent the input to the mixer diode (D6) from exceeding 1.2 volts peak-

to-peak whilst D3 is used to sense the r.f. at SK1 for the power ranges, the calibration being by adjustment of VR1 and VR2.

Construction

In order to ensure the circuit operates satisfactorily, it is essential to closely follow the recommended layout. New-comers to the construction of v.h.f. and u.h.f. equipment take heed that conventional wiring techniques will introduce stray reactance which will adversely affect the ultimate performance. Hence component leads must be as short as possible, the neatness of the wiring being a secondary consideration.

Most of the devices are mounted on a p.c.b., the remainder being fixed on the lid of the box. Ferrite beads provide the necessary r.f. decoupling, and these may be rigidly mounted by the application of a small amount of adhesive.

The dummy load resistors (R1-R4) are positioned on the screen and as close to SK1 as possible. In use, these are likely to become fairly warm, so the screen will also double as a heatsink. The free length of the resistor leads should not exceed 5mm for minimum v.s.w.r.

The full circuit of the multimeter is shown in Fig. 1 and the p.c.b. details and component layout in Figs. 2 and 3. It should be noted that many devices are vertically mounted and this should be borne in mind when shopping!

The inductor L1 consists of $3\frac{1}{2}$ turns of 20 s.w.g. enamelled copper wire, wound on a 4mm diameter ferrite-dust core. It is self-supporting and after initial adjustment should be secured with wax. Chokes L2 and L3 are each made from 6 turns of 36 s.w.g. enamelled copper wire, wound on a ferrite bead. Note the capacitor C23, which is mounted below the p.c.b. between the "hot" end of crystal X1 and the junction of R12 and R13.

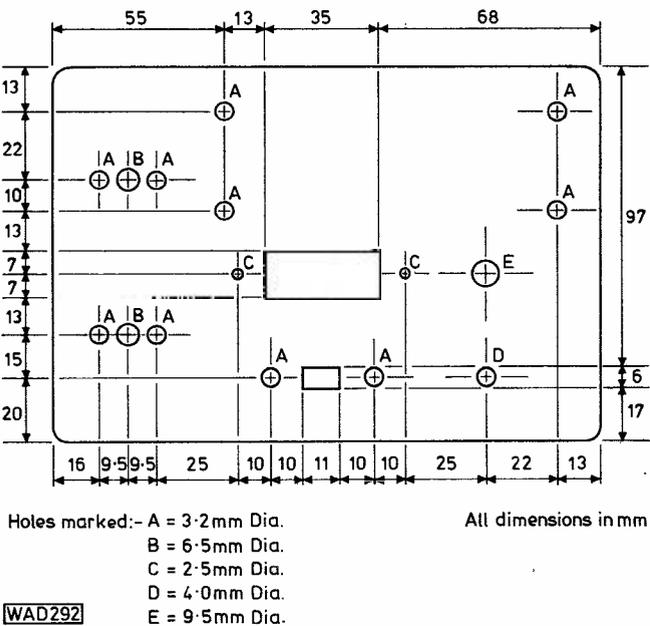


Fig. 4: Drilling details for the box lid


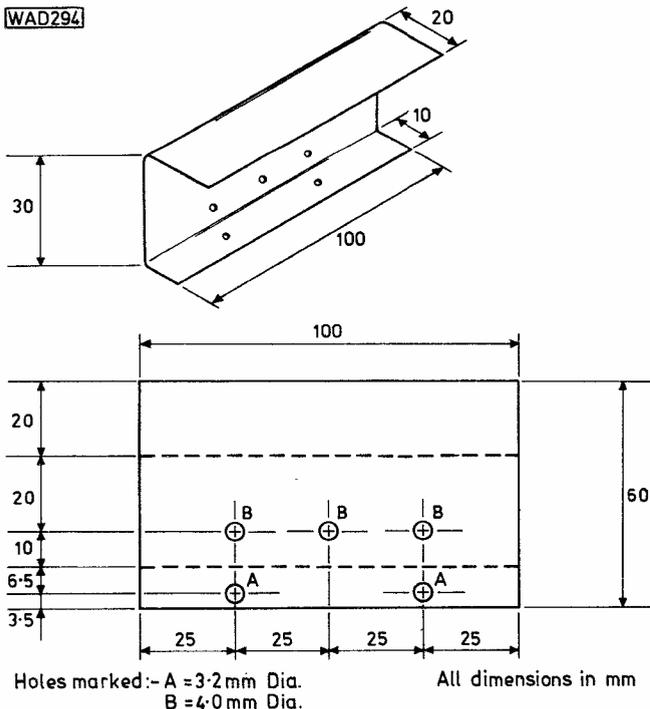


Fig. 5: Construction of the tinfoil screen

Testing and Calibration

Make a thorough visual examination of the p.c.b. when the assembly has been completed, paying particular attention to the polarity of components and soldering. Assuming all seems correct, connect the batteries and switch on, setting the function switch to "Battery Check". The meter should indicate "6" — corresponding to 12 volts — and the l.e.d. should illuminate.

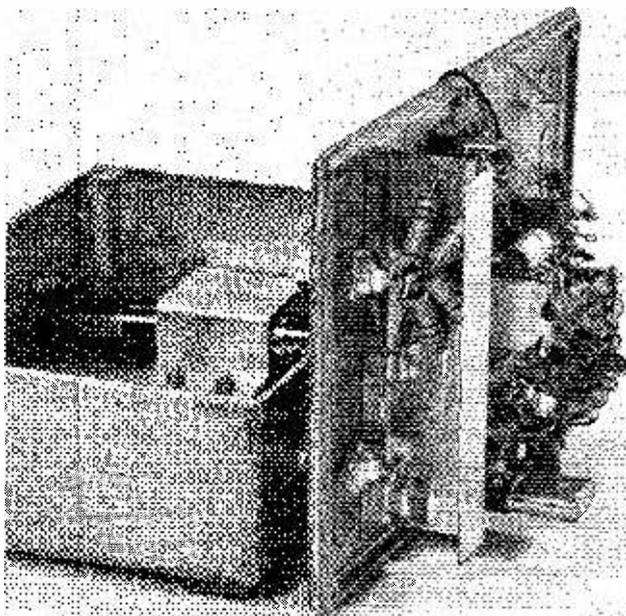Now set the function switch to "Crystal Test" and observe the meter reading: if the oscillator is working then some indication should be present. Adjust VC1 for max-



Internal view of the unit, showing arrangement of dummy load resistors

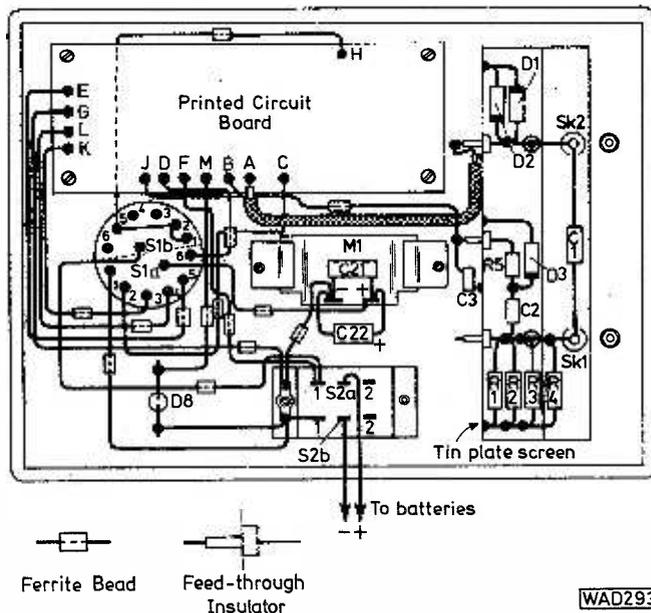


Fig. 6: Wiring diagram

★ components

Resistors

1/2W 5% Carbon film

120Ω	1	R10
1kΩ	1	R5
2-2kΩ	1	R15
3-3kΩ	4	R6,7,8,11
47kΩ	1	R16
100kΩ	4	R12,13,14,17
1MΩ	1	R9

2W High stab. carbon

180Ω	2	R2,4
220Ω	2	R1,3

Semiconductors

Transistors

BC109	2	Tr1,2
-------	---	-------

Integrated circuit

741	1	IC1 (Mini-dip type)
-----	---	---------------------

Diodes

1N4148	3	D1,2,7
OA90	4	D3,4,5,6
LED	1	D8 (Red)

Crystal

Within 8MHz range (see text), HC25 series 8.08333MHz for S20 (145.500MHz) from P. R. Gollgedge Electronics, Merriott, Somerset TA16 5NS

Sockets

50Ω BNC	2	SK1,2
HC25	1	SK3 Crystal Holder (P. R. Gollgedge Electronics)

Switches

S1	1	2-pole, 6-way rotary
S2	1	2-pole, 2-way slide

Potentiometers

Miniature skeleton pre-set, horizontal mtg.

47kΩ	1	VR3
100kΩ	1	VR1
220kΩ	1	VR2

Capacitors

Silver Mica

2-2pF	2	C1,2
10pF	1	C5

Polystyrene

68pF	2	C19,23
100pF	2	C4,20
330pF	2	C13,14

Miniature disc ceramic

1nF	8	C3,6,8,11,15,17,18,21
10nF	2	C7,12
100nF	2	C10,16

Electrolytic 16V axial leads

1μF	1	C9
22μF	1	C22

Trimmer. Single turn miniature ceramic

2-22pF	1	VC1
--------	---	-----

Miscellaneous

100μA meter, edgewise-reading. RS type 259-561. Diecast box 171 × 121 × 55mm. Ferrite beads (14 off). Battery cradle (2) to accommodate 4 × HP7-type cells. Pointer knob (Sifam). Feed-through insulators (3). 25mm stand-off pillars for mounting p.c.b. (4). Piece of tinplate approx. 100 × 60mm × 20 s.w.g. Printed circuit board.

imum deflection. Connect a receiver (or transceiver) to SK2 "Receiver Test" and tune to the test channel frequency. Peak L1, with reference to the meter, adjusting VC1 also to obtain the best indication possible. If you are fortunate enough to have access to a reliable digital frequency meter, swing VC1 to the correct fundamental frequency, as measured at the emitter of Tr2. This completes the oscillator and multiplier alignment for functions 1 and 2.

Switch to the 1 watt r.f. function and set VR1 and VR2 to mid-position. Using a variable power supply, inject 4.6 volts at point "J" on the p.c.b. and adjust VR1 for a full-scale deflection on the meter. Now select the 10 watt r.f.

power function and inject 14.6 volts at point "J"; adjust VR2 for a full-scale reading. If a commercial power meter, such as the Antenna Specialists or Bird Through-line, is available, then the meter calibration may be very accurately carried out and a chart drawn up.

Finally, select the deviation function and apply a signal of between 0.5 and 1 volt r.m.s. at a frequency of 10kHz (sine or square wave) to pin 2 of IC1, via a 10nF capacitor. Adjust VR3 for full-scale deflection of the meter.

The alignment and calibration is now complete. Typical voltages are given in Table 1 to facilitate troubleshooting should problems subsequently arise, but in practice, little difficulty should be experienced with the instrument. ●

LETTERS

continued from page 29

Sir: I agree entirely with Mr Goodier's letter. A lot of what people consider to be progress in this world is anything but. I think it must be because people don't hear what they don't like!

*G. M. Pheasant
Great Wyrley
Walsall*

Sir: I am an ardent supporter of CB, and unlike the majority of its critics, I have had five years of operating on a Citizen's Band in a more enlightened country, where I learned the true value of low-power radio communications for the general public.

I wonder why Mr Goodier singles out hikers and climbers? There are numerous situations where two-way radio could be a lifesaver. Yes, hikers would benefit—how many times do we hear of mountain and moorland rescue teams being called out each winter? But what about the owners of small boats that do not warrant a marine-band ship-to-shore radio? I think it fair to say that the lifeboat service would have been spared many hours of searching if small fishing boats and yachts had the right to carry a CB radio. What about the everyday motorist, broken down on the motorway or involved in an accident—both situations where CB would be of immense value? There are, of course, emergency telephones to cover these eventualities, but how often does one find these out of order due to vandalism? I think these points must surely form the basis of a good argument in favour of a UK Citizen's Band.

I am not so naive as to believe the band would be full of do-gooders permanently listening and waiting for emergencies. I am sure it would suffer misuse and abuse, but I think you will agree that there are very few aspects of modern life that are not abused by someone, somewhere. I can say in all honesty, that during my five years of operating CB, I encountered only a very small number of cases of illegal operating, such as the use of high-power r.f. amplifiers and v.f.o.s, etc.

I will agree with those who say the 27MHz band is in some ways unsuitable due to the ease of DXing when conditions open up. Although this would contravene the terms of the licence, I feel it much less likely to offend the listener than the fiasco on GB3LO and other repeaters. I would like to see a portion of the v.h.f. spectrum opened up to CB, but to be practical I think the 27MHz band would have to be accepted, as there is an unlimited amount of good-quality equipment already available at very modest prices.

I believe many people, especially some of my fellow amateurs, are being very guarded about this issue, but this is hardly surprising when Mr Goodier suggests using part of the amateur 2m band. There is no connection between CB and amateur radio—they are worlds apart and will always remain that way.

The suggestion of a novices' band is excellent. I have spent many enjoyable hours working slow c.w. and giving American novices some overseas contacts, and it is towards the United States that we must look when considering such a band.

I rather suspect Mr Goodier's motives to be somewhat personal, and I see them as an attempt to use 2 metres without taking the RAE. When his proposals are carefully studied, I believe they would benefit neither amateur radio nor a Citizen's Band service.

*John M. Southall G4DMT
Somersham
Suffolk*

Sir: Contrary to Mr Goodier's suggestion, 144.5–145.0MHz is not "A dead part of the 2 metre band". Many local nets use this section of the band, including the Norfolk-Lincolnshire nets, also it contains various beacons and the Dutch National (similar to RAYNET) frequencies. Why should the small amateur frequency allocations be cut up for a Citizen's Band, albeit in the guise of a novices' band?

It is quite simple these days to obtain an amateur licence without having to study Morse. Also to allow a free-for-all with 10 watts is just inviting interference problems. One watt would be more than adequate in any novices' band, but let it not be in the amateur frequency allocations, please.

*D. G. Blake G3MWW
Cromer
Norfolk*

New publication

Sir: I intend launching a new publication called *Innovation News*, initially as a newsletter, devoted to new designs, ideas, inventions, etc.

If anyone is interested in this idea, either as a subscriber or contributor, would they please contact me at the address below. An s.a.e. would be appreciated.

*B. McAleer
59 Castledine Street
Loughborough
Leicestershire
LE11 2DX*

Information Please


Sir: I would be glad to hear from readers with any knowledge of pulsed High Frequency as used in Medicine.

*G. H. Anthony
17 Ledbury Road
Hereford
HR1 2SY*

So You Want to Pass the RAE?



For details and coupon see page 78

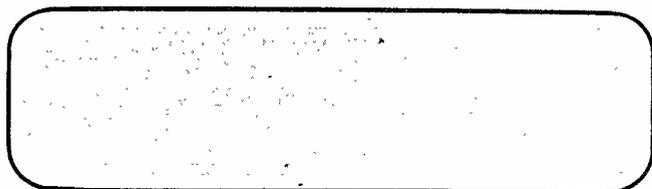

by Eric Dowdeswell G4AR

Letters from readers on aerial matters are very common, but reveal a certain misunderstanding on the results to be expected with simple half-wave dipoles. Such an aerial is usually cut to length using the formula $468/\text{frequency (MHz)}$ giving the answer in feet. It is sufficient to take the middle of the band concerned rather than a specific frequency. On 20m for example, take 14 200kHz, giving $468/14.2 = 33\text{ft}$ approximately.

This length of wire is then cut in half and fed in the centre with low-impedance feeder, preferably 75 ohm, which is led to the receiver. Some readers seem to think that this aerial will virtually eliminate all signals except those on 20m! Such an aerial is similar in electrical characteristics to a simple tuned circuit which has quite a broad selectivity curve, so it will still work, albeit with decreasing efficiency, from 10m to 160m, peaking on 20m. On the transmitting side one would not use a half-wave dipole on other than its design frequency, except perhaps on its third harmonic (a 7MHz aerial on 21MHz) but that is another matter.

I feel that it is rather pointless using an aerial designed for one band with a multi-band receiver. Much better to use a dipole, say 66ft, centre-fed with open wire tuned feeder and an a.t.u. to give optimum performance on all bands. Details with possible feeder lengths can be found in most aerial handbooks. The end-fed version, known as the "Zepp", was one of the first aerials ever designed and can be very useful in certain locations.

I am surprised that readers do not progress to simple wire element beams from end-fed wires, as they need not cost anything but can be made from copper wire obtained from old transformers, with bits of plastic strip for insulators. It seems to be thought that such beams will not work well unless the elements are nice and straight, precisely vertical or horizontal, as they appear in the books.

Nothing could be further from the truth, as the ends of elements may be drooped down and attached to such sundry supports as are available. Simple V-beams are very useful provided the legs are each at least a wavelength long, which is easily obtainable for say the 10 and 15m bands. An a.t.u. will permit operation on other bands and

still retain some gain. The legs of the "V" can even go from the top of a pole down to ground level if no distant supports are available.

The thing is to try out various designs and to experiment, but always use an a.t.u. to bring the whole system to resonance. The experience obtained will come in very useful indeed when a transmitting licence is eventually obtained.

On the Bands

In spite of finding it a problem to stay awake **Ian Marquis** A9140 of Leigh-on-Sea, Essex, has managed to cover all bands and it is very obvious that the 80m band is really waking up now with prefixes like EP2, JA, TU, ZL showing up in Ian's log, caught on his FRG-7 and "multi-band Slim Jim". A new one on me and I await details with great curiosity! On 20m Ian found a nice one in VK9XW on Christmas Island, very appropriate!

A pleasant letter from G4HLN, **Lawrence Bennett** of Bristol, who finds working DX a lot less easy than just listening to it! He has a Heathkit HW32A on 20m s.s.b. but is very keen on c.w. and would like to see some c.w. logs in this column. I agree, being a code nut, and as there must be plenty of readers studying code for their "A" licence how about some c.w. logs for a change?

Regular **Bill Rendell** from Truro, Cornwall, got very excited when he heard the "long path effect" on some OH stations on 20m and even went to the trouble of calculating the distances involved, having done some navigation in the past. However, I feel that there was probably an intense aurora borealis at the time, reflecting signals from the Scandinavian area. The effect is better known on the v.h.f. bands, when best results are obtained if all concerned turn their beams to the north. On 80m Bill logged CT2, KG4, TF, W0 and ZL4 for his first look at this band this season.

David Parker BRS40420 got his hands on some shiny new sets at the Leicester, show but didn't feel too jealous when he got back to his HQ120X. I'd plump for that set any day OM! David found Jan Mayen on 20m in the form of JX9WI for a rare one, plus ZD7SD on St. Helena.

General Notes

From Stokenchurch, Bucks, **Peter Recklin** BRS40425 found the *PW* series on the RAE to be easy reading compared to other books on the subject. Having organised the series, I feel rather good about his remarks. He, like many others, comments on the lack of interest shown by the RSGB in the "very beginners" and adds: "after all, that is where the new generation of radio amateurs will come from". Precisely! Peter had a go at an RAE course but found the pace too hot for the time he had available,

but I'm sure it was good experience. Peter has an FRG-7 modified with a Toko MFL455 filter, as per *Radio Communication*, August '78. Naturally enough, he finds reception of s.s.b. signals greatly improved.

Greg Duffy of East Kilbride, Glasgow, has been using a 15m dipole on several bands and still managed to copy things like HR3, 9N1 and YN1 on 20m on his FR50B. You may be interested in my opening few paragraphs, OM. From 23 Palace Avenue, Paignton, Devon, **Tom Hillier** writes to ask for advice on improving his ex-naval B40 receiver. There are plenty still around so if you think that you can help Tom, drop him a line direct.

With little time for DXing **Dave Wyatt** in Oswestry, Salop, found ZD9GH on Tristan da Cunha, with his BC348 and 90ft long wire on 20m. Good luck with the exams OM. Another seeking information is **Jim Clow** of 7 Montagu Road, Datchet, Berks, who has a Collins TCS10 set and no manual. "Complete stranger" **Colin Price** of Leuven in Belgium hails from Cambridge and is keen on taking the RAE with a view to getting an ON ticket, to keep in touch with home. Having just finished a post-graduate course, Colin acquired a Marconi Electra set plus an old 19 set and an a.t.u., so he's well on the way.

Through the kindness of a reader, **Chris Mortlock** of Brackley, Northants, acquired an R107 and, with the help of G3YMQ, is getting it up to scratch. Chris has been playing around with pins in maps to see what his aerial is doing on 80m as far as directivity is concerned. A good idea but a world map must be one of the great circle type that gives true direction and distance. Other maps are useless for this purpose.

Newcomers

Following my odd notes offering guidance to those newly acquainted with amateur radio, I have heard from a couple of dozen readers who were obviously standing on the sidelines, just looking in, but a bit shy to write in case they should be thought to be "slow". As I've said before, we all have to start somewhere, whatever the hobby, and it is only commonsense to seek advice and no-one will think less of us for that. **John Bull** (Laughton-en-le-Morthen [lovely!] South Yorks) wanted the aerial chart to go with his new SRX30 (Lowe Electronics).

George Grzebieniak, London W4, is 14 and collects old radios but now favours amateur radio. He has a Realistic DX160 and inside long wire. **Ian Scrimshaw** of Grimsby has an AR88 now and wonders about an aerial for 160m. Well, other than a specialised one, a long wire around 132ft and a.t.u. is probably the best answer, with a good earth connection if at all possible.

Glasgow University lecturer in biochemistry **Barry Clark** BSc, PhD, AIMLS, did not hesitate to write in, having been interested in crystal sets and simple valve sets a few years ago, at school. He is about to buy a receiver and intends to go on for his ticket. London W3 is the QTH of **Peter Smith** who has a National DR2800 but didn't have much luck with an a.t.u. I don't know this set but it sounds as if the "very long wire" is the trouble, already causing intermodulation problems on strong signals, compounded by the a.t.u.

David Allsop started recently with a CR100 in Abingdon, Oxon, and logged ZD7SS on St Helena. An FR50B has been added, greatly improving reception, with a 60ft wire. Heart attack victim **Len Wilson** of Scarborough wanted the aerial chart to go with his DX160 receiver and 60ft of wire in his bungalow loft. He, quite rightly, reckons amateur radio is for him now that he has to take things easy. Raised in the RAF on the R1155, AR88 and the R1475, **Jim Bence**, now of Hamilton,

Lanarkshire, has returned to radio with an Elizabethan Pathfinder set with 12 bands running from long waves to 470MHz, after 27 years, so not quite a newcomer!

Electronics technician **Eric Hayes** (Freckleton, Lancs) specialises in the repair of hi-fi gear but got the bug when a friend brought in a Trio QR666, and finished up buying the set! He's tried a 60ft wire and a vertical in the loft but wants something better. He intends to go for the RAE in the near future and I don't imagine you will have much difficulty OM.

In Stanford-le-Hope, Essex, **Alan Taylor** has "hung up his football boots" and with family ties having cut out sailing, gliding and skiing, he has turned to amateur radio, realising that it will keep him at home! Having been a 25 w.p.m. operator in the RAF he is well on the way to his G4 ticket. Alan, you almost had me in tears! Lastly, but certainly not the least, 13-year-old **Paul Burgess** of Lowestoft, Suffolk, has started off with a Heathkit AR3 valve set, but is concerned that it does not have a variable b.f.o. as he is keen on c.w. Hooray. If anyone can help with a manual or info write to Paul at 3 Andrew Way. With letters from 15 "newcomers" this month it ought to produce a couple of new licences at least, in due course!

Club News

Stevenage and District ARS meet first and third Thursdays at British Aerospace, Gunnels Wood Road, Stevenage, Herts, at 8pm. Programme arranged to August which gives us poor reporters a chance to get items in print in due time. Wish other clubs would do likewise! April 5 sees G3AGP talking on the problems of mobile operators, with a junk sale on the 19th. Newcomers, don't despise a junk sale, you'll never get better bargains anywhere! Sec. **Trevor Tugwell** G8KMV at 11 The Dell, Stevenage, for more info.

Southdown ARS meets on first Monday of the month (ex-Bank Holidays) at Chaseley Home for Disabled, Bolsover Road, South Cliff, Eastbourne at 1930 hours. Cyril Minns G3YSZ has ascended to the presidency and Dave Morgan G4FDW now handles the society's Newsletter. Copy please! Cyril Collins G8SC, prog. sec. would like to hear from anyone able to give talks, lectures, etc. Contact **Dick Jeffries** G8KQN, 16 James Avenue, Herstmonceux, East Sussex.

West Kent ARS have G4BWH talking on the engineering involved in the recent BBC programme changes, on March 16. On the 30th Tony Tory lectures on microprocessors in amateur radio. Meetings at the Adult Education Centre, Monson Road, Tunbridge Wells at 8pm, plus alternate Tuesdays at 8pm, at the Drill Hall, Victoria Road. More info from **Brian Castle** G4DYF, 6 Pinewood Avenue, Sevenoaks, Kent.

Wessex AR Group (sec. ed. **Geoff Cole** G4EMN, 3a Cavendish Road, Bournemouth) has a very special meeting at the lecture theatre, Bournemouth School, East Way, at 7.30pm on Friday March 16, when L. Moxon G6XN, aerial expert par excellence, will talk on Aerials and Propagation, Multi-banding of Aerials and Miniaturised Beams. Next day, on to skittles and social evening at the Moose Centre, Malmesbury Park Road, Bournemouth with special prizes for the ladies. Info on this from **Archie Hoggan** G8ASX on Bournemouth 427582.

Thames Valley ARTS are in for a treat when Dr. A. McGregor talks to them about Radio Astronomy on March 6 at usual meeting place, Giggs Hill Green Library, Thames Ditton. Meetings there first Tuesday every month. Contact **R. Blasdell** G3ZNW, 92 Bridge Road, Chessington, Surrey.

Remember, logs, letters by 15th of the month and allow for strikes, delays and other tribulations!

Log Extracts

W. Rendell:—80m CT2QN KG4W TF1AW W0MC ZL4KE 20m C5ABK EA8LS FK8CU (New Caledonia) JY5MC P29JS VK9XW 8P6IB 9Y4OV 15m C5ABK KZ5AS OX3WO 9J2TJ


L. Bennett G4HLN (worked):—20m C31OZ CT2AO FP0EE HC1BU J28BA OY81 PJ8CO YI1BGO

G. Duffy:—20m HR3JJ YN1CR 9N1MM 15m FY7AWZ KZ5RO OX3GW SU1CR TI2JV VP9JO YS1FAF ZL1BD 8P6FX 9L1AB 6W8AR

R. Bell:—20m ZL4HB ZL4LZ

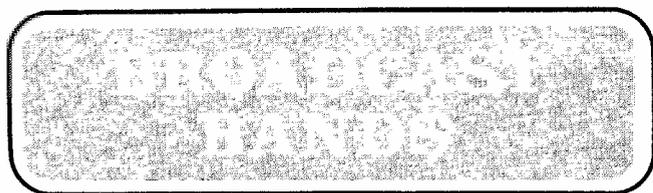I. Marquis:—160m (c.w.) K1PBW W1BB/1 80m CN8DO D4CBK EP2SL JA4BCW TU2FH ZL4KE 5B4HD 20m JY9DI VK9XW 15m VS6HG XT2AV 10m FR7ZL HZ1SH SU1DP TR8GDC

All s.s.b. except where stated otherwise.



MEDIUM WAVE DX

by Charles Molloy G8BUS

A DXer in the Shetland Islands, **Arthur Tate**, writes to say that he has modified his m.w. loop to work on the long waves simply by fitting a fixed capacitor (no value given) in parallel with the loop's tuning capacitor. Arthur asks for comments about this arrangement which works very well with BBC Radio 4 on 200kHz. Radio 4 incidentally, appears to have become semi-DX in the Shetlands since the great change around last November.

Modifying a Loop for the Long waves

The disadvantage of Arthur's method is the very restricted tuning range that is obtained. With my 40 inch loop, a parallel capacitor of 2000pF tunes it to 300kHz, but the tuning capacitor would only adjust the frequency through a range of about 20kHz! At the l.f. end of the band the situation is worse. A fixed capacitor of 6700pF tuned the loop to 155kHz, but this time the tuning control had little effect.

To cover the band, a capacitance range of 2500pF to 7200pF is required which is obviously impracticable. None-the-less, this method is of value if you want to tune the loop to a single frequency as Arthur did. Fitting "in parallel" means joining one wire of the fixed capacitor to one terminal of the tuning capacitor on the loop and joining the other end to the other terminal. No need to disconnect anything, you just bridge the fixed capacitor across the variable one.

A better method is to insert a fixed inductor in series with the loop's main winding. Disconnect one of the two wires to the tuning capacitor. Connect this wire to one end of the inductor and run a wire from the other end of the inductor to the tuning capacitor in place of the disconnected wire. You may have to put the inductor inside a metal box, which should be earthed, in order to prevent it acting as an

aerial. The inductor should have a value of about 2000 μ H, i.e. 2 millihenries, and the loop should now tune over the long-wave band. The secondary winding of a long-wave tuning coil would have about the right value of inductance. If the loop will not tune to a low enough frequency then more inductance is required. If it will not tune high enough, then remove some turns from the inductor or use one of a lower value.

Long-wave Loops

Both of these methods of modifying a m.w. loop are at best a makeshift, but they do enable the DXer to try out the long waves without too much effort. Anyone seriously interested in DXing on this band should construct a l.w. loop. It will certainly have greater pick-up than a modified m.w. loop. Pick-up is proportional to the number of turns and to the size of the loop. A 40 inch l.w. loop will have about $3\frac{1}{2}$ times the number of turns of a 40 inch m.w. loop, and therefore will have $3\frac{1}{2}$ times the pick-up.

It is difficult to specify the exact number of turns that are required as the self-capacitance of such a winding will be high. For a 40 inch loop the number should lie between 22 and 28, and if you start with the higher figure you can remove turns one at a time until the desired range is achieved. The type of wire to use is not important so long as it is insulated and rigid when wound. A 500pF tuning capacitor or thereabouts, should be adequate as the frequency ratio (highest to lowest) on the l.w.s is approx 2:1 instead of 3:1 on the m.w.s.

Readers' Letters

An interesting letter from **N. Soar**, who lives near Sheffield, and is the author of *50 Circuits using Germanium, Silicon and Zener Diodes* published by Babani. He describes how to boost the performance of a transistor portable, by placing it close to a crystal set tuning coil which in turn is connected to an aerial. If the receiver is tuned to a weak signal and the crystal set coil is tuned to the same frequency, then the coil will feed extra signal to the receiver by induction which greatly improves reception. With this set-up he was able to pick up Radios Manchester, Blackburn and Nottingham. Reception was good enough to listen to the programmes.

This method will be of interest to DXers who use a transistor portable that does not have an aerial socket, and it works on the same principle as mounting the receiver on a shelf fixed to a m.w. loop as described in this column in the December 1978 issue. You can also boost the signal by wrapping the aerial lead round the receiver two or three times, but you will boost all stations not just the one you are tuned to and this may cause overloading. It does help on some occasions though.

The well-known R1155 receiver is in use by **Chris Marcroft** at Ramsbottom, who obtained one for £3 and modified it along the lines described in an article I wrote for the March 1967 issue of *PW*. When connected to a 130ft long wire and a.t.u., this rig pulled in WINS on 1010kHz, WNEW on 1130 and VOCM 690, CJYQ 930 which are located in New York City and St John's in Newfoundland. Chris prefers his long wire to a m.w. loop as the pick-up is much greater, which is what one would expect. If you have a long wire and a loop, then it is worthwhile fixing a switch so that you can try each aerial in turn, to see which gives the best results with any particular station.

Reader **Andrew Roger** is puzzled by the number of layers in the ionosphere and how they affect DXing. So far


as the medium and long waves are concerned, only the bottom two layers, the D and the E are of interest. The D layer, which absorbs l.f. signals, is maintained by the sun and disappears after dark to allow DX to be heard. The E layer, which also is created by the sun, does not disappear entirely after dark and this is the layer that reflects the DX on the medium and long waves. In mid-winter the D layer may only appear around mid-day and consequently some DX can be heard at times during daylight hours of winter mornings and afternoons.

DX Heard

Our long-wave DXer Andrew Roger of Bristol reports hearing the USSR 1st programme on 173kHz, Tebessa Algeria on 251kHz, Lahti in Finland on 254, an unidentified station behind Czechoslovakia on 271 (Novosibirsk Siberia?) and Minsk on 281. Reception was during the evening, using a Vega Spidola with internal aerial, and Andrew draws attention to the English programme from Tebessa which is on 251kHz daily from 2000 to 2030.

Some Spanish DX comes from **Bob Bell** (Blyth) who used his Yaesu Musen FRG-7 and 20 inch mini-loop to pull in Seville on 683kHz, Malaga 729, San Sebastian 774, Seville? on 792, Murcia 1179 and La Linea on 1314. Spanish stations have been conspicuous since last November, but there has been quite a shuffling about of frequencies and you have to listen for the identification to be certain.

Chris Mancroft asks about Radio Beacons on the medium waves and he reports hearing "MW" in Morse on 1008kHz and "RO" on 1012, which appear to be at their strongest when DX conditions to North America are good. The medium waves are supposed to be used exclusively for broadcasting, though in practice some radio beacons are to be found within the band below 800kHz. It has also been the practice in some countries to leave their m.w. transmitters on the air after the programmes finish and to key the transmitter with some sort of identification. Sottens in Switzerland, now on 765kHz, used to transmit "SOT" during the night, though whether this was for navigation purposes or just to keep the frequency occupied and deter intruders, was not clear. Morse signals on the medium waves are very likely the harmonics of long-wave radio beacons. Such beacons would be of considerable value to the DXer if their locations were known as they could be used as a guide to propagation. Unfortunately it is not too easy to track down many of them.

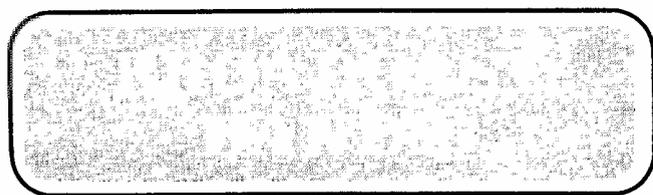

SHORT-WAVE BROADCASTS

by **Charles Molloy G8BUS**

Readers often comment on the current state of the short-wave bands which are dominated by high-power broadcasts of political propaganda and jamming. **T. W. G. Eltenham** complains that smaller countries do not get a look-in, while **George Rose** comments on the increasing number of harmonics observed on the higher frequencies, caused no doubt by a combination of super-power trans-

mitters and beam antennas. In my opinion it is an absolute waste of time to write to the offenders, who have no interest in DXers or in the hobbyist s.w. listener, but there are several things that can be done to get round the problem. After all, if DXing were all that easy then it would cease to be attractive!

When to Listen

Not every band is dominated by high-power broadcasts all of the time. Generally speaking the higher frequencies are in use during the day and lower ones at night, but there is DX to be found when the bands are quiet. Latin Americans for example, are on the 19m and 25m bands during the late evening as the path to that area is still open then. Mixed paths of daylight and darkness can also produce signals on unexpected frequencies, usually at the middle of the spectrum. Low frequencies can yield interesting catches during the day.

Out of Band Stations

As a result of overcrowding there is an unofficial spreadout, up to 100kHz beyond the limits of each s.w. band. Some of the late arrivals to international broadcasting are to be found here. Typical is Kuwait on 12 085kHz which is outside the h.f. limit of the 25m band. This station has European-style programming and is widely reported. Countries to be found around the edges of the 49m, 41m, 31m, 25m and 19m bands are Israel, Andorra, Egypt, Iran, Pakistan, Vietnam, Saudi Arabia, India, Bangladesh, Austria and Guinea, so that it is always worthwhile tuning near the upper and lower limits of each band and investigating weak signals.

Another area where interesting DX is to be found is in the spaces between the international bands, though telegraph QRM can be troublesome. Israel broadcasts its domestic service on approx 9020kHz, which is well away from the 31m band. Out-of-band transmissions appear to be used mainly for domestic broadcasting, particularly by China but also by India, Iran, Israel, Mongolia, Korea, Turkey and on the l.f. side of the 49m band by Peru, Indonesia, Bolivia and Honduras. Always check a weak signal as real DX seldom comes roaring in.

The B40 Receiver

Many thanks to *PW* readers **G. A. Cartwright**, **John Markey**, **D. Porter** and **Bill Hentall**, for responding to Roderick William's request in the January issue for suggestions for a suitable replacement for the output valve in his B40 wartime communications receiver. The B40 was used by the Navy and although bulky and heavy it is quite presentable in appearance. It has its own speaker and can be plugged straight into the mains and used without modification. It is the only set I have come across that has an anti-crossmodulation control which works by adjusting the bias to the control grid of the first r.f. valve. There were a number of variants of the B40 indicated by a suffix letter. There was also the B41, a low frequency version covering 15kHz to 720kHz in five bands—not much use for broadcast band DX as it stands.

A number of readers have referred to the B40 recently. **Robert Round** remarks wryly: "My first receiver was a B40, and to be honest I think I was a fool to get rid of it." I can sympathise Robert, I feel the same way about my old much-modified CR100 which was disposed of some time ago. **G. Stainton** is desperate for a manual for his B40. Try Brooks, Farrant House, Winstanley Road, London SW11 2EJ who supply reprints of many manuals. John Markey

would like to fit an antenna trimmer to his B40. Connect a small variable capacitor of about 50pF in parallel with the first r.f. section of the main tuning capacitor, if you can locate it. John would like to contact readers who have done any "mods" to the B40, replies direct to John please at 4 Harrison Way, Lydney Gdns, Gloucester GL4 5BN. Perhaps someone will start a club for B40 owners!

11 Metre Band

This band (25 605–26 095kHz) is gradually opening up now that increasing solar activity is bringing higher frequencies into use. **Harold Brodribb** of St. Leonards-on-Sea (AR88) reports hearing Radio RSA on 25 790kHz (also announcing 21 535 and 15 220) and Radio France on 25 630, both stations logged during the afternoon. **K. H. Smith** of Ross-on-Wye picked up the Voice of America in the early evening on his home-brew receiver on 26 040 and **Mark Hallam** of Hereford (Realistic DX160 plus long wire) logged Radio RSA on 25 790 from 1100–1200 and again between 1300 and 1530 with a very strong signal and English programming.

Other stations reported recently were Radio Liberty on 25 690 and IBA Jerusalem on 25 605kHz. 11 metres is a daytime band and worldwide reception is possible when it is open. Broadcasters will be tempted onto 11 metres to escape from the congestion on lower bands, even though it is outside the range of many domestic receivers. If your receiver will tune as high as 11 metres then it is worth giving the band a try.

Tropical Bands

The main tropical band is 60 metres which extends from 4750 to 5060kHz. Unlike the main s.w. bands, 60m is shared with commercial users and is only reserved for broadcasting in tropical areas and parts of Asia. As a result there is a lot of telegraph QRM on 60m and the newcomer to the band, especially if he listens at the wrong time of day, may not hear any broadcasting stations at all. A path of darkness between Tx and Rx is required before reception is possible, so it is a waste of time looking for DX on 60m in the middle of the day. A good outdoor aerial is an advantage, though many of the better portables will deliver DX with their internal aerial.

A good log of 60m DX comes from **Bob Bell** who lives in Blyth and uses an FRG-7. He reports hearing Radio Universo in Venezuela on 4800kHz at 0200, Benin on 4870 at 1825, Radio Casa Ecuador on 4930 at 0215, Radio Ecos Venezuela on 4980 at 0225 and two out-of-band catches, one in Chinese on 4380 at 1750 and an unidentified station in English on 4385 at 1805. **L. Lewis** (Pensilva in Cornwall) used his Realistic DX160, long wire and a.t.u. to pull in Radio Guatapuri in Colombia on 4817kHz at 0535, and Radio Garoua in Cameroon on 5010, with a programme in English at 1830. **Mark Hattam** picked up Radio ELWA Liberia on 4779 at 2200 and Radio Nigeria on 4990 at 1800 both in English.

DX Reported

A Trio 9R59D plus Joystick are in use at Mackworth near Derby by **Roy Patrick** who reports hearing Kabul, Afghanistan on 11 805 with a programme in English at 1900, Radio Nacional Chile on 11 720 at 2205, Radio Australia on 11 870 (replacing 11 855) from 1500 to 1700. Roy mentions that Radio Monitors International DX programme from SLBC Sri Lanka is on the air on Sun-

Reports on the various bands are welcome and should be sent direct, by the 15th of the month, to:


AMATEUR BANDS Eric Dowdeswell G4AR, Silver Firs, Leatherhead Road, Ashted, Surrey KT21 2TW. Logs by bands, each in alphabetical order.

MEDIUM and SW BANDS Charles Molloy G8BUS, 132 Segars Lane, Southport PR8 3JG. Reports for both bands **must** be kept separate.

VHF BANDS Ron Ham BRS15744, Faraday, Greyfriars, Storrington, Sussex RH20 4HE.

days at 1100 on 11 835, 15 120, 17 850 and again at 1900 on 9720, 11 870, 15 115 and 17 850.

From RSA-land comes a log from **David Webb** who lives in Sunnyside, Pretoria and who uses an old domestic receiver of unknown origin together with a wire put round the picture rail. With this set-up he has managed to pull in Tirana on 9500 at 1930, Australia on 9570, 11 940 at 1500, Algiers on 9500 at 1915 in English and Radio Sweden on 15 240 at 1845. A Racal 117E and 80ft long wire are in use by **V. Frankl** of Rotherham, who reports hearing out-of-band Pyongyang on 6576kHz at 2000, South Korea on 7550 at 1615 and Radio Athens on 9930 at 1920. **Andrew Rogers** of Bristol (Vega Spidola and whip) heard Amman in Jordan on 9560 at 1500 and Riyadh, Saudi Arabia on 6075 at 2110. **Roger Shepherd** of Whitstable has had his National Panasonic RF1105 for only two months, and during this time he has heard programmes in English from Turkey on 9515 at 0105, Israel on 9435 at 2005 and Spain on 9505 at 2030. **J. Pritchard** (Warsop) now has an ITT Touring CD108 with digital readout which picked up Pakistan on 17 665 at 1104 and the Voice of Nigeria on 15 185 at 1849.

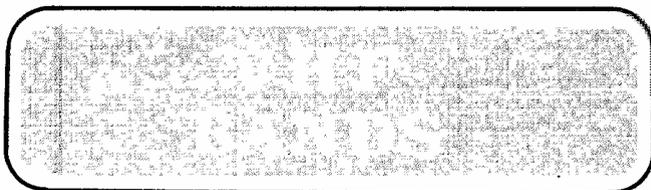

by Ron Ham BRS15744

One of the most exciting things about the radio frequency spectrum above 30MHz is that unexpected natural disturbance which can suddenly occur and take the most experienced v.h.f. enthusiast by surprise and, as my readers have shown, 1979 began in just that way.

Solar

Early in 1978, we observers of the sun were confidently expecting the then high level of sunspot activity to continue throughout the year, but, how wrong we were. Having recorded radio noise from the "active" sun on 108 out of the first 212 days (compared with 106 days for all of 1977), the count fell drastically to only 24 "active" days from the remaining 153, which means that, in future, we should consider sunspot activity on a day-to-day basis. At 1036 on December 31, **John Branegan** GM8OXQ, Saline, Fife, heard a strong burst of solar noise covering a wide frequency range, and **Cmdr Henry Hatfield**, Sevenoaks, Kent, and myself, recorded several individual bursts of solar noise, at 136 and 146MHz, on January 3 and 4, and

RST VALVE MAIL ORDER CO.

CLIMAX HOUSE, FALLSBROOK ROAD, LONDON SW16 6ED

SPECIAL EXPRESS MAIL ORDER SERVICE

SEMICONDUCTORS

AA119 0.10	ASV26 0.40	BC159 0.10*	BCY72 0.13	BF194 0.09*	BZX61 0.18	OA70 0.30	OC82 0.65	ZS271 0.23*	2N697 0.25	2N3055 0.70
AA300 0.27	ASV27 0.40	BC167 0.12*	BCZ11 1.26	BF195 0.09*	Series	OA79 0.30	OC83 0.65	ZS278 0.57*	2N698 0.30	2N3440 0.60
AA332 0.42	ASZ15 1.25	BC170 0.11*	BD115 0.45	BF196 0.10*	BZY88 0.13	OA81 0.30	OC84 0.65	ZTX107 0.11*	2N705 1.20	2N3441 0.80
AAZ13 0.18	ASZ16 1.25	BC171 0.10*	BD121 1.20	BF197 0.12*	CRS/140 0.60	OA85 0.30	OC122 1.50	ZTX108 0.10*	2N706 0.15	2N3442 1.10
AAZ15 0.34	ASZ17 1.25	BC172 0.10*	BD124 1.30	BF200 0.27	CRS/305 0.45	OA90 0.30	OC123 1.75	ZTX109 0.12*	2N708 0.20	2N3525 0.80
AAZ17 0.27	ASZ20 1.50	BC173 0.12*	BD131 0.36	BF224 0.20*	CRS/340 0.75	OA91 0.30	OC139 2.25	ZTX300 0.12*	2N930 0.20	2N3614 1.50
AC107 0.60	ASZ21 2.00	BC177 0.15	BD132 0.38	BF257 0.24	CRS/360 0.90	OA95 0.08	OC140 2.25	ZTX301 0.13*	2N1131 0.26	2N3702 0.11*
AC125 0.20	AU110 1.70*	BC178 0.14	BD133 0.34*	BF258 0.26	GEX66 1.50	OA200 0.09	OC141 3.25	ZTX302 0.15*	2N1132 0.26	2N3703 0.13*
AC126 0.20	AU113 1.70*	BC179 0.16	BD136 0.40*	BF259 0.32	GJ5M 0.75	OA202 0.09	OC170 1.00	ZTX303 0.17*	2N1302 0.35	2N3704 0.13*
AC127 0.20	AU170 1.70*	BC182 0.11*	BD139 0.43*	BF336 0.20*	GJ5M 0.75	OA206 1.00	OC171 1.00	ZTX304 0.19*	2N1303 0.35	2N3705 0.13*
AC128 0.20	BA145 0.13*	BC183 0.10*	BD140 0.44*	BF337 0.30*	GUM3078A 1.75	OA220 1.00	OC200 1.00	ZTX311 0.12*	2N1304 0.45	2N3706 0.13*
AC141 0.25	BA148 0.13*	BC184 0.11*	BD141 2.00	BF338 0.31*	KS100A 0.45*	OA221 1.00	OC201 1.75	ZTX314 0.20*	2N1305 0.45	2N3707 0.13*
AC141K 0.45	BA154 0.09	BC193 0.13*	BD144 2.00	BF351 0.20*	MJE340 0.80	OA222 1.00	OC202 1.75	ZTX300 0.50	2N1306 0.50	2N3708 0.10*
AC142 0.20	BA155 0.10	BC212 0.13*	BD181 1.10	BF358 0.20*	MJE370 1.17	OA226 1.00	OC203 1.75	ZTX501 0.14*	2N1307 0.50	2N3709 0.10*
AC142K 0.30	BA156 0.09	BC214 0.15*	BD182 1.18	BF359 0.20*	MJE371 0.61	OA226 1.00	OC204 2.50	ZTX502 0.16*	2N1308 0.55	2N3709 0.10*
AC176 0.20	BAW62 0.05	BC237 0.09*	BD238 0.55	BF360 0.20*	MJE520 0.52	OC16 2.90	OC205 2.50	ZTX503 0.17*	2N1309 0.55	2N3711 0.10*
AC187 0.20	BAX13 0.06	BC238 0.12*	BD238 0.55	BF361 0.20*	MJE521 0.55	OC20 2.50	OC206 2.50	ZTX504 0.20*	2N1613 0.25	2N3711 0.10*
AC188 0.20	BAX16 0.09	BC301 0.25	BDX10 0.91	BF362 0.20*	MJE2955 1.25	OC22 2.50	OC207 1.75	ZTX550 0.16*	2N1671 1.50	2N3773 3.00
ACV17 0.85	BAX16 0.09	BC301 0.25	BDX32 2.00	BF363 0.20*	MJE3055 0.75	OC23 2.75	ORP12 0.75	IN814 0.05	2N2147 1.75	2N3819 0.36*
ACV18 0.80	BC107 0.12	BC303 0.24	BDY20 1.25	BF364 0.26	MPE102 0.30*	OC24 3.00	R2008B 1.75*	IN816 0.07	2N2148 1.65	2N3820 0.45*
ACV19 0.75	BC108 0.12	BC307 0.10*	BDY20 1.25	BF365 0.26	MPE103 0.30*	OC26 0.90	R2009 2.25*	IN4001 0.06	2N2218 1.25	2N3823 0.55*
ACV20 0.70	BC113 0.12*	BC327 0.20*	BF115 0.50	BF366 0.26	MPE104 0.30*	OC29 2.00	R2010B 1.75*	IN4002 0.06	2N2219 0.24	2N3866 0.72
ACV21 0.75	BC114 0.13*	BC328 0.18*	BF152 0.18	BF367 0.26	MPE105 0.30*	OC35 1.50	T1C226D1.20	IN4005 0.07	2N2221 0.18	2N3904 0.13*
ACV39 1.50	BC115 0.14*	BC337 0.17*	BF153 0.20	BF368 0.26	MPE106 0.30*	OC36 1.50	T1L209 0.20	IN4006 0.08	2N2222 0.18	2N3905 0.13*
AD149 0.70	BC116 0.15*	BC338 0.18*	BF154 0.17	BF369 0.26	MPSA600.24*	OC41 0.80	T1P29A 0.44*	IN4006 0.08	2N2223 2.75	2N4058 0.14*
AD161 0.45	BC117 0.17*	BCY30 1.00	BF160 0.16	BF370 0.26	MPSA600.26*	OC42 2.25	T1P30A 0.41*	IN4007 0.08	2N2223 2.75	2N4058 0.14*
AD162 0.45	BC118 0.10*	BCY31 1.00	BF167 0.20	BF371 0.26	MPSU01.36*	OC44 0.60	T1P31A 0.45	IN4009 0.06	2N2368 0.17	2N4059 0.14*
AF106 0.45	BA155 0.10	BCY32 1.00	BF173 0.20	BF372 0.26	MPSU06.46*	OC45 0.55	T1P33A 0.69	IN4009 0.06	2N2484 0.20	2N4060 0.12*
AF114 0.35	BC126 0.20*	BCY33 0.90	BF177 0.24	BF373 0.26	MPSU66.49*	OC71 0.55	T1P34A 1.73	IN5401 0.13	2N2904 0.25	2N4061 0.12*
AF115 0.35	BC135 0.14*	BCY34 0.90	BT178 0.24	BF178 0.24	NE555 0.45	OC72 0.55	T1P41A 0.63	IS44 0.04	2N2905 0.25	2N4124 0.15*
AF116 0.35	BC136 0.15*	BCY39 3.00	BT179 0.25	BF179 0.25	NK1401 2.00	OC73 0.70	T1P42A 0.70	IS920 0.07	2N2906 0.21	2N4124 0.15*
AF117 0.35	BC137 0.15*	BCY40 1.00	BU205 1.75*	BF180 0.30	NK1401 2.00	OC74 0.65	T1P2955 1.67	IS921 0.07	2N2907 0.21	2N4286 0.20*
AF139 0.40	BC147 0.08*	BCY42 0.25	BU206 2.25*	BF181 0.30	NK1401 2.00	OC75 0.65	T1P3055 0.66	IS921 0.07	2N2907 0.21	2N4288 0.22*
AF186 1.20	BC148 0.08*	BCY43 0.25	BU208 2.00*	BF182 0.30	NK1401 2.00	OC76 0.65	T1P3055 0.66	IS921 0.07	2N2907 0.21	2N4288 0.22*
AF239 0.45	BC149 0.08*	BCY48 0.25	BY183 0.25	BF183 0.25	NK1401 2.00	OC77 1.25	IS140 0.55*	IS921 0.07	2N2907 0.21	2N4288 0.22*
AF239 0.45	BC157 0.09*	BCY70 0.15	BY126 0.14	BF184 0.25	NK1401 2.00	OC81 0.65	IS140 0.55*	IS921 0.07	2N2907 0.21	2N4288 0.22*
AF212 2.75	BC158 0.08*	BCY71 0.17	BY127 0.15	BF185 0.25	NK1401 2.00	OC82 1.25	ZS170 1.21	IS921 0.07	2N2907 0.21	2N4288 0.22*
						OC812 1.60	ZS178 0.54*	IS921 0.07	2N2907 0.21	2N4288 0.22*

VALVES

AZ31 1.10*	ECC831 0.55*	EL32 1.50*	EL33 3.50*	EL34 (Thorn) 2.20	EL34 (Mullard) 2.24	EL41 1.25*	EL42 1.25*	EL43 1.10*	EL44 0.45*	EL45 0.75*	EL46 1.10*	EL47 1.10*	EL48 1.10*	EL49 1.10*	EL50 1.10*	EL51 1.10*	EL52 1.10*	EL53 1.10*	EL54 1.10*	EL55 1.10*	EL56 1.10*	EL57 1.10*	EL58 1.10*	EL59 1.10*	EL60 1.10*	EL61 1.10*	EL62 1.10*	EL63 1.10*	EL64 1.10*	EL65 1.10*	EL66 1.10*	EL67 1.10*	EL68 1.10*	EL69 1.10*	EL70 1.10*	EL71 1.10*	EL72 1.10*	EL73 1.10*	EL74 1.10*	EL75 1.10*	EL76 1.10*	EL77 1.10*	EL78 1.10*	EL79 1.10*	EL80 1.10*	EL81 1.10*	EL82 1.10*	EL83 1.10*	EL84 1.10*	EL85 1.10*	EL86 1.10*	EL87 1.10*	EL88 1.10*	EL89 1.10*	EL90 1.10*	EL91 1.10*	EL92 1.10*	EL93 1.10*	EL94 1.10*	EL95 1.10*	EL96 1.10*	EL97 1.10*	EL98 1.10*	EL99 1.10*	EL100 1.10*			
6B8GT 1.30	6B6J 1.20*	6B6K 1.20*	6B6L 1.20*	6B6M 1.20*	6B6N 1.20*	6B6P 1.20*	6B6Q 1.20*	6B6R 1.20*	6B6S 1.20*	6B6T 1.20*	6B6U 1.20*	6B6V 1.20*	6B6W 1.20*	6B6X 1.20*	6B6Y 1.20*	6B6Z 1.20*	6B7A 1.20*	6B7B 1.20*	6B7C 1.20*	6B7D 1.20*	6B7E 1.20*	6B7F 1.20*	6B7G 1.20*	6B7H 1.20*	6B7I 1.20*	6B7J 1.20*	6B7K 1.20*	6B7L 1.20*	6B7M 1.20*	6B7N 1.20*	6B7O 1.20*	6B7P 1.20*	6B7Q 1.20*	6B7R 1.20*	6B7S 1.20*	6B7T 1.20*	6B7U 1.20*	6B7V 1.20*	6B7W 1.20*	6B7X 1.20*	6B7Y 1.20*	6B7Z 1.20*	6B8A 1.20*	6B8B 1.20*	6B8C 1.20*	6B8D 1.20*	6B8E 1.20*	6B8F 1.20*	6B8G 1.20*	6B8H 1.20*	6B8I 1.20*	6B8J 1.20*	6B8K 1.20*	6B8L 1.20*	6B8M 1.20*	6B8N 1.20*	6B8O 1.20*	6B8P 1.20*	6B8Q 1.20*	6B8R 1.20*	6B8S 1.20*	6B8T 1.20*	6B8U 1.20*	6B8V 1.20*	6B8W 1.20*	6B8X 1.20*	6B8Y 1.20*	6B8Z 1.20*

INTEGRATED CIRCUITS

7400 0.16	7412 0.25	7432 0.30	7454 0.18	7491 0.80	74118 1.00	74144 2.50	74173 1.40	74196 1.20	TBA530 1.98*	TBA920 2.90
7402 0.16	7416 0.32	7433 0.36	7470 0.35	7492 0.80	74119 1.50	74145 2.50	74174 1.50	74197 1.10	TBA5400	TBA920 2.99*
7403 0.16	7417 0.32	7434 0.32	7471 0.35	7493 0.80	74120 0.83	74146 2.00	74175 0.90	74198 2.25	TBA5500	TBA990Q 2.99*
7404 0.16	7418 0.32	7435 0.32	7472 0.35	7494 0.80	74121 0.40	74147 1.75	74176 1.20	74199 2.25	TBA5600C	TCAT700 2.99*
7405 0.16	7420 0.17	7440 0.18	7473 0.40	7495 0.72	74122 0.60	74148 1.75	74177 1.20	74200 1.75	3.22*	TCAT700A 1.38*
7406 0.16	7422 0.20	7441AN 0.95	7474 0.40	7496 0.80	74123 1.00	74149 1.75	74178 1.25	74201 1.75	LM309K 1.50	
7407 0.16	7423 0.32	7442 0.72	7475 0.54	7497 3.00	74125 0.55	74150 1.60	74179 1.25	74202 1.75	TAA570 2.30*	
7408 0.40	7424 0.32	7443 0.95	7476 0.40	7498 0.80	74126 0.55	74151 0.85	74180 1.15	74203 1.75	TAA630S	
7409 0.20	7425 0.30	7444 0.95	7477 0.40	7499 0.80	74127 0.55	74152 1.75	74181 1.25	74204 1.75	TAA700 3.91	
7410 0.20	7426 0.30	7445 0.95	7478 0.40	7500 0.80	74128 0.60	74153 0.85	74182 1.15	74205 1.75	TAA700 3.91	
7411 0.20	7427 0.30	7446 0.95	7479 0.40	7501 0.80	74129 0.60	74154 1.75	74183 1.25	74206 1.75	TAA700 3.91	
7412 0.20	7428 0.43	7447 0.95	7480 0.55	7502 0.80	74130 0.70	74155 0.85	74184 1.15	74207 1.75	TAA700 3.91	
7413 0.16	7430 0.17	7448 0.95	7481 0.55	7503 0.80	74131 0.70	74156 0.85	74185 1.15	74208 1.75	TAA700 3.91	
		7449 0.95	7482 0.75	7504 0.80	74132 0.70	74157 0.85	74186 1.15	74209 1.75	TAA700 3.91	
		7450 0.18	7483 0.90	7505 0.80	74133 0.70	74158 0.85	74187 1.15	74210 1.75	TAA700 3.91	
		7451 0.18	7484 1.00	7506 0.80	74134 0.70	74159 0.75	74188 1.15	74211 1.75	TAA700 3.91	
		7452 0.18	7485 0.35	7507 0.80	74135 0.70	74160 0.75	74189 1.15	74212 1.75	TAA700 3.91	
		7453 0.18	7486 0.35	7508 0.80	74136 0.70	74161 0.75	74190 1.15	74213 1.75	TAA700 3.91	
			7487 0.35	7509 0.80	74137 0.70	74162 0.75	74191 1.15	74214 1.75	TAA700 3.91	
			7488 0.35	7510 0.80	74138 0.70	74163 0.75	74192 1.15	74215 1.75	TAA700 3.91	
			7489 0.35	7511 0.80	74139 0.70	74164 0.75	74193 1.15	74216 1.75	TAA700 3.91	
			7490 0.52	7512 0.80	74140 0.70	74165 0.75	74194 1.15	74217 1.75	TAA700 3.	

10 to 16, inclusive. These bursts were associated with about eight groups of sunspots, some with four and six spots, seen by Henry with his spectroheliograph. On the 6th he saw five plages, on the 11th a small flare, and a bright active area was visible on the 12th and 13th.

Aurora

Considering this solar activity, it was not surprising that ionospheric disturbances were reported by the BBC World Service on January 5 and 6, and John Branegan noted auroral events on the 4th and 7th. Between 1810 and 1817 on the 4th, John heard tone "A" signals from the 2m beacons in Wrotham, GB3VHF and Kiel, DL0PR, and although the auroral signals faded out on 2m around 1820 they persisted on Band I TV until 1907. During the event, several of John's fellow GMs worked London stations on 2m. Following an auroral alert from **John Matthews** G3WZT, near Horsham, Sussex, around 1900 on the 7th, **John Cooper** G8NGO, Cowfold, Sussex, heard a French station working a GM on 2m s.s.b. and, in turn, phoned **Alan Baker** G4GNX, Newhaven, who heard some weak s.s.b. signals bouncing off the auroral display, while in nearby Lancing, **Roy Bannister** G4GPX, heard GM4DSZ. Alan also confirmed a report from **Cecil Sadler** G3JEO, Brighton, that signals in the 40m band were being influenced by the aurora. Between 1500 and 2000 on the 7th, John Branegan received auroral signals from European TV in Band I, f.m. broadcast stations in Band II, strong 2m signals from stations in DL, EI, G, GI, GM, GW, LA and SM and from beacons around the UK, in Cornwall, GB3CTC, Northern Ireland, GB3GI, Lerwick, GB3LER and Kent, GB3VHF. John also had three contacts through OSCAR-8J during the event and was told by SM5FUR that, the aurora was affecting all Sweden.

The 10 Metre Band

Mark Hattam, Hereford, using his Realistic DX-160 receiver and a long wire aerial, says that signals from Radio South Africa and Voice of America, in the 11m band, were "pounding in" on January 9, and in the 10m band he heard UN3CEY in QSO with an American station, and a harmonic of a Radio Moscow transmission around 28.750MHz. **Michael Mrzyglod**, Wallingford, Oxford, who is in the process of joining the RSGB, reports hearing several European and Russian amateurs

on 10m around noon on December 26. From December 15 to January 17 I received signals, almost daily, from the International Beacon Project stations in Bahrain, A9XC, Germany, DL0IGI and Cyprus, 5B4CY and less frequently from Bermuda, VP9BA and Florida, N4RD. The majority of these signals were received on my FR101 with a long wire aerial and averaged around 539.

DX Television

At 0910 on December 19 I heard strong television sync pulses on 49.75MHz with my R216, fed by a dipole aerial, which alerted me to switch on my JVC3060, also fed by a dipole, and there on Ch. R1, for a short while was a test card from YLE-HK1, Finland. Between 0800 and 0920 on the 20th both **Ian Rennison**, Horsham, using a JVC3040, and myself, received a very strong test card from Poland (Fig. 1), on R1, accompanied by the sound, which I received on the R216, on 56.25MHz. From 0745 until about 0930 on January 4, Ian and myself received strong pictures from both Poland and Hungary on R1 (Fig. 2), and at times both signals were fighting for predominance on our receivers.

During the afternoon of the 7th, John Branegan, using his Eddystone 770R, heard video signals on 48.25, 49.75 and 61.8MHz and TV sound, in Spanish, on 53.75 and 60.75MHz. John reports that the m.u.f. was up around 44MHz to the USA on January 5, 6 and 7 and, at 1450 on the 6th, he received French TV sound on 41.25MHz and, "strangely enough," says John, "the aerial seemed to peak around 270°".

Tropospheric

Despite the poor conditions on December 26, Roy Bannister heard signals from the new Norfolk repeater, GB3FR, on R7 when the London repeater, GB3LO, was quiet, and, during a spell of good conditions on December 18, signals from the Burnley repeater, GB3RF, also on R7, were received by **Don Campbell** G5SD, in Clymping, on the Sussex coast. A mild tropospheric opening occurred on January 6 when the atmospheric pressure, which had reached 30.4in, began to fall. Throughout the day, I received strong signals from more than a dozen Continental f.m. stations in Band II and during the evening, Ian Rennison received a strong picture from the French TV station at Lille.

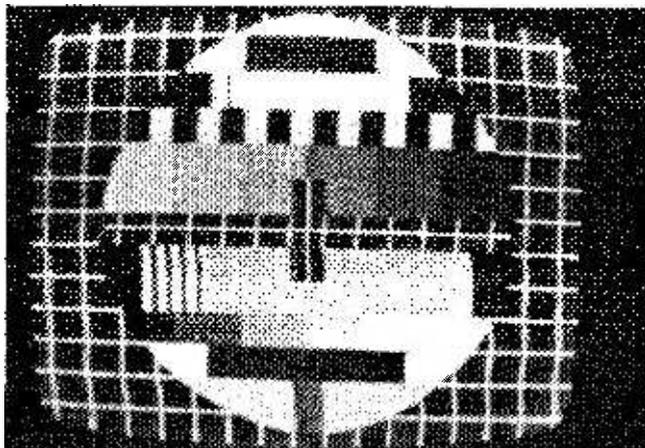


Fig. 1: Test card from Poland on 49.75MHz, received in Sussex on 20 December 1978

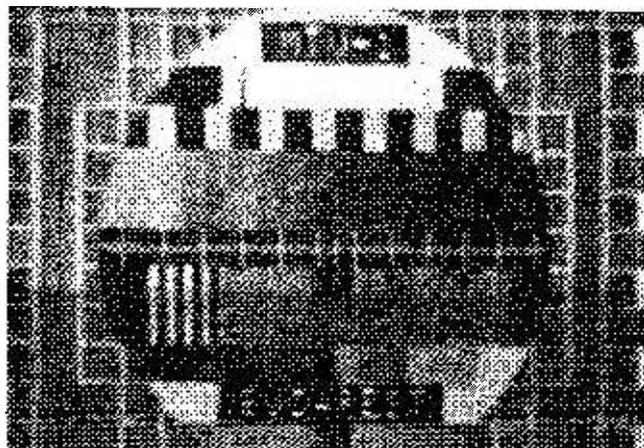


Fig. 2: Test card from Hungarian Television on 49.75MHz, received in Sussex on January 4

Around 1300, while I was receiving strong pictures from the IBA transmitter at Lichfield, Ch. 8, 189MHz, Alan Baker worked F1BBQ on 2m c.w. and later had QSOs through the French repeater, FZ2THF, on R9. During another pressure drop, at 2030 on the 3rd, **Fleming Jul-Christensen** G8RMA (ex OZ1EVA), Eastbourne, using a TS700-S, heard OE5KEJ on 2m s.s.b.

Microwaves

John Tye G4BYV, Dereham, Norfolk, is active on both 13 and 23cm with home-brew equipment into a 4ft dish aerial on both bands. During the second half of 1978 he had 10 QSOs with G stations, 11 with PA0 and 1 DK on 13cm, and 33 with G, 40 with PA0, 22 in Germany, 3 ON and 1 GW on 23cm which is a fine effort. John has now built a converter for 9cm and is waiting for the right conditions to use it.

Satellites

To celebrate the new year, John Branegan had Hogmanay QSOs with WB2OXJ and WB2SBW, both in New Jersey, just a few minutes before midnight on OSCAR-8J. All-told, John worked 16 stations in 8 countries, DB, G, GM, HB, I, PE, SM and W via 8J on New Year's Eve, and with only 4 days operating during December he had 60 QSOs on 8J, 7 of them transatlantic, including W2GEZ and WB2SBW which are new ones for him. John now has a QSL card confirming his 8J contact with C31QQ, Andorra and has now worked CN8AK, Morocco on OSCAR-8A.

Tail-piece

Congratulations to **Ern Hoare** G8BDJ, Brighton and **Alec Painter** G8EAQ, Worthing, on passing their Morse tests. They will, no doubt, soon be sporting their new call-signs.

I received a Christmas card from **Frank Luman** who, while on holiday with his parents in Denver, Colorado, is studying the DX-TV situation over there.

While on a round trip to Birmingham on January 10, Alan Baker worked through eight of the 2m repeaters, GB3BC, BM, LO, MH, PI, SN, SR, and WH, showing that mobile operators need never be alone on their journeys through and around the UK.

What do the VHF's have to offer?

Part 3

No one should harbour the idea that the v.h.f. bands have little excitement to offer the radio enthusiast. In fact, there is still so much to learn about the behaviour of radio waves between 1 and 10 metres that they are a haven for the DX hunter, experimenter and home constructor. To be successful in the world of v.h.f., one must pay great attention to detail, such as taking extra care when selecting components, keeping wiring as short as possible, soldering all joints, and making sure that aerials are securely mounted, and have a good-quality feeder. Remember, it is easy to ruin the performance of an expensive piece of v.h.f. gear with a poor aerial, badly-connected mains lead, loose loudspeaker, and microphone connections or an intermittent aerial plug.

Practical Wireless, April 1979

The Home Station

Before equipping a v.h.f. station, the operator, whether a licensed amateur, broadcast or short-wave listener, radio-astronomer, satellite enthusiast or TV DXer, must decide first where to locate his shack and then where to put his aerials. These, ideally, should be as close to the shack as possible to avoid unnecessarily long and therefore lossy feeders. The choice and size of aerial depends upon the band being used and the space available, in some cases the consent of the local planning authority is required, it is best to play safe and get this point clarified.

The Transmitting Amateur

The holder of a class B transmitting licence (G8-plus-3-letter callsign) may only use the 2m band within the v.h.f. spectrum, whereas the holders of a "full" licence (those who have passed the Morse test in addition to the RAE) may also use the 4m band. A typical aerial installation for the DX hunter is an 8-element Yagi for 2m and a 3-element Yagi for 4m, both horizontally polarised and mounted on an aerial rotator. The majority of amateurs are in favour of the VHF Band Plan, published by the RSGB, which recommends that c.w. contacts are made between 70.025 and 70.150MHz and 144.00 and 144.150MHz, and s.s.b. contacts on 70.200MHz and between 144.150 and 144.500MHz.

Operators soon learn the possible range of QSOs on each band from their location, under normal atmospheric conditions, but the real DX comes during the sporadic-E season on 4m and a tropospheric opening or aurora on 2m. Apart from the sheer thrill of working v.h.f. stations at almost impossible distances, it is advisable to exchange QSL cards to confirm contacts, because these cards are the evidence required by RSGB members who wish to claim the "Four Metres and Down" certificates offered by the Society for confirmed QSOs from: 3 Countries and 20 Counties on 4m; 5 Countries and 30 Counties on 2m. Senior awards are also offered.

Under abnormal conditions it is possible to work DX through the national and European 2m repeater network; these signals are frequency modulated and vertically polarised, so aerials such as dipoles, ground planes or crossed Yagis are normally used. Repeater contacts do not qualify for the RSGB certificates.

The Broadcast Listener

The v.h.f. hunting ground for the broadcast listener is the f.m. broadcast band, 88-108MHz, which is full of Continental broadcast stations during a tropospheric opening. East-European broadcast stations are often heard in the UK between 65 and 73MHz during the sporadic-E season. Many of my readers use a rotatable, multi-element Yagi for the broadcast DX in Band II, especially if they wish to resolve full stereo from the incoming signal.

The VHF Listener

The v.h.f. listener should make sure that his aerials are as efficient as those used by the transmitting amateurs. Listening on v.h.f. is very rewarding, especially during an atmospheric disturbance, when there is a host of DX signals about and a great opportunity to get a QSL card, from stations in rare Counties, which cannot be heard under normal conditions. To earn a QSL card, from either an amateur or a beacon keeper, the listener's report must be useful and contain such information as date, time, signal

AUDIO MODULES

1 Stereo Cassette Deck N999

Complete with electronics uses:— music centres, disco consols, tape editing etc. Freq resp 63Hz-10kHz WOW: 0.15% FLUTTER 0.18% channel: separation 55dB. Electronic speed control. ALC Mic and line inputs. JAPANESE Manufacture — requires 12V DC. **£23.95**. Top moulding **£1.00**.



2 Preamp Amp — PSU Wimborne 11W per channel

Four Rotary controls. Vol Bass Treb Bal. 2xPSUs for RF Board — cassette deck, LM 387 preamp IC driver. TIP 31+TIP 32 Output Pairs. Special price includes transformer **£16.95** (October 1978 PW)



3 AMP 041

8 watt RMS per channel amp+preamp supplied with pots. Fully complementary requires 28V DC. Price complete **£6.99**



4 AMP 020

Stereo power amp 30W RMS per channel. Class ABI TIP 34AxTIP 33A. 16 Transistor circuit Fre resp 15Hz-18kHz — 1dB. **£7.99**



5 Matching HiFi Preamplifier


Four rotary controls — Vol, Bal, Treb, Bass. Treble + or — 14dB. Bass + or — 14dB facility for loudness control **£6.99**



RF MODULES

6 Surplus RF Board 020

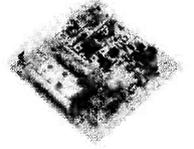Complete MW/LW/FM/MPX Tuner uses 3 stage FET front end 2 ceramic filters 3089E — 1310 Decoder. AM section built around 3132E. 2 stage tuning comes complete with 4 way switch — ferrite rod aerial — **£9.99**



7 RF 030

Improved version of above extra gain stage imposed S/N ratio and 1.5uV sensitivity for 26dB S/N way selector switch AFC stereo/mono switching — 2 additional inputs **£19.95**

8 RF 020

MW/LW/FM/MPX varicap tuned RF board as per 78 Nov/Dec PW Dual gate MOSFET front end. 2x1Fgain stages 3189 Deviation mute, interstation mute, MPX filters. STab PSU 1uV sensitivity and 75dB S/N ratio. AM Section also varicap tuned HA1197 excellent performance. Special price **£28.95**

9 VT04

FM FET Front end three stage tuning 26dB gain AFC and AGC facility 10.7MHz IF output **£3.99**

10 IF15

Matching IF Strip double conversion 10.7MHz/470kHz AM/NB FM excellent performance **£12.95**

We have all parts in stock for the Wimborne Music Centre — parts for amps/tuner amps and music centres up to 25 Watts per channel. We stock all hardware and trim to give units a professional finish. Front panels, meters, knobs, sockets, etc.

All prices include VAT paid P £1 per item. Max £2 for combined order. All models supplied with full data. **3 YEAR GUARANTEE** 7 day delivery. **E.S.E., RAILWAY HOUSE, HARDHAM CROSSING, PULBOROUGH, SUSSEX.**

CHROMASONIC electronics

your soundest connection in the world of components

Dept PW1, 56 FORTIS GREEN ROAD, MUSWELL HILL, LONDON, N10 3HN

TELEPHONE: 01-883 3705

The items shown in this advert are just a small selection taken from our new 78/79 Catalogue which is now available. It contains everything from Resistors to the latest in Micro-processors. Don't delay order your copy today. The price is only 40p (inc. 45p vouchers).

Low Power Schottky and TTL

CMOS

I.C. sockets

BITS and PIECES


Regulators

Linear I.C.'s

Low Power Schottky and TTL				CMOS				I.C. sockets				BITS and PIECES				Regulators				Linear I.C.'s			
N	LS	N	LS	N	LS	N	LS	N	LS	N	LS	N	LS	N	LS	N	LS	N	LS	N	LS	N	LS
7400.13*	19*	7449	87*	74136	39*	74191	1.21*	4000	15*	4053	81*	DIL (Texas)	Static RAM's	1+	17-63 64+	78M Series		CA3080	75				
7401.13*	19*	7450	16*	74138	55*	74192	1.21*	4001	16*	4054	1.29*	8 pin .10"	2102A (350ns)	1.05*	95*	88*	+(POS) 500mA	CA3130E	90*				
7402.15*	19*	7451	18*	74139	55*	74193	1.21*	4002	18*	4056	1.46*	14 pin .12"	2102A 2 (650ns)	1.29*	1.15*	1.08*	5v. 8v. 8v. 12v. 15v.	CA3140E	37				
7403.15*	19*	7453	16*	74141	76*	74194	1.21*	4006	92*	4059	5.18*	16 pin .13"	2111A-1 (500ns)	2.46*	2.19*	2.05*	20v & 24v.	LM301AN	30				
7404.16*	21*	7454	—	74145	75*	74195	1.01*	4007	18*	4060	1.24*	18 pin .18"	2112A-2 (250ns)	2.14*	1.90*	1.78*	All 60p* each	LM324N	73*				
7405.16*	21*	7455	—	74147	1.59*	74196	1.18*	4008	92*	4066	4.8*	20 pin .20"	21102 (350ns)	1.07*	96*	86*	79M Series	LM348N	97				
7406.26*	—	7460	16*	74148	1.32*	74197	1.18*	4009	54*	4068	2.1*	22 pin .24"	MM5257 (TMS4044)	8.10*	7.19*	6.75*	—(NEG) 500mA	LM382N	99				
7407.26*	—	7470	27*	74150	1.02*	74198	1.81*	4010	54*	4069	2.1*	24 pin .26"	2114 (450ns)	8.10*	7.19*	6.75*	5v. 8v. 8v. 12v. 15v.	LM381N	1.73				
7408.17*	19*	7472	23*	74151	87*	74199	1.81*	4011	18*	4070	2.1*	28 pin .30"	6810	3.50*	2.97*	2.52*	20v & 24v.	LM382N	1.33				
7409.17*	19*	7473	28*	74153	87*	74199	1.81*	4012	18*	4071	2.1*	40 pin .44"	CPU's				All 85p* each	LM3909N	85*				
7410.15*	19*	7474	28*	74154	1.21*	74200	—	4013	48*	4072	2.1*	8080	5.95*	Buffers			78 Series	SN7600N	102				
7411.25*	19*	7475	44*	74155	87*	74201	—	4014	92*	4077	2.1*	8 pin .23	9900	42.50*	8T26P	1.65*	+(POS) 1A	SN7600N	232				
7412.18*	19*	7476	30*	74156	87*	74202	—	4015	92*	4081	2.1*	14 pin .34"	E-Prom's UV		8T26P	1.65*	5v. 8v. 12v. 15v.	SN76013N	155				
7413.27*	40*	7478	—	74157	87*	74203	—	4016	43*	4082	2.1*	18 pin .37"	1702AQ	5.57*	8T96P	1.49*	18v & 24v.	SN76023N	155				
7414.71*	79*	7482	—	74158	58*	74204	—	4017	81*	4085	9.2*	18 pin .43"	2708D	7.87*	8T97P	1.49*	All 85p* each	T8A81DAS	90				
7415.1*	19*	7483	—	74160	1.21*	74205	—	4018	92*	4086	9.2*	20 pin .55"	TriState Buffers		8T97P	1.49*	79 Series	TC9A40	1.75				
7416.25*	—	7485	1.18*	74161	1.21*	74206	—	4019	56*	4099	1.81*	24 pin .60"	81LS95	.75*	8T98P	1.49*	—(NEG) 1A	ZN414	90				
7417.34*	—	7488	25*	74162	1.21*	74207	—	4020	92*	4502	9.2*	28 pin .60"	81LS95	.75*			5v. 8v. 12v. 15v.	ZN424E	1.35				
7420.16*	19*	7489	2.60*	74163	1.21*	74208	—	4021	92*	4508	2.46*	36 pin .95"	81LS98	.75*	Regulators		18v & 24v.	ZN425E	3.78*				
7421.1*	19*	7490	34*	74164	1.02*	74209	—	4022	92*	4510	1.07*	40 pin 1.05"	81LS98	.75*	78L Series		All 21.00* each	ZN459CT	3.54				
7422.1*	19*	7491	73*	74165	1.02*	74210	—	4023	18*	4511	95*		74365	.75*	µA723 (OIL)	40*	µA723 (OIL)	ZN1034E	2.03*				
7423.25*	—	7493	34*	74166	1.02*	74211	—	4024	65*	4514	2.70*		74366	.75*	L200	1.95*	L200	ZN1040E	8.43*				
7425.25*	—	7493	34*	74168	1.02*	74212	—	4025	18*	4515	2.70*		74367	.75*	LM304H	2.40*	LM304H	ZN116E	6.75*				
7426.25*	—	7495	54*	74169	1.02*	74213	—	4026	184*	4517	1.07*		74368	.75*	LM323K	6.25*	LM323K						
7427.39*	19*	7496	67*	74170	1.85*	74214	—	4027	51*	4518	1.07*				LM325N	2.60*	LM325N						
7428.38*	19*	74107	27*	74171	1.85*	74215	—	4028	70*	4519	1.07*				LM328N	2.60*	LM328N						
7430.16*	19*	74109	44*	74173	1.81*	74216	—	4029	118*	4519	95*				LM345K	8.10*	LM345K						
7432.25*	25*	74112	—	74174	1.01*	74217	—	4030	58*	4521	2.54*				LT29/30/31	85*	LT29/30/31						
7433.25*	19*	74113	—	74175	81*	74218	—	4032	1.08*	4522	1.89*												
7434.25*	19*	74114	—	74176	1.01*	74219	—	4034	1.88*	4526	1.89*												
7435.25*	25*	74114	—	74177	1.01*	74220	—	4035	1.06*	4529	9.2*												
7438.25*	25*	74121	27*	74180	1.01*	74221	—	4040	92*	4534	7.12*												
7440.17*	19*	74122	50*	74181	2.21*	74222	—	4042	70*	4536	3.74*												
7441.70*	—	74123	80*	74182	81*	74223	—	4043	81*	4537	4.53*												
7442.50*	55*	74124	—	74183	1.81*	74224	—	4046	1.06*	4543	1.62*												
7445.60*	—	74125	51*	74184	1.81*	74225	—	4048	43*	4553	4.53*												
7446.60*	—	74126	51*	74185	1.62*	74226	—	4049	43*	4568	1.51*												
7447.60*	87*	74132	72*	74188	2.97*	74227	—	4050	43*	4583	1.02*												
7448.60*	87*	74133	—	74189	3.17*	74228	—	4051	81*	4586	1.07*												
				74190	1.21*	74229	—	4052	81*	4586	1.07*												

VAT Inclusive prices *8% others 12.5% Export Customers deduct V.A.T. 2/27 from *1/9 from others. Postage and Packing 25p Trade and Export Inquiries most Welcome. Hours 9.00am-5.00pm.

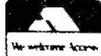Now available our ORDER-RING line, just phone your order through with your Access or Barclaycard number and providing the order is received by 3.00pm the components will be despatched the same day (min tel order £5.00)



strength, any interference, beam headings, and mention the call signs of other signals heard from the same area. Don't forget to enclose s.a.e.

Artificial Earth Satellites

A large cross-section of the v.h.f. fraternity are interested in receiving signals from both commercial and amateur radio satellites. A 10-element crossed Yagi with an alt/azm (altitude and azimuth) mount is ideal for listening to or working through the amateur satellites. Although this aerial is specifically designed for the 2m band it will suffice for receiving signals from the commercial birds in the 136/137MHz band. A permit from the Home Office is required to receive signals from commercial satellites. Both the AMSAT and Russian amateur radio satellites have uplink frequencies around 145.900MHz and downlinks around 28.400MHz. The latest information about these satellites can be obtained by listening to the AMSAT net at 1015 on Sunday on 3.780MHz.

Radio Astronomy

Briefly, a radiotelescope consists of a high-gain aerial directed toward the celestial source being observed, a sensitive receiver tuned to the observational frequency, and a recording instrument—usually a pen recorder. Radio waves from heavenly bodies are very similar to the background noise of a radio receiver, therefore the telescope must be able to distinguish between the two.

The usual practice is to connect a local noise source to the aerial socket and see how far it deflects the pen, then disconnect it, couple the aerial and measure the difference between the noise source and the incoming celestial waves. The sun, which affects our daily communications around the world, is a very powerful transmitter of radio waves when sunspots are present. For solar radio observers there is the day-to-day excitement of never knowing when this nuclear furnace, 93-million miles away, is going to send off a flare and emit radio waves between 100 and 200MHz. Radio astronomy presents a challenge to the home constructor who wishes to build v.h.f. aerials, low noise pre-amplifiers, converters and d.c. amplifiers to drive a pen recorder.

**PLEASE MENTION
PRACTICAL WIRELESS
WHEN REPLYING
TO ADVERTISEMENTS**

DX Television

It is well-known that the normal range of v.h.f. television signals is, subject to the terrain between the transmitter and receiver, about 50 miles. However, to receive signals at a greater distance, a large aerial system plus mast-head pre-amplifiers are required. Long-distance television reception is possible during an atmospheric disturbance which can affect both v.h.f. and u.h.f. signals over a wide area.

Within the UK, v.h.f. transmissions of the BBC are in Band I, 41–76MHz, and the IBA in Band III, 176–215MHz, both 405-line. Continental, African, Icelandic and Russian v.h.f. transmissions, which are the targets for the TV DXer, fall in two frequency ranges, 48–68MHz and 175–225MHz. The lower range is subject to sporadic-E and the higher range to tropospheric disturbances. Pictures from Russia can be received on Ch.R1, 49.75MHz and R2, 59.25MHz.

For super DX, which is not outside the bounds of possibility, there are American (525-line), Australian and New Zealand TV who also transmit between 46 and 68MHz. Detailed information about international television is published in *World Radio and TV Handbook*.



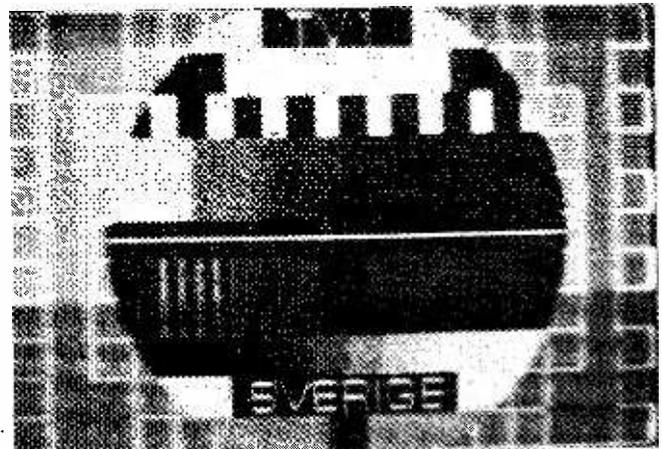


Fig. 3: Pictures from Spain and Sweden received by the author during the 1978 sporadic-E season with only a dipole aerial feeding a JVC 3060 receiver. Both stations can be received on Channels E2 (48.25MHz), E3 (55.25MHz), and E4 (62.25MHz). In each case the sound is 5.5MHz higher than the vision frequency

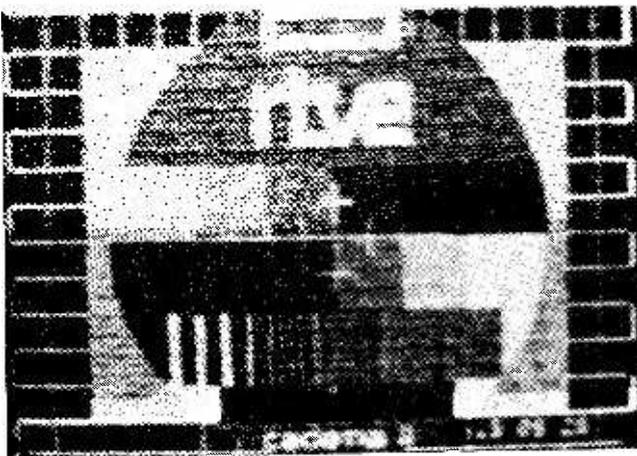

GUY STANBURY

by **RON HAM**

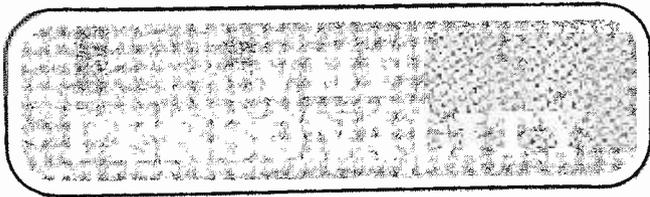


For Christmas, 1963, the 9-year-old Guy Stanbury received a Philips electronic kit. Soon after, he was borrowing copies of *Practical Wireless* from his local library, and in 1968 he became a regular reader.

Guy's interest in v.h.f. began in 1971, when he visited Bob Dewick, a keen Band II DXer at Bradwell-on-Sea, Essex, and saw Bob's Hacker receiver which could be fed from either a Rhombic aerial or four Jaybeam 4-element Yagis stacked vertically and horizontally. Very soon, Guy, at his home in Chelmsford, began experimenting with v.h.f. aerials, starting with an Antiference 4E, mounted on a cable-controlled rotating spindle, then a 6-over-6 array on a rotator followed by various long Yagis. His current installation is two Fuba UKa Stereo 8 aerials, stacked and phased according to the instructions and mounted on a Stolle rotator.

His receivers progressed from a Rigonda "Symphony" stereogram, to a PW "Sandown", which he constructed in 1975, and used for about a year until he purchased his present equipment, a tuner and i.f. modules from Ambit International. In his station, Guy has both reel-to-reel and cassette recording facilities, a frequency counter which he is trying out, an oscilloscope, and all the tools needed by the home constructor. Although he is a Band II specialist, with signals heard from stations in Greece, Italy, the low countries, Western Germany and Yugoslavia, via sporadic-E and tropospheric propagation, Guy plans to expand into the field of u.h.f. DX-TV, using a Wolseley Colour King or Colour Prince aerial.

Guy is currently on an HNC course in Electrical and Electronic Engineering, and enjoys corresponding with his fellow Band II enthusiasts, and his many friends in the world of v.h.f. radio.

So You Want to Pass the RAE ?

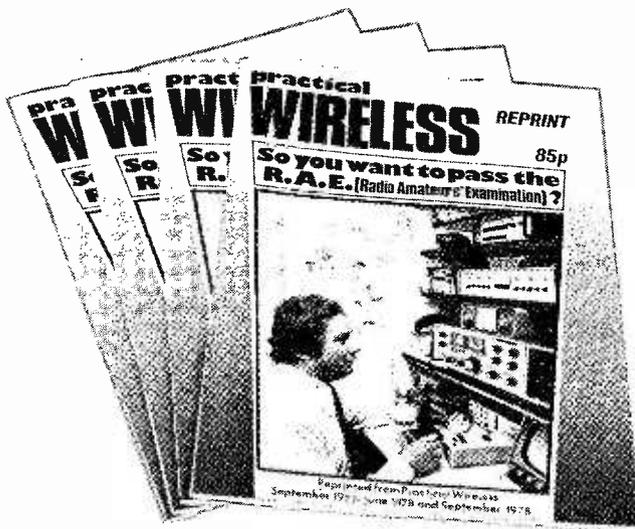

A reprint of the complete series, including details of the new examination format being introduced in 1979, is now available. The reprint costs 85p, including postage and packing to addresses within the United Kingdom.

Order your copy by completing and returning the coupon, together with your remittance, to IPC Magazines Ltd., Post Sales Department, Lavington House, 25 Lavington Street, London SE1 0PF. Please ensure that your name and address are clearly legible.

PRACTICAL WIRELESS—Radio Amateur Examination Reprint

Please send your order and remittance to:

IPC Magazines Ltd., Post Sales Department, Lavington House, 25 Lavington Street, London SE1 0PF

Please send me . . . copies at 85p each to include postage and packing

I enclose P.O./Cheque No. Value

Remittance must be crossed postal order or cheque (name and address on back please) and made payable to IPC MAGAZINES LTD

NAME
(BLOCK LETTERS)

ADDRESS
(BLOCK LETTERS)


.
.

. Post Code

Remittances with overseas orders must be sufficient to cover despatch by sea or air mail as required. Payable by International Money Order only

Company registered in England. Regd. No. 53626
A subsidiary of Reed International Limited

Cut round dotted line
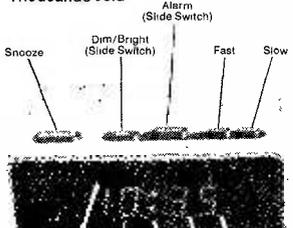
<p>HANIMEX Electronic LED Alarm Clock</p> <p>Same as ETI offer Thousands sold</p>  <p>Snooze Dim/Bright (Side Switch) Alarm (Slide Switch) Fast Slow</p> <p>p.m. Indicator Hour Display Colon Alarm On Indicator</p> <p>Time Set Lock Switch Minute Display</p> <p>Feature and Specification</p> <ul style="list-style-type: none"> ★ Hour/minute display ★ Large LED display with p.m. and alarm on indicator ★ 24 Hours alarm with on/off control ★ Display flashing for power loss indication ★ Repeatable 9-minute snooze ★ Display bright/dim modes control <p>Size 5.15 x 3.93 x 2.36 (131mm x 100mm x 60mm). Weight 1.43 lbs (0.65 kg).</p> <p>Guaranteed same day despatch</p> <p>£8.65</p>	<p>LADIES LCD</p> <p>Only 25 x 20 mm and 6 mm thick. 5 function: hours, mins, secs, day, date, + back light and auto cal. Elegant metal bracelet in silver or gold. State preference.</p>  <p>£10.95</p> <p>Guaranteed same day despatch</p>	<p>5 FUNCTION LCD</p> <p>Hours, mins, secs, month, date, auto calendar, back-light, quality metal bracelet.</p>  <p>£7.65</p> <p>Guaranteed same day despatch</p> <p>Very slim, only 6mm thick.</p>	<p>THOUSANDS SOLD 11 FUNCTION SLIM CHRONO 6 digit 11 functions</p> <ul style="list-style-type: none"> * Hours, mins, secs. * Day, date, day of week. * 1/100, 1/10, secs 10 x secs, mins. * Split and lap modes. * Back light, auto calendar. * Only 8 mm thick. <p>This same watch is being sold for £22.00 in newspaper and magazine special offer ads.</p>  <p>Metac Price £12.65 Guaranteed same day despatch</p>
<p>All products carry full 12 months guarantee. Please add 30p p&p with all orders. All prices include VAT.</p> <p>Shops open 9.30 to 6.00 daily.</p> <p>Trade enquiries welcome. Delivery: One week. Except where same day delivery is stated.</p>	<p>ALARM CHRONOGRAPH WITH DUAL TIME ZONE FACILITY</p> <ul style="list-style-type: none"> • Constant LCD display of hours and minutes, plus optional seconds or date display, plus day of the week and am/pm indication. • Perpetual calendar, day, date, month and year. • 24 hour alarm with on/off indication. • 1/10 second chronograph measuring net, lap and first and second place times. • Dual time zone facility. Night light.  <p>£29.95</p>	<p>PLEASE NOTE</p> <p>All our products carry full money back 10-day reassurance. Watches are despatched by FIRST-CLASS POST. They are fitted with new batteries, and include guarantee and instructions.</p> <p>Battery fitting service is available at our shops for no extra charge. We stock most watch batteries and this service is available to all. Metac have been selling electronic watches probably longer than anyone else in the UK. We take care of your watch not just this year but next year and the years after that.</p>	<p>Telephone Special 24-hour phone service Credit-card customers are welcome to buy by phone - simply phone 01-723 4753 with your credit-card number to place your order.</p> <p>METAC Electronics & Time Centre</p> <p>67 HIGH STREET DAVENTRY, NORTHANTS Tel. (032 72) 76545</p> <p>327 EDGWARE ROAD LONDON W2 Tel. (01) 723 4753</p> <p>Barclay & Access welcome Phone or Send Card Number with order</p>  

You know it's easy with Heathkit.

Electronics Courses

New series of courses on car electrical systems.
New series of courses on electronic equipment.
DC electronics.
AC electronics.
Semi-conductors.
Electronic circuits.
Digital techniques.
Microprocessors.

New Kits

Line printer.
Dual floppy disc.
Dual trace 5MHz and 35MHz oscilloscopes.
Memory expansion for digital trainer.
2M hand-held transceiver.

Heathkit self-instruction electronics courses are complete, low-cost learning systems. All you need is the will to learn and the Heathkit courses will teach you at your own pace.

It's easy because the courses are based on step-by-step programmed instructions, with audio records (or optional cassettes), self evaluation quizzes to test your understanding, and interesting experiments that encourage you to learn the easy "hands-on" way with the optional Heathkit experimenter-trainers.

Thousands of people just like you have already learnt electronics the easy Heathkit way - at home, in educational establishments and in industry throughout the world.

You'll find it easy too. Full details are in the Heathkit catalogue, together with hundreds of kits you can build yourself; for the home, car and workshop.

Send for your copy now.



To Heath (Gloucester) Limited, Dept PW 4/79, Bristol Road, Gloucester GL2 6EE. Please send the items I have ticked.
 Heathkit catalogue (enclose 20p in stamps). Computer brochure (enclose 20p in stamps).

Name _____

Address _____

NB. If you are already on the Heathkit mailing list then you will automatically receive a copy of the latest Heathkit catalogue without having to use this coupon. Registered in England, number 606177.



There are Heathkit Electronics Centres at 233 Tottenham Court Road, London (01-636 7349) and at Bristol Road, Gloucester. (Gloucester 29451).

OSTS

Since AMBIT introduced the "One Stop Technology Shop" to our service, we have been pleased to see just how many users of electronic components appreciate our guarantee to supply goods only from BS9000 approved sources. More than ever, professional and amateur electronics engineers cannot afford to waste time on anything less than perfect pedigree products.

SEE THE AMBIT AD TOO!

CD4000 CMOS

4000	17p	4059	563p	4522	149p
4001	17p	4060	115p	4527	157p
4002	17p	4063	109p	4528	102p
4006	109p	4066	53p	4529	141p
4007	18p	4067	40p	4530	90p
4008	80p	4068	25p	4531	141p
4009	58p	4069	20p	4532	125p
4010	58p	4070	20p	4534	614p
4011	17p	4071	20p	4536	380p
4012	17p	4072	20p	4538	150p
4013	55p	4073	20p	4539	110p
4016	52p	4075	20p	4541	141p
4017	80p	4076	90p	4543	174p
4018	80p	4077	20p	4549	399p
4019	60p	4078	20p	4553	440p
4020	93p	4081	70p	4554	153p
4021	82p	4082	20p	4556	71p
4022	90p	4085	82p	4557	388p
4023	17p	4086	82p	4558	117p
4024	76p	4089	150p	4559	388p
4025	17p	4093	50p	4560	218p
4026	180p	4094	190p	4561	65p
4027	55p	4096	105p	4562	530p
4028	72p	4097	372p	4566	159p
4029	100p	4098	110p	4568	281p
4030	58p	4099	122p	4569	305p
4031	250p	4160	90p	4572	25p
4032	100p	4161	90p	4580	600p
4033	145p	4162	90p	4581	319p
4034	200p	4163	90p	4582	164p
4035	120p	4174	104p	4583	84p
4036	250p	4175	95p	4584	63p
4037	100p	4194	90p	4585	100p
4038	105p	4501	75p		
4039	250p	4502	91p		
4040	83p	4503	69p		
4041	90p	4506	51p		
4042	85p	4507	55p		
4043	85p	4508	248p		
4044	80p	4510	99p		
4045	150p	4511	149p		
4046	130p	4512	98p		
4047	99p	4513	206p		
4048	60p	4514	260p		
4049	55p	4515	300p		
4050	55p	4516	125p		
4051	65p	4517	382p		
4052	65p	4518	103p		
4053	65p	4519	57p		
4054	120p	4520	109p		
4055	130p	4521	236p		

Micromarket

PRICES SLASHED

8800 series	8216	1.95	2114	£10
6800P	8224	3.50	2708	£10.55
6820P	8228	4.75		
6850P	8251	6.25		
6810P	8255	5.40		
6852				
MEMORIES				
2102	£1.70			
2112	£3.40			
2513	£7.54			
4027	£5.78			

TTL: Standard AND LP Schottky

N'	LSN'	N'	LSN'	N'	LSN'	N'	LSN'	LSN'				
7400	13	20	7455	35	24	74126	57	44	74185	134	74377	124
7401	13	20	7460	17		74128	74		74188	275	74378	93
7402	14	20	7463			74132	73	78	74190	115	74379	130
7403	14	20	7470	28		74133		29	74191		74386	37
7404	14	24	7472	28		74136		40	74192	105	74390	140
7405	18	26	7473	32		74138		60	74193	105	74395	139
7406	38		7474	27	38	74139		60	74194	105	74396	133
7407	38		7475	38	40	74141	56		74195	95	74398	180
7408	17	24	7476	37		74142	265		74196	99	74399	150
7409	17	24	7478			74143	312		74197	85	74445	92
7410	15	24	7480	48		74144	312		74198	150	74447	90
7411	20	24	7481	86		74145	65		74199	160	74490	140
7412	17	24	7482	69		74147	175		74248		74668	110
7413	30	52	7483A			74148	109		74249	93	74670	249
7414	51	130	7484	97		74150	99		74251	90	MISCELLANY	
7415	24	24	7485	104	99	74151	64	84	74253	105	NE555	30p
7416	30		7486		40	74153	64	54	74257	108	NE556	78p
7417	30		7489	205		74154	96		74258	153	NE558	180p
7420	16	24	7490	33	90	74155	54	110	74259	40	ICM7217	950p
7421	29	24	7491	76	110	74156	80	110	74260	153	ICM7208	1495p
7422	24	24	7492	38	78	74157	67	60	74261	353	LCD7106CP	-
7423	27		7493	32	99	74158			74266	40	LCD7106C	-
7425	27		7494	78		74159	210		74273	124	LCD DVM IC	955p
7426	36	27	7495A	65	99	74160	82	130	74275	312	LCD DVM KIT	2480p
7427	27	29	7496	58	120	74161	92	78	74279	52	3 1/2 digit LCD	1150p
7428	35	32	7497	185		74162	92	78	74283	120	ICL7107 LED	95
7430	17	24	74100	119		74163	92	78	74290	90	DVM kit 2065P	150p
7432	25	24	74104	63		74164	104		74293	95	ICM7216 - 8 digit timer	£19.82
7433	40	32	74105	62		74165	105		74295	120	(for LED C.cath)	247
7437	40	24	74107	32	38	74166			74298	100	SCALAR ICs	
7438	33	24	74109	63	38	74167	20		74324	157	8629 150MHz divide by 100	420p
7440	17	24	74110	54		74168			74325	242	95H90DC 780p	49
7441	74		74111	68		74169		200	74326	242	11C90DC 1400p	49
7442	70	99	74112	88		74170	230	200	74327	237	8618 - new/divide by 100 or 10 for 120/60MHz	77
7443	115		74113		38	74172	625		74352	100		60
7444	112		74114		38	74173	170	120	74353	100		
7445	94		74116	198		74174	87		74362	715		
7446	94		74118	83		74175	97	110	74365	49		
7447	82		74119	75		74176	75		74366	49		
7448	56	99	74120	115		74177	78		74367	49		
7449	56	99	74121	25		74180	85		74368	49		
7450	17		74122	46		74181	165	350	74373	77		
7451	17	24	74123	48		74182	160		74374	77		
7453	17		74124			74183	60	210	74375	60		
7454	17	24	74125	38	44	74184	135					

Voltage Regs

NEW LOW PRICES

7800 series UC TO220 package 1A all 95p
 7900 series UC TO220 package 1A all £1
 78MUC series TO220 package 1/2A all 90p
 78LCP series TO92 100mA all 35p

L200 up to 3A/adjustable V&A 195p
 78MGT2C 1/2amp adjustable volts 175p
 79MGT2C 1/2amp adjustable volts 175p
 723C precision controller 65p

MAINS FILTERS FOR NOISE/RFI etc
 1 amp in 1EC connector £4.83
 5 amp in 'wire in' case £3.87
 NE550A 73p

LINEARS non-consumer

BIMOS

CA3130E	84p	LM339N	66p
CA3130T	90p	LM348N	186p
CA3140E	35p	LM3900N	60p
CA3140T	72p	709HC to5	64p
CA3160E	90p	709PC di1	36p
CA3160T	99p	710HC to5	65p
		710PC di1	59p
Op amps		723CN	65p
LM301AH	67p	741CH to5	66p
LM301AN	30p	741CN 8di1	27p
LM308H	121p	747CN	70p
LM308N	97p	748CN	70p
LM318H	279p	NE531T	120p
LM318N	224p	NE531N	105p

OPTO 7 seg displays

0.43" High Efficiency HP:

5082-7650 red CA } 233p
 5082-7653 red CC
 5082-7660 yellow CA
 5082-7663 yellow CC
 5082-7670 green CA
 5082-7673 green CC

0.3" Standard HP

5082-7730 red CA } 147p
 5082-7740 red CC

0.5" Fairchild

FND500 red CC } 150p
 FND507 red CA } 150p

The ICL7216BPI is still the cheapest way to make a full 8 digit/ 10MHz frequency counter/timer, and with 10 external components + display - it is also one of the simplest. For £19.82, it takes a lot of beating. The mains filters have been extended now to include a 6amp IEC version at £5.10, and with the amount of electronic noise on the average supply (next door's fridge, for instance) it is a really worthwhile addition to any sensitive equipment. LPSN TTL now includes many more of latest types, all - of course - are absolutely prime first quality types. And don't forget our range of OPTO displays includes Hewlett Package high efficiency 0.43" types in all colours - renowned as the finest quality in the market. For other types of component - discrete LEDs, radio and audio devices, tuner modules, kits etc., see our other advertisement for more details - or send for the AMBIT catalogue system. Part one (45p) includes details of our background 'standard' items, and the new part two includes all the latest introductions and developments, plus a rundown on OSTs.

MAIL ORDER DEPT.

CRESCENT RADIO LTD

I ST. MICHAELS TERRACE, WOOD GREEN, LONDON N22 4SJ. 01-888 3206

"FLIP" PUSH BUTTON HEADS OR TAILS
 Complete kit and full instructions supplied. A pocket game, easy to build and great to play. KIT PRICE = £5-25 + 8% VAT. Post free.

75 OHM 2 1/2" (57mm) LOUDSPEAKER BARGAIN
 This ever popular many project loudspeaker. Only while stocks last. 65p + 12 1/2% VAT.

REAR SHELF CAR SPEAKERS
 5W 8 ohm good quality car stereo loudspeakers. Still only £3-75 + 12 1/2% per pair.

HEAVY DUTY XOVER 2 WAY 8 OHM
 A 2 way 8 ohm H/D Xover suitable for L/S systems up to 100 watt. Fitted with screw terminals for input and a three position 'HF LEVEL' switch which selects either Flat, -3dB or -6dB. ONLY £3-00 + 8% VAT

A CRESCENT 'SUPERBUY' Goodmans 5" 8 ohm long throw H/D loudspeaker. Mounting plate is integral with L/S chassis and has fixing holes with centres spaced at 5 1/4" (diagonally). ONLY £5-00 + 12 1/2% VAT

CR. 3000. SCREWDRIVER SET £1.75p + 8% VAT
 in neat plastic case. Consists of: awl, jewellers screwdriver, watchmaker's screwdriver, radio screwdriver, philips screwdriver. All fit into master swivelling handle.

CR. 4110. DESOLDERING PUMP ONLY 66 8% VAT
 High suction pump with automatic ejection. Knurled, anti corrosive casing. Teflon nozzle.

CR. LV1. 12v DRILL £12.00p. + 8% VAT
 BRITISH MADE 'Versadrill'. 12 volts DC. Compact battery operated power tool, sufficiently powerful to perform all the operations associated with 240v drills. Dimensions:- 150 x 50mm (dia.)

C.180-'KEYNECTOR' MAINS CONNECTOR
 Essential equipment for the showroom, workshop, factory, laboratory, home and hobby bench, the 'Keynector' provides quick, efficient and safe temporary mains connection. £6-25 + 8% VAT

FOOTSWITCH C.338
 250v, 5 amp. Non-slip base. Lead with 2.5mm plug. Body dims- 88 x 66 x 25mm. £3-75 + 8% VAT

Buy it with Access

P & P. Orders up to £5, add 30p. Orders £5-£10, add 50p. All orders over £10 post free! Please add V.A.T. as shown. S.A.E. with all enquiries please.

BARCLAYCARD

Personal callers welcome at: 21 Green Lanes, Palmers Green N13. Also 13 South Mall, Edmonton Green, Edmonton.

FOR YOUR GUIDANCE

VALUE ADDED TAX

Unless otherwise shown, all prices in advertisements are inclusive of VAT. Where prices are exclusive, readers should ensure that they have added the correct amount of VAT before ordering.

Export orders are not subject to the addition of Value Added Tax.

QUALITY QUARTZ CRYSTALS QUICKLY

OUR RANGE

10kHz 50kHz 100kHz 500kHz 1MHz 100MHz 250MHz

PLEASE INDICATE CLEARLY THE FREQUENCY RANGE OF YOUR INTEREST
 SEND SAE FOR APPROPRIATE DATA SHEET

Webster Electronics

ILMINSTER, SOMERSET, ENGLAND
 TELEPHONE (04605) 4261/2
 TELEX 46264 FRQNCY G

ambit international [®]

The PW Sandbanks Metal Locator: a kit based on this recently published design for this uniquely effective type of metal locator is available for only £35.00 + 8% VAT. The kit closely resembles the appearance as published, except that a close fitting injection molded housing replaces the vacuum molded electronics box - to improve the environmental suitability of the construction. Carriage for complete kits £1.

The New Catalogue - "Tecknowledgey Part 2"

Part 2 of the catalogue: by the time this advert reaches the press, part 2 should be on sale. Sorry it's late, but it contains so many new and interesting things that we felt we had to hold up production to include them. Part three by the autumn - and already there are many new items to go in! Part one, 45p, part 2 50p. (inc PP etc).

Radio ICs

TDA1062	HF/VHF tunerhead	1.95
TDA1083	One chip AM/FM rx	1.95
TDA1090	One chip HiFi am/fm	3.35
TDA1220	One chip am/fm rx	1.75
HA1197W	HiFi AM tuner IC	1.40
CA3123E	AM tuner IC	1.40
TBA651	AM tuner IC	1.81
CA3089E	Famous FM IF system	1.94
CA3189E	As 3089+ deviation mute	
	AF preamp, adj, agc	2.75
	Improved S/N 3089	2.20
HA1137W	limiting amp+detector	0.75
TBA120S	high gain	1.00
MC1350P	agc'd IF preamp	1.20
MC1330P	synch AM/video detector	1.35
KB4406	Cascade IF preamp	0.65
uA753	limiting FM preamp	1.95

HA1137W	Improved S/N 3089	2.20
TBA120S	high gain	1.00
MC1350P	agc'd IF preamp	1.20
MC1330P	synch AM/video detector	1.35
KB4406	Cascade IF preamp	0.65
uA753	limiting FM preamp	1.95

Communications circuits

SD6000	DMOS RF/Mixer pair	3.75
KB4412	Bal mixers, IF-agc	2.55
KB4413	AM/SSB det. squelch, agc	2.75
KB4417	mic processor	2.55
MC3357	best thing in NBFM yet	3.12
MC1496P	popular double bal mixer	1.25

Multiple decoders + noise blanker

MC1310P	popular PLL decoder	2.20
uA758	buffered 1310	2.20
CA3090AQ	RCA PLL decoder	3.25
HA1196	improved PLL decoder with stereo preamps	3.95
HA11223	19kHz pilot cancel, low distortion, high S/N	4.35
KB4437	as HA11223 with remote VCO kill facility	4.55
KB4438	stereo MUTING preamp for post decoder mute	2.22
KB4423	impulse noise blanker	2.53

Discrete devices: more than ever:

BF960	800MHz/2.8dB nf mosfet	1.60*
BF961	200MHz/2.0dB nf	0.80*
40822	FM RF amp	0.43*
40823	FM mixer	0.51*
40673	Famous MOSFET	0.55*
2SJ49/2sK133	120v/100W MOSPOWER output devices	10.50*

LEDS:

	the best value today		
	3mm	5mm	2.5x5mm
Red	0.14	0.14	0.17
Green	0.18	0.16	0.20
Yellow	0.18	0.15	0.20
Orange	0.22	0.29	0.24

100 off mix, 25% discount. All are AEG first grade types, absolutely no junk. 5mm clips for panel mounting 0.03 each

Misc. ICs for radio/audio applications

UJ237B	5 LED bargraph driver	0.80*
SAS6610	4 station touch tune IC	1.48*
SAS6710	adds 4 stations to 6610	1.48
MSM5523/4	LW,MW,SW and FM digital frequency readout plus clock, timers, stopwatch	£14*
MSM5526	LW/MW/FM DFM with direct drive for LCD	£11*
TCA730	DC volume control	3.50
TCA740	DC tone control	3.50
TDA1028	DC input switch	3.50
TDA1029	DC mode switch	3.50

Radio and Tuner modules

We cannot really list all the details we would like to here - but with advent of the new mark 3 tuner system, the Dorchester and matching AF units, Ambit offers you the widest choice ever, plus hardware and styling that matches the very high standards we have set in this new range.

At last, DIY Hi Fi which looks as if it isn't.

That's not to say it doesn't look like HiFi - just that it doesn't look like the usual sort of thing you have come to associate with DIY HiFi. The Mk3 outstrips and outperforms all British made HiFi tuners, and most imported ones too. Certainly at the price, there isn't one near it. But more than that, it looks superb. A small pic here would be an insult, so send an SAE for details on the kit that looks as if isn't. It's something else.....


- ★ Exceptionally high performance - exceptionally straightforward assembly
- ★ Baseboard and plug-in construction. Future circuit developments will readily plug in, to keep the MkIII at the forefront of technical achievement
- ★ Various options and module line-ups possible to enable an installment approach to the system

and now previewing the matching 60W/channel VMOS amplifier:

- ★ Matching both the style and design concepts of the MkIII HiFi FM tuner
- ★ Hitachi VMOS power fets - characterized especially for HiFi applications
- ★ Power output readily multiplied by the addition of further MOSFETs
- ★ VU meters on the preamp - not simply dancing according to vol level
- ★ Backed with the usual Ambit expertise and technical capacity in audio

The PW Dorchester-LW,MW,SW,& FM stereo tuner

THE DIGITAL DORCHESTER ALL BAND TUNER

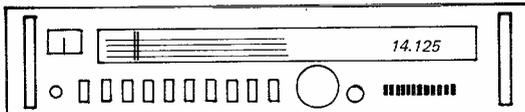

With styling and dimensions to fit in with the rest of AMBIT'S new range of tuner & audio equipment.

When the new range of OKI digital frequency display ICs was announced, the original prototype of the Dorchester had been made - but since so many of you wanted to use the OKI frequency counterdisplay system with the Dorchester, we quickly designed a unit to incorporate the necessary facilities. The Digital Dorchester is designed in 19 inch form, and forms a perfect match for the other units in the range. If you don't want to go to the expense of the full Ambit DFM1 module, with AM/FM/Time/Timers, then the MA1023 clock module can be used instead.

The Dorchester has been described in PW Dec., Jan. and Feb. issues - but for those of you who may have missed it - it is an All Band broadcast tuner, covering LW/MW/SW and FM stereo in 6 switched ranges. Construction is very straightforward, with all the switching being PCB mounted - and the revolutionary TDA1090 IC used for AM/FM.

The electronics for the radio section of the Dorchester remain unchanged at £33.00, with 12.5% VAT. The hardware package, of case, meter, PSU now costs £33.00 + 8% with the MA1023 available for an extra £5 only.

For the fully digital version, with Ambit DFM1, the price is £56.50 + 8% VAT.

2 Gresham Road, Brentwood, Essex.

NO DISCO SYSTEM IS COMPLETE WITHOUT...



CITRONIC MM 313 MIXER

Ideal for the DIY enthusiast building up a complete disco system. 4/6 ch mono. inc. LED indicators, connections via phono sockets at rear. Bargain price. including PSU
£80.46 inc. VAT (P.P. £1.50)

PIEZO HORNS

FANTASTIC SPECIAL OFFER TO READERS OF PRACTICAL WIRELESS
Tweeters for your disco, PA system or Hi-Fi. Frequency range 5K-20K. No X over required. They can be used in any PA system up to 100W. Why pay more?
OUR PRICE ONLY £4.99 each (P&P 35p each)



BULGIN OCTAL PLUGS AND SOCKETS

There's always hundreds of Bulgin Octal multiway plugs and sockets in stock at Roger Squire's. Each pin rated 6A. Perfect for your Sound to Light System. P552 SOCKET
£0.65 (P&P 35p) P551 PLUG £1.84 (P&P 35p)
Carriage on 10 or more nominal £1.00 Also available 6-way multicore cable (6 Amps per core) ex stock. £0.65 per metre. Please phone for carriage quote.



PROJECTORS

SQUIRE MULTIFLECT 150
- including rotator and effects wheel. A truly versatile projector which uses a powerful 150W Tungsten bulb, all effects attachments simply slot in ready for use
A BARGAIN AT £40.50 (P&P £1.00)



STARLITE 250

An exclusive new line to Roger Squire's Disco Centres. Superb high powered 250W quartz halogen bulb, fan cooled, accepts wide range of multiflect attachments. Unique connection slot for orbit prism revolvers. Only
£65.00 + VAT attachments extra

PLUS MANY DISCO ACCESSORIES


All Roger Squire's shops have a service department which carries large stocks of DISCO SPARES & ACCESSORIES.
For example: Fane and H. H. Disco Speakers 12" and 15" BSR and Garrard decks at discount prices.



Roger Squire's DISCO GEAR

Personal callers: ROGER SQUIRE'S DISCO CENTRES
LONDON: 175 Junction Road, Fulneck Park N19 5DQ 01-272 7474 Open from 10-5 Tues-Sat 10-8 Weds
BRISTOL: 125 Church Road, Redfield, Bristol BS5 9JR 0272-655050 Closed Mondays
MANCHESTER: 251 Deansgate M3 4EN 061-831 7676 Tel. 041 946 3303
GLASGOW: 1 Queen Margaret Rd., (off Queen Margaret Drive) Kelvinside, Glasgow G20 6DP

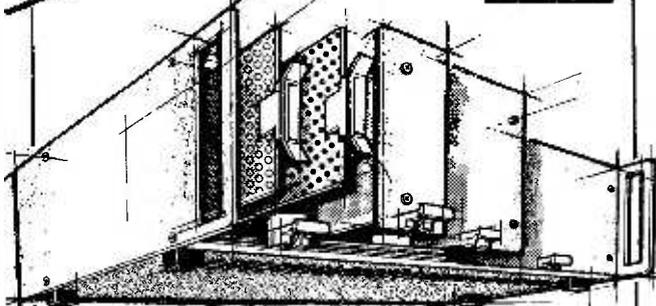OUR RANGE OF PRODUCTS ARE NOW INDIVIDUALLY AND ATTRACTIVELY PACKAGED



Our new catalogue lists a card frame system that's ideal for all your module projects - they used it on the ETI System 68 Computer. And we've got circuit boards, accessories, cases and boxes - everything you need to give your equipment the quality you demand. Send 25p to cover post and packing, and the catalogue's yours.

VERO ELECTRONICS LTD. RETAIL DEPT.
Industrial Estate, Chandlers Ford, Hants. SO5 3ZR
Telephone Chandlers Ford (04215) 2956



NOTICE TO READERS

When replying to Classified Advertisements please ensure:

- (A) That you have clearly stated your requirements.
- (B) That you have enclosed the right remittance.
- (C) That your name and address is written in block capitals, and
- (D) That your letter is correctly addressed to the advertiser.

This will assist advertisers in processing and despatching orders with the minimum of delay.

Receivers and Components

NOSTALGIA THE VINTAGE WIRELESS COMPANY COLLECTING

1920 to 1950

Receivers, valves, components, service data, historical research books, magazines, repairs and restorations. A complete service for the collector and enthusiast of vintage radio.

S.a.e. with enquiries and for monthly newsheet.

THE VINTAGE WIRELESS COMPANY, 64, Broad Street, Staple Hill, Bristol BS16 5NL. Tel. Bristol 565472.

BRAND NEW COMPONENTS BY RETURN

Electrolytic Capacitors 16V, 25V, 50V.
0.47, 1.0, 2.2, 4.7 & 10 mfd. — 5p.
22, 47 — 5½p. (50V—6p.), 100—7p. (50V—8p.).
220—8p. (50V—10p.), 470—11p. (50V—15p.).
1000/15V—15p. 1000/25V—18p. 1000/40V—35p.

Subminiature bead tantalum electrolytics.
0.1, 0.22, 0.47, 1.0 @ 35V, 4.7 @ 63V—8p.
2.2/35V & 4.7/25V—9p. 10/25V, 15/16V—12p.
22/16V, 33/10V, 47/6V, 68 & 100 @ 3V—14p.

Mullard Miniature Ceramic E12 Series 63V 2%.
10 pf. to 47 pf.—9p. 56 pf. to 330 pf.—4p.
8 Pin Dil. i.c.s. 741—18p. 555—24p.

Vertical Mounting Ceramic Plate Caps 50V.
E12 22 pf.—1000 pf. E6 1500 pf.—47000 pf.—2p.

Polystyrene E12 Series 63V. Hor. Mounting.
10 pf. to 1000 pf.—3p. 1200 pf. to 10000 pf.—4p.

Mullard Polyester 250V Vert. Mtg. E6 Series.
0.01 to 1—4p. 15, 22—5p. .33, 47—8p.
.68—11p. 1.0—14p. 1.5—20p. 2—24p.

Mylar (Polyester) Film 100V. Vertical Mtg.
0.01, .002, .005—3½p. .01, .02—4½p. .04, .05—5½p.

Miniature Film Resistors Highstab. E12 5%.
0-125 watt 10 Ω 2MΩ.....1p
0-250 watt 1 Ω to 10MΩ. (10% over 1M).....1p
0-500 watt 10 Ω to 2MΩ.....2p
1-1000 watt 10 Ω to 10MΩ.....2p

1N4148—2p, 1N4002—4p, 1N4006—6p, 1N4007—7p
BC107/8/9, BC147/8/9, BC157/8/9, BF194 & 7—9p.

20mm. fuses 15, .25, 5, 1.0, 2.0, 3.0 & 5A—3p.
Printed Circuit Holders for 20mm. fuses—5p.
Post 10p (Free over £4). Prices VAT inclusive.

THE C. R. SUPPLY CO.

127, Chesterfield Road, Sheffield S8 0RN

VALVES

Radio—T.V.—Industrial—Transmitting
Projector Lamps and Semiconductors

We Dispatch Valves to all parts of the world by return of post. Air or Sea mail, 4000 Types in stock, 1930 to 1976. Obsolete types a speciality. List 30p. Quotations S.A.E. Open to callers Monday to Saturday 9.30 to 5.00 closed Wednesday 1.00. We wish to purchase all types of new and boxed Valves, Projector Lamps and Semiconductors.

COX RADIO (SUSSEX) LTD.

Dept. P.W. The Parade, East Wittering,
Sussex PO20 8BN
West Wittering 2023 (STD Code 024366)

SMALL ADS

The prepaid rate for classified advertisements is 22 pence per word (minimum 12 words), box number 60p extra. Semi-display setting £7.50 per single column centimetre (minimum 2.5 cms). All cheques, postal orders etc., to be made payable to Practical Wireless and crossed "Lloyds Bank Ltd". Treasury notes should always be sent registered post. Advertisements, together with remittance, should be sent to the Classified Advertisement Manager, Practical Wireless, Room 2337, IPC Magazines Limited, King's Reach Tower, Stamford St., London, SE1 9LS. (Telephone 01-261 5846)

CONDITIONS OF ACCEPTANCE OF CLASSIFIED ADVERTISEMENTS

1. Advertisements are accepted subject to the conditions appearing on our current advertisement rate card and on the express understanding that the Advertiser warrants that the advertisement does not contravene any Act of Parliament nor is it an infringement of the British Code of Advertising Practice.
2. The publishers reserve the right to refuse or withdraw any advertisement.
3. Although every care is taken, the Publishers shall not be liable for clerical or printers' errors or their consequences.

RIBBON MICROPHONES with 4/8 Poleswitch 95p; Microswitches, Capacitors, Receiver and Microphone Capsules 10p each; Bakelite Telephones £2.95; Handsets 50p; Magneto Generators £1.75. P.&P. £1.50. **CONVERSATION PIECES**, 55 Swindon Road, Cheltenham. (35707).

D.V.M. THERMOMETER KIT

Based on the ICL7106 single chip DVM the kit contains a 3 digit LCD, a PCB, ICL7106, and all components and instructions to make a 0-200mV FSD DVM. Components also supplied to enable this to be converted to a digital thermometer. Requires a 2mA 9V supply (PP3 battery). ONLY £21.99

TOUCH CONTROLLED LIGHTING KITS

Directly replace conventional light switches and control up to 300W of lighting. No mains rewiring. Insulated touch plates. Easy to follow instructions.

NEW! TD300K—TOUCHDIMMER. Single touchplate with alternate action. Brief touch switches lamp on and off, longer touch dims or brightens lamp. Neon lamp helps find the switch in the dark. **£8.99**

—Extension kit for TD300K permits operation from another location, two-way switching, etc. **£1.50**

TSD300K—TOUCHSWITCH-DIMMER—One alternate ON/OFF action. TOUCHPLATE. Small knob for presetting lamp brightness. **£5.50**

TS300K—ON/OFF TOUCHSWITCH. Two touch plates. **£4.30**

TSAS300K—AUTOMATIC TOUCHSWITCH. Time delay variable 2 secs to 3½ mins. **£4.30**

LD300K—300W LIGHTDIMMER KIT **£2.90**

24 HR. CLOCK APPLIANCE TIMER KIT

Switches any appliance of up to 1KW on and off at preset times once a day. KIT contains: AY-5-1230 Clock/Appliance Timer; C.T. 0.5" LED display; mains supply, display drivers, switches, LEDs, triac, PCBs and full instructions. **£14.90**

White box 56 x 131 x 71mm with red Acrylic window **£2.20**
White box as above ready drilled for kit **£2.50**
Ready-built in box, incl. mains cable **£22.50**

400V PLASTIC TRIAC'S		OPTO COMPONENTS	
5A	58p	0.2" dia LEDs	355 28p (4 @ £1)
8A	74p	Red 12p (£1/10)	741 22p (5 @ £1)
13A	84p	Green Time 20p	LM3911
16A	108p	Yellow 25p	temperature control IC
20A	165p	DL727	£1.50
25A	190p	LCD 0.5"	£8-10
6" with trigger	80p	LDR sim	ICL7106
8A* isolated tab	80p	ORP12	50p
		Neon	8p
		TIC106D SCR	80p
		Diac	20p
		2N6027	35p
		AY-5-1230	£4.50

QUANTITY DISCOUNTS ON REQUEST
ADD 8% VAT + 25p P&P. Callers by appointment only.
Tel: 01-579 9794
T. K. ELECTRONICS
106 STUDLEY GRANGE ROAD, LONDON W7 2LX

TUNBRIDGE WELLS COMPONENTS, BALLARD'S,
108 Camden Road, Tunbridge Wells, Tel: 31803. No Lists. Enquiries S.A.E.

AM/CW/SSB COMMUNICATION RECEIVER

and prescaler modules. 453.5 KHz Mech. Filter Modules 2-1 kHz BW, with diode-switching.

CRYSTALS Brand new high precision HC33/U: 1.0, 2.0, 3.0, 1.008, 2.5625 MHz **£3.35**, 1.28 MHz **£4.15**, HC13 100 kHz **£3.25**, HC18/U: 4.0, 5.0, 6.0, 7.0, 8.0, 10.0, 10.7 MHz **£3.00**, 18.0, 20.0, 38.6667, 48.0, 100.0, 116.0 MHz **£3.50**, HC25/U 8.08333 MHz (S2.0) **£3.00**. Large stocks of standard freqs for MPU etc. Any freq made to order 6 weeks from **£3.75**.

WINKLE PICKERS. Winkle out DX from the QRM with pin-sharp 250 Hz 8-pole crystal CW filters specially manufactured to fit TR10 and YAESU: FT/FR-101, FT-301, TS-520, TS-820. **£25.90** each.
All prices inc. VAT and UK post. SAE Lists.
P. R. GOLLEDDGE ELECTRONICS
G3EDW, Merriott, Somerset, TA16 5NS
Tel: 0460 73718

Codespeed

ELECTRONIC MAIL ORDER

All full spec. devices

DIGITAL ALARM CLOCK MODULE Not a kit, but a factory built module complete with half inch LED display. All you need add to give a fully functional clock is a miniature transformer and time setting switches. Sleep, snooze and alarm output. With data only **£6.50**, Catalogue Number 205.

HEAT SINKS Two types available. Ex-equipment but in excellent condition. Most still contain a power transistor (condition unknown). Xmas tree type (62x66x35mm), Catalogue Number 705, 20p each. Rectangular type (130x63x32mm), Catalogue Number 706, 30p each. Due to the weight of these items, please ADD EXTRA 25p PER HEAT SINK for post and packing.

WRISTWATCH LIQUID CRYSTAL DISPLAY A high contrast 3-digit display, with 0.2" high digits. 0.0u. Catalogue Number 202.

CALCULATOR KEYBOARDS Two multi-function calculator keyboards. Excellent key action. Only **£1.00** the pair. Catalogue Number 101.

MEMORIES The famous 2102, A 1024 bit static RAM. Complete with data sheet, only **£1.25**. Catalogue Number 102.

CALCULATOR CHIP An MM5725 calculator chip and data book for only **£1.00**. Catalogue Number 103.

25 MINIATURE DIODES 25 miniature 1N3470 germanium diodes (600mA, 35V). All brand new. What a bargain (at just 2p each)! 11 25 diodes for **50p**. Catalogue Number 401.

P.U.T.s. Four MEU21 Programmable Unijunction Transistors (electrically similar to 2N6027). Lots of uses, long delay timers, oscillators, phase controllers and many more. With data and usage sheet. 4 for **50p**. Catalogue Number 402.

Untested Items

DEFECTIVE CALCULATORS A production line reject calculator with lots of accessible goodies inside. Detachable keyboard, display, case and PCB with approx. 25 transistors and 2 calculator chips. Not much wrong with some we tested. A bargain at only **£2.50**. Catalogue Number 104.

CALCULATOR TOPS (Untested—so no guarantees) The upper half of two hand held calculator cases with integral keyboard. Ex-equipment but believed to be o.k. Only **50p** the pair. Catalogue Number 105.

L.E.D. DISPLAYS (80% guaranteed good) Five, 7 segment L.E.D. displays. Common cathode with 0.127" high digits. 5 for **£1.00**. Catalogue Number 301.

Satisfaction guaranteed or return for replacement or refund.
For free catalogue send stamped addressed envelope.
Postage and Packing please add 25p (Overseas orders add 60p)

CODESPEED
P.O. Box 23, 34 Seafield Road,
Copnor, Portsmouth, Hants., PO3 5BJ

Equipment Wanted

Tempting prices paid for

Oscilloscopes • Signal Generators
DVM's • Small Computers
Receivers • Teletypes • VDU's etc.

Electronic Brokers Ltd
49/53 Pancras Road
London NW1 2QB
Telephone 01-837 7781

Service Sheets

REG. OFFICE 14B QUEENS PARADE, NORTH EALING W5 3HU

SERVICE SHEETS—COLOUR TV SERVICE MANUALS

Service Sheets for Mono TV, Radios, Record Players and Tape Recorders £1. Please send large Stamped Addressed Envelope.

We can supply manuals for most makes of Colour Television Receivers by return of post

**B.R.C. PYE ECKO PHILIPS ITT/KB SONY G.E.C. HITACHI BAIRD ULTRA INVICTA FERGUSON
H.M.V. MARCONI AND MANY MORE**

Let us quote you. Please send a Stamped Addressed Envelope for a prompt reply. Also comprehensive T.V. repair manuals by J. M. Court, S.A.E. for details. MAIL ONLY TO

G. T. TECHNICAL INFORMATION SERVICE
10 Dryden Chambers, 119 Oxford St., London W1R 1PA

SERVICE SHEETS for Radio, Television, Tape Recorders, Stereo, etc., with free fault-finding guide, from 50p and S.A.E. Catalogue 25p, and S.A.E. HAMILTON RADIO, 47 Bohemia Road, St. Leonards, Sussex.

LARGE SUPPLIER OF SERVICE SHEETS

and Colour Manuals. TV Mono Radios, Tuners, Tape Recorders, Record Players, Transistors, Stereograms, all at 75p each + S.A.E. except colour TV and Car Radios. State if Circuit will do, if sheets are not in stock. All TV Sheets are full lengths 24 x 12, not in Bits & Pieces. Free Fault Finding Chart or TV Catalogue with order.

C. CARANNA (Mail Order)
71, Beaufort Park, London, NW11 6BX
01-458 4882

BELL'S TELEVISION SERVICES for Service Sheets on Radio, TV etc., £1.00 plus SAE Colour TV Service Manuals on request, SAE with enquiries to B.T.S., 190 King's Road, Harrogate, N. Yorkshire. Tel: (0423) 55885.

SERVICE SHEETS, Radio, TV etc., 10,000 models. Catalogue 24p, plus S.A.E. with orders, enquiries, TELRAY, 154 Brook Street, Preston PR1 7HP.

Ladders

LADDERS varnished 22" extd. £30. Carriage £2.80. Leaflet. Also Alloy ext. up to 62ft. LADDER CENTRE (WLS3), Halesfield (1), Telford. Tel: 586644.

Educational

TELEVISION TRAINING

18 MONTHS full-time course for beginners to include all the undermentioned subjects. Short courses, combining one or more subjects, for applicants with suitable education and electronics background such as C & G, HND BSc etc.

- 13 WEEKS TECHNICAL MATHEMATICS & ENGLISH
- 13 WEEKS ELECTRONICS & RADIO
- 13 WEEKS MONOCROME TELEVISION
- 13 WEEKS COLOUR TELEVISION
- 13 WEEKS VIDEO SYSTEMS (CCTV, VCR, Teletext, etc.)

The training incorporates a high percentage of practical work.

Next session starts on April 23rd

(Also available 2½ year course in Marine Electronics & Radar for employment as ships Radio Officer)

Prospectus from:

LONDON ELECTRONICS COLLEGE

Dept. PW84, 20 Penywern Road,
London SW5 9SU. Tel. 01-373 8721

COLOUR TV SERVICING

Learn the techniques of servicing Colour TV sets through new homestudy course approved by leading manufacturers. Covers principles, practice and alignment with numerous illustrations and diagrams. Other courses for radio and audio servicing. Full details from:

ICS SCHOOL OF ELECTRONICS
Dept. F277 Intertext House, London SW8 4UJ
Tel. 01-622 9911 (all hours)
State if under 18

TECHNICAL TRAINING

Get the training you need to move up into a higher paid job. Take the first step now—write or phone ICS for details of ICS specialist homestudy courses on Radio, TV, Audio Eng. and Servicing, Electronics, Computers, also self-build radio kits. Full details from:

ICS SCHOOL OF ELECTRONICS
Dept. F277 Intertext House, London SW8 4UJ
Tel. 01-622 9911 (all hours)
State if under 18

CITY & GUILDS EXAMS

Study for success with ICS. An ICS homestudy course will ensure that you pass your C. & G. exams. Special courses for: Telecoms, Technicians, Electrical Installations, Radio, TV & Electronics Technicians, Radio Amateurs, Full details from:

ICS SCHOOL OF ELECTRONICS
Dept. F277 Intertext House, London SW8 4UJ
Tel. 01-622 9911 (all hours)
State if under 18

GO TO SEA as a Radio Officer. Write: Principal, Nautical College, Broadwater, Fleetwood, FY7 8JZ.

Record Accessories

STYLI for Hi-Fi. Music Centres. III. List free for S.A.E. also cartridges, leads, accessories. Details—FELSTEAD ELECTRONICS (PW), Longley Lane, Gatley, Cheadle, Ches. SK8 4EE.

For Sale

NEW BACK ISSUES of "PRACTICAL WIRELESS" available 70p each, post free. Open P.O. Cheque returned if not in stock—BELL'S TELEVISION SERVICE, 190 Kings Road, Harrogate, N. Yorks. Tel: (0423) 55885.

SEEN WHISTONS CAT? 5000 odds and ends. Mechanical/Electrical Cat Free. WHISTON, (Dept. PW), New Mills, Stockport.

TRIO R300 General Coverage Receiver as new £159 o.n.o. TRIO 2200G £114 o.n.o. 1-20 Watt 2M P.A. £34 o.n.o. 021-453-4748.

BACK ISSUES P.W. 1966-75, E.E.- 1976 + 77 50p each. Inclusive. Cheque/P.O. Returned if N/A. P. R. Sant, 10 Pevensey Close, Worcester.

Books and Publications

Build your own P.A., GROUP & DISCO SPEAKERS by R.F.C. Stephens

Save money with this practical guide. Plans for 17 different designs. Line source, I.B., Horn and Reflex types, for 8"-18" drive units. £3.95 post free (\$8 overseas).

THE DALESFORD SPEAKER BOOK by R.F.C. Stephens. This book is a must for the keen home constructor. Latest technology DIY designs. Plans for I.B., and Reflex designs for 10-100 watts. Also unusual centre-bass system. £2.20 post free (\$5 overseas).

VAN KAREN PUBLISHING,
5 SWAN STREET, WILMSLOW, CHESHIRE.

COMPREHENSIVE TV REPAIR INSTRUCTIONS for your set £5.00 with circuit (if requested). Free catalogue unique TV/other publications. AUSE (PW), 76 Church Street, Larkhall, Lanarkshire ML9 1HE.

Wanted

WANTED Diagram for Labgear Transmitter LG300 or/and information regarding best type of aerial. D. Collin, 8 High Street, Belford, Northumberland. NE70 7NH.

ELECTRONIC COMPONENTS PURCHASED. All Types Considered—Must be new. Send detailed list—Offer by return—. WALTONS, 55A Worcester Street, Wolverhampton.

Miscellaneous

THE SCIENTIFIC WIRE COMPANY

PO Box 30, London E.4
Reg. Office 22 Coningsby Gdns

ENAMELLED COPPER WIRE

SWG	1 lb	8 oz	4 oz	2 oz
10 to 19	2.65	1.45	.75	.60
20 to 29	2.85	1.65	.90	.70
30 to 34	3.05	1.75	1.00	.80
35 to 40	3.40	1.95	1.15	.84
41 to 43	4.55	2.55	1.95	1.30
44 to 46	5.05	3.05	2.15	1.70
47	8.00	5.00	3.00	1.80
48	15.00	9.00	6.00	3.30

SILVER PLATED COPPER WIRE

14 & 16	4.50	2.25	1.44	.90
20 & 22	5.00	2.85	1.74	1.06
24 & 26	5.70	3.31	2.00	1.22
28 & 30	6.67	3.86	2.35	1.44

Prices include P & P and VAT
SAE brings list of copper & resistance Wires
Dealer Enquiries Invited

SUPERB INSTRUMENT CASES by Bazelli, manufactured from P.V.C. Faced steel. Hundreds of people and industrial users are choosing the cases they require from our vast range. Competitive prices start at a low 90p. Chassis punching facilities at very competitive prices, 400 models to choose from, free literature (stamp would be appreciated). BAZELLI, Dept. No. 25, St. Wilfreds, Foundry Lane, Halton, Lancaster LA 6LT.

BELLS AND SIRENS

CARTERS SIREN £5.53
INDUSTRIAL SIX INCH BELL £8.27

PRICES INCLUSIVE.
SEND CHEQUE. P.O. to:

CWAS ALARM
11 Denbrook Walk,
Bradford BD4 0QS

6 to 12v D.C.

12v D.C.

SAE for full price list of Professional Burglar Alarm Equipment.

TIRRO's new mail order price list of electronic components now available on receipt of SAE. TIRRO ELECTRONICS, Grenfell Place, Maidenhead, Berks.

NICKEL CADMIUM BATTERIES

Rechargeable and suitable for 'fast charge' HP7 (AA) £1.13, SUB C £1.47, HP 11 (C) £2.15, HP 2 (D) £3.27, PP3 £4.09 (PP3 not suitable for fast charge). PP3 charger £5.31. All above Nickel Cadmium batteries are guaranteed 'EVER READY' full spec, and are supplied complete with solder tags (except PP3). Just in stock—New rechargeable sealed lead acid maintenance free batteries suitable for burglar alarms etc. 1-2 amp hr. 6v. £4.40 6 amp hr. 6v. £5.85.

Quantity prices available on request. Date and charging circuits free on request with orders over £10 otherwise 30p post and handling (specify battery type), all prices include VAT. Please add 10% P & P on orders under £10. 5% over £10.

Cheques, postal orders, mail order to: **SOLID STATE SECURITY DEPT. PW, 10, Bradshaw Lane, Parbold, Wigan, Lancs. 0257-4726.**

ALFAC etch resist transfers and other p.c. board drawing materials available from stock. SAE details. Ramar Constructor Services, Masons Road, Stratford-upon-Avon. CV37 9NF.

PW October issue 2m MOSFET CONVERTER units from the author GACFY. Kit of parts for complete PCB £8.50. Ready built and aligned units boxed £17.00. Parts available separately, 38-6667 Mhz Xtal £2.75, PCB £1.85.
1750 Tone Burst Board. Tested and Aligned 1.4in sq. £3.50.

SPECTRUM COMMUNICATIONS

12 Weatherbury Way, Dorchester, Dorset DT1 2EF.
Prices inclusive of P. & P.

LOSING DX?

RARE DX UNDER QRM? Dig it out with a Tunable Audio Notch Filter, 350-5000 Hz, 40dB notch, speaker amplifier, only £8.90.
RADIO 4 GONE? FRG7? AR88? 200 KHz to Medium Wave Converter only £9.70.
EXPLORE V.L.F. 10-150 KHz Receiver £10.70.
TIME? MSF 60KHz Receiver £13.70 or with sequential year, month, date, day, hours, minutes, seconds display parts (no case or pcb) £24.40.
SIG. GEN., 10Hz-200KHz, sine/square, £10.80.
PROGRAM YOUR OWN tunes on a MUSICAL DOORBELL, new tune each day, just needs bell transformer and speaker, £19.50.
HOW LOW CAN YOU GO? 100-600 KHz to 4-1-4-6 MHz Converter only £9.90.

Giro 21-923-4000. Each easy-assembly kit includes all parts, printed circuit, case, postage etc. money back assurance so SEND us NOW.

CAMBRIDGE KITS

45 (PR) Old School Lane, Milton, Cambridge

MORSE CODE TUITION AIDS

Cassette A: 1-12 w.p.m. for amateur radio examination.
 Cassette B: 12-24 w.p.m. for professional examination preparation.
 Morse Key and Buzzer Unit for sending practice.
 Price each Cassette (including booklets) £4.50. Morse Key and Buzzer £4.50.
 Prices include postage etc., Overseas Airmail £1.50 extra.

MHEL ELECTRONICS (Dept. P.W.), 12 Longshore Way, Milton, Portsmouth PO4 8LS.

BUILD you own 771B type Metal Detector, details SAE 117 Horton Road, Brighton, BN1 7EG.

GUITAR/PA/MUSIC/AMPLIFIERS

100 watt with superb treble bass overdrive, 12 months guarantee. Unbeatable at £40; 60 watt £35; 200 watt £56; Twin channel sep treble/bass per channel £52; 60 watt £46; 200 watt £69; 100 watt four channel sep treble/bass per channel £65; 200 watt £79; Slaves 100 watt £32; 200 watt £48; Fuzz boxes great sound £7.90; Bass fuzz £8.50; 100 watt combo superb sound overdrive, sturdy construction, castors, unbeatable £85; Twin channel £95; Bass Combo £95; Speakers 12in. 100 watt £22.50; 60 watt £14.50; Shure mic unidyne B £26.


Send Cheque or P.O. to:

WILLIAMSON AMPLIFICATION

62 Thorncliffe Ave, Dukinfield, Cheshire.
 Tel. 061-344 5007

LET LYWOOD ELECTRONICS quote for parts for your project at competitive prices. Send list of your requirements. Interested and helpful service. 20 Stourcliffe Avenue, Bournemouth BH6 3PT.

"UNIVERSAL"

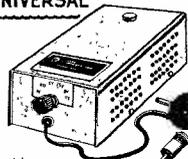

AC TO DC CONVERTER

CHOICE OF
3-4½-6-7½-9-12 VOLTS DC

This ultra wide range power supply unit converts the usual domestic AC input 220/250 volts to a choice of DC outputs 3-4½-6-7½-9-12 volts DC, selected by a rotary switch. The output multiplier is polarity reversing and combines a 3.5mm Jack plug with 2.1mm and 2.5mm power plugs PLUS 2.5mm Jack plug (slips over the 3.5mm plug). Suitable wide range of different units. Earthed, ventilated metal case with pilot light and switch. Exceptional value. Only £9.95 + 95p P&P. Also single voltage 9v 150ma model suitable for nearly all T.V. Games. £5.45 + 55p P&P.

MICROJET WELDER

A TINY FLAME UPTO 5000°F!

WELDS-BRAZES SOLDER



£24.95 INC. FLAME

TIPS

Precision tool using combination of butane and compressed oxygen or micronox. A pencil lead thin flame size, adjustable to 5,000°F. Cuts metals, welds, brazes and solders gold, silver. Ideal modelling, electricians, opticians, dentists, silversmiths, jewellery, clockmakers, electronic and computer servicing. Up to 30 minutes use on fuel supplied. Replacement set of 2 micronox, 1 butane cylinder £2.30 + 25p p&p extra. Only £24.95 + £1.35 p&p. Access accepted.

JOHN DUDLEY & CO. LTD (Dept. WP11)
 Carolyn House, Water Road, Wembley, Middx.
 (Mail Order).
 Tel. 01-435 5456, before noon.

AERIAL BOOSTERS Improve weak VHF Radio and Television reception, price £5.00 S.A.E. for Leaflets. **ELECTRONIC MAILORDER LTD.**, Ramsbottom, Bury, Lancashire BL0 9AG.

DART STATIONERY
 Presents **FOR THE AMATEUR**
 Large variety of personalised **QSL CARDS**
 - see catalogue for prices -

LOG BOOKS **£2.00** each

FOR THE DX'er

Personalised **QSL CARDS**.
RECEPTION REPORT LETTERS. Professionally styled letters printed in two colours and supplied in pads of 100 letters.

1 Pad **£1.80**
 2+ Pads **£1.60** each.
 Loose Leaf **LOG BOOKS** with 100 sheets **£2.50**

FOR THE CB'er

Personalised **QSL CARDS**.
CATALOGUES available containing complete range of radio stationery **PRICE 45p**.
EVERY ORDER CARRIES A MONEY BACK ASSURANCE IF NOT COMPLETELY SATISFIED.
 Please send cheques or P.O. payable to:—

DART STATIONERY
 20, Bromley Road, London E17 4PS, England
 Tel. 01-539 5412

NOTICE TO READERS

Whilst prices of goods shown in classified advertisements are correct at the time of closing for press, readers are advised to check with the advertiser both prices and availability of goods before ordering from non-current issues of the magazine.

ORDER FORM PLEASE WRITE IN BLOCK CAPITALS

Please insert the advertisement below in the next available issue of Practical Wireless for insertions

I enclose Cheque/P.O. for £.....

(Cheques and Postal Orders should be crossed Lloyds Bank Ltd. and made payable to Practical Wireless).

NAME.....

ADDRESS

Send to: Classified Advertisement Manager
PRACTICAL WIRELESS,
GMG, Classified Advertisement Dept., Rm. 2337,
King's Reach Tower, Stamford Street,
London SE1 9LS Telephone 01-261 5846

Rate
22p per word, minimum 12 words. Box No. **60p** extra.

Company registered in England. Registered No. 53626. Registered office: King's Reach Tower, Stamford Street, London SE1 9LS

TRANSFORMERS

ALL EX-STOCK—SAME DAY DESPATCH. VAT 8%

12 OR 24 VOLT OR 12-0-12V PRIMARY 220-240 VOLTS

Ref	12V	24V	£	P & P
111	0.5	0.25	2.20	0.45
213	1.0	0.5	2.64	0.78
71	2	1	3.51	0.78
18	4	2	4.03	0.96
85	0.5	2.5	5.00	0.79
70	8	4	5.35	0.96
108	8	4	7.42	1.14
72	10	5	8.12	1.42
116	12	6	8.99	1.32
17	16	8	10.72	1.32
115	20	10	13.98	2.08
187	30	15	17.05	2.08
226	60	30	36.74	OA

30 VOLT RANGE

Ref	30V	£	P & P
112	0.5	2.64	0.78
79	1.0	3.57	0.96
3	2.0	5.77	0.96
20	3.0	6.20	1.14
21	4.0	7.99	1.14
51	5.0	9.87	1.32
117	6.0	11.17	1.45
88	8.0	14.95	1.64
89	10.0	17.25	1.84

50 VOLT RANGE

Ref	50V	£	P & P
124	0.5	3.88	0.96
126	1.0	5.91	0.96
127	2.0	7.60	1.14
125	3.0	11.00	1.32
123	4.0	12.52	1.84
40	4.0	15.84	1.64
120	6.0	18.06	1.84
121	8.0	25.56	OA
122	10.0	29.55	OA
189	12.0	34.06	OA

AUTO TRANSFORMERS

Ref	VA (Watts)	£	P & P
113	150-115-210-240V	2.48	0.71
64	75-0-115-210-240V	4.01	0.96
4	150-0-115-200-220-240V	5.35	0.96
67	500-0-115-200-220-240V	10.99	1.64
84	1000-0-115-200-220-240V	18.76	2.08
93	1500-0-115-200-220-240V	23.36	OA
95	2000-0-115-200-220-240V	34.82	OA
73	3000-0-115-200-220-240V	59.21	OA
80s	4000-0-10-115-200-220-240V	76.86	OA
57s	5000-0-10-115-200-220-240V	89.50	OA

CASED AUDIO TRANSFORMERS

VA	£	P & P
75	7.73	1.14
150	10.01	1.14
200	9.92	1.45
250	10.49	1.45
500	19.17	1.64
750	23.41	1.76
1000	27.88	OA
1500	26.02	OA
2000	49.97	OA

50 VOLT RANGE

Ref	50V	£	P & P
102	0.5	3.41	0.78
103	1.0	4.57	0.96
104	2.0	7.16	1.14
105	3.0	8.56	1.32
106	4.0	11.41	1.50
107	6.0	15.06	1.64
118	8.0	20.26	2.08
119	10.0	24.98	OA

MAINS ISOLATORS (SCREENED)

Ref	VA (Watts)	£	P & P
*07	20	4.40	0.79
149	60	6.70	0.96
150	100	7.61	1.14
151	200	11.16	1.50
152	300	13.28	1.84
153	350	16.43	1.84
154	500	20.47	2.15
155	750	29.06	OA
156	1000	37.20	OA
157	1500	51.38	OA
158	2000	81.81	OA
159	3000	86.66	OA

HIGH VOLTAGE ISOLATORS

VA	Ref	£	P & P
60	243	6.70	1.32
350	247	16.43	1.84
1000	250	37.10	OA
2000	252	61.81	OA

SEND 15p FOR CATALOGUE

Prices correct 21-11-78. Please add VAT after P & P.

SCREENED MINIATURES

Ref	mA	Volts	£	P & P
238	200	3-0-3	2.57	0.55
212	1A, 1A	0-6-0-6	2.85	0.78
13	100	9-0-9	2.14	0.38
235	330, 330	0-9-0-9	1.99	0.38
207	500, 500	0-8-9, 0-8-9	2.77	0.71
208	1A, 1A	0-8-9, 0-8-9	3.53	0.78
236	200, 200	0-15-0-15	1.99	0.38
214	300, 300	0-20-0-20	2.80	0.78
221	700 (DC)	20-12-0-12-20	3.41	0.78
206	1A, 1A	0-15-20-0-15-20	4.63	0.96
203	500, 500	0-15-27-0-15-27	3.98	0.96
204	1A, 1A	0-15-27-0-15-27	6.04	0.96
239	10	12-0-12	2.57	0.38

COMPONENT PACKS

Ref	100V	100A*	£2-10
65	1W Metal Oxide Resistors.	2A	£0.45
65	1W Metal Oxide Resistors.	4A	£0.85
150	Mixed Value Capacitors.	6A	£1.25
10	Resistors.	12A	£2.85
50	Wire Wound Resistors.	15p P & P	*VAT 8%
10	3000mf 30V Capacitors.		
25	Assorted presets.		
50	3 tag terminal strips.		
Hardware	8A nuts, bolts.		
200	Mixed Resistors.		

AMPLIFIER MODULES

Ref	10W (AL30)	£3-75
25W (AL60)	£4-57	
35W (AL80)	£7-15	
125W (AL250)	£17-25	
Power Supply PS12	£1-30	
Power Supply SPM80	£4-25	
VAT 12 1/2% P & P 35p.		

TEST METERS

Ref	Price	£	P & P
AVO 8 MK5	£81-70	Megger BM7 battery	£45-15
AVO 73	£33-50	U4315 Budget Meter	
AVO 73	£44-20	20KΩ/V Ranges to	
AVO MM5	£28-66	1000V, 2.5A AC/DC	
Wee Megger	£66-90	500KΩ. In steel case	
EM272	£53-70		£15-85
DA116 digital	£102-00		
AVO TT169 in circuit Transistor Tester			£34-75

MINI-MULTIMETER

Ref	Price	£	P & P
DC-1000V AC-1000V DC-100mA Res-150kΩ			
1000Ω/V Bargain	£7-20	VAT 8% P & P	£2-6p

20,000 ohm/V Multimeter, mirror scale. Ranges AC/DC to 1000V DC current to 250mA Resistance to 3 Mohms. 5" x 3 1/2" x 1 1/2" £14.36. VAT 8% P & P £1-05.

NEW RANGE TRANSFORMER

Ref	Price	£	P & P
31-120V or 220/240V. Sec 0-36-48 twice to give 36-0-36V 48-0-48V 72V or 92V.			
3A	14.70	1.48	
1A	18.77	1.84	
5A	26.64	2.15	

PANEL METERS

Ref	Price	£	P & P
43mm x 43mm	82mm x 78mm		
0-50mA	£6-20	0-50mA	£6-70
0-500µA	£5-95	0-500µA	£6-70
0-1mA	£5-95	0-1mA	£6-70
0-30V	£5-95	0-30V	£6-70
0-30V	£3-36		
£2-60			

Magnetic to Ceramic Cartridge Converter MPA 30 Operating voltage 20-45V. P & P 44p. VAT 12 1/2%. £3-50

Special Offer—Quality low noise cassette tapes. C60 30p, C90 42p. P & P 15p. VAT 8%.

250VA ISOLATOR 0-200-220-240V Sec 0-240V C.T. 250VA £5-20. P & P 96p. Ref. 62.

ANTEX SOLDERING IRONS 15W £3-75 Stand £1-52 + VAT 8%. P & P 46p. VAT 12 1/2%

15V RANGE

Ref	Price	£	PP
171	500 mA	2.09	.45
172	1A	2.96	.78
173	2A	3.59	.78
174	3A	3.75	.86
175	4A	5.73	.96

Aluminium Boxes—with 1/2" lip lid & screws.

Ref	W	H	Price
B1	5 1/2"	2 1/2"	62p
B2	4	1 1/2"	62p
B3	4	2 1/2"	62p

S-DECS

Ref	Price	£	P & P
Solderless bread boarding			
S Dec 70 contacts	£3-10		
T Dec 208 contacts	£4-35		
U Dec 'A' for I.C.s etc	£4-50		
U Dec 'B' for I.C.s etc	£6-99		

Electronic Construction Kit

Home electronic teacher. Start simply and progress to a TRF radio or electronic organ. No soldering, all parts included in presentation box, full instructions. £8-29 + 96p P & P. VAT 8%.

ABS PLASTIC BOXES

Ref	Price	£	P & P
inset brass nuts, slots to take P.C. cards flush fitting lid.			
PB1 180mm x 62 x 40	65p		
PB2 100mm x 75 x 40	73p		
PB3 120mm x 100 x 45	87p		
*PB4 215mm x 130 x 85	£2.54		

Barrie Electronics Ltd.

3, THE MINORIES, LONDON EC3N 1BJ
TELEPHONE: 01-488 3316/7/8
NEAREST TUBE STATIONS: ALDGATE & LIVERPOOL ST

Mail Order Protection Scheme

The Publishers of *Practical Wireless* are members of the Periodical Publishers Association which has given an undertaking to the Director General of Fair Trading to refund monies sent by readers in response to mail order advertisements, placed by mail order traders, who fail to supply goods or refund monies owing to liquidation or bankruptcy. This arrangement does not apply to any failure to supply goods advertised in a catalogue or in a direct mail solicitation.

In the unhappy event of the failure of a mail order trader readers are advised to lodge a claim with *Practical Wireless* within three months of the date of the appearance of the advertisement, providing proof of payment. Claims lodged after this period will be considered at the Publisher's discretion. Since all refunds are made by the magazine voluntarily and at its own expense, this undertaking enables you to respond to our mail order advertisers with the fullest confidence.

For the purpose of this scheme, mail order advertising is defined as:—

'Direct response advertisements, display or postal bargains where cash had to be sent in advance of goods being delivered'. Classified and catalogue mail order advertising are excluded.



Wilmslow Audio

THE firm for speakers!

SEND 15P STAMP FOR THE WORLD'S BEST CATALOGUE OF SPEAKERS, DRIVE UNITS, KITS, CROSSOVERS ETC. AND DISCOUNT PRICE LIST.

- AUDAX ● AUDIOMASTER ● BAKER ● BOWERS & WILKINS ● CASTLE ● CELESTION ● CHARTWELL ● COLES ● DALESFORD ● DECCA ● EMI ● EAGLE ● ELAC ● FANE ● GAUSS ● GOODMAN'S ● I.M.F. ● ISOPHON ● JR ● JORDAN WATTS ● KEF ● LEAK ● LOWTHER MCKENZIE ● MONITOR AUDIO ● PEERLESS ● RADFORD ● RAM ● RICHARD ALLAN ● SEAS ● SHACKMAN ● STAG ● TANGENT ● TANNON ● VIDEOTONE ● WHARFEDALE ● YAMAHA

WILMSLOW AUDIO (Dept. P.W.)

SWAN WORKS, BANK SQUARE, WILMSLOW, CHESHIRE SK9 1HF

Discount Hi-Fi Etc. at 5 Swan Street and 10 Swan Street
Speakers, Mail Order & Export 0625 529599 Hi-Fi 0625 526213

WATFORD ELECTRONICS

33/35, CARDIFF ROAD, WATFORD, HERTS, ENGLAND
MAIL ORDER. CALLERS WELCOME. Tel. Watford 40589/9

ALL DEVICES BRAND NEW, FULL SPEC. AND FULLY GUARANTEED. ORDERS DESPATCHED BY RETURN OF POST. TERMS OF BUSINESS: CASH/CHEQUE/P.O.s OR BANKERS DRAFT WITH ORDER. GOVERNMENT AND EDUCATIONAL INSTITUTIONS OFFICIAL ORDERS ACCEPTED. TRADE AND EXPORT INQUIRY WELCOME. P.P ADD 30p* TO ALL ORDERS UNDER £10.00. OVERSEAS ORDERS POSTAGE AT COST. SEND 50p (plus 25p p&p) for our catalogue.

VAT Export orders no VAT. Applicable to U.K. Customers only. Unless stated otherwise, all prices are exclusive of VAT. Please add 8% to devices marked * To the rest add 12%.

We stock many more items. It pays to visit us. We are situated behind Watford Football Ground. Nearest Underground/Br. Rail Station: Watford High Street. Open Monday to Saturday 9 a.m.-6 p.m. Ample Free Car Parking space available.

POLYESTER CAPACITORS: Axial lead type. (Value are in μ F).
0.001, 0.0015, 0.0022, 0.0033, 0.0047, 0.0068, 0.01, 0.015 5p; 0.018 10p; 0.022, 0.033 11p; 0.047, 0.068 14p; 0.1 17p; 0.15, 0.22 24p; 0.33, 0.47 41p; 0.68 48p.
160V: 0.039, 0.15, 0.22 11p; 0.33, 0.47 19p; 0.68, 1.0 22p; 1.5 29p; 2.2 32p; 4.7 36p.
DIELECTRIC: 1000V: 0.01, 0.015 20p; 0.022 22p; 0.047 26p; 0.1 38p; 0.15 47p; 0.1 17p; 0.15 22p.

POLYESTER RADIAL LEAD (Values in μ F): 250V:
0.01, 0.015, 0.022, 0.027 5p; 0.033, 0.047, 0.068, 0.1 7p; 0.15 10p; 0.22, 0.33 10p; 0.47 11p; 0.68 19p; 1.0 22p; 1.5 30p; 2.2 32p; 4.7 36p.

ELECTROLYTIC CAPACITORS: Axial lead type. (Values are in μ F).
500V: 10 40p; 47 63p; 250V: 100 65p; 63V: 1.0, 1.5, 2.2, 2.5, 3.3, 4.7, 6.8, 8, 10, 15, 22 8p; 47, 50, 100 11p; 63, 100, 270 50p; 1.0 7p; 50, 100, 220 25p; 470 32p; 1000 50p; 40V: 22, 33 8p; 100 12p; 2200, 3300 68p; 4700 85p; 35V: 10, 33 7p; 330, 470 32p; 1000 50p; 25V: 10, 22, 47 6p; 80, 100, 160 8p; 220, 250 13p; 470, 640 25p; 1000 27p; 1500 30p; 2200 45p; 3300 62p; 4700 68p; 16V: 10, 40, 47, 68 7p; 100, 125 8p; 220, 330 14p; 470 16p; 1000, 1500 20p; 2200 34p; 10V: 100 6p; 640 12p; 1000 14p.

TANTALUM BEAD CAPACITORS
35V: 0.1 μ F, 0.22, 0.33, 0.47, 0.68, 1.0, 2.2 μ F. 3.3, 4.7, 6.8, 8, 10, 15, 20, 22, 25, 30, 33, 36, 40, 47, 50, 55, 60, 63, 68, 75, 80, 85, 90, 95, 100, 110, 120, 130, 140, 150, 160, 170, 180, 190, 200, 220, 250, 270, 300, 330, 360, 390, 420, 450, 470, 500, 550, 600, 630, 680, 750, 800, 850, 900, 950, 1000, 1100, 1200, 1300, 1400, 1500, 1600, 1700, 1800, 1900, 2000, 2200, 2500, 2700, 3000, 3300, 3600, 3900, 4200, 4500, 4700, 5000, 5500, 6000, 6300, 6800, 7500, 8000, 8500, 9000, 9500, 10000, 11000, 12000, 13000, 14000, 15000, 16000, 17000, 18000, 19000, 20000, 22000, 25000, 27000, 30000, 33000, 36000, 39000, 42000, 45000, 47000, 50000, 55000, 60000, 63000, 68000, 75000, 80000, 85000, 90000, 95000, 100000.

MYLAR FILM CAPACITORS
100V: 0.001, 0.002, 0.005, 0.01 μ F 6p
0.015, 0.02, 0.03, 0.04, 0.05, 0.056 μ F 7p
0.1 μ F, 0.2 9p.

CERAMIC CAPACITORS 50V
Range: 0.5pF to 10nF 3p
15nF, 22nF, 33nF, 47nF 4p

POLYSTYRENE CAPACITORS:
10pF to 1nF, 5p. 1.5nF to 47nF 10p.

SILVER MICA (pF)
3, 3.3, 4.7, 5, 6, 8, 10, 12, 15, 18, 22, 27, 33, 47, 50, 56, 68, 75, 82, 85, 100, 120, 150, 200, 250 9p
each.
300, 330, 360, 390, 600 & 820pF 16p each.
1000, 2200pF 20p each.

JACKSONS VARIABLE CAPS.
Dielectric 0.2 3.365pF with slow motion Drive 140p
100/300pF 140p
500/208/176 285p
1.1 μ F Ball Drive 115p
4511/D/AF Dial Drive 4103 115p
1.6/36:1 850p
Drum 54mm 30p
0.1-365pF 245p
0.02 3.365pF 165p

TRIMMERS mini
25pF, 3-10pF, 3-30pF, 10-40pF, 5-25pF, 6pF, 8pF, 30p

COMPRESSION
3-40pF, 10-80pF, 25-200pF, 100-500pF

AUDIBLE Warning
B buzzers 6V or 12V 65p

RF CHOKES
1 μ F, 4.7, 10, 22, 47, 100, 220, 470, 750, 1.5mH, 2.5, 5, 10mH

TRANSFORMERS* (Mains Prim. 220-240V)
6-0-6 100VA; 9-0-9V 75mA; 12-0-12V 100mA 95p.

8VA type: 6V-5A 6V-5A; 9V-4A 9V-4A; 12V-3A 12V-3A; 15V-2.5A 15V-2.5A 195p.

12VA: 4.5-1.3A 4.5V-1.3A; 6V-12A 6V-2A 12V-5A 12V-5A; 15V-4A 15V-4A 20V-3A 20V-3A 220p (20p p&p)

24VA: 6V-1.5A 6V-1.5A; 9V-1.2A 9V-1.2A; 12V-1A 12V-1A; 15-8A 15-8A; 20V-6A 20V-6A 220p (45p p&p)

50VA: 6V-4A 6V-4A; 9V-2.5A 9V-2.5A; 12V-2A 12V-2A; 15V-1.5A 15V-1.5A; 20V-1.2A 20V-1.2A; 25V-1A 25V-1A; 30V-8A 30V-8A 350p (85p p&p)

100VA: 12V-4A 12V-4A; 15V-3A 15V-3A; 20V-2.5A 20V-2.5A; 30V-1.5A 30V-1.5A; 40V-1.25A 40V-1.25A; 50V-1A 50V-1A 650p (60p p&p)

(N.B. P&P charge to be added above our normal postal charge.)

DENCO COILS
Dual Purpose "DP" RDT2 92p
VALVE TYPE RFC 3 chokes 91p
RFC 7 (19H) 98p

Rd. Wht. 86p
6-7 B.Y.R. 76p
1-5 Green 92p
T-type (Transistor Tuning) 104p
Ranges: 1-5 Bl. Yl. 86p
Rd. Wht. 93p

TRANSISTORS		P		P		P		P		P	
AC107*	28	BC170	18	BF167	30	MPSA55	25	TIP3055*	52	2N2160*	350
AC17*	28	BC171	11	BF173*	28	MPSA56	25	TIP42A	52	2N2217*	43
AC125*	20	BC172	11	BF177*	24	MPSA70	34	TIP43	54	2N2218A*	34
AC126*	20	BC173	12	BF178*	25	MPSU02	58	TIS44	45	2N2219A*	22
AC127*	20	BC177*	18	BF179*	20	MPSU05	50	TIS45	45	2N2220A*	26
AC128*	20	BC178*	16	BF180*	35	MPSU06	56	TIS46	45	2N2221A*	23
AC14*	24	BC182	9	BF181*	35	MPSU07	53	TIS47	45	2N2222A*	20
AC141*	24	BC183	9	BF182*	35	MPSU08	53	TIS48	50	2N2223A*	25
AC142*	24	BC184	9	BF183*	35	MPSU09	60	TIS49	50	2N2224*	23
AC142L*	38	BC182L	11	BF184*	35	MPSU10	60	TIS50	47	2N2225*	21
AC176*	20	BC183L	10	BF185	12	OC23*	170	TIS60	45	2N2369A*	15
AC187*	20	BC184L	10	BF186	12	OC25*	170	TIS62	45	2N2483*	28
AC188*	20	BC185	10	BF187	12	OC26*	170	TIS64	45	2N2484*	28
AC189*	35	BC186	21	BF188*	14	OC27*	170	TIS65	45	2N2485*	28
AC19*	40	BC187*	28	BF189	14	OC28*	105	TIS69	20	2N2784	55
AC191	40	BC188*	28	BF190	14	OC29*	160	TIS91	24	2N2904*	22
AC192	40	BC189*	28	BF191	14	OC35*	130	TIX107	12	2N2905A*	22
AC193	40	BC190*	28	BF192	14	OC36*	130	TIX108	12	2N2906*	22
AC194	40	BC191	11	BF193	14	OC41*	148	TIX109	14	2N2907*	22
AC195	40	BC192	11	BF194	14	OC42*	32	TIX110	15	2N2908*	22
AC196	40	BC193	11	BF195	14	OC43*	55	TIX300	15	2N2926G	10
AC197	40	BC194	12	BF196	14	OC44*	31	TIX301	15	2N3011*	24
AC198	40	BC195	12	BF197	14	OC45*	28	TIX302	20	2N3053*	20
AC199	40	BC196	12	BF198	14	OC46*	28	TIX303	25	2N3054*	49
AC200	40	BC197	12	BF199	14	OC47*	28	TIX304	24	2N3055*	48
AC201	35	BC198	12	BF200*	32	OC48*	28	TIX305	17	2N3056*	48
AC202	40	BC199	12	BF201*	32	OC49*	28	TIX306	15	2N3057*	48
AC203	40	BC200	12	BF202*	32	OC50*	28	TIX307	15	2N3058*	48
AC204	40	BC201	12	BF203*	32	OC51*	28	TIX308	15	2N3059*	48
AC205	40	BC202	12	BF204*	32	OC52*	28	TIX309	15	2N3060*	48
AC206	40	BC203	12	BF205*	32	OC53*	28	TIX310	15	2N3061*	48
AC207	40	BC204	12	BF206*	32	OC54*	28	TIX311	15	2N3062*	48
AC208	40	BC205	12	BF207*	32	OC55*	28	TIX312	15	2N3063*	48
AC209	40	BC206	12	BF208*	32	OC56*	28	TIX313	15	2N3064*	48
AC210	40	BC207	12	BF209*	32	OC57*	28	TIX314	24	2N3442*	140
AC211	40	BC208	12	BF210*	32	OC58*	28	TIX320	30	2N3504	55
AC212	40	BC209	12	BF211*	32	OC59*	28	TIX326	30	2N3563	20
AC213	40	BC210	12	BF212*	32	OC60*	28	TIX341	30	2N3614*	169
AC214	40	BC211	12	BF213*	32	OC61*	28	TIX342	30	2N3615*	156
AC215	40	BC212	12	BF214*	32	OC62*	28	TIX343	30	2N3616*	156
AC216	40	BC213	12	BF215*	32	OC63*	28	TIX344	30	2N3617*	156
AC217	40	BC214	12	BF216*	32	OC64*	28	TIX345	30	2N3618*	156
AC218	40	BC215	12	BF217*	32	OC65*	28	TIX346	30	2N3619*	156
AC219	40	BC216	12	BF218*	32	OC66*	28	TIX347	30	2N3620*	156
AC220	40	BC217	12	BF219*	32	OC67*	28	TIX348	30	2N3621*	156
AC221	40	BC218	12	BF220*	32	OC68*	28	TIX349	30	2N3622*	156
AC222	40	BC219	12	BF221*	32	OC69*	28	TIX350	15	2N3623*	156
AC223	40	BC220	12	BF222*	32	OC70*	28	TIX351	15	2N3624*	156
AC224	40	BC221	12	BF223*	32	OC71*	28	TIX352	15	2N3625*	156
AC225	40	BC222	12	BF224*	32	OC72*	28	TIX353	15	2N3626*	156
AC226	40	BC223	12	BF225*	32	OC73*	28	TIX354	15	2N3627*	156
AC227	40	BC224	12	BF226*	32	OC74*	28	TIX355	15	2N3628*	156
AC228	40	BC225	12	BF227*	32	OC75*	28	TIX356	15	2N3629*	156
AC229	40	BC226	12	BF228*	32	OC76*	28	TIX357	15	2N3630*	156
AC230	40	BC227	12	BF229*	32	OC77*	28	TIX358	15	2N3631*	156
AC231	40	BC228	12	BF230*	32	OC78*	28	TIX359	15	2N3632*	156
AC232	40	BC229	12	BF231*	32	OC79*	28	TIX360	15	2N3633*	156
AC233	40	BC230	12	BF232*	32	OC80*	28	TIX361	15	2N3634*	156
AC234	40	BC231	12	BF233*	32	OC81*	28	TIX362	15	2N3635*	156
AC235	40	BC232	12	BF234*	32	OC82*	28	TIX363	15	2N3636*	156
AC236	40	BC233	12	BF235*	32	OC83*	28	TIX364	15	2N3637*	156
AC237	40	BC234	12	BF236*	32	OC84*	28	TIX365	15	2N3638*	156
AC238	40	BC235	12	BF237*	32	OC85*	28	TIX366	15	2N3639*	156
AC239	40	BC236	12	BF238*	32	OC86*	28	TIX367	15	2N3640*	156
AC240	40	BC237	12	BF239*	32	OC87*	28	TIX368	15	2N3641*	156
AC241	40	BC238	12	BF240*	32	OC88*	28	TIX369	15	2N3642*	156
AC242	40	BC239	12	BF241*	32	OC89*	28	TIX370	15	2N3643*	156
AC243	40	BC240	12	BF242*	32	OC90*	28	TIX371	15	2N3644*	156
AC244	40	BC241	12	BF243*	32	OC91*	28	TIX372	15	2N3645*	156
AC245	40	BC242	12	BF244*	32	OC92*	28	TIX373	15	2N3646*	156
AC246	40	BC243	12	BF245*	32	OC93*	28	TIX374	15	2N3647*	156
AC247	40	BC244	12	BF246*	32	OC94*	28	TIX375	15	2N3648*	156
AC248	40	BC245	12	BF247*	32	OC95*	28	TIX376	15	2N3649*	156
AC249	40	BC246	12	BF248*	32	OC96*	28	TIX377	15	2N3650*	156
AC250	40	BC247	12	BF249*	32	OC97*	28	TIX378	15	2N3651*	156
AC251	40	BC248									

WATFORD ELECTRONICS

(Continued from opposite side)

DIODES	*BRIDGE RECTIFIERS	SPEAKERS
AA119 15	1A/50V 20	80Ω 3W 2.5" 65
AA129 25	1A/100V 22	400Ω 2.5" 65
AA300 15	1A/200V 25	64Ω 2.5" 65
AAZ15 25	1A/400V 29	80Ω 5W 190
BA100 20	2A/50V 35	80Ω 3W 6" x 4" 160
BY100 24	2A/100V 44	
BY126 12	2A/200V 44	
BY127 12	2A/400V 53	
CR033 148*	2A/600V 65	
OA9 75	4A/100V 72	
OA47 12	4A/200V 75	
OA70 12	4A/400V 75	
OA79 12	4A/600V 105	
OA81 15	4A/800V 120	
OA85 12	6A/100V 73	
OA90 6	6A/200V 78	
OA91 6	6A/400V 85	
OA95 8	BY164 56	
OA200 9	VM18 DIL 40	
OA202 8		
IN914 4	ZENERS	
IN916 5	Rng: 2V7-39V	
IN400/2* 5	400mW 9p	
IN400/3* 6	Rng: 3V3-33V	
IN400/4* 6	1-3W 17p	
IN400/5* 7		
IN400/6* 7		
IN4148 4	VARICAPS	
IS44 20	MMAM115120	
3A/100V* 18	BA102 25	
3A/400V* 20	BB104 40	
3A/600V* 27	BB105B 40	
3A/1000V* 30	BB106 40	
6A/600V 65		
SCR's*	Noise Diode	
1A50V 38	Z5J 160	
1A100V 42		
1A200V 47		
1A400V 52		
1A600V 50		
5A300V 35		
5A600V 43		
8A300V 48		
8A500V 58		
8A600V 59		
12A300V 85		
12A500V 92		
C106D 38		

OPTO ELECTRONICS*	SWITCHES*
LEDs - Clip	TOGGLE 2A 250V
TL209 Red 125"13	SPST 28
TL211 Grn 125"18	DPST 34
TL212 Yellow 22	DPDT 38
0.2" Red 15	4 pole on off 54
0.2" Yellow, Grn, Amber 19	SUB-MIN TOGGLE
OC871 120	SP changeover 59
ORP12 65	SPST on off 54
2N5777 45	SPST biased 85
ISOLATORS	DPDT 6 tags 70
MAN3640 165	DPDT C/OFF 79
XAN351 3" Green 180	DPDT Biased 115
TL114 85	SLIDE 250V
TL117 110	1A DPDT C/OFF 14
	1A DPDT 13
	4 pole 2-way 24
VOLTAGE REGULATORS*	PUSH BUTTON
T03 Can Type	Spring loaded
1A +ve: 5V, 12V, 15V, 18V 145p each	Latching 60
LM309K 135	SPST on off 85
LM320-12 -ve 99	DPDT 6 Tag 85
LM320-15 -ve 165	MINIATURE Non Locking
MVR5 or 12 150	Push to make 15
1A -ve: 5V, 12V 220	Push Break 25
	ROCKER: (Black) Bezel, 5A250V SPST 52
Plastic Case: -ve	
0.1A (T022) 5V, 6.2 183p	
8.2V, 12V, 15V 30	
1A (T0220) 5V, 12V, 15V, 18V, 24V 85	
VEROBOARD*	
Pitch 0.1 0.15 0.1 0.15	
0.1 +ve: 5V, 12V, 15V, 18V 145p each	
LM309K 135	
LM320-12 -ve 99	
LM320-15 -ve 165	
MVR5 or 12 150	
1A -ve: 5V, 12V 220	
FERRIC CHLORIDE*	
1lb bag Anhydrous 65p + 30p p. & p.	
DALO ETCH RESIST PEN*	
Plus spare tip 75p	
COPPER CLAD BOARDS*	
Fibre Single-sided SRBP 7.5" x 7" 60p	
Glass sided 7.5" x 7" 75p	
6" x 6" 90p	
6" x 12" 130p	
SOLECON PINS*	
1000 pins 50p; 1000 pins 400p	
DIL SOCKETS* Low Profile (TEXAS)	
8 pin 10p; 14 pin 12p; 16 pin 13p; 18 pin 20p; 20 pin 27p; 22 pin 30p; 24 pin 30p; 28 pin 42p; 40 pin 55p; 64 pin 20p	

RADIO 4 ON MW!

Yes, you can tune in to Radio 4 back on Medium Wave by using our easy to assemble LW- MW-Converter. Just place it beside your radio and you tune in as before.

Complete set of parts including assembly instructions

£4.50

Convert your TV into a VDU by using the new Thompson-CSF TV-CRT controller chip, SF.F.96364, 16 line by 64 Characters text refreshment, Cursor management, Cursor Management on screen. Line erasing. Compatible with any Computing system.

SF.F.96364E £11.75*
 AY-3-1015 £5.60*
 AY-5-1013 UART £4.50*
 SFC71301 ROM £8.20*
 SFS80102 RAM £2.05*
 74LS163 £1.18*
 UHF Modulator 250p*
 Compl. Module £136.50*
 Data Booklet 30p

ASCII Coded 56 Key Keyboard £59.50 (75pp&p)

74LS00 (TEXAS)	74LS123 70	74LS173 105	74LS251 134	74LS353 228
74LS00 131	74LS124 60	74LS174 106	74LS253 142	74LS365 65
74LS01 13	74LS125 180	74LS175 110	74LS257 110	74LS366 65
74LS02 14	74LS126 60	74LS181 398	74LS258 110	74LS367 65
74LS03 14	74LS127 60	74LS183 298	74LS259 180	74LS368 66
74LS04 14	74LS132 95	74LS188 298	74LS261 450	74LS373 180
74LS05 23	74LS136 55	74LS191 140	74LS262 52	74LS374 180
74LS08 22	74LS138 85	74LS192 132	74LS263 52	74LS375 180
74LS09 22	74LS139 85	74LS193 130	74LS264 52	74LS376 180
74LS10 20	74LS140 108	74LS194 166	74LS265 52	74LS377 212
74LS11 22	74LS141 108	74LS195 136	74LS266 52	74LS378 184
74LS12 23	74LS142 170	74LS196 100	74LS267 52	74LS379 215
74LS13 38	74LS143 170	74LS197 140	74LS268 52	74LS380 86
74LS14 75	74LS144 170	74LS198 140	74LS269 52	74LS381 86
74LS15 30	74LS145 170	74LS199 140	74LS270 52	74LS382 86
74LS16 30	74LS146 170	74LS200 348	74LS271 52	74LS383 86
74LS17 30	74LS147 170	74LS201 348	74LS272 52	74LS384 86
74LS18 20	74LS148 170	74LS202 345	74LS273 52	74LS385 86
74LS19 20	74LS149 170	74LS203 345	74LS274 52	74LS386 86
74LS20 20	74LS150 170	74LS204 345	74LS275 52	74LS387 86
74LS21 22	74LS151 96	74LS205 345	74LS276 52	74LS388 86
74LS22 22	74LS152 96	74LS206 345	74LS277 52	74LS389 86
74LS23 22	74LS153 96	74LS207 345	74LS278 52	74LS390 230
74LS24 22	74LS154 96	74LS208 345	74LS279 52	74LS391 230
74LS25 22	74LS155 96	74LS209 345	74LS280 52	74LS392 230
74LS26 22	74LS156 96	74LS210 345	74LS281 52	74LS393 230
74LS27 22	74LS157 96	74LS211 345	74LS282 52	74LS394 230
74LS28 22	74LS158 96	74LS212 345	74LS283 52	74LS395 218
74LS29 22	74LS159 96	74LS213 345	74LS284 52	74LS396 215
74LS30 22	74LS160 128	74LS214 345	74LS285 52	74LS397 216
74LS31 22	74LS161 98	74LS215 345	74LS286 52	74LS398 216
74LS32 27	74LS162 138	74LS216 345	74LS287 52	74LS399 230
74LS33 39	74LS163 102	74LS217 345	74LS288 52	74LS400 230
74LS34 39	74LS164 114	74LS218 345	74LS289 52	74LS401 230
74LS35 39	74LS165 114	74LS219 345	74LS290 52	74LS402 230
74LS36 39	74LS166 114	74LS220 345	74LS291 52	74LS403 230
74LS37 39	74LS167 114	74LS221 345	74LS292 52	74LS404 230
74LS38 39	74LS168 114	74LS222 345	74LS293 52	74LS405 230
74LS39 39	74LS169 114	74LS223 345	74LS294 52	74LS406 230
74LS40 28	74LS170 288	74LS224 345	74LS295 52	74LS407 230
74LS42 98		74LS225 345	74LS296 52	74LS408 230
		74LS226 345	74LS297 52	74LS409 230
		74LS227 345	74LS298 52	74LS410 230
		74LS228 345	74LS299 52	74LS411 230
		74LS229 345	74LS300 175	74LS412 230
		74LS230 345	74LS301 175	74LS413 230
		74LS231 345	74LS302 175	74LS414 230
		74LS232 345	74LS303 175	74LS415 230
		74LS233 345	74LS304 175	74LS416 230
		74LS234 345	74LS305 175	74LS417 230
		74LS235 345	74LS306 175	74LS418 230
		74LS236 345	74LS307 175	74LS419 230
		74LS237 345	74LS308 175	74LS420 230
		74LS238 345	74LS309 175	74LS421 230
		74LS239 345	74LS310 175	74LS422 230
		74LS240 345	74LS311 175	74LS423 230
		74LS241 345	74LS312 175	74LS424 230
		74LS242 345	74LS313 175	74LS425 230
		74LS243 345	74LS314 175	74LS426 230
		74LS244 345	74LS315 175	74LS427 230
		74LS245 345	74LS316 175	74LS428 230
		74LS246 345	74LS317 175	74LS429 230
		74LS247 345	74LS318 175	74LS430 230
		74LS248 345	74LS319 175	74LS431 230
		74LS249 345	74LS320 175	74LS432 230
		74LS250 345	74LS321 175	74LS433 230
		74LS251 345	74LS322 175	74LS434 230
		74LS252 345	74LS323 175	74LS435 230
		74LS253 345	74LS324 175	74LS436 230
		74LS254 345	74LS325 175	74LS437 230
		74LS255 345	74LS326 175	74LS438 230
		74LS256 345	74LS327 175	74LS439 230
		74LS257 345	74LS328 175	74LS440 230
		74LS258 345	74LS329 175	74LS441 230
		74LS259 345	74LS330 175	74LS442 230
		74LS260 345	74LS331 175	74LS443 230
		74LS261 345	74LS332 175	74LS444 230
		74LS262 345	74LS333 175	74LS445 230
		74LS263 345	74LS334 175	74LS446 230
		74LS264 345	74LS335 175	74LS447 230
		74LS265 345	74LS336 175	74LS448 230
		74LS266 345	74LS337 175	74LS449 230
		74LS267 345	74LS338 175	74LS450 230
		74LS268 345	74LS339 175	74LS451 230
		74LS269 345	74LS340 175	74LS452 230
		74LS270 345	74LS341 175	74LS453 230
		74LS271 345	74LS342 175	74LS454 230
		74LS272 345	74LS343 175	74LS455 230
		74LS273 345	74LS344 175	74LS456 230
		74LS274 345	74LS345 175	74LS457 230
		74LS275 345	74LS346 175	74LS458 230
		74LS276 345	74LS347 175	74LS459 230
		74LS277 345	74LS348 175	74LS460 230
		74LS278 345	74LS349 175	74LS461 230
		74LS279 345	74LS350 175	74LS462 230
		74LS280 345	74LS351 175	74LS463 230
		74LS281 345	74LS352 175	74LS464 230
		74LS282 345	74LS353 175	74LS465 230
		74LS283 345	74LS354 175	74LS466 230
		74LS284 345	74LS355 175	74LS467 230
		74LS285 345	74LS356 175	74LS468 230
		74LS286 345	74LS357 175	74LS469 230
		74LS287 345	74LS358 175	74LS470 230
		74LS288 345	74LS359 175	74LS471 230
		74LS289 345	74LS360 175	74LS472 230
		74LS290 345	74LS361 175	74LS473 230
		74LS291 345	74LS362 175	74LS474 230
		74LS292 345	74LS363 175	74LS475 230
		74LS293 345	74LS364 175	74LS476 230
		74LS294 345	74LS365 175	74LS477 230
		74LS295 345	74LS366 175	74LS478 230
		74LS296 345	74LS367 175	74LS479 230
		74LS297 345	74LS368 175	74LS480 230

A SELECTION FROM OUR STOCKS OF FULLY GUARANTEED FIRST QUALITY VALVES

1B3GT	0.65	6AX4GTB	1.00	6CY5	1.00	12AT6	0.60	ECF200	0.90	EM84	0.60	PCL81	0.65	PY82	0.55	UCC84	0.75
1R5	0.50	6AX5GT	1.30	6CV7	1.00	12AT7	0.50	ECF201	0.90	EM87	1.00	PCL82	0.80	PY83	0.70	UCC85	0.65
1X2B	1.20	6BA6	0.45	6DD6B	1.45	12AU6	0.65	ECF801	0.95	EY81	0.50	PCL84	0.75	PY88	0.75	UCF80	0.75
5A78	0.80	6BF6	0.48	6DT6	0.80	12AU7	0.47	ECF802	0.95	EY87	0.50	PCL86	0.85	PY500A	1.30	UCH42	0.80
5T4	0.75	6BF5	0.85	6DT8	0.80	12AV6	0.85	ECH42	1.10	EY88	0.55	PCL805	0.75	TT21	7.80	UCH81	0.65
5U4G	0.60	6BF6	0.75	6DW4	0.90	12AV7	1.00	ECH81	0.55	EY500A	1.50	PD510	3.35	TT22	7.00	UCH82	0.70
5U8	0.75	6BG6G	0.30	6ES5	1.00	12AX7	0.55	ECH200	0.80	EZ80	0.50	PL36	1.10	U25	1.00	UCH83	0.80
5V4G	0.60	6BH6	0.85	6EV5	1.50	12AY7	0.85	ECL80	0.60	EZ81	0.50	PL81	0.80	U28	0.50	UCH84	1.00
5X4	0.80	6BJ6	1.20	6EW6	0.80	12BA6	0.65	ECL81	0.75	GY501	0.90	PL82	0.55	UABC80	0.50	UF80	0.50
5X8	0.90	6BJ7	0.65	6GH8A	0.80	12BF6	0.67	ECL82	0.60	GZ30	0.65	PL83	0.50	UAF41	0.50	UF85	0.50
5Y3GT	0.65	6BK4B	1.40	6GK5	0.70	12BH7A	0.75	ECL83	1.15	GZ32	0.65	PL84	0.75	UBC41	0.60	UL84	0.85
5Z4GT	0.65	6BN4A	0.90	6GK6	0.90	12BL6	0.70	ECL84	0.70	GZ33	3.80	PL504	1.05	UBC81	0.60	UM80	0.60
6AB7	0.60	6BN6	0.80	6J4	1.20	12B06	0.90	ECL85	0.65	DA2	0.55	PL508	1.30	UBF80	0.60	UM81	0.75
6AC7	0.80	6BQ7A	0.65	6J5GT	0.80	12BY7A	0.80	ECL86	0.85	DA3	0.75	PL802	2.80	UBF89	0.60	UM84	0.45
6AD8	0.60	6BR8A	1.20	6J6	0.55	12CU6	0.90	EF80	0.40	DB2	0.60	PY81	0.70	UBL21	0.85		
6AF4A	0.80	6BS7	2.30	6J7	0.80	19A05	0.75	EF85	0.48	DB3	0.75						
6AG5	0.65	6BU8	0.85	6K5GT	0.75	19BG6G	0.50	EF86	0.60	DC2	1.40						
6AG7	0.85	6BW7	1.00	6K6GT	0.85	35A3	0.70	EF92	0.75	DC3	0.75						
6AH6	0.95	6BZ6	0.65	6L6GT	0.85	35B3	0.85	EF97	0.70	DD3	0.45						
6AJ5	0.65	6EZ7	0.70	6N7GT	0.85	35C5	0.70	EF98	0.90	PABC80	0.45						
6AK5	0.55	6C4	0.55	6O7	0.90	50C5	1.00	EF183	0.70	PC86	0.85						
6AK6	0.75	6C5GT	0.60	6SA7	0.80	50EH5	0.85	EF184	0.70	PC88	0.50						
6AK7	0.85	6C6	0.50	6SG7	0.80	DAF96	0.60	EFL200	1.20	PC96	0.95						
6AL5	0.40	6C8G	0.60	6SK7	0.80	DF96	0.60	EH90	0.60	PC97	1.00						
6AM6	0.70	6CB6	0.55	6SL7GT	0.70	DK92	1.00	EL33	2.50	PC900	0.50						
6AM8	0.70	6CG7	0.70	6SN7GT	0.70	DL96	0.60	EL36	0.95	PCC84	0.60						
6AN5	2.50	6CG8A	0.75	6SD7	0.80	ECC84	0.60	EL81	0.65	PCC85	0.60						
6AN6	0.85	6CM7	0.80	6SR7	0.80	ECC85	0.48	EL82	0.60	PCC88	0.75						
6AQ5	0.85	6CN7	1.20	6V8GT	0.65	ECC86	1.25	EL83	0.60	PCC89	1.00						
6AS6	1.00	6CQ8	0.75	6X4	0.60	ECC88	0.75	EL84	0.45	PCC189	0.65						
6ASTG	1.20	6CS7	0.85	6X5GT	0.60	ECC89	0.80	EL86	0.75	PCF80	0.45						
6AT6	0.75	6CU5	1.00	6X8	0.80	ECC189	0.80	EL95	0.70	PCF82	0.65						
6AU6	0.50	6CU6	1.00	12A6	0.60	ECF80	0.60	EL504	0.80	PCF84	0.65						
6AV6	0.73	6CW4	3.75	12AL5	0.65	ECF82	0.55	EM80	0.65	PCF86	0.75						
6AW8A	0.75	6CX8	1.00	12AQ6	0.60	ECF86	0.80	EM81	0.60	PCF806	1.00						

OSCILLOSCOPE TUBES


current production. Made in USSR
One inch Tube Type 3L0 11. This tube is a good replacement for 1CP31. Tube characteristics are identical with those of 1CP31. As the connections are different the tube is supplied complete with base, connection diagram and technical data **£12.00***. **Three-inch tube Type 3BP1.** This well known tube used in "PURBECK" Oscilloscope can be supplied for **£7.50*** 14-pin base for the above **£0.80.***

VAT is not included. Please add 12 1/4% on all items except those marked with asterisk, on which VAT is 8%. Postage and packing charges are **£0.10** per £ subject to a minimum of **£0.30**. Minimum order charge for Approved Credit customers **£20.00**. Minimum Transaction Charge for mail orders **£1.00**.

OUR NEW 1978/1979 CATALOGUE IS NOW READY AND WILL BE SENT ON RECEIPT OF REMITTANCE FOR **£0.30**

H.A.C. SHORT-WAVE KITS

WORLD-WIDE RECEPTION

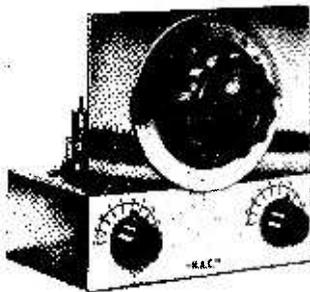

'H.A.C.' well known by amateur constructors for its Short Wave receivers, now offers a complete range of kits and accessories to suit the novice and the expert.

£10.50 INCLUSIVE—the ever popular and easy to construct DX receiver Mark III; containing all genuine short wave components, drilled chassis, valve, accessories and full instructions.

NEW T TWIN TRANSISTOR RECEIVER, selective, sensitive and with fantastic reception, yet needing only a single PP3 battery, at **£12.50** this receiver is outstanding value, and will give you hours of interest and entertainment.


Lastly the K and K plus (illustrated above) for the more advanced constructor. This receiver has recently been re-designed for even better reception. All orders despatched within 7 days. Send stamped and addressed envelope now for free descriptive catalogue of kits and accessories.

SORRY, NO CATALOGUES WITHOUT S.A.E.

"H.A.C." SHORT-WAVE PRODUCTS
P.O. Box No. 16, 10 Windmill Lane
Lewes Road, East Grinstead, West
Sussex RH19 3SZ

PLEASE
MENTION
PRACTICAL
WIRELESS
WHEN
REPLYING
TO
ADVERTISEMENTS

INTER-LOCKING PLASTIC STORAGE DRAWERS

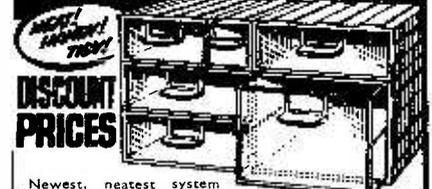

Newest, neatest system ever devised for storing small parts and components: resistors, capacitors, diodes, transistors, etc. Rigid plastic units interlock together in vertical and horizontal combinations. Transparent plastic drawers have label slots. 1D and 2D have space dividers. Build up any size cabinet for wall, bench or table top.

As supplied to Post Office, Industry and Government Depts.

SINGLE UNITS (1D) (5in x 2 1/2in x 2 1/2in). **£3.50 DOZEN.**

DOUBLE UNITS (2D) (5in x 4 1/2in x 2 1/2in). **£5.50 DOZEN.**

TREBLE (3D) **£5.50 for 8.**

DOUBLE TREBLE 2 drawers, in one outer case **(6D2) £7.90 for 8.**


EXTRA LARGE SIZE (6D1) **£6.90 for 8.**

PLUS QUANTITY DISCOUNTS

Orders over **£20**, less 5%. Orders over **£60**, less 7 1/2%.

PACKING POSTAGE CARRIAGE: Add **£1.00** to all orders under **£10**. Orders **£10** and over, please add 10% carriage. Quotations for larger quantities.

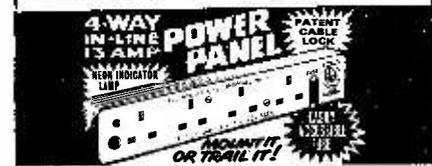
Please add 8% V.A.T. to total remittance. All prices correct at time of going to press.



Modern, slim-line power panel, countless uses in home, office, factory, showrooms. Perfectly safe, unbreakable. Can be mounted on wall or trailed anywhere in room. Neat rubber base. Smart PVC outer cover. White **£3.30** P&P 60p.

FLAIRLINE SUPPLIES (Dept. PW4)
124 Cricklewood Broadway, London NW2
Tel. 01-450 4844

Model TCSU1 Soldering Station

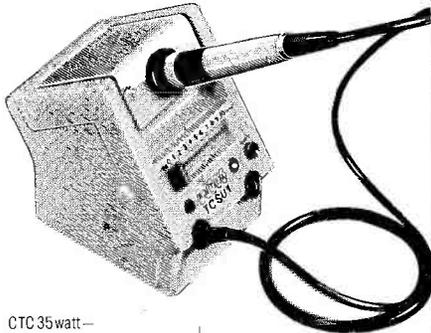

CTC 35 watt—



The TCSU1 soldering station with either the XTC 50 watt—24/26 volt soldering iron or the CTC 35 watt— soldering iron for pin point precision and exceptionally fast recovery time. We have put at least twice as much power into irons which are already well known for good recovery time. The temperature control stops them from over heating; the "fail-safe" electronic circuit provides protection even if the thermocouple fails. TCSU1 soldering station £38.10 XTC and CTC irons £14.85 inclusive of VAT and P & P.

Model CX - 17 watts



A miniature iron with the element enclosed first in a ceramic shaft, then in a stainless steel. Virtually leak-free. Only 7 1/2" long. Fitted with a 3/32" bit. £4.37 inclusive of VAT and P & P. Range of 5 other bits available from 1/8" down to 3/64"

Model X25 - 25 watts




A general purpose iron also with a ceramic and steel shaft to give you toughness combined with near-perfect insulation. Fitted with 1/8" bit and priced at £4.37 inclusive of VAT and P & P. Range of 4 other bits available.

Model SK3 Kit



Contains both the model CX230 soldering iron and the stand ST3. Priced at £6.21 inclusive of VAT and P & P. It makes an excellent present for the radio amateur, modelmaker or hobbyist.


Model SK4 Kit

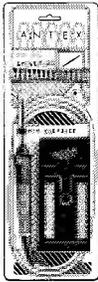

With the model X25/240 general purpose iron and the ST3 stand, this kit is a must for every toolkit in the home. Priced at £6.21 inclusive of VAT and P & P.


Model SK1 Kit

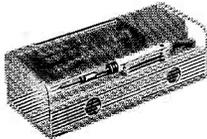This kit contains a 15 watt miniature soldering iron, complete with 2 spare bits, a coil of solder, a heat sink and a booklet. How to solder. Priced at £6.48 inclusive of VAT and P & P.



Model MLX Kit

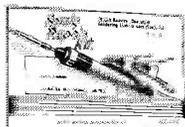The soldering iron in this kit can be operated from any ordinary car battery. It is fitted with 15 feet flexible cable and battery clips. Packed in a strong plastic envelope it can be left in a car, a boat or a caravan ready for soldering in the field. Price £4.83 inclusive of VAT and P & P.



Now heat to any level

between 145° - 400°c

(with accuracy of 2%)



With the Antex TCSC1 Soldering Station

All Antex soldering irons are made on the principle of putting the heating element inside a shaft, then the desired bit is eased over the shaft, offering maximum heat transference, this is why so often a small Antex iron can do the job of a larger conventional iron. The precision made slide on bits are silt to make them easily interchangeable.

The ANTEX multi purpose range of soldering equipment is fast becoming a must for every home. Built with precision for long life, each iron is fully tested and guaranteed.

ANTEX soldering irons are made in England to strict local and international standards of safety.

Stocked by many wholesalers and retailers or direct from us if you are desperate.



Mayflower House, Armada Way,
Plymouth, Devon.
Tel. 0752 67377/8
Telex: 45296

Please send me the Antex colour brochure I enclose cheque/P.O./ Giro No. 258 1000

Please send the following
Name _____
Address _____



Speakers from 1½ inch to 15 inch; megaphone, PA horns, crossovers etc. They're all in our catalogue. Send the coupon now!



A genuine 150W per channel stereo disco to build yourself. Full specification in our catalogue.



Our catalogue even includes some popular car accessories at marvellous prices.



Our catalogue describes a wide range of plugs and sockets, all at marvellous prices. See cat. pages 114 to 129 for details.



61-note touch-sensitive piano to build yourself. Full specification in our catalogue.



A very high quality 40W per channel stereo amplifier with a superb specification and lots of extras. Full construction details in our catalogue.



A digitally controlled stereo synthesiser the 5600S with more facilities than almost anything up to £3,000. Build it yourself for less than £700. Full specification in our catalogue.



A hi-fi stereo tuner with medium and long wave, FM stereo and UHF TV sound! Full construction details in our catalogue.



These are just some of the metal cases we stock. There are dozens of plastic ones to choose from as well. See pages 52 to 57 of our catalogue.

MAPLIN

ELECTRONIC SUPPLIES LTD


All mail to:-
 P.O. Box 3, Rayleigh, Essex SS6 8LR.
 Telephone: Southend (0702) 554155.
 Shop: 284 London Road,
 Westcliff-on-Sea, Essex.
 (Closed on Monday).
 Telephone: Southend (0702) 554155.



Multimeters, analogue and digital, frequency counter, oscilloscopes, and lots, lots more at excellent prices. See cat. pages 106 and 183 to 188 for details.



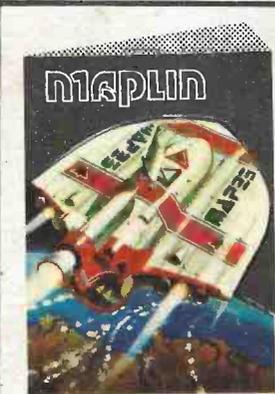A 10-channel stereo graphic equaliser with a quality specification at an unbeatable price when you build it yourself. Full specification in our catalogue.



A massive new catalogue from Maplin that's even bigger and better than before. If you ever buy electronic components, this is the one catalogue you must not be without. Over 280 pages - some in full colour - it's a comprehensive guide to electronic components with hundreds of photographs and illustrations and page after page of invaluable data.

Our bi-monthly newsletter contains guaranteed prices, special offers and all the latest news from Maplin.



A superb range of microphones and accessories at really low prices. Take a look in our catalogue - send the coupon now!

Post this coupon now for your copy of our 1979-80 catalogue price 75p. Please send me a copy of your 280 page catalogue as soon as it is published (8th Jan. 1979). I enclose 75p but understand that if I am not completely satisfied I may return the catalogue to you within 14 days and have my 75p refunded immediately. If you live outside U.K. send £1 or ten International Reply Coupons.

NAME _____

ADDRESS _____