

RADIO... ELECTRONICS... INSTRUMENTS... AUDIO...

# practical WIRELESS

50p

Australia 95c  
New Zealand 95c  
South Africa 90c  
Malaysia \$2.75


JUNE 1979

THE **P**UTRENT

150 W

BROAD-BAND  
LINEAR H.F.

AMPLIFIER  
Part 1

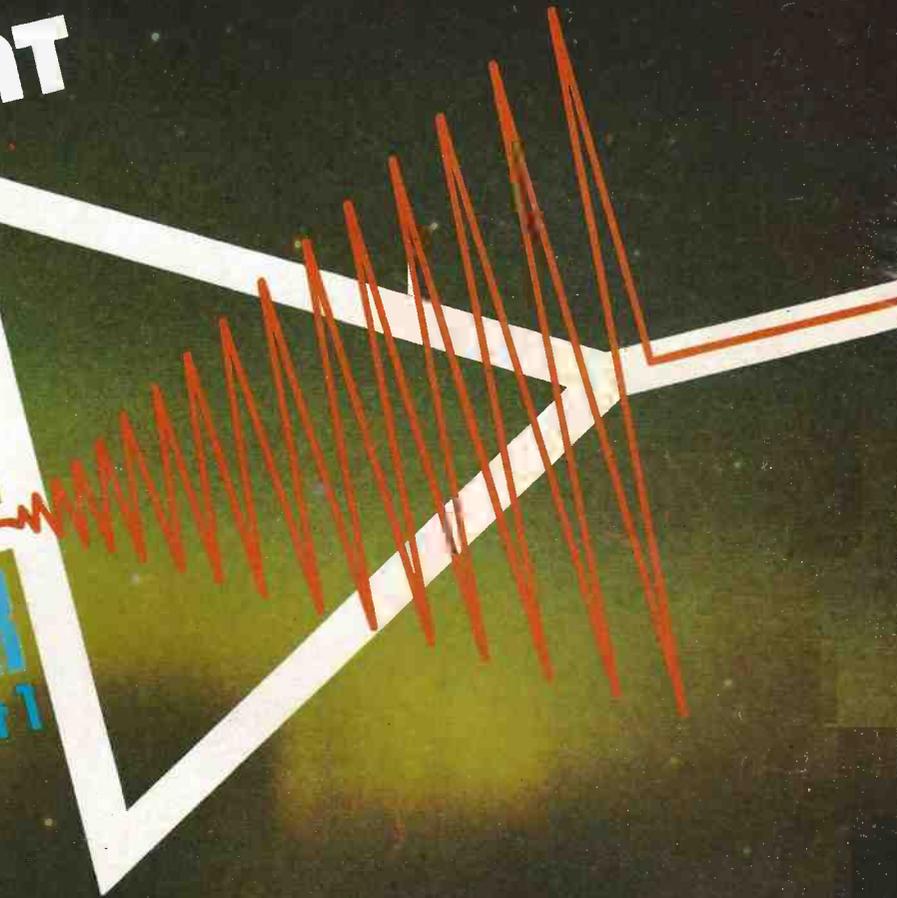

also

JUMBO  
WALL  
CLOCK



**TTL** ★ ★

74100	14p	74109	25p
74101	14p	74118	75p
74102	10p	74120	80p
74103	14p	74121	25p
74104	12p	74122	35p
74105	12p	74123	40p
7406	25p	74125	35p
7407	25p	74126	35p
7408	12p	74128	60p
7410	12p	74130	120p
7411	12p	74131	90p
7412	15p	74132	45p
7413	15p	74133	90p
7414	25p	74136	80p
7415	45p	74138	100p
7416	25p	74141	50p
7420	25p	74142	180p
7421	20p	74143	270p
7422	15p	74144	270p
7423	20p	74145	55p
7424	20p	74147	100p
7425	20p	74148	90p
7426	22p	74150	65p
7427	22p	74151	45p
7428	25p	74152	45p
7430	12p	74153	45p
7432	20p	74154	75p
7433	28p	74156	45p
7437	20p	74157	45p
7438	20p	74160	55p
7440	12p	74161	55p
7441	45p	74162	55p
7442	40p	74163	55p
7443	60p	74164	60p
7444	60p	74165	60p
7445	65p	74166	75p
7446	50p	74167	160p
7447	50p	74170	100p
7448	50p	74173	80p
7449	10p	74174	60p
7451	12p	74175	60p
7453	12p	74176	50p
7454	12p	74177	50p
7460	12p	74178	75p
7470	25p	74179	120p
7472	20p	74180	90p
7473	25p	74181	130p
7474	25p	74182	50p
7475	25p	74184	120p
7476	25p	74185	100p
7480	40p	74188	320p
7481	85p	74191	70p
7482	75p	74192	60p
7483	75p	74193	60p
7484	70p	74194	55p
7485	60p	74195	50p
7486	25p	74196	50p
7489	130p	74197	50p
7490	25p	74198	100p
7491	40p	74199	100p
7492	35p	74203	90p
7493	30p	74204	80p
7494	70p	74S10	18p
7495	45p	74S12	80p
7496	45p		
7497	120p	7805	100p
74100	80p	7812	100p
74104	40p	7813	100p
74105	40p	7815	100p
74107	25p	7818	100p
74108	100p	7824	100p

**POWER SUPPLY CAPACITORS**

2200/16	35p	4700/63	120p
2200/63	80p	4700/70	135p
2200/100	150p	10000/10	100p
3300/30	50p	10000/25	150p
3300/63	90p	15000/15	150p
4700/25	50p	22000/25	200p
4700/40	65p		

ENQUIRIES FOR ANY OTHER TYPES

**CMOS**

4000	12p	4047	80p
4001	12p	4048	50p
4002	12p	4049	25p
4006	80p	4050	25p
4007	14p	4054	100p
4009	30p	4055	130p
4011	12p	4056	120p
4012	12p	4060	100p
4013	30p	4066	35p
4015	50p	4069	12p
4016	30p	4070	12p
4017	50p	4071	12p
4018	55p	4072	12p
4019	40p	4081	12p
4020	50p	4082	12p
4022	40p	4083	70p
4023	12p	4510	60p
4024	40p	4511	70p
4025	12p	4516	65p
4026	80p	4518	65p
4027	30p	4520	65p
4028	45p	4528	80p
4029	50p	4583	70p
4030	30p		
4032	80p		
4033	100p		
4040	60p		
4043	60p		
4046	90p		

**FX1593**  
O/D 12mm, I/D 6mm  
10 for 70p

**TOGGLE SWITCHES**  
SUB MIN  
Single Pole C.O. 85p  
Single Pole C.O. Biased 85p

**RESISTORS 1/3RDW**  
100 of 1 type £1.00p £12 only

**LINEAR**

AY38500	450p	NE556	90p
CA3033	70p	NE562B	40p
CA3064	60p	S AD1024	1500p
CA3066	225p	SL917B	65p
CA3065	200p	SN76003N	150p
CA3076	250p	SN76013N	110p
CA3080	75p	SN76013ND	125p
CA3084	250p	SN76023N	110p
CA3085	85p	SN76023ND	110p
CA3086	60p	SN76033N	150p
CA3088	190p	SN76227N	160p
CA3089	160p	SN766228N	180p
CA3090AO	360p	SN7666DN	75p
CA3123E	130p	TA A350	100p
CA3130	100p	TA A350	190p
CA3140	60p	TA A550	35p
LF356	80p	TA A570	220p
LF357	80p	TA A661B	140p
LM211H	250p	TA A700	350p
LM300TR5	170p	TA A790	350p
LM301AN	30p	TA D100	150p
LM304	200p	TA D110	130p
LM307N	65p	TBA120S	60p
LM308TO5	100p	TBA120T	85p
LM308DIL	100p	TBA480Q	200p
LM309K	100p	TBA520Q	200p
LM310TO5	150p	TBA530Q	200p
LM311TO5	150p	TBA540	200p
LM317K	325p	TBA550Q	250p
LM324	70p	TBA560C	250p
LM339	60p	TBA64A12	
LM348N	90p	TBA700	250p
LM380	60p	TBA720Q	250p
LM381N	90p	TBA750Q	250p
LM392	90p	TBA800	80p
LM391	180p	TBA810	100p
LM555	25p	TBA820	100p
LM709C	40p	TBA920Q	280p
LM710TO5	60p	TC A270Q	220p
LM710DIL	65p	TC A270S	220p
LM723TO5	40p	TC A760	380p
LM730DIL	120p	TC A4500A	450p
LM733	120p	TD A1008	300p
LM741	20p	TD A1034	450p
LM748	40p	TD A2002	300p
LM1303N	100p	TD A2020	300p
LM1458	100p	TL034	120p
LM3080	70p	XR202	250p
LM3900	55p	XR2206	450p
LM3909N	65p	XR2207	450p
MC1310P	140p	XR2208	600p
MC1312P	150p	XR2216	650p
MC1314P	190p	XR2567	250p
MC1315P	230p	XR4136	150p
MM50398	650p	XR4202	150p
MM5314	380p	XR4212	150p
MM5316	480p	ZN414	100p
NE529K	150p	95H90	700p
NE555	25p		

**ELEC CAPACITORS**

0.47/25	7p	47/10	8p
1/16	7p	47/16	8p
1/25	7p	47/25	8p
1/50	7p	47/35	8p
2-2/25	7p	47/50	8p
2-2/35	7p	100/10	8p
3-3/25	7p	100/16	8p
4-7/10	7p	100/25	8p
4-7/16	7p	100/50	8p
4-7/25	7p	100/63	16p
4-7/50	7p	220/16	12p
6-8/25	7p	220/25	14p
10/10	7p	220/50	22p
10/16	7p	330/25	17p
10/25	7p	330/35	18p
22/50	7p	330/50	20p
22/63	7p	470/10	14p
22/10	7p	470/25	19p
22/16	7p	470/35	20p
22/25	7p	470/50	24p
22/35	7p	1000/16	27p
22/50	8p	1000/25	30p
33/63	7p	1000/35	35p
33/16	8p	1000/40	40p
33/25	8p	1000/63	50p
33/40	8p	1200/63	60p
33/50	9p	2200/10	30p

**POLY CAPS**

1000 PF	5p	0.1 uF	6p
2200	5p	0.22 uF	7p
3300	5p	0.33 uF	7p
4700	5p	0.47 uF	9p
6800	5p	1.0 uF	20p
0.01 uF	5p	2.2 uF	25p
0.022 uF	5p	4.7 uF	35p
0.033 uF	5p	6.8 uF	40p
0.047 uF	5p	10 uF	60p

**TANT. BEADS**

0-1/35V	14p	3-3/16V	14p
0-1/53V	14p	4-7/16V	14p
0-22/35V	14p	4-7/25V	14p
0-33/35V	14p	4-7/35V	14p
0-47/10V	14p	6-8/6V3	14p
0-47/35V	14p	6-8/35V	14p
1-00/10V	14p	1-0/35V	14p
1-00/15V	14p	2-2/15V	21p
1-00/35V	14p	3-3/16V	25p
1-5/35V	14p	4-7/3V	20p
2-2/25V	14p	4-7/16V	25p
2-2/35V	14p	100/3V	25p

★ **SPECIAL OFFER** ★  
2000uF 35v 40p 100/£30

**REED INSERTS** One Price  
25MM Long 10 for £1.00p  
50MM Long 10 for £1.00p

**TRANSISTORS**

AA113	10p	BC171	12p	BXD42	50p	BU208	220p
AA217	10p	BC172	12p	BDY10	100p	BY100	25p
AC121	30p	BC177	15p	BF115	20p	BY126	15p
AC126	20p	BC178	15p	BF120	50p	BY127	15p
AC127	20p	BC182	10p	BF121	45p	BY133	25p
AC127/01	25p	BC182L	12p	BF123	45p	BY164	50p
AC128	20p	BC183	10p	BF125	45p	BYX94	90p
AC151	25p	BC183L	12p	BF127	50p	C1130	30p
AC153	30p	BC184	10p	BF137	35p	C1164	20p
AC158K	30p	BC184L	12p	BF154	18p	E100	42p
AC154	30p	BC186	20p	BF160	18p	E300	47p
AC187	20p	BC204	12p	BF161	18p	E310	60p
AC188	20p	BC205	12p	BF173	20p	E420	180p
AC197	35p	BC212	11p	BF178	25p	E430	120p
AC199	35p	BC212L	12p	BF180	30p	MJE340	45p
AC200	35p	BC213	12p	BF181	30p	MPSA05	30p
AC222	40p	BC213L	12p	BF182	30p	MPSA06	32p
AC240	50p	BC214	15p	BF183	25p	MPSA56	30p
AC242	50p	BC214L	15p	BF184	20p	TIP29	35p
AD130	150p	BC237B	15p	BF186	10p	TIP29A	40p
AD143	150p	BC268	16p	BF195	10p	TIP29C	40p
AD149	80p	BC294	30p	BF196	10p	TIP30A	40p
AD161	30p	BC300	25p	BF197	10p	TIP30B	40p
AD162	30p	BC301	25p	BF199	25p	TIP30C	45p
AD163/2MP	70p	BC303	30p	BF199	25p	TIP31	40p
AF114	25p	BC308	15p	BF200	30p	TIP31A	45p
AF115	25p	BC317	12p	BF225	20p	TIP31B	50p
AF116	25p	BC318	12p	BF225	20p	TIP31C	50p
AF118	80p	BC323	30p	BF241	16p	TIP32	40p
AF178	95p	BC329	18p	BF241B	16p	TIP32A	80p
AF199	35p	BC337	15p	BF257	25p	TIP34	70p
AF239	45p	BC338	18p	BF257	25p	TIP35	200p
AF279	50p	BC348	20p	BF259	25p	TIP41A	70p
AU110	180p	BC461	35p	BF271	25p	TIP41B	75p
BA114	12p						

# practical WIRELESS

JUNE 1979  
VOLUME 55  
NUMBER 6  
ISSUE 868

BRITAIN'S LEADING JOURNAL FOR THE RADIO & ELECTRONIC CONSTRUCTOR

Published by IPC Magazines Ltd., Westover House, West Quay Rd., POOLE, Dorset BH15 1JG

## QUERIES

While we will always try to assist readers in difficulties with a *Practical Wireless* project, we cannot offer advice on modifications to our designs, nor on commercial radio, TV or electronic equipment. Please address your letters to the Editor, *Practical Wireless*, at the above address, giving a clear description of the problem and enclosing a stamped self-addressed envelope. Only one project per letter please.

Components are usually available from advertisers. A source will be suggested for difficult items.

## SUBSCRIPTIONS

Subscriptions are available to both home and overseas addresses at £10.60 per annum, from "*Practical Wireless*" Subscription Department, Oakfield House, Perrymount Road, Haywards Heath, West Sussex RH16 3DH.

## BACK NUMBERS AND BINDERS

Limited stocks of some recent issues of *PW* are available at 75p each, including post and packing to addresses at home and overseas.

Binders are available (Price £2.85 to UK addresses or £3.45 overseas, including post and packing) each accommodating one volume of *PW*. Please state year and volume number for which the binder is required.

Send your orders to **Post Sales Department, IPC Magazines Ltd., Lavington House, 25 Lavington Street, London SE1 0PF.**

All prices include VAT where appropriate. Please make cheques, postal orders, etc., payable to IPC Magazines Limited.

## COPYRIGHT

© IPC Magazines Limited 1979. Copyright in all drawings, photographs and articles published in *Practical Wireless* is fully protected and reproduction or imitation in whole or in part is expressly forbidden.

All reasonable precautions are taken by *Practical Wireless* to ensure that the advice and data given to readers are reliable. We cannot however guarantee it and we cannot accept legal responsibility for it. Prices are those current as we go to press.

## NEWS & VIEWS

- 18 **Editorial**  
CB?
- 18 **PW Personality**  
Keith Woodruff
- 19, 30 **News . . . News . . . News . . .**
- 54 **Kindly Note**  
PW "Soundlite", March 1979  
Car Test Probe, May 1979
- 54 **PW at the RSGB Exhibition**
- 60 **Special Product Report**  
Active Antenna AD170, Datong Electronics Ltd.
- 61 **Production Lines** . . . . . Alan Martin  
Information on the latest products
- 70 **RAE Reprint Announcement**

## FOR OUR CONSTRUCTORS

- 20 **Passive 10:1 Divider Probe** . . . . . I. Hickman  
An accessory for the PW "Purbeck" Oscilloscope
- 26 **Logical Noughts and Crosses—2** . . . . . J. D. Mitchell  
Completing the constructional details
- 36 **Jumbo Wall Clock**  
A digital clock design for kitchen, office, etc.
- 46 **Ideas Department**  
Remote aerial pre-amplifier supply
- 47 **PW "Trent" Linear HF Amplifier—1**  
A 150W broadband amplifier for 2–30MHz
- 57 **PW "Winton" Stereo Amplifier—4** . . . . . E. A. Rule  
Connecting up external equipment

## GENERAL INTEREST

- 24 **Student Radio** . . . . . C. Arundel  
A look at campus radio stations
- 33 **Direct Use of Communications Satellites**  
Developments in personal communications
- 43 **A Glance into the Past** . . . . . Chas E. Miller  
Reminiscences from the 1928 BBC Handbook
- 58 **IC of the Month** . . . . . Brian Dance  
The  $\mu$ A78HG variable voltage regulator
- 63 **On the Air**  
Amateur Bands . . . . . Eric Dowdeswell  
MW Broadcast Bands . . . . . Charles Molloy  
SW Broadcast Bands . . . . . Charles Molloy  
VHF Bands . . . . . Ron Ham  
VHF Personalities—The Rennison Brothers . . . . . Ron Ham

**Our July issue will be published on 1 June**  
(for details see page 35)

The background to our cover is a picture of the Aurora Borealis as seen in Scotland during April 1978

# FABULOUS PROFESSIONAL DISCO SYSTEM

ALL THREE UNITS PRODUCED BY BRITAIN'S LARGEST PRODUCERS OF DISCO EQUIPMENT



**FULL RANGE**  
De Luxe 80w  
**SPEAKERS**  
Normally £89.95 each

inc. Pair of  
Powerful 12"  
Bass units  
and High  
Frequency Horn  
**Carr. etc. £15**



# £399

**DEPOSIT £31.95**  
and 38 weekly  
payments of  
**£11.00**  
(Total £449.95)

**INC VAT**

**TURNTABLES:** B.S.R. P200 12SSB Belt-drive with Low-Mass 'S' arm and Magnetic Cartridge or with Garrard 12SSB Decks at £20 extra per system.  
**POWER:** 120 watts continuous RMS into 4 ohms.  
**DECK LIGHTS:** Fully adjustable flexi-beams over each turntable with independent switching.  
**CABINET:** Solidly made to withstand the rigours of transporting. Covered in heavy duty leather cloth type material in attractive colour combinations. Corner cap protectors. Recessed carrying handles.


List £320.76

## F.A.L. De Luxe PROFESSIONAL CONSOLE (Powered)

Slide Fade Controls. Autofade with Music Override on both mic and jingle inputs. Headphone pre-fade monitor with 5 Push-button selector. Illuminated V.U. meters. Illuminated rocker switches. LED cue indicators. Tape or Jingle inputs. unity gain. Mic. channel with Bass & Treble. Slave outlet.

Output into line (Slave)  
Autofade Recovery  
Microphone Input  
Tape/Jingle. 1/P

- OPEN ALL DAY SATS (5 Day-Week)**
- BRADFORD** 10 North Parade (Closed Wed.). Tel. 25349
  - BIRMINGHAM** 30/31 Great Western Arcade. (Closed Wed.). Tel. 021-236 1279
  - CARLISLE** 8 English Street (Closed Thurs.). Tel. 38744
  - COVENTRY** 17 Shelton Sq., The Precinct. (Closed Thurs.). Tel. 25983
  - DERBY** 97 St. Peter's Street (Closed Wed.). Tel. 41361
  - DEWSBURY** 9/11 Kingsway (Closed Tues.). Tel. 468058
  - DONCASTER** 3 Queensgate, Waterdale Centre. (Closed Thurs.). Tel. 63069
  - EDINBURGH** 101 Lothian Rd. (Closed Wed.). Tel. 229 9501
  - GLASGOW** 403 Sauchiehall Street (Closed Tues.). Tel. 041-332 0700
  - HULL** 7 Whitfriargate (Closed Thurs.). Tel. 20505
  - LEICESTER** 32 High Street (Closed Thurs.). Tel. 56420
  - LONDON** 238 Edgware Road, W.2 (Closed Thurs.). Tel. 723 1629

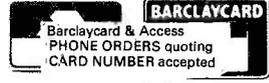

## TITAN GROUP/DISCO SPKRS

	Value	RSC Price
T12/45R 12" 45w	£15.00	£12.95
T12/60R 12" 60w	£22.50	£14.95
T12/100 12" 100w	£36.00	£25.95
T15/70 15" 70w	£28.00	£19.95
T15/100 15" 100w	£41.00	£29.95
T18/100 18" 100w	£51.00	£39.95

Carr. £1-20, under £51, over this add 6p per £1.



Rating RMS  
Imp 8-15Ω

- Prices correct at 9.2.79. E. & O.E. All items subject to availability
- MAIL ORDERS & EXPORT ENQUIRIES TO:—  
AUDIO HOUSE, HENCONNER LANE, LEEDS, 13.  
Tel. 0532 577631.  
MAIL ORDERS MUST NOT BE SENT TO SHOPS  
Phone or Write for FREE CATALOGUE
- ★ **LEEDS**  
16-18 County (Mecca) Arcade, Briggate (Closed Wed.). Tel. 449609
  - ★ **L/POOL** 35 Dawson Wav, St. John's Precinct (Closed Wed.). Tel. 708 9380
  - MIDDLESBROUGH** 103 Linthorpe Rd. (Closed Wed.). Tel. 247096
  - ★ **NEWCASTLE UPON TYNE** 59 Grainger Street (Closed Wed.). Tel. 21469
  - NOTTINGHAM** 19/19A Market Street (Closed Thurs.). Tel. 48068
  - SHEFFIELD** 13 Exchange Street (Castle Mkt. Bldg.) (Closed Thurs.). Tel. 20716
  - ★ **WOLVERHAMPTON** 6 Wulfrun Way (Closed Thurs.). Tel. 26612
- ★ **MUSICAL INSTRUMENTS & ACCESSORIES** in stock at these branches

## New Heathkit electronic test equipment course.

- Section 1. Analogue and digital meters.
- Section 2. Oscilloscopes.
- Section 3. Frequency generation and measurement.
- Section 4. Special measuring instruments.

## New Heathkit car electrical systems course.

- Section 1. Electrical principles of the car.
- Section 2. Starting system fundamentals.
- Section 3. Car charging systems.
- Section 4. Accessories and body electrical.

Two new self-instruction courses from Heathkit. Based on step-by-step programmed instructions, they let you learn at your own pace in your own home.

Each course is complete and contains audio/visual material, text, and parts for 'hands on' experiments with the optional Heathkit experimenter trainer. So all you need is a cassette player and the will to learn.

Full details of Heathkit courses are available in the Heathkit catalogue, together with hundreds of kits you can build for yourself — computers, oscilloscopes, transceivers etc. ... Send for your copy now.

There are Heathkit Electronics Centres at 233 Tottenham Court Road, London (01-636 7349) and at Bristol Road, Gloucester (0452 29451). Registered in England, No. 606177.



## New Heathkit CI 1265 Digital Tach/Speedometer.

Push-button digital readout. Displays engine speed/rpm. Accurate to 1 mph or rpm variations of 100.




To: Heath (Gloucester) Limited, Dept. PW679 Bristol Road, Gloucester, GL2 6EE.  
Please send a copy of the Heathkit catalogue. I enclose 20p in stamps.   
Please send a copy of the Computer Brochure. I enclose 20p in stamps.

Name.....  
Address.....

N.B. If you are already on the Heathkit mailing list you will automatically receive a copy of the latest Heathkit catalogue without having to use this coupon.

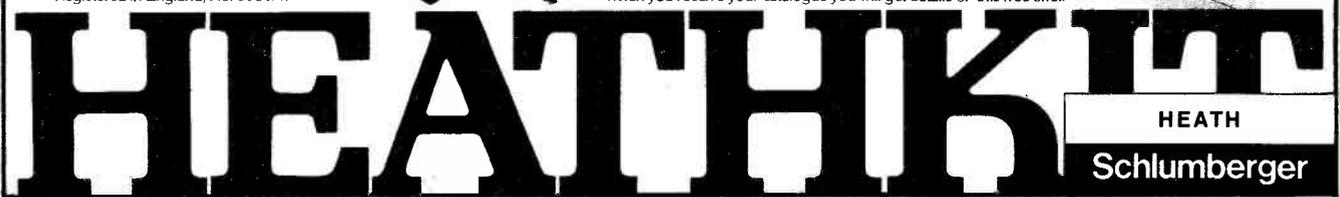When you receive your catalogue you will get details of this free offer.



# LOOK!

## Here's how you master electronics.

### .... the practical way.


This new style course will enable anyone to have a real understanding by a modern, practical and visual method. No previous knowledge is required, no maths, and an absolute minimum of theory.

You learn the practical way in easy steps mastering all the essentials of your hobby or to further your career in electronics or as a self-employed electronics engineer.

All the training can be carried out in the comfort of your own home and at your own pace. A tutor is available to whom you can write, at any time, for advice or help during your work. A Certificate is given at the end of every course.
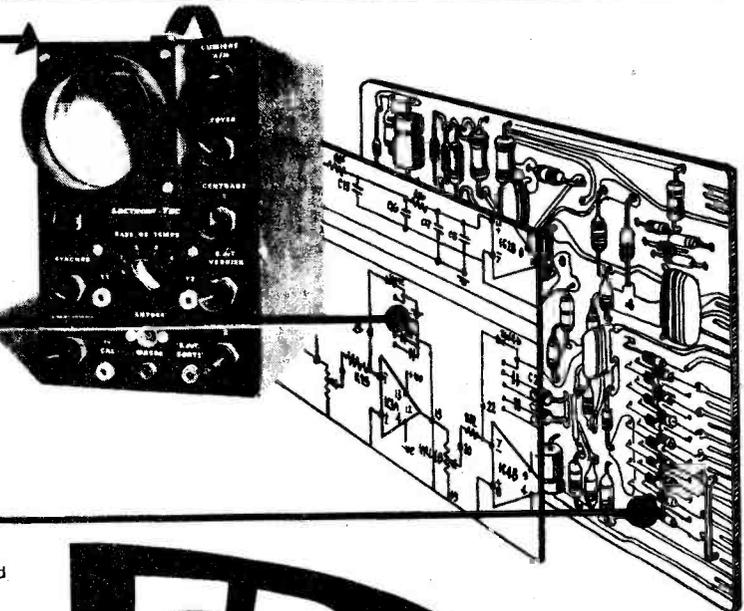
#### 1. Build an oscilloscope.

As the first stage of your training, you actually build your own Cathode ray oscilloscope! This is no toy, but a test instrument that you will need not only for the course's practical experiments, but also for later if you decide to develop your knowledge and enter the profession. It remains your property and represents a very large saving over buying a similar piece of essential equipment.



#### 2. Read, draw and understand circuit diagrams.

In a short time you will be able to read and draw circuit diagrams, understand the very fundamentals of television, radio, computers and countless other electronic devices and their servicing procedures.

#### 3. Carry out over 40 experiments on basic circuits.

We show you how to conduct experiments on a wide variety of different circuits and turn the information gained into a working knowledge of testing, servicing and maintaining all types of electronic equipment, radio, t.v. etc.

#### 4. Free Gift.

All students enrolling in our courses receive a free circuit board originating from a computer and containing many different components that can be used in experiments and provide an excellent example of current electronic practice.



Post now, without obligation, to:-

**BRITISH NATIONAL RADIO & ELECTRONICS SCHOOL**


P.O. Box 156, Jersey, Channel Islands.

NAME \_\_\_\_\_

ADDRESS \_\_\_\_\_

\_\_\_\_\_

Block caps please

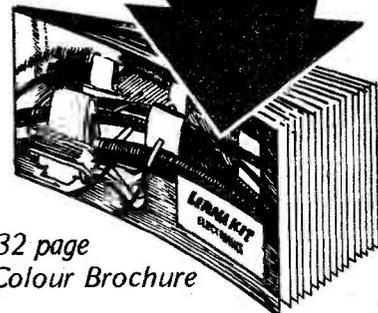

32 page  
Colour Brochure

# Can YOUR Antenna do all this?

A SMALL SELECTION FROM OUR HUGE FILE OF TESTIMONIAL LETTERS ON THE JOYSTICK VARIABLE FREQUENCY ANTENNA (-5-30MHz).

G4DJY's COPY LOG shows 68 North Americans worked in the ARRL WVE contest.

W6TYP worked WA6JPR over hundreds of miles on 40m. using the JOYSTICK VFA and MICROWATTS "equivalent to 1,000,000 MILES PER WATT"—A WORLD RECORD—we can supply conclusive evidence!

"I have used Rhombics,  $4 \times \frac{1}{2}$  waves in phase, centre fed dipoles, etc., but the success I have had with the V.F.A. has been AMAZING... only 20ft. high... in front of my mobile home, I NEVER RECEIVE LESS THAN R7 AND MOSTLY R9 ON CWDX WORKING—Bob Green, SUIK/G3APH, W.B.E., W.A.C. Phone and CW.

W7OE, U.S.A. Government Electronics Engr. (ret'd.), claims "VFA 5ft. below ground, same as dipole, elevated 15ft., one "S" point UP on dipole."

**IN USE BY AMATEUR TRANSMITTING AND SWL STATIONS WORLD-WIDE AND IN GOVERNMENT COMMUNICATION**

## JOYSTICK ANTENNAS

**SYSTEM "A" £41.00**

200 w. p.e.p. OR for the SWL

**SYSTEM "J" £47.95**

500 w. p.e.p. (Improved "Q" on receive)

## "PACKAGE DEALS"

COMPLETE RADIO STATIONS FOR ANY LOCATION

All packages include the JOYSTICK VFA (System "A") 8ft feeder, all necessary cables, matching communication headphones. Delivery Secured our risk. ASSEMBLED IN SECONDS. You SAVE £14.16 on each PACKAGE DEAL!

**PACKAGE No. 1. Features R.300 Rx. £222.00**

**PACKAGE No. 2. Features FRG7 Rx. £237.45**

**PACKAGE No. 3. Features SRX30 Rx. £212.45**

**PACKAGE No. 4. Our "Rolls"—Rx. FRG7000. £402.00**

## RECEIVERS ONLY

**R.300 £184.50 FRG7 £199.95**  
**SRX 30 £174.95 FRG 7000 £364.50**

All prices are correct at time of going to press and include VAT at 12½% and carriage.



Just telephone your card number  
 Phone 0843 62535 (ext. 5)  
 (or 62839 after office hours)



or write for details, send 9p stamp



5, Partridge House, Prospect Road, Broadstairs, CT10-1LD. (Callers by appointment).

## VALVES

A1065	1.25	EF80	0.40	PC900	1.25	SP81	0.85	3E29	5.50	6H6	4.20	12SJ7	0.55
AR8	0.60	EF83	1.50	PCC84	0.45	TT21	7.50	3S4	0.50	6J4WA	1.75	12SD7	0.55
ARP3	0.60	EF85	0.55	PCC89	0.55	U25	1.00	3VA	0.85	6J5	0.75	12YA	0.40
ATP4	0.50	EF86	0.55	PC189	0.65	U29	0.85	5B/2544	6.50	6J5GT	0.50	13BE	0.50
B12H	3.00	EF91	0.85	PCF80	0.80	U191	0.75	5B/258M	6.50	6J7	0.75	19A05	0.75
CY31	0.50	EF92	0.75	PCF82	0.40	U281	0.50	5R4GY	1.10	6J7G	0.50	19G3	10.00
DAF96	0.80	EF95	0.45	PCF86	0.65	U301	0.50	5V4G	0.95	6K7	0.70	19G6	6.00
DET22	19.50	EF183	0.65	PCF200	0.90	U801	0.80	5Y5GT	0.65	6K7G	0.35	19H5	17.00
DF96	0.60	EF184	1.60	PCF201	0.90	UABC80	0.60	EZ3	1.00	6K8GT	0.55	2001	0.50
DH76	0.40	EF804	2.00	PCF801	0.55	UAF42	0.75	5Z4G	0.70	6L6GT	0.90	20L1	1.00
DK95	0.80	EF200	0.75	PCF802	0.65	UFB80	0.55	5Z4GT	0.75	6L18	0.60	20P1	0.40
CV32	0.50	EF92	0.75	PCF805	1.80	UBF89	0.50	6AB7	0.60	6L020	0.50	20P3	0.60
DY86/87	0.55	EL32	0.90	PCF808	1.80	UB1	1.00	6AC7	0.80	607G	0.80	20P4	1.10
DY802	0.55	EL34	2.20	PCM200	0.80	UCB84	0.60	6AK5	0.55	607G	0.85	20R1	1.00
E5L	7.50	EL37	3.00	PCL81	0.60	UCC85	0.50	6AK8	0.40	6SG7	0.75	2524G	0.70
E88 CC/01	1.30	EL41	0.80	PCL82	0.65	UCF80	0.80	6AL5	0.40	6SJ7	0.70	30C15	1.00
E180CC	1.30	EL41	1.00	PCL84	1.70	UCH81	0.60	6AL5W	0.65	6J7GT	0.50	30C17	1.10
E180E	6.00	EL82	0.60	PCL85/85	0.70	UCX82	0.75	6AM5	1.60	6SK7	0.60	30C18	see
E182CC	3.50	EL84	0.60			UF41	0.80	6AM6	0.65	6SL7GT	0.75	PCF805	
EAF76	2.00	EL86	0.95	PL82	0.50	UF80	0.45	6AN8	0.85	6SN7GT	0.75	30F5	1.00
EABC80	0.50	EL90	1.30	PL504	1.30	UF85	0.50	6A05	1.30	6S0T	0.80	30F12	1.20
EB91	0.40	EL91	1.60	PL200	1.35	UL41	0.75	6A05W	0.85	6V6GT	0.80	30F12	1.20
EB33	1.00	EL95	0.70	PL36	0.80	UL84	0.75	6A05W	0.85	6X4	0.60	30F14	1.80
EBF80	0.50	EL104	0.60	PL81	0.75	UM8D	0.60	6A78	0.75	6X5GT	0.55	30L15	1.00
EBF83	0.50	EL102	1.50					6A78	0.75	6Y6G	0.95	30L17	1.00
EBF89	0.50	EL122	3.00					6A78	0.40	6Z4	0.65	30P12	1.00
EC52	0.40	EM31	0.75					6AV6	0.50	6-30L2	0.90	30P13	1.10
EC8R1	0.55	EM80	0.60	PL82	0.50	UM84	0.40	6AX5GT	1.00	7B7	0.80	30P13	1.10
EC8R2	0.50	EM81	0.60	PL83	0.50	UV82	0.55	6B07A	0.60	7V4	0.80	30P14	1.10
EC8R3	1.15	EM84	0.40	PL84	0.65	UY65	0.50	6B7	0.75	902	0.60	35L8GT	1.00
EC8R4	0.45	EM87	1.00	PL504	1.30	VR105/30	1.80	6BA6	0.40	906	0.60	35W4	0.60
EC8R5	0.50	EY51	0.45	PL508	1.30	VR150/30	1.25	6BE6	0.50	10C2	0.75	50C5	0.70
EC8R6	1.25	EY81	0.45	PL509	3.25	X66	0.75	6BG6G	1.00	10F18	0.80	50C6G	1.20
EC8R8	0.60	EY88/87	0.55	PL802	2.80	X61M	1.50	6B16	1.10	11E2	1.10	50C7	0.75
EDC189	0.80	EY88	0.55	PL80	1.80	Z800U	3.00	6B07A	0.60	12A6	0.60	75C1	0.80
ED90	0.50	EZ87	0.60	PY33	0.60	Z801U	3.50	6B7	1.00	12A7E	0.45	78	0.80
EDF82	0.45	EZ81	0.60	PY80	0.60	Z900T	1.50	6C4	0.40	12A7I	0.55	60	0.75
ECF801	0.75	GY501	0.90	PY81/800	0.55	1A3	0.60	6C6	0.55	12A7J	0.50	95A2	2.20
EDH34	0.95	GZ32	3.50	Y82	0.45	1R4	0.30	6CL16	3.00	12AV6	0.70	723A/B	11.00
EDH35	1.50	GZ33	3.50	Y88	0.65	1R5	0.55	6CL6	0.75	12BA6	0.50	803	6.00
EDH42	0.85	GZ34	2.00	Y88	0.65	1S4	0.40	6D5	0.90	12BE6	0.60	805	18.00
EDH81	0.45	EZ87	0.50	Y88	0.65	1S4	0.40	6D6	0.50	12BE6	0.60	807	1.00
EDH84	0.95	KT66	4.00	PY500	1.35	1S5	0.40	6D6	0.50	12BM7	0.60	813	10.50
ECL80	0.60	KT88	5.75	PY859	5.75	1T4	0.40	6EAB	0.80	12C8	0.55	823B	1.00
ECL82	0.55	MH4	1.00	PY801	0.60	1U4	0.60	6F66G	0.75	12E1	4.25	832A	4.50
ED83	1.20	ML6	1.00	QV03-10	2.50	1X2B	1.10	6F86	0.75	12J5GT	0.60	866A	2.80
EDL85	0.65	GA2	0.55	QV03-12	5.50	2D21	0.55	6F12	0.65	12K7GT	0.60	831A	6.00
EDL86	0.55	DB2	0.60	QV06-40A	2K25	11.00	1.80	6F14	0.80	12K8GT	0.70	831A	5.50
EP31A	1.50	PAC80	0.40	14.00				6F15	0.80	1207GT	0.50	955	0.95
EP39	2.90	PC85	0.50	0V03-12	2.00	3A4	0.60	6F17	1.00	1207GT	0.50	955	0.95
EP40	0.70	PC86	0.85	SC1/400	4.00	306	0.40	6F24	0.90	12SC7	0.55	956	0.50
EP41	0.75	PC88	0.75	SC1/600	4.00	3021	20.00	6F33	4.20	12SH7	0.70	957	0.90

Add 12½% for V.A.T.

POSTAGE: £1-£2 20p; £2-£3 30p; £3-£5 40p; £5-£10 60p; over £10 free, minimum order £1.  
 A lot of these valves are imported and prices vary for each delivery, so we reserve the right to change prices for new stock when unavoidable.

**COLOMOR** 907353/  
 (ELECTRONICS) LTD. London  
 170 Goldhawk Rd., London W.12  
 Tel. 01-743 0899  
 Open Monday to Friday  
 9-12.30, 1.30-5.30 p.m.

## CHORDGATE Ltd. SWINDON

Printed Circuit Boards. Add 27p post & packing for 1 to 3 boards. Larger quantities post & packing inclusive

Voltage Tripler P.C.B. contains 40.1 MFD 1000V, 2 pre-sets, 1 bridge rect., 4 IN4007, 9 resistors. 65p.

P.C.B. with GEC, G424 Triac control IC, 2 SGS transistors, three 9 watt WW resistors and 12 other components. 70p.

P.C.B. contains 2 TIP31 (or equiv.), MJE 340 and over 70 other resistors, diodes, zeners, transistors, bridge rect., and capacitors. 50p.

P.C.B. with 8 x BC107, 8 x BCY70, 4 pre-set pot., and over 70 other components. 75p.

P.C.B. contains 2 x 741, 2N4921 and over 40 other components and multitrn 20k pot. 60p.

Parcel of 1 each of above, 6 P.C.B.'s. £3-30.

P.C.B. contains 2 IP 10W Wafer Switches, 2 x 7490 I/C, 2 x 74141 I/C, various Logic I/Cs, IN4148 and over 50 components. 60p.

Post and packing inclusive. Audio Amplifier Boards containing 2 x BFY50, IBFX29 and output pair of 2N5293 output transistors, rated at 36 watts when heatsink mounted £1.75 or 2 for £3.00. Post and packing inclusive.

(Dept B.) 194 A DROVE ROAD, SWINDON, WILTS.

ALL OUR PRICES INCLUDE V.A.T.

**SPECIAL OFFER SEMICONDUCTORS**  
 TB800 50p. LM3400 40p. 741 8 pin 6 for £1.00. NE555 22p. ZN414 75p. IN4005 10 for 35p. 723 REGS 35p. LM340T (6VIA) REGS 40p. BX504 opto isolators 25p. 2N5062 (100V 800MA SCR) 18p.

**MINIATURE TOGGLE SWITCHES.** SPST 8x5x7mm 49p. DPDT 8x7x7mm 53p. DPDT centre off 12x11x9mm 78p. **HEAVY DUTY TOGGLE DPDT** 240V AC 10 amps 35p.

**MINIATURE SOLID STATE BUZZERS.** 33x17x15mm white plastic rectangular case, output at 3 feet 70dB. Low consumption only 15MA, 4 voltage types available, 6-9-12 or 24V DC 75p each. **LOUD BUZZER.** 50mm diameter 6 or 12 volts 60p. **GPO ADJUSTABLE BUZZER.** 6-12V DC 25p.

**DE-SOLDERING TOOL.** Good suction, Teflon nozzle, £4.75p.

**MOTORS.** Miniature model motors 1.5-6V DC 20p. 12V DC 5 pole motors 35p. 8 track replacement motors 12V DC 55p. 'Big inch' tiny precision motor 115V AC 3 rpm 30p. Surplus Clock Motor Synch., 240V AC 1 rev. per hour £1.75p.

**SURPLUS BOARDS.** No. 1 has 14 encapsulated reed relays, 12V £1.95p. No. 2 has 11 50V 2, 5 amp scrs., one relay and various transistors including UJT £1.95p. No. 3 car radio RF/IF boards 2 transistors, LM382 IC trimmers IP's etc. 65p. No. 4 car radio boards with 6 transistors including power output types IP's choke etc. 75p.

**TELEPHONE PICK UP COIL.** Suction type with lead and plug 55p.

Terms - Cash with order (or official orders from schools etc.) Postage 30p. (Overseas at cost) VAT inclusive.

SAE for illustrated lists. **PROGRESSIVE RADIO**  
 93 Dale Street,  
 Liverpool L2 2DY.

# 15-240 Watts!

## HY5 Preamplifier

The HY5 is a mono hybrid amplifier ideally suited for all applications. All common input functions (mag Cartridge, tuner, etc) are catered for internally. The desired function is achieved either by a multi-way switch or direct connection to the appropriate pins. The internal volume and tone circuits merely require connecting to external potentiometers (not included). The HY5 is compatible with all I.L.P. power amplifiers and power supplies. To ease construction and mounting a P.C. connector is supplied with each pre-amplifier.

**FEATURES:** Complete pre-amplifier in single pack—Multi-function equalization—Low noise—Low distortion—High overload—Two simply combined for stereo.

**APPLICATIONS:** Hi-Fi—Mixers—Disco—Guitar and Organ—Public address

**SPECIFICATIONS:**

**INPUTS:** Magnetic Pick-up 3mV; Ceramic Pick-up 30mV; Tuner 100mV; Microphone 10mV;

Auxiliary 3-100mV; input impedance 47kΩ at 1kHz.


**OUTPUTS:** Taps 100mV; Main output 500mV R.M.S.

**ACTIVE TONE CONTROLS:** Treble ± 12dB at 10kHz; Bass ± at 100Hz.

**DISTORTION:** 0.1% at 1kHz. Signal/Noise Ratio 68dB

**OVERLOAD:** 36dB on Magnetic Pick-up. **SUPPLY VOLTAGE:** ± 16-50V.

Price £6.27 + 78p VAT P&P free.

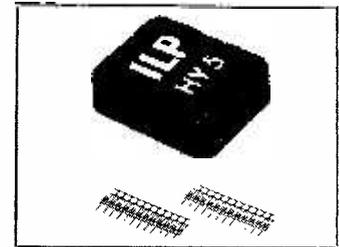

## HY30 15 Watts into 8Ω

The HY30 is an exciting New kit from I.L.P. It features a virtually indestructible I.C. with short circuit and thermal protection. The kit consists of I.C., heatsink, P.C. board, 4 resistors, 6 capacitors, mounting kit, together with easy to follow construction and operating instructions. This amplifier is ideally suited to the beginner in audio who wishes to use the most up-to-date technology available.

**FEATURES:** Complete Kit—Low Distortion—Short, Open and Thermal Protection—Easy to Build.

**APPLICATIONS:** Updating audio equipment—Guitar practice amplifier—Test amplifier—audio oscillator.


**SPECIFICATIONS:**

**OUTPUT POWER:** 15W R.M.S. into 8Ω; **DISTORTION:** 0.1% at 1.5W.

**INPUT SENSITIVITY:** 500mV. **FREQUENCY RESPONSE:** 10Hz-16kHz—3dB.

**SUPPLY VOLTAGE:** ± 18V.

Price £6.27 + 78p VAT P&P free.

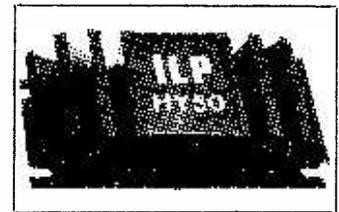

## HY50 25 Watts into 8Ω

The HY50 leads I.L.P.'s total integration approach to power amplifier design. The amplifier features an integral heatsink together with the simplicity of no external components. During the past three years the amplifier has been refined to the extent that it must be one of the most reliable and robust High Fidelity modules in the World.

**FEATURES:** Low Distortion—Integral Heatsink—Only five connections—7 amp output transistors—No external components

**APPLICATIONS:** Medium Power Hi-Fi systems—Low power disco—Guitar amplifier


**SPECIFICATIONS:** **INPUT SENSITIVITY:** 500mV

**OUTPUT POWER:** 25W RMS into 8Ω **LOAD IMPEDANCE:** 4-16Ω **DISTORTION:** 0.04% at 25W

at 1kHz **SIGNAL/NOISE RATIO:** 75dB **FREQUENCY RESPONSE:** 10Hz-45kHz—3dB

**SUPPLY VOLTAGE:** ± 25V **SIZE:** 105 50 25mm

Price £8.18 + £1.02 VAT P&P free

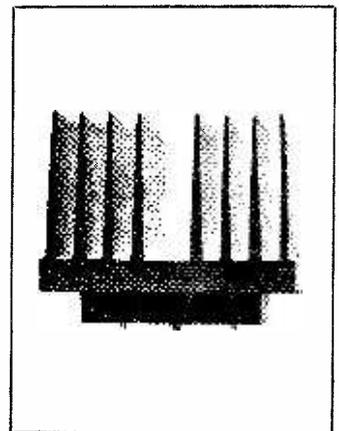

## HY120 60 Watts into 8Ω

The HY120 is the baby of I.L.P.'s new high power range. Designed to meet the most exacting requirements including load line and thermal protection this amplifier sets a new standard in modular design.

**FEATURES:** Very low distortion—Integral heatsink—Load line protection—Thermal protection—Five connections—No external components

**APPLICATIONS:** Hi-Fi—High quality disco—Public address—Monitor amplifier—Guitar and organ

**SPECIFICATIONS:**

**INPUT SENSITIVITY:** 500mV.

**OUTPUT POWER:** 60W RMS into 8Ω **LOAD IMPEDANCE:** 4-16Ω **DISTORTION:** 0.04% at 60W

at 1kHz **SIGNAL/NOISE RATIO:** 90dB **FREQUENCY RESPONSE:** 10Hz-45kHz—3dB **SUPPLY VOLTAGE:** ± 35V

**SIZE:** 114 50 85mm

Price £19.01 + £1.52 VAT P&P free.

## HY200 120 Watts into 8Ω

The HY200 now improved to give an output of 120 Watts has been designed to stand the most rugged conditions such as disco or group while still retaining true Hi-Fi performance.

**FEATURES:** Thermal shutdown—Very low distortion—Load line protection—Integral heatsink—No external components

**APPLICATIONS:** Hi-Fi—Disco—Monitor—Power slave—Industrial—Public Address

**SPECIFICATIONS:**

**INPUT SENSITIVITY:** 500mV

**OUTPUT POWER:** 120W RMS into 8Ω **LOAD IMPEDANCE:** 4-16Ω **DISTORTION:** 0.05% at 100W

at 1kHz **SIGNAL/NOISE RATIO:** 96dB **FREQUENCY RESPONSE:** 10Hz-45kHz—3dB **SUPPLY VOLTAGE:** ± 45V

**SIZE:** 114 50 85mm

Price £27.99 + £2.24 VAT P&P free.

## HY400 240 Watts into 4Ω

The HY400 is I.L.P.'s "Big Daddy" of the range producing 240W into 4Ω! It has been designed for high power disco address applications. If the amplifier is to be used at continuous high power levels a cooling fan is recommended. The amplifier includes all the qualities of the rest of the family to lead the market as a true high power hi-fidelity power module.

**FEATURES:** Thermal shutdown—Very low distortion—Load line protection—No external components.

**APPLICATIONS:** Public address—Disco—Power slave—Industrial


**SPECIFICATIONS:**

**OUTPUT POWER:** 240W RMS into 4Ω **LOAD IMPEDANCE:** 4-16Ω **DISTORTION:** 0.1% at 240W

at 1kHz **SIGNAL NOISE RATIO:** 94dB **FREQUENCY RESPONSE:** 10Hz-45kHz—3dB **SUPPLY VOLTAGE:** ± 45V

**INPUT SENSITIVITY:** 500mV **SIZE:** 114 100 85mm

Price £38.61 + £3.09 VAT P&P free.

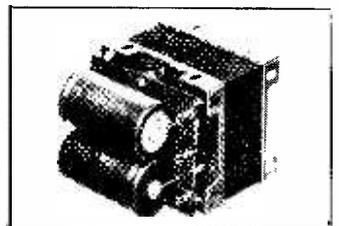

## POWER SUPPLIES

PSU36 suitable for two HY30's £6.44 plus 81p VAT. P/P free.

PSU50 suitable for two HY50's £8.18 plus £1.02 VAT. P/P free.

PSU70 suitable for two HY120's £14.58 plus £1.17 VAT. P/P free.

PSU90 suitable for one HY200 £15.19 plus £1.21 VAT. P/P free.

PSU180 £25.42 + £2.03 VAT.

B1 £0.48 + £0.06 VAT.

P & P FREE IN U.K. ONLY

TWO YEARS' GUARANTEE ON ALL OUR PRODUCTS

I.L.P. ELECTRONICS LTD., GROSSLAND HOUSE, NACKINGTON CANTERBURY, KENT, CT4 7AD.

## I.L.P. ELECTRONICS LTD.,

GRAHAM BELL HOUSE, ROPER CLOSE,  
CANTERBURY, KENT, CT2 7EP.

Tel: (0227) 54778.

Regd No. 1032630.

Please Supply \_\_\_\_\_

Total Purchase Price \_\_\_\_\_

I Enclose Cheque  Postal Orders  Money Order


Please debit my Access account  Barclaycard account

Account number \_\_\_\_\_

Name and Address \_\_\_\_\_

Signature \_\_\_\_\_

### SUPERSOUND 13 HI-FI MONO AMPLIFIER

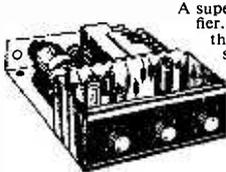

A superb solid state audio amplifier. Brand new components throughout. 5 silicon transistors plus 2 power output transistors in push-pull. Full wave rectification. Output approx. 13 watts r.m.s. into 8 ohms. Frequency response 12Hz 30KHz  $\pm$  3db. Fully integrated pre-amplifier stage with separate Volume, Bass boost and Treble cut controls. Suitable for 8-15 ohm speakers. Input for ceramic or crystal cartridge. Sensitivity approx. 40mV for full output. Supplied ready built and tested, with knobs, escutcheon panel, input and output plugs. Overall size 3" high  $\times$  6" wide  $\times$  7 1/2" deep. AC 200/250V. PRICE £16-00, P. & P. £1-20.

### HARVERSONIC MODEL P.A. TWO ZERO



An advanced solid state general purpose mono amplifier suitable for Public Address system, Disco, Guitar, Gram, etc. Features 3 individually controlled inputs (each input has a separate 2 stage pre-amp). Input 1, 15mV into 47k. Input 2, 15mV into 47k. (suitable for use with mic, or guitar etc.). Input 3 200mV into 1 meg, suitable for gram, tuner, or tape etc. Full mixing facilities with full range bass & treble controls. All inputs plug into standard jack sockets on front panel. Output socket on rear of chassis for an 8 ohm or 16 ohm speaker. Output in excess of 20 watts R.M.S. Very attractively finished purpose built cabinet made from black vinyl covered steel, with a brushed anodised aluminium front escutcheon. For ac mains operation 200/240V. Size approx. 12 1/2" w.  $\times$  5" h.  $\times$  7 1/4" d. Special introductory Price £28-00 + £2-50 carr. & p.k.

### "POLY PLANAR" WAFER-TYPE, WIDE RANGE ELECTRO-DYNAMIC SPEAKER

Size 11 1/2"  $\times$  14 1/2"  $\times$  1 1/2" deep. Weight 19oz. Power handling 20W r.m.s. (40W peak). Impedance 8 ohm only. Response 40Hz-20KHz. Can be mounted on ceilings, walls, doors, under tables, etc., and used with or without baffle. Send S.A.E. for full details. Only £8-40 each + p. & p. (one 90p, two £1-10). Now available in 8" round version. 10 watts RMS 60Hz-20KHz £5-25. P. & P. (one 65p, two 75p).

STEREO MAGNETIC PRE-AMP. Sens. 3mV in for 100mV out. 15 to 35V neg. carth. Equ.  $\pm$  1dB from 20Hz to 20KHz. Input impedance 47K. Size 1 1/2"  $\times$  2 1/2"  $\times$  5 1/2" H. £2-60 + 20p P. & P.

### MAINS OPERATED SOLID STATE AM/FM STEREO TUNER



200/240V Mains operated Solid State FM AM Stereo Tuner. Covering MW A.M. 540-1605 KHz VHF/FM 88-108 MHz.

Built-in Ferrite rod aerial for M.W. Full AFC and AGC on AM and FM. Stereo Beacon Lamp Indicator. Built in Pre-amps with variable output voltage adjustable by pre-set control. Max o/p Voltage 600mV RMS into 20K. Simulated Teak finish cabinet. Will match almost any amplifier. Size 8 1/4" w.  $\times$  4" h.  $\times$  9 1/4" d approx.

LIMITED NUMBER ONLY at £28-00 - £1-50 P. & P.

### 10/14 WATT HI-FI AMPLIFIER KIT

A stylishly finished monaural amplifier with an output of 14 watts from 2 EL84s in push-pull. Super reproduction of both music and speech with negligible hum. Separate inputs for mike and gram allow records and announcements to follow each other. Fully shrouded section wound output transformer to match 3-15  $\Omega$  speaker and 2 independent volume controls, and separate bass and treble controls are provided giving good lift and cut. Valve line-up 2 EL84s, ECC83, EF86 and EZ80 rectifier. Simple instruction booklet 25p + SAE (Free with parts). All parts sold separately. ONLY £15-50, P. & P. £1-40. Also available ready built and tested £20-00, P. & P. £1-40.

### STEREO DECODER

SIZE 2"  $\times$  3"  $\times$  1 1/2" ready built. Pre-aligned and tested for 9-16V neg. earth operation. Can be fitted to almost any FM VHF radio or tuner. Stereo beacon light can be fitted if required. Full details and instructions (including hints and tips) supplied. £6-00 plus 20p P. & P. Stereo beacon light if required 40p extra.

### SPECIAL OFFER

Slightly shop soiled radios by well-known manufacturer for AC Mains or battery use. MW and FM bands. Dynamic M/coil speakers, telescopic aerial and internal ferrite aerial. Earpiece socket for personal listening. Finished in attractive simulated teak. Size 7 1/2" H.  $\times$  9 1/2" W.  $\times$  4" D approx. Fully guaranteed. Bargain Price of only £10-00 + £1-30 p. & p.

### SPECIAL OFFER LIMITED NUMBER ONLY

GOODMANS speakers, 6 1/2" 8 ohm, long throw, ceramic magnet, full range rated 10 watts R.M.S., (when fitted in enclosure). £4-00 each + 80p p&p (p&p on two £1-20).

VYNAIR & REXINE SPEAKERS & CABINET FABRICS app. 54 in. wide. Our price £2-00 yd. length. P. & P. 50p per yd. (min. 1 yd.). S.A.E. for samples.

### HARVERSONIC SUPERSOUND 10 + 10 STEREO AMPLIFIER KIT

A really first-class Hi-Fi Stereo Amplifier Kit. Uses 14 transistors including Silicon Transistors in the first five stages on each channel resulting in even lower noise level with improved sensitivity. Integral pre-amp with Bass, Treble and two Volume Controls. Suitable for use with Ceramic or Crystal cartridges. Very simple to modify to suit magnetic cartridge—instructions included. Output stage for any speakers from 8 to 15 ohms. Compact design, all parts supplied including drilled metalwork, high quality ready drilled printed circuit board with component identification clearly marked, smart brushed anodised aluminium front panel with matching knobs, wire, solder, nuts, bolts—no extras to buy. Simple step by step instructions enable any constructor to build an amplifier to be proud of. Brief specification: Power output: 14 watts r.m.s. per channel into 5 ohms. Frequency response:  $\pm$  3dB 12-30,000 Hz. Sensitivity: better than 80mV into 1M  $\Omega$ ; Full power bandwidth:  $\pm$  3dB 12-15,000 Hz. Bass boost approx. to  $\pm$  12dB. Treble cut approx. to  $\pm$  16dB. Negative feedback 18dB over main amp. Power requirements 35v. at 1-0 amp.

Overall Size 12" w.  $\times$  8" d.  $\times$  2 1/2" h. Fully detailed page construction manual and parts list free with component identification clearly marked. AMPLIFIER KIT or send 25p plus large S.A.E.

POWER PACK KIT £6-00 P. & P. 95p CABINET £6-00 P. & P. 95p

SPECIAL OFFER—only £25-00 if all 3 items ordered at one time plus £1-25 p. & p.

Also avail. ready built and tested £31-25, P. & P. £1-50.

### HARVERSONIC STEREO 44

A solid state stereo amplifier chassis, with an output of 3-4 watts per channel into 8 ohm speakers. Using the latest high technology integrated circuit amplifiers with built in short term thermal overload protection. All components including rectifier smoothing capacitor, fuse, tone control, volume controls, 2 pin din speaker sockets & 5 pin din tape rec./play socket are mounted on the printed circuit panel, size approx. 9 1/2"  $\times$  2 1/2"  $\times$  1" max. depth. Supplied brand new & tested, with knobs, brushed anodised aluminium 2 way escutcheon (to allow the amplifier to be mounted horizontally or vertically) at only £10-00 plus 50p P. & P. Mains transformer with an output of 17v a/c at 500mA can be supplied at £2-00 + 40p P & P if required. Full connection details supplied.

All prices and specifications correct at time of press and subject to alteration without notice.

PLEASE NOTE: P. & P. CHARGES QUOTED APPLY TO U.K. ONLY. SEND SAE WITH ALL ENQUIRIES.

**HARVERSON SUPRUS CO. LTD.** (Dept. P.W.) 170 MERTON HIGH ST., LONDON, S.W.19. Tel.: 01-540 3985  
A few minutes from South Wimbledon Tube Station. Open 9.30-5.30 Mon. to Fri. 9.30-5 Sat. Closed Wed.

## ASTRA-PAK

92 GODSTONE ROAD  
WHYTELEAF SURREY CR3 0EB

All prices include V.A.T. Add 25p for P&P (Extra for overseas). Discounts over £10 less 5%, over £20 less 10%, over £50 less 15%, over £100 less 20%. Send SAE for complete list of components.

7400 0.12 0.21	7484 0.90	74183 0.80 0.82	74368 0.52	20 pin 0.27
7401 0.12 0.21	7485 0.88 0.97	74164 0.89 1.20	74366 0.56	22 pin 0.28
7402 0.12 0.21	7486 0.26	74165 0.89	74350 1.92	24 pin 0.30
7403 0.12 0.21	7488 1.50	74166 0.99	74353 2.00	28 pin 0.44
7404 0.13	7489 2.08	74167 0.99	73670	40 pin 0.55
7405 0.13 0.21	7490 0.35 0.95	74168 2.70	LM645	
7406 0.28	7491 0.85	74170 1.68 1.94	CA3045 -14 0.45	CMOS
7407 0.28	7492 0.44 0.82	74172 4.00	CA3046 -14 0.70	4000 0.14 4067 3.50
7408 0.14 0.21	7493 0.40 0.96	74173 1.18 1.12	LM3800N -14 0.82	4001 0.16 4068 0.24
7409 0.40	7494 0.80	74174 0.89 1.12	LM3811N -14 1.20	4002 0.18 4069 0.17
7410 0.13 0.22	7495 1.05	74175 0.32 1.12	LM7109N -14 0.32	4006 0.92 4070 0.17
7411 0.18 0.21	7497 2.00	74176 0.80	4007 0.18 4071 0.17	4008 0.92 4072 0.17
7412 0.21 0.21	74100 0.84	74177 0.82	MC1310P -14 1.50	4009 0.45 4073 0.17
7413 0.25 0.46	74104 0.40	74178 1.20	NE555N -8 0.30	4010 0.48 4075 0.17
7414 0.54 1.06	74105 0.82	74179 1.10	NE556N -8 0.65	4011 0.15 4076 1.05
7415 0.21	74107 0.28 0.40	74180 0.90	NE2501B -14 2.00	4012 0.16 4077 0.40
7416 0.27	74109 0.46 0.40	74181 1.75 3.38	SN7202N 0.50	4013 0.42 4078 0.22
7417 0.27	74110 0.46	74182 0.75	SN75110N 0.50	4014 0.80 4081 0.17
7420 0.13 0.21	74111 0.70	74183 2.30	SN76033N 1.35	4015 0.77 4082 0.20
7421 0.21 0.21	74112 0.40	74184 0.98	SN76023N 1.35	4016 0.42 4083 0.72
7422 0.17 0.21	74113 0.30 0.40	74185 1.20	SN76033N 1.35	4017 0.77 4086 0.78
7423 0.25	74114 0.40	74186 1.20	TA9550B 0.35	4018 0.87 4089 0.55
7425 0.20	74116 1.80	74188 2.70	TA6818B 1.40	4019 0.42 4093 1.65
7426 0.25 0.28	74118 0.82	74189 0.85	TBA120S 0.64	4020 0.92 4094 1.80
7427 0.25 0.30	74119 1.25	74190 0.95	TBA641A 1.88	4021 0.82 4095 1.10
7428 0.34 0.40	74121 0.82	74191 0.85	TBA930 0.75	4022 0.82 4096 1.10
7430 0.13 0.21	74121 0.25	74192 0.99	TC2705Q 2.00	4023 0.16 4097 3.50
7433 0.30	74122 0.50 0.58	74193 0.95 1.50	TD2420 3.20	4024 0.86 4098 1.12
7434 0.24 0.26	74124 1.25	74194 0.90 2.00	2N414 1.00	4025 0.15 4099 1.90
7437 0.24 0.28	74125 0.40 0.48	74195 0.84 1.00	OP AMPS	4026 1.28 4404 1.00
7440 0.13 0.21	74126 0.45 0.46	74196 0.80	CA1310 -1089 1.00	4027 0.50 4412 0.30
7441 0.62	74128 0.62	74197 0.90 1.15	LM301A -8 0.30	4028 0.87 4428 0.80
7442 0.55 0.70	74132 0.88 0.82	74198 1.48	LM301A -1089 0.46	4029 1.00 4508 2.25
7443 0.90	74134 0.36	74199 1.48	LM348N -14 1.00	4030 0.48 4449 0.30
7444 0.90	74135 0.68	74201 1.50	LM348N -14 1.00	4031 2.34 4501 0.17
7445 0.70	74136 0.55 0.40	74202 1.05	LM709 -8 0.40	4033 1.25 4502 0.88
7446 0.70	74137 0.94	74203 1.05	LM709 -14 0.42	4034 2.00 4507 0.50
7447A 0.60 0.94	74138 0.62	74204 0.95	LM709 -14 0.42	4035 1.00 4508 2.25
7448 0.60 0.94	74139 0.82	74205 1.00 0.95	LM741 -14 0.20	4036 2.40 4510 1.05
7449 0.13	74141 0.58	74206 1.10	LM741 -14 0.20	4037 0.99 4511 0.98
7450 0.13 0.21	74142 2.00	74207 1.12	LM741 -14 0.20	4038 1.00 4512 0.85
7451 0.13 0.21	74143 2.00	74208 0.95	LM741 -14 0.20	4039 2.80 4514 2.85
7453 0.13	74144 2.00	74209 0.95	LM741 -14 0.20	4040 0.98 4515 2.80
7454 0.13 0.21	74145 0.84 1.20	74210 0.95	LM741 -14 0.20	4041 0.77 4516 1.02
7455 0.26	74147 1.30	74211 1.00 0.95	LM741 -14 0.20	4042 0.72 4518 0.90
7456 0.13	74148 1.15	74212 1.05	LM741 -14 0.20	4043 0.82 4519 1.00
7457 0.28	74149 0.98	74213 1.25 0.85	LM741 -14 0.20	4044 0.82 4520 1.05
7472 0.22	74151 0.80 0.90	74214 1.25 0.85	LM741 -14 0.20	4045 1.40 4521 2.00
7473 0.26 0.36	74153 0.60 0.58	74215 1.70 1.00	LM741 -14 0.20	4046 1.32 4522 1.35
7474 0.26 0.38	74154 1.00 1.32	74216 1.70 1.00	LM741 -14 0.20	4047 0.84 4543 0.80
73574 0.50	74155 0.83 0.98	74217 1.70 1.00	LM741 -14 0.20	4048 0.80 4528 0.82
7475 0.30 0.42	74156 0.82 0.98	74218 1.25 0.85	LM741 -14 0.20	4049 0.92 4529 1.10
7476 0.26 0.38	74157 0.83 0.80	74219 1.25 0.85	LM741 -14 0.20	4050 0.42 4536 3.50
7478 0.26 0.38	74158 0.82 0.82	74220 1.25 0.85	LM741 -14 0.20	4051 0.84 4553 4.20
7481 0.90	74159 1.70	74221 1.25 0.85	LM741 -14 0.20	4052 0.84 4555 0.85
7482 0.90	74160 1.30	74222 1.25 0.85	LM741 -14 0.20	4053 0.84 4556 0.85
7483 0.72 0.97	74162 0.80 1.30	74223 1.25 0.85	LM741 -14 0.20	4054 1.10 4558 1.20
		74224 1.25 0.85	LM741 -14 0.20	4055 1.00 4568 1.40
		74225 1.25 0.85	LM741 -14 0.20	4056 1.00 4568 1.40
		74226 1.25 0.85	LM741 -14 0.20	4057 1.00 4568 1.40
		74227 1.25 0.85	LM741 -14 0.20	4058 0.88 4568 1.40
		74228 1.25 0.85	LM741 -14 0.20	4059 0.88 4568 1.40
		74229 1.25 0.85	LM741 -14 0.20	4060 0.88 4568 1.40
		74230 1.25 0.85	LM741 -14 0.20	4061 0.88 4568 1.40
		74231 1.25 0.85	LM741 -14 0.20	4062 0.88 4568 1.40
		74232 1.25 0.85	LM741 -14 0.20	4063 0.88 4568 1.40
		74233 1.25 0.85	LM741 -14 0.20	4064 0.88 4568 1.40
		74234 1.25 0.85	LM741 -14 0.20	4065 0.88 4568 1.40
		74235 1.25 0.85	LM741 -14 0.20	4066 0.88 4568 1.40
		74236 1.25 0.85	LM741 -14 0.20	4067 0.88 4568 1.40
		74237 1.25 0.85	LM741 -14 0.20	4068 0.88 4568 1.40
		74238 1.25 0.85	LM741 -14 0.20	4069 0.88 4568 1.40
		74239 1.25 0.85	LM741 -14 0.20	4070 0.88 4568 1.40
		74240 1.25 0.85	LM741 -14 0.20	4071 0.88 4568 1.40
		74241 1.25 0.85	LM741 -14 0.20	4072 0.88 4568 1.40
		74242 1.25 0.85	LM741 -14 0.20	4073 0.88 4568 1.40
		74243 1.25 0.85	LM741 -14 0.20	4074 0.88 4568 1.40
		74244 1.25 0.85	LM741 -14 0.20	4075 0.88 4568 1.40
		74245 1.25 0.85	LM741 -14 0.20	4076 0.88 4568 1.40
		74246 1.25 0.85	LM741 -14 0.20	4077 0.88 4568 1.40
		74247 1.25 0.85	LM741 -14 0.20	4078 0.88 4568 1.40
		74248 1.25 0.85	LM741 -14 0.20	4079 0.88 4568 1.40
		74249 1.25 0.85	LM741 -14 0.20	4080 0.88 4568 1.40
		74250 1.25 0.85	LM741 -14 0.20	4081 0.88 4568 1.40
		74251 1.25 0.85	LM741 -14 0.20	4082 0.88 4568 1.40
		74252 1.25 0.85	LM741 -14 0.20	4083 0.88 4568 1.40
		74253 1.25 0.85	LM741 -14 0.20	4084 0.88 4568 1.40
		74254 1.25 0.85	LM741 -14 0.20	4085 0.88 4568 1.40
		7		


# BUILD TWO FREE PROJECTS ON CSC

ELECTRONICS BY NUMBERS  
FREE PROJECTS  
NO 1 & NO 2

## ELECTRONICS BY NUMBERS FISH'N'CLIKS

Now using **EXPERIMENTOR BREADBOARDS** and following the instructions in "Electronics by Numbers" ANYBODY can build electronic projects. Look at the diagram, this has the same letter/number system as all EXP BOARDS. Look at the "YOU WILL NEED" list and select Q1 this is PNP transistor type HEP-230. This plugs into hole X9, A7 and C9. NOW take C1, a 50 uF capacitor, and put into holes J6 and J14 and do the same with all the components.

NOW YOU HAVE FISH'N'CLIKS

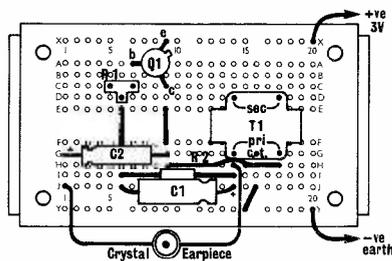

### YOU WILL NEED

- B1, B2 - 2x1.5V AAA batteries
  - C1, C2 - 50 uF, 12-VDC electrolytic capacitor
  - E1 - Crystal earphone
  - Q1 - Motorola HEP-230 pnp transistor
  - R1 - 5000-ohm pot
  - R2 - 27000-ohm, 1/4 watt resistor
  - S1 - Spst switch part of R1
  - T1 - Mini transistor output transformer; 500-ohm center tapped primary to 8-ohm secondary
- EXP - ANY EXP. BREADBOARD.

The anglers dream come true. This electronic marvel emits a CLIK-CLIK sound that makes fish really hungry. Shove the whole works in a watertight container lower it over the side and wait for the fish to grab the hook.

FILL IN THE COUPON AND WE WILL SEND YOU FREE OF CHARGE A COPY OF THE FULL PROJECT FISH'N'CLIKS, AND A COPY OF PROJECT No 1 "TWO TRANSISTOR RADIO".

### PROTO-CLIP TEST CLIPS.

Brings IC leads up from crowded PC boards. Available plain or with cable with clips at one or both ends.



- PC - 16 pin. £2.75.
- PC - 16 pin with cable. £6.00.
- PC - 16 with cable and 16 pin clips at both ends. £10.25.



Europe, Africa, Mid-East: CSC UK LTD.  
Unit 1, Shire Hill Industrial Estate,  
Saffron Walden, Essex CB11 3AQ.  
Telephone: SAFFRON WALDEN 21682.  
Telex: 817477.

## EXPERIMENTOR BREADBOARDS.

No soldering modular breadboards, simply plug components in and out of letter number identified nickel-silver contact holes. Start small and simply snap-lock boards together to build breadboard of any size.  
All EXP Breadboards have two bus-bars as an integral part of the board, if you need more than 2 buses simply snap on 4 more bus-bars with the aid of an EXP.4B.

**EXP.325.** The ideal breadboard for 1 chip circuits.  
Accepts 8,14,16 and up to 22 pin IC's.  
**ONLY £1.60.**




**EXP.350.** £3.15.  
270 contact points with two 20-point bus-bars.




**EXP. 300.**  
550 contacts with two 40-point bus-bars.  
**£5.75.**



**EXP. 650** for Micro-processors. **£3.60.**

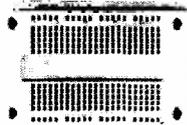

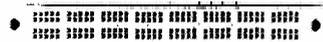**EXP 4B.**  
More bus-bars.  
**£2.30.**



ALL EXP.300 Breadboards mix and match with 600 series.

## PROTO-BOARDS.

THE ULTIMATE IN BREADBOARDS FOR THE MINIMUM COST.  
TWO EASILY ASSEMBLED KITS.



PB.6 Kit, 630 contacts, four 5-way binding posts accepts up to six 14-pin Dips.  
**PROTO-BOARD 6 KIT. £9.20.**



PB.100 Kit complete with 760 contacts accepts up to ten 14-pin Dips, with two binding posts and sturdy base. Large capacity with Kit economy.  
**PROTO-BOARD 100 KIT £11.80.**

### HOW TO ORDER AND RECEIVE FREE COPY OF FISH'N'CLIKS PROJECT WITH BONUS OF FREE TWO TRANSISTOR RADIO PROJECT.

CSC UK LTD. Unit 1, Shire Hill Industrial Estate, Saffron Walden, Essex CB11 3AQ.

It's easy. Give us your name and full postal address, in block capitals. Enclose cheque, postal order or credit card number and expiry date. OR telephone 0799 21682 and give us your Access, American Express or Barclaycard number and your order will be in the post that night.

EXPERIMENTOR BREADBOARDS.	CONTACT HOLES.	IC CAPACITY 14 PIN.DIP.	UNIT PRICE INCLUDING POSTAGE AND V.A.T.
EXP. 325	130	1	£ 2.53
EXP. 350	270	3	£ 4.21
EXP. 300	550	6	£ 7.29
EXP. 650	270	use with 0,6 pitch Dip's Bus-Bar Strip	£ 4.69
EXP. 4B.	Four 40 Point Bus-Bars		£ 3.29
<b>TEST CLIPS</b>			
PC. 16.			£ 3.78
PC.16-18.			£ 7.56
PC. 16-18 Dual Clip.			£12.15
<b>PROTO-BOARDS.</b>			
PB. 6.	630	6	£11.01
PB. 100.	760	10	£13.82

NAME .....

ADDRESS .....

FILL IN COUPON & RECEIVE FREE COPY OF  
ELECTRONICS BY NUMBERS PROJECTS No 1 AND No 2

# ambit international

**PARTS FOR CURRENT PW PROJECTS ... FROM AMBIT INTERNATIONAL**  
**VHF FM monitor RX:** A complete kit of parts for this project, which we firmly believe will be an established "standard" for years to come. The kit includes a 5 channel switched crystal oscillator added to the board end, using diode switching. Uses cheaper 3rd OT crystals, employing original oscillator as x3 stage. Price depends on filter selected (we have various types) and whether or not chip capacitors are required. More notes on the kit from our own lab. £25-£35 kit.  
**VMOS POWER TRANSISTORS FOR PW WINTON** £9.95 pair \* 2SK133/J48  
**FULL KITS FOR THE PW SANDBANKS METAL LOCATOR** (should be ex stock)  
**FULL KITS FOR THE PW DORCHESTER**

## Radio ICs

TDA1062	HF/VHF tunerhead	1.95
TDA1083	One chip AM/FM rx	1.95
TDA1090	One chip HiFi am/fm	3.35
TDA1220	One chip am/fm rx	1.75
HA1197W	HiFi AM tuner IC	1.40
CA3123E	AM tuner IC	1.40
TBA851	AM tuner IC	1.81
CA3089E	Famous FM IF system	1.94
CA3189E	As 3089; deviation mute	1.94
HA1137W	AF preamp, adj, agc	2.75
TBA120	Improved S/N 3089	2.20
TBA120S	limiting amp+detector	0.75
MC1350P	high gain	1.00
MC1350P	agc'd IF preamp	1.20
MC1330P	synch AM/video detector	1.35
KB4406	Cascade IF preamp	0.65
uA753	limiting FM preamp	1.95

## Discrete devices: more than ever:

BF960	800MHz/2.8dB nf mosfet	1.60*
BF961	200MHz/2.0dB nf	0.80*
40822	FM RF amp	0.43*
40823	FM mixer	0.51*
40673	Famous MOSFET	0.55*
2S149/2sK133	120V/100W MOSPOWER	10.50*

## LEDs:

the best value today			
Red	3mm	5mm	2.5x5mm
Green	0.14	0.14	0.17
Yellow	0.18	0.16	0.20
Orange	0.22	0.29	0.24
100 off mix, 25% discount. All are AEG first grade types - absolutely no junk. 5mm clips for panel mounting 0.03 each			

## Misc. ICs for radio/audio applications

U237B	5 LED bargraph driver	0.80*
SA56610	4 station touch tune IC	1.48*
SAS6710	adds 4 stations to 6610	1.48
MSM5523/4	LW, MW, SW and FM digital frequency readout plus clock, timers, stopwatch	£14*
MSM5526	LW/MW/FM DFM with direct drive for LCD	£11*
TC A730	DC volume control	3.50
TC A740	DC tone control	3.50
TDA1028	DC input switch	3.50
TDA1029	DC mode switch	3.50

## Radio and Tuner modules

We cannot really list all the details we would like to here - but with advent of the new mark 3 tuner system, the Dorchester and matching AF units, Ambit offers you the widest choice ever, plus hardware and styling that matches the very high standards we have set in this range.

## Communications circuits

SD6000	DMOS RF/Mixer pair	3.75
KB4412	Bal mixers, IF+agc	2.55
KB4413	AM/SSB det. squelch, agc	2.75
KB4417	mic processor	2.55
MC3257	best thing in NBFM yet	3.12
MC1496P	popular double bal mixer	1.25
<b>Multitex decoders + noise blanker</b>		
MC1210P	popular PLL decoder	2.20
uA758	buffered 1310	2.20
CA3090AQ	RCA PLL decoder	3.25
HA1196	improved PLL decoder with stereo preamps	3.95
HA11223	19kHz pilot cancel, low distortion, high S/N	4.35
KB4437	as HA11223 with remote VCO kill facility	4.55
KB4438	stereo MUTING preamp for post decoder mute	2.22
KB4423	impulse noise blanker	2.53

TERMS etc: CWO please, VAT on Ambit Items is generally 12%, except where marked (\*). Catalogue part 1:45p, part 2 50p all inclusive. Postage 25p per order, carriage on tuner kits £3. Phone Brentwood (0277) 216029/227050 9am-7pm. Callers welcome inc. Saturdays.

## At last, DIY Hi Fi which looks as if it isn't.

That's not to say it doesn't look like HiFi - just that it doesn't look like the usual sort of thing you have come to associate with DIY HiFi. The Mk3 Outstrips and outperforms all British made HiFi tuners, and most imported ones too. Certainly at the price, there isn't one near it. But more than that, it looks superb. A small pic here would be an insult, so send an SAE for details on the kit that looks as if isn't. It's something else.....


- \* Exceptionally high performance - exceptionally straightforward assembly
- \* Baseboard and plug-in construction. Future circuit developments will readily plug in, to keep the MkIII at the forefront of technical achievement
- \* Various options and module line-ups possible to enable an installation approach to the system

and now previewing the matching 60W/channel VMOS amplifier:

- \* Matching both the style and design concepts of the MkIII HiFi FM tuner
- \* Hitachi VMOS power fets - characterized especially for HiFi applications
- \* Power output readily multiplied by the addition of further MOSFETs
- \* VU meters on the preamp - not simply dancing according to vol level
- \* Backed with the usual Ambit expertise and technical capacity in audio

## The PW Dorchester-LW, MW, SW, & FM stereo tuner

THE DIGITAL DORCHESTER ALL BAND TUNER

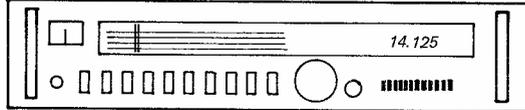

With styling and dimensions to fit in with the rest of AMBIT'S new range of tuner & audio equipment.

When the new range of OKI digital frequency display ICs was announced, the original prototype of the Dorchester had been made - but since so many of you wanted to use the OKI frequency counter/display system with the Dorchester, we quickly designed a unit to incorporate the necessary facilities. The Digital Dorchester is designed in 19 inch form, and forms a perfect match for the other units in the range. If you don't want to go to the expense of the full Ambit DFM1 module, with AM/FM/Time/Timers, then the MA1023 clock module can be used instead.

The Dorchester has been described in PW Dec., Jan. and Feb. issues - but for those of you who may have missed it - it is an All Band broadcast tuner, covering LW/MW/SW and FM stereo in 6 switched ranges. Construction is very straightforward, with all the switching being PCB mounted - and the revolutionary TDA1090 IC used for AM/FM.

The electronics for the radio section of the Dorchester remain unchanged at £33.00, with 12.5% VAT. The hardware package, of case, meter, PSU now costs £33.00 + 8% with the MA1023 available for an extra £5 only.

For the fully digital version, with Ambit DFM1, the price is £56.50 + 8% VAT.

**2 Gresham Road, Brentwood, Essex.**



# Wilmslow Audio

**THE firm for speakers!**

**SEND 15P STAMP FOR THE WORLD'S BEST CATALOGUE OF SPEAKERS, DRIVE UNITS, KITS, CROSSOVERS ETC. AND DISCOUNT PRICE LIST.**

AUDAX ● AUDIOMASTER ● BAKER ● BOWERS & WILKINS ● CASTLE ● CELESTION ● CHARTWELL ● COLES ● DALESFORD ● DECCA ● EMI ● EAGLE ● ELAC ● FANE ● GAUSS ● GOODMAN'S ● I.M.F. ● ISOPHON ● JR ● JORDAN WATTS ● KEF ● LEAK ● LOWTHER MCKENZIE ● MONITOR AUDIO ● PEERLESS ● RADFORD ● RAM ● RICHARD ALLAN ● SEAS ● SHACKMAN ● STAG ● TANGENT ● TANNYO ● VIDEOTONE ● WHARFEDALE ● YAMAHA

**WILMSLOW AUDIO** (Dept. P.W.)

**SWAN WORKS, BANK SQUARE, WILMSLOW, CHESHIRE SK9 1HF**

Discount Hi-Fi Etc. at 5 Swan Street and 10 Swan Street

Speakers, Mail Order & Export 0625 529599 Hi-Fi 0625 526213

**SINCLAIR PRODUCTS** microvision tv word mode £147.95, UK mod £89.95, mains adaptor £6.73, PDM35 £28.95, mains adaptor £3.19, case £3.19, DM350 £68.95, DM450 £97.95, DM235 £49.45, rechargeable batts £7.50, mains adaptor £3.70, case £8.45, enterprise prog calculator with accessories £22.95, cambridge prog calculator £12.13, prog library £4.45.  
**CSC MAX100** freq meter £75.40.  
**CALSCOPE** oscilloscopes send see for data or see the Calscope advert in this magazine. Super 6 £174, Super 10 £236.  
**COMPUTER GAMES** chess challenger 10 £167, chess challenger 7 £79, checker challenger £84, checker challenger 2 £50, Atari videocomputer £138, cartridges £13.45.  
**COMPONENTS** send see for full list. 1N4148 1.4p, 1N4002 2.9p, 741 15p, bc182b, bc183b, bc184b, bc212b, bc213b, bc214c 4.5p, resistors 1W 5% E12 10R to 10M 1p, 0.5p for 50+ of one value, 16V electrolytic .5/1/2/5/10/2uf 5p, 100uf 5p, 1000uf 10p, 1 lb FeCl £1.05, dala pen 7.9p.  
**TV GAMES** send see for data. AY-3-8500 + kit £8.95, rifle kit £4.95, AY-3-8600 + kit £12.50, stunt cycle chip + kit £15.70.  
**IC AUDIO AMPS** with pcb, JC12.6W £1.60, JC20 10W £2.95, send see for data.  
**TRANSFORMERS** 6-0-6v 100ma 74p, 1 1/2 £2.95, 6-3v 1 1/2 £1.89, 9-0-9v 75ma 74p, 1a £2.2a £2.60, 12-0-12v 100ma 90p.  
**BATTERY ELIMINATORS** 3-way type 6/7 1/2v 300ma £2.95, 100ma radio type with press-studs 9v £3.35, 9v-9v £4.50, car converter 12v input, output 4 1/2/6/7 1/2v 800ma £2.50.  
**BATTERY ELIMINATOR KITS** send see for data. 100ma radio types with press-studs 4 1/2v £1.40, 6v £1.40, 9v £1.40, 4 1/2+4 1/2v £1.80, 6+6v £1.80, 9+9v £1.80, stabilized 8-way types 3/4 1/2/6/7 1/2/9/12/15/18v 100ma £2.80, 1Amp £6.40, stabilized power kits 2-18v 100ma £3.60, 2-30v 1A £6.95, 2-30v 2a £10.95, 12v car converter 6/7 1/2v 1a £1.35.  
**T-DEC AND CSC BREADBOARDS** t-dec £4.02, u-deca £4.40, u-decb £6.73, exp300 £6.21, exp350 £3.40, exp325 £1.73, exp4b £2.48.  
**BI-PAK AUDIO MODULES** s460 £23.51, AL60 £4.86, pd10 £16.95, spm80 £4.47, bmt60 £5.95, stereo 30 £20.12, AL30 £3.65, PA12 £7.60, PS12 £1.39, MA60 £35.44.  
**SWANLEY ELECTRONICS Dept. PW, 32 Goldsel Rd., Swanley Kent.** Post 30p extra, prices include VAT. Official and overseas orders welcome.

**PRACTICAL WIRELESS T.V. SOUND TUNER**  
 (Nov. 75 article by A. C. Ainslie) Copy of original article supplied on request  
**IF Sub-Assembly (G8) £7.65. P&P 75p.**  
**Mullard ELC1043 V'cap UHF Tuner £6.19. P&P 35p.**  
**3-way Station Control Unit £1.35. P&P 25p.**  
**6-way Station Control Unit (Special Offer) £1.12.**  
**Power Supply Prtd Circuit Board £1.12. P&P 30p.**  
**Res, Caps, Semiconds, etc. for above £6.53.**  
**Mains Transformer for above £2.81. P&P 30p.**  
 (Price of goods includes 12 1/2% VAT) P&P all items 85p.  
 Callers welcome at shop premises.  
**MANOR SUPPLIES**  
**172 WEST END LANE, LONDON NW6**  
 (Near W. Hampstead Tube Stn.) Tel. 01-794 8751

# OSTS

Since AMBIT introduced the "One Stop Technology Shop" to our service, we have been pleased to see just how many users of electronic components appreciate our guarantee to supply goods only from BS9000 approved sources. More than ever, professional and amateur electronics engineers cannot afford to waste time on anything less than perfect pedigree products.

SEE THE AMBIT AD TOO!

## CD4000 CMOS

4000	17p	4059	563p	4522	149p
4001	15p	4060	115p	4522	157p
4002	17p	4063	109p	4528	102p
4006	109p	4066	53p	4529	141p
4007	18p	4067	400p	4530	90p
4008	80p	4068	25p	4531	141p
4009	58p	4069	20p	4532	125p
4010	58p	4070	20p	4534	614p
4011	17p	4071	20p	4536	380p
4012	17p	4072	20p	4538	160p
4013	55p	4073	20p	4539	110p
4016	52p	4075	20p	4541	141p
4017	80p	4076	90p	4543	174p
4018	80p	4077	20p	4549	399p
4019	80p	4078	20p	4553	440p
4020	93p	4081	20p	4554	153p
4021	82p	4082	20p	4556	77p
4022	90p	4085	82p	4557	386p
4023	17p	4086	82p	4558	117p
4024	76p	4089	150p	4559	388p
4025	17p	4093	50p	4560	218p
4026	180p	4094	180p	4561	65p
4027	55p	4096	105p	4562	530p
4028	72p	4097	372p	4566	159p
4029	100p	4098	110p	4568	281p
4030	58p	4099	122p	4569	303p
4031	250p	4100	90p	4572	25p
4032	100p	4101	90p	4580	600p
4033	145p	4102	90p	4581	319p
4034	200p	4103	90p	4582	164p
4035	120p	4104	105p	4583	84p
4036	250p	4105	95p	4584	100p
4037	100p	4106	95p	4585	100p
4038	105p	4501	23p		
4039	250p	4502	91p		
4040	83p	4503	69p		
4041	90p	4506	51p		
4042	85p	4507	55p	CA3130E	84p
4043	85p	4508	248p	CA3130T	90p
4044	80p	4510	90p	CA3140E	35p
4045	150p	4511	143p	CA3140T	72p
4046	130p	4512	98p	CA3160E	90p
4047	99p	4513	206p	CA3160T	99p
4048	60p	4514	260p		
4049	55p	4515	300p	Op amps	
4050	55p	4516	125p	LM301AH	67p
4051	65p	4517	382p	LM301AN	30p
4052	65p	4518	103p	LM308N	97p
4053	65p	4519	57p	LM308N	97p
4054	120p	4520	100p	LM318H	279p
4055	135p	4521	236p	LM318N	224p

## Micromarket

6800 series	8216	1.95	2114	£10
6800P	8224	3.50	2708	£10.55
6820P	8228	4.78		
6850P	8251	6.25		
6810P	8255	5.40		
6852				
3080 series	2102	£1.70		
8080	2112	£3.40		
8212	2513	£7.54		
	4027	£5.78		

## PRICES SLASHED TTL: Standard AND LP Schottky

N'	LSN'	N'	LSN'	N'	LSN'	N'	LSN'	LSN				
7400	13	20	7455	35	24	74126	57	44	74185	134	74377	124
7401	13	20	7460	17		74128	74		74188	275	74378	93
7402	14	20	7463			74132	73	78	74190	115	74379	130
7403	14	20	7470	28		74133		29	74191		74386	37
7404	14	24	7472	28		74136		40	74192	105	74390	140
7405	18	26	7473	32		74138		60	74193	105	74395	139
7406	38		7474	27	38	74139		60	74194	105	74396	133
7407	38		7475	38	40	74141			74195	95	74398	130
7408	17	24	7476	37		74142	56		74196	99	74399	150
7409	17	24	7478			74143	312		74197	85	74445	92
7410	15	24	7480	48		74144	312		74198	150	74447	90
7411	20	24	7481	86		74145	65		74199	160	74490	140
7412	17	24	7482	69		74147	175		74248		74668	110
7413	30	52	7483A			74148	109		74249		74670	249
7414	51	130	7484	97		74150	99		74251	90	MISCLELLY	
7415	30	24	7485	104	99	74151	64	84	74253	105	NE555	30p
7416	30	24	7486	205	40	74153	64	54	74257	108	NE556	78p
7417	30	24	7489			74154	96		74258	153	NE558	180p
7420	16	24	7490	33	90	74155	54	110	74259	420		
7421	29	24	7491	76	110	74156	80	110	74260	153	ICM7217	950p
7422	24	24	7492	38	78	74157	67	55	74261	353	ICM7208	1495p
7423	27	24	7493	32	99	74158	60	60	74262	40	ICL7106CP	
7425	27	24	7494	78		74159	210		74273	124	LCD DVM IC	
7426	36	27	7495A	65	99	74160	82	130	74275	312	LCD DVM KIT	
7427	27	29	7496	58	120	74161	92	78	74279	52	2480p	
7428	35	32	7497	185		74162	92	130	74283	120	3 1/2 digit LCD	
7430	17	24	74100	119		74163	92	78	74290	90	display	1150p
7432	25	24	74104	63		74164	104		74293	120	ICL7107 LED	
7433	40	32	74105	62		74165	105		74295	120	DVM kit	2065p
7437	40	24	74107	32	38	74166			74298	100	ICM7216	8 digit
7438	33	24	74109	63	38	74167	20		74324	157	10MHz DFM/	
7440	17	24	74110	54		74168			74325	242	timer	£19.82
7441	74		74111	68		74169		200	74326	247	for IEC C.Cath	
7442	70	99	74112	88		74170	230	200	74327	237	(for LEDs)	
7443	115		74113		38	74172	62		74352	100	SCALAR IC	
7444	112		74114		38	74173	70		74353	100	8629 150MHz	
7445	94		74116	98		74174	87	120	74357	100	divide by 100	
7446	94		74118	83		74175	87	110	74362	49	420p	
7447	82		74119	119		74176	75		74366	49	95H90DC	780p
7448	56	99	74120	115		74177	78		74367	43	IC900C	1400p
7449	99	99	74121	25		74180	85		74368	49	1818 new-divide	
7450	17	24	74122	46		74181	165	350	74373	77	100 or 10	
7451	17	24	74123	48		74182	160		74374	77	for 120/60MHz	
7453	17		74124			74183		210	74375	60	450p	
7454	17	24	74125	38	44	74184	135					

## Voltage Regs

**NEW LOW PRICES**

7800 series UC TO220 package 1A all 95p

7900 series UC TO220 package 1A all £1

78MUC series UC TO220 package 1/2A all 90p

78LCP series TO92 100mA all 35p

1700 up to 3A/adjustable V&A 195p

78MGT2C 1/2amp adjustable volts 175p

79MGT2C 1/2amp adjustable volts 175p

723C precision controller 65p

**MAINS FILTERS FOR NOISE/RFI etc**

1 amp in IEC connector £4.83

5 amp in 'wire in' case £3.87

NE550A 73p

## LINEARS non-consumer

**BIMOS**

CA3130E 84p

CA3130T 90p

CA3140E 35p

CA3140T 72p

CA3160E 90p

CA3160T 99p

Op amps

LM301AH 67p

LM301AN 30p

LM308N 97p

LM308N 97p

LM318H 279p

LM318N 224p

## OPTO 7 seg displays

**0.43" High Efficiency HP:**

5082-7650 red CA

5082-7653 red CC

5082-7660 yellow CA

5082-7663 yellow CC

5082-7670 green CA

5082-7673 green CC

**0.3" Standard HP**

5082-7730 red CA

5082-7740 red CC

**0.5" Fairchild**

FDN500 red CC 150p

FDN507 red CA 150p

The ICL7216BIP1 is still the cheapest way to make a full 8 digit/ 10MHz frequency counter/timer, and with 10 external components + display - it is also one of the simplest. For £19.82, it takes a lot of beating. The mains filters have been extended now to include a 6amp IEC version at £5.10, and with the amount of electronic noise on the average supply (next door's fridge, for instance) it is a really worthwhile addition to any sensitive equipment. LPSN TTL now includes many more of latest types, all of course - are absolutely prime first quality types. And don't forget our range of OPTO displays includes Hewlett Package high efficiency 0.43" types in all colours - renowned as the finest quality in the market. For other types of component - discrete LEDs, radio and audio devices, tuner modules, kits etc., see our other advertisement for more details - or send for the AMBIT catalogue system. Part one (45p) includes details of our background 'standard' items, and the new part two includes all the latest introductions and developments, plus a rundown on OSTs.

TERMS: CWO pss., VAT to be added at 8% (inland), pp 25p per order. When ordering from the OSTs and Ambit - a single combined remittance and pp charge is sufficient. Account details O.A.

**2 Gresham Road, Brentwood, Essex.**

**SOUTHERN VALVE CO.** SECOND FLOOR, 6 POTTERS ROAD, NEW BARNET, HERTS. MAIL ORDER ONLY. MINIMUM ORDER 80p Telephone 01-440/8641

Some leading makes available. VAT invoices issued on request. Do NOT carry any guarantee, Enquire prices.

NOTE: PLEASE VERIFY CURRENT PRICES. Correct only at time of going to press.

DY86/7	55p	EF86	55p	GY501	£1.40	PCF802*	£2.75	PL36	£1.00	PY500A	£1.80
DY802	55p	EF89	75p	PC86	80p	PCF805	£2.75	PL81A	70p	UBF89	50p
ECC81	60p	EF183	55p	PC88	80p	PCF806	75p	PL83	46p	UC885	55p
ECC82	63p	EF184	55p	PC97	75p	PCF808	£1.75	PL84	50p	UC881	60p
ECC83	63p	EH90	60p	PC90	65p	PCL82	65p	PL5001	£1.20	UC182	75p
ECC85	63p	EL34	£1.85	PC84	63p	PCL83	£1.00	PL5004	£1.70	UC183	95p
ECC81	55p	EL84	52p	PCC85	55p	PCL84	70p	PL5008	£1.70	UC189	55p
ECC84	85p	EL509	£3.00	PCC89	55p	PCL805	55p	PL5009	£3.05	UL41	95p
ECL80	52p	EM84	90p	PC189	50p	PCL85	55p	PL519	£3.30	UL84	90p
ECL82	55p	EB86-7	48p	PCF80	80p	PCL86	55p	PL802*	£2.90	UY86	60p
ECL86	72p	EY500A	£1.65	PCF86	60p	PCL200	£1.45	PV83	90p	U25	60p
EF80*	45p	EZ80	43p	PCF200	£1.60	PD500	£3.70	PY800	65p	U26	60p
EF85	45p	EZ81	45p	PCF801	60p	PFL200	£1.35	PY801	65p		

We offer return of post service. CWO ONLY, No C.O.D. Post free over £20. £0 to £20-80p (max). MANY OTHERS AVAILABLE

Items in stock at time of going to press but subject to possible market fluctuations. If unavoidable. One valve post 15p, each extra valve 6p. Large valves 2p each extra. Min. order 80p.

**STOP PRESS!** STOCKISTS UHF "MICRO" AERIAL! SIZE 1 1/2"x3" only £3.70p incl. ENQUIRIES WELCOME FROM TRADE AND RETAIL (same prices)

★ BARGAIN BUYS ★

from **GREENWELD** 443B Millbrook Road Southampton SO1 0HX Tel: (0703) 772501/783740

**SN76110 Stereo decoder 75p; 25/£15**

**100/£45.**

**BC184 Preformed for T05 spacing 100/£4.50 1000/£30.**

**BC213L straight leads 100/£5 1000/£33.**

**2N5060 0-8A SCR 30V. Ig 200uA 10/£2 100/£15 1000/£120.**

**1N4148, bandioliered 1000/£15 2500/£32 10,000/£90.** Loose, boxes of 10k/£75.

**741 8D1L 10/£1-80 100/£14-50.**

**555 8D1L 10/£2-40 100/£19-50.**

**1N4003 100/£2-90 1000/£24.**

**1N4007 100/£4-90 1000/£44.**

**Electrolytics: 10u40V PC mntg 25/£1-25 100/£3; 4.7u/63V V.P.C mntg, 1u/63V H.P.C mntg same price.**

**1250u/25V can 10/£1-60 100/£10.**



# Handy size reels and dispensers

of the world's finest cored solder to do a professional job at home

Ersin Multicore Solder contains 5 cores of non-corrosive flux that instantly cleans heavily oxidised surfaces and makes fast, reliable soldering easy. No extra flux is required.



handy size reels of **SAVBIT, 40/60, 60/40 and ALU-SOL** solder alloys

These latest Multicore solder reels are ideal for the toolbox. Popular specifications cover all general and electrical applications, plus a major advance in soldering aluminium. Ask for a free copy of 'Hints on Soldering' containing clear instructions to make every job easy.

Ref.	Alloy	Diam. (mm)	Length metres approx.	Use	Price inc. VAT
Size 3	40/60 Tin/Lead	1.6	10.0	For economical general purpose repairs and electrical joints.	£2-81
Size 4	ALU-SOL	1.6	8.5	For aluminium repairs. Also solders aluminium to copper, brass etc.	£2-81
Size 10	60/40 Tin/Lead	0.7	39.6	For fine wires, small components and printed circuits.	£2-81
Size 12	SAVBIT	1.2	13.7	For radio, TV and similar work. Increases copper-bit life tenfold.	£2-81



**SAVBIT**  
handy solder dispenser  
Contains 2.3 metres approx. of 1.2mm Ersin Multicore Savbit Solder. Savbit increases life of copper bits by 10 times.  
**Size 5 65p inc. VAT**

For soldering fine joints

Two more dispensers to simplify those smaller jobs. PC115 provides 6.4 metres approx. of 0.71mm solder for fine wires, small components and printed circuits.  
**78p inc. VAT**

Or size 19A for kit wiring or radio and TV repairs. 2.1 metres approx. of 1.2mm solder.  
**Size 19A 69p inc. VAT**

Sole U.K. Sales Company for the  
**Bib Hi-Fi Accessories Limited,**  
Kelsay House, Wood Lane Erd  
Hemel Hempstead, Herts. HP2 4RQ

Prices shown are recommended retail inc. VAT.  
Transistors and Diodes are shown at special prices.  
Some diodes plus 20p P & P. Prices and special features subject to change without notice.

## SOLDERING FLUX PASTES

'ERSIN' A non-corrosive, rosin based flux for general and electrical soldering in conjunction with 'Ersin' Multicore solders.  
**Ref RF10 52p inc. VAT**

'ARAX' For general metal joining in conjunction with 'Arax' Multicore solders.  
**Ref AF14 52p inc. VAT**

## BIB WIRE STRIPPER and CUTTER

Fitted with unique 8-gauge selector and handle locking device. Sprung for automatic opening. Strips flex and cable in seconds.  
**Model 8B £1-21 inc. VAT**  
Pat. No. 144913

## EMERGENCY SOLDER

Self-fluxing, tin/lead solder tape that melts with a match. For electrical and non-electrical applications.  
**Size ES36 48p inc. VAT**

## MULTICORE DESOLDERING WICK

Absorbs solder instantly from tags, printed circuits, etc. Only needs 40-50 watt soldering iron. Quick and easy to use.  
Non-corrosive. **Size AB10 £1-14 inc. VAT**

## ECONOPAK

A reel of 1.2mm 'Ersin' Multicore solder for general electrical use.  
**Size 13A £2-61 inc. VAT**

A reel of 3mm 'Arax' Multicore solder for general non electrical use.  
**Size 16A £2-61 inc. VAT**

TTLs BY TEXAS				LINEAR I.C.s				TRANSISTORS				DIODES																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																					
7400 13p	7497 180p	74221 160p	74LS192 140p	74C157 250p	LM311 19p	*MC1496 100p	AC127/8 20p	BFY51/2 22p	TIP42A 79p	2N3886 90p	1N4001 12p	1N4002 12p	1N4003 12p	1N4630 12p	1N4631 12p

## MAINS TRANSFORMERS

All these have 230/240V 50Hz  
All these have 230/240V 50Hz Primary

Voltage	Our Ref.	Price	Post
1v	2 amp	<b>£1.96</b>	<b>40p</b>
2-4v	TM 2	<b>£1.62</b>	<b>45p</b>
4v	7 amp	<b>£2.70</b>	<b>60p</b>
6v	1 amp	<b>85p</b>	<b>40p</b>
6-5v	TM 37	<b>85p</b>	<b>40p</b>
6-5v	200 mA	<b>£1.62</b>	<b>40p</b>
6-5v-0-6-5v	100 mA	<b>£1.62</b>	<b>40p</b>
6-5v-0-6-5v	750 mA	<b>£2.16</b>	<b>45p</b>
6-3-0-6-3v	100 mA	<b>£1.62</b>	<b>40p</b>
6-3v	2 amp	<b>£1.89</b>	<b>50p</b>
8-5v	1 amp	<b>£1.62</b>	<b>40p</b>
8-5-8-5v sep. winding	1 amp	<b>£1.62</b>	<b>40p</b>
9v	1 amp	<b>£1.62</b>	<b>45p</b>
9v	1 amp	<b>£1.62</b>	<b>45p</b>
9v	5 amp	<b>£2.70</b>	<b>60p</b>
10v	25 amp	<b>£4.86</b>	<b>£1.25</b>
10v-0-10v	4 amp	<b>£3.78</b>	<b>£1.25</b>
10v-0-10v	12 amp	<b>£4.86</b>	<b>£1.25</b>
12v	1 amp	<b>£1.05</b>	<b>50p</b>
13v	100 mA	<b>£1.62</b>	<b>40p</b>
13v	1 amp	<b>£2.16</b>	<b>50p</b>
12v	1 amp	<b>£1.89</b>	<b>50p</b>
12v-0-12v	50 mA	<b>£1.62</b>	<b>40p</b>
12v-0-12v	1 amp	<b>£2.16</b>	<b>45p</b>
15v tapped 9v	2 amp	<b>£1.62</b>	<b>50p</b>
17v	1 amp	<b>£1.62</b>	<b>50p</b>
18v	1 amp	<b>£1.90</b>	<b>50p</b>
20v	1 amp	<b>£1.62</b>	<b>50p</b>
20v (with 6v 1/2 amp)	2 amp	<b>£3.78</b>	<b>£1.25</b>
20v	6 amp	<b>£4.32</b>	<b>£1.25</b>
20v	12 amp	<b>£4.86</b>	<b>£1.25</b>
20v-0-20v	6 amp	<b>£4.86</b>	<b>£1.25</b>
24v	1 amp	<b>£2.16</b>	<b>60p</b>
24v	2 amp	<b>£2.70</b>	<b>60p</b>
24v+2v 7 amp	2 amp	<b>£2.97</b>	<b>70p</b>
24v	4 amp	<b>£3.78</b>	<b>80p</b>
25v	1 1/2 amp	<b>£2.43</b>	<b>60p</b>
28v	2 amp	<b>£2.88</b>	<b>60p</b>
30v	8 amp	<b>£4.86</b>	<b>£1.25</b>
37v	37 amp	<b>£31.86</b>	<b>enquire</b>
40v	3 amp	<b>£4.32</b>	<b>£1.25</b>
40v	5 amp	<b>£5.02</b>	<b>£1.25</b>
40v	6 amp	<b>£4.86</b>	<b>£1.25</b>
40v-0-40v	2 1/2 amp	<b>£5.02</b>	<b>£1.25</b>
50v & 6-3v	2 amp	<b>£2.70</b>	<b>£1.25</b>
50v	8 amp	<b>£4.86</b>	<b>£1.25</b>
60v tapped 40v & 20v	2 amp	<b>£4.32</b>	<b>£1.25</b>
70v	4.5 amp	<b>£2.70</b>	<b>£2.50</b>
75v and 63v	3 amp	<b>£3.18</b>	<b>£2.00</b>
75v	4 1/2 amp	<b>£2.70</b>	<b>£2.50</b>
80v tapped 70v & 75v	4 amp	<b>£2.70</b>	<b>£2.50</b>
80v centre tapped	2 1/2 amp	<b>£5.02</b>	<b>£1.25</b>
100v	1 amp	<b>£2.70</b>	<b>£1.75</b>
100v-0-100v	1 amp	<b>£2.70</b>	<b>£1.75</b>
200v	1 amp	<b>£2.70</b>	<b>£1.75</b>
250v-0-250v & 6-3v	50 mA	<b>£3.78</b>	<b>£1.00</b>
000v	100 mA	<b>£3.78</b>	<b>£1.00</b>
500v	50 mA	<b>£3.78</b>	<b>£1.00</b>
260v	60 mA	<b>£3.24</b>	<b>£1.00</b>
1000v	60 mA	<b>£6.50</b>	<b>£2.00</b>
4 kv	5 mA	<b>£4.05</b>	<b>70p</b>
5 kv	5 mA	<b>£7.02</b>	<b>£1.00</b>
8 kv	5 mA	<b>£4.05</b>	<b>£1.00</b>
8-5 kv	10 mA	<b>£10.26</b>	<b>£2.00</b>

Full range of Mains to 120v Auto transformers available.  
**Pot Cores.** We have now received our delivery of Ferro pot cores. These are ex unused and are of the bobbin type but of course these have to be wound and you would have to unwind. Three pairs available.

Diameter	Thickness	Price	per pair
FX 2243	4-5 cm	3-0 cm	81
FX 2242	3-5 cm	2-3 cm	70
FX 2240	2-5 cm	1-6 cm	60

Quantity discounts apply.  
**Component Panel Ref. 3055.** Taken from unused P.S.U.'s, these contain 4 x 2N-3055 power transistors with mica insulators all on heat sink and 4 variable pots, preset type with spindle locks. Real bargain at **£1-08** each.

**Component Board 421.** Again from unused equipment, major items on these are two power silicon transistors, Motor Rola ref. SJ 5433 mounted on a heat sink with mica insulators, also behind the panel are two power rectifiers ST NS 100B. Price **98p**.

**E.H.T. Mains Transformer.** With inductance control, normal primary and output voltage approx. 300-350V. Voltage can be varied by applying DC to lower bobbin. Unused, ex P.S.U.'s Price **£4-32**.

**Music Centre Dust Cover.** Size 12" x 10" x 1 1/2" with attachments for hinging. Price **£3-95**. Callers only.

**Telephone Answering Machines.** Used but apparently complete and probably in working order. However, we are allowed to supply these only for breaking up, they should be very suitable for conversion to open reel tape recorder, background music machine, echo chamber, etc. All untested but we guarantee to replace any major item in the machine should it be faulty. Machines less outer case **£7-50**, case slightly broken but substantially whole **£10-26**. Unbroken cases **£12-45**, and finally with new looking cases **£14-50**. Post **£2-50** per machine. Many accessories available for these machines. Please enquire.

**Wall Mounting Thermostat.** The Satchwell room stat. Mains 20 amp settable over normal air temperatures between 30-80°F, suitable also for greenhouse control. Nicely finished in white enamel. Price **£3-25**.

**10 r.p.m. Motor** with 230v mains coil, not like the usual of these geared motors this has a good length of 3/4" shaft. Price **£2-50 + 20p**.

**Rigonda Intermazzo 10** - 10 hi-fi amplifier with belt driven record deck with speed control and auto check. The best hi-fi offered by Rigonda original selling price was in excess of **£125**. We have approx. 50 of these unused but with various faults. Untested, believed complete except for cartridge and speakers. Offered at **£33-50**, less than the price of the very high quality deck incorporated. If cannot collect add **£3-00** to cover the special packing and carriage charge.

## MINI-MULTI TESTER

Amazing, deluxe pocket size precision moving coil instrument—jewelled bearings—1000 opv—mirrored scale.  
11 instant ranges measure:—  
DC volts 10, 50, 250, 1000.  
AC volts 10, 50, 150, 1000.  
DC amps 0-1 mA and 0-100 mA.  
Continuity and resistance 0-150K Ohms.  
Complete with insulated probes, leads, battery, circuit diagram and instructions.  
Unbelievable value only **£6-50 + 50p** post and insurance.

## MULLARD UNILEX

A mains operated 4-4 stereo system. Rated one of the finest performers in the stereo field this would make a wonderful gift for almost anyone in easy-to-assemble modular form and complete with a pair of Plessey speakers this should sell at about £30—but due to a special bulk buy and as an incentive for you to buy this month we offer the system complete at only **£15** including VAT and postage.



## 24 HOUR TIMERS

As illustrated with sun correction made for G.P.O. phone boxes used perfect **£2-95** 20 amp switching contacts.

## SHORTWAVE CRYSTAL SET

Although this uses no battery it gives really amazing results. You will receive an amazing assortment of stations over the 19, 25, 29, 31 metre bands. Kit contains chassis front panel and all the parts **£1-94**—crystal earphone **55p** including VAT and postage.

## SOUND TO LIGHT UNIT

Add colour or white light to your amplifier. Will operate 1, 2 or 3 lamps (maximum 450W). Unit in box ready to work. **£9-95**.

## BREAKDOWN PARCEL

Four unused, made for computer units containing most useful components, and these components unlike those from most computer panels, have wire ends of usable length. The transistors for instance have leads over 1" long—the diodes have approx. 1/2" leads.

List of the major components is as follows:— 17 assorted transistors—38 assorted diodes—60 assorted resistors and condensers—4 gold plated plugs in units which can serve as multipin plugs or as hook up boards for experimental or quickly changed circuits (note we can supply the socket boards which we made to receive these units). The price of this four unit parcel is **£1** including VAT and post (considerably less than value of the transistors or diodes alone). DON'T MISS THIS SPLENDID OFFER.

## TANGENTIAL HEATER UNIT

A most efficient and quiet running blower-heater by Solatron—same type as is fitted to many famous name heaters—Comprises mains induction motor—long turbo fan—split 2 kw heating element and thermostatic safety trip—simply connect to the mains for immediate heat—mount in a simple wooden or metal case or mount direct onto base of say kitchen unit—price **£4-95** post **£1-50** control switch to give 2kw, 1kw, cold blow or off available 60p extra.

2 kw. motor made in metal case with control switch **£12-00**

## MOTORISED DISCO SWITCH

With 10 amp changeover switches. Multi adjustable switches are rated at 10 amps. This would provide a magnificent display. For mains operating 8 switch model **£5-25**, 10 switch model **£6-75**, 12 switch model **£6-75**.

## FLUORESCENT TUBE INVERTOR

For camping — car repairing — emergency lighting — from a 12v battery you can't beat fluorescent lighting. It will offer plenty of well distributed light and is economical. We offer inverter for 21" 13 watt miniature tube for only **£3-75** with tube and tube holders as well.

## RELAYS

12 volt two 10 amp changeover plug in **95p**.  
12v three 10 amp changeover plug in **£1-28**.  
12v two changeover miniature wire ended **95p**.  
12 volt open single screw fixing two 10 amp changeovers **85p**.  
12 volt open three 10 amp changeovers **£1-25**.  
Latching relay mains operated 2 c/o contacts **£2-11**.  
Mains operated three 10 amp changeovers open type one screw fixing **£1-25**.  
Many other types with different coil voltages and contact arrangements are in stock, enquiries invited.

**Terms: Prices include Post & VAT. But orders under £6-00 please add 50p to offset packing. Bulk enquiries—Please Phone for Generous Discounts 688 1833.**

Access and Barclaycard accepted

## J. BULL (ELECTRICAL) LTD

(Dept. E. E.), 103 TAMWORTH RD., CROYDON CR8 1SG

## IT'S FREE

Our monthly Advance Advertising Bargains List gives details of bargains arriving or just arrived—often bargains which sell out before our advertisement can appear—it's an interesting list and it's free—just send S.A.E. Below are a few of the Bargains still available from previous lines.

**FM Tuner and decoder**, 2 very well made (Japan) units, nice clear dial, excellent reproduction. **£11-20** the pair.

**12 Volt Heavy Duty Relay**, plug in tape has three pairs of 10 amp changeover contacts. A transparent dust cover, price **£1-08** suitable 11 pin base 45.

**4 Changeover Relay**, upright mounting 4 sets of 10 amps changeover contacts, mains voltage coil **£1-72**.

**12 Volt Pump**. Designed we believe as a bilge pump, this is 12 volt AC/DC motor coupled by a long enclosed shaft to a submersible pump. Suitable for water or most any fluids. Price **£12-50**.

**High Load 24 Hour Clock Switch**, made by the famous Smiths Company for normal mains but with clockwork reserve has load capacity of 50 amps at 240V 50HZ. The reform suitable for dealing with large loads of say shop lighting, water heating, storage heaters, etc., etc. Has triggers for on and off per 24 hours but extra triggers will be available. Price **£1-50** per pair, totally enclosed. Price **£9-50**.

**Enclosed 24 Hour Clock** with contacts for breaking 10-12 amps at 240 volts. This one has two sets of on/off per 24 hours, price **£7-00**.

**Light Dimmer**, our timer module with small motors makes an excellent light dimmer. Contains a 4 amp 400V SCR so it should be suitable for loads approaching 1KV. Price of module and instructions **£2-25**.

**Push Pull Solenoids**, mains operated solenoids which will push as well as or instead of pull. Very heavy duty, estimate this at 20lbs push or pull 1 1/2" x 3 1/4" made Magnetic Devices Co. **£7-50**.

**Flashing Lights**, chasing lights, random finishes, strobe effects etc., etc. can easily be achieved using our disco switches. These switches are ex-equipment but guaranteed perfect and supplied suitable for mains working. To get some idea of loading number, each switch is 10 amp. For the light pipe or Catherine Wheel effect order the 12 switch model with light pipe data model, interconnecting the switches to give fastest speed. 8 Switch model **£5**, 9 Switch model **£9-75**, 12 Switch model **£6-20**.

**Reed Switches**, standard 60 watt glass type. Normal open contacts glass lengths 2" diameter 3/16". 10 for **£1**, 100 for **£8**, 1000 for **£70**.

**Flat Reed Switches**, for stacking, greater quantity in confined space. Price **£5p**.

**Ceramic Magnets**, suitable for operating Reed switches, central fixing hole, 10 for **£1**.

**Music Centre Transformer** 12-0-12 at 1 amp and 9 volt at 1/2 amp. Normal primary, uprighting, impregnated and varnished for quiet operation. Price **£3-50**.

**'W' Shaped Fluorescent Tubes** for porch light, box signs or where you want light evenly spaced over a confined area of approx. 10" x 10". 30 watts made by Philips. Price **£2-24**.

**Extension Speakers**, 8 ohm 4-5 watts handling power. We have 5 or 6 different models in stock, cheapest being the Partytime at **£3-95** each, again only really a bargain for callers as postage is **£1-50** per speaker.

**Auto Transformers** for working American tools and equipment, completely enclosed in sheet metal case with American type flat output socket made for computer so obviously first class 500 watts. With gang handle, offered at about half price only **£15**. These may be a bit solid but are fully guaranteed. Similar but 1000 watt for **£29-50**.

**Car Starter Charge Kit**. New version. We supply two 10 amp rectifiers, 250v transformer and the start charge switch with instructions, price **£9-75**. This is probably one of the most useful pieces of equipment you can have in your garage. Sooner or later you or someone will leave something on and you will have a flat battery, this starter will get you away usually in less than 5 minutes.

**Resetter Counter**, by Veedroot Company, 230/240V mains operated, intended for surface mounting has a fixing flange at the bottom. Price **£2-16**.

**12V Drip proof Relay**. Specially designed for going under the bonnet of a car, made by one of our big manufacturers, this really has a removable semi-hard rubber cover. Contacts look suitable for up to 10 amps so this could be the right one. If you are thinking about making an anti-theft device. Price **£1-8p**.

**High Speed Uniselector**. As many customers know, we have a very comprehensive stock of uniselectors as used in automatic telephone exchanges, light flashing etc., etc. Just arrived however is a high speed model made by famous Plessey, this is 2 pole 32 way with make before break wipers, overall size approx. 4" x 3" x 2 1/2". Price **£3-50 + 28p**.

**Pneumatic Ram** for lifting, thrusting, pulling etc., has 2 1/2" travel, looks large enough to open doors, lift, staircase, ventilators, etc. Price **£7-00**.

**Solder Gun Bargain**. The ETP, this is 100 watt solder gun, a very well made tool with lamp to illuminate work has double insulated mains transformer and is built into the shock proof thermoplastic case. Comes complete with spare tips. Mains operated of course. Price **£4-50**.

**Interested in Tape Control**. American made tape punches, really beautiful units made of sophisticated parts, designed we believe to automatically operate typewriters and they can of course be used to operate other punch tape controlled machines. Reference number is NCR Class 461-2 reference 205 H8 R56. We believe these are 8r bit paper tape punches, powered from 115V 50HZ in very good condition with tape **£16-00**, carriage is **£3-20**.

**Resettable Fuses** (thermal trips). Two new types have come in, one made by ETA is a 6 amp model which is mounted through a single hole rather like a volume control. This is suitable for 250 volts AC or 24 volts DC. Price **54p**. **4-5 Amp Model** made by AEG is held by two screws thus a bank of these could be mounted between metal straps. Price **54p**.

**Disc Motor**, mains operated. This is very thin in fact less than 1 1/2" thick and only approx 2" dia. Spindle revolves at 250 rpm and the spindle which is approx. 1/32" dia. pushes through so motor could be used to drive clockwise or anti-clockwise. The spindle being a friction fit can be pushed completely out and replaced by your own spindle, a knitting needle for instance. Price only **38p**.

**75 rpm Mains Induction Motor** with gearbox. This motor is quite powerful and has 1 1/2" stack and the final 75 rpm drive shaft is 1 1/2" long by 3/8" dia. The motor also has a spindle coming from the opposite end to which could be fitted another pulley. Overall size approx. 3" x 5" x 2 1/2" + spindles. Price **£3-35**.


**24 Hour Motor**, beautifully made by Sangamo. This is 200-240v mains driven motor with gearbox together in one housing, size approx. 1 1/2" dia. by 1 1/2" deep. If you are contemplating making a 24 hour switch with a lot of on/off's, then this is obviously the motor. Price **£1-89**.

# The latest kit innovation!
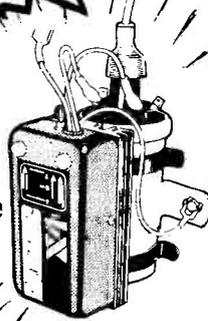
## from Sparkrite

*Sparkrite - was featured by Shaw Taylor in "DRIVE IN"*

the quickest fitting  
**CLIP ON**  
capacitive discharge  
electronic ignition  
in KIT FORM



- Smoother running
- Instant all-weather starting
- Continual peak performance
- Longer coil/battery/plug life
- Improved acceleration/top speeds
- Optimum fuel consumption

Sparkrite X4 is a high performance, high quality capacitive discharge, electronic ignition system in kit form. Tried, tested, proven, reliable and complete. It can be assembled in two or three hours and fitted in 1/3 mins.

Because of the superb design of the Sparkrite circuit it completely eliminates problems of the contact breaker. There is no misfire due to contact breaker bounce which is eliminated electronically by a pulse suppression circuit which prevents the unit firing if the points bounce open at high R.P.M. Contact breaker burn is eliminated by reducing the current to about 1/50th of the norm. It will perform equally well with new, old, or even badly pitted points and is not dependent upon the dwell time of the contact breakers for recharging the system. Sparkrite incorporates a short circuit protected inverter which eliminates the problems of SCR lock on and, therefore, eliminates the possibility of blowing the transistors or the SCR. (Most capacitive discharge ignitions are not completely foolproof in this respect). The circuit incorporates a voltage regulated output for greatly improved cold starting. The circuit includes built in static timing light, systems function light, and security changeover switch. All kits fit vehicles with coil/distributor ignition up to 8 cylinders.

### THE KIT COMPRISES EVERYTHING NEEDED

Die pressed epoxy coated case. Ready drilled, aluminium extruded base and heat sink, coil mounting clips, and accessories. Top quality 5 year guaranteed transformer and components, cables, connectors, P.C.B., nuts, bolts and silicon grease. Full instructions to assemble kit neg. or pos. earth and fully illustrated installation instructions.

NOTE - Vehicles with current impulse tachometers (Smiths code on dial RV1) will require a tachometer pulse slave unit. Price £3.85 inc. VAT, post & packing.

Electronic Design Associates, 82 Bath Street, Walsall, WS1 3DE U.K. only.

Electronics Design Associates, Dept. PW6  
82 Bath Street, Walsall, WS1 3DE. Phone: (9) 614791

Name .....

Address .....

Phone your order with Access or Barclaycard

Send SAE if brochure only required.

Inc. V.A.T. and P.P.

QUANTITY REQ'D.


I enclose cheque/PO's for

X4 KIT	£16.65
TACHOPULSE SLAVE UNIT	£3.85

£  
Cheque No.

Please state polarity pos. or neg. earth  
Access or Barclaycard No.

## Now, complete your system!

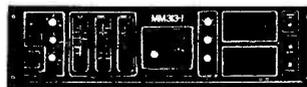

### Citronic MM313 Mixer

Ideal for the DIY enthusiast building up a complete disco system £46 ch mono. inc. 1 LED indicators, connections via phono sockets at rear. Bargain price, including PSU £84.24.

### The ultimate range of speakers

We carry a good selection of high quality chassis for the DIY speaker constructor: 12" or 15" Bass speakers and Dual Concentrics. Exponential horns from £13.77, or our fabulous Piezo Horns which handle a 5K-20K frequency range in any PA system up to 100W (No X over required) and cost only £6.18, each.




### Projectors

Come and see our specially selected projectors from £42.12 (Squire Multifact 150) to £94.50 (Tutor 11E) plus the wider array of projector attachment and effects that you'll ever see on continuous demonstration.


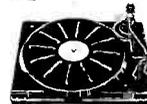
### Ropelights

Great effect at discos. 7 metres long. Multiway connectors. 4 channel. £43.20 (inc. pack of spare bulbs)



### Turntables

Our unsurpassed Disco experience has enabled us to select the best turntables for your requirements. For example the new BSI P200 belt drive. ONLY £28.12.

### Bulgin Octal plugs and sockets

There's always hundreds of Bulgin Octal multiway plugs and sockets in stock at Roger Squire's. Each pair rated 6A. Perfect for your Sound to Light System. P552 SOCKET £0.65 P551 PLUG £1.94.

Multiway Cables  
4 core (6A) 59p/metre  
5 core (6A) 73p/metre  
6 core (6A) 86p/metre

### Many disco accessories

All Roger Squire's shops have a service department which carries large stocks of DISCO SPARES & ACCESSORIES.

## Roger Squire's

# Disco Centres

**PERSONAL CALLERS ONLY**

ALL SHOPS OPEN TUE-SAT. LATE NIGHT WED. (UP TO 8 PM)

176 Junction Road, N19 5Qas Turnell Park Tube Station. Tel: 01 272 7474

125 Church Road, Redfield (Near St. George) 1 mile from end of M32

251 Deansgate 3, 15 mins from City Centre

Tel: 0272 550550

MANCHESTER Tel: 061 831 7676

GLASGOW 1 Queen Margaret Road (off Queen Margaret Drive) Kelvinside 20, just behind the BBC. Tel: 041 946 3303

## Catronics Offer!

**P. W. TRENT MEMORIES** 2102, £1.20; 2102-AN4, £1.85  
2513, £8.00; 74S262, £14.00

Parts available for this 150W Linear

Contact us for details.

## NEW LOW PRICES for TTL/LS

std			std			std			std		
N	LS	N	LS	N	LS	N	LS	N	LS	N	LS
7400	13p	18p	7430	16p	—	7496	60p	—	74166	135p	—
7402	14p	18p	743	27p	—	74107	33p	—	74170	185p	—
7403	14p	20p	7440	18p	—	74121	28p	—	74174	30p	—
7404	15p	20p	7442	58p	80p	74123	53p	—	74175	80p	—
7406	30p	—	7447	58p	—	74126	55p	—	74177	84p	—
7408	17p	22p	7473	32p	—	74132	—	74p	74180	90p	—
7410	14p	20p	7474	25p	40p	74145	80p	—	74192	95p	—
7411	22p	—	7475	35p	—	74150	95p	—	74193	95p	—
7412	24p	20p	7483	78p	95p	74153	89p	—	74195	90p	—
7414	55p	—	7485	95p	100p	74157	80p	60p	74196	100p	—
7420	16p	20p	7486	33p	40p	74161	80p	80p	74221	150p	110p
7421	31p	—	7490	31p	80p	74163	—	80p	74H00	35p	—
7427	29p	—	7492	52p	—	74164	105p	—	74H04	44p	—
7428	38p	—	7493	31p	60p	74165	112p	—	74H10	39p	—

All our i.c.s are brand new, fully guaranteed, mostly National and Texas.  
74N and 74LS quantity discounts: £10 less 10%, £20 less 20%.

## 2 Metre MONITOR RECEIVER

As featured in April issue of P.W. Kit only **£52** less crystal

We also have available a multi-channel version of the PCB, allowing up to 7 crystals to be fitted. Kit less crystals—£53-60

Components also available separately:

PCB (single channel) £4-50; (multi-channel) £5-35;  
SL6640, £4-85; Crystal filter, £24-85

All prices INCLUDE VAT at current rates.

Please note our minimum U.K. post and packing charge is 30p.  
EXPORT ORDERS welcomed.

**CATRONICS LTD., COMMUNICATIONS HOUSE,**  
**(Dept. 986) 20 WALLINGTON SQUARE,**  
**WALLINGTON, SURREY SM6 8RG.**

Tel. 01-669 6700 (9 a.m. to 5.30 p.m. Sat. 1 p.m.)

# Marshall's

Head Office and Mail Order to Dept. P.W.  
A. Marshall (London) Ltd.  
Kingsgate House, Kingsgate Place,  
London NW6 4TK. Tel: 01-624 0805

Telex 21442

Retail Sales: London: 40 Cricklewood Broadway, NW2 3ET. Tel: 01-452 0161/2. Also 325 Edgware Road, W2. Tel: 01-723 4242  
Glasgow: 85 West Regent Street, G2 2DD. Tel: 041-332 4133 And Bristol: 108A Stokes Croft, Bristol. Tel: 0272 654201.

## RESISTORS FIXED CARBON

0.25 watt ± 5% Tol. Available in E12 range 10Ω to 1 meg	PRICE
2p each	
0.5 watt ± 5% Tol. Available in E12 range 10Ω to 10 meg	PRICE
3p each	
1.0 watt ± 10% Tol. Available in E12 range 10Ω to 10 meg	PRICE
5p each	
2.0 watt ± 10% Tol. Available in E12 range 10Ω to 10 meg	PRICE
9p each	

## WIREWOUND

2.5 watt ± 5% Tol. following values only	10p each
Ohms 22, 33, 5, 1, 1.2, 1.5, 1.8, 2.2, 2.7, 3.3, 3.9, 4.7, 5.6, 6.8, 8.2, 10, 12, 15, 18, 22, 27, 33, 39, 47, 56, 68, 82, 100, 120, 150, 180, 220, 270, 330.	
5 watt ± 5% Tol. following values only	12p each
5, 1, 2.2, 3.3, 3.9, 4.7, 6.8, 8.2, 10, 12, 15, 18, 22, 25, 33, 39, 47, 60, 75, 82, 100, 120, 130, 150, 160, 220, 250, 270, 300, 330, 470, 500, 560, 680, 820, 1k, 1k2, 1k5, 2k, 2k2, 2k5, 3k3, 4k7, 5k6, 6k8, 7k5, 8k2, 10k, 12k.	
10 watt ± 5% Tol. following values only	14p each
1, 2.2, 3.3, 4.7, 6.8, 7.5, 8.2, 10, 12, 15, 18, 22, 25, 33, 39, 47, 70, 82, 100, 120, 150, 200, 250, 330, 470, 560, 680, 750, 1k, 1k2, 1k5, 1k8, 2k, 2k2, 2k7, 3k, 3k5, 4k7, 5k, 5k6, 6k8, 10k, 15k, 18k, 20k, 25k.	

## MULLARD MR25/MR30 SERIES METAL OXIDE

0.5 watt ± 2% Tol. Available in E24 range 10Ω to 1 meg  
4p each

**TOOLS**  
Box joint construction for strength. Small compact and reliable, insulated handles and smart individual wallet.

**GENERAL PURPOSE 100mm (4")**  
Diagonal Cutters £3.40  
Round Nose Pliers £3.25  
Flat Nose Pliers £3.20  
Snipe Nose Pliers £3.20  
End/Top Cutters £3.60

## BOXES AND CASES

See catalogue for full range

ALUMINIUM			
BA2 4 × 4 × 1 1/2"	£0.85	BA8 7 × 5 × 2 1/2"	£1.50
BA3 4 × 2 1/2 × 1 1/2"	£0.80	BA9 8 × 6 × 3"	£1.90
BA4 4 × 5 1/2 × 1 1/2"	£1.00	BA10 10 × 7 × 3"	£2.40
BA5 4 × 2 1/2 × 2"	£0.95	BA11 10 × 4 1/2 × 3"	£2.25
BA6 3 × 1 × 2"	£0.60	BA12 12 × 5 × 3"	£2.35
BA7 6 × 4 × 2"	£1.25	BA13 12 × 8 × 3"	£2.70

**REXINE COVERED**


RB1 6 × 4 1/2 × 1 1/2"	£1.75
RB3 9 × 5 × 2 1/2"	£2.40
RB5 11 × 7 1/2 × 3 1/2"	£3.55
RB7 15 × 8 × 4"	£5.00

Complete with screws and feet.

**ABS PLASTIC**

3 × 2 1/2 × 1 1/2"	£0.55	4 1/2 × 3 1/2 × 1 1/2"	£0.85
8 1/2 × 2 1/2 × 1 1/2"	£0.65	8 1/2 × 4 1/2 × 3 1/2"	£2.10

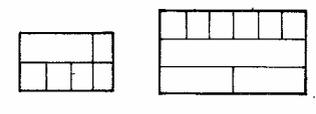**RAACO STORAGE BOXES**  
2 sizes — 4 configurations.  
B8 £0.76, B7 £0.76, B9 £1.62, B10 £1.78



**VERO CASES** — see catalogue for full range  
7 different styles — 18 sizes.

## PLASTIC CLIP CASES

Anodised aluminium front panel, two tone halves clip together

VCC1 — 84 × 40 × 154mm	£2.50
VCC2 — 85 × 60 × 154mm	£3.15
VCC3 — 85 × 80 × 154mm	£3.65

Also — instrument cases — 5 sizes from £2.10.  
Card frames, Flip top boxes, etc. etc.

## TTL See catalogue for full range.

74LS00N	£0.26	74LS95N	£0.95	74LS169N	£1.45
74LS01N	£0.26	74LS96N	£0.44	74LS170N	£1.90
74LS02N	£0.26	74LS97N	£0.64	74LS173N	£1.10
74LS03N	£0.26	74LS98N	£1.20	74LS174N	£0.75
74LS04N	£0.29	74LS99N	£0.70	74LS175N	£0.75
74LS05N	£0.26	74LS100N	£0.64	74LS181N	£2.75
74LS08N	£0.26	74LS101N	£0.70	74LS182N	£2.70
74LS09N	£0.26	74LS102N	£1.35	74LS189N	£3.74
74LS10N	£0.26	74LS107N	£0.42	74LS190N	£1.00
74LS11N	£0.26	74LS109N	£0.42	74LS191N	£1.00
74LS12N	£0.26	74LS112N	£0.42	74LS192N	£0.95
74LS13N	£0.58	74LS113N	£0.42	74LS193N	£0.95
74LS14N	£0.75	74LS114N	£0.42	74LS194N	£0.70
74LS15N	£0.26	74LS122N	£0.62	74LS195N	£0.70
74LS20N	£0.26	74LS123N	£0.83	74LS196N	£0.80
74LS21N	£0.26	74LS124N	£1.70	74C00N	£0.24
74LS22N	£0.26	74LS125N	£0.60	74C02N	£0.24
74LS26N	£0.32	74LS126N	£0.50	74C04N	£0.24
74LS27N	£0.26	74LS132N	£0.85	74C08N	£0.24
74LS28N	£0.29	74LS136N	£0.42	74C10N	£0.24
74LS30N	£0.26	74LS138N	£0.65	74C14N	£0.95
74LS32N	£0.27	74LS139N	£0.65	74C20N	£0.24
74LS33N	£0.29	74LS145N	£1.30	74C30N	£0.24
74LS37N	£0.32	74LS150N	£1.65	74C32N	£0.24
74LS38N	£0.32	74LS148N	£1.35	74C42N	£0.92
74LS40N	£0.26	74LS151N	£0.58	74C48N	£1.38
74LS42N	£0.80	74LS153N	£0.58	74C73N	£0.54
74LS47N	£1.09	74LS154N	£1.45	74C74N	£0.56
74LS48N	£1.00	74LS156N	£0.80	74C76N	£0.54
74LS49N	£1.09	74LS157N	£0.60	74C85N	£1.30
74LS51N	£0.26	74LS157N	£0.60	74C85N	£1.30
74LS54N	£0.26	74LS158N	£0.65	74C86N	£0.64
74LS55N	£0.26	74LS160N	£0.80	74C89N	£4.39
74LS59N	£1.26	74LS161N	£0.85	74C90N	£0.85
74LS73N	£0.42	74LS162N	£0.80	74C93N	£0.85
74LS74N	£0.42	74LS163N	£0.85	74C95N	£1.04
74LS75N	£0.58	74LS164N	£1.10	74C107N	£1.22
74LS76N	£0.42	74LS165N	£1.15	74C150N	£4.14
74LS78N	£0.42	74LS166N	£1.85	74C151N	£2.47
74LS83AN	£0.90	74LS168N	£1.45	74C160N	£1.11

**NEW 1979 CATALOGUE**  
48 pages — largest range of quality components in the U.K. — over 8,000 line items — 50p post paid — 40p to callers.

**MAIL ORDER**  
Add 40p P/P to all orders.  
Tel. credit card orders £10 minimum.  
ACCESS — BARCLAYCARD

## SOLDERING EQUIPMENT

**ANTEX IRONS**  
MODEL C15 — 15 watt  
Miniature soldering iron. Bits slide on and off £3.90

**17 WATT MODEL CX**  
Doubtless principle and superb insulation £3.90

**MODEL X25 — 25 watt**  
Stainless steel shaft and phenolic handle £3.90

**ST 3 STAND**  
It is suitable for all models and replaces all previous stands. The two spoons serve to keep the bits clean. Price £6.50

**DESOLDERING TOOL**  
Accurately removes solder from pcb's and components particularly when solder is grouped tightly together. Price £6.50

**SOLDER**  
Size 10 39.6 metres approx. £2.32  
Size 12 13.7 metres approx. £2.28  
Size 5 2.3 metres approx. £0.58

## CAPACITORS — Radial leads

UF	Price	UF	Price	UF	Price
0.0	£0.06	0.068	£0.07	0.47	£0.14
0.015	£0.06	0.1	£0.08	0.68	£0.20
0.022	£0.06	0.15	£0.08	1	£0.24
0.033	£0.08	0.22	£0.09	1.5	£0.36
0.047	£0.06	0.33	£0.13	2.2	£0.37

## ELECTROLYTICS — MULLARD

UF	Price	UF	Price	UF	Price
15	£0.10	250	£0.18	1.5	£0.10
33	£0.10	680	£0.73	3.3	£0.10
68	£0.13	UF	£0.40	6.8	£0.10
150	£0.16	6.8	£0.10	15	£0.13
330	£0.42	15	£0.10	88	£0.42
680	£0.50	33	£0.13	150	£0.47
1500	£0.83	150	£0.42	330	£0.78
		680	£0.83		

**TANT BEADS, ELECTROLYTIC AXIAL, RADIAL, METALLISED POLYESTER/EXTENDED FOIL, PLASTIC FOIL, MICA ETC. ETC. See catalogue.**

## KNOB AND SWITCHES

Full range in catalogue  
M1 — Black plastic with mach metal insert 25mm dia.  
£0.25. M2 — af M1 but with pointer £0.31. M5 — Black plastic with mach. insert and calibrated skirt £0.33. Car radio knob with chrome top £0.39. Switches — toggle, rocker, slide, micro, rotary, miniature, push button etc. etc. See catalogue.

# ELECTROVALUE

Your leading direct suppliers for

## RESISTORS

Carbon Film ●			
1/4 watt 1 to 10	E24 values (E12 over 1M)	ea. 2p	
1/2 watt 47 to 4M7	E12 values	ea. 2p	
1 watt 47 to 10M	E24 values	ea. 2p	
	E12 values	ea. 5p	
Metal Oxide ●			
1/2 watt ElectroSil TR5 10 to 1M	2% E24 values	ea. 5p	
Metal Film			
0.4 watt Mullard MR25 5.1 to 300K	2% E24	ea. 5p	
Wirewound			
1 watt 0.22 to 3.9	E12 values	ea. 15p	
2.5 watt 1 to 1K	E12 values (vitreous)	ea. 20p	
3 watt 1 to 10K	E12 values	ea. 10p	
7 watt 1 to 10K	E12 values	ea. 10p	

**HERMISTORS ●**  
Discs — VA1039 500 19p. VAT1040 130. VA1100 15 19p. VA1104 15-25 59p.  
Plate and Bead (vacuum) types also available from 22p to £4.80 each.

Buying from **Electrovalue** can cost you even less when purchased together with other items from our Catalogue 9 (See pages 85/86 and discounts scheme). You will find practically everything you want in our Catalogue at good prices backed by good service — so start buying the Electrovalue way today.

V.A.T. Add 8% to all prices quoted here except those marked ● which carry 12 1/2%. Prices subject to alteration without prior notice.

Discounts non allowable on Barclaycard or Access

## ELECTROVALUE LTD.

Dept. PW6, 24 St. Judes Road, Englefield Green, Egham, Surrey, TW20 0HB.  
Phone Egham 3603. Telex 264475  
Northern Branch (Personal shoppers only). 680 Burnage Lane, Burnage, Manchester M19 1NA.  
Phone (061) 432 4945

# J. BIRKETT

Radio Component Suppliers  
25 The Strait, Lincoln LN2 1JF. Tel: 20767

- 50. 1 AMP (S.C.R.'s) THYRISTORS Untested @ £1.
- 25. 5 AMP (S.C.R.'s) STUD MOUNTING Untested @ 75p.
- METAL BC 107, BC 105, BC 109 TRANSISTORS @ 6 for 50p.
- SPECIAL LOW NOISE VHF STRIPLINE VHF SET 2N 4417 @ £2.20.
- 2 GHz LOW NOISE VHF STRIPLINE NPN TRANSISTOR @ £1.
- MINIATURE VARIABLE CAPACITOR 25 × 25 × 25p @ 75p each.
- X BAND GUNN DIODES CXY11A @ £3 each.
- VERNITRON FILTERS FM4 10.7 MHz @ 50p, 3 for £1.
- R. F. TRIANGLE TRANSISTORS AF 239, BF 90 All at 50p, BF 362 @ 25p, BF 724 + 10p, MPS 6514 + 10p, BF 177 + 15p.
- VHF FETS MFE 121 + 60p, E304 + 25p, J310 + 20p, BF 256 + 25p, 2N 3819T @ 20p, 40673T @ 33p, BF 244 + 25p.
- FERRITE BEADS FX 1115 at 15p doz.
- TRIMMERS SEMI-AIRSPACED 2 To 9pf, 3 To 35pf, 6 To 45pf, 6 To 60pf, 0 To 125pf, 8 To 140pf All at 15p each.
- LED'S TIL 209 at 6 for 50p, 2" Red @ 15p, Green @ 18p.
- VHF TETTER TRIMMERS 10pf @ 18p each.
- 50. PLASTIC PNP TRANSISTORS Untested @ 57p.
- 50. PLASTIC PNP TRANSISTORS Untested @ 57p.
- 50. VARY CAP DIODES LIKE BA 102 Untested @ 57p.
- 50. OC 71 TRANSISTORS Assorted Untested @ 57p.
- 50. BC 107/8/9 TRANSISTORS Assorted Untested @ 57p.
- 100. MULLARD C280 CAPACITORS Assorted 57p.
- 50. ASSORTED DISC CERAMICS for 57p.
- MULLARD TAA 320 M.O.S.T. PRE-AMPLIFIER 1 C. with data @ 35p.
- 10 AMP THYRISTORS 100 PIV @ 25p, 400 PIV @ 50p, 800 PIV @ 60p.
- ELECTROLYTICS 100 — 200uf 275v @ 25p, 10 for £1.45, 150 + 75 of 350v.w. @ 25p, 10 for £2.20 + 200 + 100 + 32uf 325v.w. @ 25p, 10 for £2.
- MAINS TRANSFORMERS 240 volt Input. Type 1. 24 volt Tapped at 14 volt 1 amp @ £1.30 (P & P 25p). Type 2. 22-0-22 volt 500mA @ £1.60 (P & P 25p). Type 3. 45 volt 6 amp @ £4.50 (P & P 95p). Type 4. 20 volt 1 amp Twice @ £1.60 (P & P 95p). Type 5. 45 volt 2 amp, 45 volt 500mA @ £3.50 (P & P 85p). Type 6. 16 volt 2 amp @ £1.60 (P & P 25p). Type 7. 24 volt 1.75 amp @ £1.60 (P & P 25p). Type 8. 30 volt 1 amp @ £1.60 (P & P 25p).
- MINIATURE POLYSTYRENE CAPACITORS 12, 15, 20, 25, 30, 50, 66, 100, 120, 1000pf All at 20p doz.
- Ua 742 ZERO CROSSING AC TRIGGER TRI GAC with data @ 25p.
- 20. PHOTO TRANSISTORS AND DIODES Assorted Untested for £1.
- 50. TWO WATT ZENERS assorted unttested @ 57p.
- SOLID DIELECTRIC VARIABLES 195 + 80pf @ 40p.
- 100uf 100v.w. WIRE ENDED ELECTRONICS at 5 for 35p.
- 1uf 25v.w. ELECTROLYTICS at 6 for 25p.
- SUB-MINIATURE 25 × 25 × 25p VARIABLE CAPACITOR @ £1.
- HFC 600 FREQUENCY COUNTER 8 DIGIT READOUT 600 MHz @ £115.

Please add 20p for post and packing on U.K. orders under £2, overseas postage at cost.

# Sonic

HI-FI DISCOUNT CENTRES



## DISCOUNT SPEAKERS

Imp 8 or 15 as app.  
Guarantee:  
**TITAN 5 years**  
**FANE LIFETIME**  
**OTHERS 1 year**  
**ALL PRICES INC. VAT**

Prices correct at 23.1.79

### HI-FI TYPES

	List/Value	Sonic Price
5" FANE 501 Mid or Full range	Sp. Price	<b>£4-95</b>
8" A.F. Model 80 Dual Cone	Sp. Price	<b>£4-95</b>
8" A.F. Model 83 Dual Cone	Sp. Price	<b>£5-95</b>
FANE 8" 80BT Dual Cone	Sp. Price	<b>£3-95</b>
WH/FEDALE LTON 3xP Kit Pr.	£60.70	<b>£35-95</b>
" DENTON 2xP KIT pair	£39.15	<b>£21-95</b>
" GLENDALE 3xP KIT	£82.44	<b>£58-95</b>
A.F. FRI 8" SPKR KIT	Sp. Price Pair	<b>£14-95</b>
8" FANE MODE ONE KIT	Sp. Price Pair	<b>£19-95</b>
10" ELAC Model 10RM 10-15w	Sp. Price	<b>£2-50</b>

### CABINETS (TEAK VENEERED)

20" x 11 1/2" x 9 1/2" Suitable for Mode 1 or FRI Kits and Models 80, 83 or 80BT Spkrs. Limited Number **£6-95 ea.**

### GROUP/DISCO TYPES

12" TITAN T12/ASR	£15.00	<b>£12.95</b>
12" TITAN T12/80R	£22.50	<b>£14.95</b>
12" TITAN T12/100A 100w	£36.00	<b>£22.95</b>
12" CELESTION G12M	£18.50	<b>£11-95</b>
12" CELESTION G12H 30w	£22.00	<b>£14-95</b>
12" CELESTION G12/50 50w	£25.75	<b>£18-95</b>
12" GOODMANS 12 PD	Sp. Price	<b>£21-95</b>
12" GOODMANS 12 PG	Sp. Price	<b>£18-95</b>
12" FANE 'SPECIALIST' P.A. 80	£29.95	<b>£18-95</b>
12" " " DISCO 80	£29.95	<b>£19-95</b>
12" " " DISCO 100	£31.95	<b>£21-95</b>
12" " " GUITAR 80L	£25.95	<b>£18-95</b>
12" " " GUITAR 100L	£31.95	<b>£19-95</b>
12" " " GUITAR 80B	£29.95	<b>£19-95</b>
12" FANE CRESCENDO 80	£44.95	<b>£29-99</b>
12" " " 80LT	£49.95	<b>£34-95</b>
12" " " 12A	£64.45	<b>£41-95</b>
12" " " 12L	£67.67	<b>£39-95</b>
12" " " 12 BASS	£63.95	<b>£39-95</b>
15" TITAN T15/70 70w	£28.00	<b>£19-95</b>
15" TITAN T15/100 100w	£41.00	<b>£29-95</b>
15" FANE 'SPECIALIST' BASS 85	£41.95	<b>£29-95</b>
15" " " BASS 100	£44.50	<b>£31-50</b>
15" GOODMANS 15P	Sp. Price	<b>£23-95</b>
15" FANE CRESCENDO/15	£82.66	<b>£51-95</b>
15" " " BASS	£85.95	<b>£51-95</b>
15" " " 15/100LT	£74.69	<b>£51-95</b>
15" " " 15/160 160w	£107.23	<b>£72-95</b>
15" " " COLOSSUS 200w	£121.91	<b>£72-95</b>
18" TITAN T18/100 100w	£51.00	<b>£39-95</b>
18" GOODMANS 18P	Sp. Price	<b>£39-95</b>
18" CELESTION G18C	£53.00	<b>£41-95</b>
18" FANE CRESCENDO 18A	£114.97	<b>£72-95</b>
18" " " BASS	£101.86	<b>£59-95</b>
18" " " COLOSSUS 200w	£129.81	<b>£76-00</b>

PLEASE STATE IMPEDANCE.

### nuRN UNITS

CELESTION MH1000 25w	(Carr. 85p) £17.00	<b>£13-75</b>
FANE 910 MK II 50w	£17.75	<b>£10-99</b>
" 920 100w	£62.95	<b>£44-50</b>
" J44 30-50w	£7.95	<b>£4-95</b>
" J73 50w	£11.75	<b>£7-95</b>
" J104 50-70w	£16.95	<b>£10-95</b>

### HIGH POWER 'CROSS-OVERS'

FANE HPx1R or HPx2R Carr. 35p	£3-65	<b>£2-25</b>
-------------------------------	-------	--------------

### ADD-ON HIGH FREQUENCY UNITS

F.A.L. 'Add-on' Carr. £1	£41.95	<b>£35-95</b>
TITAN T1H 70w Carr. £1	£33.00	<b>£23-95</b>
TITAN TS2H 100w Carr. £1	£33.00	<b>£23-95</b>
TITAN T2H Carr. £1	£39.00	<b>£26-95</b>

### BIG DISCOUNTS ON WHARFEDALE SPEAKER KITS

LINTON 3XP	List/value	Sonic price
Power handling 30 watts DIN	£60.70	<b>£35-95</b>

DENTON 2XP	List/value	Sonic price
Power handling 25 watts DIN	£39.15	<b>£21-95</b>

Also for personal shoppers only

**AMPS, TTABLES, JINGLE MACHINES, DISCO CONSOLES, LIGHTING, CABINETS, CREDIT TERMS AVAILABLE** orders **£20** over

Phone orders accepted from Access & Barclay card holders.

403 SAUCHIEHALL STREET  
Tel: 041 332 0700

**GLASGOW**

Mail Orders/Export enquiries only ... to 24 Newgate Shopping Centre, NEWCASTLE. Add £1 carr. on Hi-Fi spkrs. or kits. Otherwise add £1.25 (12" Spkr). £1-50 (15") £2-50 (18")

## SUPERIOR WATCHES

A well known consumer magazine has published a report on watches which supports our opinion that CASIO and SEIKO are the best watches in the world, with CASIO offering unbeatable value for money.

### ★ THIS YEAR'S STAR BUY

**CASIO 46CS-27B**  
**46CS-29B**  
(29B slightly different case style)

Almost certainly the slimmest and most sophisticated ALARM CHRONOGRAPHS available today.

- L.C. Display of hours, minutes, seconds, day; And with day, date, month and year calendar.
- Optional 12 hour with am/pm or 24 hour clock display.
- 24 hour alarm setting.
- Optional hourly chimes.
- Chrono measures from 1/100 second to 6 hours.
- Net, lap, 1st & 2nd place.
- 7.8mm Stainless Steel case.
- Real mineral glass face.
- Water resistant to 100 feet.
- Less than ± 10 seconds per month.
- S/S bracelet, removable links. Backlight.



**£39.95**

### CASIO ALARM WATCHES



25CR-16B

Left, 9.1 mm

**£24.95**

25CS-16B

Right, 9.25 mm

**£34.95**

L.C. Display of hours, minutes, seconds (or date), day, am/pm; And with day, date, month and year. 24 hour alarm setting. Nightlight. 15 month battery life. Stainless Steel case and Mineral Glass face, Water Resistant to 100 feet. Matching fully adjustable bracelets.

### CASIO CHRONOGRAPHS

52QS-14B

Left, 8 mm

**£22.95**



45CS-22B

Right

**£34.95**

Net, lap and 1st & 2nd place timing to 1/100 second. Stainless Steel cases with Mineral Glass faces, Water Resistant to 66 & 100 feet. Both have nightlights.


52QS Displays hours, minutes, seconds, am/pm; And with day, date and month. Chrono times to 1 hour, with rollover.

45CS Displays hours, minutes, seconds, am/pm; And with day, date, month and year. Selectable 12 hour (with am/pm) or 24 hour clock display. Dual Time facility.

Fully adjustable S/S bracelets and removable links.


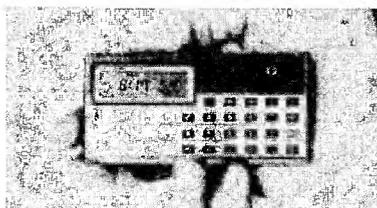
### THE AMAZING MELODY 80 Musical calculating diary watch



ADVANCE SPECIFICATION. Two separate Alarm Tunes. Calculator with keys 1-8 playing individual notes - a mini synthesizer! Complete Calendar Watch, Stopwatch - measuring net and lap times to 1/10 second - Alarm Timer and Calculator with %, √, full memory, date calculations. CASIO RRP **£31.95.**

**£25.95**

Other CASIO Calculating Diary Alarm Watches  
AQ-2000 £24.95; MQ-10 £35.95; MQ-11 £29.95.

CASIO LCD Scientific Calculators  
FX-48 £14.95; FX-80 £16.95; FX-2500 £19.95; FX-3100 £23.95; FX-58 (alarm clock, stopwatch) £24.95.

Most CASIO products available from stock.  
Send 25p for illustrated brochures of this superb range of watches or calculators (both on request).

Prices include VAT, P&P. Send cheque, PO or phone your ACCESS or BARCLAYCARD number to-

**TIMETRON**

Callers welcome by appointment

Dept. P.W., Beaumont  
Suite, 164 167, East Road,  
Cambridge CB1 1DB  
Telephone 0223 67303

ELECTRONICS SUPPLIERS  
SHOPS, IMPORTERS,  
MANUFACTURERS

# HONG KONG IS CHEAPER

Owing to the rising value of the Japanese Yen, products from Japan are becoming very expensive.

We have equivalent quality products at far better prices from Hong Kong, Taiwan and Korea.

We can supply in both large and small quantities with proven quality.

Even if you have never imported goods before, we can show you how!

86 pages, comprehensive, fully priced catalogue available: specialising in products for the electronics hobbyist.



OVER 3000 ITEMS

Catalogue \$US4.00 to cover airmail postage.

**DICK SMITH ELECTRONICS (HK) LTD.**

Retail Showroom & Buying Office  
29-39 Ashley Rd, Kowloon, H.K.

Tel. 3-669 352

Tlx. 64398

Call in when you're next in Hong Kong!

## BUILD YOUR OWN METAL DETECTOR TR/IB TR/VCO BFO . . .

Test equipment not required. Manuals for kits available at 25p each (refundable). UK prices post & VAT paid except where mentioned. Overseas: write for quote. Literature available: SAE please.

### Shadow TR/IB (illustrated)

A true transmit receive/induction balance metal detector — uses the latest circuitry for maximum range and sensitivity. Speaker or phones. Pre-assembled search head with lightweight closed cell foam encapsulated coils for thermal insulation and water resistance. A very powerful machine!



### Shadow TR/VCO

An advanced version of the above detector, use it as a sensitive TR/IB machine or switch to VCO mode when the depths achieved approach the maximum "in air" range. Low power requirement: runs on standard 9 volt batteries. The most sophisticated detector available as a kit.

Shadow TR/IB kit **£22.50 (£29.95 assembled)**  
Shadow TR/VCO kit **£27.50 (£36.95 assembled)**  
Padded stereo headphones suitable for 'Shadow' detectors **£5.50**

**Designing your own detector?** Then we can supply the 'hard to obtain' hardware "shell" including fully adjustable shaft with handle, search head moulding with hinge assembly, special clips to mount your own control housing (any box is suitable) completely non-metallic: suitable for any type of detector (TR-PI-VLF-BFO etc). Supplied undrilled as a kit with full instructions (as used on our Shadow range).

Detector Shell kit **£8.50**

**Low cost BFO detector** 200mm (8") annular search head gives wide scan with easy pinpointing. Simple high efficiency circuit draws <math>\le 3mA</math>. Extra lightweight 300gms (10.5ozs) with battery. Very detailed construction manual: ideal as a first project. Absolutely everything supplied including pre-assembled search head, tuning coil and earpiece.

ALT3 detector (kit) — **£9.95** (assembled £12.95) + £1 post & packing.  
Padded high Z headphones for ALT3: **£4.90**.

Order by post or phone (24 hours) — for quickest delivery quote credit card number.  
Callers by appointment only please!

**ALTEK** Dept. (P.W.) 1 Green Lane,  
Walton-on-Thames, Surrey.  
Phone (093 22) 44110

## Meet 'Uncle Tom'. He's on your wavelength.



Tom Beaumont — a radio enthusiast for 25 years — sells radio equipment for love! And he particularly loves Lowe — Trio for quality, value and reliability.

Tom is the sole authorised Lowe — Trio distributor for Yorkshire and North East England, and he offers the best before-and-after-sales service around on units like the top-value SRX-30 receiver illustrated.

### THE LOWE SRX-30

All the facilities of a top-class communications receiver in one top-quality, economically priced unit. Covers 500 KHz to 30 MHz with excellent dial readout and re-set accuracy. AM, CW, SSB reception. The SRX-30 is equally at home in broadcast or amateur bands.

Other features include RF gain, fine tuning selectable sidebands, built-in loudspeaker, AC mains or 12V DC operation and rugged construction at an attractive price — Just £175.00 inc. VAT.

Buy by post or call in — or phone your Barclay Card or Access number. For speedy delivery on your SRX-30, please send cheque/P.O. made out to Leeds Amateur Radio for £178.00 which includes £3.00 carriage and packing. We will deal with your order by return.

Alternatively, call in for a chat at 'Uncle Tom's Cabin'. The shop is just 10 minutes from Leeds City Station, and there's easy parking if you travel by car.

● Instant H.P. for Licenced Amateurs. ● Extended Credit Terms Available. ● Send 50p for Catalogue and Price List.

### LOWE TRIO DISTRIBUTOR



Leeds Amateur Radio are area distributors for Jay Beams, Antenna specialists and Hilomast products.

**LAR**  
LEEDS AMATEUR RADIO  
Reliability in Radio

Leeds Amateur Radio, 27 Cookridge Street, Leeds 2, West Yorkshire.  
Tel. Leeds 452657.

# Technical Training in Radio, Television and Electronics

ICS have helped thousands of ambitious people to move up into higher paid, more secure jobs in the field of electronics — now it can be your turn. Whether you are a newcomer to the field or are already working in the industry, ICS can provide you with the specialised training so essential to success.

### Personal Tuition and Guaranteed Success

The expert and personal guidance by fully qualified tutors, backed by the ICS guarantee of tuition until successful is the key to our outstanding record in the technical training field. You study at the time and pace that suits you best and in your own home. In the words of one of our many successful students: "Since starting my course, my salary has trebled and I am expecting a further increase when my course is completed."

### City and Guilds Certificates

Excellent job prospects await those who hold one of these recognised certificates. ICS can coach you for:

Telecommunications Technicians  
Radio, TV Electronics Technicians  
Technical Communications  
Radio Servicing Theory  
Radio Amateurs  
Electrical Installation Work  
Also MPT Radio Communications Certificate

### Diploma Courses

Colour TV Servicing  
Electronic Engineering and Maintenance  
Computer Engineering and Programming  
Radio, TV and Audio, Engineering and Servicing  
Electrical Engineering, Installations and Contracting

### Qualify for a New Career

Home study courses for leading professional examinations and diploma courses for business and technical subjects:—

G.C.E.	Engineering	Purchasing
60 subjects	Farming	Sales
at "O" &	Heating	Storekeeping
"A" levels	Industrial	Work Study
Accountancy	Management	
Air	Mechanical	
Conditioning		
Building		

POST OR PHONE TODAY FOR FREE BOOKLET.

## ICS To: International Correspondence Schools

SINCE 1890  
Dept H276 Intertext House, London  
SW8 4UJ or telephone 622 9911

Subject of Interest .....

Name .....

Address .....

Telephone Number .....

# SEMICONDUCTORS POTS & IRONS

## SOCKETS

1611	8 pin DIL	£0-11
1612	14 pin DIL	£0-12
1613	16 pin DIL	£0-13
1614	24 pin DIL	£0-25
1615	TO18 Transistor	£0-30
1616	TU3 Transistor	£0-12
1617	TU3 Transistor	£0-35
16117	TO5 Transistor	£0-12

## VOLTAGE REGULATORS

Positive		
MVR7805 v.a.	7805 TO220	£0-70
MVR7812 v.a.	7812 TO220	£0-70
MVR7815 v.a.	7815 TO220	£0-70
MVR7818		
MVR7824 v.a.	7824 TO220	£0-70
Negative		
MVR7905 v.a.	7905 TO220	£0-80
MVR7912 v.a.	7912 TO220	£0-80
MVR7915 v.a.	7915 TO220	£0-80
MVR7918		
MVR7924 v.a.	7924 TO220	£0-80
v.a. 723C TO95		£0-45
72723 14 pin DN		£0-45
LM309K TO3		£1-50

## ZENER DIODES

**400mw (Bzy88) DO7 Glass encapsulated.** Range of voltages available. 1.3v, 2.2v, 2.7v, 3.3v, 3.9v, 4.3v, 4.7v, 5.1v, 5.6v, 6.2v, 6.8v, 7.5v, 8.2v, 9.1v, 10v, 11v, 12v, 13v, 15v, 16v, 18v, 20v, 22v, 24v, 27v, 30v, 33v, 39v.

**No. Z48pa.**

**1w-1.5w Plastic and metal encapsulated.** Range of voltages available. 1.3v, 2.2v, 2.7v, 3.3v, 3.9v, 4.3v, 4.7v, 5.1v, 5.6v, 6.2v, 6.8v, 7.5v, 8.2v, 9.1v, 10v, 11v, 12v, 13v, 15v, 16v, 18v, 20v, 22v, 24v, 27v, 30v, 33v, 39v, 47v, 51v, 68v, 72v, 75v, 82v, 91v, 100v.

**No. Z1315pa.**

**10w Metal stud type SO10 case.** Range of voltages available. 1.3v, 2.2v, 2.7v, 3.3v, 3.9v, 4.3v, 4.7v, 5.1v, 5.6v, 6.2v, 6.8v, 7.5v, 8.2v, 9.1v, 10v, 11v, 12v, 13v, 15v, 16v, 18v, 20v, 22v, 24v, 27v, 30v, 33v, 39v, 47v, 51v, 68v, 72v, 75v, 82v, 91v, 100v.

**No. Z1035pa.**

## SILICON RECTIFIERS

<b>200mA</b>		
IS20 50v		£0-06
IS21 100v		£0-07
IS22 150v		£0-08
IS23 200v		£0-09
IS24 300v		£0-10
<b>1 Amp</b>		
IN4001 50v		£0-04
IN4002 100v		£0-05
IN4003 200v		£0-06
IN4004 400v		£0-07
IN4005 600v		£0-08
IN4006 800v		£0-09
IN4007 1000v		£0-10
<b>1.5 Amp</b>		
IS015 50v		£0-09
IS020 100v		£0-10
IS021 200v		£0-11
IS023 400v		£0-13
IS025 600v		£0-14
IS027 800v		£0-16
IS029 1000v		£0-20
IS031 1200v		£0-25
<b>3 Amp</b>		
IN5400 50v		£0-14
IN5401 100v		£0-15
IN5402 200v		£0-16
IN5404 400v		£0-17
IN5405 600v		£0-21
IN5407 800v		£0-25
IN5408 1000v		£0-30
<b>10 Amp</b>		
IS10/50 50v		£0-19
IS10/100 100v		£0-21
IS10/200 200v		£0-23
IS10/400 400v		£0-35
IS10/600 600v		£0-42
IS10/800 800v		£0-51
IS10/1000 1000v		£0-60
IS10/1200 1200v		£0-69
<b>30 Amp</b>		
IS30/50 50v		£0-56
IS30/100 100v		£0-69
IS30/200 200v		£0-93
IS30/400 400v		£1-25
IS30/600 600v		£1-76
IS30/800 800v		£1-94
IS30/1000 1000v		£2-31
IS30/1200 1200v		£2-88
<b>60 Amp</b>		
IS70/50 50v		£0-75
IS70/100 100v		£0-84
IS70/200 200v		£1-20
IS70/400 400v		£1-75
IS70/600 600v		£2-25
IS70/800 800v		£2-50
IS70/1000 1000v		£3-00
BX38/300 6A 300v		£0-45
BX38/600 6A 600v		£0-60
BX38/300 Rev 6A 300v		£0-45
BX38/600 Rev 6A 600v		£0-60

## POTENTIOMETERS

### CARBON POTS (Linear Track)

Single gang with wire end terminations, 6mm x 50mm plastic shaft 10mm bushes supplied with shake proof washer & nut. Tolerance  $\pm 20\%$  of resistance.

1831 1k ohms	£0-28*	1836 47kohms	£0-28*
1832 2k2ohms	£0-28*	1837 100kohms	£0-28*
1833 4k7ohms	£0-28*	1838 220kohms	£0-28*
1834 10kohms	£0-28*	1839 470kohms	£0-28*
1835 22kohms	£0-28*	1840 1Meg	£0-28*
		1841 2M2	£0-28*

### CARBON POTS (Log Track)

1842 4k7ohms	£0-28*	1846 100kohms	£0-28*
1843 10kohms	£0-28*	1847 220kohms	£0-28*
1844 22kohms	£0-28*	1848 470kohms	£0-28*
1845 47kohms	£0-28*	1849 1Meg	£0-28*
		1850 2M2	£0-28*

### DUAL CARBON POTS (Lin Track)

These high quality dual gang pots are fitted with wire end terminations and 6mm x 50mm plastic shaft 10mm, bush and supplied with shake proof washer & nut track tolerance  $\pm 20\%$  but matched to within 2db of each other. VC3.

1851 4k7	£0-85*	1855 100kohms	£0-85*
1852 10kohms	£0-85*	1856 220kohms	£0-85*
1853 22kohms	£0-85*	1857 470kohms	£0-85*
1854 100kohms	£0-85*	1858 1Meg	£0-85*
		1859 2M2	£0-85*

### DUAL CARBON POTS (Log Law)

1860 4k7ohms	£0-85*	1864 100kohms	£0-85*
1861 10kohms	£0-85*	1865 220kohms	£0-85*
1862 22kohms	£0-85*	1866 470kohms	£0-85*
1863 47kohms	£0-85*	1867 1Meg	£0-85*
		1868 2M2	£0-85*

### SINGLE GANG SWITCHED (Lin Law)

These potentiometers are fitted with double pole on-off switches. The switch is incorporated with the rotary action of the pot. Specification of pots as VC1. Switch rating 1.5amps at 250v AC.

1870 4k7ohms	£0-85*	1874 100kohms	£0-85*
1871 10kohms	£0-85*	1875 220kohms	£0-85*
1872 22kohms	£0-85*	1876 470kohms	£0-85*
1873 47kohms	£0-85*	1877 1Meg	£0-85*
		1878 2M2	£0-85*

### SWITCHED POT (Log Track)

Specification as VC2 but track having (log) law.

1879 4k7ohms	£0-85*	1833 100kohms	£0-85*
1880 10kohms	£0-85*	1884 220kohms	£0-85*
1881 22kohms	£0-85*	1885 47kohms	£0-85*
1882 47kohms	£0-85*	1886 1Meg	£0-85*
		1887 2M2	£0-85*

## ANTEX IRONS

O/No. 1943. 15 watt high quality soldering iron totally enclosed element in a ceramic shaft fitted with 3/32" bit. **£3-80**

O/No. 1947. Replacement element for 1943 iron. **£1-90**

O/No. 1944. Iron coated bit 3/32" for 1943 iron. **£0-46**

O/No. 1945. Iron coated bit 1/8" for 1943 iron. **£0-46**

O/No. 1946. Iron coated bit 3/16" for 1943 iron. **£0-46**

O/No. 1948. General purpose 18 watt iron fitted with iron coated bit. **£3-60**

O/No. 1952. Replacement element for 1948 iron. **£1-90**

O/No. 1949. Iron coated bit 3/32" for 1948 iron. **£0-46**

O/No. 1950. Iron coated bit 1/8" for 1948 iron. **£0-46**

O/No. 1951. Iron coated bit 3/16" for 1948 iron. **£0-46**

### DUAL GANG LOG-ANTI-LOG POT

1888 Track specification as dual gang pots VC3 but tracks mounted to log-anti-log action 100kohms **£0-75\***

### SPECIAL VOLUME CONTROLS

A miniature 16mm type replacement volume control incorporating single pole on-off switch. Resistance value 5kohms. Tolerance  $\pm 20\%$  1/8watt rating. **1889 £0-27\* VC8**

### MINIATURE ROTARY VOL CONTROL

5kohms log law with on/off switch, 20mm grooved spindle. Tag connections 17mm dia. Supplied with fixing nut. Used mainly for replacement. **1890 £0-54\* VC9**

### WIRE WOUND POTS

A range of wire wound single gang pots with linear tracks of 1 watt rating, fitted with 10mm bush and supplied with shake-proof washer and nut. VC6

1891 10ohms	£0-80	1895 220ohms	£0-80
1892 20ohms	£0-80	1896 470ohms	£0-80
1893 47ohms	£0-80	1897 1kohms	£0-80
1894 200ohms	£0-80	1898 2kohms	£0-80
		1899 4k7ohms	£0-80

### PRE-SET POTS

Miniature type for transistor circuits. The wiper of the preset is provided with a slot for screwdriver adjustment. The tags of the preset will fit printed wiring boards with a pitch of 2.54mm. All tracks are linear law. VC7

1801 100ohms	£0-09*	1808 22kohms	£0-09*
1802 200ohms	£0-09*	1809 47kohms	£0-09*
1803 400ohms	£0-09*	1810 100kohms	£0-09*
1804 1kohms	£0-09*	1811 220kohms	£0-09*
1805 2kohms	£0-09*	1812 470kohms	£0-09*
1806 4kohms	£0-09*	1813 1kohms	£0-09*
1807 10kohms	£0-09*	1814 2M2ohms	£0-09*
		1815 4M7ohms	£0-09*

### PRE-SET POTS

Miniature type for transistor circuits. Wiper adjustment is made by a screwdriver slot. Designed to fit 2.54mm pitch board. All tracks are linear law. VC8

1816 100ohms	£0-09*	1823 22kohms	£0-09*
1817 220ohms	£0-09*	1824 47kohms	£0-09*
1818 470ohms	£0-09*	1825 100kohms	£0-09*
1819 1kohms	£0-09*	1826 220kohms	£0-09*
1820 2kohms	£0-09*	1827 470kohms	£0-09*
1821 4k7ohms	£0-09*	1828 1Megohms	£0-09*
1822 10kohms	£0-09*	1829 2M2ohms	£0-09*
		1830 4M7ohms	£0-09*

## OPTOELECTRONICS

### NEW INCREASED RANGE - ALL 1ST QUALITY LED's (diffused)

O/no.	Type	Size	Colour	Price
1501	ARL209(TL209)	3mm (1.25)	RED	£0-10
1502	MIL3232(TL211)	3mm (1.25)	GREEN	£0-15
1503	MIL331 (OPL212A)	3mm (1.25)	YELLOW	£0-15
1504	ARL4850(FLY117)	5mm (2)	RED	£0-10
1505	MIL5251(TL222)	5mm (2)	GREEN	£0-15
1506	MIL5351(MV5353)	5mm (2)	YELLOW	£0-15
1509	FLY111	5mm (2)	CLEAR (fill. Red)	£0-11

### SUPER 'Hi-Brite' Type

1521	MIL32	3mm (1.25)	RED	£0-10
1522	MIL52	5mm (2)	RED	£0-10
1514	ORP12	Light dependent resistor		£0-55
1520	OCP71	Photo transistor		£0-35

### LED CLIPS

1508/125	pack of 5	125 clips		£0-15
1508/2	pack of 5	2 clips		£0-18
ALL $\pm 8\%$ V.A.T.				

### DISPLAYS

DL703	7 segment D.P. left (.30" height)	Common Anode		
RED	Single Digit	O/No. 1523		£0-70
DL707	7 segment D.P. left (.0.3" height)	Common Anode		
RED	Single Digit	O/No. 1510		£0-95
DL527	7 segment D.P. left (.50" height)	Common Anode		
RED	Two-Digit Reflector	O/No. 1524		£1-70
DL727	7 segment D.P. right (.510" height)	Common Anode		
RED	Two-Digit Light Pipe	O/No. 1521		£2-20
DL747	7 segment D.P. left (.630" height)	Common Anode		
RED	Single-Digit Light Pipe	O/No. 1511		£1-70
ALL $\pm 8\%$ V.A.T.				

### OPTO-ISOLATORS

Isolation Breakdown - Voltage 1500 - continuous fwd current 100mA

CIL74	Single-Channel 6 pin DIP standard type - optically coupled pair with infra-red LED Emitter and NPN Silicon Photo Transistor.	O/No. 1497	£0-50
CILD74	Multi-Channel 8 pin DIP Two Isolated Channels.	O/No. 1498	£1-00
CILQ74	Multi-Channel 16 pin DIP Four Isolated Channels.	O/No. 1499	£2-20
ALL $\pm 8\%$ V.A.T.			

### 2nd GRADE LED's

A pack of 10 standard sizes and colours which fail to perform to their very rigid specification, but which are ideal for amateurs who do not require the full spec. O/No. 1507 **£1-50**

## THYRISTORS

600ma	TO 18 Case	TO 48 Case	
Volts No.	Price	Price	
10 THY600/10	£0-15	50 THY7A/50	£0-48
20 THY600/20	£0-16	100 THY7A/100	£0-51
30 THY600/30	£0-20	200 THY7A/200	£0-57
50 THY600/50	£0-22	400 THY7A/400	£0-62
100 THY600/100	£0-25	600 THY7A/600	£0-78
200 THY600/200	£0-38	800 THY7A/800	£0-92
400 THY600/400	£0-44		
<b>10 Amp</b>			
Volts No.			
50 THY1A/50	£0-28	200 THY10A/200	£0-62
100 THY1A/100	£0-28	400 THY10A/400	£0-71
200 THY1A/200	£0-32	600 THY10A/600	£0-99
400 THY1A/400	£0-38	800 THY10A/800	£1-22
600 THY1A/600	£0-45		
800 THY1A/800	£0-58		
<b>16 Amp</b>			
Volts No.			
50 THY16A/50	£0-58	200 THY16A/200	£0-62
100 THY16A/100	£0-58	400 THY16A/400	£0-77
200 THY16A/200	£0-62	600 THY16A/600	£0-90
400 THY16A/400	£0-77	800 THY16A/800	£1-39
<b>30 Amp</b>			
Volts No.			
50 THY30A/50	£1-18	100 THY30A/100	£1-43
100 THY30A/100	£1-43	200 THY30A/200	£1-63
400 THY30A/400	£1-79	600 THY30A/600	£2-50
<b>No.</b>			
Price</			



EDITOR  
Geoffrey C. Arnold

ASSISTANT EDITOR  
Dick Ganderton C. Eng., MIERE

ART EDITOR  
Peter Metalli

TECHNICAL EDITOR  
Peter Preston

NEWS & PRODUCTION EDITOR  
Alan Martin

TECHNICAL ARTIST  
Rob Mackie

ASSISTANT ART EDITOR  
Keith Woodruff

SECRETARIAL  
Sylvia Barrett  
Debbie Chapman

**EDITORIAL OFFICES**  
Westover House,  
West Quay Road,  
POOLE, Dorset BH15 1JG  
Telephone: Poole 71191

**ADVERTISEMENT MANAGER**  
Telephone: 01-261 6636 Dennis Brough

**CLASSIFIED ADVERTISEMENTS**  
Telephone: 01-261 5762 Colin R. Brown

**MAKE UP & COPY DEPARTMENT**  
Telephone: 01-261 6570 Dave Kerindi

**ADVERTISEMENT OFFICES**  
Kings Reach Tower, Stamford St.,  
London, SE1 9LS  
TELEX: 915748 MAGDIV-G

## CB?

**T**HE airing given to the Citizens Band controversy in our April issue certainly did provoke some heart-felt comments from our readers, one or two of them frankly libellous! It does seem surprising that some members of the amateur radio fraternity should express quite so forcefully the view that no-one, but no-one, who has not passed the RAE should have any right whatever to any form of personal radio communication. There must be many people who, like one of our correspondents, are interested in radio but just seem unable to pass the RAE despite repeated attempts. And there are many, many thousands who could make good use of a personal, short-range communication facility.

The choice of frequency band is obviously important. It should preferably be in a presently unused portion of the spectrum, and well away from any bands for which off-the-shelf, high-powered transmitters or amplifiers are available. These requirements both put any portion of the 2 metre band out of court. The use of v.h.f. or u.h.f. is obviously preferable, in order to limit the range achievable, but this brings us back to the question of equipment cost.

Informed sources are quoting £150 as the likely cost of a UK-produced hand-portable set. Just how many would be sold, when there are reputed to be factories in the Far East with output capacities of 25 000–50 000 CB sets per month, and FOB prices for 5 W output, 40-channel car transceivers as low as £25? Without some sort of import quota system for at least a limited period, our communications industry would suffer in the same way that our hi-fi industry already has, and our balance of trade situation be made even worse.



**Keith Woodruff — Assistant Art Editor**

After leaving grammar school, Keith began his working life as a junior in the art department of a print company. He next joined Metro-Goldwyn-Mayer Film Studios as a Set Decorator, where he stayed until the studios closed down. Keith then had an unsettled spell drifting from job to job until he joined IPC in 1973.

Having lived in Hoddesdon, Hertfordshire and commuted to London, he finds that the move to

Poole has drastically cut his travelling time to work. This gives him more time with his wife and daughter, who find the move to Dorset one of the best things to have happened to them.

Keith and his family are members of Poole Camera Club, with Keith and his daughter actively engaged in competitions. His other interest is gardening, growing vegetables, soft fruit and cacti in a greenhouse.

## Catalogues

Belzer, one of Europe's leading hand tool manufacturers, have been producing high-quality tools in their West German works for almost 100 years. A selection of some 200 precision electronic tools is now available from Toolrange Ltd.

Belzer are certainly not cheap but meet the highest standards of quality and finish. The range includes, special pliers with spring-loaded handles, cutters, screwdrivers, tweezers, adjustable tools and complete tool kits.

To receive a free 32 page catalogue and price list, apply to: *Toolrange Ltd., Upton Road, Reading RG3 4JA. Tel: (0734) 29446 or 22245.*

Watford Electronics' latest catalogue contains 92 pages, packed with the most useful information for the electronics constructor. Watford also supply kits for many PW projects, including the *Purbeck Oscilloscope* (for details see Watford's advertisement).

The catalogue costs 50p plus 25p p&p, available from: *Watford Electronics, 33/35 Cardiff Road, Watford, Herts WD1 8ED. Tel: (0923) 40588/9.*

Marshall's latest catalogue has been expanded from 40 to 48 pages and includes many new items, such as, oscilloscopes, KIM and PET microcomputers, extended capacitor and switch ranges, more tools and a new digital multimeter.

A new feature of the catalogue is the limited line section covering obsolete items. The catalogue is available at 50p post paid or 40p to callers at their branches. *A. Marshall (London) Ltd., Kingsgate House, Kingsgate Place, London NW6 4TA. Tel: 01-624 0805.*

Astra, the electronic component mail order company, inform us their latest catalogue is now available. Among the many items featured are crystals, i.c.s, resistors, capacitors and electronics books. The free catalogue is available if you send a sae to; *Astra-Pak, 92 Godstone Road, Whyteleafe, Surrey CR3 0EB.*

## Teach-in

The University of Salford is again running a one-week course in July 1979 on Electronic Applications for Teachers. The aim of the course is to provide teachers who have some basic knowledge of semiconductor electronics with the opportunity to study the subject in greater depth. The

material covered will be adequate for the option of the JMB 'A' level physics syllabus, or other syllabi of comparable standard. The course will be devoted primarily to the study of operational amplifier and integrated logic circuit applications, approximately half the time being spent on experimental work.

The course organiser is Dr E. A. Flinn, of the University's Department of Electrical Engineering. For further details contact: *The Administrative Assistant (Short Courses), Room 110, Registrar's Department, University of Salford, Salford M5 4WT. Tel: 061-736 5843, extension 449.*

## Mobile Rallies

Otley Radio and Electronics Society (G8JTD, G3XNO) are holding "The Northern Mobile Rally 1979," at The Victoria Park Hall, Keighley on Sunday 20 May, between 11.30am and 5.30pm. There will be talk-in stations on S22 and SU8 also trade stands, films for the children, refreshments, bar and many other attractions. Further details from: *Jack E. Annakin G8DFZ, 25 Ashfield Place, Otley, West Yorkshire LS21 3JN.*

Maidstone YMCA Amateur Radio Society (G3TRF, G3YSC) Mobile Rally is to be held at the Y Sports centre, Melrose Close, Maidstone, Kent, on Sunday 27 May, 1979, commencing at 11.00am. In addition to talk-in stations using the callsign GB2YSC on 1925kHz s.s.b., 144.270MHz s.s.b., and S22 f.m., there will be bring-and-buy stalls (10% to club funds), covered trade accommodation, on-site parking, snack bar and special attractions for all the family. Further details from: *John Parker, 42 Mote Road, Maidstone, Kent. Tel: (0622) 50350.*

## Getting started

A new careers publication has been issued by the Institution of Electrical and Electronic Technicians Engineers (IEETE) entitled: "*Engineering a Career in the electrical and electronics industry*".

The booklet avoids excessive detail, concentrating rather on giving a general picture of the profession of electrical and electronic engineering, and the qualifications required to become a Technician Engineer, a Technician or a Chartered Engineer. The publication should be useful not

only to young people considering their career, but also to those engaged in offering careers advice and guidance.

Copies are available on request from: *The Secretary, IEETE, 2 Savoy Hill, London WC2R 0BS.*

The Department of Industry has also produced a full-colour brochure entitled: "*Microelectronics—the new technology*", which should help the non-specialist to understand the basic principles of the new "silicon-chip technology". Copies of the brochure are available from: *The Electronics Applications Division, Dean Bradley House, 52 Horseferry Road, London SW1.*

## Look you here

Barry College of Further Education Radio Society are holding their annual Welsh Amateur Radio, TV, Electronics and Computer Exhibition at the Barry Memorial Hall, Hoton Road, Barry, S. Glamorgan, on Sunday, 20 May, 1979, commencing at 11.00am. There will be all the usual attractions including a licensed bar. Further information from: *Reg Rowles GW4FOM, 4 Cowbridge Road West, Ely, Cardiff CF5 5BR. Tel: (0222) 565656.*

## Here we are again!

Once more it's time for the RSGB Amateur Radio Exhibition, at Alexandra Palace. The two-day exhibition will be open between 10.00am and 7.30pm on Friday, 11 May, and 10.00am and 6.00pm on Saturday, 12 May, 1979.

The RSGB will occupy their largest-ever stand at the exhibition with staff and members there to answer your questions and run a talk-in station GB2AP on S22 and SU8, also listening-watch on 144.28MHz s.s.b.

Among the many features of the exhibition are stands from other amateur organisations, including RAYNET, trade exhibitors, films for the newcomer, a full range of catering amenities and a larger supply of real ale than last year at the licensed bar.

Admission will be 60p (RSGB members 50p), children under 12yrs free. Facilities for the disabled are available, plus free parking for up to 2,000 cars.

Technical staff from *Practical Wireless* will be attending the exhibition on stand N10, and look forward to meeting as many as possible of our readers.

# PASSIVE

## 10:1 DIVIDER

### I. HICKMAN

# PROBE

FOR THE PW PURBECK

Most readers will know that when using a multimeter to measure the voltages at various points in a circuit, account must be taken of the usually small, but none-the-less finite, current drawn by the meter. This additional circuit loading can actually change the voltage at the point of measurement by a significant amount if the source resistance is high.

Fig. 1a shows the case where the emitter and base voltages of a small signal amplifier stage are measured separately. The figures in square boxes are the voltages as measured by a  $1k\Omega$  per volt meter on the 10V range, whilst the figures without boxes are the actual voltages when the meter is not connected. The emitter voltage changes by a negligible amount, as the transistor acts as an emitter follower, i.e. a low source resistance. However, the source resistance of the base circuit is  $16.6k\Omega$  ( $22k\Omega$  and  $68k\Omega$  in parallel), which is not negligibly low compared to the  $10k\Omega$  resistance of a  $1k\Omega$  per volt meter on the 10V range.

The erroneous conclusion one might draw if no allowance were made for the meter loading effect is that the transistor is cut off! The figures in round boxes are the voltages as measured on the 10V range of  $120k\Omega$  per volt meter and, as can be seen, the error due to meter loading is small. For this reason, multimeters specifically meant for electronic work (as distinct from general electrical work) have a sensitivity of at least  $10k\Omega$  per volt, commonly  $20k\Omega$  per volt and not infrequently  $30k\Omega$  per volt or even higher.

### Waveforms

Exactly the same problem of the measuring instrument loading the circuit and actually changing the very voltage that one is trying to measure, can arise when using an oscilloscope.

It should be obvious that with an input resistance of  $1M\Omega$ , the oscilloscope loads the circuit under test less than a  $20k\Omega$  per volt multimeter (for voltage ranges up to 50 V full scale deflection).

However, the oscilloscope is specifically used for examining voltage waveforms, i.e. voltages which are changing. Therefore, we also have to consider the input capacitance of the oscilloscope and this amounts to a few tens of picofarads (pF).

Whilst this would generally cause no problems at audio frequencies, the *PW Purbeck* might be typically used to examine, say, a 1MHz square-wave. An ideal square-wave contains harmonics extending up to an infinitely high


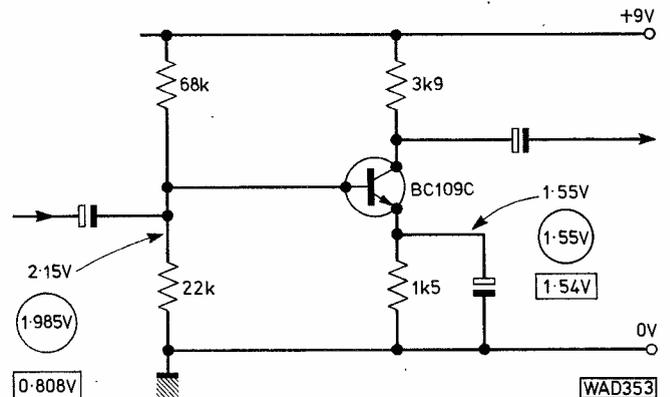


Fig. 1: (a) above, shows the effect of  $20k\Omega/V$  and  $1k\Omega/V$  meters on voltages measured. (b) below, is the circuit of a 10:1 probe to reduce circuit loading


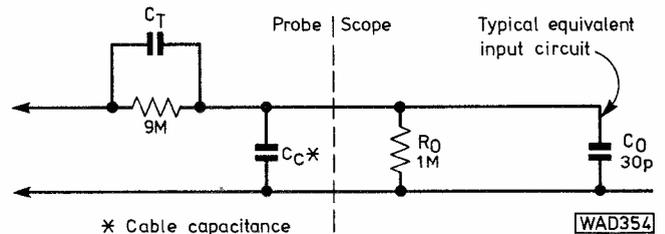


frequency and even a "practical" 1MHz square-wave will involve frequencies greater than 10MHz. Now 30pF (and the input capacitance of the *PW Purbeck* oscilloscope is of this order) has a reactance of only  $500\Omega$  at 10MHz and could thus considerably affect the waveform unless the source impedance were under  $50\Omega$ ! In fact, matters are a good deal worse than this, as we have not allowed for the capacitance to ground of a lead from the test point to the oscilloscope—trying to connect the circuit under test directly to the input connector of the oscilloscope with negligible lead lengths is always tedious and often impossible. Experience dictates that for general-purpose use, a lead of two to three feet is needed, screened to avoid hum pick up when working on high impedance circuits. Even choosing a low capacitance screened lead such as  $75\Omega$  coaxial cable, we have about 20pF per foot, so that  $2\frac{1}{2}$  feet of cable plus the input capacitance of the oscilloscope leaves us with a total of around 100pF. The purpose of a 10:1 divider probe is to reduce the effective input capacitance of the scope plus connecting lead to nearer  $10pF$ .

# ★ components

R1 30MΩ 1% (Vavard)  
 C1 12pF ceramic 500V  
 CA 2-220F trimmer (Mullard)  
 1 metre 75Ω "Uniradio 70"  
 coaxial cable  
 100.4B1C plug with hexagonal  
 screw type cable clamp  
 Tinsplate, Araldite, etc. as  
 required

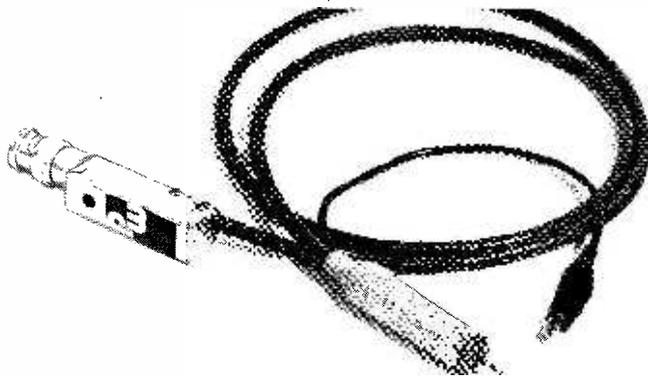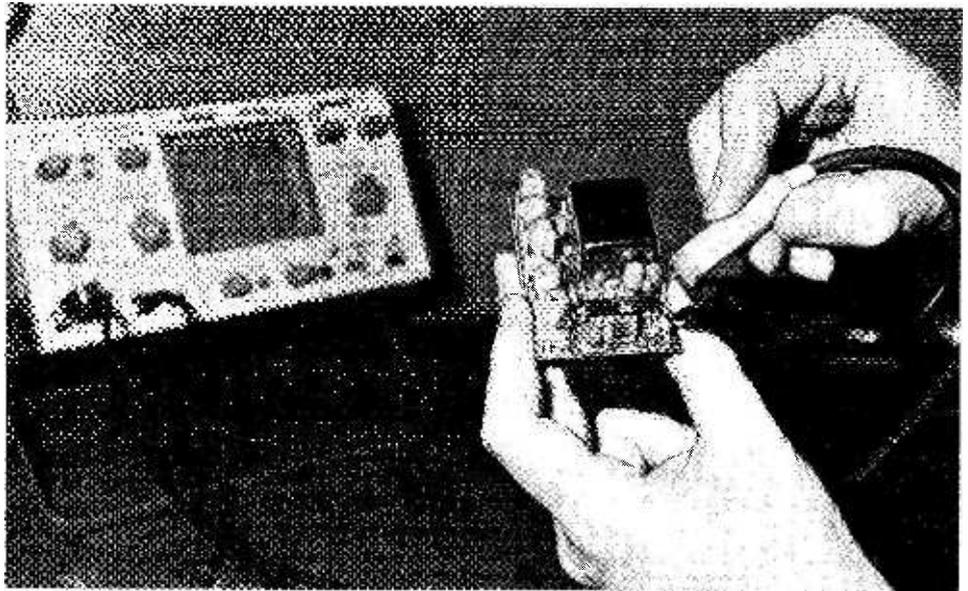**The 10:1 passive divider probe is a useful addition to the PW Purbeck oscilloscope. On the right it is seen being used with a Scopex 4D10 scope while the picture below shows the completed probe**



## Theory of Operation


Fig. 2a shows the circuit diagram of the traditional type of oscilloscope probe. The capacitance of the screened lead plus the input capacitance of the oscilloscope form one section of a capacitive potential divider. The trimmer  $C_T$  forms the other and it can be set so that the attenuation of this capacitive divider is 10:1 in volts, which is the same attenuation as provided by  $R_A$  ( $9M\Omega$ ) and the  $1M\Omega$  input resistance of the oscilloscope. When this condition is fulfilled, the attenuation is independent of frequency (Fig. 3a). Assuming  $C_E$  the cable plus 'scope input capacitance ( $C_E = C_c + C_o$ ) totals  $100pF$ ,  $C_T$  should at any frequency have a reactance nine times that of  $C_E$ . i.e. will equal  $\frac{1}{9}$  of  $C_E$ . If  $C_T$  is too small, high frequencies (e.g. the edges of a square-wave) will be attenuated by more than 10:1, whereas the attenuation of the steady level will still be 10:1 resulting in the waveform of Fig. 3b. Conversely if  $C_T$  is too large, the result is as in Fig. 3c. All of the above has assumed that  $C_E$  is constant and this will only be so if the input capacitance of the 'scope is the same on all ranges. This is the purpose of capacitors C3-6 in Fig. 2, p. 29 of the June 1978 issue of *PW* as they allow the input capacitance of positions 2-5 of S3B (Input Range) on the *PW* Purbeck to be set to the same value as on position 1.

The rounding or pip on the edges of a square-wave will be difficult to see on a very low frequency signal, as with the slow time-base speed needed, the square-wave will appear to settle very rapidly to the positive and negative levels. Conversely, at very high frequencies, the displayed square-wave amplitude will be affected by the capacitive divider only. The time constant  $CR$  of the oscilloscope


input is  $30pF \times 1M\Omega$  or 30 microseconds. Therefore, waveforms as in Fig. 3 will be seen with a square-wave input of around 1kHz.

At very high frequencies, where the length of the probe cable is an appreciable fraction of a wavelength, reflections will occur, as the cable is not terminated in its characteristic impedance of  $75\Omega$ . For this reason, commercial oscilloscope probes often incorporate a resistor of a few tens of ohms in series with the inner of the cable at one or both ends, or use a special cable with an inner made of resistance wire. Such probes are suitable for oscilloscopes with a bandwidth of 100MHz or more, but in the case of the *PW* Purbeck, a resistor is already incorporated in the input circuit of the oscilloscope, so that further resistors in the probe are unnecessary.

Fig. 2a shows  $C_T$  as a variable capacitor. However, this is mounted at the business end of the probe, where it is not very convenient to accommodate a trimmer. Therefore, a fixed capacitor is used for  $C_T$ , permitting a neat, compact design for the probe head. Adjustment is carried out by means of a trimmer mounted in a small box at the oscilloscope end of the probe. Inevitably, this means that  $C_E$  (and hence the capacitive loading of a circuit under test) is higher than with the scheme of Fig. 2a, but only slightly, and is well worth the extra convenience. With the

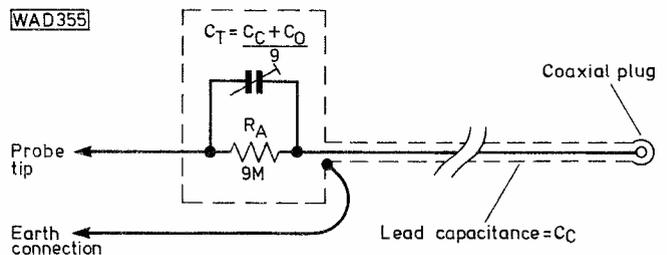

**Fig. 2: (a) above shows the traditional 10:1 divider probe and (b) below the design used for the PW Purbeck scope probe**

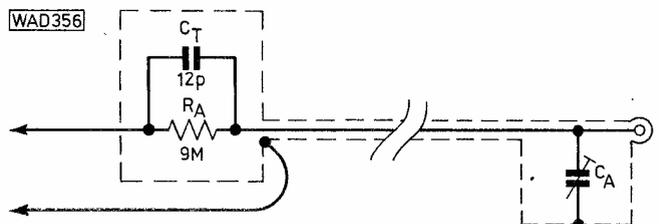

chosen design of Fig. 2b in use, CA is adjusted so that  $C_T = \frac{1}{9}(C_C + C_A + C_O)$ , by the simple procedure of setting it to reproduce a test square-wave as in Fig. 3a rather than b or c.

## Construction

This calls for the employment of a little ingenuity in the use of materials such as Araldite, tinfoil (from the proverbial cocoa tin or similar), insulating tape, etc. and of tools such as tin-snips, snipe nosed pliers and the like. If you are adept at this sort of thing, construction is really straightforward and sketches of the necessary bits and pieces are given in Fig. 4.

The housing of CA is fabricated in two parts, the body being soldered to the rear of a BNC plug and the cover fitted later when construction and testing are complete. The BNC plug used by the author had a cable clamping sleeve with hexagonal flats and the body of the CA housing was shaped and soldered to this.

The method of fixing the 75Ω coaxial cable is crude but effective, the Araldite being essential to support the cable firmly. Araldite is also used, again as a strain-relief, at the cable entry into the probe head. The body of this is also made from tinfoil and can usefully be as small as RA and CT will allow, bearing in mind that these should be firmly mounted and reliably insulated. The author used a long 8BA brass bolt as the probe tip. After assembly, the shank was filed smooth, the tip sharpened and then flatted and nicked as shown in Fig. 4. This enables it to be hooked on to wires, transistor or diode leads, etc. when checking through a circuit and is a very useful feature as it leaves the hands free.

The reliability of the earth wire is most important. Many commercial probes, even of the best known makes, give continual trouble due to the earth lead going open circuit. Ordinary stranded wire will not stand up to the continual flexing, so the author used black plastic covered extra-flexible wire as sold for multimeter leads and this has proved very successful. The free end is terminated in a miniature croc-clip, preferably the sort with an insulating plastic boot. It must be stressed that the 75Ω coaxial cable must have a stranded inner conductor, e.g. "Uniradio 70". Cable with a solid inner is too stiff to be convenient in use and with the flexing to which it will be subjected, the inner will certainly go open-circuit eventually.

Note that as the probe attenuates the waveform to the oscilloscope by a factor of 10, nine-tenths of the voltage applied to the probe will appear across RA and CT. The latter should therefore have a voltage rating adequate to cope with the highest voltage the probe may experience, say 500V working or better still, 1000V.

## Setting Up The Probe

This requires a square-wave generator with an output which can be set to around 100mV peak-to-peak at a frequency of 1kHz or thereabouts. If it has accurately known output levels it can also be used for checking the oscilloscope's "Y" gain settings and the Oscilloscope Calibrator published in the January 1977 issue of *PW* is quite suitable. Alternatively, the design shown in Fig. 5 can be used. This calibrator is powered from the front panel accessory socket of the *PW* Purbeck oscilloscope itself.

Whichever source is used, connect the probe to the oscilloscope with the "Y" gain at  $10\text{mV} \times 0.5$  and a sweep speed of  $500\mu\text{s}$  per division. Apply a square-wave source and adjust "Trig Level" for a locked picture. The

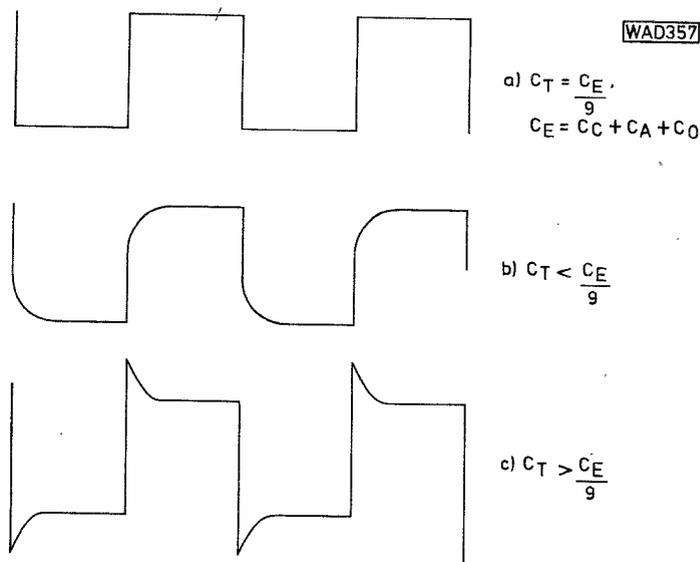


Fig. 3: The effects of misadjustment of  $C_T$

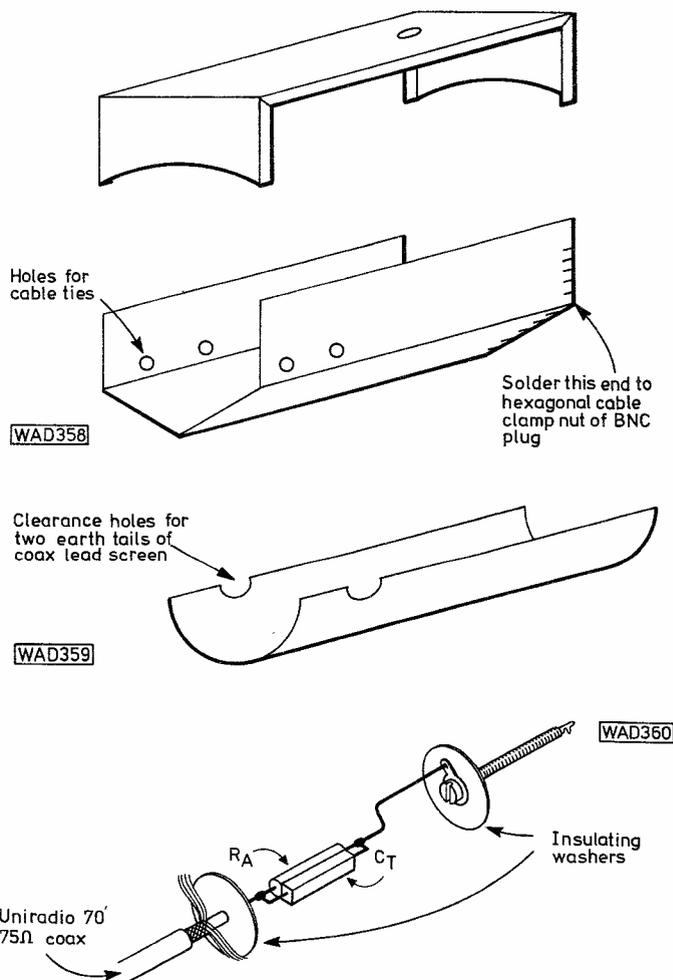


Fig. 4: The component parts of the probe housings. (Top) the housing for CA (Centre) the half shell for the probe head, two of these are needed. (Bottom) the details of the probe head wiring

Notes. CA mounted in housing at BNC plug end. RA and CT are insulated and fitted between shells which are then soldered along their seams. The screen tails are soldered to the outside of the shells. Araldite is added at both ends, the insulating washers preventing ingress. The coaxial cable is secured to the CA housing by soldering the screen tails, wire ties through the four holes provided and also by Araldite. The inner connects to CA at probe head and BNC plug inner at the other end





# student radio

C. ARUNDEL

Interesting experiments in community broadcasting are currently being conducted in three English new towns: Telford, Basildon and at Newton Aycliffe in County Durham. Further closed-circuit local broadcasting has been introduced to suburban housing developments in Greater London.

Stations operating in the medium frequency band and based at seventeen universities and colleges in the United Kingdom have broadcast successfully for several years. Indeed the oldest of these, University Radio York, recently celebrated the tenth anniversary of its first broadcast, so this would seem an appropriate time to take a look at this form of radio.

## Origins

It is often surprising how widely the effects of a simple new idea are felt, and the growth of campus radio certainly seems to fall into this pattern. It has its origins in the plan of a single student, who saw the potential value of this kind of facility as a forum for information and ideas within a university community. So it was that in 1967 the administration of York University was approached in order that the response to a scheme to operate a radio station might be gauged. It is worth pointing out at this juncture that a closed-circuit TV system had operated successfully since the University's inception several years earlier. There was therefore a generally favourable response to the idea, and representations were consequently made to the Post Office asking that the project should be allowed to proceed.

Lecturers currently at York remember the problems encountered in persuading the authorities of the feasibility of the project to create the first licensed radio station in England independent of the BBC. The fact that experimental local radio organised by that body was also planned at the time, may have been influential in their decision to provide a licence. University Radio York was eventually allocated the medium wave channel 998kHz 301 metres, on the understanding that the signal should be audible only at the University site. The experience gained at York was to prove useful at the University of Kent, where plans for a similar project were in preparation.

## Transmitting Installation

In order to restrict the signal to the campus as required, a system of aeriels known as induction loops are in use at URY and the stations which have followed. Indeed, this is the only feature of the transmission systems of campus radio to differ from local radio generally.

The signal from the transmitter is transported to each part of the campus via runs of coaxial cable terminated in a r.f. transformer. The secondary winding of this transformer is connected in parallel with a single loop aerial, composed of approximately 25 metres of insulated wire wound in a coil upon a frame and connected to a variable capacitor, so forming a parallel tuned circuit, subsequently brought to resonance at the operating frequency. (Medium wave DXers will recognise this as a further application of the popular DX reception aerial).



The on-air studio at University Radio York, showing Sony mixer and cassette decks, Thorens TD125 transcription turntables and Revox B77 tape deck


Each loop provides a high field strength of transmitted signal at short range, but signal strength is very low at distances of only a few tens of metres from the aerial, minimising the risk of off-campus radiation. The loops are then installed on the roofs of groups of buildings to be supplied with programmes.

## Developments

At URY, 30 April 1969 marked the end of a period of experimentation with the first official broadcast, a programme recorded for the occasion by BBC presenter John Peel.

The development of URY has proved to be characteristic of many of the campus stations, the initial capital outlay being donated by the University or college student union, and annual grants being provided thereafter to meet running costs, though some stations have found supplementary sources of income. University Radio Bath, for example, have shown some enterprise in running their own disco which appears four nights or so every week at venues in the town. The stations are not permitted to carry advertising.

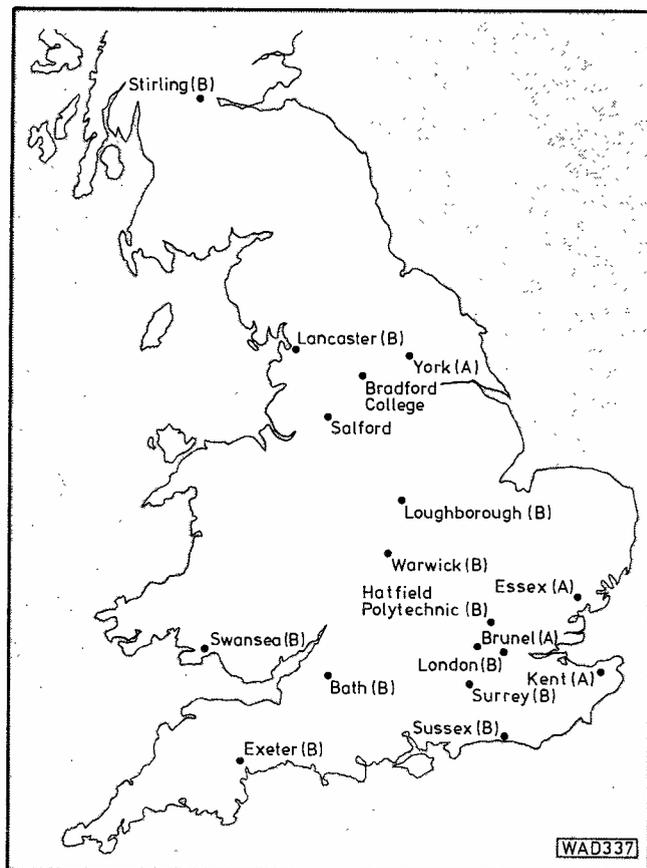As more stations came on-air it became clear that a co-ordinating organisation was required to negotiate with the licensing body and performing rights organisations, and to act as an information exchange between stations. Consequently the National Association of Student Broadcasters was formed, and each year its annual conference is hosted by one of the member stations.



**Campus stations in operation at June 1978. Stations given the suffix (A) use 999kHz, 300 metres. Those given the suffix (B) use 963kHz, 312 metres. These are the post-November 1978 channels**

## Programmes

The programme formats adopted contain music, news, "what's on" information and features; and generally, record companies are very generous in supplying a good selection of their latest material. Singles and album charts are run in conjunction with local record shops and playlists are used at many universities to ensure the music heard has a wide appeal.

Typically, a fast-moving breakfast show is broadcast daily, plus a teatime magazine programme of local news and interviews, request shows and a variety of other material until the early hours. Minority interest features are also to be heard; thus the output of UKC Radio at Kent University includes arts reviews, plays, short stories, classical music and current affairs during the 80 or so hours of their broadcasting week. Apart from programmes presented during the course of a normal week, there is often news of particular local interest, and it is on these occasions that the benefits of campus radio become clear.

Stress is placed upon putting people on the air as soon as they feel confident in the use of studio equipment. The duration of courses being as they are, roughly one-third of the personnel depart each year and the gap which they leave must be filled as soon as possible. The policy is also consistent with the concept of ease of access and a belief that the most effective way to produce competent presenters is to give them plenty of practice.

Surveys carried out by the stations have shown a demand for regular news summaries and there has therefore been a tendency to relay the hourly bulletins of Independent Radio News, by arrangement, from the v.h.f. transmissions of commercial radio. Others have formed links with the BBC; Radio Bradford college produces a weekly programme of interest to students in West Yorkshire, which is broadcast by BBC Radio Leeds, and a link has also developed between the Kent University station and BBC local radio.

## The Future

As for the future, it seems likely that campus radio will be brought within the auspices of the IBA. What the effects of this interaction will be remain to be seen, however several stations have pointed out that if the IBA was to assume responsibility for maintenance of transmitters, as is done at present with local commercial radio, it would be possible to devote more time to the basic process of programme production.

Whatever the future holds, the fact that University radio stations not only survive on relatively small budgets but that their number increase annually suggests that small community radio stations could succeed in a wide range of other environments. It is to be hoped that the next ten years of student radio prove as interesting as the last.

**PLEASE MENTION  
PRACTICAL WIRELESS  
WHEN REPLYING  
TO ADVERTISEMENTS**

# LOGICAL NOUGHTS & CROSSES

J.D. MITCHELL PART 1

## Mounting the l.e.d.s

The display l.e.d.s are mounted on PCB 3 and pushed up through holes drilled in the case lid. The board is held to the lid by the 6BA bolts used as input switching studs.


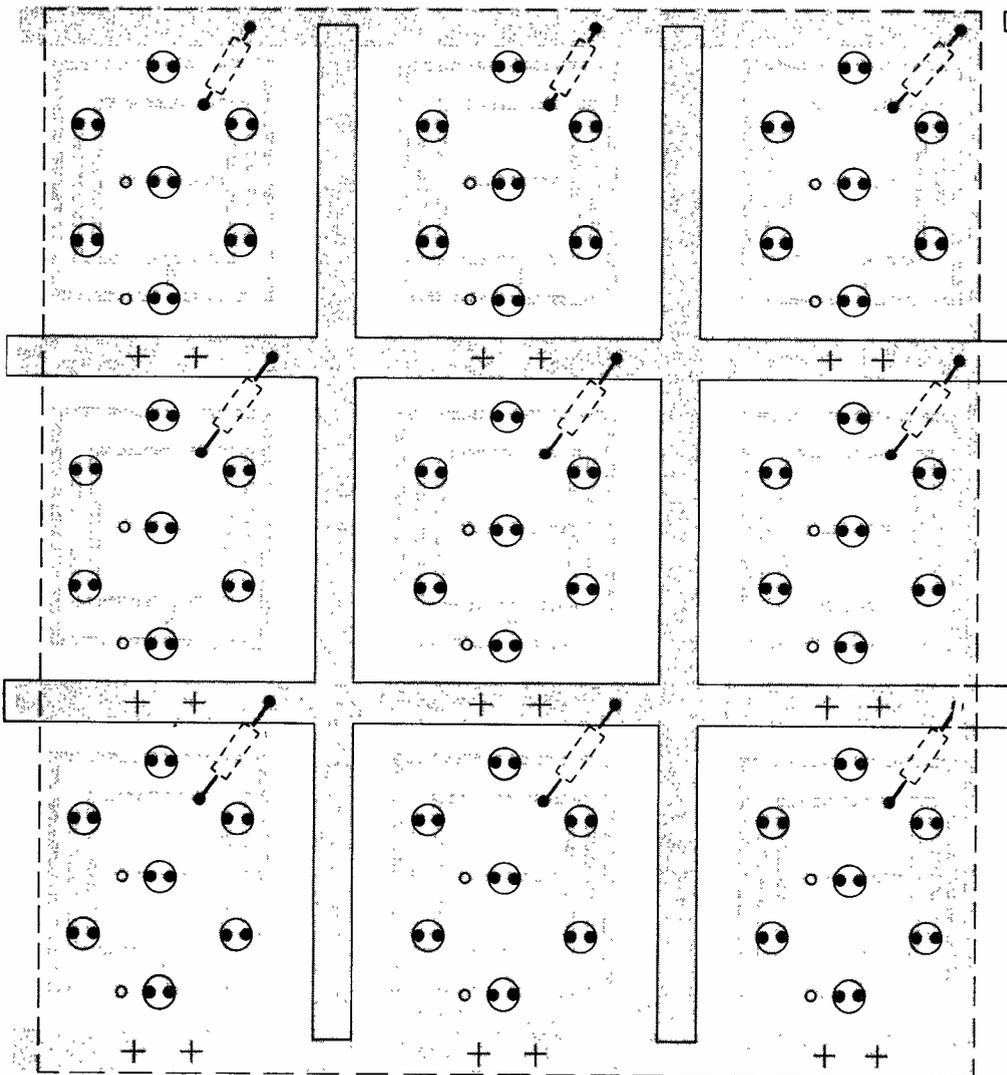


Fig. 5: Component placement layout for PCB3

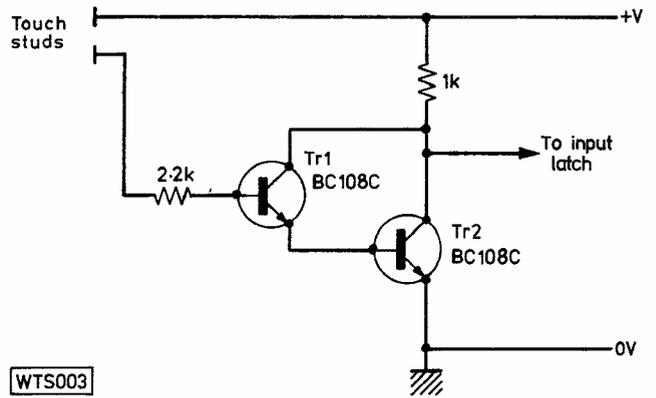


WTS003

Fig. 6: The touch-switch input circuit, note this circuit is repeated nine times on the p.c.b.

The touch-switching input components are mounted on PCB 4, which is held on edge at the switch end of the case behind the corner pillars.

The power supply used in the prototype comprises of a battery-holder containing four HP11 or type C cells held two by two, and a silicon diode. The diode reduces the positive rail from 6V to protect the input latches from damage. Alternatively, any supply giving 5V at 500mA d.c. may be built in if a larger case is used.

WAD342

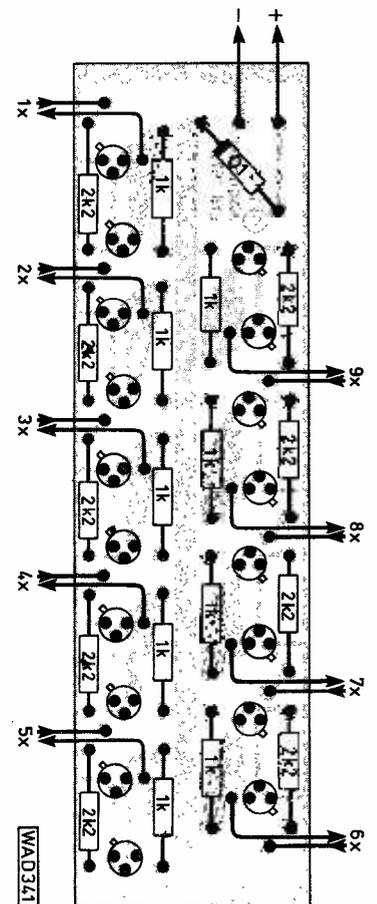

WAD341

Fig. 7: Component placement layout for PCB4

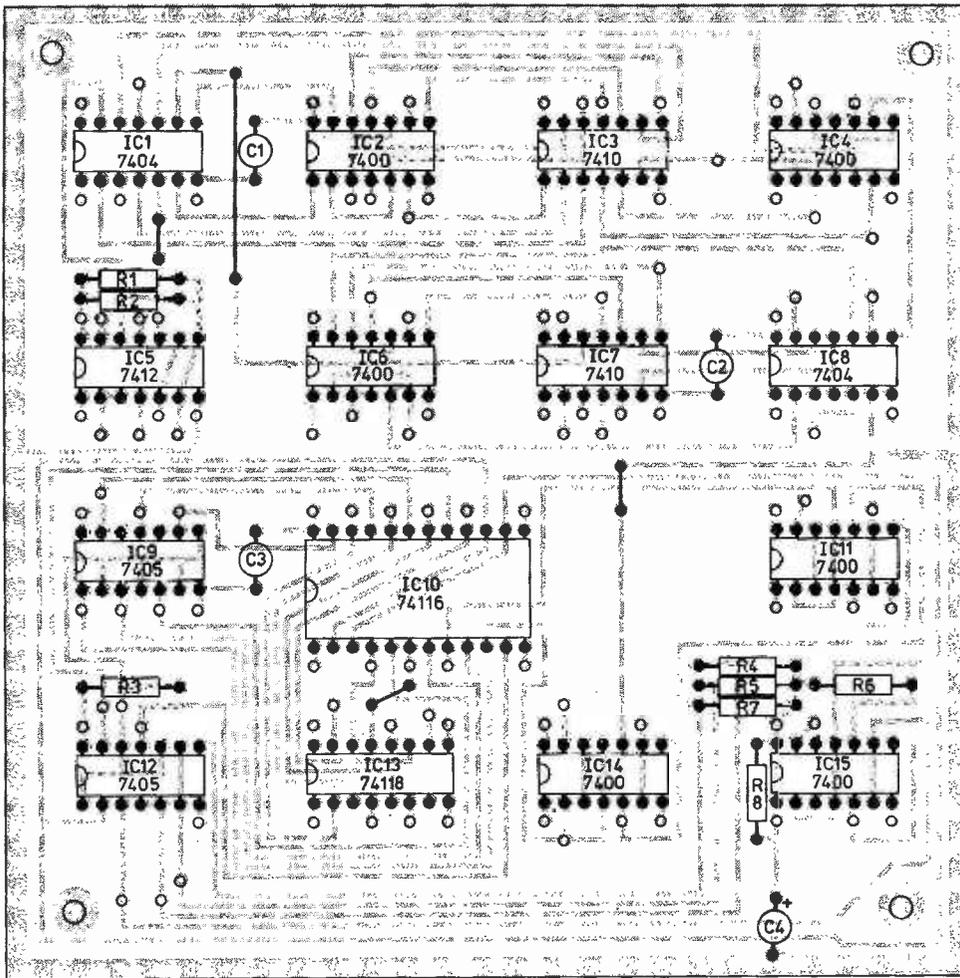


Fig. 8: Component placement layout for PCB1

WAD344


## Making the display

Display Board 3 is best constructed by inserting the l.e.d.s and initially soldering one leg only. The dropping resistors are mounted on the copper side either on pins pushed down through the board and cropped on the l.e.d. side, or by blob-soldering. Their leads should be sleeved. All connections from Board 1 are similarly made on the underside. The touch-switch screws may then be inserted


in the lid and held temporarily with strips of Sellotape. Invert the lid and drop a washer over each screw as spacers. Board 3 may then be fitted, and bolted in place.

Board 4 is mounted with the component side facing into the case. The leads from Boards 1 and 3 may be soldered in with the board close to the end of the case, and then lifted back as the board is placed in the case.

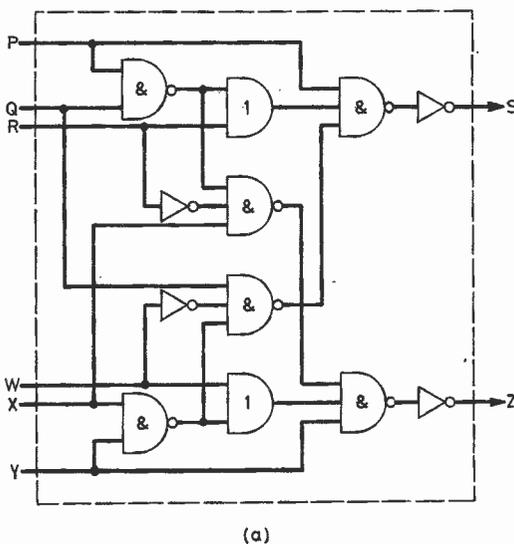It is very helpful in construction if leads between boards are colour-coded.



(a)

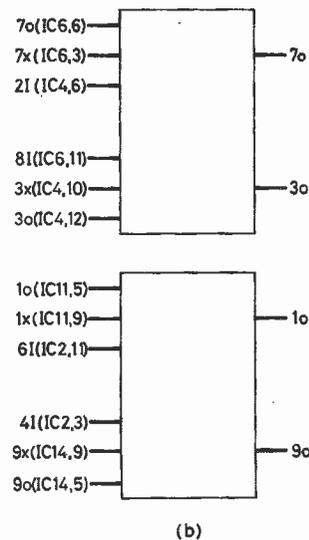

(b)

(c)

Truth table							
P	Q	R	W	X	Y	S	Z
1	1	1	1	1	1	1	1
1	1	1	1	1	0	1	0
1	1	1	1	0	1	1	1
1	1	1	0	1	1	1	0
1	1	1	0	1	0	0	0
1	1	1	0	0	1	0	1
1	1	1	0	0	0	1	0
1	1	0	1	1	1	0	0
1	1	0	1	1	0	0	0
1	1	0	1	0	1	0	1
1	1	0	1	0	0	1	1
1	1	0	0	1	1	1	0
1	1	0	0	1	0	1	0
1	1	0	0	0	1	1	1
1	0	0	1	1	1	1	0
1	0	0	1	1	0	1	1
1	0	0	1	0	1	1	0
1	0	0	1	0	0	1	1
1	0	0	0	1	1	1	0
1	0	0	0	1	0	1	0
1	0	0	0	0	1	1	0
0	1	1	1	1	1	0	0
0	1	1	1	1	0	0	0
0	1	1	1	0	1	0	1
0	1	1	1	0	0	0	0
0	1	1	0	1	1	0	0
0	1	1	0	1	0	0	0
0	1	1	0	0	1	0	0
0	1	1	0	0	0	1	0
0	1	0	1	1	1	0	0
0	1	0	1	1	0	0	0
0	1	0	1	0	1	0	0
0	1	0	1	0	0	1	0
0	1	0	0	1	1	0	0
0	1	0	0	1	0	0	0
0	1	0	0	0	1	0	0
0	1	0	0	0	0	1	0

Fig. 9: Variations on "illogical moves"

WRM112

## Illogical moves

The program of the basic circuit is designed to make no reply to certain "illogical" moves, those associated with the five 3-input NAND gates which enable the display inhibit. This was considered to be the logical response whereby 126 games may be won by the player.

A variation to the above is possible using additional output gating as shown in Fig. 9. A reply is routed to one of the two Nought displays when such a move is made (see Truth Table). The number of games which may be won by the player is reduced to 16. Two circuits as in Fig. 9(a) are required, inputs taken from display gating on PCB 1 and outputs to the l.e.d. display as shown in Fig. 9(b).

Additional components required for the above are one SN7432 (Quad 2 i/p OR), three SN7410 (Triple 3 i/p NAND), two SN7404 (Hex. inverter) and one SN7400 (Quad 2 i/p NAND). These may be mounted on an additional board above PCB 1, but a deeper case will be needed. The track between IC5-6 and 5-8 on Board 1 should be cut. R1 is replaced by a 9.1kΩ, IC5-6 is linked to IC 1-1 and R10 is replaced by a 1.5kΩ.

## Construction

The case is moulded in ABS plastic, and a number of p.c.b. fixings and other extrusions have to be removed from inside the case. This is simply done using a coarse-toothed hacksaw blade, around which a piece of tape is wrapped as a grip. In order to fit the battery-holder flush to the grooved end of the base, approx. 2.5mm must be carefully removed from the inner edges of the two nearby corner pillars, through which the screw fixing is made. This may also be done with the saw blade. The batteries are fitted here to allow clearance for the switches mounted in the lid at the lower end. The diode is soldered directly to the positive terminal of the battery-holder in the prototype, but could be mounted on Board 4.

Holes in the lid for l.e.d.s and switch studs may be positioned by gumming a tracing of Fig. 5 on top. Holes for the l.e.d.s should be drilled using a 5.10mm drill; those for the studs require a 2.95mm drill. The squares on the lid may be marked out using a sharp knife and a straight edge. "Brasso" or a similar metal polish will clean up the lid after soaking off most of the paper. The lines around

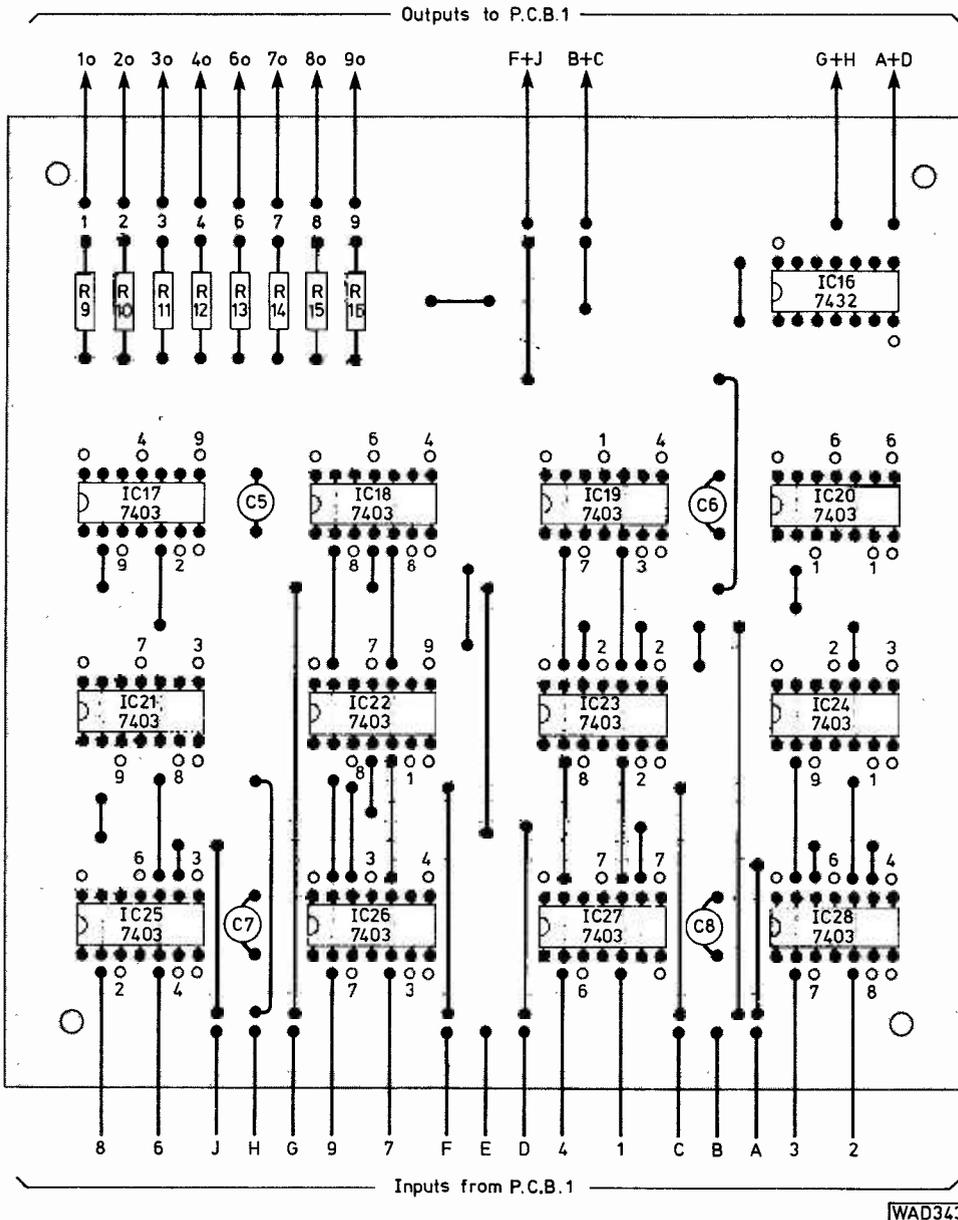


Fig. 10: Component placement layout for PCB2

WAD343

the squares may then be used as guides for thin plastic strips fixed using acetone as an adhesive (hold the strips in place and lightly brush the liquid along the edges with a fine brush. The weld will be firm in about 30 seconds).

## Minimising costs

In order to keep cost to a minimum, only single-sided p.c.b.s are used and i.c.s are soldered directly into the boards. PCB 1 should be constructed as shown, using Veropins at all points where connection is made to more than one other pin or to another board. After testing the completed board, remove R5 before connecting to PCB 2.

PCB 2 should be constructed as shown, using Veropins on all NAND gate outputs and where connections are made to Board 1. After checking, it may be mounted beneath Board 1 using 4BA nuts and bolts with 12mm spacers. Input leads from Board 1 may then be connected, and Board 2's outputs checked before connecting back to Board 1. Operation of the complete logic circuit may then be tested, using a probe as input and a logic probe. (A probe circuit is given in Fig. 11.)

The bolts holding the two boards together should be heads down. A blob of epoxy will then fix them to the floor of the case, in the space left by the battery-holder, which is fixed similarly.


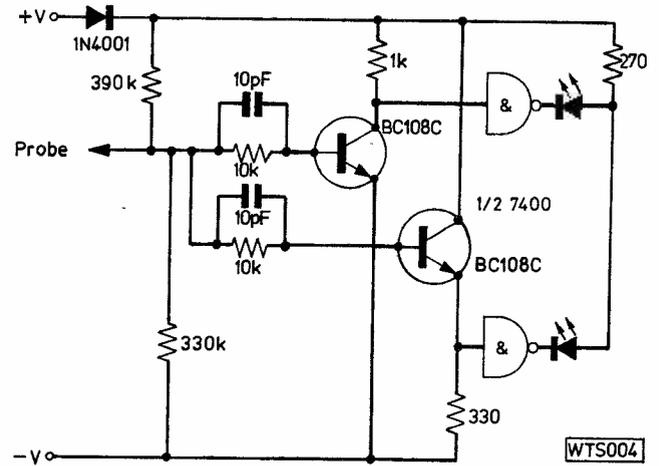


Fig. 11: The logic probe circuit diagram
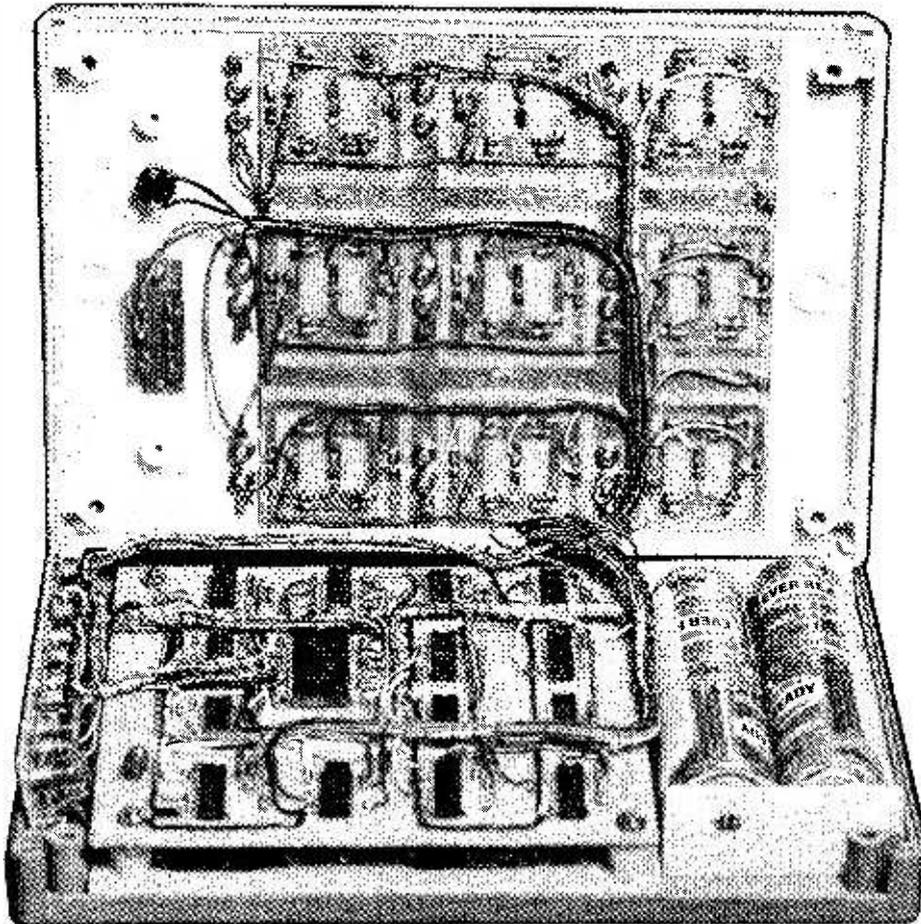
### An internal view of the Author's prototype



## Embellishment

There are of course many extras which may be added to the basic circuit, such as a win indication, delayed replies, an external larger display, etc. Deeper cases are available in the same style for those who may need the extra space. ●

Full-size paper prints of the p.c.b. layouts are available at an inclusive price of 40p. Apply to *Practical Wireless, Westover House, West Quay Road, Poole, Dorset BH15 1JG*. Cheques and P.O.s should be payable to: *IPC Magazines Ltd.*

## Mainline takeover

Arrow Electronics Ltd. of Leader House, Coptford Road, Brentwood, Essex, have acquired the entire stock of Mainline Electronics Ltd. previously of Windsor and Slough, Berks.

Mainline Electronics audio equipment will be available from Arrow and it is contemplated that production of the Mainline amplifiers will be continued, as it is proposed to merge these products with Arrow's existing "Leader" range of kits.

## Can I Help You!

Are you the secretary, organiser or general dog's body of your local radio club or any other group whose functions may interest readers of *PW*. If so, let me know and I will endeavour to publicise your rally, get-together whatever, through this column. Remember though, we compile the magazine some time ahead of publication day (e.g. this note was written in mid-March), so, the earlier I can have details, the better.

Alan Martin

## RAE Reprint

A reprint of the complete series—So You Want to Pass the RAE?—including details of the new examination format being introduced this year, is now available.

Order your copy by completing and returning the coupon on page 70.

## Hi-Fi f.m.

A new piece of equipment which greatly improves the quality of frequency modulation (f.m.) transmission has been developed in Australia.

For use with a typical £100 000 transmitter the new equipment—about the size of two cigarette packets—costs around £10.

It is the result of four years' research by Dr Keith J. Kikkert, senior lecturer in the Electrical and Electronic Engineering Department at the James Cook University of North Queensland, Townsville. Dr Kikkert, 34, was born in Amsterdam and went to Australia in 1962.

Tests of his new equipment have produced f.m. reception with a distortion factor 20 times less than the best



## New Portable Radiophone

Marconi Mobile Radio, a Division of Marconi Communication Systems Ltd, is now an approved supplier of equipment to the Post Office Radiophone Service and the new 'go-anywhere' telephone, the SV1320A, opens up completely new uses for the service.

With the extension of the East Pennine Radiophone Area coming into operation in the near future the SV1320A is a telephone that could be extremely attractive to new subscribers. The versatile equipment is designed to fit into the corner of a car boot with the control unit and handset easy to hand for the driver or

passenger. Take the equipment out of the vehicle, a simple operation taking less than a minute, and a completely portable telephone is available to take to your weekend cottage, on the boat, fishing, into the garden or wherever you need to be contacted.

With a battery or charger unit the equipment can be used as a temporary telephone at major construction sites and office accommodation before land lines are installed. The equipment works from 12 volts or by attached battery pack, which with normal operating will last a day without recharging. *Marconi Mobile Radio, M.C.S.L., Marconi House, Chelmsford CM1 1PL. Tel: (0245) 53221.*

equipment now used by large f.m. radio and t.v. stations.

Dr Kikkert said the reduction in distortion might even be much better than indicated, because there was no equipment available capable of measuring it above the "20 times" mark.

Conventional f.m. transmitters—those used in radio, television sound and microwave communication relays—generate at a high frequency. Dr Kikkert's success has been achieved by generating f.m. at a low frequency of 1MHz, which is then amplified and transmitted at 101MHz. Existing f.m. transmitters have a direct output. *Australian Information Service, Australia House, Strand, London WC2B 4LA.*




**Dr Kikkert with the piece of equipment he developed**
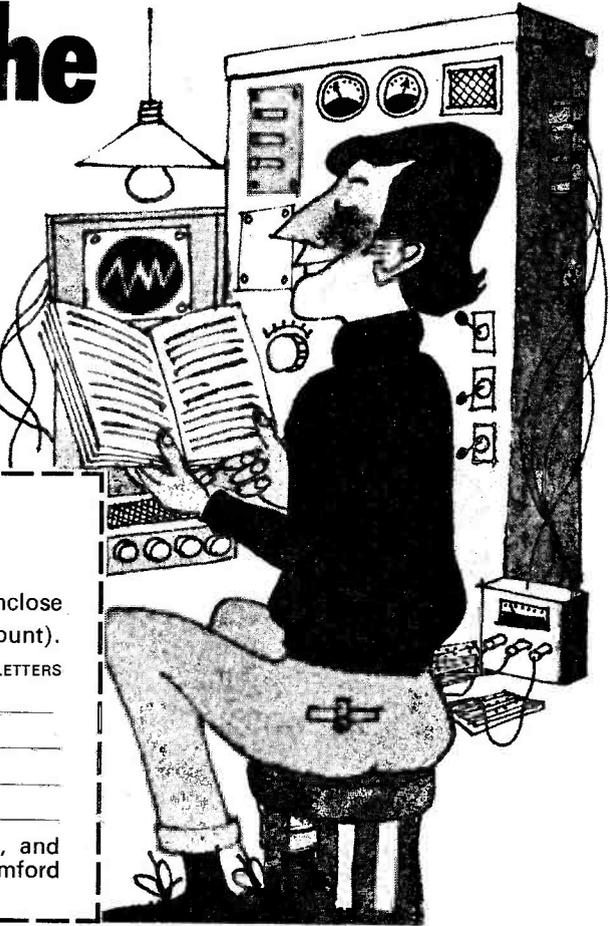
# Every month is the right frequency

When you're building a major project from a PW design, you want to be sure of getting every issue in sequence! Use this order form for a year's supply to be posted to you.

ANNUAL SUBSCRIPTION RATES (including postage and packing) U.K. £10.60. Overseas £10.60.



## practical WIRELESS SUBSCRIPTION ORDER FORM

Please send me Practical Wireless each month for one year. I enclose a Sterling cheque/international money order for..... (amount).

PLEASE USE BLOCK LETTERS

NAME Mr/Mrs/Miss

ADDRESS

POSTCODE

Make your crossed cheque/MO payable to IPC Magazines Ltd., and post to: Practical Wireless, Room 2613, King's Reach Tower, Stamford Street, London SE1 9LS.

# CHROMASONIC electronics

*your soundest connection in the world of components*

Dept PW1, 176 FORTIS GREEN ROAD, MUSWELL HILL, LONDON, N10 3HN

TELEPHONE: 01-883 3705

The items shown in this advert are just a small selection taken from our new 78/79 Catalogue which is now available. It contains everything from Resistors to the latest in Micro-processors. Don't delay order your copy today. The price is only 40p (inc. 45p vouchers).

Low Power Schottky and TTL				CMOS				I.C. sockets				BITS and PIECES				Regulators				Linear I.C.'s																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																												
N	LS	N	LS	N	LS	N	LS	N	LS	N	LS	N	LS	N	LS	N	LS	N	LS	N	LS	N	LS	N	LS	N	LS																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																					
7400.13*	19*	7449	.87*	74136	—	.39*	74191 1.21*	.75*	4000 .15*	4063 .81*	DIL (Texas)	Static RAM's	1+	17-63 64+	78M Series	CA3080	.75	7401.13*	19*	7450	.16*	74138	—	.55*	74192 1.21*	1.85*	4001 .16*	4054 1.29*	8 pin .10*	2102A (350ns)	1.05*	95*	.88*	+(POS) 500mA	CA3130E	.90	7402.15*	19*	7451	.16*	74139	—	.55*	74193 1.21*	1.85*	4002 .16*	4056 1.46*	14 pin .12*	2102A-2 (650ns)	1.29*	1.15*	1.08*	5v. 6v. 8v. 12v. 15v.	CA3140E	.37	7403.15*	19*	7453	.16*	74141	.76*	—	74194 1.21*	—	4009 .92*	4059 5.18*	16 pin .13*	2111A-1 (500ns)	2.46*	2.19*	2.05*	20v & 24v.	LM301AN	.30	7404.16*	21*	7454	.—	74145	.75*	1.05*	74195 1.01*	1.05*	4008 .92*	4060 1.24*	18 pin .18*	2112A-2 (250ns)	2.14*	1.90*	1.78*	All 60p* each	LM324N	.73	7405.16*	21*	7455	.—	74147	1.59*	—	74196 1.18*	1.05*	4007 .18*	4066 4.8*	20 pin .20*	2102 (350ns)	1.07*	.96*	.86*	79M Series	LM348N	.99	7406.26*	—	7460	.16*	74148	1.32*	—	74197 1.18*	1.05*	4009 .54*	4068 2.1*	22 pin .22*	MM5257 (TMS4044)	8.10*	7.19*	6.75*	-(NEG) 500mA	LM380N	.97	7407.26*	—	7470	.27*	74150	1.02*	—	74198 1.81*	—	4010 .54*	4069 2.1*	24 pin .26*	2114 (450ns)	8.10*	7.19*	6.75*	5v. 6v. 8v. 12v. 15v.	LM380N	1.73	7408.17*	19*	7472	2.3*	74151	.67*	.88*	74199 1.81*	—	4011 .18*	4070 2.1*	28 pin .30*	6810	3.50*	2.97*	2.52*	20v & 24v.	LM382N	1.33	7409.17*	19*	7473	.29*	74153	.67*	.48*	74201	—	4012 .18*	4071 2.1*	40 pin .44*	8080	5.95*	—	—	All 85p* each	LM3892N	.65	7410.15*	19*	7474	.28*	74154	1.21*	1.25*	74240	—	4013 .49*	4072 2.1*	—	8080	8.95*	—	—	78 Series	LM3803N	.70*	7411.25*	19*	7475	.29*	74155	.67*	.78*	74241	—	4014 .92*	4073 2.1*	—	9800	42.50*	—	—	+(POS) 1A	LM3803N	1.02	7412.18*	19*	7476	.30*	74156	.67*	.78*	74242	—	4015 .92*	4081 2.1*	—	E-Prom's UV	8126P	1.65*	—	18v & 24v.	SN78003N	2.32	7413.25*	40*	7478	.—	74157	.67*	—	74243	—	4016 .43*	4082 2.1*	—	1702A0	5.57*	—	—	5v. 6v. 12v. 15v.	SN76013N	1.55	7414.71*	79*	7482	.73*	74158	—	.58*	74247	—	4017 .81*	4085 .92*	—	27080	8.78*	—	—	All 85p* each	SN76023N	1.55	7415.25*	—	7485	1.18*	74160 1.21*	.39*	74248	—	—	4018 .92*	4086 .92*	—	TriState Buffers	8139P	1.49*	—	—	TB6810AS	.90	7417.34*	—	7488	2.50*	74162 1.21*	.65*	74249	—	—	4019 .56*	4088 9.81*	—	811395	.75*	—	—	79 Series	TC4540	1.75	7420.16*	19*	7489	2.60*	74163 1.21*	.65*	74251	—	—	4020 .92*	4099 1.8*	—	811396	.75*	—	—	-(NEG) 1A	ZM414	.30	7421.25*	19*	7490	.34*	74164 1.02*	.115*	74257	—	—	4021 .92*	4502 9.2*	—	811397	.75*	—	—	5v. 6v. 12v. 15v.	ZM424E	1.35	7422.25*	19*	7491	.73*	74165	.78*	74258	—	—	4022 .92*	4508 2.46*	—	74365	.75*	—	—	18v & 24v.	ZM425E	3.78*	7423.25*	19*	7492	.46*	74166 1.02*	.88*	74260	—	—	4023 .18*	4510 1.0*	—	74366	.75*	—	—	All £1.00* each	ZM459CT	3.54	7425.25*	—	7493	.34*	74168	—	1.85*	74266	—	4024 .65*	4511 .95*	—	74367	.75*	—	—	LM200	ZM1034E	2.03*	7426.25*	19*	7495	.54*	74169	—	1.85*	74273	—	4025 .18*	4515 2.70*	—	74368	.75*	—	—	LM304H	ZM1040E	8.43*	7427.39*	19*	7496	.67*	74170 1.85*	1.65*	74279	—	—	4026 1.84*	4516 1.0*	—	74369	.75*	—	—	LM323K	ZM116E	6.75*	7428.36*	19*	74107	.27*	74173 1.41*	.88*	74283	—	—	4027 .51*	4518 1.0*	—	74370	.75*	—	—	LM325N	—	—	7429.16*	19*	74109	.44*	74174 1.01*	1.05*	74290	—	—	4028 .70*	4518 9.5*	—	74371	.75*	—	—	LM326N	—	—	7430.16*	19*	74123	.60*	74175 1.01*	1.05*	74293	—	—	4029 1.08*	4521 2.54*	—	74372	.75*	—	—	LM326N	—	—	7432.25*	25*	74112	—	74176 1.01*	1.05*	74295	—	—	4030 .56*	4521 2.86*	—	74373	.75*	—	—	LM345K	—	—	7433.25*	19*	74113	—	74177 1.01*	1.05*	74295	—	—	4031 .56*	4522 1.89*	—	74374	.75*	—	—	LM345K	—	—	7437.25*	25*	74114	—	74178 1.01*	1.05*	74298	—	—	4032 .18*	4525 1.80*	—	74375	.75*	—	—	LM345K	—	—	7438.25*	25*	74121	.27*	74180 1.01*	—	74365	—	—	4033 1.06*	4528 .92*	—	74376	.75*	—	—	LM345K	—	—	7440.17*	19*	74122	.50*	74181 2.21*	2.99*	74366	—	—	4034 1.88*	4534 7.12*	—	74377	.75*	—	—	LM345K	—	—	7441.70*	19*	74123	.60*	74182 .81*	—	74367	—	—	4035 1.06*	4534 7.12*	—	74378	.75*	—	—	LM345K	—	—	7442.50*	55*	74124	—	74183 1.81*	—	74368	—	—	4036 1.06*	4543 1.62*	—	74379	.75*	—	—	LM345K	—	—	7445.60*	—	74125	.51*	74185 1.62*	—	74369	—	—	4037 .51*	4543 4.53*	—	74380	.75*	—	—	LM345K	—	—	7446.60*	—	74126	.51*	74186 2.97*	—	74369	—	—	4038 1.06*	4545 1.51*	—	74381	.75*	—	—	LM345K	—	—	7447.60*	.87*	74132	.72*	74189 3.17*	2.25*	74369	—	—	4039 .43*	4583 1.02*	—	74382	.75*	—	—	LM345K	—	—	7448.60*	.87*	74133	—	74190 1.21*	.75*	74369	—	—	4040 .92*	4585 1.07*	—	74383	.75*	—	—	LM345K	—	—

VAT, inclusive prices \* 8% others 12.5%. Export Customers deduct VAT 2.27 from \*19 from others. Postage and Packing 25p. Trade and Export Inquiries most Welcome. Hours 9.00am-5.00pm

Now available our ORDER-RING line, just phone your order through with your Access of Barclaycard number and providing the order is received by 3.00pm the components will be despatched the same day (min tel order £5.00).



# RADIO EXCHANGE LIMITED

## NEW ELECTRONIC MASTER KIT



With special V.H.F. Tuner Module to construct. A completely Solderless Electronic Construction Kit, with ready drilled Bakelite Panels, Nuts, Bolts, Wood Screws, etc. Also in the kit: Transistors, Capacitors, Resistors, Pots, Switches, Wire, Sleeving, Knobs, Dials, 5" x 3" Loudspeaker and Speaker Case, Crystal Earpiece, etc. Also ready wound Coils and Ferrite Rod Aerial. These are the Projects you can build with the components supplied with the kit, together with comprehensive instruction Manual Pictorial and Circuit Diagrams.

**Projects:**  
 V.H.F. Tuner Module ★ A.M. Tuner Module ★ M.W. L.W. Diode Radio ★ Six Transistor V.H.F. Earpiece Radio ★ One Transistor M.W. L.W. Radio ★ Two Transistor Metronome with variable beat control ★ Three Transistor and Diode Radio M.W. L.W. ★ Four Transistor Push Pull Amplifier ★ Eight Transistor V.H.F. Loudspeaker Receiver ★ Variable A.F. Oscillator ★ Jiffy MultiTester ★ Four Transistor and Diode M.W. L.W. Radio ★ A.F. R.F. Signal Injector ★ Five Transistor Push Pull Amplifier ★ Sensitive Hearing Aid Amplifier ★ Three Transistor and Diode Short Wave Radio ★ Signal Tracer ★ Three Transistor Push Pull Amplifier ★ One Transistor Class A Output Stage to drive Loudspeaker ★ Sensitive Transistor Pre-Amp ★ Transistor Tester ★ Sensitive Three Transistor Regenerative Radio ★ Four Transistor M.W. L.W. and Diode Tuner ★ Five Transistor M.W. L.W. Trawler Band Regenerative Radio ★ Five Transistor V.H.F. Tuner ★ Three Transistor Code Practice Oscillator ★ Five Transistor Regenerative Short Wave Radio ★ Four Transistor and two Diodes M.W. L.W. Loudspeaker Radio ★ Seven Transistor M.W. L.W. Radio with Loudspeaker Push Pull output ★ One Transistor Home Broadcaster.

**£14.99 + P & P £1.10**


## V.H.F. AIR CONVERTER KIT



Build this converter kit and receive the aircraft band by placing it by the side of a radio tuned to medium wave or the VHF band and operating as shown in the instructions supplied free with all parts. Uses a retractable chrome-plated telescopic aerial, gain control, V.H.F. tuning capacitor, transistor, etc. Size 5½" x 1½" x 3½". All parts including case and plans.

**£4.95 + P & P Ins. 60p**

## ELECTRONIC CONSTRUCTION KIT E.C.K. 2

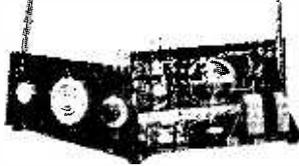


### Self Contained Multi-Band V.H.F. Receiver Kit.

8 transistors and 3 diodes. Push pull output. 3 in. loudspeaker, gain control, 7 section chrome-plated telescopic aerial, V.H.F. tuning capacitor, resistors, capacitors, transistors, etc. Will receive T.V. sound, public service band, aircraft, V.H.F. local stations, etc. Operates from a 9 volt P.P.7 battery (not supplied with kit). Complete kit of parts

**£7.95 + P & P and Ins. 90p**

## NEW MODEL R.K.1.

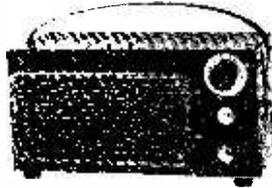

MultiBand A.M. Receiver. M.W.L.W. Trawler Band and Three Short Wave Bands. Seven Transistors and Four Diodes. Push Pull Output stage. 5" x 3" Loudspeaker. Internal Ferrite Rod Aerial. Kit includes all parts to build it up including Carrying Strap, Rubber Feet and ready-drilled Panels. Comprehensive Instruction Manual for stage by stage construction. Uses P.P.9 Nine Volt Battery.

**£8.99 + P & P 90p**

## EDU-KIT JUNIOR




Completely Solderless Electronic Construction Kit. Build these projects without Soldering Iron or Solder

- ★ Crystal Radio Medium Wave Coverage—No Battery necessary
- ★ One Transistor Radio
- ★ 2 Transistor Regenerative Radio
- ★ 3 Transistor Earpiece Radio Medium Wave Coverage
- ★ 4 Transistor Medium Wave Loudspeaker Radio
- ★ Electronic Noise Generator
- ★ Electronic Metronome
- ★ 4 Transistor Push/Pull Amplifier

All parts including Loudspeaker, Earpiece, M.W. Ferrite Rod Aerial, Capacitors, Resistors, Transistors, etc. Complete kit of parts including construction plans.

**£6.95 + P & P and Ins. 90p**

## NEW ROAMER TEN MODEL R.K.3.

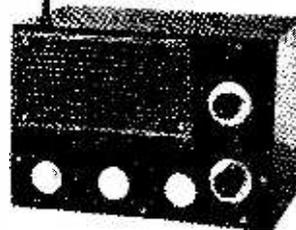

### Multiband V.H.F. and A.M. Receiver. 13 Transistors and Six Diodes. Quality 6" x 3" Loudspeaker

With Multiband V.H.F. section covering Mobiles, Aircraft, T.V. Sound, Public Service Band, Local V.H.F. Stations, etc. and Multiband A.M. section with Airspaced Tuning Capacitor for easier and accurate tuning, covering M.W.1, M.W.2, L.W. Three Short Wave Bands S.W.1, S.W.2, S.W.3 and Trawler Band. Built-in Ferrite Rod Aerial for Medium Wave, Long Wave and Trawler Band, etc., Chrome-plated 7 section Telescopic Aerial, angled and rotatable for peak Short Wave and V.H.F. reception. Push-Pull output using 600mW Transistors. Gain, Wave-Change and Tone Controls. Plus two Slider Switches. Powered by P.P.9—9 volt Battery.

Complete kit of parts including carrying strap. Building Instructions and operating Manuals.

**£14.79 + P & P £1.10**


## E.V.6 PLUS ONE



Build this exciting new design. Now with 7 Transistors and 4 diodes. MW/LW. Powered by 9V battery. Ferrite rod aerial, tuning condenser, volume control, and now with 3in. loudspeaker. Attractive case with speaker grille. Size 9in. x 5½in. x 2½in. approx. All parts including Case and Plans.

Total Building Costs:  
**£6.95 + P & P and Ins. 90p**

## EDU-KIT MAJOR

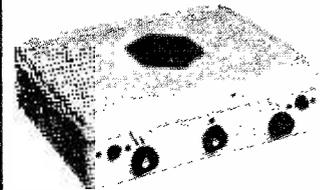

Completely solderless Electronic Construction Kit. Build fifteen projects including:—

- Signal Injector ● Transistor Tester NPN-PNP ● 7 Transistor Loudspeaker Radio MW/LW ● 5 Transistor Short Wave Radio.

### Components include:

- 24 Resistors ● 21 Capacitors ● 10 Transistors ● 5" x 3" Loudspeaker ● Earpiece ● Mica Base-board ● 3 12-way Connectors ● 2 Volume Controls ● 2 Slider Switches ● 1 Tuning Condenser ● 3 Knobs ● Ready Wound MW/LW/SW Coils ● Ferrite Rod ● 6½ yards of wire ● 1 yard of sleeving, etc. Complete kit of parts including construction plans.

Total building costs:

**£9.99 + P & P and Ins. £1.10**

## RADIO CONSTRUCTION KIT Q7



A compact small radio kit covering Medium Wave and Long Wave bands. Rugged Micamite construction and simple square design allows for easy carrying and positioning. Ideal for the Garage, Workroom, Kitchen, etc., has seven Transistors and four Diodes, quality Loudspeaker, ready wound Ferrite Rod Aerial and Carrying Strap. Size 4½" x 4½" x 4½". All parts and plans excluding 9v PP7 Battery.

**£6.25 + P & P and Ins. 75p**

## POCKET FIVE



NOW WITH 2½" LOUDSPEAKER 3 Tuneable wavebands. M.W., L.W., and Trawler Band, 7 stages, 5 transistors and 2 diodes, supersensitive ferrite rod aerial, attractive black and gold case. Size 5½" x 1½" x 3½" approx. All Parts including Case and Plans.

Total Building Costs  
**£4.95 + P & P and Ins. 80p**

All prices include VAT

## To: RADIO EXCHANGE LTD

61A High Street, Bedford MK40 ISA

Tel.: 0234 52367

- Callers side entrance "Lavells" Shop.
- Open 10-1, 2.30-4.30 Mon.-Fri. 9-12 Sat.

Reg. No. 788372

I enclose £.....for.....

Name .....

Address .....

PW579

# direct use of COMMUNICATIONS SATELLITES

We have already seen great developments in satellite communications, but far more impressive systems are likely to become available during the next ten years. Initially the larger manufacturing companies will have their own earth stations which will provide them with continuous communications facilities, but hand-held personal communications sets for direct transmission to huge spacecraft are being planned for about 1990.

In European homes the greatest impact of satellite communications occurs when a television signal is relayed from another continent. All such very long distance television links are made using satellites in geosynchronous orbit some 36 000km above the equator; such satellites orbit the earth once every 24 hours and hence remain above the same point of the earth at all times. However, television relays account for only about 2 per cent of the total use of communications satellites, the greatest demand being for ordinary telephone conversations by businessmen, together with high-speed data transmissions.

At the present time, communications satellites are used mainly for intercontinental communications by means of the INTELSAT spacecraft, although maritime and military satellite communications are also of vital importance. Very rapid developments are taking place; the European Space Agency recently launched the OTS2 vehicle which will be a forerunner of the first European satellite to carry telephone and television signals on a commercial basis across Europe.

Satellites are presently handling rather more intercontinental telephone traffic than sub-oceanic cables. The American Federal Communications Commission is apparently delaying the production and laying of a new TAT-7 transatlantic telephone cable whose 4000 telephone circuits would provide a more equally balanced capacity between cables and satellites. Cables are more expensive than satellites, but have a much longer life than the typical seven years design life of a satellite.

The INTELSAT spacecraft provide first class communications facilities over the largest distances, but involve the use of extremely expensive earth stations with parabolic reflectors of some 30 metres diameter; all points of these huge reflectors should be positioned with an accuracy of about 1 millimetre and retain this accuracy even in a high wind. Such stations became available in the mid-1960s at a cost in the order of £5 million. Some smaller, more economical earth stations with 10 metre diameter aerial reflectors are used in low density traffic areas for international communications where maximum bandwidth is not required.

The era of satellite broadcasting of television and radio programmes is now commencing. Aerials with reflector diameters of some 5 metres can be used in earth stations costing some £30 000, for receiving television signals from a geosynchronous satellite and relaying them to a whole community of users. Smaller aerials (perhaps 1 metre in diameter) can be used with more economical receivers costing no more than a few hundred pounds, to provide

television signals to individual homes in out-of-the-way places. Higher power satellite transmitters combined with very high gain satellite aerials make such economical earth stations possible for reception only, without facilities for transmitting to the satellite.

Eventually very large aerial structures will be assembled in space and, when used with far more powerful satellite transmitters, are expected to make possible the use of small hand-held transmitters for direct communications with the satellite by about 1990. The earth station reflectors may be about 100mm diameter and the total cost of the hand-held equipment about £10 on present day values. One of the advantages will be that you will eventually be able to telephone almost any person via a satellite by merely dialling his number; it will not be necessary to know whether he is working at his office, on a visit to another company, at his home, at his club or even taking a bath—although some protection of his privacy may be necessary.


One can even imagine a wrist radio communications system in the next century. Enormous satellite aerials with very high power transmitters will be required for such a system. However, it is claimed that the cost of such systems will be surprisingly low owing to the enormous amount of telephone traffic they would handle. It seems likely that the cost of a call over a distance of 3000km will be similar to that of a call to a person a few doors away in the same street. Competing with such telephone systems will be electronic letter facsimile transmission systems, which will (hopefully!) ensure the fast delivery of letters across intercontinental distances even if messages cannot be immediately delivered.

## SBS

In the more immediate future, a series of satellites will be launched in 1981 by a consortium known as SBS (Satellite Business Systems), which will provide US businessmen with direct access to the satellites for communications purposes through small company-owned unattended earth stations using 5 or 7 metre diameter aerial reflectors. One can imagine such dish reflectors being as commonplace as our present-day television aerials.

The Hughes Aircraft Company of California has been awarded a \$63 million contract by SBS for the construction of three domestic satellites for the direct transmission of voice, facsimile (printed matter), video, high-speed computer data and tele-conferencing pictures for US business and government agencies.

The SBS system will be the first US domestic commercial communications satellite system to use the higher frequency "K" Band (12 and 14GHz; that is, 12 000 and 14 000MHz). This high frequency system will enable earth stations to be located in urban areas without causing interference to terrestrial systems or to other spacecraft, whilst small and relatively inexpensive earth stations can be used at such frequencies.

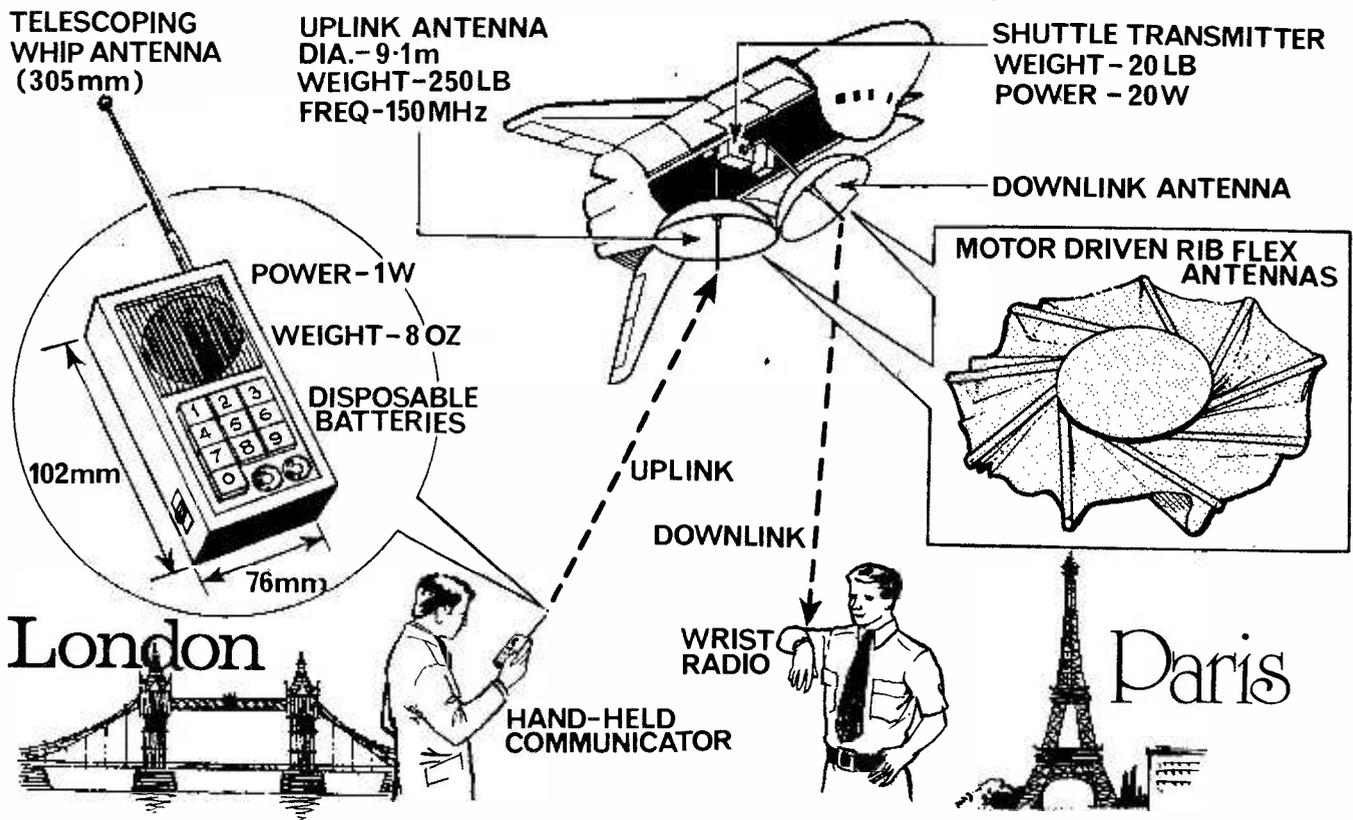

**Fig. 1: A concept of how we may be able to communicate in the future by a personal satellite link**

The SBS satellite system will cover all of the 48 contiguous states of the USA. The beam transmitted from the spacecraft will be electronically shaped so that the strongest signals are sent to the more densely populated east-central and west coast regions of the US, where SBS will install 5 metre diameter aerial reflectors on users' premises. In the remainder of the US the signals will be somewhat weaker, so 7 metre diameter aeriels will probably be employed.

Perhaps the most interesting feature of the SBS satellites is the use of a telescoping solar panel system. During the launch phase, the cylindrical solar panels are closed over one another to keep the satellite as compact as possible, but the panels will be deployed in space to provide the relatively high power level of about 914W. The spacecraft will be spin stabilised, so each part of the solar panel array comes into full sunlight in turn. It is intended that the SBS satellites will be launched by the Space Shuttle, since this type of launch will be much less costly than rocket launching. A SBS satellite will be able to sit upright in the cargo bay of the Shuttle vehicle with its aerial folded; this saves Shuttle charges, since the charge is more or less proportional to the payload bay length employed in the launch.

The travelling wave tubes in the SBS satellite transmitter will be able to provide an output power of 20W; this is higher than the more usual 5 or 6W in satellite transmitters. Ten channels, each 43MHz wide, will be available. Time Division Multiple Access (TDMA) will be used to provide the maximum signal-carrying capacity.

The specially shaped beam for providing maximum signal strength in the most heavily populated areas will be created by a 1.83 metre reflector with two reflecting surfaces. The front horizontal grid reflector is essentially

transparent to vertically polarised r.f. signals bounced off the rear reflector. Superimposition of the reflectors in a single aperture allows both of them to share structural support and have the maximum possible diameter. The two reflectors are offset from each other with a corresponding offset of their focal planes so that two separate feed arrays for transmit and receive can be employed without any mutual interference. It is expected that a minimum signal strength of 43.7dBW will be provided over the primary eastern coverage zone of the USA.

The SBS spacecraft are 2.16 metres in diameter by 6.6 metres in height when the solar panels are fully deployed. Each will weigh some 1057kg at launch, but after the apogee engine has been fired to place the craft in its correct geosynchronous orbit, the weight will be 555kg. Design life is seven years.

## Conclusions

Satellite communications are going to have an even larger impact on our lives in the future and will greatly facilitate business communications. It is interesting to note that it has been reported that the US has been using a "Pyramider" satellite communications link to enable their foreign agents to transmit short bursts of secret coded information via the satellite to their National Security Agency. Apparently Soviet agents in Mexico have purchased details of the system and former employees of a US satellite manufacturer have been charged with security offences. Presumably the US National Security Agency is rapidly searching for a replacement for their previous link. It is understood that the National Security Agency is interested in spread-spectrum links of very wide bandwidths (even up to 5GHz), since signals of such extremely wide bandwidths are very difficult to detect when transmitted at fairly low power, even with the most sophisticated receivers.

NEXT MONTH IN...

**practical**

# WIRELESS

**BREAK INTO THE NEW TECHNOLOGY!**


with the **W** **TOP BAND TRANSMITTER**

ON SALE 1ST. JUNE

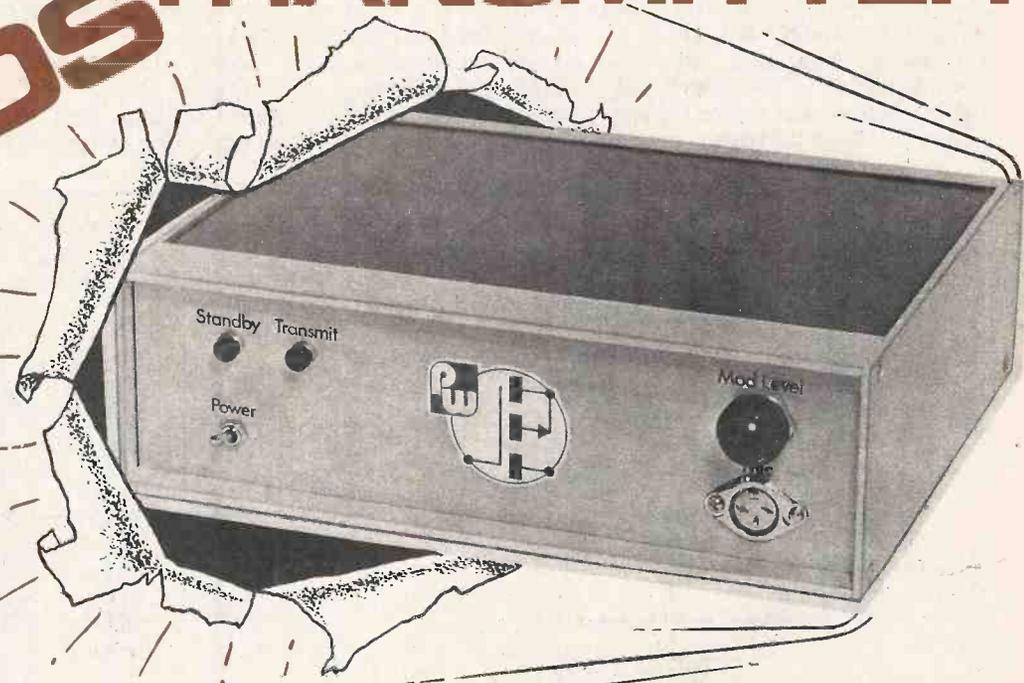**V MOS**

A low-power Top Band transmitter which takes advantage of up-to-date power f.e.t. technology. The design as published can be used as a development basis for v.f.o. frequency control and may be adapted for other h.f. bands.

No tuning is required to set up the r.f. strip, which should work from switch-on, producing about 6 watts of carrier for 10 watts d.c. input



## AM/FM FREQUENCY READOUT

Do away with tuning scales! Fit one of these modules to your HW/MW/VHF radio for really accurate indication of tuned frequency. Programmable for most commonly used i.f.s.

**SPECIAL  
PRODUCT  
REPORT**

**YAESU  
FRG-7  
RECEIVER**

# JUMBO

## Wall Clock


There have been many published designs for digital clocks, but these have almost all been for a digit height of less than 25mm. By using an array of discrete l.e.d.s, this clock has digits 64mm (2½in) high, and is ideal for use in shops, offices, kitchens, etc.

The circuit is based on the General Instrument Microelectronics clock chip AY-5-1224A, which utilises *p*-channel m.o.s. technology. Although not one of the most recent clock chips, it nevertheless incorporates a wide range of features, not all of which are used in this particular application. By the use of multiplexing techniques, a 16-pin dual-in-line package can be used. A non-multiplexed device offering similar facilities would require a 40-pin package.

### Multiplexing

The time division multiplexing technique, whereby several separate signals are passed in turn via one connection, is now widely used, particularly in digital displays and in calculator or typewriter keyboards. For the benefit of readers not familiar with the principle, a brief explanation may not be out of place. This will be based on the 7-segment, common-cathode l.e.d. displays used in this clock.

In Fig. 1(a), we show the schematic arrangement of one 7-segment display digit, with segments conventionally identified. Each digit requires eight external connections, so four digits connected in the normal way would require

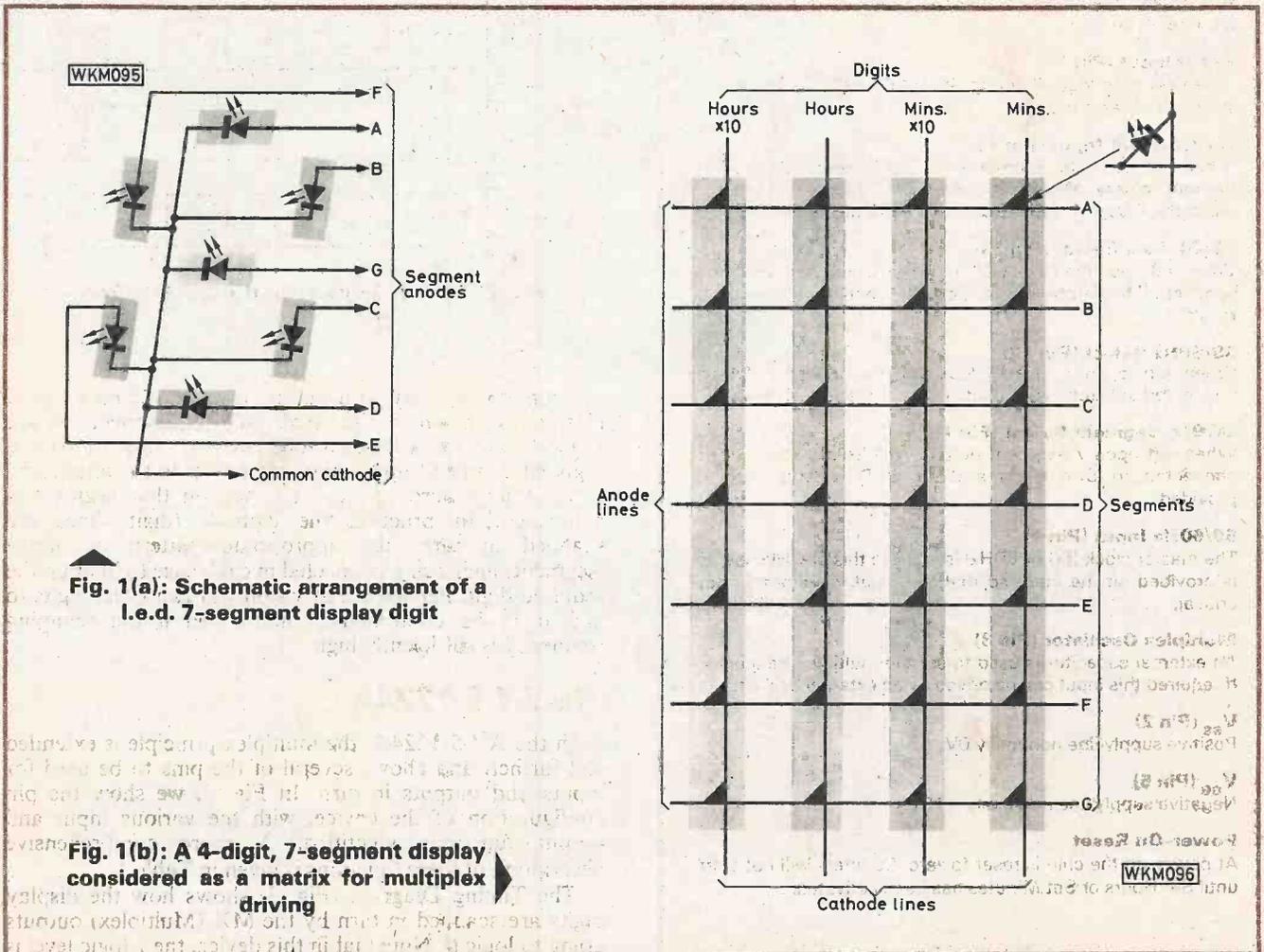

**Table 1—Pin Functions**

Pins 1 and 11 to 16 are multifunction. During multiplex times 1 to 4 they function as data outputs, either 7-segment code or BCD according to the display mode selected. During multiplex time 5 (Strobe) they function as inputs.

**Segment Outputs A-G (Pins 1 and 11 to 16)**

In 7-segment mode the digits are multiplexed out on to these pins. Normally the outputs are at logic 0 (positive to display).

**BCD Outputs 2<sup>0</sup>—2<sup>3</sup> (Pins 1, 16, 15, 14)**

In BCD mode the digits are multiplexed on to these pins in BCD code. Normally the outputs are at logic 0 (positive), i.e. code 0=0000.

**Multiplex Outputs 1-4 (Pins 10, 9, 8, 7)**

These pins are successively switched to logic 0 to select appropriate digit display. A fifth multiplex time (Strobe) is used to enable the control inputs. The multiplex rate is 1/20th the multiplex clock frequency.

**Strobe Output (Pin 6)**

This pin is used to enable the control input lines; it goes to logic 0 to enable.

**Set Hours Input (Pin 1)**

When taken to logic 0 during Strobe time this input causes the hours counter to advance at the rate of 1 hour per second.

**Set Min Input (Pin 16)**

When taken to logic 0 during Strobe time this input causes the minutes counter to advance at the rate of 1 minute per second and the hours counter to advance at the rate of 1 hour per minute.

**Reset Input (Pin 15)**

When taken to logic 0 during Strobe time this input causes the clock to reset to zero.

**Complement Input (Pin 14)**

When left open the segments and BCD outputs will have normal polarity. When connected to Strobe output via a diode the 7-segment and BCD output will be inverted.

**12/24 Hour Select (Pin 13)**

When left open the clock will run in the 12 hour mode, when connected to Strobe via a diode 24 hour operation will result.

**50/60Hz Select (Pin 12)**

When left open a 50Hz clock will be accepted. When connected to Strobe via a diode 60Hz operation will result.

**BCD/7-Segment Select (Pin 11)**

When left open 7-segment outputs will be provided, when connected to Strobe via a diode BCD outputs will be provided.

**50/60Hz Input (Pin 4)**

The master clock (50 or 60Hz) is input to this pin. Hysteresis is provided on the input so that the input waveform is not critical.

**Multiplex Oscillator (Pin 3)**

An external capacitor is used to set the multiplex frequency. If required this input can be driven by an external oscillator.

**V<sub>ss</sub> (Pin 2)**


Positive supply line nominally 0V.

**V<sub>gg</sub> (Pin 5)**


Negative supply line nominally -15V.

**Power-On Reset**

At power-on the chip is reset to zero. Counters will not start until Set Hours or Set Minutes has been activated.

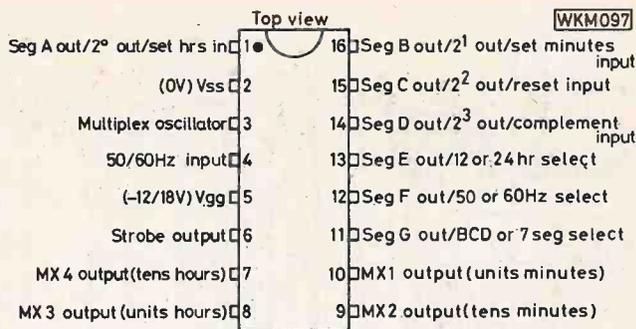

**Fig. 2: Pin configuration of the GIM AY-5-1224A clock chip**

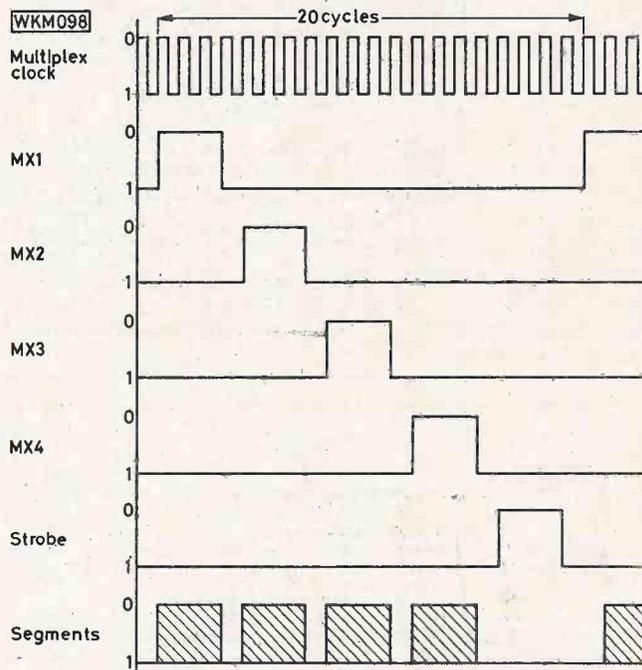

**Fig. 3: Timing diagram for the AY-5-1224A**

32 connections. By connecting the 28 segments in a matrix, as shown in Fig. 1(b), only 11 connections are needed—almost a three-to-one saving. Any individual segment can be lit up by applying power to the anode and cathode lines across whose intersection that segment is connected. In practice, the cathode (digit) lines are scanned in turn, the appropriate pattern of anode (segment) lines being connected in each case to light up the required digit. Persistence of vision will cause the digits to appear to be continuously illuminated if the scanning frequency is sufficiently high.

**The AY-5-1224A**

In the AY-5-1224A, the multiplex principle is extended still further, and allows several of the pins to be used for inputs and outputs in turn. In Fig. 2, we show the pin configuration of the device, with the various input and output functions identified. A more comprehensive description of these functions is given in Table 1.

The Timing Diagram (Fig. 3) shows how the display digits are scanned in turn by the MX (Multiplex) outputs going to logic 0. Note that in this device, the 1 logic level is


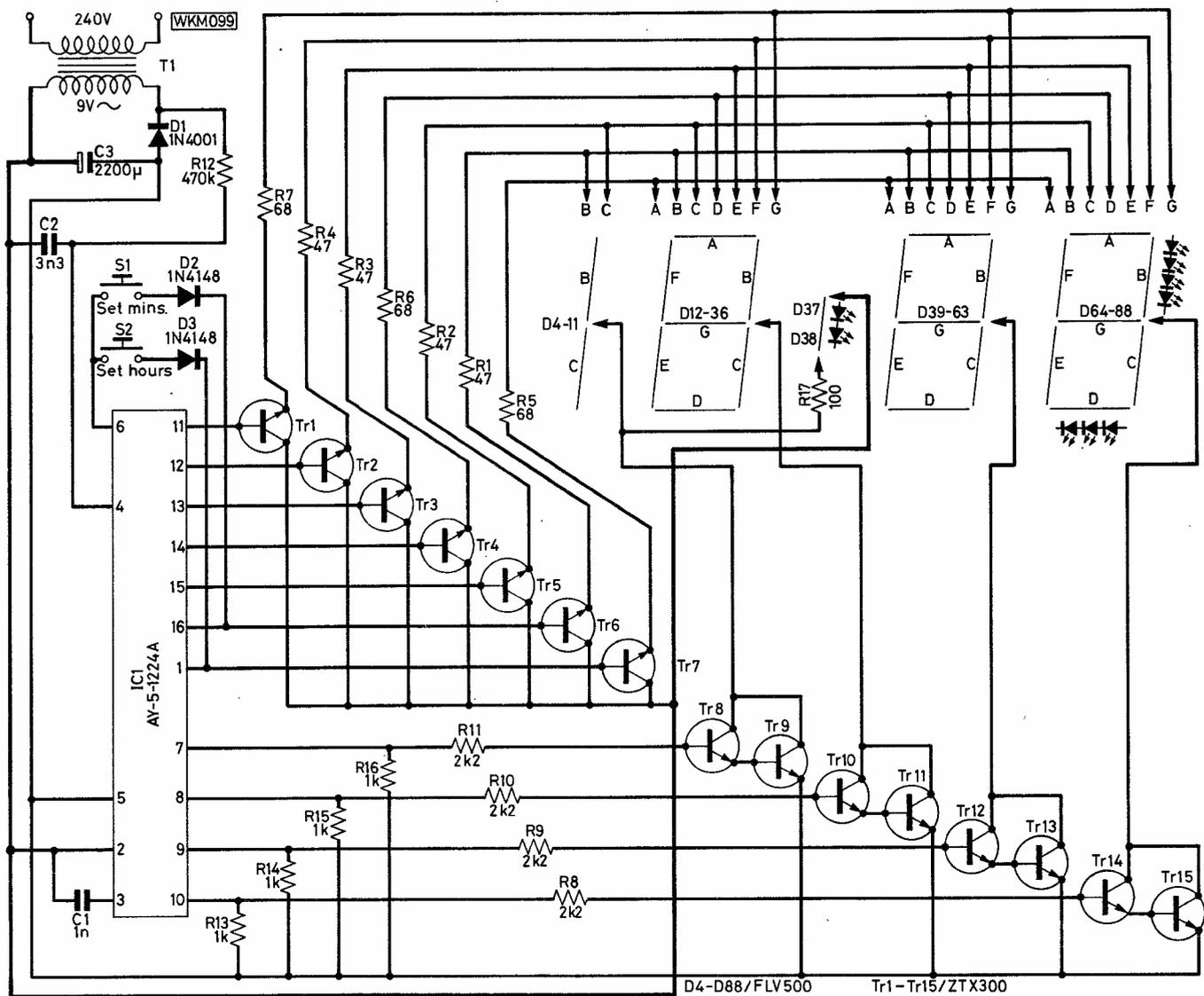


Fig. 4: Complete circuit diagram of the Jumbo Wall Clock

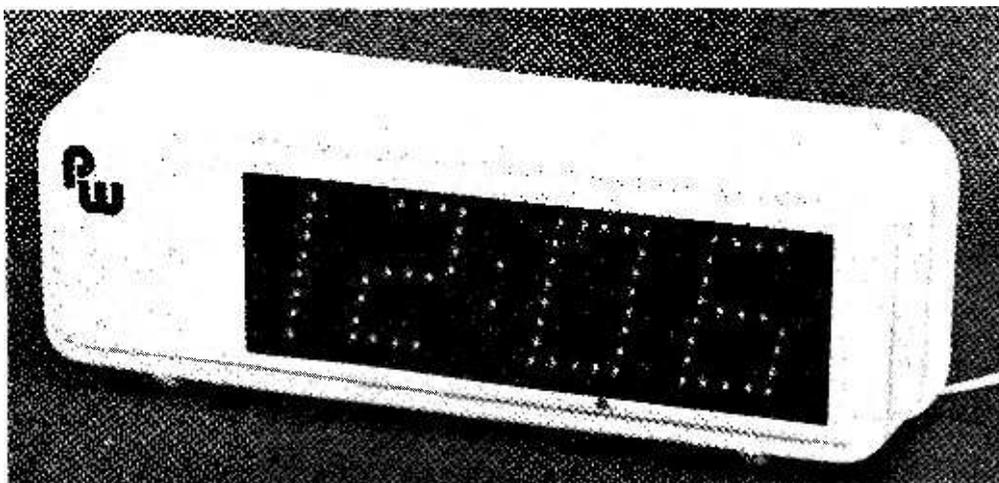

a negative voltage, approaching the  $V_{CC}$  supply rail. The input/output pins become inputs during the period that the Strobe output goes to logic 0.

## Circuit Description

The complete circuit diagram of the clock is shown in Fig. 4. Transformer T1 has a nominal 9 volt secondary, and the rectified and smoothed d.c. output across C3 will be around 13 volts. A sample of the 50Hz a.c. supply is taken from T1 secondary via R12, and after shaping by C2, is fed to pin 4 on IC1 as the Master Clock. The frequency of the on-chip Multiplex Clock is set by C1, and will be about 6.7kHz.

The 7-segment outputs are applied to transistors Tr1-7, which drive the l.e.d. arrays via limiting resistors R1-7. Each horizontal segment uses three series-connected l.e.d.s, and each vertical segment uses four. The values selected for the limiting resistors compensate for the resulting difference in voltage drop across each segment, and give an even overall brightness to the display.

The four Multiplex outputs are applied to Darlington pairs Tr8/9, 10/11, 12/13 and 14/15, and control the "Tens of hours", "Hours", "Tens of minutes" and "Minutes" digits respectively. Only two vertical segments are required for the "Tens of hours" digit, since this can only be a blank or a "1". This form of display is known in instrumentation circles as a  $3\frac{1}{2}$ -digit display, meaning that there are three full digits, each capable of displaying "0" to "9", and one half digit, capable of displaying only a blank or a "1".

The colon separating the hours and minutes digits comprises two l.e.d.s, and is scanned at the same time as the "Tens of hours" digit. The cathode end of the colon pair is fed via limiting resistor R17 directly from the 0V line.

## Construction

All the components, apart from the mains transformer and the time-setting switches, S1 and 2, are mounted on a single p.c.b., greatly simplifying construction. In the display window area, all the wire links and resistor R18 are mounted on the foil side (underside) of the board, to preserve a clean frontal appearance. The power supply reservoir capacitor C3 is also mounted on the foil side, because there is insufficient room for it between the p.c.b. and the case front.

Being an m.o.s. device, IC1 should be left in its static protection pack until it is actually to be fitted to the board.

The first step in construction is to fit the wire links. Take the length of 20 s.w.g. tinned copper wire, secure one end in a vice, hold the other end with pliers and stretch slightly. This will remove all kinks, etc., and make the wire easier to cut and bend. Cut 21 lengths, each 45mm long, and bend both ends, allowing 26mm between bends. Because these links are fitted on the foil side of the board, they must be spaced off to avoid short-circuits to other tracks. It is easier to achieve this spacing if the bends are made curved rather than sharp, as shown in the photograph. A bend of some 2-3mm radius is about right. Place the links in the foil side of the board as shown in Fig. 6, solder both ends and trim the protruding wire ends flush with the plain (top) side of the p.c.b. The plain side of the board should then be sprayed with a light coat of matt black paint, to provide maximum display contrast in high ambient light levels.

## ★ components

### Resistors

$\frac{1}{2}W$ 5%		
47 $\Omega$	4	R1-4
68 $\Omega$	3	R5-7
100 $\Omega$	1	R17
1k $\Omega$	4	R13-16
2.2k $\Omega$	4	R8-11
470k $\Omega$	1	R12

### Capacitors

#### Polystyrene 160V

1nF	1	C1
3.3nF	1	C2

#### Electrolytic Axial leads

2200 $\mu$ F 40V

### Semiconductors

#### Integrated circuit

AY-5-1224A	1	IC1
------------	---	-----

#### Transistors

ZTX300	15	Tr1-15
--------	----	--------

#### Diodes

1N4001	1	D1
1N4148	2	D2, 3
FLV110	85	D4-88 (0.2in red l.e.d.s)

### Miscellaneous

T1 9V 0.75A secondary.

S1, S2 Min. push-button, s.p. push-to-make.


Printed circuit board Ref. WR051\*

Case, Perspex window and p.c.b. mounting pillars.\*

16-pin d.i.l. socket for IC1.



1 metre 20 s.w.g. tinned copper wire.

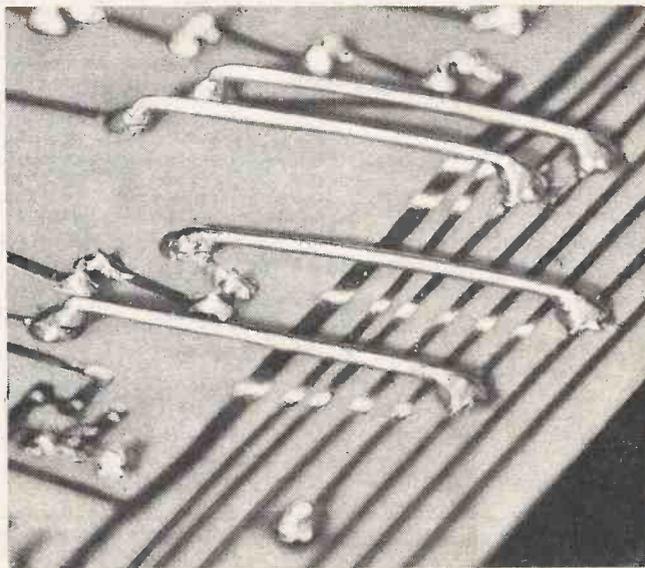\*Available from C. Bowes & Co. Ltd. (see Advertisers' Index).







This photograph shows the way in which the 20 s.w.g. wire links are made to stand clear of the board by the radiused bends to the legs at each end

© C. Bowes & Co. Ltd.  
WR051  
1979

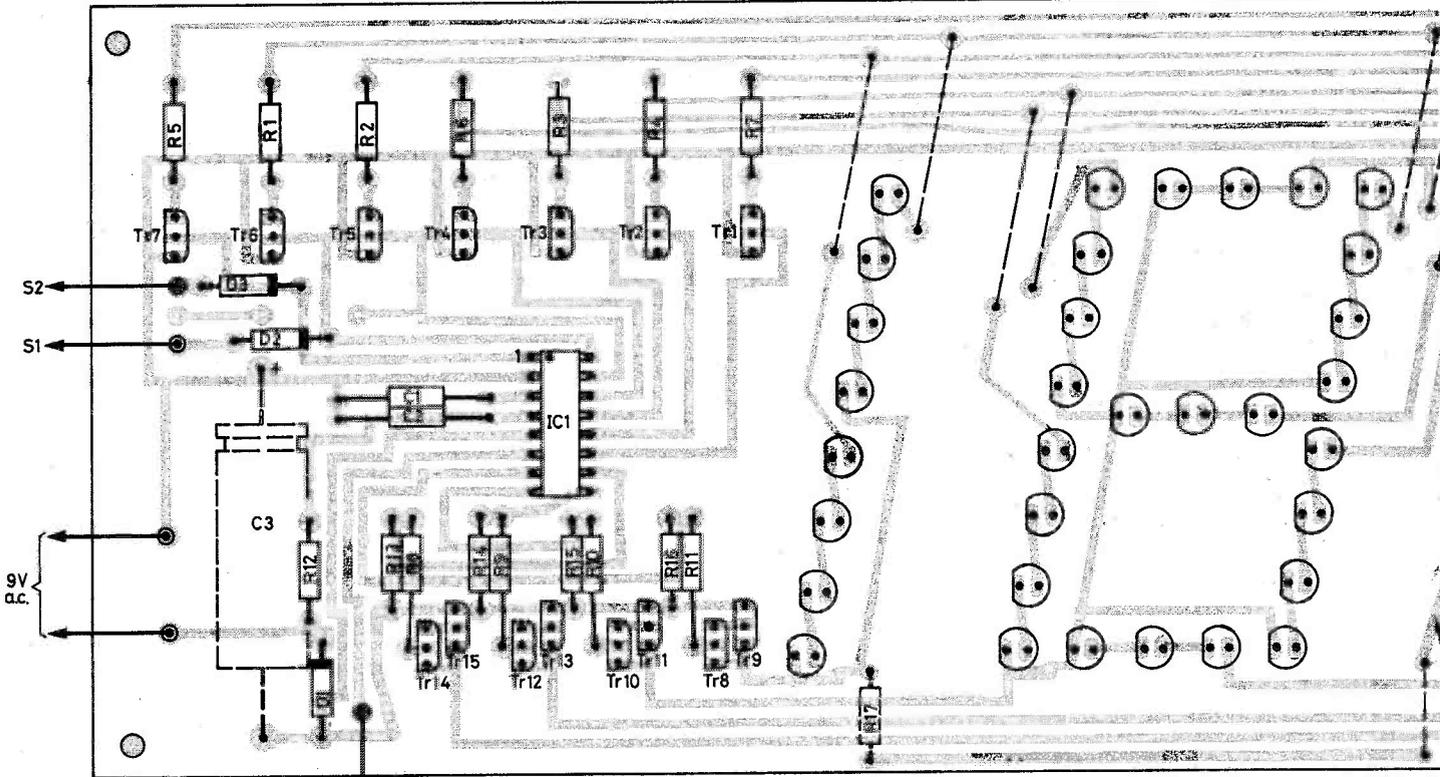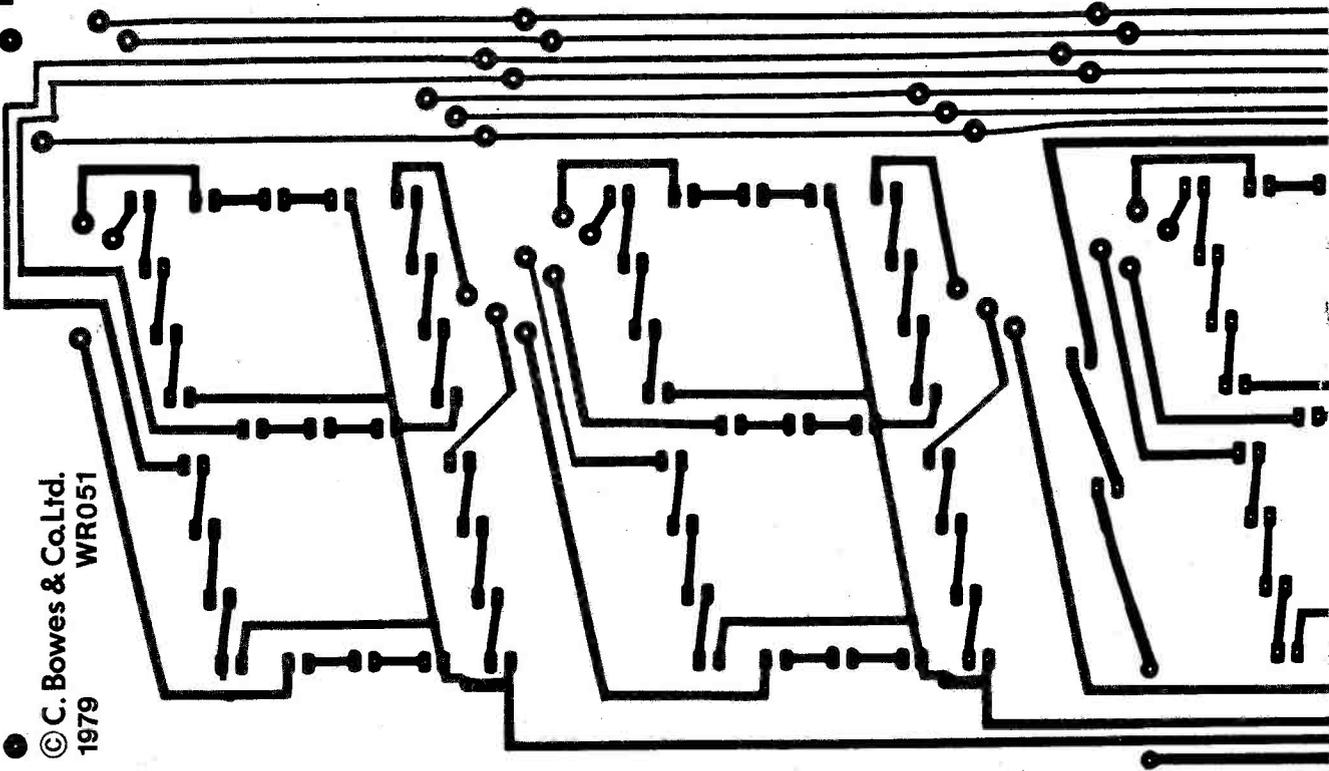

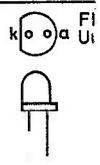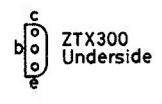All links & components R18/C3 (shown dotted) are mounted on track side of PCB.



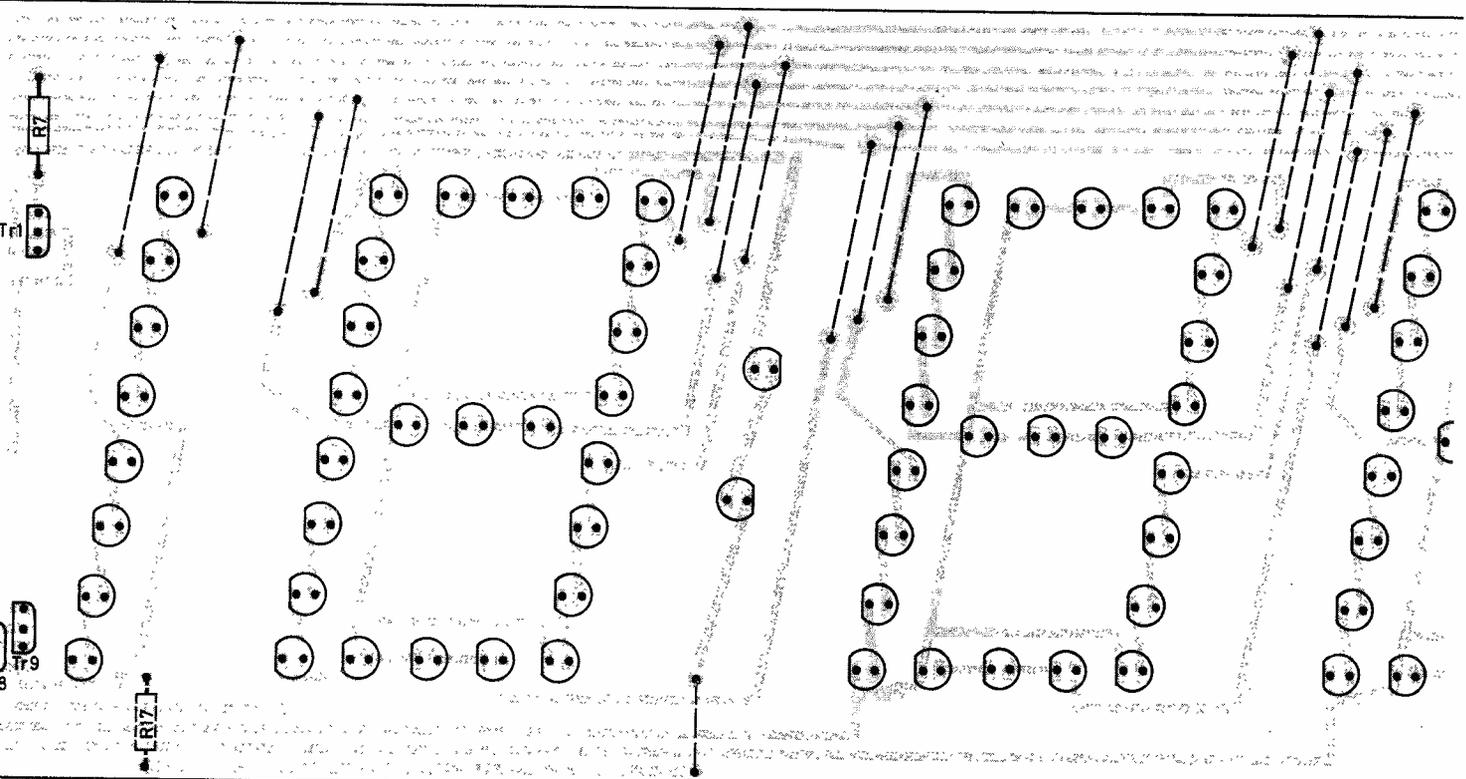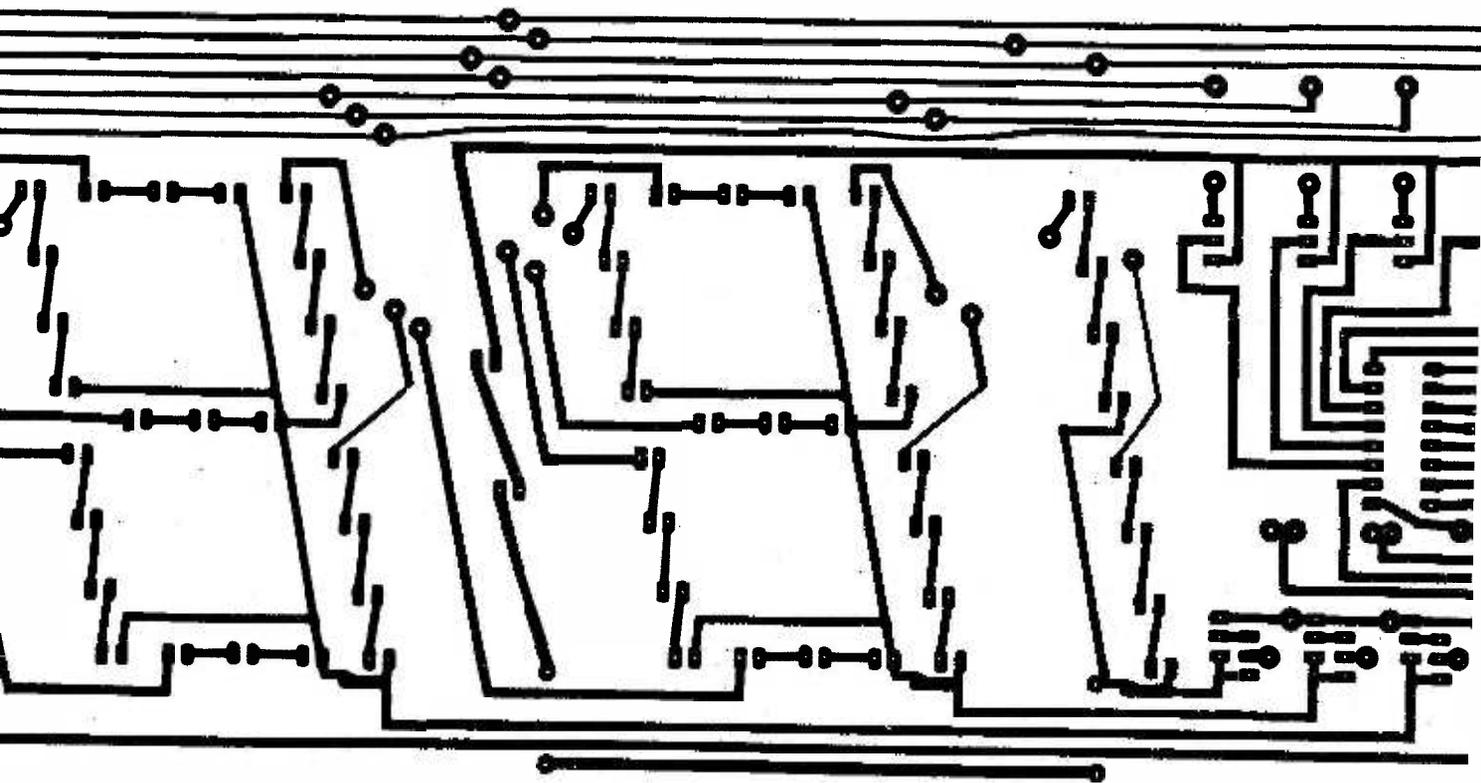

(shown dotted)  
CB.



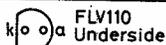


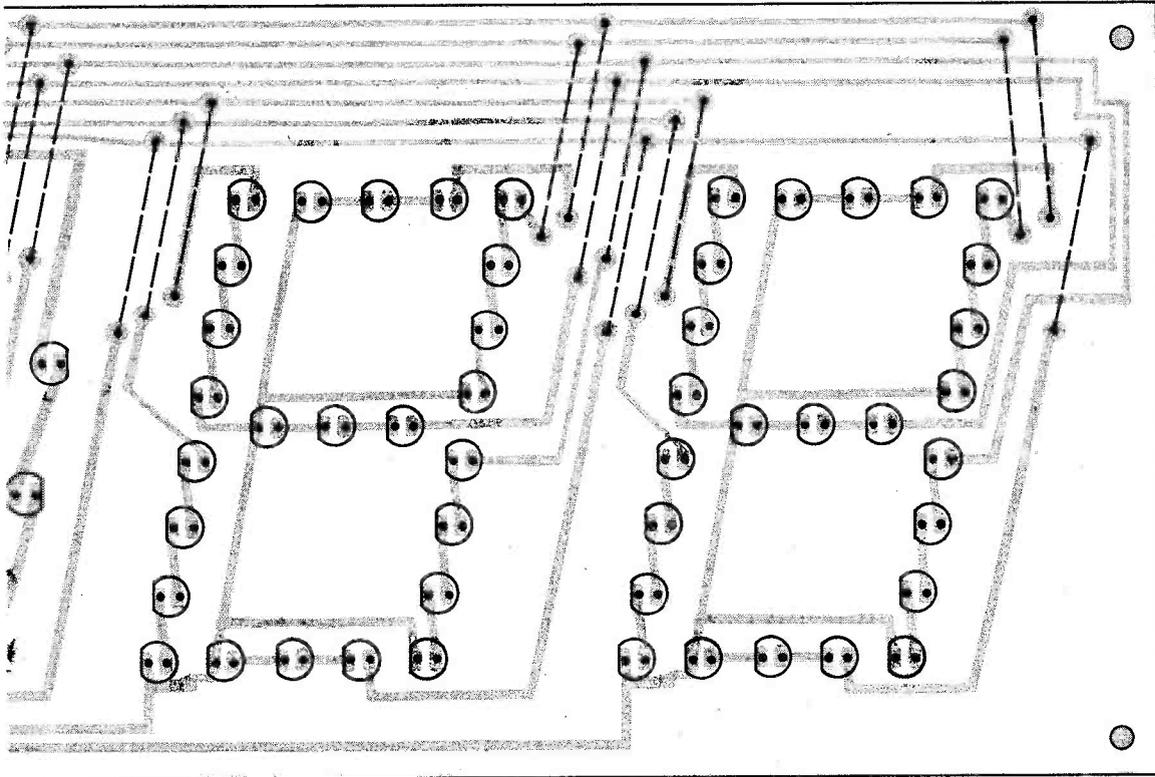


Fig. 5: The p.c.b. track pattern, shown full size

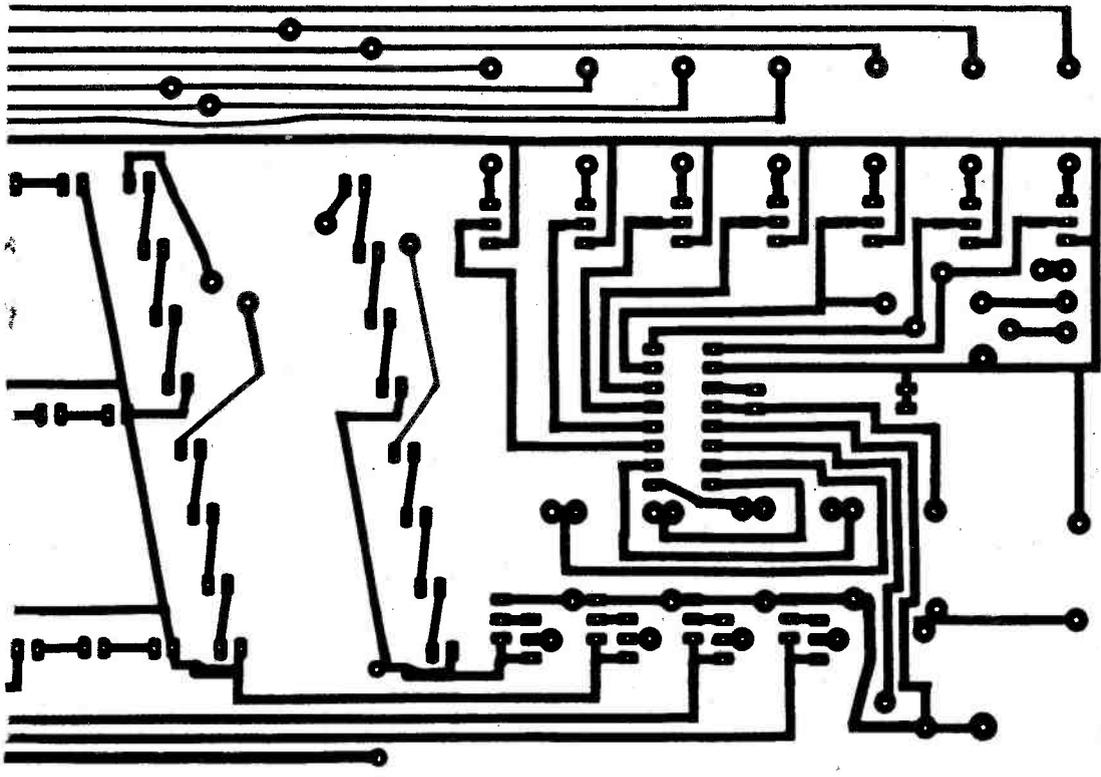

V110  
underside

WKM094

Fig. 6: Component layout and off-board connections

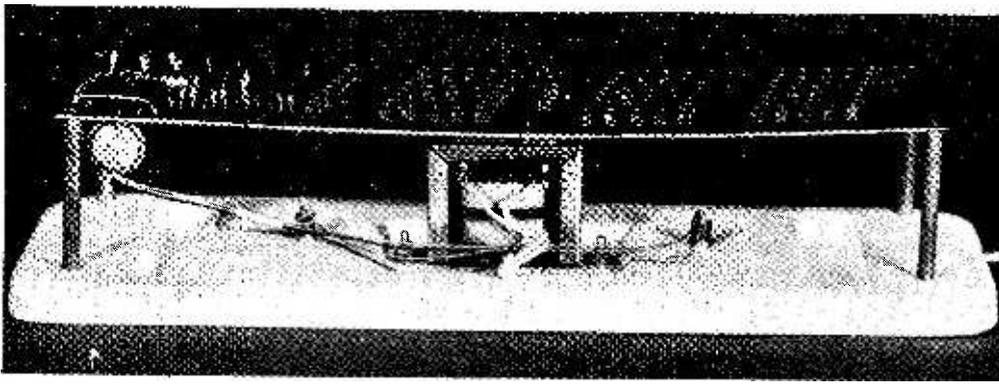

**An internal view of the clock, showing the two time-setting switches and the mains transformer mounted on the rear panel**

Insert all resistors, diodes, transistors and capacitors (except C3), and the i.c. socket, taking care to check that the semiconductors are fitted the right way round. Solder all the leads and trim the ends close to the p.c.b.

Next insert the l.e.d.s, noting that these are polarised, and should be fitted with the longest lead (the opposite side to the flat on the l.e.d. body) on the side facing away from the transistor, **except** for the two l.e.d.s forming the colon, which face the opposite way.

The l.e.d.s are easily damaged by excessive heat during soldering, and it is best to solder just one leg of each l.e.d. first, and then allow them to cool. Check that all l.e.d.s are in line and flat against the p.c.b., and then solder the second leg and trim off the excess wire ends.

Fit and solder five 300mm lengths of thin, pvc-covered wire to the p.c.b. in the positions shown in Fig. 6. Insert IC1 in its socket (**check correct orientation**). Fit C3 on the foil side of the board, noting that the negative end faces the edge of the board. After pushing the capacitor flush against the underside of the p.c.b., bend the wires over flat against the top side of the board before cutting, so as to create a mechanical fixing. Solder the leads on the foil side.

The four p.c.b. mounting pillars are made from 6mm diameter rod, and drilled 2.4mm to about 12mm deep at each end to take self-tapping screws. If the l.e.d.s and case mentioned in the components list have been used, the pillars will need to be 57mm long. If other types are used, the length will have to be adjusted to suit.

The transformer and switches are mounted on the back of the case, as shown in the photograph, and wired as shown in Figs. 4 and 6. Note that S2 (Set Hours) is on the left-hand side, behind the hours digits. The mains lead should be terminated in a fused clock connector or plug, fitted with a 1 amp fuse.

## Testing

When connected to a mains supply, the display should show three zeros and light the colon. On pressing a button at the rear of the case the appropriate digits should change, enabling the time to be set correctly.

Experience has shown that any l.e.d.s damaged internally through soldering are likely to fail during the first 24 hours of operation. It is therefore advisable to run the clock for two days out of the case.

When satisfied with the operation of the clock, the remainder of the case may be assembled. The red Perspex window should be glued into the case front with Evostik

(use sparingly to avoid spoiling the finished appearance), and the case fixed together either by means of self-tapping screws or Evostik.

## Fault Finding

If a single segment of the display fails to light when power is first applied, it is probable that one l.e.d. has been damaged when soldering. To locate the faulty l.e.d., select a number by means of the rear buttons, when it is known that the particular segment should be illuminated, and carefully short out each individual l.e.d. in that segment. The l.e.d. which, when shorted, lights the remainder, is the faulty one. Switch off the power and replace the faulty l.e.d.

If the same segment on each digit is off, check the resistor feeding the line, and the soldering of the associated transistor connections. If one digit is out completely, make the same checks on the resistors and transistor pairs at the bottom of the board.

## Noise


In common with all other multiplexed displays, it will be found that severe interference is caused to radio reception in the immediate vicinity of the clock. This interference is radiated from the display wiring, and it is not really practicable to suppress it. It will be found, however, that the noise disappears when the radio receiver is moved more than about a metre from the clock, and it should not normally prove a problem. ●

**PLEASE MENTION  
PRACTICAL WIRELESS  
WHEN REPLYING  
TO ADVERTISEMENTS**

# A Glance into the Past

Chas. E. MILLER

B.B.C. HANDBOOK

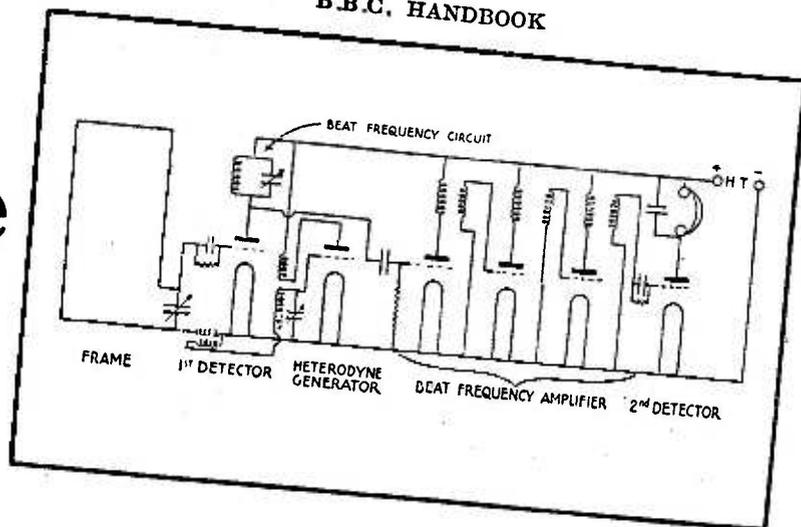

I recently acquired a copy of the BBC Handbook for 1928. It's a slim, but quite weighty volume of 384 pages, handsomely bound in dark red. Surprisingly, it contains a large number of advertisements, and at this distance in time these are arguably of at least as much interest as the text! For instance, on pages 2 and 3 we find a double-spread for Mr C. S. Dunham, late radio engineer to the Marconi Scientific Inst. Co., and a member of the BBC since its conception. (A somewhat doubtful word to employ in connection with that august organisation, I would have thought!), who has now set up in business as a manufacturer of high-class receivers. The two-valve loudspeaker set has a performance equal to many three-valve sets, at half the price and half the maintenance costs. Tuning is by a single dial with a small knob to vary reception power to individual requirements. Coils are entirely dispensed with. The larger C.S.D. 51D three-valver has a handsome cabinet fitted with a lock and key! It is a beautiful piece of furniture worthy of the most exclusive (but not presumably the most affluent) home, and is secured by a down payment of 35s 6d, and 25s monthly. Should you doubt any of the claims made, sworn statements are available for only 2d postage.

Passing on, Messrs Igranic Electric Co. Ltd. modestly announce their Neutrosomic Seven Radio Receiver, with the words: Igranic Radio Devices put life into a circuit — life in the zest and virility they give to results — life in the extraordinary length of time they continue to give such complete satisfaction. But what's this on page 17? An appeal To The Women Of Britain, no less, by a firm which has an enormous range of sizes, shapes, and designs. Of lampshades, I hasten to add. Hailwood & Ackroyd Ltd. (Morley, Nr. Leeds), enjoin the ladies to make their homes a Heaven on Earth for their menfolk by the use of their glassware. Zest, virility, and Mutual Pleasure! They certainly don't write advertisements like that any more. It makes one yearn for those far-off days when people thought a double-entendre was French for a pair of earphones.

## Origins

Ah well, on to the text. In an article entitled "BBC — the old Regime" we learn that the original British Broadcasting Company was set up in a remarkably short space of time — talks started in May, 1922, and the Company was registered on 15 December of that year. However, stations in London, Birmingham, and Manchester were commissioned on 15 November, and Newcastle had programmes from the following Christmas Eve. Thus, by the end of the year the BBC was able to claim that 40 per cent of the population were in "crystal range" of a transmitter. By the Autumn of 1925 this figure had increased to nearly 80 per cent.

In June, 1927, there were 2 299 822 licences in force for reception, which wasn't bad growth from virtually a standing start less than five years previously. Curiously enough the BBC now wished to dismantle the local stations in favour of "regional" broadcasting, not without some opposition from listeners, particularly in Birmingham, where the old 5IT transmitter in Summer Lane had already been closed down and replaced, in part, by the new high power experimental station 5GB at Daventry. High power in this instance meant 30kW; not a lot by today's standards, but vastly greater than the other stations then operating. 2LO, for example, was the next in line with 3kW, while most of the others had no more than 200 watts (0.2kW). In the light of this it is really surprising that so many people could expect to get good results on the insensitive receivers then in common use, albeit with very largely no choice of programmes.

With a glance forward to the independent radio network set up in the 70s, we find that it more closely mirrors the old British Broadcasting Company's chain of stations than does the latter day BBC's own local radio. La plus ça change, etc . . . Returning to the lack of choice in the 20s, however, it is refreshing to find that the handbook contains a list of all the major European radio stations as well as the domestic ones, for what was quaintly termed "reachers

out", or long-distance listeners. There is even a reference to broadcasting in the United States — "... many of (the stations) giving regular transmissions of fair to excellent quality..." There were, incidentally, 50 stations in Chicago alone, so choice would not seem to have been any problem!

## Programmes

Browsing along, in an article entitled "Topical Addresses", we discover that the Instant TV Pundit of today is merely a descendant of an older breed: "... the 9.20 space on Monday evening is still vacant on the morning of the same day, and somebody on the staff of the BBC is wondering whether it would not be possible to shift the centenary of Dante or King Charles the Martyr on the strength of some historical quibble, and make it, rather abruptly, that very Monday as ever is, and by the same token telephone to Professor Asterisk Space, the celebrated Italian authority, and get him to broadcast at 9.20." It appears that one talk broadcast from London was criticised in listeners' letters because it was (a) biased towards Communism, (b) Fascist propaganda, (c) anti-clerical, (d) sectarian propaganda, (e) frivolous, (f) over-intellectual. We are not told who made the broadcast in question, or what was its burden, but one hopes that the luckless author could shrug off the reaction with the time-honoured "Ah well, you can't please 'em all!"

A large section of the book is devoted to explaining how the programmes were produced, and fascinating reading it is. However, perhaps we should now confine ourselves to the technical matter, which is truly comprehensive, starting with an historical survey of "Wireless", and going on to detailed discussion of the BBC transmitters, with circuits of amplifiers and oscillators, and of other radio stations, such as that used for transatlantic telephones. This latter worked on about 5000 metres (60kHz) using single-side-band! At least there shouldn't have been too much difficulty in keeping the local b.f.o. on tune at that frequency.

## Equipment

Moving on to receivers, there are details of many types of set, from the simplest crystal to a superhet, with two stages of "h.f. magnification". The listener is warned against wearing headphones whilst making adjustments to mains-powered high tension supplies, because of the danger of electric shock. It was remarked that "modern headphones are much improved acoustically, but whether sufficient attention has been given to the response/frequency curve in every case is open to question. No doubt the necessity for a low price is responsible..." Neither could the moving-iron type of loudspeaker boast of really good reproduction, but in America the moving-

# THE PERSONAL AND EXPERIENCE OF

It was realised by Mr. C. S. Dunham (who until some time ago was Radio Engineer to Marconi Scientific Inst. Co. and had been a member of the B.B.C. since its conception) that radio appliances should not be machine-made articles designed on conventional

# RECOMMENDATION A RADIO ENGINEER

lines. So he applied his knowledge and experience to the production of a range of radio sets and components that would be entirely different in their design and performance. These, by skilful methods of production, are sold at prices which represent wonderful value.



This Dunham two-valve loud-speaker set is a handsome oak cabinet model. In performance equal to many three-valve sets (at half the price and half the maintenance cost) the design of this receiver represents a combination of simplicity with efficiency that has met with universal approval. Valves fitted internally on anti-microphonic battery. Tuning is by a single dial with a small knob to vary reception power to suit individual requirements. Coils are entirely dispensed with. Range on loud-speaker 25-50 miles on ordinary station. 100-120 miles from Daventry. Phone range includes reception from many other stations at excellent strength. Just plug in and out to start set working. This action automatically lights up valves and puts all switches on. Complete with two Cosser dull-emitter valves, slide accumulator, extra large H.T. battery (100 volts), loud-speaker, in fact an installation complete. Marconi royalty paid, for £7/19/6, or 12/6 deposit secures and 12/6 monthly.

For Home Constructors. Envelope containing all details, large H.T. battery (100 volts), wiring diagram, panel layout, complete list of components with full particulars, 7d. post free.

## TRUTH IN ADVERTISING

We are prepared to prove the claims we make for our instruments. Sworn testimony supporting these claims together with a beautifully illustrated booklet showing the full range of Dunham models will be sent per return on receipt of 2d. for part postage.

**THE DUNHAM EVERLASTING GUARANTEE IS YOUR ASSURANCE OF LASTING AND COMPLETE SATISFACTION.**


Your own set taken in part exchange.

**BEWARE OF EASY TERMS.** Buyers of various commodities have found to their cost that so-called easy terms are at times far from being what the name implies. There is a way of purchasing out of income—easy terms that are easy AND FAIR. You keep what you have paid for. This is the Dunham way. Before you buy ANYTHING out of income write for our free treatise that tells you clearly what to avoid and how to keep on the SAFE side of the deferred payment system.

THE LATEST DUNHAM TRIUMPH—A SET THAT NEEDS NEITHER AERIAL NOR EARTH
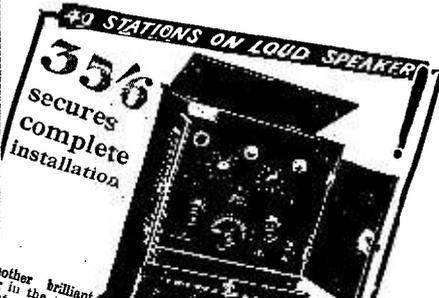
## DUNHAM "ALL-WAVE" TUNER

increases Range and Tone, and adds another valve to your receiver. Covering wavelengths from 150 to 2,000, the "ALL-WAVE" Tuner is simple to operate and has one-hole fixing. Enthusied over by Wireless Journals, this amazing instrument finally dispenses with coils and their accompanying complications. Complete with full instructions and Blueprints, Price 9/6



## Personal Installation


Another brilliant star in the firmament of Dunham achievements is the C.S.D. 51 D. A three-valve set of exceptional attributes, this set has lock and key. Valves are protected by "windows," from accidental damage. The cabinet itself is a beautifully decorated piece of furniture worthy of the most exclusive home and is secured for 36/6 deposit and 25/- monthly, complete with valves, all batteries, and long-speaker. As the set has almost entirely done away with the expensive litter of interchangeable cabinet loud-speaker, 21 guineas. Marconi royalty paid. For those who wish to construct a wireless set de Luxe, we issue full instructions that include five pictorial diagrams, Every constructional detail is clearly explained and with the assistance of the diagrams amateurs will find pleasurable and profitable occupation in building this first class set.

**C.S. DUNHAM**

ELM WORKS, ELM PARK  
BRIXTON HILL, LONDON, S.W. 2  
WRITE NOW FOR FULL PARTICULARS



## NEUTROSONIC SEVEN RADIO RECEIVER

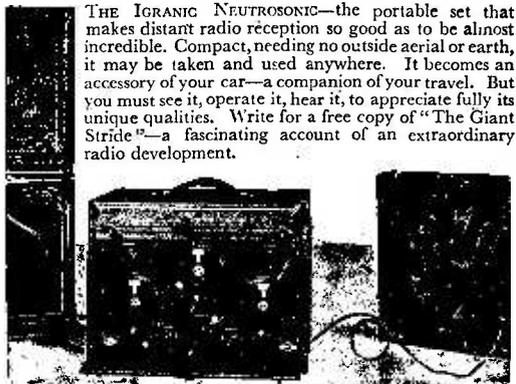

THE IGRANIC NEUTROSONIC—the portable set that makes distant radio reception so good as to be almost incredible. Compact, needing no outside aerial or earth, it may be taken and used anywhere. It becomes an accessory of your car—a companion of your travel. But you must see it, operate it, hear it, to appreciate fully its unique qualities. Write for a free copy of "The Giant Stride"—a fascinating account of an extraordinary radio development.

IGRANIC RADIO DEVICES put life into a circuit—life in the zest and virility they give to results—life in the extraordinary length of time they continue to give such complete satisfaction.

Write for lists describing our latest range of components.  
Dept. J273

### IGRANIC ELECTRIC CO LTD

149 Queen Victoria Street, LONDON  
Works: BEDFORD

coil speaker had already become widely used. Interspersed into the pages of this particular section are the numerous advertisements of the loudspeaker manufacturers. The Celestion C.12 could be had in oak for £7 5s, or in mahogany for an extra 5 shillings; but "this is but one of the 1927-28 Celestions, which range in price from £5 10s to £25.(!) They all definitely improve with age." Perhaps they matured, like wine. No doubt if anyone discovers one which had been laid down in a cellar back in 1928, it will by now out-perform anything the hi-fi merchants can offer!

And so to aeriels. Once again the advice given to listeners is applicable to all sorts of receivers and reception conditions. In general they were urged to use the maximum length of wire allowed by the receiving licence — 100ft, and no doubt they needed to if they wished to hear a 200 watt transmitter at any distance with a crystal set. The earth, too, was important, the recommended method of ensuring good results was to bury a 3 feet square plate in damp ground, with the lead-in wire soldered to several points along its top edge, with a "... small wooden cover over the joint, so that it may be inspected from time to time." This section ends, incongruously, with a picture of four aristocrats playing a hand of Bridge, which was being broadcast! There is no sign of a commentator, so perhaps the listener heard only the player's voices, plus the occasional soft thud of a well-shod foot impinging on a partner's shin!

From then on, most of the text is devoted to the do-it-yourself enthusiasts of the day, with articles by outside contributors on subjects such as "Hints for the Novice", and "The Home Constructor Scores", followed by 12 Don'ts for Listeners (e.g. DON'T forget that it is impossible practically to get true reproduction when receiving in the "silent point". How about that?), a glossary of technical terms. In this latter are some terms which are surprisingly familiar, such as, KiloHertz, Push-pull Amplification, and Cathode Ray Oscillograph.

In a limited space it is clearly impossible to do full justice to a book which is rich in interest, so here are just three more samples.

The Ormond 5-valve Portable advertised on page 306 is "... ideal for indoor and outdoor use ... and will render perfect reproduction under average conditions from a main BBC station within about 30 to 40 miles, and about 400 miles of Daventry." Price, ready for immediate use, £24 10s — but then comes the sting in the tail. Marconi Royalty, extra, was no less than £3 2s 6d, or just over 12½%. No doubt this caused as much displeasure as does VAT today! On the very last page is an ad. for the British Radio Corporation, of Weybridge. It can't be the same one owned by Thorn, can it? Anyway, their speciality of the day was a High Frequency Combination Transformer, 200-2000 metres, which sounds as though it was intended to convert ordinary t.r.f. sets into superhets, although only hinted at by the reference to a high value of intermediate frequency. A somewhat strange reticence compared with

## TO THE WOMEN OF BRITAIN

The Radio has undoubtedly helped you to keep your husband and boys away from the club and kept them at home where they thus experience the benefits of your gentle charm and influence, but you must now go *one step further* and make your home comfy and cheerful by having Hailglass Shades and Globes on your lights. Hailglass is made only by Hailwood & Ackroyd, Ltd., Morley, near Leeds. It is made in beautiful opals and is decorated or tinted with lovely colours and designs. Each piece is marked "Hailglass." Don't let your supplier foist upon you foreign glass which is made under sweated conditions. Your supplier gets a reasonable profit on our glass. We are putting up a hard fight in the face of unfair foreign competition and against certain atrocious British dealers who want *excessive profits*. Please help us to keep the Trade and British Money in Britain. Your men-folk, as they listen to the Radio in a home made bright and comfy by our charmingly coloured glassware, will indeed feel that they are in a real "Heaven on Earth," and you women of England will mutually join in this pleasure. We have an enormous range of sizes, shapes and designs.

Head Office and Works: MORLEY, Near Leeds  
Showrooms { 98 Mansell Street, LONDON, E. 1  
32 Shaftesbury Avenue, LONDON, W. 1  
21 Waterloo Street, GLASGOW

continued on page 59

# Ideas DEPARTMENT

Some original circuit ideas provided by our readers. These designs have not been proved by us, and we cannot therefore guarantee their effectiveness. They should at least provide a basis for experimentation.

Why not send us your idea? If it is published, you will receive payment according to its merits. Articles submitted should follow the usual style of PW in circuit diagrams and the use of abbreviations. Diagrams should be clearly drawn on separate sheets, not included in the text.

Each idea should be accompanied by a declaration that it is the original work of the person submitting it, and that it has not been accepted for publication elsewhere.

## REMOTE AERIAL PRE-AMP SUPPLY

There have been several published designs for remote (mast-head) aerial pre-amplifiers, but these have generally been battery powered, or fed via a separate supply cable. It is very convenient, and not difficult, to supply power via the signal coaxial cable, using the circuitry shown here to draw power from the associated tuner.

In Fig. 1, C1 isolates the d.c. supply from the pre-amp output, and L1 prevents the r.f. output from being shunted away via the pre-amp power supply circuits. Resistor R<sub>x</sub> is

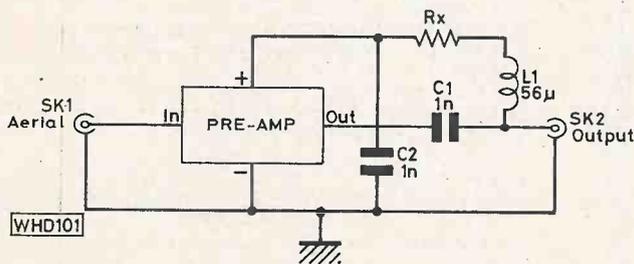


Fig. 1

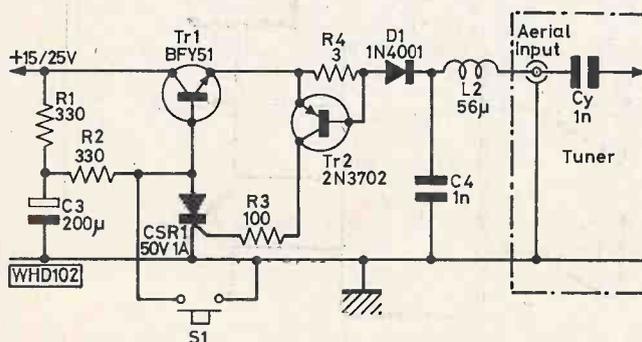


Fig. 2

chosen to reduce the supply voltage to the required value at the rated current consumption of the pre-amplifier, and also provides supply decoupling in conjunction with C2.

To prevent damage to the tuner's power supply, in the event of a short-circuit on the aerial download, some sort of overload protection is necessary. The circuit of Fig. 2 is fed from the power supply reservoir capacitor, which will often have around +15/25V on it. The series pass transistor Tr1 acts as the control element of the overload protection circuit, and also provides electronic smoothing by the action of R1, C3, R2. When an excessive current is drawn, the voltage drop across R4 will rise above about 0.6V, turning on Tr2, whose collector current triggers CSR1. When CSR1 conducts, it removes the base drive from Tr1 and so shuts off the d.c. supply to the tuner aerial socket via D1 and L2. The supply is restored by pressing S1, the "Reset" button. Diode D1 protects Tr1 from high reverse emitter-base voltages which can occur at switch-off if there is a large-value capacitor in the aerial pre-amplifier. Decoupling is provided by L2 and C4. Capacitor C<sub>y</sub> must be added to the tuner input circuit if the latter is not a d.c. open circuit.

The output voltage of the protection circuit will be about 1.5V less than the tuner supply voltage, due to the voltage dropped across Tr1, R4 and D1. With the value shown for R4, shutdown will occur at a load current of about 200mA. If some other value is required (dictated by the maximum safe additional current which can be drawn from the tuner power supply), the value of R4 can be calculated from the formula:

$$R4 = 0.6/I_c$$

where R4 is in ohms and I<sub>c</sub> is in amps.

The inductors L1 and L2 should be mounted as close as possible to the coaxial sockets, and may be made by winding about five turns of enamelled copper wire onto a ferrite bead. Other than this, the circuit layout is in no way critical.

P. J. H. Fox  
Oxford

# THE 'TRENT' 150W BROADBAND H.F. LINEAR AMPLIFIER PART ONE

This article describes the theoretical and practical considerations necessary to construct a push-pull 150 watt, solid state linear r.f. power amplifier. The unit, which provides a 15dB gain, is primarily intended for use with s.s.b. transmitters, and employs broadband technology, covering the range 2–28MHz. Operation is from a 13.8V d.c. source and the full output is achieved for only 3 watts excitation. Intermodulation products, measured at 28MHz for 150 watts p.e.p. are better than –30dB.

The amplifier, which is fairly simple to construct, uses two TRW power transistors type PT9784/A and a BD135. A schematic diagram is given in Fig. 1. Readily-available European components were a prerequisite design consideration.

## Design Criteria

In a push-pull configuration the transistor input or output impedances are in series, making the required transformation ratio one-quarter of that required for parallel operation. This method has been chosen to improve even-harmonic suppression and to simplify the matching problems due to very low input and output transistor impedances.

The circuit calculation was made in the following order:

1. Choice of the input and output transformer ratio.
2. Choice of transformer type.
3. Estimation of the transformer volumes.
4. Calculation of the transformer compensation.
5. Calculation of the input network between the input transformer and the transistors to match the two input impedances to  $3\Omega$  and to stabilise the gain/frequency characteristic.

A detailed analysis of the theoretical parameters will be given later for those wishing to study the technology. However, this should not deter the amateur from constructing the module, which requires only a little care and common sense in order to make it work.


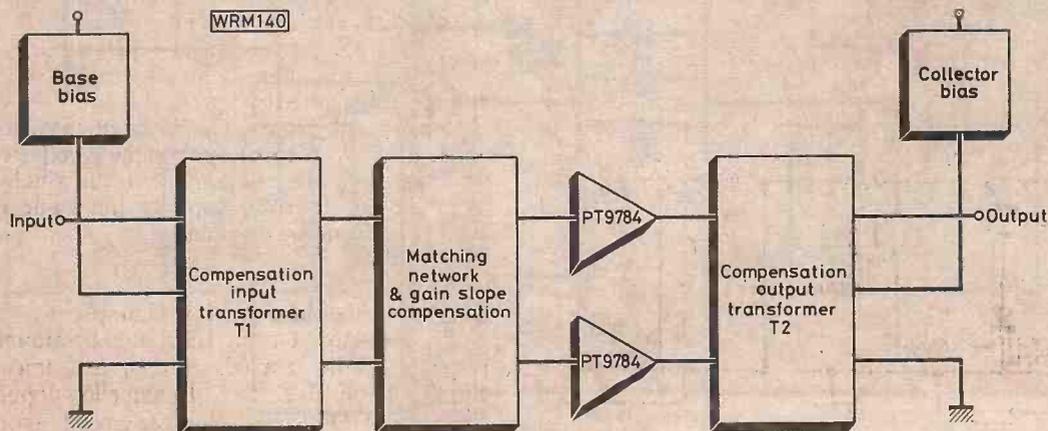


Fig. 1: Block diagram of the amplifier

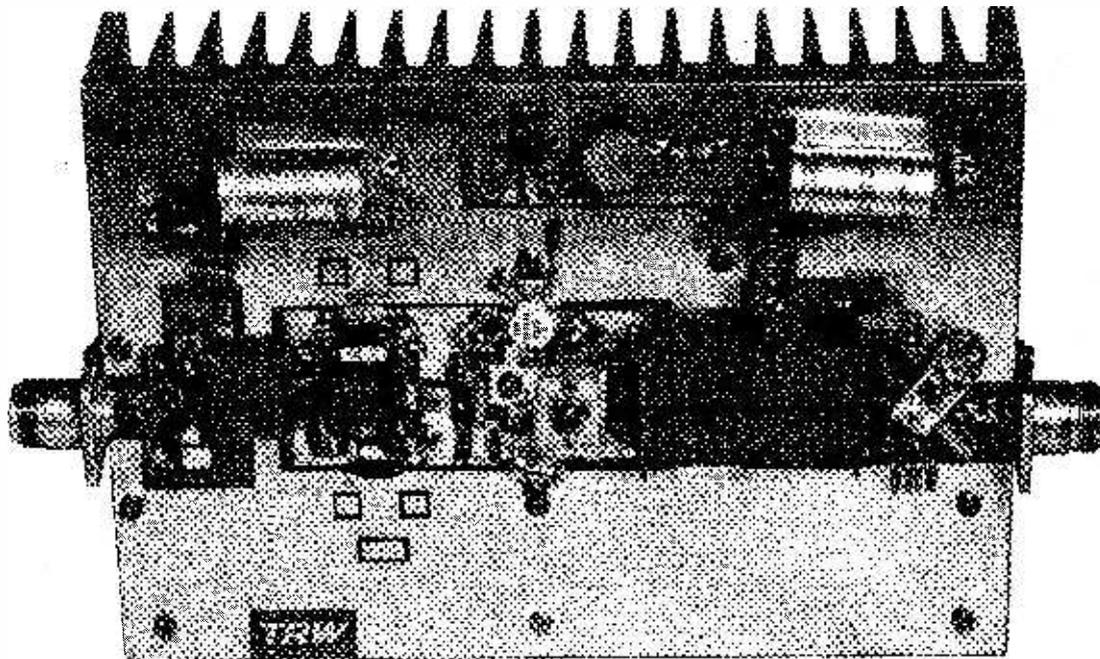

The complete circuit is shown in Fig. 2 and the p.c.b. and component locations in Figs. 6 and 7. On-the-top assembly is employed throughout and the heatsink should be drilled and countersunk to permit the power transistors to seat properly on the p.c.b. The mica chip capacitor and the transformers should be the first devices to be fixed to the board. *Note that one of the transformer end-pieces forms the centre-tap in each case.*

When the transformers for the prototype were built, some difficulty was experienced in locating brass tubing of the prescribed dimensions. It is possible that copper would suffice, but the original development module called for brass, so a supply was ultimately found, and appears in the components list. Several other devices could possibly be substituted, but those listed are those currently working in the prototype.

## Output Circuit

The equivalent r.f. output circuit is given in Fig. 3. Resistor AA, capacitor AA and inductor BB form the equivalent circuit to  $2 \times Z_{OUT}$  in series. Capacitor CC, capacitor EE and inductor FF are the transformer h.f. compensation. The transformer itself is a black box, described by its S-parameters.

Optimisation of the compensation elements was carried out with the aid of a computer and the maximum output v.s.w.r. is lower than 1.6:1.

## Input Circuit

The equivalent r.f. input circuit is shown in Fig. 4. Here IMP JJ represents the two transistor input impedances in

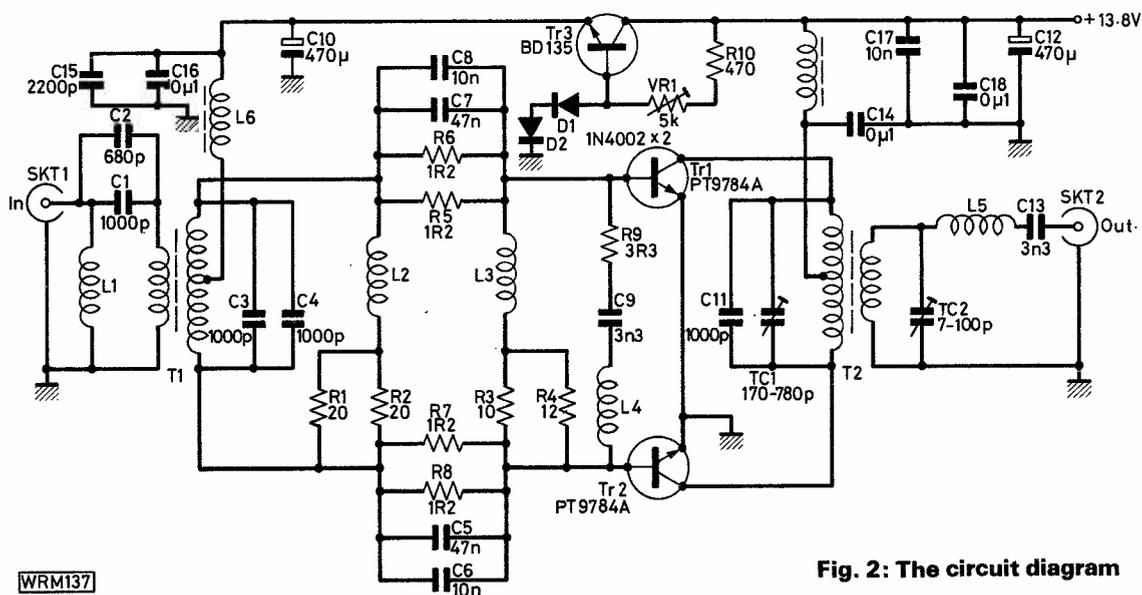


Fig. 2: The circuit diagram

Elements		Calc. value	Empirical value
CC	Cap (pF)	1474	1000+100/700 *
EE	Cap(pF)	136	20/100 *
FF	Ind. (nH)	256	90
	Cap (pF)	2993	4700

\* Variable capacitor

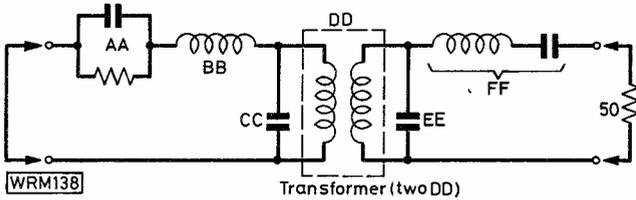


Fig. 3: Equivalent output circuit

Elements		Calc. value	Empirical value
AA	Ind. (nH)	5732	4000
BB	Cap (pF)	1294	1680
DD	Cap (pF)	1146	2000
EE	Res (Ω)	13.4	10
	Ind. (nH)	189	200
FF	Res. (Ω)	1.3	1.2
	Cap. (pF)	33350	57000
GG	Res (Ω)	7.2	5.5
	Ind (nH)	93.3	95
HH	Res (Ω)	6.8	4.3
	Ind (nH)	31.5	45
	Cap (pF)	3040	3300

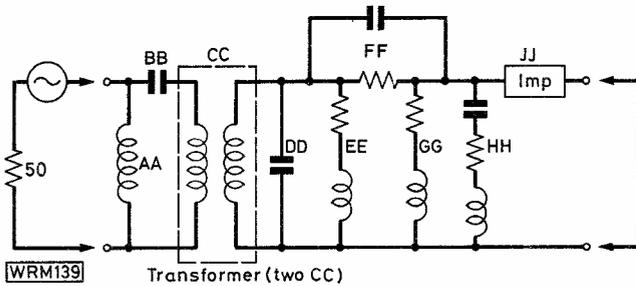



Fig. 4: Equivalent input circuit

series. Inductor AA and capacitor BB are for low-frequency transformer compensation and capacitor DD forms the high-frequency compensation.

Circuits EE, FF, GG and HH have two functions, namely to form a selective attenuator with 3Ω input impedance to stabilise the gain/frequency characteristic and to match the two transistor input impedances (which are in series) to 3Ω with the minimum of loss at the highest frequency. Again a computer program was employed to arrive at the final figures and the maximum v.s.w.r. is lower than 1.6:1.
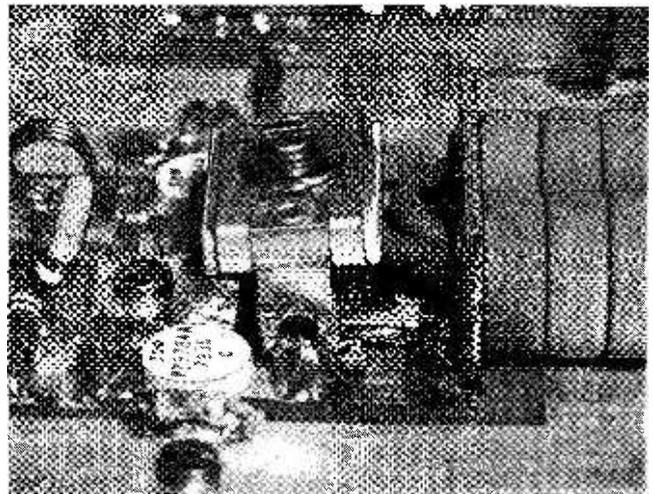
## Bias Circuit

Naturally, the two power transistors heat during operation, although this effect is reduced if the duty cycle



The mica chip capacitor can be seen between the trimmer and the end of the transformer. Note also the fins of the power transistor

is low—as in the case of c.w. or s.s.b. Never-the-less, a thermally-compensated bias current must be arranged. In this instance an emitter-follower circuit is used producing a low output resistance, in which the base voltage is fixed by a thermally-variable component—diode D2. This is fixed to the heatsink in a manner which ensures good heat transfer to take place. The method used in this project was to shape the adjacent fin on one of the power transistors into a bracket with which to secure the diode. A detailed illustration is given in Fig. 5. The diode D1 is needed to compensate the VBE of the transistor.

A more sophisticated circuit could have been evolved but this is quite adequate for the purpose. Potentiometer VR1 is used to adjust the current through the diodes by changing the voltage across them.

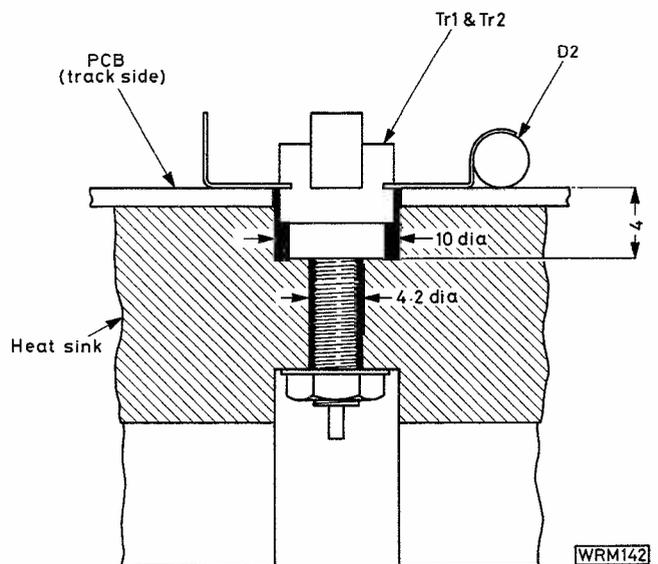


Fig. 5: Fixing diode D2 and mounting the power transistors

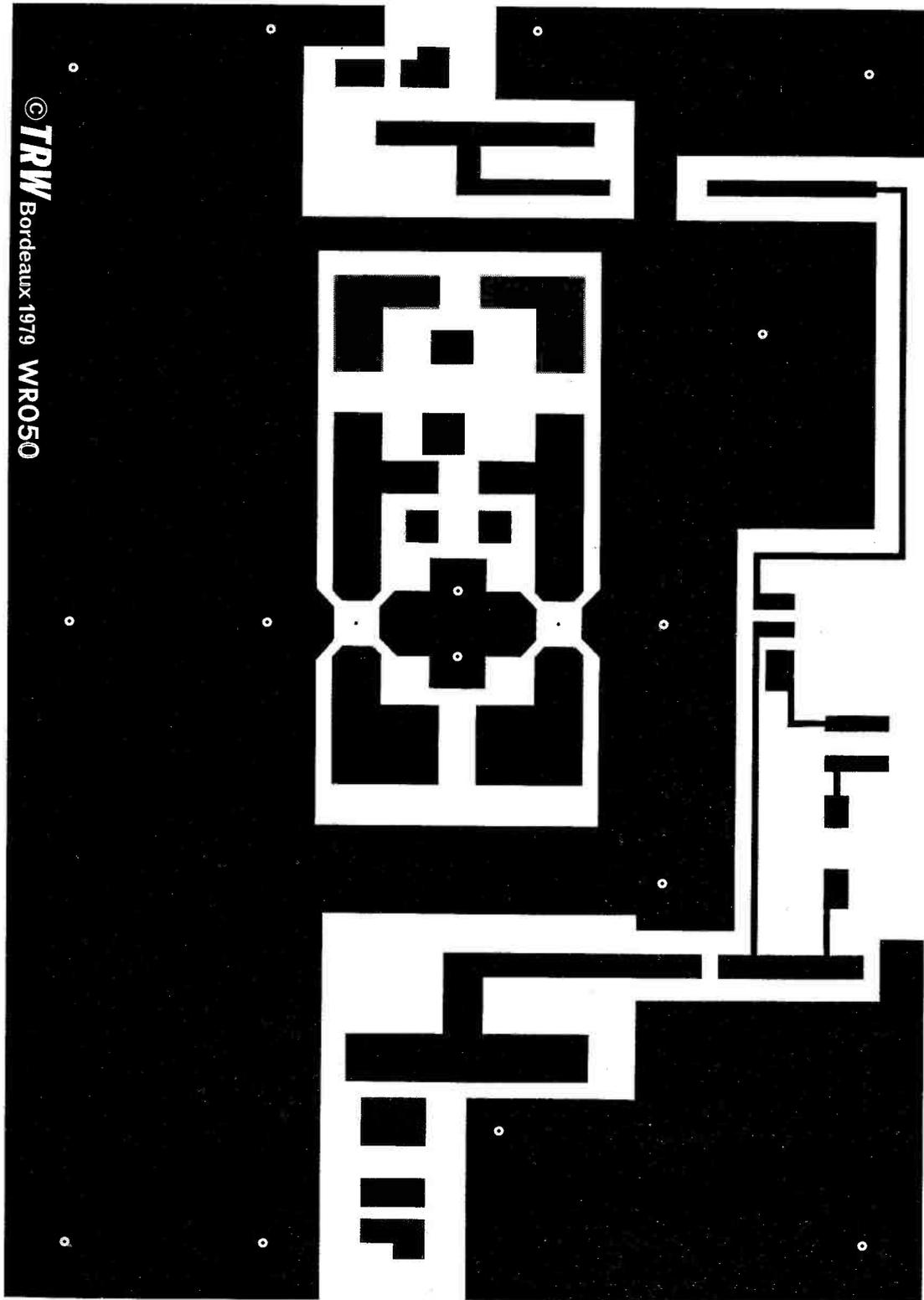


Fig. 6: Printed circuit board pattern



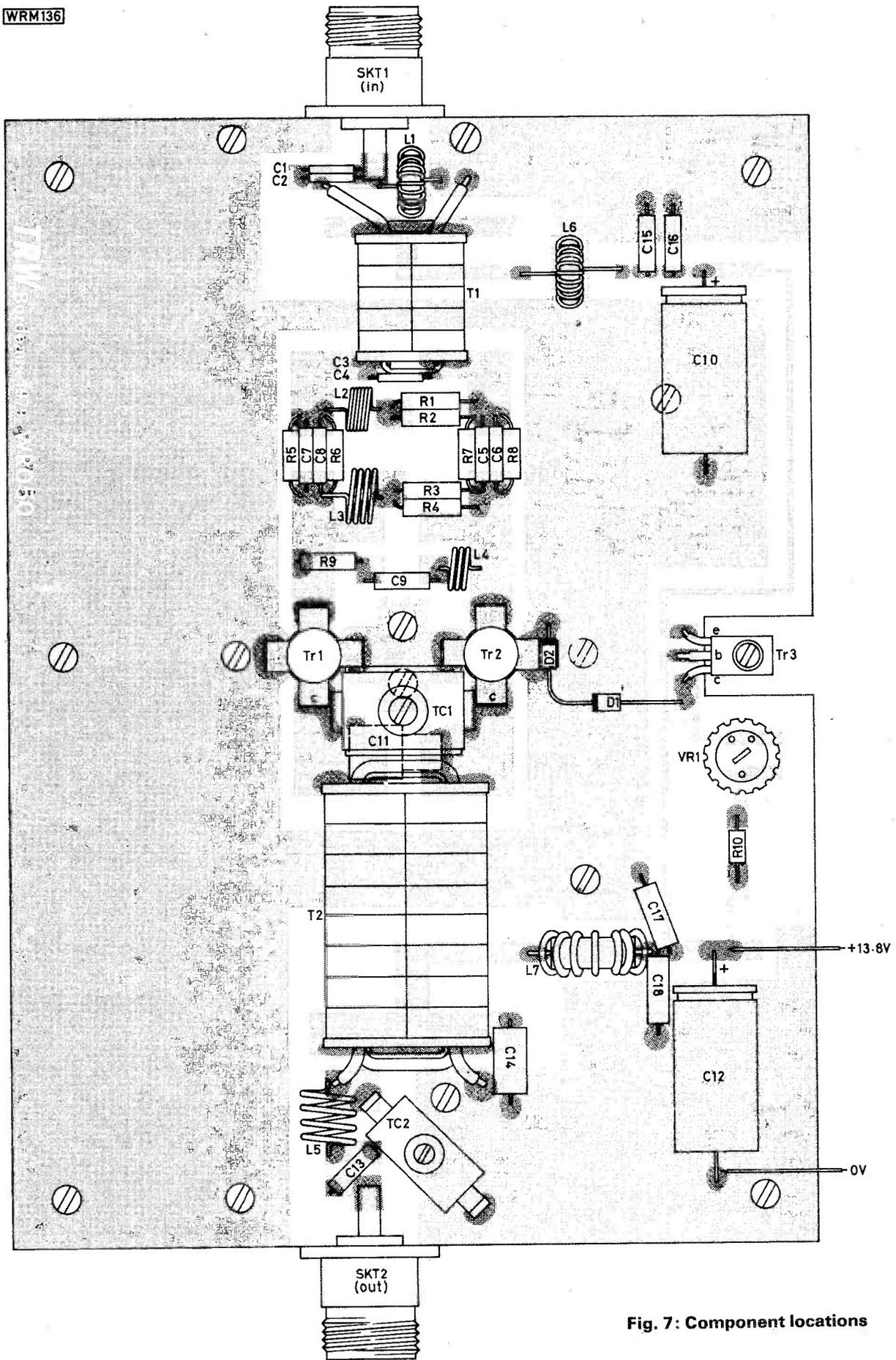
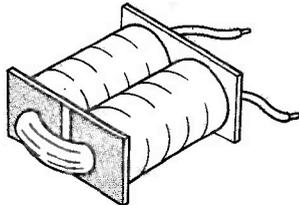
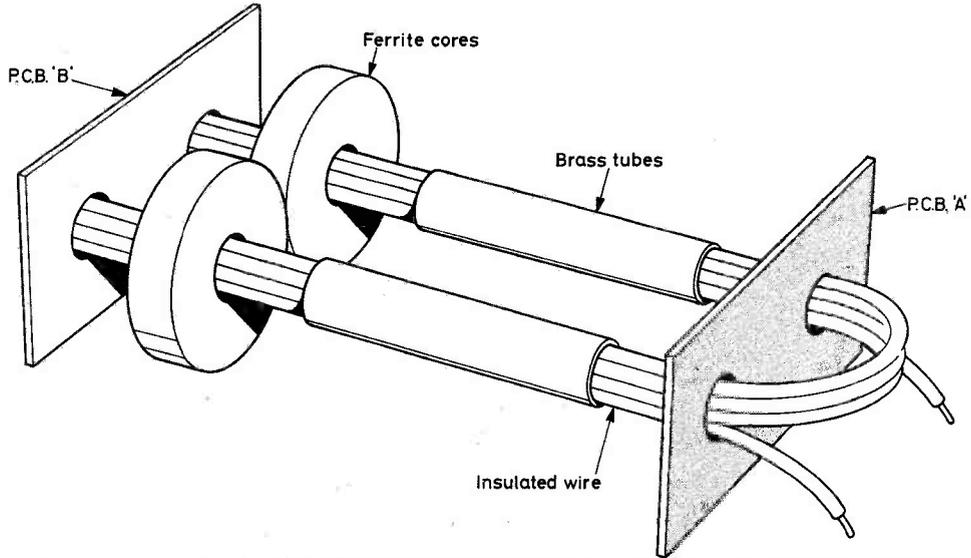
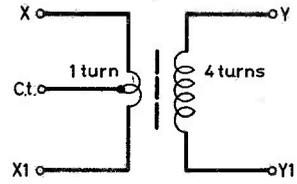
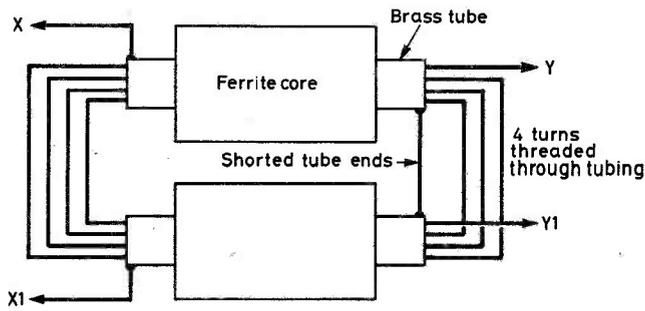
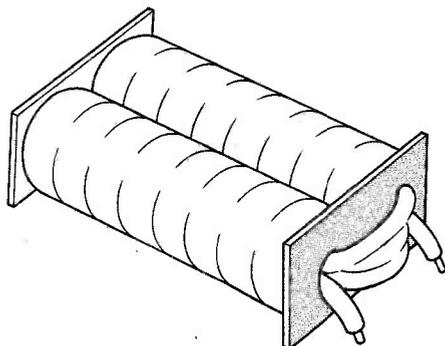




Fig. 7: Component locations

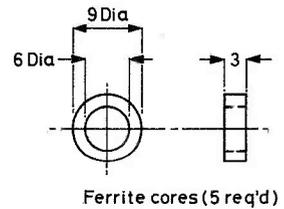

T1 (input transformer)

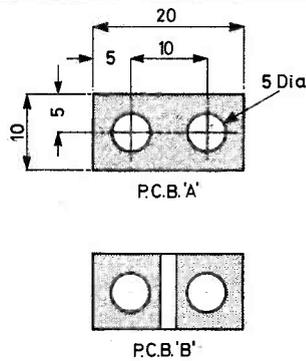

T2 (output transformer)

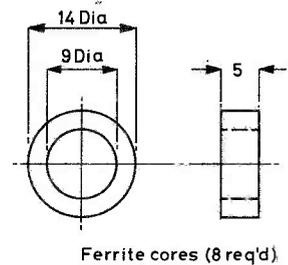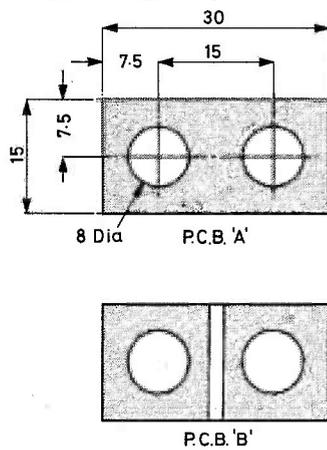

WRM134

## ★ components

### Resistors

$\frac{1}{2}$ W 10% metal oxide

1.2 $\Omega$	4	R5, 6, 7, 8
470 $\Omega$	1	R10

$\frac{1}{2}$ W 5% carbon composition

3.3 $\Omega$	1	R9
10 $\Omega$	1	R3
12 $\Omega$	1	R4
20 $\Omega$	2	R1, 2

### Potentiometers

Horizontal mounting, cermet, enclosed pre-set

5k $\Omega$	1	VR1
-------------	---	-----

### Capacitors

Miniature dipped-case polyester

2.2nF	1	C15
3.3nF	2	C9, 13
10nF	2	C6, 8
47nF	2	C5, 7

Miniature ceramic disc

680pF	1	C2
1nF	3	C1, 3, 4
10nF	1	C17

Monolithic ceramic

0.1 $\mu$ F	3	C14, 16, 18
-------------	---	-------------

Mica chip

1nF*	1	C11
------	---	-----

Tubular electrolytic. Axial leads

470 $\mu$ F 25V	2	C10, 12
-----------------	---	---------

### Trimmers

Arco compression type

7-100pF*	1	TC2 (Arco 423)
170-780pF*	1	TC1 (Arco 469)

### Semiconductors

Transistors

PT9784/A*	2	Tr1, 2
BD135	1	Tr3

Diodes

1N4002	2	D1, 2
--------	---	-------

### Coils

- L1 15 turns 0.5mm enamelled copper wire on \*RTC 4322-020-97170 toroid
- L2 6 turns 8mm inside diameter of 0.8mm enamelled copper wire
- L3 6 turns 8mm inside diameter of 1mm enamelled copper wire
- L4 4 turns 8mm inside diameter of 0.6-0.8mm enamelled copper wire 6mm long
- L5 4 turns 10mm inside diameter of 0.8-1.4mm enamelled copper wire 9mm long
- L6 25 turns 0.5mm enamelled copper wire on \*RTC 4322-020-97170 toroid
- L7 10 turns 1.5mm enamelled copper wire on \*RTC 4322-020-97180 toroid

### Transformers

T1—Primary

\* 2 x 5 ferrite cores 9 x 6 x 3mm  $\mu_r = 120$ , material 4C6 RTC reference 4322-020-97170 on 2 brass tubes 5mm o.d., 22mm long, with 10 x 20mm piece of copper-clad board at each end—see text.

T1—Secondary

4 turns of 0.5mm<sup>2</sup> insulated wire, wound through the 2 brass tubes.

T2—Primary

\* 2 x 8 ferrite cores 14 x 9 x 5mm  $\mu_r = 120$ , material 4C6, RTC reference 4322-020-97180 on 2 brass tubes 8mm o.d., 49mm long with a 15 x 30mm piece of copper-clad board at each end—see text.

T2—Secondary

4 turns of 1.8mm<sup>2</sup> insulated wire, wound through the 2 brass tubes.

### Miscellaneous

Printed circuit board (C. Bowes & Co.)  
Heatsink\*. Coaxial sockets (2)

### Component Sources

The specialised components marked with an asterisk are available from R. B. Knight, 28 Lynwood Drive, Wimborne, Dorset. Tel: (0202) 888426. These include the RTC ferrites used for the transformers and coils L1, L6 and L7. In addition, suitable brass tubing for T1 and T2 can also be obtained from this source.


## Making the Transformers (Fig. 8)

By careful reference to the drawings one should be able to reproduce the transformers with a high degree of accuracy. Note the end pieces (which are made from small rectangles of single-sided copper-clad board) very carefully. One has a narrow strip of copper removed to form two distinct and separate islands. The other joins the two brass tubes and when fixed to the main p.c.b. forms the centre-tap connection.

Only the dimensions, wire gauges and—most important—the toroids specified must be used. The transformer assemblies should be fitted to the p.c.b. before the windings of insulated wire are inserted into the tubes, otherwise heat generated during the soldering process may destroy the sleeving.

The heatsink used to accommodate the prototype can be seen to be quite substantial—around 0.5°C/W. However, the power amplifier could well be reduced in size and mounted within existing equipment, say on a metal

WRM141

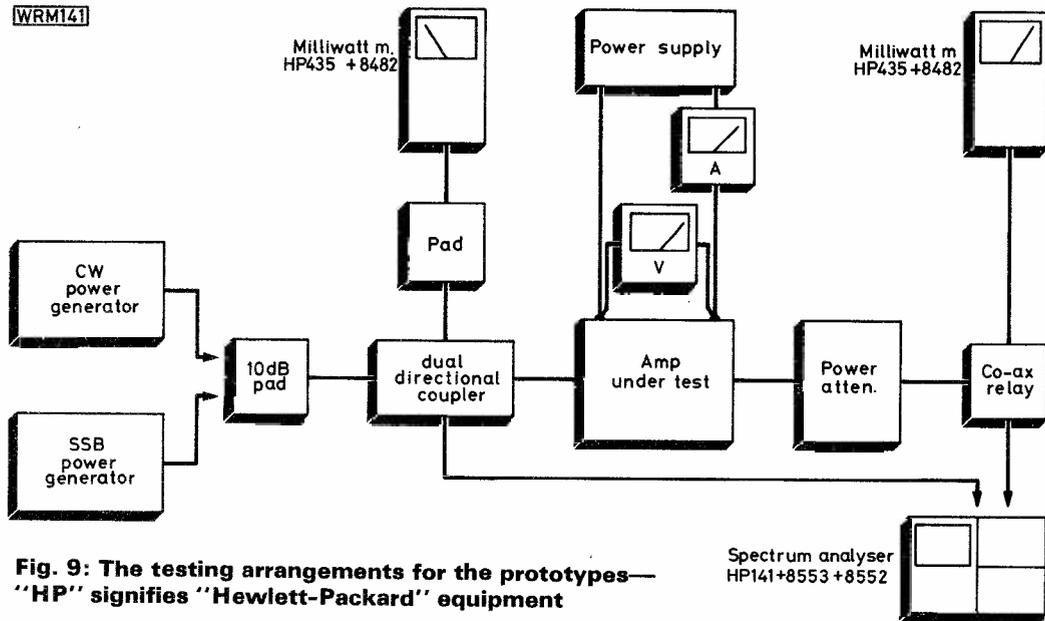

**Fig. 9: The testing arrangements for the prototypes—**  
**"HP" signifies "Hewlett-Packard" equipment**

back-plate. In this case, additional heatsinking could be provided on the outside.

If the method of mounting the power transistors used in the prototype is used, it will be necessary to put a small, flat-bottomed countersink in the heatsink to settle the devices properly (Fig. 5). Great care should be taken to ensure maximum heat transfer by making the stud holes only just large enough for the thread to pass through. Do not chamfer, but de-burr with Emery cloth. Apply a smear of thermal grease and tighten—firmly, but not so as to stretch the studding. (About 10lb. inches torque, for the perfectionist.)

Finally, note that in some areas continuity of the earth plane sections of the p.c.b. is effected by the fixings to the heatsink. If other arrangements of the amplifier are envisaged, it may be necessary to take this into account.

### Setting up the Amplifier

The technology employed in this project means that a minimum of adjustment is required to achieve acceptable performance. If you are fortunate enough to have access to a spectrum analyser, all the better. A description of the original test arrangements is given in Fig. 9.

In its quiescent state, the module will only draw a few hundred milliamps—typically 200. This is set by the

potentiometer VR1. It is a good idea to initially apply a very low level of r.f., which is increased gradually whilst carefully observing the current consumption. Judicious peaking of the trimmers should be all that is necessary to produce the required output.

## KINDLY NOTE!

### PW "Soundlite", March 1979

On Fig. 5, electrolytic capacitor labelled C18 adjacent to D12 should be C13. On Fig. 6 the labels on the Bass and Treble switches should be transposed.

### Car Test Probe, May 1979

The three l.e.d.s (D2, 3, 4) are shown connected the wrong way round in the circuit diagram. They are correctly shown in the component drawing.

**VISIT PW ON STAND A10 (NEAR THE STAGE) AT THE RSGB EXHIBITION, ALEXANDRA PALACE, LONDON N22**

**May 11, 10am to 7.30pm**

**May 12, 10am to 6pm**

**Admission 60p**

# RST VALVE MAIL ORDER CO.

## CLIMAX HOUSE, FALLSBROOK ROAD, LONDON SW16 6ED

### SPECIAL EXPRESS MAIL ORDER SERVICE

#### SEMICONDUCTORS

AA119 0.10	ASV26 0.40	BC159 0.10*	BCY72 0.13	BF194 0.09*	BZX61 0.18	QA70 0.30	OC82 0.65	ZS271 0.23*	2N697 0.25	2N3055 0.70
AA30 0.27	ASV27 0.40	BC167 0.12*	BCZ11 1.50	BF196 0.10*	BZY88 0.13	QA79 0.30	OC83 0.65	ZS278 0.57*	2N698 0.30	2N3440 0.60
AA32 0.42	ASZ15 1.25	BC170 0.11*	BD121 1.20	BF197 0.12*	Series	OA81 0.30	OC84 0.65	ZTX107 0.11*	2N705 1.20	2N3441 0.80
AA33 0.18	ASZ16 1.25	BC171 0.10*	BD123 1.20	BF200 0.27	CRS/105 0.45	OA85 0.30	OC122 1.50	ZTX109 0.10*	2N706 0.15	2N3442 1.10
AA37 0.27	ASZ20 1.50*	BC173 0.12*	BD124 1.30	BF224 0.20*	CRS/140 0.60	OA90 0.08	OC123 1.75	ZTX109 0.12*	2N708 0.20	2N3525 0.80
AC107 0.60	ASZ21 2.00	BC177 0.15	BD131 0.35	BF244 0.28*	CRS/340 0.75	OA91 0.08	OC139 2.25	ZTX300 0.12*	2N930 0.20	2N3614 1.50
AC125 0.20	AU110 1.70*	BC178 0.14	BD132 0.38*	BF257 0.24	CRS/360 0.90	OA95 0.08	OC140 2.75	ZTX301 0.13*	2N1131 0.26	2N3702 0.11*
AC126 0.20	AU113 1.70*	BC179 0.16	BD136 0.34*	BF258 0.26	GEX66 1.50	OA200 0.09	OC141 3.25	ZTX303 0.15*	2N1132 0.26	2N3703 0.13*
AC127 0.20	AU117 1.70*	BC182 0.11*	BD138 0.40*	BF259 0.32	GEX54 1.75	OA202 0.09	OC170 1.00	ZTX303 0.17*	2N1202 0.35	2N3704 0.13*
AC128 0.20	BA145 0.13*	BC183 0.10*	BD139 0.43*	BF338 0.31*	GJ5M 0.75	OA201 1.00	OC200 1.50	ZTX311 0.12*	2N1304 0.45	2N3706 0.13*
AC141 0.25	BA148 0.13*	BC184 0.11*	BD140 0.44*	BF521 3.96	GM0378A 1.75	OA206 1.00	OC201 1.75	ZTX314 0.20*	2N1305 0.45	2N3707 0.13*
AC141K 0.35	BA154 0.09	BC212 0.13*	BD144 2.00	BF528 2.23	MJ340 0.80	OC16 2.90	OC202 1.75	ZTX500 0.13*	2N1306 0.50	2N3708 0.10*
AC142 0.75	BA155 0.10	BC213 0.10*	BD181 1.18	BF531 1.10*	MJE370 1.10	OC20 2.50	OC203 1.75	ZTX501 0.14*	2N1307 0.50	2N3709 0.13*
AC142K 0.30	BA156 0.09	BC214 0.15*	BD237 0.40	BF532 0.26	MJE371 0.61	OC22 2.50	OC205 2.50	ZTX503 0.17*	2N1308 0.55	2N3710 1.00*
AC176 0.20	BAW62 0.05	BC237 0.09*	BD238 0.55	BFW11 0.65	MJE520 0.32	OC23 2.75	OC206 2.50	ZTX504 0.20*	2N1309 0.55	2N3711 0.10*
AC187 0.20	BAX13 0.06	BC238 0.12*	BDX10 0.91	BFX84 0.22	MJE521 0.55	OC24 3.00	OC207 1.75	ZTX511 0.20*	2N1671 1.50	2N3771 1.75
AC188 0.20	BAX16 0.09	BC301 0.25	BDX32 2.00	BFX85 0.23	MJE2955 1.25	OC25 0.90	OC208 2.50	ZTX511 0.20*	2N1893 0.25	2N3772 2.00
AC19 0.80	BC107 0.12	BC303 0.24	BDY00 1.25	BFX87 0.21	MJE3055 0.75	OC26 0.90	OC209 2.25*	IN915 0.07	2N2148 1.65	2N3773 3.00
AC197 0.75	BC108 0.12	BC307 0.10*	BF100 0.50	BFY80 0.26	MPF102 0.30*	OC28 2.00	R2010B 1.75*	IN4002 0.06	2N2218 0.25	2N3823 0.55*
AC20 0.70	BC109 0.13*	BC322 0.20*	BF115 0.25	BFY80 0.26	MPF103 0.30*	OC29 2.00	IC44 0.30	IN4003 0.07	2N2220 0.18	2N3866 0.72
AC21 0.75	BC114 0.12*	BC327 0.18*	BF152 0.18	BFY51 0.26	MPF104 0.30*	OC35 1.50	IC226D 1.20	IN4004 0.07	2N2221 0.18	2N3904 0.13*
AC39 1.50	BC115 0.14*	BC337 0.18*	BF153 0.20	BFY52 0.26	MPF104 0.30*	OC36 1.50	IL209 0.20	IN4005 0.08	2N2222 0.18	2N3905 0.13*
AD149 0.70	BC116 0.15*	BC338 0.17*	BF154 0.17	BFY64 0.26	MPF105 0.30*	OC41 0.80	IP29A 0.41*	IN4006 0.08	2N2223 2.17	2N3906 0.13*
AD161 0.45	BC117 0.17*	BCY30 1.00	BF159 0.23	BFY90 1.25	MPSA06 2.4*	OC42 0.75	IP30A 0.44*	IN4007 0.09	2N2368 0.27	2N4058 0.14*
AD162 0.45	BC118 0.10*	BCY31 1.00	BF160 0.16	BSX19 0.21	MPSU10 0.36*	OC43 2.25	IP31A 0.45	IN4009 0.06	2N2369A 0.21	2N4060 0.12*
AF105 0.45	BC125 0.09	BCY32 1.00	BF167 0.20	BSX20 0.21	MPSU06 0.46*	OC44 0.60	IP32A 0.48	IN4148 0.06	2N2484 0.20	2N4061 0.12*
AF114 0.75	BC126 0.10*	BCY33 0.90	BF173 0.20	BSY61 1.20*	MPS560 0.49*	OC45 0.65	IP33A 0.48	IN4149 0.06	2N2485 0.20	2N4062 0.12*
AF115 0.75	BC135 0.14*	BCY34 0.90	BF177 0.24	BT106 0.55	NE555 0.45	OC71 0.55	IP34A 1.73	IN5401 0.13	2N2904 0.25	2N4062 0.13*
AF116 0.75	BC136 0.15*	BCY39 3.00	BF178 0.24	BTY79/400R	NK740 1.70	OC72 0.55	IP41A 0.63	IS44 0.04	2N2905 0.25	2N4124 0.15*
AF117 0.75	BC137 0.15*	BCY40 1.00	BF179 0.25	BU205 3.19	NKT403 2.00	OC73 0.70	IP42A 0.70	IS920 0.07	2N2906 0.21	2N4126 0.15*
AF139 1.40	BC147 0.09*	BCY42 0.25	BF180 0.30	BU206 2.25*	NKT404 1.73	OC74 0.65	IP2955 1.67	IS921 0.07	2N2907 0.21	2N4286 0.20*
AF186 1.20	BC148 0.08*	BCY43 0.25	BF182 0.30	BU208 2.00*	OA5 0.50	OC75 0.65	IP3055 0.56	IS922 0.07	2N2924 0.21*	2N4286 0.20*
AF239 0.45	BC149 0.09*	BCY58 0.25	BF183 0.30	BU209 2.00*	OA6 0.50	OC76 0.65	IS143 1.00	IS923 0.07	2N3032 1.00	2N4389 0.24*
AF239 0.45	BC157 0.09*	BCY59 0.25	BF184 0.25	BU210 2.00*	OA7 0.50	OC77 1.20	IS143 1.00	IS924 0.07	2N3032 1.00	2N4389 0.24*
AF212 2.75	BC158 0.08*	BCY70 0.17	BF184 0.25	BU211 2.00*	OA10 0.60	OC78 0.65	IS170 1.21	IS925 0.07	2N4044 1.00	2N5457 0.35*
			BF185 0.25	BU212 2.00*	OA17 0.14	OC81 1.20	IS178 0.54*	IS926 0.07	2N4045 1.00	2N5458 0.35*
									2N4046 1.00	2N5459 0.35*

#### VALVES

AZ31 1.10*	ECC821 0.47*	MU14 1.60*	PL81A1 1.20	UR41 1.25*	5Z3 1.50*	6BH61 1.20*	6K6GT 1.30*	7H7 2.00*	85A2 1.75
CBL31 1.50	ECC831 0.55*	N78 9.00*	PL82 0.60*	UR41C 1.10*	5Z4G 1.52*	6BJ6 1.20*	6K7 1.50*	7R7 1.50*	90AG 7.96
CL33 2.00*	ECC841 0.60*	OA21 0.55*	PL83 0.55*	URF89 0.60*	5Z4GT 1.50*	6BK4 4.21*	6K8 1.75*	757 2.25*	90AV 7.96
CY31 1.00*	ECC851 0.55*	OB21 0.60*	PL84 0.75*	URC84 1.10*	6-30L2 1.80*	6BL6 85.00	6K6D 2.50*	7Y4 1.80*	90C1 1.80
DAF911 0.40*	ECC881 0.75*	OC31 0.75	PL504/500†	UC85† 0.55*	6AB7 0.75*	6BL7GT 3.86*	6L6G 6.16*	7Z4 1.85*	90CG 13.68
DAF96 1.00*	ECC911 0.55*	EL34 (Mullard)	PL508† 1.80	UCF80 1.15*	6AC7 0.75*	6BN6 0.80*	6L6GA 1.50*	12AT8 1.20*	90CV 13.30
DF911 0.40*	ECC189 1.66*	EL41 1.25*	PL509† 3.00	UCH42 1.20*	6AF4† 0.70*	6BD7A 1.50*	6L6GT 0.85*	12AT7† 0.50*	92AG 7.96
DF86 1.00*	ECC190 0.60*	EL42 1.75*	PL519† 3.20	UCH81† 0.65*	6AG7 0.75*	6BR7 4.00*	6L6GC 1.95*	12AU6 0.65*	92AV 7.96
DK92 1.25*	ECC321 0.70*	EL43 1.00*	PL801 1.10*	UCL82† 0.75*	6AH6† 0.95*	6BR8† 1.20*	6L7 2.00*	12AU7† 0.47*	150B2 2.15
DK96 1.10*	ECC381 0.70*	EL44 1.25*	PL802 3.48*	ULC83 1.44*	6AK5† 0.50*	6BS7 4.00*	6N2P 1.05*	12AV6 0.85*	150C2 1.60
DL92 0.75*	ECC42 1.15*	EL45 0.85*	PL803 3.48*	UF41 1.00*	6AK6 0.95*	6BW6 3.75*	6N3P 1.05*	12AV7 3.48*	150C4 2.30
DL94 1.20*	ECC43 1.15*	EL46 0.85*	PL804 3.48*	UF80† 0.50*	6AL5† 0.40*	6BW7 1.50*	6N3P 1.05*	12AX7 0.55*	211 6.00
DL96 1.10*	ECC44 1.15*	EL47 0.85*	PL805 3.48*	UF85† 0.50*	6AM4 2.30*	6B7GT 9.95*	6P25 3.50*	12AY7† 0.85*	723AB† 8.00
				UL1 1.80*	6AM5 3.85*	6BZ 1.75*	6D2 2.20*	12BA4† 1.00*	807† 1.20
				UL41 0.85*	6AM6† 0.70*	6C4† 0.55*	6R7 1.00*	12BA6 0.65*	811A† 3.80
				UL84† 0.85*	6AN5 5.32*	6C6BA† 0.55*	6SA7 1.45*	12BE6 1.60*	812A 3.35
				UM80 1.00*	6ANB† 0.70*	6C6GA† 0.90*	6SC7 1.50*	12BH7† 0.65*	813† 10.00
				UY41† 0.75*		6C6G† 1.72*	6SF7 1.80*	12BY7† 0.80*	814† 6.00
				UY85† 0.85*		6C6H† 1.50*	6S7 1.50*	12C1 7.00	866A 8.85
				6AQ5† 0.85*		6C6I† 1.50*	6S7 1.50*	12CA7 1.20*	872A 13.75
				6AR5 0.70*		6C6J† 1.50*	6S7 1.50*	12CA7 1.20*	872A 13.75
				6AS† 0.55*		6C6K† 1.50*	6S7 1.50*	12CA7 1.20*	872A 13.75
				6AS7† 1.50*		6C6L† 0.75*	6S7 1.50*	12CA7 1.20*	872A 13.75
				6AT6† 0.75*		6C6M† 1.50*	6S7 1.50*	12CA7 1.20*	872A 13.75
				6AUS† 4.26*		6C6N† 1.50*	6S7 1.50*	12CA7 1.20*	872A 13.75
				6AU6† 0.55*		6C6O† 1.50*	6S7 1.50*	12CA7 1.20*	872A 13.75
				6AV† 4.18*		6C6P† 1.50*	6S7 1.50*	12CA7 1.20*	872A 13.75
				6AV6† 0.75*		6C6Q† 1.50*	6S7 1.50*	12CA7 1.20*	872A 13.75
				6AW8† 1.00*		6C6R† 1.50*	6S7 1.50*	12CA7 1.20*	872A 13.75
				6AX5† 3.10*		6C6S† 1.50*	6S7 1.50*	12CA7 1.20*	872A 13.75
				6B† 0.75*		6C6T† 1.50*	6S7 1.50*	12CA7 1.20*	872A 13.75
				6B† 0.75*		6C6U† 1.50*	6S7 1.50*	12CA7 1.20*	872A 13.75
				6B† 0.75*		6C6V† 1.50*	6S7 1.50*	12CA7 1.20*	872A 13.75
				6B† 0.75*		6C6W† 1.50*	6S7 1.50*	12CA7 1.20*	872A 13.75
				6B† 0.75*		6C6X† 1.50*	6S7 1.50*	12CA7 1.20*	872A 13.75
				6B† 0.75*		6C6Y† 1.50*	6S7 1.50*	12CA7 1.20*	872A 13.75
				6B† 0.75*		6C6Z† 1.50*	6S7 1.50*	12CA7 1.20*	872A 13.75
				6B† 0.75*		6C6A† 1.50*	6S7 1.50*	12CA7 1.20*	872A 13.75
				6B† 0.75*		6C6B† 1.50*	6S7 1.50*	12CA7 1.20*	872A 13.75
				6B† 0.75*		6C6C† 1.50*	6S7 1.50*	12CA7 1.20*	872A 13.75
				6B† 0.75*		6C6D† 1.50*	6S7 1.50*	12CA7 1.20*	872A 13.75
				6B† 0.75*		6C6E† 1.50*	6S7 1.50*	12CA7 1.20*	872A 13.75
				6B† 0.75*		6C6F† 1.50*	6S7 1.50*	12CA7 1.20*	872A 13.75
				6B† 0.75*		6C6G† 1.50*	6S7 1.50*	12CA7 1.20*	872A 13.75
				6B† 0.75*		6C6H† 1.50*	6S7 1.50*	12CA7 1.20*	872A 13.75
				6B† 0.75*		6C6I† 1.50*	6S7 1.50*	12CA7 1.20*	872A 13.75
				6B† 0.75*		6C6J† 1.50*	6S7 1.50*	12CA7 1.20*	872A 13.75
				6B† 0.75*		6C6K† 1.50*	6S7 1.50*	12CA7 1.20*	872A 13.75

# P.W. JUMBO CLOCK

*Kits of parts by the designers of the clock.*

## Kit A.

Comprising of printed circuit board. **Price £8.96.** V.A.T. and postage included.

## Kit B.

Comprising of printed circuit board, case, perspex panel, pillars, transformer and l.e.d.s. **Price £22.72.** V.A.T. and postage included.

## Kit C.

Comprising of full kit, excluding mains cable and wire. **Price £29.00.** V.A.T. and postage included.

Two colours of cases are available:- Gloss White & Simulated Black Leather Grain.

Please state colour with order e.g. Kit C/Black.

## Full range of R.S. components available (48 hours service)

If you are experiencing difficulty in obtaining certain components for projects please do not hesitate to telephone us.

## I.C.'s for Soundlite Converter Type LM3900 & MC 3302

**£1.13** per pair

Postage and package 20 pence.

## P.C.B.'S FOR

## PRACTICAL WIRELESS PROJECTS

Nov. 78.	Sarum Q Meter	R030	Price £3.30 & 20 pence p & p.
Nov. 78.	S.T.D. Charge Timer	AD212	Price £2.80 & 20 pence p & p.
Nov. 78.	Porch Light Timer	AD222	Price £0.60 & 12 pence p & p.
Nov. 78.	Battery Indicator	AD225	Price £0.60 & 12 pence p & p.
Dec. 78.	Car Radio L.W. Converter	R034	Price £2.35 & 15 pence p & p.
Dec. 78.	Digital Door Chimes	R017	Price £3.78 & 25 pence p & p.
Dec. 78.	Car Radio L.W. Converter	R032	Price £2.62 & 20 pence p & p.
Jan. 79.	Acoustic Delay Line	R018	Price £3.53 & 20 pence p & p.
Jan. 79.	Dorchester	R033	Price £10.80 & 30 pence p & p.
Feb. 79.	Hythe Receiver	WR037	Price £5.94 & 20 pence p & p.
March 79.	Hythe Receiver	WR038	Price £2.70 & 20 pence p & p.
March 79.	Soundlite Converter	WK001	Price £5.98 & 20 pence p & p.
March 79.	Tone Burst Generator	R023	Price £1.60 & 15 pence p & p.
March 79.	Wide Band Noise Source	WR036	Price £0.70 & 12 pence p & p.
April 79.	PW 'Winton'	WR039	Price £15.42 & 30 pence p & p.
April 79.	FM Multitester	WR040	Price £2.70 & 15 pence p & p.
May 79.	Car Test Probe	WR042	Price £0.90 & 15 pence p & p.
May 79.	Follow up to PW Gillingham	WR044	Price £1.36 & 15 pence p & p.
May 79.	PW Imp	WR043	Price £1.42 & 15 pence p & p.
May 79.	Inline Crystal Calibrator	WR041	Price £1.58 & 15 pence p & p.
June 79.	Jumbo Clock		Price £8.66 & 30 pence p & p.


All prices include V.A.T.

Send orders to:

**C. BOWES & CO. LTD.,**  
4, WOOD STREET,  
CHEADLE,  
CHESHIRE SK8 1AQ.  
Tel. 061-428-4497.

Please state type number and enclose cheque or postal order.

## Hey, Good Looking!

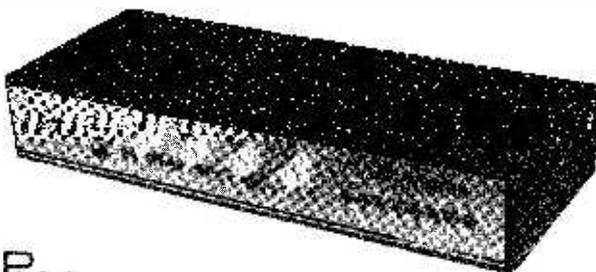

P.W.  
**'WINTON'**

Beautiful innit?, but a swish exterior can often be an eye catching cover for some very ordinary "guts", so what's so different about the WINTON?

Well, for a start we have discarded Bi-Polar output devices in favour of the far superior performance of the Hitachi Power MOS-FETS, which until now have only been available in some of the most expensive Hi-Fi Amplifiers around, (and we consider £700 to be expensive with a capital E!). Secondly, our extremely low distortion figures are obtained at FULL RATED OUTPUT with both channels driven, across the entire audio spectrum.

Further, at these power levels 2nd and 3rd order inter-modulation components are typically less than 0.005% (See the March issue of P.W. for the full spec' and a few shots from the Spectrum Analyser.) Whilst we freely admit that ownership of a Winton will not prevent your hair from falling out, nor warts from growing on your nose, you will feel a nice sense of achievement when the job is complete, and you will own an Amplifier that will make your mates positively green with envy, until that is they see the light and obtain one of their own.

The WINTON Kit is available in the following form:-

Pack (A) Capacitors & Fixed Value Resistors	Price Inc. V.A.T. & carriage.
Pack (B) Switches, Potentiometers, Pre-Sets & Knobs	<b>£21.45</b>
Pack (C) Printed Circuit Board, and Terminal Pins	<b>£13.26</b>
Pack (D) Hardware Pack, consisting of Chassis, Heat Sinks, Cabinet, Screws, Wire, Fuseholders etc., and a Brushed Aluminium Fascia Front Panel.	<b>£8.10</b>
Pack (E) Semiconductors (including HITACHI MOS Power Fets)	<b>£32.99</b>
Pack (F) Toroidal Mains Transformer	<b>£30.53</b>
Complete Kit of all parts necessary to build the WINTON	<b>£17.22</b>
	<b>£120.00</b>

ORDER WITH COMPLETE CONFIDENCE (Cash with order please) FROM:-

**T. & T. ELECTRONICS. GREEN HAYES, SURLINGHAM LANE, ROCKLAND ST. MARY, NORWICH, NORFOLK. NR14 7HH.**  
PLEASE ALLOW 28 DAYS FOR DELIVERY.

# THE PW 'WINTON' Stereo Amplifier

## Part 4

### E.A.RULE

The manner in which the peripheral components of a hi-fi system are connected to the main amplifier is very important, especially if low noise and hum are required. One extra earth connection can lead to horrible hum problems through earth loops.


The drawing (Fig. 19) shows how the connections should be made between the PW Winton amplifier and the tape, record deck and tuner unit.

Three minor errors occurred in the metalwork drawings in the April issue. Fig. 13 which shows the mounting

details of the power transistors has the chassis upside down and inside out. The right-angle fold should be at the bottom and folded away from the heat sink.


Fig. 14 the main chassis drawing has the mains transformer fixing holes shown at 75mm from the back edge of the chassis. The entire group of holes for this component should be centred at 75mm from the front edge.

Fig. 15 has the chassis front shown upside down, with the bottom fold at the top.

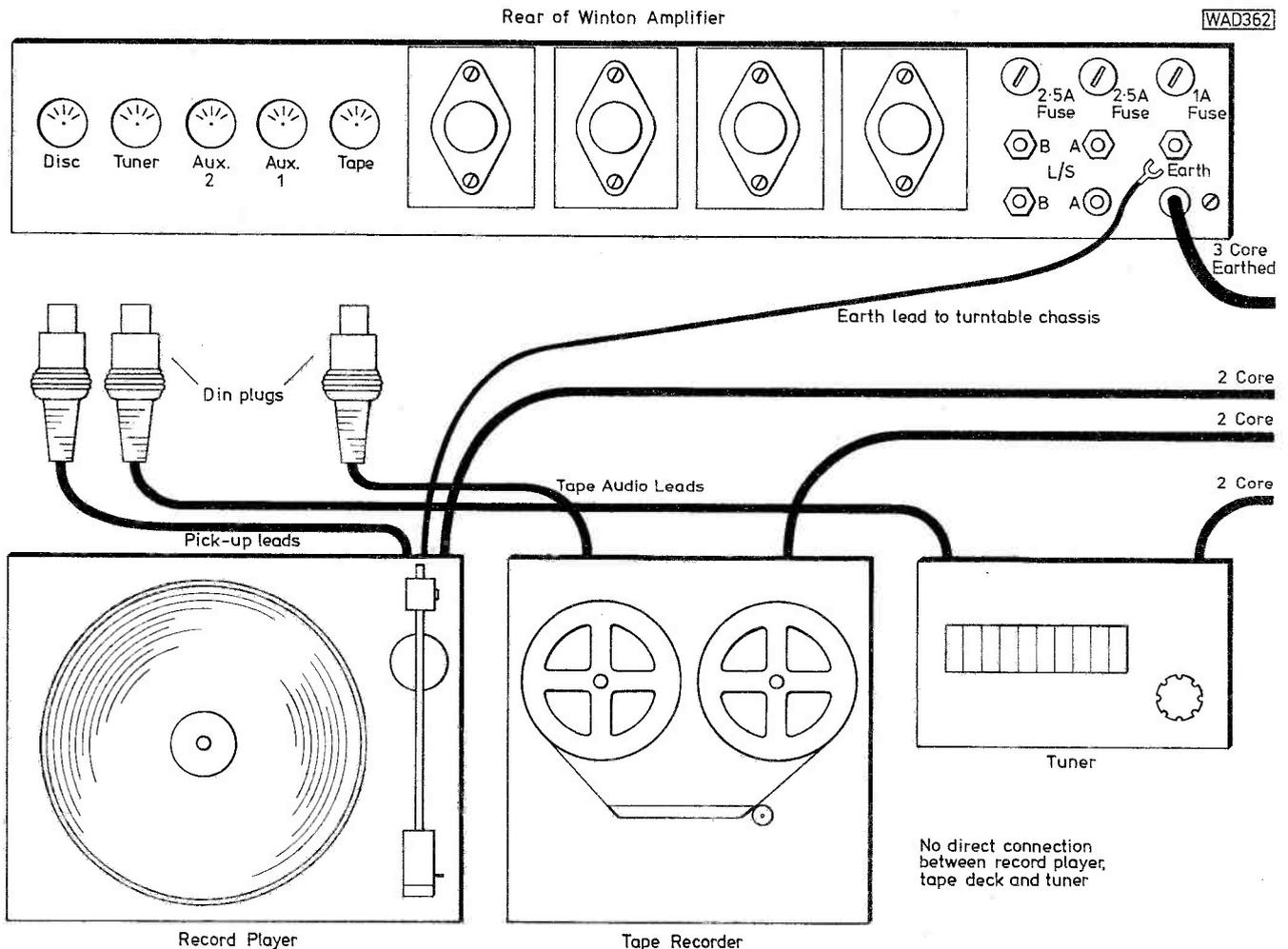

**Very Important**  
No direct connection between record player chassis and pick-up

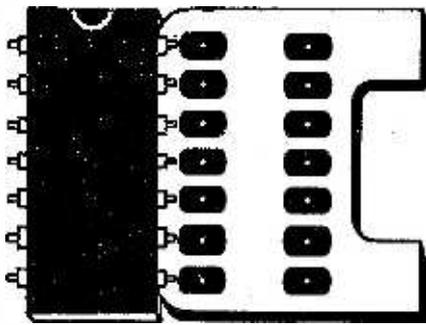**Interconnections between PW Winton amplifier and peripheral equipment**



# OF THE MONTH 76

Brian DANCE M.Sc

## FAIRCHILD μA78HG REGULATOR

Most of the currently available voltage regulators will provide only a small output current of the order of 100mA to 1A. Greater current demands require the use of a low current regulator with a series-pass transistor in a more complex circuit or a number of low current regulators.

Most regulator devices have a fixed output voltage. Although variation is possible by suitable circuit techniques, it is not generally convenient to purchase just one type of fixed voltage device and expect to be able to use it to provide a specific voltage range.

The new Fairchild μA78HG 5A regulator with variable output voltage can provide the answer to the problem of obtaining high output currents from simple circuitry over the wide operating output range of 5V to 20V.

### The μA78HG

The μA78HG is encapsulated in an hermetically sealed metal package like that of TO-3 transistors, but has the four connections shown in Fig. 1 instead of the normal three leads of a TO-3 device. The case must be bolted to a suitable heat sink where the internal power dissipation is appreciable. The letter "H" in the type number of this device signifies that it is a "hybrid" component which unlike monolithic integrated circuits contains several silicon chips joined together internally.

The μA78HG can be used in the simple circuit of Fig. 2. The internal circuitry of the device maintains the "control" pin at +5V relative to the "common" pin. It is recommended that the value of the current in R2 should be 1mA, so R2 should normally have a value of 5 kilohm.

The value used for R1 determines the output voltage. This output voltage,  $V_o$ , is given by the equation:

$$V_o = 5 \times (1 + R1/R2)$$

Thus if R1 has a value of 5kΩ, the output voltage will be 10V, whilst R1 should be 15kΩ for a 20V regulated output.

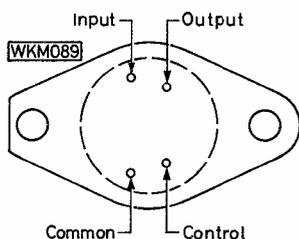


Fig. 1: The μA78HG package and connections

For a variable output voltage, R1 should be replaced with a suitable potentiometer.

### Drop-out Voltage

It must be emphasised that this type of regulator cannot supply a greater output voltage than the applied input voltage; indeed, the output will always be somewhat less than the input. As the input voltage is decreased, a point is reached at which the regulator circuit "drops out" and ceases to function. The drop-out voltage is the difference between the input and output voltages when the regulator ceases to function.

The drop-out voltage of the μA78HG is typically 2.6 volts at 3 amps output, and 3 volts at 5 amps output. Thus one should always ensure that the input voltage to the circuit is at least 3.5 volts above the maximum output voltage required. However, the input voltage must never be allowed to exceed 25 volts, even for an instant, or the regulator device may be damaged.

The μA78HG contains an internal circuit to prevent damage when the output voltage is accidentally shorted to ground. This internal circuit limits the output current to approximately 7 amps under such conditions. In addition, the device incorporates "safe operating area" protection which ensures that the power transistors in the device are kept within the safe operating area of their current/voltage characteristic. Any tendency to go outside this safe operating area will result in the device being shut down with little output current until the condition is cleared.

### Thermal Considerations

The μA78HG also has internal circuitry which prevents damage to the device by overheating, such as when an inadequate heatsink is fitted. Never-the-less, it is advisable to operate the device so that it does not become too hot, since high temperature operation tends to reduce the life by a factor of about two for each 10°C rise.

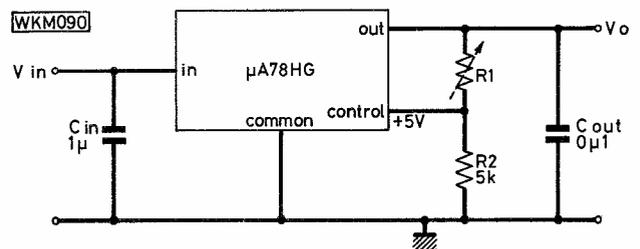


Fig. 2: A simple circuit using the μA78HG

The maximum permissible dissipation in the  $\mu A78HG$  is 50W, but this applies only when the case temperature is  $25^{\circ}C$ . At higher case temperatures the internal dissipation must be de-rated according to the graph shown in Fig. 3.

The size of the heatsink required depends on the internal thermal dissipation which in turn depends on the input voltage, output voltage and output current. The quiescent current is only 10mA, so the dissipation it produces is fairly small. The internal dissipation in watts will therefore be approximately equal to the output current multiplied by the difference between the input and output voltages.

To obtain an output voltage which can be varied over a wide range, a fairly high input voltage is necessary and the internal dissipation will be large if the output current is large. This requires a large heatsink. However, to maintain a fixed output voltage, the input voltage can be set at about 3.5 volts above this output voltage and the heat dissipated in the regulator device will then be much reduced.

The maximum value of the thermal resistance of the heatsink required may be estimated in the following way. The difference between the case temperature of the  $\mu A78HG$  (from Fig. 3) and the maximum room temperature is divided by the internal dissipation in watts. About  $0.2^{\circ}C/W$  is then deducted from the result to allow a safety factor.

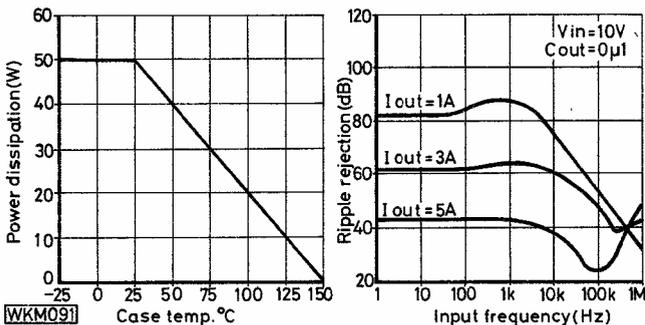


Fig. 3 (left): Maximum internal power dissipation in the  $\mu A78HG$ . Fig. 4 (right): Ripple rejection provided by the  $\mu A78HG$

The  $\mu A78HG$  contains a beryllium oxide substrate for efficient heat transfer. This material is extremely toxic, so it is very important to note that one must never cut open the case of this device. If one were to saw through the beryllium oxide, the toxic particles could enter the lungs.


### Performance

The line and load regulation are respectively the variation of the output voltage with the input voltage and with the output current; their values do not exceed 1% of the output voltage of the  $\mu A78HG$ .

The rejection of unwanted noise and ripple on the input power supply is quite high, as shown in Fig. 4 at various frequencies. The output noise voltage is typically  $50\mu V$  r.m.s. The output capacitor shown in Fig. 2 improves the transient response, whilst the input capacitor should be used if the regulator is located more than a short distance from the power supply reservoir capacitor. Solid tantalum capacitors are recommended for use in Fig. 2.

The  $\mu A78HG$  is available from Arrow Electronics Limited, Coptfold Road, Brentwood CM14 4BN.

## The ORMOND 5 VALVE PORTABLE SET

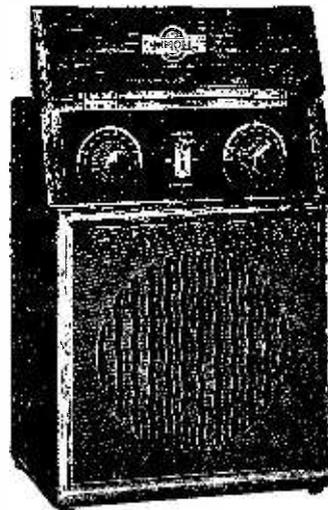

This set is ideal for indoor and outdoor use. It is contained in a Handsome Mahogany Cabinet, is extremely simple to control, and will render perfect reproduction under average conditions from a main B.B.C. Station within about 30 to 40 miles, and about 400 miles of Daventry.

A simple switch gives choice of short and long wavebands. Entirely self-contained and is fitted with a Celestion Loud Speaker. Complete with all Accessories and ready for immediate use.

Price £24 10 0  
Marconi Royalty extra £3 2 6

BAKELITE  
MOULDINGS  
Quotations given for Bakelite Mouldings of every description, for which enquiries—large and small—are invited.



In addition to the 5 valve Portable Set, Ormond Manufacture 2 and 3 valve Sets. Also, Condensers - Logarithmic S.L.F. Square Law. 2, 3 and 4 Gang Models, etc., etc.

199-205 PFINTONVILLE ROAD, KING'S CROSS, LONDON, N.1  
Telephone: Clerkenwell 9344-5-6. Telegrams: "Ormondengi, Kinicro-s."  
FACTORIES: WHISKIN ST. & HARDWICK ST., CLERKENWELL, E.C.1  
Continental Agents: Messrs. Pettigrew & Merriman Ltd., "Phonos House," 2 and 4, Bucknall Street, New Oxford Street, London, W.C.1


the hyperbole used by other firms, but perhaps explained by their not wishing to frighten-off timid constructors!

### Censorship

Lastly, now that permissiveness reigns, let us see what Sir John Reith wrote in 1928 about censorship: "The peculiar nature of Broadcasting . . . inevitably transfers the choice . . . from the listener himself to the broadcaster. The theatre manager, the editor, the preacher, deal each with his own public rather than with the public, and the . . . subject and opinions likely to be expressed is established by their assembling and buying. To impose limits upon the freedom of such publicists, therefore, is sheer censorship, to be justified or not as such. But the broadcaster's censorship, if it be fair to call it so, has a different basis. He has not to consider the willing but the unwilling audience, the people who if the matter were, say, performed in a hall would not be there. And he has further to consider that even for the same people, matter entirely proper in a hall or a newspaper may be in bad taste or even frankly objectionable in a family group. This is not Philistinism but common-sense." I don't think one needs to be too much of a Mary Whitehouse to concur with this statement, or even to wish that certain television producers would take note of it!


Our grateful thanks to the BBC for permission to reproduce the illustrations in this article

**SPECIAL  
PRODUCT  
REPORT**

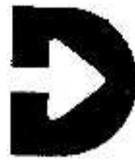

**DATONG  
ELECTRONICS  
LIMITED**

# ACTIVE ANTENNA MODEL AD170

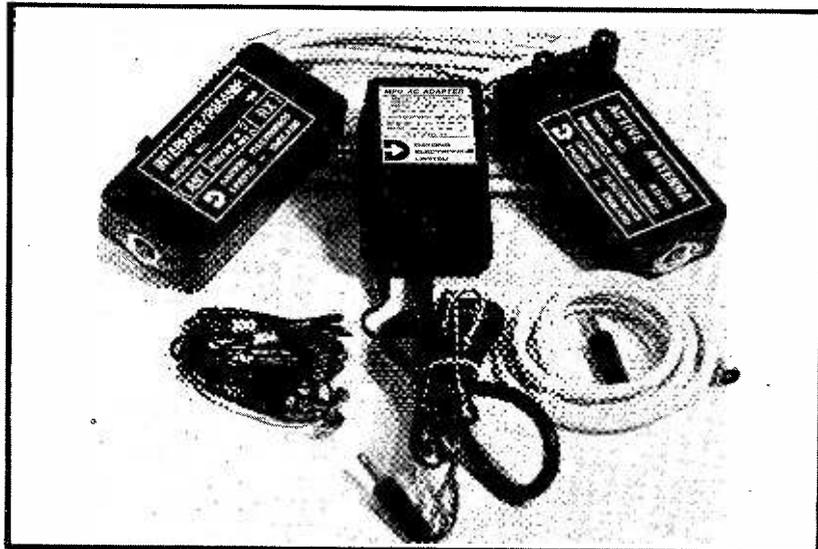

For those enthusiasts who enjoy the l.f. and h.f. bands an efficient antenna is a fundamental necessity and whilst many may dream about three-element beams on 120ft. towers, few will be fortunate enough to be able to obtain one. Some, such as those living in flats, may well be denied any outside wires at all and this group in particular should reap the greatest benefit from an active antenna.

The Datong AD170 Active Antenna is a matched set of modules which, when assembled, exhibits some of the characteristics of a full size half-wave dipole. The kit consists of a short wire dipole, each leg being connected to a high-impedance differential input amplifier whose output is arranged to match a low impedance feeder which carries the signals to the receiver. Some signal amplification is also achieved within this module.

A second "interface" unit mixes d.c. power with the r.f. output signal, which is fed via coaxial cable to the antenna module. Its power input is filtered to avoid interference pick-up and is also protected against a polarity reversal.

The Datong units are designed for indoor use and may be installed almost anywhere, an ideal position being the loft or similar high siting. Try to avoid places likely to be influenced by electrical noises, such as may be experienced from fluorescent lights. Remember also that water tanks, overflow pipes and so on will also affect the performance of any antenna.

The two wires from the head amplifier are stretched out and the ends attached to convenient fixing points (rafters, etc.) by non-conductive material—string, for example. For this purpose, two loops are provided. Optimum orientation of the dipole will depend on many factors, such as distance from the transmitter, mode of propagation, transmitter polarisation, time of day and operation frequency, so some experimentation is necessary. Vertical or near-vertical mounting is recommended for frequencies above 10MHz. This will give omnidirectional reception of ground waves (e.g. from l.f. stations) and of low-angle sky waves from DX

## ★ specification

**Frequency range:** 60kHz–70MHz

**Output impedance:** 50Ω

**Differential voltage gain of amplifier:** Unity

**Recommended dipole length:** 3m overall

**Third order intermodulation products:** typically –90dB relative to two output signals of 100mV e.m.f. (Equivalent to 100mV p.d. at the differential inputs)

**Second order intermodulation products:** typically –80dB relative to two output signals of 50mV e.m.f. (Equivalent to 50mV p.d. at the differential inputs)

**Current consumption:** 80mA

**Supply voltage:** 12V d.c. nominal

The Datong AD170 is supplied as a package containing the active aerial, the interface unit, 2 x 1.5m antenna wires, 1 x 4m jumper cable and a 3.5mm jack plug. The mains power unit shown in the photograph is an optional extra.

Price: Antenna £33.19 incl. VAT

Power Supply £6.19 incl. VAT

Both units (inclusive price) £37.13 incl. VAT

**Datong Electronics Ltd, Spence Mills, Mill Lane, Bramley, Leeds LS13 3HE Tel: 0532-552461**

stations. Reception of high-angle sky waves from medium distance stations will be relatively poor, however.

Horizontal mounting gives almost omni-directional reception of high-angle sky waves and directional reception of low-angle sky waves. In the latter case, maximum response will be obtained when the line of the dipole wires is perpendicular to the line between antenna and transmitter. Null responses occur in directions along the line of the wires and can be used to reduce local interference.

continued on page 62

# PRODUCTION LINES

alan martin


## Classic case

West Hyde Developments have recently introduced a new, versatile series of 45 different cases called the "Contil Classic II."

The main design feature of the cases is the extruded rail, which for the new Classic II has been extensively modified, giving much greater flexibility in use: The slot for the front and back panels is now stepped to give a choice of three different panel thicknesses and to allow for an added translucent panel. The screw groove has been altered to prevent thread stripping and more slots are provided for mounting a chassis or p.c.b. horizontally or vertically.

The case sizes have been carefully chosen to accept single or double Eurocards, which will fit horizontally across the "T" slots or slide vertically behind the front or back panels.

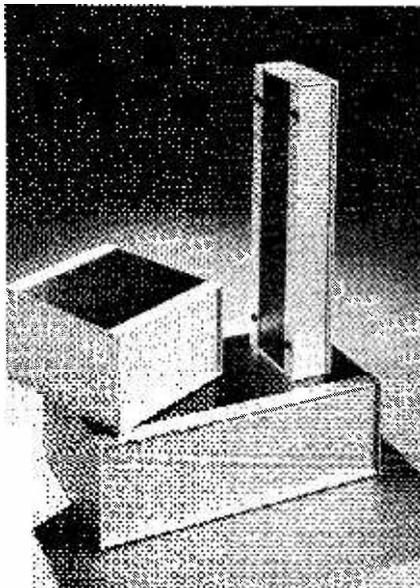The Contil Classic II is available in three widths, five heights and three depths and held in stock as component parts. For further information contact: *West Hyde Developments Ltd., Unit 9, Park Street Industrial Estate, Aylesbury, Bucks HP20 1ET. Tel: (0296) 20441/5*



## Simple wrapper

OK's new WSU-30M is about the size of a small screwdriver, but performs the complete wire-wrapping function. At one end it has a bit for making wire-wrapped terminal connections, in the middle a "no-nick" wire stripper and, at the other end, an unwrapping bit.

Designed for use with AWG30 (0.25mm) wire and 0.025in (0.63mm) square terminal posts, the all-metal tool produces a modified wrap which has a small amount of insulated wire

## If you please

Would readers kindly mention "Production Lines", when applying to manufacturers or suppliers featured on this page.

## Safety buzzer

Those who have ever had a freezer full of food ruined because the power to the unit has been accidentally switched off, or a fuse has blown, will be well aware of the value of the Buzz Plug recently introduced by Videotime Products.

Wired like an ordinary plug and looking not much larger, the Buzz Plug may be fitted as a direct replacement for a standard plug.

The slightly thicker top contains the circuit which continuously monitors the mains supply. Should the power fail the plug produces a loud instantaneous warning which will persist until some action is taken.

The plug is powered by a single inexpensive battery which will give up to 48 hours warning. Typical applications include use with freezers, fridges, incubators and equipment which must run constantly or would require recalibration. The RRP is £5.95, and is available from: *Videotime Products, 56 Queens Road, Basingstoke, Hants. Tel: (0256) 56417.*

around the terminal, in addition to the bare wire, to improve vibration resistance. The connection, which takes only seconds to make, is considerably stronger than solder, has excellent conductivity characteristics but can be quickly "undone" if necessary.

The WSU-30M is available at a VAT and carriage inclusive price of £5.64 from: *OK Machine & Tool (UK) Ltd., 48a The Avenue, Southampton, Hants SO1 2SY. Tel: (0703) 38966/7.*

# PRODUCTION LINES

alan martin

## A better 555

Rapid Recall Ltd. are now distributing to retailers the ICM7555 and 7556 timers, which provide a significantly improved performance over the standard SE/NE555/6 and 355 timers and are direct replacements for these devices in most applications.

The devices are manufactured by Intersil using a low-power CMOS process and will provide time delays from a few microseconds to several hours.

Operating from any d.c. power source within the range of 2V to 18V, and consuming only 80µA (typical), the ICM7555 or the ICM7556 (160µA) can be used without the special decoupling arrangements which are mandatory with standard 555 devices.

This is because the 7555/6 creates switching spikes on the power rail of only 2 or 3mA compared with 200 to 300mA with standard devices. Also, because the CMOS comparators on the chip possess a very high impedance, control voltage decoupling capacitors are unnecessary. Therefore, in many applications the two or three capacitors needed with the 555/6 are not needed with the 7555/6.

For details of availability and price contact: *Watford Electronics, 33/35 Cardiff Road, Watford, Herts. Tel: (0923) 40588/9.*

## Display bezel

Newly-available from Vero Electronics, is a moulded "display bezel AB064" in


two sizes to attractively frame and highlight a display and at the same time cover unsightly tool marks around a panel cut-out.

Designed to fit into a single rectangular cut-out, the bezel is positioned in the cut-out by four removable location pegs, and firmly secured by two moulded-in screwed studs which also secure the display mounting board on spacers provided.

A choice of lenses are offered—neutral, red and clear, polarised or unpolarised and a full range of compatible mounting boards for both i.e.d. and l.c.d. displays is available.

Prices range from £1.50, for a 4-digit bezel with clear lens, to £2.65 for a 6-digit bezel with coloured lens.

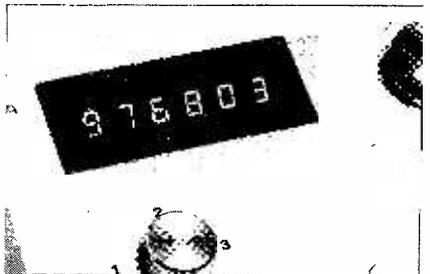Further details from: *Vero Electronics Ltd., Industrial Estate, Chandler's Ford, Eastleigh, Hants SO5 3ZR. Tel: (04215) 69911.*



## DATONG ACTIVE ANTENNA

continued from page 60

The AD170 has a frequency range of 60kHz to 70MHz. On "medium" and "long" waves there are many strong stations which call for a very good intermodulation performance from a unit such as this. At -80dB on second-order products and -90dB on third-order products the Datong antenna fulfils this requirement admirably.

The interface unit previously referred to contains a switchable amplifier of 12dB gain which will help compensate for the poorer h.f. performance of some older receivers, but is not essential if the unit is to be used with more modern equipment. It is, however, very convenient to have a couple of S-points extra gain available when required to winkle out that elusive DX station.

On test, the AD170 gave very impressive results. It should be fully-understood, however, that the level of signal at the receiver will only compare with that from a full-size dipole at frequencies of about 16MHz, appearing to be about one S-point better at 30MHz.

Below 16MHz the "gain" relative to a full-size resonant half-wave dipole falls at approximately 6dB per octave and at 2MHz will be three S-points down on a 75 metre passive dipole. However, this may not be as dramatic as may first appear, because at 2MHz the level of signal received on a full-sized dipole is considerable, as is the noise level. The active antenna worked quite satisfactorily at these frequencies and its all-important signal-to-noise ratio was at worst equal to and in many cases better than the full-size dipole against which comparisons were made.

Peter Preston

## BINDERS FOR PW

Keep your copies together  
Keep them clean  
with the  
PW Easi-Binder

*The Easi-Binder is attractively bound with the title blocked in gold on the spine with the current (or last) volume number and year. For any previous volume numbers please advise year and volume and a separate set of gold transfer figures will be supplied.*

*£2.85 inclusive of VAT and post and packaging from: Post Sales Department, IPC Magazines Ltd., Lavington House, 25 Lavington Street, London, SE1 0PF.*

*(Overseas orders please add 60p).*



**by Eric Dowdeswell G4AR**

An oft-repeated complaint by readers of this column concerns interference on the amateur bands, generally between amateur stations, but frequently from other services. It is often assumed that the amateur bands are exclusive allocations, but a look at the allotments will show that sharing with other services is not uncommon. The 80m band is a typical example.

Such QRM can be the making or breaking of a newcomer to the amateur bands, especially if the equipment in use is relatively simple or unsuitable, which is frequently the case. I would say from my correspondence that about 50 per cent of budding amateurs buy equipment on the strength of ads in the popular press, instead of seeking advice from those having some experience of amateur radio.

All too often, sums of well over £100 are spent on receivers claimed to be able to "get the world", on a telescopic aerial! "Listen to the amateurs" they say, about a receiver that does not have a b.f.o., when the vast majority of amateurs today use single-sideband on our h.f. bands, necessitating the use of a b.f.o. "Eavesdrop on the aircraft bands, the police, the taxis etc.," is quite common, all of which is illegal in this country, but it sounds good in advertising.

So my advice must be to contact another person before buying a receiver for use either on the amateur bands or

for general s.w. listening. Avoid also the sets that claim to cover the long-wave band through to the v.h.f. or even u.h.f. bands! There are few, if any, sets that can do this efficiently over such a wide range of frequencies. Get a good communications set for the h.f. bands and use its facilities in conjunction with a converter for the v.h.f. and u.h.f. bands. There must be another amateur not too far away, or a radio club of some kind, where you can seek advice on buying a set. An intelligent look at the advertising in magazines devoted to amateur radio is as good a start as any.

A good secondhand receiver is not to be despised, can be quite cheap, and can always be sold or swapped for another set if it is not up to expectations. Old valved sets, especially those with i.f. filters intended for use on s.s.b., can frequently out-perform many solid-state receivers under the conditions of interference that prevail on some amateur bands. They are virtually free of the bugbear of most transistorised sets, cross-modulation, where signals which are on adjacent channels, or even far apart in terms of frequency, inter-modulate giving the effect of interference on the desired signal. It is frequently almost impossible to convince a listener that the interfering station is not on an adjacent channel! Turning down the r.f. gain can usually prove the point.

## What's on the Bands

From Marple, near Stockport, **John and Steven Goodier** used their FRG-7 and 30ft wire to log J6LFU, a new prefix for St. Lucia, previously VP2L, plus suffix. On 20m s.s.b. FW0TT on Wallis Is. was a good find as well as JX9WT, much nearer home on Jan Mayen but still quite rare. S8AAT is another unusual prefix, this time for the Transkei while D68AD in the Comoro Is. is not heard all that often.

School work doesn't prevent **Ian Marquis** BRS41426 in Leigh-on-Sea, Essex, from digging out some goodies with his FRG-7, such as EA8CR and VO1HP on 160m c.w., FP8, HR3, TI5, 6W8 and 9K2 on 80m s.s.b. in spite of the rising sunspot number, or is it? **David Palmer** writes for the first time from Stowmarket, Suffolk, with a goodly selection of DX heard on his Trio JR310 with indoor dipoles for 10, 15 and 20m, and a 100ft wire for the l.f. bands, plus an a.t.u. I have suggested that David tries the wire on the h.f. bands, too, if he hasn't already done so. He found 10m quite good with prefixes like C5, DU1, HH2, H44, J28 and 6W8. David's two precepts for good DX are, getting on at the right time, and skill in operating the receiver. *D'accord!*

Finally, some more grist for the June DX mill, says **Bill Rendell** in Truro, Cornwall. He's been trying his h.f. dipoles as centre-fed "T"s on 80m using an a.t.u., as well

Reports on the various bands are welcome and should be sent direct, by the 15th of the month, to:

**AMATEUR BANDS** Eric Dowdeswell G4AR, Silver Firs, Leatherhead Road, Ashted, Surrey KT21 2TW. Logs by bands, each in alphabetical order.

**MEDIUM and SW BANDS** Charles Molloy G8BUS, 132 Segars Lane, Southport PR8 3JG. Reports for both bands **must** be kept separate.

**VHF BANDS** Ron Ham BRS15744, Faraday, Greyfriars, Storrington, Sussex RH20 4HE.

as on the design frequencies of 20 and 15m. Bill's still hankering after a new set to replace his beloved Heathkit AR3, but so far an AR88 in the pipeline has been vetoed by the XYL! The QTH of AA6AA turned out to be Los Angeles much to Bill's disappointment as did KG4W in Virginia. However, he did manage three ZLs on the same band, 80m, while on 20m VK2AGT on Lord Howe Is. was some compensation. VP8SO seems to be a new one on from Signy Is. with QSLs via G3KTJ, S79MC is still a mystery to Bill, and me, so if anyone can enlighten us please do so. Could it be old timer VS5MC?

## The Month's Mail

**Andrew Smith** in Glasgow admits to being just a beginner but is lucky to be off the mark with an FRG-7 and Joystick aerial and a.t.u. He thought of contacting someone else in his area who might also just be starting, but my advice in such a case is to find the local radio society or group and get among the experienced amateurs and listeners who will be only too willing to assist. G4HWB hides the identity of **Mike Stollov** of Blackley, near Manchester, who complains that although modern technology has given him colour TV and non-stick frying pans it hasn't indicated how he can pay for all the modern amateur radio gear!

However, he has an FRG-7, and being keen on c.w. he ought not to have much trouble getting hold of one of the older c.w. rigs such as the LG300 for next to nothing. Another recruit from the BC bands is **Martin Gill** (Kirkby Lonsdale, Cumbria) who has been active on 10, 15 and 20m with a Barlow-Wadley XCR30 and logged 67 countries in four months. **David Wyatt** a 14-year-old from Oswestry, Salop, is starting to copy c.w. on his BC348 and queries a few prefixes. I can only advise, as I do most months, buying Geoff Watt's prefix list for the grand sum of 45p from 62 Belmore Road, Norwich. His weekly news sheet is also good value for those keen on keeping up with the latest DX news.

A note of warning for owners of Realistic DX160 receivers comes from **D. Dempster** of Birmingham, who points out that the set's on-off switch only cuts the internal low-voltage supply and not the mains supply in the conventional manner. The set is therefore always live, which could be dangerous if one is poking around inside believing the mains is switched off. **W. Semmens**, writing from Penzance, Cornwall, says that he is handicapped but very keen to take up amateur radio, if he had a receiver, so if anyone in his area can help with a secondhand set at a reasonable price please let me know.

The above note on the DX160 should be of interest to **P. C. Hawkes** who uses his with a 100ft wire. A beginner of only a few months, P.C.H. has been disappointed at not finding a radio amateur's map of the world at his local bookshops. Only source for these are the RSGB and *Short Wave Magazine*, and to be of any use such maps must be on a great-circle projection which gives true direction, so important when used with rotary beams. Incidentally P.C.H. sold part of a stamp collection to take up our hobby, but I can assure him he will never be disappointed with his choice.

After five years of studying electronics **Phil Charlesworth**, now BRS41107, in Southport, went to a mobile rally with G8EFQ and fell for amateur radio. He passed the RAE last December and is going all out on his code before getting his G4+3. He even threatens to send in some c.w. logs! **Alan Billington** is very lucky indeed, as his Dad is teaching him the code and he sits the RAE in May, Alan, that is! He is only 16 and has a Lafayette HA350 plus 80ft aerial and homebrew a.t.u. Alan is BRS40845

and wonders if there are any other SWLs in Morecambe, Lancs.

**John Cassidy** of Shanklin, IOW, is 13 and recently bought a five-valve set from AH Supplies of Sheffield, and wonders if any reader has a circuit diagram. He'd also like to get hold of a pair of 4kΩ headphones (so would I!) at a reasonable price. John lives at 15 Sibden Road if anyone can help. Some comments on the National DR2800 mentioned in the April column, from **John Gomer** (Colchester). He had one but swapped it for a Hammarlund SP600JX which sounds like a good swap to me. He heard subsequently that the 2800 was traded for a VW Beetle! John is dedicating a couple of nights a week for RAE study so good luck OM.

## News from the Clubs

Editor of *SWM*, G3KFE, will be talking to the **West Kent ARS** on making homebrew equipment on Friday May 25 at the Adult Education Centre, Monson Road, Tunbridge Wells where meetings are held fortnightly. Alternate Tuesdays for informal meetings, Morse practice and chat at the Drill Hall, Victoria Road. **Bury RS** (G3BRS) will benefit from a chat on modifying Pye gear by G8EUM on May 8 at Mosses Centre, Cecil St., Bury, and every Tuesday evening. Contact: G4GSY at 7 Rothbury Close, Ainsworth Road, Bury, or ring 061-761 5083.

**Stevenage & District ARS** normally meet first and third Thursdays but contact Trevor G8KMV, 11 The Dell, Stevenage for details of the 2m DF Hunt on May 10, or ring 0438 54689. An anonymous secretary has sent details of the **Loughor Amateur Radio & Electronics Club** operating near Swansea. Only formed late last year the club is looking for more members so ring said Sec on 0792 893392.

A little detective work on the **Crawley ARC** (W. Sussex) Newsletter reveals that it meets on the last Wednesday of the month with informal gatherings at a member's QTH on the second Wednesday. Formal meetings at Trinity United Reformed Church Hall, Ifield Drive, Ifield but write to "Dot and Vernon" G3MER and G3MSK respectively for details of club activity, at 16 Newmarket Road, Crawley, W. Sussex.

Don't forget, letters and logs by 15th of the month and don't miss the RSGB's Exhibition at Alexandra Palace on May 11 and 12.

## Log Extracts

**M. Gill:—20m** HS1WR VU2JNA VP2LFZ TU2HS  
15m ZP5LN HC7DR 10m FM7WY ZP5CDE YS9RE

**R. Bell:—20m** HC9CB HP7OP VP2MFO YA3DM  
YB61B 15m TR8AC 10m CX8CN JR2LDM

**W. Rendell:—80m** CO2JA CT2SH (QSL W3HMK)  
HR0QL KG4W PJ2FR VP2SK XE1OW YV5ANS  
ZL2BT/ZL4AP 20m C5AAL CT2YB HS1ABD  
TU2AE VK2AGT (Lord Howe Is.) VK7AE VP2MF  
VP8SO 15m CT2CP C6ANU D4CBS HK3AXT  
J3AAE S79MC TG5WQ

**D. Palmer:—15m** C5ABK J28AY VQ9MR YB0WR  
10m C5AAP HH2PW HR0QL H44JD J28AG TA1MB  
VS6EZ YB0TZ YS9RVE 6W8DY 7Z2AP

**J. & S. Goodier:—20m** FW0TT JX9WT J6LFU  
KA1MI S8AAT 5U7AG 15m D68AD VP2AC  
9Y4TRV 10m C5AAP ZE2JK

**I. Marquis:—80m** CT2SH VE3BWK/4U 20m  
VP8SO ZD7PL 4S7DJ 5U7AG 15m FC9VN FG7AX  
HR0QL VP2LFZ 6W8DY

All above loggings were on s.s.b.



## MEDIUM WAVE DX

by Charles Molloy G8BUS

While tuning round the medium waves recently, I was intrigued by the number of 1kHz heterodynes that could be heard. A quick check brought a surprising total of 33, some quite strong, which indicates in each case there was a station still working on the old pre-Geneva frequency, 1kHz below the correct channel. If two stations are operating 1kHz apart then they will interfere with each other, and the difference in frequency between them will appear as a 1kHz audio tone at the loudspeaker.

A note over Sweden Calling DXers shed some light on the problem when it was stated that a number of countries have not (yet?) adopted the Geneva plan. Algeria, Iraq, Jordan, Lebanon, Libya and Tunisia it was claimed had not changed over at all, while several others in the same area have altered only a few of their transmitters. Algeria is still on 251kHz on the long-waves, while 520kHz now appears to be an out-of-band frequency at the l.f. end of the medium waves, inhabited by low-power Austrian and German stations.

## Heterodynes and DXing

Although a heterodyne is usually associated with a frequency difference between two signals that is at least great enough to generate an audible note, it is possible to have a sub-audio heterodyne. These are called "beats". A beat is generated when two stations, nominally on the same frequency, are separated by only a few hertz, which is usually the case when two signals are not synchronised. This is of particular interest to the DXer, as the beat will show up on the "S" meter. Even a weak station swamped by a much stronger one on the same channel will produce a beat strong enough to be indicated on the "S" meter and thus reveal its presence to the DXer. If you come across such a beat then stay on the frequency for a few minutes. DX on the medium waves is usually subjected to slow cyclic fading, so the strong station may fade and the weak one may increase in strength and even become dominant for a short while. I have often picked up interesting DX just by sitting on a channel that has a strong signal with a beat.

## West African DX

Sunset along the West African coast occurs at much the same hour as in the UK, which makes this part of the world attractive to anyone who would like to DX during a summer's evening. Since the DX is coming from the south and any interference will most likely be from other directions, a loop will be useful in getting rid of unwanted co-channel interference.

Radio Las Palmas in the Canary Islands is now conspicuous, in Spanish, on 1008kHz after Lopik in Holland signs-off. The Radio Nacional España outlet in Tenerife can be heard with the call "Centro Emisor del Atlantico" on 621kHz, but there will be QRM from Batra

in Egypt which a loop should be able to deal with. Brussels, which is on the same frequency, signs-off at 2245. Radio Dakar in Senegal shares 765kHz with Sottens in Switzerland and it is often heard in the UK with African music and French announcements. Conakry in Guinea is a regular on 1404kHz with the call "La voix de la Revolution," and it is difficult to miss it after 2300 when the France Cultur network on the same channel goes off for the night. Bissau, located in Guinea-Bissau, is now on 1071kHz and the time to look for this one is after 2100 when the France Inter network closes down.

## World Radio and TV Handbook

The 1979 edition of this handbook is now available and it contains the latest changes on the medium and long waves. As well as listing the stations authorised under the Geneva Plan, it also indicates those that are not yet on the air, or are operating with less than maximum power. This is the only up-to-date list of medium- and long-wave stations that is available at the time of writing. The *WRTVH* contains all sorts of information that is useful to the DXer including station addresses, schedules, and details of interval signals from broadcasters in every country in the world, and it covers the long, medium, short, v.h.f. and TV bands. The 1979 edition costs £8.50. It is published by Billboard, distributed in the UK by Argus Books, 14 St James Rd, Watford, Herts and it can be ordered through bookshops.

## WARC 1979

These initials stand for the World Administrative Radio Conference, which is due to be held in Geneva in September this year. This conference is concerned with the allocation of frequencies to different users, and when I wrote about its possible effects on s.w. broadcasting last month, it did not occur to me that the conference would concern itself with the medium waves. There is, however, a proposal to the conference from the US Government, that the medium waves should be extended to 1860kHz in Region 2, which covers North, Central and South America.

Radio amateurs will be far from happy at the prospect of having broadcasting in the lower 60kHz of the 160m band, and one can only hope that this part of the proposal is not implemented. The US intention is to use the extended part of the band to provide another 14 channels which would be occupied by 700 low-power local stations. Each would become what is known as a graveyard channel, like 1230, 1240, 1340, 1480 and 1490kHz are at the moment. These frequencies are the resting place for hundreds of stations with powers of 500 watts or less, some of which operate during the daytime only.

It is hard to predict what DXing among these new channels would be like, but experience of existing graveyarders indicates that some interesting and unpredictable results can be expected.

## Readers' Letters

"Perhaps the internal ferrite rod interferes," writes **D. R. A. Lowe** from Lichfield, who has been trying to use a m.w. loop with a Philips 543A receiver. He found that the loop exhibited no directional properties. Yes, this is what is wrong. The receiver is picking up signals from the internal ferrite rod aerial at the same time that the loop is trying to null-out this signal. You should only connect a loop to a receiver that does not have an internal aerial, and preferably a receiver that is well screened in a metal

cabinet, so that the receiver wiring does not act as an aerial. It is easy to test the receiver. Unplug the loop and the receiver should now be dead.

A similar problem comes from **Roy Haynes** who has been trying a loop with his Realistic DX160 and cannot get directional reception. Unplug the loop and see if the receiver still picks up the station you are trying to null-out. If it does then the loop is OK and it is the receiver that is causing the problem. Some versions of the DX160 are fitted with a ferrite rod aerial for m.w. reception, and this will have to be disconnected before a loop can be used with it. The ferrite rod should be fitted at the back, externally to the metal cabinet.

**Chris Constantinides** would like to listen to any of the Greek medium-wave stations and wonders if he should swap his DX160 for a better receiver. A more selective receiver will not help Chris, as the interference you are experiencing comes from stations operating on the same frequency as the signals you are trying to pick up. Try a m.w. loop along with your DX160, making sure that the latter does not have an aerial of its own. Don't be optimistic about obtaining regular reception from Greece on the m.w.s as there is a lot of co-channel interference to overcome.

Athens is now on 729kHz and signs-off at 2300. The power is 150kW but there is high-power interference from Egypt, USSR and Finland, and also from stations in East Germany and Spain. Similarly with the main Yened outlet which is on 981kHz with 200kW, there is QRM from Algeria, Bulgaria, Cyprus and Sweden. The best time to listen to the Eastern Mediterranean is from 0400 onwards when, owing to the different time zones, stations in that area are signing-on while those further west are still off for the night.

## DX Heard

Using a DX160, 90ft long wire, a.t.u. and pre-amp **K. Lewis** (Pensilva, Cornwall) pulled in Radio Margarita, Venezuela on 1020kHz, WINS New York on 1010, Radio Coro Venezuela on 1210 and Radio Paradise, St Kitts 1265, all heard between 0145 and 0330 in mid-March. Listen at this time of the year for North America and the Caribbean during the hour before sunrise. Reception is often good and QRM is light.



## SHORT-WAVE BROADCASTS

by **Charles Molloy G8BUS**

A three-transistor receiver is in use at Fareham by **Simon Pegler**, who finds he gets improved reception if he unplugs the aerial from the receiver and runs the aerial lead close to a piece of wire which is plugged into the aerial socket. Similar results would be obtained by fitting a low-value fixed capacitor in series with the aerial. **Peter Simms** has a similar problem with his 9-valve, semi-vintage domestic receiver, which he uses with a 40ft inverted "L" aerial.

This set-up works well on some bands but not on others: "It picks up very little and selectivity becomes poor. This does not happen if I use short lengths of wire . . ."

It is possible to electrically shorten an aerial by inserting a capacitor between the aerial and the receiver. A variable capacitor with a maximum value of about 50pF will do the trick on the main short-wave bands. This dodge is as old as radio itself and it was once the subject of a patent held, I believe, by Scott Taggart who designed the famous ST series of receivers. A long aerial picks up a lot of signal which is useful when you are listening to a weak station, but it can cause receiver overloading with strong signals, as well as damping the receiver input tuned circuits as in the two cases quoted above. A capacitor in series with the aerial will be found beneficial with many sets.

## Tropical Bands

Some very good DX has been reported on the Tropical Bands recently. **Bob Bell** (Blyth) used an FRG-7, a.t.u. and a vertical aerial to pull in Radio Nepal at Katmandu on 3425kHz in the 90m band at 0030, Radio Bolivar Venezuela 4770kHz (60m) at 0100, Radio Tallin in English on 4860 at 0105, Radio Naçional Luanda 4820 at 0120, Dacca in Bangladesh 4790 at 2050, Radio RSA 4875 at 2350 with sign-off, Gansu in China on 4865 at 2155 in Chinese with jamming, an unidentified station in Arabic on 4845 at 2215, Alma Ata on 5035 at 2205 in Chinese, and Ashkhabad on 4895 at 2350.

From Pensilva in Cornwall, **K. Lewis** reports hearing Radio Guatapuri in Colombia on 4817kHz at 0535 and Radio Garoua in Cameroon on 5010 at 1840 in English, the receiver being a DX160. **Peter Ramsey** (Ayrshire) used an AR88 and a loft aerial to pull in Radio Singapore on 5010 at 0315, Tegucigalpa Honduras on 4820 at 0330 and Lagos, Nigeria on 4990 at 0440. **David Wyatt** (BC348) heard Radio Reloj in Costa Rica on 4832 at 0755, Nouakchott in Mauretania on 4845 at 2305, Cotonou Benin on 4870 at 0550, Radio Rumbos (Villa de Cora) in Venezuela on 4970 at 0625, Radio Colosal (Neiva) Colombia on 4945 plus two he could not identify—Radio Superas on 4879 (R: Super at Medellin Colombia is on 4870) and Radio Cosanti on 4950 (anyone any ideas?).

DXers who have not tried the Tropical Bands should study the above carefully as it is representative of what can be heard. Listen after dark during the summer for African stations and throughout the night for Latin Americans.

## "Long Live Short-Wave"

This is the title of an album (12 inch LP) issued by the well-known songwriter and record producer Mitch Murray. Mitch, who is a keen DXer himself, is the narrator who in the space of an hour, guides the listener through just about every aspect of DXing. One advantage of this type of presentation is that the audience can actually hear what it is all about, whether it is a signal from a satellite, WWVH in Hawaii, or QRM such as facsimile or Teletype. Station announcements and interval signals from a number of stations, some everyday and some exotic, are presented and I must admit there were a couple that were new to me. A few words from Henry Hatch of the BBC World Radio Club are included.

The album, which is advertised on page 159 of the 1979 *World Radio and TV Handbook* is accompanied by an explanatory booklet. It is available from Trans-Island Productions, PO Box 24, Douglas, Isle of Man, either as a record or cassette for £3.50, post paid. It should provide a

**QUARTZ LCD  
5 Function**

Hours, mins., secs., month, date, auto calendar, back-light, quality metal bracelet.

**£6.65**

Guaranteed same day despatch.  
Very slim, only 6mm thick.



M1

**QUARTZ LCD  
7 Function**

Hours, mins., secs., month, date, auto calendar, back-light, seconds STOPWATCH.

**£9.65**

Guaranteed same day despatch.  
Very slim, only 6mm thick.



M2

**QUARTZ LCD  
11 Function SLIM CHRONO**

6 digit, 11 functions. Hours, mins., secs., day, date, day of week. 1/100th, 1/10th, secs., 10X secs., mins. Split and lap modes. Back-light, auto calendar. Only 8mm thick. Stainless steel bracelet and back. Adjustable bracelet. Metac Price

**£12.65** Thousands sold!

Guaranteed same day despatch.



M3

**QUARTZ LCD  
ALARM 6 Function**

Hours, mins., secs., month, date, back-light, 24 hour ALARM. Adjustable stainless steel bracelet. Only 9mm thick.

**£12.65**

Guaranteed same day despatch.



M4

**QUARTZ LCD  
ALARM 7 Function**

Hours, mins., secs., day, date, alpha day, back-light, auto calendar. Adjustable stainless steel bracelet. Only 9mm thick.

**£17.65**

Guaranteed same day despatch.



M5

**QUARTZ LCD Alarm  
Chronograph with Dual  
Time Zone Facility**

Constant LCD display of hours and minutes, plus optional seconds or date display, plus day of the week and am/pm indication. Perpetual calendar, day, date, month and year. 24 hour alarm with on/off indication. 1/10 second chronograph measuring net, lap and first and second place times. Dual time zone facility night light. Only 9mm thick.

**£22.65**



M6

**SOLAR QUARTZ LCD  
Chronograph with Alarm  
Time Zone Facility**

Constant LCD display of hours and minutes, plus optional seconds or date display, plus day of the week and am/pm indication. Perpetual calendar, day, date, month and year. 24 hour alarm with on/off indication. 1/10 second chronograph measuring net, lap and first and second place times. Dual time zone facility night light. Only 9mm thick.

**£25.65**



M7

**QUARTZ LCD  
Alarm Chrono**

22 function, 6 digit. Hours, mins., secs., date, day of week, stopwatch, split time, alarm, second watch (dual time), back-light. FRONT BUTTON OPERATION.

**£22.65**

Guaranteed same day despatch.

METAC PRICE



M8

**SOLAR QUARTZ LCD  
Chronograph**

6 digit, 11 function. Hours, mins., secs. 1/100, 1/10 secs., mins. Split and lap modules. Auto calendar and back light. Powered from solar panel with battery back-up.

**£13.95**

M9



**SEIKO Alarm Chrono**

LCD, hours, mins., secs., day of week, month, day and date, 24 hour Alarm, 12 hour chronograph, 1/10th secs., and lap time. Back light, stainless steel, HARDLEX glass. List Price £130.00

METAC PRICE

**£105.00**



M10

**SEIKO Chronograph**

LCD, hours, mins., secs., day of week, month, day, date, 12 hour chronograph, 1/10th secs. and lap-time. Back light, stainless steel water resistant, HARDLEX glass.

List Price £85.00

METAC PRICE

**£68.00**



M11

**SOLAR QUARTZ LCD  
5 Function**

Genuine Solar Solar panel with battery back-up. Back light and auto calendar. Hours, mins., secs., day, date. Quality metal bracelet.

**£8.95**

Guaranteed same day despatch.



M12

**HANIMEX  
Electronic  
LED Alarm Clock**



Features and Specification: Hour/minute display. Large LED display with p.m. and alarm on indicator. 24 Hours alarm with on/off control. Display flashing for power loss indication. Repeatable 9-minute snooze. Display bright/dim modes control. Size: 5.15" x 3.93" x 2.36" (131mm x 111mm x 60mm). Weight: 1.43 lbs (0.65 kg). AC power 220V.

**£8.65** Thousands sold!

Guaranteed same day despatch.

M13

**QUARTZ LCD  
Ladies Slim Bracelet**

5 function. Hours, mins., secs., day, date and back light and auto calendar. Elegant metal bracelet in silver or gold. State preference.

**£15.95**

Guaranteed same day despatch.



M14

**QUARTZ LCD  
Ladies 5 Function**

Only 25 x 20mm and 6mm thick. 5 function. Hours, mins., secs., day, date and back light and auto calendar. Elegant metal bracelet in silver or gold. State preference.

**£9.95**

Guaranteed same day despatch.



M15

**DIGITAL  
LED CLOCK**



Automatic brightness control. Weekend alarm cancel.

Features and Specification: Hour/minute display. Large LED display with p.m. and alarm on indicator. 24 Hours alarm with on/off control. Display flashing for power loss indicator. Repeatable 9-minute snooze. Automatic brightness control. Weekend alarm cancel.

**£10.95**

Guaranteed same day despatch.

M16

**HOW TO ORDER**

Payment can be made by sending cheque, postal order, Barclay, Access or American Express card numbers. Write your name, address and the order details clearly, enclose 30p for post and packing or the amount stated. We do not wait to clear your cheque before sending the goods so this will not delay delivery. All products carry 1 year guarantee and full money back 10 day reassurance. Battery fitting service is available at our shops. All prices include VAT.

Trade enquiries: Send for a complete list of trade prices - minimum order value £100. Telephone Orders: Credit card customers can telephone orders direct to Daventry or Edgware Rd., 24 hour phone service at both shops: 01-723 4753 03272-76545.



CALLERS WELCOME  
Shops open 9.30 - 6.00.

**Metac**

ELECTRONICS  
& TIME CENTRES

North & Midlands  
67 High Street, DAVENTRY  
Northamptonshire  
Telephone: 03272 76545

South of England  
327 Edgware Road  
LONDON W.2  
Telephone: (01) 723 4753

novel introduction to the hobby for the newcomer as well as being of interest to many old hands like myself.

## Frequency Standard and Time Signal Stations

Fourteen-year-old David Wyatt (Oswestry) got hold of a BC348 surplus receiver which was made in 1942, and is the type that was used in the wartime Flying Fortress. When used with a 90ft long wire, it pulled in IBF in Turin, Italy on 5MHz at 0700 with identification in Italian and English plus IBF in Morse, VNG Lyndhurst, Australia on 12MHz at 0915 and WWV Fort Collins USA on 10MHz at 0955. David finds these frequency standard stations useful to check the calibration of his receiver. This is, of course, one of the reasons why these stations are on the air. Others that are logged now and again (I nearly said from time to time) are Podebrady, Czechoslovakia 3170kHz, BPV Shanghai and JJY Tokyo on 10MHz, CHU in Ottawa on 14 670kHz, RWM Moscow and WWVH Hawaii on 15MHz.

## Readers' Letters

Fourteen-year-old Alistair Dupres (Cardiff) has made a good start with DXing by logging Radio Japan on 15 195kHz at 2200, using his Vega Selena MB 210/2 with telescopic aerial; their address is 2-2-1 Jinnan, Shibuya-Ku, Tokyo. Alistair asks: "what is a QSL card?" A QSL card is a colourful picture postcard, or a card with an artistic design, that a station will send to a listener in return for a reception report. See the front cover of the August 1978 issue of *PW* and my article on QSLs in the same issue. The card will usually have the station callsign or slogan printed on it together with the verification details that will confirm that the DXer actually heard the station.


A Hitachi Radio Cassette Type TRK5320E with telescopic aerial is in use by P. W. Oliver of Paisley, who wonders if he would get improved reception by joining an additional aerial to the telescopic one. I would not recommend it as you may get overloading. A series capacitor will help, but I like the method suggested by Mitch Murray in *Long Live Short-Wave*, which is to wrap a piece of insulated wire round the whip aerial without making direct contact with it. Then join your aerial to one end of this piece of wire, the degree of coupling being adjusted by altering the number of turns.

"What is a mechanical filter?" asks Michael Welsh, who is thinking of investing in a Collins R390A which possesses "mechanical intermediate frequency filters for selectivity." It is an electromechanical device which replaces an i.f. transformer. It will give results equal to, if not better than a crystal filter, and its main advantage is the steep sides of the reponse curve. A mechanical filter should not be confused with a ceramic filter which gives results similar to an i.f. transformer. Since the ceramic filter does not require adjustment it has advantages from the manufacturer's viewpoint and they are now widely used for domestic receivers.

Ian McLean has a Pye Cambridge R35 and he wonders if anyone could put an age to it. Replies direct to Ian at 46 Golf Drive, Port Glasgow, Scotland. Used with a PR40 preselector and 50ft long wire this receiver pulled in Radio Australia on 17 785kHz at 0306 and Radio Pakistan in English on 17 890 at 0245, both in the 16m band. Derek Vivian would like to contact any reader who has fitted an "S" meter to the CR100 and his address is 9 Dymock House, 19 Malden Rd, Wallington, Surrey.

Radio Tinian crops up again with a suggestion from Dr S. K. Kellet Smith (Guernsey) that this station might be

located on an island called Tinian in the Marianas Group in the SW Pacific (Micronesia). This would really be DX! Unfortunately, broadcasting in this area (according to the *WRTVH*) is on the medium waves and v.h.f., neither of them being likely to be heard in the UK. Dr Kellet Smith, who is now retired, has a Sanyo RP990 with telescopic aerial which pulled in Australia on 11 855kHz after midnight for him. Receiver trouble is being experienced by 15-year-old Julien Smith who has a Philips 341A which has blown a valve and also a new replacement. Julien lives at 48 Seafeld Close, Seaford, Sussex, and help from anyone in his area would be appreciated as he is currently "off the air". Neil Devlin writes from Dundee to say that his Ferguson 5-valve domestic receiver and 60ft long wire pulled in Vietnam on 12 035 at 2115, Iran on 9022 at 1705 (out-of-band) and Radio Yugoslavia on 9620 at 2202 and Radio Australia on 6005 at 1705.

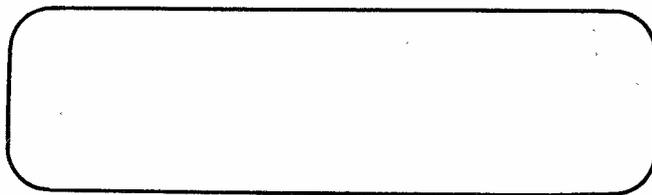

**by Ron Ham BRS15744**

I always enjoy attending the RSGB's annual VHF Convention and this year's event, held on March 10, at the Winning Post Hotel, Whitton, was no exception mainly because it is a wonderful opportunity to meet many of our readers and to feel the pulse of the current v.h.f. affairs.

## Sudden Ionospheric Disturbance

Soon after I arrived at Whitton, Mark Deutsch G3VJG, told me about the Sudden Ionospheric Disturbance which occurred between 1035 and 1142 on March 9. Shortly afterwards I met Charlie Newton G2FKZ, with the same news and Cmdr Henry Hatfield, Sevenoaks, who was not a bit surprised because, at that time, he recorded solar radio noise at both 136 and 1296MHz. Another old friend, Harry Gratton G6GN, up for the day from Bristol, knew something had happened because 10m conditions were extra good at midday. At 1215 he worked VK2QL on c.w. and as late as 1400 he heard a VK in QSO with a GW on the key.

## Aurora

The Convention was a mine of information and during the afternoon lecture session, Charlie Newton explained, with illustrations, how the equipment aboard SkyLab improved our knowledge of the sun's coronal holes, great solar filaments that unwind like a knotted rope, and the occurrence of auroral events. "Information is vital," said Charlie, "I often have a thousand observers on the air throughout Europe during an event," and he told Angus McKenzie G3OSS, London, who recently achieved a tone-A contact with a GM on 70cm, that auroral contacts on the u.h.f.s and microwaves should be attempted. Many of the pundits were expecting an aurora after the previous day's s.i.d., and soon after I arrived home from Whitton, Alan Baker G4GNX, Newhaven, phoned around 2300, saying that signals on 20m had gone auroral. By midnight, John Cooper G8NGO, Cowfold, had received a GM and Roy Bannister G4GPX, Lancing, almost completed a

## TRANSISTORISED INVERTERS

12v or 24v DC  
INPUTS  
200/240v AC  
OFF LOAD OUT  
SQUARE WAVE



FREQUENCY  
48/52Hz  
DEPENDING  
ON LOAD  
SILICON POWER  
TRANSISTORS  
DC INPUT  
FUSED

### ECONOMY MODELS

#### 12v DC inputs:

EC1 - 6" x 4" x 4" approx. 20 watts	<b>£9.50</b>
EC2 - 6" x 4" x 4" approx. 40 watts	<b>£12.80</b>
EC3 - 11" x 7 1/2" x 4 1/2" approx. 150 watts	<b>£25.48</b>
EC4 - 11" x 7 1/2" x 4 1/2" approx. 200 watts	<b>£32.20</b>
EC5 - 11" x 7 1/2" x 5" approx. 300 watts	<b>£39.00</b>

ED1 - 11" x 7 1/2" x 4 1/2" approx. 100 watts	<b>£22.10</b>
ED2 - 11" x 7 1/2" x 4 1/2" approx. 150 watts	<b>£26.80</b>
ED3 - 11" x 7 1/2" x 5" approx. 200 watts	<b>£33.50</b>
ED4 - 11" x 7 1/2" x 5" approx. 300 watts	<b>£42.00</b>

Please add £2.00 per unit carriage.  
All units assembled to order approx. 28 days.  
Caged sizes are subject to variations.

TEL: **ELECTROVANCE**  
01-736 0685 P.O. Box 191, London SW6 2LS


**THE NEW**

## EUROSOLDERSUCKER

This 195mm long, all metal, high suction, desoldering tool with replaceable Teflon tip enables removal of molten solder from all sizes of pcb pads. Primed and released by thumb, it incorporates an anti-recoil system and built in safety guard. Only £6.80 inc. VAT & P.P.

**THE UNIQUE**

## EUROBREADBOARD

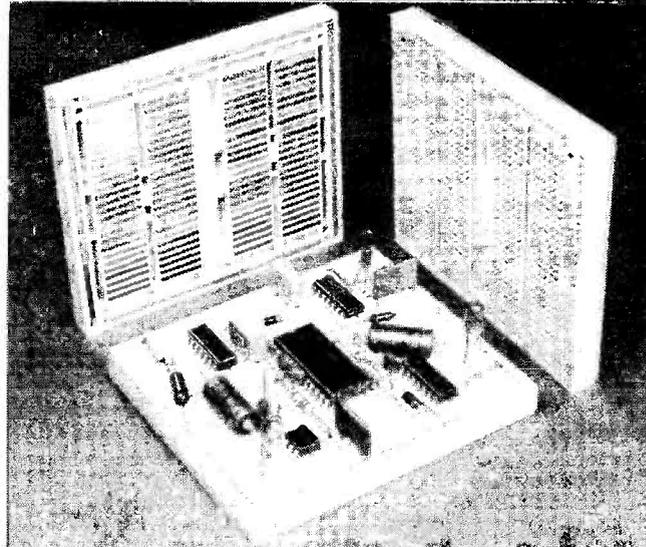

Logically laid out to accept both 0.3" and 0.6" pitch DIL packages as well as Capacitors, Resistors, LED's, Transistors and components with leads up to .85mm dia.

500 individual connections in the central breadboarding area, spaced to accept all sizes of DIL package without running out of connection points, plus 4 Integral Power Bus Strips around all edges for minimum inter-connection lengths.

**All connection rows and columns are now numbered or lettered enabling exact location indexing.**

Double-sided nickel silver contacts for long life (10K insertions) and low contact resistance (<10m. ohms).

Easily removable, non-slip rubber backing allows damaged contacts to be rapidly replaced.

No other breadboard has as many individual contacts, offers all these features and costs only £5.80 each or £11.00 for 2 - inclusive of VAT and P.P.

Snip out and Post

David George Sales, r/o 74 Crayford High St., Crayford, Kent DA1 4EF

**David George Sales**  
r/o 74 Crayford High Street,  
Crayford, Kent, DA1 4EF.

Please send me 1 EuroSolderSucker @ £6.80  Please  
or 1 EuroBreadBoard @ £5.80  Tick  
or 2 EuroBreadBoards @ £11.00

(All prices include VAT and P.P., but add 15% for overseas orders).


Name .....

Company .....

Address .....

Tel. No. ....

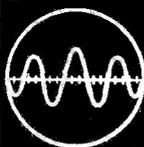Please make cheque/P.O.'s payable to David George Sales




## TUAC

TRANSISTOR UNIVERSAL AMPLIFICATION CO. LTD.  
PHONE 01-672 3137/672 9080  
MANUFACTURERS OF QUALITY AMPLIFICATION AND LIGHTING  
CONTROL SYSTEMS

### NEW FROM TUAC

TD500

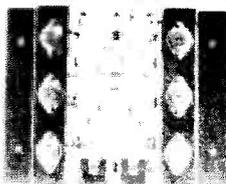

TD150



**7" x 9" x 1 3/4" ULTRA QUALITY HIGH POWER 5" x 5" x 2"**  
**New D.C. Coupled Design**  
**AMPLIFIERS**

**Featuring**—Electronic Short Open and Thermal Overload Protection.  
**Brief Spec.**—Input Sensitivity 0.775 v. R.M.S. (O.D.B.) at 25K Ohms.  
Frequency Response 20 Hz-20 KHz. T.H.D. at full power 0.1%.  
Hum and Noise—100 dB Relative full output.

**T.D. 500** 3000W into 2 Ohms. 220W into 4 Ohms. 140W into 8 Ohms ..... **£45.00**  
Power supply P.S. 300 ..... **£30.00**

**T.D. 150** 150W into 4 Ohms. 100W into 8 Ohms ..... **£26.25**  
Power supply P.S. 150 ..... **£19.50**

**T.D. 150** 60 Version 60W into 8 Ohms. 40W into 15 Ohms ..... **£19.50**  
Power supply P.S. 60 ..... **£15.50**

Note—P.S. 300 will drive 2 T.D. 150 amplifiers.  
All output ratings are R.M.S. continuous sine wave output.

#### TO ORDER BY POST

Make cheques/P.O.s payable to TUAC LTD., or quote Access/Barclay Card No. (We accept holders phone orders 01-672 9080).

Post to—

**TUAC LTD., 119-121 CHARLTON ROAD, LONDON SW17 9AB.**

Send stamp for our free 36 page catalogue of LIGHTING & AMPLIFIER MODULES, etc.

## So You Want to Pass the RAE?



A reprint of the complete series, including details of the new examination format being introduced in 1979, is now available. The reprint costs 85p, including postage and packing to addresses within the United Kingdom.

Order your copy by completing and returning the coupon, together with your remittance, to IPC Magazines Ltd., Post Sales Department, Lavington House, 25 Lavington Street, London SE1 0PF. Please ensure that your name and address are clearly legible.

### PRACTICAL WIRELESS—Radio Amateur Examination Reprint

Please send your order and remittance to:

**IPC Magazines Ltd., Post Sales Department,  
Lavington House, 25 Lavington Street,  
London SE1 0PF**

Please send me . . . copies at 85p each to include postage and packing

I enclose P.O./Cheque No. .... Value .....

Remittance must be crossed postal order or cheque (name and address on back please) and made payable to IPC MAGAZINES LTD

**NAME** .....  
(BLOCK LETTERS)

**ADDRESS** .....  
(BLOCK LETTERS)

..... Post Code .....

Remittances with overseas orders must be sufficient to cover despatch by sea or air mail as required. Payable by International Money Order only

Company registered in England. Regd. No. 53626

A subsidiary of Reed International Limited

Cut round dotted line

tone-A QSO with a GM on 2m. SM4IVE told **John Branegan** GM8OXQ, Saline, Fife, that an aurora manifested east of northern Sweden around 1925 on February 24, and John saw the effect of a weak aurora on Band I television on the 26th. Between 1900 and 2200 on the 21st, John received auroral signals from the 2m beacons in Germany DL0PR, Cornwall GB3CTC, Northern Ireland GB3GI and from three amateur stations in Scotland.

## Solar

There is little doubt that the February aurorae were caused by the solar activity which was recorded by **Robin Knight**, South East Essex Astronomical Society on 60MHz, Henry Hatfield on 136MHz, **John Smith**, Rudgwick, Sussex, on 142MHz, and myself on 146MHz, between the 19th and 23rd. Also on the 23rd, Henry, using his spectrohelioscope, saw a sunspot group nearing the western limb. Alan Baker visited Henry on the 25th and saw a prominence, several sunspots and a cloud of gas through Henry's machine. At 1052 on March 1, Henry located a bright area and a prominence just inside the east limb which may well have caused the solar radio noise recorded earlier by himself and John Branegan.

## Satellites

I chatted to **Ron Broadbent** G3AAJ, Secretary/editor of AMSAT-UK at the Convention, and he sent me a copy of their journal, *OSCAR News*, in which I am delighted to read that Britain's first Amateur Radio Spacecraft is in the pipeline and will be built at the University of Surrey. Ron is going to update us on all future developments. (Full details were given in "News" in our last issue. Ed.)

On March 4, John Branegan received a QSL card from W3JPT, Washington, DC, confirming his best OSCAR-8J DX to date. John raises an interesting point in his letter, "The intense high pressure to the east side of the UK on February 25 and 26 had a marked effect on satellite results, creating a barrier which slowly moved south-south-east. It was not possible to put a 2m signal into a satellite through this barrier when the satellite's elevation was below 25°." (My barograph recorded 30.75in at that time.)

Several stations have given John propagation data by coming back to his OSCAR-Mode J CQs, in particular the 11 QSOs with each of VE2LI Montreal, WA3ZHW Pennsylvania and WB2OXJ New Jersey.

## The 10 Metre Band

**Harold Brodribb**, St Leonards-On-Sea, writes: "Now that 10m is so brilliant and the Russian stations so numerous, we have a new field to hunt in." Harold has far too many American and Russian stations for a detailed report, which shows that his AR88 and loft-mounted, inverted "V" dipole are going well. Harry Gratton has been concentrating on 10m and in just two weeks has worked 60 JAs on the key. Between February 20 and March 18, I heard signals almost daily from the International Beacon Project stations in Bahrain A9XC, Cyprus 5B4CY, Germany DL0IGI, and periodically at midday, Bermuda VP9BA.

## DX TV

Both **Ian Rennison**, Horsham, and myself noticed frequent short bursts of signals on Channel R1, 49.75MHz during the early mornings. Around 0956 on

February 26, I received an unidentifiable picture, with vertical bars, on R1 and at 0900 on March 6 there were bursts of test card. **Ian Roberts**, Glenstantia, Rep. South Africa, says that conditions for DXTV were good on March 3 and writes: "The spectrum was literally jammed at the low-frequency end and the only pictures I could make out in detail were on R2 at 1609 GMT and later in the evening from 2053 to 2200, local time, Channel E2, Kenya." At 2300 Ian could still hear video signals above the receiver noise on Channels E2, R1 and IA. At the suggestion of young **Stuart Hardy**, Loudham, Notts, I wrote to Granada Television, Manchester, to find out more about the Granada caption that several of us saw during a Band I sporadic-E disturbance last year. In reply, one of our readers, **Arthur Brennan** G2AUC, of their engineering department said: "I can confirm that it was a Granada Television International caption which you saw. We do export to all European Countries and during sporadic-E we do have reports of our own station at Winter Hill, Lancashire, being received in Holland, Sweden and Norway". Arthur also expressed his interest in the "Five Metre Story" (*PW* March 78), because he and GW2CPU listened to the Snowdon tests, in 1932, with a super-regen receiver situated 800ft a.s.l. some 10 miles inland from Aberystwyth.

From Western Australia, **Anthony Mann** writes: "I spent February 10 and 11 modifying a valved TV set for 405 lines, just in time to lock B1 video, 45.0MHz, on the 12th, and B1 was in again on the 14th, 16th, 17th, 20th and 21st. Without doubt February 21 was the best B1 opening so far. Next day was completely different, absolutely dead, as is often the case with enhanced F2 conditions the day before." Anthony also heard B1 sound, 41.5MHz, briefly on March 8, 9 and 10 and signals from China on R1, on February 14 and March 2.

## Tropospheric

Anthony Mann tells me that on December 29, 1978, a two-way QSO on 1296MHz established a new world record between VK6KZ, 160km west of Albany, across the Great Australian Bight to VK5MC, 70km west of Mt Gambier. Our congratulations to the participants.

Although the atmospheric pressure rose from 29.1in at midday on February 13 to a record of 30.75in on the 25th, the v.h.f.s did not open as much as we hoped. However, some DX was about and on the 19th, **David Wakefield** G8RVK, Worthing, worked ON1YW and ON4VN; on the 20th, G3CHN, south Devon and at 1815 on the 26th, GU3KFT. David has a Mizuho SB-2M portable rig and a 10 watt linear on loan from **Mitch Tribe** G8PMT, and has worked G, GJ, GU, GW, F and ON and had QSOs in 13 different QRA locator squares including ZM, YJ and YK. On the 21st, a newly licensed husband and wife team, **John** G8RZP and **Jackie** G8RZO, **Brakespeare**, Slough, worked into Belgium and Holland on 2m s.s.b. During the evening of the 25th, Alan Baker worked F1ANH and ON5UN on s.s.b., ON6CP on c.w. and F1FJT through the Brighton repeater GB3SR, R3. At the Convention, Random Electronics displayed a massive, eye catching, 21ft long, 2m Yagi, French made by Tonna, which, along with their 70cm beams were selling well. Harry Gratton uses one of these beams and is delighted with its performance. During one of the Convention lectures, **Ray Flavell** G3LTP, talked about the mechanics of tropospheric openings and explained how to use the data published in the RSGB's VHF Manual. He also emphasised the importance of getting the "upper air data"

when obtaining daily met. information which is available from many sources.

## 144/432MHz Contest

Although conditions were generally poor for the RSGB's 144/432MHz and SWL Contest held on March 3 and 4, Alan Baker worked four French stations, one ON, one GW and a GJ on 2m s.s.b., and **David Wakefield**, a first timer, made 30 QSOs including 2 Fs and 1 GW. The multi-operators of the Hastings Electronics and Radio Club, G6HH/P, made 496 QSOs during the event with a best DX of 620km into France.

## St Dunstan's Weekend

Among the guests at the AGM of the St Dunstan's Amateur Radio Society held at Ian Fraser House, Ovingdean, Nr Brighton, on February 24, were Alan Baker, President of the Brighton and District Radio Society, **Barry Cook** G4BWJ, Royal Naval Amateur Radio Society, **Eric Letts**, Chairman of the Mid-Sussex Amateur Radio Society and **John O'Houlihan** G4BLJ and **Len Wooller** G9GEZ, of the Post Office Radio Division. After the official business a talk was given by **Louis Varney** G5RV, and during the weekend the St Dunstaners contacted several Ws on 10m and many locals on 2m through the Brighton repeater.

## Raynet

On March 1, several of our readers took part in an East Sussex Raynet exercise designed to assist the Red Cross ambulance service if the need arose. The group covered a wide area from Worthing along the south coast to Eastbourne and inland to Crowborough, with **Dermot Cronin** G3GRO, on the Royal Sovereign Light as a relay station. Many Sussex Raynet members were again on exercise on March 11 when they operated throughout Sussex in conjunction with the County Emergency Planning Officer, using 80m and 2m, s.s.b. and f.m.

## Amateur Co-operation

On February 25, F1FJT of Radio Club de Normandie wanted to contact **Geoff Ellis** G3LFZ of the Southdown Amateur Radio Society, so Alan Baker, who worked the Frenchman, called Geoff on the land line and they were soon in QSO. During the evening of March 9, Alan heard G5BYU/M on 2m s.s.b. in Haywards Heath and G3IIR, in London, calling each other in order to arrange a meeting at the VHF Convention the following day. By breaking in, Alan linked the two stations together.


## Sporadic-E

I was fortunate to be chairman for the Convention lectures given by Charlie Newton, Ray Flavell and **Professor Martin Harrison** G3USF, who began by playing tape recordings of music from Budapest, and an Italian commercial heard around 70MHz during a sporadic-E disturbance last summer. Martin explained some of the theories about sporadic-E, and emphasised that it was an erratic phenomenon occurring annually between May and August and most likely to affect the 2m band in the late afternoon.
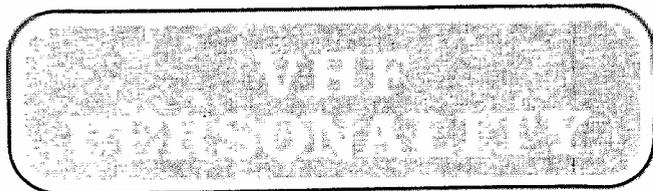
## The VHF Convention

During the morning I met my two opposite numbers, **Graham Knight** and **Norman Fitch**, the v.h.f. columnists for *Radio Communication* and *Short Wave Magazine*, who, like myself were surveying the trade stands which were laden with components especially for the home constructor. Among the trade exhibitors, who were all most helpful, were Messrs Burns, Cambrian, C and C, Display, Garex, Heller, J.M.G., Modular and S.G.S. Electronics, J Birkett, Catronics, Crayford, Hamvel,

Packer, South Midlands Communications, SOTA, S.W. Webb, Wood and Douglas, Amateur Radio Technical Service and Amateur Radio Exchange. At the end of the day Westlake Electronics told me that they had their usual run on coaxial cables, and John Fisher Electronics sold a lot of finishing materials, such as knobs, pilot lampholders and bits for making p.c. boards. The RSGB's bookstall and Bring and Buy sale were well supported and **Mike Dormer** G3DAH, and his lady assistants at the reception desk, were kept very busy as approximately 800 visitors arrived for the convention.



## THE RENNISON BROTHERS

by **RON HAM**

A variety of receivers belonging to radio enthusiasts, David and Ian Rennison, are installed in their respective bedrooms at their parents' home in Horsham, Sussex.

David, an 18-year-old trainee electrician, caught the bug for radio from his elder brother Ian and Ian's friend, Chris Otley G4CYA, some six years ago when the Rennisons lived in Sheffield. Ian, a 28-year-old bank employee, recalls that he began around the age of 14, when Chris and he listened to the medium waves on an old valved set which, after taking some 30 minutes to warm up, gave about 30 minutes good service before developing a loud squeal.

Ian's first communications receiver was a Codar 70A which he used to take around to Chris's home, in a shopping bag, because, with a bigger garden, Chris had a larger aerial and more signals were heard. David, a member of the Horsham Amateur Radio Club, is more inclined toward amateur radio than Ian whose main interests are medium wave DX, Band II broadcast listening and v.h.f. television DXing.

Both David and Ian use Trio 9R59 communications receivers with Codar preselectors. David uses an NR56 v.h.f. receiver for the 2m repeaters and a dual-gate MOSFET converter for general coverage of the 2m band, while Ian uses a Aiwa 5080A, with its wide bandspread for the f.m. stations in Band II, and a JVC 3040 UKC receiver for the European TV Channels, E2-4 and 5-12.

Both brothers have sound recording facilities and use sundry home-constructed items, such as aerial tuning units and crystal calibrators, and, in the large loft of the Rennison home, David has a Slim Jim, a 5/8 ground-plane and a home-brew 2m beam, while Ian has a dipole for Band I and a Yagi for Band III.

David is also keen on motor car engineering, while, over the years, Ian has built a large collection of pop records. As a regular reader of *Practical Wireless*, Ian makes frequent contributions to the columns of Charles Molloy and myself.

Although living under the same roof, their mutual interest in radio is separated by the different wavebands which suit the needs of Ian, the BCL and David, the SWL.



David Rennison operating his Trio receiver



Ian Rennison with his DX TV gear

# U.K. RETURN OF POST MAIL-ORDER SERVICE ALSO WORLD WIDE EXPORT SERVICE

## R.C.S. LOUDSPEAKER BARGAINS

3 ohm. 6 x 4in. £1-50. 7 x 4in. £1-50. 8 x 5in. £2-50. 5in. £1-50. 6 1/2in. £1-80. 8in. £2-60. 10in. £3. 12in. £4. 8 ohm. 2 1/2in. £1-50. 3in. £1-50. 5in. £1-50. 10in. £3. 12in. £4. 16 ohm. 6 x 4in. £1-50. 7 x 4in. £1-50. 5in. £1-50. 8in. £2-60. 10in. £3. 12in. £4. 10 x 6in. £3-50.


**THE "INSTANT" BULK TAPE ERASER**  
Suitable for cassettes, and all sizes of tape reels.  
A.C. mains 200/249V.  
Leaflet S.A.E. **£5-50** Post 50p



**HEAD DEMAGNETISER PROBE £4-75**
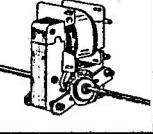
## A.C. ELECTRIC MOTORS

2 Pole, 240V, .2 Amp. Spindle — 1.43 x 0.212in. £1-75. 2 pole, 240V, .15 Amp. Double spindle — 1.75 x 0.16in. Each £1-50. 2 Pole, 120V, .5 Amp. Spindle — 0.75 x 0.2in. Two in series — 240V. 75p each. Brush Motor. From a Food Mixer 240V, .3 Amp. High Speed and Powerful. Spindle — 0.5 x 0.25in. £2-95 post 50p each.



**BLANK ALUMINIUM CHASSIS**, 18 s.w.g. 2 1/2in. sides, 6 x 4in. 95p; 8 x 6in. £1-40; 10 x 7in. £1-55; 14 x 9in. £1-90; 16 x 6in. £1-85; 12 x 3in. £1-20; 16 x 10in. £2-20; 12 x 8in. £1-70.

**ALUMINIUM PANELS**, 18 s.w.g. 6 x 4in. 24p; 8 x 6in. 38p; 10 x 7in. 54p; 12 x 5in. 44p; 12 x 8in. 70p; 16 x 6in. 70p; 14 x 9in. 94p; 12 x 12in. £1; 16 x 10in. £1-16.

**ALUMINIUM ANGLE BRACKET** 6 x 1/2 x 2in. 20p.  
**ALUMINIUM BOXES, MANY SIZES IN STOCK.**  
4 x 2 x 2in. 86p; 3 x 2 x 1in. 60p; 6 x 4 x 2in. £1; 8 x 6 x 3in. £1-90; 12 x 5 x 3in. £2; 6 x 4 x 4in. £1-30. 10 x 7 x 3in. £2-20.

## DE LUXE BSR HI-FI AUTOCHANGER

Plays 12in. 10in. or 7in. records  
Auto or Manual. A high quality unit backed by BSR reliability with 12 months guarantee. A.C. 200/250V. Size 13 1/2 x 11 1/2in.  
Above motor board 3 1/2in.  
Below motor board 2 1/2in.  
With **CERAMIC STEREO CARTRIDGE**  
Garrard 5300. Autochanger with ceramic cartridge. **£14-95**  
Garrard Minichanger. Plays all size records. Ceramic cartridge. Stereo. **£8-95**  
BSR. P182. Snake arm, flared Aluminium Turntable Stereo ceramic cartridge. Latest model. **£22-50**  
BSR. Disco Single Player Cueing Device 11in. Turntable. Budget price **£19-50**  
RSC Disco Deck 3 speed Stereo **£8 or £15 pair**



## BAKER 50 WATT AMPLIFIER £59



Superior quality ideal for Halls/PA systems. Disco's and Groups. Two inputs with Mixer Volume Controls. Master Bass, Treble and Gain Controls. 50 watts RMS. Three loudspeaker outlets 4, 8, 16 ohm. AC 240V (120V available). Blue wording on black cabinet.

**BAKER 150 Watt AMPLIFIER 4 inputs £79.**

**DRILL SPEED CONTROLLER/LIGHT DIMMER KIT.** Easy to build kit. Controls up to 480watts AC mains. Post 35p **£3-25**

**STEREO PRE-AMP KIT.** All parts to build this pre-amp. 3 inputs for high medium or low gain per channel, with volume control and P.C. Board. Can be ganged to make multi-way stereo mixers. Post 35p **£2-95**

## R.C.S. SOUND TO LIGHT DISPLAY MK 2

Complete kit of parts with R.C.S. printed circuit. Three channels. Up to 1,000 watts each. Will operate from 200MV to 100watts signal source. Suitable for home HI-FI and all Disco Amplifiers. Cabinet extra £4. **£17**


200 Watt Rear Reflecting White Light Bulbs. Ideal for Disco Lights. Edison Screw 75p each or 6 for £4. or 12 for £7-50.

## MAINS TRANSFORMERS

6 VOLT 1/2 AMP. £1-00 3 AMP. £1-95 9 VOLT 3 AMP. £2-75  
12 VOLT 300 MA. £1-00 750 MA. £1-30 20 VOLT 2 AMP. £2-50  
30 VOLT 5 AMP. AND 34 VOLT 2 AMP. C.T. £3-45  
20 VOLT 1 AMP. £2-00 20-0-20 VOLT 1 AMP. £2-95  
30 VOLT 1 1/2 AMP. £2-75 40 VOLT 2 AMP. £2-95 30V 2 AMP. £3  
0-20-40-60 VOLT 1 AMP. £3-50 2 x 18 VOLT 6 AMP. £9.  
Low Voltage 0-8-12V. 3 AMP £3.  
Low Voltage 12-0-12V. 2 AMP £3.  
GENERAL PURPOSE LOW VOLTAGE. Voltages available at  
2A, 3, 4, 5, 6, 8, 9, 10, 12, 15, 18, 24 and 30V **£5-80**  
1A, 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60 **£5-80**  
2A, 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60 **£5-50**  
3A, 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60 **£11-00**  
5A, 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60 **£14-50**
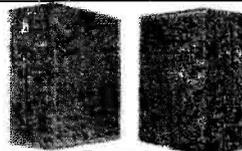
## R.C.S. TEAK COMPACT SPEAKERS

13 x 10 x 6in.  
50 to 14,000 cps.  
10 watts. 4 or 8 ohms.  
**£16 pair** Post £1-50



## BAKER SPEAKERS "BIG SOUND"

Robustly constructed to stand up to long periods of electronic power. Useful response 30-13,000 cps. Bass resonance 55 cps.  
**GROUP "35"** **£14-00**  
12in. 40 watt  
4, 8 or 16 ohms.  
**GROUP "50/12"** **£21-00**  
12in. 60 watt professional model. 4, 8 or 16 ohms. Response 30—16,000 cps. With aluminium presence dome.  
**GROUP "50/15"** **£33-00**  
15in. 75 watt  
8 or 16 ohms.  
Send for leaflets on Disco, P.A. and Group Gear.




## EMI. 1 1/2 x 8in SPEAKER SALE!

With tweeter. And crossover. 10W. State 3 or 8 ohm. Illustrated **£8-95** Post 45p  
**15W Model** **£10-50** Post 65p  
8 ohms Bass unit only.  
**GOODMANS 20 Watt Woofer**  
Size 12 x 10in. 4 ohms. Rubber cone surround. **£9-95**  
Hi-Fi Bass unit. Post 65p  
**GOODMANS TWIN AXIOM 8**  
8in. 8 ohm Hi-Fi Twin Cone Special unit **£9-95** Post 50p


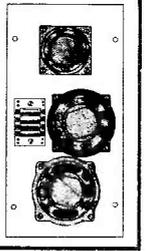
## R.C.S. MINI MODULE HI-FI KIT 15 x 8 1/2in 3-way Loudspeaker System.

EMI 5in. Bass 5in. Middle 3in. Tweeter with 3-way Crossover and Ready Cut Baffle. Full assembly instructions supplied. Response = 60 to 20 000cps 12 watt RMS. 8 ohm. **£10.95 per kit.** Two kits **£20.** Postage 75p. One or two kits.



# RADIO COMPONENT SPECIALISTS 337 WHITEHORSE ROAD, CROYDON

Minimum post 30p. Components List 20p. Phone orders. Access & Barclay VISA only. Open 9—6 Sat. 9—5 (Closed all day Wednesday) Tel. 01-684 1665

# Electronics. Make a job of it....

Enrol in the BNR & E School and you'll have an entertaining and fascinating hobby. Stick with it and the opportunities and the big money await you, if qualified, in every field of Electronics today. We offer the finest home study training for all subjects in radio, television, etc., especially for the CITY AND GUILDS EXAMS (Technicians' Certificates); the Grad. Brit. I.E.R. Exam; the RADIO AMATEUR'S LICENCE; P.M.G. Certificates; the R.T.E.B. Servicing Certificates; etc. Also courses in Television; Transistors; Radar; Computers; Servo-mechanisms; Mathematics and Practical Transistor Radio course with equipment. We have OVER 20 YEARS' experience in teaching radio subjects and an unbroken record of exam successes. We are the only privately run British home study College specialising in electronics subjects only. Fullest details will be gladly sent without any obligation.



## Become a Radio Amateur.

Learn how to become a radio-amateur in contact with the whole world. We give skilled preparation for the G.P.O. licence.

Brochure without obligation to:

## British National Radio & Electronic School

P.O. Box 156, Jersey, Channel Islands.

NAME \_\_\_\_\_

ADDRESS \_\_\_\_\_

Block caps please

**Free!**



### NOTICE TO READERS

When replying to Classified Advertisements please ensure:

- That you have clearly stated your requirements.
- That you have enclosed the right remittance.
- That your name and address is written in block capitals, and
- That your letter is correctly addressed to the advertiser.

This will assist advertisers in processing and despatching orders with the minimum of delay.

### Receivers and Components

#### VALVES

Radio - T.V. - Industrial - Transmitting  
Projector Lamps and Semiconductors

We Dispatch Valves to all parts of the world by return of post, Air or Sea mail. 4000 Types in stock. 1930 to 1976. Obsolete types a speciality. List 30p. Quotations S.A.E. Open to callers Monday to Saturday 9.30 to 5.00 closed Wednesday 1.00. We wish to purchase all types of new and boxed Valves, Projector Lamps and Semiconductors.

COX RADIO (SUSSEX) LTD.

Dept. P.W. The Parade, East Wittering,  
Sussex PO20 8BN  
West Wittering 2023 (STD Code 024366)

NEW SHOP in East Kent. Vast range of Electronic Components, equipment, hardware. Technocraft, 143 Tankerton Road, Whitstable (265091). Open Tuesday to Saturday. Easy Parking.

#### BRAND NEW COMPONENTS BY RETURN

**Electrolytic Capacitors** 16V, 25V, 50V.  
0.47, 1.0, 2.2, 4.7, 10 mfd. — 5p.  
22, 47—5p. (50V—6p.), 100—7p. (50V—8p.),  
220—8p. (50V—10p.), 470—11p. (50V—16p.),  
1000/15V—15p. 1000/25V—18p. 1000/40V—35p.

**Subminiature bead tantalum electrolytics.**  
0.1, 0.22, 0.47, 1.0 @ 35V, 4.7 @ 6.3V—8p.  
2.2/25V & 4.7/25V—9p. 10/25V, 15/16V—12p.  
22/16V, 33/10V, 47/6V, 68 & 100 @ 3V—14p.

**Mullard Miniature Ceramic E12 Series 63V 50V.**  
10 pf. to 47 pf.—3p. 56 pf. to 330 pf.—4p.

**Vertical Mounting Ceramic Plate Caps 50V.**  
E12 type—1000 pf. E6 1500 pf.—47000 pf.—2p.

**Polystyrene E12 Series 63V. Hor. Mounting.**  
10 pf. to 1000 pf.—3p. 1200 pf. to 10000 pf.—4p.

**Mullard Polyester 250V Vert. Mtg. E6 Series.**  
.01 to .1—4p. .15, .22—5p. .33, .47—8p.  
.68—11p. 1.0—14p. 1.5—20p. 2.2—24p.

**Mylar (Polyester) Film 100V. Vertical Mtg.**  
.001, .002, .005—3p. .01, .02—4p. .04, .05—5p.

**Miniature Film Resistors Highstab. E12 5%.**  
0.125 watt 10 Ω 2MΩ.....1p  
0.250 watt 1 Ω to 10MΩ (10% over 1M).....1p  
0.500 watt 10 Ω to 2MΩ.....2p  
1.000 watt 10 Ω to 10MΩ.....2p

1N4148—2p. 1N4002—4p. 1N4006—6p. 1N4007—7p  
BC107/8/9, BC147/8/9, BC157/8/9, BF194 & 7—9p.  
8 Pin Di. i.c.s 741's—18p. 555's—24p.

20mm. fuses .15, .25, .5, 1.0, 2.0, 3.0 & 5A—3p.  
20mm. fuseholders P.C. or Chassis Mtg.—5p.  
Post 10p (Free over £4). Prices VAT inclusive.

#### THE C. R. SUPPLY CO.

127, Chesterfield Road, Sheffield S8 0RN

**COMPONENTS:** 32 Leds (12R, 10G, 10Y) £3, 10 packs £25; LM741 15p, 10 for £1.40; NE555 22p, 10 for £2; LM3900 40p, 10 for £3.50; LM380 65p, 10 for £6; CPU's Z80 £10, 6800 £7; 8080 £6, Z80A £14, TMS2708 £6.50, all Micros include socket; - 2102-1 (450n) 80p; Trans. 2N2222A 13p - RESISTORS 4p mix; CERAMIC DISC 27pF to 8n2 1p any mix; P & P. 12p, CMOS, TTL, MICROS free list. Tel. (0506 632337). R. Machnik, 13 Hoperfield Place, Blackburn, West Lothian.

# SMALL ADS

The prepaid rate for classified advertisements is 22 pence per word (minimum 12 words), box number 60p extra. Semi-display setting £7.50 per single column centimetre (minimum 2.5 cms). All cheques, postal orders etc., to be made payable to Practical Wireless and crossed "Lloyds Bank Ltd". Treasury notes should always be sent registered post. Advertisements, together with remittance, should be sent to the Classified Advertisement Manager, Practical Wireless, Room 2337, IPC Magazines Limited, King's Reach Tower, Stamford St., London, SE1 9LS. (Telephone 01-261 5846)

### CONDITIONS OF ACCEPTANCE OF CLASSIFIED ADVERTISEMENTS

- Advertisements are accepted subject to the conditions appearing on our current advertisement rate card and on the express understanding that the Advertiser warrants that the advertisement does not contravene any Act of Parliament nor is it an infringement of the British Code of Advertising Practice.
- The publishers reserve the right to refuse or withdraw any advertisement.
- Although every care is taken, the Publishers shall not be liable for clerical or printers' errors or their consequences.

**RIBBON MICROPHONES** with 4/8 Poleswitch 95p; Microswitches, Capacitors, Receiver and Microphone Capsules 10p each; Bakelite Telephones £2-95; Handsets 50p; Magneto Generators £1-75. P.&P. £1-50. **CONVERSION PIECES**, 55 Swindon Road, Cheltenham. (35707).

#### D.V.M. THERMOMETER KIT



Based on the ICL7106 single chip DVM the kit contains a 3 digit LCD, a PCB ICL7106, and all components and instructions to make a 0.200mV FSD DVM. Components also supplied to enable this to be converted to a digital thermometer. Requires a 2mA 9V supply (FP3 battery). ONLY £21.99

#### TOUCH CONTROLLED LIGHTING KITS

Directly replace conventional light switches and control up to 300W of lighting. No mains rewiring. Insulated touch plates. Easy to follow instructions.

**NEW! TD300K—TOUCHDIMMER!** Single touchplate with alternate action. Brief touch switches lamp on and off, longer touch dims or brightens lamp. Neon lamp helps find the switch in the dark. £1.99

—Extension kit for TD300K permits operation from another location, two-way switching, etc. £1.50

**TS300K—ON/OFF TOUCHSWITCH.** Two touch-plates. £2.40

**TS300K—AUTOMATIC TOUCHSWITCH.** Time delay variable 2 secs to 3 1/2 mins. £4.30

**LD300K—300W LIGHTDIMMER KIT** £2.90

★ SPECIAL OFFER ★

10% discount on any 4 lighting control kits.

#### 24 HR. CLOCK APPLIANCE TIMER KIT



Switches any appliance of up to 1KW on and off at preset times once a day. KIT contains: AY-5-1230 Clock/Appliance Timer IC, 0.5" LED display, mains supply, display drivers, switches, LEDs, triac PCBs and full instructions. £14.90

White box 56 x 131 x 71mm with red Acrylic window £2.20

White box as above ready drilled for kit £2.50

Ready-built in box, incl. mains cable £22.50

#### 400V PLASTIC TRIACS OPTO COMPONENTS

3A	49p	0.2" dia LEDs	555 22p (4 for 90p)
6A	62p	Red 12p (1/10)	741 22p (5 for 90p)
12A	70p	Green 17p	LM3911
16A	50p	Y./low 17p	Temperature
20A	165p	DL727 £1.50	control IC £1.00
25A	190p	LED 0.5" £8-10	ZN1034E £1.80
5" with trigger	35p	LDR mix	ICL7106 £7.50
3 1/2"	50p	ORP12	50p TIC106D SCR 50p
* isolated tab	50p	Neon	2N6027 34p
DIAC	18p		AY-5-1230 £4.50

QUANTITY DISCOUNTS ON REQUEST  
ADD 8% VAT + 25p P&P. Callers by appointment only.  
Tel: 01-579 9794

T. K. ELECTRONICS  
106 STUDLEY GRANGE ROAD, LONDON W7 2LX

**TUNBRIDGE WELLS COMPONENTS, BALLARD'S,**  
108 Camden Road, Tunbridge Wells, Tel: 31803. No Lists.  
Enquiries S.A.E.

#### AM/CW/SSB COMMUNICATION RECEIVER and preselector modules

153.5 kHz Mech. Filter Modules 2-1 kHz BW, with diode-switching.  
**CRYSTALS** Brand new high precision HC33/U: 1.0, 2.0, 3.0, 1.008, 2.5625 MHz £3-35. 1.28 MHz £4-15. HC13 100 kHz £3-25. HC18/U: 4.0, 5.0, 6.0, 7.0, 8.0, 10.0, 10.7 MHz £3-00. 18.0, 20.0, 38.6667, 48.0, 100.0, 118.0 MHz £3-60. HC25/U 8.0833 MHz (S20) £3-00. Large stocks of standard freqs for MPU etc. Any freq made to order 6 weeks from £3-75.  
**WINKLE PICKERS.** Winkle out DX from the GRM with pin-sharp 250 Hz 8-pole crystal CW filters specially manufactured to fit TRIO and YAESU: FT/FR-101, FT-301, TS-50, TS-820, £25-90 each.

All prices inc. VAT and UK post. SAE Lists.  
**P. R. GOLLEGE ELECTRONICS**  
G3EDW, Merriott, Somerset, TA16 5NS  
Tel: 0480 73718

### NOSTALGIA THE VINTAGE COLLECTING WIRELESS COMPANY

1920 to 1950

Receivers, valves, components, service data, historical research books, magazines, repairs and restorations. A complete service for the collector and enthusiast of vintage radio. S.a.e. with enquiries and for monthly newsheet.  
**THE VINTAGE WIRELESS COMPANY, 64, Broad Street, Staple Hill, Bristol BS16 5NL. Tel. Bristol 565472.**



#### Codespeed

ELECTRONIC MAIL ORDER  
All full spec. devices

- 4 DIGIT LIQUID CRYSTAL DISPLAY.** A super, high contrast 4 digit non-multiplexed display. Digit height is 0.5" and the display is supplied with data and a special, easy to solder, edge connector. £5.95. Catalogue Number 206
- MM5314 CLOCK CHIP 8PIN.** A bulk purchase allows us to offer these digital clock chips at the unbelievable price of only £1.99 each. With data, Catalogue Number 207
- POLARISING FILTER MATERIAL.** A slightly tinted polarising filter material, manufactured by "Polaroid", in 0.006" plastic film. Any size cut, from 1 sq. inch to a maximum size of 19" by 250 feet. Our price — only 2p per square inch. Catalogue Number 701
- DIGITAL ALARM CLOCK MODULE.** A digital alarm clock module, complete with 0.5" LED display. Just add mini transformer and time setting switches for fully functional clock. With data and instructions, only £5.80. Catalogue Number 205
- DIGITAL MULTIMETER CHIP.** This MM5330 d.v.m. chip can be used to build a high accuracy d.v.m. or panel meter. Has auto polarity and over-range indication. Supplied with data and circuit. Requires some additional circuitry. Only £3.95. Catalogue Number 404
- 8 DIGIT LIQUID CRYSTAL DISPLAY.** This calculator style L.C.D. has 0.33" high digits with R.H. decimal points and overflow indicator. White digits on clear glass. With data £2.95. Catalogue Number 302
- 5 DIGIT MICRO L.E.D. DISPLAY.** Built on top of a 16 pin dual in line package this 7 segment display has 5 bright 0.09" high digits. Terrific value for only 75p. Catalogue Number 308
- LED CLOCK DISPLAY.** A superb 24 hour LED clock display with 0.8" high digits. Display panel is common cathode and non-multiplexed. A snip at only £3.85. Catalogue Number 204
- CALCULATOR KEYBOARDS.** Two multifunction calculator keyboards. Excellent key action. Only £1.00 the pair. Catalogue Number 101
- 9 DIGIT DISPLAY.** A 9 digit, 7 segment gas discharge display. Super, bright 0.25" high digits. With data, only 75p. Catalogue Number 310

#### Untested Items

- DEFECTIVE CALCULATORS.** A production line reject calculator with lots of accessible goodies inside. Detachable keyboard, display, case and PCB with approx. 25 transistors and calculator chip. Not much wrong with some we tested. A bargain at only £2.50. Catalogue Number 104
  - CALCULATOR TOPS** (Untested — so no guarantees). The upper half of two hand held calculator cases with integral keyboard. Equipment but believed to be o.k. Only 80p the pair. Catalogue Number 105
- Satisfaction guaranteed or return for replacement or refund.  
New Spring catalogue now available. Send Medium sized S.A.E. for your free copy.  
Postage and Packing please add 25p (Overseas orders add 60p).

#### CODESPEED

P.O. Box 23, 34 Seafield Road,  
Copnor, Portsmouth, Hants., PO3 5BJ



#### Record Accessories

STYLI, Cartridges For MUSIC CENTRES, etc. FREE List No. 29 For S.A.E. includes Leads, Mikes, Phones etc. FELSTEAD ELECTRONICS, (PW), Longley Lane, Gatley, Cheshire, SK8 4EE.

#### Ladders

LADDERS varnished 22" extd. £30. Carriage £2.80. Leaflet. Also Alloy ext. up to 62 1/2". LADDER CENTRE (WLS3), Halesfield (1), Telford. Tel: 586644.

## Service Sheets

**The Big Suppliers of:—**

**ALL SERVICE SHEETS & MANUALS**  
1 sheet £1. 6 for £5. 25 for £20. 100 for £75.  
Most manuals by return post. All enquiries welcome, please enclose S.A.E. **Colour T.V. data specialists**

**COMPLETE BRITISH MONO T.V. REPAIR SYSTEM**  
Every main circuit/layout in luxury binder with the 4 McCourt Repair Manuals for only £30.

**G.T. TECHNICAL INFORMATION SERVICES (PW)**  
10 Dryden Chambers, 119 Oxford Street,  
London W1R 1PA.  
(Mail Order Department only)

**T.V. REPAIRS  
MADE EASY**  
Full, easy-to-follow instructions for the repair of almost any T.V. set.  
Send details of set, plus £5 (Circuit £1 extra) to —  
T.I.S.(W) 76 Church St.,  
Larkhall, Lanarkshire ML9 1HE,  
Scotland.  
(Callers welcome)

**LARGE SUPPLIER OF  
SERVICE SHEETS**  
and Colour Manuals, TV Mono Radios, Tuners, Tape Recorders, Record Players, Transistors, Stereograms, all at 75p each + S.A.E. except colour TV and Car Radios. State if Circuit will do, if sheets are not in stock. All TV Sheets are full lengths 24 x 12, not in Bits & Pieces. Free Fault Finding Chart or TV Catalogue with order.

**C. CARANNA (Mail Order)**  
71, Beaufort Park, London, NW11 6BX  
01-458 4882

**SERVICE SHEETS** for Radio, Television, Tape Recorders, Stereo, etc., with free fault-finding guide, from 50p and S.A.E. Catalogue 25p, and S.A.E. HAMILTON RADIO, 47 Bohemia Road, St. Leonards, Sussex.

**SERVICE SHEETS**, Radio, TV etc., 10,000 models. Catalogue 24p, plus S.A.E. with orders, enquiries. TELRAY, 154 Brook Street, Preston PR1 7HP.

**BELL'S TELEVISION SERVICES** for Service Sheets on Radio, TV etc., £1.00 plus SAE Colour TV Service Manuals on request. SAE with enquiries to B.T.S., 190 King's Road, Harrogate, N. Yorkshire. Tel: (0423) 55885.

## Books and Publications

**Build your own  
P.A., GROUP & DISCO SPEAKERS**  
by R. F. C. Stephens  
Save money with this practical guide. Plans for 17 different designs. line source. I.B., Horn and Reflex types, for 8"-18" drive units. **£3-95** post free (\$8 overseas).

**THE INFRA-BASS LOUDSPEAKER**  
by G. Holliman  
(full constructional details for versions using 15", 12" and 10" drive units). **£2-95** post free (\$6 overseas).

**THE DALESFORD SPEAKER BOOK**  
by R. F. C. Stephens  
This book is a must for the keen home constructor. Latest technology DIY designs. Plans for I.B., and Reflex designs for 10-100 watts. Also unusual centre-bass system. **£2-20** post free (\$5 overseas).

**VAN KAREN PUBLISHING**  
5 SWAN STREET, WILMSLOW, CHESHIRE

## Educational

**TELEVISION &  
VIDEO SYSTEMS  
ENGINEERING**

**15 MONTHS full-time Diploma course to include a high percentage of practical work.**

- ELECTRONIC PRINCIPLES
- MONO & COLOUR TELEVISION
- CLOSED CIRCUIT TELEVISION
- VIDEO CASSETTE RECORDING
- DIGITAL TECHNIQUES
- TELETEXT & TV GAMES

**Shortened courses for applicants with suitable electronics background.**

Next session starts September 17th.

(Also available 2½ year course in Marine Electronics & Radar for employment as ships Radio Officer.)

Prospectus from:

**LONDON ELECTRONICS  
COLLEGE**

Dept. B6, 20 Penywern Road,  
London SW59SU. Tel. 01-373 8721.

**GO TO SEA** as a Radio Officer. Write: Principal, Nautical College, Broadwater, Fleetwood, FY7 8JZ.

**COLOUR TV SERVICING**  
Learn the techniques of servicing Colour TV sets through new homestudy course approved by leading manufacturers. Covers principles, practice and alignment with numerous illustrations and diagrams. Other courses for radio and audio servicing. Full details from:  
**ICS SCHOOL OF ELECTRONICS**  
Dept. H277 Intertext House, London SW8 4UJ  
Tel. 01-622 9911 (all hours)  
State if under 18

**TECHNICAL TRAINING**  
Get the training you need to move up into a higher paid job. Take the first step now—write or phone ICS for details of ICS specialist homestudy courses on Radio, TV, Audio Eng. and Servicing, Electronics, Computers, also self-build radio kits. Full details from:  
**ICS SCHOOL OF ELECTRONICS**  
Dept. H277 Intertext House, London SW8 4UJ  
Tel. 01-622 9911 (all hours)  
State if under 18

**CITY & GUILDS EXAMS**  
Study for success with ICS. An ICS homestudy course will ensure that you pass your C. & G. exams. Special courses for: Telecoms, Technicians, Electrical Installations, Radio, TV & Electronics Technicians, Radio Amateurs, Full details from:  
**ICS SCHOOL OF ELECTRONICS**  
Dept. H277 Intertext House, London SW8 4UJ  
Tel. 01-622 911 (all hours)  
State if under 18

**WHETHER SEA-GOING OR SHORE-BASED**, an exciting life awaits you as a Marine Radio Officer. Full details from the Principal, Barking College of Technology, Dagenham Road, Romford RM7 0XU. (Tel: Romford 66841).

## For Sale

SEEN WHISTONS CAT? 5000 odds and ends. Mechanical/Electrical Cat Free. WHISTON, (Dept. PW), New Mills, Stockport.

**REALISTIC DX160 S.W. Receiver** £105. Joystick VFA (System A) £35. Phones £3. Excellent condition, little used. G. Barlow, 37 Tanhouse Lane, Malvern Link, Worcs.

**NEW BACK ISSUES** of "PRACTICAL WIRELESS" available 70p each, post free. Open P.O. Cheque returned if not in stock—BELL'S TELEVISION SERVICE, 190 Kings Road, Harrogate, N. Yorks. Tel: (0423) 55885.

**P.W. F.M. Multitester P.C.B. 90p.** H.T.E. 4 watt Electronic Siren P.C.B./circuit 90p. Complete kit £3.49. P.C.B.'s manufactured from your design at realistic prices. H.T.E. 50 Milnefield Avenue, Elgin, Morayshire.

## Wanted

**ELECTRONIC COMPONENTS PURCHASED.** All Types Considered—Must be new. Send detailed list—Offer by return—WALTONS, 55A Worcester Street, Wolverhampton.

**WANTED** Instructions circuit for Wireless set 19 MKII conversion to 240 ac mains. T. Edwards, 2 Pembroke Terrace, Varteg, Pontypool, Gwent.

**CIRCUIT DIAGRAM** and detailed parts list to build a radio permanently tuned to 194 metres or 1546 kHz with pre-set volume and nine volt battery supply or have such a radio constructed in a wooden or sturdy plastic box to be inserted into a padded bag or details of how to replace a variable tuning capacitor with a pre-set one. **THE JOB IS FOR AN IN-PATIENT OF WARLINGHAM PARK HOSPITAL WHO IS SUFFERING FROM A TERMINAL DISEASE WHICH SEEMS LIKE A TWENTY-FOUR HOUR EPILEPTIC FIT AND MAY SUBJECT THE RADIO TO ROUGH TREATMENT INCLUDING DROPPING IT!** Offers please to:—BM BEDSITTER, LONDON, WC1V 6XX.

## Miscellaneous

**AERIAL BOOSTERS** Improve weak VHF Radio and Television reception, price £5-00 S.A.E. for Leaflets. **ELECTRONIC MAILORDER LTD.**, Ramsbottom, Bury, Lancashire BL0 9AG.

**THE SCIENTIFIC  
WIRE COMPANY**  
PO Box 30, London E.4  
Reg. Office 22 Coningsby Gdns

**ENAMELLED COPPER WIRE**

SWG	1 lb	8 oz	4 oz	2 oz
10 to 19	2.65	1.45	.75	.60
20 to 29	2.85	1.65	.90	.70
30 to 34	3.05	1.75	1.00	.75
35 to 40	3.40	1.95	1.15	.84
41 to 43	4.55	2.55	1.95	1.30
44 to 46	5.05	3.05	2.15	1.70
47	8.00	5.00	3.00	1.80
48	15.00	9.00	6.00	3.30

**SILVER PLATED COPPER WIRE**

14, 16, 18	4.50	2.25	1.44	.90
20 & 22	5.00	2.85	1.74	1.06
24 & 26	5.70	3.31	2.00	1.22
28 & 30	6.67	3.86	2.35	1.44

Prices include P & P and VAT  
SAE brings list of copper & resistance Wires  
Dealer Enquiries Invited

**SUPERB INSTRUMENT CASES** by Bazelli, manufactured from P.V.C. Faced steel. Hundreds of people and industrial users are choosing the cases they require from our vast range. Competitive prices start at a low 90p. Chassis punching facilities at very competitive prices, 400 models to choose from, free literature (stamp would be appreciated). **BAZELLI**, Dept. No. 25, St. Wilfreds, Foundry Lane, Halton, Lancaster LA 6LT.

**LOSING DX?**

**RARE DX UNDER QRM?** DIG it OUT with a Tunable Audio Notch Filter, 350-5000Hz, 40dB notch, speaker amplifier, only £8.90.

**V.L.F.?** Explore with a 10-150KHz Receiver, £10.70.

**MISSING RARE DX?** Get SPOT-ON with a Crystal Calibrator, 1MHz, 100, 25KHz markers, £13.80.

**RADIO 4 GONE?** FRG7? AR88? 200KHz to Medium Wave Converter, coax and inductive outputs, £9.70.

**TIME?** MSF 60KHz Receiver £13.70. Sequential year, month, date, day, hours, minutes, seconds display parts (no case or pcb) for receiver £10.70.

**SIG. GEN.**, 10Hz-200KHz, logic and variable sine or square wave outputs, linear frequency scale, £10.80.

**GOING DOWN?** 100-600KHz to 4-1-4.6MHz Converter, built-in antenna tuner, extend your coverage, £9.90.

Please write for overseas prices. Each easy-assembly kit includes all parts, printed circuit, case, instructions, postage etc., money back assurance so SEND off NOW.

**CAMBRIDGE KITS**  
45 (PT) Old School Lane,  
Milton, Cambridge.

**KIT OF PARTS** for Wireless World Stereo Tuner, or Ready Built and aligned, Semiconductors, Knobs, Meters, Resistors, Capacitors, Switches, Transformers. Catalogue 35p. R.B. Electronics, 24 Springfield Park, Holyport, Maidenhead. 39798.

**MORSE CODE TUITION AIDS**

Cassette A: 1-12 w.p.m. for amateur radio examination.  
 Cassette B: 12-24 w.p.m. for professional examination preparation.  
 Morse Code and Buzzer Unit for sending practice.  
 Price each Cassette (including booklets) **£4-50**. Morse Key and Buzzer **£4-50**.  
 Prices include postage etc.. Overseas Airmail £1-50 extra.  
**MHEL ELECTRONICS (Dept. P.W.), 12 Longshore Way, Milton, Portsmouth PO4 8LS.**

**GUITAR/PA MUSIC AMPLIFIER**

100 Watt with superb treble bass overdrive 12 months guarantee, unbeatable at **£42**; 60 watt **£37**; 200 watt **£58**; 100 watt twin channel sep treble/bass per channel **£55**; 60 watt **£48**; 200 watt **£72**; 100 watt four channel sep treble/bass per channel **£75**; 200 watt **£92**; Slaves 100 watt **£32**; 200 watt **£49**; Fuzz boxes great sound **£8-50**; Bass fuzz **£9-50**; Overdriver: fuzz with treble & bass boosters **£14**; 100 watt combo superb sound overdrive, sturdy construction castors, unbeatable **£89**; twin channel **£99**; Bass combo **£99**; speakers 15in. 100 watt **£35**; 12in. 100 watt **£22-50**; 60 watt **£14-50**. Send Cheque or P.O. to:

**WILLIAMSON AMPLIFICATION**

62 Thorncliffe Ave., Dukinfield, Cheshire.  
 Tel 061-344 5007 or 061-308 2064

ALFAC etch resist transfers and other p.c. board drawing materials available from stock. SAE details. Ramar Constructor Services, Masons Road, Stratford-upon-Avon. CV37 9NF.

Resistors 1/4W 5% 2R2-2M2 (E12). 10 each or more of each value 90p/100. 100 assorted, our mixture 75p/100. C60 cassettes in library cases 30p each. Miniature relays 17 x 30 x 28mm 6000 coil 4 sets change over contacts 50p each. Prices include V.A.T. Add 10% postage.

**SALOP ELECTRONICS**  
 23 Wyle Cop, Shrewsbury.

**KEEP ONE HANDY IN THE WORKSHOP**



The unique aerosol treatment for minor burns and scalds. From Boots and other Chemists.

**CATALOGUE OF WIDE** Range of components FREE on request. J. R. Hartley, Electronics Components, 78B High Street, Bridgnorth, Salop WV16 4DY. Tel: 07462-3865.

**DART STATIONERY**

Presents **FOR THE AMATEUR RECEPTION REPORT LETTERS**. Professionally styled letters printed in two colours and supplied in pads of 100 letters.

LOG BOOKS ..... **£2.00** each

**FOR THE DX'er**

Personalised **QSL CARDS**.  
**RECEPTION REPORT LETTERS**. Professionally styled letters printed in two colours and supplied in pads of 100 letters.

1 Pad **£1.80**

2+ Pads **£1.60** each.

Loose Leaf **LOG BOOKS** with 100 sheets..... **£2.50**

**FOR THE CB'er**

Personalised **QSL CARDS**.  
**CATALOGUES** available containing complete range of radio stationery **PRICE 45p**.

**EVERY ORDER CARRIES A MONEY BACK ASSURANCE IF NOT COMPLETELY SATISFIED.**  
 Please send cheques or P.O. payable to:—

**DART STATIONERY**

20, Bromley Road, London E17 4PS, England  
 Tel. 01-539 5412

TIRRO's new mail order price list of electronic components now available on receipt of SAE. TIRRO ELECTRONICS, Grenfell Place, Maidenhead, Berks.

**BELLS AND SIRENS**

CARTERS SIREN **£5.95**  
 INDUSTRIAL SIX INCH BELL **£8.27**

PRICES INCLUSIVE  
 SEND CHEQUE. P.O. to:

**CWAS ALARM**

11 Denbrook Walk,  
 Bradford BD4 0QS

6 to 12v D.C.



12v D.C.

SAE for full price list of Professional Burglar Alarm Equipment.

**EX MINISTRY AND SURPLUS EQUIPMENT**  
 A neat 2 1/2" dia DC Moving coil indicator, F.S.D. 1mA resistance 60 ohms, scaled 0-500 and 0-125 no caption (ideal for transistor tester) supplied unused **£3-30**.  
 24V DC Motor 1 1/2" dia x 2" long + 1/8" long removable worm on a 1/4" dia shaft, a quality made motor supplied unused **£2-80**.  
 50K ohms Ten Turn potentiometer 2 1/2" dia, servo mounting with a 1/4" dia shaft, supplied unused **£1-25**.  
 Seven segment nine digit Gas Discharge Display 180 V/W, character height .27", supplied unused **£1-20**.  
 Elliott Transistor Curve Tracer type 8079, requires an oscilloscope with D/C X and Y Amps to operate **£30-00**.  
 All prices include postage. Lots of other items in stock S.A.E. for lists. Shop hours 9.30am to 2pm weekdays, closed Thursdays, Saturday 9.30am to 5.30pm.  
**A.E. SUPPLIES,**  
 1 Arnolds Yard, Old Market Place, Altrincham, Cheshire.

**NOTICE TO READERS**

*Whilst prices of goods shown in classified advertisements are correct at the time of closing for press, readers are advised to check with the advertiser both prices and availability of goods before ordering from non-current issues of the magazine.*

**ORDER FORM** PLEASE WRITE IN BLOCK CAPITALS

Please insert the advertisement below in the next available issue of Practical Wireless for ..... insertions

I enclose Cheque/P.O. for £ .....

(Cheques and Postal Orders should be crossed Lloyds Bank Ltd. and made payable to Practical Wireless).


NAME .....

ADDRESS .....

Send to: Classified Advertisement Manager

**PRACTICAL WIRELESS,**  
 GMG, Classified Advertisement Dept., Rm. 2337,  
 King's Reach Tower, Stamford Street,  
 London SE1 9LS Telephone 01-261 5846

Rate  
**22p** per word, minimum 12 words. Box No. **60p** extra.

Company registered in England. Registered No. 53626. Registered office: King's Reach Tower, Stamford Street, London SE1 9LS

# TRANSFORMERS

EX-STOCK—SAME DAY DESPATCH

12 OR 24 VOLT OR 12-0-12V PRIMARY 220-240VOLTS				
Ref	Amps	VAT	P & P	Inc.
111	0.5	2.38	0.49	0.84
207	1.0	3.26	0.84	1.04
71	2	3.79	1.04	1.23
18	4	4.35	1.04	1.23
85	0.5	4.86	0.85	1.04
70	6	6.78	1.04	1.23
108	8	8.02	1.23	1.43
72	10	8.77	1.23	1.43
116	12	9.71	1.43	1.62
17	16	11.58	1.43	1.62
115	20	15.10	2.25	2.45
187	30	19.36	2.25	2.45
226	60	39.03	0A	0A

30 VOLT RANGE				
Ref	Amps	VAT	P & P	Inc.
Pri 220/240	Sec 0-12-15-20-24-30V	Volts available 3, 4, 5, 6, 8, 9, 10, 12, 15, 18, 20, 24, 30V or 12V-0-12V & 15V-0-15V		
112	0.5	2.12	0.84	1.04
79	1.0	2.86	1.04	1.23
3	2.0	6.23	1.04	1.23
20	3.0	6.70	1.23	1.43
21	4.0	8.63	1.23	1.43
51	5.0	10.66	1.43	1.62
117	6.0	12.06	1.57	1.77
88	8.0	16.15	1.77	1.99
89	10.0	18.63	1.99	2.19
90	12	20.70	2.19	2.39
91	15	23.72	2.25	2.45
92	20	31.81	0A	0A

50 VOLT RANGE				
Ref	Amps	VAT	P & P	Inc.
Pri 220/240V	Sec 0-20-25-33-40-50V	Volts available 5, 7, 8, 10, 13, 15, 17, 20, 33, 40 or 20V-0-20V & 25V-0-25V		
102	0.5	3.68	0.84	1.04
103	1.0	4.94	1.04	1.23
104	2.0	7.73	1.23	1.43
105	3.0	9.24	1.43	1.62
106	4.0	12.32	1.62	1.82
107	6.0	16.26	1.77	1.99
118	8.0	21.88	2.25	2.45
119	10.0	26.98	0A	0A
109	12	31.21	0A	0A

60 VOLT RANGE				
Ref	Amps	VAT	P & P	Inc.
Pri 220/240V	Sec 0-24-30-40-48-60V	Volts available 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60 or 24V-0-24V or 30V-0-30V		
124	0.5	4.19	1.04	1.23
126	1.0	6.38	1.04	1.23
127	2.0	8.21	1.23	1.43
125	3.0	11.88	1.43	1.62
123	4.0	13.52	1.62	1.82
120	5.0	17.11	1.99	2.19
120	6.0	19.50	1.99	2.19
121	8.0	27.60	0A	0A
122	10.0	31.91	0A	0A
189	12.0	36.78	0A	0A

MAINS ISOLATORS (SCREENED)				
Ref	VA (Watts)	VAT	P & P	Inc.
Pri 120/240V	Sec 120/240V CT			
*07	20	4.75	0.85	1.04
149	60	7.24	1.04	1.23
150	100	9.23	1.23	1.43
151	200	17.05	1.43	1.62
152	250	14.34	1.99	2.19
153	350	17.74	1.99	2.19
154	500	22.11	2.32	2.52
155	750	31.38	0A	0A
156	1000	40.18	0A	0A
157	1500	55.49	0A	0A
158	2000	66.75	0A	0A
159	3000	93.59	0A	0A

AUTO TRANSFORMERS				
Ref	VA	VAT	P & P	Inc.
113	15	2.68	0.77	0.97
64	75	4.33	1.04	1.23
4	150	5.78	1.04	1.23
69	250	7.60	1.23	1.43
67	500	240 to 115	11.87	1.77
84	1K	20.26	2.25	2.45
93	1.5K	25.14	0A	0A
95	2K	37.61	0A	0A
73	3K	63.95	0A	0A
80s	4K	83.01	0A	0A
57s	5K	96.66	0A	0A

HIGH VOLTAGE ISOLATORS				
Ref	VAT	P & P	Inc.	Ref
Pri 200/220V or 400/440V				
Sec 110/120V CT or 200/240CT				
60	243	7.24	1.43	1.62
350	247	17.74	1.99	2.19
1000	250	45.10	0A	0A

CASED AUTO TRANSFORMERS				
Ref	VA	VAT	P & P	Inc.
240V cable in 115V USA flat pin outlet				
20	5.95	6.43	1.04	1.23
75	7.73	8.35	1.23	1.43
150	10.01	10.81	1.23	1.43
200	9.92	12.01	1.57	1.77
250	12.17	13.15	1.57	1.77
500	19.17	20.70	1.77	1.99
1K	27.88	30.11	0A	0A
1.5K	26.02	35.48	0A	0A
2K	49.97	53.97	0A	0A

SCREENED MINIATURES				
Ref	mA	VAT	P & P	Inc.
238	200	3-0-3	2-78	0-59
212	1A, 1A	0-6-0-6	3-08	0-84
13	100	9-0-9	2-31	0-41
235	330	0-8-0-9	2-15	0-41
207	500, 500	0-8-9, 0-8-9	2-89	0-77
208	1A, 1A	0-8-9, 0-8-9	3-81	0-84
236	200, 200	0-15-0-15	2-15	0-41
214	300, 300	0-20-0-20	3-02	0-84
217	700 (DC)	20-12-0-12-20	3-68	0-84
206	1A, 1A	0-15-20-0-15-20	5-00	1-04
203	500, 500	0-15-27-0-15-27	4-31	1-04
204	1A, 1A	0-15-27-0-15-27	6-52	1-04
239	50	12-0-12	2-78	0-41

COMPONENT PACKS				
Ref	mA	VAT	P & P	Inc.
65	1W Metal Oxide Resistors.			
65	1W Metal Oxide Resistors.			
150	Mixed Value Capacitors.			
10	Reed Switches.			
50	Wire Wound Resistors.			
100	3000mf 30V Capacitors.			
25	Assorted presets.			
60	3 tag terminal strips.			
	Hardware, BA nuts, bolts.			
	200 Mixed Resistors.			
	10 mixed valve electrologic caps			
	39p mf to 2000 mf.			
	79p per pack.			
	43p P & P VAT incl.			

BRIDGE RECTIFIERS				
Ref	VAT	P & P	Inc.	Ref
100V	25A	£2.36		
200V	2A	£0.61		
200V	4A	£0.56		
400V	6A	£1.61		
500V PM7A6	12A*	£3.08		
	P & P 16p incl. VAT.			

TEST METERS				
Ref	Net	VAT	P & P	Inc.
AVO 8 MK5	88-10	95-15		
AVO 71	36-00	38-88		
AVO 73	48-70	52-60		
AVO MM5	32-95	35-89		
Wee Megger	74-85	80-19		
EM272	57-80	62-42		
DA116 digital	108-90	117-61		

15V RANGE				
Ref	VAT	P & P	Inc.	Ref
O.C.T. 15V.				
171	500 mA	2-26	0-49	
172	1A	3-20	0-84	
173	2A	3-88	0-84	
174	3A	4-05	0-93	
175	4A	6-19	1-04	

Special Offer				
Ref	VAT	P & P	Inc.	Ref
BE3	100V Line to 40 7/10W	£2.21		
BE4	0-120V x 2 (120V or 240V) Screen Sec. 9-0-9V 1 amp	£2.59		
BE5	15W matching trans. sec 150V suit EL84	£1.62		
BE6	Pri 0-220V Sec 4500V 10mA	£4.86		
BE7	0-110-120-220V Pn 240V sec 20V 1 amp	£1.62		
BE8	0-240 15-0-15V 2A £1.50 P & P 78p			
Ref 30	240-240 iso-lator 200VA	£4.54		
Ref 59	0-240V 25-0-25V 4A	£6.32		
BE9	Miniature Pri. 0-240V SCR Sec 12-0-12V 50mA	£9.7p		

MINI-MULTIMETER				
Ref	Net	VAT	P & P	Inc.
DC-1000V AC-1000V DC-100mA Res-150k Ω				
1000µV Bargain	£7.78	P & P 67p incl. VAT.		

S-DECS				
Ref	Net	VAT	P & P	Inc.
Solderless bread boarding				
S Dec 70 contacts	£3.35			
T Dec 208 contacts	£4.70			
U Dec "A" for I.C.s etc	£4.86			
U Dec "B" for I.C.s etc	£7.85			

Electronic Construction Kit				
Ref	Net	VAT	P & P	Inc.
Home electronic starter. Start simply and progress to a TRF radio or electronic organ. No soldering. All parts included in presentation box. Full instructions.	£8.95	P & P £1.04 incl. VAT.		

NEW RANGE TRANSFORMER				
Ref	Net	VAT	P & P	Inc.
Pri 120V or 220/240V. Sec 0-36-48 twice to give 36-0-36V 48-0-48V 72V or 92V.				
3A	15-88	1-60		
4A	20-27	1-99		
5A	28-77	2-32		

ABS PLASTIC BOXES				
Ref	Net	VAT	P & P	Inc.
inset brass nuts, internal slots to take P.C. cards, flush fitting lid.				
PB1 180mm x 62 x 40	70p			
PB2 100mm x 75 x 40	79p			
PB3 120mm x 100 x 45	94p			
*PB4 215mm x 130 x 85	£2.76			

MAGNETIC TO CERAMIC CARTRIDGE CONVERTOR				
Ref	Net	VAT	P & P	Inc.
Magnetic to Ceramic Cartridge Convertor MPA 30 Operating voltage 20-45V				
P & P 48p incl. VAT.	£3.94			

PANEL METERS				
Ref	Net	VAT	P & P	Inc.
43mm x 43mm				
82mm x 78mm				
0-50µA	£6.70	0-50µA	£7.24	
0-500µA	£6.43	0-500µA	£7.24	
0-1mA	£6.43	0-1mA	£7.24	
0-30V	£6.43	0-30V	£7.24	

250VA ISOLATOR				
Ref	Net	VAT	P & P	Inc.
0-200-220-240V. Sec 0-240V C.T. 250VA				
£5.62. P & P £1.04 incl. VAT. Ref. 62.				

ANEX SOLDERING IRONS				
Ref	Net	VAT	P & P	Inc.
15W	£4.27	Stand £1.71 + VAT 8%.		
25W	£4.27	Stand £1.71 + VAT 8%.		

CASED AUTO TRANSFORMERS				
Ref	VA	VAT	P & P	Inc.
20	5.95	6.4		





### A SELECTION FROM OUR STOCKS OF FULLY GUARANTEED FIRST QUALITY VALVES

1B3GT	0-84	6AX4GTB	1-13	6CY5	1-13	12AT6	0-68	ECF200	1-01	EM84	0-68	PCL81	0-73	PY82	0-62	UCC84	0-84
1R5	0-56	6AX5GT	1-46	6CY7	1-13	12AT7	0-56	ECF201	1-01	EM87	1-13	PCL82	0-80	PY88	0-79	UCC85	0-68
1X2B	1-35	6BA6	0-61	6D06B	1-63	12AU6	0-73	ECF801	1-07	EY81	0-82	PCL84	0-84	PY83	0-84	UCF80	0-84
5AT8	0-90	6BE6	0-54	6DT6	0-80	12AU7	0-53	ECF802	1-07	EY87	0-56	PCL86	0-96	PY500A	1-69	UCH42	1-13
5T4	0-84	6BF5	0-96	6DT8	0-90	12AV6	0-96	ECY42	1-24	EY88	0-82	PCL805	0-90	TT21	10-69	UCH81	0-73
5U4G	0-88	6BF6	0-84	6DW4	1-01	12AV7	1-13	ECY81	0-82	EY500A	1-89	PD510	3-78	TT22	10-69	UCL81	0-79
5U8	0-84	6BG6G	0-34	6E55	1-13	12AX7	0-62	ECH200	0-90	EZ80	0-56	PL36	1-24	U25	1-13	UCL82	0-84
5V4G	0-68	6BH6	0-96	6E55	1-69	12AY7	0-96	ECL80	0-88	EZ81	0-56	PL81	0-90	U26	1-13	UCL83	0-90
5X4G	0-90	6BJ6	1-35	6EW6	0-90	12BA6	0-73	ECL81	0-84	GY501	1-01	PL82	0-62	UAC80	0-65	UF41	1-13
5X8	1-01	6BJ7	0-73	6GH8A	0-90	12BF6	0-75	ECL82	0-88	GZ30	0-68	PL83	0-56	UAF41	0-90	UF80	0-56
5Y3GT	0-73	6BK4B	1-58	6GK5	0-79	12BH7A	0-84	ECL83	1-30	GZ32	0-73	PL84	0-84	UBC41	0-79	UF85	0-56
5Z4GT	0-73	6BN4A	1-01	6GK6	1-01	12BL6	0-79	ECL84	0-79	GZ33	4-28	PL504	1-35	UBC81	0-65	UL84	0-96
6AB7	0-68	6BN6	0-90	6J4	1-35	12B06	1-01	ECL85	0-73	OA2	0-70	PL508	1-58	UBF80	0-68	UM80	0-88
6AC7	0-90	6B07A	0-79	6J5GT	0-90	12BY7A	0-90	ECL86	0-96	OA3	0-81	PL802	3-15	UBF89	0-68	UM81	0-84
6AD8	0-68	6BR8A	1-35	6J6	0-62	12CU6	1-01	EF80	0-45	OB2	0-76	PY81	0-79	UBL21	1-01	UM84	0-51
6AF4A	0-90	6BS7	2-59	6J7	0-90	19A05	0-84	EF85	0-54	OB3	0-81						
6AG5	0-73	6BU8	0-96	6K5GT	0-84	19B66G	0-56	EF86	0-68	OC2	1-51						
6AG7	0-96	6BW7	1-13	6K6GT	0-96	35A3	0-79	EF92	1-13	OC3	0-92						
6AH6	1-07	6BZ6	0-73	6L6GT	1-24	35B3	0-73	EF97	0-79	OD3	0-81						
6AJ5	0-73	6C7	0-79	6N7GT	0-96	35C5	0-96	EF98	1-01	PAB80	0-51						
6AK5	0-62	6C4	0-62	6D7	1-01	50C5	1-13	EF183	0-79	PC86	1-01						
6AK6	0-84	6CSGT	0-68	6SA7	0-90	50E55	0-96	EF184	0-79	PC88	1-01						
6AK7	0-96	6C6	0-56	6SG7	0-90	DAF96	0-68	EF1200	1-01	PC96	0-56						
6AL5	0-45	6C8G	0-68	6SK7	0-40	DF96	0-68	EH90	0-68	PC97	1-07						
6AM6	0-79	6C8B	0-62	6SL7GT	0-79	DK92	1-13	EL33	2-81	PC900	1-13						
6AM8	0-79	6C67	0-79	6SN7GT	0-79	DL96	0-68	EL36	1-69	PC884	0-56						
6AN5	2-81	6CS8A	0-84	6S07	0-90	ECC84	0-68	EL81	0-68	PC85	0-68						
6AN6	0-96	6CM7	0-90	6SR7	0-90	ECC85	0-54	EL82	0-68	PC888	0-73						
6AO5	0-96	6CN7	1-35	6V8GT	0-90	ECC86	1-41	EL83	0-68	PC899	0-84						
6AS6	1-13	6C08	0-84	6X4	0-79	ECC88	0-84	EL84	0-73	PC189	1-13						
6AS7G	1-35	6CS7	0-96	6X5GT	0-68	ECC89	0-90	EL86	0-84	PCF80	0-96						
6AT6	0-84	6C16	1-13	6X8	0-90	ECC189	0-90	EL95	1-07	PCF82	0-51						
6AU6	0-56	6C18	1-13	12A6	0-68	ECF80	0-68	EL504	0-79	PCF84	0-73						
6AV6	0-84	6CW4	3-75	12AL5	0-73	ECF82	0-62	EM80	0-73	PCF86	0-84						
6AW8A	0-84	6CX8	1-13	12A05	0-68	ECF86	0-90	EM81	0-68	PCF806	1-13						

### OSCILLOSCOPE TUBES

current production. Made in USSR  
**One inch Tube Type 3L0 11.** This tube is a good replacement for 1CP31. Tube characteristics are identical with those of 1CP31. As the connections are different the tube is supplied complete with base, connection diagram and technical data **£12.00** plus £0.96 VAT. **Three-inch tube Type 3BP1.** This well known tube used in "PURBECK" Oscilloscope can be supplied for **£7.50** plus £0.65 VAT. 14-pin base for the above **£0.80** plus £0.06 VAT.

Prices are inclusive of VAT (at current rates) except where shown separately. Postage and packing charges are **£0.10** per £ subject to a minimum of **£0.30**. Minimum order charge for Approved Credit customers **£20.00**. Minimum Transaction Charge for mail orders **£1.00**.

OUR NEW 1978/1979 CATALOGUE IS NOW READY AND WILL BE SENT ON RECEIPT OF REMITTANCE FOR £0.30

## FOR YOUR GUIDANCE

# VALUE ADDED TAX

Unless otherwise shown, all prices in advertisements are inclusive of VAT. Where prices are exclusive, readers should ensure that they have added the correct amount of VAT before ordering.

Export orders are not subject to the addition of Value Added Tax.

## EVERYBODY'S DOING IT!

Doing what? Sending for the latest Home Radio Catalogue. It's the most comprehensive components catalogue you can get. 128 pages, about 2,500 items listed, and profusely illustrated. Now only £1.25 with a free bargain list. Send your cheque or postal order now.

**HOME RADIO COMPONENTS LTD.**  
Dept. PW, 234 London Road  
Mitcham, Surrey CR4 3HD

## OSMABET LTD

We make transformers amongst other things  
**LOW VOLTAGE TRANSFORMERS: Prim 240V ac.**  
6-3V 1-5A **£2.95**; 3A **£3.60**; 6A CT **£6.85**; 12V 1-5A **£3.35**; 3A CT **£6.85**; 6A CT **£6.50**; 15V 0-5A **£2.75**; 18V 1-5A CT **£6.85**; 24V 1-5A **£6.85**; 3A CT **£8.50**; 5A CT **£15.50**; 8A CT **£26.75**; 12A CT **£35.00**; 40V 3A CT **£12.25**.

**TWIN SEC TRANSFORMERS: Prim 240V ac.**  
6V 0-6A + 6V 0-6A; 9V 0-4A - 9V 0-4A; 12V 0-3A + 12V 0-3A; 20V 0-15A + 20V 0-15A; all at **£3.65** each; 15V 0-75A + 15V 0-75A **£5.65**; 15V 1-5A + 15V 1-5A **£7.75**; 18V 1A + 18V 1A **£6.85**; 18V 1-5A + 18V 1-5A **£8.50**; 20V 1-5A + 20V 1-5A **£8.50**; 12V 4A + 12V 4A **£10.50**; 25V 2A + 25V 2A **£10.50**.

**MIDGET RECTIFIER TRANSFORMERS: Prim 240V ac.**  
6-0-6V 1-5A or 9-0-9V 1A **£3.00** each; 12V-0-12V 1A or 20V-0-20V 0-75A **£3.75** each; 9-0-9V 0-3A or 12V-0-12V 0-25A or 20V-0-20V 0-15A **£2.85** each.

**LT TRANSFORMERS TAPPED SEC. prim 240V ac.**  
0-10-12-14-16-18V 2A **£6.50**; 4A **£8.25**; 0-12-15-20-24-30V 2A **£7.35**; 4A **£10.50**; 0-20-30-60V 1A **£8.25**; 2A **£10.50**; 0-40-50-80-80-100-110V 1A **£10.50**.

**MAINS TRANSFORMERS SPECIAL OFFER:**  
prim 240V ac.  
250-0-250V 60Ma, 6-3V 1A **£2.00**; 250V 100Ma, 6-3V 2A **£3.00**; 9V 3A **£2.50**, 25V 0-3A **£1.00**.

**LOUDSPEAKERS**  
2 1/2in 8Ω, 2 1/2in 8Ω or 25Ω, 2 1/2in 8Ω, 3in 25Ω, 3 1/2in 3, 8, 16 or 80Ω, all at **1-25** each; 5 x 3in 4, 15 or 25Ω, **£1.50**; 7 x 4in 4, 8, 16, 25 or 80Ω, **£1.75**; 8 x 5in 4, 8 or 25Ω, **£3.00**; 8in 8Ω, **£2.50**.

**"INSTANT" BULK CASSETTE/TAPE ERASER**  
Instant erasure of cassettes, and any diameter of tape spools, demagnetises tape heads. **200/240V ac. £6.00**

**POWER SUPPLY, TWIN OUTPUT: Prim 240V ac.**  
New, British manufacture, smoothed d.c. output 20V 1-5A, plus stabilised output of 15V 100 Ma, plus 12V ac 0-5A output, complete with diagram. **£3.50**

**EDGEWISE LEVEL METER FSD 200/μA**  
Size 19 x 18 x 20mm 8000 **£1.10**

**CHARGING METERS 1 1/2** ins diameter  
2A or 3A **£1.25** each; 5A or 10A **£1.50** each.

**SYNCHRONOUS GEARED MOTORS, 240V ac.**  
Brand new, built in gear box, 1 or 20 RPH, **£1.25** each.

**O/P TRANSFORMERS FOR VALVE AMPLIFIERS**  
P.P. sec tapped 3-8-15Ω, A-A 6k, 30W **£15.25**; A-A 3K, 50W **£22.75**; 100W (EL31, KT88, etc.) **£31.25**.

**G.E.C. MANUAL OF POWER AMPLIFIERS**  
Covers valve amplifiers 30W to 400W **£1.00**.

**MULTIWAY SCREENED CABLE, PVC COVERED**  
36 way **£1.90**; 25 way **75p**; 14 way **50p**; 8 way **25p**; 4 way **20p**; 2 way **10p**; 1 way **8p**; 4 way individually screened 25p per metre, fig 8 twin stereo do screened **15p**, metre.

**MAINS CABLE**  
4 way, 3A **30p** metre; fig 8 for loudspeakers etc. **£5.00** 100 metres.

**CONDENSERS**  
Electrolytic, 400/400V **75p**; 2000/30V **30p**; 1200/75 **50p**; 2200/40V **40p**; 8-8/450V **40p**; Paper tubular, W/E 4/160V, 6/160V, 2/150V, 0-1/2000V **25p** each.

**CARRIAGE EXTRA ON ALL ORDERS**  
**ALL PRICES INCLUDE V.A.T.**  
Callers by appointment only. S.A.E. Enquiries, Lists.  
**46, Kenilworth Road, Edgware, Middx.**  
**HA8 8YG. Tel: 01-958 9314**



# Why buy colour films?

When you get a Kodak colour film

# FREE

for every one you send in for processing by the Practical Electronics Colour Print Service!



## Send no money

But don't send any money until you see the colour of your prints. We're so confident in the reliability of the service and the quality of our prints, every one of which is checked by professionals at our laboratories.

## Luxury colour prints

You'll be amazed at the crisp, sharp, high-definition sheen finish of the prints we supply . . . borderless to give you maximum picture area. And coming with the prints will be your FREE Kodak colour film, worth around £1, the same size as the one you sent us for processing.

## Unbeatable value

What about prices? Ours are certainly much less than those you would pay in most shops—quite apart from the free film you get every time we develop and print for you.

Our Colour Print Service charges you only 15p for each print, plus 85p towards developing, postage and packing. The minimum charge is 85p inc. VAT (that is, if no prints can be made). The offer is limited to the UK, Eire, CI and BFPO.

## Reliability at less cost

Photography can cost you a lot less these days. If you know how to go about it. Like the hundreds of thousands of magazine readers who are

delighted with this reliable Colour Print Service — and the replacement films that come FREE to every customer! So why don't you give it a try?

Here's what you do. Send us any make of colour print film inside the envelope enclosed in this issue. Or fill in the coupon below and send it with your film in a strong envelope to: The Practical Wireless Colour Print Service, Freepost, Teddington, Middlesex, TW11 8BR. No stamp is required.

## More benefits to you

You benefit in two additional ways. Firstly, you enjoy a personal service with every care taken over each individual order. And secondly, you pay only for what you get—with no credit vouchers as with many other companies. An invoice comes with your prints so it's a straight business transaction.

Use this label if you haven't got an envelope, or pass it to a friend who might like to take advantage of our offer. It is used to send your prints and free film.

*(Offer Exc. Minolta & Sub-miniature. Roll Film 10p surcharge 400 ASA 20p surcharge).*

**From: Practical Wireless Colour Print Service,  
Freepost, Teddington, Middlesex TW11 8BR**

Mr/Ms \_\_\_\_\_

Address \_\_\_\_\_

Postcode \_\_\_\_\_



Speakers from 1½ inch to 15 inch; megaphone, PA horns, crossovers etc. They're all in our catalogue. Send the coupon now!



A genuine 150W per channel stereo disco to build yourself. Full specification in our catalogue.



Our catalogue even includes some popular car accessories at marvellous prices.



Our catalogue describes a wide range of plugs and sockets, all at marvellous prices. See cat. pages 114 to 129 for details.



61-note touch-sensitive piano to build yourself. Full specification in our catalogue.



A very high quality 40W per channel stereo amplifier with a superb specification and lots of extras. Full construction details in our catalogue.



A digitally controlled stereo synthesiser the 5600S with more facilities than almost anything up to £3,000. Build it yourself for less than £700. Full specification in our catalogue.



A hi-fi stereo tuner with medium and long wave, FM stereo and UHF TV sound! Full construction details in our catalogue.



These are just some of the metal cases we stock. There are dozens of plastic ones to choose from as well. See pages 52 to 57 of our catalogue.

# MAPLIN

**ELECTRONIC SUPPLIES LTD**

All mail to:-  
 P.O. Box 3, Rayleigh, Essex SS6 8LR.  
 Telephone: Southend (0702) 554155.  
 Shop: 284 London Road,  
 Westcliff-on-Sea, Essex.  
 (Closed on Monday).  
 Telephone: Southend (0702) 554155.



Multimeters, analogue and digital, frequency counter, oscilloscopes, and lots, lots more at excellent prices. See cat. pages 106 and 183 to 188 for details.



A 10-channel stereo graphic equaliser with a quality specification at an unbeatable price when you build it yourself. Full specification in our catalogue.



A massive new catalogue from Maplin that's even bigger and better than before if you ever buy electronic components, this is the one catalogue you must not be without. Over 280 pages - some in full colour - it's a comprehensive guide to electronic components with hundreds of photographs and illustrations and page after page of invaluable data.

Our bi-monthly newsletter contains guaranteed prices, special offers and all the latest news from Maplin.



A superb range of microphones and accessories at really low prices. Take a look in our catalogue - send the coupon now!

**Post this coupon now for your copy of our 1979-80 catalogue price 75p.** Please send me a copy of your 280 page catalogue as soon as it is published (8th Jan. 1979). I enclose 75p but understand that if I am not completely satisfied I may return the catalogue to you within 14 days and have my 75p refunded immediately. If you live outside U.K. send £1 or ten International Reply Coupons.

NAME \_\_\_\_\_

ADDRESS \_\_\_\_\_