

# PRACTICAL WIRELESS

OCTOBER  
1971

20p

**EXTRA INSIDE**


**8 PAGE SUPPLEMENT**

**SMALL  
WORKSHOP  
TOOLS**

*plus*

Wall Chart

**CIRCUIT  
BUILDING  
BRICKS**

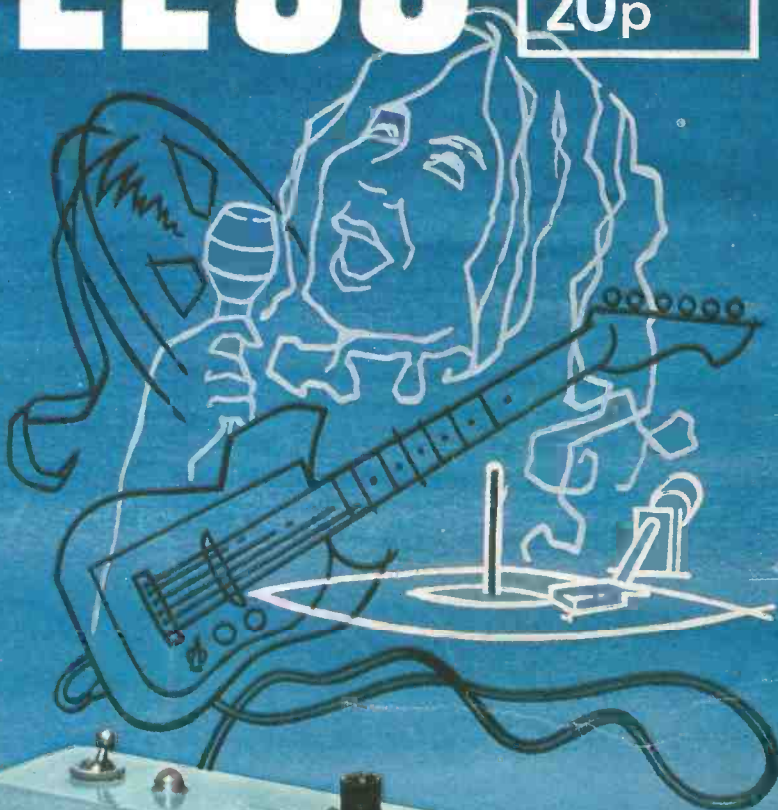

**MODULAR AUDIO MIXING SYSTEM**

# ADCOLA Soldering Instruments add to your efficiency

## THE NEW 'INVADER'

### ADCOLA L.646

for Factory Bench Line Assembly

A precision instrument—supplied with standard 3/16" (4.75 mm) diameter, detachable copper chisel-face bit\*. Standard temp. 360 c at 23 watts. Special temps. from 250°c—410°c.

\*Additional Stock Bits (illustrated) available

#### COPPER

B 38  $\frac{1}{8}$ " — 3.2 mm CHISEL FACE

B 14  $\frac{3}{32}$ " — 2.4 mm CHISEL FACE

B 24  $\frac{1}{4}$ " — 4.75 mm SCREWDRIVER FACE

B 12  $\frac{3}{16}$ " — 4.75 mm EYELET BIT

B 58  $\frac{1}{2}$ " — 6.34 mm CHISEL FACE

#### LONG LIFE


B 42 LL  $\frac{1}{4}$ " — 4.75 mm CHISEL FACE

B 38 LL  $\frac{1}{8}$ " — 3.2 mm CHISEL FACE

B 14 LL  $\frac{3}{32}$ " — 2.4 mm CHISEL FACE

B 44 LL  $\frac{1}{4}$ " — 4.75 mm SCREWDRIVER FACE

PRICE  
£1.85

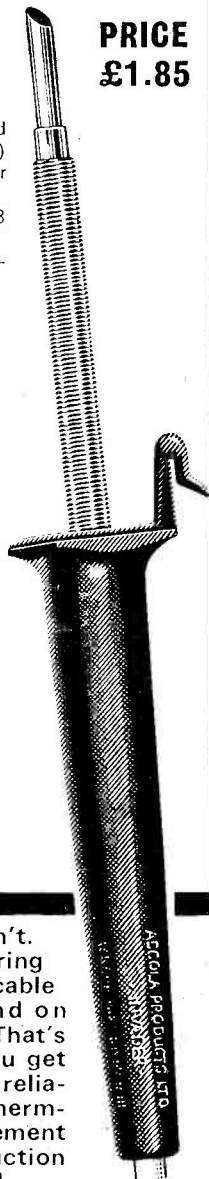

Don't take chances. We don't. All our ADCOLA Soldering Instruments are of impeccable quality. You can depend on ADCOLA day after day. That's why they're so popular. You get consistent good service... reliability... from our famous thermally controlled ADCOLA Element and the tough steel construction of this ideal production tool.

# ADCOLA

(Regd Trade Mark)

**ADCOLA PRODUCTS LTD.,**

(Dept. M), ADCOLA HOUSE, GAUDEN RD., LONDON, S.W.4.  
Telephone: 01-622 0291/3 • Telegrams: Soljoint London Telex • Telex: Adcola London 21851

\* Write for price list and catalogue



**for fast, easy, reliable soldering**

Contains 5 cores of non-corrosive flux, instantly cleaning heavily oxidised surfaces. No extra flux required.

### SAVBIT ALLOY ALSO REDUCES COPPER BIT WEAR.

Economically packed for general electrical and electronic soldering. 75ft. 18 gauge on plastic reel. Recommended retail price **75p**  
Size 12



**THIN GAUGE SOLDER, ESSENTIAL FOR** soldering small components and thin wires. High tin content, low melting point, 60/40 alloy, 170ft. 22 gauge on plastic reel. Recommended retail price **75p**  
Size 10



### A RANGE OF SOLDERS IN HANDY DISPENSERS.

REF. ALLOY SWG  
19A 60/40 18 18p\*  
Size 5 (Ultra-Savbit)  
15 60/40 22 22p\*  
\*Recommended Price



**INVALUABLE FOR STRIPPING FLEX, THE NEW AUTOMATIC OPENING BIB WIRE STRIPPER AND CUTTER,** easily adjustable for all standard diameters. Plastic covered handles can also be used as wire cutter. Recommended retail price **50p**




From Electrical and Hardware shops. If unobtainable, write to: **Multicore Solders Ltd., Hemel Hempstead, Herts.**


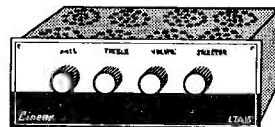
## RANGE OF SOLID STATE A.C. MAINS AMPLIFIERS

Employing only high grade components and transistors.  
**LTA 15 WATT AMPLIFIER**


**HIGH FIDELITY OUTPUT SWITCHED INPUTS FOR GRAM, 'MIKE', TAPE, AND RADIO**  
Frequency Response 10-40,000 cps-3dB. Bass Control-17dB to-16dB at 40cps. Treble Control-17dB to-14dB at 14Kcs. Hum and Noise-80dB. Harmonic Distortion 0.2% at rated output. Output for 3-8-15 ohm Loudspeakers.



Recommended **£19**  
Retail Price  
Size 9 1/2 x 3 1/2 x 5 1/2 in. approx.
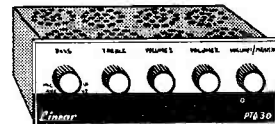
### PTA30 HI-FI PUBLIC ADDRESS AMPLIFIER

**A SUCCESSOR TO OUR POPULAR CHORCHORD 30 WATT UNIT**  
Input Sensitivity 2 mv (max.)  
Output 30 watts.  
Output Sockets for Loudspeaker or combination of Speakers with total impedance between 3 ohms and 30 ohms. Three individually controlled Inputs for mixing purposes. Housed in fully enclosed stove enamelled steel case. Controls Vol. (1) Vol. (2) Vol. (3) with mains switch, Treble 'lift', and 'cut', Bass 'lift' and 'cut'.



Recommended **£24**  
Retail Price  
Size 12 x 3 1/2 x 6 in. approx.

**AN IDEAL UNIT FOR VOCAL AND INSTRUMENTAL GROUPS. SUITABLE FOR ANY KIND OF 'MIKE' AND INSTRUMENT PICK-UP, ALSO FOR RADIO, TAPE OR GRAM.**

Please send a stamped addressed envelope for full descriptive details of above units.


If required an attractive wood cabinet with veneer finish can be supplied for any model.  
Prices from **£3.50**

**AVAILABLE FROM YOUR LOCAL HI-FI DEALER**  
Wholesale and Retail enquiries to:

**LINEAR PRODUCTS LTD,**  
Electron Works, Armley, Leeds

## SUPER SPEAKER BARGAINS WHARFEDALE DENTONS

A compact system sold in matched pairs for a perfectly balanced stereo system. Each Denton contains an 8in. bass unit with 3in. pressure unit, coupled by a Wharfedale crossover network. Rated input: 15 watts maximum. Frequency response: 65-17,000Hz. Impedance: 4/8 ohms. Cabinet 9 1/2in. x 14in. x 8 1/2in. These most attractive units are available in oiled teak, white or walnut and are small enough to blend in with most surroundings.

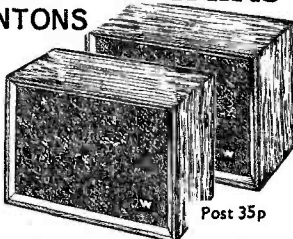

Post 35p

LIST PRICE £39.00 **£28.00** Walnut White

**£27.00** Teak


## WHARFEDALE TRITONS

A new and exciting addition to the Wharfedale range, this three speaker system will satisfy the most ardent Hi-Fi enthusiast. Shelf or floor standing—hand finished in oiled teak or polished walnut. Frequency response 55-22,000Hz. C.A.B. Dome pressure unit. Bass unit 8in. Mid-range unit 5in. Treble unit 2in. Impedance 8 ohms. Size 2 1/2in. x 9 1/2in. x 9in.

LIST PRICE £59.90

**LASKY'S £36.00** Teak

**PRICE £38.00** Walnut White

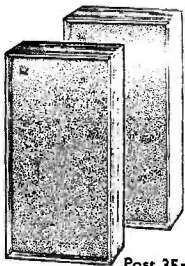

Post 35p.

## BSR McDONALD MP60

High precision low-mass counterbalanced pick-up arm, heavy balanced turntable, simple to operate controls, viscous cueing device, slide in cartridge carrier, 4 pole motor.

**LASKY'S PRICE £12.50** Post 35p

### BSR McDONALD UNITS & PACKAGES

A. Chassis only. B. Complete with Lasky's plinth and cover. C. Complete with Lasky's plinth, cover and AD76K cartridge. D. Comp. wired on BSR plinth with cover. E. As D plus AD76K cartridge.

| MODEL | A      | B      | C      | D      | E      |
|-------|--------|--------|--------|--------|--------|
| 610   | £15.45 | £18.75 | £22.50 | £24.50 | £28.50 |
| 510   | £13.45 | £16.95 | £20.75 | £22.00 | £26.00 |
| 310   | £9.95  | £13.45 | £17.25 | £21.00 | £23.50 |
| MP60  | £12.50 | £15.75 | £19.50 | £21.50 | £25.50 |



## GARRARD UNITS AND PACKAGES

### GARRARD SL 55B

Four speed autochanger

**LASKY'S PRICE £10.50** Post 35p



|                                     |        |
|-------------------------------------|--------|
| Garrard SP25 Mk. III                | £11.50 |
| Garrard SP25 Mk. III wired          | £12.00 |
| Garrard SP25 Mk. III with 9TA cart. | £13.95 |

|                               |        |
|-------------------------------|--------|
| Garrard SL40B                 | £9.95  |
| Garrard AP76 without cart.    | £20.95 |
| Garrard 3000 with 9TA cart.   | £10.50 |
| Garrard 2025TC with 9TA cart. | £9.85  |

## GARRARD PACKAGES

|                                                                        |     |
|------------------------------------------------------------------------|-----|
| Garrard AP76 with AD76K cart. and Lasky's plinth and cover             | £35 |
| Garrard AP76 with Shure M44E cart. and Lasky's plinth and cover        | £40 |
| Garrard SP25 Mk. III, AD76K cart. and Lasky's plinth and cover         | £20 |
| Garrard SP25 Mk. III, Micro M2100/e cart. and Lasky's plinth and cover | £25 |

Post on packages 50p

## LASKY'S NEW LOW NOISE CASSETTES FROM THE USA

| Type  | Singles | 5     | 10    | 20     |
|-------|---------|-------|-------|--------|
| C-60  | 41p     | £1.82 | £3.41 | £6.55  |
| C-90  | 63p     | £3.04 | £5.78 | £10.89 |
| C-120 | 96p     | £4.13 | £7.43 | £13.41 |

Post Each 5p. 5-20p. 10-25. 20-50p.

## SONY 8FC 59W SCOOP

### DIGITAL AM/FM CLOCK RADIO

Digital Alarm Clock Radio. The digital clock shows you the time minute by minute with matchless accuracy and once set the Digimatic will wake you up at the same time every morning without having to be re-set. The radio section features Sony's unique sleep button, you fall gently to sleep lulled by the sweet tone of the radio, which switches itself off at a predetermined time. Available in either black, white or red (8FC-59W). Frequency range 530-1,605KHz (AM); 87-108MHz (FM). Uses 8 transistors and 8 semi-conductors, built-in ferrite aerial and 3 1/2in. loudspeaker. Power requirements: 230V AC 50Hz. Dimensions: 12 1/2in. x 3 1/2in. x 5 1/2in.



LIST PRICE £30.00

**LASKY'S PRICE £22.50** Post free in U.K.

## KATONE AM/AIRCRAFT PORTABLE RADIO


### BATTERY/MAINS

A combined battery and mains portable of exceptionally attractive design. Housed in a leatherette covered case, size 8 1/2in. x 5 1/2in. x 3 1/2in., fitted with an 8-section external telescopic aerial for FM and internal ferrite rod for MW wave bands, and clear easy-to-read dial with logging scale. Wave band coverage is FM 88-108MHz, AM 535-1,600KHz. A highly selective circuit using 9 transistors and 9 semi-conductors operating from either 4 x 1.5 volt torch batteries or direct from 230 volts 50Hz AC house mains, from a built-in mains unit. A socket is fitted for a personal earphone. Easy-to-use silver colour knobs, with "woodgrain" panel enhances the appearance of this fine radio.



**LASKY'S PRICE £9.95** Post 15p

## DIGITAL CLOCK SCOOP

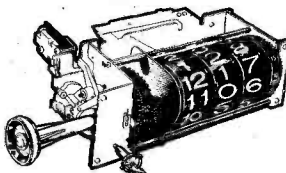

EXCLUSIVELY  
FROM LASKY'S

for you to mount into any housing. The clock measures 4 1/2 W x 1 1/2 H x 3 1/2 D (overall from front of drum to back of switch). SPEC.: 210/240V a.c., 50Hz operation; switch rating 250V 5A. Complete with instructions. HUNDREDS OF APPLICATIONS. COMPLETE WITH KNOBS.

**LASKY'S PRICE £6.95** Post 18p

- MADE ESPECIALLY FOR LASKY'S BY FAMOUS MAKER
  - MAINS OPERATION
  - 12-HOUR ALARM
  - AUTO "SLEEP" SWITCH
  - HOURS, MINUTES AND SECONDS READ-OFF
  - FORWARD AND BACKWARD TIME ADJUSTMENT
  - SILENT OPERATION SYNCHRONOUS MOTOR
  - SHOCK AND VIBRATION PROOF
  - BUILT IN ALARM BUZZER
- SPECIAL QUOTES FOR QUANTITIES

## TRIO HS.1 & HS.2 STEREO HEADPHONE BARGAINS

Models HS-1 and HS-2. Both these sets by TRIO offer really superb stereo reproduction in a lightweight, fully adjustable headset designed for optimum comfort. Listening fatigue is unknown with TRIO headphones. Brief spec. both models: input imp. 80 nominal (matching 4 to 80); max. input 0.5W; frequency response 20-19 kHz; output sensitivity at 1mW input; HS-1 118 dB, HS-2 111 dB; weight 0.66lbs. Identical in appearance—both models are finished in ivory with contrasting foam filled ear pads and head band.



LIST PRICE £8.40

LIST PRICE £6.75

**HS.1 £5.20p HS.2 £4.15p** Post 18p

## Lasky's Radio Limited

Branches

207 EDGWARE ROAD, LONDON, W.2 Tel: 01-723 3271

33 TOTTENHAM C. RD., LONDON, W.1 Tel: 01-636 2605

Open all day 9 a.m. - 6 p.m. Monday to Saturday

152/3 FLEET STREET, LONDON, E.C.4 Tel: 01-353 2833

Open all day Thursday, early closing 1 p.m. Saturday

The Home of High Fidelity

42-45 TOTTENHAM CT. RD., LONDON, W.1 Tel: 01-580 2573

Open all day 9 a.m. - 6 p.m. Monday to Saturday

**NEW CITY BRANCH NOW OPEN**

109 FLEET STREET, LONDON, E.C.4 Tel: 01-353 5812

Open all day Thursday, early closing 1 p.m. Saturday

ALL MAIL ORDERS AND CORRESPONDENCE TO: 3-15 CAVELL ST., TOWER HAMLETS, LONDON, E.1 Tel: 01-790 4821







# THE RADIO CONSTRUCTOR

## September Issue

Constructional Articles include

### SEMI-CONDUCTOR GATE-DIP OSCILLATOR

Bringing the grid-dip oscillator up to date with the aid of a modern low-cost field-effect transistor. The unit described is capable of operation from 4 to 145MHz.

### BRAKE LIGHT FAILURE INDICATOR

### AUTOMATIC MORSE PRACTICE KEYS

### HIGH IMPEDANCE TRANSISTOR PRE-AMPLIFIER

PLUS

- MORE CONSTRUCTIONAL PROJECTS
- NEWS COVERAGE
- SHORT WAVE SCENE
- SUPPORTING FEATURES
- DATA SHEET 54

## ON SALE NOW 20p

Copies may also be obtained direct from the Publishers  
24p including postage. Published by:  
Data Publications Ltd., 57 Maida Vale, London W.9

### 4-STATION INTERCOM



£6.75

Solve your communication problems with this 4-Station Transistor Intercom system (1 master and 3 Subs), in de-luxe plastic cabinets for desk or wall mounting. Call/talk/listen from Master to Subs and Subs to Master. Ideally suitable for Business, Surgery, Schools, Hospital, Office and Home. Operates on one 9V battery. On/Off switch. Volume control. Complete with 3 connecting wires each 66ft. and other accessories. P. & P. £0.40.

### MAINS INTERCOM

No batteries—no wires. Just plug in the mains for instant two-way loud and clear communication. On off switch and volume control. Price £13.95 P. & P. £0.25.

### INTERCOM/BABY ALARM



OUR PRICE ONLY £3.35

Same as 4-Station Intercom for two-way instant communication. Ideal as Baby Alarm and Door Phone. Complete with 66ft. connecting wire. Battery 13p. P. & P. £0.25.



£2.98

Why not boost business efficiency with this incredible De-luxe Telephone Amplifier. Take down long telephone messages or converse without holding the handset. A useful office aid. On/Off switch. Volume Control. Battery 13p. extra. P. & P. 20p. Full price refunded if not satisfied in 7 days.

WEST LONDON DIRECT SUPPLIES (P.W.S.)  
189 KENSINGTON HIGH STREET, LONDON, W.8.

### The Unique MULTI-MINI TWIN-VICE



An extra "Pair of hands" for those tricky jobs

ASSEMBLY—SOLDERING—GLUING—WIRING—DRILLING ETC.

- INDEPENDENT ADJUSTMENT OF THE TWO VICE HEADS TO ANY ANGLE WITH POSITIVE LOCKING.
- JAWS WILL FIRMLY GRIP, ROUND, FLAT, SQUARE, OR HEXAGONAL PARTS.

TWIN VICE: £5.90 (24p P & P)

ALSO AVAILABLE

SINGLE VICE: £3.37½ (20p P & P)


COVENTRY MOVEMENT CO LTD.

Dept. P.W.3

BURNSALL ROAD, COVENTRY CV5 6BU

STD 0203-74363
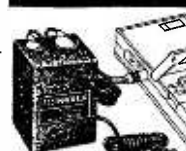
### MAINS UNITS for all types of TRANSISTOR EQUIPMENT



### RUN YOUR TAPE RECORDER OFF A.C. MAINS

Mains unit supplied complete and ready to plug into your cassette recorder. (State voltage, model and plug required.)

£2.50 P. & P. 15p

### 12 VOLT CAR BATTERY UNIT

Enables you to run your cassette recorder off 12V. car battery. (State 6v or 7½v output, model and plug required.)

£2.00 P. & P. 15p

### PLUS-3

### MAINS UNIT

Provides three separate switched output voltages 6v, 7½v, and 9v. D.C. attractive case with indicator light, mains lead output socket, plug and lead. Size 4½ x 3½ x 2½ in.

£3.00 P. & P. 15p.



Extra lead with plug to fit your cassette recorder 50p. (State model and plug required.)

MAINS UNIT FOR ALL TRANSISTOR RADIOS, ETC., USING PP3 TYPE BATTERY. (ALSO AVAILABLE FOR 6V.)

£1.15 P. & P. 10p.

### MAIN UNITS

For single outputs, 6v, 9v, 12v, 18v, £2.00. For two separate outputs, 4½v + 4½v, 6v + 6v, 9v + 9v, £2.50. P. & P. 15p. per unit. (Please state outputs reqd.)

All units are completely isolated from mains by double wound transformer ensuring 100% safety.

R.C.S. PRODUCTS (RADIO) LTD.  
(Dept. P.W.), 31 Oliver Road, London, E.17



# BI-PRE-PAK LIMITED

## FULLY TESTED AND MARKED

|               |      |                          |      |
|---------------|------|--------------------------|------|
| AC107         | £p   | OC170                    | £p   |
| AC126         | 0-15 | OC171                    | 0-23 |
| AC127         | 0-17 | OC200                    | 0-25 |
| AC128         | 0-13 | OC201                    | 0-25 |
| AC176         | 0-25 | 2G301                    | 0-13 |
| ACY17         | 0-15 | 2G303                    | 0-13 |
| AF239         | 0-37 | 2N711                    | 0-50 |
| AF186         | 0-50 | 2N1302-3                 | 0-20 |
| AF139         | 0-37 | 2N1304-5                 | 0-25 |
| BC154         | 0-25 | 2N1306-7                 | 0-30 |
| BC171 = BC107 | 0-13 | 2N1308-9                 | 0-35 |
| BC172 = BC108 | 0-13 | 2N3819FET                | 0-45 |
| BF194         | 0-15 |                          |      |
| BF274         | 0-15 | <b>Power Transistors</b> |      |
| BFY50         | 0-20 | OC20                     | 0-50 |
| BSY25         | 0-57 | OC23                     | 0-30 |
| BSY26         | 0-13 | OC25                     | 0-25 |
| BSY27         | 0-13 | OC26                     | 0-25 |
| BSY28         | 0-13 | OC28                     | 0-30 |
| BSY29         | 0-13 | OC35                     | 0-30 |
| BSY95A        | 0-15 | OC36                     | 0-37 |
| OC41          | 0-13 | AD149                    | 0-30 |
| OC44          | 0-13 | AUY10                    | 1-25 |
| OC45          | 0-13 | 25034                    | 0-25 |
| OC71          | 0-13 | 2N3055                   | 0-63 |
| OC72          | 0-13 |                          |      |
| OC73          | 0-17 | <b>Diodes</b>            |      |
| OC81          | 0-13 | AAY42                    | 0-10 |
| OC81D         | 0-13 | OA95                     | 0-19 |
| OC83          | 0-20 | OA79                     | 0-09 |
| OC139         | 0-13 | OA81                     | 0-09 |
| OC140         | 0-17 | IN9114                   | 0-07 |

# FREE!

PACKS OF YOUR OWN CHOICE UP TO THE VALUE OF 50p WITH ORDERS OVER £4

## CLEARANCE LINES

|                                          |      |       |      |
|------------------------------------------|------|-------|------|
| SL403D Audio Amp.                        | 1.10 | 10.50 | 50+  |
| IC 709C Linear Opp. Amp.                 | 2-00 | 1-95  | 1-80 |
| A.E.I. Fully marked & tested             | 50p  | 40p   | 35p  |
| Gates                                    | 25p  | 22p   | 20p  |
| A.E.I. Fully marked & tested             | 50p  | 40p   | 30p  |
| Flipflops                                | 5p   | 5p    | 4p   |
| OC71/72 Fully tested, unmarked           | 25p  | 20p   | 15p  |
| Matched Sets 1-OC44, 2-OC45              |      |       |      |
| Per set                                  | 15p  | 12p   | 10p  |
| Matched Sets, OC45, 1st & 2nd            | 15p  | 15p   | 12p  |
| I.F. Per set                             |      |       |      |
| TIC45 Thyristors, 6A, 60V Texas          | 3p   | 3p    | 2p   |
| OA47 Gold bonded Diodes, marked & tested | 5p   | 4p    | 3p   |
| 1W Zener Diodes                          | 5p   | 4p    | 3p   |
| 6.8V, 7.5V, 24V, 27V, 30V & 43V          |      |       |      |
| 10W Zener Diodes:                        | 20p  | 17p   | 15p  |
| 7.5V, 11V, 13V, 20V & 100V               |      |       |      |
| Micro Switches, S/P, C/O Popular size    | 25p  | 20p   | 15p  |
| 1 Amp Bridge Rectifiers 25V, RMS         | 25p  | 22p   | 20p  |

1 Amp Plastic Rectifiers. These are voltage, reverse Polarity and other rejects from the BY 127 range. Ideal for low voltage Power Units etc. Price £1 per 100.

## COLOUR T.V. LINE OUTPUT TRANSFORMERS

Designed to give 25kV when used with PL509 and PY500 valves. As removed from colour receivers at the factory.

ONLY £1 each  
Post and packing 23p.

## BUMPER BUNDLES

These parcels contain all types of surplus electronic components, printed panels, switches, potentiometers, transistors and diodes, etc.

2 LBS IN WEIGHT FOR £1

Post and packing 25p.

## OUR VERY POPULAR 3p TRANSISTORS

FULLY TESTED & GUARANTEED

TYPE "A" PNP Silicon alloy, metal TO-5 can. 25300 type, direct replacement for the OC200/203 range.

TYPE "B" PNP Silicon, plastic encapsulation, low voltage but good gain, these are of the 2N3702/3 and 2N4059/62 range.

TYPE "E" PNP Germanium AF or RF—please state on order. Fully marked and tested.

TYPE "F" NPN Silicon plastic encapsulation, low noise amplifier of the 2N3708, 9, 10, 11.

## BULK BUYING CORNER

NPN/PNP Silicon Planar Transistors TO-18 mixed untested similar to 2N706-6A-8, BSY26-7A9-95A and BCY70 etc. £4-25 per 500. £8 per 1000.

NPN Silicon Planar transistors plastic encapsulation untested similar to 2N3707 to 3711. £4-25 per 500. £8 per 1000.

Silicon planar diodes do-7 glass similar to OA200-202, BAY31-36. £4-50 per 1000.

NPN/PNP Silicon planar transistors plastic TO-18 similar to BC113-4, BC153-4, BF153-160, etc. £4-25 per 500. £8 per 1000.

NPN Silicon planar transistors TO-5 can similar to BC142/3, BFY50-2-3. £5-25 per 500. £10 per 1000.

OC44, OC45 transistors fully marked and tested 500 to 999, 8p each, 1000+ 6p each.

OC71 transistors fully marked and tested, 500 to 999, 6p each, 1000+ 5p each.

A amp miniature plastic diodes IN4001 at 500 to 999, 4p each, 1000+ 3p each. IN4004 at 500 to 999, 5p each, 1000+ 4p each. IN4006 at 500 to 999, 6p each, 1000+ 5p each. IN4007 at 500 to 999, 8p each, 1000+ 7p each.

## NEW UNMARKED UNTESTED PAKS

|     |     |                                                                  |     |
|-----|-----|------------------------------------------------------------------|-----|
| B66 | 150 | Germanium Diodes Min. glass type                                 | 50p |
| B83 | 200 | Trans. manufacturers' rejects all types NPN, PNP, Sil. and Germ. | 50p |
| B84 | 100 | Silicon Diodes DO-7 glass equiv. to OA200, OA202                 | 50p |
| B86 | 50  | Sil. Diodes sub. min. IN914 and IN916 types                      | 50p |
| B88 | 50  | Sil. Trans. NPN, PNP equiv. to OC200/1, 2N706A, BSY95A, etc.     | 50p |
| B60 | 10  | 7 Watt Zener Diodes Mixed Voltages                               | 50p |
| H6  | 40  | 250mW. Zener Diodes DO-7 Min. Glass Type                         | 50p |
| H10 | 25  | Mixed volts, 1½ watt Zeners. Top hat type                        | 50p |
| H11 | 30  | MAT Series "alloy" pnp Transistors                               | 50p |
| H15 | 30  | Top Hat Silicon Rectifiers, 750mA. Mixed volts                   | 50p |
| H16 | 8   | Experimenters' Pak of Integrated Circuits. Data supplied         | 50p |
| H20 | 20  | BY126/7 Type Silicon Rectifiers, 1 amp plastic. Mixed volts.     | 50p |

## NEW TESTED AND GUARANTEED PAKS

|     |     |                                                                   |     |
|-----|-----|-------------------------------------------------------------------|-----|
| B2  | 4   | Photo Cells, Sun Batteries. 0.3 to 0.5V, 0.5 to 2mA.              | 50p |
| B79 | 4   | IN4007 Sil. Rec. diodes, 1,000 PIV lamp plastic                   | 50p |
| B81 | 10  | Reed Switches, mixed types large and small                        | 50p |
| B99 | 200 | Mixed Capacitors. Postage 13p Approx. quantity, counted by weight | 50p |
| H4  | 250 | Mixed Resistors. Postage 10p. Approx. quantity counted by weight  | 50p |
| H7  | 40  | Wirewound Resistors. Mixed types and values. Postage 8p.          | 50p |
| H8  | 4   | BY127 Sil. Recs. 1000 PIV. 1 amp. plastic                         | 50p |
| H9  | 2   | OC71 Light Sensitive Photo Transistor                             | 50p |
| H12 | 20  | NKT155/259 Germ. diodes, brand new stock clearance                | 50p |
| H18 | 10  | OC71/75 uncoded black glass type PNP Germ.                        | 50p |
| H19 | 10  | OC81/81D uncoded white glass type PNP Germ.                       | 50p |
| H28 | 20  | OC200/1/2/3 PNP Silicon uncoded TO-5 can                          | 50p |
| H29 | 20  | OA47 gold bonded diodes coded MCS2                                | 50p |

## F.E.T. PRICE BREAKTHROUGH!!

This field effect transistor is the 2N3823 in a plastic encapsulation, coded as 3823E. It is also an excellent replacement for the 2N3819.

Data sheet supplied with device.

1-10 30p each, 10-50 25p each, 50+ 20p each.

Make a Rev. Counter for your Car. The 'TACHO BLOCK'. This encapsulated block will turn any 0-1mA meter into a linear and accurate rev. counter for any car. **£1 each**

## FREE CATALOGUE AND LISTS for:—

**ZENER DIODES  
TRANSISTORS, RECTIFIERS  
FULL PRE-PAK LISTS  
& SUBSTITUTION CHART**

MINIMUM ORDER 50p CASH WITH ORDER PLEASE. Add 10p post and packing per order. OVERSEAS ADD EXTRA FOR AIRMAIL.

**P.O. RELAYS** **8 FOR £1**  
Various Contacts and Coil Resistances. No individual selection. Post & Packing 25p

**FREE! A WRITTEN GUARANTEE WITH ALL OUR SEMICONDUCTORS**

# BI-PRE-PAK LTD

DEPT. D, 222-224 WEST ROAD, WESTCLIFF-ON-SEA, ESSEX  
TELEPHONE: SOUTHEND (0702) 46344

# JUST BEGINNING?

*Then try out*

**8-Watt, 10-Transistor  
Stereo Amplifier R.137**

**ROC  
price  
£10.50**

Separate tone and volume controls for each channel, inputs for turntable (ceramic cartridge), tuner and tape. Attractive black crackle finish with brushed aluminium front. Frequency response: 70-20,000 Hz  $\pm$  3dB. Output: 4 watts per channel @ 8 ohms. Inputs: Phono 80mV; tuner/aux 80mV.

Normal retail price: **£14.70**




# FIRST STEP TO STEREO!

**5-Watt Transistor Stereo Amplifier Chassis R.123**

Completely self-contained, fully transistorised, mains-powered (240v AC) amplifier, needing only cabinet and knobs. Ideal for adapting mono players to stereo. Frequency response: 40-17,000 Hz  $\pm$  3dB. Output: 2.5 watts per channel @ 8 ohms. Input: Phono 600mV.

Normal retail price: **£7.30**

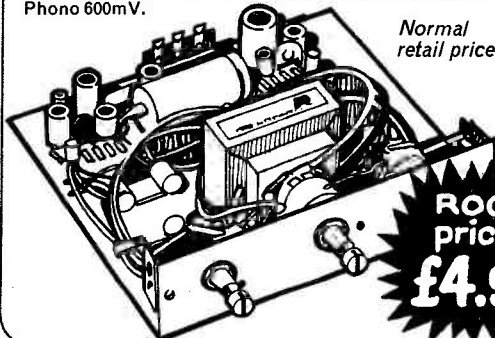

**ROC  
price  
£4.95**

# SOUNDS SENSATIONAL

**AM/FM/MPX  
Stereo Tuner  
Amplifier  
R.124**

A top quality amplifier with facility for receiving stereo broadcasts. Separate bass and treble controls, automatic frequency response, stereo headphone socket, output power: 8 watts. FM frequency range 88-108 MHz; AM frequency range 535-1605 KHz. Inputs for turntable (ceramic cartridge) and tape. Frequency response: 50-10,000 Hz  $\pm$  3dB. Output: 4 watts per channel @ 8 ohms. Inputs: Phono 200mV, tape 100mV. FM: Sensitivity 20 $\mu$ V, stereo separation 26dB, image rejection 55dB. AM: Sensitivity 300 $\mu$ V.

Normal retail price: **£42.00**

**ROC price: £29.95**




# World wide reception

**Professional Solid-state, Four-band  
Communications Receiver R.135**

Fully transistorised with continuous coverage from 555K Hz to 30 MHz in four bands (with illuminated bandspread for 160-10 metres). Incorporates internal speaker, automatic noise limiter, SSB/AM/CW switch, AVC switch, S Meter, Receive and Standby switch, external socket for headphone or speaker, bandspread control, BFO control, on/off/AF gain, band selector, antenna trimmer and RF gain. Runs off 240 v AC, batteries or any 12 v DC negative ground source. Frequency ranges (in MHz): Band A, 535-1.6; B, 1.55-4.5; C, 4.5-13; D, 13-30. Sensitivity: 0.5 $\mu$ V @ 30MHz. Bandspread: 10-160 metres.

Normal retail price: **£65.00**

**ROC  
price:  
£45.00**

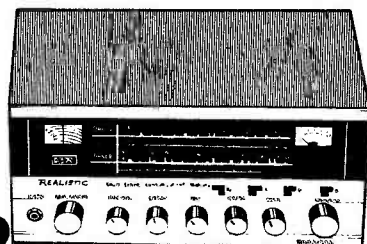


# AMAZING OFFER!

**Stereo  
Cassette  
Tape  
Unit R.142**

Complete stereo record and playback unit with line and microphone inputs. Fitted with tape counter, separate pause control, recording level metres for each channel, pop-up cassette ejection. Supplied complete with two pencil microphones. Wow & flutter better than 0.3%, frequency response 100-10,000 Hz. Tape speed: 1 $\frac{1}{2}$  IPS, 4.75 CMS. Rewind time: Better than 60 sec (C.60 cassette). Normal retail price: **£65.00**

**ROC  
price  
£49.50**

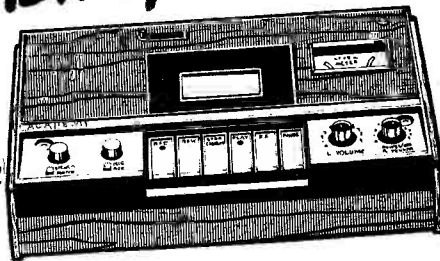


# We don't want you to

Every piece of electronic or audio-equipment we sell is built to our specifications. It comes complete with a Guarantee. And it's tested before it leaves us.

We bend over backwards in our advertising to make sure everything we say is factually accurate. But, buying mail-order, even though you're buying from us, we accept you could still end up with a piece of equipment that's not exactly what you wanted. And we think that's unfair.

# FANTASTIC BARGAIN

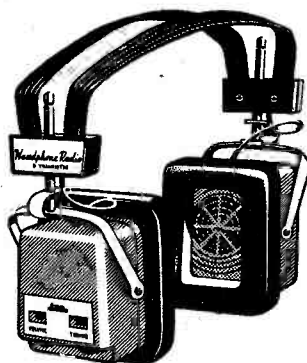

## Headphone Radio R.143


For completely private listening without the distortion of the ordinary earphone adaptor. Battery operated; PP3. Fully transistorised. Frequency range: 535-1600 K Hz, Medium Wave Band. Maximum output: 300mW.

**ROC price**  
**£6.90**

Normal retail price: £9.40

# 2 for the price of one!

## Matched Stereo Speakers R.446

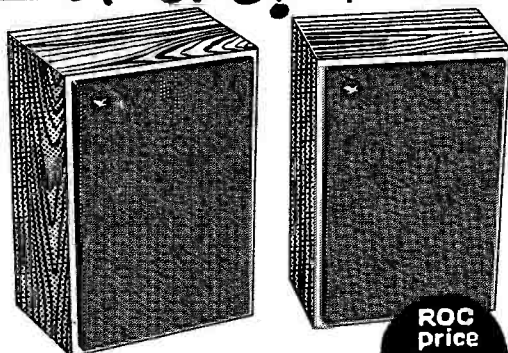

Heavily lagged teak finish cabinets each with large dual cone base unit and separate tweeter. Power handling: 10 watts peak; frequency range: 40-18,000 Hz, impedance: 8 ohms. Size: 14 x 8½ x 6½.

Normal retail price: £19.60

**ROC price**  
**£16.40**

# pay for your mistakes

So we've got a proposition for you. If you buy a piece of Roc equipment, and it's not quite what you expected, send it back within seven days, and as long as it's as good as new we'll give you your money back. O.K.?

Return of post mail-order service; orders over £10 post free, (U.K. only) add 25p for p & p to orders under £10. HP terms available.

## ROC ELECTRONICS LIMITED

B. Jory Esq 193 Edgware Rd., London W2 1ET. 01-723 6211. Callers at Shop welcome 9-6 Mon to Sat (Thurs 1pm)

# STEREO headphones

*only*  
**£2.40**




## Stereo Headphones R.328

Light and comfortable, with a frequency response of 30-15,000 Hz for real listening pleasure. Complete with jack plug, impedance 8-16 ohms. Normal retail price: £2.95

# Don't read this!
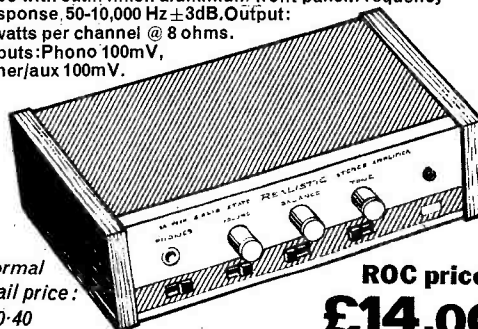
## 10-watt Transistor Stereo Amplifier R.136

Ganged volume, balance and tone controls. Inputs for turntable (ceramic cartridge), tuner (see R.134) or tape. Oiled walnut case with satin finish aluminium front panel. Frequency response: 50-10,000 Hz  $\pm$  3dB. Output: 5 watts per channel @ 8 ohms. Inputs: Phono 100mV, tuner/aux 100mV.



Normal retail price: £20.40

**ROC price:**  
**£14.00**

# The Perfect match!

## AM/FM/MPX Stereo Tuner R.134



Matching unit to the R.136 amplifier. Covers AM and FM tuning bands with automatic stereo signal light. FM frequency range: 88-108MHz; AM frequency range: 535-1605kHz. FM: Sensitivity 5µV, stereo separation 25dB @ 1kHz, image rejection 50dB. AM: Sensitivity 250µV.

Normal retail price: £28.60

**ROC price**  
**£22**






## High Salary A Dream House A New Car And A Secure Future

Get into the Computer Industry the fast and easy way.

Now for the first time, anybody (no special qualifications are needed) can train outside the computer industry for an exciting career as a **computer operator in only 4 weeks** — and can earn £2,000 ++ p.a.

How? We are the only commercial training organisation in the U.K. permitted to use the famous 'Eduputer'.

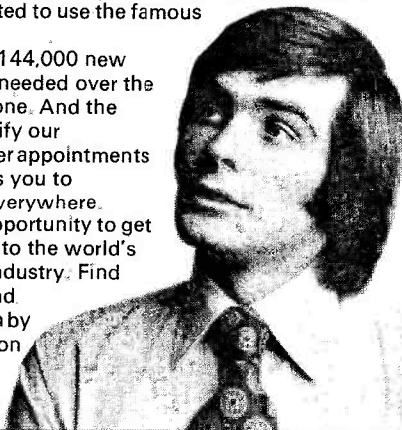**JOBS GALORE!** 144,000 new operators will be needed over the next five years alone. And the moment you qualify our exclusive computer appointments bureau introduces you to computer users everywhere. This is your big opportunity to get out of a rut and into the world's fastest growing industry. Find out more **FREE** and without obligation by posting this coupon **TO-DAY.**



### London Computer Operators Training Centre

**C19**, Oxford House, 9/15, Oxford Street, London, W1.  
Telephone: 01-734 2874  
127/131 The Piazza, Dept. **C19**, Piccadilly Plaza,  
Manchester 1. Telephone: 061-236 2935.

Please send me your **FREE** illustrated brochure on exclusive Eduputer 'hands on' training for computer operating.

Name

Address

Tel

### BATTERY/MAINS

SUPERHETERODYNE

## PORTABLE RECEIVER

**8 WAVEBANDS.** The most exciting radio ever! Picks up ALL THE USUAL BBC Programmes. All the new local radio stations. \*Continental. \*World-wide transmissions. \*Pop. \*Pirates. \*Radio Mams. \*Aircraft. \*Shipping. \*Police. \*Taxi. \*R.A.C. \*A.A. \*Fire Brigades. \*T.V. Sound. \*Ambulances and 1,000s more. **THE BEST PORTABLE RADIO EVER MADE!** We think so. What radio priced at under £120 gives you such a varied choice of transmissions! As well as the standard long and medium wavebands it has three shortwave bands (including the Marine and Trawler Band) AND NO LESS THAN THREE V.H.F. BANDS — truly a complete **WORLD-WIDE** communications Receiver. Hours and hours of enjoyable listening **JUST THINK!** One minute you can be listening to your favourite B.B.C. programme and then — at the flick of a switch — you can tune into the control tower and hear a crippled airliner being talked down to safety. Or listen to the trawlers and Ocean-going liners! Eavesdrop on the taxi-cabs, fire brigades, ambulances, A.A., R.A.C. and 100s of other R.T. mobiles — even your local police! Extensive shortwave coverage can give you Australia, Pakistan, Luxembourg, North America, Far East, etc., etc. you name it — it gets it! Manufactured by one of the world's leading specialists in communications and T.V. equipment each set carries a **FULL 3-YEAR WRITTEN GUARANTEE.** Beautifully finished in teak wood and stainless steel — will add distinction to any living room. Completely portable 12in. x 9in. x 4in. using standard batteries — or can be plugged directly into mains. 14 transistors, 7 diodes, 1 thermister, r.f. output, 1,200 mW output, internal ferrite rod aerial PLUS two external telescopic antennae — with sockets for additional aerials or car aerials. Automatic Frequency Control — locks onto a station and ensures Drift Free reception. Very latest sliding tone and volume controls. Fine squelch control. Hi-Frequency earphone which automatically cuts out the main speaker when in use, local DX switch. **FREQUENCIES:** Long W 150-350 Kcs. Medium W 540-1665 Kcs. Marine 1.6-4 Mcs. Short W 1.3-7 Mcs. Short W 2.7-22 Mcs. F.M. (V.H.F.) 88-108 Mcs. Aircraft (V.H.F.) 108-136 Mcs. Public Service (V.H.F.) 148-174 Mcs.

**NOT JUST A RADIO — BUT A COMPLETE COMMUNICATIONS RECEIVER**

**THE ULTIMATE** in communications Receivers — used by professionals and Amateur Enthusiasts all over the world. **INSTANT CASH REFUND** if not overwhelmed by the superb tone, clarity and performance range


**CASH PRICE**

**£47.50**

Plus 50p post & packing or sent for £12.50 deposit and 6 monthly payments of £7. (Total Credit Price £54.50 plus 50p p. & p.). Refund guarantee.

### SCIENTIFIC AND TECHNICAL SERVICES (P.W.2).

507-511 London Road, Westcliff, Essex.

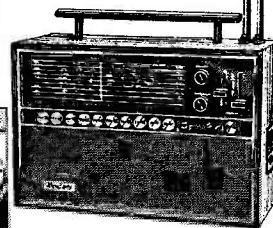

## FANTASTIC BARGAIN OFFER! TRANSEUROPEAN

Transistorised Stereophonic High Fidelity  
AM FM Tuner Amplifier System.




This system includes this elegantly styled solid state Teak finished cabinet tuner/amplifier. Covering VHF/FM, Medium and long wavebands. The latest 4 Speed B.S.R. Mono/Stereo record changer with 2-10in. x 6in matching elliptical speakers. A complete Hi-Fi Stereo Radiogram at less than half normal price. **Easily fitted no technical knowledge necessary.**

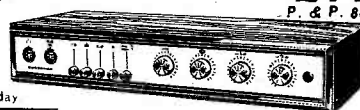**SPECIAL OFFER £44**

P. & P. 88

Credit Terms available. First monthly payment of £5.83 followed by 9 monthly payments of £4.95. Total Credit Sale Price £49.50. Send £5.83 today



### FABULOUS VALUE

Hi-Fi stereo at a new low. System Ten-Ten: 4 speed BSR autochanger with cue and pause control plus solid state amplifier, 20 watt total output. Frequency response 20-20,000 Hz. Two elliptical speakers in book shelf enclosures — 100% complete.

**ONLY £4.93 DOWN**

**CREDIT SALE TERMS:** Send £4.93 (being the first of TEN monthly payments of £4.05 plus 88p Carriage and Packing). To be followed by NINE monthly payments of £4.05 (Total Credit Sale Price £40.50)

**EASY TO INSTALL NO TECHNICAL KNOWLEDGE REQUIRED.**


**CALLERS WELCOME**  
PLEASE SEND ME FREE DETAILS OF YOUR RANGE

Name   
Address

Post coupon NOW for...  
**FREE** leaflets

**LEWIS radio** 100, Chase Side London N14  
Tel: 01-886 3733/9666
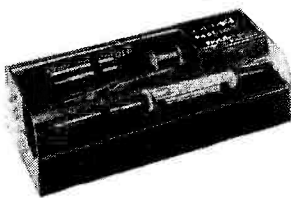
# cut out this coupon and answer your soldering problems



## SK1 SOLDERING KIT

In rigid plastic "tool box" containing Model CN - 15 watts - 240 volts miniature iron fitted with  $\frac{3}{16}$ " bit. Spare bits  $\frac{5}{32}$ " and  $\frac{3}{32}$ ". Reel of resin-cored solder, heat sink, cleaning pad, stand and booklet "How to Solder".

£2.75



## SK2 SOLDERING KIT

In polystyrene pack, containing 15 watt miniature soldering iron, 240 volts fitted with  $\frac{3}{16}$ " bit, 2 spare bits  $\frac{5}{32}$ " and  $\frac{3}{32}$ ". Coil of resin-cored solder, heat sink, 1A fuse and booklet "How to Solder".

£2.40



Model CN 240/2  
- 15 watts  
- 240 volts

Fitted with nickel plated  $\frac{3}{32}$ " bit and packed in handy transparent box.


£1.70



ES240 D 25 watt  
soldering iron

In transparent display pack, fitted with long life iron-coated bit  $\frac{1}{8}$ " diam. Interchangeable spare bits  $\frac{5}{32}$ ",  $\frac{3}{16}$ ",  $\frac{1}{4}$ " (extra) available. Improved design to ensure strong and reliable high speed iron. Heats up in 2 minutes.

£1.83

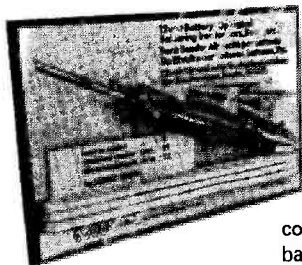

M.E.S.  
Battery-operated  
12 volt  
soldering iron

Complete with 15 ft (4.50m) lead, 2 heavy gauge clips for instant

connection to car battery and a guide 'How to Solder'. Packed in strong plastic wallet.

£1.95



from electrical and radio shops or by Free Post (No stamp required) from ANTEX Ltd. FREE POST. PLYMOUTH, PL1 1BR Tel: (0752) 67377/8

- ☐ Please send the ANTEX colour catalogue.
- ☐ Please send the following:

I enclose cheque / P.O. / Cash (Giro No. 2581001)

NAME

ADDRESS

PW10

# LOW PRICE, HIGH QUALITY SPEAKER SYSTEMS

All cabinets are new and carefully designed acoustically with speakers mounted on tin. chipboard baffles. All speakers are ex-TV high quality with hi-flux magnets carefully matched and tested.

We still do the well known Shelley and Caxton column speaker systems.




## STEREO HEADPHONE JUNCTION BOX

Simple unit connects direct to amplifier and speakers to give attenuated headphone output, has 2 position switch to give headphones only—speakers only.  
Only £1.37 each P & P 12½.
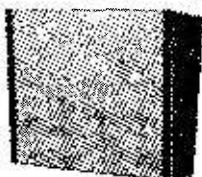
## CARTRIDGES-Stereo

Sonotone 9TA H/C Diamond £2.40, Ronette S105 Medium Output, £1.40, S106 High Output £1.40, Acos GP93/1 Sapphire, £1.90, GP94 1 Sapphire, £2. TA700 equivalent to B.S.R. SX1M, £1.75. Japanese equivalent to B.S.R. TC8s, £1.75. P. & P. 7np on each.



## DUDLEY

11" x 9½" x 5" deep, tapering to 3½" deep covered in Black Reseal and Mottled fawn Vynair £2.10 P & P 25p.

## SPEAKERS

E.M.I. 13½ x 8in, 3 ohm £2.50, 15 ohm. P. & P. 30np. E.M.I. 13½ x 8in, fitted two 2½in. tweeters, 15 ohm £4.50. P. & P. 30np. E.M.I. 13½ x 8in. (15 ohm) Hi-Fi quality £6.25. P. & P. 30np. Bakers 12in. 25 watt 8 and 15 ohms £7. P. & P. 30np. Eagle Crossover 86np. P. & P. 5np.

## VYNAIR

Widths from 50 to 54 in., 75np yd. off roll. P. & P. 10np. ¼ yard 40np. P. & P. 10np. Send 5np stamps for samples.



## IMP

Wedge shaped extension speaker 7½ x 6½ x 4in. (max.). Covered in walnut wood grain cloth with mottled Vynair front. Keyhole slot at back. Fitted with 3 ohm speaker unit. Only £1.25. P. & P. 36np each

## CARTRIDGES-Mono

GP.91 Stereo Compatible £1.25. Acos GP67/2 will replace Collaro and Garrard Mono cartridges, 95np. T.T.C. Crystal High Gain, 75np. B.S.R. TC8H Jap. equivalent £1.25. P. & P. 7np.

## SPEAKER MATCHING


TRANSFORMERS 3, 7, 15 ohms. 8 watt, 70np. P. & P. 17np.

## FARRADAY

5½" x 11" x 4½" covered in White, Green or Black rexine or Teak cloth with Silver coloured metal front  
£2.90 P & P 25p.




## CLARENCE

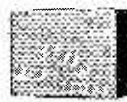

11" wide x 8½" x 4½" deep with volume control covered in Black rexine and Mottled Vynair.  
£2.25 P & P 25p.

## NOCTURNE 73 STEREO SYSTEM

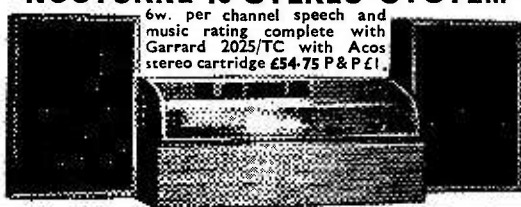

6w. per channel speech and music rating complete with Garrard 2025/TC with Acos stereo cartridge £54.75 P & P £1.

# BROADWAY ELECTRONICS

82 MITCHAM ROAD, TOTTENHAM BROADWAY, LONDON S.W.17 01-672 3984 (Closest all Wednesday)

# M. & B. COMPONENTS (LEEDS) LTD.

(INCORPORATING M. & B. RADIO)

PO Box 125, 38 BRIDGE END, LEEDS 1 Telephone 0532-35649

**MB2/20A TWO METRE TRANSCEIVER.** Rx Tuneable over 2 metre band, 20 watts RF output AM modulated. Ideal for mobile or fixed station. Only requires connection to speaker, aerial and 12v DC supply to become fully operational. (Full details on list.)  
£50 inc. carr. U.K.

**AD 108D MARCONI COMMUNICATION RECEIVERS.** 9 miniature valves plus Xtal filter and tuneable BFO covering 260 to 510 Kc/s and 2 to 18.5 Mc/s in 4 switched bands. Slow motion dial with logging scale. Originally intended for 24v DC operation but supplied with details for converting to mains operation. In very clean, tested condition.  
£15.50 inc. carr. U.K.

**EX-ARMY 88 WALKIE TALKIES.** 3 channel, less handset. Untested but complete and in clean condition. With circuit.  
ONLY £4.75 or £8 for 2 inc. carr. U.K.

**6 TO 12 VOLTS DC TRANSISTOR CONVERTOR.** Brand new 6v DC input, 12v DC output at 4 amps conservatively rated. Ideal VW owners.  
£5.40 inc. carr. U.K.

**9 TRANSISTOR 455 KC/S IF STRIPS.** Ideal basis for receiver.  
BARGAIN. Only £1.20 inc. carr. U.K.

**GEIGER COUNTERS.** Well known contamination meter comprised of main unit fitted with meter marked in Milli Rontgens/hour, probe lead and carrying case. Audio output available from socket on front panel. Supplied new or as-new condition. Model I fitted with vibrator PSU using 5 pen cell batteries.  
£4.85 inc. carr. U.K.

**12v INVERTER TRANSFORMERS.** Complete with circuit to build inverter to give 350v output at 300 m/a. £2.20 inc. carr. U.K.

Send S.A.E. for complete list of items in stock.

# VALVES

SAME DAY SERVICE  
NEW! TESTED! GUARANTEED!

**SETS** 1R5, 1B5, 1T4, 384, 3V4, DAF91, DF91, DK91, DL92, DL94. Set of 4 for £1.02, DAF96, DF96, DK96, DL96, 4 for £1.48.

|        |    |        |    |        |    |        |    |        |    |             |    |
|--------|----|--------|----|--------|----|--------|----|--------|----|-------------|----|
| 1R5    | 28 | 25U4GT | 57 | DY86   | 26 | EL600  | 62 | PCL82  | 83 | UABCS80     | 83 |
| 1B5    | 28 | 30C1   | 29 | DY87   | 26 | EM80   | 41 | PCL83  | 59 | UAF42       | 51 |
| 324    | 18 | 30C15  | 65 | DY802  | 40 | EM81   | 41 | PCL84  | 85 | UBC41       | 52 |
| 324    | 28 | 30C17  | 30 | EAB030 | 32 | EM84   | 32 | PCL85  | 42 | UBF80       | 34 |
| 3V4    | 37 | 30C18  | 68 | EAF42  | 50 | EM87   | 80 | PCL86  | 40 | UBF89       | 83 |
| 5U4G   | 26 | 30F5   | 70 | EB41   | 40 | EY51   | 38 | PCL88  | 72 | UCC84       | 83 |
| 5V4G   | 45 | 30FL1  | 68 | EB91   | 41 | EY86   | 81 | PCL800 | 77 | UC85        | 86 |
| 5Y3GT  | 28 | 30FL12 | 70 | EB93   | 40 | EZ40   | 43 | PEN44  | 77 | UC80        | 84 |
| 5Z4G   | 85 | 30FL14 | 70 | EB94   | 44 | EZ41   | 43 | PEN36C | 70 | UCH42       | 82 |
| 6J90L2 | 58 | 30L1   | 80 | EB90   | 22 | EZ80   | 22 | PFL200 | 68 | UCB1        | 32 |
| 6AL5   | 11 | 30L15  | 59 | EBF80  | 85 | EZ81   | 23 | PL36   | 49 | UCL82       | 84 |
| 6AM6   | 18 | 30L17  | 71 | EBF89  | 31 | GZ30   | 35 | PL81   | 48 | UCL83       | 55 |
| 6AQ5   | 26 | 30P4   | 65 | ECC81  | 17 | GZ32   | 42 | PL81A  | 49 | UF41        | 66 |
| 6AT6   | 22 | 30P12  | 77 | ECC82  | 20 | GZ34   | 60 | PL82   | 81 | UF89        | 81 |
| 6AU6   | 21 | 30P19  | 65 | ECC83  | 35 | KT41   | 77 | PL83   | 33 | UL41        | 80 |
| 6BA6   | 21 | 30P11  | 68 | ECC85  | 26 | KT61   | 65 | PL84   | 30 | UL44        | 81 |
| 6BE6   | 28 | 30PL13 | 78 | ECC804 | 47 | KT66   | 61 | PL800  | 64 | UL84        | 33 |
| 6BJ6   | 41 | 30PL14 | 67 | ECC80  | 30 | LN319  | 62 | PL604  | 64 | UM84        | 82 |
| 6BW7   | 55 | 30PL15 | 90 | ECC82  | 28 | LN329  | 72 | PM84   | 85 | UY41        | 40 |
| 6CD6G  | 17 | 35L6GT | 45 | ECH55  | 30 | LN339  | 63 | PX25   | 81 | UY85        | 88 |
| 6F14   | 42 | 35W4   | 25 | ECH42  | 81 | N78    | 87 | PY32   | 65 | VP4B        | 77 |
| 6F83   | 70 | 35Z4GT | 65 | ECH81  | 29 | P61    | 46 | PY33   | 66 | Z77         | 82 |
| 6F95   | 40 | 807    | 45 | ECH83  | 40 | PABCS0 | 84 | PY81   | 87 | Transistors |    |
| 6K7G   | 12 | 6063   | 62 | ECH84  | 38 | PC86   | 48 | PY82   | 25 | AC107       | 17 |
| 6K8G   | 17 | AC/VP2 | 77 | ECL80  | 32 | PC88   | 48 | PY83   | 28 | AC127       | 18 |
| 6Q7G   | 28 | B349   | 65 | ECL82  | 31 | PC96   | 48 | PY88   | 38 | AD140       | 87 |
| 6SN7GT | 80 | B729   | 62 | ECL86  | 38 | PC97   | 40 | PY800  | 84 | AF115       | 80 |
| 6V6G   | 23 | CCX35  | 67 | EF89   | 38 | PC900  | 33 | PY801  | 84 | AF116       | 80 |
| 6V6GT  | 31 | CY31   | 32 | EF41   | 60 | PC84   | 30 | R19    | 30 | AF117       | 80 |
| 6X4    | 28 | DAF91  | 22 | EF80   | 23 | PC85   | 87 | R20    | 69 | AF118       | 48 |
| 6X5GT  | 28 | DAF96  | 38 | EF85   | 28 | PC88   | 42 | U25    | 65 | AF125       | 17 |
| 7B7    | 38 | DF33   | 38 | EF86   | 31 | PC89   | 46 | U26    | 69 | AF127       | 17 |
| 10P13  | 58 | DF91   | 18 | EF89   | 89 | PCC189 | 48 | U47    | 66 | OC26        | 85 |
| 12AH8  | 22 | DF96   | 38 | EF91   | 13 | PC805  | 59 | U49    | 59 | OC44        | 12 |
| 12AT7  | 17 | DH77   | 22 | EF183  | 23 | PC870  | 29 | U50    | 59 | OC45        | 12 |
| 12AU6  | 29 | DK32   | 37 | EF184  | 31 | PCF82  | 31 | U52    | 31 | OC71        | 18 |
| 12AU7  | 20 | DK91   | 28 | EH90   | 37 | PCF86  | 45 | U78    | 24 | OC72        | 12 |
| 12AX7  | 28 | DK92   | 42 | EL33   | 55 | PCF800 | 67 | U91    | 80 | OC75        | 12 |
| 19BG6G | 87 | DK96   | 38 | EL34   | 45 | PCF801 | 81 | U93    | 42 | OC81        | 12 |
| 20F2   | 40 | DL35   | 40 | EL41   | 54 | PCF802 | 44 | U251   | 66 | OC81D       | 12 |
| 20F2   | 30 | DL92   | 30 | EL94   | 63 | PCF805 | 63 | U301   | 45 | OC82        | 12 |
| 20F4   | 92 | DL94   | 87 | EL90   | 28 | PCF806 | 68 | U329   | 68 | OC82D       | 12 |
| 25L6GT | 20 | DL96   | 88 | EL95   | 83 | PCF808 | 70 | U801   | 98 | OC170       | 82 |

# READERS RADIO

85 TORQUAY GARDENS, REDBRIDGE, ILFORD, ESSEX. Tel. 01-550 7441.

Postage on 1 valve 5p, on 2 or more valves 3p per valve extra. Any parcel insured against damage in transit 3p extra.

# Build yourself a TRANSISTOR RADIO

## NEW! ROAMER 10 WITH VHF INCLUDING AIRCRAFT

**10 TRANSISTORS. 9 TUNABLE WAVEBANDS, MW1, MW2, LW, SW1, SW2, SW3, TRAWLER, BAND, VHF AND AIRCRAFT BAND**


Built in Ferrite Rod Aerial for MW/LW. Retractable, chrome plated 7 section Telescopic Aerial, can be angled and rotated for peak short wave and VHF listening. Push Pull output using 600mw Transistors. Car Aerial and Tape Record Sockets. Switched Earpiece Socket complete with Earpiece. 10 Transistors plus 3 Diodes. 7in x 4in Speaker. Air Spaced ganged Tuning Condenser with VHF section. Volume on/off, Wave Change and Tone Control. Attractive Case in black with silver blocking. Size 9" x 7" x 4". Easy to follow instructions and diagrams. Parts price list and easy build plans 30p (FREE with parts).

Total building cost

**£8-50**

P. P. & Ins. 50p

(Overseas P. & P. £1)

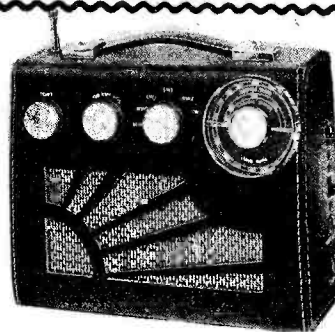

### ROAMER EIGHT Mk I

**NOW WITH SWITCHED TONE CONTROL**

7 Tunable Wavebands: MW1, MW2, LW, SW1, SW2, SW3 and Trawler Band. Built in Ferrite Rod Aerial for MW and LW. Retractable chrome plated Telescopic aerial for Short Waves. Push pull output using 600mw Transistors. Car aerial and Tape record sockets. Selectivity switch. Switched earpiece socket complete with earpiece. 8 transistors plus 3 diodes. 7in x 4in. Speaker. Air spaced ganged tuning condenser. Volume/on/off, tuning, wave change and tone controls. Attractive case in rich chestnut shade with gold blocking. Size 9 x 7 x 4in. approx. Easy to follow instructions and diagrams. Parts Price List and Easy Build Plans 25p (FREE with parts).

Total building cost **£6-98** P. P. & Ins. 41p.  
(Overseas P. & P. £1)



### ROAMER SEVEN MK IV

7 Tunable Wavebands: MW1, MW2, LW, SW1, SW2, SW3 and Trawler Band. Extra Medium waveband provides easier tuning of Radio Luxembourg, etc. Built in ferrite rod aerial for MW and LW. Retractable 4 section 24in. chrome plated telescopic aerial for SW. Socket for Car Aerial. Powerful push-pull output. 7 transistors and 2 diodes, including Micro-Alloy R.F. Transistors. 7 x 4in. P.M. speaker. Air spaced ganged tuning condenser. Volume/on/off, tuning and wave change controls. Attractive case with carrying handle. Size 9 x 7 x 4in. approx. Easy to follow instructions and diagrams. Parts price list and easy build plans 15p (FREE with parts). Earpiece with plug and switched socket for private listening, 30p extra.


Total building costs **£5-98** P. P. & Ins. 41p.  
(Overseas P. & P. £1)


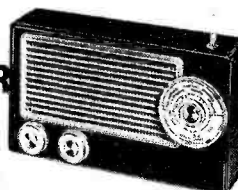
### ROAMER SIX

6 Tunable Wavebands: MW, LW, SW1, SW2, Trawler Band plus an extra M.W. band for easier tuning of Luxembourg, etc. Sensitive ferrite rod aerial and telescopic aerial for Short Waves. 3in. Speaker. 8 stages—6 transistors and 2 diodes including Micro-Alloy R.F. Transistors, etc. Attractive black case with red grille, dial and black knobs with polished metal inserts. Size 9 x 6 1/2 x 2 1/2in. approx. Easy build plans and parts price list 15p (FREE with parts). Earpiece with plug and switched socket for private listening 30p extra.


Total building costs **£3-98** P. P. & Ins. 26p.  
(Overseas P. & P. £1)


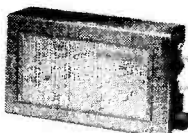
### POCKET FIVE

3 Tunable Wavebands: MW, LW, Trawler Band with extended M.W. band for easier tuning of Luxembourg, etc. 7 stages—5 transistors and 2 diodes, supersensitive ferrite rod aerial, fine tone moving coil speaker. Attractive black and gold case. Size 5 1/2 x 1 1/2 x 3 1/2in. Easy build plans and parts price list 10p (FREE with parts). Earpiece with plug and switched socket for private listening 30p extra.

Total building costs **£2-23** P. P. & Ins. 21p.  
(Overseas P. & P. 65p)




### TRANSONA FIVE

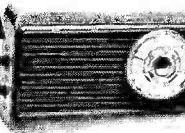**NOW WITH 3in SPEAKER**

3 Tunable Wavebands: MW, LW and Trawler Band. 7 stage—3 transistors and 2 diodes, ferrite rod aerial, tuning condenser volume control, fine tone 3in. moving coil speaker. Attractive case with red speaker grille. Size 6 1/2 x 4 1/2 x 1 1/2in. Easy build plans and parts price list 10p (FREE with parts). Earpiece with plug and switched socket for private listening 30p extra.


Total building costs **£2-50** P. P. & Ins. 22p.  
(Overseas P. & P. 63p)


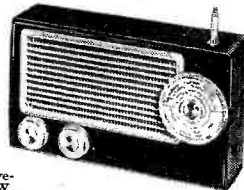
### TRANS EIGHT

6 Tunable Wavebands: MW, LW, SW1, SW2, SW3 and Trawler Band. Sensitive ferrite rod aerial for M.W. and L.W. Telescopic aerial for Short Waves. 3in. Speaker. 8 improved type transistors plus 3 diodes. Attractive case in black with red grille, dial and black knobs with polished metal inserts. Size 9 x 6 1/2 x 2 1/2in. approx. Push pull output. Battery economiser switch for extended battery life. Ample power to drive a larger speaker. Parts price list and easy build plans 25p (FREE with parts). Earpiece with plug and switched socket for private listening 30p extra.

Total building costs **£4-48** P. P. & Ins. 31p.  
(Overseas P. & P. £1)



## NEW! "EDU-KIT"

**BUILD RADIOS, AMPLIFIERS, ETC., FROM EASY STAGE DIAGRAM. FIVE UNITS INCLUDING MASTER UNIT TO CONSTRUCT.**

**COMPONENTS INCLUDE:**  
Tuning Condenser: 2 Volume Controls: 2 Slider Switches: 4"x2 1/2" Speaker: Terminal Strip: Ferrite Rod Aerial: 3 Plugs and Sockets: Battery Clips: 4 Tag Boards: Balanced Armature Unit: 10 Transistors: 1 Diodes: Resistors: Capacitors: Three 1" Knobs.  
Units once constructed are detachable from Master Unit, enabling them to be stored for future use. Ideal for Schools, Educational Authorities and all those interested in radio construction.

All parts including Case and Plans **£5-50** P. P. & Ins. 31p.  
(Overseas P. & P. £1)



**FULL AFTER SALES SERVICE**

\* Callers side entrance Barratts Shoe Shop  
\* Open 10-1, 2.30-4.30 Mon.-Fri. 9-12 Sat.

## RADIO EXCHANGE CO

61 HIGH STREET, BEDFORD. Tel. 0234 52367

I enclose £..... please send items marked

|                                        |                                       |
|----------------------------------------|---------------------------------------|
| ROAMER TEN <input type="checkbox"/>    | ROAMER SEVEN <input type="checkbox"/> |
| ROAMER EIGHT <input type="checkbox"/>  | TRANS EIGHT <input type="checkbox"/>  |
| TRANSONA FIVE <input type="checkbox"/> | ROAMER SIX <input type="checkbox"/>   |
| POCKET FIVE <input type="checkbox"/>   | EDU-KIT <input type="checkbox"/>      |

Parts price list and plans for .....

Name .....

Address .....

PW.34



## DISCOTHEQUE EQUIPMENT PACKAGE OFFERS

|                                                                                                                                                 |                                                  |                                                 |
|-------------------------------------------------------------------------------------------------------------------------------------------------|--------------------------------------------------|-------------------------------------------------|
| <b>F.A.L. PHASE 50 MKII AMPLIFIER</b><br>PR. FANE POP 25/2 5W L/SPEAKERS<br>Terms: Deposit £5.50 and 9 monthly payments of £4.72 (Total £47.98) | <b>£33.50</b><br><b>£13.50</b><br><b>£47.00</b>  | <b>PACKAGE PRICE</b><br><b>£44</b> carr. £1     |
| <b>F.A.L. PHASE 50 MKII AMPLIFIER</b><br>PR. FANE POP 50 L/SPEAKERS<br>Terms: Deposit £10.50 and 9 monthly payments of £5 (Total £55.50)        | <b>£23.50</b><br><b>£21</b><br><b>£54.50</b>     | <b>PACKAGE PRICE</b><br><b>£49.50</b> carr. £1  |
| <b>F.A.L. PHASE 100 AMPLIFIER</b><br>PR. L125 60W L/S in cabinets<br>Terms: Deposit £22 and 9 monthly payments of £11 (Total £113)              | <b>£61.95</b><br><b>£59.80</b><br><b>£121.75</b> | <b>PACKAGE PRICE</b><br><b>£110</b> carr. £1.50 |
| <b>F.A.L. PHASE 100 AMPLIFIER</b><br>4 FANE POP 50 L/SPEAKERS<br>Terms: Deposit £14 and 9 monthly payments of £10 (Total £104)                  | <b>£51.95</b><br><b>£42</b><br><b>£103.95</b>    | <b>PACKAGE PRICE</b><br><b>£94</b> carr. £1.50  |

## F.A.L. DISCOTHEQUE CONSOLE



Incorporating twin Garrard SP25 Mk.III turntables and Goldring CS90 Ceramic Cartridges with diamond styli. Separate Vol. Bass and Treble controls for each turntable plus MONITORING FACILITIES. Black Rexine covered Cabinet with lid.

**£65**  
Carr. £1.25

Terms: Deposit £11 and 9 monthly payments of £6.70 (Total £71.30)

## AUDIOTRINE HI-FI SPEAKER SYSTEMS

Consisting of matched 12in. 11,000 line 15 Watt 15 ohm high quality speaker, cross-over unit and tweeter. Smooth response and extended frequency range ensure surprisingly realistic reproduction.

**£5.75**

OR SENIOR 15 WATT INC. £6.75 Carr. 30p  
HF126 15,000 LINE SPEAKER carr. 35p

## AUDIOTRINE HIGH FIDELITY LOUDSPEAKERS



Heavy construction. Latest high efficiency ceramic magnets. Treated Cone surround. "D" indicates Tweeter Cone providing extended frequency range up to 15,000 c.p.s. Impedance 3 or 8-15 ohms. Please state choice. Exceptional performance at low cost.

|                |       |                |       |
|----------------|-------|----------------|-------|
| HF801D 8" SW   | £2.71 | HF180D 18" 15W | £4.75 |
| HF102D 10" 15W | £3.40 | HF126 12" 15W  | £5.60 |
| HF120 12" 15W  | £4.25 | HF126D 12" 15W | £5.90 |

## FANE 807 HIGH FIDELITY LOUDSPEAKER

A full range 8in. 10 watt unit for excellent sound quality, in suitable enclosure. Cast chassis Roll P.T.C. cone surround and least throw voice coil to achieve very low fundamental resonance of 30 c.p.s. Tweeter cone is fitted to extend high note response. Frequency range 25 Hz to 15 KHz. Impedance 3 or 8-15 Ohm. Gauss 10,000. Remarkable value.

**£3.50**

## HI-FI SPEAKER ENCLOSURES

Modern design. Teak veneer finish. Acoustically lined. All sizes approx. Carr. 30p. per enclosure  
JES Size 16 x 11 x 9in. Pressurised. Gives pleasing results with any 8in. Hi-Fi speaker.  
SES For optimum performance with any 8in. Hi-Fi speaker. Size 22 x 15 x 9in. Ported  
SE10 For outstanding results SE12 For excent prfmanee with 12in. with 10in. Hi-Fi speaker and Tweeter.  
Size 24x16x10in. P.t.d. **£6.74** Hi-Fi speaker and Tweeter. **£7.87**  
Size 25 x 15 x 10in.

## R.S.C. BATTERY/MAINS CONVERSION UNITS



**TYPE BML** An all-dry battery eliminator. Size 5 1/2 x 4 1/2 x 2in. approx. Completely replaces batteries supplying 1.5v and 90v, where A.C. mains 200/250v. 50c/s is available. Complete kit Assembled ready with diagram **£3** for use **£3.50**

## R.S.C. TA6 6 Watt HI-FI SOLID STATE AMPLIFIER



200-250v. AC mains operated. Frequency Response 20-20,000 c.p.s. -2dB. Harmonic Distortion 0.3% at 1,000 c.p.s. Separate Bass and Treble. Input selector switch. Output for 3-15 ohm spkrs. Max. sensitivity 5mV. Output rating I.H.F.M. Fully enclosed enamelled case, 9 1/2 x 2 1/2 x 6 1/2in. Attractive brushed silver finish fascia plate 10 1/2 x 3 1/2in. and matching knobs. Complete kit of parts with full wiring diagrams and instructions. **£7.50** Carr. 40p.

OR FACTORY BUILT WITH 12 MONTHS' GUARANTEE **£9.75**

## R.S.C. A11 HI-FI 12-14 WATT AMPLIFIER



**PUSH-PULL OUTPUT.** Two input sockets with sep. vol. controls for mixing. High sensitivity. 5 valves. Bass and treble controls. Response  $\pm 3dB$  30-20,000 c/s. Hum level -60dB. Sensitivity 40 millivolts. For Crystal or Ceramic P.U.s. High Impedance "mikes". For Musical Instruments etc.

SAE A.C. mains. For 3 & 15 ohm spkrs. Complete kit. Full instructions and point-to-point wiring diagrams. Carr. 60p  
SAE for leaflet. Twin handled metal cover **£1.75**  
Factory built **£14.75** or Dep. £3 and 9 mthly pymts of £1.60 (Total £17.40.)

## R.S.C. COLUMN SPEAKERS

IDEAL FOR VOCALISTS AND PUBLIC ADDRESS



All types 15 Ohms covered in Rexine Vynair  
TYPE C4100 IS ALSO SUITABLE FOR BASS GUITAR OR ELECTRONIC ORGAN

### TYPE C485 25-30 WATTS

Fitted four 8" high flux 8 watt speakers.  
Overall size approx 48 x 10 x 5 in. Carr. 60p  
Terms: Dep £3 and 9 monthly payments £2 (Total £21) **£17.75**

### TYPE C4125 50 WATTS

Fitted four 12" 11,000 line 15 watt speakers: Overall size approx 56 x 14 x 9 in. Carr. 75p  
Terms: Dep. £4 and 9 monthly payments £2 (Total £31) **£27.50**

**TYPE C4100 100 WATTS** Inc. four 12" 50 watt speakers for conservative tuning. Extra heavy construction. Size approx 68 x 16 x 10" Acoustically filled and pressurised. Terms: Dep. £7.50 and 9 mthly. pyts. £5.45 (Total £56.55). Carr. £1

## 30 WATT HI-FI AMPLIFIER FOR GUITAR, VOCAL OR INSTRUMENTAL GROUP.

A 2 or 4 input, 2 vol. control HI-Fi unit with Separate Bass and Treble controls. Current valves. Peak output rating. Strong Rexine covered cabinet with handles. Attractive black/gold P.V.C. fascia. Neon indicator. For 200-250v. A.C. mains. For 3 or 15 ohm speakers. Send S.A.E. for leaflet.

Terms: Deposit £3.70 and 9 monthly payments of £2.10 (Total £22.60) **£19.95** Carr. 65p



## HIGH QUALITY LOUDSPEAKER UNITS

### IN TEAK VENEERED CABINETS

L13 13" x 8" 10 Watt L12 12" Also  
10,000 lines 3 or 15 25 WATT supplied  
ohms. State impedance 10,000 lines Rexine  
required. 15 ohms. covered

**£5.25** carr. 40p **£10.50** carr. 45p

### L125 50 WATT

Two tone Rexine and vynair finish. Fitted pair of 12" 50 watt high flux speakers for conservative tuning. Impedance 8-15 ohms. Or deposit £4 and 9 monthly payments of £3.35. Total £24.15 **£31** Carr. 75p



## R.S.C. BASS REGENT 50 WATT AMPLIFIER

A powerful high quality all-purpose unit for lead, rhythm, bass guitar, vocalist, gram, radio, tape. Peak Output rating.

Loudspeaker unit optional horizontal or vertical mounting. **£60** Carr. £1.50

★ Two extra heavy duty 12in. Loudspeakers.  
★ Four Jack inputs and two Volume Controls for simultaneous use of up to four pick-ups or "mikes".  
Bass and Treble controls. Send S.A.E. for leaflet.  
Credit Terms Deposit £16 and 9 monthly payments of £5.75 (Total £67.75)



## FAL PHASE 50 MKII AMPLIFIER 50W

Solid state 4 Separately controlled inputs. Plus master vol. control. Ind. Bass and Treble Controls. Protective circuit to guard against damage from accidental shorts. Output for Speaker/s 3-30 ohms. Size 17" x 7" x 7" 200-250v. A.C. mains. Output 60 watts music rating. Or deposit £8 & 9 monthly payments £3.50. Total £37.50. Carr. 65p

## FAL PHASE 100 AMPLIFIER 100W

Solid State. 4 Separately controlled inputs. Plus master volume control. Ind. Bass and Treble Controls. Output for speaker/s 3-30 ohms. Protective circuit to guard against damage from accidental shorts. I.H.F.M. Output rating. Or deposit £12 & 9 monthly payments £6.25. Total £68.25. Carr. 75p. Send S.A.E. for leaflets.

## FANE ULTRA HIGH POWER LOUDSPEAKERS

All power ratings are R.M.S. continuous. 2 YEARS' GUARANTEE

High flux ceramic magnets. Heavy cast chassis. All carr. free.

### 'POP' 100

18" 100Watt  
14,000 gauss  
8/15Ω  
**£22.05**

Dep. £6 and 9 monthly payments £3.10 (Total £24.15)

### 'POP' 60

15" 60 Watt  
14,000 gauss  
8/15Ω  
**£12.90**

Dep. £3.80 and 9 monthly payments. £1.30 (Total £15.10)

### 'POP' 50

12" 50 Watt  
13,000 gauss  
15Ω  
**£10.50**

Dep. £2 and 9 monthly payments £1.15 (Total £12.65)

Pair suitable for all purposes

## F A N E


### LOUDSPEAKERS

### 'POP' 25/2
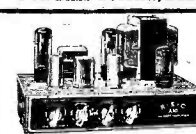
### 12in. 25 WATT

Dual Cone 15Ω (for uses other than Bass Guitar or Electronic Organ). **£6.75** Carr. free

or Dep. £1 and 9 mthly payments 75p (Total £7.75)



## R.S.C. A10 30 WATT ULTRA LINEAR HI-FI AMPLIFIER

Highly sensitive. Push-Pull high output. Hum level -70dB. Response  $\pm 3dB$  30-20,000 c/s. All high grade components. Valves EF86, EF85, ECC83, 6X4, 6X5, 6X6, 6X7, 6X8, 6X9, 6X10, 6X11, 6X12, 6X13, 6X14, 6X15, 6X16, 6X17, 6X18, 6X19, 6X20, 6X21, 6X22, 6X23, 6X24, 6X25, 6X26, 6X27, 6X28, 6X29, 6X30, 6X31, 6X32, 6X33, 6X34, 6X35, 6X36, 6X37, 6X38, 6X39, 6X40, 6X41, 6X42, 6X43, 6X44, 6X45, 6X46, 6X47, 6X48, 6X49, 6X50, 6X51, 6X52, 6X53, 6X54, 6X55, 6X56, 6X57, 6X58, 6X59, 6X60, 6X61, 6X62, 6X63, 6X64, 6X65, 6X66, 6X67, 6X68, 6X69, 6X70, 6X71, 6X72, 6X73, 6X74, 6X75, 6X76, 6X77, 6X78, 6X79, 6X80, 6X81, 6X82, 6X83, 6X84, 6X85, 6X86, 6X87, 6X88, 6X89, 6X90, 6X91, 6X92, 6X93, 6X94, 6X95, 6X96, 6X97, 6X98, 6X99, 6X100. Complete kit of parts with full wiring diagrams and instructions. **£15.75** Carr. 65p

TERMS: Deposit £4 and 9 monthly payments of £2.10 (Total £22.60). Send S.A.E. for leaflet.

## RSC TRANSFORMERS, L.F. CHOKES & RECTIFIERS

FULLY GUARANTEED. Impregnated and Interleaved where necessary

### Primarys 200-250v. 50c/s. Screened

### MIDGET CLAMPED TYPE 2 1/2 x 2 1/2 in.

250v. 60mA. 6.3v. 2a. **£1.05**

### FULLY SHROUDED UPRIGHT MOUNTING

250-0-250v. 60mA. 6.3v. 2a. 0-5-6.3v. 2a. **£1.40**

250-0-250v. 100mA. 6.3v. 4a. 0-5-6.3v. 3a. **£2.20**

300-0-300v. 100mA. 6.3v. 4a. 0-5-6.3v. 3a. **£2.20**

300-0-300v. 100mA. 6.3v. 4a. c.t. 6.3v. 1a. **£2.45**

For Mullard 610 Amplifier **£2.45**

350-0-350v. 100mA. 6.3v. 4a. 0-5-6.3v. 3a. **£2.20**

425-0-425v. 150mA. 6.3v. 4a. c.t. 5v. 3a. **£2.45**

425-0-425v. 200mA. 6.3v. 4a. c.t. 6.3v. 3a. 5v. **£2.50**

450-0-450v. 250mA. 6.3v. 4a. c.t. 6.3v. 3a. **£2.50**

TOP SHROUDED DROP-TYPE

250-0-250v. 70mA. 6.3v. 2a. 0-5-6.3v. 2a. **£1.35**

250-0-250v. 100mA. 6.3v. 3.5a. **£1.55**

350-0-350v. 80mA. 6.3v. 2a. 0-5-6.3v. 2a. **£1.65**

250-0-250v. 100mA. 6.3v. 4a. 0-5-6.3v. 3a. **£2.20**

300-0-300v. 100mA. 6.3v. 4a. 0-5-6.3v. 3a. **£2.20**

300-0-300v. 150mA. 6.3v. 4a. 0-5-6.3v. 3a. **£2.20**

Suitable for Mullard 610 Amplifier **£2.60**

350-0-350v. 100mA. 6.3v. 4a. 0-5-6.3v. 3a. **£2.20**

425-0-425v. 100mA. 6.3v. 4a. 0-5-6.3v. 3a. **£2.60**

### FILAMENT OR TRANSISTOR POWER PACK

Types 6.3v. 1.5a. 49p; 6.3v. 2a. 54p; 6.3v. 3a. 76p;

6.3v. 6a. £1.30; 12v. 1a. 55p; 12v. 2a. 55p;

1.5a. £1.35; 0.9-1.8v. 1.5a. £1.10; 0.12-25-43v. 2a. £1.76

CHARGER TRANSFORMERS 0-9-15v. 1.5a. 89p;

2A. £1.10; 3A. £1.25; 5A. £1.45; 6A. £1.65; 8A. £2.00

AUTO (Step UP/Step DOWN) TRANSFORMERS

0-110/120v. 200-250v. 50-80 watts £1.10;

150 watts £1.30 250 watts £2.75; 500 watts £5.75.

### OUTPUT TRANSFORMERS

Standard Pentode 5,000 Ω or 7,000 Ω to 3 Ω 50p

Push-Pull 8 watts EL84 to 3 Ω or 15 Ω **85p**

Push-Pull 10 watts 6V6, 6CL8 to 3 Ω, 5 Ω or 15 Ω **£1.37**

Push-Pull EL84 to 3 or 15 Ω 10-12 watts **£1.85**

Push-Pull Ultra Linear for Mullard 610, etc. **£2.20**

Push-Pull 15-18 watts, sectionally wound 6L6, KT68, etc. for 3 or 15 Ω **£1.99**

Push-Pull 20 watt high quality sectionally wound EL34, 6L6, KT68 etc. to 3 or 15 Ω **£3.30**

SMOOTHING CHOKES 150mA. 7-10H. 250 Ω 70p;

100mA. 10H. 200 Ω 60p; 80mA. 10H. 350 Ω 60p; 60mA. 10H. 400 Ω 25p.

### SELENIUM RECTIFIERS F. W. (Bridged)

All 6/12v. D.C. output. Max. A.C. input 18v.

1a. 25p. 2a. 35p. 3a. 50p. 4a. 65p. 6a. 80p.

# Introducing R.S.C. MkIII SUPER 30 HI-FI STEREO AMPLIFIER

A COMPLETELY NEW DESIGN FURTHER IMPROVED IN BOTH APPEARANCE and PERFORMANCE. REPRESENTING VALUE FAR HIGHER THAN THE PRICES SUGGEST.

Only high grade components by leading manufacturers. COMPLETE KIT OF PARTS

£25 Carr. £35

Or FACTORY BUILT with 12 months guarantee Dep. £3-75 and 9 monthly payments £3-50 (Total £37-25) Or FACTORY BUILT in cabinet as illustrated Dep. £8 and 9 monthly payments £3-80 (Total £40-74)

PRINTED CIRCUITRY, TWENTY SILICON TRANSISTORS. FOUR DIODES, FOUR RECTIFIERS. TECHNICAL DETAILS (Applying to each channel where appropriate) CONTROLS: PUSH-BUTTON SELECTOR (1) Dial (2) Radio (3) Tape (4) Mono L (5) Mono R (6) SPEAKER DIS. (7) Mains on/off. Bass, Treble, and Balance. Plus Ceramic/Mag P.U. Switch.



- ★ SATIN SILVER METAL FACIA with black lettering. Black edged knobs with bright silver centres.
- ★ PUSH-BUTTON SELECTOR SWITCHING
- ★ NEON INDICATOR
- ★ JACK SOCKET FOR HEADPHONES
- ★ CABINETED MODEL VENEERED IN SATIN TEAK. SUITABLE FOR ANY MODERN PICK-UP CARTRIDGE CERAMIC or MAGNETIC, REGARDLESS OF PRICE.
- ★ WE RECOMMEND USE WITH THE BEST ANCILLARY EQUIPMENT THAT CAN BE AFFORDED.

OUTPUT: 15 watts R.M.S. (Continuous) into 8 ohms. 10 watts R.M.S. (Continuous) into 15 ohms. HUM & NOISE - 75dB Min. Vol. - 65dB Full Vol. HARMONIC DISTORTION FREQUENCY RESPONSE: -3dB 7Hz to 70KHz 0-1% at 1000 Hz 10 Watts TREBLE CONTROL: +16dB to -12dB at 14KHz BASS CONTROL: +17dB to -16dB at 40Hz CROSS TALK - 58dB SENSITIVITIES: Diac Mag. 2-5mV. Ceramic 35mV. Radio 120mV. Tape 120mV. REAR PANEL SOCKETS ARE FOR 3 PAIRS OF INPUTS (1) P.U. (2) Radio. (3) Tape Amp. Plus pair for tape recorder signal take off and 2 pairs for speaker connections.

## RSC HIGH FIDELITY STEREO PACKAGE OFFERS

- ★ Four fully wired units ready to 'plug in'.
- ★ SUPER 30 AMPLIFIER (15 + 15 watt) in veneered housing
- ★ GARRARD SP25 MKIII Turntable on Plinth with cover
- ★ GOLDRING CS90 Ceramic Pick up Cartridge with diamond stylus
- ★ PAIR OF STANWAY II Speaker Units

£79-80

Matching as recommended for optimum performance. Send S.A.E. for coloured brochure showing other money-saving offers.

Package prices apply providing all individual units are purchased from any branch within 3 months. See leaflet.



Stanway II



ATTRACTIVE TEAK or AFROREMOSIA VENEERED CABINETS and PLINTHS

- ★ TA12 AMPLIFIER 6-5 + 6-5 watt in veneered housing
- ★ GARRARD SP25 MK III Player unit on Plinth
- ★ GOLDRING CS90 Ceramic P.U. Cartridge with diamond stylus
- ★ PAIR OF DORCHESTER Loudspeaker Units

£58

Special Total Price Carr. £1-25 Or Deposit £7-15 and 9 monthly payments £6-35 (Total £64-30). Trans. Plastic Cover £3-15 extra.

Package as above but with Garrard 8000 Auto-changer and Sontone 95A Ceramic Cartridge in lieu of SP25 £51-75 Carr. £1-25 and CS90

Or Deposit £6 and 9 monthly payments £5-70 (Total £57-30) Trans. Plastic cover £3-15 extra.

- ★ Super 30 Amplifier (15 + 15 watt) in veneered housing
- ★ Goldring GL69 II Transcription Turntable on Plinth as illustrated
- ★ Goldring Magnetic P.U. Cartridge.
- ★ Pair of Stanway II speaker units

£96-75

TERMS AVAILABLE ON ALL PACKAGE OFFERS

### 'YORK' HIGH-FIDELITY 3 SPEAKER SYSTEM



- ★ Moderate size only 25 x 14 x 10in.
- ★ Response 30-20,000 c.p.s. Impedance 15 ohms
- ★ Performance comparable with units costing considerably more. Consists of (1) 12in. 15 watt Bass unit with cast chassis, Roll rubber cone surround for ultra low resonance, and ceramic magnet. (2) 3-way quarter section series cross-over system (3) 8 x 5in. high flux middle range speaker. (4) High efficiency tweeter. (5) Appropriate quantity acoustic damping material. (6) Handsome Teak veneered cabinet. (7) Circuit and full instructions. Terms: Dep. £4-50 and 9 monthly payments £2-25 (Total £24-75).

COMPLETE KIT Carr. 63p £22

DEMONSTRATIONS AT ALL BRANCHES

### RSC G66 6+6 WATT high quality STEREO AMPLIFIER

Individual Ganged controls: Bass, Treble, Volume and Balance. Printed circuit construction employing 10 Transistors plus Diodes. Output rating I.H.F.M. Frequency range 20-20,000 c.p.s. Suitable for Crystal Pick-ups, etc., and for loudspeaker output impedances of 3 to 15 ohms. For standard 200-250v A.C. mains operation. Attractive silver finished metal face plate & matching control knobs. COMPLETE KIT OF PARTS INCLUDING FULLY WIRED PRINTED CIRCUIT and comprehensive wiring diagram and instructions £9-99 carr. 40p. Or FACTORY BUILT IN TEAK VENEERED CABINET as illustrated £12-99 or dep £2-50 and 9 mthly pymnts. £1-45 (Total £15-55).



### HIGH FIDELITY LOUDSPEAKER UNITS



Cabinets latest style Satin Teak veneer. Acoustically lined or filled acoustic damping. Ported where appropriate. Credit terms available. DORCHESTER (Illustrated) Size 16 x 11 x 9in. appr. Range 45-15,000 c.p.s. Rating 8-10 watts. Fitted High flux 13 x 8in. Dual Cone speaker. Imp. 3 or 15 ohms. £9-45 Carr. 40p. STANWAY II Size 20 x 10 1/2 x 9 1/2in. approx. Rating 10 watts. Inc. 13 x 8in. speaker with highly flexible cone surround, long throw voice coil and 10,000 line magnet. High flux tweeter. Handsome Scandinavian design cabinet. Range 35-20,000 c.p.s. Imp. 15 ohms. Gives smooth realistic sound output. See 'package offers' for illustration £17-85

### R.S.C. TA12 MKIII 6-5 + 6-5 WATT STEREO AMPLIFIER FULLY TRANSISTORISED. SOLID STATE CONSTRUCTION HIGH FIDELITY OUTPUT OF 6.5 WATTS PER CHANNEL

Designed for optimum performance with any crystal or ceramic Gram. P.U. cartridge. Radio tuner, Tape recorder etc. ★ 3 separate switched input sockets on each channel ★ Separate Bass and Treble controls ★ Slide Switch for mono use ★ Speaker Output 3-15 ohms ★ For 200-250v. A.C. mains ★ Frequency Response 20-20,000 c.p.s. - 2dB ★ Harmonic Distortion 0.3% at 1,000 c.p.s. Hum and Noise - 70dB ★ Sensitivities (1) 50mV (2) 400mV (3) 100mV. Output rating I.H.F.M. ★ Handsome finish Facia plate & Knobs. COMPLETE KIT OF PARTS WITH FULL WIRING DIAGRAMS & INSTRUCTIONS. Factory built with 12 months guarantee £19-50 or Deposit £3 and 9 mthly pymts £2-18 (Total £22-55). Or in Teak veneer housing £23 Dep. £3 and 9 mthly payments £2-55 (Total £25-95). Send S.A.E. for leaflet



### R.S.C. PLINTHS

Superior Solid Natural Wood Construction



WITH TRANSPARENT PLASTIC COVER

for Record Playing unit, cut for Garrard 1025, 2025, 3000, AT80, SP25 etc. £3-15 £6-30

### SPECIAL HI-FI OFFERS

WHARFEDALE/F.A.L. 1 pr Wharfedale Super Linton Speakers, 1 F.A.L. Phase 32 15 + 15 watt Stereo Amplifier Total Rec. Retail Price £67-70 PACKAGE PRICE £66-50 Above brand new goods. Following have been unpacked for display purposes only:- LEAK MINI-SANDWICH (Teak finish) £18

ROGERS RAVENSBROOK STEREO AMPLIFIER £39 TANDBERG 62X TAPE RECORDER (Stereo) £88 GOLDRING GL68 Transcription Turntable and Pick-up £14-50 GOODMANS AUDIOM 91 £19-95

### LOW DEPOSIT CREDIT TERMS

AVAILABLE ON PURCHASES OVER £8 (KITS OF PARTS EXCEPTED) INTEREST CHARGES REFUNDED ON CREDIT SALES SETTLED IN 3 MONTHS

BRADFORD 10 North Parade. (Half-day Wed.) Tel. 25349 BLACKPOOL (Agent) O. & C. Electronics, 227 Church Street BIRMINGHAM 30/31 Gt. Western Arcade (Half-day Wed.) Tel. 021-336-1279 DERBY 26 Osmaston Rd., The Spot (Half-day Wed.) Tel. 41361 DARLINGTON 18 Priestgate (Half-day Wed.) Tel. 68043 EDINBURGH 133 Leith St. (Half-day Wed.) Tel. 556 5766 GLASGOW 326 Argyle St. (Half-day Tues.) Tel. City 4158 HULL 91 Paragon Street (Half-day Thursday) Tel. 20505



MAIL ORDERS TO: Audio House, Henconner Lane, Leeds 15. Terms C.W.O. or C.O.D. No C.O.D. under £1. Postage 25p extra under £2. 30p extra over £2 or as quoted. Trade supplied. S.A.E. please with enquiries. Branches open all day Sats. MAIL ORDERS MUST NOT BE SENT TO SHOPS

32 High Street (Half-day Thurs.) Tel. 56420 LEICESTER 5-7 County (Mecca) Arcade, Briggate (Half-day Wed.) Tel. 28252 LEEDS 73 Dale St. (Half-day Wed.) Tel. CENTRAL LIVERPOOL 239 Edgware Road, W2 (Half-day Thurs.) Tel. 3573 LONDON 60A Oldham Street (Half-day Wed.) Tel. CENTRAL 2778 MANCHESTER 106 Newport Rd. (Half-day Wed.) Tel. 47096 MIDDLESBROUGH 41 Blackett Street (Opp Fenwicks Store) (Half-day Wed.) Tel. 21469 NEWCASTLE UPON TYNE 13 Exchange Street (Castle Market Bldgs.) (Half-day Thursday) Tel. 20716 SHEFFIELD

### BC221 MAINS POWER UNITS

200/250v I/P, O/Ps 135v at 20 mA from electronic stabiliser also 6.3v AC for heaters. Uses 4 valves made to fit in battery compartment of unit with small control box with swt and fuses. Supplied new with circ and mains lead.

Price £6.00 plus 60p carr.

Spares for above, set of 4 new valves £1.00

New mains trans £1.50 both post paid.

### R.F. 26 TUNING UNITS

These tune 50 to 65 Mc/s use 3 valves I.F. O/P 7 Mc/s will mod up to 100 Mc/s fitted slow motion dial etc. Supplied in good cond. with circ. Price £2.10 plus 40p post.

Rx unit 3645 for use with above £2.25 carr. paid

### METER UNITS

Radio altimeter units 6.5 mA F.S.D. 270° scale size front 3½" sq. fitted on/off and range swt ideal for use as rev. counters; good condition.

Price 80p plus 15p post

### AMPLIFIER UNIT 115v 50c/s I/P

These are a small self contained unit, uses 3 valves 6X4 Rect, 6AK6 O/P and 12AX7 Amp; these are low impedance I/P & 500 ohm O/P, fully enclosed size 10 x 3½ x 3½". Supplied with circ. & mods. for 3 ohm O/P, ideal unit for beginner, Ex USAF surplus good cond. Price £2.50 plus 25p post. Small 230/110 trans for above 75p post paid.

### HEAVY DUTY MAINS TRANS.

Pria 200/220/240v 50c/s Sec 500-0-500 at 400 mA or can be connected to give 1 kV at 200 mA; varnish finish tag connections; size overall 5½ x 5½ x 4½; supplied in new condition ex service.

Price £2.25 plus 40p post.

### POWER UNITS

These are a transistorised power unit high cycle I/P and contain 8 type 2S012A Silicon NPN pow transis (Texas); these are Vc 70v 1c 2a good to 2 Mc/s also 18 Silicon diodes 200 P.I.V. 5a to 8a large Ledex swt, large board with transistors, etc. misc potted trans supplied new crated, modern Guided Missile equip.

Price £4.50 plus 75p carr.

### MISC. ITEMS

Scope tube 3BP1 3" green screen with base and Mu Met shield and base connections £2.50. Crystal units 100 Kc high grade with base £1.40. Relays coil 14K 1p c/o sealed new ex equip also 24v 700 ohm 2p c/o sealed both 2 for 30p. Block conds 8µf 1Kv 2 for 90p. 8µf 750v 2 for 60p. Valves 6SN7 or 6SL7 5 for 50p. Relay panel with 4x min 2p c/o relays coil 1K new ex equip 55p. Diodes type GJ5M 300 P.I.V. 1 amp mounted on small h/s 8 for 40p. Miniature plug and sk 18 way with clamp and cover good quality 15p pair. L.V. Smoothing Conds 4000µf 50v 5 x 2" 50p. 2500µf 75v 4 x 2" 50p. 800µf 50v 5 x 1½ 30p all with fully insulated cases and fix brackets, good quality. I.F. strips 30 Mc/s wide band 10 valves miniatures, size 18 x 4 x 4". USAF surplus £1.80. Pre Amp for I.F. strip 90p. Relays coil 6/12v D.C. 1p N.O. rated 20a 40p. Control knobs to fit ½ shafts assorted 12 for 50p. Pot Cores LA66 4 for 50p. LA2503 Vinkors 4 for 50p. American 73 Radio Mag new back issues 8 for £1.15. Speaker units portable 8" unit in case 18 x 18 x 8" 3 ohm with 600 to 3 ohm trans new £2.90. Test unit with 2x LA2503 Vinkors 4 Sil Transis 4 min relays min valves etc. new boxed 85p. T.S.210 (test osc) covers 20 to 85 Mc/s in 4 bands with xtal check noise gen etc. reqs 250v ht and 6.3v with charts good cond. £3.90. Swt unit yax type 4p 4w 4b with 12/745pf trimmers 35p Tuning Cond air spaced 60pf with small drive 35p. EHT Cond. 1 x 5µf 2kV wk size 4 x 2 x 2" inc term 50p. Group board with 7x 400 P.I.V. 500 mA diodes, min relay II tant conds etc. new ex equip. 50p. OC16 med pwr transis P.N.P. type 2 for 25p. Transformers Pria 115/120v sec 850-0-850v at 600 mA or 1700v 300 mA potted type new Amer supplied in pairs £4.60. Circuit diagrams, 1392 Rx, 1155Rx, 1475 (88) Rx all 30p. Schemes CD513.2 £1.50. 13A, CD518 (CT310), Os-8, 50p ea. CT38 later series 50p.

All above prices include post or carr. All goods ex equipment unless stated otherwise. S.A.E. with enquiry

## A. H. SUPPLIES

57 MAIN ROAD, SHEFFIELD S9 5HL



### EX RENTAL TV'S

19" — £29.95

23" — £39.95

All Channels 405/625

2 Years Guarantee.

Free List by return.

17" Slim line TV's £11-95, 19" Slim line TV's £15-95. Guaranteed 2 years. Send for List. Carr. & Ins. all sets £1-95. Daily demonstrations to personal shoppers.

### TEAK HI-FI STEREO CABINETS £14.95

Brand New 44" wide x 16" deep x 18" high with Legs. A superb piece of furniture. Carr. £1-00.

TRANSISTOR GANG CONDENSERS 30p. Miniature AM precision Tape Motors £1-95 famous German manufacturer. 200/250V. Post 20p.

Transistor Radio Cases: 25p each. Size 9½" x 6½" x 3½". P. & P. 15p. SPEAKERS 50p 2½" 8Ω BRAND NEW. P. & P. 5p.

### TRANSISTORS Post Free

|        |        |          |
|--------|--------|----------|
| AC 128 | AF 179 | OC 81    |
| AC 128 | OC 44  | OC 81D   |
| AF 114 | OC 45  |          |
| AF 117 | OC 71  | 15p each |

### POTENTIOMETERS 23p each

|                   |               |           |
|-------------------|---------------|-----------|
| Double & Switched | 500 KΩ/500 KΩ | 3½" shaft |
| Double & Switched | 500 KΩ/100 KΩ | 2" shaft  |
| Double & Switched | 1 MEG/100 KΩ  | 1½" shaft |

Post. & Pack. 5p.—4 for 10p

### KNOBS 100,000 to clear (Brand New)


100 assorted Radio & T.V. knobs 50p. Postage 10p. (If you require sets 2 to 6 just ask)

## DUKE & CO. (LONDON) LTD.

621/3 Romford Road, Manor Park, E.12

Phone 01-478 6001-2-3 Stamp for Free List

### TV TUBES REBUILT. GUARANTEED 2 YEARS

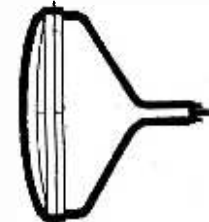

14"—£3.95, 17"—£5.95,

21" & 23"—£8.45.

Exchanged Bowls. Carr. 53p.

### Selections from FELSTEAD ELECTRONICS' List


(Sent free for stamped addressed envelope to address below)

Transistors etc. AC126 12½p. AF115 20p. AF116 15p. AF117 20p. OA5 7½p. OA10 7½p. OA81 7½p. OA85 7½p. OC23 82½p. OC25 80p. OC26 37½p. OC28 42½p. OC35 42½p. OC44 14p. OC45 12½p. OC71 12½p. OC72 12½p. OC75 12½p. OC81 12½p. OC81D 12½p. OC82D 12½p. OC170 20p. OC171 12½p. Many more in list. S.D.R. BY100 800piv 14p. 6 amp series: BY213 300piv 20p. BY212 600piv 25p. BY211 900piv 30p. BY210 1200piv 35p. (Charges 5½p up to 1, paid for 12 and over). Sub-Min Transistors: OUTPUT 3 Ω for OC72 etc. 14p (up to 1.5 5½p). SOLDERING IRON, Slim, modern, British highspeed 8½", all parts replaceable, highest quality, full guarantee: £1-07½ (10p). DIAMOND STYLII Replacements for BSR TC8/LP, TC8/S, TC8/LP/STEREO: COLLARO 'O' : RONETTE BF 401P; Garrard GC2/LP and GC8/LP: ACOS GP65/67, all at 40p (6p). ACOS GP73, (GP91, GP91SC, GP104: BSR ST4 (ST3, ST5), ST8 (ST9), SONOTONE STA, STA, STAHIC, PHILLIPS AG3806, 3060 (3063, 3066, 3301, 3302, 3304); Garrard GK825, GCM21, GCR23 and many more 'Garrard' etc. types. All at 75p. (6p). All are of the very highest quality. DOUBLE DIAMOND: ST4 (ST3, ST5), ST10 (ST9, ST8), STA, STAHIC, 3306, GP91 (Por. GP92, GP93, GP94 cartridges); GP91-SC for all GP91-SC Cartridges. All at £1-50 each (6p). SAPPHIRE STYLII. All those types shown above under Diamond StylII at 40p also GP37 at 17½p each (6p) and GP91 and GP91SC at 40p (6p). No others. PICK-UP CARTRIDGES. All Standard fittings and stylII. Mono GP67/2 50p. STEREO-COMPATIBLE (MONO) STEREO STAHIC (DIA.) £2-40. RECORDING TAPE. Still the finest quality British Mylar available: Standard 5" 600ft. 36p. 5½" 900ft. 50p. 7" 1200ft 56p. LONG PLAY 5" 900ft. 50p. 5½" 1200ft. 56p. 7" 1200ft. 80p. (7½p on 5" and 5½", 9p on 7"). Other sizes of Tapes, also Cassettes in list. MICROPHONES. Crystal Mic 91, hand/desk 8½p. MIC45. Curved metal hand-grip 21-00. CM21 Grey hand desk 62½p. Stick '60' 11-02½. CM70 'Planet' machined metal tapered stick type with neck cord, adaptor to fit floor stands £1-47½ (all 6p). LAPEL (or hand) with clip 32½p (6p). All are fitted with leads. Dynamic MS10 50K Ω for desk, tapered with base and slide-on adaptor 21-97½. MS11. Similar, but fixed on swivel swan neck to switch-fitted base. £2-22½ (Either 15p). Type 209 Cardioid ball. 50K/600 Ω, omnidirectional, built-in vol. control, on/off switch, special lead, handle (as good as money can buy) £2-30. UD180 Uni-Di. Ball, mesh, 50K/600 Ω, Adap., cable, jack plug £4-20. (20p). DML60. omnidirectional. Ball, 50K Cable adaptor £2-87½ (all at 27½p). MICROPHONE INSERTS. Dia. 1-75" OR 0-9" either size 27½p (6p). EARPIECES with lead and min. jack plug (2.5 or 3.5 mm., state which). Magnetic 9p Crystal (3.5 only) 24p (Up to 3 for 6p on any). HEADPHONES De-luxe STEREO 8-16 Ohms £2-47½. Same, fitted vol. control each earpiece £4-20. Both have lead and stereo jack plug (17½p). High Res. 2000 ohm. Adjustable 92½p (77p). SPEAKERS 12" ROUND fitted tweeter, 3 or 16 Ω (state which) £8-77½ (27½p) or for Stereo £4-25 pair, carr. paid. 21", 3 OR 8 Ω (state which) 87½p (6p). EMI 12" x 8" 3, 8 or 16 Ω (state which) £2-12½ (25p). (Both with two tweeters and exp. pins. 87½p). 12V 7-pin Synch. (12SR7) 62½p. (Both types 6½p per vibrator). CONNECTING WIRE. Packs of 5 coils asstd. coils. ea. coil 14p. Solid core 14p (6p). Flexible 16p (74p). Super thin for transistor wiring 16p (6p). PICK-UP WIRE. Super thin twin flex, screened and sheathed 6p yd. (6p up to 6yds.—over free). RETRACTABLE Flex. Leads. (Curtles) Phonograph each and 12ft. 30p. 6½ phone plug/phone socket other and 25p. 12ft 42½p (6p per lead all types). SEND S.A.E. for full free list of mains eliminators, amplifiers, extension aerials (car and portable), electrolytics, vol. controls, more microphones, transistors, thyristors and SDRs and other devices, switches of many types, rotary, toggle min. and sub-min. slide types, multitest meters, panel meters, all types of British and continental plugs and sockets, croc. clips, terminals, valve holders also Goldring G880 series cartridges etc. etc. Special Offer lines at very low prices.

### FELSTEAD ELECTRONICS (PW 49)

LONGLEY LANE, GATLEY, CHEADLE, CHES. SK8 4EE  
Cash with order only. No COD or Caller Service. Charges (Min. 6p) in brackets after all items. Regret Orders under 25p excluding postage, unacceptable. S.A.E. please for enquiries or cannot be replied to. Charges apply G.B. and Eire only. Overseas orders welcomed (lists free overseas).
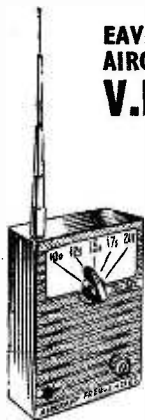
## EAVESDROP ON THE EXCITING WORLD OF AIRCRAFT COMMUNICATIONS—JUST OUT V.H.F. AIRCRAFT BAND CONVERTER



ONLY  
**£2-37**  
(47/8)

Many thousands of v.h.f. Aircraft Band Converters now selling in U.S.A. Listen in to AIRLINES, PRIVATE PLANES, JETPLANES. Eavesdrop on exciting cross-talk between pilots, ground approach control, airport tower. Hear for yourself the disciplined voices hiding tenseness on talk downs. Be with them when they have to take nerve-ripping decisions in emergencies—Tune into the international distress frequency. Covers the aircraft frequency band including HEATHROW, GATWICK, LUTON, RINGWAY, PRESTWICK ETC. ETC. CLEAR AS A BELL. This fantastic fully transistorised instrument can be built by anyone in under two hours. (Our design team built four—everyone worked first time). No knowledge of radio or electronics required. No soldering necessary. Fully illustrated simply worded instructions take you step-by-step. Uses standard PP3 battery. Size only 4½" x 3" x 1½". All you do is extend rod aerial, place close to any ordinary medium-wave radio (even tiny portables) NO CONNECTIONS WHATEVER NEEDED. Use indoors or outdoors. THERE WILL BE ENORMOUS DEMAND FOR THIS NEW DESIGN. SEND NOW, ONLY £2-37 (47/8) + 23p (4/8) p. & p. for all parts, including case nuts, screws, wire, etc., etc. (Parts available separately).

## FIND BURIED TREASURE! TREASURE LOCATOR TRANSISTORISED

NOW IT'S HERE AT LAST, after experimenting for four and a half months with a multitude of different circuits and carrying out actual field tests with prototypes, our design team have come up with this real winner. This fully portable transistorised metal locator detects and tracks down buried metal objects—it signals exact location with loud audible sound (no phones used)—uses any transistor radio which fits inside—no connections needed. FINDS GOLD, SILVER, LOST COINS, JEWELLERY, KEYS, WAR SOUVENIRS, ARCHAEOLOGICAL PIECES, METALLIC ORE, NUGGETS ETC. ETC. Outdoors or indoors. Extremely sensitive, will signal presence of certain objects buried several feet below ground! No knowledge of radio or electronics required. Can be built with ease in one short evening by anybody from nine years of age upwards, with the wonderfully clear, easy to follow, step-by-step, fully illustrated instructions—it really is as easy as A.B.C. transistorised—no valves. Uses standard PP3 battery. No soldering necessary. Size of detector head 13½" x 10" x 2½". Great demand expected at this remarkably low price—ORDER WHILE PRESENT STOCKS LAST. All parts including detector head case, nuts, screws, wire, simple instructions etc. etc. ONLY £2-37 (47/8) + 27p (5/6) p. & p. (Sectional handle as illustrated 75p (15/-) extra). Parts available separately. Made up looks worth £15!



ONLY  
**£2-37**  
(47/8)

Great demand expected at this remarkably low price—ORDER WHILE PRESENT STOCKS LAST. All parts including detector head case, nuts, screws, wire, simple instructions etc. etc. ONLY £2-37 (47/8) + 27p (5/6) p. & p. (Sectional handle as illustrated 75p (15/-) extra). Parts available separately. Made up looks worth £15!

## BUILD 5 RADIO AND ELECTRONIC PROJECTS



TOTAL BUILDING PRICE  
**£1-97**

(39/6)  
Amazing Radio Construction set! Becomes a radio expert for £1-97 (39/6). A complete Home Radio Course. No experience needed. Parts including simple instructions for each design. Illustrated Step-by-step plans, all Transistors, loudspeaker, personal phone, knobs, screws, etc., all you need. Presentation Box 37p (7/8) extra as illus. (if required) (extra parts available separately) no soldering necessary. Send only £1-97 (39/6) + 23p (4/8) p. & p.

phone, knobs, screws, etc., all you need. Presentation Box 37p (7/8) extra as illus. (if required) (extra parts available separately) no soldering necessary. Send only £1-97 (39/6) + 23p (4/8) p. & p.



## Only FIND BURIED TREASURE WITH THIS £4-95 READY BUILT & TESTED (99/-) Treasure Locator Module

BRAND NEW FULLY TRANSISTORISED PRINTED CIRCUIT METAL DETECTOR MODULE. Ready built and tested—just plug in a PP3 battery and 'phones and it's working. Put it in a case, screw a handle on and YOU HAVE A PORTABLE TREASURE LOCATOR EASILY WORTH ABOUT £20! Extremely sensitive—penetrates through earth, sand, rock, wood, dirt, water, etc.—EASILY LOCATES COINS, GOLD, SILVER, WATCHES, JEWELLERY, NUGGETS, METALLIC ORE, HISTORICAL RELICS, BURIED PIPES, KEYS, NAIL-IN-TREES, ETC. ETC. Signals exact location by 'beep' pitch increasing as you near buried metallic objects. PRINTED CIRCUIT SEARCH COIL so stable and sensitive it will detect certain objects buried SEVERAL FEET BELOW GROUND! GIVES CLEAR SIGNAL ON ONE COIN! You could even pay for your holidays with two or three days electronic beachcombing—it's almost like having a licence to print money! Unclaimed treasure now exceeds the combined wealth of all nations. ORDER NOW WHILE PRESENT STOCKS LAST—TREMENDOUS DEMAND EXPECTED AT THIS REMARKABLY LOW PRICE. DEMONSTRATIONS DAILY. ORDERS DESPATCHED IN STRICT ROTATION. SEND NOW £4-95 + 30p carr. (99/- + 8/-) etc. (High quality Danish Stethoscope headphones £2-75 (55/-) extra if required).

## SHORTWAVE TRANSISTOR RADIO

Can be built in one evening

At last! After trying countless circuits searching for easy build, work first-time short wave. Giving advanced world-wide performance, we chose this 'Sky Room'. Anyone from 3 years up can follow the step-by-step, easy-as-A.B.C. fully illustrated instructions. (We built ten prototypes and everyone worked first time) no soldering necessary. 76 stations logged on rod aerial in 30 mins.—Russia, Africa, USA, Switzerland, etc. Experience thrills of world wide news, sport, music, etc. Eavesdrop on unusual broadcasts. Uses PP3 battery. Transistorised (no valves). Size only 3" x 4½" x 1½". As tremendous demand anticipated price held to only £2-25 (45/-) + 17p (3/6) p. & p. for all parts incl. Cabinet, screws, instructions etc. (Parts available separately).

ONLY  
**£2-25**  
(45/-)



## SOOTHE YOUR NERVES, RELAX WITH THIS AMAZING RELAXATRON

CUTS OUT NOISE POLLUTION—SOOTHS YOUR NERVES! Don't underestimate the uses of this fantastic new design—the RELAXATRON is basically a pink noise generator based on avalanche operated transistors. Besides being able to mask out extraneous unwanted sounds, it has other very interesting properties. For instance, many people find a rainstorm mysteriously relaxing, a large part of this feeling of well-being can be directly traced to the sound of falling raindrops!—a well known type of pink noise. A group of Dentists have experimented on patients with this pink noise—NO ANESTHETICS WERE USED! The noise ostensibly created a most definite reaction on these patients' nervous systems with the result that their pain systems were blocked. IF YOU FEEL IN NOISY OR DISTRACTING SITUATIONS, IF YOU HAVE TROUBLE CONCENTRATING, IF YOU FEEL TIRED, UNABLE TO RELAX—then build this fantastic Relaxatron. Once used you will never want to be without it—use this amazing pink noise generator whenever you feel uneasy, can't relax or wish to concentrate. TAKE IT ANYWHERE, pocket sized. Uses standard PP3 batteries (current used so small that battery life is almost shelf-life) CAN BE EASILY BUILT BY ANYONE OVER 12 YEARS OF AGE using our unique, step-by-step, fully illustrated plans. No soldering necessary. All parts including case, a pair of crystal phones, Components, Nuts, Screws, Wire, etc. etc. no soldering. Send only £2-25 + 25p (45/- + 5/-) p. & p. Parts available separately.)

only  
**£2-25**  
(45/-)



## GET A GOOD NIGHT'S SLEEP—EVERY NIGHT! INGENIOUS ELECTRONIC SLEEP INDUCER

only  
**£2-75**  
(55/-)



CAN'T SLEEP AT NIGHTS? DO YOU WAKE UP IN THE NIGHT AND CAN'T GET OFF TO SLEEP AGAIN? WOULD YOU LIKE TO BE GENTLY SOOTHOED OFF TO SATISFYING SLEEP EVERY NIGHT? Then build this ingenious electronic sleep inducer. If even stops by itself so you don't have to worry about it being on all night! The loudspeaker produces soothing audio-frequency sounds, continuously repeated—but as time goes on the sounds gradually become less and less—until they eventually cease altogether, the effect it has on people is amazingly very similar to hypnosis. A control is provided for adjusting the length of times etc., all transistor, can be built by anyone over 12 years of age in about two hours. No knowledge of electronics or radio needed. Extremely simple, easy-to-follow, step-by-step, fully illustrated instructions included. No soldering necessary. Works off standard batteries—extremely economical. Size only 3" x 4½" x 1½"—take it anywhere. All parts including case, loudspeaker, components, nuts, wire, screws, etc. etc. THERE WILL BE A GREAT DEMAND FOR THIS UNIQUE NEW DESIGN—SEND NOW £2-75 + 25p (55/- + 5/-) p. & p. (Parts available separately).

## REAL WORKING ELECTRONIC ORGAN



ONLY  
**£2-75**  
(55/-)


Anyone from nine years upwards can build it easily in one short evening following the fully illustrated step-by-step, simply worded instructions. BIG DEMAND ANTICIPATED FOR THIS UNIQUE INSTRUMENT at our low, low building price. ONLY £2-75 (55/-) + 23p (4/8) p. & p. for all parts, including case, loudspeaker, transistors, condensers, resistors, knobs, transformer, volume control, wire, nuts, screws, simple (but full) instructions, etc. etc. Use standard battery (parts available separately). Have all the pleasure of making it yourself, finish with an exciting gift for someone.

Don't confuse with ordinary electric organs that simply blow air over mouth-organ type reeds etc. Eight months were spent in creating and testing this superb, revolutionary electronic organ. Fully transistorised—no valves. Proper self-contained loudspeaker. Fifteen separate keys span two full octaves—play the "Yellow Rose of Texas", play "Silent Night", play "Auld Lang Syne", play lots and lots of similar tunes on this real working electronic organ. Although it's no theatre organ it's certainly no tiny thing. It measures 13½" x 10" x 2½". You have the thrill and excitement of building it together with the pleasure of playing a real, live, throbbing electronic organ. Take it anywhere—play it anywhere, NO PREVIOUS KNOWLEDGE OF ELECTRONICS NEEDED—NONE WHATEVER. No soldering necessary. It really is as simple as a.b.c. to make.

EXAMINE AT HOME FOR 7 DAYS. YOUR MONEY REFUNDED IN FULL IF NOT 100% DELIGHTED.

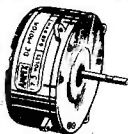**CONCORD ELECTRONICS LTD (Dept. PW24)** 8 Westbourne Grove, London W.2.  
(STAFF WANTED FOR ALL DEPARTMENTS) (Nr Bayswater & Queensway Tubes. 1 minute ABC Cinema)  
Callers Welcome 9 a.m.-6 p.m. inc. Saturday





**AMPEX 7.5v. D.C. MOTOR.** This is an ultra-precision tape motor designed for use in the AMPEX model AG20 portable recorder. Torque 450GM/CM. Stall load at 500ma. Draws 60 ma on run. 600rpm +5% speed adjustment. Internal AF/RF suppression  $\frac{1}{2}$ " dia. 17" spindle, motor 3" dia. 1 $\frac{1}{2}$ ". Original cost £16.50. Our price £4.25. P. & P. 25p. Metal enclosure available 75p each.

**SYNCHRONOUS MOTORS.** 220/380 v. 50/60 Hz. 250-300 rpm. 75p each.

**MYCALEX MAINS.** Shaded pole, 1425 rpm.  $\frac{1}{8}$ " spindle. 2 for £1.25. Carriage Paid.

**MAINS INDUCTION MOTOR.** Open frame,  $\frac{3}{8}$ " spindle, weight  $\frac{1}{2}$  lb. Powerful. 88p each. P. & P. 12p.

**GEARED MOTORS.** Shaded pole 240v. 50 Hz. 200 rpm. 10lb. in. £2.50. P. & P. 25p.

**MYCALEX.** Open frame, shaded pole motors, 240v. 50 Hz. 7 rpm. 28 lb. in. 80 rpm. 12 lb. in. £2.25 each. P. & P. 25p.

**"CROUZET" TYPE 965.** 115/240v. 50 Hz. 47/68 watts. 50 rpm. Stoutly constructed. Size: 2 $\frac{1}{4}$ " dia. x  $\frac{3}{4}$ " long plus spindle 1" x  $\frac{1}{2}$ " dia. Anti-clock. £2.75. P. & P. 25p.

**TYPE 955.** Same as above, but 3 rpm. £3.00. P. & P. 25p.

**"MALLERY" LONG LIFE BATTERIES.** Type A. RM12 cell 1.35v. 3,600 ma/H. CAP. 250/300 ma cont. current. Size: 2" x  $\frac{1}{2}$ ". 5 for £1.00 or £2.00 per doz. Carr. Paid. Type B. Comprises 8 x RM 625 cells. Nom. volts. 1.35 each 10.5v. Overall, 350ma/H CAP. 20/25 ma cont. current. Size: 2 $\frac{1}{2}$ " x  $\frac{1}{2}$ ". 3 for £1.00 or £3.00 per doz. Carr. Paid.

**A.C./D.C. M/IRON AMMETERS.** 0-5 amps or 0-8 amps (suitable battery chargers etc.). Perspex front. Size:  $\frac{1}{2}$ " x  $\frac{1}{2}$ ". Any 2 for £1.10. Carr. Paid.

**ERNEST TURNER 800/2A METER.** 160Q movement, 2" case elliptic, plastic front. Green-Red-Green uncalibrated scale £1.50 each. Carriage paid.

**PAINTON BOURNS TRIMPOTS.** 1k, 2k, 2.5k, 5k, 10k, 20k, 50k, 500k. Other Trimmer pots in stock. RIL 10k. MORGANITE 1k. MEC 200  $\Omega$  (tubular) 50 $\Omega$ . Any 3 for £1.10 carr. paid.

#### PROGRAMME TIMER BY HONEYWELL

A bank of 15 micro-switches are each independently operated by 15 pairs of cams which in turn are individually adjustable to give switching periods of zero to 12 seconds with infinitely variable combinations. A mains synchronous motor drives the cam shaft at 1 rev. per 12 seconds (5 R.P.M.). Originally cost £15.00 plus. Many applications such as lighting effects etc. New in original makers cartons. First class value at £5.75 plus 25p. P. & P.



**PRECISION FAN CO. (SMITHS INDUSTRIES) DOUBLE ENTRY CENTRIFUGAL FAN/BLOWER.** This is a beautifully balanced, particularly quiet running unit giving approx. 90 cubic ft./min. The motor is a 2 pole shaded pole Mycalox, drawing only 240ma on run. Weight 2 $\frac{1}{2}$  lbs. Size: case dia. 3.1 ins. width (case only) 3.125 ins. Width overall (inc. 5.25 ins. Aperture 3.125 ins x 1.85 ins. Offered well below makers price at £2.95. P. & P. 25p.

**Brand New "DISCUS" Centrifugal Blower by Watkins & Watson.** 240v. 50 Hz. Powered by A.E.I. continuous rating 2850 rpm motor. Cowl diameter 10". Outlet flange 2" I.D. Coupling flange supplied. These superb precision units are ideally suited for Organ construction. Offered at approx. half makers price £12.50. Carriage £1.50.

#### PLUNGER SWITCHES.

Spring return 3 P.D.T. 1 amp. Single action. Size: 1 $\frac{1}{2}$ " x  $\frac{1}{2}$ " plus plunger. £1.50 per doz. Carr. Paid

**"HONEYWELL" TYPE 23AC-NE.** 15 amp. change-over micro switch is fitted on angled metal mount with spring-loaded plastic rod operating cam. 50p. each.

**VINKOR POT CORE ASS. TYPE LA.** 2103 (core LA. 2100). Normal price £1.48. Our price 75p each. Special quote for quantity.

**UNISELECTORS.** 8 Bank 25-way, 24 volt Double sweep. Brand new in maker's boxes £5.25 P. & P. 25p.

**Special offer of AMPEX professional tape heads.** mu-metal shrouded. (Designed for model AG20). Full track record, or playback, £3.00. Erase head £2.00. Set of 3 with mounting bracket and cover £7.50. Half track record only. £3.00 each. Carriage paid.



**"BENSON BROS." 12v. D.C. HEAVY DUTY SOLENOID.** Size: 3" overall x  $\frac{1}{2}$ " x 1". Very powerful, with secondary low current hold coil. Cont. rated £1.00 each. P. & P. 15p.

**"DECCO" MAINS SOLENOID.** Compact and very powerful. 16 lb. pull.  $\frac{1}{2}$ " travel which can be increased to 1" by removing captive-end-plate. Overall size 2" x  $\frac{1}{2}$ " x 2 $\frac{1}{2}$ " high. £4.50. P. & P. 25p.

**"MAGNETIC DEVICES" Mains Solenoid.** 2" x  $\frac{1}{2}$ " x  $\frac{1}{2}$ " approx. 2lb. pull. Plunger Travel  $\frac{1}{2}$ ". New in makers boxes; offered at half original cost. 75p. P. & P. 25p.

**"FIBRE GLASS" COPPER CLAD.** Top grade. One size only. 7 $\frac{1}{2}$ " x 4 $\frac{1}{2}$ " x  $\frac{1}{16}$ ". 3 panels £1.00. 12 panels £3.50. P. & P. 15p.

**"SRBP" COPPER CLAD.** Sizes: 7 $\frac{1}{2}$ " x 4 $\frac{1}{2}$ " x  $\frac{1}{16}$ ", 16 for £1.00. 14 $\frac{1}{2}$ " x 5 $\frac{1}{2}$ " x  $\frac{1}{16}$ ", 8 for £1.00. 19 $\frac{1}{2}$ " x 7 $\frac{1}{2}$ " x  $\frac{1}{16}$ ", 4 for £1.00.

**SLIDER SWITCHES.** 3 amp. type 3 P.D.T. 1" x  $\frac{1}{2}$ " x  $\frac{1}{2}$ " deep. 1 amp. type 3 P.D.T. 1" x  $\frac{1}{2}$ " x  $\frac{1}{2}$ " deep. £1.25 per doz. Either type or mixed as required. Carr. Paid.

**L.T. TRANSFORMERS.** Prim. 0-110-240v. Sec. 4.5-0-4.5v. at 1 amp. Size: 1 $\frac{1}{2}$ " x 1 $\frac{1}{2}$ " x 1 $\frac{1}{2}$ ". 60p. P. & P. 15p. Prim. 220/240 v. Sec. 0-5-10-15-20 v. at 2 amps. £1.25. P. & P. 15p.

Prim. 200/240v. Sec. 0-1-56-58-60 at 3.5 amps plus 0-90 at 100 ma. wax impregnated with screw term blocks. Weight 10 lbs £3.60 plus 40p P. & P.

**CURRENT FLOW INDICATOR.** Ideal for all types of battery operated equipment (portable machines, tape recorders etc.). Four white segments appear when current flows. Coil is 600 $\Omega$  6/12v. Drawing only 8 ma on function. Neat in appearance. Size: dia.  $\frac{1}{2}$ " x 1 $\frac{1}{2}$ " deep. Fixing centres  $\frac{1}{2}$ ". £1.25 each. Carr. Paid.



## ELECTRO-TECH SALES

**BUSINESS HOURS:**  
9.30-6 (1 p.m. Sat.)

**264 PENTONVILLE ROAD, LONDON, N.1**  
P.W.10 (ONE MIN. FROM KINGS X STATION)

Tel. 01-837 74012

# YOUR CAREER in RADIO & ELECTRONICS ?

Big opportunities and big money await the qualified man in every field of Electronics today—both in the U.K. and throughout the world. We offer the finest home study training for all subjects in radio, television, etc., especially for the **CITY & GUILDS EXAMS** (Technicians' Certificates); the Grad. Brit. I.E.R. Exam.; the **RADIO AMATEUR'S LICENCE**; P.M.G. Certificates; the R.T.E.B. Servicing Certificates; etc. Also courses in Television; Transistors; Radar; Computers; Servo-mechanisms; Mathematics and Practical Transistor Radio course with equipment. We have **OVER 20 YEARS'** experience in teaching radio subjects and an unbroken record of exam. successes. We are the only privately run British home study College specialising in electronics subjects only. Fullest details will be gladly sent without any obligation.

To: British National Radio School, Reading, Berks.

Please send FREE BROCHURE to

NAME ..... Block

ADDRESS ..... Caps.

..... Please

10/71

**BRITISH NATIONAL RADIO SCHOOL**

## UNBEATABLE RUSSIAN VALUE



**TECHNICAL DATA :**  
Waveband (frequency)  
LW 2000-735-5m.  
MW 571.4-185-9m  
SW3 53.1-40.54p  
SW2 31.91-24.79m  
SW1 19.87-16.76m  
VHF 3.43-288m  
(5-104 mc/s)  
17 transistors, 8 diodes

**SEBA ELECTRONICS, Dept. M/O, 104 Uxbridge Road, Hanwell, London, W7.**  
Phone: 01-579 5644

**PERFORMANCE CAN BE COMPARED WITH 265 RADIOS!**  
Sockets for tape recorder, record player, extension speaker, earphone, external power supply (12v DC), external line and dipole aerials. Battery life approx. 800 hours.

At last, the Astrad Solar Radio combining quality with value and a specification not before available from Russia. Designed for the man who appreciates the extras necessary for quality performance. This 6 waveband Radio has twin speakers for quality. Fully independent Treble and Bass tone controls for ultimate performance and twin separate tuning controls for AM & FM broadcasts. 12 push buttons for waveband selection including automatic frequency control on VHF. This is the big set from Russia, overall dimensions—14" x 9 $\frac{1}{2}$ " x 4 $\frac{1}{2}$ ". Included in this incredible specification is an inbuilt tuning meter to ensure that you are spot-on the station you select. Telescopic aerial on universal joint and a push-button dial light. All presented in a luxurious padded case with carrying handle. This fabulous Radio is fully warranted for 1 year. Only limited supplies available at a never to be repeated price.

#### NEW BUDGET PRICES

**£22-97**

Earphones 25p. P. & P. 75p

## A CASE FOR "IMPEX"

**PROBLEM :** I have a tuner, timer, mixer and digital clock for which I require suitable cases.

**ANSWER :** "IMPEX" Instrument Cases.

**PROBLEM :** All the instruments are different sizes.

**ANSWER :** "IMPEX" have a standard range of 36 sizes.

**PROBLEM :** I want them to be robust and stylish.

**ANSWER :** "IMPEX" cases are both functional and attractive.

**PROBLEM :** My budget is strictly limited.

**FINAL ANSWER :** "IMPEX" cases are very competitively priced.

Find out how they answer many problems. Details from:

**"IMPEX"**

**P.O. Box 2BB, Newcastle-upon-Tyne. NE99 2BB.**  
(Makers of the M.S.T. Magnetic Pickup Pre-amplifier)

## TRANSISTORS

NEW LIST—NEW PRICES  
SEND FOR FREE COPY TODAY  
Brand New Fully Guaranteed

|             |             |             |
|-------------|-------------|-------------|
| 2N404 20p   | BC107 12p   | BY213 25p   |
| 2N696 15p   | BC108 12p   | BY215 100   |
| 2N697 15p   | BC110 12p   | GET880 37p  |
| 2N706 10p   | BC113 15p   | MAT100 25p  |
| 2N706A 12p  | BC114 25p   | MAT101 80p  |
| 2N930 25p   | BC115 20p   | MAT120 25p  |
| 2N1131 25p  | BC116 25p   | MAT121 30p  |
| 2N1132 25p  | BC116A 25p  | MAT122 30p  |
| 2N1302 25p  | BC118 25p   | MJ2901 25p  |
| 2N1303 20p  | BC119 35p   | MJE370 87p  |
| 2N1304 25p  | BC124 25p   | MJE620 87p  |
| 2N1305 25p  | BC135 20p   | MJE2955     |
| 2N1306 25p  | BC136 22p   | 21 37       |
| 2N1307 25p  | BC137 25p   | MJE305 587p |
| 2N1308 25p  | BC138 25p   | MFF102 42p  |
| 2N1309 25p  | BC147 17p   | MFF103 32p  |
| 2N1613 25p  | BC148 12p   | MFF104 37p  |
| 2N1711 25p  | BC149 20p   | MFF105 40p  |
| 2N2147 75p  | BC154 37p   | NKT217 40p  |
| 2N2160 60p  | BC157 20p   | NKT277 20p  |
| 2N2218 20p  | BC168 17p   | NKT403 75p  |
| 2N2219 20p  | BC169 15p   | NKT494 62p  |
| 2N2222 20p  | BC169C 15p  | OA5 20p     |
| 2N2222A 25p | BC177 25p   | OA9 10p     |
| 2N2369 20p  | BC178 25p   | OA10 25p    |
| 2N2494 35p  | BC179 27p   | OA17 10p    |
| 2N2646 50p  | BC182L 12p  | OA70 10p    |
| 2N2904 20p  | BC185L 12p  | OA73 10p    |
| 2N2904A 25p | BC184 15p   | OA79 10p    |
| 2N2905 25p  | BC212 12p   | OA81 10p    |
| 2N2906 20p  | BCY30 25p   | OA85 12p    |
| 2N2906A 25p | BCY31 30p   | OA90 10p    |
| 2N2907 25p  | BCY32 50p   | OA91 7p     |
| 2N2926 10p  | BCY33 25p   | OA95 7p     |
| 2N3011 25p  | BCY34 30p   | OA200 7p    |
| 2N3055 20p  | BCY34 30p   | OA202 10p   |
| 2N3054 50p  | BCY39 85p   | OC16 50p    |
| 2N3055 75p  | BCY40 50p   | OC20 97p    |
| 2N3525      | BCY58 25p   | OC22 60p    |
| 2N3701 10p  | BCY59 25p   | OC23 60p    |
| 2N3703 10p  | BCY70 15p   | OC24 60p    |
| 2N3704 15p  | BCY72 15p   | OC25 37p    |
| 2N3705 15p  | BCY78 30p   | OC26 25p    |
| 2N3707 15p  | BCY79 30p   | OC28 60p    |
| 2N3709 10p  | BCZ10 30p   | OC29 60p    |
| 2N3710 10p  | BCZ11 30p   | OC35 50p    |
| 2N3819 25p  | BD112 30p   | OC41 25p    |
| 2N3820 60p  | BD121 65p   | OC42 30p    |
| 2N4068 15p  | BD123 80p   | OC43 40p    |
| 2N4061 15p  | BD124 75p   | OC44 17p    |
| 2N5457 30p  | BD125 50p   | OC45 15p    |
| 2N5458 37p  | BD131 75p   | OC71 15p    |
| 2N5469 50p  | BD132 75p   | OC72 25p    |
| 2N5801 50p  | BD153 62p   | OC73 30p    |
| 2N5802 50p  | BD156 57p   | OC73 30p    |
| 2N5803 50p  | BDY102L 25p | OC74 30p    |
| 2N5804 75p  | BDY112L 62p | OC75 25p    |
| 40250 50p   | BDY172L 50p | OC76 25p    |
| 40361 50p   | BDY182L 75p | OC77 40p    |
| 40362 55p   | BDY183L 87p | OC81 25p    |
| AAV30 10p   | RDY612L 25p | OC82 25p    |
| AAV42 15p   | RDY621L 10p | OC83 25p    |
| AAZ13 12p   | BF115 25p   | OC84 25p    |
| AAZ17 10p   | BF152 30p   | OC139 25p   |
| AC107 37p   | BF154 40p   | OC140 30p   |
| AC126 25p   | BF155 30p   | OC141 62p   |
| AC127 25p   | BF159 60p   | OC170 25p   |
| AC128 25p   | BF167 25p   | OC171 30p   |
| AC176 25p   | BF170 35p   | OC200 40p   |
| AC187 30p   | BF173 30p   | OC201 70p   |
| AC188 30p   | BF177 30p   | OC202 80p   |
| ACV17 30p   | BF178 30p   | OC203 40p   |
| ACV18 25p   | BF179 40p   | OC204 40p   |
| ACV19 25p   | BF180 35p   | OC205 75p   |
| ACV20 20p   | BF181 35p   | OC206 90p   |
| ACV21 20p   | BF182 30p   | OC207 90p   |
| ACV22 10p   | BF184 30p   | OC217 30p   |
| ACV39 50p   | BF185 20p   | ORP12 50p   |
| AD140 15p   | BF194 17p   | ORP60 40p   |
| AD140 50p   | BF195 15p   | ORP61 42p   |
| AD149 50p   | BF196 15p   | TP28A 50p   |
| AD161 37p   | BF197 15p   | TP30A 60p   |
| AD162 37p   | BF200 37p   | TP32A 62p   |
| AF114 25p   | BF274 37p   | TP32A 75p   |
| AF115 25p   | BFX13 25p   | TP33A 75p   |
| AF116 25p   | BFX29 25p   | 21-00       |
| AF117 25p   | BFX30 25p   | TP34A 22-00 |
| AF118 62p   | BFX37 32p   | TP34S 40p   |
| AF124 25p   | BFX84 25p   | TP360 22p   |
| AF125 20p   | BFX85 30p   | TP360 22p   |
| AF126 17p   | BFX86 25p   | TP361 25p   |
| AF127 17p   | BFX87 25p   | TP362 27p   |
| AF139 30p   | BFX88 20p   | ZTX107 15p  |
| AF178 47p   | BFY15 30p   | ZTX108 15p  |
| AF179 85p   | BFY50 22p   | ZTX300 15p  |
| AF180 55p   | BFY61 20p   | ZTX301 15p  |
| AF181 45p   | BFY62 15p   | ZTX302 20p  |
| AF186 40p   | BFY63 17p   | ZTX303 20p  |
| AF239 40p   | BFY90 65p   | ZTX304 25p  |
| ASV26 25p   | BSX20 17p   | ZTX305 25p  |
| ASV27 32p   | BSX21 20p   | ZTX306 25p  |
| ASV28 25p   | BSX76 15p   | ZTX307 25p  |
| ASV29 30p   | BSV85 25p   | ZTX308 25p  |
| ASV67 47p   | BSV86 15p   | ZTX309 25p  |
| ASZ21 42p   | BY100 15p   | ZTX331 30p  |
| BA115 7p    | BY126 15p   |             |
| BA164 10p   | GY127 20p   |             |
| BA173 6p    | HY182 85p   |             |
| BA186 7p    | BY210 40p   |             |
| BAV31 7p    | BY211 30p   |             |
| BAV32 17p   | BY212 30p   |             |

## HENRY'S LOW COST INTEGRATED CIRCUITS

WE OFFER FROM STOCK AN EXCLUSIVE RANGE OF BRAND NEW CERAMIC FULL SPECIFICATION LOW COST TTL 7400 RANGE BY I.T.T., TEXAS, FAIRCHILD

| Part No. | Description                                                        | 1-24  | 25-99 | 100   | 250+ |
|----------|--------------------------------------------------------------------|-------|-------|-------|------|
| 7400     | Quadruple 2-input NAND Gate                                        | 20p   | 18p   | 15p   | 13p  |
| 7401     | Quadruple 2-input Positive NAND Gate (with open collector output)  | 20p   | 18p   | 15p   | 13p  |
| 7402     | Quadruple 2-input Positive NOR Gates                               | 20p   | 18p   | 15p   | 13p  |
| 7403     | Quadruple 2-input Positive NAND Gates (with open collector output) | 20p   | 18p   | 15p   | 13p  |
| 7404     | Hex Inverters                                                      | 20p   | 18p   | 15p   | 13p  |
| 7405     | Hex Inverter with open collector                                   | 20p   | 18p   | 15p   | 13p  |
| 7410     | Triple 3-input Positive NAND Gates                                 | 20p   | 18p   | 15p   | 13p  |
| 7412     | Dual 4-input Schmitt Trigger                                       | 35p   | 32p   | 28p   | 25p  |
| 7420     | Dual 4-input Positive NAND Gates                                   | 20p   | 18p   | 15p   | 13p  |
| 7430     | 8-input Positive NAND Gates                                        | 20p   | 18p   | 15p   | 13p  |
| 7440     | Dual 4-input Positive NAND Buffers                                 | 20p   | 18p   | 15p   | 13p  |
| 7441     | BCD to decimal nixie driver                                        | 87p   | 77p   | 66p   | 60p  |
| 7442     | BCD to decimal decoder (4-10 lines, 1 of 10)                       | 87p   | 77p   | 66p   | 60p  |
| 7447     | BCD-Reven-Segment Decoder/Drivers (15-V Output)                    | 1-10  | 1-10  | 1-10  | 1-10 |
| 7450     | Expandable dual 2-input AND-OR-INVERT                              | 20p   | 18p   | 15p   | 13p  |
| 7451     | Dual 2-wide 2-input AND-OR-INVERT GATES                            | 20p   | 18p   | 15p   | 13p  |
| 7453     | Quad 2-input Expandable AND-OR-INVERT                              | 20p   | 18p   | 15p   | 13p  |
| 7454     | 4-wide 2-input AND-OR-INVERT GATES                                 | 20p   | 18p   | 15p   | 13p  |
| 7450     | Dual 4-input Expander                                              | 20p   | 18p   | 15p   | 13p  |
| 7470     | Single-phase J-K Flip-Flop                                         | 85p   | 32p   | 28p   | 25p  |
| 7472     | Master-slave J-K Flip-Flop                                         | 43p   | 40p   | 37p   | 33p  |
| 7473     | Dual Master-slave J-K Flip-Flop                                    | 43p   | 40p   | 37p   | 33p  |
| 7474     | Dual O type Flip-Flop                                              | 43p   | 40p   | 37p   | 33p  |
| 7475     | Quad latch                                                         | 47p   | 45p   | 43p   | 40p  |
| 7476     | Dual J-K with pre-set and clear                                    | 47p   | 45p   | 43p   | 40p  |
| 7480     | Full Adder                                                         | 87p   | 77p   | 66p   | 60p  |
| 7481     | 16-bit read/write memory                                           | 1-30  | 1-25  | 1-15  | 1-10 |
| 7482     | 2-bit Binary Full Adders                                           | 1-30  | 1-20  | 1-10  | 85p  |
| 7483     | Quad Full Adder                                                    | 87p   | 77p   | 66p   | 60p  |
| 7484     | Quad 2 input Exclusive OR Gates                                    | 80p   | 70p   | 60p   | 50p  |
| 7489     | BCD decade counter                                                 | 87p   | 77p   | 66p   | 60p  |
| 7491     | 8-bit Shift Registers                                              | 21-31 | 21-30 | 21-30 | 75p  |
| 7492     | Divide-by-Two counters                                             | 87p   | 77p   | 66p   | 60p  |
| 7493     | 4-bit Binary Counters                                              | 87p   | 77p   | 66p   | 60p  |
| 7494     | Dual entry 4-bit shift register                                    | 87p   | 77p   | 66p   | 60p  |
| 7495     | 4-bit up-down shift register                                       | 87p   | 77p   | 66p   | 60p  |
| 7496     | 5-bit Parallel in parallel out Shift Register                      | 87p   | 77p   | 66p   | 60p  |
| 74100    | 8-bit Bistable Latches                                             | 1-10  | 1-10  | 1-10  | 1-10 |
| 74118    | Hex Set-Reset Latches                                              | 1-30  | 1-20  | 1-10  | 85p  |
| 74121    | Monostable Multivibrators                                          | 87p   | 77p   | 66p   | 60p  |
| 74141    | BCD-to-Decimal Decoder/Driver                                      | 87p   | 77p   | 66p   | 60p  |
| 74145    | BCD-to-Decimal Decoder/Drivers                                     | 1-30  | 1-20  | 1-10  | 1-10 |
| 74151    | 8-bit Data Selectors (with Strobes)                                | 1-10  | 1-10  | 1-10  | 1-10 |
| 74153    | Dual 4-Line-to-1-Line Data Selectors/Multiplexers                  | 1-10  | 1-10  | 1-10  | 1-10 |
| 74181    | Binary Counter reversible                                          | 2-50  | 2-25  | 2-20  | 1-10 |

Devices may be mixed to quality for quantity price.  
Data available for above series in booklet form, price 10p. (Ref No. 30).  
Larger quantity prices Ext'n. 4. Dual Inline 14 Pin Socket 30p each 16 Pin 35p each.

## SILICON RECTIFIERS

### 1 AMP MINIATURE WIRE ENDED PLASTIC RECTIFIERS

| Type   | P.I.V. | 1-49 | 50+ | 100+ | 500+ | 1000+ |
|--------|--------|------|-----|------|------|-------|
| IN4001 | 50     | 7p   | 6p  | 5p   | 4p   | 4p    |
| IN4002 | 100    | 8p   | 7p  | 6p   | 5p   | 4p    |
| IN4003 | 200    | 10p  | 9p  | 7p   | 6p   | 5p    |
| IN4004 | 400    | 10p  | 9p  | 8p   | 7p   | 6p    |
| IN4005 | 600    | 12p  | 10p | 9p   | 7p   | 6p    |
| IN4006 | 800    | 15p  | 14p | 12p  | 11p  | 9p    |
| IN4007 | 1000   | 20p  | 18p | 15p  | 12p  | 10p   |

### 1.5 AMP MINIATURE WIRE ENDED PLASTIC RECTIFIERS

| Type   | P.I.V. | 1-49 | 50+ | 100+ | 500+ | 1000+ |
|--------|--------|------|-----|------|------|-------|
| PL4001 | 50     | 10p  | 9p  | 7p   | 6p   | 5p    |
| PL4002 | 100    | 11p  | 10p | 8p   | 7p   | 6p    |
| PL4003 | 200    | 12p  | 11p | 10p  | 9p   | 8p    |
| PL4004 | 400    | 12p  | 11p | 10p  | 9p   | 8p    |
| PL4005 | 600    | 15p  | 13p | 11p  | 10p  | 9p    |
| PL4006 | 800    | 17p  | 15p | 12p  | 11p  | 9p    |
| PL4007 | 1000   | 20p  | 17p | 15p  | 12p  | 10p   |

### 3 AMP PLASTIC WIRE ENDED RECTIFIERS

| Type   | P.I.V. | 1-49 | 50+ | 100+ | 500+ | 1000+ |
|--------|--------|------|-----|------|------|-------|
| PL7001 | 50     | 20p  | 18p | 17p  | 15p  | 13p   |
| PL7002 | 100    | 20p  | 18p | 17p  | 15p  | 13p   |
| PL7003 | 200    | 22p  | 20p | 19p  | 18p  | 16p   |
| PL7004 | 400    | 25p  | 23p | 21p  | 20p  | 18p   |
| PL7005 | 600    | 28p  | 24p | 23p  | 22p  | 20p   |
| PL7006 | 800    | 27p  | 25p | 24p  | 23p  | 21p   |
| PL7007 | 1000   | 30p  | 28p | 26p  | 24p  | 22p   |

### POTTED BRIDGE RECTIFIERS (SILICON) SIZE 1 x 1 x 1 in.

| Type | P.I.V. | rent   | 1-49 | 50+  | 100+ | 500+ |
|------|--------|--------|------|------|------|------|
| 1002 | 100    | 2 amps | 60p  | 55p  | 50p  | 45p  |
| 2002 | 200    | 2 amps | 70p  | 65p  | 60p  | 55p  |
| 4002 | 400    | 2 amps | 80p  | 75p  | 70p  | 65p  |
| 1004 | 100    | 4 amps | 70p  | 65p  | 60p  | 55p  |
| 2004 | 200    | 4 amps | 75p  | 70p  | 65p  | 60p  |
| 4004 | 400    | 4 amps | 80p  | 75p  | 70p  | 65p  |
| 6002 | 600    | 2 amps | 90p  | 80p  | 75p  | 70p  |
| 6004 | 600    | 4 amps | 90p  | 80p  | 75p  | 70p  |
| 1006 | 100    | 6 amps | 75p  | 70p  | 65p  | 60p  |
| 2006 | 200    | 6 amps | 80p  | 75p  | 70p  | 65p  |
| 4006 | 400    | 6 amps | 110p | 100p | 90p  | 80p  |
| 6006 | 600    | 6 amps | 125p | 110p | 100p | 90p  |

### DISCOUNTS

|              |          |          |
|--------------|----------|----------|
| 15% 12+      | 10% 100+ | 5% 1000+ |
| Any one type |          |          |

## SEMI-CONDUCTORS

LOOK AT THESE PRICES FOR QUANTITIES FROM STOCK

|                                                                                             |                                                                                            |
|---------------------------------------------------------------------------------------------|--------------------------------------------------------------------------------------------|
| <b>AF114 Mullard 25p</b><br>25 + 20p<br>100 + 17p<br>500 + 15p                              | <b>AF115 Mullard 25p</b><br>25 + 20p<br>100 + 17p<br>500 + 15p                             |
| <b>AF116 Mullard 25p</b><br>25 + 20p<br>100 + 17p<br>500 + 15p                              | <b>AF117 Mullard 25p</b><br>25 + 20p<br>100 + 17p<br>500 + 15p                             |
| <b>2N3055 75p</b><br>Mullard 115watt<br>Silicon Power<br>25 + 35p<br>100 + 25p<br>500 + 50p | <b>2N3819 Texas 35p</b><br>25 + 30p<br>100 + 25p<br>500 + 20p<br>1000 + 18p                |
| <b>BFY90 65p</b><br>1000 MC/S<br>25 + 60p<br>100 + 55p<br>500 + 50p                         | <b>2N2646 40p</b><br>Motorola<br>Unijunction<br>25 + 35p<br>100 + 30p<br>500 + 25p         |
| <b>AF139 30p</b><br>Siemens V.H.F.<br>25 + 25p<br>100 + 22p<br>500 + 19p                    | <b>AF186 40p</b><br>Mullard V.H.F.<br>25 + 35p<br>100 + 30p<br>500 + 25p                   |
| <b>OC170 Mullard 25p</b><br>25 + 21p<br>100 + 17p<br>500 + 15p                              | <b>BYZ13 25p</b><br>Mullard 6a 200v<br>25 + 20p<br>100 + 17p<br>500 + 15p                  |
| <b>OC171 Mullard 30p</b><br>25 + 27p<br>100 + 22p                                           | <b>BC107, BC108, BC109 12p each</b><br>I.T.T. Planars<br>25 + 11p<br>100 + 10p<br>500 + 8p |
| <b>BY127 Mullard 20p</b><br>1000v 1 amp Plastic<br>25 + 17p<br>100 + 15p<br>500 + 13p       | <b>OC71 97p</b><br>Mullard Photo<br>25 + 85p<br>100 + 80p<br>500 + 75p                     |
| <b>BC113 SGS 15p</b><br>25 + 13p<br>100 + 11p<br>500 + 9p                                   | <b>OC28 62p</b><br>Mullard Power<br>25 + 55p<br>100 + 50p<br>500 + 42p                     |
| <b>OA202 10p</b><br>SILICON Diodes<br>25 + 8p<br>100 + 6p<br>500 + 5p<br>1000 + 4p          | <b>OC71 Mullard 15p</b><br>25 + 12p<br>100 + 10p<br>500 + 8p                               |
| <b>OC42 Mullard 30p</b><br>25 + 25p<br>100 + 23p<br>500 + 21p<br>1000 + 18p                 | <b>ORP12 Mullard 50p</b><br>25 + 45p<br>100 + 42p<br>500 + 40p                             |
| <b>OC45 Mullard 15p</b><br>25 + 13p<br>100 + 12p<br>500 + 10p<br>1000 + 8p                  | <b>2N930 25p</b><br>25 + 23p<br>100 + 20p<br>500 + 17p<br>1000 + 15p                       |
| <b>OC75 Mullard 25p</b><br>25 + 21p<br>100 + 17p<br>500 + 15p<br>1000 + 13p                 | <b>OC72 Mullard 25p</b><br>25 + 20p<br>100 + 17p<br>500 + 15p<br>1000 + 13p                |
| <b>OC20 97p</b><br>Mullard 100v<br>25 + 85p<br>100 + 80p<br>500 + 75p                       | <b>OC83 25p</b><br>25 + 20p<br>100 + 17p<br>500 + 15p<br>1000 + 13p                        |
| <b>OC44 Mullard 17p</b><br>25 + 15p<br>100 + 13p<br>500 + 11p<br>1000 + 10p                 | <b>OC84 25p</b><br>25 + 20p<br>100 + 17p<br>500 + 15p<br>1000 + 13p                        |
| <b>OC139 Mullard 25p</b><br>25 + 20p<br>100 + 17p<br>500 + 15p                              | <b>AF239 42p</b><br>25 + 35p<br>100 + 30p<br>500 + 25p<br>1000 + 20p                       |
| <b>OC81 Mullard 25p</b><br>25 + 20p<br>100 + 17p<br>500 + 15p                               |                                                                                            |

# 28watts, r.m.s. 40Hz to 40kHz $\pm 3\text{dB}$



## Viscount III Audio Suite complete £49

There are two stereo amplifiers—the R100 for ceramic cartridges, the R101 for magnetic. Both incorporate FETs (FIELD EFFECT TRANSISTORS), just like top-priced units. FETs give you more of the signal you want, and almost none of the background hiss you don't. Both units have a jack socket to plug in headphones and there's a separate output for tape recorder. Filters (an unusual feature in this price range) and tone controls give a wide range of bass and treble adjustment which compensate for input deficiencies and domestic acoustic conditions.

**PRICES SYSTEM 1**  
Viscount III R101 amplifier £22.00 + 90p p&p  
2 x Duo Type II speakers, £14.00 + £2 p&p  
Garrard SP25 Mk. III with MAG.  
cartridge plinth and cover £23.00 + £1.50 p&p

Total £59.00

Available complete for only £52.00 + £3.50 p&p

**SYSTEM 2**  
Viscount R101 amplifier £22.00 + 90p p&p  
2 x Duo Type III speakers £32.00 + £3 p&p  
Garrard SP25 Mk. III with MAG.  
cartridge, plinth and cover £23.00 + £1.50 p&p

Total £77.00

Available complete for £69 + £4 p&p

**SYSTEM 3**  
Viscount III Amplifier R100 £17.00 + 90p p&p  
2 x Duo Type II speakers, pair £14.00 + £2 p&p  
Garrard SP25 Mk. III with CER. diamond  
cartridge, plinth and cover £21.00 + £1.50 p&p

Total £52.00

Available complete for only £49.00 + £3.50 p&p

### SPEAKERS Duo Type II

Size 17" x 10½" x 6½". Drive unit 13" x 8" with parasitic tweeter. Max. power 10 watts, 3 ohms. Simulated Teak cabinet. £14 pair + £2 p&p.

Duo Type III Size 23½" x 11½" x 9½". Drive unit 13½" x 8½" with H.F. speaker. Max. power 20 watts at 3 ohms. Freq. range 20Hz to 20kHz. Teak veneer cabinet. £32 pair + £3 p&p.

### SPECIFICATION R100/101


14 watts per channel into 3 to 4 ohms. Total distortion @ 10W @ 1kHz 0.1%. P.U.1 (for ceramic cartridges) 150mV into 3 Meg. P.U.2 (for magnetic cartridges) 4mV @ 1kHz into 47K, equalised within  $\pm 1\text{dB}$  R.I.A.A. Radio 150mV into 220K. (Sensitivities given at full power). Tape out facilities; headphone socket, power out 250mV per channel. Tone controls and filter characteristics. Bass: +12dB to -17dB @ 60Hz. Bass filter: 6dB per octave cut. Treble control: treble +12dB to -12dB @ 15kHz. Treble filter: 12dB per octave. Signal to noise ratio: (all controls at max) R101—P.U.1 and radio—65dB. P.U.2. —58dB. R100 same as R101 but P.U.2 (for crystal cartridges) 450mV into 3 Meg. Cross talk better than -35dB on all inputs. Overload characteristics better than 26dB on all inputs. Size 13½" x 9" x 3½".

# R+TV

Radio and TV Components (Acton) Ltd, 21c High Street, Acton, London W3 6NG  
323 Edgware Road, London, W.2. Mail orders to Acton. Terms C.W.O. All enquiries S.A.E.  
Goods not despatched outside U.K.

# SOUND 50

50 WATT AMPLIFIER & SPEAKER SYSTEM

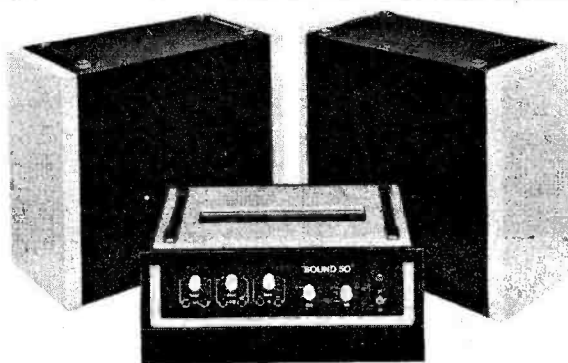

The Sound Fifty valve amplifier and speakers are sturdily constructed with smart housings and thoroughly tested electronics. They are designed to last—to withstand the knocks and bumps of life on the road. Built for the small and medium sized gig, they are easy to handle and quick to set up and can be relied upon to come over with all the quality and power you need.

Output Power: 45 watts R.M.S. (Sine wave drive). Frequency response: —3dB points 30Hz at 18KHz. Total distortion: less than 2% at rated output. Signal to noise ratio: better than 60dB.

Speaker Impedance: 3, 8 or 15 ohms. Bass Control Range: ±13dB at 60Hz. Treble Control Range: ±12dB at 10 KHz. Inputs: 4 inputs at 5mV into 470K. Each pair of inputs controlled by separate volume control. 2 inputs at 200mV into 470K.

To protect the output valves, the incorporated fail safe circuit will enable the amplifier to be used at half power.

**SPEAKERS!** Size 20" x 20" x 10" incorporating 12" heavy duty 25 watt high flux, quality loudspeaker with cast frame. Cabinets attractively finished in two tone colour scheme—Black and grey.

**COMPLETE SYSTEM £50** Plus £6 P. & P.  
Sound 50 amp and 2 speakers  
or available separately. Amplifier £28.50 plus £1.50 P. & P.  
Speakers £12.50 each plus £2.25 P. & P.

## RELIANT mk.IV



The Reliant Mk. IV provides a high standard of sound reproduction, with full mixing facilities. It's versatility makes it suitable for: Discotheque, P.A., Home Entertainment Applications, etc.

- \* Five Electronically Mixed Inputs
- \* Three Individual Mixing Controls
- \* Separate bass and treble controls common to all five inputs
- \* Mixer employing F.E.T. (Field Effect Transistor)
- \* Solid State Circuitry
- \* Attractive Styling

**£9.50** PRICE plus P. & P. 60p.

### SPECIFICATIONS

**INPUTS:**—1. Crystal Mic or Guitar 9mV. 2. Moving coil Mic or Guitar 8mV. Inputs 3, 4 & 5 are suitable for a wide range of medium output equipment (Gram, Tuner, Monitor, Organ, etc.) All 250mV sensitivity.

**CONTROLS:**—3 Volume controls. Bass control range ±13dB @ 60 Hz. Treble control range ±12dB @ 15KHz. Separate ON/OFF Switch, Neon Indicator.

**POWER OUTPUT:**—12 Watts R.M.S. into 3 to 4 ohms speaker.

**SIGNAL/NOISE:**—Better than —60db on inputs 3, 4 and 5 & —50db on 1 & 2.

**SUPPLY:**—220 — 250 AC. Mains.

**SIZE:**—12½" x 6" x 3½".

## THE ELEGANT SEVEN Mk. III

(350m W Output)




7 transistor fully-tunable M.W.—L.W. superhet portable. Set of parts. Complete with all components, including ready etched and drilled printed circuit board—back printed for foolproof construction.

**MAINS POWER PACK KIT:** 75p extra.

Price £5.25 plus 50p. P. & P.

Circuit 13p FREE WITH PARTS.

## THE DORSET (600m W Output)

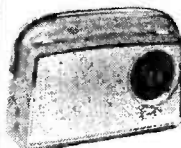


7-transistor fully tunable M.W.—L.W. superhet portable. Set of parts. The latest modulated and pre-alignment techniques make this simple to build. Sizes: 12 x 8 x 3in.

Price £5.25 plus 50p P. & P.

Circuit 13p FREE WITH PARTS
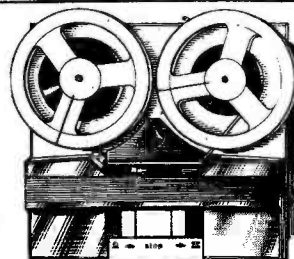
## CONTINENTAL 4 TRACK, 3 SPEED TAPE DECK



with high impedance heads

R.C. 74 tape deck. Three speeds—7½, 3½ and 1½ ips.

4-track record/playback head. Plus 4-track erase head. Positive pressure pad system. Takes any tape spool up to and including 7". The R.C. 74 is driven by a powerful 200/250V 50-cycle A.C. motor. A heavy, accurately balanced, flywheel brings wow and flutter levels down to approx. 0.3% total at 3½ and 7½ ips. Fast rewind in both directions.

Controls couldn't be simpler! Just five push buttons that interlock to cut out accidental tape damage. Efficient servo-action type braking. Easy drop-in tape loading.

The R.C. 74 comes with an attractive moulded deck cover, which has positions for tone and volume controls. The unit is built into a rigid die-cast frame, and overall size of the whole unit is 12½ x 11½ x 6 inches. Every single deck fully tested before dispatch. Spools not supplied.

Price complete £15-00. Plus 75p P. & P.

## TOURIST MARK 3 CAR RADIO



### ALL TRANSISTOR

Beautifully designed to blend with the interiors of all cars. Permeability tuning and long wave loading coils ensure excellent tracking, sensitivity and selectivity on both wave bands. R.F. sensitivity at 1MHz is better than 8 micro volts. Power output into 3 ohm speaker is 3 watts. Pre-aligned I.F. module and tuner together with comprehensive instructions guarantees success first time. 12 volts negative or positive earth. Size 7in x 2in x 4½in deep.

### SET OF PARTS

**£6.30**

plus P. & P. 50p.

See previous page  
for address

Circuit diagram 13p. Free with parts  
Speaker, baffle and fixing kit £1.25  
extra plus 25p. p. & p. Postage free  
when ordered with parts.

RADIO & TV COMPONENTS  
**R+TV**  
(ACTON) LIMITED



**ONLY FROM US! LATEST SHIPMENT JUST ARRIVED!**

**BRAND NEW 1971 Model!**

**RUSSIAN WORLD BEATER!**

**6 WAVEBAND 10 TRANSISTOR PORTABLE RADIO**

**WORLD WIDE RECEPTION**

**£9.97**

THOUSANDS OF TRANSMISSIONS AND STATIONS THE WORLD OVER!

BOX POST ETC. 43p

**NOT JUST A RADIO—BUT TECHNOLOGICAL MAGIC!**

THE LATEST 1971 MODEL, SUPERSEDING ALL PREVIOUS MODELS—FANTASTIC BRAND NEW RUSSIAN "MERIDIAN" 6-WAVEBAND PORTABLE RADIO. DESIGNED FOR WORLD WIDE RECEPTION. Only put into production after incorporation of every conceivable possible up-to-date technological improvement had been carefully considered and thoroughly examined. So advanced it will probably make your present radio seem like a "crystal set"! It's far better than any 6-wave radio even they have produced! Finest value we've ever offered! We're almost giving them away at £9.97—a mere fraction of even today's Russian miracle price! We challenge you to compare performance and value with that of £34 radios! ★ Instant refund if you are not astounded! Purer and sweeter tone than ever! Much wider band spread than hitherto for "pin-point" station selection. Once again the Russians have proved their fantastic ability in electronics—brilliantly reflecting their advanced micro-circuitry techniques in the field of spaceship and satellite communications. YOU GET THIS AMAZING SET FROM US AT A PRICE THAT BEARS NO RELATION TO TRUE VALUE! Yes, 6 separate wavebands, including Standard Long, Medium and Short Waves to cover world! Unique side control waveband selection unit gives incredible ease of station tuning! Thousands of different transmissions and stations at your fingertips 24 hours a day, even ships at sea and messages from all over world—nothing is secret! The radio enthusiast has the world in his hand! Superb, sweet tone—controlled from a whisper to a roar. Push-pull output! Separate ON/OFF volume and Treble Bass tone controls! Take it anywhere—runs economically on standard batteries. Internal ferrite aerial plus built-in telescopic aerial extending to full 33½ in. length. It's also a fabulous CAR RADIO—any speed, requires no additional aerial. UNIQUE! Elegant Black, White and Chrome finish case. SIZE 10½" x 8" x 3½" overall approx. Magnificently designed, made to give years of perfect service. With WRITTEN GUARANTEE, manual with simple operating instructions and circuit diagram. **ONLY £9.97, POST ETC. 43p.** Standard batteries 25p extra. Can also be used through extension amplifier, tape recorder or public address.

**SAVE £13.98 NOW!**

**FIRST CLASS MAKERS**

**BRAND NEW Cassette TAPE RECORDER and PLAYER**

**fabulous 1971 Model**

**RECOMMENDED LIST PRICE £26.97**

**OUR PRICE £12.99**

POST ETC 30p

WITH REMOTE CONTROL MICROPHONE

MAKE NO MISTAKE—this is the EXPENSIVE model with "PIANO KEYBOARD" CONTROL PANEL and "MAGIC FEE" AUTOMATIC RECORDING LEVEL.

SAVE £13.98! Due to price we cannot mention famous maker's name—but rest assured you're getting one of the BEST! 1971 cassette model—no fiddling with awkward tape and reels, just "slap-in a cassette and off you go! (takes 30, 60 or 90 minute standard Philips cassette tapes obtainable everywhere). Amazing performance ensures perfect tapings and superb reproduction! Remote control microphone. Separate volume control! Rapid rewind! Beautiful tone from a whisper to a roar! Completely self-contained—record anywhere. Separate jacks for remote control microphone, etc. Size 9" x 4½" x 2½" overall approx. With carry strap. **WRITTEN GUARANTEE** and instructions. Only £12.99, post 30p. Refund g'v'ee. **BONUS** one per customer: Cassette tape, set of standard batteries AND microphone stand all for 51p extra if required.

Send to Uxbridge Road or call at either store. (COMMERCIAL TRAVELLERS' NOTE: Merchandising Office at Holborn)

**SHOPUNITIES LTD. SL** Dept. WF/10, 184 UXBRIDGE RD. (Facing Shepherd's Bush Green)

London, W12 8AQ. (Thurs. 1, Fri. 7). Also 37, High Holborn, London. WC1 (Thursday 7 p.m.) Both Stores open from Monday to Saturday from 9 a.m. to 6 p.m.

## Train for tomorrow's world in Radio and Television at The Pembrige College of Electronics

### Your first day on Television: 5th January, 1972

This is your opportunity to train as a television and radio engineer on our full-time 2 year College Diploma Course. That is the way to get into a rapidly growing industry with a tremendous demand for skilled technicians. You will be given theoretical and practical instruction on colour television receivers, following a syllabus specially designed to cover the new City and Guilds Radio, Television and Electronic Technicians' Course.

Minimum entrance requirements are Senior Cambridge or 'O' Level, or equivalent in Mathematics and English.

Complete the coupon below and we will send you the details about training for an exciting, new career.



**To: The Pembrige College of Electronics, (Dept. PW6), 34a Hereford Road, London, W2 5AJ.**

Please send, without obligation, details of the Full-time Course in Radio, Television and Electronics.

NAME .....

ADDRESS .....

# AUDIO SUPPLIES

## SLASH PRICES! UP TO 60%

### SUPERB Plinths & Covers



ONLY

**£3.25** P. & P. 30p

for GARRARD and B.S.R. SP25, SL65B, 3500, 3000 2025TC, 2000, 1025, 5100, AT6, AT60, 40B, B.S.R. McDonald range. All decks are finished in teak polish and will blend in any modern home. The covers are of tinted Perspex (please state deck when ordering).

**SUPERIOR PLINTHS AND COVERS FOR GARRARD AP75, AP76, SL72B, SL75B and SL95B.**  
£4.99. P.P. 60p (R.R.P. £9.50)

#### STEREO AMPLIFIERS p.p. 50p

|                |        |
|----------------|--------|
| ARMSTRONG 521  | £40.00 |
| AMSTRAD 8000   | £15.00 |
| H.L. SA707     | £18.00 |
| TELETON SAQ206 | £16.00 |
| VICEROY VAS70  | £42.00 |
| VICEROY 55     | £16.00 |

|                                   |        |
|-----------------------------------|--------|
| SANSUI full range in stock P.O.A. |        |
| METRO SOUND ST20                  | £24.00 |
| SINCLAIR 2000 MkII                | £22.00 |
| SINCLAIR 3000                     | £32.00 |
| SINCLAIR NEOTERIC                 | £46.00 |
| SINCLAIR A.F.U.                   | £4.50  |
| SINCLAIR S60 + 2 Z30/PZ5          | £15.00 |
| SINCLAIR S60 + 2 Z30/PZ5          | £17.50 |
| SINCLAIR S60 + 2 Z50 + PZ8 and    |        |
| Mains trans.                      | £23.00 |

Sonab special offer for personal callers only

#### TUNER AMPLIFIERS p.p. 50p

|                             |         |
|-----------------------------|---------|
| ARMSTRONG 526               | £80.00  |
| ARMSTRONG 525               | £70.00  |
| RODGERS RAVENSBROOK         | P.O.A.  |
| TELETON CR107 with speakers | £25.50  |
| TELETON F2100               | £30.00  |
| PHILIPS RH781               | £165.00 |
| WHARFEDALE 100-1            | £53.00  |
| GOODMANS MODULE 80          | £72.00  |
| TELETON R8000 with speakers | £35.00  |
| TOSHIBA range P.O.A.        |         |

Sonab special offer for personal callers only

#### TUNERS p.p. 50p

|                            |        |
|----------------------------|--------|
| ARMSTRONG M8               | £7.75  |
| ARMSTRONG 523              | £40.00 |
| ARMSTRONG 524              | £31.00 |
| TELETON GT101              | £32.00 |
| SINCLAIR Pro. 60           | £19.50 |
| RODGERS RAVENSBROOK FET2   |        |
| Chassis                    | £45.00 |
| LEEK STEREO STETIC Chassis | £48.00 |

Easy to find—50 yards from (B.R.)  
Stoke Newington Stn.  
67, 149, 247, 73, 76, 243 Buses Pass our  
door.

STEREO LPs  
of the great  
musicians

3 for £1.15 free p. & p.

Send S.A.E. for lists

### WHY PAY MORE?

### Post Budget Purchase Tax Reductions.

Send S.A.E. for quote on  
equipment you require.

Most good  
manufacturers products  
available.

**GOODMANS MAGISTERS**  
£80.00 per pair, p. & p. £2.50

#### PICK-UP ARMS p.p. 45p

|                       |        |
|-----------------------|--------|
| SME 3009/S2           | £25.00 |
| SME 3012/S2           | £26.50 |
| GOLDRING L75          | £10.00 |
| GOLDRING L69          | £8.00  |
| AUDIO TECHNICA AT1005 | £16.25 |

**VISIT OUR 3-STORY WARE-  
HOUSE PACKED WITH HI-FI &  
STEREO EQUIPMENT. 1000's OF  
ITEMS ALWAYS AVAILABLE  
TO SELECT FROM.**

**FOR ALL YOUR NEEDS IN HI-FI  
EQUIPMENT SEND A LARGE S.A.E.  
or PAY A VISIT**

**2 SHOWROOMS DEVOTED TO  
DEMONSTRATING SPECIALLY  
SELECTED SYSTEMS**

### SPECIAL OFFERS

**GARRARD SP25 Mk. III  
GOLDRING G800 Superb Plinth  
and Cover.**

**SINCLAIR Project 60—Stereo 60  
Pre-Amplifier and Control Unit,  
2 Z30's and PZ5. 2 WHARFEDALE  
Unit 3. List Price £84.00. OUR PRICE  
£55. P. & P. £1.75.**

**GARRARD SP25 Mk III  
GOLDRING G800 H**

Plinth and Cover complete  
**OUR PRICE £18.00. P. & P. 75p.**

**ARMSTRONG 526  
GARRARD AP76  
SHURE M55E**

Plinth & Cover complete  
STE-MA 400 speakers  
**OUR PRICE £148.00. P. & P. £1.25**

#### CARTRIDGES p.p. 3p

|                     |        |
|---------------------|--------|
| GOLDRING G850       | £3.50  |
| GOLDRING G800H      | £5.00  |
| GOLDRING G800       | £7.00  |
| GOLDRING G800/E     | £10.75 |
| GOLDRING G800/SE    | £16.00 |
| SHURE M50           | £4.75  |
| SHURE M44/57/C      | £7.00  |
| SHURE M55E          | £8.00  |
| SHURE M75E type 2   | £15.00 |
| SHURE V15 type 2    | £30.00 |
| SHURE 44E           | £8.50  |
| SHURE 31E           | £8.00  |
| SHURE 32E           | £8.25  |
| SONATONE 9TAHCD     | £1.50  |
| AUDIO TECHNICA AT66 | £4.00  |
| ADC 10/E MkII       | £25.00 |

#### GARRARD 0/100 IN STOCK SPECIAL PRICE ON APPLICATION

#### TURNTABLES p.p. 60p

|                                                         |        |
|---------------------------------------------------------|--------|
| GARRARD SP25/Mk. III                                    | £10.00 |
| GARRARD 2025TC with Sonotone 9TAHC<br>Diamond Cartridge | £8.00  |
| GARRARD A70 Mk. II                                      | £19.97 |
| GARRARD SL65B                                           | £12.75 |
| GARRARD AP76                                            | £18.00 |
| GARRARD SL72B                                           | £25    |
| GARRARD SL75B                                           | £27.00 |
| GARRARD 401                                             | £27.40 |
| GARRARD SL95B                                           | £34    |
| GOLDRING GL75P                                          | £35    |
| GOLDRING GL75                                           | £28.50 |
| GOLDRING GL69                                           | £21    |
| THORENS TD125                                           | £82    |
| THORENS TD150AB/2                                       | £38    |
| PIONEER PL11AC complete                                 | £39    |
| Dual 1219                                               | £49    |
| DUAL 1209                                               | £34    |
| PHILIPS 202A                                            | £54    |

#### OPEN

Monday - Wednesday 9.30 a.m.-6 p.m.  
Half day Thursday until 1 p.m.  
Late night Friday until 8 p.m.  
**SATURDAY 9.30 a.m.-6 p.m.**

SEND CHEQUES, P.O., MONEY ORDER, etc. to—

# AUDIO SUPPLIES

PERSONAL CALLERS PLEASE NOTE—Cheques are only accepted when accompanied by a Bank Cheque Card (not Barclay Card).

PW10, 50 STAMFORD HILL, LONDON, N.16.  
Telephone: 01-806 3611/7311

All prices subject to change without notice

# The largest selection

## NEW LOW PRICE TESTED S.C.R.'s

| PIV | 1A   | 3A    | 7A    | 10A   | 18A   | 30A   |
|-----|------|-------|-------|-------|-------|-------|
|     | TO-5 | TO-66 | TO-66 | TO-48 | TO-48 | TO-48 |
| 50  | 0-25 | 0-25  | 0-47  | 0-50  | 0-53  | 1-15  |
| 100 | 0-25 | 0-25  | 0-57  | 0-58  | 0-58  | 1-40  |
| 200 | 0-25 | 0-25  | 0-57  | 0-61  | 0-75  | 1-40  |
| 400 | 0-43 | 0-47  | 0-77  | 0-75  | 0-98  | 1-75  |
| 600 | 0-53 | 0-57  | 0-77  | 0-97  | 1-25  | —     |
| 800 | 0-63 | 0-70  | 0-90  | 1-20  | 1-50  | 4-00  |

## SIL. RECTS. TESTED

| PIV  | 300mA | 750mA | 1A   | 1-5A | 3A   | 10A  | 30A  |
|------|-------|-------|------|------|------|------|------|
|      |       |       |      |      |      |      |      |
| 50   | 0-04  | 0-05  | 0-05 | 0-07 | 0-14 | 0-21 | 0-47 |
| 100  | 0-04  | 0-08  | 0-05 | 0-13 | 0-18 | 0-23 | 0-75 |
| 200  | 0-05  | 0-09  | 0-08 | 0-14 | 0-20 | 0-24 | 1-00 |
| 400  | 0-06  | 0-13  | 0-07 | 0-20 | 0-27 | 0-37 | 1-25 |
| 600  | 0-07  | 0-16  | 0-10 | 0-23 | 0-34 | 0-45 | 1-85 |
| 800  | 0-10  | 0-17  | 0-13 | 0-25 | 0-37 | 0-55 | 2-00 |
| 1000 | 0-11  | 0-25  | 0-15 | 0-30 | 0-46 | 0-63 | 2-50 |
| 1200 | —     | 0-33  | —    | 0-33 | 0-57 | 0-75 | —    |

## TRIACS

| VBO | 2A   | 6A    | 10A   |
|-----|------|-------|-------|
|     | TO-1 | TO-66 | TO-88 |
| 100 | 0-50 | 0-63  | 1-00  |
| 200 | 0-70 | 0-90  | 1-25  |
| 400 | 0-90 | 1-00  | 1-60  |

## 2A POTTED BRIDGE RECTIFIERS 200V 50p

## UNIJUNCTION

UT46. Eqty. 2N2646, Eqty. TIS43. BEX3000 27p each, 25-99 25p 100 UP 20p.

## NPN SILICON PLANAR

BC107/8/9, 10p each; 50-99, 5p; 100 up, 8p each; 1,000 off, 7p each. Fully tested and coded TO-18 case.

## FREE

One 50p Pak of your own choice free with orders valued \$4 or over.

## AF299 VHF GERM.

SIEMENS PNP TRANSISTORS. RF MIXER & OSC. USE AS REPLACEMENT FOR AF139-AF186 & 100's OF OTHER USE IN VHF. OUR SPECIAL LOW PRICE: 1-24 57p each, 25-99 34p each 100 + 30p each.

## FET'S

2N 3819 ..... 35p  
2N 3820 ..... 35p  
MFF105 ..... 80p

## CADMIUM CELLS

ORP12 43p  
ORP60, ORP61 40p each

## PHOTO TRANS.

OC771 Type. 43p

## SIL. G.P. DIODES

300mW. 30 0-50  
40P (Min.) 100 1-50  
Sub-Min. 500 1-50  
Full Tested 1,000 9-00  
Ideal for Organ Builders

## D18D1 Silicon Unilateral

switch 50p each.  
A Silicon Planar, monolithic integrated circuit having thyristor electrical characteristics, but with an anode gate and a built-in "Zener" diode between gate and cathode. Full data and application circuits available on request.

## SILICON HIGH VOLT.

AGE RECTIFIERS  
10-Amp 3-K.V. (3000 P.I.V.) Stud Type with Flying Leads, 80p each.

## DIACS

FOR USE WITH TRIACS  
BR100 ..... 87p each

## ADI61

NPN

## ADI62

PNP

MATCHED COMPLEMENTARY PAIRS OF GERM. POWER TRANSISTORS.

For mains driven output stage of Amplifiers and Radio receivers. OUR LOWEST PRICE OF 63p PER PAIR

## 2N3055 115 WATT SIL.

POWER NPN  
OUR PRICE 63p EACH

## FULL RANGE OF

ZENER DIODES  
VOLTAGE RANGE  
2-33V. 400mW (DO-7 Case) 13p ea. 11W (Top-Hat) 18p ea. 10W (80-Stud) 25p ea. All fully tested 5% tol. and marked. State voltage required.

## BRAND NEW TEXAS

GERM. TRANSISTORS  
Coded and Guaranteed  
Pak No. Eqty.  
T1 8 2G371A OC71  
T2 8 2G374 OC75  
T3 8 2G374A OC81D  
T4 8 2G381A OC81  
T5 8 2G382T OC82  
T6 8 2G344A OC44  
T7 8 2G345A OC45  
T8 8 2G378 OC78  
T9 8 2G389A 2N1302  
T10 8 2G417 AF117  
All 50p each pak

## 2N2060 NPN SIL. DUAL

TRANS. CODE D1899  
TEXAS. Our price 25p each.

## 120 VCB MIXIE DRIVER

TRANSISTOR. Silm.  
B8X21 & C407, 2N1893  
FULLY TESTED AND  
CODED ND130, 1-24  
17p each. TO-5 N.P.N.  
25 up 15p each.

## Sil. trans. suitable for

P.E. Organ, Metal TO-18  
Eqvt. ZTX300 5p each.  
Any Qty.

## EX-EQUIPMENT

MULLARD  
AF117 transistors. Large  
can 4 leads type. Leads  
cut short but still usable,  
real value at 15 for 50p.

## KING OF THE PAKS Unequalled Value and Quality

## SUPER PAKS

## NEW BI-PAK UNTESTED SEMICONDUCTORS

Satisfaction GUARANTEED in Every Pak, or money back.

| Pak No. | Description                                                                                                       | Price |
|---------|-------------------------------------------------------------------------------------------------------------------|-------|
| U1      | 120 Glass sub-min. general purpose germanium diodes                                                               | 0-50  |
| U2      | 60 Mixed germanium transistors AF/RF                                                                              | 0-50  |
| U3      | 75 Germanium gold bonded diodes sim. OA5, OA47                                                                    | 0-50  |
| U4      | 40 Germanium transistors like OC81, AC128                                                                         | 0-50  |
| U5      | 60 200mA sub-min. Sil. diodes                                                                                     | 0-50  |
| U6      | 30 Silicon planar transistors NPN sim. BSY95A, 2N706                                                              | 0-50  |
| U7      | 16 Silicon rectifiers Top-Hat 750mA up to 1,000V                                                                  | 0-50  |
| U8      | 50 Sil. planar diodes 250mA, OA/200/202                                                                           | 0-50  |
| U9      | 20 Mixed volts 1 watt Zener diodes                                                                                | 0-50  |
| U11     | 30 PNP silicon planar transistors TO-5 sim. 2N1132                                                                | 0-50  |
| U13     | 30 PNP-NPN sil. transistors OC200 & 2S104                                                                         | 0-50  |
| U14     | 150 Mixed silicon and germanium diodes                                                                            | 0-50  |
| U15     | 25 NPN Silicon planar transistors TO-5 sim. 2N697                                                                 | 0-50  |
| U16     | 10 3-Amp silicon rectifiers stud type up to 1000 PIV                                                              | 0-50  |
| U17     | 30 Germanium PNP AF transistors TO-5 like ACY 17-22                                                               | 0-50  |
| U18     | 8 6-Amp silicon rectifiers BYZ13 type up to 600 PIV                                                               | 0-50  |
| U19     | 25 Silicon NPN transistors like BC108                                                                             | 0-50  |
| U20     | 12 1.5-Amp silicon rectifiers Top-Hat up to 1,000 PIV                                                             | 0-50  |
| U21     | 30 A.F. germanium alloy transistors 2G300 series & OC71                                                           | 0-50  |
| U23     | 30 Mat's like MAT series PNP transistors                                                                          | 0-50  |
| U24     | 20 Germanium 1-Amp rectifiers GJM up to 300 PIV                                                                   | 0-50  |
| U25     | 25 300Mc/s NPN silicon transistors 2N708, BSY27                                                                   | 0-50  |
| U26     | 30 Fast switching silicon diodes like IN914 micro-min                                                             | 0-50  |
| U28     | Experimenters' assortment of integrated circuits, untested. Gates, flip-flops, registers, etc., 8 assorted pieces | 1-00  |
| U29     | 10 1-Amp SCR's TO-5 can up to 600 PIV CR81/25-600                                                                 | 1-00  |
| U31     | 20 Sil. Planar NPN trans. low noise amp 2N3707                                                                    | 0-50  |
| U32     | 25 Zener diodes 400mW D07 case mixed volts, 3-18                                                                  | 0-50  |
| U33     | 15 Plastic case 1 amp silicon rectifiers IN4000 series                                                            | 0-50  |
| U34     | 30 Sil. PNP alloy trans. TO-5 BCY26, 2S302/4                                                                      | 0-50  |
| U35     | 25 Sil. planar trans. PNP TO-18 2N2906                                                                            | 0-50  |
| U36     | 25 Sil. planar NPN trans. TO-5 BFY50/51/52                                                                        | 0-50  |
| U37     | 30 Sil. alloy trans. 80-2 PNP, OC200 28322                                                                        | 0-50  |
| U38     | 20 Fast switching sil. trans. NPN, 400Mc/s 2N3011                                                                 | 0-50  |
| U39     | 30 RF germ. PNP trans. 2N1303/5 TO-5                                                                              | 0-50  |
| U40     | 10 Dual trans. 6 lead TO-5 2N2060                                                                                 | 0-50  |
| U41     | 25 RF germ. trans. TO-1 OC45 NKT72                                                                                | 0-50  |
| U42     | 10 VHF germ. PNP trans. TO-1 NKT567 AF117                                                                         | 0-50  |

Code Nos. mentioned above are given as a guide to the type of device in the Pak. The devices themselves are normally unmarked.

## GENERAL PURPOSE GERM. PNP POWER TRANSISTORS

Coded GP100. BRAND NEW TO-3 CASE. POSS. REPLACEMENTS FOR:—OC25-28-29-30-35-36. NKT 401-403-404-405-406-430-431-402-453. T13027-3028, 2N250A, 2N456A-457A-458A, 2N511 A & B. 2G220-222, ETC.  
SPECIFICATION  
VCBO 80V VCEO 50V IC 10A PT. 30 WATTS Hfe 30-170.  
PRICE 1-24 25-99 100 up  
43p each 40p each 36p each

## GENERAL PURPOSE SILICON NPN POWER TRANSISTORS

Coded GP200. BRAND NEW TO-3 CASE. POSS. REPLACEMENT FOR:—2N3055, BDY20, BDY11.  
SPECIFICATION  
VCBO 100V, VCEO 60V, IC 15AMPs, PT. 115 WATTS. Hfe 20-100. FTI MHZ  
PRICE 1-24 25-99 100 up  
55p each 50p each 47p each

## GENERAL PURPOSE NPN SILICON SWITCHING TRANS. TO-18 SIM. TO 2N706/8, BSY27/28/55A. All usable devices no open or short circuits. ALSO AVAILABLE IN PNP Sim. TO 2N2906, BCY70. When ordering please state preference NPN or PNP.

|  | 20 | For | 50   | For  | 75  | For   |
|--|----|-----|------|------|-----|-------|
|  | 50 | For | 1-00 | 1000 | For | 18-00 |

## SILICON PHOTO TRANSISTOR.

TO-18 Lens end. NPN Sim. to BP x25 and P21. BRAND NEW. Full data available. Fully guaranteed.  
Qty. 1-24 25-99 100 up  
Price each 45p 40p 35p

## RTL MICROLOGIC CIRCUITS

Price each  
Epoxy TO-5 case 1-24 25-99 100 up  
uL900 Buffer 35p 33p 27p  
uL914 Dual 2i/p gate 35p 33p 27p  
uL923 J-K flip-flop 35p 33p 27p  
Data and Circuits Booklet for I.C's 7p Price 7p.

## NEW QUALITY TESTED PAKS

| Pak | Description                                   | Price |
|-----|-----------------------------------------------|-------|
| Q1  | 20 Red spot trans. PNP AF                     | 0-50  |
| Q2  | 16 White spot R.F. trans. PNP                 | 0-50  |
| Q3  | 4 OC77 type trans.                            | 0-50  |
| Q4  | 6 Matched trans. OC44/45/81/81D               | 0-50  |
| Q5  | 4 OC72 transistors                            | 0-50  |
| Q6  | 4 OC72 transistors                            | 0-50  |
| Q7  | 4 AC128 trans. PNP high gain                  | 0-50  |
| Q8  | 4 AC128 trans. PNP                            | 0-50  |
| Q9  | 7 OC81 type trans.                            | 0-50  |
| Q10 | 7 OC71 type trans.                            | 0-50  |
| Q11 | 2 AC127/128 comp. pairs PNP/NPN               | 0-50  |
| Q12 | 3 AF116 type trans.                           | 0-50  |
| Q13 | 3 AF117 type trans.                           | 0-50  |
| Q14 | 3 OC171 H.F. type trans.                      | 0-50  |
| Q15 | 3 2N2926 sil. epoxy trans.                    | 0-50  |
| Q16 | 2 2N2980 low noise germ. trans.               | 0-50  |
| Q17 | 3 NPN 1 BT141 & 2 BT142                       | 0-50  |
| Q18 | 4 Mat's 2 MAT 100 & 2 MAT 120                 | 0-50  |
| Q19 | 3 Mat's 2 MAT 101 & 2 MAT 121                 | 0-50  |
| Q20 | 4 OC44 germ. trans. A.F.                      | 0-50  |
| Q21 | 3 AC127 NPN germ. trans.                      | 0-50  |
| Q22 | 20 NKT trans. A.F. R.F. coded                 | 0-50  |
| Q23 | 10 OA202 sil. diodes sub-min.                 | 0-50  |
| Q24 | 8 OA81 diodes                                 | 0-50  |
| Q25 | 6 IN914 sil. diodes 75P1V 75mA                | 0-50  |
| Q26 | 8 OA95 germ. diodes sub-min. IN69             | 0-50  |
| Q27 | 2 10A 600P1V sil. recta. 1845R                | 0-50  |
| Q28 | 2 Sil. power recta. BYZ13                     | 0-50  |
| Q29 | 4 Sil. trans. 2 x 2N696, 1 x 2N697, 1 x 2N698 | 0-50  |
| Q30 | 7 Sil. switch trans. 2N706 NPN                | 0-50  |
| Q31 | 6 Sil. switch trans. 2N708 NPN                | 0-50  |
| Q32 | 3 PNP sil. trans. 2 x 2N1131, 1 x 2N1132      | 0-50  |
| Q33 | 3 Sil. NPN trans. 2N1711                      | 0-50  |
| Q34 | 7 Sil. NPN trans. 2N2389, 500MHZ.             | 0-50  |
| Q35 | 3 Sil. PNP TO-5 2 x 2N2904 & 1 x 2N905        | 0-50  |
| Q36 | 7 2N3646 TO-18 plastic 300MHZ                 | 0-50  |
| Q37 | 3 2N3039 NPN sil. 2N3703                      | 0-50  |
| Q38 | 7 PNP trans. 4 x 2N3703, 3 x 2N3702           | 0-50  |
| Q39 | 7 NPN trans. 4 x 2N3704, 3 x 2N3705           | 0-50  |
| Q40 | 7 NPN amp. 4 x 2N3707, 3 x 2N3708             | 0-50  |
| Q41 | 3 Plastic NPN TO-18 2N3904                    | 0-50  |
| Q42 | 6 NPN trans. 2N5172                           | 0-50  |
| Q43 | 7 BC107 NPN trans. 4 x BC108, 3 x BC109       | 0-50  |
| Q44 | 7 NPN trans. 4 x BC108, 3 x BC109             | 0-50  |
| Q45 | 3 BC113 NPN TO-18 trans.                      | 0-50  |
| Q46 | 3 BC115 NPN TO-8 trans.                       | 0-50  |
| Q47 | 6 NPN high gain 3 x BC167, 3 x BC168          | 0-50  |
| Q48 | 4 BCY70 NPN trans. TO-18                      | 0-50  |
| Q49 | 4 NPN trans. 2 x BFY51, 2 x BFY52             | 0-50  |
| Q50 | 7 BSY28 NPN switch TO-18                      | 0-50  |
| Q51 | 7 BSY95A NPN trans. 300MHZ                    | 0-50  |
| Q52 | 8 BY100 type sil. rect.                       | 1-00  |
| Q53 | 25 Sil. & germ. trans. mixed all marked new   | 1-50  |

## PRINTED CIRCUITS—EX-COMPUTER

Packed with semiconductors and components, 10 boards give a guaranteed 30 trans and 30 diodes. Our price 10 boards, 50p. Plus 10p P. & P. 100 Boards 25p, P. & 30p.

## JUMBO COMPONENT PAKS

## MIXED ELECTRONIC COMPONENTS

Exceptionally good value (no rubbish)

Resistors, capacitors, pots, electrolytics and coils plus many other useful items. Approximately 31bs in weight. Price incl. P. & P

£1.50 only

Plus our satisfaction or money back guarantee.

## NEW EDITION 1971

## TRANSISTOR EQUIVALENTS BOOK.

A complete cross reference and equivalents book for European, American and Japanese Transistors. Exclusive to BI-PAK 90p each.

## GERM. POWER TRANS.

| Type | Price each | Type  | Price each |
|------|------------|-------|------------|
| OC20 | 50p        | OC29  | 40p        |
| OC22 | 30p        | OC35  | 33p        |
| OC23 | 33p        | OC36  | 40p        |
| OC25 | 25p        | AD140 | 40p        |
| OC26 | 25p        | AD142 | 40p        |
| OC28 | 40p        | AD149 | 40p        |

## OUR STOCKS of individual devices

are now too numerous to mention in this Advertisement. Send S.A.E. for our listing of over 1,000 Semiconductors. All available Ex-Stock at very competitive prices.

## Dual-In-Line Low Profile Sockets

14 and 16 Lead Sockets for use with Dual-In-Line Integrated Circuits

| Order No.       | 1-24 | 25-99 | 100 up |
|-----------------|------|-------|--------|
| T80 14 pin type | 30p  | 27p   | 25p    |
| T80 16 pin type | 35p  | 32p   | 30p    |

# -the lowest prices!

## 74 series T.T.L. I.C's

### DOWN AGAIN IN PRICE

Check our 74 Series List before you buy any I.C's. Our prices are the lowest possible. All devices ex-stock. Full spec. guaranteed.

| BI-PAK Order No. | Similar Types to:—Description                             | Price and qty. prices |       |        |
|------------------|-----------------------------------------------------------|-----------------------|-------|--------|
|                  |                                                           | 1-24                  | 25-99 | 100 up |
| BP00 = 7400      | Quad 2-input NAND gate                                    | 0-15                  | 0-14  | 0-12   |
| BP01 = 7401      | Quad 2-input pos. NAND gate (with open collector output)  | 0-15                  | 0-14  | 0-12   |
| BP02 = 7402      | Quad 2-input pos. NOR gates                               | 0-15                  | 0-14  | 0-12   |
| BP03 = 7403      | Quad 2-input pos. NAND gates (with open collector output) | 0-15                  | 0-14  | 0-12   |
| BP04 = 7404      | Hex Inverters                                             | 0-15                  | 0-14  | 0-12   |
| BP05 = 7405      | Hex Inverter (with open collector output)                 | 0-15                  | 0-14  | 0-12   |
| BP10 = 7410      | Triple 3-input pos. NAND gates                            | 0-15                  | 0-14  | 0-12   |
| BP13 = 7413      | Dual 4-input Schmitt trigger                              | 0-29                  | 0-28  | 0-24   |
| BP20 = 7420      | Dual 4-input pos. NAND gates                              | 0-15                  | 0-14  | 0-12   |
| BP30 = 7430      | 8-input pos. NAND gates                                   | 0-15                  | 0-14  | 0-12   |
| BP40 = 7440      | Dual 4-input pos. NAND buffers                            | 0-15                  | 0-14  | 0-12   |
| BP41 = 7441      | BCD to decimal nixie driver                               | 0-87                  | 0-84  | 0-58   |
| BP42 = 7442      | BCD to decimal decoder (4-10 lines, 1 of 10)              | 0-87                  | 0-84  | 0-58   |
| BP46 = 7446      | BCD-to-seven-segment decoder/driver                       | 2-00                  | 1-75  | 1-50   |
| BP47 = 7447      | BCD-to-seven-segment decoder/driver (15V outputs)         | 0-97                  | 0-94  | 0-88   |
| BP48 = 7448      | BCD-to-seven-segment decoder/driver                       | 0-97                  | 0-94  | 0-88   |
| BP50 = 7450      | Expandable dual 2-input and-or-invert                     | 0-15                  | 0-14  | 0-12   |
| BP51 = 7451      | Dual 2-wide 2-input and-or-invert gates                   | 0-15                  | 0-14  | 0-12   |
| BP53 = 7453      | Quad 2-input expandable and-or-invert                     | 0-15                  | 0-14  | 0-12   |
| BP54 = 7454      | 4-wide 2-input and-or-invert gates                        | 0-15                  | 0-14  | 0-12   |
| BP60 = 7460      | Dual 4-input expander                                     | 0-15                  | 0-14  | 0-12   |
| BP70 = 7470      | Single-phase J-K flip-flop                                | 0-29                  | 0-28  | 0-24   |
| BP72 = 7472      | Master slave J-K flip-flop                                | 0-29                  | 0-28  | 0-24   |
| BP73 = 7473      | Dual Master slave J-K flip-flop                           | 0-37                  | 0-35  | 0-32   |
| BP74 = 7474      | Dual D type flip-flop                                     | 0-37                  | 0-35  | 0-32   |
| BP76 = 7476      | Quad latch                                                | 0-47                  | 0-45  | 0-42   |
| BP78 = 7478      | Dual J-K with pre-set and clear                           | 0-43                  | 0-40  | 0-38   |
| BP80 = 7480      | Gated full adders                                         | 0-67                  | 0-64  | 0-58   |
| BP81 = 7481      | 16-bit read/write memory                                  | 0-67                  | 0-64  | 0-58   |
| BP82 = 7482      | 2-bit binary full adders                                  | 0-97                  | 0-94  | 0-88   |
| BP83 = 7483      | Quad full adder                                           | 1-10                  | 1-05  | 0-95   |
| BP86 = 7486      | BCD 2-input exclusive NOR gates                           | 0-32                  | 0-30  | 0-28   |
| BP90 = 7490      | BCD decade counter                                        | 0-67                  | 0-64  | 0-58   |
| BP91 = 7491      | 8-bit shift registers                                     | 0-67                  | 0-64  | 0-58   |
| BP92 = 7492      | Divide-by-twelve counters                                 | 0-67                  | 0-64  | 0-58   |
| BP93 = 7493      | 4-bit binary counters                                     | 0-67                  | 0-64  | 0-58   |
| BP94 = 7494      | Dual entry 4-bit shift register                           | 0-77                  | 0-74  | 0-68   |
| BP95 = 7495      | 4-bit up-down shift register                              | 0-77                  | 0-74  | 0-68   |
| BP96 = 7496      | 5-bit parallel in parallel out shift register             | 0-77                  | 0-74  | 0-68   |
| BP100 = 74100    | 8-bit bistable latches                                    | 0-77                  | 0-74  | 0-68   |
| BP104 = 74104    | Single J-K flip-flop equivalent 9000 series               | 1-75                  | 1-65  | 1-55   |
| BP105 = 74105    | Single J-K flip-flop equivalent 9001 series               | 0-97                  | 0-94  | 0-88   |
| BP107 = 74107    | Dual Master-slave flip-flops                              | 0-40                  | 0-38  | 0-36   |
| BP110 = 74110    | Gates master-slave flip-flops                             | 0-55                  | 0-53  | 0-50   |
| BP111 = 74111    | Dual data lock-out flip-flop                              | 1-25                  | 1-15  | 1-00   |
| BP118 = 74118    | Hex set-reset latches                                     | 1-00                  | 0-95  | 0-90   |
| BP119 = 74119    | Hex set-reset latches, 24-pin                             | 1-35                  | 1-25  | 1-10   |
| BP121 = 74121    | Monostable multivibrators                                 | 0-67                  | 0-64  | 0-58   |
| BP141 = 74141    | BCD-to-decimal decoder/driver                             | 0-67                  | 0-64  | 0-58   |
| BP145 = 74145    | BCD-to-decimal decoder/driver O/C                         | 1-50                  | 1-40  | 1-30   |
| BP150 = 74150    | 16-bit data selector                                      | 1-80                  | 1-70  | 1-60   |
| BP151 = 74151    | 8-bit data selectors (with strobe)                        | 1-00                  | 0-95  | 0-90   |
| BP153 = 74153    | Dual 4-line-to-1-line data                                | 1-20                  | 1-10  | 0-95   |
| BP154 = 74154    | 4- to 16-line decoder                                     | 1-80                  | 1-70  | 1-60   |
| BP155 = 74155    | Dual 2- to 4-line decoder                                 | 1-40                  | 1-30  | 1-20   |
| BP156 = 74156    | Dual 2- to 4-line decoder O/C                             | 1-40                  | 1-30  | 1-20   |
| BP160 = 74160    | Sync. decade counter                                      | 1-80                  | 1-70  | 1-60   |
| BP161 = 74161    | Sync. 4-bit binary counter                                | 1-80                  | 1-70  | 1-60   |
| BP190 = 74190    | Sync. up-down BCD counter                                 | 3-50                  | 3-25  | 3-00   |
| BP191 = 74191    | Sync. binary up-down counter (single clock line)          | 3-50                  | 3-25  | 3-00   |
| BP192 = 74192    | Sync. up-down decade counter                              | 2-10                  | 1-95  | 1-75   |
| BP193 = 74193    | Sync. binary up-down counter (two clock lines)            | 2-10                  | 1-95  | 1-75   |
| BP196 = 74196    | Pre-settable 50MHz decade counter                         | 1-80                  | 1-70  | 1-60   |
| BP197 = 74197    | Pre-settable 50MHz binary counter                         | 1-80                  | 1-70  | 1-60   |
| BP198 = 74198    | 8-bit parallel L-R shift register                         | 5-50                  | 5-00  | 4-00   |
| BP199 = 74199    | 8-bit parallel access shift register                      | 5-50                  | 5-00  | 4-00   |

Devices may be mixed to qualify for quantity price. Larger quantities—prices on application (TTL 74 Series only). Data is available for the above series of I.C's in booklet form. Price 13p.

### TTL INTEGRATED CIRCUITS


Manufacturers' "Fall outs"—out of spec. devices including functional units and part function but classed as out of spec. from the manufacturers' very rigid specifications. Ideal for learning about I.C's and experimental work.

| PAK No.            | PAK No.            | PAK No.           |
|--------------------|--------------------|-------------------|
| UIC00 = 12 x 7400N | UIC45 = 5 x 7450N  | UIC80 = 5 x 7480N |
| UIC01 = 12 x 7401N | UIC50 = 12 x 7450N | UIC82 = 5 x 7482N |
| UIC02 = 12 x 7402N | UIC51 = 12 x 7451N | UIC83 = 5 x 7483N |
| UIC03 = 12 x 7403N | UIC60 = 12 x 7460N | UIC86 = 5 x 7486N |
| UIC04 = 12 x 7404N | UIC70 = 8 x 7470N  | UIC90 = 5 x 7490N |
| UIC05 = 12 x 7405N | UIC72 = 8 x 7472N  | UIC92 = 5 x 7492N |
| UIC10 = 12 x 7410N | UIC73 = 8 x 7473N  | UIC93 = 5 x 7493N |
| UIC20 = 12 x 7420N | UIC74 = 8 x 7474N  | UIC94 = 5 x 7494N |
| UIC40 = 12 x 7440N | UIC75 = 8 x 7475N  | UIC95 = 5 x 7495N |
| UIC41 = 5 x 7441AN | UIC76 = 8 x 7476N  | UIC96 = 5 x 7496N |

Pak cannot be split but 20 assorted pieces (our mix) is available as PAK UICX1 Every Pak carries out BP-PAK Satisfaction or money back GUARANTEE.

## ANOTHER BI-PAK FIRST!
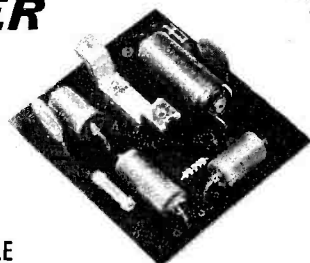
### THE NEW S.G.S. EA 1000 AUDIO AMPLIFIER MODULE



### \*GUARANTEED NOT LESS THAN 3 WATTS RMS

Especially designed by S.G.S. incorporating their proven Linear I.C. Audio Amp. TA/621 providing unlimited applications for the enthusiast in the construction of radios, record players, Audio and Stereo units. Also ideal for intercom systems, monitoring applications and phone answering machines. OTHER USES: portable applications where supply rails as low as 9V are of prime importance.

- Sensitivity 40 mV for 1 watt VOLTAGE GAIN 40dB but can be varied up to 73dB for some applications.
- Signal to Noise Ratio 86dB.
- Frequency response better than 50 Hz to 25 KHz for -3dB.
- Normal supply Voltage 9-24V.
- Suitable for 8-16 OHM Loads.
- Overall Size 2" x 3" x 1".
- Typical Total Harmonic distortion at 1 watt less than 1%.

\*Supply voltage (Vs) = 24V 15ohm load.

Module Tested and Guaranteed

Quantity 1-9 10-25

Price each £2.63 £2.28

Larger quantities quoted on request

Full hook-up diagrams and complete technical data supplied free with each module or available separately at 10p each.

### ROCK BOTTOM PRICES—CAN'T BE BEATEN!

| LOGIC    |                                                     | DTL 930 SERIES |       | IC's   |       |
|----------|-----------------------------------------------------|----------------|-------|--------|-------|
| Type No. | Function                                            | 1-24           | 25-99 | 100 up | Price |
| BP930    | Expandable dual 4-input NAND                        | 12p            | 11p   | 10p    |       |
| BP932    | Expandable dual 4-input NAND buffer                 | 13p            | 12p   | 11p    |       |
| BP933    | Dual 4-input expander                               | 13p            | 12p   | 11p    |       |
| BP935    | Expandable Hex Inverter                             | 13p            | 12p   | 11p    |       |
| BP936    | Hex Inverter                                        | 13p            | 12p   | 11p    |       |
| BP944    | Dual 4-input NAND expandable buffer without pull-up | 13p            | 12p   | 11p    |       |
| BP945    | Master-slave JK or RS                               | 25p            | 24p   | 22p    |       |
| BP946    | Quad, 2-input NAND                                  | 12p            | 11p   | 10p    |       |
| BP948    | Master-slave JK or RS                               | 25p            | 24p   | 22p    |       |
| BP951    | Monostable                                          | 65p            | 60p   | 55p    |       |
| BP962    | Triple 3-input NAND                                 | 12p            | 11p   | 10p    |       |
| BP9093   | Dual Master-slave JK with separate clock            | 40p            | 38p   | 35p    |       |
| BP9094   | Dual Master-slave JK with separate clock            | 40p            | 38p   | 35p    |       |
| BP9097   | Dual Master-slave JK with Common Clock              | 40p            | 38p   | 35p    |       |
| BP9099   | Dual Master-slave JK Common Clock                   | 40p            | 38p   | 35p    |       |

Devices may be mixed to qualify for quantity price. Larger quantity prices on application. (DTL 930 Series only).

### BRAND NEW LINEAR I.C's—FULL SPEC.

| Type No.       | Case   | Leads | Description                  | 1-24 | 25-99 | 100 up |
|----------------|--------|-------|------------------------------|------|-------|--------|
| BP 201C—SL201C | TO-5   | 8     | G.P. Amp                     | 63p  | 53p   | 45p    |
| BP 701C—SL701C | TO-5   | 8     | OP Amp                       | 83p  | 50p   | 45p    |
| BP 702C—SL702C | TO-5   | 8     | OP Amp Direct OP             | 83p  | 50p   | 45p    |
| BP 702—72702   | D.L.L. | 14    | G.P. OP Amp (Wide Band)      | 53p  | 45p   | 40p    |
| BP 709—72709   | D.L.L. | 14    | High OP Amp                  | 53p  | 45p   | 40p    |
| BP 709P—7A709C | TO-5   | 8     | High Gain OP Amp             | 53p  | 45p   | 40p    |
| BP 711—7A711   | TO-5   | 10    | Dual comparator              | 58p  | 50p   | 45p    |
| BP 741—72741   | D.L.L. | 14    | High Gain OP Amp (Protected) | 75p  | 60p   | 50p    |
| 7A703C—7A703C  | TO-5   | 6     | R.F. I.F. Amp                | 45p  | 35p   | 27p    |
| TAA 263—       | TO-72  | 4     | A.F. Amp                     | 70p  | 60p   | 55p    |
| TAA 293—       | TO-74  | 10    | G.P. Amp                     | 90p  | 75p   | 70p    |

All prices quoted in new pence Giro No. 388-7006

Please send all orders direct to warehouse and despatch department

# BI-PAK


P.O. BOX 6, WARE, HERTS

Postage and packing add 7p. Overseas add extra for airmail.

Minimum order 50p. Cash with order please.

Guaranteed Satisfaction or Money Back



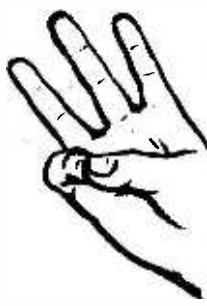

# 3 WAYS

HOME RADIO (Components) LTD.  
Dept. PW, 234-240 London Rd.,  
Mitcham, CR4 3HD. 01-648 8422

## of obtaining components *quickly & easily*

# 1

**CALL AT No. 240  
London Rd., Mitcham**

If you live within easy reach of Mitcham or are in the area at any time do call on us. We are almost opposite Mitcham Baths. We open 9 a.m. every weekday. On Wednesdays we close 1 p.m. and all other days, including Saturdays, 5.30 p.m. On Saturdays we have extra staff to deal with queries. We carry a vast stock of components, and 999 times out of a 1,000 we can immediately lay our hands on the particular item required.

# 2

**JOIN OUR CREDIT  
ACCOUNT SERVICE**

We began our Credit Account Service about 18 months ago and it has proved extremely popular. Little wonder! Our customers find it a very simple and convenient way of purchasing all their radio and electronic needs. We supply pre-paid envelopes and order forms and no matter how many orders you send us you make only one payment per month. There are several other advantages with our Credit Account Service. Please write or phone for details.

The price of 70p applies only to catalogues purchased by customers in the U.K. and to BFPO addresses.

# 3

**and  
ORDER BY MAIL  
OR TELEPHONE**

Although we are kept busy selling "over the counter" we supply even more by Mail Order. You can telephone any time of day or night, Sundays included. If you ring out of office hours a recording machine takes your message for us to deal with as soon as we open shop again. Our number is 01-648 8422. If you wish to order by post our address is in the panel at the top of the page. We deal with all orders promptly.



**WHICHEVER WAY YOU  
CHOOSE** you need the  
Home Radio Catalogue

In its 315 pages are listed over 8,000 components, over 1,500 of them illustrated. Each copy contains 10 Vouchers, each worth 5p when used as instructed. Free Supplements are supplied regularly to keep you up-to-date. The Catalogue costs 50p over the counter, or 70p including postage and packing.

*Post this Coupon with  
Cheque or PO for 70p*

*Please write Name and Address in block capitals.*

Name .....

Address .....

.....

**HOME RADIO (Components) LTD.  
Dept. PW, 234-240 London Rd., Mitcham, CR4 3HD**

# PRACTICAL WIRELESS

VOL 47 NO 6

Issue 776

OCTOBER 1971

## Who makes what?

**W**ELL, of course, that's easy! When you buy a radio set, hi-fi amplifier or piece of electrical equipment, the trade mark tells you that. Or if the mark is an unfamiliar one you can find the piece moulded on the cabinet or printed on the carton which says 'Made in Outer Mongolia' or whatever.

People are interested in where products are made for a variety of reasons. The possible standard of workmanship, value-for-money, reputation, reliability, the position of after-sales service, availability of spare parts—or even personal political motives—are all valid reasons why a purchaser would want to know who makes what, and where.

From November 30th, however, the Merchandise Marks Act comes to an end and from that date it will no longer be obligatory for imported goods to bear a 'country-of-origin' mark. The casual customer will therefore not be sure if he is buying a radio set made in Birmingham or Baluchistan, or an amplifier which is a Chinese-copy of an American design made in Hong Kong or Japan.

Of course, there will still be trade marks which proclaim that the goods are true-blue British or come from well-respected foreign companies. Sadly, though, things are not always what they seem for many tape recorders, radio and TV receivers, bearing the names of old-established British manufacturers have for some time been made overseas and imported for the home market.

From November 30th, protection of the consumer has been thrown at the retailer who, when asked, will be expected to disclose where a particular product is made. Unfortunately in many cases he will have no way of giving the required information. For instance, 'household-name' UK companies are none too keen to admit that some of their goods are being made in low-cost labour countries. Moreover, if a retailer does not know the country of origin, or (even inadvertently) gives the wrong answer, he will be at risk under the Trade Descriptions Act!

Apart from the factors mentioned earlier, which allow a customer to assess the advisability or otherwise of making a purchase, a particularly disturbing aspect of electrical goods (notably electric blankets and appliances) is that safety specifications may fall far short of those imposed on British-made goods and expose the user to potential hazards.

So, together with the British Radio Equipment Manufacturers' Association, the Radio and Television Retailers' Association and the Association of Manufacturers of Domestic Appliances, we beg the Secretary for Trade and Industry to think again. And to would-be purchasers after November 30th we can only say, most emphatically *caveat emptor!*

W. N. STEVENS—Editor.

## NEWS AND COMMENT

|                                      |     |
|--------------------------------------|-----|
| Leader                               | 471 |
| News . . . News . . . News . . .     | 472 |
| MW Column by <i>Charles Molloy</i>   | 478 |
| Practically Wireless by <i>Henry</i> | 518 |
| On the Short Waves                   |     |
| by <i>Malcolm Connah</i> and         |     |
| <i>David Gibson</i> , G3JDG          | 521 |
| Electronotes by <i>S. Ginsberg</i>   | 534 |

## CONSTRUCTIONAL

|                                           |     |
|-------------------------------------------|-----|
| Modular Audio Mixing System               |     |
| by <i>F. C. Judd</i>                      | 474 |
| Digital Frequency Counter/Timer,          |     |
| Part 2 by <i>John Thornton Lawrence</i> , |     |
| GW3JGA                                    | 480 |
| General Purpose Power Supply              |     |
| by <i>M. Wallis</i>                       | 492 |
| Wavemeter Monitor by <i>R. F. Graham</i>  | 529 |
| Take 20, No. 30, Automatic Light,         |     |
| by <i>Julian Anderson</i>                 | 533 |

## OTHER FEATURES

|                                        |     |
|----------------------------------------|-----|
| Testing Surplus Transistors            |     |
| by <i>R. A. Butterworth</i>            | 489 |
| Transistor Circuitry for Beginners,    |     |
| Part 1, by <i>H. W. Hellyer</i>        | 507 |
| I.C. of the Month,                     |     |
| LM373 Multiple-mode Detector           |     |
| by <i>L. A. J. Ireland</i>             | 510 |
| SERVICING—Part 6, by <i>G. J. King</i> | 513 |
| Going Back by <i>Colin Riches</i> and  |     |
| <i>Arthur Dow</i>                      | 525 |

## SPECIAL FEATURES

|                               |     |
|-------------------------------|-----|
| Choosing Small Workshop Tools |     |
| by <i>S. Yeatman</i>          | 497 |
| FREE WALL CHART:              |     |
| Circuit Building Blocks       |     |

**NOVEMBER ISSUE WILL BE  
PUBLISHED ON OCTOBER 8th**

©IPC Magazines Limited 1971. Copyright in all drawings, photographs and articles published in "Practical Wireless" is fully protected, and reproduction or imitations in whole or in part are expressly forbidden. All reasonable precautions are taken by "Practical Wireless" to ensure that the advice and data given to readers are reliable. We cannot, however, guarantee it, and we cannot accept legal responsibility for it. Prices are those current as we go to press. All correspondence intended for the Editor should be addressed to Fleetway House, Farringdon Street, London, EC4A 4AD. Queries must be accompanied by a stamped, addressed envelope. Address correspondence regarding advertisements to Advertisement Manager, Fleetway House, Farringdon Street, London, EC4A 4AD.

# NEWS... NEWS... NEWS...

## Viscount value



The Viscount III Audio System is the first of a range of audio equipment marketed in the UK by R+TV Components (Acton) Ltd. under the Viscount brand name.

The complete system includes a choice of two amplifiers, a Garrard SP25 Mk III turntable and two Duo type II or type III speakers.

Amplifier RT100 is for ceramic cartridges and model RT101 which has an additional input stage accepts magnetic types. Both amplifiers incorporate f.e.t.'s giving excellent signal to noise ratios.

Prices are: RT100, £17; RT101, £22; Garrard SP25 with ceramic cartridge, £21 or with magnetic cartridge, £23. Duo type II speakers cost £14 the pair and Duo type III, £32.

Savings can be made by buying complete systems.

## Impex cases

In last month's issue we stated the following about Impex instrument cases:

"At no additional cost, Impex cases can be supplied with all or some of these specifications: alternative colours of blue or bronze; no hood; no ventilating slots or back/front anodised front/rear panels".

What we should have mentioned is that these additions can only be supplied free of charge for quantities over 24.

## NHK's anniversary

June 1 saw the anniversary of the Radio Japan Service. Thirty-six years ago NHK commenced this service in commemoration of the 10th anniversary of radio broadcasting in Japan and the attainment of 2 million licensed subscribers.

From June 1934 to 1945, NHK broadcast its domestic programmes to Korea, Taiwan and Manchuria, then Japan's outlying territories, utilising telephone channels of the International Telephone Company. Shortwave broadcasts were received in various parts other than the areas directed, and reception reports

began to come to NHK from Japanese residing abroad and from large numbers of overseas people. In those days, Japanese living in various parts of the world totalled nearly two million. These people raised their voices requesting the establishment of an overseas broadcasting service. In Japan, too, commencement of an overseas broadcasting service was also strongly desired, since this country had been isolated after her withdrawal from the League of Nations and was in need of reinforcing its public relations abroad. At first the service was known as Radio Tokyo (Radio Japan was first used in 1952).

## Avo wall chart


Avo Limited (Thorn Group) announce a new wall chart featuring the latest Mark 4 version of the Avometer Model 8. The design and layout is such that it will prove of great interest not only to Avometer users but also to technical schools and general education establishments as a teaching aid.

Information is presented in a clear, logical manner and the theoretical and practical information is both concise and easy to understand. Magnetic theory is developed pictorially to outline the operation of the moving coil movement whilst a mathematical treatment is used to derive the various ranges of a multimeter.

Illustrations of the interior of the instrument include an exploded view of the movement to simplify the constructional detail and a circuit diagram provides an introduction to standard symbols and references.

The Avometer chart (size 20×30in., 508×762mm.) is ideal for black-board or wall presentation and is available from *Spares Dept., Avo Limited, Avocet House, Dover*, at 75p per copy, including post and packing.

## AVOMETERS

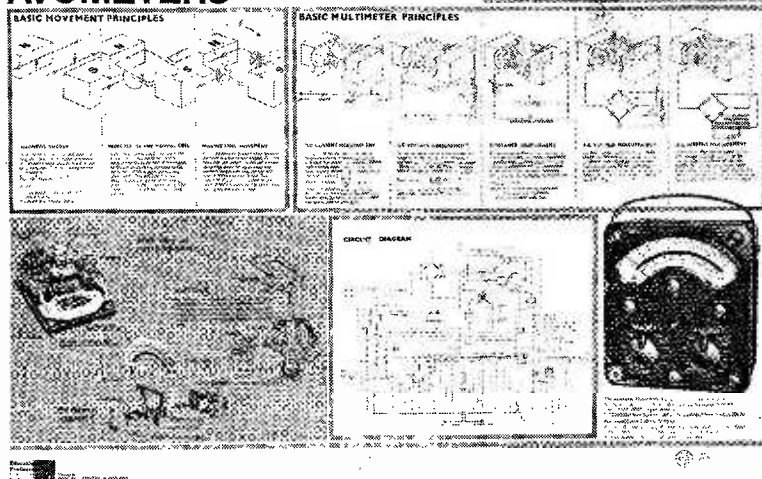

### Windermere VHF

The v.h.f. radio services from the Windermere relay station started on August 7. Radio 2 is on 88.6MHz, Radio 3 on 90.8MHz and Radio 4 on 93.0MHz, all with horizontal polarization.

The v.h.f. radio transmissions from this new relay station, which is situated on Claife Heights, above the western shore of Lake Windermere, will serve Ambleside, Windermere town, Bowness-on-Windermere, and an area around the northern shores of the lake.

### Stereo from Rowbridge

The necessary equipment has now been installed at Rowridge to enable the Radio 3 transmitter (90.7MHz) to broadcast stereophony. This is being brought into use immediately, so that listeners can hear the Promenade Concerts in stereo—all except four of the concerts will be broadcast stereophonically in Radio 3. The stereo transmissions from Rowridge will initially be on an engineering test basis; every effort will be made to maintain them, but there may be occasions when it will be necessary to revert to monophonic transmissions. The date for the start of the full stereophonic service will be announced later.

### Miniature Electric Tools

A range of battery-operated miniature tools has been introduced by Expo (Drills) Ltd., 62 Neal Street, London, W.C.2.

Two basic models are available. The 'Reliant' is designed for lighter work such as model making, and has a full load current of 1.5A. Its rated torque is 1.38oz. in. (100 gm.cm.). For jobs requiring a more powerful tool and for professional applications the 'Titan Super' is rated at 3.5A on full load. It has a rated torque of 350cmp operating at 4000-9000rpm. An extremely large range of accessories is also available for both models. Various collets and accessories are supplied with the different models, which range in price from £3 to £5.50.

### Lectures


THE Polytechnic of North London Department of Electronic and Communications Engineering is running a course on Audio and Acoustic Measurements on Thursdays 6.30-8.30 p.m. 1971/2. 1971: Oct., 28, Parameters and Standards of Measurement R. N. Baldock, B.Sc., F.B.K.S.T.S. Nov. 4, Measurement of Microphone Performance, H. D. Harwood, B.Sc., B.B.C. Research; 11, Electrical and Mechanical Measurements in Tape Recording, R. L. West, B.Sc., C.Eng., F.I.E.R.E.; 18, Measurements in Professional Recording, Angus McKensie; 25, Electrical and Mechanical Measurements on Disc, Pickups and Accelerometers, S. Kelly, C.Eng., F.I.E.R.E. Dec. 2, Measurement of Loudspeaker Performance I, R. L. West; 9, Measurement of Loudspeaker Performance II, R. C. Driscoll, M.Sc.; 16, Measurement of Studio Characteristics, R. C. Driscoll, M.Sc. 1972: Jan. 13, Measurement of Noise Transmission, J. Moir C.Eng., F.I.E.E.; 20, Assessment of Noise Nuisance, J. Moir, C.Eng., F.I.E.E.; 27, Visit to A.I.R.O. Laboratories, Hemel Hempstead, G. Berry, B.Sc., C.Eng., M.I.Mech.E. and Assocs.

### Grand Junk Sale

The Star Short Wave Club, G3ZWA, is holding a "Grand Junk Sale" in aid of Radio Amateur Invalid Bedfast Club funds. It is to be held at the New Inn Hotel, Bramley Town Street, Bramley, Leeds 13. The date is Wednesday September 15th and time 7.30.

If any readers have any junk, the Star Club will collect within a radius of 25 miles from Leeds. Please contact Mr. T. Leeman, G8BUU, 115 Asket Drive, Seaforth, Leeds, LS14 1HX.

### Chip "C's"

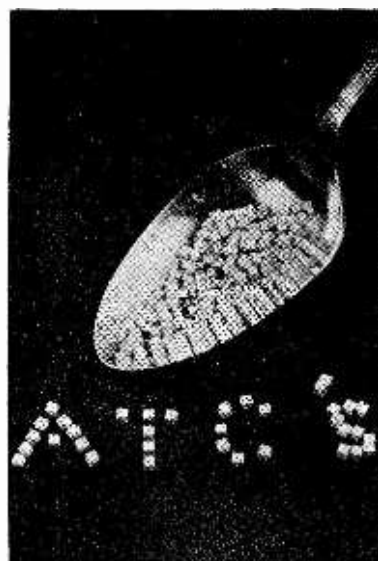


Featuring a very low insertion loss, a very high Q and high capacitance-to-volume ratios, a new range of ceramic and porcelain chip capacitors from Guest International Limited is ideal for u.h.f. and microwave applications. Apart from the basic pellet and chip, there is a wide choice of lead variations: stripline, axial and radial wire, axial and radial ribbon.

ATC 100 series are porcelain chips with an insertion loss of 0.03dB, a Q of over 10,000 and a capacitance range of 0.1 to 1000pF. In a case size of only 0.110in.square, the working voltage is up to 500V d.c.

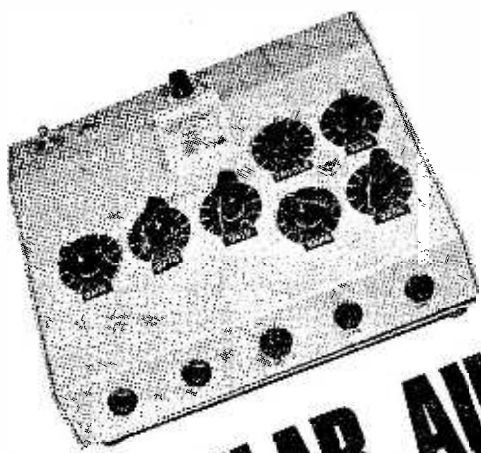ATC 200 series are ceramic chips with an insertion loss of 0.05dB. The capacitance range is 10pF to 1.2μF and chips are available in case sizes 0.050, 0.110 and 0.250in.square, depending on the value and the working voltage.







# MODULAR AUDIO MIXING SYSTEM

F.C. JUDD



So many audio sources are now in common use that an article describing a specific design would meet the needs of only a few. This problem is overcome here by giving circuits for virtually all sources and care in design has made possible a large number of permutations so that a custom built audio mixer is possible even for those readers unable to design their own. The clever constructional method employed also allows for rapid modification to meet any mixing need.

**A** STUDY of the four block diagrams in Fig. 1 will show how the various signal preamplifiers, the tone control unit and line amplifier etc. can be used to build audio signal mixing systems to cater for tape recording, public address, discotheque and even Hi-Fi applications. The combinations given are but a few of the permutations which can be extended for stereo use simply by duplication.

Each signal preamp has the same output level, 100mV, and will match directly into either the tone control unit or the line amplifier, both of which are designed to accept a signal level of 100mV. The tone control has unity gain so this provides 100mV output to match into the line amplifier. Any group of signal preamplifiers can therefore be coupled directly to the line amplifier or via the tone control unit and then to the line amplifier. This allows any of the signal preamplifiers to be used with or without the tone control unit.

The line amplifier has a nominal output of 1V r.m.s. at a fairly low impedance and can be used to drive a power amplifier module requiring between 500mV. to 1V input, or it can be coupled to a tape recorder or radio input, or to a public address or music amplifier with inputs rated for 500mV to 1V. Groups of the preamplifiers and line amplifier can be run from batteries or from an 18V mains power supply.

## COMBINATIONS


A fairly simple arrangement is shown in Fig. 1a and is intended for use as a general purpose signal mixer as shown on the front cover. This would be suitable for tape recording, as it has two microphone inputs, one input for low impedance pick-up (with R.I.A.A. correction), and two line level (200mV to over 1V) inputs. The tone control operates for the mic. and pickup inputs, whilst the line inputs go directly to the line amplifier. The system also includes a VU meter with variable control so that the meter can be set to read with the level meter on a tape recorder.

The combination shown in Fig. 1b has the same input channels but no tone control unit. The arrangement in Fig. 1c might be suitable for a small discotheque with one mic. input, two pickup inputs both via a tone control unit and one line input, suitable for the output from a tape recorder. For music application, Fig. 1d provides two mic. and two guitar inputs with separate tone control units for each guitar input. In each case the VU meter is optional but can be used as an overload indicator as will be shown later.


## PERFORMANCE SPECIFICATIONS

Seven preamplifiers will be described, each catering for specific signal sources as follows:—

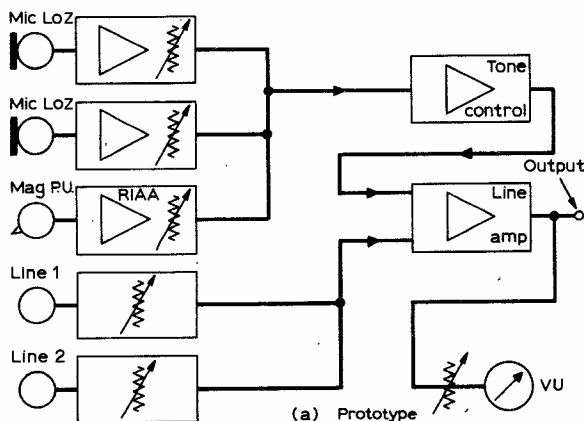
1. **LOW IMPEDANCE MICS.** (25 to 600Ω). Direct input, no transformer required. Input sensitivity 50μV. Output 100mV. Frequency response ±1dB. 30 to 30,000Hz. Signal-to-noise -50dB. (Code: Mic. Lo-Z).
2. **FOR MICROPHONES WITH BUILT-IN TRANSFORMERS.** Medium to high impedance. Input sensitivity 1mV. Output 100mV. Frequency response ±1dB 20 to 30,000Hz. Signal-to-noise -60dB. (Code: Mic. Hi-ZT).
3. **FOR CRYSTAL MICS.** High impedance. Input sensitivity 2mV. Output 100mV. Frequency response ±1dB 30 to 12,000Hz. Signal-to-noise -50dB. (Code: Mic. Hi-ZX).
4. **MAGNETIC PICKUP.** Impedance 56kΩ. Input sensitivity 5mV. Output 100mV. Frequency response to R.I.A.A. as shown in Fig. 2. Signal-to-noise -60dB. (Code: PU Mag.)




(a) Prototype

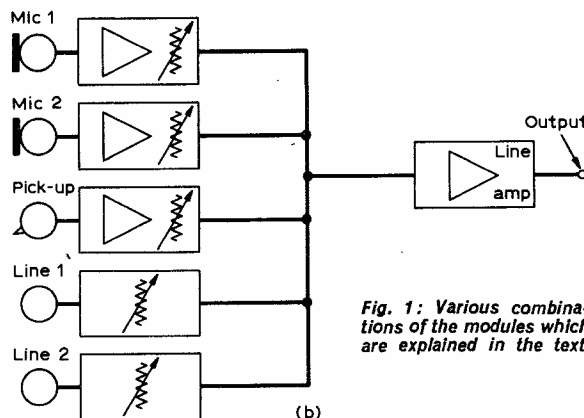

(b)

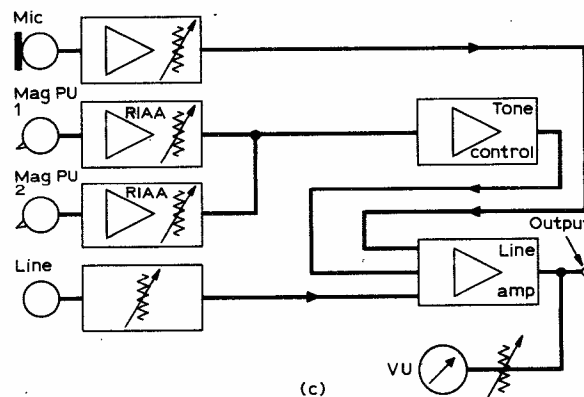

(c)

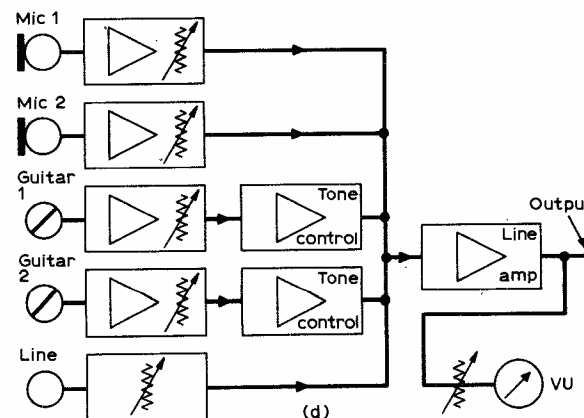

(d)

Fig. 1: Various combinations of the modules which are explained in the text.

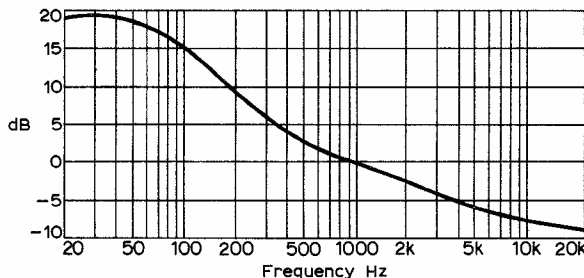


Fig. 2: The RIAA response curve incorporated in the magnetic pickup module.

5. CERAMIC PICKUP. Input impedance 2M $\Omega$ . Input sensitivity 60mV. Output 100mV. Frequency response approximately 20 to 20,000Hz  $\pm$ 1dB. Equalisation automatic due to high input impedance. Signal-to-noise -50dB. (Code: PU Cer.)
6. CRYSTAL PICKUP. Input impedance about 1M $\Omega$ . Input sensitivity 850mV. Output 100mV. Frequency response approximately 20 to 20,000Hz  $\pm$ 1dB. Equalisation automatic due to high input impedance. Signal-to-noise -60dB. (Code: PU Xtal.)
7. GUITAR PREAMP. Input impedance medium, 10 to 100k $\Omega$ . Input sensitivity variable. 50 to 100mV. Output 100mV. Frequency response  $\pm$ 1dB 20 to 30,000Hz. Signal-to-noise -50 to -60dB. (Code: G.)

The tone control unit will take the output from any of the preamps and provides 100mV output so that it can be coupled directly to the line amplifier. Its performance is as follows:— With tone controls neutral the flat response is 10 to 80,000Hz  $\pm$ 1dB. The response of the bass and treble controls is shown in Fig. 3 providing 15dB lift and 12dB cut at 40Hz and 15dB lift to 12dB cut at 20,000Hz. The signal to noise performance is better than -90dB. (Code: TC).

The line amplifier unit will accept the output from any of the preamps or the tone control unit and therefore has an input sensitivity of 100mV. The output signal level available is 1V r.m.s. at an impedance of approximately 600 $\Omega$ . The frequency response is flat from 10 to nearly 100,000Hz and the signal-to-noise performance -80dB. The output can be fed simultaneously to one or more tape recorders and/or amplifiers via series output resistors as will be shown. The overall gain of the line amplifier is adjustable i.e., the input sensitivity can be increased. (Code: LA.)

The line inputs do not require separate pre-amplifiers as these are arranged in passive network coupling directly to the line amplifier. The input sensitivity will be 200mV to over 1V r.m.s. at approximately 10k $\Omega$  impedance. (Code: L input.)

## CONSTRUCTION

The construction of each of the preamplifier modules is such that the circuit board is mounted on a small screen this, in turn, being secured to the fixing bush of the gain control (VR1 in each circuit). The complete preamp can therefore be secured to a front panel by the lock nut of the gain control. The tone control unit is similar except that there are two potentiometers and both are mounted on the small screen and then secured to the panel. The line amplifier can be simply mounted on a piece of aluminium angle ( $\frac{3}{8} \times \frac{3}{8}$  in) or on stand-off pillars as convenient. It need not be fixed to a panel but must

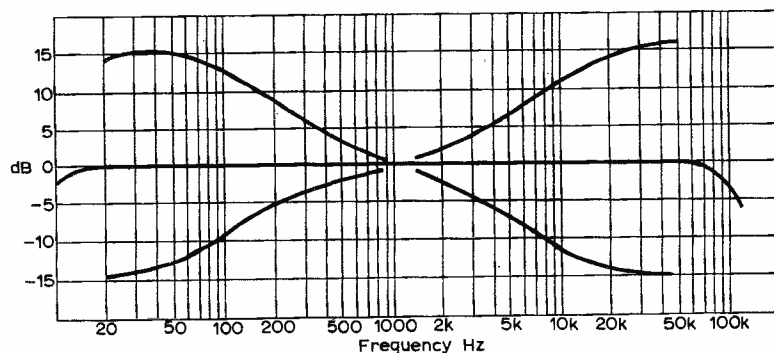


Fig. 3: Response curves of the tone control module.

be fairly well clear of mains power supply components. The input sockets for all inputs must be insulated from the front panel and earthed only at the common earthing point on the preamplifier board. If the mixing unit is to be mains powered, the components for the power supply must be kept as far away from the amplifier boards as possible and preferably with a screen around them.

The seven preamplifier boards are exactly the same and details for construction are given in Fig. 4. In each case the gain control (VR1) is fitted as shown


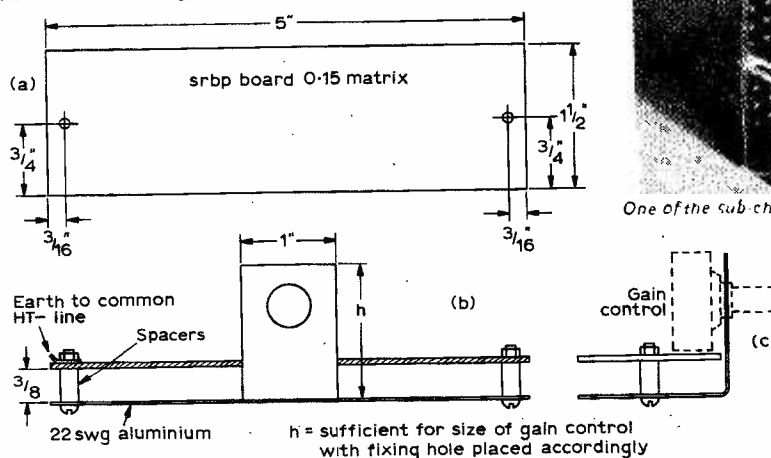


Fig. 4: Details of the sub-chassis used for each module.

in Fig. 4c. The construction of the tone control board is similar except that two controls have to be fitted so the screen has two flaps as shown in Fig. 5. The height of each flap and the position of the fixing hole will depend on the physical size of the potentiometers used.
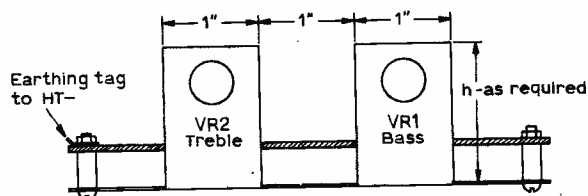
## CIRCUITS AND ASSEMBLY OF THE MODULES

Each of the amplifier modules and the tone control




Controls mounted as in Fig. 4 (c)

Fig. 5: Modified sub-chassis for the tone control module.

can be tested separately by operating them from an 18V battery (two 9V units) and by checking each one with an audio signal generator and audio voltmeter or by connecting an appropriate input signal source and feeding the output to an amplifier.
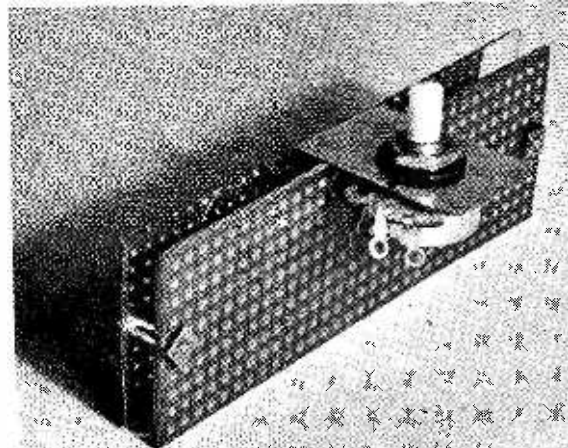
## LINE AMPLIFIER


The best order of construction is to build the line amplifier (code: LA) first so that the preamps can be tested with it as each is completed. The circuit is given in Fig. 6 and the board layout in Fig. 7. As



One of the sub-chassis before the components are fitted; dimensions are given in Fig. 4.

with all the circuits except the tone control unit only one type of transistor is used—the BC109 silicon NPN—which is readily available and inexpensive. The line amplifier employs three of these beginning with Tr1 as an emitter follower input stage with Tr2 as the amplifier.

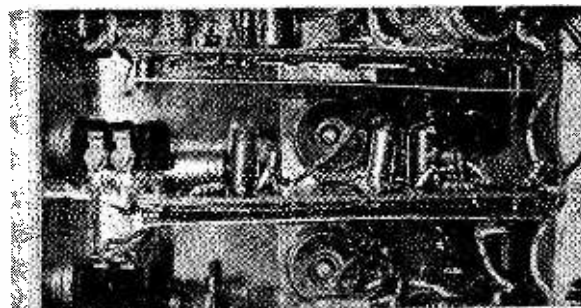Negative feedback between Tr2 and Tr1 via the pre-set PR1 ensures a linear response and some adjustment over total gain. The pre-set should be adjusted so that with a 100mV input signal the output at C6 is exactly IV. If a signal generator and audio voltmeter are unavailable, set PR1 to mid-way position. The output transistor Tr3 operates as an emitter follower and provides a low impedance



An internal view of the prototype showing one of the modules. The input jack is on the left with the common wiring on the right.

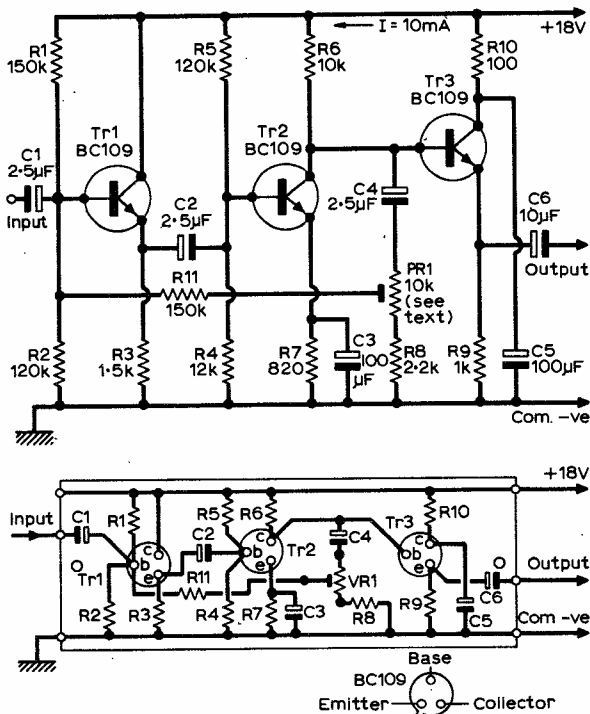


Fig. 6: (above) and Fig. 7 (below): The circuit and layout of the line amplifier module.

output. Details for feeding more than one power amplifier and/or tape recorder from the line amplifier output will be given later.

## MICROPHONE PREAMP (Mic Lo-Z)

The circuit is given in Fig. 8 and the board layout

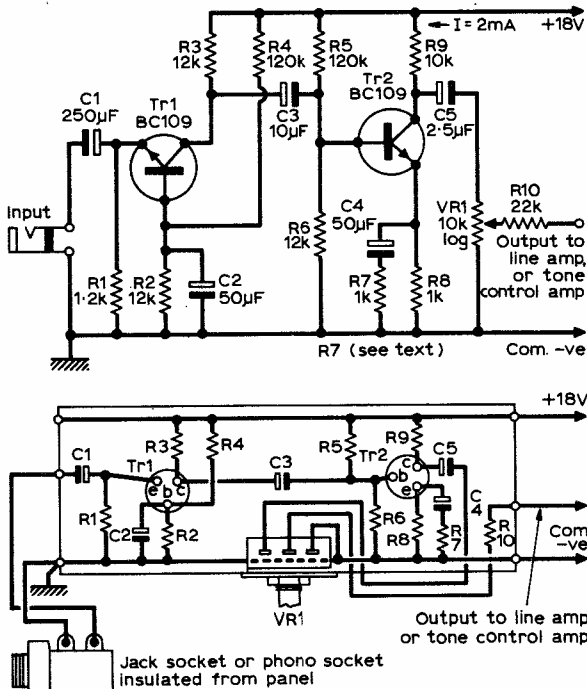


Fig. 8 (above) and Fig. 9 (below): The circuit and layout of the low impedance microphone preamplifier module.

## ★ components list

### Amplifier Modules Circuit Boards

7-15 mm x 15 mm s.r.b. board to sizes given. 22 g w/g. aluminium for module screens to sizes given.

### Line Amplifier (LA)

Tr1, Tr2, Tr3 BC109  
PR1 10kΩ Miniature carbon pre-set

#### Resistors

|    |       |     |       |
|----|-------|-----|-------|
| R1 | 150kΩ | R6  | 10kΩ  |
| R2 | 120kΩ | R7  | 820Ω  |
| R3 | 1.5kΩ | R8  | 2.2kΩ |
| R4 | 12kΩ  | R9  | 1kΩ   |
| R5 | 120kΩ | R10 | 100Ω  |

All 1W, 10% types

#### Capacitors

|    |       |     |    |       |     |
|----|-------|-----|----|-------|-----|
| C1 | 2.5μF | 25V | C4 | 2.5μF | 25V |
| C2 | 2.5μF | 25V | C5 | 100μF | 25V |
| C3 | 100μF | 25V | C6 | 10μF  | 25V |

### Microphone Pre-amplifier (Mic. Lo-Z)

Tr1, Tr2 BC109  
VR1 10kΩ Log. Potentiometer

#### Resistors

|    |       |     |      |
|----|-------|-----|------|
| R1 | 1.2kΩ | R6  | 10kΩ |
| R2 | 12kΩ  | R7  | 1kΩ  |
| R3 | 12kΩ  | R8  | 1kΩ  |
| R4 | 12kΩ  | R9  | 10kΩ |
| R5 | 120kΩ | R10 | 22kΩ |

All 1W, 10% types

#### Capacitors

|    |       |     |    |       |     |
|----|-------|-----|----|-------|-----|
| C1 | 250μF | 25V | C4 | 50μF  | 25V |
| C2 | 50μF  | 25V | C5 | 2.5μF | 25V |
| C3 | 10μF  | 25V |    |       |     |

### Power Supply

Transformer T1 18V Secondary Henry's Radio Type MT95  
Bridge Rectifier MR1 Henry's Radio Type LT118

C1 250μF 25-30V  
C2 5000μF 25-30V  
R 1W - see text

On/Off mains toggle switch

Panel neon indicator

All electrolytics used in the amplifier circuits should be rated for at least 25V working.

Each pre-amplifier will require an input jack socket or phono socket of the type that can be insulated from the panel on which they are mounted.


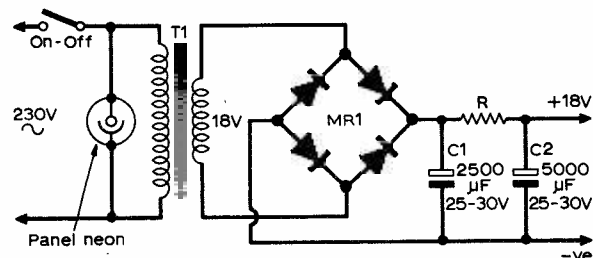


Fig. 10: Suggested circuit for a mains power supply to power the mixer.


in Fig. 9. The input transistor Tr1 operates as a grounded base amplifier and provides a very low impedance input. Tr2 is a signal amplifier with negative feedback introduced by R7 in series with the emitter by-pass capacitor C4. This resistor can be reduced a little in value to obtain more gain for very low output microphones, although it should not be less than 680Ω otherwise the noise level will rise excessively. As with all the preamplifiers the output is taken to the gain control VR1 and thence via the series resistor (R10) which becomes part of the passive mixing network common to all the preamps.
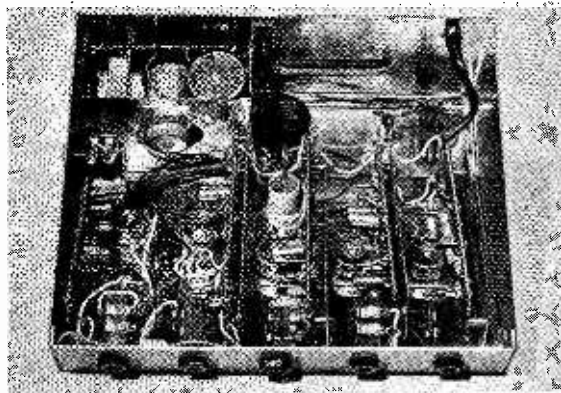
## MAINS POWER SUPPLY

The current consumption of the preamplifiers at



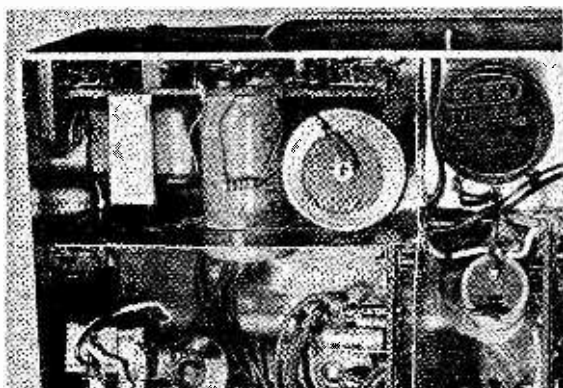*Internal view of the completed prototype.*



*The power supply should be properly screened as shown.*

18V varies between about 2 and 5mA. The line amplifier takes 10mA and the tone control unit 5mA. Four preamplifiers, a line amplifier and say one tone control unit, would require about 25mA which could be drawn from an 18V battery with reasonable economy. Two PP9 batteries would be ideal. Larger mixing units, particularly if built for stereo use and requiring duplication of preamps etc. are best operated from a mains power supply. One that will provide well over 100mA is given in Fig. 10 (see components list for transformer and rectifier details). The resistor R will be around 1kΩ for low current drain and of lower value for higher current drain. With the mixing circuits running, adjust R to obtain 18V across C2.

Part 2 next month, will deal with the rest of the preamplifier modules.

**TO BE CONTINUED**

CHARLES MOLLOY

# THE Medium Wave Column

A NEW 1000kW station on 1457kHz located near Tirana in Albania is being heard in this country as a background to BBC Radio 4, (South and West). It relays Radio Peking and has been heard at 2100hrs GMT with the identification 'Govarit Peking' followed by programmes in Russian. An increasing number of superpower broadcasters are appearing on the medium waves. Urumchi in Western China (2000kW) is audible all evening on 1525kHz; listen between Prague 1520kHz and Vatican Radio 1529kHz for Russian speech plus jamming. Libya has two megawatters—El Beida on 1124kHz and Tripoli on 1250kHz. El Beida is the stronger of the two; it is heard with EAJ15 Barcelona on the same frequency throughout the evening. Tripoli suffers from interference from Dublin/Cork until 2245hrs when the latter close down, leaving the channel clear. Further east, Riyadh (1200kW) in Saudi Arabia is on 587kHz and has been logged before midnight with Arabic programming.

Calcutta 1130kHz (1000kW) was heard frequently last winter before sign-off at 1700hrs. It is now on extended schedule and has been several times during the summer at 2230hrs GMT, as it changes from Chinese to Indian programming. There are three Voice of America stations in the Far East, each with 1000kW, all of which have been heard in the U.K. Bangkok, Thailand 1580kHz was logged at the end of September last year at 2200hrs GMT while Poro 1140kHz in the Phillipines and Okinawa 1178kHz in the Ryuku Islands are both heard in winter before sign-off at 1700hrs.

'Book of the World 1971' is the title of an unusual paperback now on sale in the bookshops. Sections deal with 181 different countries, each with a map plus details of the type of government, languages spoken, religions and currency. As well as providing the DXer with a valuable aid to station identification, this book gives background information on countries logged and adds interest to the hobby.

Broadcasts in English on the medium waves can be heard from a number of unexpected places during the late evening. Timisoara, Rumania on 755kHz has a programme in English, French and German at 2230hrs GMT, which should not be confused with the Voice of the West, in Portugal, also on 755, which starts its English programmes at 2245hrs. The Voice of America in Rhodes is 1259kHz is heard regularly in English between 2100hrs and midnight, with some interference from Wroclaw in Poland. Rhodes is one of the Dodecanese Islands situated near the coast of Turkey, which are usually counted as a separate country by DXers. The VOA is also heard in English from Thessalonika, Greece 791kHz between 2100hrs and 2130hrs. Enugu, Nigeria 1320kHz, although only 10kW, is a weak but consistent signal at 2300hrs GMT when it carries it's final news in English before closing down. ELBC Monrovia, Liberia on 629kHz has English programming and is usually logged between 2330hrs and sign-off at 0045hrs.



**\*  
IN NEXT MONTH'S**

**PRACTICAL  
WIRELESS**

**2-Octave  
Miniature Organ**

**Special Feature**

**\*  
What  
to look  
for at the  
AUDIO  
FAIR  
\***

**ALL IN THE NOVEMBER ISSUE  
ON SALE OCTOBER 8th**

**COMPREHENSIVE MULTI-BAND RECEIVER**


Do you want to build a communications receiver in easy stages? This design initially provides a basic 3 valve receiver, complete in itself, covering 550kHz to 30MHz with full bandwidth. At your leisure add an RF stage, a simple crystal filter, a carrier oscillator/product detector for receiving SSB/CW and finally a crystal marker. Full constructional details.

**BASIC SIGNAL GENERATOR**

A signal generator is essential for the testing, alignment and calibration of receivers and for quick tests of audio circuits. For the beginner or occasional dabbler, this basic design should prove ideal, with modulated or unmodulated outputs from 150kHz to 1.6MHz plus a direct audio source; all outputs are fed via a variable attenuator.

Plus many other constructional articles and all the regular features. Be certain not to miss the next issue, price 20p.

# DIGITAL FREQUENCY COUNTER/TIMER

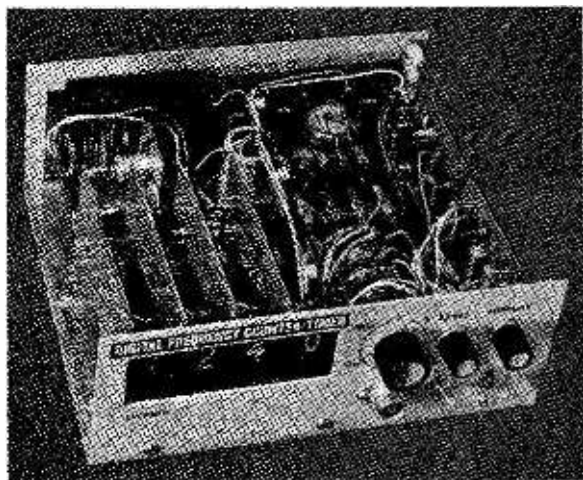

J. THORNTON-LAWRENCE GW3JGA

## PART 2 (continued from the September issue)

This negative going step is passed by C5 to Tr7 base which moves by -5 volts thus cutting off Tr7 and allowing the collector of Tr7 to rise to +5V.

The current through VR2 and R14 discharges C5 so that the negative voltage on Tr7 base rises exponentially until Tr7 conducts. The rate is determined by the setting of VR2, the DISPLAY control.

When Tr7 conducts, its collector voltage starts to fall, turning off Tr6 and thus increasing the base current to Tr7 and producing a fast negative going voltage at Tr7 collector. This voltage step is differen-

tiated by C7, R16 and R17 and inverted by IC2d to give a positive pulse of 200 $\mu$ S duration.

The positive going edge of this pulse resets the counter to zero and the negative going edge sets the JK flip-flop IC1a and causes the cycle of operation to be repeated. The time for which the reading is displayed is controlled by the DISPLAY control and this is adjustable from about 0.5 second to 2 seconds.

### NOTE

Several wiring connections were omitted from figure 6 in the September issue. Pin 10, on IC's 3, 4, 5, 6 and 7, should be shown connected to the 0V rail. Pins 1 and 12 on IC's 9, 11, 13 and 15, should be shown joined.

On IC1, pin 4 is the +5V supply rail and pin 11 is 0V supply rail. On IC2, pin 14 is +5V supply rail and pin 7 0V supply rail. These latter connections were omitted from figure 6 for clarity.

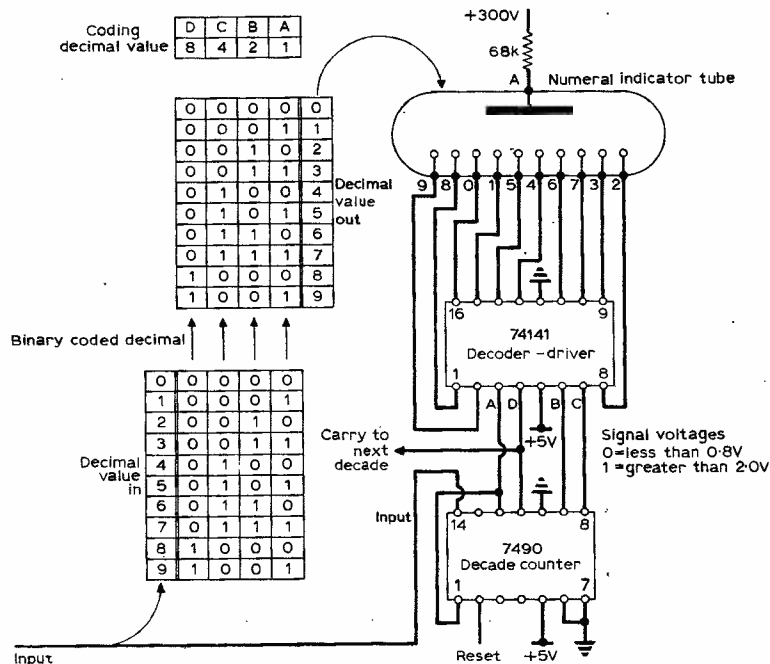


Fig. 9: Table showing the operation of the decade counter and decoder-driver.

## Counter and Display

The counter and display has four decades, each decade operates in the same way. The output of one decade is linked to the input of the next higher decade to perform the 'carry' operation and a reset connection is common to all decades.

The input to the counter is a series of pulses. The counting has to be carried out in binary form and then decoded into decimal form for display.

This is done using a decade counter I.C. type SN7490N, which consists of 4 master-slave flip-flops forming a  $\div 2$  counter and a  $\div 5$  counter.

The input signal goes to the input of the  $\div 2$  counter (pin 14) and the output of this (pin 12) is linked externally to the input of the  $\div 5$  counter (pin 1).

The outputs of the four flip-flops are called A, B, C, D and have a decimal value of 1, 2, 4, 8 respectively. The table showing the operation of the decade counter is included in Fig. 9.

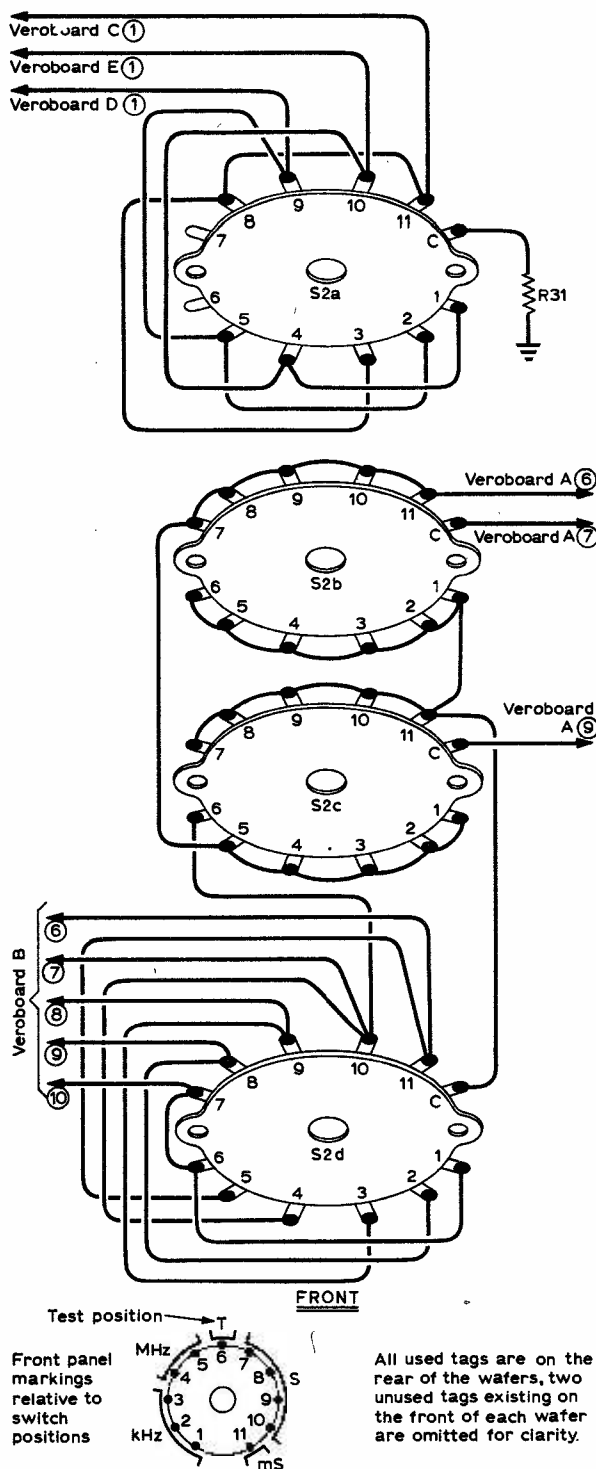


Fig. 10: Exploded view of the function switch S2, viewed from the front.

The counter can be reset to zero at any time by the application of a positive pulse to pin 2.

The binary coded decimal output from the counter, A, B, C, D is connected directly to the inputs of the decoder/numeral tube driver I.C. type SN74141N. Here the inputs are decoded back into decimal form

for driving the numeral tube (Hivac Type XN13).

The numeral tube contains neon gas at low pressure and has an anode and 10 wire cathodes in the form of numerals, 0-9.

With the anode connected to HT+ through a current limiting resistor, any cathode which is connected to 0V will be surrounded by a glow showing up the shape of the number.

The outputs of the decoder-driver are collector circuits of high voltage transistors which, when made to conduct, effectively connect the appropriate cathode to 0V. For example, suppose the input to the decade counter receives 5 pulses or cycles of input signal. The output will be D low, C high, B low, A high, representing a binary number of 0101. This number is decoded in the decoder/driver to figure 5 and the figure 5 output (pin 14) becomes switched to 0V causing the figure 5 to be displayed in the numeral tube.

Each counter, decoder/driver and tube is built on a Veroboard panel and the inter connection of these panels is shown in the main diagram Fig. 6.

The decimal indication is provided by miniature wire ended neon indicator lamps mounted between two numeral tubes and these are switched by the function switch S2a.

## Function Switch

The function switch S2 is made up from Radiospares Miniature 'Maka Switch' parts and consists of a shafting unit and 4 break-before-make 1 pole 12 way wafers. The wafers are spaced by 2 spacers on each side. Only 11 positions are used and the stop on the indexing mechanism is adjusted accordingly.

The wafers are lettered a, b, c and d, starting at the rear and working towards the indexing mechanism. Wafer 'a' controls the decimal point neon lamps, wafer 'b' the clock period input to the gate, wafer 'c' the signal input to the gate and wafer 'd' the output from the clock divider.

In the frequency positions 1 to 5, the output from the input stage is fed to the 'Signal Input' of the gate and the appropriate clock signal is fed to the 'Clock Period Input' of the gate. In the time positions, 7 to 11 of the switch, the output from the input stage is fed to the 'Clock Period Input' of the gate and the appropriate clock signal is fed to the 'Signal Input' of the gate.

A test position is provided in position 6 where the 1kHz clock output is counted for a period of 1 second to give a reading of 1,000. The test position only serves to check that the gate, counter and display are functioning, it does not provide a check of the crystal oscillator frequency.

The wiring and connections to the switch are shown in Fig. 10. The method of assembly is as follows:

1. On the shafting unit, check that the lengths of studding are screwed fully into the indexing mechanism plate and remove the end nuts and washers.
2. Rotate the switch spindle to the fully anti-clockwise position (as viewed from the front). The flats on the wafer end of the spindle should be in line with the studding. This is position "1".
3. The switch should now be held so that the lengths

of studding are at each side and the control knob end of the spindle is towards you, as shown in Fig. 10.

4. Take a 1 pole 12-way wafer and hold this with the side having the majority of tags, away from you and with the two tags that are facing you positioned in the top right hand segment. Rotate the rotor section until the common or rotor contact is making contact with tag 1. The slot in the rotor should now be horizontal.

5. Assemble the wafer on to the shafting assembly, keeping the side with the majority of tags facing away from the indexing mechanism. This wafer is now wafer "d" in Fig. 10.

6. Fit 2 spacers on each piece of studding.

7. Fit another wafer as described in operation 4 and 5 (wafer "c").

8. Repeat operations 6 and 7 until four wafers have been fitted (wafers "b" and "a").

9. Fit washers and fixing nuts to the studding.

10. The rotation of the switch should now be checked to see that all parts operate smoothly.

11. The rotatable stop plate, which is located on the face of the indexing mechanism, should now be set to give 11 positions, working clockwise and commencing from the maximum anti-clockwise position. This is the position at which all the wafers have been set. The stop plate may be held in place temporarily by the mounting nut, ready for assembly to the front panel.

12. The wiring of the switch may now be carried out as shown in Fig. 10. 22 s.w.g. tinned copper wire is used for wiring from tag to tag, sleeving being necessary only when crossing between wafers.

13. The correctness of the wiring can be checked by using an ohm or continuity meter and measuring between the appropriate tags whilst the switch is rotated, e.g. S2b/C is connected to S2d/C in positions 1, 2, 3, 4, 5 and 6.

## Power Supply

The power supply consists of a Radiospares Midget Mains transformer which with its associated rectifiers smoothing and regulators provides

|               |             |
|---------------|-------------|
| +300V at 10mA | Unregulated |
| +5V at 350mA  | Regulated   |
| -5V at 5mA    | Regulated   |

The output from the 250 volt secondary winding is rectified by D7 and smoothed by C12 to give about +300V output. The negative return is through R24 and D9 to 0V. The negative supply derived in this way is smoothed by C13 and regulated by the zener diode D9 to give -5V. The I.C. logic requires about 350mA at +5V and this is provided by the 6.3 volt filament winding on the transformer.

The 6.3 volt output is full wave bridge rectified to give about +7.5 volt across the reservoir capacitor C14. This feeds the zener diode D6 and the power emitter follower Tr11 to give the required 5V output.

## Veroboard Panels

The layout drawings of the 0.1x0.1in matrix Veroboard show the copper strip side of the panel the components on the reverse side being "seen through" the copper strips.

Each copper strip is given a letter code and each

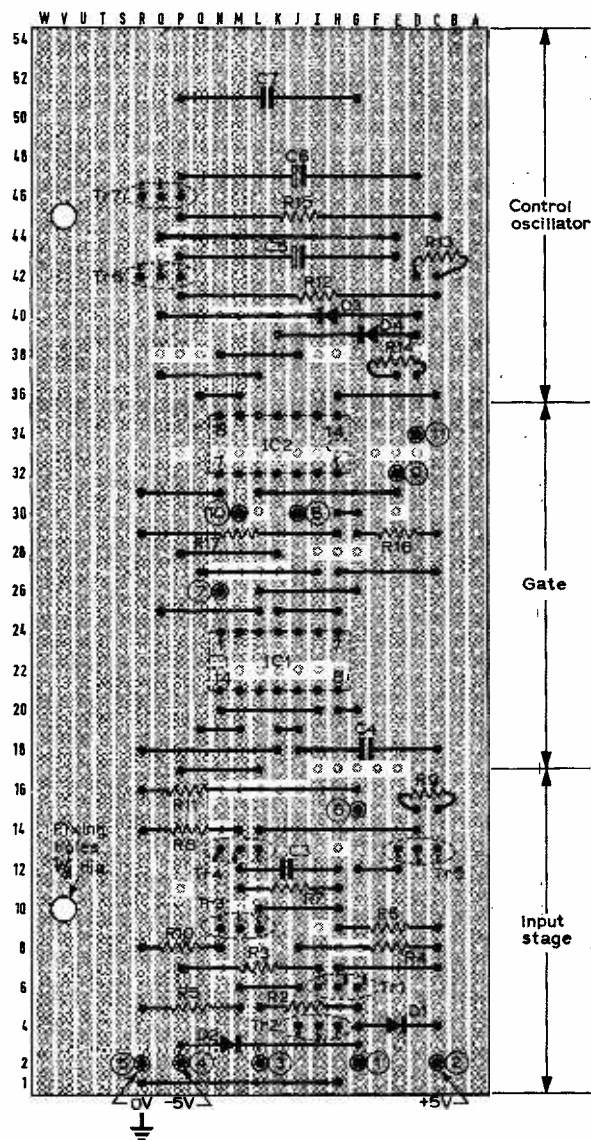


Fig. 11. Veroboard panel A. Input stage, gate and control oscillator. Viewed from copper side. Note correct orientation of integrated circuits when fitting. The integrated circuits and their holders are indented at one end to assist orientation.

horizontal row of holes, a number.

All solid horizontal lines represent wire links which connect one strip to another.

The orientation of integrated circuits and transistors should be noted carefully, some transistors may have unusual lead positions and these may have to be crossed over for the connections to be correct. Assembly of the components, etc., must be carried out in a systematic manner or errors will result. A suggested method is as follows:

1. Cut the Veroboard to the correct dimensions using a fine toothed saw and working from the copper side. Apart from checking the physical dimensions, also check that the correct number of holes appear in each direction.

2. Fix strips of masking tape on all four edges of the Veroboard panels. Also fix masking tape to the same edges on the reverse (copper) side of the board.

# DISCOUNTS UP TO 60% ON BRANDED GOODS

ALL BRAND NEW in manufacturer's sealed cartons. GUARANTEED 12 MONTHS.

SONY · LEAK · SINCLAIR · TELETON · ARMSTRONG · THORENS · PHILIPS · K.E.F. · TEAC · ROGERS · PIONEER

## SPECIAL OFFER

Garrard SP25 Mk.III.

Goldring G800H

Teak plinth and tinted cover. Ready wired for immediate use.

Please add £1.15 for post & packing

£18.50

## TURNTABLES

Please add 50p for post and packing

|                                     |        |
|-------------------------------------|--------|
| *Garrard SP25 Mk.III                | £10.75 |
| *Garrard 2025TC with stereo cart.   | £8.00  |
| *Garrard 2025TC with Sonotone 9TAHC | £8.95  |
| *Garrard 3000 with Sonotone 9TAHC   | £10.25 |
| *Garrard SL65B                      | £13.25 |
| *Garrard AP76                       | £18.75 |
| *Garrard SL72B                      | £24.00 |
| *Garrard SL73B                      | £28.00 |
| *Garrard SL95B                      | £35.50 |
| Garrard 401                         | £27.00 |
| *B.S.R. MP60                        | £11.00 |
| Pioneer PL12AC                      | £39.00 |
| Thorens TD 126                      | £62.50 |
| Thorens TD 126AB                    | £68.50 |
| Thorens 150 AB11                    | £42.50 |
| Goldring GL69/2                     | £21.50 |
| Goldring GL69 P2                    | £29.50 |

\* Items marked can be mounted in plinth and cover, ready wired for £4.50 extra plus 25p for post & packing.

## AMPLIFIERS

Please add 50p for post and packing

|                                   |        |
|-----------------------------------|--------|
| Armstrong 521 (cased)             | £41.95 |
| Armstrong 8000                    | £17.75 |
| Dulci 207                         | £15.95 |
| Dulci 207M                        | £21.00 |
| Eurolphon 10+10                   | £14.50 |
| H.L. Audio 707                    | £17.75 |
| Metrosonic ST20E                  | £29.00 |
| Philips R580                      | £20.50 |
| Pioneer SA600                     | £41.50 |
| Pioneer SA700                     | £58.00 |
| Pioneer SA900                     | £59.50 |
| Rogers Ravensbrook Chassis        | £39.00 |
| Rogers Ravensbrook Cased          | £41.00 |
| Rogers Ravensbourne Chassis       | £45.00 |
| Rogers Ravensbourne Cased         | £49.50 |
| Sinclair 2000-Mk1                 | £21.00 |
| Sinclair 2000 Mk1I                | £22.25 |
| Sinclair 3000                     | £23.50 |
| Sinclair PRO 60/2 x Z80/P25       | £15.75 |
| Sinclair PRO 60/2 x Z30/P26       | £18.00 |
| Sinclair PRO 60/2 x Z50/P28/Trans | £22.95 |
| Teleton SAQ206                    | £18.00 |

## TUNERS

Please add 50p for post and packing

|                                  |        |
|----------------------------------|--------|
| Armstrong 523 AM/FM              | £40.00 |
| Armstrong 524 FM                 | £31.00 |
| Dulci FMT7                       | £19.50 |
| Dulci FMT7 Stereo                | £27.00 |
| Teleton GT101 MP1X               | £50.50 |
| Rogers Ravensbrook FET 2 Chassis | £45.50 |
| Rogers Ravensbrook FET 2 Cased   | £49.00 |
| Rogers Ravensbrook FET 4 Chassis | £37.50 |
| Rogers Ravensbrook FET 4 cased   | £53.00 |

## PICK-UP ARMS

Please add 35p for post and packing

|                       |        |
|-----------------------|--------|
| SME 3009/82           | £23.95 |
| SME 3012/82           | £25.75 |
| Goldring L75          | £9.50  |
| Goldring L69          | £7.50  |
| Audio-Technica AT1005 | £14.95 |

## TUNER AMPLIFIERS

Please add 75p for post and packing

|                             |         |
|-----------------------------|---------|
| Armstrong 525FM             | £38.75  |
| Armstrong 526 AM/FM         | £78.75  |
| Teleton CR10T with speakers | £26.25  |
| Teleton F2300 (new product) | £38.50  |
| Teleton CR55                | £27.00  |
| Teleton TRF50               | £31.75  |
| Teleton F2000               | £31.00  |
| Wharfedale 100-1            | £103.00 |
| Teleton TRF50LA             | £80.00  |
| Teleton 2100                | £34.00  |

## SPEAKERS

Please add £1.25 for post and packing

(PRICE PER PAIR)

|                     |           |
|---------------------|-----------|
| Wharfedale Denton   | £29.75    |
| Wharfedale Melton   | £49.90    |
| Wharfedale Triton   | £45.75    |
| Wharfedale S/Linton | £40.75    |
| Keletron KN500      | £15.00    |
| Keletron KN700      | £18.00    |
| Keletron KN123/3    | £11.50    |
| Keletron KN1000     | £27.50    |
| Keletron KN1500     | £27.00    |
| Keletron KN2000     | £41.50    |
| K.E.F.              | by letter |
| Celestion D110N 120 | £25.50    |
| Celestion D110N 15  | £49.50    |
| Celestion D110N 25  | £101.00   |
| Celestion D110N 10  | £67.50    |
| Ste-Ma 400          | £34.00    |
| Ste-Ma 300          | £48.50    |
| Ste-Ma HI-F1 4      | £78.00    |
| Ste-Ma HI-F1 115    | £17.50    |
| Ste-Ma HI-F1 3      | £69.50    |

## GLOBAL CONTRACT SERIES

|                                 |        |
|---------------------------------|--------|
| Contract 8 3-way 7 watts R.M.S. | £16.00 |
| Contract 6 3-way 5 watts R.M.S. | £10.75 |

## SPEAKER KITS

|                   |        |
|-------------------|--------|
| Wharfedale Unit 3 | £20.50 |
| Wharfedale Unit 4 | £27.00 |
| Wharfedale Unit 5 | £39.00 |

## CARTRIDGES

Please add 10p for post and packing

|                        |        |
|------------------------|--------|
| Goldring G850          | £3.75  |
| Goldring G800H         | £5.50  |
| Goldring G800          | £8.75  |
| Goldring G800E         | £10.50 |
| Goldring G800SE        | £15.25 |
| Sonotone 9TAHC Diamond | £1.75  |
| Shure M3DM             | £4.75  |
| Shure M445/7/C         | £7.00  |
| Shure M55              | £9.00  |
| Shure M75E             | £14.00 |
| Shure V15 Type 2       | £28.00 |
| Shure M44E             | £8.00  |
| Shure M81E             | £8.50  |
| Shure M52E             | £8.00  |
| Audio-Technica AT66    | £4.95  |
| Audio-Technica AT35    | £14.25 |
| SMC 101                | £2.75  |
| MC15                   | £4.50  |

## TAPE DECKS & RECORDERS

Please add 75p for post and packing

|                  |        |
|------------------|--------|
| Teleton FXB 510D | £44.75 |
| Teleton TCR150   | £22.90 |

## PERSONAL CALLERS VERY WELCOME!

Come and browse through our multi

1,000 foot warehouse/showroom.

**NO PARKING PROBLEM**

## PURCHASE TAX CUT!!

—we pass these reductions to you

The following branded names are not allowed to be advertised at Discount Rates—SONY, SANYO, BANG & OLUFSEN, TRIO, RADFORD, SONAB, NIKKO, CHILTON, FERROGRAPH, LUXOR, CELESTION, AKAI, TANNAY, TANDBERG, TEAC, CAMBRIDGE, ARENA, ROTEL. Send a stamped addressed envelope for a GUARANTEED DISCOUNT PRICE.

## PLINTHS & COVERS

(as illustrated)

£3.20



plus 35p post and packing

Finished in real teak veneer with tinted dustcover. Ready to use (fully assembled). Suitable for Garrard SP25; 2025TC; 3000; AT60; 2000; 2500; 3500; 5100; 1025; SL65B.

ALSO FOR

B.S.R. McDONALD MP60 AND OTHERS

Plinths and Covers for AP76; AP75; SL72B; SL75B; SL95B; £4.20 plus 35p post and packing.

Also finished in walnut to match Japanese equipment—no extra charge.

## GLOBAL TRANSEUROPEAN COMBO

Made by world famous European manufacturer

## COMPLETE HI-FI STEREO SYSTEM VHF/MEDIUM/LONG WAVE Tuner Amplifier

4 watt per channel, separate tone and balance controls.

Two neat speakers with wooden slatted front. Single play deck in plinth and cover. Finished in teak. Fully guaranteed 12 months. On constant demonstration.

£37.50

plus £1.25 carriage



## GLOBAL AUDIO DISCOUNT WAREHOUSES

Dept. (P.W.2.) 174 Pentonville Road, London, N1. Telephone 01-278 1769


Open Monday to Saturday 9.30 a.m. to 6 p.m. LATE NIGHT FRIDAY 7 p.m.

2 minutes from KING'S CROSS, EUSTON & ST. PANCRAS on main road leading to the East and West Country

**MAIL ORDERS:** Order with confidence. Send Postal Order, Cheque, Money Order, Bank Draft, Giro or Cash by Registered Mail. CALLERS: Please note that cheques can only be accepted together with cheque cards (not Barclay Card).




## BETTER GET 'SET'

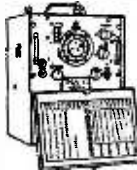

**BEST OFFER YET!**  
**FAMOUS BC.21**  
**FREQUENCY METER**  
125 KHz-20 MHz. Complete  
with valves, crystal and charts.  
ONLY £18.50. Carr. £1.50.  
LIMITED NUMBER - ORDER  
NOW!
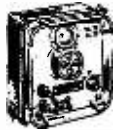
### CRYSTAL CALIBRATOR

**No. 10** Crystal controlled hetero-  
dyne wave-meter covering 500 KHz-  
10 MHz (Harmonics up to 30 MHz).  
Power required 300V. D.C. 15mA.  
12v. 0.3A. D.C. Test equipment for  
GEM/EC.  
ONLY £4.25. P. & p. 50p.  
**FEW ONLY—No. 63 TM/EC**  
1.5-10 MHz £17.50. Carr. £2.



**MARCONI 801A SIGNAL GENERATOR**  
10-310 MHz. In original transit case. £45. Carr. £2.50.

### AERIAL MAST

#### EQUIPMENT

**20' TELESCOPIC MASTS**

£3.75. Carr. £1.

5' 2" Extension Sections to

fit bottom of above mast to

increase height. £1.25 each

(any number supplied).

**35' MAST** 7-5" 2" inter-

locking sections with base


plate and 12 nylon guys with

semi-auto tensioner.

£23.50. Carr. £2.50.

**70' MAST** Ditto 18 guys, block

and tackle. £45. Carr. £2.75.

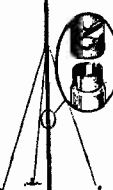

### AERIAL RODS 3ft.

Screw-in 1" dia. sections. Brand New, green finish. Suitable  
for many other uses. 10 for £2. Carr. 50p. 25 for £5. Carr.  
Paid.



### R.F. ANTENNA

#### TUNER (A.T.U.)

Cylinder design 10" x 4 1/2". Pre-  
cision calibrated scale. Suitable  
for tuning most aerials for  
increased signal strength. A must  
for serious operators for RC or  
TM. Full instructions.  
ONLY £1.75. P. & p. 25p.

### R.F. ANTENNA TUNER (A.T.U.)

#### OPEN TYPE

Mounted on ceramic former and feet.



"Boiler Coaster" design 16 G  
silver or silver plated wheel  
turning on wire on ceramic  
former. Will handle consider-  
able R.F.  
In original packing. As used  
with No. 53 Transmitter.  
ONLY £2.50. P. & p. 50p.



### No. 19 SET

#### TRANSMITTER

#### RECEIVER

Rebuilt. Complete station with  
PSU, Cables, Mic, Aerial, etc.  
£23.50. Carr. £3.

**No. 19 SET 500uA METERS**  
Scaled 0-600 and 0-15V. Brand new, boxed £1.25 Post  
Paid. (Quantity prices on request.)



**R.F. AMPLIFIER.** To increase  
output of No. 19 Set.  
ONLY £3.75. Carr. £1.25.  
Instruction Book for R.F. Amp.  
87p Post Paid.

### ALL No. 19 SPARES

#### IN STOCK

Complete instruction book  
with circuits for No. 19  
Equipment. 37p Post Paid.

### HEAVY DUTY

#### BATTERIES

New in metal cases with

carrying handles.

6v. 85 AH

18" x 9 1/4" x 7"



£3.25. Carr. £1.25

### FAMOUS TELE 'F'

#### FIELD TELEPHONES

Suitable for Farms, Building  
Sites etc. Communication up  
to 5 miles or more. Rugged  
construction, will last a lifetime.

ONLY £5.75 PAIR. Carr. £1.

(Twin telephone wire for above available—ask for price.)  
Many other Ex-Govt. Surplus Equipment items in stock.  
Receivers etc. in small quantities too numerous to mention.  
Enquiries invited. LIST 25p Post Paid. (Refundable  
against purchases over £3.)

C.W.O. Carriage charges apply to Mainland only.



**NEW 3in. SPEAKERS** 16 ohms 75p. p. & p. 10p.

**BARGAIN PARCELS** 14lb at £1.45 plus 24p p.p.; 28lb at  
£2.75 plus 52p p.p.; 56lb at £4.50 plus £1.25 p.p. Contain  
pots, Res, Valves, Diodes, Tagboards, Chassis, Valve-  
holders, etc. Good value save £222. Lucky Dip Service.

**NEW 6 ft. VHF AERIALS.** Freq. 75-78 Mc/s. 70 ohms.  
£2.50p. p. & p. 50p.

**VHF Receiver, Type 715,** less crystal 60-100 Mc/s can be  
operated on 2 or 4 meters or made tunable 12 volt input,  
not tested: complete with valves and speaker. £3 plus £1 p.p.

**VHF AERIAL TUNING UNITS** consisting of the following:  
1-1 1/2" 500 micro/ampmeter. 1 small 2-gang 75 PF  
capacitor. 1 various large wattage resistors for dummy  
load. Pair gears B.N.C. type sockets. Will tune 10 mtrs  
with 25/30 watts R.F. input. Size only 1 1/2" x 4 1/2" x 8"  
Sealed. Price £1.37p p.p. 25p

**CRYSTALS AS NEW:** Hc 6u, 5.345; 5.030; 5.005; 4.945;  
4.875; 4.840; 4.795; 4.860; 4.820; 4.810; 2.300;  
2.295 Kc/s. 50p each plus 8p. p.p.

**SCOOP PURCHASE OF BRAND NEW CARBON RESIS-**  
**TORS.** 10% tolerance & 1 watt. Preferred values in  
packets of 10. Our price 50p per 100. 50p per 200. £1.35 per  
300, 50p at £2.12p. Our selection. p.p. 8p per 100 and 21p  
per extra 100.

**TRIMMER BARGAINS.** These are 10PF sub-min. air-  
spaced trimmers on board with min. wire ended Xtal.  
Brand new. No details: Contents 12 trimmers, some  
ceramic caps. Xtal frequency 3RD overtone 249 mc/s-  
250 Mc/s, 255 Mc/s. No choice.  
Trimmers without Xtal—50p per doz. plus 17p p.p.  
Trimmers with Xtal—75p per doz. plus 17p p.p.  
Also 20 PF min. brand new air spaced.  
50p per doz. plus 17p p.p.

**ANY HEIGHT AERIAL TUBULAR SECTIONS** 1" dia  
x 3 ft. long. Brass screw in type, copper coated and  
painted. New 20p each. p.p. 5p. each. Minimum order 6.

**BRAND NEW HARTLEY OSCILLOSCOPES** CT318 in  
original packing. Band width up to 5 Mc/s. Mains supply.  
Price £40. p. & p. £1.50p.

**AERIALS NEW CONDITION.** Whip type 4ft 25p, 14ft.  
77p. Used condition 4ft. 20p, 14ft. 62p. All collapsible  
type p. and p. 4ft. 10p, rest at 17p. Bases for above 25p.  
p.p. 12p. New matching unit coax connection for above  
80p. p.p. 5p.

Huge release of valves for the 62 set TX/BX. in original  
rubber packing consisting of QV04/7 x 61M, AR12 etc.  
10 valves in all at the bargain price as seen  
87p plus 17p p.p.

R209. Set of valves 62p. p.p. 25p.

New Headphone and Mike. rubber muff type. Low  
impedance. 97p. p. & p. 17p.

**NEW AERIAL WIRE ON BOARDS 7/82 UNCOVERED.**  
75ft, 40p, 90ft, 47p, 100ft 55p, 150ft, 75p, 180ft, 95p,  
250ft, £1.30p, p & p 12p.

Headphones, ex Gov. DLR No. 5 high impedance.  
New 87p 17p p.p. Used condition 62p 17p p.p.

### MURHEAD DECADE A.F. SIGNAL GENERATOR.

This precision instrument can be used:

1. To Measure Gain up to 50 db.
2. To Measure Loss up to 45 db.
3. To compare Power Levels (A.F.).
4. As an Audio Frequency Generator covering 100 Hz  
to 41 kHz. With a dial setting accuracy of ±0.5 Hz.  
Output: —1 M/W into 600 Ω. Complete with mains  
power unit. Tested. Good Condition. £12. p & p. 75p.

Heavy New Coax Cable 750HM will handle at least 1KW  
50ft lengths. Plug on end, £1.70p + 30p.p.

Also 1" 75 ohm Coax in 50ft coils with BNC plugs good  
condition. price £1 + 30p. p.p.

2 BNC plugs on short length coax cable large size low loss  
plugs 30p + 5p. p.p.

Block Type capacitor TCC 8UF + 15% 350 VDC WK4  
60°C, 250 VDC WK9 70°C Type 62 CIM Price 40p + 13p  
p.p. New.

C.W.O. CARRIAGE CHARGES MAINLAND ONLY

## STROBE! - STROBE!

Build a Strobe Unit, using the latest type  
Xenon white light flash tube. Solid state timing  
and triggering circuit. 230/240V a.c. operation.  
**EXPERIMENTERS' ECONOMY KIT**  
Speed adjustable 1 to 36 flash per sec. All  
electronic components including Veroboard  
S.C.N. Unijunction Xenon Tube and instructions  
£6.30 plus 25p P. & P.

### NEW INDUSTRIAL KIT

Ideally suitable for schools, laboratories, etc.  
Roller tin printed circuit. New trigger coil,  
plastic thyristor. Speed adjustable 1-80 f.p.s.  
Price £10.50. P. & P. 50p.

### HY-LIGHT STROBE MK III

This strobe has been designed and produced  
for use in large rooms, halls and the photo-  
graphic field, and utilizes a silica plug-in tube  
for longer life expectancy, printed circuit for  
easy assembly, also a special trigger coil and  
output capacitor. Speed adjustable 0-30 f.p.s.  
Light output approx. 4 joules. Price £12.00  
P. & P. 50p. Suitable metal case £3.50 extra.

### AND NOW!

### THE 'SUPER' HY-LIGHT KIT

Approx. four times the light output of our well  
proven Hy-Light strobe.  
Incorporating:

- Heavy duty power supply.
- Variable speed from 1-23 flash per sec.
- Fantastic Octal based tube with massive  
electrodes.
- Reactor control circuit producing an  
intense white light.

The brilliant light output of the 'SUPER'  
HY-LIGHT gives fabulous effects with colour  
filters.

Never before a Strobe Kit with so HIGH an  
output at so LOW a price. ONLY £20 plus.  
75p P. & P. Suitable metal case £5.50 extra.

**7-inch POLISHED REFLECTOR**  
Ideally suited for above Strobe kits. Price 53p.  
P. & P. 13p or post paid with kits.

### LIGHT SENSITIVE SWITCHES

All parts incl. ORP.12, relay, trans-  
istor and circuit. 6 or 12v. operation  
Price £1.25 plus 12p P. & P.  
**120/240 AC MAINS MODEL**

Transformer, rectifier, special relay  
1 make, 1 break. £2.38. P. & P. 20p  
inc. circuit.



### INSULATED TERMINALS

In black, red, white, yellow,  
blue and green. New, 10p each  
post paid.

### VENNER ELECTRIC

#### TIME SWITCH

200/250V Ex. GPO. Tested.  
Manually set 2 on, 2 off every 24h.  
Override switch: 10A £2.75, 15A  
£3.25, 20A £3.75. P. & P. 20p.  
Also available with solar dial ON dusk, OFF  
dawn. Price as above.

### 200-250V A.C. NEON INDICATOR

Available in red or amber  
at 20p each. Or in green at  
32p each. Minimum order 3 units. P. & P. 5p.



### ELECTRONIC

#### ORGAN KIT

Easy to build, Solid State. Two full octave  
(less sharps and flats). Fitted hardwood case.  
Powered by two penlite 1 1/2V batteries. Complete  
set of parts including speaker etc., together  
with full instructions and 10 tunes. Price £3.00.  
P. & P. 22p.

**50 in 1 ELECTRONIC PROJECT KIT**  
50 easy to build Projects. No soldering,  
no special tools required. The kit includes Speaker,  
Meter, Relay, Transformer, plus a host of other  
components and a 56-page instruction leaflet.  
Some examples of the 50 possible Projects are:  
Sound Level Meter, 2 Transistor Radio,  
Amplifier, etc. Price £7.75. P. & P. 30p.

### CRYSTAL RADIO KIT

Complete set of parts, including Crystal  
Diode, Ferrite Aerial, Drilled Chassis and  
Personal Ear Piece. No soldering, easy to build,  
full set by step instructions. £1.75 inc. post.

### 12 VOLT DC MOTOR

Powerful 1 amp. RE-  
VERSIBLE motor. Speed  
3750 RPM complete  
with external gear train  
(removable) giving final speed of  
125 RPM. Size: 4 1/2" x 2 1/2" dia. Price 95p inc. p



## SERVICE TRADING CO


All Mail Orders, Also Callers, Parking Space.  
Dept. PW10, 57 BRIDGMAN ROAD,  
LONDON, W4 5BB. Phone 01-995 1360.  
Showrooms now open, Mon.-Fri.

Personal Callers only. Open SAT.  
9 LITTLE NEWPORT ST.  
LONDON, WC2H 7JJ 01-437 0576.

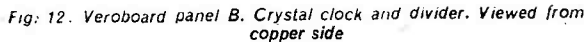
## Surplus Electronic Trading

DRIVERS END LANE, CODICOTE,  
HITCHIN, HERTS, SG4 8TP

Hours of business: 8-5 Mon.-Fri., 8-12 Sat.  
Telephone: Codicote 242 for appointment



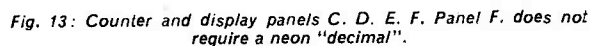4. The breaks in the copper may be made using the appropriate Vero tool, part No. 2022 or by using a  $\frac{5}{16}$  in. drill held in a pin vice. Each copper break on the layout drawing should be identified by its co-



Check each soldered joint using a magnifying glass as it takes only a very small piece of swarf

or solder to bridge the 0.025in gap between the copper strips.

8. Connections to the Veroboard panel are made to pins inserted in the appropriate places and soldered to the copper strip. These pins are Vero type TP 11032 or similar.

An insertion tool for this pin is Vero part No. IT 2151.

9. Tick off each break, link, component and pin on the drawings as they are fitted, this will identify any items which otherwise might be missed.

## Semiconductors

The 3702 and 3704 transistors are specified in the components list as being the '2N' types, these are the most popular version and are readily available.

The 3702 and 3704 transistors are also available

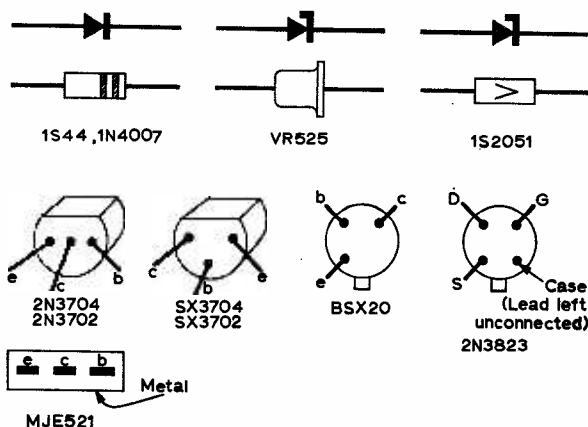


Fig. 14 (left) Cabinet and chassis construction.

in an 'SX' version. The lead connections for these types are all different from each other and are shown in the diagram above.


It should be noted that on the Veroboard panels, the connections run e.b.c. and when the '2N' version is used, the collector and base leads will have to be crossed over to line up with the appropriate holes in the Veroboard panel.

## Sockets for Integrated Circuits

Sockets are used for all the integrated circuits and although this increases the overall cost and is not essential for the operation of the instrument, it does provide the facility for disconnecting or changing an I.C. should a fault condition exist, also it does allow various parts of the instrument to be tested without incurring the expense of buying all the I.C.'s at once, 16-way sockets are required for I.C.8, 10, 12 and 14 and 14-way sockets for all the others.

The instrument is built using a simple aluminium chassis, panel and cover type of construction, as shown in Fig. 14. The finished chassis size is 8×7×3/8in deep and has a front and rear panel, each size 8×3in, fastened to the front and rear edges with 6BA screws and nuts.

(To be continued)

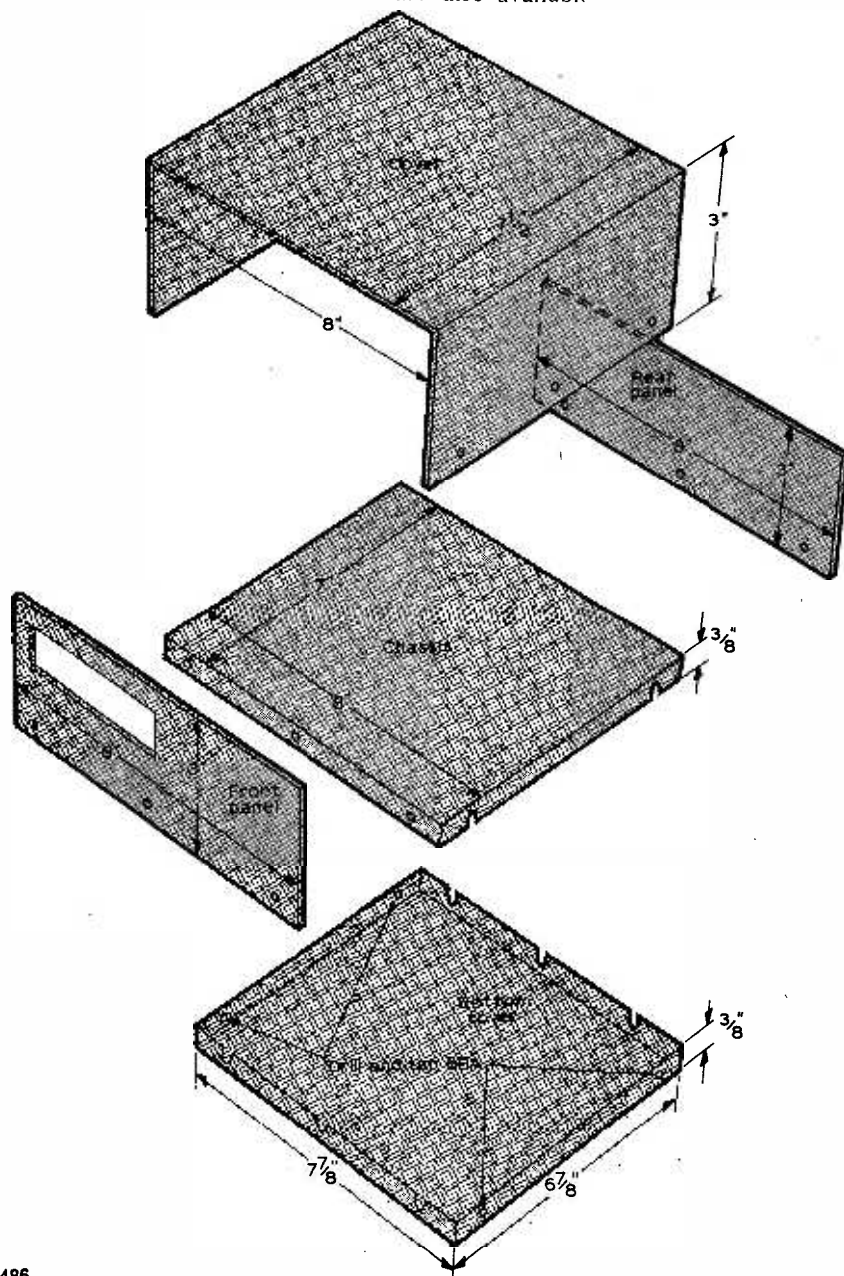

# ATTRACTIVE DISCOUNTS at all times

# ELECTROVALUE Electronic Component Specialists

EVERYTHING BRAND NEW & TO SPEC • LARGE STOCKS • NO SURPLUS

## BARGAINS IN NEW SEMI-CONDUCTORS

MANY AT NEW REDUCED PRICES • ALL POWER TYPES WITH FREE INSULATING SETS

|         |     |         |     |        |     |        |     |        |     |
|---------|-----|---------|-----|--------|-----|--------|-----|--------|-----|
| 40361   | 55p | 2N2905  | 44p | 2N4291 | 15p | BC148  | 9p  | BFX87  | 29p |
| 40362   | 68p | 2N2906A | 47p | 2N4292 | 15p | BC149  | 10p | BFX88  | 26p |
| 2N696   | 17p | 2N2924  | 20p | AC107  | 48p | BC153  | 19p | BFY60  | 23p |
| 2N697   | 18p | 2N2925  | 22p | AC126  | 20p | BC154  | 20p | BFY51  | 20p |
| 2N706   | 12p | 2N2926  | 11p | AC127  | 20p | BC157  | 12p | BFY52  | 23p |
| 2N930   | 29p | 2N3053  | 27p | AC128  | 20p | BC158  | 11p | BSX20  | 16p |
| 2N1131  | 29p | 2N3055  | 60p | AC153K | 22p | BC159  | 12p | C407   | 17p |
| 2N132   | 29p | 2N3702  | 18p | AC176  | 16p | BC167  | 11p | MC140  | 25p |
| 2N1302  | 19p | 2N3703  | 13p | ACY20  | 20p | BC168  | 10p | MP8531 | 35p |
| 2N1303  | 19p | 2N3704  | 13p | ACY22  | 16p | BC169  | 11p | MP8534 | 30p |
| 2N1304  | 28p | 2N3705  | 13p | AD140  | 63p | BC177  | 14p | NKT211 | 25p |
| 2N1305  | 28p | 2N3706  | 13p | AD142  | 50p | BC178  | 13p | NKT212 | 25p |
| 2N1306  | 33p | 2N3707  | 13p | AD149  | 58p | BC179  | 14p | NKT214 | 23p |
| 2N1307  | 33p | 2N3708  | 10p | AD161  | 33p | BC182L | 11p | NKT214 | 18p |
| 2N1308  | 36p | 2N3709  | 11p | AD162  | 36p | BC183L | 10p | NKT243 | 55p |
| 2N1309  | 36p | 2N3710  | 13p | AF114  | 24p | BC184L | 11p | NKT405 | 79p |
| 2N1613  | 28p | 2N3711  | 13p | AF115  | 24p | BC212L | 16p | OC71   | 38p |
| 2N1711  | 28p | 2N3819  | 23p | AF117  | 22p | BC213L | 16p | OC81   | 25p |
| 2N1893  | 54p | 2N3904  | 35p | AF124  | 24p | BC214L | 16p | OC81D  | 25p |
| 2N2147  | 95p | 2N3906  | 35p | AF127  | 22p | BCY70  | 18p | ZTX300 | 14p |
| 2N2218  | 34p | 2N4058  | 13p | AF139  | 36p | BCY71  | 18p | ZTX301 | 16p |
| 2N2218A | 44p | 2N4059  | 10p | AF239  | 36p | BCY72  | 15p | ZTX302 | 22p |
| 2N2219  | 38p | 2N4060  | 11p | ASY26  | 27p | BF115  | 23p | ZTX303 | 22p |
| 2N2219A | 53p | 2N4061  | 11p | ASY28  | 27p | BF167  | 18p | ZTX304 | 27p |
| 2N2270  | 62p | 2N4062  | 12p | BC107  | 12p | BF173  | 19p | ZTX500 | 18p |
| 2N2369A | 19p | 2N4124  | 18p | BC108  | 11p | BF194  | 14p | ZTX501 | 21p |
| 2N2483  | 35p | 2N4126  | 27p | BC109  | 12p | BF195  | 15p | ZTX502 | 25p |
| 2N2484  | 42p | 2N4254  | 15p | BC125  | 15p | BFX29  | 31p | ZTX503 | 22p |
| 2N2646  | 47p | 2N4256  | 15p | BC126  | 22p | BFX84  | 32p | ZTX504 | 52p |
| 2N2904A | 42p | 2N4259  | 15p | BC147  | 10p | BFX85  | 25p |        |     |

Appointed distributors for  
**SIEMENS (U.K.) LTD.**

Appointed stockists for  
**NEWMARKET TRANSISTORS  
RADIOHM POTENTIOMETERS**

## SAVE £6.25 ON THE NEW ENGLEFIELD 840 AMPLIFIER

This latest Peak Sound high fidelity amplifier incorporates many strikingly original features including facility for adding in stereo FM tuner. Superb performance characteristics and luxurious styling Electrovalue choice of simulated soft leather covering in black, blue, red or dark green. As now advertised at £49.50. Our price **£38.75** nett

## MAINLINE AMPLIFIER KITS

70W. £12.60 nett. (main amplifier module).

## 30 WATT BAILEY AMPLIFIER PARTS

Transistors and PCB for one channel £6.46  
Capacitors, resistors (metal oxide), and transistors, one channel. £8.41.  
Complete unregulated power supply pack, £4.75.  
Suitable heatsink 10DN 400C. 55p.

## SIEMENS' TTL INTEGRATED

We stock a large range of all types for very wide range of applications. For full details, see our latest catalogue.

## S-DeC RANGE

S-DeC £1.44; DeCSTOR £2.88; S-DeC 4 Pack £5.10; T-DeC £2.88; µDeC 'A' £3.18; µDeC 'B' £5.91.  
All prices increased approx. 20% since publication of our 1971 catalogue (pages E1-33). Guide prices unchanged.

## INDICATOR LAMPS

NEON chrome bezel, round red NR/R. 24p; chrome bezel, round amber NR/A. 24p; chrome bezel, round clear NR/C. 24p. Neon, square red type LS5C/P. 18p; amber type LS5C/A. 18p; clear type LS5C/C. 18p. All above are for 240V mains operation. Filament types: 6V. 0.04A square red type LS5C/R-6V. 30p; 6V 0.04A amber type LS5C/A-6V. 30p; 6V 0.04A clear type LS5C/C-6V. 30p; 6V 0.04A green type LS5C/G-6V. 30p; 12V 0.04A LS5C/R-12V. 34p; 34V 0.04A LS5C/R-28V. 45p.

## SIEMENS' POLYCARBONATE CAPACITORS

5% tolerance  
250V up to 0.1mF. 100V 0.1mF and above.  
0.01, 0.012, 0.015, 0.018, 0.022, 0.027, 5p; 0.033, 0.039, 0.047, 0.056, 0.068, 0.082, 0.1, 0.12, 0.15, 0.18, 0.22, 6p; 0.27, 7p; 0.33, 9p; 0.39, 9p; 0.47, 10p; 0.56, 13p; 0.68, 15p

## DIN CONNECTORS

|             |    | plug            | socket |
|-------------|----|-----------------|--------|
| Loudspeaker | .. | 2-pole          | 12p    |
| Audio       | .. | 3-pole          | 13p    |
| Audio       | .. | 4-pole          | 14p    |
| Audio       | .. | 5-pole 180 deg. | 15p    |
| Audio       | .. | 5-pole 240 deg. | 15p    |
| Audio       | .. | 6-pole          | 15p    |

Handbook of transistor equivalent and substitutes, 40p. (Postage 3p if ordered alone).

ELECTROVALUE 1971 CATALOGUE. 64 pages and covers. Packed with items and information. Post free 10p

## RESISTORS 10%—5%—2%

| Code | Power | Tolerance    | Range        | Values available | 1 to 9 | 10 to 99<br>(see note below) | 100 up |
|------|-------|--------------|--------------|------------------|--------|------------------------------|--------|
| C    | 1/20W | 5%           | 82 Ω—220K Ω  | E12              | 9      | 8                            | 7      |
| C    | 1/8W  | 5%           | 47 Ω—470K Ω  | E24              | 1      | 0-8                          | 0-7    |
| C    | 1/4W  | 10%          | 47 Ω—10M Ω   | E12              | 1      | 0-8                          | 0-7    |
| C    | 1/2W  | 5%           | 47 Ω—10M Ω   | E24              | 1-2    | 1                            | 1-9    |
| MO   | 1W    | 10%          | 47 Ω—10M Ω   | E12              | 2-5    | 2                            | 3      |
| MO   | 1/2W  | 2%           | 10 Ω—1M Ω    | E24              | 4      | 3-5                          | 3      |
| WW   | 1W    | 10% ± 1/20 Ω | 0.22 Ω—3.9 Ω | E12              | 7      | 7                            | 6      |
| WW   | 3W    | 5%           | 12 Ω—10K Ω   | E12              | 7      | 7                            | 6      |
| WW   | 7W    | 5%           | 12 Ω—10K Ω   | E12              | 9      | 9                            | 8      |

Codes: C = carbon film high stability low noise  
MO = metal oxide Electrosl TR5 ultra low noise  
WW = wire wound Plessey.

Values:  
E12 denotes series: 10, 12, 15, 18, 22, 27, 33, 39, 47, 56, 68, 82 and their decades.  
E24 denotes series: as E12 plus 11, 13, 15, 20, 24, 30, 36, 43, 51, 62, 75, 91 and their decades.

## ZENER DIODES

5% full range E24 values; 400mW: 2.7V to 30V 15p each  
1W: 6.8V to 82V 27p each 1.5W: 4.7V to 75V 60p each  
Clip to increase 1.5W rating to 3 watts (type 266F) 4p.

## CARBON TRACK

### POTENTIOMETERS, long spindles

Double wiper ensures minimum noise level.  
Single gang linear 220 Ω, to 2.2M Ω 12p  
Single gang log 4.7K Ω to 2.2M Ω 12p  
Dual gang linear 4.7K Ω to 2.2M Ω 42p  
Dual gang log 4.7K Ω to 2.2M Ω 42p  
Log/anti-log 10K, 47K, 1M Ω only 42p  
Any type with 1A D.P. mains switch, extra 12p

Please note: only decades of 10, 22 and 47 are available within ranges quoted.

## CARBON SKELETON PRE-SETS

Small high quality, type PR. linear only 100 Ω, 220 Ω, 470 Ω, 1K, 2K2, 4K7, 10K, 22K, 47K, 100K, 220K, 470K, 1M, 2M2, 5M, 10M Ω Vertical or horizontal mounting 5p each.

ENAMELLED COPPER WIRE even No S.W.G. only.  
30z reels 16.22 S.W.G. 25p; 34-30 S.W.G. 30p; 32-34 S.W.G. 33p; 36-40 S.W.G. 35p; 40z reels 16.22 S.W.G. only 41p.

## MULLARD polyester C280 series

250V 20%; 0.01; 0.022; 0.033; 0.047 3p ea. 0.068; 0.1, 0.15 4p, 0.22 5p, 10%; 0.33 7p, 0.47 8p, 0.68 11p, 1µF 14p, 1.5µF 21p, 2.2µF 24p.

## MULLARD SUB-MIN ELECTROLYTIC

C426 range axial lead 6p each  
Values (µF/V): 0.64/64; 1/40; 1.6/25; 2.5/16; 3.5/84; 4/10; 4/40; 5/54; 6.4/64; 6.4/25; 8/4; 10/25; 10/18; 10/64; 12.5/25; 16/40; 20/18; 20/64; 25/64; 25/25; 32/4; 32/10; 32/40; 32/64; 40/18; 40/25; 50/64; 50/25; 50/40; 64/4; 64/10; 80/25; 80/16; 80/25; 100/64; 125/4; 125/10; 125/16; 160/25; 200/64; 200/10; 250/4; 320/25; 320/64; 400/4; 500/25.

## LARGE CAPACITORS

High ripple current types: 1000/25 28p; 1000/50 41p; 1000/100 35p; 2000/25 37p; 2000/50 57p; 2000/100 41.44; 2500/64 77p; 2500/70 98p; 5000/25 62p; 5000/50 41.10; 5000/100 22.91; 10000/50 22.40.

## COMPONENT DISCOUNTS

10% on orders for components for £5 or more. 15% on orders for components for £15 or more (No discount on nett items).

## POSTAGE AND PACKING

Free on orders over £2. Please add 10p if orders under £2. Overseas orders welcome: carriage and insurance charged at cost. Prices subject to alteration without notice.  
U.S.A. CUSTOMERS. U.S.A. orders charged at prices as advertised by ELECTROVALUE AMERICA, P.O. Box 27, Swarthmore, PA 19081.

# ELECTROVALUE

(Dept. PW.1071) 28 ST. JUDES ROAD, ENGLEFIELD GREEN, EGHAM, SURREY

Hours: 9—5.30; Sat. 1 p.m. Tel.: Egham 5533 & 4757 (STD 0784-3) Telex 264475



## CASH & CARRY GOODS



### SINCLAIR Project 60

SAVE nearly £7 Normal price £23-90

Designed for building into  
plinth etc., complete with  
two 230 Output stages  
(20 watt) and power supply unit.  
Send S.A.E. for full technical brochure.

plus  
50p  
carr.

Sinclair 2000 £24  
Sinclair 3000 £33  
Metrosound ST20 £27  
Teleton 203  
(Demonstration) £17  
Teleton F2000  
Tuner/Amp. £31  
Teleton SAQ 206 £19.75  
Alpha F212 £26

Please add 50p carr. per  
amplifier. Other Ampli-  
fiers — Tuners — Tape  
Recorders etc. Prices on  
application.

## This MONTH'S Best Buy ...



### AKG K50 Dynamic Stereo headphones

Complete with spare ear muffs.

Total (value £10.40) Our Price **£5.90** + 23p p. & p.

Available only from us at this price. Due to entire  
purchase of manufacturer's remaining stock this  
fantastic offer is open only while stocks last.

- \* High-fidelity reproduction due to broad frequency response (20-20,000Hz)
- \* Substantially increased stereo effect
- \* Headphones fit the head gently and do not shift
- \* Earpieces fit ears snugly (Cardanic suspension)
- \* Tone quality superior to conventional loudspeakers
- \* Only expensive studio loudspeakers can match the reproduction quality of the K50
- \* Music can be reproduced at concert hall volume (1), preserving the lower bass notes and brilliant treble tones without causing any strain to the listener.




### GARRARD SP25 mk III

£12.50 Plus 50p carriage

Normal price £15.57  
Wired with mains cable and 5ft.  
twin screened stereo cable,  
5 pin din plug, 53p extra.  
AP75 Complete with base and  
cover £25 plus 75p carriage.

PLINTH AND COVER SUIT-  
ABLE FOR GARRARD RANGE  
£5.25 plus 50p p. & p.

## PLUGS

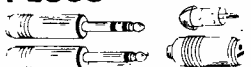

Pack 107 5-Pin Din ... 20p  
Pack 108 3-Pin Din ... 18p  
Pack 135 1/2" Jack ... 25p  
Pack 130 1/2" Jack Stereo ... 48p  
Pack 103 Loudspeaker Plug ... 15p  
Pack 100 Phono Plug ... 6p  
Pack 230 3-Pin Socket ... 23p  
Pack 238 5-Pin Socket ... 30p  
Pack 234 Loudspeaker Socket ... 30p

Ready-made Leads  
3-pin to 3-pin Din ... 63p  
3-pin to open end ... 53p  
5-pin to 5-pin Din ... 80p  
5-pin to open end ... 65p  
5-pin to 4 phono plugs ... 93p  
5 speaker lead Din to spade 12ft ... 38p  
Extension lead Din plug to socket 12ft 85p  
All leads approx. 6ft. in length. Post free, by return.

## Replacement Stereo DIAMOND STYL

8TA 9TA 9TAHC  
GPH ST4 ST9  
EV28 GC9

75p each

others on request +13p p. & p.

### Countdown SPEAKER

Teak Cabinet

£12 insurance & carr. 38p

A speaker of out-  
standing speci-  
fications and tech-  
nical merit. Solid  
teak cabinet size: 14" x 10" x 6".  
Originally designed for use with our  
Countdown stereo budget system  
but now available separately.



## EMI 20w matched loudspeaker set 350

Frequency range: 20 to 20,000Hz. £7.50

Normal price £13 plus 40p p. & p.

### EMI 10w matched loudspeaker set 450

Our price £3.75 plus 25p p. & p.

13 1/2" x 8 1/2" elliptical loud-  
speaker and independ-  
ent high frequency  
units with associated  
crossover network. Fre-  
quency range 55 to  
13000Hz. The cone of  
the bass unit has a sur-  
round designed for high  
travel giving freedom from distortion  
when operated at low frequencies.  
Also 150 KIT 10W £2.50 plus  
3, 8 or 15 ohms 40p p. & p.



## Magnetic cartridges Diamond styl

£4.75

plus 13p p. & p.

Today's value £8.

Stylus replacement  
can be carried out without removing  
cartridge. Fully guaranteed.

Ronette 105 Stereo cartridge (Sapphire 78 Diamond LP) £1.25 + 13p. p. & p.



## SONOTONE Cartridge ...

(Fitted Diamond Styl)  
(Ceramic) list price £4.10

£2.50

Sensitivity: 97mV/cm/sec

rms. minimum at 45° plus

1,000Hz measured on 13p

Decca SX12057 p. & p.

# J. J. FRANCIS

(WOOD GREEN) LTD

123 ALEXANDRA ROAD, HORNSEY,  
LONDON, N.8.

Tel: 01-888 1662

# YOUR OWN PROFESSIONAL SOLID STATE CLOSED CIRCUIT TELEVISION CAMERA

ONLY  
**£70** INCLUDING LENS  
& VIDICON TUBE


## INCLUDING LENS & VIDICON TUBE

Designed by the Mullard Educational  
Service, and shown on the BBC's  
'Tomorrow's World' programme, the  
Linstead camera provides a com-  
posite output comprising sync, pulse  
and picture information.

### Free 78-page manual

We give you a superb, fully illustrated  
78-page construction and service  
manual with this kit. Apart from full  
assembly instructions, a complete  
description of basic camera prin-  
ciples, vidicon tube operation and  
circuit diagram, this manual shows  
all waveforms within the circuitry.  
We also supply a copy of the BBC  
Test Card F.

**Linstead**

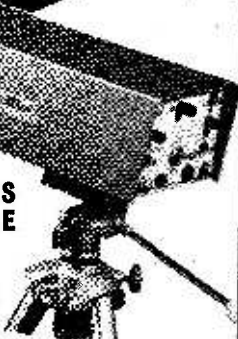

The basic kit, excluding  
lens and tube  
costs only

**£45**

## A COMPLETE FULLY CON- STRUCTED AND TESTED CAMERA COST ONLY **£99.85**

Components are also avail-  
able separately (for instance  
mains transformer  
£2.50 each)

For full details, send  
S.A.E. today.


RoslynWorks, Roslyn Rd.  
LONDON, N.15  
Telephone: 01-802 5144

Newest, neatest  
system ever de-  
vised for storing  
small parts and  
components: re-  
sistors, capacitors,  
diodes, transis-  
tors, etc. Rigid  
plastic units, in-  
terlock together  
in vertical and  
horizontal com-  
binations. Trans-  
parent plastic  
drawers have label  
slots / removable  
space dividers. Build up  
any size cabinet for wall, bench or table top.

## INTER-LOCKING PLASTIC STORAGE DRAWERS

NEAT!  
HANDY!  
TIDY!

DISCOUNT  
PRICES

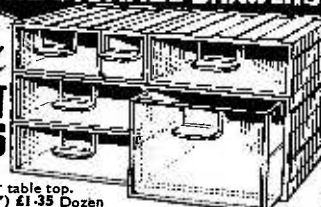

**DOUBLE UNITS** £2.25 Dozen  
**TREBLE (3D)** £2.35 for 8  
**DOUBLE TREBLE** 2 draws in one outer case (6D2) £3.65  
for 8 extra large size (6D1) £3.30 for 8.

**PLUS QUANTITY DISCOUNTS!** Order £5 and over Deduct 5% in the £. Order  
£10 and over Deduct 7 1/2% in the £. Order £20 and over Deduct 10% in the £.  
Pack./Post./Carr.: Add 35p to all orders under £5. Orders over £5 P/P/C free.  
(Dept PW10) 124 CRICKLEWOOD  
BROADWAY, LONDON N.W.2

## NEW VALVES!

Guaranteed and Tested  
24-HOUR SERVICE

|        |     |        |     |        |     |       |     |        |     |       |     |
|--------|-----|--------|-----|--------|-----|-------|-----|--------|-----|-------|-----|
| 1R5    | -26 | 30L17  | -68 | EABC80 | -30 | EF91  | -12 | PCF80  | -28 | PY801 | -33 |
| 1B5    | -21 | 30P4   | -60 | EB91   | -10 | EF183 | -28 | PCF86  | -44 | R19   | -30 |
| 1E4    | -14 | 30P13  | -60 | ECB33  | -38 | EF184 | -28 | PCF801 | -30 | U25   | -64 |
| 3B4    | -28 | 30P16  | -60 | EDF59  | -28 | EL33  | -64 | PCF802 | -43 | U26   | -58 |
| 3V4    | -37 | 30PL13 | -77 | ECB31  | -16 | EL37  | -75 | PCF805 | -62 | U191  | -59 |
| 5Y3GT  | -27 | 30PL14 | -65 | ECC82  | -19 | EL84  | -22 | PCF82  | -32 | U261  | -65 |
| 6J30L2 | -56 | DAF91  | -21 | ECC83  | -22 | EY51  | -34 | PCL84  | -34 | U329  | -65 |
| 6A4Q5  | -24 | DAF96  | -35 | ECC85  | -25 | EY86  | -30 | PCL85  | -40 | UBF89 | -31 |
| 6BW7   | -55 | DC90   | -80 | ECC80  | -27 | EZ80  | -21 | PL86   | -38 | UCC85 | -34 |
| 6P1    | -60 | DF96   | -35 | ECF82  | -26 | EZ81  | -22 | PFL200 | -52 | UCH81 | -30 |
| 6P25   | -55 | DK91   | -28 | ECH85  | -27 | PC94  | -34 | PL86   | -37 | U191  | -59 |
| 6N7GT  | -28 | DK92   | -40 | ECH81  | -27 | KT66  | -80 | PL81   | -45 | UCL83 | -48 |
| 25L6GT | -20 | DK96   | -36 | ECL82  | -30 | PC86  | -47 | PL82   | -30 | UFR89 | -29 |
| 30C15  | -60 | DL92   | -26 | ECL86  | -35 | PC88  | -47 | PL84   | -30 | UY85  | -66 |
| 30C18  | -62 | DL94   | -37 | EF99   | -36 | PC97  | -38 | PL500  | -62 | Z77   | -18 |
| 30F7   | -97 | DL96   | -36 | EF80   | -23 | PC900 | -32 | PL504  | -63 |       |     |
| 30FL1  | -60 | DY86   | -24 | EF85   | -30 | PC94  | -30 | PY81   | -24 |       |     |
| 30FL14 | -69 | DY87   | -24 | EF86   | -30 | PC98  | -45 | PY82   | -24 |       |     |
| 30L15  | -58 | DY802  | -38 | EF99   | -24 | PC139 | -45 | PY80   | -33 |       |     |

Postage on 1 valve 5p, on 2 or more valves 3p per valve extra. Any parcel insured against  
damage in transit 3p extra. Office address, no callers.

## GERALD BERNARD

83, OSBALDESTON RD., STOKE NEWINGTON, LONDON, N.16



# TESTING

R A BUTTERWORTH



## surplus transistors

THE technical press offer so many transistor projects that many of us have bought and acquired a fair stock of transistors gathered from bargain packs or labouriously removed them from surplus computer boards. We then go through them only to find that many are un-marked, indecipherable, or have some queer markings not contained in any lists. The manufacturers are reluctant to supply data because they have been made to "customer requirements". A few hours spent in sorting these into NPN or PNP and grading them into four categories will save a lot of time, patience and money on the next project development. The methods of grading are only approximate and there are only four grades:—

1. RF types.
2. Low gain types.
3. High gain types.
4. All others which do not pass the tests described.

### PRELIMINARY TESTING

First do a thorough visual examination and sort the transistors into *known* and *unknown*. The *knowns*, however, should be put through the tests since they may be blown or below spec. If your collection contains transistors removed from computer boards, the leads will be short. Fortunately when these boards are assembled, small plastic

spacers are fitted, in most cases to comply with manufacturer's recommendations as to bending and heat dissipation. The makers also usually bend over about  $\frac{1}{8}$  in on the solder side with the result that the lead lengths are in a safe condition. Any that are too short should be thrown away. Figure 1 shows the bases of seven categories into which these recovered units fall. Some may have a coloured dot, usually red or white, indicating the collector lead, also some are internally connected collector-to-can. Do not be


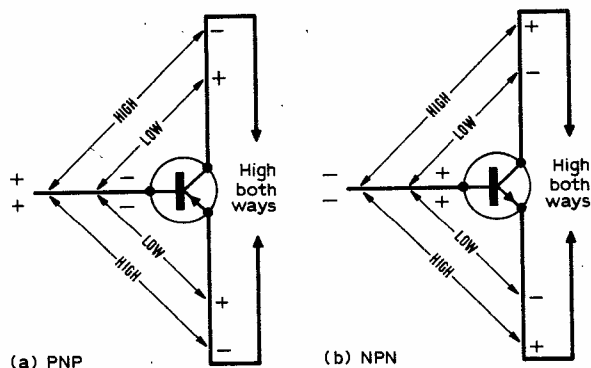



Fig. 2 : Resistance readings found on a good transistor—see text for details.

Fig. 1: Some transistor lead connections. These are only the most common arrangements and variations do exist.

Square metal can

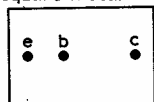


May have colour dot

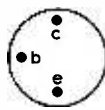


Metal no tab




Plastic

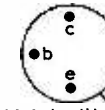


Metal with tab

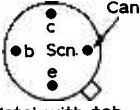

Metal with tab and screen

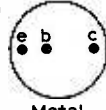

Metal or glass

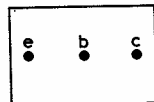

Square metal can

fooled however by coloured sleeving on the leads; not all manufacturers use the same code. Of course a really good transistor checker can make things very easy but this will cost a good deal of money.

### IDENTIFYING THE LEADS

The first checks, sorting the PNP and NPN types and the leads are done with a multimeter on its low ohms range. A word of warning first about that multimeter. Most meters on the ohms range give positive volts at the NEGATIVE LEAD and negative at the POSITIVE lead, so check first. Figure 2 illustrates the method of finding out whether the transistor is PNP or NPN. Never be scared of reversing the leads from the meter; with about 1.5V, which is usually

available from the meter on low ohms ranges, you won't do any harm. Should you get a low resistance reading both ways between base and either of the other connections you can be fairly certain that there is an internal short. If you get a low reading between the base and one lead and a high at the other it is either bad or you are not on the base. It is probable that you will meet with marginal readings at times, so make tests as follows with reference to Fig. 3.

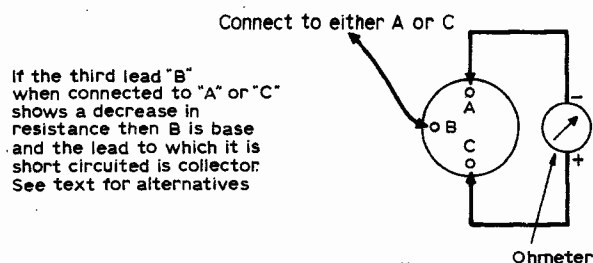


Fig. 3: Tests for identifying the base connections.

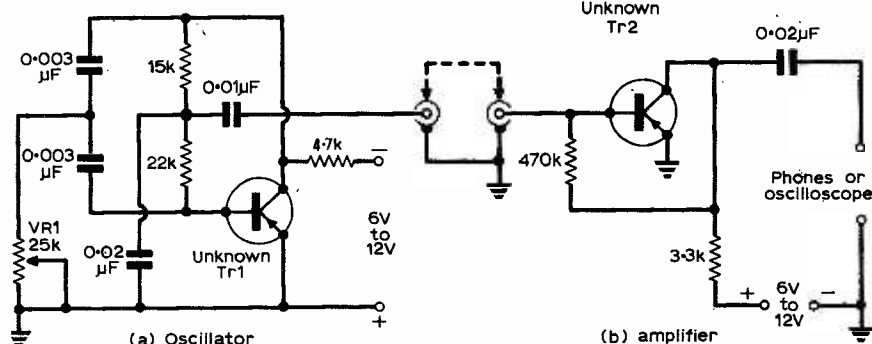


Fig. 4: The circuit used for the gain and amplification tests. Note that for NPN devices the battery polarity must be reversed.

Draw a base diagram of the base of the transistor and mark them 'A', 'B', 'C'; you are now faced with three permutations, of pairs 'AB', 'AC' 'BC'. Now take any pair and connect to the ohmmeter on low ohms range, then connect the other lead to each lead in turn: if the resistance falls the unpaired lead is the base lead and the lead to which the base was shorted is the collector. Check to see if this lead is connected to the metal can, this could confirm that it is the collector. If you do not get these results then check each of the three pairs using the same procedure. If the base cannot be identified for certain and there is high resistance both ways it is most probable that the third lead is base. To check, assume this is base and check with the meter whether it is a PNP or NPN in Fig. 1. You should then have established the base connection; the emitter and collector connections will be identified by reversing the leads in the grading test.

#### TESTING FOR GAIN

To test for gain two simple circuits are required as shown in Fig. 4. Good quality transistor sockets are essential since we are most likely dealing with short leaded transistors and soldering in and out will become tedious. The assembly of the the circuits is an individual choice, though the author used 'S-Dec' and found it ideal. When the test rig is assembled, put in two good known transistors, say an OC44 or OC45 for Tr1 and an OC70 or OC72 for Tr2, connect up the battery and headphones. If you can use a

'scope, all the better. Now adjust VR1 until a tone (or trace) is observed, then start to substitute the unknowns for Tr1. If a tone is present the gain will be more than 30, if no oscillation occurs then it is less than 30. At this point those transistors which have connections which are difficult to identify can be checked and identified by insertion, keeping the assumed base connection and reversing the other two unknown leads in the socket. If no oscillation occurs, keep it for the two further tests. Do not be afraid to reverse leads even at this higher voltage; if it blows then it was probably useless anyway.

#### AMPLIFICATION TEST

Now replace the original test transistor i.e. the OC44/45 (or one of the good ones known to oscillate) and then one by one test all those which failed the high gain test by substitution in the Tr2 position. The note heard in the headphones will tell you if it will amplify at all. If it is possible to use an oscilloscope, a little more information will be gained on this last test which is for low gain. By means of the trace shown on the 'scope, you can classify some transistors in the large signal class because the waveform will be distorted or clipped. The assumption in the tests up to now has been that the surplus transistors are in the small signal group.

#### R.F. TESTS

All the transistors available should be put through the r.f. test, irrespective of whether they have passed the previous tests. The r.f. test circuit is shown in Fig. 5. Here the reader will have to arrange for the crystal, Tr1, L1 and C1, according to what he has available, to check frequency. As a guide, with a 20MHz overtone crystal, an OC170, L1 being eight turns of 18s.w.g. on a  $\frac{1}{2}$ in former, tuned with a 50pF capacitor, the circuit will cover the range up to

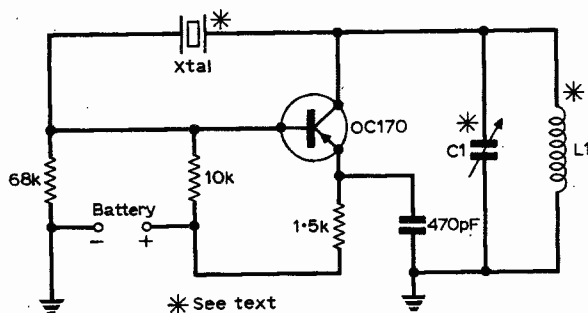


Fig. 5: The r.f. test circuit. For NPN devices the battery polarity must be reversed.

30MHz. Here a receiver or G.D.O. is necessary to detect the oscillation. Once oscillation is established it is merely a matter of substituting as before.

With your collection graded, as outlined, it is simply a matter of substitution of various types within that grade for optimum results in a particular project. The methods described are by no means comprehensive but at least you will have got a little order out of chaos and the building of many projects will be made much easier. ■

## HEARING AID AMPLIFIERS

(Ex behind ear deaf aids) 3 transistors on tiny P.C. board with volume control—whole thing only about half as big as Oxo cube. £1.75 or with sub-miniature microphone and L.S. attached £3-50.



## MAINS OPERATED SOLENOIDS

Model 772—small but powerful 1" pull—approx size 1 1/2" x 1 1/2" x 1 1/2".  
Model 400/1 1/2" pull. Size 2 1/2" x 2 1/2" x 1 1/2".

Model TT10 1 1/2" pull Size 2 1/2" x 2 1/2" x 1 1/2"—£1-80 plus 20p post and insurance.

## BEST QUALITY BRITISH MADE ELECTRICAL PLUGS AT APPROX. HALF PRICE

15 amp 3 pin 10p each or ten for 90p, 5 amp 3 pin 8p each or ten for 70p, 5 amp 2 pin 5p each or ten for 45p.

## DRILL CONTROLLER NEW IKW MODEL

Electronically changes speed from approximately 10 revs. to maximum. Full power at all speeds by finger-tip control. Kit includes all parts, case, everything and full instructions. £1-50 plus 18p post and insurance. Made up model also available, £2-25 plus 13p post & n.



**CONTROL DRILL SPEEDS**



## PRECISION MOTOR

Precision made — as used in record decks and tape recorders—ideal also for extractor fan, blower, heaters, etc. New and perfect. Snip at 50p. Postage 15p for first one then 5p for each one ordered.

## NEED A SPECIAL SWITCH?

Double Leaf Contact. Very slight pressure closes both contacts. 6p each, 80p doz. Plastic push rod suitable for operating, 5p each, 45p doz.

## MINIATURE WAFER SWITCHES

2 pole, 2 way—4 pole, 2 way—3 pole, 3 way—4 pole, 3 way—2 pole, 4 way—3 pole, 4 way—2 pole 6 way—1 pole, 12 way. All at 18p each, £1-80 dozen, your assortment.

SEE LAST MONTH for prices of STANDARD WAFER SWITCHES

## MICRO SWITCH

5 amp. changeover contacts, 8p each, £1 doz. 15 amp. on/off 10p each, 15 amp changeover 15p each, 10 for £1-35.

## MAINS OPERATED CONTACTOR

220/240v. 50 cycle solenoid with laminated core so very silent in operation. Closes 4 circuits each rated at 10 amps. Extremely well made by a German Electrical Company. Overall size 2 1/2" x 2" x 2 1/2". £1 each.

## FAPST MOTORS

Est. 1/40th h.p. Made for 110-120 volt working, but two of these work ideally together off our standard 240 volt mains. A really beautiful motor, extremely quiet running and reversible. £1-50 each. Postage one 23p, two 35p.



## EXTRACTOR FAN

Cleans the air at the rate of 10,000 cubic ft. per hour. Suitable for kitchens, bathrooms, factories, changing rooms, etc., it's so quiet it can hardly be heard. Compact, 5 1/2" casing with 5 1/2" fan blades. Kit comprises motor, fan blades, sheet steel casing, pull switch, mains connector, and fixing brackets, £2 plus 36p post and ins.

## MAINS TRANSISTOR POWER PACK

Designed to operate transistor sets and amplifiers. Adjustable output 8v. 9v. 12 volts for up to 500mA (class B working). Takes the place of any of the following batteries: PPI, PPS, PP4, PP6, PP7, PP9 and others. Kit comprises: mains transformer rectifier, smoothing and load resistor, condensers and instructions. Real snip at only 85p, plus 18p postage.

## COMPONENT BARGAINS

100 Eerie 1 watt resistors, 50 different values up to 1 meg. 50p.  
50 assorted capacitors, 25 different values up to 5,000 p.f. 60p.  
Both parcels £1 post paid.

## RADIO STETHOSCOPE

Easiest way to fault find—traces signal from aerial to speaker—when signal stops you've found the fault. Use it on Radio, TV, amplifier, anything—complete kit comprises two special transistors and all parts including probe tube and crystal earpiece. £2—twin stethoscope instead of earpiece 75p extra—post and ins. 20p.



## BATTERY CONDITION TESTER

Made by Mallory but suitable for all batteries made by Ever Ready and others, most of which are zinc carbon types but also mercury manganese—lead—silver oxide and alkaline batteries may be tested. The tester puts a dummy load on the battery and the meter scale indicates the condition depending upon which section the pointer rests. The section reads "replace", "weak" or "good". The tester is complete in its case, size 3 1/2" x 6 1/2" x 2 1/2" with leads and prods. Price £1-75 plus 20p postage.

## 1 HOUR MINUTE TIMER


Made by famous Smiths company, these have a large clear dial, size 4 1/2" x 3 1/2", which can be set in minutes up to 1 hour. After preset period the bell rings. Ideal for processing, a memory jogger or, by adding simple lever, would operate micro-switch £1-15.



## THIS MONTH'S SNIP
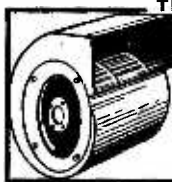
### CENTRIFUGAL FAN

Mains operated, turbo-blower type. Pressed steel Housing contains motor and aluminium impeller. Motor is 1/10th hp giving considerable air flow but virtually no noise. Approx. dimensions 10 1/2" wide by 12" dia. Outlet into trunking 10 1/2" x 4 1/2". £4-95 + £1.



## MICROSONIC KEYCHAIN RADIO

7 transistor Keychain Radio in very pretty case, size 2 1/2" x 2 1/2" x 1 1/2".—complete with soft leather zippered bag. 7 transistor, ferrite rod. Loudspeaker. In transit from the East these sets suffered corrosion as the batteries were left in them but when this corrosion is cleared away they should work—offered without guarantee except that they are new. Price only £1-25 less batteries plus 13p. post 6 for £7 post free. Pair of rechargeable batteries and charger 85p.



## 24-HOUR TIME SWITCH

Made by Smiths, these are AC mains operated, NOT CLOCKWORK. Ideal for mounting on rack or shelf or can be built into box with 13A socket. 2 completely adjustable time periods per 24 hours, 5 amp changeover contacts will switch circuit on or off during these periods. £2-50 post and ins. 23p. Additional time contacts 50p pair

## DIGITAL FREQUENCY COUNTER TIMER

as described in this and last months issues. Kit of parts including case £39-50 post paid.

## THE FULL-FI STEREO SIX

The amplifier




to blend with modern furnishings, this amplifier uses an integrated solid state circuit with an output power of 8 watts R.M.S. split over the two channels. The amplifier is ideal for use with normal pick-ups and tuners. It has a double wound mains transformer and ganged volume and tone controls—also switching for Mono to Stereo, tuner or pick-up. Other controls include "treble lift and cut", "balance" and separate mains on/off switch. UNREPEATABLE PRICE is £9 plus 33p post and insurance.

## DISTRIBUTION PANELS

Just what you need for work bench or lab. 4 x 13 amp sockets in metal box to take standard 13 amp fused plugs and on/off switch with neon warning light. Supplied complete with 7 feet of heavy cable. Wired up ready to work, £2 less plus 35p with fitted 13 amp plug; £2-40 with fitted 15 amp plug, plus 23p P. & I.
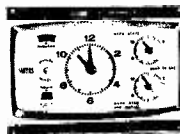
## ELECTRIC CLOCK WITH 20 AMP SWITCH


Made by Smith's these units are as fitted to many top quality cookers to control the oven. The clock is mains driven and frequency controlled so it is extremely accurate. The two small dials enable switch on and off times to be accurately set—also on the left is another time or alarm—this may be set in minutes up to 1 hour. At the end of the period a bell will sound. Offered at only a fraction of the regular price—£2-50, less than the value of the clock alone—post and ins. 15p.



## CAPACITOR DISCHARGE CAR IGNITION
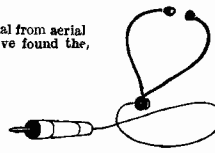
### ELECTRONIC IGNITION

This system which has proved to be amazingly efficient and reliable was first described in the Wireless World about a year ago. We can supply kit of parts for improved and even more efficient version (P.W. June), price £4-95. When ordering please state whether for positive or negative systems. Plus 30p post.



## FLUORESCENT CONTROL KITS

Each kit comprises seven items—Choke, 2 tube ends, starter, starter holder and 2 tube clips, with wiring instructions. Suitable for normal fluorescent tubes or the new "Grolux" tubes for fish tanks and indoor plants. Chokes are super-silent, mostly resin filled Kit A—16-20 w. £1 Kit B—30-40 w. £1 Kit C—80 w. £1-20. Kit E—60 w. £1-20. Kit F for 8ft. 125 w. tube £1-75. Kit MP1 is for 6in., 9in. and 12in. miniature tubes £1. Kit MP2 for 21in. 13 w. miniature tube £1. Postage on Kits A and B 23p for one or two kits then 23p for each two kits ordered. Kits C, D and B 23p on first kit then 18p for each kit ordered. Kit F 33p then 23p for each kit ordered. Kit MP1 15p on first kit then 15p on each two kits ordered.

## THYRISTOR LIGHT DIMMER

For any lamp up to 200 watt. Mounted on switch plate to fit in place of standard switch. Virtually no radio interference. Price £1-99 Plus 20p post and insurance.



## TREASURE TRACER

Complete Kit (except wooden batteries) to make the metal detector as described editorially in Practical Wireless August issue. £2-50 plus 20p post and insurance.



## TELESCOPIC AERIAL

for portable, car radio or transmitter. Chrome plated 5 sections, extends from 7 1/2 to 47in. Hole in bottom for 8BA screw. 38p. KNUCKLED MODEL FOR P.M. 50p.

## QUICK CUPPA

Mini Immersion Heater, 350w. 200/240v. Boils full cup in about two minutes. Use any socket or lamp holder. Have at bedside for tea, baby's food, etc. £1-25, post and insurance 14p. 13v. car model also available same price. Jug heater £1-50 plus p. & p. 14p.



## SLAVE FLASH UNIT

as described in last months P.W. Kit with case £1 + p. & p. 20p.



## 12 VOLT 1 1/2 AMP POWER PACK

This comprises double-wound 230/240V mains transformer with full wave rectifier and 2000 mfd/50 smoothing. Price £1-50 + p. & p. 20p.

## REED SWITCHES

Glass encased, switches operated by external magnet—gold welded contacts. We can now offer 3 types: Miniature. 1in. long x approximately 1/4in. diameter. Will make and break up to 1A up to 300 volts. Price 13p each. £1-20 dozen. Standard. 2in long x 3/16in. diameter. This will break currents of up to 1A, voltages up to 250 volts. Price 10p each, 80p per dozen. Flat. Flat type, 2in. long, just over 1/16in. thick, approximately 1in. wide. The Standard Type flattened out, so that it can be fitted into a smaller space or a larger quantity may be packed into a square solenoid. Rating 1 amp 200 volts. Price 30p each. £3 per dozen. Small ceramic magnets to operate these reed switches 5p each, 50p per dozen.

## METER BOX

Designed to take 3 1/2" flush mounting meter. This has a 2 1/2" diameter hole with 3 meter fixing holes. Overall size of box 4" x 4" x 2 1/2" deep, hinged to a metal base 2 1/2" x 4 1/2" x 3" deep. Price 50p.

## PILOT BULBS

6-4 Volts 15 amp tubular MES British made good quality. 1 dozen in a box. 25p per box.

A New Service to Readers. A bulletin bringing news of new lines, special snips and "too few to advertise" lines will be posted to subscribers during first week of each month. The bulletin will be called "Advance Advert News" and the subscription is 60p per year. Subscribers will also receive our completed 1971 catalogue when this is published.

# J. BULL (ELECTRICAL) LTD.

Dept. P.W. 7, Park Street, Croydon CRO 1YD



# GENERAL PURPOSE

## power supply

M. WALLIS

IN the "good old days" of valves, power supplies were simple. Some 90 per cent of equipment operated with an h.t. supply of about 300V and the heaters were nearly all 6.3V. A single power supply would operate the vast majority of equipment that one was experimenting with. Today the semiconductor rules the day and power supplies are very much less standardised. Checking through a recent copy of *Practical Wireless* showed that there were six circuits given—and five different supply voltages were specified, ranging from 6V to 30V. Batteries can cope with a number of these, especially the most common 9V supply, but even the most half-hearted experimenter needs quite a range of batteries to pursue his hobby—even for quick lash-ups.

One can of course build a sophisticated, stabilised power supply with variable output covering quite a large range but such circuits are expensive, are by no means simple in their construction and most of the time the sophistication is not required.

By incorporating a simple two-pole, six-way rotary switch into the circuit of a standard power supply, it is possible to build a power unit with six different outputs—all with low internal impedance—and which will simulate exactly the supply that you finally build into the equipment.

A few refinements can be incorporated into such a power supply such as an indicator neon and fuse protected output which are not always necessary on the final supply which is fitted permanently but which make life simpler (and cheaper!) while experimenting.

### the circuit

The wide proliferation of supply voltages needed for semiconductor designs has brought about the introduction of mains transformers with a wide range of secondary windings and it is simply by selecting the appropriate ones of these that various output voltages can be obtained.

The transformer specified in the components list is a good one to use but other types with multiple secondaries can be adopted.

This one is fitted with 12, 15, 20, 24 and 30V windings (these of course refer to a.c. r.m.s. volts)

TABLE 1

| VOLTS (d.c.) | VOLTS (a.c.) | Connections from which derived |
|--------------|--------------|--------------------------------|
| 4.5          | 3            | 12-15                          |
| 6            | 4            | 20-24                          |
| 7.5          | 5            | 15-20                          |
| 9            | 6            | 24-30                          |
| 12           | 8            | 12-20                          |
| 13.5         | 9            | 15-24                          |
| 15           | 10           | 20-30                          |
| 18           | 12           | 0-12 or 12-24                  |
| 22.5         | 15           | 0-15 or 15-30                  |
| 27           | 18           | 12-30                          |
| 30           | 20           | 0-20                           |
| 37.5         | 24           | 0-24                           |
| 45           | 30           | 0-30                           |

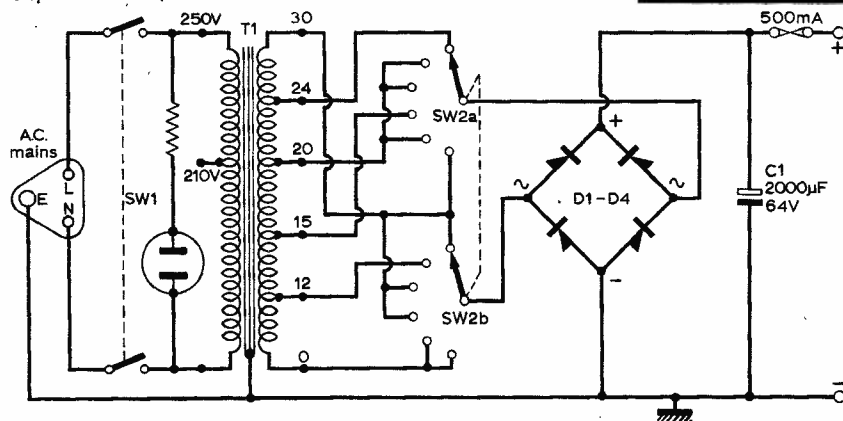


Fig. 1: The circuit of the general purpose power supply.

and a total of 13 different voltages can be selected from this as shown in the table. Those shown in the drawings, and for which the wiring is done, tend to be the higher voltages as batteries are still the best bet up to about 9V but it is a matter of personal choice which are selected.

Note that the d.c. voltages are those which should be read with no loading and are only approximate. In any case it has been found by

## ★ components list

|       |                                                                                                              |
|-------|--------------------------------------------------------------------------------------------------------------|
| T1    | Main transformer, 250V primary, 500mA<br>mains, secondary as shown, 500mA<br>Douglas Type MT112AT or similar |
| D1-D4 | Silicon Bridge Rectifier, BY164 or similar                                                                   |
| C1    | 2000 $\mu$ F 64V                                                                                             |
| SW1   | Double pole on-off switch                                                                                    |
| SW2   | 2-pole, 6-way rotary switch                                                                                  |
|       | Panel neon with built-in resistor                                                                            |
|       | 20mA line and 10mA line                                                                                      |
|       | Red and black insulated terminals                                                                            |
|       | Tap drill for switch                                                                                         |
|       | Capacitor clamps                                                                                             |
|       | Aluminium chassis, 6" x 4" x 1/2" H. L. Smith, Ltd.,<br>287 Edgware Rd., London W2                           |

experience that the secondary taps are by no means always accurate and quite large differences have been measured from the theoretical voltage but as exact voltages are rarely needed, variations are allowable.

The output voltage from the prototype, which can be seen marked on the chassis, are those measured, not those calculated, and these discrepancies can only be due to winding inaccuracies as it is wired up exactly as in Fig. 1.

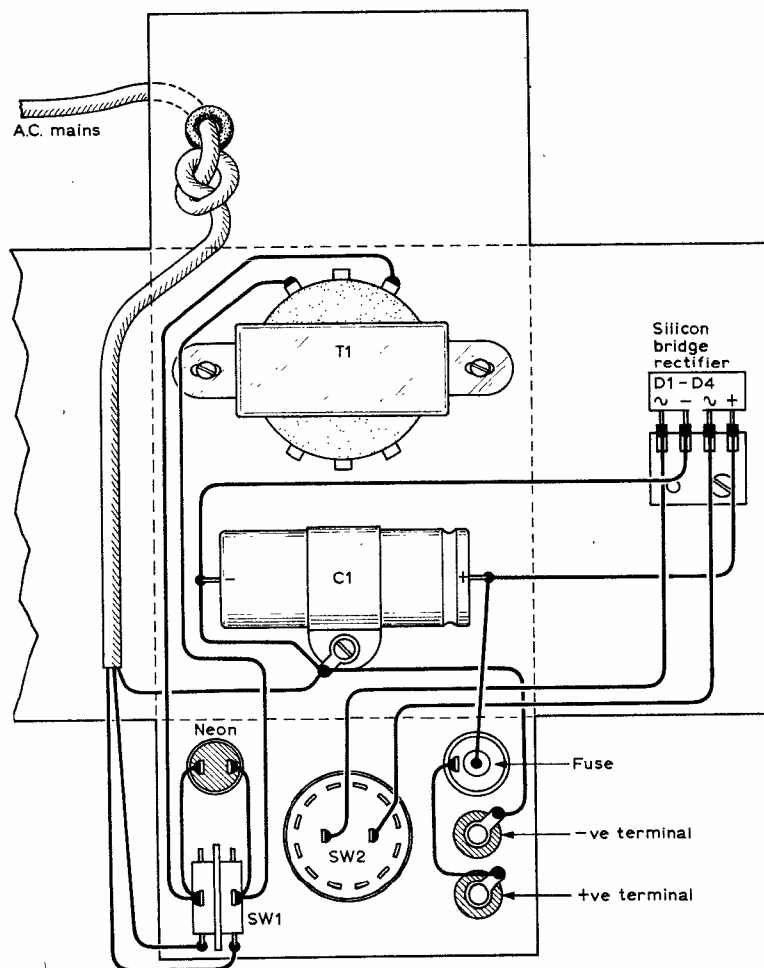


Fig. 2: The component layout and wiring details.

The current rating required from a general purpose power supply will depend on the uses to which it is put. Only power amplifiers at peaks take more than about 500mA and that was the rating chosen; it is sufficient for nearly all experimental work.

More than one company makes transformers with the voltage taps used here, but the most widely available is possibly the Douglas MT112AT. The same transformer with a 2A rating is coded MT3AT and although it will just fit into the chassis shown, it is a tight fit and a larger one is recommended.

The mains supply is connected to the correct primary (either 210V or 250V) of the transformer via a double-pole switch. A panel neon, connected

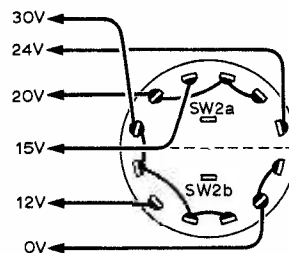


Fig. 3: The switch wiring used on the prototype.

across the primary is very useful. Today most neons are supplied with a built-in resistor but if one is not fitted, a 220k $\Omega$  should be wired in series as shown in the circuit.

The earth line is shown connected to the negative line but may equally well go to the positive if used in conjunction with PNP type equipment which is earthed by some other means. Whatever happens the aluminium chassis should be earthed for safety reasons.

The various connections to the voltage selector switch are taken from the appropriateappings and the switch wipers are connected directly to the bridge rectifier a.c. contacts. Plastic encapsulated silicon bridge rectifiers are widely available at reasonable prices and come under a variety of codings. The ratings must be 50V peak, 1A. The Mullard BY164 is suitable here.

Adequate smoothing for all purposes is provided by the 2000 $\mu$ F capacitor; the voltage rating of this should be well above the 45V or so applied and a 64V type was used in the prototype.

To provide a measure of protection, a 500mA fuse should be connected in the supply as shown.

## construction

The prototype was built in a



small aluminium chassis size 5 x 4 x 2½ inches, fitted with a drop-in lid. These chassis are available from H. L. Smith Ltd., the address is given in the components list.

The layout of the components is shown in Fig. 2 and can be seen in the photograph.

The bridge rectifier can be mounted on a small tag strip on one long side. the transformer and the


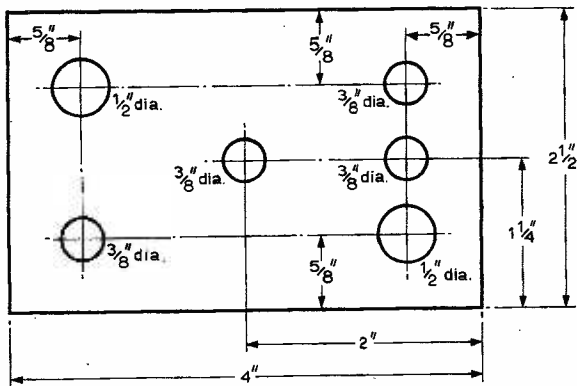


Fig. 4: The front panel drilling details.

capacitor on the base, with the remaining components on the front panel.

The switch wiring needs quite a lot of planning unless that used in the prototype is copied exactly, this is shown in Fig. 3. If other voltages, selected from the table, are required, the wiring should be planned carefully first of all. It is far easier to do the wiring on the switch leaving a few inches of wire which will finally be wired to the transformer.

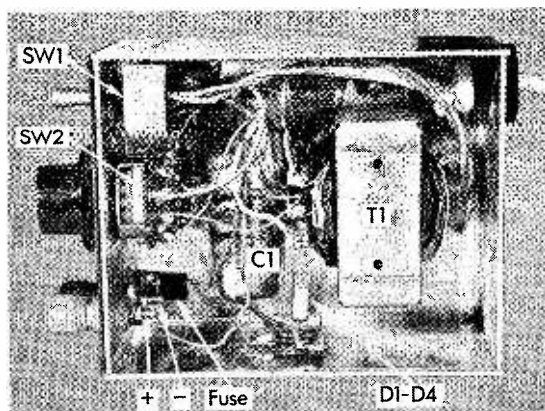When all wiring is completed a thorough check should be made to see that there is no possibility of



Internal view of the prototype showing component siting. Compare this with Fig. 2.

mains being applied to the case and that no bare wires can touch each other.

Connect a voltmeter to the terminal sockets and switch on, ensuring that a voltage reading is obtained in each switch position. Wrong wiring on a switch of this sort can lead to a direct short of the secondary and—unless noted very quickly—unpleasant things can happen to both the transformer and the switch.

There may be a very small amount of sparking while switching but this does no harm. The prototype has been in use continuously for several months with no ill effects.

There is just one point that must be made. The charge stored in a smoothing capacitor of this size lasts for a long while and if the power supply has been on a high range the capacitor should be shorted out (with the mains switch off) before being applied to a circuit where a high voltage could cause damage. This should be done through a resistor, not directly, as the fuse may blow otherwise.

If, due to the nature of the experimenting, a considerable amount of switching is envisaged, a resistor can be wired permanently between the output terminals so that a small current is drawn at all times and the capacitor will then settle down very quickly to the applied voltage. A 4.7kΩ resistor with a ½W rating will serve this purpose.

## CROSSWORD No.2

### WINNERS and SOLUTION

The Practical Wireless Crossword Competition No.2, published in the June 1971 issue, has now closed and the prizes of £10 vouchers, exchangeable with any advertiser in Practical Wireless have been awarded to:

Mr. J. Rutter  
Newcastle-upon-Tyne


Mr. D. Bell  
Silvertown, London E.16

Mr. R. W. Clarke  
Bedfont, Middx.

Mr. W. Easton  
Whitby, Yorks

Mr. M. R. Edmunds  
Southampton, Hants

## SOLUTION TO COMPETITION NO. 2

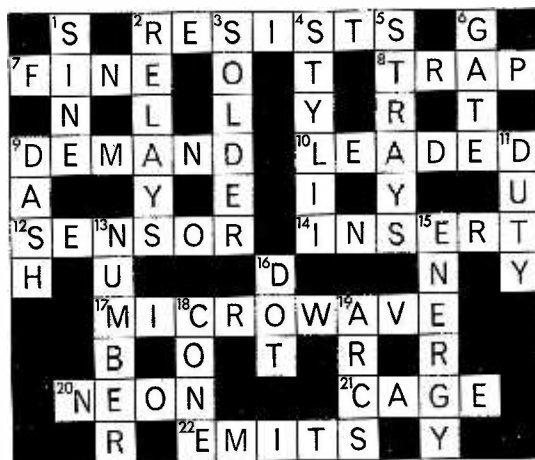

# INCREASE YOUR KNOWLEDGE



Established 1891


**MANY COURSES TO CHOOSE FROM incl.**  
 RADIO & TV ENGINEERING & SERVICING,  
 TRANSISTOR & PRINTED CIRCUIT SERVICING,  
 COLOUR TV SERVICING, ELECTRONICS,  
 NUMERICAL CONTROL ELECTRONICS,  
 TELEMTRY TECHNIQUES, CONTROL SYSTEMS,  
 ELECTRONICS FOR AUTOMATION,  
 COMPUTERS, ETC.

## ALSO EXAMINATION COURSES FOR

C. & G. Telecommunication Technicians' Certificates  
 Radio Operator Certificates  
 Radio Amateurs' Examination  
 General Certificate of Education, etc.
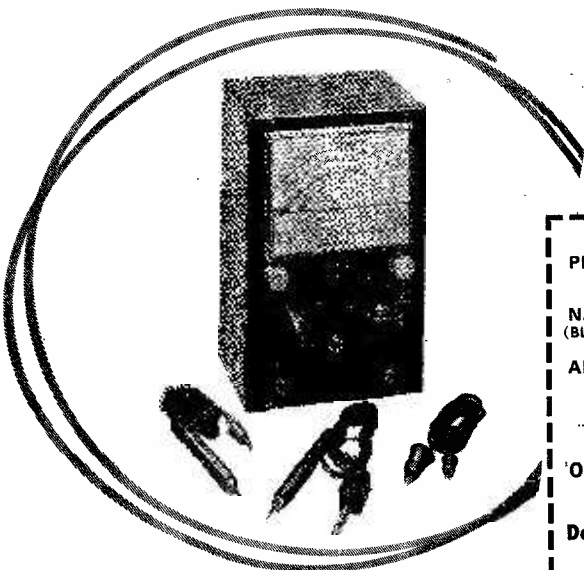
## BUILD YOUR OWN RADIO AND INSTRUMENTS

With an ICS Practical Radio & Electronics Course you gain a sound knowledge of circuits and applications as you build your own 5-valve Superhet Receiver, Transistor Portable, and high-grade test instruments (shown below). Everything simply explained. All components and tools supplied. For illustrated brochure, post coupon below.



# RADIO TELEVISION ELECTRONIC ENGINEERING

MEMBER OF THE ASSOCIATION  
OF BRITISH CORRESPONDENCE COLLEGES

## THERE IS AN ICS COURSE FOR YOU

Whether you need a basic grounding, tuition to complete your technical qualifications, or further specialized knowledge, ICS can help you with a course individually adapted to your requirements.

There is a place for you among the fully-trained men. They are the highly paid men—the men of the future. If you want to get to the top, or to succeed in your own business, put your technical training in our experienced hands.

ICS Courses are written in clear, simple and direct language, fully illustrated and specially edited to facilitate individual home study. You will learn in the comfort of your own home—at your own speed. The unique ICS teaching method embodies the teacher in the text; it combines expert practical experience with clearly explained theoretical training. Let ICS help you to develop your ambitions and ensure a successful future. Invest in your own capabilities.

## FILL IN AND POST THIS COUPON TODAY

You will receive the **FREE ICS Prospectus** listing the examination and ICS technical courses in radio, television and electronics **PLUS** details of over 150 specialized subjects.

PLEASE SEND FREE BOOK ON.....

NAME .....  
(BLOCK CAPITALS PLEASE)

ADDRESS .....

OCCUPATION..... AGE.....

INTERNATIONAL CORRESPONDENCE SCHOOLS  
 Dept. 170, INTERTEXT HOUSE, STEWARTS ROAD, London, SW8 4UJ.

10/71

# AT HOME SOLDERING ?

Our miniature irons are used all over the world in that most exacting market—the modern electronics industry, the rapidly developing technology of which has made possible the enormous growth of activities available to the technical hobbyist.

He now also requires equipment to the highest commercial standards. Like our soldering irons, for example.

Look at the ADAMIN Model 15. If there is a smaller iron for mains use, we haven't seen it. It weighs a mere  $\frac{1}{2}$  oz (less flex) and is about 7 inches long.

But it has a big performance. Used with interchangeable bits from  $\frac{3}{32}$ " to  $\frac{3}{16}$ " it is suitable for all work, from Hearing Aids to Colour Television.

Use the mains version at home or clip the 12 volt model to the car battery or 12 volt power unit (consumption only 1.25A).

Send for HOBBY PACK 10 consisting of Model 15 iron with four bits,  $\frac{3}{32}$ ",  $\frac{3}{16}$ ",  $\frac{1}{8}$ " and tube of Bit Lubricant. State voltage required—12v or 220/240v.

**PRICE: HOBBY PACK £2.30**  
p & p FREE

## LIGHT SOLDERING DEVELOPMENTS LTD.

28 Sydenham Road, Croydon, CR9 2LL  
Telephone 01-688 8589 and 4559



## JERMYN 50p BARGAIN PACKS

All fully coded, all from well-known manufacturers and now available, while stocks last, at better than bulk-buyer's prices! Cash with order only.

### THIS MONTH:

|                        |                                          |            |
|------------------------|------------------------------------------|------------|
| <b>1N4148</b> (=1N914) | Signal Diode                             | 18 for 50p |
| <b>1N5060</b> (=A14D)  | 1 Amp Rectifier 400V avalanche protected | 7 for 50p  |
| <b>2N2926</b> (Red)    | NPN Silicon Transistor hfe 55-110        | 8 for 50p  |
| <b>2N2923</b>          | NPN Silicon Transistor hfe 90-180        | 7 for 50p  |
| <b>2N2646</b>          | Versatile Unijunction                    | 3 for 100p |

Post and packing 10p for 1 or 2 packs; 3 packs or more post free.

Order any quantity, till sold (but we regret packs cannot be subdivided).



P.O. or Cheque payable Jermyn Industries, Vestry Estate, Sevenoaks, Kent.

## BAKER 12in. REGENT

An inexpensive unit for the beginner in high fidelity and for general purposes. May be used to advantage with any Radio, Amplifier or Television receiver.

Maximum Power 15 watts

Bass Resonance 45 c.p.s.

Flux Density 12,000 gauss

Voice Coil impedance 3 or 8 or 15 ohm models


Useful response 45-13,000 c.p.s.

Nett weight 5 lbs.

25 watt rating

Latest catalogue 5p with enclosure plans.

**£7**

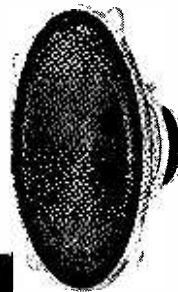

**Baker Reproducers Ltd**

Bensham Manor Road Passage, Thornton Heath, Surrey. 01-684-1665

When in LUTON, BEDS, you must visit the . . .

### SELF-SERVICE RADIO COMPONENTS SHOP

Serve yourself from a selection of 1,200 boxes of Manufacturer's surplus stocks and save money.

9 a.m. to 5.30 p.m. every day.

Closed all day Wednesday.

**SURPLECTRONICS**

216 LEAGRAVE ROAD, LUTON, BEDS



**PRACTICAL WIRELESS  
SUPPLEMENT  
OCTOBER 1971**

Choosing

# SMALL WORKSHOP TOOLS

S. YEATMAN

**S**INCE YOU ARE reading Practical Wireless the chances are that you have already tried your hand at constructing one of our projects. If you are already well fitted out with tools or have access to workshop facilities the bending up of a piece of aluminium to make a chassis or the punching and drilling of various holes would not have presented you with much of a problem. But if you are a newcomer to home electronics you have probably employed 'knife and fork' techniques, utilising kitchen knives and similar tools!

This really is doing things the hard way and the effort involved can put a considerable damper on anyone's enthusiasm for home construction, apart from any ensuing domestic problems when the lady of the kitchen discovers that her best kitchen knife now looks like a hacksaw blade!

If you are really taken with the idea of constructing electronic gear then be prepared to start off properly by buying a few good essential tools designed for the job in hand. Forget Dad's woodworking screwdriver with its  $\frac{1}{2}$ " wide blade filed so thin that it seems to fit any screw head from 8BA upwards! Very convenient, of course, but what a mess it makes of screw heads! Dad's pliers, too, are very handy—they 'fit' any size of nut you like to mention but by the time they have slipped a couple of times that nut looks pretty sorry for itself.

When you find out what fun these electronic projects can be you will begin to take pride in the finished job and Mum's knives and Dad's tools just won't be good enough. So, start off on the right foot by getting the proper tools and remember that, like most 'bargains', cheap tools can turn out to be expensive in the long run. Spend a little more on tools from manufacturers of repute and scorn imported tools made of inferior materials.

The following review lists small workshop tools more or less in the order of necessity bearing in mind the requirements of the home constructor. The soldering iron takes precedence since even the simplest bought kit of parts needs the odd soldered joint or two.

In a review of this kind only general reference can be made to the great variety and range of tools that are available today. Specific recommendations are impossible without some knowledge of the amount of money it is intended to spend and the precise nature of the work to be undertaken in the workshop.

Workshops tend to 'just grow' from a few simple tools. As the limitations of these tools become apparent so more tools are bought to fill the gaps, thus it can be seen that a large initial outlay is not necessary.

Spreading the cost over a period allows emphasis to be made here on the requirement to buy quality, a policy which, if followed, will not be regretted.



**SOLDERING IRONS.** There is a wide variety of electric soldering irons available today, the main problem being the selection of one of a suitable wattage for the home constructor of radio gear. For the average Practical Wireless project a 25 watt iron should prove satisfactory but if a lot of work is likely to be done on printed circuit boards a 15 watt iron would be more appropriate. These circuit boards often contain many small components fitted quite close together and thus vulnerable to the heat of a soldering iron. Excessive heat can also damage the copper strips of the board itself.

With these irons goes a wide range of copper bits of differing diameters, some straight and some angled. Initially a straight bit  $\frac{1}{8}$ " or  $\frac{3}{16}$ " in diameter can be chosen for general purpose work with an angled bit for the awkward spots. At a little extra cost special bits are available which contain additives to the copper designed to prolong the life of the bit.


For home use a soldering iron operating directly from the 230 volt mains supply is usual but, for anyone who might feel a little happier with a lower working voltage, irons are available to work from as low as 6 volts via a mains isolating transformer.

When wiring an electric iron to its mains plug ensure that the instructions supplied with the iron are strictly adhered to so that the iron is properly earthed. This is a very important point for the builder of electronic equipment when wiring in transistors and other solid-state devices. Irreparable damage can be caused to these devices by stray earth currents if the soldering iron is not properly earthed.

Advancing rapidly in popularity are the soldering guns or 'heat guns', as they are sometimes known. The copper bit is, in fact, part of a low voltage secondary winding of the built-in transformer. Exaggerated claims are sometimes made concerning the short heat-up time for these guns,



## Choosing SMALL WORKSHOP TOOLS

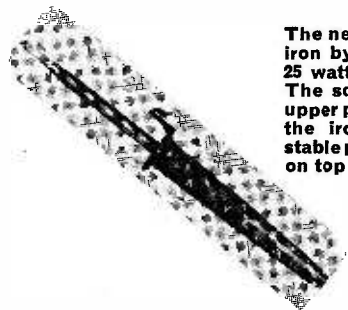


The new Invader soldering iron by Adcola is rated at 25 watts and has a  $\frac{1}{8}$ " bit. The square styling of the upper part of handle causes the iron to remain in a stable position when placed on top of the workbench.

One of the Litesold range of irons available in ratings from 10 to 60 watts, covering all requirements in



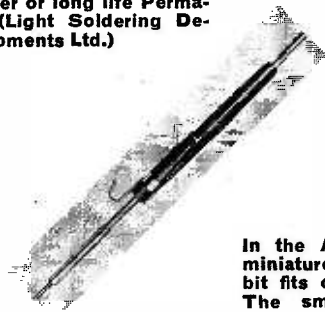electronic soldering. Various tips are obtainable in copper or long life Permatip. (Light Soldering Developments Ltd.)



In the Adamin series of miniature irons the copper bit fits over the element. The smallest, Model 6, has a rating of only 6 watts at 6 volts. (L.S.D. Ltd.)



This soldering iron bench stand guards against accidental burns or even fires. The iron maintains its normal operating temperature while in the stand. A bit cleaning pad is fixed to the front of the stand. (L.S.D. Ltd.)

typically 10 seconds, but the better known makes can be relied upon in this respect.

The trigger style on-off switch on these guns often has two positions, for fast heat-up and for running heat, thus giving a dual-heat facility. Sometimes other types of bit are available which can be used to cut sheet plastics or to weld plastic sheet and so on.

Solder today, as used on electronic work, invariably has several cores of flux to ensure better distribution of the flux around the joint and consequently a better joint. The solder contains tin and lead in varying proportions which affect the temperature at which the solder will melt. The usual ratio of tin to lead is 60/40 for radio work and the diameter of the solder can be between 18 and 22 s.w.g. depending upon the fineness of the work being done.

While short lengths of solder can be bought for a few pence the  $\frac{1}{2}$  or 1lb. reel will be found to be more economical for the home constructor. If however he wishes to experiment with various solders he will find many easy-to-use dispensers and handy-packs available with different types of solder such as 40/60 or 60/40 tin-lead alloys as well as solders containing a small amount of copper which is calculated to reduce the amount of wear on the copper soldering bit.

Although soldering irons are usually fitted with a hook of some kind so that they can be hooked onto a convenient point it is a good policy to provide some kind of metal stand for use on top of the bench. Such a stand can be easily made out of an odd piece of aluminium or tinplate.

Soldering iron manufacturers naturally produce their own stands or 'protective shields' for their irons and these are designed to ensure that the iron does not overheat when the iron is not being used but is still switched on. For convenience a cleaning pad for the bit may be incorporated and possibly a holder for a reel of solder.

A 'must' in soldering is a sharp pick or long needle for clearing out holes in soldering tags and removing surplus solder. Commercial versions are usually made of aluminium, to prevent the solder sticking to the needle, and with a plastic handle or covering. One end may be pointed and the other end split to enable wires to be unravelled from tags etc., while the solder is molten.

Another de-soldering aid available is in the form of copper wire braid. When the end of the braid is touched on a hot soldered joint surplus solder travels up the braid by capillary action. The end of the braid is snipped off ready for the next joint.



**PLIERS AND CUTTERS.** Again a very large field of choice and again the rejoinder to pay a bit extra to get quality. Two pairs of pliers will suffice for most constructional work, a long-nosed pair with tapered jaws coming to a reasonable fine point and a heavier pair with stocky jaws, maybe  $\frac{1}{2}$ " wide, and probably incorporating a pair of sidecutters.

The long-nosed pliers will always be in the hand of the electronics constructor, for twisting wires round tags and forming the wire ends of components before soldering them into position. Don't forget that a wiring joint should always be mechanically sound before it is finally soldered, although the true experimenter will not go along with this principle because he will want to use the same components time and again!

Variations on the pliers theme include those with angled



jaws of various lengths, round jaws and flat narrow jaws rather than pointed ones. When buying pliers see that the opening and closing action is not too loose or the jaw tips will not close together properly and it will be difficult to get hold of fine wires when wiring up.

Wirecutters will be used as often as the pliers so, again, only the best must be chosen. They should be about the same size as the long-nosed pliers with the cutting edges at an angle to the body. Other types have the cutting edges across the top or parallel with the body.

When buying sidecutters hold them up to the light and see that the cutting edges come together cleanly and evenly throughout their length. Try this test with a cheap imported pair of cutters and see the difference! The previous remarks concerning the action of pliers applies just as much to sidecutters. A loose action and the cutting action will be greatly impaired. On the other hand, there is nothing more annoying than a pair of cutters or pliers that need two hands to open them!

**WIRESTRIPPERS.** Different people have different ways of stripping the insulation from wire, varying from the use of the front teeth to an old kitchen knife! If the wire is nicked, and it often is, it will eventually break if it is subject to vibration or flexing. The ordinary sidecutters are frequently pressed into service as wirestrippers mainly because they will have just been used to cut off a piece of wire and are still in the hand! However there are plenty of wirestrippers on the market designed for the job so there is no excuse for improvisation.

Wirestrippers usually have some means of adjustment to cater for different size wires. It is important not to try to strip wires of a larger gauge than that for which the wirestripper has been set, or the wire will be nicked. One of the latest style wirestrippers on the market has a four position cam that can be adjusted immediately to another gauge of wire, while still held in the hand. Incidentally, this model also has wire cutters which have ground edges, a great improvement.

A feature on some types of wirestrippers, which the author considers of great importance, is the provision of a spring that keeps the cutters normally open, the cutting action taking place against the spring.

**SCREWDRIVERS.** Strictly speaking, every different sized screw needs its own screwdriver, if the blade is to fit the screw slot properly, but not many of us are likely to go to that extreme. The width of the blade should be about the diameter of the screw head or wider, rather than narrower. For electronic construction work it is best to buy a set of screwdrivers with blade widths from about  $\frac{1}{8}$ " up to  $\frac{1}{2}$ " or  $\frac{5}{16}$ ". Three screwdrivers should be sufficient. A useful addition is one for the Philips style screws, that is the screws with crossed slots.

Screwdriver sets are available consisting of several blades that can be fitted to a common handle. Although these may be cheaper than individual screwdrivers they are less convenient in practice.

The screwdriver blade itself should be about 6" or so long depending upon the blade width. One very useful size of blade is one about  $\frac{3}{32}$ " wide for use with knob setscrews. The blade should be as long as possible so as to reach a knob in spite of the clutter of other knobs, dials etc. on a panel.


Don't take any notice of the markings on some screwdrivers that seem to indicate that one can use them with safety on 10000 volt circuits! Anyone having that sort of voltage around should know the precautions he should take. They would not include the use of a screwdriver on 10000 volts!

Variations on the basic screwdriver include the ratchet


A most useful de-soldering aid is a reel of specially treated copper braid which will completely remove unwanted solder from a joint by capillary action.



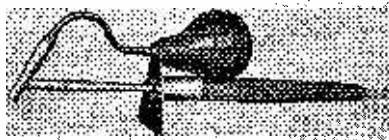The Adcola protective shield is intended for wall or bench mounting and has slots for a spindle carrying a reel of solder.



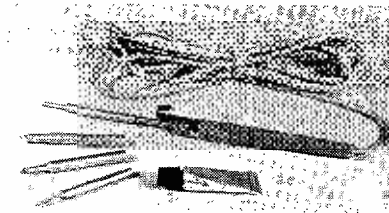
This de-soldering tool (L.S.D. Ltd.) could be invaluable when stripping components from surplus equipment. It is self-contained and simple to operate and may be used as a conventional soldering iron.




The Adamin miniature iron, Model 15, can be obtained complete with a set of four bits of differing size. The tube of special lubricant is used to prevent the bits from sticking to the heating element.




## SMALL WORKSHOP TOOLS

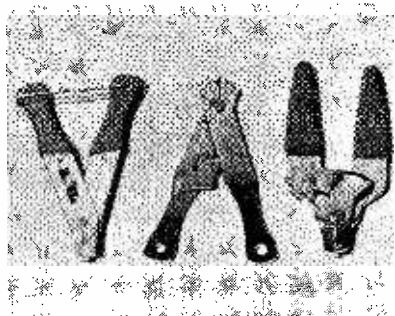

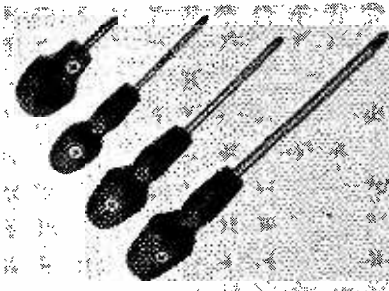Three of the Bib range of wirecutter, strippers by Multicore Solders Ltd. The latest, centre, is the Model 3A with an instantly adjustable cam enabling the strippers to deal with most wire sizes. The cutters have ground cutting edges. The ends of the arms are, in fact, flat spanners for 4 and 6BA nuts, a most unusual feature.



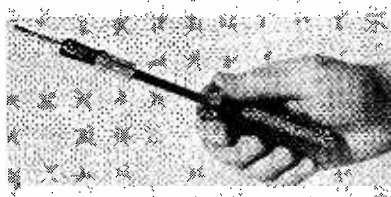A set of Stanley 'Pozidrive' screwdrivers enabling Philips type screws to be reached in the most awkward corners.



The Stanley range of 'Spee-D-Grip' screwdrivers incorporating a spring clip which holds screws in position for starting in inaccessible places.

types which remove the necessity of continually lifting the screwdriver from a screwhead thus, incidentally, reducing the risk of the blade slipping and doing damage. Of course, if one used a screwdriver properly, the blade should never leave the slot, but this seldom happens!

A most valuable addition to a set of screwdrivers is one having a spring attachment at the tip of the blade to firmly hold a screw while it is being inserted into place. Its value in awkward spots is inestimable. Such an attachment can sometimes be bought separately for use on almost any screwdriver.

**SPANNERS.** There is always a temptation to use a pair of pliers on any nut that needs tightening, usually because the pliers are ready to hand. It should be remembered that the opposite faces of a nut are parallel to each other where-as the jaws of a pair of pliers are only parallel when they are closed. That's why the pliers always slip off the nut and cause damage.

First of all, get a set of box spanners covering 0 to 8BA either single or double ended. The single ended ones with a wooden or plastic handle are recommended. Just two, for 4 and 6BA, are worth their weight in gold in a workshop. Having long stems they are invaluable for placing nuts into odd corners where fingers or pliers cannot reach.

It is always good practice, wherever possible, to tighten a nut on to a screw rather than use a screwdriver on the screwhead. This is particularly important where the screwhead is visible such as on the front panel of a piece of equipment where a damaged slot on a screw would be an eyesore.

Another requirement in the spanner line is a set of flat spanners, again covering the BA sizes, possibly 0 to 8BA. These can very well be double ended ones since the length of the spanners is not of much importance.

Some sets are single ended but bolted together at one end so that one can be selected and the others swung out of the way, rather like a set of feeler gauges.



**DRILLS.** In the past a hand drill would have been a first acquisition in a workshop, followed by an electric drill when the money was available. Today the cost of electric drills is such as to justify buying one from the outset.

The simple electric drill will have a single speed and accommodate drills up to  $\frac{1}{2}$ " in diameter, ('twist drill' is really the proper name for the bit that does the cutting). This model will perform just about all the routine drilling jobs in a workshop where electronic projects predominate. A chuck adaptor to take drills up to  $\frac{3}{8}$ " in diameter is highly desirable, enabling the usual holes for mounting potentiometers etc. to be drilled without having to resort to files or reamers.

If the drill is likely to be used for other duties around the house then the two speed drill with a chuck taking drills up to  $\frac{1}{2}$ " in diameter can be considered. A popular accessory for the electric drill is the speed controller which is an electronic device enabling the speed to be varied continuously from a few r.p.m. to maximum speed. Such controllers are available in kit form or ready assembled.

If a lot of drilling is anticipated, particularly on chassis work, a drill stand will prove a boon. Most electric drill manufacturers have such stands but their design is such that they will accommodate most makes of drill. Such

stands ensure that holes are drilled vertically, which may not be very important on sheet metal work but could be critical with a deep hole. Holes will be more accurate both in size and positioning when drilled on a stand rather than with a hand held electric drill.

When using drill adaptors enabling, say, a  $\frac{3}{8}$ " drill to be used in a chuck of nominal  $\frac{1}{4}$ " capacity, remember not to overload the motor by exerting excessive pressure on the drill especially in hard materials.

Hand operated drills suitable for the small workshop range from the simplest single speed ones with a  $\frac{1}{4}$ " capacity to those taking drills up to  $\frac{1}{2}$ " and having an integral gearbox providing either a low speed or a high speed at the chuck. A little extra spent on a good hand drill will be a worthwhile investment. In particular the gears will run more smoothly and require less energy and the chuck will be of a better quality.

Now, what about the twist drills themselves? These are bought singly, as required, or, if starting more or less from scratch, then in a set complete with a stand for use on top of the bench. They may be had in sizes from about  $\frac{1}{32}$ " to  $\frac{1}{2}$ " in diameter or in a numbered range from No. 80 (0.0135") to No. 1 (0.228"). Letter drills carry the range on upwards from 'A' (0.234") to 'Z' (0.413").

For many years the author has had just four drills always to hand, No's 12, 24, 32 and 43. These will cover the drilling of holes for tapping or clearing for 2, 4 and 6BA screws.

As far as the quality of twist drills is concerned, it is necessary to take a little more care over their selection than with other tools since there are a lot of drills on the market that seem to be made of little more than soft iron! So once again beware of cheap imitations and if the pocket will stand it, buy a small set of genuine high speed drills. These will last for ever and seldom need sharpening if not abused.

**PUNCHES.** Whenever it is required to drill a hole in a chassis, or anywhere else for that matter, it is essential to use a centre punch to mark the spot where the hole is required. Otherwise it is almost certain that the drill will wander off the spot, scratching or damaging the surface being drilled. This particularly applies to hard surfaces and when using a hand held electric drill especially if care is not taken to keep the drill vertical.

There's not much to say about centre punches. A good one will be of tempered steel with a sharp round point, usually machine ground. Spring loaded punches are available which obviate the need for a hammer, so these punches are very convenient and the extra cost well justified.

Chassis punches are a necessity although the number bought for a small workshop will probably depend upon the funds available. These punches will cut holes ranging from  $\frac{3}{8}$ " to 3" in diameter but it is recommended that at least two be obtained,  $\frac{3}{8}$ " diameter for B7G valveholders and  $\frac{1}{2}$ " diameter for B9A valveholders. These punches require a suitable Allen key to operate them and their cutting limit is about 16 s.w.g. mild steel. They will cut through the usual 16 s.w.g. aluminium sheet like the proverbial knife through butter, thus saving a great deal of time and energy.

A useful tip... the resulting hole will have a burr on one side so place the cutting part of the punch on the side of the panel or chassis that might be of some importance from the point of view of appearance.

Other chassis cutters are available that will cut square or rectangular shaped holes but the infrequent need for such cutters does not justify their purchase.


The predecessor of the chassis cutter was the tank cutter. This had an adjustable cutting bar for different diameters of hole, but unless used in a lathe or drill press,




This bench clamp enables a portable electric drill to be used with grinding, polishing or other attachments (Wolf). The drill is a Wolf Sapphire 73.



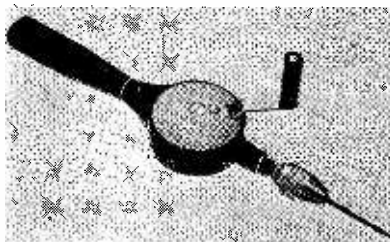
For precision drilling a bench drill stand is essential. The spring loaded press magnifies the hand pressure some ten times. (Wolf)



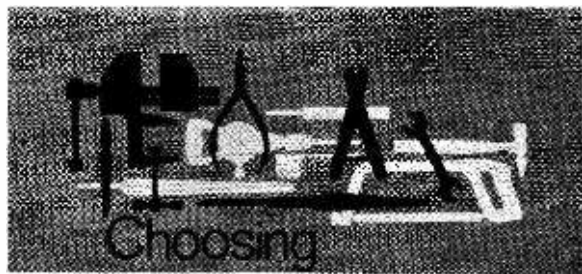The old-fashioned hand drill now has a streamlined appearance. In this Stanley drill the gears are completely enclosed protecting them from dirt, swarf etc. and obviating nipped fingers!




## Choosing SMALL WORKSHOP TOOLS

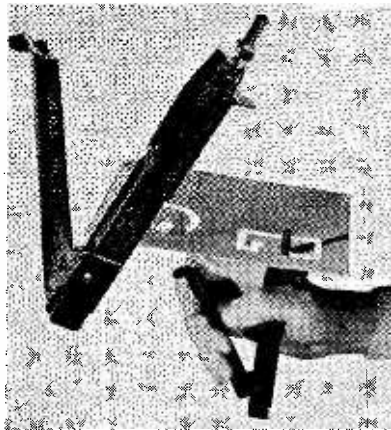

Requiring only a  $\frac{1}{8}$ " hole to begin operations this Adel nibbling tool will cut a hole of any shape or size in sheet steel up to 18 gauge steel or aluminium up to 16 gauge. (West Hyde Developments Ltd.) The punch and die action cuts without distorting the metal.



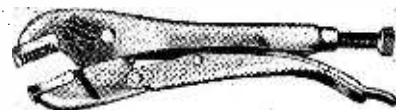This precision made Mole 'Supercut' tool has a powerful action capable of cutting long straight lengths, curves or angles in sheet materials such as steel, aluminium, plastic laminates etc. A replacement blade can be fitted very easily.



The standard Mole wrench has many uses in the small workshop. In spite of its immense gripping power it can be opened at a touch on the release lever.

the resulting hole could be a little rough in appearance. A slow cutting speed was essential and for this a carpenter's brace was ideal.

Other hand tools for cutting holes in sheet metal include the family of 'nibblers'. A small hole is first drilled in the sheet metal, the nibbler inserted and the action of the tool nibbles the material away to form a hole of almost any shape desired. The hole can be finished off with the usual files.

Shears, or tinsnips, will be needed for cutting sheet metal and a 10" pair with straight jaws should suffice for general work. The will make a straight cut in sheet metal for a limited distance although the 'goosebill' type will usually prove better for this work.

**TAPS.** Now and again the necessity will arise to tap a thread in a hole and for this two taps for each size thread are required, together with a tap wrench. The first tap is tapered, to start the thread, and the second tap is full size. Sometimes a third tap of intermediate taper is used but this is not really required for small threads.

The tap sizes most likely to be required are the usual 2, 4 and 6BA. Taps can be broken off relatively easily and for this reason a proper tap wrench is strongly recommended.

The simplest and probably the best tap wrench is the bar type with a screw grip on to the tap. The chuck model is more expensive but it does enable the tap to reach positions that would be inaccessible with the bar type wrench.



**FILES.** For finishing off the edges of metalwork and suchlike a 10" flat file will be quite adequate. That known as 'second cut' will prove best being neither too coarse nor too fine for work on soft metals. A similar sized half round file is very useful for finishing off large holes such as those required for meters. While smaller holes, for valveholders etc., can be cut with chassis punches the cost of similar punches for large meter holes tends to be prohibitive, especially as they are used relatively infrequently. Such large holes can be made by drilling a circle of small holes, then knocking out the disc of metal and finishing the work with a half round file.

A  $\frac{1}{4}$ " round file completes the essential complement of files. This will find most use in enlarging small holes in the absence of a reamer or for 'drifting' holes that are not quite where they ought to be! Perhaps the spot was not properly spotted with a centre punch before drilling!

With the advent into common use of slide switches on electronic equipment the need has arisen for a couple of small needle files, one round and the other square, for finishing off the rectangular holes required in panels for these switches. If a set of needle files can be managed then so much the better as these sets contain files of circular, triangular and flat sections as well as those already recommended.

When buying files get suitable wooden handles for them at the same time. Don't try to use a file without a handle or there will be a grave risk of the tang of the file entering the wrist if the file should jam or stick in the work.

**HAMMERS.** As far as hammers are concerned the small workshop should have one with a plastic or rubber head for bending sheet metal, without causing undue marking of the metal. A second hammer should be a light

one of the 'ball-pein' variety for general work around the place. A good make is advisable to ensure that the hammer-head is properly attached to the shaft as a hammerhead in orbit around the workshop is not funny!

**REAMERS.** During the construction of a piece of electronic equipment one always seems to need to drill a hole that is between the sizes of the drills available. In such a case a tapered reamer can be invaluable, as an alternative to filing out the hole with a round file, a process that does not endear one to one's family, if they are within earshot!

A pair of reamers can deal with holes between  $\frac{1}{8}$ " and 1" in diameter producing a clean circular hole with little or no burr. They are usually intended for use in a hand brace but can on occasion be held in the hand.

**VICES.** If a bench or table is permanently available for constructional work then a vice of some sort will prove to be a great boon especially when fabricating metal work. While smaller sizes are obtainable, an engineer's vice with 4" wide jaws should be the smallest size to be considered. Such a vice is extremely rugged and will take a lot of punishment, including using it as an anvil!

Since the vice jaws are made of hardened steel, and serrated at that, it is essential to make up a pair of soft jaws to protect work held in the vice. These jaws can be made from pieces of aluminium or other soft metal. Other vices have clip-on jaws which are plain, serrated or slotted to hold tubing or round material more securely. Another model of vice has a separate mounting plate that can be attached to almost any flat surface by means of a suction pad.

A carpenter's vice with 6" or 8" jaws is even better for sheet metal work since the jaws can be opened to a far greater extent than those of an engineer's vice. However the space needed to permanently mount a carpenter's vice, especially below and behind the vice, is considerably more than that needed for an engineer's vice. However, there are some portable vices on the market that seem to combine the best points of both types.


Although one may possess a bench vice there is always a need for a portable clamping or holding device and this is where the wrench comes in very handy.

The modern version of the wrench has an easily operated lever that allows the wrench to be locked on to the work and just as easily released. A clamp to hold the wrench is also available, which can be fitted to a table or bench top with a single clamping screw, thus providing a fixed vice if necessary. The jaw opening of the wrench can be adjusted over a wide range by a single screw fitting.


**RULES.** For marking out on sheet metal a rule and a square (trysquare) will be required, if an accurate job is to be done. A 12" rule is good enough and although it would seem that choosing such a simple tool would be no problem, the choice is, in fact, very wide indeed, ranging from rather inaccurate wooden rules, with printed graduations, to engraved steel ones.

Although a 6" square can be bought separately it really pays to buy a combination square since this incorporates a rule and square, usually of reasonable quality.

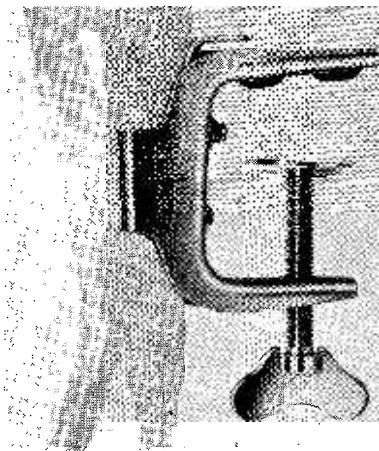**HACKSAWS.** The hacksaw will come in for quite a bit of use in the small workshop, mainly for cutting sheet metal to size before forming into a chassis. Some of the cheaper hacksaw frames will be found to twist when the blade is tightened up, so a good quality frame will be a sound buy. The adjusting nuts, too, can be difficult to turn owing to poorly formed threads.



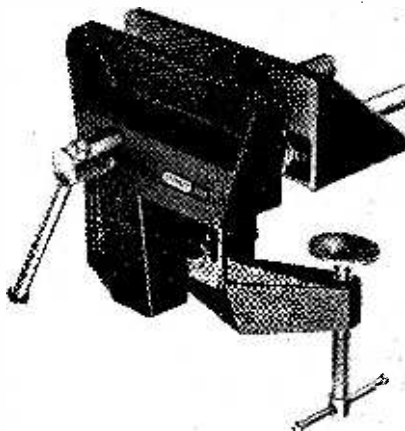The versatility of the Mole wrench can be greatly increased by the use of this table or bench clamp, converting the wrench into a portable vice.




This Stanley aluminium portable vice has 5" jaws and can be clamped to any convenient surface. It is eminently suitable for bending sheet metal into chassis etc.




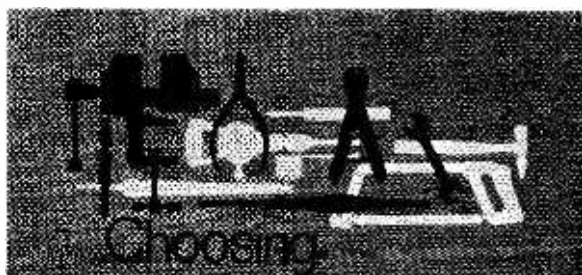The Mini-Mole is just 5" long and very useful for getting into those tight corners, inaccessible to its 'big brother'. The curved jaws provide maximum contact with round or irregular shapes.






## SMALL WORKSHOP TOOLS

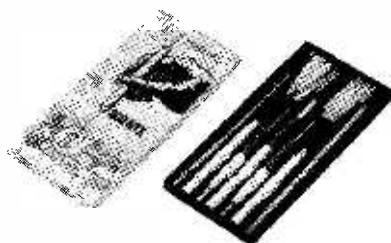

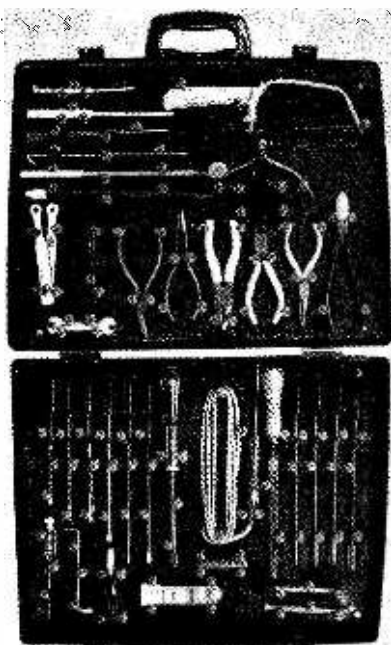This set of Philips trimming tools and adaptors will cover every conceivable requirement when aligning electronic equipment. The compact packaging makes the set particularly useful to the service engineer. (Combined Electronic Services Ltd.)



If you don't feel like tramping around the tool shops to gather together your collection of small workshop tools then this very comprehensive tool kit may be the answer. It has a wide variety of spanners, screwdrivers, pliers, cutters, a soldering iron and solder, and even an angled mirror for viewing components tucked away in tight corners. (C.E.S Ltd.)

A frame to take 10" or 12" blades is big enough and the blades themselves can be of the low tungsten flexible type. These will deal with general cutting of mild steel, brass and aluminium etc. and absorb a lot of misuse without breaking. For maximum performance high speed flexible blades are to be preferred although they are a little more expensive.

For maximum efficiency the size of the teeth on the blade must be related to the material being cut. For soft metals, such as aluminium, a coarse blade is desirable to prevent the teeth from clogging, but on harder metals such as brass or on thin sheet metal a finer toothed blade is required. The number of teeth per inch of blade normally runs from 14 to 32 for hand held saws.

A very useful addition to the standard hacksaw is the 'junior' or bow-frame saw in which the blade is held under tension by the bow. The standard blade is 6" long with fine teeth. This saw is very handy for the smaller, finer jobs where the standard hacksaw would prove clumsy. In the electronic workshop the bow saw will be used a great deal for shortening the spindles of potentiometers, capacitors etc. Remember to hold the unwanted end of the spindle in the vice while cutting, rather than the component itself.

**TRIMMING TOOLS.** Although perhaps it is wandering into the realms of servicing it is not inappropriate in this review to mention trimming tools for electronic equipment. After all, having built a lovely radio set in our nice new workshop, it won't be of much use unless the tools to align it are to hand.

These trimming tools can be bought individually, as needed, but preferably they ought to be obtained as a kit. This will prevent the use of ordinary screwdrivers for adjusting iron cores which can only cause damage in the long run.

A kit may consist of one basic tool holder with several types of trimming tool that can be fitted into the holder or, in the more expensive kits, a complete trimmer for each purpose, such as adjusting iron cores, capacitors and special types of capacitors, such as the Philips pre-set beehive capacitors, which are met with quite frequently.


In conclusion it should be pointed out that for every basic tool mentioned in this review there are a dozen or more variations on the market. Like women, there are short ones, tall ones, thin ones and fat ones! Each one to his own fancy! The average D.I.Y. or tool shop is sated with gadgets that promise to relieve us of the tedium and work required to do a particular job. Few succeed, and those that do probably take twice as long to set up to do the job as one would take using basic tools alone.

It's surprising how often one resorts to basic methods and tools in the workshop. If funds are limited then put them to good use by buying only the best in tools from reliable manufacturers. If their names happen to be a household words they would not have reached those dizzy heights by selling rubbish.



## SMALL WORKSHOP TOOLS

## PHILIPS PORTABLE PLAYER CABINET

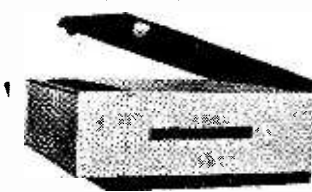

Size 18 x 16 1/2 x 7 1/2 in. Cut for B.S.R. VAI2/14/15/16/25 deck. Amplifier space 14 x 5 x 3 1/2 in. Aluminium front grille. Really smart appearance. £4 Post 25p

## BSR C.109 SUPERSLIM STEREO AND MONO CHANGER

Plays 12", 10" or 7" records. Auto or Manual. A high quality unit backed by BSR reliability with 18 months' guarantee. AC 200/250V. Size 18 1/2 x 11 1/2 in. Above motor board 3 1/2 in. below motor board 2 1/2 in. with STEREO and MONO XTAL £7.75 Post 25p



GARRARD PLAYERS with Sonotone 9TA Cartridges. Stereo Diamond and Mono Sapphire. SP25 MK II £16 Model 3500 Stereo and Mono Autochanger £14. Post 25p

RECORD PLAYER PORTABLE CABINET. Space for amplifier and autochanger. Post 25p

800 DE-LUXE 8 WATT AMPLIFIER. Ready made with 2-stage triode pentode valve, 8 watts output. Tone and volume controls. Isolated mains transformer, knobs, loudspeaker valves ECL82, E280. Response 50-12,000 cps. Sensitivity 200mV. Post 25p. £4

RSO 2 WATT AMPLIFIER with loudspeaker and valves UCL82 and UY85 Post 25p £3

R.C.S. TEAKWOOD BASE. Ready out for mounting (State player make and model) £2.75

R.C.S. PLASTIC COVERS FOR ABOVE BASE £2.75

EMI PICK-UP ARM with mono xtal and stylus £1.25

HI-FI PICK-UP CARTRIDGES. Diamond Stereo/Mono. 9TA £2.90; GP94 £2.75; GP98 £2.25; Mono GP91 £1.50; GC8 £1.25; AC09 L.P. only 50p. All standard fixing complete with stylus.

PHILIPS TRANSISTOR FM STEREO MULTIPLEX DECODER

As used in LEAK Troughline Tuner. Brand New. Pre-aligned with 9 semi conductors. 24V. D.C. at 62mA. Post Complete with circuit and connections 3 1/2 x 2 1/2 in. £4 Post Free

WEYRAD P50-1 TRANSISTOR COILS

RA2W Ferrite Aerial 65p  
Osc. P50/1A0 30p  
I.F. P50/200 470 k.c./s. 30p  
3rd I.F. P50/300 30p  
P51/1 or P51/2 30p  
P50/3V 30p  
Mullard Ferrite Rod 8 x 1 1/2 in. 20p. 6 x 1/2 in. 25p

VOLUME CONTROLS

Long spindles. Midsize Size 5 k. Ohms to 2 Meg. LOG or LIN. L/S 15p. D.P. 25p. STEREO L/S 55p. D.P. 75p. Edge 5K. S.P. Transistor 25p

WIRE-10Q TO 30 K. 25p

VEROBOARD 0-15 MATRIX

2 1/2 x 5 in. 19p. 2 1/2 x 3 1/2 in. 19p. 3 1/2 x 5 in. 20p. EDGE CONNECTORS 16 way 25p; 24 way 35p. PINS 36 per packet 17p. FACE CUTTERS 35p. S.R.B.P. Board 0-15 MATRIX 2 1/2 in. wide 3p per lin. 3 1/2 in. wide 4p per lin.; 5 in. side 5p per lin. (up to 17 in.). S.R.B.P. undrilled 1/2 in. Board 10 x 5 in. 15p.

BLANK ALUMINIUM CHASSIS. 18 s.w.g. 2 1/2 in. sides. 6 x 4 in. 45p; 8 x 6 in. 50p; 10 x 7 in. 70p; 14 x 9 in. 90p; 16 x 9 in. 90p; 12 x 3 in. 50p.

ALUMINIUM PANELS 18 s.w.g. 6 x 4 in. 8p; 8 x 6 in. 15p; 10 x 7 in. 17p; 12 x 9 in. 28p; 14 x 9 in. 27p; 12 x 12 in. 32p.

1 1/2 inch DIAMETER WAVE-CHANGE SWITCHES 25p. 2p, 2-way, or 3p. 6-way or 3p. 4-way 25p each. 1 p. 12-way, or 4 p. 2-way, or 4 p. 3-way 25p.

1 inch DIAMETER Wavechange "MAKITS" 1 p. 12-way, 2p. 6-way, 3p. 4-way, 4 p. 3-way, 3p. 2-way, 1 water 60p, 2 water 30p. Extra wafers up to six 30p each.

TOGGLE SWITCHES. 1/4 in. 14p; 1/2 in. 18p; 3/4 in. 24p.

ALL PURPOSE HEADPHONES

H.R. HEADPHONES 2000 Ohms Super Sensitive 21.75  
LOW RESISTANCE HEADPHONES 8-5 Ohms 28.00  
DE LUXE STEREO HEADPHONES 8 Ohms 25.25

"THE INSTANT" BULK TAPE ERASER AND RECORDING HEAD DEMAGNETISER 200/250 v. A.C. Leaflet S.A.E. £2.35 Post 15p

Minimum Post and Packing 15p

RETURN OF POST DESPATCH.

HI-FI STOCKISTS.

CUSTOMERS FREE CAR PARK.

CALLERS WELCOME

337 WHITEHORSE ROAD, CROYDON

Open 9-6 p.m. (Wednesdays 9-1 p.m., Saturdays 9-5 p.m.)

Buses 133, 68 pass door. S.R. Stn. Selhurst. Tel. 01-684-1665

List 5p. Written guarantee with every purchase. (Export: Remit cash and extra postage.)

505

## GENERAL PURPOSE TRANSISTOR PRE-AMPLIFIER BRITISH MADE

For Mike, Tape, P.U., Guitar, etc. Battery 9-12v or H.T. line 200-300V D.C. operation. Size 1 1/2 x 1 1/2 x 1 1/2. Response 25 cps. to 25 Kc/s. 20db gain. For use with valve or transistor equipment. Full instructions supplied. Brand new. Guaranteed. Details S.A.E. 90p Post 10p

## NEW TUBULAR ELECTROLYTICS

2/350V 14p 100/35V 10p 1-16/100V 55p  
4/350V 14p 250/25V 14p 50-50/350V 35p  
8/450V 14p 500/35V 20p 60-100/350V 65p  
18/450V 14p 8-8/450V 18p 32-32/250V 18p  
32/450V 20p 8-16/450V 20p 32-32/450V 33p  
50/25V 10p 16-10/450V 85p 32-32+32/350V 43p  
60/25V 10p 32-32/350V 35p 100-10+50/350V 43p

SUB-MIN. ELECTROLYTICS. 1, 2, 4, 5, 8, 16, 20, 50, 100, 200mF 15V 10p; 500, 1000mF 15V 18p; 2000mF 25V 35p.

CERAMIC 10pF to 0.01 mF, 4p. Silver Mica 2 to 5000pF, 4p. PAPER 350V-0.1 4p, 0.5 18p; 1mF 15p; 2mF 150V 15p. 500V-0.001 to 0.05 4p; 0.1 5p; 0.25 5p; 0.47 25p. 1.000V-0.001, 0.0022, 0.0047, 0.01, 0.02, 0.05, 0.1, 0.2, 0.47, 0.1, 10p.

SILVER MICA. Close tolerance 1:1, 2.2-500pF 8p; 500-2000pF 10p; 2.700-5.000pF 20p; 6.800pF-0.01 mfd 30p; each.

TWIN GANG. "0-0" 200pF+170pF, 65p; Slow motion drive 385+385 with 25+25pF, 50p 600pF slow motion, standard 45p; small 8-gang 500pF £1.10. SHORT WAVE. Single 25pF 55p

CHROME TELESCOPE AERIAL, swivel base, 22in. 80p. TURNING. Solid dielectric. 100pF, 500pF, 35p each. TUNING. Compression 30, 50, 70pF, 5p; 100pF, 150pF, 8p; 250pF, 10p; 600pF, 10p; 750pF 10p; 1250pF 10p.

RECTIFIERS CONTACT COOLED 1 wave 60mA 38p; 85mA 45p. SILICON BYZ12 30p; BY100 30p; BY127 30p. EX-GOVERNMENT RECTIFIERS 250V, 200mA, 30p.

NEON PANEL INDICATORS 250V AC/DC Red or Amber 20p. RESISTORS. 1 w. 1/2, 20p; 1/4 w. 10p. HIGH STABILITY. 1 w. 1/2, 20p; 1/4 w. 10p. Ditto 5%. Preferred values 10 Ohms to 10 meg. 4p.

WIRE-WOUND RESISTORS 5 watt, 10 watt, 15 watt 10 Ohms to 100K, 10p each; 2 1/2 watt, 1 Ohm to 2.2 Ohms 10p.

## Q MAX CHASSIS CUTTER

Complete: a die, a punch, an Allen screw and key 1 1/2 in. 35p 1 1/2 in. 95p 1 1/2 in. 21.20 2 1/2 in. 22.21 1 1/2 in. 35p 1 1/2 in. 95p 1 1/2 in. 01.03 1 1/2 in. 21.45 2 1/2 in. 22.86 1 1/2 in. 34p 1 1/2 in. 95p 1 1/2 in. 01.08 1 1/2 in. 21.99 1 in. sq. 21.83

## AM-FM/VHF TUNING GANG

Super quality small size 1 1/2 x 1 1/2 x 1 1/2 in. plus spindle 1 1/2 x 1 1/2 in. 385 + 385 pF with 25 + 25 pF. British made. Geared slow motion drive 6:1. Plastic dust cover. CBA tapped front fixings. Cast aluminium frame 50p Post Free

## MAINS TRANSFORMERS

250-0-250 50 mA. 6-3 v. 2 amps. centre tapped £1.10  
250-0-250 80 mA. 6-3 v. 4 amp. £1.40  
250-0-250 80 mA. 6-3 v. 3.5 a. 6-3 v. 1 a. or 5 v. 2 a. £2.00  
350-0-350 80 mA. 6-3 v. 3.5 a. 6-3 v. 1 a. or 5 v. 2 a. £2.00  
300-0-300 v. 120 mA. 6-3 v. 4 a. C.T. 6-3 v. 3 a. £2.50

MINIATURE 200 v. 20mA. 6-3 v. 1 a. 2 1/2 x 2 1/2 in. 75p  
MIDGUT 220 v. 45 mA. 6-3 v. 3 a. 2 1/2 x 2 1/2 in. 90p  
P.E. AURORA TRANS. 12 + 12v. 500mA £1.50  
MINI-MAINS 200, 100mA. 1 1/2 x 1 1/2 x 1 1/2 in. 50p  
HEATER TRANS. 0-3v. 3 a. 60p

Ditto tapped sec. 1.4 v. 2, 3, 4, 5, 6-3 v. 1 1/2 amp. 80p  
GENERAL PURPOSE LOW VOLTAGE. Tapped Outputs at 2 amp. 3, 4, 5, 6, 9, 10, 12, 15, 18, 25 and 30 v. £2.00  
1 amp. 3, 4, 5, 6, 9, 10, 12, 15, 18, 20, 24, 30, 36, 40, 45, 60, £2.00  
2 amp. 0, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 45, 60, £2.00

AUTO TRANSFORMERS 115v. to 280v. or 280v. to 115v. Input/Output. 150w. 42.00; 600w. 25; 1000w. 21£.  
CHARGER TRANSFORMERS. Input 200/250V. for 6 or 12v. 1 amp. 21.50; 2 amp. 41.50; 4 amp. 42.00.

FULL WAVE BRIDGE CHARGER RECTIFIERS: 6 or 12 v. Outputs. 1 1/2 amp. 40p; 2 amp. 55p; 4 amp. 85p. All transformers Postage 25p extra.

## E.M.I. 13 1/2 x 8 in. LOUSPEAKERS

With flared tweeter cone and ceramic magnet. 10 watts. Bass res. 45-50 cps. Flux 10,000 gauss. State 3 or 8 or 15 ohm. Post 15p

Also with twin tweeters and crossover. 10 watt. State 3 or 8 or 15 ohm. Post 15p (As Illustrated) £4

Recommended Teak Cabinet Size 16 x 10 x 3 in. Post 25p £5

## 10W MINI-MODULE LOUSPEAKER KIT

Triple speaker system combining on ready cut baffle. 1 in. chipboard 15 in. x 8 1/2 in. Separate Bass, Middle and Treble loudspeakers and crossover condenser. The heavy duty 5 in. Bass Woofer unit has a low resonance cone. The mid-Range unit is specially designed to add drive to the middle register and the tweeter recreates the top end of the musical spectrum. Total response 20-15,000 cps. Full instructions for 8 or 15 ohm. TEAK VENEERED BOOKSHELF ENCLOSURE. 16 1/2 x 10 1/2 x 3 in. Modern Design, dark grey Tygan covered baffle £5 Post 25p

## ALL MODELS "BAKER SPEAKERS" IN STOCK

80-14,500 c.p.s., 12in. double cone, woofer and tweeter cone together with a BAKER ceramic magnet assembly having a flux density of 14,000 gauss and a total flux of 145,000 Maxwells. Bass resonance 40 cps. Rated 20 watts. Voice coils 3 or 8 or 15 ohms. Post Free

Module kit, 30-17,000 c.p.s., with tweeter, crossover, baffle and instructions. £11.50

## 'Group 25' 'Group 35' 'Group 50'

12 ohm £7 12 ohm £9 15 ohm £19  
25 watt 35 watt 50 watt  
3 or 8 or 15 ohm 3 or 8 or 15 ohm 8 or 15 ohm

## TEAK HI-FI SPEAKER CABINETS

Fluted wood front for 12in. round Loudspeaker £20. Post 25p  
For 12 x 8 in. Loudspeaker £25. Post 25p  
For 10 x 8 in. round Loudspeaker £24. Post 25p  
LOUDSPEAKER CABINET WADING 18in. wide, 15p in.

## THIS ELAC CONE TWEETER IS OF THE VERY LATEST DESIGN AND GIVES A HIGHER STANDARD OF PERFORMANCE THAN MORE EXPENSIVE UNITS.

The moving coil diaphragm gives a good radiation pattern to the higher frequencies and a smooth curve of total response from 1,000 cps to 15,000 cps. Size 3 1/2 x 2 1/2 in. deep. Rating 10 watts. 3 ohm or 15 ohm models. £1.90 Post 10p

## TWO-WAY XOVER NETWORK 3000 c/s.

With variable tweeter attenuator giving accurate high/low frequency balance. Mounted on panel 5 1/2 in. x 4 in. with control knob, tweeter and woofer leads and 15 ohm input terminals. Suitable for 3 to 8 ohm imp. £1.90 Post 10p

## GOODMANS HEAVY DUTY 10in. WOOFER IS 90W

10w. Large ceramic magnet. 30-12,000 cps. Ideal P.A., Systems, Columns, Hi-Fi, Enclosures etc. £4  
Horn Tweeters 2-16kc/s, 10W 8 ohm or 15 ohm £1.50  
De Luxe Horn Tweeters 2-18 Kc/s, 15W, 8 ohm 2£.  
TWO-WAY 3000cps CROSSOVERS 3 or 8 or 15 ohm 2£.  
SPECIAL OFFER: 30 ohm, 2 1/2 in. dia.; 35 ohm, 3 in. 25 ohm, 3 in. dia.; 6 x 4 in.; 8 x 4 in.; 12 in. dia. 6 watt 3 or 8 or 15 ohm models £1.95 each. Post 15p.

## OUTPUT TRANS. EL84 etc. 25p; MIKE TRANS. 50:1 25p.

SPEAKER COVERING MATERIALS. Samples Large S.A.E. GOODMANS OUTPUT TRANSFORMERS 5 watt push-pull for valves EL84 etc., 3, 8 and 15 ohms 85p. Post 25p.

## 100 WATT ALL PURPOSE POWER AMPLIFIER

4 inputs speech and music. Response 10-30,000 cps. Matches all loudspeakers. A.C. 200/250V. £36 Post Free  
Table and Base Controls Details. S.A.E.

## ALL EAGLE PRODUCTS

SUPPLIED AT LOWEST PRICES  
ILLUSTRATED EAGLE CATALOGUE 80p. Post Free.  
BARGAIN AM TUNER. Medium Wave. Transistor Superhet. Ferrite aerial. 9 volt. £4  
BARGAIN 4 CHANNEL TRANSISTOR MIXER. Add musical highlights and sound effects to recordings. Will mix Microphone, records, tape and tuner with separate controls into single output. 9 volt. £3  
BARGAIN FM TUNER 93-108 Mc/s Six Transistor. 6 volt Printed Circuit. Calibrated dial dual tuning. Walnut Cabinet. Size 7 x 5 x 4 in. £10  
BARGAIN FM TUNER as above less cabinet £7.50  
BARGAIN 3 WATT AMPLIFIER. 4 Transistor Push-Pull Ready built, with volume control. 9v. £3.50

## COAXIAL PLUG 6p. PANEL SOCKETS 6p. LINE 18p.

OUTLET BOXES, SURFACE OR FLUSH 25p.  
BLANKED TWIN FEEDERS 6p. 80 ohms or 300 ohms.  
JACK SOCKET Std. open-circuit 14p. closed circuit 22p.  
Chrome Lead Socket 45p. Phone Plugs 5p. Phone Socket 5p.  
JACK PLUGS Std. Chrome 15p; 8-5mm Chrome 14p. DIN SOCKETS Chassis 3-pin 10p; 5-pin 10p. DIN SOCKETS Lead 3-pin 18p; 5-pin 25p. DIN PLUGS Chassis 18p; 5-pin 25p. VALVE HOLDERS, 6p; CERAMIC 5p; GANS 5p.

## E.M.I. TAPE MOTORS

120v. or 240v. A.C. 1.800 r.p.m. 4 pole 125mA. Spindle 0.187 x 0.75 in. Size 3 1/2 x 2 1/2 x 2 1/2 in. (Illustrated). Post 15p. £1.25

## BALFOUR GRAM MOTORS

120v. or 240v. A.C. 1.800 r.p.m. 4 pole 50mA. Spindle 1 x 3/8 in. Size 2 1/2 x 2 1/2 x 1 1/2 in. Post 15p. 85p

# Out now! The 1971/2 Mullard data book.

An easy reference guide to the Mullard consumer electronics range of semiconductors, valves, television picture tubes and passive components.

Pocket size and colour coded for handy reference.

All components concisely listed in alpha-numeric sequence with Mullard equivalents, comparables and replacements.

Concise data on component types.

All this for just

**30p**



## How to get your copy:

available from your local bookseller or cash with order plus 5p for p & p from Selrøy Book Co., 60 Hayes Hill, Bromley, Kent.

The new Mullard book

## 'Applications of Infrared Detectors'


also now available.

CED 137

## CESCENT RADIO LTD

**MAIL ORDER DEPARTMENT**  
No. 11 Mayes Rd., London, N22 6TL

### BARGAIN COMPUTER BUMPER BOARDS

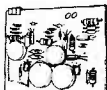

Many Resistors, Condensers, Diodes and Transistors (minimum of 4 transistors on each board).  
**5 BOARDS FOR 120p.**  
Post Free.



### BLACK TERMINALS

Length as indicated 1 inch  
10p per pair P. & P. 3p.

### BATTERY ELIMINATOR

Plug your Transistor Radio, Amplifier, Cassette, etc., into the a.c. mains through this compact eliminator. 2 1/2 in x 2 in x 3 in approx. 4 1/2 V £1.50, 6V £1.50, 9V £1.50, 7 1/2 V complete with cable and plug for Philips Cassette. **£2** plus 8p P. & P. each.



**SEND S.A.E. FOR GREAT BARGAINS IN MICROPHONES, AMPS, DECKS, COMPLETE DISCOTHEQUE CONSOLES, SPEAKERS AND MANY OTHER ITEMS**

### LIGHT DIMMER

The unit comes complete with MK Ivory Front Plate and Control Knob, when used in place of Light Switch it will control your room lighting from off to full brightness. Power—up to 300 watts interference suppressed.  
**£2.75 P. & P. 8p**



### SOLID STATE BLOCK MODULES

Phono pre-amp E1311 Input 100k, gain 28dB max out 3 volt; max input 50mV. Tape pre-amp as above E1313. Power amp E1314 Input 1,000 ohms gain 20dB 300mW. Organ tone osc E1315 tone freq. 200-1k, Hz output 80mW. All above modules 9 volt. Dual flasher E1318 flash time 1-4 secs power 6 volt. Lamp 6v 150mA. All at **£1.25 P. & P. 10p**



### D.P.D.T. SLIDE SWITCH



SIZE 1 1/4 in long x wide  
**13p** each  
3p Postage

### Transformer Scoop

Primary 220, 250 v. fused. Secondary 220 v. at 50mA, 6-8v. at 1 amp. Overall size 2 1/4" x 2" x 2 1/4" high. **63p** each. P. & P. 15p.



### COMPONENT CENTRE

|                                           |          |
|-------------------------------------------|----------|
| 8 x 6 Printed circuit board               | 10p each |
| By100 Type rectifier 800 Piv 750 mA       | 18p "    |
| 4 Pin transistor holders                  | 2p "     |
| 2 1/2 8-ohm speaker                       | 33p "    |
| U2 Battery holders                        | 5p "     |
| 100OHM W/W Pots                           | 13p "    |
| OC81 Heat clips (double)                  | 3p "     |
| Tape rev counters                         | 25p "    |
| 1,500mF 150v DC 4" x 2" dia approx        | 40p "    |
| Flex connector 2amp approx non-reversible | 13p "    |
| Ideal for loudspeaker connections         | 8p "     |
| 2 1/2 80 ohm Speaker                      | 35p "    |

Please include Post & Packing  
Send S.A.E. for return of post quote of your electronic project.


### CHROMOSONIC SOUND OPERATED LIGHT DISPLAY

This compact unit (size 8 1/2" x 5 1/2" x 3" high) is connected directly across the speaker output of an amplifier. It will then convert audio signals into a spectacular three colour light display (500 watts light output each colour). Send S.A.E. for further details or call in at any branch for demonstration.  
**£18.50** P. & P. 33p



## 100 WATT

### HIGH POWER AMPLIFIER

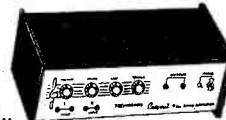

- In excess of 100 watt peak output
- Open and short circuit proof
- Sensitivity 10mV for full output
- Frequency Response 10-25,000Hz
- Safe with all loudspeaker systems 4 to 16 ohms
- Silicon transistors used throughout
- F.E.T. Front end

Send S.A.E. for further details.  
▲ **£42.00** if purchased with light unit above **£40.00**  
Post and Insurance £1.00.

**GUARANTEED 12 MONTHS**


### DWELL TIME UNIT

These small units contain the following components: 700 ohm DPT relay with base, 1uF 250v. paper, 0.01uF 400v. paper, 50uF 35v. electrolytic, 3 diodes OC200 transistor, a 2N2926 type transistor unmarked, a skeleton pre-set pot, 4 pin din plug & skt., 4 foot of 4 core screen. All housed in a small neat metal box. Can be made into many timing devices. **43p** P. & P. 8p


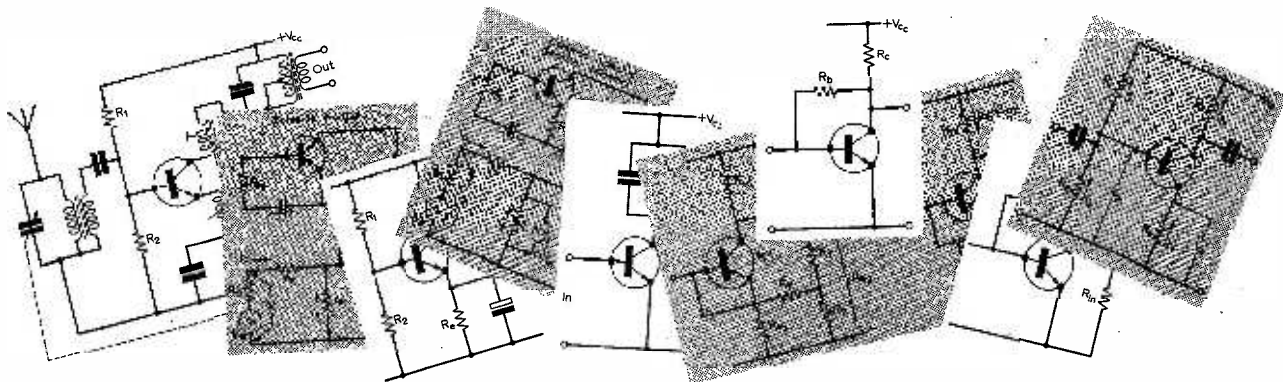
## BRANCHES

11e 40 MAYES RD LONDON N22 888 3206  
13 SOUTH MALL EDMONTON GREEN LONDON N9 803 1685



# TRANSISTOR CIRCUITRY for beginners'

PART 1

H.W.HELLYER

**SPECIAL SERIES-READ IN CONJUNCTION WITH OUR FREE WALL CHART!**

**W**HEN the idea for this series was first broached, everything seemed straightforward and simple. We would entitle the wallchart 'Building Bricks,' said the Editor, in an inspired moment, and the articles would take up each 'brick' and develop it so that newcomers to transistor circuitry could understand what was happening inside those inscrutable black boxes.

Which was all very fine—but it completely overlooked the fact that any beginner worth his salt is going to say 'But Why??'

No good my declaring '... an input signal to the base of Tr1 turns it on, which causes Tr2 to turn off and Tr3 and Tr4 to return to the stable mode, releasing Tr5, which now bottoms and allows ... etc.' It would sound like a paragraph from Henry!

To understand transistor action, it is imperative that we begin by understanding what makes the darned things tick. That means going back to pure physics, not too deeply, preferably without mathematics, and then progressing to the methods of construction and the reasons why there are essential parameters—rules of operation, if you like—and this is what we shall begin with.

## Semiconduction

As the name implies, the semiconductor is neither pure insulator nor electrical conductor, but something in between. Its resistivity lies roughly midway between that of conductors and insulators. This resistivity, moreover, decreases with increase of temperature (the resistance of a conductor increases slightly as the temperature is raised). This is one important difference between semiconductors and conductors.

Next, perhaps more important, is the way in which current flows in a semiconductor. There can be two processes; either a flow of negative electrons, as in the case of a conductor, or a flow in the opposite direction of positive 'holes'. The concept of hole flow is so vital to the understanding of transistor operation that we must begin with a simple discussion of atomic structure in order to get a grasp of it.

## Atomic Structure

An atom consists of a central nucleus containing positively charged protons with a number of negatively charged electrons orbiting around it. The negative charge carried by an electron is equal to, and exactly opposite to, the positive charge of a proton. In a neutral atom, the numbers of each are equal.

Different elements have atoms containing different numbers of electrons, orbiting at different distances from the nucleus. The electrons close to the nucleus are tightly bound to the nucleus, but those circling in the outer orbits are more loosely bound, and are easier to dislodge from the parent atom. The outer ring is called the **valence ring**, and the valence electrons are those with which we are mainly concerned in this work. The looser they are bound to the atom—in any material—the better a conductor a piece of that material will make. This is because loosely bound valence electrons are free to be attracted by a positive charge, such as a voltage applied across a conductor by means of a battery.

Electrons flow out of the conductor into the battery at the positive connection, but an equal number pass from the negative connection of the battery into the conductor at the negative terminal, keeping the overall total of electrons the same.

Conversely, an insulator is a material in which all electrons are tightly bound to the nucleus, so that a large amount of energy is needed to break any loose to make a current flow.

## Crystal Structure

The structure of a crystal of germanium or silicon is depicted in Fig. 1. It can be seen that there are four valence electrons in the outer ring and these are balanced in the nucleus by four positively charged protons, as indicated. In the three-dimensional structure that exists in reality, every atom is equi-distant from four other atoms and each valence electron forms a pair with one from an adjacent atom.

In two-dimensional form this can be shown as in Fig. 1, with pairs of electrons forming co-valent



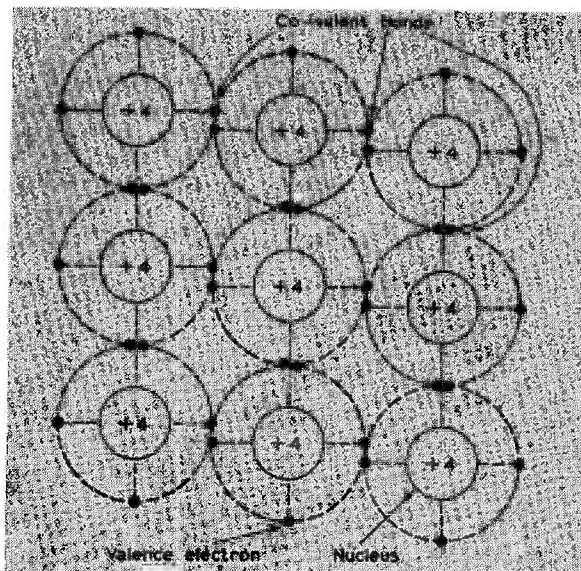


Fig. 1: Illustrating the structure of a germanium or silicon crystal.

bonds. This is a perfect crystal, with no impurities; and no electrons are dislodged from their atoms. This is, in fact, the basic structure of a perfect insulator, at absolute zero temperature, but as temperature increases, the energy of each atom is increased and some electrons can break away. If a voltage is applied, these free electrons are attracted to the positive pole and a current flow results. The space left in the crystal structure by a dislodged electron is termed a 'hole' and this represents a net positive charge.

We can therefore think of a movement of negative electrons toward the positive voltage terminal and a virtual movement of positive 'holes' (as successive electrons move to fill the vacant spaces) toward the negative pole.

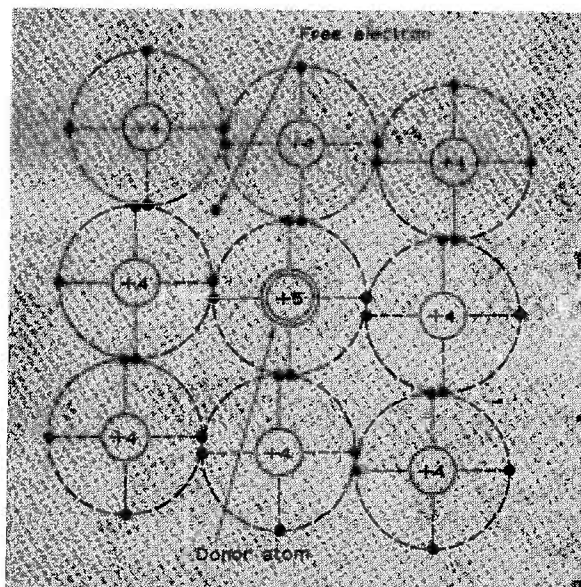


Fig. 2: Adding a 'donor' atom producing an excess free electron. N-type crystal.

## N- and P-Type Semiconductor

This is a simplified explanation, but suffices to show the principle of hole movement. In a pure semiconductor there must be one hole for each free electron. Such a pure semiconductor is termed an **intrinsic material**. However, if an element of impurity is added to the intrinsic material an imbalance is obtained. If, for example, a "donor atom" having five valence electrons is added to the crystal, as in Fig. 2, there is an excess free electron. Four of the donor atom's valence electrons form co-valent bonds, in the manner previously described, but the free atom cannot do so and orbits loosely.

Some materials with a valency of five are antimony, arsenic and phosphorus. These can be added to the germanium or silicon crystal in proportions of as little as one part in a hundred million and reduce the resistivity of the germanium from 70 ohms/cm to 1 ohm/cm. Because the donor atoms in such a material contribute free electrons, which carry a negative electric charge, a material "doped" in this

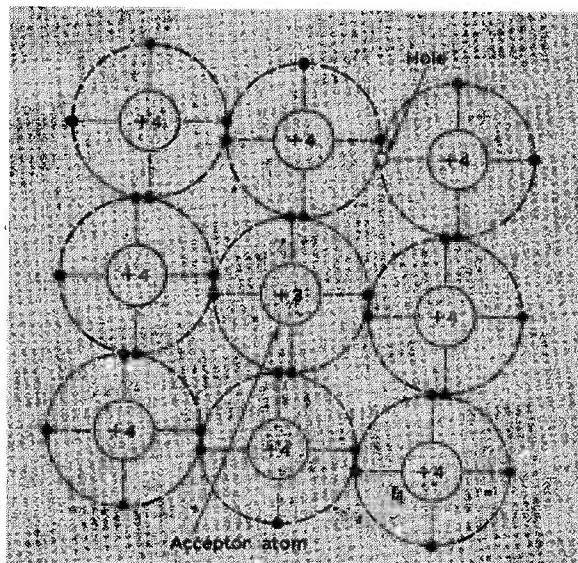


Fig. 3: In this case, an 'acceptor' atom creates a 'hole'. P-type crystal.

way is called an **n-type** semiconductor (i.e. it possesses an excess of negative current carriers).

The opposite process takes place if indium, borium or aluminium atoms are added to the basic semiconductor material, germanium or silicon. These materials have three valence electrons, and the addition of them creates holes in the semiconductor material, as shown in Fig. 3. The resultant semiconductor material has an excess of positively charged holes and is termed **p-type**.

## Minority Carriers

Minority carriers are another important factor of semiconductor physics. If a few electrons are injected into p-type material they are called minority carriers (the majority of current carriers in p-type material being, as we have seen, holes). Recombination takes place as the electrons move to fill the holes.

Similarly, holes injected into an n-type material



form minority carriers in this type of material, and small currents arise as recombination takes place. The time this takes to happen, termed the minority carrier lifetime, is an important property of a semiconductor material and the operation of most transistors depends on the movement of minority carriers.

## PN Junction

A single piece of p-type or n-type semiconductor material is purely resistive: reversing the applied voltage does not alter the current flow. But if p-type and n-type regions are formed in a piece of semiconductor material, with the regions adjoining each other, a rectifying device is formed: when voltage is applied in one direction, current flows, but in the other direction little or no current flows. Such an arrangement is termed a pn junction.

In Fig. 4, the region to the right of the centre line is n-type, possessing a certain density of free electrons. To the left of the line is a region of p-type material possessing a number of positively charged holes. When the junction is first formed, it becomes an area of activity for a short period as free electrons tend to cross into the p-type region and holes move over to the n-type region.

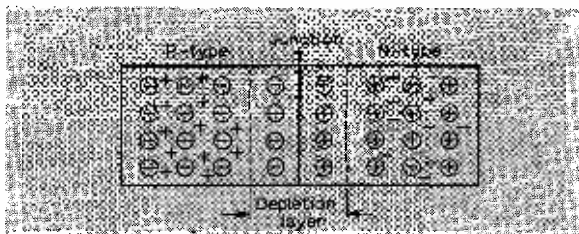


Fig. 4: Showing the charges existing in an unbiased PN junction.

This process of diffusion results in a potential building up across the junction, as the p-region gains a net negative charge with respect to the n region in the vicinity of the junction, and vice-versa, and this potential prevents further diffusion. This potential is termed the barrier potential and the region in the immediate vicinity of the junction, where there are very few free current carriers remaining after the initial diffusion, is termed the depletion layer or region, as shown in Fig. 4.

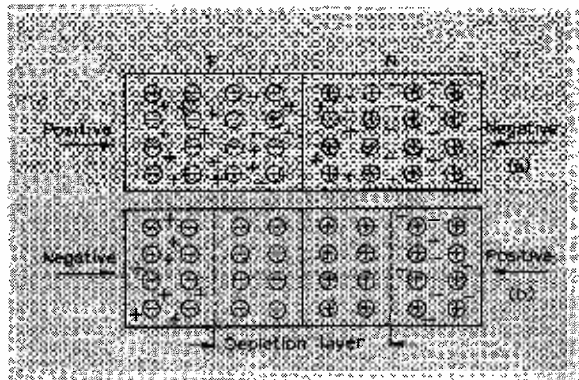


Fig. 5(a): Position of the charges with forward biasing and Fig. 5(b): with reverse biasing.

## Forward and Reverse Biasing

We now have a piece of material with pronounced non-linear characteristics: when an external voltage is applied, current will flow in one direction only. If the p-type side is made positive with respect to the n-type (see Fig. 5(a), forward biasing), the effect is that the barrier potential is reduced. Majority carrier holes will diffuse across to the n-type (where they become minority carriers), and majority carrier electrons will move in to the p-type region. A relatively large current can flow across the junction in this way.

Reversing the bias, i.e. applying it as shown in Fig. 5(b), increases the barrier potential (since the external voltage adds to that across the depletion layer already) so that current flow is made very low—in fact virtually nil. However, due to the effect of temperature a number of holes and free electrons will be generated on either side of the junction—this happens even at room temperatures—and this will give the effect of a small reverse current flowing across the junction. The forward current may be quoted in milliamps but the reverse current only in microamps.

## Characteristics of PN Junction

Fig. 6 shows the characteristics of a pn junction. As the forward voltage is increased from zero, the forward current increases slowly at first until the junction barrier is overcome, then rises rapidly. (In alternative terms, it can be said that the resistance of the forward biased junction is low.) In the reverse direction, the current remains low and practically


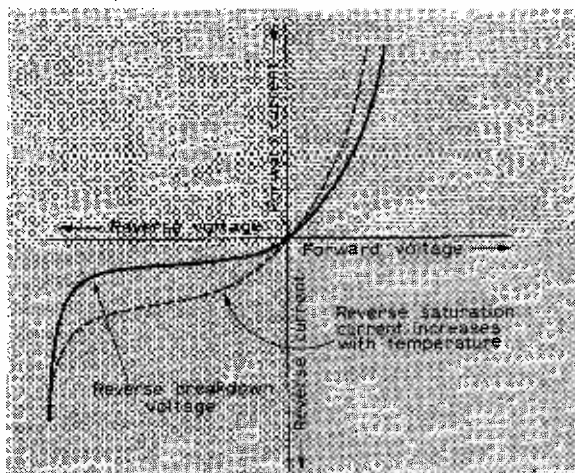


Fig. 6: The electrical characteristics of a PN junction.

constant as voltage is increased, i.e. reverse resistance is very high. Eventually, however, a point is reached where the reverse voltage accelerates the reverse current carriers to such a speed that they break down covalent bonds in the crystal structure, thereby releasing more carriers and producing an avalanche breakdown (when the junction may be destroyed). The value of voltage at which this occurs depends on the resistivity of the material.

As the reverse saturation current is due to the effect of heat, it increases with temperature, giving

—continued on page 512

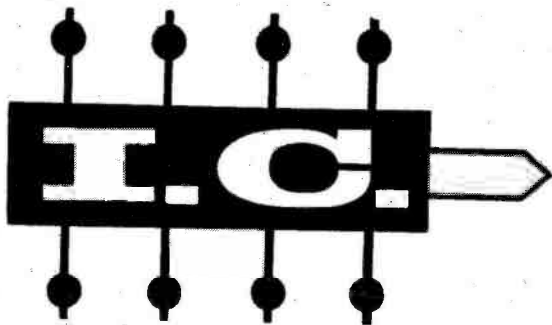

# OF THE MONTH

L.A.J. IRELAND

Number 24

LM373 Multiple-mode Detector

SOME months ago these notes described the Motorola MC1596 balanced mixer integrated circuit and outlined its operation as a multiple-mode detector in receiver circuits. The unit discussed now goes further; full i.f. amplification facilities, at any chosen frequency up to 12MHz., are incorporated, as well as multiple-mode detection. It is the National Semiconductors (U.S.A.) type LM373, available in the U.K. from: Athena Semiconductor Marketing Co. Ltd., 140 High Street, Egham, Surrey; or Rastra Electronics Ltd., 275 King Street, Hammersmith, London W.6.

## Uses

The unit is intended, not just to operate in each mode, but to make it possible to design a receiver in which intermode switching would be simple without reduction of performance. As well as the standard a.m. and f.m. modes, as used for broadcast entertainment in the m.f. and v.h.f. bands, the LM373



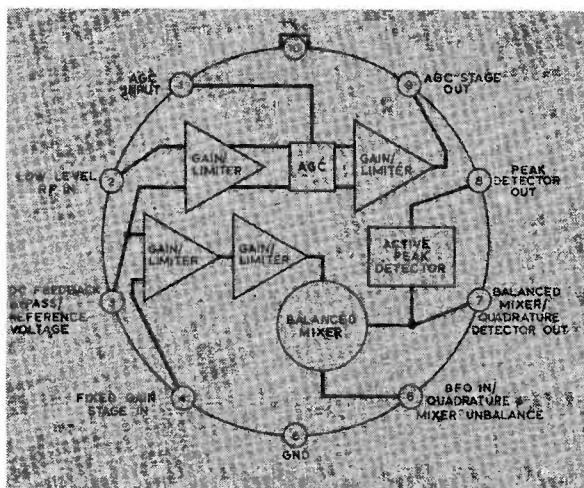


Fig. 1: The equivalent circuit of the LM373 (below) with (above) the top view of the pin connections to the various 'blocks'.

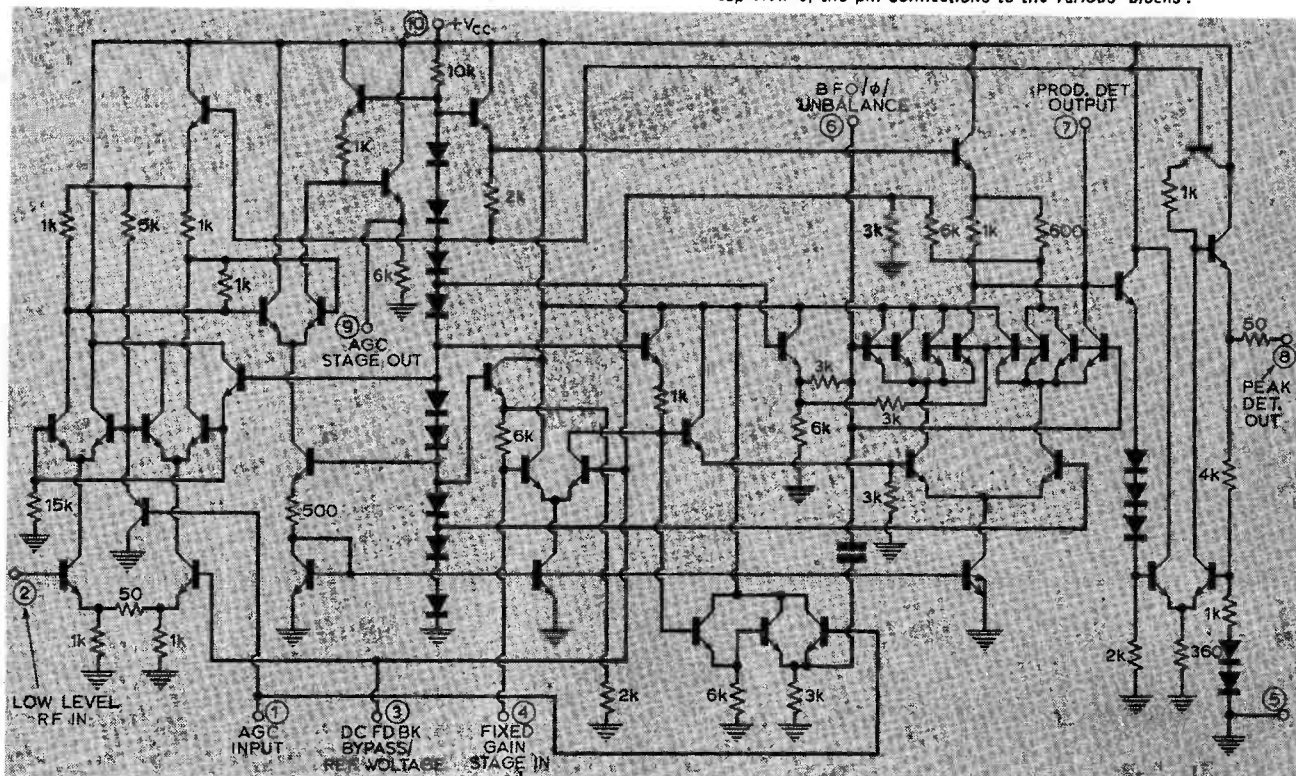

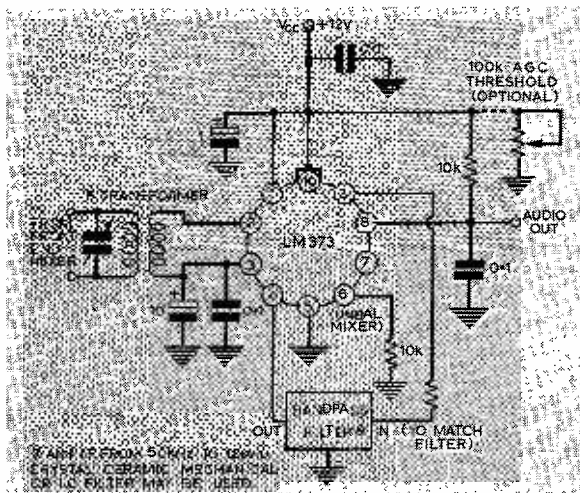


can handle n.b.f.m. (narrow-band frequency modulation) increasingly used in mobile radiotelephone systems, and s.s.b. (single sideband suppressed carrier) transmissions of commercial or amateur origin.

## Design

Considerable ingenuity is exercised in the design of the i.c. to reconcile the conflicting demands of each transmission system with the minimum of intermode switching in the receiver. A.M. and s.s.b. receivers must have a linear amplitude response, maintained, despite the wide range of signal strength received off the air, by an automatic gain control subcircuit. An f.m. i.f. amplifier strip, on the other hand, is essentially nonlinear, in that any input signal is amplified to a limiting level before application to the detector stage. It follows that automatic gain control has no place in such a system.

To provide the facilities indicated, the LM373 incorporates four gain blocks, which can be operated in a limiting mode, as well as an automatic gain

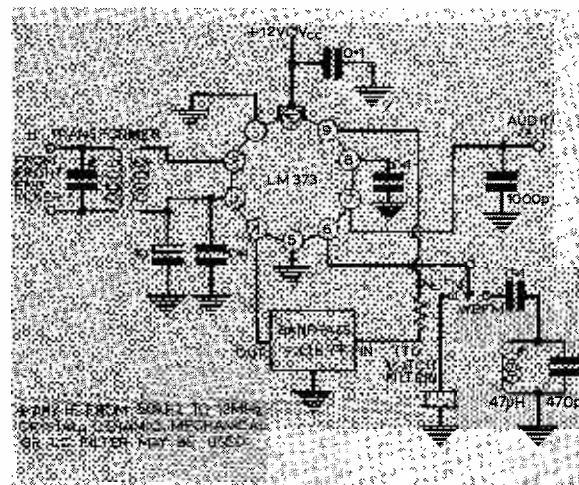


**Fig. 3: The LM373 in its role of an FM IF strip suitable for narrow or wideband reception.**

control system and two detectors, one a balanced mixer similar to that in the Motorola circuit already mentioned, and the other a peak detector for a.m. operation. The equivalent circuit and pin diagram given in Fig. 1 allows these sections to be identified.

## Operation

Some discussion of the circuit would appear necessary. Each gain block is essentially the familiar differential amplifier, which can be operated in its linear region when the circuit is used for a.m. or s.b. reception, or driven to full gain as a limiter for f.m.

The automatic gain control characteristic is secured through a pair of transistors shunting the differential interstage coupling components. When no a.g.c. voltage is applied, these transistors are cut off, but as the control voltage is increased, they draw off an increasing fraction of the signal current; finally the point is reached where the signal from

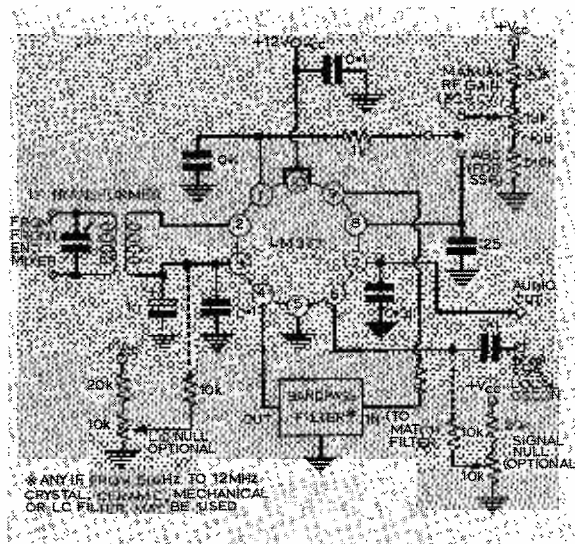

**Fig. 4: The SSB/CW IF strip shown here further demonstrates the versatility of the LM373.**

the first gain block is shorted out, and coupling to the second is merely through stray capacitance.

This approach secures the unusual a.g.c. range of over 70dB., enabling linear a.m. detection to be attained with input signals from 40 microvolts up to 200 millivolts. The string of reference diodes and emitter follower transistors from the d.c. +ve. line provide power supplies with decoupling to each stage of the amplifier strip, together with appropriate bias voltages to set the operating point of each element. As well as simplifying the external decoupling requirements of the circuit, these imply that each stage essentially has its own regulated supply, so minimising the effects of power line variations.

The balanced mixer stage is easily identified by the cross-coupling of its component transistors. For f.m. it operates as a quadrature detector, a system outlined when describing the MC1496, as was the product detector system used for s.s.b. In a.m. operation, this section is deliberately unbalanced by an externally applied bias, leaving only one side of

the differential system connected to its load effectively.

N.b.f.m. demodulation requires a quadrature element of a higher Q factor, i.e. more rapid change of phase with frequency, and therefore a quartz crystal is substituted for the more familiar l.c. circuit. The final section is the peak detector, acting as a.m. detector and a.g.c. voltage source for linear a.m. and s.s.b. operation.

A few precautions are necessary for successful operation. The a.g.c. stage output at pin 9 has a very low impedance, being taken from an emitter follower. A value of 70 ohms is quoted, so that if a high Q crystal filter is employed here a series resistor is advocated, so that the resonance peak of the component will not be damped. The manufacturer of the crystal in question will quote a recommended source impedance, allowing selection of an appropriate resistor.

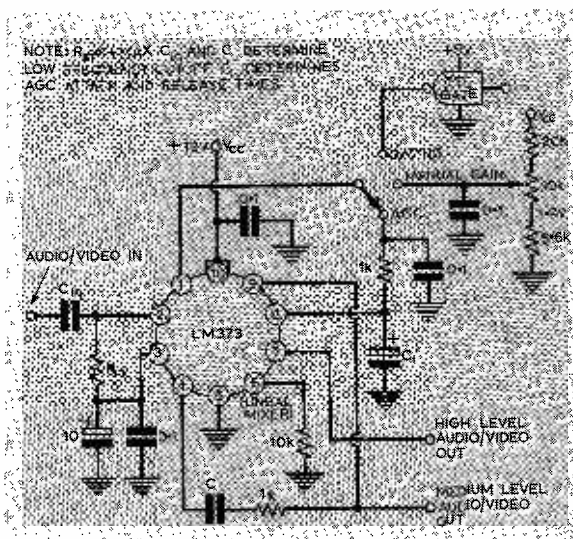


Fig. 5: In TV circuitry the LM373 can be used as an audio/video amplifier with a.g.c., manual gain control or gating.

The d.c. feedback loop at pin 3 must be carefully bypassed, since the decoupling must be effective throughout the passband of the LM373; an electrolytic or tantalum capacitor, as used for a.f. decoupling, has too high a reactance at high frequencies to be effective alone, so a small disc ceramic or silver mica is added.

For s.s.b., bypassing of r.f. at pin 7 is particularly important, as any local oscillator component reaching the peak detector would increase the a.g.c. voltage generated, and lead to an unnecessary reduction of system gain. The optional nulling circuits may be used to maximise gain should that prove necessary (an unlikely event).

Figs. 2-5 indicate the circuitry in which the LM373 may be employed, and it should be noted that the communications receiver applications for which it was designed do not exhaust the potential of this versatile unit, as is indicated by the circuit for a wideband amplifier indicated in Fig. 5. Other reported applications have included use as an amplitude-modulated r.f. oscillator, an s.s.b. generator, or indeed any of the applications open to the balanced mixer circuit in which extra wideband gain is useful. So presumably more will be heard of the LM373!

## TRANSISTOR CIRCUITRY FOR BEGINNERS

—continued from page 509

the effect shown by the dotted line in Fig. 6.

Junction devices of this type are known as diodes, and widely used in radio, television and other electronic applications. The diode is essentially a one-way valve, as we have seen from the forward and reverse bias characteristics.

Germanium diodes were the first types developed for commercial use, but the current-handling capacity of these devices was limited, and it was not until research provided a means of treating silicon that power rectifier semiconductors became a practical proposition. Silicon is more difficult to melt and purify than germanium, but can be doped with donor and acceptor impurities in the same way as germanium, is less sensitive to temperature, and will handle higher powers more efficiently. Common types pass currents of half-an-ampere and more with a practically negligible forward resistance. Silicon diodes have a high reverse voltage rating. (On the other hand, a germanium has greater efficiency at low voltages and at higher frequencies, and is thus retained for signal circuits.)

The pn junction forms the basis of most forms of semiconductor diode and transistor. One other form of construction is important in connection with diodes—the point contact type. In this the rectifying property is possessed by a contact between a thin metal wire and a piece of semi-conductor material. Though junction devices predominate today, point contact diodes are still much used as detectors in radio equipment. Their characteristic is similar to that of the pn junction, shown in Fig. 6, except that as the reverse current increases beyond the reverse breakdown point, reverse voltage tends to fall.

TO BE CONTINUED

# TELEVISION

SEPTEMBER

## TV INTEGRATED CIRCUITS

Integrated circuits are beginning to appear in the new TV chassis in increasing numbers, particularly in colour receivers. The types used have been specifically developed to fulfil the signal processing requirements of TV sets but nevertheless bring with them numerous new techniques. In a new series starting this month we shall be examining these new i.c.s. to familiarise readers with the various changes in TV set design they involve.

## SERVICING TV RECEIVERS

Recent articles have concentrated on fairly up-to-date chassis. This month however we are going back to a widely distributed "625-line convertible" chassis, the Sobell ST195/ST282 series. This will give us an opportunity to examine the faults common in older sets.

PLUS ALL THE REGULAR FEATURES

ON SALE NOW







Better quality receivers have been made with a pair of triode-pentodes in each channel to provide push-pull working. In this type of circuit the two pentodes are the push-pull output valves, while the two triodes are arranged as phase splitters supplying the anti-phase drives to the pentodes. However, since few receivers like this are in the field, there is not much point in detailing the circuit, but it is worth bearing in mind.

Let us return to Fig. 1. The audio signal from pickup or radio detector is coupled by C1 to the top of the volume control VR1, the selected level of signal then being applied via C2 to the triode grid. Note that the grid is returned to chassis through R1 (10M $\Omega$ ) and that the cathode of the triode is returned direct to chassis. This is a common trick to secure grid bias for the triode. Contact potential in the valve causes a minute current to flow through R1, and because of the high value of this resistor a small potential developed across it, and since it is negative at the grid it serves as grid bias. It requires an electronic testmeter to measure this bias (since a normal meter would swamp the 10M $\Omega$  with its own resistance).

A common cause of distortion in this kind of circuit stems from a faulty triode, the fault resulting in excessive grid current and hence a potential across R1 in opposite polarity to that of the bias. The triode anode current rises, and often the valve tends to overheat.

R2 is the triode anode load, with R3 and C3 the decoupling components. The signal across R2 is coupled by C4 to g1 of the pentode, which is biased by the voltage drop across the cathode resistor R4, the grid being returned to chassis through R5. C5 is the cathode bypass capacitor (always an electrolytic in audio output stages).

The anode of the pentode is loaded by the low impedance speaker via the output transformer T1. C6 across the primary attenuates high-order harmonic distortion and makes the reproduction more palatable, as there is no negative feedback and no cancellation of second-harmonic distortion by any push-pull action.

## FAULTS

Owing to the simplicity of this circuit, (Fig. 1) faults are not generally very difficult to define or locate. A cause of bad distortion is poor insulation of the coupling capacitor C4. This would permit a positive potential to exist at the control grid of the pentode with a consequent counteracting of the negative bias. It would be accompanied by excessive positive voltage at the cathode of the pentode, which could result in the failure of C5. The valve would also

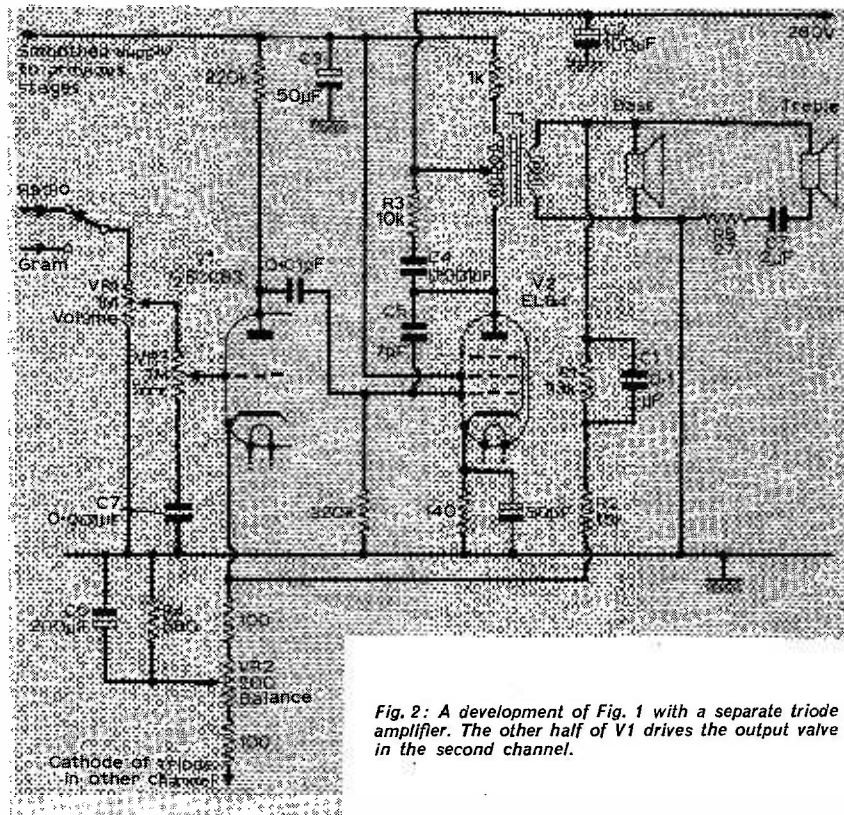


Fig. 2: A development of Fig. 1 with a separate triode amplifier. The other half of V1 drives the output valve in the second channel.

run very hot, possibly with the pentode anode glowing red.

Complete failure (e.g., audio drive at the top of the volume control VR1, but no speaker output) should first lead to a valve test, followed, if necessary, by voltage checks on the appropriate electrodes. C6 is subjected to audio voltage peaks which sometimes result in it shorting. This would cut the output completely, of course, but without affecting the pentode anode voltage much, so look out for this if the valve and electrode voltages seem to be normal.

Open-circuit of T1 primary deletes the pentode anode voltage, a fault condition which is often revealed by the screen grid (g2) of the pentode glowing red hot.

Low gain or volume at maximum volume control setting, assuming normal audio drive from the detector or gram pickup, is not uncommonly caused by C5 going open-circuit or low in value. This results in negative current feedback from the audio then developed across R4. The quickest way of checking this is by shunting an electrolytic across C5.

The symptom can also be caused (possibly accompanied by distortion) by the triode anode load R2 going high. If R3 goes high or C3 becomes electrically 'leaky,' the voltage at the top of R2, and hence the triode anode voltage, will drop, which again will cause low gain and possible distortion.

Before going on to more modern transistor circuits, let us have a look at some possible fault conditions in the valve circuit in Fig. 2. The faults described for Fig. 1 circuit would also be applicable here, with one or two qualifications. First, there are two separate valves involved, the triode voltage amplifier in this case being one section of a double-triode, the other triode serving as the voltage amplifier of the partnering stereo channel (not shown).

If one channel only is in trouble one can easily compare the voltages, etc. with those at the same points in the active channel, which is a quick way of bringing the fault to light. It is also possible to substitute the same type of valves (V2, for example) between the two channels, which would tell conclusively whether the valve is responsible.

There are refinements in Fig. 2, not found in Fig. 1 circuit. For example, voltage negative feedback is applied from the secondary of the output transformer T1 to the cathode of the voltage amplifier V1, and for this to happen one side of the secondary has to be connected to chassis. The amount of feedback is determined by R1 and R2, while C1 in parallel with R1 corrects the phase of the feedback signal, ensuring that it remains substantially negative over the audio spectrum. Thus, if there is a significant rise in gain (e.g., full output at a low setting of the volume control VR1) and abnormally high distortion, then R1 and R2 should be checked for value.

C1 open-circuit could encourage instability at certain frequencies, and this is sometimes 'triggered' by transients of the music. The oscillation could be at a frequency above audio, and the only way to prove this is by connecting an oscilloscope across the secondary of the output transformer T1, preferably when the amplifier is driven by a sinewave signal from an audio generator. The oscillogram in Fig. 3 gives some idea of what the spurious signal could look like on the sinewave. The audio generator would be coupled to the grid of the triode, of course.

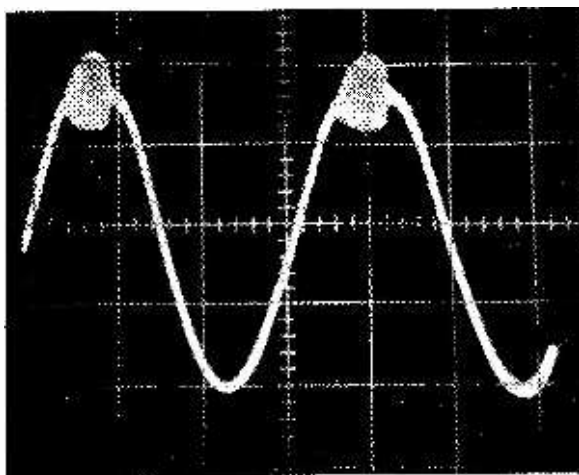


Fig. 3: This oscillogram shows spurious oscillation triggered off by transients in the signal

If the earth and feedback connections are reversed on the transformer the feedback would be positive and the amplifier would turn into a violent oscillator! Take care, therefore, when fitting a replacement transformer! Moreover, designs like this are geared to an output transformer of specific characteristics, so if it becomes necessary to replace the transformer, and the exact type is not available, then it might be necessary to alter the feedback resistors and the phase-correcting capacitor so that the values provide the correct conditions of feedback.

An interesting feature of the circuit is the tap on T1 primary. An output transformer of this kind serves both for speaker coupling and for 'smoothing' the h.t. supply fed to the earlier stages. In fact, it acts in part rather like a smoothing choke. In the

circuit, C2 is the reservoir capacitor across the power supply output and C3 is the main smoothing electrolytic.

R3 and C4 series combination across the signal part of T1 primary attenuates the higher-frequency distortion components while, with C5, providing a degree of corrective phase shift.

The triode V1 in this circuit is cathode-biased, the main cathode resistor being R4, decoupled by C6. VR2 is the stereo balance control, which feeds either side the 100-ohm resistors (one to the cathode circuit of the partnering channel). The 100-ohm resistors provide a small degree of negative current feedback since they are out of the decoupling influence of C6. The voltage developed either side of VR2 relative to the slider also contributes to the feedback. Thus it will be appreciated that by adjusting VR2 from its centre setting, the feedback on one channel will decrease, while increasing on the other channel. This, therefore, allows the gains of the two channels to be adjusted relatively for the most desirable stereo effect.

VR3 is a simple 'tone' control which works as a reactive potential-divider in conjunction with C7. With increasing frequency the reactance of C7 falls, which means that as the slider of VR3 is turned towards this end of the track the bass is lifted and the treble diminished.

It will also be seen that two speaker units are employed. That for bass is connected directly across the secondary of T1, while the treble unit receives drive via R5 and C7. R5 reduces the power, while C7 passes only the higher frequency signals. This is a very simple frequency-divider, which cannot be regarded as 'hi-fi.'

## HI-FI CIRCUIT

One channel of a slightly different circuit which, possibly differing in detail, is found in some hi-fi equipment. This is the power amplifier department only, Fig. 4, where Tr1 is the input transistor, coupling to the d.c.-coupled pair Tr2/Tr3 via C1. The coupling is from Tr1 emitter (the collector 'earthed') to signal through C2). The stage is thus an emitter-follower, which has a relatively high base input impedance, giving the correct match from the control section.

Tr4/Tr5 constitute a complementary driver pair (complementary because one is n.p.n and the other p.n.p.). These drive the push-pull output transistors Tr6/Tr7 alternatively into conduction and cut-off on each half-cycle of signal. It will be noted that the base of Tr4 is fed from the same source (e.g., Tr3 collector) as the base of Tr5. Thus on a positive half-cycle Tr4 conducts and pushes a positive half-cycle into Tr6 base. At the same time Tr5 is driven downwards and since Tr7 base is connected this time to Tr5 collector a negative half-cycle appears at Tr7 base, pushing this transistor into cut-off. On a negative half-cycle of drive the conditions reverse, so that Tr6 is driven into cut-off and Tr7 into conduction.

The two half-cycles are reconstituted as a complete waveform in the load comprising the speaker, coupled through C3.

C4 is a bootstrapping capacitor which applies feedback in such a way as to increase the driver input impedance. A.C. negative voltage feedback is applied to Tr2 emitter circuit from the push-pull pair, via C5

However, in Fig. 4 VR1 adjusts the balancing and VR2 the quiescent current, which leads us neatly to hi-fi equipment fault-finding and tests. But before going on to this it is noteworthy that temperature stabilisation is often provided in or around VR2 circuit to hold the quiescent current steady with increase in temperature of 'thermal element,' TH1 in function.


## AMPLIFIER TESTS AND FAULT FINDING

For detailed testing in audio circuits, especially high quality circuits in which transistors are employed, we require an audio signal generator, audio millivoltmeter and an oscilloscope, at least. For distortion tests, we require in addition a distortion factor meter or similar instrument.

If it is assumed that the radio or pickup source signal is reaching the input of the amplifier and there is no output from the speaker, then we should check as far as possible into the amplifier with a signal tracer (e.g., pair of headphones, etc.—see Part 3, PW July 1971). In Fig. 4, for example, we could get to the base of Tr2, but possibly not any further owing to the d.c. couplings of the subsequent stages. Indeed, it is often necessary to consider the power amplifier proper as a complete circuit from the testing point of view. This is because a faulty transistor or component in one stage could reflect fault conditions into the other stages as a result of the d.c. couplings. This possibility is often overlooked when testing in circuits of this kind.

When we reach the point where the signal disappears, therefore, we may have to continue the exercise in terms of voltage measurements at the electrodes of the various transistors, comparing them with the correct values given in the service manual or on the circuit. Complete failure commonly implies significant change in the d.c. conditions, so the fault area should soon be revealed by voltage testing. If a coupling capacitor has failed, then signal tracing should reveal this without much trouble.

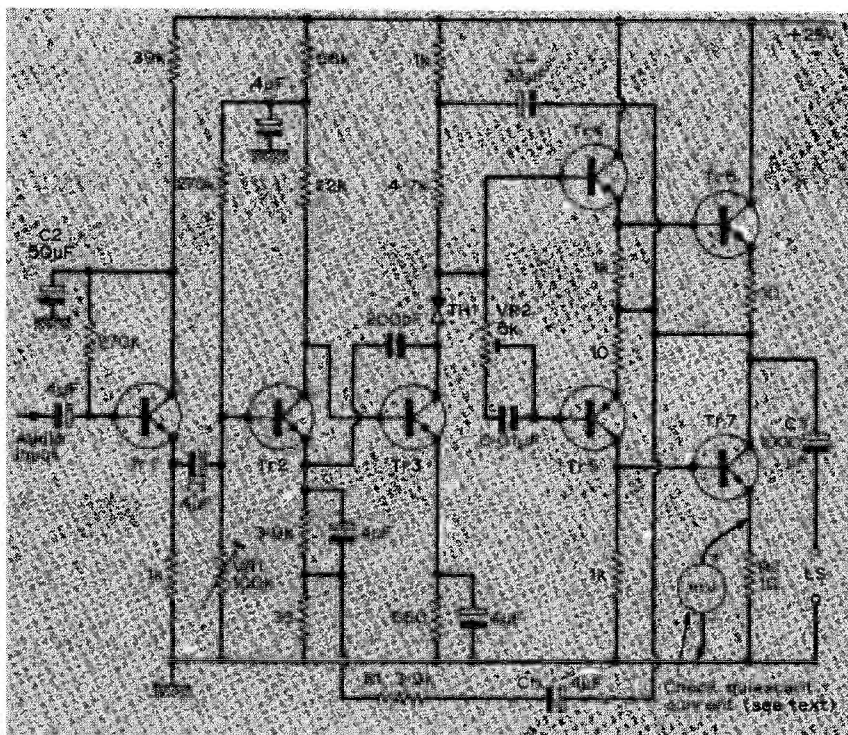
More difficult faults to locate are those resulting in low gain, intermittent crackling and distortion at all powers or only at high power. Starting first with distortion, a preliminary test should be that of



quiescent current (assuming the amplifier to be 'Class B,' which it usually is in these days of transistors).

If possible, one should avoid connecting a milliammeter in series with the output pair for this test, owing to the resistance of the meter movement. In a circuit like that in Fig 4, the voltage across the emitter resistor (R2) of Tr7 should be measured on a d.c. millivoltmeter. The voltage will be very low because R2 is only 1 ohm! Anyway, suppose we measure 25mV, then by Ohm's law we can calculate that the current is 25mA (1 ohm resistor, since  $I=V/R$ , where I is in mA when V is in mV). A current of 25mA is, in fact, a common quiescent current value, and it can be adjusted accurately by a preset such as VR2.

If there is no preset and the current is way out, the values of the resistors associated with this part of the circuit should be measured (also the thermistor, etc., if used). Excessive quiescent current will cause the output transistors to run hot and limit the output

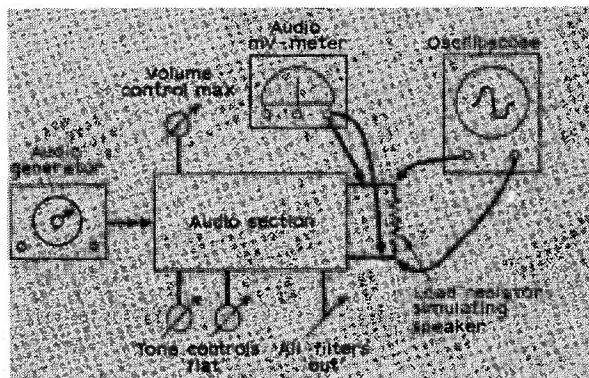

**Fig. 5: Equipment set-up required to check the balance of output transistors.**

power, while too low a value will precipitate high distortion (crossover distortion) at low volume.

Balancing requires an oscilloscope to monitor the output sinewave fed in from an audio generator. The setup is shown in Fig. 5 where it will be seen that the speaker is replaced by a load resistor of suitable power rating (to match the steady-state power of the amplifier). The volume control should be fully advanced, and the generator signal increased until the tips of the displayed waveform commence to clip. When the balancing is correct both tips will clip together. If one clips before the other then the balancing preset (such as VR1 in Fig. 4) should be adjusted for symmetrical clipping. The waveforms are shown in Fig. 6.

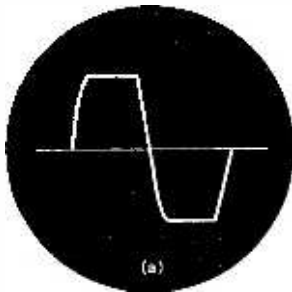


Fig. 6(a) Symmetrical clipping of the waveform when the gain is advanced indicates correct balance.

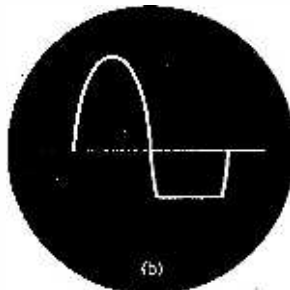


Fig. 6(b) Output waveform with an unbalanced stage.

We can use the setup in Fig. 5 to measure the steady-state power of the amplifier. For this test the oscilloscope should either be accurately calibrated in peak-to-peak voltage (so that the r.m.s. voltage of the waveform can be determined by multiplying the peak voltage—i.e., half p-p voltage—by 0.7) or an r.m.s.-reading audio millivoltmeter should also be connected across the load, as shown in Fig. 5.

The load voltage just prior to the clipping point should be noted, and the steady-state power in watts is equal to the load voltage squared divided by the load value in ohms (i.e.,  $W = V^2/R$ ). The power is usually taken at 1kHz, but the power bandwidth can be appraised by noting the reduction in power at the low and high frequency ends of the spectrum.


Low power, but good waveshape often signifies low supply rail voltage, and this can result from low mains voltage or incorrect mains voltage tapping.

## DISTORTION TEST

Finally, total harmonic distortion testing. For this we require either a complete distortion factor meter or the set-up in Fig. 5 with a distortion measuring unit which, as was noted in the Test Instrument supplement, April 1971, is a 'notch filter' which

tunes out the fundamental frequency of the output signal, leaving only the harmonic components, the voltage sum of which is compared in ratio with the voltage of the fundamental frequency across the load, to give the dB or percentage total harmonic distortion.

The complete set-up is shown in Fig. 7. The voltage across the load is first measured at the required power (use the oscilloscope for maximum power test to indicate the clipping level) with the switch in position A, then switching to position B, allowing the audio millivoltmeter to read the voltage of the summed harmonics. For this to happen, however, the distortion measuring unit needs to be very accurately tuned and balanced for the least indication on the audio millivoltmeter, which requires the range of the millivoltmeter progressively to be stepped down. The total harmonic distortion is the voltage ratio between the readings at switch positions A and B.

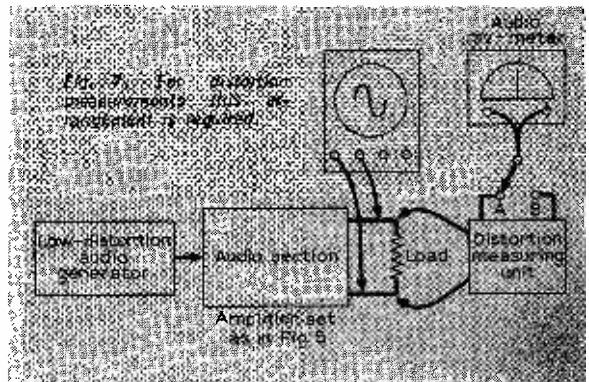

For example, if voltage A is 9V (which across 8 ohms would correspond to about 10W) and voltage B is 90mV, the ratio would be 100:1 or 40dB, corresponding to 1% t.h.d. With 9mV at B it would represent a ratio of 1000:1 or 60dB, corresponding to 0.1% t.h.d.

Remember, though, that a simple distortion measuring set 'notches out' only the fundamental, leaving wideband noise as well as t.h.d. components, so the distortion readout will include noise. Residual hum is generally removed by a high-pass filter in the test set-up, but such filtering, of course, cannot be used for distortion measurements at low-frequency for obvious reasons.

## END OF PART SIX

### Back Numbers Important Announcement

We regret to inform readers that owing to the closure by the Company of the department concerned it will no longer be possible to supply back numbers of **Practical Wireless** and **Television**.

To ensure obtaining regular copies of these magazines readers are strongly urged to place a regular order with their local newsagent, or to take out an annual postal subscription.

Reference to past issues of the magazines may sometimes be obtained at certain public libraries who may hold bound volumes. A few libraries are said to offer a photostat service. Alternatively, we are always willing to insert a free request for specific back numbers in our "CQ" column which appears in most issues.

# practically wireless commentary by HENRY

No. 84

Ted  
and  
Lid

NO, not *that* Ted. Henry is not taking the lid off political chicanery—leave that to out-of-office politicians. TED, or, more properly, T.E.D., is a beautiful phrase I heard during a broadcast interview recently. That ubiquitous character, A. Spokesman, was defending the Post Office in the face of polite but relentless attacks from the BBC, who were following up listeners' complaints about crossed lines.

'How does it happen,' came the suave question, 'that we pick up our telephone and find our conversation interrupted by a pair of drooling lovers or an irate customer who has lost his laundry?'

Ah, well, our indefatigable spokesman countered, that is probably caused by a Transient Equipment Defect. Isn't that lovely? Imagine, Joe, when wifey grumbles about the birdies that chirp unwantingly during her 'Housewives' Choice', being able to say airily: "Can't do much about that, I'm afraid. That's TED."

The point is that the faults are not just short-lived, ephemeral, unidentified phenomena—giving them a name has fixed them, preserved them for posterity, entered them on the list of recognisable bugbears.

Wireless work is full of such



We cheer when we get a half-scale reading . . .

instances; for example, the intermittently blowing fuse. We pursue diligent tests before replacing the offending glass tube. We measure resistance, cheer when we get a half-scale reading, then remember that we intended to change the battery of the meter last time we used it.

Baffled by the lack of short-circuits we decide to beat the brute by checking the current. Meter in series—ah, which way round? Switch on. No, the other way around: is that pointer bent? But the reading is no greater than expected, and certainly less than the rating of the fuse, which we refit. Perhaps it is the result of overheating. We cover the now smug-looking set with our jacket and wait.

It is a bad habit of some manufacturers to let dirty great heat-sinks jut out at the back, and the fallacy about cool-running transistors is shattered as we smell singeing Harris Tweed and realise we have a Class A output to contend with.

Touching the fins to confirm our nose, we snatch fingers back with a howl and, sucking them, muse that the problem could not have been temperature at all. And the fuse still holds.

Obviously, TED has been at work. He is only waiting for us to settle comfortably with a book and a glass at our elbow before blowing the fuse again. Or, more likely, lulling us into a false sense of security, will allow us the whole evening's listening, then, while we sleep through the small CQ hours, will sneakily contract that vulnerable thread of wire again so that rising betimes, we gaily throw the switch and get: silence!

TED is no fool. That Post Office bloke urged 'sweet reasonableness' upon subscribers when their lines were crossed. The inference was that if we pretended not to notice the fault it would go away. Any PW reader could have told him that is the wrong approach.



. . . and we snatch our fingers back with a howl.

How many times have you had a piece of equipment propped up on the bench, festooned with test leads, bedizened with warning lights, burbling away in the corner of your mind, and leaped into the breach as the expected fault occurs, only to be greeted with a return to normality the moment you touch the chassis?

Tracking down TED is the work of an expert. One tests piecemeal. One uses not sweet reasonableness, but bitter reason. Diagnosis, as our soon-to-finish series on Servicing has emphasised, is the secret of success. And for diagnosis, where TED is concerned, read *inspired guesswork*. This is where LID comes in. LID is one of those contractions I am no longer likely to forget, since talking to Bob Stockwell, publicity manager of Bang & Olufsen, the day after an exhausting exhibition.


'How do you manage to organise it?'

'It's not easy,' he said, 'but we begin by catering for the Largest Imaginable Disaster and take it from there. . . .'

That is the secret of dealing with TED. Put the LID on him: when the fuse blows, imagine the worst that could happen and assume that it has! But don't try to telephone the repairman—you will probably get the laundry company again.



# electronics mastered!\*

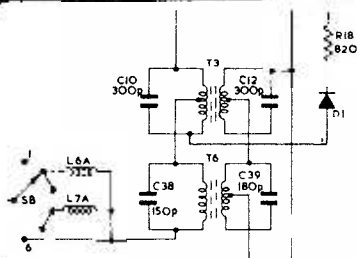

by our highly practical  
**BUILD, SEE & LEARN** system

Step by step we take you through the apparent intricacies of electronics and show you how easily you can master the subject. Write for the brochure which shows, in full detail, how you can do it.

**1**

We provide a full range of components and sub-assemblies, with details of what they do, so that you learn to recognise all the 'bits and pieces'. Using some of these you are instructed in how to build this oscilloscope, simply and quickly.



**2**

You are shown how to read and understand circuit diagrams so that you can later build more advanced equipment or draw your own diagrams.

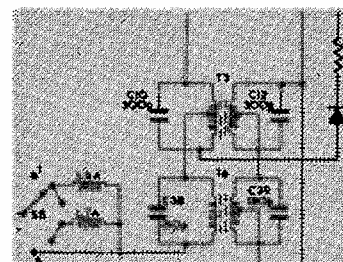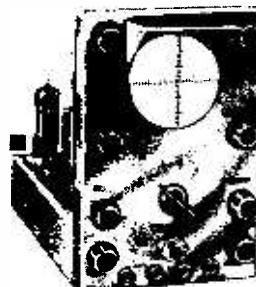**3**

You can construct over 40 kits, including:—

- Valve experiments
- Transistor experiments
- Amplifiers
- Oscillators
- Signal tracer
- Photo electric circuit
- Computer circuit
- Basic radio receiver
- Electronic switch
- Simple transmitter
- a.c. experiments
- d.c. experiments
- Simple counter
- Time delay circuit
- Servicing procedures



This course has been designed to help even those who are complete newcomers to electronics. **No Maths needed!**

**POST NOW  
FOR  
FREE BROCHURE**

BLOCK CAPITALS PLEASE

To: **British National Radio School, Reading, Berks.**

Please send your free Brochure, without obligation, to:

NAME

ADDRESS

P10/71

**FREE**

**SPECIAL ELECTRONIC GIFT  
to all our Students POST COUPON NOW!**

# ELECTRONIC VALVES

|        |      |        |      |        |      |           |      |
|--------|------|--------|------|--------|------|-----------|------|
| 0A2    | 0-35 | 6AL7GT | 0-35 | DY87   | 0-35 | PC88      | 0-55 |
| 0A3    | 0-35 | 6AL7GT | 0-35 | DY88   | 0-35 | PC89      | 0-55 |
| 0B2    | 0-35 | 6BQ7   | 0-40 | E88CC  | 0-55 | PC189     | 0-55 |
| 0B3    | 0-60 | 6BR7   | 0-40 | E180F  | 0-55 | PC285     | 0-55 |
| 0C3    | 0-35 | 6T8    | 0-35 | E810F  | 2-90 | PC386     | 0-80 |
| 0D3    | 0-35 | 6U4GT  | 0-40 | EABCS0 | 0-35 | PCF80     | 0-30 |
| 1B3GT  | 0-35 | 6U8A   | 0-40 | EAF42  | 0-55 | PCF82     | 0-30 |
| 1C3T   | 0-60 | 6V6GT  | 0-35 | EB3C3  | 0-50 | PCF84     | 0-50 |
| 1L4    | 0-20 | 6X4    | 0-30 | EB3C4  | 0-50 | PCF86     | 0-50 |
| 1R4    | 0-35 | 6X5GT  | 0-35 | EB3C1  | 0-30 | PCF87     | 0-50 |
| 1R5    | 0-35 | 6X8    | 0-55 | EBF80  | 0-40 | PCF801    | 0-50 |
| 1S4    | 0-27 | 6Y6G   | 0-60 | EBF83  | 0-40 | PCF802    | 0-50 |
| 1S5    | 0-25 | 7Y4    | 0-60 | EBF89  | 0-30 | PCF805    | 0-75 |
| 1T4    | 0-25 | 9BW6   | 0-50 | EC53   | 0-50 | PCF806    | 0-70 |
| 1U4    | 0-27 | 10C1   | 0-50 | EC58   | 0-60 | PCF808    | 0-75 |
| 1U5    | 0-50 | 10D1   | 0-50 | EC60   | 0-60 | PCF809    | 0-70 |
| 1V2    | 0-45 | 10D2   | 0-40 | EC90   | 0-35 | PC181     | 0-50 |
| 1X2B   | 0-40 | 10F1   | 0-50 | EC91   | 0-50 | PC182     | 0-35 |
| 2D21   | 0-35 | 10F9   | 0-50 | EC92   | 0-35 | PC183     | 0-55 |
| 3A4    | 0-35 | 10L18  | 0-45 | EC93   | 0-50 | PC184     | 0-45 |
| 3B28   | 2-15 | 10L18  | 0-45 | EC8010 | 2-25 | PC185     | 0-40 |
| 3BF1   | 2-75 | 10L11  | 0-50 | EC904  | 0-50 | PC186     | 0-45 |
| 3Q4    | 0-40 | 10P13  | 0-55 | EC881  | 0-35 | PC188     | 0-40 |
| 384    | 0-35 | 10P14  | 1-10 | EC92   | 0-30 | PC189     | 0-40 |
| 3V4    | 0-45 | 12AB5  | 0-60 | EC93   | 0-30 | PC1801    | 0-70 |
| 5B4GY  | 0-60 | 12AC8  | 0-40 | EC94   | 0-30 | PD500     | 1-50 |
| 5Y4G   | 0-35 | 12AL5  | 0-45 | EC95   | 0-40 | PR86      | 0-60 |
| 5Y4GB  | 0-45 | 12AC5  | 0-45 | EC96   | 0-40 | PR88      | 0-55 |
| 5Y4G   | 0-45 | 12AT6  | 0-35 | EC97   | 0-40 | PFL200    | 0-70 |
| 5Y3GT  | 0-35 | 12AT7  | 0-35 | EC99   | 0-30 | PL3       | 0-35 |
| 5Z3    | 0-50 | 12AU6  | 0-30 | EC1189 | 0-60 | PL36      | 0-45 |
| 5Z4G   | 0-40 | 12AU7  | 0-30 | ECF80  | 0-35 | PL81      | 0-50 |
| 6/30L2 | 0-75 | 12AV6  | 0-35 | ECF82  | 0-35 | PL82      | 0-45 |
| 6AB4   | 0-35 | 12AV7  | 0-40 | ECF86  | 0-55 | PL83      | 0-45 |
| 6AF4A  | 0-60 | 12B3T  | 0-40 | ECF89  | 0-40 | PL84      | 0-50 |
| 6AG7   | 0-40 | 12AX7  | 0-70 | ECH42  | 0-70 | PL302     | 0-80 |
| 6AH6   | 0-50 | 12B44A | 0-65 | ECH81  | 0-30 | PL504     | 0-80 |
| 6AJ8   | 0-30 | 12BA6  | 0-55 | ECH83  | 0-40 | PL508     | 0-90 |
| 6AK5   | 0-30 | 12BA7  | 0-35 | ECH84  | 0-45 | PL509     | 1-30 |
| 6AK6   | 0-57 | 12BE6  | 0-35 | ECL80  | 0-40 | PL801     | 0-80 |
| 6AL5   | 0-45 | 12B17  | 0-40 | ECL81  | 0-45 | PM84      | 0-50 |
| 6AL5   | 0-45 | 12B3T  | 0-40 | ECL82  | 0-45 | PM89      | 0-50 |
| 6AM5   | 0-32 | 12K5   | 0-55 | ECL83  | 0-45 | PY33      | 0-85 |
| 6AM6   | 0-33 | 12K7GT | 0-35 | ECL84  | 0-55 | PY80      | 0-35 |
| 6AQ5   | 0-35 | 12Q7G  | 0-30 | ECL85  | 0-55 | PY81      | 0-30 |
| 6AQ6   | 0-55 | 12R7   | 0-35 | ECL86  | 0-40 | PY82      | 0-30 |
| 6AR5   | 0-35 | 14S7   | 0-80 | ECL87  | 0-50 | PY83      | 0-38 |
| 6AR6   | 0-40 | 12B17  | 0-40 | ECL88  | 1-50 | QD1       | 0-50 |
| 6AR11  | 1-25 | 20L1   | 1-10 | EF37A  | 0-60 | PY900     | 0-50 |
| 6AS5   | 0-35 | 20P1   | 0-50 | EF38   | 0-40 | PY900     | 0-50 |
| 6AS7G  | 0-30 | 20P4   | 1-10 | EF40   | 0-50 | PY901     | 0-50 |
| 6AT6   | 0-30 | 20P5   | 1-20 | EF41   | 0-55 | PZ30      | 0-35 |
| 6AU5   | 0-25 | 25C5   | 0-50 | EF42   | 0-70 | QVQV2-6   | 2-15 |
| 6AV6   | 0-30 | 25L6GT | 0-45 | EF80   | 0-25 | QVQV3-10  | 1-25 |
| 6AW5A  | 0-55 | 25Z4G  | 0-60 | EF83   | 0-55 | QVQV3-20A | 5-25 |
| 6BA4   | 0-25 | 25Z6GT | 0-65 | EF85   | 0-55 | QVQV4-4A  | 5-50 |
| 6BE6   | 0-30 | 30A5   | 0-45 | EF86   | 0-30 | TT21      | 2-65 |
| 6BF5   | 0-50 | 30AE3  | 0-40 | EF89   | 0-28 | TT22      | 2-90 |
| 6BF6   | 0-50 | 30C1   | 0-30 | EF91   | 0-33 | U18/20    | 0-75 |
| 6BR5   | 0-45 | 30C15  | 0-80 | EF92   | 0-40 | U25       | 0-75 |
| 6BR6   | 0-45 | 30C17  | 0-80 | EF93   | 0-45 | U31       | 0-45 |
| 6BK7A  | 0-55 | 30C18  | 0-75 | EF97   | 0-55 | U37       | 1-50 |
| 6BN6   | 0-43 | 30F5   | 0-55 | EF98   | 0-65 | U50       | 0-35 |
| 6BQ5   | 0-25 | 30FL1  | 0-70 | EF183  | 0-30 | U76       | 0-30 |
| 6BR8   | 0-65 | 30FL12 | 0-75 | EF184  | 0-35 | U91       | 0-75 |
| 6BR9   | 0-65 | 30FL14 | 0-95 | EF800  | 1-00 | U201      | 0-85 |
| 6B87   | 1-30 | 30L1   | 0-50 | EF804  | 1-25 | U281      | 0-40 |
| 6BW6   | 0-55 | 30L15  | 0-55 | EK90   | 0-30 | U32       | 0-35 |
| 6BW7   | 0-70 | 30L17  | 0-80 | EK93   | 1-25 | U78       | 0-30 |
| 6BX6   | 0-25 | 30P12  | 0-80 | EL34   | 0-50 | U191      | 0-75 |
| 6BZ6   | 0-35 | 30P19  | 0-80 | EL36   | 0-50 | U201      | 0-85 |
| 6C4    | 0-33 | 30P11  | 0-70 | EL37   | 1-25 | U281      | 0-40 |
| 6C5GT  | 0-40 | 30P13  | 0-70 | EL41   | 0-55 | U32       | 0-35 |
| 6C6    | 0-30 | 30P14  | 0-80 | EL42   | 0-58 | U301      | 0-40 |
| 6CD6GA | 1-15 | 35A3   | 0-55 | EL81   | 0-55 | U403      | 0-50 |
| 6C67   | 0-50 | 35A5   | 0-75 | EL83   | 0-42 | U404      | 0-50 |
| 6C80   | 0-55 | 35B5   | 0-65 | EL84   | 0-25 | U801      | 1-00 |
| 6C85   | 0-50 | 35C5   | 0-60 | EL85   | 0-43 | UACB80    | 0-35 |
| 6C94   | 0-50 | 35D5   | 0-60 | EL86   | 0-40 | UAF41     | 0-50 |
| 6C95   | 0-45 | 35L6GT | 0-50 | EL90   | 0-35 | UAF42     | 0-55 |
| 6C97   | 0-55 | 35W4   | 0-30 | EL95   | 0-35 | UBC41     | 0-50 |
| 6D3    | 0-45 | 35Z3   | 0-30 | EL98   | 1-00 | UBC81     | 0-40 |
| 6DC6   | 0-75 | 35Z4G  | 0-60 | EL821  | 0-55 | UBF80     | 0-40 |
| 6DK6   | 0-45 | 35Z6GT | 0-40 | EL822  | 0-80 | UBF89     | 0-35 |
| 6DQ6B  | 0-35 | 35A5   | 0-75 | EL830  | 0-70 | UBL4      | 0-50 |
| 6DS4   | 0-75 | 50B5   | 0-45 | EM34   | 0-90 | UBL21     | 0-60 |
| 6EA8   | 0-58 | 50C5   | 0-40 | EM71   | 0-75 | UC92      | 0-35 |
| 6E87   | 0-50 | 50CD6G | 1-55 | RM80   | 0-40 | UC95      | 0-40 |
| 6EJ7   | 0-35 | 50L6GT | 0-50 | RM81   | 0-80 | UCF80     | 0-55 |
| 6EY6   | 0-55 | 85A2   | 0-40 | EM84   | 0-35 | UCF81     | 0-50 |
| 6F1    | 0-70 | 90A6   | 2-40 | EM85   | 1-00 | UCF82     | 0-50 |
| 6F5    | 0-50 | 90A7   | 2-50 | EM87   | 0-55 | UCH43     | 0-75 |
| 6F6G   | 0-30 | 90C1   | 0-60 | EN91   | 0-35 | UCH81     | 0-35 |
| 6F11   | 0-38 | 90CV   | 1-25 | EY51   | 0-40 | UCL81     | 0-30 |
| 6F13   | 0-38 | 807    | 0-50 | EY80   | 0-45 | UCL82     | 0-60 |
| 6F14   | 0-65 | 813    | 3-75 | EY81   | 0-40 | UCL83     | 0-80 |
| 6F15   | 0-85 | 866A   | 0-75 | EY83   | 0-55 | UFA1      | 0-60 |
| 6F18   | 0-45 | 5642   | 0-65 | EY86   | 0-40 | UF42      | 0-60 |
| 6F23   | 0-80 | 6080   | 1-50 | EY87   | 0-43 | UF43      | 0-60 |
| 6F24   | 0-75 | 6146   | 1-50 | EY88   | 0-43 | UF80      | 0-35 |
| 6F25   | 0-75 | 6380   | 1-25 | EZ40   | 0-45 | UF85      | 0-40 |
| 6F26   | 0-35 | 6870   | 2-50 | EZ41   | 0-45 | UF89      | 0-35 |
| 6F28   | 0-60 | 6930   | 2-15 | EZ50   | 0-85 | UL41      | 0-85 |
| 6J4    | 0-60 | 7199   | 0-75 | EZ51   | 0-95 | UL84      | 0-30 |
| 6J5GT  | 0-30 | 7360   | 1-80 | GY501  | 0-80 | UM54      | 0-20 |
| 6J7    | 0-45 | 7586   | 1-25 | GZ30   | 0-40 | UY1N      | 0-50 |
| 6K6GT  | 0-55 | 7886   | 1-25 | GZ31   | 0-33 | UY11      | 0-65 |
| 6K7    | 0-35 | 9002   | 0-35 | GZ32   | 0-48 | UY41      | 0-45 |
| 6K8G   | 0-35 | 9003   | 0-50 | GZ33   | 0-70 | UY82      | 0-50 |
| 6K25   | 0-75 | AZ1    | 0-45 | GZ34   | 0-80 | UY86      | 0-30 |
| 6L6GT  | 0-45 | AZ31   | 0-55 | HABCS0 | 0-40 | WZ29      | 0-60 |
| 6L7    | 0-40 | CB11   | 0-80 | HK90   | 0-35 | Z759      | 1-85 |
| 6L18   | 0-45 | CB13   | 0-90 | KT66   | 2-05 | Z803U     | 0-80 |
| 6LD20  | 0-40 | CY31   | 0-35 | KT88   | 2-00 |           |      |
| 6N7GT  | 0-40 | DAF96  | 0-42 | N78    | 1-45 |           |      |
| 6P1    | 0-60 | FABCS0 | 0-40 | PC86   | 0-60 |           |      |
| 6P25   | 1-25 | DK40   | 0-55 | PC88   | 0-60 |           |      |
| 6P28   | 0-65 | DK92   | 0-50 | PC89   | 0-60 |           |      |
| 6Q7    | 0-40 | DK96   | 0-42 | PC97   | 0-50 |           |      |
| 6SA7   | 0-40 | DL96   | 0-42 | PC90   | 0-48 |           |      |
| 6SG7   | 0-35 | DM180  | 0-65 | PC94   | 0-40 |           |      |
| 6SK7   | 0-35 | DY86   | 0-33 | PC95   | 0-40 |           |      |

# STEPHENS

ELECTRONICS  
P.O. BOX 26  
AYLESBURY, BUCKS.

SEND S.A.E. FOR LISTS  
GUARANTEE:—  
TERMS CASH WITH ORDER ONLY.  
POST AND PACKING PAYABLE  
ON ORDERS UP TO £6, AFTER  
THAT FREE, EXCEPT C.R.T's

Satisfaction or money refunded.

ALL ITEMS ADVERTISED IN LAST  
MONTH'S ISSUE ALWAYS IN  
STOCK FOR SAME DAY  
DISPATCH

## SEMICONDUCTORS BRAND NEW MANUFACTURERS MARKINGS NO REMARKED DEVICES

|        |     |        |       |       |       |        |       |        |      |       |     |
|--------|-----|--------|-------|-------|-------|--------|-------|--------|------|-------|-----|
| 2N388A | 62p | 2N3702 | 17p   | ACV18 | 25p   | AF127  | 17p   | BC184  | 22p  | BFY52 | 22p |
| 2N614  | 30p | 2N3704 | 22p   | ACV19 | 25p   | AF139  | 37p   | BC187  | 22p  | B8X21 | 37p |
| 2N697  | 20p | 2N3705 | 20p   | ACV20 | 25p   | AF173  | 45p   | BC213L | 26p  | OC25  | 50p |
| 2N698  | 20p | 2N3711 | 20p   | ACV21 | 25p   | AF179  | 45p   | BCY32  | 37p  | OC26  | 32p |
| 2N706  | 12p | 2N3819 | 35    | ACV22 | 20p   | AF180  | 52p   | BCY58  | 22p  | OC28  | 62p |
| 2N706A | 12p | 2N3826 | 30p   | ACV28 | 20p   | AF181  | 42p   | BCY70  | 20p  | OC29  | 75p |
| 2N930  | 27p | 2N3905 | 37p   | ACV40 | 20p   | AF186  | 64p   | BD115  | 78p  | OC35  | 40p |
| 2N1132 | 32p | 2N3914 | P.A.  | ACV41 | 25p   | AF239  | 42p   | BD121  | 65p  | OC36  | 62p |
| 2N1303 | 17p | R.C.A. | ACV44 | 40p   | ASV28 | 25p    | BD123 | 32p    | OC42 | 25p   |     |
| 2N1305 | 25p | 40253  | P.A.  | AD140 | 40p   | BC107  | 15p   | BD124  | 32p  | OC44  | 20p |
| 2N1306 | 25p | 40258  | P.A.  | AD142 | 58p   | BC108  | 15p   | BD131  | 37p  | OC45  | 12p |
| 2N1307 | 25p | 40458  | P.A.  | AD149 | 57p   | BC109  | 15p   | BD132  | 37p  | OC46  | 15p |
| 2N1711 | 25p | 2N4061 | 22p   | AD150 | 62p   | BC113  | 27p   | BF115  | 25p  | OC70  | 15p |
| 2N1747 | 72p | 2N4062 | 22p   | AD161 | 37p   | BC114  | 37p   | BF117  | 47p  | OC71  | 12p |
| 2N2100 | 67p | 2N4286 | 17p   | AD162 | 37p   | BC115  | 32p   | BF160  | P.A. | OC72  | 12p |
| 2N2614 | 30p | 2N4281 | 17p   | AF102 | 85p   | BC116  | 62p   | BF161  | P.A. | OC74  | 32p |
| 2N2646 | 57p | AC107  | 30p   | AF106 | 42p   | BC116A | 37p   | BF168  | 35p  | OC75  | 22p |
| 2N2905 | 40p | AC117  | 80p   | AF114 | 25p   | BC117  | 39p   | BF187  | 25p  | OC76  | 22p |
| 2N2926 | 40p | AC126  | 20p   | AF115 | 30p   | BC118  | 32p   | BF173  | 32p  | OC77  | 27p |
| Green  | 14p | AC127  | 25p   | AF116 | 25p   | BC134  | 57p   | BF178  | 35p  | OC78  | 25p |
| Yellow | 12p | AC128  | 20p   | AF117 | 25p   | BC135  | P.A.  | BF179  | 72p  | OC81  | 20p |
| Orange | 12p | AC154  | 25p   | AF118 | 60p   | BC136  | P.A.  | BF180  | 35p  | OC81D | 20p |
| 2N3053 | 27p | AC176  | 25p   | AF119 | 20p   | BC137  | P.A.  | BF181  | 32p  | OC83  | 25p |
| 2N3055 | 75p | AC187  | 62p   | AF124 | 22p   | BC138  | P.A.  | BF184  | 25p  | OC84  | 25p |
| 2N3391 | 20p | AC188  | 37p   | AF125 | 20p   | BC142  | 30p   | BF192  | 25p  | OC89  | 20p |
| 2N3392 | 20p | ACV17  | 27p   | AF126 | 20p   | BC143  | P.A.  | BF195  | 22p  | OC140 | 32p |

# SHORT WAVES

## MONTHLY NEWS FOR DX LISTENERS

THE first report this month comes from a new reporter D. A. Hairon from Jersey in the Channel Islands. The equipment used was a Codar CR70A receiver, a 50ft long wire and a 19 metre band dipole. This combination enabled him to hear the following stations:—

- 9480 Radio Peking in English at 0130.
- 9625 CBC, Canada in English at 0200.
- 11710 R. Nacional de Espana in Spanish at 0130.
- 11720 CBC, Canada in English at 0200.
- 11730 R. Nederland, Bonaire, English at 0200.
- 11745 HCJB, Quito, Ecuador, English at 0000.
- 11775 TWR, Bonaire in Spanish at 0215.
- 11810 RAI, Rome in English at 0100.
- 15195 R. Ankara, Turkey, Turkish at 1600.
- 15250 RSA, South Africa in French at 1856.
- 15300 HCJB, Quito, Ecuador in Spanish at 2145, and in Portuguese at 0000.
- 15305 SBC, Switzerland in English at 1315.
- 15345 Radio Kuwait in English at 1630.
- 15355 ABC, Australia in English at 0530.
- 17655 R. Cairo, U.A.R. in English at 1730.
- 17715 ABC, Australia in French at 2315.
- 17810 R. Nederland, Bonaire in Spanish at 2130.
- 17830 R. Lebanon in English at 1830.
- 17825 NHK, Japan in English at 0800.
- 21525 WNYW, U.S.A. in English at 1800.
- 21640 R. Nederland, Bonaire, English at 1830.
- 25730 R. Norway in English at 1200.

Ray Warren of Bury St. Edmunds has used his Koyo 1661 receiver to good effect and heard the following:—

- 3980 Voice of America in English at 1720.
- 5970 R. Free Europe, Germany at 1450.
- 6075 WNBC, New York, news at 1630.
- 6085 R. Nederland in English at 0930.
- 9030 R. Peking in English at 2050.
- 9390 R. Tirana, Albania in English at 1530.
- 9750 SBC, Switzerland, news in English, 1540.
- 15300 HCJB, Quito, Ecuador, English news, 1410.

Peter Hall of Pocklington, Yorkshire, has a Meridian 10 transistor superhet and a 50 foot aerial which enabled him to hear:—

- 6070 R. Sofia, Bulgaria in English at 1930.
- 6130 HCJB, Quito, Ecuador in English at 0800.
- 7275 RAI, Rome in English at 1940.
- 9550 Radio Finland in English at 1815.
- 9580 BBC, Ascension Island relay at 2115.
- 9620 R. Belgrade, Yugoslavia at 1800.
- 9625 Israel B.C. in English at 2045.
- 9630 R. Trans Europe, Portugal at 2100.
- 9700 R. Sofia, Bulgaria in English at 2140.
- 11620 AIR, Delhi in English at 2010.
- 11672 R. Pakistan in English at 2030.

## THE BROADCAST BANDS

Malcolm Connah

Frequencies in kHz ● Times in GMT

- 11755 R. Finland in English at 0930.
- 11915 BBC, Cyprus relay at 1645.
- 11965 TWR, Monaco in English at 1700.

Ross Pullen of Crawley used his Murphy A72 communications receiver and a 100 foot long-wire to hear some interesting stations:—

- 6015 VOA, Rhodes, music and talk at 2200.
- 6145 R. Nacional, Brazil in Spanish at 2245.
- 9510 R. Noumea, New Caledonia, French at 0910.
- 9605 HCJB, Quito, Ecuador, English at 0730.
- 9745 R. Baghdad, Iraq in English at 2015.
- 9775 R. Diffusion-Television Nationale Congolaise, African music at 2200.
- 11672 R. Pakistan, English at 2002.
- 11965 Rwanda relay of Deutsche Welle at 2037.
- 17705 R. Havana, Cuba, Spanish news at 2015.

F. Wall of Walthamstow, London, E.17, has a homebrew 5-valve superhet and a 20 foot wire aerial, this equipment enabling him to hear:—

- 6035 R. Warsaw with Polish news at 1620.
- 6070 R. Sofia, Bulgaria in English at 1930.
- 9912 AIR, Delhi English news at 2000.
- 9630 R. Sweden 'Calling DXers' at 1230.
- 9660 R. Trans Europe in English at 1250.
- 9833 R. Budapest, Hungary, requests at 1945.
- 11735 R. Belgrade, Yugoslavia, English at 1530.
- 11740 ABC, Australia at 1530.
- 11755 R. Finland in English at 1500.
- 11765 ABC, Australia, sports programme at 0830.
- 11955 BBC, Malaysian relay at 1815.
- 15325 CBC, Canada, sports news at 1200.
- 21460 HCJB, Quito, Ecuador sign-on in French at 2015.
- 21535 RSA, South Africa, English news at 0930.
- 21595 CBC, Canada with news at 1910.
- 25790 RSA, South Africa, English news at 1500.

Stephen Mathews of Hull with his Bush 4-valve domestic receiver and 90 foot loft aerial heard the following:—

- 9660 YVLM Radio Rumbos, Venezuela at 0320.
- 9833 R. Espana Independiente, clandestine at 2230.
- 11765 ZYB8, R. Diffusion, Brazil at 0220.
- 11795 WINB, Red Lion, U.S.A. English at 2100.
- 11815 ZYW24, R. Brazil Central at 0045.
- 15260 FEBA, Seychelles testing at 1700.
- 17890 BED-40, Taiwan, weak at 0330.
- 21690 WIBS, Grenada in English at 1945.
- 21720 R. Ghana in English at 1445.

Reports should arrive by the 15th of the month and be addressed to the author at 5 Ranelagh Gardens, Cranbrook, Ilford, Essex.

# SHORT WAVES

## THE AMATEUR BANDS

David Gibson, G3JDG

Frequencies in kHz • Times in GMT

**H**IGH noise levels have been the main complaint this past month with many people confessing to giving up and going off to watch television (sacrilege!). Despite these conditions there was still a large number of listeners who persisted, despite the noise, and managed to log some worthwhile DX as reward for their labours. Just goes to show, while you are busy moaning about the QRM and QRN, someone else is just getting on with it and working half the world.

News that G5ZT has received slow-scan television pictures from FG7XT in Guadeloupe makes you think. Many people would be only too pleased to hear an FG7 on c.w. **John Rimmer** (Deal) warns that VS9MF is on from Gan—a small island in the Maldiv group of islands. Listen on 14 and 21MHz; sorry, no specific freqs given.

No activity reported on ten metres this month and it rather looks as though everyone has migrated to 14MHz. This latter band is an early morning/late night affair nowadays with everything dying out from mid-morning to late afternoon. On fifteen metres the same remarks apply, although occasionally South American stations appear during the daytime. For those who would like to persist on 28MHz, suggested time for a listen is from 1400 to 1600hrs.

Incidentally, this is one of the best bands on which to play with aerials since these normally work out to a very reasonable size. A quarter wave vertical is only around the 8ft. 6in. mark, exact size depending upon frequency since ten metres is one of the widest bands we have among those l.f. of 144MHz. If sunspot counts are any indication, then September would be a very good time for ten metres.

A few contests this month just to get your ears in trim for the long winter evenings. September 11 and 12, WAE phone contest; 12, 3.5MHz Field Day; October 2 and 3, u.h.f./s.h.f. Field Day; 2 and 3, Oceania contest—a chance to bag a nice list of VK/ZL callsigns; 2 and 3, IARU Region 1 u.h.f./s.h.f. contest. Don't forget the Cumulative Activity on 70MHz from October 9 to December 30. This is our "use or lose" band and all support is very welcome, if not essential. You might try listening for some of the RAEN activity on four metres. The Radio Amateur Emergency Network has numerous "local" groups and the favourite band is 70MHz. How about listening out for your local group, or perhaps even joining them? Name and address of the Secretary of RAEN is; E. Bassett, 57 Upper St Helen's Road, Hedge End, Southampton, SO3 4LG.

## Logs

A solitary log for two metres arrived this month from **David Sheekay** (Ashford). Gear is a super-regen using three transistors and an i.c. audio amplifier, homebrew, and antenna is described as "telescopic". Stations logged include; G2JF, G2VB, G3EFX/P, G3JXN, G3LTF, G3TDP/M, G3UNT,

G4AAR, G4AAZ/M, G5OX, G8BYC, G8CCO, G8EBV, G8ELW and F0UJ. What about it all you converter and superhet types—you can't let a super-regen show you up, or can you?

**Richard Mortimore** (Cardiff), is now up to 20 w.p.m. at c.w. and says that he recommends all s.w.l.s to learn morse. Small sample from his list of c.w. pickings on 21MHz includes; CR6ID, JA3IL, KZ5BB, PY2EYE, PY4UK, W4NZK, WB4QVQ.

**Mark Marsden** (Ilford) uses a cassette tape recorder which has its input wired in parallel with the headphones. He claims this is very useful for checking calls heard against calls logged afterwards. Seems a very good idea. Calls heard, checked, recorded and logged on 14MHz include signals from; CE5ID, JA3JH, KV4HE, KZ5JF, PY2ZAC, PY4AEB, SV0WZ, VK3ART, VK4PJ, VP2AA, WA1DYR/MM, WB6YIY/MM, YV5CPA, YN2SC, ZL5ISJ, 4X4JU, 4X4OC, 9Q5IA.

"My uncle has given me all the PWs he can spare", writes **Kevin Davies**. Receiver is an R107 and the antenna 120ft. l.w. The following were in evidence on 14MHz s.s.b.; CT1ZE, EA3KO, EA4LM, EL2C, EL4A, HR3VSJ, JA1VK, K1WPS/CT1, LU4DMG, W1CMG/P1, W1MYA/MM, WA5KHM, WB6YIY, 4U1ITU, 4X4HT.

**Paul Newman** is at a new QTH which is some 680ft. a.s.l. Antenna at present is an 80ft. end fed and the receiver a modified BC348R ex G3HXS. With this gear, and from his lofty perch at Aylesbury, Paul bagged these on 14MHz; OD5BV, PY6AT, PY8LM, (Sao Luis Island), WA5STY/P/YV5 (Caracas) 4X4BL, 4X4GV, 5Z4KL, 9K2AL.

**Jim Martin** says that as it's the start of his holidays he thought he'd send in a report. (May the sun shine on your antenna, Sir.) His recently-purchased HA500 is nourished with an inverted V and rewards on 14MHz were; CR6EF, CR7IK, EL2CY, FP8CS, HC6CB, JA3IXL, JA4EDY, JA6FUV, JY9XL, KG4AN, KH6FP, KH6BB (Kure Island), KL7DIV, KR6US, KV4AD, KZ5AO, LG5LG, MP4MBC, PY1FN, PJ2MI, PZ1AD, PZ1AW, TG9GF, VK3JS, VP2MO, VQ9R, VS5CB, VS9MT, VU2BEZ, YV5EC, ZE1DO, ZP5GU.

On 3.5MHz c.w. it was UA1YUZ. Up on 7MHz, signals came from CX6CG, LX1BJ, PYCVX, PZ1AX, UW3NG, ZB2A, and ZP5AR. Gear is a JR500SE with 132ft. end fed. Operator's ears belong to **Julian Iredale** (Llandudno), and up on 14MHz s.s.b. Julian heard CR6GA, HV3SJ, OG5A, (Finnish Field Day prefix), PY2ZAC, PY4ATL, PZ1DL, TI2J, 5A4DL.

**P. McKay** advises that he never notices any logs for 7MHz in the Amateur Bands, and sends in a list of G-stations heard on this band. Well, the G's must have been working someone, so how about a listen this month?

*Logs, in alphabetical order please, to arrive by the 15th of the month to:*

**12, Cross Way, Harpenden, Herts.**

# BUDGET HIGH-FIDELITY STEREO SYSTEMS



**PREMIER STEREO SYSTEM "ONE"** Consists of an all transistor stereo amplifier, Garrard 2025 T/C auto manual record player unit fitted stereo mono ceramic cartridge with diamond stylus and mounted in teak finish plinth with perspex cover and two matching teak finish loudspeaker systems. Absolutely complete and supplied ready to plug in and play. 2000 amplifier has an output of 5 watts per channel with inputs for pick-up, tape and tuner also tape output socket. Controls: Bass, Treble, Volume, Balance, Selector, Power on/off. Solid teak cabinet with aluminium front panel. Size 12½" x 4½" x 3½" high (Amplifier available separately if required £14.95 Carr. 40p).  
**PREMIER STEREO SYSTEM "TWO"**, as above but with Garrard SP25 MK III—ONLY £47. Carr. £1.75

**ONLY  
£40-95**  
carr. £1.75

**ONLY  
£57-75**  
carr. £1.75

**PREMIER STEREO SYSTEM "THREE"** This consists of KLINGER KC903 stereo amplifier giving 6 watts rms per channel with Bass, Treble, Volume and Balance Controls. Inputs for Magnetic and ceramic pickup, tuner, tape in and out. Stereo earphone socket. Garrard SP20 Mk III in teak finish plinth with cover and fitted Sonotone 9TAHC diamond stereo cartridge. A pair of HMF Speakers size 16½" x 10½" x 9" fitted EMI units complete the matching system.  
**ONLY £67-75 Carr. £1.75**

**ALL SYSTEMS SUPPLIED WITH FREE LEADS AND PLUGS**

## PREMIER HI-FI OFFERS!

- Rogers Ravensbrook II Stereo Amplifier in teak case (List £52.50) **£39-50**
- Rogers Ravensbourne Stereo Amplifier in teak case (List £64) **£49-00**
- Metrosound ST20 Stereo Amplifier in teak case (List £36) **£24-50**
- Garrard SP25 III less cartridge **£11-90**
- Garrard AP76 less cartridge **£19-50**
- Garrard 2025 T/C with Sonotone 9TAHC Diamond Cartridge **£8-97**

### SPECIAL BARGAINS!

- Garrard 2025 T/C with Sonotone 9TAHC Diamond Cartridge ready wired in teak plinth with cover **£14**

Carriage and Insurance 50p extra any item.

## SP25 MKIII SPECIAL!



GARRARD SP25 MK III SINGLE RECORD PLAYER FITTED AT66 MAGNETIC STEREO CARTRIDGE as available. COMPLETE IN TEAK PLINTH WITH RIGID PERSPEX COVER.  
Total list price over £29.

**PREMIER PRICE**

**£19-90**

P. & P. 50p.



### HI-FI STEREO HEADPHONES

Designed to the highest possible standard. Fitted 2½in speaker units with soft padded ear muffs. Adjustable headband. 8 ohms impedance. Complete with 8ft lead and stereo jack plug.

**£2.47 P. & P.**

25p.

STEREO STETHOSCOPE SET Low imp. £1.25

P. & P. 10p

MONO STETHOSCOPE SET Low imp. 52p. P. & P. 10p.



### E.M.I. 13x8in.

### HI-FI SPEAKERS

Fitted two 2½in tweeters and crossover network. Impedance 8 or 15 ohm. Handling capacity 10W. Brand new.

**£3-47 P. & P. 40p**

## PREMIER QUALITY MICROPHONES



Precision made, beautifully designed and offering reliability at reasonable price.

**FANON MKO-47 MINIATURE DYNAMIC**  
Frequency response 60-13,000 Hz. Impedance 50K ohms (-50 db). Can be used with stand, hand held or around neck. Diecast body satin chrome finish. Features removable windscreen. Complete with 8ft. cable, stand adaptor and Lavalier cord.

**PREMIER PRICE £5-97. P. & P. 20p.**  
**FANON MKO-46 3-WAY DYNAMIC**  
Frequency response 100-10,000 Hz. High impedance. Complete with 8ft. cable, and table stand.

**PREMIER PRICE £2-87. P. & P. 20p.**  
**FANON MKC-54 DYNAMIC**  
Frequency response 60-12,000 Hz. Impedance 50K ohms (-60 db) and 150 ohms (-71 db). On/Off switch. Complete with 20ft. cable and stand adaptor.

**PREMIER PRICE £3-97. P. & P. 20p**



### TAPE CASSETTES

|      |            |     |             |
|------|------------|-----|-------------|
| C60  | (60 min.)  | 37p | 3 for £1.05 |
| C90  | (90 min.)  | 62p | 3 for £1.80 |
| C120 | (120 min.) | 87p | 3 for £2.55 |

P. & P. 5p.

**FREE CASSETTE HEAD CLEANER with every 10 cassettes purchased.**

All cassettes can be supplied with library cases at 3p. extra each

### VERITAS V-149 MIXER

Battery operated 4-channel audio mixer providing four separate inputs. Size 6 x 3 x 2in. suitable for crystal microphone low impedance microphone, with transformer, radio, tape, etc. Max. input 1.5v. Max. output 2.5v. Gain 6 dB. Standard jack plug socket inputs, phono inputs. Attractive teak wood grain finish case.



**MONO MODEL £3**

**STEREO MODEL £3.47 P. & P. 12p**



**MULTIMETER 20,000 O.P.V.**  
Features large easy-to-read meter, wide choice of ranges. With test leads, batteries and manual. Size: 4½" x 3½" x 1". RANGES D.C. Voltages 0-5-25-50-250-500-2500v. A.C. Voltages 0-10-50-100-500-1000v. D.C. Current: 0-50µA-2-5mA-250mA. Resistance: 0-500 ohms 0-5 megohms (300 ohms and 20 Kohms, at centre scale). Capacity: 10 µF to 0.001µF, 0.001µF to 1µF. Labels -20 to +220B. £4-90. P. & P. 17p.

## "VERITONE" RECORDING TAPE

**SPECIALLY MANUFACTURED IN U.S.A. FROM EXTRA STRONG PRE-STRETCHED MATERIAL. THE QUALITY IS UNEQUALLED.** TENSILISED to ensure the most permanent base. Highly resistant to breakage, moisture, heat, cold or humidity. High polished splice free finish. Smooth output throughout the entire audio range. Double wrapped-attractively boxed.

|              |               |                               |                         |
|--------------|---------------|-------------------------------|-------------------------|
| LPS 3" 350'  | P.V.C.        | 28p                           | 51" 1200' POLYESTER 75p |
| TT3 3" 450'  | POLYESTER 37p | DT8 51" 1800' POLYESTER £1.12 |                         |
| DT3 3½" 600' | POLYESTER 87p | TT3 51" 2400' POLYESTER £1.87 |                         |
| SP5 5" 600'  | P.V.C. 42p    | SP7 7" 1200' P.V.C. 75p       |                         |
| LP5 5" 900'  | P.V.C. 50p    | LP7 7" 1800' ACETATE 75p      |                         |
| DT5 5" 1200' | POLYESTER 75p | DT7 7" 2400' POLYESTER £1.25  |                         |
|              |               | TT7 7" 3800' POLYESTER £2.50  |                         |

**TAPE SPOOLS 3" 5p, 5½", 5", 7", 8p, Post and Packing 3" 5p, 5½", 5", 7", 10p. (3 reels and over Post Free).**



# PREMIER RADIO

10 & 23, TOTTENHAM COURT ROAD, LONDON, W.1 TEL: 01-636 3451/2639  
HEAD OFFICE & MAIL ORDER DEPT. 23, TOTTENHAM CT. RD. TEL: 01-636 3451





# TECHNICAL TRAINING in radio television and electronics

Whether you are a newcomer to radio and electronics, or are engaged in the industry and wish to prepare for a recognized examination, ICS can further your technical knowledge and provide the specialized training so essential to success. ICS have helped thousands of ambitious men to move up into higher paid jobs—they can help you too! Why not fill in the coupon below and find out how?

Many diploma and examination courses available, including expert coaching for:

- C. & G. Telecommunication Techns'. Certs.
- Radio Amateurs' Examination
- Radio Operator Certificates
- General Certificate of Education, etc.

Now available Colour T.V. Servicing

Examination Students coached until successful

## NEW SELF-BUILD RADIO COURSES

Learn as you build. You can learn both the theory and practice of valve and transistor circuits, and servicing work while building your own 5-valve receiver, transistor portable, and high-grade test instruments—all under expert tuition. Transistor Portable available as separate course.

## POST THIS COUPON TODAY

for full details of ICS courses in Radio, T.V. and Electronics.



### INTERNATIONAL CORRESPONDENCE SCHOOLS

Dept. 171, Intertext House, Stewarts Road, London, S.W.8 4UJ  
Please send me the ICS prospectus—free and without obligation.  
(state Subject or Exam).....

NAME .....  
(BLOCK CAPITALS PLEASE)

ADDRESS .....

AGE.....OCCUPATION..... 10/71

**INTERNATIONAL CORRESPONDENCE SCHOOLS**

### OSCILLOSCOPES

|                                                                             |      |
|-----------------------------------------------------------------------------|------|
| E.M.I. WM18. Complete with Dual Trace Plug-in Amp/Differential Plug-in Amp. | £175 |
| SOLARTRON CD.1220. With Wide Band Unit                                      | £190 |
| SOLARTRON CD.1220. With Dual Trace Unit                                     | £220 |
| SOLARTRON CD.1220. With Differential Amp Unit                               | £240 |
| SOLARTRON CD.7115.2. Double Beam.                                           | £80  |
| CAWKELL REMSCOPE S.O.I. Storage Oscilloscope                                | £200 |
| E.M.I. W.M.8. Complete with Amplifier Type 8                                | £55  |

### TEST GEAR

|                                                                       |      |
|-----------------------------------------------------------------------|------|
| WAYNE KERR. Universal Bridge Type B.221                               | £65  |
| MARCONI Q Meter Type TF 329G                                          | £45  |
| MARCONI Video Oscillator Type TF 885A 25HZ-5MHz                       | £45  |
| MARCONI Vacuum Tube Voltmeter TF 1041A.                               | £80  |
| MARCONI FM/AM Signal Generator TF995A/4                               | £175 |
| POWER UNIT. 240V. a.c. 1/F.D.C. Output 400V 170mA/6-3V 3A.            | £10  |
| R.F. GENERATOR. 200 Mc/s. 275 Watts                                   | £25  |
| R.F. GENERATOR. 25 Watts                                              | £15  |
| SERVOMEX CONTROLS LTD. Motor Controller Type MC47 Complete with Motor | £65  |

### T.V. CAMERA LENSES

|                                                                                     |          |
|-------------------------------------------------------------------------------------|----------|
| RANK TAYLOR HOBSON VIDITAL LENSES. Standard -C" Mounts. Focal lengths 2cm, 5cm, 8cm | £25 each |
| R.C.A. AR88. Receiver                                                               | £40      |

### MINIATURE GEARED MOTORS

|                                                            |               |
|------------------------------------------------------------|---------------|
| 1 R.P.M. HAYDEN. 240V a.c. Clockwise Rotation              | } .. 80p each |
| 1/5 R.P.M. CROUZET. 240V a.c. Anticlockwise Rotation       |               |
| 2 R.P.M. CROUZET. 20V a.c./12V d.c. Anticlockwise Rotation |               |

### RELAYS

|                                                                       |                                          |
|-----------------------------------------------------------------------|------------------------------------------|
| SIEMENS/VARLEY PLUG-IN. Complete with Transparent Dust Cover          | 2 Pole C/o 35p each. 4 Pole C/o 50p each |
| S.T.C. Miniature Sealed Relays. 6V, 12V, 24V, 48V. 2 Pole C/o         | 50p each                                 |
| G.P.O. Relays, 2000Q2.                                                | 2p C/o 50p. 4p C/o 60p each              |
| HEAVY DUTY. Relays 5A and 10A Contacts 12V, 24V, d.c. 110V, 240V a.c. | 2p. C/o .. 90p each                      |
| LATCHING RELAYS. B. & R. Type HO2/T498 2p. C/o                        | 95p each                                 |

### SOLENOIDS

|                                |             |
|--------------------------------|-------------|
| 12V. d.c. 2 1/2" x 1 1/2" Dia. | .. 50p each |
|--------------------------------|-------------|

### WIRE WOUND POTENTIOMETERS

|                                                        |                 |
|--------------------------------------------------------|-----------------|
| COLVERN. RELIANCE. All Values from 1Ω-100KΩ. Brand New | .. 19p each     |
| 360° WIRE WOUND POTS. COLVERN CLR/6605/418 10KΩ        | } .. £1.50 each |
| CLR/6605/ 18 100KΩ                                     |                 |
| BOURNS. 10 Turn Pots. 10KΩ ± 5% LIN 0-25%              | £1.98 each      |

### ILLUMINATED PUSH BUTTON SWITCHES

|                          |             |
|--------------------------|-------------|
| Non-Locking Only. 2p C/o | .. 35p each |
|--------------------------|-------------|

### PUSH BUTTON SWITCHES

Multibank Push Button Switch assemblies now in Stock. Any combination, latching, non-latching, push-push, push to change over, push to hold etc.

|         |                 |
|---------|-----------------|
| 2p. C/o | 20p per button. |
| 4p. C/o | 30p per button. |
| 6p. C/o | 40p per button. |

### MULTIPIN PLUGS AND SOCKETS

PAINTON/JONES 2/4/6/8/12/18/24/33 Way.  
P.E.T., B.N.C., AMPHENOL, CANNON, D.I.N., Plus Complete Audio Range.

### TRANSFORMERS

|                                                            |                     |
|------------------------------------------------------------|---------------------|
| D. C. TIBBLES & CO. PRI. 0-100-110-220-240V. SEC. 12V. 20A | £6-50 each          |
| MINIATURE TRANSFORMERS. PRI. 240V SEC 12V 100mA            | } AH Types 65p each |
| 2" x 1 1/2" x 1 1/2"                                       |                     |
| PRI. 240V SEC 0, 20V, 30V 100mA                            |                     |
| PRI. 240V SEC 0, 18, 36, 0, 18, 36 100mA                   |                     |
| SHROUDED TRANSFORMERS. PRI. 0-120-240V SEC. 24V 1/2A       | £1.25 each          |
| PRI. 0-240V SEC 20V 1A                                     | £1.60 each          |
| C-CORE TRANSFORMERS. PRI. 240V SEC 0, 7.1, 15V 1A          | £1.20 each          |
| HEATER TRANSFORMERS. PRI. 0-110-200-220-240 SEC 6-3V 3A    | £1.00 each          |

### ALARM BELLS

|                                                           |            |
|-----------------------------------------------------------|------------|
| Suitable for Burglar Alarms. AGRO Type 4145 200/250V a.c. | £3-50 each |
|-----------------------------------------------------------|------------|

### PANEL METERS

|                                                               |              |
|---------------------------------------------------------------|--------------|
| SIFAM MOVING COIL 1mA Size 4 1/2" x 4"                        | £3-25 each   |
| SIFAM MOVING COIL 100μA Size 3 1/2" x 3"                      | £3-00 each   |
| TAYLOR MOVING COIL 50-0-50μA Edgewise 2 1/2" scale            | £4-25 each   |
| ERNEST TURNER 270° Movement/Centre zero Circular 0-5-0-5 mA   | } £2-00 each |
| 2 1/2" Dia.                                                   |              |
| ERNEST TURNER 270° Movement/Centre zero Circular 1-0-1mA      | } £4-25 each |
| 3 1/2" Dia.                                                   |              |
| SANGAMO-WESTON ILLUMINATED METER 500μA F.S.D. 4 1/2" x 3 1/2" | £3-90 each   |
| SANGAMO WESTON. 50μA F.S.D. 4 1/2" x 3 1/2"                   | £4-75 each   |

We also have a large number of assorted meters of different shapes/sizes/movements in stock.

|                                                              |             |
|--------------------------------------------------------------|-------------|
| <b>SOUND-TO-LIGHT MODULES SUITABLE FOR DISCOTHEQUES ETC.</b> |             |
| SINGLE CHANNEL 750 Watt Model                                | £6-00 each  |
| THREE CHANNEL MODEL                                          | £18-00 each |
| 150W. LIQUID OIL WHEEL PROJECTORS COM-<br>PLETE WITH WHEEL   | £35-00 each |
| EXTRA WHEELS 6" Dia                                          | £6-00 each  |

### COMPONENTS

METAL OXIDE RESISTORS. 2%. T.R.5 Complete Range always in Stock. 1 off 5p each. 100 off 81p each.  
MULLARD ELECTROLYTIC CAPACITORS. Complete Range always in stock.  
MULLARD POLYESTER CAPACITORS. Complete Range always in Stock.  
LEMCO SILVER MICA CAPACITORS. Complete Range always in Stock.  
POLYETHYLENE CAPACITORS. Complete Range always in Stock.  
WIREWOUND RESISTORS. 1W, 3W, 6W, 12W, 15W, 30W. Complete Range always in Stock.  
SEMICONDUCTORS. Transistors, Diodes, Rectifier Blocks, Thyristors, U.J.T.'s  
Diodes, Triacs, F.E.T.'s, Zeners, Photocells etc.  
10% DISCOUNT On any Cash Sale for Customers Presenting this Advertisement. 10% DISCOUNT

## C. T. ELECTRONICS

267, ACTON LANE, LONDON, W.4


01-994-6275

Nearest Underground—Chiswick Park (District Line), Acton Town (Piccadilly Line)—  
Bus Routes E3, 88, 207, 15, 7, 260.

(Please note: As yet we do not have a catalogue available. Any queries please phone or  
call at the above address).

BUSINESS HOURS: MON.-SAT. 9.30 a.m.-6 p.m. WED. 9.30 a.m.-1 p.m.  
WANTED. SURPLUS OR REDUNDANT COMPONENTS AND TEST EQUIPMENT

# GOING BACK...

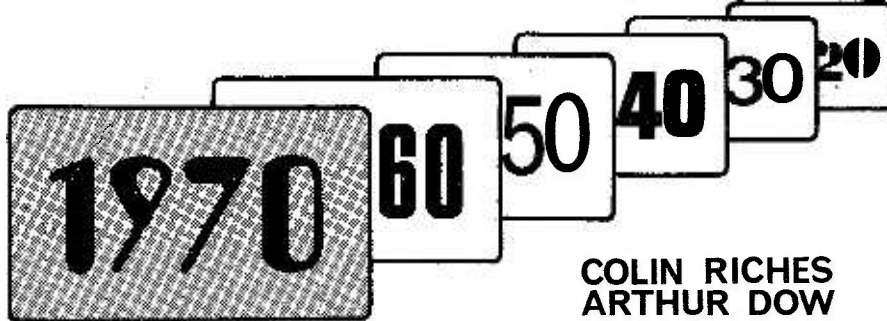

**M**ANY readers have written to ask us if we can suggest any gramophone records that may help them to bring alive even more vividly the days of vintage radio. After a certain amount of research we have discovered that Fountain Press, the book publishers, have now announced a new "Fountain" record label of Vintage Jazz music. The first 12in. LP releases feature historic jazz and blues recordings but future plans include Music Hall, Opera and other music of the "Good Old Days".

The records are housed in attractive double sleeves which open, displaying an authentically documented note section with accurate historical background information and photographs.

The first two releases are: "Original Dixieland Jazz Band and the Louisiana Five"—from the extremely rare Aeolian sessions of 1917 (catalogue number FJ-101). "Ladd's Black Aces—Vol. 1"—the first 16 sides recorded by another pioneer white jazz band during 1921-1922 (Cat. No. FJ-102). Following soon are "Naylor's Seven Aces" (c 1923-4). "Jelly Roll Morton" 1923-4 piano solos. "Lovie Austin's Blues Serenaders" (1924-6), and "Annette Hanshaw. Vol. 1"—Miss Hanshaw enjoyed public acclaim as a singer of popular songs in the 1920's and 1930's and her records are great collectors' items today.

These records are available from record shops at £2.10 or direct at £2.25 which includes post and packing, from *Fountain Records, 46 Chancery Lane, London WC2A 1JU*.

If you have any questions or queries on these records or any other Vintage records or performers please write to us at *Practical Wireless* and we'll do our best to help you.

## The Mystery of the ST.200

We would, at this point, like to thank the many enthusiasts who have been kind enough to write and help us try to clear up the mystery of the missing John Scott Taggart design "ST.200" mentioned in "Going Back", August 1971.

One theory put forward by **Mr. F. W. Snow**, Belper, Derby, is that there never was a design called the ST.200 but one called "The ST Twin"—a 2-valve reflex. It was published in *The Wireless Constructor* and not the *Popular Wireless* magazine during the late 1924's and early 1925's.

**Mr. J. Crossley** hailing from Failsworth, Manchester, also maintains that the ST.200 never existed. He

says that J.S.T. visited the United States just after the advent of the ST.100. On his return, he was full of enthusiasm about a gentleman by the name of Armstrong, and *Popular Wireless* published a circuit by this man which J.S.T. had brought back with him. It was the "Armstrong Regenerative Circuit". J.S.T. then went on to publish the ST.300 design, so it appears that Armstrong's receiver may have taken the place of the missing ST.200.

**Mr. A. H. Jenkins**, Dringhouses, York, writes to say that as far as he recollects, the ST.200 may well have been just a mains-operated version of the ST.100 and therefore did not differ operationally from that design. It did however, need an extra valve. Mr. Jenkins also informs us that the S.T. series did not start at ST.100, although this was the most famous. He says that he used to have a limp covered book of J.S.T. circuits which started at crystal sets and worked up through one valvers. He seems to remember an ST.37 which was quite well-known at the time.


## Vintage Sets

**Mr. William Pozniak**, from 37 Manley Road, Oldham, Lancashire, has loaned us some photographs. He says that for three years he has been routing through old cellars and derelict radio shops throughout the North (we hope you came out for food now and again, Mr. Pozniak) and has produced the collection of Vintage gear shown in the first picture. He says that it takes him most of his time to strip down and restore these sets to as near as possible their original condition. The sets he has are as follows: The Burndept Screened Four, The Burndept Portable Five, the Burndept Ethophone Five and the Burndept Ethophone Two.


Mr. Pozniak believes there were about 20 Burndept receivers. This figure is agreed by Mr. Keith Lancaster who we mentioned some time ago as wanting to start a Vintage Radio Club. Incidentally, response has not been too good and if readers are interested in such a Club, would they please contact *Keith Lancaster, 40 Great Gardens Road, Hornchurch, Essex*.

The rest of Mr. Pozniak's collection contains a Marconiphone Type 32 three valver, a domestic Cossor two valver, a small set in a metal case named a GECOPHONE Victor 3 and a few home-constructed receivers.

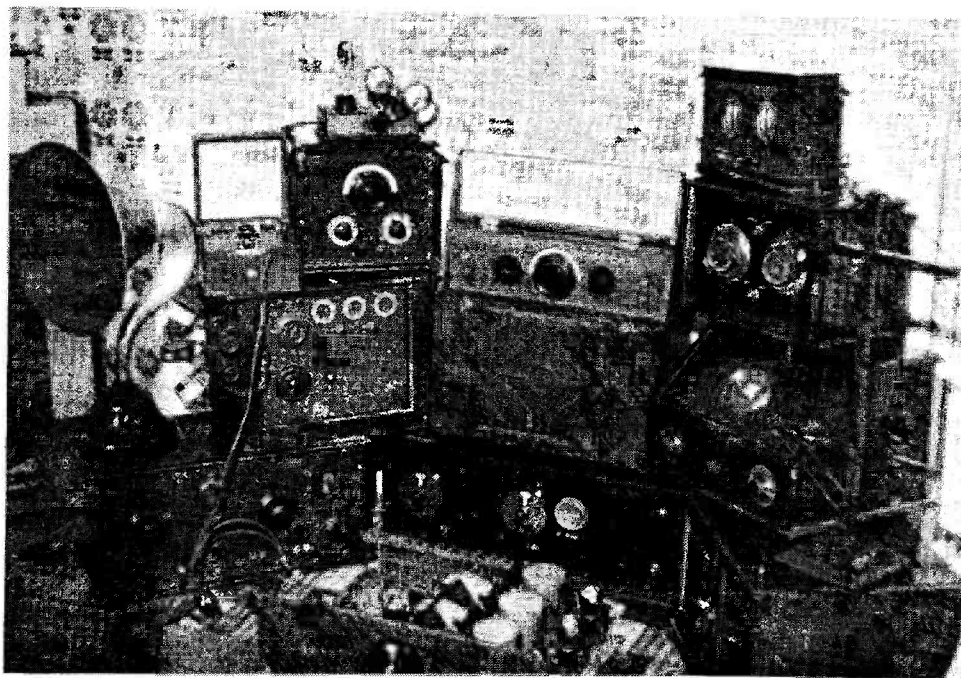The receiver shown in the second picture is a



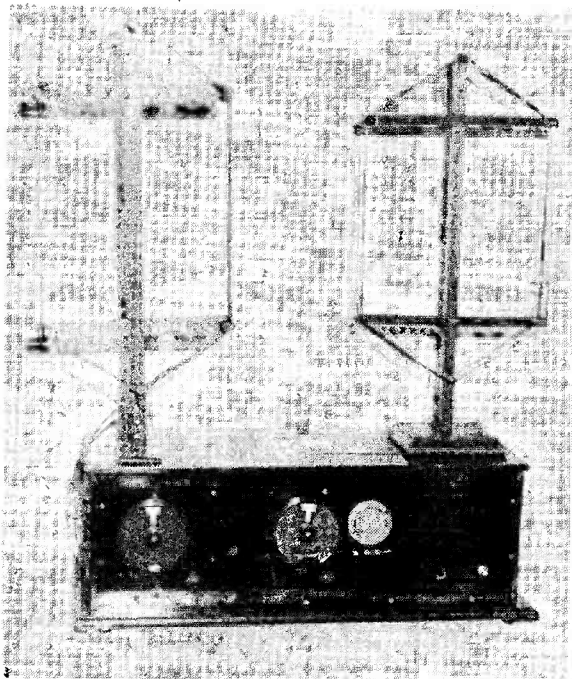
An overall view of Mr. Pozniak's collection of Burndept receivers. The small receiver shown at the top centre of the picture and the set in the centre of the picture together with frame aerials are shown enlarged below.



The James Super Six All Waver (c 1927).

1927 James Super Six All Waver (medium, long and short). The reader says that he purchased this set from an old radio shop which was a booming concern in the 1920's, together with a BTH horn speaker, and the person who sold it to him, told him, as he removed the set from the dusty shelf, that he was the first person to touch the set in 40 years.

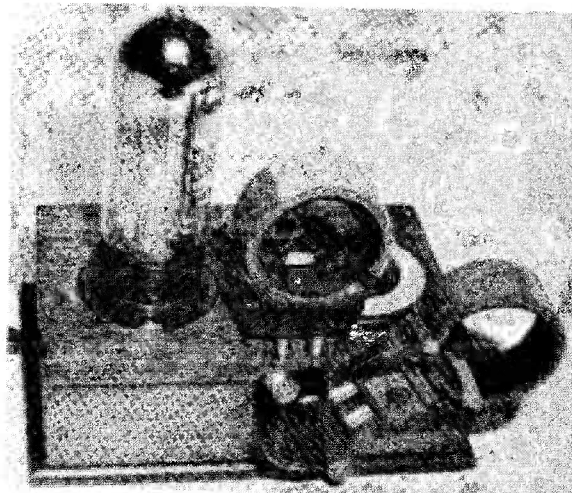The neat little receiver shown in the third photograph seems to Mr. Pozniak to be an unusual type, for he says that there appear to be two resistors and



Louwe receiver with encapsulated components.

two capacitors encapsulated in glass tubes which have then been assembled inside the glass envelope of the valve. The make on the case reads "Louwe Radio Berlin" and on the valve it states "Louwe Radio British Made". This set is in working order on headphones although it was originally made to drive some sort of speaker. The reader would like to know the date and origin of this set if anyone can help him and he would also be interested if anyone could supply him with original Burndept valves for any of their makes of receivers.

#### TITANIC DISASTER

We would like to thank the many readers who have written to us about the Titanic Disaster. We are gradually answering all the letters and we hope you will bear with us.

## SPECIAL PURCHASE!

### BRAND NEW FM MULTIPLEX STEREO DECODER UNITS.

Manufactured by PHILIPS. Size 2" x 3 1/4" x 1". All transistor 24v. at 6 mA. Supplied pre-aligned with full circuit diagram and connection details. £4 each Post Free.

### FEW ONLY—LEAK MK I TRANSCRIPTION PICK-UP ARMS

Using the world famous gimbal pivot system. Complete but less pick up head. £2-50 P. & P. 20p


### INPUT MATCHING TRANSFORMER

Beautifully made in heavy Mu-metal cylindrical case for minimum hum pick-up. Size 1 1/2" high x 1 1/2" dia. Ratio 150:1 approx. Especially suitable for matching dynamic or ribbon mikes or pick up from low to high impedance or vice versa. 75p each Post Free

### BLACK ANODISED 16c. ALUMINIUM HEAT SINKS

For TOS, complete with mica's & bushes. Size 2 1/2" x 3" approx. 25p pair P. & P. 5p.
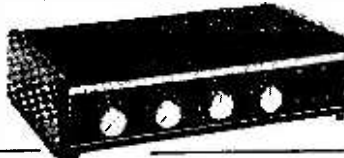
## HARVERSONIC SUPER SOUND 10 + 10 STEREO AMPLIFIER KIT



### NEW IMPROVED MODEL WITH HIGHER OUTPUT AND INCORPORATING HIGH QUALITY READY DRILLED PRINTED CIRCUIT BOARD FOR EASY CONSTRUCTION

A really first-class Hi-Fi Stereo Amplifier Kit. Uses 14 transistors including Silicon Transistors in the first five stages on each channel resulting in even lower noise level with improved sensitivity. Integrated pre-amp with Bass, Treble and two Volume Controls. Suitable for use with Ceramic or Crystal cartridges. Output stage for any speakers from 5 to 15 ohms. Compact design, all parts supplied including drilled metal work, high quality ready drilled printed circuit board, attractive front panel, knobs, wire, solder, nuts, bolts—no extras to buy. Simple step by step instructions enable any constructor to build an amplifier to be proud of. Brief specification: Power output: 14 watts r.m.s. per channel into 5 ohms. Frequency response  $\pm 5$ dB 15-20,000 Hz. Sensitivity: better than 80mV into 1M $\Omega$ . Full power bandwidth:  $\pm 3$ dB 12-15,000 Hz. Bass boost approx. to  $\pm 12$ dB. Treble cut approx. to -16dB. Negative feedback 18dB over main amp. Power requirements 35v. at 1.0 amp. Overall Size 12" w. x 8" d. x 2 1/2" h.

Fully detailed 7 page construction manual and parts list free with kit or send 18p plus large S.A.E.

|                                                 |                    |
|-------------------------------------------------|--------------------|
| PRICES                                          |                    |
| AMPLIFIER KIT                                   | £10-50 P. & P. 15p |
| POWER PACK KIT                                  | £3-00 P. & P. 30p  |
| CABINET                                         | £3-00 P. & P. 30p  |
| (Post Free if all units purchased at same time) |                    |

Full after sales service  
Also available ready built and tested £20-40. Post Free.  
Note: The above amplifier is suitable for feeding two mono sources into inputs (e.g. mike, radio, twin record decks, etc.) and will then provide mixing and fading facilities for medium powered Hi-Fi Discosque use, etc.

### SPECIAL PURCHASE OF MANUFACTURERS SURPLUS!

All Transistor F.M. tuner head with twin A.M. Gang Incorporated. Beautifully finished with precision geared reduction drive. V.M.F.R. Transistor, oscillator/Mixer and first I.F. stage (10.7 Mc/s) output with optional A.F.C. connection. Built on printed circuit panel and fully screened. Extremely stable over range 88-108Mc/s. Brand new and pre-aligned. Size 2 1/2" h. x 1 1/2" w. x 2 1/4" d. For 6v D.C. at 2.8mA. A.M. Gang fitted with trimmers which can be connected to standard A.M. aerial and oscillator circuits if required. LIMITED NUMBER. Only £2-25 post free. Connection details supplied.

### HIGH GRADE COPPER LAMINATE BOARDS.

8 x 6 x 1/4 in. FIVE for 50p. P. & P. 13p.  
TELESCOPIC AERIALS WITH SWIVEL JOINT. Can be angled and rotated in any direction. 6 section Lacquered Brass. Extends from 6in. to 22 1/2 in. approx. Maximum diameter 1/4 in. 25p each. P. & P. 5p.

BRAND NEW MULTI-RATIO MAINS TRANSFORMERS. Giving 13 alternatives. Primary: 0-210-240v. Secondary combinations 0-5-10-15-20-25-30-35-40-50v. half wave at 1 amp. or 10-0-10, 20-0-20, 30-0-30v. at 2 amps full wave. Size 3in. long x 3 1/2 in. wide x 3in. deep. Price £1-75 P. & P. 30p.

MAINS TRANSFORMER. For transistor power supplies. Pri. 200/240v. Sec. 9-0-9 at 500mA. 70p. P. & P. 13p. Pri. 200/240v. Sec. 12-0-12 at 1 amp. 85p. P. & P. 13p. Pri. 200/240v. Sec. 10-0-10 at 2 amp. £1-85. P. & P. 30p. Tapped Primary 200-220-240v. Sec. 21.5v. at 500mA. 65p. P. & P. 13p.

Open 9-5.30 Monday to Saturday

Early closing Wed. 1 p.m.

A few minutes from South Wimbale Tube Station.

## SPECIAL OFFER! HI-FI LOUDSPEAKER SYSTEMS

Beautifully made teak finish enclosure with most attractive Tegan-Ynair front. Size 16 1/2" high x 10 1/2" wide x 11 1/2" deep. Fitter with E.M.I. Ceramic Magnet 13" x 5" bass unit, two H.F. tweeter units and crossover. Power handling 10 watts. Available 3 or 8 or 15 ohms impedance.

### OUR PRICE £8.40 Carr. 65p

Cabinet Available Separately £4-50 Carr. 60p  
Also available in 8 ohms with EMI 13" x 8" bass speaker with parasitic tweeter £6-50 Carr. 65p

### LOUDSPEAKER BARGAINS

3" x 4 ohm 50p. P. & P. 8p. 5in. 3 ohm 80p. P. & P. 15p. 7 x 4in. 3 ohm £1-05. P. & P. 20p. 10 x 6in. 3 or 15 ohm £1-90. P. & P. 30p. E.M.I. 8 x 5in. 3 ohm with high flux magnet £1-82. P. & P. 20p. E.M.I. 13 1/2" x 8in. 3 ohm with high flux ceramic magnet £2-10 (15 ohm £2-25). P. & P. 30p. E.M.I. 13 x 8in. 3 or 15 ohm with two inbuilt tweeters and crossover network £4-20. P. & P. 30p. E.M.I. 13" x 8" twin cone (parasitic tweeter) 8 ohm £2-25 P. & P. 30p.

BRAND NEW. 12in. 15w. H/D Speakers, 3 or 15 ohms. Current production by well-known British maker. Now with Hifux ceramic ferrobar magnet assembly £5-50. Guitar models: 25w. £8-50, 35w. £8-50. P. & P. 35p. E.M.I. 3 1/2 in. HEAVY DUTY TWEETERS. Powerful ceramic magnets. Available in 3 or 8 or 15 ohms 85p each. P. & P. 13p.

12in. "RA" TWIN CONE LOUDSPEAKER. 10 watts peak handling, 3 or 15 ohm £2-20. P. & P. 30p.

35 ohm SPEAKERS 3in. only 65p. P. & P. 13p.

VYNAIR & REXINE SPEAKERS & CABINET FABRICS app. 54 in. wide. Usually £1-75 yd., our price 75p yd. length. P. & P. 15p (min 1 yd.) S.A.E. for samples.

### HI-FI STEREO HEADPHONES

Adjustable headband with comfortable flexiform ear-muffs. Wired and fitted with E.M.I. stereo 3 1/2 in. jack plug. Frequency response 30-15,000Hz. Matching impedance 8-16 ohms. PRICE £2-95. P. & P. 15p.

SINGLE HEADPHONE. With aluminium headband. Approx. 200 ohm, 25p. P. & P. 8p

CRYSTAL MIKES. High imp. for desk or hand use. High sensitivity, 93p. P. & P. 8p

HIGH IMPEDANCE CRYSTAL STICK MIKES.

OUR PRICE £1-05. P. & P. 8p

### GENERAL PURPOSE HIGH STABILITY TRANSISTOR PRE-AMPLIFIER

For P.U. Tape, Mike, Guitar, etc. and suitable for use with valve or transistor equipment. 9-18v. battery or from H.T. line 200/300v. Frequency response 15Hz-25KHz. Gain 26dB. Solid encapsulation size 1 1/2" x 1 1/2" x 1". Brand new complete with instructions. Price 85p. P. & P. 15p.

BRAND NEW E.M.I. LIGHTWEIGHT PICK-UP ARM WITH ARM REST. Fitted mono t/o stylus and cartridge for LP/78. ONLY £1. P. & P. 13p.

### QUALITY RECORD PLAYER AMPLIFIER MK II

A top quality record player amplifier employing heavy duty double wound mains transformer, ECC83, EL84, and rectifier. Separate Bass, Treble and Volume controls. Complete with output transformer matched for 3 ohm speaker. Size 7in. wide x 3in. deep x 6in. high. Ready built and tested. PRICE £2-75 P. & P. 40p

ALSO AVAILABLE mounted on board with output transformer and speaker ready to fit into cabinet below. PRICE £4-88 P. & P. 50p.

DELUXE QUALITY PORTABLE R/P CABINET MK II. 5in. front board size 14 1/2 x 12in. clearance 2in. below. Unit above. Will take above amplifier and any B.S.R. or GARRARD changer or Single Play (except AT60 and SP25). Size 18 x 15 x 5in. PRICE £3-98. P. & P. 50p.

## 10/14 WATT HI-FI AMPLIFIER KIT


A stylishly finished monaural amplifier with an output of 14 watts from 2 EL84s in push-pull. Super reproduction of both music and speech, with negligible hum. Separate inputs for mike and gram allow records and announcements to follow each other. Fully shrouded section wound output transformer to match 3-15  $\Omega$  speaker and 2 independent volume controls, and separate base and treble controls are provided giving good lift and cut. Valve line-up 2 EL84s, ECC83, EF86 and E280 rectifier. Simple instruction booklet 13p (Free with parts). All parts sold separately. ONLY £7-27 P. & P. 55p. Also available ready built and tested complete with std. input sockets, £9-97. P. & P. 55p.

BRAND NEW TRANSISTOR BARGAINS. GET 15 (Matched pair) 75p; V16/100 50p; OC71 25p; OC76 30p; AC117 15p; 2G39 (NPN) 15p. Set of Mullard 6 transistors OC44, 2-OC45, AC128D matched pair AC128 £1-25; ORP12 Cadmium Sulphide Cells 53p. All post free.

## SPECIAL PURCHASE! SPEAKER CABINET FROM FAMOUS MAKER!

Beautifully made all wooden construction cabinet with medium walnut finish front, gold anodised expanded aluminium grille and dark sides. Approx. size overall 11 1/2" high x 5" deep x 13 1/2" wide at base. Easily removable baffle cut for 8" speaker. Fibre board back. Could accommodate amplifier or radio together with speaker. An expensively made cabinet at a give away price. LIMITED NUMBER ONLY £1-98 Post Free.

## DE LUXE STEREO AMPLIFIER

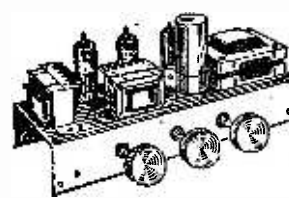

Valve line up: 2 x ECL86 Triode Pentodes, 1 x E280 as rectifier. Two dual potentiometers are provided for bass and treble control, giving bass and treble boost and cut. A dual volume control is used. Balance of the left and right hand channels can be adjusted by means of a separate 'Balance' control fitted at the rear of the chassis. Input sensitivity is approximately 300mV for full peak output of 4 watts per channel (8 watts mono), into 3 ohm speakers. Full negative feedback in a carefully calculated circuit, allows high volume levels to be used with negligible distortion. Supplied complete with knobs, chassis size 11" w x 4" d. Overall height including valves 5". Ready built & tested to a high standard. PRICE £8-92 P. & P. 45p

### 4-SPEED RECORD PLAYER BARGAINS

Mains models. All brand new in maker's packing.

LATEST B.S.R. C109/A21 4-SPEED AUTOCHANGER.

With latest mono compatible cartridge £6-97 Carr. 50p.

With stereo cartridge £7-97 Carr. 50p.

SUITABLE PLINCH UNIT FOR ABOVE with rigid plastic cover. £5-75 complete P. & P. 50p.

LATEST GARRARD MODELS. All types available 1995, 2025, SP25, 3000, AT60 S.A.E. for latest Prices!

PLINCH UNITS cut out for Garrard Models, 1025, 2025, 2000, 3000, 3500 etc. With rigid transparent plastic cover. Special design enables above models to be used with cover in position. Also suitable for housing AT60 and SP25. OUR PRICE £5-75 complete. P. & P. 50p.

LATEST ACOS GP81/150 mono compatible cartridge with t/o stylus for LP/EP/78. Universal mounting bracket. £1-50 P. & P. 8p.

SONOTONE STACH COMPATIBLE STEREO CARTRIDGE T/O stylus Diamond Stereo LP and Sapphire 78.

ONLY £2-50 P. & P. 10p. Also available fitted with twin Diamond T/O stylus for Stereo LP. £3. P. & P. 10p.

LATEST RONETTE T/O STEREO/COMPATIBLE CARTRIDGE for EP/LP Stereo 78. £1-83 P. & P. 10p.

LATEST RONETTE T/O MONO COMPATIBLE CARTRIDGE for playing EP/LP/78 mono or stereo records on mono equipment. Only £1-50 P. & P. 10p.

### 8-VALVE AUDIO AMPLIFIER HA34 MK II.

Designed for Hi-Fi reproduction of records. A.C. Mains operation. Ready built on plated heavy gauge metal chassis, size 7 1/2" w. x 4 1/2" d. x 4 1/2" h. Incorporates ECC83, EL84, E280 valves. Heavy duty, double wound mains transformer and output transformer matched for 3 ohm speaker. Separate volume control and now with improved wide range tone controls giving bass and treble lift and cut. Negative feedback line. Output 4 1/2 watts. Front panel can be detached and leads extended for remote mounting of controls. Complete with knobs, valves, etc., wired and tested for only £4-75. P. & P. 30p.

HSL "FOUR" AMPLIFIER KIT. Similar in appearance to HA34 above but employs entirely different and advanced circuitry. Complete set of parts, etc. £3-98. P. & P. 40p.

### HARVERSON'S SUPER MONO AMPLIFIER

A superb quality gram amplifier using a double wound fully isolated mains transformer, rectifier and ECL82 triode pentode valve as audio amplifier and power output stage. Impedance 3 ohms. Output approx. 3.5 watts. Volume and tone controls. Chassis size 7in. wide x 3in. deep x 6in. high overall. AC mains 200/240v. Supplied absolutely Brand New completely wired and tested with good quality output transformer.

FEW ONLY. £2.75 P. & P. 35p

### HANDBOOK OF TRANSISTOR EQUIVALENTS AND SUBSTITUTES

A must for servicemen and home constructors. 1971 edition including many 1000's of British, A.E.I., European and Japanese transistors. ONLY 40p Post 5p.

## HARVERSON SURPLUS CO. LTD.

170 HIGH ST., MERTON, LONDON, S.W.19

Tel.: 01-540 3985

SEND STAMPED ADDRESSED ENVELOPE WITH ALL ENQUIRIES

(Please write clearly)

PLEASE NOTE: P. & P. CHARGES QUOTED APPLY TO U.K. ONLY. P. & P. ON OVERSEAS ORDERS CHARGED EXTRA.

## Fully guaranteed Individually packed VALVES

|          |        |        |     |        |     |
|----------|--------|--------|-----|--------|-----|
| B12H     | £1.75p | ECH200 | 62p | OA2    | 35p |
| CY31     | 35p    | ECL50  | 45p | OB2    | 35p |
| DAF96    | 38p    | ECL82  | 62p | PAB380 | 37p |
| DF96     | 38p    | ECL83  | 65p | PC87   | 40p |
| DR96     | 41p    | ECL86  | 42p | PC900  | 47p |
| DL92     | 32p    | EP36   | 45p | PC854  | 37p |
| DL94     | 40p    | EP37A  | 45p | PC859  | 45p |
| DL96     | 41p    | EP39   | 40p | PC8189 | 55p |
| DM70     | 30p    | EP40   | 50p | PC800  | 75p |
| DY86     | 45p    | EP41   | 62p | PCF80  | 30p |
| DY87     | 56p    | EP80   | 62p | PCF82  | 33p |
| DY89     | 45p    | EP85   | 65p | PCF84  | 46p |
| EB80C/01 | 45p    | EP85   | 32p | PCF86  | 37p |
| EB80C    | 45p    | EP86   | 31p | PCF200 | 77p |
| EB80C    | 45p    | EP89   | 25p | PCF201 | 77p |
| EB81CC   | 90p    | EP91   | 18p | PCF801 | 47p |
| EB82CC   | 90p    | EP92   | 37p | PCF802 | 48p |
|          |        | EP93   | 30p | PCF806 | 72p |
|          |        | EP95   | 32p | PCF806 | 72p |
|          |        | EP96   | 32p | PCF806 | 72p |
|          |        | EP97   | 32p | PCF806 | 72p |
|          |        | EP98   | 32p | PCF806 | 72p |
|          |        | EP99   | 32p | PCF806 | 72p |
|          |        | EP100  | 32p | PCF806 | 72p |
|          |        | EP101  | 32p | PCF806 | 72p |
|          |        | EP102  | 32p | PCF806 | 72p |
|          |        | EP200  | 32p | PCF806 | 72p |

## TRANSISTORS, ZENER DIODES etc.

|                      |      |        |       |              |        |        |             |           |        |     |
|----------------------|------|--------|-------|--------------|--------|--------|-------------|-----------|--------|-----|
| <b>SPECIAL OFFER</b> | OC25 | 37p    | OC200 | 40p          | 2N3055 | 75p    | AD149       | 50p       | BYZ13  | 25p |
| <b>OBJ tube</b>      | OC26 | 25p    | OC201 | 60p          | 2N3730 | 50p    | AD161       | 37p       | BYZ16  | 68p |
|                      | OC28 | 62p    | OC206 | 90p          | 2N3731 | £2.75p | AD162       | 37p       | CRS110 | 25p |
| <b>£1.75</b>         | OC29 | 62p    | IN21  | 17p          | 2N5109 | £2.65p | AF118       | 62p       | CRS120 | 35p |
| OA5                  | 20p  | OC35   | 50p   | IN21B        | 25p    | AF127  | 17p         | CRS130    | 40p    |     |
| OA10                 | 25p  | OC38   | 42p   | IN25         | 60p    | AF139  | 30p         | CRS135    | 45p    |     |
| OA70                 | 10p  | OC44   | 17p   | IN43         | 10p    | AF178  | 45p         | CRS140    | 45p    |     |
| OA71                 | 10p  | OC45   | 15p   | IN70         | 7p     | AF186  | 40p         | CRS105    | 30p    |     |
| OA73                 | 10p  | OC70   | 15p   | IN702-7235p  | 35p    | AF191  | 15p         | CRS120    | 35p    |     |
| OA74                 | 10p  | OC71   | 15p   | IN823A £1.80 | 35p    | ASV26  | 25p         | CRS130    | 45p    |     |
| OA79                 | 10p  | OC72   | 25p   | IZMT5        | 35p    | ASV28  | 25p         | CRS25/025 | 75p    |     |
| OA81                 | 10p  | OC73   | 25p   | IZMT10       | 35p    | ASV67  | 45p         |           |        |     |
| OA81                 | 7p   | OC75   | 25p   | IZT10        | 67p    | BAW19  | 25p         |           |        |     |
| OA200                | 7p   | OC76   | 25p   | IZT10        | 65p    | BC107  | 12p         |           |        |     |
| OA202                | 10p  | OC81   | 25p   | 3G335        | 51p    | BC108  | 12p         |           |        |     |
| OA210                | 25p  | OC81D  | 20p   | 2G403        | 15p    | BC113  | 25p         |           |        |     |
| OA211                | 37p  | OC81DM | 20p   | IN4785       | 50p    | BC118  | 35p         |           |        |     |
| OA2200               | 55p  | OC82   | 25p   | IN2N77       | 35p    | BCY72  | 15p         |           |        |     |
| OA2301               | 50p  | OC83DM | 30p   | IN2N18       | 37p    | BF115  | 25p         |           |        |     |
| OA2302               | 50p  | OC83B  | 15p   | IN2N184      | 25p    | BF173  | 30p         |           |        |     |
| OA2304               | 42p  | OC84   | 25p   | IN2N1306     | 25p    | BFY51  | 25p         |           |        |     |
| OA2207               | 47p  | OC84   | 25p   | IN2N1306     | 25p    | BFY52  | 25p         |           |        |     |
| OA2308               | 47p  | OC122  | 50p   | IN2N1307     | 25p    | AC127  | 25p         |           |        |     |
| OA2213               | 32p  | OC139  | 25p   | IN2N147      | 75p    | AC128  | 25p         |           |        |     |
| OA2223               | 30p  | OC140  | 37p   | IN2N1904A    | 35p    | AC176  | 25p         |           |        |     |
| OA2225               | 30p  | OC171  | 30p   | IN2N3053     | 25p    | AC177  | 30p         |           |        |     |
| OC16                 | 50p  | OC172  | 37p   | IN2N3054     | 50p    | ACV28  | 17p         |           |        |     |
| OC22                 | 50p  |        |       |              |        |        | BTU00 £1.80 | V405A     | 40p    |     |



ALL valves  
guaranteed

brand

|        |        |         |        |              |         |
|--------|--------|---------|--------|--------------|---------|
| 6H6    | 20p    | 12K5    | 55p    | 957          | 30p     |
| 6J4WA  | 75p    | 12K8GT  | 45p    | 991          | 40p     |
| 6J5    | 40p    | 12K9GT  | 45p    | 1622         | £1.00p  |
| 6J6GT  | 25p    | 12K9GT  | 30p    | 2051         | 55p     |
| 6J6    | 20p    | 12K9GT  | 35p    | 5383         | £1.15p  |
| 6J7G   | 35p    | 1487    | 75p    | 6057         | 50p     |
| 6J7M   | 40p    | 19A95   | 40p    | 6060         | 50p     |
| 6K8GT  | 50p    | 19G38   | £4.25p | 6064         | 45p     |
| 6K7    | 32p    | 19G6    | £1.50p | 6065         | 85p     |
| 6K70   | 20p    | 19H4    | £5.00p | 6080         | £1.87p  |
| 6K8GT  | 45p    | 20P4    | £1.00p | 6146         | £1.50p  |
| 6K25   | 70p    | 25L6GT  | 40p    | 9020         | £2.25p  |
| 68A7   | 40p    | 30C15   | 75p    | 9001         | 25p     |
| 68A7GT | 32p    | 30C17   | 80p    | 9002         | 25p     |
| 68C7GT | 25p    | 30C18   | 75p    | 9003         | 50p     |
| 68C7   | 35p    | 30P5    | 84p    | 9004         | 15p     |
| 68J7   | 37p    | 30P19   | 70p    | 9006         | 15p     |
| 68J7GT | 32p    | 30P12   | 92p    | C.R. Tubes   |         |
| 68K7   | 35p    | 30P13   | 50p    | VCR97        |         |
| 68L7GT | 32p    | 30P14   | 75p    | VCR517B      | £4.50p  |
| 68N7GT | 35p    | 30P15   | 85p    | VCR517B      | £3.50p  |
| 68Q7   | 39p    | 30P17   | 80p    | VCR517C      | £7.50p  |
| 68Q7GT | 35p    | 30P13   | 80p    |              |         |
| 6V6G   | 17p    | 30P19   | 70p    |              |         |
| 6V6GT  | 30p    | 30P11   | 70p    |              |         |
| 6X4    | 27p    | 30P13   | 92p    | 88D          | £9.00p  |
| 6X6    | 55p    | 30P14   | 85p    | 88J          | £9.00p  |
| 6X6GT  | 45p    | 30P15   | 80p    | 88L          | £9.00p  |
| 6Y6G   | 60p    | 35W4    | 50p    | Photo Tubes  |         |
| 6Z6    | 30p    | 630L2   | 75p    | CMG25        | £2.75p  |
| 6Z4    | 32p    | 42      | 45p    |              |         |
| 7B7    | 45p    | 50C5    | 40p    | 631A         | £3.50p  |
| 7C5    | 30p    | 50C6G30 | 60p    | 6097C        | £17.50p |
| 7C6    | 40p    |         |        |              |         |
| 7E7    | 35p    | 50EH5   | 60p    | Special Vhrs |         |
| 7Y4    | 40p    | 75      | 40p    |              |         |
| 8D6    | 37p    | 76      | 40p    |              |         |
| 11E2   | 22p    | 80p     | 78     |              |         |
| 12AT6  | 30p    | 80p     | 40p    |              |         |
| 12AT7  | 30p    | 80p     | £3.25p | JP97D        | £37.50p |
| 12AV6  | 30p    | 80p     | £3.00p |              |         |
| 12AX7  | 30p    | 812     | £3.75p | K301         | £5.00p  |
| 12BA6  | 35p    | 823A    | £3.00p | K305         | £12.00p |
| 12BB6  | 35p    | 866A    | 75p    | K308         | £16.00p |
| 12BH7  | 27p    | 954     | 40p    | K337         | £16.00p |
| 12C8   | 25p    | 955     | 40p    | K322         | £16.00p |
| 12E1   | £1.25p | 956     | 20p    | 725A         | £16.00p |

Colomur (Electronics) Ltd.

170 GOLDHAWK ROAD, LONDON W12.

Open 9-12.30, 1.30-5.30 p.m. Thursday 9-1 p.m.

29/41ft. AERIALS each consisting of ten 3ft. 7in. dia. tubular screw-in sections. 11ft. (6-section) whip aerial with adaptor to fit the 7in. rod, insulated base, stay plate and stay assemblies, pegs, reamer, hammer, etc. Absolutely brand new and complete ready to erect. In canvas bag £4. P. & 50p.

## METERS

Full List of our very large stock of meters on request.

## INTERATED COURSES— MANY OTHERS IN STOCK

RCA. CA 3005 wide band R.F. Ampl. 300mW diss £1.20  
CA 3012 wide band ampl. 150mW diss £0.90  
CA 3020 Audio power ampli. £1.37  
CA 3036 Audio pre-ampl. £0.90  
General Electric PA 230 £1.40; PA 234 £1; PA 237 £1.40  
Mullard TAA 300 £1.75; TAA 320 73p



# The 'New Picture-Book' way of learning BASIC ELECTRICITY (5 VOLS.) BASIC ELECTRONICS (6 VOLS.)

You'll find it easy to learn with this outstandingly successful NEW PICTORIAL METHOD—the essential facts are explained in the simplest language, one at a time, and each is illustrated by an accurate, cartoon-type drawing. The books are based on

the latest research into simplified learning techniques. This has proved that the PICTORIAL APPROACH to learning is the quickest and soundest way of gaining mastery over these subjects.

TO TRY IT, IS TO PROVE IT



# WAVE METER

# MONITOR

R. F. GRAHAM

**T**HIS unit has four switch-selected bands, covering from 1600kHz to 100MHz and it can be used as a wavemeter, field strength meter or phone transmission monitor. It is fully enclosed, self-contained, and requires no battery.

Figure 1 shows the circuit. One pole of the switch, S1, selects the inductors L1, L2, L3 or L4, which are tuned by VC1. Pole S2 switches the diode D1 to the appropriate small coupling winding. When the circuit is tuned to resonance by VC1, rectified current is indicated by the meter.

To monitor phone signals, high impedance headphones or earpiece can be plugged into the phone jack and the phones are then in series with the meter. C1 is for r.f. and a.f. by-pass purposes, while C2 is an r.f. by-pass capacitor.

## INDUCTORS

L1, L2 and L3 are wound on  $\frac{1}{2}$ in. diameter paxolin formers. These can be prepared by cutting  $1\frac{1}{2}$ in. lengths of  $\frac{1}{2}$ in. diameter tube, and drilling small holes to secure the ends of the windings. The tubes can later be fixed with adhesive, with small brackets or by having them a push fit on small discs of insulating material screwed in place. Surplus or junk box formers could probably be utilised, but if these are of different diameter it may be necessary to modify the number of turns to suit.

L1 is wound with 34 s.w.g. enamelled copper wire. The tuned portion A to B is 65 turns, in a compact pile about  $\frac{3}{16}$ in. long. A space of about  $\frac{3}{16}$ in. is left and section B to C is wound on in the same direction, and has 8 turns side by side.

L2 also uses 34 s.w.g. enamelled copper wire. A to B is 50 turns wound side by side. A space is left as before, and a 4 turn coupling winding ends at C.

L3 uses 24 s.w.g. enamelled wire and has  $12\frac{1}{2}$  turns from A to B, and 2 turns from B to C. Figure 2 shows the general construction of L1, L2 and L3.

The windings are doped, smeared with clear Bostik 1 or with some other suitable coil cement.

L4 is self-supporting, of 16 s.w.g. bare wire, and is shown in Fig. 3. It is wound and shaped to have 8 turns in all and is  $\frac{1}{2}$ in. outside diameter, and 1in. long. B is a tapping 2 turns from end C. This coil is soldered directly to tags A and C of the 4-way switch as shown in Fig. 3. A lead runs from tapping B

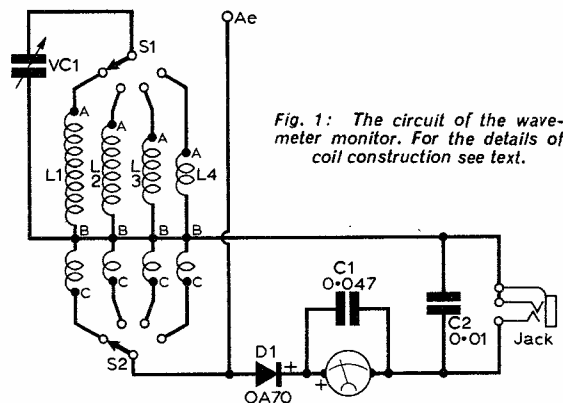
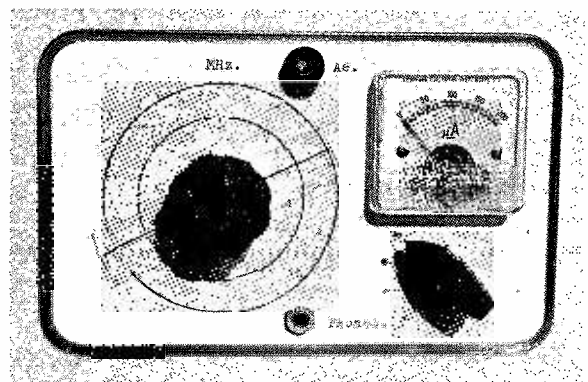


Fig. 1: The circuit of the wave-meter monitor. For the details of coil construction see text.

## ★ components list

VC1 200pF Wavemaster variable capacitor.  
C1 0.047μF or similar.  
C2 0.01μF or similar.  
D1 OA7 or OA81 diode.  
S1 15A 2-pole 4-way miniature rotary switch.  
Small closed circuit jack.  
200μA miniature meter.  
Inductors as text.  
Paxolin, paxetex, box about 6 x 3½ x 2½in., aerial socket, knobs etc.

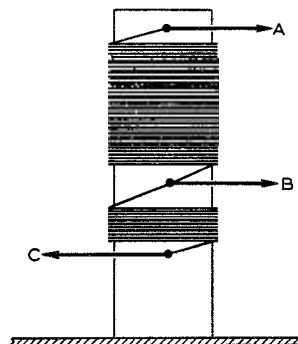


Fig. 2: The general construction of coils L1, L2 and L3 wound on  $\frac{1}{2}$ in. diameter paxolin formers. Details of L4 are given in the text and in Fig. 3.

directly to the moving plates tag of the variable capacitor.

## CONSTRUCTION


The wavemeter was built to occupy a rigid plastic 'snack box' approximately 6in.  $\times$  3 $\frac{1}{2}$ in.  $\times$  2 $\frac{1}{2}$ in. deep. A piece of paxolin sheet, a little under 6in.  $\times$  3 $\frac{1}{2}$ in., was cut to fit inside the box lid. The wavemeter is built wholly on this paxolin panel.

Screws holding L1, L2 and L3 are countersunk. A piece of stout paper to bear dial markings is cut the same size as the paxolin, and cemented to it. The wavemeter is then assembled and calibrated and the scales are marked. The meter and fixing nuts of the switch, jack, and VC1 are then removed and the paxolin panel is fitted inside the box lid. This places the scales under the transparent material of the lid. Paxolin and lid are held together by the meter and the nuts mentioned.

Holes for the jack, switch and VC1 are first drilled in the paxolin and the meter hole cut with an adjustable washer or tank cutter. The paxolin is then placed in the lid, and the positions of holes marked on the lid itself, so that they can be made to match up correctly with those in the paxolin.

The box should be of material which is reasonably strong. It should be drilled and cut with tools which are really sharp, and without forcing, to avoid cracking.

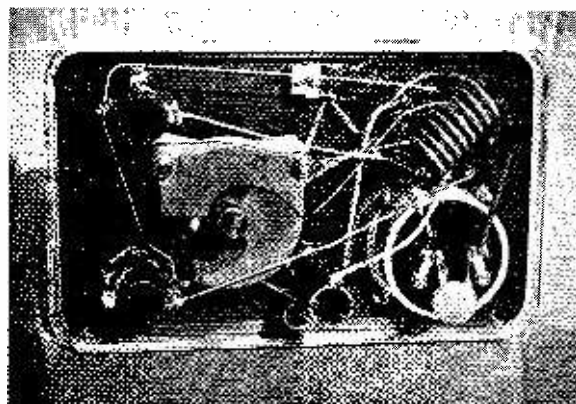A suitable case could be assembled from  $\frac{1}{4}$ in. thick wood, glued and pinned at the joints. The paxolin panel would then be large enough to be fixed with small wood screws.



An internal view of the completed prototype.

The dial cursor is a 2 $\frac{3}{4}$ in. piece of perspex about  $\frac{5}{8}$ in. wide, marked with a hair line. Readings will be confused if VC1 can rotate through 360°, so the extreme corner of the back moving plate was turned up with pliers to limit rotation to about 180°.

Values used for C1 and C2 are not particularly important. A medium or high impedance pair of headphones will give best general results.

## CALIBRATION

Actual band coverage with the inductors described is as follows

|         |           |
|---------|-----------|
| Range 1 | 1.6-4MHz  |
| Range 2 | 2.8-10MHz |
| Range 3 | 8-32MHz   |
| Range 4 | 21-100MHz |

This gives 160 and 80m bands in Range 1, 80 and 40m bands in Range 2, all h.f. bands 20-10m in Range 3, and 15-10m bands and harmonics in Range 4, without having to use the extreme h.f. end of the ranges, where readings become close together.

The simplest means of calibration is to use a grid dip oscillator, placing its coil 2in. or so from the appropriate inductor in the wavemeter. This allows complete calibration of all ranges with a minimum of difficulty.

A transmitter can be used for calibration in the amateur bands, and these will probably be of most importance. Place the wavemeter some distance from the transmitter, its dummy load or the aerial lead or tuner, as required to obtain a deflection on the meter.

Some signal generators have an r.f. level meter. If the output of the generator is coupled to the wavemeter by a small loop, a dip may be observed on the level meter when the wavemeter is tuned to resonance. This offers another possible way to secure calibration.

If the wavemeter is coupled to a receiver having a sensitive S-meter, a slight dip in the S-meter reading can be observed when the wavemeter is tuned to the receiver frequency. Input to the receiver can be from a signal generator, or transmission.

All calibration is made with no external connection to the wavemeter and minimum coupling to avoid unnecessary inaccuracy.

## USES

A wavemeter is normally used to indicate frequency bands and harmonics, not exact frequencies within a narrow band. It is placed or held to pick up sufficient r.f. energy from the circuit being investiga-

—continued on page 534

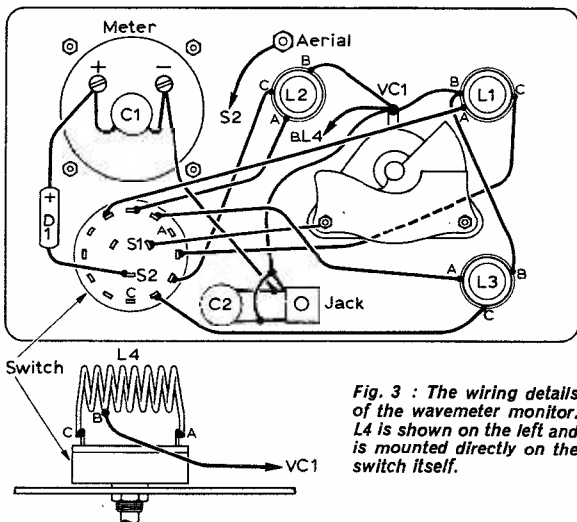


Fig. 3: The wiring details of the wavemeter monitor. L4 is shown on the left and is mounted directly on the switch itself.

All wiring is shown in Fig. 3. Connections should be of stout wire and run clear of each other, and should be reasonably short and direct, especially for L3 and L4.

VC1 is 200pF, but this exact value is not essential, provided that the ranges overlap a little. If an alternative diode is fitted, be sure it is suitable for frequencies up to 100MHz.

A 100 $\mu$ A meter would be a little more sensitive than the one specified, but would also cost a little more. Should a 500 $\mu$ A meter be to hand, it is suitable, though less sensitive. The sensitivity with a 1mA meter becomes rather low so an instrument in the neighbourhood of 200 $\mu$ A is probably most suitable.

# BRAND NEW GUARANTEED

# SEMICONDUCTORS & COMPONENTS

SOLE AGENTS FOR SOLID STATES DEVICES INC., (USA). IN U.K.

# RETURN OF POST SERVICE

## TRANSISTORS

|         |       |         |       |        |       |        |        |        |     |          |     |
|---------|-------|---------|-------|--------|-------|--------|--------|--------|-----|----------|-----|
| 2G301   | 20p   | 2N3404  | 32p   | 40310  | 45p   | BC212L | 13p    | BSX28  | 32p | NKT281   | 27p |
| 2G302   | 20p   | 2N3405  | 45p   | 40311  | 35p   | BCY30  | 27p    | BSX60  | 82p | NKT401   | 87p |
| 2G303   | 20p   | 2N3414  | 45p   | 40312  | 47p   | BCY31  | 30p    | BSX61  | 62p | NKT402   | 80p |
| 2G304   | 42p   | 2N3415  | 25p   | 40314  | 47p   | BCY32  | 30p    | BSX76  | 22p | NKT403   | 75p |
| 2G305   | 42p   | 2N3416  | 25p   | 40315  | 47p   | BCY33  | 25p    | BSX77  | 22p | NKT404   | 62p |
| 2G306   | 30p   | 2N3417  | 37p   | 40320  | 47p   | BCY34  | 30p    | BSX78  | 27p | NKT405   | 75p |
| 2G371   | 15p   | 2N3570  | 11-25 | 40324  | 47p   | BCY38  | 40p    | BSY10  | 27p | NKT406   | 62p |
| 2G374   | 20p   | 2N3572  | 77p   | 40326  | 37p   | BCY39  | 60p    | BSY11  | 27p | NKT451   | 62p |
| 2G381   | 22p   | 2N3605  | 27p   | 40329  | 37p   | BCY40  | 50p    | BSY24  | 15p | NKT452   | 62p |
| 2G406   | 22p   | 2N3606  | 27p   | 40342  | 47p   | BCY42  | 15p    | BSY26  | 15p | NKT453   | 47p |
| 2G696   | 20p   | 2N3607  | 29p   | 40347  | 57p   | BCY43  | 15p    | BSY26  | 15p | NKT453   | 47p |
| 2G697   | 17p   | 2N3702  | 11p   | 40348  | 57p   | BCY44  | 32p    | BSY27  | 17p | NKT453   | 47p |
| 2G698   | 25p   | 2N3703  | 10p   | 40360  | 42p   | BCY45  | 28p    | BSY28  | 17p | NKT453   | 47p |
| 2G706   | 12p   | 2N3704  | 11p   | 40361  | 47p   | BCY46  | 28p    | BSY28  | 17p | NKT453   | 47p |
| 2G706A  | 12p   | 2N3705  | 10p   | 40362  | 47p   | BCY47  | 28p    | BSY28  | 17p | NKT453   | 47p |
| 2G708   | 30p   | 2N3706  | 09p   | 40370  | 32p   | BCY70  | 20p    | BSY36  | 25p | NKT781   | 30p |
| 2G709   | 62p   | 2N3707  | 11p   | 40406  | 57p   | BCY71  | 20p    | BSY37  | 25p | NKT10419 | 30p |
| 2G718   | 25p   | 2N3708  | 07p   | 40407  | 40p   | BCY72  | 17p    | BSY37  | 25p | NKT10419 | 30p |
| 2G726   | 30p   | 2N3709  | 09p   | 40408  | 52p   | BCZ10  | 27p    | BSY39  | 25p | NKT10419 | 30p |
| 2G727   | 30p   | 2N3710  | 09p   | 40410  | 62p   | BCZ11  | 42p    | BSY40  | 32p | NKT10519 | 37p |
| 2G914   | 17p   | 2N3711  | 12p   | 40467A | 57p   | BD116  | 11-12p | BSY51  | 32p | NKT20329 | 32p |
| 2G916   | 17p   | 2N3715  | 11-23 | 40468A | 57p   | BD121  | 65p    | BSY52  | 32p | NKT20329 | 32p |
| 2G918   | 30p   | 2N3716  | 11-23 | 40469  | 57p   | BD123  | 82p    | BSY53  | 37p | NKT20333 | 47p |
| 2G921   | 22p   | 2N3717  | 11p   | 40470  | 57p   | BD124  | 82p    | BSY54  | 40p | NKT20333 | 47p |
| 2G930   | 27p   | 2N3819  | 35p   | AC126  | 20p   | BD131  | 75p    | BSY56  | 60p | NKT80111 | 37p |
| 2N1000  | 22p   | 2N3823  | 97p   | AC127  | 20p   | BD132  | 85p    | BSY78  | 47p | NKT80112 | 77p |
| 2N1001  | 22p   | 2N3854  | 27p   | AC128  | 20p   | BDY10  | 11-37p | BSY79  | 45p | NKT80112 | 77p |
| 2N1131  | 25p   | 2N3854A | 27p   | AC128  | 20p   | BDY11  | 11-37p | BSY82  | 62p | NKT80112 | 77p |
| 2N1132  | 25p   | 2N3855  | 27p   | AC128  | 20p   | BDY17  | 11-37p | BSY90  | 57p | NKT80112 | 77p |
| 2N1302  | 27p   | 2N3855A | 30p   | AC128  | 20p   | BDY18  | 11-37p | BSY95A | 12p | NKT80112 | 77p |
| 2N1303  | 27p   | 2N3856  | 30p   | AC128  | 20p   | BDY19  | 11-37p | BSY95A | 12p | NKT80112 | 77p |
| 2N1304  | 22p   | 2N3856A | 35p   | AC128  | 20p   | BDY20  | 11-12p | BSW70  | 27p | NKT80212 | 82p |
| 2N1305  | 22p   | 2N3858  | 25p   | AC128  | 20p   | BDY38  | 97p    | C111   | 75p | NKT80212 | 82p |
| 2N1306  | 25p   | 2N3858A | 30p   | AC128  | 20p   | BDY90  | 11-25  | C424   | 27p | NKT80212 | 82p |
| 2N1307  | 25p   | 2N3859  | 27p   | AC128  | 20p   | BDY61  | 11-25  | C425   | 55p | NKT80212 | 82p |
| 2N1308  | 30p   | 2N3859A | 32p   | AC128  | 20p   | BF102  | 11-25  | C426   | 40p | NKT80212 | 82p |
| 2N1309  | 30p   | 2N3860  | 30p   | AC128  | 20p   | BF115  | 25p    | C428   | 40p | NKT80212 | 82p |
| 2N1507  | 17p   | 2N3866  | 11-50 | AC128  | 20p   | BF117  | 47p    | C434   | 30p | NKT80212 | 82p |
| 2N1613  | 25p   | 2N3877  | 40p   | AC140  | 20p   | BF163  | 37p    | D16P1  | 37p | NKT80215 | 82p |
| 2N1681  | 35p   | 2N3877A | 40p   | AC141  | 20p   | BF167  | 18p    | D16P2  | 40p | NKT80215 | 82p |
| 2N1682  | 30p   | 2N3900  | 37p   | AC144  | 40p   | BF173  | 18p    | D16P3  | 47p | NKT80215 | 82p |
| 2N1688  | 27p   | 2N3901  | 47p   | AD147  | 53p   | BF177  | 30p    | D16P7  | 37p | NKT80215 | 82p |
| 2N1689  | 27p   | 2N3901  | 47p   | AD147  | 53p   | BF178  | 30p    | GET102 | 20p | NKT80215 | 82p |
| 2N1671B | 11-00 | 2N3903  | 35p   | AD150  | 62p   | BF179  | 30p    | GET113 | 20p | OC20     | 75p |
| 2N1711  | 25p   | 2N3904  | 35p   | AD161  | 37p   | BF180  | 35p    | GET114 | 20p | OC22     | 50p |
| 2N1889  | 32p   | 2N3905  | 37p   | AD162  | 37p   | BF181  | 32p    | GET118 | 20p | OC23     | 60p |
| 2N1893  | 37p   | 2N3906  | 37p   | AP106  | 42p   | BF184  | 25p    | GET119 | 20p | OC24     | 60p |
| 2N1897  | 37p   | 2N3906  | 37p   | AP106  | 42p   | BF185  | 42p    | GET120 | 62p | OC25     | 50p |
| 2N1898  | 37p   | 2N3906  | 37p   | AP106  | 42p   | BF186  | 42p    | GET121 | 62p | OC26     | 50p |
| 2N1899  | 37p   | 2N3906  | 37p   | AP106  | 42p   | BF187  | 42p    | GET122 | 62p | OC27     | 50p |
| 2N1914  | 57p   | 2N4059  | 11p   | AF115  | 25p   | BF195  | 15p    | GET180 | 30p | OC28     | 62p |
| 2N1916  | 57p   | 2N4060  | 11p   | AF116  | 25p   | BF196  | 15p    | GET181 | 30p | OC29     | 62p |
| 2N1918  | 40p   | 2N4061  | 12p   | AF117  | 25p   | BF197  | 42p    | GET182 | 30p | OC30     | 62p |
| 2N1938A | 42p   | 2N4062  | 12p   | AF118  | 25p   | BF197  | 42p    | GET183 | 30p | OC31     | 62p |
| 2N1944  | 40p   | 2N4063  | 12p   | AF119  | 25p   | BF198  | 42p    | GET184 | 30p | OC32     | 62p |
| 2N2171  | 27p   | 2N4285  | 17p   | AF124  | 22p   | BF200  | 42p    | GET185 | 30p | OC33     | 62p |
| 2N2218  | 25p   | 2N4292  | 12p   | AF125  | 22p   | BF201  | 42p    | GET186 | 30p | OC34     | 62p |
| 2N2219  | 25p   | 2N4287  | 17p   | AF126  | 22p   | BF202  | 42p    | GET187 | 30p | OC35     | 62p |
| 2N2220  | 25p   | 2N4288  | 17p   | AF127  | 17p   | BF203  | 25p    | GET188 | 30p | OC36     | 62p |
| 2N2221  | 25p   | 2N4289  | 17p   | AF128  | 37p   | BF204  | 25p    | GET189 | 30p | OC37     | 62p |
| 2N2222  | 30p   | 2N4290  | 17p   | AF128  | 37p   | BF205  | 25p    | GET190 | 30p | OC38     | 62p |
| 2N2270  | 47p   | 2N4291  | 17p   | AF129  | 72p   | BF206  | 47p    | GET191 | 30p | OC39     | 62p |
| 2N2271  | 47p   | 2N4292  | 17p   | AF130  | 72p   | BF207  | 47p    | GET192 | 30p | OC40     | 62p |
| 2N2368  | 17p   | 2N4303  | 47p   | AF181  | 42p   | BF208  | 47p    | GET193 | 30p | OC41     | 62p |
| 2N2369  | 17p   | 2N4304  | 47p   | AF182  | 42p   | BF209  | 47p    | GET194 | 30p | OC42     | 62p |
| 2N2369  | 17p   | 2N4305  | 47p   | AF183  | 42p   | BF210  | 47p    | GET195 | 30p | OC43     | 62p |
| 2N2369A | 17p   | 2N4306  | 47p   | AF184  | 42p   | BF211  | 47p    | GET196 | 30p | OC44     | 62p |
| 2N2410  | 42p   | 2N5029  | 47p   | AF280  | 62p   | BF242  | 37p    | GET197 | 30p | OC45     | 62p |
| 2N2483  | 37p   | 2N5030  | 42p   | AF281  | 32p   | BF243  | 37p    | GET198 | 30p | OC46     | 62p |
| 2N2484  | 37p   | 2N5031  | 42p   | AF282  | 32p   | BF244  | 37p    | GET199 | 30p | OC47     | 62p |
| 2N2589  | 30p   | 2N5174  | 52p   | ASV27  | 37p   | BF245  | 37p    | GET200 | 30p | OC48     | 62p |
| 2N2640  | 22p   | 2N5175  | 52p   | ASV28  | 37p   | BF246  | 37p    | GET201 | 30p | OC49     | 62p |
| 2N2613  | 35p   | 2N5176  | 45p   | ASV29  | 27p   | BF247  | 37p    | GET202 | 30p | OC50     | 62p |
| 2N2614  | 30p   | 2N5222A | 30p   | ASV36  | 25p   | BF248  | 37p    | GET203 | 30p | OC51     | 62p |
| 2N2646  | 52p   | 2N5223  | 30p   | ASV37  | 25p   | BF249  | 37p    | GET204 | 30p | OC52     | 62p |
| 2N2656  | 32p   | 2N5246  | 42p   | ASV38  | 32p   | BF250  | 37p    | GET205 | 30p | OC53     | 62p |
| 2N2711  | 25p   | 2N5249  | 47p   | ASV39  | 32p   | BF251  | 37p    | GET206 | 30p | OC54     | 62p |
| 2N2712  | 25p   | 2N5255  | 33-25 | ASV86  | 32p   | BF252  | 37p    | GET207 | 30p | OC55     | 62p |
| 2N2713  | 27p   | 2N5256  | 28-75 | AU103  | 11-25 | BF253  | 37p    | GET208 | 30p | OC56     | 62p |
| 2N2714  | 30p   | 2N5267  | 28-82 | ASV21  | 42p   | BF254  | 37p    | GET209 | 30p | OC57     | 62p |
| 2N2715  | 62p   | 2N5268  | 37p   | BF107  | 10p   | BF255  | 37p    | GET210 | 30p | OC58     | 62p |
| 2N2904  | 30p   | 2N5303  | 40p   | BC109  | 15p   | BF256  | 37p    | GET211 | 30p | OC59     | 62p |
| 2N2904A | 32p   | 2N5307  | 37p   | BC109  | 15p   | BF257  | 37p    | GET212 | 30p | OC60     | 62p |
| 2N2905  | 37p   | 2N5308  | 37p   | BC113  | 15p   | BF258  | 37p    | GET213 | 30p | OC61     | 62p |
| 2N2905A | 40p   | 2N5309  | 62p   | BC115  | 15p   | BF259  | 37p    | GET214 | 30p | OC62     | 62p |
| 2N2906  | 25p   | 2N5310  | 42p   | BC116A | 15p   | BF260  | 37p    | GET215 | 30p | OC63     | 62p |
| 2N2906A | 27p   | 2N5354  | 27p   | BC118  | 10p   | BF261  | 37p    | GET216 | 30p | OC64     | 62p |
| 2N2907  | 30p   | 2N5355  | 27p   | BC121  | 20p   | BF262  | 37p    | GET217 | 30p | OC65     | 62p |
| 2N2923  | 15p   | 2N5356  | 32p   | BC122  | 20p   | BF263  | 37p    | GET218 | 30p | OC66     | 62p |
| 2N2924  | 15p   | 2N5365  | 47p   | BC125  | 20p   | BF264  | 37p    | GET219 | 30p | OC67     | 62p |
| 2N2925  | 15p   | 2N5366  | 32p   | BC126  | 20p   | BF265  | 37p    | GET220 | 30p | OC68     | 62p |
| 2N2926  | 15p   | 2N5367  | 37p   | BC140  | 37p   | BF266  | 37p    | GET221 | 30p | OC69     | 62p |
| Green   | 14p   | 2N5457  | 77p   | BC147  | 10p   | BF267  | 37p    | GET222 | 30p | OC70     | 62p |
| Yellow  | 12p   | 2N5458  | 77p   | BC148  | 10p   | BF268  | 37p    | GET223 | 30p | OC71     | 62p |
| Orange  | 12p   | 2N5459  | 77p   | BC149  | 10p   | BF269  | 37p    | GET224 | 30p | OC72     | 62p |
| 2N3011  | 30p   | 2N5102  | 60p   | BC152  | 17p   | BF270  | 37p    | GET225 | 30p | OC73     | 62p |
| 2N3014  | 32p   | 2N5103  | 25p   | BC157  | 80p   | BF271  | 37p    | GET226 | 30p | OC74     | 62p |
| 2N3053  | 18p   | 2N5104  | 25p   | BC158  | 11p   | BF272  | 37p    | GET227 | 30p | OC75     | 62p |
| 2N3054  | 46p   | 2N5105  | 32p   | BC159  | 12p   | BF273  | 37p    | GET228 | 30p | OC76     | 62p |
| 2N3055  | 82p   | 2N5106  | 32p   | BC160  | 12p   | BF274  | 37p    | GET229 | 30p | OC77     | 62p |
| 2N3133  | 30p   | 2N5203  | 27p   | BC167  | 11p   | BF275  | 37p    | GET230 | 30p | OC78     | 62p |
| 2N3134  | 30p   | 2N5204  | 27p   | BC168  | 11p   | BF276  | 37p    | GET231 | 30p | OC79     | 62p |
| 2N3135  | 25p   | 2N5205  | 27p   | BC169  | 11p   | BF277  | 37p    | GET232 | 30p | OC80     | 62p |
| 2N3136  | 25p   | 2N5206  | 27p   | BC170  | 11p   | BF278  | 37p    | GET233 | 30p | OC81     | 62p |
| 2N3137  | 25p   | 2N5207  | 27p   | BC171  | 11p   | BF279  | 37p    | GET234 | 30p | OC82     | 62p |
| 2N3138  | 25p   | 2N5208  | 27p   | BC172  | 11p   | BF280  | 37p    | GET235 | 30p | OC83     | 62p |
| 2N3139  | 15p   | 2N5209  | 27p   | BC173  | 11p   | BF281  | 37p    | GET236 | 30p | OC84     | 62p |
| 2N3140  | 15p   | 2N5210  | 27p   | BC174  | 11p   | BF282  | 37p    | GET237 | 30p | OC85     | 62p |
| 2N3141  | 15p   |         |       |        |       |        |        |        |     |          |     |

# Now! A FAST EASY WAY TO LEARN BASIC RADIO & ELECTRONICS



Build as you learn with the exciting new **TECHNATRON** Outfit! No mathematics. No soldering—you learn the *practical way*.

Learn basic Radio and Electronics at home—the fast, modern way. Give yourself essential technical “know-how”—like reading circuits, assembling standard components, experimenting, building—quickly and without effort, and enjoy every moment. B.I.E.T.’s Simplified Study Method and the remarkable **TECHNATRON** Self-Build Outfit take the mystery out of the subject, making learning easy and interesting.

Even if you don’t know the first thing about Radio now, you’ll build your own Radio set within a month or so!

... and what’s more, you will understand exactly what you are doing. The **TECHNATRON** Outfit contains everything you need, from tools to transistors—even a versatile Multimeter which we teach you to use. All you need give is a little of your spare time and the surprisingly low fee, payable monthly if you wish. And the equipment remains yours, so you can use it again and again.

## You LEARN—but it’s as fascinating as a hobby

Among many other interesting experiments, the Radio set you build—and it’s a good one—is really a bonus. This is first and last a teaching course, but the training is as fascinating as any hobby and it could be the spring-board for a career in Radio and Electronics.

A 14-year-old could understand and benefit from this Course—but it teaches the real thing. The easy to understand, Practical Projects—from a burglar-alarm to a sophisticated Radio set—help you master basic Radio and Electronics—even if you are a “non-technical” type. And, if you want to make it a career, B.I.E.T. has a fine range of Courses up to City and Guilds standards.

## New Specialist Booklet

If you wish to make a career in Electronics, send for your FREE copy of “OPPORTUNITIES IN TELECOMMUNICATIONS / TV AND RADIO”. This brand new booklet—just out—tells you all about **TECHNATRON** and B.I.E.T.’s full range of courses.



# FREE

## BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY

Dept. B8, ALDERMASTON COURT, READING RG7 4PF

### POST THIS COUPON FOR FREE BOOK

To B.I.E.T. Dept. B8 Aldermaston Court, Reading RG7 4PF  
Please send books and full information — FREE and without obligation.



NAME..... AGE.....

ADDRESS.....

OCCUPATION.....

BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY

# WICKS FOR BARGAINS

## E.A. STEREO AMPLIFIER:

5 watts per channel; In attractive afrormosia veneered sleeve. Controls: On-off volume: Bass: Treble: Balance: Selector: Headphone Jack. Ceramic or Magnetic PU. Radio and Tape Inputs: Tape output and speaker output. Fully guaranteed 12 months parts. 6 months free service. Size 14½"W x 9½"D x 45"H approx. £16.50 inc. post.

## 3 WAY SPEAKER SYSTEM:

8" twin cone Bass speaker and 3" tweeter, fitted in extremely elegant teak veneered cabinet. Size: 18½"H x 11½"W x 10"D. 8 ohms handle 10 watts. £7.50 inc. Carr.

## GARRARD OFFERS

Garrard SP25 Mk III (Rec. Price (£15.85) Our Price £11.25. Carr. & Ins. 50p.

Garrard SP25 Mk III ready wired in beautiful teak plinth with tinted perspex cover. (Fitted with 5-pin DIN plug or phono plugs—state choice) (Rec. Price £23.19). Our Price £16. Carr. & Ins. 75p.

Or with choice of fitted cartridges.

SP25 Mk III/Sonotone 9TAHC (Rec. Price £27.29) Our Price £18. Carr. & Ins. 75p.

SP25 Mk III/Shure M3DM (Rec. Price £31.02) Our Price £20. Carr. & Ins. 75p.

SP25 Mk III/Goldring G800 (Rec. Price £36.19) Our Price £21. Carr. & Ins. 75p.

SP25 Mk III/Shure M55E (Rec. Price £36.16) Our Price £21. Carr. & Ins. 75p.

Note! Garrard SL65B (Automatic Changer version of SP25 Mk III) alternatively supplied—please add £3 to above prices.

Garrard AP76 (Rec. Price £27.85) Our Price £18.85. Carr. & Ins. 50p.

Garrard AP76 ready wired in beautiful teak plinth with perspex cover (fitted with 5 pin DIN or Phono plugs). Please state choice. (Rec. Price £39.85). Our Price £24.94 Carr. & Ins. 75p.

## OR WITH CHOICE OF FITTED CARTRIDGES.

Garrard AP76/Shure M3D (Rec. Price £47.26) Our Price £28.94. Carr. & Ins. 75p. Garrard AP76/Shure M55E (Rec. Price £52.82). Our Price £31.35. Carr. & Ins. 75p.

Garrard AP76/Goldring G800 (Rec. Price £52.82) Our Price £31.35. Carr. & Ins. 75p.

Garrard 2025TC fitted with stereo/mono cartridge. £8.99. Carr. Paid.

TEAK PLINTH & PERSPEX COVER Ready cut to take 2025TC, SP25 III, SL65B available at £4.99. Carr. & Ins. 35p.

## CARTRIDGES (All with diamond stylus)

Sonotone 9TAHC dia. Rec. Price £4.10. Our Price £1.99

Shure M3DM (Rec. Price £7.41) Our Price £4.87.

Shure M55E (Rec. Price £12.97) Our Price £9.00.

Goldring 800 (Rec. Price £13.00) Our Price £7.50.

Goldring 800 H (Rec. Price £10.69) Our Price £6.99.

P & P 18p any type

● Guaranteed all brand new best quality goods. No rubbish.

● Mail order only.

● All enquiries SAE please.

**Special Offer!**  
Grundig GDM312 Dynamic Microphones. List £7.35 OUR PRICE £3. P & P 30p

**Hi-Fi Stereo Headphones**  
(Value £5.00)  
Only £2.25 inc. post.

**Speaker Cloth**  
Best quality. Width 36". Under half price at 55p per yd. Black with gold fleck, will blend with any room setting. End of stock line, yds and yds must go.

## Plugs, Sockets and Leads.

Phono plugs; 3p each 30p per dozen.  
2 pin Din spkr. plugs 10p each.  
3 pin Din plugs. 15p each  
5 pin Din plugs. 15p each.  
5 pin Din sockets (chassis) 7p each.  
Stereo Jack Sockets c/cct. 13p each.  
Phono sockets (chassis) 2 way 3p; 3 way 4p; 4 way 5p.  
6ft. stereo lead 5 pin Din to open end, 45p  
6ft. stereo lead 2 pin phono to open end, 37p  
12ft. spkr. lead 2 pin Din to open end, 40p.  
Please add P & P 5p.

## 100 Mixed Resistors

½ watt 10% all best quality (no ex government) 40p.

## Pots

100K x 100K lns & Logs. stereo. 35p inc. post.  
100K DP switch stereo, log. 45p inc. post.  
50K single Balance. 15p inc. post.

**4 B.A. brass nuts**  
50 for 25p inc. post.

## Speaker cabinets

Attractively veneered in afrormosia, black front. Size approx. 7½"W x 9½"D x 4½"H. Ready cut to take 8" x 5" speaker. £1.99. P. & P. 12p.

**D. T. WICKS & CO.** 49 North Station Rd, Colchester, Essex.  
Tel: (0206) 78807

# TAKE 20

JULIAN ANDERSON

**A series of simple transistor projects, each using less than twenty components and costing less than one pound to build.**

**W**HAT's an automatic light?" you may well ask. Well, lights are only needed when it's dark, and a very simple electronic switch circuit can be made to turn a small light on as soon as the general light level drops below a certain level; this has its most obvious application in motor cars. Many parts of the country have local regulations requiring cars to display lights shortly after sunset, even when parked. In other areas car parking lights are needed only when the local street lighting is turned off, which in some areas is as late as 2 a.m. There cannot be many people who relish the thought of going out to their cars at that hour to turn on the porch or parking lights.

Porch lights which automatically turn themselves on after dusk are another application and although the circuit as shown is not really meant for this, many readers will realise the potential and modify the circuit to operate a thyristor or relay to apply the mains supply to the porch light.

## THE CIRCUIT

Like last month we are making use of a light dependent resistor, that is a resistor whose value in ohms falls with an increase in light falling on it. Also like last month this component is coupled into the base bias potential divider circuit, thus controlling the bias on the transistor, Tr1. R1 may have to be altered in value in order to make the "switch" operate at the correct light level.

As darkness falls, the potential at the base of Tr1 falls as the value of the LDR rises and after a certain point Tr1 begins to turn off, less current is passed and the potential between the emitter and the collector rises. This in turn starts to turn Tr2 on. This transistor, when light was falling on the LDR, thus holding Tr1 on, was off since the potential between base and emitter was held at a very low level due to the small potential across Tr1. As soon as Tr2 begins to conduct this increases the current through R4, thus causing Tr1 to cut off even more and in turn switching Tr2 more on. This action takes place very quickly and Tr2 is switched fully on, applying the supply voltage across the bulb causing it to light up.

This switching circuit is known as the *Schmitt Trigger* and a very useful circuit, it is too, with applications in many fields of electronics. As can be seen, only a few components are required and the switching action, using modern transistors, is very rapid and very positive. As soon as the potential at the base of Tr1 either reaches or falls to a preset level, Tr2 will switch.

The supply necessary to operate the circuit is taken directly from the car battery, though it is good practice to take this via the car's fuse as any

—continued overleaf

## No. 30 AUTOMATIC LIGHT

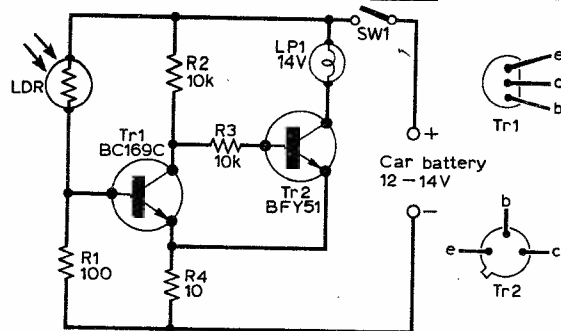


Fig. 1: The circuit of the automatic light with the lead connections of the transistors shown on the right.

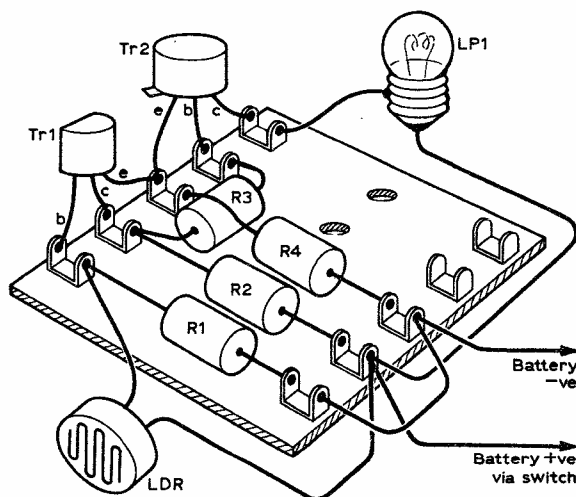


Fig. 2: A suggested component layout on a small piece of tag board.

## ★ components list

|                                                        |                               |     |
|--------------------------------------------------------|-------------------------------|-----|
| Tr1                                                    | BC169C                        | 10p |
| Tr2                                                    | BFY51                         | 20p |
| LDR                                                    | Light Dependent Resistor      | 40p |
| R1                                                     | 100Ω 10% 1W                   | 7p  |
| R2                                                     | 10kΩ 10% 1W                   | 7p  |
| R3                                                     | 10kΩ 10% 1W                   | 7p  |
| R4                                                     | 10Ω 10% 1W                    | 7p  |
| LP1                                                    | 14V LED Lamp Radiomarine 4000 | 12p |
| SW1                                                    | 1PDT toggle switch            | 5p  |
|                                                        |                               | 85p |
| † Electronic Ltd.                                      |                               |     |
| † J. G. Electronics Ltd.                               |                               |     |
| † Radiomarine Radio Store                              |                               |     |
| The Radiomarine Store is available from most main      |                               |     |
| component stores. Prices are those currently available |                               |     |
| and may have changed. No alternative is made for       |                               |     |
| material order. Date of the change and pricing         |                               |     |
| should be checked before ordering.                     |                               |     |



mistakes or serious component failure could create a fire risk.

Car batteries are capable of giving very high currents and therefore the quiescent current is of no great importance but it is in fact low, in the order of 2mA. The recommended bulb draws 40mA and it can be seen that these currents can be supplied by a number of dry batteries, though operation in this manner will not be cheap.

The bulb should last a considerable time as it is being slightly under-run; there is of course a small volts drop across R4 and Tr2.

## CONSTRUCTION

A suggested layout is shown in Fig. 2 but this is not critical. One point must be watched however; if the light from the bulb is allowed to fall onto the LDR it will switch the circuit in the same way that sunlight will. This will cause the circuit to oscillate; this can easily be seen as the bulb will flicker or flash. To avoid this the LDR must be pointed away from the bulb.

## WAVEMETER MONITOR—by R. F. GRAHAM

continued from page 530

ted. Tuning resonance is shown by maximum meter reading. In driver and similar circuits with small power, the wavemeter needs to be reasonably close to the circuit inductor. For P.A. and high power circuits, it can be at some small distance.

To check the frequency of low level multipliers and similar circuits, or those which are inaccessible, a link line may be used. This is twin flex or co-axial cable about 2ft. long with a loop of two or three turns each end. One loop is held near the equipment inductor, and the other near the wavemeter inductor. Clipping a lead to jack and aerial socket also allows the coil primaries to be used for coupling. Resonance will be shown by a dip in grid current in a subsequent stage.


To monitor the audio of an outgoing transmission, plug in phones, tune to resonance and situate the unit where pick-up gives adequate volume.

To tune an aerial, transmitter, tuner or coupling device for maximum radiation from the aerial, a vertical rod or wire is plugged into the aerial socket of the unit, which should be at some distance. Adjustments are then for maximum meter reading, which corresponds to maximum field strength. It is also possible to link couple a dipole or aerial-earth system to the wavemeter for this purpose, or take a short aerial to VC1, ignoring calibration.

The wavemeter produces no signal. It can be used to find bands on a t.r.f. receiver by adjusting the latter until oscillation just arises, and holding the wavemeter coil in line with the receiver coil. Resonance when tuning the wavemeter is then shown by the receiver going out of oscillation.
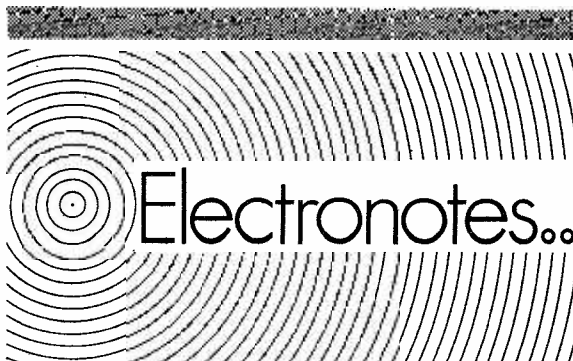
## BLUEPRINT SERVICE

We would like to draw readers' attention to the fact that the BLUEPRINT SERVICE has been discontinued and therefore no further BLUEPRINTS are available.



## S. GINSBERG

IN the beginning there were photocells enclosed in glass envelopes. Variations of these were more sensitive and multi-electrode secondary emission cells appeared like the 931A photomultiplier tube.

In more recent years, many experimenters, and indeed, most of the electronics industry too, has opted for solid state when thinking in terms of a light sensing device. An example here is the ORP12 light-dependent resistor, not to mention the earlier plastic-encapsulated transistors with some of their paint removed!

In America, work is currently proceeding on a technique known as charge coupling for imaging devices. One oxidised surface of a tiny silicon chip is covered with some 288 minute electrodes. These are arranged into groups of three, the last electrode in each group being a common conductor for the whole array.

The area immediately beneath each group of three elements forms a tiny light sensitive device in its own right. Minority carriers are generated in the silicon beneath the electrodes whenever light is focussed onto them. The greater the intensity of the light, the greater the charge, thus forming a direct relationship between light intensity and electrical charge.

The centre electrode of each group is purposely made more positive than the other two elements and thus the charges on minority carriers are attracted to, and congregate at, these centre electrodes.

Individual charges are next moved along the array from one electrode group to the next by putting a successively greater positive voltage on the electrode next to the one which is holding the charge. Eventually all the charges will have been passed along to the end of the device where they are collected by an output electrode.

Because the size of the charge will be dependent upon the amount of original light applied, the final electrode has, in effect, an analogue electrical signal which has a linear relationship to original light patterns of intensity.

How big is a 100,000µF capacitor—think of the size of some electrolytics. Now imagine how big a one Farad capacitor would be. Just to stretch the imagination even further, think of a 50 Farad capacitor. Fantastic—but they exist and are for sale. Twist in the tale is that the 50F is contained within one-third of a cubic inch. The devices will also retain their storage (if charged with a voltage) and leakage is so low that even after 16 months they will have retained over 97 per cent of the original charge. Think; they could be charged up and used as a form of battery. When discharged, they could simply be recharged again ad infinitum.

# SEW PANEL METERS

USED EXTENSIVELY BY INDUSTRY, GOVERNMENT DEPARTMENTS, EDUCATIONAL AUTHORITIES, ETC.  
 • LOW COST • QUICK DELIVERY • OVER 200 RANGES IN STOCK  
 • OTHER RANGES TO ORDER

## NEW "SEW" DESIGNS! CLEAR PLASTIC METERS BAKELITE PANEL METERS



**TYPESW.100**  
 100 x 80 mm.

|             |             |       |             |             |       |
|-------------|-------------|-------|-------------|-------------|-------|
| 500μA       | 20V. D.C.   | 22-97 | 500μA       | 50V. D.C.   | 22-97 |
| 500-0-500μA | 300V. D.C.  | 22-97 | 100μA       | 300V. D.C.  | 22-97 |
| 100μA       | 1 amp. D.C. | 22-97 | 100-0-100μA | 5 amp. D.C. | 22-97 |
| 100-0-100μA | 300V. D.C.  | 22-97 | 500μA       | 300V. D.C.  | 22-97 |
| 500μA       | 300V. D.C.  | 22-97 | 1mA         | VU Meter    | 22-97 |

**TYPE S-80**  
 80 mm. square fronts

|           |             |       |             |             |       |
|-----------|-------------|-------|-------------|-------------|-------|
| 50μA      | 20V. D.C.   | 22-97 | 500μA       | 50V. D.C.   | 22-97 |
| 50-0-50μA | 300V. D.C.  | 22-97 | 100μA       | 300V. D.C.  | 22-97 |
| 100μA     | 1 amp. D.C. | 22-97 | 100-0-100μA | 5 amp. D.C. | 22-97 |
| 500μA     | 300V. D.C.  | 22-97 | 500μA       | 300V. D.C.  | 22-97 |
| 1mA       | VU Meter    | 22-97 |             |             |       |

## "SEW" CLEAR PLASTIC METERS



**Type MR.35P. 4 1/4 in. x 4 1/4 in. fronts.**


|           |             |       |             |             |       |
|-----------|-------------|-------|-------------|-------------|-------|
| 50μA      | 20V. D.C.   | 22-97 | 500μA       | 50V. D.C.   | 22-97 |
| 50-0-50μA | 300V. D.C.  | 22-97 | 100μA       | 300V. D.C.  | 22-97 |
| 100μA     | 1 amp. D.C. | 22-97 | 100-0-100μA | 5 amp. D.C. | 22-97 |
| 500μA     | 300V. D.C.  | 22-97 | 500μA       | 300V. D.C.  | 22-97 |
| 1mA       | VU Meter    | 22-97 |             |             |       |

**Type MR.35P. 2 1/4 in. square fronts.**

|           |             |       |             |             |       |
|-----------|-------------|-------|-------------|-------------|-------|
| 50μA      | 20V. D.C.   | 22-97 | 500μA       | 50V. D.C.   | 22-97 |
| 50-0-50μA | 300V. D.C.  | 22-97 | 100μA       | 300V. D.C.  | 22-97 |
| 100μA     | 1 amp. D.C. | 22-97 | 100-0-100μA | 5 amp. D.C. | 22-97 |
| 500μA     | 300V. D.C.  | 22-97 | 500μA       | 300V. D.C.  | 22-97 |
| 1mA       | VU Meter    | 22-97 |             |             |       |

**Type MR.35P. 3 1/4 in. x 3 1/4 in. fronts.**

|           |             |       |             |             |       |
|-----------|-------------|-------|-------------|-------------|-------|
| 50μA      | 20V. D.C.   | 22-97 | 500μA       | 50V. D.C.   | 22-97 |
| 50-0-50μA | 300V. D.C.  | 22-97 | 100μA       | 300V. D.C.  | 22-97 |
| 100μA     | 1 amp. D.C. | 22-97 | 100-0-100μA | 5 amp. D.C. | 22-97 |
| 500μA     | 300V. D.C.  | 22-97 | 500μA       | 300V. D.C.  | 22-97 |
| 1mA       | VU Meter    | 22-97 |             |             |       |

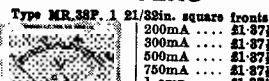

**Type MR.35P. 1 21/32 in. square fronts.**

|           |             |       |             |             |       |
|-----------|-------------|-------|-------------|-------------|-------|
| 50μA      | 20V. D.C.   | 22-97 | 500μA       | 50V. D.C.   | 22-97 |
| 50-0-50μA | 300V. D.C.  | 22-97 | 100μA       | 300V. D.C.  | 22-97 |
| 100μA     | 1 amp. D.C. | 22-97 | 100-0-100μA | 5 amp. D.C. | 22-97 |
| 500μA     | 300V. D.C.  | 22-97 | 500μA       | 300V. D.C.  | 22-97 |
| 1mA       | VU Meter    | 22-97 |             |             |       |

**Type MR.45P. 2 1/4 in. square fronts.**

|           |             |       |             |             |       |
|-----------|-------------|-------|-------------|-------------|-------|
| 50μA      | 20V. D.C.   | 22-97 | 500μA       | 50V. D.C.   | 22-97 |
| 50-0-50μA | 300V. D.C.  | 22-97 | 100μA       | 300V. D.C.  | 22-97 |
| 100μA     | 1 amp. D.C. | 22-97 | 100-0-100μA | 5 amp. D.C. | 22-97 |
| 500μA     | 300V. D.C.  | 22-97 | 500μA       | 300V. D.C.  | 22-97 |
| 1mA       | VU Meter    | 22-97 |             |             |       |

**Type MR.45P. 3 1/4 in. square fronts.**

|           |             |       |             |             |       |
|-----------|-------------|-------|-------------|-------------|-------|
| 50μA      | 20V. D.C.   | 22-97 | 500μA       | 50V. D.C.   | 22-97 |
| 50-0-50μA | 300V. D.C.  | 22-97 | 100μA       | 300V. D.C.  | 22-97 |
| 100μA     | 1 amp. D.C. | 22-97 | 100-0-100μA | 5 amp. D.C. | 22-97 |
| 500μA     | 300V. D.C.  | 22-97 | 500μA       | 300V. D.C.  | 22-97 |
| 1mA       | VU Meter    | 22-97 |             |             |       |

**Type MR.45P. 4 1/4 in. square fronts.**

|           |             |       |             |             |       |
|-----------|-------------|-------|-------------|-------------|-------|
| 50μA      | 20V. D.C.   | 22-97 | 500μA       | 50V. D.C.   | 22-97 |
| 50-0-50μA | 300V. D.C.  | 22-97 | 100μA       | 300V. D.C.  | 22-97 |
| 100μA     | 1 amp. D.C. | 22-97 | 100-0-100μA | 5 amp. D.C. | 22-97 |
| 500μA     | 300V. D.C.  | 22-97 | 500μA       | 300V. D.C.  | 22-97 |
| 1mA       | VU Meter    | 22-97 |             |             |       |

**Type MR.45P. 5 1/4 in. square fronts.**

|           |             |       |             |             |       |
|-----------|-------------|-------|-------------|-------------|-------|
| 50μA      | 20V. D.C.   | 22-97 | 500μA       | 50V. D.C.   | 22-97 |
| 50-0-50μA | 300V. D.C.  | 22-97 | 100μA       | 300V. D.C.  | 22-97 |
| 100μA     | 1 amp. D.C. | 22-97 | 100-0-100μA | 5 amp. D.C. | 22-97 |
| 500μA     | 300V. D.C.  | 22-97 | 500μA       | 300V. D.C.  | 22-97 |
| 1mA       | VU Meter    | 22-97 |             |             |       |

**Type MR.45P. 6 1/4 in. square fronts.**

|           |             |       |             |             |       |
|-----------|-------------|-------|-------------|-------------|-------|
| 50μA      | 20V. D.C.   | 22-97 | 500μA       | 50V. D.C.   | 22-97 |
| 50-0-50μA | 300V. D.C.  | 22-97 | 100μA       | 300V. D.C.  | 22-97 |
| 100μA     | 1 amp. D.C. | 22-97 | 100-0-100μA | 5 amp. D.C. | 22-97 |
| 500μA     | 300V. D.C.  | 22-97 | 500μA       | 300V. D.C.  | 22-97 |
| 1mA       | VU Meter    | 22-97 |             |             |       |


**Type MR.45P. 7 1/4 in. square fronts.**

**Type MR.45P. 8 1/4 in. square fronts.**
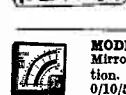
# MULTIMETERS for EVERY purpose!



**TECH PT-34.** 1,000 O.P.V. 0/10/50/250/500/1,000V. A.C. and D.C. 0/1/100/500mA. D.C. 0/100Ω. 1/100Ω. P. & P. 12p.



**MODEL TE-200** 20,000 O.P.V. Mirror scale, overload protection. 0/5/25/125/1,000 V.D.C. 0/10/50/250/1,000 V.A.C. 0/50 uA/250 mA. 0/600K/5 MegΩ. -20 to +62 db. 23-75. P. & P. 15p.



**MODEL TE-70.** 30,000 O.P.V. 0/15/60/300/600/1,200V. D.C. 0/5/30/120/600/1,200V. A.C. 0/30uA/3/300mA. 0/16K/160K/1.6M/16 MegΩ. 45-50. P. & P. 15p.




**MODEL TE-12** 20,000 O.P.V. 0/0.6/6/30/120/600/1,200/3,000/6,000V. D.C. 0/6/30/120/600/1,200V. A.C. 0/60uA/6/60/600mA. 0/6K/60K/6Meg. 60 MegΩ. 50pF. 0.2mF. 25-97. P. & P. 17p.



**MODEL PL436** 20KΩ/Volt D.C. 8KΩ/Volt A.C. Mirror scale. 0/5/12/30/120/600V D.C. 3/30/120/600V A.C. 50/600uA/60/600 mA. 10/100K/1 Meg/10 MegΩ. -20 to +46db. 25-97. P. & P. 12p.



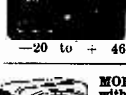**MODEL 500** 80,000 O.P.V. with overload protection. Mirror scale 0/5/25/10/25/100/250/500/1,000V. D.C. 1/2-5/10/25/100/250/500/1,000V. A.C. 0/50uA/5/50/500mA. 12 amp. D.C. 0/60K/6 Meg. 180 MegΩ. 25-97. Post paid.




**TEK MODEL TW-20CB FEATURING** RESETTABLE OVERLOAD BUTTERFLY. 20KΩ/Volt D.C. 5KΩ/Volt A.C. D.C. Volts: 0-0.5, 2.5, 10, 50, 250, 1,000V. A.C. Volts: 0-2.5, 10, 50, 250, 1,000V. D.C. Currents: 0-0.05, 0.5, 5, 50, 500mA. Resistance: 0-5K, 50K, 0-500K. 5 MEGΩ. Decibels: -20 to +52 db. 111-50. P. & P. 17p.



**TEK LAB TESTER.** 100,000 O.P.V. 6 1/2 in. Scale Buzzer Short Circuit Check. Sensitivity: 100,000 O.P.V. D.C. 5KΩ/Volt A.C. D.C. Volts: 0-0.5, 2.5, 10, 50, 250, 1,000V. A.C. Volts: 0-2.5, 10, 50, 250, 1,000V. D.C. Current: 0, 100uA, 10, 100, 500mA, 2.5, 10 amp. Resistance: 1K, 10K, 100K, 10MEG, 100 MEGΩ. Decibels: -10 to 49 db. Plastic Case with Carrying Handle. Size 7 1/4 in. x 3 1/4 in. 111-50. P. & P. 25p.



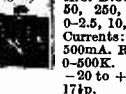
**270° WIDE ANGLE** 1mA METERS MW1-6 60mm square 23-97 MW1-8 80mm square 24-97 P. & P. extra




**TE-40 HIGH SENSITIVITY A.C. VOLTMEETER** 10 meg. Input 10 ranges: 01/003/1/3/13/130/100/300V. R.M.S. 4cps.-1-2 Mc/s. Decibels -40 to +50db. Supplied brand new complete with leads and instructions. Operation 230V. A.C. 117-50. Carr. 25p.



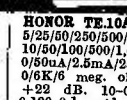
**TE-45 VALVE VOLTMEETER** High quality instrument with 28 ranges. D.C. volts 1-5-1,500V. A.C. volts 1-5-1,500V. Resistance up to 1,000 megohms. 200/240V. A.C. operation. Complete with probe and instructions. 117-50. P. & P. 30p. Additional probes available. R.F. 22-12; H.V. 22-50.



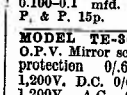
**HONOR TE-10A** 20KΩ/Volt 5/25/50/250/500/2,500 V. D.C. 10/50/100/500/1,000 V. A.C. 0/80uA/2.5mA/250mA. D.C. 0/6K/6 meg. ohm. -20 to +22 db. 10-0, 100 mid. 0.100-0.1 mfd. 23-47. P. & P. 15p.



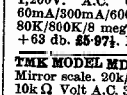
**MODEL TE-300.** 30,000 O.P.V. Mirror scale, overload protection. 0/6/3/15/60/300/1,200V. D.C. 0/6/30/120/600/1,200V. A.C. 0/30uA/6mA/60mA/300mA/600mA. 0/8K/80K/800K/8 meg. ohm -20 to +63 db. 25-97. P. & P. 15p.



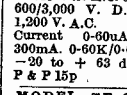
**TEK MODEL MD.120** Mirror scale. 20KΩ/Volt D.C. 10KΩ/Volt A.C. 0/30/60/300/600/600/3,000 V. D.C. 6/120/1,200 V.A.C. Current 0-60uA/0 -12/300mA. 0-60K/0-6 Mohms -20 to +63 db. 24-62. P. & P. 15p.



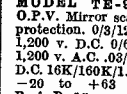
**MODEL TE-90** 50,000 O.P.V. Mirror scale, overload protection. 0/3/12/60/300/600/1,200 V. D.C. 0/6/30/120/600/1,200 V. A.C. Resistance D.C. 16K/160K/1.6M/16 MEGΩ. -20 to +63 db. 27-50. P. & P. 15p.



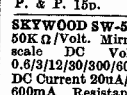
**SKYWOOD SW-500** 50KΩ/Volt. Mirror scale Dec. Volts 0.5/12/30/300/600/600K Current 20mA/60/100mA Resistance 10K/100K/1 Meg/10 Meg. Decibels -20 to +57 db. 27-50. P. & P. 15p.



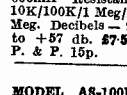
**MODEL AS-100D.** 100KΩ/Volt. 5in. mirror scale. Built-in meter protection 0/3/12/60/120/300/600/1,200 V. D.C. 0/6/30/120/300/600 V. A.C. 0/10mA/0/60/300mA/12 Amp. 0/2K/200K/2M/200KΩ. -20 to +17 db. 112-50. P. & P. 17p.



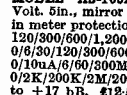
**TE-900** 20,000 O.P.V. VOLT GIANT MULTIMETER. Mirror scale and overload protection. 6in. full view meter. 2 colour scale. 0/2.5/10/250/1,000/5,000 V. A.C. 0/25/12.5/10/50/250/1,000/5,000 V. D.C. 0/50uA/110/100/500mA/10 amp. D.C. 0/2K/200K/20 MEG. OHM. 215. P. & P. 25p.



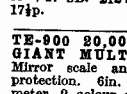
**FTC-401 TRANSISTOR TESTER** Full capabilities for measuring A, B and ICO. NPN or PNP. Equally adaptable for checking diodes. Supplied complete with instructions, battery and leads. 28-97. P. & P. 15p.




**HONEYWELL DIGITAL VOLTMEETER VT.100**

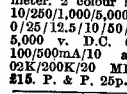


Can be panel or bench mounted. Basic meter measures 1 volt D.C. but can be used to measure a wide range of AC and DC volt, current and ohms with optional plug-in cards. Specification: Accuracy: ± 0.2 ± 1 digit. Resolution: 1mV. Number of digits: 3 plus fourth overrange digit. Overrange: 100% (up to 1.999) Input impedance: 1000 Meg ohm. Measuring cycle: 1 per second. Adjustment: Automatic zeroing, full scale adjustment against an internal reference voltage. Overload: to 100V. D.C. Input: Fully floating (3 poles). Input power: 110-230V. A.C. 50/60-cycles. Overall size: 5 1/2 in. x 2 1/2 in. x 3 1/2 in.

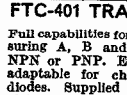




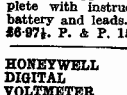
AVAILABLE BRAND NEW AND FULLY GUARANTEED AT APPROX. HALF PRICE



**£49-97 1/2 Carr. 50p.**

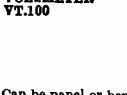

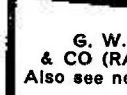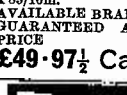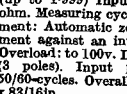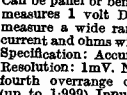**G. W. SMITH & CO (RADIO) LTD.** Also see next two pages



## \*MOVING IRON— ALL OTHERS MOVING COIL Please add postage

## SEW EDUCATIONAL METERS



**Type ED.107.** Size overall 100mm x 90mm x 108mm. A new range of high quality moving coil instruments ideal for school experiments and other bench applications. 3" mirror scale. The easily accessible to demonstrate internal working. Available in the following ranges:

|           |            |       |           |            |       |
|-----------|------------|-------|-----------|------------|-------|
| 50μA      | 20V. d.c.  | 23-97 | 50μA      | 50V. d.c.  | 23-97 |
| 100μA     | 20V. d.c.  | 23-97 | 100μA     | 50V. d.c.  | 23-97 |
| 1mA       | 300V. d.c. | 23-97 | 1mA       | 300V. d.c. | 23-97 |
| 50-0-50μA | 23-97      |       | 50-0-50μA | 23-97      |       |
| 1-0-1mA   | 23-97      |       | 1-0-1mA   | 23-97      |       |
| 1A d.c.   | 23-97      |       | 1A d.c.   | 23-97      |       |
| 5A d.c.   | 23-97      |       | 5A d.c.   | 23-97      |       |
| 10V d.c.  | 23-97      |       | 10V d.c.  | 23-97      |       |

## EDGWISE METERS

**Type FE.70.** 3 17/32 in. x 1 15/32 in. x 2 1/4 in. deep.

|             |           |       |             |           |       |
|-------------|-----------|-------|-------------|-----------|-------|
| 50μA        | 20V. d.c. | 23-97 | 50μA        | 50V. d.c. | 23-97 |
| 50-0-50μA   | 23-97     |       | 50-0-50μA   | 23-97     |       |
| 100μA       | 20V. d.c. | 23-97 | 100μA       | 50V. d.c. | 23-97 |
| 100-0-100μA | 23-97     |       | 100-0-100μA | 23-97     |       |
| 200μA       | 23-97     |       | 200μA       | 23-97     |       |

Send for illustrated brochure on SEW Panel Meters—discounts for quantities.

**ALL DEVICES BRAND NEW AND FULLY GUARANTEED**

|                            |          |            |          |      |
|----------------------------|----------|------------|----------|------|
| <b>Integrated Circuits</b> | FJH101   | 25p        | SN7430   | 23p  |
|                            | FJH111   | 75p        | SN7440   | 22p  |
|                            | FJH121   | 25p        | SN7441AN | 25p  |
| CA3000 130p                | FJH131   | 25p        |          | 87p  |
| CA3005 117p                | FJH141   | 25p        | SN7442   | 87p  |
| CA3007 282p                | FJH151   | 25p        | SN7446   | 126p |
| CA3011 76p                 | FJH161   | 70p        | SN7447   | 110p |
| CA3013 58p                 | FJH171   | 25p        | SN7448   | 100p |
| CA3015 105p                | FJH181   | 25p        | SN7450   | 23p  |
| CA3014 124p                | FJH221   | 25p        | SN7451   | 23p  |
| CA3018 94p                 | FJH231   | 25p        | SN7453   | 23p  |
| CA3018A                    | FJH241   | 25p        | SN7454   | 23p  |
|                            | FJH251   | 25p        | SN7460   | 23p  |
| CA3019 84p                 | FJH301   | 50p        | SN7472   | 35p  |
| CA3020 198p                | FJH311   | 25p        | SN7473   | 48p  |
| CA3020A                    | FJH321   | 60p        | SN7474   | 23p  |
|                            | FJH331   | 60p        | SN7475   | 47p  |
| CA3021 156p                | FJH341   | 125p       | SN7476   | 45p  |
| CA3022 130p                | FJH381   | 75p        | SN7483   | 87p  |
| CA3023 126p                | FJH391   | 65p        | SN7486   | 50p  |
| CA3026 100p                | FJH311   | 125p       | SN7480   | 100p |
| CA3028 74p                 | FJH321   | 125p       | SN7482   | 87p  |
| CA3028B                    | FJH331   | 125p       | SN7483   | 87p  |
|                            | FJH341   | 25p        | SN7486   | 87p  |
| CA3029 87p                 | IC10     | 250p       | SN7496   | 87p  |
| CA3029A                    | IC12     | 250p       | SN74107  | 43p  |
|                            | L800     | 40p        | SN74103  | 140p |
| CA3080 187p                | L81      | 40p        |          |      |
| CA3035 125p                | L923     | 40p        | SN74154  | 23p  |
| CA3036 72p                 | MC724P   | 60p        |          |      |
| CA3039 82p                 | MC780P   | 247p       | SN74160  |      |
| CA3041 109p                | MC788P   | 82p        |          | 180p |
| CA3042 109p                | MC780P   | 124p       | SN74161  |      |
| CA3043 125p                | MC792P   | 60p        |          | 180p |
| CA3045 125p                | MC799P   | 60p        | SN74164  |      |
| CA3045 125p                | MC1303L  |            |          | 230p |
| CA3046 81p                 |          | 282p       | SN74165  |      |
| CA3047 137p                | MC1304P  |            |          | 225p |
| CA3048 204p                |          | 275p       | SN74193  | 225p |
| CA3049 180p                | MC1305P  |            |          | 225p |
| CA3050 180p                |          | 386p       | SN74193  |      |
| CA3051 134p                | MC1383P  | 540p       | TAA241   |      |
| CA3052 168p                |          |            |          | 162p |
| CA3053 48p                 | MC1435P  |            |          |      |
| CA3054 109p                |          | 345p       | TAA242   | 425p |
| CA3055 240p                | MC1552C  |            |          | 150p |
| CA3059 180p                |          | 481p       | TAA243   | 150p |
| CA3064 120p                | MC1709CG |            | TAA263   | 75p  |
| FCH101 85p                 |          | 94p        | TAA293   | 87p  |
| FCH111 105p                | MFC4000P |            | TAA300   | 175p |
| FCH121 105p                |          | 112p       | TAA310   | 125p |
| FCH131 60p                 | PA232    | 457p       | TAA320   | 75p  |
| FCH141 60p                 | PA230    | 100p       | TAA350   | 147p |
| FCH151 105p                | PA234    | 100p       | TAA349   | 147p |
| FCH161 50p                 | PA237    | 185p       | TAA521   | 133p |
| FCH171 105p                | PA246    | 245p       | TAA522   | 360p |
| FCH181 105p                | PA244    | 235p       | TAA530   | 495p |
| FCH191 105p                | PA264    | 447p       | TAA811   | 445p |
| FCH201 105p                | MC724P   | 60p        | TAA101   | 97p  |
| FCH211 105p                | SN7400   | 23p        | TAD100   | 197p |
| FCH221 130p                | SN7401   | 23p        | TAD110   | 197p |
| FCH231 150p                | SN7402   | 23p        | SL403A   | 187p |
| FJH101 160p                | SN7403   | 23p        | SL702C   | 147p |
| FJH111 160p                | SN7404   | 23p        | U4702A   | 290p |
| FJH121 275p                | SN7405   | 23p        | U4703C   | 150p |
| FJH131 275p                | SN7406   | 40p        | U4708C   | 187p |
| FJH141 525p                | SN7408   | 23p        | U4709C   | 125p |
| FJH201 100p                | SN7409   | 23p        | U4710C   | 125p |
| FJH211 275p                | SN7410   | 23p        | U4716    | 187p |
| FOK101 480p                | SN7411   | 23p        | U4730C   | 162p |
| FOK201 180p                | SN7412   | 23p        | U4730C   | 162p |
| PCY101 105p                | SN7420   | 23p        | U4741C   | 87p  |
| <b>BRIDGE</b>              |          | 60 PIV 4A  | 80p      |      |
| <b>RECTIFIERS</b>          |          | 100 PIV 4A | 80p      |      |
| <b>PLASTIC</b>             |          | 200 PIV 4A | 75p      |      |
| <b>ENCAPSULATED</b>        |          | 400 PIV 4A | 80p      |      |
| 600 PIV 1A                 | 50p      | 50 PIV 6A  | 62p      | </   |


|       |        |              |       |
|-------|--------|--------------|-------|
| 3522A | 80p    | EL95         | 35p   |
| 3522B | 80p    | EM90         | 40p   |
| 3522C | 80p    | EM90         | 40p   |
| 3522D | 80p    | EM90         | 40p   |
| 35C15 | 60p    | EM34         | 35p   |
| 35C17 | 85p    | EM35         | 41-00 |
| 35C18 | 75p    | EM87         | 40p   |
| 35F05 | 85p    | ET61         | 40p   |
| 35F11 | 70p    | EY86         | 40p   |
| 35F13 | 92p    | EY87         | 40p   |
| 35F14 | 92p    | EY87         | 40p   |
| 35L14 | 80p    | EZ41         | 45p   |
| 35L15 | 85p    | EZ41         | 45p   |
| 35L17 | 80p    | EZ80         | 25p   |
| 35P12 | 80p    | EZ81         | 25p   |
| 35P19 | 80p    | GZ32         | 45p   |
| 35P21 | 70p    | GZ34         | 60p   |
| 35P23 | 80p    | GZ34         | 60p   |
| 35P44 | 90p    | KT88         | 42-00 |
| 35L5  | 50p    | MU14         | 60p   |
| 35W4  | 80p    | PBC80        | 60p   |
| 35Z4  | 80p    | PCC6         | 60p   |
| 35Z5  | 40p    | PCC8         | 60p   |
| 35Z6  | 40p    | PCC8         | 60p   |
| 50C5  | 40p    | PC900        | 43p   |
| 50    | 50p    | PC84         | 40p   |
| 50A   | 50p    | PC85         | 40p   |
| 1027  | 50p    | PC88         | 55p   |
| 1025  | 50p    | PC88         | 55p   |
| 5768  | 70p    | PC189        | 55p   |
| 5769  | \$1.00 | PC189        | 55p   |
| AZ31  | 50p    | PCF82        | 34p   |
| CY31  | 35p    | PCF84        | 50p   |
| DAF91 | 25p    | PCF86        | 50p   |
| DAF96 | 42p    | PCF80        | 80p   |
| DF81  | 25p    | PCF80        | 80p   |
| DF82  | 25p    | PCF80        | 80p   |
| DK91  | 35p    | PCF805       | 75p   |
| DK92  | 50p    | PCF806       | 75p   |
| DK96  | 42p    | PCF808       | 75p   |
| DL92  | 42p    | PLC82        | 35p   |
| DL94  | 42p    | PLC85        | 60p   |
| DM70  | 42p    | PLC85        | 60p   |
| DM82  | 42p    | PLC85        | 60p   |
| DY86  | 33p    | PLF80        | 40p   |
| DY87  | 35p    | PLF82        | 75p   |
| EH80C | 65p    | PL86         | 55p   |
| EH80F | 65p    | PL82         | 55p   |
| ECB50 | 60p    | PL82         | 55p   |
| EA745 | 25p    | PL83         | 45p   |
| EB41  | 20p    | PL84         | 40p   |
| EB41  | 55p    | PL500        | 75p   |
| ECB81 | 30p    | PL504        | 80p   |
| EBR80 | 60p    | PY32         | 55p   |
| EBF83 | 40p    | FY33         | 55p   |
| EBF85 | 40p    | FY36         | 55p   |
| EBL21 | 60p    | FY81         | 30p   |
| EC86  | 60p    | FY82         | 30p   |
| EC88  | 60p    | FY83         | 35p   |
| EC89  | 60p    | FY88         | 35p   |
| EC940 | 60p    | FY88         | 35p   |
| EC984 | 30p    | FY800        | 50p   |
| EC985 | 30p    | FY801        | 50p   |
| EC988 | 40p    | U25          | 75p   |
| ECF80 | 35p    | U26          | 75p   |
| ECF82 | 35p    | U50          | 32p   |
| ECF86 | 65p    | U82          | 35p   |
| ECM21 | 67p    | U81          | 75p   |
| ECM22 | 67p    | U81          | 75p   |
| ECM42 | 70p    | U282         | 40p   |
| ECM81 | 30p    | U301         | 40p   |
| ECM83 | 40p    | U801         | 41-00 |
| ECI80 | 40p    | UBC80        | 35p   |
| ECI82 | 35p    | UBA42        | 55p   |
| ECI83 | 35p    | UBA41        | 40p   |
| ECI86 | 40p    | UBC81        | 35p   |
| EF97A | 40p    | UBF80        | 35p   |
| EF99  | 40p    | UBF89        | 35p   |
| EF40  | 50p    | UC084        | 45p   |
| EF46  | 65p    | UC085        | 45p   |
| EF48  | 65p    | UCF80        | 55p   |
| EF80  | 25p    | UCM21        | 60p   |
| EF85  | 35p    | UCH42        | 70p   |
| EF86  | 30p    | UCM81        | 35p   |
| EF89  | 35p    | UCL82        | 35p   |
| EF91  | 33p    | UCL53        | 60p   |
| EF92  | 33p    | UCL53        | 60p   |
| EFI83 | 30p    | UF80         | 35p   |
| EFI84 | 35p    | UF85         | 40p   |
| EH90  | 40p    | UF89         | 35p   |
| EL34  | 50p    | UL41         | 65p   |
| EL35  | 41-25  | UL54         | 80p   |
| EL36  | 40p    | UL54         | 80p   |
| EL42  | 55p    | UY85         | 30p   |
| EL81  | 65p    | VR105/30/35p |       |
| EL84  | 25p    | VR150/30/35p |       |
| EL85  | 25p    | AD12p in 3s  |       |
| EL91  | 32p    | for postage  |       |

| RECTIFIERS |     |      |     |
|------------|-----|------|-----|
| BA164      | 12p | GJ7M | 37p |
| BAK13      | 12p | OA5  | 70p |
| BAK14      | 12p | OA5  | 70p |
| BAY31      | 7p  | OA10 | 20p |
| BAY38      | 17p | OA9  | 19p |
| BY100      | 15p | OA47 | 7p  |
| HY103      | 25p | OA70 | 70p |
| YI122      | 87p | OA73 |     |

# HI-FI EQUIPMENT

## SAVE UP TO 33 1/3% OR MORE
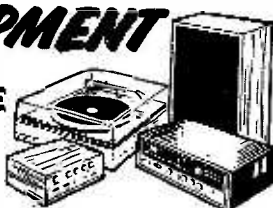
### SEND S.A.E. FOR DISCOUNT PRICE LISTS AND PACKAGE OFFERS!



## RECORD DECKS

|                 |        |
|-----------------|--------|
| B.S.R.          |        |
| Mini Mono†      | £4-97  |
| Q125*           | £8-70  |
| MP60            | £11-30 |
| 610             | £15-15 |
| 510             | £12-47 |
| 310             | £10-55 |
| MP60 T.P.D.I.   | £18-75 |
| MP60 T.P.D.2    | £17-55 |
| 610 T.P.D.1     | £22-12 |
| 510 T.P.D.1     | £20-19 |
| 210 Package*    | £11-30 |
| H.T.70          | £16-90 |
| Mini 70 Package | £24-00 |
| THORENS         |        |
| TD125           | £59-85 |
| TD125AB         | £94-25 |
| TX25            | £6-70  |
| TD150AII        | £34-60 |
| TD150ABII       | £41-35 |
| TX11            | £3-77  |

† Mono \* Stereo Cartridge  
All other models less Carriage  
Carriage 50p extra any model.

## RECORD DECK PACKAGES


Decks supplied ready wired in plinth and cover fitted with cartridge.

Garrard 2025 T/C with Sonotone STACD £18-95  
Garrard SP20II Goldring G800... £18-95  
Garrard AP78 Goldring G800... £21-00  
BSR MP60 Audio Technica AT.55... £27-50  
Goldring GL69/2 Goldring G800... £45-50  
Goldring GL75 Goldring G800E... £45-50  
Carriage 50p extra any model.



|           |        |
|-----------|--------|
| GARRARD   |        |
| A40 II*   | £8-40  |
| 2025 T/C* | £8-50  |
| 3500*     | £9-75  |
| SP25 III  | £11-80 |
| AP70 II   | £11-97 |
| SL65B     | £14-40 |
| AP76      | £20-20 |
| SL72B     | £26-00 |
| SL75B     | £27-50 |
| SL95B     | £37-00 |
| 401       | £38-40 |
| GOLDRING  |        |
| GL69/2    | £21-25 |
| GL69P/3   | £28-50 |
| GL75      | £28-97 |
| GL75P     | £38-50 |
| LID99/75  | £21-40 |
| G99       | £21-97 |
| PIONEER   |        |
| PL12AC    | £38-50 |

## TELETON SAQ-206 STEREO AMPLIFIER

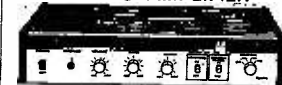

Latest exciting release. Brand new model. 6 + 6 watts rms. Inputs for mag. xtal, aux tape. Volume, bass, treble, sliding balance, scratch filter and loudness controls. List £32.50 OUR PRICE £18.50 Carr. 37p.

## TELETON SPECIAL OFFER!



CR10T AM/FM STEREO TUNER AMPLIFIER WITH MATCHING PAIR SA1003 SPEAKER SYSTEMS. Output 4 watts per channel. Excellent reception. AFC, built-in MPX. Cer/XTAL Input. Total List £50-25. OUR PRICE £29-95. Carr. 62p. Also available with Garrard 2025T/C Record Changer, Plinth, cover and stereo cartridge. Ready wired £42-50. Carr. £1-00.

## ★ TRANSISTORISED FM TUNER

6 TRANSISTOR HIGH QUALITY TUNER. SIZE ONLY 6x4x2 1/2 in. 3 I.F. stages. Double tuned discriminator. Auto tune to feed most output to feed most amplifiers. Operates on 9 V battery. Coverage 88-108Mc/s. Ready built ready for use. Fantastic value for money. £6-97. P. & P. 12p. Stereo multiplex adapters £4-97.



TE-1085 STEREO HEADPHONES  
Low cost high performance stereo headphones. Foam rubber ear cups. Adjustable head-band. 8 ohm impedance. 25-18,000 Hz. With lead and stereo jack plug. ONLY £1-97. P. & P. 12p

## BELCO DA-20 SOLID STATE DECADE AUDIO OSCILLATOR


New high quality portable instrument. Sine 1 Hz to 100 KHz. Square 20 Hz to 20 KHz. Output max + 10 dB (10 K ohms). Operation 220/240V. A.C. Size 216mm x 150mm x 120mm. Price £27-50. Carr. 25p.

## TE-20 RF SIGNAL GENERATOR

Accurate wide range signal generator covering 120 kc/s-200 Mc/s on 6 bands. Directly calibrated variable R.F. attenuator. Operation 200/240V a.c. Brand new with instructions. £15. P. & P. 37p. S.A.E. for details.

B.C. 221 FREQUENCY METERS  
latest release 125 KHz-20 MHz. Excellent condition. Fully tested and checked and complete with calibrator charts. £27-50 each. Carr. 50p.
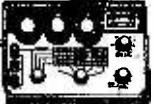
## TRANSISTORISED L.C.R. A.C. MEASURING BRIDGE



A new portable bridge offering excellent range and accuracy at low cost. Ranges: R. 1 G-11 meg Ω. L. 1 μ H - 111 HENRY'S. C. 2 pF-1110 pF. 6 Ranges ± 2%. TURNS RATIO 1:1/1000-1:1110. 6 Ranges ± 1%. Bridge voltage at 1,000 cps. Operates from 9 volts. 100μA. Meter indication. Attractive 2 tone metal case. Size 7 1/4 x 5 x 2 1/2 in. £20. P. & P. 25p



TE-16A Transistorised Signal Generator. 5 ranges 400KHz-30MHz. An inexpensive instrument for the handyman. Operates on 9v battery. Wide easy to read scale. 800KHz modulation. 5 1/4 x 5 1/4 x 3 1/4 in. Complete with instructions and leads. £7-97. P. & P. 20p.

## LAFAYETTE TE-46 RESISTANCE CAPACITY ANALYSER

2 pF-2000 mFΩ. 20 ohms 200 megohms. Also checks impedance, turns ratio, insulation. 200/250V. A.C. Brand New £17-50. Carr. 37p.

## RUSSIAN 22 RANGE MULTIMETER

Model U437 20,000 o.p.v. A first class versatile instrument manufactured in U.S.S.R. to the highest standards. Ranges: 2-5/10/50/250/500/1000V D.C. 2-5/10/50/250/500/1000V A.C. DC Current 100 uA/1/10/100mA/1A. Resistance 300 ohms/3/30/300K/3M Ω. Complete with batteries, test leads, instructions and sturdy steel carrying case. OUR PRICE £5-97 P. & P. 25p.

## RUSSIAN C1-16 DOUBLE BEAM OSCILLOSCOPES

5 MHz Pass Band, Separate Y1, Y2 amplifiers. Calibrated triggered sweep from .2 sec to 100 milli sec/cm. Supplied complete with all accessories and instructions £87. Carr. paid.

## TE111. DECADE RESISTANCE ATTENUATOR

Variable range 0-111dB. Connections. Unbalanced T and Bridge T. Impedance 600 Ω range (0.1dB x 10) + (1dB x 10) + 10 + 20 + 30 + 40dB. Frequency d.c. to 500KHz. Accuracy: 0.05dB. + Indication dB. 0.01. Maximum input less than 4W (50V). Built in 600 Ω load resistance with internal/external switch. Brand new. £27-50. P. & P. 25p.

## ROUND SCALE TYPE PENCIL TESTER MODEL TS.68

Completely portable, simple to use pocket sized tester. Ranges 0/3/30/300V AC and DC at 2,000 o.p.v. Resistance 0-20K ohms. ONLY £1-97 P. & P. 13p.

## POWER RHEOSTATS

High quality ceramic construction. Windings embedded in vitreous enamel. Heavy duty brush wiper. Continuous rating. Wide range ex-stock. Single hole fixing, 1/4 in. dia. shafts. Bulk quantities available. 50 WATT. 10/25/50/100/250/500/1000/1500/2500 or 5000 ohms, 72p. P. & P. 7p. 100 WATT. 10/25/50/100/250/500/1000/1500/2500 or 5000 ohms, £1-06 P. & P. 7p. 500 WATT. 15/25/50/100/250/500/1000 or 2500 ohms, £1-37 P. & P. 7p.

## "YAMABISHI" VARIABLE VOLTAGE TRANSFORMERS

Excellent quality . Low price . Immediate delivery  
S-800 General Purpose Bench Mounting  
1 Amp £5-50  
2.5 Amp £6-75  
5 Amp £9-75  
8 Amp £14-50  
10 Amp £18-50  
12 Amp £21-00  
20 Amp £27-00  
S-250B Panel Mounting  
1 Amp £5-50  
2.5 Amp £6-62  
Please add postage  
ALL MODELS  
INPUT 230 VOLTS,  
50/60 CYCLES,  
OUTPUT VARIABLE  
0-260 VOLTS.  
Special discounts for quantity



## UR-1A SOLID STATE COMMUNICATION RECEIVER

4 Bands covering 550kc/s-30mc/s. PET, 8 Meter, Variable BFO for SSB, Built-in Speaker, Bandspeed, Sensitivity Control. 220/240V. A.C. or 12V D.C. 10 1/2 x 4 1/2 x 7 1/2 in. Brand new with instructions. £25. Carr. 37p.



## UNR-30 RECEIVER

4 Bands covering 550kc/s-30mc/s. B.F.O. Built-in Speaker 220/240V. A.C. Brand new with instructions. £15-75. Carr. 37p.

## LAFAYETTE HA-600 SOLID STATE RECEIVER

General coverage 150-400kc/s, 550 kc/s-30mc/s. PET front end. 2 mech. filters, product detector, variable B.F.O., noise limiter, S. Meter, Bandspeed. RF Gain. 15" x 9 1/2" x 8 1/2". 18 lbs. 220/240V. A.C. or 12V D.C. Brand new with instructions. £45. Carr. 50p.

## CRYSTAL CALIBRATORS NO. 10

Small portable crystal calibrator. Size 7 x 7 x 4 in. Frequency range 500 Kc/s-10 Mc/s (up to 30 Mc/s on harmonic). Calibrates dial. Power requirements 300V. D.C. 15mA and 12V D.C. 0.3A. Excellent condition. £4-47. Carr. 37p.

## SOLID STATE VARIABLE A.C. VOLTAGE REGULATORS

Compact and panel mounting. Ideal for control of lamps, drills, electrical appliances etc. Input 230/240V. A.C. Output continuously variable from 20v-230v. Model MR 3305 5 amp 58 x 45 x 45mm £3-71. £11-97. Postage 12p.

## AUTO TRANSFORMERS


0/15/250V. Step up or step down. Fully shrouded.  
150 W. £2-37 P. & P. 17p  
300 W. £2-25 P. & P. 22p  
500 W. £4-97 P. & P. 32p  
1000 W. £7-47 P. & P. 42p  
1500 W. £8-97 P. & P. 42p  
5000 W. £38-00 P. & P. £1

## VOLTAGE STABILISER TRANSFORMERS

180-260V. input. Output 230v. Available 150w or 225w. £12-50. Carr. 25p.
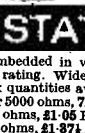
## 230 VOLT A.C. 50 CYCLES RELAYS

Brand new 3 sets of changeover contacts at 5 amp rating. 50p each. P. & P. 10p (100 lots £40) Quantities available.



## SINCLAIR EQUIPMENT

Project 60. Package offers.



2 x Z80 amplifier, stereo 60 pre-amp, PZ5 power supply. £12-75 Carr. 37p. Or with PZ8 power supply £18-95 Carr. 37p. 2 x Z80 amplifier, stereo 60 pre-amp, PZ8 power supply. £20-25 Carr. 37p. Transformer for PZ8. £2-97 extra. Add to any of the above £4-97 for active filter unit and £16 for a pair of Q16 speakers. Project 60 FM Tuner £20-97. Carr. 37p. All other Sinclair products in stock. 2000 Amp £24-50 Carr. 37p.; 3000 Amp £31-50 Carr. 37p.; Neoteric Amp £45-97 Carr. 37p. IC10/IC12 £2-50

## LATEST CATALOGUE



SEND NOW!  
•  
STILL ONLY 37 1/2 P  
P & P 10p

Our new 6th edition gives full details of a comprehensive range of HI-FI EQUIPMENT, COMPONENTS, TEST EQUIPMENT and COMMUNICATIONS EQUIPMENT. FREE DISCOUNT COUPONS VALUE 50p 272 pages, fully illustrated and detailing thousands of bargains.

# G.W.SMITH & CO. (RADIO) LTD

27 TOTTENHAM CT. RD. LONDON, W.1  
3 Lisle Street, London, W.C.2  
34 Lisle Street, London, W.C.2  
311 EDGWARE ROAD, LONDON, W.2

Tel: 01-636 3715  
Tel: 01-437 8204  
Tel: 01-437 9155  
Tel: 01-262 0387

All Mail Orders to:-  
11-12, Redington Green,  
London W.2  
Tel: 01-262 6562  
Trade supplied

OPEN 9-5 MONDAY TO SATURDAY



# BENTLEY ACOUSTIC CORPORATION LTD.

38 CHALCOT ROAD, CHALK FARM, LONDON, N.W.1  
THE VALVE SPECIALISTS Telephone 01-722-9090

|        |      |        |     |         |       |           |       |         |       |        |       |       |       |        |        |          |        |         |      |       |       |       |       |       |       |       |     |
|--------|------|--------|-----|---------|-------|-----------|-------|---------|-------|--------|-------|-------|-------|--------|--------|----------|--------|---------|------|-------|-------|-------|-------|-------|-------|-------|-----|
| 0A2    | .30  | 6CL6   | .48 | 6X5GT   | .25   | 20P1      | .88   | AC/TP   | .98   | ECC81  | .18   | EL93  | .34   | PC84   | .28    | PKX25    | 1.16   | UL84    | .81  | AC176 | .55   | BF194 | .15   | OA202 | .10   |       |     |
| 0B2    | .30  | 6CU5   | .50 | 7A7     | .88   | 20P3      | .88   | AL90    | .78   | ECC82  | .19   | EL94  | .34   | PC85   | .28    | PKY32/50 | .50    | UM80    | .53  | AC177 | .28   | BFY90 | .32   | OA202 | .08   |       |     |
| 1A7GT  | .33  | 6CW4   | .63 | 7B7     | .38   | 20P4      | .89   | ATP4    | .12   | ECC83  | .22   | EL95  | .34   | PC88   | .48    | PKY80    | .33    | UT21N   | .91  | AC178 | .25   | BFY61 | .19   | OA203 | .38   |       |     |
| 1B3GT  | .37  | 6DE7   | .50 | 7B7     | .38   | 20P6      | 1.00  | AZ1     | .40   | ECC84  | .28   | EL96  | .34   | PC89   | .48    | PKY81    | .33    | UT21    | .55  | AC180 | .20   | BFY92 | .20   | OA204 | .38   |       |     |
| 1B5GT  | .38  | 6D10   | .50 | 7C6     | .30   | 20A6G     | .29   | AZ31    | .40   | ECC85  | .25   | EL97  | .34   | PC90   | .48    | PKY82    | .25    | UT25    | .55  | AC181 | .20   | BFY93 | .20   | OA205 | .38   |       |     |
| 1L4    | .18  | 6EW6   | .55 | 7H7     | .23   | 25L6G     | .22   | AZ41    | .53   | ECC86  | .40   | EL98  | .34   | PC92   | .30    | PKY83    | .28    | UT85    | .25  | ACY20 | .18   | BY105 | .18   | OA206 | .38   |       |     |
| 1N3GT  | .37  | 6F1    | .59 | 7R7     | .65   | 25Y5      | .38   | CL33    | .90   | ECC87  | .35   | EL99  | .34   | PC95   | .30    | PKY84    | .28    | UT85    | .25  | ACY21 | .18   | BY114 | .18   | OA207 | .60   |       |     |
| 1R5    | .27  | 6F6    | .63 | 7Z4     | .50   | 25Y6G     | .43   | CY1C    | .53   | ECC88  | .44   | EL100 | .34   | PCF86  | .44    | PKY85    | .33    | UT18/20 | .75  | ACY28 | .18   | BY127 | .18   | OA208 | .60   |       |     |
| 1R4    | .22  | 6F6G   | .25 | 9D7     | .78   | 25Z4G     | .30   | CY31    | .31   | ECC89  | .54   | EL101 | .34   | PCF87  | .44    | PKY86    | .33    | UT18    | .75  | ACY29 | .18   | BY128 | .18   | OA209 | .60   |       |     |
| 1U4    | .29  | 6F13   | .33 | 10C1    | 1.25  | 25Z5      | .40   | DAF91   | .20   | ECC90  | .70   | EL102 | .34   | PCF88  | .44    | PKY87    | .33    | UT18    | .75  | ACY30 | .18   | BY129 | .18   | OA210 | .60   |       |     |
| 1U5    | .48  | 6F14   | .43 | 10C2    | .50   | 25Z6G     | .43   | DAF96   | .20   | ECC91  | .70   | EL103 | .34   | PCF89  | .44    | PKY88    | .33    | UT18    | .75  | ACY31 | .18   | BY130 | .18   | OA211 | .60   |       |     |
| 2D21   | .35  | 6F18   | .45 | 10D17   | .50   | 30C1      | .28   | DF91    | .14   | ECC92  | .70   | EL104 | .34   | PCF90  | .44    | PKY89    | .33    | UT18    | .75  | ACY32 | .18   | BY131 | .18   | OA212 | .60   |       |     |
| 2Z4C   | .35  | 6F22   | .68 | 10F9    | .45   | 30C15     | .60   | DF96    | .38   | ECC93  | .65   | EL105 | .34   | PCF91  | .44    | PKY90    | .33    | UT18    | .75  | ACY33 | .18   | BY132 | .18   | OA213 | .60   |       |     |
| 3Q4    | .38  | 6F24   | .68 | 10F18   | .35   | 30C17     | .77   | DF97    | .63   | ECC94  | .65   | EL106 | .34   | PCF92  | .44    | PKY91    | .33    | UT18    | .75  | ACY34 | .18   | BY133 | .18   | OA214 | .60   |       |     |
| 3Q5GT  | .35  | 6F25   | .68 | 10LD11  | .53   | 30C18     | .60   | DF176   | .68   | ECC95  | .68   | EL107 | .34   | PCF93  | .44    | PKY92    | .33    | UT18    | .75  | ACY35 | .18   | BY134 | .18   | OA215 | .60   |       |     |
| 3S4    | .27  | 6F28   | .70 | 10P13   | .54   | 30F5      | .70   | DK40    | .25   | ECC96  | .61   | EL108 | .34   | PCF94  | .44    | PKY93    | .33    | UT18    | .75  | ACY36 | .18   | BY135 | .18   | OA216 | .60   |       |     |
| 3V4    | .32  | 6F28   | .15 | 10P14   | 1.10  | 30F11     | .60   | DK92    | .38   | ECC97  | .27   | EL109 | .34   | PCF95  | .44    | PKY94    | .33    | UT18    | .75  | ACY37 | .18   | BY136 | .18   | OA217 | .60   |       |     |
| 5V4G   | .35  | 6GHR8A | .50 | 12A6    | .63   | 30F12     | .60   | DK96    | .65   | ECC98  | .39   | EL110 | .34   | PCF96  | .44    | PKY95    | .33    | UT18    | .75  | ACY38 | .18   | BY137 | .18   | OA218 | .60   |       |     |
| 5Y3GT  | .28  | 6GUT   | .50 | 12AC6   | .40   | 30F12     | .70   | DL96    | .65   | ECC99  | .34   | EL111 | .34   | PCF97  | .44    | PKY96    | .33    | UT18    | .75  | ACY39 | .18   | BY138 | .18   | OA219 | .60   |       |     |
| 6Z4C   | .35  | 6H3GT  | .15 | 12AD6   | .40   | 30F14     | .65   | DM70    | .38   | ECC100 | .65   | EL112 | .34   | PCF98  | .44    | PKY97    | .33    | UT18    | .75  | ACY40 | .18   | BY139 | .18   | OA220 | .60   |       |     |
| 6/30L2 | .55  | 6J5G   | .19 | 12AE6   | .48   | 30L1      | .29   | DM71    | .38   | ECC101 | .65   | EL113 | .34   | PCF99  | .44    | PKY98    | .33    | UT18    | .75  | ACY41 | .18   | BY140 | .18   | OA221 | .60   |       |     |
| 6A8G   | .33  | 6J5GT  | .29 | 12AT6   | .33   | 30L15     | .58   | DY87/8  | .25   | ECC102 | .52   | EL114 | .34   | PCF100 | .44    | PKY99    | .33    | UT18    | .75  | ACY42 | .18   | BY141 | .18   | OA222 | .60   |       |     |
| 6AC7   | .15  | 6J6    | .18 | 12AT7   | .16   | 30L17     | .69   | DY802   | .37   | ECC103 | .55   | EL115 | .34   | PCF101 | .44    | PKY100   | .33    | UT18    | .75  | ACY43 | .18   | BY142 | .18   | OA223 | .60   |       |     |
| 6A6G   | .25  | 6J7G   | .24 | 12AU6   | .21   | 30P4MR    | .95   | E80F    | 1.20  | ECC104 | .55   | EL116 | .34   | PCF102 | .44    | PKY101   | .33    | UT18    | .75  | ACY44 | .18   | BY143 | .18   | OA224 | .60   |       |     |
| 6AK5   | .25  | 6J7GT  | .38 | 12AU7   | .19   | 30P12     | .69   | E83F    | 1.20  | ECC105 | .68   | EL117 | .34   | PCF103 | .44    | PKY102   | .33    | UT18    | .75  | ACY45 | .18   | BY144 | .18   | OA225 | .60   |       |     |
| 6AM5A  | .50  | 6K7G   | .10 | 12AV6   | .28   | 30P19     | .69   | E88CC   | .60   | ECC106 | .63   | EL118 | .34   | PCF104 | .44    | PKY103   | .33    | UT18    | .75  | ACY46 | .18   | BY145 | .18   | OA226 | .60   |       |     |
| 6AN8   | .49  | 6K7GT  | .18 | 12B6    | .40   | 30P4      | .55   | E90CC   | .40   | ECC107 | .63   | EL119 | .34   | PCF105 | .44    | PKY104   | .33    | UT18    | .75  | ACY47 | .18   | BY146 | .18   | OA227 | .60   |       |     |
| 6AQ5   | .22  | 6K8G   | .16 | 12BA6   | .30   | 30P11     | .59   | E180F   | .90   | ECC108 | .63   | EL120 | .34   | PCF106 | .44    | PKY105   | .33    | UT18    | .75  | ACY48 | .18   | BY147 | .18   | OA228 | .60   |       |     |
| 6AT6   | .18  | 6L1    | .98 | 12BE6   | .30   | 30P113    | .75   | E192CC1 | .13   | ECC109 | .63   | EL121 | .34   | PCF107 | .44    | PKY106   | .33    | UT18    | .75  | ACY49 | .18   | BY148 | .18   | OA229 | .60   |       |     |
| 6AU6   | .20  | 6L6GT  | .39 | 12BH7   | .27   | 30P14     | .65   | E1948   | .50   | ECC110 | .63   | EL122 | .34   | PCF108 | .44    | PKY107   | .33    | UT18    | .75  | ACY50 | .18   | BY149 | .18   | OA230 | .60   |       |     |
| 6AV6   | .30  | 6L7GT  | .63 | 12E1    | .85   | 30P15     | .87   | E450    | .18   | ECC111 | .63   | EL123 | .34   | PCF109 | .44    | PKY108   | .33    | UT18    | .75  | ACY51 | .18   | BY150 | .18   | OA231 | .60   |       |     |
| 6AW8A  | .54  | 6L18   | .45 | 12J7GT  | .33   | 30A3      | .50   | E476    | .58   | ECC112 | .63   | EL124 | .34   | PCF110 | .44    | PKY109   | .33    | UT18    | .75  | ACY52 | .18   | BY151 | .18   | OA232 | .60   |       |     |
| 6B8G   | .13  | 6LD20  | .48 | 12K7GT  | .34   | 35W4      | .23   | E4C91   | .38   | ECC113 | .63   | EL125 | .34   | PCF111 | .44    | PKY110   | .33    | UT18    | .75  | ACY53 | .18   | BY152 | .18   | OA233 | .60   |       |     |
| 6BA6   | .20  | 6N7GT  | .40 | 12Q7GT  | .28   | 35Z4GT    | .24   | E4F42   | .48   | ECC114 | .63   | EL126 | .34   | PCF112 | .44    | PKY111   | .33    | UT18    | .75  | ACY54 | .18   | BY153 | .18   | OA234 | .60   |       |     |
| 6BC8   | .50  | 6Q7    | .43 | 12S4GT  | .30   | 35Z5GT    | .30   | E434    | .20   | ECC115 | .63   | EL127 | .34   | PCF113 | .44    | PKY112   | .33    | UT18    | .75  | ACY55 | .18   | BY154 | .18   | OA235 | .60   |       |     |
| 6BE6   | .21  | 6Q7G   | .27 | .40     | 50EH5 | .55       | E591  | .11     | EFC85 | .26    | KTW61 | .63   | EL128 | .34    | PCF114 | .44      | PKY113 | .33     | UT18 | .75   | ACY56 | .18   | BY155 | .18   | OA236 | .60   |     |
| 6BE6   | .43  | 6R7    | .55 | 128C7   | .35   | 50L6GT    | .45   | EBC41   | .48   | EFC86  | .30   | KTW62 | .63   | EL129  | .34    | PCF115   | .44    | PKY114  | .33  | UT18  | .75   | ACY57 | .18   | BY156 | .18   | OA237 | .60 |
| 6BJ6   | .39  | 6R7G   | .35 | 128GT   | .22   | 55A2      | .43   | EFC81   | .35   | EFC82  | .38   | KTW63 | .50   | EL130  | .34    | PCF116   | .44    | PKY115  | .33  | UT18  | .75   | ACY58 | .18   | BY157 | .18   | OA238 | .60 |
| 6BQ7A  | .38  | 6SA7GT | .35 | 12SH7   | .15   | 90C1      | .59   | EBC01   | .30   | EFC83  | .17   | MH16D | .75   | EL131  | .34    | PCF117   | .44    | PKY116  | .33  | UT18  | .75   | ACY59 | .18   | BY158 | .18   | OA239 | .60 |
| 6BR7   | .78  | 6SA7M  | .35 | 12SJ7   | .23   | 807       | .59   | EBCF80  | .30   | EFC84  | .30   | N78   | 2.05  | EL132  | .34    | PCF118   | .44    | PKY117  | .33  | UT18  | .75   | ACY60 | .18   | BY159 | .18   | OA240 | .60 |
| 6BR8   | .63  | 6SC7GT | .38 | 12SK7   | .24   | 5763      | .50   | EBCF83  | .38   | EFC85  | .38   | N808  | .95   | EL133  | .34    | PCF119   | .44    | PKY118  | .33  | UT18  | .75   | ACY61 | .18   | BY160 | .18   | OA241 | .60 |
| 6BW6   | .72  | 6SG7GT | .38 | 12SG7GT | .38   | AC2/PEN   | .98   | EBCF89  | .27   | EFC86  | .38   | PL83  | .33   | EL134  | .34    | PCF120   | .44    | PKY119  | .33  | UT18  | .75   | ACY62 | .18   | BY161 | .18   | OA242 | .60 |
| 6BW7   | .55  | 6SH7   | .63 | .40     | 50EH5 | .55       | E591  | .11     | EFC85 | .26    | KTW61 | .63   | EL135 | .34    | PCF121 | .44      | PKY120 | .33     | UT18 | .75   | ACY63 | .18   | BY162 | .18   | OA243 | .60   |     |
| 6BZ6   | .31  | 6S7    | .35 | 1487    | 1.15  | AC2/PEN   | .98   | EBC121  | .60   | EFC87  | .29   | PL84  | .33   | EL136  | .34    | PCF122   | .44    | PKY121  | .33  | UT18  | .75   | ACY64 | .18   | BY163 | .18   | OA244 | .60 |
| 6CB6A  | .25  | 6SK7GT | .22 | 12AQ5   | .24   | DD        | .38   | ECC88   | .60   | EFC88  | .38   | PL85  | .33   | EL137  | .34    | PCF123   | .44    | PKY122  | .33  | UT18  | .75   | ACY65 | .18   | BY164 | .18   | OA245 | .60 |
| 6C9    | .73  | 6SQ7GT | .38 | 19G6    | 1.45  | AC6PEN(7) | .98   | ECC92   | .35   | EFC89  | .38   | PL86  | .33   | EL138  | .34    | PCF124   | .44    | PKY123  | .33  | UT18  | .75   | ACY66 | .18   | BY165 | .18   | OA246 | .60 |
| 6CDS6  | 1.08 | 6V6G   | .17 | 20D4    | 1.05  | AC/PEN(7) | .98   | ECC93   | 1.50  | EFC90  | .38   | PL87  | .33   | EL139  | .34    | PCF125   | .44    | PKY124  | .33  | UT18  | .75   | ACY67 | .18   | BY166 | .18   | OA247 | .60 |
| 6CG8A  | .50  | 6V6GT  | .30 | 20P2    | .65   | .98       | ECC93 | 1.50    | EFC90 | .38    | PL88  | .33   | EL140 | .34    | PCF126 | .44      | PKY125 | .33     | UT18 | .75   | ACY68 | .18   | BY167 | .18   | OA248 | .60   |     |
| 6CH6   | .38  | 6X4    | .20 | 20L1    | .98   | AC/TH1    | .50   | ECC40   | .60   | EL37   | .37   | PL89  | .33   | EL141  | .34    | PCF127   | .44    | PKY126  | .33  | UT18  | .75   | ACY69 | .18   | BY168 | .18   | OA249 | .60 |

Only use these tags: `div`, `div`, `div`, `div`, `div</`

All valves are unused, boxed, and subject to the standard 90 day guarantee. Terms of business — Cash or cheque with order only. Post/packing 0.03 per item, subject to a minimum of 0.09. Orders over 5.00 post/packing free. Same day despatch by first class mail. Any parcel insured against damage in transit for only 0.03 extra per order. Complete catalogue with conditions of sale price 0.07 post paid. Business hours Mon.-Fri. 9-5.30 p.m. Sat. 9-1 p.m. We do not handle seconds nor rejects, which are often described as "New and Tested" but have a limited and unreliable life. No enquiries answered unless S.A.E. is enclosed for reply.

## RSGB BOOKS FOR YOU

### VHF-UHF MANUAL

By G. R. Jessop, C Eng, MIERE, G6JP

2nd edition. Considerably enlarged and revised. Transmitters, receivers and test equipment for use at vhf and uhf are all fully covered on a practical basis in this new edition. **£1.80 post paid**

### RADIO COMMUNICATION HANDBOOK

832 pages of everything in the science of radio communication. The Handbook's U.K. origin ensures easy availability of components. Complete coverage of the technical and constructional fields. A superb hard-bound volume. **£3.50 post paid**

### A GUIDE TO AMATEUR RADIO

By Pat Hawker, G3VA

Fourteenth edition. 100 pages. The latest edition of this indispensable aid to all who want to know more about amateur radio. Designed to assist the newcomer to this unique hobby. Revised and expanded. **47p post paid**

These are three of a complete range of technical publications, log books and maps, all obtainable from:

## RADIO SOCIETY OF GREAT BRITAIN

35 DOUGHTY STREET, LONDON, WC1N 2AE

## PADGETTS RADIO STORE OLD TOWN HALL, LIVERSEDE, YORKS

TEL. HECKMONDWIKE 4285

Latest Air Ministry Release. Radio Receiver Type R4187. 2-8 To 18 M.H.Z. in 17 Bands. Comes with 17 Miniature Valves, 26 Volt Motor Power Supply Motor and Manually Tuned. Very Clean Condition but not tested. **£5. Carriage and Insurance 75p.**

Control Unit Type 4190. Complete with Three Miniature Valves 1 1/2 500 U.A. Meter, Six Relays, Model Makers Motor with Gears, 24 Press Buttons, lots of Spares. Very Clean condition. **£1.50. Carriage and Insurance 75p.**

Autotabulator Amplifier Unit. Complete with Carpenter Relay and Base. Many Spares. **50p. P/P 33p.**

Brand New Manufacturers Surplus Mains Transformers 250-0 250 30M.A. 6-3 4 Amps. **£1.05. P/P 25p.**

Reclaimed T.V. Tubes. All with 12 Months Guarantee. **AW43/88 £2. AW43/80 £1.50. MW43/69 £1.**

Special Offer Brand New British Tubes. C17P.M. £1. Many older Types in Stock. Carriage and Insurance on any Tube **£1.10.**

Speakers Ex T.V. Tested and in perfect condition all **25p each Post Paid.** 5" Round. 6" Round. 7x4. 6x4. 8x2. In Dozen lots mixed if required **£2.75.**

Toggle Switches. Ex Units. D.P.D.T. 10p. D.P.S.T. 5p. S.P.S.T. Spring loaded 10p. D.P.S.T. Press Button Spring Loaded 10p. P/P on any Switch 4p Doz Lots Post Paid.


G.P.O. Relays Ex Units. 400 Ohms and 600 Ohms. 50p doz. P/P 25p. Sample Relay 6p P/P 5p.

Miniature Lamp Holder, Brass



# new

## Super IC-12

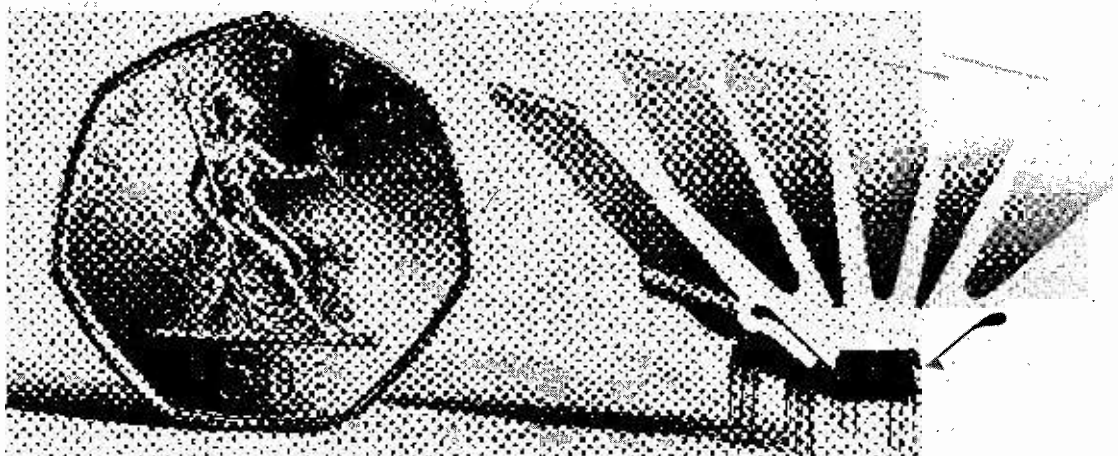

### High fidelity Monolithic Integrated Circuit Amplifier

Two years ago Sinclair Radionics announced the World's first monolithic integrated circuit Hi-Fi amplifier, the IC.10. Now we are delighted to be able to introduce its successor, the Super IC.12. This 22 transistor unit has all the virtues of the original IC.10 plus the following advantages:

1. Higher power.
2. Fewer external components.
3. Lower quiescent consumption.
4. Compatible with Project 60 modules.
5. Specially designed built-in heat sink. No other heat sink needed.
6. Full output into 3, 4, 5 or 8 ohms.
7. Works on any voltage from 6 to 28 volts without adjustment.
8. NEW 22 transistor circuit.

**Output power** 6 watts RMS continuous (12 watts peak).

**Frequency Response** 5 Hz to 100KHz  $\pm$  1 dB.

**Total Harmonic Distortion** Less than 1%. (Typical 0.1%) at all output powers and all frequencies in the audio band.

**Load Impedance** 3 to 15 ohms.

**Power Gain** 90dB (1,000,000,000 times) after feedback.

**Supply Voltage** 6 to 28 volts (Sinclair PZ-5 or PZ-6 power supplies ideal).

**Size** 22 x 45 x 28 mm including pins and heat sink.

**Input Impedance** 250 Kohms nominal.

**Quiescent current** 8mA at 28 volts.

With the addition of only a very few external resistors and capacitors the Super IC.12 makes a complete high fidelity audio amplifier suitable for use with pick-up, F.M. tuner etc. Alternatively, for more elaborate systems, modules in the Project-60 range such as the Stereo 60 and A.F.U. may be added. The comprehensive manual supplied with each unit gives full circuit and wiring diagrams for a large number of applications in addition to high fidelity. These include car radios, oscillators etc. The very low quiescent consumption makes the Super IC.12 ideal for battery operation.



Price, inc. **FREE**  
printed circuit board  
for mounting.

**£2.98** Post  
free




Sinclair Radionics Ltd, London Rd, St. Ives  
Huntingdonshire PE17 4HJ  
Telephone St Ives (048 06) 4311

## sinclair

**SINCLAIR GENERAL GUARANTEE**  
Should you not be completely satisfied with your purchase when you receive it from us, return the goods without delay and your money will be refunded in full, including cost of return postage, at once and without question. Full service facilities are available to all Sinclair customers.

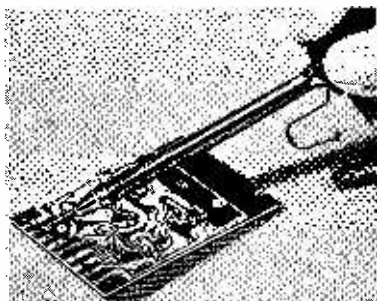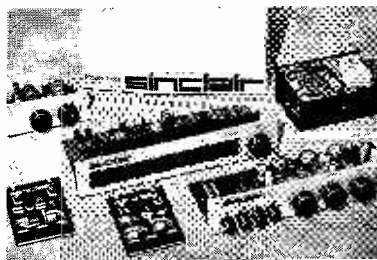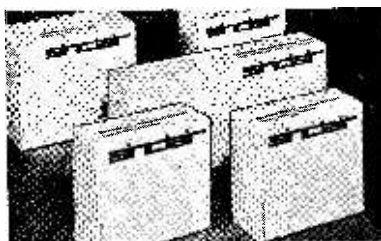
# Sinclair Project 60

The World's leading range of high fidelity modules



Sinclair Radionics Limited, London Road,  
St. Ives, Huntingdonshire PE17 4HJ.  
Tel: St. Ives (048 06) 4311

**sinclair**

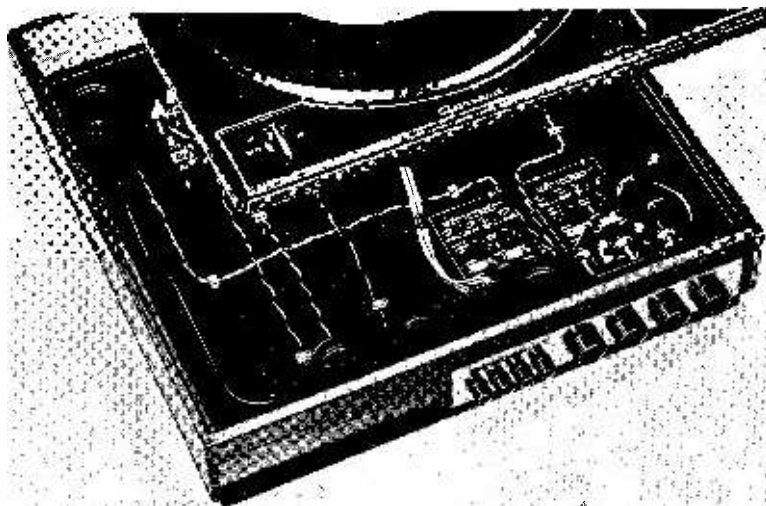

Project 60 offers more advantage to the constructor and user of high fidelity equipment than any other system in the world.

Performance characteristics are so good they hold their own with any other available system irrespective of price or size.

Project 60 modules are more versatile – using them you can have anything from a simple record player or car radio amplifier to a sophisticated and powerful stereo tuner-amplifier. Either power amplifier can be used in a wide variety of applications as well as high fidelity. The Stereo 60 pre-amplifier control unit may also be used with any other power amplifier system, as can the AFU filter unit. The stereo FM tuner operates on the unique phase lock loop principle to provide the best ever standards of sensitivity and audio quality. Project 60 modules are very easily connected together by following the 48 page manual supplied free with all Project 60 equipment. The modules are great space savers too and are sold individually boxed in distinctive white and black cartons. With all these wonderful advantages, there remains the most attractive of all – price. When you choose Project 60 you know you are going to get the best high fidelity in the world, yet thanks to Sinclair's vast manufacturing resources (the largest in Europe) prices are fantastically low and everything you buy is covered by the famous Sinclair guarantee of reliability and satisfaction.

## Typical Project 60 applications

| System                                                   | The Units to use                               | together with                                                      | Cost of Units |
|----------------------------------------------------------|------------------------------------------------|--------------------------------------------------------------------|---------------|
| Simple battery record player                             | <b>Z.30</b>                                    | Crystal P.U., 12V battery volume control                           | <b>£4.48</b>  |
| Mains powered record player                              | <b>Z.30, PZ.5</b>                              | Crystal or ceramic P.U. volume control etc.                        | <b>£9.45</b>  |
| 20 + 20 W. stereo amplifier for most needs               | <b>2 x Z.30s, Stereo 60, PZ.5</b>              | Crystal, ceramic or mag. P.U., F.M. Tuner, etc.                    | <b>£23.90</b> |
| 20 + 20 W. stereo amplifier with high performance spkrs. | <b>2 x Z.30s, Stereo 60, PZ.6</b>              | High quality ceramic or magnetic P.U., F.M. Tuner, Tape Deck, etc. | <b>£26.90</b> |
| 40 + 40 W. R.M.S. de-luxe stereo amplifier               | <b>2 x Z.50s, Stereo 60 PZ.8, mains trsfmr</b> | As above                                                           | <b>£34.88</b> |
| Indoor P.A.                                              | <b>Z.50, PZ.8, mains transformer</b>           | Mic., guitar, speakers, etc., controls                             | <b>£19.43</b> |

F.M. Stereo Tuner (**£25**) & A.F.U. Filter Unit (**£5.98**) may be added as required.

# from a simple amplifier to a complete stereo tuner amplifier with Project 60 modules

## Z.30 & Z.50 power amplifiers



The Z.30 and Z.50 are of advanced design using silicon epitaxial planar transistors to achieve unsurpassed standards of performance. Total harmonic distortion is an incredibly low 0.02% at full output and all lower outputs. Whether you use Z.30 or Z.50 amplifiers in your Project 60 system will depend on personal preference, but they are the same size and may be used with other units in the Project 60 range equally well.

**SPECIFICATIONS (Z.50 units are interchangeable with Z.30s in all applications).**

### Power Outputs

**Z.30** 15 watts R.M.S. into 8 ohms using 35 volts; 20 watts R.M.S. into 3 ohms using 30 volts.

**Z.50** 40 watts R.M.S. into 3 ohms using 40 volts; 30 watts R.M.S. into 8 ohms using 50 volts.

**Frequency response:** 30 to 300,000Hz  $\pm 1$  dB.

**Distortion:** 0.02% into 8 ohms.

**Signal to noise ratio:** better than 70dB unweighted.

**Input sensitivity:** 250mV into 100 Kohms.

For speakers from 3 to 15 ohms impedance.

**Size:** 14 x 80 x 57 mm.

### Z.30

Built, tested and guaranteed with circuits and instructions manual.

**£4.48**

### Z.50

Built, tested and guaranteed with circuits and instructions manual.

**£5.48**

## Project 60 Stereo F.M. Tuner



*First in the world to use the phase lock loop principle*

The phase lock loop principle was used for receiving signals from space craft because of its vastly improved signal to noise ratio. Now, Sinclair have applied the principle to an F.M. tuner with fantastically good results. Other original features include varicap diode tuning, printed circuit coils, an I.C. in the specially designed stereo decoder and squelch circuit for silent tuning between stations. Good reception is possible in difficult areas, and often a few inches of wire are enough for an aerial. In terms of a high fidelity this tuner has a lower level of distortion than any other tuner we know. Stereo broadcasts are received automatically as the tuning control is rotated, a panel indicator lighting up as the stereo signal is tuned in. This tuner can also be used to advantage with any other high fidelity system.

**SPECIFICATIONS—Number of transistors:** 16 plus 20 in I.C. **Tuning range:** 87.5 to 108 MHz. **Capture ratio:** 1.5dB. **Sensitivity:** 2 $\mu$ V for 30dB quieting; 7 $\mu$ V for full limiting. **Squelch level:** 20 $\mu$ V. **A.F.C. range:**  $\pm 200$  KHz. **Signal to noise ratio:** > 65dB. **Audio frequency response:** 10 Hz – 15 KHz ( $\pm 1$ dB). **Total harmonic distortion:** 0.15% for 30% modulation. **Stereo decoder operating level:** 2 $\mu$ V. **Cross talk:** 40dB. **Output voltage:** 2 x 150mV R.M.S. **Operating voltage:** 25-30 VDC. **Indicators:** Mains on; Stereo on; tuning.

**Size:** 93 x 40 x 207 mm.

Built and tested. Post free.

**£25**

## Stereo 60 Pre-amp/control unit



Designed for Project 60 range but suitable for use with any high quality power amplifier. Again silicon epitaxial planar transistors are used throughout, achieving a really high signal-to-noise ratio and excellent tracking between channels. Input selection is by means of push buttons and accurate equalisation is provided for all the usual inputs.

**SPECIFICATIONS—Input sensitivities:** Radio—up to 3mV. Mag. p.u. 3mV; correct to R.I.A.A. curve  $\pm 1$ dB; 20 to 25,000 Hz. Ceramic p.u.—up to 3mV; A.U.—up to 3mV. **Output:** 250mV. **Signal to noise ratio:** better than 70dB. **Channel matching:** within 1dB. **Tone controls:** TREBLE +15 to -15dB at 10 KHz; BASS +15 to -15dB at 100Hz. **Front panel:** brushed aluminium with black knobs and controls. **Size:** 66 x 40 x 207 mm.

Built, tested and guaranteed.

**£9.98**

## Power Supply Units

Designed special for use with the Project 60 system of your choice. Use PZ.5 for normal Z.30 assemblies and PZ.6 where a stabilised supply is essential.

**PZ.5** 30 volts un stabilised **£4.98**

**PZ.6** 35 volts stabilised **£7.98**

**PZ.8** 45 volts stabilised

(less mains transformer) **£7.98**

**PZ.8** mains transformer **£5.98**



## A.F.U. High & Low Pass Filter Unit



For use between Stereo 60 unit and two Z.30s or Z.50s, and is easily mounted. It is unique in that the cut-off frequencies are continuously variable, and as attenuation in the rejected band is rapid (12dB/octave), there is less loss of the wanted signal than has previously been possible. Amplitude and phase distortion are negligible. The A.F.U. is suitable for use with any other amplifier system. Two filter stages—rumble (high pass) and scratch (low pass). Supply voltage—15 to 35V. Current—3mA. H.F. cut-off (-3dB) variable from 28KHz to 5KHz. L.F. cut-off (-3dB) variable from 25Hz to 100Hz. Distortion at 1KHz (35V supply) (0.02% at rated output. **Size:** 66 x 40 x 90 mm.

Built tested and guaranteed.

**£5.98**

## The Sinclair Guarantee

If within 3 months of purchasing Project 60 modules directly from us, you are dissatisfied with them, we will refund your money at once. Each module is guaranteed to work perfectly and should any defect arise in normal use we will service it at once and without any cost to you whatsoever provided that it is returned to us within 2 years of the purchase date. There will be a small charge for service thereafter. No charge for postage by surface mail. Air-mail charged at cost.

To: SINCLAIR RADIONICS LTD LONDON ROAD ST. IVES HUNTINGDONSHIRE PE17 4HJ

Please send

Name

Address


I enclose cash/cheque/money order.

PW 10


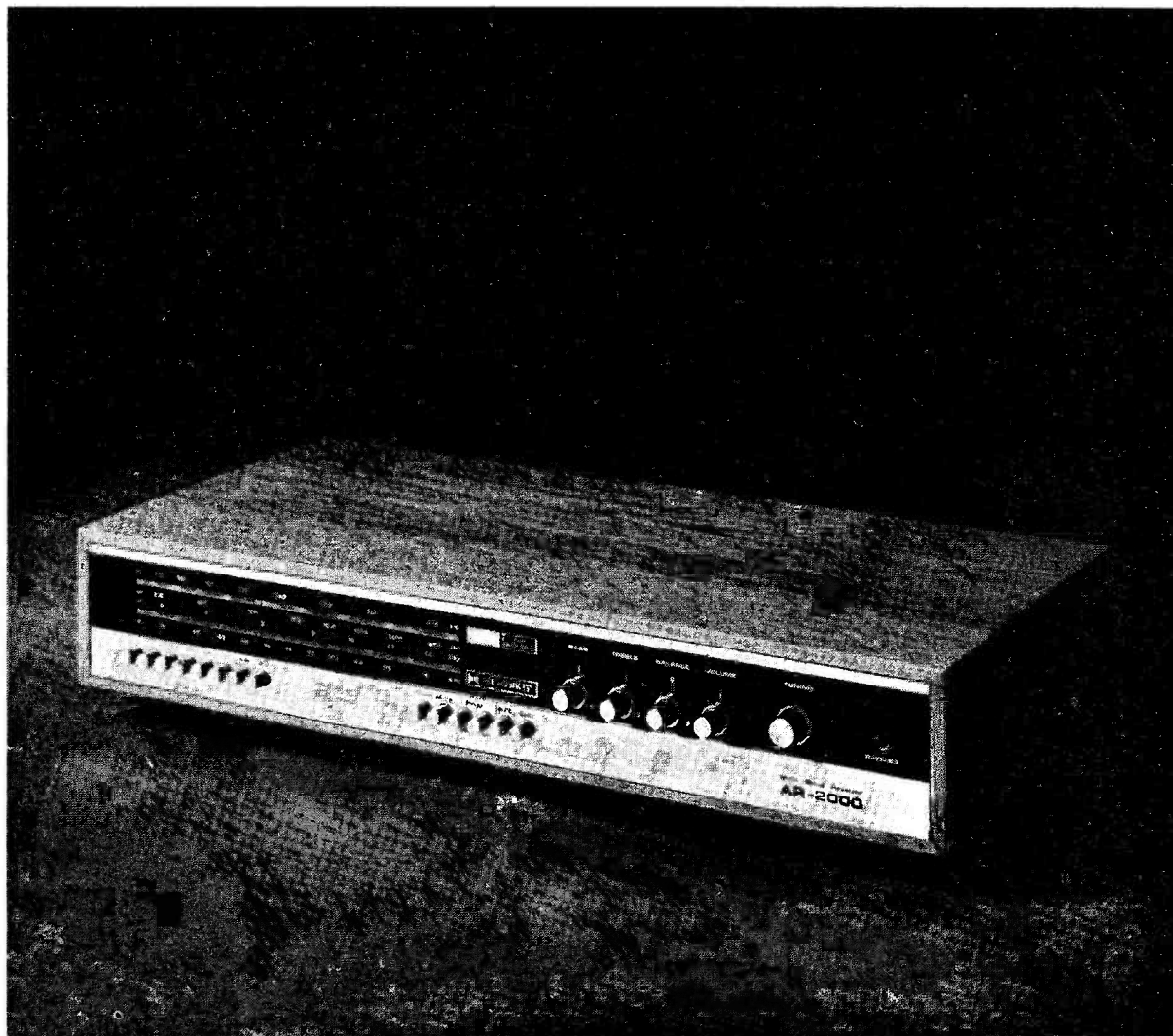
# Send for Heathkit – and send for the best

The best in hi-fi; the best in short-wave;  
the best in domestic, marine and auto equipment;  
the best in everything electronic.



The new AR 2000

Heathkit comes direct from the world's leading suppliers of top-quality electronic equipment. You assemble your components using the unique Heathkit 'step-and-check' method and there's a team of experts ready to help and advise you on any problem. But you won't need them. Hardly anyone does! Send for your FREE catalogue – NOW.

---  
Please send me details of your complete  
range of kits.  
Name \_\_\_\_\_  
Address \_\_\_\_\_

Heath (Gloucester) Limited,  
Gloucester, GL2 6EE.  
  
a Schlumberger Company  
PW 10



# COMET

## HI-FI DISCOUNT WAREHOUSES

## STEREO AMPLIFIERS

|                                                                | Rec. Retail Price | Comet Price |
|----------------------------------------------------------------|-------------------|-------------|
| ALBA UA 700                                                    | 34.50             | 26.00       |
| ANSTRAD 8000                                                   | 25.95             | 16.95       |
| ARMSTRONG 521                                                  | 56.00             | 42.50       |
| DULCI 207M                                                     | 32.00             | 21.95       |
| FERROGRAPH F307                                                | 62.00             | 44.00       |
| GOODMANS Maxamp                                                | 54.00             | 38.00       |
| LEAK Stereo 30 Plus                                            | 56.50             | 43.00       |
| LEAK Stereo 30 Plus, in teak case                              | 62.50             | 47.95       |
| LEAK Stereo 70 Chassis                                         | 69.00             | 52.00       |
| LEAK Stereo 70 cased                                           | 75.00             | 58.95       |
| METROSOUND ST20E                                               | 39.50             | 28.50       |
| PHILIPS RH 591                                                 | 79.00             | 61.50       |
| PHILIPS RH 590                                                 | 52.00             | 39.50       |
| PHILIPS RH 580                                                 | 29.00             | 23.00       |
| PIONEER SA500                                                  | 62.10             | 41.95       |
| PIONEER SA700                                                  | 98.00             | 68.95       |
| PIONEER SA900                                                  | 134.10            | 99.95       |
| PIONEER Reverberation                                          | 45.10             | 31.95       |
| RANK Rotel 610                                                 | 69.00             | 49.95       |
| ROGERS Ravensbourne                                            | 59.50             | 45.95       |
| ROGERS Ravensbourne (cased)                                    | 64.00             | 49.50       |
| ROGERS Ravensbrook Mk. II                                      | 47.50             | 36.50       |
| ROGERS Ravensbrook (cased)                                     |                   |             |
| Mk. II                                                         | 52.50             | 41.50       |
| SINCLAIR 2000                                                  | 35.00             | 23.95       |
| SINCLAIR Project 60/2 x Z30/PZ5                                | 23.90             | 16.50       |
| SINCLAIR PROJECT 60/2 x Z50/PZ3/trans                          | 34.96             | 23.25       |
| SINCLAIR AFU                                                   | 9.95              | 4.95        |
| SINCLAIR Neoteric                                              | 61.95             | 46.00       |
| SINCLAIR 3000                                                  | 45.00             | 32.50       |
| TELETON SAQ 206                                                | 29.00             | 18.50       |
| TELETON GA101                                                  | 37.50             | 28.50       |
| VOLTEX 100w. Stereo Discotheque, 8 electronically mixed inputs | 185.00            | 139.00      |

All the above take both ceramic and magnetic cartridges.

**TUNERS**

|                               |        |        |
|-------------------------------|--------|--------|
| *ARMSTRONG 523 AM/FM          | 53.76  | 42.00  |
| *ARMSTRONG 524 FM             | 41.99  | 33.00  |
| ARMSTRONG M8 Decoder          | 61.95  | 46.00  |
| DULCI FMT 7 FM                | 26.00  | 22.00  |
| DULCI FMT 7S Stereo           | 35.00  | 28.25  |
| GOODMANS Stereomax            | 82.52  | 49.95  |
| LEAK Stereofetic Chassis      | 66.50  | 52.00  |
| LEAK Stereofetic in teak case | 72.50  | 58.90  |
| PHILIPS RH 690                | 47.00  | 36.00  |
| PHILIPS RH 681                | 89.00  | 75.50  |
| PIONEER TX500 AM/FM           | 77.94  | 63.50  |
| PIONEER TX900 AM/FM           | 153.69 | 123.00 |
| RANK Rotel 320                | 54.57  | 42.95  |
| ROGERS Ravensbourne chassis   | 61.99  | 47.95  |
| ROGERS Ravensbrook            | 45.01  | 31.95  |
| ROGERS Ravensbrook (cased)    | 51.26  | 41.00  |
| TELETON GT 101                | 45.50  | 31.95  |

All above Tuners are complete with MPX Stereo Decoder except where starred.

## TUNER/AMPLIFIERS

|                                  |        |        |
|----------------------------------|--------|--------|
| AKAI AA 8500                     | 229.00 | 181.00 |
| AKAI 6600                        | 142.53 | 112.00 |
| AKAI 6300                        | 128.85 | 99.95  |
| ARENA R500                       | 82.00  | 67.00  |
| ARENA 2400                       | 90.30  | 72.00  |
| ARENA 2700                       | 105.00 | 85.00  |
| ARENA T9000                      | 303.45 | 258.00 |
| ARMSTRONG M8 Decoder             | 9.50   | 8.00   |
| ARMSTRONG 525                    | 91.89  | 74.50  |
| ARMSTRONG 526                    | 104.71 | 84.50  |
| GOODMANS Mod. 80, 35w. R.M.S.    | 95.00  | 72.00  |
| MIDLAND 19/542                   | 49.56  | 37.50  |
| PHILIPS RH 790                   | 139.00 | 112.00 |
| PIONEER SX770 AM/FM              | 180.43 | 126.00 |
| PIONEER SX900 AM/FM              | 194.74 | 150.00 |
| PIONEER 440                      | 111.10 | 89.00  |
| TANDBERG 1171 comp. with decoder | 110.00 | 94.00  |
| *TELETON F2000                   | 51.50  | 39.50  |
| TELETON 7AT20                    | 105.00 | 77.95  |
| TELETON 10AT1 150w. RMS          | 160.00 | 103.00 |
| TELETON TFS50                    | 82.50  | 59.00  |
| TELETON TFS 80LA MW/LW/VHF       | 87.50  | 63.50  |
| *TELETON R 3000 with Speakers    | 63.25  | 37.50  |
| TELETON CR55                     | 120.00 | 87.00  |
| WHARFEOALE 100-1                 | 149.00 | 119.00 |

Starred items above take ceramic cartridges only.

All others take both ceramic and magnetic cartridges.

All the above Tuners and Tuner/Amplifiers include MPX Stereo Decoder with the exception of Armstrong where decoder is extra as listed.

## CARTRIDGES

|                      |       |       |
|----------------------|-------|-------|
| GOLDING 800E         | 13.00 | 6.95  |
| GOLDING 800E         | 18.95 | 10.95 |
| GOLDING 800 Super E  | 26.01 | 19.50 |
| *GOLDING CS90 Stereo | 5.20  | 4.25  |
| *GOLDING CS91/E      | 7.81  | 6.25  |

|                           | Rec. Retail Price | Comet Price |
|---------------------------|-------------------|-------------|
| GOLDING G850              | 6.50              | 5.25        |
| EMPIRE 1000ZE/X           | 63.00             | 52.50       |
| EMPIRE 999VE/X            | 44.50             | 36.00       |
| EMPIRE 999TE/X            | 27.80             | 22.50       |
| EMPIRE 999SE/X            | 21.00             | 17.00       |
| EMPIRE 999E/X             | 16.50             | 13.00       |
| EMPIRE 999/X              | 11.50             | 9.25        |
| EMPIRE 909E/X             | 12.85             | 10.25       |
| EMPIRE 909/X              | 9.00              | 7.50        |
| EMPIRE 909E/X             | 9.75              | 8.00        |
| ORBIT Magnetic NM 22      | Special Price     | 2.00        |
| PICKERING V15 AC2         | 29.65             | 23.75       |
| ORTOFON SL15              | 7.00              | 5.25        |
| ORTOFON 2X15K Transformer | 7.41              | 5.50        |
| SHURE M31E                | 12.05             | 8.95        |
| SHURE M32E                | 11.10             | 8.25        |
| SHURE M32-3               | 10.20             | 8.00        |
| SHURE M44-5               | 11.10             | 7.95        |
| SHURE M44-7               | 10.20             | 8.00        |
| SHURE M44C                | 10.20             | 8.00        |
| SHURE M44E                | 12.05             | 8.25        |
| SHURE M55E                | 12.95             | 9.50        |
| GOLDING Lenco L75         | 12.33             | 10.50       |
| GOLDING Lenco L69         | 9.29              | 7.00        |
| SME 3009 with S2 Shell    | 34.47             | 27.00       |
| SME 3012 with S2 Shell    | 36.71             | 30.50       |

Starred cartridges above are ceramic. All others are magnetic.

## PICKUP ARMS

|                        |       |       |
|------------------------|-------|-------|
| GOLDING Lenco L75      | 12.33 | 10.50 |
| GOLDING Lenco L69      | 9.29  | 7.00  |
| SME 3009 with S2 Shell | 34.47 | 27.00 |
| SME 3012 with S2 Shell | 36.71 | 30.50 |

## TURNABLES

The following Turntables are complete with base, plinth, perspex cover and cartridge. Fully wired and ready for use. All at special prices.

|                                         |                      |
|-----------------------------------------|----------------------|
| GARRARD SP25 Mk 111 with Goldring G.800 | Special Price £21.98 |
| GARRARD SP25 Mk 111 with Shure M.44-7   | Special Price £22.95 |
| GARRARD SP25 Mk 111 with Shure M.155E   | Special Price £23.95 |
| GARRARD AP76 with Goldring G800         | Special Price £30.95 |
| GARRARD AP76 with Shure M55E            | Special Price £32.95 |
| GARRARD AP76 with Shure M75E            | Special Price £36.95 |
| GARRARD 2025 with Sonotone STAHK        | Special Price £15.50 |
| GOLDING 705/P with G850                 | Special Price £15.95 |
| GOODMANS 3025 with G800                 | Special Price £28.90 |

|                                                          |               |       |
|----------------------------------------------------------|---------------|-------|
| DUAL 1219 transcription                                  | 60.40         | 50.00 |
| DUAL 1209 transcription                                  | 42.62         | 35.00 |
| GARRARD SP25 Mk III                                      | 16.45         | 11.90 |
| GARRARD SL65 B                                           | 21.25         | 15.50 |
| GARRARD SL75 B                                           | 39.20         | 26.50 |
| GARRARD SL95 B                                           | 50.01         | 35.50 |
| GARRARD 401                                              | 39.67         | 32.50 |
| GARRARD SL72 B                                           | 33.11         | 25.50 |
| GARRARD 3500, with GKS Cart.                             | 17.23         | 12.90 |
| Base and Cover to fit GARRARD SP25, SL55, SL65B and 3500 | Special Price | 4.00  |
| GARRARD 405                                              | 13.84         | 10.97 |
| GARRARD AP76                                             | 28.88         | 21.50 |
| GOLDING GL69 Mk. II                                      | 26.63         | 21.25 |
| GOLDING GL89P Mk. II                                     | 35.14         | 28.50 |
| GOLDING GL75                                             | 36.41         | 31.50 |

|                                                             | Rec. Retail Price | Comet Price |
|-------------------------------------------------------------|-------------------|-------------|
| GOLDING GL75P                                               | 46.94             | 38.50       |
| GOLDING Covers for 69P and 75P                              | 4.21              | 3.50        |
| GOLDING C99-plinth and cover for 699                        | 11.45             | 9.90        |
| GOLDING G99                                                 | 26.00             | 22.00       |
| GOODMANS 3025                                               | 37.74             | 28.90       |
| MCDONALD MP 50                                              | 15.75             | 11.75       |
| MCDONALD 610                                                | 20.00             | 15.75       |
| Base and Cover for MCDONALD MP 60 and 810                   | Special Price     | 4.50        |
| PHILIPS 222                                                 | 20.00             | 17.00       |
| PHILIPS GA146                                               | 31.50             | 25.00       |
| PHILIPS 302 Electronic                                      | 69.00             | 54.00       |
| PHILIPS 306 transcription unit complete with base and cover | 39.00             | 32.95       |
| PIONEER PL12A with base & cover                             | 49.93             | 37.95       |
| THORENS TX25 cover                                          | 8.85              | 7.00        |
| THORENS TD125                                               | 70.04             | 61.95       |
| THORENS TD125AB                                             | 150.20            | 88.00       |
| THORENS TD150A Mk. II                                       | 46.16             | 35.95       |
| THORENS TD150AB Mk. II                                      | 49.96             | 42.95       |
| THORENS TX11 Cover                                          | 4.43              | 3.95        |

## SPEAKERS

|                         |        |        |
|-------------------------|--------|--------|
| B & W Model 70          | 159.50 | 121.95 |
| B & W DM3               | 63.00  | 49.95  |
| B & W DM1               | 32.00  | 25.50  |
| CELESTION Ditton 120    | 34.00  | 19.90  |
| CELESTION Ditton 15     | 32.00  | 25.50  |
| CELESTION Ditton 25     | 65.00  | 50.95  |
| GOODMANS Minister       | 25.00  | 20.50  |
| GOODMANS Magister       | 62.80  | 47.95  |
| GOODMANS Maxim          | 20.89  | 16.50  |
| GOODMANS Magnum K8      | 34.00  | 25.95  |
| J & S Model SXMT (pair) | 26.95  | 14.95  |
| KEF Cresta              | 22.17  | 18.00  |

## KELETRON Speakers

|                               |       |       |
|-------------------------------|-------|-------|
| KN500 4 speaker system (pair) | 23.00 | 15.50 |
| KN700 4 speaker system        | 27.50 | 18.25 |
| KN1000 4 speaker system       | 19.25 | 13.95 |
| KN1500 4 speaker system       | 24.75 | 18.95 |
| KN2000 4 speaker system       | 28.75 | 20.95 |
| LEAK 200                      | 24.95 | 18.90 |
| LEAK 300                      | 32.50 | 23.95 |
| LOWTHER Acousta (with PM6)    | 49.50 | 38.50 |
| LOWTHER Acousta (with PM7)    | 53.00 | 46.00 |
| LOWTHER Ideal Baffle          | 35.50 | 30.00 |
| METROSOUND HFS103 (pair)      | 25.00 | 17.95 |
| METROSOUND 202                | 21.50 | 15.95 |
| METROSOUND HFS20 (pair)       | 39.00 | 27.95 |
| METROSOUND HFS10 (pair)       | 27.44 | 22.95 |
| PHILIPS RH481                 | 11.00 | 8.95  |
| PHILIPS RH482                 | 18.00 | 14.95 |
| SINCLAIR Q16                  | 8.98  | 6.95  |
| STE-M 275 3 speaker system    | 23.10 | 15.95 |
| TANDBERG TAN 7                | 22.50 | 18.50 |
| TANDBERG TAN 11               | 19.30 | 16.50 |
| TANDBERG TAN 15               | 45.00 | 35.95 |

## WHARFEOALE Speakers

|                    |       |       |
|--------------------|-------|-------|
| Airedale           | 69.50 | 54.95 |
| Denton             | 19.95 | 16.75 |
| Super Linton       | 24.95 | 20.50 |
| Melton             | 32.50 | 24.95 |
| Dovedale 3         | 42.50 | 31.95 |
| Rosedale           | 65.00 | 50.95 |
| Trifton (pair)     | 59.90 | 45.95 |
| Unit 3 Speaker Kit | 13.00 | 10.00 |
| Unit 4 Speaker Kit | 18.00 | 13.95 |
| Unit 5 Speaker Kit | 26.00 | 19.95 |

## CHASSIS SPEAKERS

|                        |       |       |
|------------------------|-------|-------|
| GOODMANS Axielle 8     | 8.10  | 6.50  |
| GOODMANS Twinaxlette 8 | 9.17  | 7.50  |
| GOODMANS Axiom 10      | 9.16  | 7.75  |
| GOODMANS Axiom 80      | 28.31 | 23.75 |
| GOODMANS Axiom 201     | 14.45 | 10.95 |
| GOODMANS Axiom 401     | 17.86 | 14.95 |
| GOODMANS Audiom 8P     | 5.55  | 4.25  |
| GOODMANS Audiom 10P    | 6.05  | 3.95  |

## COMET for

after-sales service

THROUGHOUT THE U.K.

Pictured, Service Dept.

at Clough Rd., Hull


also at Leeds,

Stockton, Goole,

Wakefield, Doncaster,

Bridlington and

Birmingham

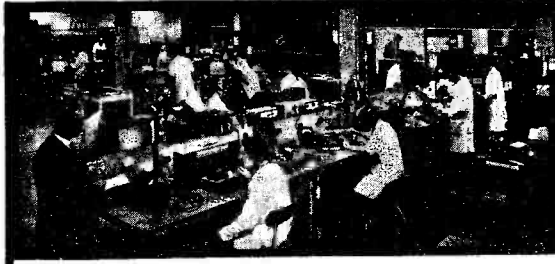

(OVER 1,520 sq. yds.)

# OVER 1000 ITEMS ALWAYS IN STOCK

## ALL FULLY GUARANTEED - WITH AFTER-SALES SERVICE

All items offered are brand new, latest models in manufacturers' sealed cartons

### COMPLETE HI-FI SYSTEMS

Completely wired, mounted and ready for use.

|                                      | Rec. Price | Retail Price | Comet Price |
|--------------------------------------|------------|--------------|-------------|
| GOODMANS Audiom 51                   | 13-05      | 18-95        | 9-75        |
| GOODMANS Audiom 61                   | 12-37      | 14-00        | 10-00       |
| GOODMANS 15P                         | 20-00      | 26-97        | 16-97       |
| GOODMANS Audiom 18P                  | 34-00      | 42-95        | 26-97       |
| GOODMANS Twin Axom 10                | 10-23      | 12-37        | 8-25        |
| GOODMANS ARU172                      | 4-50       | 5-50         | 3-50        |
| GOODMANS Trebas 100                  | 8-60       | 10-00        | 6-00        |
| GOODMANS Trebas 5K/20XL              | 9-70       | 11-50        | 7-50        |
| GOODMANS Midax                       | 12-95      | 15-00        | 9-00        |
| GOODMANS Attenuator                  | 3-55       | 4-50         | 2-50        |
| GOODMANS Crossover Networks          |            |              |             |
| XO/950/8000                          | 9-75       | 11-50        | 7-25        |
| GOODMANS Crossover Networks          |            |              |             |
| XO/950                               | 7-40       | 8-50         | 5-75        |
| GOODMANS Crossover Networks          |            |              |             |
| XO/5000                              | 2-85       | 3-50         | 2-00        |
| WHARFEDALE 8in. Bronze/RS/DD         | 5-00       | 6-00         | 4-00        |
| WHARFEDALE Super 8/RS/DD             | 8-50       | 10-00        | 7-00        |
| WHARFEDALE Super 10/RS/DD            | 14-00      | 16-00        | 11-50       |
| WHARFEDALE WMT1 Matching Transformer | 0-84       | 1-00         | 0-75        |

#### HI-FI STEREO SYSTEMS COMPLETE

|                                          |        |        |
|------------------------------------------|--------|--------|
| ALBA MR15                                | 145-00 | 169-95 |
| ALBA UA552                               | 45-88  | 55-50  |
| ALBA UA682                               | 60-32  | 66-95  |
| DECCA Sound 6013                         | 69-89  | 77-95  |
| DECCA Sound 6014                         | 70-86  | 78-95  |
| DECCA Sound 1204                         | 95-30  | 105-00 |
| DECCA Compact 3                          | 100-14 | 109-95 |
| DECCALIAN 5 complete with stand          | 65-50  | 71-95  |
| EKCO SRG 609                             | 85-44  | 95-50  |
| EKCO ZUS                                 | 159-29 | 179-00 |
| FERGUSON 3422                            | 84-80  | 91-95  |
| FERGUSON 3423                            | 114-15 | 124-95 |
| FERGUSON 3424                            | 119-00 | 129-95 |
| FERGUSON 3425                            | 120-10 | 129-95 |
| FIDELITY UA2 Music Master                | 44-41  | 51-95  |
| FIDELITY UA1 Music Master                | 103-30 | 113-95 |
| HMV 2416                                 | 129-70 | 139-95 |
| HMV 2045/5                               | 109-00 | 119-95 |
| HMV 2452                                 | 65-65  | 71-95  |
| HMV 2450 with stereo radio               | 134-20 | 144-95 |
| KB KA1250 complete with two 653 speakers | 71-55  | 78-50  |
| KB KA1250 complete with two 651 speakers | 80-25  | 86-95  |
| KB 2010 with radio                       | 73-40  | 80-95  |
| LEAK 30/Goldring/Wharfedale              | 182-65 | 192-95 |
| LEAK 70/Thorens/Wharfedale               | 226-87 | 236-95 |
| MARCONI Unit 4                           | 74-77  | 80-95  |
| MARCONI Unit 3                           | 84-79  | 91-95  |
| METROSOUND Stereo 1010                   | 92-30  | 99-95  |
| PHILIPS 580/481/105                      | 71-00  | 78-95  |
| PHILIPS GF 823                           | 47-79  | 51-95  |
| PHILIPS GF 824                           | 67-09  | 71-95  |
| PHILIPS GF 833                           | 65-16  | 71-95  |
| PHILIPS GF 834                           | 84-85  | 89-95  |
| PHILIPS GF 417                           | 96-08  | 101-95 |
| PHILIPS 892                              | 96-50  | 101-95 |
| TELETON 2580F with radio                 | 72-40  | 78-95  |
| TELETON 8TK Stereo System                | 54-75  | 58-50  |
| TOSHIBA SP8507                           | 248-00 | 268-95 |
| ULTRA 6405                               | 77-00  | 84-95  |

#### TAPE RECORDERS AND TAPE DECKS

|                                      |        |        |
|--------------------------------------|--------|--------|
| AKAI 1720L                           | 93-67  | 101-95 |
| AKAI 4000 D 4-track stereo deck      | 86-68  | 91-95  |
| AKAI CR 80D 8-track stereo tape deck | 91-56  | 98-95  |
| AKAI CR80 8-track stereo recorder    | 110-83 | 118-95 |
| AKAI X200D                           | 183-07 | 193-95 |
| AKAI 1800SD                          | 182-16 | 192-95 |
| AKAI 2000SD                          | 300-00 | 318-95 |
| BUSH Diacast Stereo 2000             | 21-18  | 22-95  |
| BUSH TP60 Cassette tape recorder     | 28-38  | 30-95  |

|                                                                           |        |        |
|---------------------------------------------------------------------------|--------|--------|
| BUSH TP70 Cassette battery/mains tape recorder                            | 28-81  | 30-50  |
| FERGUSON 3245 Twin track                                                  | 38-70  | 41-95  |
| FERGUSON 3248 4-track                                                     | 42-55  | 45-95  |
| FERGUSON 3247 4-track                                                     | 47-93  | 50-95  |
| FERGUSON 3248 4-track                                                     | 52-76  | 55-95  |
| FERGUSON 3252 2-track                                                     | 100-70 | 105-95 |
| FERROGRAPH 704/W 4-track tape deck                                        | 220-22 | 230-95 |
| FERROGRAPH 722                                                            | 220-22 | 230-95 |
| FERROGRAPH 724                                                            | 257-52 | 268-95 |
| GRUNDIG C200 De Luxe Cassette                                             | 38-46  | 41-95  |
| GRUNDIG TK 121 twin track                                                 | 55-30  | 58-95  |
| GRUNDIG TK 140 4-track                                                    | 57-63  | 60-95  |
| GRUNDIG TK 141 4-track                                                    | 61-82  | 64-95  |
| GRUNDIG TK 146 4-track Auto                                               | 67-30  | 70-95  |
| GRUNDIG 222 stereo cassette                                               | 57-70  | 60-95  |
| GRUNDIG TK 147 4-track Auto                                               | 93-96  | 97-95  |
| MIDLAND TC 144 cassette                                                   | 18-00  | 19-95  |
| PHILIPS 2202 cassette                                                     | 26-89  | 28-95  |
| PHILIPS 2204 cassette battery/mains                                       | 32-30  | 34-95  |
| PHILIPS 2205 cassette tape recorder                                       | 41-59  | 43-95  |
| PHILIPS 3302 cassette tape recorder                                       | 23-04  | 24-95  |
| PHILIPS 4303 new release                                                  | 40-55  | 43-95  |
| PHILIPS 4307 4-track                                                      | 47-78  | 50-95  |
| PHILIPS 4308 De Luxe 4-track                                              | 58-40  | 61-95  |
| PHILIPS 4404 2-track stereo recorder                                      | 91-71  | 95-95  |
| PHILIPS 4407 4-track stereo recorder                                      | 106-19 | 110-95 |
| PHILIPS 4500 4-track stereo tape deck                                     | 121-64 | 126-95 |
| PHILIPS 4408 4-track stereo                                               | 134-18 | 139-95 |
| PHILIPS Cassette Stereo N2503                                             | 52-05  | 55-95  |
| PYE Cassette Recorder/Radio 9000                                          | 43-86  | 46-95  |
| PHILIPS 2400 stereo cassette less L/S                                     | 65-55  | 68-95  |
| TANDBERG 1841 4-track stereo tape deck                                    | 69-75  | 72-95  |
| TANDBERG 3010 4-track stereo                                              | 109-90 | 114-95 |
| TANDBERG 3014X 4-track stereo                                             | 109-90 | 114-95 |
| TANDBERG 4021X twin track stereo                                          | 180-00 | 185-95 |
| TANDBERG 4041X 4-track stereo                                             | 180-00 | 185-95 |
| TANDBERG 6041X 4-track stereo                                             | 188-00 | 193-95 |
| TANDBERG 6041X twin track stereo                                          | 22-00  | 23-95  |
| TELETON TC110 cassette battery/mains                                      | 26-79  | 28-95  |
| TELETON TRC130 cassette with VHF/AM Radio Batt./Mains twin motors         | 40-31  | 42-95  |
| TELETON 811 battery/mains cassette                                        | 29-50  | 31-95  |
| TELETON FXB 510 D 4-track stereo                                          | 65-16  | 68-95  |
| TOSHIBA GT 601V twin track                                                | 43-95  | 46-95  |
| TOSHIBA 850 SA 4-track stereo tape deck                                   | 91-50  | 95-95  |
| TOSHIBA GT 840S 4-track stereo tape deck                                  | 105-20 | 109-95 |
| WHARFEDALE Dolby DC9 cassette stereo tape deck                            | 110-40 | 114-95 |
| BASES AND COVERS                                                          |        |        |
| GARRARD WBI Base                                                          | 3-86   | 4-25   |
| GARRARD WB4 Base                                                          | 5-69   | 6-08   |
| GARRARD SPC 1 Cover                                                       | 3-74   | 4-13   |
| GARRARD SPC 4 Cover                                                       | 4-44   | 4-83   |
| Special offer of Base and Cover to fit GARRARD SP25, SL55, SL65B and 3500 |        |        |
| GOLDRING Plinth 69                                                        | 8-52   | 9-00   |
| GOLDRING Covers for 69P and 75P                                           | 4-21   | 4-50   |
| THORENS TX25 (for TD125AB)                                                | 8-22   | 8-50   |
| THORENS TX11 Cover                                                        | 4-11   | 4-50   |
| Base and Cover for TD 125                                                 | 15-18  | 15-95  |
| SME Plinth System 2000                                                    | 39-20  | 41-95  |
| MOTORBOARDS only                                                          | 4-95   | 5-00   |

|                                                                                                                                                                                                                                                           |        |        |
|-----------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------|--------|--------|
| GOODMANS AUDIO SUITE, Goodmans Maxamp stereo amplifier, Goodmans stereomax AM/FM Tuner with decoder. Pair of Goodmans Magnum K2 speakers, Garrard AP78 turntable in base, complete with cover and Goldring G800 Cartridge. Beautifully finished in walnut | 257-13 | 268-95 |
| GOLDRING 705P turntable complete with G800 Cartridge, Midland Tuner/Amp., pair of Melrosound 103 Speakers                                                                                                                                                 | 99-56  | 105-95 |
| GOODMANS Module 80 Tuner/Amplifier, Garrard AP78 Turntable with Goldring G800 Cartridge and 2 Goodmans Minister Speakers                                                                                                                                  | 199-00 | 209-95 |
| METROSOUND 448 8-track stereo play-back unit complete with 2 HFS 10 Speakers                                                                                                                                                                              | 83-56  | 88-95  |
| GOLDRING 705P turntable complete with G800 Cartridge, Teleton 206 Amplifier, pair of Keletron KN500 Speakers                                                                                                                                              | 77-00  | 81-95  |
| TELETON STP 801 Stereo 8 track tape Audio system complete with speakers                                                                                                                                                                                   | 54-75  | 58-95  |
| GARRARD SP 25, Mk. III mounted in base, plinth and cover with GOLDRING G800 Cartridge. Teleton 206 Stereo Amplifier 12 watts RMS, and 2 KELETRON KN500 Speakers, each speaker is a 4 speaker system                                                       | 88-33  | 93-95  |
| PIONEER PL 12 turntable, Goodmans Maxamp, Shure M55E Cartridge, 2 Keletron KN 700 speakers (each speaker cabinet contains 4 speakers)                                                                                                                     | 144-38 | 150-95 |
| GARRARD AP78 turntable complete with Goldring G800 Cartridge, base and cover, Rogers Ravensbrook Amplifier in teak case and 2 Goodmans Minister Speakers                                                                                                  | 142-51 | 148-95 |
| LEAK 30/THORENS/WHARFEDALE                                                                                                                                                                                                                                | 182-65 | 188-95 |
| GOLDRING GL 75P mounted in teak base with hinged perspex cover complete with GOLDRING G800E Cartridge, Leak Stereo 30 Plus Amplifier in Teak case, 2 GOODMANS Mezzo 3 Speakers                                                                            | 200-50 | 205-95 |
| THORENS TD 150AB Mk. II with TX11 dust cover, SHURE M55E Cartridge, LEAK Stereo 70 Amplifier in Teak case, 2 Wharfedale Dovedale 3 Speakers                                                                                                               | 226-87 | 231-95 |
| THORENS TD 125AB Electronic Turntable complete with cover, SHURE V15-1 Cartridge, GOODMANS Maxamp, GOODMANS Stereomax AM/FM Tuner, 2 GOODMANS Magister Speakers                                                                                           | 422-48 | 428-95 |
| TELETON STP 801, Stereo 8 track Tape Audio Systems comp. with speakers                                                                                                                                                                                    | 54-75  | 58-95  |



All in-stock items delivered by  
**SECURICOR**  
WITHIN 72 HOURS  
(Add £1.75 only for Securicor delivery)  
ALL GOODS FULLY INSURED AGAINST  
LOSS OR DAMAGE WHILST IN TRANSIT

Open daily to  
the public from  
9-0 A.M. until—

5-30 P.M. MON.  
1-0 P.M. TUES.  
8-0 P.M. WED.  
8-0 P.M. THUR.  
8-0 P.M. FRI.  
5-30 P.M. SAT.

Customers are  
welcome to call—  
Ample car parking  
facilities

Complete Price List FREE on request!

## COMET HIGH FIDELITY DISCOUNT WAREHOUSES

(Dept. P.W.) Reservoir Rd., Clough Rd., Hull HU6 7QD Tel. 407906

(Dept. P.W.) 68A Armley Rd. (Artist St.), Leeds LS12 2EE and 407877

(Dept. P.W.) Teesway, Portrack Lane, North Teesside Tel. 32055

(Dept. P.W.) Industrial Estate, Teesside, TS18 2RH (5 lines)

(Dept. P.W.) Heeley Road, Selly Oak, Birmingham Tel. 66132/

Tel. 021-472 6181 65215

Comet guarantees that all prices quoted are genuine. All items offered available at these prices at the time this issue closed for press.  
Add 75p for postage, packing and insurance on all orders (Cartridges 20p) or, if Securicor delivery required, add £1.75 only.  
Make cheques, Money Orders payable to "COMET".

Free  
Technical  
Advisory  
Service. If  
in doubt,  
ask us!

# Practical Wireless Classified Advertisements

The pre-paid rate for classified advertisements is 8½p per word (minimum 12 words), box number 7½p extra. Semi-displayed setting £6 per single column inch. All cheques, postal orders, etc., to be made payable to PRACTICAL WIRELESS and crossed "Lloyds Bank Ltd." Treasury notes should always be sent *registered post*. Advertisements, together with remittance, should be sent to the Classified Advertisement Manager, PRACTICAL WIRELESS, IPC Magazines Ltd., Fleetway House, Farringdon Street, London, EC4A 4AD for insertion in the next available issue.

## Educational



## TELEVISION TRAINING

(MONOCHROME AND COLOUR)

This private College provides theoretical and practical training in Radio and TV Servicing. Courses of 16 months' duration, with daily attendance, are available for beginners and shorter courses for men with previous training in Electronics and Radio. Training courses in Marine Radiocommunication and Radar are also available. Write for prospectus to: **London Electronics College, Dept. A/10, 20 Penywern Road, Earls Court, London SW5 9SU. Tel. 01-373 8721.**

**RTEB CERTS.,** City & Guilds, Colour TV, Radio, Computers, Radio Amateurs Cert., Practical Electronics (with kit). Thousands of successes. Send for full details of Home Study Courses and illustrated book—FREE: BIET, (Dept. H.7), Aldermaston Court, Reading, RG7 4PF.

### Situations Vacant

**EAGLE INTERNATIONAL** require Audio Engineers; excellent prospects. Must be fully conversant with Stereo Amplifiers, Tuners, Multiplex, etc. Contact Mr. Morrow 01-636 0961.

**GO TO SEA** as a Radio Officer. Write: Principal, National College, Broadwater, Fleetwood FY7 8JZ.

### TRAIN FOR SUCCESS WITH ICS

Study at home for a progressive post in Radio, TV and Electronics. Expert tuition for City & Guilds (Telecoms Techn's Cert. and Radio Amateurs') R.T.E.B., etc. Many non-exam courses incl. Colour TV Servicing, Numerical control & Computers. Also self-build kit courses—valve and transistor.

Write for **FREE** prospectus and find out how ICS can help you in your career.

**ICS, DEPT. 541 INTERTEXT HOUSE, STEWARTS ROAD, LONDON, SW8 4UJ**

**CIE, AMSE, City & Guilds, etc.,** on 'Satisfaction or Refund' terms. Thousands of exam. successes. Postal Courses for all branches of Engineering. Illustrated prospectus **FREE**. Please state subject of interest: BIET, (Dept. H.8), Aldermaston Court, Reading, RG7 4PF.

### Receivers and Components

#### MICROCIRCUITS:

|       |       |        |       |           |     |
|-------|-------|--------|-------|-----------|-----|
| 709   | 36p   | SL402A | £1.75 | 7430      | 19p |
| 741   | 73p   | MEL 11 | 35p   | 7473      | 42p |
| PA230 | 87p   | D40C1  | 55p   | 7474      | 44p |
| PA234 | 86p   | 7400   | 19p   | 7486      | 33p |
| PA237 | £1.55 | 7410   | 19p   | DIL conn. | 25p |

#### TRANSISTORS:

|        |     |        |     |        |     |
|--------|-----|--------|-----|--------|-----|
| 2N3055 | 54p | ME0402 | 21p | ME4102 | 12p |
| 2N5172 | 7p  | ME0412 | 20p | ME6001 | 13p |
| BOY70  | 16p | ME0413 | 15p | ME6101 | 15p |
| BD124  | 73p | ME1002 | 12p | MEF104 | 45p |
| BFX86  | 15p | ME4101 | 11p | MP8111 | 35p |

#### 1 AMP RECTIFIERS

|         |    |      |     |      |     |       |     |
|---------|----|------|-----|------|-----|-------|-----|
| 57V     | 3p | 400V | 6p  | 600V | 9p  | 1000V | 14p |
| Bridges | —  | 50V  | 25p | 100V | 26p | 200V  | 27p |

Printed Circuit Resist Pen .. 80p

#### JEFF ELECTRONICS (P.W.9)

York House, 12 York Drive, Grappenhall, Warrington, Lancs. Mail Order Only. C.W.O.

P.&P. 5p per order. Overseas 40p.

Money back if not satisfied.

List free on application.

### NEW MODEL V.H.F. KIT MK2

Our latest Kit, improved design and performance plus extra Amplifier Stage, receives Aircraft, Amateurs, Mobile, Radio 2, 3, 4, etc.

This novel little set will give you endless hours of pleasure and can be built in one evening. Powered by 9 Volt Battery, complete with easy to follow instructions and built in Jack Socket for use with Earphones or Amplifier.

Only £3.40. P. & P. Free U.K. only

Illustrated Catalogue of Selected Kits and Components 12½p. P. & P. Free.

Cheques, Postal orders to:

Dept. P.W.

Galleon Trading Co., 25 Avelon Road, Romford, Essex

**EX COMPUTER PRINTED CIRCUIT PANELS** 2in x 4in packed with semi-conductors and top quality resistors, capacitors, diodes, etc. Our price, 10 boards **50np** + 7np P. & P. With a guaranteed minimum of 35 transistors. Data on transistors included.

**SPECIAL BARGAIN PACK.** 25 boards for £1. P. & P. 18np. With a guaranteed minimum of 85 transistors. Data on transistors included.

**PANELS** with 2 power transistors similar to OC28 on each board + components. 2 boards (4 x OC28) **50np** + 6np P. & P.

9 OAS, 3 OA10, 3 Pot Cores, 26 Resistors, 14 Capacitors, 3 GET 872, 3 GET 872B, 1 GET 875. All long leaded on panels 13in x 4in. 4 for £1 + 25np P. & P.

#### LARGE CAPACITY ELECTROLYTICS

10000MFD 30V }  
16000MFD 12V } **40np** + 6np P. & P.  
or **£3.50** per doz. Carr. 50np

**250 MIXED RESISTORS** **62np**  
± ½ watt.

**150 MIXED HI STABS** **62np**  
± ½ & 1 watt 5% and better.

#### QUARTZ HALOGEN BULBS

With long leads, 12V 55W for car spot lights, projectors etc. 50p each p & p 5p.

#### DIODES SILICON

1 Amp 1000 PIV. 4 for **50np**. + 5np P. & P.

#### BARGAIN RELAY OFFER

Single pole change over silver contacts. 25V to 50V. 2.5kΩ coil. 8 for **50np**. + 5np P. & P.

#### KEYTRONICS mail order only

**44 EARLS COURT ROAD, LONDON W.8 01-478 8499**

## RADIO OPERATORS

**DO YOU HOLD PMG II OR PMG I OR NEW GENERAL CERTIFICATE OR HAD TWO YEARS' RADIO OPERATING EXPERIENCE?**

Looking for a secure job with good pay and conditions?

Then apply for a post with the Composite Signals Organisation. These are Civil Service posts, with opportunities for service abroad, and of becoming established, i.e., non-contributory pension scheme. Specialist Training Courses (free accommodation) starting January, April and September, 1972.

If you are British born and resident in the United Kingdom, under 35 years of age (40 for exceptionally well qualified candidates), write **NOW** for full details and an application form from:—

#### GOVERNMENT COMMUNICATIONS HEADQUARTERS,

Recruitment Officer,  
Oakley, Priors Road, Cheltenham, Glos.  
GL52 5AJ.  
(Telephone: Cheltenham 21491, Ext. 2270.)

# Kits for P.W. CONSTRUCTIONAL ARTICLES

**Amateur Bands Communications Receiver £23.85**, p. & p. 75p (or in 3 parts). RF Detector £9.64 p. & p. 25p. Signal Injector Tracer £3.95 p. & p. 20. **Workshop Oscilloscope £28.35** p. & p. 60p. Crystal Companion £1.95 p. & p. 20p. Hi-Z Voltmeter £4.52 p. & p. 20p. 10W Audio Amplifier £8.75 p. & p. 35p. Hi-Fi Signal Generator £11.30 p. & p. 35p. Simple Signal Generator £6.95 p. & p. 30p. Electronic Ignition System £6.30 p. & p. 30p. Solid State Enlarger Timer £6.30 p. & p. 35p. For prices of recent kits please send S.A.E.

**F. & B. ELECTRONICS** 5, Staples Inn, Holborn Bars, London WC1V 7QH

C.W.O. mail order only—please enquire for overseas p. & p.

COMPLETE RANGE of receivers by Trio, Lafayette, Hallicrafters, etc. Chassis, panels, cabinets. S.A.E. for lists. Stephens-James Ltd., 70 Priory Road, Liverpool 4. Tel. 051-263 7829.

| PROJECT 60 OFFERS                                                      | Post 37p |
|------------------------------------------------------------------------|----------|
| Stereo 60/2 Z30/PZ5 .. .. .                                            | £16.40   |
| Stereo 60/2 Z30/PZ6 .. .. .                                            | £19.00   |
| Stereo 60/2 Z30/PZ8 .. .. .                                            | £21.25   |
| Transformer for PZ8 .. .. .                                            | £2.20    |
| Project 60 FM tuner .. .. .                                            | £20.50   |
| Active Filter Unit .. .. .                                             | £4.75    |
| Q16 Loudspeaker .. .. .                                                | £7.70    |
| Kit of extra capacitors, plugs, cables, fuse to complete Project 60 .. | £2.40    |
| Antex 15W soldering iron CN240/2                                       | £1.70    |
| All items available separately.                                        |          |

**SINCLAIR SUPER IC-12**  
Ideal for use with PZ5 power unit.  
Supplied with instructions and free PC board .. .. . £2.45

**SINCLAIR BARGAINS**  
Power units: PZ5 £3.80, PZ6 £4.40, PZ8 £5.40  
Transformer for PZ8 £2.20.  
Amplifiers: Z30 £3.60, Z50 £4.35, Stereo 60 £8.35.  
Receivers: Micromatic kits £2.25, Assembled £2.75. Batteries 27p extra.

**SINCLAIR SYSTEM 3000**  
£32.90, Post 37p

**S-DECS**  
S-DeCs £0.95, T-DeCs £2.25,  $\mu$ -DeC A £3.10  
Carriers with sockets to mount 14 and 16 pin in line ICs on T-DeCs and  $\mu$ -DeC A £1.25.

**MULLARD UNILEX**  
EP9000 Amp £2.40, EP9001 Pre-amp £2.60, EP9002 Power unit £3.90, Control unit £2.80, Unilex booklet £0.22.

**THE 0.7P TRANSISTOR**  
PNP silicon transistors from 2S300 series with data. Typical  $V_{cb}=25V$ ,  $h_{fe}=35$ ,  $f_t=1Mc$ ,  $P_{max}=300mW$ . Untested and unmarked, but at least 80% are perfect to maker's spec. 50 for 40p, 100 for 70p.

**SWANLEY ELECTRONICS**  
32 GOLDSER RD., SWANLEY, KENT  
Mail order only.  
Minimum postage 10p per order.

**CIRCUITS CIRCUITS CIRCUITS**  
Ten exciting circuits per month with instructions to build. Every month a completely new set. This month's circuits cover

**MISCELLANEOUS PROJECTS**  
Only 50p per set of ten p & p free  
Free Data and Technical A-Z cards (build up the complete set month by month).  
Cheques and PO to Dept PWC Photonics, 3 Whitehall Gardens, London, E4.

**COMMUNICATION RECEIVERS**  
Checked, tested HRO, AR88, B40 and many others, also Power Supplies, Testgear etc. SAE please, stating requirements.

**STC AIRCRAFT RECEIVERS**  
Small compact 16 valve double conversion RX of modern design, covering 2-8-18.5 MHz in 3 bands. Features include: Unit Construction, Variable Selectivity, Xtal Controlled BFO, Manual or Remote Tuning, Illuminated Dial.  
The RX is designed to operate from 24 volts DC on 24 channels but can easily be modified for continuous tuning and mains operation. Circuit and modification details supplied with each unit. Excellent condition. £6.95. Carr. £1.

**RICHARD SELLERS**  
EASTINGTON, GOOLE, YORKSHIRE.  
04-305 254

## TV's TV's TV's

### SPECIAL OFFER LIMITED PERIOD ONLY

19" slim Thorn 800 TV's. 13 channel  
Good working order. Polished cabinets.  
Only £9.50 PLUS £1.50 Carr.

### EX-RENTAL TV's (Untested)

Complete with 13 channel tuners. Good cabinets.  
Carriage £1.50 extra.

|                             |        |
|-----------------------------|--------|
| 17" Semi Slim (90° Tube) .. | £8.50  |
| 17"/21" Slim (110° Tube) .. | £4.50  |
| 19" Slimline .. .. .        | £8.50  |
| 23" Slimline .. .. .        | £8.50  |
| 19" BBC2 Sets .. .. .       | £14.50 |

### PERFECT SPEAKERS EX T.V.

Pm 8 ohm (minimum order two) 5 in. round, 8 in by 2 in rectangular—12½p each. Add 7½p per speaker p. & p.

### VALVES EX EQUIPMENT

|        |      |       |      |       |      |
|--------|------|-------|------|-------|------|
| EB91   | 5p   | 30F4  | 12½p | FY81  | 15p  |
| EBF89  | 12½p | PC97  | 17½p | FY800 | 15p  |
| ECC82  | 12½p | PCF86 | 17½p | FY82  | 7½p  |
| EC180  | 7½p  | PC84  | 7½p  | FY338 | 22½p |
| EF80   | 12½p | PCF80 | 7½p  | UY191 | 17½p |
| EF85   | 12½p | PC89  | 12½p | 6F23  | 17½p |
| EF183  | 12½p | PCL85 | 22½p | 30PL1 | 22½p |
| EF184  | 12½p | PCL82 | 17½p | 30P12 | 20p  |
| EV86   | 17½p | PCL86 | 12½p | 30F5  | 10p  |
| 30PL13 | 20p  | PCL83 | 12½p |       |      |
| 630LZ  | 12½p | PL36  | 22½p |       |      |
| 30L15  | 12½p | PL81  | 17½p |       |      |

Add 2½p per valve p. & p., orders over £1 p. & p. free

### UHF TUNERS

For Ferguson 850 900 chassis adaptable for KB, Ekco T415, 1084 Chassis £2.50, p. & p. 50p.

### SLOT METERS

### SPECIAL OFFER

Smiths Mk. II 6d. Convertible to 5p. (Smiths Kit costs 35p each) £1 each inc. p. & pkg. or 10 for £5 inc. p. & pkg.

Please write with SAE for quotations on any spares.

## TRADE DISPOSALS (Dept. T.S.)

Thornbury Roundabout, Leeds Road, Bradford.  
(Telephone 665670)

### AERIAL BOOSTERS (£2.95)

We make four types of R.F. high gain transistorized pre-amplifiers L45 U.H.F. TV, L12 V.H.F. TV, L11 V.H.F. radio, L10 medium and short wave. For full details send S.A.E.

### PRINTED CIRCUIT BOARDS

2—9in by 4in boards with etching powder and instructions. 50p

### MAINS DROPPER

Three section 33 ohms by 33 ohms by 33 ohms. 9p each

### TV VALVES (EX EQ)

Any 5—45p, 10—70p, ECC82, ECL80, EF80, EF85, EF183, EB91, EY86, PCC84, PCC89, PCF80, PCF86, PCL82, PCL83, PCL84, PL36, PY33, PY81, PY82, Y800, 30L15

P & P ALL ORDERS 10p, SAE for details

**VELCO ELECTRONICS**, 62a Bridge St, Ramsbottom, Bury, Lancs.

### 3 MILLION RESISTOR SCOOP

Fantastic savings by huge purchase from manufacturer. High stability, close tolerance (1% to 5%) Carbon Film and a few Electrodisks, 1 watt to 2 watt, 20 to 40 Meg  $\Omega$  packed in 10's except 2 watt in 5's. Big choice values and wattages with plenty small types. Our selection: 85p per 500 car, 25p

£1.50 per 1,000 car, 28p

£15 per 10,000 car, free

DON'T MISS THIS BARGAIN

OFFER CANNOT BE REPEATED

**ELEY ELECTRONICS**

112 Groby Road, Glenfield,

Leicester LE3 8GL

## Stella Nine Range Cases

### LIST OF PRICES AND SIZES

| Width | Depth | 4" Height | 6" Height | 7 1/2" Height |
|-------|-------|-----------|-----------|---------------|
| 64"   | 34"   | 90p       | £1.05     | £1.23         |
| 64"   | 42"   | 96p       | £1.23     | £1.40         |
| 84"   | 34"   | £1.05     | £1.40     | £1.40         |
| 84"   | 64"   | £1.40     | £1.74     | £2.00         |
| 104"  | 74"   | £1.88     | £2.28     | £2.45         |
| 124"  | 34"   | £1.40     | £1.74     | £2.03         |
| 124"  | 54"   | £1.85     | £2.25     | £2.43         |
| 124"  | 84"   | £2.30     | £2.74     | £2.93         |
| 144"  | 34"   | £1.65     | £2.03     | £2.25         |
| 144"  | 94"   | £2.73     | £3.50     | £3.65         |
| 164"  | 64"   | £2.45     | £2.93     | £3.24         |
| 164"  | 104"  | £3.15     | £4.05     | £4.45         |

Cases—Post 25p. per order.

Discounts available on quantities.

**CHASSIS in Aluminium, Standard Sizes, with Gusset Plates**

Sizes to fit Cases. All 21 1/2" Walls

|         |     |          |     |           |     |
|---------|-----|----------|-----|-----------|-----|
| 6" x 3" | 33p | 10" x 7" | 51p | 14" x 3"  | 44p |
| 6" x 4" | 34p | 12" x 3" | 40p | 14" x 9"  | 84p |
| 8" x 3" | 39p | 12" x 5" | 45p | 16" x 6"  | 64p |
| 8" x 6" | 46p | 12" x 8" | 64p | 16" x 10" | 95p |

Chassis—Post 15p. per order.

Discounts available on quantities.

Electro magnetic counters. New Boxed.  
500 ohm 4 digit 30p post free.  
Copper Laminated Board "A" single sided.  
12" x 12" 30p. post free.  
P.O. relays (600 Type) 500 ohm + 500 ohm. 1 make 1 break 2 change over  
New boxed 30p post free.  
Heavy duty sliding reostat. 1 ohm 12 amp  
New boxed £1.25p. post free.

## E. R. NICHOLLS

Manufacturer of Electronic Instrument Cases

46 LOWFIELD ROAD  
STOCKPORT - CHESHIRE  
Tel: 061-480 2179

## CHROMASONIC electronics

supply only brand new guaranteed goods

### LOW NOISE HI-STABS

1 watt 5% all E24 values 3 for 5p plus p. & p. 6p up to 50 resistors + 1p for each additional 50.

### CAPACITORS

Mullard C280 -01  $\mu$ F, -015  $\mu$ F, -022  $\mu$ F, -033  $\mu$ F, -047  $\mu$ F, 3p each. -068  $\mu$ F 8p, -1  $\mu$ F, -15  $\mu$ F 4p, -22  $\mu$ F 5p, -33  $\mu$ F 8p, -47  $\mu$ F 8p, -68  $\mu$ F 11p, 1  $\mu$ F 13p, 15  $\mu$ F 80p, 2-2  $\mu$ F 24p.

Q439 series now all 5p. Also in stock C383, C431 and C437 series, plus polystyrene and S. mica.

### INTEGRATED CIRCUITS

|                                                         |               |
|---------------------------------------------------------|---------------|
| SN7400N, 1, 2, 4, 5, 10, 20, 26, 30, 40, 50, 51, 54     | all 23p ea.   |
| SN7400N, 42, 75, 81, 82, 90, 92, 93, 94, 95 all 87p ea. |               |
| MC1303L £1.55                                           | PA234 87p     |
| MC1304P £2.60                                           | PA237 87p     |
| MC1305P £2.50                                           | PA246 87p     |
| MFC4000P 70p                                            | TAA263 87p    |
| MFC4010P 75p                                            | TAA681B £1.90 |

### TRANSISTORS

|            |                |              |
|------------|----------------|--------------|
| BC107 12p  | AC128 17p      | BF167 25p    |
| BC108 11p  | AD161/162 68p  | BF173 25p    |
| BC109 12p  | 2N2484 87p     | BD100 87p    |
| BC168 15p  | 2N2926 O/Y 15p | BD105G 87p   |
| BC261 30p  | 2N3707 15p     | BZY88 series |
| BFY51 21p  | 2N4058 17p     | 7eners 15p   |
| 2N3053 25p | 2N5458 48p     | 2N3819 35p   |
| 2N3054 50p | 0A81/90/91 7p  | TY84 39p     |
| 2N3055 70p | 1N914 7p       | 1N4004 10p   |

### FREE CATALOGUE p. & p. 3p.

P. & p. on all orders other than resistors 6p  
56 FORTIS GREEN ROAD, LONDON, N10 3HN

## Receivers and Components

**EX-GOVT. COMMUNICATIONS RECEIVERS.** calibrators, signal generators, components, etc., with money back guarantee. SAE list. Callers welcome, please phone first.—P. R. Gollidge, G3EDW, Glen Tor, Torrington, Devon. (STD 08-052) 2411.

**BRAND NEW COMPONENTS** by return. Electrolytics 15 or 25 volts, 1, 2, 5, 10 mfd. 3-5p 25, 50 4p, 100 5p. Mylar film 100V .001, .002, .005, .01, .02 2p, .04, .05, .1 2-5p. Mullard miniature Carbon Film Resistors 1/2 W E.12 series 10-10M08 for 5p. Postage 5p. The C.R. Supply Co., 127 Chesterfield Road, Sheffield S8.

## Service Sheets

# SERVICE SHEETS & MANUALS

LARGE RANGE OF MODELS AVAILABLE FOR RADIO, TELEVISION, TAPE RECORDERS, ETC.  
FROM 40p EACH - S.A.E. WITH ENQUIRIES PLEASE - 1971 INDEX LIST AVAILABLE 20p  
MULLARD TRANSISTOR AUDIO AND RADIO CIRCUITS (PRICE £1.70p)  
T.V. FAULT FINDING BOOK by DATA PUBLICATIONS LTD. " 57p  
MULLARD VALVE & SEMI CONDUCTOR DATA BOOK " 25p ) POST  
MAZDA VALVE & PICTURE TUBE DATA BOOKLET " 25p ) FREE  
BRIMAR VALVES & TELE-TUBE DATA LIST " 20p  
RESISTOR COLOUR CODE INDICATOR DISC " 13p  
Large selection of Television Colour Manuals available - Prices on request.

## BELL'S TELEVISION SERVICES

Albert Place, Harrogate, Yorkshire. Tel. 0423 - 86844

**SERVICE SHEETS.** Radio, TV etc. 8,000 models. List 10p. S.A.E. enquiries. TELRAY, 11 Maudland Bank, Preston.

**SERVICE SHEETS** (1925-1971) for Televisions, Radios, Transistors, Tape Recorders, Record Players, etc.; by return post, with free Fault-Finding Guide. Prices from 5p. Over 8,000 models available. Catalogue 13p. Please send S.A.E. with all orders/enquiries. Hamilton Radio, 54 London Road, Bexhill, Sussex. Telephone Bexhill 7097.

**SERVICE SHEETS.** TV, Radio, etc., 40p. Large stocks. S.A.E. with enquiries please, callers welcome. K. L. Bower, 35 Briarwood Drive, Wibsey, Bradford.

## TRADER SERVICE SHEETS

40p. each plus postage

We can supply Trader Service Sheets for most makes and types of Radios, Tape Recorders and Televisions—Manuals for some.

Cheques and open P.O.s returned if sheets not available.

## OAKFIELD ENTERPRISES LIMITED

29 CHURCH ROAD, TUNBRIDGE WELLS, KENT

| Make | Model | Radio/TV |
|------|-------|----------|
|      |       |          |
|      |       |          |
|      |       |          |

1971 List now available at 10p. plus postage

If list is required indicate with X

From .....

Address .....

enclose remittance of .....

(and a stamped addressed envelope) s.a.e. with enquiries please

**MAIL ORDER ONLY**

**RADIO, TELEVISION** and Tape Recorders, 50 mixed odd sheets 50p. Also large stock of Obsolete/Current Valves. John Gilbert TV, 1B Shepherds Bush Road, London W6. 01-743 8441. SAE enquiries.

## LARGE SUPPLIER OF SERVICE SHEETS

(T.V., RADIO, TAPE RECORDERS, RECORD PLAYERS, TRANSISTORS, STEREOGRAMS, RADIOGRAMS, CAR RADIOS)

Only 25p each, Manuals from 50p.  
"PLEASE ENCLOSE LARGE S.A.E. WITH ALL ENQUIRIES & ORDERS"  
Otherwise cannot be attended to  
(Uncrossed P.O.s please, original returned if service sheets not available.)

## C. CARANNA

71 BEAUFORT PARK LONDON, N.W.11

We have the largest supplies of Service Sheets (strictly by return of post). Please state make and model number alternative.

Free TV fault tracing chart or TV list on request with order.  
Mail order only.

## QUICK, EFFICIENT, UNIQUE SERVICE SHEET SERVICE

Very Large Stock  
TVs, Radio, Amps, Test Gear.  
Special Telephone Service available to Trade Customers.  
Colour TV and Test Gear Circuits.  
Exchange Service.

Full details with First Order.  
List price 10p post free.

State Make and Model Number  
Large S.A.E. and 25p unfilled P.O.

Mail Order Only.

**A.S.L., 21c Drydon Chambers,**  
119 Oxford Street,  
London, W1R 1PB

## Courses

## BOURNEMOUTH COLLEGE OF TECHNOLOGY

DEPARTMENT OF ELECTRICAL AND ELECTRONIC ENGINEERING

## B.Sc. (Eng.) HONOURS DEGREE

in Electrical and Electronic Engineering

Entrance Requirements G.C.E. O or A Levels, O.N.D., O.N.C. or H.N.C.

## DIPLOMA IN COMPUTER TECHNOLOGY

Two year full-time course of O.N.D. standard. Entrance requirements G.C.E., O or C.S.E.

For details and application forms write to T. A. Goodchild, Head of Department of Electrical and Electronic Engineering, Room E3, College of Technology, Lansdowne, Bournemouth, BH1 3JJ.

## For Sale

## MORSE MADE !! EASY !!

**FACT NOT FICTION** If you start **RIGHT** you will be reading amateur and commercial Morse within a month (normal progress to be expected).

Using scientifically prepared 3-speed records you automatically learn to recognise the code RHYTHM without translating. You can't help it. It's as easy as learning a tune. 18 W.P.M. in 4 weeks guaranteed.

For details and course G.O.D. ring 8.T.D. 01-660 2896 or send 4p stamp for explanatory booklet to:

G3HSO (Box 19), 45 GREEN LANE, PURLEY, SURREY

**YUKAN SELF-SPRAY**

Get these **air drying GREY HAMMER** **OR BLACK WRINKLE (CRACKLE) Finishes** **NOW!**

Yukan Aerosol sprayk contains 4536 fine quality durable easy instant spray. No stove baking required. Hammers available in grey, blue, Modern Eggshell Black Wrinkle (Crackle) all at 85p in our counter or 90p carriage paid, per push-button self-spray can. Also Durable, heat and water resistant Black Matt finish (359p, self-spray can only). 75p carriage paid.

**SPECIAL OFFER:** I can plus optional transferable suction trigger handle (value 25p) for 90p, carriage paid. Choice of 13 self-spray plain colours and primer (Motor or quality) also available. Please enclose cheque or crossed P.O. for total amount direct to:

**Dept: M9 YUKAN, 307A, EDGWARE ROAD, LONDON, W2 1BN**

We supply many Government, Department, Municipal, Authorised, Magistrates and Leading Industrial Organisations. We can supply you too.

Open all day Saturday, Closed Thursday afternoon.

**SEEN MY CAT?** 5,000 items. Mechanical & Electrical Gear, and materials. S.A.E. K. R. WHISTON, Dept. PW, NEW MILLS, Stockport.

**BUSH TP60** Cassette Recorder, Mains supply, microphone, extra output socket, good condition, maker's carton, £12 o.n.o.—Box No. 98.



## Wanted

**WE BUY New Valves and Transistors.**  
State price: A.D.A. MANUFACTURING  
CO., 116 Alfreton Road, Nottingham.

**TOP PRICES PAID for NEW VALVES**  
popular T.V. and Radio types.

**KENSINGTON SUPPLIES (C),**  
367 Kensington Street, Bradford 8,  
Yorkshire.

**WE BUY New Valves, Transistors and**  
clean new components, large or small  
quantities, all details, quotation by  
return. **WALTON'S WIRELESS**  
**STORES, 55 Worcester Street, Wolver-**  
**hampton.**

**CASH PAID for New Valves. Payment**  
by return. **WILLOW VALE, ELEC-**  
**TRONICS, 4 The Broadway, Hanwell,**  
**London, W.7. 01-567/5400-2971.**

**WANTED. Ex-RAF HF Transmitter**  
Type T1119 or T1138. Circuit. Condition  
not important. Box No. 97.

**HIGHEST POSSIBLE cash prices for**  
Akai, B. & O., Brenell, Ferrograph,  
Revco, Sanyo, Sony, Tandberg, Uher,  
Vortexion, etc. 9.30-5.00. 01-242 7401.

## Ladders

**VARNISHED TIMBER LADDERS** from  
manufacturer. Lowest prices anywhere.  
15½ ft. extd. £6-20, 17ft. ext. £6-50, 20ft.  
ext. £7, 21½ ft. ext. £7-75, 24½ ft. ext.  
£8-90, 29ft. ext. £10-25, 31½ ft. triple  
ext. £12-25, 36ft. triple ext. £16. Carr.  
80p. Free lists. Also Aluminium Ext. &  
Loft Ladders. Callers welcome.—(Dept.  
W.L.S.) Home Sales, Baldwin Road,  
Stourport, Worcs. Phone 02-993 2574/  
5222. Placing order on C.O.D.

## Metal Work

**METAL WORK:** All types cabinets,  
chassis, racks, etc., to your specifica-  
tions. **PHILPOTTS METAL WORKS**  
**LTD., Chapman Street, Loughborough.**

## Miscellaneous

## TOP TRANSISTORS

Brand New and Individually Tested Tran-  
sistors supplied unmarked, but packed  
separately for identification and guaranteed  
to be within their correct specification or  
money refunded. All at 9p. each or

Any 25 transistors for only £1.90

|       |       |        |        |
|-------|-------|--------|--------|
| ACY22 | BFY51 | OC72   | 2N3702 |
| BC108 | BFY52 | OC202  | 2N3703 |
| BC109 | BSY27 | ZTX300 | 2N3705 |
| BC168 | OC45  | 2N706  | 2N3706 |
| BC169 | OC71  | 2N2926 | 2N3708 |

Money back guarantee, P. & P. 10p.

**J. M. KING (M)**

17 Buckridge, Portpool Lane, London, E.C.1

## LIGHTWEIGHT TREASURE-PROBE

Look for **BURIED COINS**, silver, gold  
and metal relics **PROFESSIONALLY**  
with the **BOFFIN** solid-state **TREASURE-**  
**PROBE**. An extremely **EASY-TO-BUILD**  
kit that **REALLY DOES WORK!** **SIMPLE-**  
**TO-FOLLOW INSTRUCTIONS.** It comes  
to your doorstep with maximum-copper  
**PRINTED-CIRCUIT BOARD** plus **ALL**  
**ELECTRONIC COMPONENTS** including  
search-coil and earphone. Think of the  
fun you'll have **BEA CHOMBING** with  
the sensitive **TREASURE-PROBE** and  
the expectancy of hearing its **LOUD**  
**'BEEP'** to tell you **"YOU'RE ON TO**  
**SOMETHING!" GET YOUR TREASURE-**  
**PROBE SEND £5-95 NOW!**

### BOFFIN PROJECTS

4, CUNLIFFE RD.  
STONELEIGH EWELL  
SURREY

Designed by **GERRY BROWN & JOHN**  
**SALMON** and presented on TV

## THE NEW

## ELECTRONIC MUSIC FOR YOU

Then how about making yourself an elec-  
tric organ? Constructional data available  
—full circuits, drawings and notes! It has  
5 octaves, 2 manuals and pedals with 24  
stops—uses 41 valves. With its variable  
attack you can play Classics and Swing.  
Write **NOW** for free leaflet and further  
details to **C. & S., 20 Maude Street,**  
**Darlington, Durham.** Send 2½p stamp.

## 12 VOLT FLUORESCENT LIGHTS



Beat Power Cuts, 12 ins 8 watt Tube, Ideal  
for Caravan, Tent, Emergency Lighting etc,  
Fully Transistorised, Low Battery Drain,  
With ON/OFF Switch and 12v Socket to  
Run other Lights or 12V Equipment.

Unbeatable at **£3-30** post paid  
or in kit form **£2-90**

**SALOP ELECTRONICS** Callers welcome  
23 Wyle Cop  
Shrewsbury, Shropshire S.A.E. for lists

## INCOMPARABLE V.H.F. KIT

CV2—unique triple-purpose (Converter,  
Receiver, Tuner-Feeder) kit for the Amateur  
enthusiast. Fantastic transistorized per-  
formance, World Wide Sales. Complete  
kit of top grade parts with coils covering  
80-180 MHz, plus easy/built diagrams and  
instructions. £4 direct from makers or  
S.A.E. for free literature.

### JOHNSONS (RADIO)

**ST. MARTINS GATE WORCESTER**  
Est. 1943 Tel. 24864

(A division of the G-BAN Organisation)

## TAPE HEADS PICK-UP CARTRIDGES

**SERVICE MANUALS** for Pre 1958  
H.M.V. and E.M.I. MODELS.  
Radio and Record Player Manuals  
25p each. Television Manuals  
37½p each. Send C.W.O. stating  
model required.

Send stamp for comprehensive  
lists of transformers, condensers,  
resistors, cartridges and tape  
heads.

**R. D. I. LTD.,**

Chilton Works, Garden Road,  
Richmond, Surrey.

## 17' BBC/ITV TELEVISIONS £5

Working Perfectly  
plus P&P £1 CWO.

## SUITABLE FOR ANY AREA

3 Channel 19in D/S TVs. ITV, BBC 1, BBC 2,  
£25 inc. carriage. 17in 13 Channel, complete  
but untested £21-50 each, plus £1 P&P. CWO.

### SPEAKERS

6in x 4in, 7in x 4in 30HMM  
20p plus 8p P&P each. CWO.

Regular deliveries throughout England and  
N. Ireland.

### TRADE TV'S

407 Thornton Road, Gillington, Bradford 8,  
Yorks.

## NO NEED TO WORRY ABOUT A TRANSMITTING LICENCE

because this GPO approved transmitter/receiver  
kit does not use R.F. and you can get one easily.  
Your transmissions will be virtually **SECRET** since  
they won't be heard by conventional means.  
Actually it's **TWO KITS IN ONE** because you get all  
the printed-circuit boards and components for both  
the transmitter AND receiver. You're going to find  
this project **REALLY FUN-TO-BUILD** with the  
**EASY-TO-FOLLOW** instructions. An extremely  
flexible design with quite an **AMAZING RANGE**—  
has obvious applications for **HOUSE-TO-HOUSE**  
**USE, SCHOOL PROJECTS, LANGUAGE**  
**LABORATORIES, SCOUT CAMPS, etc.**

**GET YOURS! SEND £5-20 NOW**

**TO: 'BOFFIN PROJECTS'**

DEPT. KW2010  
4 CUNLIFFE ROAD  
STONELEIGH, EWELL, SURREY

## JOHN SAYS...

**RING MODULATOR** by Dewtron is  
professional, transformerless, 5-transistor,  
has adjustable FI/F2 rejection. Module £7.  
Unit £8-90. WAA-WAA Pedal kit of all  
parts, incl. all mechanics & instr. Only  
£2-45. **AUTO RHYTHM** from Dewtron  
modules. Simple unit for waltz, foxtrot  
etc. costs £16-55 in modules. **SYNTHES-**  
**ISER MODULES** and other miracles.  
Send 15p for illust. list.  
**D.E.W. Ltd., 254 Ringwood Road,**  
**Ferndown, Dorset.**

We stock all those components and  
materials required by the home Hi-Fi  
constructor, including speaker grille  
fabrics, BAF wadding, speaker kits,  
cabinets, cross-over networks, inductors,  
etc. **AT TOP DISCOUNTS.** Price list free  
of charge. Send 2 x 3p stamps for pattern  
card of speaker grille fabrics. Mail order  
**ONLY.** No callers please.

**AUDIOSCAN** Dept. PW9  
4 PRINCES SQUARE  
HARROGATE, YORKS.

**SERVICE MANUALS** for Pre 1958 H.M.V. and E.M.I. MODELS. Radio and Record Player Manuals 25p each. Television Manuals 37½p each. Send C.W.O. stating model required. Also limited range of components and spares. Send details of your requirements. R.D.I. Ltd., Chilton Works, Garden Road, Richmond Surrey.

**DAILY UFO** Flight Patterns, 37½p. UFO Map, S. England, 37½p. TV Notes on UFO Detection, two Optical Circuits, 50p. UFO Wave Pattern and Prediction, 45p. R & P Publications, "Highlands," Needham Market, Suffolk.

**PETERBOROUGH MOBILE RALLY** will be held on Sunday, 26th September. From 11 a.m. to 5 p.m., at Walton School, Walton, 3 miles north of Peterborough.

## SYNTHESISER MODULES

Send SAE for details of voltage-controlled modules for synthesiser construction to D.E.W. Ltd., 254 Ringwood Road, Fern-down, Dorset.

**HEADPHONES** (Stereo) Diplomat Model by S. G. Brown, 10 pairs. Bargain £4.95 each. R.J.W. 27 Huxley Road, London, E.10. Tel. 01-556 8362.

**BUILD IT** in a DEWBOX quality cabinet. 2in x 2½in x any length. D.E.W. Ltd., Ringwood Road, FERN-DOWN, Dorset. S.A.E. for leaflet. Write now—Right now.

**RECORD TV SOUND** using our loud-speaker isolating transformer. Provides safe connection to recorder. Instructions included. 70p +10p P&P. CROWBOROUGH ELECTRONICS (P.W.), Eridge Road, Crowborough, Sussex.

## FAMOUS TELETON-AM/FM

### Stereo Tuner Amplifier R8000


Supplied complete with 2 speakers. Total 12 watts RMS. Specification MPX Beacon, AFC Connections for Tape Recorder, Stereo Headphone Socket, etc. Mfgs. Rec. Price £63.50

P.S.P. FANTASTIC OFFER **only £39.95**



Plus GARRARD DECK 2025 Complete with plinth and perspex cover. Fitted with superb Sonotone 9TAHC cartridge. P.S.P. offer **ONLY IF YOU**

**BUY THE ABOVE only £15.40**

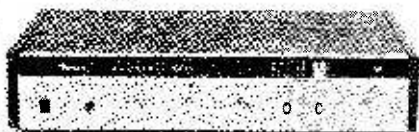

**PERSONAL SHOPPERS PLAN LTD.**

The Centre

36-38 West Green Road, Tottenham, N.15

Tel. No. 01-800 5533

SAVE £££

**ANOTHER PSP  
SUPER  
SCOOP**



All orders C.W.O. Special Securicor fast delivery £3.

### TELETON SAQ 206 STEREO AMPLIFIER

Latest release, beautifully styled in walnut case, 6+6 watts r.m.s. Switched inputs for magnetic X tal, aux, Tape. Incorporates volume, bass, treble and, slide balance control, scratch filter and loudness control. Rec. £32.50.

Our price £19.95.

Suggested System.

SAQ 206 Amplifier, SP25 III Plinth and Cover, G800 cartridge, pair large 3-way speaker system size 18" x 10" x 7" Would normally cost £85 complete. Our price £59.95

## The BATTERIES That Won't Let You Down! RECHARGEABLE

Cells in U2, U11  
and Penlite  
U7 sizes  
Kestrel Battery  
Charging Unit



### Uses:

Tape recorders, Portable radio and TV, Radio controlled model aircraft and boats, Cine cameras, Flashguns, Cordless shavers and other battery appliances.

Whenever you must have utterly dependable battery power—then these new Alkaline-Manganese rechargeable cells will provide it. The cells can be recharged many times, a simple job with the Kestrel Charging Unit which has been specially designed for these new type batteries.

### PRICES

Batteries U2 equiv. £1-25

Penlite U7 equiv. 50p

U11 equiv. £1-03

Charging unit £3-99 with one battery holder



Send to:

275 WEST END LANE  
LONDON, N.W.6  
01-794 9611

## LOOK AT THESE PRICES

### CARTRIDGES

Acos GP67-2, GP91-85C £1-12½; Acos GP93-1 £1-33½; Acos GP94-1 £1-62½; Sonotone 9TAHC £1-97. All above in makers' cartons. BSR X4H £1-50.

### THIS MONTH'S SPECIAL OFFER

Garrard SP25 Mk. III with K840A cartridge. In good quality teak plinth with perspex dust cover. Complete with all leads ready to use £20. SP25 Mk. III deck only less cartridge £11-87.

### PLUGS & SOCKETS

Phono plugs, assorted colours 4½p; 45p per doz. Coaxial plugs, aluminium 7½p; Coaxial couplers 7½p; 2 pin DIN plugs 15p; 3 pin DIN plugs 15p; 5 pin DIN plugs 17p; 2 pin, 3 pin & 5 pin DIN sockets 7½p; Wanderer plugs 2½p; sockets 3½p; Banana plugs 5½p; Sockets 5p; 3-5mm J/Plugs 7½p and 12½p; Standard J/Plugs with solder terminals 10p; Chrome 15p; Side Entry J/Plugs black and chrome 24p; Insulated J/sockets—o/cet 20p, e/cet 17p.

### ELECTROLYTIC CAPACITORS

4uF 160v 4p; 8uF 500v 15p; 10uF 160v 4p; 12uF 25v 4p; 16uF 450v 14p; 16uF + 16uF 450v 23½p; 30uF 10v 4p; 50uF 10v 4p; 100uF 9v 4p; 100uF 12v 4p; 150uF 12v 4p; 320uF 9v 5p; 1500uF 30v 19p; 10uF 16v 7½p; 5000uF 25v 50p; 10,000uF 25v 75p; 20,000uF 30v £1-05.

### MICROPHONES

Acos Mic 45 £1-12½; Acos Mic 60 99p; Planet CM70 £1-50; Hand Mike 75p.

### VALVES

PY81 36p; PCL82 39p; EF183 45p; EF184 45p

Postage extra.

**GEORGE FRANCIS (Dept PW),**

12-14, MIDDLE GATE, NEWARK, NOTTS.  
Telephone: Newark 4733.

## U.H.F. T.V. AERIALS

SUITABLE FOR COLOUR AND MONO-CHROME RECEPTION

All U.H.F. aerials now fitted with tilting bracket and 4 element reflector.

**LOFT MOUNTING ARRAYS**  
7 element 2-25, 11 element 2-75, 14 element 3-25, 18 element 3-75.  
**WALL MOUNTING c/w WALL ARM & BRACKET**  
7 element 3-25, 11 element 3-75, 14 element 4-25, 18 element 4-75. **CHIMNEY MOUNTING ARRAYS c/w MAST & LASHING KIT.** 7 element 4-00, 11 element 4-50, 14 element 4-75, 18 element 5-25. **MAST MOUNTING arrays only.** 7 element 2-25, 11 element 2-75, 14 element 3-25, 18 element 3-75. Complete assembly instructions with every aerial. **LOW LOSS** coaxial cable 9np yd. **KING TELEBOOSTERS** from 3-75. **LABGEAR** all band V.H.F.—U.H.F.—F.M. radio mains operated pre-amps 7-50. State clearly channel number required on all orders. P.p. on all aerials 50np. Accs. 15np. C.W.O. Min. C.O.D. charge 25np.

**BBC-ITV-FM AERIALS**  
**BBC** (band 1) Wall S/D 2-00. **LOFT** inverted 'T' 1-25. **EXTERNAL 'H'** array only 3-00. **ITV** (band 3) 5 element loft array 2-50. 7 element 3-00. **COMBINED BBC-ITV, loft 1+5-2-75, 1+7-3-50, WALL & CHIMNEY UNITS ALSO AVAILABLE.** Pre-amps from 3-75. **COMBINED U.H.F.—V.H.F.** aerials 1+5+9 4-00, 1+5+14 4-50, 1+7+14 5-00. **F.M. RADIO** loft S/D 1-00 3 element 3-25, 4 element 3-50. Standard coaxial plugs 9np. Coaxial cable 5np yd. Outlet box 30np. P.p. all aerials 50np. Accs. 30np. C.W.O. Min. C.O.D. charge 25np. Send 5np for fully illustrated lists.

**CALLERS WELCOMED  
OPEN ALL DAY SATURDAY  
K.V.A. ELECTRONICS  
40-41 MONARCH PARADE, LONDON  
ROAD, MITCHAM, SURREY  
Telephone 01-648 4884**

## S-DeC BREADBOARD

Solderless bread-board panels, for fast, reliable component connections. Single DeC's.

One S-DeC with Control Panel and booklet "Projects on S-DeC" giving construction details for a variety of circuits. £1. P. & P. 17p.

4-DeC KIT. Four S-DeCs with two Control Panels, and the booklet "Projects on S-DeC" all contained in a strong attractive plastic case. Ideal for the professional user. £3.95. P. & P. 17p.


T-DeC KIT £2.50. P. & P. 17p.

S-DeC STOR £2.50. P. & P. 17p.

## VHF AIRCRAFT BAND CONVERTER

When placed within 1in. of a MW band radio full coverage of VHF Aircraft Band 110-135 Mc/s can be obtained. All transistor, 9V battery operation. Fully tunable 18in. x 7 section telescopic aerial. Size 4in. x 2 1/2in. x 1 1/2in. OUR PRICE £3.60. P. & P. 20p

British Made

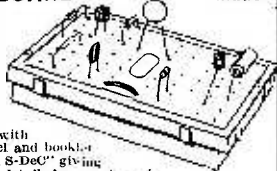

## GARRARD TURNTABLES

SP25 Mk.III £11.75

2025 T/C... £9.87

Base and cover for above... £5.98

AP76... £19.50

SL72B... £24.97

SL75B... £28.35

SL95B... £39.45

401... £31.50

Cover, 50p.

Base and cover for above £8.97-£9.45. P. & P. Decks, 62p. Base & Deck/Base/Cover, 87p.

### This Months Special Offers:

SP25 Mk.III with base £18.98. P. & P. 75p

SP25 Mk.III with Sonotone £18.75. P. & P. 75p

9TAHCD cartridge and base £16.75. P. & P. 75p

## LIND-AIR AUDIO

(DEPT. PW10), 53 TOTTENHAM COURT ROAD LONDON. W.1. Tel.: 01-637 1601



## PIEZO DYNAMIC MICROPHONE

50k  $\Omega$  £1.00 pp 8p

MULLARD SCREW TERMINAL CAP

4,300uf 64v 50p pp 13p.

BELLING LEE 1.5 amp in-line rubber covered

Interference suppressor 25p pp 8p.

SOLENOIDS 12 VOLT PULL ACTION

2" x 1" x 1/4" 40p pp 8p.

STO SEALED RELAYS DOUBLE POLE

CHANGOVER

48v 2500 Ex-equip. 15p pp 5p. Miniature 12v 280

New 2 changeover 40p pp 8p new.

SIEMENS MINIATURE RELAY. Double pole

changeover dust cover/base 48v 2500 50p pp 5p new.

TELESCOPIC AERIALS

Chromed 7" closed 28" extended 6 section ball

jointed base 22p pp 8p new.

MULLARD 4 DM 180 INDICATORS in plastic

holder/cover ex-equip. size approx. 1 1/2" x 1 1/2" x 3/8" 30p pp 8p.

PRINTED CIRCUIT BOARD/19 ACY 19's 10 OA200

Diodes: 1 reed relay: 10 AZ 229 zenner ass. capacitor/

resistors. Power supply 22v 250 m/A DC. Output

240v. AC £1 pp 20p ex-equip.

TOGGLE SWITCHES. Single pole Double Throw

ex-equip. new condition. 50p doz. pp 13p.

FIBRE GLASS TAPE. 100 yd. roll: 3" 3 1/2" wide

£1 per roll pp 20p.

PAINTON PLUG SOCKETS Type 139 series working

voltage 350v AC/DC current max. 3 amp AC/DC

7 pin plug & socket 50p pp 10p. 15 pin plug & socket

£1 pp 10p.

CASH WITH ORDER PLEASE

# FIELD ELECTRIC LIMITED


3 SHENLEY ROAD, BOREHAMWOOD, HERTS.

Adjacent Elstree Mainline Station

Tel: 01-953 6009.

## H.A.C. SHORT-WAVE KITS

### WORLD-WIDE RECEPTION

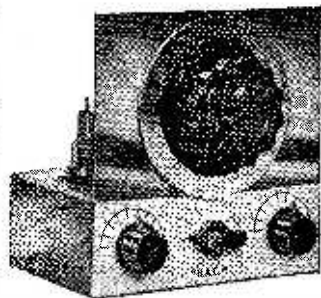

Famous for over 35 years for Short-Wave Equipment of quality, "H.A.C." were the Original suppliers of Short-Wave Receiver Kits for the amateur constructor. Over 10,000 satisfied customers—including Technical Colleges, Hospitals, Public Schools, R.A.F., Army, Hams, etc.

### NEW "DX" RECEIVER

Improved one-valve model "DX" mark 2. Complete kit—price £3.30 (post & packing 20p.). Customer writes: "Australia, India and America at loud volume."—"I am 14 years of age and have logged over 130 stations, plus countless Amateurs from all over the world."

Send S.A.E. for test report.

This kit contains all genuine short-wave components, drilled chassis, valve, accessories and full instructions. Ready to assemble, and of course, as all our products—fully guaranteed. Full range of other S.W. kits, including the famous model "K" and "K plus" (illustrated above). All orders despatched by return. (Mail order only.) Send now for free descriptive catalogue & order form.

"H.A.C." SHORT-WAVE PRODUCTS  
29 Old Bond Street, London W.1

# INDEX TO ADVERTISERS

|                                                |                    |
|------------------------------------------------|--------------------|
| ASL .. .. .                                    | 548                |
| Adcola Products Ltd. ..                        | Cov. II            |
| A. H. Supplies .. .. .                         | 460                |
| Antex .. .. .                                  | 455                |
| Audio Supplies .. .. .                         | 467                |
| AudioScan .. .. .                              | 549                |
| Baker Reproducers Ltd. ..                      | 496                |
| Bell's Television .. .. .                      | 548                |
| Bentley Acoustic Corporation Ltd. ..           | 536                |
| Bernard, Gerald .. .. .                        | 488                |
| B.I.E.T. .. .. .                               | 456, 532, Cov. III |
| Bi-Pak Semiconductors ..                       | 468, 469           |
| Bi-Pre-Pak Ltd. .. .. .                        | 451                |
| Boffin Projects .. .. .                        | 549                |
| Bournemouth College of Technology .. .. .      | 548                |
| British National Radio School ..               | 462, 519           |
| Broadway Electronics .. .. .                   | 456                |
| Bull, J., Electrical Ltd. ..                   | 491                |
| Bush & Meissner Ltd. .. .. .                   | 550                |
| C. and S. .. .. .                              | 549                |
| Caranna, C. .. .. .                            | 548                |
| Chromasonic Electronics .. .. .                | 547                |
| Colomar (Electronics) Ltd. ..                  | 528                |
| Comet High Fidelity Discount Warehouse .. .. . | 544, 545           |
| Concord Electronics Ltd. ..                    | 464                |
| Coventry Movement .. .. .                      | 450                |
| Crescent Radio .. .. .                         | 506                |
| C. T. Electronics .. .. .                      | 524                |
| Data Publications Ltd. .. .. .                 | 450                |
| D.E.W. Ltd. .. .. .                            | 549, 550           |
| Duke & Co. (London) Ltd. ..                    | 460                |
| Electro Value .. .. .                          | 487                |
| Electrotec .. .. .                             | 462                |
| Elektron Enterprises .. .. .                   | 542                |
| Eley Electronics .. .. .                       | 547                |
| F. and B. Electronics .. .. .                  | 547                |
| Felstead Electronics .. .. .                   | 560                |

|                                                   |               |
|---------------------------------------------------|---------------|
| Field Electric Ltd. .. .. .                       | 551           |
| Francis, George .. .. .                           | 550           |
| Francis, J. J. (Wood Green) Ltd. ..               | 488           |
| Galleon Trading Co. .. .. .                       | 546           |
| Global Audio Discount Warehouse ..                | 483           |
| Government Communications Headquarters .. .. .    | 546           |
| 'HAC' Shortwave Products .. .. .                  | 551           |
| Harverson Supplies Co. Ltd. .. ..                 | 527           |
| Heath (Gloucester) Ltd. .. .. .                   | 543           |
| Henry's Radio Ltd. .. .. .                        | Cov. IV       |
| Home Radio (Components) Ltd. ..                   | 470           |
| International Correspondence Schools .. .. .      | 546, 495, 524 |
| Ivoriet .. .. .                                   | 488           |
| Jef Electronics .. .. .                           | 546           |
| Jermyn Industries .. .. .                         | 496           |
| Johnsons (Radio) Ltd. .. .. .                     | 549           |
| KVA Electronics .. .. .                           | 550           |
| Kensington Supplies .. .. .                       | 549           |
| Keytronic .. .. .                                 | 546           |
| King, J. M. .. .. .                               | 549           |
| Lasky's Radio Ltd. .. .. .                        | 449           |
| Light Soldering Developments Ltd. ..              | 496           |
| Lindair (Optronics) Ltd. .. .. .                  | 551           |
| Linear Products .. .. .                           | Cov. II       |
| Lewis Radio .. .. .                               | 454           |
| Linstead .. .. .                                  | 488           |
| London Computer Operators Training Centre .. .. . | 454           |
| London Electronics College .. .. .                | 546           |
| M & B Components (Leeds) Ltd. ..                  | 456           |
| Marshall, A., Son. .. .. .                        | 531           |
| McArdle & Brainsby (Import & Export) Ltd. .. .. . | 462           |
| Multicore Solders Ltd. .. .. .                    | Cov. II       |
| Nicholls, E. R. .. .. .                           | 547           |
| Oakfield Enterprises .. .. .                      | 548           |

|                                              |               |
|----------------------------------------------|---------------|
| Padgetts Radio .. .. .                       | 536           |
| Pembroke College of Electronics, The .. .. . | 466           |
| Personal Shoppers Plan Ltd. .. ..            | 550           |
| Photronics .. .. .                           | 547           |
| Premier Radio .. .. .                        | 523           |
| R.D.I. Ltd. .. .. .                          | 549           |
| Radio Components Specialist .. ..            | 505           |
| Radio Exchange Co. .. .. .                   | 457           |
| Radio Society of Great Britain .. ..         | 536           |
| Radio & T.V. Components (Acton) Ltd. .. .. . | 464, 465      |
| Readers Radio .. .. .                        | 456           |
| ROC Electronics Ltd. .. .. .                 | 452, 453      |
| RCS Products Ltd. .. .. .                    | 450           |
| RSC Hi Fi Centres Ltd. .. .. .               | 458, 459      |
| RST .. .. .                                  | 542           |
| Scientific & Technical Services .. ..        | 454           |
| SEBA Electronic Photography .. ..            | 462           |
| Service Trading Co. .. .. .                  | 484           |
| Salop Electronics .. .. .                    | 549           |
| Sellers, Richard .. .. .                     | 547           |
| Selray Book Co., The .. .. .                 | 500, 528      |
| Sinclair Radionics Ltd. .. .. .              | 539, 540, 541 |
| Shoptunities Ltd. .. .. .                    | 466           |
| Smith G. W. & Co. (Radio) Ltd. .. .. .       | 535, 536, 537 |
| Stephens Electronics .. .. .                 | 520           |
| Suprlectronics .. .. .                       | 496           |
| Surplus Electronics Trading .. .. .          | 484           |
| Swanley Electronics .. .. .                  | 547           |
| Thacker, A. H. .. .. .                       | 484           |
| Trade TV's .. .. .                           | 549           |
| Velco Electronics .. .. .                    | 547           |
| West London Direct Supplies .. ..            | 450           |
| Wicks, D. T. & Co. .. .. .                   | 532           |
| York Electronics .. .. .                     | 542           |
| Yukan .. .. .                                | 548           |
| Z & I Aero Services Ltd. .. .. .             | 552           |

Head Office and Warehouse

44A WESTBOURNE GROVE

LONDON W2

Tel: 727 5641/2/3

# Z & I AERO SERVICES LTD.

Please send all correspondence and Mail-Orders to Head Office

When sending cash with order, please include 12½p in £ for postage and handling

MINIMUM CHARGE 15np. No C.O.D. orders accepted

Please note that the valves offered below are not necessarily of U.K. origin

Retail Shop

85 TOTTENHAM COURT ROAD

LONDON W1

Tel: 580 8403

Open all day Saturday

First Quality Fully Guaranteed




ELECTRONIC VALVES

|            |            |            |             |            |            |            |            |
|------------|------------|------------|-------------|------------|------------|------------|------------|
| 0A2 0.88   | 6AR11 1.25 | 6F11 0.40  | 10D2 0.50   | EP98 0.65  | GZ34 0.60  | PL82 0.45  | U301 0.40  |
| 0A3 0.45   | 6AS5 0.45  | 6F13 0.45  | 10F1 0.75   | EP183 0.30 | HAB080.45  | PL83 0.45  | U403 0.60  |
| 0B2 0.35   | 6AS7G 0.85 | 6F14 0.70  | 10F9 0.80   | EP184 0.35 | HE90 0.40  | PL84 0.40  | U404 0.60  |
| 0B3 0.70   | 6AT6 0.35  | 6F15 0.65  | 10F18 0.50  | EF800 1.00 | KT66 2.05  | PL902 0.35 | U801 0.80  |
| 0C3 0.38   | 6AU0 0.25  | 6F18 0.50  | 10L1 0.50   | EK90 0.30  | KT88 2.00  | PL504 0.80 | UABCS0     |
| 0D3 0.85   | 6AV6 0.30  | 6F23 0.85  | 10LD11 0.85 | EL33 1.25  | N78 1.50   | PL508 0.90 | 0.40       |
| 1B6GT 1.00 | 6AW8A 0.80 | 6F24 0.75  | 10P13 0.80  | EL34 0.50  | PABCS00.40 | PL509 1.10 | UAF41 0.50 |
| 1CP31 7.00 | 6BA6 0.25  | 6F25 1.00  | 10P14 1.10  | EL36 0.50  | PC86 0.60  | PL801 0.80 | UAF42 0.55 |
| 1L4 0.40   | 6BE8 0.30  | 6F26 0.35  | 12AB5 0.70  | EL37 1.80  | PC88 0.60  | PL802 0.95 | UBC41 0.50 |
| 1R4 0.45   | 6BF5 1.00  | 6F28 0.85  | 12AC6 0.50  | EL41 0.60  | PC87 0.50  | PM84 0.80  | UBC81 0.50 |
| 1R5 0.40   | 6BF6 0.55  | 6J4 0.50   | 12AD6 0.55  | EL42 0.65  | PC900 0.48 | PY31 0.30  | UF80 0.40  |
| 1S4 0.30   | 6BH6 0.75  | 6J5GT 0.30 | 12AE6 0.55  | EL81 0.55  | PC94 0.40  | PY33 0.83  | UF89 0.35  |
| 1S6 0.80   | 6BJ6 0.50  | 6J6 0.20   | 12AL5 0.55  | EL83 0.42  | PC95 0.40  | PY80 0.40  | UBL1 0.60  |
| 1T4 0.50   | 6BTA 0.60  | 6J7 0.45   | 12AQ5 0.50  | EL84 0.25  | PC98 0.55  | PY81 0.30  | UBL21 0.55 |
| 1U4 0.30   | 6BN6 0.45  | 6K6GT 0.60 | 0.80        | EL85 0.43  | PC99 0.55  | PY82 0.35  | UC92 0.40  |
| 1U5 0.80   | 6BN6 0.45  | 6K7 0.35   | 12AT7 0.35  | EL86 0.40  | PC189 0.55 | PY83 0.38  | UC96 0.40  |
| 1V2 0.50   | 6BR5 0.25  | 6K8G 0.40  | 12AU6 0.35  | EL90 0.38  | PC306 0.85 | PY88 0.40  | UC98 0.50  |
| 1X2B 0.50  | 6BR8 0.70  | 6K25 0.75  | 12AU7 0.30  | EL95 0.35  | PC306 0.85 | PY500 1.00 | UCH21 0.60 |
| 2D21 0.38  | 6B87 1.30  | 6L6GT 0.45 | 12AV6 0.40  | EL921 0.60 | PCF80 0.30 | PY800 0.40 | UCH42 0.70 |
| 3A1 0.40   | 6B96 0.85  | 6L7 0.40   | 12AV7 0.65  | EL922 1.30 | PCF82 0.35 | PY801 0.50 | UCH81 0.40 |
| 3B1 3.00   | 6BW7 0.50  | 6L18 0.45  | 12B7 0.75   | EL923 0.70 | PCF84 0.60 | PZ30 0.35  | UCL81 0.35 |
| 3V4 0.35   | 6BX6 0.25  | 6LD20 0.50 | 12B7G 0.75  | EM1 0.80   | PCF86 0.60 | QV02-6     | UCL82 0.35 |
| 384 0.48   | 6BZ6 0.40  | 6N7GT 0.45 | 12B4 0.60   | EM80 0.45  | PCF87 0.60 | QV03-10    | UCL83 0.60 |
| 5R4GY 0.75 | 6C4 0.38   | 6P1 0.60   | 12BA6 0.40  | EM81 0.60  | PCF88 0.50 | UF42 0.60  | 0.40       |
| 5U4G 0.35  | 6CG5T 0.40 | 6P28 0.65  | 12BA7 0.40  | EM82 0.35  | PCF89 0.50 | UF43 0.60  | 0.40       |
| 5V4G 0.40  | 6CB8 0.85  | 6Q7 0.40   | 12BE6 0.40  | EM83 0.35  | PCF89 0.50 | UF44 0.60  | 0.40       |
| 5Y3GT 0.40 | 6CGA 0.25  | 6Q7 0.40   | 12B7 0.45   | EM84 0.35  | PCF89 0.50 | UF45 0.60  | 0.40       |
| 5Z3 0.80   | 6CG7 0.55  | 6SG7 0.40  | 12B7 0.45   | EM85 1.00  | PCF89 0.50 | UF46 0.60  | 0.40       |
| 5Z4G 0.40  | 6CH6 0.80  | 6SK7 0.40  | 12K5 0.70   | EM87 0.70  | PCF89 0.50 | UF47 0.60  | 0.40       |
| 6J0L2 0.80 | 6CL6 0.55  | 6SL7GT0.35 | 12K7GT0.40  | EN61 0.35  | PCF89 0.50 | UF48 0.60  | 0.40       |
| 6AB4 0.35  | 6CWA 0.45  | 6SN7GT0.35 | 12Q7GT0.40  | EN61 0.35  | PCF89 0.50 | UF49 0.60  | 0.40       |
| 6AF4A 0.55 | 6CY5 0.45  | 6SQ7 0.40  | 12Q87 0.40  | EN61 0.35  | PCF89 0.50 | UF50 0.60  | 0.40       |
| 6AG7 0.40  | 6CY7 0.70  | 6SR7 0.40  | 20D1 0.50   | EN61 0.35  | PCF89 0.50 | UF51 0.60  | 0.40       |
| 6AIE 0.50  | 6DC 0.50   | 6T5 0.30   | 20L1 1.10   | EN61 0.35  | PCF89 0.50 | UF52 0.60  | 0.40       |
| 6AJ8 0.30  | 6DC8 0.80  | 6U4GT 0.65 | 20P1 0.50   | EN61 0.35  | PCF89 0.50 | UF53 0.60  | 0.40       |
| 6AK5 0.35  | 6DK6 0.50  | 6U8A 0.40  | 20P4 1.10   | EN61 0.35  | PCF89 0.50 | UF54 0.60  | 0.40       |
| 6AK6 0.60  | 6DQ6B 0.70 | 6V6GT 0.40 | 20P5 1.20   | EN61 0.35  | PCF89 0.50 | UF55 0.60  | 0.40       |
| 6AL3 0.43  | 6D84 0.75  | 6X4 0.35   | 25C5 0.50   | EN61 0.35  | PCF89 0.50 | UF56 0.60  | 0.40       |
| 6AL5 0.20  | 6EAS 0.80  | 6X5GT 0.40 | 25L6GT0.50  | EN61 0.35  | PCF89 0.50 | UF57 0.60  | 0.40       |
| 6AM5 0.35  | 6E7 0.70   | 6X8 0.60   | 25L6GT0.50  | EN61 0.35  | PCF89 0.50 | UF58 0.60  | 0.40       |
| 6AM6 0.38  | 6E7 0.70   | 6Y6G 0.70  | 25L6GT0.50  | EN61 0.35  | PCF89 0.50 | UF59 0.60  | 0.40       |
| 6AQ5 0.38  | 6EW6 0.70  | 7Y4 0.65   | 30A5 0.50   | EN61 0.35  | PCF89 0.50 | UF60 0.60  | 0.40       |
| 6AQ6 0.65  | 6F1 0.75   | 9BW6 0.60  | 30A6 0.50   | EN61 0.35  | PCF89 0.50 | UF61 0.60  | 0.40       |
| 6AR5 0.45  | 6F5 0.75   | 10C2 0.50  | 30C1 0.30   | EN61 0.35  | PCF89 0.50 | UF62 0.60  | 0.40       |
| 6AR6 0.55  | 6FGG 0.45  | 10D1 0.55  | 30C15 0.80  | EN61 0.35  | PCF89 0.50 | UF63 0.60  | 0.40       |

## TRANSISTORS

|              |             |             |
|--------------|-------------|-------------|
| 2N696 0.17   | AC127 0.20  | BD121 0.65  |
| 2N697 0.17   | AC128 0.15  | BD123 0.80  |
| 2N698 0.30   | AC135 0.35  | BD131 0.85  |
| 2N705 0.70   | AC135 0.80  | BD132 0.85  |
| 2N706 0.10   | AC154 0.15  | BD135 0.80  |
| 2N708 0.15   | AC157 0.20  | BF115 0.20  |
| 2N753 0.25   | AC169 0.10  | BF167 0.18  |
| 2N929 0.22   | AC176 0.25  | BF173 0.20  |
| 2N930 0.25   | AC187 0.30  | BF178 0.25  |
| 2N957 0.30   | AC188 0.30  | BF179 0.30  |
| 2N1131 0.25  | AC177 0.275 | BF180 0.35  |
| 2N1132 0.25  | AC178 0.20  | BF181 0.25  |
| 2N1184 1.25  | AC179 0.25  | BF184 0.25  |
| 2N1301 0.40  | AC180 0.20  | BF185 0.20  |
| 2N1302 0.75  | AC181 0.20  | BF194 0.15  |
| 2N1304 0.25  | AC182 0.15  | BF196 0.15  |
| 2N1305 0.25  | AD140 0.50  | BF196 0.20  |
| 2N1306 0.25  | AD149 0.50  | BF197 0.20  |
| 2N1307 0.30  | AD161 0.35  | BF200 0.35  |
| 2N1308 0.25  | AD162 0.35  | BFW87 0.25  |
| 2N1309 0.50  | AD161 1.25  | BFW88 0.25  |
| 2N1613 0.22  | AD212 1.25  | BFW89 0.20  |
| 2N1711 0.25  | AF114 0.20  | BFW91 0.20  |
| 2N1756 0.75  | AF115 0.20  | BFX88 0.25  |
| 2N2147 0.75  | AF116 0.20  | BFY17 0.40  |
| 2N2160 0.65  | AF117 0.20  | BFY19 0.60  |
| 2N2178 0.70  | AF118 0.20  | BFY20 0.60  |
| 2N2218 0.30  | AF125 0.25  | BFY51 0.20  |
| 2N2219 0.55  | AF127 0.20  | BFY52 0.25  |
| 2N2369A 0.20 | AF180 0.35  | BSY26 0.20  |
| 2N2477 0.65  | AF181 0.35  | BSY27 0.20  |
| 2N2646 0.80  | AF186 0.40  | BSY28 0.20  |
| 2N2905 0.30  | AF199 0.40  | BSY65 0.20  |
| 2N2923 0.15  | AF211 0.45  | BSY95A 0.15 |
| 2N2924 0.15  | ASV26 0.25  | OC16 0.50   |
| 2N2926 0.125 | ASV27 0.30  | OC22 0.50   |
| 2N3053 0.25  | ASV28 0.25  | OC23 0.60   |
| 2N3054 0.60  | ASV29 0.30  | OC24 0.60   |
| 2N3055 0.75  | ASV30 0.35  | OC25 0.35   |
| 2N3133 0.30  | ASZ15 0.75  | OC26 0.35   |
| 2N3134 0.30  | ASZ16 0.70  | OC28 0.60   |
| 2N3391 0.20  | ASZ17 0.75  | OC29 0.60   |
| 2N3392 0.15  | ASZ18 0.75  | OC30 0.75   |
| 2N3393 0.15  | ASZ20 0.25  | OC35 0.50   |
| 2N3394 0.15  | ASZ21 0.40  | OC36 0.60   |
| 2N3395 0.20  | BC107 0.125 | OC40 0.30   |
| 2N3402 0.15  | BC108 0.125 | OC44 0.20   |
| 2N3403 0.15  | BC109 0.125 | OC45 0.15   |
| 2N3404 0.35  | BC113 0.25  | OC70 0.10   |
| 2N3414 0.30  | BC118 0.30  | OC71 0.12   |
| 2N3415 0.15  | BC124 0.30  | OC72 0.25   |
| 2N3416 0.25  | BC147 0.175 | OC73 0.30   |
| 2N3417 0.25  | BC148 0.15  | OC75 0.20   |
| 2N3702 0.12  | BC149 0.15  | OC76 0.20   |
| 2N3703 0.12  | BC152 0.15  | OC78 0.25   |
| 2N3704 0.17  | BC158 0.15  | OC78D 0.20  |
| 2N3707 0.15  | BC175 0.20  | OC81 0.25   |
| 2N3709 0.12  | BC186 0.25  | OC81D 0.15  |
| 2N3710 0.12  | BCY30 0.25  | OC83 0.20   |
| 2N3819 0.35  | BCY31 0.40  | OC139 0.30  |
| 2N3906 0.20  | BCY33 0.25  | OC140 0.35  |
| 2S702 0.50   | BCY34 0.30  | OC141 0.60  |
| 2S746 0.25   | BCY72 0.20  | OC170 0.25  |
| AC113 0.15   | BCZ10 0.30  | OC171 0.25  |
| AC126 0.30   | BCZ11 0.40  | OC200 0.30  |
| AC126 0.50   | BD115 0.80  | OC202 0.55  |

## SYNCHROSCOPE TYPE C1-5

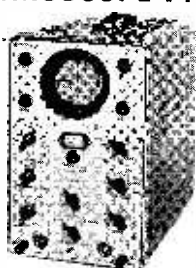

3-in tube fitted with telescopic viewing hood, giving bright display in full daylight.  
Bandwidth 10 c/s-10 Mc/s. Triggered sweep pre-set at 1-2-5-10-30-100-300-1000-3000  $\mu$ sec per stroke. Free-running time base 20 c/s to 2000k/s with built-in crystal calibrator providing timing marks at .05-.2-1-5-20-100  $\mu$  sec + 5%.  
Amplitude calibrator directly calibrated in volts.  
Input attenuator 1-10-100.  
Power supplies 127/230V AC.

PRICE £39.00. Packing and carriage 1.50

## MINIATURE CERAMIC CAPACITORS 25V WORKING

5% tolerance 22-27-33-39-47-56-68-82-100-120-150-180-220-270-330-390-470-560-680-820-1000pF  
All at 20np per twenty.  
+50%-20% tolerance 1500-2200-3300-4700-6800-10,000-15,000 pF—All at 23np per twenty.  
+80%-20% tolerance 0.022-0.033-0.047  $\mu$ F.  
All at 28np per twenty.  
Minimum orders 20 of one size.

## 10% TOL. METAL CASED PAPER CAPACITORS

250V DC: 0.05-0.10-0.25-0.5-1.0 $\mu$ F £1.00 per twenty  
500V DC: 0.025-0.05-0.10-0.25-0.50 $\mu$ F £1.25 per twenty  
Minimum Orders: 20 Capacitors

## 10-AMP SILICON STUD MOUNTED RECTIFIERS

BYX42-3000 piv 0.35  
BYX42-600 piv 0.40  
BYX42-900 piv 0.55  
BYX42-1200 piv 0.65  
All these are available also with reversed polarity, i.e. stud anode.

## TWO NEW MULTIMETERS FROM RUSSIA



Type U4312  
U4313

with AC current ranges

Type U4312—Low sensitivity instrument (667 o.p.v.) 1% accuracy on DC (30 $\mu$ A to 6A)

DC and 1-5% on AC. 9 current ranges on AC (1.5mA to 6A). 9 voltage ranges 0.3 to 900V AC/DC. Resistance 0.2 to 30k  $\Omega$ . Mirror scale.

PRICE, complete with leads and steel carrying case £9.75

Type U4313—20,000 o.p.v. DC and 2,000 o.p.v. on AC. 8 DC current ranges 60 $\mu$ A to 1-5A. 6 AC current ranges 0.5 to 1-5A. 9 DC and AC voltage ranges 1-5-500V. Resistance ranges 0.5-500k  $\Omega$ . Accuracy 1-5% DC and 2-5% AC. Mirror scale.

PRICE, complete with test leads and steel carrying case £10.50



## AC/DC MULTIMETER AND TRANSISTOR TESTER

8-DC voltage ranges 3-900V  
6-AC voltage ranges 1.5-750V  
5-DC current ranges 0-60-600mA  
4-AC current ranges 0.3-300mA  
4-resistance ranges 0.5-500 Kohms  
Transistor cut-off current 60 $\mu$ A max  
Transistor DC current gain 10-350  
Sensitivity: 16700  $\Omega$ /V DC;  
3300  $\Omega$ /V AC  
PRICE £10.50

OUR NEW 1971/1972 CATALOGUE IS NOW READY AND AVAILABLE FREE OF CHARGE. PLEASE SEND QUARTO STAMPED AND ADDRESSED ENVELOPE FOR THIS VALUABLE SOURCE OF REFERENCE LISTING MANY THOUSAND TYPES OF VALVES, SEMICONDUCTORS, TUBES, ETC.

# In just 2 minutes, find out how you can qualify for promotion or a better job in Engineering...

That's how long it will take you to fill in the coupon below. Mail it to B.I.E.T. and we'll send you full details and a free book. B.I.E.T. has successfully trained *thousands* of men at home - equipped them for higher pay and better, more interesting jobs. We can do as much for YOU. A low-cost B.I.E.T. Home Study Course gets results fast - makes learning easier and something you look forward to. There are no books to buy and you can pay-as-you-learn on 'SATISFACTION - OR REFUND OF FEE' terms. If you'd like to know how just a few hours a week of your spare time, doing something constructive and enjoyable, could put you out in front, post the coupon today. No obligation.

## WHICH SUBJECT WOULD INTEREST YOU?

### Mechanical

A.M.S.E. (Mech.)  
Inst. of Engineers  
Mechanical Eng.  
Maintenance Eng.  
Welding  
General Diesel Eng.  
Sheet Metal Work  
Eng. Inspection  
Eng. Metallurgy  
C. & G. Eng. Crafts  
C. & G. Fabrication

### Draughtsmanship

A.M.I.E.D.  
Gen. Draughtsmanship  
Die & Press Tools  
Elec. Draughtsmanship  
Jig & Tool Design  
Design of Elec. Machines  
Technical Drawing  
Building

### Electrical & Electronic

A.M.S.E. (Elec.)  
C. & G. Elec. Eng.  
General Elec. Eng.  
Installations & Wiring  
Electrical Maths.  
Electrical Science  
Computer Electronics  
Electronic Eng.

### Radio & Telecomms.

C. & G. Telecomms.  
C. & G. Radio Servicing  
Radio Amateurs' Exam.  
Radio Operators' Cert.  
Radio & TV Engineering  
Radio Servicing  
Practical Television  
TV Servicing  
Colour TV  
Practical Radio & Electronics (with kit)

### Auto & Aero

A.M.I.M.I.  
MAA/IMI Diploma  
C. & G. Auto Eng.  
General Auto Eng.  
Motor Mechanics  
A.R.B. Certs.  
Gen. Aero Eng.

### Management & Production

Computer Programming  
Inst. of Marketing  
A.C.W.A.  
Works Management  
Work Study  
Production Eng.  
Storekeeping  
Estimating  
Personnel Management  
Quality Control  
Electronic Data Processing  
Numerical Control

Planning Engineering  
Materials Handling  
Operational Research  
Metrication

### Constructional

A.M.S.E. (Civ.)  
C. & G. Structural  
Road Engineering  
Civil Engineering  
Building  
Air Conditioning  
Heating & Ventilating  
Carpentry & Joinery  
Clerk of Works  
Building Drawing  
Surveying  
Painting and Decorating  
Architecture  
Builders' Quantities

### General

C.E.I.  
Petroleum Tech.  
Practical Maths.  
Refrigerator Servicing  
Rubber Technology  
Sales Engineer  
Timber Trade  
Farm Science  
Agricultural Eng.  
General Plastics

### General Certificate of Education

Choose from 42 'O' and 'A' Level subjects including:

English  
Chemistry  
General Science  
Geology  
Physics  
Mathematics  
Technical Drawing  
French  
German  
Russian  
Spanish  
Biology  
B.I.E.T. and its associated schools have recorded well over 10,000 G.C.E. successes at 'O' and 'A' level.

WE COVER A WIDE RANGE OF TECHNICAL AND PROFESSIONAL EXAMINATIONS.

Over 3,000 of our Students have obtained City & Guilds Certificates. Thousands of other exam successes.

## THEY DID IT—SO COULD YOU

"My income has almost trebled . . . my life is fuller and happier." - Case History G/321.

"In addition to having my salary doubled, my future is assured." - Case History H/493.

"Completing your Course meant going from a job I detested to a job I love." - Case History B/461.

## FIND OUT FOR YOURSELF

These letters - and there are many more on file at Aldermaston Court - speak of the rewards that come to the man who has given himself the specialised know-how employers seek. There's no surer way of getting ahead or of opening up new opportunities for yourself. It will cost you a stamp to find out how we can help you.

# Free!

Why not do the thing that really interests you? Without losing a day's pay, you could quietly turn yourself into something of an expert. Complete the coupon (or write if you prefer not to cut the page). We'll send you full details and a FREE illustrated book. No obligation and nobody will call on you . . . but it could be the best thing you ever did.

## BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY

Dept B2, Aldermaston Court, Reading RG7 4PF.

(Write if you prefer not to cut this page)



## POST THIS COUPON TODAY

To: B.I.E.T., Dept B2, Aldermaston Court, Reading RG7 4PF.  
Please send me book and details of your Courses in

Name..... Age.....

Address.....

Occupation.....

453A

B.I.E.T.—IN ASSOCIATION WITH THE SCHOOL OF CAREERS—ALDERMASTON COURT, BERKSHIRE

Published approximately on the 7th of each month by IPC Magazines Limited, Fleetway House, Farringdon Street, London, E.C.4. Tel: 01-634 4444. Printed in England by Index Printers, Dunstable, Beds. Sole Agents for Australia and New Zealand—Gordon and Gotch (A/asia) Ltd.; South Africa—Central News Agency Ltd.; Rhodesia and Zambia—Kingston Ltd.; East Africa—Stationery and Office Supplies Ltd. Subscription rate (including postage); For one year to any part of the world £2-65.

PRACTICAL WIRELESS is sold subject to the following conditions, namely, that it shall not, without the written consent of the Publishers first given, be lent, resold, hired out or otherwise disposed of by way of Trade at more than the recommended selling price shown on the cover, and that it shall not be lent, resold or hired out or otherwise disposed of in a mutilated condition or any unauthorised cover by way of Trade, or affixed to as part of any publication or advertising, literary or pictorial matter whatsoever.

www.americanradiohistory.com




# HENRY'S RADIO LIMITED

## ENGLAND'S LEADING ELECTRONIC CENTRES

HENRY'S RADIO

HI-FI · COMPONENTS · TEST · PA · DISCOTHEQUE · ELECTRONIC ORGANS · MAIL ORDER
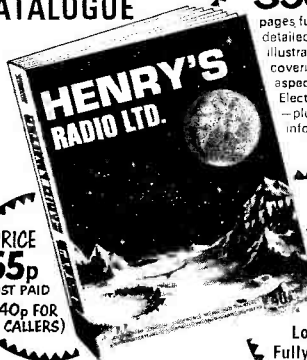
### COMPLETELY NEW 10th EDITION CATALOGUE



**350**

pages fully  
detailed and  
illustrated  
covering every  
aspect of  
electronics  
—plus date and  
information

**PRICE  
55p**  
POST PAID  
(40p FOR  
CALLERS)

**10,000**  
Stock lines  
at Special  
Low Prices and  
Fully Guaranteed

**PLUS! FIVE 10p VOUCHERS  
FOR USE WITH PURCHASES**

Send to this address—Henry's Radio Ltd., (Dept. PW),  
3 Albemarle Way, London, E.C.1.—for catalogue only.

**A NEW HENRY'S CATALOGUE IS  
A MUST FOR ELECTRONICS TODAY!**

### TEST EQUIPMENT FOR EVERY PURPOSE



SE508 Pocket pencil signal injector. Price £1.75, p.p. 15p.  
SE500 Pocket pencil signal tracer. Price £1.50, p.p. 15p.  
TE200 RF generator. Price £15, p.p. 40p.  
TE22D Matching audio generator. Price £17, p.p. 40p.  
TE15 Grid dip meter. Price £12.50, p.p. 40p.  
TO3 Scope 3 in. tube. Price £37.50, p.p. 50p.  
TE22 Audio Generator. Price £17, p.p. 40p.



### PANEL METERS

Complete range in stock. 38, 65 and 85 types plus large range Edge types also 240°-250° types.  
(Get a copy of our latest catalogue for full specifications and further ranges.)


**MORE OF EVERYTHING AT LOW  
PRICES ALWAYS FROM HENRY'S**

★ **COMPONENTS IN STOCK FOR  
ALMOST ALL PUBLISHED DESIGNS.  
YOUR ENQUIRIES INVITED. SEND  
LARGE S.A.E. FOR QUOTATION.**

See our advertisement inside this magazine for the largest range of transistors etc. available in U.K.—Free list No. 36 on request.

**HENRY'S SUPPLY ALL YOUR  
AUDIO-ELECTRONIC NEEDS!**

### TRANSISTOR AMPLIFIERS

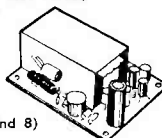

(Leaflets Ref. No. 6 and 8)

Post, etc. 20p.

4-300 4TR 9V 300mW £1.75 PA7 6TR 16V 7W £3.62  
104 4TR 9V 1W £2.12 608 6TR 24V 10W £4.12  
304 4TR 9V 3W £2.47 410 4TR 28V 10W £4.97  
555 6TR 12V 3W £2.15 MPA12/3 6TR 18V 12W £4.50

OPTIONAL POWER SUPPLIES

P500 (1 or 2) for 104, 304 £2.62  
P520 (1 or 2) for PA7 £3.47  
MU24/40 (1 or 2) for MPA12/3 or MPA12/15 £4.50  
P11 for 608 £2.87 P15 for 410 £2.62

### SINCLAIR PROJECT 60 PACKAGE DEALS—SAVE POUNDS!



2x230 amplifier, stereo 60 pre-amp, PZ5 power supply, £16.75, Carr. 40p. Or with PZ6 power supply £18.25. Carr. 40p.  
2x230 amplifier, stereo 60 pre-amp, PZ8 power supply £20.25 Carr. 40p. Transformer for PZ8 £2.45 extra. Any of the above with Active Filter unit add £4.75 or with pair Q16 speakers add £16. Also new FM Tuner £21. 2000 Amplifier £24.50, p.p. 50p. 3000 Amplifier £31.50, p.p. 50p. Also IC12 £2.50.

### LOW COST HI-FI SPEAKERS

E.M.I. Size 13½" x 8½"

TYPE 150 6 watt, 3, 8 or 15

ohms £2.12. Post 22p.

TYPE 150TC Twin cone ver-

sion £2.75. Post 22p.

TYPE 450 10 watt with twin

tweeters and crossover, 3, 8

or 15 ohms. £3.50. Post 25p.

TYPE 350 20 watt with tweeter

and crossover, 8 and 15 ohms.

£7.50. Post 26p.

POLISHED CABINETS

For 150, 150TC and 450 £4.50. Post 30p.


TERRIFIC RANGE OF SPEAKERS, KITS

AND CABINETS IN STOCK—SEE CATA-

LOGUE OR YOUR ENQUIRIES INVITED.



### HI-FI TO SUIT EVERY POCKET

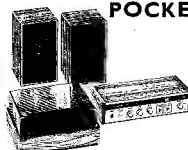

TELETON '206', Garrard  
SP25 Mk.III, Goldring G800  
Series Cart., Plinth/Cover,  
10 watt 3 way bookshelf  
Speaker Systems. All leads  
etc. (Rec. Price £81).

SAVE £59.45 Carr. £2  
£21.55 PLUS FREE STEREO  
HEADPHONES.

TELETON F2000, Med.  
Wave, Stereo FM Tuner  
Amplifier, Garrard 2025TC,  
9TAHC Diam., Plinth/  
Cover, 10 watt Speaker  
Systems as above, all leads  
etc. (Rec. Price £91).

SAVE £64.50 Carr. £2  
£26.50 PLUS FREE STEREO  
HEADPHONES.

THE TWO MOST POPU-  
LAR SYSTEMS EVER—  
PLUS FULL 12 MONTHS'  
GUARANTEE AS WITH  
ALL "HENRY'S" OFFERS!

FREE 12 page Audio-  
Hi Fi Stock and  
Stereo Systems Discounts  
Lists. Save up to 40%!  
Demonstrations and Credit  
Terms (to callers) plus 12  
months' guarantee.

### MONO, STEREO AND MIXING EQUIP- MENT. HIGH QUAL- ITY WITH LOW PRICES.



### SELF POWERED SILICON- FET CONTROL UNITS / PRE- AMPLIFIERS

FET 9/4 Mono or single channel.  
Adjustable levels. All facilities plus  
microphone. Mixing. Price £12.50  
FET 154 Stereo with all facilities,  
magnetic cart. input etc. Price  
£16.50

### SILICON POWER AMPLI- FIERS FOR USE WITH ABOVE

PA 25 25 watts into 8 ohms £7.50  
PA 50 50 watts into 4 ohms £9.50  
MU42 Power Supply for 1 or 2  
PA25's or 1 only PA50 £6.00.  
Post 20p.

FREE BROCHURE NO. 25 ON  
REQUEST.

NO SOLDERING—ALL UNITS  
INTERCONNECTING ON "356"

### BUILD THIS VHF FM TUNER

5 MULLARD TRANSISTORS

300 kc/s BAND-WIDTH.

PRINTED CIRCUIT. HIGH

FIDELITY REPRODUCTION.

MONO AND STEREO.

A popular VHF FM Tuner for

quality and reception of mono

and stereo. There is no doubt

about it—VHF FM gives the

REAL sound. All parts sold

separately.

Free Leaflet No. 3 & 7.

TOTAL £6.97 p.p. 20p. Cabinet 100p. Decoder Kit £5.97

Tuning meter £1.75

Mains unit (optional) Model PS900 £2.47

Mains unit for Tuner and Decoder PS1200 £2.62



### BUILD YOURSELF A QUALITY RADIO

Excellent printed circuit

design with full power

output. Fully tuneable on

both MW/LW bands. 7

Mullard transistors. Fitted

Sin. speaker. Room filling

power. Easy to build with

terrible results. Two colour

leather-cloth cabinet with


silvered front. All local

and continental stations.

Complete detailed instructions.

Total cost £6.98 p.p. 35p. All parts sold separately.

Ask for leaflet No. 1.

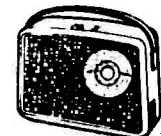

### PUBLIC ADDRESS AND DISCOTHEQUE EQUIPMENT

The largest and most versatile range available—all your requirements for outdoor, indoor, mobile and permanent installations. Sound and lighting supplied. Brochure No. 18 on request or call into "309" and see for yourself. Also Electronic Organs in Kit form—ask for Brochure No. 9.

**Electronic Components,  
Audio and Test Gear Centre**  
356 EDGWARE ROAD,  
LONDON, W.2.  
Tel: 01-402 4736

**High Fidelity Sales &  
Demonstrations Centre**  
354 EDGWARE ROAD,  
LONDON, W.2.  
Tel: 01-402 5854

**Electronic Organs,  
P.A. & Discotheque Centre**  
309 EDGWARE ROAD,  
LONDON, W.2.  
Tel: 01-723 6963

**Mail Orders, Special Bargain  
Shop, Industrial Sales**  
303 EDGWARE ROAD,  
LONDON, W.2.  
Tel: 01-723 1008/9

"354" & "356" OPEN SIX FULL DAYS A WEEK 9 am to 6 pm MONDAY TO SATURDAY

# **Circuit Building Bricks**


# CIRCUIT BUILDING BRICKS

PRESENTED FREE WITH PRACTICAL WIRELESS OCTOBER 1971


COMPLEMENTARY TO A NEW SERIES OF ARTICLES ESPECIALLY WRITTEN FOR THE BEGINNER STARTING IN THE OCTOBER ISSUE OF PRACTICAL WIRELESS.



## BIASING CIRCUITS

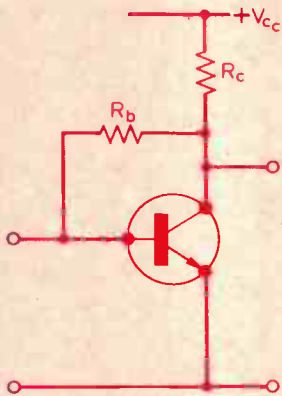


Working out the bias resistors. This circuit is suitable for silicon transistors where  $I_{cbo}$  is usually negligible. Collector voltage is about half the supply voltage  $V_{cc}$ . So  $V_{ce} = V_{cc} - I_c R_c$ . If we know the d.c. current gain ( $h_{FE}$ ), we can work out  $R_b$  as  $h_{FE} R_c$ , choosing the mid-point of the manufacturer's quoted figures. Collector current is approximately emitter current and base current is the voltage dropped across the load resistor, divided by  $R_b + h_{FE} R_c$ .

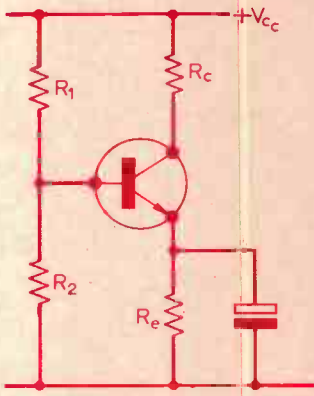

For germanium transistors (with a significant collector/base leakage current) this arrangement may be used. Remember, base-emitter voltage of silicon transistors at low current is 0.7V, but for germanium transistors, 0.1 to 0.2 volts. Here, we can say:

$$V_b = \frac{R_2 V_{cc}}{R_1 + R_2}$$

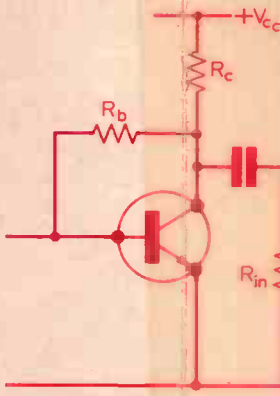
Input impedance is increased by current feedback, via  $R_e$ . Voltage across  $R_e$  is proportional to collector current,  $I_c$ .



Coupling two stages this way makes the input resistance of the second stage effectively the load resistance of the first. The value of coupling capacitor depends on the low frequency response of the amplifier. The base bias resistors are in parallel with the input resistance and with the emitter resistance plus internal emitter resistance of the transistor. Voltage-derived feedback is obtained from  $R_b$ , effectively reducing input impedance.




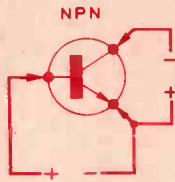P.N.P. transistors shown are relative to P-region, positive emitter (holes in region). Collector is negatively biased, drawing holes from




N.P.N. transistors shown are relative to N-type emitter, negatively biased w.r.t. base, and collector positive. N-type emitter injects free electrons into P-type base.

## RF CIRCUITS

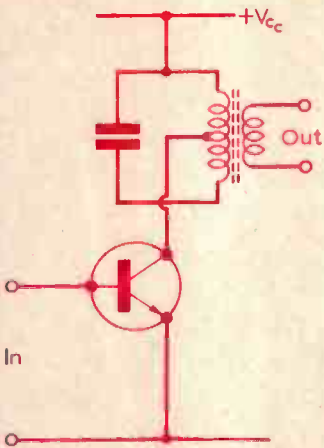


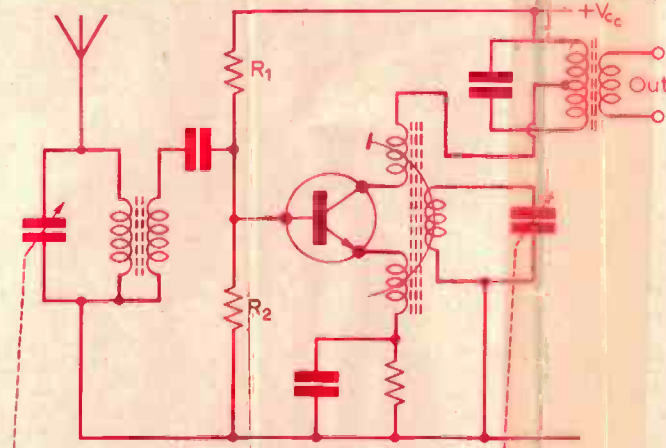Typical circuit of r.f. amplifier, with the collector tapped down the tuned circuit to preserve matching. Bias will be obtained from a.g.c. applied to the input circuit.



A typical self-oscillating mixer circuit. Oscillator feedback for the emitter is taken through low-impedance coils from the collector. The transistor is biased to Class A by  $R_1$ ,  $R_2$ . As oscillation

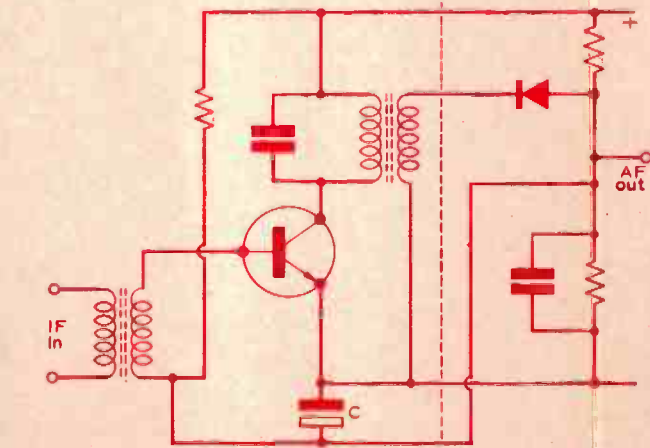risks, rectification of the oscillating signal occurs through the base/emitter diode. Loop gain decreases after each cycle, stabilising the amplitude, causing quiescent emitter current to rise.




A.G.C. is derived from the detector circuit (to the right of the dotted line) and applied to the input of the first i.f. amplifier. A large electrolytic capacitor,  $C$ , is provided to decouple a.f. from the a.g.c. line.

The i.f. transformer may be damped by a diode to improve bandwidth characteristics. The stage shown is for a.m. It is not so necessary to provide a.g.c. for f.m. i.f. stages, where limiting is already applied.

## COMMON TRANSISTOR SYMBOLS A

|           |   |                                                                                   |
|-----------|---|-----------------------------------------------------------------------------------|
| $V_{be}$  | = | Base/emitter voltage                                                              |
| $V_{ce}$  | = | Collector/emitter voltage                                                         |
| $I_b$     | = | Base current                                                                      |
| $I_c$     | = | Collector current                                                                 |
| $\beta$   | = | Collector/base current ratio                                                      |
| $\alpha$  | = | Collector/emitter current ratio                                                   |
| $\alpha'$ | = | $\frac{\alpha}{(1-\alpha)}$ $\left[ \alpha = \frac{\alpha'}{(1+\alpha')} \right]$ |
| $V_{CBO}$ | = | Max. collector/base voltage                                                       |
| $V_{CEO}$ | = | Max. collector/emitter voltage                                                    |
| $V_{EBO}$ | = | Max. emitter/base voltage                                                         |
| $I_{CM}$  | = | Max. peak collector current                                                       |
| $I_{CBO}$ | = | Max. collector/base reverse current                                               |
| $I_{EBO}$ | = | Max. emitter/base reverse current                                                 |

## MULTIVIBRATORS

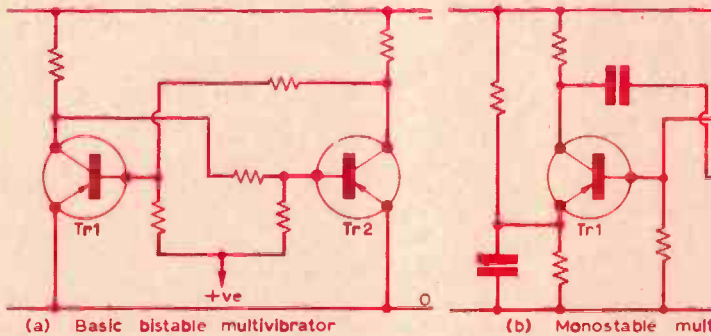

Three types of transistor switched device are in common use as pulse generators. When a transistor remains in a given state until compelled to change by an external 'trigger' signal, it is termed 'stable'. If, when placed in this state, it then reverts, after a while, to its former state without further external stimulus, it is termed 'unstable'.

Another class of circuit is free-running; that is, it does not stay in either state but automatically switches between 'bistable' when an external trigger pulse is needed to switch it and 'monostable' when it always reverts to its former state after triggering.

This type is called 'astable'. The astable circuit switches at a frequency determined by the circuit time constants. It can be synchronised by an external signal. The multivibrator can be made monostable, bistable or astable by alteration of bias conditions.


In (a) the basic bistable circuit is given. When one transistor is conducting, its collector potential causes the other to be cut off. An external signal causes a change in state. A second external signal causes the circuit to revert to the first state. A recurrent triggering signal will cause a rect-




transistor. Polarities are relative to emitter. In a p-n-p transistor, the p-region is forward-biased, the n-region is reverse-biased, and the collector is reverse-biased.

transistor. Polarities are relative to emitter. In a p-n-p transistor, the p-region is forward-biased, the n-region is reverse-biased, and the collector is reverse-biased.


emitter

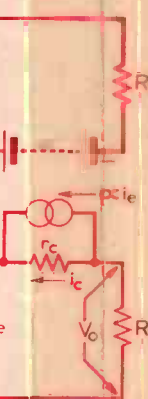

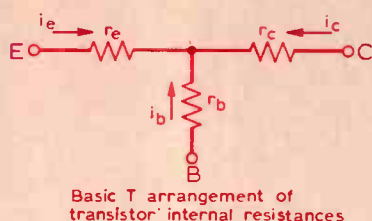
High (50)  
Medium (1kΩ)  
Medium (40kΩ)  
High (about 250)



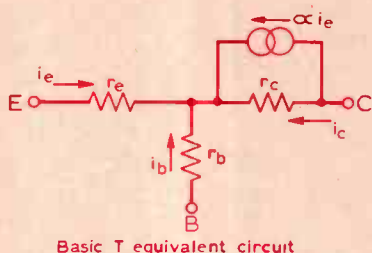Basic T arrangement of transistor internal resistances




Basic T equivalent circuit

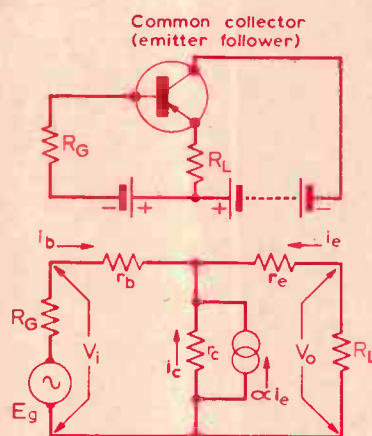

Current Gain High (50)  
Input Resistance High (100kΩ)  
Output Resistance Low (1kΩ)  
Voltage Gain Unity

## AND ABBREVIATIONS

|               |                                                              |
|---------------|--------------------------------------------------------------|
| $V_{CE(sus)}$ | = Collector/emitter sustaining voltage                       |
| $V_{CE(sat)}$ | = Collector/emitter saturation voltage                       |
| $h_{FE}$      | = D.C. current gain                                          |
| $h_{ie}$      | = Forward current gain, common emitter, output shorted       |
| $h_{re}$      | = Reverse voltage feedback ratio, common emitter, input open |
| $h_{ic}$      | = Input resistance, common emitter, output shorted           |
| $h_{oc}$      | = Output admittance, common emitter, input open              |
| $I_{co}$      | = Collector leakage current (grounded emitter)               |
| $I_{c0}$      | = Collector leakage current (grounded base)                  |

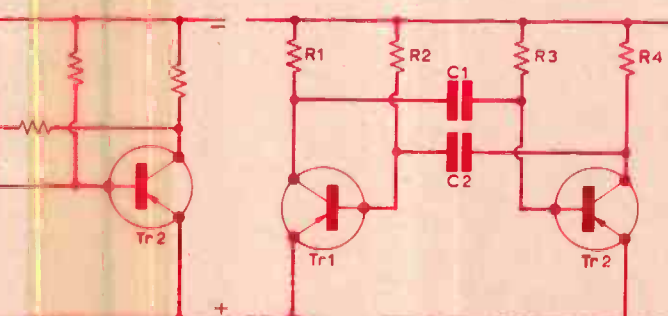

multivibrator


angular voltage waveform to appear at each collector, at half the frequency of the triggering signal.

In (b) is shown the monostable multivibrator circuit, similar to the bistable, except for a change of bias and a capacitor coupling. In the stable state, Tr1 is off and Tr2 on; in its unstable state, Tr2 is off and Tr1 on. The duration of the unstable state is the time the base potential of the non-conductive transistor takes to fall to zero.

If both the inter-stage couplings are made capacitive, an astable multivibrator is obtained. In (c) there is no

emitter bias, both bases returned via resistors to the supply line. If  $R_1=R_2=R_3$ , and  $C_1=C_2$ , the multivibrator is symmetrical. As a result, a square waveform should be produced, at both collectors, with a periodicity  $T=1.38RC$ . The free-running frequency is the reciprocal of  $T$ , i.e.  $\frac{1}{1.38RC}$ . An example of this type of circuit used as an oscillator in a 405-line television receiver, free-running frequency 7.5kHz, triggered frequency 10-125kHz, would have  $R_1$  and  $R_4$ , 3kΩ;  $R_2$  and  $R_3$ , 100kΩ;  $C_1$  and  $C_2$  0.001μF. A number of transistors will perform adequately in this kind of circuit.

## DC CONDITIONS

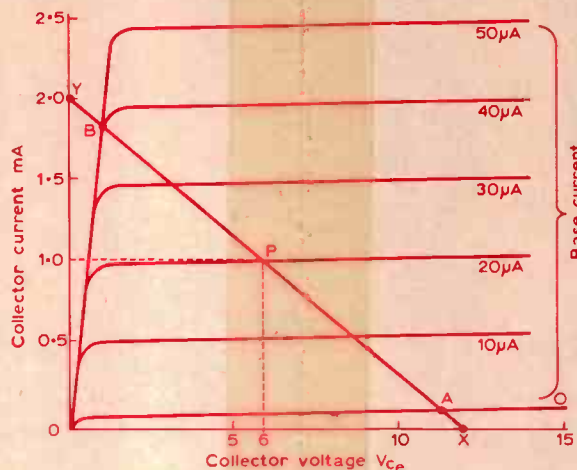


Choosing the right transistor is made easier by reference to its operating conditions. This is a series of curves for different base currents, with collector current plotted against collector voltage. Joining the supply line voltage to the saturation current (quoted in maker's literature) produces a 'load line'. Choose a point midway along this—P in the diagram. Then, in the example, a base current of 20 microamps is required for a collector current of 1mA and a collector voltage of 6 volts. Multiplying the base current for d.c. conditions by the current gain of the transistor gives the required value of collector current.


The potentiometer,  $R_1$ ,  $R_2$ , across the supply, provides a tapping point for base control voltage. A bit more bias can be provided by the negative feedback of  $R_e$ , in series with the emitter. Ideally,  $R_1$  and  $R_2$  should be as low as possible, but this

imposes a drain on the supply, so a compromise solution is reached. For a typical stage with a supply voltage of 6V, the values of  $R_1$  and  $R_2$  would be 23kΩ and 5kΩ respectively (for a transistor with a current gain of about 50) and  $R_e$  would be around 1kΩ. Choice of values is partly determined by the transistor, partly by the power supply.  $R_1$ ,  $R_2$  must provide a bleed current about ten times that of the base current, but about a fifth of

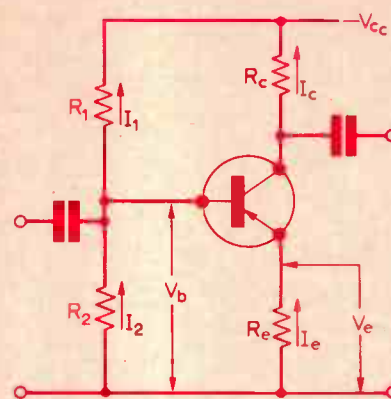the collector current. Silicon transistors, with little collector leakage current and a higher 'starting' voltage, will have higher values of  $R_e$ . For a typical stage with a supply of 7 volts (positive, this time, for the n.p.n. transistor),  $R_1$  and  $R_2$  would both be 15kΩ.  $R_e$  might be 2.7kΩ for a transistor with an  $h_{FE}$  of 100 (50-150) using an emitter current of 1mA.




## AF CIRCUITS

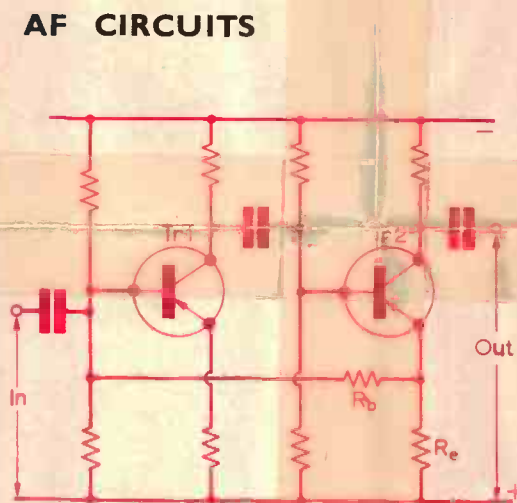


The basis of much simple audio design—a two-stage current amplifier. The current amplifier gives a current output for a voltage input and has a low input resistance and a high output resistance. D.C. stabilisation is included as before and feedback is obtained by  $R_b$  from the emitter of Tr2 to the base of Tr1. Overall current gain can be given by  $R_b/R_e$  and is independent of transistor parameters. The emitter of

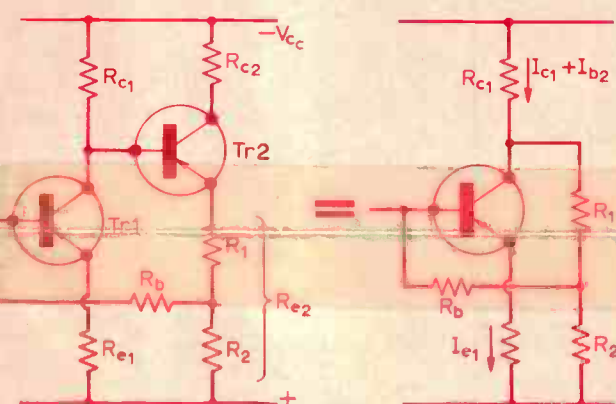Tr1 is decoupled for a.c. negative feedback—i.e., the feedback is frequency-dependent. For a voltage amplifier (high input resistance, low output resistance), it is more usual for the feedback  $R_b$  to be taken from the collector of Tr2 to the emitter of Tr1. The emitter of Tr2 is decoupled and overall voltage gain is again  $R_b/R_e$ , but this time  $R_e$  is the emitter resistor of Tr1.



Direct coupling of the two-stage amplifier saves components by stabilisation of Tr1 by Tr2. A circuit equivalent shows the way this system operates, with the 'collector' current the sum of Tr1 collector current and Tr2 base current. Bias stability is superior to the previously described two-stage circuit. In a typical pre-amplifier using silicon n.p.n. transistors, such as the BC109 or

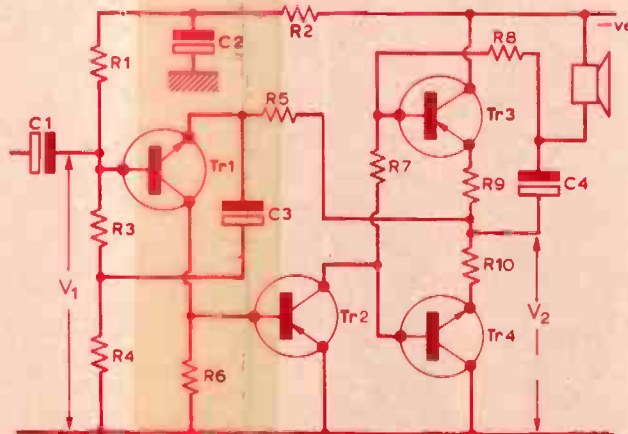BC108 as Tr1 and Tr2, with a supply voltage of 20 volts, the only practical modification would be a further stage of decoupling between the supply to Tr1 and the main supply, which would be positive. This might consist of a 100kΩ resistor with a 2.5μF electrolytic to chassis. Then  $R_{c1}$  would be 100kΩ;  $R_{e1}$ , 680Ω;  $R_{c2}$ , 12kΩ;  $R_{e2}$ , 560Ω and  $R_b$ , 220kΩ.



The basic complementary push-pull circuit has the signal from the driver transistor Tr2 simultaneously driving the bases of a pair of transistors, one of which is p.n.p. and the other, n.p.n. These conduct during alternate half-cycles of signal. Tr1 is a pre-amplifier and a difference-amplifier to compare the voltages of input and output.

The quiescent bias voltage for the output transistors is developed across  $R_7$ . Bias is set for a linear combined transfer characteristic, to reduce crossover distortion. In practice, compensation for temperature changes would be made by fitting a thermistor across  $R_7$ , and for supply changes by the use of diodes in this part of the circuit.