

FOR THE RADIO ENTHUSIAST...


NOVEMBER 1980

Practical Wireless

Australia \$1.15
New Zealand \$1.25
Malaysia \$4.00

65p

FREE

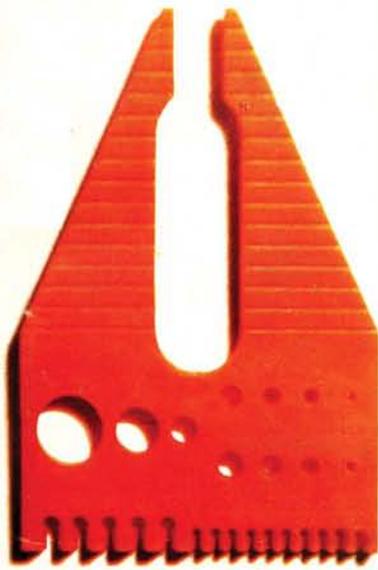

LEAD BENDING GAUGE

SURVEY OF 2m
MULTI-MODES


'SLIM JIM'
FOR 28MHz

AND
FEATURING



HELFORD

PART 1

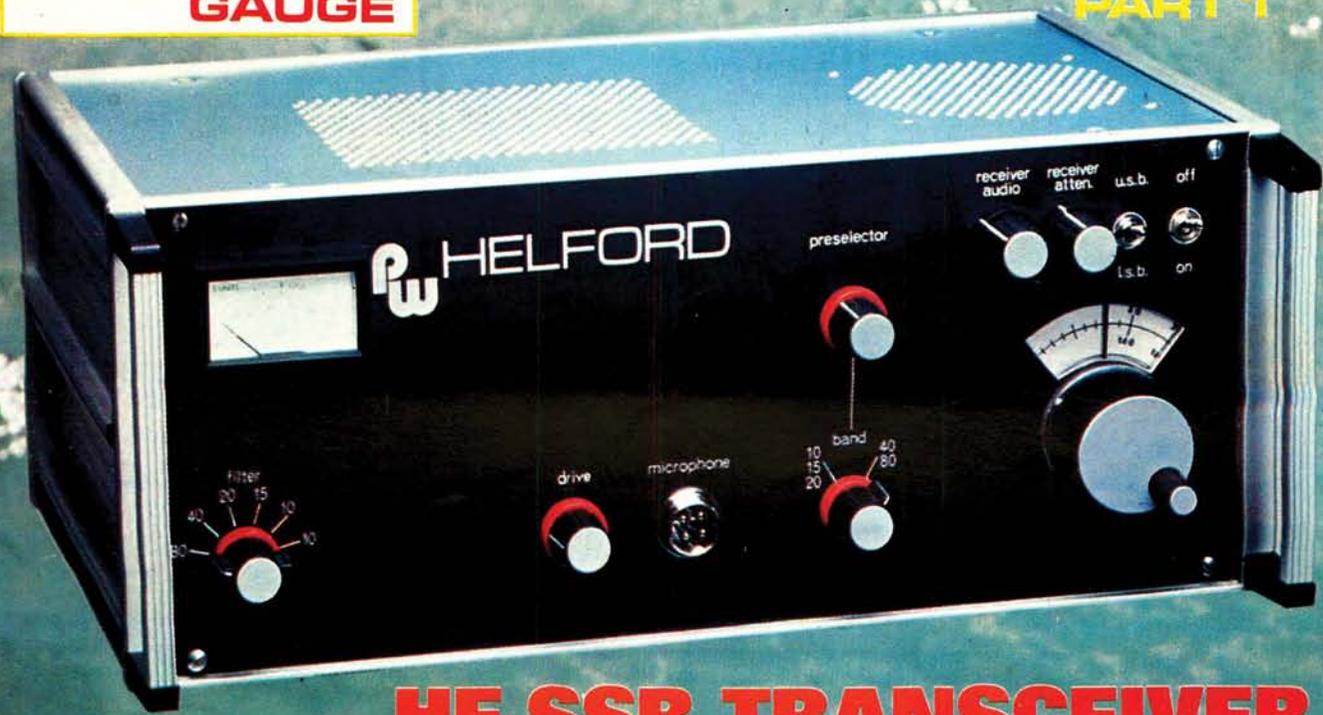

HF SSB TRANSCEIVER

CONTACT BREDHURST
FOR NEWS OF THE FRG 7700
THE LATEST H.F. RECEIVER
FROM YAESU.

Bredhurst electronics

HIGH ST., HANDCROSS, W. SUSSEX O444 400786

MULTIMODES - MULTICHOICE

YAESU FT 480R

£359, inc. VAT & CARRIAGE



TRIO TR9000

£345, inc. VAT & CARRIAGE



ICOM IC 260E

£339, inc. VAT & CARRIAGE



FDK MULTI 750E

£299, inc. VAT & CARRIAGE



"A handy talkie"
"A pocket portable"



IC 2E £159

inc. VAT & CARRIAGE



- Fully synthesized - covering 144-145.995 in 5KHz steps.
- 1.5W power output with 9V battery as supplied.
- Optional 6V or 12V packs for lower or higher power.
- BNC antenna output socket for helical or external antenna.
- Weight - only 450 grams, with supplied battery pack and helical.
- Send/battery indicator - indicates transmit until time for battery recharge.
- Duplex/Simplex switch - Hi/Low power switch.
- Optional external speaker microphone available now.
- Full 12 months guarantee for all rigs bought from Bredhurst Electronics.

H.F. TRANSCEIVERS	
TRIO TS120V	£347.00
TRIO TS120S	£432.00
TRIO TS205E	£437.00
YAESU FT707	£500.00
YAESU FT101Z	£488.00
YAESU FT101ZD	£569.00
TRIO TS180S (with DFC)	£679.00
YAESU FT107M	£690.00
Z.M. MOBILES	
FDK Multi 700EX	£199.00
STANDARD C8800	£250.00
ICOM IC255E	£255.00
TRIO TR7800	£265.00
HANDHELDS	
FDK PALM II	£99.00
YAESU FT302I	£99.00
FDK PALMSIZER	£149.00
ICOM IC2E	£159.00
FDK PALM IV	£159.00
AOR AR240A	£165.00
TRIO TR2300	£166.00
YAESU FT207R	£199.00
TRIO TR2400	£210.00
Z.M. MULTIMODES	
FDK MULTI 750E	£299.00
ICOM IC260E	£339.00
TRIO TR9000	£345.00
YAESU FT480	£359.00
ICOM IC251E	£479.00

H.F. RECEIVERS	
LOWE SRX30	£158.00
YAESU FRG7	£199.00
TRIO R1000	£298.00
YAESU FRG7000	£299.00
Z.M. F.M.	
SEARCH 9	£45.00
A.O.R. AR22	£83.00
FDK TM56B	£75.00
BEARCAT 220FB	£258.00
MARINE V.H.F.	
SEARCH 9	£45.00
S.R.11 (+ scan)	£59.00
FDK TM56B	£75.00
BEARCAT 220FB	£258.00
AIRBAND	
WALTHAM W144	£29.95
R517	£49.95
AP12	£120.00
BEARCAT 220FB	£258.00

ACCESSORIES	
KEYERS HK707 (Up/down)	£10.50 (€0.50)
KEYERS HK704 (Squeeze)	£14.50 (€0.50)
KEYERS EK150 (Semi/fully auto with monitor) 240V/12V	£74.00 (—)
HELICAL BNC - 2 metres	£4.50 (€0.25)
HELICAL PL259 - 2 metres	£4.50 (€0.25)
DUMMY LOAD DL20	£6.00 (€0.30)
DUMMY LOAD T80	£21.95 (€0.75)
DUMMY LOAD T100	£22.95 (€0.75)
DUMMY LOAD T150	£32.00 (€0.75)
DUMMY LOAD T200	£34.00 (€0.75)
MOBILE SPEAKERS YAESU 8 ohm 6W	£9.95 (€0.75)
POWER SUPPLIES 13.8V 4A	£22.95 (€1.00)
POWER SUPPLIES 13.8V 6A	£29.95 (€1.50)
POWER SUPPLIES 13.8V 25A	£92.00 (€2.00)
MICROPHONES, ADONIS desk compressor	£39.95 (—)
desk compressor	£59.95 (—)
MICROPHONES, YAESU YD148 dual imp.	£20.95 (€0.75)
WORLD CLOCK QTR24	£18.40 (€0.75)
WORLD CLOCK QTR24D (Quartz)	£24.50 (€0.75)
LOW PASS FILTERS TRIO LF30A	£18.40 (€0.75)
LOW PASS FILTER YAESU FF501DX	£19.95 (€0.75)
LISTENERS A.T.U. MIZUHO KX2	£29.95 (€0.75)
AUDIO PROCESSOR MIZUHO AP-MI	£33.00 (€0.75)
DIP METER TRIO DM-800	£51.00 (€0.75)
WAVE METER FX1	£28.00 (€0.75)
SWR25	£13.00 (€0.50)
SWR110	£35.00 (€0.50)
SWR CN620 (2M)	£52.00 (€0.50)
SWR CN630 (70cm)	£71.00 (€0.50)
7 MHz TRAPS	£6.95 (€0.50)
FERRITE RINGS 2 OFF	£0.80 (€0.20)

"SAFETY"

KEEP BOTH HANDS ON THE WHEEL
USING THE LATEST IN MOBILE MICROPHONES

These consist of a high quality condenser microphone used in conjunction with an F.E.T. preamplifier with approx. 12dB gain. Fix the boom microphone to a convenient point such as the sun visor. Position the amplifier and TX/RX switch on the gear lever. Connect the mic plug and power lead and its ready for use.

MM202S £20.95 inc. VAT (carriage 50p)
MM202H - Head hand £28.00 inc. VAT (carriage 50p)

TRY OUR
MAIL ORDER
SERVICE

VISIT OUR
RETAIL PREMISES
MON-SAT 9-5.30

BUDGET ACCOUNT - ACCESS - BARCLAYCARD - PART EXCHANGE

MID SUSSEX HOUSE · HIGH ST. · HANDCROSS · WEST SUSSEX RH17 6BW

MAIL ORDER

TEL: 0444 400786 9am-5.30pm

RETAIL CALLERS

TO ORDER ANY OF THE ABOVE ITEMS SIMPLY WRITE, ENCLOSING A CHEQUE OR PHONE YOUR CREDIT CARD NUMBER

EDITORIAL OFFICES
Practical Wireless
Westover House
West Quay Road
Poole, Dorset BH15 1JG
☎ Poole 71191

Geoff Arnold G3GSR
Editor

Dick Ganderton C.Eng., MIERE, G8V FH
Assistant Editor

Peter Metalli
Art Editor

John Fell G8MCP
Technical Editor

Alan Martin G8ZPW
News & Production Editor

Elaine Howard
Technical Sub-Editor

Rob Mackie
Technical Artist

Keith Woodruff
Assistant Art Editor

Sylvia Barrett, Sharron Breeze
Secretarial

ADVERTISEMENT OFFICES
Practical Wireless
King's Reach Tower
Stamford Street
London SE1 9LS
Telex: 915748 MAGDIV-G

Dennis Brough
Advertisement Manager
☎ 01-261 6636

Roger Hall G8TNT (Sam)
Ad. Sales Executive
☎ 01-261 6807

Claire Gerrish
Secretary
☎ 01-261 6636

Colin R. Brown
Classified Advertisements
☎ 01-261 5762

Dave Kerindi
Make-up & Copy
☎ 01-261 6570

COPYRIGHT

© IPC Magazines Limited 1980. Copyright in all drawings, photographs and articles published in *Practical Wireless* is fully protected and reproduction or imitation in whole or in part is expressly forbidden. All reasonable precautions are taken by *Practical Wireless* to ensure that the advice and data given to our readers are reliable. We cannot however guarantee it and we cannot accept legal responsibility for it. Prices are those current as we go to press.


Practical Wireless

NOVEMBER 1980 VOL. 56 NO. 10 ISSUE 884


contents

- 22 **Linear Scale Resistance Meter**
R. A. Penfold
- 27 **Introducing RTTY—3**
Jeff Maynard G4EJA
- 32 **Model Radio Control—8 Field Test Set**
J. Burchell & W. S. Poel
- 36 **PW Survey**
2m Mobile Multi-mode Transceivers
- 41 **Slim Jim for 28MHz**
Fred Judd G2BCX
- 43 **PW "Helford" HF SSB Transceiver—1**
Vic Goom G4AMW
- 52 **PW "Sherborne" Synthesised Tuner—2**
W. S. Poel
- 64 **PW "Nimbus" Follow-up**
M. Tooley G8CKT & D. Whitfield G8FTB
- 67 **Air Test**
MML432/50 Linear. AR-22 Monitor
- 69 **IC of the Month—SG3524**
Brian Dance
- 72 **Our Gift**
Lead Bending Gauge
- 104 **Advert Index**
- 67 **Air Test**
- 19 **Comment**
- 69 **IC of the Month**
- 65 **Mods**
- 20 **News**
- 51 **Next Month**
- 75 **On the Air**
- 63 **Out of Thin Air**
- 21 **Production Lines**
- 78 **RAE Reprint**
- 19 **Services**

Pure ind

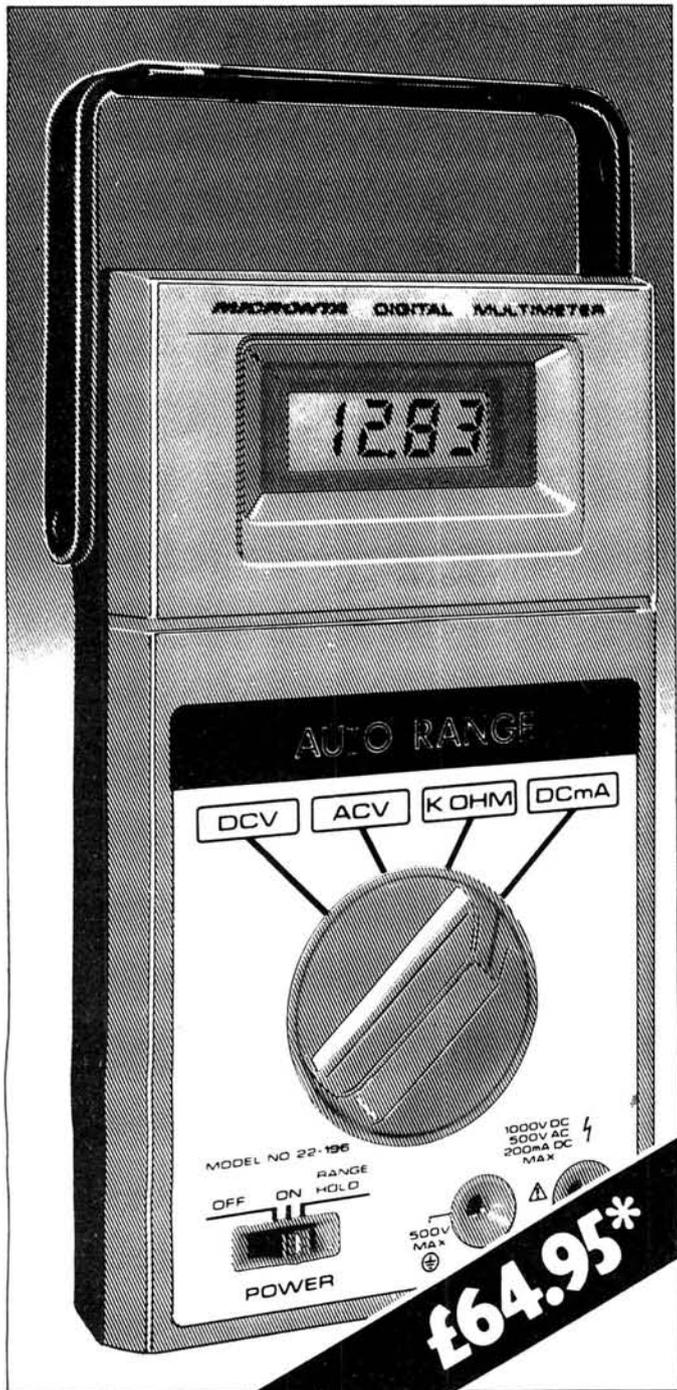

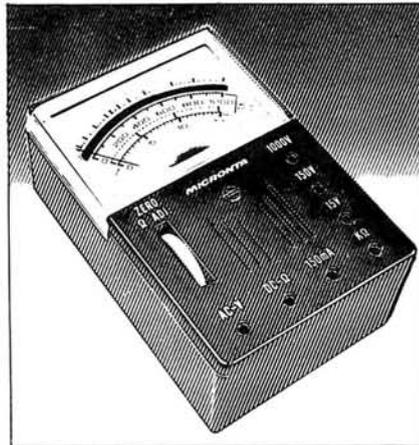
Micronta Auto Range Multimeter Gives you correct polarity, range and measurement — every time. Single function switch lets you choose DC 4 ranges; AC 4 ranges; DC current resistance. 4 ranges. LCD readout. Exclusive range hold facility. 22-196



Micronta 1000 Ohms/Volt Multitester Very compact at 89 x 59 x 32 mm. Easy to read colour meter, pin jacks for all 8 ranges. Reads AC V, DC current and ohms. Mirrored scale. 20-027



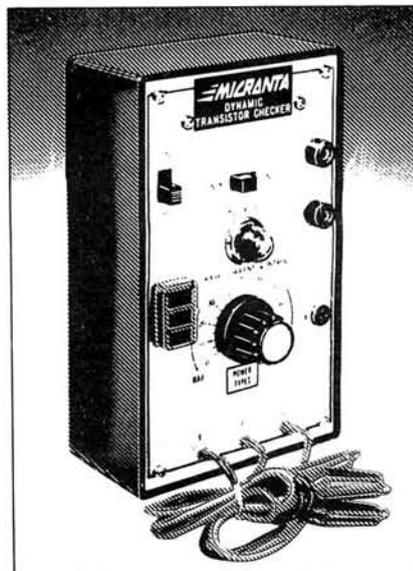Micronta Transistorized Signal Tracer Spot circuit troubles, check RF, IF and audio signals from aerial to speaker on all audio equipment. It has built in 5 cm speaker with volume control. 50 x 143 x 38 mm. 22-010





Micronta Dynamic Transistor Checker Shows current gain and electrode open and short circuit. Tests low medium or high power PNP or NPN types. Go/no-go tests from 5-50 mA on power types. "Quick-check" sockets. 22-024

Wigence.

Realistic Direct Entry Programmable Scanning Receiver Hear real-life drama on six exciting bands. With direct access to all frequencies, you can punch in actual frequencies for monitoring, storing in the computer's memory or just exploring. Big fluorescent display. Phase locked loop security. 20-9111

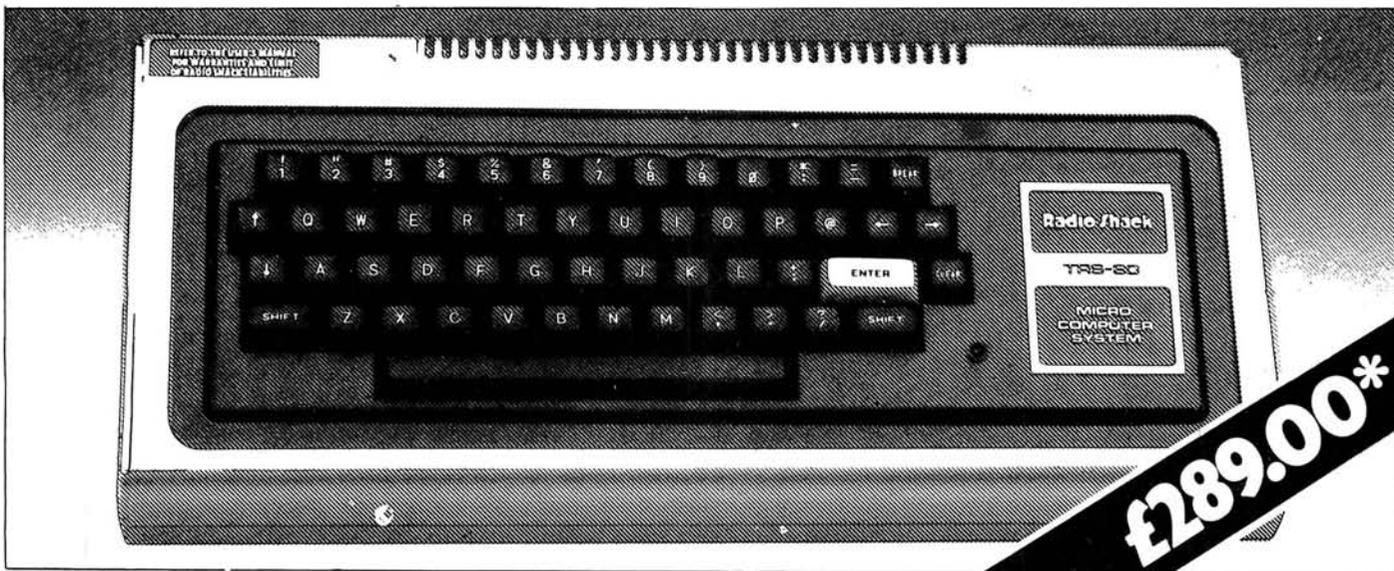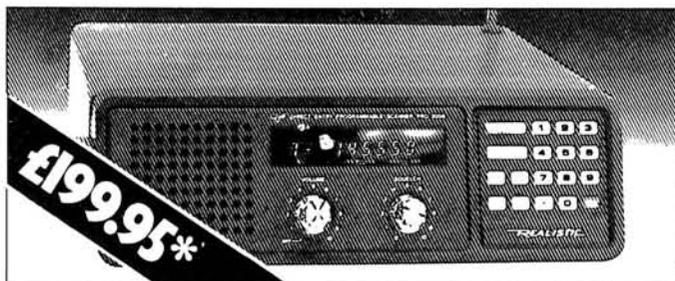TRS-80 Model I C.P.U.'s Ready to run from your TV monitor. Plug in and start computing. Contains 4096 bytes of user memory and can be expanded to 16K. 26-9051



- | | | | | | | | |
|---|---|---|--|--|--|---|--|
| <p>ACCRINGTON
37 Union Street</p> <p>ALDRIDGE
2268 Coventry Road</p> <p>BARNESLEY
55 Market Street</p> <p>BASINGSTOKE
22 London Street</p> <p>BIRKENHEAD
Kwik Save Centre, Prenton</p> <p>BRADFORD COMPUTER CENTRE
2/4, Forster Square</p> <p>BIRMINGHAM AREA</p> <p>BULL RING
528 Bridge Link Shopping Centre</p> <p>CAPE HILL
44-46, Cape Hill</p> <p>CORPORATION STREET
80, Corporation Street</p> <p>DALE END
57-58, Dale End</p> <p>EDGBASTON COMPUTER CENTRE
Edgbaston Shopping Centre</p> <p>ERDINGTON
218 High Street</p> <p>HALESOWEN
5-7, Queensway</p> <p>NORTHFIELD
749 Bristol Road South</p> | <p>PERRY BARR
20 Lynton Square</p> <p>SHELDON
6/8 St. John Street</p> <p>BROMSGROVE
6/8 St. John Street</p> <p>BROWNHILLS
60 High Street</p> <p>BURY (Lancs)
91, The Rock</p> <p>CARDIFF
9 Wood Street</p> <p>CHELTENHAM
31 Cambray Place</p> <p>CHESTER
Kwik Save Centre</p> <p>COVENTRY
Sealand Road</p> <p>BOURNEMOUTH
132/4 Commercial Road</p> <p>BRADFORD
9 Petergate</p> <p>BRIGHTON
70 London Road</p> <p>BRISTOL AREA</p> <p>BISHOPSTON
13 Gloucester Road</p> <p>BRISTOL COMPUTER CENTRE
Colston Centre</p> <p>CLIFTON
146 Whiteslades Road</p> <p>DOWNE
5 Badminton Road</p> <p>KNOWLE
Broadwalk Shopping Centre</p> <p>YATE
4 North Parade</p> | <p>HUDDERSFIELD
Packhorse Shopping Centre</p> <p>HULL
Status City, Clough Road</p> <p>LEAMINGTON SPA
53 Warwick Street</p> <p>LEEDS
72 Merrion Centre</p> <p>LEEDS
3 Eastgate</p> <p>LEICESTER
Market Street</p> <p>LETCHEWORTH
25 Commerce Way</p> <p>LINGOLN
High Street</p> <p>LIVERPOOL AREA</p> <p>ALLERTON
90 Allerton Road</p> <p>BOOTLE
New Strand Precinct</p> <p>OLD SWAN
649 Prescott Road</p> <p>ST. JOHNS PRECINCT
168 Market Way</p> <p>LONDON AREA</p> <p>BARKING
8-10 North Street</p> <p>BAYSWATER
The Colonades, Rochester Road</p> | <p>BECKENHAM
144 High Street</p> <p>CATFORD
23 Catford Broadway</p> <p>CHESHUNT
92 Turners Hill</p> <p>CHINGFORD
3 Hall Lane</p> <p>CLAPHAM
84 Clapham High Street</p> <p>COLLIER ROW
27 Collier Row</p> <p>CROUCH END
42 The Broadway</p> <p>DAGENHAM
297 Heathway</p> <p>EDGWARE
128 Burnt Oak</p> <p>EDMONTON
23 North Mall</p> <p>ENFIELD
10 Colman Parade</p> <p>HAMMERSMITH
142-4 King Street</p> <p>HENDON
24 Sentinel Square</p> <p>CEPPINGTON
5 The Walnuts</p> <p>PALMERS GREEN
375 Green Lanes</p> <p>ROMFORD
27 Collier Row Road</p> <p>SEACOLL LANE
1, 2, Seacoll Lane</p> | <p>STREATHAM
254 Streatham High Road</p> <p>TOTTENHAM
455 High Road</p> <p>WALTHAMSTOW
123 High Street</p> <p>WALWORTH
239 Walworth Road</p> <p>WANDSWORTH
107 9 High Street</p> <p>WELLING
7 Embassy Court</p> <p>WIMBLEDON
124 6 The Broadway</p> <p>LUTON
157 Dunstable Road</p> <p>MANCHESTER AREA</p> <p>ARNDALE
Unit 71, Arndale Centre</p> <p>BRAMHALL
14, 15 The Centre</p> <p>CHADERTON
67 High Street</p> <p>CHADDLE
67 High Street</p> <p>DEANSGATE COMPUTER CENTRE
36 Market Place</p> <p>HYDE
4 8 The Mall</p> <p>RADCLIFFE
25 Blackburn Street</p> <p>SALE
The Mall</p> | <p>CITY CENTRE
Arndale Centre</p> <p>STRETFORD
Arndale Centre</p> <p>NEWBURY
14 Bartholomew Street</p> <p>NORTHAMPTON
Weston Favel Shopping Centre</p> <p>NOTTINGHAM AREA</p> <p>ARNOLD
126 8 Front Street</p> <p>BESTON
30 The Square</p> <p>NUNEATON
1 Church Street</p> <p>OXFORD
9-10 St. Clements</p> <p>PAIGNTON
35 Hyde Road</p> <p>PLYMOUTH
64 Royal Parade</p> <p>PORT TALBOT
Aberystwyth Centre</p> <p>READING
18 The Butts Shopping Centre</p> <p>RUGBY
25 Church Street</p> <p>RUNCORN
120 Runcorn Shopping City</p> <p>SCUNTHORPE
140 High Street</p> | <p>SHREWSBURY
20 Shop Latch</p> <p>SITTINGBOURNE
20 The Forum Shopping Centre</p> <p>SLOUGH
253 High Street</p> <p>SOUTHAMPTON
East St. Centre</p> <p>STAFFORD
6 Sheridan Shopping Centre</p> <p>ST. HELENS
Fingerpost Centre</p> <p>STOKE-ON-TRENT
Hanley 16 Charles Street</p> <p>SUNDERLAND
4 Fawcett Street</p> <p>SURREY
206 High Street</p> <p>SUTTON (Surrey)
206 High Street</p> <p>TORQUAY
134 Union Street</p> | <p>TYNE AND WEAR AREA</p> <p>NEWGATE
23 Newgate Centre</p> <p>SHEFFIELD
19-20, Hillsborough Shopping Centre</p> <p>SHIELDS ROAD
184-6 Shields Road</p> <p>WASHINGTON NEW TOWN
Galleries</p> <p>SHOPPING CENTRE</p> <p>WAKEFIELD
Kirkgate Shopping Centre</p> <p>WALSALL
74 Bradford Street</p> <p>WALLASEY
The Precinct</p> <p>WORCESTER
8 St. Nicholas Street</p> <p>WORKSOP
7-9 Bridge Place</p> <p>YORK
5 Church Street</p> |
|---|---|---|--|--|--|---|--|

Offers subject to availability. Instant credit available in most cases. Prices may vary in individual stores. Access Barclaycard and Trustcard welcome. Most items also available at Tandy Dealers. Look for this sign in your area.



*All prices include VAT.

IT'S POSSIBLE, ONLY AT Tandy
Better Equipment. Lower Prices. No Middlemen.

2 SUPERB NEW KITS!

£2 OFF SPECIAL OFFER



1st
Top of all systems tested by independent national authority July '79

C300/ES200

high performance electronic ignition, to add power, economy, reliability, sustained smooth peak performance, instant all weather starting, to your car.

Surefire has sold in its thousands in ready made form from big name accessory firms, but it is now available in quality kit form to fit all vehicles with coil ignition up to 8 cylinders.

ES200. A high performance inductive discharge ignition incorporating a power integrated circuit (special selection); electronic variable dwell circuit (maximises spark energy at all speeds); pulse processor (overcomes contact breaker problems). Coil governor (protects coil). Long burn output. Negative earth only. Compatible with all rev. counters.

C300. In it's ready built form (C3000) it came top of all systems tested by an independent national authority July '79. A high energy capacitive discharge ignition incorporating a high output short circuit proof inverter, top grade Swedish output capacitor, pulse processor circuit, transient overload protection. Fast rise bidirectional output ideal for fuel injection, sports carburation, oily engines. Compatible with most rev. counters. (Low cost adaptors available for rare cases. Application list enclosed with each kit. Note: Vehicles with Smiths/Jaeger rev. counters code RVI on dial will require adaptor type TCI).

What's in the kits. Surefire's own precision anodised aluminium extruded case. P.C. mounted security changeover switch, static timing light. Special selection Motorola semi-conductors. Capacitors, resistors etc. selected after 5 years experience. Glass fibre pcb, solder, complete down to last washer. Fully illustrated comprehensive instructions and full technical back up service.

SUREFIRE ELECTRONIC IGNITION

Suretron Systems (UK) Ltd. Dept. PW5
Bayer Buildings, Lower Bristol Road, Bath BA2 3EF.
Tel: Bath (0225) 332317

Name: _____
Address: _____

	Quantity required		
ES200: Neg	1	£13.95	£11.95
C300: Pos	1	£17.95	£15.95
C300: Neg	1	£17.95	£15.95
Tacho Adapt. TCI	1	£3.90	

Enclose chq/PO's
£ Chq No



Wilmslow Audio

THE firm for speakers!

SEND 50p FOR THE WORLD'S BEST CATALOGUE OF SPEAKERS, DRIVE UNITS, KITS, CROSSOVERS ETC. AND DISCOUNT PRICE LIST.

- AUDAX ● AUDIOMASTER ● BAKER ●
- BOWER & WILKINS ● CASTLE ● CELESTION ●
- CHARTWELL ● COLES ● DALESFORD ●
- DECCA ● EAGLE ● ELAC ● EMI ● FANE ●
- GAUSS ● GOODMAN'S ● HARBETH ●
- ISOPHON ● I.M.F. ● JORDAN ● JORDAN
- WATTS ● KEF ● LOWTHER ● MCKENZIE ●
- MISSION ● MONITOR AUDIO ● MOTOROLA ●
- PEERLESS ● RADFORD ● RAM ● ROGERS ●
- RICHARD ALLAN ● SEAS ● SHACKMAN ● STAG ●
- TANNOY ● VIDEOTONE ● WHARFEDALE ●

WILMSLOW AUDIO (Dept. P.W.)
SWAN WORKS, BANK SQUARE, WILMSLOW,
CHESHIRE SK9 1HF

Tel: 0625 529599
FOR MAIL ORDER & EXPORT OF DRIVE UNITS, KITS ETC.
Tel: 0625 526213
(SWIFT OF WILMSLOW) FOR HI-FI & COMPLETE SPEAKERS

DON'T BUY A QUARTZ WATCH

Until you have seen our incredible new collection of probably THE MOST TECHNICALLY ADVANCED WATCHES IN THE WORLD!

So you thought there was nothing else they could possibly incorporate in an electronic watch? You will be absolutely amazed at all the desirable features packed into these incredible watches.

At the time of going to press these watches have not been officially released so we cannot reveal the name of this world famous manufacturer or publish full specifications, but to whet your appetite we can tell you that they all have: AN ALARM, AN HOURLY TIME SIGNAL, A COUNTDOWN ALARM TIMER AND A FULL STOPWATCH FUNCTION plus many other unique features.



How about a 100 metre water resistant watch you can swim in - from around £20? How about a built-in orchestra playing a selection of tunes - and three date memories? How about our incredible LCD ANALOGUE watch with much much more? Probably THE ULTIMATE WATCH.


SEND A 12p STAMP FOR FULL DETAILS TODAY - AND START SAVING!

As soon as these watches are released we will send you full details. Please ORDER QUICKLY - demand will far exceed supply this year. Don't risk disappointment.

We also have the SEIKO DUO DISPLAY WATCH from £59.95 and two Seiko 100 m water resistant alarm chronographs - one solar powered.

TEMPUS Tempus (Dept. PW)
FREEPOST, 164-167 East Road
Cambridge CB1 1BR. Tel. 0223 312866

be complete with ANTEX

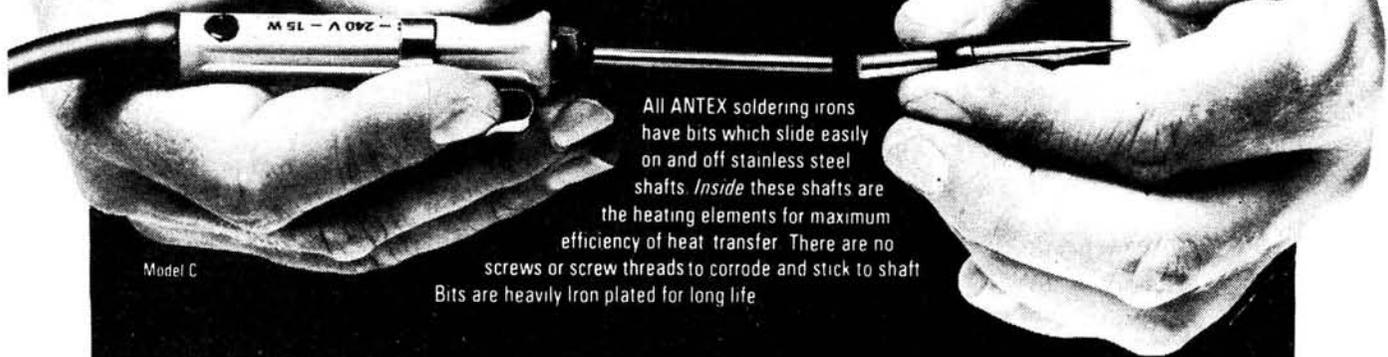

Model C

All ANTEX soldering irons have bits which slide easily on and off stainless steel shafts. Inside these shafts are the heating elements for maximum efficiency of heat transfer. There are no screws or screw threads to corrode and stick to shaft. Bits are heavily Iron plated for long life.

- * Model C Miniature — 15 Watts Price £4.20
- * Model CX — 17 Watts Price £4.40
- * Model X25 — 25 Watts Price £4.40
- * S.T. 3 Stand to fit all irons Price £1.60
- * Model S.K. 1 Kit contains a 15 Watt miniature iron with 2 spare bits, a coil of solder, a heat sink and a booklet "How to Solder" Price £6.25
- * Model S.K. 3 Kit contains Model CX 230 iron — 17 Watts with the S.T. 3 Stand Price £6.00
- * Model S.K. 4 Kit contains Model X25/240 iron — 25 Watts with the S.T. 3 Stand Price £6.00.

Model TCSUI. Temperature controlled soldering stations, now made from the toughest of tough plastics, have anti-static earthing connections to protect your MOS devices. They come with either the miniature CTC or the XTC low voltage (24V) iron. Included also is a range of 3 sizes of bits, 2m anti-static cable, jack, crocodile clip, separate sponge tray. Zero voltage switching to prevent spikes or arcing; no magnetic fields. Temperatures can be set between 65° and 420°C. Current leakage is negligible. Price £38.00. All prices are exclusive of VAT and postage.



Model S.K. 3

Model S.K. 1

Model CTC

S.T. 3 Stand

Model TCSUI

Model X25

Model XTC

Model CX

Model S.K. 4



✂

Please send me the following:

Quantity	Model	Price
.....
.....
.....

ANTEX (Electronics) Ltd.
 Mayflower House, Plymouth, Devon.
 Telephone: Plymouth (0752) 67377/8.
 Telex: 45296. Giro: 2581000

Please send me the Antex Colour Catalogue.
 I enclose cheque/P.O./Cash Value

Name

Address

Telephone:

Stocked by many wholesalers and retailers or direct from us

P.W.11

GARLANDS

It's Bargain Time At Garlands
 These Goodies available while stocks last.

- | | |
|---------------------------|---------------------|
| Piezo Tweeters £4.50 | 555 Timer 22p |
| Peerless Tweeters £1.99 | 4001B 20p |
| Dynamic Microphone £8.50 | 4011B 20p |
| Knackered Car Radio £5.00 | IN4148 2p |
| VU Meters £1.10 | IN4001 5p |
| 12V Solenoids 10p | IN4004 7p |
| 0.1µf-100V Caps 4p | 100µf 250V Caps 10p |

75p PACKS

- | | |
|---|----------------------------|
| 150 Assorted Capacitors | 30 Electrolytic Capacitors |
| or | or |
| 200 Assorted Resistors | 75 Transistor Coils |
| or | or |
| 40 Wirewounds | 10 Slider Pots |
| Multimeters, more than 20 ranges, including H.F.E. £12.55 | |
| Sound to Light Unit, including bulbs and Holders £35.00 | |

We also stock a wide range of electronic, CB and audio components.
 Our range has to be seen to be believed – we stock over 4,000 lines.

Mail Orders Add 50p Post & Packing

All Prices include VAT.

Garlands, Deptford Broadway, London, SE8. Tel. 01-692 4412

MARCO TRADING

ZENER DIODES: 400m/w. 3V to 33V: 8p each, 100 for £6.00 (Your Mix) 1 Watt. 3V to 200V: 15p each, 100 for £12.50 (Your Mix).

I.C. SOCKETS: 6pin - 7p; 8pin - 8p; 14pin - 10p; 16pin - 11p; 18pin - 13p; 20pin - 16p; 22pin - 18p; 24pin - 20p; 28pin - 28p; 40pin - 32p. QUANTITY PRICES ON APPLICATION.

RESISTORS: 1/4W - 40C, 1/3W - 70C, Low Noise, High Stab. 5% Tolerance, Carbon Film, E12 Series, 2.2ohm to 10M. 2p each, 10 for 15p, 100 for 95p, 1000 mixed in 100's only £8.00.

SPECIAL RESISTOR PACK: 10 of each value 2.2Ω to 2MΩ, 730 resistors only £6.00. Amazing Value.

1W Resistors: E12 range from 2.2ohm to 10M All 5%, 5p each.

2W Resistors: E12 range from 20ohm to 10M All 5%, 8p each.

CERAMICS: 63V Working, Subminiature, Low Tolerance, 1.8pF-100nF. 4p each.

TANTALUMS: 35V, 0.1µ, 0.15µ, 0.22µ, 0.33µ, 0.47µ, 0.68µ, 1.0µ - 12p each, 2.2µ, 3.3µ, 4.7µ, 6.8µ, 35V - 14p each, 100 35V 18p, 22/35 38p, 47/10V 25p, 33/10V 22p, 100/3V 20p, 68/3V 20p each.

L.E.D.s: 3mm RED 12p each, Green 18p each, Yellow 18p each, Incl. Clips.

5mm RED 12p each, Green 18p each, Yellow 18p each, Incl. Clips.

SKELETON PRE-SETS: 100Ω to 1M Vertical & Horizontal All 5p each, 100 (Your Mix) for £4.50.

TRANSISTORS:

BC107/8/9	10p	BC212/3/4	9p	2N3055	45p
BC147/8/9	8p	212/3/4/L	10p	2N3819	23p
BC182/3/4	9p	BF180/B1	29p	2N3053	20p
BC172	8p	AC128	20p	BC125	10p
BF200	28p	AD151/2	45p	BF262/3	30p

ELECTROLYTICS: A denotes Wire Ended, R denotes Single Ended:

1/63V	A	7p	25/25	A	3p	220/16	A	3p
2/25	R	4p	47/16	R	5p	470/16	A	12p
4/725	R	5p	47/25	A	6p	1000/16	A	16p
10/16	R	4p	100/3	A	5p	1000/3	A	62p
22/16	R	4p	100/16	R	6p	4700/16	T	55p

MANY MANY MORE VALUES IN STOCK SEE CATALOGUE DETAILS BELOW.

SLIDER POTENTIOMETERS: Metal, Made by NOBLE, 50mm travel, SUPER OFFER: 500Ω LIN MONO - 30p; 50K LOG STEREO - 40p; 100K LIN STEREO - 40p; 1Meg LOG STEREO - 40p. INCLUDING FREE KNOB.

This advert is only a fraction of our range, send 20p for our latest catalogue. Please add 35p P/P to all orders. (Free over £5.00). Add 15% VAT to total. Send orders to: **Dapt PW1, Marco Trading, The Old School, Edataston, WEM, Shropshire, SY4 5RZ. Tel: (094872) 464/465.**

REMEMBER: This is only a fraction of our range, send for latest catalogue.

ALL ORDERS DESPATCHED BY RETURN OF MAIL. Export add SEA/AIR at cost. Wholesale enquiries invited, trade supplied, callers welcome.

NICKEL CADMIUM BATTERIES

	AA (HP7) 0.5Ahr	SUB 'C' 1.2Ahr	'C' (HP11) 1.65Ahr	'C' (HP11) 2.0Ahr	'D' (HP2) 4.0Ahr	PP3 0.1Ahr
1-24	£0.85	£1.38	£1.69	£2.25	£2.97	£3.79
25-49	£0.82	£1.28	£1.58	£2.10	£2.77	
50-99	£0.80	£1.24	£1.52	£2.02	£2.67	
100 up	£0.70	£1.15	£1.41	£1.87	£2.47	

All cells are brand new full spec devices from reputable mfrs. All Nickel Cadmium cells (except PP3) are supplied complete with solder tags and are 'VENTED' devices suitable for fast charge.

CHARGERS - single or dual O/P to charge PP3, AA or SUB 'C' cells in 12-14 hrs (chargers will charge 'C' and 'D' cells but with longer charging time). Units supplied complete in plug top case with flying leads. Number of cells (10 max) in series and type must be specified for each required O/P when ordering.

SINGLE O/P CHARGER £5.04
 DUAL O/P CHARGER £5.72

TRANSFORMERS - as used in chargers, 2 x 12 volt 0.25 amp secondaries 240v primary, tag connections £1.57 each.

Data and charging circuits free with orders over £10 otherwise 30p post.
 P&P 10% if order less than £10. 5% if order over £10. Prices DO NOT INCLUDE VAT and this should be added to the total order.

Cheques, P.O.'s Mail Order to:-
SOLID STATE SECURITY,
 Dept. (PW), Bradshaw Lane,
 Parbold, Wigan, Lancs.
 Telephone 02576-3018.



SAFGAN Presents **DT-400** series from **£159 + VAT**

HIGH QUALITY **DUAL TRACE** OSCILLOSCOPES
 AT PRICES EVERYONE CAN AFFORD


- | | | | | |
|--------------|--------|---------|-------|--------------|
| Model DT-410 | 4" CRT | 5mv/div | 10MHz | @ £159 + VAT |
| Model DT-412 | 4" CRT | 5mv/div | 12MHz | @ £172 + VAT |
| Model DT-415 | 4" CRT | 5mv/div | 15MHz | @ £185 + VAT |

SPECIFICATION FOR ALL MODELS

- ★ CH1, CH2: 5mv/div-20v/div in 12 cal steps
- ★ BANDWIDTH: 10MHz (DT-410), 12MHz (DT-412), 15MHz (DT-415)
- ★ TIME BASE: 0.5us/div-200ms/div in 18 cal steps
 x5 Expansion to 100ns/div
 x5 Multiplier to 1s/div
- ★ XY FACILITY: Matched inputs X=CH1, Y=CH2
- ★ TRIGGER: Level Control, ± slope
 Bright Line AUTO, NORMAL, TV Triggering CH1, CH2 0.5 div; EXT Trig 100mv
- ★ Z Modulation
- ★ Graticule blue ruled 8 x 10 div (6.4 x 8cm²)
- ★ Size: H215mm W165mm D280mm Weight 4.5kg
 PROBE (X1-REF-X10) £11.50 + VAT

ORDERS TO: **SAFGAN ELECTRONICS LTD.** (Goods + 15% + £3 P&P)
56 BISHOPS WOOD, ST. JOHNS, WOKING, SURREY GU21 3QB
 OFFICIAL GOVERNMENT AND EDUCATIONAL ORDERS ACCEPTED

TEL: WOKING 66836
 OR WOKING 69560

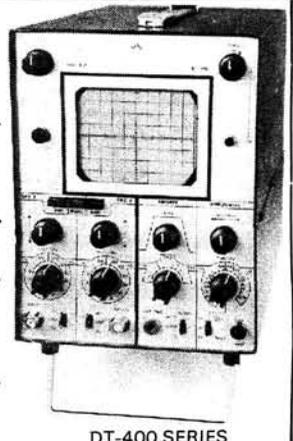

DT-400 SERIES

PRIME COMPONENTS LOW PRICES

NEW

SPECIAL OFFER!

**4K CMOS RAM (1K x 4) 450 NS
ONLY £6.95 (8 for £45).**

The TC 5514P from Toshiba, CMOS equivalent of the 2114!

- Low Power Dissipation 10pW/BIT (TYP.) 3.0V (STAND BY)
- 100W/BIT (TYP.) 5.0V (OPERATING)
- Data Retention Voltage 2V to 5.5V
- Single SV Power Supply
- 18 Pin Plastic Package
- Full Static Operation
- Three State Output
- Input/Output TTL Compatible
- Fast Access Time 450NS

Toshiba's TC5514P (industry type 6514) is a full static read write memory organised as 1024 words by 4 bits

using CMOS technology. Ultra low power dissipation means it can be used as battery-operated portable memory system and also as a non-volatile memory with battery back-up. Operates from a single 5V power supply with static operation, hence no refresh periods and a much simplified power supply circuit design. Three state outputs simplify memory expansion for minimum data retention voltage is 2V, the battery back-up system needs only simple circuit. Toshiba's original CMOS technology also means wide operating and noise margins. The TC 5514P is moulded in a dual-in-line 18 pin plastic package 0.3 inch in width.

All our micro chips are at micro prices. Don't be fooled by low prices. We do not offer for sale sub-spec or rebranded devices. All our parts are guaranteed new, first quality, factory prime. Full spec devices. It is also our policy to offer you the best new devices that become available and these are featured regularly. Prices are exclusive of p&p and VAT - please refer to "Ordering Information" before ordering. Official orders from Schools, Colleges, Universities and Gov. Authorities accepted.

DTL	4028	75p	MEMORIES	6502	795p
930	4029	80p	2114 300 NS	6504	795p
935	4030	60p	4116 200 NS	6505	795p
937	4031	195p	4116 150 NS	6800	695p
944	4033	145p	4315 (4k-1) CMOS	6802	995p
946	4035	104p	RAM 450 NS 995p	8080A	525p
947	4036	290p	6514 (1k-4) CMOS	8085A	1095p
962	4037	105p	RAM 450 NS 795p	280A	795p
965	4038	110p		280A	995p
9099	4039	290p		28001	12500p
	4040	99p		28002	9500p
	4042	75p		WD9000B	19900p

7400	4043	86p	EPROMS	7400	30p
7400	4044	88p	1702A	7406	60p
7401	4045	185p	2708 450 NS	7407	145p
7402	4046	105p	2716 5V 450 NS	7408	125p
7403	4047	99p	2532 32k 450 NS	7409	125p
7404	4048	56p		7410	110p
7409	4049	56p		7411	145p
7410	4050	40p		7412	145p
7412	4051	69p		7413	145p
7513	4052	75p		7414	145p
7420	4053	73p		7415	145p
7422	4054	111p		7416	145p
7432	4055	121p		7417	145p
7440	4056	56p		7418	145p
7442	4057	56p		7419	145p
7448	4058	112p		7420	145p
7473	4059	112p		7421	145p
7474	4060	112p		7422	145p
7475	4061	112p		7423	145p
7476	4062	422p		7424	145p
7490	4063	112p		7425	145p
7492	4064	112p		7426	145p
7493	4065	112p		7427	145p
7495	4066	56p		7428	145p
74121	4067	25p		7429	145p
74123	4068	25p		7430	145p
74154	4069	25p		7431	145p
74157	4070	28p		7432	145p
74122	4071	25p		7433	145p
74125	4072	25p		7434	145p
74154	4073	25p		7435	145p
74157	4074	25p		7436	145p
74122	4075	25p		7437	145p
74125	4076	25p		7438	145p
74154	4077	25p		7439	145p
74157	4078	25p		7440	145p
74122	4079	25p		7441	145p
74125	4080	25p		7442	145p
74154	4081	25p		7443	145p
74157	4082	25p		7444	145p
74122	4083	25p		7445	145p
74125	4084	25p		7446	145p
74154	4085	25p		7447	145p
74157	4086	25p		7448	145p
74122	4087	25p		7449	145p
74125	4088	25p		7450	145p
74154	4089	25p		7451	145p
74157	4090	25p		7452	145p

74LS	4091 <th>225p</th> <th>CHARACTER GENERATOR</th> <th>7400</th> <th>30p</th>	225p	CHARACTER GENERATOR	7400	30p
74LS00	4092	225p <td>RO-3-2513 UC</td> <td>7401</td> <td>30p </td>	RO-3-2513 UC	7401	30p
74LS01	4093	325p <td>KEYBOARD ENCODER</td> <td>7402</td> <td>30p </td>	KEYBOARD ENCODER	7402	30p
74LS02	4094	110p <td>AY-5-2376</td> <td>7403</td> <td>30p </td>	AY-5-2376	7403	30p
74LS04	4095	110p <td>FLOPPY DISK CONTROLLERS</td> <td>7404</td> <td>30p </td>	FLOPPY DISK CONTROLLERS	7404	30p
74LS08	4096	325p <td>FD1771 B-01</td> <td>7405</td> <td>30p </td>	FD1771 B-01	7405	30p
74LS10	4097	110p <td>S/D Inverted Bus</td> <td>7406</td> <td>30p </td>	S/D Inverted Bus	7406	30p
74LS11	4098	110p <td>FD1791 B-01</td> <td>7407</td> <td>30p </td>	FD1791 B-01	7407	30p
74LS12	4099	110p <td>D/D Inverted Bus</td> <td>7408</td> <td>30p</td>	D/D Inverted Bus	7408	30p
74LS13	4100	110p <td>FD1792 B-01</td> <td>7409</td> <td>30p </td>	FD1792 B-01	7409	30p
74LS14	4101	110p <td>S/D Inverted Bus</td> <td>7410</td> <td>30p </td>	S/D Inverted Bus	7410	30p
74LS15	4102	110p <td>FD1793 B-01</td> <td>7411</td> <td>30p </td>	FD1793 B-01	7411	30p
74LS16	4103	110p <td>D/D True Bus</td> <td>7412</td> <td>30p </td>	D/D True Bus	7412	30p
74LS17	4104	110p <td>FD1794 B-01</td> <td>7413</td> <td>30p </td>	FD1794 B-01	7413	30p
74LS18	4105	110p <td>S/D True Bus</td> <td>7414</td> <td>30p </td>	S/D True Bus	7414	30p
74LS19	4106	110p <td>FD1795 B D/D Inverted Bus, side select</td> <td>7415</td> <td>30p </td>	FD1795 B D/D Inverted Bus, side select	7415	30p
74LS20	4107	110p <td>FD1797 B D/D True Bus, side select</td> <td>7416</td> <td>30p </td>	FD1797 B D/D True Bus, side select	7416	30p
74LS21	4108	110p <td>SUPPORT DEVICES</td> <td>7417</td> <td>30p </td>	SUPPORT DEVICES	7417	30p
74LS22	4109	110p <td>6520</td> <td>495p</td>	6520	495p	
74LS23	4110	110p <td>6522</td> <td>795p</td>	6522	795p	
74LS24	4111	110p <td>6523</td> <td>895p</td>	6523	895p	
74LS25	4112	110p <td>6524</td> <td>1095p</td>	6524	1095p	
74LS26	4113	110p <td>6810</td> <td>375p</td>	6810	375p	
74LS27	4114	110p <td>6820</td> <td>425p</td>	6820	425p	
74LS28	4115	110p <td>6821</td> <td>425p</td>	6821	425p	
74LS29	4116	110p <td>6822</td> <td>425p</td>	6822	425p	
74LS99	4186	110p <td>6892</td> <td>425p</td>	6892	425p	
74LS00	4187	110p <td>6893</td> <td>425p</td>	6893	425p	
74LS01	4188	110p <td>6894</td> <td>425p</td>	6894	425p	
74LS02	4189	110p <td>6895</td> <td>425p</td>	6895	425p	
74LS03	4190	110p <td>6896</td> <td>425p</td>	6896	425p	
74LS04	4191	110p <td>6897</td> <td>425p</td>	6897	425p	
74LS05	4192	110p <td>6898</td> <td>425p</td>	6898	425p	
74LS06	4193	110p <td>6899</td> <td>425p</td>	6899	425p	
74LS07	4194	110p <td>6900</td> <td>425p</td>	6900	425p	
74LS08	4195	110p <td>6901</td> <td>425p</td>	6901	425p	
74LS09	4196	110p <td>6902</td> <td>425p</td>	6902	425p	
74LS10	4197	110p <td>6903</td> <td>425p</td>	6903	425p	
74LS11	4198	110p <td>6904</td> <td>425p</td>	6904	425p	
74LS12	4199	110p <td>6905</td> <td>425p</td>	6905	425p	
74LS13	4200	110p <td>6906</td> <td>425p</td>	6906	425p	
74LS14	4201	110p <td>6907</td> <td>425p</td>	6907	425p	
74LS15	4202	110p <td>6908</td> <td>425p</td>	6908	425p	
74LS16	4203	110p <td>6909</td> <td>425p</td>	6909	425p	
74LS17	4204	110p <td>6910</td> <td>425p</td>	6910	425p	
74LS18	4205	110p <td>6911</td> <td>425p</td>	6911	425p	
74LS19	4206	110p <td>6912</td> <td>425p</td>	6912	425p	
74LS20	4207	110p <td>6913</td> <td>425p</td>	6913	425p	
74LS21	4208	110p <td>6914</td> <td>425p</td>	6914	425p	
74LS22	4209	110p <td>6915</td> <td>425p</td>	6915	425p	
74LS23	4210	110p <td>6916</td> <td>425p</td>	6916	425p	
74LS24	4211	110p <td>6917</td> <td>425p</td>	6917	425p	
74LS25	4212	110p <td>6918</td> <td>425p</td>	6918	425p	
74LS26	4213	110p <td>6919</td> <td>425p</td>	6919	425p	
74LS27	4214	110p <td>6920</td> <td>425p</td>	6920	425p	
74LS28	4215	110p <td>6921</td> <td>425p</td>	6921	425p	
74LS29	4216	110p <td>6922</td> <td>425p</td>	6922	425p	
74LS30	4217	110p <td>6923</td> <td>425p</td>	6923	425p	
74LS31	4218				

Britain's first computer kit.

The Sinclair ZX80.

£79.95

Price breakdown
 ZX80 and manual: £69.52
 VAT: £10.43
 Post and packing FREE



Please note: many kit makers quote VAT-exclusive prices.

You've seen the reviews... you've heard the excitement... now make the kit!

This is the ZX80. 'Personal Computer World' gave it 5 stars for 'excellent value.' Benchmark tests say it's faster than all previous personal computers. And the response from kit enthusiasts has been tremendous.

To help you appreciate its value, the price is shown above with and without VAT. This is so you can compare the ZX80 with competitive kits that don't appear with inclusive prices.

'Excellent value' indeed!

For just £79.95 (including VAT and p&p) you get everything you need to build a personal computer at home... PCB, with IC sockets for all ICs; case; leads for direct connection to a cassette recorder and television (black and white or colour); *everything!*

Yet the ZX80 really is a complete, powerful, full-facility computer, matching or surpassing other personal computers at several times the price.

The ZX80 is programmed in BASIC, the world's most popular computer language for beginners and experts alike.

The ZX80 is pleasantly straightforward to assemble, using a fine-tipped soldering iron. It immediately proves what a good job you've done; connect it to your TV... link it to an appropriate power source*... and you're ready to go.

Your ZX80 kit contains...

- Printed circuit board, with IC sockets for all ICs.
- Complete components set, including all ICs—all manufactured by selected world-leading suppliers.
- New rugged Sinclair keyboard, touch-sensitive, wipe-clean.
- Ready-moulded case.
- Leads and plugs for connection to domestic TV and cassette recorder. (Programs can be **SAVED** and **LOADED** on to a portable cassette recorder.)
- FREE course in BASIC programming and user manual.

Optional extras

- Mains adaptor of 600 mA at 9 V DC nominal unregulated (available separately—see coupon).
- Additional memory expansion boards allowing up to 16K bytes RAM. (Extra RAM chips also available—see coupon).

*Use a 600 mA at 9 V DC nominal unregulated mains adaptor. Available from Sinclair if desired (see coupon).

The unique and valuable components of the Sinclair ZX80.

The Sinclair ZX80 is not just another personal computer. Quite apart from its exceptionally low price, the ZX80 has two uniquely advanced components: the Sinclair BASIC interpreter; and the Sinclair teach-yourself BASIC manual.

The unique Sinclair BASIC interpreter offers remarkable programming advantages:

- **Unique 'one-touch' key word entry: the ZX80 eliminates a great deal of tiresome typing. Key words (RUN, PRINT, LIST, etc.) have their own single-key entry.**
- Unique syntax check. Only lines with correct syntax are accepted into programs. A cursor identifies errors immediately. This prevents entry of long and complicated programs with faults only discovered when you try to run them.
- Excellent string-handling capability—takes up to 26 string variables of any length. All strings can undergo all relational tests (e.g. comparison). The ZX80 also has string input to request a line of text when necessary. Strings do not need to be dimensioned.
- Up to 26 single dimension arrays.
- FOR/NEXT loops nested up to 26.
- Variable names of any length.
- BASIC language also handles full Boolean arithmetic, conditional expressions, etc.
- Exceptionally powerful edit facilities, allows modification of existing program lines.
- Randomise function, useful for games and secret codes, as well as more serious applications.
- Timer under program control.
- PEEK and POKE enable entry of machine code instructions. USR causes jump to a user's machine language sub-routine.
- High-resolution graphics with 22 standard graphic symbols.
- All characters printable in reverse under program control.
- Lines of unlimited length.


Fewer chips, compact design, volume production—more power per pound!

The ZX80 owes its remarkable low price to its remarkable design: the whole system is packed on to fewer, newer, more powerful and advanced LSI chips. A single SUPER ROM, for instance, contains the BASIC interpreter, the character set, operating system, and monitor. And the ZX80's 1K byte RAM is roughly equivalent to 4K bytes in a conventional computer—typically storing 100 lines of BASIC. (Key words occupy only a single byte.)




The display shows 32 characters by 24 lines.

And Benchmark tests show that the ZX80 is faster than all other personal computers.

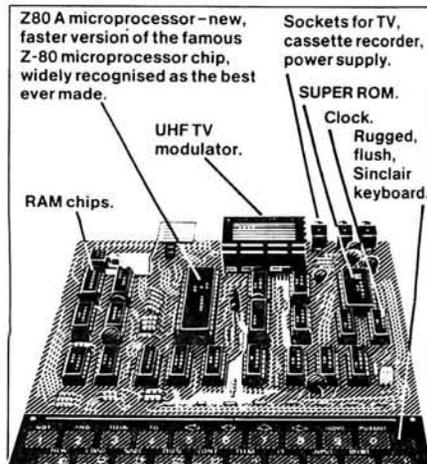No other personal computer offers this unique combination of high capability and low price.



plete

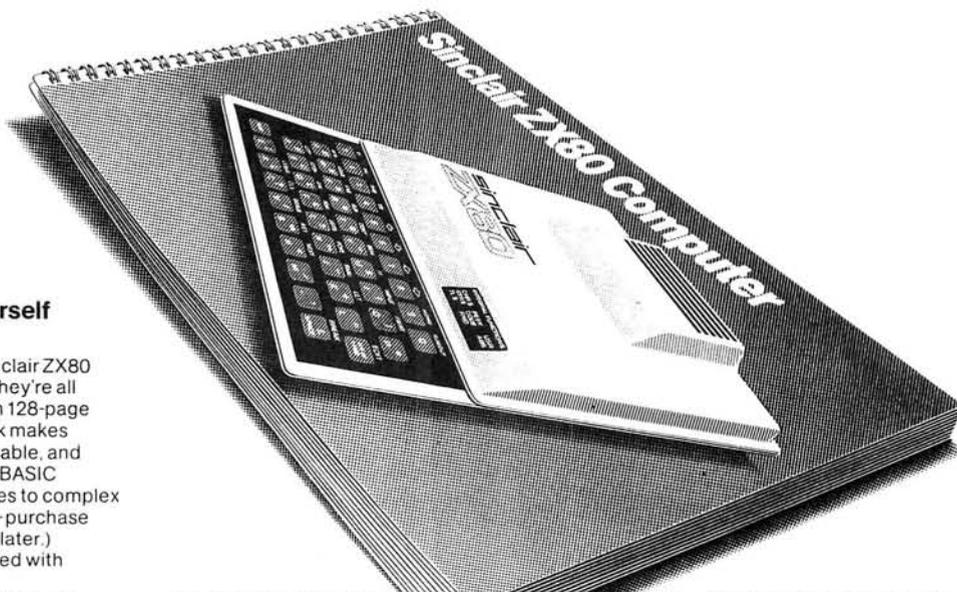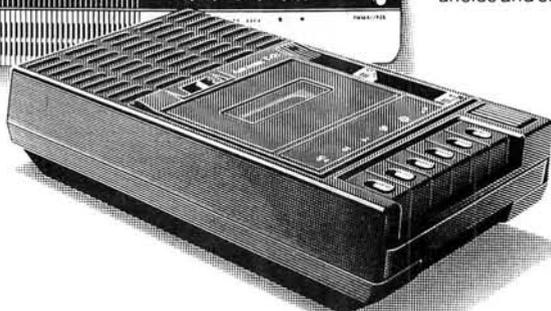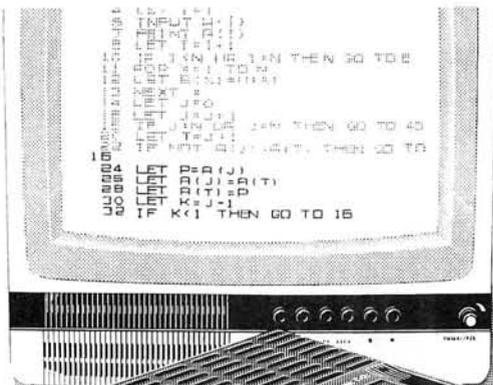

ZX80 software – now available!

See advertisements in Personal Computer World, Electronics Today International, and other journals.

New dedicated software – developed independently of Science of Cambridge – reflects the enormous interest in the ZX80. More software available soon – from leading consultancies and software houses.

The Sinclair teach-yourself BASIC manual.

If the specifications of the Sinclair ZX80 mean little to you – don't worry. They're all explained in the specially-written 128-page book *free* with every kit! The book makes learning easy, exciting and enjoyable, and represents a complete course in BASIC programming – from first principles to complex programs. (Available separately – purchase price refunded if you buy a ZX80 later.) A hardware manual is also included with every kit.

The Sinclair ZX80. Kit: £79.95. Assembled: £99.95. Complete!

The ZX80 kit costs a mere £79.95. Can't wait to have a ZX80 up and running? No problem! It's also available, ready assembled and complete with mains adaptor, for only £99.95.

Demand for the ZX80 is very high: use the coupon to order today for the earliest possible delivery. All orders will be despatched in strict rotation. We'll acknowledge each order by return, and tell you exactly when your ZX80 will be delivered. If you choose not to wait, you can cancel your order immediately, and your money will be refunded at once. Again, of course, you may return your ZX80 as received within 14 days for a full refund. We want you to be satisfied beyond all doubt – and we have no doubt that you will be.

sinclair

ZX80





Science of Cambridge Ltd
6 Kings Parade, Cambridge, Cambs., CB2 1SN.
Tel: 0223 311488.

ORDER FORM		To: Science of Cambridge Ltd, 6 Kings Parade, Cambridge, Cambs., CB2 1SN. Remember: all prices shown include VAT, postage and packing. No hidden extras. Please send me:	
Quantity	Item	Item price £	Total £
	Sinclair ZX80 Personal Computer kit(s). Price includes ZX80 BASIC manual, excludes mains adaptor.	£79.95	
	Ready-assembled Sinclair ZX80 Personal Computer(s). Price includes ZX80 BASIC manual and mains adaptor.	£99.95	
	Mains Adaptor(s) (600 mA at 9 V DC nominal unregulated)	8.95	
	Memory Expansion Board(s) (each one takes up to 3K bytes)	12.00	
	RAM Memory chips – standard 1K bytes capacity	16.00	
	Sinclair ZX80 Manual(s) (manual free with every ZX80 kit or ready-made computer)	5.00	
		TOTAL	£
NB. Your Sinclair ZX80 may qualify as a business expense			
I enclose a cheque/postal order payable to Science of Cambridge Ltd for £ _____			
Please print			
Name: Mr/Mrs/Miss _____			
Address _____			
			PW 11/80

NEW! LERNA-KITS!

● HIGH QUALITY EDUCATIONAL KITS

- LATEST SOLID STATE TECHNOLOGY – DESIGNED & MADE IN THE U.K.
- DETAILED STAGE BY STAGE BUILDING INSTRUCTIONS
- FREE ADVISORY SERVICE THROUGHOUT THE BUILDING
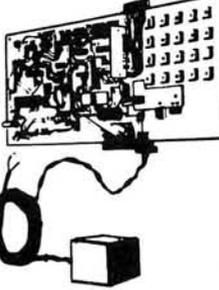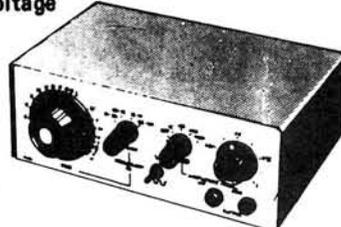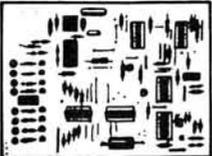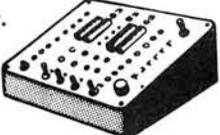
<p>LK1 OSCILLOSCOPE Solid state circuitry; D.C. coupled; 7 cm. dia. tube; Y input 0.3 v/cm. to 50 v/cm.; X input 1 volt/cm.; 1v. and 10v. cal. signals; response to 1MHz; Time base ranges to 8µS per cm.; Size 230 x 130 x 190mm. Wt. 2Kg. Operates from 110 volt or 220/240 volt A.C. High quality kit complete with carrying case.</p>  <p style="text-align: right;">£130.00</p>	<p>LK2 DIGITAL MULTIMETER Solid state circuitry with large digital display. Ranges are up to 1000v. D.C. and A.C. and current D.C. to 100mA. Resistance ranges 100K ohms. Battery operated. Size 185 x 110 x 60mm. Digital display : 37 x 16mm</p>  <p style="text-align: right;">£40.00</p>
<p>LK3 HOME COMPUTER Ideal simple computer for beginners. Microprocessor has 8 bit data bus and 12 bit address bus. Ready programmed ROM has 4K bits. RAM of 0.5 x 8k bits fully addressable. 8 digit LED display. Hexadecimal read out. Hexadecimal keyboard. Re-set switch and single shot facility. Power supply kit included. Provision for cassette and V.D.U. operation.</p>  <p style="text-align: right;">£190.00</p>	<p>LK4 AUDIO GENERATOR Covers 10Hz to 100kHz in four switched stages. Variable voltage output. Distortion below 0.02%. Sine and square wave output. Ideal for HI-FI work and as signal tracer.</p>  <p style="text-align: right;">£40.00</p>
<p>LK5 DIGITAL ELECTRONIC TECHNIQUES Experiments carried out on a P.C. board, size 190 x 150mm covering operational amplifiers; integrators; basic logic circuits; NAND, NOR gates; Flip-Flops; Multi-vibrators; clock generator; 4 bit comparator feed back; analogue switching; building simple digital meter circuits; Timer. Note:— for full benefit with this kit a C.R.O. is desirable although circuits can be built without one.</p>  <p style="text-align: right;">£35.00</p>	<p>LK6 LOGIC DEMONSTRATION PANEL Basic introduction to computer technology; AND and OR gates; NOR and NAND; Data line selector; Truth tables; AND and INVERT gate; Half and Full Adder; Latches; Flip-Flops; Shift register; Binary coded decimal counter. Over 16 experiments are performed with panel. Battery operated.</p>  <p style="text-align: right;">£70.00</p>
<p>LK7 ANALOGUE TEST METER Basic multi range test meter kit with 20,000 ohm/volt sensitivity. Ranges: D.C. and A.C. volts 0-5, 0-25, 0-100, 0-500; 2.5kV. D.C. 0-5mA, 0-500mA, 0-50µA Resistance 0-50K; 0-5M. Size 150 x 75 x 50mm.</p>  <p style="text-align: right;">£17.00</p>	<p>LK8 SHORT WAVE RECEIVER A simple 3 stage short wave only radio receiver for the amateur. Very good selectivity and sensitivity and will give hours of enjoyment. Simple to construct by people of any age.</p>  <p style="text-align: right;">£25.00</p>

To:— LERNAKITS, 4 Cleveland Road, Jersey, Channel Islands. (Est. 40 years)

Please supply Kit at £.....	add £2 postage U.K. only. £10 postage overseas Air Mail.	PW/11/819
BLOCK CAPS PLEASE	Catalogue available on receipt 12p stamp.	
NAME	ALL CREDIT CARDS ACCEPTED	
ADDRESS	Name of Card	
.....	No. <input type="text"/>	
.....	Signature	
(Dispatch is normally within 1 week of receipt of order)		

OFF THE SHELF
DELIVERY ON THESE



BRAND NEW FROM FLUKE... NOW AVAILABLE THE 8024A HAND HELD DMM

This model incorporates all the features of the 8020A but in addition has:

- A peak hold switch which can be used in AC or DC for volts and current functions.
- Audible continuity testing and level detection for sensing logic levels.
- A temperature (°C) range for use with a thermocouple.

£135

Carriage and Insurance £3

The following accessories are in stock now

Y8008 Touch and Hold Probe.....	£18.00
80K-40 High Voltage Probe.....	£45.00
81RF RF Probe to 100 MHz.....	£32.00
80T-150C Temperature Probe (C).....	£55.00
801-600 Clamp-on AC Current Probe	£55.00



HERE IT IS... THE EVER POPULAR 8022A HAND-HELD DMM

Consider the following features:
6 resistance ranges from 200 ohm-20 ohms.
8 current ranges from 2mA-2A AC/DC.
10 voltage ranges from 200 mv-1000v DC-200 mc-750V AC.
Pocket size - weighing only 370 gms.
Full overload protection - will withstand 6kv spikes.
Rugged construction - virtually indestructible.
Meets tough military specs. - drop proof.
In line, pushbutton operation for single-handed usage.
Incorporates low power cmos chip for low power consumption.
All this plus a 2-year full guarantee.



For only **£89**

Carriage and Insurance £3

Soft carrying case
£7 extra


Even more sophisticated the Fluke 8020A.
Identical in most respects to the 8022A but in addition incorporates a conductance range from 2mS-200nS.

Price **£112**

Carriage and Insurance £3.00

A handsome soft carrying case is included (this model only)

OFF THE SHELF
DELIVERY ON THESE

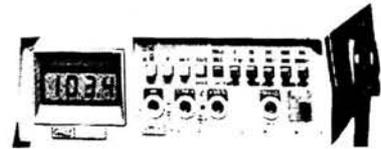

8010A AND 8012A BENCH MODEL D.M.M.s

The 8010A is a general purpose, bench/portable digital multimeter with more functions and features than ever offered for such a low price. Its companion, the 8012A, has identical characteristics except that it has two additional low resistance ranges, 2Ω and 20Ω to replace the 8010A's 10 ampere current range.

The 8010A and 8012A feature:
10 voltage ranges from 200mv-1000v dc, 200mv-75v ac.
3 conductance ranges from 2mS-200nS.
6 resistance ranges from 200Ω-20mΩ - the 8012A has two additional resistance ranges 2Ω and 20Ω.
10 current ranges from 200μA-2A AC/DC - the 8010A has two additional current ranges 10A AC and 10A DC.

8010A **£159** 8012A **£199**

Carriage and Insurance £3.

The 8010A is also available with two rechargeable Nicard size C batteries installed in option -01 a+ **£179.00.**

PLEASE ADD 15% VAT TO ALL ORDERS except where items marked "VAT Included". CALLERS WELCOME.

We are open 9 a.m.-6 p.m. Monday-Saturdays. We carry a very large selection of electronic components and electro-mechanical items. Special quotations on quantities.

ELECTRO-TECH COMPONENTS LTD.

364 EDGWARE ROAD, LONDON, W.2. TEL: 01-723 5667

P.W. KITS

P. W. NIMBUS

Transceiver (PCB & all components except channel xtals)	£46.00
Modulator (PCB & all components)	£4.50
General Assembly (Aerial, mike, box, speakers etc.)	£32.50
Complete Kit (if all parts purchased)	£80.00

ADD ON BASE UNIT

Complete Kit	£38.00
--------------	--------

Many other P.W. Kits including:

Transceiver Power Unit	Tamar
Linear Frequency Meter	Beginners 2m Converter
Tone Burst & Timer Module	High Impedance Voltmeter
	Model Railway Controller

We also stock Kits for projects published in most magazines.

Personal callers welcome - but please phone first to check availability

All Prices include post and VAT.

T. POWELL 306 St. Paul's Road, Highbury Corner,
London N1. Telephone: 01-226 1489.

ACCESS/VISA ACCEPTED
Shop open: Mon. to Fri. 9-5.30. Sat. 9-4.30.

DIGITAL VOLTMETER MODULE



Fully built and
tested, ONLY

£11.95 VAT

- Reads positive and negative voltages with a sensitivity of 0 - +999mV and 0 - -99mV
- Requires only single supply between 7 & 12 volts (220mA)
- High accuracy +0.1% +1 digit
- Large bright 0.43" high efficiency displays
- 4 readings per second sampling rate
- Size only 41 x 95 x 10mm
- Supplied with full data & applications information

This brand new, quality module manufactured by Autona Limited (who are one of the U.K.'s largest module manufacturers) means you can build accurate test equipment, multi-meters, thermometers, etc. easily and at a fraction of the cost of ready-made equipment. Full details are provided showing how to measure A.C. voltage, current, resistance and temperature.

Send your cheque or P.O. (£11.95 + £1.79 V.A.T. + 50pp. & p. = £14.24) now to:-

Dept. P.W.1.
RISCOMP LIMITED
21 Duke Street
Princes Risborough
Bucks. HP17 0AT

**BUCKINGHAMSHIRE'S NEW
ELECTRONICS CENTRE**
8 miles off the M40
50 minutes from London
Telephone: (084 44) 6326

AND THERE'S MORE WHERE THIS CAME FROM

It's a long time since one of our adverts was presented in 'list' form - but simply because we do not try to squeeze this lot in every price doesn't mean that it's not available. Our new style price list (now some 40 pages long) includes all this and more, including quantity prices and a brief description. The kits, modules and specialized RF components - such as TOKO coils, filters etc. are covered in the general price list - so send now for a free copy (with an SAE please). Part 4 of the catalogue is due out now (incorporating a revised version of pt.1).

LINEAR ICs - NUMERIC LISTINGS

TBA120S	1.00	KB4413	1.95
L200	1.95	KB4417	1.80
U237B	1.28	TDA4420	2.25
U247B	1.28	KB4420B	1.09
U257B	1.28	KB4423	2.30
U267B	1.28	KB4424	1.65
LM301H	0.67	KB4431	1.95
LM301N	0.30	KB4432	1.95
LM308H	0.96	KB4433	1.52
LM308N	0.65	KB4436	2.53
LM339N	0.66	KB4437	1.75
LM348N	1.86	KB4438	2.22
LF351N	0.38	KB4441	1.35
LF352N	0.76	KB4445	1.29
LM374N	3.75	KB4446	2.75
LM380N-14	1.00	KB4448	1.65
LM380N-8	1.00	NE5044N	2.26
LM381N	1.81	NE5532N	1.85
2N419CE	1.95	SD6000	3.75
NE544N	1.80	SL6270	2.03
NE555N	0.30	SL6310	2.03
NE556N	0.50	SL6600	3.75
NE560N	3.50	SL6640	2.75
NE562N	4.05	SL6690	3.20
NE564N	4.29	SL6700	2.35
NE565N	1.00	ICL8038CC	4.50
NE566N	1.60	MSL9362	1.75
NE567N	3.85	MSL9363	1.75
SL624	3.28	HALL1211	1.95
TBA651	1.81	HALL1223	2.15
UA709HC	0.64	HALL1225	1.45
UA709PC	0.36	HALL2002	1.45
UA710HC	0.65	HALL2017	0.80
UA710PC	0.59	HALL2402	1.95
UA741CH	0.66	HALL2411	1.20
UA741CN	0.27	HALL2412	1.55
UA747CN	0.70	LF13741	0.33
UA748CN	0.36	SW76660N	0.80
UA753	2.44		
UA758	2.35		

FREQUENCY DISPLAY & SYNTHESIZER ICs

SAA1056	3.75
SAA1058	3.35
SAA1059	3.35
LN1232	14.00
LN1242	19.00
MSL2318	3.84
MSM5523	11.30
MSM5524	11.30
MSM5525	7.85
MSM5526	7.85
MSM5527	9.75
MSM5527L	9.75
ICM7106CP	9.55
ICM7107CP	9.55
ICM7216A	19.25
ICM7217B	9.55
SPB629	3.85
SPB647	6.00
9SH90CP	6.00
HDI0551	2.45
HD4015	4.45
HD12009	6.00
HD4752	8.00

CMOS 4000 SERIES

4001	0.17
4000	0.17
4002	0.23
4008	0.80
4009	0.58
4010B	0.58
4011AE	0.20
4011B	0.20
4012	0.55
4013	0.55
4014	0.91
4016	0.52
4017	0.80
4019	0.60
4020B	0.93
4021	0.82
4022	0.90
4023	0.17
4024	0.76
4025	0.17
4026	1.80
4028	0.72
4029	1.00
4030	0.58
4035	1.20
4040	0.83
4042	0.85

TTL N and LSN

7443N	1.15	74LS112	0.38
7444N	1.12	74LS113	0.38
7445N	0.94	74LS114	0.38
7446N	0.94	74LS118	0.83
7447N	0.89	74LS120	1.15
7448N	0.96	74LS121	0.42
7449N	0.59	74LS122	0.46
7450N	0.99	74LS123	0.73
7451N	0.17	74LS124	1.75
7452N	0.38	74LS125	0.44
7453N	0.17	74LS125	0.38
7454N	0.24	74LS126	0.57
7455N	0.24	74LS126	0.44
7456N	0.24	74LS128	0.74
7457N	0.17	74LS129	0.73
7458N	1.24	74LS132	0.78
7459N	0.28	74LS136	0.40
7460N	0.28	74LS138	0.60
7461N	0.28	74LS138	0.60
7462N	0.28	74LS138	0.60
7463N	0.32	74LS141	0.56
7464N	0.32	74LS142	2.65
7465N	0.27	74LS143	3.12
7466N	0.28	74LS144	3.12
7467N	0.38	74LS145	0.97
7468N	0.37	74LS147	1.75
7469N	0.38	74LS148	1.09
7470N	0.48	74LS148	1.19
7471N	0.48	74LS150	0.99
7472N	0.69	74LS151	0.55
7473N	1.04	74LS151	0.84
7474N	0.99	74LS153	0.54
7475N	0.96	74LS153	0.54
7476N	2.05	74LS155	1.10
7477N	0.33	74LS155	1.10
7478N	0.27	74LS156	0.80
7479N	0.76	74LS157	0.55
7480N	1.10	74LS157	0.55
7481N	0.38	74LS158	0.60
7482N	0.35	74LS159	2.10
7483N	0.32	74LS160	0.82
7484N	0.32	74LS160	1.30
7485N	0.65	74LS161	0.92
7486N	1.14	74LS162	1.30
7487N	0.58	74LS163	0.92
7488N	1.20	74LS163	0.78
7489N	1.85	74LS164	1.04
7490N	0.87	74LS164	1.30
7491N	0.63	74LS165	1.04
7492N	0.67	74LS165	1.04
7493N	0.54	74LS167N	2.50
7494N	0.68		

VOLTAGE REGULATORS

78Series	0.95
79Series	1.00
78MSeries	0.65
78LSeries	0.35
79L05	0.85
79M02ZC	1.75
79M02ZC	1.75
723CN	0.65
L200	1.95
TD1412	0.75
NE5553N	1.25
LM317MP	1.48
LM337MP	1.48
4043	0.85
4044	0.80
4046	1.30
4047	0.99
4049	0.52
4050	0.55
4051	0.65
4052	0.65
4053	0.65
4063	1.09
4066	0.56
4068	0.25
4069	0.20
4070	0.20
4071	0.20
4072	0.20
4073	0.20
4075	0.20
4076	0.90
4077	0.20
4078	0.20
4082	0.20
4093	0.78
4175	0.95
4503	0.69
4506	0.51
4510	0.99
4511	1.49
4512	0.98
4514	2.55
4518	1.03
4520	1.09
4521	2.36
4522	1.49
4529	1.41
4539	1.10
4549	3.50
4554	1.53
4560	2.18
4566	1.59
4568	2.18
4569	3.03
4572	3.00
4585	1.10

MICROMARKET

8080A/2	7.50
8212	2.30
8214	3.50
8216	0.95
8224	3.50
8251	6.25
8255	5.40
6800P	7.50
6810	5.95
6820	7.45
6850	4.90
6852	4.85
MC2708	7.50
2114	6.50
4027	5.78
2102	1.70
2112	3.40
2513	7.54
HM4716	4.50
81LS97	1.25

VARICAP

74LS169	2.00
74LS170	2.30
74LS171	1.20
74LS172	0.87
74LS173	1.10
74LS174	0.75
74LS175	1.15
74LS176	0.75
74LS177	0.78
74LS178	1.65
74LS179	3.50
74LS180	2.10
74LS181	2.50
74LS182	1.34
74LS183	2.10
74LS184	1.35
74LS185	1.34
74LS186	0.92
74LS187	1.05
74LS188	1.05
74LS189	1.80
74LS190	1.05
74LS191	0.99
74LS192	1.10
74LS193	1.10
74LS194	1.05
74LS195	1.05
74LS196	1.10
74LS197	1.10
74LS198	1.50
74LS199	1.60
74LS200	0.93
74LS201	1.08
74LS202	1.53
74LS203	0.52
74LS204	0.52
74LS205	0.80
74LS206	1.80
74LS207	1.95
74LS208	1.30
74LS209	1.40

TOKO COILS AND FILTERS

SEE THE EXTENSIVE SECTION IN OUR NEW PRICE LISTS AND CATALOGUE

LF/HF FIXED INDUCTORS

LF/HF FIXED INDUCTORS	
-FULL E12 RANGE	
7BA series LuH-1mH	0.16
8BB series	
100uH-3mH	0.19
10RB series	
3mH-120mH	0.33
120mH-1.5H	0.55
PIEZO SOUNDER	
PB2720	0.44

CRYSTAL FILTER PRODUCTS

10.7MHz 2 POLE TYPES:	
10M15A 15kHz BW	2.49
10.7MHz 8 POLE TYPES:	
10M41 15kHz BW	14.50
H4402 7.5kHz BW	15.50
10M22D 2.4kHz SSB	17.20
HF FIRST FILTER:	
B34F8A 34.5MHz HF	32.00

RADIO CONTROL CRYSTALS

(No splits available)	
AM TX:-	
3rd Oct 30P HC25U	1.65
AM/FM RX:-	
3rd Oct 30P HC25U	1.65
FM TX :-	
Fund 20P HC25U	1.85
Pairs FM	3.25
Pairs AM	3.10

LCDs

3.5 digit	9.45
4 digit	8.95
5 digit	8.95

CRYSTALS

32.768 kHz	2.70
100kHz	3.85
455kHz	5.00
1.0MHz	3.00
3.2768MHz	2.70
4.000MHz	2.00
4.19439MHz	2.30
6.5536MHz	2.10
10.0MHz	2.50
10.6985MHz	2.50
10.7015MHz	2.50
10.245MHz	2.50
10.7MHz	3.00
11.52MHz	2.50
100MHz	3.00

LEDs

5MM RED	0.12
3MM RED CLEAR	0.15
3MM RED	0.15
2.5 x 5MM RED	0.17
5MM GREEN	0.15
3MM GN CLEAR	0.16
3MM GREEN	0.16
2.5 x 5MM GN	0.20
5MM YELLOW	0.15
3MM YELLOW CL	0.16
3MM YELLOW	0.18
2.5 x 5MM YE	0.20
5MM ORANGERED	0.20
5MM ORA CL	0.29
3MM ORANGERED	0.19
2.5 x 5MM ORA	0.24
5MM INFRA RED	0.56
BPM41 IR DET	1.51
IR OPT CPLR	1.44
5MM CLIP	0.04

SCHOTTKY DIODE BAL

MIXERS (SBL1=MDL08)	
SBL1-1-500MHz	4.25
SBL1-8-1-200MHz	4.55
SBL1-X-10-100MHz	5.75
SRA1-5-500MHz	8.45
SRA1-1-1-500MHz	9.25
SRA1H-5-500MHz	13.35
SRA3-0.25-200MHz	10.25

TRANSISTORS

BA102	0.30
BA121	0.30
ITT210	0.30
BB204B	0.36
BB105B	0.36
BB109	0.27
MM125	1.05
BB212	1.95
KV1210	2.45
KV1211	1.75
KV1226	1.95
KV1225	2.75
KV1215	2.55
KV1225	2.75

SWITCHING AND PIN DIODES

IN6263	0.62
BA182	0.19
BA244	0.17
BA379	0.35
TDA1061	0.95

SHOTTKY DIODES

IN6263	0.62
BA182	0.19
BA244	0.17
BA379	0.35
TDA1061	0.95

SIGNAL DIODES & RECTIFIERS

IN4148	0.06
IN4001	0.06
IN4002	0.07
IN5402	0.15
QA91	0.07
AAL12	0.25



MUSICAL MICRO 24 TUNE DOOR BELL



BUILD THE WORLD FAMOUS CHROMA-CHIME

Give your friends a warm welcome. Yes, think how delighted and amazed they will be to hear the musical Chroma-Chime play when they press your button!

The Chroma-Chime uses a microcomputer to play 24 well-known tunes. The kit is simplicity itself for ease of construction. Absolutely everything needed is supplied, including:

- ★ Resistors, Capacitors, Diodes, Transistors, I.C. Socket and all hardware
- ★ Texas Instruments TMS 1000 microcomputer
- ★ Comprehensive kit manual with full circuit details
- ★ Ready drilled and legended PCB included

ONLY £11.95 + 75p p&p UK ONLY

Plays 24 well-known tunes including: Star Spangled Banner, William Tell Overture, Greensleeves, Rule Britannia, Colonel Bogey, Oh come all ye faithful, plus many other popular tunes.

- ★ No previous microcomputer experience necessary
- ★ All programming retained is on chip ROM
- ★ Fully guaranteed
- ★ Ideal present any time

TMS 1000N

-MP0027A Micro-computer chip available separately if required. Full 24 tune spec device fully guaranteed.

This unique chip can be used not only for electronic door chimes but for other projects requiring musical output.

£4.95

Car Horns Musical Boxes Alarms Amusement Machines Public Address etc. For 200 separately.

ALL CHROMATRONICS PRODUCTS SUPPLIED WITH MONEY BACK GUARANTEE PLEASE ALLOW 7-21 DAYS FOR DELIVERY

Please send me: PW/11/80
 TO: CHROMATRONICS, RIVER WAY, HARLOW, ESSEX.
 Telephone (0279) 418611
 NAME _____
 ADDRESS _____

 I enclose cheque/PO value £ _____
 or debit my ACCESS/BARCLAYCARD account no. _____

 Signature _____

CHROMATRONICS

RST VALVE MAIL ORDER CO.

Climax House
159 Fallsbrook Road, London SW16 6ED
SPECIAL EXPRESS MAIL ORDER SERVICE

AZ31 1-10	EM87 1-50	PY81 0-84	6AN5 4-74	607 2-20
CL33 2-00	EN91 3-50	PY82 0-80	6AN8A 3-45	65A7 1-45
DY86/7 0-84	EY51 1-75	PY83 0-70	6AQ5 0-96	65C7 1-50
DY802 0-84	EY86 0-84	PY88 0-88	6AR5 1-98	65J7 1-60
EB8CC 3-36	EY88 1-75	PY800A 1-80	6AS6 4-98	65K7 1-30
E180F 8-40	EY500A 1-94	PY800 0-84	6AS7GA 6-75	65L7GT 2-68
E180F 14-47	E280 0-84	PY801 0-84	6AT6 0-85	65N7GT 1-60
E180F 14-47	E281 0-84	QV02-6 12-56	6AU5GT 4-32	65S7 1-80
EABC80 1-20	GY501 2-75	QV03-10 5-80	6AU6 1-08	65G7M 2-80
EB91 0-82	G232 1-25	QV03-20A 17-50	6AW8A 3-39	6U8 0-80
EBF80 0-50	G233 4-00	QV06-40A 36-34	6B7 1-80	6V8GT 1-60
EBF89 0-85	G234 2-50	QV03-12 4-48	6B8 1-75	6X4 1-20
EC91 7-56	G237 4-00	R18 4-25	6BA6 1-00	6X5GT 0-85
ECC33 3-50	KT61 3-50	R19 1-20	6BA7 5-12	7C5 2-95
ECC35 3-50	KT66 10-00	SP41 6-00	6BE6 1-08	7C6 2-28
ECC81 0-88	KT77 8-00	SP41 6-00	6BH6 1-52	7S7 2-25
ECC82 0-72	KT88 12-00	SP19 2-00	6BQ7 1-08	12A7 1-20
ECC83 0-88	N78 9-00	SP19 2-00	6BN6 1-65	12A7T 0-72
ECC85 1-20	OA2 1-60	U19 13-75	6BQ7A 3-72	12AU7 0-88
ECC88 1-90	OB2 2-55	U19 13-75	6BR7 4-00	12AX7 0-72
EC91 8-93	OC3 1-92	U25 2-16	6BR8 1-75	12BA6 2-19
ECH80 1-50	OD3 1-92	U26 1-44	6BS7 4-00	12BE6 2-43
ECH35 2-00	PC66 1-40	U37 9-00	6BW6 4-00	12BY7 1-80
ECH42 1-15	PC88 1-40	UABC80 1-25	6BW7 1-52	12BY7A 2-10
ECH81 1-20	PC92 1-28	UBF89 1-20	6BZ6 2-37	12HG7 4-77
ECL80 1-00	PC97 1-20	UCH42 1-20	6C4 0-88	30FL1/2 1-12
ECL82 1-00	PC900 1-20	UCH81 2-32	6C6 1-75	30P4 1-20
ECL83 1-50	PCF80 1-00	UCL82 1-04	6CB6A 2-49	30P19 1-20
ECL86 1-20	PCF82 1-40	UCL83 1-44	6CD6GA 5-07	30PL13 1-80
EF37A 3-50	PCF86 1-60	UF89 1-44	6CH6 8-50	30PL14 1-88
EF39 2-75	PCF801 1-60	UL41 2-50	6CL6 3-72	75C1 2-38
EF41 2-00	PCF802 1-90	UL84 1-20	6CW4 7-88	85A2 2-10
EF42 2-00	PCF805 1-60	UV41 1-25	6D6 1-75	90C1 2-35
EF50 1-50	PCF88 1-08	UV85 1-50	6D05 5-94	15082 2-90
EF54 5-00	PCH200 1-80	VR105/30 1-92	6EA8 4-00	15082T 2-85
EF55 2-50	PCL82 1-00	VR150/30 1-92	6EH5 1-85	15024 2-30
EF80 0-80	PCL83 2-00	Z759 16-80	6F6 1-75	57C8 27-50
EF86 1-52	PCL84 1-00	Z803U 7-90	6G6 2-67	805 20-00
EF91 1-80	PCL85 1-08	ZD21 3-50	6H6 1-80	807 3-75
EF92 1-50	PCF88 1-08	3B28 16-80	6HS6 3-77	811A 15-93
EF183 0-80	PCL805 1-08	4CX250B 27-50	6J5 2-50	812A 15-88
EF184 0-84	PD500 3-60	5R4QY 2-00	6J7 2-50	866A 8-85
EH90 1-40	PFL200 1-80	5U4G 1-52	6J86A 4-56	872A 15-67
EL32 1-50	PL36 1-20	5V4G 1-82	6J86C 5-58	931A 14-76
EL33 3-50	PL81 1-20	5Y3GT 0-85	6K4N 1-25	2050 6-96
EL34 2-50	PL82 1-20	5Z3 1-50	6K6GT 1-30	5783 3-75
EL36 1-60	PL83 1-08	5Z4GT 1-50	6K7 1-50	5814A 3-72
EL81 2-50	PL84 1-08	6/3DL2 1-56	6K8 1-75	5842 12-09
EL84 1-00	PL504 1-40	6A87 1-50	6KD6 6-36	6080 6-85
EL86 2-50	PL508 1-80	6AH6 4-71	6L6G 2-50	6146A 5-96
EL91 7-14	PL509 3-20	6AK5 3-80	6L6GC 2-50	6146B 7-06
EL95 1-32	PL519 3-20	6AL5 0-82	6L7 1-50	6883B 11-19
ECL360 8-50	PL802 1-80	6AM6 1-80	6LQ6 6-72	6973 3-87
EM81 1-00	PY33 1-10			7360 9-96
				7586 10-14
				7587 17-49

Open daily to callers: Mon-Fri 9 a.m.-5 p.m.
 Valves, Tubes and Transistors - Closed Saturday
 Terms C.W.O. only. Tel. 01-87 7242-7.
 Quotations for any types not listed S.A.E.
 Prices excluding VAT add 15% Post and Packing 30p per order

Telex 846708 Prices correct when going to press

L.B. ELECTRONICS

SPECIAL OFFER: -5" LED displays. FND500 Full spec. 50p each, larger quantities P.O.A. P/P 25p.

ASTEC UM1111 E36 Modulators (Pull Outs) 65p each, P/P 25p.

JUST ARRIVED: Battery eliminator 6V 200mA, brand new 95p each, P/P 35p. 5K Multi turn trim pots, PCB Mounting, pack of 14 £2.50. P/P 25p.

CAPACITOR SCOOP: 1600uf at 10V, 160uf at 25V axial lead 24 at £1.00 (mixed), P/P 25p.

GIVE AWAY: 22 pin low profile DIL socket, gold plated 12p each, 10 at £1.00. P/P 25p.

PEWEC: Mini fans 80mm x 80mm approx. 115V £4.50. P/P £1.00.

TANTALUM CAPACITORS: 4.7uf at 25V, 14 for £1.00. P/P 25p.

LEDS: -2" Red 12p, TIL209 10p, OCP70 25p, 2114 (450NS) £4.50, 2526 (Character Generator) £2.95. 2716 Eprom (single rail full spec.) £9.95 P/P 25p.

★ ALL I.C.'s POSTAGE AND PACKING 25p ★
★ ALL PRICES INCLUSIVE OF V.A.T. ★
★ MANY SURPLUS COMPUTER BARGAINS ★
ACCESS AND BARCLAYCARD ACCEPTED

L.B. ELECTRONICS

11 Hercies Road, Hillingdon, Middlesex UB10 9LS.
 Telephone: (89) 55399.

£2 BARGAIN CAPACITOR PACKS

100-Mullard C280/C281 from .01 µF to 1.5 µF at 250V/WV; Good mixed selection and 25 mixed electrolytics from 10 µF to above 500 µF. Mixed voltage working.

All for **£2.00 plus P&P.**

AERIAL BOOSTERS

Aerial amplifiers can produce remarkable improvement on the picture and sound in fringe or difficult areas.

B45 - For Mono or Colour this is tunable over complete UHF television band.

B11 - For stereo or standard VHF/FM radio.

Next to the set fitting. Price **£6.70 each.**

Signal Injectors with (pre-set) variable AF, which emits RF harmonics into the UHF band. Protected up to 300 volts DC. Complete with leads **£5.70 each.**

All Prices Include VAT at 15%. P & P per Order 30p. S.A.E. for Leaflets. Access Cards.

ELECTRONIC MAILORDER LTD,

62 Bridge St, Ramsbottom, via Bury, Lancs. BL0 9AGW.
 Tel Rams (070 682) 3036.

14 Practical Wireless, November 1980

www.americanradiohistory.com



The biggest name in solder worldwide

Products that help you make a better job of it.



Arax Multicore Solder.
Economy pack for general non-electrical use. Replaces solid wire and stick solder. (B.S. 219 Grade L). Econopak 200g reel of 3mm dia. Size 16A. **£4.14 per reel.**



Handy Dispensers		Per pack
PC115	for printed circuits.	£1.15
SV130	for radio and TV repairs.	£1.61
AR140	for non-electrical applications, except aluminium	£1.38
SS160	for stainless steel and silver jewellery.	£2.53
19A	for printed circuit boards – non-corrosive.	96p
AL150	for aluminium.	£1.93
BCA16	solder cream for stainless steel, jewellery and household products (non-electrical).	£3.22
BCR10	solder cream for electronic and electrical use.	£1.38
BCA14	all purpose solder cream, non-electrical jointing and repairing.	£1.38



Econopak.
Ersin Multicore 5-core solder. Contains non-corrosive flux for electrical applications. 1.2mm dia. 200g Econopak. Size 13A. **£4.14 per reel.**



Toolbox Reels.
Multicore 5-core solder for general use. Suitable for electrical joints (B.S. 219 Grade C). 40/60 tin/lead. 1.6mm dia. Size 3. **£3.91 per reel.**
Savbit.
Multicore 5-core solder for radio, TV and similar work. Reduces copper erosion. Suitable for service engineers and manufacturers using small quantities of solder. 1.2mm dia. Size 12. **£3.91 per reel.**



Metal Soldering.
Arax Multicore 4-acid-core solder for metal fabrication (not aluminium) and repairs. 40/60 tin/lead. 1.6mm dia. Size 11. **£3.91 per reel.**



Multicore Wick.
Multicore solder-wick for removing solder from virtually any joint. 17mm dia. Size AB10. **£1.38 per reel.**

Tip Kleen.
Multicore Tip Kleen. Soldering-iron tip wiping pad. Replaces wet sponges. (Should not be used above 350°C). **81p per pack.**




TV and Radio Soldering.
Savbit Multicore for radio, TV and similar work. Reduces copper erosion. 1.2mm dia. Size 5. **90p per handy dispenser.**
Econopak.
General purpose solder suitable for all electrical joints. 40/60 alloy. 1.2mm dia. Size 6. **58p per handy plastic dispenser.**



Aluminium Soldering.
Alu-Sol Multicore 4-core solder for soldering most types of aluminium. No extra flux needed. 1.6mm dia. Size 4. **£11.50 per reel.**



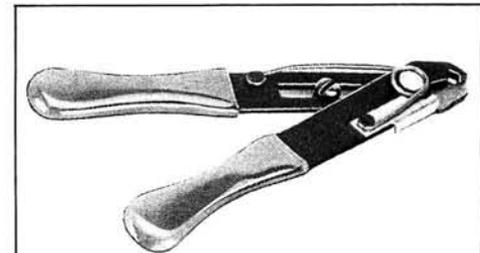Soldering Flux Pastes.
Multicore soldering flux paste. Extra fast, non-corrosive, rosin-flux for electrical and general purpose soldering.
Rosin R.F.10. 35g net. **69p per pack.**
Multicore soldering flux paste for soft metals (except aluminium) and stainless steel. Non-electrical.
Arax A.F.14. 35g. **69p per pack.**



Wire Stripper and cutter.
Wire stripper and cutter with precision ground and hardened steel jaws. Adjustable to most wire sizes. With handle locking-catch and easy-grip plastic covered handles.
Ref: 9. **£2.69 per pair.**

Bib Hi-Fi Accessories Ltd., (Solder Division), Kelsey House, Wood Lane End, Hemel Hempstead, Hertfordshire HP2 4RQ. Telephone: (0442) 61291.

All recommended retail prices shown are inclusive of VAT. If you have difficulty in obtaining any of these products send direct with 40p for postage and packing. For free colour brochure send S.A.E.

CHOOSE FROM OVER
20 TOP QUALITY
MODULES

HIGHEST QUALITY

build a "tailor made"


BI-PAK Audio Modules are famous for their variety, quality of design and ruggedness. For over 10 years BI-PAK have been suppliers to manufacturers of high quality audio equipment throughout the world – to date, well over 100,000 modules have been sold – this is why discerning amateur enthusiasts insist on using BI-PAK modules in their equipment. They know that every item is designed and tested to do the job for which it is intended before it leaves the factory. Whatever you are building, there is a kit or module

in the BI-PAK range to suit your every need from 5 watts to 125 watts, from amplifiers to equalisers. AND if you cannot see what you require in this advertisement, just write or phone us – we are waiting to help you!

WORLDWIDE
SUPPLIERS OF AUDIO
EQUIPMENT FOR
OVER 10 YEARS

DESIGNED AND MADE
IN BRITAIN

COMPLETELY
GUARANTEED

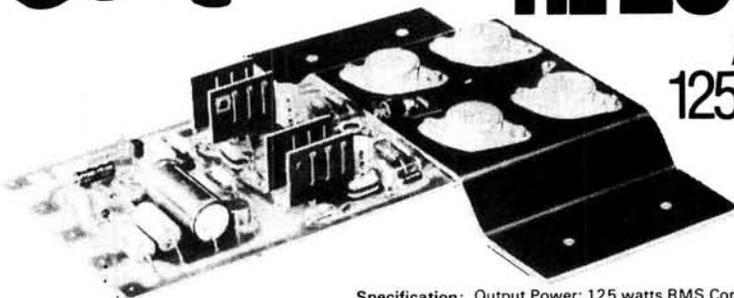

AL250 POWER AMPLIFIER 125 Watts r.m.s.

SPECIALLY DESIGNED
FOR USE IN – DISCO
UNITS, P.A. SYSTEMS,
HIGH POWER HI-FI,
SOUND REINFORCE-
MENT SYSTEMS

Specification: Output Power: 125 watts RMS Continuous. Operating voltage: 50-80. Loads: 4-16 ohms. Frequency response: 25Hz-20kHz Measured at 100 watts. Sensitivity for 100 watts output at 1kHz: 450mV. Input impedance: 33K ohms. Total harmonic distortion: 50 watts into 4 ohms: 0.1%, 50 watts into 8 ohms: 0.06%. S/N ratio: better than 80dBs. Damping factor: 8 ohms: 65. Semiconductor complement: 13 transistors, 5 diodes. Overall size: Heatsink width 190mm, length 205mm, height 40mm.

ONLY
22.54
£

AMPLIFIERS

AL10. 3 watt Audio Amplifier Module 22-32v supply	£3.63
AL20. 5 watt Audio Amplifier Module 22-32v supply	£4.11
AL30A. 7-10 watt Audio Amplifier Module 22-32v supply	£4.78
AL60. 15-25 watt Audio Amplifier Module 30-50v supply	£5.92
AL80. 35 watt Audio Amplifier Module 40-60v supply	£9.28
AL120. 50 watt Audio Amplifier Module 50-70v supply	£15.11

AL250. 125 watt Audio Amplifier Module 50-80v supply	£22.54
--	--------

STEREO PRE-AMPLIFIERS

PA12. Supply voltage 22-32v input sensitivity 300mv. Suit: AL10/AL20/AL30	£9.83
PA100. Supply voltage 24-36v inputs: Tape, Tuner, Mag P.U. Suit: AL60/AL80	£20.30
PA200. Supply voltage 35-50v inputs: Tape, Tuner, Mag P.U. Suit: AL80/AL120/AL250	£20.98

BI-KITS

STA5. 5 watts per channel Stereo Amplifier Kit consisting of: 2xAL20 amplifiers, 1xPA12 pre-amplifier, 1xPS12 power supply, 1x2036 transformer and necessary wiring diagram **£22.14**

STA10. 10 watts per channel Stereo Amplifier Kit consisting of 2xAL30 amplifiers, 1xPA12 pre-amplifier, 1xPS12 power supply, 1x2036 transformer and necessary wiring diagrams **£23.72**

STA15. 15 watts per channel Stereo Amplifier Kit consisting of: 2xAL60 amplifiers, 1xPA100 pre-amplifier, 1xSPM80 power supply, 1x2034 transformer, 2x coupling capacitors for 8 ohms 470mfd 30v and necessary wiring diagram **£42.27**

BI-KITS

STA25. 25 watts per channel Stereo Amplifier Kit consisting of: 2xAL60 amplifiers, 1xPA100 pre-amplifier, 1xSPM120/45 power supply, 1x2040 transformer, coupling capacitors for 8 ohms 470mfd 45v, 1xreservoir capacitor 2200mfd 100v and necessary wiring diagram **£46.58**

STA35. 35 watts per channel Stereo Amplifier Kit consisting of: 2xAL80 amplifiers, 1xPA100 pre-amplifier, 1x2035 transformer, 2x coupling capacitors 470mfd at 50v for 8 ohms, 1x reservoir capacitor 2200mfd 100v and necessary wiring diagram **£52.62**

BI-KITS

STA50. 50 watts per channel Stereo Amplifier Kit consisting of: 2xAL120 amplifiers, 1xPA200 pre-amplifier, 1x2041 transformer, 2xcoupling capacitors 1000mfd 63v, 1xreservoir capacitor 3300mfd 100v and necessary wiring diagram **£68.87**

STA100. 100 watts per channel Stereo Amplifier Kit consisting of: 2xAL250 amplifiers, 1xPA200 pre-amplifier, 2xSPM120/65 power supplies, 2x2041 transformers, 2xcoupling capacitors 1000mfd 100v and necessary wiring diagram **£97.38**

hi-fi system with bi-pak!

MONO PRE-AMPLIFIERS

MM100. Supply voltage 40-65v inputs: Tape, Mag P.U. Microphone Max output 500mv **£14.29**

MM100G. Supply voltage 40-65v inputs: 2 Guitars, Microphones Max output 500mv **£14.29**

POWER SUPPLIES

PS12. 24v Supply. Suit: 2xAL10, 2xAL20, 2xAL30 & PA12/S.450 **£1.90**

SPM80. 33v Stabilised supply. Suit: 2xAL60, PA100 to 15 watts **£5.57**

SPM120/45. 45v Stabilised supply. Suit: 2xAL60, PA100 to 25 watts **£7.34**

SPM120/55. 55v Stabilised supply. Suit: 2xAL80, PA200 **£7.34**

SPM120/65. 65v Stabilised supply. Suit: 2xAL120, PA200, 1xAL250 **£7.34**

SG30. 15-0-15 Stabilised power supply for 2xGE100MK11 **£4.37**

MISCELLANEOUS

MPA30. Stereo Magnetic Cartridge Pre-Amplifier - input 3.5mv Output 100mv **£3.76**

S.450. Stereo FM Tuner Supply Voltage 20-30v - Varicap tuned **£29.40**

STEREQ 30. Complete 7 watt per channel Stereo Amplifier Board - includes amps, pre-amp, power supply, front panel, knobs etc - requires 2050 Transformer **£24.25**

BP124. 5 watt 12v max. - Siren Alarm Module **£4.43**

GE100MK11. 10 channel mono-graphic equaliser, complete with sliders and knobs **£26.45**

VPS30. Variable regulated stabilised power supply 2-30v 0-2 amps **£8.74**

PS250. Consists - 1 capacitor & 4 diodes for constructing unbalanced power supply for AL250 to 125 watts **£3.78**

TRANSFORMERS

2034. 1.7 amp 35v. Suit SPM80 **£5.40**

2035. 2 amp 55v. **£6.35**

2036. 750mA 17v. Suit PS12 **£3.20**

2040. 1.5 amp 0-45v-55v. Suit: SPM120/45, SPM120/55v **£5.20**

2041. 2 amp 0-55v-65v. Suit: SPM120/55, SPM120/65v **£6.80**

2050. 1 amp 0-2v. Suit Stereo 30 **£3.25**

1725. 150mA 15-0-15v. Suit SG30 **£1.77**

ACCESSORIES

139. Teak Cabinet. Suit: Stereo 30, 320x235x81mm **£6.45**

140. Teak Cabinet. Suit: STA15, 425x290x95mm **£9.77**

FP100. Front Panel for PA100 & PA200 **£1.80**

BP100. Back Panel for PA100 & PA200 **£1.60**

GE100FP. Front Panel for one GE100MK11 **£1.75**

2240. Kit of parts including Teak Cabinet, chassis sockets, knobs, to build 15 watt stereo amplifier **£19.95**

Full data sheets are available FREE on request, please enclose a S.A.E.

Access and Barclaycards accepted - just telephone our Orderline - Ware (STD 0920) 3182.

All prices include V.A.T., add 50p. postage per order. Terms: C.W.O., cheques,

Postal Orders payable to Bi-Pak at address below.

BI-PAK

SEMICONDUCTORS

Dept. PW11, P.O. BOX 6, WARE, HERTS.

Tel: Ware (STD 0920) 3442. Telex: 817861.

Giro No. 388006.

Visit our shop at: 3, Baldock St, Ware, Herts.



NEW PRACTICAL ELECTRONICS PROJECT 125 WATT POWER AMP KIT

SPECIFICATIONS

Max. Output power 125 watt RMS
 Operating voltage (DC) 50-80 Max.
 Loads 4-16 ohms
 Frequency response Measured at 100 watts 25Hz-20kHz
 Sensitivity for 100 watts 400mV @ 47K
 Typical T.H.D. @ 50 watts 4 ohms load 0.1 %
 Dimensions 205 x 90 and 190 x 36 mm

The P.E. power amp kit is a module for high power applications—disco units, guitar amplifiers, public address systems and even high power domestic systems. The unit is protected against short circuiting of the load and is safe in an open circuit condition. A large safety margin exists by use of generously rated components, the

output stage uses four 115 watt transistors normally only two would be used, result, a high powered rugged unit. The PC Board is backprinted, etched and ready to drill for ease of construction, and the aluminium chassis is preformed and ready to use, supplied with all parts and circuit diagrams.

125 watt power amp kit **£9.50** plus £1.00 p&p

ACCESSORIES £1.00 plus 20p p&p
 Suitable L.S. coupling electrolytic

Suitable Mains Power Supply Unit **£7.50** plus £2.75 p&p
 sufficient for one power amp


ACCESSORIES available only when purchasing packs.



AS FEATURED IN
PRACTICAL ELECTRONICS
 OCTOBER ISSUE

DIY STEREO BARGAIN PACKS FEATURING FAMOUS BUILT MULLARD PREAMP MODULES

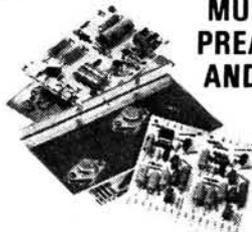MULLARD STEREO PREAMP MODULES AND TWO 12 WATT POWER AMP KITS.




In easy to build form P.C.B. s backprinted, etched and drilled ready to use.

BUILD A 12 WATTS PER CHANNEL STEREO AMPLIFIER ACCESSORIES AND L.S. KIT EXTRA (not available separately) **£6.00**

DIY PACK 1 2 x power amp kits LP1182/ preamp module, suitable for ceramic and auxiliary inputs. **£6.00** plus £1.10 p&p

DIY PACK 2 2 x power amp kits LP1184 preamp module suitable for magnetic ceramic and auxiliary inputs. **£8.50** plus £1.15 p&p

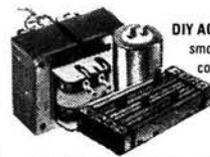DIY SPEAKER KIT Two 8" x 5" approx. 4 ohm bass. **£3.50** plus £1.70 p&p



DIY ACCESSORIES Mains transformer smoothing capacitor rectifier 4 x slider controls, for base, treble and volume.

£3.00 plus £1.60 p&p

ACCESSORIES: Available only at time of purchase of Bargain Packs

12 + 12 WATT AMPLIFIER KIT

NOTE: for use with 4 to 8 ohms speakers.

With up-to-the-minute features. To complete you just supply screws, connecting wire and solder. Features include din input sockets for ceramic cartridge, microphone, tape or tuner. Outputs—tape, speakers and headphones. By the press of a button it transforms into a 24 watt mono disco amplifier with twin deck mixing. The kit incorporates a Mullard LP1183 pre-amp module, plus 2 power amplifier assembly kits and mains power supply. Also featured 4 slider level controls, rotary bass and treble controls and 6 push button switches. Silver finish fascia panel with matching knobs. Easy to assemble teak simulate cabinet and ready made metal work. For further information instructions are available price 50p. Free with kit. Size 9 1/4" x 8 3/4" x 4" approx.

£13.95 plus £2.55 p&p

NOTE: for use with 4 to 8 ohms speakers.

BSR chassis record player deck with manual set down and return, complete with stereo ceramic cartridge. **£8.50** plus £2.75 p&p when purchased with amplifier available separately **£10.50** plus £2.75 p&p.



TWO WAY SPEAKER KIT. 2 Phillips 8" approx speakers **£4.75** per stereo pair plus £1.50 p&p when purchased with amplifier available separately **£6.75** plus £1.50 p&p.

ALSO AVAILABLE Stereo magnetic pre-amp conversion kit all components including P.C.B. to convert your ceramic input on the 12 + 12 amp to magnetic. **£2.00** when purchased with kit featured above. **£4.00** separately inc. p&p.

BSR Manual single play record deck with auto return and cueing lever. Fitted with stereo ceramic cartridge 2 speeds with 45 rpm spindle adaptor ideally suited for home or disco use.



£12.25 OUR PRICE plus £2.75 p&p

PHILLIPS RECORD PLAYER DECK GC037

Size approx 15 1/4" x 12 1/2"

Hi Fi record player deck, 2 speed, damped cueing, auto shut-off, belt drive with floating sub chassis to minimise acoustic feedback. Complete with GP401 stereo magnetic cartridge—LIMITED STOCK. UNBEATABLE OFFER AT



£27.50 complete plus £2.75 p&p

OFFER! SAVE MONEY by purchasing 12 + 12 amp kit, BSR record deck and speaker kit together for only **£25.50** p&p £4.50.

PRACTICAL ELECTRONICS CAR RADIO KIT **£10.50** (Constructors pack 7) plus £1.75 p&p

2 Wavebands MW and LW



- * Easy to build * 5 push button tuning
- * Modern styling design * All new unused components
- * 6 watt output * Ready etched & punched P.C.B.
- * Incorporates suppression circuits * Now with tape input socket

All the electronic components to build the radio, you supply only the wire and solder as featured in the Practical Electronics March issue. Features: Pre-set tuning with five push button options, black illuminated tuning scale, with matching rotary control knobs, one, combining on/off volume and tone-control, the other for manual tuning, each set on wood simulated fascia.

The P.E. Traveller has a 6 watts output, neg ground and incorporates an integrated circuit output stage, a Mullard IF module LP1181 ceramic filter type, pre-aligned and assembled and a Bird pre-aligned push button tuning unit. The radio fits easily in or under dashboards. Complete with instructions.


CONSTRUCTORS PACK 7A

Suitable stainless steel fully retractable locking aerial and speaker (approx. 6" x 4") is available as a kit complete **£1.95** p&p £1.00

Pack 7A may only be purchased at the same time as Pack 7.

NOTE: Constructor's pack 7A sold complete with radio kit **£15.20** including p&p.

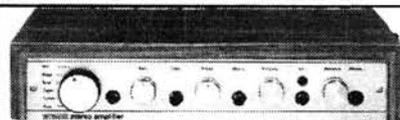FEATURED PROJECT IN PRACTICAL ELECTRONICS.



30 + 30 WATT STEREO AMPLIFIER BUILT AND TESTED

Viscount IV unit in teak simulate cabinet silver finished rotary controls and pushbuttons with matching fascia, red mains indicator and stereo jack socket. Functions switch for mic magnetic and crystal pickups, tape and auxiliary. Rear panel features fuse holder. DIN speaker and input socket 30 + 30 watts. RMS 60 + 60 watts peak for use with 4 to 8 ohm speakers. Size 14 1/4" x 10" approx.

READY TO PLAY **£32.90** plus £3.30 p&p



323 EDGWARE ROAD, LONDON W2
 21C HIGH STREET, ACTON W3 6NG

ACTON: Mail Order only. No callers
 ALL PRICES INCLUDE VAT AT 15 %
 All items subject to availability. Price correct at 1.9.80 and subject to change without notice.

For further information send for instruction booklet.

NOTE: 20p plus stamped addressed envelope.

Persons under 16 years not served without parent's authorisation.

BARGAIN OFFER!!



ARISTON PICK UP
 Ariston pick-up arm manufactured in Japan. Complete with headshell. Listed price over £30.00 **£11.95** plus £2.50 p&p


100 WATT MONO DISCO AMPLIFIER

Brushed aluminium fascia and rotary controls. Size approx 14" x 4" x 10 1/2". Five vertical slide controls, master volume, tape level, mic level, deck level. PLUS INTER DECK FADER for perfect graduated change from record deck No. 1 to No. 2, or vice versa. Pre fade level controls (PRL) lets YOU hear next disc before fading it in. VU meter monitors output level. Output 100 watts RMS 200 watts peak. **£76.00** plus £4.00 p&p



50 WATT MONO DISCO AMPLIFIER

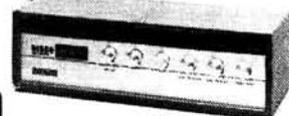Size approx 13 1/4" x 5 1/4" x 6 3/4". 50 watts rms. 100 watts peak output. Big features include two disc inputs, both for ceramic cartridges, tape input and microphone input. Level mixing controls fitted with integral push-pull switches. Independent bass and treble controls and master volume.



£30.60 plus £3.20 p&p



comment...

Open Channel

THE long-awaited Home Office Green Paper on the UK version of Citizens' Band—*Open Channel*, a Discussion Document—has proved to be something of a non-event. It devotes fourteen pages to saying what could equally well be said in about four, the sum total of which is:

1. To minimise interference with domestic radio and TV, a frequency just above 928MHz is favourite. It says that some other countries are looking at CB in the same band, but neglects to point out that they are also looking at the effects on the human body of radiation at those frequencies. There appears to be a definite link with cataracts of the eye, a significant point when considering the use of hand-portable transceivers with integral microphones.
2. An ultimate allocation of 40 channels at 25kHz spacing is envisaged, though the question of what modulation mode should be used is ignored completely.
3. A range of 15km (just over 9 miles) is thought adequate and desirable. However, the paper then goes on to quote test results from several sources to prove that in practice, ranges are likely to be between 10 and 50 per cent of this distance.
4. The Home Office intends to wash its hands of any involvement whatsoever in trying to control in-band interference, so the jammers, the music players, the heavy breathers, etc., etc., will have a free rein!

Send for your copy of *Open Channel* to: Officer in Charge, Home Office, Supply and Transport Branch, Royston Road, Cambridge CB2 8PN, and get your comments in to the Radio Regulatory Department of the Home Office by November 30 at the latest.

THIS month we are introducing several changes and new features to *Practical Wireless*, largely as a result of suggestions and requests from our readers. And there will be more new features coming into the magazine over the next few months. We hope that they will turn out to be just what you wanted, and would like to say a big thank you to all who took the trouble to send us their views.

For an explanation of the new "Rating" system for constructional articles, see below.

I AM sorry that some readers writing to us with queries in the past few months have had a very long wait for answers. Two of our technical staff recently decided that journalism was not for them, and have left us to resume their careers in industry, leaving us very short-staffed. We have now filled the gaps, and hope that we shall be well on the way to clearing the backlog of letters by the time this issue is published.



services

QUERIES

While we will always try to assist readers in difficulties with a *Practical Wireless* project, we cannot offer advice on modifications to our designs, nor on commercial radio, TV or electronic equipment. Please address your letters to the Editor, "*Practical Wireless*", Westover House, West Quay Road, Poole, Dorset BH15 1JG, giving a clear description of the problem and enclosing a stamped self-addressed envelope. Only one project per letter please.

Components for our projects are usually available from advertisers. For more difficult items, a source will be suggested in the "Buying Guide" box included in each constructional article.

SUBSCRIPTIONS

Subscriptions are available to both home and overseas addresses at £11.80 per annum, from "*Practical Wireless*" Subscription Department, Room 2813, King's Reach Tower, Stamford Street, London SE1 9LS. Airmail rates for overseas subscriptions can be quoted on request.

BACK NUMBERS AND BINDERS

Limited stocks of some recent issues of *PW* are available at 95p each, including post and packing to addresses at home and overseas.

Binders are available (Price £4.30 to UK addresses and overseas, including post and packing) each accommodating one volume of *PW*. Please state the year and volume number for which the binder is required.

Send your orders to **Post Sales Department, IPC Magazines Ltd., Lavington House, 25 Lavington Street, London SE1 0PF**. All prices include VAT where appropriate. Please make cheques, postal orders, etc., payable to IPC Magazines Limited.

PROJECT COST

The approximate cost quoted in each constructional article includes the box or case used for the prototype. For some projects the type of case may be critical; if so this point will be mentioned in the Buying Guide.

CONSTRUCTION RATING

Each constructional project will in future be given a rating, to guide readers as to its complexity:

Beginner

A project that can be tackled by a beginner who is able to identify components and handle a soldering iron fairly competently. Generally this category will be used for simple projects, but sometimes for more complicated ones of wide appeal. In this case, construction and wiring will be dealt with in some detail.

Intermediate

A project likely to appeal to a wide range of constructors, and requiring only basic test equipment to complete any tests and adjustments. A fair degree of experience in building electronic or radio projects is assumed.

Advanced

A project likely to appeal to an experienced constructor, and often requiring access to workshop facilities and test equipment for construction, testing and alignment. Constructional information will generally be limited to the more critical aspects of the project. Definitely not recommended for a beginner to tackle on his own.

NEWS NEWS NEWS

Amateur Radio Supplies

As from 1 August 1980, a new amateur radio communications shop has been opened at Kempston near Bedford.

The new company, named Bedford Audiocom, at present hold agencies for Yaesu, FDK, Jaybeam and Bantex, and others will follow. Bedford Audiocom intend to specialise in mobile and portable rigs and a wide range of aerials and accessories.

Further information from: *Bedford Audiocom, 76 Bedford Road, Kempston, Beds. MK42 8BB. Tel: Bedford (0234) 854133.*

New Component Centre

A new component shop has recently been opened by Riscomp Ltd. in order to supply a wide range of components, test equipment and books to the amateur and enthusiast.

In addition, the full range of audio modules from Autona Ltd. will be stocked.

Opening hours are, Monday to Saturday 9.00am to 5.00pm, closed all day Wednesday.

Riscomp Ltd., 21 Duke Street, Princes Risborough, Bucks. Tel: (084 44) 6326.

Solent Audio 80

Hamilton Electronics Ltd. of Southampton are the host exhibitor at Solent Audio 80. which is being held on 25 and 26 October.

Solent Audio is now established as a major regional Hi-Fi show and this year is supported by thirty leading manufacturers.

Three complete floors have been booked at the Post House Hotel, Southampton, and each exhibitor will have an individual demonstration room. Representatives of the manufacturers will be in attendance throughout the show.

Further details from: *Hamilton Electronics Ltd., 35 London Road, Southampton SO1 2AD. Tel: (0703) 28622.*

BANDSTAND
25p ED 11



Giving Two-Way Radio Its Voice

Bandstand Monthly

"Bandstand", the monthly publication of a group promoting the legalisation of CB Radio, is having to increase its cover price.

I understand from its Editor, Mike Evans, that the circulation of "Bandstand" is increasing very nicely.

The new price for "Bandstand" is 25p per copy, or a 12-month subscription for £4.44 (1st Class Post) and £4.20 (2nd Class Post). Applications should be sent to: *B.M. Bandstand, London WC1V 6XX.*

Special Event

Ormskirk Amateur Radio Club will be operating a special amateur radio station GB2MS, for the Jamboree on the Air, to be held on 18 and 19 October 1980, from the 8th Sefton East Scout Group HQ, United Reformed Church, Horthway, Maghull, Nr Liverpool.

Operation will be on all h.f. bands between 1300 and 1700, on both days. It is hoped to interest the scouts in the hobby with various constructional projects, demonstrations and to run a course for the Scout "Communications" badge.

Further details from: *P. J. Kay G4GCB, "Norin", 6 Shireoaks, Belper, Derbyshire.*

Diary Date

The British Amateur Television Club are holding their "BATC Convention 80" on 5 October 1980 at the Post House Hotel, Braunston Way, Leicester.

The hotel is located off the A46 about one mile from the M1 motorway.

There will be many attractions for the amateur TV buff.

Details from: *Mike Cox G8HUA, 16 Woodclose Road, Scunthorpe, South Humberside DN17 1RU.*

Nascom Exercise Programs

A booklet of BASIC games programs for the Nascom 1 and 2 microcomputers entitled "BASIC Programs Book 1" has been produced by the International Nascom Microcomputer Club priced £2.50 plus 40p postage.

Ten programs have been "LISTed" from programs running in a Nascom using the 8K BASIC and are primarily intended as exercises in learning how to use the machines. Although they all run, the INMC recommends users to enter the programs and not only to make them work but also to study how they work.

The booklet, additionally, lists a number of sub-routines and a complete table of HEX codes for reserved words and graphics, and offers guidance on overcoming two minor bugs and dealing with "Listening to Tape" in BASIC using NAS-SYS 1 and NAS-BUG.

The booklet is available from the: *INMC, c/o Oakfield Corner, Sycamore Road, Amersham, Bucks.*

Disco D.I.Y. Centre

Roger Squire's have recently opened their sixth outlet in Ilford, Essex.

As usual with all Squire's shops a big range of spares and d.i.y. products will be available for the Disco operator.

The product range will include, speaker chassis, turntables, cartridges and styli, plugs, sockets, bulbs, spots of many different types, and all types of cable for Discos and lighting rigs.

The new Roger Squire's shop is at: *415 Ilford Lane, Ilford, Essex. Tel: 01-478 1153.*

PRODUCTION LINES

ALAN MARTIN G8ZPW

New Scanning Receiver

The SX-200 Scanner covers the bands 26–88MHz, 108–180MHz and 380–514MHz on both a.m. and f.m. modes, and incorporates a digital clock.

Frequency entry is by keyboard, and the SX-200 will scan the channels stored in its 16 memories or search any band between user-programmed limits. Two-speed scanning or searching, and optional scan delay are featured.

Either the integral whip or external 50–75Ω antennas may be used, and there is a switched 20dB attenuator for local reception. The power supply is 12V d.c., or a.c. mains via an external adaptor.

The SX-200 measures just 75 × 210 × 235mm and weighs around 2.8kg. It is priced at £241.50 which includes VAT and p&p, and is available from: *Gareth Electronics, 7 Norvic Road, Marsworth, Tring, Herts. HP23 4LS. Tel: Cheddington (0296) 668684.*



Portable Cap. Meter

The recently introduced Model 820 portable capacitance meter from Havant Instruments Ltd., is an economical multi-range instrument combining digital accuracy with complete portability. Its ten ranges cover capacitances from 0.1pF to 1 farad.



Accuracy is 0.5% or 1% of full scale, and resolution down to 0.1pF according to range.

In use, the capacitor leads are simply inserted into a pair of slots and the capacitance is indicated on the clear 4-digit l.e.d. display. A flashing display provides overrange indication. Provision is also made for using jack plugs when measuring in-circuit capacitances.

Housed in a robust moulded case, the 820 weighs only 675g (1.51lb) and is powered by either rechargeable or disposable cells, facilities for using a charger are provided. A tilt stand, spare fuse and 26-page operating manual are also supplied.

Costing £80 plus VAT, the unit is obtainable from: *Havant Instruments Ltd., Unit 3, Westfields, Portsmouth Road, Horndean, Hants. Tel: (0705) 596020.*

Safety Tape

An increasing number of yachts and small boats are being fitted by their owners with v.h.f. radiotelephone equipment, as a means of keeping in touch and of summoning help in an emergency. As the marine v.h.f. band gets busier, it is more important than ever that the correct operating procedure is used. In fact, life could depend on it.

A novel way of learning that procedure is from a pre-recorded stereo tape cassette, part of a package called the "VHF Guide". The cassette covers just about every eventuality, including making a link telephone call, talking to coastguards, marinas and port operations stations, listening to weather and navigation warning broadcasts, and, most important, making emergency and distress (Mayday) calls. There is also

If you please

Please mention "Production Lines", when applying to manufacturers or suppliers featured on this page.

More on pages 73 and 74

Cassette Eraser

S.G.I. Ltd. is marketing a video eraser which will erase video and audio cassettes and tapes in seconds.

Called the Videoraser, it is used instead of the recorder's own internal mechanism and leads to a reduction of wear on the video head and consequently their costly replacement.

It is claimed to erase 100 times better than a recorder thus enabling higher re-recording standards to be achieved and prolong the usable life of the tape. The Videoraser measures 120 × 114mm, weighs 2 kilos, is powered by a.c. mains and provides a magnetic flux of 1400 gauss which makes it possibly the most powerful eraser of its type and can erase a two inch cassette.

Costing £56.93, VAT included, it is a worthwhile investment for the domestic user and can be obtained on a cash-with-order basis from: *S.G.I. Ltd., Fircroft Way, Edenbridge, Kent TN6 6HA. Tel: (0732) 864111.*



information on licensing the station and operators.

A handy reference booklet and a Mayday "prompt" card complete the package, which was prepared in close co-operation with HM Coastguard, the British Post Office and the Royal Yachting Association.

The VHF Guide costs £5.95 plus 45p postage and packing from: *Double-Tee Productions, 35 Mall Road, London W6 9DG.*

Linear Scale Resistance Meter

Robert GOFFIN

No doubt most readers are already equipped to measure resistance since resistance measuring ranges are a feature of every multimeter. However, analogue test meters normally use a very simple form of resistance meter circuit which basically just consists of adding the meter, a battery, a variable resistor, and the test resistor in series. The variable resistor is adjusted for full-scale deflection of the meter with the test prods shorted together, and adding a resistor across the test prods then results in reduced current flow and a correspondingly lower meter reading.

This produces the familiar and rather inconvenient reverse reading resistance scale. The scale is also non-linear with severe cramping at the high-resistance end, and this also tends to be a little inconvenient and with rather poor accuracy.

Linear Scale

The conventional method of obtaining a forward reading linear resistance-scale is to feed the test resistor from a constant current source and measure the resultant voltage using a high impedance voltmeter, which will not draw a significant proportion of the constant current generator's output.

The voltage needed to drive a given current through a resistance is obviously dependant upon the value of the resistance, and will rise in proportion to the value of the resistance. For example: 1 volt is needed in order to drive 1 ampere through 1 ohm. Doubling the resistance to 2 ohms would require 2 volts for the same current flow, 3 ohms would need 3 volts, and so on. Thus a forward reading linear scale is produced.

Circuits of this type often use current source and meter circuits which fall clearly into two separate sections, but

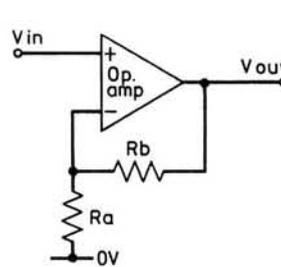


Fig. 1(a)

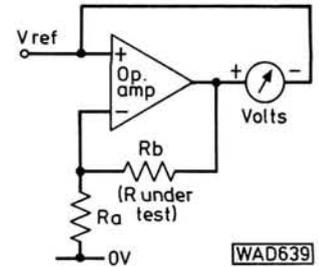


Fig. 1(b)

others use a disguised form of circuit which employs operational amplifier techniques. The unit described in this article falls into the latter category, and this enables an extremely simple circuit to be used. In fact this circuit is not really much more complicated than the ordinary resistance meter circuit, and the unit is well within the scope of any constructor, including the beginner.

Circuit Operation

The unit is based on an operational amplifier connected in the non-inverting amplifying mode. The circuit of Fig. 1(a) shows this basic amplifying arrangement. The input is applied to the non-inverting (+) input and a negative feedback loop consisting of two resistors is connected between the output and inverting (-) input.

The voltage gain of this circuit is equal to $(R_a + R_b)$ divided by R_a . This is because the output voltage is equal to the voltage difference across the inputs multiplied by the open loop voltage gain of the operational amplifier.

Theoretically an operational amplifier has infinite gain


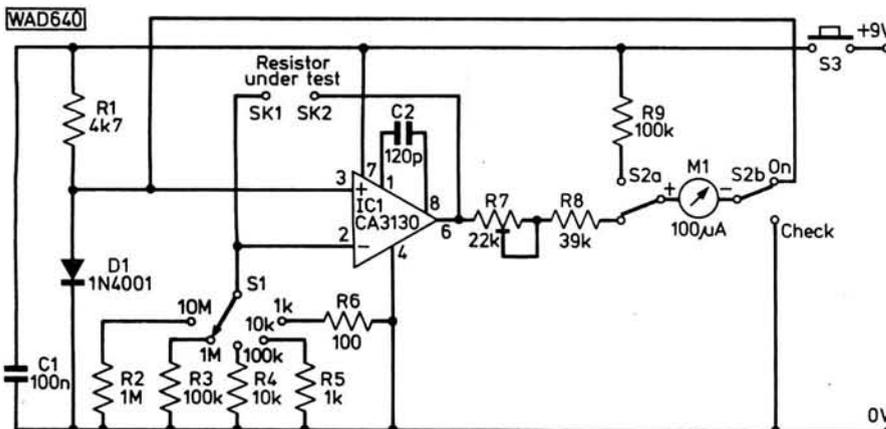


Fig. 2: The complete circuit diagram of the resistance meter

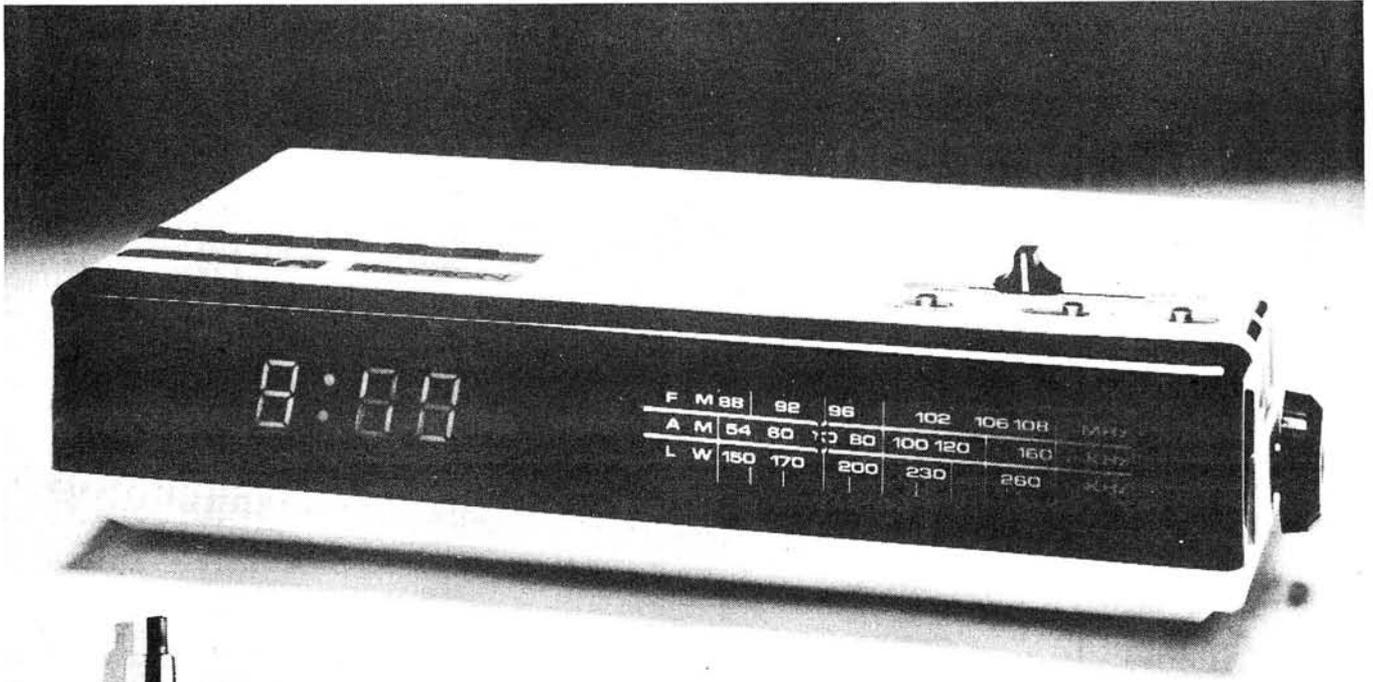

MITRAD

The premier mail order house specialising in quality products and superior after-sales care.

ZETRON CLOCK RADIO Full fidelity AM-FM-LW radio with green tube electronic time display. Alarm, settable anywhere in 24 hour period, can also activate radio to provide wake-to-music facility. 60 minute sleep timer with auto shut-off and touch snooze control. Auto brightness control. Power failure indication.
£16.95 + 85p p&p.

SEIKO QUARTZ LCD MEMORY-BANK CALENDAR WATCH
 Displays hour, minute, second, month, day of the week and date in 12 hour indication – or 24 hour at the touch of a button. Button touch also displays month and year and dates for

a designated month with Sunday dates flashing. Stores dates in memory up to 11 ahead, flashes 'MEMO' on designated dates. Illuminated time and calendar display. Display flashes when battery nears life end. Stainless steel case and wrist strap (adjustable). In presentation case with instructions.
£49.95 + 85p p&p.

PANTER QUARTZ PEN WATCH
 Five function LCD pen watch showing hours, minutes, seconds, month and date. Computerised four year date memory. Ball point pen. Stainless steel case. Price includes presentation case and full instructions.
£12.00 inc. p&p.

To: Mitrad, 68-70 High Street, Kettering, Northants.

Please send me:

Zetron clock radio(s) at £17.80 inc p&p

Seiko Watch(es) at £50.80 inc p&p

Pen Watch(es) at £12.00 inc p&p

Total value of my order £

I enclose cheque/PO or debit my Access/Barclaycard



No. _____ Signature _____

Name _____ (block letters please)

Address _____

From the collection of 12 month guaranteed leading make products offered through Mitrad's 48 hour distribution system and backed by Mitrad's own service organisation. For complete product range, ring or write for catalogue. Trade price list available for bulk buyers.



MITRAD 68-70 High St.,
 Kettering, Northants.
 Telephone 0536 522024



Credit card holders may telephone (0536) 522024 24 hours a day stating card number for immediate attention. All orders despatched within 48 hours. Delivery subject to availability. Full refund if not completely satisfied. Mitrad. Registered in England No. 1500613. Code: PW.



PRESENT

RTTY TERMINAL UNIT CT100

Incorporating **COMPLETELY AUTOMATIC** receive/transmit modes. Protected and buffered input provided for TTY keyboard. Automatic re-generation of incoming tones. Special r.f. interference suppression circuit, etc., etc.

INPUTS FOR:

Audio FSK signal in; Data in from VDU (e.g. G3PLX); TTY Keyboard or Tape Reader.

OUTPUTS FOR:

VDU or other TTL compatible equipment; TTY Magnet - single or double current; AFSK to drive Transmitter.

Featuring a unique digitally controlled 'Autoprint' circuit which is a superior replacement for the 'Antispace' and 'Autostart' facilities found on some other terminal units. The terminal will ignore most CW and phone signals but will respond to a correct RTTY signal.

All prices include VAT: CT101 Receive/Transmit VDU only **£99.60**. CT103, with Teleprinter interface **£104.90**. All models plus £2.50 towards delivery.

ALSO A MATCHING VIDEO DISPLAY UNIT MODEL CD300 especially designed for the RTTY ENTHUSIAST!

The video display unit is designed to be an all-electronic replacement for a Teleprinter, and therefore does *NOT* suffer the disadvantages of bulk, unreliability and noise.

The basic function is to take Murray Code - either from a Terminal Unit (on receive) or from a Keyboard - and produce a complete TV signal. This signal may be fed into a monitor or modulated and fed into the aerial of an ordinary domestic TV set.

It may also be used (with a keyboard) to send Murray Code signals for transmit purposes.

16 lines per page. 64 characters per line.

TTL compatible input. Standard IV video output.

Flashing cursor. Auto-scroll at end of page.

Front panel controls for:

Letter shift. Figure shift. Page reset.

Carriage return. Line feed.

Built-in mains P.S.U. Styled to match the Catronics CT100 Terminal Unit. Cabinet size 9" x 2½" x 7" approx.

Now with built-in UHF Modulator for only £170 incl. VAT (plus £2.50 delivery).

PLESSEY SL1600 Series ICs

SL1610 £1.62	SL1611 £1.62	SL1612 £1.62	SL1613 £2.30
SL1621 £2.15	SL1623 £3.20	SL1626 £2.60	SL1630 £2.15
SL1640 £2.42	SL1641 £2.42		

Other parts for SSB transceiver also available.

ALL PRICES INCLUDE VAT but please add 40p min. postage.
Access and Barclaycards welcome



COMMUNICATIONS HOUSE
20 WALLINGTON SQUARE,
WALLINGTON, SURREY SM6 8RG.
Tel: 01-669 6700.

Shop/showroom open Monday-Friday: 9-5.30
(closed for lunch: 12.45-1.45) Saturdays: 9.00-1.00.

NEW MAIL ORDER SERVICE FOR CONSTRUCTORS IN DEVON & CORNWALL

I.C.s., all discreet components, die cast & instrument cases, S.Dec breadboards, matrix & copper clad boards, panel meters and speakers, AC/DC convertors, DC adaptors, in fact everything the constructor may require

ENQUIRIES WELCOME

also: soldering irons, multimeters, transistor testers, SWR meters, test leads etc.

SPECIAL OFFERS:— mains neons (amber + red) 30p.

S.P.S.T. toggle switches @ 38p. D.P.D.T. toggles @ 50p. plus special offers on headphones (from £3) etc.



Providence Street,
North Hill, Plymouth. PL4 8JG
Tel. (0752) 21581-2

Callers welcome 9 a.m.-5.30 p.m. Mon.-Sat. inc.

P.A. equipment, scanning monitors, mobile radio accessories/aerials also stocked.

STEPHENS-JAMES LIMITED

COMMUNICATION ENGINEERS

47 WARRINGTON ROAD, LEIGH WN7 3EA

ENGLAND

Telephone (0942) 676790

Everything for the Short Wave Listener.

We stock receivers and listening aids by most of the world's leading manufacturers. Full range of VHF receivers—transceivers. Mobile equipment pre-selectors—filters—antennas. Stabilised power supplies from 2 to 20 Amp.

Antenna switches—converters. Aluminium masts—clamps. Antenna rotators.

Trio R1000 Receiver

Digital readout general coverage receiver covering 200KHz to 30MHz with a P.L.L. synthesiser. Also incorporating quartz digital clock. £298.00.

Trio R820

Amateur Band Receiver £690.00.

Send for full specifications of our full range of receivers covering from 200KHz to 520MHz. Our secondhand equipment changes daily. Send SAE for up to date lists. Part exchange welcome. Good clean Equipment bought for cash.

We have a good range of secondhand equipment at all times. Send large S.A.E. for details or telephone. Open 6 days a week.

Bearcat 220FB Receiver

Scanning Receiver. 66-88MHz-118-136MHz. 144-148MHz-144-148MHz. 420-450MHz-450-470MHz. 470-512MHz £258.75
Send S.A.E. for details of our range Aircraft Band Receivers.



DEACs
VARTA BUTTONS
(1-24V PER CELL)

VAT included
P+P 60p per order
RECHARGEABLE
BATTERIES.

Size/Cell
4-8V Pack
6-0V Pack
9-6V Pack

225mA DKZ
25mm dia x 9mm
£3.20

600mA DKZ
34½mm dia x 10mm
£5.55
£6.94
£11.10

CYLINDRICAL NICADS .HP7 Size 80p only; HP11 Size £2.35; HP2 Size £3.20; PP3 £4.00; PP3 Charger £5.00.

CONSTANT CURRENT CHARGER - Switched 9mA/25mA/50mA/120mA/200mA/400mA output - charges 1 to 12 nicads - £13.95.

V & F SMALLCRAFT (POPLAR) LTD
38, STONELEIGH ROAD, CLAYHALL, ILFORD, ESSEX
Tel: 01-550-6642

LIMITED TRADE DISCOUNTS POSSIBLE ON DEACs.

and any difference between the input voltages will result in the output going fully positive if the (+) input is at the higher potential, or fully negative if the (-) input is at the higher voltage. Practical operational amplifiers do not achieve theoretical perfection of course, but their open loop gain is normally in the region of 200 000 times and can be regarded as infinite for most practical purposes.

In the circuit of Fig. 1(a), applying an input voltage will unbalance the inputs and cause the output voltage to rise or fall, depending upon the polarity of the input signal. As it does so, due to the coupling through R_b it will raise or lower the voltage at the inverting input, as appropriate, and once again balance the inputs.

If R_b has a value of zero, the output will assume the same potential as the non-inverting input in order to balance the input potentials. If R_a and R_b have the same value, then due to a potential divider action the output must be double the input voltage in order to balance the inputs. Making R_b two times the value of R_a will produce an output voltage three times that of the input voltage, since the potential divider action across R_a and R_b will result in only one third of the output voltage appearing at the inverting input. It will be apparent from this that the equation given earlier is, therefore, correct.


This resistance meter circuit uses the basic configuration shown in Fig. 1(b). Here a stable reference is applied to the non-inverting input, and R_b is the test resistance. A voltmeter is connected between the operational amplifier output and the reference voltage.

If, for the sake of this example, we assume that the reference voltage is 1 volt and R_a is 1k Ω , with R_b at zero the circuit will have unity gain and the meter will read zero because 1 volt will be present at both its terminals. If R_b is raised to 1k Ω , the circuit will have a voltage gain of two, 2 volts will appear at the amplifier output, and the meter will register the 1 volt developed across its terminals. With R_b at say 5k Ω , the circuit will have a voltage gain of six, 6 volts will appear at the output of the amplifier, and the meter will register the 5 volts present across its terminals.

This gives the required forward reading linear scale resistance meter action with the meter reading being proportional to the test resistance. Note that the current through R_a and R_b is constant and does not vary with changes in the value of R_b, and that the voltmeter reading is equal to the voltage across R_b. The circuit is therefore really using the constant current generator/high impedance voltmeter system mentioned earlier, but in a disguised form.

The complete circuit diagram is shown in Fig. 2.

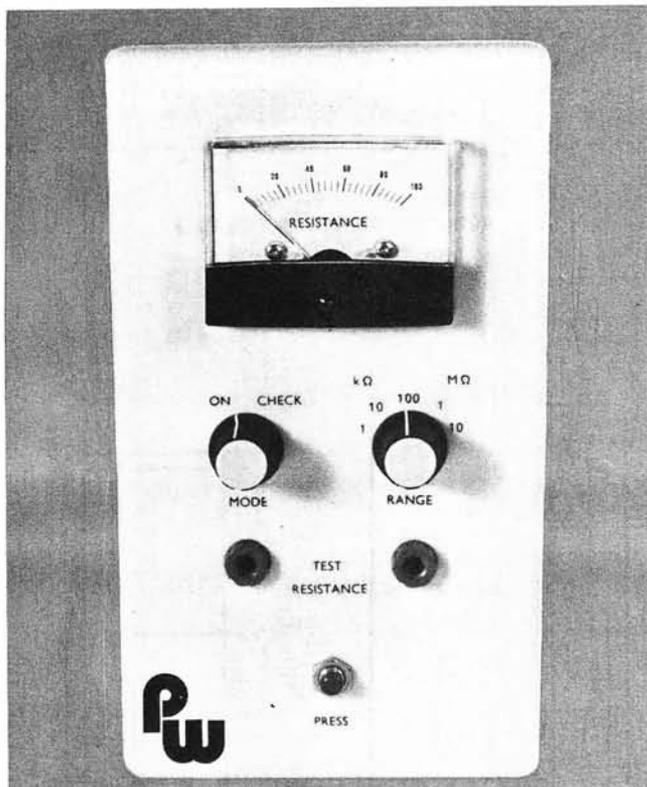A reference voltage of about 0.6 volts is provided by





forward biased silicon diode D1. R7, R8 and M1 comprise the voltmeter circuit which has a sensitivity of about 6 volts f.s.d. (i.e., ten times the reference voltage). The voltmeter sensitivity can be varied to some extent by adjustment of R7 for calibration purposes. R2 to R6 are the equivalent of R_a in Fig. 1(b), and one of these is selected by S1. This provides the unit with five measuring ranges of 0–1k Ω , 0–10k Ω , 1–100k Ω , 0–1M Ω , and 0–10M Ω .

C2 is the compensation capacitor for IC1, which is a CA3130 device. This particular operational amplifier has been chosen because it has an extremely high input impedance of typically 1 500 000M Ω , and this removes inaccuracies on the higher ranges due to the input impedance of the amplifier shunting the lower feedback resistor. It is also necessary to use a device, such as the CA3130, that operates with its inputs and output close to the 0V rail.

With S1 in the position shown, the circuit works normally, but when it is in the alternative position the meter is disconnected from the main circuitry and is connected across the supply lines via R9. This converts M1 to a



★ components

Resistors			Capacitors			Switches		
$\frac{1}{4}$ W 5%			<i>Polyester</i>			1 pole 5 way	1	S1
4.7k Ω	1	R1	100nF	1	C1	2 pole 2 way	1	S2
39k Ω	1	R8	<i>Ceramic Plate</i>			S.p.s.t. push-to-make	1	S3
$\frac{1}{2}$ W 2%			120pF	1	C2			
100 Ω	1	R6	Semiconductors			Miscellaneous		
1k Ω	1	R5	<i>Integrated Circuits</i>			188 x 110 x 60mm plastic case;		
10k Ω	1	R4	CA3130			Printed circuit board; Meter 60 x 45mm moving coil 100 μ A f.s.d.;		
100k Ω	2	R3, R9				PP3 battery and connector to suit;		
1M Ω	1	R2				Knobs (2); 4mm terminals, red (1), black (1).		
<i>0.1W horizontal preset</i>			Diodes					
22k Ω	1	R7	1N4001			1		
						D1		

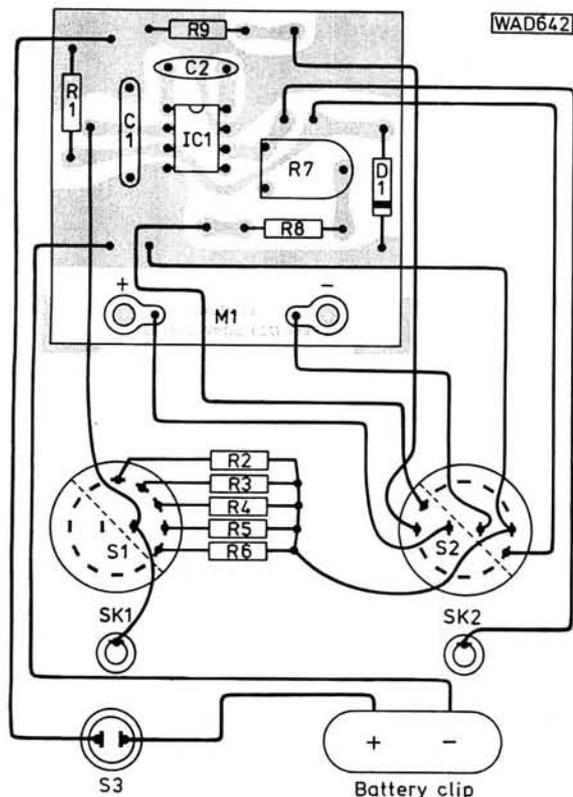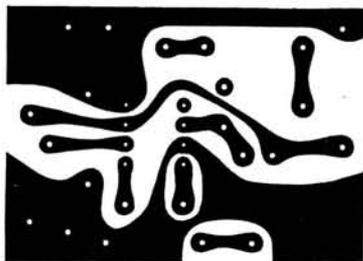

WAD642

Fig. 3: The p.c.b. copper track pattern is shown full size at the top. The component placement is indicated, together with the other wiring above

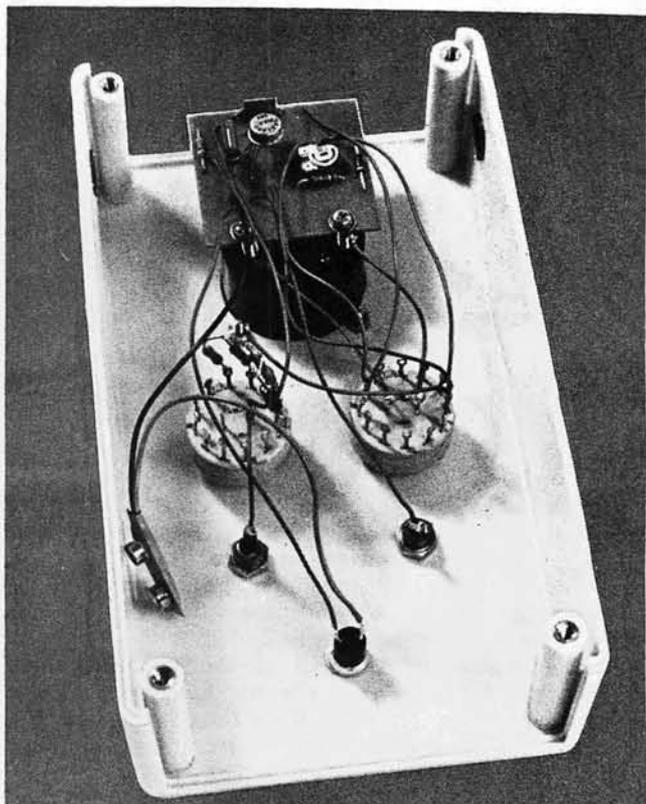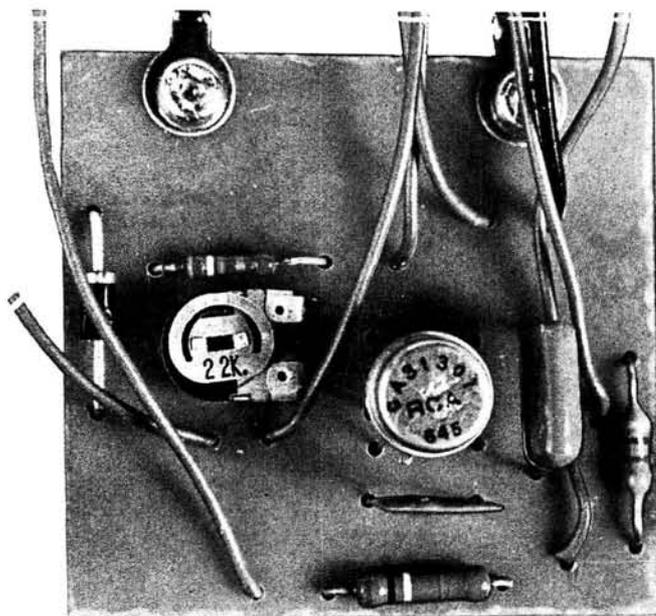

0-10V voltmeter which can be used to check the loaded supply potential. The battery should be replaced when this falls much below 8V.

C1 is a supply decoupling capacitor and S2 is the on/off switch. A non-locking push-to-make type is used here as the supply should only be connected when a test resistor is connected into circuit and a measurement is actually to be made. This is because the meter will be driven beyond f.s.d. with no test resistor in circuit. The circuit has been designed so that a maximum meter overload of only about 50 per cent can occur, and while this is unlikely to damage the meter it is not advisable to risk this.

Current consumption is about 4mA, or so on all ranges except 1k Ω when it is approximately 9mA, and this can be supplied by a PP3 or other small 9 volt battery.

Construction

A 188 x 110 x 60mm plastic case is used to house the prototype, but the unit could be fitted into a much smaller case if desired. The general arrangement of the unit is not critical and any sensible layout can be used.

R2 and R6 are mounted direct onto S1 and the other small components are assembled on a small printed circuit. Once this board and the other wiring have been completed, the p.c.b. is mounted on the meter terminals. Details of the p.c.b. and wiring are illustrated in Fig. 3.

Calibration

In order to calibrate the unit a close tolerance resistor, 1 per cent or better, having a value equal to the f.s.d. value of one range of the unit is required. With this connected across the test clips, S1 switched to the appropriate range, and with R7 initially set for maximum resistance (fully clockwise), S3 is depressed and R7 is adjusted for precisely full scale deflection of S1. The resistance meter is then ready for use.

introducing

RTTY

part 3

Jeff MAYNARD G4EJA

We have already seen in Part One of this series that the simplest method of generating RTTY for transmission is with an AFSK unit. This can then produce AFSK or FSK by modulating the appropriate transmitter. Accordingly, it is not proposed to discuss any FSK circuits in detail. Various suggestions for producing AFSK are given below; however, before that is done it will be helpful to consider interface circuits again so that the AFSK units need only be designed for TTL-compatible input operation.

The most common terminal output arrangement is the two-way switch biased to mark as shown in Fig. 21. In a TTY system this could be arranged with $-80V$ on the mark contact and $+80V$ on the space so that the tongue switched between these two values. It is just as easy, however, to arrange for the tongue to be grounded and the mark and space contacts used to switch a flip-flop as shown in Fig. 22 (which also serves to debounce the input).

Conversion of 80V signals can be done simply by using a potential divider as shown in Fig. 23. A safer method is

Fig. 21: The most common terminal output arrangement, a switch biased in the marked condition

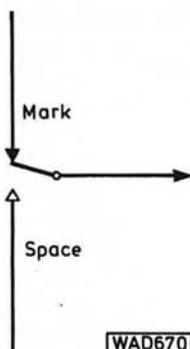


Fig. 22: An alternative form of terminal output, a flip-flop which also "de-bounces" the switch contact

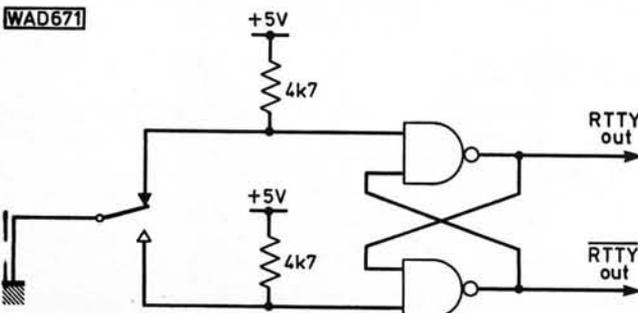


Fig. 23: The simplest method of converting 80 volt signals down to TTL levels, but not the safest. Consider, for instance, the result of the 470Ω resistor going open-circuit

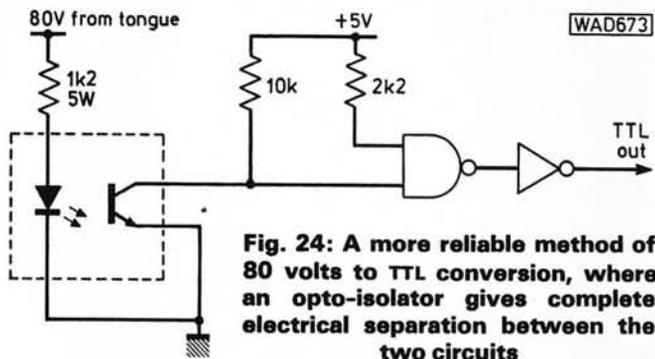
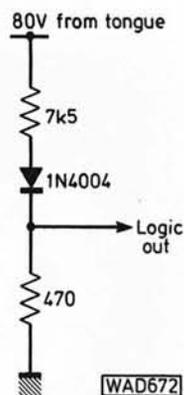


Fig. 24: A more reliable method of 80 volts to TTL conversion, where an opto-isolator gives complete electrical separation between the two circuits

to isolate the 80V supply completely from the TTL circuitry by means of an opto-isolator as shown in Fig. 24.

In these methods only the $+80V$ supply is needed and is connected to the space contact. An advantage of using 80V is that the terminal contacts are "wetted" at each changeover and are thus, as intended, kept free of oil and other contamination from the mechanical parts of the terminal. The opto-isolation method can of course be changed for other voltages, simply by altering the value of the resistor in series with the l.e.d.

Generating AFSK

Having developed a TTL-compatible signal as the output of the terminal (with 1 representing mark and 0 representing space), the next task is to produce an AFSK signal, with an output of 1445Hz for mark and 1275Hz for space. Four basic methods are available for the generation of AFSK signals: switching between two oscillators; switching the frequency-determining element of a single oscillator; variable division of a crystal-controlled oscillator and use of a special integrated circuit.

For the first method, almost any type of audio frequency oscillator can be used—f.e.t., multivibrator, 555 and so on. For example, two circuits based on Fig. 25 could be used with a suitable switching mechanism.

A reduced component count is one advantage of the second method—using a single oscillator with alternative frequency-determining components, rather than two distinct oscillators. Again, any number of different types of oscillator can be employed. *RTTY The Easy Way* uses a simple two-transistor multivibrator that the author used for many successful QSOs. This circuit is shown in Fig. 26. The pre-set potentiometers should be of the multi-turn variety. With a mark input, the 10kΩ pot is adjusted for 1445Hz output; then the 5kΩ pot is adjusted for 1275Hz output with a space input, the latter pot being switched in and out of circuit by the BC108 transistor.

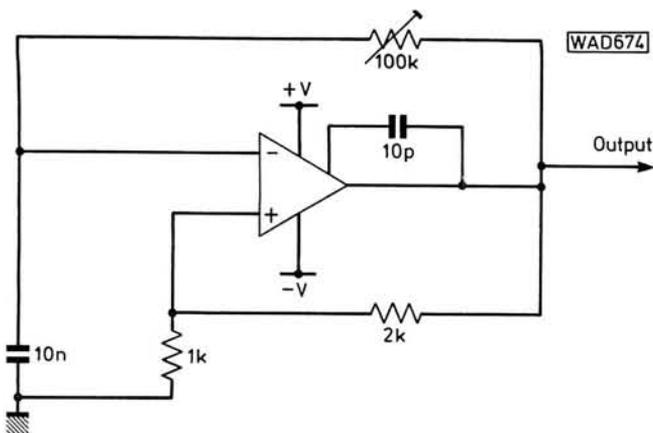


Fig. 25 ▲

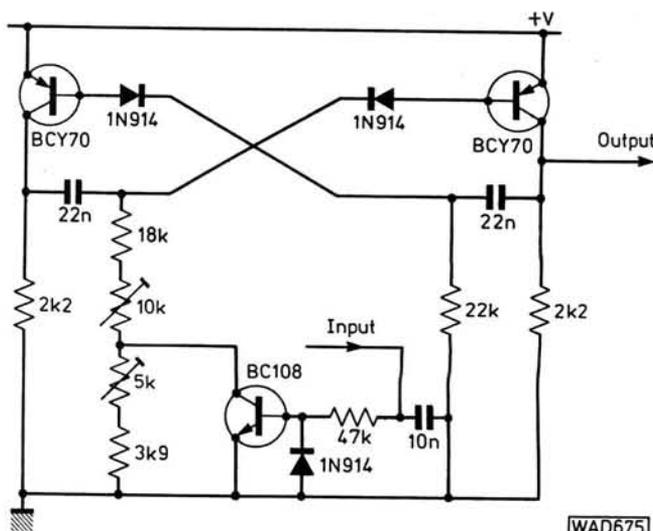


Fig. 26 ►

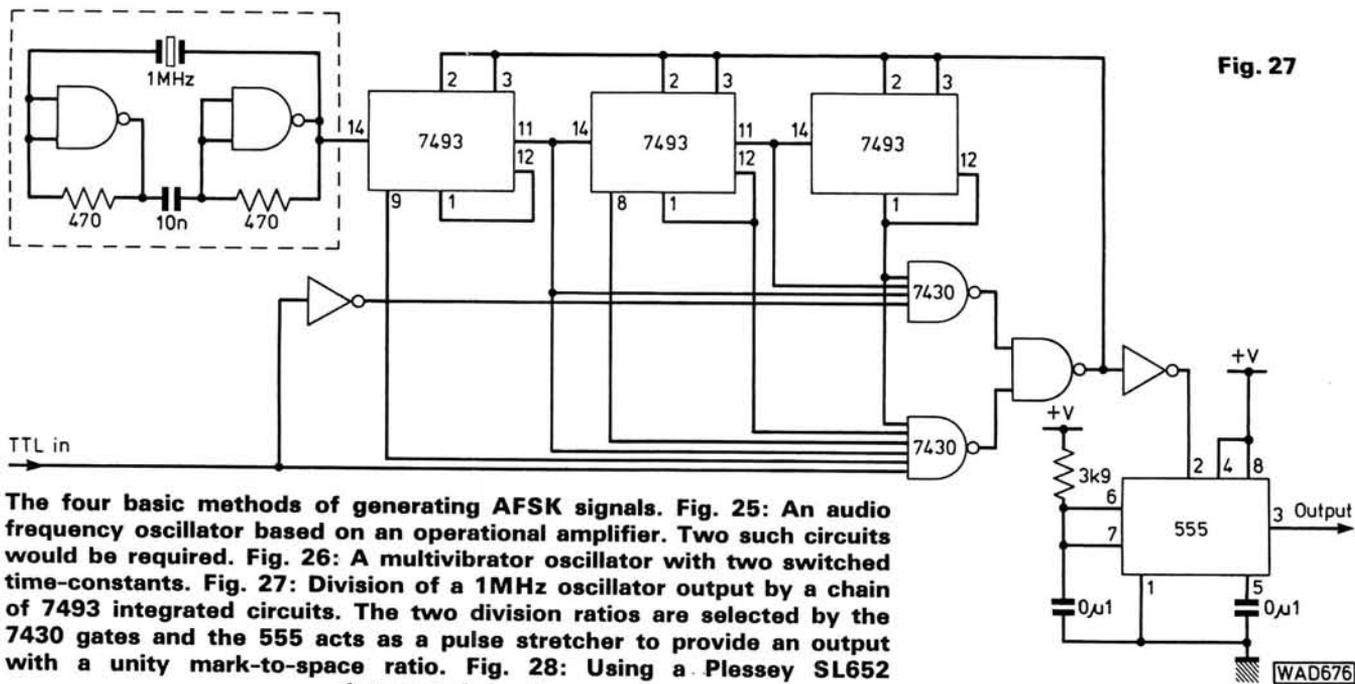


Fig. 27

The four basic methods of generating AFSK signals. Fig. 25: An audio frequency oscillator based on an operational amplifier. Two such circuits would be required. Fig. 26: A multivibrator oscillator with two switched time-constants. Fig. 27: Division of a 1MHz oscillator output by a chain of 7493 integrated circuits. The two division ratios are selected by the 7430 gates and the 555 acts as a pulse stretcher to provide an output with a unity mark-to-space ratio. Fig. 28: Using a Plessey SL652 integrated circuit

Generating AFSK tones by division of a crystal-controlled oscillator is a useful method, particularly if an accurate source of, say, 1MHz is already available from a counter, MPU or other test oscillator.

Division of 1MHz by 784 and 692 respectively will produce outputs of 1275Hz and 1445Hz, both within 1Hz of the desired frequency. This is easily done with 7493 dividers as shown in Fig. 27, which also shows an optional crystal-controlled oscillator. The 555 timer is used to lengthen the very short reset pulses from the gate, in order that the output waveform has an even mark-to-space ratio. Unused inputs of all the gates should be taken to the positive 5V rail via 2.2kΩ resistors. This circuit has the advantage that, given an accurate source of 1MHz pulses, the constructor can produce an AFSK unit that does not require any line-up procedure.

Several "custom" i.c.s can be used to produce AFSK with minimum external components. The author has experimented with the Plessey SL652, which may be used as a stable tone source as shown in Fig. 28. The 10kΩ preset

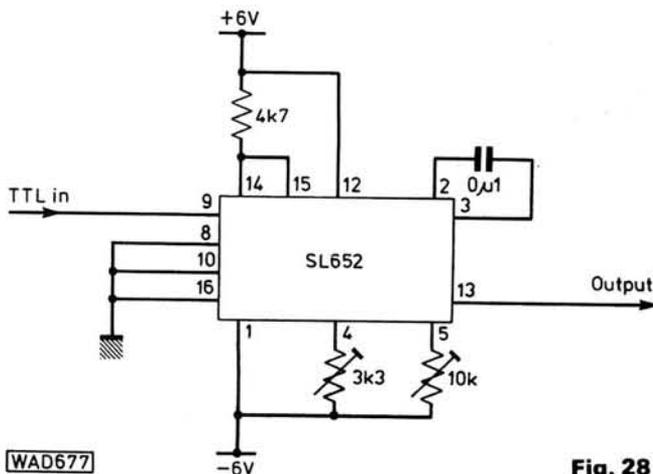


Fig. 28

Lee Electronics Ltd

LEE

Londons Leading Stockists Of:
STANDARD YAESU ICOM FDK KDK MICROWAVE MODULES LUNAR SST SHURE HI-MOUND CDE STOLLE
TELECOMM ANTENNAE J-BEAM SWAN KATSUMI ETC.

LEE



C7800

The C7800 is one of the most advanced mobile 70cm transceivers available. Features include:- * Digital Readout * Five Memories * Two Speed Scan Rate * L.E.D.

£274.85
inc. VAT

(C8800 is the matching 2m unit)

Power and S Meter and many more. Why not try one for yourself.



NEW LOW PRICE
FRG 7 £199.00

TRIO R1000



BEAT THIS PRICE!! £289 inc. VAT
FREE HEADPHONES WITH THIS SET AND WITH FRG7


THE NEW C800



This 10 channel scanner out performs many of its rivals due to its highly sensitive front end and excellent filtering. A one channel 50MW transmitter is incorporated and is ideal for local use. Controls include squelch, volume, auto scan and manual channel stepping. The unit comes complete with channels S20, R1, R2, R7, Nicads, Charger, helical antenna and wire antenna.

PRICE £80.45 inc. VAT
CARRIAGE FREE

Just a small selection from our comprehensive range of accessories.

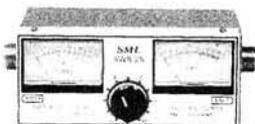

SWR25: This ever-popular twin SWR and Power meter covers 3.5-150MHz at **£12.65** inc. VAT. P&P 50p.




DL-30 Dummy load 25W DC-150 MHz **£6.35** inc. VAT. P&P 25p.

T-100 80W Dummy load DC-500 MHz **£24.10** inc. VAT. P&P 25p.

T-200 150W Dummy load DC-500 MHz **£35.60** inc. VAT. P&P 25p.



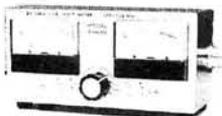SWR200B swr/power meter covering 3-200MHz 50/75 Ohm power range 3-30MHz, 20/200/2kW, VHF 2/20/200W **£40.20**. P&P £1.00.



T-435: VHF/UHF swr and power meter with 2/20/120 watt through line power measurement **£34.45** inc. VAT. P&P 75p.



CT-1 Coax Toggle 3 SO239's **£6.85** inc. VAT. P&P 25p.
CT-2 Coax Toggle 2 SO239's 1 PL259 **£6.85** inc. VAT. P&P 25p.



PX402 13.8V DC 3 amp continuous 4 amp max fully stabilized power supply with overload protection **£22.95** inc. VAT. P&P £2.00.
Also available:
PH5000, 5A continuous, 7A surge. **£P2500**, 25A continuous, 30A surge.

We are London's Largest Stockist of Microwave Modules products.

TRANSVERTERS:

MMT28/144	(10m linear transverter)		
MMT144/28	(2m linear transverter)	90.85	B
MMT432/28-S	(70cm linear transverter)	99.00	B
MMT432/144-R	(70cm linear transverter)	136.85	B
MMT70/28	(4m linear transverter)	173.65	B
MMT70/144	(4m linear transverter)	115.00	B
MMT1296/144	(23cm linear transverter)	115.00	B
		184.00	C

LINEAR AMPLIFIERS:

MML144/25	(2m 25 watt linear amplifier)	48.30	B
MML144/100	(2m 100 watt linear amplifier)	142.60	D
MML144/40	(2m 40 watt linear amplifier)	69.00	B
MML432/20	(70cm 20 watt linear amplifier)	69.00	B
MML432/50	(70cm 50 watt linear amplifier)	113.85	D
MML432/100	(70cm 100 watt linear amplifier)	228.65	D

RECEIVE CONVERTERS:

MM2000	(RTTY to TV converter)	169.00	B
MMC28/144	(10m converter)	24.90	A
MMC50/28	(6m converter)	24.90	A
MMC50/28L0	(6m converter)	26.90	A
MMC70/28	(4m converter)	24.90	A
MMC70/28L0	(4m converter)	26.90	A

Price £

inc. VAT

Post

Rate

MMC144/28	(2m converter)	24.90	A
MMC144/28L0	(2m converter)	26.90	A
MMC432/28-S	(70cm converter)	29.90	A
MMC432/144-S	(70cm converter)	29.90	A
MMC1296/28	(23cm converter, 10m output)	32.20	A
MMK1296/144	(23cm converter, 2m output)	59.80	B

FREQUENCY COUNTER:

MMD050/500	(500MHz digital frequency meter)	69.00	A
MMD600P	(600MHz prescaler)	23.00	A
MMDP1	(frequency counter probe)	11.50	A

RECEIVE PREAMPLIFIERS:

MMA28	(10m preamplifier)	14.95	A
MMA144V	(2m RF switched preamplifier)	29.90	A
MMA1296	(23cm preamplifier)	29.90	A

FILTERS:

MMF144	(2m filter)	6.90	A
MMF432	(70cm filter)	6.90	A

VARIOUS:

MMV1296	(70cm to 23cm varactor tripler)	34.50	A
MMS384	(384MHz frequency source)	27.60	A

ATTENUATOR:

MMR15/10	(15dB attenuator, BNC terminations)	5.75	A
----------	-------------------------------------	------	---

THE ABOVE PRICES ARE INCLUSIVE OF VAT BUT NOT POSTAGE. PLEASE ADD POSTAGE TO THE ABOVE PRICES AT THE FOLLOWING RATES:
UNITS 'A': £0.675 UNITS 'B': £1.75 UNITS 'C': £2.25 UNITS 'D': £2.75

400 EDGWARE ROAD
LONDON W2
01-723 5521 Tlx: 298765



INSTANT H.P.
& P/EX. WELCOME

Send 25p for
full details
of our range.

Multimeters. what price excellence?

... certainly less than you think. By incorporating a custom made LSI chip, these fully auto-ranging 3½ digit multimeters are available at prices from under £50.00.

SK-6110
(illustrated)

£67.17

+ VAT

SK-6220

£45.43

+ VAT



Supplied complete with batteries, test leads, spare fuse and instruction manual.

SK-6110 and SK-6220

- Full auto-ranging on both voltage and resistance
- Current measurement up to 10A DC and AC
- Unit and range automatically displayed
- Auto polarity and auto zero
- Only 5mW dissipation—200 hours continuous use
- Zero adjust key to correct for test leads on low value measurements
- High impact ABS case
- Low battery indication

SK-6110

- Audible continuity test function
- Range hold function
- Audible over-range indication

Telephone orders welcome for Access and Barclaycard and all account customers. All prices inc. P.&P.



WEST HYDE

West Hyde Developments Limited,
Unit 9, Park Street Industrial Estate, Aylesbury, Bucks. HP20 1ET.
Telephone: Aylesbury (0926) 20441/5.

New 7th edition AMATEUR RADIO TECHNIQUES

JUST
PUBLISHED!

Basically an ideas and source book, this ever-popular work by Pat Hawker, G3VA, brings together a large selection of novel aerials, circuits and devices, together with many fault-finding and constructional hints. In this latest edition some 50 new or revised pages describe the most recent techniques; the "quick guides" now cover such topics as microprocessors and vmos power fets.

Chapter titles are: Semiconductors; Components and construction; Receiver topics; Oscillator topics; Transmitter topics; Audio and modulation; Power supplies; Aerial topics; Fault-finding and test units.

368 pages

£6.08

Price includes postage, packing and VAT where applicable. Postal terms: cheques/POs with order (not stamps or book tokens). Goods are obtainable (less P & P) at RSGB HQ, 9.30-5pm, Monday - Friday.

The RSGB is the national society representing all UK radio amateurs and membership is open to all interested in the hobby, including listeners. The Society also publishes a complete range of books, log books and maps for the radio amateur. Contact the membership services section for more information about amateur radio, the RSGB and its publications.



Radio Society of Great Britain
35 Doughty Street, London WC1N 2AE
Telephone 01-837 8688

WOOD & DOUGLAS

With the winter evenings approaching, the constructional season for radio amateurs is about to begin. If you are undecided on your winter project perhaps you can find something in our range of over 30 kits and modules to suit you.

70FM05TR In case you missed last months review of this single channel FM transceiver for 70 cms here are a few details. The receiver sensitivity is typically 0.4 V and uses dual gate MOSFETS and a high quality crystal filter. The audio output drives an 8Ω speaker. The transmitter gives 500mW of RF and has a modulator on the pcb. Both boards use readily available crystals and measure a very compact 6" by less than 1½".

Kit RX £38.50 Assembled RX £47.25
TX £17.80 TX £25.95

70MC06TR When one channel is not enough then by adding this two pcb set you will have 6 channels on tx/rx. This includes a toneburst for repeaters and a scanner to ease monitoring.

Kit RX £18.60 Assembled RX £26.05
TX £11.30 TX £18.10

144SY25B An FM synthesiser for 25KHz steps at 144-146MHz. The output frequencies are 5.5, 11, 22 or 45MHz on receive and 6, 12 or 24MHz on transmit. This will feed most commercial radio telephones and also the PW NIMBUS. So for the cost of ten crystal channels you get full band coverage, crystal controlled toneburst, repeater ±600KHz offset, out of lock inhibit and channel selection by channel number.

Kit £50.95 Assembled £69.70

INTERESTED? If you would like further details of these and our many other products then send a large SAE (please!) for the latest lists. The above prices include VAT at the current rate but please add 60p p&p on the total order. The prices include all items to make a working pcb module. We do not supply external hardware such as boxes or switches etc. This leaves you free to use the modules in whatever configuration you wish and yet have confidence that the electronics will perform well. We will gladly service any of our products providing it has been built as directed. We make a small charge for this facility depending on complexity. Kits when in stock are return of post otherwise 10-14 days. Assembled items 10-14 days.

9 HILLCREST, TADLEY
BASINGSTOKE, HANTS RG26 6JB



(which should be multi-turn) sets the mark frequency (pin 9 high), after which the 3.3kΩ preset (also multi-turn) is used to set the space frequency (pin 9 low). For a minimum-chip terminal unit for transmission and reception the reader is referred to *Radio Communication Handbook* by Plessey Semiconductors, which suggests a method by which a single SL652 may be used for both functions. If experimenting with the SL652, great care must be taken not to exceed 6 volts on either power rail. Op. amps., for an active filter say, can be run from ±6V in conjunction with an SL652.

Each of the AFSK circuits described above produces a squarewave output. This should not be fed directly to a transmitter but should first be passed through a low-pass filter. A simple CR network such as shown in Fig. 29 will suffice, although the user may care to add an active band-pass filter based on a 741 if desired.

Storing Messages

Using a combination of circuits discussed so far, the licensed amateur can very easily join the ranks of active RTTY enthusiasts, assuming of course he has some form of terminal. However, with the exception of microprocessor owners (dealt with in a later article), it will soon become evident that some additional equipment is highly desirable. This is because of the difficulty of sending repetitive messages from a keyboard—particularly for the one-finger typist. The most obvious message that needs to be sent repeatedly is CQ, although even this has variants

Fig. 29: A simple CR low-pass filter to limit the AFSK generator output spectrum

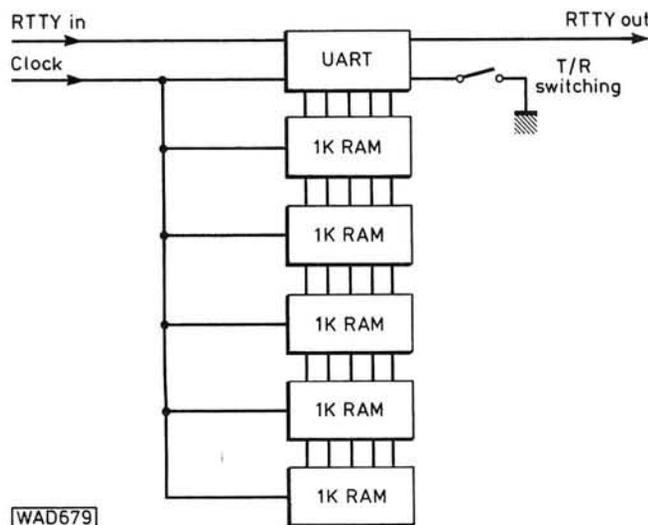
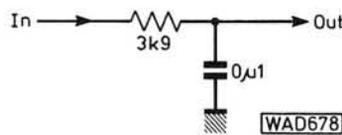


Fig. 30: Basic block diagram of a 1K RTTY store


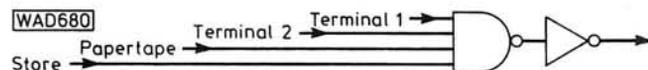


Fig. 31: Combining several message-originating devices onto a single TTL bus

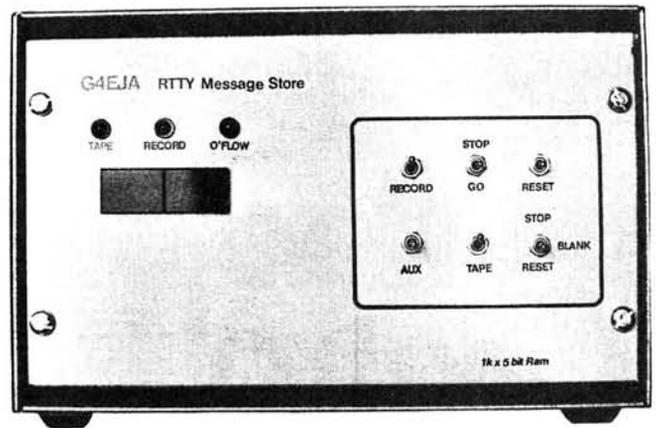

The control panel of the author's 1K RTTY message store

(CQ DX, CQ CONTEST, etc.). Other messages can include test patterns, one's own call sign (particularly when beset by QRM) and RTTY pictures.

Incidentally the two most common test patterns are the "fox" message (the quick brown fox jumped over the lazy dog in the stable), because it includes every letter of the alphabet, and a string of RYs because this is the resulting output when keying alternate mark/space.

Traditionally the source of such standard messages has been paper tape. Many of the older TTY terminals include a paper-tape reader and punch, and stand-alone units are still readily available if rather cumbersome. Messages on tape can be made into continuous loops and sent as required. For example, a tape might contain:

CQ CQ CQ CQ DE G4EJA G4EJA

followed by a carriage return and line feed. This can be formed into a loop and sent about ten times as a means of initially establishing a contact.

A favourite tape-loop subject is a description of one's particular station, which would normally be sent during each QSO. Many terminals have an auxiliary contact that is made or closed when figure J (or bell) code is received. This can be used to stop the paper tape reader when, for example, some variable information has to be inserted into the transmission (such as a contest report and number).

Two electronic alternatives to paper tape are available (excluding microprocessors). These are the diode matrix and RAM (Random Access Memory). The former is not really a good idea for anyone starting from scratch because it is cumbersome to set up, difficult to change, and no cheaper now than using some form of semiconductor storage.


An RTTY message can be started in RAM such as the 2102. If five 1K chips are used then 1K RTTY characters can be stored. A UART (Universal Asynchronous Receiver Transmitter) is used to convert from serial RTTY to the parallel mode needed to load the RAM. A block diagram of such a system is shown in Fig. 30, where the necessary clock—at 16 times the baud rate—can be derived by further division if a crystal-controlled AFSK generator is used. A detailed circuit description is beyond the scope of this article; interested readers are referred to a design by G3PLX in the *BARTG Newsletter*, December 1977.

Remembering that any RTTY device is in the mark condition when idle, it is easy to see how a number of message-originating devices can be paralleled onto a single TTL bus (Fig. 31).

Part 4, next month, deals with some proprietary terminal units, providing a method of getting into RTTY with minimum delay.

Model Radio Control

PW

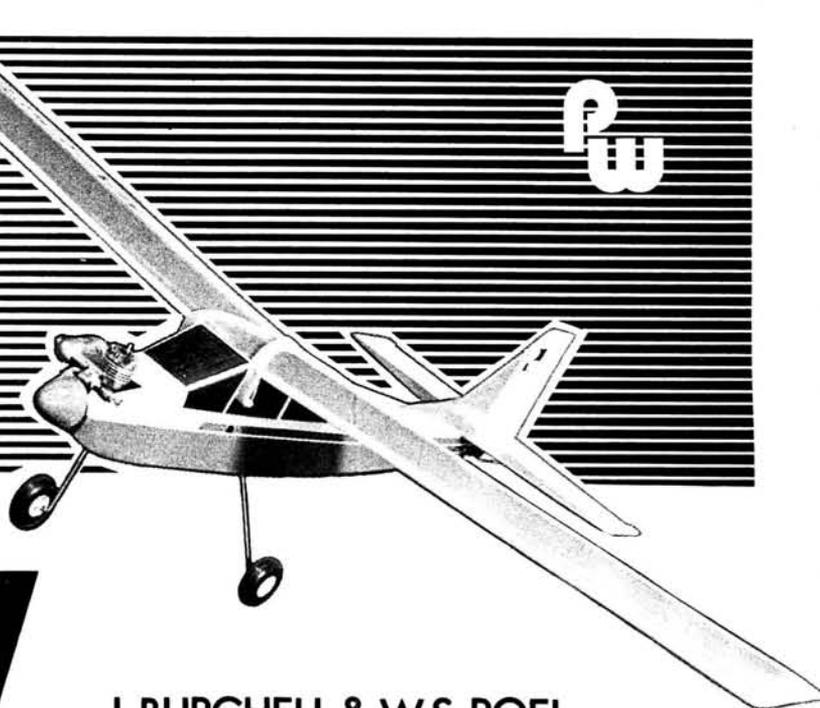

Part 8

THE PW FM-80 SYSTEM

J. BURCHELL & W.S. POEL

Most radio modellers rely on very simple equipment for setting up and checking the performance of their radio gear. This unit is a sophisticated test system which provides all the facilities for alignment and checking of almost any modern digital radio control system, and while it is sophisticated it is also relatively easy to put together, thanks to the availability of pre-aligned modules.

The absorption wavemeter is rather novel and is in reality a very simple spectrum analyser enabling the wanted 27MHz output to be peaked while keeping an eye on the unwanted crystal fundamental frequency and the dreaded 54MHz harmonics.

Circuit

The circuit diagram of the wavemeter is shown in Fig. 1 and, as can be seen, is simply three parallel tuned circuits connected in series. The output of each parallel tuned circuit is taken to an individual 0-200 μ a meter, which provides an indication of the r.f. signal level at that particular frequency.

Several other circuit configurations were tried, including some in which the 13.5MHz and 54MHz components were subtracted from the 27MHz component and displayed on a single meter. This meter then showed a representation of the overall "goodness" of the transmission.


However, it was found that having simultaneous display of all three components made it a great deal easier to tune up the transmitter for the best output, and imparted somewhat more of an intuitive feel to the user as to how to tweak the coils for the optimum signal out. In fact, it is a "poor man's" spectrum analyser and the design could be extrapolated to cover as many frequencies as the user desired.


The digital frequency meter (d.f.m.) is based around a commercially available l.c.d. readout unit which is in two parts. A front panel unit consists of the l.c.d. readout, the timebase crystal and an Oki i.c. Type MSM 5527 which

contains all of the display and measuring electronics for a d.f.m. with a basic range of 3999.9kHz.

A prescaler board, which offers $\div 10$ and $\div 100$ facilities, thus extending the range of the basic unit to 399.9MHz, plugs onto the front panel. The prescaler board also contains a matrix board on which diodes may be placed to select the various options and i.f. offset values of the front panel unit.

The unit used in the FM-80 Field Test Set was programmed to read Frequency directly with the prescaler selected to $\div 10$, thus giving a resolution of 1kHz to 39.999MHz and is used in this mode to check both the Tx and Rx frequency. The Rx frequency should, of course, be 455kHz below the Tx frequency. One of the programming options available on the unit allows the subtraction of 455Hz from the input frequency whilst in the short-wave mode. This facility can be used to enable a reading of what the Rx Local Oscillator frequency should be whilst actually measuring the Transmitted Frequency.

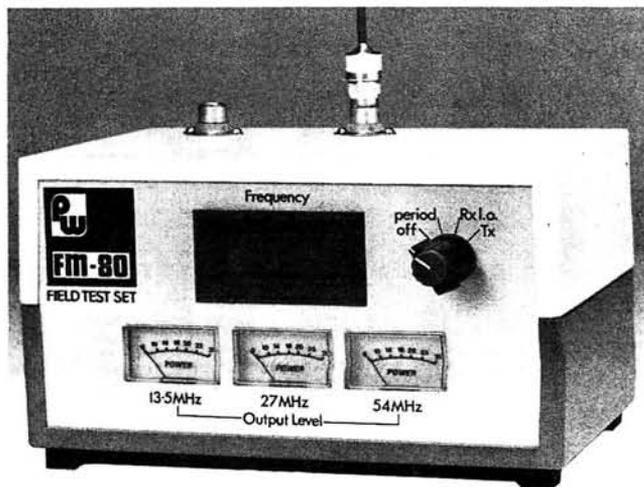

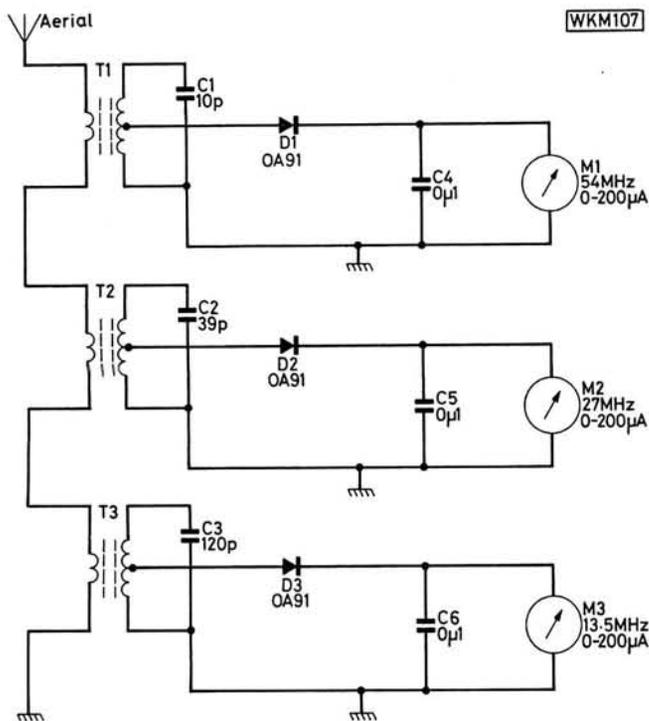

WKM107


Fig. 1: The circuit diagram of the three frequency wavemeter

Period Measurement

One of the modes available on the front panel unit is event count. In this mode, transitions on the input are counted and displayed on the l.c.d. until the rest line is pulsed, when the display is set to zero. Due to the fact that within the MSM5527 all pulses being applied to the display counter are divided by eight, it actually takes eight transitions on the input to increase the display reading by one.

Fig. 2 shows a block diagram of the period measuring add-on unit. The rising edge of the incoming pulse is used to reset the counter to zero, the rest of the pulse being delayed whilst this is happening. The delayed pulse is then applied to the gated oscillator and is used to turn it on for a period of time equal to itself. The gated oscillator thus presents a series of pulses, for as long as the input signal is high, to the front panel module, which are counted and displayed. Nothing further happens until the next pulse arrives, when the whole process repeats itself. If the oscillator is set to a frequency of 800Hz the display will count to 100 in 1ms giving adequate resolution for our purposes.

The unit is capable of displaying the period of any single input pulse providing the count from the gated oscillator does not exceed 39999. If, however, the input is a

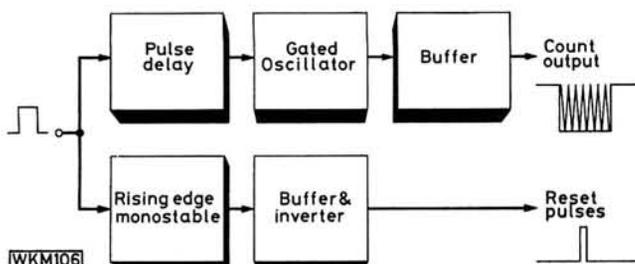



WKM106

Fig. 2: Block diagram of the add-on period measuring unit

pulse train then the mark to space ratio should not be less than about 5:1 as the display is not blanked during the actual measuring time of the input pulse and must therefore be allowed to remain stationary for most of its time in order to be read properly by the user.

The original unit gave an unambiguous display for input signals up to 8ms at a repetition rate of 70Hz which means that it is more than capable of measuring the typical servo output pulse train.

The circuit diagram of the period measuring add-on is shown in Fig. 3, and is constructed from a single CD4093 with the barest minimum of external components. The rising edge detector is formed from C1, R1, IC1a. This is then buffered, inverted and applied to the reset input of the MSM5527. While this is going on the pulse is delayed by R2, C2 and then applied to the gate of the oscillator formed from IC1c, C3, VR1. The output is then buffered and applied to the input of the MSM5527. IC1 must be a schmitt device in order to enable the oscillator circuit to function and provide good recovery of the pulse after it has been delayed by C2, R2.

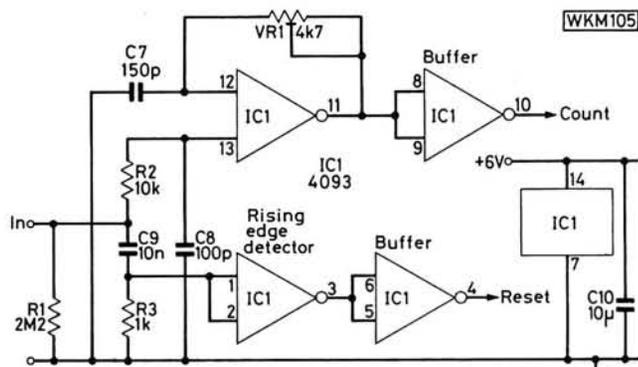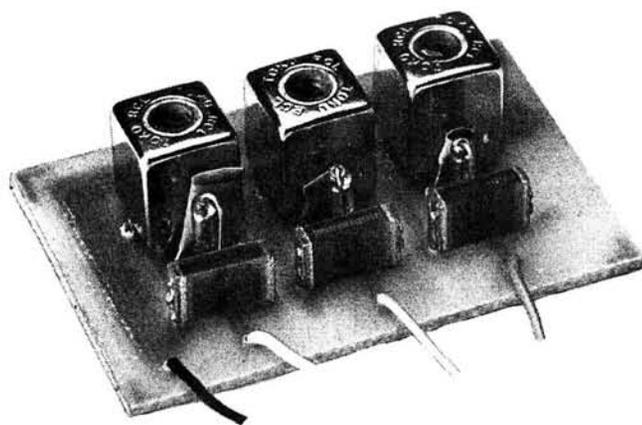


WKM105

Fig. 3: Circuit diagram of the period measuring unit


Construction and Testing

Although, providing good r.f. practice is followed, it is possible to build the wavemeter on plain matrix board, it is strongly recommended that the printed circuit board is used, as the exact layout, and hence the stray capacitance, will affect the values of the parallel tuning capacitors particularly at 54MHz. The only way to set the wavemeter up is with the aid of a signal generator capable of being tuned to 13.5MHz, 27MHz and 54MHz—you can of course use the digital frequency readout to check it—then rotate the cores of T1, T2 and T3 to give maximum deflection on the relevant meter. It should be found that the ranges do not interfere with each other.

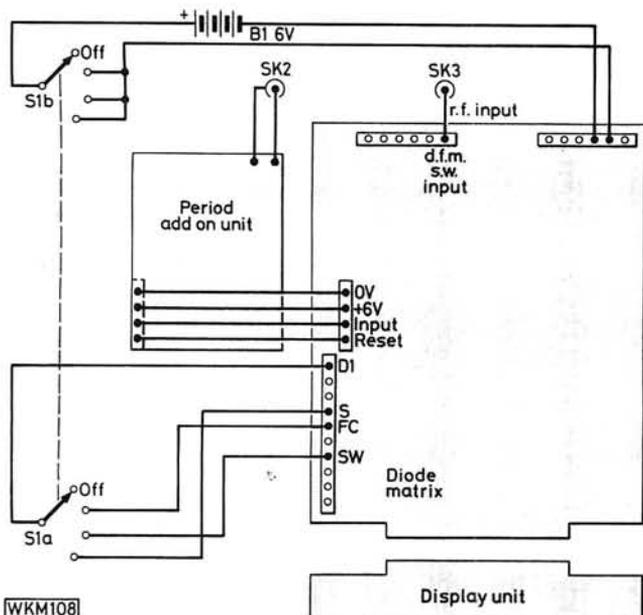

WKM108

Fig. 4: Connections of the d.f.m. board and display showing the switching arrangements and power supply connections used in the prototype unit. Other arrangements are possible to allow the d.f.m. to be used for other purposes and these are detailed in the comprehensive instruction booklet supplied with the d.f.m. module

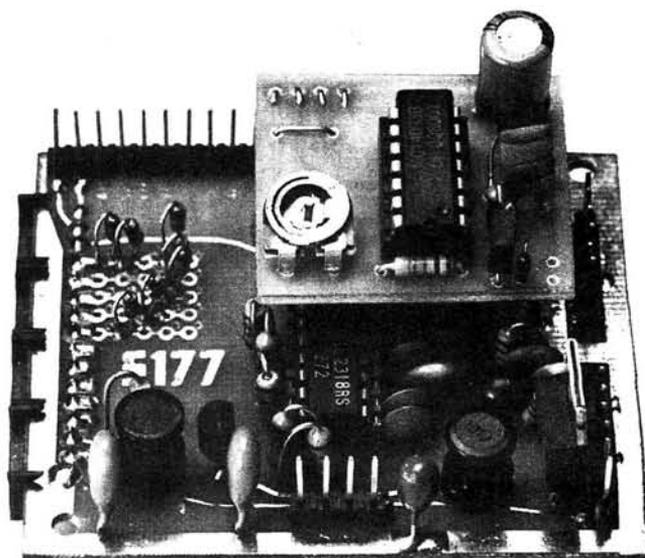

The main d.f.m. board with the add-on unit in position. Note that some extra support for the add-on board will be needed and could be provided by the use of "Sticky Fixers"

Period Measuring Add-on Unit

This is designed to be built on a small p.c.b. which then connects to a purpose-designed connector on the prescaler module. To test its operation connect the period measuring board to a +6V supply and connect the input to a logic high (+6V) for the time being. The gated oscillator will now be turned permanently on and it should be possible to measure its frequency at the output of IC1d. Using VR1, adjust to between 810–815kHz (N.B.—it is set somewhat high compared to its theoretical value due to some pulse shortening which occurs in the pulse delay network). You can use the digital frequency unit in its frequency mode to do this. Now connect up a suitable signal source (1–2ms pulses every 20ms from the Tx encoder output) and check that everything works. The display should be stable and for 1.5ms pulses will show 15.0, e.g., the display must be divided by ten to obtain the reading in milliseconds.

If all is not well, check for the presence of bursts of 800kHz on the count line and for reset pulses on the reset line. Also check that the right value components have been used.

Digital Frequency Meter

There is, of course, no construction or testing to be carried out here and all that one must do is decide which programming options are desired and install the relevant diodes. The unit comes with a four-page booklet which fully describes its working and method of connection. As stated earlier, the unit used in the prototype was programmed into the frequency count mode with the prescaler selected to $\div 10$ giving a display range of $3999.9\text{kHz} \times 10$ and to read short-wave minus 455kHz, allowing one to see what the Rx local oscillator frequency should be whilst measuring the transmitter frequency. The unit was also programmed into the event count mode for use with the period measuring add-on. Fig. 4 shows the switching employed in the prototype.

It is, of course, possible to use the unit as a general piece of testgear in which case suitable switching of the input source and prescaler will have to be arranged by the constructor.

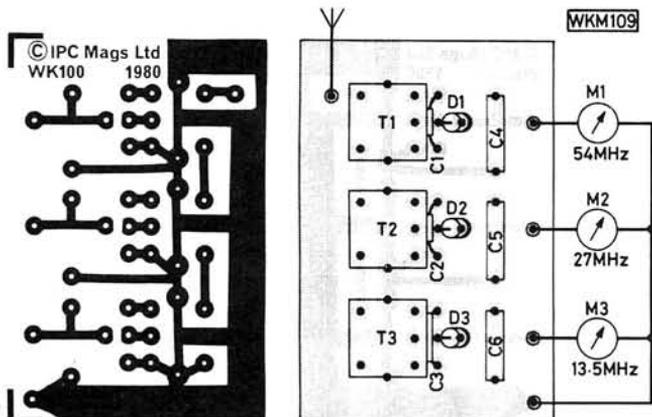


Fig. 5: The copper track pattern of the wavemeter p.c.b. shown here full size. Fig. 6 (above right): The component placement drawing of the wavemeter p.c.b. Ambit International will be able to supply ready built and aligned boards for those constructors without the necessary gear

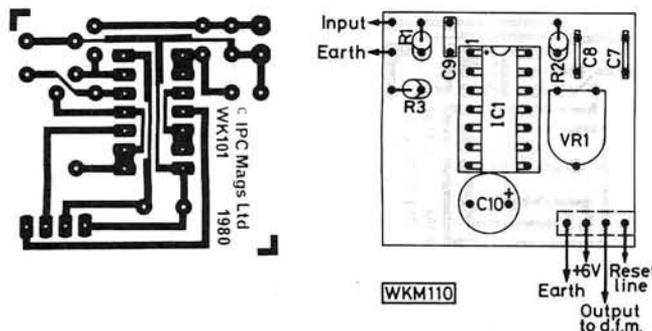


Fig. 7: The copper track pattern of the add-on period measuring unit shown here full size. Fig. 8 (above right): The component placement drawing for the add-on unit. This board plugs directly onto the main d.f.m. board as shown in Fig. 4

WAVEMETER

Capacitors

Ceramic

10pF	1	C1
30pF	1	C2
120pF	1	C3

Polyester

0.1μF	3	C4,5,6
-------	---	--------

Semiconductors

Diodes

OA91	3	D1,2,3
------	---	--------

Inductors

KXNK3335 (Toko)	3	T1,2,3
-----------------	---	--------

Miscellaneous

200μA f.s.d. meters (3); p.c.b.; sockets for aerial and leads (3).

The following items are only available as ready made modules:

- Display unit MSM5527 (Ambit)
- Prescaler board (Ambit)

The wavemeter board is available ready built and pre-aligned from Ambit International at a special price of £5.50 complete with 3 meters.

PERIOD MEASURING ADD-ON UNIT

Resistors

$\frac{1}{4}W$ 10%

1kΩ	1	R3
10kΩ	1	R2
2.2MΩ	1	R1

Potentiometers

Min. Horizontal present

4.7kΩ	1	VR1
-------	---	-----

Capacitors

Ceramic

100pF	1	C8
150pF	1	C7
10nF	1	C9

Electrolytic p.c.b. type

10μF 16V	1	C10
----------	---	-----


Semiconductors

Integrated Circuits

4093	1	IC1
------	---	-----

Miscellaneous

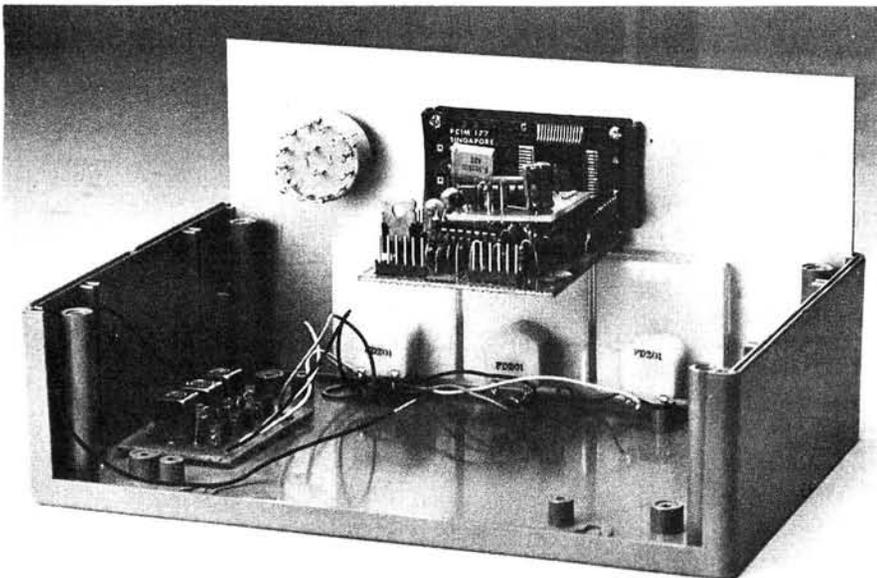14-pin d.i.l. socket (1); p.c.b.; Midget Wafer Switch 3p4w (1); 6V battery and connector; Knob (1); suitable case (see text); Bezel.



Internal view of the test set before final wiring. Note that the d.f.m. main p.c.b. has yet to have its extra support pillar fitted. This will be fitted between the bottom of the Verobox and the hole drilled in the rear corner of the p.c.b. and will consist of a suitable length pillar

The prototype was built into a large Verobox as this was the only case to hand with a large enough front panel to accept the three meters and the d.f.m. Any suitable box can be used, and either the wavemeter or the d.f.m. could be built into a smaller box on its own.

The d.f.m. display unit is mounted onto the bezel using the four screws and two plastic clamps supplied with the bezel. The four outer screws holding the display p.c.b. to the plastic front of the display must be carefully removed and the four holes in the p.c.b. carefully enlarged and continued right through the plastic panel to clear the bezel screws. Extra support is needed for the added board and the main p.c.b. to prevent strain.

The wavemeter aerial is a suitable length of thick copper wire soldered into a standard TV type of plug. The length is not particularly critical.

Three TV coaxial sockets are mounted on the top of the case and one is used for the wavemeter aerial while the other two are the inputs for the period counter and the digital frequency meter.

Power is supplied to the d.f.m. from a PP7 6V dry battery but a 9V battery could also be used by feeding the 9V into the appropriate pin on the d.f.m. board. Rechargeable NiCad cells could also be used and there is plenty of room in the box to accommodate the battery charger and servo tester described earlier in the series.

2 metre mobile multi-mode transceivers



FDK Multi-750E

ICOM IC-260E

Synthesiser steps	100Hz, 5kHz	100Hz, 1kHz (c.w./s.s.b.) 1kHz, 5kHz (f.m.)
Frequency stability	<500Hz (1-30min, <200Hz (1hr)	<±1.5kHz
Frequency read-out	5-digit green fluorescent	7-digit red l.e.d.
Reverse repeater mode	No	Yes
Memories	None	3 channels
Non-standard offsets	Yes (2 v.f.o.s)	Yes (2 gangable v.f.o.s)
Supply requirements⁽²⁾	Transmit: 3A/2A ⁽³⁾ Receive: 0.4A/0.8A ⁽⁴⁾ Memory back-up 1.5mA	Transmit: 3.1A/1.6A ⁽³⁾ 2.2A s.s.b. Receive: 0.6A/0.8A ⁽⁴⁾ Memory back-up: ■
Case size (H x W x D)	73 x 163 x 260mm	64 x 185 x 223mm
Weight	2.6kg (approx.)	2.7kg
TRANSMITTER		
Power output⁽³⁾	10W/1W	10W/1W
Spurious emissions	Below -60dB	Below -60dB
Microphone	500-600Ω dynamic	1.3kΩ dynamic ⁽⁶⁾
Repeater access tone	Auto burst	Auto burst
Satellite frequency unlock	No	No
RECEIVER		
Intermediate frequencies	10.7MHz and 455kHz (c.w./s.s.b) 10.7MHz (f.m.)	10.75MHz and 455kHz (c.w./s.s.b.) 10.75MHz (f.m.)
Sensitivity: c.w./s.s.b. f.m.	0.4μV for 10dB S/N 0.6μV for 20dB quieting	0.5μV for 10dB S+N/N 0.6μV for 20dB quieting
Selectivity⁽⁷⁾: c.w./s.s.b. f.m.	2.2kHz/6kHz 15kHz/25kHz ⁽⁸⁾	2.4kHz/4.8kHz 15kHz/30kHz
Spurious response rejection	>60dB	>60dB
RF Gain control	Yes	No
AGC Fast/Normal switch	No	Yes
Audio output into 8Ω	>1.2W at 10% t.h.d.	>2W
Programmable band scan	No	Yes
Scan for vacant or busy channel	No	No
Priority channel monitor	No	No
PRICE		
Including standard accessories and VAT	£299 Waters and Stanton Electronics Ltd.	£339 Thanet Electronics Ltd.



Trio TR-9000

100Hz, 10kHz⁽¹⁾ (c.w./s.s.b.)
 100Hz, 12.5kHz, 25kHz (f.m.)
 <±500Hz (1-60min)
 <50Hz any 30min thereafter
 5-digit red l.e.d.
 No
 5 channels
 Yes (Memory channel 5)
 Transmit: 2.9A/1.3A⁽³⁾
 Receive: 0.4A
 Memory back-up: 2.5mA
 68 x 170 x 234mm
 2.5kg

10W/1W⁽⁵⁾
 Below -60dB/-46dB⁽³⁾
 500Ω dynamic
 Auto burst
 No

10.695MHz and 455kHz (c.w./s.s.b.)
 10.695MHz (f.m.)
 0.2μV for 10dB S/N
 0.2μV for 10dB S/N
 2.2kHz/4.8kHz
 12kHz/25kHz
 >70dB
 Yes
 No
 >2W at 10% t.h.d.
 Yes⁽¹⁰⁾
 No
 No

£365

Lowe Electronics Ltd.



Yaesu FT-480R (FT-280)

10Hz, 100Hz, 1kHz (c.w./s.s.b.)
 1kHz, 25kHz, 100kHz (f.m.)
 ■
 7-digit blue fluorescent
 No⁽⁹⁾
 4 channels
 Yes (2 v.f.o.s)
 Transmit: 3A
 Receive: 0.5A
 Memory back-up: ■
 60 x 180 x 240mm
 2.6kg

10W/W
 Below -60dB
 600Ω dynamic
 Manual from front panel or
 microphone⁽⁹⁾
 Yes

■
 ■
 0.5μV for 20dB S/N
 0.5μV for 20dB S/N
 2.4kHz/4.1kHz
 14kHz/25kHz
 >60dB
 No
 No
 2W at 10% t.h.d.
 No
 Yes⁽⁹⁾
 Yes

£359

South Midlands Communications Ltd.
 (FT-280 from Amateur Radio Exchange)

2 metre mobile multi-mode transceivers

Notes:

1. In "Decade Scan" mode.
2. All rigs run on 13.8V d.c. nominal (negative ground).
3. The first figure is for full power, the second for low power.
4. The first figure is on standby (receiver squelched), the second for full audio output.
5. Low power not available on s.s.b.
6. Built-in pre-amplifier.
7. The first figure is the minimum -6dB bandwidth, the second the maximum -60dB bandwidth.
8. Maximum -70dB bandwidth.
9. The FT-280 is imported direct from Japan by Amateur Radio Exchange, and modified by them to suit the European market. It differs from the FT-480R only in that: (a) It has auto toneburst. (b) It has reverse repeater facility from front panel and microphone controls. (c) It does not have the "Vacant/Busy" scan mode selection switch.
 We understand that stocks of the FT-280 are very limited.
10. Any kilohertz decade can be scanned on c.w./s.s.b.

Common Features

All the rigs listed are based on digital p.l.l. v.c.o. synthesisers, and cover the range 144.0000-145.9999MHz, recycling at the band edges. Emissions available are: A1 (c.w.), A3J (u.s.b. and l.s.b.), and F3 (f.m.). Maximum deviation of F3 is ±5kHz. Aerial impedance is 50Ω in all cases. On A3J, suppression of the carrier and unwanted side-band is greater than 40dB, and all rigs are provided with impulsive noise blankers and r.i.t. controls.

Each transceiver can retain the frequencies set on the dial and memories, so long as 13.8V d.c. remains available. None incorporates a separate back-up battery, though, so all programmed frequencies are lost when shifting from house to car, etc.





2 metre mobile multi-mode transceivers

All the data given is extracted from the instruction manual specification tables, presented in a way to allow sensible comparison, so far as practical. A black square (■) denotes that no information appears in the manual.

The memory systems, etc., in all sets but the FDK, are somewhat complex in the facilities they provide, more so than we have space to deal with here, and we have simply tried to summarise the salient features.

First Impressions

FDK Multi-750E

The FDK Multi-750E is a somewhat more basic rig than the others listed in this survey; it has no memory facilities, for example, but this is well reflected in the price. It is very easy to drive.

The transmitter audio quality was reported by distant stations to be marginally less good than that from the other sets. The frequency read-out is big and bright, but the little "14" indicating the tens of megahertz seems an unnecessary embellishment, looking almost like a channel number. The "MHz" shift button provides a quick and easy way of hopping between the f.m. and sideband sections of the band. The push-buttons, by the way, are a most unusual shape, and handle very well. The "High/Low" power switch is on the rear panel, which has the effect of encouraging you to use full power all the time. The instruction manual is very basic.

One feature of interest to 70cm devotees is the ability to transvert or even work cross-band with an optional 430-440MHz transverter unit which will be available shortly.

ICOM IC-260E

The ICOM IC-260E is a very versatile rig, having two independent v.f.o.s which can be ganged together if required, tracking across the band at a

given separation for non-standard frequency offsets. The tuning control has a decidedly "gritty" feeling and has a very low rate. In fact, a little clip-on handle is supplied which can be fitted to speed things up. An optional microphone with scanning and frequency step controls makes a useful substitute to the main tuning knob.

Scanning of a limited portion of the band is possible, by programming the two band limits into memory positions 2 and 3, and the IC-260E is unusual in that it will auto-stop on a station on all modes, rather than just f.m. as all the other sets do.

All controls are on the front panel, and the frequency read-out is large and reasonably bright for daylight use. The mobile mounting bracket is of the quick-release type, with catches on each side.

The instruction manual is very comprehensive, with a detailed operational guide, trouble-shooting and voltage charts, block diagram, circuit diagram and printed circuit board layouts.

Trio TR-9000

The most unusual feature of the Trio TR-9000 is its decade scan, which allows any selected 10kHz segment of the band to be scanned rapidly in 100Hz steps when operating on c.w. or s.s.b. The same control allows the band to be scanned rapidly in 25 or 12.5kHz steps when on f.m. On c.w./s.s.b. you can hear the station(s) being swept through, but punching the button at the right moment to stop the scan actually on the station is rather akin to trying to hit the target in those video shooting gallery games.

All the controls are on the front panel, and easy to operate (apart from the above).

The frequency read-out is nowhere near bright enough, and on a bright sunny day in the car it just about completely disappears.

The receiver audio output has got plenty of punch, and of all the sets tested, is most easily heard above the usual mobile background.

The instruction manual is in the usual Trio format, with lots of information, but somewhat disjointed and therefore hard to follow in places.

Yaesu FT-480R/FT280


The Yaesu FT-480R (and its half-brother the FT-280—see Note 9) are the very latest arrivals in multi-modes, and incorporate a couple of novel features. The frequency read-out is a small and very bright fluorescent display, no problems on bright sunny days here. If anything, Yaesu have gone to the other extreme, and should perhaps incorporate a dimmer for night-time use, since the display has a tendency to "halo" in dull surroundings. The i.e.d. power/"S" meter is bright and easily readable, though it has a disconcertingly long decay time. The r.i.t. is digital, and the shift is added into the receive frequency read-out. Control is by means of the main tuning knob. For some reason, Yaesu call this facility a clarifier, which does not accord with the normal use of the term. The memory selector and frequency step controls are concentric and are fitted with rather unsuitable knobs, so that we found we tended to turn the wrong one nearly every time in our tests. A very thoughtful feature is the "F-SET" button, which zeroes the frequency in on the selected step when changing from, say, 100Hz to 25kHz, without having to wind off all the redundant digits manually.

Both the '280 and the '480 which we had on test had a very occasional tendency to switch suddenly to 144.900MHz when you tried to QSY off a calling channel. It was generally necessary to switch the set off to restore normal operation, which could be somewhat inconvenient.


The front panel on this rig is small, not much bigger than the average f.m.-only mobile. This has been achieved at the cost of a bulge underneath, to house the loudspeaker, and more significantly three switches under the front lip (two in the FT-280). These are the "Satellite" switch, which allows the transmitter frequency to be changed whilst actually transmitting, the "Busy/Manual/Open" scan control switch, and the "Simplex/+/-" mode switch. It is annoying, to say the least, to have to peer under the rig to operate the last two, although I suppose you would eventually get used to them.

The instruction manuals were provisional and very sketchy. No doubt the final ones will be to the usual Yaesu standard.


AMATEUR RADIO EXCHANGE

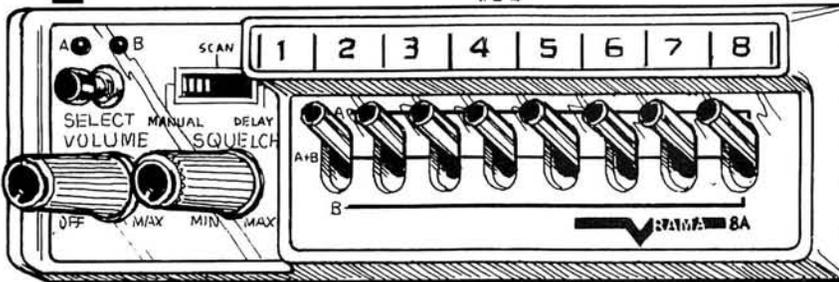

**A RAMA-8A
AIR-BAND
SCANNER**

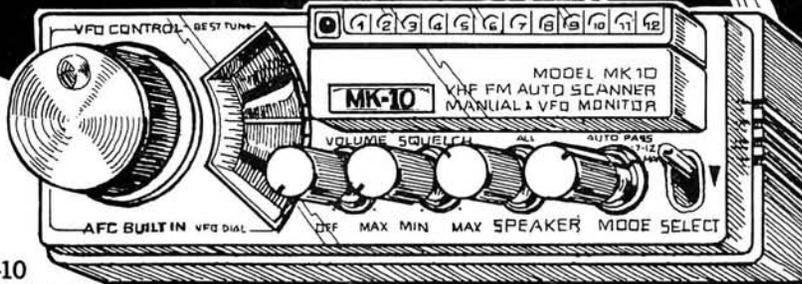

**B MK-10
AMATEUR-BAND
RECEIVER**

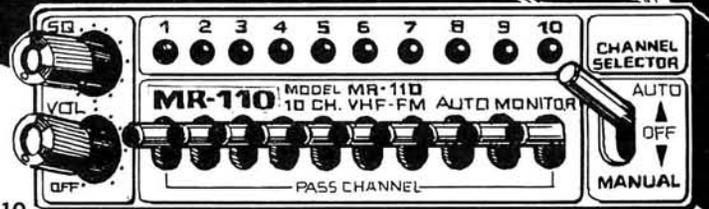

**C MR-110
AMATEUR-BAND
RECEIVER**



**D MR-1000A
POCKET SCANNING
RECEIVER**

HERE...NOW..

A really competitive range of scanning receivers, all offering top-grade technical specifications and unbelievable value for money. Come and try them in the shop, or phone your orders and enquiries (24-hour answer service when we're closed).

A RAMA-8A 16-channel capability crystal-controlled air-band scanning receiver, covering 108–136 MHz. Choose 8 or 16-channel scanning, or manual operation. Sensitivity $1\mu\text{v}$ (10 db S/N). 12v or mains. **BASIC PRICE £79.**

B MK-10 VHF scanning receiver, covering 144–152MHz. Scanning or manual tuning through up to 12 crystal-controlled frequencies, **OR** VFO control on main dial. Automatic lock-out facility. Sensitivity $1\mu\text{v}$ (25 db S/N). 12v only. **BASIC PRICE £69.**

C MR-110 VHF scanning receiver. 10-channel capability, with lock-out facility. Sensitivity $0.8\mu\text{v}$ (20 db S/N). 12v only, ideal for mobile operation. **SPECIAL PRICE JUST £49 FITTED 5 CHANNELS EX-STOCK.**

D MR-1000a The finest-value pocket receiver ever offered. VHF scanner, 10 channels, and allowing scan or manual tuning across selected crystal-controlled channels. Complete with Nicads and charger. **BASIC PRICE ONLY £39.**

**CRYSTALS: £2 PER CHANNEL FOR ALL MODELS.
ALL PRICES ARE POST-FREE AND INCLUDE VAT.**

AMATEUR RADIO EXCHANGE,
2 Northfield Road, Ealing, London, W13 9SY.
Telephone: 01-579 5311.

CREDIT CARD
SALES BY
TELEPHONE.



Antennas Receivers Transceivers

your
BARGAIN
Shopping List!

ANTENNAS

THE JOYSTICK VFA

● THE MICROSCOPIC 230cm. GIANT Joystick VFA (Variable Freq. Antenna) ● Simple, rapid erection ● Not only 6-band but CONTINUOUS 0.5 – 30 Mhz., incl BC ● Omnidirectional ● Substantially harmonic-FREE ● 1 million miles per watt, world-record! ● Poor QTH's enhanced! ● QUOTE from RADIO ZS (South Africa) "A remarkable antenna with great possibilities. Its physical size makes confined space operation a practical proposition".

SYSTEM "A" Includes matching ATU For the SWL or 160m. Tx. **£48.55**

NEW JOYMASTER SYSTEMS

● Amateur Bands 3.5 – 30 Mhz ● System "J" has been superseded by our IMPROVED JOYMASTER SYSTEM "JM2" ● SYSTEM "JM3" is a NEW DEVELOPMENT for the PRISONER OF CIRCUMSTANCE! ● THE HIGH-RISE BLOCK DWELLERS DREAM! ● Can be co-ax fed at a distance.

SYSTEM "JM2" Includes matching ATU 500 w.p.e.p. **£69.00**
SYSTEM "JM3" Includes matching ATU 500 w.p.e.p. **£90.00***

*Does not include 50 ohm. coax. cable where required to feed remotely located JOYSTICK VFA.

RECEIVERS

● FRG7 ● FRG7000 ●

COMPLETE RECEIVING STATIONS – ASSEMBLED IN SECONDS!

● FRG7 + free wire aerial ONLY £187.00 ● FRG7000 + free wire aerial ONLY £336.00 ● Package "R.1." (FRG7 + ATU + World Record VFA and FREE HEADPHONES) £218.00 ● Package "R.2." (FRG7000 + ATU + World Record VFA and FREE HEADPHONES) 368.00.

TRANSCEIVERS ETC.


We reckon we're offering the
LOWEST YAESU PRICES

Try phoning us for your *personalised* quote, with or without Partridge antennas. For example:

● FT901DM – ONLY £790!! ● FT101ZD – ONLY £567!! ● FT7B – ONLY £369!! If you take Partridge products as part of a "Package" deal, you'll save even more!

VHF BUSINESS RADIO

● We can help! Just phone or send stamp.

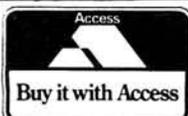

JUST TELEPHONE YOUR CARD NUMBER

0843 62535 (ext 5) (62839 after office hours) or send 12p stamp for FREE literature. Prices correct as at press. NOTE our prices are always INCLUSIVE OF VAT, carriage. Prompt service too, goods usually despatched WITHIN 48 HOURS!

5 Partridge House,
Prospect Road, Broadstairs, Kent CT10 1LD
(Callers by appointment).

G3CED
G3VFA



TR9000

READ THE REVIEW IN THIS ISSUE,
AND THEN COME ALONG AND
TRY IT FOR YOURSELF AT

M.R.S.
COMMUNICATIONS LTD.

76 Park Road, Whitchurch,

CARDIFF

Tel: Cardiff (0222) 616936

OPEN
9 am to 5 pm
6 Days



MORSE TUTOR

The uniquely effective method of improving and maintaining Morse Code proficiency. Effectiveness proven by thousands of users world-wide.



- ★ Practise anywhere, anytime at your convenience.
- ★ Generates a random stream of perfect Morse in five character groups.
- ★ D70's unique "DELAY" control allows you to learn each character with its correct high speed sound. Start with a long delay between each character and as you improve reduce the delay. The speed within each character always remains as set on the independent "SPEED" control.
- ★ Features: long life battery operation, compact size, built-in loudspeaker plus personal earpiece.

ACTIVE RECEIVING ANTENNAS

Datong active antennas are ideal for modern broadband communications receivers – especially where space is limited.



Price **£49.45**

- ★ highly sensitive (comparable to full-size dipoles).
- ★ Broadband coverage (below 200 kHz to over 30 MHz).
- ★ needs no tuning, matching or other adjustments.
- ★ two versions AD170 for indoor mounting or AD370 (illustrated) for outdoor use.
- ★ very compact, only 3 metres overall length.
- ★ professional performance standards.

Prices: Model AD170 (indoor use only) **£42.55**
Model AD370 (for outdoor use) **£56.35**
Both prices include mains power unit.

VERY LOW FREQUENCY CONVERTER

If your communications receiver gives poor results below 500 kHz Model VLF is the answer.

- ★ Connects between antenna and receiver input.
- ★ Converts signals between DC and 500 kHz to the range 28 to 28.5 MHz with low noise and high sensitivity.
- ★ Crystal controlled for high stability.
- ★ Quality construction in diecast aluminium box (size 112 x 62 x 31mm), SO239 connectors, LED indicator, in/out switch.
- ★ Operates from internal 9 volt battery or external supply (5-15 volts DC).

Price: only **£25.30**

Our full catalogue plus further details of any product are available free on request.
All prices include VAT and postage and packing.

**DATONG
ELECTRONICS
LIMITED**

Spence Mills, Mill Lane,
Bramley, Leeds LS13 3HE
England.
Tel: (0532) 552461

'SLIM JIM'

FRED JUDD G2BCX

for 28MHz

Since the publication of my article on the "Slim Jim" omni-directional aerial for 2 metres, many readers have written about its possible use for the 28MHz (10 metre) band. Indeed, quite a number have already tried it for themselves by scaling up the dimensions, and have discovered that excellent results are possible.

It is appreciated that a version for 10 metres cannot be constructed to exactly the same format as that for 2 metres. The general configuration is the same, however, and a suggested design is shown in Fig. 1. For the benefit of new readers, and as a reminder to others, Fig. 1(a) shows the electrical behaviour of the aerial. It consists simply of a half-wave folded radiator, fed at one end from a quarter-wave stub which is used to obtain an impedance transfer from 50 or 70 ohm coaxial cable to the high impedance connection to the half-wave section of the aerial. Fig. 1(b) gives the required dimensions of the elements, which may be of heavy gauge copper wire (14 or 16 s.w.g. or multi-strand copper "aerial" wire). Tinned or enamelled wire would be preferable.

The main support could be a bamboo pole which is quite light in weight and strong, although finding a single pole this long is not easy. It might be possible to acquire a couple of the 15ft canes used to roll carpets on and join them end-to-end. Whatever method is used to join them (wooden dowel glued down the centres, or plastics water pipe used as a sleeve, are two suggestions), it will then be necessary to stay the pole at top and centre. The stays (three at each level, spaced at approximately 120° intervals) should be either of non-conducting rope, or of wire rope broken up with "egg" insulators. The lengths of the stay sections should be around one third of a wavelength (3.3m) and preferably not all exactly the same length.

An alternative way of erecting the aerial, if you have a couple of support points at around 10m above ground level, would be to suspend the "Slim Jim" from a stay run between them.

Small wood spreaders fitted with miniature stand-off insulators are used to support the wire elements. The feed cable can be 50 or 70 ohms impedance, and the correct tapping points to the stub section, about 300mm up from the bottom, are found by temporarily connecting the cable with crocodile clips, and moving them up and down until minimum v.s.w.r. is obtained. This should be less than 1.5 to 1. This adjustment can be made with the bottom of the aerial a metre or so off the ground, but standing vertically of course.

In a situation where there are a lot of buildings around, the operational height should be such that the bottom of the aerial is 3 to 5 metres above ground. The theoretical optimum vertical angle of radiation of about 15° to 20°, as in Fig. 1, is obtained when the centre point of the radiating section is about $\lambda/2$ above ground, but this applies only where the soil beneath has good conductivity and the aerial is situated in very clear surroundings. It would be worthwhile to experiment with height. Radiation is of course vertically polarised and omni-directional, but

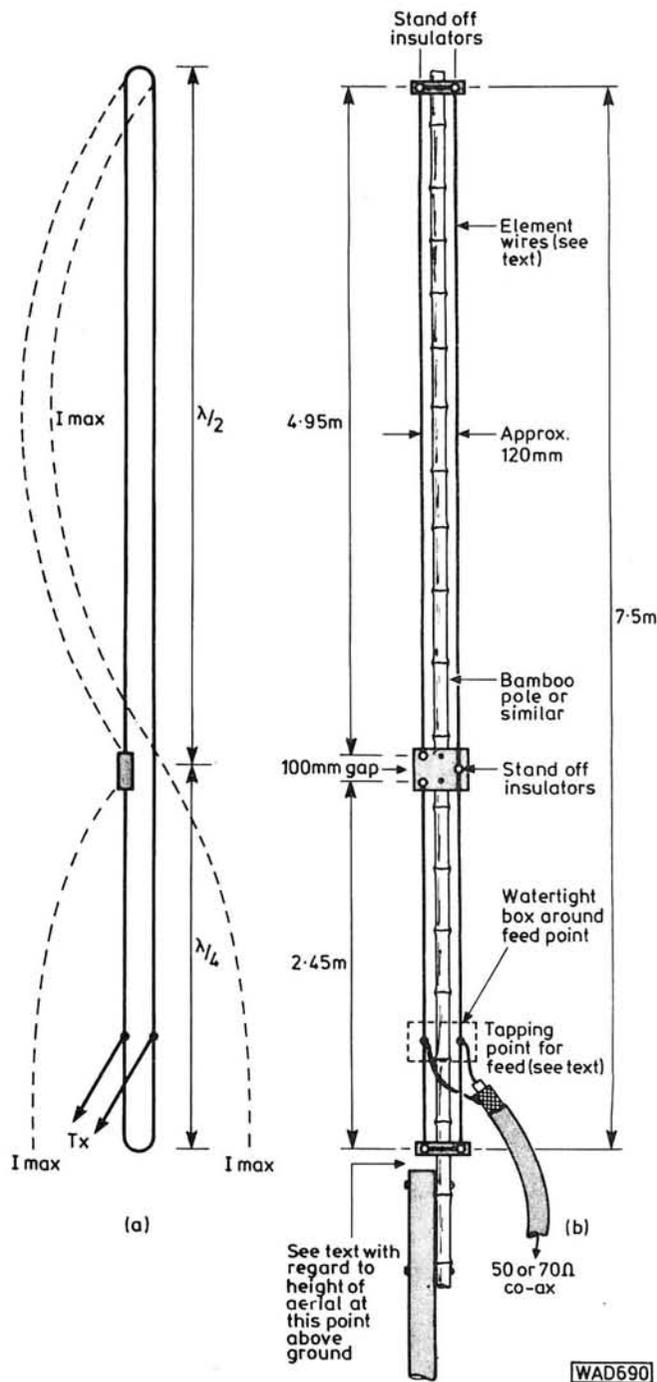


Fig 1: (a) Electrical function of the "Slim Jim" aerial. (b) Suggested method of constructing a "Slim Jim" for 28MHz (10 metres)

continued on page 86 ▶▶▶

COMPARE THESE FEATURES

- ★ MICROPROCESSOR CONTROLLED 32,000 CHANNELS
- ★ AM & FM ALL BANDS
- ★ WIDER COVERAGE: 26-58, 58-88, 108-180, 380-514MHz; includes 10m, 4m, 2m, & 70cm Amateur bands.
- ★ 5kHz & 12½kHz FREQUENCY INCREMENTS
- ★ 16 MEMORY CHANNELS WITH DIRECT ACCESS
- ★ SELECTIVE PRIORITY CHANNELS WITH LOCKOUT
- ★ 2 SPEED SCAN SCAN DELAY CONTROL
- ★ 2 SPEED SEARCH UP AND DOWN
- ★ SEARCH BETWEEN PRESET LIMITS UP AND DOWN
- ★ 3 SQUELCH MODES inc. CARRIER & AUDIO
- ★ Dx & LOCAL CONTROL
- ★ RELAY OUTPUT FOR Aux. CONTROL
- ★ EXTERNAL SPEAKER & TAPE OUTPUTS
- ★ LARGE GREEN DIGITRON DISPLAY BRIGHT/DIM
- ★ AM-PM CLOCK DISPLAY
- ★ 12v DC, 230V AC OPERATION

"See us on Stand 27 at the ARRA Exhibition at the Granby Halls, Leicester. 6th, 7th & 8th November."

U.K. IMPORTERS & DISTRIBUTORS:
REVCO ELECTRONICS LTD.
POUNDWELL STREET
MODBURY, DEVON, PL21 0RQ
Tel: Modbury (0548) 830665
Dealer enquiries invited

SX200

THE ULTIMATE SCANNER



£241.50 INC. VAT Delivered

MAIN SERVICE & SALES AGENTS:
GAREX ELECTRONICS
7 NORVIC ROAD
MARSWORTH, TRING
HERTS HP23 4LS
Tel: Cheddington (0296) 668684



OSMABET LTD

We make transformers amongst other things.

TRANSFORMERS TO ORDER

We have capacity for the supply of transformers to specification, either one off, or production runs, your enquiries please.

LOW VOLTAGE TRANSFORMERS: Prim 240V ac.
 6.3V 1.5A £3.00; 3A £4.15; 6A CT £7.90; 12V 1.5A £3.75; 3A CT £7.90; 6A CT £9.75; 15V 0.5A £3.00; 18V 1.5A CT £7.90; 24V 1.5A CT £7.90; 3A CT £9.75; 5A CT £18.00; 8A CT £29.25; 12A CT £37.50; 40V 3A CT £13.50.

MIDGET RECTIFIER TRANSFORMERS: Prim 240V ac.
 6.0-6V 1.5A or 9.0-9V 1A £3.40 each; 12.0-12V 1A or 20.0-20V 0.75A £4.15 each; 9.0-9V 0.3A or 12V 0.12V 0.25A or 20V 0.20V 0.15A £3.00 each.

LT TRANSFORMERS TAPPED SEC: Prim 240V ac.
 0-10-12-14-16-18V 2A £7.50; 4A £9.40; 0-12-15-20-24-30V 2A £8.25; 4A £12.00; 0-20-30-60V 1A £9.00; 2A £12.00; 0-40-50-60-80-100-110V 1A £12.00.

AUTO & ISOLATION TRANSFORMERS 240/110V ac.
 30 to 4000 watts, many types ex stock. Lists.

MAINS TRANSFORMERS. SPECIAL OFFER. Prim 240V ac.
 300-0-300V 80 Ma; 6.3V 1A CT; 6.3V 1A £5.50; 250-0-250V 60 Ma; 6.3V 1A £3.00; 9V 3A £2.50; 25V 300 Ma 90p.

LOUDSPEAKERS
 1½", 1½", 2½", 2½", 2½" 8Ω £1.25 each; 3" 35Ω 31", 3, 8, 16, 80Ω, 7x4" 3 or 80Ω £1.75; 8x8" 25Ω £2.50.

Goodman 5" Hi-Fi speaker mid range, C/M 3 25 watt systems £6.50. Goodman 3½" Tweeters C/M, 80 for 25V systems. £2.50.

"INSTANT" BULK CASSETTE/TAPE ERASER
 Instant erasure of cassettes, and any diameter of tape spools, demagnetises tape heads, 200/240V ac. leaflet £8.00.

EDGWISE LEVEL METER FSD 200/µA
 Size 19x18x20mm 8000 £1.50.

CHARGING METERS 1½in diameter
 2A or 3A £1.25 each; 5A or 10A £1.50 each.

SINGLE STRANDED WIRE PVC COVERED
 32/0.2mm (10A) black or blue, £6.50 100m, 0.5mm £2.50 100m special prices per 1000m and over.

POWER SUPPLY, TWIN OUTPUT Prim 240V ac:
 New, British manufacturer, smoothed d.c. output 20V, 1.5A, plus STABILISED output of 15V 100 Ma, plus further 12V ac 0.5A, complete with diagram, £4.00.

O/P TRANSFORMERS FOR VALVE AMPLIFIERS
 P.P., sec tapped 3-8-15Ω A-A 6KΩ, 30W £17.50; A-A 3KΩ 50W £26.00; 100W (EL31, KT88 etc) £35.00.

G.E.C. MANUAL OF POWER AMPLIFIERS
 Covers valve amplifiers 30W to 400W £1.25.

MULTIWAY SCREENED CABLE, PVC COVERED
 36 way £1.00; 25 way 75p; 14 way 50p; 6 way 25p.

CONDENSERS AC 50Hz, 4.33/250V, 6/330V, £1.50.
 Electrolytic 400 µ 400V 75p; 2000/30V 30p; 2200/40V 40p; Paper tubular, W/E, 4/160V; 6/160V 30p each, 2mfd 150V 25p, 0.1mfd 2KV 50p.

CARRIAGE EXTRA ON ALL ORDERS
ALL PRICES INCLUDE V.A.T.

Callers by appointment only. S.A.E. Enquiries, Lists.

46, Kenilworth Road, Edgware, Middx.
HAB BYG. Tel: 01-958 9314

HOME BRU RADIO

(Mail order only)

G4CLF P.C.B.

SPECIAL OFFER

SET OF IC's and P.C.B.

To include:— 1 off G4CLF P.C.B.,

2 off SL1612, 1 off SL1621,

1 off SL1626 or SL6270,

2 off 1640, 1 off SL6310,

£18 incl. VAT.

+30p. p&p.

G4CLF P.C.B. **£4.24**

SL1612 **£1.56**

SL1621 **£2.07**

SL1626 or SL6270 **£2.51**

SL1640 **£2.07**

SL6310 **£2.51**

+30p. p&p.

"HELFDORD"

TROUBLESHOOTING

(A unique service by the designers of the Helford)

Any query regarding building we receive, providing it is accompanied with a S.A.E. and one of our INVOICE NUMBERS, we will do our best to answer.

HOME BRU RADIO

(Mail order only)

55 Ashley Road, Parkstone,
Poole BH14 9BT.

H.A.C. SHORT-WAVE KITS

WORLD-WIDE RECEPTION

'H.A.C.' well known by amateur constructors for its Short Wave receivers, now offers a complete range of kits and accessories which have been up-dated to suit the novice and the expert.

£14.50 INCLUSIVE — the ever popular and easy to construct DX receiver Mark III; containing all genuine short wave components, drilled chassis, valve, accessories and full instructions.

AT LAST — a battery eliminator kit, which will last you a lifetime — for use in all H.A.C. valve receivers. H.T. batteries are now unobtainable, this will solve your problems for only £9.60.

T TWIN TRANSISTOR RECEIVER, selective, sensitive and with fantastic reception, yet needing only a single PP3 battery, at £17.50 this receiver is outstanding value, and will give you hours of interest and entertainment.

NEW — TRIPLE-T RECEIVER, a more advanced super three transistor receiver, loud, clear reception, value unequalled at bargain introductory price of £24.00.

All orders despatched within 7 days. Send stamped and addressed envelope now for free descriptive catalogue of kits and accessories.

SORRY, NO CATALOGUES WITHOUT S.A.E.

"H.A.C." SHORT-WAVE PRODUCTS
P.O. Box No. 16, 10 Windmill Lane
Lewes Road, East Grinstead, West
Sussex RH19 3SZ



HF SSB TRANSCEIVER

Vic Goom G4AMW

Back in 1974, when the first SL600 board designed by G3ZVC was published, a rather primitive single band (20 metres) transceiver was built. Although only pushing out 5 watts this was a great success, even working into VK and W6—ultimately adding another dimension to Continental motoring, as being quite small it sat happily on the armrest between the seats.

When the PW Helford was in the early design stages, James Bryant, Plessey's applications manager offered to produce a new board, tailor-made for the job. It was therefore possible to press on with a completely compatible design, and for good measure Peter Chadwick, Plessey's applications engineer produced the power amplifier filters. Thanks are also due to the late Col Geoff Cole for the information on the driver and the p.a. which were obtained from T.R.W. of California.

In order to harness the G4CLF Board satisfactorily certain criteria have to be observed. The first essential is a stable v.f.o. and a very effective layout for this was drawn up by Peter Trowbridge. Secondly, the mixer must have a drive of 500mV from the buffer. A slightly modified cascade amplifier from a Plessey handbook provided this.

Although the PW Helford is presented here as a transceiver for 80 and 20 metres, it is intended to develop an oscillator and second-mixer board to convert it into a Five Band rig, already allowed for in the preselector.

The popular choice appears to be five wide-band double-tuned sets of coils a lot of wire and wave-change wafers with no means of tuning them. Thanks to the production of a four-gang tuning capacitor a rather neat solution was arrived at. By connecting the 80 metre pair of coils to two gangs and the 20 metre pair of coils to the remaining two gangs it was possible, with no top coupling switching, to put on the nose any frequency from 80 to 10 metres. It is felt that this can only enhance the dynamic range of the hot carrier diode mixer.

On the transmit side there can be no doubt that the ability to actually put 100W plus into the aerial, coupled with the Voice Operated Gain Adjusting Device (VOGAD) facility, does give the operator considerable talk power. Indeed when this rig was only at the drive stage so potent was the signal that it was difficult to get off the air to actually build the p.a., as Phil Ciotti, builder of the original Helford would readily admit.

The basic straight-forward simplicity of this transceiver is to some extent displayed by the block diagram (Fig. 1), but to a greater extent by the fact that the wavechange switch has only three wafers—as opposed to 12 to 15, which seems to be the going rate for commercial rigs.

Possibly the biggest shock to the proposed constructor is that the cost of the case is on a par with the filter. Of course a cheaper case could be used, but the precision and

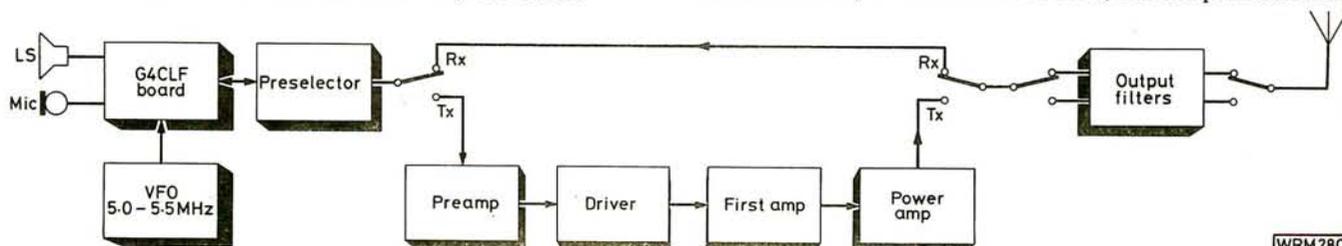


Fig. 1: The block diagram of the complete Helford transceiver

WRM280

CONSTRUCTION RATING **Advanced**

BUYING GUIDE

Builders of the *PW Helford* should have little difficulty in obtaining the components. The case is available from West Hyde, the meter and knobs from Sifam, while the variable tuning capacitors are by Jackson Bros and can be obtained from Watford Electronics. The components for the G4CLF Board can be obtained from Ambit International.

APPROXIMATE COST **£200**

accessibility of the West Hyde case does give the whole thing a stable, well-engineered feel.

It is obviously important to follow all the construction details closely but this is particularly so with regard to the preselector, a little bit of double checking before it is all fitted into the box is a very good idea, as shorts in this area are very difficult to trace—practically everything is grounded through the coils!

In practical terms what is the *PW Helford* capable of? When it was put on 20 metres for the first time, during the second week in June, conditions were generally reckoned to be pretty poor as at the time radio contact with the transatlantic yacht race was causing concern. However, working only the odd hour or so in the evening between June 9 and 15 the following stations were worked. PY1ZBS (5/7). ZS61W (5/5). CTIEL (5/8). CN8CW (5/8). 4NIU (5/9). WA9DJQ/M/M (5/9). VK2DM (5/6). PY4AH (5/8). J28AA (5/9). (DJIBOUTI) VP8HZ (5/6). (The antenna used was a 2-element beam at 30ft). The fact that this quite interesting collection of DX was worked on a relatively poor band with the European QRM in full spate, displayed not only the punch of which the *Helford* is capable, but that the receiver selectivity is not wanting either.

This first part of the series deals with the G4CLF Board designed especially for the *PW Helford* by James Bryant.

The G4CLF Board

This is a direct descendant of the SL600 transceiver described by Brian Comer, G3ZVC, in "Radio Communication" for September 1974 and afterwards in a number of other journals around the World. The original design used the Plessey SL600 series of communications integrated circuits and consisted of a single-sided board measuring 127 x 83mm and carrying nine integrated circuits, two transistors and a diode ring mixer. The board contained the entire works of an s.s.b. transceiver capable of working at any frequency from 10kHz to 500MHz with the exception of the local oscillator, preselector, r.f. power amplifier, power supply, microphone and loudspeaker.

This new version is smaller, only 102 x 76mm, and contains a number of improvements but uses an extra

integrated circuit and three extra transistors. The major improvements are increased sensitivity (0.2 μ V against 0.5 μ V), higher audio output (800mW against 100mW), tailored audio response (24dB/octave above 3.5kHz), on-board supply regulation (in fact two of the integrated circuits used in this design are regulators so the new version may, in one sense, be considered to have one less integrated circuit rather than one more), better filter matching and higher r.f. output. Minor improvements include the location of all input and output interfaces along one side of the board, trimmers on the sideband oscillator crystals, a better partition of gain between the i.f. and a.f. stages and lower oscillator radiation.

The circuit diagram of the transceiver is shown in Fig. 2 and may be broken down into six sections: the mixer, the bi-directional amplifier, the sideband filter, the receiver, the transmitter and the sideband oscillators.

The Mixer

The mixer consists of an Anzac MD-108 hot carrier diode ring mixer, identical to that used in the previous design. These mixers have three parts, each of 50 Ω impedance, an upper frequency limit of 500MHz and a lower limit on two parts of 5MHz and on the third of d.c. This transceiver uses the d.c. part as its r.f. port to permit operation at r.f. frequencies below 5MHz so that the 5MHz limit is unimportant on the other two ports.

The MD-108 has a third-order intercept point of +15dBm and an insertion loss of 7dB. It requires a local oscillator power of about +7dBm (500mV r.m.s.). The MD-108 has an elder, and more expensive, brother called the MD-138 which has a higher third-order intercept point but there is no point in using it in this particular design since the intermodulation performance of the system is set by the mixer, the bi-directional amplifier and the filter and improving one without improving the other will do little for the overall performance of the system.

Since the MD-108 is a passive device it is bi-directional and no switching is necessary between transmission and reception. It is important, however, that it is driven from 50 Ω sources and drives 50 Ω loads, otherwise its gain and intermodulation performance will suffer. On the board this 50 Ω match is performed by the bi-directional amplifier.

Table 1. G4CLF Board Performance

RECEIVE	
(+12V, +7dBm, Local Oscillator at 90MHz)	
Sensitivity:	Less than 0.3 μ v for 10dB SINAD
Dynamic Range:	114dB (Wanted Signals) 88dB (Off-frequency Signals)
Third-order Intercept:	+7dBm
Audio Output:	800mW
Current Consumption:	60mA (Minimum Audio Output)
TRANSMIT	
(+12V Supply, +7dBm, Local Oscillator at 90MHz)	
Output Level:	-5dBm (Single Tone)
Carrier:	-49dBm
Intermodulation Products:	-50dBm (Two tones 1.2kHz and 1.4kHz)
Dynamic Range of Audio a.g.c.:	(Without R32) 40dB (R32 = 1k Ω)
Current Consumption:	45mA

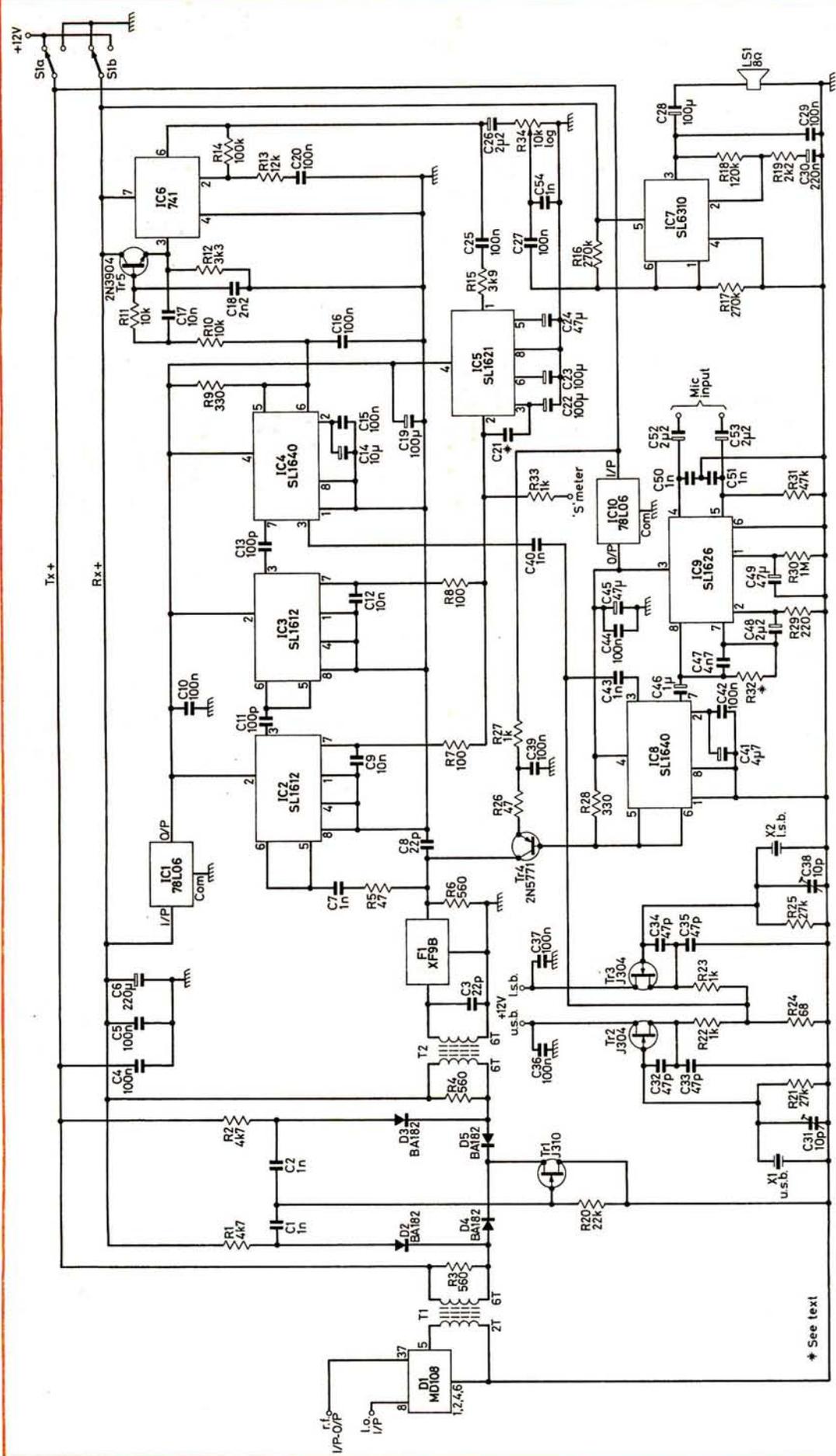


Fig. 2: The circuit diagram of the G4CLF Board

The Bi-Directional Amplifier

The bi-directional amplifier consists of a field-effect transistor, Tr1, four low capacity switching diodes, D2–D5, two transformers, T1 and T2, two capacitors, C1 and C2, and five resistors, R1–R4 and R20. The transformers act as impedance matching devices, together with resistors R3 and R4, and ensure that the mixer and the crystal filter are correctly terminated.

The diodes D2–D5 are used to reverse the direction of amplifier gain between reception and transmission. During reception the receiver power line is at +12 volts and the transmitter line is grounded. Diodes D2 and D5 are conducting and diodes D3 and D4 are biased off. Signal then passes from T1 via D2 and C1 to the gate of the f.e.t., whose output goes to T2 via D5.

When the power supplies are reversed during transmission the system works in exactly the same way but now diodes D3 and D4 conduct and the signal from T2 is amplified and passed to T1—and hence to the mixer.

The choice of diodes and f.e.t. in this amplifier is critical. If the diodes have too large a capacity when in the “off” state the amplifier can become unstable. The diodes chosen, Mullard BA182s, were designed for switching r.f. in television tuners and are ideal for this application.

The f.e.t. must have a high gain and also good intermodulation performance. To some extent as the gain increases the intermodulation performance falls off but this may be compensated by using a high current device. The f.e.t. finally chosen was a Siliconix J310, a junction f.e.t. in a TO92 plastic package, which has a standing current at zero gate bias of between 20mA and 60mA.

The original G3ZVC design used a single transformer between the mixer and the filter. The bi-directional amplifier offers a number of advantages: both the mixer and the filter are better matched, giving improved intermodulation and passband ripple; losses in the mixer are regained before further losses take place in the filter (in fact during reception there is 8dB gain from the input of the mixer to the output of the filter as opposed to about 9dB loss in the original design); and the gain during transmission allows a greater r.f. drive to the p.a. The improved performance seems to be worth the increased complexity.

The Filter

This design uses an XF9-B or a QC1246AX crystal filter, manufactured by KVG and Salford respectively. These are 8-pole 2.4kHz filters with a centre frequency of 9MHz. They require termination of 500Ω in parallel with 25pF which is provided by T2, R4 and C3 on the mixer side of the filter and R6 and C8 on the other side.

Many other filters might be used in this transceiver but there are a number of points to be considered. If a 4-pole or 6-pole filter is used the stopband suppression is reduced from over 90dB to as little as 50dB. This can degrade adjacent channel performance and lead to intermodulation problems in the i.f. from very strong local signals but there are compromises which may be accepted. Another problem can arise from the use of cheaper 4-pole or 6-pole filters which is not acceptable—blocking due to local oscillator leakage. The MD-108 has local oscillator attenuation of about 40dB which means that there may be 5mV r.m.s. of local oscillator signal present at its output and therefore some 25mV at the input to the filter. If the filter attenuation is 90dB this leakage is reduced to less than 0.8μV, which is unimportant, but if it is only 50dB then the i.f. strip sees 80μV of local oscillator leakage. If the transceiver is being used at v.h.f. this is unimportant since

the SL1612s in the i.f. strip have no gain at v.h.f. But in an h.f. transceiver this 80μV may be sufficient to block the i.f. strip, particularly if no a.g.c. is present. The problem was far worse in the original design which had three i.f. stages but it can cause trouble even with the present design.

The solution is simple. At v.h.f. lower performance filters may be used—at h.f. they may not!

Intermediate frequencies other than the 9MHz used here are perfectly acceptable. The system will work unchanged at 5.3MHz and 10.7MHz but i.f.s of over 15MHz or under 5MHz cannot be used. Above 15MHz the gain of the i.f. amplifier starts to drop and below 5MHz the MD-108 mixer loses gain. There is no way of extending the upper frequency limit but the lower one may be reduced by either of two methods.

One is to use the d.c. port of the MD-108 as the i.f. port. This allows the use of any i.f. down to 100kHz but prevents the use of r.f. or local oscillator frequencies below 5MHz which may or may not be a disadvantage. It will also be necessary to modify the p.c.b.

The other method is to replace the MD-108 with an MD-109. This is a lower frequency version of the MD-108 which is rather more expensive but has a frequency response from 200kHz to 200MHz. Of course with an MD-109 while it is possible to use i.f.s down to 200kHz it is not possible to work with r.f.s above 200MHz. This is unlikely to be a problem since the use of i.f.s below 5MHz with r.f.s above 200MHz is likely to lead to image problems and thus will tend to be avoided anyway.

If the transmitter performance is not to be degraded the bandwidth of the filter must not exceed 2.7kHz and the shape factor should be as good as possible.

Finally, if the filter is changed it may be necessary to change R4 and R6 and C3 and C8 to match it with the correct impedance. The resistors should be 10 per cent higher than the value given in the filter specification and the capacitors should be about 3pF lower and the circuit is not suitable for use with filters having impedances much greater than 1kΩ. If R6 is increased then R27 must be increased in the same ratio to preserve the d.c. levels on the transmitter driver transistor Tr4.

The Receiver

The receiver consists of two i.f. stages, a product detector, a low-pass filter, an audio amplifier, an audio-derived a.g.c. system and an audio output stage.

The i.f. amplifier uses two SL1612 circuits. These are similar to the SL612 circuits used in the original design but are supplied in 8-lead plastic minidip packages instead of metal ones. This lowers the price and makes the circuits easier to mount but has negligible effect on performance. All the circuits used in this transceiver, with the exception of the TO92 voltage regulators, are in 8-lead minidips.

Each SL1612 has a voltage gain of 34dB and an a.g.c. range of 70dB. The i.f. strip therefore has a gain of 68dB (2500 times) and an a.g.c. range of 140dB which cannot, of course, be used since the strip would overload with an input of 250mV r.m.s.—equivalent to dynamic range of about 114dB.

Each SL1612 has its own internal supply decoupling but the supply line is also decoupled near to them by C10, a ceramic 0.1μF capacitor. Interstage coupling capacitors are kept low to minimise the l.f. gain of the strip and eliminate possible interaction of the a.g.c. circuitry and the detector.

The detector, IC4, can use an SL1640 or an SL1641 as a product detector. These are both “transistor tree” double-balanced modulators and differ only in their output circuitry—the SL1640 has an internal load resistor as its

output on pin 5 and an emitter follower output on pin 6, the SL1641 has a free collector output on pin 5 and no connection to pin 6. In this application pins 5 and 6 are joined so that if an SL1640 is used its emitter follower is turned off. If an SL1641 is used an external load resistor of 330Ω is necessary (R9) but with an SL1640, R9 must not be used, and the position on the board must be left open-circuit.

The detector uses only two other components, the bias decoupling capacitors C14 and C15. The entire i.f. strip and detector therefore uses only three integrated circuits, three or four resistors, and eight capacitors. Being a broad-band system it does not use any further coils or filters and needs no set-up adjustment.

The output of the detector contains the sum and difference of its two inputs (signal from the i.f. strip and carrier from the sideband oscillator). The signal from the i.f. strip consists mainly of a 9MHz signal but there is a certain amount of broad-band noise in the range 100kHz to 20MHz. The sideband oscillator signal consists of a single frequency of 8.9985MHz or 9.0015MHz depending on the sideband in use, there is some noise here too, but it is low enough to be disregarded. The output therefore consists of a low frequency signal (the difference output) which is the output we want, a high frequency signal

around 18MHz (the sum output), and broad-band noise extending from d.c. to at least 30MHz. It is necessary to remove the h.f. output before the audio stages, and will give a more pleasant output signal if as much of the audio noise as possible is also removed.

This is done by a low-pass filter which is placed between the detector and the audio amplifier. This filter is designed to have 18dB/octave roll-off above 3.5kHz and consists of a single-pole filter formed by C16 and R9 (or the internal resistor equivalent to R9 if an SL1640 is used) followed by a two-pole Sallen and Key filter formed by R10, R11, C17, C18 and Tr5. The original design used a 2N3904 as Tr5 but if ever there was an application where the exact transistor used was unimportant this is it—all that is needed is a silicon npn transistor with a beta of over 80 and a V_{ce0} of over 9V.

The filter has a gain of unity and since the audio is still at a very low level (about 5 to 10mV r.m.s.) it is then amplified by 18dB in a 741 operational amplifier. Since the audio level is so low there is no possibility of clipping in this amplifier so bias is obtained by directly coupling the audio path from the detector through the low-pass filter to the 741. This saves components but provides no l.f. roll-off so that all subsequent audio coupling capacitors should be chosen to give roll-off below 300Hz, as should the

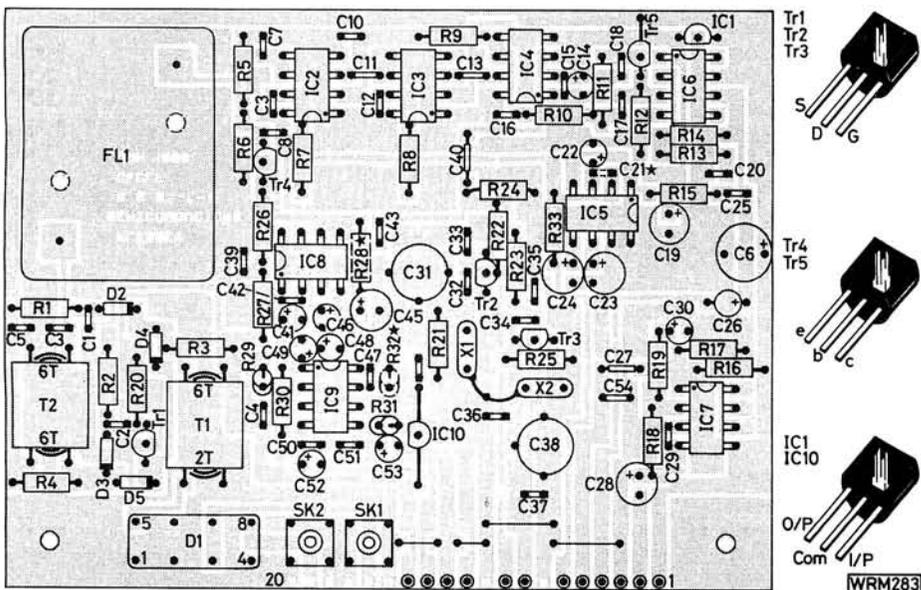
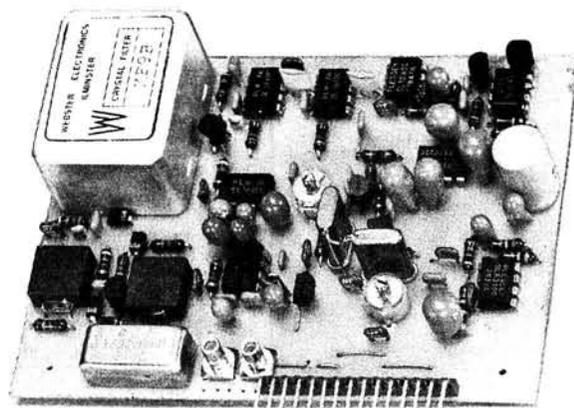
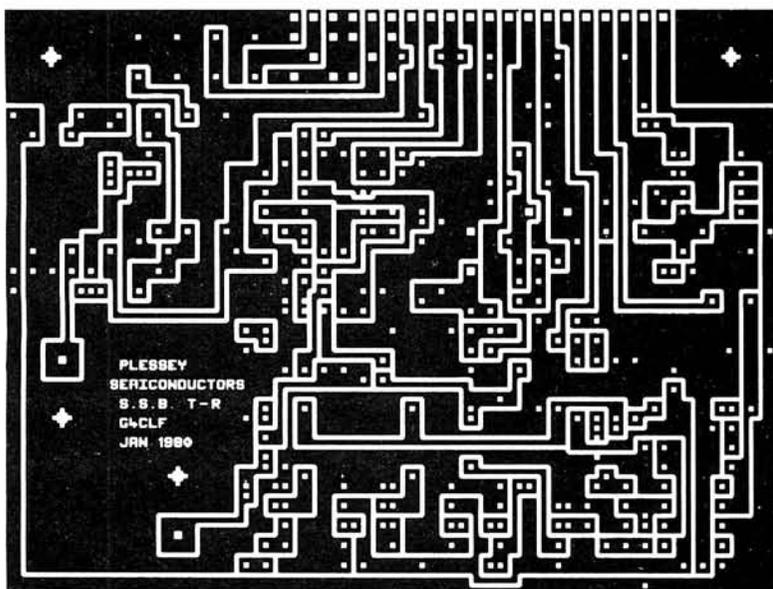


Fig. 3 (Top left): The copper track pattern shown full size, for the G4CLF Board

Fig. 4 (Left): The component placement details of the G4CLF Board. The photograph above shows the completed G4CLF Board before installation into the PW Helford

G4CLF Board

Resistors

10% 1/4W

47Ω	2	R5,6
68Ω	1	R24
100Ω	2	R7,8
220Ω	1	R29
330Ω	2	R9,28 (SL1641 only)
560Ω	3	R3,4,6
1kΩ	4	R22,23,27,33
2.2kΩ	1	R19
3.3kΩ	1	R12
3.9kΩ	1	R15
4.7kΩ	2	R1,2
10kΩ	2	R10,11
12kΩ	1	R13
22kΩ	1	R20
27kΩ	2	R21,25
47kΩ	1	R31
100kΩ	1	R14
120kΩ	1	R18
270kΩ	2	R16,17
1MΩ	1	R30

Semiconductors

Diodes

BA182	4	D2,3,4,5
MD-108 (Anzac)	1	D1

Transistors

J304 (Siliconix)	2	Tr2,3
J310 (Siliconix)	1	Tr1
2N3904	1	Tr5
2N5771	1	Tr4

Integrated Circuits

741	1	IC6
78L06	2	IC1,10
SL1612	2	IC2,3
SL1621	1	IC5
SL1640 or SL1641	2	IC4,8
SL1626 or SL6270	1	IC9
SL6310	1	IC7

Capacitors

Ceramic Sub-miniature Plate

22pF	2	C3,8
47pF	4	C32,33,34,35
100pF	2	C11,13

Monolithic Resin-Dipped Ceramic

1nF	8	C1,2,7,40,43,51,54
2.2nF	1	C18
4.7nF	1	C47
10nF	3	C9,12,17
100nF	14	C4,5,10,15,16,20,25, 27,29,36,37,39,42,44

Tantalum

220nF 35V	1	C30
1μF 35V	1	C46
2.2μF 35V	4	C26,48,52,53
4.7μF 35V	1	C41
10μF 16V	1	C14
47μF 16V	3	C24,45,49
100μF 10V	4	C19,22,23,28

Electrolytic P.c.b. Mounting

220μF 16V	1	C6
-----------	---	----

Miniature Trimmers

2-10pF	2	C31,38
--------	---	--------

Potentiometers

10kΩ log	1	R34
----------	---	-----

Miscellaneous

XF9-B or QC1246AX filter F1 (1); Crystals 30pF X1, X2 (see text); P.c.b.; B1 ferrite double aperture cores 11.3 x 11.3 x 5.8mm Mullard FX2249 (2); Min. coaxial sockets "smb" p.c.b. type (2).

decoupling capacitors in the feedback of the amplifiers IC6 (the 741) and IC7 (the output stage). The output from the audio amplifier goes to a volume control, which is off the board, and then to the audio output stage. It also goes directly to the a.g.c. system.

In the best s.s.b. receivers the a.g.c. is derived from the detected audio, and this technique is used here. The audio is applied, via a dropper resistor (R15), to the input of an SL1621 audio a.g.c. circuit. In this circuit, which requires only three external components, C22, C23 and C24, forms a sophisticated audio a.g.c. system which adapts quickly to new signals, tracks rising or fading signals at up to 20dB/s, holds a.g.c. constant during speech pauses, and reverts almost instantly to full system gain if a speech pause continues beyond one second—indicating a probable end of transmission.

The a.g.c. output from IC5 is applied to the two i.f. stages via 100Ω resistors (R7, R8) and is also taken off the board to act as the "S" Meter drive. The a.g.c. line has a value of about 2V at the a.g.c. threshold and increases by about 12.5mV for each dB increase in signal (80dB/V). The 2V threshold is temperature dependant and may be

compensated by three silicon diodes. A simple "S" Meter is generally adequate as shown in Fig. 6. This is another circuit where the actual transistors used are unimportant—any small-signal silicon *npn* transistors and small silicon diode will do. The 1.5kΩ resistor (R35) may need some slight adjustment to give the correct range.

The capacitor C21, shown in the circuit diagram, should not be necessary if the receiver is to be used for speech only and will probably not be necessary with c.w. But under some circumstances it is possible to find low frequency instability in the a.g.c. system during the reception of c.w. The insertion of C21, which may have a value between 0.1μF and 1.0μF, cures the problem.

The audio output stage uses a new circuit, the SL6310, which is an audio power amplifier in an 8-lead minidip package capable of delivering between 800mW and 1W into 8Ω with a 12V supply. As can be seen the SL6310 uses few components (R16 and R17 are at present needed to provide input bias but may not be needed with later versions of the SL6310) and no adjustments. If more than 800mW of audio is desired the SL6310 should be omitted from the board and an external high power amplifier used.

The Transmitter

This section is more accurately described as the sideband exciter. It uses two integrated circuits and a transistor. The first integrated circuit is an audio amplifier with a.g.c. which is used to ensure that the output of the transmitter is substantially unchanged by varying audio input levels. Such a circuit is known as a VOGAD.

Two different VOGADS may be used in this equipment—the SL1626 or the SL6270. The SL1626 has been available for several years while the SL6270 is more recent. They are identical in pin connections and functions but the SL6270 has better performance when used with an unbalanced input. A balanced input is when the two terminals of the microphone are connected to the two input terminals of the VOGAD, an unbalanced input is when one of the microphone terminals is grounded and the other is connected to one terminal of the VOGAD, the other being unused. If a balanced microphone input is used then either circuit will give equally good performance. R29 (220Ω) need only be used with the SL1626 and R31 (47Ω) need only be used with the SL6270, but both resistors may be used with either circuit without any problems occurring.

These circuits require the use of a low impedance microphone (500Ω or less) with an output in the range 1mV to 30mV. The a.g.c. range is about 60dB and this may be too large for some applications where high levels of background noise are present, but may be reduced by shunting C47 with a 1kΩ resistor (R32). If this resistor is used C47 should be increased from 4.7nF to 47nF to preserve the h.f. roll-off characteristic of the VOGAD.

The two capacitors C52 and C53 isolate the VOGAD inputs at d.c. and the capacitors C50 and C51 decouple any r.f. which may be induced on the microphone leads. The audio from the VOGAD is coupled to the double-balanced modulator by C46.

As in the receiver the double-balanced modulator may be either an SL1641 and again a 330Ω resistor is required only if the SL1641 is used (R28).

The principle of a single-sideband generation used in this transmitter is simple. Audio and carrier are applied to a double-balanced modulator, the output of this modulator consists of a d.s.b.s.c. (double-sideband suppressed carrier) signal which is filtered in a narrow filter to remove one sideband. Which sideband is selected depends on the carrier frequency chosen.

The d.s.b. signal from the double-balanced modulator is amplified and buffered by Tr4 and applied to the crystal filter. Tr4 is a high frequency *pnp* transistor, the original design used a 2N5771 but any high frequency silicon *pnp* transistor with a low C_{ob} would be suitable. A transistor is used in this buffer rather than an integrated circuit because it does not present any load to the filter when it is turned off during reception. The gain of the transistor amplifier is set by R26 and may be altered if necessary. Bias for the transistor is obtained by direct coupling from the double-balanced modulator.

The Sideband Oscillators

One might expect the title of this section to be "The Sideband Oscillator" but there are in fact two separate oscillators. The original design used a single oscillator and diode switching of two crystals but varying capacity between diodes from different manufacturers led to a number of problems. When this design was started we investigated various ways of switching one oscillator between two crystals and decided in the end that the most reliable solution was the use of two separate oscillators. Interestingly enough, this solution was also as cheap as any other.

Each oscillator uses a Siliconix J304 f.e.t. in a Colpitts circuit. The quartz crystals supplied with the XF9-B or QC1246AX filters are 30pF parallel resonant types and the oscillators are designed to work with these. If 20pF parallel resonant types are used it is probably sufficient to reduce C32, C33, C34 and C35 to 33pF each, but if series resonant crystals are to be used more changes will be necessary. The trimmer capacitors C31 and C38 are used for fine adjustments of the u.s.b. (8.9985MHz) and l.s.b. (9.0015MHz) crystals respectively.

The output voltage from both oscillators is developed across R24. In the prototypes R24 and 68Ω and the output voltage is about 80mV r.m.s. If this voltage falls outside the range 60–200mV r.m.s. then R24 should be adjusted until the voltage is within this range but this is not very likely to happen since the prototype boards all had outputs lying between 70mV and 100mV and they used f.e.t.s from a number of batches and crystals of widely varying activity.

The oscillator to be used is selected by applying a 12V supply to its power input pin. The other oscillator's power supply should be off and, preferably, grounded.

Construction

The p.c.b. layout for this transceiver is shown in Fig. 4 and the component placing in Fig. 5.

Resistors are carbon or metal film $\frac{1}{4}$ W types, capacitors below 1nF are miniature Mullard or RS ceramic types, between 1nF and 100nF miniature monolithic ceramic types with 0.1 inch lead spacing. All capacitors above 100nF with the exception of C6 which is an aluminium electrolytic are miniature resin dipped tantalum electrolytics. The transformer T1 and T2 are wound on blocks of B1 ferrite 11.3 × 11.3 × 5.8mm ($\frac{1}{2}$ in × $\frac{1}{2}$ in × $\frac{1}{4}$ in) with two holes. (Mullard Part No. FX2249 "Double Aperture Core.") These blocks are glued to the circuit board with epoxy resin and then wound with 32–36 s.w.g. self-fluxing

Table 2. G4CLF Board Connections

Pin	Function	RFC details
1	+12V Rx/Earth Tx	2½T on FX1115
2	Audio output to 8Ω speaker	=
3	Earth	=
4	Volume control potentiometer (Top)	3½T on FX1115
5	Volume control potentiometer (Wiper)	3½T on FX1115
6	'S' Meter output	=
7	Earth	=
8	+12V (l.s.b.)	2½T on FX1115
9	+12V (u.s.b.)	2½T on FX1115
10	Earth	=
11	Microphone input (500Ω)	=
12	Earth	=
13	Microphone input (500Ω)	=
14	+12V Tx/Earth Rx	3½T on FX1115
15	Earth	=
16	Mixer port (r.f.) d.c. to 500MHz	=
17	Earth	=
18	Earth	=
19	Mixer port (l.o.) 5 to 500MHz	=
20	Earth	=

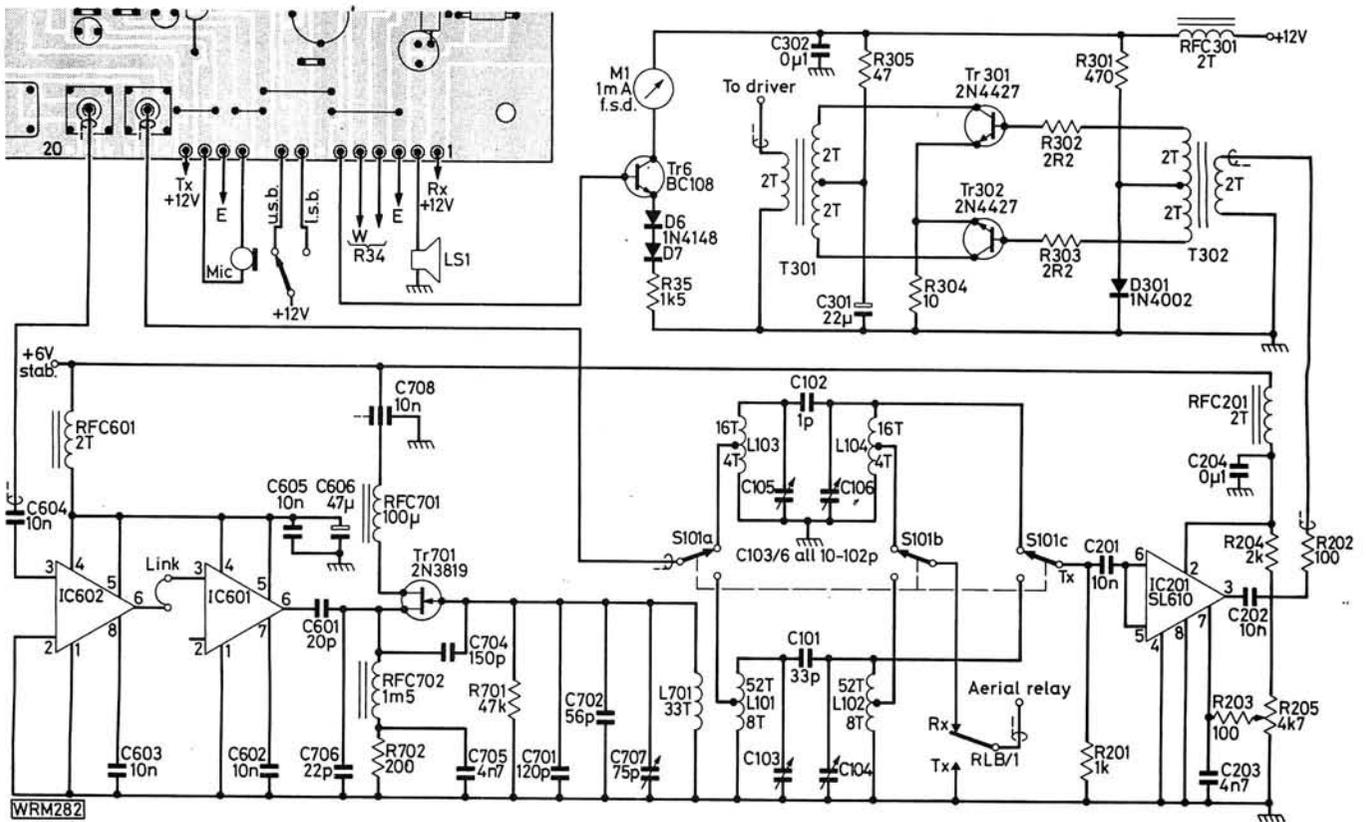


Fig. 5: The circuit diagram of the external circuitry needed to operate the G4CLF Board. This is the complete PW Helford with the exception of the power supply and relay switching circuits

copper wire. T1 has a two-turn primary (on the D1 side) and a six-turn secondary, T2 has six turns on both windings.

There are four wire links on the board to connect various earth tracks together for minimum h.f. impedance. There is also a hole near to the quartz crystals through which passes a piece of wire which is soldered, as quickly as possible, to avoid damage to the crystal cans to ground them. If this is not done the crystals tend to radiate.

All components must be mounted with the shortest possible leads and i.c. sockets must not be used.

Assembly of the board should be in the following order:

1. Glue down the ferrite cores. When the glue has set wind the transformers T1 and T2.
2. Insert Tr1 and diodes D2, D3, D4 and D5. Mount D1 and F1. Insert the resistors and capacitors of the bi-directional amplifier.
3. Insert IC2, IC3, IC4 and IC6, checking that they are inserted the correct way round. Insert resistors R5 to R15, insert capacitors C7 to C18 and C20, then Tr4 and Tr5.
4. Insert IC5, and C22 to C26 and C6.
5. Insert crystals X1 and X2 and trimmer capacitors C31 and C38. Solder and cut leads and solder wire to ground cans. Insert resistors R21 to R25, capacitors C32 to C37, and Tr2 and Tr3.
6. Insert IC7, resistors R16 to R19, capacitors C27 to C30 and the four wire links.
7. Insert IC8 and IC9, resistors R26 to R31, and capacitors C39 to C53 (the ceramic capacitors should all be mounted first, then the tantalum electrolytics).
8. Finally insert IC1 and IC10, the remaining components, and the pins, sockets or wires, which are to be used to make the connections to the board.

The connections to the board are given in Table 2. The r.f. and l.o. signals may either be connected via the same 0.1 inch pitch connections, as the rest of the signals and

supplies, or via miniature co-axial sockets. The latter are used in the Helford.

The board is powered from a single +12V supply but will work between +10V and +15V without damage or significant change in performance. It is essential to ground the transmitter supply during reception and the receiver supply during transmission. This is not merely to prevent spurious transmission of signals as was the case in the original design, but is because these other lines are actually used as d.c. return paths.

When the board is complete the sideband oscillators should be set up by connecting a frequency meter across R24 and connecting power to each oscillator and adjusting its trimmer until its frequency is within 10Hz of nominal.

If for any reason the board does not perform properly when first connected it should be checked for short-circuits and then the integrated circuits should be checked with a high impedance voltmeter for correct operating voltages. (The correct operating voltages are given in the "Plessey Semiconductor's Radio Communications Handbook", available from any Plessey Semiconductor Office or distributor.) If this method also fails then signals must be traced through the board with the aid of a signal generator and an oscilloscope or spectrum analyser.

Readers who intend to operate the Helford should be in possession of the appropriate licence issued by the Home Office to those who have passed the City and Guilds Radio Amateurs' Examination. Details may be obtained from: The Home Office, Radio Regulatory Department, Amateur Licensing Section, Waterloo Bridge House, Waterloo Road, London SE1 8UA.

Next month in *PW*


FREE WORKSHOP TWEEZERS

You wouldn't believe us if we told you how much a pair of tweezers cost these days, so we won't. Just remember, every home should have a pair of our orange ones—free of course.

THE FIRST 'YL'

One of the most active of the early amateur YL operators was Barbara Dunn 6YL (later G6YL), who was involved in monitoring the famous Southern Cross on its transatlantic flight 50 years ago. Ron Ham recounts 6YL's achievements.

PW 'TwyNHAM'

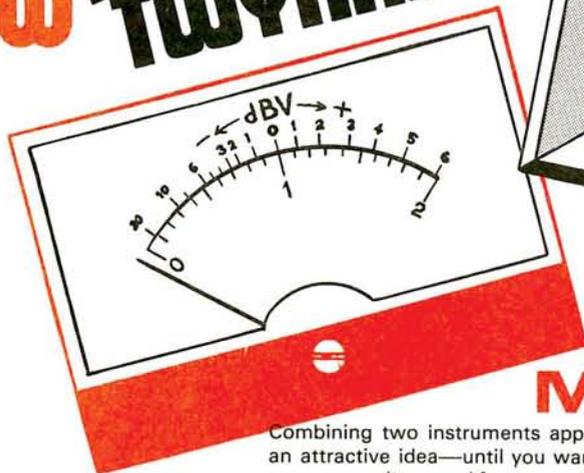

DIGITAL/ANALOGUE MULTIMETER

Combining two instruments appears to be an attractive idea—until you want to measure, say, voltage and frequency together!

The *PW* "TwyNHAM" is a mains powered multimeter which gives you simultaneous

analogue and digital readouts for both accuracy and trend watching.

Twelve ranges plus a constant current test facility for semiconductor junctions are all part of the specification.

plus

index to vol. 56

ON SALE 7 NOV

THE **PW**

'SHERBORNE'

**SYNTHESISED
AM/FM TUNER**

PART 2

W.S.POEL

The synthesiser has so far been described in isolation from the radio hardware of the complete tuner. This is partly because the synthesiser itself is suitable for use with a variety of different tuner configurations—and partly because the entire circuit would appear impossibly complicated. This would be unfortunate, as it falls neatly into a series of building blocks that may be considered “jointly and separately” in the context of this article, or as “separates” for substitution or addition into existing designs.

The synthesiser unit is replacing the following traditional features:

1. Tuning potentiometer
2. Preset station selection
3. Frequency indication/readout
and takes care of these less obvious aspects:
4. All tuning voltage stabilisation cared for
5. Requirement for a.f.c. non-existent
6. Greatly simplified switching
7. A plethora of otherwise unattainable features.


Those features fulfilled by the synthesiser are also vastly improved by the fact that everything is referred to a quartz crystal for frequency determination. The penalty is the close proximity of digital processing to a sensitive radio environment, so some care is needed to avoid radiation of the harmonics into the broadcast bands.

The tuner design must take into account the signals required by the MPU when operating in the scanning mode, and thus must provide:

- (a) Local oscillator output for both a.m. and f.m.
- (b) Scan stop information
- (c) Simple bandswitching
- (d) Stereo decoder with v.c.o. defeat
- (e) High impedance tuning voltage lines.

The interconnections required between the synthesiser and tuner modules are shown in detail in Fig. 10, which will also serve later as the inter-unit wiring diagram for the complete tuner.

A medium-priced tuner is described here. Considerable efforts have been made to develop a design that can be repeatedly assembled and made to work by a wide range of enthusiasts with different levels of experience. The result is an a.m./f.m. tuner that will out-perform any previously published design, so it can scarcely be described as a compromise. Much of the credit must go to the advances made in the past year or so in the state of component technology—such as new linear-phase ceramic i.f. filters,

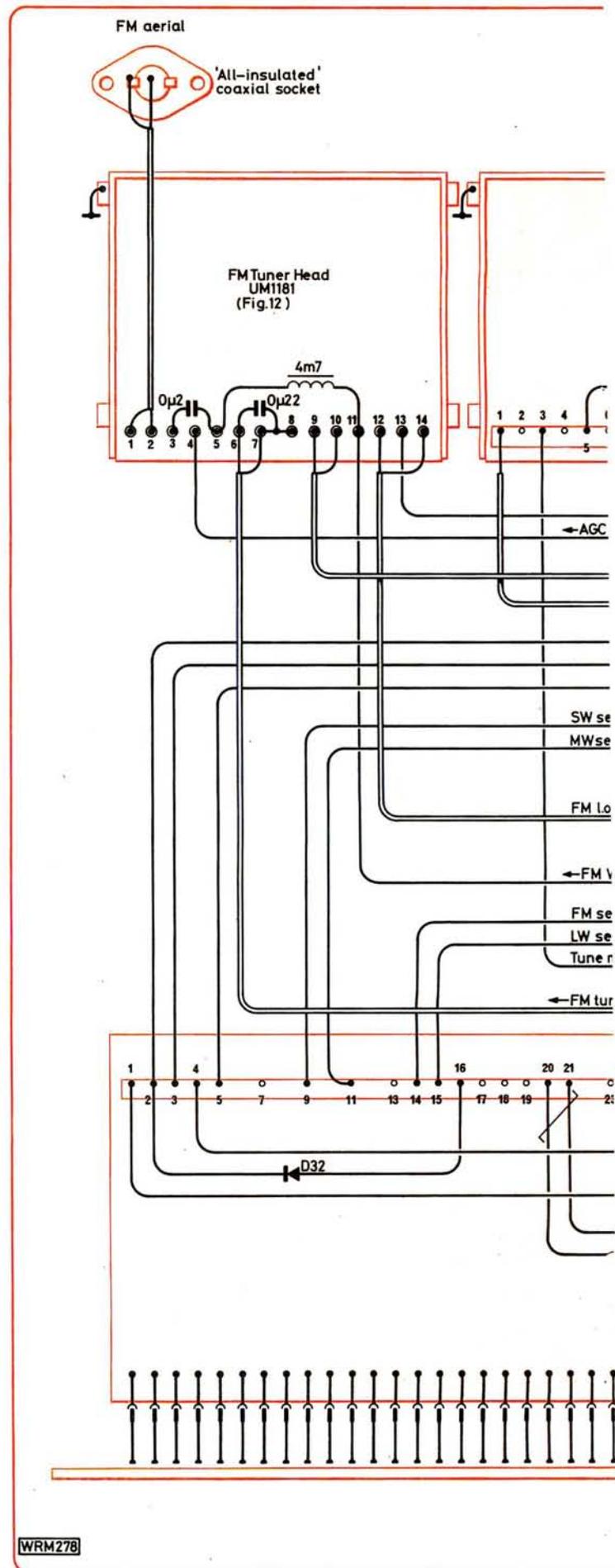

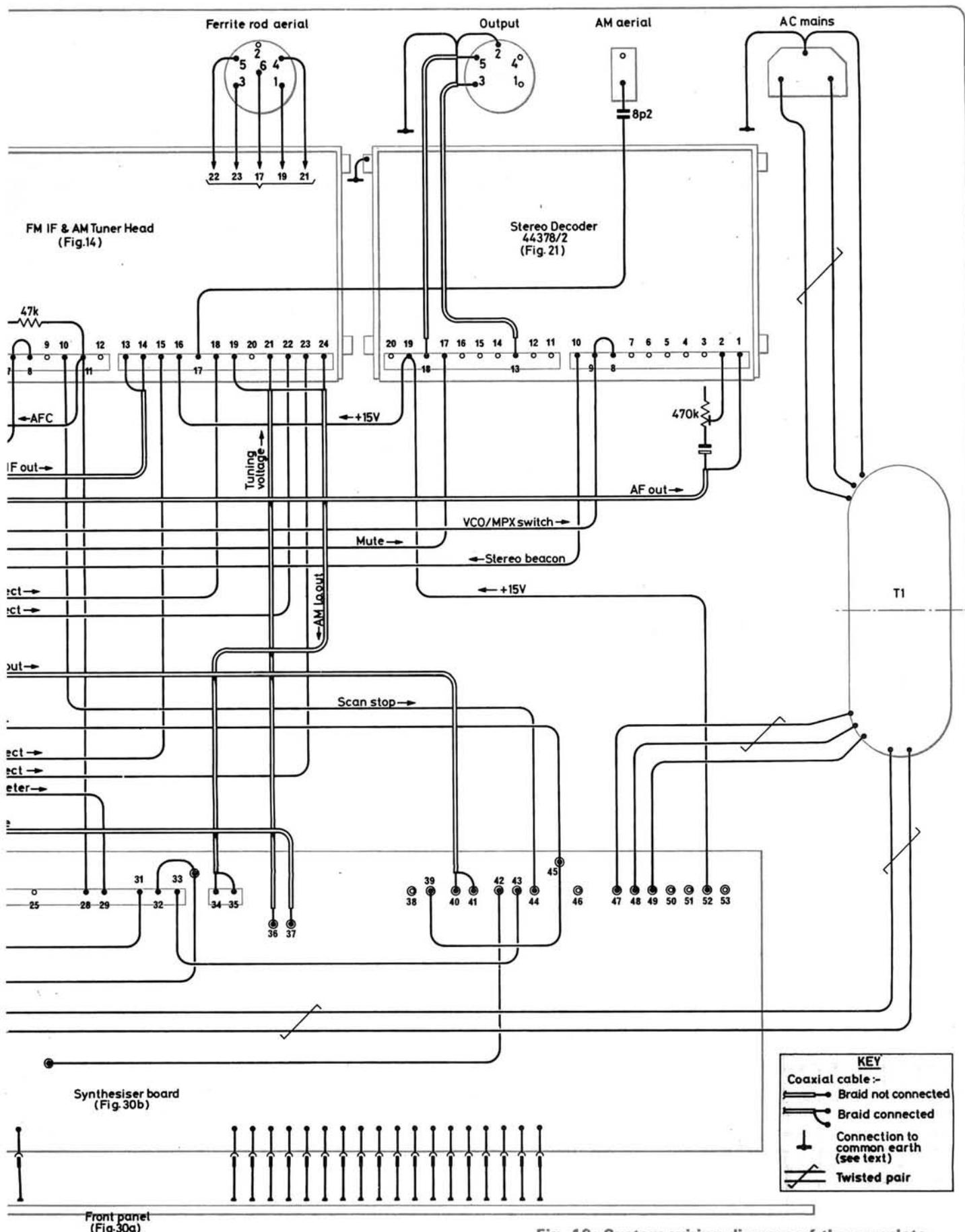


Fig. 10: System wiring diagram of the complete tuner, identifying signal flows and control requirements

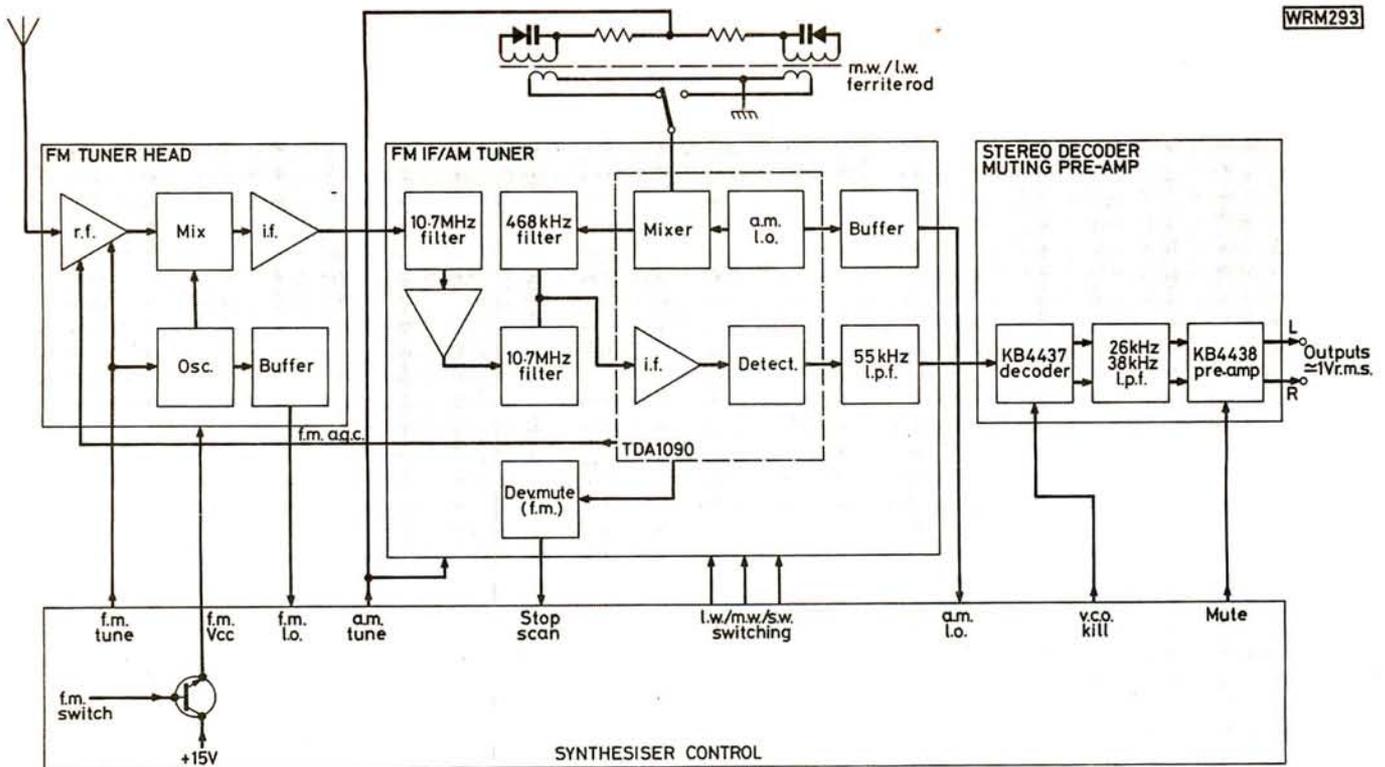


Fig. 11: Simplified block diagram of the complete tuner system

very low-noise members of the universally appreciated CA3089/3189 families of f.m. i.f. amplifier and detector i.c.s, MOSFETS, etc.

A higher specification tuner system was considered unsuitable, since accurate alignment of a more complicated i.f. would not be feasible for anyone without access to thousands of pounds worth of advanced test equipment. Nevertheless, the tuner synthesiser described last month is quite capable of driving alternative r.f./i.f. designs if required.

The Tuner

The tuner divides down into three blocks as shown in the simplified system diagram of Fig. 11: a front end (the UM1181 and the Alps FD811UX are described); a combined f.m. i.f. amplifier and detector, with three-band a.m. tuner section built around the Sprague ULN2242A; and a stereo decoder common to both designs that uses the Toko KB4437 pilot-cancel stereo decoder, followed by the KB4438 matching muting audio pre-amplifier.

The front ends are available only as prebuilt and tested items, but the circuit diagrams are nonetheless relevant to a comprehensive description of the circuit function. The UM1181 and FD811UX adopt similar circuitry although the Alps unit is perhaps constructed more thoughtfully.

In the UM1181 (Fig. 12) the antenna circuit is a single-stage-tuned coil, feeding gate 1 of v.h.f. MOSFET r.f. amplifier. Automatic gain control (a.g.c.) is provided on gate 2 of this MOSFET (via R2) although if left open circuit, R3 will pull the gate bias up to ensure maximum gain. The filter between the r.f. and mixer stages is an interesting feature, being basically a triple-tuned stage and bottom inductance coupled. The advantage of this method of coupling is that the coupling points are at a far lower impedance than with top-capacity coupling, enabling some of the fastidious screening to be omitted inside the can. However, although the small-signal selectivity is impressive at 90dB or better, really strong signals at the antenna can leak across—but these are levels rarely ex-

perienced under UK conditions, unless a beam antenna is employed in an already strong signal environment.

The mixer is a common source JFET, with source injection of the local oscillator, and a JFET i.f. pre-amp in common-gate mode (high stability/medium gain/broadband) between the drain load i.f. coil and the output matching coil. The local oscillator (10.7MHz high) is the classical Colpitts design, with feed taken from the relatively low-impedance emitter to both the mixer and the oscillator buffer amplifier. Approximately 300mV of l.o. is thus available for the input of the prescaler on the synthesiser control board.

In the FD811 (Fig. 13) a similar input arrangement exists, although the physically larger construction of the coils used in the FD811 series enables a higher Q to be achieved at each stage, thus enhancing selectivity. The a.g.c. system in this tuner is not returned to the positive supply rail, and unless an external bias is applied to the a.g.c. terminal, the r.f. stage will be operating under conditions of minimum gain.

A quadruple-tuned filter is used between the r.f. and mixer stages, the input and output couplings being via inductive proximity, and the centre two via capacitor top coupling. Capacitor coupling is avoided at the input and output sections because of the capacitive loading effects of the drain on the r.f. stage and the gate of the mixer—these “unknowns” will affect the calculation of the ideal coupling capacitor for the correct coupling constants. The capacitive coupling section with the coils well screened from one another enables the filter to provide excellent strong-signal selectivity. In designs with a second r.f. stage (Ambit EF5800), the excess gain can be used to iron out the lumps in entirely top-coupled filter sections, since slightly staggered tuning will be far less serious to the overall tracking of the system.

The output of the mixer goes through a double-tuned i.f. filter stage before reaching a f.e.t. buffer amplifier; the load presented is resistive (R22), which is more suitable for the following f.m. i.f. filter stage in many instances.

The local oscillator (10.7MHz high), is again the


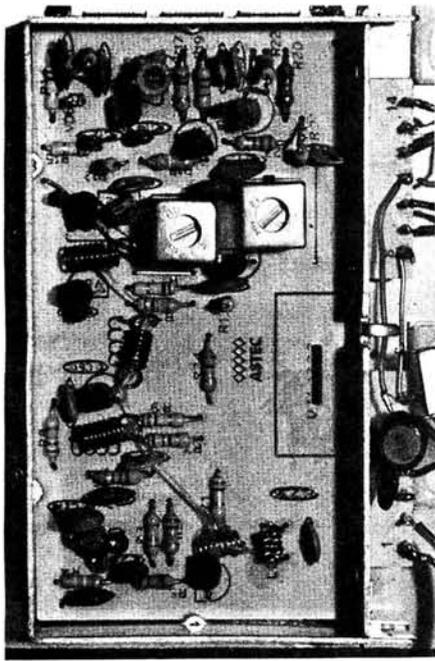


Fig. 12: Circuit diagram of the Astec UM1181 v.h.f. tuner head, with (left) a view of the module

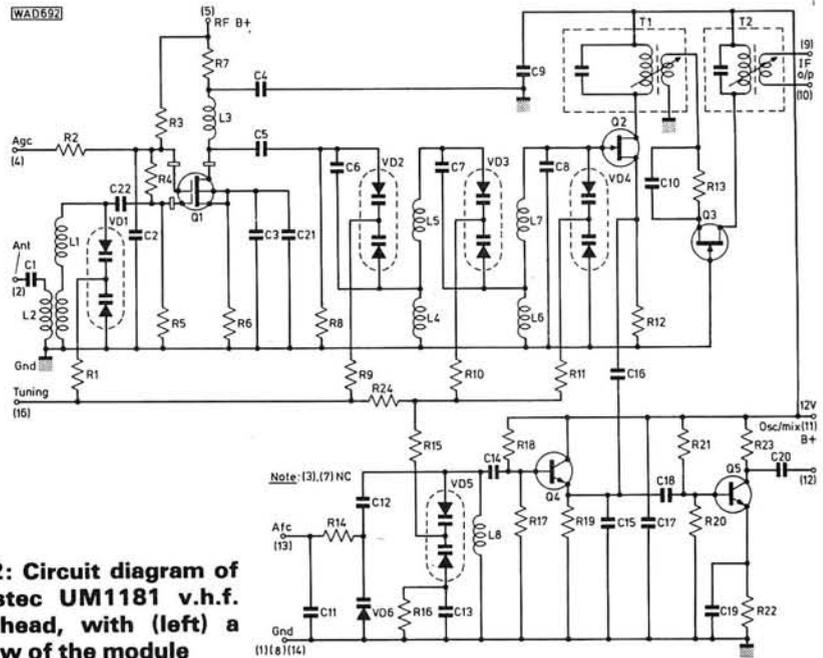

Colpitts circuit, used at a lower level. This reduces oscillator drift due to the heating of tuned circuit components, and prevents the local oscillator causing non-linearities in the tuning diode characteristics. As it happens, the synthesiser can take care of drift anyway (since the only drift possible occurs in the reference oscillator, which is crystal controlled), but it also provides a very low-noise signal, subsequently raised in level by a common-base transistor amplifier (Tr6), and fed to the gate of the mixer MOSFET via an emitter-follower buffer. Thus a very high degree of isolation is maintained between the l.o. and mixer signals. A second emitter-follower buffer is used to provide l.o. signal for the synthesiser system.

The FM IF/AM 3-band Tuner Module

As can be seen from Fig. 14, the TDA1090 is used for both these major functions. The i.c. was described in some detail in conjunction with the PW "Dorchester" multi-

band broadcast tuner, so only a brief resumé is offered here.

The device (Fig. 15) uses the same basic i.f. amplifier for both f.m. and a.m., although the detector for f.m. is a quadrature coil system (as in the CA3089 families) fed from a phase correction choke. Under f.m. conditions, the i.f. amplifier is driven into limiting by grounding the a.g.c. terminal, providing a squarewave i.f. output rich in harmonics. The quadrature coil helps to restrain this somewhat, but the whole assembly is placed inside a screening can to prevent unwanted radiation.

Listeners in the London area may have noticed that many tuners give an unaccountably high level of hiss or birdy response when tuned to 95.8MHz (Capital Radio). The answer is simple, since $95.8 = 9 \times 10.64$, some 60 kHz away from the i.f. centre of 10.7MHz, and well within the filter pass-band. The noise is very mushy and warbly, since in the process of being multiplied nine times, the deviation is also increased nine times—so at no time

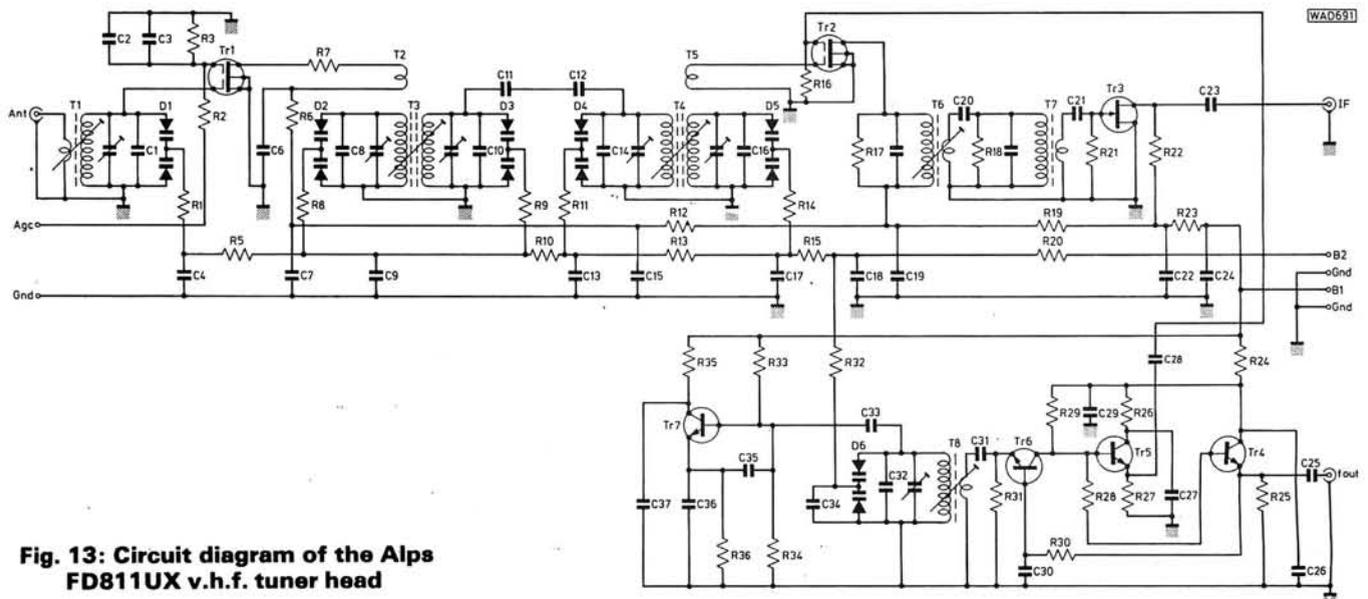


Fig. 13: Circuit diagram of the Alps FD811UX v.h.f. tuner head

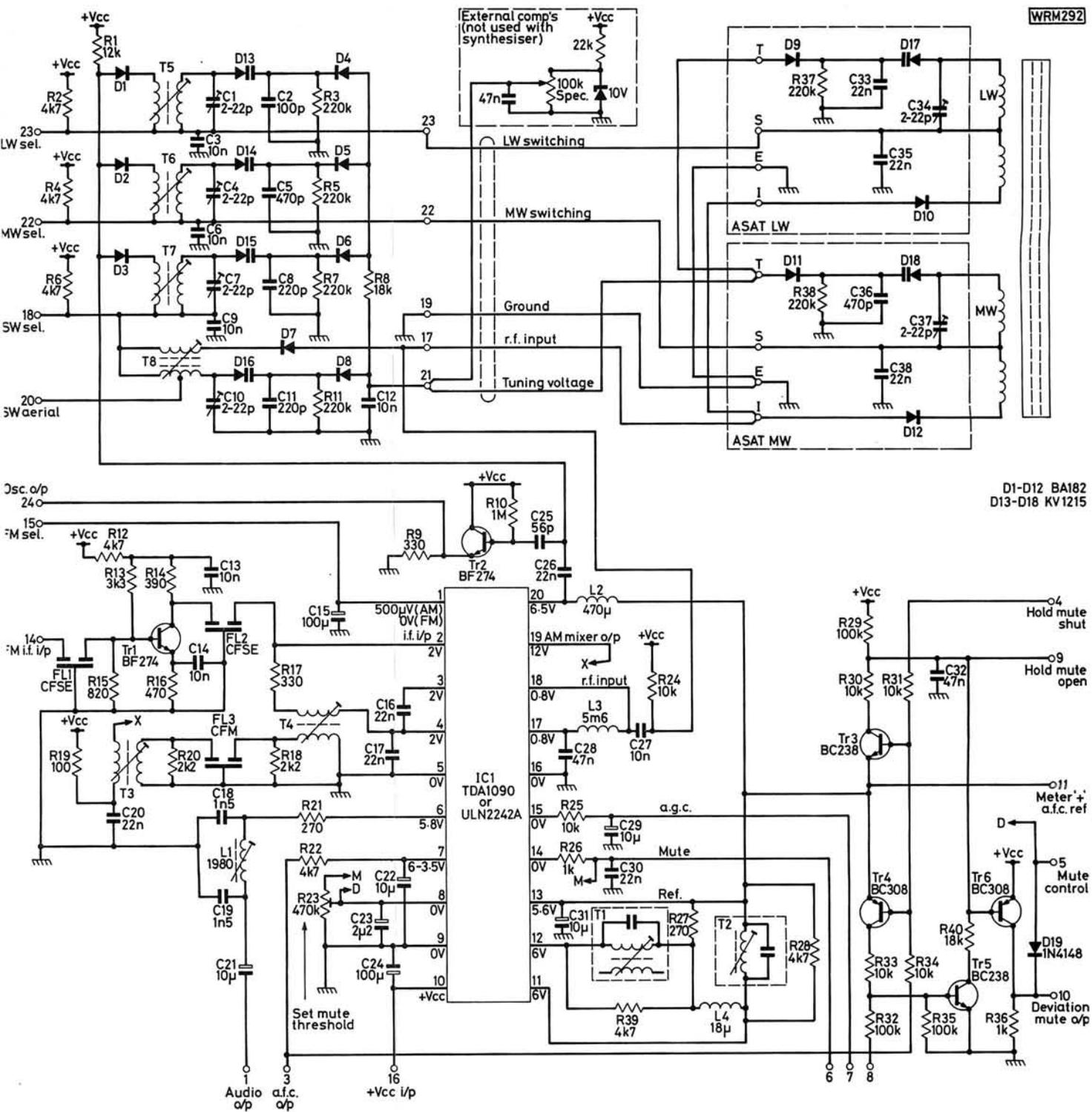


Fig. 14: Circuit diagram of the f.m. i.f./a.m. tuner module, with associated remote tuned and switched ferrite rod aerial

will such a harmonic provide an intelligible signal to the detector.

Careful decoupling and earthing of the f.m. i.f. and detector system is required, for the same reasons as discussed in connection with the prescaler on the input to the synthesiser's phase-locked loop in last month's article.

The f.m. section of the TDA1090 possesses a signal level mute (as does the CA3089E)—but no deviation muting. This shortcoming is easily rectified with a few external transistors, using the a.f.c. voltage to operate a

“window” through which the f.m. mute will be allowed to open. The same signal is used in this design to provide the scan-stop information for the tuner, since it can be set to give a signal when the synthesiser has stopped precisely on a wanted f.m. signal. The behaviour of this signal with regard to detuning effect is shown in Fig. 16. The actual bandwidth is determined by the voltage developed across the a.f.c. output and the reference voltage. The a.f.c. output is basically a current source, and so the larger the value of the resistor used, the larger will be the a.f.c. voltage developed for a given degree of detuning. Ohm's Law states that $V = IR$ (within the limits of the supply available on the i.c.).

WATERS & STANTON ELECTRONICS

CHECK-OUT THE ALL-NEW



FDK MULTI-750E 2 METRE 'ALL-MODE' RIG


The Multi 750 is FDK's new, all mode 2 metre unit for both base or mobile use. Using the same cabinet dimensions as the M700EX, this really does provide the basis for an action-packed, go anywhere station. To list all its features would be impossible in the space available on this page. However, we will list its main points so you can get some idea of just what this amazing package is capable of.

144-146MHz at 10 WATTS OUTPUT (Minimum!); ALL MODES - FM/USB/LSB/CW: REPEATER OPERATION - normal or reverse with automatic crystal controlled tone-burst; DUAL VPO's - these are selectable at the press of a button so that one vfo can be left at the SSB end of the band and the other at the FM end; NOISE BLANKER - a really efficient circuit to take out those ignition pulses on ssb; DUAL SPEED TUNING - enables 1kHz or 100Hz step tuning on SSB/CW and 1kHz steps on FM; RIT - essential for accurate tuning of the received SSB signal; LOW EFFECTIVE PRICE - and the option of 70cms operation. At the end of the summer the UHF EXPANDER will be available to provide instant QSY to 70cms or even cross-band operation. This unit will be in a matching cabinet which together with the AC mains module will build into a complete 2m/70cms base or mobile station.

- Simple and smooth VFO control gives either 100Hz or 5kHz steps on both FM and SSB modes for optimum convenience.
- The large green fluorescent display tube gives full frequency readout to 100Hz and provides safe and clear readout for both night and day operation.
- Standard features include noise-blanker, RIT control with switch, RF attenuator gain control, automatic crystal controlled tone-burst, high and low power switching and remote up/down frequency control microphone unit.
- Compare its compact size and light weight, its smart appearance and comprehensive front panel controls. Simple and reliable operation is made possible by employing advanced solid-state and logic techniques.
- A dual VFO is employed for the selection of two independent frequencies anywhere in the band. This also enables split frequency operation, particularly useful when used in conjunction with the optional "UHF-EXPANDER" transverter.

For normal repeater operation a pre-programmed shift is selected by front panel selector.

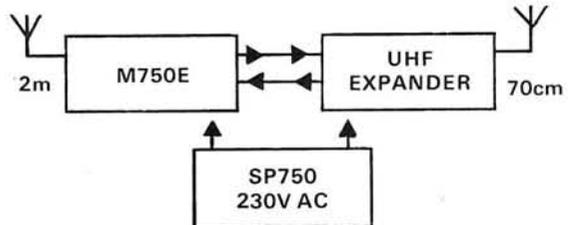M750 BUILDS INTO A 2m & 70cm PACKAGE
(70cm module available late summer)



SURELY TODAY'S BEST VALUE

**Pound
for
Pound**

£299

**Incl. VAT
& Delivery**

**Feature
for
Feature**

SEE REVIEW THIS ISSUE OF P.W.

Waters & Stanton Electronics, Warren House, 18-20 Main Road, Hockley, Essex.

Tel: 0702 206835 & 204965

To: WATERS & STANTON ELECTRONICS

*Please supply Multi 750E by return. Cheque/P.O. enclosed: £299

*Please send full colour literature on the Multi 750E

*Please send H.P. forms for completion. Deposit of £60 enclosed.

NAME

ADDRESS

*DELETE WHICHEVER NOT APPLICABLE

ORDER WITH CONFIDENCE . . . OUR REPUTATION IS YOUR GUARANTEE

Callers welcome:- We are open 9am-5.30pm Monday-Saturday, Ex. Wednesday 9am-1.00pm.


Telephone orders:- Simply 'phone in your Barclaycard or Access number and we will despatch goods within 24 hours.

Mail Orders:- Send cheque or postal order for correct amount printing name and address clearly.



WARREN HOUSE, 18-20 MAIN ROAD, HOCKLEY, ESSEX. TEL: 0702 206835 & 204965


MICROWAVE MODULES

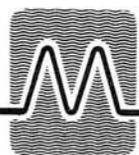

EX-STOCK FROM

2M & 70CM LINEARS

MML 144/25	£48.30
MML 144/100	£142.60
MML 144/40	£69.00
MML 432/20	£69.00
MML 432/50	£113.85
MML 432/100	£228.65

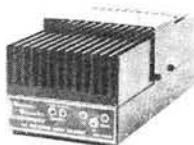

2M PRE-AMPLIFIER

MMA 144V
ULTRA LOW NOISE
RF SWITCHED GAIN 15dB
NOISE FIGURE 1.3dB



ONLY £29.90

Bredhurst electronics

HIGH ST., HANDCROSS, W. SUSSEX 0444 400786

TRANSVERTERS

MMT 28/144	£90.85
MMT 144/28	£99.00
MMT 432/144R	£173.00
MMT 70/144	£155.00



CONVERTERS

MMC 50/28	£24.90
MMC 70/28	£24.90
MMC 144/28	£24.90
MMC 432/285	£29.90
MMC 432/1445	£29.90



MMD 50/500 FREQUENCY METERS £69.00

For further information on any of the above items, or any other MICROWAVE MODULES products please contact:

BREDHURST ELECTRONICS,

The High Street, Handcross, Sussex. Tel. 0444 400786

MAIL

ORDER

ALL PRICES INCLUDE VAT, CARRIAGE AND A FULL 12 MONTH GUARANTEE

RETAIL

CALLERS

TO ORDER ANY OF THE ABOVE ITEMS SIMPLY WRITE, ENCLOSING A CHEQUE OR PHONE YOUR CREDIT CARD NUMBER



... the sign of fine communications

SRX30 SWL RECEIVER £158

TRIO EQUIPMENT

		Price inc. VAT £
R1000 SWL	PLL Receiver 200KHz to 30MHz	297.85
R820	The ultimate SWL receiver	690.00
YG455C	CW filter 500Hz	58.85
YG455CN	CW filter 250Hz	60.95
SP820	Speaker	37.95
HS5	Communications headphones, tailored response	21.85
HS4	Communications headphones, tailored response	10.35
VHF AMATEUR RECEIVERS		
SR9	Tunable/crystal 2m FM receiver 144-146MHz	46.00
AMR217B	Scanner with 8 crystals. Mains/battery	120.75
ROTATORS, TUNERS & SWITCHES		
AR40	(5 core cable required)	54.83
SU2000	For lightweight 2m beams	£48.00
KX2	AK Antenna Tuner 0.5-30MHz	29.90
CX3	SWL 3-way Antenna Switch	7.20
DAIWA	CS201. 2-way Antenna Switch	11.98
LAR	1kW Feeder Switch	£16.95
AIR BAND RECEIVERS		
SHARP	Air Bands Portable Receiver	18.75
FX-213-AU		
LOWE AP12	Crystal Controlled air band portable receiver c/w ni-cad batteries, charger and fitted 12 crystals	118.45
	COPAL-24 Hour Digital Clock Mains Operated	12.95

All prices include new VAT rate

(Securicor carriage available if required)

Buy by post or phone your Barclay Card or Access number.

Alternatively, call in for a chat. The shop is just 10 minutes from Leeds City Station, and there's easy parking if you travel by car. Instant H.P. for licenced Amateurs. Extended Credit Terms Available. Send 50p for Catalogue and Price List.

LOWE TRIO DISTRIBUTOR




LAR are area distributors for Jay Beams, Antenna Specialists, Hillomast ICOM and Microwave Modules Products.

LEEDS AMATEUR RADIO
27 Cookridge Street,
Leeds, W. Yorks. Tel. 452687

NORTHERN COMMUNICATIONS

AMATEUR * COMMERCIAL * MARINE

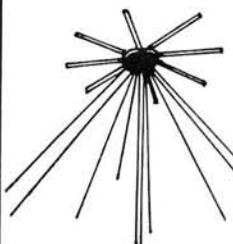

NORCONE 512 (66-512 MHz)

It's here! A no compromise, precision made, full 16 element discone antenna, made in Britain, Standard S0239 connector, with cover. Supplied with 1" diameter, 30" mounting support mast and complete instructions.

An ideal partner for the "Bearcat" and other scanning receivers. It may also be used for transmission and in particular where antenna space is limited. Full coverage of 70.144, 432MHz Amateur bands plus Aircraft, Marine and Commercial bands.

£24.95 p.p. £1.50

NCMC-1. In line vertical mounting kit for 1" to 2" mast.

£2.45 p.p. £0.50

ZL-12 SPECIAL

13db gain, compact 2 metre Yagi. 10'6" boom, lightweight rugged design. Hundreds of this award winning antenna already in use. Send for details.

£28.75 p.p. £1.50

ZL-8 SPECIAL

9db gain, super compact 2 metre Yagi. 6'0" boom, lightweight rugged design. Ideal for limited spaces and portable operation.

£17.25 p.p. £1.50

YAESU FT480R. FDK 750E MULTIMODES

Both of these new 2 metre multimodes transceivers are amongst our full range of Amateur Radio equipment and accessories. Ring or call for complete information:

Tues-Sat. 9.45am-5.30pm.

Telephone (0422) 40792.

303, Claremount Road, Halifax HX3 6AW,

West Yorkshire. G3UGF.



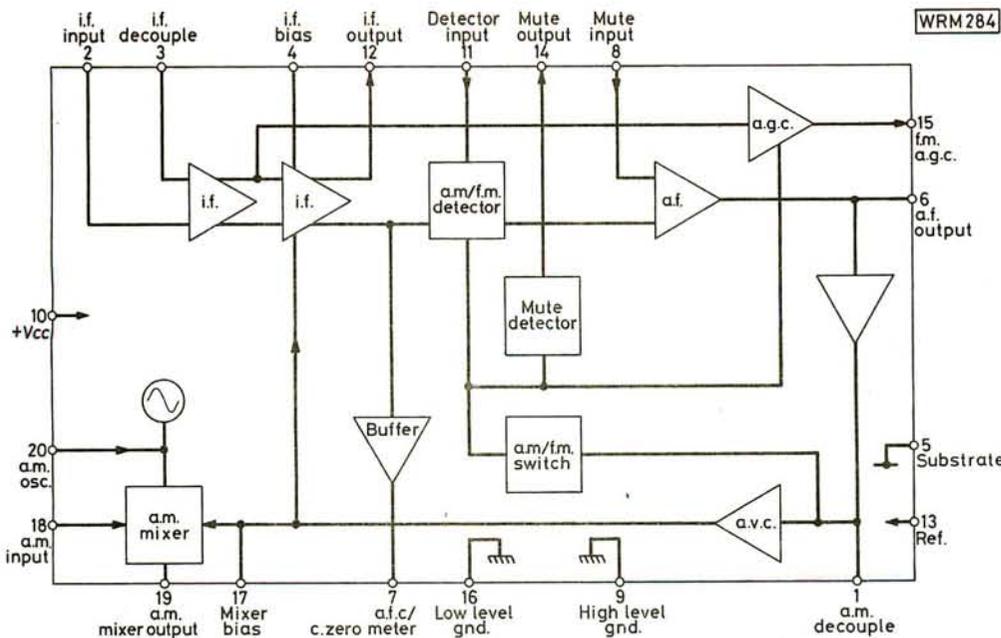


Fig. 15: Block diagram of the ULN2242A/TDA1090 integrated circuit

Fig. 16: Operation of the deviation mute circuit

Fig. 17 (bottom): Amplitude and group delay characteristics of an i.f. filter. The solid line is the group delay



An output is also available from the TDA1090 in a form suitable to drive the front end. If required, this a.g.c. signal can be used to drive the muting signal system (both signals go low with increasing input), since the a.g.c. operates somewhat after the standard noise-operated muting, enabling selection of strong signals only, without any background hiss under critical stereo listening conditions.

The FM IF Amplifier

The TDA1090 provides the same facilities as the CA3089E with the exception of a signal level indicator output. However, the a.g.c. output of the TDA1090 may be regarded as a reference of signal level, albeit the onset of the indication occurs at greater input levels than with the CA3089 type of circuit. However, the gain of the front end and i.f. pre-amp is such that the a.g.c. indication starts at about 70µV input.

In f.m. mode, the a.m. local oscillator is turned off and the i.f. amplifier is turned into a limiting amplifier by ground pin 1 of the i.c. In this application, the f.m. tuner-head supply voltage is also switched—since the module would still be susceptible to the output of the f.m. tuner-head when in the a.m. mode, as the i.f. amplifier is common to both a.m. and f.m. A single transistor i.f. pre-amplifier provides some 20dB of additional gain at 10.7MHz, as well as providing matching for the ceramic filters.

Various types of ceramic filter are available these days, and the technology has come a long way since the first types were introduced. The Toko CFSE series is used here, although the Murata ultra-linear phase i.f. filters in the SFE10.7ML series could be used. However, the extreme tuning accuracy of the synthesiser makes the choice of filter easier, since it is no longer necessary to worry about a fairly broad detuning tolerance. In fact, a narrower filter can be used if desired. Under UK band-listening conditions, this is of little benefit except under sporadic-E conditions, and might possibly cause unnecessary problems during alignment.

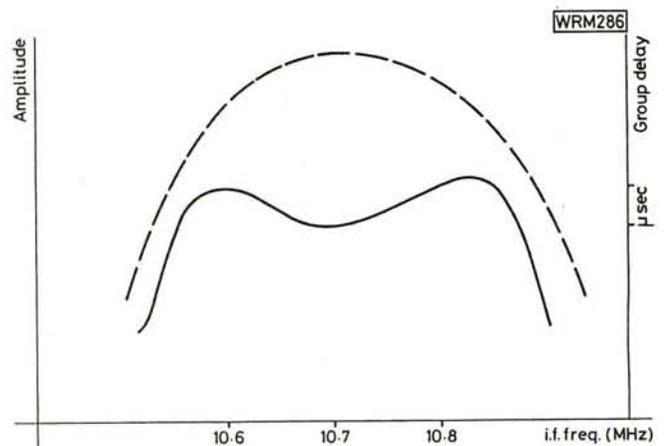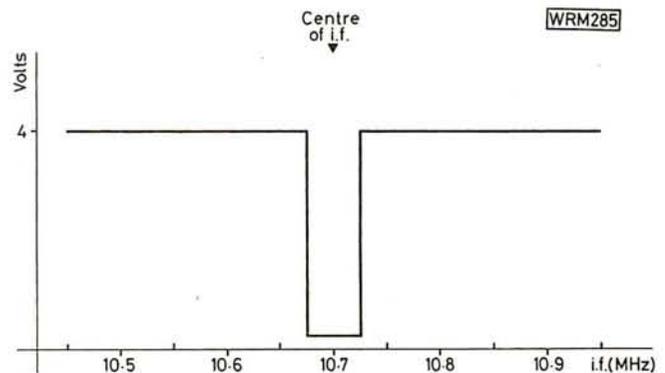

The crucial feature of any f.m. filter is the group delay (see Fig. 17)—which is related to the phase linearity by: $\text{Group Delay} = \text{Phase change/frequency change}$. The ideal phase change from one side of the filter to the other is a straight line. This is the same as the slope of the f.m. detector, which uses exactly the same principle when demodulating f.m. signals in a quadrature system, to convert frequency change into amplitude change.

Distortion at the extremes of the slope will cause ripples in the group delay, causing these parts of the modulation

spectrum to arrive at the detector at slightly different times. This phase error will cause problems in the Zenith-GE multiplex stereo system, where the phase accuracy between the 19kHz pilot tone and the 38kHz subcarrier is the cornerstone of the theory. A full analysis of the theory of f.m. and multiplex is beyond the scope of this feature—but suffice it to say the composite f.m. stereo signal, with an audio bandwidth of 53kHz, requires approximately 220kHz of r.f. i.f. linear phase bandwidth. As f.m. sidebands theoretically extend to infinity (but diminishing to an infinitesimally small amplitude quite quickly), opinions as to the ideal bandwidth for stereo f.m. vary from 180kHz (favoured by some applications notes written at Philips) to 280kHz. A compromise value of 220kHz does not adversely affect stereo programme material in any way that can be detected using current broadcast standards.

The detector in the TDA1090 uses a form of quadrature—with the signal fed to the phase-shift coil via a fixed choke of 18 μ H. This choke is used to compensate for delays in the signal path of the other input to the quadrature detector—so the midpoint of the detector slope is exactly in the middle of the d.c. characteristic (Fig. 18). This also applies to the CA3089E families. If the signal path correction is wrong, then the detector exhibits a d.c. offset, although the demodulation characteristic will not be adversely affected by even quite a large d.c. offset.

As this d.c. characteristic is used to drive the a.f.c., it may appear to be irrelevant in a synthesised tuner—but in this instance, the a.f.c. is used in the deviation muting system to provide a signal to stop the tuning synthesiser from scanning, and so must be accurate and fast in operation.

The a.m. i.f. transformer T1 is apparently in the way of the f.m. i.f. signal, but the reactance of the 180pF capacitor in the a.m. i.f.t. is a low value at 10.7MHz, and thus does not affect operation at f.m. However, this i.f. is in a sensitive path for the f.m. signal with regard to the detector time delay mentioned above. Any extra capacity

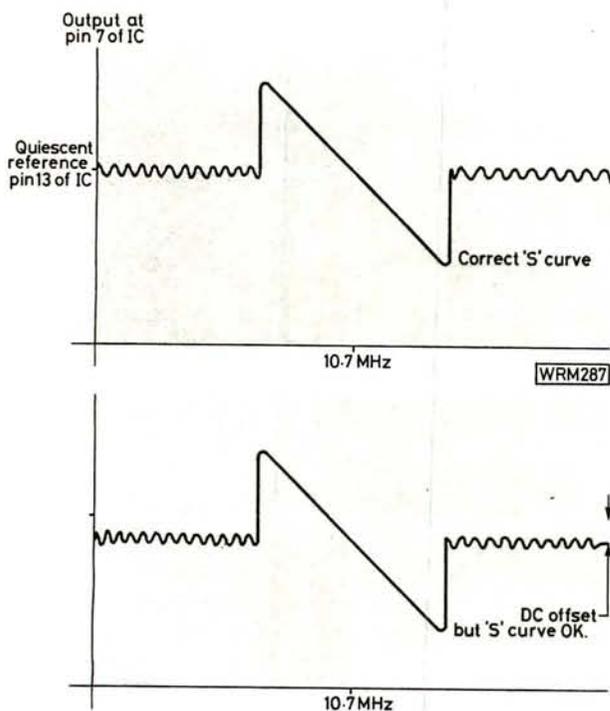


Fig. 18: The effect of a d.c. level shift at the f.m. detector

CONSTRUCTION RATING

Advanced

BUYING GUIDE

Some of the component types for this project, especially in the f.m. i.f./a.m. tuner module, are critical from the point of view of physical size. The specialised semiconductors and all the filters and inductors are available from Ambit International (see Advertisers' Index). Ambit are also able to supply the ready-built f.m. tuner modules, and kits for the remainder of the modules and units.

The non-specialised components and the printed circuit boards should also be available from regular suppliers among our advertisers.

The cost quoted below is for the parts required to build the complete tuner, in the case shown in our photographs.

APPROXIMATE COST

£150


here will cause d.c. offset to occur, and will confuse the choice of choke. No part of the secondary of the a.m. i.f.t. should be grounded, since the capacity between the i.f. primary and secondary will be enough to cause an incurable offset if the secondary is more than just a couple of turns.

Such stray capacity effects may be compensated by changing the value of the choke feeding the f.m. quadrature coil, but then the amplitude of the i.f. signal passing through would be attenuated if the choke value were increased. The signal level muting of the TDA1090 relies on the i.f. signal at pin 11 being 160mV r.m.s. under limiting conditions.

The original aim of offering the a.m. i.f. with a secondary was to provide an undetected output of the 468kHz i.f. signal for use in such things as product detectors, n.b.f.m. ratio detectors, etc. In a number of applications, the d.c. offset created by grounding one side of the secondary may not adversely affect the f.m. audio quality—but absolute accuracy of the a.f.c. output is necessary for the correct operation of the scan detector circuitry.

As the TDA1090 does not possess internal deviation (detune) muting, it is necessary to provide these facilities externally. Transistors Tr3 and Tr4 form a differential amplifier with their emitters referred to the i.c. reference voltage at pin 13. Transistor Tr5 is driven from either the signal muting (pin 14) or the a.g.c. (pin 15). Using the muting signal from the a.g.c. source enables selection of only the high-level input signals, to avoid stopping at each of those signals recognised by the standard muting system, since many will be noisy under stereo listening conditions. This option has been "hardwired" in the tuner described here, although it could be switched if required. The excep-

**DMM
BREAKTHROUGH**

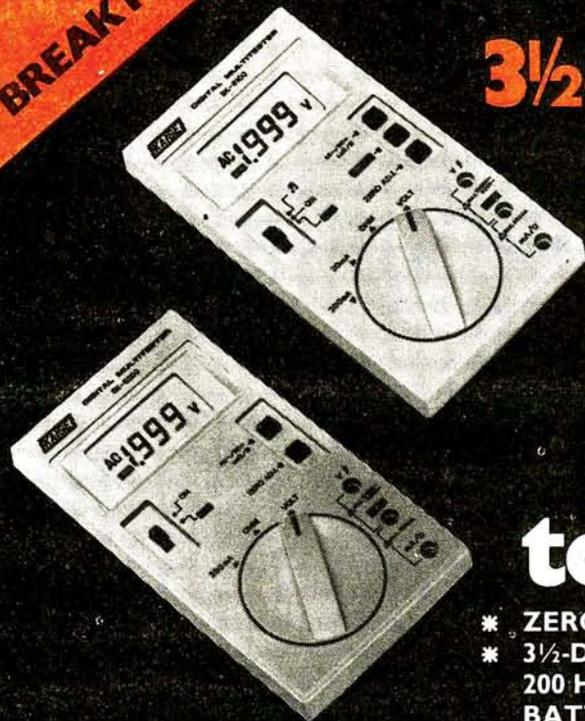

If you want an Autoranging 3 1/2-digit LCD DMM For only

£39.95

(inc VAT)

We've got to hand it to you!

- * ZERO ADJUSTMENT
- * 3 1/2-DIGIT LCD WITH 200 HRS CONTINUOUS BATTERY LIFE
- * AUTO 'BATT' WARNING
- * FULL AUTORANGING
- * AUTO UNIT DISPLAY
- * CONTINUITY TEST (6110 and 6100 only)
- * 10 AMP AC/DC (6110 and 6220 only)

Introducing the latest professional state-of-the-art 3 1/2-digit DMM – at really old-fashioned prices! From just an unbelievable £39.95 inc. VAT, plus £1.15 p&p!

	6100	6110	6200	6220
RESOLUTION	1mV, 10µA, 0.1Ω on all models			
FULL AUTO RANGING	✓	✓	✓	✓
RANGE HOLD	✓	✓	✓	✓
UNITS OF MEASUREMENT DISPLAYED	mV, V, mA	mV, V, mA, A	mV, V, mA	mV, V, mA, A
FUNCTIONS DISPLAYED	Ω, KΩ, AUTO, BATT, ADJ, LO, – and AC			
MEASURES DC VOLTAGE TO	1000V	1000V	1000V	1000V
MEASURES AC VOLTAGE TO	750V	750V	750V	750V
MEASURES AC/DC CURRENT TO	200mA	10A	200mA	10A
ZERO ADJUSTMENT	Zeros out minute test-lead resistances for precise measurements			
ACCURACY	0.5%	0.5%	0.8%	0.8%
LOW POWER OHM RANGES	For in-circuit resistance measurements on all models			
BUZZER – Continuity Test	✓	✓	✓	✓
BUZZER – Over Range Indicator	✓	✓	✓	✓
COMPLETE WITH	Batteries, pair of Test Leads, Spare Fuse, One Year's Guarantee			
PRICE	ONLY £64.95	ONLY £74.95	ONLY £39.95	ONLY £49.95
p&p	£1.15	£1.15	£1.15	£1.15

Why such a low, low price? Because the A/D converter and display are custom built! This is a genuine top-spec DMM. Check these features for unbeatable value – you won't find a hand-held DMM with these features at these prices again!

Maclin-Zand Electronics Ltd.,
38 Mount Pleasant, London WC1X 0AP

I believe you! Please send me the DMM/s as marked.

_____ 6200 @ **£41.10** each, inc. VAT, p&p. Total price £ _____
 _____ 6220 @ **£51.10** each, inc. VAT, p&p. Total price £ _____
 _____ 6100 @ **£66.10** each, inc. VAT, p&p. Total price £ _____
 _____ 6110 @ **£76.10** each, inc. VAT, p&p. Total price £ _____

Total cash/cheque enclosed £ _____
 Cheques payable to
 Maclin-Zand Electronics Ltd., please.

Available exclusively from the company that gives you tomorrow's technology today.
 38 Mount Pleasant, London WC1X 0AP.
 Tel. 01-278 7369/01-837 1165

ACCESS orders taken. Please write card no: and signature.

ACCESS NO _____

Name _____

Address _____

Signed _____



Maclin-Zand

Making state-of-the-art affordable.

To: Maclin-Zand Electronics Ltd., 38 Mount Pleasant, London WC1X 0AP.
 Despatch by return. For overseas orders, please add £5 to cost of total order package.

2PW

★ components

FM IF & AM TUNER MODULE

Resistors

$\frac{1}{4}$ W 5% carbon film

100Ω	1	R19
270Ω	2	R21,27
330Ω	2	R9,17
390Ω	1	R14
470Ω	1	R16
820Ω	1	R15
1kΩ	2	R26, 36
2.2kΩ	2	R18, 20
3.3kΩ	1	R13
4.7kΩ	7	R2,4,6,12,22,28,39
10kΩ	5	R24,25,30,31,34
12kΩ	1	R1
18kΩ	2	R8,40
47kΩ	1	R33
100kΩ	3	R29,32,35
220kΩ	6	R3,5,7,11,37,38
1MΩ	1	R10

0.1W min. horizontal preset

470kΩ	1	R23
-------	---	-----

Semiconductors

Integrated circuits

ULN2242A		
or TDA1090	1	IC1

Transistors

BC238	2	Tr3,5
BC308	2	Tr4,6
BF274	2	Tr1,2

Diodes

BA182	12	D1-12
KV1215-100*	2	D13-18
1N4148	1	D19

*Triple discrete varicap (Toko)

Miscellaneous

IC socket, 20-pin x 0.3in d.i.l. P.c.b. connectors, 0.1in pitch, board/wiring: 2 off 12-way. Printed circuit board. Screening box assembly.

Capacitors

Polystyrene

100pF	1	C2
220pF	2	C8,11
470pF	2	C5,36
1.5nF	2	C18,19

Sub-min. plate ceramic

56pF	1	C25
------	---	-----

Low voltage disc ceramic

10nF	8	C3,6,9,12,13,14,27
22nF	7	C16,17,20,26,30,33, 35,38
47nF	3	C28,32

Tantalum bead, 10V

100μF	1	C24
-------	---	-----

Tantalum bead, 25V

2.2μF	1	C23
10μF	2	C22,31

Electrolytic, p.c. mounting, 16V

10μF	1	C21,29
100μF	1	C15

Trimmers, foil (Dau TC2)

2-22pF	6	C1,4,7,10,34,37
--------	---	-----------------

Filters & Inductors

FL1, FL2 CFSE (2 off, must have same colour group)

FL3	CFM2 468B
L1	7mH Can 1980
L2	470μH 8RB 471J
L3	5.6mH 8RB 562K
L4	18μH 7BA 180JE
T1	7E LMC4102A
T2	10K KACSK586
T3	Can 4718
T4	Can 4786
T5	RWO 6A 7752
T6	YXRS18576AQ 78443
T7	154AN 7A 6441
T8	154FN 8A 6439

tionally keen can even arrange for the muting level to be switched from a circuit that checks to see if the signal is stereo or mono, and selecting the muting level rate accordingly.

The emitters of Tr3 and 4 are held at reference (approx. 5.6V); their bases are commoned and monitor the decoupled a.f.c. output from pin 7 of the i.c. The a.f.c. swing centres on the reference voltage, thus if the a.f.c. voltage goes approximately 0.6V either high or low of the reference, then either Tr3 or Tr4 conducts (respectively). If Tr3 conducts, Tr6 conducts holding the deviation muting output (pin 10 of the module) in a high state. If Tr4 conducts, then Tr5 also conducts, thus Tr6 conducts—and the muting output stays high. Transistor Tr5 also monitors either the a.g.c. (by linking pins 7 and 8 on the module)—or mute (link 6 & 8). If a.g.c./mute is high (low signal level), then Tr5 conducts, Tr6 conducts, and once again the mute output stays high.

Only if the a.g.c. or mute is low (signal tuned in) and the a.f.c. is centred within 0.6V on the reference can Tr6 turn off, driving the deviation mute output low. Applying this to

the muting input of the i.c. on pin 8 via diode D19, means that the deviation mute signal cannot hold the mute shut (audio off) when the signal is high. However, it can assist in holding the mute open (audio on) when the signal is low.

The full deviation muting facility is available when a 47kΩ resistor is applied between pins 5 and 11 of the module. This holds the mute open if the deviation mute output is high. Thus, manual override of all deviation mute facilities is available at pin 5 of the module.

The operational bandwidth of the deviation muting system is set by the voltage at the bases of Tr3 and Tr4. The swing of the a.f.c. voltage at pin 7 is determined by the resistance from pin 7 to V_{ref} (i.c. pin 13), since the a.f.c. output is a current source/sink, and not a voltage in its own right. Values are chosen for a ± 20 kHz bandwidth of operation (or "window"), to enable the scan detection to operate accurately with the synthesiser selecting the f.m. band in 50kHz steps (Fig. 19).

The detected audio output appears at pin 6, together with a lot of unwanted i.f. signal, and unless the i.f. is effectively decoupled, it will lead to instability if it gets near the


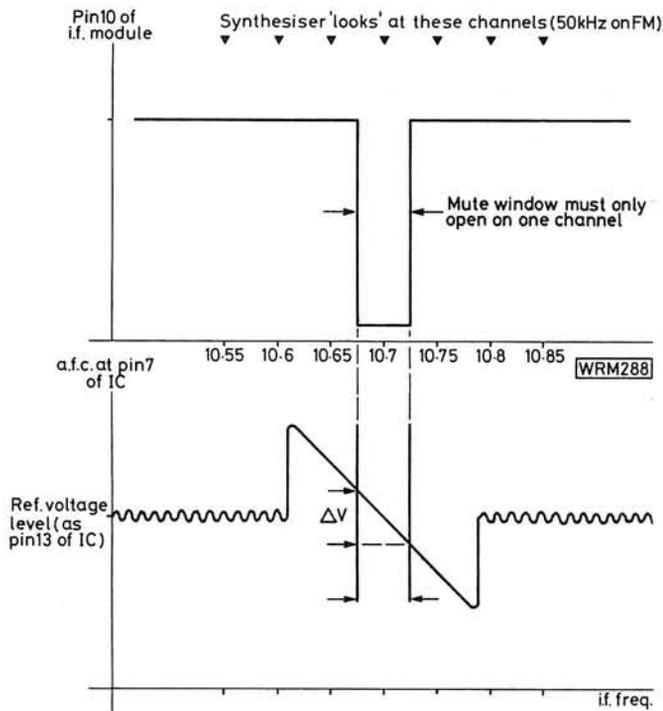


Fig. 19: Deviation mute window determination. The values of R22 and R34 are chosen so that the a.f.c. voltage swing is sufficient to turn on Tr3 and Tr4 (Fig. 14) at the extremes of the mute window

Fig. 20: Requirements for the multiplex birdy filter

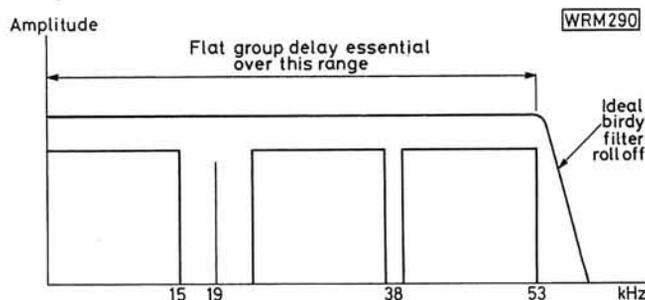

answer is a correctly designed 55kHz low-pass filter, sometimes referred to in this context as a "birdy" filter, which offers large attenuation at anything above 55kHz, but does not affect the band of frequencies below 55kHz (Fig. 20). This filter also helps to reduce stereo birdy noises brought about by the presence of the extremes of adjacent f.m. signals in the 55kHz composite baseband, since although the centre frequencies of two f.m. signals may be separated by 200kHz (unusual under normal UK listening conditions), there is plenty of scope for the extreme sidebands to mix and produce high frequency products above 55kHz. This filter is formed by C18, L1 and C19.

Next month, we deal with the decoder, a.m. tuner and remote switched/tuned ferrite rod aerial, and begin constructional details.

10.7MHz input. The usual tricks don't work. A 10nF ceramic disc capacitor will get rid of the i.f. signal, but also reduce the audio bandwidth long before the 53kHz required for a composite stereo signal has passed through. A value of 100pF would be better, but since the TDA1090 is also an a.m. i.c., the 468 kHz i.f. of the a.m. section must be taken out as well, or the a.m. will become unstable. The

Aerials and aerial accessories are very definitely among the most popular topics covered in *Practical Wireless*. In response to requests from readers, we've reprinted a selection of articles from the past three years, plus two new features—one by Ron Ham on v.h.f. propagation, the other describing the "Ultra-Slim Jim", a new version of that most popular 2-metre aerial design by Fred Judd.

Out of Thin Air has 80 pages, 295 x 216mm, and is available from W. H. Smith price £1.25, or by post from Post Sales Department, IPC Magazines Ltd., Lavington House, 25 Lavington Street, London SE1 0PF, price £1.50 including postage and packing to UK addresses, or £1.80 by surface mail overseas. Please ensure that your name and address are clearly legible.

OUT OF THIN AIR

Please send your order and remittance to:

**IPC Magazines Ltd., Post Sales Department,
Lavington House, 25 Lavington Street,
London SE1 0PF**

Please send me.....copies at £1.50 each to include postage and packing (£1.80 surface mail overseas)

I enclose P.O./Cheque No.....Value
UK remittances must be by crossed postal order or cheque (name and address on back please) and made payable to IPC MAGAZINES LTD

NAME
(BLOCK LETTERS)

ADDRESS
(BLOCK LETTERS)

.....
.....
..... Post Code

Remittances with overseas orders must be sufficient to cover despatch by sea or air mail as required. Payable by International Money Order only

Company registered in England. Regd. No. 53626

A subsidiary of Reed International Limited

— Cut round dotted line —

Follow-up to

THE PW

NIMBUS

M. TOOLEY & D. WHITFIELD

The next module in the PW "Nimbus" series, a 16-channel scanner with lock-out facilities, will commence in our January 1981 issue

It may seem a little odd to publish a follow-up article before the series has even finished, but we thought it would be helpful to pass on some comments and advice which have arisen out of readers' experiences in building the basic PW "Nimbus" transceiver and the base-station adaptor.

In general, the comments have concerned the receiver, most constructors having found that the transmitter works satisfactorily, although for some the problems have been the other way around.

1. Large transmitter output at half-frequency (72.5MHz). First of all, as most constructors will have realised, coils L7 and L8 are fitted with tuning slugs. Standard "500 grade" cores, as supplied by Maplin Electronics, were used successfully in the prototypes in L1-L8, but increased output could undoubtedly be obtained with v.h.f. "900 grade" cores in L5 onwards.

Very careful alignment of L7, L8 and TC5 is required to provide clean drive at 145MHz to Tr6. If 72MHz radiation is still a problem, then a series-resonant trap circuit (Fig. 1) should be connected across the transmitter output. To set up this trap, simply adjust the core to "suck out" the 72MHz signal. Alternatively, pre-tune it to 72MHz with a grid dip oscillator, connecting the coil and capacitor as a parallel resonant circuit for this adjustment.

2. Instability in the transmitter p.a. stage. The 2N4427 was selected for this stage because of its rather "tame" performance compared with other transistors (e.g., 2N3866), capable of producing a higher output but prone to go into self-oscillation when not correctly tuned. It may well be that there is a variation in performance of 2N4427s from one manufacturer to another, and in very difficult cases a 100Ω $\frac{1}{4}W$ carbon resistor wired in parallel with RFC1 could be helpful. The resistor should be soldered to the underside of the p.c.b., with the shortest possible leads.

It is, of course, important that all decoupling capacitors (C7, etc.) are ceramic disc types, fitted close to the p.c.b. and with the shortest possible leads. They will otherwise be useless at the frequencies involved.

3. Squelch circuit ineffective. Regrettably, the CA3089/3189 is well-known for its poor squelch system, though it may be adequate for broadcast f.m. tuners! It is advisable to check that the quadrature coil (L105) has been connected correctly, with the primary winding to pins 9 and 10 of IC101, since with less than about 150mV of signal drive at pin 9, the squelch circuit will not operate at all.

On the prototypes, the squelch range was rather limited, and it was for this reason that the control was made a pre-set, rather than completely variable.

4. Large residual reading on the "S" meter. A large residual reading could be due to incorrect alignment of L104, since it is caused by 10-245MHz leaking into the second i.f. stages. If this cannot be reduced, try the modification shown in Fig. 2, which will provide a zero to full-scale "S" meter reading.

In cases where the residual reading is acceptable (it was about 10 per cent of f.s.d. on the prototypes) but full scale is not reached on an "S9" signal, reduce the value of R128 (try 2.2k Ω) to produce f.s.d.

The calibration of any "S" meter fitted to the PW "Nimbus" will be only somewhat arbitrary, and a 0-5 scale may well be preferable to a conventional dB scale.

5. Receiver first oscillator problems. As most constructors will have realised, the contents of Tables 3 and 4 (page 60, PW May 1980) have been transposed, although the formulae are correctly placed.

The first oscillator uses 45MHz overtone crystals, but the oscillator is basically a fundamental mode circuit with collector tuned broadly to 45MHz to select the third harmonic of the frequency of the signal at the base of Tr102. The reason for employing this rather unusual arrangement

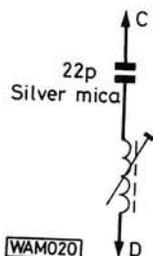


Fig. 1: A 72MHz trap. The coil is 4 turns of 22 s.w.g. enamelled copper wire, wound on a 4.8mm diameter former fitted with a dust iron core

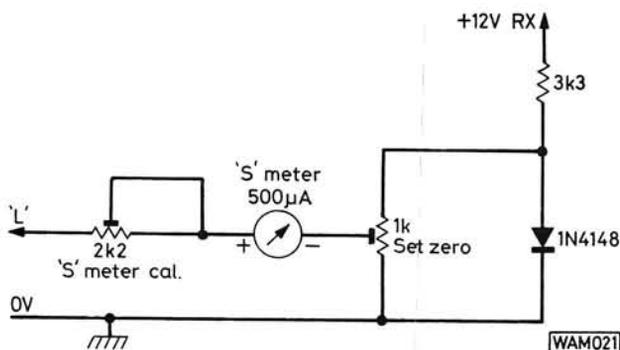


Fig. 2: Suggested "S" meter modification

continued on page 72 ▶▶▶

MODS

IMPORTANT—The ideas presented here are suggestions only, and as they are untried by this magazine, we cannot accept responsibility for any resultant damage, however caused. Before alterations are attempted, care should be taken to ensure that any guarantee is not invalidated, and it should also be borne in mind that modifications usually have an adverse effect on resale prices. In cases where specialist skills or equipment are needed, most dealers will undertake the work for a reasonable fee.

Roger Hall G8TNT(Sam)

No. 1

The title of this feature will be self-explanatory to most amateurs, but for those who think it has something to do with the fitting of chromed bubbles and eight-foot aerials to Vespas, it should be explained that, in this instance, "Mods" has no connection with "Mods & Rockers". It is, of course, an abbreviation of the word modifications, and is used by amateurs to describe alterations that can be made to improve the performance, or to extend the facilities of standard amateur equipment.

Mods come from a variety of sources; some from the manufacturers, some from dealers' workshops, and a large proportion from people who enjoy tinkering with their sets. Whilst some mods are adopted universally, some are known only to the originator and his immediate circle of friends. With this in mind, I hope to use this feature to extend some of the lesser-known ideas to a wider audience. In order to do this, I would like anyone who has modified any piece of amateur equipment, and who would like his idea published, to write to me at the address below. Please don't forget to include your name and address so that you can be given the credit (or the blame) for the idea. Initially we will be publishing dealers' mods, but I would like to use as many readers' ideas as possible, so please write to me if you have any tips to pass on.

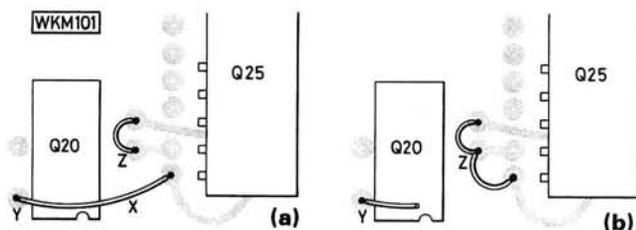


Fig. 1: Extending the frequency range. In some later models Q20 (TC9122P) and Q25 (μ PD 651C-13) are numbered Q14 and Q15 respectively

This month, Lowe Electronics have suggested two very useful modifications for the Trio TR2400. The first is for those of you who may be holidaying abroad, and who wish to extend the range of the 2MHz European model to 4MHz, with direct keyboard entry over the entire range. Before starting, please note that although it is very simple elec-

tronically, physically it requires a fine-tipped soldering iron and a steady hand. Steve Boler, the Sales Manager of Lowe Electronics, has stressed that he does not want to be inundated with 2400s containing molten microprocessors.

The first step is to remove the faceplate, by undoing the two screws at the top of the back, and the two screws in the battery compartment, underneath the battery pack. Having done this, locate the two integrated circuits, Q20 and Q25, and the link wire X, shown in Fig. 1(a). Cut this wire approximately in the middle, strip back some of the insulation from the end that is still attached to Q25, then resolder it to point Z, see Fig. 1(b). Ignore the end attached to point Y. Now replace the faceplate, because that's all there is to it. It should now be possible to select any frequency between 143.900 and 148.495MHz by pressing the appropriate buttons on the keypad. One more word of caution, again from Lowes, beware of winning the WACS (Worked All Cop Shops) award, as the band above 146MHz is allocated to the police in the UK.

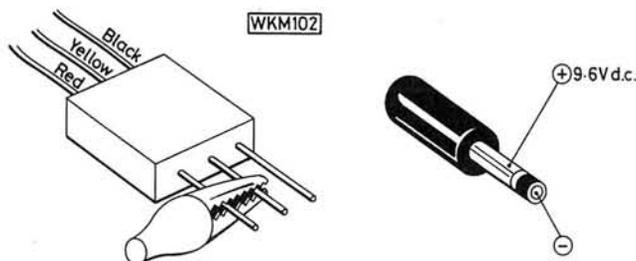


Fig. 2 (left): Identifying leads to be shorted Fig. 3 (right): Polarity of the external power connector

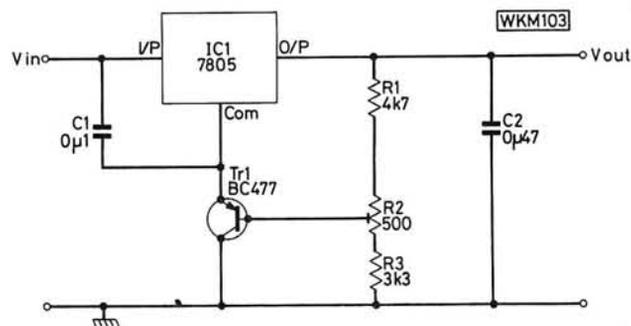


Fig. 4: A stabiliser circuit capable of providing +9.6V at currents up to 1A from a 12V car battery supply

The second modification enables the TR2400 to be run from an external power supply, and is even easier to carry out. The first step is to remove the battery pack and short out two of the pins on the connector inside the set, as shown in Fig. 2. A miniature crocodile clip is adequate, but if repeated use is anticipated, it would be better to obtain a suitable female connector, and to short out the appropriate two sockets, and to use this instead of the clip. With the pins shorted together, a 9.6V power supply can now be plugged into the "Charger" socket. Please note the polarity, see Fig. 3. A circuit for a suitable 9.6V supply is shown in Fig. 4.

A modified TR2400, used with a suitable power supply and a small power amplifier, could make an effective mobile or base station, without the inconvenience of the batteries dying halfway through a QSO.

The address to write to if you have any modifications for publication is: R. S. HALL, Practical Wireless, King's Reach Tower (Hatfield House), Stamford Street, London SE1 9LS.

73's
Sam G8TNT

LOWE ELECTRONICS LTD.



TRIO R1000

£298 inc VAT

THE FINEST HF COMMUNICATIONS RECEIVER FROM THE LEADING COMPANY IN THE FIELD

R 1000 BY TRIO

THIS RECEIVER IS SO ADVANCED, IT MAKES ANYTHING ELSE IN ITS PRICE RANGE COMPLETELY OBSOLETE.

And we should know, because we at Lowe Electronics have been firmly committed to Trio ever since we were appointed to be the UK distributors many years ago, and we are your direct contact with the Trio factory if you need advice or information. As the Trio distributors, we maintain the finest amateur radio workshop in the country here at Matlock, and our customers will tell you of our renowned service.

We stock and sell the complete Trio range, and operate a fast, efficient mail order and Securicor delivery service so that you are as close to us as your nearest letter box. We also recently introduced a terrific new credit card scheme which gives you, the customer, real purchasing power with instant credit.

As an example, should you wish to pay £12.50 per month, you have instant credit of £300.00 which is enough to buy your R1000 right away; no hefty deposits, no fuss and as a further bonus, should you need accessories, or even a new transceiver, you can extend the credit on your card to suit. The Lowe blue card is a really powerful purchasing aid and you shouldn't be without it. Why not ask us for details right away and also for full information on all that's good in Amateur radio.



The new digital flight scan receiver from Regency of America is a stunning improvement on any other air band monitor receiver. Utilising its own micro computer system to control an advanced synthesiser, the flight scan allows you to monitor any air band frequency in the range 108-136 MHz and to store up to 16 channels which can then be scanned continuously. Other features include fast keyboard entry of frequency, full band search facilities, channel lockout and much more. For the latest word in air band monitors contact us today. Also available - M1000 digital FM scanner covering 30-50 MHz, 144-174 MHz and 430-512 MHz.

FLIGHT SCAN £199 inc VAT carr £4.50
M1000 FM SCAN £192 inc VAT carr £4.50



R820

The ultimate in receiver design. Trio R820. With more features than ever before available in a ham band receiver. This triple-conversion (8-83 MHz, 455 KHz and 50 KHz I.F.s.) receiver, covering all amateur bands from 160 through 10 metres, as well as several short wave broadcast bands, features digital and analog frequency readouts, notch filter, I.F. shift, variable bandwidth tuning, sharp I.F. filters, noise blanker, stepped R.F. attenuator, 25 KHz calibrator, and many other features providing more operating conveniences than any other ham band receiver. Price £690.00, including V.A.T. Carriage £4.50.

SP820


Matching speaker to fit the R820, with built-in filters, 8 ohms impedance. Price £37.95, including V.A.T. Carriage £1.50.

SRX30

The SRX-30 represents a new step forward for the keen short wave listener or the radio amateur who needs to tune frequencies outside the amateur bands. In the past, the performance of general coverage receivers has been limited by the difficulty inherent in setting to a known frequency - OK, so you know that Radio Peking is on 8547 KHz but how do you set the receiver dial?

The SRX-30, due to application of new technology solves the problem by utilising a drift cancelling loop system converting to a very high (40 MHz) first IF so as to remove image interference problems. This is followed by a stable VFO controlled tunable second IF with excellent reset accuracy. The frequency range covered by the SRX-30 is 500 KHz - 30 MHz in thirty bands, each 1 MHz wide. If you wish to tune to say 14250 KHz, simply set the MHz dial to 14, the KHz dial to 250 and there you are, no fuss, no twiddling, no need to use calibrators, etc. (remember the drift cancelling system).

The SRX-30 is housed in a rugged metal case and operates from 240V ac mains or 12V dc supply. Reception modes are USB/LSB/AM/CW to cater for all HF operation and the receiver is equally at home on VHF using an external converter. This receiver combines small size, accurate readout, ease of use, all mode operation, mains/battery power supply and excellent performance at a remarkably low price. See it, use it and you will like it.

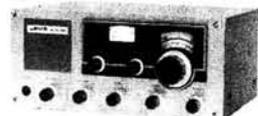

Price £178.00 including V.A.T. Carriage £4.50.



FS10

The FS10 VHF FM monitor receiver is a high performance unit in such a small lightweight package that it will fit into a pocket. The receiver can be aligned for the 2 metre amateur band or the VHF marine band and provides top performance on either band.

The FS10 automatically scans up to ten crystal controlled channels, stopping on any channel where a signal is present. Manual selection of any channel is also provided. Complete with rechargeable battery pack, charger and personal earphone with provision for external antenna.

Price £82.00, including V.A.T., crystals extra. (Fitted ten channels £109.25, including V.A.T.) Carriage £1.50.



AMR217B

The AMR217B VHF FM monitor is an outstanding receiver suitable for either the 2 metre amateur band or the VHF marine FM band and can be supplied for either band on request. The AMR217B has an eight channel scanning facility and can also accommodate up to ten additional switched channels to extend its versatility even further. The receiver is extremely sensitive and is one of the best monitor receivers available to either the amateur or professional user. It is completely self-contained with a built-in speaker and operates from 240V AC mains or 12V DC supplies. A matching mobile mount is supplied to allow easy installation in boat or car.

price £120.75, including V.A.T. (fitted 8 crystals). Carriage £1.50.



SR9

The SR9 represents the finest value for money ever offered in the FM monitor receiver market. Available in two versions to suit the 2 metre amateur band or the VHF marine FM band the SR9 gives fully tunable coverage of either band and also incorporates the facility for installing optional crystals which will provide up to eleven fixed channels for the most popular frequencies.

The SR9 is completely self-contained with built-in speaker and requires only 12V DC at around 200 mA to operate. Mounting hardware is provided for easy installation anywhere.

Price £46.00, including V.A.T. Carriage £1.50.



API2

The API2 is a 12 channel crystal controlled airband monitor receiver covering a frequency range from 108 to 136 MHz which utilises a micro-computer which automatically peaks the R.F. oscillator and mixer stages in accordance with the crystal frequency in use. This means that you can install crystals for any frequency in the entire band without any drop in performance. Supplied complete with rechargeable battery pack, charger and personal earphone. Price £89.70, including V.A.T. Fitted 12 channels: £118.45, including V.A.T. Carriage £1.50



R512

The R512 airband receiver is a high performance unit which automatically scans up to eight crystal controlled channels. The receiver will stop on any channel on which there is a transmission, stepping on again at the end of transmission. You may lock the receiver onto any channel of your choice for continuous monitoring and if any channel should be more or less permanently occupied you may also lock out the channel to permit scanning of other channels. These facilities are available on any or all channels. Covering the full band from 108-136 MHz, the R512 is completely self-contained including built-in speaker and is supplied with mains and 12V DC power leads, whip antenna, mobile mounting bracket and personal earphone. Price including five fitted channels is £138.00, including V.A.T. Carriage £1.50.



For all that's good in Amateur Radio, contact;
LOWE ELECTRONICS LTD., Chesterfield Road, Matlock, Derbyshire. Tel: 0629 2430 or 2817.
For full catalogue, simply send 48p in stamps and request catalogue CPW.

air test

USER REPORTS ON SETS AND SUNDRIES

Microwave Modules MML 432/50



Microwave Modules make a wide range of linear amplifiers and transverter units, and the subject of this report is their 50 watt linear for the 70cm amateur band. They also make a 100W linear, but the 50W version is the more popular, probably because of the price.

The MML 432/50 is housed in a substantial sheet steel box with the printed circuit board fitted to the large aluminium finned heatsink which forms the box top. The power switch is fitted to one end of the box, and the connectors for the r.f. input and the aerial are on the opposite end. A robust mounting bracket is attached to the sides, bridging the heatsink to allow the linear to be mounted in a vehicle.

The 13.8V supply is fed to the amplifier via two heavy leads, and the supply is fused by a panel-mounted fuseholder next to the cable entry. When the MML 432/50 is being driven to its full power output of 50W, the current drain from the power supply is 8A, so it is essential to keep the power lines as short and direct as possible.

As well as the linear amplifier, the unit contains a 70cm pre-amplifier, the changeover from transmit to receive being carried out automatically by a VOX system operating on the r.f. input to the amplifier. The VOX can be overridden by an external switching system if desired, but the automatic system worked very well, and during the tests it was the only switching used.


Initial tests were carried out using the Standard C7800 f.m. rig to drive

the linear. The power supply used for base-station tests was a large car battery, float-charged during use, this being the only means available at the time capable of meeting the high current demands. The C7800 pushes out about 12W, and this should have been more than enough to drive the linear to its full rated output of 50W. However, the maximum output measured was 48W, probably due to voltage drop on the supply lines. Reducing the input power to around 1W reduced the output of the linear to 5W. The 12dB or so of gain in the pre-amplifier section made no difference to the Standard as a base station, but this was put down to the superb performance of its receiver.

When used in the car, the linear did improve the coverage obtained from the Weymouth repeater GB3SD, but the improvements were only marginal with the C7800. Difficulty was found in getting the full rated power output from the linear, in this case definitely due to voltage drop along the wiring from the battery. In fact with the motor turned off and the linear driven by the Standard, the r.f. power output could be seen to fall off rapidly on the wattmeter, as the battery voltage decayed to its off-charge level.

The unit was also tested with a Philips FM321 transceiver, and the improvements here were dramatic. The pre-amplifier gain brought the receiver performance up to the same level as that of the C7800, and the linear improved the 6W output to a healthy 30W. This allowed simplex operation between the Standard as a base station and the Philips run mobile over a range of some 15 miles, compared to about 6 miles or so with the Philips running barefoot.

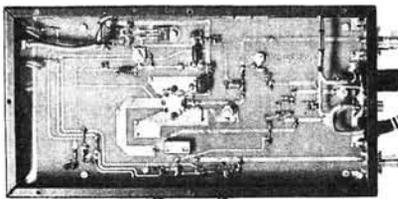The MML 432/50 was not tried with s.s.b. equipment, and this is undoub-



tedly where its benefit would be most noticeable. Obviously it is essential to ensure that the unit is supplied with 13.8V through cable of sufficient size to prevent undue power loss due to voltage drop. Otherwise, the unit is very simple to install and use, and can really transform a rig with an average performance.

The MML 432/50 costs £116.60 including carriage and VAT, from **Microwave Modules Ltd., Brookfield Drive, Aintree, Liverpool L9 7AN, telephone 051-523 4011**, to whom we offer our thanks for the loan of the review unit. It is also available from authorised retail stockists around the UK.

AR-22 PLL FM Receiver



The AR-22 is a pocket-sized v.h.f. f.m. receiver tuning over a range of 141.000MHz to 149.995MHz, which includes, of course, the 2m amateur band. A phase-locked loop synthesiser


gives coverage in 5kHz steps, with direct setting and read-out of tuned frequency by three digital push-switches and a slide switch. Sensitivity is quoted as 0.2 μ V for 12dB SINAD, with a -60dB bandwidth of 24kHz. Dual conversion is used (i.f.s are 10.7MHz and 455kHz) with spurious and image rejection specified as better than 50dB down.

The AR-22's diminutive size (136 x 64 x 25mm overall) also houses a 225mAh 4.8V NiCad battery pack. Consumption is quoted as around 25mA with the receiver squelched, rising to around 100mA when delivering its maximum rated 100mW into an 8 Ω load.

Supplied with the set are a 100mm helical whip antenna, a $\lambda/4$ wire antenna, an earpiece, a charger unit capable of restoring the battery pack to full vigour in around 10 hours, and an owner's manual.

Results

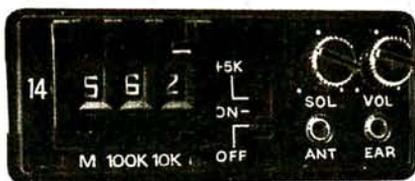The AR-22 is a very sensitive receiver with a sound output of very adequate volume and quality. Best results are obtained with the wire antenna, as might be expected, but the more convenient "mini rubber duck"



does well for itself. At the home QTH, some three quarters of a mile from GB3SC, that station comes through, albeit noisily, even with no antenna plugged in. This is obviously due to the lack of any screening in the plastics case, plus a fair length of unscreened wire between the antenna jack and the p.c.b., which although double-sided does not incorporate an earth-plane. The manual in fact warns against using the set in the vicinity of a transmitter, where the field strength might exceed 1V/m.

With its small size and low weight (around 200g) the AR-22 is truly a pocket set. It is a shame that its designers went completely overboard on the arrangement of the controls. Frequency setting arrangements are alright, but the knobs on the Squelch and Volume controls are each 7mm in diameter and 7mm high including the bar on top. The clearance between them is only 2mm, and between the

Squelch knob and the base of the helical antenna only 1mm. The controls themselves are stiff anyway, and even using just finger- and thumb-nails on the top bar, are very difficult to adjust sensibly.

The manual gives the specification and operating instructions, but no service information whatever. Looking inside the set, it is so miniaturised and tightly packed that any repairs would be beyond the capabilities and facilities of most owners anyway, so this is perhaps a minor point.

The AR-22 costs £99 including carriage and VAT from **Bredhurst Electronics, Mid Sussex House, High Street, Handcross, West Sussex RH17 6BW, telephone 0444 400786**, to whom we offer our thanks for the loan of the review unit.

Have you seen
our survey of
Multi-mode
2m mobiles?

DEMAND THE "ORIGINAL"

SPECIAL QUOTES!

ON 27 TO 1000 MHz
FIBREGLASS ANTENNAS
ANYWHERE IN THE WORLD!

'Firestik'[®]
ANTENNAS

NOW IN SIX COLOURS!

- SILVER-GREY
- RED
- WHITE
- BLACK
- SPUN GOLD
- CLEAR

THE No. 1 HELICALLY WIRE WOUND AND MOST COPIED ANTENNA IN THE WORLD!

CB • 2 METRE • MARINE TELE • LAND MOBILE TELE

- TRUE HIGH dB GAIN ANTENNAS
- LOW ANGLE OF RADIATION
- $\frac{5}{8}$ and $\frac{3}{4}$
- LOW SWR PROVEN
- POWER RATED UP TO 1400 WATTS
- RUGGED SHATTER-PROOF FIBREGLASS
- FACTORY PRE-TUNED
- THE ULTIMATE PERFORMERS


SERVING THE CB AND COMMUNICATIONS MARKET WITH 27-1000 MHz EQUIPMENT SINCE 1962

'FIRESTIK' ANTENNA COMPANY ● 2614 EAST ADAMS ● PHOENIX, ARIZONA 85034 U.S.A.

DISTRIBUTED IN THE
UNITED KINGDOM BY:

WINTJOY Ltd.

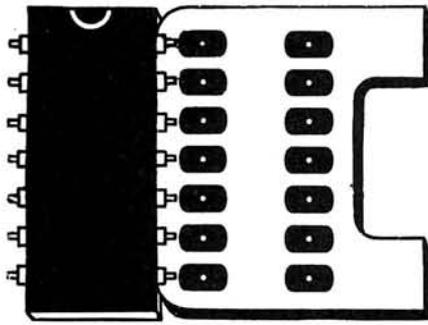103 High Street, Shepperton, Middlesex
Tel: Walton-on-Thames 48145



OF THE MONTH

Brian DANCE M.Sc

The SG3524 Regulating Pulse Width Modulator

Introduced by Silicon General Inc. in 1976 as the first monolithic switching regulator control device, the SG3524 was soon second-sourced by Texas Instruments Ltd., and is now an "industry-standard" type—which means it is produced by many manufacturers. Containing all of the semiconductor devices required to make a regulated power supply, inverter or switching regulator circuit integrated onto a single chip, it can also be employed as the controlling element of a high power circuit.

The SG3524 was designed for switching regulators of either polarity, transformer-less d.c.-to-d.c. converters, transformer-less voltage doublers and for polarity converter applications employing fixed-frequency pulse-width-modulation techniques, and also for other power control applications.

Encapsulated in a 16-pin dual-in-line package with the connections shown in Fig. 1, the device contains a voltage reference which is used as a standard voltage, an error amplifier, an oscillator circuit, a pulse-width-modulator circuit, a pulse steering flip-flop circuit, a pair of alternating output switching devices together with current limiting and protective shut-down circuitry.

The absolute maximum power supply voltage rating for the SG3524 is 40V, but it is wise to regard the maximum as being about 35V to prevent the possibility of damage with supply fluctuations or transient voltage spikes. The quiescent current is about 8mA, increasing when a load is applied, with a maximum permissible current from collector 1 or collector 2 of 100mA.

The internal reference block provides an output of 4.6V to 5.4V (typically 5.0V) at pin 16, and current of up to 50mA may be taken from this pin. As the input voltage increases from 8V to 40V, the voltage of pin 16 varies typically by 10mV (maximum 30mV) and, as the load current at this pin increases from 0 to 20mA, the voltage varies by about 20mV (maximum 50mV). The variation of the reference voltage with temperature is typically 0.3 per cent (maximum 1 per cent) over the range 0°C to +70°C and the long-term stability at 25°C some 20mV per 1000 hours of use.

The Oscillator

The internal oscillator circuit requires an external resistor R_T from pin 6 to ground and an external capacitor C_T from pin 7 to ground. The charging of the capacitor by a current passing through the resistor provides a linear ramp waveform for timing the oscillator circuit. The charging current is equal to about 3.6V divided by R_T , so the value of R_T should be 1.8k Ω to give 2mA.

It is recommended that the values of C_T should lie in the range 1nF to 100nF, since the value of this capacitor determines the pulse width of the oscillator output pulse; a pulse width of less than about 200ns may allow false triggering of one output by removing the blanking pulse

before the flip-flop has reached a stable state. It is possible to synchronise a SG3524 to an external signal or to another SG3524.

In many cases a stabilising network consisting of a resistor and a capacitor in series will be required from pin 9 to ground. A 50k Ω resistor in series with a 1nF capacitor will usually be satisfactory for stabilisation of the error amplifier.

A current of 200 μ A taken from pin 9 will disable the SG3524.

The output circuit consists of two transistors with both the collectors and emitters available at external pins. Both transistors have anti-saturation circuitry which limits the current through each transistor to a maximum of 100mA for a fast response.

Applications

The SG3524 can be employed in a very wide variety of applications. Broadly speaking these can be classified into three main types:

1. Capacitor-diode coupled voltage multipliers.
2. Inductor-capacitor implemented single ended circuits.
3. Transformer coupled circuits.

Capacitor-diode Circuit

The capacitor-diode circuit of Fig. 3 is a simple polarity converter which produces a -5V supply from a +15V input. This circuit can provide an output of up to 20mA without any additional current boosting transistors.

The output transistors are current limited by the internal circuitry of the device, so no additional protection circuitry is required. A particular feature of this very

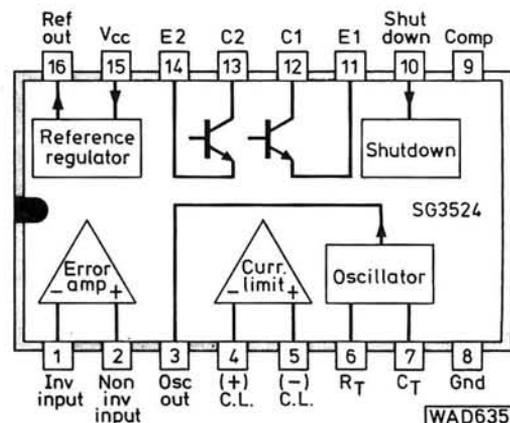


Fig. 1: The connections to the SG3524 device

YAESU MUSEN —

General Coverage Communications

Receiver FRG-7

£199.00

VAT included



● 0.5-29.9MHz Coverage with 10kHz Readout

The FRG-7 is a precision-built all-purpose communications receiver, featuring all solid state construction for long life and high performance. Utilizing the Wadley Loop drift cancellation system in conjunction with a triple conversion superheterodyne circuit, the FRG-7 boasts high sensitivity along with excellent stability. It provides broadcast listeners with such features as a 3-position tone selector, an RF attenuator, and an automatic noise suppression circuit. For many years of satisfying reception, the FRG-7 is the receiver for you.

**ALWAYS THE BEST
NOW EVEN BETTER
VALUE!**


Digital Display Communications

Receiver with CPU

Digital Clock & Timer FRG-7000

£299.00

VAT included

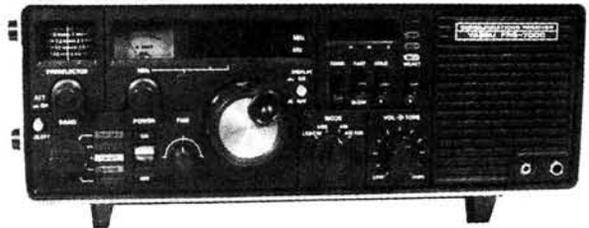

● 0.25 Thru 29.9MHz Coverage with 1kHz Readout

Computer technology and convenience features are brought together in the FRG-7000, a digital-display general coverage receiver for the discriminating SWL. The digital clock and timer, controlled by a CPU (Central Processing Unit) chip, will read out both local and GMT time, and will control peripheral station equipment such as a tape recorder. Improved SSB selectivity, ease of operation, and rugged construction are yours with the FRG-7000 from YAESU.

FULL DETAILS OF THESE RECEIVERS AND THE NEW LOW FACTORY PRICE LIST FROM
BRITAIN'S NO. 1 IMPORTER

EX-STOCK — INSTANT CREDIT — FREE SECURICOR DELIVERY

AMATEUR ELECTRONICS UK



508-514 ALUM ROCK ROAD

021-327 1497

BIRMINGHAM 8

6313

Telex 337045



BURGLAR ALARMS

SUPPLIES AND EQUIPMENT

S.A.E. for free catalogue.

LARGE SIZE PRESSURE MATS 28in x 5in £1.89.

MAGNETIC SWITCHES WITH MAGNETS FROM 75p.


**BELLS · SIRENS · ALARM UNITS · CABLE BELL COVERS
WINDOW FOIL · VIBRATION CONTACTS · ULTRASONIC
AND INFRA-RED DETECTORS · INERTIA SWITCHES**

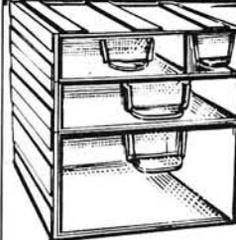A. D. ELECTRONICS

**217, WARBRECK MOOR, AINTREE,
LIVERPOOL L9 0HU.
Telephone: 051-525-3440**



NEAT! TIDY!
HANDY! 1D 2D 3D 6D
**INTERLOCKING
PLASTIC STORAGE DRAWERS**



**AS SUPPLIED:
TO POST OFFICE
& GOVT DEPTS**

SINGLE UNITS (1D) (5in x 2 1/2in) **£4.90** DOZEN
DOUBLE UNITS (2D) (5in x 4 1/2in x 2 1/2in) **£7.50** DOZEN
TREBLE (3D) **£7.50** for 8.
DOUBLE TREBLE 2 drawers, in one outer case (6D2)
£10.90 for 8.
EXTRA LARGE SIZE (6D1) **£8.50** for 8.

Newest, neatest system ever devised for storing small parts and components: resistors, capacitors, diodes, transistors, etc. Rigid plastic units interlock together in vertical and horizontal combinations. Transparent plastic drawers have label slots. 1D and 2D have space dividers. Build up any size cabinet for wall, bench or table top.

As supplied to Post Office, Industry and Government Depts.

PLUS QUANTITY DISCOUNTS
Orders over £60, less 5% PACKING/POSTAGE/
CARRIAGE: Add £1.30 to all orders under £10. Orders
£10 and over, please add 10% carriage.

QUOTATIONS FOR LARGER QUANTITIES.

Please add 15% V.A.T. to total remittance.

All prices correct at time of going to press.

**FLAIRLINE
SUPPLIES**

(PW11) 124 Cricklewood Broadway, London NW2
Telephone 01-450 4844

AMATEUR RADIO RETAILERS ASSOCIATION

Secretary: Fred Hopewell, P.O. Box 36, Loughborough LE11 1DW

Presenting the **NINTH**

AMATEUR RADIO AND ELECTRONICS

★ **EXHIBITION** ★

at the **GRANBY HALLS, LEICESTER ON 6th, 7th AND 8th NOVEMBER 1980** OPEN DAILY, 10 a.m. to 6 p.m.

£500 IN VOUCHER PRIZES TO BE WON!

PLUS FABULOUS FREE DRAW PRIZES THROUGHOUT THE EXHIBITION!

DON'T MISS THIS EXCITING EVENT — BARGAINS GALORE

REFRESHMENTS, BAR AND ALL THE USUAL AMENITIES

ADMISSION: 75p. Concessionary Tickets 50p for Parties of 15 or over

NO ADVANCE TICKETS. ON RECEIPT OF YOUR REMITTANCE WITH ORDER, TICKETS WILL BE RESERVED FOR YOU TO PICK UP AT THE BOX-OFFICE. IF YOU REQUIRE AN ACKNOWLEDGEMENT, PLEASE ENCLOSE A STAMPED ADDRESSED ENVELOPE.

BOOK THE DATES NOW FOR THE SHOW OF THE YEAR!

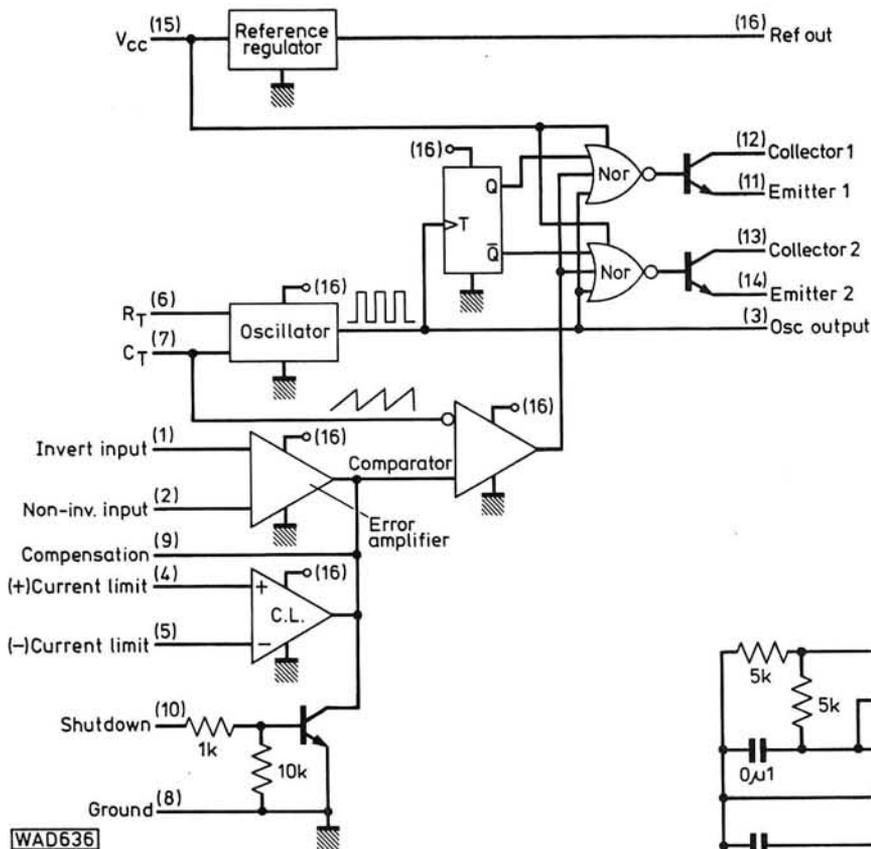


Fig. 2: Internal circuitry, in block form, of the SG3524

simple circuit is the absence of inductions which saves the constructor the problems associated with obtaining components.

During the time a current passes to the collector 1, this current flows from emitter 1 to charge the 20μF capacitor so that its left-hand side is positive. A fraction of a second later transistor 2 conducts; this means that collector 2 is effectively earthed, since emitter 2 is earthed. As the left-hand side of the 20μF capacitor is now earthed and as it is more positive than the right-hand side, the latter must be a negative potential. This negative charge is used to charge the 50μF output reservoir capacitor through a 1N916 diode. This type of circuit with two diodes is known as a diode pump, since charge is pumped through it to be stored in the 50μF reservoir capacitor at the output.

The output voltage is fed back through the 15kΩ resistor, stabilising the output voltage.

More Current

The circuit of Fig. 4 shows how the SG3524 may be used to provide a stabilised output of +5V at a current of up to 1A suitable for driving TTL circuits. The SG3524 cannot itself provide more than 100mA of output current and therefore an additional device is required which can pass the larger current and which is controlled by the collector outputs of the SG3524. In the circuit shown this device is a TIP115 power Darlington manufactured by Texas Instruments Ltd.

As in the circuit of Fig. 3, the inverting and non-inverting inputs of the error amplifier are kept at a potential of +2.5V. In the circuit of Fig. 4, the positive output voltage is divided into two equal parts and fed to the inverting input of the error amplifier, while the +5V reference output is similarly divided. The feedback mechanism maintains the potentials of pins 1 and 2 approximately equal. If the output voltage tends to rise above

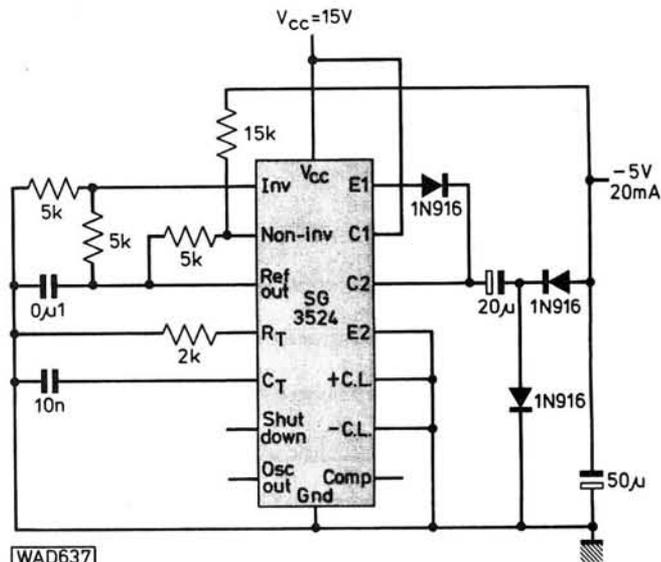


Fig. 3: An inverter circuit providing an output of -5V, 20mA

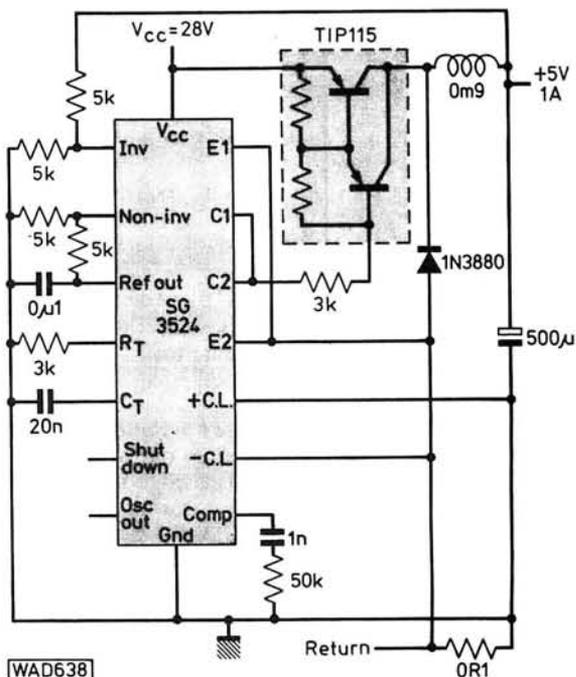


Fig. 4: This circuit uses an external TIP115 Darlington to boost the maximum output current to 1A

+5V, less charge will be fed into the 500 μ F output capacitor per unit time so that the output voltage drops towards +5V. Similarly, if the output voltage falls below +5V, more charge per unit time will flow into the output capacitor to raise the voltage to +5V (in the Fig. 3 circuit, the feedback is taken to the non-inverting input, since the output is negative).

The inductor used in Fig. 4 must have a very low series resistance if the circuit is to operate at maximum efficiency. A Mullard "RM" core with an inductance factor of 250nH can be used; this means that the inductance of a one turn coil is 250nH. As the inductance is proportional to the square of the number of turns, 60 turns will provide the required 900 μ H inductance. The wire diameter should be as large as can be accommodated on the former of a RM10 core; and should be about 0.7 to 0.75mm. Smaller cores of the "RM" series, such as the RM6 type, would result in the use of thinner wire of higher resistance; lowering the power efficiency of the circuit.

Conclusions

In order to avoid interference problems, the output capacitor should be soldered as close to the SG3524 as possible, and must be a good quality component. A capacitor of about 10 μ F should also be soldered directly between pins 15 and 8 to decouple the power input supply, unless the lead from the raw power supply is very short.

The SG3524 device and the RM10 core are available from Arrow Electronics Ltd., Leader House, Coptfold Road, Brentwood, Essex CM14 4BN.

PW "NIMBUS" FOLLOW-UP

▶▶▶ continued from page 64

was that crystals in the 15MHz region for 2m receivers are not generally available, whilst overtone types at 45MHz are available from several sources, cheaply, and ex-stock.


It was also found that this arrangement, when used with overtone crystals operating on their fundamental ($45 \div 3$), does give quite a large trimming range using capacitor trimmers, rather than the inductor trimmers more commonly used with overtone crystals.

Incidentally, crystals from two sources were tried in the prototypes, and no difficulties were experienced in getting the overtone crystals to oscillate readily in the fundamental (Colpitt's) circuit of the PW "Nimbus". The slight error in frequency which occurs when overtone crystals are operated at their fundamental was easily accommodated by means of the series trimming capacitors.

6. Low output from the base-station adaptor. The use of the optional filter unit on the output of the amplifier is strongly recommended, in order to reduce spurious emissions to the absolute minimum. The loss of 145MHz due to this filter should not exceed about 1.5dB. If it does, repeat the alignment process for the filter and check that the coupling capacitor C101 is a suitable type for use in r.f. power circuits. A possible alternative is to replace it by a "gimmick" capacitor, formed by twisting together two short lengths of pvc-insulated solid wire. The value can be adjusted by trimming the length of the wires and repeating the filter alignment process until the insertion loss is acceptable.

DON'T GET CAUGHT BENDING!

USE OUR FREE GIFT THIS MONTH

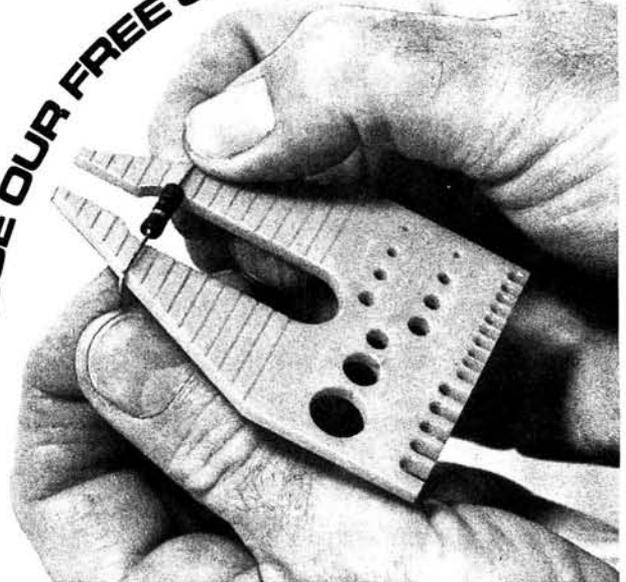

A neat printed circuit board is the hallmark of a good radio constructor, but to achieve this, all the leads of axial components such as resistors and diodes need to be accurately bent at precisely the correct hole spacing before being fitted to the board.

With the *Practical Wireless* Lead Bending Gauge, presented free with this issue, you can perform this neat bending simply and quickly.

The tapered end of the tool allows a variety of different hole spacings to be accommodated. Simply select the appropriate groove to give the desired spacing, place the component centrally in the slot, with its leads lying along the groove, and carefully fold the leads over the sides of the tool.

Other lead bending gauges have stopped at folding the leads—ours is different! At the opposite end is a useful set of gauges. The holes have been chosen to enable you to check on the sizes of drills needed to fit commonly-used screws and components such as potentiometers and switches. Around the outside of the tool is a series of slots. To check the gauge of a wire, gently try it for fit in the slots until you find the one that just lets the wire slip through to the inner hole. This slot gives you the wire gauge size. Do not force the wire through the slot, as this will tend to open it up, making it useless for further checks. Note that the slot is the gauge, **not** the inner hole.

★ specification

Component length: 11mm (maximum).

Range of lead spacings: 13mm to 50mm (approximately).

Drill sizes gauged: 0.8mm, 1.0mm, 4mm, $\frac{1}{4}$ in, $\frac{3}{8}$ in, tapping and clearance sizes for 4, 6 and 8BA screws.

Wire sizes gauged: 16 s.w.g. to 44 s.w.g. (even sizes only).

PRODUCTION LINES

ALAN MARTIN G8ZPW

New Shure Mic.

Over many years the Shure Model 444 has been regarded as the "standard" among fixed-station microphones, now an improved version has been introduced, it is the Shure Model 444D.

Among the new features is a high/low impedance selector switch, located beneath the base of the unit, which will increase compatibility with existing fixed-station equipment, also an easy-to-use slide switch is provided for normal/VOX operation. These new features join the unit's existing momentary or locking p.t.t. switch bar, the Controlled Magnetic microphone, height adjuster and tough Armo-Dur case that is impervious to rust and deterioration.

Other added features are a coiled input cable, personalised nameplate with your station callsign, and a new wiring guide which provides instructions for wiring the microphone to major manufacturers equipment.



Priced at £31.80 plus VAT, the Model 444D is available from most good amateur radio equipment stockists or direct from: *Shure Electronics Ltd., Eccleston Road, Maidstone ME15 6AU. Tel: (0622) 59881.*

Ring Main Tester


At the very least, an incorrectly wired socket can damage valuable electrical equipment; at its worst it can be physically dangerous.

Martindale, the Neasden-based company that specialises in industrial safety equipment and electrical test instruments, has now introduced its simple Ring Main Tester for use by the householder.

No larger than a conventional plug, the Tester is simply fitted into a standard 13A socket to give instant visual identification of the polarity of the wiring. Correct wiring, faulty earth connections, faulty neutral and reversed live/neutral connections are immediately shown by combinations of the carefully selected neons on the face of the Tester adjacent to ex-

planatory diagrams. A fault in the live connection or supply is indicated when no neons are lit.

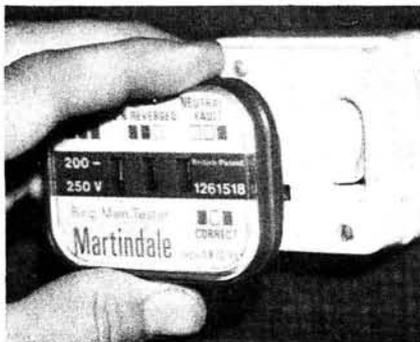The Ring Main Testers are available from local hardware, do-it-yourself and electrical retail outlets at around £4.70 plus VAT. Any difficulty in obtaining the Tester should be referred to: *Martindale Electrical Co. Ltd., Neasden Lane, London NW10 1RN. Tel: 01-450 8561.*



RTTY to TV Converter

Recently introduced by Microwave Modules Ltd. is the MM2000, a RTTY to TV converter which, among others, should be of particular interest to readers of the "Introducing RTTY" series currently running in *Practical Wireless*.

The unit requires only an audio signal link from a receiver, a 12V d.c. supply and a suitable link to a TV, to enable a live display of "off-air" RTTY and ASCII on a domestic standard u.h.f. TV set.

The following modes of reception are accepted by the converter: Amateur Standard ASCII, 300 baud; Murray Coded RTTY, 45.5, 50 and 75 baud. In each of these four modes, the converter will accept FSK and AFSK signals.

Fuelstretcher

Following a mention in "Production Lines" of specialised low-cost fuel conservation and car electronics components in the June issue of *Practical Wireless*. The company concerned, *Envirosystems Ltd.*, announce the availability of kits using these devices.

The FSX20 petrol consumption monitor displays an instantaneous digital read-out of m.p.g., with a choice of two update frequencies to suit individual driving conditions, automatic clear-down under idling and simple owner calibration facility, which makes the system generally applicable to most vehicles with carburettor fuel systems and cable driven speedometer. A unique petrol injection option is available to compensate for fuel returned to the tank.

The FSX10 petrol consumption recorder displays total gallons used, with reset facility to allow determination of overall fuel consumed and average m.p.g. This kit is lower priced as it requires fuel sensor input only.

Both kits are suitable for vehicles employing a 12V d.c. negative earth system and come complete with digital transducers, p.c.b.s and all other components, including an attractive display case. Construction and installation instructions are provided with the kits and a technical back-up service is available.

Prices inclusive of VAT and p&p for the UK are as follows: FSX10 kit £34.80; Basic FSX20 £47.50, and including the petrol injection option £65.90.

Further details from: *Envirosystems Ltd., Hampsfell Road, Grange-over-Sands, Cumbria LA11 6BE. Tel: (044 84) 4233.*

Utilising two m.p.u.s and 21 i.c.s, the MM2000 is constructed on two p.c.b.s, all housed in a black diecast enclosure measuring 187 x 120 x 53mm and weighs only 1kg.

The MM2000 costs £169 which includes VAT, and is available from: *Microwave Modules Ltd., Brookfield Drive, Aintree, Liverpool L9 7AN. Tel: 051-523 4011.*



PRODUCTION LINES

ALAN MARTIN G8ZPW

VHF Wavemeter

If you hold an amateur radio licence, one of the conditions of that licence reads something like this, "an absorption device of suitable frequency range and accuracy is necessary . . . and the frequency coverage must extend up to the second . . . harmonic . . ."

Packer Communications can supply an accurate and reasonably priced absorption wavemeter, called the WM-2a. The range covered is 130MHz to 300MHz and each unit is individually calibrated, the unit also employs a sensitive 50µA meter.

The WM-2a costs £19.95 plus VAT and 85p p&p, other models are available covering 100kHz to 1GHz.

Further details from: *Packer Communications, Bridge End Barn, Soutergate, Kirkby-in-Furness, Cumbria LA17 7TW. Tel: (022 989) 448.*



Bib Record Clamp

The trouble with plastic records is that they are prone to warp, through bad storage or heat. With delicate stylus tracking pressures it is imperative that the record is not allowed to float up and down the centre spindle, thus creating distortion as the stylus is thrown from one side to the other of the microgroove.

The Bib Record Clamp, especially designed to overcome the problem, fits over the centre spindle on single play decks and is locked in position, creating a firm bond between the record and turntable. This helps to flatten the warped record and eliminate vibration. The fitted stroboscopic disc allows determination of r.p.m.

The Bib Record Clamp is generally available through most good Hi-Fi dealers and record shops, priced around £2.50 which includes VAT.

Bib Hi-Fi Accessories Ltd., Kelsey House, Wood Lane End, Hemel Hempstead, Herts HP2 4RQ. Tel: (0442) 61291.

DMM Kits

Lascar Electronics are now also selling their digital l.c.d. multimeters in kit form.

The kits are being made especially as an educational aid, giving an insight into design of digital measuring instruments, the constructor also gains practical experience in working with double-sided p.c.b.s and l.s.i. integrated circuits. Being in kit form the instruments also offer a large cost saving.

Both models feature a 0.5in l.c.d.



readout with "battery low" warning, five functions (a.c./d.c. volts, a.c./d.c. current and resistance) with ability to check diodes.

Inputs are fully protected against overloads and transients, with ability to withstand mains on any range.

The LMM-200 is a hand-held multimeter with a 0.5% basic accuracy, and 15 ranges. The LMM-100 is suitable for field or bench use, has a 0.1% basic accuracy, and 25 ranges. It also features an adjustable and digital hold facility.

The kits are priced as follows: LMM-200 £39.04, LMM-100 £69.80, both prices include VAT and p&p.

Lascar Electronics Ltd., Unit 1, Thomasin Road, Burnt Mills, Basildon, Essex SS13 1LH. Tel: (0268) 727383.

Soldering Station

The new version of the Antex TCSU1 soldering station, meets the latest requirements for precision temperature-controlled soldering. The station is constructed in one of the toughest and most durable moulding materials available.


A significant addition is the anti-static earth connection to protect m.o.s. devices from damage caused by static electricity, this is achieved by inserting the jack with the special earthing cable in the socket at the side of the unit, which makes contact to a specifically made "earth", thus eliminating any static charge.


The station is supplied with either the miniature CTC 40 watt iron or the XTC 50 watt model. Both irons are fitted with 5-core, silicone, burn-free cable with 5-pin DIN socket which connects with the 24V supply from the station. Thermocouples, at the front of the irons, sense the temperature which is kept at a pre-set level between 65°C and 420°C with an accuracy of 2%. A range of three long-lasting bits, heavily coated with iron, is included with each iron for micro, miniature or general soldering work. The bits slide easily on or off the iron's stainless steel shaft.

Temperature control switching is done electronically at zero voltage, avoiding such evils as magnetic fields, arcing transients or spikes. A separate sponge tray is supplied with each station.

Like all Antex products, the TCSU1 is made in England to a British design, and costs (with either of the irons) £38 plus VAT and £1.75 p&p. Separately the irons cost £9.75 plus VAT and 45p p&p.

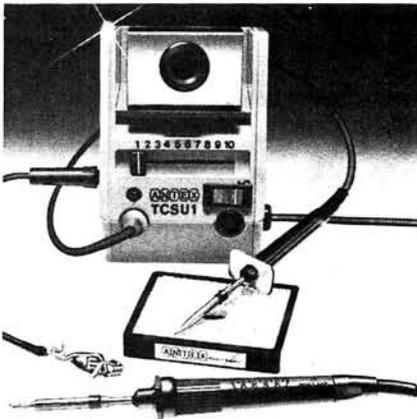Available from many retail outlets throughout the country, or direct from: *Antex, Mayflower House, Plymouth, Devon. Tel: (0752) 67377.*



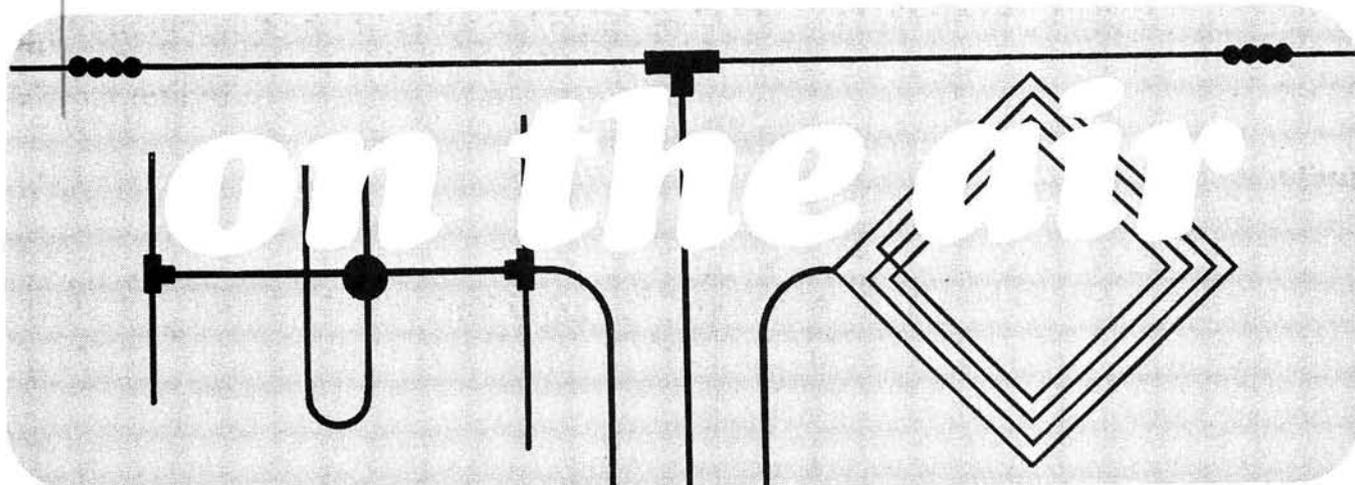

Amateur Bands

by Eric Dowdeswell G4AR

Reports to: Eric Dowdeswell G4AR
Silver Firs, Leatherhead Road,
Ashted, Surrey KT21 2TW.
Logs by bands in alphabetical order.

There is one sure way for the DXer to hear a lot of countries on the h.f. amateur bands in a very short time, and that is to listen to the control station making a "list" of stations wanting to QSO a particularly rare bit of DX who wants to do things the easy way! Readers frequently ask what all this "list" business is about so a brief explanation may help.

DX pile-ups have existed ever since amateurs were interested in working as many different countries or prefixes as possible, usually by calling the DX station on his own frequency, with the strongest signal getting through for a very brief exchange of reports and nothing more. When the big boys have made it, the weaker stations may have a chance, provided conditions haven't changed too much in the meantime. There is a definite technique to be learned in pile-ups if one is to be successful without the aid of high power or expensive aerial systems. Personally speaking, I always enjoy a pile-up but there are many who don't!

The operator at the DX end can handle a pile-up quite expeditiously if at all experienced, but if he happens to be new to the game then all is chaos and he frequently just gives up, which is a pity. The current alternative to the pile-up is for an experienced DXer, generally with a potent, world-wide signal, to take the DX station under his wing and to act as a control station, taking down a list of stations wanting to work the DX station, by inviting them to call in, usually by continents or countries or prefixes. So when control asks: "any G4's?" I just say "G4AR" and if he repeats my call I know I'm on the list!

The eventual length of the list can be quite staggering but when a halt is finally called our controlling hero checks that the DX station is on frequency and asks the first one on the list to exchange reports with the DX fellow, and so on down the list, as called out by the control station. And this is where the first fault in the system raises

its nasty head! For the DX station can hear the call of the next bod on the list, which is half the battle normally in getting through! And if there are problems in exchanging reports there is always someone on frequency prepared to pass on the reports! I have even heard control stations do this in order to keep things moving, making a nonsense of the whole idea.

In fact, it is not unlike the repeater systems on v.h.f. and u.h.f. which increase distances covered on these frequencies but have little intrinsic merit as far as the operator's capabilities are concerned. Of course there are those not on the "list" who can hear the DX quite well and want to work him in the normal way, often not realising that the list system is operating but, rightly or wrongly, they are soon told the error of their ways by control or others on the list. In the meantime the clever DX listener should have been taking down all these calls and picking up some new countries or prefixes or whatever, and all quite legitimately.

Just for fun I recently got on the "list" for H44SH in the Solomon Islands with American AD1S acting as control, but it took another 45 minutes before I was "allowed" to contact H44SH with a 5 and 7 each way. Since the control station now has, in effect, the log of the DX station he can send out suitably printed QSL cards for these contacts as requested, which explains why cards are often forthcoming in a matter of days for a QSO with some distant, lonely DX station. Effective? Yes, but it cannot give the thrill that receiving a card direct from the DX station does, complete with a handsome stamp.

In some cases two control stations are involved in different parts of the world. This helps if one cannot get on to a list because of skip problems, if, for example, a G station is one control on the 20m band. In this case one may have to QSO a VK to get on the list!

With such easy world-wide communication on the amateur bands the mere listener should ask himself if there is still any point in spending time and much money on sending QSL cards to stations who already know they cover the world with their signals. Much better to use these valuable assets in achieving a pass in the Radio Amateurs' Examination so that he can join in the fun and get on to a DXer's list!

Happy People!

Yes, the RAE results from the May exam are coming in and the first of the happy people is **Arthur White** of Aisby, Grantham, Lincs, with credits in both parts as a result of being thumped round the ears regularly by G3ZOA, who

had the additional satisfaction of learning that his XYL has also passed, not only the RAE but the code test as well. So he won't be able to get his hands on his gear for a while! Good luck Arthur and best wishes with the Morse test he has promised to take 'ere long. Oh, yes, Arthur would still like to get hold of a genuine S-meter for his AR88D, so any offers to me please in the first instance.

Now to **Rod Williams** (Brecon, Powys) who also got credits in the RAE and I must quote from his letter: "I thought the RAE was some nasty exam put there by the Home Office boys to stop one getting on the air. I can now see it is there to help one and to make one aware of the responsibilities one has in upholding a licence." Rod worked entirely on his own from books including, dare I say it, *PW's* RAE Reprint, studying an hour every night from February to April in spite of mundane jobs like looking after the children! Rod also quotes the golden rules for taking any exam: "Follow the instructions given, read the question paper thoroughly before starting, re-check all answers in good time even if you haven't finished all the questions." It certainly worked for Rod, and so on to the code test!

Third with the good news is **John Sparks** of Darlington with credits yet again (what is it with these *PW* readers?) who supplemented self-study with a weekly forty mile each way journey to RAE classes at a technical college. Ex-RAF op. John should have no trouble now with the Morse exam, blaming me for his re-entry into the operating field!

Can anybody help **C. F. Perham**, PO Box 2042, Kopeopeo, Whakatane, New Zealand with info on an aerial article in magazine *Old Man* of July 1970 by IIBER? Write to me in the first instance if you wish.

Following my comments in the April *PW* on Beverage aerials, I had a long and interesting letter on their operation from **Max Gill** of Gordon, NSW, Australia, who threatens to write an article on the subject for *PW*. I'm sure he wouldn't mind if I stated the letter for anyone interested.

Now for the DX

Some funny callsigns in the log of **Colin Frankland** of Hull until he pointed out that his typewriter's figure 1's look like his letter l's! So with his Trio 9R59DS, a Codar PR30 preselector and two dipole aerials indoors, it was 8P6CS among many on 14MHz s.s.b. with 21MHz producing 3D6BB, 5N0DOG, HM2JN, VU2USE (US Embassy, New Delhi), TU2HG, JR6RYU on Okinawa and HP1XFN.

With a new long wire of 132ft plus indoor 20m dipole **Basil Woodcock** BRS44266 in Leeds has persuaded his SRX-30 to pick up such as CE1BLL, HH2FH, J6LOU, KC6IN, VP2MO, VP2VAG and VS5DD on 15m, and 5N2KY, 9N1MM, 8P6BO, SU1BA, 6W8GT and 9X5AV for his 20m catch. Using his FRG-7 with a 66ft aerial and a.t.u., **David Coggins** of Knutsford, Cheshire, comments on YB0WR working into Europe on 7MHz in the evenings and the Pacific net with goodies like YJ8NPS, H44JB and P29NRL around 21 150kHz between midday and 1500 with DK9KG exercising some sort of control. Other catches include OJ0MA on Market Reef on 160m, LU3AJW, VK6LK and YB0WR on 40m, FO8FI, VK1WB, VK9ZG, VR6TC (Box 1, Pitcairn Is), 5H3FW, and 5W1BP on Samoa all on 20m, with AH8A on American Samoa, A22VP (Botswana), HM000, H44JB, VE4AFQ/8 (Ellesmere Is), YC1GJ, 3D2CS and 9M2GZ for 15m and, finally on 10m CE1BLL, J6LB/M (mobile on St Lucia!), ZS3N and 5N2DOG.

Paul Barker G4HPS of Sunderland is still the only reader to send in a c.w. log, in his case all worked with his

TS189 transceiver and 18AVT vertical aerial system. Not DX but fairly rare all the same was DJ9GI/HB0 on 10m, plus HK0BKX on San Andres & Providencia Is on 15m for a welcome new one. Chasing US states Paul managed WB7RMI in Wyoming and AI0M in Nebraska but who'd guess that from that call!

From Lee-on-Solent, Hants, **Alec Bell** writes in for the first time with the news that he will be after the RAE in December, in the meantime keeping an eye on things with an FRG-7, a.t.u., trap dipole for 10m to 80m and a 100ft wire. On 20m Alec found HM1HR, HS5DLD, 6Y5HM and 9Y4OV with 15m coming up with CE3OE, JR6BRE, SV0AW and EA8JP. First report also from 13-year-old **Mark Ryder** BRS43580 (Oldham) also with an FRG-7 and wire some 120ft long. He likewise threatens to have a go at the December RAE, in the meantime frequenting the Manchester & District ARS. The all-s.s.b. log reads VO1GK and W1MX on 80m, HI8VBR, KG4KK, 5N0RHK on 40m, C31DV, C5AAA, D4CBC, FB8ZO, J6LOU, VP2VBK and XT2AW on 20m. Nothing of note was found on 10m which has been very patchy of late.

Phil Charlesworth G8SNG kindly keeps me posted as to his activities. Having got his BSc he has decided against going for the jackpot PhD, and to apply for a commission in the RAF, needless to say in electronics and communications. Interesting log entries were OJ0MA on Market Reef, SV6ZA and 4X6AW, all on 80m s.s.b. Phil queries a couple of Y21's which I'm afraid are just East Germany.

Allan Stevens (Crowthorne, Berks) is considering the Datong up-converter feeding into a 10m set-up yet to be built. September's *PW* had a good write-up on this unit. On 15m recently, on what seemed to be a dead band, up popped a number of stations enabling Allan to log all continents in a very short time including a nice one in ZK1AA on Cook Is. Others found on the band included HS1AMM, OH1KB/OH0 on Aaland Is, S79MC, XT2AY, YC1BY and 4S7DJ.

A QSL received here from A4XGR, PO Box 981, Muscat, Oman, says he'd like to renew old acquaintances in G-land after wanderings in the UK area and previous activity as VS6EZ, with A4 as the starting point. Likely frequencies will be 21 150 and 28 490 plus the Sea Net at 1200Z on 14 320kHz. Three IRCs or a 20p postal order will get a QSL by return airmail.

Down in Feoch, Truro, Cornwall, **Bill Rendell** has continued to virtually rebuild his HRO and yet manage to keep it operational. He still likes his preselector in front of it in spite of the two r.f. stages in the set itself. To prove it, Bill made a note of C5ACO, C31MS, OJ0MA, VR6TC and YS9RVE (QSL Box 0543, San Salvador) on 20m s.s.b. and expects me to believe YO0000. He must be joking—should have kept that one for next April! 15m came up with C5ACO, N6HR/KX6, TY9ER (where's that?), VP8SB, VS5DD (QSL Box 1200, BSB, Brunei), 5N0DOG and 8Q7AZ.

Club Time

If you have only just come into contact with amateur radio there is no better way to get to know more about it than by visiting or joining a local club of which there are hundreds scattered around the UK. If there is nothing suitable in the list below then try some recent past issues of *PW*. Failing that contact the RSGB at 35 Doughty Street, London WC1N 2AE, to whom the great majority of these clubs are affiliated.

Crawley ARC. Seems from the club's Newsletter that meetings take place at the Trinity United Reformed Church Hall, Ifield, on Wednesdays, like 22 October when Mike Underhill G3LHZ will be holding forth on a.t.u.s

LOW PRICES ON YAESU!!

Whether you are just starting, taking an R.A.E. course, just licensed, or an old timer, SMC has something for you... And at the lowest ever prices (FRG7000 Saves £76, FT901DM saves £121, FT225RD saves £59 on last list prices).

Advertised prices here include VAT at 15%, include Securicor's speedy delivery and include a two year Warranty (remember as Yaesu Musen UK distributors our guarantee is factory backed). We take Access and Barclaycard over the phone, offer attractive HP quotations (including a FREE FINANCE SCHEME on many regular priced items) on application and have branches and agents conveniently situated across the country plus the biggest mail order department right here in Totton. Remember what is shown here is only a tiny proportion of our stock and our range of accessories, antennas, rotators and masts are second to none.



FT202R
£99

1W, 6 Chanl.
2m. Handheld.

FT207R
£199

3W, 12½KHz
Synthesized
2m.



FT101ZD £569

10-160m. SSB, CW, AM, Digital. Variable IF bandwidth. (Analogue version £488.57!!)



FT225RD £499

2m. SSB, CW, FM, AM, Digital readout. 25+ watts. (Analogue version £449.00)



FT901DM £799

10-160m. SSB, CW, AM, FM, Deluxe Digital. (DE version £713.00. 'D' version £724.50)



FT480R £359

2m. Synthesized. 100, 25, 1KHz steps FM 1KHz, 100, 10Hz, steps SSB, 10W PEP.



FT7B £399

10-80m. 100W PIP. SSB, AM, CW, Mobile 12v Transceiver.



FT707 £500

10-80m. 100W PEP. SSB, AM, CW. Variable IF Bandwidth. Digital (ills + FV707DM).



FRG7 £199

0.5-30MHz General Coverage Receiver. 230V AC. 12V DC, + Battery pack. AM/SSB.

PRICES INCLUDE VAT @ 15%



FRG7000 £299

0.25-30MHz General Coverage Receiver. 230V AC + 12V option. Timer, digital. AM/SSB.

FREE SECURICOR DELIVERY



FT707M £690

160-10m + 2 Aux. SSB, CW, FSK, AM. Memory option. Deluxe all solid state transceiver.

2 YEAR DISTRIBUTOR WARRANTY



SOUTH MIDLANDS COMMUNICATIONS LIMITED

S. M. HOUSE, OSBORNE ROAD, TOTTON, SOUTHAMPTON, SO4 4DN, ENGLAND
Tel: Totton (0703) 867333, Telex: 477351 SMCOMM G, Telegram: "Aerial" Southampton

S.M.C. (Jack Tweedy) LTD

Roger Baines, G3YBO
79 Chatsworth Road,
Chesterfield, Derbyshire
Chesterfield (0246) 34982
9-6: Tuesday-Saturday

NORTHERN (Leeds) BRANCH

Colin Thomas, G3PMS
257 Otley Road,
Leeds 16, Yorkshire.
Leeds (0532) 782326
9-5.30 Monday-Saturday

S.M.C. (Jack Tweedy) LTD

Jack Tweedy, G3ZY
150 Hornecastle Road,
Woodhall Spa, Lincolnshire
Woodhall Spa (0526) 52793
9-5: Tuesday-Sat (+ appointments)



G3ZUL Brian Stourbridge (03843) 5917	GW3TMP Howarth Pontyodkin (035287) 846/324	GM8GEC Jack Edinburgh (031665) 2420
GW4GSW Alan Swansea (0792) 24140	GI3KDR John Bangor (0247) 55162	GI3WVY Mervyn Tandraee (0762) 84056

MAKE A GOOD START (With New Low Prices)

A GOOD START is essential to short wave listening and expert advice is important in achieving this – So here's some – If you've made up your mind to buy a receiver you should be aware it will perform only as well as the antenna it sees. The old adage regarding wire antennas "As long and as high as you can" is still good, but at best is only good for PEAK PERFORMANCE on one or two frequencies, at worst none.

Whichever frequency you tune your receiver to, for PEAK PERFORMANCE on all frequencies you need good matching between your Receiver and Antenna to hear the best from it. If you plan to listen on the high frequency bands up to 30MHz then you know you can't have an antenna for every frequency! Or can you? – Well Not quite! BUT we can offer you MUCH IMPROVED PERFORMANCE from your receiver by using an antenna tuning unit, that will electrically change the length of your antenna to match the frequency you select – In other words – A MATCH AT ALL FREQUENCIES. You'll see many antennas being advertised under gimmicky names, but when it comes down to it they're only random wires or odd configurations. At the end of the day, if you're expecting the performance the manufacturers want you to have, you'll still have to buy an antenna tuning unit.

Tell you what we'll do – we'll prove it to you – we'll give you one ABSOLUTELY FREE when you buy your FRG 7 or FRG 7000 and we'll give you complete advice on an antenna to suit your available space, which should only cost you a couple of pounds!

So let's put the offer in big print for you!

1 YAESU FRG 7 + AMTECH 200 ATU	£199.00
1 YAESU FRG 7000 + AMTECH 300 ATU	£299.00
VAT included	

What's the difference between the Amtech 200 and Amtech 300? Well both will tune any random length of wire but the Amtech 300 will do a little extra – it will also match co-axial fed antennas – Their normal selling price, The Amtech 300 £39.95 – The Amtech 200 £25.95 – What can you lose?

So get cracking MAKE A GOOD START! HAVE PEAK PERFORMANCE FROM THE OFF.

JAYBEAM – HYGAIN – BANTEX – AMTECH – CUSHCRAFT – SWAN – ATLAS
and 50 other major lines – all ex stock.




AMCOMM SERVICES

194A NORTHOLT ROAD, SOUTH HARROW, MIDDX. Tels: 01-864 1166 & 01-422 9585

OPENING HOURS: Tues-Sat 9.00-5.30 Sunday by appointment.



So You Want to Pass the RAE?

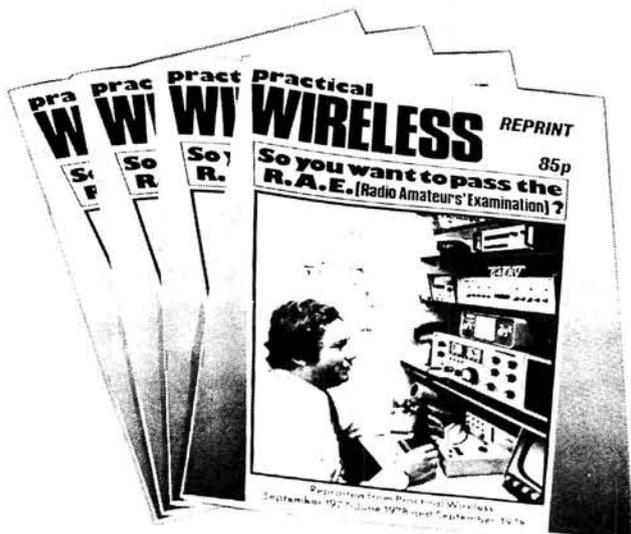

A reprint of the complete series, including details of the new examination format introduced in 1979, is now available. The reprint costs 85p, including postage and packing to addresses within the United Kingdom.

Order your copy by completing and returning the coupon, together with your remittance, to IPC Magazines Ltd., Post Sales Department, Lavington House, 25 Lavington Street, London SE1 0PF. Please ensure that your name and address are clearly legible.

PRACTICAL WIRELESS—Radio Amateur Examination Reprint

Please send your order and remittance to:

**IPC Magazines Ltd., Post Sales Department,
Lavington House, 25 Lavington Street,
London SE1 0PF**

Please send me . . . copies at 85p each to include postage and packing

I enclose P.O./Cheque No. Value

Remittance must be crossed postal order or cheque (name and address on back please) and made payable to IPC MAGAZINES LTD

NAME
(BLOCK LETTERS)

ADDRESS
(BLOCK LETTERS)

.....
.....
.....

..... Post Code

Remittances with overseas orders must be sufficient to cover despatch by sea or air mail as required. Payable by International Money Order only

Company registered in England. Regd. No. 53626

A subsidiary of Reed International Limited

— Cut round dotted line —

and aerals, with all standing to attention when RSGB Regional Rep G3MDO and Area Rep G3JMB visit on November 26. CARC celebrated its 21st in September having been started by old friend Ron Vaughan G3FRV, now VK6RV, in 1959. Club competition seeks new name for Newsletter which it seems has been "temporary" for 21 years.

St Neots & District ARS. Newly-formed, welcomes new faces at The Ernulf Community School, Barford Road, Eynesbury, St Neots, Cambs, at 7.30pm Mondays, but contact Sec Paul Herod G8TQI, 49 Luke Road, Eynesbury, St Neots, Cambs, for meeting details or try Huntingdon 74642.

West Kent ARS. The Adult Education Centre, Monson Road, Tunbridge Wells, sees Ambit International talking about choosing the right component on October 10 with G5XB holding sway on the Hellschreiber on the 24th. G3ROO is on the ball with advice on how to get on to the new bands without buying a new rig, on November 7. But Brian Castle G4DYF can tell you more on Sevenoaks 56708.

Bolsover ARS. Wednesdays 8pm, Angel Hotel, Bolsover, with RAE classes already going great guns. Being formed recently, the club particularly welcomes new members whether licensed or newly interested in the hobby. Contact: Allan Turford G8HPQ, 103 Hilltop, Bolsover, near Chesterfield, Derbys S44 6NJ or on Chesterfield 824972.

Bournemouth RS. First and third Fridays at the Dolphin Hotel, Holdenhurst Road, Bournemouth with October 3 being AGM night, or talk with G. R. Freeth G4GQH, 9 South Avenue, New Milton, Hants on New Milton 618092.

Wirral ARS. First and third Wednesdays at 7.45pm at the Sports Centre, Grange Road West, Birkenhead with AGM on 15 October, so go along and see what makes a club tick. Recent interesting Newsletter holds inquest on this year's HF NFD which is always a good way to ensure a better effort next year.

Exeter ARS. Has club stations G4ARE and GB3EX for use by licensed members with code lessons for those wishing to go from B to A! Advance notice of meeting on November 3 when Any Questions will be conducted by an electronics lecturer from Exeter College, and November 10 when surplus gear will be flogged off! Incidentally November 3 will also be the occasion for a discussion on the RAE syllabus with a view to the December exam. Try G. W. Draper BRS44198 at 1 Carlyon Close, Heavitree, Exeter EX1 3AZ or Exeter 37170.

Durham University Radio & Electronics Society at Grey College, Durham, will be organising two special event stations, hopefully GB2DUC and GB8DUC, in connection with the Charities Week in that fair city at the beginning of November with all-band operation promised. Informant Ian Jefferson G4IXT even threatens to get on the key. Write to him at the College for more details.

Mexborough & District ARS. Friday night is meeting night at the Dolcliff Hall, in the road of that name, Mexborough at 7 pip emma (early Roman phonetic code!) with a station on the air, code classes, junk sales and lectures, but not all together! Ian Abel G3ZHI of 9 Grove Terrace, Maltby, Rotherham, Yorks can tell you more or chat on 0709814911 (that's what he wrote! Looks more like my electricity account number).

Derby & District ARS. Chairman Dick Buckby G3VGW expresses pleasant surprise at the amount of amateur radio matter in *PW* these days, which ought to lead to more people getting along to the club on Wednesdays at 7.30pm at 119 Green Lane, Derby, in fact the top floor of the Oddfellows Hall; "Very appropriate!" Dick's words, not mine! Tea, coffee and snacks available! First

Wednesday each month is junk sale night on top of which there are code classes on Tuesdays and Wednesdays at the same spot. They must be churning out G4 + 3's like a sausage machine! But more on that from Jenny Shardlow G4EYM, 19 Portreath Drive, Darley Abbey, Derby DE3 2BJ, or if you dare risk the wrath of the OM then its 0332 556875.

Bedford & District RC. Winnie The Pooh conceals the identity of the club station G3WTP located three miles north of Bedford, near the car park, near the barn, near the Ravensden Church. Sorry no QTH, just a map! By a valiant effort Dave Whitty G4FEV has resurrected the club magazine, last heard of in 1970, and a good one it is too with several short but interesting projects, with clear drawings and diagrams, so often the weak point of such newsletters. Dave will be glad to tell you more about the club and its activities if you drop him a line to 16 Fairmead Crescent, Rushden, Northants NN10 9NB or call him on Rushden 56768.

Edgware & District RS. Second and fourth Thursdays at 8pm, Watling Community Centre, 145 Orange Hill Road, Burnt Oak, Edgware with other evenings being filled in by G3ASR and his RSGB slow Morse transmissions on Mondays and first and third Thursdays on Top Band and 2m. If that is not enough there are code classes before each meeting. Vintage Radio is theme of G3IEE on October 9 and November 13 should see G3BNL expounding on microwaves. In the meantime why not tackle PRO Howard Drury G4HMD, 39 Wemborough Road, Stanmore which is also 01-952 6462.

A note to all clubs. Why not help the **Radio Amateur Invalid & Blind Club** by joining as a supporter? Syphoning off a few per cent from those junk sales and dinner/dances could help to get someone on the air or provide a receiver for a new and enthusiastic member. Work can always be found for a willing pair of hands in the many tasks that arise in assisting members. Drop a line to Frances Woolley G3LWY, 9 Rannoch Court, Adelaide Road, Surbiton, Surrey KT6 4TE. She is secretary of the RAIBC.

Medium Wave
Broadcast
Band DX
by Charles Molloy G8BUS
Reports to: Charles Molloy G8BUS
132 Segars Lane, Southport PR8 3JG.

The medium-wave band is allocated to short-range domestic broadcasting. Propagation is by means of the ground wave which, as the name suggests, travels close to the earth's surface where it is attenuated rapidly. There is some radiation skywards from the transmitting mast, though efforts are made to minimise it. Absorption takes place in the D layer of the ionosphere during the day and nothing returns to ground. After dark the D layer disap-

pears and the radio waves reach higher layers where they are refracted, mainly by the E layer, and returned to earth some considerable distance from the transmitter, well outside the ground-wave service area. This is the reason why many more stations are to be heard at night than during the day and it is also the phenomenon that makes medium-wave DXing possible. Rule number one for the m.w. DXer: Reception can only take place when there is a path of darkness between transmitter and receiver. No use looking for DX in the middle of the day as you won't find any.

North American DX

Readers express surprise when they learn that North American medium-wave stations can be heard in the UK, yet this type of reception is as old as broadcasting itself. In the 1920s, veterans such as WGY in Schenectady were heard regularly with the simple equipment in use at the time. Nowadays, the band is full of Europeans at night, but many do close down around 2300 and since the north Atlantic path will be in darkness this is the time to hunt for DX.

Locate Brussels on 927kHz. The language is French and the station goes off the air between 2250 and 2315. Once the tuning notes are finished and the carrier goes off, tune up-frequency slightly to 930kHz where, if conditions are favourable, you ought to pick up CJYQ which is a 50kW broadcaster at St John's in Newfoundland. Identification is easy since the callsign (CJYQ) or its contraction (Q Radio) is used repeatedly and time checks will reveal a Time Zone 3½ hours behind our own.

Do not be disappointed if you fail to hear CJYQ at the first attempt. Conditions vary a lot and the signal may be strong one night and absent for the following few nights. Be prepared too for the slow cyclic fading that is typical of a m.w. DX signal. Over a couple of minutes it may go from strong to inaudible and then come slowly back. Stay on the channel for a few minutes in case there is a fade.

If you do hear CJYQ then try for two other Newfoundlanders; CKVO in Clarendville on 710kHz and CBGY in Bonavista Bay on 750. Look for WHDH in Boston on 850 and for two stations in New York City; WNEW on 1130 and WQXR on 1560.

Beverage Antennas

From Galway in the west of Ireland comes a request for help from reader **Neil Sharkey** who is having difficulty picking up the BBC, particularly Radio 3 on 1215kHz. There are quite a few areas over here where reception is far from good! Neil has tried a simple dipole without much success and he wonders if there is some sort of beam antenna that he could construct that would improve reception on 1215.

The mind boggles at the thought of a multi-element beam for use on 247 metres but what is really required is a Beverage which is a very long, long wire, at least two wavelengths in length. It runs from the receiver in the direction of the transmitter and is joined to earth at the remote end by a 600 ohm resistor.

This aerial is directional along the length of the wire away from the receiver. It gives a substantial increase in signal strength as well as an improvement to signal-to-noise ratio, and the wire need only be fixed a few feet above ground level. I have heard recordings of low-power North Americans made in New Zealand with a domestic radio connected to a mile-long Beverage and the results were quite staggering. Unfortunately the Beverage is not the antenna for the city dweller, nor even for those who live in the country, but where space is available this is the ultimate aerial for m.w. DXing.

5000 WATTS	1140 KCS
RADIO STATION C B I	
SYDNEY, N. S., CANADA	
OWNED AND OPERATED BY CANADIAN BROADCASTING CORP.	
Thank you for your report on our program, your times and details check with our log and we are pleased to verify your reception of C B I.	
Yours truly,	
Canadian Broadcasting Corporation	
Per <i>Stephen W. Tyson</i> Tech. Supervisor	

A QSL Card confirming transatlantic reception by the author some years ago

Semiconductors

"I have a valve-operated Q Multiplier which has its own power supplies. Can this be used with a transistorised receiver or are the voltages too high?" is the question posed by reader **Vernon Graham** who lives at St Pieters-Leeuw in Belgium.

Personally, I would not risk it. On the face of it there is no reason why the two cannot be connected together, since a commercially-made Q Multiplier will certainly have its internal voltages isolated from the "output", but — there is always the risk of a short-duration high-voltage spike appearing and if it finds its way into a transistorised receiver it will certainly destroy any semiconductors in its path.

Talking of semiconductors. Some time ago I came across the expression "half conductor" in a translation made by someone without a technical background.

DX Circle

This is the name of a programme in English that can be heard at 1900 every Tuesday over the 600kW West German Deutschlandfunk on 1269kHz. It is written and presented by DXer **Alan Thompson** who says: "The programme has evolved into a five-minute chat-show about things to do with radio." It has been on the air now for some ten years to my knowledge.

Alan has recently acquired an Eddystone 770R v.h.f. communications receiver. He has a copy of the manual but he wonders if any *PW* reader could explain the



"This new Z-match I've got is great—the s.w.r. is better than 1 to 1!"

... heard by G3RZP

"I'm not surprised there was no modulation, I never said anything."

... Brighton & District RS Newsletter

Western

Western FOR GENERAL COVERAGE RECEIVERS

Western FOR HF TRANSCEIVERS

Western FOR VHF/UHF TRANSCEIVERS



We are direct importers of **YAESU** and **TRIO**

We also stock equipment from **ICOM** and **FDK**

Send SAE for details and prices



Western CAN ALSO FIX YOU UP WITH . . .

ROTATORS

from the well-known **EMOTO** range – now with 360° DIAL PRESENTATION! (Models 103 and 502 only)

EMOTO 103SAX (NEW!) For light HF and large VHF arrays	£86.25
EMOTO 502SAX For heavier beams plus VHF/UHF	£125.35
EMOTO 1102MXX The really big one for the largest HF monobanders and big VHF/UHF arrays	£189.75
EMOTO 1103MXX As the 1102MXX but slower rotation speed and greater turning power	£194.35
EMOTO MB-300 The well-known rotary mast bearing	£13.80
COMMANDER EP-200 A budget-priced, lightweight but robust rotor for VHF/UHF arrays	only £29.95

UNBEATABLE VALUE FOR MONEY

POWER/SWR METERS

Western PEAK READING WATTMETERS
(Patent Protected)

PM-2000 Reads peak or RMS RF power from 3.5 to 30MHz. Patent peak-reading facility for direct reading of SSB, PEP during normal transmission. Impedance 50 ohms, power ranges up to 2kW	£51.75
PM-2001 Similar to PM-2000 (above) but covers VHF from 50 to 150MHz and has power ranges up to 200W	£51.75
OSKER SWR-200 An established favourite, this power/SWR meter has a place in many shacks. Power measurement up to 2kW (RMS only) with 15% accuracy; dual impedance 50/75 ohms, frequency range 3.5 to 150MHz. Now reduced in Price to	£39.00

STATION ACCESSORIES

DUMMY LOADS— W1 type. MDL1000. Extruded finned, heat-sink housing, oil-filled load resistor, 52 ohms, 1kW for 3 mins, or 300W continuous. A high quality load at a good price. (Similar to Trio RD-300 – but not in price!)	£29.95
WESTERN DL-1000 can-type, 250 watts	£14.15
MORSE KEYS SRK-1 High quality "straight" key as made for the professional users and now available to the amateur	£12.65
VIBROPLEX "Original" Standard "bug" key	£39.65
"Champion" "bug" key – the economy version	£37.35
NEW "Iambic" twin paddle for el-bugs	£39.65
"Vibrokeyer" single paddle for el-bugs	£39.65
Valves – 6146B, 6JS6C, 6KD6, 12BY7A and Others, SAE for prices. Also Baluns, Traps, Plugs, Cable, Etc. Etc.	

HF MOBILE ANTENNAS

NOW IN STOCK AGAIN – the best HF mobile antenna system there is for 10 to 80 metres.



Choose from: BM-1 bumper mount	£11.44
or C-32 ball mount	£4.95
Then add: MO-2 fold-over mast (54in long)	£13.63
Then choose your resonators: RM-10 for 10 metres	£6.50
RM-15 for 15 metres	£6.56
RM-20 for 20 metres	£8.17
RM-40 for 40 metres	£10.06
RM-80 for 80 metres	£11.44
Accessories (optional): RSS-2 resonator spring	£4.08
QD-1 quick disconnect	£10.06
Add carriage £2.30 (Antenna) or 60p (accessories)	

THE VERY BEST FOR HF MOBILE

HF ANTENNAS

Designed and manufactured in UK by **Western**

Terrific Value! Terrific Performance!

WESTERN DX-5V 5-band vertical, 10–80m	£89.00
WESTERN DX-31 Rotary dipole, 10/15/20m	£46.00
WESTERN DX-32 2-ele beam, 10/15/20m	£80.50
WESTERN DX-33 3-ele beam, 10/15/20m	£121.90
WESTERN DX-34 4-ele beam, 10/15/20m	£161.00

Also available: CONVERSION KITS to upgrade DX-31 to 32 etc.

TRAP DIPOLES ALSO AVAILABLE

VHF/UHF ANTENNAS

BY **PANORAMA**

"Modular" Series of VHF/UHF and 10m mobile antennas. Choose which and base combinations below: AV/C58M/145 2m $\frac{1}{2}$ whip and coil	£7.25
ACU/433 70cm. Gain colinear	£6.21
AC10 Centre loaded 10/11m whip	£6.84
NEW! BB Miniature ball-joint base with 4m coax	£5.75
MB Boot-lip base (no hole) with 4m coax	£5.29
MM Magnetic mount with 4m coax	£15.18
M4 Standard base, $\frac{1}{2}$ in hole fixing	£3.28
NEW! MLW Window clip base (needs counterpoise)	£6.15
PVX Counterpoise for MLW (2 metres)	£4.72
FXU Counterpoise for MLW (70 centimetres)	£5.06

Carriage – add **£1.75** for up to 5 whips/bases

ALL PRICES INCLUDE 15% VAT

Western Electronics (UK) Ltd

HEAD OFFICE (All Mail/Enquiries)

FAIRFIELD ESTATE

LOUTH, LINGS LN11 0JH

Tel: Louth (0507) 604955

Telex: 56121 WEST G

Our Agents

Southern: Alan Paxton, G4BIZ, Southampton, Hants

(0703) 582182

Scotland: Jim Henderson, GM4HKW, Falkirk (0324) 25559

N. Ireland: Les Lyske, G13CDF, Newtownards (0247) 812449

Opening hours:

LOUTH: 9-12; 1-5pm Mon-Fri. By appointment Sat. 9-12.

LEICESTER: may's Hi-Fi, Churchgate (Tel: 0533 58662).

Mon-Sat. 9-6pm; closed Thurs.



THE RECEIVER FOR LF, MF & HF



★ SALES ★ SERVICE ★



RADIO SHACK LTD. 188 BROADHURST GARDENS, LONDON NW6 3AY



Giro Account No. 5887151 Telephone: 01-624 7174 Cables: Radio Shack, NW6.
Telex: 23718

significance of the S/77R/8 and the two 12-pin sockets fitted to the back panel. Replies direct to Alan please at 16 Ena Avenue, Neath, West Glamorgan SA11 3AD.

Eddystone

Reader **Tony Jover** has drawn my attention to the Eddystone EB35 Mark 3 "Statesman", which does not have an internal aerial for use on the medium wave and can be used with a m.w. loop. My own second receiver, the EB36, is a variant of the original EB35 and I have found it to be remarkably free from overloading on the medium waves, even when used with a 60ft long wire. The EB35 is similar in appearance to the well-known EC10, and details of the EB35 and others in the range are obtainable from the Eddystone main agents who are Sonic Sound Audio of Tottenham Court Road in London.

Saudi Arabia

An up-to-date picture of the high power m.w. transmitters in Saudi Arabia comes from G4BHH. There are two sites, one at Qurayat (Q) and the other at Dhuba (D). Daytime means 0300 to 1600 and night-time means 0300-0500 and 1400-2300, all in GMT.

549kHz (Q) 2MW into a 6-element beam. Daytime.

594kHz (D) 2MW into a 6-element beam. Daytime.

900kHz (Q) 1MW into a 3-element beam. Night-time.

1521kHz (D) 2MW into a 6-element beam. Night-time.

The beam elements consist of 30ft triangular-section masts one quarter wavelength high and those at Qurayat (Q) are on a great circle heading that extends towards the UK. If you have not yet logged Saudi Arabia, try one of the above frequencies.

Short Wave Broadcast Bands

by Charles Molloy G8BUS

Reports: as for medium wave DX,
but please keep separate.

"I have difficulty in finding and tuning into stations on the short-wave bands," writes **T. Ernest Hall**, who is referring to his attempts to pick up the BBC World Service while travelling in France and Spain.

This is not an unusual problem when tuning round the short waves on a general-coverage receiver. It occurs because a short-wave tuning scale displays a much larger portion of the frequency spectrum than a medium- or long-wave scale. A receiver tuning from 6MHz to 22MHz covers 16 times the frequency range of the medium waves and inevitably stations are 16 times closer together. What can be done about it?

Bandsread

Bandsread is one solution. The receiver has two scales; a main scale and a bandsread scale. The pointer on the main scale is set to a spot or mark for bandsreading and stations are then tuned in on the bandsread scale where they are spread out more and are easier to tune in and locate. This arrangement is used on some communications receivers but seldom on domestic-type sets.

Another remedy is to have a separate scale for each short-wave broadcast band, so that stations are spread out like they are on the medium and long waves. The Grundig Satellit and similar receivers use this method, but it means a large number of scales and associated circuitry and consequent expense. The snag with this method is that you cannot tune to out-of-band stations, but this should not bother the s.w.l. too much though it could be a disadvantage to the DXer.

My Vega 204 works partly on this principle. It has only a single pointer which travels over eight separate scales, one each for the 13m, 16m and 19m bands, one covering 9.3MHz to 12.1MHz which includes the 25m and 31m bands, one covering 5MHz to 7.5MHz to include 41m and 49m and another tuning over 3MHz to 5MHz to cover the tropical bands. The remaining scales are for the medium and long waves.

Digital Readout

The best and most recent solution to the station location problem is digital readout. The frequency in kHz (MHz \times 1000) is shown on a digital clock-type display, and provided the receiver has a reasonable slow-motion drive

then you can hardly go wrong. Rotate the tuning control until the frequency you want appears on the display. At the moment, digital display is only available on the more expensive receivers but it cannot be long until every set is equipped with this ultimate aid to easy tuning.

Aerial Tuning Units

"Can I use an aerial tuning unit (a.t.u.) with a receiver that has an aerial trimmer control?" asks **Thomas Glennon** of Cork. The function of the aerial trimmer is to compensate for any loading that the aerial may place on the receiver. The a.t.u. will minimise aerial loading by matching the aerial to the receiver and consequently the aerial trimmer will then have little effect. Of the two, I much prefer the a.t.u. and it is worthwhile using one with a receiver that has an aerial trimmer as such a set-up may occasionally give a boost to a weak signal.

It is always a good idea to experiment with different aerials along with an a.t.u., rather than speculate what might happen. You will not damage a receiver by joining an a.t.u. between the aerial and aerial socket. At worst it will make no difference; at best it will give a valuable boost to a weak signal. Details of how to make an a.t.u. appeared in the Aerial Data Chart contained in the November 1979 edition of *Practical Wireless*, but they are available from advertisers in *PW* and other magazines.

Volmet

My comments about Volmet in the April issue brought an interesting reply from **K. Todd** of Kaiapoi in New Zealand who enclosed an article on the subject from an

... TO COMPLETE THE RANGE OF VHF & UHF



UK IMPORTERS
& DISTRIBUTORS

stamps for details.



RADIO SHACK LTD. 188 BROADHURST GARDENS,
LONDON NW6 3AY

Giro Account No. 5887151 Telephone: 01-624 7174 Cables: Radio Shack, NW6.

Telex: 23718



U.A.E. DUBAI RADIO AND COLOUR TELEVISION
RECEPTION REPORT CONFIRMATION

FREQUENCY 17,775 KHz test
DATE 28/6/80
TIME 0730 GMT

WE HAVE PLEASURE IN CONFIRMING
YOUR RECEPTION REPORT.

Handwritten signature
CHIEF ENGINEER
DUBAI RADIO & COLOUR
TELEVISION

P. O. Box 1695
DUBAI,
UNITED ARAB EMIRATES
TEL. : 470255
TLX : 5605 BRCAST DB

W. Higgins,
15, Russell Avenue
Southcourt, Aylesbury
Bucks HP21 8NE
U.K.

A QSL Card confirming reception of a test transmission from Dubai Radio by reader W. Higgins of Aylesbury

American magazine. A lot of confusion exists among DXers as a result of differences between the law in the USA and this country. In the UK it is illegal to even listen to anything other than broadcasting stations or amateurs, unless you have a licence and this is not normally issued to private individuals. As a result, information about point-to-point, Volmet, etc., cannot be included in this column. Very sorry but that is the position. Utility DXing is illegal in the UK!

Readers' Letters

"I heard the BBC World Service on approximately 20460kHz in s.s.b.," says **G. R. Ellis** from Aylesbury, who wonders if he was listening to some sort of freak transmission. You were probably listening to a feeder, which is a transmission to an overseas location for re-broadcasting. It is not intended for direct reception by the public as it merely replaces the usual landline between the studio and transmitter.

"Have fixed the old Rx up again and find things to be quite interesting s.w.l.-wise anyway," says **N. C. Dove** of Lockerbie in Scotland, who first started DXing in 1937. His receiver is a home-made ten valver which covers 3.2MHz to 22MHz in nine switched bands. The station you heard on the 31m band was probably FEBA, the Far East Broadcasting Association which transmits religious programmes from the Seychelles. Listen for Pakistan during the afternoons on the 13m band (21755kHz and 21486kHz) and the 16m band (17910kHz) and during the evening on 21485kHz and 17760kHz.

DX Heard

A test transmission from Dubai was picked up on 17775kHz at 0730 by **W. Higgins** of Aylesbury, who was using his FRG-7 with Joystick System A plus Cambridge notch filter and home-brew noise limiter. A reception report brought a QSL card in less than three weeks.

Reykjavik Radio is reported on approximately 13910kHz from 2210 until past 2330 on 29 June SIO 454 by **David Wyatt** (Oswestry) using an AR88LF and loft aerial. Although not listed on the short waves, Icelandic Radio does use one of the Post Office transmitters on a part-time basis for broadcasting to fishermen.

Trans World Radio Guam is reported by **Alan Scholefield** of South Shields, who picked it up on 15365kHz between 1430 and 1459 where it is on the air

on Fridays at the time of writing. Reception reports to TWR, PO Box 66, Agana, Guam 96910, USA.

While trying to pick up Radio Australia on 9570kHz in the 31m band with his Marconi Atalanta, **George E. Lee** of Ossett picked up Port Moresby in Papua New Guinea instead. This station transmits on 9520kHz and 9570kHz with a power of 10kW and George wonders if any other *PW* reader has heard this rather rare DX.

VHF Bands

by Ron Ham BRS15744

Reports to: Ron Ham BRS15744
Faraday, Greyfriars, Storrington,
Sussex RH20 4HE.

Very often when reading your letters, I sense the pioneering spirit and the excitement, which I share, when you report that bit of super DX. With that same enthusiasm, the true spirit of amateur radio prevailed during the weekend of August 9 and 10 when many of my Sussex readers, equipped with their 2m gear, played their part with Raynet and joined the hunt on the South Downs for a missing child, which, thanks to all concerned, had a happy ending.

Solar

Both **Cmdr Henry Hatfield**, Sevenoaks, and **Ted Waring**, Bristol, were prevented by the recent bad weather from using their optical equipment as much as they would like. However, Ted managed to see the sun and count 86 sunspots on July 21, 8 on August 1 and 5, and 40 on the 11th and Henry, using his spectroheliograph on the 9th, saw some activity developing on the eastern solar limb which may well have been responsible for the sudden large burst of radio noise (Fig. 1) which was recorded by **Reg Taylor**, Shillington, Henry and myself, at 151MHz, 136MHz and 143MHz respectively, at 1250 on the 14th. Large individual bursts of noise were also recorded on July 21, 27, 30 and August 12.


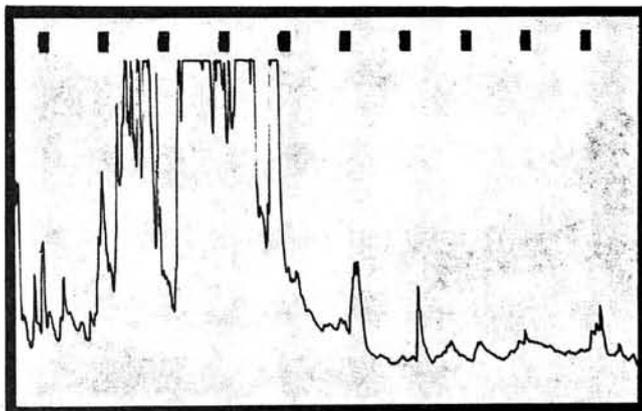


Fig. 1: The author's recording of the burst of radio noise which occurred at 1250 on August 14

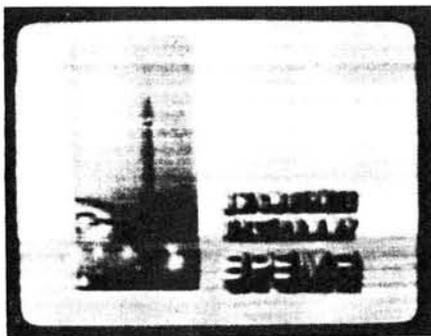

Three of the pictures received from Russian Television by the author on July 23

Perseids Meteor Shower

"Meteor scatter has been excellent since August 3, usually from 0800 to 1200 with long pings showing video for up to a minute at a time," writes **John Branegan** GM4IHJ, Saline, Fife. On the 9th and during the evening of the 11th, near the peak of the Perseids, **Mike Hearsey** G8ATK, Farnham, heard brief pings of signals on 2m from amateur stations in F, LA, OE, OK, OY, OZ, SP and YU. It is well worth observing again when the earth passes through the Leonid meteor shower between November 15 and 19, with a predicted peak on the 17th.

The 10 Metre Band

Throughout the period July 21 to August 19, signals from the International Beacon Project stations were relatively sparse, except during sporadic-E events when signals from the two German beacons, DK0TE and DL0IGI and the Norwegian beacon LA5TEN, were prominent and often peaking 599. Under normal conditions both Ted Waring and I periodically heard signals from the beacons in Cyprus 5B4CY, and occasionally the two in South Africa, ZS6DN and ZS6PW. **George Grzebieniak** RS41733, London, commented about the short skip conditions on July 26 when he heard s.s.b. signals from stations in EA, IS and ZS.

Sporadic-E

Strong signals from east-European f.m. broadcast stations were received between 65MHz and 73MHz during sporadic-E disturbances around 0800 on July 24 and August 4 and 12, at midday on July 22 and August 5, and around 1800 on August 10 and 11. The most intense of these events was on the 11th, when I counted 30 such stations with only a dipole feeding my R216 receiver. **George Grzebieniak** also heard music around 71MHz on August 5, and during the sporadic-E season users of the 4m amateur band and the "low band" commercial frequencies are often pestered by the strength of these signals. At 1809 on the 10th, the disturbance briefly extended its influence into the 2m band and **Mike Hearsey** nearly completed a QSO with IS0DSQ/P and heard IS0DKU/P.

Tropospheric

The good conditions on 2m during the week July 21 to 27 enabled **John Cooper** G8NGO, Cowfold, Sussex, to work 9 Fs (one of these, F6GQE/P, on the Spanish border was only using 3 watts), 2 ONs and 5 PAs on the 21st, a DD, 25 Fs and 2 ONs on the 22nd, and an F, 2 ONs and

5 PAs on the 23rd. On the 24th, he heard signals from the 2m beacon in Angus, GB3ANG and worked 8 Fs, a GM and a PA. The signals from the Angus beacon proved to **John** that the opening was changing direction, because on the 26th he worked 2 EIs and a GJ and he finished in style on the 27th by working 2 EAs, 24 Fs, a GJ and a GU.

During that week, **George Grzebieniak** heard 2m signals from Belgium, France, Holland and both northern and southern Ireland. **Mike Hearsey** also worked many French stations and several near the Spanish border during that period, and on August 9 **Mike** worked 25 stations in the south-east of France, 2 EAs, and C31RN in Andorra. On the 10th **Mike** heard C31VF in QSO with French and Spanish stations but could not get in. To date, while **Mike** has worked 106 QRA squares on 2m and has only 3 French squares left to work, **John Cooper** has confirmed 40 squares and 10 countries toward his RSGB award.

Like the others on July 22 and 28, **John Cleaton** G4GHA, Wareham, worked many French stations on 2m, one (F1FJJ) on the French-Swiss border and another (F1DSQ) on the Spanish border. During the evening of August 9, **John** heard several EAs but although audible, they were not workable from his QTH. He also heard several contacts between EA and GW.

During the brief spell of good conditions on August 19, **Alan Baker** G4GNX, Newhaven heard strong signals from a couple of GW mobiles in QSO on 2m f.m. simplex. Signals from the Cambridge repeater GB3PI, R6, were so strong, said **Alan**: "That they were overpowering the, almost local, Crawley repeater GB3BP. Strong signals were also heard in Sussex from the Leicester repeater GB3CF, R0.

DXTV

At 0721 on July 23, I watched a cartoon film on Channel R1, 49.75MHz, and at 1723 the prevailing sporadic-E disturbance produced a mixture of pictures on E2, 48.25MHz and R1 where pictures of Olympic swimming were fighting for predominance. Both **Harold Brodribb**, St Leonards-on-Sea, Sussex, and I saw the Olympic swimming on R1 and R2, 59.25MHz, and at 1800 a clock showing 2100, three hours ahead of GMT, appeared suggesting that the signals were coming from the Moscow area. This clock was followed by Russian news on both R1 and R2.

Around 0700 on the 24th I received a strong test card from MTU, Budapest, and a clock showing 0900, two hours ahead of GMT, followed by a YL announcer. **Harold** told me that at 1110 on the 22nd he received a brief test card from TV1—Sverige and at 1345 a news bulletin from Spain on E2. At 1400, R1 was carrying the

large letters "POLSKA 80" and 10 minutes later, on E2, he saw a Spanish picture with a road sign "Barcelona", and later an advert showing a detergent, "Luzil", going into a washing machine and another about the fruit juice, "Fruco". While using his RL85 communications receiver to tune through Band I, Harold heard Spanish sound on E2, 53.75MHz relaying the Olympics with Spanish commentary overlaying the Russian announcements from the Moscow stadium.

David Appleyard, Uppsala, Sweden, was using his equipment during the sporadic-E disturbance between 1000 and 1400 on August 5 and writes: "It started with a brilliant test card from Budapest on R2. The same picture was visible on R1 at half strength, with bursts of Grünten on E2. By 1050 the +PTT-SRG1 test card plus classical music had appeared on E2 and was also coming in on E3 next to the strong Budapest signal on R2." Around 1400 both Harold Brodribb and I watched a mixture of pictures on R1, with the Russian stations becoming predominant as Harold said in his letter: "At times male announcers were seen with brief captions of their names in Russian letters."

Another of our keen TV DXers is **T. Amp**, London, who tells me that he has, and I think wisely, invested in good equipment for his interests. For Band II reception he uses a National Panasonic DR49, and he has a Nordmende Colorsonic 2400, SK3 series, for television. "The beauty of this set," writes T. Amp, "is that it picks up very weak signals and it has scanning facilities up to 99 channels (including satellite reception) which helps a lot for DXing. Secondly it has memories from 24 channels so if I find a weak signal I put it in the memory and then, at least for a week or two, I try it often." In addition to his three Fuba aerials, one for each band, he has pre-amplifiers installed as required and a JVC 3660EK video recorder from which he gets very good replay results.

During the 1980 sporadic-E season he has received most European test cards on v.h.f., and since February has seen u.h.f TV signals from Belgium, Germany and Holland.

At 1736 on August 11 I watched part of a film about the Olympic opening ceremony on R1 with the bear "Mischa" very much to the fore. Around 1700 on the 18th, I received a strong test card on E2, made up of small graduated squares, mixing with a test card from RTP, Portugal and a caption from Spain which was headed, RTVE Control Central. Just as the disturbance was fading away I saw the RTP clock followed by a YL announcer.

Electronic Mail Order Ltd. sent me their gen sheet on the pre-amplifiers which they supply for Bands I, II and V, designed with the f.m. and TV DXer in mind. Details available from the firm's office at 62 Bridge Street, Ramsbottom, Bury, Lancs.

"All my receiving equipment has been working overtime during the past few weeks," writes **Andrew Rogers**, Bristol, on August 14. "I had a small party at my house and one of my friends turned on the TV. Wondering what the small stickers on the push-buttons meant, he shunned BBC1 and ITV and pressed R1. I had left the upconverter plugged in and to his surprise, he was greeted with the caption "TB CCCP!" Reception continued all evening and quite spoilt the party." I like that story Andrew, I bet your friends are now envious of you and your TV gear. On July 21 Andrew received TVE all evening on E2 and TV CCCP on R1, test card from RAI, Italy on 1A, 53.75MHz, during the afternoon of the 22nd and again between 0950 and 1100 on the 23rd. An extract from Andrew's log for August shows that he received pictures from Italy and Spain on the 7th and 11th and CST, Czechoslovakia and TVP, Poland, on the 11th.

News Items

David Thorpe G4FKI, Ilford, has prepared an extensive list of amateurs who are active on the 4m band, and by what I have seen it is well worth the 30p he is asking for the document, to cover printing and postage costs. Readers interested should write to G4FKI, QTHR. David is active himself on 4m, all modes.

Congratulations to **Sue Houlihan**, who along with several other students of the Brighton & District Radio Society's RAE class, passed the exam and is now working on her Morse. Sue was out with husband John, G4BLJ, when about 30 members of West Sussex Raynet reported for duty, at the request of the Police, to assist in the hunt for a missing child, code name Operation Elizabeth, on the Sussex downs during the weekend of August 9 and 10. Between two and four Raynet members with their portable sets accompanied each search party, and their control station, supplied by RSGB Council member, **Robin Bellerby** G3ZYE, Hove (also among the searchers), was in a prominent position with an FT-221R feeding a 6-element 2m quad mounted on a 40ft pump-up mast. At the end of the operation Raynet were congratulated and thanked by a senior police officer.

Alan Baker has fitted a 3SK59 MOSFET to the receiver front-end of his FT-221 and is pleased with the results. Alan, who repairs these sets, has had a lot of experience with them and has incorporated a variety of mods to suit his own requirements.

Can anyone help **Herb Bartlett** G5QA, QTHR, with a 3.5MHz to 7MHz coil-pack for an HRO receiver.

Congratulations to George Grzebieniak who through sheer hard listening has received the RSGB 432MHz listeners' award and to **Arthur White**, Grantham, on passing the RAE with credits in both papers.

SLIM JIM for 28MHz

▶▶▶ continued from page 41

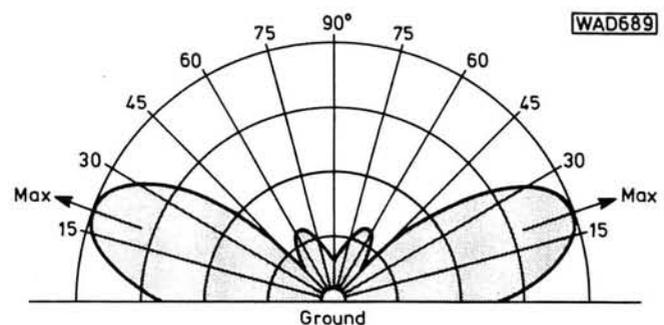


Fig. 2: Approximate vertical radiation pattern when the centre point of the radiating section is $\lambda/2$ above ground of good conductivity, and the aerial is situated in very clear surroundings

there is usually sufficient polarisation twist during long-range propagation to effect good transmission and reception to and from stations using horizontally polarised aerials.

One final note, make sure that the feed point is fully protected from rain water. A small plastics box could be used for this, with the element wires passing right through from top to bottom. A couple of coats of paint or varnish should be applied to the support mast and element spreaders.



MICROWAVE MODULES LTD

HAVE YOU BEEN CONVERTED?

Our wide range of high quality VHF & UHF frequency converters and preamplifiers will expand your existing equipment (YAESU FRG7, TRIO R1000, etc.), to provide coverage of the ever-popular VHF & UHF bands, at the least expense possible. No modifications to your equipment are necessary. Just put one of our converters in place of your existing aerial connection, connect a suitable aerial, a 12 volt DC supply – and that's all there is to it!! **DO YOURSELF AND YOUR RECEIVER A JUSTICE, BUY ONE OF OUR TOP QUALITY PRODUCTS – AND SEE WHAT YOU'VE BEEN MISSING!!**

MMC 144/28

2 METRE DOWN TO 10 METRE CONVERTER

Gain: 30dB typ.
Noise figure: 2.5dB max.
Image rejection: 65dB typ.
Our "old faithful" will give you a 2 metre facility, immediately.

JUST £24.90 inc. VAT
(p+p 65p)



MMA 144V

2 METRE ULTRA LOW NOISE RF SWITCHED PREAMPLIFIER

This preamplifier is an essential addition for the serious operator.
Gain: 15dB typ.
Noise figure: 1.3dB max.
This unit is designed to be left in the aerial lead at all times, and will accept a through power of 100 watts.

£29.90 inc. VAT (p+p 65p)



MM 2000

RTTY TO TV CONVERTER

This NEW converter contains a terminal unit and a microprocessor controlled TV interface, and requires only an audio input from your FRG7, TRIO R1000, or similar, and a 12 volt DC supply, to enable a live display of "off-air" RTTY and ASCII signals on a domestic UHF standard TV set.



- FEATURES INCLUDE:-**
- Complete terminal unit/TV interface
 - Automatic speed sensing
 - Microprocessor controlled
 - Will accept RTTY and amateur standard ASCII


ALL THIS FOR JUST £169 inc. VAT
(p+p £1.75)

MMC 70/28

4 METRE DOWN TO 10 METRE CONVERTER

Gain: 30dB typ.
Noise figure: 2.5dB max.
Image rejection: 65dB typ.

JUST £24.90 inc. VAT
(p+p 65p)

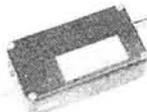


MMA 28

10 METRE LOW NOISE PREAMPLIFIER

Now that the winter months are nearing, and HF conditions will be better, hot up the performance of your 10 metre receiver with this low-noise preamp.
Gain: 20dB typ.
Noise figure: 1.8dB max.

£14.63 inc. VAT
(p+p 65p)

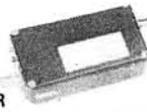

MMC 28/144

10 METRE DOWN TO 2 METRE CONVERTER

For those of you with an existing 2 metre receiver, here is a simple means of listening to the 10 metre band.
Gain: 15dB typ.
Noise figure: 1.8dB max.

£24.90 inc. VAT
(p+p 65p)



MMC 432/28-S

70 CM DOWN TO 10 METRE CONVERTER (with dual range coverage)

This 70cm converter covers 432-434 MHz and 434-436 MHz in two switched ranges, both for an IF output of 28-30 MHz. This facility allows satellite and repeater coverage as well as the usual simplex mode.
Gain: 30dB typ. Noise figure: 3.0dB max.
Also available with an IF of 144-146 MHz – (MMC 432/144-S).

£29.90 inc. VAT
(p+p 65p)



BARCLAYCARD AND ACCESS WELCOME




MICROWAVE MODULES
BROOKFIELD DRIVE, AINTREE, LIVERPOOL L9 7AN, ENGLAND

Telephone: 051-523 4011 Telex 628608 MICRO G

Callers are welcome, please telephone first.

Your orders and enquiries will be dealt with both efficiently and courteously by our experienced sales dept.
Monday-Friday, 9-12.30, 1-4.30 pm.

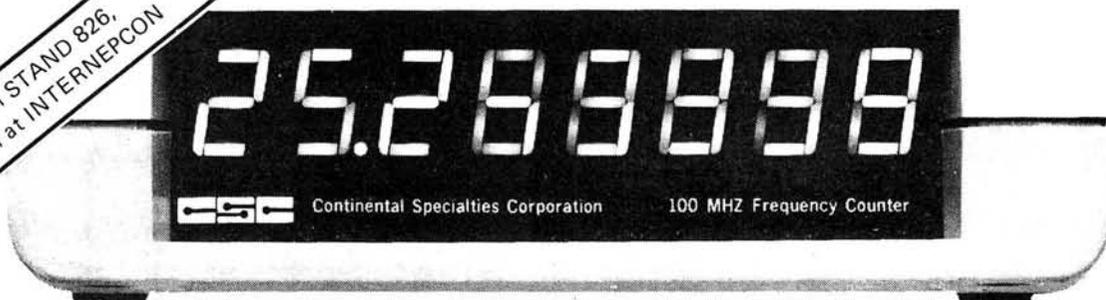See us on STAND 826,
Green Hall at INTERNEPCON



5HZ TO 100MHZ

TOMORROW'S TOOLS TODAY

CONTINENTAL SPECIALTIES CORPORATION



C.S.C. (UK) Limited Dept. 6D
Unit 1, Shire Hill Industrial Estate,
Saffron Walden, Essex. CB11 3AQ
Telephone: Saffron Walden (0799) 21682
Telex: 817477

Instant frequency indication from 5Hz to 100MHz; no range selection problems; a brilliant 8-digit LED display; mains or battery operation; an accuracy of 4 parts per million ± 1 count; and totally automatic operation – all this for only £77.55* with CSC's new Max-100 frequency counter.

Just take a look at our spec. Where else could you find anything similar at the price?
*Frequency range 5Hz - 100 MHz *Input impedance 1M shunted by 10pF *Sensitivity 30mV from 1KHz up to 50MHz; 120mV r.m.s. over full frequency range *Timebase accuracy ± 4 parts in 10^6 (from 5 to 45°C) *Maximum aging rate 10 parts in 10^6 per year *Over-frequency indication *Low-battery-power alarm *Operates from dry or rechargeable cells, an external 7.5 to 10VDC supply, or a car battery (via an adaptor) *Dimensions: 45 x 187 x 143mm *Options: 12V adaptor; battery eliminator; r.f. antenna, low-loss r.f. tap, carrying case.

Fill in the coupon for further details . . .

*price excludes post, packing and VAT

C.S.C. (UK) Ltd., Dept. 6D Unit 1, Shire Hill Industrial Estate, Saffron Walden, Essex. CB11 3AQ

MAX 100	FREQ. COUNTER	Unit price inc P&P 15% VAT £90.91	Qty	Retn
---------	---------------	-----------------------------------	-----	------

Name _____
Address _____

I enclose cheque/P.O. for £ _____ or debit my Barclaycard/Access/
American Express card no. _____ exp. date _____

FOR IMMEDIATE ACTION The C.S.C. 24 hour, 5 day a week service.
Telephone (0799) 21682 and give us your Barclaycard, Access, American
Express number and your order will be in the post immediately.

For FREE catalogue tick box



SIMPLY AHEAD
and staying there

The range grows... bigger...better...

New Profile Amplifiers - Two New Series

MOSFET

CHOOSE AN I.L.P. MOSFET POWER AMP when it is advantageous to have a faster slew rate, lower distortion at higher frequencies, enhanced thermal stability, the ability to work with complex loads without difficulty, and complete absence of cross-over distortion. I.L.P.'s exclusive encapsulation technique within fully adequate heatsinks has been taken a stage further with specially developed computer-verified 'New Profile' extrusions. These ensure optimum operating efficiency from our new MOSFETS, and are easier to mount. Connections via five pins on the underside. I.L.P. MOSFETS ARE IDENTICAL IN PERFORMANCE TO THE COSTLIEST AMPLIFIERS IN THIS EXCITING NEW CATEGORY BUT ARE ONLY A FRACTION OF PRICES CHARGED ELSEWHERE.

Model	Output Power RMS	Distortion Typical at 1KHz	Slew Rate	Rise Time	Signal/Noise Ratio DIN AUDIO	Price & VAT
MOS120	60W into 4-8Ω	0.005%	20V/μs	3μs	100dB	£25.88 + £3.88
MOS200	120W into 4-8Ω	0.005%	20V/μs	3μs	100dB	£33.46 + £5.02


BIPOLAR

CHOOSE AN I.L.P. BIPOLAR POWER AMP where power and price are first consideration while maintaining optimum performance with hi-fi quality and wide choice of models. From domestic hi-fi to disco and P.A., for instrument amplification, there is an I.L.P. Bipolar to fill the bill, and as with our new Mosfets, we have encapsulated Bipolars within our New Profile extrusions with their computer-verified thermal efficiency and improved mounting lugs. Connections are simple, via five pins on the underside and with our newest pre-amps and power supply units, it becomes easier than ever to have a system layout housed the way you want it.


Model	Output Power RMS	Distortion Typical at 1KHz	Slew Rate	Rise Time	Signal/Noise Ratio DIN AUDIO	Price & VAT
HY30	15W into 4-8Ω	0.015%	15V/μs	5μs	100dB	£6.34 + 95p
HY60	30W into 4-8Ω	0.015%	15V/μs	5μs	100dB	£7.24 + £1.09
HY120	60W into 4-8Ω	0.01%	15V/μs	5μs	100dB	£15.20 + £2.28
HY200	120W into 4-8Ω	0.01%	15V/μs	5μs	100dB	£18.44 + £2.77
HY400	240W into 4Ω	0.01%	15V/μs	5μs	100dB	£27.68 + £4.15



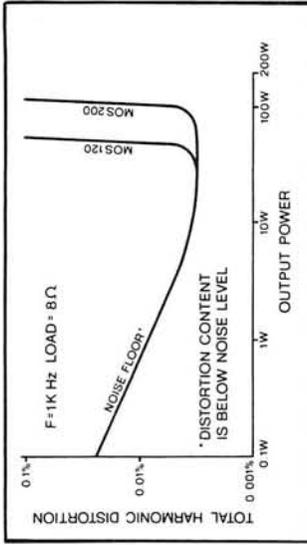
I.L.P. POWER AMPS ARE ENCAPSULATED FOR THERMAL STABILITY AND LONGER LIFE



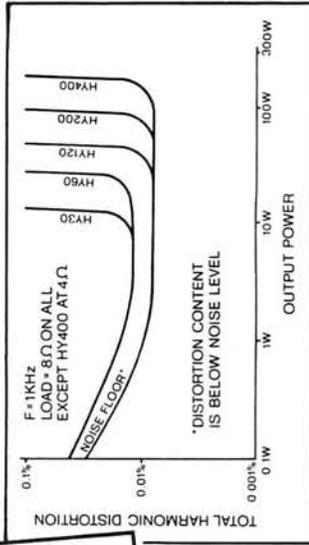Load impedance both models 4Ω ∞ Input sensitivity both models 100KΩ
Frequency response both models 15Hz-100KHz-3dB



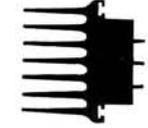Load impedance all models 4Ω ∞ Input impedance all models 100KΩ
Input sensitivity all models 500mV Frequency response all models 15Hz-50KHz-3dB



THE NEW PROFILE EXTRUSIONS
The introduction of standard heatsink extrusion for all I.L.P. power amplifiers achieves many advantages - Research shows they provide optimum thermal dissipation and stability. Slotted shoulders allow easy mounting; standardisation enables us to keep our prices competitive. Surfaces are matt black, anodised for lower thermal conductivity. Extrusions vary in size according to module number.

NEW PRE-AMPS

HY6 (mono) and HY66 (stereo) are new to I.L.P.'s range of advanced audio modules. Their improved characteristics and styling ensure their being compatible with all I.L.P. power-amps both MOSFET and BIPOLAR, giving you chance to get the best possible reproduction from your equipment. HY6 and HY66 pre-amps are protected against short circuit and wrong polarity. Full assembly instructions are provided. Mounting boards are available as below.

- Sizes - HY6 - 45 x 20 x 40 mm. HY66 - 90 x 20 x 40 mm.
- Active Tone Control circuits provide ± 12 dB cut and boost.
- Inputs Sensitivity - Mag. PU - 3mV; Mic - selectable 1-12mV; All others 100mV. Tape O/P - 100mV; Main O/P - 500mV; Frequency response - D.C. to 100KHz - 3dB.
- HY6 mono £5.60 + 84p VAT Connectors included
- HY66 stereo £10.60 + £1.59 VAT Connectors included
- B6 Mounting Board for one HY6 78p + 12p VAT
- B66 Mounting Board for one HY66 99p + 15p VAT

NEW POWER SUPPLY UNITS

Of the eleven power supply units which comprise our current range, nine have toroidal transformers made in our own factory. Thus these I.L.P. power supply units are space-saving, more efficient and their better overall design helps enormously when assembling building. All models in the range are compatible with all I.L.P. amps and pre-amps with types to match whatever I.L.P. power amps you choose.

- PSU30 ± 15 V at 100mA to drive up to 12 x HY6 or 6 x HY66 £4.50 + 0.68p VAT
- THE FOLLOWING WILL ALSO DRIVE I.L.P. PRE-AMPS
- PSU36 for 1 or 2 HY30's £8.10 + £1.22 VAT
- PSU50 with toroidal transformer for 1 or 2 HY60's £9.75 + £1.46 VAT
- PSU60 with toroidal transformer for 1 HY120 £9.75 + £1.46 VAT
- PSU65 with toroidal transformer for 1 MOS120 £9.75 + £1.46 VAT
- PSU70 with toroidal transformer for 1 or 2 HY120's £13.61 + £2.04 VAT
- PSU75 with toroidal transformer for 1 or 2 MOS120 £13.61 + £2.04 VAT
- PSU90 with toroidal transformer for 1 HY200 £13.61 + £2.04 VAT
- PSU95 with toroidal transformer for 1 MOS200 £14.75 + £2.21 VAT
- PSU180 with toroidal transformer for 1 HY400 or 2 HY200 £23.02 + £3.45 VAT
- PSU185 with toroidal transformer for 1 or 2 MOS200 £24.20 + £3.63 VAT

★ Freepost facility

When ordering or writing about I.L.P. products, you do not need to stamp the envelope. Mark it FREEPOST plus the code shown in the address below. We pay the postage for you.


★ TO ORDER

Send cheque or money order payable to I.L.P. Electronics Ltd and crossed. Or pay by ACCESS or BARCLAYCARD. Cash payments must be in registered envelope; if C.O.D. payment is wanted, please add £1.00 to TOTAL value of order.



ELECTRONICS LTD.
 FREEPOST 1 Graham Bell House, Roper Close,
 Canterbury Kent CT2 7EP.
 Telephone (0227) 547780 Telex 965780

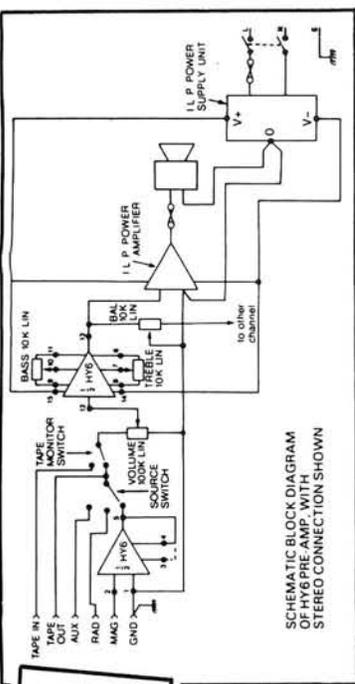Available also from MARSHALLS, WATFORD ELECTRONICS and certain other selected retailers



SCHEMATIC BLOCK DIAGRAM OF HY6 PRE-AMP WITH STEREO CONNECTION SHOWN

COMPATIBLE WITH ALL I.L.P. MODULES

- DISTORTION TYPICALLY 0.005%
- S/N RATIO - 90dB (Mag. P.U. - 68 dB)
- 38 dB overload margin on Mag. P.U.
- LATEST HIGH QUALITY CONNECTORS
- ONLY POTS, SWITCHES AND PLUGS/SOCKETS NEED ADDING
- NEEDS ONLY UNREGULATED POWER SUPPLY $\pm 15 \pm 60$ V

IN A RANGE OF 11 MODELS USING LATEST TOROIDAL TRANSFORMERS

1971-1980 TEN YEARS OF PLANNED PROGRESS

When, as a young man in 1971, Ian L. Potts founded his now world-famous company, he realised the need for a different and more rational approach to exploiting to the maximum, the potential of modular construction. New thinking was badly needed. The result was a range of modules completely revolutionary in concept. The rightness of Ian Potts' thinking is shown in the size of the company today. Its new factory, its vast exports, its acceptance by constructors as the modules to build with. The range grows bigger and better. New lines (in no way replacing existing ones) are well past drawing board stage. This is why I.L.P. are simply ahead and staying there - we don't rest on our laurels.



BRITAIN'S FASTEST GROWING MODULE SUPPLIERS

To: I.L.P. ELECTRONICS LTD. CANTERBURY CT2 7EP

Please supply
 Total purchase price £.....
 I enclose Cheque Postal Orders International Money Order
 Please debit my Access/Barclaycard Account No.


NAME
 ADDRESS
 Signature

ALL U.K. ORDERS DESPATCHED POST FREE

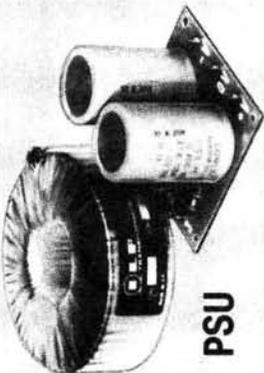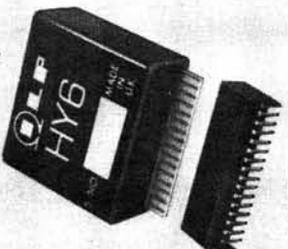

NO QUIBBLE 5 YEAR GUARANTEE
 7-DAY DESPATCH ON ALL ORDERS
 BRITISH DESIGN AND MANUFACTURE
 FREEPOST SERVICE

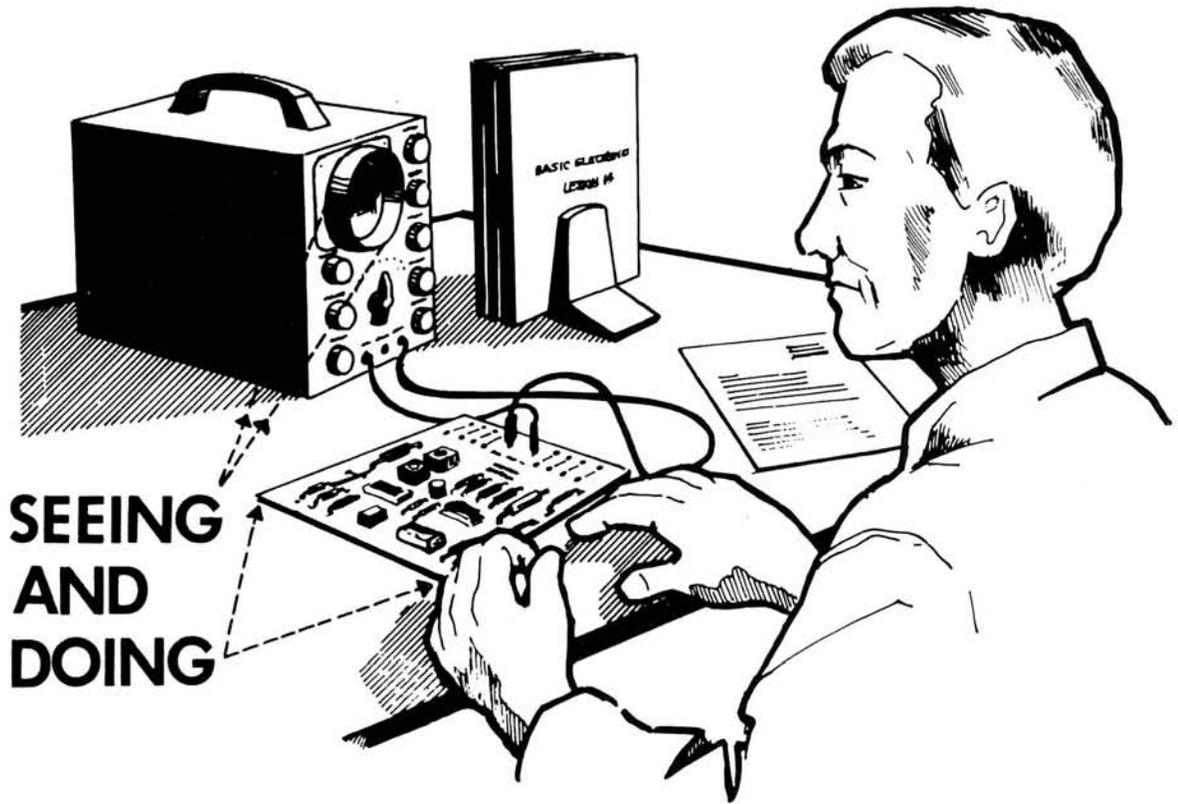Master Electronics the new Practical way.



**SEEING
AND
DOING**

Conquer the 'Chip' — Easy-Fast-Exciting!

AND MASTER ALL THE NEW TECHNIQUES
IN MODERN ELECTRONICS.

- Build an Oscilloscope.
- Carry out over 40 full experiments including work on Digital Electronic Circuits.
- Recognition of Electronic Components.
- Understand and draw Circuit Diagrams.
- Experience with handling Solid State Circuits and "Chips".
- Testing and Servicing of Radio, T.V., Hi-Fi and all types of modern computerised equipment.

Colour Brochure — without any obligation. Post to :—

PW/11/812

BRITISH NATIONAL RADIO & ELECTRONICS SCHOOL
4 Cleveland Road, Jersey, Channel Islands.

Name

Address

.....

.....

BLOCK CAPS PLEASE

ENR

GMT ELECTRONICS **Freeport E Birmingham B19 1BR** **021-233-2400**

■ FREEPOST ON ORDERS ● ACCESS
 ■ VAT INCLUSIVE PRICES ● VISA
 ■ ADD 30p P&P ● CASH
 ■ 24 HR PHONE ANSWERING SERVICE ● CHEQUE

ALL PRICES IN PENCE EACH UNLESS OTHERWISE STATED

C-MOS		LINEAR		SEMICONDUCTORS	
HEF4040A	22	HEF4312	120	CA3046	84
HEF4041	22	HEF4316	136	CA3086	77
HEF4042	22	HEF4317	137	CA3100	99
HEF4043	119	HEF4318	116	CA310E	48
HEF4047	22	HEF4319	59	CA319E	293
HEF4048	100	HEF4320	150	LM301AN	34
HEF4049	22	HEF4321	239	LM339N	78
HEF4051	22	HEF4328	124	LM380N	104
HEF4051A	22	HEF4329	116	LM3818N	198
HEF4051B	22	HEF4329	116	LM3900N	75
HEF4051C	22	HEF4329	116	2N2955	13
HEF4051D	22	HEF4329	116	2N3053	19
HEF4051E	22	HEF4329	116	NE531	131
HEF4051F	22	HEF4329	116	NE53ET	209
HEF4051G	22	HEF4329	116	2N2055	55
HEF4051H	22	HEF4329	116	2N3056	15
HEF4051I	22	HEF4329	116	2N3057	15
HEF4051J	22	HEF4329	116	2N3058	15
HEF4051K	22	HEF4329	116	2N3059	15
HEF4051L	22	HEF4329	116	2N3060	15
HEF4051M	22	HEF4329	116	2N3061	15
HEF4051N	22	HEF4329	116	2N3062	15
HEF4051O	22	HEF4329	116	2N3063	15
HEF4051P	22	HEF4329	116	2N3064	15
HEF4051Q	22	HEF4329	116	2N3065	15
HEF4051R	22	HEF4329	116	2N3066	15
HEF4051S	22	HEF4329	116	2N3067	15
HEF4051T	22	HEF4329	116	2N3068	15
HEF4051U	22	HEF4329	116	2N3069	15
HEF4051V	22	HEF4329	116	2N3070	15
HEF4051W	22	HEF4329	116	2N3071	15
HEF4051X	22	HEF4329	116	2N3072	15
HEF4051Y	22	HEF4329	116	2N3073	15
HEF4051Z	22	HEF4329	116	2N3074	15
HEF4052	112	HEF4329	116	2N3075	15
HEF4053	22	HEF4329	116	2N3076	15
HEF4054	22	HEF4329	116	2N3077	15
HEF4055	22	HEF4329	116	2N3078	15
HEF4056	22	HEF4329	116	2N3079	15
HEF4057	22	HEF4329	116	2N3080	15
HEF4058	22	HEF4329	116	2N3081	15
HEF4059	22	HEF4329	116	2N3082	15
HEF4060	22	HEF4329	116	2N3083	15
HEF4061	22	HEF4329	116	2N3084	15
HEF4062	22	HEF4329	116	2N3085	15
HEF4063	22	HEF4329	116	2N3086	15
HEF4064	22	HEF4329	116	2N3087	15
HEF4065	22	HEF4329	116	2N3088	15
HEF4066	22	HEF4329	116	2N3089	15
HEF4067	22	HEF4329	116	2N3090	15
HEF4068	22	HEF4329	116	2N3091	15
HEF4069	22	HEF4329	116	2N3092	15
HEF4070	22	HEF4329	116	2N3093	15
HEF4071	22	HEF4329	116	2N3094	15
HEF4072	22	HEF4329	116	2N3095	15
HEF4073	22	HEF4329	116	2N3096	15
HEF4074	22	HEF4329	116	2N3097	15
HEF4075	22	HEF4329	116	2N3098	15
HEF4076	22	HEF4329	116	2N3099	15
HEF4077	22	HEF4329	116	2N3100	15
HEF4078	22	HEF4329	116	2N3101	15
HEF4079	22	HEF4329	116	2N3102	15
HEF4080	22	HEF4329	116	2N3103	15
HEF4081	22	HEF4329	116	2N3104	15
HEF4082	22	HEF4329	116	2N3105	15
HEF4083	22	HEF4329	116	2N3106	15
HEF4084	22	HEF4329	116	2N3107	15
HEF4085	22	HEF4329	116	2N3108	15
HEF4086	22	HEF4329	116	2N3109	15
HEF4087	22	HEF4329	116	2N3110	15
HEF4088	22	HEF4329	116	2N3111	15
HEF4089	22	HEF4329	116	2N3112	15
HEF4090	22	HEF4329	116	2N3113	15
HEF4091	22	HEF4329	116	2N3114	15
HEF4092	22	HEF4329	116	2N3115	15
HEF4093	22	HEF4329	116	2N3116	15
HEF4094	22	HEF4329	116	2N3117	15
HEF4095	22	HEF4329	116	2N3118	15
HEF4096	22	HEF4329	116	2N3119	15
HEF4097	22	HEF4329	116	2N3120	15
HEF4098	22	HEF4329	116	2N3121	15
HEF4099	22	HEF4329	116	2N3122	15
HEF4100	22	HEF4329	116	2N3123	15

GMT SELL P.A. EQPT. PLEASE SEND AN SAE FOR DETAILS

CAPACITORS		Polyester Radial Leads		Electrolytic Radial Leads	
Electrolytic Axial	Order Code	Doped Type, C280-252 Style	Order Code	-10% to +50% Tol	Order Code
-10% to +50% Tol	Cap 01R + P	Mounted Type, 10 2mm Pitch	Cap 352	Cap 352	Cap 034 + P
1.0	1	1.0	1	1.0	1
1.5	1	1.5	1	1.5	1
2.2	1	2.2	1	2.2	1
3.3	1	3.3	1	3.3	1
4.7	1	4.7	1	4.7	1
6.8	1	6.8	1	6.8	1
10	1	10	1	10	1
15	1	15	1	15	1
22	1	22	1	22	1
33	1	33	1	33	1
47	1	47	1	47	1
68	1	68	1	68	1
100	1	100	1	100	1
150	1	150	1	150	1
220	1	220	1	220	1
330	1	330	1	330	1
470	1	470	1	470	1
680	1	680	1	680	1
1000	1	1000	1	1000	1
1500	1	1500	1	1500	1
2200	1	2200	1	2200	1
3300	1	3300	1	3300	1
4700	1	4700	1	4700	1
6800	1	6800	1	6800	1
10000	1	10000	1	10000	1
15000	1	15000	1	15000	1
22000	1	22000	1	22000	1
33000	1	33000	1	33000	1
47000	1	47000	1	47000	1
68000	1	68000	1	68000	1
100000	1	100000	1	100000	1
150000	1	150000	1	150000	1
220000	1	220000	1	220000	1
330000	1	330000	1	330000	1
470000	1	470000	1	470000	1
680000	1	680000	1	680000	1
1000000	1	1000000	1	1000000	1
1500000	1	1500000	1	1500000	1
2200000	1	2200000	1	2200000	1
3300000	1	3300000	1	3300000	1
4700000	1	4700000	1	4700000	1
6800000	1	6800000	1	6800000	1
10000000	1	10000000	1	10000000	1
15000000	1	15000000	1	15000000	1
22000000	1	22000000	1	22000000	1
33000000	1	33000000	1	33000000	1
47000000	1	47000000	1	47000000	1
68000000	1	68000000	1	68000000	1
100000000	1	100000000	1	100000000	1
150000000	1	150000000	1	150000000	1
220000000	1	220000000	1	220000000	1
330000000	1	330000000	1	330000000	1
470000000	1	470000000	1	470000000	1
680000000	1	680000000	1	680000000	1
1000000000	1	1000000000	1	1000000000	1
1500000000	1	1500000000	1	1500000000	1
2200000000	1	2200000000	1	2200000000	1
3300000000	1	3300000000	1	3300000000	1
4700000000	1	4700000000	1	4700000000	1
6800000000	1	6800000000	1	6800000000	1
10000000000	1	10000000000	1	10000000000	1
15000000000	1	15000000000	1	15000000000	1
22000000000	1	22000000000	1	22000000000	1
33000000000	1	33000000000	1	33000000000	1
47000000000	1	47000000000	1	47000000000	1
68000000000	1	68000000000	1	68000000000	1
100000000000	1	100000000000	1	100000000000	1
150000000000	1	150000000000	1	150000000000	1
220000000000	1	220000000000	1	220000000000	1
330000000000	1	330000000000	1	330000000000	1
470000000000	1	470000000000	1	470000000000	1
680000000000	1	680000000000	1	680000000000	1
1000000000000	1	1000000000000	1	1000000000000	1
1500000000000	1	1500000000000	1	1500000000000	1
2200000000000	1	2200000000000	1	2200000000000	1
3300000000000	1	3300000000000	1	3300000000000	1
4700000000000	1	4700000000000	1	4700000000000	1
6800000000000	1	6800000000000	1	6800000000000	1
10000000000000	1	10000000000000	1	10000000000000	1
15000000000000	1	15000000000000	1	15000000000000	1
22000000000000	1	22000000000000	1	22000000000000	1
33000000000000	1	33000000000000	1	33000000000000	1
47000000000000	1	47000000000000	1	47000000000000	1
68000000000000	1	68000000000000	1	68000000000000	1
100000000000000	1	100000000000000	1	100000000000000	1
150000000000000	1	150000000000000	1	150000000000000	1
220000000000000	1	220000000000000	1	220000000000000	1
330000000000000	1	3300000000000			

PCB'S FOR PRACTICAL WIRELESS PROJECTS

Jan. 80.	Nimbus Radio Control Encoder	WR061	Price £2.28 30 pence p&p.
Jan. 80.	Nimbus Radio Control Rec.	WR064	Price £2.92 30 pence p&p.
Jan. 80.	A.F. Speech Processor	WR068	Price £2.28 30 pence p&p.
Jan. 80.	Wide Band Pre Amp.	WR067	Price £0.70 30 pence p&p.
Jan. 80.	Nimbus Radio Control T.X.	WR062	Price £2.26 30 pence p&p.
April 80	Signal Generator	WR070	Price £2.71 30 pence p&p.
April 80.	P.W. Nimbus Relay	WR075	Price £0.55 30 pence p&p.
April 80.	P.W. Nimbus Modulator	WR074	Price £0.70 30 pence p&p.
April 80.	Nimbus Transceiver	WR073	Price £5.30 30 pence p&p.
May 80.	Hundred Second Photo Timer	WR078	Price £2.48 30 pence p&p.
June 80.	Audio Limiter Main Board	WK076	Price £2.00 30 pence p&p.
June 80.	Audio Limiter	WK077	Price £1.15 30 pence p&p.
June 80.	Audio Limiter RF Input Board	WR079	Price £1.30 30 pence p&p.
June 80.	VHF/UHF Repeater Timer Main	WR080	Price £1.90 30 pence p&p.
June 80	P.W. Nimbus Base		
	Station Adpt.	WR083	Price £2.60 30 pence p&p.
June 80.	Acoustic Flash Trigger	WRK84	Price £1.25 30 pence p&p.
Aug. 80	Model Railway Controller	WR085	Price £2.17 30 pence p&p.
Sept. 80	Transceiver Power Unit	WR095	Price £0.62 30 pence p&p.
Sept. 80	P.W. Nimbus Tonedruster/ Timer Module	WR096	Price £1.85 30 pence p&p.
Sept. 80	Beginners 2m Converter	WAD634	Price £1.08 30 pence p&p.
Sept. 80	P.W. Tamar Board 1	WR086	Price £0.80 30 pence p&p.
Sept. 80	P.W. Tamar Board 2	WR087	Price £1.50 30 pence p&p.
Sept. 80	P.W. Tamar Board 3	WR088	Price £1.71 30 pence p&p.
Sept. 80	P.W. Tamar Board 4	WR089	Price £1.71 30 pence p&p.
Oct. 80	P.W. Tamar Board 5	WR090	Price £3.70 30 pence p&p.
Oct. 80	P.W. Tamar Board 6	WR091	Price £3.70 30 pence p&p.

FULL RANGE OF RS COMPONENTS AVAILABLE

THIS MONTH'S SPECIAL OFFER

8" x 5" ELLIPTICAL SPEAKERS

£2.30 EACH PLUS 75p p&p.

RATED AT FIVE WATTS. 15 OHM SPEECH COIL.


C. BOWES ELECTRONICS

252A Stockport Road, Cheadle Heath,
Stockport, Cheshire SK3 0LX.

Tel: 061-428 4497

Please enclose cheque or postal order with order.

The 'WINTON' 50+50 WATTS

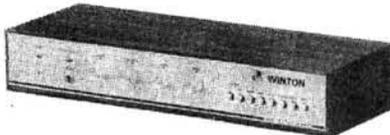

- ★ Power MOS-FET output stage.
- ★ Bi-Fet op-amps.
- ★ Inputs for Disc, Tape, Tuner & two Aux'.
- ★ HF & LF Active Filters.
- ★ Very low noise Disc input stage.
- ★ Easy to build.
- ★ Unconditionally Stable.
- ★ Non-magnetic chassis.

During the past eighteen months the WINTON amplifier has set a new standard in Hi-Fi kits and is highly regarded throughout the world. Taking around twenty hours to build and not requiring special equipment for setting up, it represents incredible value for money and is undoubtedly one of the best kits around today.

A 12p stamp will bring you the full details or better still, send your cheque for the best amplifier kit around. POWER MOS-FET's RULE, O.K.

COMPLETE KIT, of all parts necessary to build the P.W. WINTON £133.50

Order with complete confidence (C.W.O. only please) from:

T.&T. ELECTRONICS

Green Hayes, Surlingham Lane, Rockland St. Mary,
Norwich, NR14 7HH. Telephone 05088 632

PRICE INCLUSIVE OF V.A.T. & CARRIAGE.

Callers by appointment only

Technical Training in Radio, Television and Electronics

ICS have helped thousands of ambitious people to move up into higher paid, more secure jobs in the field of electronics—now it can be your turn. Whether you are a newcomer to the field or are already working in the industry, ICS can provide you with the specialised training so essential to success.

Personal Tuition and Guaranteed Success

The expert and personal guidance by fully qualified tutors, backed by the ICS guarantee of tuition until successful is the key to our outstanding record in the technical training field. You study at the time and pace that suits you best and in your own home. In the words of one of our many successful students: "Since starting my course, my salary has trebled and I am expecting a further increase when my course is completed."

City and Guilds Certificates

Excellent job prospects await those who hold one of these recognised certificates. ICS can coach you for:

Telecommunications Technicians
Radio, TV Electronics Technicians
Technical Communications
Radio Servicing Theory
Radio Amateurs
Electrical Installation Work
Also MPT Radio Communications Certificate

Diploma Courses

Colour TV Servicing
Electronic Engineering and Maintenance
Computer Engineering and Programming
Radio, TV and Audio, Engineering and Servicing
Electrical Engineering, Installations and Contracting

Qualify for a New Career

Home study courses for leading professional examinations and diploma courses for business and technical subjects:—

G.C.E.	Engineering	Purchasing
60 subjects	Farming	Sales
at "O" &	Heating	Storekeeping
"A" levels	Industrial	Work Study
Accountancy	Management	
Air	Mechanical	
Conditioning		
Building		

POST OR PHONE TODAY FOR FREE BOOKLET.

ICS To: International Correspondence Schools



SINCE 1890
Dept. Z276 Intertext House, London
SW8 4UJ or telephone 622 9911

Subject of Interest

Name

Address

Telephone Number

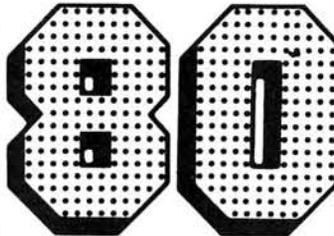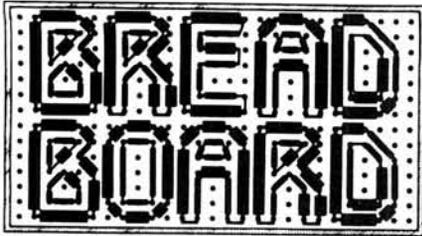

26th Nov - WEDNESDAY - 10am-6pm
 27th Nov - THURSDAY - 10am-8pm
 28th Nov - FRIDAY - 10am-6pm
 29th Nov - SATURDAY - 10am-6pm
 30th Nov - SUNDAY - 10am-4pm

COMPONENTS DEMONSTRATIONS SPECIAL OFFERS MAGAZINES BOOKS

Royal Horticultural Halls Elverton Street

Westminster London SW1

November 26-30 1980

It's all at Breadboard '80

This is **the** exhibition for the electronics enthusiast. From November 26-30 there is only one place in the universe for the electronics enthusiast to be - Breadboard '80, at the Royal Horticultural Hall in London. The majority of leading companies will be exhibiting, including all the top monthly magazines in the field. There will be demonstrations on most stands and many feature special offers that are **EXCLUSIVE** to Breadboard!

All aspects of this fascinating field are catered for, from CB to home computing, so whether you want to buy a soldering iron or a synthesiser - or just keep up to date with your hobby - don't miss Breadboard '80.

AVOID QUEUES - GET ADVANCE TICKETS

Send to: Advance Tickets, Modmags Ltd,
 145 Charing Cross Rd, London WC2H 0EE

Please send: tickets @ £1.50

..... tickets @ £1.00 (Student/Child/OAP)

TO:

I enclose P.O./Cheque for £

THE VALVE AND TUBE SPECIALIST
VALVES AT NEW LOW PRICES

RECEIVING, SQ, TRANSMITTING, DISPLAY, GAS FILLED, ETC.

Type No.	Price ea.						
BK448	95.65	EF37A	4.43	M8137	1.20	QY4-250	72.00
BT58	33.15	EF39	2.10	M8162	4.00	OZ06-20	24.10
D77	0.80	EF80	0.80	M8163	2.65	RG1-240A	16.00
DF61	0.56	EF85	0.91	M8212	0.85	TY2-125	61.80
DM160	3.20	EF86	0.80	ME1400	3.50	TY4-400	62.27
DY86/87	0.64	EF89	0.72	OA2	2.10	XG1-2500	59.60
E55L	15.00	EF91	1.85	OB2	2.55	5U4G	1.95
E80CC	5.65	EF92	2.20	EN92	3.10	5V4G	1.35
E80CF	11.02	EF93	0.60	PC86	0.83	6AK6	2.40
E90F	6.32	EF95	4.88	PC88	0.83	6A06	1.30
E82CC	1.85	EF183	1.60	PC97	1.40	6A06	0.95
E83CC	3.50	EF184	0.75	PC900	0.58	6BH6	1.20
E83F	2.10	EH90	0.86	PCC85	1.10	6BQ7A	1.85
E86C	6.20	EK90	0.90	PCC89	1.50	6BR7	6.00
E88C	5.84	EL34	1.64	PCC189	1.75	6BS7	4.00
E88CC	4.00	EL36	0.82	PCF80	0.87	6BW6	5.30
E92CC	1.65	EL37	5.20	PCF86	1.58	6C4	1.30
E99F	16.30	EL81	1.48	PCF200	2.15	6L6GT	1.60
E130L	4.65	EL84	0.96	PCF801	0.95	6S4A	1.25
E180CC	4.65	EL86	1.65	PCF802	0.81	6SJ7G	1.10
E180F	5.45	EL90	1.25	PCF805	1.40	6SL7GT	2.68
E182CC	8.00	EL91	5.85	PCF808	1.40	6SN7GT	0.90
E186F	5.50	EL95	6.20	PCH200	1.10	6V6GT	0.95
E288CC	7.40	EN30	1.30	PCL82	0.74	6X5GT	0.95
E810F	14.47	EN91	2.56	PCL84	0.83	12A5	1.85
EAF801	3.15	EN92	3.18	PCL85	0.85	12AU6	1.85
ECB81	0.85	EY51	1.66	PCL86	0.85	12BH7	0.98
EB91	0.95	EY84	8.08	PD500	3.90	12SN7GT	2.00
EC91	1.82	EY86	0.64	PL36	1.15	29C1	10.00
EC92	0.94	EY88	1.25	PL81	0.80	30FL2/1	1.20
ECC81	0.78	EY500A	1.65	PL84	0.75	30PL14	1.95
ECC82	0.60	EY802	0.96	PL95	1.10	90C1	2.80
ECC83	0.78	EZ80	0.58	PL504	1.58	90CG	13.68
ECC84	1.19	EZ81	0.75	PL508	1.85	90CV	9.00
ECC85	0.82	EZ90	1.30	PL509	2.75	92AG	7.96
ECC88	1.20	GXU1	15.00	PL802	2.90		
ECC88	1.20	GZ32	1.45	PY88	0.78		
ECC91	2.10	GZ33	1.55	PY500A	1.55		
ECC2000	4.50	GZ34	1.45	PY800	1.20		
ECF80	0.80	KT61	5.10	PY81/801	0.68		
ECF82	0.80	KT66	4.25	QV06-20	11.50		
ECF82	0.80	KT88	7.15	QV03-20	22.75		
ECH81	0.75	M8079	10.69	QV06-40A	21.85		
ECL80	0.95	M8081	4.40	QV02-6	12.04		
ECL82	0.63	M8082	2.14				
ECL85	0.82	M8083	3.50				
ECL86	0.94	M8100	3.00				
		M8136	0.85				

DORAM DORAM ELECTRONICS LTD

Fitzroy House, Market Place,
 Swaffham, Norfolk, PE37 7QH.

New Catalogue

40p

to be refunded with first order

FREE competition entry with catalogue

REF. Dept. PW

Please send me a copy of your new catalogue

NAME: _____

ADDRESS: _____

I enclose cheque/postal order for 40p

INTEL ELECTRONIC COMPONENTS LTD.
 30/50 Ossory Road, London SE1 5AN. Tel: 237 0404

SIX DIGIT COUNTERS

One pulse moves one digit—Type 1 for 230v AC not resettable. Price £89—Type 2 for 48v DC or 115v AC and resettable £1.35.



DOOR MOVING MOTOR

Franco reversible single phase 240v AC motor with gear box giving final speed 56 rpm very powerful motor, weight approx. 13lb. Price £15 carriage £3 mainland only.

SIREN OR BLEEPER

American Delta mechanical type, works on 6 to 12v to DC or 12 to 24v AC. Price 75p or £60 per 100. Electronic Bleeper TH3S emits high pitched wailing note of varying pitch. In red plastic case with fixing bracket. £5.00.



CASSETTE PLAYER/RECORDERS

With record and playback heads, all electronics, switches and speaker. Price £95 (surely this must be the bargain of the year). Music centre replacement stereo with heads but not electronics. £14.95.

FRUIT MACHINE HEART

4 wheels with all fruits, motorised and with solenoids for stopping the wheels, with a little ingenuity you can defy your friends getting the "jackpot". £9.95 + £4 carriage.

DESOLDERING PUMP

Ideal for removing components from computer boards as well as for service work generally. Price £6.35.



4 CORE FLEX CABLE

White pvc for telephone extensions, disco lights etc. 10 metres £2, 100 metres £15. Other multicore cable in stock.

HEADPHONE AMPLIFIER (STEREO)

With volume, tone and balance control 9v operation. All made up ready to go. Price £4.50.



MUGGER DETERRENT

A high note bleeper, push latching switch, plastic case and battery connector. Will scare away any villain and bring help. £2.50 complete kit.

RELAYS

Open type with 2, 10 amp c/o contacts—single screw fixing £1.25 each, please state the coil voltage you require.

HUMIDITY SWITCH

American made by Honeywell. The action of this device depends upon the dampness causing a membrane to stretch and trigger a sensitive micro-switch, very sensitive—breathing on it for instance will switch it on. Micro 3 amp., at 250V a.c. Only £1.15.




SAFE BLOCK

Mains quick connector will save you valuable time. Features include quick spring connectors, heavy plastic case and auto on and off switch. Complete kit £1.95.

VERSA DRILL

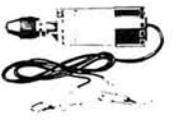A 12 volt battery operated power drill, not just suitable for printed circuit boards but will do all the jobs and is powerful enough to perform all the functions and operations normally expected of Black & Decker and other mains drills. Its chuck accepts up to 1/8" drills. Size approx. 150mm x 50mm. Price £16.75.



TWIST DRILLS

Precision Swiss made—normal price 50p each 10 diff. sizes covering 1/16" to 1/4". £1.99 the lot—don't miss this super bargain.

MAINS SOLENOIDS

All have powerful pull. T72 size 1 1/2" x 2 1/2" x 2". Price £2.95. T76 size 2 1/2" x 3 1/2" x 2". Price £3.50. T110 size 3" x 2 1/2" x 2". Price £4.86.

MOTORISED DISCO SWITCH

With 10 amp changeover switches. Multi adjustable switches are rated at 10 amps. This would provide a magnificent display. For mains operating, 8 switch model £6.25, 12 switch model £6.75, 12 switch model £7.25.



MULLARD UNILEX

A mains operated 4+4 stereo system. Rated one of the finest performers in the stereo field this would make a wonderful gift for almost anyone. In easy-to-assemble modular form this should sell at about £30—but due to a special bulk buy and as an incentive for you to buy this month we offer the system complete at only £16 including VAT and postage. FREE GIFT—Buy this month and you will receive a pair of Goodman's elliptical 8" x 5" speakers to match this amplifier.



NEW KITS

5 WAVE BAND SHORT WAVE KIT Bands spread covering 13.5 to 52 metres. Complete kit includes case, materials, six transistors and diodes, condensers, resistors, inductors, switches etc. Nothing else to buy, if you have an amplifier to connect it to or a pair of high resistance headphones. Special price is £11.95 inc.

SUB-MIN MICROPHONE

Size only 1/8" x 3/16" so small enough for a bugging device, ex-hearing aids but guaranteed. Price £1.50.

TRANSMITTER SURVEILLANCE

Tiny, easily hidden but which will enable conversation to be picked up with FM radio. Can be made in a matchbox—all electronic parts and circuit. £2.30.

RADIO MIKE

Ideal for discos and garden parties, allows complete freedom of movement. Play through FM radio or tuner amp. £6.90.



DRILL CONTROLLER

Electronically changes speed from approximately 10 revs to maximum. Full power at all speeds by finger-tip control. Kit includes all parts, case, everything and full instructions. £3.45 Made up model £1.00 extra

VENNER TIME SWITCH

Mains operated with 20 amp switch, one on and one off per 24 hrs. repeats daily automatically correcting for the lengthening or shortening day. An expensive time switch but you can have it for only £2.95. These are new but without case, but we can supply plastic cases (base and cover) £1.75 or metal case with window £2.95. Also available is adaptor kit to convert this into a normal 24 hr. time switch but with the added advantage of up to 12 on/off per 24 hrs. This makes an ideal controller for the immersion heater. Price of adaptor kit is £2.30.



THIS MONTH'S SNIP

includes a Free Gift, a desoldering PUMP, the one we are currently selling at £6.35. The snip is perhaps the most useful breakdown parcel we have ever offered, 50 nearly all different computer panels, on these panels you will find over 300 ICs, over 300 diodes, over 200 transistors and several thousand other parts, resistors, condensers, multi-turn pots, rectifiers, etc., etc. You can have the parcel for only £2.50 which when you deduct value of the desoldering PUMP, work out just a LITTLE OVER 4p per panel. Surely this is a bargain you should not miss so send your ORDER today. Add £3.26 for Post and VAT.

SOUND AND LIGHT UNITS

3 CHANNEL SOUND TO LIGHT KIT Complete kit of parts for a three channel sound to light unit controlling over 2000 watts of lighting. Use this at home if you wish but it is plenty rugged enough for Disco work. The unit is housed in an attractive two-tone metal case and has controls for each channel, and a master on/off. The audio input and output are by 1/2" sockets and three panel mounting fuse holders provide thyristor protection. A four pin plug and socket facilitate ease of connecting lamps. Special snip price is £13.50 in kit form or £16.50 assembled and tested.


REMOTE CONTROL for Sound to Light (ours or any other circuit) saves connecting to speaker or amp—kit consists of 1 watt amplifier, crystal mike, case, sundries and diagram. Price £3.95.

LIGHT EXPANDER AND LATCH for Sound to Light, enables 3000 watts of lighting to be controlled by single channel or each channel and enables lights to be latched on. Kit consists of latching relay, control switch, case, sundries and diagram. Price £4.25.

SINGLE CHANNEL KIT still available. Price £5.18

DELAY SWITCH

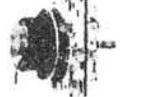Mains operated—delay can be accurately set with pointers knob for periods of up to 2 1/2 hrs. 2 contacts suitable to switch 10 amps—second contact opens a few minutes after 1st contact. £1.50.



MINI-MULTI TESTER

Deluxe pocket size precision moving coil instrument, jewelled bearings—2000 o.p.v. mirrored scale.

11 instant ranges measure:—DC volts 10, 50, 250, 1000, AC volts 10, 50, 250, 1000, DC amps 0-100 mA, Continuity and resistance 0-1 meg ohms in two ranges. Complete with Test Prods and instruction book showing how to measure capacity and inductance as well. Unbelievable value only £6.75 + 50p post and insurance.



FREE Amps ranges kit to enable you to read DC current from 0-10 amps, directly on the 0-10 scale. It's free if you purchase quickly but if you already own a mini tester and would like one, send £2.50.

TERMS: Cash with order—but orders under £10 must add 50p to offset packing, etc.

BULK ENQUIRIES INVITED. PHONE: 0444-54563.

ACCESS & BARCLAYCARD ACCEPTED.

J. Bull [ELECTRICAL] Ltd.

(DEPT. PW11)

34-36 AMERICA LANE,
HAYWARDS HEATH SUSSEX.
RH16 3QU

BURGLAR ALARM CONTROL PANEL

Contains labelled connection block, latching relay, test switch and removable key control switch. Simplifies the whole installation, all you have to do is to take wires to pressure pads and to alarm bell. Price £6.90 + 90p. With complete diagram.

PRECISION MAINS OPERATED CLOCK

For only £1.50 + 22p. Sounds unbelievable but that's what you can have if you send your order right away. The clocks which have large clear dials were made by the famous Smiths Company for use with their domestic cooker switch and are brand new and guaranteed.

15-0-15v @ 2 AMP MAINS TRANSFORMER

Mains transformer, upright mounting primary and secondary wound on separate bobbins with fixing lugs. Price £3 + 45p. Post 60p.

25-0-25v @ 750 mA MAINS TRANSFORMER

Mains transformer C core construction, heavily varnished for dead quiet operation. Upright mounting with fixing lugs. Price £2.75 + 41p. Post 50p.

25 WATT MID-RANGE SPEAKER 5 1/2"

Made by Goodmans so there's none better. 4 ohm coil. Price £3.50 + 45p. Post £1.00.

8 OHM TWEETER

Made by Goodmans. 3 1/2" square, 4" across fixings. Price £1.50 + 22p. Post 30p.

NEW KITS

PRECISION PARKING PAD KIT as specified. £2.50.

LIGHT FAILURE MONITOR KIT as specified. £7.50.

WATERPROOF HEATING WIRE

As used for electric blankets, etc. This has dozens of other applications—in gloves or socks for people with poor circulation are obvious uses. One unusual use suggested by a customer is a 'grow' bag heater. The wire which consists of an element wound on glass fibre then PVC covered has a resistance of 60 ohms per yard. The price is 20p + 3p per yard.

TELEPHONE PICK-UP coil attaches by suction to phone body, enabling conversation to be recorded, put through amp or headphones. Price £1 + 15p.

TRANSDUCERS

As used remote control T.V. receivers. Price £1.50 + 22p.

LIGHT CHASER

Gives a brilliant display—a psychedelic light show for discos, parties and pop groups. These have three modes of flashing, two chase-patterns and a strobe effect. Total output power 750 watts per channel. Complete kit. Price £14 + £2.10. Ready made up for £4 extra.

PRINTED CIRCUIT KIT

4 copper plated boards and the chemical for etching the printed circuits, also 50 interesting designs of all sorts of electronic gadgets which can be made on these boards. Price £1.70+30p.

MAINS TRANSISTOR POWER PACK to operate transistor radio, cassettes, amplifiers, etc., take the place of any of the following batteries, PP1, PP3, PP4, PP6, PP9 and others. You can make voltage output anything from 3v to 16v at up to 300 mA. Complete kit but no case £1.75 + 26p. Case 75p + 13p.

TELESCOPIC AERIAL

5 sections, 21" when extended. Nickel plated superior make, one nut fixing, folds over for FM. Price 95p + 15p.

FISH BITE INDICATOR enables anglers to set up several lines then sit down and read a book. As soon as one has a bite the loudspeaker emits a shrill note. Kit. Price £4.50+68p.

6 WAVEBAND SHORT WAVE RADIO KIT

Complete kit covering 13.5 to 52 metres. Based on circuit which appeared in recent issue of Radio Constructor. Complete kit, includes case materials, six transistors and diodes, condensers, resistors, inductors, switches, etc. Nothing else to buy, if you have an amplifier to connect it to on a pair of high resistance headphones. Special price to get this kit off the ground. Is £11.95 inc VAT and postage.

3" EDGEWISE PANEL METER

0.25 MA moving coil made for the G.P.O. A very useful instrument especially when panel space is limited. £2.50 + 38p.

PANEL METER 0-1mA

Japanese made full vision perspex front, flush mounting. Price £3 + 45p.

12v SUBMERSIBLE PUMP

Our drill pump is useful, but this new one is even more so. Just join it to your car battery, drop it into the liquid to be moved and up it comes, no messing about, no priming, etc. and you get a very good head. Suitable for water, paraffin and any non-explosive, non-corrosive liquid. One use if you are a camper, make yourself a shower. We are not sure how much the voltage may be increased or decreased but using a 9 volt battery we seem to get a rise or fall of about 50 volts. Ex unused P.S.U.'s. Price £2 + 30p. Post 40p.

E.H.T. MAINS TRANSFORMER with inductance control, normal primary, secondary output by our equipment, 3.5 kv 3 mA. E.H.T. voltage can be varied by applying a DC voltage to the lower normally unused bobbin. We are not sure how much the voltage may be increased or decreased but using a 9 volt battery we seem to get a rise or fall of about 50 volts. Ex unused P.S.U.'s. Price £2 + 30p. Post 40p.

SHORT WAVE CRYSTAL RADIO

All the parts to make up the beginners model. Price £2 + 30p. Crystal carriage 57p + 8p. High resistance headphones (give best results) £3.25 + 50p. Kit includes chassis and front but not case.

RADIO STETHOSCOPE

Easy way to fault find—start at the aerial and work towards the speaker—when signal stops you have found the fault. Complete kit £4.25 + 65p.

INTERRUPTED BEAM KIT

This kit enables you to make a switch that will trigger when a steady beam of infra-red or ordinary light is broken. Main components—relay, photo transistor, resistors and caps, etc. Circuit diagram but no case. Price £2 + 30p.

Toroidal TRANSFORMERS



We use advanced winding technology to make our toroidal transformers. They have only half the weight and height of their laminated equivalents and are appreciably more efficient. Our toroidals cost virtually the same as their now outdated laminated equivalents and hum is down to a negligible tenth of what it used to be. Supplied with rigid mounting kit with centre bolt, two neoprene and one steel washer. Available so far in a range of 37 sizes with more to come.

TYPE	VA	SECONDARY RMS VOLTS	SECONDARY RMS CURRENT	DIA. x HT in mm	WEIGHT Kg	PRICE
2X010	50	6+6	4.16	80 x 35	0.9	EACH £5.40 +£1.10 P&P +98p VAT
2X011		9+9	2.77			
2X012		12+12	2.08			
2X013		15+15	1.66			
2X014		18+18	1.38			
2X015		22+22	1.13			
2X016		25+25	1.00			
3X010	80	6+6	6.64	90 x 30	1.0	EACH £5.76 +£1.20 P&P +£1.04 VAT
3X011		9+9	4.44			
3X012		12+12	3.33			
3X013		15+15	2.66			
3X014		18+18	2.22			
3X015		22+22	1.81			
3X016		25+25	1.60			
3X028		110	0.72			
3X029		220	0.36			
3X030		240	0.33			
4X010	120	6+6	10.00	90 x 40	1.2	EACH £6.72 +£1.30 P&P +£1.20 VAT
4X011		9+9	6.66			
4X012		12+12	5.00			
4X013		15+15	4.00			
4X014		18+18	3.33			
4X015		22+22	2.72			
4X016		25+25	2.40			
4X028		110	1.09			
4X029		220	0.54			
4X030		240	0.50			
5X016	160	25+25	3.20	110 x 40	1.8	EACH £8.88 +£1.40 P&P +£1.54 VAT
5X017		30+30	2.66			
5X028		110	1.45			
5X029		220	0.72			
5X030		240	0.66			
6X016	300	25+25	6.00	110 x 50	2.6	EACH £12.27 +£1.50 P&P +£2.07 VAT
6X017		30+30	5.00			
6X018		35+35	4.28			
6X026		40+40	3.75			
6X025		45+45	3.33			
6X028		110	2.72			
6X029		220	1.36			
6X030		240	1.25			

CHOICE OF 3 PRIMARY INPUTS

L.L.P. Toroidal Transformers are available in choice of 110V, 220V, 240V, coded as follows: (Secondaries can be connected in series or parallel)

For 110V Primary insert 0 in place of "X" in type number.
For 220V Primary insert 1 in place of "X" in type number.
For 240V Primary insert 2 in place of "X" in type number.

Example - 120VA 240V 15+15V. 4A = 42013.

* TYPES TO SPECIFICATION CAN BE SUPPLIED TO ORDER IN QUANTITY, AGENCIES IN CERTAIN COUNTRIES AVAILABLE ENQUIRIES INVITED

FREEPOST facility.

We pay postage on U.K. enquiries and orders. Simply address envelope to FREEPOST T5 to address below. NO STAMP REQUIRED.

TO ORDER Enclose cheque/Postal Order/Money Order payable to L.L.P. Electronics Ltd or quote your ACCESS or BARCLAYCARD account No. To pay C.O.D. add £1 extra to TOTAL value of order.




FREEPOST T1 GRAHAM BELL HOUSE ROPER CLOSE
CANTERBURY CT2 7EP Phone (0227) 54778 Telex 965 780

OHIO SCIENTIFIC SUPERBOARD II

50HZ BLACK AND WHITE SUPERBOARD II £159.95 - 15% VAT POST FREE.
50HZ COLOURBOARD II, THE NEW COLOUR VERSION £205 - 15% VAT.

50HZ UK BLACK AND WHITE SUPERBOARD II £159.95+15% VAT POST FREE.
COLOURBOARD II £205 - 15% VAT.

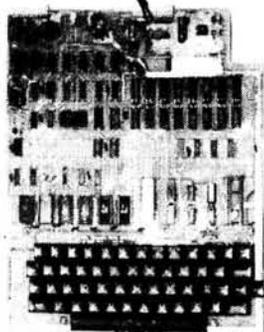THE UNIQUE SPECIAL OFFER YOU CAN'T RESIST



- *****
- * If bought with superboard or colourboard these items are at the reduced prices shown first. Also sold separately at the bracketed prices. Add 15% VAT. Modulator and power supply kit £7.95 (£11). 4K extra ram £20 (£24). Display expansion kit approx 30 lines, 54 characters £15 (£20).
 - * Case £23 (£26). Colour conversion board fully assembled £45 (£45).
 - * Cassette recorder £13 (£15). Extended monitor £20 (£20).
 - * Assembler/Editor £25 (£25). 610 Expansion board £160 (£160).
 - * Minifloppy with psu and 2 copies DOS £275 (£275).
- *****

COMPUTER GAMES

Chess challenger 7 £79. Atari video-computer £129. Space invaders cartridge £27.50 (only £17 if bought with the video-computer).

SINCLAIR (THANDAR) PRODUCTS

SC110 10MHz oscilloscope £144.95. PFM200 £51.95, case £2.07, adaptor £4.20, connector kit £13.95. Microvision TV £89, mains adaptor £6.85. PDM35 £34.23, mains adaptor £4.20, case £2.07. DM350 £76.70, DM450 £102.17, DM235 £55.55. Accessories for all 3 models:- rechargeable batts £7.99, mains adaptor/charger £4.20, case £8.90. Enterprise prog calculator £19.95. TG105 £87. TF200 £150.

SUPER PRINT 800MST



The ideal impact matrix printer for Superboard, UK101, pet, apple, trs80, 80 lines/minute, 5 print densities of 72, 80, 96, 120 or 132 chr/line. Tractor and friction feed for up to 9 1/2" tractor paper. Graphics with user definable set in ram. RS-232 20ma. IEEE488 and centronics I/O. SPECIAL OFFER:- Supplied with free word processor program and interface components £359 + 15% VAT.

SWANLEY ELECTRONICS

Dept. PW, 32 Golsal Rd., Swanley, Kent BR8 8EZ.

Mail order only. Please add 35p postage. Prices include VAT unless stated. Lists 27p post free. Overseas customers deduct 13%. Official credit orders welcome.



TECHNICAL BOOKS

MAIL ORDER

ELECTRONICS - RADIO - AUDIO

Why waste time and money shopping around for that book you want? - We have a comprehensive range by well-known authors and publishers.

AMATEUR RADIO - HI-FI - TAPE RECORDING - DIY ELECTRONICS - IC CIRCUITS - MICROPROCESSORS
RADIO - CB - ELECTRONIC MUSIC - TEST GEAR
VIDEO - ETC. ETC.

LATEST BOOKS ON CB RADIO

Send only 12p stamp with your address for catalogue of titles and prices plus contents of books FREE - Real leather embossed book mark with orders over £5.

NEW! RECOMMENDED BOOKS

- Q and A Amateur Radio - F. C. Judd - (Newnes) **£1.75**
- 1980 Edition. Guide to Broadcast Stations (Newnes) **£3.40**
- Beginners Guide to Digital Electronics - I. Sinclair (Newnes) **£3.50**
- Electronics - Build and Learn - R. A. Penfold (Newnes) **£3.00**
- Two Metre Antenna Handbook - F. C. Judd (Newnes) **£3.95**

All in stock books despatched first class post same day as order received. All prices include packing and postage.

Tel: Freethorpe 821 (STD 049 370). 9 am-5 pm Mon-Fri only.

Z. L. COMMUNICATIONS CANTLEY, Nr. NORWICH, Norfolk NR13 3RT.

(Netherlands Branch - De Ruyterstraat 3, 3134 XN, Vlaardingen, Holland)

Marshall's

A. Marshall (London) Ltd., Kingsgate House,
Kingsgate Place, London NW6 4TA
Industrial Sales: 01-328 1009
Mail Order: 01-624 8582 24hr. service
Also retail shops: 325 Edgware Road, London W2
40 Cricklewood Broadway, London NW2 85 West Regent St., Glasgow
108A Stokes Croft, Bristol

We now supply the extremely reliable and cost conscious LEADER range of testgear.

SINGLE TRACE OSCILLOSCOPES		
LBO 510A 5" 40Hz 20mV	£175.00	
LBO 512A 5" 100Hz 10mV	£170.00	
LBO 513A 5" 100Hz 10mV	£275.00	
LBO 507A 5" 200Hz 10mV	£239.00	
DUAL TRACE OSCILLOSCOPES		
LBO 308S 3" 200Hz 2mV	£419.00	
LBO 508A 5" 200Hz 10mV	£299.00	
LBO 520A 5" 350Hz 5mV	£375.00	
LBO 514 5" 100Hz 5mV	£250.00	
T.V. RADIO TEST GEAR		
LSG 16 Signal Generator	£49.00	
LSG 231 FM Stereo Signal Generator	£169.00	
LCG 397U PAL B Pattern Generator	£189.00	
AUDIO TEST GEAR		
LAG 26 Audio Generator	£60.00	
LAG 120A Audio Generator	£133.00	
LDM 1/0 Distortion Meter	£275.00	
LFI 39A Wow Flutter Meter (dual)	£249.00	
LFI 39A Wow Flutter Meter (dual)	£299.00	
LAV 191 Audio Tester	£249.00	
LAG 175 Low Distortion Audio Generator	£279.00	
GENERAL TEST GEAR		
LCR 740 LCR Bridge	£135.00	
LTC 906A Transistor Checker	£90.00	
LVI 22 Jet Transistor Checker	£119.00	
LIC 907 Transistor Checker	£139.00	
LAI 47 Attenuator	£135.00	
LAI 45 Attenuator	£75.00	
LFG 1300 Sweep Function Generator	£299.00	
AMATEUR RADIO		
LDM 815 DIP Meter	£43.00	
LIM 870A Antenna Impedance Meter	£41.00	
LPM 880 HF Power Meter	£69.00	
LPM 885 SWL Watt Meter	£44.00	
LAC 895 Antenna Coupler	£85.00	
LAC 896 Antenna Coupler	£85.00	
LAC 897 Antenna Coupler	£41.00	

Please send large SAE for special catalogue. All prices exclusive VAT/carriage.

The new Marshall's 80/81 catalogue is now available. A veritable treasure house of components, test gear, tools, etc.



Lots of old friends, but also many new products including leader test gear, Crimson Hi Fi Modules, Rechargeable Ni Cad batteries and chargers (very competitive). More components including SN74ALS series, new tools etc. Available by post, UK 75p post paid: Europe 95p post paid: Rest of world £1.35 post paid.

SINCLAIR INSTRUMENTS		
Digital Multimeter		
"	PDM35	£ 34.50
"	DM235	£ 52.50
"	DM350	£ 72.50
"	DM450	£ 99.00
Digital Frequency Meter		
	PFM200	£ 49.80
Low Power Oscilloscope		
	SC110	£139.00

NEW		
TF200	Frequency Meter	£145.00
TGF105	Pulse Generator	£ 85.00

CRIMSON ELEKTRIK HI FI MODULES		
CE608	Power Amp	£20.09
CE1004	" "	£23.43
CE1008	" "	£26.30
CE1704	" "	£33.48
CE1708	" "	£33.48
CPS1	Power Unit	£19.52
CPS3	" "	£23.52
CPS6	" "	£30.00
CPR1	Pre Amp	£32.17
CPR1S	Pre Amp	£42.52
All Prices + VAT + postage/ packaging		
Don't forget! We also carry an impressive range of semi conductors, passive components, electro mechanical components, tools etc.		

TTLS BY TEXAS		74221 160p		74LS192 140p		74C157 250p		LINEAR I.C.s		TRANSISTORS		TIP41C 75p		DIODES			
7400	11p	7497	160p	74251	140p	74C160	155p	AY1-0212	600p	MC1496	100p	BFY51/2	22p	2N3866	90p	BY127	12p
7401	12p	74100	130p	74259	250p	74C161	155p	AY1-1313	668p	MC3340	120p	BFY56	33p	2N3903/4	18p	OA47	12p
7402	14p	74104	65p	74265	90p	74C162	155p	AY1-5050	212p	MC3360	120p	BFY90	90p	2N4036	65p	OA81	15p
7403	14p	74105	65p	74279	100p	74C163	155p	AY5-1224A	225p	MK50599	750p	BC107/8	11p	2N4059/12p	90p	OA85	15p
7404	14p	74107	34p	74279	100p	74C164	120p	AY5-1315	600p	NE531	100p	BC109/11p	11p	TIS43	34p	OA90	9p
7405	18p	74107	34p	74283	190p	74C173	120p	AY5-1317	780p	NE543K	225p	BC147/8	9p	BU105	190p	OA91	9p
7406	32p	74110	55p	74284	400p	74C174	120p	AY5-1320	320p	NE555	25p	BC149	10p	BU108	250p	2N4129/12p	90p
7407	32p	74111	70p	74285	400p	74C175	210p	CA5019	80p	NE556	70p	BU205	220p	ZT X300	11p	2N4125/22p	90p
7408	19p	74116	200p	74290	150p	74C182	150p	CA3046	70p	NE561B	425p	BU208	240p	ZT X500	15p	2N4289	20p
7409	19p	74118	130p	74294	200p	74C189	150p	CA3048	725p	NE562B	425p	BU406	145p	ZT X502	18p	2N4401/3	27p
7410	15p	74119	210p	74294	200p	74C192	150p	CA3080E	225p	NE565	130p	BU406	145p	ZT X504	30p	2N4427	90p
7411	24p	74120	115p	74298	200p	74C194	220p	CA3080E	225p	NE566	135p	MJ2501	225p	2N4574	250p	1N4148	4p
7412	20p	74121	28p	74365	150p	74C195	110p	CA3090A	375p	NE567	175p	MJ2955	100p	2N5087	27p	ZENER	5p
7413	30p	74122	48p	74366	150p	74C221	175p	CA3090A	375p	NE567	175p	MJ3001	225p	2N5089	27p	1N4003/4	6p
7414	60p	74123	48p	74367	150p	4000	15p	CA3140E	70p	SP8515	750p	MJE340	65p	2N5172	27p	1N4005	6p
7416	27p	74125	55p	74368	150p	4000	15p	CA3160E	75p	SP8515	750p	MJE2955	100p	2N5179	27p	1N4006/7	7p
7417	27p	74126	60p	74390	200p	81LS95	140p	FX209	750p	TBA811B1	225p	MJE3055	70p	2N5191	83p	1N5401/3	14p
7420	17p	74128	75p	74393	200p	81LS96	140p	ICL7108	925p	TBA800	90p	MPF102	45p	2N5194	90p	1N5404/7	19p
7421	40p	74132	115p	74490	225p	81LS97	140p	ICL8038	340p	TBA810	100p	MPF103/4	40p	2N5245	40p	ZENER	5p
7422	22p	74136	60p	74LS		81LS98	140p	LM301A	36p	TBA820	90p	MPF105/6	40p	2N5256	55p	2-7V-33V	6p
7423	34p	74141	70p	SERIES		81LS98	140p	LM301A	36p	TBA820	90p	MPSA06	30p	2N5401	50p	400 mW	9p
7425	30p	74142	200p	74LS00	14p	8208	230p	LM312	290p	TDA1008	300p	MPSA12	50p	2N5457/8	40p	1 W	15p
7426	40p	74145	90p	74LS02	14p	8302	175p	LM317	40p	TDA1008	300p	MPSA16	50p	2N5478	40p	SPECIAL	
7427	34p	74147	190p	74LS04	14p	8302	175p	LM324	70p	TDA1008	300p	MPSA16	50p	2N5478	40p	OFFERS	
7428	36p	74148	150p	74LS08	22p	8310	275p	LM339	90p	TDA1008	300p	MPSA16	50p	2N5485	44p	100-741	
7430	17p	74150	100p	74LS10	20p	8311	275p	LM348	95p	TDA1022	600p	MPSU06	65p	2N5622	48p	ET6	
7432	30p	74151A	70p	74LS13	38p	8312	160p	LM377	175p	XR2208	400p	MPSU06	65p	2N5622	48p	100-555	
7433	40p	74153	70p	74LS14	70p	8314	160p	LM380	75p	XR2207	400p	OC28	130p	2N5644	30p	100-555	
7437	35p	74154	100p	74LS20	22p	8316	225p	LM3801AN	150p	XR2208	400p	OC35	130p	2N5644	30p	100-555	
7438	35p	74155	90p	74LS22	22p	8316	225p	LM389N	140p	XR240	400p	R2008B	200p	2N5644	30p	100-555	
7440	17p	74156	100p	74LS27	30p	8318	200p	LM709	36p	ZN414	90p	R2010B	200p	2N5644	30p	100-555	
7441	70p	74157	70p	74LS30	30p	8320	200p	LM710	50p	ZN425A	135p	TIP29A	40p	2N5644	30p	100-555	
7442A	60p	74159	100p	74LS47	90p	8374	200p	LM733	100p	ZN425A	135p	TIP29C	55p	2N5644	30p	100-555	
7443	112p	74160	100p	74LS55	30p	8601	100p	LM741	29p	ZN425A	135p	TIP30A	40p	2N5644	30p	100-555	
7444	112p	74161	100p	74LS73	30p	9602	225p	LM747	70p	95H90	800p	TIP30C	60p	2N5644	30p	100-555	
7445	100p	74162	100p	74LS74	40p	9602	225p	LM747	70p	95H90	800p	TIP31A	58p	2N5644	30p	100-555	
7446A	53p	74163	100p	74LS75	40p	9602	225p	LM748	30p			TIP31C	62p	2N5644	30p	100-555	
7447A	19p	74163	100p	74LS83	110p	MC1488	100p	LM301A	36p			TIP32A	88p	2N5644	30p	100-555	
7448	80p	74165	130p	74LS85	100p	MC1489	100p	LM301A	36p			TIP33C	85p	2N5644	30p	100-555	
7450	17p	74166	100p	74LS86	40p	75107	160p	LM317	40p			TIP33A	90p	2N5644	30p	100-555	
7451	17p	74167	200p	74LS90	60p	75182	230p	LM4136	120p			TIP33C	85p	2N5644	30p	100-555	
7453	17p	74170	240p	74LS93	60p	75182	230p	LM4310P	120p			TIP33C	85p	2N5644	30p	100-555	
7454	17p	74172	720p	74LS107	45p	75451/2	72p	MC1458	45p			TIP34A	114p	2N3702/3	12p	40A10	85p
7459	17p	74173	720p	74LS112	100p	75451/2	72p	MC1458	45p			TIP34A	114p	2N3702/3	12p	40A10	85p
7470	36p	74174	85p	74LS123	75p	C-MOS I.C.s		MC1458	45p			TIP34A	114p	2N3702/3	12p	40A10	85p
7472	30p	74175	85p	74LS132	90p	74C00	25p	MC1458	45p			TIP34A	114p	2N3702/3	12p	40A10	85p
7473	34p	74176	90p	74LS133	90p	74C02	25p	MC1458	45p			TIP34A	114p	2N3702/3	12p	40A10	85p
7474	30p	74177	90p	74LS138	60p	74C04	27p	MC1458	45p			TIP34A	114p	2N3702/3	12p	40A10	85p
7475	30p	74178	100p	74LS139	60p	74C08	27p	MC1458	45p			TIP34A	114p	2N3702/3	12p	40A10	85p
7476	35p	74178	100p	74LS151	100p	74C10	27p	MC1458									



SMALL ADS

The prepaid rate for classified advertisements is 24 pence per word (minimum 12 words), box number 60p extra. Semi-display setting £8.00 per single column centimetre (minimum 2.5 cms). All cheques, postal orders etc., to be made payable to Practical Wireless and crossed "Lloyds Bank Ltd". Treasury notes should always be sent registered post. Advertisements, together with remittance should be sent to the Classified Advertisement Manager, Practical Wireless, Room 2337, IPC Magazines Limited, King's Reach Tower, Stamford St., London, SE1 9LS. (Telephone 01-261 5846).

NOTICE TO READERS

Whilst prices of goods shown in classified advertisements are correct at the time of closing for press, readers are advised to check with the advertiser both prices and availability of goods before ordering from non-current issues of the magazine.

When replying to Classified Advertisements please ensure:

- That you have clearly stated your requirements.
- That you have enclosed the right remittance.
- That your name and address is written in block capitals, and
- That your letter is correctly addressed to the advertiser.

This will assist advertisers in processing and despatching orders with the minimum of delay.

Receivers and Components

BRAND NEW COMPONENTS BY RETURN

HIGH STABILITY RESISTORS.

1/4W Carbon Film E12 Series 1R-10M. (E24 2R-6M2)—1p
1/4W 1/8W & 1W Metal Film E12 Series 10R-2M2—2p

CAPACITORS.
MULLARD Min. Ceramic E12 100V 2% 1.8pf. to 47pf.—3p
2% 56pf. to 330pf.—4p, 10% 390pf. to 4700pf.—4p

Plate Ceramic 50V Wkg. Vertical Mounting.
E12 22pf. to 1000pf. & E6 1K5pf. to 47Kpf.—2p

Miniature Polyester 250V Wkg. Vertical Mounting.
0.01, 0.015, 0.022, 0.033, 0.047 & 0.068 mfd.—4p

0.1—5p, 0.15 & 0.22—6p, 0.33 & 0.47—8p
0.68—11p, 1.0—15p, 1.5—20p, 2.2—22p

ELECTROLYTIC. Wire Ended (Mfds/Volts).

0.47/50	5p	22/25	5p	100/25	7p	470/25	11p
1/0/50	5p	22/50	8p	100/50	8p	470/40	16p
2/2/50	5p	47/16	5p	220/16	8p	1000/15	15p
4/7/50	5p	47/25	5p	220/25	8p	1000/25	18p
10/50	5p	47/50	8p	220/50	10p	1000/40	35p
22/16	5p	100/16	7p	470/16	11p	2200/16	20p

TANTALUM BEAD SUBMINIATURE ELECTROLYTICS.

0.1, 0.22, 0.47, 1.0, 2.2 = 35V & 4.7 = 6.3V—14p
4.7/16V & 25V—15p, 10/16 & 22/6—20p, 10/25—29p

10/35V, 22/16V, 47/16.3V, 68/3V & 100/3V—30p
15/25, 22/25, 47/10—35p, 47/16—80p, 220/16—£1.20

Polyethylene 63V Wkg. E12 Series Long Axial Wires.
10 pf. to 820 pf.—3p, 1000 pf. to 10,000pf.—4p

TRANSISTORS.

BC107/8/9 10p BC182L 8p BF197 9p
BC147/8/9 10p BC184L 8p BFY50/51/52 18p

BC157/8/9 10p BC212L 8p BFX88 25p
BC547/8/9C 7p BCY70 15p 2N2926 7p

BC557C/BC/9C 7p BF194 9p 2N3055 50p

8 Pin D.I.L. i.c.'s 741 Op/amp.—18p, 555 Timer—24p
Holders 8 pin—9p, 14 Pin—12p, 16 Pin—14p, 28 Pin—25p
40 Pin—30p.

DIODES (p.i.v./amps).

75/25mA 1N4148 2p 1250/1A BY127 10p

100/1A 1N4002 4p 400/3A 1N5404 14p

800/1A 1N4006 6p 60/1.5A S1M1 5p

1000/1A 1N4007 7p 30/150mA AAY32 12p

ZENER DIODES.

E24 Series 3V3 to 33V 400mW—8p, 1W—10p
L.E.D.'s 3 mm. & 5 mm. Red—10p, Green, Yellow—14p

Grommets for 3 mm.—1p. Holders for 5 mm.—2p
FUSES, 20 mm. Glass, 100mA to 5A, Q.B.—3p, A/S—5p

VOLTAGE REGULATORS, +5V, 8V, 12V, 15V 100mA—35p
5V, 8V, 12V, 15V, 18V & 24V 0.5A—60p, 1A—65p

PRESET POTENTIOMETERS
50mW & 1/4W 100R to 1M0.—6p

THE C. R. SUPPLY CO.

127, Chesterfield Road, Sheffield S8 0RN.
V.A.T. Inclusive Prices, Postage 15p
(FREE over £5.00)

CLEARANCE PARCELS: Transistors, Resistors, Boards, Hardware. 10lbs only £5.80! 1,000 Resistors £4.25, 500 Capacitors £3.75, BC108, BC171, BC204, BC230, 2N5061, CV7497 Transistors, 10 70p, 100 £5.80, 2N 3055, 10 for £3.50, S.A.E. Lists: W.V.E. (1) 15 High Street, Lydney, Gloucestershire.

BUILD a professional VLF/TR metal detector for £19.00. Moulded coil, prealigned and assembled circuit board. Phone Storrington 4830.

CB SPARES

Original transistors and integrated circuits for all types of 40/120/24C etc. channel rigs.

McLAUGHLIN ELECTRONICS,
44 Carlisle Road,
Londonderry,
Northern Ireland BT48 6JW.
Tel. 0504 65002.

CRYSTALS MADE TO ORDER within 6 weeks.
4-105MHz, wire or pins. £3.90 each inclusive. HARTLEY
CRYSTALS. Green Lane, Milford, Godalming, Surrey
GU8 5BG.

FM DX!

88-108MHz Mosfet preamplifier

Vastly superior performance over bi-polar preamplifiers. Mains powered unit. **£25.95** inc. pp.

SAE data to: **H. Cocks,**
Cripps Corner, Robertsbridge, Sussex.
Tel: 058083-317.

WE SUPPLY most Vintage Radio component parts with a friendly service worldwide. Vintage British Radio Components Co., Weldon Park, Weldon, Near Corby, Northants. Tel. Corby 61875.

VALVES

Radio - T.V. - Industrial - Transmitting
Projector Lamps and Semiconductors

We Dispatch Valves to all parts of the world by return of post, Air or Sea mail, 4000 Types in stock, 1930 to 1976. Obsolete types a speciality. List 50p. Quotations S.A.E. Open to callers Monday to Saturday 9.30 to 5.00 closed Wednesday 1.00. We wish to purchase all types of new and boxed Valves, Projector Lamps and Semiconductors.

COX RADIO (SUSSEX) LTD.

Dept. P.W. The Parade, East Wittering,
Sussex PO20 8BN
West Wittering 2023 (STD Code 024366)

CRYSTALS Brand new high-precision. You benefit from very large stocks held for industrial supplies. All normal freq standards, baud rates, MPU, and all magazine projects inc: HC33/U: 1.0, 1.008, 2.5625 MHz, £3.50, 1.280 MHz, £4.15, HC18/U: 4.0, 5.0, 6.0, 7.0, 8.0, 9.0, 10.0, 10.7, 12.0, 15.0, 16.0, 18.0, 20.0, 6.9375, 38.6667, MHz, £3.25. Selected freqs stocked in Glider, Marine and 27 MHz bands. Any freq made to order in 6 weeks from £3.90.

FILTERS Your best source for 6 and 8 pole and monoliths for AM, CW, SSB, FM, on 455 kHz, 1.6, 9.0, 10.7, 21.4 MHz, etc.
Prices inc. VAT and UK post. SAE lists.

P. R. GOLLEDGE ELECTRONICS
G3EDW, Merriott, Somerset, TA16 5NS.
Tel: 0480 73718

100 MIXED TRANSISTORS £3.50. List 15p. **SOLE ELECTRONICS.** (P.W.) 37, Stanley Street, Ormskirk, Lancs. L39 2DH.

Southern Valve Co.,

2nd Floor, 6 Pottera Road, New Barnet, Herts.
Tel: 01-440 8641 for current prices & availability. All popular valves stocked. **NO CALLERS.** SAE Lists. Cash with order. Same Day Postal Despatch. Telephone afternoons preferred.

Valves, Tubes, Aerials etc by LEADING-MAKERS. Send SAE Lists or Phone for current prices. Counter or MAIL ORDER. NO COD. Speedy Despatch assured. No order under £1.

Philip Bearman, 6 Pottera Road, New Barnet, Herts.
Tel: 01-449 1934/5 (1934 Recording Machine).
Telephone for Shop Hours.

Books and Publications

WHY NOT START YOUR OWN BUSINESS REWINDING ELECTRIC MOTORS. A genuine opportunity to success. LARGE PROFITS. You can't help but make money if you follow the easy, step by step, instructions in our fully illustrated manual showing how to rewind Electric Motors, Armatures and Field coils as used in Vacuum Cleaners, Electric Drills and Power Tools. NO PREVIOUS KNOWLEDGE IS REQUIRED, as the manual covers in 13 chapters, where to obtain all the work you need, materials required, all instructions, rewind charts and how to take data etc. A gold mine of information. How to set up your home workshop and how to cost each job to your customer. £4.50 inclusive of P&P. UK. CWO to: INDUSTRIAL SUPPLIES, 102 Parrswood Rd., Withington, Manchester 20, Dept. PW.

RADIO BOOK SERVICE

WORLD RADIO TV HANDBOOK 1980 Edition	£9-30
Radio Stations Guide	£1-60
How to make Walkie-Talkies	£1-55
Beginners Guide to Microprocessors & Computing	£4-95
How to build your own Metal & Treasure Locators	£1-15
How to build Advanced Short Wave Receivers	£1-35
How to build your own Solid State Oscilloscope	£1-65
ELEMENTS OF ELECTRONICS	
Book 1. The Simple Electronic Circuit & Components	£2-40
Book 2. Alternating Current Theory	£2-40
Book 3. Semiconductor Tech	£2-40
SET OF 3 BOOKS	£7-00
PRICES INCLUDE POSTAGE & PACKING.	
4 CHILCHESTER COURT, WICKHAM RD, BECKENHAM KENT BR3 2QW	

FULL REPAIR court any named T.V. £5.50, with circuits, layouts, etc., £7. (AUSW) 76 Church Street, Larkhall, Lanarks ML9 1HE.

Build your own

P.A., GROUP & DISCO SPEAKERS

by R. F. C. Stephens
Save money with this practical guide. Plans for 17 different designs, line source, I.B., Horn and Reflex types, for 8"-18" drive units. £3-95 post free (\$8 overseas).

THE INFRA-BASS LOUDSPEAKER

by G. Holliman
(full constructional details for versions using 15", 12" and 10" drive units.) £2-95 post free (\$6 overseas)

THE DALESFORD SPEAKER BOOK

by R. F. C. Stephens
This book is a must for the keen home constructor. Latest technology DIY designs. Plans for I.B., and Reflex designs for 10-100 watts. Also unusual centre-bass system. £2-20 post free (\$5 overseas).

VAN KAREN PUBLISHING

5 SWAN STREET, WILMSLOW, CHESHIRE

Record Accessories

STYLI, Cartridges for Music Centres, etc. FREE List no. 29 for S.A.E. includes Leads, Mikes, Phones etc. **FELSTEAD ELECTRONICS (PW),** Longley Lane, Gatley, Cheshire. Chas. SK8 4EE.

Service Sheets

G.T. THE TECHNICAL INFORMATION SERVICE

.76 CHURCH ST., LARKHALL, LANARKS ML9 1HE

Any single service sheet for £1 and large S.A.E.

1000's of different service sheets, service manuals and repair manuals always kept in stock for immediate despatch. S.A.E. brings newsletter; pricelist; bargain offers such as service sheets under 40p; quotations for any requested service sheets/manuals without obligation. Phone 0698 883334.

Save time and money - 2 giant catalogues listing thousands of service sheets/manuals plus £4 worth of vouchers free - send £2 + large S.A.E.

SERVICE SHEETS. Radio, TV etc., 10,000 models. Catalogue 24p, plus S.A.E. with orders, enquiries. TELRAY, 154 Brook Street, Preston PR1 7HP.

BELL'S TELEVISION SERVICES for Service Sheets on Radio, TV etc., £1.00 plus S.A.E. Colour TV Service Manuals on request, S.A.E. with enquiries to B.T.S., 190 Kings Road, Harrogate, N. Yorkshire. Tel. (0423) 55885.

SERVICE SHEETS from 50p and S.A.E. Catalogue 25p and S.A.E. Hamilton Radio, 47 Bohemia Road, St. Leonards, Sussex.

30,000 SERVICE SHEETS IN STOCK COLOUR MANUALS ALSO AVAILABLE

TV Monos, Radios, Tuners £1. - Tape Recorders, Record Players, Transistors from £1.25 - Car Radios, Stereograms, Radiograms from £1.25 - Except Colour TV Circuits from £2. - State, if circuit will do, if sheets are not in stock. All TV sheets are full length 24x12", not in Bits & Pieces. All other Data full lengths. Free Fault Finding Chart or TV Catalogue with order. Crossed P.O.s returned, if sheets not in stock. S.A.E. please.

C. CARANNA

71, Beaufort Park, London NW11 6BX
01-458 4882 (Mail Order)

For Sale

SOLARTRON CD 1400 Oscilloscope. Dual Beam V.G.C. £125. Marconi U.H.F. signal generator 1700 MHz-2500 MHz £30. Brentwood 223055.

SONY 32 BAND GLOBAL RADIO 'CRF 320'. Frequency synthesizer on short wave bands with digital LED readout. Sold at £875 in shops. Available for £600 as new. Write to Mr. Withanage, 8 Cromer Mansions, Cheam Road, Sutton, Surrey.

ORGAN (Home Built) 2 x 61 note + 32 note PED. Drawstops! 01-452 9975 PAUL BANKS.

MULLARD LP1164 AM/FM I.F. Modules Guaranteed Unused, £1.50. P.P. C.W.O. S.A.E. lists. Tennex, Stock Road, Industrial Estate, Southend, Essex.

AR88D RECEIVER 5-METER MANUAL and some spare valves £40. Buyer collects. Mr. D. Clark, Hillside, Butchers Hill, Shore, Nr. Gravesend, Kent.

LOWE SAX30 with A.T.U. £100. Phone Alnwick 710004. Weekends.

NEW BACK ISSUES OF "PRACTICAL WIRELESS" available 80p each, post free. Open P.O./Cheque returned if not in stock - BELL'S TELEVISION SERVICE, 190 Kings Road, Harrogate, N. Yorks. Tel: (0423) 55885.

DECCA STEREO cassette deck model 5359. Dolby deck vortex permally head and auto stop with circuit diagram £20.00. 100 metres single screen wire 7/0. 2mm. £5.50. Pyral Maxima C90 cobalt cassettes, 10 for £8.50. Two Way TV aerial splitter £1.50. (Condenser) 1" Terry Clips. 100 for £4.00. Prices inc. VAT and UK post. SURPLELECTRONICS, 216, Leagrave Road, Luton, Beds. LU3 1JD.

Courses

COURSES - RADIO AMATEURS EXAMINATION. City & Guilds. Pass this important examination and obtain your G8 licence, with an RRC Home Study Course. For details of this and other courses (GCE, professional examinations etc) write or phone - THE RAPID RESULTS COLLEGE, DEPT. JX1, Tuition House, London SW19 4DS. Tel: 01-947 7272 (Careers Advisory Service) or for prospectus requests ring 01-946 1102 (24hr Recordcall).

Educational

CAREERS in Marine Electronics, Courses commencing September and January. Further details, The Nautical College, Fleetwood FY7 8JS. Tel. 03917 79123.

COMPUTERS

Learn to really understand computers - how they work and how they are programmed. Home study course with skilled Tutor available ensures success. No previous experience needed. Colour brochure from: -Dept. PW.

British National Radio & Electronic School.,
4 Cleveland Rd, St. Helier,
Jersey, Channel Islands.

Wanted

ELECTRONIC COMPONENTS PURCHASED. All types considered - Must be new. Send detailed list - Offer by return - WALTONS, 55A Worcester Street, Wolverhampton.

EDDYSTONE EA12 WANTED. Also recent Amateur HF Transceiver. For sale. EC 10; £55. 01-935 7119 Days.

WANTED Heathkit HFV-1 Knightkit KG687 alignment generators. 7, Firtree Road, Hastings, Sussex. Tel. 0424 427374.

PX4, PX25 and equivalent valves, new or used, plus all types of bright emitter valves, Vintage Wireless Co., (see advert on Page 82).

VALVE ENTHUSIAST wants books 1940-60 on valve theory, practice and repair, including basic maths for radio and electronics; Colebrook & Head. Radio & Electronic Lab. Handbook; Langford-Smith, Fundamentals of Electronics 1st Ed. E. N. Lurch. Also circuit diagram for Furzehill V.V.M. Type V220. J. Hadlow. 01-689 6450.

WANTED. 2 pairs of headphones 4000 OMS suitable for crystal sets. Preferably with ear piece adjustment. Also detector crystals 6. G. C. Munton, Willoughby House, 31, Church Street, Digby, Lines.

Aerials

JAYBEAM AERIALS Mail Order Service. SAE to Michael Day Ltd, Place Farm Way, Princes Risborough, Bucks.

COPPER AERIAL WIRE 14swg hard drawn 70' £3.50, 140' £7.00 inc VAT. Postage £1.75. T.M.P. Electronics, Supplies, Britannia Stores, Leeswood, Nr. Mold, N. Wales.

KILL THAT INTERFERENCE

G2DYM ANTI-T.V.I. TRAP DIPOLES:

S.W.L. Indoor models £14.50 & £27.50

S.W.L. Outdoor models £30.00 & £34.50

Tx-ing models £42.50, £52.50 & £59.75

Lists 10 x 8in 17p SAE. Aerial Guide 50p.

Indoor and invisible aerials for S.W.L.'s £3.50.

G2DYM, Uplowman, Tiverton, Devon.

EX-GOVT: Miniature Co-axial Relays 18V-28V £5.00, Large Toggle Switches D.P.D.T. £1.00, Earth Tags (x20) £0.50. M. K. SMITH (Factors Agent), 16 High Wiend, Appleby, Cumbria.

Veteran & Vintage

"SOUNDS VINTAGE"

The only magazine for all vintage sound enthusiasts, packed with articles by top writers, covering gramophones, phonographs, 78s, wireless, news, history, reviews, etc.

Bi-monthly. Annual subscription £6.00 (airmail extra). Send 75p for sample copy.

28 Chestwood Close, Billericay, Essex

Situations Vacant

MAKE YOUR HOBBY YOUR CAREER! An opportunity for a school-leaver to join London's largest independent radio-telephone company. We are looking for a trainee, preferably with G.C.E.'s in English, Maths and Physics and an interest and enthusiasm in two-way radio. Whilst working and training with us you will be given day-release at college to enable you to qualify as a radio-telephone engineer. Call or write Mike Rawlings or Bill Clarke, London Communications (Equipment) Ltd., 30 Boundary Road, St. John's Wood, London NW8. Telephone 01-328 5344.

TESTERS, Test Technicians, Test Engineers - Earn what you're really worth in London Working for a World Leader in Radio & Telecommunications. Phone Len Porter on 01-874 7281 or write - REDIFON TELECOMMUNICATIONS LTD., Broomhill Road, Wandsworth, London SW18.

UNIVERSITY OF SUSSEX SCHOOL OF ENGINEERING AND APPLIED SCIENCES ELECTRONICS TECHNICIAN

A vacancy exists in the School of Engineering and Applied Sciences for an Electronics Technician. The successful applicant will be required to assist in the teaching and research laboratories on a variety of interesting projects, should have had considerable experience with electronic circuits, preferably some experience of Teletype Servicing.

Salary on the scale £4431-£5097 pa or £4776-£5577 pa, depending on experience and qualifications.

Applications, in writing, should be addressed to:

The Laboratory Superintendent,
School of Engineering and
Applied Sciences,
University of Sussex,
Falmer, Brighton BN1 9QT.

Please mention

PRACTICAL WIRELESS

when replying

to advertisements

TRANSFORMERS

30 VOLT RANGE
Sec Voltages available 3, 5, 6, 8, 9, 10, 12, 15, 18, 20, 24, 30V or 12V-0-12V or 15V-0-15V.

Ref	Amps	Price	P & P
112	0.5	2.90	0.90
79	1.0	3.93	1.10
3	2.0	6.35	1.10
20	3.0	7.39	1.31
21	4.0	8.79	1.31
51	5.0	10.86	1.52
117	6.0	12.29	1.67
88	8.0	16.45	1.89
89	10.0	18.98	1.89
90	12.0	21.09	2.24
91	15.0	24.18	2.39
92	2.0	32.40	O.A.

50 VOLT RANGE
Sec 50V Voltages available 5, 7, 8, 10, 13, 15, 17, 20, 30, 40 or 20V-0-20V or 25V-0-25V.

Ref	Amps	Price	P & P
102	0.5	3.75	0.90
103	1.0	4.57	1.10
104	2.0	7.88	1.31
105	3.0	9.42	1.52
106	4.0	12.82	1.73
107	6.0	16.37	1.89
118	8.0	22.29	2.39
119	10.0	27.48	2.39
109	12.0	32.88	O.A.

MAINS ISOLATORS (SCREENED)
Sec 120/240 Sec 120/240V CT

Ref	VA	Price	P & P
*07	20	4.84	0.91
149	60	7.37	1.10
150	100	8.38	1.31
151	200	12.28	1.31
152	250	14.61	1.73
153	350	18.07	2.12
154	500	22.52	2.47
155	750	32.03	O.A.
156	1000	40.92	O.A.
157	1500	58.52	O.A.
158	2000	67.99	O.A.
159	3000	95.33	O.A.

*Pri 0-220-240V Sec 115 or 240V. State sec. volts required.

CASED AUTO TRANSFORMERS
240V cable in 115V USA flat pin outlet

VA	Price	P & P	Ref
20	6.55	1.03	56W
75	8.50	1.31	64W
150	11.00	1.31	49W
250	13.88	1.67	69W
500	20.13	1.89	67W
1K	30.67	2.65	84W
1500VA	42.82	O.A.	93W

Voltages stated are on full load

Continuous Ratings + VAT 15%

60 VOLT RANGE
Pri 220/240V sec 0-24-30-40-48-60V. Voltages available 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60 or 24V-0-24V or 30V-0-30V.

Ref	Amps	Price	P & P
124	0.5	4.27	1.10
126	1.0	6.50	1.10
127	2.0	8.36	1.31
125	3.0	12.10	1.31
123	4.0	13.77	2.12
40	5.0	17.42	1.89
120	6.0	19.87	2.12
121	8.0	27.92	O.A.
122	10.0	32.51	O.A.

Soldering Iron - 25W to BS spec. £1.75 P&P 30p + VAT

Solder Gun - 100W include bulb for spot on vision and joints £7.50 P&P 70p + VAT

De-Solder Pumps - Spring loaded with quick action button release for one handed working. Large £5-10 P&P 35p + VAT

Small £4-75 P&P 30p + VAT

Replacement tips Small 65p + VAT. Large 86p + VAT

ABS Plastic Boxes: inset brass nuts, slots to take PC cards (boards) flush fitting lid.

PB1	80mm x 62 x 40	80p
PB2	100mm x 75 x 40	90p
PB3	120mm x 100 x 45	£1.04
PB4	215mm x 130 x 85	£2.68

P&P 33p + VAT.

Metal Oxide Resistors 1/2W 5% TR4 (Electrosil)

390Ω/470Ω/510Ω/560Ω/820Ω/1K/1K1/1K2/1K6
1K8/2K/2K4/3K/16K/20K/22K/24K/47K/82K/100K
110K/120K/130K/180K/220K/270K/300K
£1.50/100 + VAT. in 100's only.

Antex Soldering Irons 15W & 25W £4.58 each
Safety Stand £1.75 P & P 52p each

P.W. Purbeck oscilloscope transformer 250-0-250; 6-3V; 12-9V £8.42 £1.04 (author approved)

12 OR 24V OR 12-12V
Pri 220-240 volts

Ref	12V	24V	Price	P&P
111	0.5	0.25	2.42	0.52
213	1.0	0.5	2.90	0.90
71	2	1	3.96	1.10
18	4	2	4.46	1.10
85	0.5	2.5	6.16	1.10
70	6	3	6.99	1.10
108	8	4	8.16	1.31
172	12	5	8.93	1.31
116	10	6	9.99	1.52
17	16	8	11.79	1.52
115	20	10	15.38	2.39
187	30	15	19.72	2.39
226	60	30	40.41	O.A.

SPECIAL OFFER
Multimeter 20KΩ B/V - with combined audio/L.F. test oscillator at 1 KHz and 465 KHz AC/DC to 1000 volts DC current to 500mA resistance to 1KΩ. Size 160x97x40mm
£8.50 P & P £1.00 VAT 15%.

AVO 8 MK5 £100-50

AVO TEST METERS
AVO 71 £40-80
AVO 73 £25-40
AVO MM5 minor £35-95
AVO Wee Megger £82-20
AVO T1169 in circuit transistor tester £42-60
AVO EM272 316K - Volts £63-40
AVO DA116 Digital £110-90
AVO 17 Megger £55-40
AVO Clamp Meter to 300A £59-10
All Avo Meggers and accessories available. P & P £1.32 VAT 15%

20,000 ohm/V Multimeter, mirror scale Ranges AC DC to 1000V DC current to 250mA Resistance to 3 Mohms
5" x 3 1/2" x 1 1/2" £14-36 P & P £1.00 VAT 15%

U4315 Budget Meter, 20KΩ/V Ranges to 1000V, 2.5A AC/DC 500KΩ Res. In steel case £15-85. PP £1.15 VAT 15%

NEW RANGE TRANSFORMERS
2 windings 0-36V-48V/36V-0-36V 48V-0-48V
72V or 96V

Amps	Ref	Price	P & P
1	430	4.88	0.76
2	431	8.12	0.99
3	432	13.35	1.31
4	433	16.17	1.40
5	434	20.65	1.11
6	435	29.30	2.47
8	436	36.69	O.A.
8	437	40.03	O.A.

PANEL METERS
43mm x 43mm 0.50mA £6-20
0.500mA £5-95
0.1mA £5-95
0.30V £5-95
82mm x 78mm 0.50mA £6-70
0.500mA £6-70
0.1mA £6-70
0.30V £6-70
VU ind Panel 40mm x 40mm or 48mm x 45mm 250µF fsd
VU edge SV041 centre zero 250µF £2-60
Carrage 76p VAT 15%

Send 20p stamps for Catalogue. Prices correct 31/1/1980.

SCREENED MINIATURES

Ref	mA	Volts	£	P&P	
238	200	3-0-3	2.83	0.83	
212	1A, 1A	0-6, 0-6	3.14	0.90	
13	100	9-0-9	2.35	0.44	
0.90	235	330, 330	0-9, 0-9	2.19	0.44
207	500	500	0-8-9, 0-8-9	0.05	0.85
208	1A, 1A	0-8-9, 0-8-9	3.88	0.90	
236	200, 200	0-15, 0-15	2.19	0.44	
214	300, 300	0-20, 0-20	3.08	0.90	
211	700 (DC)	20-12-0-12-20	3.75	0.90	
206	1A, 1A	0-15-20-0-15-20	6.09	1.10	
203	500, 500	0-15-27-0-15-27	4.39	1.10	
204	1A, 1A	0-15-27-0-15-27	6.64	1.10	
239	50	12-0-12	2.88	0.37	

BRIDGE RECTIFIERS
100V 25A £2.86 500V
200V 2A £0.52 PM7A6
200V 4A £0.75 12A
400V 4A £0.98
400V 6A £1.44 £3.75

END OF LINE OFFERS
Ref
30 - Isolator 240V:240V 200VA £4.62 £1.10
M616 - 0-240V: Screen 1) 13-0-13 1A £1.50 60p
2) 12V 150ma
M489 - 0-240V: 1400V-150ma, 6-3V - 4A £5.50 £1.04
M708 - 6K to 3K matching trans. 5 watt 90p 40p
M679 - 240V, 36V 1-6A £3.00 78p
M865 - 100V Line to 4 10 watts £1.90 60p
M1020 - 0-240V 12-0-12V - 50ma £1.90 30p
M1126 - 120/240V: 9-0-9V - 1A £1.79 71p

Split Bobbin Type
0-12-15-20-24-30V
Ref 009 1 Amp £2.98 P & P £1.10
Ref 010 2 Amp £4.62 P & P £1.10

15V RANGE (7 5-0-7 5V) 0-CT 15V
Ref
171 500 mA 2.30 0.52
172 1A 3.26 0.90
173 2A 3.95 0.90
174 3A 4.13 0.99
175 4A 6.30 1.10

MAINS ELIMINATORS
Plugs into 13A socket 3V = 100ma or 6, 9, 12V @ 300ma £4.60. P&P 55p + VAT


EDUCATIONAL METERS (Moving Coil)
0-10A (0-1A), 2A, 0-15V, 0-30V
Freestanding large scale easily read meters with top screw terminals for quick connections. £4.50 P&P 65p + VAT

AUTO TRANSFORMERS

Ref	VA (Watts)	£	P&P
113	15 0-115-210-240	2.73	0.81
64	75 0-115-210-240	4.41	1.10
4	150 0-115-210-240	5.89	1.10
67	500 0-115-210-240	12.09	91
84	1000 0-115-210-240	20.64	2.39
93	1500 0-115-210-240	25.81	0A
95	2000 0-115-210-240	38.31	0A
73	3000 0-115-210-240	85.13	0A
80S	4000 0-115-210-240	84.55	0A
57S	5000 0-115-210-240	98.45	0A

Step up & step down

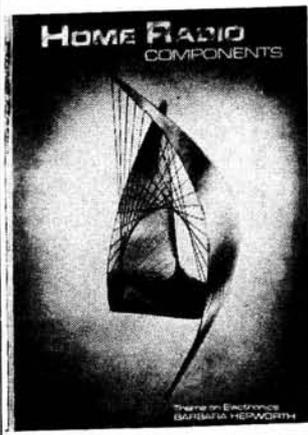Barrie Electronics Ltd.
3, THE MINORIES, LONDON EC3N 1BJ
TELEPHONE: 01-488 3316/7/8
NEAREST TUBE STATIONS ALDGATE & LIVERPOOL ST



Top Priority for every constructor - HOME RADIO CATALOGUE


- About 2,000 items clearly listed.
- Profusely illustrated throughout.
- Large A-4 size pages.
- Bargain list, order form and 2 coupons each worth 25p if used as directed, all supplied free.

Price £1, plus 50p for post, packing and insurance.
Send cheque or P.O. for £1.50

HOME RADIO Components LTD
Dept. PW, P.O. Box 92, 215 London Road, Mitcham, Surrey. 01-543 5659

JUMP TO IT!

Climb aboard the breadboarding bandwagon with CSC's new WK-1 wire jumper kit - just what you've always wanted to make breadboarding easier and quicker than ever before. Here, in one neatly compartmented box, are all those different lengths of insulated hook-up wire you need - 25 pieces of each, in 14 lengths ranging from 0.1 inch to 4 inches. What's more, the CSC kit makes your job even easier by colour-coding all the different lengths and providing a quarter-inch length at each end with the insulation stripped off and bent through 90°. So CSC jumper wires come ready to plug straight into your quick-test sockets, bus strips or breadboard system. No more fiddling around with wire cutters, strippers or pliers - everything you need in one box. Take the plunge right now by filling in the CSC coupon.

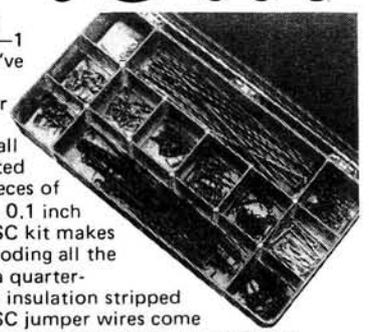

CSC (UK) Ltd. Dept. 6RR, Unit 1, Shire Hill Industrial Estate, Saffron Walden, Essex CB11 3AQ. Telephone: (0799) 21682. Telex: 817477.

WK-1 Jumper Kit £5.00 Nett. Unit price inc. P&P 15% VAT £6.90 Qty Req'd
Please deduct £1 postage from each additional order.

I enclose cheque/PO for £
or debit my Barclaycard, Access, American Express card
No Exp. date
or Tel: (0799) 21682 with your card number and your order will be in the post immediately.

NAME _____
ADDRESS _____

CONTINENTAL SPECIALTIES CORPORATION
CSC FREE catalogue tick box

Continental Specialties Corporation (UK) Limited, Dept. 6RR
Unit 1, Shire Hill Industrial Estate, Saffron Walden, Essex CB11 3AQ.

TOMORROW'S TOOLS TODAY

WATFORD ELECTRONICS

33/35, CARDIFF ROAD, WATFORD, HERTS, ENGLAND
MAIL ORDER, CALLERS WELCOME. Tel. Watford 40588/9

ALL DEVICES BRAND NEW, FULL SPEC. AND FULLY GUARANTEED. ORDERS DESPATCHED BY RETURN OF POST. TERMS OF BUSINESS: CASH/CHEQUE/P.O. OR BANKERS DRAFT WITH ORDER. GOVERNMENT AND EDUCATIONAL INSTITUTIONS OFFICIAL ORDERS ACCEPTED (TELEPHONE ORDERS BY ACCESS NOW ACCEPTED Minimum £10.00 please). TRADE AND EXPORT INQUIRY WELCOME. P & P ADD 40p TO ALL ORDERS UNDER £10.00. OVERSEAS ORDERS POSTAGE AT COST.

VAT Export orders no VAT. Applicable to U.K. Customers only. Unless stated otherwise, all prices are exclusive of VAT. Please add 15% to the total cost.

We stock many more items. It pays to visit us. We are situated behind Watford Football Ground. Nearest Underground/Br. Rail Station: Watford High Street. Open Monday to Saturday 9 a.m.-6 p.m. Ample Free Car Parking space available.

POLYESTER RADIAL LEAD CAPACITORS: 250V;
100V, 15n, 22n, 27n 6p; 33n, 47n, 68n, 100n 7p; 150n 10p; 220n, 330n 13p; 470n 17p; 680n 19p; 1µ 22p; 1µ5 30p; 2µ 34p.

ULTRASONIC TRANSDUCERS
350p per pair

ELECTROLYTIC CAPACITORS (Values are in µF).

500V: 10 50p; 47 78p; 250V: 100 65p; 63V: 0.47, 1.0, 1.5, 2.2, 3.3, 4.7, 6.8, 9p; 10, 15, 22, 33p; 32, 47, 50, 140p; 63, 100, 27p; 50V: 50, 100, 220, 470, 320, 1000 80p; 40V: 22, 33p 8p; 100 12p; 220, 330 85p; 470 115p; 35V: 10, 33 8p; 330 47 32p; 25V: 10, 22, 47, 100 8p; 160, 220, 250 15p; 470 25p; 640, 1000 35p; 1500 40p; 220 54p; 3300 77p; 4700 92p; 15V: 10, 40, 47 7p; 100, 125 8p; 220, 330 16p; 470 20p; 1000, 1500 30p; 2200 36p; 100V: 100 7p.

TANTALUM BEAD CAPACITORS
35V: 0.1µF, 0.22, 0.33, 0.47, 0.68, 1.0, 1.5, 2.2, 3.3, 4.7, 10, 20, 30, 47, 100, 220, 330, 470, 1000 20p; 15V: 2.2, 3.3, 4.7, 10, 20 8p; 5V: 2.2, 3.3, 4.7, 10, 20 8p; 10V: 15, 22, 33, 47, 100 8p; 6V: 4.7, 10, 20 8p; 3V: 100 23p.

POTENTIOMETERS: Carbon Track 0.25W Log and Linear Values.
4700, 6800 1K, 2K (Lin only) Single 29p
5K to 2M Single gang 29p
5K to 2M Single with D/P switch 69p
1K to 2M Dual gang 88p
1W Wirewound 500-20K 105p

POLYESTER (MYLAR) CAPACITORS
100V: 0.001, 0.002, 0.005, 0.01µF 6p
0.015, 0.02, 0.03, 0.04, 0.05, 0.056µF 7p
0.1µF 8p, 50V: 0.47µF 12p

CERAMIC CAPACITORS 50V
Range: 0.5pF to 10nF 4p
15nF, 22nF, 33nF, 47nF 5p 100nF 7p

POLYSTYRENE CAPACITORS:
10pF to 1nF, 8p 1.5nF to 47nF 10p.

RESISTORS—5% carbon, High Stab. Minimum, Low Noise
Range: 1-999 100-1000
0.25W 202-4M7 E24 2p 1p
0.5W 202-5M1 E12 2p 1p
1W 202-10M E12 5p 3p
2% Metal Film 10Q-1M E24 6p 4p
1% 50W 51Q-1M E24 10p 8p
N.B. 100- price applies to Resistors of each type not listed values.

VEROBOARD
0 1 0 1 0 1 5
(copper clad) (in plain)

21-34 66p 59p 47p 34p
21-5 75p 69p 39p
34-34 75p 82p 72p 63p
34-5 86p 260p 210p 178p
41-17 387p 280p
Pkt of 36 pins 20p VQ Board 144p
Spot face cutter 107p DIP Board 326p
Pin insertion tool 147p Veroblock 324p

COPPER CLAD BOARDS
Fibre Single Double SRBP
Glass sided sided 9.5" x 8.5"
6" x 6" 90p 110p 95p
6" x 12" 150p 200p

FERRIC CR25E
1lb 225p +40p p&p

SOLDERCON PINS
100 pins 60p;
500 pins 275p

DIL SOCKETS
Profile Wire
8 pin 10p 25p 2 10 way 1 156
14 pin 12p 35p 2 15 way 1 85p
16 pin 13p 46p 2 22 way 110p 120p
18 pin 16p 52p 2 25 way 149p 160p
20 pin 22p 65p 2 30 way 170p
22 pin 25p 70p 2 36 way 194p
24 pin 30p 78p 2 40 way 210p
28 pin 35p 85p 2 43 way 232p
36 pin 40p 105p
40 pin 40p 109p

EDGE CONNECTORS
2 10 way 1 156
2 15 way 1 85p
2 18 way 110p 120p
2 22 way 130p 135p
2 25 way 149p 160p
2 30 way 170p
2 36 way 194p
2 40 way 210p
2 43 way 232p

DENCO COILS
Dual Purpose 'DP'
VALVE TYPE
Ranges: 1-5 Bl. YL
Rd. Wht. R 109p
6-7 B, Y, R 95p
1-5 Green 130p
T-type (Transistor Tuning)
Ranges: 1-5 Bl. YL
Rd. Wht. 128p

JACKSONS VARIABLE CAPS.
Dielectric
100/300pF 205p
500pF 250p
6:1 Bl Drive 145p
4511/DAF
Dial Drive 4103
6:1/36:1 725p
6 Drum 54mm 55p
0-1-365pF 375p
00-2-365pF 395p
00-2-500pF 550p

EURO BOARD 520p
DALO ETCH
RESIST PEN 50p
VEROWIRING
PEN +spool 325p

LINEAR IC's
702 75 LM308T 23
709 8 pin 37 LM311H 80
710* 8 pin 67 LM324A 48
747C 14 pin 7 LM339 70
748C 8 pin 36 LM348 90
753 8 pin 185 LM349 125
813 10 pin 159 LM379 375
AY-1-0212 690 LM380 80
AY-1-1324 590 LM381 145
AY-1-1320 315 LM381AN 248
AY-1-5050 160 LM382 125
AY-1-5051 160 LM386 99
AY-1-67212 620 LM387 150
AY-3-1270 810 LM389 93
AY-3-8500 390 LM733 125
AY-8-10 850 LM1458 40
AY-5-1224A 235 LM390N 70
AY-5-1230 450 LM3909N 70
AY-5-1315 595 LM3911 125
AY-5-1317A 630 LM3914 240
AY-5-3500 510 LM3915 240
AY-5-3507A 490 LM13600 138
AY-5-4007D 638 M252AA 625
AY-5-8100 735 M253AA 1150
CA3011 110 MC1303 88
CA3014 157 MC1304P 260
CA3018 68 MC1310P 190
CA3020 186 MC1312PQ 155
CA3023 191 MC1494 595
CA3028A 80 MC1495 595
CA3035 235 MC1496L 92
CA3036 215 MC1596 225
CA3034 275 MC1710 79
CA3045 365 MC1302 150
CA3046 71 MC3340 150
CA3048 214 MC3360P 120
CA3059 170 MC3401 52
CA3075 213 MC3405 150
CA3080E 365 MC3080 97
CA3081 190 MMS303 635
CA3089E 215 MMS303 635
CA3090AQ 375 MMS307 1275
CA3123 150 MMS7160 620
CA3130 85 MMS5526 850
ICL7106 40 N513K 210
ICL7107 95 N544 185
ICL7108 95 N545 185
ICL8038CC 340 N555 22
ICM7205 1150 N555DB 55
ICM7215 1025 N560 325
ICM7216A 1065 N561 395
ICM7216B 1950 N562B 435
ICM7216C 1950 N562A 435
ICM7217A 790 N565A 120
ICM7555 89 N566 180
LD1045 452 N567V 170
LF305 90 N570 450
LM10 300 N571 214
LM10 300 N571 214
LM10 300 N571 214
LM10 300 N571 214

CMOS*
4062 995 4511 150
4063 120 4512 98
4066 58 4513 225
4067 430 4515 290
4068 26 4516 120
4069 26 4517 450
4070 30 4518 105
4071 25 4519 115
4072 25 4520 115
4073 25 4521 250
4074 25 4522 150
4075 25 4523 150
4076 25 4524 150
4077 48 4525 150
4078 30 4526 150
4079 45 4527 150
4080 28 4528 175
4081 28 4529 175
4082 28 4530 89
4083 90 4531 165
4084 90 4532 140
4085 150 4533 575
4093 89 4536 195
4094 240 4538 160
4095 105 4539 135
4096 105 4541 135
4097 350 4543 175
4098 115 4544 290
4099 80 4545 290

CMOS*
4000 18
4001 18
4002 18
4200 18

CMOS*
4000 18
4001 18
4002 18
4200 18

CMOS*
4000 18
4001 18
4002 18
4200 18

CMOS*
4000 18
4001 18
4002 18
4147 18

INDEX TO ADVERTISERS

A.D.E. Security	70
A.H. Supplies	90
A.R.R.A.	70
Amateur Electronics	70
Amateur Radio Exchange	39
Ambit International	13
Amcomms Services	78
Antex Electronics Ltd	5
Barrie Electronics	101
Bearman, Phillip	98
Bib Hi-Fi Accessories Ltd	15
Bi-Pak	16-17
Birkett, J.	92
Bowes, C.	93
Bredhurst	Cover II, 58
British National Radio & Electronics School	11, 91
Bull, J.	95
Cambridge Kits	100
Caranna C	99
Catronics Ltd	24
Chromatronics	14
Colomar (Electronics) Ltd	90
Continental Specialties Corporation	87, 101
Cox Radio (Sussex) Ltd	98
C.R. Supply Co	98
Datong Electronics	40
Doram Electronics	94
Electro-Tech	12
Electrovalue Ltd	10
Electronic Mail Order	14
Flairline	70
Garax	42
Garland	6
Gollidge Electronics P.R.	98
GMT Electronics	92
G T Technical Information Service	99
G2 Dym Aerials	99
HAC Shortwave	42
Harversons	104
Homebru Radio	42
Home Radio (components) Ltd	101
HTE Electronics	98
ICS Intertech	93
ILP Electronics	88-89, 96
Industrial Supplies	98
Intel Components Ltd	94
Interface Components	10
L.B. Electronics	14
Lee Electronics	29
Leeds Amateur Radio	58
Lowe Electronics	66
Maclin-Zand	61
Manor Supplies	92
Maplin Electronic Supplies	Cover IV
Marco Trading	6
Marshall A (London) Ltd	97
Mhel Electronics	100
Microcircuits	7
Micro Wave Modules	87
Mitrad	23
MRS Communications	40
Northern Communications	58
Osmabet	42
Partridge Electronics	40
Powell, T.	12
Progressive Radio	92
R.S.T. Valve Mail Order	14
Radio Components Specialists	103
Radiofon	24
Radio Shack	82-83
Radio Society of Great Britain	30
Riscomp Ltd (Autona)	12
R & TV Components	18
Safgan	6
Sandwell Plant	100
Science of Cambridge	8-9
Scientific Wire Company	100
Solid Stage Security	6
South Midlands Communications Ltd	77
Spectrum Communications	100
Stephen-James Ltd	24
Suretron Systems	4
Swanley Electronics	96
Tandy Corporation (UK) Ltd	2-3
Technomatic Ltd	97
Tempus	4
Thanet Electronics	Cover III
Trident Exhibition (Breadboard '80)	94
T. & T. Electronics	93
V & F Smallcraft	24
Van Karen Publishing	98
Vintage Wireless Company	99
Waters & Stanton Electronics	57
Watford Electronics	102
West Hyde Developments Ltd	30
Western Electronics	81
Williamson Amplifications	100
Wimslow Audio	4
Wintjoy Ltd	68
Wood & Douglas	30
Z. L. Communications	96

BAKER SPEAKERS "STAR SOUND"

Post
£1.50 ea.

GROUP 45-12 £15

12in. 45 watt
4, 8 or 16 ohms.

GROUP 75-12 £22

12in. 75W professional
model. 4, 8 or 16 ohms
Response 30 - 16,000.
With aluminium presence dome.

DISCO 100/12 £26

12 in 100W model
8 or 16 ohm

DISCO 100-15 £29

15in. 100 watt
8 or 16 ohms.

Send for leaflets on Disco, P.A. and Group Gear.



E.M.I. 13 1/2 x 8in SPEAKER SALE!

With tweeter. And crossover. £9.95

10W. State 3 or 8 ohm. Post £1

Illustrated 15W model £10.95

8 ohms Post £1

GOODMANS 20 Watt Woofer

Size 12 x 10in. 4 ohms. £8.50

Rubber cone surround. Post £2.00

Hi-Fi Bass unit

GOODMANS TWIN AXIOM 8


8in. 8 ohm Hi-Fi Twin Cone £9.95

Special unit 15 watts 95p



EMI MINI MODULE HI-FI KIT 3-way Loudspeaker System, EMI 5in Bass, 5in Middle, 3in Tweeter, with 3-way Crossover and Ready Cut Baffle. 15 x 8 1/2 in.

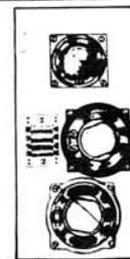Full assembly instructions supplied. Response = 60 to 20,000 cps 12 watt RMS. 8 ohm. £10.95 per kit. Two kits £20. Postage £1.50.



R.C.S. LOUDSPEAKER BARGAINS

3 ohm. 6 x 4in. £1.50. 7 x 4in. £1.50. 8 x 5in. £3.00. 6 1/2 in. £3.00. 8in. £3.50. 10in. £3.50. 12in. £4.50. 8 ohm. 2 1/2 in. £1.50. 3in. £1.50. 5in. £1.50. 10in. £3.50. 12in. £4.50. 16 ohm. 6 x 4in. £1.50. 7 x 4in. £1.50. 5in. £1.50. 8in. £3.50. 12in. £4.50. 10 x 6in. £3.50.

LOW VOLTAGE ELECTROLYTICS

1, 2, 4, 5, 8, 16, 25, 30, 50, 100, 200mF 15V 10p.
500mF 12V 15p; 25V 20p; 50V 30p;
1000mF 12V 20p; 25V 35p; 50V 50p; 1200mF/76V 80p.
2200mF 6V 25p; 25V 42p; 40V 60p.
2500mF 50V 70p; 3000mF 25V 50p; 50V 65p.
3300mF 63V £1.20; 4700mF 63V £1.20; 2700mF/76V £1.
5000mF 35V 85p.

HIGH VOLTAGE ELECTROLYTICS

8/350V 35p 8+8/450V 75p 50+ 50/300V 50p
16/350V 45p 8+16/450V 75p 32+32/450V 95p
32/500V 75p 16+16/450V 75p 100+100/275V 65p
50/350V 80p 32+32/350V 50p 150+200/275V 70p
50/500V £1.20 50-50/500V £1.80 220/450V 95p
MANY OTHER ELECTROLYTICS IN STOCK

SHORT WAVE 100pf air spaced gangable tuner, 95p.
TRIMMERS 10pF, 30pF, 50pF, 5p, 100pF, 150pF, 15p.
CERAMIC, 1pF to 0.01mF, 5p. Polystyrene 2 to 5000pF, 5p.
PAPER 350V-0.1 7p; 0.5 15p; 1mF 150V 20p; 2mF 150V 20p
400V-0.001 to 0.05 5p; 0.1 15p; 0.25 25p; 0.47 35p.
MICRO SWITCH SINGLE POLE CHANGE OVER 20p.
SUB-MIN MICRO SWITCH. 25p. Single pole change over.
TWIN GANG, 385pF £1; 365pF £1; 365 + 365 + 25 + 25pF.
Slow motion drive £1; 120pF 50p; 3 gang 365pF £2.
120pF TWIN GANG, 50p; 365pF TWIN GANG, 75p.
TWIN GANG 25p slow motion 95p
NEON PANEL INDICATORS 250V. Amber or red 30p.
ILLUMINATED ROCKER SWITCH. Single pole. Red 65p.
RESISTORS. 10Ω to 10M. 1W, 1/2W, 1W, 20% 2p; 2W, 10p.
HIGH STABILITY. 1/2W 2% 10 ohms to 1 meg., 12p.
Ditto 5%. Preferred values 10 ohms to 10 meg., 5p.
RELAYS. 12V DC 85p. 6V DC 85p. 240V AC 95p.
BLANK ALUMINIUM CHASSIS. 6 x 4-95p; 8 x 6-£1.40; 10 x 7-£1.55; 12 x 8-£1.70; 14 x 9-£1.90; 16 x 6-£1.85; 16 x 10-£2.20. ANGLE ALI. 6 x 2 x 1in.-25p.
ALUMINIUM PANELS. 6 x 4-24p; 8 x 6-38p; 14 x 3-40p; 10 x 7-54p; 12 x 8-70p; 12 x 5-44p; 16 x 6-70p; 14 x 9-94p; 12 x 12-£1.16; 16 x 10-£1.46.
PLASTIC AND ALI BOXES IN STOCK. MANY SIZES
EG Black plastic construction box with brushed aluminium fascia size 6 1/2 x 2 1/2 £1.50
CASSETTE MECHANISM. Stereo heads with motor £5.00.
BRIDGE RECTIFIER 200V PIV 1/2 amp 50p. 2 amp £1.00.
4 amp £1.50. 8 amp £2.50.
TOGGLE SWITCHES SP 30p. DPST 40p. DPDT 50p.
MANY OTHER TOGGLES IN STOCK. Please enquire.
PICK-UP CARTRIDGES ACOS, GP91 £2.00. GP94 £2.50.
SONOTONE 9TAHC Diamond £3.75. Magnetics £7
WIRE-WOUND RESISTORS 5 watt, 10 watt, 15 watt 15p.
CASSETTE MOTOR. 6 volt £1.00.

MAINS TRANSFORMERS

Post

6V, 500mA £2.00 6-0-6V 100mA £1.80
12V, 100mA £1.30 9-0-9V 50mA £1.50
12V, 750A £1.75 12V, 3 amp £3.50
10-0-10V 2amp £3.00 10V, 30V, 40V, 2 amp £3.50
30V, 5 amp and £3.00 2 of 25V, 1 amp £5.00
17V-0-17V, 2 amp £4.00 20V, 1 amp £3.00
0, 5, 8, 10, 16V, 1/2 amp £2.50 20V-0-20V, 1 amp £3.50
9V, 3 amp £3.50 2 of 18V, 6 amp, each £11.00
15-0-15V 2 amp £3.00 12-0-12V, 2 amp £3.50
30V, 2 amp £3.50 9V, 1/2 amp £1.50
30V, 1/2 amp £3.30 28V, 1 amp+28V 1 amp £5.00
20V, 40V, 60V, 1 amp £4.00 32-0-32V 6-5A £11.00
P-P 50p Access-Barclay-Visa. Lists 20p. Closed Wed.

Radio Components Specialists

337 WHITEHORSE ROAD
CROYDON, SURREY, U.K. TEL. 01-684 1665



WESTERN MAGAZINE

**For the very first time
legend teams up
with reality**

The West as it really was. And the West as you've always enjoyed it. What a magnificent combination!

Now, at long last, here's a magazine that's packed with new stories written by best-selling Western authors and illustrated by top Western artists—plus the raw truth that lies behind the fiction.

Thrill to the explosive action, gory gunfights, cattle stampedes, jaw-crunching saloon riots, smouldering passion and Indians on the war path...

Read about real people and real events—crazy pioneers, lonesome cowhands, crooked lawmen, blood-lusting Indians and fun-loving dance-hall girls...

DON'T MISS YOUR COPY!



SUPERSOUND 13 HI-FI MONO AMPLIFIER

A superb solid state audio amplifier. Brand new components throughout. 5 silicon transistors plus 2 power output transistors in push-pull. Full wave rectification. Output approx. 13 watts r.m.s. into 8 ohms. Frequency response 12Hz-30KHz \pm 3db. Fully integrated pre-amplifier stage with separate Volume, Bass boost and Treble cut controls. Suitable for 8-15 ohm speakers. Input for ceramic or crystal cartridge. Sensitivity approx. 40mV for full output. Supplied ready built and tested, with knobs, escutcheon panel, input and output plugs. Overall size 3" high \times 6" wide \times 7 1/2" deep. AC 200 250V. PRICE £18.40, P. & P. £1-60.

HARVERSONIC MODEL P.A. TWO ZERO

An advanced solid state general purpose mono amplifier suitable for Public Address system, Disco, Guitar, Gram, etc. Features 3 individually controlled inputs (each input has a separate 2 stage pre-amp). Input 1, 15mV into 47k. Input 2, 15mV into 47k (suitable for use with mic. or guitar etc.). Input 3, 200mV into 1 meg. suitable for gram, tuner, or tape etc. Full mixing facilities with full range bass & treble controls. All inputs plug into standard jack sockets on front panel. Output socket on rear of chassis for an 8 ohm or 16 ohm speaker. Output in excess of 30 watts music power. Very attractively finished purpose built cabinet made from black vinyl covered steel with a brushed anodised aluminium front escutcheon. For ac mains operation 200/240 volts. Size approx. 12 1/2" wide \times 5 1/2" high \times 7 1/2" deep. Special price £29.00 + £3.00 carriage and packing.



MAINS OPERATED SOLID STATE AM/FM STEREO TUNER




200/240V Mains operated Solid State FM AM Stereo Tuner. Covering M.W. A.M. 540-1605 KHz VHF/FM 88-108 MHz. Built-in Ferrite rod aerial for M.W. Full AFC and AGC on AM and FM. Stereo Beacon Lamp Indicator. Built in Pre-amps with variable output voltage adjustable by pre-set control. Max o/p Voltage 600mV RMS into 20K. Simulated Teak finish cabinet. Will match almost any amplifier. Size 8 1/4" w \times 4" h \times 9 1/4" d approx.

LIMITED NUMBER ONLY at £29.00 + £2.00 P. & P.

10/14 WATT HI-FI AMPLIFIER KIT

A stylishly finished monaural amplifier with an output of 14 watts from 2 EL84s in push-pull. Super reproduction of both music and speech with negligible hum. Separate inputs for mike and gram allow records and announcements to follow each other. Fully shrouded section wound output transformer to match 3-15 Ω speaker and 2 independent volume controls, and separate bass and treble controls are provided giving good lift and cut. Valve line-up 2 EL84s, ECC83, EF86 and EZ80 rectifier. Simple instruction booklet 50p + SAE (Free with parts). All parts sold separately. ONLY £18.40, P. & P. £2.00. Also available ready built and tested £22.50, P. & P. £2.00.

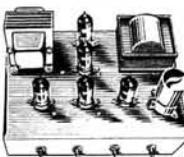

HARVERSONIC SUPERSOUND 10 + 10 STEREO AMPLIFIER KIT

A really first-class Hi-Fi Stereo Amplifier Kit. Uses 14 transistors including Silicon Transistors in the first five stages on each channel resulting in even lower noise level with improved sensitivity. Integral pre-amp with Bass, Treble and two Volume Controls. Suitable for use with Ceramic or Crystal cartridges. Very simple to modify to suit magnetic cartridge—instructions included. Output stage for any speakers from 8 to 15 ohms. Compact design, all parts supplied including drilled metalwork, high quality ready drilled printed circuit board with component identification clearly marked, smart brushed anodised aluminium front panel with matching knobs, wire, solder, nuts, bolts—no extras to buy. Simple step by step instructions enable any constructor to build an amplifier to be proud of. Brief specification: Power output: 14 watts r.m.s. per channel into 5 ohms. Frequency response: \pm 3dB 12-30,000 Hz Sensitivity: better than 80mV into 1M Ω ; Full power bandwidth: \pm 3dB 12-15,000 Hz. Bass boost approx. to \pm 12dB. Treble cut approx. to -16dB. Negative feedback 18dB over main amp. Power requirements 35v. at 1.0 amp. Overall Size 12" w. \times 8" d. \times 2 1/2" h. Fully detailed 8 page construction manual and parts list free with kit or send 50p plus large S.A.E. AMPLIFIER KIT £14.95 P. & P. £1-20 (Magnetic input components 33p extra) POWER PACK KIT £6-20 P. & P. £1-50 CABINET £6-20 P. & P. £1-50 SPECIAL OFFER—only £25.80 if all 3 items ordered at one time plus £2.80 P. & P. Full after sales service Also avail. ready built and tested £32.20, P. & P. £2.80.

HARVERSONIC STEREO 44

A solid state stereo amplifier chassis, with an output of 3-4 watts per channel into 8 ohm speakers. Using the latest high technology integrated circuit amplifiers with built in short term thermal overload protection. All components including rectifier smoothing capacitor, fuse, tone control, volume controls, 2 pin din speaker sockets & 5 pin din tape rec. play socket are mounted on the printed circuit panel, size approx. 9 1/2" \times 2 1/2" \times 1" max. depth. Supplied brand new & tested, with knobs, brushed anodised aluminium 2 way escutcheon (to allow the amplifier to be mounted horizontally or vertically) at only £10.40 plus 90p P. & P. Mains transformer with an output of 17v a/c at 500mA can be supplied at £2.15 + 70p P. & P. if required. Full connection details supplied.

All prices and specifications correct at time of press and subject to alteration without notice.

PLEASE NOTE: P. & P. CHARGES QUOTED APPLY TO U.K. ONLY. SEND SAE WITH ALL ENQUIRIES.

"POLY PLANAR" WAFER-TYPE, WIDE RANGE ELECTRO-DYNAMIC SPEAKER

Size 11 1/2" \times 14 1/2" \times 1 1/2" deep. Weight 19oz. Power handling 20W r.m.s. (40W peak). Impedance 8 ohm only. Response 40Hz-20KHz. Can be mounted on ceilings, walls, doors, under tables, etc., and used with or without baffle. Send S.A.E. for full details. Only £8.80 each + p. & p. (one £1-20, two £1-50).

STEREO MAGNETIC PRE-AMP. Sens. 3mV in for 100mV out. 15 to 35V neg. earth. Equ. \pm 1dB from 20Hz to 20KHz. Input impedance 47K. Size 1 1/2" \times 2 1/2" \times 1 1/2" H. £3-20 + 22p P. & P.


STEREO DECODER MK.II SIZE 1 1/2" \times 2 1/2" \times 1 1/2" ready built. Pre-aligned and tested for 10-16V neg. earth operation. Can be fitted to almost any FM VHF radio or tuner. Stereo beacon light can be fitted if required. Full details and instructions supplied £7.00 plus 25p P. & P. Stereo beacon light if required 40p extra.

Mullard LP1159 RF IF module 470KHz £2.50 + P. & P. 40p. Full specification and connection details supplied. Pye VHF FM Tuner Head covering 88-108MHz 10-7 MHz I.F. output. 7.8V + earth. Supplied pre-aligned, with full circuit diagram with precision geared F. gang and 323PF + 323PF A.M. Tuning gang only £3.40 + P. & P. 60p.

MAINS TRANSFORMERS. 240V Pri. 12.0-12.4 at 400 Ma. Fully shrouded. Size approx. 1 1/2" H \times 1 1/2" D \times 2" L. £2.00 + 60p P. & P. MAINS TRANSFORMER. Pri. 0-110-240. Sec. 28V at 1.8 amps. Also tapped at 12V 300 Ma. Size 2 1/2" H \times 3 1/2" W \times 2 1/2" D. £2.75 + £1-20 P. & P.

HARVERSON SURPLUS CO. LTD. (Dept. P.W.) 170 MERTON HIGH ST., LONDON, S.W.19. Tel.: 01-540 3985
A few minutes from South Wimbledon Tube Station. Open 9.30-5.30 Mon. to Fri. 9.30-5 Sat. Closed Wed.

Published on approximately the 7th of each month by IPC Magazines Limited, Westover House, West Quay Road, POOLE, Dorset BH15 1JG. Printed in England by Chapel River Press. Andover, Hants. Sole Agents for Australia and New Zealand—Gordon and Gotch (Asia) Ltd.; South Africa—Central News Agency Ltd. Subscriptions INLAND and OVERSEAS £10.60 payable to IPC Services, Oakfield House, Perryman Road, Haywards Heath, Sussex. PRACTICAL WIRELESS is sold subject to the following conditions, namely that it shall not, without the written consent of the Publishers first having been given, be lent, resold, hired out or otherwise disposed of by way of Trade or more than the recommended selling price shown on the cover, excluding Hire where the selling price is subject to V.A.T. and that it shall not be lent, resold, hired out or otherwise disposed of in a mutilated condition or in any unauthorised cover by way of Trade or affixed to or as part of any publication or advertising, literary or pictorial matter whatsoever.

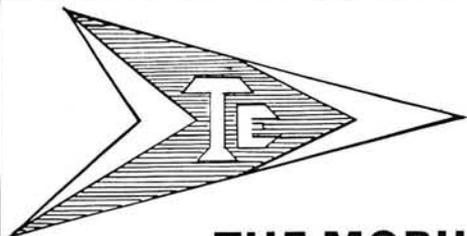

THE MOBILE/PORTABLE CHECKLIST:—

IC240	The most popular, simplest to operate, synthesized 10w – 2m – FM mobile ever made	★ £169 INC VAT
IC255E	The 25w, digital, synthesized, 2m – FM mobile for the man that wants just a little more. Now with improved receiver and scanning mic available	★ £255 INC VAT
IC260E	The 10w, multimode, synthesized, digital, 2m mobile for the man that wants even more again! ★ Scanning mic now available.	★ £339 INC VAT
IC2E	The smallest, synthesized, 2m – FM, hand-portable available	★ £159 INC VAT
IC202S	The <i>BEST</i> SSB/CW, 3w-2m, portable made	★ £169 INC VAT
IC402	The <i>ONLY</i> SSB/CW, 3w-70cm portable made	★ £242 INC VAT

Note all our prices include VAT, some dealers prefer to show the lower VAT-less prices – so don't get caught out.

We offer FREE DELIVERY for all equipment tool.

ANNOUNCING A NEW COMMUNICATIONS COMPUTER!



£640 inc.

The new THETA 7000E means that every Amateur can enjoy the visual display of CW, RTTY, and ASCII in both transmit and receive modes. Just connect the TONO to any TV set via the antenna terminals or to a page printer from the parallel port provided. Bring up your CW speed in receiving or sending by either watching receiver sent or from recorded cassettes. Connection to the transceiver is via the key, phone and mic sockets.

Some of the Outstanding Features

COMMUNICATIONS COMPUTER THETA 0-7000E

VHF and Composite Video Output Provided
Printer interface ★ Wide range of transmitting and

Theta 7000E

receiving speeds – 10CW speeds + 8RTTY ★ Built-in demodulator for high performance for 170, 425 and 820 Hz shift ★ Crystal controlled modulator for AFSR – Hi or Lo tone ★ Convenient ASCII key arrangement ★ Large capacity display memory – 2 pages 32 chr × 16 lines split screen for Rx & Tx if required ★ Automatic transmit/receive switch ★ Anti noise circuit ★ Battery backed-up memory 7 channels of 64 chrs ★ Send function ★ Buffer memory – 53 character type ahead, rub out function ★ Simultaneous access of the memory ★ Pre-loading function ★ CR (carriage return) LF (line feed) cancel function ★ Cursor control function ★ Word mode operation ★ Automatic CR/LF (72, 60 or 80 chrs per line) ★ Echo function ★ Word Wrap around function ★ Transmit/receive in ASSC11 mode in RTTY ★ CW identification function ★ Mark and break (space and break) system ★ Monitor circuit ★ CW practice function ★ Variable CW weights ★ Cross pattern checking output terminal ★ Log computer output provided ★ Test message function (Ry and QBF).


Dot Printers, Monitors, Receive Only Units now available. Please ask for details.

BARCLAYCARD

VISA

THANET ELECTRONICS

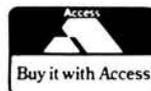143 Reculver Road, Beltinge, Herne Bay, Kent (02273 63859)



MAPLIN

announce the opening of their new LONDON shop

259-261
King St.
Hammersmith
London W6
01-748 0926



- Excellent metered parking
- Close to Hammersmith Underground Station for Piccadilly, District & Metropolitan Lines
- Bus no's 260·266·704·27·91 267·290 stop outside



Opens Tuesday 16th September, 1980


Opening Hours 9.45 am to 5.30 pm Tuesday to Saturday (Closed Monday)

**Maplin mail-order —
Now better than ever!**

- * Up to 8% discount for use with next order
- * All prices include VAT
- * Same day service on in-stock lines
- * Over 95% of our stock lines in stock
- * Large range of all the most useful components
- * First class reply paid envelope with every order
- * Quality components — no rejects — no re-marks
- * Competitive prices
- * Your money is safe with a reputable Company

On price, service, stock, quality and security, it makes sense now more than ever to make **Maplin** — your first choice for components every time!

Stereo Cassette Tape Deck

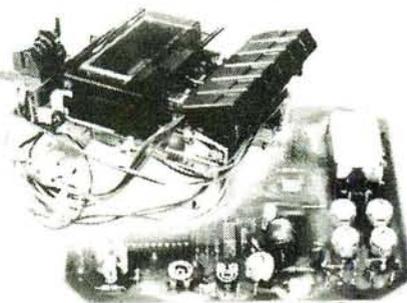

Utilising the superb JVC deck made for Tandberg and a ready-made pre-aligned, tested and guaranteed module, this cassette deck has a superb sound and a high quality specification. We've got everything you need (except cabinet) including full instruction leaflet for only £39.95. Order as XY36P (Cassette Recorder Kit)

Space Invaders

Fight the space invaders, be a polaris captain or a spaceship commander. Full colour action on your own TV set and over 450 games to play.

Basic console with Combat cartridge (AC00A) £99.50 + £2.50 carriage

All cartridges available including:

Space Invaders (AC26D)	£29.95	Adventure (AC22Y)	£23.95
Indy 500 (AC24B)	£34.50	Skydiver (AC13P)	£16.95
Chess (8levels) (AC28F)	£34.50	Breakout (AC05F)	£16.95
Golf (9holes) (AC18U)	£16.95	Slot Racers (AC19V)	£16.95
Air Sea Battle (AC01B)	£16.95	Programming (AC27E)	£34.50
Space War (AC02C)	£16.95	Olympics (AC04E)	£16.95
Brain Games (AC16S)	£16.95	Street Racer (AC14Q)	£16.95
Outlaw (AC03D)	£16.95	Keyboards per pair (AC29G)	£11.95

All prices include VAT and carriage except where shown.

Post this coupon now for your copy of our 1979-80 Catalogue price 70p

Please send me a copy of your 280 page catalogue. I enclose 70p (plus 46 p.p.p.) If I am not completely satisfied I may return the catalogue to you and have my money refunded. If you live outside the U.K. send £1.35 or ten International Reply Coupons. I enclose £1.16.

Name: _____

Address: _____

PW. 11.80

MAPLIN

Maplin Electronic Supplies Ltd

All mail to: P.O. Box 3, Rayleigh, Essex SS6 8LR.
Telephone: Southend (0702) 554155.

Shop: 284 London Road, Westcliff-on-Sea,
Essex. (Closed on Monday)
Telephone: Southend (0702) 554000.



Catalogue now available in all branches of WHSMITH Price £1.00