

FOR THE RADIO ENTHUSIAST ...

Practical Wireless

APRIL 1981

Australia \$1.15
New Zealand \$1.25
Malaysia \$4.00.


65p

The **Pw**

'WINTON'
STEREO TUNER


LW·MW·SW·VHF
plus TV SOUND

Part 1

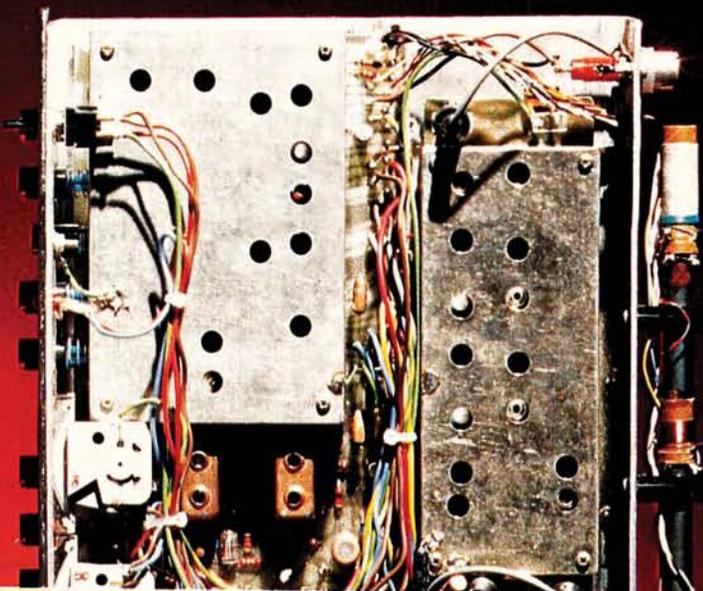

also:
BOAT ENGINE
HOURS COUNTER

MOBILE
SUPPRESSION
TECHNIQUES

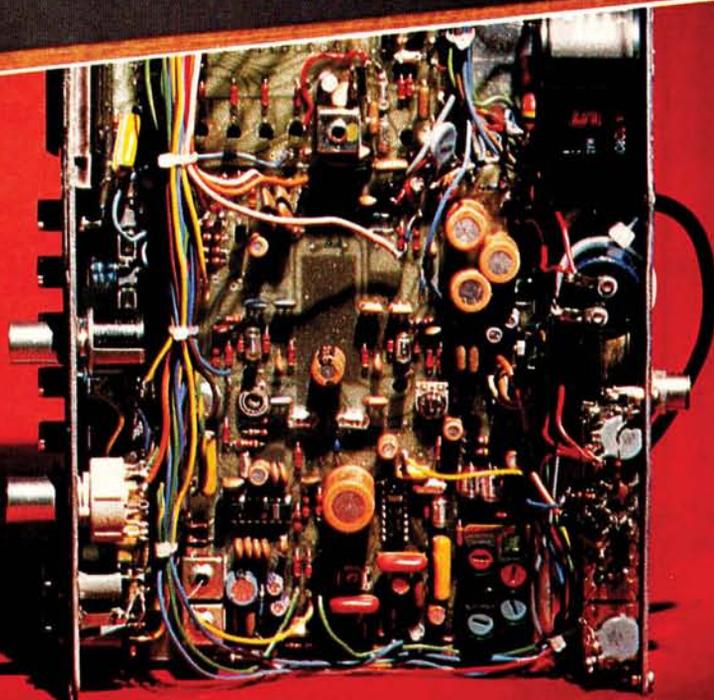

Bredhurst electronics

HIGH ST., HANDCROSS, W. SUSSEX O444 400786

TRY OUR TELEPHONE SALES SERVICE



FOR TWO METRES
ICOM
IC 2E £159
inc. VAT & CARRIAGE




FDK MULTI 700EX
£199, inc. VAT
free Delivery



YAESU FT480R
£359 inc. VAT
free Delivery

TRANSCIVERS

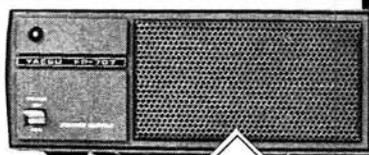


FP707
£109

H.F. (All fitted new bands)	
TRIO TS130V	£404.00
YAESU FT707S	£465.00
TRIO TS130S	£491.00
YAESU FT101Z	£488.00
YAESU FT707	£499.00
YAESU FT101ZD	£569.00
TRIO TS830S	£639.00
YAESU FT107M	£690.00



FT707
£499

HANDHELDS	
FDK PALM II	£99.00
ICOM IC2E	£159.00
FDK PALM IV	£159.00
TRIO TR2300	£166.00
AOR AR245A	£178.00
TRIO TR2400	£198.00
YAESU FT207R	£199.00

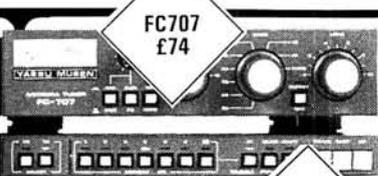

FC707
£74

2M MOBILES	
ICOM IC240 FM	£169.00
FDK Multi 700EX FM	£199.00
STANDARD C8800 FM	£250.00
ICOM IC255E FM	£255.00
TRIO TR7800 FM	£265.00
FDK Multi 750E Multimode	£299.00
ICOM IC260E Multimode	£339.00
TRIO TR9000 Multimode	£345.00
YAESU FT480R Multimode	£359.00

FV707 DM
£178

RECEIVERS



TRIO R1000
£285

H.F.	
LOWE SRX30	£158.00
YAESU FRG7	£189.00
TRIO R1000	£285.00
YAESU FRG7700	£309.00
2.M. F.M.	
SEARCH19	£45.00
A.O.R. AR22	£83.00
FDK TM50B	£79.00
BEARCAT 220FB	£258.00
MARINE V.H.F.	
SEARCH19	£45.00
FDK TM50B	£79.00
BEARCAT 220FB	£258.00



YAESU FRG7700
£309

ACCESSORIES

MORSE EQUIPMENT	
HK 707 Up/Down Key	£10.50 (£0.50) Carriage
MK 704 Squeeze paddle	£10.50 (£0.50)
EK 121 Fibreg. Antenna	£29.95 (£0.50)
EKM12 Matching side tone oscillator	£10.95 (£0.50)
EK 150 Electronic keyer	£74.00 (—)
SWR - POWER METERS	
YW 3 Twin Meter	£11.50 (£0.50)
TOYO T435 (144-435 MHz)	£34.45 (£0.75)
DAIWA SW110A (1.8-150 MHz)	£35.00 (£0.75)
WELZ SP300 (1.8-150 MHz)	£49.95 (£0.75)
WELZ SP400 (130-500 MHz)	£49.95 (£0.75)
DAIWA CN620A (1.8-150MHz)	£52.80 (—)
WELZ SP300 (1.8-500MHz)	£69.95 (—)
DAIWA CN630 (140-500MHz)	£71.00 (—)
SAFETY MICROPHONES	
ADONIS MM2025 Clip on	£20.95 (£0.50)
ADONIS MM2021H Head Band + Up/Down	£29.90 (£0.50)
ADONIS MM202FU Swan Neck + Up/Down	£30.00 (£0.50)
DAIWA RM940 infra red link	£45.00 (£0.50)
DESK MICROPHONES	
YAESU YD148 (Dual Imped)	£20.95 (£0.75)
TRIO MC50 (Dual Imped)	£24.15 (£0.75)
ADONIS AM502 Compressor Mic	£39.00 (£0.75)
ADONIS AM802 Compressor Mic 3 O/P	£59.00 (£0.75)
PROBLEMS WITH T.V.	
YAESU Low Pass Filter FF501DX (1KW)	£19.95 (£0.75)
TRIO Low Pass Filter LF30A (1KW)	£18.40 (£0.75)
HP3A High Pass Filter (TV down lead)	£3.50 (£0.25)
Ferrite Rings (Pair)	£0.80 (£0.20)

AT LAST A POWER SUPPLY WITH

Overvoltage Crowbar Protection
Current Limit with Voltage Foldback
Thermal Overload Protection

AND IT'S MADE IN THE UK!

DRAE 13-8V Power supplies.

4 amp	£27.95 (£1.50)
6 amp	£44.95 (£2.00)
12 amp	£69.00 (£2.00)
24 amp	£92.00 (£3.00)

N.B. These are prices for Fully Protected British power supplies.

MOBILE ANTENNAE (All with PL259 fitting)	
14 MHz 1/4 (20SE)	£13.80 (£1.50) Carriage
21 MHz 1/4 (15SE)	£11.50 (£1.50)
28 MHz 1/4 (10SE)	£11.50 (£1.50)
144 MHz 1/4 (6dB)	£1.50 (£0.50)
144 MHz 5/8 (5dB)	£8.50 (£1.50)
144 MHz 7/8 (4.5dB)	£13.00 (£1.50)
432 MHz 2 5/8 (5-5dB)	£11.50 (£1.00)
CABLE MOUNT	£3.50 (£0.50)
GUTTER CLIP	£3.50 (£0.50)
MAGNETIC MOUNT	£6.95 (£0.50)
BOOT LIP MOUNT	£3.50 (£0.50)
MICROWAVE MODULES	
MMC 144/28 converter	£27.90 (£0.75)
MMC 432/28 converter	£34.90 (£0.75)
MMC 432/144S converter	£34.90 (£0.75)
MMC 1296/28 23cm converter	£32.20 (£0.75)
MMC 1296/144 23cm converter	£59.80 (£1.00)
MMT 144/28 transverter	£99.00 (£1.00)
MMT 432/28 transverter	£149.00 (£1.00)
MMT 432/144R transverter	£184.00 (£1.00)
MMT 1296/144 transverter	£184.00 (£1.00)
MML 144/25 linear	£59.00 (£0.75)
MML 144/40 linear	£77.00 (£0.75)
MML 144/100P linear	£142.60 (£1.00)
MML 432/20 linear	£77.00 (£1.00)
MML 432/50 linear	£119.00 (£1.00)
MML 432/100 linear	£228.00 (£1.00)
MMD 50/500 500 MHz counter	£69.00 (£0.75)
MMA28 10M Preamp	£14.95 (£0.75)
MMA 144V Preamp RF switched	£34.90 (£0.75)



MAIL ORDER - RETAIL CALLERS 9-5.30 PM.
HIGH ST., HANDCROSS, W. SUSSEX. 0444 400786



TO ORDER ANY OF THE ABOVE ITEMS SIMPLY WRITE, ENCLOSING A CHEQUE OR PHONE YOUR CREDIT CARD NUMBER

EDITORIAL OFFICES
Practical Wireless
Westover House
West Quay Road
Poole, Dorset BH15 1JG
☎ Poole 71191

Geoff Arnold G3GSR
Editor

Dick Ganderton C.Eng., MIERE, G8VFN
Assistant Editor

Peter Metalli
Art Editor

John Fell G8MCP
Technical Editor

Alan Martin G8ZPW
News & Production Editor

Elaine Howard
Technical Sub-Editor

Rob Mackie
Technical Artist

Keith Woodruff
Assistant Art Editor

Sylvia Barrett, Sharron Breeze
Secretarial

ADVERTISEMENT OFFICES
Practical Wireless
King's Reach Tower
Stamford Street
London SE1 9LS
Telex: 915748 MAGDIV-G

Dennis Brough
Advertisement Manager
☎ 01-261 6636

Roger Hall G8TNT (Sam)
Ad. Sales Executive
☎ 01-261 6807

Claire Gerrish
Secretary
☎ 01-261 6636

Colin R. Brown
Classified Advertisements
☎ 01-261 5762

Dave Kerindi
Make-up & Copy
☎ 01-261 6570

COPYRIGHT

© IPC Magazines Limited 1981. Copyright in all drawings, photographs and articles published in *Practical Wireless* is fully protected and reproduction or imitation in whole or in part is expressly forbidden. All reasonable precautions are taken by *Practical Wireless* to ensure that the advice and data given to our readers are reliable. We cannot however guarantee it and we cannot accept legal responsibility for it. Prices are those current as we go to press.

Practical Wireless

APRIL 1981 VOL. 57 NO. 4 ISSUE 889

contents

- 24 **Dear Sir . . .**
H. A. Crookes
- 25 **Kindly Note**
Beginners 2m Converter, Sep. 80. *PW* "Sherborne," Nov. 80.
PW "Twynham," Jan. 81. Tape/Slide Controller, Jan. 81.
Active Receiving Antenna, Mar. 81. Frequency Allocation
Chart, Mar. 81
- 26 **Audio Power Amplifiers—3**
M. J. Darby
- 31 **IC of the Month—SL6310C Audio Amplifier**
Brian Dance
- 38 ***PW* "Helford" HF SSB Transceiver—6**
Vic Goom G4AMW
- 44 **Mobile Suppression Techniques—1**
John M. Fell G8MCP
- 51 ***PW* "Winton" Stereo Tuner—1**
E. A. Rule
- 67 **Air Test**
Microwave Modules MM2000 RTTY/TV Converter
HF-60 Frequency Counter
AR-245 2m Hand-held
- 70 **Boat Engine Hours Counter**
F. C. Judd

Please see page 56 for a special
announcement regarding the *PW*
"Winton" Stereo Tuner

- | | | | |
|-----|-----------------|----|------------------|
| 103 | Advert Index | 33 | News |
| 19 | Comment | 37 | Next Month |
| 31 | IC of the Month | 74 | On the Air |
| 62 | In Control | 20 | Production Lines |
| 25 | Kindly Note | 88 | RAE Reprint |
| 34 | Letters | 19 | Services |
| 61 | Mods | 23 | Uncle Ed |

THE SHIMIZU SS105S *80-10 metres ssb/cw transceiver*



This super new transceiver covers 80-10 metres, gives 10W out and is smaller than anything else we have seen so far. Ideal for transverter driving, the SS105S has FM transmit and receive options as well as excellent performance on SSB/CW for HF band use. The SS105S is supplied in semi kit form so as to keep down the price, but all the RF and mixer boards are ready built and aligned so no test equipment is required. All the cabinet work has been carried out so all you have to do is assemble the IF strip, xtal oscillator, and fit them to the completed chassis. Great idea and it brings back the flavour of home brew with the added advantage that the rig will work when you've finished it. For more info, just ask us or come along and see it. It's a great little rig.


		NETT.	inc. VAT	CARR.
SS105S	80-10m solid state SSB/CW/FM transceiver. Semi kit form	225.00	258.75	4.50
SE-NB	Noise blanker kit	6.75	7.76	.50
SE-FMrx	RX FM discriminator kit	15.00	17.25	1.00
SE-FMtx	TX FM generator kit	11.00	12.65	1.00
SE-MK	RX marker kit	9.60	11.04	.50
0.5 CWF	500 Hz CW filter	19.50	22.43	.50
Optional band crystals		3.00	3.45	.25

AR 245 *2 metre hand held synthesized 144-146 5/1 watt.*

AR 240A *2 metre hand held synthesized 144-146 1½ watt.*

AR 245 £178 inc. VAT. AR 240A £158 inc. VAT. Carriage £1.50.

CORDLESS INFRARED MOBILE MIKE

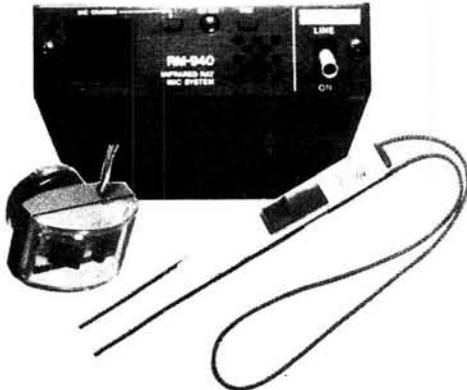

The Daiwa infrared mike system, comprising of a control box, sensor and infrared mike enables you to dispense with the hand mike and cable when operating in your car or shack. By using an infrared beam audio is transmitted from the mike to the sensor and then to the control box which activates the transmitter. To transmit, press the locking switch on the mike and talk. To receive, release the switch and your rig immediately returns to receive. When you have finished your contact return the mike to its slot in the control box and the mike nicad battery is maintained at full charge. For those of you who like fresh air and drive with all windows open there is a matching wind shield available at an additional 75p. So there we are, the latest in technology to bring safety to your mobile operation, the Daiwa infrared mike.

DAIWA INFRARED MIKE SYSTEM
£45.00 inc. VAT.
 Carriage £1.50.



FREQUENCY COUNTER *Model HFC 55.*

The HFC55 is a sensibly priced, easy to use digital frequency meter covering 10 kHz-55 MHz in a single range. The bright 5 digit display gives a direct reading of frequency when the built in telescopic aerial is placed near a source of RF. The HFC 55 operates from internal dry batteries and is housed in a strong metal case to withstand regular and continuous use.

HFC55 Frequency Counter £36.50 inc. VAT. Carriage £1.50

POWER SUPPLY UNITS

the PP1305 4 amp 13.8 volts d.c. £18.40 inc. VAT.

the PP137 7 amp 13.8 volts d.c. £32.00 inc. VAT.

the PP1310 10 amp 13.8 volts d.c. £49.50 inc. VAT.

Carriage £2.00.



**LOWE
ELECTRONICS LTD**

CHESTERFIELD ROAD, MATLOCK, DERBYSHIRE. Tel. 0629/2817.





pacesetter in amateur radio

TR-9000 *compact rig with FM/SSB/CW, scan and 5 memories.*

The TR-9000 combines the convenience of FM with long distance SSB and CW. It is extremely compact . . . perfect for mobile operation. Matching accessories are available for optimum fixed-station operation.

TR-9000 FEATURES:

- FM, USB, LSB, and CW.
- Only 6-11/16 inches wide, 2-21/32 inches high, 9-7/32 inches deep.
- Two digital VFOs.
- Digital frequency display.
- Covers 144-146 MHz.
- SSB/CW search of selectable 9.9-kHz bandwidth segments.
- Five memories.
- UP/DOWN microphone (standard) for manual band scan.
- Noise blanker for SSB and CW.



SP-120

TR-9000

BO-9

PS-20

- RIT (receiver incremental tuning) for SSB and CW.
- RF gain control.
- CW sidetone.
- Selectable RF power output . . . 10 W (HI)/1 W (LO).
- Mobile mounting bracket with quick-release levers.
- LED indicators . . . ON AIR, BUSY, and VFO.

OPTIONAL ACCESSORIES:

- PS-20 fixed-station power supply.
- SP-120 fixed-station external speaker.
- BO-9 System Base . . . with power switch, memory-backup power supply, and headphone jack.

TR-9000 £345 inc. VAT.

Securicor carriage £4.50.

R-1000

*hear, there and everywhere
easy tuning, digital display.*



The R-1000 is an amazingly easy-to-operate, high-performance, communications receiver, covering 200 kHz to 30 MHz in 30 bands. This PLL synthesized receiver features a digital frequency display and analog dial, plus a quartz digital clock and timer.

R-1000 FEATURES:

- Covers 200 kHz to 30 MHz continuously.
- 30 bands, each 1 MHz wide.
- Five-digit frequency display with 1-kHz resolution and analog dial with precise gear dial mechanism.
- Built-in 12-hour quartz digital clock with timer to turn on radio for scheduled listening or control a recorder through remote terminal.
- Step attenuator to prevent overload.
- Three IF filters for optimum AM, SSB, CW. 12-kHz and 6-kHz (adaptable to 6-

kHz and 2.7-kHz) for AM wide and narrow, and 2.7-kHz filter for high-quality SSB (USB and LSB) and CW reception.

- Effective noise blanker.
- Terminal for external tape recorder.
- Tone control.
- Built-in 4-inch speaker.
- Dimmer switch to control intensity of S-meter and other panel lights and digital display.
- Wire antenna terminals for 200 kHz to 2 MHz and 2 MHz to 30 MHz. Coax terminal for 2 MHz to 30 MHz.

R-1000 receiver £285.20
inc. VAT. **Matching speaker**

£26.45 inc. VAT.

Securicor carriage £4.50.

TR-7800 *the only 2 metre FM mobile transceiver.*

Frequency selection with the TR-7800 2-metre FM mobile transceiver is easier than ever. The rig incorporates new memory developments for repeater shift, priority, and scan.

TR-7800 FEATURES:

- 15 multifunction memory channels, selected with a rotary switch. M0 to M12 . . . memorize frequency and offset (\pm 600 kHz or simplex). M13 and 14 . . . memorize transmit and receive frequencies independently for non-standard offset.
- Internal backup for all memories, by installing four AA NiCd batteries (not supplied) in battery holder.
- Priority channel (memory "14") and priority alert.
- Covers 144-146 MHz, in 25-kHz or 5-kHz steps.
- Front-panel keyboard for selecting frequency, transmit offset, programming memories, and controlling scan.



- Automatic scan of entire band (5-kHz or 25-kHz steps) and memories.
- Manual scan of band and memories, with UP/DOWN microphone (standard).
- Repeater REVERSE switch.
- Selectable power output. 25 W (HI)/5 W (LOW).

- LED S/Rf bar meter.
- TONE switch to activate 1750 kHz repeater access tone.

TRIO TR-7800 £268 inc. VAT.

Securicor carriage £4.50.

HEAD OFFICE AND SERVICE CENTRE

Chesterfield Road, Matlock, Derbys. Tel. 0629 2817 or 2430.

Open Tuesday-Friday 9-5.30, Saturday 9-5.00. Closed for lunch 12.30-1.30.

For all that's best in ham radio, contact us at Matlock.

For full catalogues send 70p in stamps with your address. Mark enquiry PW.



B-P-PAK NEW EXTENDED 1981 RANGE

TRANSISTORS

AC107	25	BC107B	11	BC173	09	BC549	11	BD200	99	BF163	30	BF852	25	MPSA05	20	TIP30A	40	2N707	48	2N2714	22	2N3823	60	
AC125	30	BC107C	12	BC174	05	BC550	14	BD201	80	BF164	50	BF862	24	MPSA06	20	TIP30B	42	2N708	48	2N2904	24	(FET)	35	
AC126	22	BC108	10	BC175	35	BC551	16	BD202	80	BF165	50	BF879	28	MPSA55	20	TIP30C	44	2N711	30	2N2905A	26	2N3903	12	
AC127	22	BC108A	11	BC176	14	BC552	13	BD201-202	M/P	BF170	25	BF885	25	MPSA56	20	3P31	30	2N712	30	2N2905A	26	2N3904	12	
AC128	11	BC108B	12	BC177	14	BC553	14	BD203	80	BF171	24	BF890	25	ND120	18	TIP31A	40	2N718	25	2N2905A	26	2N3905	12	
AC128K	37	BC108C	12	BC179	14	BC559	14	BD204	80	BF172	24	BF892	25	OC19	185	TIP31B	42	2N718A	50	2N2906	18	2N3906	12	
AC132	26	BC109	10	BC180	12	BC560	10	BD204	80	BF177	24	BF930	30	OC20	1.85	TIP31C	44	2N726	29	2N2906A	20	2N4058	12	
AC141	26	BC109A	11	BC181	10	BC571	10	BD203-204	M/P	BF178	25	BF984	24	OC22	1.50	TIP32	38	2N727	29	2N2907	20	2N4059	14	
AC141K	40	BC109B	11	BC182	10	BC572	85	M/P	1.70	BF179	30	BF985	26	OC23	1.50	TIP32A	40	2N743	20	2N2907A	22	2N4060	14	
AC142	26	BC109C	12	BC183	10	BC573	85	BD205	80	BF180	30	BF986	26	OC24	1.35	TIP32B	42	2N744	20	2N2908	15	2N4061	12	
AC142K	40	BC113	16	BC183	10	BC574	85	BD206	80	BF181	30	BF987	26	OC25	1.00	TIP32C	44	2N744	20	2N2924	15	2N4062	12	
AC176	24	BC114	17	BC183L	10	BC570	14	BD207	80	BF182	30	BF988	26	OC26	1.00	TIP41A	44	2N718	30	2N2925	15	2N4220	10	
AC176K	40	BC115	18	BC184	10	BC571	15	BD208	80	BF183	30	BF990	55	OC28	90	TIP41B	46	2N929	20	2N2926G	10	(FET)	35	
AC187	25	BC116	19	BC184L	10	BC572	15	BD222	47	BF184	22	BF950	20	OC29	95	TIP41C	48	2N930	18	2N2926Y	09	2N4284	28	
AC187K	40	BC116A	20	BC186	15	BC210	70	BD225	47	BF185	22	BF951	20	OC35	95	TN82	44	2N946	40	2N2926Y	09	2N4285	28	
AC188	40	BC117	19	BC187	18	BC211	70	BD232	85	BF187	26	BF952	20	OC36	90	TIP42B	46	2N1131	24	2N2926Y	09	2N4285	28	
AC188K	40	BC118	17	BC207	11	BC212	70	BD233	55	BF187	26	BF953	20	OC41	20	TIP42C	48	2N1132	24	2N2926B	09	2N4287	28	
ACY17	50	BC119	29	BC208	11	BD106	50	BD234	55	BF188	32	BF950	80	OC42	22	TIP2955	60	2N1302	25	2N3010	20	2N4288	28	
ACY18	50	BC120	35	BC209	12	BD115	50	BD235	55	BF194	10	BF919	38	OC44	24	TIP3055	50	2N1303	28	2N3011	20	2N4289	28	
ACY19	50	BC125	25	BC212	10	BD116	50	BD236	58	BF195	10	BF920	38	OC45	20	TIS43	22	2N1304	28	2N3053	22	2N4290	28	
ACY20	50	BC126	30	BC212L	10	BD121	65	BD237	65	BF196	12	BF919-20	80	OC70	24	TIS90	20	2N1305	28	2N3054	45	2N4291	28	
ACY21	50	BC132	18	BC213	16	BD123	65	BD238	65	BF197	12	BF921	80	OC71	15	TIS91	22	2N1306	35	2N3055	42	2N4292	28	
ACY22	50	BC134	18	BC214	16	BD124	75	BD239A	60	BF198	15	BF939	39	OC72	24	TIS92	22	2N1307	35	2N3402	21	2N4293	28	
AD130	75	BC135	18	BC214	10	BD131	35	BD240A	50	BF199	15	BSX19	20	OC74	26	UT46	20	2N1308	40	2N3403	21	2N4860	60	
AD140	70	BC136	20	BC214L	10	BD132	35	BD239A/240A	1.00	BF200	30	BSX20	20	OC75	30	ZTX107	10	2N1309	40	2N3404	29	(FET)	60	
AD142	85	BC137	20	BC225	26	BD131/132	80	BD240	45	BF224	20	BSY95	13	OC77	35	ZTX108	10	2N1599	35	2N3405	42	2N4923	65	
AD143	85	BC138	28	BC226	36	M/P	80	BD241	45	BF240	11	BSY95A	13	OC79	40	ZTX109	10	2N1613	28	2N3414	16	2N5135	10	
AD149	70	BC139	32	BC237	13	BD133	40	BD242	45	BF241	18	BSY95B	13	OC81	22	ZTX300	12	2N1711	30	2N3415	16	2N5136	10	
AD161	40	BC140	38	BC238	18	BD134	40	BD243	45	BF242	18	BSY95C	13	OC82	24	ZTX301	12	2N1889	45	2N3416	29	2N5172	14	
AD162	40	BC141	28	BC238	18	BD136	35	BD244	45	BF243	18	BSY95D	13	OC83	24	ZTX302	16	2N1890	45	2N3417	29	2N5194	56	
AD161-162	M/P	BC142	25	BC251	15	BD137	35	BDX32	2.20	BF257	30	BU05	02	1.95	OC82	24	ZTX303	16	2N1893	40	2N3418	29	2N5195	56
AF114	80	BC143	25	BC251A	16	BD138	35	BDY11	1.30	BF258	30	BU204	1.40	OC82D	30	ZTX304	20	2N1247	75	2N3615	1.05	2N5294	50	
AF115	50	BC145	46	BC300	30	BD139	38	BDY17	1.80	BF259	35	BU205	1.40	OC83	26	ZTX330	15	2N1248	70	2N3616	1.05	2N5296	50	
AF116	50	BC147	09	BC301	30	BD140	38	BDY55	1.40	BF263	60	BU208	1.90	OC84	32	ZX500	20	2N1192	30	2N3646	10	2N5448	12	
AF117	50	BC148	09	BC302	29	M/P	80	BDY56	1.60	BF270	36	02	2.25	OC139	80	ZX501	12	2N193	38	2N3702	09	2N5457	32	
AF118	65	BC149	09	BC303	28	BD155	50	BF115	25	BF271	31	GP300	40	OC169	80	ZX502	16	2N194	38	2N3703	09	(FET)	32	
AF124	50	BC150	20	BC304	28	BD175	60	BF117	50	BF273	36	MJ480	95	OC170	80	ZX503	25	2N2218	25	2N3704	09	(FET)	32	
AF125	50	BC151	22	BC307	13	BD176	60	BF118	75	BF274	38	MJ481	1.05	OC201	80	ZX531	25	2N218A	25	2N3705	09	(FET)	32	
AF126	50	BC152	22	BC307	12	BD177	60	BF119	75	BF275	38	MJ482	1.05	OC202	80	ZX532	25	2N218A	25	2N3706	09	(FET)	32	
AF127	50	BC153	25	BC328	12	BD178	68	BF121	50	BF336	34	MJ491	1.15	OC200	46	ZX550	25	2N219	28	2N3707	10	(FET)	35	
AF139	38	BC154	19	BC337	13	BD179	75	BF123	60	BF337	34	MJ2955	90	OC202	1.20	2N388A	56	2N2220	20	2N3708A	09	2N6027	34	
AF239	42	BC157	10	BC338	13	BD180	75	BF125	50	BF338	38	MJE340	50	OC203	85	2N404	20	2N2221	20	2N3709	09	(P.U.T.)	34	
AL102	1.90	BC158	10	BC384	14	BD185	68	BF127	60	BF371	26	MJE370	55	OC204	90	2N404A	24	2N221A	22	2N3710	10	2N6121	70	
AL103	1.80	BC159	10	BC400	14	BD186	68	BF152	25	BF457	37	MJE371	60	OC205	1.15	2N527	50	2N222	20	2N3711	10	2N6122	70	
AS276	50	BC160	26	BC441	30	BD187	75	BF153	25	BF458	38	MJE372	60	OC206	1.15	2N527	50	2N222	20	2N3712	10	2N6123	70	
AS277	50	BC161	38	BC460	32	BD188	78	BF154	25	BF459	38	MJE373	60	OC207	1.15	2N527	50	2N222	20	2N3713	10	2N6124	70	
AS278	50	BC167	11	BC461	32	BD189	78	BF155	35	BF459A	30	MJE2955	90	TIC44	2.60	2N598	46	2N2369	14	2N3772	1.60	2S301	50	
AS279	50	BC168	10	BC477	20	BD190	78	BF156	28	BF459B	28	MJE3055	65	TIC45	3.50	2N696	24	2N2369A	14	2N3773	2.20	2S302	43	
AU104	1.90	BC169	10	BC478	20	BD195	90	BF157	28	BF459C	28	MJE3440	52	TIP29	30	2N697	24	2N2411	25	(FET)	18	2S303	56	
AU110	1.90	BC169C	11	BC479	20	BD196	90	BF158	28	BF459D	24	MPB113	52	TIP29A	55	2N698	30	2N212	25	2N3820	16	2S304	71	
AU113	1.90	BC170	09	BC546	10	BD197	95	BF159	28	BF460	25	MPF102	60	TIP29B	44	2N699	32	2N214	22	2N3821	35	2S305	80	
BC107	10	BC171	09	BC547	10	BD198	95	BF160	28	BF462	25	MPF104	60	TIP29C	44	2N706	10	2N217	25	2N3821	35	2S306	80	
BC107A	11	BC172	09	BC548	10	BD199	95	BF162	24	BF465	25	MPF105	35	TIP30	38	2N706A	12	2N2712	22	(FET)	60	2S307	80	

DIODES

AA119	08	BB104	30	BY176	75	OA79	10	74LS00	13	74LS78	46	74LS165	1.20	74LS279	85
AA120	03	BY206	30	OA81	10	74LS01	13	74LS79	46	74LS166	1.20	74LS280	2.40	74LS282	85
AA129	09	BY210/60009	30	OA85	10	74LS02	15	74LS85	65	74LS167	1.20	74LS281	2.40	74LS283	85
AA330	09	BY210	22	OA90	07	74LS03	15	74LS86	38	74LS168	1.80	74LS290	90	74LS291	90
AAZ13	15	BY211	45	OA91	07	74LS04	15	74LS90	38	74LS169	1.80	74LS292	90	74LS293	1.00
AAZ17	15	BY212	40	OA95	07	74LS05	22	74LS91	1.10	74LS170	2.50	74LS294	1.00	74LS295	1.00
BA100	10	BY213	40	OA182	13	74LS06	22	74LS92	6.80	74LS171	95	74LS296	1.50	74LS297	1.50
BA102	20	BY214	40	OA202	18	74LS07	21	74LS93	5.80	74LS172	95	74LS298	3.00	74LS299	3.00
BA144	09	BY216	36	OA208	07	74LS10	20	74LS95	9.00	74LS173	2.70	74LS300	1.50	74LS301	1.50</

LARGEST SELECTION - LOWEST PRICES

AERIALS		AUDIO LEADS		A.B.S. PLASTIC BOXES		VERO CASES		INSTRUMENT CASES		ALUM BOXES		CASSETTES		CAPS, CHOKES, TRIMMERS		CABLE		ELECTROLYTIC CAPACITORS		KNOBS		MICROPHONES etc.		SEMICONDUCTOR HARDWARE		POTS		MIN PRESETS 9p EACH		TRANSFORMERS		BATTERY HOLDERS		FUSES		QUICK BLOW 20mm:		FUSE HOLDERS		SWITCHES		BATTERY HOLDERS		ETCHANT AND PENS		TOOLS CROC CLIPS ETC		MATERIALS																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																											
105	Adjustable Aerial Gutter Mount	3.00		110	5 pin - 3.5mm 3 & 5 connected	0.65		141	4" x 1" x 2"	1.08		152	23/16" - 2" - 1" Black	0.47		155	8" x 5 1/2" x 2"	1.70		159	5 1/2" x 2 1/2" x 1 1/2"	0.83		301	Low Cost C60	0.36		327	Jackson Coupling	0.74		390	Light Mic Cable	per metre		430	470uF 50v	0.30		1102	Black/Sliver Knob	0.28		1325	Crystal Desk Mike	0.95		867	T0220	0.20		1831	1K Lin Single Pots	29		1816	13 Amp Rubber Plug	0.52		1818	13 Amp Plastic Plug	0.46		1819	13 Amp Free Socket	0.50		1820	13 Amp 2K Free Socket	0.50		1821	13 Amp 2K Free Socket	0.50		1822	13 Amp 4K Free Socket	0.50		1823	13 Amp 4K Free Socket	0.50		1824	13 Amp 4K Free Socket	0.50		1825	13 Amp 4K Free Socket	0.50		1957	13 Amp 4K Free Socket	0.50	

CHOOSE FROM OVER
20 TOP QUALITY
MODULES


AL20A-30A

AUDIO
AMPLIFIER
MODULES




AL80

AUDIO
AMPLIFIER
MODULE
35 Watts RMS

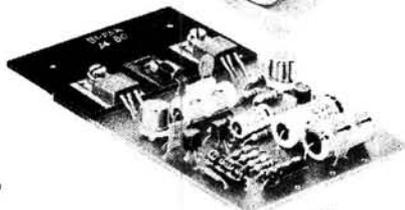

AL120


AUDIO AMPLIFIER
50W RMS

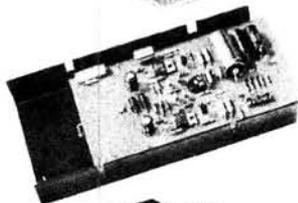

AL250


POWER
AMPLIFIER

With integral heat
sink and short-
circuit protection

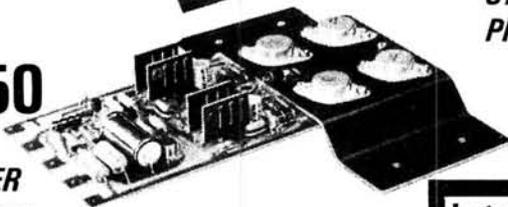

Stereo 30

COMPLETE
AUDIO
CHASSIS

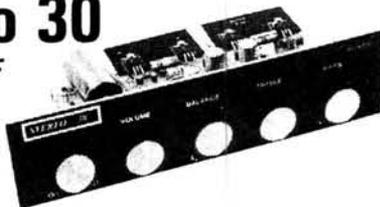

BI-PAK Audio Modules are famous for their variety, quality of design and ruggedness. For over 10 years BI-PAK have been suppliers to manufacturers of high quality audio equipment throughout the world – to date, well over 100,000 modules have been sold – this is why discerning amateur enthusiasts insist on using BI-PAK modules in their equipment. They know that every item is designed and tested to do the job for which it is intended before it leaves the factory. Whatever you are building, there is a kit or module

in the BI-PAK range to suit your every need from 5 watts to 125 watts, from amplifiers to equalisers. AND if you cannot see what you require in this advertisement, just write or phone us – we are waiting to help you!

AL60

AUDIO
AMPLIFIER
MODULE
25 Watts RMS




PA12

STEREO
PRE-AMPLIFIER

PA100 & PA200

STEREO
PRE-AMPLIFIER

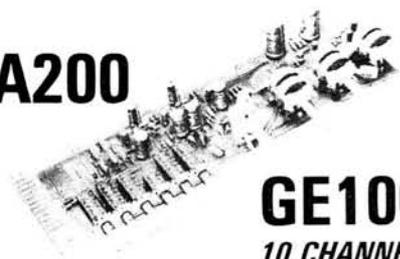


GE100

10 CHANNEL
MONOGRAPHIC

Latest addition

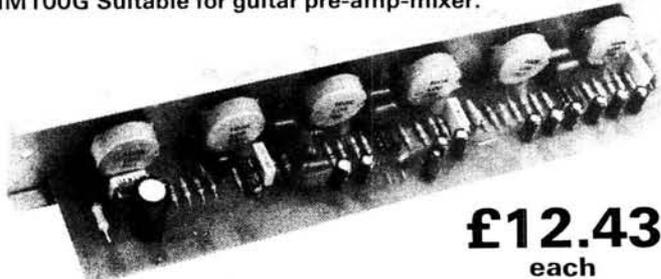MM100 Suitable for disco mixer.
MM100G Suitable for guitar pre-amp-mixer.



£12.43
each

BI-PAK

COMPLETELY
GUARANTEED

AMPLIFIERS

AL10. 3 watt Audio Amplifier Module 22-32v supply.	£3.08
AL20. 5 watt Audio Amplifier Module 22-32v supply.	£3.57
AL30A. 7-10 watt Audio Amplifier Module 22-32v supply.	£4.16
AL60. 15-25 watt Audio Amplifier Module 30-50v supply.	£5.15
AL80. 35 watt Audio Amplifier Module 40-60v supply.	£8.07
AL120. 50 watt Audio Amplifier Module 50-70v supply.	£13.14

AL250. 125 watt Audio Amplifier Module 50-80v supply. £19.60

STEREO PRE-AMPLIFIERS

PA12. Supply voltage 22-32v input sensitivity 300mv. Suit: AL10/AL20/AL30.	£8.55
PA100. Supply voltage 24-36v inputs: Tape, Tuner, Mag P.U. Suit: AL60, AL80.	£17.65
PA200. Supply voltage 35-50v inputs: Tape, Tuner, Mag P.U. Suit: AL80/AL120/AL250.	£18.24

BI-KITS

STA5. 5 watts per channel Stereo Amplifier. Kit consisting of: 2 x AL20 amplifiers, 1 x PA 12 pre-amplifier, 1 x PS12 power supply, 1 x 2036 transformer and necessary wiring diagram. **£19.52**

STA10. 10 watts per channel Stereo Amplifier. Kit consisting of: 2 x AL30 amplifiers, 1 x PA12 pre-amplifier, 1 x PS12 power supply, 1 x 2036 transformer and necessary wiring diagrams. **£20.63**

STA15. 15 watts per channel Stereo Amplifier. Kit consisting of: 2 x AL60 amplifiers, 1 x PA100 pre-amplifier, 1 x SPM80 power supply, 1 x 2034 transformer, 2 x coupling capacitors for 8 ohms 470mfd 30v and necessary wiring diagram. **£36.76**

BI-KITS

STA25. 25 watts per channel Stereo Amplifier. Kit consisting of: 2 x AL60 amplifiers, 1 x PA100 pre-amplifier, 1 x SPM120/45 power supply, 1 x 2040 transformer, coupling capacitors for 8 ohms 470 mfd 45v, 1 x reservoir capacitor 2200mfd 100v and necessary wiring diagram. **£40.50**

STA35. 35 watts per channel Stereo Amplifier. Kit consisting of: 2 x AL80 amplifiers, 1 x PA200 pre-amplifier, 1 x 2035 transformer, 2 x coupling capacitors 470mfd at 50v for 8 ohms, 1 x reservoir capacitor 2200mfd 100v and necessary wiring diagram. **£45.76**

BI-KITS

STA50. 50 watts per channel Stereo Amplifier. Kit consisting of: 2 x AL120 amplifiers, 1 x PA200 pre-amplifier, 1 x 2041 transformer, 2 x coupling capacitors 1000mfd 63v, 1 x SPM120/65, 1 x reservoir capacitor 3300mfd 100v and necessary wiring diagram. **£59.89**

STA100. 100 watts per channel Stereo Amplifier. Kit consisting of: 2 x AL250 amplifiers, 1 x PA200 pre-amplifier, 2 x SPM120/65 power supplies, 2 x 2041 transformers, 2 x coupling capacitors 1000mfd 100v and necessary wiring diagram. **£84.68**


PS12

POWER
SUPPLY MODULE




SPM80

STABILISED
POWER SUPPLY

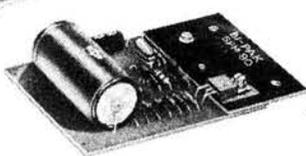


SPM120

STABILISED
POWER
SUPPLY

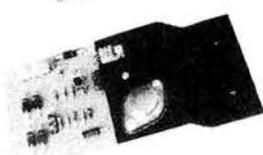

MPA30

MAGNETIC CARTRIDGE
PRE-AMPLIFIER

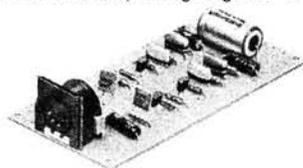


BP124

SIREN
ALARM
MODULE




S450

STEREO
FM TUNER
Fitted with
phase lock-loop

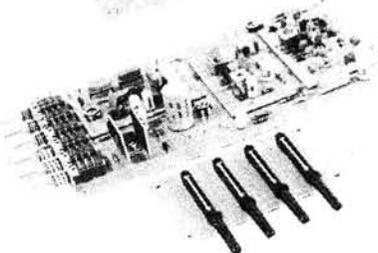

Mk II

EQUALISER

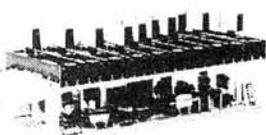

MONO PRE-AMPLIFIERS

MM100. Supply voltage 40-65v inputs: Tape, Mag P.U. Microphone Max output 500mv. **£12.43**

MM100G. Supply voltage 40-65v inputs: 2 Guitars. Microphones Max output 500mv. **£12.43**

POWER SUPPLIES

PS12. 24v Supply. Suit: 2 x AL10, 2 x AL20, 2 x AL30 & PA12/S.450. **£1.65**

SPM80. 33v Stabilised supply. Suit: 2 x AL60, PA100 to 15 watts. **£4.84**

SPM120/45. 45v Stabilised supply. Suit: 2 x AL60, PA100 to 25 watts. **£6.38**

SPM120/55. 55v Stabilised supply. Suit: 2 x AL80, PA200. **£6.38**

SPM120/65. 65v Stabilised supply. Suit: 2 x AL120, PA200, 1 x AL250. **£6.38**

SG30. 15-0-15 Stabilised power supply for 2 x GE100MK11. **£3.80**

MISCELLANEOUS

MPA30. Stereo Magnetic Cartridge Pre-Amplifier - input 3.5mv Output 100mv. **£3.27**

S.450. Stereo FM Tuner Supply Voltage 20-30v - Varicap tuned. **£25.56**

STEREO 30. Complete 7 watt per channel Stereo Amplifier Board - includes amps, pre-amp, power supply, front panel, knobs etc - requires 2039 Transformer. **£21.09**

Transformers are not included with power supplies.
SPM120 Range also require reservoir and output capacitors.

BP124. 5 watt 12v max. - Siren Alarm Module. **£3.85**

GE100MK11. 10 channel mono-graphic equaliser, complete with sliders and knobs. **£23.00**

VPS30. Variable regulated stabilised power supply 2-30v 0-2 amps. **£7.60**

PS250. Consists - 1 capacitor & 4 diodes for constructing unstabilised power supply for AL250 to 125 watts. **£2.90**

TRANSFORMERS

2034. 1.7 amp 35v. Suit SPM80. **£4.90**

2035. 2 amp 55v. **£6.65**

2036. 750mA 17v. Suit: PS12. **£2.85**

2040. 1.5 amp 0-45v-55v. Suit: SPM120/45, SPM120/55v. **£6.45**

2041. 2 amp 0-55v-65v. Suit: SPM120/55, SPM120/65v. **£8.46**

2039. 1 amp 0-20v. Suit Stereo 30. **£3.50**

2043. 150mA 15-0-15v. Suit: SG30. **£2.40**

ACCESSORIES

139. Teak Cabinet. Suit: Stereo 30, 320 x 235 x 81mm. **£7.00**

140. Teak Cabinet. Suit: STA15, 425 x 290 x 95mm. **£9.50**

FP100. Front Panel for PA100 & PA200. **£1.80**

BP100. Back Panel for PA100 & PA200. **£1.60**


GE100FP. Front Panel for one GE100MK11. **£1.75**

2240. Kit of parts including Teak Cabinet, Chassis, Sockets and Knobs etc. (To house STA15 Amplifier.) **£19.95**

Full data sheets are available FREE on request, please enclose a S.A.E.

VPS30

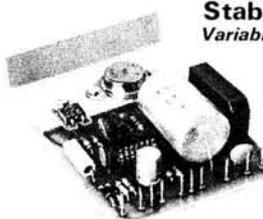REGULATED VARIABLE
STABILISED
POWER SUPPLY



KIT £20 + V.A.T.

Access and Barclaycards accepted - just telephone our Orderline - Ware (STD 0920) 3182. All prices exclude V.A.T., add 50p. postage per order. Terms: C.W.O., cheques, Postal Orders payable to Bi-Pak.

Stabilised Power Supply Kit

Variable from 2-30 volts and 0-2 Amps

Kit includes:

- 1 - VPS30 Module.
- 1 - 25 volt 2 Amp transformer.
- 1 - 0-50v 2" Panel Meter.
- 1 - 0-2 Amp 2" Panel Meter.
- 1 - 470 ohm wirewound potentiometer.
- 1 - 4K7 ohm wirewound potentiometer.

Wiring Diagram Included.

BI-PAK – SATISFACTION OR YOUR MONEY BACK!

PLUGS AND SOCKETS

1625	2mm Plug RED	£0.16
1626	2mm Plug BLACK	£0.16
1628	2mm Socket RED	£0.16
1629	2mm Socket BLACK	£0.16
1634	4mm Plug BLACK	£0.16
1637	4mm Plug RED	£0.16
1640	4mm Socket BLACU	£0.16
1643	4mm Socket RED	£0.16
1652	2 Pin DIN Chassis Socket	£0.08
1654	5 Pin 180° DIN Chassis Socket	£0.12
1655	5 Pin 240° DIN Chassis Socket	£0.12
1656	2.5mm Chassis Socket	£0.10
1657	3.5mm Chassis Socket	£0.10
1658	Metal Std. Jack Chassis Socket (mono)	£0.18
1659	Metal Std. Jack Chassis Socket (stereo)	£0.24
1660	Single Phono socket	£0.09
1661	Double Phono Socket	£0.12
1662	Coax surface socket	£0.22
1663	Coax Flush Socket	£0.22
1664	Plastic Std. Jack Socket (mono)	£0.20
1665	Plastic Std. Jack Socket (stereo) for headphones	£0.32
1666	Car Aerial Chassis Socket	£0.18
1667	AC Chassis Socket	£0.12
1668	4 Way Phono Chassis Socket	£0.22
1669	Plastic Std. Jack Chassis socket stereo switched	£0.32
1670	AC switched non rev. socket	£0.32
1672	2 Pin DIN line socket	£0.10
1674	5 Pin 180° DIN line socket	£0.17
1675	5 Pin 240° DIN line socket	£0.20
1676	2.5mm Plastic line socket	£0.12
1677	3.5mm Plastic line socket	£0.12
1678	Std. jack plastic line socket (mono)	£0.17
1679	Std. jack metal line socket (mono)	£0.30
1680	Std. jack plastic line socket (stereo)	£0.22
1681	Std. jack metal line socket (stereo)	£0.38
1682	Phono in line metal socket	£0.16
1684	Coax line socket	£0.34
1685	Coax back-back socket	£0.14
1686	AC linesocket (2 pin USA Type)	£0.18
1687	Phono in line plastic socket	£0.12
1688	Phono back-back socket	£0.20
1689	2 Pin DIN plug	£0.10
1692	5 Pin 180° DIN plug	£0.14
1693	5 Pin 240° DIN plug	£0.14
1696	2.5mm Plug (Metal)	£0.15
1697	3.5mm Plug (Plastic)	£0.12
1698	3.5mm Plug (Metal)	£0.16
1699	Std. Plastic Jack Plug (Mono)	£0.30
1700	Std. Metal Jack Plug (Mono)	£0.30
1701	Std. Metal Jack Plug (Stereo)	£0.35
1702	Plastic Phono Plug	£0.11
1703	Car Aerial Plug	£0.24
1704	Coax TV Plug	£0.22
1705	Right Angle Jack Plug (Mono)	£0.20
1706	2.5mm Plastic Plug	£0.12
1707	Std. Plastic Jack Plug (Stereo)	£0.22
1708	Metal Phono Plug	£0.14
1709	2.1mm DC Plug	£0.12
1710	2.5mm DC Plug	£0.12
1711	AC Plug (2 pin USA Type)	£0.16
1712	AM Aerial Plug	£0.17
1713	Cassette AC Input Plug	£0.15
1714	FM Aerial Plug	£0.13
1715	PL 259 Plug	£0.40
1716	SO239 Socket 4 hole fixing	£0.38
1717	SO239 Socket single hole fixing	£0.40
1718	PL258 Double Ended Female Coupler	£0.40
1719	NC555 Reducer for PL259 (Small)	£0.16
1720	NC555 Reducer for PL259 (Large)	£0.16
1721	M358 Right Angle Coupler PL259 SO239	£0.12
1722	M358 T Connector Female-Male-Female	£0.85
1723	NC563 Inline Coupler PL259 x 2	£0.60
1724	9NC15 50 ohm standard plug	£0.64
1725	BNC1502 Chassis mounting socket	£0.75
1726	BNC1503 Chassis mounting socket single hole fixing	£0.70
1727	BNC1520 BNC male to SO239 female	£0.85
1728	BNC1521 BNC female to PL259 male	£0.85
1729	Junction Box one in two out	£0.80
1730	Low loss splitter	£1.00

BREADBOARD

2195	EXP325	£1.84
2196	EXP350	£3.62
2197	EXP650	£4.14
2198	EXP300	£6.61
2199	EXP48	£2.65
2200	EXP600	£7.25

VEROBOARD

2201	2.5" x 5" .1 copper	£0.76
2202	3.5" x 3.75" .1 copper	£0.66
2203	2.5" x 17" .1 copper	£2.28
2204	3.75" x 5" .1 copper	£0.86
2205	3.75" x 3.75" .1 copper	£0.76
2206	3.75" x 17" .1 copper	£2.96
2207	4.75" x 17.9" .1 copper	£3.90
2208	2.5" x 1" 5 in pack	£0.92
2209	3.75" x 17" .1 Plain	£1.92
2210	3.75" x 2.5" .1 Plain	£0.48
2211	5.0" x 3.75" .1 Plain	£0.72
2212	vero pins Double sided .040mm .1" (in 100's)	£0.52
2213	vero pins Single sided .040mm .1" (in 100's)	£0.52
2214	DIP Breadboard	£3.26
2215	Verob Cutter	£1.06
2216	Insertion Tool 1	£1.46
2218	12 volt mini drill	£7.00
2219	Right Angle Bracket 1 1/4" x 1 1/2"	£0.07
2220	Right Angle Bracket 1 1/4" x 1 1/2"	£0.06

EARPIECES & BUZZERS

500	Solid State Buzzer 4-25v	£0.75
501	Crystal Earpiece	£0.42
502	8 ohm Earpiece 2.5mm Plug	£0.18
503	8 ohm Earpiece 3.5mm Plug	£0.18
505	200 ohm Earpiece 3.5mm Plug	£0.44

COMPONENT PACKS

C26	300 Preformed carbon resistors mixed 1/4-1/2w	£1.00
C27	50 2-10 watt wire wound resistors mixed	£1.00
C28	300 Approx Resistors mixed values (count by weight)	£1.00
C29	200 Approx Capacitors mixed values and types (count by weight)	£1.00
C30	60 Precision Resistors 1-5% tol	£1.00
C31	100 Approx 1/8 watt min Resistors mixed values	£1.00
C32	6 Pieces Ferrite Rods	£1.00
C33	60 Metres Single strand wire assorted colours	£1.00
C34	15 Reed switches glass type	£1.00
C35	5 Micro switches assorted types including min.	£1.00
C36	6 Assorted Audio jack sockets and plugs	£1.00
C37	100 Disc ceramic caps mixed values	£1.00
C38	20 Assorted pots	£1.00
C39	40 C280 type capacitors metal foil	£1.00
C40	60 Electrolytics assorted	£1.00
C41	50 Assorted polyester/polystyrene	£1.00
C42	60 Low voltage Electrolytics mixed values up to 10v.	£1.00
C43	15 Assorted slider pots	£1.00
C44	10 Dual gang pots log and lin assorted	£1.00
C45	1 Pack assorted Hardware nuts/bolts etc.	£1.00
C46	10 Assorted switches slide/rocker/mains	£1.00
C47	3 Relays 24v coil	£1.00
C48	20 Assorted knobs push, screw and slider types	£1.00
C49	20 Assorted Tag strips and panels	£1.00
C50	4 Wave change switches rotary	£1.00
C51	1 Pack of assorted PVC sleeving and markers	£1.00
C52	100 1/2 watt resistors mixed values	£1.00
C53	35 Presets assorted type and values	£1.00
C54	40 Metres stranded wire assorted colours	£1.00
C55	10 Assorted Din/sockets/Coax/speakers/phone	£1.00
C56	10 Assorted plugs Din/coax/speakers/etc.	£1.00
C57	10 Metres assorted cable. Mains/speaker/coax/microphone	£1.00
C58	100 sq in copper clad board single side paper	£1.00
C59	75 sq in copper clad fiberglass board	£1.00
C60	15 Assorted IC sockets 8, 14, 16 pin	£1.00

BABANI BOOKS

No.	TITLE	PRICE
BP160	Coil Design and Construction Manual	1.25
BP202	Handbook of Integrated Circuits (IC's) Equivalents & Substitutes	1.45
BP205	First Book of Hi-Fi Loudspeaker Enclosures	0.95
BP207	Practical Electronics Science Projects	0.75
BP208	Practical Stereo and Quadraphony Handbook	0.75
BP211	First Book of Diode Characteristics Equivalents and Substitutes	1.25
BP213	Electronic Circuits for Model Railways	1.00
BP214	Audio Enthusiasts Handbook	0.85
BP218	Build Your Own Electronic Experiments Laboratory	0.85
BP219	Solid State Novelty Projects	0.85
BP220	Build Your Own Solid State Hi-Fi and Audio Accessories	0.85
BP221	28 Tested Transistor Projects	1.25
BP222	Single State Short Wave Receivers for Beginners	1.25
BP223	50 Projects Using IC CA3130	1.25
BP224	50 CMOS IC Projects	1.25
BP225	A Practical Introduction to Digital IC's	1.25
BP226	How to Build Advanced Short Wave Receivers	1.20
BP227	Beginners Guide to Building Electronic Projects	1.25
BP228	Essential Theory for the Electronics Hobbyist	1.25
BP26	Engineers and Technicians Reference Tables	1.25
BP7	Radio and Electronic Colour Codes and Data Chart	0.70
BP14	Second Book of Transistor Equivalents and Substitutes	1.10
BP23	First Book of Practical Electronic Projects	0.75
BP24	52 Projects Using IC741	0.90
BP27	Chart of Radio Electronic Semiconductor and Logic Symbols	0.65
BP28	Resistor Selection Handbook (International Edition)	0.60
BP29	Major Solid State Audio Hi-Fi Construction Projects	0.85
BP32	How to Build Your Own Metal and Treasure Locators	1.35
BP33	Electronic Calculator Users Handbook	1.25
BP34	Practical Repair and Renovation of Colour TVs	1.25
BP35	Handbook of IC Audio Pre-amplifier & Power Amplifier Construction	1.25
BP36	Resistor Selection Handbook (International Edition)	0.75
BP37	50 Projects Using Relays, SCR's and TRIACs	1.25
BP38	Fun and Games with Your Electronic Calculator	0.75
BP39	50 (FET) Field Effect Transistor Projects	1.50
BP40	Digital IC Equivalents and Pin Connections	2.50
BP41	Linear IC Equivalents and Pin Connections	2.75
BP42	50 Simple L.E.D. Circuits	0.95
BP43	How to Make Walkie-Talkies	1.50
BP44	IC555 Projects	1.75
BP45	Projects in Opto-Electronics	1.25
BP46	Radio Circuits Using IC's	1.35
BP47	Mobile Discotheque Handbook	1.25
BP48	Electronic Projects for Beginners	1.35
BP49	Popular Electronic Projects	1.45
BP50	IC LM3900 Projects	1.35
BP51	Electronic Music and Creative Tape Recording	1.25
BP52	Long Distance Television Reception (TV-DX) for the Enthusiast	1.95
BP53	Practical Electronic Calculations and Formulae	2.25
BP54	Your Electronic Calculator and Your Money	1.35
BP55	Radio Stations Guide	1.75
BP56	Electronic Security Devices	1.45
BP57	How to Build Your Own Solid State Oscilloscope	1.50
BP58	50 Circuits Using 7400 Series IC's	1.35
BP59	Second Book of CMOS IC Projects	1.50
BP60	Practical Construction of Pre-amps, Tone Controls, Filters & Attn.	1.45
BP61	Beginners Guide to Digital Techniques	0.95
BP62	Elements of Electronics - Book 1	2.25
BP63	Elements of Electronics - Book 2	2.25
BP64	Elements of Electronics - Book 3	2.25
BP65	Single IC Projects	1.50
BP66	Beginners Guide to Microprocessors and Computing	1.75
BP67	Counter, Driver and Numerical Display Projects	1.75
BP68	Choosing and Using your Hi-Fi	1.65
BP69	Electronic Games	1.75
BP70	Transistor Radio Fault-Finding Chart	0.50
BP71	Electronic Household Projects	1.75
BP72	A Microprocessor Primer	1.75
BP73	Remote Control Projects	1.75
BP74	Electronic Music Projects	1.75
BP75	Electronic Test Equipment Construction	1.75
BP76	Power Supply Projects	1.75
BP77	Elements of Electronics - Book 4	2.95
BP78	Practical Computer Experiments	1.75
BP79	Radio Control for Beginners	1.75
BP80	Popular Electronic Circuits - Book 1	1.95

BUDGET STEREO HEADPHONES

BLACK WITH PADDED EARCUPS
IMPEDANCE 8 ohms
FREQUENCY RESPONSE
30-18,000 HZ
WEIGHT 300gms
£4.20

GOOD QUALITY STEREO HEADPHONES

DOUBLE PADDED HEAD BAND
CIRCULAR VENTED PADDED
EARPIECES
BLACK AND ALUMINIUM FINISH
IMPEDANCE 8 ohms
FREQUENCY RESPONSE
20-19,000 HZ
WEIGHT 350gms
£8.25

SUPERIOR QUALITY STEREO HEADPHONES

WIDE BLACK PADDED HEAD
BAND AND MATT
ALUMINIUM EARCUPS
IMPEDANCE 8 ohms
FREQUENCY RESPONSE
15-25,000 HZ
WEIGHT 290gms
£15.85

LAST MINUTE ITEMS

We offer the following
Fairchild Power Transistors
at much reduced prices

TYPE	Pol.	£ p
2N3054	NP	0.32
2N3713	NP	0.35
2N3714	NP	0.36
2N3716	NP	0.36
2N3767	NP	0.34
2N3789	PNP	0.45
2N4901	PNP	0.40
2N4903	PNP	0.42
2N4910	NP	0.25
2N4911	NP	0.27
2N4912	NP	0.30
2N4913	NP	0.30
2N4914	NP	0.32
2N4915	NP	0.34
2N5630	NP	0.50
2N5631	NP	0.60
2N5838	NP	0.60
2N5886	NP	0.50
2N6031	PNP	0.70
2N6123	NP	0.25
2N6129	NP	0.25
2N6130	NP	0.30
2N6131	NP	0.32
2N6133	PNP	0.32
2N6134	PNP	0.35
2N6487	NP	0.35
2N6490	PNP	0.40
BD220	NP	0.25
BD223	PNP	0.30
BD225	PNP	0.30
FT49	NP	0.25
FT317a	NP	0.28
FT417a	PNP	0.32
FT417b	PNP	0.34
FT423	NP	0.40
MJ802	NP	0.45
TIP61A	NP	0.25
TIP61B	NP	0.26
TIP62A	PNP	0.28
TIP62B	PNP	0.28
TIP110	NP	0.30
TIP111	NP	0.32
TIP112	NP	0.35

BRIDGE RECTIFIERS

10 Amp RMS	1.40
BR10/50v	1.50
BR10/200v	1.60
BR10/400v	1.90
25 Amp RMS	1.85
BR25/50v	1.95
BR25/100v	2.05
BR25/200v	2.90
BR25/400v	51
BY164	


Access and Barclaycards accepted – just telephone our
Orderline – Ware (STD 0920) 3182. All prices exclude
V.A.T., add 50p postage per order. Terms: C.W.O.,
cheques, Postal Orders payable to Bi-Pak.

THE BI-PAK OPTO SHOW

LED's


1501	TIL209 Red LED .125"	£0.10
1502	TIL211 Green LED .125"	£0.16
1503	TIL213 Yellow LED .125"	£0.16
1504	FLV117 Red LED 2"	£0.10
1505	FLV310 Green LED 2"	£0.16
1506	FLV410 Yellow LED 2"	£0.16
1507	2nd Grade LED pack 10 assorted	£0.80
1522	MIL32 Clear illuminating Red LED .125"	£0.12
1523	FLV111 Clear illuminating Red LED 2"	£0.12
1524	COX21 Red Flashing LED	£0.65
1525	COX95 two colour LED	£0.75

NEW SHAPE LED's

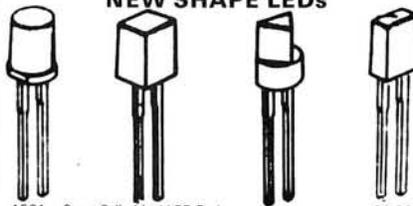

1561	3mm Cylindrical LED Red	£0.26
1562	3mm Square LED Red	£0.26
1563	3mm Triangular LED Red	£0.26
1564	5mm Rectangular LED Red	£0.26
1565	5mm Cylindrical LED Red	£0.26
1566	5mm Square LED Red	£0.26
1567	5mm Triangular LED Red	£0.26
1568	3mm Cylindrical LED Green	£0.28
1569	3mm Square LED Green	£0.28
1570	3mm Triangular LED Green	£0.28
1571	5mm Rectangular LED Green	£0.28
1572	5mm Cylindrical LED Green	£0.28
1573	5mm Square LED Green	£0.28
1574	5mm Triangular LED Green	£0.28
1575	3mm Cylindrical LED Yellow	£0.28
1576	3mm Square LED Yellow	£0.28
1577	3mm Triangular LED Yellow	£0.28
1578	5mm Rectangular LED Yellow	£0.28
1579	5mm Cylindrical LED Yellow	£0.28
1580	5mm Square LED Yellow	£0.28
1581	5mm Triangular LED Yellow	£0.28

LED CLIPS AND HOUSINGS

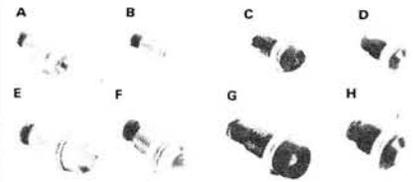

1548	LED Plastic clips .125"	£0.15
1549	LED Plastic clips .2"	£0.18
1550	LED Housing (nickel plated) .125"	£0.26
1551	LED Housing (nickel plated) .125"	£0.22
1552	LED Housing (matt black) .125"	£0.37
1553	LED Housing (matt black) .125"	£0.31
1554	LED Housing (nickel plated) .2"	£0.34
1555	LED Housing (nickel plated) .2"	£0.28
1556	LED Housing (matt black) .2"	£0.44
1557	LED Housing (matt black) .2"	£0.36

OPTO-ISOLATORS

1515	Opto-isolator IL74 Single	£0.55
1516	Opto-isolator ILQ74 Dual	£1.16
1517	Opto-isolator ILQ74 Quad	£2.10

7 SEGMENT LED DISPLAYS

1508	BDL307 7 segment LED display .3"	£0.80
1509	BDL527 dual 7 segment LED display .5"	£1.80
1510	BDL707 7 segment LED display .3"	£0.98
1511	BLD747 7 segment LED display .6"	£1.75
1512	BDL727 dual 7 segment LED display .5"	£1.90

MISCELLANEOUS

1514	ORP12 Light Dependent Resistor	£0.60
1518	Photo transistor P20 NPN	£0.60
1519	Photo Darlington MEL11 NPN	£0.26
1520	Photo transistor OCP71 PNP	£0.40
1526	FPE100 Infra Red Emitter	£0.38
1527	COY89 Infra Red LED	£0.38

Beginners Pak: No. 1

100 Transistors

A pack of well known transistors. As used in many popular projects. A must for beginners (and very useful to experienced constructors too).

10	BC107/8	T018	Metal	NPN
5	BC237	T092	Plastic	NPN
5	BC177/8	T018	Metal	PNP
5	BC251	T092	Plastic	PNP
10	BFY51-BC141	T039	Metal	NPN
5	BC160	T039	Metal	PNP
5	2N3055	T03	Metal	NPN
2	BD312/MJ2955	T03	Metal	PNP
5	TIP29-31	T0220	Plastic	NPN
2	TIP30-32	T0220	Plastic	PNP
10	OC71-76	Germanium	PNP	PNP
5	AC128-188	Germanium Metal	PNP	PNP
5	AC176	Germanium Metal	NPN	NPN
5	OC44-45	Germanium	PNP	PNP
5	TIS43-UT46	Unijunction Plastic		
5	2N3819	F.E.T.		
2	MEL11	Photo Transistor Plastic		
2	BD131	T0126	Plastic	NPN
2	BD132	T0126	Plastic	PNP

100 TOTAL

All devices - brand new and full spec as per device coding. Data and lead out details included in pak. Normal Retail Value £23.00. Our Special Offer Price £15.00

Beginners Pak: No. 2

100 Rectifiers, SCR's, Triacs, Diodes.

20	IN4001-IN4007	1 Amp Silicon Rectifier
20	IN5401-IN5407	3 Amp Silicon Rectifier
20	IN4148	Fast switch diodes Silicon
10	OA200 BAX13-6	General Purpose Diode Silicon
5	1C106D	Thyristor 400v T0202 Case
2	10Amp Triacs 400v T0220	Case Isolated Tab
2	4Amp Triacs 400v T0220	Case Non-isolated Tab
10	Assorted 3Amp Thyristors	50-60Volts T064-T066 Case
5	Assorted 1Amp Thyristors	50-60Volts T039 Case
6	OA81-91	General Purpose Germanium Diodes

100 TOTAL

All devices brand new and full spec Data and lead out details included. Normal Retail Value £17.00. Our Special Offer Price £11.00

UNTESTED SEMICONDUCTOR PAKS

U1	150 germ Gold Bonded Diodes OA47	£1.00
U2	150 germ point contact diodes OA81	£1.00
U3	150 Silicon G.P. 200mA Diodes OA200	£1.00
U4	150 Silicon Fast Switch Diodes IN4148	£1.00
U5	25 Stud type Silicon Rectifiers up to 10A	£1.00
U6	10 SCR's 5Am- T066	£1.00
U7	40 Sil Trans NPN T018 Case BC107/8/9	£1.00
U8	40 Sil Trans PNP T018 Case BC177/8/9	£1.00
U9	40 Sil Trans NPN T018 Case 2N7061	£1.00
U10	40 Sil Trans NPN T05/39 2N697/2N1711	£1.00
U11	40 Sil Trans PNP T05/39 2N2905/1132	£1.00
U12	30 Sil Trans NPN T039 BFY51-BC141	£1.00
U13	30 Sil Trans PNP T039 BC160-161 etc	£1.00
U14	10 Sil Trans NPN T03 2N3055	£1.00
U15	10 Sil Trans NPN T0220 TIP29-31-33	£1.00
U16	10 Sil Trans PNP T0220 TIP30-32-34	£1.00
U17	30 Sil Trans NPN T039 High Vits. BF258/115	£1.00
U18	40 Sil Trans T092 BC237/8	£1.00
U19	40 Sil Trans T092 BC251	£1.00
U20	40 Sil Trans NPN T092 BC183-4	£1.00
U21	40 Sil Trans PNP T092 BC257 BC212L	£1.00

Code No's mentioned above are given as a guide to the type of device in the pak. The devices themselves are normally unmarked.

ELECTROLYTIC PAKS

A range of paks each containing 25 first quality, mixed value miniature electrolytics.		
EC1	Values from .46mFD-10mFD	£1.00
EC2	Values from 10mFD-100mFD	£1.00
EC3	Values from 100mFD-1000mFD	£1.00

CERAMIC PAKS

Containing a range of first quality miniature ceramic capacitors.

MC1	40 miniature ceramic capacitors: 5 of each value: 22pf, 27pf, 33pf, 39pf, 47pf, 56pf, 68pf, 82pf.	£1.00
MC2	40 miniature ceramic capacitors: 5 of each value: 100pf, 120pf, 150pf, 180pf, 220pf, 270pf, 330pf, 390pf.	£1.00
MC3	40 miniature ceramic capacitors: 5 of each value: 470pf, 560pf, 680pf, 820pf, 1000pf, 1500pf, 2200pf, 3300pf.	£1.00
MC4	35 miniature ceramic capacitors: 5 of each value: 4700pf, 6800pf, .01uf, .015uf, .022uf, .033uf, .047uf.	£1.00

SPEAKERS AND CROSSOVERS

1901	Dome Tweeter 3 1/2" 8 ohms 50w	£3.20
1902	Dome Tweeter 3" 8 ohms 20w	£2.60
1903	Flared Horn Tweeter 8 ohms 30w	£3.80
1904	2 way crossover 15w 8 ohms	£1.24
1905	2 way crossover 40w 8 ohms	£2.70
1906	3 way crossover 60w 8 ohms	£3.50
1907	Piezo Tweeter	£5.20
1914	70mm 8 ohm speaker	£1.20
1915	70mm 8 ohm speaker	£0.95
1916	56mm 8 ohm speaker	£0.65
1917	2 1/2" 8 ohm speaker	£0.75
1918	2 1/2" 64 ohm speaker	£0.82
1919	5 1/2" woofer 4 ohms 10w	£3.90
1920	5 1/2" woofer 8 ohms 10w	£5.90
1921	5 1/2" Dual cone wide range 8 ohms	£5.80
1922	8" Dual cone long throw 8 ohms 15w	£4.84
1923	8" woofer dual 4 : 8 ohms rubber edge 20w	£7.80

DIL SOCKETS

1601	14 Pin	£0.11	1606	22 Pin	£0.24
1603	16 Pin	£0.12	1607	24 Pin	£0.28
1604	18 Pin	£0.18	1608	28 Pin	£0.32
1605	20 Pin	£0.20	1609	40 Pin	£0.36

LATE ADDITIONS - High Current Transistors

BFT32	VCEO	VCBO	I.C. Max	£0.60
BFT33	60	80	3A	£0.62
BFT34	80	100	3A	£0.65
BFT34	100	120	3A	£0.65
BFT37	100	120	3A	£0.95
RPY76A	Infra Red Detector			£0.65

BULBS AND NEONS

1534	LES Bulb 6v 0.36w	£0.24
1535	LES Bulb 6.5v 1w	£0.24
1536	LES Bulb 14v 0.75w	£0.24
1538	MES Bulb Round 6v .04A	£0.24
1539	MES Bulb Round 6.5v .15A	£0.20
1540	MES Bulb Round 6.5v .3A	£0.20
1541	MES Bulb Round 12.0v .1A	£0.20
1542	MES Bulb Round 12.0v 2.2w	£0.20
1543	Neon Red Round 240v	£0.34
1544	Neon Red Rectangular 240v	£0.34
1545	Neon Orange Rectangular 240v	£0.34
1546	Neon Green Rectangular 240v	£0.34
1547	MES Batten Holder	£0.18

CARBON FILM RESISTOR PAKS

These paks contain a range of Carbon Film Resistors, assorted into the following groups:

R1	80 Mixed 1w 100 ohms-820 ohms	£1.00
R2	80 Mixed 1w 1K ohms-8.2K ohms	£1.00
R3	80 Mixed 1w 10K ohms-82K ohms	£1.00
R4	80 Mixed 1w 100K ohms-1M	£1.00
R5	60 Mixed 1w 100 ohms-820 ohms	£1.00
R6	60 Mixed 1w 1K ohms-8.2K ohms	£1.00
R7	60 Mixed 1w 10K ohms-82K ohms	£1.00
R8	60 Mixed 1w 100K ohms-1M	£1.00

TANTALUM BEAD CAPACITORS

401	0.1uf 16v	£0.11	414	47.0uf 16v	£0.55
402	0.22uf 16v	£0.11	415	100uf 10v	£0.62
403	0.33uf 16v	£0.11	416	1uf 35v	£0.12
404	0.47uf 16v	£0.11	417	22uf 35v	£0.12
405	0.68uf 16v	£0.11	418	33uf 35v	£0.12
406	1.0uf 16v	£0.11	419	47uf 35v	£0.12
407	2.2uf 16v	£0.12	420	68uf 35v	£0.12
408	3.3uf 16v	£0.13	421	1.0uf 35v	£0.12
409	4.7uf 16v	£0.14	422	2.2uf 35v	£0.13
410	6.8uf 16v	£0.15	423	3.3uf 35v	£0.15
411	10.0uf 16v	£0.16	424	4.7uf 35v	£0.18
412	22.0uf 16v	£0.28	425	6.8uf 35v	£0.30
413	33.0uf 16v	£0.50	426	10.0uf 35v	£0.38

FAIRCHILD/DARLINGTONS

TYPE	Pol	VCEO	VCEO	I.C.	HFE	CASE	£ p
2N6052	PNP	100v	100v	12A	750-18K	T03	1.50
2N6282	NPN	60v	60v	20A	750-18K	T03	1.25
MJ3000	NPN	60v	60v	10A	1KMN	T03	1.00
SE9300	NPN	60v	60v	10A	1000	T0220	0.90
SE9031	NPN	80v	80v	10A	1000	T0220	0.95
SE9304	NPN	80v	80v	10A	1000	T03	0.95
SE9305	NPN	100v	100v	10A	1000	T03	1.00
SE9401	PNP	-80v	80v	10A	1000	T0220	1.10
TIP115	PNP	60v	60v	2A	1A	T0220	0.40
TIP117	PNP	100v	100v	2A	1K	T0220	0.50
TIP120	NPN	60v	60v	5A	1K	T0220	0.60
TIP121	NPN	80v	80v	5A	1K	T0220	0.65
TIP122	NPN	100v	100v	5A	1K	T0220	0.68
TIP126	PNP	80v	80v	5A	1K	T0220	0.70
TIP127	PNP	100v	100v	5A	1K	T0220	0.72

POWER SUPPLIES

137	AC-DC Adaptor 6, 7, 9 & 12 volts	£3.75
138	DC-AC Adaptor 6, 7, 9 volts	£2.70

CABINETS

139	Teak 30 Case	£7.00
140	Teak 60 Case	£9.50

Access and Barclaycards accepted - just telephone our Orderline - Ware (STD 0920) 3182. All prices exclude V.A.T., add 50p postage per order. Terms: C.W.O., cheques, Postal Orders payable to Bi-Pak at addresses below.

BI-PAK

SEMICONDUCTORS
Dept. PW4, P.O. BOX 6, WARE, HERTS.
Tel: Ware (STD 0920) 3442. Telex: 817861.
Giro No. 3887006.
Visit our shop at: 3, Baldock St, Ware, Herts.



We're giving away this soldering iron worth over £10.



Choose any of 10 selected kits from the Heathkit catalogue as your first order, and we'll give you a superb soldering iron worth over £10. Plus a 10% discount!

These kits have been specially designed with first-time kit builders in mind. So even if you've never built an electronic kit before you won't find it difficult. In fact, the simple to follow step-by-step instructions make it easy to build any Heathkit kit.

And with your special offer discount you can afford to see just how easy it is.

Full details of this FREE offer are available in the Heathkit 48 page catalogue. So send the coupon for your copy now.

To: Heath Electronics (UK) Limited, Dept. (PW4), Bristol Road, Gloucester, GL2 6EE.

Please send me a copy of the Heathkit catalogue. I enclose 25p in stamps.

Name _____

Address _____

NB: If you are already on the Heathkit mailing list you will automatically receive a copy of the latest Heathkit catalogue without having to use this coupon.

RST

VALVE MAIL ORDER CO.
Climax House
159 Fallsbrook Road, London SW16 6ED
SPECIAL EXPRESS MAIL ORDER SERVICE

AZ31	1.0	EM87	1.50	PY81	0.84	6AN5	4.74	607	2.20
CL33	2.00	EN81	3.50	PY82	0.80	6AN8A	3.45	62A7	1.45
DY86/7	0.84	EY81	1.75	PY83	0.70	6A0	0.96	6SC7	1.50
DY802	0.84	EY86	0.84	PY88	0.88	6AR5	1.98	6SJ7	1.60
E88CC	3.36	EY88	1.75	PY500A	1.80	6AS6	4.98	6SK7	1.30
E180F	8.40	EY500A	1.94	PY800	0.84	6AS7GA	6.75	6SL7GT	2.68
E181F	12.72	EZ80	0.84	PY801	0.84	6AT6	0.85	6SN7GT	1.60
EABC80	1.20	EZ81	0.84	QV02-6	12.56	6AUSGT	3.72	6X5GT	2.35
EB91	0.82	GY501	2.75	QV03-10		6AU6	1.08	6SG7M	2.50
EBF80	0.50	GZ32	1.25	QV03-10A	5.80	6AW8A	3.39	6U8	0.80
EBF89	0.85	GZ33	4.00	QV03-20A		6B7	1.50	6V6GT	1.60
EC31	7.56	GZ34	2.50		17.50	6B8	1.75	6X4	1.20
ECC33	3.50	GZ37	4.00	QV06-40A		6BA6	1.00	6X5GT	0.85
ECC35	3.50	KT66	10.00	QV03-12	4.46	6BE6	1.08	7C5	2.95
ECC81	0.88	KT77	8.00	R18	4.25	6BH6	1.52	7C6	2.25
ECC82	0.72	KT88	12.00	R19	1.20	6BJ6	1.08	7S7	2.25
ECC83	0.88	N78	9.00	SP41	6.00	6BN6	1.65	12A7E	1.20
ECC85	1.20	OA2	1.92	SP61	2.00	6BQ7A	3.72	12A7G	0.88
ECC88	1.90	OC2	2.80	U119	13.75	6BR7	4.00	12AX7	0.88
ECC91	8.93	OC2	1.92	U25	1.16	6BR8	1.75	12BA6	2.19
ECF80	1.08	OD3	1.92	U26	1.44	6BS7	4.00	12BE6	2.43
ECH35	2.00	PC86	1.40	U37	9.00	6BW6	4.00	12BY7	2.70
ECH42	1.15	PC88	1.40	UABC80	1.25	6BW7	1.52	12BY7A	2.70
ECH81	1.20	PC82	1.28	UBF89	1.20	6BZ6	2.37	12GH7	4.17
ECL80	1.00	PC97	1.20	UCH42	1.20	6C4	0.88	30FL1/2	1.12
ECL82	1.00	PC900	1.20	UCH81	2.32	6C6	1.75	30P4	1.20
ECL83	1.50	PCF80	1.00	UCL82	1.04	6CB6A	2.49	30P19	1.20
ECL86	1.20	PCF82	1.00	UCL83	1.44	6CD6GA	5.07	30PL13	1.80
EF37A	3.50	PCF86	1.60	UF89	1.44	6CH6	8.50	30PL14	1.68
EF38	1.60	PCF81	1.60	UL1	2.50	6CL6	3.72	57B	27.85
EF41	2.00	PCF802	1.90	UL84	1.20	6CW4	7.68	85A2	2.39
EF42	2.00	PCF805	1.60	UY41	1.25	6D6	1.75	90C1	2.44
EF50	1.50	PCF808	1.60	UY85	1.04	6DQ5	5.94	150B2	3.02
EF54	5.00	PCH200	1.60	VR105/30	1.92	6EAB	2.94	150C2	1.92
EF55	2.50	PCL82	1.00	VR150/30	1.92	6EH5	1.85	150C4	2.39
EF60	0.80	PCL83	2.00	Z803	16.80	6F6	1.75	6G7	2.39
EF86	1.52	PCL84	1.00	Z803U	7.90	6GK6	2.67	80S7	20.00
EF91	1.80	PCL85	1.08	ZD21	3.50	6H6	1.50	807	3.75
EF92	5.81	PCL86	1.08	3B28	16.80	6HS6	3.77	811A	15.93
EF183	0.80	PCL805	1.08	4CX250B		6J5	2.50	812A	15.88
EF184	0.84	PD500	3.60		27.50	6J6	3.50	813	74.67
EH90	1.40	PFL200	1.80	5R4GY	1.80	6J7	2.50	866A	4.35
EL32	1.50	PL36	1.20	5U4G	1.52	6JB6A	4.56	872A	18.67
EL33	3.50	PL81	1.20	5V4G	1.52	6JS6C	5.58	931A	14.76
EL34	2.20	PL82	1.20	5Y3GT	0.85	6K4N	1.25	2050	6.96
EL36	1.60	PL83	2.22	5Z3	1.50	6K6GT	1.30	5763	3.75
EL81	2.50	PL84	1.08	5Z4GT	1.50	6K7	1.50	5B14A	4.32
EL84	1.00	PL504	1.40	6/3DL2	1.56	6K8	1.75	5842	12.09
EL86	2.50	PL508	1.80	6AB7	1.50	6KD6	6.36	6080	6.85
EL91	7.14	PL509	3.20	6AH6	4.71	6LG6	2.50	6146A	8.96
EL95	1.32	PL519	3.20	6AK5	3.60	6L6GC	2.50	6146B	7.06
EL360	8.50	PL802	2.96	6AL5	0.82	6L7	2.00	6883B	11.19
EM81	1.00	PY33	1.10	6AM6	1.80	6L6	6.72	6973	3.87

Open daily to callers: Mon-Fri 9 a.m.-5 p.m.
Valves, Tubes and Transistors - Closed Saturday
Terms C.W.O. only Tel. 01-677 2424-7.
Quotations for any types not listed S.A.E.
Prices excluding VAT add 15% Post and packing 35p per order
Telex 946708 Prices correct when going to press

PCB's FOR PRACTICAL WIRELESS PROJECTS

March 79	Wide Band Noise Source	WRO36	£1.10
April 79	FM Multitester	WRO40	£3.35
May 79	Car Test Probe	WRO42	£2.28
May 79	Follow up to Gillingham	WRO44	£1.75
May 79	PW Imp	WRO43	£1.72
May 79	Inline Crystal Calibrator	WRO41	£1.98
June 79	Jumbo Clock PCB - Special Offer		£7.00
July 79	Logical Noughts and Crosses	WRO46/7/8/9	£12.00
July 79	A/V Voltmeter	WRO55	£1.35
July 79	AAM/FM Frequency Readout	WRO52	£3.96
July 79	V. Moss Top Band Trans.	WRO56	£4.28
August 79	Sound Operated Switch	WRO056	£4.00
August 79	Telephone Bell Repeater	WRO53	£1.35
August 79	Automatic Intercom	WRO45	£6.50
August 79	Automatic Intercom Part 2	WRO58	£8.95
September 79	Noise Blanking	WRO57	£1.55
September 79	Burglar Alarm	WRO59	£1.53
October 79	Burglar Alarm	WRO60	£2.25
January 80	Radio Control Receiver	WRO64	£2.68
January 80	A. F. Speech Processor	WRO68	£2.68
January 80	Parkhurst Alarm	WRO63	£2.81
January 80	Wide Band RF Pre Amp	WRO67	£1.05
January 80	Radio Control Encoder	WRO61	£2.56
January 80	Radio Control TX	WRO62	£2.56
March 80	Duel Trace Unit - Special Offer	WRO69	£4.00
April 80	Speed Controller	WRO65	£1.70
April 80	Stereo Auto Fader Mike Pre Amp	WRO71	£3.46
April 80	Stereo Auto Main Board	WRO72	£3.00
April 80	Signal Generator	WRO70	£3.00
April 80	Nimbus Relay	W075	£0.95
April 80	Nimbus Modulator	WRO74	£1.10
April 80	Nimbus Transceiver	WRO73	£5.50
May 80	Hundred Second Photo Timer	WRO78	£2.78
May 80	N.B.F.M. Demodulator	WAD509	£2.20
June 80	Audio Limiter Main Board	WKO76	£2.30
June 80	Audio Limiter	WKO77	£1.45
June 80	Audio Limiter RF Input Board	WRO79	£1.60
June 80	VHF/UHF Repeater Timer Board	WRO80	£2.25
June 80	Nimbus Base Station Adpt.	WRO83	£2.90
June 80	Acoustic Flash Trigger	WKO84	£1.65
August 80	Model Railway Controller	WRO85	£2.47
September 80	Tranceiver Power Unit	WRO95	£1.05
September 80	Nimbus Toneburst/Timer Mod.	WRO96	£2.15
September 80	Beginners 2 Meter Converter	WAD634	£1.38
September 80	Tamar Boards, Full set - Special Offer		£7.00
October 80	Direct Conversion Receiver	WRO82	£1.70
October 80	Nimbus 7	WRO97	£1.10
November 80	Linear Scale Res. Meter	WAD641	£1.25
November 80	Field Test Set	WK100	£1.25
November 80	Field Test Set	WK101	£1.25
December 80	P.W. Helford	C4CLF	Set of Two £2.59
December 80	P.W. Helford V.F.O.	WR104	£0.85
December 80	P.W. Helford Buffer Amp.	WR103	£1.25
December 80	Bird Scarer	WRO101	£1.29
December 80	Bird Scarer	WRO102	£1.40
January 81	P.W. Twynham Multimeter	WR111	£4.47
January 81	P.W. Helford Preselector	WRO54	£1.20
January 81	P.W. Helford T.X. Pre Amp	WR105	£1.20
February 81	P.W. Helford T.X. First Pre Amp	WR107	£1.20
February 81	Accented Metronome	WK102	£1.86
February 81	P.W. Morse Tutor	WRO81	£3.70
February 81	P.W. Morse Tutor Power Supply	WR114	£1.20
February 81	Tape Slide Controller	Set of three	£7.50

Prices include VAT Post free
Full range of R. S. Components available please phone for quote
C. BOWES ELECTRONICS
252A STOCKPORT ROAD, CHEADLE HEATH, CHESHIRE SK3 0LX.
Tel: 061-428 4497 ex. 5

High Precision Quartz Timepieces. Low 'Only-From- Mitrad' Prices.

Special limited period offer of Mitrad quartz watches and pen watch at sensationally low, low, prices.

MITRAD MD610 GENTLEMAN'S QUARTZ MELODY ALARM CHRONOGRAPH

A super slim and elegantly styled high precision quartz watch with very clear digital presentation. Continuous display of hours, minutes and seconds plus date and mode indications. 'Running horse' style chronograph accurate to 1/10 second. 12 hour alarm plays 30 seconds of 'The Yellow Rose of Texas'. Pushbutton illumination. Stainless steel case (only 5mm thick) with black panel. Infinitely adjustable stainless steel strap.

SPECIAL OFFER PRICE

Only £12.95

plus £1.25 p&p

Trade £8. Add 15% VAT + £1.50 p&p per order (minimum order 5 items, one style or mix of styles).

MITRAD MD605 LADIES QUARTZ MELODY ALARM CHRONOGRAPH

Beautifully simple styling combined with high precision quartz technology. Continuous display of hours, minutes and seconds with an optional display of day, date and month. Auto calendar. Chronograph with lap timing facility accurate to 1/10 second. 24 hour alarm plays 30 seconds of Beethoven's 'Für Elise'. Pushbutton illumination. Stainless steel case (9mm thick) with black panel. Infinitely adjustable stainless steel strap.

SPECIAL OFFER PRICE

Only £11.95

plus £1.25 p&p

Trade £8. Add 15% VAT + £1.50 p&p per order (minimum order 5 items, one style or mix of styles)

MITRAD PEN WATCH

Elegant stainless steel ballpoint pen cleverly combined with a quartz high precision timepiece. The five function LCD watch continuously displays hours and minutes, with alternative displays of seconds or month and date. Computerised four year date memory. In presentation case with spare pen refill.

SPECIAL OFFER PRICE

Only £9.95

plus £1.25 p&p

Trade £7. Add 15% VAT + £1.50 p&p per order (minimum order 5 items, one style or mix of styles)

The premier mail order house specialising in quality products and superior after-sales care.

☎ Credit card holders may telephone (0536) 522024 24 hours a day stating card number for immediate attention.



MITRAD

68/70 High Street, Kettering,
Northants. NN16 8SY
Telephone 0536 522024

NB. Please do not use the coupon for trade orders.

To Mitrad 68/70 High Street, Kettering, Northants.

Please send me

- Mitrad MD610 Gentleman's Quartz Melody Alarm Chronograph at £14.20 (incl. p&p)
- Mitrad MD605 Ladies Quartz Melody Alarm Chronograph at £13.20 (incl. p&p)
- Mitrad Pen Watch at £11.20 (incl. p&p)

Total value of my order £ _____

Allow up to 28 days for delivery. Full refund if not completely satisfied. Registered in England No. 2554356.

I enclose cheque/PO made payable to Mitrad

Or debit my Access/Barclaycard No. _____


Signature _____

Name _____

Address _____

PW 4/81

(BLOCK LETTERS PLEASE)

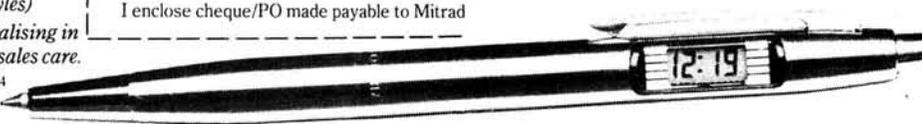

HIGH POWER MODULE KITS

SPECIFICATIONS

Max. Output power 125 watt RMS
 Operating voltage (DC) 50-80 Max.
 Loads 4-16 ohms
 Frequency response Measured at 100 watts 25Hz-20KHz
 Sensitivity for 100 watts 400mV @ 47K
 Typical T.H.D. @ 50 watts 4 ohms load 0.1%
 Dimensions 205 x 90 and 190 x 36mm.
 The P.E. power amp kit is a module for high power applications—disco units, guitar amplifiers, public address systems and even high power domestic systems. The unit is protected against short circuiting of the load and is safe in an open circuit condition. A large safety margin exists by use of generously rated components, result, a high powered rugged unit. The PC Board is backprinted, etched and ready to drill for ease of construction, and the aluminium chassis is preformed and ready to use. Supplied with all parts, circuit diagrams and instructions.

ACCESSORIES

Suitable LS coupling electrolytic for 125W. model £1.00 plus 25p p&p.
 Suitable LS coupling electrolytic for 200W. model £1.25 plus 25p p&p.
 Suitable Mains Power Supply Unit for 125W. model £7.50 plus £3.15 p&p.
 Suitable Twin Transformer Power Supply for 200W. model £13.95 plus £4.00 p&p.

125 WATT MODEL

£10.50
 plus £1.15 p&p. (Illustrated)


200 WATT MODEL

£14.95
 plus £1.15 p&p

FREE!

MULLARD LP1183 STEREO PREAMP

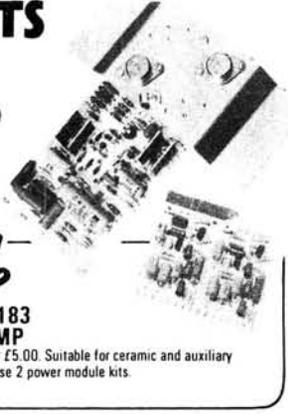Original listed price over £5.00. Suitable for ceramic and auxiliary inputs, when you purchase 2 power module kits.



STEREO DISCO PREAMPLIFIER

Matching other modules, suitable for twin deck mixing with P.F.L. output and Mic/Tape input. Ready built, ready to play with circuit diagram and application notes to suit our power module kits.

£21.95
 plus £1.72 p&p



10+10 WATT STEREO HI-FI AMPLIFIER KIT

● Featuring latest SGS/ATES/TDA 2006 10 watt output I.C.'s with in-built thermal and short circuit protection.

£14.95

plus £2.90 p&p

● Mullard Stereo Preamplifier module
 ● Attractive ready made black vinyl finish cabinet
 ● Converts to a 20 Watt Disco amplifier
 To complete you just supply connecting wire and solder. Features include din input sockets for ceramic cartridge, microphone, tape or tuner. Outputs—tape, speakers and headphones. By the press of a button it transforms into a 20 watt mono disc amplifier with twin deck mixing. The kit incorporates a Mullard LP1183 pre-amp module, plus power amplifier assembly kit and mains power supply. Also featured 4 slider level controls, rotary bass and treble controls and 6 push button switches. Silver finish fascia panel with matching knobs and contrasting ready made black vinyl finish cabinet and ready made metal work. For further information instructions are available price 50p. Free with kit. Size 9" x 8 1/2" x 3 1/2" approx.

SPECIFICATIONS Suitable for 4 to 8 ohms speakers. Frequency response - 40Hz-20KHz. Input Sensitivity - P.U. 150mV Aux. 200mV Mic. 1.5mV. Tone controls - Bass \pm 12db @ 60Hz; Treble \pm 12db @ 10KHz; Distortion - 1% typically @ 4 watts; Mains supply - 220-250 volts 50Hz.

BSR chassis record deck with manual set down and return, complete with stereo ceramic cartridge! **£8.50** plus £3.15 p&p when purchased with amplifier. Available separately **£10.50** plus £3.15 p&p.

8" SPEAKER KIT, 2 8" approx. twin cone domestic use speakers. **£4.75** per pair plus £1.70 p&p when purchased with amplifier. Available separately **£6.75** plus £1.70 p&p.

STEREO MAGNETIC PRE-AMP CONVERSION KIT
 All components including P.C.B. to convert your ceramic input on the 10+10 amp to magnetic. **£2.00** when purchased with kit featured above. **£4.00** separately inc. p&p.



30 + 30 WATT STEREO AMPLIFIER BUILT AND TESTED

Viscount IV unit in teak simulate cabinet silver finished rotary controls and pushbuttons with matching fascia, red mains indicator and stereo jack socket. Functions switch for mic magnetic and crystal pickups, tape and auxiliary. Rear panel features fuse holder. DIN speaker and input socket 30 + 30 watts. RMS 60 + 60 watts peak for use with 4 to 8 ohm speakers. Size 14 1/2" x 10" approx.

READY TO PLAY £32.90 plus £3.80 p&p

PRACTICAL ELECTRONICS CAR RADIO KIT

£10.50 plus £2.00 p&p


2 WAVE BAND MW LW

*Easy to build *5 push button tuning
 *Modern styling design *All new unused components
 *6 watt output *Ready etched & punched P.C.B.
 *Incorporates suppression circuits *Now with tape input socket

All components and instructions to build the radio, you supply only the wire and solder. Pre-set tuning with five push button options, black illuminated tuning scale, matching control knobs, one combining on/off volume and tone-control, the other for manual tuning.

The P.E. Traveller has a 6 watts output, neg ground and an integrated circuit output stage, a Mullard IF module LP1181 ceramic filter type, pre-aligned and assembled and a Bird pre-aligned push button tuning unit. Fits easily in or under dashboards.

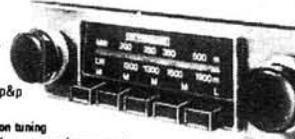Suitable stainless steel fully retractable locking aerial and speaker (approx. 6" x 4") is available as a kit complete **£1.95** per pack, p&p £1.15



323 EDGWARE ROAD, LONDON W2 Mail Order 21c HIGH ST. ACTON W3 6NG

ALL PRICES INCLUDE VAT AT 15%. All items subject to availability. Price correct at 5.2.81 and subject to change without notice. For further information send for instructions 20p plus stamped addressed envelope. Goods despatched to mainland and N. Ireland only. NOTE: Persons under 16 years not served without parent's authorisation. Personal Shoppers EDGWARE ROAD LONDON W2 Tel 01-723 8432 9.30am-5.30pm Closed all day Thursday. ACTON: Mail Order only. No callers.



Wilmslow Audio

THE firm for speakers!

SEND 50p FOR THE WORLD'S BEST CATALOGUE OF SPEAKERS, DRIVE UNITS, KITS, CROSSOVERS ETC. AND DISCOUNT PRICE LIST.

- AUDAX ● AUDIOMASTER ● BAKER ● BOWER & WILKINS ● CASTLE ● CELESTION ● CHARTWELL ● COLES ● DALESFORD ● DECCA ● EAGLE ● ELAC ● EMI ● FANE ● GAUSS ● GOODMAN'S ● HARBETH ● ISOPHON ● I.M.F. ● JORDAN ● JORDAN WATTS ● KEF ● LOWTHER ● McKENZIE ● MISSION ● MONITOR AUDIO ● MOTOROLA ● PEERLESS ● RADFORD ● RAM ● ROGERS ● RICHARD ALLAN ● SEAS ● SHACKMAN ● TANGENT ● TANNOY ● VIDEOTONE ● WHARFEDALE ●

WILMSLOW AUDIO LTD. (Dept. P.W.)

35/39 CHURCH STREET, WILMSLOW, CHESHIRE SK9 1AS

Tel: 0625 529599

FOR MAIL ORDER & EXPORT OF DRIVE UNITS, KITS ETC.

Tel: 0625 526213

(SWIFT OF WILMSLOW) FOR HI-FI & COMPLETE SPEAKERS

OHIO SCIENTIFIC COMPUTERS new series 2 Challenger C1P Cheapo 4K version **£202**. Ohio 8K version **£259**. Special offer—Superboard 3 with free power supply and modulator kit and guard band kit (gives 32-32 extended display, 1200 and 300 baud tape speeds, 50% higher computing speed and 50Hz conversion) **£159** the lot. Guard band kit also sold separately **£10**. 4K extra ram **£16.95**. Case **£27**. Cassette recorder **£16**. Cegmon improved monitor rom **£29.50**. Assembler/Editor **£25**. Word processor **£10**. Display expansion kit 30 lines-54 characters for superboard TWO **£20**.
SHARP MZ80K COMPUTER with free tape of 50 programs 20K **£415**. 36K **£437**. 48K **£459**.
PRINTERS supplied with free interface and word processor for Superboard and UK101: Seikosha GP80 **£225**. Oki Microline 80 **£329**. Base 2 800MST **£299**.
SINCLAIR PRODUCTS SC110 **£145**. PFM200 **£51.95**. DM450 **£109**. PDM35 **£32.50**.
TV GAMES AY-3-8600 - kit **£12.98**. AY-3-8550 - kit **£9.26**.
BATTERY ELIMINATORS 3-way type 6/7; 9v 300ma **£3.50**. 100ma radio type with press studs 9v **£4.77**, 9 - 9v **£5.99**. Car converter 12v input, output 4 1/2; 6/7; 9v **800ma** **£3.04**.
MEMORIES 2114 450ns **£2.15**. 4116 200ns **£2.83**. 4027 **£1.30**. All low current.
BATTERY ELIMINATOR KITS 100ma radio types with press studs 9v **£1.64**, 9 - 9v **£2.30**. Stabilized 8-way types 3/4; 6/7; 9/12/15/18v 100ma **£3-12**, 1 Amp **£8-10**. Stabilized power kits 2-18v 100ma **£3-12**, 1-30v 1A **£8-30**, 1-30v 2A **£14-82**. TTL and computer supplies 5v stabilized 1-5A **£9**, 3A **£11**, 6A **£16**. 12v car converter 6/7; 9v 1A **£1-62**.
T-DEC AND S-DEC BREADBOARDS s-dec **£3-79**. t-dec **£4-59**. exp4b **£2-64**. exp300 **£6-61**.
BI-PAK AUDIO MODULES AL30A **£4-53**. AL60 **£5-62**. SPM80 **£5-26**. BM780 **£6-36**.
IC AUDIO AMPS with pcb. JC12 6W **£2-50**. JC20 10W **£3-54**.

SWANLEY ELECTRONICS

Dept. PW, 32 Goldsel Rd., Swanley, Kent. Post 40p extra. Add VAT except on sections marked *. Lists 27p post free. Phone Swanley 64851. Official and overseas orders welcome.

AERIAL SPLITTERS

Two way in white box with three black insulated co-ax sockets. Completely made up with two spare co-ax plugs. Price only **£1.70** each.

CALLERS WELCOME

Large stock of capacitor, resistors, P.C.B. etching compound, TV valves, loft aerial and co-ax cable. Open for Callers: Tuesday, Thursday, Friday and Saturday morning.

AERIAL BOOSTERS

Aerial amplifiers can produce remarkable improvement on the picture and sound in fringe or difficult areas.

B45 - For Mono or Colour this is tunable over complete UHF television band.

B11 - For stereo or standard VHF/FM radio.

Next to the set fitting. Price **£6.70** each.

Signal Injectors with (pre-set) variable AF, which emits RF harmonics into the UHF band. Protected up to 300 volts DC. Complete with leads **£5.70** each.

All Prices include VAT at 15%. P & P per Order 30p. S.A.E. for Leaflets. Access Cards.

ELECTRONIC MAILORDER LTD.

62 Bridge St. Ramsbottom, via Bury, Lancs. BL0 9AGW.

Tel Rams (070 682) 3036.

AND THERE'S MORE WHERE THIS CAME FROM

It's a long time since one of our adverts was presented in 'list' form - but simply because we do not try to squeeze this lot in every time doesn't mean that it's not available. Our new style price list (now some 40 pages long) includes all this and more, including quantity prices and a brief description. The kits, modules and specialized RF components - such as TOKO coils, filters etc. are covered in the general price list - so send now for a free copy (with an SAE please). Part 4 of the catalogue is due out now (incorporating a revised version of pt.1).

LINEAR ICs - NUMERIC LISTINGS

TBA120S	1.00	KB4413	1.95
L200	1.95	KB4417	1.80
U237B	1.28	TD4420	2.25
U247B	1.28	KB4420B	1.09
U257B	1.28	KB4423	2.30
U267B	1.28	KB4424	1.65
LM301H	0.67	KB4431	1.95
LM301N	0.30	KB4432	1.95
LM308H	0.96	KB4433	1.52
LM308N	0.65	KB4436	2.53
LM339N	0.66	KB4437	1.75
LM348N	1.86	KB4438	2.22
LF351N	0.38	KB4441	1.35
LF352N	0.76	KB4445	1.29
LM374N	3.75	KB4446	2.75
LM380N-14	1.00	KB4448	1.65
LM380N-8	1.00	NE5044N	2.26
LM381N	1.81	NE5532N	1.85
ZN419CE	1.95	SD6000	3.75
NE544N	1.80	SL6270	2.03
NE555N	0.30	SL6310	2.03
NE556N	0.50	SL6600	3.75
NE560N	3.50	SL6640	2.75
NE562N	4.05	SL6690	2.60
NE564N	4.29	SL6700	2.35
NE565N	1.00	ICL8038CC	4.50
NE566N	1.60	MSL9362	1.75
NE570N	3.85	MSL9363	1.75
SL624	3.28	HA11211	1.95
TB9651	1.81	HA11223	2.15
uA709BC	0.64	HA11225	1.45
uA709BC	0.36	HA12002	1.45
uA710HC	0.65	HA12017	0.80
uA710PC	0.59	HA12402	1.95
uA7141C	0.66	HA12411	1.20
uA7141CN	0.27	HA12412	1.55
uA7147CN	0.70	LF13741	0.33
uA748CN	0.36	SN76660N	0.80
uA753	2.44		
uA758	2.35		
TB810AS	1.09		
TB820M	0.75		
TC9A04E	1.80		
TD11028	2.11		
TD11029	2.11		
TD1054	1.45		
TD1062	1.95		
TD1072	2.69		
TD1074A	5.04		
TD1083	1.95		
TD1090	3.05		
HA1137	1.20		
HA1196	2.00		
HA1197	1.00		
TD1220	1.40		
LM1303	0.99		
LM1307	1.55		
MC1310P	1.90		
MC1330	1.20		
MC1350	1.20		
HA1370	1.90		
HA1388	2.75		
LM1498	1.86		
MC1496P	1.25		
SL1610P	1.60		
SL1611P	1.60		
SL1621P	1.60		
SL1620P	2.17		
SL1621P	2.17		
SL1623P	2.24		
SL1624C	3.28		
SL1625P	2.17		
SL1626P	2.44		
SL1630P	1.62		
SL1640P	1.89		
SL1641P	1.89		
TD2002	1.25		
UJ2242A	3.00		
UJ2283B	1.00		
CA3308E	0.70		
CA3308E	1.84		
CA33090AQ	1.35		
CA3123E	1.40		
CA3130E	0.80		
CA3130T	0.90		
CA3140E	0.46		
CA3189E	2.20		
MC3357P	2.35		
LM3902N	0.60		
LM3909N	0.68		
LM3914N	2.80		
LM3915N	2.80		
KB4400	0.80		
KB4406	0.60		
KB4412	1.95		

TTL Nand LSN

7443N	1.15	74LS112	0.38
7444N	1.12	74LS113	0.38
7445N	0.94	74LS114	0.38
7446N	0.94	74LS118	0.83
7447N	0.89	74LS120	1.15
7448N	0.56	74LS121	0.42
7449N	0.99	74LS122	0.46
7450N	0.20	74LS123	0.73
7451N	0.17	74LS124	1.75
7452N	0.20	74LS125	0.38
7453N	0.17	74LS125	0.44
7454N	0.17	74LS126	0.57
7455N	0.24	74LS128	0.74
7456N	0.28	74LS129	0.73
7457N	0.38	74LS132	0.78
7458N	0.17	74LS136	0.40
7459N	0.24	74LS138	0.60
7460N	0.17	74LS141	0.56
7461N	0.38	74LS142	2.65
7462N	0.28	74LS143	3.12
7463N	0.38	74LS144	3.12
7464N	0.28	74LS145	0.97
7465N	0.37	74LS147	1.75
7466N	0.37	74LS148	1.09
7467N	0.44	74LS148	1.19
7468N	0.38	74LS150	0.99
7469N	0.86	74LS151	0.55
7470N	0.69	74LS151	0.84
7471N	1.04	74LS153	0.64
7472N	0.99	74LS153	0.54
7473N	0.24	74LS155	1.10
7474N	0.29	74LS155	1.10
7475N	0.33	74LS156	0.80
7476N	0.27	74LS157	0.67
7477N	0.27	74LS157	0.55
7478N	0.44	74LS158	0.60
7479N	0.35	74LS159	2.20
7480N	0.17	74LS159	0.99
7481N	0.24	74LS160	1.30
7482N	0.25	74LS161	0.92
7483N	0.25	74LS161	0.78
7484N	0.40	74LS162	1.30
7485N	0.33	74LS163	0.92
7486N	0.24	74LS163	0.78
7487N	0.17	74LS164	1.04
7488N	0.24	74LS164	1.05
7489N	0.74	74LS165	1.04
7490N	0.70	74LS165	2.50
7491N	0.54		
7492N	0.68		

FREQUENCY DISPLAY & SYNTHESIZER ICs

SAAL056	3.75
SAAL058	3.35
SAAL059	3.35
11C90DC	14.00
LA1232	19.00
LA1242	19.00
MSL2318	3.84
MSM5523	11.30
MSM5524	11.30
MSM5525	7.85
MSM5526	7.85
MSM5527	9.75
MSM5527I	9.75
ICM7106CP	9.55
ICM7107CP	9.55
ICM7118A	19.25
ICM7121A	9.50
SP8629	3.85
SP8647	6.00
95H90PC	6.00
HD10551	2.45
HD44015	4.45
HD12009	6.00
HD44752	8.00

CMOS 4000 SERIES

4001	0.17
4000	0.17
4002	0.23
4008	0.80
4009	0.58
4010B	0.58
4011AE	0.20
4011B	0.20
4012	0.55
4013	0.55
4015	0.95
4016	0.52
4017	0.80
4019	0.60
4020B	0.93
4021	0.82
4022	0.90
4023	0.17
4024	0.76
4025	0.17
4026	1.80
4028	0.72
4029	1.00
4030	0.58
4035	1.20
4040	0.83
4042	0.85

VOLTAGE REGULATORS

78series	0.95
79series	1.00
78Mseries	0.65
78Lseries	0.35
79L05	0.85
78M27C	1.75
79M27C	1.75
723CN	0.65
L200	1.95
TD1412	0.75
NE5553N	1.25
LM317MP	1.48
LM337MP	1.48

MICROMARKET

8080A/2	7.50
8212	2.30
8214	3.50
8216	1.95
8224	3.50
8251	6.25
8255	5.40
6800P	7.50
6810	5.95
6820	7.45
6850	4.90
6852	4.85
MC2708	7.50
2114	6.50
4027	5.78
2102	1.70
2112	3.40
2513	7.54
HM4716	4.50
81LS97	1.25

TOKO COILS AND FILTERS

SEE THE EXTENSIVE SECTION IN OUR NEW PRICE LISTS AND CATALOGUE

LF/HF FIXED INDUCTORS

-FULL E12 RANGE-

7BA series 1uH-1mH 0.16

8RB series 0.19

100uH-33mH 0.19

10RB series 0.33

33mH-120mH 0.33

10RH series 0.55

120mH-1.5H 0.55

PIEZO SOUNDER PB2720 0.44

CRYSTAL FILTER PRODUCTS

10.7MHz 2 POLE TYPES: 5MM RED 0.12

10M15A 15KHZ BW 2.49 3MM RED CLEAR 0.15

10.7MHz 8 POLE TYPES: 3MM RED 0.15

10M41 15kHz BW 14.50 2.5 X 5MM RED 0.17

H4402 7.5kHz BW 15.50 5MM GREEN 0.15

10M22D 2.4kHz SSB 17.20 3MM GN CLEAR 0.16

HF FIRST FILTER: 3MM GREEN 0.16

B34F8A 34.5MHz HF 32.00 2.5 X 5MM GN 0.20

5MM YELLOW 0.15

3MM YELLOW CL 0.16

3MM YELLOW 0.18

2.5 X 5MM YE 0.20

5MM ORANGERED 0.20

5MM ORA CL 0.29

3MM ORANGERED 0.19

2.5 X 5MM ORA 0.24

5MM INFRA RED 0.56

BW41 IR DET 1.51

IR OPT CPLR 1.44

5MM CLIP 0.04

CRYSTALS

32.768 kHz 2.70

100kHz 3.85

455kHz 5.00

1.0MHz 3.00

3.276MHz 2.70

4.000MHz 2.30

4.19439MHz 2.00

6.5536MHz 2.10

10.0MHz 2.50

10.6985MHz 2.50

10.7015MHz 2.50

10.245MHz 2.50

10.7MHz 3.00

11.52MHz 2.50

100MHz 3.00

VARICAP

BA102	0.30
BA121	0.30
ITT210	0.30
BB2048	0.36
BB1058	0.36
BB109	0.27
MM125	1.05
BB212	1.95
KV1210	2.45
KV1211	1.75
KV1226	1.95
KV1225	2.75
KV1215	2.55
KV1225	2.75

SWITCHING AND PIN DIODES

SHOTTKY DIODES

1N6263 0.62

BA182 0.19

BA244 0.17

BA379 0.35

TD1061 0.95

SIGNAL DIODES & RECTIFIERS

1N4148 0.06

1N4001 0.06

1N4002 0.15

1N5402 0.07

OA91 0.07

AA112 0.25

BRIDGES:

1A/50V 0.35

6A/200V 0.75

TRANSISTORS

AUDIO DEVICES

BC237	0.08
BC238	0.08
BC239	0.08
BC307	0.08
BC308	0.08
BC309	0.08</

Technical Training in Radio, Television and Electronics

ICS have helped thousands of ambitious people to move up into higher paid, more secure jobs in the field of electronics—now it can be your turn. Whether you are a newcomer to the field or are already working in the industry, ICS can provide you with the specialised training so essential to success.

Personal Tuition and Guaranteed Success

The expert and personal guidance by fully qualified tutors, backed by the ICS guarantee of tuition until successful is the key to our outstanding record in the technical training field. You study at the time and pace that suits you best and in your own home. In the words of one of our many successful students: "Since starting my course, my salary has trebled and I am expecting a further increase when my course is completed."

City and Guilds Certificates

Excellent job prospects await those who hold one of these recognised certificates. ICS can coach you for:

- Telecommunications Technicians
- Radio, TV Electronics Technicians
- Technical Communications
- Radio Servicing Theory
- Radio Amateurs
- Electrical Installation Work
- Also MPT Radio Communications Certificate

Diploma Courses

- Colour TV Servicing
- Electronic Engineering and Maintenance
- Computer Engineering and Programming
- Radio, TV and Audio, Engineering and Servicing
- Electrical Engineering, Installations and Contracting

Qualify for a New Career

Home study courses for leading professional examinations and diploma courses for business and technical subjects:—

G.C.E.	Engineering	Purchasing
60 subjects	Farming	Sales
at "O" & "A" levels	Heating	Storekeeping
Accountancy	Industrial	Work Study
Air	Management	
Building	Mechanical	

POST OR PHONE TODAY FOR FREE BOOKLET.

ICS To: International Correspondence Schools

SINCE 1890
Dept. 276E Intertext House, London
SW8 4UJ or telephone 622 9911

Subject of Interest

Name

Address

Telephone Number

PM COMPONENTS LTD

VALVE & COMPONENT SPECIALISTS
CONINGSBY HOUSE, WROTHAM RD.,
MEOPHAM, KENT.

VALVES		PL509		6080		BC213L		BU108	
DY86	0.55	PL802	2.50	6146A	4.45	BC214	0.09	BU205	1.30
DY802	0.60	PY85	0.72	6146B	4.85	BC214L	0.09	BU208	1.39
E180F	5.65	PY500A	1.35	7012	7.05	BC237	0.09	BU208A	1.52
EABC80	0.56	PY801	0.60	7360	7.50	BC238	0.08	BU340	0.40
EBF89	0.70	QV02-6	8.25	7591	2.35	BC307	0.09	OC71	0.22
ECC81	0.55	QV03-20A				BC327	0.10	R2008B	1.70
ECC82	0.55		12.25			BC337	0.10	R2010B	1.70
ECC83	0.55	QV06-40A				BC461	0.30	R2540	2.48
ECC85	0.60		13.95			BC478	0.20	TIP29	0.40
ECC88	0.65	QV03-12	3.25	AC127	0.22	BC547	0.10	TIP29C	0.42
ECC807	1.30	TB2.5/300		AC128	0.28	BC548	0.10	TIP30C	0.43
ECF80	0.65		42.00	AC141K	0.34	BC549A	0.08	TIP31C	0.42
ECF82	0.60	TY2-125A	30.00	AC176	0.22	BC557	0.07	TIP32C	0.42
ECH81	0.58	U19	11.95	AC176K	0.31	BC558	0.07	TIP41C	0.45
ECL82	0.58	UCH81	0.70	AC187	0.22	BD131	0.32	TIP42C	0.47
ECL83	1.13	UCL82	0.70	AC187K	0.28	BD132	0.35	TIP47	0.65
ECL86	0.74	UL84	0.78	AC188	0.22	BD133	0.40	TIP2955	0.84
EF80	0.48	UY85	0.70	AD149	0.70	BD135	0.30	TIP3055	0.60
EF86	0.70	Z759	9.00	AD161	0.39	BD136	0.30	TIS91	0.20
EF89	0.65	ZD21	1.60	AD161/2	1.04	BD137	0.28	2N3054	0.59
EF91	1.22	4CX250B	21.75	AD162	0.39	BD138	0.30	2N3055	0.58
EF93	0.65	5R4GY	1.25	AF127	0.32	BD139	0.32	2N3702	0.12
EF94	0.65	5U4G	0.90	AF139	0.42	BD140	0.30	2N3703	0.12
EF95	0.78	6XK6	2.50	AF239	0.42	BD144	1.20	2N3704	0.12
EF183	0.56	6J6	0.65	BC107	0.10	BF115	0.35	2N3705	0.12
EF184	0.56	6JS6C	5.00	BC107B	0.10	BF167	0.24	2N3706	0.12
EL34	1.54	6KD6	4.50	BC108	0.10	BF179	0.34	2N3708	0.12
EL84	0.60	6L6GC	1.75	BC108C	0.10	BF180	0.29	2N5294	0.38
EM84	0.65	6LD20	0.60	BC109B	0.10	BF183	0.29	2N5296	0.48
EZ80	0.48	6LQ6	6.50	BC140	0.31	BF194	0.11	2N5298	0.38
EZ81	0.56	6SN7GT	0.90	BC141	0.25	BF195	0.11		
GZ32	0.76	6V6GT	1.05	BC142	0.21	BF196	0.11	IC's	
GZ33	1.85	757	2.00	BC143	0.24	BF197	0.11	MC1307	1.00
GZ34	2.00	12AT7	0.60	BC147	0.09	BF198	0.10	MC1350	1.00
KT61	3.50	12AU7	0.60	BC148	0.09	BF199	0.14	MC1495	3.00
KT66	4.00	12AX7	0.65	BC149	0.09	BF200	0.30	SN76003M	1.65
KT77	5.00	12B6A	0.80	BC157	0.10	BF257	0.28	SN76013M	1.15
KT88	6.00	12BE6	1.05	BC158	0.09	BF258	0.25	SN76013ND	1.15
N78	8.90	12BH7	0.95	BC159	0.09	BF259	0.25		
OA2	0.78	12HG7	3.50	BC160	0.28	BF336	0.34	SN76023M	1.35
PCF80	0.72	85A2	1.20	BC170B	0.10	BFX29	0.30	SN76033M	1.35
PCF802	0.66	90C1	1.69	BC171	0.08	BFX84	0.26	SN76131M	1.30
PCF808	1.48	807	1.09	BC172	0.09	BFX85	0.28	SN76227M	1.05
PCL82	0.68	811A	9.00	BC173B	0.10	BFX86	0.30	SN76660M	0.60
PCL84	0.72	813	11.30	BC182	0.09	BFX88	0.25	TA6618	1.20
PCL86	0.75	833A	47.85	BC183	0.09	BFY50	0.21	TBA120S	0.70
PCL805	0.80	866A	2.50	BC184LA	0.09	BFY51	0.21	TBA540	1.25
PFL200	1.13	2050A	3.90	BC212	0.09	BFY52	0.25	TBA550Q	1.55
PL504	1.13	5763	3.20	BC212L	0.09	BFY90	0.73	TBA641-B11	1.50
PL508	1.48	5814A	2.75	BC213	0.09	BU105	1.22		1.90

Prices exclude VAT
Please add 15%
P&P 50p per order

Many other types available
including vintage valves.
PHONE 0474 813225



Top Priority for every constructor—HOME RADIO CATALOGUE

- About 2,000 items clearly listed.
- Profusely illustrated throughout.
- Large A-4 size pages.
- Bargain list, order form and 2 coupons each worth 25p if used as directed, all supplied free.

Price £1, plus 50p for post, packing and insurance.

Send cheque or P.O. for £1.50

HOME RADIO Components LTD
Dept. PW, P.O. Box 92, 215 London Road,
Mitcham, Surrey. 01-543 5659

NICKEL CADMIUM BATTERIES

	AA (HP7) 0.5Ah	SUB 'C' 1.2Ah	'C' (HP11) 1.65Ah	'C' (HP11) 2.0Ah	'D' (HP2) 4.0Ah	PP3 0.1Ah
1-24	£0.85	£1.38	£1.69	£2.25	£2.97	£3.79
25-49	£0.82	£1.28	£1.58	£2.10	£2.77	
50-99	£0.80	£1.24	£1.52	£2.02	£2.67	
100 up	£0.70	£1.15	£1.41	£1.87	£2.47	

All cells are brand new full spec devices from reputable mfrs. All Nickel Cadmium cells (except PP3) are supplied complete with solder tags and are 'VENTED' devices suitable for fast charge.

CHARGERS—single or dual O/P to charge PP3, AA or SUB 'C' cells in 12-14 hrs (chargers will charge 'C' and 'D' cells but with longer charging time). Units supplied complete in plug top case with flying leads. Number of cells (10 max) in series and type must be specified for each required O/P when ordering.

SINGLE O/P CHARGER £5.04
DUAL O/P CHARGER £5.72

TRANSFORMERS—as used in chargers, 2 x 12 volt 0.25 amp secondaries 240v primary, tag connections £1.57 each.

Cheques, P.O.'s Mail Order to:-

SOLID STATE SECURITY,
Dept. (PW), Bradshaw Lane,
Parbold, Wigan, Lancs.
Telephone 02576-3018.

Data and charging circuits free with orders over £10 otherwise 30p post.
P&P 10% if order less than £10, 5% if order over £10. Prices DO NOT INCLUDE VAT and this should be added to the total order.

POPULAR KITS AND PARTS

TRANSMITTER SURVEILLANCE

Tiny, easily hidden but which will enable conversation to be picked up with FM radio. Can be made in a matchbox—all electronic parts and circuit. £2.30.

RADIO MIKE

Ideal for discos and garden parties, allows complete freedom of movement. Play through FM radio or tuner amp. £6.90.

SAFE BLOCK

Mains quick connector will save you valuable time. Features include quick spring connectors, heavy plastic case and auto on and off switch. Complete kit £1.95.

LIGHT CHASER

Gives a brilliant display—a psychedelic light show for discos, parties and pop groups. These have three modes of flashing, two chase-patterns and a strobe effect. Total output power 750 watts per channel. Complete kit. Price £16. Ready made up £4 extra.

FISH BITE INDICATOR enables anglers to set up several lines then sit down and read a book. As soon as one has a bite the loudspeakers emits a shrill note. Kit. Price £4.90.

6 WAVEBAND SHORTWAVE RADIO KIT

Bandspread covering 13.5 to 32 metres. Based on circuit which appeared in a recent issue of Radio Constructor. Complete kit. Includes case materials, six transistors, and diodes, condensers, resistors, inductors, switches, etc. Nothing else to buy, if you have an amplifier to connect it to on a pair of high resistance headphones. Price £11.95.

SHORT WAVE CRYSTAL RADIO

All the parts to make up the beginner's model. Price £2.30. Crystal earpiece 65p. High resistance headphones (give best results) £3.75. Kit includes chassis and front but not case.

RADIO STETHOSCOPE

Easy to fault find—start at the aerial and work towards the speaker—when signal stops you have found the fault. Complete kit £4.95.

INTERRUPTED BEAM KIT

This kit enables you to make a switch that will trigger when a steady beam of infra-red or ordinary light is broken. Main components—relay, photo transistor, resistors and caps etc. Circuit diagram but no case. Price £2.30.

OUR CAR STARTER AND CHARGER KIT has no doubt saved many motorists from embarrassment in an emergency you can start car off mains or bring your battery up to full charge in a couple of hours. The kit comprises: 250w mains transformer, two 10 amp bridge rectifiers, start/charge switch and full instructions. You can assemble this in the evening, box it up or leave it on the shelf in the garage, whichever suits you best. Price £11.50 + £2.50 post.

G.P.O. HIGH GAIN AMP/SIGNAL TRACER. In case measuring only 5 1/2" x 3 1/2" x 1 1/2" is an extremely high gain (70dB) solid state amplifier designed for use as a signal tracer on G.P.O. cables etc. With a radio it functions very well as a signal tracer. By connecting a simple coil to the input socket a useful mains cable tracer can be made. Runs on standard 4 1/2v battery and has input, output sockets and on-off volume control, mounted flush on the top. Many other uses include general purpose amp, curing amp, etc. An absolute bargain at only £1.85. Suitable 80 ohm earpiece 69p.

VU METER

Edgewise mounting, through hole size 1 1/2" x 1" approx. These are 100 micro amp I.S.D. and fitted with internal 6 volt bulb for scale illumination, also have zero reset. The scale is not calibrated but has very modern appearance. Price £2.89p.

BALANCE METER

Edgewise mounting 100 UA centre zero. Price £2.30p.

1 1/2" SQUARE PANEL METER

Eagle full vision plastic front, 50 UA. Price £4.60p 1 mA Price £4.03p.

WATERPROOF HEATING WIRE

60 ohms per yard. This is a heating element wound on a fibre glass coil and then covered with p.v.c. Dozens of uses—around water pipes, under grow boxes in gloves and socks. 23p metre.

DIAL INDICATOR

As used in tool making and other precision measuring operations, the famous John Bull accurately shows differences of 0.1mm. A beautifully made precision instrument, price in most tool shops would be £12-£15. We have a fair quantity. Price £9.20p.

COMPONENT BOARD Ref. W0998.

This is a modern fibre glass board which contains a multitude of very useful parts, most important of which are: 35 assorted diodes and rectifiers including four 3 amp 400v types (made up in a bridge) 8 transistors type BC 107 and 2 type BFY 51 electrolytic condensers, SCR ref. 2N 5062 25 00V 100v DC and 100v 25v DC and over 100 other components including variable and fixed wire wound resistors, electrolytic and other condensers. A real snip at £1.15.

FRUIT MACHINE HEART.

4 wheels with all fruits, motorised and with solenoids for stopping the wheels with a little ingenuity you can defy your friends getting the "jackpot." £9.95 + £4 carriage.

DESOLDERING PUMP

Ideal for removing components from computer boards as well as for service work generally. Price £6.35.

4-CORE FLEX CABLE

White pvc for telephone extensions, disco lights, etc. 10 metres £2, 100 metres £15. Other multicore cable in stock.

MUGGER DETERRANT

A high-note bleeper, push latching switch, plastic case and battery connector. Will scare away any villain and bring help. £2.50 complete kit.

HUMIDITY SWITCH

American made Honeywell. The action of this device depends upon the dampness causing a membrane to stretch and trigger a sensitive microswitch. Very sensitive breathing on it for instance will switch it on. Micro 3 amp at 250V a.c. Only £1.15.

MINI-MULTI TESTER

Deluxe pocket size precision moving coil instrument, jewelled bearings—2000 o.p.v. mirrored scale.
11 instant range measure:
DC volts 10, 50, 250, 1000.
AC volts 10, 50, 250, 1000.
DC amps 0-100 mA.
Continuity and resistance 0-1 meg ohms in two ranges. Complete with test Prods and instruction book showing how to measure capacity and inductance as well. Unbelievable value only £6.75 + 50p post and insurance.

FREE Amps ranges kit to enable you to read DC current from 0-10 amps, directly on the 0-10 scale. It's free if you purchase quickly but if you already own a mini-tester and would like one, send £2.50.


SUPER HI-FI SPEAKER CABINETS.

Made for an expensive Hi-fi outfit—will suit any decor. Resonance free cut-outs for 8" woofer and 4" tweeter. The front material is carved Dacron, which is thick and does not need to be stuck in and the completed unit is most pleasing. Colour black. Supplied in pairs, price £6.90 per pair (this is probably less than the original cost of one cabinet) carriage £3 the pair.



CHASSIS BARGAIN

3 wave band radio with stereo amplifier. Made for incorporation in a high-class radiogram, this has a quality of output which can only be described as superb. It is truly hi-fi. The chassis size is approximately 14". Push buttons select long, medium, short and gram. Control are balance, volume, treble and bass. Mains power supply. The output is 6 + 6 watts. Brand new and in perfect working order, offered at less than value of stereo amp alone, namely £6.90. Post £2.00.

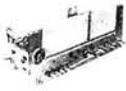

MULLARD UNILEX

A mains-operated 4 + 4 stereo system. Rated one of the finest performers in the stereo field this would make a wonderful gift for almost anyone. In easy-to-assemble modular form this should sell at about £30—but due to a special bulk buy and as an incentive for you to buy this month we offer the system complete at only £16 including V.A.T. and postage. **FREE GIFT**—Buy this month and you will receive a pair of Goodman's elliptical 8" - 5" speakers to match this amplifier.



THIS MONTH'S SNIP

THERMOSTAT ASSORTMENT 10 different thermostats, 7 bi-metal types and 3 liquid types. There are the current stats which will open the switch to protect devices against overload, short circuits, etc. or when fitted say in front of the element of a blower heater, the heat would trip the stat if the blower fuses; appliance stats, one for high temperatures, others adjustable over a range of temperatures which could include 0-100° C. There is also a thermostatic pod which can be immersed, an oven stat, a calibrated boiler stat, finally an ice stat which, fitted to our waterproof heater element, up in the loft could protect your pipes from freezing. Separately, these thermostats would cost round about £15.00—however, you can have the parcel for £2.50.


WALL MOUNTING THERMOSTAT.

Danfoss, a handsome 2 tone this is intended for living rooms but is just as efficient in a greenhouse or store. It is suitable for normal air temperature range 32F-80F—price £4.60.




TANGENTIAL HEATER UNIT

A most efficient and quiet running blower-heater by Solatron—standard replacement in many famous name heaters—comprises mains induction motor—long turbo fan—split heating element and thermostatic safety trip—simply connect to the mains for immediate heat—mount in a simple wooden or metal case or mount direct into base of say kitchen unit. Price £5.95, post £1.50. Control switch to give 2kw, 1kw, cold blow or off available 60p extra. 3kw model £6.95. Control Switch 95p.

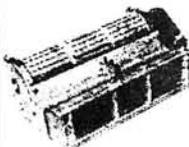

3 KW Mode
£6.95
+ £1.50 P & P

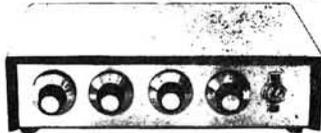

3-CHANNEL SOUND TO LIGHT KIT

Complete kit of parts for a three-channel sound to light unit controlling over 2,000 watts of lighting. Use this at home if you wish but it is plenty rugged enough for Disco work. The unit is housed in an attractive two-tone metal case and has controls for each channel, and a master on/off. The audio input and output are by 1/2" sockets and three panel mounting fuse holders provide thyristor protection. A four-pin plug and socket facilitate ease of connecting lamps. Special snip price is £14.95 in kit form or £19.95 assembled and tested.

8 POWERFUL BATTERY MOTORS

For models, Meccanos, drills, remote control planes, boats, etc. £2.

TERMS: Cash with order—but orders under £10 must add 50p to offset packing, etc.

BULK ENQUIRIES INVITED. PHONE: 0444-54563.

ACCESS & BARCLAYCARD WELCOMED.

J. Bull [ELECTRICAL] Ltd.

(DEPT. PW4)

34-36 AMERICA LANE,
HAYWARDS HEATH SUSSEX.

RH16 3QU

IT'S FREE

Our monthly Advance Advertising Bargains List gives details of bargains arriving or just arrived—often bargains which sell out before our advertisement can appear—it's an interesting list and it's free—just send S.A.E. Below are a few of the Bargains still available from previous lines.

DUE TO THE HIGH & RISING PRICES OF FUEL many companies and probably many householders are looking around for ways of saving some of this cost. One Company bought a number of fans from us and fitted these on the ceiling of their workshops where the hot air tends to collect and they blow this hot air downwards. Another Company has bought fans from us to suck the exhaust from their oil fired central heaters through a zig zag of asbestos pipes, the asbestos pipes being in a separate chamber which becomes a hot air chamber, the hot air from this is blown through ducting to where ever it is needed. Basically, they have cut out the normal chimney and replaced this with one of our high power extractor fans. If you have any other good ideas on heat cost savings, let us know and we will pass it on to other readers.

EXTRACTOR FANS

Ex-Computer made by Woods of Colchester, ideal also as blower; central heating systems, fume extraction etc. Easy fixing through panel, very powerful 2,500 r.p.m. but quiet running. Choice of 2 sizes, 5", £5.50, 6", £6.50; post £1 per fan.



PING PONG BALL BLOWER-UPPERS Have you got to organise a Christmas Party or Charity Fund-Raising Event? Then one always popular way is to have ping pong balls going up and down and being caught. We have some powerful blowers and these should be ideal for this, and of course for more serious purposes. They are 4 stage blowers, coupled to synchronised A.C. mains motors of approximately 1 h.p. They have a terrific suction as well as a high velocity blow. Ex computers, price £26.00.

TWO MORE BLOWERS Both "snail" type, one very small and compact and suitable for cooling projectors or other equipment. Impeller size 2" - 1", coupled to mains voltage induction motor, outlet size approximately 1 1/2" - 1 1/2". Price £5.50 + 68p. The other is a larger **FLANGED BLOWER** for direct coupling to ducting, outlet size 3 1/2" - 2 1/2" + 1" flange, holed for easy fixing to trunking. Impeller size 5 1/2" - 1 1/2". Powered by 1 1/2 h.p. mains motor. £11.75.

RECHARGEABLE SOLID GEL BATTERY 12v 5 AH new and unused made by or for Elpover Corporation of California. Dimensions, 6" long, 3 1/2" high and 2 1/2" wide. Regular price of similar batteries, R.S. Components is £26.00. Limited quantity available at £15.80.

DUAL DIGITAL TIMER Short delay, left time adjustable 0-2 secs right timer 0-9.9 secs. Made by Techno Instruments Ltd., catalogue no. 010 18/1. We have very little information on these, but they are battery operated, to use you simply set the digital switches in the desired position, turning the rotary indicator to the chosen time. The lamp will light up when the right timer is in operation. Periodic or single action possible. This is a precision instrument 4 1/2" wide, 1 1/2" high and 5 1/2" deep. We understand that these cost over £60.00 from the Makers. Limited quantity only at £23.00.

SOLID STATE VARIACS By Lewis and Holtzman Ltd—their "Elvar", 230-240v AC in and out, 10 amp model is cylindrical approximately 3 1/2" diameter 4 1/2" deep. Price £13.80. 5 amp model, again cylindrical, 2 1/2" diameter, 4 1/2" deep. Price £9.20.

E.H.T. UNITS One of our specialities has always been E.H.T. transformers, and we probably have bigger stocks than most of our contemporaries. It is surprising what uses these high voltages can be put to—killing flies and weeds, lighting central heating boilers, lifting paper, extracting dust, etc. etc. A new one this month is 14.5 KV, (dc) 0.5mA—made by **ADVANCE ELECTRONICS**—this unit is completely enclosed and has input and output sockets—size of the unit is approximately 6" - 3" - 3 1/2", price £15.38 post £1. To remind you of the E.H.T. Transformers we stock, here is a list:

3-4 KV 3 mA ex equipment £2.90
5 KV 5 mA ex new equipment £1.15
5 KV 5 mA with outer casing and E.H.T. outlets £9.45
8.5 KV 10 mA totally enclosed with E.H.T. outlets £13.50

LEDs are used increasingly and are now being recommended for nearly all indicators and for games and novelties. Due to a factory purchase, this month we are able to offer 10 led's for £1. These are the small ones equivalent to the TIL 209. Bulk price £60.00 per 1,000 + V.A.T.

FIG. 8. FLEX is always in demand, especially when doing the Christmas decorations. We are able to offer white Fig. 8 5 amp type on 50 metre roll for £2.83, ditto but dark grey with tracer lead, suitable for speaker extensions, 50 metres £3.38.

500 WATT MERCURY VAPOUR LAMP Mazda, ref. 90-S104 M.A.T.V. blends. These give a really powerful light but, of course, have to be used with the correct control gear. We are expecting to get this control gear early in the New Year. Price of the lamp is £3.38 + 38p. Post 50p.

ANTI FROST THERMOSTAT The normal refrigerator type thermostat, switches off as the temperature falls and so is not suitable for anti-frost devices. However, we have the **ice stat**—this switches on as the temperature falls and is set to switch on just above freezing point. It is a skeleton stat so would require boxing, but the price is modest at £1.10.

THIN CONNECTING WIRE 500 metre drums, 7 stranded copper core p.v.c. covered available in 10 different colours. Price £7.15.

OCTOBER/NOVEMBER CONSTRUCTOR'S SNIP. Here's a super bargain for you, 100 twist drills, regular tool shop price over £50, yours for only £11.50. With these you will be able to drill metal, wood, plastic etc from the tiniest holes in P.C.B. right up to about 1/2". Don't miss this snip—send your order today.

SUPER BREAKDOWN PARCEL with free gift of a desoldering pump, perhaps the most useful breakdown parcel we have ever offered. Consists of 50 nearly all different computer panels on which you will find: over 300 ICs, over 300 diodes, over 200 transistors and many hundreds of other parts, resistors, condensers, diode turn pots, rectifiers, SCR etc. etc. for only £8.50, which when you deduct the value of the desoldering pump, works out to just a little over 4p per panel, + £1.27 VAT + £2.20 post (it's a big parcel).



TIME SWITCH BARGAIN Large clear mains frequency controlled clock, which will always show you the correct time + start and stop switches with dials. Complete with knobs £2.50.



SIMPLY AHEAD
and staying there

The range grows bigger... better...

New Profile Amplifiers - Two New Series

MOSFET!



CHOOSE AN I.L.P. MOSFET POWER AMP when it is advantageous to have a faster slew rate, lower distortion at higher frequencies, enhanced thermal stability, the ability to work with complex loads without difficulty and complete absence of cross-over distortion. I.L.P.'s exclusive encapsulation technique within fully adequate heatsinks has been taken a stage further with specially developed computer-verified 'New Profile' extrusions. These ensure optimum operating efficiency from our new MOSFETs, and are easier to mount. Connections via five pins on the underside. I.L.P. MOSFETS ARE IDENTICAL IN PERFORMANCE TO THE COSTLIEST AMPLIFIERS IN THIS EXCITING NEW CATEGORY BUT ARE ONLY A FRACTION OF PRICES CHARGED ELSEWHERE.

Model	Output Power RMS	Distortion at 1KHz	Slew Rate	Rise Time	Signal/Noise Ratio DIN AUDIO	Price & VAT
MOS120	60W into 4-8Ω	0.005%	20V/μs	3μs	100dB	£25.88 + £3.88
MOS200	120W into 4-8Ω	0.005%	20V/μs	3μs	100dB	£33.46 + £5.02


BIPOLAR

STANDARD O/P TRANSISTORS
CHOOSE AN I.L.P. BIPOLAR POWER AMP where power and price are first consideration while maintaining optimum performance with hi-fi quality and wide choice of models. From domestic hi-fi to disco and P.A., for instrument amplification, there is an I.L.P. Bipolar to fill the bill, and as with our new Mosfets, we have encapsulated Bipolars within our New Profile extrusions with their computer-verified thermal efficiency and improved mounting shoulders. Connections are simple, via five pins on the underside and with our newest pre-amps and power supply units, it becomes easier than ever to have a system layout housed the way you want it.


Model	Output Power RMS	Distortion at 1KHz	Slew Rate	Rise Time	Signal/Noise Ratio DIN AUDIO	Price & VAT
HY30	15W into 4-8Ω	0.015%	15V/μs	5μs	100dB	£7.29 + £1.09
HY60	30W into 4-8Ω	0.015%	15V/μs	5μs	100dB	£8.33 + £1.25
HY120	60W into 4-8Ω	0.01%	15V/μs	5μs	100dB	£17.48 + £2.62
HY200	120W into 4-8Ω	0.01%	15V/μs	5μs	100dB	£21.21 + £3.18
HY400	240W into 4Ω	0.01%	15V/μs	5μs	100dB	£31.83 + £4.77

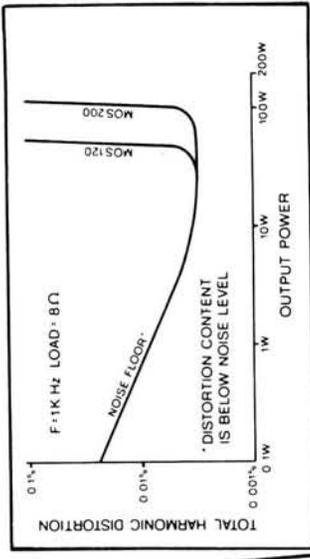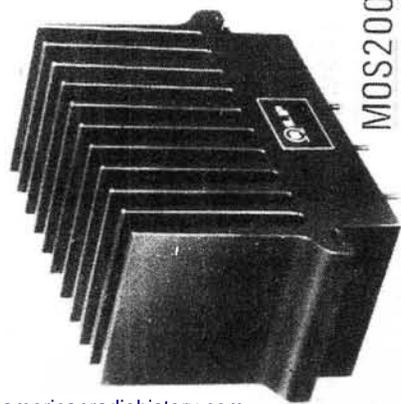

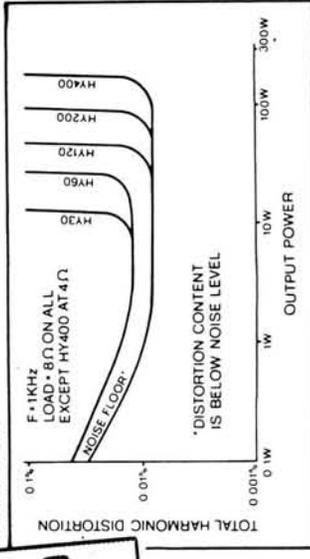Load impedance both models 4Ω. ∞ Input sensitivity both models 100KΩ. Frequency response both models 15Hz-100KHz-3dB



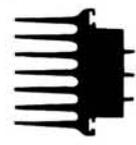Load impedance all models 4Ω. ∞ Input impedance all models 100KΩ. Input sensitivity all models 500mV. Frequency response all models 15Hz-50KHz-3dB



THE NEW PROFILE EXTRUSIONS
The introduction of standard heatsink extrusion for all I.L.P. power amplifiers achieves many advantages: - Research shows they provide optimum thermal dissipation and stability. Slotted shoulders allow easy mounting; standardisation enables us to keep our prices competitive. Surfaces are matt black, anodised for higher thermal conductivity. Extrusions vary in size according to module number.

I.L.P. PRE-AMPS

HY6 (mono) and HY66 (stereo) are new to I.L.P.'s range of advanced audio modules. Their improved characteristics and styling ensure their being compatible with all I.L.P. power-amps both MOSFET and BIPOLAR, giving you chance to get the best possible reproduction from your equipment. HY6 and HY66 pre-amps are protected against short circuit and wrong polarity. Full assembly instructions are provided. Mounting boards are available as below.

- Sizes - HY6 - 45 x 20 x 40 mm. HY66 - 90 x 20 x 40 mm.
- Active Tone Control circuits provide ± 12 dB cut and boost.
- Inputs Sensitivity - Mag. PU. - 3mV; Mic - selectable 1-12mV; All others 100mV. Tape O/P - 100mV; Main O/P - 500mV; Frequency response - D.C. to 100KHz - 3dB.
- HY6 mono £6.44 + 97p VAT Connectors included
- HY66 stereo £12.19 + £1.83 VAT Connectors included
- B6 Mounting Board for one HY6 78p + 12p VAT
- B66 Mounting Board for one HY66 99p + 15p VAT

I.L.P. POWER SUPPLY UNITS

Of the eleven power supply units which comprise our current range, nine have toroidal transformers made in our own factory. Thus these I.L.P. power supply units are space-saving, more efficient and their better overall design helps enormously when assembling building. All models in the range are compatible with all I.L.P. amps and pre-amps with types to match whatever I.L.P. power amps you choose.

- PSU30 + 15V at 100mA to drive up to 12 x HY6 or 6 x HY66 £4.50 + 0.68p VAT
- THE FOLLOWING WILL ALSO DRIVE I.L.P. PRE-AMPS £8.10 + £1.22 VAT
- PSU36 for use with 1 or 2 HY30's
- ALL THE FOLLOWING USE TOROIDAL TRANSFORMERS
- PSU50 for use with 1 or 2 HY60's £10.94 + £1.64 VAT
- PSU60 for use with 1 HY120 £13.04 + £1.96 VAT
- PSU65 for use with 1 MOS120 £13.32 + £2.00 VAT
- PSU70 for use with 1 or 2 HY120's £15.92 + £2.39 VAT
- PSU75 for use with 1 or 2 MOS120 £16.20 + £2.43 VAT
- PSU90 for use with 1 HY200 £16.20 + £2.43 VAT
- PSU95 for use with 1 MOS200 £16.32 + £2.45 VAT
- PSU180 for use with 1 HY400 or 2 HY200 £21.34 + £3.20 VAT
- PSU185 for use with 1 or 2 MOS200 £21.46 + £3.22 VAT

★ Freepost facility

When ordering or writing about I.L.P. products, you do not need to stamp the envelope. Mark it FREEPOST plus the code shown in the address below. We pay the postage for you.


★ TO ORDER

Send cheque or money order payable to I.L.P. Electronics Ltd and crossed. Or pay by ACCESS or BARCLAYCARD. Cash payments must be in registered envelope; if C.O.D. payment is wanted, please add £1.00 to TOTAL value of order.

ELECTRONICS LTD.

FREEPOST 1 Graham Bell House, Roper Close, Canterbury, Kent CT2 7EP.
Telephone (0227) 54778 (Technical (0227) 64723) Telex 965780
Available also from MARSHALLS, WATFORD ELECTRONICS and certain other selected retailers

COMPATIBLE WITH ALL I.L.P. MODULES

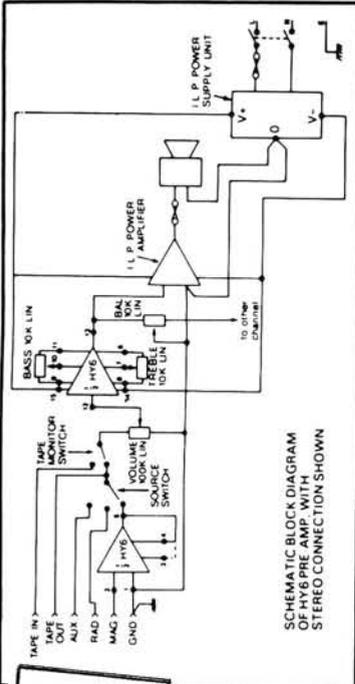

- DISTORTION TYPICALLY 0.005%
- S/N RATIO - 90dB (Mag. P.U. - 68 dB)
- 38 dB overload margin on Mag. P.U.
- LATEST DESIGN HIGH QUALITY CONNECTORS
- ONLY POTS, SWITCHES AND PLUGS/SOCKETS NEED ADDED
- NEEDS ONLY UNREGULATED POWER SUPPLY ± 15 to ± 60 V

IN A RANGE OF 11 MODELS USING LATEST TOROIDAL TRANSFORMERS

1971-1980 TEN YEARS OF PLANNED PROGRESS

When, in 1971, Ian L. Potts founded his now world-famous company, he saw the need for a different and more rational approach to exploiting to the full, the potential that lay in modular construction. New thinking was badly needed. The result was a range of modules revolutionary in concept. The rightness of this new thinking is shown by the size of the company today, its new factory, its vast exports, its acceptance by constructors as the modules to build with. The range grows bigger and better. Exciting new lines (in no way conflicting with existing ones) are well past drawing board stage. This is why I.L.P. are simply ahead and staying there.

BRITAIN'S LEADING QUALITY MODULE SUPPLIERS

To: I.L.P. ELECTRONICS LTD. CANTERBURY CT2 7EP

Please supply

..... Total purchase price f.

I enclose Cheque Postal Orders International Money Order


Please debit my Access/Barclaycard Account No.

NAME


ADDRESS

Signature

ALL U.K. ORDERS DESPATCHED FREEPOST

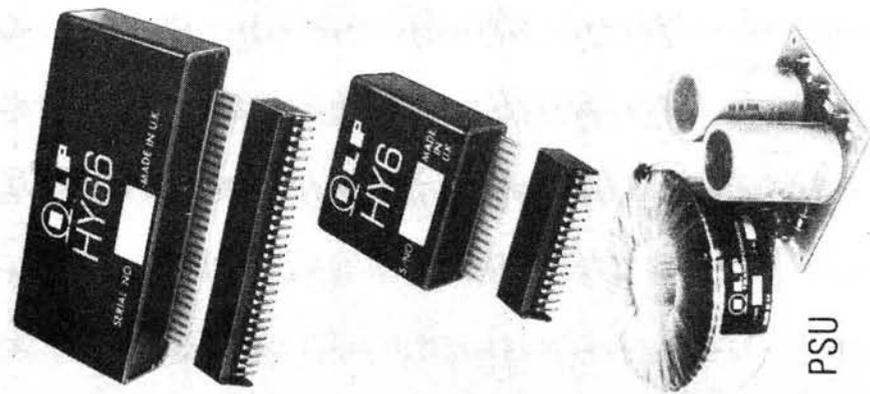

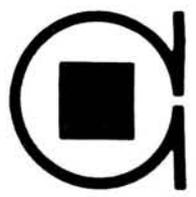NO QUIBBLE 5 YEAR GUARANTEE
7-DAY DESPATCH ON ALL ORDERS
BRITISH DESIGN AND MANUFACTURE
FREEPOST SERVICE



TRIO**LAR****AUTHORISED****DEALER****...the sign of fine communications**

Authorised Distributor for TRIO equipment in Yorkshire and the North East.

THIS MONTH'S LAR SPECIAL - Trio CO1303G 5MHz monitor-scope with two-tone oscillator £140.00 inc VAT.**TRIO EQUIPMENT**

	Price inc. VAT
NEW1	Trio 9000 multi-mode..... £365.00
R1000	200kHz to 30MHz PLL Receiver with digital readout 285.00
R820	The ultimate matching receiver to the TS820..... 690.00
TS830S	160 10M transceiver with the new bands. Successor to the TS820..... 639.52
VFO230	Digital VFO with memories and digital readout..... 194.45
AT230	All band ATY and power meter. Matches TS830S..... 106.72
SP230	External speaker unit with switched filters..... 33.14
DFC230	Digital frequency remote controller. Four memories etc..... 163.13
YK88C	500Hz CW Filter..... 17.25
YK88CN	270Hz CW Filter..... 28.62
SM220	Monitor scope..... 197.80
BS8	TS820 scan board for SM220..... 48.30
AT200	1.8 to 30MHz antenna tuner..... 82.80
TL922	HF linear amplifier 160-10m/2kW P.E.P. 595.70
TS520SE	1.8 30MHz SSB transceiver 200W P.E.P. 437.00
SP520	Matching speaker..... 17.25
DG5	Digital display/40MHz frequency counter 103.50
DK520	Conversion kit allows use of DG5 with TS520 10.35
YG3395C	CW filter..... 37.95
TS120V	80-10m mobile transceiver 20W P.E.P. 347.30
TS130S	8 band 200W pep mobile transceiver 491.05
TS130V	8 band 20W pep mobile transceiver 404.34
SP40	New mobile speaker unit..... 26.89
TL120	80-10m 200W P.E.P. linear 128.80
PS20	AC power supply for TS120V 44.85
MB100	Mobile mounting bracket..... 17.25
YK88C	CW filter..... 28.75
SP120	Matching speaker..... 25.30
VFO120	Remote VFO..... 89.70
AT120	Antenna tuner (100W)..... 55.20
TS120S	80-10m mobile transceiver 200W P.E.P. 432.40
PS30	AC PSU for TS120S, TA130 & TS180S 85.10
TS770E	2m 70cm all mode dual bander..... 730.25
SP70	Matching speaker..... 18.40
TR7600	2m synthesised mobile FM 10 Watt..... 220.00
TR7800	2m synthesised mobile FM 25 Watt..... 268.00
PS8	PSU for TR7625 only..... 80.00
TR2300	2m FM portable transceiver..... 166.75
VB2300	10W booster..... 49.45
MB2	Mobile mount..... 17.25
RA1	Helical rubber antenna..... 6.90
TS180S	160 10m Solida State Transceiver. Digital memory system. 200W pep 679.65
VFO180	External VFO..... 96.60
SP180	Speaker..... 36.80
AT180	1.8 30MHz antenna tuner 95.45
PB10	Pack of 10 ni-cad batteries..... 10.35
TR2300	Spare power lead..... 1.30
LAR PS1200	Power supply unit and ni-cad charger for TR2200GX/ TR2300/TR3200 and ICOM portables. You can charge and operate at the same time 29.50
SRX30	0.5 to 30MHz SWL Receiver..... £158.00
HS5	Communications headphones, tailored response..... 21.85
HS4	Communications headphones, tailored response..... 10.35

MC50	De luxe desk microphone dual impedance..... 24.15
MC35S	50K fist microphone (noise cancelling)..... 13.80
MC30S	500 ohm fist microphone (noise cancelling)..... 13.80
LF30A	HF low pass filter 1kW 90dB. Stop band rejection..... 18.40
LAR	1kW P.E.P. 3-way antenna switch..... 16.95

VHF AMATEUR RECEIVERS

SR9	Tuneable/crystal 2m FM receiver 144 146MHz..... 46.00
AMR217B	Scanner. The best mains/battery operated..... 120.75

HF MOBILE ANTENNAS

'G' whip tribander helical 20/15/10..... 24.72
'C' whip multimobile 20/15/10..... 28.75
L.F. coils for the above whips (specify whether tribander or multi-mobile)..... 6.56
Telescopic whips for the above..... 3.34
Base mounts for all 'G' whips..... 4.48

VHF/UHF 'J' BEAM S. All 'J' Beam products available

Famous Ringo Ranger 2m co-linear..... 27.60
Slim Jim 2m vertical..... 21.00
GDX2 VHF/UHF Discone Antenna 50-480MHz..... 39.50

ROTATORS

Sky King SU2000..... 46.00
DR7500 Will take 3 element tribander..... 108.10
DR7600 Will take a 2 element 40 metre beam..... 154.10
DR8600P As above but with preset or manual controller..... 204.70
Channel Master 9502A..... 56.00
Channel Master HD/9508..... 78.00

VHF MOBILE WHIPS A.S.P. (Telecoms Accessories)

All ASP mobile antennas and accessories available

NEW HF VERTICAL ANTENNA

HF5 80 10m vertical..... 48.50
HF5R Operational radial kit for roof mounting..... 28.00

ICOM PRODUCTS

IC240 FM mobile synthesised transceiver 2m..... 169.00
IC215E FM portable (LAR PS1200 available!) 2m..... 162.00
IC202S SSB portable (LAR PS1200 available!) 2m..... 169.00
IC211E All mode 2m transceiver..... 450.00
IC701 1.8 to 30MHz HF transceiver..... 899.00
IC255E 25 watt FM 2m mobile with memory and scanner..... 255.00
IC2E 2m FM hand portable..... 159.00
IC260E 2m all mode mobile..... 339.00
IC251E All mode transceiver..... 479.00

Securicor delivery arranged if required

HOW TO BUY!

OFF THE PAGE - Simply choose the product and then complete the coupon and enclose cheque.

* Open Mon-Fri 9.15-6.30pm

Saturday 9.15-5.30pm

* H.P. Terms on request

POST NOWI enclose cheque for £..... Plus 50p for Brochure* to purchase.....
* Cheque if not applicable

Name.....

Address.....

CITY LIBRARY

No. 27

COOKRIDGE STREET

THE HEADROW

FROM THE SHOP - We're close to the station and car parks. Do call in and discuss your requirements.

Authorised Distributor for TRIO, Equipment & Area Distributors for JAY BEAM, ANTENNA SPECIALISTS & HILOMAST PRODUCTS.

**LEEDS AMATEUR RADIO**27 Cookridge Street, Leeds 2
Telephone: Leeds 452657

Post to: Leeds Amateur Radio, 27 Cookridge Street, Leeds 2.

TO BARCLAYCARD/ACCESS

I authorise you to debit my Barclaycard/Access Account with the amount of £..... My No. is

[] [] [] [] [] [] [] [] [] []

Signature





comment...

Round the Clock

TECHNIQUES advance so rapidly in radio and electronics that it is very easy to become blasé about them. Whether each development is viewed as good or bad depends upon an individual's personal preference and experience. For example, I must confess that I still like a receiver to have traditional-style manual tuning, rather than step-up/step-down synthesiser tuning, though I am a convert to digital frequency readout.

Some of these new techniques have far-reaching effects, not always immediately obvious, and this is perhaps nowhere more true than in the case of the change from analogue to digital displays. This was brought home to me recently in a rather unusual way, whilst visiting a relative in hospital. To pass the time, she had been working through a book of puzzles, including the sort where you have to fit six-letter words into an interlocking honeycomb pattern of hexagons. Answers to clues with odd numbers go anti-clockwise and those with even numbers clockwise.

With the clues there was a little drawing to explain this rule, and my first reaction was: "Surely people don't have to be told which are odd numbers and which are even!" Thinking about it a bit more, I realised that it might be more necessary to explain the meaning of clockwise and anti-clockwise, for it would be quite possible for a child nowadays to grow up entirely in a world of digital clocks and watches, at home, at school and in public places. The term "clockwise" could well mean nothing to such a person, but what

could you use instead? The instruction to turn a receiver volume control to the right, for instance, would be equivalent to clockwise providing you considered the top of the knob as your reference point. If it was a pointer knob, and the pointer was towards the bottom, you could argue equally well that "to the right" equalled anti-clockwise.

As it happens, quartz analogue watches and clocks have started to become more popular, and the digital tide has been turned, but if this were not so, what a mess we could have got into in giving adjustment and operating instructions for radio and electronic equipment, and many other fields besides. Can you think of an alternative term for clock-wise that is brief and capable of only one interpretation?

* * * * *

Congratulations to all those who passed the December 1980 Radio Amateurs' Examination especially to our Technical Sub-Editor Elaine Howard who will shortly be adding a G4 to our masthead.



services

QUERIES

While we will always try to assist readers in difficulties with a *Practical Wireless* project, we cannot offer advice on modifications to our designs, nor on commercial radio, TV or electronic equipment. Please address your letters to the Editor, "Practical Wireless", Westover House, West Quay Road, Poole, Dorset BH15 1JG, giving a clear description of the problem and enclosing a stamped self-addressed envelope. Only one project per letter please.

Components for our projects are usually available from advertisers. For more difficult items, a source will be suggested in the "Buying Guide" box included in each constructional article.

PROJECT COST

The approximate cost quoted in each constructional article includes the box or case used for the prototype. For some projects the type of case may be critical; if so this will be mentioned in the Buying Guide.

CONSTRUCTION RATING

Each constructional project will in future be given a rating, to guide readers as to its complexity:

Beginner

A project that can be tackled by a beginner who is able to identify components and handle a soldering iron fairly competently. Generally this category will be used for simple projects, but sometimes for more complicated ones of wide appeal. In this case, construction and wiring will be dealt with in some detail.

Intermediate

A project likely to appeal to a wide range of constructors, and requiring only basic test equipment to complete any tests and adjustments. A fair degree of experience in building electronic or radio projects is assumed.

Advanced

A project likely to appeal to an experienced constructor, and often requiring access to workshop facilities and test equipment for construction, testing and alignment. Constructional information will generally be limited to the more critical aspects of the project. Definitely not recommended for a beginner to tackle on his own.

SUBSCRIPTIONS

Subscriptions are available to both home and overseas addresses at £11.80 per annum, from "Practical Wireless" Subscription Department, Room 2613, King's Reach Tower, Stamford Street, London SE1 9LS. Airmail rates for overseas subscriptions can be quoted on request.

BACK NUMBERS AND BINDERS

Limited stocks of some recent issues of *PW* are available at 95p each, including post and packing to addresses at home and overseas.

Binders are available (Price £4.30 to UK addresses and overseas, including post and packing) each accommodating one volume of *PW*. Please state the year and volume number for which the binder is required.

Send your orders to Post Sales Department, IPC Magazines Ltd., Lavington House, 25 Lavington Street, London SE1 0PF. All prices include VAT where appropriate.

Please make cheques, postal orders, etc., payable to IPC Magazines Limited.

PRODUCTION LINES

ALAN MARTIN G8ZPW

News from Icom

The IC-240 has had a face lift, enabling operation over the full 2m band without pre-programming. The new set, called the IC-24G, has a combined digital selector and readout visible in the brightest sunlight. All the "works" are exactly the same as the IC-240 which has built an enviable reputation for reliability. Power output is 1 or 10 watts. Channel steps of

12.5kHz and 25kHz, and simplex/repeater/full reverse repeater operation are all selectable from the front panel. Manual tone-burst is provided. The IC-24G will cost £199 including VAT from *Thanet Electronics, 143 Reculver Road, Beltinge, Herne Bay, Kent. Tel: Herne Bay (02273) 63859*. A remote readout and channel-change unit will be available as an optional extra.



2m Base Antenna



As a development of their original range of rugged CB antennas, the Firestik Antenna Company have recently introduced two v.h.f. vertical base station devices intended for the 2m Amateur and 156MHz Marine/Land Mobile bands.

Both feature a spiral wound wire driven element, bonded onto a fibreglass supporting shaft and fully enclosed in heat shrunk polyolifin sleeving.

The $5\lambda/8$ (physical and electrical) driven element, which comes factory set for optimum match at the band centres, screws into a composite base mount that incorporates a PL-259 coaxial adapter and inserts for three, 534mm long, solid aluminium ground plane radial elements.

The base is recessed to allow mounting of the antennas on a 32mm diameter tubular mast. The coaxial feeder passes up through the tubular support to the feed point connector and is thus protected from the adverse effects of the weather.

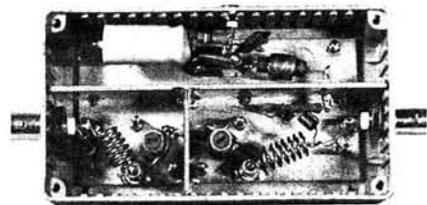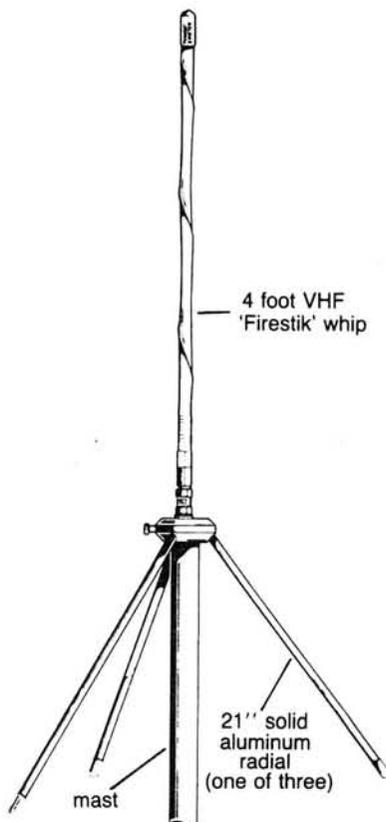Each antenna has a nominal impedance of 50–52 ohms with a quoted



Super Pre-amp

We have recently received a 2m GaAs f.e.t. pre-amplifier for evaluation from R & S Developments. This, their MK II device has been designed for the v.h.f. operator requiring the lowest possible noise figures and best receiver sensitivity.

The unit is available, fully built, in an r.f. tight stove-enamelled diecast box, provided with b.n.c. sockets for in-line connection. An internal regulator supply feeds the circuit with the necessary highly stable voltage; input voltage being in the range 9–15V d.c.

A future "Air Test" will provide the full laboratory test figures but a provisional trial in conjunction with a good "state-of-the-art" transceiver has indicated the effectiveness of this device. R & S quote a gain of 27dB and a noise figure, typically, of 0.6dB! The current price of the pre-amp is £40 plus 80p p&p.

Other products available are a 70cm version of the above with an identical specification, and price, an electronic keyer board for c.w. and an active audio filter board.

Further details of all R & S Developments products can be obtained by sending an s.a.e. to: *20 Beweshill Crescent, Winlaton, Blaydon-on-Tyne, Tyne and Wear NE21 6BW*.

gain, over a quarter-wave, of 3dB. Standing wave ratios, measured at band centre, are specified as 1.1 to 1. As supplied the bandwidth of the 2m antenna covers 144MHz to 148MHz and the Marine/Land Mobile version 156.250MHz to 158.715MHz, however instructions are provided to allow "pruning" adjustment to higher frequencies.

Additional points of interest include power handling capability of 400W a.m.–800W p.e.p., a low angle of radiation and an inherent resistance to static noise.

The VAT and carriage inclusive price for the kit is £33.75, and is obtainable from: *Wintjoy Ltd., 103 High Street, Shepperton, Middlesex TW17 9BL. Tel: Walton-on-Thames (093 22) 48145*.

Increase Your "Talk Power"

T & T Electronics have recently introduced a new speech processor called the Persuader. It is simple to install and connects between the microphone and the transmitter.

A switch is provided to switch the unit in or out of circuit as required, when switched in the Persuader will remove unwanted audio frequencies below 300Hz and above 3kHz and will also greatly increase the average level a.f. relative to the peaks. An extra gain of 15dB can be achieved which represents an increase in "talk power" of 32 times.



The input will accept signals over the range 0.5mV to 100mV and is suitable for most standard microphones. Once the "set level" control has been adjusted to show the correct level on the two l.e.d.s, the output will be automatically correct for the rig and microphone being used.

Available at an all inclusive price of £38.18, the Persuader can be obtained from: T & T Electronics, Green Hayes, Surlingham Lane, Rockland St Mary, Norwich NR14 7HH. Tel: Surlingham (050 88) 632.


Cut It Out

West Hyde Developments Ltd. has added two new products to its range of cutting tools. Both are hand reamers with integral tommy-bars, one designed for increasing hole sizes to anything from 3.2mm to 12.7mm and the other with a range from 9.7mm to 25.4mm (C in photograph).

Other items in the cutting tool range include matching reamers for use with a hand brace, a range of four Conecut powered reamers with an overall range of finished aperture sizes from 3mm to 52mm (B), the very useful Adel hand-

operated nibbling tool, capable of cutting almost any size or shape hole in up to 16-gauge aluminium without distortion (A), and the versatile Bradrad drilling and deburring tool which is available in four sizes to drill and deburr in one operation (D).

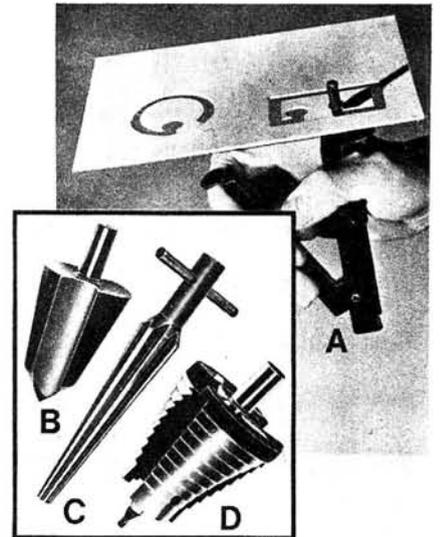For further information and prices contact: West Hyde Developments Ltd., Unit 9, Park Street Industrial Estate, Aylesbury, Bucks HP20 1ET. Tel: (0296) 20441/5.



TOMORROW'S WORLD

CHANGEOVER
Imperial/metric units

MPG MPH GPH
Instant and average information updated every 1.5 seconds

AVG INST
Instant/average pre-selection button

FUEL
Total fuel used over a day, week, month or trip

TIME
Time of day and elapsed time from start of trip

DIST
Distance travelled on trip/distance travelled since reset

RUN
Calibration switch to line tune the computer

FuelStretcher® At the touch of a button everything you need to know for maximum fuel economy, trip scheduling and record keeping yet it's as easy to fit as a car stereo.

Drive Computer

AS SEEN ON TV

FuelStretcher®
UK's first digital MPG monitor used now by thousands of motorists to make their fuel go up to 20% further.

CONTROL UNIT
Mounting on flat surface or stalk optional

ENGAGE/RESUME Button

ON/OFF SWITCH

SPEED ADJUSTMENT DIAL

TURN SIGNAL LEVER or Auxiliary Arm provided

EnviroCruise
World's first 100% electronic cruise control maintains steady preset vehicle speed, up and down hill while you relax, save fuel and prevent speeding tickets.

TODAY

You can order these super in-car products directly from the suppliers and save EEC's from day one.

Name

Address

Please send me your leaflet "TOMORROW'S WORLD TODAY" or send me directly

	retail	your price	qty reqd	
FuelStretcher	£67.90	£46.95		I enclose cheque/
FS Drive Computer	£139.00	£79.95		POs for £
EnviroCruise	£98.90	£69.95		Cheque No
Inst/opener manual only	—	£ 2.50		

Mail/Phone your order with Access or Barclaycard No.

* Prices include VAT, but exclude P&P at £1.75 per product. Allow 14 days for delivery.

EnviroSystems Ltd., Hampsfell Road, Grange-over-Sands, Cumbria LA11 6BE
Tel: 04484 4233/4

PRODUCTION LINES

ALAN MARTIN G8ZPW

Check It Out

If you want to check that a test pin has a voltage on it the new range of Steinel check probes could provide the ideal means.

The six different models offer a wide choice of ranges and indications from the simplest Volt Check which indicates that a voltage in the range 4.5V to 450V is present and shows either that it is a.c. or d.c. and in the latter case indicates the polarity, to the sophisticated Master Check.

Master Check covers 6V to 450V with discrete l.e.d. indicators for 6, 12, 24, 50, 110, 240 and 415V with polarity indication as well. Like the rest of the checkers these are two-lead

devices fully insulated and claimed to be virtually unbreakable.

Steinel also produce an electronic version of the old electrician's standby, the neon screwdriver tester. Called the Mono Check this tool can be used to indicate voltages of between 80 and 250V a.c. and has an internal resistance of 10M Ω and will operate even on a wooden stepladder standing on insulated flooring.

Prices range from £3.21 for the simplest Volt Check to £12.36 for the top of the range Master Check (Inc. VAT).

Further details from *Steinel KG, 288 Chester Road North, Sutton Coldfield, West Midlands B73 6RR. Tel: 021-355 5328.*




New Slimmer Jim

Remember the "Slim Jim" antenna designs published in *Practical Wireless*, which have since become recognised as a highly adaptable standard-setter in antenna design? Well, *PW* contributor, Fred Judd G2BCX, has designed an even slimmer, more versatile omnidirectional vertical antenna for 2m, called the "Slim Jim Super" which should prove ideal for mobile, base or even portable operation and measures only 1068mm (42in).

Being a free-space antenna, the "Slim Jim Super" does not rely on the ground-plane effect and can be used on vehicles with fibre-glass bodies or roof tops at full efficiency. All models are weather protected and feature an external sleeve adjuster for minimum v.s.w.r. setting.

Typical ground plane antenna **WAM035**

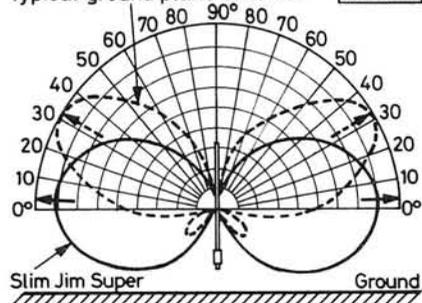


Typical vertical radiation patterns

The smaller dimensions and high efficiency have been made possible by a unique high-"Q" helical stub matching system which gives the antenna a claimed 50 per cent greater efficiency over most other ground-

Ultra Low-Power d.p.m.

Lascar Electronics introduce the DPM-200, a new l.c.d. digital panel meter which is claimed to be the first of a new generation of d.p.m.s, giving at least ten times the battery life of any existing type. A PP3 battery will power the meter for typically two years, if operated for eight hours a day, seven days a week.

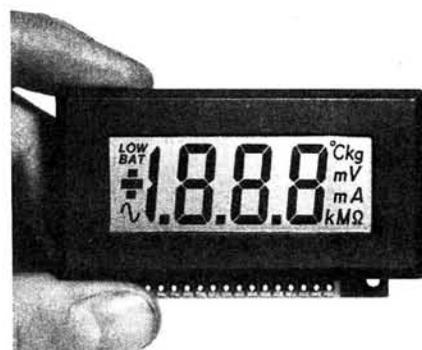LCD watch manufacturing techniques are used to reduce the depth to a minimum, the meter is fitted into a DIN bezel measuring 72 x 36mm, with large 15mm digits and the display also contains many other useful annunciators.




Other standard features include a digital hold facility, auto-zero, auto-polarity, external band-gap reference for maximum stability, single-rail supply of 5V to 15V d.c. drawing 200 μ A, programmable decimal points and a 200mV f.s.d.

The data sheet provided with the meter describes 10 small hand-held instruments, including multimeters, thermometer, pH meter, etc.

The VAT and carriage inclusive price of the DPM-200 is £23.51, supplied with a free purpose-built instrument case (normally costing £2.25) with every meter ordered during 1981. Available from: *Lascar Electronics Ltd., Unit 1, Thomasin Road, Burnt Mills, Basildon, Essex SS13 1LH. Tel: (0268) 727383.*

plane or single element antennas. Specification details include: gain, 6dB over a typical 5 λ /8 ground-plane at a vertical angle of 0 degrees; angle of maximum radiation with respect to ground, five degrees approx.; impedance, 50 ohms; v.s.w.r., average 1.2:1 or less across the band.

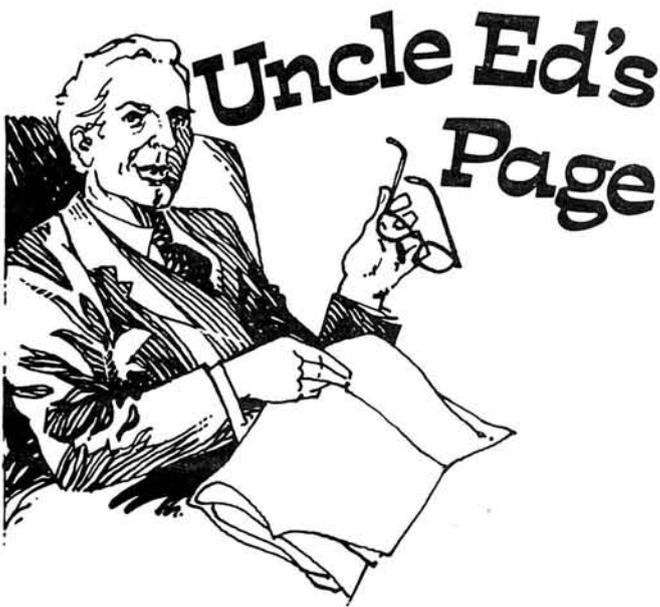Prices which include VAT and carriage are, £17.50 for the "Slim Jim Super", £3.50 for wall/mast mounting bracket and U-clamp, or £21 for both. *Wrenpro Systems, Reedham, Norfolk. Tel: Freethorpe (049 370) 245.*



A monthly look at some aspect of the radio/electronics hobby that seems to bug the beginner, or occasionally a more advanced topic seen from an unusual angle.

SINGLE SIDEBAND (s.s.b.) Part 2

Last month, I introduced the ideas of looking at an amplitude-modulated transmission from the point of view of its waveform, and of its frequency spectrum. We had just got as far as saying that we could suppress the carrier and one of the two sidebands as well.

In fact, there are several varieties of "s.s.b." modulation, but the one normally used in the amateur service is as described above. The unwanted sideband and carrier cannot be completely eliminated, but they are usually suppressed to at least 40dB below the peak power of the remaining sideband. As a general rule, most services use lower sideband (l.s.b.) below 10MHz, and upper sideband (u.s.b.) above 10MHz.

If we take the transmission of Fig. 4 last month and suppress the lower sideband and the carrier, we are left with a single transmission, which so far as the distant receiver is concerned, would look exactly the same as an unmodulated carrier from an ordinary a.m. station. If the modulating audio tone was to be keyed in Morse code, the transmitter would effectively be radiating c.w., and in fact this is how many modern amateur multi-mode transmitters produce c.w., because it's much easier than altering the circuitry to product real keyed carrier. Perhaps an example will make the whole thing clearer.

If we take a 20m band s.s.b. transmitter, tuned to a carrier frequency of 14 100kHz and set for u.s.b., and modulate it with a keyed 1kHz tone, it will effectively radiate c.w. on 14 101kHz. To receive this, we need a receiver having a beat frequency oscillator (b.f.o.) to "beat" the incoming signal against, so that it can be detected and turned back into an audio tone. Here, I am going to assume for simplicity that we are using a "straight" (t.r.f.) or direct-conversion receiver rather than the more common superhet, so that the b.f.o. would be set to 14 100kHz, thus replacing the original carrier and reproducing the 1kHz tone. In this arrangement, the b.f.o. could be set to 14 102kHz with the same end result, but this wouldn't necessarily work with a superhet, and certainly not in a transceiver.

If the b.f.o. (or carrier insertion oscillator (c.i.o.), as it is usually called in a s.s.b. receiver) was not set exactly to 14 100kHz, the audio tone coming out of the receiver loudspeaker or 'phones would not be exactly 1kHz. As an example, if the c.i.o. is set to 14 100.2kHz, the audio tone would be 200Hz low, at 800Hz. This wouldn't usually be too important, and indeed a c.w. operator will always tune his receiver to produce the beat note which he favours, unless he is using some sort of fixed-tune audio filter as a selectivity aid.

Consider, though, what would happen if the signal that had to be transmitted consisted of two simultaneous audio tones, one being the second harmonic of the other at, say, 750Hz and 1500Hz. Heard on our receiver with its 200Hz tuning error, these would come out as 550Hz and 1300Hz, and would sound completely different, being rather discordant compared with the smooth sound of a note and its second harmonic. (1300 does not equal 2×550 , of course.)

What is more commonly transmitted over an s.s.b. link is speech, which is made up of a whole mixture of frequencies, some harmonically related and some not. To tune in such a signal on a receiver is really a two-stage process: 1. Finding the wanted signal; in other words, getting it within the receiver's passband. 2. Resolving the signal—getting the tuning of the c.i.o. close enough to the original carrier frequency to turn the output of the receiver into understandable speech, of acceptable quality.

This final part of the tuning process is difficult to describe on paper, although reasonably easy to demonstrate. I was able to teach my 16-year-old daughter to tune an s.s.b. signal properly with about five minutes practice. The secret, having got the signal to the "intelligible" stage, is to try to get rid of what I can best describe as the "frog-in-the-throat" sound to the distant speaker. A quiet room is essential if you're using a loudspeaker, but headphones are better still. The slower the rate of tune (fewer kHz per turn) of the main or fine tuning controls on the receiver, the easier this will be. A professional s.s.b. receiver will have a fine tune control (often called a "Clarifier") with a swing which may be as little as ± 100 Hz. Trying to do the same job on an amateur-grade receiver with a fine tune range of ± 3 kHz or ± 5 kHz, or even no fine tune control at all, is not easy.


How accurate the c.i.o. frequency must be depends upon the purpose of the link and the experience of the listener. For a receiver forming part of a public telephone service, where the listeners are unskilled and it is more or less essential that the voice at the far end is recognisable, errors of less than 10Hz are desirable, and over 30Hz unacceptable. An experienced s.s.b. operator, on the other hand, can quite easily cope with 100Hz or more off tune, although prolonged listening in such conditions is very wearing.

Sometimes it will prove impossible to banish the "frog-in-the-throat" completely, generally as a result of deficiencies such as intermodulation distortion in the distant transmitter.

If you try to listen to an s.s.b. speech transmission on an ordinary broadcast receiver without a b.f.o., all you will hear is a "monkey chatter" resulting from the sideband components beating against one another, with completely unintelligible results. If you listened on such a receiver to the two-tone transmission I described above, you would hear the difference frequency—750Hz—because the receiver sees the two signals as a "carrier" and a "tone" and extracts the difference. Incidentally, two-tone signals are used to test s.s.b. transmitters, though the tones employed are then **not** harmonically related.

continued on page 28 ►►►

DEAR SIR, It all began like this...

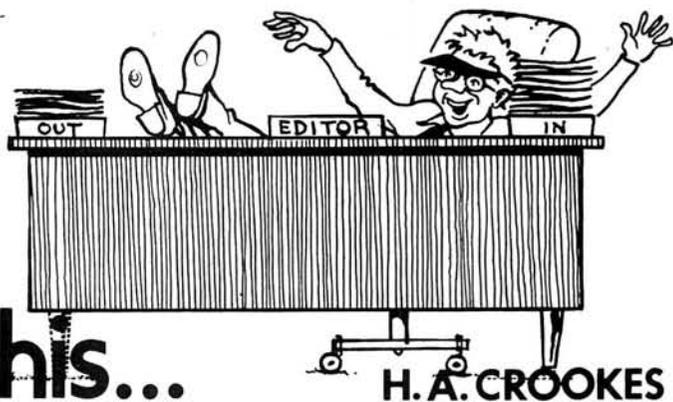

I thought, Mr Editor, that you might be interested in my initiation into the world of short-wave radio. If you are not—well, you can always make a paper plane with this letter and fly it across the office.

I used to do Photography, actually. I did my own processing and the spare room was not so spare as dark. But somehow I seemed to have more success in ruining the carpet and staining the cat than I did in producing good prints. David Bailey has nothing to fear from me I told myself, and decided to finish with photography for good.

I discussed a divorce with The Wife, scrubbed the cat and turned my thoughts heavenwards—to the Ionosphere. I'd have a go at Amateur Radio, I thought.

The Wife was pleased (well, it's not so messy, is it?) and I did, after all, redecorate the spare room. And, when the carpet dried out the stains seemed to blend in with the pattern; even the cat seemed to have suffered no deep psychological harm. Just the odd twitch, perhaps.

Vision

So I went off and bought a copy of—yes, you've guessed it, *Practical Wireless*. I gazed in wonder at the adverts and the good-looking bloke on the cover and that was it; I couldn't understand the rest. But I persevered and sent for a kit of parts—I would, I decided, build a one-valve set.

Eagerly I waited for the parts to arrive, in my ignorance rewiring the spare room in a frantic fervour. Perhaps I would need a direct supply from the local power station; a supergrid feeder, even.

"He tried to poison himself with photographic," said The Wife, encouraging as ever, "now he's trying to electrocute himself." A man with a vision, I pressed on regardless.

The great day arrived at last and a parcel was delivered—my kit of parts. It was something of an anticlimax, really—not exactly like the BBC main transmitter or as I had imagined. Feverishly, spilling coffee and recklessly smashing the marmalade pot on the floor, I tore the package apart and stood gazing in wonder at the components within.

"He'll never get that lot to work," muttered The Wife. "It took him three months to put a plug on the toaster." O thou of little faith, thought I.

Wire-less

Undaunted, I scooped it all up and retreated to the spare room—now renamed "The Radio Room". True, I lost dignity as I trod an amalgam of glass and marmalade

into the carpet, but undaunted I remained. We Radio Enthusiasts are above such mundane concerns.

One hour, one cut thumb and two burnt fingers later I had it all finished and crammed the phones onto my head (I did know that much). Eagerly I twiddled the knobs and got—nothing. Perhaps you know the feeling.



The cat glaring malevolently at me from the safe distance of the window-sill, I desperately rechecked my wiring. Five minutes later (not really that much to a one-valver, is there?), I had discovered the fault—a missing wire. The aerial wire, as a matter of fact.

"Well?" enquired The Wife, "have you got Australia yet?" She fell about in an uncontrolled fit of laughter.

Through a Window

Not having a garden but only a small courtyard created a problem where the aerial was concerned. I decided to overcome it by fixing a pole to the roof of the back door porch.

Taking my tools, the wire, some nails and my life in both hands and warmed by the early morning sunshine, I climbed out of an upstairs window and onto the roof of the porch. The cat could fully appreciate this part of the operation and carefully selected a good vantage point from which to watch. Its golden irises shone as it peered keenly up at me, licking its lips in anticipation of the crash that must surely follow. The Wife—interested as ever—went out shopping.

"Let me know which hospital he's taken to, won't you Mildred?" she called to our neighbour. Very reassuring, The Wife.



To confound them all, I fixed the pole and the aerial and managed to get back into the house unscathed. Okay, I admit to having broken a vase and part of the window-frame in the process but the main thing is that when I plugged in the aerial, the thing *worked*—all one valve of it. And to a Radio Enthusiast, to hear a station on a set that you have built yourself is the very pinnacle of achievement, even if it is in Welsh.

And Now . . .

And since then I've never really looked back, you know. The walls are papered with QSL cards, the courtyard is positively festooned with aerials and, would you believe it, even The Wife is getting interested. The cat, admittedly, exudes an air of haughty disdain; its owners, it evidently considers, have gone bananas.

But the point that I am trying to make, Mr Editor, is that to enjoy our hobby we don't need loads of fancy gear and proper facilities, and certainly not a cat. You just need an understanding wife and a thick skin. If you are not married, you shouldn't be sitting in night after night listening to the radio anyway, of course. But I hope you see what I am getting at.

If it's a wet dismal day and I haven't achieved anything else, I hope I've cheered you up a bit. My one-valver has passed into history now, of course, and my present-day rig is like the flight deck of Concorde by comparison, but that is another story. I'll tell you about it sometime, if you like.

Good listening!

Kindly note!

Beginners 2m Converter, Sept. 1980

If unwanted coverage and spurious responses are found when using the converter, these may be removed by "taming" the oscillator. Increasing the value of R3 to 330kΩ will effect a cure.

PW Sherborne, Nov. 1980

In Fig. 10, the lead from a.m. antenna socket should go to pin 20 on the f.m. i.f. and a.m. tuner head, not pin 17 as shown.

PW Twynham, Jan. 1981

A short link is required between the left-hand end of R21 (Fig. 17) and the display anodes +5V rail, of the p.c.b. Pins 13 and 14 of IC1 should be linked.

PW Tape Slide Controller, Jan./Feb. 1981

On the component overlay Fig. 10, R33 has been duplicated, the component lying below C17 should be R35, not R33 as shown. In the circuit diagram Fig. 3, the bottom end of R18 should not be connected to 0V, but should be connected to the same point as the wiper. The same applies to R37.

The polarity of C29 is drawn incorrectly on the p.c.b. layout in Fig. 14, the circuit diagram is correct.

Active Receiving Antenna, March 1981

The left-hand end track leadout of potentiometer R7 should **not** be connected to the earth plane. Remove sufficient copper from around this pin to ensure **no** connection is made.

Frequency Allocation Chart, March 1981

We should have made it clear that, with certain exceptions, the allocations shown are either world-wide, or where regional variations occur, those for Region 1 (broadly speaking comprising Europe, Africa and the USSR).

Considerable variations occur locally, which are detailed in the official International Table of Frequency Allocations in three columns and nearly 500 footnotes. To give just one example—the 160 metre amateur band—15 European countries can allocate up to 200kHz of additional space to amateurs on a secondary-user basis. In the UK, this is fixed as 1.8–2.0MHz.

It is obviously impossible to detail all these variations in a chart, and where allocations on your Amateur Licence, for instance, differ from the chart, it is the licence which you should follow.

AUDIO POWER AMPLIFIERS

PART 3

M. J. DARBY

In this, the final part of the series, we look at an integrated circuit driver, and two high-power amplifier circuits, one capable of a mean output power of 1.5kW.

Audio Driver

Another way of constructing a high-quality audio amplifier involves the use of an audio power driver integrated circuit. This type of device is not common, but the National Semiconductor LM391N-60 power driver has recently become available through a retail source (Arrow Electronics Ltd., Coptfold Road, Brentwood, CM14 4BN). It can be used in the circuit of Fig. 17 to drive discrete power transistors externally connected as a complementary pair of Darlington's. The circuit shown will provide an output of 20W into an 8Ω load or 30W into a 4Ω load with a total harmonic distortion of about 0.01% at 1kHz rising to 0.3% at 10kHz. The response is level to ± 0.25 dB from 20Hz to 20kHz.

The gain of this circuit is determined by the feedback resistors and is equal to $(1 + R4/R1)$ or about 20.6 with the values shown. The input voltage required for full output power is about 614mV for the 20W version with an 8Ω load, and 532mV for the 30W, 4Ω version. If the gain is increased to 200, the distortion is increased to about 0.05% at 1kHz, rising to about 0.14% at 10kHz owing to the reduced amount of negative feedback. The presence of C1 reduces the amplifier gain to unity at zero frequency as previously discussed. The frequency compensation capacitor C4 sets the gain-bandwidth product.

The resistors R7 and R15 in the base circuits of the output transistors remove stored charge in the bases of these components. The 0.22Ω resistors R9 and R12 in the output transistor emitter circuits increase the thermal stability in these stages. The output inductor L1 in parallel with the resistor R10 can be made as a single component by winding about 25 turns of enamelled wire around a 10Ω, 2W resistor; it is required for capacitive loads. The components R11 and C8 form the normal Zobel network.

Pin 8 of the device can provide a current of 5mA to Tr1, whilst pin 5 can sink (that is, accept) a current of 5mA from Tr3. The overall gain of each of these driver transistors and their output transistors must have such a value that, when it is multiplied by the 5mA base current available from the integrated circuit, will enable the required output current to be delivered to the load.

The driver transistors Tr1 and Tr3 in the circuit shown each have a current gain of not less than 40 at a collector current of 0.2A, and the power output devices Tr2 and Tr4 a gain of not less than 30 at 4A. Thus the driver current could reach $40 \times 0.005 = 0.2$ A and the output current $30 \times 0.2 = 6$ A; this exceeds the peak current of 3.87A required into 4Ω for a 30W output and 2.24A into 8Ω for a 20W output.

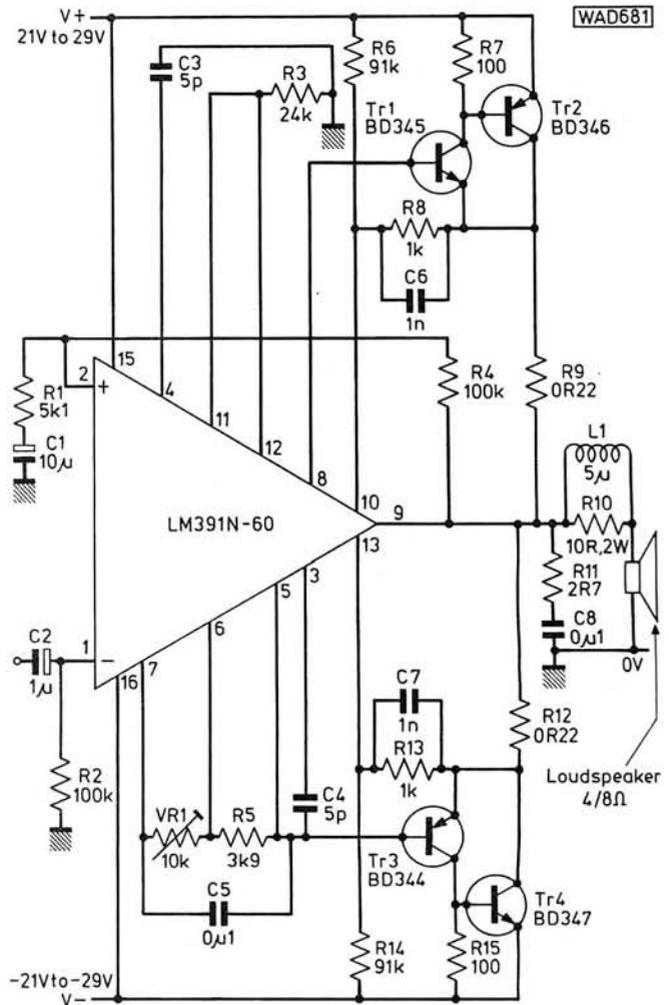


Fig. 17: A power amplifier using an integrated circuit power driver

Any other transistors with ratings of V_{CE0} 60V, I_c 4A and a suitable power rating could be used in the output stages if they satisfy the above condition. The thermal resistance of the heatsink used for each power transistor in the Fig. 17 circuit has been recommended as not more than 4.8°C/W . The driver devices, Tr1 and Tr3 do not require heatsinks.

75W Amplifier

The circuit of Fig. 18 shows an amplifier which can operate from ± 32 V balanced power supplies to feed an output of up to 75W into a 4Ω load. The TIP141 and

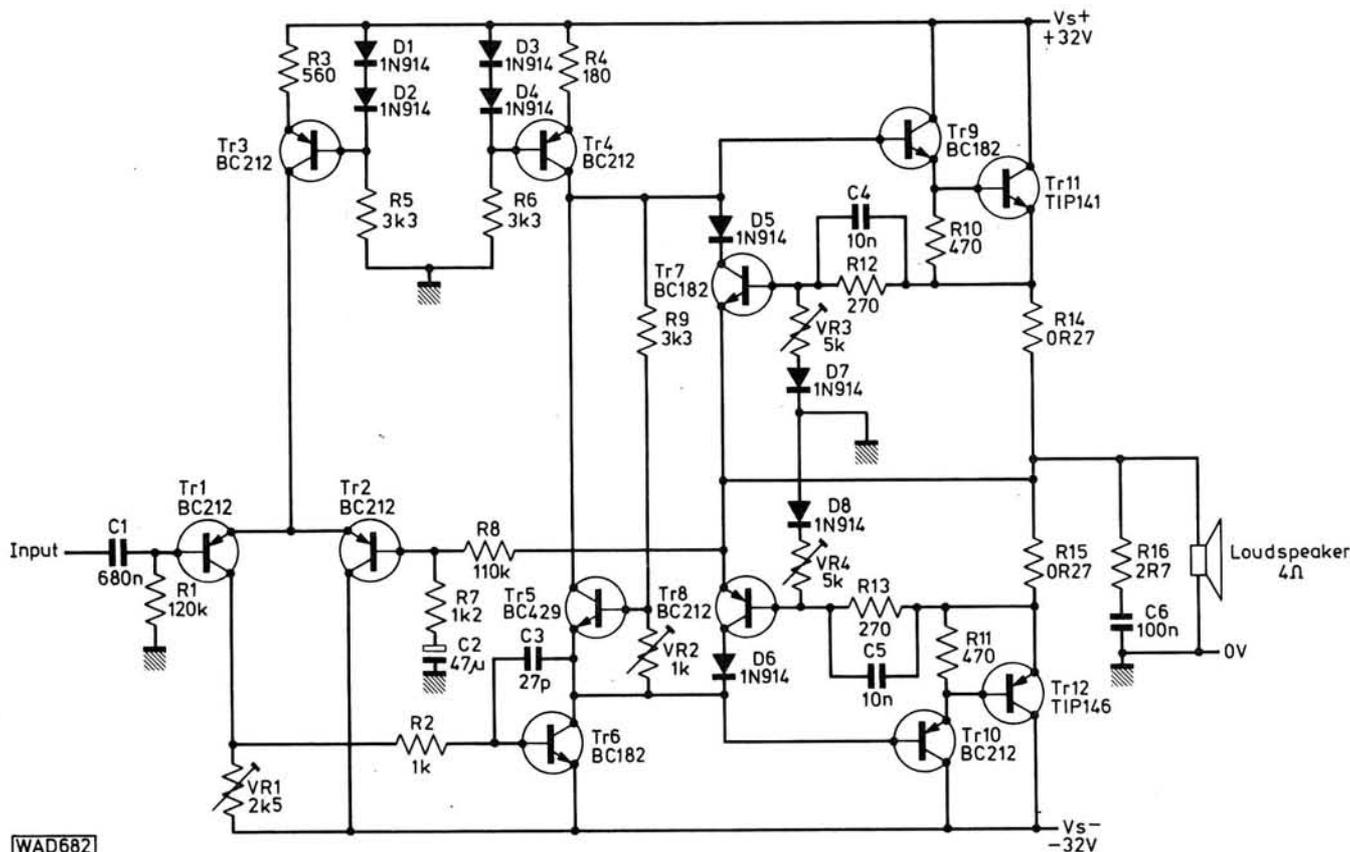


Fig. 18: A 75W amplifier circuit

TIP146 complementary power Darlington devices are used in the output stages, this circuit having been designed by Texas Instruments Limited. As in the case of most amplifiers which are directly coupled to a loudspeaker without a d.c. blocking capacitor, a differential input stage is employed; in the circuit shown, two discrete transistors are employed in this input stage, but a somewhat more expensive dual transistor would provide rather better stabilisation of the circuit with temperature variations.

The constant-current source incorporating Tr3 controls the current to the input stage, whilst the Tr4 circuit controls the constant current in the Tr5 and Tr6 circuits. Tr5 is the V_{BE} multiplier circuit and it is recommended that VR2 is adjusted for a quiescent current in the output stages of 50mA. The Miller capacitor C3 controls the high frequency response and improves stability. The use of the constant-current source of Tr4 in the driver stage increases the rejection of mains hum and enables a high performance to be obtained without the use of a "bootstrap" capacitor. However, the use of a constant-current source providing about 20mA for an adequate drive to the output Darlington is not practical owing to the relatively high power involved.

The additional emitter followers Tr9 and Tr10 are therefore used in this circuit between the Tr6 stage and the output Darlington. This enables the Tr4 current to be set at a little over 3mA, and Tr4 and Tr6 can be low-power devices.

The circuit of Fig. 18 incorporates automatic limiting of the output current by means of the circuit of Tr7 and Tr8 which limit the current in Tr11 and Tr12 respectively. The current level at which limiting occurs is determined by the settings of VR3 and VR4. If a current of 20A flows in Tr11, this current will develop a voltage of 5.4V across the resistor R14. The components R12, VR3 and D7 act as a potential divider, and if the potential at the base of Tr7 exceeds about 0.6V, this transistor will conduct so that part

of the current which would normally flow into the base of Tr9 flows into Tr7. Hence the current in Tr11 is limited to a required maximum value. Similarly the maximum current in Tr12 is set by VR4.

The feedback in this circuit is conventional, the gain being equal to $(1 + R8/R7)$ or about 92 with the values shown.

Ultra-High Power

A circuit which can provide very high power outputs at high currents is shown in Fig. 19. The input part of this circuit is similar to that of Fig. 16, but a MAT-01 ultra-matched dual transistor is used in the input stage. The complementary Darlington pair, Tr6 and Tr7, are 100V devices instead of the 80V devices used as the output devices in Fig. 16. However, in Fig. 19 the Darlington are not the output devices, but the output current from each Darlington feeds three 30A power transistors, each with a current-sharing emitter resistor.

If the supply lines are stabilised at $\pm 48V$ and each output transistor passes 25A, there will be a 5V drop across each emitter resistor. Nevertheless, if the output voltage can swing by $\pm 40V$ and the peak output current is 75A, this corresponds to a peak power of 3kW or a mean power of 1.5kW. In order to obtain such output levels, the load impedance must be about 0.53Ω ; such a low impedance is best obtained by connecting a number of loudspeakers in parallel. A current-limiting circuit like that of Fig. 18 is required, omitted from Fig. 19 for simplicity.

The output transistors shown in Fig. 19 have a 90V V_{CEO} rating, so it is not possible to increase the supply voltages appreciably; higher voltage transistors could be used, but such devices which can deliver high currents are expensive. Each transistor must be mounted on a large

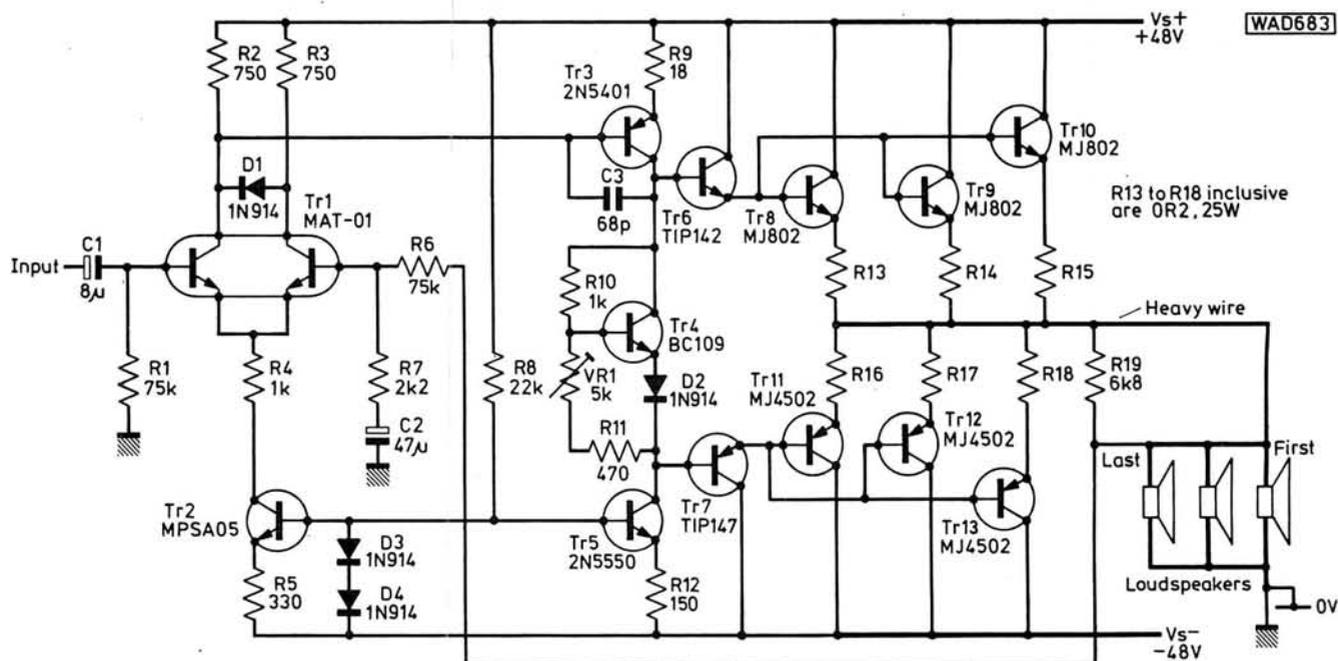


Fig. 19: An amplifier for very high output power levels

heatsink and the Darlington devices must also be mounted on heatsinks. The V_{BE} multiplier device Tr4 should be mounted in thermal contact with these heatsinks. Lower power levels can be obtained by using one or two pairs of complementary output transistors, but the number of output devices which can be used is limited by the current which can be supplied to their bases by Tr6 and Tr7.

The gain of the Fig. 19 circuit is equal to $(1 + R6/R7)$, or about 34 with the values shown. The resistor R19 does not normally have any effect, but if the negative feedback circuit from the speakers should be broken during use, R19 will ensure the feedback level is kept almost unchanged. This arrangement in which the feedback is taken off the last loudspeaker in the chain enables any effects due to the line impedance to be minimised.

This type of circuit is suitable for use as a concert hall amplifier or whenever very high power output levels are required. Distortion is around 0.03% at 1kHz, but increases to about 0.07% at 10kHz. VR1 should be adjusted so that each pair of output transistors passes a quiescent current of some 50mA.

Conclusion

The principles of operation of typical Class B amplifiers have been discussed together with a variety of conventional circuits. No attempt has been made to mention other types of audio amplifier, such as those using VMOS f.e.t.s which can produce very low distortion, or the Class D type (using pulse-width modulation) which offer a very high power efficiency but which produce relatively high levels of distortion (although this may not be true in the case of recent designs). Neither have current dumping amplifiers been examined.

The constructional techniques used when making amplifiers are of much importance. Problems of unwanted oscillation can occur if the input and output circuits are brought into close proximity, whilst inadequate decoupling of the power supply lines can also produce oscillation; decoupling must be effective at very high frequencies as well as at audio and power supply frequencies. Con-

siderable attention must be given to the correct use of earth returns, since if the signal grounding connection is used for the decoupling capacitors, an increased level of third harmonic distortion is likely to arise. The signal ground should be returned directly to the power supply unit and the other ground leads connected together in the amplifier and returned to the power supply ground separately. ●

UNCLE ED'S PAGE

▶▶▶ continued from page 23

Internationally agreed symbols are allotted to all the various modulation types, ordinary double sideband amplitude modulation (d.s.b. a.m.) being A3. The letter "A" means amplitude modulation, and the figure "3" means telephony (speech or music). Suffix letters, which at one time were small letters, but are now always capitals, indicate particular varieties of modulation. For s.s.b. with the carrier and one sideband suppressed, the symbol is A3J. This is what I've been talking about this month. Another variety is A3A, which is s.s.b. with the carrier level reduced rather than suppressed. Figures of 16dB or 26dB below the peak power of the remaining sideband are common, with the constant carrier being used for automatic frequency control (a.f.c.) and/or automatic gain control (a.g.c.). This mode was widely used when transmitter and receiver oscillators were not as stable as they are now, though not normally among amateurs.

"Compatible s.s.b.", symbol A3H, comprises one sideband and full carrier. It has the advantage of saving bandwidth whilst still being able to be received on a d.s.b. receiver without a b.f.o. (hence "compatible"), and with less critical tuning. In practice, the carrier level is often reduced by 6dB, giving a power saving at the transmitter without affecting the signal's compatibility.

Transmission of speech via a s.s.b. link does not require the receiver c.i.o. to be **in phase** with the transmitter carrier oscillator, merely on the same frequency. Some types of data transmission do require the two oscillators to be in phase, otherwise the received pulses are distorted.

AMATEUR RADIO EXCHANGE



Brenda (G8SXY) and Bernie (G4AOG) invite you to visit the only shop in London where you can see and try ALL the leading makes of Amateur Radio equipment under one roof . . . YAESU, ICOM, TRIO/KENWOOD . . . and special this month a really marvellous new receiver from SONY . . . not a name you expect us to be promoting, but then we've always said that the only way to buy a rig is to compare as many alternatives as possible side by side, and then choose the one that's right for you. So, come to the shop where you can do just that . . . and have a cup of Brenda's coffee too!

NOW WITH FM


ARE YOU A G8 ABOUT TO TAKE YOUR 'A' LICENCE? OR ARE YOU TAKING YOUR G4 STRAIGHT AWAY?

Either way, why not start listening right now on a Yaesu FT-101 transceiver? It really knocks spots off the average general coverage receiver, with better selectivity, better sensitivity, better stability . . . And remember, cooling fans and microphones come FREE with 101s from A R E!!

So, buy your rig now, and claim your mic and fan when you get your G4.

FT-101Z £488 inc. VAT

FT-101ZD £569 inc. VAT

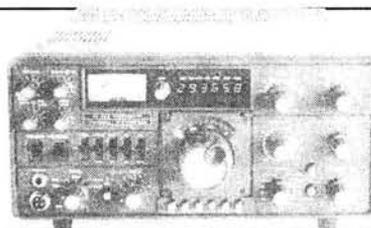


FRG-7

Still the finest value-for-money communications receiver on the market at only **£185** inc. VAT and free Heliscan aerial worth **£15**.

FRG-7700

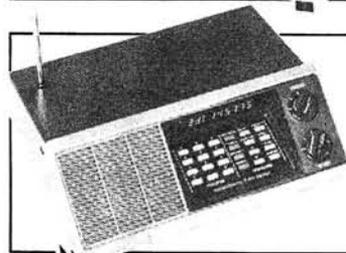Yaesu's latest receiver with FM right across the band and optional memory facility plus excellent filtering. **£299** inc. VAT and free Heliscan aerial worth **£15** (Memory extra).




BEARCAT 220FB

The super scanner which brings you all the excitement of the VHF and UHF frequencies . . . aircraft, marine, amateur, plus so much more. **£258.75** inc. VAT.

SX-200

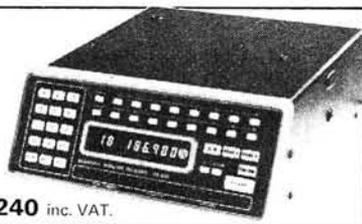Another of our sophisticated scanning receivers. Similar functions to the BEARCAT, but even wider frequency coverage, and with AM and FM right across its range. **£240** inc. VAT.



NEW

THE FANTASTIC NEW SONY ICF-2001

At last, from one of the world's electronics giants, not just a new HF communications receiver, but a whole new breed of radio which supplants the conventional multi-band concept and replaces tuning knob and dial with a direct-access tuning keyboard and Liquid Crystal Display. LCD digital frequency readout confirms exact, drift-free reception. As easy to use as a calculator, and so compact you can slip it in your briefcase.

- FM/AM/SSB/CW wide spectrum coverage, AM/SSB/CW 150kc to 30 MHz and FM 76MHz to 108MHz
- Dual-conversion superhet AM circuitry assures high sensitivity and interference rejection
- Quartz-crystal PLL frequency synthesis for all bands ensures utmost tuning stability without tuning drift
- Direct-access digital tuning keyboard and LCD digital frequency readout give quick key-touch station selection
- Manual tuning or automatic scanning for effortless signal searching, easy DXing, plus "Scan Auto Stop" facility
- Six station pre-sets, plus two auxiliary pre-sets, for instant reception of memorised stations on any band, plus LCD memory indication
- 5-step LED signal-strength indicator ● Local/Normal/DX sensitivity selector for AM and SSB/CW Clarifier/Fine-Tune Control ● Low distortion reception ● Sleep timer, with LCD readout, can be set in 10-minute increments for up to 90 minutes playing time before automatic shut-down

And all for the amazingly low price of just £149 inc. VAT




Closed Wednesday, but use our 24-hour Ansafone service. LICENSED CREDIT BROKERS. *Ask for written quotation. INSTANT HP AND 6 MONTHS NO INTEREST HP TERMS AVAILABLE FOR LICENSED AMATEURS AND BANK/CREDIT CARD HOLDERS.



Credit Card Sales by telephone.

2 NORTHFIELD ROAD, EALING, LONDON, W13 9SY. TEL: 01-579 5311

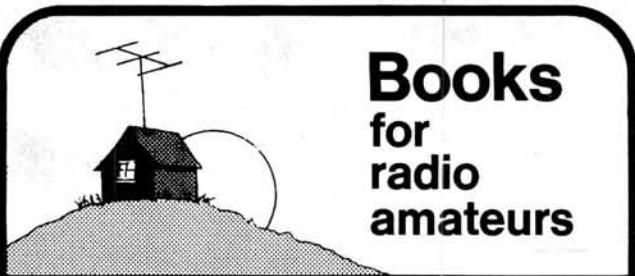So easy for Overseas visitors - Northfields is just seven stops from Heathrow on the Piccadilly Line.



Books for radio amateurs

RSGB Publications

A Guide to Amateur Radio (18th edn, paperback)	£3.07
A Guide to Amateur Radio (18th edn, hardback)	£6.32
Amateur Radio Awards (2nd edn)	£3.41
Amateur Radio Operating Manual	£4.96
Amateur Radio Techniques (new 7th edn)	£6.16
Morse Code for Radio Amateurs	£1.31
OSCAR - Amateur Radio Satellites	£4.50
RSGB Amateur Radio Call Book (latest 1981 edn)	£4.37
Radio Amateurs' Examination Manual (8th edn)	£2.73
Radio Communication Handbook (5th edn) Vol 1	£10.20
Radio Communication Handbook (5th edn) Vol 2	£9.06
Radio Data Reference Book (4th edn)	£5.02
Test Equipment for the Radio Amateur (2nd edn)	£5.86
TVI Manual (2nd edn)	£1.95
VHF/UHF Manual (3rd edn)	£8.70
World at their Fingertips	£4.28

Logbooks

Amateur Radio Logbook	£2.86
Mobile Logbook	£1.14
Receiving Station Logbook	£2.68

Wall maps

Great Circle DX Map	£2.12
IARU QTH Locator Map of Europe	£1.34
QTH Locator Map of Western Europe	£1.34
World Prefix Map	£2.23

Morse instruction

Morse Code Cassette Stage 1 (5wpm)	£3.85
------------------------------------	-------

Other Publications

A Course in Radio Fundamentals (ARRL)	£3.24
Active Filter Cookbook (Sams)	£12.69
All About Cubical Quad Antennas (RPI)	£2.92
Antenna Anthology (ARRL)	£3.71
ARRL Electronics Data Book	£3.58
Beam Antenna Handbook (RPI)	£4.22
Beginner's Handbook of Amateur Radio (Sams)	£8.26
Better Short Wave Reception (RPI)	£3.65
Care & Feeding of Power Grid Tubes (Varian)	£2.98
CMOS Cookbook (Sams)	£9.59
FM & Repeaters for the Radio Amateur (ARRL)	£4.08
Hints and Kinks for the Radio Amateur (ARRL)	£3.32
Practical Antennas for the Radio Amateur (SCELBI)	£8.02
Radio Frequency Interference (ARRL)	£3.09
Shortwave Listeners Guide (Sams)	£4.44
Simple Low-cost Wire Antennas (RPI)	£3.16
Single Sideband for the Radio Amateur (ARRL)	£3.84
Solid-state Basics (ARRL)	£4.85
Solid-state Design for the Radio Amateur (ARRL)	£6.25
The ARRL Antenna Book	£4.30
The Complete Handbook of Slow Scan TV (Tab)	£5.76
The Radio Amateur's Handbook, 1981 (ARRL)	£8.56
The Radio Amateurs VHF Manual (ARRL)	£4.15
Understanding Amateur Radio (ARRL)	£4.32
World Atlas (RACI)	£1.91
World Radio TV Handbook, 1981 (Billboard)	£10.62
80m DXing (CTI)	£3.03
99 Ways to Improve Your Short-wave Listening (Sams)	£4.44

Prices include postage, packing and VAT where applicable. Postal terms: cheques/POs with order (not stamps or book tokens). Goods are obtainable (less P & P) at RSGB HQ, 9.30-5pm, Monday - Friday.

The RSGB is the national society representing all UK radio amateurs and membership is open to all interested in the hobby, including listeners. The Society also publishes a complete range of books, log books and maps for the radio amateur. Contact the membership services section for more information about amateur radio, the RSGB and its publications.



Radio Society of Great Britain
35 Doughty Street, London WC1N 2AE
Telephone 01-837 8688

MICROWAVE MODULES

RTTY DECODER

AR245

HFC 55 FREQUENCY COUNTER
READ THE REVIEWS IN THIS ISSUE,
AND THEN COME ALONG AND
TRY THEM AND THE **SX200**
SCANNING RECEIVER AT

M.R.S.
COMMUNICATIONS LTD.

76 Park Road, Whitchurch,

CARDIFF

Tel: Cardiff (0222) 616936

OPEN
9 am to 5 pm
6 Days



WOOD & DOUGLAS

With the winter evenings approaching, the constructional season for radio amateurs is about to begin. If you are undecided on your winter project perhaps you can find something in our range of over 30 kits and modules to suit you.

70FM05TR In case you missed October's review of this single channel FM transceiver for 70 cms here are a few details. The receiver sensitivity is typically 0.4µV and uses dual gate MOSFETS and a high quality crystal filter. The audio output drives an 8Ω speaker. The transmitter gives 500mW of RF and has a modulator on the pcb. Both boards use readily available crystals and measure a very compact 6" by less than 1 1/4".

Kit	RX £38.50	Assembled	RX £47.25
	TX £17.80		TX £25.95

70MC06TR When one channel is not enough then by adding this two pcb set you will have 6 channels on tx/rx. This includes a toneburst for repeaters and a scanner to ease monitoring.

Kit	RX £18.60	Assembled	RX £26.05
	TX £11.30		TX £18.10


144SY25B An FM synthesiser for 25KHz steps at 144-146MHz. The output frequencies are 5-5, 11, 22 or 45MHz on receive and 6, 12 or 24MHz on transmit. This will feed most commercial radio telephones and also the **PW NIMBUS**. So for the cost of ten crystal channels you get full band coverage, crystal controlled toneburst, repeater ±600KHz offset, out of lock inhibit and channel selection by channel number.

Kit	£50.95	Assembled	£69.70
-----	--------	-----------	--------

INTERESTED? If you would like further details of these and our many other products then send a large SAE (please!) for the latest lists. The above prices include VAT at the current rate but please add 60p p&p on the total order. The prices include all items to make a working pcb module. We do not supply external hardware such as boxes or switches etc. This leaves you free to use the modules in whatever configuration you wish and yet have confidence that the electronics will perform well. We will gladly service any of our products providing it has been built as directed. We make a small charge for this facility depending on complexity. Kits when in stock are return of post otherwise 10-14 days. Assembled items 10-20 days.

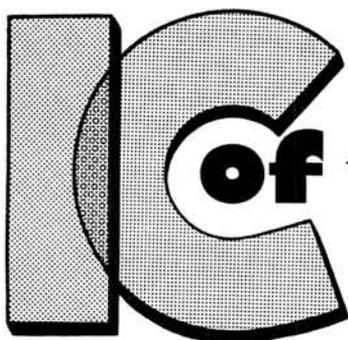9 HILLCREST, TADLEY
BASINGSTOKE, HANTS RG26 6JB





of the month

Brian DANCE M Sc

Plessey SL6310C

There are quite a wide variety of audio amplifier i.c.s on the market at the present time. They are all basically operational amplifiers which are able to provide moderately high output current with a reasonably high output voltage swing, so that they can feed adequate power to the loudspeaker. The fairly new Plessey SL6310C device can deliver only a small output power level (of the order of 0.5W), but it has the advantage of having two muting pins so that it can be switched off by either a "high" or a "low" voltage being applied to the appropriate pin.

The device requires a low quiescent current of about 5mA (a quoted maximum of 7mA for any device), but obviously needs more power than this when feeding an appreciable signal to a loudspeaker or other load. When muted the current consumption is only about 0.6mA. Therefore this device is very suitable for use with battery power supplies, such as an audio amplifier in a portable radio receiver, or an audio amplifier for hi-fi headphones.

Output Power

As with any audio amplifier, the maximum output power is closely related to the power supply voltage used to drive the device. When fed from a 9V power supply, the SL6310C is guaranteed to be able to deliver at least 400mW into an 8Ω loudspeaker load, a value of 500mW is typical for this type of device. Variation of output power with change in the supply voltage for the 4Ω, 8Ω and 16Ω load impedances is shown in Fig. 1.

The SL6310C is specified for operation over the power supply voltage range of 4.5V to 13V: 13V should be regarded as the upper working limit, so as to allow some tolerance for any supply variation. If the supply potential exceeds 15V, even for a small fraction of a second, the device may be damaged.

Connections

The SL6310C is available in an 8-pin d.i.l. package with the connections as shown in Fig. 2 and also an 8-lead circular metal i.c. package with connections as in Fig. 3. There are no real differences in performance, although the d.i.l. package can dissipate up to 0.5W and the circular metal package 0.45W both at 85°C.

It may be noted that the device has the usual non-inverting and inverting inputs of an operational amplifier together with the two muting pins whose use will be discussed later.

Amplifier Circuit

A simple audio amplifier circuit using the SL6310C is shown in Fig. 4. The input resistors R1 and R2 apply a bias to the non-inverting input of pin 1 of about half the power supply line voltage, and this raises the quiescent output voltage to a similar value so that a maximum out-

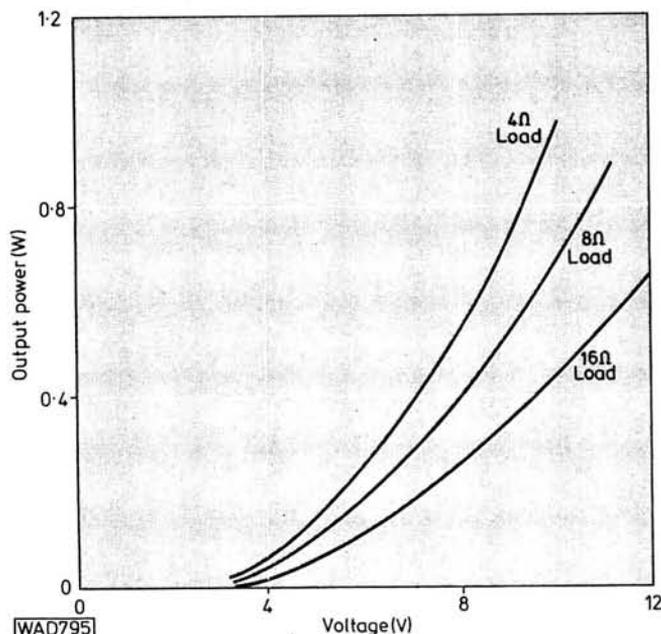


Fig. 1: Output power with varying supply voltage

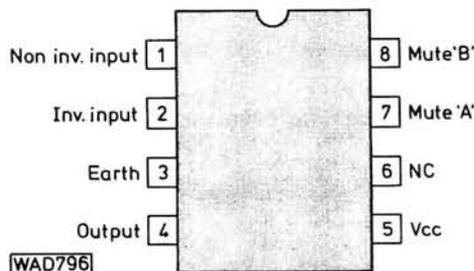


Fig. 2: Pin-outs for 8-pin d.i.l. package

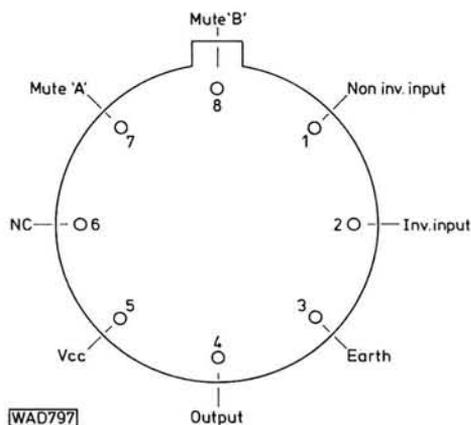


Fig. 3: Pin-outs for circular package

put voltage swing can be obtained. The input impedance is approximately equal to R1 in parallel with R2; about 100kΩ with the values shown. The input capacitor pre-

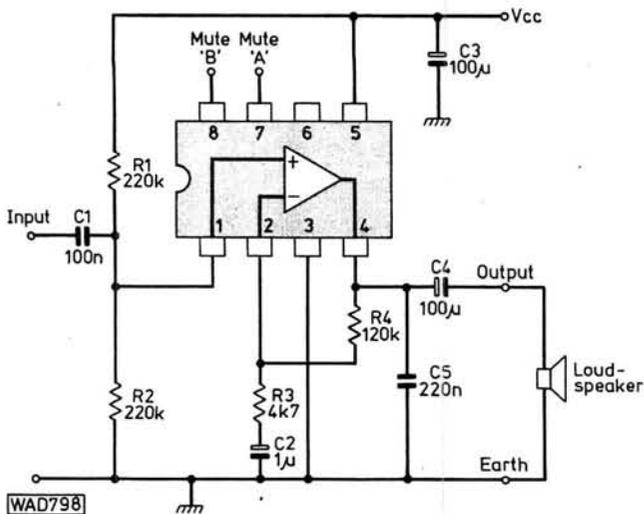


Fig. 4: A simple audio amplifier using the SL6310C

vents the bias voltage from being affected by any input connection made to the device. The input signal is fed to the non-inverting input for convenience so as to keep the input impedance of the circuit high.

The voltage gain of the SL6310C device without feedback is not less than 40dB and is typically 70dB, but the feedback provided by the resistors R3 and R4 reduces this gain. The voltage gain is equal to $(R3 + R4)/R3$ and the manufacturer recommends that this should be between 3 and 30 for best results.

The gain of the device without feedback falls off at frequencies over 600Hz (shown in Fig. 5). The high frequency response can be reduced by connecting a small capacitor across R4 to provide increased negative feedback at high frequencies. The response at low frequencies is determined by the input and output coupling capacitors and by the capacitor C2.

Muting

If the muting facility of the SL6310C is not required, the two muting connections may be left unconnected as in Fig. 4. If mute control "A" at pin 7 is left open-circuit or connected to a potential within 1V of the positive supply line through a 100kΩ resistor, it will not affect the operation of the circuit. However, when the potential of this pin is reduced to within 1V of the negative supply potential (through a 100kΩ resistor), the audio output from the SL6310C is muted.

Similarly the mute control "B" of pin 8 may be left open-circuit or connected to a potential of less than 1V for normal operation of the amplifier circuit. If a potential of over 2.5V is applied to pin 8, the amplifier will be muted. As the input resistance of the pin 8 circuit is of the order of 100kΩ, this pin is suitable for interfacing with the output of c.m.o.s. logic devices.

It should be noted that the manufacturer recommends that only one of the muting pins be used at any one time. The unused pin should be left unconnected.

The variation of the quiescent supply current required by this amplifier is shown in Fig. 6, for both the muted state (left-hand vertical scale) and for normal non-muted state (right-hand vertical scale).

When an output power of 400mW is being obtained using a 9V power supply and with the gain set to 28dB, the typical total harmonic distortion is 0.4 per cent (with a maximum value of 3 per cent).

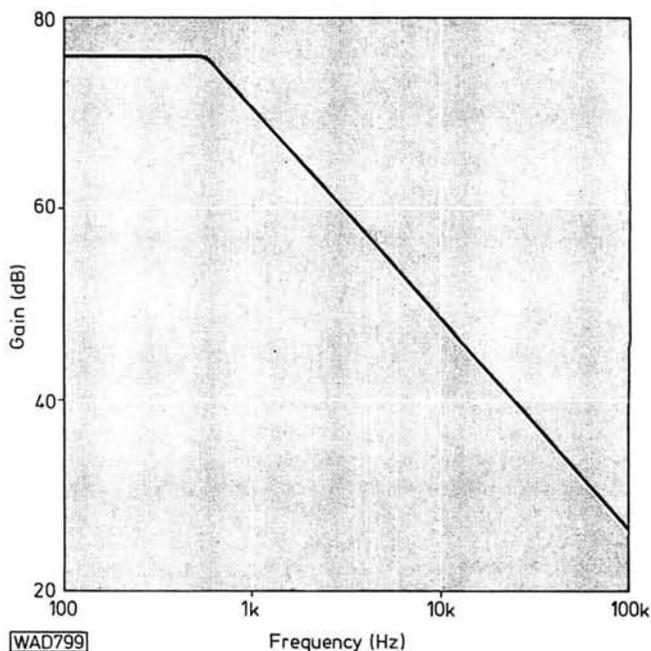


Fig. 5: Open-loop gain versus frequency

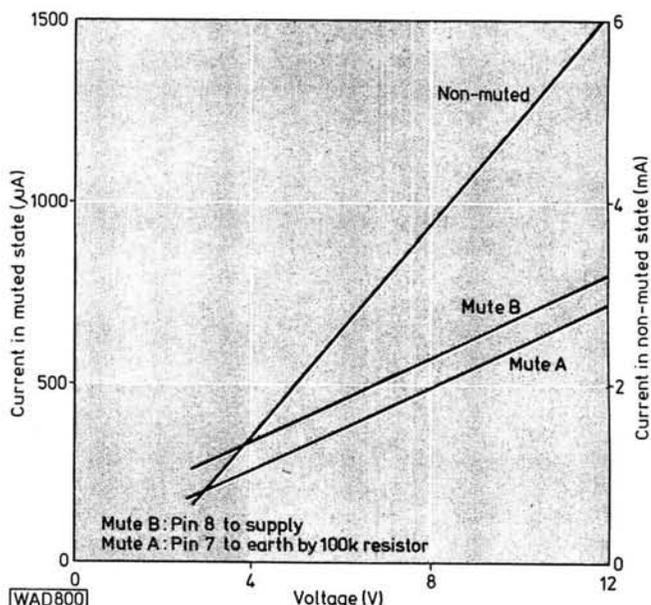


Fig. 6: Quiescent supply current variation

The input bias current from the amplifier is typically 0.2µA with a maximum value of 1µA. This current flows out of pins 1 and 2, since *pnp* transistors are used in the internal input stage of the device.

A switchable audio amplifier circuit of this type can be used when it is necessary to silence the circuit whilst someone is speaking. For example, in an intercom system it could be used to ensure that the audio is muted when one is speaking at the end of the link concerned. The muting could be controlled by the output from a suitable logic circuit device. It would also be possible to silence the amplifier when acoustic feedback from the loudspeaker to a microphone produces a "howl".

continued on page 63 ►►

NEWS NEWS NEWS

Mobile Rallies

In response to my "Can I Help You" notices in the "News" column, I am receiving club activity information in good time for publication; many thanks to all club secretaries. This will enable me to let readers have a reasonable notice of forthcoming events.

Have you got your diaries out? Yes, then off we go!

Southend and District Radio Society have organised their mobile rally at *Southend Airport Exhibition Centre, Aviation Way, Southend-on-Sea, Essex*, on Sunday, 26 April. Among the many attractions will be bring and buy stalls, aircraft museum, talk-in station, licensed bar, refreshments and parking for 300 cars. Further details from: *F. Thorogood G8ORV, 30 Grange Gardens, Southend-on-Sea, Essex. Tel: (0702) 616239.*

The Drayton Manor Mobile Rally organised by The Midland Amateur Radio Society and Stoke-on-Trent Amateur Radio Society will take place on Sunday, 26 April at Drayton Manor Park near Tamworth, Staffordshire.

The Park is located on the A4091, which is within easy reach of the M1, M5 and M6 motorways, it is well signposted.

There will be all the usual attractions including special entertainments for all the family. Further details and free car stickers are available on request to: *Norman Gutteridge G8BHE, 68 Max Road, Quinton, Birmingham B23 1LB. Tel: 021-422 9787.*

The YMCA Amateur Radio Club in Maidstone are holding their rally on Sunday, 3 May at the *YMCA Sportscentre, Melrose Close, Cripple Street, Maidstone ME15 6BD. Tel: (0622) 43317.*

All the Sportscentre space has been allocated to the rally and there will be a special section for the XYL and YLs. Also this year there will be a licensed bar. Further details from the Sportscentre.

Plymouth Radio Club, following a very successful rally last year, will be holding their fourth annual rally on Sunday, 24 May at their meeting place at *Tamar Secondary School, Paradise Road, Millbridge, Plymouth PL1 5QW.* Further details from: G4KXZ at the club QTH.

G-QRP × 1000

December 1980 represents an important landmark in the history of the G-QRP Club, the organisation devoted to promoting interest and growth in low power amateur radio communication (5 watts or less). The landmark was the enrolment of their 1000th member, John Bazley G3HCT. John, a past President of the RSGB, is a very keen DXer and is currently on the ARRL Honour Roll with 350 countries confirmed.

The G-QRP Club has come a long way since the winter of 1974/75 when "Sprat" No. 1, the Clubs' quarterly bulletin, was published by George Dobbs G3RJV, the founder of the Club, and circulated to just 30 members. By the winter of 1976/77 the membership list stood at 500 and included enthusiasts from all over the world.

The Club has members in 32 countries and all continents. Membership is open to any amateur or s.w.l. in the world with an interest in QRP. The subscription is £3.50 or \$9 US, and all enquiries regarding membership should be sent to: *The Secretary, George Dobbs G3RJV, 17 Aspen Drive, Chelmsley Wood, Birmingham B37 7QX.*

Computer Club Call

With computer technology extending into virtually every aspect of electronics, readers may be interested in learning of the activities of the Amateur Computer Club.

The A.C.C., one of the oldest, if not the oldest, amateur computer club in the country (founded 1972), is a national organisation to promote interest in amateur computers and computing, to facilitate the exchange of information and ideas, and to help members with their home computer systems.

A.C.C. membership is currently £4.50 per year, and is open to anyone with an interest in computers and computing. Further details and membership forms are available from (s.a.e. please): *Membership Secretary, Jim MacDonald, 1 Carlton Court, Studley Grange Road, London W7 2LU.*

Offer from Ambit

Ambit International, the component suppliers, have asked me to pass on to readers their standing offer of "free bits" for enthusiasts with viable ideas for equipment designs where the intention is to produce a magazine article at the end of the project.

Further details from: *Ambit International, 200 North Service Road, Brentwood, Essex CM14 4SG. Tel: (0277) 230909.*

Classic by G3VA

The 18th edition of the very popular book, "A Guide to Amateur Radio" by Pat Hawker G3VA is now available.

Priced at £5.20 (£6.18 incl. p&p), the 148-page book can be obtained from: *RSGB, 35 Doughty Street, London WC1N 2AE. Tel: 01-837 8688.*

New Catalogue

Greenweld, the electronic component and equipment suppliers of Southampton, recently published their 1981 catalogue.

New additions this year include kits, r.f. connectors, keyboard switches, new multimeters, many more transistors and i.c.s, etc. Also included are discount vouchers worth 60p, a 1st class reply paid envelope and free bargain list.

The catalogue costs 50p plus 20p p&p and is available from: *Greenweld Electronics Ltd., 443 Millbrook Road, Southampton SO1 0HX. Tel: (0703) 772501.*

New President For SERT

The Council of the Society of Electronic and Radio Technicians recently announced that Mr T. Bryce McCrerrick had accepted an invitation to become President effective from 1 January 1981, in succession to Air Vice-Marshal A. A. Morris who has held office since 1976.

SERT, 57/61 Newington Causeway, London SE1 6BL. Tel: 01-403 2351.

Letters to the Editor intended for publication must be original, and not duplicated to or copied from other publications. We reserve the right to shorten or edit them if necessary.

Letters

CB Australia

Sir: Having suffered the clumsy introduction of 27MHz CB radio in Australia, having seen the profound social advantages of it and having been deeply involved in the debate relating to its continuation and expansion, it is very sad for me to see, as an interested citizen and radio amateur, your magazine taking such a negative attitude to 27MHz CB radio. Australian CB operators and amateurs hope that this form of CB radio will continue with gradual lifting of the restrictions on its use. It is to be effectively policed.

With a little bit of luck, the rest of the world will have 27MHz CB, as its allocation in countries such as Japan spoils the megahertz for any other use. I hope the British Government is more generous than your magazine suggests, and that a final decision on their part awaits the investigation into the matter being undertaken at present in this country.

*F. E. Stewart Mair FRACP VK3BSM
Victoria, Australia*

Speech Processor

Sir: You may be interested to learn that the AF Speech Processor design published in *PW*, January 1980, has been a resounding success in Sydney, Australia, where to my own knowledge at least a dozen units are in use.

Users include: Ken VK2VHQ, Reg, 'AKY, Peter 'VJB, Eunice 'VHB, John 'VUZ, Doug 'VVG, John 'VSF, Peter 'AGB, Ted 'LF, Ron ZL3SA, and me, plus a number of CB operators who, because of the illegal use of such equipment, naturally prefer to remain anonymous! The use of CB gear is legal but it may not be modified in any way, and that includes the use of any add-on equipment.

My own 80 metre s.s.b. rig is entirely home-brew and radiates a whole 2 watts p.e.p. via a home-brew transmatch into a half-wave antenna. In recent weeks I have had two ZL contacts plus one into Tasmania, and plenty into Victoria and Queensland.

In all DX contacts, reports indicate a definite improvement in readability, though at the expense of speech quality. However, the 1200 miles to ZL-land on 2 watts s.s.b. on 80m is pretty gratifying in anyone's language. If the going gets really rough, I use a little linear built around a single 2N5590 to put 8 watts up the spout—real QRO stuff. On behalf of those Down Under, thanks for a good design.

*Clive S. Wallis VK2VWK/YTC
Miranda, NSW
Australia*

Introducing RTTY

Sir: I am writing to compliment you on your recent publication of Jeff Maynard's introduction to radio teletype. If you will permit me, I would like to bring your readers up to date in respect of membership and the activities of the British Amateur Radio Teleprinter Group, which Mr Maynard kindly praised at the end of his article.

At its Annual General Meeting earlier this month, the Group's annual subscription was slightly increased to £2.50, with a joining fee of 50p for new members. The member now responsible for membership matters, from whom further information may be obtained, is:

Mrs Irene Double,
89 Linden Gardens,
Enfield,
Middlesex.

Your readers may also like to know that the times and frequencies of the GB2ATG news bulletins are included in the quarterly Group Newsletter, which all members receive upon joining.

The 1981 BARTG Convention will be held in Harpenden Public Hall on Saturday, 18 July.

*Trevor Campbell Davis,
Chairman, BARTG,
London W3*

Amateur Radio in NI

Sir: I have just read "Big Muff's" letter in January '81 *PW* and I am appalled at the naivety of his enthusiasm for CB in Northern Ireland. As elsewhere in the UK the problems caused by these head-cases are enormous. Let me give you a few illustrations. How many people are being charged for TV service where the problem is, in fact, 27MHz TVI and find the problem is just as bad when the set is returned? I know several in my own street. This week I was stopped by a police motorcyclist on a country road who thought my $\frac{7}{8}\lambda$ 2-metre whip was for 27MHz. He complained of interference being caused on certain police channels here by "good buddies".

In Northern Ireland we have a very friendly bunch of radio amateurs numbering now about 800 licences. In recent months several of the newly licensed amateurs I have spoken to have turned out to be disillusioned CBers. The RAE classes all around Northern Ireland this winter are overflowing with "good buddies" only too keen to escape the confines of the constant interference, foul language and restricted range of 27MHz. More power to them I say. What really annoys me is that a number of kids are managing to buy (or steal in certain known instances) 145MHz equipment, instead of 27MHz equipment, and pollute our three repeater stations GB3NI, GB3WT and GB3LY with their "30 for a copy" nonsense.

May I take the opportunity of informing "Big Muff" and any other Northern Ireland CB readers of *PW* that the radio amateurs here are not against you. Religion and politics have never had a place in amateur radio. As the chairman of the oldest amateur club in Ireland we would welcome anyone with an interest in radio communication. We meet every Tuesday evening in our clubroom on the fourth floor of the City of Belfast YMCA in Wellington Place. We also meet on Saturday afternoons and our station G16YM is known worldwide. Last year we made contact with over 3000 stations in all parts of the world.

*David Hutchinson
G14FUM/EI4DJ
City of Belfast YMCA Radio Club*



Lee Electronics Ltd

Londons Leading Stockists Of:
STANDARD YAESU ICOM FDK KDK MICROWAVE MODULES LUNAR SST SHURE HI-MOUND CDE STOLLE
TELECOMM ANTENNAE J-BEAM SWAN KATSUMI ETC.

NEW FROM STANDARD THE C78 UHF FM SYNTHESIZED TRANSPORTABLE

JUST LOOK AT THE FOLLOWING FEATURES:

- ★ Full 10MHz coverage 430-440MHz in 25kHz steps
- ★ LCD digital readout
- ★ S and RF power meter
- ★ Programmable repeater shift and tone burst
- ★ 5 Programmable memories for your favourite channels
- ★ Full scanning facilities of vacant or occupied channels
- ★ A full 1W/10W switchable RF power
- ★ Up/down channel control on the microphone
- ★ Can be used from dry cell or rechargeable batteries
- ★ Optional mobile mount and 10W booster available
- ★ ONLY 5"W + 2"H + 7½"D




THE C78 IS MADE TO THE SAME HIGH STANDARD AS THE C8800 AND C7800 SO YOU CAN BE ASSURED OF FIRST CLASS QUALITY AND VALUE FOR MONEY

Price: C78 - £209.50, Mounting Bracket - £17.75
Carrying case - £6.95, Linear Amp (10W) - £65

SPECIAL OFFER - IF ALL BOUGHT TOGETHER £289 inc VAT and postage

STANDARD C8800 - The 2m mobile rig - ex stock £251.25

Just a small selection from our comprehensive range of accessories.

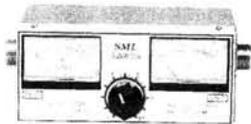

SWR25: This ever-popular twin SWR and Power meter covers 3.5-150MHz at **£12.65** inc. VAT. P&P 50p.




DL-30 Dummy load 25W DC-150 MHz **£6.35** inc. VAT. P&P 25p.

T-100 80W Dummy load DC-500 MHz **£24.10** inc. VAT. P&P 25p.

T-200 150W Dummy load DC-500 MHz **£35.60** inc. VAT. P&P 25p.



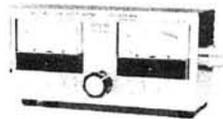SWR200B swr/power meter covering 3-200MHz 50/75 Ohm power range 3-30MHz, 20/200/2kW, VHF 2/20/200W **£40.20**. P&P £1.00.



T-435: VHF/UHF swr and power meter with 2/20/120 watt through line power measurement **£34.45** inc. VAT. P&P 75p.



CT-1 Coax Toggle 3 SO239's **£6.85** inc. VAT. P&P 25p.
CT-2 Coax Toggle 2 SO239's 1 PL259 **£6.85** inc. VAT. P&P 25p.



PX402 13-8V DC 3 amp continuous 4 amp max fully stabilized power supply with overload protection **£22.95** inc. VAT. P&P £2.00.

Also available:
PH5000, 5A continuous, 7A surge **£45.94**.
EP2500, 25A continuous, 30A surge **£91.94**.

We are London's Largest Stockist of Microwave Modules products.

The latest from YAESU FRG7700



Basic **£309**
Memory unit **£83.95**
FRG7700 with memory fitted **£389**

(Free headphones included with both receivers)

TRIO R1000



ONLY £285

400 EDGWARE ROAD
LONDON W2
01-723 5521 Tlx: 298765



INSTANT H.P.
& P/EX. WELCOME

Send 25p for
full details
of our range.

YAESU MUSEN – FRG-7700



A NEW BREAKTHROUGH IN RECEIVER TECHNOLOGY

Yes indeed, the exciting new FRG-7700 GENERAL COVERAGE RECEIVER from YAESU MUSEN, the world's largest manufacturer of Amateur Radio equipment, will satisfy the demands of the most critical Short Wave Listener or Licensed Operator with it's superb performance and incredible specification – just consider the following condensed details:

Frequency coverage 150 KHz–29.999 MHz.

- Modes AM (fitted Narrow, Medium and Wide Filters).
 USB, LSB, CW and FM.
 Memory option with twelve channels and automatic band selection.
 CPU Digital Clock and Timer.
 State-of-the-Art Noise Blanker.
 FM Squelch Control.
 Mains or Battery operation.
 Digital and Analogue read-out.



Send today for full details of the new FRG-7700 or if you would like the full Yaesu catalogue as well 36 pence in stamps will bring you this together with our credit voucher for £3.60 – a 10 to 1 winning offer!

FRG-7700 £309. Memory unit £83.95. FRG-7700M (with fitted memory) £389

FULL DETAILS AND THE NEW LOW FACTORY PRICE LIST FROM
BRITAIN'S NO. 1 IMPORTER
 EX-STOCK – INSTANT CREDIT – FREE SECURICOR DELIVERY



AMATEUR ELECTRONICS UK



508-516 ALUM ROCK ROAD 021-327 1497
BIRMINGHAM 8 Telex 337045

THE SUPER SLIM JIM

2 Metre Omni-ANTENNA

* Designed by F.C. Judd (G2BCX) this new version of the famous **SLIM JIM** is only 42 inches long and so slim it is now available for mobile as well as base station operation and ideal for portable use also.

* The smaller dimensions and extremely high efficiency have been made possible by a unique high 'Q' helical stub matching system.

* The **SUPER SLIM JIM** is 50% more efficient than any other single element base station or mobile antenna.

* Base station model (LJ2) fully enclosed and protected against all weather conditions. Base socket makes to PL259 plug.

* Mobile model (MJ2) suitable for hole fixing gutter mount or mag-mount. Can be used on fibreglass roof tops. Stainless steel flexible element and weather protected. Base connection (PL259) makes to socket.

* A special feature of the **SUPER SLIM JIM** is an external sleeve adjuster for minimum VSWR.

* Bandwidth 145 to 146MHz. Gain 3dbi. Imp. 50 ohms. Send SAE for further details.

Base station (LJ2) or mobile model (MJ2) £17.50 inc. VAT P & P.

Base Station combo mast/wall mounting bracket with 'U' clamp £3.50 inc. VAT P & P. – Prices quoted UK only.

CASH WITH ORDERS ONLY. Cheques PO's payable to ZL COMMUNICATIONS.

TECHNICAL BOOKS

We stock a wide range of technical books – Amateur and CB Radio – Electronics – Audio – Microprocessing etc. For catalogue send 30p (or in stamps) (NOT SAE).

ZL COMMUNICATIONS

Cantley, Nr. Norwich, Norfolk, NR13 3RT.

Tel: 049 370 821

(9-5.30 Monday to Friday only).

Callers by appointment only.



LISTEN TO VHF MARINE or AMATEUR BAND with an SR9 RECEIVER



The SR-9 represents the finest value-for-money ever offered in the FM monitor receiver market. Giving fully tunable coverage of the 2 metre amateur band from 144-146 MHz, or Marine Band from 156-162 MHz, the SR-9 also incorporates the facility for installing optional crystals which will provide up to ELEVEN fixed channels for the most popular frequencies – mobile calling channel, local repeater channels, distress channel etc.

The SR-9 is completely self contained, even to the loudspeaker, and needs only 12 volts dc (negative earth) at approx. 200 mA to operate. Mounting hardware is provided for installation.

SR9 Receiver £46 (+£1.50 carr.) – State Amateur or Marine version.
 Special Package Deal No. 1: SR9 + Mains Power Supply + Amateur Band Loft/Roof Aerial for £72 (+£2 carr.)
 Special Package Deal No. 2: SR9 + Car Gutter Clip Aerial for £51. (+£1.50 carr.)

AR245 2m TCVR

As featured in this issue: £178

PW 'HELFORD' TX/RX

Components and kits available to build this SSB Tx/Rx inc. PCB, SL1600 i.c.'s etc.

Ask for details and prices.

ALL OUR PRICES INCLUDE VAT

CREDIT TERMS available. Access and Barclaycards welcome



CATRONICS LTD. (Dept. 184),
 COMMUNICATIONS HOUSE,
 20, WALLINGTON SQUARE,
 WALLINGTON, SURREY SM6 8RG.

Tel. 01-669 6700 (9a.m. to 5.30p.m. Sat. 1p.m.) Closed lunch 12.45-1.45.

Next month in *Pw*

free inside

Practical
wireless

MAY
1981

2m Repeaters

DATA CARD

Channel	Repeater Input (MHz)	Repeater Output (MHz)
R0	145.000	145.600
R1	145.025	145.625
R2	145.050	145.650
R3	145.075	145.675
	145.100	145.700
		145.725

plus supporting article -


USING 2 METRES

Get on 160 metres with the

Pw

'STOUR'

TOP-BAND TRANSCEIVER

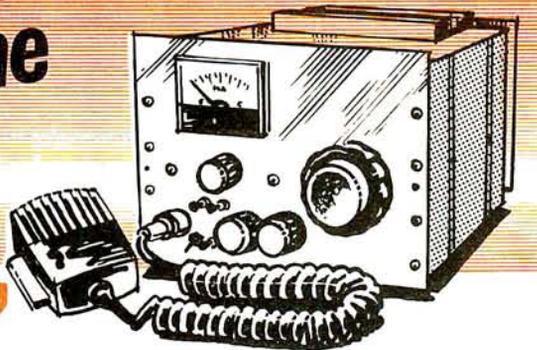



Modular design lets you build and align this rig without need for expensive test gear. Covers sideband and c.w. modes and operates from a 12V d.c. supply

ON SALE
3 APRIL

SUPPRESSING & PROTECTING THYRISTORS

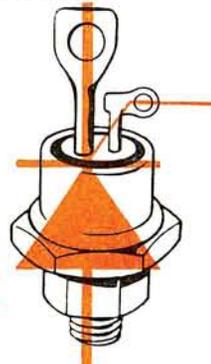The use of thyristors is increasing daily. This series looks at ways of containing the interference which they generate, and of protecting them against destruction



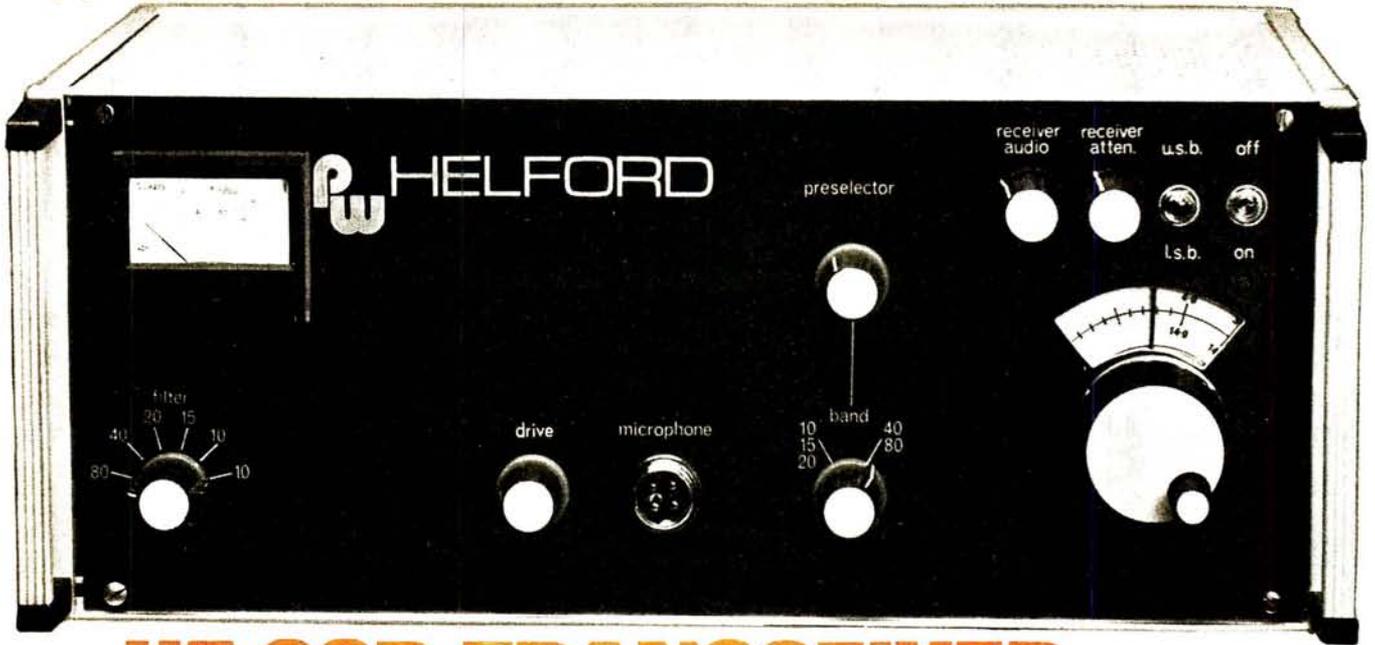

HF SSB TRANSCEIVER

Vic Goom G4AMW

By now you should have the basic radio side of the Helford completed leaving the power supply switching and the main metalwork to finish the project.

The p.a. and driver stage bias regulators were covered in an earlier part and the only remaining power supply circuit is the 6V stabiliser. This is a conventional regulated supply using a 7805 5V regulator chip with the common terminal lifted by 1V to give the required 6V. The circuit diagram of the supply is shown in Fig. 27 and the constructional details in Fig. 29. A heatsink is needed and this is of the finned variety having a thermal resistance of 10°C/W.

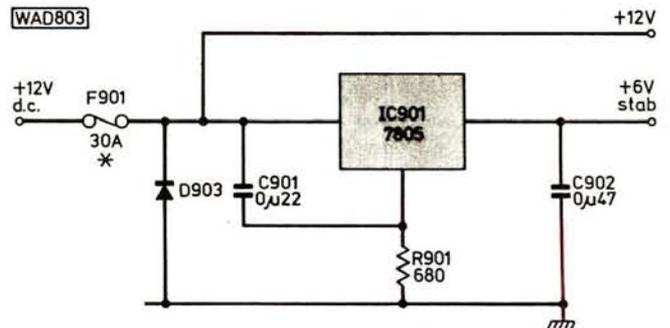


Fig. 27: The circuit diagram of the 6V stabiliser

6V STABILISER

Resistors

$\frac{1}{4}$ W 10%		
680Ω	1	R901

Capacitors

Polyester		
0.22µF	1	C901
0.47µF	1	C902

Semiconductors

Diodes		
1N4148	2	D901,902
See text	1	D903

Integrated Circuits

7805	1	IC901
------	---	-------

Miscellaneous

Heatsink 10°C/W; Printed circuit board; Insulating kit for IC901; Fuse 30A and holder to suit.

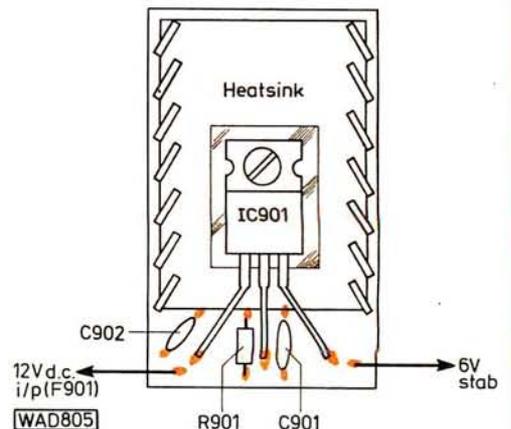


Fig. 28: Full size copper track pattern for the 6V stabiliser board. Fig. 29 (right): Component placement. Components are soldered directly to the copper

Power Supply Switching

The receive/transmit mode of the rig is controlled by switching the d.c. supply rails to the appropriate sections of the circuit and this is carried out by relays operated by the p.t.t. switch. At the same time the antenna is switched to or from the receiver or transmitter. Fig. 30 shows the relay and power supply switching details. The nominal 12V d.c. supply is protected against short-circuits by the protection diode D903. Connections to F, G, H and I in Fig. 30, are made to the appropriate +12V rails on the bias regulators and amplifiers.


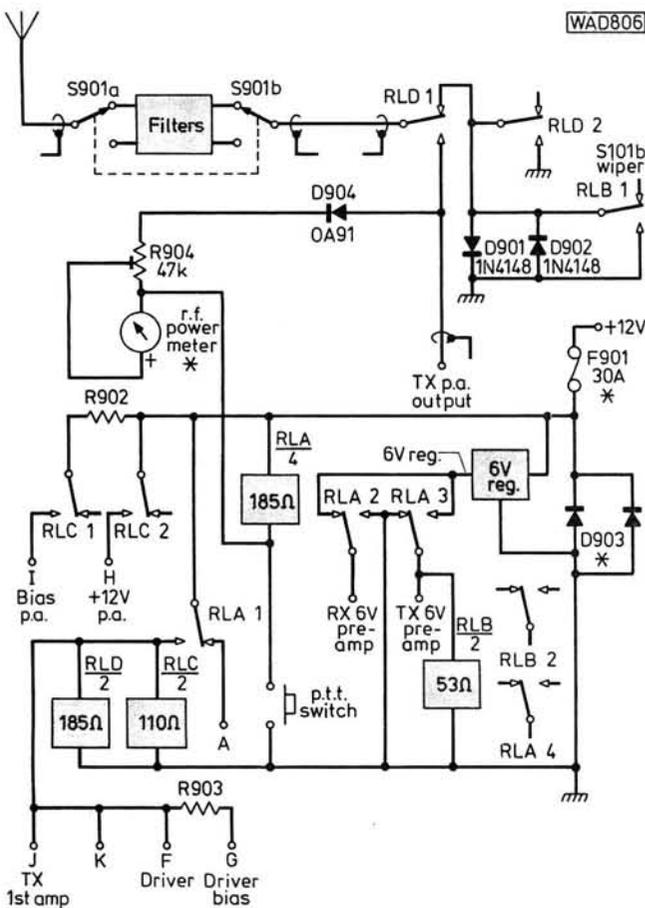


Fig. 30 (above): The circuit for the power switching of the PW Helford. D903 can be a single diode of, say, 50A current rating if available. If not then two 26A diodes may be used. The connection points referred to appear in Fig. 31, except F, G, H and I (see text)

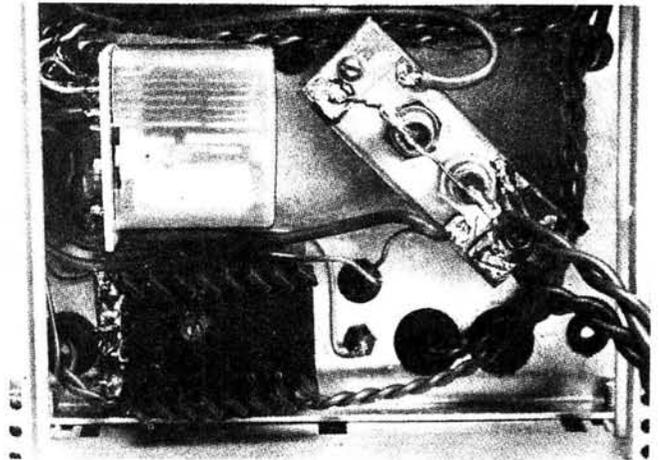

The photograph above shows the 6V stabiliser, relay A and the protection diodes D903


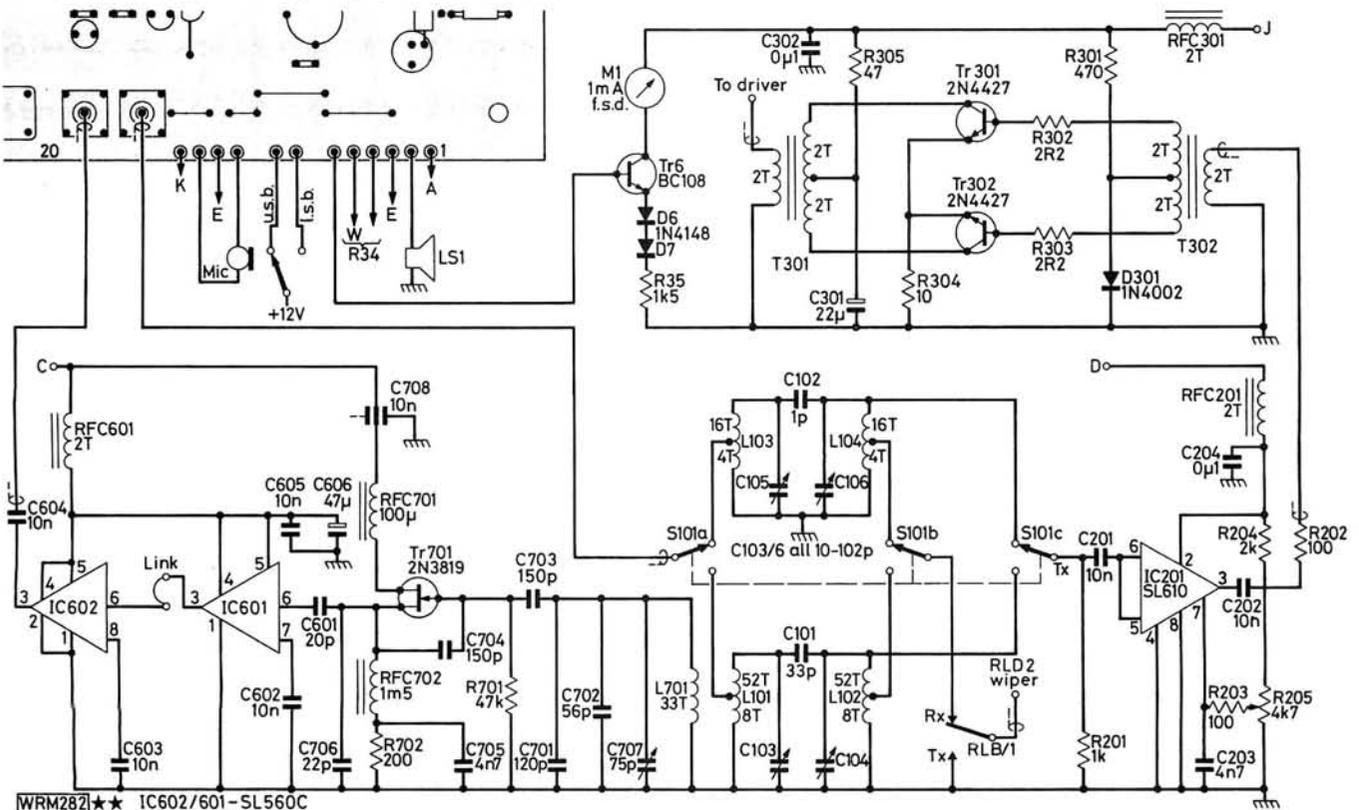


Fig. 31: This is a modified and corrected version of Fig. 5

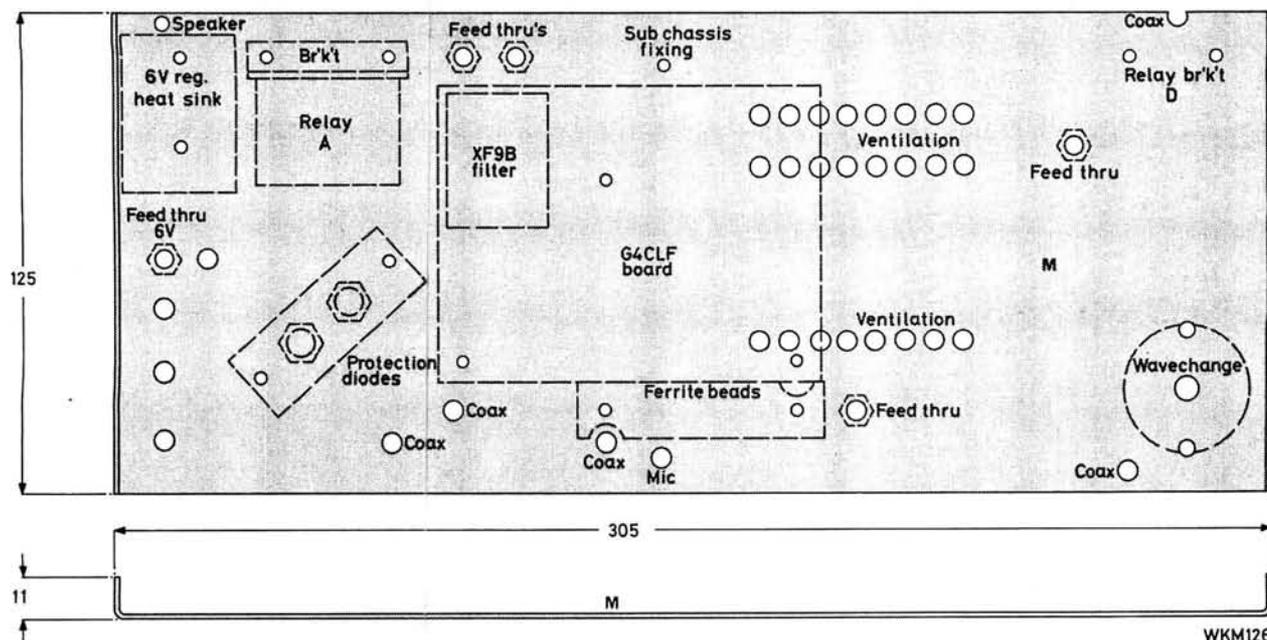

WKM126

Fig. 32: Details of the rear screen of the *PW Helford*. The picture on the left shows this panel


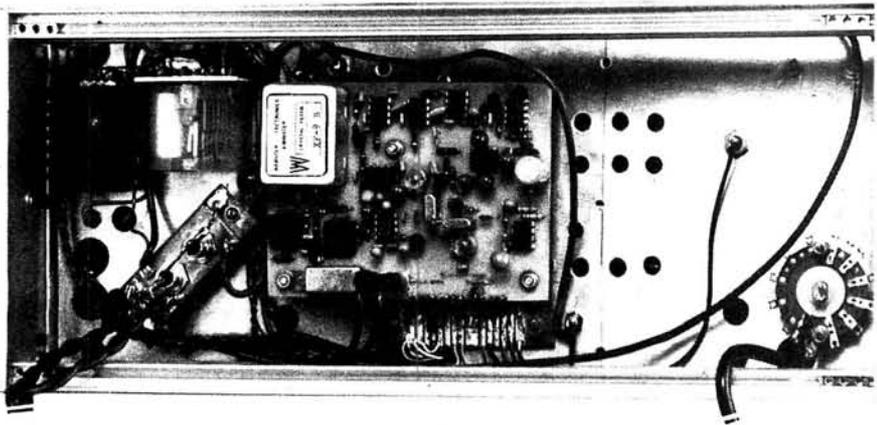


Fig. 33 (below): Exploded view of the various component parts of the *PW Helford* metalwork. These are made from 18 s.w.g. aluminium sheet. Parts H and L are the heatsinks for the two bias regulators

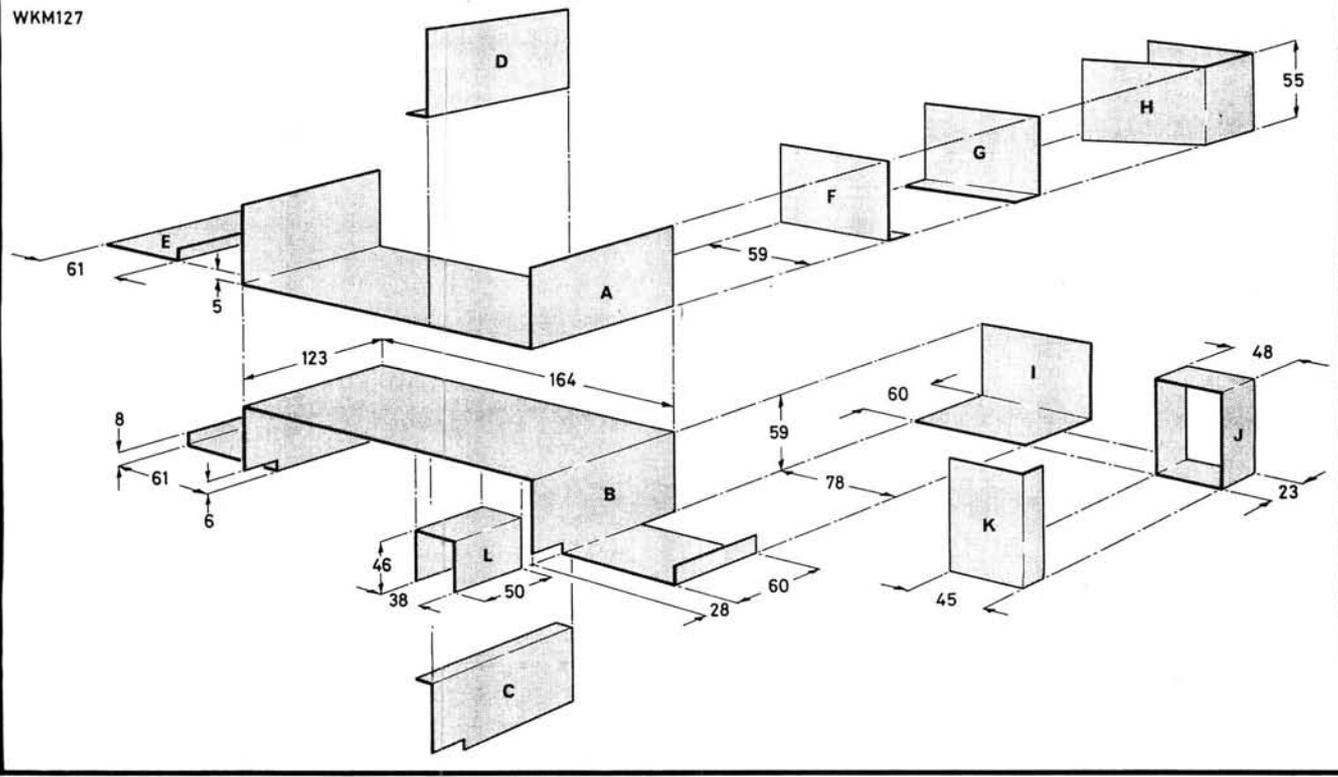

WKM127


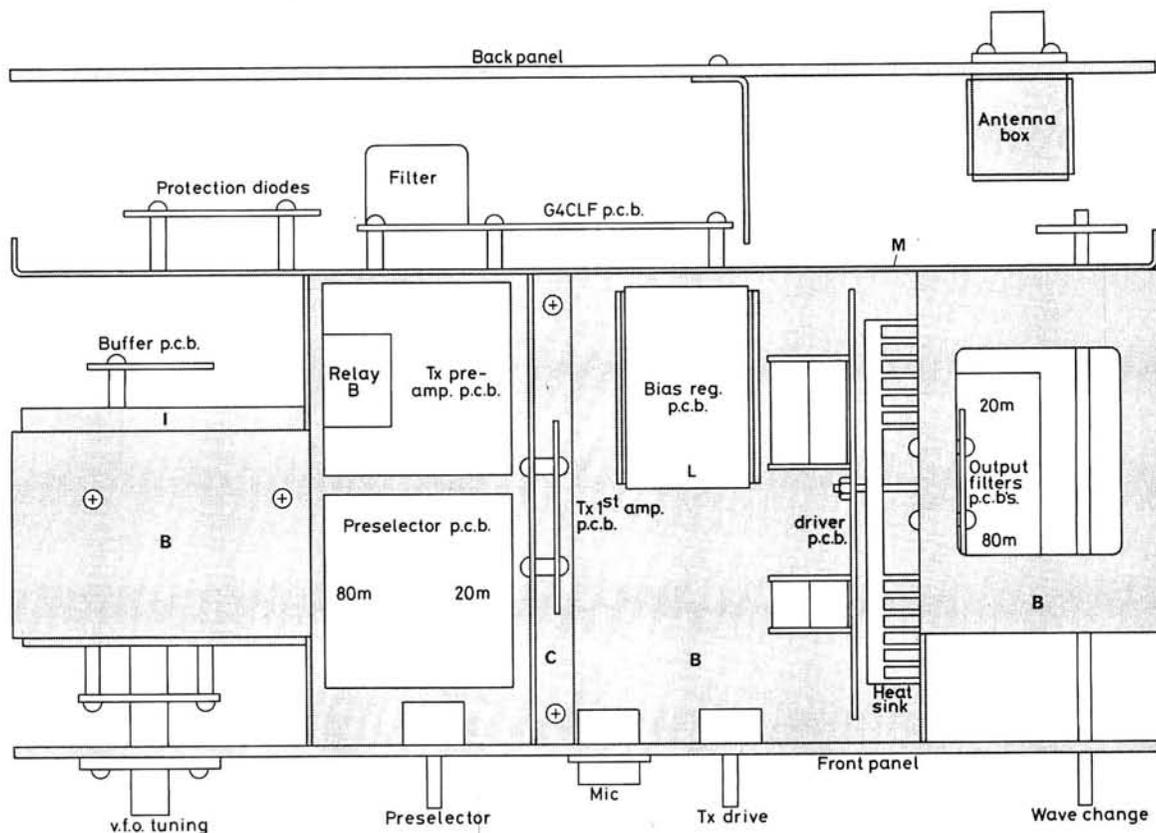


Fig. 34 (above): Underside view of the PW Helford case showing how the various screens and p.c.b.s mount. Fig. 35 (below): Top view of the case

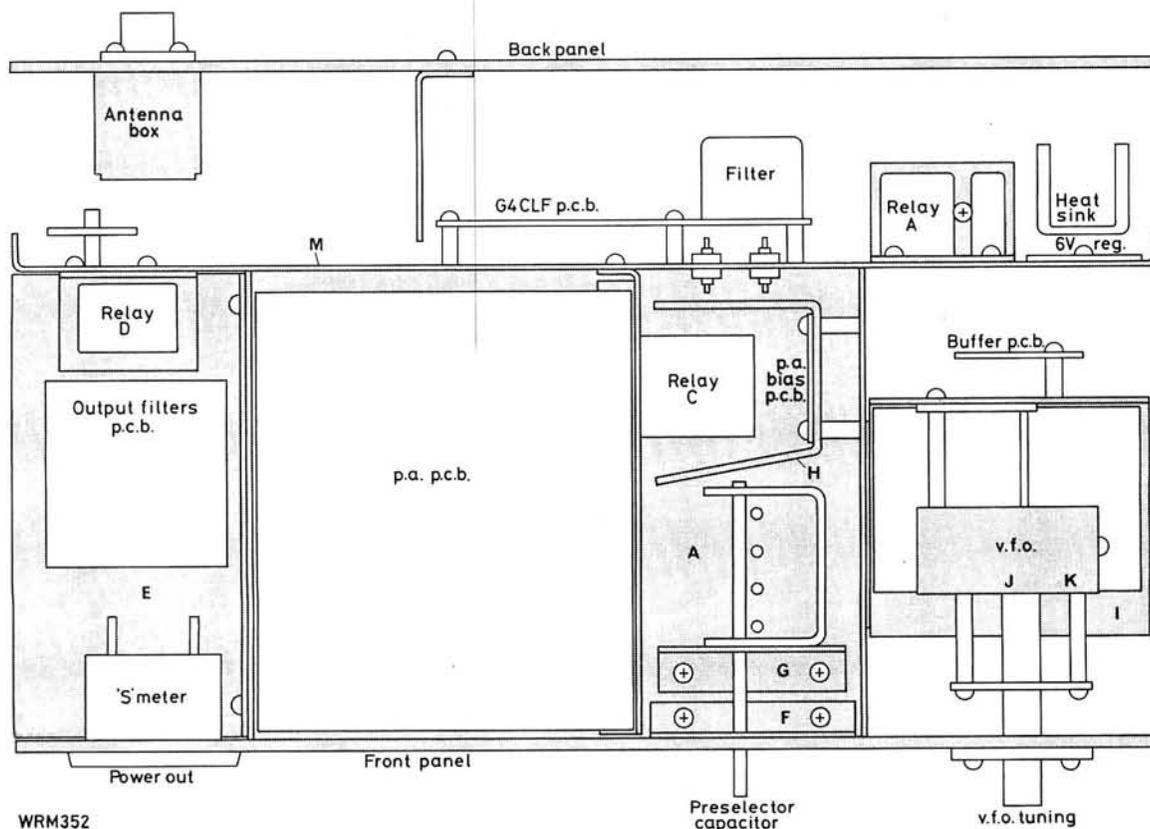

WRM352

Metalwork

The project was designed right from the start to fit into the West Hyde case specified. It is recommended that you stick to this design unless you are satisfied that you know exactly what you are doing and do not expect either the magazine staff or the designers to come to your aid if you run into problems.

The metalwork is built up from 18 s.w.g. sheet aluminium following the drawings given in Figs. 32 to 35. The main sections are screwed to the rails of the case and unless you are really expert at sheet metalwork it pays to make a card replica first to check on the fits. The card patterns can then be used to mark out the aluminium sheet.


Where leads pass through the metal screens, feed-through capacitors are used except in the case of co-axial cables when grommets should be used to prevent chaffing. Check on the fits and clearances around the various p.c.b.s before the final wiring is completed.

In detailing the various metal screens no dimensions have been given for fixing holes for the p.c.b.s, as it is intended that constructors should use the boards themselves as templates to ensure that the fixing holes are correctly placed.

No details are given of the antenna socket screening box as the dimensions for this will depend upon the socket chosen by the constructor. It should be made from aluminium sheet and be screwed to the rear panel to completely encase the rear of the antenna socket.

Relays should be mounted on suitable brackets and again no details have been given as these will vary from relay to relay.

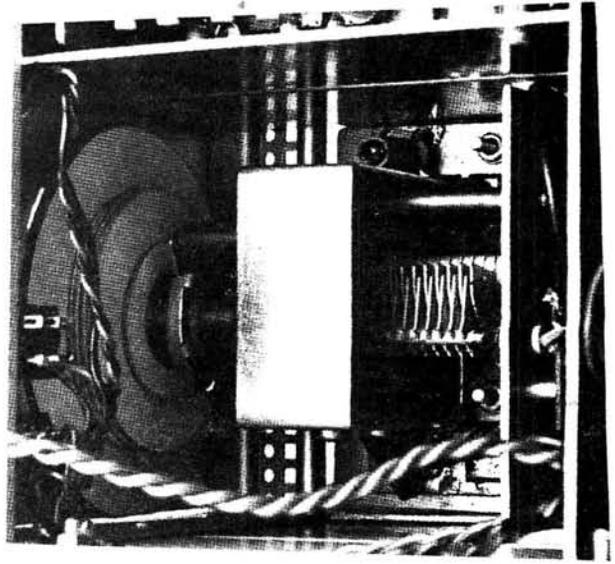
The wave-change switch is long enough to pass through the main screen so as to be able to accommodate future extension of the transceiver. It is advisable to add an extra dummy wafer to the end of the switch behind the main screen to act as an extra bearing for the shaft.



Details of the v.f.o. tuning capacitor mounting bracket (J) together with the dial arrangements

Dial

The dial is made up from layers of card cut into circles and stuck together with double-sided adhesive tape. The dial when complete and marked up is screwed to the flange on the reduction drive. The calibrations should be drawn so as to appear in the window cut-out of the front panel. A transparent film overlay ready calibrated for sticking over the card dial former is available from *PW* Editorial Offices, price 75p including postage.

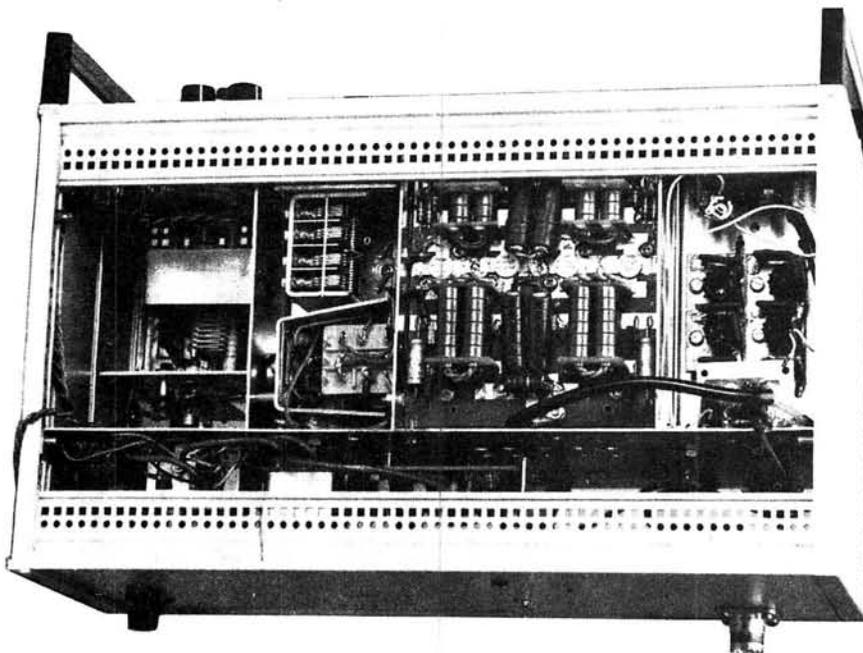

View of the top of the *PW* Helford with the lid removed. The p.a. is central with the preselector capacitor and the v.f.o. to its left. The speaker is mounted on the lid with its magnet fitting into the space above the v.f.o. capacitor

Readers who intend to operate the Helford should be in possession of the appropriate licence issued by the Home Office to those who have passed the City and Guilds Radio Amateurs' Examination. Details may be obtained from: The Home Office, Radio Regulatory Department, Amateur Licensing Section, Waterloo Bridge House, Waterloo Road, London SE1 8UA.

Front Panel

The front panel should be carefully drilled for the switches and other controls and the large cut-out for the meter made. The aperture for the dial must be very carefully cut out and filled to shape. Our prototype front panel was made for us by D. J. Pattle, Juniper, Hillbury Road, Alderholt, Fordingbridge, Hants. For those constructors who wish to make their own front panel a transparent overlay is available from the *PW* Editorial Offices, price £2.00 including postage.

Final Checks


When the final wiring has been finished a complete visual check should be made for possible errors or short-circuits.

All the individual boards should have been checked out before assembly into the case and final setting up can be completed using a suitable dummy load across the antenna socket.

This completes the description of the *PW* Helford as a two-band transceiver. The whole project has been aimed at the advanced constructor to enable him, or her, to build an advanced h.f. transceiver at a reasonable cost.

PW Helford Builders' Net

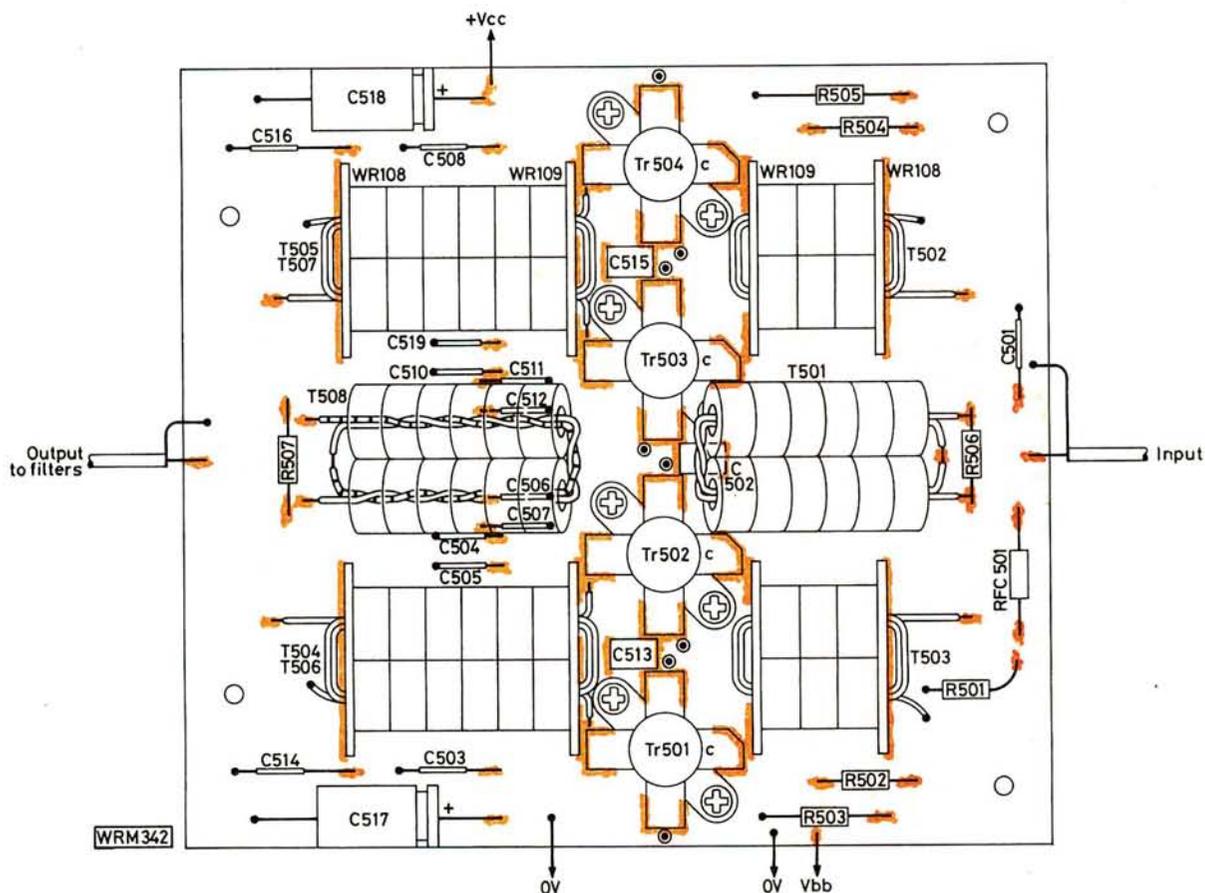The designer, Vic Goom G4AMW, has started a net on 80m for builders and users of the *PW* Helford. The net is held every Monday evening at about 1930 on 3.72±QRM and will be run either by G4AMW or G3XBZ who will be prepared to answer queries and problems.




As readers will no doubt have realised, the printed circuit track pattern in Fig. 23: Component placement drawing (page 43 last month), was printed upside down. We therefore repeat it here, with apologies

Future Developments

The *PW* Helford is proving very popular in its present two band form. The author, along with Phil Ciotti G3XBZ is working on additional boards to add further bands to the rig, and these will be published as soon as they are ready and proven.

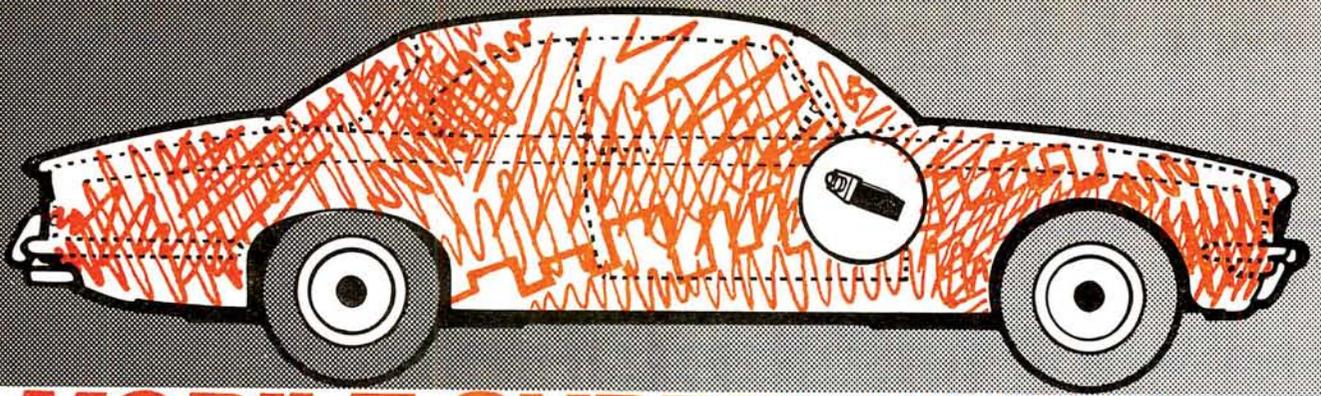Read *Practical Wireless* regularly and you will not miss these exciting developments. ●



MOBILE SUPPRESSION TECHNIQUES PART 1

John M. FELL G8MCP

Have you ever installed an item of radio equipment in a vehicle and experienced the effects of radio interference breakthrough? The chances are reasonably high that you have, as a motor vehicle probably represents one of the most hostile of radio environments. It is the object of this article to provide practical information to enable you to identify and cure this unnecessary annoyance. In general, the techniques of suppression that follow apply equally when dealing with all types of broadcast, p.m.r. and amateur band interference at frequencies of up to 450MHz.

Radio Interference

Before commencing with details of corrective techniques it is useful to establish the nature of the problem. The electrical circuit of a vehicle consists of a number of separate circuits inter-connected by the wiring harness. It is normally possible to identify three main circuits: ignition, generation system and accessories. All are capable of creating noise and transmitting this via the wiring loom. The worst offending items are usually those that are the most inductive.

Radio interference is caused by the rapid change or interruption in the flow of alternating or direct current, which forms the basis of normal operation in many items of a vehicle's electrical equipment. These rapid transitions of current flow create the electromagnetic fields that the installed receiving equipment can detect in the same manner as the wanted signal. This results in varying degrees of noise mixing into the signal with effects ranging from intermittent "thumps" to harsh crackling, preventing worth-while reception.

The classic definition identifies noise as "Any unwanted form of energy tending to interfere with the proper and easy reception of wanted signals."

Transmission Methods

The way in which interference energy is transferred to the equipment is by one or more routes. Those most usually encountered are as follows:

- Radiated emissions from the offending electrical equipment being directly picked up by the receiving antenna.
- Conduction along the vehicle distribution wiring and into the receiver via the power input leads.

- Conduction along the vehicle wiring and subsequent radiation coupling into the antenna.
- Radiated energy, induced into the conductive elements of the vehicle, re-radiating and coupling into the antenna.
- Inadequate screening of the receiver and supply lead de-coupling deficiency, allowing radiation pick-up.

Any attempt at vehicle suppression must embody techniques that will combat all these transmission modes.

Legal Requirement

Standard production vehicles in the UK are only required by law to provide suppression of the ignition system, to prevent interference with domestic radio and television services in the frequency range 40–250MHz. The specified levels of emission and methods of measurement are based on the recommendations of *British Standard Institute 833:1970*. Vehicles produced since the implementation of this legislation, in 1974, must achieve suppression levels as specified and it is a further requirement that the owner must **maintain** the vehicle at this same ex-works standard.



The ability of a vehicle to meet these requirements does not mean that the residual emissions will be at a level that prevents interference breakthrough to the vehicle's own on-board equipment.

Preliminary Checks

Before attempting any work on the suppression of a vehicle, it must be remembered that interference can originate from many external sources and emissions from all of these sources must first be eliminated. Always ensure that the vehicle is positioned in a location well away from fluorescent light fittings, or overhead power transmission lines, as both can produce effects identical in nature to vehicle originated interference.

When investigating broadcast receivers fitted with antenna trimming capacitors check that they can be "peaked" for a maximum signal strength, on a constant level transmission. If a peak cannot be obtained check the antenna and feeder cable for continuity. In the absence of a signal or whilst receiving extremely low-level signals, even an adequately suppressed vehicle can appear noisy.


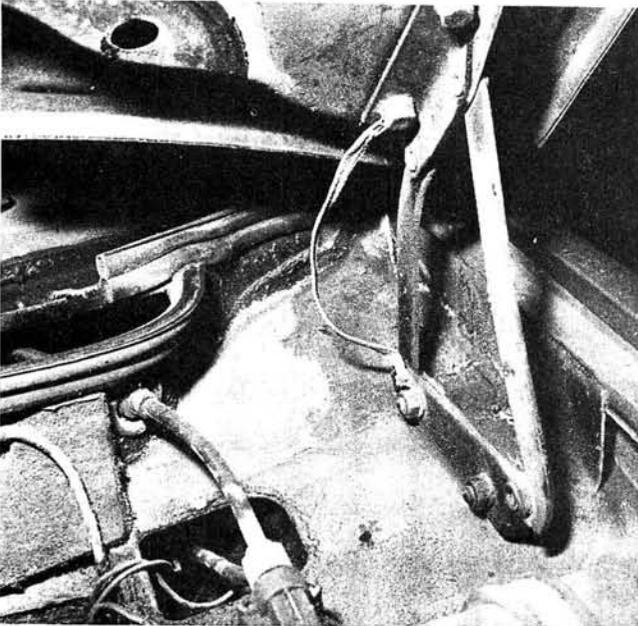


Fig. 1: Additional bonnet bonding strap fitted to an Austin Maxi

At v.h.f. frequencies background noise of a "rushing" nature is an indication of poor signal strength and is not the product of interference. In the same way, when travelling through a built-up area, signal cancellation due to reflections can occur and appear as a noisy signal. In both cases the cure cannot be effected by additional suppression.

Always ensure that the antenna base mounting is bonded to the earthed bodywork at the point at which the feeder cable is connected. Never rely on the outer sheath of the co-axial feeder cable to provide an earth return path for the receiving equipment.

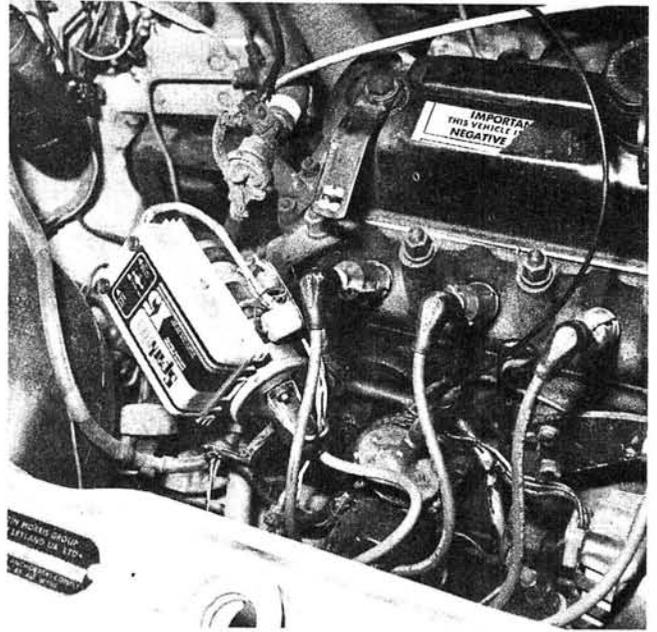Check the earthing security of the receiving equipment, by temporarily applying an earth braiding strap from the case to a known good earth point on the vehicle bodywork. When using straps it is essential to use the shortest possible length of good quality tinned copper braid. (Refer to the test equipment illustrations for the details of a suitable, temporary, "quick-fit" strap.)



If the interference still cannot be reduced to an acceptable level after these initial checks have been completed it is time to consider the vehicle sub-systems in detail. (Refer next to Fig. 5: Further Suppression.)

Ignition Systems

By far the most frequent cause of vehicle interference is the ignition system. In its normal mode of operation, high tension energy propagates through the system, in turn producing wideband impulse noise within the various component parts.

The audible effect of ignition breakthrough consists of a composite crackling noise, varying with engine revs and not dissimilar to the noise produced by a two-stroke trials motorcycle exhaust. The low tension (l.t.) and high tension (h.t.) circuits contribute to the overall effect.

By fitting a $1\mu\text{F}$ capacitor between earth and the switch terminal, marked SW or "+" (but never the CB or "-" terminal), the l.t. side of the ignition may be dismissed. It is good practice to fit this component in any event, otherwise there may be unwanted noise when driving through poor

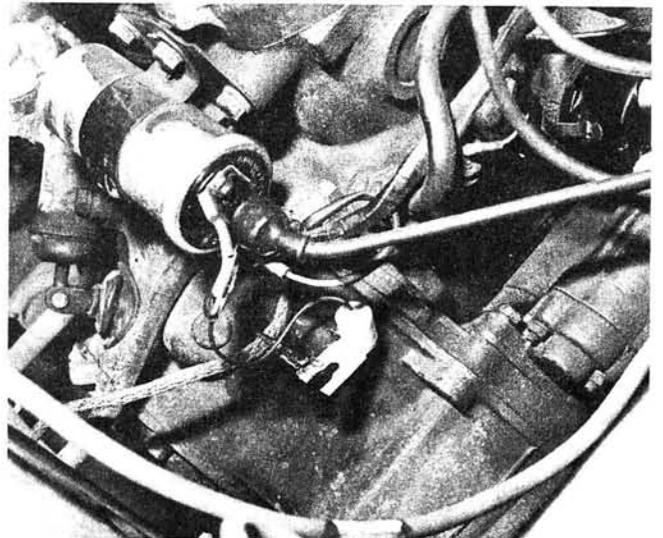


Fig. 2: Temporary quick-fit capacitor connected between the h.t. coil + terminal and earth



signal strength areas. See also suppression of electronic tachometers if interference persists.

The noise created by the h.t. side of the ignition system is at a higher frequency, sharp and spiky in nature and also varying with changes in engine revolutions. Referring to Fig. 5, the initial checks refer mainly to defects created during assembly of the vehicle and are relatively easy to locate and rectify.

Metallic bodywork plays a vital part in screening unwanted emissions from the ignition system. It is essential that all of the bodywork is at a common "earthy" potential, to obtain the best shielding effect. This also includes the engine bonnet which is often found to have been insulated by paint or rust at the hinge points. In persistent cases of interference other items that have been found to re-radiate ignition pulses and that should also be bonded to earth are: the radiator, rocker box cover, air cleaners, and in fact any items in close proximity to the h.t. system that are not earthed.

Once again, in all cases, when bonding to earth use good quality braided conductor straps of the shortest possible length.

Having now eliminated the initial stages it is necessary to turn to the "active" components of the h.t. system.

HT Leads

It is most probable that at some time you have been advised to dispose of all the "carbon impregnated string" or resistive h.t. cable as it is known in the trade, and replace it with "good quality" solid-cored cable with resistive plug cap suppressors.

This course of action not only degrades the suppression of the vehicle above 30MHz, it could render you liable to prosecution under the relevant legislation, as the vehicle may no longer possess the designed degree of suppression provided by the manufacturer at frequencies above 40MHz. Folklore has evolved around resistive h.t. cables and it is wrongly assumed that the higher levels of resistance encountered will reduce the effectiveness of the ignition spark. Initially, resistive carbon h.t. leads required replacement at 18 month intervals to maintain their effectiveness. Leads produced since 1978 have a manufacturers' recommended lifetime of 100 000 miles. The

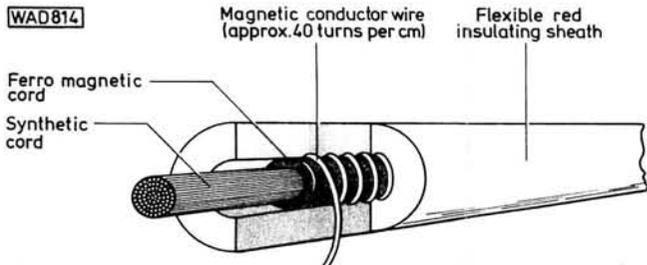


Fig. 3: Cross-sectional view of Sparkrite ferro-inductive h.t. lead

breakdown resistance at the plug points is many orders of magnitude greater than all "in circuit" suppression devices added together.

In suppression terms, copper core h.t. cable, used in conjunction with carbon composition plug caps, behave as lumped constants, useful only at the lower frequencies. At higher frequencies, where the filtering action has little effect, the physical length of the cables approaches that of the received frequency wavelengths and they can, in fact, start to act as individual antennas.

Resistive carbon impregnated leads, on the other hand, possess a distributed capacitance which allows them to act as an RC filter network whose effective suppression increases with rising frequency. Fig. 10, in Part 2, indicates the effectiveness of the various suppression elements across the operating bandwidth.

Many imported vehicles of continental manufacture are fitted with inductively wound h.t. cable which is very effective at v.h.f. frequencies and above, but suppression at low frequencies falls to a very low level. To cure ignition breakthrough in these cases, it will be necessary to fit

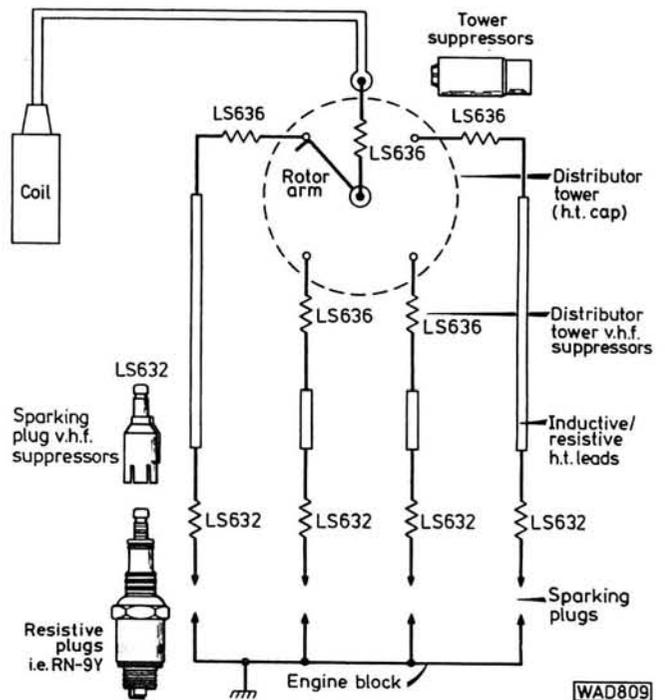


Fig. 4: Block diagram of a fully suppressed h.t. distribution system

additional "in-line" resistive elements. Perhaps a cheaper method would be to replace with carbon impregnated or inductively cored ferrite composition leads such as the Sparkrite type.

In-Line HT Suppression

If ignition interference is still evident at v.h.f. frequencies it will be necessary to fit further "in-line" elements. Start by fitting Lucas LS636 type distributor suppressors to each of the h.t. lead outlets on the distributor cap. Angled versions of the same device are available if space is limited.

This should further reduce the noise breakthrough but if this is still not sufficient, fit an earthed screening can around the distributor cap. It is not necessary to completely enclose the cap, but the swept plane of the rotor

Whether you are: just starting, taking an R.A.E. course, just licensed, or an old timer, SMC has something for you. . . . And at our **LOWEST** ever prices.

Advertised **PRICES** on this page **INCLUDE VAT** at 15%, **INCLUDE SECURICOR** speedy delivery and **INCLUDE A TWO YEAR WARRANTY** (remember as Yaesu Musen UK distributors our guarantee is **FACTORY BACKED**).

We take **ACCESS AND BARCLAYCARD OVER THE PHONE**, offer attractive **HP** (including a **FREE FINANCE SCHEME** on many regular priced items) on application, and have branches and agents conveniently situated across the country plus the biggest mail order department right in Totton. Whatever your requirements SMC . . . your single stop service.



FT/FP200 £345

10-80m. SSB, CW, 240W PIP. Premix VFO. C/W FP200 AC PSU/Speaker.



FRG7700

- ★ 150kHz-30MHz no gaps
- ★ SSB-CW-AM and FM
- ★ Up-conversion no preselector
- ★ 12 channel memory option
- ★ Mains and 12 volts dc option
- ★ Clock/timer built-in

From 30MHz to 150KHz (lower at reduced spec.) in 1MHz bands. SSB, CW, AM, FM. On 10m and with a convertor the NBFM detector with squelch plus a noise blanker opens new horizons.

4 filters fitted as standard! SSB, 2.7KHz and FM 15KHz. For AM, 3 positions! Narrow 2.7KHz, Medium 6KHz and Wide 12KHz, with tone control, and switchable AGC.

No preselectors! Up conversion with a 48MHz crystal filtered IF plus dual PLL system provides automatic selection of the input bandpass filter direct from the band selector or memory.

The inbuilt quartz clock/programmable timer has battery back-up.

12 frequencies anywhere within the range may be stored by simply touching the M button, no preselector adjustment, no range switch adjustment. The memory is tunable by ± 1 KHz and is kept alive year long by 3'AA' dry cells.

FRG7700 £309 FRG7700M £389



★ FT901DM(i) £715
★ FT901DE(i) £645
★ FT901D(i) £655

FT902DM £799

10-160m. SSB, CW, AM, FM, 9 bands (DE version £713 D version £724)



★ FT101ZD(i) £515
★ FT101Z(i) £445

FT101ZD £569

10-160m. SSB, CW, AM, Digital 9 bands model. (Analogue version £488.00)



FRG7 £199

0.5-30MHz General Coverage Receiver. 230V AC. 12V DC. Battery pack. AM/SSB.

PRICES INCLUDE VAT @ 15%



FRG7000 £259

0.25-30MHz General Coverage Receiver. 230V AC. AM/SSB Timer, AM/SSB.

FREE SECURICOR DELIVERY



★ FT107M(i) £625

FT107M £690

160-10m 2 Aux. SSB, CW, FSK, AM. Memory option. Deluxe 9 band model.

2 YEAR DISTRIBUTOR WARRANTY



SOUTH MIDLANDS COMMUNICATIONS LIMITED

S. M. HOUSE, OSBORNE ROAD, TOTTON, SOUTHAMPTON, SO4 4DN, ENGLAND
Tel: Totton (0703) 867333, Telex: 477351 SMCOMM G, Telegram: "Aerial" Southampton

S.M.C. Agents

G3UL Stourbridge (03843) 5917
GMBGC Edinburgh (031665) 2420
G13WVY Trandree (0762) 840656
G13KDR Bangor (0247) 55162
GW3TMP Pontybodkin (035287) 846/324
GW8EBB Swansea (0792) 872525
GJ4ICD St. Saviour (0534) 26788

S.M.C. (Leeds) BRANCH

LEEDS.
Colin Thomas, G3PSM
257 Otley Road,
Leeds 16, Yorkshire.
Leeds (0532) 782326
9-5.30 Monday-Saturday

S.M.C. (Jack Tweedy) LTD

CHESTERFIELD.
Roger Baines, G3YBO
79 Chatsworth Road,
Chesterfield, Derbyshire
Chesterfield (0246) 34982
9-6: Tuesday-Saturday

S.M.C. (Jack Tweedy) LTD

WOODHALL-SPA,
Jack Tweedy, G3ZY
150 Horncastle Road,
Woodhall Spa, Lincolnshire
Woodhall Spa (0526) 52793
9-5: Tues-Sat (- appointments)

Further Suppression – Ignition systems


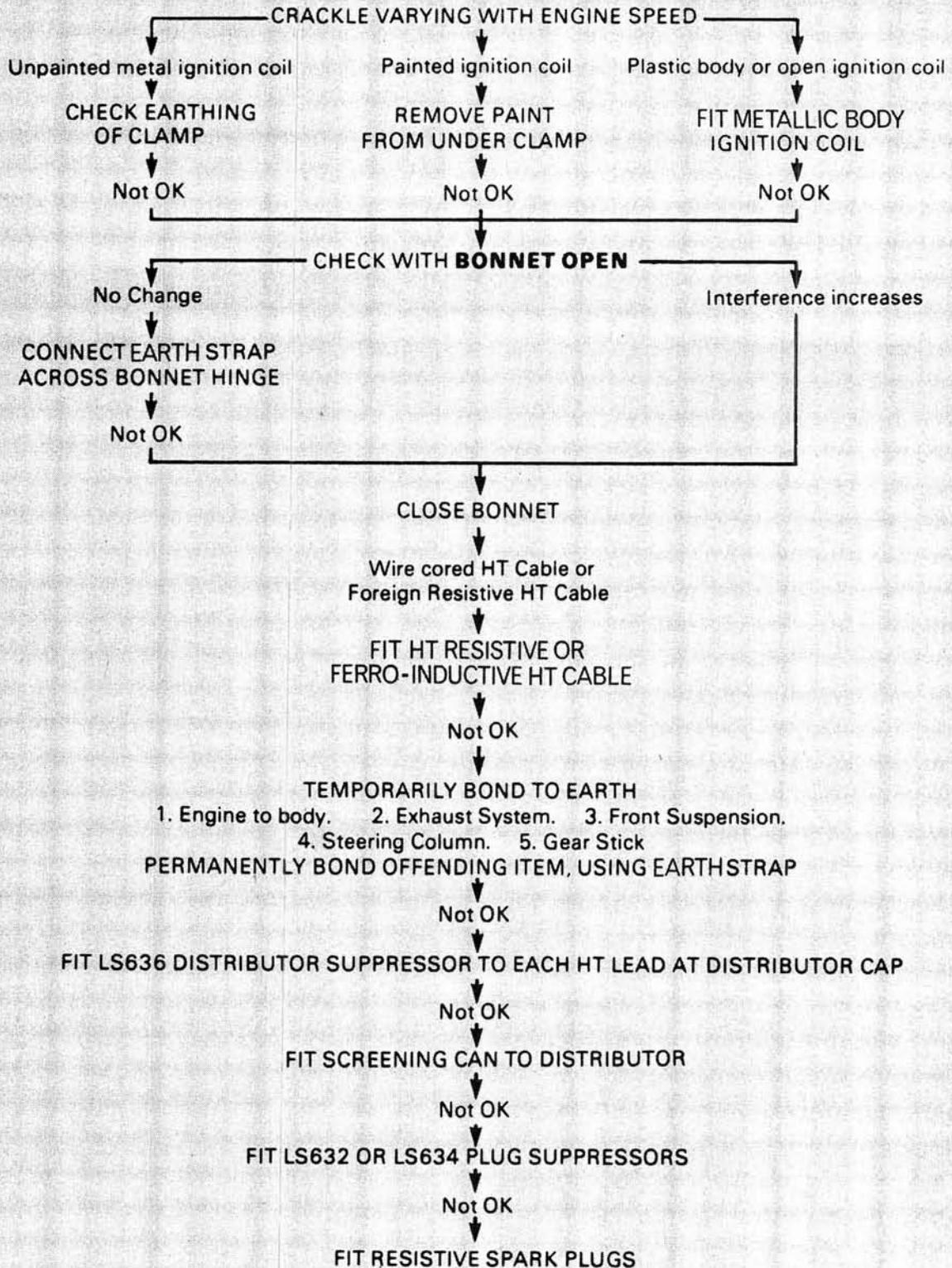


Fig. 5: Flow chart detailing the complete path of h.t. suppression

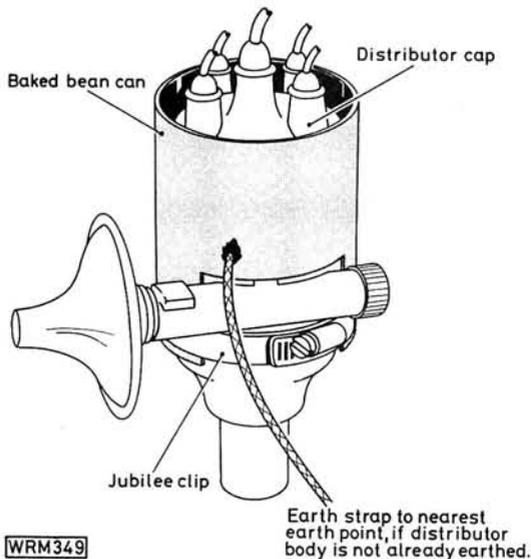

WRM349


Fig. 6: DIY distributor cap screen. The area screened needs only to cover the plane of the rotor arm

arm must be surrounded by the shield. Fig. 6 shows the construction of a suitable screening device.

Having progressed down the ignition distribution system, the final element in the system and the point at which the h.t. energy is discharged, is at the spark plug. Normal plug caps are made from Bakelite or rubber materials, the latter containing only a spring clip connector. To further reduce the noise level on weak signals at v.h.f. frequencies, the use of a metallic screened plug cap suppressor is recommended. This unit is available in straight or right-angled format and incorporates an in-line inductive resistor within the body shell.

Finally, if noise still remains on low level v.h.f. signals, a special resistive spark plug is available to directly replace most equivalent standard plug ranges. Suppressed plug variants are recognisable by the prefix R in the serial number. For example, the common Champion N9Y would be specified as RN9Y.

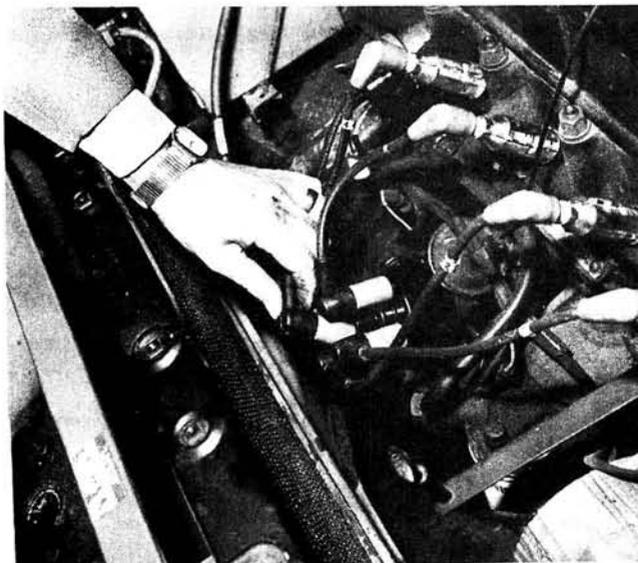Before the ignition system is finished with, it is worthwhile considering the feed to the electronic tachometer, if fitted. The pulse input for this device is normally obtained from the terminal marked CB or "+" on the h.t. coil. As




the cable passes from the electrically noisy area of the engine compartment, through the bulkhead screen, into the interior of the vehicle, it is good practice to fit a 3A in-line choke close to the coil terminal.

Capacitor Discharge Systems—Warning

Before fitting suppression components to the l.t. side of vehicles equipped with electronic ignition, always check the manufacturer's recommendations. Inserting a suppression capacitor between the output lead of such units and earth can cause damage to the drive circuit and destroy the suppressor, due to applied over-voltage.

Charging Systems

The vehicle battery charging system is often found to be a cause of interference. Depending on the age of your vehicle the prime mover in the system will be either a d.c. generator (dynamo), or an alternator, which has an a.c. output that is subsequently rectified by semiconductor diodes.

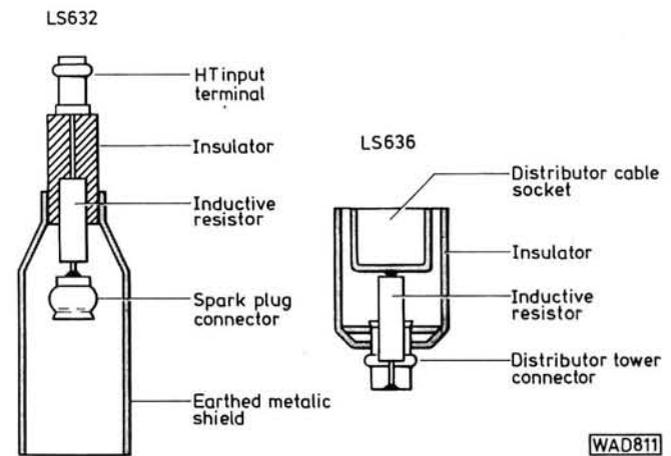


WAD811

Fig. 7: Cross-sectional view of "in-line" distributor tower and metallic screened plug-cap suppressors

Suppression techniques are similar for both devices, the audible effect produced being recognised as a whine that varies in intensity with variation in engine speed.

Dynamo

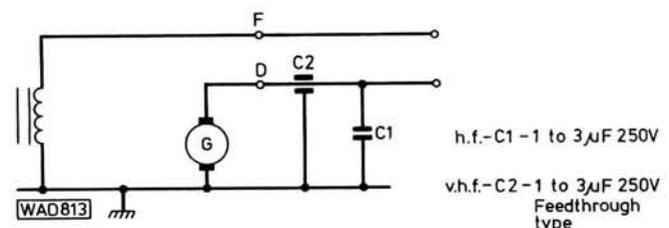For suppression within the h.f. bands up to 30MHz, either a single 1 μ F or 3 μ F capacitor must be fitted to the "D" or output terminal of the dynamo. As the received



h.f.-C1 - 1 to 3 μ F 250V

v.h.f.-C2 - 1 to 3 μ F 250V
Feedthrough type

Fig. 8: Dynamo suppression methods

Suppression Range

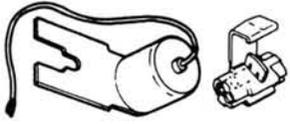
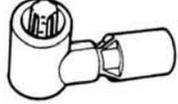
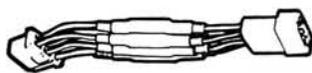
	LS No.	Part No.	Description		LS No.	Part No.	Description
	LS627	60600385	1 μF Capacitor with connector, for Ignition		LS642	60670350	General Purpose Bonding Strap
	LS628	60600386	1 μF Capacitor with connector, for Generator		LS646	60460665	Inline Resistor for Wire HT Cables
	LS720	60460741	3 μF Capacitor with connector, for Generator				
	LS629	54200297	3 μF Capacitor for internal mounting on 15-16-17-18 ACR Alternators		LS648	60460666	Right Angled Plug Suppressor, with shroud
	LS630	60460085	Inline Choke		LS673	54200423	3 μF Capacitor for internal mounting on 23-25 ACR Alternators.
	LS632	54421964	Straight VHF Plug Suppressor		LS680	78139	1 μF Capacitor with Dual Connectors
	LS634	54422760	Right Angled VHF Plug Suppressor		LS682	54201329	3 μF Capacitor for internal mounting on 20 ACR Alternators
	LS636	54421441	Straight VHF Distributor Suppressor		LS721	60946618	8 A Line Filter Insulated case
	LS638	54423567	Right Angled Distributor Suppressor				
	LS639	60150093	7 A Inline Choke		LS684	60150114	Dynamo Feed through Capacitor
	LS640	60150094	3 A Inline Choke				
	LS641	60670378	7 A Choke Assembly for 14-15-16W Wiper Motors				

Fig. 9: The Lucas Audio Systems range of suppression components

frequency increases, the suppression effect will decrease, so short lead lengths are essential to maximise the effects. In the range 30–150MHz an additional feed-through type capacitor must be used. Associated with the dynamo system is the separate voltage regulator control box which can cause constant level whine or crackle. This can be cured by connecting a 1μF capacitor from the “D” terminal to earth, or in persistent cases by fitting a line filter (normally available from the dynamo manufacturer).

Alternator

Interference from the alternator system usually only extends over the h.f. frequency bands up to 30MHz.

The characteristic noise produced by an alternator is like that of a dentist’s drill and is very distinctive. Again the cure is to fit a 3μF capacitor within the body of the device from the output terminal to earth.

In the concluding part of this article next month, detailed information is given to enable suppression of the remaining electrical equipment and accessories

THE PW 'WINTON' Stereo Tuner

Part 1

* E. A. RULE

The PW Winton Tuner is intended for the more experienced constructor who would like to build a top quality tuner with a specification equal to the best commercial designs available, but at a cost within a sensible domestic budget.

The tuner covers the u.h.f. TV band as well as the normal a.m. and v.h.f. f.m. bands, it also has a limited coverage of the s.w. band. Each tuner section uses the latest techniques available making it suitable for the home constructor who may not have access to sophisticated test equipment.

This may seem a large and complex project, but providing the constructor can solder properly and follow the step-by-step instructions he should be able to produce a tuner equal to those available commercially at much higher prices. Take each section in turn and look upon it as a complete project in its own right, in other words do not treat it as one mammoth project but as a series of smaller ones. Take your time over the various sections, by not rushing, mistakes can be avoided.

The full circuit details are shown in Figs. 1, 2, 3 and 4, with a simplified block and inter-wiring diagram in Fig. 5. These should be referred to as required while reading the general circuit description.

On the front panel the tuner has controls for MANUAL TUNING and DISPLAY FUNCTION, with 13 push-buttons for selecting (from left-to-right): LW, MW, SW, FM, TV, MUTE, AFC, B-W (filter bandwidth selectivity) MANUAL TUNE, and then four pre-set stations which are used in conjunction with the eight pre-set potentiometers to the right of the push-buttons. To the right of the main DISPLAY FUNCTION switch there are four push-buttons which control the various clock functions, i.e., hours set, minutes set, etc. The STAND-BY toggle switch is in the top left-hand part of the panel and to its right is the stereo l.e.d. beacon, to the right of this are two meters, the first indicates the signal strength on all bands and the other indicates the correct tuning point on f.m. and TV. The main digital fluorescent display is to the right of the meters.

The rear panel of the tuner has antenna sockets for a.m., f.m., TV and a DIN socket for audio output. The ferrite antenna rod and mains fuse-holder are also mounted on the rear panel.

Circuit Description


The f.m. r.f. section is one of the most important parts of any hi-fi tuner system. If the signal is degraded at this point there is nothing that can be done at a later stage to put things right. Received signals can vary in strength from a few microvolts to several hundreds of millivolts when close to a transmitter. The weaker signals must be amplified, without adding any noise or distortion, to a suitable level for the mixer stage, and very strong signals may need to be reduced in level to prevent overload of the mixer.

In practice a range of signals of from one microvolt to around 0.1V could be encountered and this represents a range of 100 000:1 (100dB). Should the r.f. section fail to handle this range of signals then cross-modulation and other undesirable effects could take place. Also, under practical conditions, there would be more than one signal present at any time and the r.f. section has to select the wanted signal and reject all others, so a high degree of r.f. selectivity is also an important requirement. In general the more tuned circuits before the mixer stage the better the rejection of unwanted signals.

The selected signal is mixed with a local oscillator and the difference between the two (10.7MHz) is the i.f. or intermediate frequency required. All further amplification and processing is carried out at this frequency. As the i.f. amplifier has a narrow bandwidth (approximately 250kHz), to provide good adjacent-channel selectivity the local oscillator must be very stable in frequency, otherwise the resulting i.f. signal would drift out of the i.f. passband and distortion of the signal would result. For the Winton Tuner it was decided to use a commercial r.f. unit in each section. ALPS Electric Co., of Japan specialise in producing top quality r.f. units for many leading hi-fi manufacturers in Japan, although they are not so well-known in the UK. The unit decided upon for f.m. was the FD811U, this uses a dual-gate MOSFET in the r.f. amplifier, and also a dual gate MOSFET in the mixer stage. The input signal from the antenna is passed through a single-tuned circuit to gate 1 of the r.f. amplifier and automatic gain control voltage applied to gate 2. The signal then passes through four




* T&T Electronics

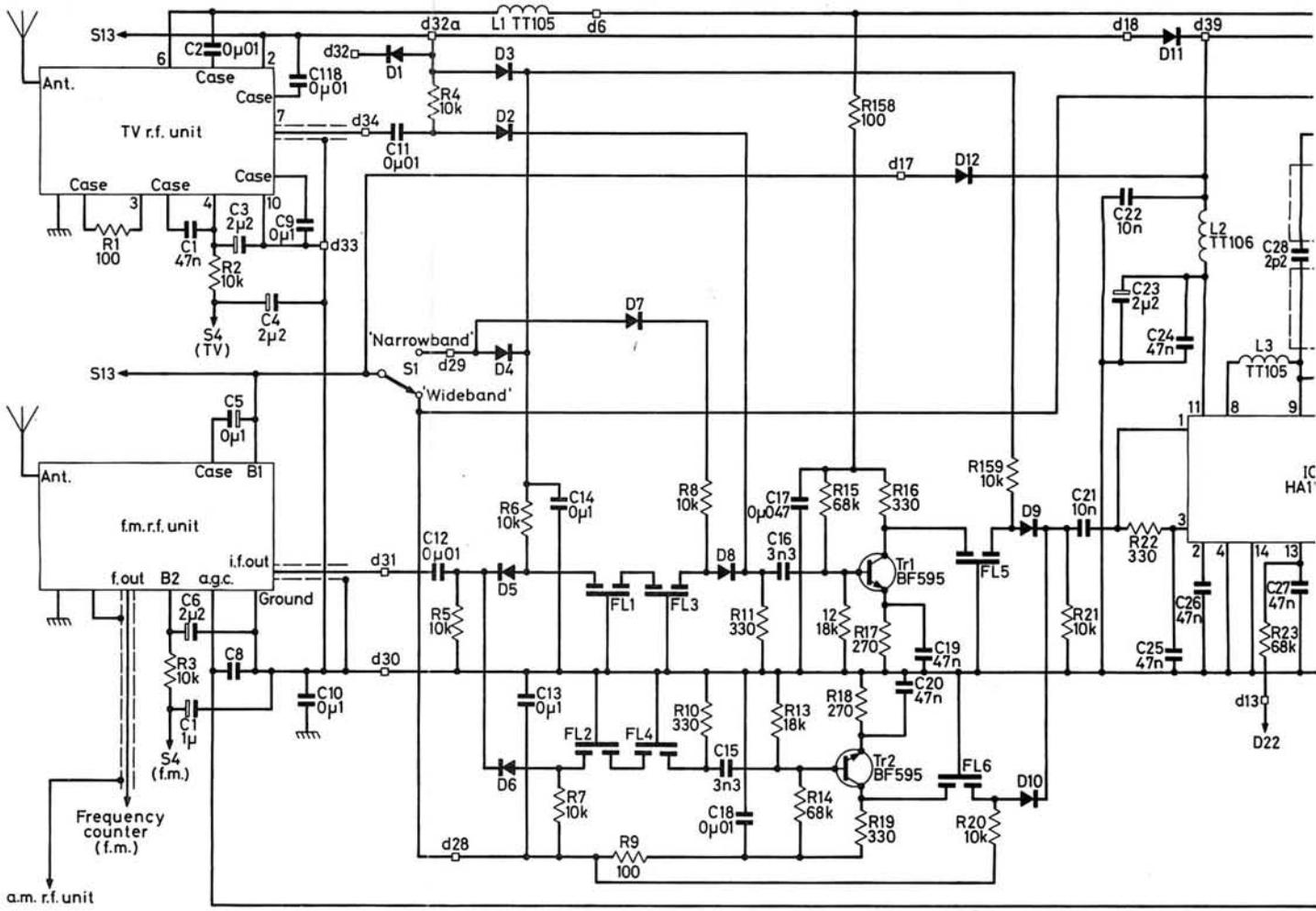

WRM345

FL1 to FL6-10.7MHz.
All diodes 1N4148 unless otherwise stated.

ont

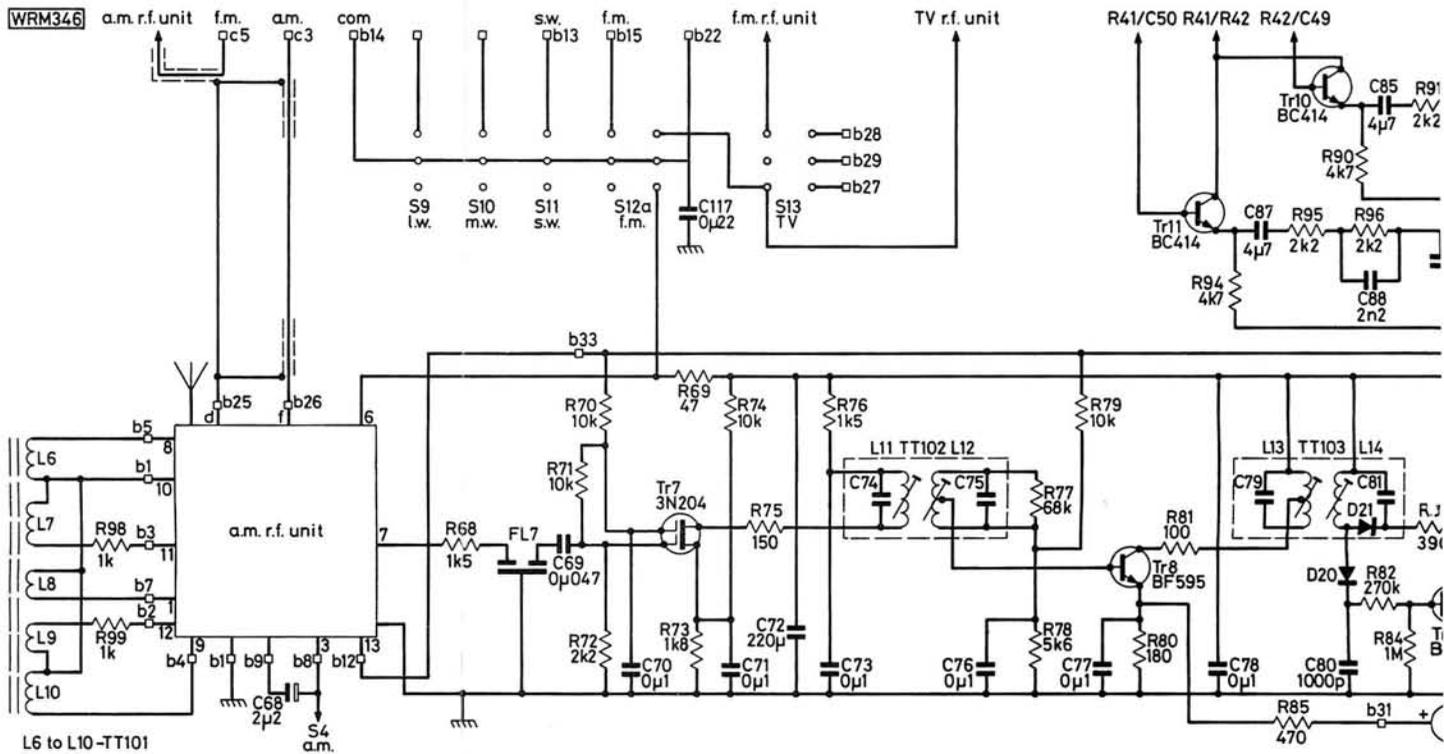

WRM346

L6 to L10-TT101

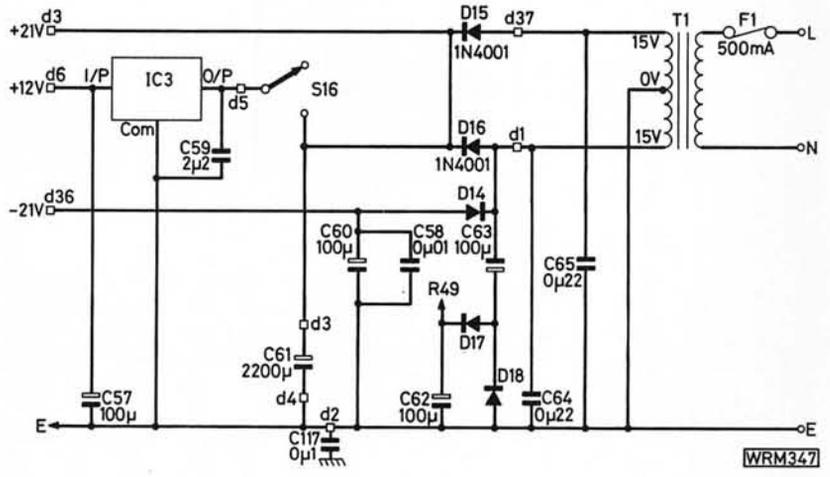
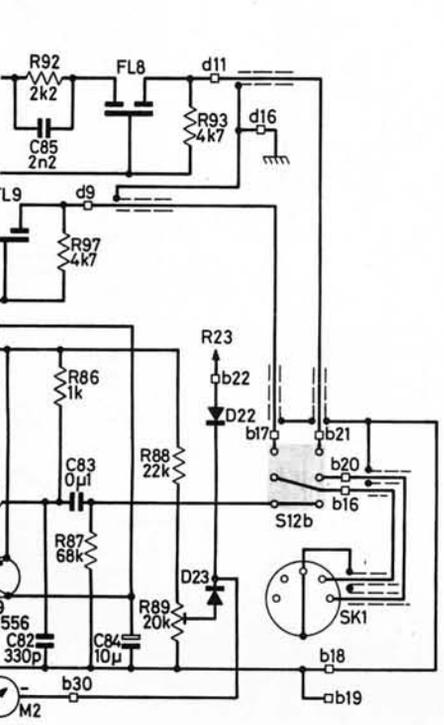
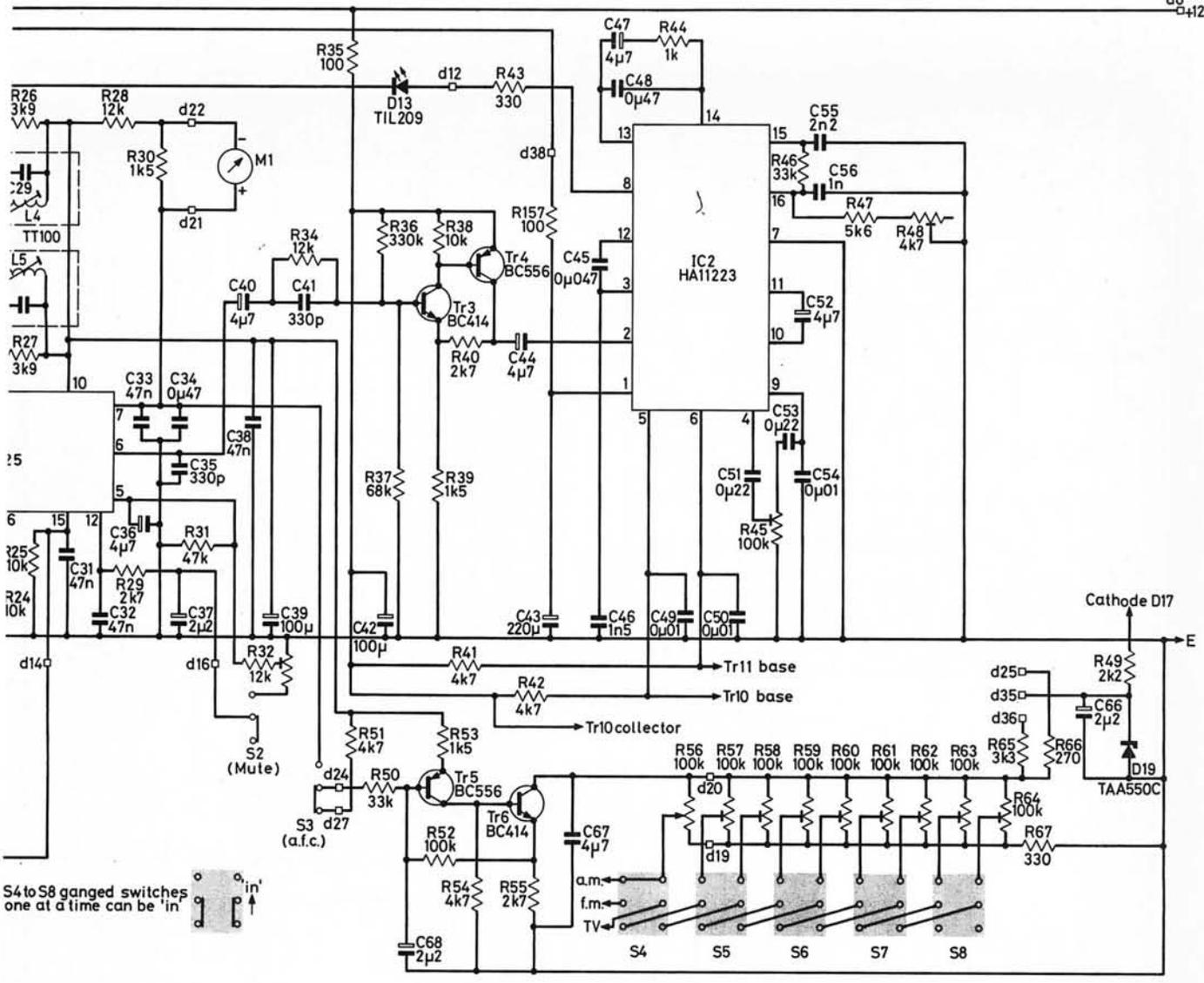


Fig. 1 (top): Circuit diagram of f.m. and TV sections of the PW Winton Tuner

Fig. 2 (left): Circuit diagram of a.m. section

Fig. 3 (above): Circuit diagram for PW Winton power supply

bandpass-tuned circuits to gate 1 of the mixer with the oscillator injection on gate 2. To generate the local oscillator signal a transistor is used, followed by a two-stage buffer amplifier which also has a buffered output for feeding into the digital frequency counter. The i.f. signal from the mixer stage passes through another bandpass filter to a single-gate f.e.t. i.f. amplifier stage.

The result of this excellent design is an r.f. section that can handle the very wide range of signal strengths encountered in practice, and can select only the wanted signal out of the many presented to it. The image and spurious signal rejection is over 120dB, the advantage of this high rejection figure is that a high-gain aerial may be used to enable weak signals to be received without the danger of cross-modulation from strong local signals. As all the tuned circuits are varicap tuned this unit also allows pre-set station selection.

The IF Amplifier

The main task of the i.f. amplifier in an f.m. tuner is to provide selectivity, to remove unwanted impulse noise and any other amplitude modulation (a.m.) on the signal. This section also detects the frequency modulated signal and converts it to audio, provides automatic gain control voltages for the r.f. amplifier and also control voltages for automatic frequency control.

In the Winton Tuner the signal from the r.f. unit which is now at the i.f. of 10.7MHz is passed via diode switching circuits to either the wide-band (stereo) or narrow-band (mono) filters. These filters both use a double ceramic filter followed by a transistor amplifier and then another ceramic filter. The output from this section is then passed via a diode switch to the Hitachi HA11225, IC1.

The HA11225 is the latest development in f.m. i.f. integrated circuits, and is similar in many ways to the popular CA3089 family. However, it has a specification that puts it right at the top as far as overall performance goes. For example, it is possible to obtain a recovered audio signal with distortion as low as 0.03 per cent or better, and to achieve this with a signal-to-noise ratio of around 84dB. Compared with the old CA3089 with figures of around 1 per cent distortion and signal-to-noise ratios of 68dB the improvement is quite considerable. The HA11225 also has much better muting circuits, and for this project was considered the best i.c. for use in the Winton Tuner.

The HA11225 has a quadrature detector and by using a double-tuned discriminator circuit (L4, L5) the full benefit of its low distortion is realised. The i.c. provides a delayed a.g.c. voltage for the ALPS tuner unit as well as providing a voltage for a.f.c. The a.f.c. voltage is amplified by transistors Tr5 and Tr6 before being applied to the varicap diode tuning circuits. The recovered audio signal is passed on to the stereo decoder which uses a Hitachi HA11223, (IC2). Two meters are also driven by the HA11225, one for signal strength and the other for a centre-zero tuning indication.

The use of dual selectivity is to optimise the overall performance in either mono or stereo. The bandwidth required for optimum signal-to-noise ratio and distortion with a mono signal is around 180kHz and on a stereo signal is around 280kHz. If the 180kHz bandwidth was used on stereo the signal would be degraded considerably, because the stereo information contained in the sidebands of the transmitted signal would be "chopped off" resulting in poor separation and increased high-frequency distortion. If the 280kHz bandwidth was used for mono it would be much wider than required and let more noise through, resulting in a poor signal-to-noise ratio on weak signals. Most commercial tuners compromise by using a

bandwidth somewhere between the two, i.e., normally around 220kHz, this results in reasonable performance but not the best possible. For the Winton Tuner it was decided to provide optimum bandwidth for either type of signal. Two separate sections are used for this and are selected by diode switching controlled by the selectivity switch S1.

Stereo Decoder

The Hitachi HA11223 is the latest development in phase-lock loop stereo demodulator i.c.s. It has very low audio distortion because it makes use of 100 per cent negative feedback, the distortion introduced during the decoding process being less than 0.06 per cent. The signal-to-noise ratio is also exceptional at around 86dB. It has automatic mono/stereo change-over and an output for driving an l.e.d. to indicate that a stereo transmission is being received, it can also be switched for mono operation only. In the Winton Tuner this is done in the narrow i.f. bandwidth mode. It is possible to modify the tuner for stereo reception in the narrow-band position if required.

After the decoding process there exists at the output of the decoder the wanted left- and right-channel audio signals and also spurious signals produced by the decoding process itself. These could cause problems when recording and must be filtered out. The HA11223 uses a phase-shift system to remove the residual 19kHz pilot tone from the output and this would normally be considered enough. However this tuner also makes use of a low-pass filter in the output of each channel to reduce all spurious signals to extremely low levels, these filters are numbered FL8 and FL9 on the circuit diagram.

Only a single pre-set potentiometer R48, requires adjustment to set the correct frequency of the phase-lock loop for optimum stereo separation.

TV Section

The r.f. unit used for the TV section is a modified Mullard U321. This has been modified to provide a 10.7MHz i.f. output suitable for feeding directly into the f.m. i.f. section of the tuner. The i.f. output from the Mullard unit is fed via diode switching to the base of Tr1, the reason for this is that the i.f. output from the Mullard unit is less than the ALPS f.m. unit. To compensate for this difference it was decided to bypass the first two ceramic filters and their 12dB insertion loss. As TV stations are spaced much more widely than f.m. stations the requirements for adjacent-channel selectivity are not so stringent and one ceramic filter is all that is required. The mono section of the i.f. circuits is used for TV, but should stereo TV ever happen it is possible to modify the tuner to receive stereo in the narrow-band position.

Because the Mullard unit has been modified to a lower i.f. frequency than it was designed for there is some reduction in the image rejection and this is now only around 20dB or so, however in practice this is not a problem and switching the a.f.c. on will quickly check if you are on the correct signal. If you are on the image the a.f.c. will push the station off tune, also the difference in signal strength between the image and fundamental is shown clearly on the meter.

The AM Section

The a.m. r.f. section uses a modified ALPS unit FX811B, and this is fitted with the switching required for selecting the various bands. It covers the normal l.w. and

PLEASE NOTE!

As this issue was about to go to press, we learned that, despite previous assurances, the a.m. tuner head FX-811B selected for the *PW* "Winton", had been discontinued by the manufacturer, ALPS Electric Co. Ltd.

We are investigating ways of overcoming the problem, and hope to have some news in time for our next issue.

m.w. and in addition has a s.w. coverage from 3.3MHz to 6.3MHz which includes the 49m broadcast band.

A ferrite antenna is used on the l.w. and m.w. bands but an external antenna is required for s.w. The input signal is fed into the base of a transistor mixer stage, and a separate transistor oscillator and buffer amplifier used with their output fed into the emitter circuit of the mixer. A separate buffer stage is used to provide an output for the digital frequency display unit. The 455kHz i.f. signal is taken from a single-tuned transformer in the mixer collector circuit and passed to the a.m. ceramic i.f. filter FL7. The a.g.c. voltage is applied to the mixer base circuit.

Following the ceramic i.f. filter the signal passes to a dual-gate MOSFET, Tr9. A dual-gate f.e.t. was used in this stage as it was found that a larger range of input signal levels could be handled without distortion due to overload. The signal is fed to gate 1 and the a.g.c. voltage to gate 2. The output from this stage is passed via a double-tuned i.f. transformer L11, L12 to the base of Tr8, this amplifies the signal to a suitable level for feeding to the detector circuit via a single-tuned transformer L13/14. Detection is carried out by diode D21 and the resulting audio passed via C83 to switch S12b. Resistor R83 and C82 form an r.f. filter to prevent any residual i.f. signal reaching the audio stages.


The a.g.c. voltage is produced by diode D20 and is fed to Tr9 which amplifies the a.g.c. voltage to a suitable level to control the various stages. This amplified a.g.c. results in a flatter audio output for a large variation in input signal levels.

Power Supply

Like the *PW* Winton Amplifier, the *PW* Winton Tuner uses a toroidal transformer so that the external magnetic field is kept to a minimum and therefore hum is not induced into the wiring. A standard type of transformer should not be used as the higher magnetic field will degrade the hum-and-noise figures by at least 10dB.

A full-wave rectifier system, D15 and D16 is used for the main d.c. supply and this is smoothed by C61. The un-stabilised supply is then fed via S15 (stand-by switch) to IC3 (7812), which stabilises the supply at 12V. This 12V supply is switched to the various circuits via S1, S12a, S13 and "steering diodes" D1-7, D11, D12. These diodes "steer" the voltage into the correct part of the circuit and prevent the voltage being fed back into other circuits which are "off". The use of these diodes greatly simplifies the amount of switching required.

The un-stabilised supply is also fed to IC6, which provides a stabilised 5V supply for the l.s.i. A further diode D12 and C60 provide a negative 18V supply for the 6-LT-09 display. Finally a voltage doubler D15 and D16 with C62 and C63 provide approximately 40V for the varicap supply via the special i.c., D17 which stabilises at 30V. The STAND-BY switch S15 is mounted on the front panel and removes the h.t. supply from the tuner in the OFF position and switches the display into the clock mode. No mains switch is provided, as removal of the mains would switch off the clock, and the time and any timer settings would be lost. Those readers who feel that a mains switch should be fitted could fit a suitable switch on the rear panel next to the mains transformer so that the complete tuner can be switched off when going on holiday, etc.

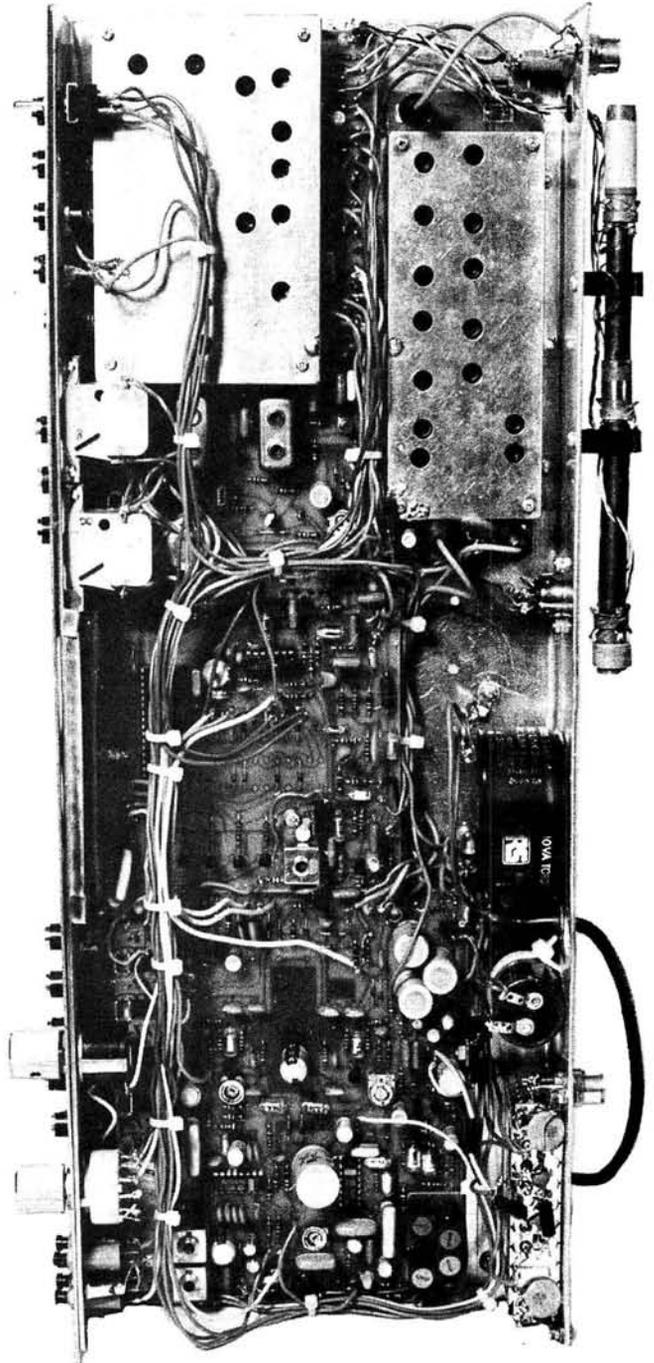

The internal view of the *PW* Winton Tuner

H. LEXTON LIMITED

HARVEY G4JDT

RADIO AND ELECTRONIC ENGINEERS

DAVE G8SYG

YOUR EAST LONDON HAM STORE

We are the main UK Service Contractors to Hitachi Sales UK and we have fully trained engineers on the premises. We have been in the service industry for 15 years and we know what we are doing.

STANDARD

The Standard Twins

C7800 C8800
£270 £250

The very latest from Standard. The **C78** 70cms trans-portable.

NOW IN STOCK **£209.50**

ICOM NOW AVAILABLE

IC2E	£159.00
BP5	Hi Power Pack.....	£30.00
BP4	Empty Pack.....	£5.00
LC3	Carry Case.....	£3.00
HMP9	Mic/Speaker.....	£12.00
ICCP1	Mobile Charges Cord.....	£2.75

IC 251

Multimode Base/mobile CPU control
Multi-purpose scanning
Dual VFO's - Squelch on SSB/CW.
Really Outstanding Performance.

ONLY £479 incl.

TRIO/KENWOOD

TS 130S

3.5-30MHz (including the new bands) I.F. shift - Digital Display - speech processor - SSB/CW narrow/wide filters.

£491.05p

TR 7800

2 mtr Mobile Fully synthesized with Keypad Frequency control

£268

TS 830S

160-10 metres (including the newbands) - variable I.F. bandwidth - Adjustable noise blanker - plus much, much more - only

£639.52

SWAN

100MX	235W P.E.P Analogue mobile.....	£365.00
Astro 150	(Including mounting bracket).....	£551.00

1500ZA	1500W Linear Amp.....	P.O.A.
103BX	235W P.E.P. W.A.R.C.....	£810.00
PSU6	(102BX).....	£140.00
PSU5	(100MX) 13.8V DC, 20 amp.....	£132.00

CUSHCRAFT AMATEUR ANTENNAS

H.F.

A3	20/15/10 3ele Beam 8dB gain.....	£147.00
ATV5	80-10 Trapped Vertical.....	£74.40
ATV3	20/15/10 Trapped Vertical.....	£34.00
ATV4	40/20/15/10 Trapped Vertical.....	£68.00

VHF (144 MHz)

A3219	19ele-Long 'Boomer' Yagi 16.2dB gain.....	£62.00
214B	14ele Jnr 'Boomer' Yagi 15.2dB gain.....	£49.50
ARX2	Ringo Ranger 6dB gain vertical.....	£24.75
A144-4	4ele Yagi 9.0dB gain.....	£16.25

A144-7	7ele Yagi 10.0dB gain.....	£20.31
A144-11	11ele Yagi 11.3dB gain.....	£25.72
DX120	20ele Array 13.2dB gain.....	£47.20
ARX2B	Ringo Ranger II.....	£28.75
ARB2K	Conversion Kit for Ringo to Mk II version...	£12.75
CS100	Communication Speakers.....	£11.50
TAP3009	5/8 Side Mount and snap in 2MTR.- 144-174 MHz.....	T.B.A.

TAP677	£18.50
K220	Mag Mounts Base 17' Cable & PL259.....	£8.67
TAP/432 MHz	Snap in for K220.....	TBA

EXCLUSIVE TO US

1KW VHF Linear amplifier - 600W SSB - 350W FM (Due in soon)..... **£449**
Power Supply - 6 Amp continuous - 8 Amp surge (13.8V)..... **£24.95**

TRADE ENQUIRIES INVITED



Also available:- Video - Hi-Fi - T.V. - Music Centres, e.g. Hitachi SDT 300-auto-reverse music centre with pre-set FM, Dolby, strobe turntable, 25 + 25W per channel, including speakers only **£269.95** - These are either Sample or Demonstration units. Many other Hitachi Demonstration models available, Hi-Fi, Portable Stereo Radio Cassettes etc.



Telephone 01-558 0854

191 FRANCIS ROAD, LEYTON, LONDON E10

Telex 8953609



Opening Times: 9-5.30 Mon.-Fri.
10.00-1.00 pm Sat.

or any time by appointment.



★ specifications

FM

There has recently been introduced a new standard for testing and evaluating the performance of hi-fi f.m. tuners and receivers. This standard is known by the shortened title of IHF-T-200: 1975, and is now accepted world-wide.

One of the most important things to come out of the new standard is that the sensitivity is no longer quoted in microvolts. This is because there was always the possibility of a 6dB error, as more often than not it was never stated if it referred to e.m.f. or p.d. This ambiguity is resolved by expressing sensitivity in terms of available power, this being constant with both IEEE and IEC standardisation. Input signal levels are standardised in terms of dBf, with one femtowatt (10^{-15} W) as the reference level. At a 300Ω impedance level, 1dBf corresponds to 1.1μV open-circuit, or e.m.f., while 120dBf corresponds to 1.1V.

As it was felt a number of readers may be confused by this new standard, the measurements on the f.m. section of the PW Winton Tuner have been made using the methods in IHF-T-200 but quoted in both the old microvolts and the new dBf. This should enable the tuner to be compared with most other published specifications.

Tuning range: 80–109MHz

Sensitivity:

0.9μV p.d. (10.33dBf) 75Ω for 30dB signal-to-noise-plus-distortion

Stereo sensitivity: 2μV (17.26dBf)

Quieting sensitivity (50dB signal-to-noise-plus-distortion):

Mono, 6.3μV (27.23dBf)

Stereo, 20μV (37.26dBf)

Muting level (adjustable):

Approx. 25μV (39.20dBf)

Signal-to-noise ratio (485μV 65dBf):

Mono, 75dB

Stereo, 73dB

Distortion (1kHz 100% modulation):

Mono, 0.15%

Stereo, 0.15%

Distortion (100Hz):

Stereo L–R 100% modulation, 0.25%

Distortion (6kHz):

Stereo L–R 100% modulation, 0.2%

Distortion (de-tuned by ± 100kHz):

Stereo 1kHz at 100% modulation, L–R not more than 0.5%

Stereo separation:

20Hz–40dB

100Hz–40dB

1kHz–40dB

5kHz–32dB

10kHz–26dB

15kHz–22dB

Spurious r.f. responses:

Image better than 120dB

F1 + ½ i.f. better than 120dB

2F1 – F2 better than 64dB

Audio frequency response:

–1dB for 14Hz–15kHz

–1.5dB for 16kHz

Pilot tone rejection:

Stereo, better than 70dB

Selectivity:

	Wideband	Narrow band
Adjacent	7.5dB	20dB
Alternative	73dB	75dB

Capture ratio:


Wideband, less than 1dB

Narrow band, less than 2dB


AM suppression:

Wideband, better than 60dB

Narrow band, better than 65dB

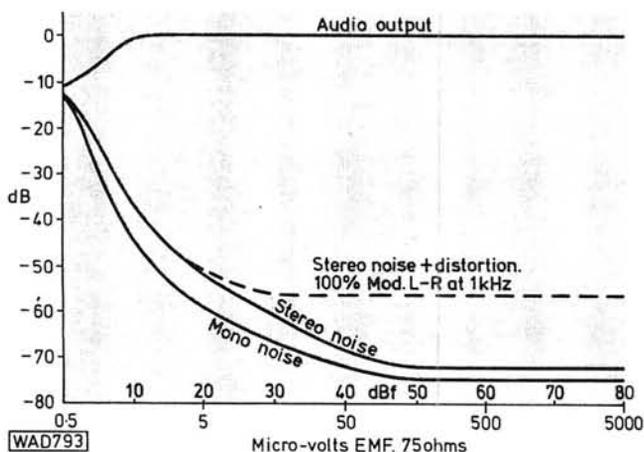

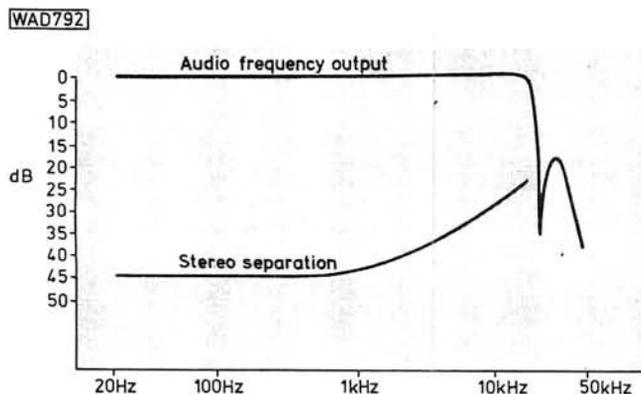Graph showing audio output and signal-to-noise and signal-to-noise-plus-distortion on stereo for various input signal levels on 98MHz



Graph showing audio frequency response and separation on stereo

AFC (off-set):

Less than 20kHz

AFC correction factor: 5**Signal strength meter range:**0.8 μ V to 1mV**Audio output (full limiting 100% modulation):**

280V

Modulation level:

100mV output-33%

TV**Frequency range:**

Approx. 460MHz to 860MHz

Channels: 21 to 69**Logging scale reading:**

Approx. 200 to 500

Sensitivity:100 μ V for 30dB signal-to-noise-plus-distortion**Image rejection: 20dB****AFC correction factor: Mid-band, 12****AM****Frequency coverage:**

LW, 140kHz to 280kHz

MW, 500kHz to 1625kHz

SW, 3-3MHz to 6.3MHz

Sensitivity (for 10dB signal-to-noise-plus-distortion):LW, 70 μ VMW, 23 μ VSW, 16 μ V**Image rejection: 18dB at 6MHz****Selectivity:**

-3dB bandwidth 5kHz


-15dB at \pm 10kHz-50dB at \pm 20kHz**Audio Frequency response:**

-3dB at 40Hz and 3kHz

-10dB at 22Hz and 4.5kHz

Distortion:

2% at 1kHz and 30% modulation

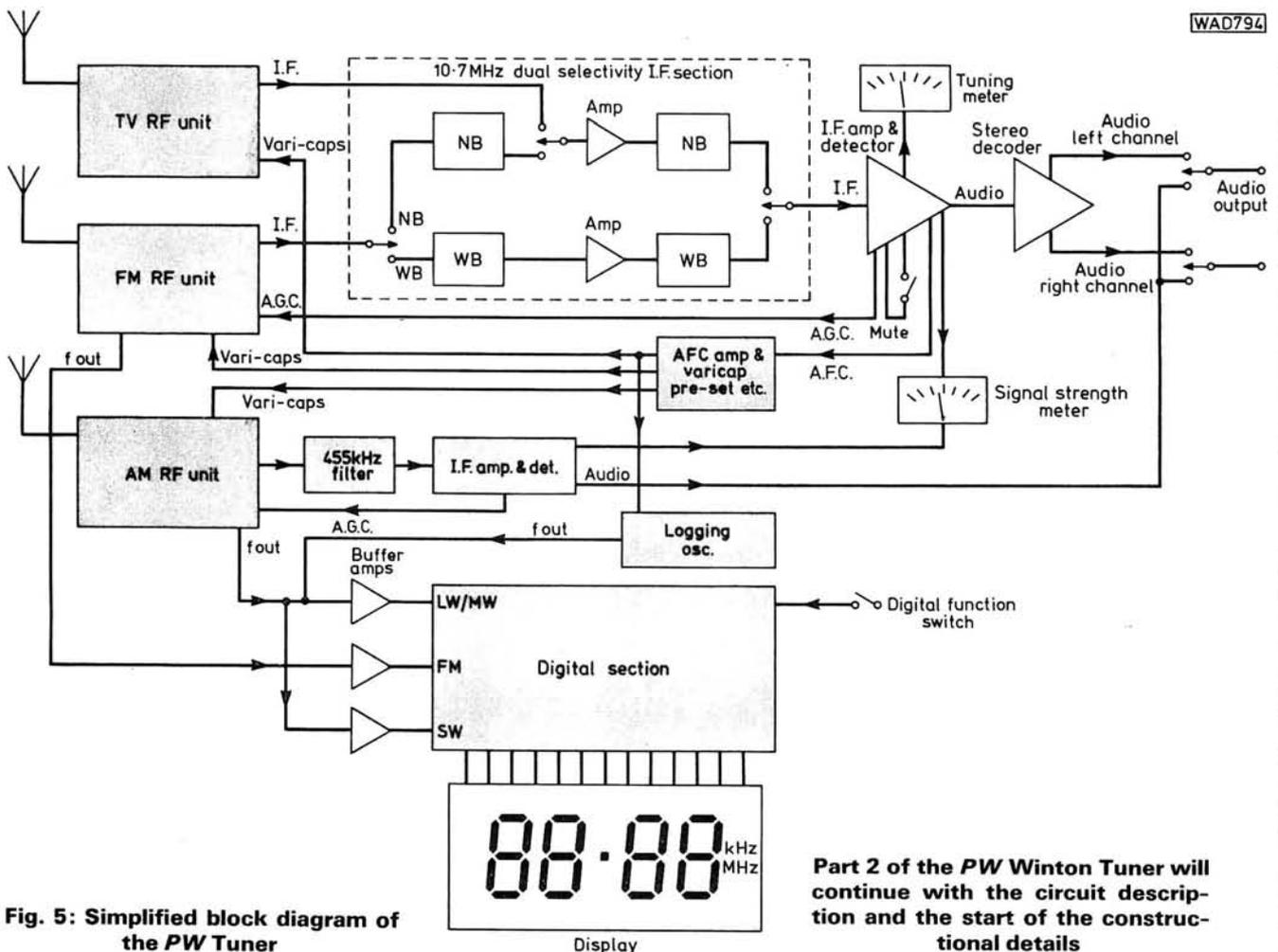**Fig. 5: Simplified block diagram of the PW Tuner****Part 2 of the PW Winton Tuner will continue with the circuit description and the start of the constructional details**

SOUND ADVICE – SOUND VALUE

A GOOD START is essential to short wave listening and expert advice is important in achieving this – So here's some – If you've made up your mind to buy a receiver you should be aware it will perform only as well as the antenna it sees. The old adage regarding wire antennas "As long and as high as you can" is still good, but at best is only good for PEAK PERFORMANCE on one or two frequencies, at worst none.

Whichever frequency you tune your receiver to, for PEAK PERFORMANCE on all frequencies you need good matching between your Receiver and Antenna to hear the best from it. If you plan to listen on the high frequency bands up to 30MHz then you know you can't have an antenna for every frequency! Or can you? – Well, not quite! BUT we can offer you MUCH IMPROVED PERFORMANCE from your receiver by using an antenna tuning unit, that will electrically change the length of your antenna to match the frequency you select – In other words – A MATCH AT ALL FREQUENCIES.

You'll see many antennas being advertised under gimmicky names, but when it comes down to it they're only random wires or odd configurations. At the end of the day, if you're expecting the performance the manufacturers specified, then you'll still have to buy an antenna tuning unit.

Tell you what we'll do – we'll prove it to you – we'll give you one ABSOLUTELY FREE when you buy your FRG 7700 or FRG 7700M and we'll give you complete advice on an antenna to suit your available space, which should only cost you a couple of pounds! So let's put the offer in big print for you!

1 YAESU FRG 7700 + AMTECH 200 ATU	£309.00
1 YAESU FRG 7700M + AMTECH 300 ATU	£389.00
VAT included	

What's the difference between the Amtech 200 and Amtech 300? Well both will tune any random length of wire but the Amtech 300 will do a little extra – it will also tune co-axial fed antennas – Their normal selling price? The Amtech 300 **£43.95** – The Amtech 200 **£29.95** – What can you lose? So get cracking MAKE A GOOD START! HAVE PEAK PERFORMANCE FROM THE OFF.

JAYBEAM – HYGAIN – BANTEX – AMTECH – CUSHCRAFT – SWAN – ATLAS
and 50 other major lines – all ex stock



AMCOMM SERVICES

194A NORTHOLT ROAD, SOUTH HARROW, MIDDX.

Tels: 01-864 1166 & 01-422 9585

Opening hours: Tues–Sat 9.00–5.30, Sundays by appointment. Closed Monday.



Western

THE COMMUNICATIONS SPECIALISTS
EVERYTHING FOR THE RADIO AMATEUR

ANTENNAS . . . FOR THE HF BANDS

BRITISH MADE BY **Western**

TRAP DIPOLES (3 types)

TD1/10-80	10, 40 and 80m	£34.44
TD1/15-80	15, 20, 40 and 80m	£34.44
TD-P	Portable type with winding spools (TD1 are of 14 gauge copper; TD-P is copper/terylene braid)	£30.48

VERTICAL

DX-5V	10-80 metres; approx 26ft high; slimline	£89.00
-------	--	---------------

BEAM ANTENNAS (and Rotary Dipole)

DX-31	Rotary dipole for 10, 15, 20m	£46.00
DX-32	2-element beam for 10, 15, 20m	£80.50
DX-33	3- " " " " " "	£121.90
DX-34	4- " " " " " "	£161.00
DX-103	3-element monoband beam for 10m	£74.75
DX-105	5- " " " " " "	£97.75

★ Other Antenna Accessories available – see our Price List ★

ALL PRICES INCLUDE VAT (15%) AND FREE DELIVERY UK.

Send large SAE for further details of this and other equipment – or use our Answerphone after hours.

Western Electronics (UK) Ltd

HEAD OFFICE (All Mail/Enquiries)

FAIRFIELD ESTATE

LOUTH, LINGS, LN11 0JH

Tel: Louth (0507) 604955/6/7

ACCESS
VISA
H.P.

Belle Vue Radio and Electronics Exhibition

in the Lancaster Hall
on Sunday 29th March 1981
Doors open at 11.00 a.m.

The North's Premier Amateur Radio and Electronics event
features:

Inter-Club Quiz	Grand Raffle	Radio Society's Stands and Trophy
Construction Contest	Amateur Computer Stands	Morse Code Challenge
R.S.G.B. Book Stall		Home Office and Raynet Stands.

TRADES STANDS who have booked space

Eurova Ltd.	GH ₂ Enterprises
M & B Radio	Wilson's Valves
J. Birkett	Mechanelec Ltd.
The Amateur Radio Shop	W. H. Westlake
Radiotronics	D.S. Electronics
Lowe Electronics Ltd.	Microdigital Ltd.
Bredhurst Electronics	Arrow Electronics Ltd.
Crayford Electronics	Telecom
S.M.C. (Jack Tweedy) Ltd.	Royd Electronics
J.M.G. Electronics	F. R. Galka
Sota Communication Systems Ltd.	Contour Electronics
Amateur Radio Exchange	Tandy Corporation (U.K.)
Richard White	Ace Maitronix Ltd.
Johns Radio	Sound Service
N.W. Repeater Group (Bring & Buy)	Marco Trading
S.G.S. Electronics	Minicost Trading Ltd.
	Jewell & Powers

Belle Vue has ample car parks.

F.M. Talk in on GB3NRS & G8NRS/A on 145MHz Chs S22,
R2-R6 and on 433MHz Chs SU8, RB4 & RB14.

**ADMISSION 40p BY RAFFLE TICKET AND EXHIBITION PLAN
ENTER AT REAR OF BELLE VUE OPPOSITE MAIN CAR PARK
OFF HYDE ROAD A57**

MODS

IMPORTANT—The ideas presented here are suggestions only, and as they are untried by this magazine, we cannot accept responsibility for any resultant damage, however caused. Before alterations are attempted, care should be taken to ensure that any guarantee is not invalidated, and it should also be borne in mind that modifications usually have an adverse effect on resale prices. In cases where specialist skills or equipment are needed, most dealers will undertake the work for a reasonable fee.

Roger Hall G8TNT(Sam)

No. 5

Trio R-1000

Chris Attrell, a s.w.l. from Brighton, has telephoned me to point out that, although the Trio R-1000 bandwidth mod that I described in Mods No. 3 (January) works perfectly, some readers are justifiably reluctant to cut and resolder wires inside a brand new piece of equipment. He has suggested a far simpler way to achieve the same results.

Just above the plug that has the relevant wires running to it (Fig. 1 Mods 3), is an empty socket. To change the bandwidths from 12kHz (wide) and 6kHz (narrow) to 6kHz (wide) and 2-7kHz (narrow), simply remove the plug from its original socket and replace it in the empty one. This mod is easily reversible when it comes to selling the set, and this is a definite improvement on the original. Thanks Chris.

Standard C8800

I have received numerous letters, telephone calls and "on the air" requests for a reverse repeater mod for the Standard C8800, and I would like to thank John Armstrong G8MVH, who worked on this mod whilst he was running the service department of Lee Electronics before he left to start his own business, for the details.

The mod, which gives full reverse repeater operation, is based on the principle that if, when R1 is selected, pin 7 of plug JL05 is low on receive and high on transmit, then by reversing this to high on receive and low on transmit, the reverse of the standard function can be obtained.

An element of personal choice as an extra switch could be mounted almost anywhere; on the front or back of the rig, underneath, on the microphone, etc. In this instance it has been incorporated using the existing switches and with the minimum of alterations to the circuit.

The additional components that are required are BC182L or equivalent (Tr1) 1 off, 10Ω ½W resistor (R1) 1 off, 1N914 (D1) 1 off. First remove the bottom cover and locate pin 7 of plug JL05. Attached to this pin is a yellow wire that must then be separated from the others and pulled towards the BUSY/VACANT switch, SM01. Now cut this wire, but make sure that the cut is in a position such that once the ends have been bared they will still reach the appropriate pins of SM01.

Next, short together pins 1 and 4 on SM01 with a short piece of insulated wire (Fig. 3), and then solder the yellow

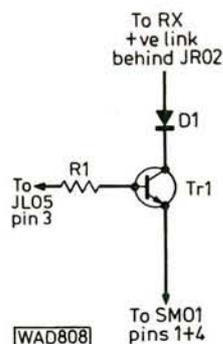


Fig. 1:


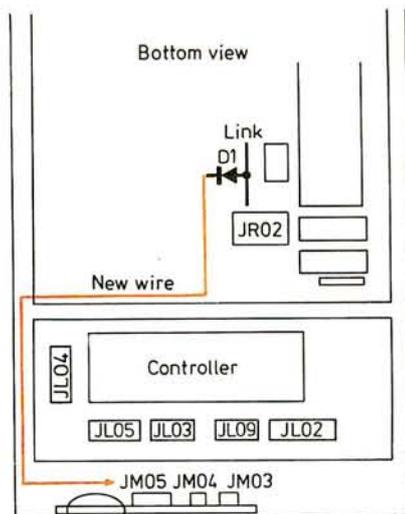


Fig. 2:

Fig. 3:

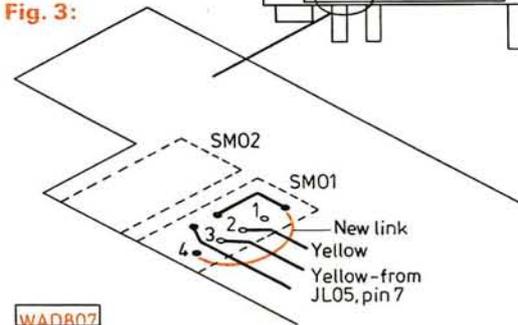

WAD807

wire coming from pin 7 of JL05 to pin 3 of SM01, and then solder the remaining piece of yellow wire to pin 2 of SM01. Solder the emitter of Tr1 to SM01 at either pin 1, pin 4 or to the linking wire.

Just behind JR02 is a link (Fig. 2). Solder the anode of D1 to this link and then cut a new length of insulated wire, and use it to join the cathode of D1 to the collector of Tr1. Keep the cathode of D1 as short as possible and make sure that it is kept well clear of associated circuitry. Run the new wire around the controller board as in Fig. 2. Now solder R1 between the base of Tr1 and pin 3 of JL05.

This small circuit (Tr1, D1 and R1 in Fig. 1) should be self-supporting, if made carefully, but could be made on a small piece of Veroboard and mounted in any convenient position.

If, after having done all this, you find that nothing happens when reverse repeater is selected, don't panic. Some batches of these rigs were fitted with slightly different BUSY/VACANT switches and reversing the wires to pins 2 and 3 should solve the problem.

When modified, the C8800 will operate normally in the simplex and duplex modes, if the BUSY/AUTO/VACANT switch is in the AUTO position. With the switch in the BUSY or VACANT position, duplex (R1) gives reverse repeater. It should be noted that in this mode scan, memory recall, repeater shift (R2 and R30), etc., will be inoperative and the switch must be returned to the AUTO position before these functions will operate.

Wanted


Would whoever left the C7800 reverse repeater mod with Norman G8THJ, at Lee Electronics, please contact either him or me as we no longer have your name and address, and I need to contact you before I can publish the mod. Please write to: R. S. Hall, Practical Wireless, King's Reach Tower (Hatfield House), Stamford Street, London SE1 9LS.

73's
Sam G8TNT



IN CONTROL

Dick GANDERTON G8V FH

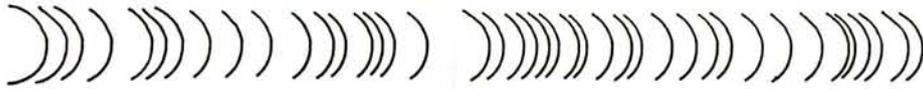

This is the first of a new series which will look at aspects of systems used for the control of models of all descriptions.

By now most radio control enthusiasts will be aware that as from 1 January 1981 a licence is no longer required for r.c. operation. However you will still have to comply with all the regulations—which were printed on the licence—which you no longer have! Also, from the same date, you may now use the frequencies between 35.005MHz to 35.205MHz, but only for model aircraft control and only with narrow-band f.m. systems. This leaves other modellers, and a good few aircraft types as well, stranded on 27MHz besieged by an unspecified number of illegal “good buddies”.

For some months now the Home Office have been issuing to *bona fide* r.c. clubs a special licence to allow them to monitor 27MHz frequencies for interference. (Listening on 27MHz without such a licence is, according to the Wireless Telegraphy Act, illegal.)

As it could be of immense use to a modeller to monitor the frequency he is about to use I am offering details of a simple monitor based on a cheap Oriental transistor radio.

The original idea and development came from P. A. Julian of Wimborne.

A Radio Control Monitor

In these days of increasing illegal 27MHz activity, it is important that the radio-control operator knows if there is any traffic on his frequency before going on the air. Many enthusiasts do not possess a monitor receiver and often take a chance rather than pay out for an extra piece of

equipment. But radio interference can cause loss of control resulting in damage to a valuable model and even possible injury to spectators.

Although a reasonably cheap monitor is available on the market for about £20, it is tuneable and, for those requiring spot-on accuracy, a crystal controlled monitor is the answer. Moreover, a crystal controlled receiver is relatively simple to alter to 35MHz, now that band has been granted by the Home Office for r.c. use, requiring only a change of antenna coil and crystal.

For these reasons, ways of producing a simple but effective monitor were considered.

Circuits

In the end it was decided to attempt to modify an existing portable radio since it is often cheaper to buy a ready-built medium wave set than it is to buy the individual components and assemble them.

Crystals commonly available for r.c. use are for 455kHz i.f.s while transistor radios imported from the Far East also have nominal 455kHz i.f.s and can often be picked up second-hand very reasonably. Attempts were made to modify the front end of one of these, but using as much of the original circuit as possible. Fig. 1 shows a typical front end.

Looking at circuits for r.c. receivers it was seen that two transistors were used in the front end, one as a mixer and the other as the crystal controlled oscillator. To copy this would have involved building at least the oscillator on a

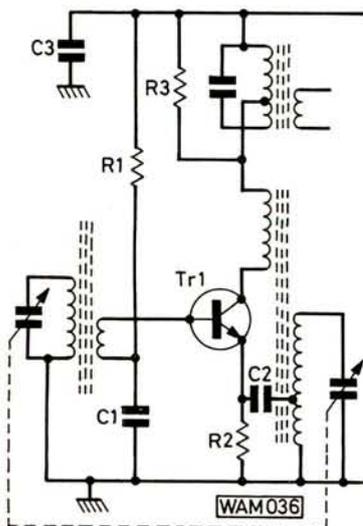


Fig. 1:

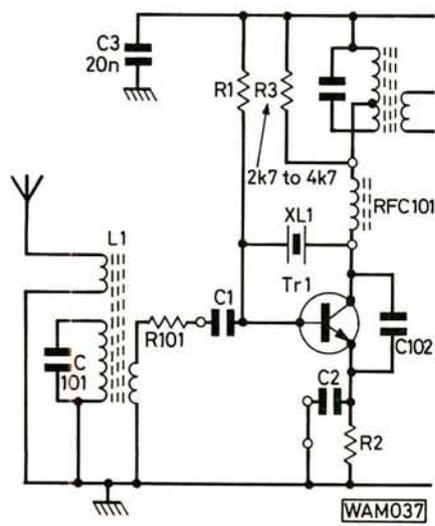


Fig. 2:

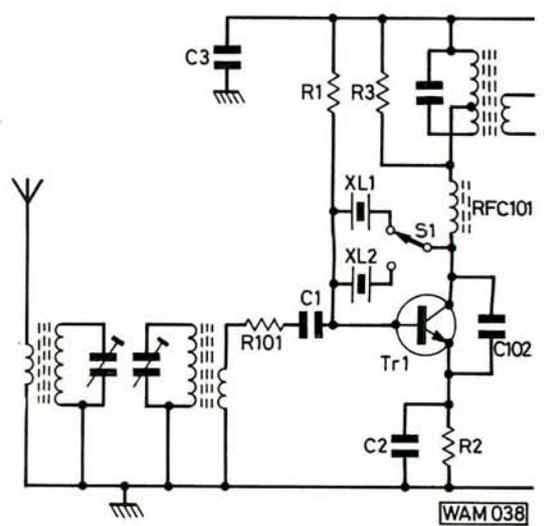


Fig. 3:

separate board and then fixing it to the receiver circuit board, so an unusual mixer/oscillator combination was tried and the original circuit was modified as shown in Fig. 2. This was found to be quite satisfactory since a minimum of extra components was required and even the original mixer/oscillator transistor was used.

At first it was thought that a tuned circuit would be needed between the collector of Tr1 and the first i.f.t. but a small r.f. choke from an old TV proved sufficient. R101 is needed to prevent the aerial tuned circuit from damping and killing oscillation. C102 introduces some feedback and encourages the crystal to oscillate and also helps to overcome the damping effect of L1.

Modifying the Set

It is suggested that the set to be modified should have three i.f. stages (four cans on the circuit board including the oscillator coil) as two stages will probably not be selective enough.

The circuit board should be taken out of the case and the tuning condenser, ferrite rod antenna and oscillator coil carefully removed. Any holes needed for mounting the 27MHz coil and crystal holder can be drilled. The free end of C2 should be connected to earth and RFC101 fitted between the collector of Tr1 and the first i.f. coil. The holes revealed by the removal of the oscillator coil can be used. C102 is best fitted to the underside of the board and soldered between the emitter and collector of Tr1. The base of Tr1 should be connected to the junction of C1 and R1. Unused sections of the printed circuit can be used for making connections where needed. The grounded end of C1 should be disconnected and joined to one end of R101. The antenna coil and crystal holder should be glued in place. The coil can be connected and C101 soldered in place. The crystal holder is wired between the collector and base of Tr1. If there is not enough height between the board and the lid of the case for the crystal to stand upright, then the holder will need to be the type which allows the crystal to be plugged in sideways.

When the modification is complete, check the wiring against the circuit diagram and switch on. When the receive crystal is plugged in, a slight change in noise level should be noticed. Next test by switching on a r.c. transmitter with the correct transmit crystal plugged in and make sure the i.f. transformers are aligned. The antenna coil slug can then be adjusted for maximum signal. The actual telescopic antenna will have to be chosen and fitted to suit the case.

★ components

Resistors

$\frac{1}{4}$ W 10%
220 Ω 1 R101

Capacitors

Disc Ceramic
22pF 2 C101,102

Miscellaneous

Crystal (see text); Crystal holder; 1A TV choke (RFC101); 7mm coil former; 26 s.w.g. enamelled copper wire; Oriental transistor radio.

Coil Winding Details

Primary	12T 26 s.w.g. on 7mm former
Secondary	3T 26 s.w.g. on 7mm former
Antenna Coupling	3T 26 s.w.g. on 7mm former

Any final adjustments can be made with the transmitter some distance away from the monitor. If there is any instability in operation, try changing the value of R101 but first check C3 and R3, the addition of these components if not in circuit could make quite a difference.

If the set being modified is a l.w./m.w. version, the wave-change switch should be removed or all connections to it carefully cut with a sharp knife. However, this switch could usefully be used to change crystals (Fig. 3) and the l.w. trimmer capacitor could be used in place of C101.

Other improvements in performance include replacing Tr1 with a suitable v.h.f. type (checking whether the original is *npn* and *npn*), and having an additional tuned circuit as in Fig. 3. It should be possible to alter older British sets using germanium transistors in the same way although the mixer/oscillator transistor may have to be changed for another type such as an OC170. Also note that the i.f. frequency of these older sets will have to be lowered from 465/470kHz to 455kHz unless the older 470kHz i.f. receiver crystals as once produced by Macgregor can be obtained, perhaps second-hand.


Of course a monitor will not prevent the effects of interference but because this particular type of circuit resembles an r.c. receiver, it will give a very good indication of what an r.c. receiver will "hear". It will even have a similar image response, i.e., the Rx crystal frequency minus 455kHz. Even though this is an a.m. set, it will also give adequate reproduction of an f.m. signal for our purposes.

IC OF THE MONTH—SL6310C

▶▶▶ continued from page 32

The SL6310C can also be used in applications where a small amount of controlled power is required. Its use in controlling the speed of a small motor is shown in Fig. 7. Balanced $\pm 7V$ supplies are used here, so that one side of the motor can be connected to ground. No appreciable current will flow through the motor when the two inputs of

Fig. 7: A simple motor driver

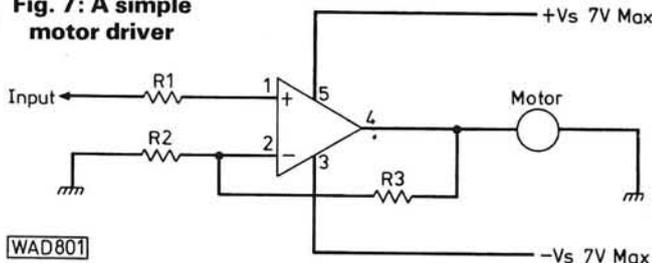


the amplifier are at the same potential; that is, when the input is at ground potential. As the input is made positive with respect to ground the motor will rotate in one direction, but when the input is made negative, the motor will rotate in the other direction. Resistors R2 and R3 set the gain and therefore the sensitivity of the circuit.

Availability

The SL6310C device is available from Ambit International Ltd., 200 North Service Road, Brentwood, Essex CM14 4SG.

A permanent bind

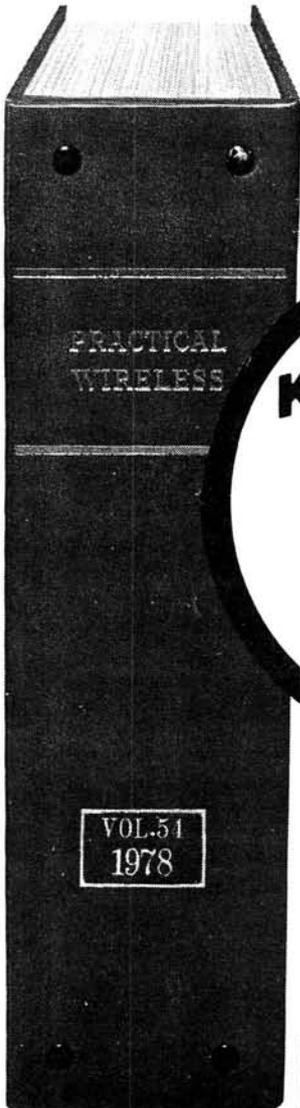

It's so easy and tidy with the Easibind binder to file your copies away. Each binder is designed to hold approximately 12 issues and is attractively bound and blocked with the PRACTICAL WIRELESS logo. Gold Letraset supplied for self blocking of volume numbers and years.

Keep your copies of practical WIRELESS for easy reference

Price £4.30 including postage, packing and VAT. Why not place your order now and send the completed coupon below with remittance to: IPC Magazines Ltd., Post Sales Dept., Lavington House, 25 Lavington Street, London SE1 0PF.

it's easy with EASIBIND



Order form PRACTICAL WIRELESS


I enclose P.O./cheque value for binders

Years required
(BLOCK LETTERS PLEASE)

Name

Address

Date

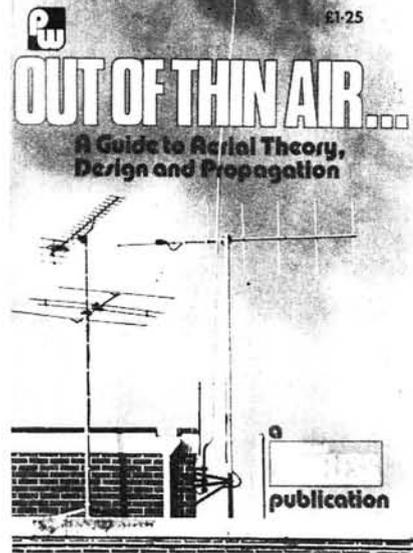

Aerials and aerial accessories are very definitely among the most popular topics covered in *Practical Wireless*. In response to requests from readers, we've reprinted a selection of articles from the past three years, plus two new features—one by Ron Ham on v.h.f. propagation, the other describing the "Ultra-Slim Jim", a new version of that most popular 2-metre aerial design by Fred Judd.

Out of Thin Air has 80 pages, 295 x 216mm, and is available from W. H. Smith price £1.25, or by post from Post Sales Department, IPC Magazines Ltd., Lavington House, 25 Lavington Street, London SE1 0PF, price £1.50 including postage and packing to UK addresses, or £1.80 by surface mail overseas. Please ensure that your name and address are clearly legible.

OUT OF THIN AIR

Please send your order and remittance to:

**IPC Magazines Ltd., Post Sales Department,
Lavington House, 25 Lavington Street,
London SE1 0PF**

Please send me.....copies at £1.50 each to include postage and packing (£1.80 surface mail overseas)

I enclose P.O./Cheque No.....Value !.....

UK remittances must be by crossed postal order or cheque (name and address on back please) and made payable to IPC MAGAZINES LTD

NAME
(BLOCK LETTERS)

ADDRESS
(BLOCK LETTERS)

.....
.....
..... Post Code

Remittances with overseas orders must be sufficient to cover despatch by sea or air mail as required. Payable by International Money Order only

Company registered in England. Regd. No. 53626

A subsidiary of Reed International Limited

— Cut round dotted line —

WATERS & STANTON ELECTRONICS

18/20 MAIN ROAD, HOCKLEY, ESSEX. TEL (0702) 206835

4,000 SQ FT DEVOTED TO RADIO COMMUNICATION

"SUCH NICE PEOPLE"



SR9 VHF RECEIVER
AMATEUR/
MARINE
£46 inc. VAT

The SR9 must be one of the most popular monitors for 2 metre amateur radio enthusiasts. (Also available as a marine version at the same price). It is fully tuneable across the band with the option of also installing up to 11 xtal controlled channels. Power requirements are 12v DC negative earth at 200ma approx. The unit comes complete with mobile mounting kit and built-in speaker.

PROFESSIONAL AIRCRAFT MONITOR R517 £49.50
(as supplied to pilots, ground crew etc.)



The R517 is a professional aircraft monitor receiver, having superb sensitivity and capable of tuning across the entire aircraft band 118-143MHz. For easy tuning there is both a coarse and fine tuning control. In addition there is a 3 position switch for selecting xtal controlled channels (xtals £3.00 extra) for your local airport. The unit is completely portable running off self-contained batteries.

AR22 VHF FM MONITOR
OUR PRICE £83 inc. VAT



Truly amazing! The AR22 tunes across the 2 metre FM band 142-148MHz (also includes Police and Fire Brigade) in 5kHz steps. So small it will fit into a shirt pocket and yet nothing is sacrificed in terms of performance. Price includes rechargeable batteries, mains charger, fly aerial etc. You won't find a smaller monitor anywhere.



TRIO R1000
COMMUNICATIONS RECEIVER
OUR PRICE £285 (Free Securicor Delivery)

The R1000 has really caused a stir in the receiver market! Its performance matches professional receivers costing many times more and with our new competitive price of £285 it must be the best value on the market today. Full digital readout from 200kHz (actually it operates right down to 20kHz but with reduced sensitivity) means accurate tuning and the 30 position band selector switch means really good bandspread for easy operation. Other features include noise blanker (a really good one!) built-in speaker, digital clock/timer and both 230v AC/12v DC operation. (Yes we include the 12v DC kit free!) Each model is fully checked and delivered anywhere in the U.K. within 24 hours of receipt of payment!



YAESU COMMUNICATIONS RECEIVER
FRG7700 £309
FRG7700MEM £380
PLUS FREE GLOBAL 3-30MHz Aerial

Free Securicor Delivery

The FR7700 is a new model from Yaesu that replaces the FRG7000. Full coverage is provided between 200kHz and 30MHz with bright digital readout that also doubles as a clock. Features include noise blanker, FM detector, internal speaker, 230 volt AC operation and built-in timer. As an optional extra there is also a memory unit which enables up to 12 selected frequencies to be stored and selected.



PS134 4 AMP 13.8v POWER SUPPLY. STABILISED & SHORT CIRCUIT PROOF
£23 plus £1.50 p&p

This is the power supply that we've been advertising and selling for several months. It really is a robust little unit with a transformer 50% larger than its competitors. Some cheap power supplies get hot, hum and even go bang! This one stays silent and keeps on working. It is fully protected against short circuit and overload and is capable of delivering 4 amps continually at 13.8v DC. Ideal for transceivers.



SWR/POWER/FIELD STRENGTH MEASURING METER
SPECIAL OFFER
£11.95 + 60p p&p

As used by CB and Amateur radio operators.

The YW3 is used by amateur radio and CB operators around the World. It's offered to you at a really low price because we import them direct from Japan. It tells you the VSWR, power output and field strength and covers 3.5 to 150MHz. If you want the strongest signal in town - you'll find the YW3 the sure answer.

28MHz FM!

NEW AZDEN PCS2800



£169.00

Here's an exciting new 20 watt input (10 watts output) transceiver with a host of features to put it head and shoulders above the competition. Compare its features:- 200 channels, high/low power switch, computer control touch pad, 6 programmable memory channels, automatic band searching, automatic memory scanning, microphone frequency control button, priority channel, digital frequency readout, removable control panel (permits main transceiver to be mounted remotely), slide in mobile bracket, built in speaker and a host of other features. Its high power and very sensitive receiver gives it better coverage than its competitors. Send for details today or come and see our demonstration model.



SX200 MONITOR
26-500MHz

£240 inc. VAT

Here's a really wide coverage receiver going all the way from 26MHz to 500MHz (with just a few gaps). Mains or battery operation, FM or AM, means it can be used just about anywhere for anything. Channel memory, scanning and built-in clock are just a few of its features. If you're interested in amateur radio, aircraft, Police, taxis, etc., then this receiver covers them all.

STOP TRANSMITTER INTERFERENCE



HP3A £3.50 each
Ferrite Filters £1.00 for 2

If you are suffering from or causing transmitter interference to TV or audio equipment, then these are the items for you. Our HP3A TV filter simply plugs into the TV lead and cuts out transmitter interference (ideal for 27MHz). Our ferrite ring filters are ideal for cases of interference to hi-fi systems.

STOP PRESS:- SEND 14p STAMP FOR NEW 1981 CATALOGUE ON RADIO COMMUNICATIONS

MAIL ORDER SLIP to: Waters & Stanton Electronics, Warren House, Main Road, Hockley, Essex.

Name..... Goods required

Address.....

Please rush me the above. Cheque enclosed for £...../Please charge to credit card No.....

MAIL
ORDER

Photo Acoustics Ltd

MICRO COMMUNICATIONS DIVISION

BUDGET
ACCOUNT



TR7800 £268



R1000 £285



TR9000 £345

TRIO

TS-1805 160-10m 200W transceiver £679.65
 TS-1305 80-10m mobile 200W transceiver £491.00
 TS-130V 80-10m mobile 20W transceiver £404.00
 TS-8305 160-10m transceiver (includes new bands, various 1.F. options, digital display, 2 x 6.146 PA, plus many other features) £639.52
 TS 770E 2m/70cm multimode base station £763.60
 TR 2300 2m handheld (80 channels) £166.75
 TR 2400 2m synthesized handheld £198.00

Receivers
 R 820 Simply the best amateur receiver £690.00
 SRX 30 SSB/AM/CW 0.5-30MHz £158.00
 SR 9 144-146 or 156-162MHz tuneable or xtal £46.00
 AMR 217B Marine or amateur band 8 channel scanner - xtal £120.75
 SL 1600 2m 16 channel scanner £39.50
 FRG 7700 The latest from Yaesu £389.00
 R 517 Air band portable-tuneable & xtal £49.45
 SX 200 26-514MHz scanner, AM and FM £235.00

ICOM

IC 2E 2m handheld-synthesized £159.00
 IC 240 2m 10W mobile £169.00
 IC 255E 2m 25W scanning mobile £255.00
 IC 260E 2m Multimode mobile £339.00
 IC 251E 2m Multimode base station £479.00
 IC 215E Supplied with S20, 22, R0-9 £149.00
 IC 402 70cm s.s.b. portable £242.00
 IC 202s 2m s.s.b. portable £169.00
 IC 720 0.1-30MHz 100W transceiver, all bands, SSB/CW/Rtty/AM £795.00
 IC 451E Latest 70cm multimode base station £579.00

All Icom accessories available
 Aerials - J. Beams - Revco - Hokushin - G. Whip.
 Power supplies - microphones - plugs - sockets - dummy loads - lightning arresters etc all available.

ACCESSORIES

RM 940 Infra Red remote mike £45.00
 CN 1001A Automatic ATU and SWR £129.45
 CN 620 Cross pointer SWR 1-8-150MHz £52.81
 CN 630 Cross pointer SWR 140-450MHz £71.00
 CN 650 Cross pointer SWR 1-2-2-5Ghz £95.00
 T 3170L 3-5 150MHz SWR £12.94
 RW 151D Watt meter 0-150W, 0-500MHz £69.00

Rotators
 NS 200 VHF - UHF Beams £29.50
 AR 40 For mini Beams £59.80
 DR 7500X For 3 element HF Beams Preset controller £98.04
 DR 7600X Up to 2 element 40m Beams Preset controller £135.00

Many other models available + 5 core-6 core cable UR43 - UR 67 - twin feeder.
 Full range of MICROWAVE MODULES L.A.R. and S.E.M. products available.
 Full range of R.S.G.B. Books stocked.

COMPUTERS

New CBM 8032 80 column + 24k Rom £1029.25
 New CBM 8050 dual drive £1029.25
 CBM 2001-8 8k, including cassette £435.88
 CBM 3008 8k. Query keyboard £457.70
 CBM 3016 16k, Green screen £569.25
 CBM 3032 32k, Green screen £718.75
 CBM 3022 80 Column dot matrix printer £440.45
 CBM 3040 Dual drive mini floppy £718.75
 CZN Cassette deck £56.98
 KIM 1 The ideal teaching aid £106.95
 KIM 45 Mother Board £74.75
 KIM 3B Ram Board £110.40
 KIM 4S Mother Board £74.75
 All P.E.T. leads and accessories and manuals available + full range of NASCOM and APPLE products.
VIDEO GENIE-EG 3003 Tandy level 2 compatible, with 16k Ram, integral cassette, boxed and ready to go, only £325 inc. VAT.
 Full range of consumables (disks, cassettes, labels, ribbons etc) available + Petsoft - Commodore - BSF - Monitor and everything from Space Invaders to a complete Business System. Also a large range of books in stock.
 32 K. Version with sound box £399.99.

Please phone for quotation on any items not listed.

ALL PRICES INCLUDE VAT

PART EXCHANGE

Let us sell your rig for you - no commission charged if you purchase new rig from us.
 Monday-Saturday 9.30am-5.30pm.

AUTHORISED

 DEALER

58 HIGH STREET, NEWPORT PAGNELL, BUCKS. ● TEL. 0908 610625

TRIO




YOUR SOMMERKAMP IMPORTER

1 Railway Road, Blackburn, Lancs. Telephone: 51842.
(Telephone Evenings: Bolton 592929 G4GHE)

SOMMERKAMP TS280 FM 80 channels, 2 metre FM Mobile Transceiver

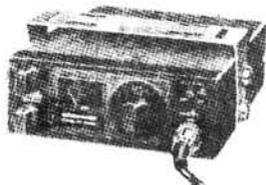Rapid channel change with illuminated read-out, 25KHz steps. Complete with mobile mount and microphone (which also incorporates a volume control). Two versions available - 50W output, switchable down to 2 watts at £199, and 10W output switchable down to 1 watt at £159. Can be used as base station with a Sommerkamp Power Supply.



SOMMERKAMP TS802

80 channel, 2 metre FM Hand-held Transceiver.

Fully synthesized, switchable reverse scan, digital readout, repeater shift, tone burst. 2 watts output switchable down to 0.2 watts. Price includes leather carry case, flexible aerial and a free battery charger - a bargain at £129. Set of Nicads £10. £2 post, packing and insurance.

SOMMERKAMP

FRG7 Receiver.....	£188
FRG7700 Receiver, inc. 12 memories.....	£379
FT2772D HF Transceiver 160-10 metre.....	£599
FT767 HF Mobile Transceiver 80-10 metre.....	£499
FT480 2 metre Mobile Transceiver.....	£359
FT227RAE 2 metre Mobile Transceiver.....	£255
FT307CBM HF Transceiver 160-10 metre.....	P.O.A.
FT902DM HF Transceiver 160-10 metre.....	P.O.A.

Will be at most of the rallies in 1981 - come and see us.

We also stock genuine Sommerkamp accessories:

Power supplies, SWR bridges, power output meters etc.

SEND FOR DETAILS - LATEST PRICES

All prices include VAT. Barclaycard, Access, Part Exchanges etc.

FIT A DIGITAL DISPLAY TO YOUR FRG7 OR SRX30.

These units come complete, with only three wires to connect. The FDU7 for the Yaesu FRG7 can be fitted in place of the KHz dial, or can be supplied for external use. (Please state when ordering) The FDU3 for the SRX30 is supplied for top of the set use only.
 (Full Fitting Instructions are supplied.)

(FDU7) for FRG7

@ £44.77

(FDU3) for SRX30

@ £44.77

We also manufacture an R.T.T.Y. Converter.

The MB6R (Receive only) and the MB6R/T (Receive/Transmit).

We supply these units with single or double current loops for connection to teleprinter To Order. T.T.L.-C-MOS Logic Levels and Oscilloscope Outputs are provided. Dimensions (84x304x210).

(MB6R Double or single current) @ £77.96

(MB6R/T Double or single current) @ £83.25

(All Units are fully Guaranteed, and come complete)
 (No extras needed)

(All prices inclusive of postage and V.A.T.)

(Payment by P.O., Cheque or Access)

**B. BROOKES ELECTRONICS, 69 Leicester Street,
 NORWICH NR2 2DZ, ENGLAND.
 Tel: 0603-24573.**

STEPHENS-JAMES LIMITED

COMMUNICATION ENGINEERS

47 WARRINGTON ROAD, LEIGH WN7 3EA

ENGLAND
 Telephone (0942) 676790

Everything for the Short Wave Listener.

We stock receivers and listening aids by most of the world's leading manufacturers. Full range of VHF receivers—transceivers. Mobile equipment pre-selector—filters—antennas. Stabilised power supplies from 2 to 20 Amp.

Antenna switches—converters. Aluminium masts—clamps. Antenna rotators.

TRIO R1000 Receiver

Digital readout general coverage receiver covering 200KHz to 30MHz with a P.L.L. synthesiser. Also incorporating quartz digital clock. £285.20.

TRIO R820

Amateur Band Receiver £690.00.

Send for full specifications of our full range of receivers covering from 200KHz to 520MHz. Our secondhand equipment changes daily. Send SAE for up to date lists. Part exchange welcome. Good clean Equipment bought for cash.

Drake

R7 Solid state receiver digital readout 1-5 to 30MHz £989.

J.R.C.

NRD515 Solid state synthesised digital receiver 100KHz to 30MHz. £948.

Bearcat

220FB Receiver Scanning Receiver. 66-88MHz-118-136MHz. 144-148MHz-144-148MHz. 420-450MHz-450-470MHz. 470-512MHz £258.75.
 Send S.A.E. for details of our range Aircraft Band Receivers.

air test

USER REPORTS ON SETS AND SUNDRIES

MM2000 RTTY to TV Converter


This unit, which has recently been designed and developed by **Microwave Modules**, is the quickest way for the short-wave listener and licensed amateur to receive RTTY, Murray coded and amateur band ASCII signals (the standard types of transmission used by amateurs). The Converter will receive and convert the four baud rates at present in use by commercial and amateur users. This receive-only device may subsequently whet the appetite for the transmitting scene with its exchange of contacts with other radio amateurs.

The MM2000 converts RTTY signals which then appear, suitably modulated, on u.h.f. TV channel 35 i.e., 583MHz in the commercial TV band. All that is required to use the unit is a signal from a suitable radio receiver and a d.c. supply of 12V. In the reviewers case the output from the receiver is taken from the "record" socket of a Trio R-1000 general coverage receiver. This output is at 30mV, more than ample for this unit; the signal is unaffected by the position of the volume control, so enabling monitoring via the speaker or headphones. One point found with the receiver is that the use of a filter, such as the Datong FL2, narrows the bandwidth and prevents the QRM, ever

present on most amateur band RTTY. The minimum bandwidth is 2.7kHz, a little too wide for single-signal reception, which gives the best "copy" on the TV screen.

To return to the Converter. Signals from the receiver are filtered and amplified before being passed to the discriminator: accurate tuning indication of the signal being by means of two l.e.d.s. This method of alignment is very advantageous, when using an ordinary home constructed terminal unit and teleprinter, because overprinting will occur if the receiver is incorrectly tuned. In the Converter this is prevented by the incorporation of an automatic carriage return on RTTY signals. An innovation with this unit is the provision of an "auto-sensing" unit which enables it to sense the correct speed of the code transmission and indicate this on the appropriate l.e.d. for that speed. Manual override selection is also provided, if required.

Should an alternative, special code, be required, this is easily accomplished and involves re-programming of the internal EPROM by loading in a suitable program from cassette tape. So that the unit can be used in countries using positive sync. on the TV signal, a rear-mounted toggle switch is provided, giving instant access to either standard. This switch is a feature recently introduced by the manufacturers, to replace previous "hard-wired" internal links.

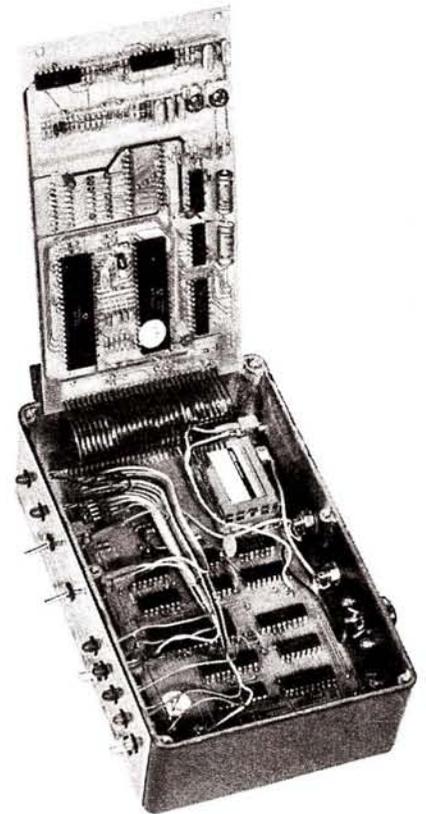

The picture information consists of 16 rows, each containing 64 characters and when using a 14in screen TV the characters are easy to read. The receiver used for driving the Converter should be stable and not prone to drift, otherwise continual adjustment of the tuning and b.f.o. will be required to retain the information. It is possible to copy both AFSK and FSK signals with this unit. These signals are easily recognisable: a warbling tone for AFSK and frequency variations for FSK. The actual frequency is varied, noticeably so when the receive b.f.o. is switched on.

Latest state-of-the-art techniques are used in the design of the Converter which employs two microprocessors and 21 i.c.s. All the circuits are built into a black enamelled aluminium die-cast box measuring 187 x 120 x 53mm, and mounted on two glass-fibre p.c.b.s using a plug-in connector technique which makes servicing that much easier.

Connections to the u.h.f. TV monitor and audio input from the receiver are



made by means of phono sockets. The power supply input of 12.5V, at approximately 1A, is by means of a DIN socket. Plugs are supplied with the unit for connection to these sockets.

Operating Procedure

Having powered-up, or cleared the system, the user is presented with a heading line containing the information "Microwave Modules MM2000 programme 3.4". The 45.5 baud l.e.d. illuminates and the Converter is ready to receive Baudot coded signals at this rate. Pushing the SELECT button, steps the speed indicators through 50 and 75 bauds and eventually ASCII together with one of the three-speed l.e.d.s giving sequentially 110, 150 and 300 baud ASCII coded signals.


Further pushing of the SELECT button beyond the 300 baud ASCII point will force the unit into the AUTO SENSE mode for Baudot signals. At all stages user indications of state are provided by front panel mounted l.e.d.s.

During reception of noisy signals or with incorrect speed or shift settings, the microprocessor sampling the incoming signal may not verify the stop bit in its correct position. In these circumstances it will print a full stop on the screen. With the case control in the "on" position and when the unit is receiving Murray coded signals, the microprocessor controller will automatically force the letter shift after 15 consecutive different characters in figure shift. By switching the case control OFF this feature can be overridden, allowing response to letter and figure shift codes as normal.

To prevent the rapid replacement of a previously displaced page, the latest software allows only two consecutive carriage return line-feed operations, when receiving Murray coded signals.

The MM2000 is available at the VAT inclusive price of £169 direct from **Microwave Modules Ltd., Brookfield Drive, Aintree, Liverpool L9 7AN. Tel: 051 523 4011**; or through their many appointed agents.

AR 245 2m Hand-held Transceiver

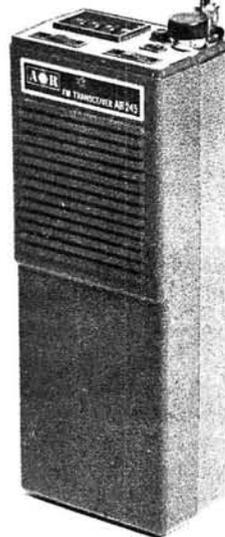

The latest contestant in the 2-metre hand-held battle stakes is the AR 245 fully synthesised transceiver.

At five watts output this rig must be the most powerful hand-held on the market and, although not quite as small as the IC2E reviewed last December, in terms of watts per cubic centimetre it is an amazing performer.

The transceiver is compact, with the rechargeable battery pack fitted inside the plastics case. Unlike other hand-helds the battery pack is not removeable and this has the disadvantage of not allowing the user to carry a spare fully-charged pack around.

The operating controls are on the top of the case except for the repeater shift and power level switches which are on the back.

The p.t.t. switch is a large pad on the side with the tone-burst button in its centre. This proved to be rather awkward to use as the p.t.t. switch required quite a large pressure to operate, while pushing the tone button at the same time for half-a-second or so and then releasing it without relaxing pressure on the p.t.t. needed some effort. However this was soon mastered and the rig was quite easy to use.

The antenna provided is a telescopic whip which screws into a plain threaded bush on the top. A helical whip is available as an extra if preferred, but the telescopic whip proved to be more than adequate and also very convenient as it retracted completely into the set top.

HF-60 Handy Frequency Counter

The Model HF-60, frequency counter, has recently been made available in the UK by **Low Electronics** of Matlock.

The unit is a self-contained, hand-held battery powered device and is capable of frequency measurements in the range 1kHz to 55MHz. Accuracy is quoted as 0.003 per cent and our



bench tests indicate stability to be of a high order for an instrument of this type.

Signal sampling is carried out by means of an extendable telescopic whip antenna, provided as standard,

and stored internally for ease of transportation. The proximity of the antenna to the signal source, is determined by the anticipated level and quaintly described by the instruction leaflet: "when transceiver is with strong power you can be 10m away"!

Applications, quoted by the manufacturer, include amateur h.f. band emissions, radio control models, including the new aircraft-only band on 35MHz and, if and when available in the UK, CB radio.

Internal construction is kept to the briefest minimum, all components being mounted on one single-sided p.c.b. Four i.c.s and approximately twenty discrete components provide the signal processing and five-digit, 7-segment display drive. The remaining 50 per cent of the case is occupied by four AA size dry-cell batteries.

The HF-60 has found itself used for a variety of measurements in our workshop, not least of which was diagnosing the demise of a recent radio controlled Christmas present.

The only problem encountered in operation concerned the position of the side-mounted ON-OFF slide switch which had inadvertently been enabled when the unit was replaced in its cardboard box. The moral is, leave it where you can see it.

The HF-60 frequency counter is currently available at the very reasonable price of £36.50 including VAT from **Low Electronics, Chesterfield Road, Matlock, Derbys. Tel: 0629 2817**, to whom we offer our thanks for the loan of the review sample.

continued on page 73 ▶▶▶



Amateur Radio Shop

Tel: 20774

4 Cross Church Street
Huddersfield
West Yorkshire

ANNOUNCEMENT

LANCASHIRE AGENT. Ted Whittaker G3UUA at 414 Rossendale Road, Burnley, is now our man in Lancashire.
NEW MEMBER OF STAFF. Normal Hodson G3WAH has joined our company, and will be in charge of sales and service of ham equipment etc.

NOW IN OUR 20th YEAR—ESTABLISHED 1960


NEW G4MH MINI BEAM

Price: £77.50 +£2.50 p&p in UK
PACKAGE: beam, rotator, 15m coax UR43,
15m 5 core — £145.00

Designed and manufactured in the UK

SPECIFICATION	
Element length	11 feet
Boom length	60 inches
Turning radius	7 feet
Operating frequencies	10m, 15m, 20m
Forward gain (ref D pole 1:00)	3.6 dB
SWR at resonance	1.5 to 1:00 maximum
Power rating	1400 watts PEP
Input impedance	50 ohms
Wind resistance	80 mph
Weight	14 lbs
Rotator requirements AR40	

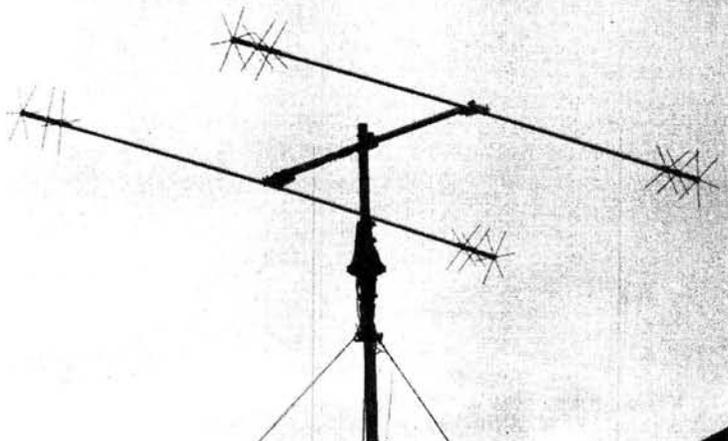SAE for details, Coax UR43, UR67 and 5 core available



IN STOCK —

Yaesu — Trio — Sommerkamp — Bearcat — S.E.M. — J-Beam — G-Whips

FACILITIES —

Instant HP — CREDITCARD — Barclaycard — Access

SECONDHAND —

Always large stocks, ever-changing — SAE for lists — We buy secondhand gear, cash

YAESU —

FT7B **£399** — FT107 **£690** — FT901DM **£799.25** — FT101Z **£488.75**
FT101ZD **£569.25** — FT707 **£499** — FT480 **£359**
FRG7 **£199** — FRG7000 **£299**

NEW! —

FRG7700 now in stock — **£308**

TRIO —

TS520SE **£437** — R1000 **£298** — etc

NEW! —

2 metre 5/8 wave mobile antenna, 3.5dB with mag mount — only **£12** complete (Whip inc balun, mag mount, PL259 fitted)

FULL RANGE —

SWR inds — coax — keys — books — etc

ALSO ON DISPLAY —

MICROPROCESSORS — Apple — Sharp — Video Genie — PET — Super Board — Sorcerer

PX WELCOME —

We have Hi-Fi — Ham Radio — Computers — What have you?

OVER 2000 sq.ft SHOWROOM AREA

Visit our Stand at the:

Belle Vue rally Manchester
White Rose rally Leeds

Drayton Manor Park rally
(Nr Tamworth, Staffs)

Our Staff: Jim G4MH, Ray G810F, Chris G8PUT, Ted G3UUA, Norman G3WAH

Open Mon-Sat 9.00 am to 5.30 pm, late night Thursday till 8.00 pm.

Send 50p for our comprehensive catalogue. Trade enquiries welcome.

PW1

Boat Engine Hours Counter

F. C. JUDD



Owners of power-driven boats and particularly those with outboard engines are no doubt aware of the importance of regular maintenance and oil changing, etc. For example, the average outboard engine requires a change of gear box oil after a specified number of hours running otherwise damage could result, and repairs and replacement parts are very expensive. Regular spark plug gap adjustment or change of plugs is also necessary as well as greasing and other items of maintenance essential for smooth and reliable running.

All boat engines have to operate under much more arduous conditions than the average motor car engine and as any experienced owner of a power-driven boat will verify, boat engines always seem to fail at the wrong time and in the wrong place, often with the possibility of putting life at risk. Such failures are more often than not due to lack of care and appropriate servicing.

Keeping a record of engine hours run is simple enough if one remembers to do it. Better, therefore, to have a device that doesn't forget and which in the end will more than pay for itself in savings made on repairs.

A version of the engine hour counter described in this article has been used by the writer for several years on a power craft fitted with twin outboard engines. The circuitry has been updated and a suitable five-figure reset counter is readily available. It will operate from a 9V PP9 dry battery or from a 12V supply such as the boat lighting supply.

The Circuitry

The circuit is shown in Fig. 2 and consists of a 555 timer i.c. triggering a pulse circuit Tr1, Tr2 and Tr3 which, in turn, actuates the counter. The counter has five figures, the first three being used to indicate whole hours up to 999 and the two remaining for one-tenth and one-hundredth of an hour respectively. The counter will therefore record to three figures and two decimal places from 000.01 up to 999.99 and can be reset to 000.00 after recording any required number of hours up to 999.99.

The time constants for the 555 consist of R9/R3 with R2 and the two 10 μ F tantalum capacitors C3 and C4. The timing and duty cycle duration sequence is illustrated in Fig. 1 and begins with a negative going pulse from

IC1. This is inverted by Tr1 and drives Tr2, Tr3 on with a 100 millisecond pulse every 36 seconds or 0.01 of an hour. The short duration pulse of 100ms is essential to the operation of the specified counter.

The circuit will operate at any voltage between 9V and about 13V but R9 must be set to obtain the 36-second interval with whatever operating voltage is used. Inaccuracy in timing due to falling battery voltage or temperature effects, etc., will not amount to more than plus or minus one hour in 100 hours, which is nothing to worry about.

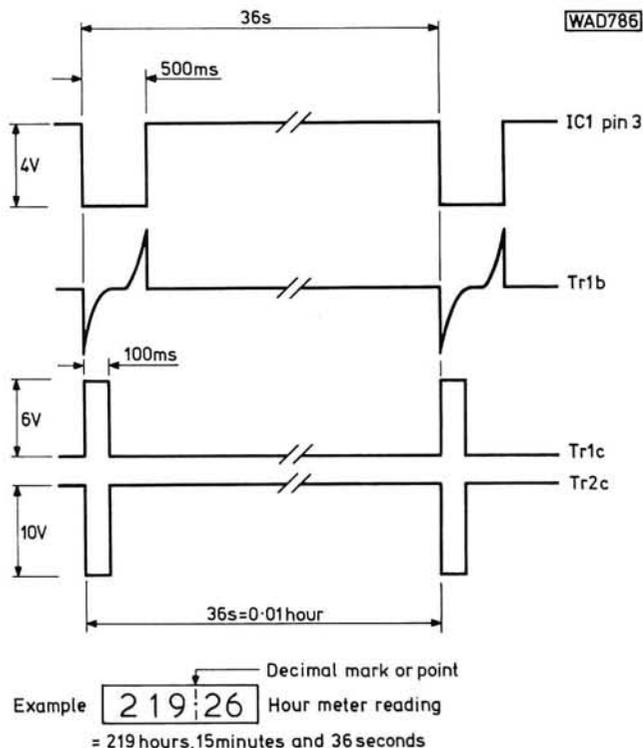




Fig. 1: The timing and duty cycle duration sequence for the counter

Construction

The box chosen for housing the circuitry and counter is also just large enough to accommodate a PP9 battery. A smaller box could be used if the counter is to be operated from an external battery.

Position and mounting of the circuit board and counter within the box is shown in Fig. 3. The case is fitted with right-angled brackets so the unit can be bulkhead mounted. Note that what is normally the lid of the box now becomes the rear panel.


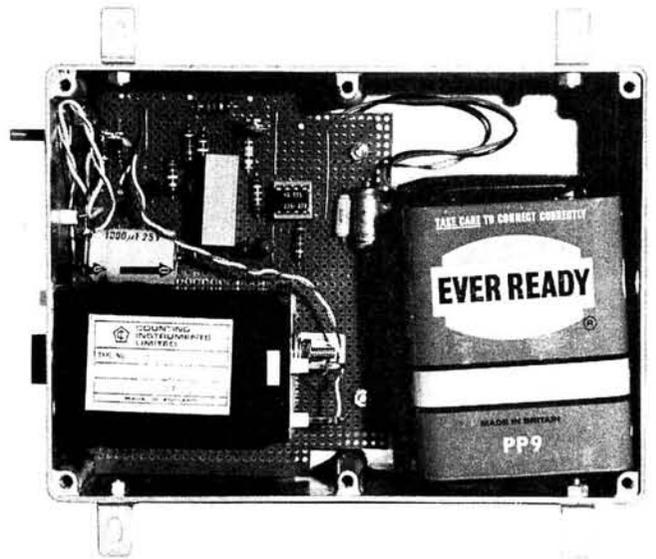
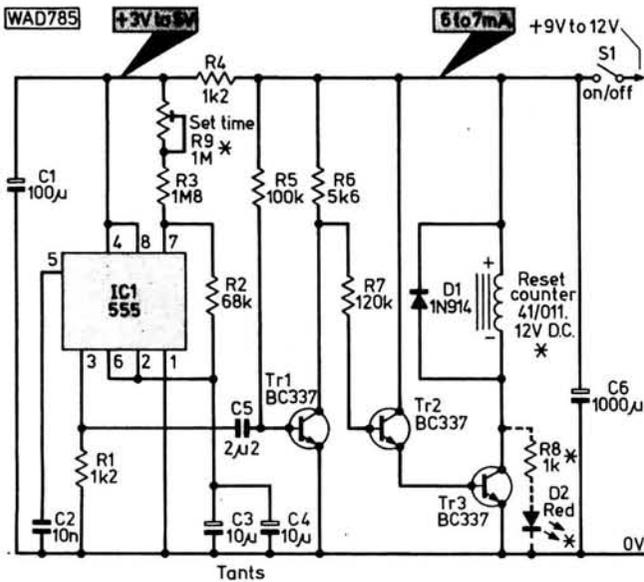
Circuit board tracks and component positions are shown in Fig. 4. Plain matrix board and component-to-component wiring may be used if desired by following the layout given.



Internal view of the prototype engine hours counter. This unit was built using plain matrix board instead of the p.c.b. which was developed from the original layout

Fig. 2 (left): The circuit diagram of the engine hours counter

Fig. 3 (below): The unit is constructed in a diecast box as shown in this drawing

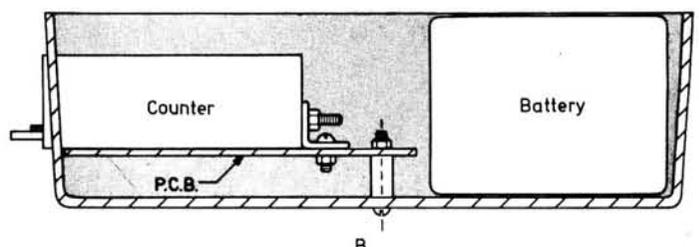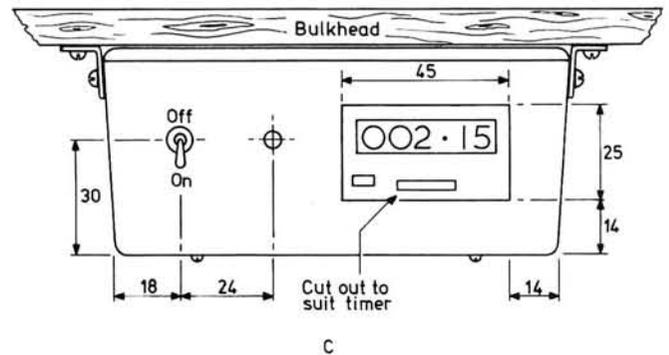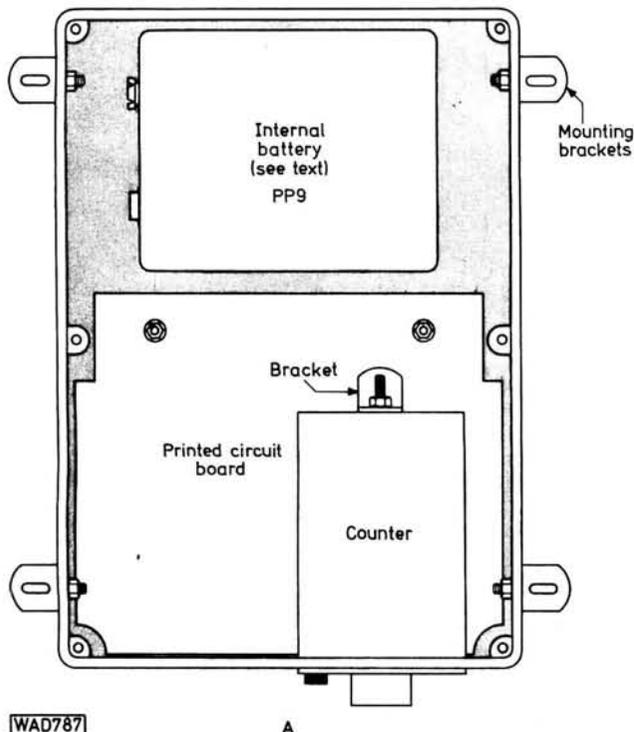

BOAT ENGINE HOURS COUNTER


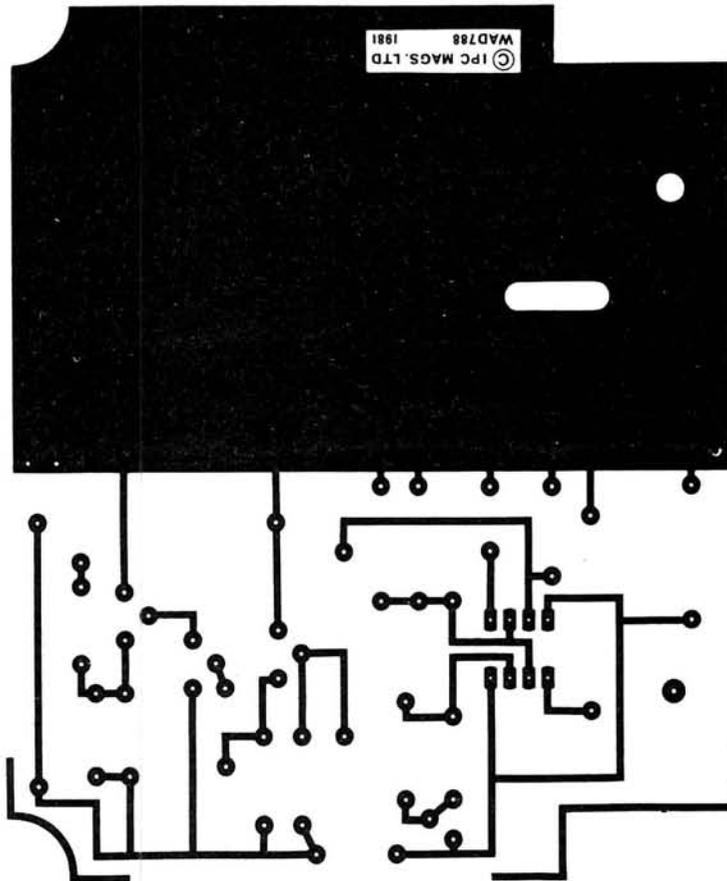


Fig. 4 (above): The copper track pattern of the p.c.b. shown full size. Fig. 5 (below): The component placement for the p.c.b.

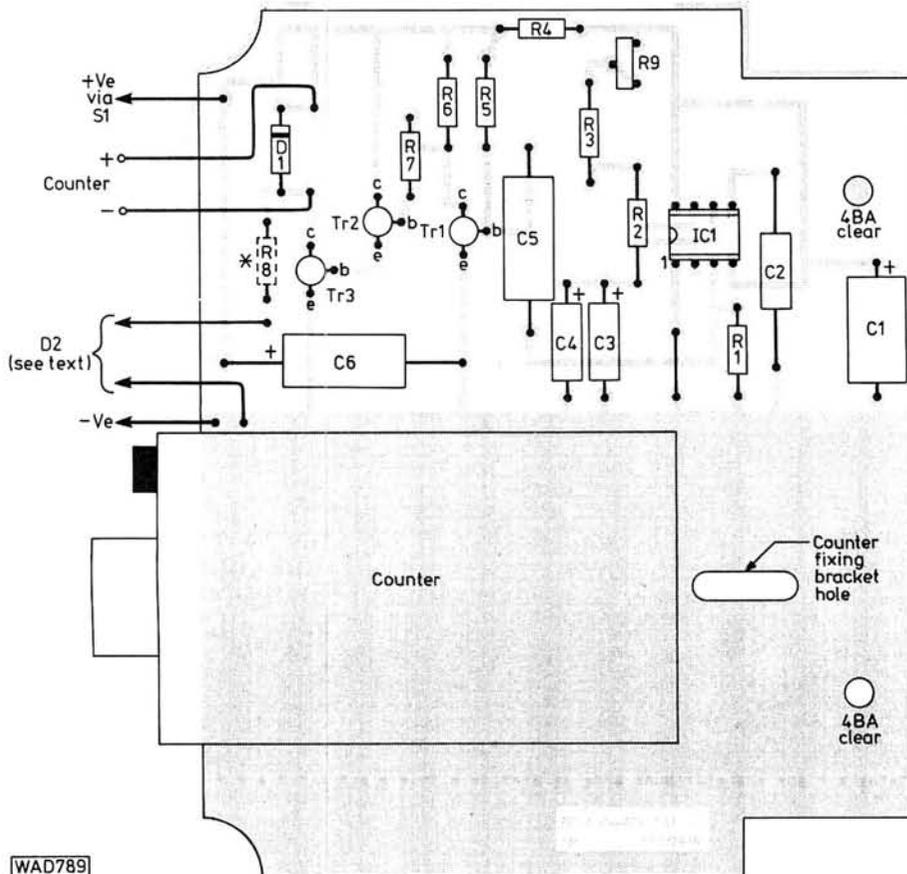

WAD789

★ components

Resistors		
<i>¼W 5% carbon film</i>		
1kΩ	1	R8 (see text)
1.2kΩ	2	R1,4
5.6kΩ	1	R6
68kΩ	1	R2
100kΩ	1	R5
120kΩ	1	R7
1.8MΩ	1	R3
<i>Miniature Preset Vertical Mounting</i>		
1MΩ	1	R9
Capacitors		
<i>Polyester</i>		
10nF	1	C2
2.2µF	1	C5
<i>Electrolytic</i>		
100µF 16V	1	C1
1000µF 16V	1	C6
<i>Tantalum bead</i>		
10µF 16V	2	C3,4
Semiconductors		
<i>Diodes</i>		
IN914	1	D1
Red l.e.d.	1	D2 (see text)
<i>Transistors</i>		
BC337	3	Tr1,2,3
<i>Integrated Circuits</i>		
555 timer	1	IC1
Miscellaneous		
Diecast box 171 × 121 × 55mm; Counter, 5 figure reset (Counting Instruments Ltd.) Type 41/011, 12V; Miniature s.p.d.t. toggle switch; printed circuit board.		

CONSTRUCTION RATING **Beginner**

BUYING GUIDE

Readers should have little difficulty in obtaining the electronic components for this useful project. The special counter (Type 41/011 12 volts) is available from Counting Instruments Ltd., 5 Elstree Way, Boreham Wood, Herts WD6 1SF. *Practical Wireless* should be mentioned when ordering.

APPROXIMATE COST **£22**

Operation

If the counter is operated from a 9V internal battery then it is suggested that the optional l.e.d. indicator is not used as it consumes current and would make the total current drawn by the circuit in excess of 10mA. Hence the resistor R8 and the l.e.d. D2 are marked optional although pads for R8 are provided for on the circuit board. If the counter can be operated from a 12V battery (boat lighting battery) then the l.e.d. can be fitted. It will flash *off* each time the counter clicks over. If the boat is equipped with ignition switch type self-start then the voltage for the counter could be obtained via this in which case it will operate automatically when the engine is running. However, the preset R9 must be adjusted according to the voltage used. Set at about halfway and time the counter operation. Increase or decrease R9 so that the counter clicks over once every 36 seconds or 0.01 of an hour. The more precise this timing the more accurate will be long-term readouts.

AIR TEST—AR 245

▶▶▶ continued from page 68

Frequency selection is by a three-digit thumbwheel switch set into the top panel and proved to be easily operated. The final 5kHz segment of the frequency is set by a small slide switch alongside the thumbwheels. For repeater operation the -600kHz shift is set by a slide switch on the rear panel. A +600kHz shift can also be set. The coverage is 144.000MHz to 147.995MHz in 5kHz steps.

For use with a linear amplifier or different antenna system the r.f. output is also fed to a miniature jack on the top

adjacent to the screwed bush.


The ON-OFF switch is operated along with the volume control and, like the squelch is a recessed edge operated knob. A red l.e.d. just above the speaker grille gave an indication of the operation of the p.t.t. switch and also of low battery state. A simple mains charger is supplied as standard equipment and a charging lead to fit a car cigar lighter is available.

The r.f. power output is switchable between a fixed 5W on high power and an internally adjustable 0.5W to 1.5W

on the low power setting.

In use the unit proved to be sensitive on receive and with the 5W available on transmit allowed operation through GB3SC over paths of almost 20 miles with no difficulty.

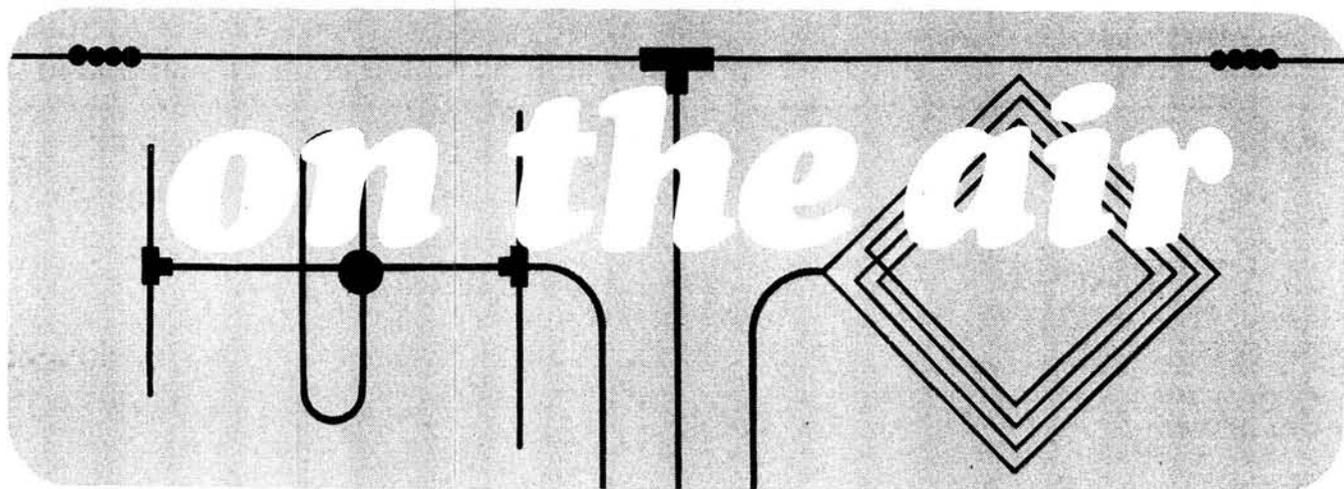The AR 245 measures 180 × 70 × 50mm and weighs 500g complete. At the current price of £178 including VAT it is available from **Lowe Electronics, Chesterfield Road, Matlock, Derbys. Tel: 0629 2817** to whom we offer our thanks for the loan of the review unit.



Amateur Bands

by Eric Dowdeswell G4AR

Reports to: Eric Dowdeswell G4AR
Silver Firs, Leatherhead Road,
Ashted, Surrey KT21 2TW.
Logs by bands in alphabetical order.

Among the monthly grumbles and grizzles that reach me in the mail, the most prominent is that concerning the QRM to amateur stations in the 80m band from non-amateur stations. It does not seem to be realised that the amateur's "rights" vary with the band in question, from being a primary service with exclusive rights to a secondary service sharing a band with one or more other services.

A very interesting exercise for the newcomer, and even for those not so new to amateur radio, is to study the frequency limits of amateur bands not only in the UK but in other countries, particularly the United States. In the US, for instance, there are sub-divisions within bands for different classes of licence and for c.w. and telephony operation that are part of the legislation. In the UK there are no legal sub-divisions, the separation between c.w. and telephony having been established many years ago and respected ever since by what is essentially a "gentleman's" agreement. In fact, they have been copied by almost everyone else!

The overall band limits are determined at ITU conferences from time to time, the last one in 1979 coming up with three new h.f. bands, to everyone's surprise! Just what part or parts of a band are allocated to an amateur is a matter for the government or administration concerned. The ITU regulations are littered with hundreds of footnotes making minor amendments to the standard allocations in order to satisfy the demands of many different countries. The Top Band around 160m probably has more variations from country to country than any of the others, with some amateurs allowed the whole spectrum and others only very narrow bands of a few kilohertz, and generally on a secondary basis to safeguard what an administration regards as a more important primary service.

The 80m band in particular is shared with several other services, hence the QRM, and where the amateur service is a secondary one then the amateur is supposed to ensure that he does not interfere with the primary service on that band. Whether he ever does I will leave to your imagination!

Still on 80m, many s.w.l.s do not realise that the US band runs up above our own UK limit of 3.8MHz to 4MHz where many US stations can be heard relatively free from QRM. But the mind boggles at the resulting complications in the US where five classes of licence are linked to separate sub-divisions for c.w., c.w. and telephony, and c.w. plus telephony plus SSTV!

Note should also be made of the practice of some countries of allowing their novice licensees to use the 10m band, the USSR and Australia being typical examples. However the callsign is usually distinctive. One of the best examples of voluntary amateur discipline occurs in the 160m band where US amateurs on c.w. call between 1800kHz and about 1810kHz, listening in what is termed the "DX window" between about 1825kHz and 1830kHz for European and other DX stations. This greatly enhances the chance of a contact with UK stations with their low power limit of 10W.

For those who would like more detailed information on the US bands and sub-divisions, the *Amateur Radio Operating Manual* from the RSGB is essential reading.

DXing

First letter from **S. Bowler** (Wakefield) who has discovered the joy of the amateur bands on his R-1000 receiver, KX2 antenna tuning unit, fed from a 46 metre long wire "mounted in the loft". Some loft, but perhaps it is folded around a bit! An outside vertical is being considered at present, always a good alternative to the conventional horizontal wire. Some of the DX logged included SV0AW/9 on Crete, VP9CP on 21MHz plus ZL3MF and CT2AP on 14MHz. The ZL3 was at 1900GMT over the short path.

David Warr BRS44127 of Weymouth, Dorset let his 9R59DS roam mostly over the 10m band driven by a G5RV aerial system, keeping an eye on the DX net on about 28880kHz run by G4CHP. Up came OA8CP, 6Y5DA, DU1DPC, J3AH, HK0FBF on San Andres Is, and FM7AV, while on 15m he captured XL3LON special event station in VE-land, FG0FOL/FS, 6W8AR, TG4NX and CP7HLX. The 40m band provided a nice one in H44DX, and ZL4BO with VK2AVA on 80m. Best catch was probably VR6TC on 20m.

Drake R-7 Synthesized, General Coverage Receiver



Model 1240

Full general coverage reception, 0-30 MHz, with no gaps or range crystals required.

Continuous tuning all the way from vlf thru hf. Superb state-of-the-art performance on a-m, ssb, RTTY, and cw - and it transceives with the Drake TR-7.

Price £879.75



R1000 £285.20 inc VAT

The R-1000 is a high class general coverage receiver covering 30 bands between 200KHz and 30MHz with a PLL synthesizer that incorporates all of Trio's sophisticated electronic technology developed over recent years.

Both digital display readout (1KHz resolution) and analog display (10KHz resolution) are provided for easy and accurate tuning.

The R-1000 also includes a quartz digital clock with timer, three IF filters, RF ATT and tone control, etc. to ensure the best receiving conditions for each mode.

Due consideration has been given to innovative design and compactness, making the R-1000 an incomparable station receiver for amateur radio operators, professionals, BCL's and SWL's, etc.

THE 2 METRE FM MOBILE TRANSCEIVER

TR7800 £268 inc VAT



The new TR7800 is the only 2 metre FM mobile transceiver. Its performance both in your car and shack has to be experienced to be believed. Power output is 25 watts, a needle bending signal. The rig has keyboard entry for fixed station use and for programming the 15 memories. When used with the up/down shift switch on the mike the 15 memories, each having a repeater shift facility, make mobile operation a sheer pleasure. The scan facility, both on memory and 25/5Kc on keyboard means no missed contacts. Five second hold on each occupied channel gives you time to identify the station before the rig moves on to the next QSO, press the mike switch and the scan instruction is cancelled. Add the priority facility and you have it, the only 2 metre FM mobile rig.

Bearcat® 220FB

With 4m, 2m & 70cm FM Amateur Bands

FREQUENCY COVERAGE . . . 66-88MHz FM; 118-136MHz AM (Aircraft Band); 144-174MHz FM; 420.45-512MHz FM. This coverage includes the 70cm; 2m; 4m FM AMATEUR BANDS. To programme this Receiver you simply punch in the frequencies you wish to monitor. To AUTOMATICALLY SEARCH MARINE FREQUENCIES YOU JUST PRESS ONE BUTTON. The Bearcat 220FB will also AUTOMATICALLY SEARCH the AIRCRAFT BAND.

Power requirements: 240v AC/12v DC. Accessories included in the price are Mounting bracket and hardware. DC cord and telescoping antenna.

£258.75 inc VAT. Delivery by Securicor



Importers & Distributors for Hy-Gain, CDE, Rockwell-Collins, Macrotronics Bencher, R. L. Drake, Ten-Tec, A E A, Bearcat, stockists of all Amateur & Computer Products

RADIO SHACK LIMITED
TELEX 23718

188 BROADHURST GARDENS, LONDON, NW6 3AY
TELEPHONE 01-624 7174

From the World-Record Joystick People! A REVOLUTIONARY ANTENNA THEY CALLED "IMPOSSIBLE"

THE JOYFRAME (Patent Applied for) Amateur Bands 3.5-30 MHz, plus 27 MHz (where legal) and "New" bands - ALSO 2m. band RECEIVE.

The ultimate in small package, poor QTH, versatile antennas. Comes in easily assembled package which makes up to a 21" x 21" x 21" (inches) triangle. The unit JUST STANDS ON TOP OF TX/RX! Two knob control - and is rotated by hand for directivity on 80m. Is omnidirectional on higher freq.'s and for many SW BC stations. Incredible low angle radiation. Tested at 2 watts (only) CW at our works - world wide contacts! "Soak test" with G2VF using only 30 watts has satisfyingly filled his log with world wide QSO's. Loop TRANSMISSION performance with such a small unit has, we believe, never been seriously contemplated before, but rather written off as "impossible". Years of research from the firm that produced the JOYSTICK VFA and related systems now offers the JOYFRAME to the amateur fraternity and is the answer to the "maidsen prayer" to everyone with a space problem. All the benefits of JOYSTICK products: substantially harmonic-free, low angle, efficiency, compact.

COMPLETE JOYFRAME (incl. ATU) £60.00
(or write - 14p - or phone for literature)

ANTENNAS (our regular lines)

THE JOYSTICK VFA (Variable Freq. Antenna)

● Only 230cm long, easily assembled and installed. ● Continuous tuning 0.5-30Mhz ● Omni-directional ● Substantially harmonic-FREE

SYSTEM "A" For the SWL or 160m. Tx. £48.55

One small antenna for 2m. band, 80/40/20/15/10m., + 3 "NEW" bands, 27 Mhz. CB Band (where legal). 500 w capability, no TVI creating harmonics. SWL's - SHORT WAVE BROADCAST BANDS AT THEIR BEST!

All this from the NEW PARTRIDGE

SUPERMATCH SYSTEM £82.00

Can be used from "impossible" locations, "no antenna space" locations, caravans, high rise blocks, adaptable for mobile!

The associated JOYMATCH

SUPERMATCH ATU £50.00

converts your existing JOYSTICK VFA to a SUPERMATCH SYSTEM and will match about every other HF band antenna!

RECEIVERS

Get on the air in seconds!

● FRG7700 plus FREE purpose built ATU worth £10.50 £298 (£376 with Memory) ● FRG7 plus FREE wire aerial plus FREE ATU value £10.50 £184 ● Package "R.1" FRG7 + ATU + World Record VFA and FREE HEADPHONES £218 ● Package "R.3" FRG7700 (without Memory), VFA, ATU, Headphones £345.50 ● Package "R.4" FRG7700 (with Memory), VFA, ATU, Headphones £425.50.

TRANSCEIVERS ETC. We reckon we're offering LOWEST YAESU PRICES

Try phoning us for your PERSONALISED quote with or without Partridge antennas. For example: ● FT101ZD - only £559 ● FT902DM - only £795 ● FT7B - only £395.



JUST TELEPHONE YOUR CARD NUMBER

0843 62535 (ext 5) (62839 after office hours) or send 14p stamp for FREE literature. Prices correct as at press. NOTE our prices are always INCLUSIVE OF VAT, carriage. Prompt service too, goods usually despatched WITHIN 48 HOURS!

5 Partridge House,
Prospect Road, Broadstairs, Kent CT10 1LD
(Calls by appointment).




G3CED
G3VFA



BUILDING YOUR OWN HI-FI SYSTEM?

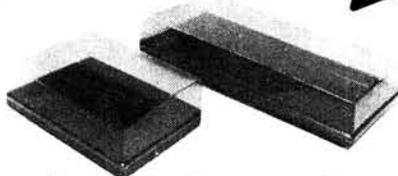Get a professional finish to your own tailor made system by purchasing a smoked acrylic lift-off lid with contrasting black ABS leather grained base direct from the manufacturer by post.



A

B

INTERNAL SIZES

Model A

Lid: $17\frac{1}{2}'' \times 12\frac{1}{2}'' \times 3\frac{1}{2}''$
tapering to 3".
Base: $17\frac{1}{2}'' \times 12\frac{1}{2}'' \times 3''$.

Model B

Lid: $31\frac{1}{2}'' \times 14\frac{1}{2}'' \times 3\frac{1}{2}''$.
Base: $31\frac{1}{2}'' \times 14\frac{1}{2}'' \times 2\frac{1}{2}''$.

State model required and send cheque or P.O. for the amount quoted (VAT & Postage paid) to:-

TAURUS PLASTICS LTD

2 CHARLES ST.
WALSALL
WEST MIDLANDS
Tel. Walsall 644113

MORSE TUTOR

The uniquely effective method of improving and maintaining Morse Code proficiency. Effectiveness proven by thousands of users world-wide.




- ★ Practise anywhere, anytime at your convenience.
- ★ Generates a random stream of perfect Morse in five character groups.
- ★ D70's unique "DELAY" control allows you to learn each character with its correct high speed sound. Start with a long delay between each character and as you improve reduce the delay. The speed within each character always remains as set on the independent "SPEED" control.
- ★ Features: long life battery operation, compact size, built-in loudspeaker plus personal earpiece.

Price £49.45

ACTIVE RECEIVING ANTENNAS

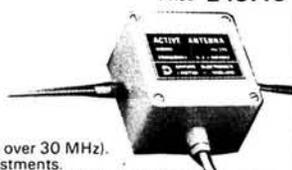Datong active antennas are ideal for modern broadband communications receivers - especially where space is limited.



- ★ highly sensitive (comparable to full-size dipoles).
- ★ Broadband coverage (below 200 kHz to over 30 MHz).
- ★ needs no tuning, matching or other adjustments.
- ★ two versions AD170 for indoor mounting or AD370 (illustrated) for outdoor use.
- ★ very compact, only 3 metres overall length.
- ★ professional performance standards.

Prices: Model AD170 (indoor use only) £42.55

Model AD370 (for outdoor use) £56.35

Both prices include mains power unit.

VERY LOW FREQUENCY CONVERTER

If your communications receiver gives poor results below 500 kHz Model VLF is the answer.

- ★ Connects between antenna and receiver input.
- ★ Converts signals between DC and 500 kHz to the range 28 to 28.5 MHz with low noise and high sensitivity.
- ★ Crystal controlled for high stability.
- ★ Quality construction in diecast aluminium box (size 112 x 62 x 31mm), SO239 connectors, LED indicator, in/out switch.
- ★ Operates from internal 9 volt battery or external supply (5-15 volts DC).

Price: only £25.30

Our full catalogue plus further details of any product are available free on request.
All prices include VAT and postage and packing.



**DATONG
ELECTRONICS
LIMITED**

Spence Mills, Mill Lane,
Bramley, Leeds LS13 3HE
England.
Tel: (0532) 552461

In Northchurch, Herts, **Jonathan Kempster** BRS45205 has dumped his Vega set for a nice FRG-7 second-hand from local G4DRA which ought to set him on the path for some real DX, like ZL2S, JY9FW, HP1XOG, CO2RX and 8P6GG on 28MHz, with 14MHz dishing up CR9CT, DU6JM, and HS1AMM, all from dipoles on each band. At the moment O-level exams are keeping Jonathan away from his RAE studies, but I'm sure he knows which is the more important.

Colin Frankland BRS45342 has moved QTH about three miles in the Hull area to a pre-nuptial house where he managed to organise a 27 metre long garden in place of the previous indoor arrangements. Temporarily he has a 23 metre long wire and found a big improvement on the i.f. bands as one would expect. Sole item of interest was 6U25YP in Khartoum celebrating 25 years of independence. Pity I didn't hear this one as I was there at the time, as ST2AR!

It's hello from **Bill Rendell** again, from Truro, and his HRO, considerably improved in performance seemingly by fitting separate r.f. and i.f. gain controls. The 40m band produced the inevitable ZL4BO. On swopping to 20m Bill found C6ANU, J6LOU, the SV0AW/9 who said QSL to Box 299, Iraklion, Crete, VP2AZE (Box 1203, St John's, Antigua), VP2MH and XT2AW. Bill also found the FG0FOL/FS on 15m with FY7AN, J3AAC (QSL W2BJI), S8AAP, VK4NIC/3X (QSL W4FRU), VP5GT on Grand Turk, plus 9X5MH. Just to prove the HRO is no slouch even on 10m Bill logged CO2OM, and TU2IN with QSLs to K3HBP.

In Leeds **Basil Woodcock** is still pondering over a new receiver, considering both the FRG-7700 and R-1000. In the meantime his SRX-30 plus 40 metre long horizontal wire (oh, that it could be vertical!) and a.t.u., sought out VK4NIC/3X, 3B8AE/3B9 on Rodriguez Is, FG0FOL/FS from the YASME DXpedition (anyone NOT heard him?), and VP5STA/HK1 all on 10m s.s.b., sole interesting one on 15m being P29NAB. On 20m KH6ATI and TJ1AY appeared, with a nice one in AP2ZR on 80m. **Ed Baker** (Cramlington, Northumberland, took time off from editing ISWL mag *Monitor* to tell me about N6YK/VP2A heard on both 40m and 80m s.s.b., with the latter band also coming up with AP2ZR, A7XD, HI8RF, JA5ANP, J3AM, 8P6OS and 9V4VU, all on his SX100 and 20 metre long wire. 40m also saw FM0FJE, HC1FF, and 6W8AR, with 20m contributing FR0FLO, KC4MS and VU2RHK. For the lucky ones who may have copped JT0LAJ and FYU, Ed says to send cards to Box 180, Ulan Bator, Mongolia, and the best of luck! I shouldn't be so cynical since I have three JT QSLs for QSOs some years ago now!

Now to our two lively lads **John** and **Steven Goodier** in Marple, near Stockport, G4KUC and G4KUB respectively, who have given up s.s.b. operation with their FT101Z and now concentrate just on c.w! That really warms the cockles of my old heart! A 600Hz filter has been fitted to the i.f. stages for improved c.w. reception. I have suggested that they have a go in some of the c.w. contests that take place in the next few months. All good experience. Best worked so far on 21MHz with a vertical antenna is ZL2AP.

Dave Coggins in Knutsford, Cheshire, admits to over-doing it a bit over Christmas and the New Year and I'm not talking about DXing! Serious intentions are to get cracking on SSTV very soon. In the meantime VKs on 80m have been logged around 1900GMT with favourite spot on 3675kHz more or less, with VK2AVA, VK3CR, VK3XI, VK3BM, VK4AZX mostly working Europe and the UK. Dave keeps an ear open for Australian time signal station VNG on 7500kHz during the daytime and on 4500kHz in the early evenings as an indication of likely

conditions on the 3.5MHz and 7MHz bands. Both Bill Rendell and Dave mentioned what appeared to be a big aurora on December 19 when very short skip working was observed on the 10m band.

Other DX copied by Dave included CR9CT (QSL G3KDB), J20CN (QSL K2FV), J73PP, KG6DX, 3B8DB and 9G1DY on 10m. 15m turned up DU1CK, FK8CR and J3AE. Equally good DX, on 40m, included H44DX, J3AAE, KL7AY and OX3ZM with, finally on 160m c.w., it was HB9BZA, OH0NA and OL1BCJ.

The Clubs

Merion ARS. Following the January write-up on this club in *PW*, a technician from BBC Wales organised a live TV interview with Dave Morgan, now GW4KYZ, who spoke on amateur radio generally and the Merion club, followed by an inevitable question on CB matters. Since starting last year the club has five new GW4s, with five more taking the December RAE. Interested? then write to Dave at Penybont, Gellilydan, Blaenau Ffestiniog, Gwynedd.

Sunderland & District ARC. A new one for Sunderland, previously devoid of a club, meeting at the Brewery Yard, Westbourne Road, Sunderland on Monday evenings at 7.30pm. All interested in radio and electronics most welcome to come along to a programme that includes code classes and RAE instruction. Contact: Dave Holland, 17 Egerton Road, West Harten, South Shields or ring South Shields 551045.

Bury RS. Make a note of March 10, with G8GTP advising on getting started on the 23cm band being one of the regular second Tuesday of the month meetings at 7.30pm. On other Tuesdays it is code classes and practice and club constructional projects, with 25 attending present RAE lectures. Contact: Chris Marcroft G4JAG, 24 Lancaster Avenue, Ramsbottom, Bury or Ramsbottom (070682) 2168. The meeting place is Mosses Community Centre, Cecil Street, Bury.

Braintree & District ARS. First and third Mondays at 7.45pm, at Braintree Community Centre, Victoria Street, next to the bus station (the Nag's Head is not very far away!). On March 16, G4HFR discourses on Airfield Communications and Navigation Systems, and make an advanced note of the trip to Radio Orwell on May 28. Janet Storey, 33 Redwood Close, Witham, Essex CM8 2PL will be delighted to expand on the club's activities.

Worcester & District ARC. At least eight members got their tickets following last May's RAE. One got into the game following QRM from the Hon Sec's rig! Meetings Mondays at the Old Pheasant, New Street, Worcester at 8pm. Special note: mobile rally on July 12 will be at a new venue of Droitwich. Contact: Hon Sec Mike Tittensor G4EKG, 16 Durcott Road, Evesham, Worcs or Evesham 41105.

Chesham & District ARS. Recently resurrected, the club meets Wednesdays at 8pm, Chesham Whitehill Centre with negotiations under way for something permanent. New members and visitors will be welcomed with open arms but in the meantime contact Hon Treasurer Andy Scott G8PUC at 8 Lynton Road, Chesham or (02-405) 5625 or try a call over the air.

Grafton RS. This old-established club is moving home to the Five Bells, East End Road, Finchley, London N2 with second and fourth Fridays at 8pm to be noted. An extensive programme for the coming year is being formulated, but in the meantime more members are being sought. Have a QSO with John Thomson G8SYD on 01-959 8785 or drop a line to 70a Deans Lane, Edgware, Middx HA8 9NN.

Ipswich RC. Another group moving into new premises

by the time this appears. Second and last Wednesdays 8pm at the Rose & Crown, 77 Norwich Road, Ipswich with assurances that clubroom is detached from public bars and juniors just as welcome as anyone else. Club has many projects under way like RAE and code classes, but Jack Tootill G4IFF, 76 Fircroft Road, Ipswich IP1 6PX will gladly tell you all, or try (0473) 44047. Excellent club magazine *QUA* carries many articles on diverse aspects of amateur radio, the secret being the carrying of extensive advertising by both local and nationally-known radio dealers. Other clubs seldom seem to take advantage of this means of extra support.

Sutton & Cheam RS. Members are looking forward to the annual Dinner/Dance at the Woodstock Hotel, North Cheam, Surrey on Saturday, April 4, and by all accounts it ought to be quite a night. Next regular meeting is on Friday, March 13, when Dick Biddulph talks on safety in the shack, at the Sutton College of Liberal Arts. The annual constructional contest sees the judging on the 27th at the Banstead Institute. For more info on what happens where, contact G. Brind G4CMU, 26 Grange Meadow, Banstead, Surrey. (Thinks: Now that my office is in Sutton (IPC Business Press), I ought to drop in on this mob some time!)

Midland ARS. The University of Aston, Room 118, is the venue of a meeting on March 24 when Ray Withers G4KZH should be holding forth on repeaters at 7.30pm. A membership drive is under way so a note to G8ODT at 138 Hillside Road, Great Barr, Birmingham B43 6QN will get you all the details.

Exmoor RC. A series of projects for the younger and less experienced member is underway, like a code oscillator for the G8s wanting to get their G4s, all part of a programme of diverse club activities including club station G8SSS now on the air. Meetings 7.30pm every Thursday at Loughrigg, East Street, South Molton, but still awaiting her RAE result is secretary Pat Jemmison, Homedale, Brayford, near Barnstaple, N. Devon, or Brayford 327.

Wolverhampton ARS. Club's contest team took first place in September's 144MHz contest with call GW8BHH/P so v.h.f. enthusiasm runs high every Monday evening at 8pm at Neachells Cottage, Stockwell End, Tettenhall where club station is G8TA. March 9 is natter-night with the 16th devoted to organising the Wolverhampton Fiesta on May 28/30 next. More from John Cook G8EDG, 75 Windmill Lane, Castlecroft, Wolverhampton WV3 8HN.

Verulam ARC. Advance notice of a talk by no less than G3XAP on aerial systems for the l.f. bands, not to be missed on any account. Club contact Hilary Clayton-Smith G4JKS was delighted to see YL Column in the Jan *PW* but considerably deflated when it failed to appear in Feb! (Note: This is one of a series of new features, each appearing every three or four months. Ed.) Meetings fourth Tuesday at Charles Morris Memorial Hall, Tyttenhanger Green, Tyttenhanger, which is near to St Albans, around 7.30pm will do.

Exeter ARS. Second Monday sees the club at the Community Centre, St David's Hill, Exeter at 7.30pm and for March it is D. Sellars G3PVB holding forth on propagation matters. Locals can get update info on the EARS 2m network at 7.30pm on Tuesdays. PRO is Geoff Draper BRS44198, 1 Carlyon Close, Heavitree, Exeter EX1 3AZ.

Waterside SWRC. Blackfield Community Centre at 7pm fourth Tuesday generally with lecture and informal discussion plus activity with club station G4JNY. So if you are in the Hythe, Fawley or New Forest area try Clive Sanders G4KCM, 35 Forest Edge Estate, Fawley, Southampton, Hants SO4 1FN, which is also Fawley 893200.

East Antrim ARC. Just a year old the club meets

second Tuesdays at Carntall Hall, near Mossley, at 8pm with wide range of activities to suit all tastes. Jim Welsh GI4JXM at 20 Bryantang Brae, Doagh, Ballyclare, Co Antrim BT39 0RJ will be glad to provide more details. Incidentally, if any EI readers want to know more about the national EI society I can put them on the right path.

Bolsover ARS. Also quite young but thriving, the club welcomes visitors every Wednesday at around 8pm at the Angel Hotel, Bolsover, where RAE classes ought to be well under way now, with first entrants in the forthcoming May exam. Waiting to elucidate is Allan Turford G8HPQ, 103 Hilltop, Bolsover, Derbys S44 6NJ or Chesterfield 824972.

Mexborough & District ARS. Where Ian Abel G3ZHI will welcome you at 7pm any Friday night at the Dolcliff Hall, Dolcliff Road, Mexborough, with activities including a club station on the air, code classes and fascinating surplus gear sales from time to time. Ian lives at 9 Grove Terrace, Maltby, Rotherham, Yorks, or ring 0709 814911.

Now an appeal to editors or others responsible for the production of club newsletters and such like. PLEASE put the FULL name and address of the person to be contacted by visitors or prospective members, plus a telephone number, together with full details of where and when the club meets, all in a prominent place on the first page of the newsletter. This should be followed by a list of forthcoming events and if your committee hasn't organised such a list, chuck 'em out! Newsletters tend to go far beyond the area of the club and to put "contact Fred G4XXX QTHR" is just not good enough. Ta.

**Medium Wave
Broadcast
Band DX**

by Charles Molloy G8BUS

Reports to: Charles Molloy G8BUS
132 Segars Lane, Southport PR8 3JG.

When a reader asked recently: "How do you tune a loop?", it struck me that while we have covered the problems of loop antenna construction in some depth in recent issues, little attention has gone to actually using one. Why do we need a loop, what does it do, how do we use it, what are its limitations? These are the questions that come to mind.

Tuning a Loop

A loop is both tuneable and directional. These are the features that we make use of. By tuneable I mean that the main winding and the tuning capacitor together form a tuned circuit which can be made to resonate at the fre-

quency we are listening to. Set the receiver to the desired station; now adjust the loop tuning control for maximum output. Since a loop gives a boost to a chosen frequency then clearly it possesses selectivity, and when you connect a loop to a receiver you provide additional selectivity over and above that of the receiver.

We could use an aperiodic or untuned loop. Disconnect the tuning capacitor and you now have an untuned loop. The signals applied to the receiver will be weaker and no preference is given to any of them. In short, no selectivity and reduced pick-up. We are better off with a tuned loop.

Directional Effect

A loop has maximum pick-up along the plane of its windings, and little or no pick-up at right angles to the windings. There are two maxima in opposite directions to one another. There are also two nulls, which are the directions of minimum pick-up and these too lie in opposite directions to each other. It is the nulls that interest us and they are quite sharp compared to the maxima which are rather broad.

Tune your receiver to a channel with more than one station on it, say 585kHz after dark. In the UK you will hear Madrid mixed with Vienna. Peak up the loop with its tuning control and then slowly turn the loop (rotate it about its vertical axis). You will find that with the loop in one position Vienna will disappear leaving Madrid in the clear, while in another position Vienna will be on its own. What we are doing is to null-out an unwanted station so that we can listen to a wanted one on the same frequency. We are reducing co-channel interference and a loop will do this, provided the wanted and unwanted signals are in different directions.

This is not the end of the story of the loop antenna by any means, though if we used one just to reduce co-channel QRM then it would be well worth the effort involved in making it. Next month we will see how, on occasion, a loop will deal with static, with electrical interference, adjacent channel interference, receiver overloading, sideband splatter and even how it can occasionally perform as a selective attenuator or as a substitute for a tuneable audio notch filter. We will also look at its limitations: what a loop antenna will not do and why it is that you cannot use a loop with a portable receiver.

BBC Radio Wales

Dave Morgan GW4KYZ tells me that he was interviewed by BBC Radio Wales last December 12 when they did a programme from Blaenau Ffestiniog. The producer was rather interested in propagation, particularly as he had a request to send greetings to North America. He asked Dave if he could help in finding out how far his programme went out, and Dave in turn is asking readers of *Practical Wireless* for assistance.

Anyone living outside the service area of the transmission on 882kHz (340m) and who picked up the programme on December 12, as well as readers who have had long-distance reception of Radio Wales at any other time, are invited to send details to Dave Morgan, Penybont, Gellilydan, Blaenau Ffestiniog, Gwynedd, Wales. No doubt Dave will let us know the results in due course.

To my knowledge Radio Wales on 882kHz is logged regularly by DXers in eastern USA, and it ought to be audible under favourable conditions as far as Australia and New Zealand. It is interference rather than propagation that limits the range of signals on the medium waves. The only other two provisos are that there should be a path of darkness between Tx and Rx and the Great Circle

track between the two should not pass near either of the earth's magnetic poles.

DX from the East

In order to minimise interference (QRM) when DXing on the medium waves it is desirable to use a selective receiver and a m.w. loop antenna. One can also make use of the different channel spacing used in Region 2 (the Americas) to look for DX in parts of the band where it lies between European channels and this idea was pursued in the January issue. Is there anything else that can be done to combat QRM?

If you attempt to listen to Asia during the evening you are not likely to be successful. Apart from the high level of QRM, many of the countries you are looking for sign-off much earlier than Europeans because they are in time zones ahead of Europe. India is 5½ hours ahead of GMT, the United Arab Emirates are on GMT + 4, Saudi Arabia GMT + 3, while many Middle East countries use GMT + 2.

There is a compensation though. Although these broadcasters close down earlier in the evening they also start up earlier in the morning and this is the time to catch them when QRM is light. The further east they are the earlier they appear. Six in the morning local time in Pakistan is the start of their domestic programmes and this corresponds to 0100 GMT.

Look for India on 747kHz and 1314kHz, Pakistan on 927kHz, Saudi Arabia on 1512kHz (Jeddah) and 1521kHz (Dubai). Muscat Oman on 1242kHz and the BBC relay on Oman on 1413kHz have been heard as early as midnight, Dubai on 1481kHz by 0230, Istanbul

WITS RADIO 1510

115 Broadway, Boston, Massachusetts 02116 • 617-426-1700

We heard from you that you
heard from us, glad to hear it.

Thanks for listening **sports
alive**

The 50,000 Watt Sports Voice of New England

Another from Boston (WITS)

WINS RADIO 1010
ALL NEWS. ALL THE TIME
NEW YORK, N.Y.

A regular from New York City (WINS)

on 1017kHz and Diyakabir 1067kHz both in Turkey have been logged at 0300 sign-on. Tel Aviv (Israel) has been heard before 0200 on 1287kHz. The BBC relay in Cyprus on 720kHz has been picked up at various times, while Bulgaria is in the clear on 747kHz before Holland starts tuning up around 0420.


One should remember that as the days lengthen, long-range DXing to the east will cease, but more about summer DXing next time.

DX Heard

Reader **Rhys Thomas** (Bridgend) bought a new Trio R-1000 last August, which he uses with a "40 inch" loop. By September he had logged a number of North Americans and he sent me three QSLs which he thought might be of interest to readers. They are WINS New York City on 1010kHz, WITS in Boston on 1510kHz and CBGY in Gander on 750kHz. Thanks for the loan of the cards Rhys, I'm sure readers will be interested in what can be heard with the latest in receivers.

Saudi Arabia has attracted the attention of **Harold Emblem** (Mirfield) since he came out of hospital. Between 2250 and the 2300 sign-off it is possible to hear Riyadh on 585kHz, Jeddah on 1512kHz and Duba on 1521kHz, all carrying the home service programme. Best wishes for a speedy recovery Harold. Local radio is the attraction for **Roy Patrick** (Derby) who says that 15 locals are audible at his QTH. Roy draws attention to the new BBC Radio Lincolnshire on 1368kHz and to Radio Norfolk 855kHz, both of whom come in well, while the low power R Norfolk relay at King's Lynn on 1602kHz is just audible.

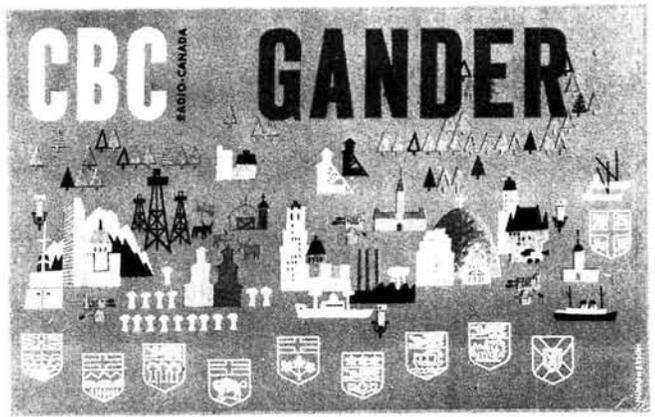A Hallicrafters SX100 and 39 metre long wire were



CBGY is in Newfoundland

used by old-timer **Ed Baker** of Cramlington in Northumberland to pull in CJYQ 930kHz with a fair to good signal during December. WNEW New York on 1130kHz was fair with Euro QRM nearly all the time, Dakar Senegal on 764kHz was weak/fair when Switzerland signs off, Radio Ougadougou in Upper Volta (tentative), Radio Margarita was heard on 1020kHz and Radio Globo Brazil on 1220kHz, while the BBC relay in Cyprus put in a good signal in English on 1323kHz from 0300 onwards.

Thanks for the log Ed. Readers will note the method of reporting where the terms good, fair, weak are used instead of SINPO or SIO codes, and I think you will agree that it gives quite an adequate picture to other DXers of what was heard.

**Short Wave
Broadcast
Bands**

by **Charles Molloy G8BUS**

Reports: as for medium wave DX,
but please keep separate.

receivers, and it should be useful to newcomers to the hobby if we have a look at what each has to offer.

Portables

The portable type of receiver is the one for the growing band of listeners who are turning to the short waves for an additional or alternative source of entertainment. The receiver is self-contained with its whip antenna and can be used anywhere, indoors or outdoors, except of course where it is screened as it might be away from the window in a steel-framed building or in a car or caravan. Among the more expensive sets in this class are the Panasonic RF2200 (a *PW* reader recently used one to listen to Radio New Zealand) and the Grundig Satellit 1400, and there are a number of others in the same price range. Less expensive ones include the Grundig Yacht Boy, Panasonic R1105 and the Russian-made Vega and Selena receivers.

Communications Receivers

If you want to listen to radio amateurs then your set must be able to receive single sideband (s.s.b.). If you are interested in Morse (c.w.) then you need a set with a beat frequency oscillator (b.f.o.). If you want to try DXing, i.e., listening to distant and weak stations which may not have much programme value, then you need a sensitive set with good selectivity which will function properly when connected to an outdoor antenna—some portables only work well with their whip. All this points to a communications receiver which may also be equipped with a noise limiter, an input attenuator and additional panel controls such as r.f. gain, a.g.c. on/off, which make it possible to squeeze the last drop of DX out of a receiver.



MICROWAVE MODULES LTD

AS REVIEWED IN THIS ISSUE!

RTTY TO TV CONVERTER: MM 2000



FEATURES

- ★ Complete terminal unit/TV interface
- ★ Includes modulator to enable direct connection to a standard UHF TV set
- ★ Latest state of the art microprocessor system
- ★ Automatic speed sensing
- ★ Automatic carriage return/line feed
- ★ Automatic letter shift facility
- ★ Upper and lower case display for ASCII

SPECIFICATION

POWER REQUIREMENTS	: 12.5V at 700 mA nominal
POWER SOCKET	: 5 pin DIN
AUDIO INPUT SOCKET	: Phono
TV (UHF OUTPUT) SOCKET	: Phono
VIDEO OUTPUT SOCKET	: Phono
MODES OF RECEPTION	: Amateur Standard ASCII: 110, 150 and 300 baud Murray Coded RTTY: 45.5, 50 and 75 baud IN ALL OF THESE MODES, THE CONVERTER WILL ACCEPT FSK AND AFSK SIGNALS
WEIGHT	: 1 Kg (2lb 2oz)
OVERALL SIZE	: 187 x 120 x 53 mm (7 ³ / ₈ x 4 ³ / ₄ x 2 ¹ / ₁₆ inches).

**ALL THIS
FOR £169 inc. VAT
P&P £2.00**

DESCRIPTION

This converter, MM 2000, contains a terminal unit and a microprocessor controlled TV interface, and requires only an audio input from a short-wave receiver, and a 12 volt DC supply, to enable a live display of "Off-air" RTTY and ASCII on a domestic UHF standard TV set. The display format is 16 lines of text, each 64 characters wide. This may be displayed on the screen as black on white, or white on black, and is switch selectable on the rear panel. When receiving ASCII, upper and lower case text is displayed.

The input stage of the converter is a balanced bridge frequency discriminator, with a transition frequency of 1360 Hz. Thus the converter will accept narrow or wide shift radio-teletype signals at the above mentioned speeds. In addition, the unit offers the capability to receive Kansas City standard 300 baud ASCII, at 1200/2400 Hz shift.

Red, yellow and green LED status lights provide a visual indication of correct "centre-tuning" and the RTTY or ASCII speed being received.

The inclusion of automatic software routines eliminates the possibility of information being corrupted or over-written, by the incorporation of automatic carriage return/line feed (RTTY signals only).

After 15 different characters in figure shift have elapsed, the converter will automatically return to letter shift. This feature alleviates the problem caused by a corrupt character forcing figure shift, but allows for repetitive underline characters. This facility may be overridden when the front-panel mounted "case control" switch is in the "off" position. This enables reception of continuous figure shift characters, e.g. Oscar prediction tables (RTTY signals only).

The converter utilises two microprocessors and 19 integrated circuits, and all circuitry is constructed on two, high quality glass-fibre printed circuit boards.

The unit is housed in a highly durable black diecast enclosure, and plugs for the DC power socket, audio input and TV UHF output sockets are provided.

The Murray/ASCII conversion program is contained in a user interchangeable EPROM, facilitating re-programming should software modification be required (e.g. alternative code-speed etc.).

MICROWAVE MODULES

BROOKFIELD DRIVE, AINTREE, LIVERPOOL L9 7AN, ENGLAND

Telephone: 051-523 4011 Telex 628608 MICRO G

Sets currently available that fall into this category are the Yaesu FRG-7700, the Trio R-1000 and the Lowe SRX-30.

Portable or Communications?

It is not normally feasible to convert a portable to receive s.s.b. or Morse, or to work with a long wire if the particular set does not like this type of antenna. There are a few sets though like the Grundig Satellit 2400 and Panasonic RF2600 which will receive s.s.b.

Personally, I would go for the communications set, but then I am a DXer as well as a short-wave listener, and I have two good outdoor antennas. If you are unable or unwilling to put up an outdoor antenna then a portable may be the receiver for you and you will be able to take it with you when you go on holiday. I have to make do with a domestic portable or car radio when away from home.

DX Seasons

"Could you tell me what has happened to the Voice of Chile and Radio Japan—they seem to have disappeared," enquires reader **L. Harding**. The propagation of short waves through the ionosphere varies according to whether the path between transmitter and receiver is in daylight or darkness, and to a lesser extent whether it is summer or winter. What you hear over a particular path in the evening will depend on the time of year, since on one occasion it may be daytime and on the other it may be dark. Broadcasters divide the year into four "seasons" starting in March, May, September and November which are the occasions for a great shuffle around of frequencies to keep up with the advancing seasons. Generally there will be a move towards higher frequencies in March and May and to lower ones in the autumn.

A short-wave frequency list only gives details of channels that are in use by individual broadcasters at some time of the day or year. An up-to-date schedule from a radio station is required to keep up with changes in frequencies and programme timing. The majority of international broadcasters will supply a schedule on request.

This information can also be found in the *World Radio and TV Handbook Newsletter* which comes out three times a year as an up-dater, or from the magazine *Voices* (PO Box 226, Helsinki 17, Finland) or from DX programmes such as *Sweden Calling DXers* which is on the air in English on Tuesdays, or from the bulletins of DX clubs.



Two QSL cards lent by Martin Whittington of Dartford: The Voice of Free China (Taiwan) 15 270kHz and Radio Kuwait 11 665kHz

Lightning Arresters

From Sheffield comes a query from **Trevor Corns** who writes: "Have read that it is wise to fix up a lightning arrester on antenna but can't find out where to get one or exactly what to do with it—no doubt you have a lively imagination and will tell me." I don't know where you can get one as they seem to have gone out of fashion these days. Perhaps a reader will help. In the early days of radio it was usual to earth an outdoor antenna when not in use. In our household we had a large knife switch for this purpose, plus some sort of spark gap made from two bolts mounted on brackets fixed to a piece of wood.

A lightning arrester will not protect your gear from a direct hit or even a near miss. During a thunderstorm the antenna may become charged to several hundred volts and you need some sort of device such as a neon tube or spark gap to discharge it. It is dangerous to interfere with an antenna during a thunderstorm, even to the extent of unplugging it from the receiver.

Spurious Responses

John Cook G4GAR writes: "It is often interesting, when a transmission pops up in a receiver somewhere it has no right to be, to try and work out why." But one really needs more information than was published about Mark Slater's discovery of BBC1 TV sound on approximately 13 700kHz in the February *PW* to be able to do much more than guess.

John starts off by assuming a receiver i.f. of 450kHz. The BBC1 TV sound is on 41.5MHz which would require an oscillator harmonic of 41 950kHz to produce an i.f. signal at 450kHz. This corresponds to a fundamental on $41\,950/3 = 13\,983\text{kHz}$ which would occur when the receiver is tuned to 13 533 (13 983 - 450). Is this near enough to the place where he finds it, to fit? concludes John. A rather ingenious guess!

Readers' Letters

A newly-acquired Eddystone EC10 has a small circular dial to the right of the main scale which puzzles reader **G. R. Ellis**. This is a logging dial and is used in conjunction with the pointer and bottom scale marked 0, 100, 200, 300, 400, 500 to provide 500 logging points. If you are tuned to a station and want to be able to return to it in the future then look at the circular dial which may, for exam-



ple, display 65. Then look at the main pointer which may be a little more than half-way between 200 and 300. The log scale reading is now 265 and if you want to come back to your station then switch to the correct band, set the log scale to 265 and rock the tuning knob slightly and you should locate the station. Our reader would like to contact anyone who has more information on the EC10. Replies direct to G. R. Ellis, 41 Brooke Road, Princes Risborough, Bucks HP17 9HJ.

In reply to **James Reilly** of Bangor. The BRT 400 is a 14-valve communications receiver of 1952 vintage and is now only available second-hand. A Christmas present of a Datong Active Antenna to use with his FRG-7 enabled **Conrad Fox** (West Auckland) to pull in RAE Argentina on 11 710kHz with a programme in English at 2215 and VLQ9 Brisbane of the ABC domestic s.w. service on 9660kHz at 1201. A couple of nice catches Conrad. Welcome to the column, hope to hear from you again.

VHF Bands

by Ron Ham BRS15744

Reports to: Ron Ham BRS15744
Faraday, Greyfriars, Storrington,
Sussex RH20 4HE.

The propagation of radio waves is so very dependent upon the behaviour of the sun and the structure of the earth's atmosphere that readers, who are unfamiliar with this aspect of the subject, should find it well worth while taking a look at the astronomical books in their local library.

Solar

Both **Cmdr Henry Hatfield**, Sevenoaks and I recorded a variety of solar bursts on December 23, 24, 25, 28, 29 and January 2, 10, 11, 14, 15 and 16, and a noise storm on December 26 and 27. On the 26th, Henry, using his spectroheliograph found six sunspot groups, one of which was very active and no doubt responsible for the prevailing noise storm. The solar noise was so strong on the 26th that my pen was at f.s.d. while the sun passed through my aerial beam. Towards the end of the observation, the sun, which was low in the sky, went (relatively speaking) behind a ridge of the South Downs near my home, and drew a profile of the hill in radio noise on my recording chart. Although the low sun made visual observation difficult for **Ted Waring**, Bristol, he did count 42 spots on December 15, 20 on the 18th, 34 on the 27th, 20 on January 1, 12 on the 3rd and 25 on the 10th. Henry recorded a lot of solar noise at 198MHz on the 29th, and at 1313 on January 16, we both recorded a very strong solar burst, lasting 2-5 minutes, at 136 and 143MHz. Henry also recorded it, although less intense, at 198MHz.

Aurora

Despite varying reports about the length of the auroral disturbance on December 19, I think it fair to say that the conditions prevailed, by changing degrees of intensity, from about 1400 to midnight. Between 1844 and 2023, **John Cooper** G8NGO, Cowfold, Sussex, worked

GI5MPS and heard GI8UPV, worked GM8BDX, GM8DMZ and GM8TKA on 2m s.s.b., and could still hear auroral signals when he closed down at 2340.

On arrival home for the Christmas break, **Jonathan Brisley** G8YQZ, Peterborough, switched on his rig and heard: "Weird whispering signals on the s.s.b. end of 2m." He then swung his beam north, found a spare frequency and began calling "CQ Aurora". After his first contact with GM8OFV at 1623, the QSOs came thick and fast and by 1930 he had worked three Ds, five northern Gs, two GJs, a GM, a GW, two OZs, 10 PA0s and three SMs. Jonathan's best DX was SM7DVR at 910km during the Scandinavian peak, which he estimates was between 1755 and 1815. During this event, Jonathan, who uses an Icom IC260E, a Lunar linear p.a. and a 10-element Yagi at 10m a.g.l., added two more countries to his list. **Mark Hattam** G4KGA, Hereford, listening to auroral signals for the first time, heard seven Gs, two GWs, F and PA0 between 1830 and 1930, and **George Grzebieniak** RS41733, London, heard two Ds, two GMs, and two PA0s between 1650 and 1830, and his best DX was OF3XU at 730km. Readers not familiar with auroral propagation should bear in mind that these DX signals have been reflected from an area of temporary ionisation in the earth's polar atmosphere, resulting from a disturbance on the sun.

Meteor Scatter

Another form of temporary ionisation is caused by the large numbers of tiny meteor particles (often described as shooting stars) that burn up daily within the earth's atmosphere.

On December 14, John Cooper had an s.s.b. contact on 2m via meteor trail reflection with SM0IOT who received John's signal spread over two pings and 12 bursts; the longest burst was seven seconds and the QSO took 25 minutes to complete. John also worked YU2IO and on the 13th, EA3LL via the same mode and during the Quadrantid meteor shower on January 4 he worked two YUs.

The 10m Band

Conditions on 10m remained generally good between December 16 and January 19 with daily contacts around the world. Mark Hattam is QSL manager of the Oxford University Radio Society's club station G3OUR, and says that this callsign often attracts a pile-up of stations from the USA. Among the many interesting 10m QSOs was one between PJ2KI on the Island of Curaçao and DL3YAO at 1340 on December 28. Both stations were very strong with me and when the QSO finished there was a pile-up of stations calling the PJ who then worked G3RZX and a YL station, G4IQY in Manchester who gave him 59.

I heard JA stations during the early mornings of December 16, 17, 27 and January 4 and 18, VKs on December 19, 25, 26, 29 and January 1, 2, 5, 6, 9, 12, 16 and 17, and ZL on January 10. The band was generally quiet around 0850 on the 20th and at 0906 on the 25th I heard strong echoes on a German signal and a QSO between UA3ACE (56) and VK5NOA (52). Strong echoes, this time on G stations, were again heard at 0915 on the 29th and 0930 on January 9. During the 35-day period between December 16 and January 19, I received signals from the International Beacon Project stations in Bahrain A9XC on 34 days, Bermuda VP9BA (mainly at midday) 30 days, Cyprus 5B4CY 29 days, Germany DLOIGI 35 days and DK0TE 21 days, and Mauritius 3B8MS 15 days. Although Ted Waring's results are similar to mine he frequently heard the beacons in Florida W4ESY and

South Africa ZS6DN and ZS6PW, and on a few days, Canada VE2TEN.

"Excellent reception of USSR in the mornings and very many USA from noon onwards," writes **Harold Brodribb**, St Leonards-on-Sea, Sussex, on January 6 which about sums it up. Harold also keeps an ear on those strong harmonics which come up in the 10m band from lower frequency broadcast stations, and one of his favourites is Alma Ata on 29.800MHz. George Grzebieniak has purchased a new 10m converter and on December 26 he listened to stations in LA, VK, 9K and 9Y.

Tropospheric

Like George Grzebieniak, I first noticed a tropospheric disturbance around 2000 on December 23 and while he was listening to signals from PA0 on 2m, I heard GW mobiles working through the Bristol Channel repeater GB3BC, R6, and a 529 signal from the Sutton Coldfield beacon GB3SUT, on 70cm. At 0830 on the 24th I again heard GW mobiles through GB3BC, and local stations working through the Crawley repeater GB3BP, also on R6, talking about hearing signals from the Continental repeaters. A little later at 0948, George heard GW8ELR on s.s.b. During the afternoon of the 24th, while the atmospheric pressure (30.2in or 1022mb) was slowly falling, **Phil Hodson** G8RBY, Melton Mowbray, using a TS700G with home-brew BF900 pre-amplifier and modified mixer board, a home-brew linear with 2 x 4CX250Bs and a 10-element Yagi at 14 metres a.g.l., soon had one Belgian and eight German stations on 2m s.s.b. in his log.

Although the pressure shot up again at noon on the 27th to 30.5in (1032mb), and did not begin to fall until midday on the 30th, the expected lift in v.h.f. conditions was disappointing. At 1516 on the 28th, George heard G8MJO/P on 2m s.s.b. at 230km, and around 2300 on the 30th he received s.s.b. signals on 70cm from DF1EQ, DF3EE and GW8GKF. Throughout the 28th, 29th and 30th, I received signals averaging 539 from GB3SUT with only a dipole feeding my receiver. This was repeated on January 5 and 12 when short periods of very high pressure were ending. George has now installed a barometer in his shack to give him an early warning of a v.h.f. lift. At 1345 on January 1, I listened to an interesting QSO through GB3BP, R6, between SM6YF/MM on a Swedish motor vessel in the English Channel, near Eastbourne, heading for Liverpool and G4FNL/M, followed by G8XZP/A in central Brighton.

Between 2100 and 2125 on December 30, **Simon Hamer**, Presteigne, Wales, using a Grundig Satellit 1400 receiver, heard three French stations in Band II, and from 1815 to 2031 on January 11 he listened to programmes from the two London IBA stations, Capital Radio and LBC, BBC Radio Solent and two French stations between 94MHz and 98MHz.

Horizontal FM

Mitch Tribe G8PMT, Lancing, was one of the founder members of the "Southern Horizontal FM Group" which, like many other such groups in the UK is growing rapidly. "There is a tremendous interest in horizontal f.m.," said Mitch, who along with other group organisers is hoping to arrange a national contest later in the year. Although Mitch lives in Sussex, and behind a chunk of the South Downs, he has already worked stations in 40 counties using 50 watts to an 8-element Yagi, and during the evening of January 5, G8PVH worked a station in north Yorkshire from his home in Alton, Hampshire. A national net on

144.670MHz is active on Mondays at 1930, and s.w.l. reports to stations over 100 miles away are always welcome.

RTTY

"I am avidly interested in DX RTTY, yet it seems rare to hear RTTY stations active during lift conditions," writes **Phil Hodson**, who runs the full legal power into a 10-element beam. Phil is also keen to try RTTY via meteor scatter and will be pleased to arrange skeds with, as Phil puts it: "Anyone else daft enough to sit up all night." Many people think us daft Phil, but it is experiments like you propose that puts the radio amateurs at the top of the DX league. **Mitch Tribe** is also active on RTTY, v.h.f. and u.h.f. 144.6MHz and 432.6MHz and local nets 145.3MHz and 433.3MHz respectively. Mitch often uses a Creed 7E teleprinter from which he has made punch tapes of CQs, contest CQs and basic station gen to use on his automatic tape transmitter. Like Phil, Mitch is always looking for skeds and s.w.l. reports are always welcome. I hope to be active in this field very soon, because I have purchased a Microwave Modules MM2000 RTTY to TV converter, but owing to the pressure of work on this manuscript, I have not had time to play, so watch this space next time folks.

News Items

Congratulations to **Mark Hattam**, who passed the Morse test last April and the RAE in May and is now active on all bands from 1.8MHz to 1296MHz with the callsign G4KGA. Mark is a student at Oxford University and, during term, is often on the air from the club station, G3OUR or as G4KGA/A.

Congratulations also to **Arthur Poulter**, who passed the RAE last May and now sports the callsign G8XMG, and will no doubt be in QSO with his son, **Derek G3WHK**, who lives nearby. Derek is now operational on all bands and was delighted to work Spain on 70cm from his home in Morden, Surrey, last November.

For readers who require a working knowledge of astronomy, including our subjects, such as aurora, the earth's atmosphere and the sun, I can thoroughly recommend a new book. *The Practical Astronomer* by **Colin A. Ronan**, Pan Books ISBN 0 330 26231 9.


National Astronomy Week, 1981, will be held from April 20 to 26 to mark the bicentenary of the discovery of the planet Uranus in 1781 by the amateur astronomer, **William Herschel**. This is the first British attempt to make the science of astronomy and its achievements more widely known. More information available from **Don Miles**, 15 Bevan Road, Lovedean, Portsmouth, Hants PO8 9QH.

Congratulations to **Margaret** and **Richard Brownlow**, Brighton, on passing their Morse tests on January 2 and changing their G8 callsigns for G4LCU and G4LCV respectively. Also to **Barry Ainsworth** G4GPW, Lancing, on receiving the Cycle 21 Crossband Award from The Six Meter Amateur Radio Operators of Region 2, in appreciation of his 6m work in the true spirit of amateur radio.

The Barking Radio and Electronics Society are holding their 144MHz contest between 1300 and 1700 on March 29. There are sections for all licensed operators residing in Essex, another for those living outside the county, and one for all s.w.l.s. Certificates will be awarded to the winners and two runners-up in each section. The address for more information and contest logs is **A. L. Sammons** G8IZN, 80 Lyndhurst Gardens, Essex IG11 9XZ.

NORTHERN COMMUNICATIONS

AMATEUR • COMMERCIAL • MARINE

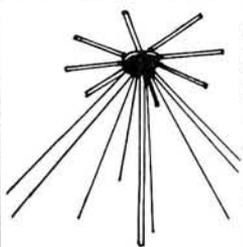

NORCONE 512 (66-512 MHz)

It's here! A no compromise, precision made full 16 element disccone antenna made in Britain. Standard S0239 connector, with cover. Supplied with 1" diameter, 30" mounting support mast and complete instructions.

An ideal partner for the SX200A, "Bearcat" and other scanning receivers. It may also be used for transmission and in particular where antenna space is limited.

Full coverage of 70.144,432MHz Amateur bands plus Aircraft, Marine and Commercial bands.

£24.95 p.p. £1.50

NCMK-1. In line vertical mounting kit for 1" to 2" mast. **£2.45** p.p. £0.50

NCMK-2.

Chimney lashing kit, including hardware and lashing wire. **£2.95** p.p. £1.00
NCCK-1. Low loss coaxial cable kit, 10 metres, with connectors and fixing clips.

£3.75 p.p. 50p

SX200A SCANNER HF-VHF-UHF Receiver. **£241.50**

Special Offer SX 200A - Norcone 512. Complete, inc. VAT-delivery. **£260.00**

Special Offer Bearcat 220 - Norcone 512. Complete inc. VAT-delivery. **£273.95**

ZL-12 COMPACT YAGI

13db gain, compact 2 metre Yagi. 10'6" boom, lightweight rugged design. Hundreds of this award winning antenna already in use. Send for details.

£28.75 p.p. £1.50

ZL-8 SUPER COMPACT YAGI

9db gain, super compact 2 metre Yagi. 6'0" boom, lightweight rugged design. Ideal for limited spaces and portable operation. Send for details.

£17.25 p.p. £1.50

YAESU FT480R. FDK 750E. FRG7700

These are amongst our full range of Amateur Radio equipment and accessories. Ring or call for complete information:

299-303, Clarendon Road, Halifax HX3 6AW,
West Yorkshire. G3UGF.

Tues-Sat. 9.45am-5.30pm.

Telephone (0422) 40792.

24 hour Ansafone Service.



"RIGS GALORE"

YOU SAID IT TO US - "THE BEST & WIDEST SELECTION IN EASTERN ENGLAND!!"

FT707 "Wayfarer" HF WARC Transceiver	£529
FT767DX Sommerkamp WARC Model + Extras	£559
FT1012D Yaesu WARC Model HF Base Stn.	£569
FT902DM Yaesu WARC Competition Model AM/FM/FSK/SSB	£799
FT7B Still one of the best Mobile HF Transceivers made	£399

AND A COMPLETE LINE OF ACCESSORIES FOR THESE RIGS FROM STOCK - MICS, PSU's TRANSVERTORS, ATU's...

FRG7 General Coverage SW Receiver Now with <u>FREE</u> Headphones	£199
--	-------------

FRG7700 Come and try it and get <u>FREE</u> Headphones for the price:	£309
---	-------------

AND TO GO WITH THEM HOW ABOUT OUR MULTI BAND TRAP DIPOLES	£25.50
--	---------------

FT202 6 Ch. 2M FM 3 ch. fitted	£99
--------------------------------	------------

FT207R 12.5 kHz 2M MPU Controlled	£195
-----------------------------------	-------------

IC2E Icom's famous Mini 2M Handy with <u>FREE</u> Leather Case	£159
--	-------------

AR245 5 Watt Handy 2M NOW IN AT LAST DISCOUNT PRICE!	£169
--	-------------

C78 JUST IN! New Standard 70cm FM 10 Watt Burner, quick release mount & carry case also from stock.	£209
--	-------------

TR7800 One of the best 2M FM rigs we have ever used!	£267
--	-------------

TS280FM The Famous High Power 2M FM with auto select repeaters	£199
--	-------------

NOW WITH REPEATER DEFEAT & AUTO TONE (EXTRA).

MULTI-MODES - BOY HAVE WE GOT MULTI-MODES!!

TR9000 **£345**, FT480R (Two models) **£339, £359**.
IC251E Base **£475**. FT225RD **£565**.

AND NOW: FT780R YAESU 70cm ALL-MODE MOBILE	£409
--	-------------

Please send for our list (S.A.E. appreciated) with Sommerkamp/ Yaesu / Trio-Kenwood / Icom / Standard / Swan / Cushcraft / Ascot / Western / Microwave Modules & Accessories galore **PLUS** our Spares & Component Listings (over 5000 lines).

UK AUTHORISED IMPORTERS FOR SOMMERKAMP.

WE TAKE TELEPHONE ORDERS FOR SAME-DAY DESPATCH BY FREE SECURICOR DELIVERY & YOU CAN PAY BY ACCESS OR BARCLAYCARD/VISA.

Our showrooms are open Monday-Saturday 9-5 (closed Thurs.) and you can telephone 24 hour orders on: 0277 219435 (Ansafone) or 0277 226470 daytime.

Credit sale facilities available.

ALL PRICES INCLUDE VAT + DELIVERY.

Helford components:-

PT9795	per pair	£17.90
Monolithic R/D Ceramic 100NF	each	£0.20
VFO P.C.B.		£1.15
Buffer P.C.B.		£1.15
G4CLF P.C.B.		£4.24
Preselector P.C.B.		£1.48
Pre-Amp P.C.B.		£1.42
Ist-Amp P.C.B.		£1.36
SL1612		£1.56
SL1621		£2.07
SL6270		£2.51
SL1640		£2.07
SL6310		£2.51
2N5771		£0.31
SL560C		£4.97
BA182		£0.36
78L06		£0.59
J304		£0.54
J310		£0.87
FX2249	per pair	£0.60
SBL-1 -- (MD108)		£4.90
SL560C		£4.97

Postage & Packing £0.35.

VFO/CAP 4170/75/023 incl. 12 **£8.84**

VFO ADJ/TORQ. Ball Drive 5620 **£4.41**

4 Gang (Preselect) CAP. **£7.73**

5318/4/102 **£7.73**

Preselector (Reduction Drive) **£1.76**

5870/3 **£1.76**

Postage & Packing £0.50

HELFDORD

(Troubleshooting by the designers.)
Any problems send S.A.E. + Invoice Number.

HOME BRU RADIO

(Mail order only)

55 Ashley Road, Parkstone,
Poole BH14 9BT.

Delivery on Jackson Capacitors
4/6 weeks.

ARROW ELECTRONICS LIMITED

7 COPTFOLD ROAD, BRENTWOOD,
ESSEX CM14 4BN.

73's de G3LST & Staff.

Get a great deal from Marshall's

CRIMSON ELEKTRIK HI FI MODULES

CE 608	Power Amp	£20.09
CE 1004	Power Amp	£23.43
CE 1008	" "	£26.30
CE 1704	" "	£33.48
CE 1708	" "	£33.48

CPS 1	Power Unit	£19.52
CPS 3	" "	£23.52
CPS 6	" "	£30.00

CPR 1	Pre Amp	£32.17
CPR 1S	" "	£42.52

SINCLAIR INSTRUMENTS

Digital Multimeter	PDM35	£34.50
" "	DM235	£52.50
" "	DM350	£72.50
" "	DM450	£99.00
Digital Frequency Meter	PFM200	£49.80
Low Power Oscilloscope	SC110	£139.00
TF200 Frequency Meter		£145.00
TGF 105 Pulse Generator		£85.00


NEW

LCD Multimeter	TM351	£99.00
LCD Multimeter	TM352	£49.95
Prescaler	TP600	£37.50

New

Presensitised PC Boards, Developer. U.V. units, Toyo miniature Fans 230v AC £9.95
Mini Metal Detector/Voltage Tester for locating cable under plaster £9.95
Flow/Speed Sensors for monitoring fuel consumption electronically in vehicles

Just one of the exciting Leader range

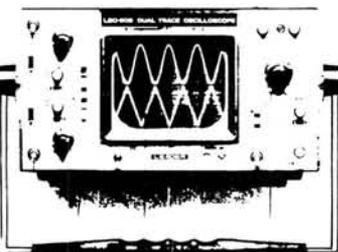

LB0508A
OSCILLOSCOPE
With 20MHz DC bandwidth and 10 mv input sensitivity on a 5" screen this universal oscilloscope is suitable for a wide range of applications.

Send SAE for details of full range.

Marshall's 80/81 catalogue is now available by post, UK 75p post paid Europe 95p post paid: Rest of world £1.35 post paid.

A. Marshall (London) Ltd., Kingsgate House,
Kingsgate Place, London NW6 4TA.
Industrial Sales: 01-328 1009
Mail Order: 01-624 8582 24hr service.

Also retail shops: 325 Edgware Road, London W2.
40 Cricklewood Broadway, London NW2. 85 West Regent St.,
Glasgow. 108A Stokes Croft, Bristol.

ILP HI FI MODULES

Power Amplifiers

HY30	£7.29
HYY60	£8.33
HY120	£17.48
HY200	£21.21
HY400	£31.83

Pre Amplifiers

HY6	£6.44
HY66	£12.19


Power Supplies

PSU30	£4.50
PSU36	£8.10
PSU60	£4.75
PSU70	£13.04
PSU180	£21.34

MULTIPLEX NICKEL CADMIUM CELLS

Type S101 (HP4)	£0.98
Type SubC (HP11)	£1.75
Type SubD (HP2)	£1.95
Friwo Chargers for above Penlight 4: accommodates 1-4 size HP7	£5.50
Combibox FW611: accommodates HP7, HP11	£13.25

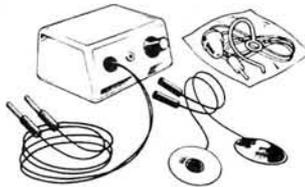NOTE ALL PRICES NET. EXCLUDING VAT. POSTAGE/PACKING



BIO FEEDBACK

A high sensitivity GSR monitor for development of your inner potential and powers. Kit contains ALL you will need, including ready drilled case, to build and experiment with the monitor. Accessories include skin electrodes, conductive jelly, earpiece, and full instructions for assembly and use.
Kit £9.80 Built and tested £12.13
Details supplied FREE — just send S.A.E.

TRANSISTORS

CIL108 (plastic BC108), BC171A, BC320, BF393, 2N5447, 2N5449, all at 9p each, 10 for 70p, 100 for £5.80.



MIXED COMPONENT PACKS

CAPACITORS
Assorted types and values, polyester, polystyrene, ceramic, electrolytics, etc. A fine selection of useful components. 100 for £1.00 500 for £3.20.

RESISTORS

Carbon film, composition, oxide, etc. Mainly 5% E24 series, 1/4 and 1/2 Watt, but some precision 1% and 2% generally included, also a few 1 Watt and above. A wide range for all purposes. 250 for £1.20 1,000 for £3.60.

ELECTROLYTICS

Radial, axial and PCB types, values from 1mf to 1000mf. Not to be missed! 100 for £2.60 500 for £10.80.

Bargain lists of quality components FREE Send S.A.E. for your copy today!

Postage free above £10.00, please add 60p below this amount. 15% VAT should be added to your order total.
ACCESS orders accepted: write or phone Dean (0594) 41267.

Wye Valley Electronics

15 HIGH STREET, LYDNEY, GLOUCESTERSHIRE GL15 5DP



OPTO SWITCH

Type OPB814. Consists of an infra-red source and sensor in a slotted mounting allowing the beam to be broken by any solid object in the 3 x 8mm slot. Useful for limit switching, end of tape detection, and even contactless electronic ignition.
R.S. Components trade price £2.25 each. OUR PRICE 85p each! 10 for £7.20



ZETTLER LOW PROFILE RELAY

Type A2535-08-1. Only 11mm deep, allowing PCB's to fit in confined spaces. Coil resistance 440R, operating voltage 17.5V to 28V (24V nominal). Contacts: SPc/o silver with gold flash. Rated 110V D.C. 125V A.C. Max. current 3A. A high quality professional relay at a ridiculously low price: 48p each, 10 for £3.60.



TRANSFORMER

240V primary, tapped for 115V. Secondary 12-0-12, rated 4VA. Connections by spalls for PCB mounting, wire wrap, or normal soldered connections.
95p each, 10 for £7.40



OPERATIONAL AMPLIFIER

Op. amp. type 708. A general purpose device in a 14-pin DIL package. Applications similar to 741, but external frequency compensation allows operation at higher frequencies too. 18p each, 10 for £1.50.

RISCOMP LIMITED

DIGITAL VOLTMETER



MODULE

Fully built and tested, ONLY

£11.95 + VAT
£1.79

- ★ Reads positive and negative voltages with a sensitivity of 0 - 999mV and 0 - 99mV
- ★ Single supply between 7 & 12 volts (220mA)
- ★ High accuracy -0.1% - 1 digit
- ★ Large bright 0.43" high efficiency displays
- ★ Size only 41 x 95 x 10mm
- ★ Supplied with full data & applications information

This brand new, quality module manufactured by Autona Limited (who are one of the U.K.'s largest module manufacturers) means you can build accurate test equipment, multimeters, thermometers, etc. easily and at a fraction of the cost of ready-made equipment. Full details are provided showing how to measure A.C. voltage, current, resistance and temperature.

CMOS PRICES				SPECIAL OFFERS	
Type	Price	4023	20p	4068	21p
4001	19p	4024	62p	4069	19p
4002	19p	4025	20p	4070	19p
4006	81p	4026	130p	4071	19p
4007	19p	4027	41p	4072	19p
4008	77p	4040	86p	4081	22p
4011	22p	4044	82p	4082	21p
4013	39p	4046	95p	4085	72p
4015	73p	4048	42p	4093	55p
4016	36p	4049	43p	4501	24p
4017	76p	4050	42p	4510	77p
4018	76p	4051	74p	4511	85p
4020	85p	4052	68p	4518	77p
4021	77p	4060	100p	4520	91p
4022	77p	4066	42p	4528	82p
5	555	Timer			£1.00
6	741	Op Amp			£1.00
3	TBA120	FM IF			£1.00
3	76115 (1310)	Stereo Decoder			£1.00
5	LM3014 14 pin	O P Amp			£1.00
50	1N4148	GP Diode			£1.00
50	1N4004	400V 1 Amp			£1.00
10	1N5402	200V 3 Amp			£1.00
25	BC183	NPN			£1.00
25	BC212	PNP			£1.00
4	BD 239A	60V 4 Amp NPN			£1.00
4	BD240A	60V 4 Amp PNP			£1.00
3	1458	Dual 741			£1.00

Also soldering irons, test meters, transistors, IC's etc. etc. etc.

Add VAT 15% - 50p p&p per order.



EXPRESS DELIVERY

Shop Opening hours: 9am-5pm Mon-Sat. 1pm Wed



Dept. P.W.4, RISCOMP LIMITED,
21 Duke Street, Princes Risborough, Bucks. HP17 0AT. (08444) 6326.

TV

by Ron Ham BRS15744

Reports: as for VHF Bands,
but please keep separate.

"I must thank you very warmly for the television instrument you have put into Downing Street. What a marvellous discovery you have made! When I look at the transmissions I feel that the most wonderful miracle is being done under my eye," wrote Prime Minister Ramsay MacDonald to Mr Baird on 5 April, 1930. I found this letter published in a 50-year-old copy of *Television*, the then official organ of The Television Society, who pointed out that: "Mr MacDonald was one of the first to come to the Baird studios to be televised." These were the days of the mechanical disc receiver and subjects were transmitted by the Baird Company from Brookman's Park, some six years before the BBC began broadcasting with a 405-line system. Now we enthusiasts have sophisticated equipment and go looking for pictures, not over a limited area, but from stations in other parts of the world.

Pictures via F2

The usual mixture of smeary pictures appeared on Ch. R1, 49.75MHz, via the F2 region of the ionosphere on December 21, 24, 26, 27, 31 and January 4. Like Sam Faulkner, I tried to sort out a mixture of what looked like

a music programme, sports and a cartoon film between 0830 and 1000 on the 21st, and a good assortment of test cards, various electronic patterns and the one Sam photographed (Fig. 1) between 0800 and 0900 on the 26th. From 1125 to 1200 on the 22nd, T. Ampy saw two types of Russian test card and at 1130, a clock appeared showing 1430, followed by the caption, familiar to most DXers, "HOB0CTN". Around 1500 on the 24th, he received pictures from Poland, Programme 1, on both Channels R1 and R2, 59.25MHz. At 0856 on the 24th there was a blurred caption on R1, followed by what looked like a monk talking, and at 0930 on the 27th the prevailing smeary pictures became clear and I saw a male programme presenter, with an almost bald head and glasses, showing books followed by a possibly Russian caption.

At 0928 on the 31st, unreadable captions were rising over a street shot and moving cars were visible. On the 27th, Sam received bursts of American 525-line video on Ch. A2, 55.25MHz, at 1515, and by 1530 strong but blurred and rather ghostly pictures were seen, possibly a variety programme or an early morning children's show. Sam could see two men on stage, then a YL singer and some cartoon characters until about 1540. Between 1220 and 1251 on the 30th, Sam received strong colour bars and chequer-board and Cadena test cards from RTVE, Spain, on Ch. E3, 55.25MHz, and between 1215 and 1300 on the 31st both Sam and T. Ampy received test cards from ORF Austria on E2, and Sam received signals from TVP Poland on Ch. R1.

My best results began at 0815 on January 4, when I heard weak sync pulses on Ch. R1 with my R216 communications receiver and saw several strong bursts of picture, which looked like a film about students, on my JVC. At 0910 the bursts were showing, first a man with a bear and then with a donkey. By 0914, a youth choir was

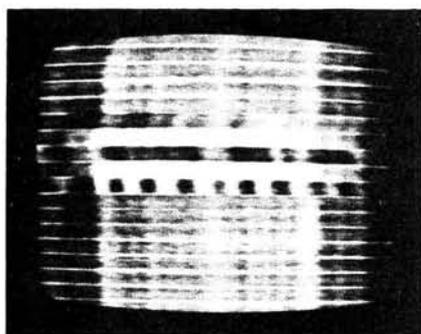


Fig. 1: An electronic test pattern seen by Sam Faulkner on December 26



Fig. 2: SSTV picture from ZS6BTD received by Sam Faulkner

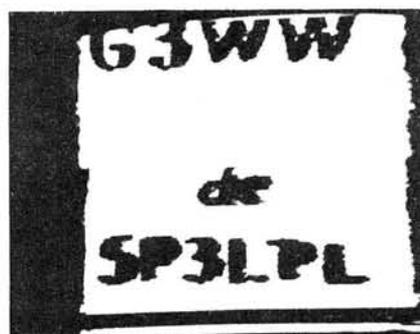


Fig. 3: Call received by Richard Thurlow G3WW from SP3LPL on 20m



Fig. 4: Self portrait of SP3LPL received by Richard Thurlow on SSTV



Fig. 5: Picture from DL6HP recorded on cassette by Richard Thurlow



Fig. 6: DF2TV's self portrait relayed by WA8YJU, both on 20m SSTV

solidly on screen and at 0918 a male singer, backed with female dancers, was performing on a lavish set. From 0925 a YL announcer was sitting at the right of a small TV screen with a large letter "A" in the bottom right-hand corner until 0926, when a full-screen caption, "BIS" followed by WTOREK PROGRAM I and a male announcer appeared. By 0932, WTOREK PROGRAM II was seen followed by a pianist at a grand piano with a YL singer and just before it faded out at 0939, a strong caption "STUDIO GAMA" was seen.

Tropospheric

During the evening of December 23 there was considerable patterning on several u.h.f. television channels and at times, as the prevailing tropospheric disturbance ebbed and flowed, there was total absorption of the signal. For most of the evening and the morning of the 24th, I received strong pictures from the IBA transmitter at Lichfield on Ch. 8, 189MHz, with only a dipole aerial feeding my receiver. At 1230, T. Ampi received pictures from France on Ch. 46, and between 1300 and 1500 from the Belgian Stations BRT on Chs. 47 and 62, RTB on Ch. 52, and Germany WDR on Chs. 48 and 53.

Meteor Scatter


Both **Harold Brodribb** and Sam Faulkner received many brief, sometimes 1- or 2-second, bursts of picture on Channels E2 and R1 during the Quadrantid meteor shower on January 3 and 4, and at times the bursts were long enough for Sam to identify cartoon pictures.

SSTV

"Still quite a lot of interesting activity found on the SSTV calling channel, 28-680MHz and often 29-180MHz, when the band is busy," writes Sam Faulkner, who logged Ws 1, 2, 3, 4, 5, 8, 9 and 0 between December 14 and January 10. At 1535 on December 25 he logged VE3DDB, and at 1500 on January 4, VE1KG, both in Nova Scotia. Sam says that VE3EGO is on between 1600 and 1700 most weekends with colour transmissions. Pictures from I7PQD and OH5RM were both seen between 1300 and 1400 on December 21, and HK3DBQ, Bogota, new to SSTV, was seen at 1700 on the 22nd and 23rd. Around 1230 on January 4, Sam received pictures from ZS6BTD (Fig. 2), in Johannesburg, who was then transmitting pictures of himself and equipment identified simultaneously on the screen by his name and callsign.

A fine Christmas present for **Richard Thurlow** G3WW, March, Cambs, came on December 24 when he had a two-way SSTV QSO with YO8FR on 28-680MHz, giving Richard his 106th country, Roumania. His 107th was notched up on December 29 and 30, when HB9AZY set up his SSTV equipment at 4U1ITU on 14-230MHz, and gave a new country to the world, including G3GRJ and G3IAD. **Nevil Jackson** G3IAD, has already added four new countries to his "2nd in the world 2 x SSTV DXCC" and Richard holds No. 3. On November 25, SP3LPL called Richard on 20m (Fig. 3), and while in QSO he sent a picture of himself (Fig. 4) which was received by Richard, on his Robot 400 + 2 memories, through heavy interference. On the same day he also received a picture from the West German station, DL6HP (Fig. 5), which he recorded on an audio cassette tape. Another interesting aspect of SSTV is to receive a self-portrait replay such as that in Fig. 6. This had been sent from DF2TV in Germany to WA8YJU in Michigan, and recorded by Richard during the replay from across the Atlantic.

So You Want to Pass the RAE?

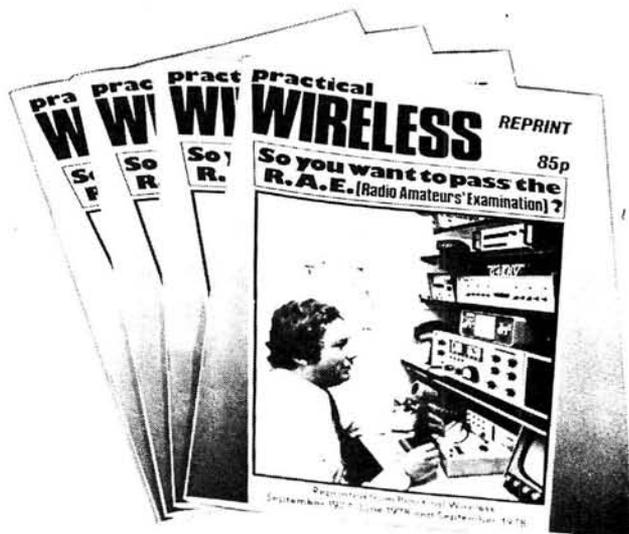

A reprint of the complete series, including details of the new examination format introduced in 1979, is now available. The reprint costs 85p, including postage and packing to addresses within the United Kingdom.

Order your copy by completing and returning the coupon, together with your remittance, to IPC Magazines Ltd., Post Sales Department, Lavington House, 25 Lavington Street, London SE1 0PF. Please ensure that your name and address are clearly legible.

PRACTICAL WIRELESS—Radio Amateur Examination Reprint

Please send your order and remittance to:

**IPC Magazines Ltd., Post Sales Department,
Lavington House, 25 Lavington Street,
London SE1 0PF**

Please send me . . . copies at 85p each to include postage and packing

I enclose P.O./Cheque No. Value

Remittance must be crossed postal order or cheque (name and address on back please) and made payable to IPC MAGAZINES LTD

NAME
(BLOCK LETTERS)

ADDRESS
(BLOCK LETTERS)

.....
.....
.....
..... Post Code

Remittances with overseas orders must be sufficient to cover despatch by sea or air mail as required. Payable by International Money Order only

Company registered in England. Regd. No. 53626

A subsidiary of Reed International Limited

Cut round dotted line

GAREX (G3ZV1)

RESISTOR KITS a top-selling line for many years. E12 series, 5% carbon film, 10Ω to 1M, 61 values, general purpose ratings ¼W or ½W (state which)

Starter pack 5 each value (305 pieces) **£3.10**
 Standard pack 10 each value (610 pieces) **£5.55**
 Mixed pack, 5 each ¼W + ½W (610 pieces) **£5.55**
 Giant pack, 25 each value (1525 pieces) **£13.60**

NICAD RECHARGEABLES physically as dry cell: AA(U7) **£1.30**; C(U11) **£3.35**; PP3 **£5.55**. Any 5+: less 10%, any 10+: less 20%.

AMPLIFIER MODULE new, fully assembled 6W IC unit, 12V DC. Low impedance (4-8Ω) input and output for extn. speaker amplification, with circuit **£2.75**

CRYSTALS FOR 28.5MHz 3rd. overtone, suit most 'CB' rigs. 28.5MHz Tx and 28.045MHz Rx. HC18U **£4.60 per pair**

CRYSTAL FILTER 10.7MHz, 12½kHz channel spacing, ITT type 901C **£6.90**

CO-AXIAL CONNECTORS & ADAPTORS see full list.

PL259 UHF plug with reducer **75p**; SO239 UHF socket, panel mtd. **60p**; 2 x SO239 inline coupler **£1**; 2 x PL259 inline coupler **£1**. Any 5+ connectors: less 10%

HT TRANSFORMER multi-tap pri.: 5 secs.: 35v 200mA, 115v 150mA, 50v 500mA, 150v 300mA, 220v 300mA **£5**

HT CHOKE top grade type, 9H 240mA **£3.50**

PYE CAMBRIDGE SPARES (our speciality, see full list). Ex. equip., fully guaranteed. Rx RF board 68-88MHz **£5.95**. 10.7MHz I.F. **£3.65**. 2nd mixer 10.7MHz to 455kHz **£3**. 455kHz block filter 12½kHz **£9.40**, ditto 25kHz **£3**. 455kHz AM I.F. **£3.65**. Audio bd. **£1.95**, and many more. Vanguard & Westminster spares also.

MONITOR RECEIVERS

SX-200 VHF-UHF AM-FM SCANNER

Covers 26-88MHz, 108-180MHz and 380-514MHz, AM + FM, it scans, seeks, memorises and beats all the others. See full details.

HF-12 POCKET SIZE FM 12 channel xtal controlled. 4MHz bandwidth in range 130-174MHz. With nicad and charger **£57.95** Xtals extra, see below.

SOUNDAIR 008 PORTABLE FM SCANNER 8 channel xtal controlled 140-170MHz. With nicad and charger. **£59** Xtals extra.

SR-9 top-selling monitor: 2m FM with 144-146MHz full coverage VFO + 11 xtal controlled channels; ideal for fixed, /M, /P use. 12V DC operation **£47.50**

Marine band SR-9, 156-162MHz, same spec. and price.

CRYSTALS FOR NR-56, SR-9, SR-11, HF-12, TM-56B All 2m channels from 0 (145.00) to 32 (145.80) incl. at **£2.46** (+15p post per order). Over 40 popular marine channels at **£2.85** (+15p post). Non-stock xtals made-to-order in 3 weeks at **£4.30** each. See list.

'SCAN-X' VHF/UHF BROADBAND FIXED STATION AERIAL **£19.90** Ideal for SX-200 and other VHF/UHF receivers.

We also stock the:

KDK 2025 2m SYNTHESISED TRANSCEIVER Full band coverage 25 or 12½kHz steps/10 channel memory/scans memories or selected band portion/3W or 25W Tx/all the features you need at **£225**

YAESU FRG 7700 GENERAL COVERAGE RECEIVER 150kHz - 30MHz AM/USB/LSB/CW and FM **£309**

MAINS PSU British made by GAREX 12 volt 1 Amp regulated, adjustable 10-16v **£15.95**

MAIN DISTRIBUTOR OF REVCO AERIALS & SPECIAL PRODUCTS (trade enquiries welcome)

PRICES INCLUDE UK POST & PACKING & 15% VAT.

GAREX ELECTRONICS

7 NORVIC ROAD, MARSWORTH, TRING, HERTS HP23 4LS.

Phone 0296 668684. Callers by appointment only.



Conquer the chip.

Be it a career, hobby or interest, like it or not the Silicon Chip will revolutionise every human activity over the next ten years.

Knowledge of its operation and its use is vital. Knowledge you can attain, through us, in simple, easy to understand stages.

Learn the technology of the future today in your own home.

MASTER ELECTRONICS

LEARN THE PRACTICAL WAY BY SEEING AND DOING

- Building an oscilloscope.
- Recognition of components.
- Understanding circuit diagrams.
- Handling all types Solid State 'Chips'.
- Carry out over 40 experiments on basic circuits and on digital electronics.
- Testing and servicing of Radio, T.V., Hi-Fi and all types of modern computerised equipment.


MASTER COMPUTERS

LEARN HOW TO REALLY UNDERSTAND COMPUTERS, HOW THEY WORK - THEIR 'LANGUAGE' AND HOW TO DO PROGRAMS.

- Complete Home Study library.
- Special educational Mini-Computer supplied ready for use.
- Self Test program exercise.
- Services of skilled tutor available.

MASTER THE REST

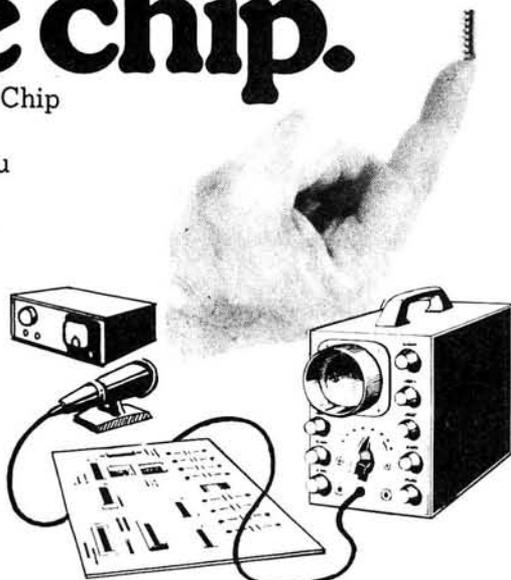- Radio Amateurs Licence.
- Logic/Digital techniques.
- Examination courses (City & Guilds etc.) in electronics.
- Semi-conductor technology.
- Kits for Signal Generators - Digital Meters etc.



FREE	Please send me a FREE information product (subject to):	I am interested in -
	Name	PRACTICAL ELECTRONICS
	Address	COMPUTER TECHNOLOGY
	OTHER SUBJECTS
BLOCK CAPS PLEASE		(Please state your interest)

PW/4/813

BRITISH NATIONAL RADIO & ELECTRONICS SCHOOL
 4 CLEVELAND ROAD, JERSEY, CHANNEL ISLANDS.

Why the Sinclair ZX80 is Britain's best-selling

Built: £99.⁹⁵

Including VAT, post and packing, free course in computing, free mains adaptor.

Kit: £79.⁹⁵

Including VAT, post and packing, free course in computing.

This is the ZX80. A really powerful, full-facility computer, matching or surpassing other personal computers at several times the price. 'Personal Computer World' gave it 5 stars for 'excellent value'. Benchmark tests say it's faster than all previous personal computers.

Programmed in BASIC—the world's most popular language—the ZX80 is suitable for beginners and experts alike. And response from enthusiasts has been tremendous—over 20,000 ZX80s have been sold so far!

Powerful ROM and BASIC interpreter


The 4K BASIC ROM offers remarkable programming advantages:

- * Unique 'one-touch' key word entry: the ZX80 eliminates a great deal of tiresome typing. Key words (RUN, PRINT, LIST, etc.) have their own single-key entry.
- * Unique syntax check. A cursor identifies errors immediately.
- * Excellent string-handling capability—takes up to 26 string variables of any length. All strings can undergo all relational tests (e.g. comparison).
- * Up to 26 single dimension arrays.
- * FOR/NEXT loops nested up to 26.
- * Variable names of any length.
- * BASIC language also handles full Boolean arithmetic, condition expressions, etc.
- * Randomise function, useful for games and secret codes, as well as more serious applications.
- * Timer under program control.
- * PEEK and POKE enable entry of machine code instructions.
- * High-resolution graphics.
- * Lines of unlimited length.

Unique RAM

The ZX80's 1K-BYTE RAM is the equivalent of up to 4K BYTES in a conventional computer—typically storing 100 lines of BASIC.

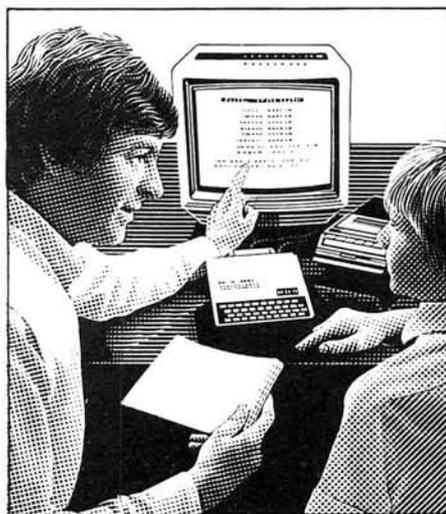No other personal computer offers this unique combination of high capability and low price.



The ZX80 as a family learning aid. Children of 10 years and upwards are quick to understand the principles of computing—and enjoy their personal computer.

The Sinclair teach-yourself BASIC manual

If the specifications of the Sinclair ZX80 mean little to you—don't worry. They're all explained in the specially-written 128-page book (free with every ZX80). The book makes learning easy, exciting and enjoyable, and represents a complete course in BASIC programming—from first principles to complex programs.


Kit or built—it's up to you

In kit form, the ZX80 is pleasantly easy to assemble, using a fine-tipped soldering iron. And you may already have a suitable mains adaptor—600 mA at 9V DC nominal unregulated. If not, see the coupon.

Both kit and built versions come complete with all necessary leads to connect to your TV (colour or black and white) and cassette recorder. Plug in and you're ready to go. (Built versions come with mains adaptor.)

personal computer.

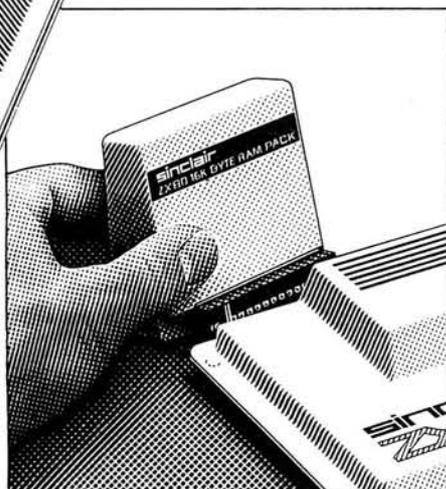Now available for the ZX80... New 16K-BYTE RAM pack



Massive add-on memory. Only £49.95.

The new 16K-BYTE RAM pack is a complete module designed to provide you – and your Sinclair ZX80 – with massive add-on memory. You can use it for those really long and complex programs – or as a personal database. (Yet it can cost as little as half the price of competitive add-on memory for other computers.)

For example, you could write an interactive or 'conversational' program to show people what your ZX80 can do. With 16K-BYTES of RAM, they could be talking to your computer for hours!

Or you can store a mass of data – perhaps in a fairly simple program – such as a name and address list, or a telephone directory.

And by linking a number of separate programs together into one giant, but modular, program, you can achieve the same effect as loading several programs at once.


We're also confident that it won't be long

before you can buy cassette-based software using the full 16K-BYTE RAM. So keep an eye on the personal computer magazines – and brush up your chess perhaps!

The RAM pack simply plugs into the existing expansion port on the rear of the ZX80. No wires, no soldering. It's a matter of seconds and you don't need another power supply. You can only add one RAM pack to your ZX80 – but with 16K-BYTES who could want more!

How to order

Demand for the ZX80 exceeds all other personal computers put together! So use the coupon to order today for the earliest possible delivery. All orders will be despatched in strict rotation. We'll acknowledge each order by return, and tell you exactly when your ZX80 will be delivered. If you choose not to wait, you can cancel your order immediately, and your money will be refunded at once. Again, of course, you may return your ZX80 as received within 14 days for a full refund. We want you to be satisfied beyond all doubt – and we have no doubt that you will be.

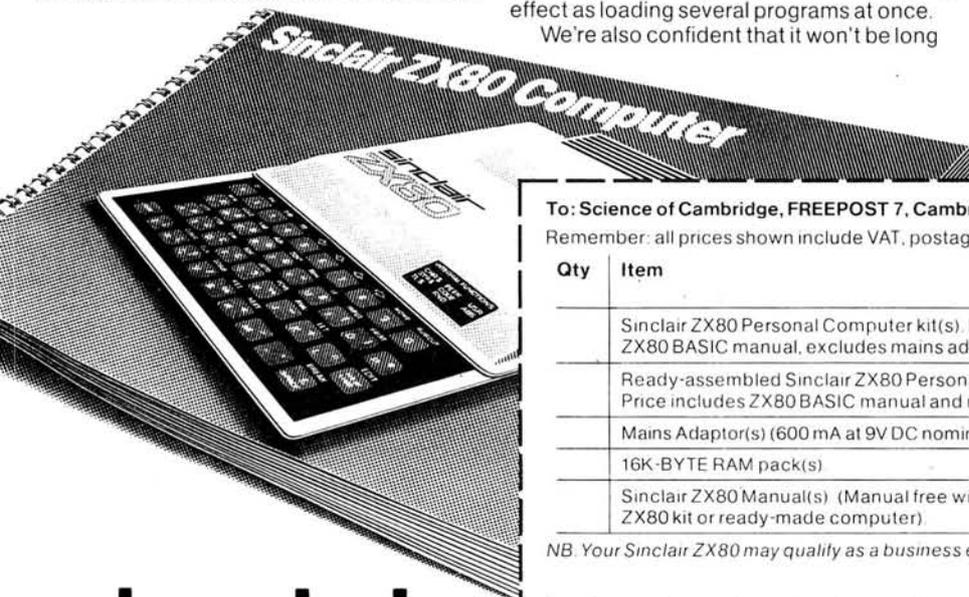

To: Science of Cambridge, FREEPOST 7, Cambridge CB2 1YY.

Remember: all prices shown include VAT, postage and packing. No hidden extras. Please send me

Qty	Item	Code	Item price £	Total £
	Sinclair ZX80 Personal Computer kit(s). Price includes ZX80 BASIC manual, excludes mains adaptor.	02	79.95	
	Ready-assembled Sinclair ZX80 Personal Computer(s). Price includes ZX80 BASIC manual and mains adaptor.	01	99.95	
	Mains Adaptor(s) (600 mA at 9V DC nominal unregulated)	03	8.95	
	16K-BYTE RAM pack(s)	18	49.95	
	Sinclair ZX80 Manual(s) (Manual free with every ZX80 kit or ready-made computer).	06	5.00	

NB. Your Sinclair ZX80 may qualify as a business expense.

TOTAL: £

I enclose a cheque/postal order payable to Science of Cambridge Ltd for £ _____
Please print

Name: Mr/Mrs/Miss _____

Address _____

FREEPOST – no stamp needed.

PRW04

sinclair ZX80

Science of Cambridge Ltd.

6 Kings Parade, Cambridge, Cambs., CB2 1SN.
Tel: 0223 311488.



We use advanced winding technology to make our toroidal transformers. They have only half the weight and height of their laminated equivalents and are appreciably more efficient. Our toroids cost virtually the same as the older types which they are rapidly replacing. Induced hum is reduced by a factor of ten. Supplied with rigid mounting kit with centre bolt, steel and neoprene washers.

30VA 70mm dia. x 30mm Weight 0.45 Kg **£4.71**
(+£1.00 p.p. + 0.86 VAT)

TYPE	SECONDARY RMS VOLTS	SECONDARY RMS CURRENT
1X010	6+6	2.50
1X011	9+9	1.66
1X012	12+12	1.25
1X013	15+15	1.00
1X014	18+18	0.83
1X015	22+22	0.68
1X016	25+25	0.60
1X017	30+30	0.50

50VA 80mm dia. x 35mm Weight 0.9 Kg **£5.19**
(+£1.10 p.p. + 0.94 VAT)

2X010	6+6	4.16
2X011	9+9	2.77
2X012	12+12	2.08
2X013	15+15	1.66
2X014	18+18	1.38
2X015	22+22	1.13
2X016	25+25	1.00
2X017	30+30	0.83
2X028	110	0.45
2X029	220	0.22
2X030	240	0.20

80VA 90mm dia. x 30mm Weight 1 Kg **£5.76**
(+£1.20 p.p. + £1.04 VAT)

3X010	6+6	6.64
3X011	9+9	4.44
3X012	12+12	3.33
3X013	15+15	2.66
3X014	18+18	2.22
3X015	22+22	1.81
3X016	25+25	1.60
3X017	30+30	1.33
3X028	110	0.72
3X029	220	0.36
3X030	240	0.33

120VA 90mm dia. x 40mm Weight 1.2 Kg **£6.72**
(+£1.30 p.p. + £1.20 VAT)

4X011	9+9	6.66
4X012	12+12	5.00
4X013	15+15	4.00
4X014	18+18	3.33
4X015	22+22	2.72
4X016	25+25	2.40
4X017	30+30	2.00
4X028	110	1.09
4X029	220	0.54
4X030	240	0.50

160VA 110mm dia. x 40mm Weight 1.8 Kg **£8.88**
(+£1.40 p.p. + £1.54 VAT)

TYPE	SECONDARY RMS VOLTS	SECONDARY RMS CURRENT
5X012	12+12	6.66
5X013	15+15	5.33
5X014	18+18	4.44
5X015	22+22	3.63
5X016	25+25	3.20
5X017	30+30	2.66
5X018	35+35	2.28
5X028	110	1.45
5X029	220	0.72
5X030	240	0.66

225VA 110mm dia. x 45mm Weight 2.2 Kg **£10.59**
(+£1.50 p.p. + £1.81 VAT)

6X014	18+18	6.25
6X015	22+22	5.11
6X016	25+25	4.50
6X017	30+30	3.75
6X018	35+35	3.21
6X028	40+40	2.81
6X028	110	2.04
6X029	220	1.02
6X030	240	0.93

300VA 116mm dia. x 50mm Weight 2.6 Kg **£12.27**
(+£1.60 p.p. + £2.08 VAT)

7X016	25+25	6.00
7X017	30+30	5.00
7X018	35+35	4.28
7X026	40+40	3.75
7X025	45+45	3.33
7X028	110	2.72
7X029	220	1.36
7X030	240	1.25

500VA 146mm dia. x 60mm Weight 4 Kg **£16.35**
(£1.70 p.p. + £2.71 VAT)

8X017	30+30	8.33
8X018	35+35	7.14
8X026	40+40	6.25
8X025	45+45	5.55
8X033	50+50	5.00
8X028	110	4.54
8X029	220	2.27
8X030	240	2.08

• I.L.P. TOROIDAL TRANSFORMERS ARE GUARANTEED FOR 5 YEARS

CHOICE OF 3 PRIMARY INPUTS

I.L.P. Toroidal Transformers are available in choice of 110V, 220V, 240V, coded as follows: (Secondaries can be connected in series or parallel)
For 110V Primary insert 0 in place of "X" in type number.
For 220V Primary (Europe) insert 1 in place of "X" in type number.
For 240V Primary (U.K.) insert 2 in place of "X" in type number.
Example - 120VA 240V 15+15V, 4A = 42013.

• CUSTOMER DESIGN ENQUIRIES INVITED. QUANTITY PRICE LIST AVAILABLE.

FREEPOST facility (U.K. only).

Simply address envelope to **FREEPOST** to address below. NO STAMP REQUIRED.

TO ORDER Enclose cheque/Postal Order/Money Order payable to I.L.P. Electronics Ltd or quote your ACCESS or BARCLAYCARD account No. To pay C.O.D. add £1 extra to TOTAL value of order. Also available from ELECTROVALUE and MARSHALLS.



VALVES		PDS00/510		UAF42		5B/255M		6F12	
A1065 1.40	ECH42 1.20	EY51 0.95	4.30	JBF40 1.20	11.50	6F12 1.50	6F12 1.50	6F12 1.50	6F12 1.50
A2293 8.80	ECH81 0.70	EY81 0.65		JBF80 0.70	8.80	6F15 1.30	6F15 1.30	6F15 1.30	6F15 1.30
A2900 9.20	ECH84 0.80	EY86/87 0.60		JBL1 1.25	9.20	6F17 1.15	6F17 1.15	6F17 1.15	6F17 1.15
AR8 0.75	ECL80 0.70	EZ80 0.65	2.85	JBL21 1.75	1.75	6F23 0.75	6F23 0.75	6F23 0.75	6F23 0.75
ARP3 0.70	ECL82 0.75	EZ81 0.70	1.80	JCC84 0.85	0.85	6F24 1.75	6F24 1.75	6F24 1.75	6F24 1.75
ATP4 3.60	ECL83 1.40	EZ82 1.30	0.60	JCC85 0.70	0.70	6F33 10.50	6F33 10.50	6F33 10.50	6F33 10.50
B12H 3.90	ECL85 0.80	EZ83 1.05	0.60	JCC86 0.70	0.70	6F38 0.95	6F38 0.95	6F38 0.95	6F38 0.95
CV31 1.40	ECL86 0.90	EZ84 2.30	1.45	JCC87 0.75	0.75	6F46 1.50	6F46 1.50	6F46 1.50	6F46 1.50
DAF96 0.70	EF37A 1.50	EZ85 1.95	0.90	JCC88 0.95	0.95	6F52 0.75	6F52 0.75	6F52 0.75	6F52 0.75
DET22 21.95	EF39 1.25	EZ86 3.30	1.50	JCC89 0.70	0.70	6F54 1.25	6F54 1.25	6F54 1.25	6F54 1.25
DF96 0.70	EF40 1.25	EZ87 2.30	1.50	JCC90 0.70	0.70	6F56 1.50	6F56 1.50	6F56 1.50	6F56 1.50
DK96 1.20	EF41 1.30	EZ88 8.95	13.80*	JCC91 0.75	0.75	6F57 1.30	6F57 1.30	6F57 1.30	6F57 1.30
DH76 0.75	EF80 0.65	EZ89 2.50	1.50	JCC92 0.70	0.70	6F58 0.60	6F58 0.60	6F58 0.60	6F58 0.60
DL92 0.60	EF83 1.75	EZ90 2.90	1.50	JCC93 0.85	0.85	6F59 0.60	6F59 0.60	6F59 0.60	6F59 0.60
DY86/87 0.65	EF85 0.60	EZ91 2.90	1.50	JCC94 0.85	0.85	6F60 0.60	6F60 0.60	6F60 0.60	6F60 0.60
E551 14.20	EF86 0.75	EZ92 2.90	1.50	JCC95 0.85	0.85	6F61 0.60	6F61 0.60	6F61 0.60	6F61 0.60
EB8CC 1.60	EF88 0.75	EZ93 2.90	1.50	JCC96 0.85	0.85	6F62 0.60	6F62 0.60	6F62 0.60	6F62 0.60
EB8CC01 3.10	EF89 0.65	EZ94 2.90	1.50	JCC97 0.85	0.85	6F63 0.60	6F63 0.60	6F63 0.60	6F63 0.60
EB8CC 1.20	EF83 0.80	EZ95 2.90	1.50	JCC98 0.85	0.85	6F64 0.60	6F64 0.60	6F64 0.60	6F64 0.60
EB8CC 2.80	EF184 0.80	EZ96 2.90	1.50	JCC99 0.85	0.85	6F65 0.60	6F65 0.60	6F65 0.60	6F65 0.60
EB8CC 4.95	EF804 4.95	EZ97 2.90	1.50	JCC100 0.85	0.85	6F66 0.60	6F66 0.60	6F66 0.60	6F66 0.60
EB8CC 1.25	EF812 1.25	EZ98 2.90	1.50	JCC101 0.85	0.85	6F67 0.60	6F67 0.60	6F67 0.60	6F67 0.60
EB8CC 2.25	EF1200 1.85	EZ99 2.90	1.50	JCC102 0.85	0.85	6F68 0.60	6F68 0.60	6F68 0.60	6F68 0.60
EB8CC 0.60	EH90 0.85	EZ100 2.90	1.50	JCC103 0.85	0.85	6F69 0.60	6F69 0.60	6F69 0.60	6F69 0.60
EB91 0.60	EL32 1.10	EZ101 2.90	1.50	JCC104 0.85	0.85	6F70 0.60	6F70 0.60	6F70 0.60	6F70 0.60
EB93 1.15	EL34 1.80	EZ102 2.90	1.50	JCC105 0.85	0.85	6F71 0.60	6F71 0.60	6F71 0.60	6F71 0.60
EB98 0.60	EL37 4.40	EZ103 2.90	1.50	JCC106 0.85	0.85	6F72 0.60	6F72 0.60	6F72 0.60	6F72 0.60
EB98 0.60	EL38 4.60	EZ104 2.90	1.50	JCC107 0.85	0.85	6F73 0.60	6F73 0.60	6F73 0.60	6F73 0.60
EB98 0.60	EL41 1.40	EZ105 2.90	1.50	JCC108 0.85	0.85	6F74 0.60	6F74 0.60	6F74 0.60	6F74 0.60
EC52 0.85	EL81 0.95	EZ106 2.90	1.50	JCC109 0.85	0.85	6F75 0.60	6F75 0.60	6F75 0.60	6F75 0.60
EC91 3.40	EL82 0.70	EZ107 2.90	1.50	JCC110 0.85	0.85	6F76 0.60	6F76 0.60	6F76 0.60	6F76 0.60
EC92 0.85	EL84 0.80	EZ108 2.90	1.50	JCC111 0.85	0.85	6F77 0.60	6F77 0.60	6F77 0.60	6F77 0.60
EC98 0.60	EL86 0.85	EZ109 2.90	1.50	JCC112 0.85	0.85	6F78 0.60	6F78 0.60	6F78 0.60	6F78 0.60
EC98 0.60	EL86 0.85	EZ110 2.90	1.50	JCC113 0.85	0.85	6F79 0.60	6F79 0.60	6F79 0.60	6F79 0.60
EC98 0.65	EL91 4.20	EZ111 2.90	1.50	JCC114 0.85	0.85	6F80 0.60	6F80 0.60	6F80 0.60	6F80 0.60
EC98 0.60	EL95 0.80	EZ112 2.90	1.50	JCC115 0.85	0.85	6F81 0.60	6F81 0.60	6F81 0.60	6F81 0.60
EC98 0.60	EL95 0.80	EZ113 2.90	1.50	JCC116 0.85	0.85	6F82 0.60	6F82 0.60	6F82 0.60	6F82 0.60
EC98 0.60	EL95 0.80	EZ114 2.90	1.50	JCC117 0.85	0.85	6F83 0.60	6F83 0.60	6F83 0.60	6F83 0.60
EC98 0.60	EL95 0.80	EZ115 2.90	1.50	JCC118 0.85	0.85	6F84 0.60	6F84 0.60	6F84 0.60	6F84 0.60
EC98 0.60	EL95 0.80	EZ116 2.90	1.50	JCC119 0.85	0.85	6F85 0.60	6F85 0.60	6F85 0.60	6F85 0.60
EC98 0.60	EL95 0.80	EZ117 2.90	1.50	JCC120 0.85	0.85	6F86 0.60	6F86 0.60	6F86 0.60	6F86 0.60
EC98 0.60	EL95 0.80	EZ118 2.90	1.50	JCC121 0.85	0.85	6F87 0.60	6F87 0.60	6F87 0.60	6F87 0.60
EC98 0.60	EL95 0.80	EZ119 2.90	1.50	JCC122 0.85	0.85	6F88 0.60	6F88 0.60	6F88 0.60	6F88 0.60
EC98 0.60	EL95 0.80	EZ120 2.90	1.50	JCC123 0.85	0.85	6F89 0.60	6F89 0.60	6F89 0.60	6F89 0.60
EC98 0.60	EL95 0.80	EZ121 2.90	1.50	JCC124 0.85	0.85	6F90 0.60	6F90 0.60	6F90 0.60	6F90 0.60
EC98 0.60	EL95 0.80	EZ122 2.90	1.50	JCC125 0.85	0.85	6F91 0.60	6F91 0.60	6F91 0.60	6F91 0.60
EC98 0.60	EL95 0.80	EZ123 2.90	1.50	JCC126 0.85	0.85	6F92 0.60	6F92 0.60	6F92 0.60	6F92 0.60
EC98 0.60	EL95 0.80	EZ124 2.90	1.50	JCC127 0.85	0.85	6F93 0.60	6F93 0.60	6F93 0.60	6F93 0.60
EC98 0.60	EL95 0.80	EZ125 2.90	1.50	JCC128 0.85	0.85	6F94 0.60	6F94 0.60	6F94 0.60	6F94 0.60
EC98 0.60	EL95 0.80	EZ126 2.90	1.50	JCC129 0.85	0.85	6F95 0.60	6F95 0.60	6F95 0.60	6F95 0.60
EC98 0.60	EL95 0.80	EZ127 2.90	1.50	JCC130 0.85	0.85	6F96 0.60	6F96 0.60	6F96 0.60	6F96 0.60
EC98 0.60	EL95 0.80	EZ128 2.90	1.50	JCC131 0.85	0.85	6F97 0.60	6F97 0.60	6F97 0.60	6F97 0.60
EC98 0.60	EL95 0.80	EZ129 2.90	1.50	JCC132 0.85	0.85	6F98 0.60	6F98 0.60	6F98 0.60	6F98 0.60
EC98 0.60	EL95 0.80	EZ130 2.90	1.50	JCC133 0.85	0.85	6F99 0.60	6F99 0.60	6F99 0.60	6F99 0.60
EC98 0.60	EL95 0.80	EZ131 2.90	1.50	JCC134 0.85	0.85	6F100 0.60	6F100 0.60	6F100 0.60	6F100 0.60
EC98 0.60	EL95 0.80	EZ132 2.90	1.50	JCC135 0.85	0.85	6F101 0.60	6F101 0.60	6F101 0.60	6F101 0.60
EC98 0.60	EL95 0.80	EZ133 2.90	1.50	JCC136 0.85	0.85	6F102 0.60	6F102 0.60	6F102 0.60	6F102 0.60
EC98 0.60	EL95 0.80	EZ134 2.90	1.50	JCC137 0.85	0.85	6F103 0.60			

OFF THE SHELF
DELIVERY ON THESE



BRAND NEW FROM FLUKE ... NOW AVAILABLE THE 8024A HAND HELD DMM

This model incorporates all the features of the 8020A but in addition has:

A peak hold switch which can be used in AC or DC for volts and current functions.

Audible continuity testing and level detection for sensing logic levels.


A temperature (°C) range for use with a thermocouple.

£149

Carriage and Insurance £3

The following accessories are in stock now

Y8008 Touch and Hold Probe.....	£18.00
80K-40 High Voltage Probe.....	£45.00
81RF RF Probe to 100 MHz.....	£32.00
80T-150C Temperature Probe (C).....	£55.00
801-600 Clamp-on AC Current Probe.....	£55.00

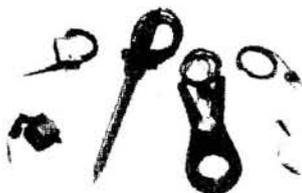

HERE IT IS ... THE EVER POPULAR 8022A HAND-HELD DMM

Consider the following features:
6 resistance ranges from 200 ohm-20 ohms.
8 current ranges from 2mA-2A AC/DC.
10 voltage ranges from 200 mv-1000v DC-200 mc-750V AC.
Pocket size - weighing only 370 gms.
Full overload protection - will withstand 6kv spikes.
Rugged construction - virtually indestructible.
Meets tough military specs. - drop proof.
In line pushbutton operation for single-handed usage.
Incorporates low power CMOS chip for low power consumption.
All this plus a 2-year full guarantee.



NOW only £75

Carriage and Insurance £3

**Soft carrying case
£7 extra**


Even more sophisticated the Fluke 8020A.
Identical in most respects to the 8022A but in addition incorporates a conductance range from 2mS-200nS.

Price £125

Carriage and Insurance £3.00

A handsome soft carrying case is included (this model only)

OFF THE SHELF
DELIVERY ON THESE

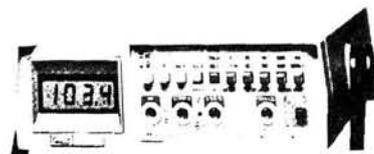

8010A AND 8012A BENCH MODEL D.M.M.s

The 8010A is a general purpose, bench/portable digital multimeter with more functions and features than ever offered for such a low price. Its companion, the 8012A, has identical characteristics except that it has two additional low resistance ranges, 2Ω and 20Ω to replace the 8010A's 10 ampere current range.

The 8010A and 8012A feature:
10 voltage ranges from 200mv-1000v dc; 200mv-75v ac.
3 conductance ranges from 2mS-200nS.
6 resistance ranges from 200Ω-20MΩ the 8012A has two additional resistance ranges 2Ω and 20Ω.
10 current ranges from 200μA-2A AC DC the 8010A has two additional current ranges 10A AC and 10A DC.

8010A £159 8012A £199

Carriage and Insurance £3.


The 8010A is also available with two rechargeable Nicad size C batteries installed in option 01 a - **£179.00.**

PLEASE ADD 15% VAT TO ALL ORDERS except where items marked "VAT Included". CALLERS WELCOME.

We are open 9 a.m.-6 p.m. Monday-Saturdays. We carry a very large selection of electronic components and electro-mechanical items. Special quotations on quantities.

ELECTRO-TECH COMPONENTS LTD.

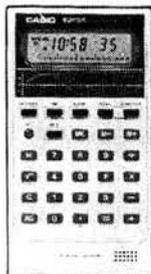364 EDGWARE ROAD, LONDON, W.2. TEL: 01-723 5667



BIOLATOR & WATCH

CASIO BQ-1100

Clock, calendar, two alarms, countdown alarm, stopwatch, time memory, three date memories.
Calculator with date calculations & BIORHYTHM CALCULATIONS
Forecast your physical, emotional and intellectual performance potential.
Chart your peak, ebb and critical days and reschedule to avoid mistakes.
2 silver oxide batteries last approx. 1 year.
Dims: 1/4 x 2 7/16 x 4 3/8 inches.
Supplied with leatherette wallet.

ONLY £14.95

JOIN THE KEYBOARD REVOLUTION!

A remarkable new concept in electronic keyboard instruments using a totally new technology. Pitch, timbre and harmonics of a variety of instruments have been measured, digitalised and stored in an electronic chip memory for faithful and exciting reproduction.

NEW CASIOTONE

401
£295
RRP £345



Polyphonic playing of 14 instruments.

A total of 16 different rhythm functions with full-in auto-rhythm Casio Auto Chord allows you to perform single-finger accompaniment. Just press the key with a single finger and it will play chord and bass accompaniments automatically. At-a-glance, simple-to-use operational panel contains vibrato, delayed vibrato, sustain and hold. A compact 4 3/8 x 3 1/8 x 12 3/8 inches with integral amplifier and speaker, the light weight (28.2lb) allows playing anywhere there is an A.C. socket.

SEND 25p for details of Casiotone keyboards, Casio quality calculators and the ultimate quality watches from Casio and Seiko.

PRICES include VAT, P.&P. Remember we will try and beat lower prices. Return of post service. Send cheques, P.O. or phone your ACCESS or BARCLAYCARD number to:

TEMPUS

Dept. PW, Beaumont Centre, 164-167 East Rd.,
Cambridge CB1 1DB Tel: 0223 312866



68
LARGER
PAGES

The larger
Catalogue
that means
FREE POSTAGE
IN U.K.

- ADDITIONAL DISCOUNTS
 - KEEN PRICES
 - GUARANTEED SATISFACTION
 - GOOD STOCKS
 - GOOD DELIVERY
- We Pay Postage

Semi-Conductors • I.C.s • Opto-devices • Rs and Cs in great variety
• Pots • Switches • Knobs •
Accessories • Tools • Materials •
Connectors


ELECTROVALUE

FREE FOR THE ASKING

ELECTROVALUE LTD. (PW2),
28 St. Jude's Road, Englefield Green, Egham, Surrey TW20 0HB.
Phone: 33603 (London 87) STD 0784. Telex 264475.
NORTHERN (Personal Shoppers Only): 680 Burnage Lane, Burnage,
Manchester M19 1NA. Phone (061) 432 4945.

MICROSCOPE

Illuminated pocket microscope — zooms in

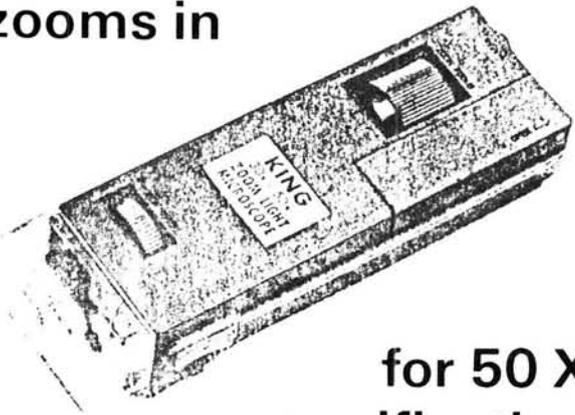

for 50 X magnification

Measuring only 130 x 40 x 18 mm, this Intel illuminated pocket microscope has a normal magnification of 30 X which can be increased to 50 X by using the zoom facility. Focus control and illumination are built-in so that the instrument can typically be used in the close inspection of specimens, samples and tissues by medical students, doctors, technicians and medical laboratory scientists. It uses longlife batteries and comes in a plastic case.

Price: £12.99 incl. case, V.A.T. and post/packing.
For immediate despatch send cheque with order to:

THE VALVE AND TUBE SPECIALIST VALVES AT NEW LOW PRICES

RECEIVING, SQ. TRANSMITTING, DISPLAY, GAS FILLED, ETC.

Type No.	Price ea.						
BK448	95.65	EF37A	4.43	M8137	1.20	QY4-250	72.00
B75B	33.15	EF39	2.10	M8162	4.00	QZ06-20	24.10
D77	0.80	EF80	0.80	M8163	2.85	RG1-240A	16.00
DF61	0.56	EF85	0.91	M8212	0.85	TY2-125	61.80
DM160	3.20	EF86	0.80	ME1400	3.50	TY4-400	62.27
DY86/87	0.64	EF89	0.72	OA2	2.10	XG1-2500	59.60
E55L	15.00	EF91	1.85	OB2	2.55	5U4G	1.95
E80CC	5.65	EF92	2.20	EN92	3.10	5V4G	1.35
E80CF	11.02	EF93	0.60	PC86	0.83	6AK6	2.40
E80F	6.32	EF95	4.88	PC88	0.83	6A06	1.30
E82CC	1.85	EF183	1.60	PC97	1.40	6AU6	0.95
E83CC	3.50	EF184	0.75	PC900	0.58	6BH6	1.20
E83F	2.10	EH90	0.86	PCC65	1.10	6BR7	6.00
E86C	6.20	EK90	0.90	PCC89	1.50	6BS7	4.00
E88C	5.84	EL34	1.64	PCC189	1.75	7BW6	5.30
E88CC	4.00	EL36	0.82	PCF80	0.87	6BW7	1.45
E92CC	1.65	EL37	5.20	PCF86	1.58	6C4	1.30
E99F	4.00	EL81	1.48	PCF200	2.15	6L6GT	1.60
E130L	16.30	EL84	0.96	PCF801	0.95	6S4A	1.25
E180CC	4.65	EL86	1.65	PCF802	0.81	6SJ7G	1.10
E180F	5.45	EL90	1.25	PCF805	1.40	6SL7GT	2.68
E182CC	8.00	EL91	5.85	PCF808	1.40	6SN7GT	0.90
E186F	5.50	EL95	1.28	PCH200	1.10	6V6GT	0.95
E288CC	7.40	EL360	6.20	PCL82	0.74	6X5GT	2.00
E810F	14.47	EN91	2.56	PCL84	0.83	12A15	1.85
EAFB01	3.15	EN92	3.18	PCL85	0.85	12A06	1.85
EBC81	0.85	EY51	1.66	PCL86	0.85	12BH7	0.98
EB91	0.95	EY84	0.88	PD500	3.90	12SN7GT	2.00
EC91	1.82	EY86	0.64	PL200	1.40	29C1	10.00
EC92	0.94	EY88	1.25	PL36	1.15	30FL2/1	1.20
ECC81	0.78	EY500A	1.65	PL81	0.80	30PL14	1.95
ECC82	0.60	EY802	0.96	PL84	0.75	90C1	2.80
ECC83	0.78	E280	0.58	PL95	1.10	90CG	13.68
ECC84	1.19	E281	0.75	PL504	1.58	90CV	9.00
ECC85	0.82	E290	1.30	PL508	1.85	92AG	7.96
ECC88	1.20	GXU1	15.00	PL509	2.75		
ECC91	2.10	G232	1.45	PL802	2.90		
ECC2000	4.50	G234	1.45	PY88	0.78		
ECF80	0.80	KT61	5.10	PY500A	1.55		
ECF82	0.80	KT66	4.25	PY800	1.20		
ECH81	0.75	M8079	10.69	PY81/801	0.68		
ECL80	0.95	M8081	4.40	QV06-20	11.50		
ECL82	0.63	M8082	2.14	QV03-20	22.75		
ECL85	0.82	M8083	3.50	QV06-40A	21.85		
ECL86	0.94	M8100	3.00	QV02-6	12.04		
		M8136	0.85				

INTEL ELECTRONIC COMPONENTS LTD.
30/50 Ossory Road, London SE1 5AN. Tel: 237 0404

INTERESTED IN ELECTRONICS? TRY A ZEDPACK! COMPONENTS AT A PRICE EVERYONE CAN AFFORD

- Z1 300 mixed 1/2 and 1/4 watt resistors £1.95
- Z2 150 mixed 1 and 2 watt resistors £1.50
- Z3 300 mixed capacitors, most types £3.95
- Z4 100 mixed electrolytics £2.20
- Z5 100 mixed polystyrene caps £2.20
- Z6 300 mixed printed circuit components £1.95
- Z7 300 mixed printed circuit resistors £1.45
- Z9 100 mixed miniature ceramic and plate caps £1.20
- Z10 25 assorted pots. £1.50
- Z11 25 assorted presets, skeleton etc. £1
- Z12 20 assorted vdr's and thermistors £1.20
- Z13 1lb mixed hardware. Nuts, bolts self-tappers, sleeves, etc. £1.20
- Z14 100 mixed, new and marked, full spec. transistors. Pack includes:- BC148, BF154, BF274, BC212L, BC238, BC183L, PBC108 and, or lots of similar types. £4.95
- Z15 100 mixed diodes including:- zener, power, bridge, signal, germanium, silicon etc. All full spec. £4.95
- Z18 20 assorted zeners. 1 watt and 400mw £1.50
- Z20 10 assorted switches. Slide, push-button, multibank, miniature, reed etc. £1.20
- TBA 800 Audio I.C. 80p ea. 3 for £2.
- Delux FIBREGLASS printed circuit etching kits. £1.20
- Includes 100 sq. ins. of copperclad F/G board, 1lb ferric chloride, (made for U.S. Army to MIL SPEC), 1 dalo etch resist pen, abrasive cleaner, tweezers, etch resist dish and instructions. OUR PRICE £5.95
- 1lb of FeCl. £2.25
- 150 sq. ins. single sided board. £2.20
- 150 sq. ins. double sided board. £3.30
- UHF, Transistors T.V. TUNER with slow motion drive, AE.skt. and leads. £1.95
- 100 Miniature reed switches. £2.30
- MINIATURE MAINS TRANSFORMERS
- Top quality. Split bobbin construction will give 4.5V-0.4.5V at 250MA. 1 1/2" x 1 1/2" x 1 1/2", all sorts of uses. ONLY £1.3 for £2.50
- TO: "GEMINI ELECTRONIC COMPONENTS" DEPT PW "THE WAREHOUSE" SPEEDWELL ST. LONDON S.E.8.
- Please Quote ZED Code, Where shown. Send Cheque* or Postal Order. Plus 60p P&P. *Schools etc. SEND OFFICIAL ORDER
- ZED PACKS now available for Callers at 50 Deptford Broadway, London, S.E.8.

PP3 Battery Connectors 10 for 50p
Miniature Press to Make Switches, Red knob, 3 for 50p
Subminiature S.P.C.O. Slide Switches. 6 for 50p.
Miniature D.P.C.O. Slide Switches. 6 for 50p.
Standard 2P, 3 Position Slide Switch. 4 for 50p.
4 - HP11 Battery Holders (2 - 2 Flat type) with leads. 2 for 50p.
Assorted Fuse Holders including 20mm, P.C. Panel and chassis types. Pack of 7 for 50p.
3.5mm Jack Sockets, switched. Enclosed type. P.C. or panel mounting. With nuts and washers. 4 for 50p.

R.C. SUPPRESSORS
250V, 1" x 1/2" x 1/2". Ideal for fluorescent light suppression, car, and relays. Also for snubber networks. 3 for £1

ALTERNATOR RECTIFIERS
Make lovely 60 amp 150V bridges. Ideal for High Power Battery Chargers. Type 4AF1. Set of 4 (2 neg. case - 2 pos. case) £2.

Special Purchase enables us to offer Mullard C280 Polyester Capacitors (Liquorice Allsorts) at the unbeatable price of £2 for 100 mixed. These consist of factory clearance lots i.e. spillages, floor sweepings, cosmetic rejects etc. Also Mullard miniature electrolytics 200 mixed £2.

TELESCOPIC AERIALS
Chrome on brass, 9 section, 25" extended. Plugs into any 3.5mm jack socket. Ideal for S.W.R., metre, portable TV, etc. ONLY £1

BB105B VARICAP DIODES
20 for £1.50.

Professional quality TV Plugs (coax.)
Diecast alloy body, Silver Plated solid brass centre pin, brass grubcrew for centre conductor. 50p ea, 5 for £2. Ideal for video's.

UHF MODULATORS
Calibrated to Channel 36 625 line UHF. Housed in metal box, 2 1/2" x 2" x 1/2". Complete with 9 feet of coax lead and TV plug. 5p operation, ideal for video games, computers etc. £2.50 ea with connection Data.

Vernitron FM4 10.7MHz ceramic filters
50p ea, 3 for £1.

SPECIAL OFFER SURPLUS STOCK TO CLEAR. BULK PURCHASE.

Qty.	Pence	Qty.	Pence	Qty.	Pence	Qty.	Pence
8-2114	1800	10-AD162	230	5-BU208	500	5-7447	250
8-4116	2100	2-AU113	250	5-C106D	130	5-7490	140
1-2708	320	10-BC107	80	5-DL704	300	10-7473DC	180
1-2716	650	10-BC108	80	5-DL707	600	10-7474	250
1-2114	300	10-BC109	80	10-LM380	650	5-7485	400
10-4116	300	5-BCY34	200	100-NE555	1800	10-7493	250
10-7805	480	10-BD131	250	10-OC29	800	5-7495	250
10-7812	480	10-BD132	250	10-OC35	900	10-74107J	200
10-7815	480	10-BD135	220	5-R2540	600	5-74119	500
10-7905	450	10-BD137	210	5-TBA550	500	5-74141	190
10-AC126	160	10-BD139	210	5-TBA800	280	5-74157	300
10-AC127	160	10-BF180	200	5-TBA920	550	5-74175	250
10-AC128	160	10-BF258	200	10-TIP41	250	5-74180	350
10-AC187	160	10-BFY50	150	5-TIP2955	225	5-74182	350
10-AC188	160	10-BFY51	150	5-TIP3055	225	10-2N5061	200
10-AD149	500	10-BT106	650	5-7414	200	5-2N3055	210
10-AD161	230	5-BU205	400				

MAIL ORDER ONLY

Please add 30p P&P and VAT at 15%. Govt. Colleges, etc. Orders accepted. Quotations given for large quantities.

SUNMIT ELECTRONICS

96 PEEL ROAD, WEMBLEY, MIDDLESEX, ENGLAND.
Tel. 01-908 1928.

MARCO TRADING

ZENER DIODES: 400mw, 3V to 33V 8p each, 100 for £6.00 (your mix). 1 Watt, 3V to 200V 15p each, 100 for £12.50 (your mix).
I.C. SOCKETS: 5 pin - 7p, 8 pin - 9p, 14 pin - 10p, 16 pin - 11p, 18 pin - 13p, 20 pin - 16p, 24 pin - 20p, 28 pin - 28p, 40 pin - 32p. QUANTITY PRICES ON APPLICATION.
RESISTORS: 1W, Low Noise, High Stab. 5% Tolerance, Carbon Film, E12 Series, 2.2 ohm to 10M 2p each, 15p/10, 100 for 95p, 1000 mixed in 100's only £8.00.
SPECIAL RESISTOR PACK: 10 of each value 2.2Ω to 2MΩ, 730 resistors only £6.00. Amazing value. 1W Resistors, E12 range from 2.2 ohm to 10M. All 5%. 5p each. 2W Resistors, E12 range from 100 ohm to 10M. All 5%.

CERAMICS: 63V Working Subminiature, Low Tolerance, 1.8pF-100nF, 4p each.
TANTALUMS: 35V, 0.1µ, 0.15µ, 0.22µ, 0.33µ, 0.47µ, 0.68µ, 1.0µ = 12p each, 2.2µ, 3.3µ, 4.7µ, 6.8µ, 35V = 14p each. 10/35V 18p, 22/35 38p, 47/10V 25p, 33/10V 22p, 100/3V 20p, 68/3V 20p each.

L.E.D.s: 3mm RED 12p each, Green 18p each, Yellow 18p each, incl. Clips. 5mm RED 12p each, Green 18p each, Yellow 18p each, 100 Red (3 or 5mm) for £5.50 excluding Clips. E12 range from 100 ohm to 10M. Vertical & Horizontal, all 5%.

SKELTON PRE-SETS: 1000 to 1M Vertical & Horizontal, all 5%.

BRIDGE REC'S: 1) A 50V 36p, 2A 200V 44p, 25A 50V £2.38, 25A 100V £2.41.

TRANSISTORS: BC107/8/9 10p, BC147/8/9 8p, BC182/3/4 9p, BC172 8p, BF200 28p, BC212/3/4 9p, 212L/3/4L 10p, BF180/81 29p, AC128 20p, AD161/2 45p, 2N3055 22p, 2N3819 25p, 2N3053 20p, BC125 10p, BF262/3 30p, 1N4001 5p, 1N4007 8p, 741 20p, NE555 25p, LM380 80p.

CMOS: 4001B 20p, 4011B 20p, 4076 90p, 4081 20p, 2N414 90p.

ELECTROLYTICS: A is Axial; R is Radial; 1/63C A 7p, 2.2/25 R 4p, 4.7/25 R 5p, 10/16 R 4p, 22/16 R 4p, 28/25 A 3p, 47/16 R 5p, 47/25 A 5p, 100/3 A 5p, 100/16 R 6p, 220/16 A 9p, 470/16 A 12p, 1000/16 A 16p, 1000/63 A 62p, 4700/16 R 55p.

This advert is only a fraction of our range, send 25p for our latest catalogue. Please add 35p P/P to all orders. (Free over £5.00). Add 15% VAT to total. Send orders to:

Dept. PW6, MARCO TRADING,
The Old School, Edstaston, WEM, Shropshire SY4 5RJ.
All orders despatched by return of mail. Tel: (094872) 464/465.

MONOLITH

QUALITY REEL TO REEL & CASSETTE TAPE HEADS + MECHANISMS

YOUR EXTRA HEAD!

A NEW TAPE HEAD COULD TRANSFORM THE QUALITY OF YOUR TAPE RECORDER

MEET OUR NEW C42RPS18, THE HIGH PERFORMANCE STEREO HEAD WITH SEPARATE RECORD & PLAYBACK CHANNELS FOR IMPROVED DYNAMIC RANGE & RECORD MONITORING.

POPULAR UNIVERSAL CASSETTE TAPE HEADS

B12-02 Mono Record/Playback.....	£4.62	C42RPH04 Stereo GLASS FERRITE R/P.....	£13.34
B24-01 Stereo Playback.....	£4.62	C42RPS18 Stereo TWIN GAP R + P.....	£28.99
B24-02 Stereo Record/Plbk.....	£7.66	C21ES18 Mono/stereo erase.....	£2.13
B24-07 Stereo R/P. (Dolby Stsm).....	£7.87	C44RPH03 Quad 1/2 track R/P.....	£15.15
C42RPH20 Stereo SENDUST R/P.....	£10.67	C44RP2ES01 Quad 1/2 track combined R/P + Erase.....	£30.42
C42RP1ES01 Stereo combined R/P + Erase.....	£12.57	C22ES03 Twin half track erase.....	£5.43
		C42ES02 DC 1/2 track erase.....	£4.23

SEND FOR OUR TAPE HEAD CATALOGUE 30p

MONOLITH

PLEASE ENCLOSE 20p P&P WITH ORDER

THE MONOLITH ELECTRONICS CO. LTD. ALL PRICES INCLUDE VAT

5/7 CHURCH ST., CREWKERNE, SOMERSET, ENGLAND. (0460) 74321

All these advantages...

- Instant all-weather starting
- Smoother running
- Continual peak performance
- Longer battery & plug life
- Improved fuel consumption
- Improved acceleration/top speed
- Extended energy storage

..in kit form

SPARKRITE X5 is a high performance, top quality inductive discharge electronic ignition system designed for the electronics D.I.Y. world. It has been tried, tested and proven to be utterly reliable. Assembly only takes 1-2 hours and installation even less due to the patented 'clip on' easy fitting

The superb technical design of the Sparkrite circuit eliminates problems of the contact breaker. There is no misfire due to contact breaker bounce which is eliminated electronically by a pulse suppression circuit which prevents the unit firing if the points bounce open at high R.P.M. Contact breaker burn is eliminated by reducing the current by 95% of the norm

There is also a unique extended dwell circuit which allows the coil a longer period of time to store its energy before discharging to the plugs. The unit includes built in static timing light, systems, function light, and security changeover switch. Will work all rev counters.



Fits all 12v negative-earth vehicles with coil/distributor ignition up to 8 cylinders.

THE KIT COMPRISES EVERYTHING NEEDED
Die pressed case Ready drilled, aluminium extruded base and heat sink, coil mounting clips and accessories. All kit components are guaranteed for a period of 2 years from date of purchase. Fully illustrated assembly and installation instructions are included.

Roger Clark the world famous rally driver says "Sparkrite electronic ignition systems are the best you can buy."



Sparkrite

HIGH PERFORMANCE ELECTRONIC IGNITION
Electronics Design Associates, 82 Bath Street, Walsall, WS1 3DE.

TRAIN AT HOME

Be an ELECTRONIC ENGINEER

Do something PRACTICAL about your future. Firms all over Britain are crying out for qualified people. With the right training, you could take your pick of these jobs.

Now, the British Institute of Engineering Technology will train you in your spare time to be an Electrical Engineer.

You risk nothing! We promise to get you through your chosen course—or, refund your fee!

So, join the thousands who have built a new future through home study Engineering courses.

- Courses in
- C & G Elect. Technicians
 - C & G Elect. Installations
 - Telecomms. Technicians Exams
 - Television Servicing
 - Radio Maint. & Repairs (BIET)
 - Pract. Radio & Electronics
- Plus over 60 other home study courses.

POST COUPON FOR FREE 44 PAGE GUIDE

BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY

Aldermaston Court, Dept TPW11, Reading RG7 4PF.

NAME (Block capitals please) _____

ADDRESS _____

POSTCODE _____

Other Subjects _____ AGE _____

Accredited by CACC Member of ABCC

Electronics Design Associates, Dept. PW481
82 Bath Street, Walsall, WS1 3DE. Phone: (0922) 614791

Name _____

Address _____

Phone your order with Access or Barclaycard
Inc. V.A.T and P.P. QUANTITY REQD. I enclose cheque/PO's for

X5KIT £16.95

ACCESS OR BARCLAY CARD No. _____

£ _____

Cheque No. _____

Send SAE if brochure only required.

THE SHAPE OF THINGS TO COME!

MOTOR CYCLING

April issue on sale Sat., March 14.

Keep in touch with the dramatic changes in the motorcycling world by reading our great value-for-money magazine, every month.

In the April issue.

SPRING BIKE BUYERS GUIDE

What to look for in performance and economy when choosing a new or second hand bike.

SUZUKI SPECIAL

Off-road sports plans for 1981 and a road test of their GSX 400 and GSX 550LT models.

TOOLS OF THE TRADE

Home servicing pays if you've got the right equipment for a basic workshop.



THREE BIKE TRAIL TEST
An off-road, rough rider look at the BMW R80 G/S, Can-Am 350 and Kawasaki KE 125. How do they cope when the going gets rough.

and all your regular features and tests!
Motorcycling out every month...
everything for the motorcyclist.
Place a regular order! 60p.

AH ELECTRONICS

20 BARBY LANE, HILLMORTON, RUGBY, WARWICKSHIRE CV22 5QJ. TEL: 76473 EVE 71066.

Mail Order Only or callers by appointment. All prices include VAT but add 50p post & packing.

VHF RF. POWER TRANSISTORS:-

Type	Gain (db)	Output (watts)	Volts	Freq.	Price
2N6083	5.7	30w.	12	175MHz	£6.50
BLY87A	9	8	12	175	£4.00
SD1212-6	8.2	3	12	175	£2.50
BLW16A	10	3	12	175	£0.75
PT4236A	10	1 min.	12	175	£0.75
PT4555	8	25	12	80	£3.50
PT4556C	7	40	12	80	£4.50
2N5070	13	25(pep)	24	30	£5.00

MDA800 8 amp 50 volt bridge rectifier OK for 12v PSU etc. 65p. 2 for £1.15. DUAL-GATE MOSFETS 3SK51 (40673) 80p, BFR84 75p.

FETs E5565 (2N3819) 30p, TIS88A 40p, BF256C 40p, 2N4381 40p. BIPOLARS:- BF576, pnp VHF RF amp, FT1200 MHz 20p, 2N4957 pnp

VHF/UHF RF amp of only 3db = 1GHz 30p, BF180 30p, BF166 VHF RF amp 25p, BF90 UHF RF amp 95p, BF152 VHF mix/osc. 15p.

SILICON PIN DIODES for switching oscillators etc. up to 1000MHz - BA243 (VHF) 20p, BA244 (UHF) 25p.

AUDIO AMP IC. TDA1010 6 watt output adjustable to 9 watt. + 14 volt single-line type & ideal for transceivers, receivers, record players, cassette players etc. BARGAIN OFFER ONLY £1.35 two for £2.40. Supplied with data sheet showing construction of stereo amp. full data sheet (19 pages) 20p.

27-30 MHz RECEIVER PRE-AMP. Have you a tired or old receiver with poor performance above 25MHz then one of our super pre-amps is what you want - 50 ohm imp. in & out 25db gain with better than 1db nf. ready built on PCB 60mmx40mm, adjustable gain control, only £8.00 or built into grey hammer finish die cast box with BNC sockets £12.50.

10.7 MHz SSB CRYSTAL FILTERS Cathode type BP4133 lower sideband only, new & unused small size 38mm x 18mm x 15mm 200 ohm imp. give away PRICE ONLY £4.00 each two for £7.00.

10.7 MHz CRYSTAL FILTER for AM/FM 12 1/2 KHz channel spacing +3 1/2 KHz + 3db ITT type 024DE/923L. £7.00 ea.

MOTOROLA CAR RADIO PCBs complete less vol. cont. tuner etc. with circuit 80p ea. four for £3.00.

CAR RADIO 470 KHz IF AMPS with stereo pre-amp IC. with circuit 65p.

CAR RADIO/CASSETTE PLAYER stereo amps 5 watt/chan. with multigang pot. matching amp to above IF amp board. Contains 2 TA7205P ICs, with circuit £2.75.

BAG MIXED ELECTROLYTIC CAPACITORS 2.2mf - 1000Mfd 100 £1.60.

BAG OF MIXED RESISTORS 1/2 watt carbon film pre-formed type all with long leads plus some 1/2 watt std types 250 for £1.60.

FEEDTHROUGH CAPACITORS 1000pf 500v solder in type 1/2" dia. 10 for 28p.

FERRITE RINGS 12mm dia 10p ea. FERRITE BEADS FX1115 10 for 20p.

PRICE LIST 15p STAMP - FREE WITH ORDER.

PROGRESSIVE RADIO

ALL ORDERS DESPATCHED BY RETURN POST

SEMICONDUCTORS. 2N5062 (100V 800mA) SCR 18p. BX504 opto isolator 25p. CA3130 95p. TBA800 50p. Tag4443 SCR 45p. Texas R1038 power trans. 50p. TDA1151 25p.

SWITCHES. Min. toggles. SPST 8x5x7mm 42p. DPDT 8x7x7mm 55p. DPDT c/off 12x11x9mm 77p. HEAVY DUTY-DPDT 240VAC 10 Amp 35p. PUSH TYPE, push on 16x6mm

15p, push to break version 17p. MERCURY (TILT) SWITCH. 1" x 1/2" 35p.

ANTEX SOLDERING IRONS: Models C15, CX17 and X25 all £3.95 each. NSA1198 8 1/2 digit multiplexed displays, com. cath. with data sheet £1.45p. SPECIAL OFFER TIL209 Red LED's 10 for 75p. 0.2" LEDs, red, yellow, green 10p each.

LINEAR I.C.'s. LM300 40p, LM301 55p, LM308 £1.30, LM324 £1.00, LM388 95p, LM388 50p, LM386 90p, LM3900 80p, LM3909 75p, CA1310 £1.70, CA3018 £1.00, CA3028 £1.40, CA3035 £2.20, CA3046 85p, CA3098 95p, CA3130 95p, CA3140 37p, MC1303 £1.40, MC1312 £1.60, MC1330 £1.40, MC1458 40p, NE550 £1.00, NE544 £1.40, NE565 £1.70, NE566 £1.70, TAA550 40p, TAA621 £2.20, NE556 50p, C106D SCR 35p.

GPO TELEPHONE DIALS £1.00 (new). JACKSONS C804 50pf var. capacitors 50p each.

TOOLS. 5 piece precision screwdriver sets, individual handles only £1.05 set. JUMPER TEST LEAD SETS. 10 pairs of leads with insulated crocs each end 90p.

40KHZ TRANSDUCERS, RX/TX £3.50 pair.

STC BREAK GLASS FIRE ALARM UNITS, new with mounting box £1.50p.


MINIATURE SOLID STATE BUZZERS. 2 voltages available, 6 or 12VDC 75p each. Loud 12 volt buzzers 65p.

Cash with order please, official orders welcome from schools etc., please add 30p postage and packing, VAT inclusive. SAE for latest illustrated stock list.

31, CHEAPSIDE, LIVERPOOL L2 2DY

METALFILM RESISTORS

1% Tolerance, 1/4 Watt

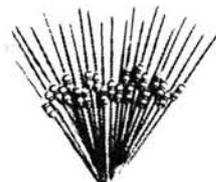

ONLY 4P EACH

Minimum order £10
Minimum 5 pcs per value
89 Values (E24)

100R	1k	10k	100k
110R	1k1	11k	110k
120R	1k2	12k	120k
130R	1k3	13k	130k
150R	1k5	15k	150k
160R	1k6	16k	160k
180R	1k8	18k	180k
200R	2k	20k	200k
220R	2k2	22k	220k
240R	2k4	24k	240k
270R	2k7	27k	270k
300R	3k	30k	—
330R	3k3	33k	330k
360R	3k6	36k	—
390R	3k9	39k	—
430R	4k3	43k	—
470R	4k7	47k	470k
510R	5k1	51k	—
560R	5k6	56k	560k
620R	6k2	62k	—
680R	6k8	68k	680k
750R	7k5	75k	—
820R	8k2	82k	820k
910R	9k1	91k	910k

Special Offer: 5 PCS of EACH (445 RESISTORS) ONLY £16.50.
High Quality, High Stability, High Strength.
VAT inclusive. Add £1.00 p&p all areas.

ORION SCIENTIFIC PRODUCTS LTD.
10 Wardour St., London W1.

TTLs BY TEXAS			LINEAR I.C.s			TRANSISTORS			DIODES								
7400	11p	7487	160p	74LS192	140p	74C157	250p	MC1496	100p	BFY51/2	22p	TIP41C	78p	2N3866	90p	BY127	12p
7401	12p	74100	130p	74LS193	140p	74C160	155p	MC3340	120p	AD127/8	20p	TIP42C	70p	2N3903/4	18p	OA47	9p
7402	14p	74104	65p	74LS195	140p	74C161	155p	MC3360	120p	AD161/2	45p	TIP2955	78p	2N4036	65p	OA81	15p
7403	14p	74105	65p	74LS196	140p	74C162	155p	MC5098	100p	BC107/8	11p	TIP35	34p	2N4060	12p	OA90	9p
7404	14p	74107	34p	74LS221	100p	74C163	155p	NE543K	225p	BC109	11p	TIS93	34p	2N4061/2	18p	OA91	9p
7405	18p	74109	55p	74LS240	175p	74C164	120p	AY5-1224A	225p	BC147/8	9p	TIS93	34p	2N4123/4	22p	OA95	9p
7406	32p	74110	55p	74LS241	175p	74C174	160p	AY5-1317	750p	BU108	250p	TIS93	34p	2N4125/6	22p	OA200	10p
7407	32p	74111	55p	74LS242	175p	74C175	210p	AY5-1317	750p	BU108	250p	TIS93	34p	2N4125/6	22p	OA202	10p
7408	19p	74116	20p	74LS243	175p	74C192	150p	CA3046	70p	BU108	250p	TIS93	34p	2N4125/6	22p	OA202	10p
7409	19p	74118	130p	74LS244	195p	74C193	150p	CA3048	72p	BU108	250p	TIS93	34p	2N4125/6	22p	OA202	10p
7410	15p	74119	210p	74LS245	200p	74C194	220p	CA3080E	225p	BU108	250p	TIS93	34p	2N4125/6	22p	OA202	10p
7411	24p	74120	11p	74LS246	200p	74C195	110p	CA3080E	225p	BU108	250p	TIS93	34p	2N4125/6	22p	OA202	10p
7412	20p	74121	28p	74LS247	200p	74C221	175p	CA3080E	225p	BU108	250p	TIS93	34p	2N4125/6	22p	OA202	10p
7413	30p	74122	48p	74LS248	200p	4000 SERIES		CA3080E	225p	BU108	250p	TIS93	34p	2N4125/6	22p	OA202	10p
7414	60p	74123	48p	74LS249	200p	CA3130E	100p	CA3130E	100p	BU108	250p	TIS93	34p	2N4125/6	22p	OA202	10p
7415	60p	74124	48p	74LS250	175p	CA3140E	70p	CA3140E	70p	BU108	250p	TIS93	34p	2N4125/6	22p	OA202	10p
7416	27p	74125	55p	74LS251	175p	CA3160E	75p	CA3160E	75p	BU108	250p	TIS93	34p	2N4125/6	22p	OA202	10p
7417	27p	74126	60p	74LS252	220p	CA3170E	75p	CA3170E	75p	BU108	250p	TIS93	34p	2N4125/6	22p	OA202	10p
7418	27p	74127	60p	74LS253	220p	CA3180E	75p	CA3180E	75p	BU108	250p	TIS93	34p	2N4125/6	22p	OA202	10p
7419	27p	74128	75p	74LS254	220p	CA3190E	75p	CA3190E	75p	BU108	250p	TIS93	34p	2N4125/6	22p	OA202	10p
7420	17p	74129	75p	74LS255	220p	CA3200E	75p	CA3200E	75p	BU108	250p	TIS93	34p	2N4125/6	22p	OA202	10p
7421	40p	74132	75p	74LS256	220p	CA3210E	75p	CA3210E	75p	BU108	250p	TIS93	34p	2N4125/6	22p	OA202	10p
7422	22p	74136	60p	74LS257	220p	CA3220E	75p	CA3220E	75p	BU108	250p	TIS93	34p	2N4125/6	22p	OA202	10p
7423	34p	74141	70p	74LS258	220p	CA3230E	75p	CA3230E	75p	BU108	250p	TIS93	34p	2N4125/6	22p	OA202	10p
7424	30p	74142	200p	74LS259	220p	CA3240E	75p	CA3240E	75p	BU108	250p	TIS93	34p	2N4125/6	22p	OA202	10p
7425	30p	74145	90p	74LS260	220p	CA3250E	75p	CA3250E	75p	BU108	250p	TIS93	34p	2N4125/6	22p	OA202	10p
7426	40p	74146	150p	74LS261	220p	CA3260E	75p	CA3260E	75p	BU108	250p	TIS93	34p	2N4125/6	22p	OA202	10p
7427	34p	74147	190p	74LS262	220p	CA3270E	75p	CA3270E	75p	BU108	250p	TIS93	34p	2N4125/6	22p	OA202	10p
7428	36p	74148	150p	74LS263	220p	CA3280E	75p	CA3280E	75p	BU108	250p	TIS93	34p	2N4125/6	22p	OA202	10p
7429	36p	74149	150p	74LS264	220p	CA3290E	75p	CA3290E	75p	BU108	250p	TIS93	34p	2N4125/6	22p	OA202	10p
7430	17p	74150	100p	74LS265	220p	CA3300E	75p	CA3300E	75p	BU108	250p	TIS93	34p	2N4125/6	22p	OA202	10p
7431	17p	74151	100p	74LS266	220p	CA3310E	75p	CA3310E	75p	BU108	250p	TIS93	34p	2N4125/6	22p	OA202	10p
7432	17p	74152	100p	74LS267	220p	CA3320E	75p	CA3320E	75p	BU108	250p	TIS93	34p	2N4125/6	22p	OA202	10p
7433	40p	74153	70p	74LS268	220p	CA3330E	75p	CA3330E	75p	BU108	250p	TIS93	34p	2N4125/6	22p	OA202	10p
7434	40p	74154	70p	74LS269	220p	CA3340E	75p	CA3340E	75p	BU108	250p	TIS93	34p	2N4125/6	22p	OA202	10p
7435	35p	74155	90p	74LS270	220p	CA3350E	75p	CA3350E	75p	BU108	250p	TIS93	34p	2N4125/6	22p	OA202	10p
7436	35p	74156	90p	74LS271	220p	CA3360E	75p	CA3360E	75p	BU108	250p	TIS93	34p	2N4125/6	22p	OA202	10p
7437	35p	74157	90p	74LS272	220p	CA3370E	75p	CA3370E	75p	BU108	250p	TIS93	34p	2N4125/6	22p	OA202	10p
7438	35p	74158	90p	74LS273	220p	CA3380E	75p	CA3380E	75p	BU108	250p	TIS93	34p	2N4125/6	22p	OA202	10p
7439	35p	74159	90p	74LS274	220p	CA3390E	75p	CA3390E	75p	BU108	250p	TIS93	34p	2N4125/6	22p	OA202	10p
7440	17p	74160	100p	74LS275	220p	CA3400E	75p	CA3400E	75p	BU108	250p	TIS93	34p	2N4125/6	22p	OA202	10p
7441	70p	74161	100p	74LS276	220p	CA3410E	75p	CA3410E	75p	BU108	250p	TIS93	34p	2N4125/6	22p	OA202	10p
7442	60p	74162	100p	74LS277	220p	CA3420E	75p	CA3420E	75p	BU108	250p	TIS93	34p	2N4125/6	22p	OA202	10p
7443	112p	74163	100p	74LS278	220p	CA3430E	75p	CA3430E	75p	BU108	250p	TIS93	34p	2N4125/6	22p	OA202	10p
7444	112p	74164	100p	74LS279	220p	CA3440E	75p	CA3440E	75p	BU108	250p	TIS93	34p	2N4125/6	22p	OA202	10p
7445	100p	74165	100p	74LS280	220p	CA3450E	75p	CA3450E	75p	BU108	250p	TIS93	34p	2N4125/6	22p	OA202	10p
7446	93p	74166	100p	74LS281	220p	CA3460E	75p	CA3460E	75p	BU108	250p	TIS93	34p	2N4125/6	22p	OA202	10p
7447	70p	74167	100p	74LS282	220p	CA3470E	75p	CA3470E	75p	BU108	250p	TIS93	34p	2N4125/6	22p	OA202	10p
7448	80p	74168	100p	74LS283	220p	CA3480E	75p	CA3480E	75p	BU108	250p	TIS93	34p	2N4125/6	22p	OA202	10p
7449	80p	74169	100p	74LS284	220p	CA3490E	75p	CA3490E	75p	BU108	250p	TIS93	34p	2N4125/6	22p	OA202	10p
7450	17p	74170	200p	74LS285	220p	CA3500E	75p	CA3500E	75p	BU108	250p	TIS93	34p	2N4125/6	22p	OA202	10p
7451	17p	74171	200p	74LS286	220p	CA3510E	75p	CA3510E	75p	BU108	250p	TIS93	34p	2N4125/6	22p	OA202	10p
7452	17p	74172	200p	74LS287	220p	CA3520E	75p	CA3520E	75p	BU108	250p	TIS93	34p	2N4125/6	22p	OA202	10p
7453	17p	74173	200p	74LS288	220p	CA3530E	75p	CA3530E	75p	BU108	250p	TIS93	34p	2N4125/6	22p	OA202	10p
7454	17p	74174	200p	74LS289	220p	CA3540E	75p	CA3540E	75p	BU108	250p	TIS93	34p	2N4125/6	22p	OA202	10p
7455	17p	74175	200p	74LS290	220p	CA3550E	75p	CA3550E	75p	BU108	250p	TIS93	34p	2N4125/6	22p	OA202	10p
7456	17p	74176	200p	74LS291	220p	CA3560E	75p	CA3560E	75p	BU108	250p	TIS93	34p	2N4125/6	22p	OA202	10p
7457	30p	74178	160p	74LS292	220p	CA3570E	75p	CA3570E	75p	BU108	250p	TIS93	34p	2N4125/6	22p	OA202	10p
7458	30p	74179	160p	74LS293	220p	CA3580E	75p	CA3580E	75p	BU108	250p	TIS93	34p	2N4125/6	22p	OA202	10p
7459	30p	74180	160p	74LS294	220p	CA3590E	75p	CA3590E	75p	BU108	250p	TIS93	34p	2N4125/6	22p	OA202	10p
7460	30p	74181	160p	74LS295	220p	CA3600E	75p	CA3600E	75p	BU108	250p	TIS93	34p	2N4125/6	22p	OA202	10p
7461	100p	74182	90p	74LS296	220p	CA3610E	75p	CA3610E	75p	BU108	250p	TIS93	34p	2N4125/6	22p	OA202	10p
7462	100p	74183	90p	74LS297	220p	CA3620E	75p	CA3620E	75p	BU108	250p	TIS93	34p	2N4125/6	22p	OA202	10p
7463	100p	74184	150p	74LS298	220p	CA3630E	75p	CA3630E	75p	BU108	250p	TIS93	34p	2N4125/6	22p	OA202	10p
7464	100p	74185	150p	74LS299	220p	CA3640E	75p	CA3640E	75p	BU108	250p	TIS93	34p	2N4125/6	22p	OA202	10p
7465	100p	74186	150p	74LS300	220p	CA3650E	75p	CA3650E	75p	BU108	250p	TIS93	34p	2N4125/6	22p	OA202	10p
7466	100p	74187	150p	74LS301	220p	CA3660E	75p	CA3660E	75p	BU108	250p	TIS93	34p	2N4125/6	22p	OA202	10p
7467	100p	74188	150p	74LS302	220p	CA3670E	75p	CA3670E	75p	BU108	250p	TIS93	34p	2N4125/6	22p	OA202	10p
7468	100p	74189	150p	74LS303	220p	CA3680E	75p	CA3680E	75p	BU108	250p	TIS93	34p	2N4125/6	22p	OA202	10p
7469	100p	74190	150p	74LS304	220p	CA3690E	75p	CA3690E	75p	BU108	250p	TIS93	34p	2N4125/6	22p	OA202	10p
7470	100p	74191	150p	74LS305	220p	CA3700E	75p	CA3700E	75p	BU108							



When replying to Classified Advertisements please ensure:

- (A) That you have clearly stated your requirements.
- (B) That you have enclosed the right remittance.
- (C) That your name and address is written in block capitals, and
- (D) That your letter is correctly addressed to the advertiser.

This will assist advertisers in processing and despatching orders with the minimum of delay.

Receivers and Components

BRAND NEW COMPONENTS BY RETURN

HIGH STABILITY RESISTORS.

1W Carbon Film E12 Series 1R-10M. (E24 2R-6M2)—1p
1/2W 1/4W & 1W Metal Film E12 Series 10R-2M2—2p

CAPACITORS.
MULLARD Min. Ceramic E12 100V 2% 1.8pf. to 47pf.—3p
2% 56pf. to 330pf.—4p. 10% 390pf. to 4700pf.—4p

E12 22pf. to 1000pf. & E6 1K5pf. to 47Kpf.—2p
Plate Ceramic 50V Wkg. Vertical Mounting.

Miniature Polyester 250V Wkg. Vertical Mounting.
.01. .015. .022. .033. .047 & .068 mfd.—4p
0.1—5p. 0.15 & 0.22—6p. 0.33 & 0.47—8p
0.68—11p. 1.0—15p. 1.5—20p. 2.2—22p

ELECTROLYTIC. Wire Ended (Mfds/Volts)

0.47/50	5p	22/25	51p	100/25	7p	470/25	11p
10/50	5p	22/50	6p	100/50	8p	470/40	16p
2/250	5p	47/16	6p	220/15	8p	1000/15	15p
4/750	5p	47/25	6p	220/25	8p	1000/25	18p
10/50	5p	47/50	6p	220/50	10p	1000/40	35p
22/16	6p	100/16	7p	470/16	11p	2200/16	20p

TANTALUM BEAD SUBMINIATURE ELECTROLYTICS.
0.1. 0.22. 0.47. 1.0. 2.2 + 35V & 4.7 + 6.3V—14p
4.7/16V & 25V—15p. 10/16 & 22/6—20p. 10/25—29p
10/35V. 22/16V. 47/6.3V. 68/3V & 100/3V—30p
15/25. 22/25. 47/10—35p. 47/16—80p. 220/16—£1.20

Polystyrene 63V Wkg. E12 Series Long Axial Wires.
10 pf. to 820 pf.—3p. 1000 pf. to 10,000pf.—4p

TRANSISTORS.

BC107/8/9	10p	BC182L	8p	BF197	10p
BC147/8/9	10p	BC184L	8p	BFY50/51/52	18p
BC157/8/9	10p	BC212L	8p	BFY88	25p
BC547C/8C/9C/7p	BCY70	15p	2N2926	7p	
BC557C/8C/9C/7p	BF194	10p	2N3055	50p	

B Pin D.I.L. i.c.s 741 Op/amp.—18p. 555 Timer—24p
Holders 8 pin—9p. 14 Pin—12p. 16 Pin—14p. 28 Pin—25p
40 Pin—30p.

DIODES (p.i.v./amps).

75/25mA	1N4148	2p	1250 1A	BY127	10p
100 1A	1N4002	4p	400/3A	1N5404	14p
800 1A	1N4006	6p	60 1.5A	51M1	5p
1000 1A	1N4007	7p	30 150mA	AAV32	12p

ZENER DIODES.

E24 Series 3V3 to 33V 400mW—8p. 1W—10p
L.E.D.'s 3 mm. & 5 mm Red—10p. Green, Yellow—14p
Grommets for 3 mm.—13p. Holders for 5 mm.—2p
FUSES. 20 mm. Glass. 100mA to 5A. O.B.—3p. A/S—5p

VOLTAGE REGULATORS.—5V. 8V. 12V. 15V 100mA—35p
5V. 8V. 12V. 15V. 18V & 24V 0.5A—60p. 1A—65p
PRESET POTENTIOMETERS
50mW & 1/4W 100R to 1MΩ.—6p

THE C. R. SUPPLY CO.

127, Chesterfield Road, Sheffield S8 0RN.
V.A.T. Inclusive Prices, Postage 15p
(FREE over £5.00)

Southern Valve Co.,

2nd Floor, 6 Potters Road, New Barnet, Herts.

Tel: 01-440 8641 for current prices & availability, all popular valves stocked. SAE Lists. Cash with order. Same Day Postal Despatch. Telephone afternoons preferred.

Valves, Tubes, Aerials etc by LEADING-MAKERS. Send SAE Lists or Phone for current prices. Counter or MAIL ORDER. NO COD. Speedy Despatch assured. No order under £1.

Philip Bearman, 6 Potters Road, New Barnet, Herts.

Tel: 01-449 1934/5 (1934 Recording Machine).

Telephone for Shop Hours.

SMALL ADS

The prepaid rate for classified advertisements is 28 pence per word (minimum 12 words), box number 60p extra. Semi-display setting £9.50 per single column centimetre (minimum 2.5 cms). All cheques, postal orders etc., to be made payable to Practical Wireless and crossed "Lloyds Bank Ltd". Treasury notes should always be sent registered post. Advertisements, together with remittance should be sent to the Classified Advertisement Manager, Practical Wireless, Room 2337, IPC Magazines Limited, King's Reach Tower, Stamford St., London. SE1 9LS. (Telephone 01-261 5846).

VALVES

Radio—T.V.—Industrial—Transmitting
Projector Lamps and Semiconductors

We Dispatch Valves to all parts of the world by return of post, Air or Sea mail, 4000 Types in stock, 1930 to 1976. Obsolete types a speciality. List 50p. Quotations S.A.E. Open to callers Monday to Saturday 9.30 to 5.00 closed Wednesday 1.00. We wish to purchase all types of new and boxed Valves, Projector Lamps and Semiconductors.

COX RADIO (SUSSEX) LTD.

Dept. P.W. The Parade, East Wittering,
Sussex PO20 8BN
West Wittering 2023 (STD Code 024366)

PREWAR ONWARD VALVES, WIRELESS. SAE. Sole Electronics, 37 Stanley Street, Ormskirk, Lancs.

CRYSTALS Brand new high-precision. You benefit from very large stocks held for industrial supplies. All normal freq standards, baud rates, MPU, and all magazine projects inc: HC33 U: 1.0. 1.008. 2.5625 MHz. £3.60. 1.280 MHz. £4-15. HC18 U: 4.0. 5.0. 6.0. 7.0. 8.0. 9.0. 10.0. 10.7. MHz. £3.00. 12.0. 15.0. 16.0. 18.0. 20.0. 8-9375. 38-6667 MHz. £3-25. Selected freqs stocked in Glider, Marine and 27 MHz bands. Any freq made to order in 6 weeks from £3-90.

FILTERS Your best source for 6 and 8 pole and monolithics for AM, CW, SSB, FM, on 455 kHz, 1.6. 9.0. 10.7. 21.4 MHz etc.

Prices inc. VAT and UK post. SAE lists.

P. R. GOLLEDD ELECTRONICS
G3EDW, Merriott, Somerset, TA16 5NS.
Tel: 0460 73718

BOURNEMOUTH/BOSCOMBE. Electronic components specialists for 33 years. Forrester's (National Radio Supplies) late Holdenhurst Rd. now at 36, Ashley Rd., Boscombe. Tel. 302204. Closed Weds.

CRYSTALS MADE TO ORDER within 6 weeks. 4-105MHz, wire or pins. £3.90 each inclusive. HARTLEY CRYSTALS. Green Lane, Milford, Godalming, Surrey GU8 5BG.

£1 BARGAIN PACKS

All packs £1 each; any 12 for £10. Post 25p. All top-grade new components — no rubbish.

PC1 12 BC107	PC9 10 T03 sockets
PC2 14 BC108	PC10 15 0.1/35V tants
PC3 12 BBC109	PC11 14 3mm red LEDs
PC4 3 2N3055	PC12 12 5mm red LEDs
PC5 7 BFY51	PC13 8 741
PC6 16 BC182	PC14 6 555
PC7 60 1N4148	PC15 15 12V zeners
PC8 25 1N4003	PC16 200 1k 1/4W 5% Rs

Send S.A.E. for 8-page list/enquiries.

PC ELECTRONICS,
5 Thornhill, Romsey Road,
Whiteparish, Salisbury, SP5 2SD

TVDX. VHF-UHF Converter (upconverter). Ideal way to start DX on band 1 using UHF TV. £10.50 inc. pp. S.a.e. data lists. H. Cocks, Cripps Corner, Robertsbridge, Sussex. Tel. 058083-317.

1920 VMCR 1960

Old wireless sets, valves and components. Repair, overhaul & restoration. SAE for lists:
VINTAGE MODERN & COMMUNICATIONS RADIOS,

The Old School, Staindrop,

Nr. Darlington, Co. Durham.

Tel: Staindrop (0833) 60452 or 60630

(24 hour telephone answering service)

VINTAGE BRITISH RADIO COMPONENTS CO. offers you a friendly service. Please note our new address: 22, Thurso Walk, Corby, Northants. Tel. Corby 61697.

NOTICE TO READERS

Whilst prices of goods shown in classified advertisements are correct at the time of closing for press, readers are advised to check with the advertiser both prices and availability of goods before ordering from non-current issues of the magazine.

HEATHKIT SW717 4 band short wave receiver. £35. Tel. Rugby 78921.

BALLARD'S OF TUNBRIDGE WELLS have moved to 54 Grosvenor Road, no lists. S.A.E. all enquiries phone Tunbridge Wells 31803.

Books and Publications

Build your own

P.A., GROUP & DISCO SPEAKERS

by R. F. C. Stephens

Save money with this practical guide. Plans for 17 different designs, line source, I.B., Horn and Reflex types, for 8"-18" drive units. £3-95 post free (£8 overseas).

THE INFRA-BASS LOUDSPEAKER

by G. Holliman

(full constructional details for versions using 15", 12" and 10" drive units.) £2-95 post free (£6 overseas)

THE DALESFORD SPEAKER BOOK

by R. F. C. Stephens

This book is a must for the keen home constructor. Latest technology DIY designs. Plans for I.B., and Reflex designs for 10-100 watts. Also unusual centre-bass system. £2-20 post free (£5 overseas).

VAN KAREN PUBLISHING

5 SWAN STREET, WILMSLOW, CHESHIRE

BOOKS

by return of post

How to Make Walkie-Talkies	£1.50
Radio Control for Beginners	£1.75
How to Build Advanced Short Wave Receivers	£1.20
How to Build Your Own Solid State Oscilloscope	£1.50
Remote Control Projects	£1.95
Beginners Guide to Building Electronic Projects	£1.25
IC 555 Projects	£1.75
2nd Book of Transistor Equivalents & Substitutes	£1.10
A Microprocessor Primer	£1.75
Elements of Electronics (set of 3 books)	£6.95

Postage: 1 or 2 books, add 25p. 3 or more post free.

SOLON ELECTRONICS, Dept PW
115 Crescent Drive South, Brighton, BN2 6SB.

Record Accessories

STYLE, cartridges for Music Centres, etc. Free list no. 30 for S.a.e. includes Leads, Mikes, Phones etc. Felstead Electronics, Longley Lane, Gatley, Cheshire, SK8 4EE. Please note closed from March 19th to April 12th, 1981.

Holiday Accommodation

PEMBROKESHIRE — SOLVA. Radio Amateurs — Enjoy a self-catering holiday in our luxury cottages on magnificent unspoilt coast. Near sandy beaches and secluded bays. Equipped and maintained to highest standards by resident owner. Colour T.V., linen, fridge/freezer, washing machine, central heating, VHF and HF antennas available. For colour brochure — M. J. Probert GW4HXO (PW), Ynys, Dawel, Solva, Haverfordwest, Dyfed. Tel. Solva 491.

Wanted

COLLECTOR requires 1920/39 wireless crystal T.V. set also interesting wireless items of the period. Tel. Sevenoaks 62811.

ELECTRONIC COMPONENTS PURCHASED. All types considered — Must be new. Send detailed list — Offer by return — WALTONS, 55A Worcester Street, Wolverhampton.

Educational

CAREERS in Marine Electronics. Courses commencing September and January. Further details, The Nautical College, Fleetwood FY7 8JS. Tel. 03917 79123.

TECHNICAL TRAINING

Get the training you need to move up into a higher paid job. Take the first step now—write or phone ICS for details of ICS specialist homestudy courses on Radio, TV, Audio Eng. and Servicing, Electronics, Computers, also self-build radio kits. Full details from:

ICS SCHOOL OF ELECTRONICS
Dept. 277F Intertext House, London SW8 4UJ
Tel. 01-622 9911 (all hours)
State if under 18

COLOUR TV SERVICING

Learn the techniques of servicing Colour TV sets through new homestudy course approved by leading manufacturers. Covers principles, practice and alignment with numerous illustrations and diagrams. Other courses for radio and audio servicing. Full details from:

ICS SCHOOL OF ELECTRONICS
Dept. 277F Intertext House, London SW8 4UJ
Tel. 01-622 9911 (all hours)
State if under 18

CITY & GUILDS EXAMS

Study for success with ICS. An ICS homestudy course will ensure that you pass your C. & G. exams. Special courses for: Telecoms, Technicians, Electrical Installations, Radio, TV & Electronics Technicians, Radio Amateurs. Full details from:

ICS SCHOOL OF ELECTRONICS
Dept. 277F Intertext House, London SW8 4UJ
Tel. 01-622 9911 (all hours)
State if under 18

TELEVISION COMPUTER & RADAR SYSTEMS SERVICING

TWO YEAR full-time Modular Diploma course to include a high percentage of practical work.

- ELECTRONIC PRINCIPLES
- MONO TV & CCTV
- COLOUR TV & VCR
- DIGITAL TECHNIQUES
- COMPUTERS & MICROPROCESSORS
- RADAR

Each of the above Modules are 12 weeks in duration. Individual Modules can be arranged for applicants with suitable electronics background.

Tuition fees (UK & Overseas) £430 per Module. — Computer Module £500.

Next session starts April 21st.

Prospectus from:

LONDON ELECTRONICS COLLEGE

Dept: PP, 20 Penywern Road,
London SW5 9SU. Tel: 01-373 8721.

Miscellaneous

MORSE CODE TUITION AIDS


Cassette A: 1-12 w.p.m. for amateur radio examination.
Cassette B: 12-24 w.p.m. for professional examination preparation. Each Cassette are type C90.
Morse Key and Buzzer unit for sending practice.
Price each Cassette (including booklets) £4-75. Morse Key and Buzzer £4-75.
Prices include postage etc. Overseas Airmail £1-50 extra.
MHEL ELECTRONICS (Dept 2), 12 Longshore Way, Milton, Portsmouth PO4 8LS.

UK AIRCRAFT FREQUENCIES list spot HF, VHF, UHF, frequencies, airports, air traffic control, etc. £1. UK Marine Frequencies list spot MF, HF, VHF, frequencies, coast stations, ship to shore, etc. £1. International Distress Frequencies chart 75p. PLH Electronics, 20 Vallis Road, Frome, Somerset BA11 3EH.

DIY QSL CARDS, just add your own callsign etc. Also SWL design. 50 for £2.00, 100 for £3.15 inc. p&p. SAE for samples. UHF High pass TV1 filter. £2.40 inc. p&p. Lam Electronics, Dept PW, 47 Golden Miller Road, Cheltenham, Glos. (Tel: 0242 43891 24Hr).

If it's a case of making your project look good, then use one of ours.

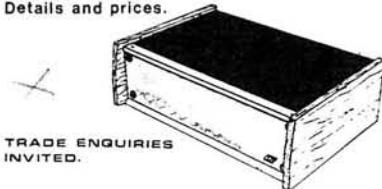Simply send a S.A.E. for Details and prices.



TRADE ENQUIRIES
INVITED.

H.M. ELECTRONICS, P.W.
271a/275a Fulwood Road.
Broomhill
Sheffield S10 3BD

C.W.A.S. ALARM. Send now for the latest discount catalogue of Professional Burglar Alarm Equipment. C.W.A.S. Alarm, 11 Denbrook Walk, Bradford BD4 0QS, W. Yorks. Phone 0274 682674.

TIME WRONG?

MSF CLOCK is ALWAYS CORRECT — never gains or loses, self setting at switch-on, 8 digits show Date, Hours, Minutes and Seconds, auto GMT/BST and leap year, also parallel BCD output and audio to record and show time on playback, receives Rugby 60KHz atomic time signals, built-in antenna, 1000Km range, ABSOLUTE ACCURACY, £54.80.

RARE DX UNDER QRM? DIG IT OUT with a Tunable Audio Notch Filter, between your receiver and speaker, BOOST your DX/QRM ratio, 40dB notch, hear WEAK DX, £10.90.

CAN'T FIND DX? Get SPOT-ON with a Crystal Calibrator, between your antenna and receiver, 1MHz, 100, 25KHz markers to vhf, bypassed when off, MORE DX, £19.80.

V.L.F.? EXPLORE 10-150KHz. Receiver £13.70.
LONG WAVE DX? Exciting 100-600KHz Converter to 4.1-4.6MHz, built-in antenna tuner, £13.90.

Each fun-to-build kit includes all parts, printed circuit, case, postage etc. money back assurance, so GET yours NOW.

CAMBRIDGE KITS

45 (PR) Old School Lane, Milton, Cambridge.

SUPERB INSTRUMENT CASES by Bazelli, manufactured from P.V.C. Faced steel. Hundreds of people and industrial users are choosing the cases they require from our vast range. Competitive prices start at a low £1.05. Chassis punching facilities at very competitive prices. 400 models to choose from. Suppliers only to Industry and the Trade. BAZELLI, (Dept No. 25), St. Wilfrid's, Foundry Lane, Halton, Lancaster LA1 6LT.

ENAMELLED COPPER WIRE

SWG.	1 lb	½ lb	¼ lb
10 to 19	2.95	1.70	0.85
20 to 29	3.05	1.75	0.95
30 to 34	3.45	1.90	1.00
35 to 39	3.75	2.10	1.15
40 to 43	4.95	2.75	2.15
44 to 46	5.90	3.50	2.40

FREE WIRE TABLES WITH EACH ORDER

INDUSTRIAL SUPPLIES

102 Parrswood Road, Withington,
Manchester 20

Prices include P & P in UK

GUITAR/PA/ MUSIC AMPLIFIERS

100 watt superb treble/bass overdrive. 12 months guarantee. Unbeatable at £50; 60 watt £44; 200 watt £68; 100 watt twin channel sep. treble/bass per channel £65; 60 watt £52; 200 watt £78; 100 watt four channel sep. treble/bass per channel £75; 200 watt £98; slaves 100 watt £34; 200 watt £60; 250 watt £70; 500 watt £140; fuzz boxes £12.00; bass fuzz £12.90; overdrive fuzz £22; 100 watt combo superb sound overdrive, sturdy construction, castors, unbeatable £98; twin channel £115; bass combo £118; speakers 15in. 100 watt £36; 12in. 100 watt £24; 60 watt £16; microphone Shure Unidyne B £25; 3-Channel sound/light £26.

Send cheque or P.O. to:

WILLIAMSON AMPLIFICATION

62 Thorncliffe Avenue, Dukinfield, Cheshire.
Tel: 061-308 2064

PRINTED CIRCUITS. Make your own simply, cheaply and quickly! Golden Fotolac Light Sensitive Lacquer — now greatly improved and very much faster. Aerosol cans with full instructions £2.25. Developer 35p. Ferric Chloride 55p. Clear Acetate sheet for master 14p. Copper-clad Fibre-glass. Board approx. 1mm thick £1.70 sq. ft. Post/Packing 75p. **WHITE HOUSE ELECTRONICS**, P.O. BOX 19, Castle Drive, Penzance, Cornwall.

PSYCHOTRONIC GENERATORS, gravity lazars, electrokinesis, electropotography, skinvision. S.a.c. 4x9", Paralab, Downton, Wilts.

KEEP ONE HANDY IN THE WORKSHOP



The unique aerosol treatment for minor burns and scalds. From Boots and other Chemists.

EX GOVT BATTERIES HT AND LT. Send SAE for list. A. Messom, 22, Oakwood Close, Warsash, Southampton, Hants.

P.W. PROJECT PCB'S

(All Boards to be Pre-paid CWO)

Please add P&P at 25p to each Board.

Sept. 80	WRO 95	65p	Oct. 80	WRO 91	450p
Sept. 80	WAD 634	1.85p	Oct. 80	WRO 97	95p
Sept. 80	WRO 96	1.85p	Oct. 80	WRO 82	2.30p
Sept. 80	WRO 86	65p	Nov. 80	WAD 641	60p
Sept. 80	WRO 87	2.25p	Nov. 80	WK 101	58p
Sept. 80	WRO 88	1.40p	Dec. 80	WR 103/103A	1.40p
Sept. 80	WRO 89	1.30p	Dec. 80	WR 101	1.30p
Oct. 80	WRO 90	4.50p	Dec. 80	WR 102	1.30p

Fibreglass Strip Boards (3" x 4") 14 strips 60p each
PCB's made to your own specification. Prototypes or production runs. Full photographic facilities. Other boards not shown available at 15p per sq. inch (min. 60p) + p.&p.

Details or quotation from:

WINSTON PROMOTIONS (P.W.)
9 HATTON PLACE, LONDON EC1N 8RU
TELEPHONE 01-405 0960/4127

THE SCIENTIFIC WIRE COMPANY

PO Box 30, London E 4
Telephone 01 531 1588

ENAMELLED COPPER WIRE

SWG	1 lb	8 oz	4 oz	2 oz
8 to 29	2.76	1.50	0.80	0.60
30 to 34	3.20	1.80	0.90	0.70
35 to 39	3.40	2.00	1.10	0.80
40 to 43	4.75	2.60	2.00	1.42
44 to 47	8.37	5.32	3.19	2.50
48 to 49	15.96	9.58	6.38	3.69

SILVER PLATED COPPER WIRE

14 to 30	6.50	3.75	2.20	1.40
----------	------	------	------	------

TINNED COPPER WIRE

14 to 30	3.85	2.36	1.34	0.90
----------	------	------	------	------

Prices include P&P, VAT and Wire Data.
Orders under £2 please add 20p. SAE for list.
Dealer enquiries welcome.

**PLEASE MENTION
PRACTICAL WIRELESS
WHEN REPLYING
TO ADVERTISEMENTS**

TRANSFORMERS + VAT 15%

30 VOLT RANGE (Split Sec)
Sec Voltages available 3, 4, 5, 6, 8, 9, 10, 12, 15, 18, 20, 24, 30V or 12V-0-12V or 15V-0-15V.

Ref.	30V 15V	Price	P&P
112	5 1	2.90	1.00
79	1 2	3.93	1.00
3	2 4	6.35	1.20
20	3 6	7.39	1.44
21	4 8	8.79	1.60
51	5 10	10.86	1.60
117	6 12	12.29	1.72
88	8 16	16.45	1.96
89	10 20	18.98	1.84
90	12 24	21.09	O.A.
91	15 30	24.18	O.A.
92	20 40	32.40	O.A.

UK postage shown
Overseas post extra
Voltages stated are on full load
Continuous Ratings

60 VOLT RANGE (Split Sec)
Pri 220/240V sec 0-24-30-40-48-60V. Voltages available 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60 or 24V-0-24V or 30V-0-30V.

Ref.	Amps	Price	P&P
124	5 1	4.27	1.20
126	1 2	6.50	1.20
127	2 4	8.36	1.60
125	3 6	12.10	1.72
123	4 8	13.77	1.96
40	5 10	17.42	1.84
120	6 12	19.87	2.04
121	8 16	27.92	O.A.
122	10 20	32.51	O.A.
189	12 24	37.47	O.A.

50 VOLT RANGE (Split Sec)
Sec 50V Voltages available 5, 7, 8, 10, 13, 15, 17, 20, 30, 40 or 20V-0-20V or 25V-0-25V.

Ref.	50V 25V	Price	P&P
102	5 1	3.75	1.20
103	1 2	4.57	1.20
104	2 4	7.88	1.44
105	3 6	9.42	1.60
106	4 8	12.82	1.72
107	6 12	16.37	1.84
118	8 16	22.29	2.20
119	10 20	27.48	O.A.
109	12 24	32.88	O.A.

MAINS ISOLATORS (SCREENED)
Pri 0-120: 0-100-120V (120, 220, 240V). Sec 60-55-0-55-60 (twice to give 55, 60, 110, 115, 120, 125, 175, 180, 220, 225, 230, 235, 240).

Ref.	VA	Price	P & F
*07	20	4.84	1.20
149	60	7.37	1.20
150	100	8.38	1.44
151	200	12.28	1.72
152	250	14.61	2.04
154	500	22.52	2.20
155	750	32.03	O.A.
156	1000	40.92	O.A.
157	1500	56.52	O.A.
158	2000	67.99	O.A.
159	3000	95.33	O.A.

*Pri 0-240V Sec 115 or 240V
State sec. volts required.

CASED AUTO TRANSFORMERS
240V cable in 115V USA flat pin outlet

VA	Price	P & P	Ref.
20	5.55	0.95	56W
75	8.50	1.20	64W
150	11.00	1.44	4W
250	13.39	1.44	69W
500	20.13	2.04	67W
1K	30.67	2.20	84W
1500VA	42.82	O.A.	93W

12 OR 24V OR 12-0-12V
Pri 220/240 volts

Ref.	12V	24V	Price	P&P
111	0 5	0 25	2.42	0.95
213	1 0	0 5	2.90	1.00
71	2 1	1	3.86	1.00
18	4 2	2	4.48	1.20
85	0 5	2 5	6.18	1.20
70	6 3	3	6.99	1.20
108	8 4	4	8.16	1.44
172	10 5	5	8.93	1.60
116	12 6	6	9.89	1.60
17	16 8	8	11.79	1.72
115	20 10	10	15.37	1.84
187	30 15	15	19.72	2.04
226	60 30	30	40.41	O.A.

SCREENED MINIATURES

Ref.	mA	Volts	£	P&P
236	200	3-0-3	2.83	0.50
212	1A, 1A	0-6-0-6	3.14	1.00
13	100	9-0-9	2.35	0.50
235	330, 330	0-9-0-9	2.19	0.60
207	500, 500	0-8-9-0-8-9	3.05	0.95
208	1A, 1A	0-8-9-0-8-9	3.88	1.20
236	200, 200	0-15-0-15	2.19	0.60
214	300, 300	0-20-0-20	3.08	1.00
221	700 (DC)	20-12-0-12-20	3.75	1.00
206	1A, 1A	0-15-0-15	5.09	1.20
203	500, 500	0-15-27	4.39	1.20
204	1A, 1A	0-15-27	6.84	1.20
239	50	12-0-12	2.88	0.50
234	500	6-0-6	2.19	0.44

Send 20p stamps for Catalogue. Prices correct 1/1/81.

AUTO TRANSFORMERS
Voltages available: 105, 115, 190, 200, 210, 220, 230, 240, for step up and step down.

Ref.	VA (Watts)	£	P&P
113*	15	2.73	1.00
64	80	4.41	1.20
4	150	5.89	1.20
53	350	10.08	1.44
67	500	12.09	1.84
84	1000	20.64	2.20
93	1500	25.61	O.A.
95	2000	38.31	O.A.
73	3000	65.13	O.A.
80S	4000	84.55	O.A.
57S	5000	98.45	O.A.

*0, 115, 220, 240.

END OF LINE OFFERS
B7 - 0-110-120-240V 20V

M616 - 0-240V: Screen 11 13-0-13 1A, 21 12V 150mA **£1.50** £1.20

M708 - 6k to 30 matching trans 5 watt **90p** 95p

M679 - 240V, 36V 1.6A **£3.00** 80p

M865 - 100V Line to 40 10 watts **£1.90** £1.00

M1020 - 0-240V 12-0-12V 50mA **75p** 50p

M1126 - 120/240V: 9-0-9V **£1.19** £1.60p

NEW RANGE TRANSFORMERS

2 windings 0-36V-48V/36V-0-36V 48V-0-48V 72V or 96V

Amps	Ref.	Price	P&P
430	4.88	1.20	
1.0	4.31	8.12	1.44
2.0	4.32	13.35	1.22
3.0	4.33	16.17	1.96
4.0	4.34	20.65	2.04
5.0	4.35	29.30	2.20
6.0	4.36	36.69	O.A.
8.0	4.37	40.03	O.A.

Split Bobbin Type
0-12-15-20-24-30V
Ref 009 1 Amp **£2.98** P & P £1.10
Ref 010 2 Amp **£4.62** P & P £1.10

OTHER PRODUCTS

AVO TEST METERS

AVO 8 MK5. Latest Model	£106.40
AVO 71	£43.10
AVO 73	£58.60
AVO MM5 minor	£36.90
AVO Wee Megger	£87.00
AVO T1169 in circuit transistor tester	£45.00
AVO EM272 316K -Volts	£63.40
AVO DA116 Digital	£108.90
DA211 L.C.D.	£47.00
DA212 L.C.D.	£67.00

All Avos Meggers and accessories available.
P & P £1.32 VAT 15%

SPECIAL OFFER
Multimeter 20KΩ B/V - with combined audio/i.f. test oscillator at 1 KHz and 465 KHz AC/DC to 1000 volts DC current to 500mA resistance to 1M. Size 160x97x40mm
£8.50 P & P £1.00 VAT 15%.

EDUCATIONAL METERS (Moving Coil)
0-10A, 0-15V, 0-30V. Freestanding large scale easy read meters with top screw terminals for quick connections.
£4.50 P&P 66p+VAT. Size 75x78mm scale.

Antex Soldering Irons CCN240 15W & 25W
£4.58 each. Safety Stand £1.75 P&P 52p each.

P.W. Purbeck oscilloscope transformer 250-0-250; 6:3V; 12-9V (author approved)
£9.42 £1.04

Soldering Iron - 25W to BS spec. £1.75 P&P 30p+VAT

De-Solder Pumps - Spring loaded with quick action button release for one handed working. Large **£5-10 P&P 35p+VAT**
Small **£4-75 P&P 30p+VAT**. Replacement tips Small **65p+VAT**. Large **86p+VAT**.

Telephones - Latest model, brand new, boxed, 2 tone grey
£11.50 P&P £1.20+VAT.

Metal Oxide Resistors - 1/2W 5% £1.00 per 100. **30p P&P +VAT.**
390Ω/470Ω/510Ω/560Ω/820Ω/1K/1K1/1K2/1K6
1K8/2K/2K4/3K/16K/20K/22K/24K/47K/82K/100K
110K/120/120K/130K/180K/220K/270K/300K
Use instead of Carbon Film (100's only)

43mm x 43mm	82mm x 78mm	500Ω	500V
0 50ΩA	6-20	0 50ΩA	6-70
0 500ΩA	5-95	0 500ΩA	6-70
0 1mA	5-95	0 1mA	6-70
0 30V	5-95	0 30V	6-70

BRIDGE RECTIFIERS
100V 25A **£1.80** 500V
100V 50A **£2.20** PM7A6
200V 2A **£0.52** 12A
200V 4A **£0.75** **£3-75**
400V 1A **£0.25**
400A 4A **£0.98** P&P 20p
400V 6A **£1.44** -VAT.

Barrie Electronics Ltd.
3, THE MINORIES, LONDON EC3N 1BJ
TELEPHONE: 01-488 3316/7/8
NEAREST TUBE STATIONS ALDGATE & LIVERPOOL ST

It's easy to complain about advertisements.

The Advertising Standards Authority.
If an advertisement is wrong, we're here to put it right.
A.S.A. Ltd., Brook House, Torrington Place, London WC1E 7HN.

MODULAR ELECTRONICS

95 HIGH STREET SELSEY, Nr CHICHESTER, SUSSEX. TEL: SELSEY (024361) 2916
DISTRIBUTOR FOR SOLID STATE MICROWAVE (THOMPSON CSF) RF PRODUCTS GBCDS

Type	P/out	Gain	Volts	Freq.	Price
2N3866	1w	10dB	28	175MHz	£0.92
2N4427	1w	10dB	12	175MHz	£1.08
2N3553	2.5w	9dB	28	175MHz	£1.17
2N5913	2w	7dB	12	470MHz	£1.61
SD1127	4w	12dB	12	175MHz	£2.42
2N6080	4w	12dB	12	175MHz	£4.72
SD1143	10w	10dB	12	175MHz	£6.90
2N6081	15w	6.3dB	12	175MHz	£7.48
2N6082	25w	5.7dB	12	175MHz	£8.83
2N6084	40w	4.5dB	12	175MHz	£12.69
SD1428	45w	6.5dB	12	175MHz	£13.28
SD1416	70w	6.7dB	12	175MHz	£24.15
SD1477	100w	6.0dB	12	175MHz	£28.75
2N5590	10w	5.2dB	13.6	175MHz	£6.33
2N5591	25w	4.4dB	13.6	175MHz	£7.49
2N5844	2w	9dB	12	470MHz	£8.78
2N5845	4w	8dB	12	470MHz	£8.83
SD1135	5w	7.5dB	12	470MHz	£5.20
SD1136	10w	6dB	12	470MHz	£7.77
2N5846	10w	6dB	12	470MHz	£10.93
SD1088	25w	6.8dB	12	470MHz	£18.40
SD1089	40w	4.3dB	12	470MHz	£25.30
SD1434	50w	6.0dB	12	470MHz	£28.45

Ex Equip 2N5070 2-30MHz 25wPEP **£2.50**
Ex Equip 2N3632 175MHz 13w **£2.50**
2N5914 RCA 12v 470MHz 2w 7dB **£4.60**
2188BL Mul Studless BLY38 2w 470MHz **£3.45**
61387 RCA Studless Sim C1 12 CTC **£3.45**
Free data sheets with all purchases which include typical circuits etc

LOW NOISE SMALL SIGNAL SEMICONDUCTORS.

BFR90 Mul T Pack 2.5dB N/F 1GHz **£2.82**
BFR91 Mul T Pack 2.5dB N/F 1.2GHz **£3.45**
BFR34a T Pack 4dB N/F GHz **£2.25**
BFT66 Low Intermitt. T072 **£2.59**
SD306 "D" MOS MOSFET **£2.60**
40673 RCA MOSFET **£0.92**
BFR90 UHF MOSFET Equip 3SK88 **£1.30**

UNELCO Cased RF Mica Caps. Following Pfs
10/20/30/40/50/60/70/80pF **£1.61**; 100/150/180/250pF **£1.73**; 1000pF **£1.84**
PFE Sheet 0.25mm 300mm Square **£2.30**
PYE 951170 12v Aerial Relays: SPST Good to 1296MHz **£6.60**
Silver Plated RG43 Type

FINISHED MADE UP AND TESTED EQUIPMENT

PA2 Preamplifier for 2 meters, using the latest UHF stripline MOSFET the BFR90 1" square for fitting in the ng 50Ω in/out imp. Only **£8.05** with instructions.
PAU2 432MHz Preamp. stripline using the BFR34a 14dB gain N/F < 2dB **£8.63.**

LINEAR AMPLIFIER MODULES, without Ch/Over: Size 55x92mm with thermal interface. 50Ω
PM2 10 0.4w in 10w out 13.8V **£18.40**
PM2 15 1.5w in 15w out 13.8V **£19.55**
PM2 25 4w in 25w out 13.8V **£20.99**
CPM LINEAR AMPS with full RF Changeover size 82x102mm preamp can be fitted in RX. SPEC. AS FOR PM Series. Specify CPM type and add **£7.48** to PM series prices.

PRESALER BOARD + 10 Size 55x93mm with input amplifier 12x BFR34a sens 40mV 432mc. uses MGT MC120121 IC. 500MHz typ 600MHz. Only **£23.00.** 5w MGT E supply.

Barrieland or Access an orders above £10.
POST and PACKING add 50p to ALL ORDERS.
Orders sent 1st Class Post where weight permits.
SAME DAY DISPATCH ON ALL IN STOCK ITEMS.
Minimum invoiced order to approved customers **£100.00.**
ALL PRICES NOW INCLUDE VAT AT 15%

WATFORD ELECTRONICS

33/35, CARDIFF ROAD, WATFORD, HERTS, ENGLAND
MAIL ORDER, CALLERS WELCOME. Tel. Watford 40588/9

ALL DEVICES BRAND NEW, FULL SPEC. AND FULLY GUARANTEED. ORDERS DESPATCHED BY RETURN OF POST TERMS OF BUSINESS: CASH/CHEQUE/P.O. OR BANKERS DRAFT WITH ORDER. GOVERNMENT AND EDUCATIONAL INSTITUTIONS OFFICIAL ORDERS ACCEPTED (TELEPHONE ORDERS BY ACCESS NOW ACCEPTED Minimum £10.00 please). TRADE AND EXPORT INQUIRY WELCOME. P & P ADD 40P TO ALL ORDERS UNDER £10.00. OVERSEAS ORDERS POSTAGE AT COST.

VAT Export orders no VAT. Applicable to U.K. Customers only. Unless stated otherwise, all prices are exclusive of VAT. Please add 15% to the total cost.

We stock many more items. It pays to visit us. We are situated behind Watford Football Ground. Nearest Underground/Br. Rail Station: Watford High Street. Open Monday to Saturday 9 a.m. - 6 p.m. Ample Free Car Parking space available.

POLYESTER RADIAL LEAD CAPACITORS: 250V:
10n, 15n, 22n, 27n 6p; 33n, 47n, 68n, 100n 7p; 150n, 220n 10p;
300n, 470n 13p; 580n 19p; 1µ, 2µ, 3µ 46p.

ULTRASONIC TRANSDUCERS
350p per pair.

ELECTROLYTIC CAPACITORS (Values in µF) 50V: 10 52p; 47 78p; 250V: 100 65p; 63V: 1.0 1.5 2.2 3.3 8p; 4.7 9p; 6.8 10 10p; 15 22 12p; 33 15p; 47 12p; 100 19p; 1000 70p; 50V 47 12p; 88 20p; 220 24p; 470 32p; 2200 90p; 40V: 4.7 1.5 2.2 9p; 3300 90p; 4700 120p; 25V: 1.5 5.6 8.10 22 8p; 33 9p; 47 8p; 100 11p; 150 12p; 220 15p; 330 22p; 470 25p; 680 34p; 2200 50p; 3300 76p; 4700 92p; 16V: 40, 47, 100 9p; 125 12p; 220 13p; 470 20p; 680 34p; 1000 27p; 1500 31p; 2200 36p; 3300 74p; 4700 79p.

TRANSISTORS
AC125 35 BC516 40 BU208 200 ZTX107 11
AC126 35 BC517 40 E42 250 ZTX109 12
AC127 25 BC547 14 MJ400 150 ZTX131 11
AC128 25 BC548 14 MJ491 175 ZTX302 16
AC141 30 BC554 14 MJ2955 90 ZTX303 25
AC142 30 BC557 15 MJ340 54 ZTX304 17
AC176 28 BC558 15 MJ370 100 ZTX314 25
AC177 70 BC561 15 MJ371 100 ZTX316 30
AC178 70 BC562 15 MJ372 100 ZTX317 30
AC179 70 BC563 15 MJ373 100 ZTX318 30
AC518 70 BC902 15 MJ712 100 ZTX657 30

OSMABET LTD We make transformers amongst other things.
TRANSFORMERS TO ORDER
 We have capacity for the supply of transformers to specification, either one off, or production runs, your enquiries please.

LOW VOLTAGE TRANSFORMERS: Prim 240V ac.
 6.3V 1.5A £3.00; 3A £4.15; 6A CT £7.90; 12V 1.5A £3.75; 3A CT £7.90; 6A CT £9.75; 15V 0.5A £3.00; 18V 1.5A CT £7.90; 24V 1.5A CT £7.90; 3A CT £9.75; 6A CT £18.00; 8A CT £29.25; 12A CT £37.50.

MIDGEE RECTIFIER TRANSFORMERS: Prim 240V ac.
 6-0-6V 1.5A or 9-0-9V 1A £3.40 each; 12-0-12V 1A or 20-0-20V 0.75A £4.15 each; 9-0-9V 0.3A or 12V-0-12V 0.25A or 20V-0-20V 0.15A £3.00 each.

LT TRANSFORMERS TAPPED SEC: Prim 240V ac.
 0-10-12-14-16-18V 2A £7.50; 4A £9.40; 0-10-15-20-24-30V 2A £8.25; 4A £12.00; 0-20-30-60V 1A £9.00; 2A £12.00; 0-40-50-60-80-100-110V 1A £12.00.

AUTO & ISOLATION TRANSFORMERS 240/110V ac.
 30 to 4000 watts, many types ex stock, lists.

MAINS TRANSFORMERS. SPECIAL OFFER. Prim 240V ac.
 300-0-300V 80Ma; 6.3V 1A CT; 6.3V 1A £5.50; 250-0-250V 60Ma; 6.3V 1A £3.00; 9V 3A £2.50; 25V 300Ma 90p; 15-0-15V 0.5A £2.50; 12V 4A £4.00.

LOUDSPEAKERS
 1" 1", 2", 2 1/2", 3", 3 1/2", 8Q £1.50 each; 3" 35Q 3P; 3" 16; 8Q £1.75 each; Goodman mid range 5" Hi Fi speaker 8Q for 25W systems £5.50; Do Tweeter 3 1/2" C/M 8Q for 25W systems £2.50; F/Range Hi Fi speakers 4" 10W, 8Q £3.50; 5" do 25W 8Q £5.00.

"INSTANT" BULK CASSETTE/TAPE ERASER
 Instant erasure of cassettes, and any diameter of tape spools, demagnetises tape heads, 200/240V ac, leaflet £8.00. Cassette/Tape Head Demagnetiser, £3.50.

"BIB" Video Tape Eraser £20.

EDGWISE LEVEL METER FSD 200/µA
 Size 19 x 18 x 20mm 8000 £1.50.

CHARGING METERS 1 1/2 in diameter
 2A or 3A £1.25 each; 5A or 10A £1.50 each.

MINI FLEX CABLE
 4 core, for Intercom, telephone, burglar alarm extensions, etc. white pvc, 10 metres £2, 100 metres £15.

POWER SUPPLY, TWIN OUTPUT Prim 240V ac:
 New, British manufacturer, smoothed d.c. output 20V, 1.5A, plus STABILISED output of 15V 100Ma, plus further 12V ac 0.5A, complete with diagram, £4.50.

O.P. TRANSFORMERS FOR VALVE AMPLIFIERS
 P.P. sec tapped 3-8-15V A-A 6KΩ, 30W £17.50; A-A 3KΩ 50W £26.00; 100W (EL31, KT88 etc) £35.00.

G.E.C. MANUAL OF POWER AMPLIFIERS
 Covers valve amplifiers 30W to 400W £1.25.

MULTIWAY SCREENED CABLE, PVC COVERED
 36 way £1, 25/75p; 14/50p; 6/25p; 4/20p.

CONDENSERS AC 50Hz, 4.33/250p; 6/330V, £1.50.
 Electrolytic 400 µF 400V 75p; 2000/30V 30p; 2200/40V 40p; Paper tubular, W/E, 4/160V; 6/160V 30p each.

CARRIAGE EXTRA ON ALL ORDERS.
ALL PRICES INCLUDE V.A.T.

Callers by appointment only. S.A.E. Enquiries, Lists.
46, Kenilworth Road, Edgware, Middx. HA8 8YG. Tel: 01-958 9314

H.A.C. SHORT-WAVE KITS
WORLD-WIDE RECEPTION

"H.A.C." well known by amateur constructors for its Short Wave receivers, now offers a complete range of kits and accessories which have been up-dated to suit the novice and the expert.

£14-50 INCLUSIVE - the ever popular and easy to construct DX receiver Mark III; containing all genuine short wave components, drilled chassis, valve, accessories and full instructions.

AT LAST - a battery eliminator kit, which will last you a lifetime - for use in all H.A.C. valve receivers. H.T. batteries are now unobtainable, this will solve your problems for only £9-60.

TWIN TRANSISTOR RECEIVER, selective, sensitive and with fantastic reception, yet needing only a single PP3 battery, at £17-50 this receiver is outstanding value, and will give you hours of interest and entertainment.

NEW - TRIPLE-T RECEIVER, a more advanced super three transistor receiver, loud, clear reception, value unequalled at bargain price of £24-00.

All orders despatched within 7 days. Send stamped and addressed envelope now for free descriptive catalogue of kits and accessories.

SORRY, NO CATALOGUES WITHOUT S.A.E.

"H.A.C." SHORT-WAVE PRODUCTS
P.O. Box No. 16, 10 Windmill Lane Lewes Road, East Grinstead, West Sussex RH19 3SZ

BAKER SPEAKERS Post £2 ea.

"STAR SOUND"

GROUP 45-12 £15
 12in. 45 watt
 4, 8 or 16 ohms.

GROUP 75-12 £22
 12in. 75W professional model, 4, 8 or 16 ohms
 Response 30 - 16,000.

DISCO 100/12 £26
 12 in 100W model
 8 or 16 ohm

DISCO 100-15 £29
 15in. 100 watt
 8 or 16 ohms.

AUDITORIUM 15 £35
 Bass woofer 15in. Special cone surround
 Heavy duty cone. 60 watts. 20 to 8000 cps.

E.M.I. 1 1/2" x 8in SPEAKER SALE!

With tweeter. And crossover. £9-95
 10W. State 3 or 8 ohm.

15W model Post £1
 £10-95

8 ohms Post £1
GOODMANS 20 Watt Woofer
 Size 8in. 4 ohms. £6-00
 Rubber cone surround. Post £1.

GOODMANS TWIN AXIOM 8 Post £1
 8 in. 15 ohm Hi-Fi Twin Cone
 Special unit 15 watts £8-00

EMI MINI MODULE KIT 3-way
 Loudspeaker System, EMI 5in Bass, 5in Middle, 3in Tweeter, with 3-way Crossover and Ready Cut Baffle. 15 x 8 1/2 in.
 Full assembly instructions.
 Response = 60 to 20,000 cps
 12 watt RMS. 8 ohm. £10 ea.
 £18-50 pair. Postage £1-50.

R.C.S. LOUDSPEAKER BARGAINS

3 ohm: 6 - 4in. £1-50, 7 - 4in. £1-50, 8 - 5in. £3-00, 6 1/2 in. £3-00, 8in. £3-50, 10in. £4-00, 12in. £4-50.
 8 ohm: 2 1/2 in. £1-50, 3in. £1-50, 5in. £1-50, 8in. £3-50, 12in. £4-50
 16 ohm: 6 - 4in. £1-50, 5in. £1-50, 8in. £3-50, 12in. £4-50.
 10 - 6in. £3-50, 25 ohm 3 1/2 in. 35 ohm 3in. £1-50.

LOW VOLTAGE ELECTROLYTICS

1, 2, 4, 5, 8, 16, 25, 30, 50, 100, 200µF 15V 10p.
 500µF 12V 15p; 25V 20p; 50V 30p;
 1000µF 12V 20p; 25V 35p; 50V 50p; 1200µF 75V 80p.
 2200µF 6V 25p; 25V 42p; 40V 60p; 200µF 100V £1-20.
 2500µF 50V 70p; 3000µF 25V 50p; 50V 65p.
 3300µF 63V £1-20; 4700µF 63V £1-20; 2700µF 76V £1.
 5000µF 35V 85p; 50V 95p; 5600µF 76V £1-75.

HIGH VOLTAGE ELECTROLYTICS

8/350V 35p 8-8/450V 75p 50-50/300V 50p
 16/350V 45p 8-16/450V 75p 32-32/325V 75p
 32/350V 75p 20-20/450V 75p 100-100/275V 65p
 50/350V 80p 32-32/350V 50p 150-200/275V 70p
 50/500V £1-20 32-32/500V £1-80 220/450V 95p

MANY OTHER ELECTROLYTICS IN STOCK

TRIMMERS 100pF, 30pF, 50pF, 5p, 100pF, 150pF, 15p.
CONDENSERS VARIOUS, 1pF to 0.01µF, 3p.
PAPER 350V-0.1 7p; 0-5 13p; 1mF 150V 20p; 2mF 150V 20p
 400V-0.001 to 0.05 5p; 0-1 15p; 0-25 25p; 0-47 35p.
MICRO SWITCH SINGLE POLE CHANGE OVER 20p.
SUB-MIN MICRO SWITCH, 25p. Single pole change over.
TWIN GANGS 120pF 50p; 500pF £1.
GEARED TWIN GANGS 25pF 95p; 365pF £1;
 365 - 365 - 25 - 25pF £1.
NEON PANEL INDICATORS 250V. Red 1 1/2" x 1/2" 45p.
ILLUMINATED ROCKER SWITCH. Single pole. Red 65p.
RESISTORS. 10Ω to 10M. 1/2W, 1/4W, 1W, 20% 2p; 2W, 10p.
HIGH STABILITY. 1/2W 2% 10 ohms to 1 meg. 8p.
 Ditto 5%. Preferred values 10 ohms to 10 meg. 3p.
ALUMINIUM CHASSIS 18 s.w.g. Undrilled, 4 sides, riveted corners, 6 - 2 1/2 in. - £1-20; 8 - 6 2 1/2 in. - £1-50; 10 - 7 - 2 1/2 in. - £1-90; 14 - 9 - 2 1/2 in. - £2-50; 16 - 7 - 2 1/2 in. - £2-40; 12 - 3 - 2 1/2 in. - £1-50; 12 - 8 - 2 1/2 in. - £2-20; 18 - 10 - 2 1/2 in. - £2-70. **ANGLE BRACKET** 6 - 1/2 in. - 25p.
ALUMINIUM PANELS 18 s.w.g. 12 - 12 in. - £1-30; 14 - 9 in. - £1-20; 6 - 4 in. - 36p; 12 - 8 in. - 90p; 10 - 7 in. - 80p; 8 - 6 in. - 60p; 14 - 3 in. - 60p; 12 - 5 in. - 60p; 16 - 10 in. - £1-40; 16 - 6 in. - 90p.
BLACK PLASTIC construction box with brushed aluminium fascia size 6 1/2 x 4 1/2 - 2" £1-50. Many other sizes.
BRIDGE RECTIFIER 200V PIV 1/2 amp 50p. 2 amp £1-00.
4 amp £1-50, 8 amp £2-50.
TOGGLE SWITCHES SP 30p. DPST 40p. DPDT 50p.
MANY OTHER TOGGLES IN STOCK. Please enquire.
BSR 172 BUDGET SINGLE PLAYER ideal for disco or small three-speed Hi-Fi system with stereo cartridge cueing device and bias compensator. £20 Post £2
BSR STEREO CARTRIDGES SC7 medium SC8 High output £2. Sonotone 9TA-HC £2-50. V.100 Magnetic £7.
WIRE-WOUND RESISTORS 5 watt, 10 watt, 15 watt 15p.
CASSETTE MOTOR. 6 volt £1-00.

MAINS TRANSFORMERS Post 99p

6V 500mA £2-00 6-0-6V 100mA £1-80
 12V 100mA £1-30 9-0-9V 50mA £1-50
 12V 750A £1-75 12V 3A £3-50; 5A £4-00
 16V-0-16V 2amp £3-00 10V, 30V, 40V, 2 amp £3-50
 30V, 5 amp and
 17V-0-17V, 2 amp £4-00 20V, 1 amp £3-00
 0, 5, 8, 10, 16V, 1/2 amp £2-50 20V-0-20V, 1 amp £3-50
 9V, 3 amp £3-50 2 of 18V, 6 amp, each £11-00
 15-0-15V 2 amp £3-00 12-0-12V, 2 amp £3-50
 35V, 2 amp £3-50 9V, 1 amp £1-50
 30V, 1 1/2 amp £3-36 28V, 1 amp + 28V 1 amp £5-00
 20V, 40V, 60V, 1 amp £4-00 32-0-32V 6-5A £11-00


Radio Component Specialists
 337, WHITEHORSE ROAD
 CROYDON, SURREY, U.K. TEL: 01-684 1665
 Post 50p Minimum. Callers Welcome.
 Access-Barclay-Visa. Lists 20p. Closed Wed.

INDEX TO ADVERTISERS

A. H. Supplies	92	M.R.S. Communications	30
A. J. H. Electronics	96	Manor Supplies	97
Amateur Electronics	36	Maplin Electronic Supplies	Cover IV
Amateur Radio Exchange	29	Marco Trading	84
Amateur Radio Shop	69	Marshall A. (London) Ltd.	96
Ambit International	13	Mhel Electronics	100
Amcom Services	60	Microwave Modules	81
Arrow Electronics	85	Mitrad	11
		Modular Electronics	101
Barrie Electronics	101	Monolith Electronics	95
Bi-Pak	4, 5, 6, 7, 8, 9		
Birkett J.	97	Northern Communications	85
Bowes Electronics C.	10	Northern Radio Society	60
Bredhurst Electronics	Cover II		
British Institute of Electrical Technology	95	Orion Scientific Products	96
British National Radio & Electronics School	89	Osmabet	103
Brookes B.	66		
Bull J.	15	P.C. Electronics	98
Burneze	100	P.M. Components	14
		Partridge Electronics	76
Cambridge Kits	100	Pearl Acoustics	66
Caranna C.	99	Progressive Radio	96
Catronics Ltd.	36		
Colomar (Electronics) Ltd.	92	RST Valve Mail Order	10
Cox Radio	98	Radio Component Specialists	103
C.R. Supply Co.	98	Radio Shack	75
		Radio Society of Great Britain	30
Datong Electronics	76	Riscomp (Autonal)	86
		R & TV Components	13
Electronic Design Associates	95	Science of Cambridge	90, 91
Electrovalve Ltd.	93	Scientific Wire Company	100
Electro-Tech	93	Solid State Security	14
Electronic Mail Order	12	Solon Electronics	98
Environmental Systems	21	Southern Valve	98
		South Midlands Communications Ltd	47
Garex	89	Stephens-James Ltd.	66
Gemini Electrical Components	94	Sunmit Electronics	94
Gemini Communications	66	Swanley Electronics	12
Golledge Electronics PR	98		
GT Technical Information Service	99	Taurus Electronics	76
G2 Dym Aerials	99	Technomatic Ltd.	97
		Tempus	93
H.M. Electronics	100	Thanet Electronics	104, Cover III
H.A.C. Shortwave	103		
Heath Electronics	10	V & F Smallcraft	97
Homeburr Radio	85	Van Karen Publishing	98
Home Radio (Components) Ltd.	14	Vintage Modern & Communications Club	98
I.C.S. Intertex	14, 100	Waters & Stanton	65
I.L.P. Electronics Ltd.	16, 17, 92	Watford Electronics	102
Industrial Supplies	100	Western Electronics	60
Intel.	94	Williamson Amplification	100
		Wimslow Audio	12
Lee Electronics	35	Winston Promotions	100
Leeds Amateur Radio	18	Wood & Douglas	86
Lexton Harvey	57	Wye Valley Electronics	30
London Electronics College	100		
Low Electronics	2, 3	Z.L. Communications	36

It's Small- but very Sensitive

IC-2E Handy Talky £159_{INCL.}

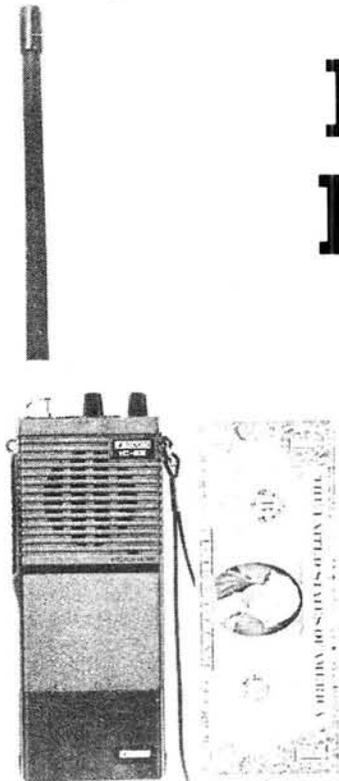

CHECK THE FEATURES

FULLY SYNTHESIZED — covering 144-145.995 in 400 5kHz steps.
POWER OUTPUT — 1.5W with the 9V rechargeable battery pack as supplied — but lower or higher output available with the optional 6V or 12V packs.
BNC ANTENNA OUTPUT SOCKET — 50 ohms for connecting to another antenna or use the Rubber Duck supplied.


SEND/BATTERY INDICATOR — Lights during transmit, but when battery power falls below 6V it doesn't light indicating the need for a recharge.
FREQUENCY SELECTION — by thumbwheel switches, indicating the frequency.

+5kHz SWITCH — adds 5kHz to the indicated frequency.
DUPLEX SIMPLEX SWITCH — gives simplex or plus 600kHz or minus 600 kHz Transmit.
HI-LOW SWITCH — reduces power output from 1.5W to 150mW reducing battery drain.
EXTERNAL MICROPHONE JACK — If you do not wish to use the built-in electret condenser mic an optional microphone/speaker with PTT control can be used. Useful for pocket operation.
EXTERNAL SPEAKER JACK — for speaker or earphone.
 This little beauty is supplied ready to go complete with nicad battery pack, charger, rubber duck.

IC2E OPTIONS

BATTERY PACKS			CHARGERS ETC	
ICBP3	9 VOLT PACK (AS FITTED) REPLACEMENT	£15.50	IC-DC1	9 VOLT REGULATOR PACK £7.50
ICBP2	(7.2 VOLT) (1 WATT)	£22.00	IC-CP1	CAR CHARGER LEAD WITH CIGAR PLUG £2.75
ICBP4	EMPTY CASE (WILL TAKE SIX 'AA' SIZE NI-CADS)	£5.00	IC-BC25	CHARGER FOR BP3 AS SUPPLIED £3.70
ICBP5	11 VOLT PACK (2-3 WATTS)	£30.50	IC-BC30	DESK CHARGER FOR ALL NI-CAD PACKS FAST FOR IC-BP5 + BP2 (1½ hours) £34.00

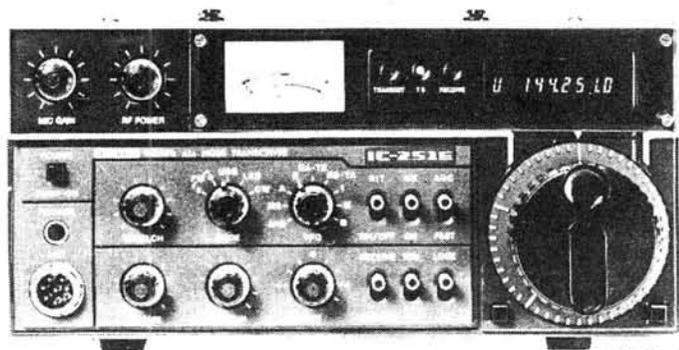It will seduce you in it's own way the ICOM IC 251E



only
£479_{INCL.}

SEND FOR TECHNICAL DETAILS

Thanet for



ICOM

143 RECVLVER RD.,
BELTINGE,
HERNE BAY, KENT.
Tel: 02273/63859



Published on approximately the 7th of each month by IPC Magazines Limited, Westover House, West Quay Road, POOLE, Dorset BH15 1JG. Printed in England by Chapel River Press, Andover, Hants. Sole Agents for Australia and New Zealand—Gordon and Gotch (Asia) Ltd. South Africa—Central News Agency Ltd. Subscriptions INLAND and OVERSEAS £11.80 payable to IPC Services, Oakfield House, Perrymount Road, Haywards Heath, Sussex. PRACTICAL WIRELESS is sold subject to the following conditions, namely that it shall not, without the written consent of the Publishers first having been given, be lent, resold, hired out or otherwise disposed of by way of Trade at more than the recommended selling price shown on the cover, excluding Eire where the selling price is subject to V.A.T. and that it shall not be lent, resold, hired out or otherwise disposed of in a mutilated condition or in any unauthorised cover by way of Trade or affixed to or as part of any publication or advertising, literary or pictorial matter whatsoever.

**for only
£255
INCL.**

IC-255E

An experts mobile choice

**NOW WITH
IMPROVED
FRONT-END**



**25 Watts – 5 Memories – Scanning – 600kHz
AND User Selectable Repeater Shift – Full Coverage in 5kHz or 25kHz Steps.**

- Crystal controlled Tone Burst
- Full band coverage – extendable to 148MHz if required
- Four digit LED display
- 25 Watts output or 1W low power
- A superb receiver using grounded gate FET front end
- Scanning over a user programmable range
- Memory scan
- Stop on empty or busy channels
- Tuning in 25kHz or 5kHz steps
- 5 Memories – retained while the power is connected to the rig
- Built-in 600kHz Repeater Shift
- Alternative programmable shift
- Reverse Repeater facilities
- RIT (± 3kHz for those off channel stations)
- Scan control from the microphone (optional mic available)
- Good loud audio
- Optically coupled tuning between control knob and CPU
- Multiway 24 pin socket on back for touchpad, computer, or external control
- Rugged modular PA (Guaranteed of course!)
- Mobile mount which can be padlocked
- Up-down scanning microphone available

CAN YOU RESIST SUCH A TEMPTATION

Enjoy VHF mobile at it's best-IC-260E

The IC-260E offers such extras as full frequency read out, upper and lower sideband, and scanning as well as FM and CW. Thus, it makes an ideal base station, when used with a DC power supply, as well as a mobile. Now supplied with up-down scanning mic.



£339 INCL.

SEND FOR TECHNICAL DETAILS

AGENTS (PHONE FIRST – All evenings and weekends only, except Burnley)
 Scotland Jack GM8GEC (031-665-2420) Midlands Tony G8AVH (021-329 2305)
 Wales Tony GW3FKO (0874 2772) North West Gordon G3LEQ (Knutsford (0565) 4040)
 Burnley (0282 38481)



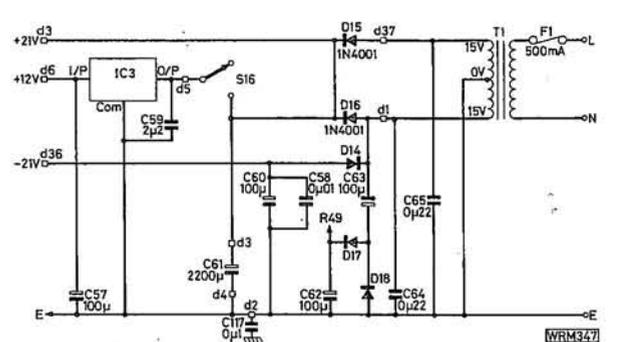
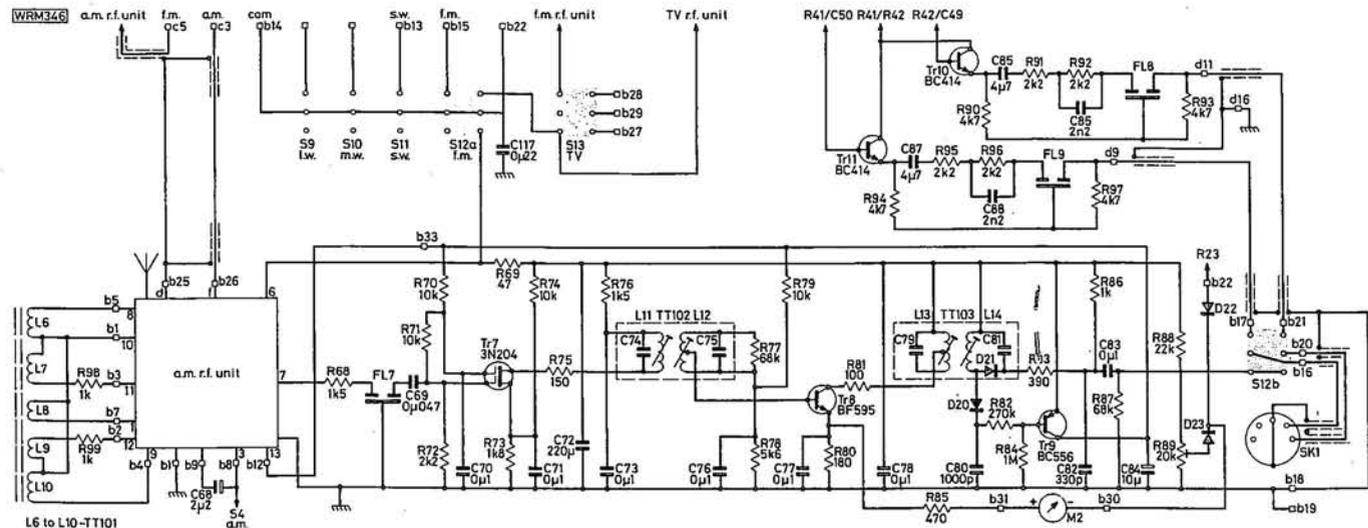
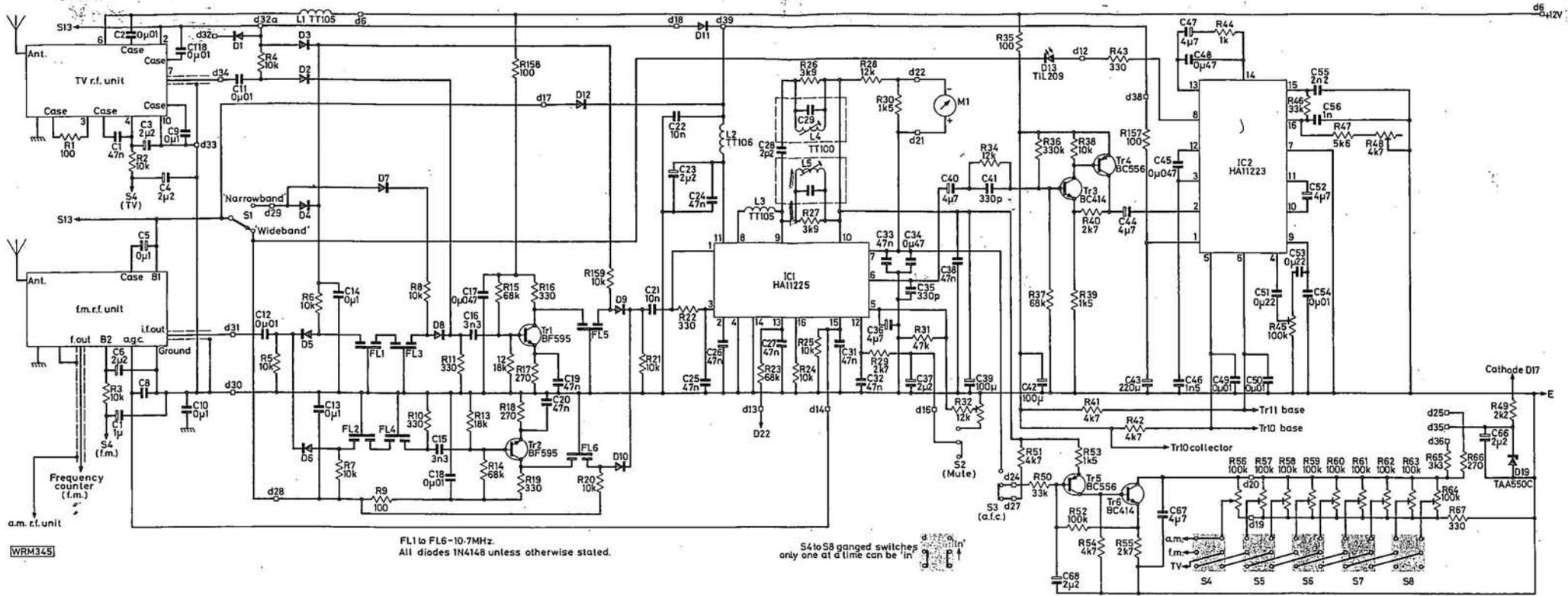


Fig. 1 (top): Circuit diagram of f.m. and TV sections of the PW Winton Tuner
 Fig. 2 (left): Circuit diagram of a.m. section
 Fig. 3 (above): Circuit diagram for PW Winton power supply