

FOR THE RADIO ENTHUSIAST ...

FEBRUARY 1982

Practical Wireless

Australia \$1.28
New Zealand \$1.30
Malaysia \$4.50
IR £1.07 (inc. VAT)

75p


MODULATED WAVEFORM GENERATOR

SPECIAL OFFER

TIMESTEP

DFC4
Digital Frequency Counter Kit

as used here!

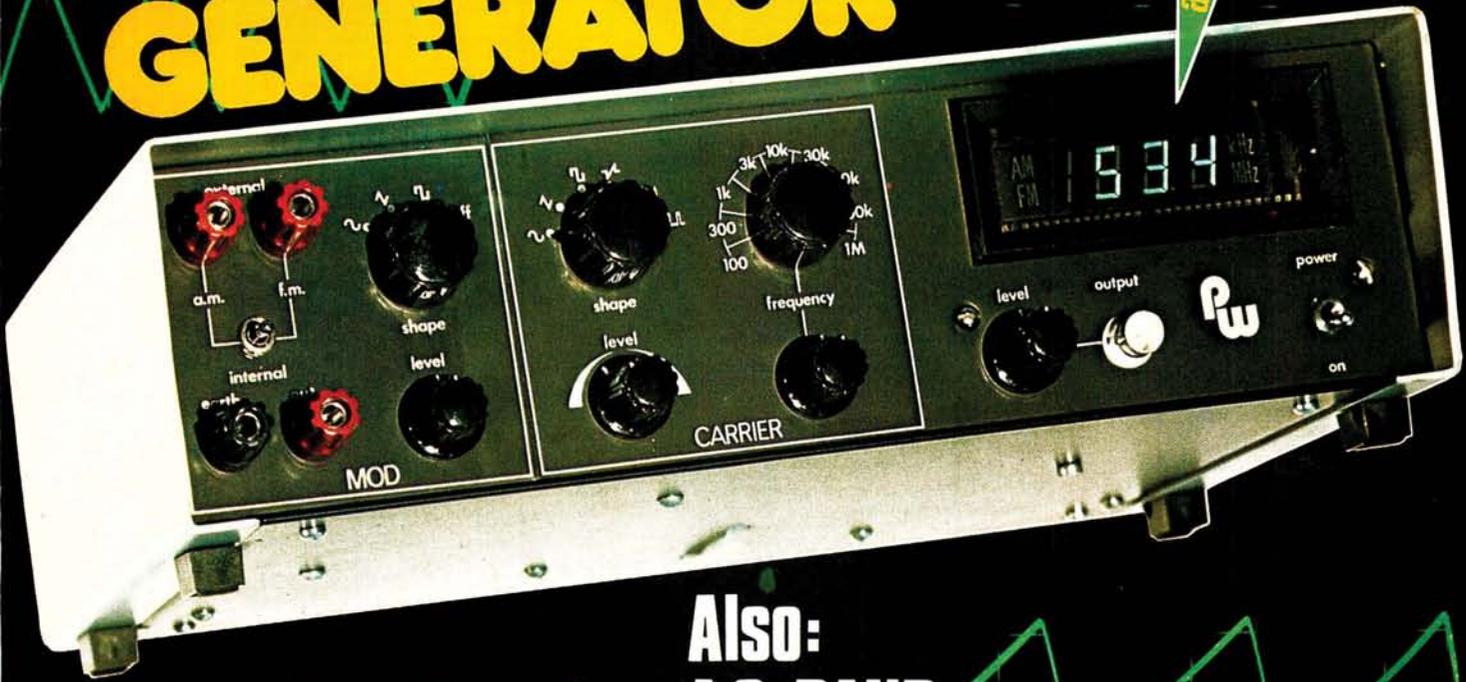

Also:
A 3-BAND
SHORT-WAVE
CONVERTER

MAIL ORDER

THE EASY WAY - THE BREDHURST WAY
TO ORDER ANY OF THE ITEMS LISTED BELOW
SIMPLY WRITE ENCLOSING A CHEQUE OR PHONE
AND QUOTE YOUR CREDIT CARD NO.
- WE DO THE REST!

Bredhurst electronics

TS 7730



£247 inc. VAT

TRIO		£	Carr.
TS830S	160-10m Transceiver 9 Bands	694.00	(—)
VFO230	Digital V.F.O. with Memories	215.00	(2.00)
AT230	All Band ATU/Power Meter	119.00	(2.00)
SP230	External Speaker Unit	34.96	(1.50)
DFC230	Dig. Frequency Remote Controller	179.00	(1.50)
YK88C	500Hz CW Filter	29.60	(0.50)
YK88CN	270Hz CW Filter	32.66	(0.50)
TS130S	8 Band 20W Pwp Transceiver	525.00	(—)
TS130V	8 Band 20W Pwp Transceiver	445.00	(—)
VFO120	External V.F.O.	85.00	(1.50)
TL120	200W Pwp Linear for TS120V	144.00	(1.50)
MB100	Mobile Mount for TS130/120	17.00	(1.50)
SP120	Base Station External Speaker	23.00	(1.50)
AT130	100W Antenna Tuner	79.00	(1.50)
PS20	AC Power Supply - TS130V	49.45	(2.50)
PS30	AC Power Supply - TS130S	88.50	(5.00)
MA5	5 Band Mobile Aerial System	86.00	(5.00)
MC50	Dual Impedance Desk Microphone	25.76	(1.50)
MC35S	Fist Microphone 50K ohm IMP	13.80	(0.75)
MC30S	Fist Microphone 500 ohm IMP	13.80	(0.75)
LF30A	HF Low Pass Filter 1KW	17.90	(1.50)
TR9000	2M Synthesised Multimode	371.00	(—)
B09	Base Plinth for TR9000	34.90	(1.50)
TR7800	2M Synthesised FM Mobile 25W	284.00	(—)
TR7730	2M Synthesised FM Compact Mobile 25W	247.00	(—)
TR2300	2M Synthesised FM Portable	166.00	(—)
VB2300	10W Amplifier for TR2300	58.00	(1.50)
MB2	Mobile Mount for TR2300	17.71	(1.50)
RA1	Flexible Rubber Antenna for TR2300	6.90	(0.50)
TR2400	2M FM Synthesised Handheld	198.00	(—)
SMC24	External Speaker/Microphone for 2400	13.80	(1.50)
ST1	Base Stand and Quick Charger	45.00	(1.50)
BC5	12V Quick Charger	18.40	(1.00)
SC3	Soft Carrying Case Plus Belt Hook	11.50	(0.50)
PB24	Spare Battery Pack and Charger Lead	15.87	(0.75)
TR8400	70cm FM Synthesised Mobile Transceiver	334.00	(—)
PS10	Base Station Power Supply for 8400	64.00	(2.00)
TR9500	70cm Synthesised Multimode	449.00	(—)
R1000	Synthesised 200KHz-30MHz Receiver	297.00	(—)
SP100	External Speaker Unit	26.90	(1.50)
HC10	Digital Station World Time Clock	58.80	(1.50)
HS5	Deluxe Headphones	21.85	(0.75)
HS4	Economy Headphones	10.35	(0.75)
SP40	Mobile External Speaker	12.40	(1.50)

ICOM		£	Carr.
IC730	HF Mobile Transceiver 8 Band	586.00	(—)
IC720A	HF Transceiver & Gen. Cov. Receiver	883.00	(—)
PS15	Power Supply for 720A	99.00	(3.00)
IC251E	2M Multimode Base Station	499.00	(—)
IC25E	2M Synthesised Compact 25W Mobile	259.00	(—)
IC29E	2M Multimode Mobile	366.00	(—)
IC2E	2M FM Synthesised Handheld	169.00	(—)
IC L1/2/3	Soft Cases	3.50	(0.50)
IC HM9	Speaker/Microphone	12.00	(0.75)
IC BC30	230V AC Base Charger and Hod	39.00	(1.50)
IC BC25	230V AC Trickle Charger	4.25	(0.75)
IC CP1	Car Charging Lead	3.20	(0.50)
IC BP2	6V Nicad Pack for IC2E	22.00	(1.00)
IC BP3	9V Nicad Pack for IC2E	17.70	(1.00)
IC BP4	Empty Case for 6x AA Nicads	5.80	(0.75)
IC BP5	11.5V Nicad Pack for IC2E	30.50	(1.00)
IC DC1	12V Adaptor Pack for IC2E	8.40	(0.75)
IC ML1	10W Booster	49.00	(1.00)

TV INTERFERENCE AIDS		£	Carr.
Ferrite Rings 1" dia. per pair		0.80	(0.20)
Toroid Filter TV Down Lead		2.00	(0.50)
Low Pass Filter LP30 100W		3.95	(0.50)
Trio Low Pass Filter LF30A 1kW		17.90	(0.75)
Yaesu Low Pass Filter FF501DX 1kW		23.00	(0.75)
HP4A High Pass Filter TV Down Lead		5.95	(—)

ANTENNA BITS		£	Carr.
H1-Q Balun 1:1 5kW pep (PL259 Fitting)		9.95	(0.75)
Piece Polyprop Dipole Centre		1.00	(0.20)
Ceramic Strain Insulators		0.40	(0.10)
Small Egg Insulators		0.40	(0.10)
Large Egg Insulators		0.50	(0.10)
75 ohm Twin Feeder - Light Duty-Per Meter		0.16	(0.02)
300 ohm Twin Feeder - Per Meter		0.14	(0.02)
URM67 Low Loss 50 ohm Coax-Per Meter		0.60	(0.20)
UR76 50 ohm Coax-Per Meter		0.25	(0.05)

MICROWAVE MODULES		£	Carr.
MMT144/28	2M Transverter for HF Rig	99.00	(—)
MMT432/28S	70cm Transverter for HF Rig	149.00	(—)
MMT432/144R	70cm Transverter for 2M Rig	184.00	(—)
MMT70/28	4M Transverter for HF Rig	115.00	(—)
MMT70/144	4M Transverter for 2M Rig	115.00	(—)
MMT1296/144	23cm Transverter for 2M Rig	184.00	(—)
MML144/25	2M 25W Linear Amp (3W I/P)	59.00	(—)
MML144/40	2M 40W Linear Amp (10W I/P)	77.00	(—)
MML144/100S	2M 100W Linear Amp (10W I/P)	129.00	(—)
MML432/20	70cm 20W Linear Amp (3W I/P)	77.00	(—)
MML432/50	70cm/50W Linear Amp	119.00	(—)
MML432/100	70cm 10/100W Linear Amp	228.64	(—)
MM2000	RTTY to TV Converter	169.00	(—)
MM4000	RTTY Transceiver	269.00	(—)
MMC50/28	6M Converter to HF Rig	27.90	(—)
MMC70/28	4M Converter to HF Rig	27.90	(—)
MMC144/28	2M Converter to HF Rig	27.90	(—)
MMC432/28S	70cm Converter to HF Rig	34.90	(—)
MMC432/144S	70cm Converter to 2M Rig	34.90	(—)
MMC435/600	70cm ATV Converter	27.90	(—)
MMK1296/144	23cm Converter to 2M Rig	59.80	(—)
MMD050/500	600MHz Dig. Frequency Meter	69.00	(—)
MMD600P	500MHz Prescaler	23.00	(—)
MMDP1	Frequency Counter Probe	11.50	(—)
MMA28	10M Preamp	14.95	(—)
MMA144V	2M RF Switched Preamp	34.90	(—)
MMF144	2M Band Pass Filter	9.90	(—)
MMF432	70cm Band Pass Filter	9.90	(—)
MMS1	The Morse Talker	115.00	(—)

DATONG PRODUCTS		£	Carr.
PC1	Gen. Coverage Converter HF on 2M Rig	120.75	(—)
VLF	Very Low Frequency Converter	25.30	(—)
FL1	Frequency Agile Audio Filter	67.85	(—)
FL2	Multi-mode Audio Filter	89.70	(—)
ASP/B	Auto RF Speech Clipper (Trio Plug)	79.35	(—)
ASP/A	Auto RF Speech Clippers (Yaesu Plug)	79.35	(—)
R75	Manually controlled RF Speech Clipper	56.35	(—)
RFC/M	RF Speech Clipper Module	26.45	(—)
D70	Morse Tutor	48.45	(—)
AD270	Indoor Active Dipole Antenna	37.95	(—)
AD370	Outdoor Active Dipole Antenna	51.75	(—)
MPU1	Mains Power Unit	6.90	(—)



MORSE EQUIPMENT		£	Carr.
MK704	Squeeze Paddle	10.50	(0.50)
HK707	Up/Down Key	10.50	(0.50)
DK704	Deluxe Up/Down Key	14.90	(0.50)
EK121	Practise Oscillator	8.75	(0.50)
EK121	Elbug	29.95	(0.50)
EKM1A	Matching Side Tone Monitor	10.95	(0.50)
EK150	Electronic Keyer	74.00	(—)

ROTATORS		£	Carr.
KR250	Kenpro Lightweight 1-1/2" mast	44.95	(2.00)
Hirschman	RO250 VHF Rotor	49.95	(2.00)
9502B	Colorator (Med. VHF)	49.95	(2.00)
KR400RC	Kenpro - inc lower clamps	99.95	(2.50)
KR600RC	Kenpro - inc lower clamps	139.95	(3.00)

DESK MICROPHONES		£	Carr.
SHURE 44-D	Dual Impedance	29.95	(1.50)
SHURE 52B7	Mix II Power Microphone	39.95	(1.50)
ADONIS AM502	Compression Mic 1 O/P	39.00	(—)
ADONIS AM601	Compression Mic + Meter 1 O/P	49.00	(—)
ADONIS AM 802	Compression Mic + Meter 3 O/P	59.00	(—)

MOBILE SAFETY MICROPHONES		£	Carr.
ADONIS AM 202S	Clip-on	20.95	(—)
ADONIS AM 202F	Swan Neck + Up/Down Buttons	30.00	(—)
ADONIS AM 202H	Head Band + Up/Down Buttons	30.95	(—)
DAIWA RM940	Infra Red Link	45.00	(0.75)

HAND MICROPHONES		£	Carr.
T.A. 600	Fist Mic.	4.95	(0.50)
Power Mic.	Wide Impedance	9.95	(0.75)
TRIO MC30/35	600/50K IMP	13.90	(0.75)
YAESU Y7A/Y84S	600/50K IMP	5.75	(0.75)
SHURE 201	High IMP. Quality Mic.	14.50	(0.75)

TEST EQUIPMENT		£	Carr.
Drae VHF Wavemeter	130-450MHz	24.95	(—)
FXI Wavemeter	250MHz MAX	28.00	(0.75)
DM81	Trio Dip Meter	51.75	(0.75)
MMD50/500	Dig. Frequency meter (500MHz)	69.00	(0.75)

Co-AXIAL SWITCH		£	Carr.
3 Way Rotary (H.F.)		10.95	(0.50)
2 Way Diacast (V.H.F.)		10.00	(0.50)
2 Way Toggle (V.H.F.)		6.50	(0.50)

HELIAL ANTENNAS		£	Carr.
2M BNC or PL259 (state which required)		4.50	(0.50)
2M Thread for TR2300 or FT290R (state which)		4.50	(0.50)
70cm BNC		4.50	(0.50)

YAESU		£	Carr.
FT902DM	160-10m 9 Band Transceiver	885.00	(—)
FC902	All Band A.T.U.	135.00	(1.50)
SP901	External Speaker	31.00	(1.50)
FT101Z	160-10m 9 Band Transceiver (FM)	590.00	(—)
FT101ZD	160-10m 9 Band Transceiver (FM) Digital R.O.	665.00	(—)
DCT101Z	DC/DC Power Pack	42.55	(1.50)
FAN101Z	Cooling Fan for 101Z/ZD	13.80	(0.75)
FT707	8 Band Transceiver 200W Pwp	569.00	(—)
FT707S	8 Band Transceiver 20W pep	485.00	(—)
FT707	Matching Power Supply	125.00	(5.00)
FT707R(2)	Transverter - 2M	198.00	(—)
FV707DM	Digital V.F.O.	186.00	(—)
FC707	Matching A.T.U./Power Meter	85.00	(1.00)
MR7	Metal Rack for FT707	15.70	(1.00)
MMB2	Mobile Mounting Bracket for FT707	16.10	(1.00)
FRG7	General Coverage Receiver	189.00	(—)
FRG7700	200KHz-30MHz Gen. Coverage Receiver	329.00	(—)
FRG7700M	As above but with Memories	409.00	(—)
FR7700	Antenna Tuning Unit	37.00	(1.00)
FT208R	2M FM Synthesised Handheld	209.00	(—)
FT290R	2M Portable Synthesised Multimode	249.00	(—)
FT708R	70cm FM Synthesised Handheld	219.00	(—)
NC7	Base Trickle Charger	26.88	(1.30)
NC8	Base Fast/Trickle Charger	44.10	(1.50)
NC9C	Compact Trickle Charger	8.00	(0.75)
FB2	Battery Sleeve for use with NC7/8	3.05	(0.50)
FN82	Spare Battery Pack	17.25	(0.75)
PA3	12V DC Adaptor	13.40	(0.75)
FT480R	2M Synthesised Multimode	379.00	(—)
FT780R	70cm Synthesised Multimode (1.6MHz Shift)	459.00	(—)
FP80	Matching 230V AC Power Supply	63.00	(1.50)

★ AS REVIEWED ★

FT290R	2M Portable Synthesised Multimode	£	Carr.
MMB11	Mobile Mounting Bracket	20.70	(1.00)
CSC1	Soft Carrying Case	3.45	(0.75)
NC11C	240V AC Trickle Charger	8.05	(0.75)
FL2010	Matching 10W Linear	64.40	(1.20)
Nicads	2.2 AMP HR Nicads	Each 2.50	(—)
FL2100X	160-10m 1200 Watt Linear	425.00	(5.00)
FF501DX	H.F. Low Pass Filter 1kW	23.00	(0.75)
FSP1	Mobile External Speaker 8 ohm 6W	9.95	(0.75)
YH55	Headphones 8 ohm	10.00	(0.75)
YH77	Lightweight Headphones 8 ohm	10.00	(0.75)
QTR24D	World Clock (Quartz)	28.00	(0.75)
YM24A	Speaker/Mic 207/208/708	16.85	(0.75)
YD148	Stand Microphone Dual IMP		
	4 Pin Plug	21.00	(1.50)
YM34	As 148 but 8 Pin Plug	21.45	(1.50)
YM38	As 34 but up/down Scan Buttons	24.90	(1.50)

FDK VHF/UHF EQUIPMENT		£	Carr.
Multi 700EX	2M FM Synthesised 25W Mobile	199.00	(—)
Multi 750E	2M Multimode Mobile	289.00	(—)
Expander	70cm Transverter for M750E	219.00	(—)

STANDARD VHF/UHF		£	Carr.
C78	70cm FM Portable	219.00	(—)
CPB78	10W Matching Linear	67	

EDITORIAL OFFICES
Practical Wireless
Westover House
West Quay Road
Poole, Dorset BH15 1JG
☎ Poole 71191

Geoff Arnold T.Eng(CEI) G3GSR
Editor

Dick Ganderton C.Eng., MIERE, G8VFH
Assistant Editor

Peter Metalli
Art Editor

John Fell G8MCP
Technical Editor

Alan Martin G8ZPW
News & Production Editor

Elaine Howard G4LFM
Technical Sub-Editor

Rob Mackie
Technical Artist

Keith Woodruff
Assistant Art Editor

Sylvia Barrett
Secretarial

ADVERTISEMENT OFFICES
Practical Wireless
King's Reach Tower
Stamford Street
London SE1 9LS
Telex: 915748 MAGDIV-G

Dennis Brough
Advertisement Manager
☎ 01-261 6636
☎ 01-261 6872

Roger Hall G8TNT (Sam)
Ad. Sales Executive
☎ 01-261 6807

Claire Gerrish
Secretary
☎ 01-261 6636

Barbara Blake
Classified Supervisor
☎ 01-261 5897

Dave Kerindi
Make-up & Copy
☎ 01-261 6570

COPYRIGHT

© IPC Magazines Limited 1982. Copyright in all drawings, photographs and articles published in *Practical Wireless* is fully protected and reproduction or imitation in whole or in part is expressly forbidden. All reasonable precautions are taken by *Practical Wireless* to ensure that the advice and data given to our readers are reliable. We cannot however guarantee it and we cannot accept legal responsibility for it. Prices are those current as we go to press.

Practical Wireless


FEBRUARY 1982 VOL. 58 NO. 2 ISSUE 899

contents

- 22 Valves Used in the Early Days**
G. Jessop G6JP
- 26 Air Test**
Sota SCL 144PS 2m Linear Amplifier
- 29 PW Modulated Waveform Generator**
Geoff Arnold G3GSR
- 39 CB Rig Check**
Commtron CB-40F
- 42 IC of the Month—LM10 Op. Amp/Voltage Reference**
Brian Dance
- 47 PW "Winton" Stereo Tuner—5**
E. A. Rule
- 51 Passport to Amateur Radio—7**
John Thornton-Lawrence GW3JGA
- 58 3-Band Short Wave Converter—1**
R. F. Haigh
- 62 The CB Code of Practice**

OUR SPECIAL OFFER THIS MONTH
Timestep DFC4 Frequency Meter Kit
(see page 45)

- | | | | |
|----|-----------------|----|------------------|
| 95 | Advert Index | 40 | News |
| 26 | Air Test | 41 | Next Month |
| 39 | CB Rig Check | 65 | On the Air |
| 19 | Comment | 20 | Production Lines |
| 42 | IC of the Month | 19 | Services |
| 25 | Mods | 64 | YL Column |

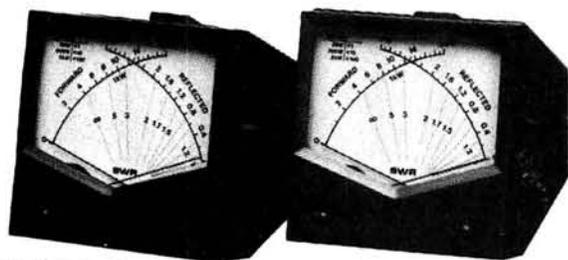

CN540

50MHz · 150MHz
£35.00 inc VAT
carr £1.50

CN520

1.8MHz · 60MHz
£32.50 inc VAT carr £1.50



The UL1000 is a new concept in receiving station accessories and will help any keen listener to improve the performance of his station, particularly in the difficult conditions existing in the medium wave band (500KHz-1.6MHz).

The UL1000 is a self-contained variable gain, tuned preamplifier suitable for use with various aerial systems. A particular feature of the UL1000 is the use of a high Q loop aerial for the 500KHz-1.6MHz band.

UL1000

£39.50 inc VAT Carriage £1.50



HONOR

Carriage on meters £1.00
KRT100 £5.75 KRT200 £10.50 KRT500 £19.50



For those of you who enthuse over portable SSB operation on the hills and mountains of the UK, or wish to chat to the local lads whilst seated by your fireside, then the Mizuho SB2X 2 metre SSB portable is the rig for you. One watt output on the SSB frequencies 144.000 to 144.600 and the ability to listen to the beacon frequencies from 144.800 to 145.000 (also transmit).

£165.00 inc VAT Carr £4.50

MIZUHO SB2X

UHF VHF



TR9000 The exciting TR9000 2-metre all-mode transceiver combining the convenience of FM with long distance SSB and CW in a very compact, very affordable package. Because of its compactness the TR9000 is ideal for mobile installation, add on its fixed station accessories and it becomes the obvious choice for your shack.

TR 9000

£394.00 inc VAT. Securicor carr £4.50



The TR9500, a 70cm multimode mobile giving SSB, FM and CW operation in a compact rig based on the phenomenally successful 2 metre 9000. Combining the convenience of FM with the "DX ability" of SSB on the 70cm band this is the rig all discerning VHF and UHF amateurs have been waiting for.

TR 9500

£449.88 inc VAT. Securicor carr £4.50



TR7800 Trio's remarkable TR7800 2-metre FM mobile transceiver provides all the features you could desire for maximum operating enjoyment. Frequency selection is easier than ever, and the rig incorporates new memory development for repeater shift, priority, and scan. The TR7800 by Trio, the only FM mobile.

TR 7800

£284.97 inc VAT. Securicor carr £4.50

HEAD OFFICE AND SERVICE CENTRE

Chesterfield Road, Matlock, Derbys. Tel. 0629 2817 or 2430.

Open Tuesday-Friday 9-5.30, Saturday 9-5.00. Closed for lunch 12.30-1.30.

For all that's best in ham radio, contact us at Matlock.

For full catalogues send 70p in stamps with your address. Mark enquiry PW.

Goods are normally despatched by return.





TRIO *pacesetter in amateur radio*

HF

We've handled a lot of equipment in our time as radio amateurs but the TS830S really took us by storm. As you will hear if you listen on the air, it's reputation is high all round the world. We think the TS830S is exactly right for the operator who has carefully considered all the features necessary for top performance, put aside all the gimmickry and found the TS830S.

This rig offers you all band coverage; true frequency readout on all modes; variable bandwidth *and* passband tuning; rugged, reliable 6146B valves in the PA; top quality both in construction and design; and, above all, the Trio reputation for giving you the best equipment at a reasonable price. Thousands of happy users worldwide will confirm that if you want total satisfaction, try the TS830S. Send for comprehensive details today.

TS 830S

£694.30 inc VAT

Securicor Carriage £4.50



A recent addition to the Trio HF range, and proving amazingly popular is the new TS530S. Designed as a "little brother" to the TS830S, the TS530 uses the same PLL system, same RF boards, same readout system and many other features of the 830 but without the variable bandwidth facility. You do, of course, have the famous Trio I.F. shift system for dodging the QRM.

We really believe that the TS530S is the finest mid-price HF base station transceiver on the market and we would like the opportunity to prove it to you. Why not call us, or call in person to see and try out this super rig.

If you like to read lists of features, how about 160-10 metres including new bands: passband tuning on all modes: 6146B PA tubes for low intermod: low power tune up: digital readout shows true frequency at all times: VOX built in: CW sidetone: speech processor: noise blanker: etc. etc.

TS 530S

£534.98 inc VAT

Securicor Carriage £4.50



For the keen mobile/portable enthusiast, the "no-tune" solid state transceiver has proved irresistible, and the Trio TS130S is probably the best of the bunch. When the original TS120 was introduced, there were gasps of amazement at Trio's achievement in making a first class HF rig in such a small size. With the advent of the TS130S, the mobile rig really comes to maturity. Imagine an 8 band transceiver with digital readout, I.F. shift, vox, speech processor, single conversion PLL derived transmitter and receiver, 100W output, red hot receiver – and all in a package you can carry on the palm of one hand. It's really a staggering thought.

The unquestioned excellence of Trio design and manufacture shows in every aspect of the TS130S – why not see it and try it for yourself.

TS 130S.V

£525.09 inc VAT

Securicor Carriage £4.50



The compact DFC230 Digital Frequency Controller provides maximum efficiency and flexibility for mobile and fixed operation by combining a 20Hz step digital VFO with 4 memories. ● 20Hz step digital VFO: ● Four memories: Frequency can be transferred from VFO to memory or from memory to VFO. ● Built-in digital display: Shows digital VFO or memory frequency. ● Perfect for mobile installation. ● UP/DOWN manual scan: Frequency can be shifted with UP/DOWN microphone (supplied with DFC-230) or with FAST STEP switch on front panel. ● Cross-operation switch: Allows split-frequency operation, with transceiver VFO on transmit and DFC-230 (VFO or memory) on receive, or vice-versa. ● RIT (receiver incremental tuning). ● RIT, VFO, and MEMO indicators: LEDs show functions in operation. ● Compatibility with TS-830S, TS-120S/V and TS-130S/V.

DFC 230

£179.86 inc VAT Securicor carr. £4.50

LOWE IN LONDON

NOW OPEN, OUR EMPORIUM IN THE CITY

278 PENTONVILLE ROAD, LONDON N1 9NP [NO MAIL ORDERS]

THE EMPORIUM IS IN THE BASEMENT OF THE "HEPWORTHS" SHOP



Buy direct from us, get two years full

The Tiny Tiger!

IC25E. 25W 2M FM Mobile.



Amazingly small, yet very sensitive. Two VFO's, five memories, priority channel, full duplex and reverse, LED S-meter, 25KHz or 5KHz step tuning, same multi-scanning functions as the 290 from mic or front panel. All in all the best 2M FM mobile ICOM have ever made.

IC290E. 2M Multimode Mobile.



10W RF output on SSB, CW and FM. Standard and non-standard repeater shifts. 5 memories and priority channel. Memory scan and band scan, controlled at front panel or microphone. Two VFO's. LED S-meter. 25KHz and 1KHz on FM – 1KHz and 100KHz tuning steps. Instant rev-repeat.

IC24G. 10W 2M FM Mobile.



This is the low-cost, easy to use economy model. Full bank – 80 channels at 25KHz spacing by easy to use press button switches. 12 $\frac{1}{2}$ KHz spacing if required, and the same reliable performance as the famous IC240. Price £169.

IC202S/402
3W 2M or 70cm.
SSB Portables.



These two have been around for a long time and are well proven. SSB, CW and side-tone. They come fitted with 144 – 144.4 (IC202S) and 432 – 432.4 (IC402). Battery or 12v operation. Built-in antenna or socket for external antenna.

IC2E £159-IC4E £199



– Nearly everybody has an IC2E – the most popular amateur transceiver in the world – now there is the 70 cm. version which is every bit as good and takes the same accessories. Check the features:

Fully Synthesized – Covering 144 – 145.995 in 400 5KHz steps. (430-439.999 4E).

Power Output – 1.5W with the 9v rechargeable battery pack as supplied – but lower or higher output available with the optional 6v or 12v packs.

BNC Antenna Output Socket – 50 ohms for connecting to another antenna or use the Rubber Duck supplied (flexible $\frac{1}{4}$ λ whip – 4E)

Send/Battery Indicator – Lights during transmit but when battery power falls below 6v it does not light, indicating the need for a recharge.

Frequency Selection – by thumbwheel switches, indicating the frequency. + 5KHz switch – adds 5KHz to the indicated frequency.

Duplex Simplex Switch – gives simplex or plus 600KHz or minus 600KHz transmit (+ 1.6MHz and listen input on 4E).

Hi-Low Switch – reduces power output from 1.5W to 150mW reducing battery drain.

External Microphone Jack – If you do not wish to use the built-in electret condenser mic. an optional microphone/speaker with PTT control can be used. Useful for pocket operation.

External Speaker Jack – for speaker or earphone. This little beauty is supplied ready to go complete with nicad battery pack, charger, rubber duck.

A full range of accessories in stock.

		£ p
ICML1	10W mobile booster for IC2E	49.00
BP5	11 volt battery pack	30.50
BP4	Empty battery case for for 6 x AA cells	5.80
BP3	Standard battery pack	17.70
BP2	6 volt pack	22.00
BC30	Base charger for above	39.00
BC25	Mains charger as supplied	4.25
DC1	12 volt adapter pack	8.40
HM9	Speaker/microphone	12.00
CP1	Mobile charging lead	3.20
IC1/2/3	cases	3.60
		each

All prices include VAT

The IC4E is going to revolutionise 70cm!

Practical Wireless, February 1982

or our agents and warranty on all equipment.

**ICOM produce the
complete HF line-up!**

IC730. 100W HF All Band Mobile.



80 – 10M, 8 bands SSB, AM and CW. Two VFO's with 10Hz – 100Hz and 1KHz steps. Memory for each band. Noise blanker, vox, CW monitor, APC and SWR detector. Speech processor and fan. Switchable RF pre-amp and WWV. 13v DC operation or use ICPS15 mains.

**IC720A. 100W HF
+ Gen Coverage Transceiver.**



This is the best money can buy. AM, SSB, RTTY and CW. Built-in fan, speech processor, two VFO's and APC. Tuning rates down to 10Hz and memories. General coverage receiver from 100KHz to 30MHz (transmit too if you have a licence!) Run from 13vDC or use PS15 mains PSU.


For the complete station.

Controlled remotely from the ICOM range (or by one switch for other HF rigs):-
IC2KL.

The superb solid state linear to give you the legal limit on all HF bands with no tuning and a very clean signal.

**Please Ring us for the Latest Prices,
you may call after hours using our
Ansaphone on: 02273 63850.**

ICAT500.

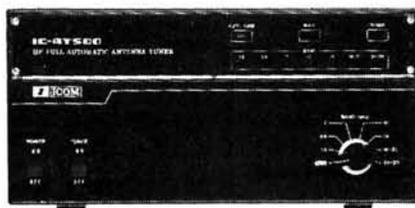

Automatic ATU which really is automatic and even selects the correct antenna for you! Faster than its competitors. Handles 500W (1Kw PEP) – 100W version is AT-100.

**IC251E and IC451 2M and 70cm.
All Mode Base Stations.**



Both well proven designs with twin VFO's, variable tuning rates and power output, scanners and memory channels, automatic repeater operation with full reverse, 144 – 146 or 430 – 440, low output on FM, SSB and CW, built-in 12 and 240v supplies. None other like them.

TONO PRICE LIST

	Communications	£ p
7000E	CW/RTTY/ASC11 Terminal Tx/Rx	599.00
350	CW/RTTY/ASC11 Terminal Rx Only	259.00
CRT 120G	VDU 12 inch Green Screen Mains Power	125.00
HC900	Intelligent Line Printer 4 Cases +	590.00
HC800	Line Printer Centronics	449.00
SK7	Plug Adaptor For Printers	8.50

Linears

2M-50W	40 Watt Linear For 2 Metres	65.00
2M-100W	90 Watt Linear for 2 Metres	115.00
MR-150W	140 Watt Linear For 2 Metres	159.00
MR-250W	210 Watt Linear For 2 Metres	259.00
MR28	100 Watt Linear for 10 Metres	65.00
UC70	50 Watt Linear For 70cms	149.00

Preamps

RX-144	Mast Head Preamp For 2 Metres	65.00
RX-430	Mast Head Preamp For 2 Metres	70.00

SWR/Power

ASW-180	1.8-160 Mhz	45.80
ASW-430	430 Mhz	49.50

TASCO TELEREADER

	Communications	£ p
CWR-685	CW/RTTY Terminal + VDU + Keyboard. Tx & Rx	699.00
CWR-680	CW/RTTY Terminal Rx Only No VDU	189.00
CWR-670	As Above But De-Luxe Model	259.00

Thanet Electronics 

143 Reculver Road, Herne Bay, Kent. Tel: 02273 63859

AGENTS (PHONE FIRST - evenings and weekends only)

Scotland Jack GM8GEC (031-665-2420) Wales Tony GW3FKO (0874 2772 or 3992)
North West Gordon G3LEQ (0565 4040) Midlands Tony G8AVH (021-329-2305)
Ansafone Service available

WATERS & STANTON ELECTRONICS

18/20 MAIN ROAD, HOCKLEY, ESSEX. TEL (0702) 206835

4,000 SQ FT
DEVOTED TO
RADIO COMMUNICATION

24 HOUR TURN ROUND
ON ALL ORDERS!

"SUCH NICE PEOPLE"

5 miles from Southend-on-Sea
Why not bring the whole family for a day out?
(Early Closing: Wednesday 1.00 pm)




TUNE INTO THE WORLD... FROM YOUR ARMCHAIR! FRG7700 £319



Securior £5.00 extra

Here's a complete monitoring system that builds up into a comprehensive listening system for a wide variety of transmissions, both locally and from the other side of the World. As communications engineers, we know there is good equipment and poor equipment. We rate the FRG7700 very highly. It forms the main unit of the system and provides one of the most cost effective ways of listening to the entire shortwave band. Listen to all the World news direct as it comes in from stations stretching round the Globe, international family requests from Australia and New Zealand, sport from America, topical news comment from Russia and China. If you're interested in Amateur Radio then the SSB facility lets you listen in on conversations with amateurs from places far and near. Hear a mobile operator motoring through the traffic in Manchester or going home from work in Perth, Australia. Listen to expeditions in Africa or the Antarctic. It's all possible and the more skilled the operator, the more interesting it becomes. The possibilities are endless, ship to shore radio, aircraft on the Atlantic run, foreign news agencies, etc. And if this is not enough plug in the optional VHF converter and listen to private, commercial and military air traffic over the U.K., local airports, local shipping, taxis, radio amateur repeaters and many other interesting transmissions. To improve reception, there's also the matching aerial tuning unit. So why not send S.A.E. today for full coloured leaflets and enjoy a new hobby from the comfort of your fireside. Go on - treat yourself!

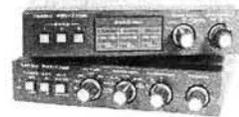AERIAL TUNER £37.00
VHF CONVERTERS From £69.95



NEW FROM SONY ICF-2001

The new SONY ICF-2001 is a desk top receiver that covers the World. 150kHz to 30MHz SSB and AM plus FM 76-108MHz. Full digital readout, scanning and memories are included and controlled by a microprocessor. Power requirements are either 230V AC, 12v DC or internal HP2 cells. At present deliveries are slow so please phone for latest information.



£152 inc carriage

KILL TV INTERFERENCE DEAD! HP4A TV FILTER £5.95

If you're suffering from or indeed causing TV interference through CB or Amateur Radio transmissions then this is the answer. Specially designed for us in Japan for the UK TV channels it incorporates both filter and braid-breaker. Its the most effective filter we have come across.

FERRITE RINGS £1 for 2 p&p inc.

These rings are purpose designed for curing audio interference. Simply wind the signal or speaker lead around it.



REMEMBER - WE OFFER THE FASTEST MAIL ORDER SERVICE IN THE UK!
SEND S.A.E. FOR 1982 CATALOGUE

HF TRANSCEIVERS

Trio	TS830S SSB/CW 100W 230V AC	£694.00	(n/c)
Trio	AT230 Aerial tuner & power meter	£118.00	(2.00)
Trio	TS530S SSB/CW 100W 230V AC	£534.00	(n/c)
Trio	TS130S SSB/CW 100W 12V DC	£525.00	(n/c)
Trio	TS130V SSB/CW 10W 12V DC	£445.00	(n/c)
Trio	MS100 Mobile mounting for above	£17.00	(1.50)
Trio	PS30 230V PSU for TS130S	£88.50	(5.00)
Yaesu	FT-1 AM, FM, SSB & CW 100W	P.O.A.	(n/c)
Yaesu	FT101ZFM SSB/CW/FM 100W 230V AC	£590.00	(n/c)
Yaesu	FT101ZFM As above with digital	£645.00	(n/c)
Yaesu	FR302DM AM/FM/SSB/CW 100W 230V AC	£885.00	(n/c)
Yaesu	FL1100Z 160-10W 1.2kw linear	£425.00	(n/c)
Yaesu	FT707 SSB/CW/AM 100W 12V DC	£549.00	(n/c)
Yaesu	FP707 230V AC PSU for above	£125.00	(5.00)

VHF TRANSCEIVERS

Trio	TS770E 2m/70cm 10W 230V AC	£784.00	(n/c)
Trio	TR9000 2m FM/SSB 10W 12V DC	£374.00	(n/c)
Trio	PS20 AC PSU for above	£48.00	(2.50)
Trio	B05 Base plinth for TR9000	£34.95	(1.75)
Trio	TR730 2m FM 25W 12V DC	£247.00	(n/c)
Trio	TR7800 2m FM 25W 12V DC	£284.00	(n/c)
Trio	TR7850 2m FM 40W 12V DC	£314.00	(n/c)
Trio	TR2300 2m FM 1W Portable	£186.75	(n/c)
Trio	TR2400 2m FM 1W hand-held	£198.00	(n/c)
Trio	TR2500 2m FM 1W hand-held	P.O.A.	(n/c)
Trio	TR8400 70cm FM 10W 12V DC	£334.00	(n/c)
Trio	TR9500 70cm FM/SSB 10W 12V DC	£448.00	(n/c)
Yaesu	FT480R 2m FM/SSB 10W 12V DC	£365.00	(n/c)
Yaesu	FT230R 2m FM/SSB 3W portable	£248.00	(n/c)
Yaesu	FT208 2m FM 2W portable	£205.00	(n/c)
Yaesu	FT708 70cms FM 2W portable	£218.00	(n/c)
FDK	M700EX 2m FM 25W 12V DC	£199.00	(n/c)
FDK	M750E 2m FM/SSB/CW 10W 12V DC	£289.00	(n/c)
FDK	Expander 70cm adaptor for above	£219.00	(n/c)
FDK	PS750 230V AC PSU	£96.00	(2.00)
FDK	FT1200 2m FM portable	£178.00	(n/c)
FDK	Palm II 2m FM portable	£109.00	(n/c)
FDK	Palm IV 70CM FM portable	£148.00	(n/c)
Azden	PCS3000 2m FM 25W 12V DC	£219.00	(n/c)
Azden	PCS300 2m FM 3W portable	£184.00	(n/c)
Azden	PCS2600 28MHz FM 10W 12V DC	£179.00	(n/c)

HF RECEIVERS

Trio	R1000 200kHz-30MHz SSB/AM/CW	£297.00	(n/c)
Trio	R600 200kHz-30MHz SSB/AM/CW	P.O.A.	(n/c)
Yaesu	FRG7 500kHz-30MHz SSB/AM/CW	£199.00	(n/c)
Yaesu	FRG7700 200kHz-30MHz SSB/AM/FM/CW	£319.00	(n/c)
Yaesu	FRG7700M As above but with memory	£469.00	(n/c)
Yaesu	FR7700 Matching a.t.u.	£37.75	(1.50)
Lowes	SRX30 500kHz-30MHz SSB/AM/CW	£158.00	(n/c)
Lowes	SRX300 500kHz-30MHz Digital	£195.00	(n/c)
Global	AT1000 swl atu. 200kHz to 30MHz	£31.95	(1.50)
Yaesu	FRV7700A Rx converter 118-150MHz	£89.75	(1.50)
Yaesu	FRV7700B Rx converter 50-80, 118-130, 140-150MHz	£75.50	(1.50)
Yaesu	FRV7700C Rx converter 140-170MHz	£65.95	(1.50)
Yaesu	FRV7700D Rx converter 70-80, 118-130, 140-150MHz	£72.45	(1.50)

NOTE: above converters only work with FRG7700 receivers.

VHF RECEIVERS

TMS58	2m FM Scan 230V or 12V DC	£89.00	(n/c)
SAD8	2m FM hand-held	£55.00	(n/c)
SAM161	2m FM mobile 12V DC	£55.00	(n/c)
BEARCAT	220FB 66-500MHz 230V AC	£229.00	(n/c)
SX200N	28-500MHz 230V AC	£280.00	(n/c)
SR9	2m FM tuneable 12V DC	£48.00	(2.00)
SR9	Marine version	£48.00	(2.00)
AR22	2m FM 600 channel hand-held	£89.00	(1.50)
AR22M	Marine version of above	£95.00	(1.50)
RS17	Air band hand-held	£49.50	(1.50)
RS28	Air band scanner	£89.50	(1.00)
Sharp	FX213 Air-band monitor	£13.50	(1.00)

ROTATORS

CDE AR40	suits large VHF aerials (5 core)	£82.00	(2.50)
Channelmaster	9502 suits VHF aerials (3 core)	£54.00	(2.50)
KR400RC	suits HF aerials (6 core)	£98.00	(2.50)
Hirschmann	250 suits VHF aerials (3 core)	£43.00	(2.50)
CDE	alignment bearing	£9.00	(1.25)
Hirschmann	and Channelmaster alignment bearings	£11.75	(1.25)

SWR/POWER METERS

WELZ SP200	1.8-160MHz 20-200-1KW	£59.95	(n/c)
WELZ SP300	1.8-500MHz 20-200-1KW	£79.00	(n/c)
WELZ SP400	130-500MHz 5-20-150W	£59.00	(n/c)
WELZ SP45	140-470MHz 3-20-100W	P.O.A.	(n/c)
WELZ SP15M	1.8-160MHz 2.5-20-200W	£29.95	(n/c)

MISC ACCESSORIES

SEIF	13.8V 4 amp DC power supply	£24.95	(2.00)
PS125	13.8V 5 amp DC power supply	£29.95	(2.50)
Global	PS15 6 amp DC power supply	£32.95	(2.50)
EK121	Electronic Morse key	£29.00	(1.50)
Deluxe	Telegraph Morse key (manual)	£10.50	(0.75)
CW2A	general purpose Morse code oscillator	£8.95	(0.75)
MF210	Self powered 2m FM monitor	£9.00	(0.50)
FX1	deluxe station wavemeter	£33.00	(1.00)
DM81	700kHz-250MHz dip meter	£69.00	(1.50)
Station	Log books	£1.95	(0.75)
BL40X	balun 3-40MHz 1KW	£11.25	(0.75)
HP3A	TV1 filter	£3.95	(0.40)
Drake	TV3300 low pass filter	£18.40	(1.00)
Shure	4440 base station mic	£27.50	(1.50)
Shure	201 hand mic	£12.50	(1.00)
MM202S	Mobile safety mic	£20.95	(1.00)
MM202H	Mobile safety mic	£29.00	(1.00)
AMS02	Base station compressor mic	£39.00	(1.25)
AM802	Base station deluxe mic	£59.00	(1.25)
AM801	High low compressor mic	£44.00	(1.25)

WE ALSO STOCK
FULL RANGE OF:-


DATONG
MICROWAVES
TAL AERIALS
HYGAIN
JAYBEAM etc.

**LEGAL BASE
AERIAL!**

"BLUE DIAMOND"

- ★ 27-60-28MHz
 - ★ Ideal for UK FM
 - ★ Weatherproof
- THIS IS A REAL
TOP PERFORMER**

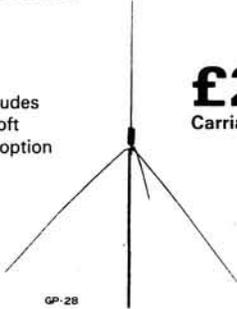*Price includes compact loft mounting option kit.



£25*
Carriage £2.50

**ATTENTION SERIOUS CB'ERS
NEW! DATONG £29.30
"CODE CALL" p&p 50p**

This compact little unit enables you to have a completely private channel on your CB rig. Only the person dialling one of over 4000 channels on the self contained "code call" will be able to break the squelch on your rig (which also has to be fitted with an identical unit). No more noisy channels to monitor and only a single connection to the speaker output.
INTERNAL SWITCH SETTING MODEL
£27.60 + 50p p&p

**PROFESSIONAL AIRCRAFT MONITOR
R517 £49.50**
(as supplied to pilots, ground crew etc.)

The R517 is a professional aircraft monitor receiver, having superb sensitivity and capable of tuning across the entire aircraft band 118-143MHz. For easy tuning there is both a coarse and fine tuning control. In addition there is a 3 position switch for selecting xtal controlled channels (xtals £3.00 extra) for your local airport. The unit is completely portable running off self-contained batteries.

AZDEN POWER MIC

The new Azden DX-354 desk mic is purpose made for ham radio & CB by one of Japan's foremost audio engineering companies. With its heavy die cast metal casing, built-in variable compressor and 500-50k ohm o/p, it matches any transceiver. Our ridiculously low price makes it a must.

£29.00

**MAIL ORDER –
FASTEST IN THE
BUSINESS!**

**TEL
(0702)
206835
or
204965
FOR
ACTION!**

**JUST
ARRIVED!**

**AZDEN
PCS300**

3 Watts FM
144-146MHz
12½KHz steps

£184

inc battery & charger
Available February

You're looking at a picture of a most remarkable hand-held transceiver at an equally remarkable price! Over 3 watts output, high/low power switching, 3 way scanning of band, segment, or memories. And talking about memories its miserly back-up circuit consumes only a fraction of 1ma. No more flat batteries in the morning! The clear LCD display provides steps of 12½KHz and even has a bar S-meter. In short it's incredible value and an incredible performer.

**FDK
M750E TRANSCEIVER
2M FM-SSB-CW**

- ★ 1/10 Watts
- ★ All modes
- ★ Digital readout
- ★ 144-146MHz
- ★ Tone burst
- ★ RF gain control
- ★ Dual FVO
- ★ Up/down Mic
- ★ Hardware kit

£289 (carriage free)
SAE FOR COLOUR LEAFLET

**SUPER
DEAL**

**FDK
M700EX TRANSCEIVER
2M FM 25 WATTS**

- ★ Synthesized
- ★ 25 & 12½ KHz steps
- ★ Priority scanning
- ★ Variable power
- ★ Digital display
- ★ Tone burst
- ★ Reverse repeater
- ★ Fully protected
- ★ Hardware kit

£199 (carriage free)
SAE FOR COLOUR LEAFLET

**SUPER
DEAL**

C.B. ANNOUNCEMENT

CB is now legal and we now have in stock a good selection of transceivers and associated equipment. With 10 years in the telecommunications business behind us you can be assured of sound advice and a good deal. Every item we sell conforms to the UK CB specification and we have extremely comprehensive test facilities for pre-delivery checking and after sales backup. It makes sound sense to come to the specialists but if you are too far away we shall be happy to despatch your CB equipment to you via our MAIL ORDER DEPARTMENT. So whether its instant advice or instant despatch why not give us a call on the telephone.

**AMSTRAD
FIDELITY
CYBERNET etc etc**
Prices start at
£69 Phone for latest prices

**YW-3
£12.50**
Post free

An swr meter is essential if you want the strongest signals and also protection for your rig. We have seen many models but without doubt we haven't seen anything that will beat the YW-3 for accuracy. Its great value. Order yours today.

**THE COMPLETE ELECTRONICS CENTRE
FOR AMATEUR RADIO - CB - HI-FI - VIDEO E&OE**

MAIL ORDER SLIP to: Waters & Stanton Electronics, Warren House, Main Road, Hockley, Essex.

Name..... Goods required

Address.....

.....

.....

Please rush me the above. Cheque enclosed for £...../Please charge to credit card No.....

Neosid Ltd., Brownfields, Welwyn Garden City, The Specialists for:

FERRITE COMPONENTS ● COIL FORMERS ● BOBBINS ● INDUCTOR PARTS

PW Kits currently available:

PW10 "NIMBUS" COIL COMPONENTS

Formers, cans, bases, cores and beads required for this project. Kit includes winding wire and trimming tool.

REF PW10 PRICE **£6.65** inc. P&P

PW30 "HELFDOR" COIL COMPONENTS

Type A6 coil assemblies, balun cores, 6mm coil former, screening beads.

REF PW30 PRICE **£3.95** inc. P&P

REF650 TRIMMING TOOL KIT

Adjusters for I.F. coils, 3mm & 4mm. Convergence coils 6mm including hexagonal type.

REF 650 PRICE **£1.25** inc. P&P

CATALOGUE OF STANDARD PARTS
AVAILABLE - SEND S.A.E.

Don't be short of coil parts, buy our PW20 kit and be prepared!

GENERAL INDUCTOR COMPONENTS



Kit comprises:
Type A6 assemblies.
3mm coil formers and screw cores.
4mm coil formers and screw cores.
Ferrite rods.
Miniature balun cores.
Suppression beads.
Axial leaded choke cores.
Trimming tools 3mm & 4mm.

REF PW20 PRICE **£6.10** inc. P&P

PLEASE ALLOW 10-14 DAYS FOR DELIVERY

"STOUR" TRANSCEIVER

THE RECENT ADDITION TO OUR RANGE OF KITS FOR CONSTRUCTORS

comprising:
Type A6 assembly.
Type HA2 assemblies.
Ferrite toroids.

REF PW40 PRICE **£10.90** inc. P&P

RF NOISE BRIDGE LATEST PW PROJECT Toroid and winding wire.

REF PW50 PRICE **£1.00** inc. P&P

CERAMIC MAGNETS

Selection of 20 assorted ceramic magnets - varying shapes and magnetisation patterns. Educational/Practical - Hobby/Leisure - Even Fun.

REF MP110 PRICE **£4.50** inc. P&P

PLEASE SUPPLY:

.....PW/REF..... £.....inc. P&P

.....PW/REF..... £.....inc. P&P

I ENCLOSE PO/CHEQUE No. for £.....

NAME.....

ADDRESS.....

NEOSID SMALL ORDERS

NEOSID SMALL ORDERS
P.O. BOX 86
WELWYN GARDEN CITY
HERTS AL7 1AS

NEOSID

TELECOM.

ICOM:-	£	SOMMERKAMP	£
IC720A	883	TS280FM	179
IC730	586	FT7B	399
IC251	495	YC7B	77
IC451	599	FT209R	229
IC290	369	FT101ZD	575
IC2E	169	FT707	569
		FT207	169
		FT707	109
		FRG7	199


PLUS ALL ICOM ACCESSORIES

WE CARRY A RANGE OF SWR AND POWER METERS. ANTENNA SWITCHES - DUMMY LOADS - ROTATORS - REVCO WHIPS - CABLES - CONNECTORS ETC.

ACCESS/BARCLAY HP TERMS
6 NEW ST., BARNSELY, SOUTH YORKS.
Phone: 0226 5031

HEAR MORE

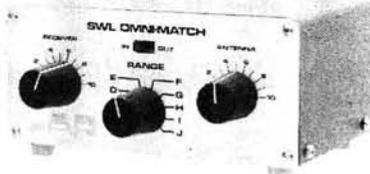£29.95
inc. VAT
p & p £1.75
add £2.00
for SO239.



SAE for leaflet
Transmitting
Omni-matches
also available

WITH THE SWL OMNI-MATCH

- Better matching
- Clearer signals
- Latest design
- Wider coverage
- Optimised for receiving 200 kHz-30 MHz.
- Improves any antenna/receiver combination. Goods by Return.

LAR
MODULES LIMITED

60 Green Road,
Leeds LS6 4JP
Telephone 0532 782224

ANSAFONE
VISA
MasterCard

ADAPTORS
HIGH QUALITY TRANSFORMERS
AND POWER SUPPLIES



EYEBALL!! EYEBALL!!


POWER SUPPLY ONLY **£10.95** + VAT & P/P
13.8v 3/5 AMP

WITH OVERVOLTAGE PROTECTION



TYPE CB3500

MADE IN ENGLAND

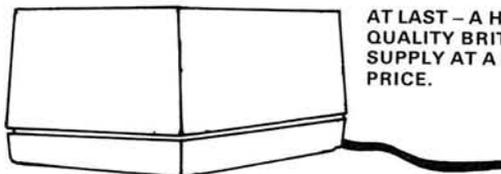

AT LAST - A HIGH-QUALITY BRITISH POWER SUPPLY AT A FANTASTIC PRICE.

PLEASE SUPPLY _____ (QTY) CB 3500 POWER SUPPLIES AT £10.95 Each
+ £1.64 VAT AND £1.75 P/P TOTAL £14.34

I enclose Cheque/PO for £ _____ Name _____

Address _____

The CB 3500 is full of features you would expect on units costing nearly three times as much. HOW IS IT DONE? Quite simply by design and the advantages of mass production.

The CB 3500 is housed in a durable metal case and comes with full instructions for use. The output is fused on the PCB and there is also a thermal fuse on the transformer for added protection.

SEND TODAY - your money back if not completely satisfied.

Please allow 28 days for delivery.

SEND TO TITAN TRANSFORMERS, DEPT. PW, CENTRAL HALL, DUNCOMBE STREET, GRIMSBY, SOUTH HUMBERSIDE, DN32 7EG

CHATTER- BOXES SERVED HERE.



Realistic is the biggest name in Citizens Band Radio and accessories – and you will be able to buy the full range at Tandy – the world's largest retailer of CB equipment!

REALISTIC®
CB from Tandy

WATCH PRESS FOR FORTHCOMING ANNOUNCEMENTS

VALVES

V.A.T. INCLUDED

A1065	1.40	EF83	1.75	PC850	0.80	U27	1.15	SV4G	0.75	6J56C	2.95	2001	0.80
A2293	0.80	EF85	0.80	PC85	0.80	U191	0.85	5Y3GT	0.80	6K7	0.80	20F2	0.85
A2900	0.20	EF80	0.75	PC88	0.95	U281	1.70	5Z1	1.50	6EM4	0.80	20E1	1.20
A98	0.75	EF91	1.50	PC89	0.95	U301	0.85	5Z4G	0.75	6L6G	2.00	20P1	0.85
ARP3	0.70	EF91	1.50	PC89	0.95	U301	0.85	5Z4GT	1.05	6L6GC	2.10	20P3	0.75
ATP4	0.60	EF92	2.00	PC89	0.95	U301	0.85	6B02L	0.90	6L6GT	1.25	20P4	1.25
B12H	1.90	EF95	0.85	PC89	0.95	U301	0.85	6B07	0.70	6L6G	2.00	20P5	1.25
CY1	1.40	EF96	0.80	PC89	0.95	U301	0.85	6B07	0.70	6L6G	2.00	20P5	1.25
DAF90	0.70	EF183	0.80	PC89	0.95	U301	0.85	6B07	0.70	6L6G	2.00	20P5	1.25
DET22	2.85	EF184	0.80	PC89	0.95	U301	0.85	6B07	0.70	6L6G	2.00	20P5	1.25
DF96	0.70	EF204	4.95	PC89	0.95	U301	0.85	6B07	0.70	6L6G	2.00	20P5	1.25
DW16	0.75	EF212	1.85	PC89	0.95	U301	0.85	6B07	0.70	6L6G	2.00	20P5	1.25
DL52	0.60	EF240	1.85	PC89	0.95	U301	0.85	6B07	0.70	6L6G	2.00	20P5	1.25
DY86/87	0.85	EH90	0.85	PC89	0.95	U301	0.85	6B07	0.70	6L6G	2.00	20P5	1.25
DY902	0.70	EL32	1.10	PC89	0.95	U301	0.85	6B07	0.70	6L6G	2.00	20P5	1.25
ES2	14.80	EL34	2.90*	PC89	0.95	U301	0.85	6B07	0.70	6L6G	2.00	20P5	1.25
EBBC	1.40	EL37	4.40	PC89	0.95	U301	0.85	6B07	0.70	6L6G	2.00	20P5	1.25
EBBC/01	1.10	EL37	4.40	PC89	0.95	U301	0.85	6B07	0.70	6L6G	2.00	20P5	1.25
E102C	1.20	EL81	2.45	PC89	0.95	U301	0.85	6B07	0.70	6L6G	2.00	20P5	1.25
E102CC	2.80	EL82	0.70	PC89	0.95	U301	0.85	6B07	0.70	6L6G	2.00	20P5	1.25
E182CC	4.95	EL86	0.95	PC89	0.95	U301	0.85	6B07	0.70	6L6G	2.00	20P5	1.25
EAT8	2.25	EL90	1.00	PC89	0.95	U301	0.85	6B07	0.70	6L6G	2.00	20P5	1.25
SAB200	0.80	EL91	4.20	PC89	0.95	U301	0.85	6B07	0.70	6L6G	2.00	20P5	1.25
EB91	0.80	EL95	0.80	PC89	0.95	U301	0.85	6B07	0.70	6L6G	2.00	20P5	1.25
EB93	1.15	EL95	0.80	PC89	0.95	U301	0.85	6B07	0.70	6L6G	2.00	20P5	1.25
EB930	0.90	EL93	5.90	PC89	0.95	U301	0.85	6B07	0.70	6L6G	2.00	20P5	1.25
EB930	0.80	EL93	5.90	PC89	0.95	U301	0.85	6B07	0.70	6L6G	2.00	20P5	1.25
EB93	0.80	EL93	5.90	PC89	0.95	U301	0.85	6B07	0.70	6L6G	2.00	20P5	1.25
EB93	0.80	EL93	5.90	PC89	0.95	U301	0.85	6B07	0.70	6L6G	2.00	20P5	1.25
EB93	0.80	EL93	5.90	PC89	0.95	U301	0.85	6B07	0.70	6L6G	2.00	20P5	1.25
EC52	0.85	EL822	0.95	PC89	0.95	U301	0.85	6B07	0.70	6L6G	2.00	20P5	1.25
EC31	3.40	EM31	1.60	PC89	0.95	U301	0.85	6B07	0.70	6L6G	2.00	20P5	1.25
EC32	0.85	EM80	0.85	PC89	0.95	U301	0.85	6B07	0.70	6L6G	2.00	20P5	1.25
EC81	0.85	EM81	0.85	PC89	0.95	U301	0.85	6B07	0.70	6L6G	2.00	20P5	1.25
EC82	0.80	EM84	0.85	PC89	0.95	U301	0.85	6B07	0.70	6L6G	2.00	20P5	1.25
EC83	0.85	EM81	0.85	PC89	0.95	U301	0.85	6B07	0.70	6L6G	2.00	20P5	1.25
EC84	0.80	EM81	0.85	PC89	0.95	U301	0.85	6B07	0.70	6L6G	2.00	20P5	1.25
EC85	0.80	EM81	0.85	PC89	0.95	U301	0.85	6B07	0.70	6L6G	2.00	20P5	1.25
EC86	1.70	EM88/87	0.80	PC89	0.95	U301	0.85	6B07	0.70	6L6G	2.00	20P5	1.25
EC88	0.80	EM88	0.80	PC89	0.95	U301	0.85	6B07	0.70	6L6G	2.00	20P5	1.25
EC89	0.80	EM88	0.80	PC89	0.95	U301	0.85	6B07	0.70	6L6G	2.00	20P5	1.25
EC89/01	0.80	EM88	0.80	PC89	0.95	U301	0.85	6B07	0.70	6L6G	2.00	20P5	1.25
EC90	0.80	EM88	0.80	PC89	0.95	U301	0.85	6B07	0.70	6L6G	2.00	20P5	1.25
EC91	0.80	EM88	0.80	PC89	0.95	U301	0.85	6B07	0.70	6L6G	2.00	20P5	1.25
EC92	0.80	EM88	0.80	PC89	0.95	U301	0.85	6B07	0.70	6L6G	2.00	20P5	1.25
EC93	0.80	EM88	0.80	PC89	0.95	U301	0.85	6B07	0.70	6L6G	2.00	20P5	1.25
EC94	0.80	EM88	0.80	PC89	0.95	U301	0.85	6B07	0.70	6L6G	2.00	20P5	1.25
EC95	0.80	EM88	0.80	PC89	0.95	U301	0.85	6B07	0.70	6L6G	2.00	20P5	1.25
EC96	0.80	EM88	0.80	PC89	0.95	U301	0.85	6B07	0.70	6L6G	2.00	20P5	1.25
EC97	0.80	EM88	0.80	PC89	0.95	U301	0.85	6B07	0.70	6L6G	2.00	20P5	1.25
EC98	0.80	EM88	0.80	PC89	0.95	U301	0.85	6B07	0.70	6L6G	2.00	20P5	1.25
EC99	0.80	EM88	0.80	PC89	0.95	U301	0.85	6B07	0.70	6L6G	2.00	20P5	1.25
EC00	0.80	EM88	0.80	PC89	0.95	U301	0.85	6B07	0.70	6L6G	2.00	20P5	1.25

VALVES and transistors

Telephone enquiries for valves, transistors, etc: retail 749 3934, trade and export 743 0899.

COLOMOR 907/3530 London
(ELECTRONICS) LTD.
170 Goldhawk Rd., London W.12

*SPECIAL QUALITY
POSTAGE: £1-£3 45p; £3-£5 55p; £5-£10 60p; £10-£15 75p; £15-£20 90p; over £20 free.
PRICES MAY VARY Delivery by return of post.
Tel. 01-743 3934
Open Monday to Friday 9-1 pm, 2.00-5.30 pm.

AI ELECTRONICS

20, Barby Lane, Hillmorton, Warwickshire CV22 5QJ.
Tel: Rugby (0788) 78473

Cash with order, mail order only or callers by appointment. All prices include VAT at 15%, please add 60p post & packing. Full money back guarantee on all items.

FT101 NBFM ADAPTER



Suitable for all models up to FT101E

With increasing interest in using FM mobile on ten meters & also the new legalisation of FM for 27 MHz CB use you can now use your older FT101 on these bands by adding one of our super FM Adapters. This unit will give transmit and receive facility without having to drill any holes or any modifications to your FT101, just plugs into existing sockets at the rear of the FT101, only one wire to be soldered across the clarifier control—this wire is only required for the transmit mode. The adapter also has built in 17.5KHz crystal controlled tone burst generator for accessing repeaters when the FT101 is used in conjunction with a transmitter for VHF/UHF. No need to unplug when changing modes or bands just switch the adapter off and this reverts the FT101 back to normal operation. Deviation, Mic gain & tone burst are all adjustable with pre-set control internally so can be set to your requirements size only 185x105x42mm, PRICE £75.00. Data sheet available on request.

27MHz RECEIVER PRE-AMP item up with that old type Rx. with our ready made unit size only 60x40mm. 25db gain with 1db NF. with pre-set gain control. PCB only — £8.00 or built into grey hammer finish die cast box with BNC sockets £12.00.

RF POWER TRANSISTORS—
2N6083 £6.50, SD1212-6 £2.50, PT4555 £4.00, PT4556 £4.50, PT4236A 75p, PT4236B £3.00, PT4236C £4.50, 2N5070 £5.00, 2N3866 75p, BFW16A 75p, RCA40081 50p, 2N2631 50p, 2SC1909 £2.25, 2SC2078 £2.50, 2SC1306 £2.50, 2SC1307 £3.00.

FETS/MOSFETS—
3SK88 super low noise 1.1db = 150 MHz with 25db gain, 16db gain 3.5db n = 900 MHz. ONLY £1.40 each, with data sheet.

3SK60 sim. (3N204) 75p, 3SK51 sim. (40673) 70p, 3SK45 50p, BFR84 sim. (40673) 60p, T558A 40p, ES565 (2N3819) 30p, BF256 38p, 2N4381 "P" chan. 35p.

BIPOLAR-VHF/UHF RF amps—
BF180 30p, BF166 25p, BF152 15p, BF576 (pnp 1200 MHz) 20p, 2N4957 (pnp 1GHz 3 1/2 db NF) 30p, ST2110 (BSX20) 15p.

MOA800 50 volt = 8 amp bridges 70p each.
VHF/UHF SWITCHING DIODES BA243 (VHF) 20p, BA244 (UHF) 25p.

VARIABLE DIODES ITT20 20p, BB105 set of 4 60p, BB141 20p.
PLUGS/SOCKETS—PL259 plugs 50p, S239 soc. 45p, PL259 right angle plugs for UR76, RG58 etc 70p, PL258 couplers for plug + plug 60p, BNC flange sockets 65p, BNC cable mount sockets 40p, PL259 reducers for RG58 etc 15p.

CRYSTAL FILTERS—ITTO24DE 10.7 MHz ±3 KHz £5.00, LQU/445/909B 10.7 MHz ±7 KHz ex-equipment £6.00, BF4133 10.7 MHz SSB 1sb only £4.00.

LOW PROFILE RELAY two pole change over ideal for AE. switching at 145 MHz will handle up to 60 watts RF. 12 volt coil. PC mounting ONLY £2.50.

OXLEY PTFE BARB feedthrough insulators 3mm dia. 6p each, 25 for £1.00.
SOLDER IN FEEDTHROUGH INSULATORS silver plated 4mm dia. 60p per 100.
SOLDER IN FEEDTHROUGH CAPACITORS 1000pf 500v. 3mm dia. 30p per 10.

LEADLESS SMD CERAMICS 1000pf 250v. 5mm dia. 30p per 10.
CERAMIC TRIMMERS 10mm dia. 2.5pf, 4.2pf, 20p each.
FILM TRIMMER 10mm dia. 2-25pf 10p each, 7mm dia. 1-10pf 12p each.
10pf TETTER TRIMMER 8mm dia, or 10mm sq, both types 35p each.
CERAMIC COMPRESSION TRIMMER 14x10mm, 10-80pf 10p each, 10-40pf 10p each.

"YAESU MUSEN" EQUIPMENT let us quote you competitive prices for your requirements.

BI-PAK

CB users. Home base POWER SUPPLY 3A Rugged Powerful British Made

FEATURES ★ Safe 3 Amp operation — 13.8V Fully regulated ★ Electronic short circuit & overload protected ★ Latest technology I.C. design ★ Attractive compact case ★ Competitively priced

SPECIFICATIONS ★ Input voltage — 240 V.a.c. 50Hz ★ Output voltage — 13.8V d.c. ±1% Maximum with mains input variation ±10% load 0-2.5A ★ Output current — 0-3Amp ★ Ripple — less than 2mV up to full load ★ Dimensions — 175lg x 100w x 75h (mm)

OUR PRICE **only £15.00** ORDER NO. 3GA

CB Rigs and Accessories in stock. Send S.A.E. for full listings.

8 Bit MICROPROCESSOR

National INS8080AN 40 Pin DIL N. Channel Silicon GATE MOS TECHNOLOGY As used in Nationals NB800 Micro Computer Family

Instruction Cycle Time 2 µs

Supplied with functional Block Diagram

BRAND NEW — NOT seconds or reclaims

100% perfect ORDER NO. SX8080 Normal Sell price £4.50 each

Our BI-PAK Special Price **only £2.00**

SO HURRY — LIMITED STOCKS



40 Pin IC Socket to fit SX8080 Offer price **30p**

TECASBOTY

The Electronic Components and Semiconductor Bargain of the Year. A host of Electronic components including potentiometers — rotary and slider, presets — horizontal and vertical. Resistors of mixed values 22ohms to 2M2 — 1/8 to 2 Watt. A comprehensive range of capacitors including electrolytic and polyester types plus disc ceramics etcetera. Audio plugs and sockets of various types plus switches, fuses, heatsinks, wire, nuts/bolts, gromets, cable clips and ties, knobs and P.C. Board. Then add that to 100 Semiconductors to include transistors, diodes, SCR's opto's, all of which are current everyday usable devices. In all a Fantastic Parcel. No rubbish all identifiable and valued in current catalogues all well over £25.00. Our Fight Against Inflation

— Beat the Budget
— Down with Depression

Price — **JUST £6.50.**

Fantastic Audio Bargains

15 watts per channel stereo amplifier kit
Consisting of — ORDER NO. STA15
2 x AL60 amplifiers
1 x PA100 pre-amplifier
1 x SPM80 power supply
1 x 2034 transformer
2 x coupling capacitors for 8 ohms 470mfd
50v and necessary wiring diagrams.
— now only
Save over £10 on this kit **£26.00**

COMPLETE AUDIO CHASSIS
STEREO 30 Complete 7 watt per channel Stereo amp board — includes amps, pre-amp, power supply, front panel, knobs and transformer
Almost 1/2 PRICE
£12.50
ORDER NO. ST30

5 watt (RMS) Audio Amp

High Quality audio amplifier Module. Ideal for use in record players, tape recorders, stereo amps and cassette players, etc. Full data and back-up diagrams with each module.

Specification:
● Power Output 5 watts RMS ● Load Impedance 8-16 ohms ● Frequency response 50Hz to 25 KHz—3db ● Sensitivity 70 mv for full output ● Input Impedance 50k ohms ● Size 85 x 64 x 30mm ● Total Harmonic distortion less than 5%

BI-PAK'S give away price **£2.25**
You could not Build one for this price.

MONO PRE-AMPLIFIERS

MM100 suitable for disco mixer. MM100G suitable for guitar pre-amp mixer.
The MM100 and MM100G mono pre-amplifiers are compatible with the AL60, AL80, AL120 and AL250 power amplifiers and their associated power supplies.
MM100 Supply voltage 40-65v inputs. Tape Mag P.U.
Microphone Max output 500mv **£12.45** MM100G Supply voltage 40-65v inputs: 2 Guitars, Microphones Max output 500mv **each £10**

1 Amp SILICON RECTIFIERS

Glass Type similar IN4000 SERIES IN4001-IN4004 50 — 500v — uncodded — you select for VLTS. All perfect devices — NO Duds Min 50v. 50 for £1.00 — worth double ORDER NO. SX76

Silicon General Purpose NPN Transistors TO-18 Case Lock fit leads — coded CV7644 Similar to BC147 — BC107 — ZT89 ALL NEW! Vce 70v IC500mA Hfe 75-250 50 off 100 off 500 off 1000 off
PRICE: **£2.00 £3.80 £17.50 £30.00**

Silicon General Purpose PNP Transistors TO-5 Case Lock fit leads coded CV9507 similar 2N2905A to BFX30 VC 60 IC 600mA Min Hfe 50 ALL NEW!
50 off 100 off 500 off 1000 off
PRICE: **£2.50 £4.00 £19.00 £35.00**

Silicon NPN 'L' Type Transistors

TO-92 Plastic centre collector
Like BC182L — 183L — 184L
VCE 45 VCE30 IC200mA Hfe 100-400

ALL perfect devices — uncodded ORDER AS SX183L
50 off 100 off 500 off 1000 off
£1.50 £2.50 £10.00 £17.00

PNP SILICON TRANSISTORS:

Similar ZTX500 — ZTX21

BI-PAK BARGAINS

"IRRESISTABLE RESISTOR BARGAINS"

Pak No.	Qty*	Description	Price
SX10	400	Mixed "All Type" Resistors	£1
SX11	400	Pre-formed 1/4-watt Carbon Resistors	£1
SX12	200	1/4 watt Carbon Resistors	£1
SX13	200	1/4 watt Carbon Resistors	£1
SX14	150	1/4 watt Resistors 22 ohm-2m2 Mixed	£1
SX15	100	1 and 2 watt Resistors 22 ohm-2m2 Mixed	£1

Paks SX12-15 contain a range of Carbon Film Resistors of assorted values from 22 ohms to 2.2 meg. Save pounds on these resistor paks and have a full range to cover your projects.

*Quantities approximate, count by weight.

"CAPABLE CAPACITOR PAKS"

Pak No.	Qty*	Description	Price
SX16	250	Capacitors Mixed Types	£1
SX17	200	Ceramic Capacitors Miniature Mixed	£1
SX18	100	Mixed Ceramics 1p1-56p1	£1
SX19	100	Mixed Ceramics 68p1-0.5mf	£1
SX20	100	Assorted Polyester/Polystyrene Capacitors	£1
SX21	60	Mixed C280 type capacitors metal foil	£1
SX22	100	Electrolytics, all sorts	£1
SX23	50	Quality Electrolytics 50-1000mf	£1
SX24	20	Tantalum Beads, mixed	£1

*Quantities approximate, count by weight.

AUDIO PLUGS, SOCKETS AND ACCESSORIES

25 pieces of Audio Plugs, Sockets and Connectors to include DIN 180°-240°, Inline 3-6 Pin, Speakers, Phono, Jack, Stereo and Mono, etc. etc. Valued at well over £3 normal. Order No. SX25. Our Price £1.50 per pak. Guaranteed to save you money.

SX26	3 Pcs. of 6 pin 240° DIN Plugs and Chassis Sockets	50p
SX27	1 x Right Angle Stereo Jack Plug 6.3mm plus matching metal chassis mounting socket.	30p
SX28	4 Phono plugs and 2 dual phono connectors.	30p
SX29	1 x 2.5mm Plug to 3.5mm Socket adaptor.	20p
SX30	1 x 3.5mm Plug to 2.5mm Socket adaptor.	20p
SX31	1 x 3.5mm Plug to Phono Socket adaptor.	20p



SX32	1 x Standard Jack Plug to Phono Socket adaptor.	25p
SX33	1 x Toggle Switch SPST Miniature. 125v 10A	40p
SX34	1 x Toggle Switch SPDT Miniature. 125v 10A	40p
SX35	1 x Rocker Switch SPDT Miniature. 240v 5A	40p
SX36	1 x Right Angle Mono Jack Plug	15p
SX37	20 pieces. 1. 2 & 4mm plugs and sockets (Banana). Matching colours and sizes.	£1
SX50	10 Assorted Switches. Toggle, Slide, Rocker, Push Button.	£1
SX77	25 mixed cable clips and ties round grommets & plastic feet. Always sought by the project builder	50p

TRIACS — PLASTIC

4 AMP — 400v — T0202 — TAG 136G.	100 OFF	50 OFF	100 OFF
40p	£3.75	£17.50	£30.00
8 AMP 400v — T0220 — TAG 425			
60p	£5.75	£27.50	£50.00

Everyday Electronics

Teach-in '81
Kit 1 £15.85 (Kits 1 & 2 combined)
Kit 2 £ 8.94 price £23.00

All prices include V.A.T. & postage.

SX40	250 Silicon Diodes—Switching like IN4148 DO-35. All good—uncoded. Worth double our price. 45v 75mA.	£1.25
SX41	250 Silicon Diodes—General Purpose, like OA200/202. BAX13/16. Uncoded. 30-100v 200mA DO-7.	£1.25
SX44	10 5A SCR's T064. 3 x 50v. 3 x 100v. 2 x 200v. 2 x 400v. Super value less than 1/2 price.	£1
SX45	10 5A SCR's T066. 2 x 50v. 2 x 100v. 4 x 200v. 2 x 400v. All coded. Brand new, a giveaway at...	£1



SEMICONDUCTORS FROM AROUND THE WORLD

100

A Collection of Transistors, Diodes, Rectifiers, Bridges, SCR's, Triacs, IC's both Logic and Linear plus Opto's all of which are current everyday usable devices.

100

Guaranteed Value over £10 at Normal Retail Price

yours for only

£4.00

Data etc. in every pak. Order No. SX56



BI-PAK'S OPTO BARGAIN OF THE YEAR!




25

Valued at over £10—Normal Retail—we offer you a pack of 25 Opto devices to include LED's Large and Small in Red, Green, Yellow and Clear. 7 Segment Displays both Common Cathode and Common Anode PLUS bubble type displays—like DL-33. Photo Transistors—similar to OCP71 Photo Detectors—like MEL11-12. This whole pack of 25 devices will cost you just

£4.00

25

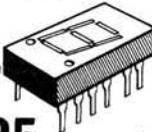AND we guarantee your money back if you are not completely satisfied. FULL data etc included. Order No. SX57.



BARGAINS

SX42	20 small .125 Red LED's	£1
SX43	10 Rectangular Green LED's .2	£1
SX46	30 Assorted Zener Diodes 250mw-2 watt mixed voltages, all coded. New	£1
SX47	4 Black Instrument Knobs—winged with pointer 1/4" Standard screw. Fit size 29 x 20mm.	50p
SX49	20 Assorted Slider Knobs. Black/Chrome, etc.	£1
SK80	12 Neons and Filament Lamps. Low voltage and mains — various types and colours — some panel mounting	£1

MORE BARGAINS!

SX51	60 metres PVC covered Hook-up wire single and stranded. Mixed colours.	£1
SX58	25 Assorted TTL Gates 7400 Series. 7401-7460.	£1
SX59	10 Assorted Flip Flops and MSI TTL	£1
SX60	20 Assorted Slider Potentiometers	£1
SX61	25 Assorted Potentiometers, Rotary, Dual, etc.	£1
SX62	40 Assorted Pre-Sets Hor./Vert. etc.	£1
SX79	10 Reed Switches — glass type 3 Micro Switches — with lever	£1

STILL MORE!

SLIDER POTENTIOMETERS

SX63	5 x 470 ohms Lin	SX67	5 x 47k Lin
SX64	5 x 1k Lin	SX68	5 x 47k Log
SX65	5 x 22k Lin	SX69	5 x 100k Lin
SX66	5 x 22k Log	SX70	5 x 1 meg Lin

All at 50p per pack.

SX71 50 BC108 "Fallouts". Manufacturers out of spec on volt/gain. You test. £1

SX72 A mixed bundle of Copper clad Board, Fibre glass and paper. Single and double sided. A fantastic bargain. £1

SX78 Genuine MULLARD OC71 Germanium PNP Transistors. Brand New 10 for £1

5 watt (RMS) Audio Amp

High Quality audio amplifier Module. Ideal for use in record players, tape recorders, stereo amps and cassette players, etc. Full data and back-up diagrams with each module.

Specification
● Power Output 5 watts RMS ● Load Impedance 8-16 ohms ● Frequency response 50Hz to 25 KHz—3db ● Sensitivity 70 mv for full output ● Input Impedance 50k ohms ● Size 85 x 64 x 30mm ● Total Harmonic distortion less than 5%

BI-PAK'S give away price

£2.25

You could not Build one for this price.



BI-PAK'S COMPLETELY NEW CATALOGUE

Completely re-designed. Full of the type of components you require, plus some very interesting ones you will soon be using and of course, the largest range of semiconductors for the Amateur and Professional who could hope to find.

There are no wasted pages of useless information so often included in Catalogues published nowadays. Just solid facts i.e. price, description and individual features of what we have available. But remember, Bi-Pak's policy has always been to sell quality components at competitive prices and THAT WE STILL DO.

BI-PAK'S COMPLETELY NEW CATALOGUE is now available to you. You will be amazed how much you can save when you shop for Electronic Components with a Bi-Pak Catalogue. Have one by you all the time—it pays to buy BI-PAK.

To receive your copy send **75p** plus 25p p.p.

£1 FREE PAK

Get a £1 FREE PACK. Orders over £10 excluding VAT. Choose £1 Pack free (or 2 x 50p) add it to your order and save even more money.

This offer only applies to this advertisement

Guarantee

Satisfaction or your money back has always been BI-PAK'S GUARANTEE and it still is. All these Sale items are in stock in quantity and we will despatch the same day as your order is received.

IC SOCKETS

The lowest price ever.

Pin	10 off	50 off	100 off
8	75p	£3.00	£5
14	80p	£3.25	£5.50
16	80p	£3.25	£5.50



VOLTAGE REGULATORS T0220

Positive +	Negative +	(please state voltage required)
7805 — 50p	7905 — 55p	
7812 — 50p	7912 — 55p	
7815 — 50p	7915 — 55p	
7824 — 50p	7924 — 55p	

Other types: LM340K — 5 volt — 18 volt — 24 volt.
T03 — 40p. UA723 — 14 pin DIL — 40p



SX52 6 Black Heatsink will fit T0-3 and T0-220. Ready drilled. Half price value. £1

SX53 1 Power Finned Heatsink. This heatsink gives the greatest possible heat dissipation in the smallest space owing to its unique staggered fin design, pre drilled. T0-3 Size 45mm square x 20mm high 40p

SX54 T0-66 size. 35mm x 30mm x 12mm 35p

SX55 1 Heat Efficiency Power Finned Heatsink. 90mm x 80mm x 35mm High. Drilled to take up to 4 x T0-3 devices. £1.50 each



SX38 100 Silicon NPN Transistors—all perfect. Coded mixed types with data and eqvt sheet. No rejects. Real value. £2.50

SX39 100 Silicon PNP Transistors—all perfect. Coded mixed types with data and eqvt sheet. No rejects. Fantastic value. £2.50

2K3055 The best known Power Transistors in the World — 2N3055 NPN 115w. Our BI-PAK Special Offer Price: 10 off £3.50 50 off £16.00 100 off £30.00

BD312 COMPLIMENTARY PNP POWER TRANSISTORS: TO 2N3055. Equivalent MJ2955 — BD312 — T03. SPECIAL PRICE £0.70 each 10 off £6.50



BI-PAK

Send your orders to Dept PW2, BI-PAK PO BOX 6 WARE HERTS SHOP AT 3 BALDOCK ST. WARE HERTS. TERMS: CASH WITH ORDER. SAME DAY DESPATCH. ACCESS. BARCLAYCARD ALSO ACCEPTED. TEL (09201) 3182. GIRD 388 7006. ADD 15% VAT AND 50p PER ORDER POSTAGE AND PACKING



Use your credit card. Ring us on Ware 3182 NOW and get your order even faster. Goods normally sent 2nd Class Mail. Remember you must add VAT at 15% to your order. Total. Postage add 50p per Total order.

HOW TO SUCCEED IN THE ELECTRONICS BUSINESS:

Available at your
newsagent or
direct for
**60p p&p
inc**

INVEST 60p AND MAKE £2.40 net profit

Buy Ambit's new concise component catalogue and get £1 vouchers. Use them for a £1 discount per £10 spent. But even without this, you will still find WR&E offers the low prices, fast service and technical support facility second to none.

Here are some examples from the current issue:



Z80 SERIES	I.C. SOCKETS	DISCRETES	BC556	12p	2SK168	35p
Z80A 4.99	A range of high quality, low cost, low profile DIL sockets ideally suited for both the OEM and hobbyist. All types feature double sided phosphor bronze contacts, tin-plated for low contact resistance.	BC237 8p	BC550 12p	J310 69p		
Z80ADRT 7.50	8 x 0.3" 12p	BC238 8p	BC560 12p	J176 65p		
Z80APIO 4.10	14 x 0.3" 13p	ZTX238 9p	BC639 22p	40823 65p		
Z80ASIO/1 14.00	16 x 0.3" 13p	BC239 8p	BC640 23p	3SK45 49p		
Z80ASIO/2 14.00	22 x 0.3" 20p	BC307 8p	2SC1775A 22p	3SK51 54p		
Z80ASIO/9 14.00	24 x 0.4" 20p	BC308 8p	2SA872A 18p	3SK60 58p		
Z80CTC 4.00	24 x 0.6" 22p	BC309 8p	2SD666A 30p	3SK88 99p		
Z80ACTC 4.50	18 x 0.3" 18p	BC413 10p	2SB646A 30p	MEM680 75p		
Z8001 65.00	28 x 0.6" 25p	BC414 11p	2SD668A 30p	BF960 99p		
	20 x 0.3" 19p	BC415 10p	2SB648A 40p	BF961 70p		
	40 x 0.6" 35p	BC416 11p	BF256 38p	BF963 99p		
	20 x 0.4" 19p	BC546 12p	2SK55 28p			
PROM						
2708 2.00						
2716 3.55						
2532 8.50						
2732 8.50						
RAM						
2102 1.70	VOLTAGE REGULATORS	XTALS				
2112 3.40	78XX1A TO-220 pos 0.58	1MHz 3.00				
2114/2 1.49	78XX1A TO-220 neg 0.60	3.2768MHz 2.00				
4027 5.78	78G 1A TO-220 adj pos 1.10	4MHz 1.70				
4116/2 1.59	78G 1A TO-3 adj pos 3.95	4.194MHz 1.70				
4116/3 1.49	78H5A TO-3 5v pos 4.25	4.43MHz 1.25				
4864P 12.50	78H5A TO-3 12v pos 5.45	5MHz 2.00				
6116P-3 12.50	78HG5A TO-3 adj pos 7.45	6.5536MHz 2.00				
6116P-4 11.25	79HG5A TO-3 adj neg 7.45	7MHz 2.00				
8264 12.50	LM317.5A adj pos 1.30	8MHz 2.00				
	LM337.5A adj neg 1.75	9MHz 2.00				
	78S401.5A adj pos sw reg 1.20	10MHz 2.00				
		11MHz 2.00				


Prices shown exclude VAT. Postage 50p per order (UK). ACCESS/ BARCLAYCARD may be used with written or telephone orders - official MA details on application, and a special prize for those who read our ads carefully - a free 4 or 8MHz crystal filter with every CPU IC you buy - just clip out the paragraph and attach it to your order. E&OE.

AMBIT international

TELEPHONE (STD 0277) 230909 TELEX 995194 AMBIT G POSTCODE CM14 4SG
200 North Service Road, Brentwood, Essex

MICROSCOPE

Illuminated pocket microscope — zooms in

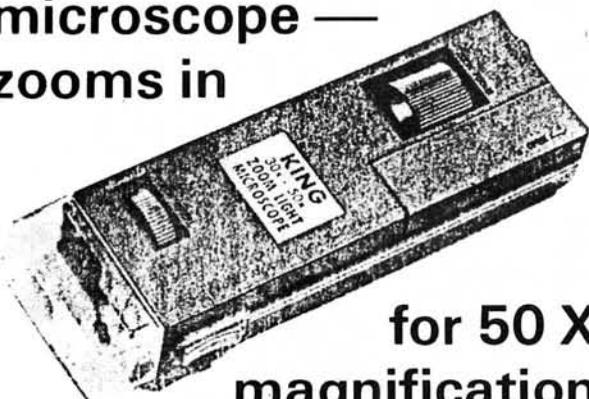

for 50 X magnification

Measuring only 130 x 40 x 18 mm, this Intel illuminated pocket microscope has a normal magnification of 30 X which can be increased to 50 X by using the zoom facility. Focus control and illumination are built-in so that the instrument can typically be used in the close inspection of specimens, samples and tissues by medical students, doctors, technicians and medical laboratory scientists. It uses longlife batteries and comes in a plastic case.

Price: £12.99 incl. case, V.A.T. and post/packing.

For immediate despatch send cheque with order to:



INTEL ELECTRONIC COMPONENTS LTD.
30/50 Ossory Road, London SE1 5AN. Tel: 237 0404

WIRELESS BURGLAR ALARMS

D.I.Y. Perimeter Protection Kit

This D.I.Y. kit consists of 3 individual transmitters that will detect windows and doors opening. They can also be used as 'Panic' buttons. When activated, these transmitters send a radio signal to the Central Console which is also provided. This is a multi-function unit that has facilities for delayed action, self-testing and secret number entry via a touch sensitive keypad. Once activated, the alarm sounds a loud siren which is also provided. The doors and windows are not connected to the Central Console by anything other than radio waves - no wiring is needed.

THE COMPLETE KIT COSTS ONLY £195!!

If you want to experiment with the separate units, or if you need more coverage than this kit can provide, we can supply individual transmitters, receivers, auto-diallers that will call the police when an alarm is activated, CCTV systems etc. etc. We can either supply **all** the items that you will need to install your own Wireless Burglar alarm or we can install a system for you. Please write or telephone for further details.



**REGD. OFFICE,
PARK CHAMBERS,
7 INVERNESS PLACE,
LONDON, W2 4RG, ENGLAND.
(Tele 01-229 5407)**

(Home Office approved equipment available)

An entire range of low-cost high-performance instruments



sabtronics 

'Making Performance Affordable'

*2010A 3½-Digit L.E.D. Bench DMM	5020A 1Hz-200KHz Function Generator
*2015A 3½-Digit L.C.D. Bench DMM	*8110A 100MHz 8-Digit Frequency Meter
2020 3½-Digit L.E.D. Bench DMM with Microcomputer Interface	*8610A 600MHz 8-Digit Frequency Meter
2033 3½-Digit L.C.D. Hand DMM	*8610B 600MHz 9-Digit Frequency Meter
*2035A 3½-Digit L.C.D. Hand DMM	8000B 1GHz 9-Digit Frequency Meter
*2037A 3½-Digit L.C.D. Hand DMM with Temp.	8700 10MHz Universal Frequency Counter/Timer
LP-1 10MHz Logic Probe	PSC-65 600MHz Prescaler
	9005 5MHz Single Trace Oscilloscope

* Also available in kit form.

Test our low priced test equipment. It measures up to the best. Compare our specs and our prices - no-one can beat our price/performance ratio.

Full colour illustrated brochure and price list from:

BLACK STAR LTD.,
9a Crown Street, St. Ives,
Cams. PE17 4EB
Tel: (0480) 62440. Telex 32339



Right first time.



Rechargeable Light



Portable VOM

If you've never built a kit before, Heathkit have some very pleasant surprises for you. Their kits are easy to build. Simple, but detailed instructions take you through every stage. Everything is included. Even the solder you need is there.

Follow the steps and you'll end up with a hand-crafted, well designed piece of equipment. Much better than shop bought, mass-produced. Because you built it yourself.



Digital Clock

There's a great range of kits to start you off. From a buzzer alarm to a digital electronic clock, or a portable rechargeable fluorescent light to a portable VOM.

With all this going for you, you can count yourself very lucky you started off with Heathkit. Because all first time kit builders will get a free soldering iron and 10% discount off ten selected kits.



Buzzer Alarm

To: Heath Electronics (UK) Limited,
Dept (PW2). Bristol Road,
Gloucester GL2 6EE.

To start me off, please send me a copy of the Heathkit catalogue. I enclose 28p in stamps.

Name _____


Address _____

PW2 

You build on our experience

HEATHKIT

HEATH
ZENITH

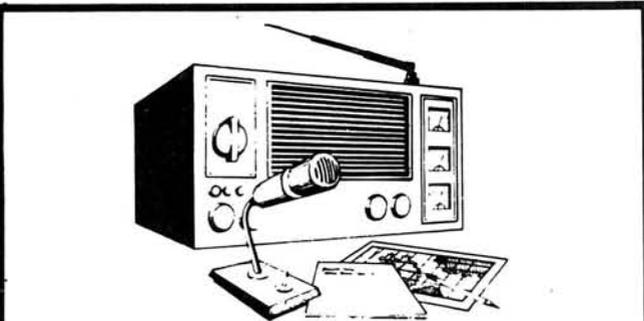

BECOME A RADIO AMATEUR

Learn how to become a radio amateur in contact with the whole world. We give skilled preparation for the G.P.O. licence.

No previous knowledge required.

Brochure without obligation to :-

British National Radio & Electronic School
READING, BERKS. RG1 1BR

Name

Address

PW/2/815

BLOCK CAPS PLEASE

PM COMPONENTS LTD. VALVE & COMPONENTS SPECIALISTS

SELECTRON HOUSE, WROTHAM ROAD, MEOPHAM GREEN, MEOPHAM, KENT

PHONE 0474 813225. TELEX 965966 WEST ST G



NEW BRANDED VALVES			INTEGRATED CIRCUITS			SEMICONDUCTORS			TIP31C		
AZ087 11.50	ECF86 1.50	EZ80 0.75	PCL85 0.90	6A87 0.60	7B7 1.40	AC127 0.22	BC170B 0.10	BF197 0.11	TIP31C 0.42		
A2134 9.00	ECF812 1.20	EZ81 0.56	PCL86 0.80	6A88 0.66	7S7 3.00	AC128 0.20	BC171 0.08	BF198 0.10	TIP32C 0.42		
A2293 7.20	ECF83 2.50	EZ90 0.96	PCL805 1.60	6A7 1.00	11E2 16.50	AC141K 0.34	BC172 0.09	BF200 0.30	TIP41C 0.45		
A2900 10.90	ECF85 1.50	G10/18 8.00	PL200 1.13	6A6F4 1.20	12AD6 0.80	AC176 0.22	BC173B 0.10	BF258 0.25	TIP42C 0.47		
DAF91 0.45	ECF84 1.00	G55/1K 8.00	PL36 1.05	6A6H 1.00	12AE6 1.85	AC176K 0.31	BC182 0.09	BF259 0.26	TIP2955 0.84		
DAF96 0.65	ECF84 1.00	G120/18 8.00	PL81A 0.75	6A6J 1.00	12AG8 1.50	AC187 0.25	BC187 0.12	BF259 0.26	TIP3055 0.66		
DF91 0.45	ECF84 1.00	GS10C 12.00	PL84 0.85	6A6K 2.00	12AH8 5.50	AC187K 0.28	BC184LA 0.05	BF259 0.26	TIS91 0.20		
DF92 0.60	ECF84 1.00	GUX50 12.50	PL500 1.12	6A6L 0.52	12AT6 0.59	AC188 0.22	BC212 0.09	BF259 0.26	TIP3055 0.52		
DF96 0.65	ECF84 1.00	GS10C 12.00	PL508 1.75	6A6M 2.50	12AT7 0.55	AC188K 0.22	BC212L 0.09	BF259 0.26	TIP3055 0.52		
DK91 0.90	ECF84 1.00	GZ501 1.20	PL509 2.95	6A6N 1.30	12AT7WA 2.50	AD149 0.70	BC213 0.09	BF259 0.26	TIP3055 0.52		
DK92 1.20	ECF84 1.00	GZ501 1.20	PL519 3.15	6A6P 2.00	12AU6 0.60	AD161 1.04	BC213L 0.09	BF259 0.26	TIP3055 0.52		
DK96 1.00	ECF84 1.00	GZ501 1.20	PL802 2.75	6A6Q 0.82	12AU7 0.55	AD162 0.39	BC237 0.09	BF259 0.26	TIP3055 0.52		
DL92 0.60	ECF84 1.00	GZ501 1.20	PL802 2.75	6A6Q 0.82	12AV6 0.80	AF124 0.34	BC238 0.09	BF259 0.26	TIP3055 0.52		
DL94 1.20	ECF84 1.00	GZ501 1.20	PL802 2.75	6A6Q 0.82	12AX7 0.75	AF125 0.32	BC307 0.09	BF259 0.26	TIP3055 0.52		
DL96 1.00	ECF84 1.00	GZ501 1.20	PL802 2.75	6A6Q 0.82	12AX7WA 2.50	AF126 0.32	BC327 0.10	BF259 0.26	TIP3055 0.52		
DLS10 9.00	ECF84 1.00	GZ501 1.20	PL802 2.75	6A6Q 0.82	12AY7 4.00	AF127 0.32	BC337 0.10	BF259 0.26	TIP3055 0.52		
DLS16 10.00	ECF84 1.00	GZ501 1.20	PL802 2.75	6A6Q 0.82	12AZ7A 1.50	AF139 0.42	BC461 0.30	BF259 0.26	TIP3055 0.52		
DY86/87 0.55	ECF84 1.00	GZ501 1.20	PL802 2.75	6A6Q 0.82	12BA4 1.60	AF239 0.42	BC478 0.20	BF259 0.26	TIP3055 0.52		
DY802 0.60	ECF84 1.00	GZ501 1.20	PL802 2.75	6A6Q 0.82	12BA6 0.75	AF239 0.42	BC547 0.10	BF259 0.26	TIP3055 0.52		
E55L 14.00	ECF84 1.00	GZ501 1.20	PL802 2.75	6A6Q 0.82	12BA6 0.75	AF239 0.42	BC548 0.10	BF259 0.26	TIP3055 0.52		
E80CC 4.75	ECF84 1.00	GZ501 1.20	PL802 2.75	6A6Q 0.82	12BA6 0.75	AF239 0.42	BC548 0.10	BF259 0.26	TIP3055 0.52		
E80F 6.25	ECF84 1.00	GZ501 1.20	PL802 2.75	6A6Q 0.82	12BA6 0.75	AF239 0.42	BC548 0.10	BF259 0.26	TIP3055 0.52		
E81CC 2.50	ECF84 1.00	GZ501 1.20	PL802 2.75	6A6Q 0.82	12BA6 0.75	AF239 0.42	BC548 0.10	BF259 0.26	TIP3055 0.52		
E82CC 2.50	ECF84 1.00	GZ501 1.20	PL802 2.75	6A6Q 0.82	12BA6 0.75	AF239 0.42	BC548 0.10	BF259 0.26	TIP3055 0.52		
E83CC 2.50	ECF84 1.00	GZ501 1.20	PL802 2.75	6A6Q 0.82	12BA6 0.75	AF239 0.42	BC548 0.10	BF259 0.26	TIP3055 0.52		
E83F 2.50	ECF84 1.00	GZ501 1.20	PL802 2.75	6A6Q 0.82	12BA6 0.75	AF239 0.42	BC548 0.10	BF259 0.26	TIP3055 0.52		
E86C 6.00	ECF84 1.00	GZ501 1.20	PL802 2.75	6A6Q 0.82	12BA6 0.75	AF239 0.42	BC548 0.10	BF259 0.26	TIP3055 0.52		
E88C 6.00	ECF84 1.00	GZ501 1.20	PL802 2.75	6A6Q 0.82	12BA6 0.75	AF239 0.42	BC548 0.10	BF259 0.26	TIP3055 0.52		
E88CC 2.60	ECF84 1.00	GZ501 1.20	PL802 2.75	6A6Q 0.82	12BA6 0.75	AF239 0.42	BC548 0.10	BF259 0.26	TIP3055 0.52		
E130L 13.00	ECF84 1.00	GZ501 1.20	PL802 2.75	6A6Q 0.82	12BA6 0.75	AF239 0.42	BC548 0.10	BF259 0.26	TIP3055 0.52		
E180F 5.25	ECF84 1.00	GZ501 1.20	PL802 2.75	6A6Q 0.82	12BA6 0.75	AF239 0.42	BC548 0.10	BF259 0.26	TIP3055 0.52		
E182CC 4.50	ECF84 1.00	GZ501 1.20	PL802 2.75	6A6Q 0.82	12BA6 0.75	AF239 0.42	BC548 0.10	BF259 0.26	TIP3055 0.52		
E810F 12.50	ECF84 1.00	GZ501 1.20	PL802 2.75	6A6Q 0.82	12BA6 0.75	AF239 0.42	BC548 0.10	BF259 0.26	TIP3055 0.52		
E8AC80 0.56	ECF84 1.00	GZ501 1.20	PL802 2.75	6A6Q 0.82	12BA6 0.75	AF239 0.42	BC548 0.10	BF259 0.26	TIP3055 0.52		
EAF42 1.40	ECF84 1.00	GZ501 1.20	PL802 2.75	6A6Q 0.82	12BA6 0.75	AF239 0.42	BC548 0.10	BF259 0.26	TIP3055 0.52		
E891 1.42	ECF84 1.00	GZ501 1.20	PL802 2.75	6A6Q 0.82	12BA6 0.75	AF239 0.42	BC548 0.10	BF259 0.26	TIP3055 0.52		
E8C81 0.85	ECF84 1.00	GZ501 1.20	PL802 2.75	6A6Q 0.82	12BA6 0.75	AF239 0.42	BC548 0.10	BF259 0.26	TIP3055 0.52		
E8C83 0.85	ECF84 1.00	GZ501 1.20	PL802 2.75	6A6Q 0.82	12BA6 0.75	AF239 0.42	BC548 0.10	BF259 0.26	TIP3055 0.52		
E8C89 0.85	ECF84 1.00	GZ501 1.20	PL802 2.75	6A6Q 0.82	12BA6 0.75	AF239 0.42	BC548 0.10	BF259 0.26	TIP3055 0.52		
EC90 0.60	ECF84 1.00	GZ501 1.20	PL802 2.75	6A6Q 0.82	12BA6 0.75	AF239 0.42	BC548 0.10	BF259 0.26	TIP3055 0.52		
EC81 0.55	ECF84 1.00	GZ501 1.20	PL802 2.75	6A6Q 0.82	12BA6 0.75	AF239 0.42	BC548 0.10	BF259 0.26	TIP3055 0.52		
EC82 0.55	ECF84 1.00	GZ501 1.20	PL802 2.75	6A6Q 0.82	12BA6 0.75	AF239 0.42	BC548 0.10	BF259 0.26	TIP3055 0.52		
EC82 Mullard	ECF84 1.00	GZ501 1.20	PL802 2.75	6A6Q 0.82	12BA6 0.75	AF239 0.42	BC548 0.10	BF259 0.26	TIP3055 0.52		
EC83 Mullard	ECF84 1.00	GZ501 1.20	PL802 2.75	6A6Q 0.82	12BA6 0.75	AF239 0.42	BC548 0.10	BF259 0.26	TIP3055 0.52		
EC83 Mullard	ECF84 1.00	GZ501 1.20	PL802 2.75	6A6Q 0.82	12BA6 0.75	AF239 0.42	BC548 0.10	BF259 0.26	TIP3055 0.52		
EC85 0.80	ECF84 1.00	GZ501 1.20	PL802 2.75	6A6Q 0.82	12BA6 0.75	AF239 0.42	BC548 0.10	BF259 0.26	TIP3055 0.52		
EC88 0.85	ECF84 1.00	GZ501 1.20	PL802 2.75	6A6Q 0.82	12BA6 0.75	AF239 0.42	BC548 0.10	BF259 0.26	TIP3055 0.52		
EC91 0.85	ECF84 1.00	GZ501 1.20	PL802 2.75	6A6Q 0.82	12BA6 0.75	AF239 0.42	BC548 0.10	BF259 0.26	TIP3055 0.52		
EC804 0.40	ECF84 1.00	GZ501 1.20	PL802 2.75	6A6Q 0.82	12BA6 0.75	AF239 0.42	BC548 0.10	BF259 0.26	TIP3055 0.52		
EC807 1.30	ECF84 1.00	GZ501 1.20	PL802 2.75	6A6Q 0.82	12BA6 0.75	AF239 0.42	BC548 0.10	BF259 0.26	TIP3055 0.52		
EC80 0.85	ECF84 1.00	GZ501 1.20	PL802 2.75	6A6Q 0.82	12BA6 0.75	AF239 0.42	BC548 0.10	BF259 0.26	TIP3055 0.52		
EC82 0.60	ECF84 1.00	GZ501 1.20	PL802 2.75	6A6Q 0.82	12BA6 0.75	AF239 0.42	BC548 0.10	BF259 0.26	TIP3055 0.52		

Many other items available

Please phone send list for quote

CALLERS WELCOME

★ Entrance on A227 50yds South of Meopham Green by Little Blue House

★ Hours Mon.-Fri. 9.30-5.30 Saturday 9.30-12.00

P. & P. 50p. Please add V.A.T. at 15%

★ 24-HOUR ANSAPHONE SERVICE ★

T. POWELL

IONISER KIT

This negative ion generator gives you the power to saturate your home or office with millions of refreshing ions. Without fans or moving parts it puts out a pleasant breeze. A pure flow of ions pours out like water from a fountain, filling your room. The result? Your air feels fresh, pure, crisp and wonderfully refreshing.

All parts, PCB and full instructions £12.50
A suitable case, including front panel, neon switch etc. £6.50

P.W. KITS

PW NIMBUS - Complete kit still available £80.00 (without xtals)
Add-on base unit £38.00
Wideband RF Pre-Amp £7.50
AF Speech Processor £18.00
Beginners 2 meter Converter £15.00
Model Railway Controller £21.50
VHF/UHF Repeater Station Timer (Main board only) £22.50
Active receiving Antenna £9.00
Beginners Short Wave Receiver (Components only) £13.50
Audio Field Strength Meter £10.00
Automatic Cut Out Power Supply P.O.A.
Supplementary Car Audio Amplifier P.O.A.


SPECIAL OFFERS

FUSEHOLDERS (20mm chassis mounting) 10 for 30p
..... 100 for £2.50
..... 1000 for £20.00
TOSHIBA TA 7205 £1.50
PHILIPS SCOPE TUBES - 5" CV 2191/DG 132 £12.65
MULLARD COMPUTER ELECTROLYTICS 21,000/40V £4.50
All prices include VAT and postage & packing.
Please allow 28 days for delivery.

Callers: Please ring to check availability of kits before calling.

PLEASE NOTE OUR NEW ADDRESS:
Advance Works, 44 Wallace Rd., London N1.

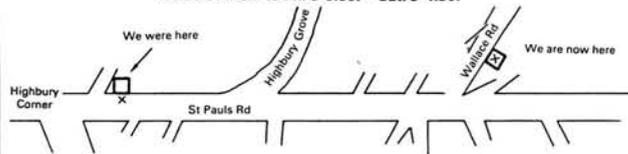Our 'Phone number is still: 226 1489
HOURS: Mon. to Fri. 9-5.30. Sat. 9-4.30.



RADIATION DETECTORS

BE PREPARED

VIEW THRU LENS



- THIS DOSIMETER WILL AUTOMATICALLY DETECT GAMMA AND X-RAYS
- UNIT IS SIZE OF FOUNTAIN PEN & CLIPS ONTO TOP POCKET
- PRECISION INSTRUMENT METAL CASED WEIGHT 20Z
- MANUFACTURERS CURRENT PRICE OF A SIMILAR MODEL DV8R £25 EACH

British design & manufacture
Tested & fully guaranteed
Ex-stock delivery

£6.95 inc VAT
Post & Pack 60p

Ideal for the experimenter
COMPLETE WITH DATA



404 EDGWARE ROAD LONDON W2 1ED

HIGH GAIN AERIAL BOOSTERS

B45 H/G UHF Television - Tunable over the complete UHF band. Gain above 20dB, noise 2.8dB.
B14 - Band 3 VHF Television - Tunable over the complete Band 3 (Channels (E) 5 to 13). Also covers Aircraft & 2 meter Amateur Bands. Gain above 28dB. Noise 2.8dB.
PRICE each £8.70.

Signal Injectors with (pre-set) variable AF, which emits RF harmonics into the UHF band. Protected up to 300 volts DC. Complete with leads £5.70 each.

All Prices include VAT at 15%. P & P per Order 30p. S.A.E. for Leaflets. Access Cards.

ELECTRONIC MAILORDER LTD,
62 Bridge St, Ramsbottom, via Bury, Lancs. BLO 9AGW.
Tel. Rams (070 682) 3036. Goods by return of post.

AERIAL AMPLIFIERS

Aerial amplifiers can produce remarkable improvement on the picture and sound in fringe or difficult areas.

B45 - For Mono or Colour this is tunable over complete UHF television band.

B11 - For stereo or standard VHF/FM radio.

B12 - for VHF television band 1 & 3. All amplifiers are complete and ready to use Battery type PP3 or 8V to 18V DC next to the set type fitting.

PRICES £6.70 each.

ELECTROVALUE

Popular components from "CATALOGUE 82", all prime stock, no seconds or fall-outs. Buy in quantity for even better value.

COMPONENT PACKS

CP1 100 ceramic capacitors from 1.8p to .1u. The selection is determined by the popularity of different values. **£4-20.**

Resistor Decade Pack 1/3W, 5% tolerance; each pack 100 items, selection determined by relative popularity of each value: Price £1.50 each pack.

RD: 1R0-8RT; **RD2:** 10R-82R; **RD3:** 100R-820R; **RD4:** 1K-8K2; **RD5:** 10K-82K; **RD6:** 100K-82K; **RD7:** 1M-10-10M. **£1-50 each Decade Pack.**

SEMICONDUCTOR PACKS

LD30A red LED's (2.9mm): 25 for **£1-57.**

LD41A red LED's (5mm): 25 for **£1-57.**

1N4148 diodes: 25 for **68p.**

1N4007 (1000V, 1A) diodes: 25 for **£1-30.**

1N5402 (200V, 3A) diodes: 25 for **£2-80.**

BC107/BC109: 25 for **£2-97.**

BC182/182L/183/183L/184/184L: 25 for **£2-00.**

BC212/212L/213/214/214L: 25 for **£2-00.**

Other popular items: unit prices.

VOLTAGE REGULATORS	BD139	30p
	BD140	32p
7805/12/15/24:	TIP41A	45p
7905/12/15/24:	TIP42A	45p
78L05/12/15/24:	TIP2955	64p
79L05/12/15/24:	TIP3055	64p
	2N3819	22p
	2N3055	70p

SPECIAL OFFER

25 x 4116 (300nS) **£20-00 only.**

Please mention this journal when ordering or writing.

ELECTROVALUE LTD. DEPT. PW2, 28 St. Jude's Road, Englefield Green, Egham, Surrey TW20 0HB.

Phone Egham 33603 (STD 0784, London 87), Telex 264475

Northern Branch (Personal Shoppers only) 580 Burnage Lane, Burnage, Manchester M19 1NA, Phone (061) 432 4945.

CATALOGUE 82

ESSENTIAL READING FOR THE Electronics Enthusiast Computing Freak Equipment Manufacturer

PACKED WITH INFORMATION ON MORE THAN 6,000 STOCK ITEMS:
Active and Passive Components Boxes, Cases, Computer Housings, Knobs, Pots, Switches, Relays, Everything from A's and C's to Computing Systems.

ALL ITEMS BRAND NEW AND GUARANTEED SPEEDY MAIL ORDER SERVICE

No P/P charges on U.K. C.W.D. orders over £5.75 inc. V.A.T. (add 40p handling charge if under)

When ordering please add 15% V.A.T. to total value of all orders. Shop Hours: 9-5.30. Saturdays: 9-1 pm.

To obtain your copy of **CATALOGUE 82** Send 70p, post free includes 70p voucher to be reclaimed against orders valued £10.00 or over.

REGULATED POWER SUPPLY
With short circuit protection, Nominal 13.8 volts at 5 amps continuous or up to 8 amp intermittent, made for use with CB rigs, but this power supply is equally suitable for any other 12v equipment. Nicely made in ventilated metal case with switch and pilot light on front and terminals at back. **£14.95.** + Post £1.50.

HOME BASE POWER SUPPLY
13.8v 20amp - built and regularly used by G3VCJ, all regular features including protection trip, 500 watt transformer and all parts including case. **£39.50,** carriage £5.00.

TRANSMITTER SURVEILLANCE*
Tiny, easily hidden but which will enable conversation to be picked up with FM radio. Can be made in a matchbox - all electronic parts and circuit. **£2.30.**

RADIO MIKE*
Ideal for discos and garden parties, allows complete freedom of movement. Play through FM radio/tuner amp. **£6.90** comp. kit.

6 WAVEBAND SHORTWAVE RADIO KIT
Bandspread covering 13.5 to 32 metres. Complete kit includes case. Nothing else to buy if you have an amplifier to connect it to or a pair of high res. headphones. Price **£11.95.**

MW & 2 SHORT -- CRYSTAL RADIO
All the parts to make up the beginner's model. Price **£2.30.** Crystal earpiece 65p. High resistance h/phones (gives best results) **£3.75.** Kit includes front but not case.

INTERRUPTED BEAM
This kit enables you to make a switch that will trigger when a steady beam of infra-red or ordinary light is broken. Main components: relay, photo-transistor, resistors, caps, etc. Circuit diagram but no case. Price **£2.30.**

CAR STARTER AND CHARGER KIT
You can start car immediately or bring your battery up to full charge in a couple of hours. The kit comprises: 250w mains transformer, bridge rectifiers, start/charge switch and full instructions. Price **£11.50 + £2.50** post.

GPO HIGH GAIN AMP/SIGNAL TRACER
In case measuring only 5 1/4" x 3 3/4" x 1 1/4" is an extremely high gain (70db) solid state amp designed for use as a signal tracer on GPO cables, etc. With a radio it functions very well as a signal tracer. By connecting a simple coil to the input sockets a useful mains cable tracer can be made. Many other uses including general purpose amp, cueing amp, etc. An absolute bargain at only **£1.85.** suitable 80 ohm e/p 69.

FREE! OUR CURRENT BARGAIN LIST WILL BE ENCLOSED WITH ALL ORDERS MULLARD UNILEX

A mains operated 4 + 4 stereo system. Rated one of the finest performers in the stereo field this would make a wonderful gift for almost anyone. In easy to assemble modular form this should sell at about **£30** but due to a special bulk buy and as an incentive to buy, we offer the system complete at only **£16.75** inc. VAT + post. **PLUS FREE GIFT** - buy this month and you will receive a pair of Goodmans elliptical 8" x 5" speakers to match this amplifier.

TIME SWITCH BARGAIN
Large clear mains frequency controlled clock, which will always show you the correct time + start and stop switches with the dials. Comes complete with knobs. **£2.50.**

8 POWERFUL BATTERY MOTORS
For models, Meccanos, drills, remote control planes, boats, etc. **£2.50.**

WATERPROOF HEATING WIRE
60 ohms per yard, this is a heating element wound on a fibre-glass coil and then covered with PVC, dozens of uses - around water pipes, under grow boxes in gloves and socks. **23p/metre.**


MORSE TRAINER KIT
Consists of morse tone module, morse key, battery connector, case & instructions. **£2.99.**

AERIAL DIRECTION INDICATOR
Kit includes 16 read switches, magnet, 16 LED's and chart which has the 16 compass points and lights up where aerial is pointing. **£5.90.**

AERIAL ROTATOR
Comprises mains motor with pulley and vee belt, electro-mechanical aerial base unit and control switch enables you to set your aerial mast in any direction. **£19.50,** carriage **£5.**

RADIO STETHOSCOPE
Easy to find fault - start at the aerial and work towards the speaker - when signal stops you have found the fault. **Complete kit £4.95.**

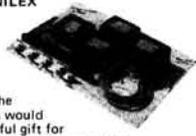Cash, P.O. or cheque with order. Orders under £10.00, add 60p. Access & B/card orders by phone to Haywards Heath (0444) 54563. Delivery by return.



J. BULL (Electrical) Ltd. Established 30 YEARS
(Dept PW), 34 - 36 AMERICA LANE, HAYWARDS HEATH, SUSSEX RH16 3QU.

It's easy to complain about advertisements.

The Advertising Standards Authority. ✓
If an advertisement is wrong, we're here to put it right.
A.S.A. Ltd., Brook House, Torrington Place, London WC1E 7HN.

U.H.F. RECEIVER TYPE R278 designed by Collins Radio used as ground station Rx provides up to 1750 channels spaced in 100Kc steps in freq. range 225 to 400 Mc/s any 10 of these can be selected from front panel plus one service channel, unit is triple conversion with some 38 crystals, no ext crystals are required, all controls etc are on front panel for use on 230v 50c, AF O/P 600 ohm 2 watts. Also provision for remote chan selection, 19" rack mounting unit about 50Kg supplied with circ & manual. **£87.**

MARCONI AIRCRAFT H.F. Rx high grade 6 band Rx covers 150/510Kc in two bands & 2 to 18.5 Mc/s in 4 bands uses 11 min valves with 2x RF, BFO, Xtal Cal, AF O/P for low imp phones, reqs 28v DC supply, as high resolution film scale for the 4 HF bands, compact unit weight 10 Kg supplied with circ. **£75.**

COMMUNICATIONS Rx made by Murphy Radio for RN covers 60/560Kx in two bands & 1.5 to 30Mc/s in 3 bands uses 13 miniature valves with 2x RF, 3x IFs at 800Kc, BFO, Xtal Cal etc Swt Selectivity of 8, 3, 1 Kc & 200c/s, AF O/P for 100 ohm phones or 2 watts into 600 ohm, in case size 13x14x14" supplied tested with handbook, note these require ext supplies of 250v HT 100 Ma 150v Stab & 6.3v AC at 4 amps. **£115.**

PAN & TILT HEADS HD type for outdoor use for 240v mains give 360° pan & ±45° tilt fixing by 6" dia ring possible use as Aerial or Dish mounts **£35.**

RADIOSONDE UNIT TYPE 11 older type unit as 3 valves, AF, Osc, Mod & RF Osc at 27Mc/s (reqs 90v ht & 2v It) as 3 var freq osc in range 600/1000c/s for Temp. Press & RH these are selected in turn by swt unit and are used to mod the RF from Tx. Supplied in new cond with chart & circ. **£6.50** also have a few M.60 R/S at **£12.50.**

RECEIVER UNIT part of Army 128 Set tunes 2 to 8 Mc/s in two bands 4x min valves plus BFO in case size 8x5x4" req 135v & 1.5v O/P for HR phones with circ. **£15.** Batteries **£4.50,** 2 for **£8.**

Above prices include Carr/Postage & VAT. Please allow approx. 14 days for delivery. Goods ex equipment unless stated new, SAE with enquiry or 2 x 14p stamps for list 27.

A. H. SUPPLIES
122, Handsworth Rd., SHEFFIELD S9 4AE.
Phone 444278 (0742).

SMC SERVICE

Free Finance on many items. Two-year guarantee on Yaesu. Free Securicor on major Yaesu items. Access and Barclaycard over the telephone. Biggest Branch, Agent and Dealer network. Ably staffed, courteous, Service Department. "B Services" Securicor contract at £3.50!! Biggest stocks of amateur equipment in UK. Twenty-two years of professional experience.

FREE FINANCE

On regular priced items from: Yaesu, Ascot SMCHS, CDE, HyGain, Channel Master, Hansen, SMC, MFJ, KLM, Mirage and Hy Mound, on invoices over £100 SMC offers Free Finance! How is it done? Simple, pay 20%, split the balance equally over 6 months or pay 50% down and split the balance over a year. You pay no more than the cash price!!

YAESU MUSEN

SMC are proud to be UK agents for Yaesu Musen the brand leader in Amateur Radio. Their exclusive concentration on communications equipment – The most diverse product line and a reputation for continuous innovation are your assurances that SMC and Yaesu can provide equipment to exactly fit your needs and you will be at, and remain at, the forefront of today's high technology.

GUARANTEE

Yaesu's own warranty does not extend outside Japan. Repairs are the responsibility of the UK dealer selling the set. SMC's two-year guarantee is backed, as UK distributors, by daily contact with the factory and many tens of thousands of pounds of spares and test equipment. Avoid hawkers offering sets without serial numbers, spares, service or advice back-up.



FT ONE £1295 (inc. VAT)

COVERAGE

RX; 150 KHz-30 MHz. Continuous general coverage.
TX; 160-10m (9 bands). 1.5-30 MHz commercial version.

MODES

All modes; AM, CW, FM, FSK, LSB, USB.
Tx and Rx on opposite sidebands possible.

FREQUENCY SELECTION

No bandswitch. Multiple methods of frequency setting. Main dial; "velvet smooth" 10 Hz resolution, 3 speeds; Set MHz, KHz/R – Normal, KHz/R – Fine, Controls RIT or offset (synthesised clarifier).
Inbuilt Keypad; direct digital entry to 100 Hz, Fast/slow, up/down tuning, Scanning manual or auto mode.

RECEIVER

Receiver dynamic range up to 100 dB. Pair of low noise power transistors in RF. Ring mixer with LO injection at 10 dBm. Advanced variable threshold noise blanker. AGC: slow-fast-off. Squelch control. Variable RF attenuator and RF gain circuits. SSB; Variable bandwidth and IF shift. 3 CW and 2 FSK bandwidth positions. 300 Hz, 600 Hz, 2,400 → 300 Hz, 6 KHz, 12 KHz.

TRANSMITTER

100w RF, (50% duty FSK) all solid state. No preselector, no "plate" tune, no loading controls. Mains and 12V DC. Switch-mode PSU built in. CW change over delay adjustable through to *full break in*. Electronic keyer built in. Drive level control. Front panel adjustable VOX. Signal monitor feature. RF processor, compression control concentric with mic gain. Auto mic gain, reduces extraneous off mic noises.

MEMORY

Two memory banks (A + B) each with 10 slots. Simplex or Semi duplex A, B, RxA/TxB, TxA/RxB. ANY frequency storable. ANY TX-RX split within coverage. RIT offset stored together with memory channel.

METERING

Two large moving coil meters (+3 digitals and 12 leds). R.H. (Rx-TX); 'S' (1-9, + 20, + 40, + 60 dB) and ALC level. L.H. switched; Ic (20A), Va, Discriminator (FMzero), Compression (0-25 dB), Forward, Reflected. Digital readout to 100 Hz. Analogue markings for "feel". Dedicated digital readout of RIT offset to ±9.9 KHz. Digital readout of memory channel number recalled. LED's; Processor, Noise blanker, Auto mic gain, Monitor, Peak – Notch filter, Scan, Transceive, TX – RX Clarify, Dial Lock, Tx Disabled.

NEW BRANCHES – SPECIAL OFFER

WE ARE PROUD to announce the opening of two new branches, and would be so delighted if you went along and said hello to Ian G3PRR in Grimsby or Peter G4GSA in Stoke that for the fortnight Monday January 4th until Saturday January 16th, we will be, for personal callers only, be offering,

FIVE PER CENT OFF OUR LIST PRICES
(see "Free Finance" section for eligible items)



FT208R
£209.00
2.5w, 2m
12.5/25 KHz
Synthesised

FT708R
£219.00
1w, 70cms
25 KHz
Synthesised



FRG7700 £329

0.15-30 MHz General Coverage Receiver
AM/SSB/CW/FM (Memory Version £409).



FT902DM £885

10-160m. SSB, CW, AM, FM, Deluxe
digital, Keyer, fan, variable bandwidth etc.

★FT902D £800
★FT902DE £790

9
0
2

FTV901R Transverter Frame, 3 band **£195**
FV901DM Digital VFO, 40 mem. Scan **£260**
YO901P Monitor scope/Panadaptor **£330**
FC902 Antenna tuner unit **£135**
SP901 Speaker (Patch version £55) **£31**



FT707 £569

10-80m. 100w PEP. SSB, AM, CW. Variable
IF bandwidth, Digital (10w model £485).

7
0
7

FP707 Mains P.S.U. (20A) **£125**
FC707 Antenna tuner **£85**
FV707DM Digital VFO 6 Mem **£203**
FTV707R Transverter Frame, 1 Band **£90**
50TV 50MHz **£70**, 70TV 70MHz **£80**,
144TV 144MHz **£100**, 430TV 432MHz **£185**.



FT209R £249

2m, synthesised. 25 + 12½ KHz steps FM,
1 KHz + 100 Hz steps SSB. 2½W PEP.



FT480R £379

2m Synthesised, 25 12½, 1 KHz steps FM.
1 KHz, 100, 10 Hz steps SSB. 10W PEP.



FT107M £725

10-160m. 100w PEP. SSB, AM, CW. Vari-
able IF. Deluxe all solid state. (DMS version
£799).

1
0
7

FP107E Mains PSU External **£113**
FP107 Mains PSU Internal **£102**
FTV107 Transverter frame 2 band **£119**
FV107 External VFO **£98**
FC107 Antenna Tuner **£112**

PRICES INCLUDE VAT @ 15%

FREE SECURICOR DELIVERY

2 YEAR IMPORTER WARRANTY



SOUTH MIDLANDS COMMUNICATIONS LIMITED

S. M. HOUSE, OSBORNE ROAD, TOTTON, SOUTHAMPTON, SO4 4DN, ENGLAND
Tel: Totton (0703) 867333, Telex: 477351 SMCMM G, Telegram: "Aerial" Southampton

GRIMSBY
S.M.C. (Grimsby)
247A Freeman St.,
Grimsby, Lincolnshire.
Grimsby (0472) 59388

STOKE-ON-TRENT
S.M.C. (Stoke)
76 High Street,
Talkie Pits, Stoke.
Kidsgrove (07816) (72644)

LEEDS S.M.C. (Leeds)
257 Otley Road,
Leeds 16, Yorkshire.
Leeds (0532) 782326
9-5.30 Monday-Saturday

CHESTERFIELD
S.M.C. (Jack Tweedy) LTD, 102 High
Street, New Whittington, Chesterfield.
Chesterfield (0246) 453340
9-5 Tuesday-Saturday

WOODHALL SPA S.M.C.
(Jack Tweedy) LTD, 150 Horncastle
Road, Woodhall Spa, Lincolnshire.
Woodhall Spa (0526) 52793
9-5 Tuesday-Saturday

Bangor
Tandraage
Edinburgh

John
Mervyn
Jack

G13KDR (0247) 55162
G13WWY (0762) 840656
GM8GEC (031665) 2420

Stourbridge
Redcar

Brian
Simon

SMC AGENTS
G3UL
G4EQS

(03843) 5917
(0642) 480808

Pontybodkin
Swansea
Jersey

Howarth
Peter
Geoff

GW3TMP
GW8EBB
GJ4ICD

(0244) 549563
(0792) 872525
(0534) 26788



comment...

The Unexpected

IN THE FIRST FEW WEEKS after the legalisation of CB in the United Kingdom, an amazing change has taken place in the pattern of activity on the 27MHz band. Despite the limited number of rigs available so far, the new legal f.m. channels are even busier in the Bournemouth and Poole area than the a.m. band was earlier in 1981, and the a.m. channels are almost deserted. Our spies tell us that the pattern is much the same in London and the other big cities too. I am sure that not even Willie Whitelaw or Timothy Raison in their wildest dreams would have forecast that such a state of affairs would come about so soon. Interference from sideband CB operation, particularly Italian and French, is still a problem during daylight hours, spreading right across the UK f.m. band, though this should soon disappear with the falling sunspot count. It is to be hoped that the Home Office will quickly clamp down on s.s.b. operation here, possibly by the simple expedient of making it illegal to **possess** any unlicensable transmitter.

CB has aroused an interest in many people who have moved on to amateur radio, swelling the clubs, filling the RAE evening classes, and completely overwhelming the Home Office department which deals with amateur licences. The final licence resulting from the May 1981 exam wasn't issued until the end of November, and there were 5000 (yes, 5000) entrants for the December 1981 exam.

While amateur radio clubs have been enjoying a rapid rise in

membership, the CB clubs have seemingly been melting away. One south coast group is said to have dropped from a membership of well over a thousand to just one hundred after legalisation.

Quite a few of our readers have queried what *PW's* coverage of CB will be, now that we have a legal system. Well, we shall be treating it as just another application of radio of interest to the hobbyist, with articles on installation which will also be of help to radio amateurs, plus some rig reviews.

What we shall very definitely not be doing is to devote space to DXing on the CB bands—CB is intended to be a short-range mobile telephone system, not another amateur radio service. Nor shall we be giving coverage to "10-codes", jive talk, truckers' talk, etc. If CB is to be the most use to the most people, plain language is absolutely essential, and the whole system must be easily understood. The *CB Code of Practice*, which you will find on page 62 of this issue, really tells the CBer all he needs to know, and covers several points which are of relevance to amateur radio too.

Geoff Arnold



services

QUERIES

While we will always try to assist readers in difficulties with a *Practical Wireless* project, we cannot offer advice on modifications to our designs, nor on commercial radio, TV or electronic equipment. Please address your letters to the **Editor, "Practical Wireless", Westover House, West Quay Road, Poole, Dorset BH15 1JG**, giving a clear description of the problem and enclosing a stamped self-addressed envelope. Only one project per letter please.

Components for our projects are usually available from advertisers. For more difficult items, a source will be suggested in the "Buying Guide" box included in each constructional article.

PROJECT COST

The approximate cost quoted in each constructional article includes the box or case used for the prototype. For some projects the type of case may be critical; if so this will be mentioned in the Buying Guide.

CONSTRUCTION RATING

Each constructional project will in future be given a rating, to guide readers as to its complexity:

Beginner

A project that can be tackled by a beginner who is able to identify components and handle a soldering iron fairly competently. Generally this category will be used for simple projects, but sometimes for more complicated ones of wide appeal. In this case, construction and wiring will be dealt with in some detail.

Intermediate

A project likely to appeal to a wide range of constructors, and requiring only basic test equipment to complete any tests and adjustments. A fair degree of experience in building electronic or radio projects is assumed.

Advanced

A project likely to appeal to an experienced constructor, and often requiring access to workshop facilities and test equipment for construction, testing and alignment. Constructional information will generally be limited to the more critical aspects of the project. Definitely not recommended for a beginner to tackle on his own.

SUBSCRIPTIONS

Subscriptions are available to both home and overseas addresses at £13.00 per annum, from "**Practical Wireless**" Subscription Department, Room 2613, King's Reach Tower, Stamford Street, London SE1 9LS. Airmail rates for overseas subscriptions can be quoted on request.

BACK NUMBERS AND BINDERS

Limited stocks of some recent issues of *PW* are available at 95p each, including post and packing to addresses at home and overseas.

Binders are available (Price £4.30 to UK addresses and overseas, including post and packing) each accommodating one volume of *PW*. Please state the year and volume number for which the binder is required.

Send your orders to **Post Sales Department, IPC Magazines Ltd., Lavington House, 25 Lavington Street, London SE1 0PF**. All prices include VAT where appropriate.

Please make cheques, postal orders, etc., payable to IPC Magazines Limited.

PRODUCTION LINES

ALAN MARTIN G8ZPW


New Inexpensive d.m.m.

Recently introduced by Centemp is a very competitively priced digital multimeter called the Model 3T.

This d.m.m. provides six functions in 16 ranges which permits measurement of d.c. voltages, a.c. voltages, d.c. current, resistance, diode/continuous check and a transistor h_{FE} measurement facility, all displayed on a 12.5mm high liquid crystal readout.

Function selection is via push-button switches at the side of the instrument which is of robust construction and is claimed to have a long battery life.

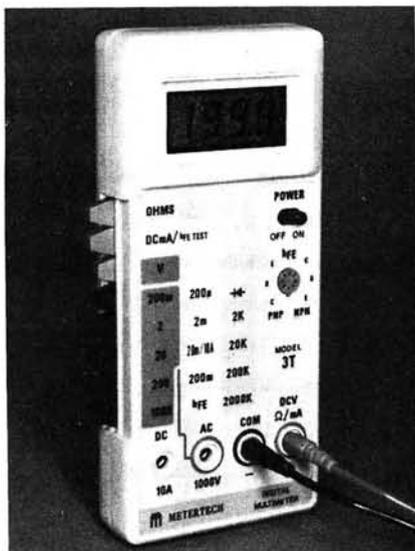Supplied complete with battery, test leads and instruction manual, the Model 3T costs just £49.99 which includes VAT and carriage, and is obtainable from: *Centemp, 62 Curtis Road, Whitton, Hounslow, Middlesex TW4 5PT. Tel: 01-894 2723.*



Antenna Mount

Most amateur radio enthusiasts, at some time, will have experienced difficulty in fixing their base station antenna mount, especially if they live in a flat. The Altron QM1 could help to solve this problem.

Designed to fit into window apertures, the QM1 antenna mounting system is capable of accommodating small or light antennas such as those for v.h.f., u.h.f., CB or TV.


Installation is simple and fast, requiring no drilling of walls and the unit locks in position, either vertically or horizontally, in most window apertures between 635mm and 1.07m (other sizes are available).

The QM1 is supplied zinc plated for weather protection and with a range of optional accessories provides a versatile mounting system that can be adapted to accommodate a small rotator and even a v.h.f. beam. Further

details are available in return for an s.a.e.

Prices for the QM1, which includes VAT, are £27.60 for the standard bright metal finish and £29.60 for the deluxe black finish, plus £1.50 p&p.

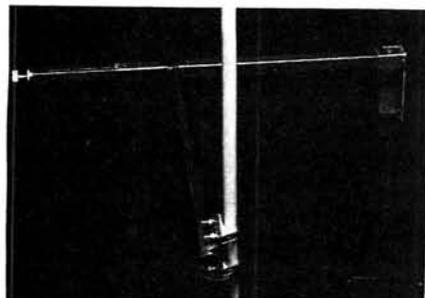The QM1 is obtainable on a cash-with-order basis, from the manufacturer: *Allweld Engineering, Unit 6, 232 Selsdon Road, South Croydon CR2 6PL. Tel: 01-680 2995, 01-681 6734.*



New Trio from Trio

Latest information from Lowe Electronics lists three new pieces of Trio equipment.

First, the TR-2500, a compact 2m f.m. hand-held transceiver which features keyboard channel selection, 10 channel memory with improved memory back up, memory scan, programmable automatic band scan, r.f. power 2.5W (Hi) and 0.3W (Low), plus a variety of new accessories. The photograph shows the TR-2500 installed in the ST-2 base stand/charger which allows the unit to be used whilst the NiCad battery pack is being recharged. Price for the TR-2500 will be in the region of £210.

Second, the R-600, a basic general coverage receiver designed specifically for the newcomer to short wave listening and intended to complement Trio's range of general coverage receivers. Price will be approximately £250.

And last, but by no means least, the TS-780 v.h.f./u.h.f. all-mode dual bander base station.

Among its many features are: frequency ranges 144-146MHz on 2m and 430-440MHz on 70cm, 10 memories including two priority memory positions (9 and 10); comprehensive scanning facility of programmed frequencies or band of frequencies; i.f. shift and r.i.t.; two v.f.o.s allow independent frequency setting within either band which enables efficient cross-band operation. The price is expected to be around £750.

All three of these products should be available in the UK by early January 1982. For further details of price and availability contact: *Lowe Electronics Ltd., Bentley Bridge, Chesterfield Road, Matlock, Derbyshire DE4 5LE. Tel: (0629) 2817 or 2430.*



▲The R-600

◀The TR-2500

▼The TS-780




IC-2E Offsprings

Thanet Electronics has recently introduced two new Icom hand-held transceivers, whose design is based on the very popular IC-2E.

First, the IC-4E, a 70cm f.m. transceiver which possesses the following features: frequency range 430 to 439.995MHz; receiver sensitivity 0.5 μ V (0.3 μ V); transmitter output power 1.5W (2.3W) on the BP3 battery pack (as supplied) to 2.3W (3.3W) on the BP5 (high-power) battery pack; repeater shift +1.6MHz; tone burst (via push switch on volume control) 1750Hz \pm 0.1Hz; and finally a very useful new feature is the switch selectable "listen-input" facility which allows the repeater input to be monitored by lifting the receiver input by 1.6MHz. The figures shown in brackets are test results obtained, by



The IC-4E

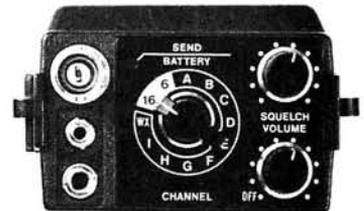

The IC-M12

Thanet Electronics, from their demonstration model.

The second new transceiver is the IC-M12, probably the first synthesised hand-held marine band transceiver, which has 12 channels (pre-programmable to the customer's choice), semi-duplex operation, which is automatic, and r.f. output power of 1W.

Many of the optional accessories for the IC-2E are suitable for use with

these transceivers, excepting those which are frequency sensitive.

The VAT and p&p inclusive price of the IC-4E is £199 and it is expected the price of the IC-M12 will be about the same.

By the time this issue of *Practical Wireless* is published, these transceivers will be obtainable from: *Thanet Electronics Ltd., 143 Reculver Road, Beltinge, Herne Bay, Kent CT6 6PL. Tel: (02273) 63859.*

Power Supplies


Yorkshire-based Fisher Karpark Industries Ltd., one of the UK's leading auto accessory and transformer manufacturers, has launched two new mains-operated power supply units, called CB Radio Powerpaks.

Both units provide a regulated 13.8V d.c. with a ripple factor of less than 50mV r.m.s. at their respective continuous rating.

The smaller model is designed to deliver 3A continuously and accommodate short surges of up to 5A; the larger unit delivers 6A continuously and 8A at peak. Both units feature electronic short-circuit and overload protection. Prices are 3-5A model £15.90 and 6-8A model £20.45.

Both F.K.I. Powerpaks carry a 12 month guarantee and are available from Halfords or most CB shops.

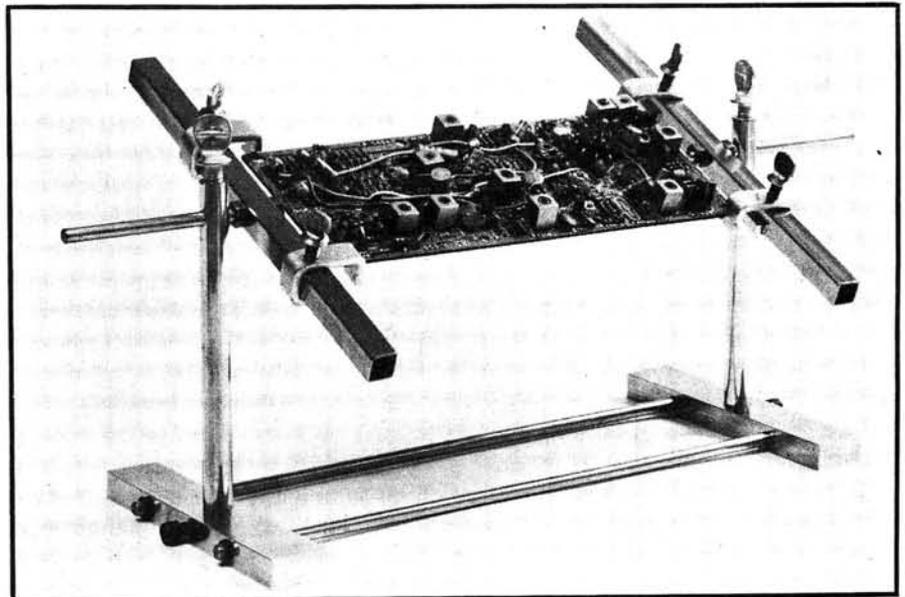Fisher Karpark Industries Ltd., Gratix Works, Gratix Lane, Sowerby Bridge, West Yorkshire HX6 2PH. Tel: (0422) 33533.



PCB Holders

Two new p.c.b. holders have recently been announced by their British manufacturers, Carlton Nichol & Co. Ltd. Both are constructed of aluminium and plated steel, and allow easy rotation of p.c.b.s through 360° with positive locking at any angle.

First, the CNC 6 will accommodate p.c.b.s measuring up to 254 x 178mm which are held in the frame by spring-loaded clips. The larger CNC 9 will accept p.c.b.s up to 203 x 203mm and these are held in position by sliding vee clamps. The clamps locate on the very edges of the board thus avoiding the risk of face damage to the p.c.b.

An anti-static foam pad is also available as an optional extra. The pad, which is on a backing plate, clips on to

the rotating arms of the p.c.b. holder.


A larger version of the CNC 9 will shortly be available and this will accommodate double-Euro size boards.

The VAT inclusive prices for these products are: CNC 6 £13.80, CNC 9 £15.95 and the anti-static foam pad (203 x 203mm) £9.20 plus £1.50 p&p.

The holders are available direct from: *Carlton Nichol & Co. Ltd., Goldkey Industrial Estate, Kelvedon, Essex.*

If you please

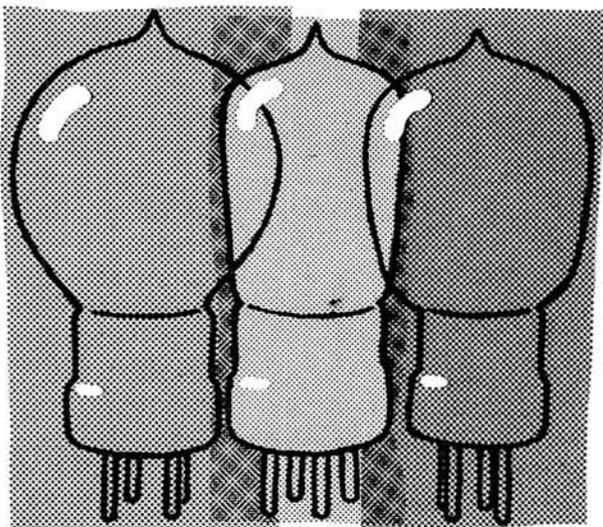Please mention "Production Lines", when applying to manufacturers or suppliers featured on these pages.



Valves used in the early days

G. JESSOP G6JP

In the early days of wireless it was necessary to buy a receiving licence for even the simplest of receivers. If you wanted to conduct transmitting experiments you had to apply to the Post Office for an experimental licence. You had to detail the experiments you wanted to carry out, if they were not satisfied then the licence would not be granted.

It was at the outbreak of the First World War that these licences were revoked, and there was a considerable delay before experimental licences were then restored. Even then the licences for receiving apparatus included the following restriction. "Thermionic valves shall not be used without special permission from the Post-Master General." As a result of pressure by the Wireless Society of London and its affiliated societies, the Post Office introduced a new Wireless Telegraphy Bill for the approval of Parliament, and experimental licences became available in the spring of 1920.

British experimenters were therefore about 18 months behind the Americans. The British had not been idle, they had been busy getting to know something of the new devices, the thermionic triode, so that they could introduce them into their equipment, replacing the spark transmitters and crystal receivers.

During the war very substantial developments in the production of valves had been made so that as soon as the experimenters were permitted to use them there was a considerable supply both from war surplus and also new production.

Bright Emitter Types

All the valves were fundamentally of elementary electrode construction and there were both "soft" and "hard" versions of receiving types available, the "soft" valve being gas filled and the "hard" valve being devoid of all gas. The "soft" valve had been favoured by both the Navy and the Air Force for detector purposes on account of its considerably higher sensitivity than the "hard" type; however, critical adjustment of its operating conditions eventually caused it to be discontinued.

The basic valve which was to be used in quantity by the experimenters was the "R" type. This was generally similar to the valve developed by the French Telegraphie Militaire known as "TM" type, and was made by all the

existing manufacturers: Osram-Robertson Lamp Works, Z Electric Lamp Co., Edison-Swan Electric Co., British Thomson-Houston Co.

The electrode system had a cylindrical electrode mounted at right angles to the pinch (seal), which only had the minimum of electrode support wires. The filament used was a single straight wire of pure tungsten. Commercially, some of the makers used different types of references for the same model of valve.




Although the "R" valve was initially used both for transmission and reception, both by the services and later experimenters, there were a number of variants of the basic type for transmission purposes. In these, higher power was needed and for this a larger filament was used. To get this within the electrode system the filament was either crimped or coiled, with such type references as "B", "B2", "A" or "T15" given to these variants.

All these valves were substantially of similar characteristics, having an amplification factor (M) of around 9, anode impedance (R) of 30k Ω and a "slope" (M/R) mutual conductance of about 0.3mA/V. With this low slope it was often found that oscillation over a wide band could not be maintained. It should be remembered that at this time wavelengths of 440m (685kHz) and 1000m (300kHz) or more were being used and this together with an interest in short waves such as 200m (1494kHz) led to a good deal of circuit experimentation. Probably the most notable change was the use of a separately tuned aerial circuit in place of the then customary direct connection of the aerial to the oscillatory (anode and grid) circuit, often with the valves' h.t. voltage on the aerial.

The same type of valves had to be used in all stages of the receiving equipment—for high frequency amplifiers, detectors and low frequency amplifiers. In the h.f. amplifiers one of the most often used circuits was resistance capacity coupling or aperiodic (untuned) transformers which were often wound with resistance wire to reduce any tendency to self-oscillate.

In the detector (rectifier) stage, the most important item was the high resistance grid leak, which in the early days had to be home-made. It was often made adjustable using anything from wet cotton in an electrolyte to a pencil lead track on a suitable bobbin with a roller or sliding contact.

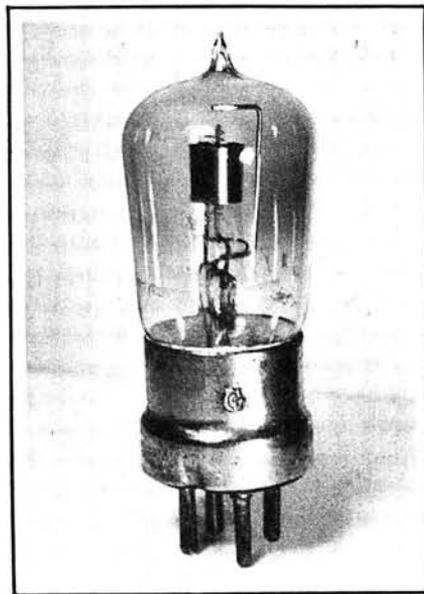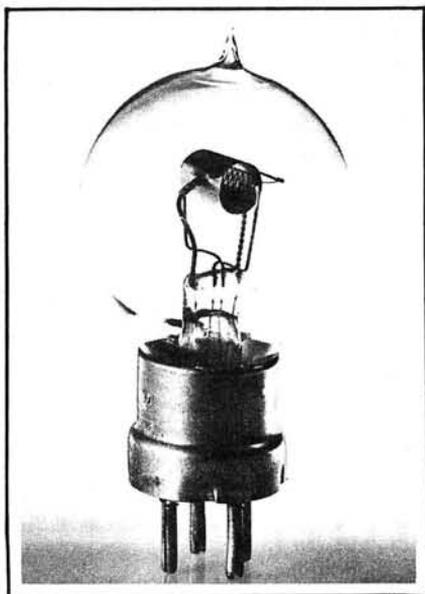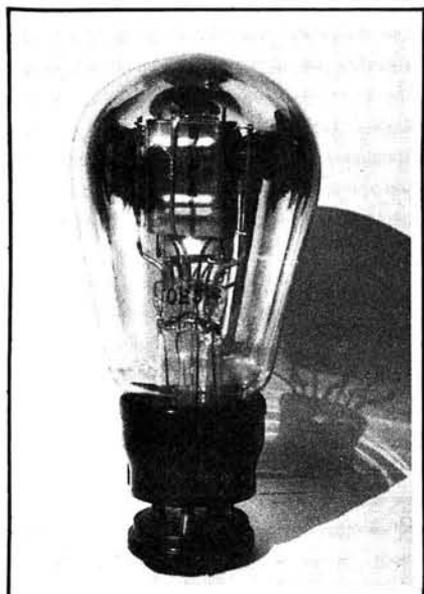In low frequency stages, these were almost always transformer coupled, although resistance capacity couplings were soon adopted, often being claimed to be less



Three examples of early valves each with its very distinctive shape, all of these and many others are in the author's own collection

noisy! Because of the low gain obtained with these low slope valves, there was a tendency to use multiple stages if you could afford the cost of valves and components.

In addition to the generic "R" type there was a radically different design produced by Osram for Captain H. J. Round (Marconi Co.); this was the low capacity tubular type "V24". Characteristically the "V24" was similar to the "R" valve, but a different type was developed for rectifier purposes. This had a high amplification factor (50) and was known as the "Q", which had a grid mesh; the "QX" variation followed shortly after with a close pitch wound grid. Both of these valves were intended to operate effectively without a grid leak as anode or bottom bend rectifiers.

Another type which was developed by Captain Mullard had a small vertically mounted electrode system which was fitted into a special cap known as "Acorn". This, the 53, had the anode and grid contacts at the side and one of the filament contacts at the bottom, the other filament connection was a small piece of metal connected by copper tape to the base, the metal cap being cemented to the top pip of the bulb. Larger versions of these valves were known as "C" and "D" (soft versions) and commercially as ORA "B".

This design may have had the apparent advantages proposed by the "V24"; they were in practice rather unsatisfactory owing to poor insulation of the acorn cap material. In addition to this they did not possess the low capacity feature of the "V24".

A newcomer to the valve producers, "Cossor", produced a valve "P1" of very different electrode structure. In this the filament was arranged as part of a loop enclosed by a grid, formed into an inverted mesh basket which was enclosed by a hood type anode.

All these valves having bright emitter filaments (pure tungsten), in order to obtain adequate emission, had to be operated at or near their maximum rated voltage. Most filament supplies were at this time obtained from accumulators, which in a fully charged state were higher than the nominal 2V per cell, and the valves were rated with odd voltages, making it necessary to provide some means of setting the voltage to the rated value. Also because valves varied slightly, in multi-valve sets it was necessary to provide individual adjustable resistances (rheostats).

The life of such filaments was limited, and there was some advantage in reducing the operating temperature to the lowest possible consistent with adequate performance, if for no other reason than to prolong the life as much as possible.

As mentioned earlier the stage gain obtainable using these valves was quite small, but it soon became apparent that when reaction was applied, if critically adjusted, a detector's sensitivity was vastly increased. This method of improving a receiver's performance soon became standard practice. Sometimes the reactance was applied from the detector to the aerial circuit even when there were several h.f. amplifiers between the aerial circuit and the detector.

Usually, when reaction was applied to the aerial circuit there was some radiation from the aerial, which caused considerable interference. Some experimenters used to key their receivers by use of a finger being applied to the aerial connection for short distance contacts (several miles).

So far the valves mentioned have largely referred to those used for receivers; however, there were power valves for transmitters. By the end of 1919 triodes of anode dissipation of more than 500W were available. These were also all bright emitter filaments and of a miscellany of filament voltages. Probably the most popular with the transmitting experimenters were the Marconi Osram "T50", "T100", "T1" or "T250", or the Mullard "0/50", "0/150" and "0/250". In service considerable operational experience was gathered by the makers, from their use at decreasing wavelengths by the experimenters, thus enabling them to introduce improvements into the valve structures.

All the early Mullard transmitting valves were distinguished from the Marconi Osram types by the relatively large extension tubes at the top and bottom of the bulb. One of these was the exhaust tube, the lower was the filament seal. This practice was subsequently dropped and the more usual seal off made at the side of the bulb. These transmitting types were of course of relatively high impedance for use with anode voltages between 1500V and 5000V. Their cost was quite high and they were only used in the early days by those of substantial income.

The usual circuit used at this period was in the main a single valve self-oscillator for c.w. operation. Modulation was either some form of variable grid-leak provided by a valve, an absorber valve connected to the aerial circuit, or


in the so called choke control method, where the oscillator and the modulator were connected together with an iron cored choke in series with the h.t. supply.

In some more elaborate transmitters a second r.f. valve was used; this was an oscillator to drive an amplifier usually of a larger power size. The main problem was the prevention of self-oscillation in the amplifier, neutralisation was not developed until some years later.

Dull Emitter Types

The first major step forward in higher efficiency occurred when filaments were made of thoriated tungsten, which only required a quarter or less of the power needed by the earlier types, though the other characteristics were very similar. Many new types appeared at fairly regular intervals from most of the makers, though they were mainly intended for the entertainment market (broadcast receivers). There were a few "power" valves intended for the output stage of these receivers, which because of their improved characteristics, especially lower impedance, attracted the experimenters for use in their transmitters. Perhaps the best of these were the "B4", "DE5" and "LS5". All of these had a slope of around three times that of the old "R" type. They all had filaments of some form of "V" shape in place of the earlier single wire, they also had a flat oval shaped grid and a correspondingly larger anode.

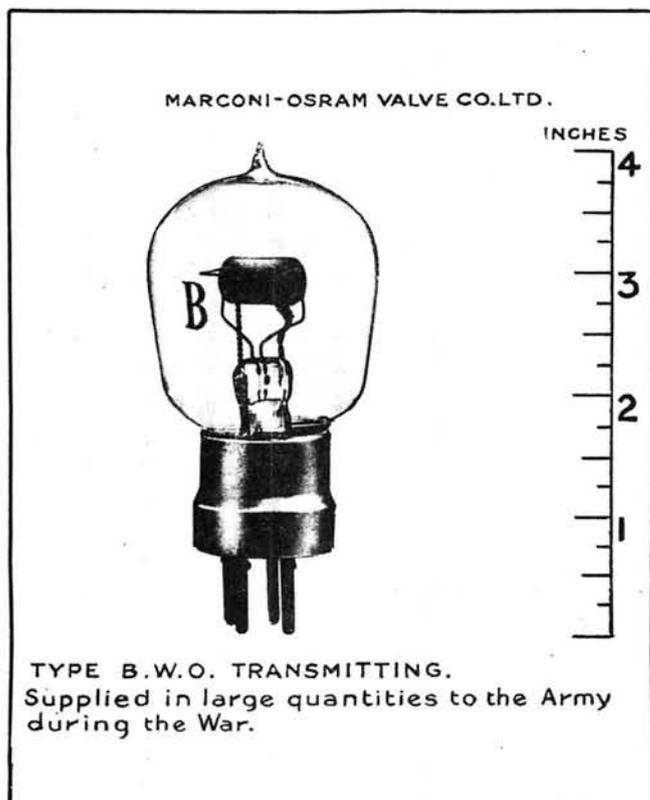Of these types the "LS5" was probably used by a larger number of operators than any other type. Although its characteristics were similar to the others, it had a higher anode rating, both in power and maximum voltage. Apart from its use as indicated, it was adopted by the Post Office for telephone repeater service, where it was known as "VT25".



An early Marconi-Osram Valve Co. transmitting valve

(Marconi Co.)

Mullard 0/50 valve showing the two extension tubes at the ends of the glass envelope



(Mullard Ltd)

This valve was eventually made in three different impedances with corresponding amplification factors. The high impedance type was the "LS5B" intended for use in resistance capacity coupled low frequency amplifiers. The low impedance type "LS5A" was intended for low frequency output stages to drive large loudspeakers of the moving coil type. Later, yet another version appeared known as the "LS5D" and was similar to the "LS5", but

Dull Emitters

Company	Type No.	Volts	Amps	M	R	M/R
BTH	B4	6.0	0.25	6	7kΩ	0.86
BTH	B5	2.8	0.06	7.5	20kΩ	0.375
BTH	B6	3.0	0.12	7.5	10kΩ	0.75
Ediswan	R	4.0	0.75	8	25kΩ	0.324
Ediswan	AR	4.0	0.65	5.5	22kΩ	0.4
Ediswan	ARDE	1.8	0.3	10	25kΩ	0.4
Ediswan	ARO6	2.7	0.06	13	45kΩ	0.29
Mullard	DO6LF	2.2	0.06	7	25kΩ	0.28
Mullard	DO6HF	2.2	0.06	20	55kΩ	0.36
Mullard	D3HF	1.8	0.35	10.5	40kΩ	0.26
Mullard	D3LF	1.8	0.35	6	15kΩ	0.4
Mullard	DFORA	2.6	0.07	4.5	17kΩ	0.225
Osram	DER	1.8	0.37	8	25kΩ	0.32
Osram	DE3	2.8	0.06	6	17.5kΩ	0.34
Osram	DE5	5.0	0.25	7	8kΩ	0.875
Osram	DE5B	5.0	0.25	20	26kΩ	0.77
Osram	DE6	1.8	0.4	5	13kΩ	0.385
Osram	LS5	5.0	0.8	5	6.5kΩ	0.77
Osram	DEV	2.75	0.2	6	22kΩ	0.27
Radion	Az	3.5/4	0.25	5.5	42.5kΩ	0.129
Radion	D4	3.5/4	0.25	11.5	55kΩ	0.21

continued on page 36▶▶▶

MODS

IMPORTANT—The ideas presented here are suggestions only, and as they are untried by this magazine, we cannot accept responsibility for any resultant damage, however caused. Before alterations are attempted, care should be taken to ensure that any guarantee is not invalidated, and it should also be borne in mind that modifications usually have an adverse effect on resale prices. In cases where specialist skills or equipment are needed, most dealers will undertake the work for a reasonable fee.

Roger Hall G8TNT (Sam)

No. 13

In Mods 12, memory back-up and semi-reverse repeater details were given for the Trio TR-9000. This month continues with further mods for this popular 2m multi-mode rig.

Memory Scan

I said last month there are some mods that are recommended only for the very experienced constructor.

The same is true of this next mod from Kris G8AUU, who is probably better known as the co-author of the *International v.h.f. f.m. Guide*. Kris has noticed that several of the Trio rigs use the same microprocessor even though they don't all make use of the same functions, and he has suggested taking a closer look at the μ PD 650C inside the TR-9000. This is the same chip that is used in several other sets and they have memory scan on them. It is then reasonable to assume that this chip can be persuaded to scan the memories of the TR-9000 and if we look at Fig. 5 we can see how easily this can be achieved.

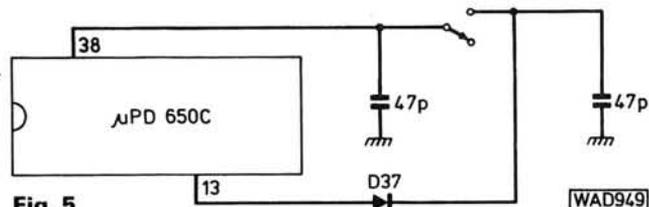


Fig. 5

Merely connecting a diode (almost anything will do) between pins 13 and 38 on the chip will start it scanning. The interconnecting lines should be decoupled, as in the diagram, and the switch can be mounted anywhere you like. You may even be able to use a couple of the pins inside the microphone socket, if you don't mind losing the Up/Down scan facility.

Extending the Frequency Range

The last of this month's mods deals with extending the frequency range. Mr J. R. Walker sent in a very descriptive letter which detailed the procedure for doing this. He suggests moving a diode (D32) and running two new wires and his idea works perfectly, but Kris G8AUU has improved on the original idea.

When rigs are made in Japan, the manufacturer knows that he has to sell his product all over the world and the trend now is for them to make sets that will work

anywhere in the world with only one or two small mods needed to adjust the band edges and channel spacing. The Trio TR-9000 conforms to this pattern and the two key components are D31 and D32.

There are four basic markets for 2 metre amateur equipment and as you can see from Table 1, the TR-9000 can be made to work in any of them by just altering the two diodes. Mr Walker suggested moving the diode in position D31 to position D32 and this would indeed give us an extended frequency range *but* it would also give us channel spacings of 10 and 5kHz. This may suit some people but I far prefer 25kHz spacing when I'm operating mobile and I find it inconvenient to have to keep spinning the dial on a rig that has 5kHz spacing. Kris has solved the problem very simply and in the process he has made the TR-9000 into a rig that will work anywhere in the world, with any of the band edges coupled with any of the channel spacings and all for the price of a switch and two resistors.

Table 1

Zone	Diodes	Band Limits	Channel Spacings	
Japan	None	144.000– 145.999	20	10
USA	D31	143.800– 148.995	10	5
Europe	D32	144.000– 145.9875	25	12½
Aus/NZ	D31+D32	144.000– 147.995	25	5

First of all remove all the knobs and the microphone socket threaded ring from the front panel. Then remove the top and bottom covers and the four screws holding the front panel, which can now be carefully pulled forward enough to allow the l.e.d.s to be disconnected. Remove the two screws on each side to allow the front chassis to drop forward and then it should be possible to remove the multi-way connectors from the MPU board. In the middle of this board is D32 and you should now lift the anode end of this diode.

You will need an s.p.d.t. switch (RS No. 316-973 is suitable) and this should be mounted anywhere you like on the set. Mine is on the back panel because there is a space for another hole there, but the position is not important.

Now run a wire from the anode of D32 to the common tag on the switch, then run two more wires from the other two tags back to the p.c.b. and solder them to the anode pads for D32 and D31. These are printed on the board and you will be able to see where the anodes would go if the diodes were there (see Fig. 6).

Two 470 ohm resistors should now be soldered to pins 17 and 18 on Q15 on the control board (X53-1160-61) and then two wires should then be soldered onto the free ends of these resistors. The other ends of these wires can then be soldered to pins 14 and 15 of Q15 on the p.l.l. board. The resistors should be properly sleeved and then they can be allowed to lie on the top of the chip.

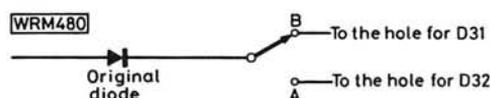


Fig. 6

The mod is now complete but it still needs to be explained. We must first differentiate between powering-up the set and turning it on. To power up something is to apply power to the power input socket, whereas turning something on means rotating the On/Off switch.

continued on page 57

air test

USER REPORTS ON SETS AND SUNDRIES

SOTA COMMUNICATION SYSTEMS

SCL 144PS

Linear Amplifier

Introduced to their expanding range of amateur radio equipment during last year, the Sota SCL 144PS is a very well constructed, mains powered 2m linear amplifier.

When provided with an input r.f. drive level of 10W the amplifier will deliver 100W from its single SD 1416, high gain r.f. power device.

To complement this 10dB TX gain, a switchable receiver pre-amplifier is included within the package. The p.c.b. mounted pre-amplifier features a U310 low noise and wide dynamic range f.e.t., providing a realistic 12dB gain figure and respectable associated 1.5dB noise factor. Pre-amplifiers that achieve a greater gain are realisable, but with currently available receiver front-end stages, apart from a "psychological" "S" Meter boost, the degradation in strong signal handling and reduction in spurious-free dynamic range incurred, make the exercise non-viable.

Power for the amplifier is obtained from a conservatively rated, compact mains p.s.u., featuring an ILP toroidal transformer and 25A full wave bridge rectifier, series regulated by three TIP 3055 power transistors. All the active components of the p.s.u. are mounted on a large, 200 x 130 x 25mm, black anodised finned heatsink, which forms one of the end cheeks of the housing. Heatsink fins are configured vertically to provide maximum thermal efficiency.

Due to the efficient layout of the r.f. amplifier and p.s.u. stages a resulting compact, 250 x 140 x 205mm, overall size is obtained. All operating controls are mounted on the grey stove enamelled aluminium front panel and

comprise a large mains rocker switch and three small toggle switches for selection of p.a., pre-amp and f.m./s.s.b. operation options. The latter switch selects the "hang" time constant appropriate for the operating mode.

A phono type socket is provided on the rear apron to allow direct p.t.t. line over-ride, "hard" switching, if required, supplementing the alternative r.f. VOX operation. In the mains off condition the amplifier reverts to straight-through bypass operation. LED indicators, adjacent to the front panel



toggle switches, are provided to display the selected operating pattern.

Additional rear apron features include INPUT/OUTPUT SO 239 u.h.f. sockets and a 15A fuse receptacle, providing protection on the d.c. supply line.

Operation

The SCL 144PS has been extensively tested over a period of six months, during which time it has constantly performed, on demand, without any discernible problems.

It should go without saying that any amplifier device that has survived without incident the rigours of a 24-hour outing during v.h.f. National Field Day must have a lot going for it! Judging from the reports received by members of the Bournemouth Radio Society, during and after the event, all were well pleased. The reviewer was able to observe "on air" signal performance first hand on this occasion, being located within 15 miles of the NFD


site and beaming head-on. A very clean, spurious-free, linear signal was received from the contest station exhibiting none of the splatter effects occasionally encountered as a result of the search for the last drop of drive.

During subsequent operations from the home QTH in Poole, the SCL 144PS has been used in conjunction with several current 2m transceivers, including the Trio 7800, Yaesu FT-290R and Icom 202-S. In all cases a very useful increase in range capability was obtained, the lower powered rigs producing a proportionally reduced output.

With rigs such as the Trio 7800, which are able to provide well in excess of the normal input requirements of the amplifier, an attenuator must be fitted. In this event Sota are able to provide this facility, once furnished with relevant details of the driving rig.

Whilst the r.f. power transistor used in the SCL 144PS is extremely rugged and reliable, normal precautions should be taken to avoid operation into open or short circuit loads, or high v.s.w.r. conditions.

John M. Fell

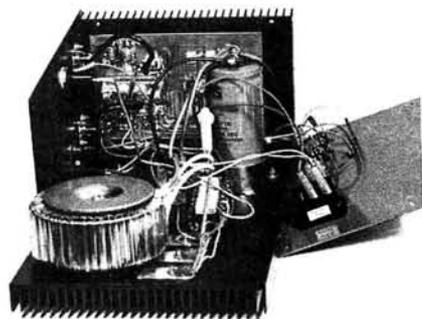


Our thanks for the extended loan of the review sample go to Mr. Ian Barton of: **Sota Communication Systems Ltd., 24-26 Childwall Lane, Bowring Park, Liverpool L14 6TX. Tel: 051-480 5770.**

The current VAT inclusive price of the SCL 144PS linear amplifier is £172.50 and it is available direct from the above address.

Catronics

— the
South East England
Specialists
in Everything for the
New Computer Age.

video genie system

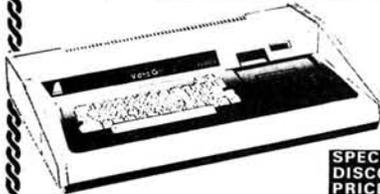

- 12K MICROSOFT BASIC
- 16K RAM
- UHF MODULATOR
- INTERNAL CASSETTE
- 2nd CASSETTE INTERFACE

SPECIAL DISCOUNT PRICE **£343** INCL. VAT

- ★ EXPANSION BOX AVAILABLE
- ★ DISK DRIVE IF REQUIRED
- ★ 100's OF PROGRAMS
- ★ TRS-80 LEVEL II SOFTWARE COMPATIBLE

If you cannot call write for FREE illustrated leaflet

COMPUTER-RTTY PACKAGE for TRS-80 and VIDEO GENIE

The New Catronics CT600 RTTY package enables a TRS-80 (16K, level II) or Video Genie computer to send AND receive Radio Teletypewriter Messages. The package includes a pcb module and a program cassette. The pcb carries the terminal unit which includes a PLL discriminator for reception and can handle wide shift as well as narrow. Also on the pcb is an audio oscillator which plugs into the microphone socket of your SSB or FM transmitter to produce FSK or AFSK transmissions. The Transmit/Receive relay on the pcb is keyboard controlled, as are all other functions. The software allows operation on 4 speeds - 45, 50, 75 and 110 bands. Text transmission is simplified with automatic letters/figures shift and there is provision for 10 memories, which can be stored on cassette. Transmit text (including memories) is displayed and entered into buffer, even whilst receiving.

Send now for complete details!

CT600 complete package: £121.90 (plus £1.50 p&p)

Special package (saving over £35 on list price):

Video Genie Computer + CT600 for only £460 INCL. VAT.

CREDIT TERMS available. Pay by Access, Barclaycard, Catronics Creditcharge Card.

Personal Shoppers Welcome



Catronics (Dept. 282), 20 WALLINGTON SQUARE,
WALLINGTON, SURREY SM6 8RG.
Tel. 01-669 6700 (9 a.m. to 5.30 p.m. Sat 12.45 p.m.) Closed lunch 12.45-1.45

PMR DEALERS

Please call us for an ICOM Dealership.

Ask for Dave Stockley.



THE ICOM IC100E
HIGH BAND MOBILE & BASE
HOME OFFICE APPROVED



Thanet Electronics Ltd
143 Reculver Rd, Herne Bay,
Kent. Tel. 02273 63859
Telex 965179

SOTA'S LINE OF LINEAR AMFILERS

Model No. SCL 144/30 £50 + VAT
RF drive 2/3 Watts RF output 20/30 watts
Receiver pre amp independently controllable.

Model No. SCL 144/40 £60 + VAT
RF drive 10 watts RF output 40 watts
Receiver pre amp independently controllable.

Model No. SCL 144 £80 + VAT
RF input 10 watts RF output 100 watts
Receiver pre amp not applicable.

Model No. SCL 144P £100 + VAT
RF input 10 watts RF output 100 watts
Receiver pre amp independently controllable.

All the above Models are designed for a nominal 12 volt supply. If AC mains operation is required, please see our Model SCL 144/PS as featured on page 26 of the February issue of Practical Wireless.

Sota Communication System also manufacture Receiver pre amps for 28 MHz and 144 MHz these being two versions one which operates as pre amp for installation internally in Transceivers and the other version which has an RF switching facility and is mounted in a neat aluminium case.

The above specifications are a brief outline to our Product Range please send an S E A or telephone for further information.

Trade and export enquiries welcome. We are Northern Representative for "VHF Communications" Magazines & Kits. Telephone credit card orders taken. Carriage or postage on all equipment.

Please all 28 days for delivery

Sota Communication Systems Ltd.

22-26 Childwall Lane, Bowring Park, Liverpool L14 6TX, England
Tel. 051-480 5770 Telex: 628702 SOTA G
Hours 9am-6pm Monday to Friday. 9am-1pm Saturday
Radio Consultants, Suppliers and Manufacturers

BARCLAYCARD

AMERICAN EXPRESS

ACCESS



MICROWAVE MODULES LTD

LOOK!!

THE NEW 144/100-S!!

**EVEN BETTER FACILITIES!!
EVEN BETTER VALUE!!
NOW FITTED WITH S0239 CONNECTORS**



**A COMPATIBLE 12 AMP REGULATED MAINS POWER SUPPLY IS AVAILABLE AT £72 inc. VAT AND POSTAGE, SO THAT FIXED STATION AND MOBILE USE MAY BE OBTAINED FROM THIS VERSATILE AMPLIFIER.
DO YOU HAVE ANY CHOICE??**

This new 144MHz solid state linear amplifier, MML 144/100-S, is intended for use with any existing 144MHz equipment having an output power of 10-15 watts. When used in conjunction with such a drive source this linear amplifier will provide an output power of 100 watts.

Several front panel mounted switches controlling the internal switching circuitry, allow the unit to be left in circuit at all times. The linear power amplifier and the ultra low-noise receive pre-amplifier, which are incorporated into the unit, can both be independently switched in and out of circuit. In this way, all four operational combinations are possible.

By means of an internal RF vox circuit the linear will automatically switch onto transmit, when 144MHz drive is applied to the input socket. It is possible to override this facility by the connection of an earth to the phono socket, located on the rear panel. This connection is compatible with all current transceiver PTT lines. The RF vox circuit is suitable for both SSB and FM modes.

The inclusion of the latest state of the art power transistor (rated at 145W dissipation) guarantees highly reliable and ultra-linear performance, thus making the unit ideal for all modes of operation (SSB, FM, AM, CW and SSTV).

The amplifier utilises recently developed matching techniques, which allow safe operation even when improperly subjected simultaneously to 50% overdrive and a supply voltage of 15V. The PA transistor is thermally tracked against temperature variation and operational temperature rise.

The receive preamplifier uses one of the latest dual gate MOSFETs (3SK88) in a noise-matched configuration. This technique together with careful optimisation of overall gain makes the pre-amplifier ideal for use ahead of any popular 2 metre transceiver. The sensitivity of most current 2 metre transceivers is such that a preamplifier gain of 12dB is sufficient to ensure an excellent overall system noise figure. A preamplifier with gain in excess of this figure will prove unduly detrimental to the strong signal-handling performance of the transceiver.

All circuitry is constructed on high quality glass fibre printed circuit board and protection is included against reverse polarity. The unit is housed in a highly durable, extruded aluminium enclosure. RF input and output sockets are located on the rear panel together with the phono socket, fuseholder and power lead. The unit is supplied complete with all necessary connectors.

FEATURES

- ★ 100 WATTS OUTPUT POWER
- ★ LINEAR ALL MODE OPERATION
- ★ STRAIGHT THROUGH OPERATION WHEN TURNED OFF
- ★ ULTRA-LOW NOISE RECEIVE PREAMP – FRONT PANEL SELECTABLE
- ★ EQUIPPED WITH RF VOX AND MANUAL OVERRIDE
- ★ LED STATUS LIGHTS FOR POWER, TRANSMIT & PREAMP ON
- ★ SUPPLIED WITH ALL CONNECTORS

SPECIFICATION

Power output:	100 watts (within 0-5dB) typical
Power input:	10 watts nominal
Power requirements:	13.8 volts ± 12 amps for 100 watts output
Overall preamp power gain:	12dB
Overall preamp noise figure	Better than 1-5dB
RF connectors:	S0239
Weight:	1.5Kg (3lb 5oz)
Overall size:	265 × 117 × 54mm (10 ⁷ / ₁₆ × 4 ⁵ / ₁₆ × 2 ¹ / ₁₆ in)

**MML144/100-S:
£129.95 inc VAT
(P&P £2.75)
TELEPHONE YOUR ORDER FOR
IMMEDIATE DESPATCH**

ALL MICROWAVE MODULES PRODUCTS ARE FULLY GUARANTEED FOR 12 MONTHS (INCLUDING PA TRANSISTORS)



WELCOME


MICROWAVE MODULES
BROOKFIELD DRIVE, AINTREE, LIVERPOOL L9 7AN, ENGLAND
Telephone: 051-523 4011 Telex: 628608 MICRO G

CALLERS ARE WELCOME, PLEASE TELEPHONE FIRST

**HOURS:
MONDAY-FRIDAY
9-12.30, 1-5.00**

MODULATED WAVEFORM GENERATOR

Geoff ARNOLD G3GSR

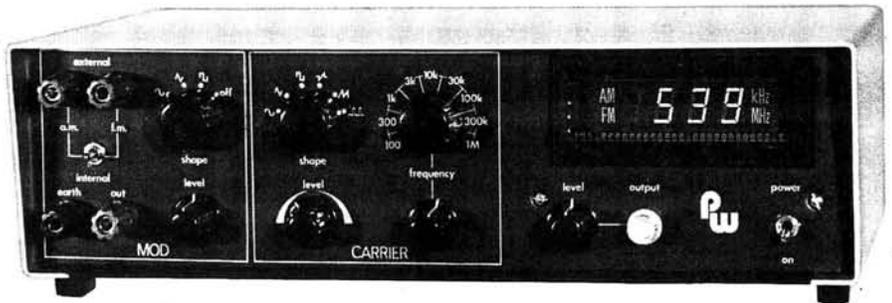

Though many home constructors like to design and build their circuits from transistors, resistors and capacitors, others take advantage of the wide variety of "building blocks" available to them. These building blocks are often just integrated circuits, though some of these are extremely complex in themselves, but more and more sub-assembly kits or modules are offered to the enthusiast, giving him the chance to put together a complex unit quickly and easily. That unit can generally be modified or adapted to do the particular job that the constructor has in mind.

The *PW* Modulated Waveform Generator is a unit based on this sort of approach, though as presented here it has not started on its process of development or adaptation. The data sheets which come with the two kits used give many ideas for other functions. The rest is up to you.

Modulated waveform generators or function generators—sources of sine, square or triangular waveforms, etc., are fairly common animals nowadays, giving outputs well up into the lower radio frequency bands. Many of them can be frequency modulated or swept, but so far as I know, the only reasonably priced generator i.c. providing amplitude modulation (including suppressed carrier d.s.b.) by means of an on-chip balanced modulator is the Exar XR-205.

The XR-205 comes in a 16-pin dual-in-line package and has three separate circuit sections: a voltage-controlled oscillator (v.c.o.) which generates the basic periodic waveforms; a balanced modulator which provides amplitude or phase modulation; and a buffer amplifier section with a low-impedance output (typically 50Ω) and high current drive capability of around $\pm 10\text{mA}$ peak-to-peak. The system block diagram and pin-outs of the XR-205 are shown in Fig. 1.

The combination of v.c.o. and balanced modulator can provide sine, triangle, square, sawtooth, ramp and pulse waveforms; double-sideband amplitude modulation, including suppressed carrier modulation; frequency modulation; sweep generation; tone-burst generation; simultaneous a.m./f.m.; frequency-shift keyed (f.s.k.) signal generation; phase-shift keyed (p.s.k.) signal generation; on/off keyed oscillation. Power supply requirements are either a single +12V rail or balanced $\pm 12\text{V}$ rails.

By using two XR-205 i.c.s, one to provide the carrier signal and the other the modulation, a versatile, easily-assembled signal source for testing purposes, or for generating demonstration waveforms for use in classrooms or lecture theatres, is produced.

Generator Circuit

The circuit diagram of the *PW* Modulated Waveform Generator, based on the XR-205K kit, of which more later, is shown in Fig. 2. The modulation generator, IC1, can provide sine, square or triangular wave outputs, as selected by S3, at a fixed frequency of about 1.2kHz. This could be made variable if required. The output of IC1 is available at front-panel terminals for external use, with a peak-to-peak amplitude of about 2.6V (sine), 2.1V (triangle) or 1V (square). It is also fed via S4, which selects internal a.m. or f.m., to IC2. The a.m. input is applied via pin 3 to the balanced modulator, whilst the f.m. input is applied to the v.c.o. via pin 13, where it is superimposed on the standing voltage from the wiper of R31, the CARRIER FREQUENCY control. External a.m. and f.m. can

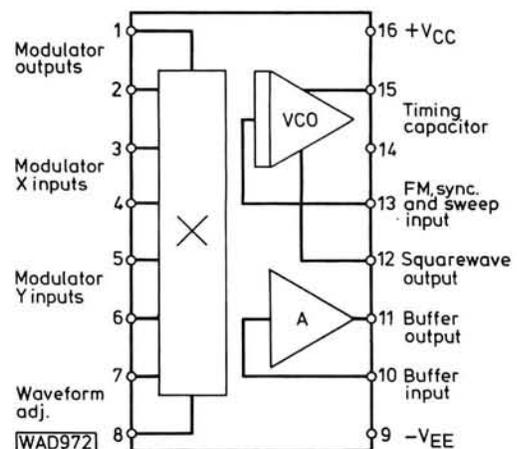


Fig. 1: XR-205 system block diagram and pin-outs

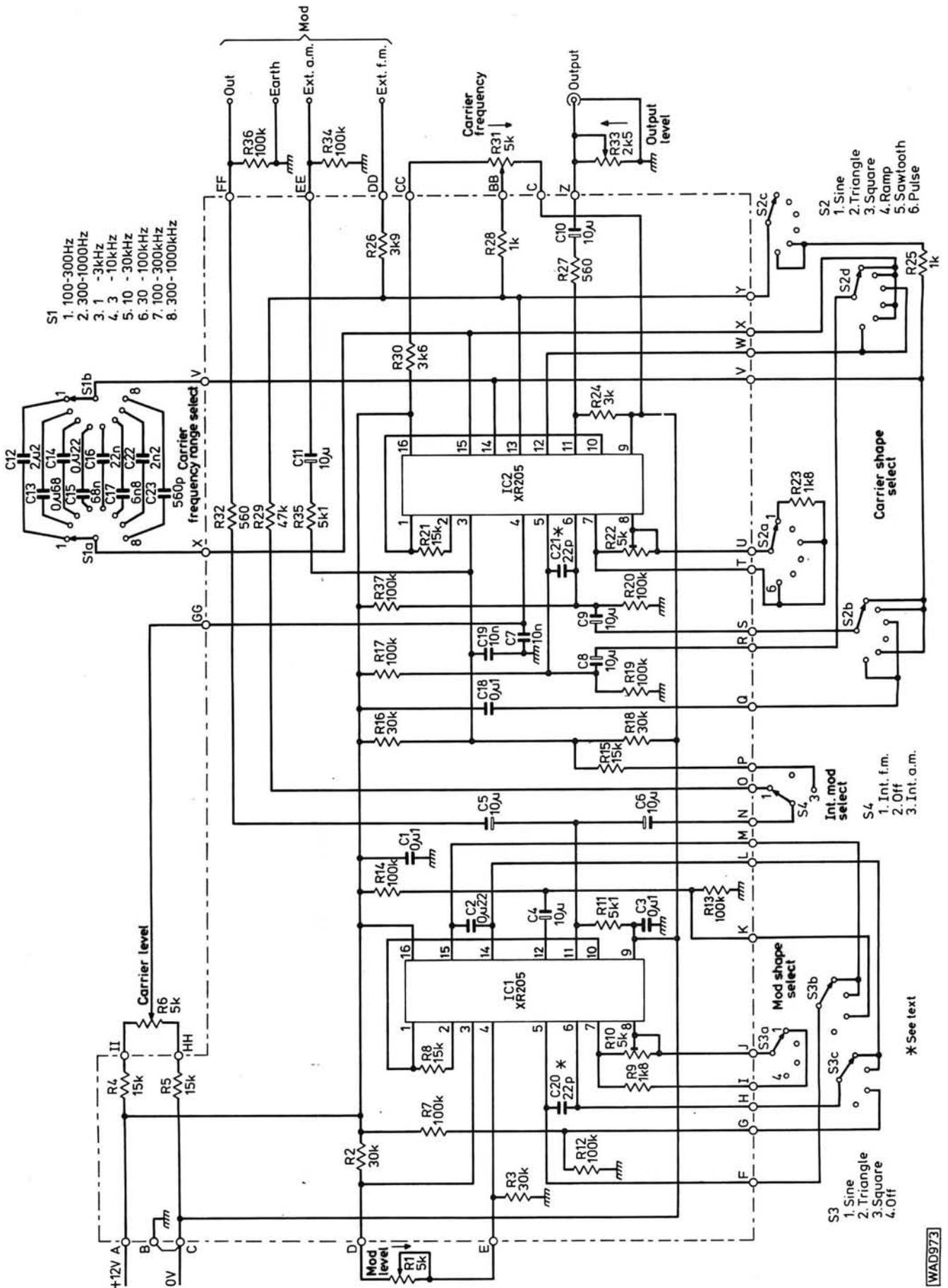


Fig. 2: Circuit diagram of the modulated waveform generator, less power supply

* See text

WAD973

also be applied via front panel terminals, so that simultaneous a.m. and f.m. can be imposed on the output waveform. The output level from IC1 is set by R1, the MOD LEVEL control.

The carrier signal is generated by IC2, providing sine, triangle, square, ramp, sawtooth or pulse waveforms, as set by S2, the CARRIER SHAPE switch. The carrier frequency range is selected by S1 in a 1—3—10 sequence from 100Hz to 1MHz (nominal). In fact, at least 10 per cent overlap is provided at either end of each range, and the overall span (depending upon component tolerances) will be about 70Hz to 1.15MHz.

The CARRIER LEVEL control, R6, applies a bias voltage to one input of the balanced modulator (pin 4) of IC2. When R6 is set to approximately mid-position, the carrier will be suppressed (specified as typically -52dB at the null point for frequencies below 1MHz), allowing double-sideband, suppressed carrier (d.s.b.s.c.) amplitude-modulated signals to be produced. Carrier will be produced with increasing amplitude as R6 is turned to either side of the null, with the sawtooth, ramp and pulse outputs having a polarity dependent on which way the control is moved.

For simplicity, a single-rail power supply configuration was used, based on a 12 volt 3-terminal regulator i.c. The circuit is shown in Fig. 3. The measured current requirement of the completed waveform generator board is around 30mA maximum, and so a 100mA rated supply would be more than adequate. However, in looking at the prices of the necessary mains transformer, rectifier bridge, reservoir capacitor and regulator chip, it seemed worth while to spend a little extra and build in a power supply with a reserve of capacity which could be used to drive other circuits needing a 12V d.c. stabilised supply, providing they did not mind the negative rail being earthed. Therefore, a 1A supply was included, available to the outside world via terminals on the back panel. The regulator i.c. is foldback-protected against overload, so there is no danger to it from external short-circuits, and no point in putting a fuse in the line to the back panel terminals.

Frequency Readout

Although not an essential part of the waveform generator, we decided that it would be useful to demonstrate one application of our Special Offer this month (see page 45), by building in a digital frequency readout. The Timestep DFC4 has two limitations which affect its use in this particular project; these are its 1kHz resolution and its lower frequency limit of 10kHz, but it has still proved very useful. The Timestep data sheet suggests improving the audio frequency performance by the use of an external clock oscillator with dividers, instead of the on-chip crystal oscillator, but this has not been tried.

The alternative to using a digital frequency readout would be to calibrate the CARRIER FREQUENCY control, R31, although this would probably require some juggling of the values of capacitors associated with the CARRIER FREQUENCY RANGE switch, S1, to make the scales coincide, unless panel space could be found for a separate scale for each range.

Circuit diagram information for the DFC4 comes with the kit, but Fig. 4 shows the power supply circuitry, and Fig. 7 the p.c.b. external connections. The DFC4 incorporates a bright blue-green phosphorescent $3\frac{1}{2}$ -digit readout, and requires +12V, -9V and 3V a.c. supplies. It is therefore not possible to run it from the same supply as the waveform generator board, and in any case the kit includes its own power supply components.

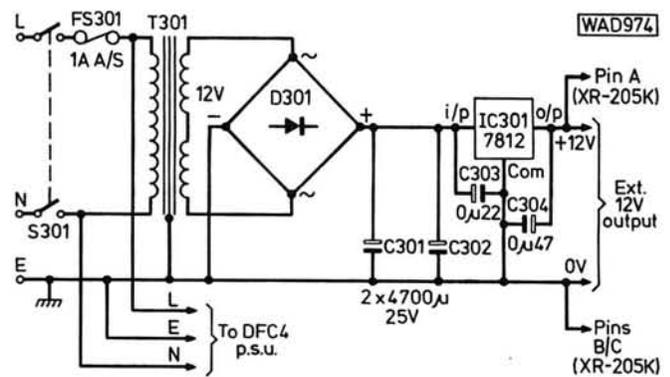


Fig. 3: Waveform generator power supply circuit

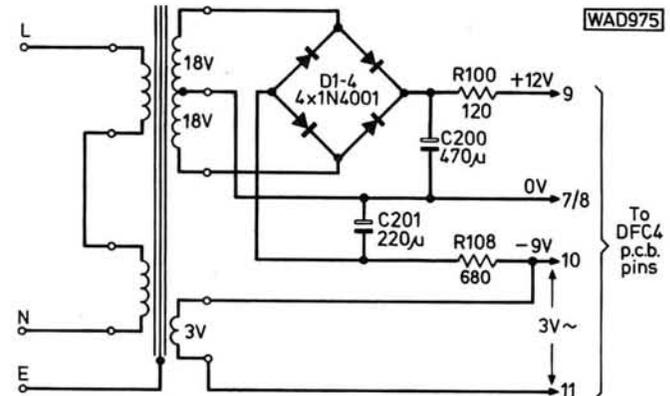


Fig. 4: Power supply for the DFC4 digital frequency counter

Construction—Generator

A kit comprising two XR-205 i.c.s, a printed circuit board etched and drilled ready for assembly, plus comprehensive data and instructions is available in the UK from Rastra Electronics Ltd. The rest of the components (resistors, capacitors and switches) plus a power supply and a box to build it all into, have to be provided by the constructor.

The p.c.b. which comes with the kit is fairly big (140 x 76mm) but there is really little point in making it smaller in view of the large number of external controls required, which means that you cannot use too small a box or case.

Most of the waveform generator components mount on the supplied p.c.b. as shown in the layout drawing supplied with the XR-205K kit, the exceptions being the four potentiometers, three fixed resistors, and the frequency range capacitors which are mounted on S1. To avoid problems with parasitic oscillations, S3 should be mounted as close as possible to IC1, and similarly S2 and IC2. Capacitors C20 and C21 can be fitted if necessary to suppress parasitics. The instructions supplied with the kit suggest that the interconnecting wiring to S2 and S3 should not be longer than about 50mm. The layout of the prototype as shown in the photographs does not quite achieve this ideal, though it could be improved by mounting the switch wafers further back on the mechanisms. The rotary switches used are supplied with rear shafts about 60mm long, which are cropped to the required length. See the comments under "Operation".

Switch S1 should have the range capacitors soldered into place between the two wafers, and flying leads at-

tached to the rotor contact tags before mounting the switch on the front panel. If you have difficulty locating the correct value capacitors for C13 and C15, they can be made up by paralleling 0.47 μ F and 0.22 μ F, and 47nF and 22nF respectively.

Switch S2 should also have flying leads, plus all the links and resistors R23 and R25 attached before mounting, otherwise the underneath contact tags are inaccessible. S3 is a single-wafer switch and all its tags are accessible after fitting, so that it does not matter whether the connecting wires are attached to the switch or the p.c.b. first.

It is essential to fit terminal pins to the p.c.b. for all external connections. The board is mounted on the floor of the case using two 4BA screws and nuts with short spacers.

Apart from the transformer and reservoir capacitors, all the waveform generator power supply components can be easily accommodated on a small piece of Veroboard, as shown in Fig. 5. The board can be mounted by means of the heatsink tab of the 7812 regulator, with Sticky Fixers between the board edge and the case rear panel to minimise flexing of the regulator package legs. The board is so light that no further fixing is really required.

Two 4700 μ F capacitors (C301 and C302) are used rather than a single 10000 μ F for the reservoir, partly because of a slight cost saving and partly because they are smaller and easier to accommodate. They are secured by means of a nylon cable-tie, fitted through two holes drilled in the case floor. The holes should have their sharp edges chamfered to prevent cutting into the tie when it is tightened.

CONSTRUCTION RATING Intermediate

BUYING GUIDE

The wafer switch parts and other items listed with RS Components stock numbers are available from several of our advertisers, including C. Bowes Electronics Ltd. The XR-205K kit is available from Rastra Electronics Ltd., 275-281 King Street, Hammersmith, London W6 9NF, price £16.99 including post, packing and VAT. See page 45 for availability of the Timestep DFC4 kit.

APPROXIMATE COST £85

Construction—Counter

The Timestep DFC4 kit comes with instructions for assembly and wiring into equipment, plus programming

★ components

Resistors

$\frac{1}{2}$ W 5% Carbon film

560 Ω	2	R27, 32
1k Ω	2	R25, 28
1.8k Ω	2	R9, 23
3k Ω	1	R24
3.6k Ω	1	R30
3.9k Ω	1	R26
5.1k Ω	2	R11, 35
15k Ω	5	R4, 5, 8, 15, 21
30k Ω	4	R2, 3, 16, 18
47k Ω	1	R29
100k Ω	10	R7, 12-14, 17, 19, 20, 34, 36, 37

Potentiometers

$\frac{1}{2}$ W linear law, $\frac{1}{4}$ in spindle

5k Ω 3 R1, 6, 31*

$\frac{1}{2}$ W log law, $\frac{1}{4}$ in spindle

2.2k Ω 1 R33 (or 2.5k Ω)

$\frac{1}{4}$ W Cermet presets

5k Ω 2 R10, 22

Switches

S1	2-pole, 8-way	} See Table 1
S2	4-pole, 6-way	
S3	3-pole, 4-way	
S4	Single-pole changeover with centre "off" position, miniature toggle	
S301	2-pole on/off, miniature toggle	

Capacitors

Ceramic plate

22pF 2 C20, 21*

Ceramic disc

10nF 2 C7, 19

0.1 μ F 3 C1, 3, 18

Polyester film, 250V

22nF 1 C16

68nF 1 C15*

0.22 μ F 2 C2, 14

0.68 μ F 1 C13*

2.2 μ F 1 C12

Polystyrene

220pF 1 C24

560pF 1 C23

2.2nF 1 C22

6.8nF 1 C17

Tantalum bead, 35V

0.22 μ F 1 C303

0.47 μ F 1 C304

Electrolytic, 25V double-ended

10 μ F 7 C4-6, 8-11

4700 μ F 2 C301, 302

Semiconductors

Integrated circuit regulator

7812 1 IC301 (12V 1A)

Diode bridge

200V 1.6A 1 D301 (RS Components 261-491)

Miscellaneous

Mains transformer T301, 12V 1.6A secondary. Fuse FS301, 1A anti-surge, 20mm with holder. BNC round socket with earth tag. Screw terminals/4mm sockets: 4 red, 2 black. Pointer knobs: 3 21mm, 4 14.5mm, for $\frac{1}{4}$ in shafts. Case, Vero 202-21091E. Display bezel, Vero 203-22236A. Exar XR-205K kit, comprising 2 XR-205 i.c.s, p.c.b. and data sheets. Timestep DFC4 kit, comprising all components, display, p.c.b. and data sheets. Veroboard. Terminal pins.

Fig. 5: Waveform generator rectifier/regulator board

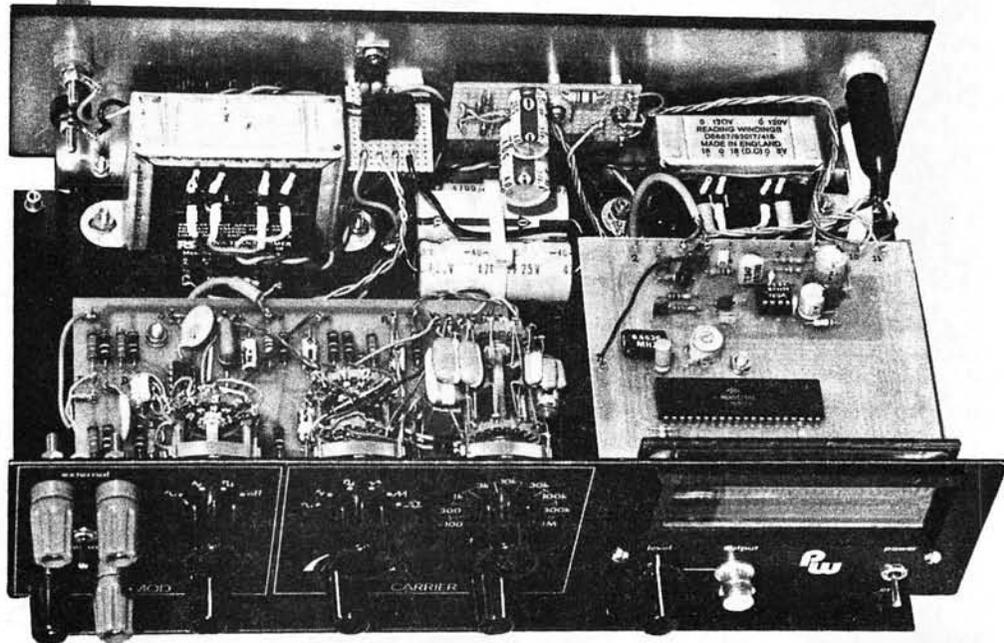
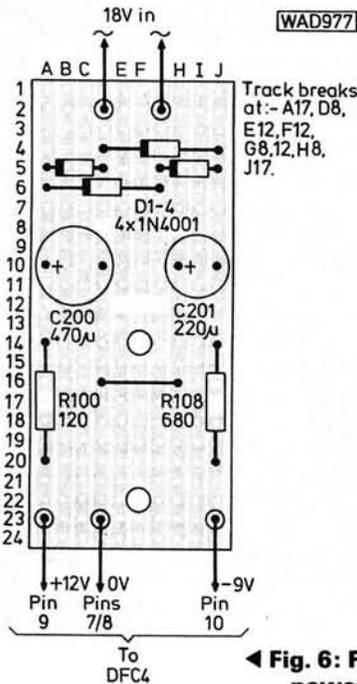
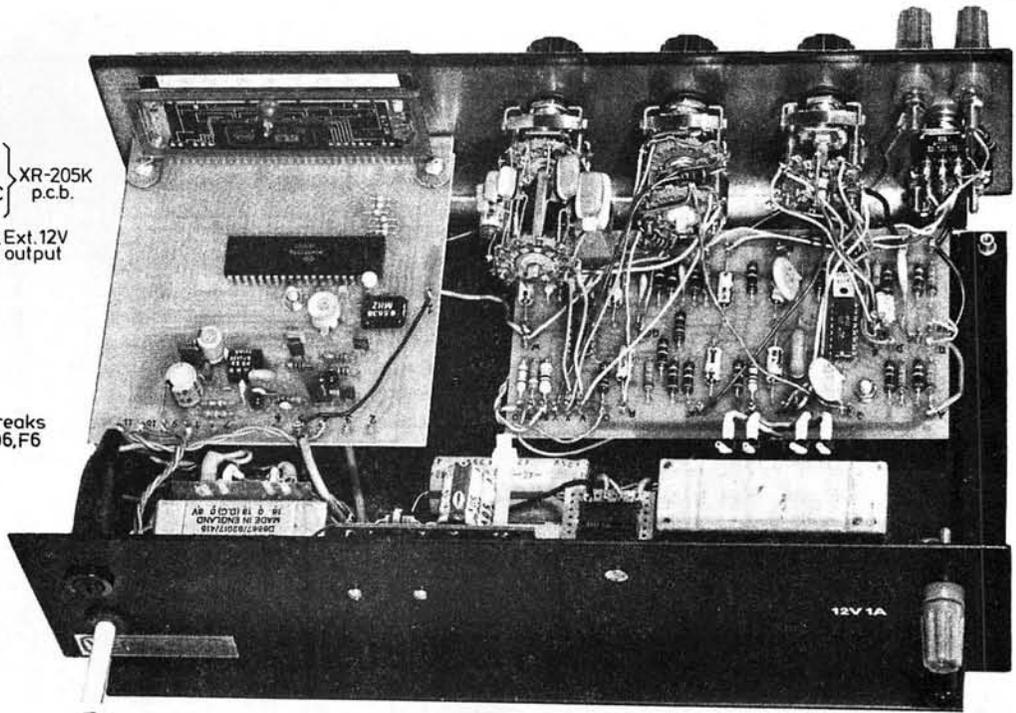
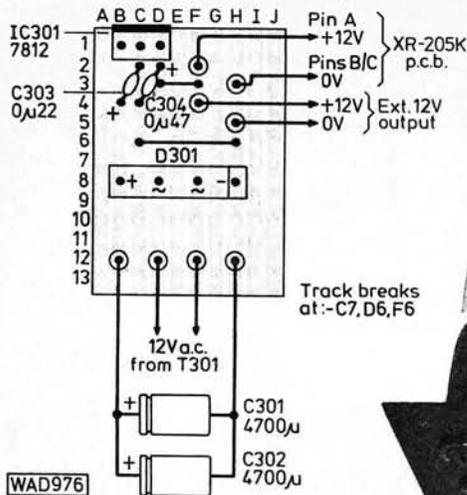


Fig. 6: Frequency counter power supply board

details to achieve the required frequency offsets when used as a tuning readout in a radio receiver. In the present application, the DFC4 is required to operate as a straight frequency counter, without i.f. offset, using the direct (long/medium wave) input. Drive for the counter is tapped off from the OUTPUT LEVEL control, R33, via a 220pF capacitor, C24, and a short length of screened cable. The board is secured at its front edge by means of two small angle brackets (not part of the kit), fixed to the board by 4BA screws and nuts and to the front panel by 4BA screws and hank bushes. If hank bushes are not available, nuts can be used instead but are much more difficult to fit. The board is steadied by a long 4BA screw and a 34mm spacer between its centre and the case floor.

Unfortunately, there does not seem to be a bezel specifically designed for phosphorescent displays. Or if there is, it's not available on the hobbyist market. So, to

Table 1 — Wafer Switches

S1 — S3 are all made up from RS Components Miniature Switch Kits. Each comprises a mechanism, **Stock No. 327-311 (total 3 required)**, fitted with wafers and spacers as follows:

S1 **2 off 1-pole, 12-way wafers, Stock No. 327-349** spaced 40mm apart, using 20 spacers (10 per side)

S2 **2 off 2-pole, 6-way wafers, Stock No. 327-355** spaced 13mm apart, using 8 spacers (4 per side)

S3 **1 off 3-pole, 4-way wafer, Stock No. 327-361** spaced back from mechanism by 6 spacers (3 per side)

Mechanism end-stops set for correct rotation limits (S1 used as 8-way only).

Total of 34 spacers used (**4 packs Stock No. 327-327 required (10 spacers per pack)**).



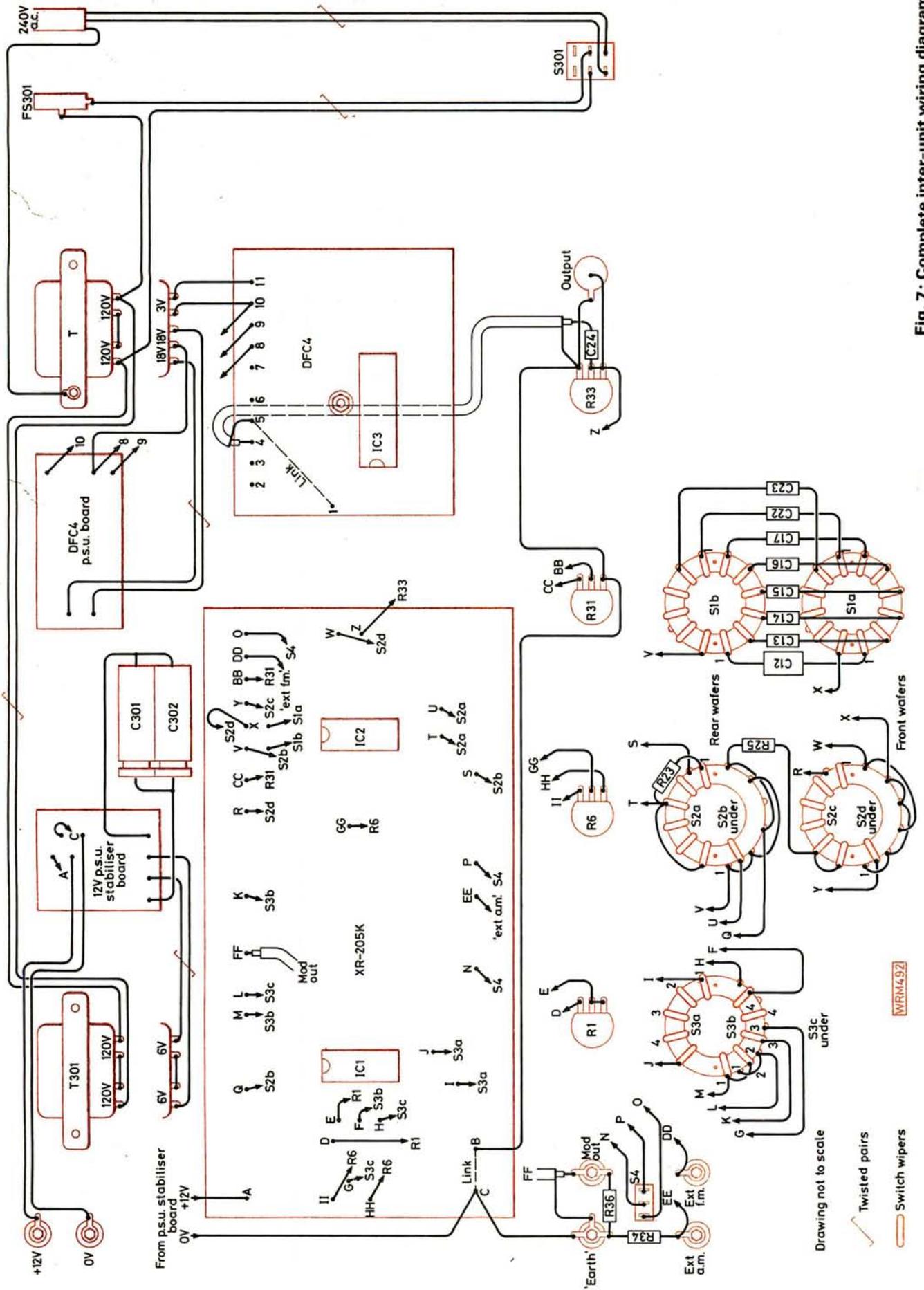



Fig. 7: Complete inter-unit wiring diagram

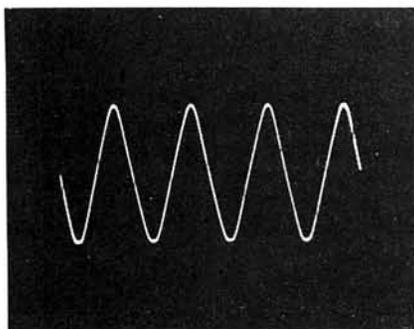


Sinewave

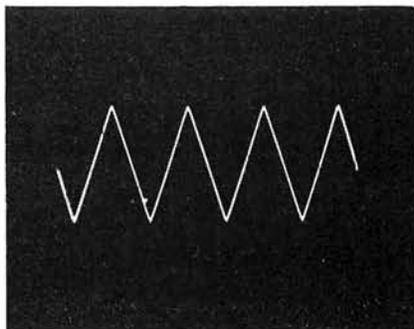


Triangular wave

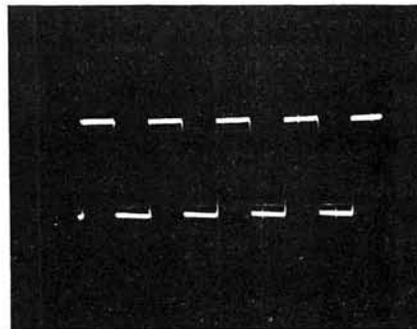


Squarewave

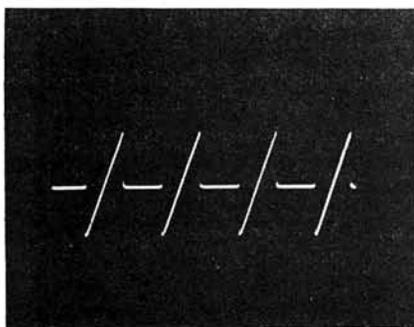

Ramp

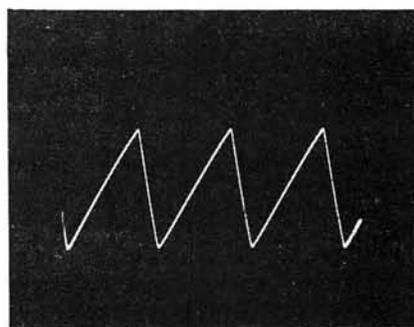

Sawtooth

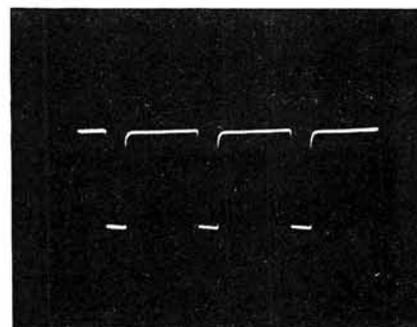

Pulse

The six basic output waveforms

finish off the display cut-out neatly, we used a Vero bezel, adapting it to fit by removing the usual fixing screws and clamps, and securing it to the front panel by a few dabs of glue. As shown in the photographs of the finished unit, the "AM", "FM", "kHz" and "MHz" legends on the display are visible through the bezel window, though they are not used when operating without frequency offset. You may like to hide them by painting the ends of the display with photographic dead-black or blackboard paint.

The power supply components are mounted on another small piece of Veroboard, stood off the case rear panel with two 6BA screws and short spacers. The layout is shown in Fig. 6.

Details of all the inter-unit wiring are shown in Fig. 7. For safety reasons, all terminals carrying mains voltage (fuse-holder, on/off switch and both transformers) should be protected against accidental contact by heat-shrink sleeving or similar means.

Operation

There is not a great deal to say about operating the *PW* Modulated Waveform Generator. Read the advice given in the XR-205 data sheet, connect the generator to an oscilloscope, switch on and play around with it until you find out what it can do. You will come across some really intriguing waveforms, especially when you try modulating a very low frequency carrier, or doing simultaneous a.m. and f.m.

There are just three adjustments to make when you first switch on. One of these is the crystal trimmer in the DFC4, which requires some external source of reference such as another frequency counter or a medium wave receiver. Hints are given in the kit instructions.


The other adjustments are to R10 and R22 on the waveform generator board, which are adjusted for

Transparent film overlays of the front panel are available from the Editorial Office at Poole, price £1.60 including post and packing.


minimum distortion on sinewave outputs from IC1 and IC2 respectively. The XR-205, like most function generator chips, produces a sinewave by "distorting" the triangle wave output, rather than generating a true sinewave. The presets R10 and R22 control the amount of this "distortion" which is introduced. If you have access to an audio distortion meter then the job is very easy, as you just twiddle the appropriate potentiometer for minimum reading. Otherwise you can adjust by judging how good the sinewave looks on an oscilloscope. You will find that you have to compromise between pointed peaks and flattened peaks, but check that you haven't turned the level control up to the point where the XR-205 buffer amplifier is beginning to limit. Minimum sinewave distortion is typically 2.5 per cent, which is not as good as some of the more recent waveform and function generator i.c.s, but then they don't offer you a built-in balanced modulator.

No connection points are provided on the waveform generator p.c.b. for C20 and C21, and they were not initially fitted. However, when the prototype was first switched on, the modulation oscillator had a positive-going notch in its sinewave output, just before the negative peak. The suggested 22pF for C20 distorted the sinewave to an extent that could not be corrected by adjustment of R10, but it was found by experiment that about 17pF (15pF and 2.2pF in parallel) connected across terminal pins "F" and "H" did the trick.


Some examples of the waveforms produced by the prototype generator are shown in the photographs. The XR-205 data sheet shows many more waveforms and describes how they can be achieved. Note that it is not possible to produce the classic over-modulated a.m. waveform with this generator because of the use of a balanced modulator. The amount of frequency modulation or sweep achievable from the internal modulation oscillator is limited, but is a maximum when the CARRIER

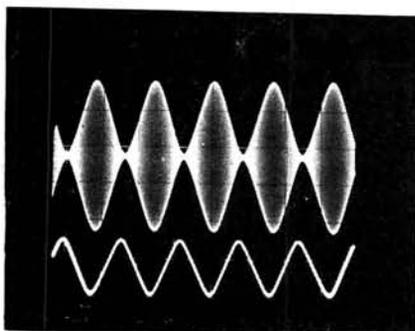

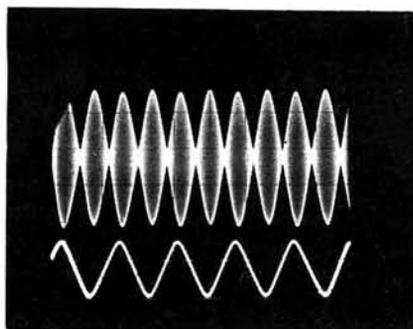
A 90% modulated a.m. waveform (top). Note how the envelope follows the modulating waveform shown on the bottom trace



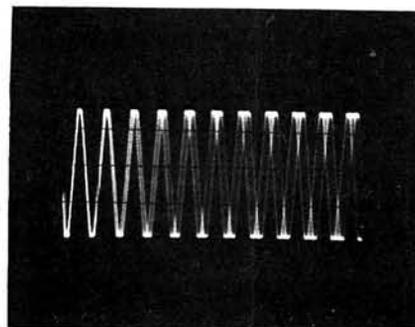A d.s.b. suppressed carrier a.m. waveform (top). Note the two envelope peaks per cycle of the modulating waveform



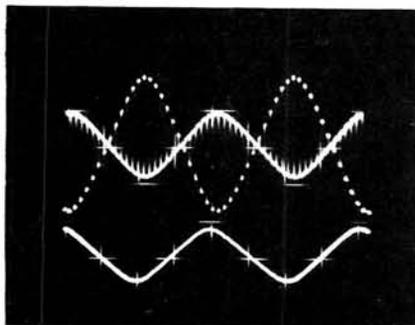A frequency-modulated carrier. The oscilloscope trace is triggered, and therefore steady at the left-hand end



One of the weird waveforms you can produce. Suppressed-carrier mod of pulses by an a.f. sinewave. Note the polarity reversal of the pulses on each half-cycle

All the waveform photographs in this article were taken from the screen of a Telequipment D43 oscilloscope, using a Shackman 7000 camera and Polaroid 3000ASA film. Exposure was $\frac{1}{4}$ s or $\frac{1}{2}$ s at f:8.

FREQUENCY control R31 is set fully anti-clockwise. Using an external modulating source, a frequency sweep range of 7:1 or more can be produced.

If a wire-wound potentiometer is used for R31, the output frequency will change in very small but noticeable steps when getting up into the r.f. region. This is of course due to the wiper moving from one turn of the track winding to the next, and is a problem in all CR oscillators operating at r.f. If continuous change of frequency is required, a good quality carbon track potentiometer should be used in this position.

Remember that you must turn the CARRIER LEVEL control R6 away from its null point whilst using the frequency counter.

EARLY VALVES

▶▶▶ continued from page 24

in this case the grid connection was brought out through the side of the bulb for short wave oscillator use.

The "LS5B" later became favoured as a frequency doubler for output on 20m (14MHz), they were also used for similar work on 10m (28MHz). In a few cases, uncapped valves were used on this wavelength and the shorter 5m (60MHz) wavelength, but reduced rating was normally applied.

It is of interest to note that at the same period the American experimenters were using a very similar valve for their transmitters, this was the "UX210". It had originated from a demand for a power valve for low frequency amplifiers, to drive the then new Rice-Kellogg moving coil loudspeakers. It was similarly priced to the "LS5", being nine dollars compared with two pounds ten shillings (£2.50).

The first dull emitter valve specially produced for transmitter use was the Marconi-Osram "DET1" (40 watt) quickly followed by an equivalent from Mullard known as "DO40". Both these valves were characteristically better than any of the earlier types, having a slope of around 2mA/V. The "DET1" advertisements of the day quoted: "Owing to the remarkable results obtained with "LS5" valve as a 10W transmitter, this type has been developed".

These valves were fitted with a large low capacity cap and it was claimed that the valve would oscillate down to 5m (60MHz). The "DO40" quoted that it was suitable for

Bright Emitters

Company	Type No.	Volts	Amps	M	R	M/R
BTH	R	4	0.65	6.5	25kΩ	0.26
Ediswan	R	4	0.65	8	25kΩ	0.324
Osram	R	4	0.7	9	35kΩ	0.26
Mullard	ORA	4	0.7	8	26kΩ	0.24
Cossor	P1	4	0.72	6.6	18kΩ	0.24
Cossor	P2	4	0.72	12	50kΩ	0.238
Radion	GP	4.25	0.48	9	45kΩ	0.20
Osram	R5V	5	0.65	9	30kΩ	0.30
Osram (RAF)	C	5	0.75	6	19kΩ	0.316
Mullard	HF	4	0.7	7.3	32kΩ	0.225
Mullard	LF	4	0.7	6	23kΩ	0.26
Osram	V24	5	0.45	6	22kΩ	0.27
Osram	Q	5	0.45	50	150kΩ	0.33
Osram	QX	5	0.45	20	100kΩ	0.25

short wave transmission, down to 40m (7MHz). Both valves cost five guineas (£5.25) each.

From the foregoing, it will be appreciated that early experimenters were faced with relatively expensive items and the cost was very much greater than nowadays. For example, in the early twenties, when the average weekly wage for a craftsman was around thirty to thirty-five shillings (£1.50 to £1.75), to buy a "R" valve took half a week's money, and an "LS5" required nearly two weeks' pay! ●

The EUROCOMM Range

27 MHz CB Transceivers to MPT 1320

EUROCOMM 40

A compact 40 channel unit offering high sensitivity, ease of operation and switched Channel 9 selection

Features: Large LED Channel Display
Illuminated Signal/Power Meter
Tx and Rx Status LED's
Hi/Lo Power Switch
CB/PA Selector Switch
Volume and Squelch Controls
Internal Speaker

The Eurocomm 40 is supplied complete with fused power cord, mobile mount, microphone and mounting clip.

PRICE: £69.00 inc. VAT



EUROCOMM DX40

A robust unit ideal for mobile and base use.

Features: Large LED Channel Display
Illuminated Signal/Power Meter
Tx and Rx Status Indicators
Hi/Lo Power Switch
CB/PA Switch
Volume and Squelch Controls
Internal Speaker

The Eurocomm DX40 is supplied complete with a universal mounting bracket, fused power cord, microphone and clip.

PRICE: £79.00 inc. VAT



TONE SIGNALLING PRODUCTS


A range of boards are available to fit the Eurocomm range. When switched in, these enable only breakers with the appropriate tones included in their transmissions to open the squelch. Ideal for users who need to monitor a channel continuously for a call, but find the interference annoying. These small sized modules interface with virtually any type of two way radio equipment, and when switched out allow normal operation of the rig. Units are programmable for multiple calling tones. Details on request.

PRICES:

CTCSS (Tone Mute) — £31.00 to £61.00 inc VAT

5 Tone Selcall — £99.00 inc VAT

TRADE ENQUIRIES INVITED

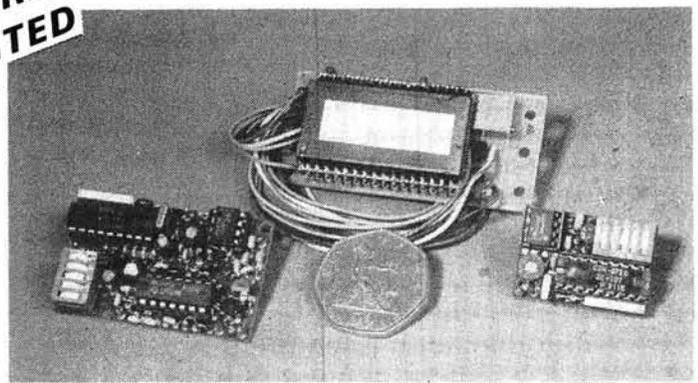

STABILISED POWER SUPPLIES

Rugged professional quality units at realistic prices

5 Amp — £18.40 inc VAT

7 Amp — £32.00 inc VAT



Zycomm Electronics Ltd.

G3ZYC G8CNB G3NJK G3ZYD G8ZYC

47/51 Pentrich Rd., Ripley, Derby DE5 3DS

Tel Ripley (0773) 44281 Telex 377477

We supply a comprehensive range of test equipment, power supplies and PL259 plugs/accessories — prices on request.

Benefit from our experience in the supply and maintenance of commercial and amateur equipment.

MAIL
ORDER

Photo Acoustics Ltd

MICRO COMMUNICATIONS DIVISION

BUDGET
ACCOUNT

WE ARE AUTHORISED DEALERS FOR:-



TR-7730



FT-707



IC-251



MULTI-750E

H.F. Transceivers

	P&P
Trio TS830S	£694.83 (4.50)
Trio TS530S	£534.98 (4.50)
Trio TS130S	£529.09 (4.50)
Trio TS130V	£445.05 (4.50)
Yaesu FT1	£1295.00 (4.50)
Yaesu FT902DM	£285.00 (4.50)
Yaesu FT101ZDFM	£685.00 (4.50)
Yaesu FT707	£569.00 (4.50)

2 Metre & 70 cms

	P&P
Trio TS770E	£784.99 (4.50)
Trio TR900	£374.90 (4.50)
Trio TR7730	£247.94 (4.50)
Trio TR2300	£166.75 (4.50)
Trio TR8400	£334.88 (4.50)
Trio TR9500	£449.88 (4.50)
Trio TR2500	(T.B.A.)

2 Metre & 70 cms

	P&P
Icom IC251E	£499.00 (4.50)
Icom IC290E	£366.00 (4.50)
Icom IC25E	£259.00 (4.50)
Icom IC2E	£169.00 (2.50)
Yaesu FT290R	£249.00 (4.50)
Yaesu FT708R	£219.00 (2.50)
Yaesu FT208R	£209.00 (2.50)
Yaesu FT430R	£379.00 (4.50)
Yaesu FT780R	£449.00 (4.50)
FDK M700EX	£199.00 (4.50)
FDK M750E	£299.00 (4.50)
AZDEN PCS3000	£219.00 (4.50)

FOR THE LARGEST RANGE IN C.B.
LCL 2740 COLT
UNIDEN CYBERNET
FIDELITY MIDLAND
ROTEL LOWE TX40
REFTEC (934MHz)

RECEIVERS

	P&P
Trio R1000	£297.85 (4.50)
Lowe SRX 30D	£195.00 (4.50)
Yaesu FRG7700	£329.00 (4.50)
Yaesu FRG7700M	£409.00 (4.50)
SX200N	£264.50 (4.50)
R517 Airband Receiver	£49.45 (1.00)
Academy CB-Airband	£14.95 (1.00)

COMPUTERS
CASH & CARRY PRICES
AVAILABLE ON:
APPLE
PET
VIDEO GENIE

AERIALS
J BEAM
CUSHCRAFT
AVANTI
HOXIN
HOKUSHIN
G-WHIP
HALBAR

ACCESSORIES

	P&P
Ferrite rings	£0.40 each
AR40 rotatory	£65.50 (4.50)
DAIWA DR7500R	£107.98 (4.50)
9502 rotator	£56.50 (4.50)
5 amp PSU Barmec	£14.75 (1.25)
10 amp PSU PP1310	£49.50 (4.50)
20 amp PSU Yaesu	£125.00 (4.50)
FX1 Wavemeters	£33.00 (1.25)
DM801 G.D.O.	£60.03 (1.25)
SP15M SWR & Power Meter	£29.99 (2.50)
SP300 1.8-500 Mhz	£79.99 (2.50)
SP400 130-500 Mhz	£59.99 (2.50)
CNA 1001 Auto ATU	£129.95 (2.50)
CNA2002 Auto ATU	£228.00 (2.50)
SW110A SWR/Power	£31.33 (1.25)
CN820A Twin Pointer SWR	£52.81 (2.50)
LAR VHF Omni Match	£34.99 (2.50)
LAR HF Omni Match	£69.25 (2.50)
FULL RANGE OF MICROWAVE MODULES	

— 24 HOUR ANSWERPHONE CREDITCHARGE PART EXCHANGE —
58 HIGH STREET, NEWPORT PAGNELL, BUCKS.
TEL: 0908 610625



MARCO TRADING

DEVELOPMENT PACKS: These famous resistor packs are now available in two sizes: Carbon film 5% resistors, every value individually packed in a clearly labelled bag, 10 of every value in the E24 range between the values stated:

1/4 Watt Pack: 10 ohm to 1 Meg (610 resistors) **£5.00 per pack + VAT**

1/2 Watt Pack: 10 ohm to 2M2 (655 resistors) **£5.00 per pack + VAT**

MULTIMETER SPECIAL Russian type U4324 (Advertised elsewhere in this magazine for over £15.00 each recently).

d.c. Voltage: 0.6, 1.2, 3, 12, 30, 60, 120, 600, 1200.

a.c. Voltage: 3, 6, 15, 60, 150, 300, 600, 900.

d.c. intensity mA: 0.05, 0.6, 6, 60, 600, 3000.

a.c. intensity mA: 0.3, 3, 30, 300, 3000.

d.c. resistance: 0.2, 5, 50, 500, 5000, kOhm.

g.e. level dB: -10 to +12.



FANTASTIC SPECIAL PRICE:
£12.00 including PIP and VAT

TRANSFORMERS



British made transformers at very attractive prices.

Primary	Secondary	Current	1+	10+	100+
240v:	4.5-0-4.5v	400mA	50p	45p	35p
240v:	6-0-6v	100mA	58p	52p	43p
240v:	6-0-6v	500mA	65p	60p	48p
240v:	9-0-9v	200mA	75p	70p	58p

Manufacturers note: We can supply FROM STOCK, 1000+ quantities of the above transformers and adaptors below.

EUROPEAN ADAPTORS



These very high quality British made two pin European adaptors are ideal for driving Radios, cassette recorders, TV games, calculators etc. The adaptors fit the UK shaver socket.

REF.	D.C. Voltage	Current	1+	10+	100+
EOB	4.5V	200mA	50p	45p	32p
EM3	6V	200mA	£1.00	80p	55p
EO9	6V	400mA	£1.50	£1.25	85p
ET4	9V	150mA	£1.50	£1.25	85p

Please note that there is no extra P/P charge on the above transformers & adaptors.

Export please add Sea/Air mail at cost.

Callers welcome Mon-Fri 9-5.

This advert is only a fraction of our range, send 25p for our latest catalogue. Please add 35p P/P to all orders. (Free over £5.00). Add 15% VAT to total. Send orders to:

Dept. PW2, MARCO TRADING,
The Old School, Edstaston, WEM, Shropshire SY4 5RJ.
Tel: (094872) 464.

Special Offer Test Equipment Catalogue available upon request. Send S.A.E. or Telephone.

All orders despatched by return of mail.

ZENER DIODES: 400m/w, 3V to 33V 8p each, 100 for £6.00 (your mix). 1 Watt, 3V to 200V 15p each, 100 for £12.50 (your mix).

I.C. SOCKETS: 6 pin = 7p, 8 pin = 8p, 14 pin = 10p, 16 pin = 11p, 18 pin = 13p, 20 pin = 16p, 24 pin = 20p, 28 pin = 28p, 40 pin = 32p. QUANTITY PRICES ON APPLICATION.

CERAMICS: 63V Working. Subminiature. Low Tolerance. 1.8pF-100nF. 4p each.

TANTALUMS: 35V, 0.1µ, 0.15µ, 0.22µ, 0.33µ, 0.47µ, 0.68µ, 1.0µ = 12p each. 2.2µ, 3.3µ, 4.7µ, 6.8µ, 35V = 14p each. 10/35V 18p, 22/35 38p, 47/10V 25p, 33/10V 22p, 100/3V 20p, 68/3V 20p each.

L.E.D.s: 3mm RED 12p each, Green 18p each, Yellow 18p each, incl. Clips. 5mm RED 12p each, Green 18p each, Yellow 18p each, incl. Clips. 100 Red (3 or 5mm) for £5.50 excluding Clips.

SKELETON PRE-SETS: 100Ω to 1M Vertical & Horizontal, all = 6p each, 100 (your mix) for £4.50. BRIDGE RES'S: 1 1/2A 50V 38p, 2A 200V 44p, 25A 50V £2.38, 25A 100V £2.41.

TRANSISTORS: BC107/8/9 10p, BC147/8/9 8p, BC182/3/4 9p, BC172 8p, BF200 28p, BC212/3/4 9p, 212L/3/4L 10p, BF180/81 29p, AC128 20p, AD161/2 45p, 2N3055 45p, 2N3819 23p, 2N3053 20p, BC125 10p, BF262/3 30p, 1N4001 5p, 1N4007 8p, 741 20p, NE555 25p, LM380 80p.

CMOS: 4001B 20p, 4011B 20p, 4076 90p, 4081 20p, ZN414 90p.

ELECTROLYTICS: A is Axial; R is Radial; 1/63C A 7p, 2.2/25 R 4p, 4.7/25 R 5p, 10/16 R 4p, 22/16 R 4p, 22/63 R 8p, 25/25 A 3p, 47/16 R 5p, 47/25 A 6p, 100/3 A 5p, 100/16 R 6p, 220/16 A 9p, 470/16 A 12p, 1000/16 A 16p, 1000/63 A 62p, 4700/16 R 55p, 2200/40 A 65p, 4700/63V 1/£1.90.

RESISTORS FROM STOCK!

Over 4 million 1/4W and 1/2W 5% carbon film resistors *in stock*.

Prices as follows:-

1/4W 1,000 + per valve **£3.00**

1/2W 1,000 + per valve **£3.50**

Full details and larger quantity prices upon application.



COMMTRON CB 40F

CB is a mobile short-range telephone system. You require a licence to use it, £10 p.a. from Post Offices.

The CB 40F is Commtron's first rig purpose-built to the UK 27MHz f.m. CB specification MPT 1320. They have some years of experience in producing transceivers for the US market under several well-known brand-names and it certainly shows in the standard of design of this set.

FACILITIES

Full 40 channels with red l.e.d. digital readout. Switch for Channel 9 priority selection. Illuminated power/"S" meter. Hi/Lo power switch. Public Address facility. Socket for 8/16 Ω external loudspeaker. Supplied with microphone; mobile mounting bracket; microphone bracket; 12V d.c. power lead 1.5m long with in-line fuse; instruction manual.

DESIGN

Looks very competent, with clean internal layout. Main board, single-sided and with all components identified, carries all circuitry except channel selector switch and display decoder which are on a small separate board. Extensive r.f. filtering on control and audio leads coming off-board.

A p.l.l. synthesiser is used, with receiver i.f.s of 10.695MHz and 455kHz, both including ceramic filters.



CONSTRUCTION

Generally good, although a few solder balls and wire ends stuck to p.c.b. reveal a need for improved quality control.

HANDBOOK

The 14-page instruction manual supplied covers specifications, brief description, operating controls and features, installation, operation, alignment, main p.c.b. layout, circuit diagram and block diagram. Although (like the rig) the handbook is produced in Korea, it is in good English and sets a standard others might follow.

HOW IT HANDLES

First, the moans: 1. The microphone plug is of the non-latching DIN variety (5-pin). If it is pulled out, the receiver output disappears because the loudspeaker earth return is via the back contact of the p.t.t. switch. 2. The knobs are chrome finish and could cause trouble with reflections when in a car. Worse still, they are very smooth, and the channel selector takes quite a grip to turn it. 3. The receiver audio output comes out of the p.a. loudspeaker when on radio, which would not please neighbours or passers-by!

Now the good points: 1. The audio quality is good on both transmit and receive, with enough clean audio from the loudspeaker for even a noisy car. 2. The


transmitter output will withstand short-term accidental short-circuit or open-circuit antenna conditions without disappearing in a puff of smoke, as proved during lab tests.

We tested two rigs mobile, using Avanti Moonraker AV-241M antennas, which are base-loaded, 1.22m long with mag-mount base. One rig was also tested as a home-base, using an AV-241M in the loft with a makeshift ground-plane of two 3m lengths of aluminium strip arranged as an "X". Results were good, with mobile-to-mobile contacts up to about 5 miles in a semi built-up area, despite considerable sideband interference from the Continent during afternoon tests. Monitoring during the evening showed much activity but no problems with interference from strong stations on adjacent channels.

HOW MUCH?

You should find the CB 40F in the shops at around £75.

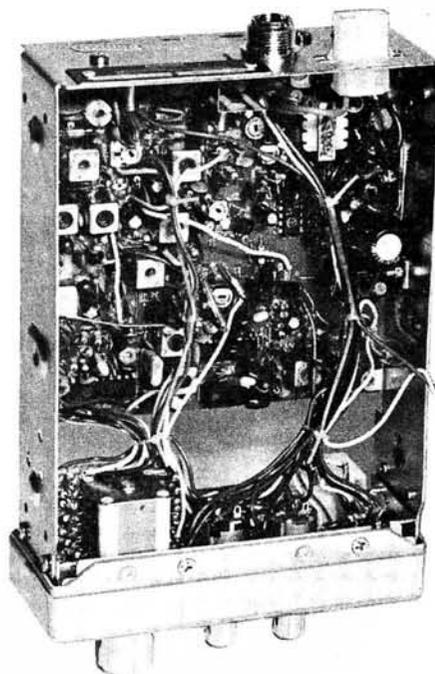Our thanks to Des Walsh of Tritel Group, 1043 Leeds Road, Thornbury, Bradford BD3 8ES, telephone 0274-665670, Commtron importers, for his co-operation, and to Stour Valley Communications, 112 Stour Road, Christchurch, Dorset, who lent the review rigs.



IN THE LAB

Feature	Spec	On test
<i>Transmitter</i>		
Power out: HI	4W	3.8W
LO	0.4W	0.45W
Spurious:	<0.25 μ W	— ⁽¹⁾
Adjacent channel:	-60dBc	-80dBc ⁽²⁾
Frequency error:	<1.5kHz	<100Hz
<i>Receiver</i>		
Sensitivity: ⁽³⁾	<1 μ V	1 μ V
Selectivity: (\pm 10kHz)	-60dB	—
Audio output: (8 Ω)	3-5W	—

Feature	Spec	On test
<i>General</i>		
Consumption:		
Standby	250mA	230mA
Transmit	<1.5A	1.1A
Size:	54 x 132 x 194mm (excluding projections).	
Weight:	1.4kg approximately.	

Notes

1. Test equipment available for these tests would not measure below 0.4 μ W. All spurious outputs below this level.
2. dBc means dB relative to the carrier power.
3. For 20dB (S+N)/N, with 1kHz tone and 1.5kHz deviation.
4. All tests on 13.8V d.c. supply.

ZX80/ZX81 Users Club

The Club was founded early in 1980 as the ZX80 Users Club, an independent user group run by enthusiasts of the ZX80 microcomputer. It has now been expanded to cover the ZX81.

The Club caters for all types of user and produces a regular newsletter containing articles on basic computing, educational computing and, of course, ZX80 and ZX81 hardware and software. A special feature of the newsletter is the "Cambridge Hot-Line" with the latest news direct from Sinclair Research Ltd.

As well as technical support, the Club has set up a software bank available to members at minimal cost.

The annual membership fee, which includes the cost of the newsletters and software bank index, is £6 for UK members and £10 for overseas members.

Further information will be supplied in return for an s.a.e. to: *ZX80/ZX81 Users Club, PO Box No. 159, Kingston upon Thames, Surrey KT2 5UQ.*

Cushcraft Antennas

The sole importer of the entire range of Cushcraft Antennas is now: *Communications Products Ltd., PO Box 23, Halifax HX3 6AN.*

Repeater News

70cm repeater GB3NF at QRA location ZK14H, map reference SU428048 which in layman's terms is adjacent to Southampton Water in Hampshire, has become operational on channel RB11. The site is 130 feet above sea level and the antenna, a single 6dB gain colinear, is 80 feet above ground level. Further information is available from G4KCM, QTHR.

2m repeater GB3WH closed-down at its original site on 20 November 1981, and on the same day GB3VA at Brill commenced operation on R4. Approximately two weeks after that date GB3WH will rise, phoenix like, from a new site south of Swindon on R2.

A proposal is under preparation to establish a 70cm repeater on the island of Guernsey, site etc. details are not known at this time, but if the licence is granted, this installation would be the most southerly unit in the UK. In addition to its primary function, the repeater will provide a very useful test facility for u.h.f. propagation over a seaward path.

A great amount of interest has been shown in the re-opening of u.h.f. repeater GB3WS, following the enforced close-down by the R.S.G.B. The Society hope to re-issue the licence to a new controlling group in the near future.

PW Exe

Those readers residing in the Irish Republic who intend building the PW Exe microwave transceiver, may be interested to learn of a Dublin supplier of parts for this project.

Two suitable annealed copper parabolic dishes are available, one is 500mm diameter and the other is 490mm diameter with a side lobe shielding cylinder, focal length for both dishes is 130mm. Either dish costs IR£12.00 each and is supplied with a protective polyurethane coating.

Also available are 3mm and 6.5mm acrylic rods for focus mounted doppler modules at £3.00 per 2 metre length (p&p not included).

Further details are available in exchange for an s.a.e. from: *John F. Hitchcock (jnr.), 99 Avondale Park, Raheny, Dublin 5, Ireland.*

Moving On

Hull and District Amateur Radio Society notify me that they have moved. As from 4 December 1981 their new base will be at West Park Recreation Centre, Walton Street, Hull. Further details from: *The Secretary, H. V. Cunliffe G6DUL. Tel: (0482) 447355.*

Golden Anniversary

Scarborough Amateur Radio Society celebrates its 50th anniversary in 1982 and it is planned to issue a certificate to commemorate this occasion.

To qualify for the award contact must be made with the club station, G4BP, and five members of SARS during 1982.

Full details of how to claim the award and a list of SARS members can be obtained by sending an s.a.e. to: *D. E. Mappin G4EDR, 39 Clarence Drive, Filey, N. Yorkshire YO14 0AZ.*

Stolen Equipment

Two local amateurs report that during November 1981 their cars were broken into and the following equipment stolen.

One Kyokuto Digital 2—Model FM144 which has 144.690MHz programmed into the personal channel. Also a unique Jaybeam end-fed window mount antenna. Stolen on 9 November from G2HCG, QTHR.

One Trio TR-9000, serial No. 1041020 minus mobile bracket and will probably have dents in sides, one Cobra 40 channel f.m. mobile CB rig and one Oscar, SMC, 40 channel f.m. mobile CB rig. Stolen on 25 November from G8YBT, QTHR.

If you are offered, or have any information of these items, please contact either the owners or Poole Police, tel: Bournemouth 22099.

Can I Help You!

Are you the secretary, organiser or general dog's body of your local radio club or any other group whose functions may interest readers of *PW*. If so, let me know and I will endeavour to publicise your rally, get-together whatever, through this column. Remember though, we compile the magazine some time ahead of publication day (e.g. this note was written in November), so, the earlier I can have details, the better.

Alan Martin

Next month in **Pw**

ON SALE
5 FEB

EXTRA

PULL-OUT



World Amateur Prefix List
plus Maps of European
Prefix areas and QRA
Locator Squares


Pw
**IAMBIC
KEYER**




Take the strain out of your c.w. — build our iambic keyer to complement that iambic key you have always wanted. This unit is simple to build and will interface any iambic key to your rig


plus

2 SIMPLE HF ANTENNAS

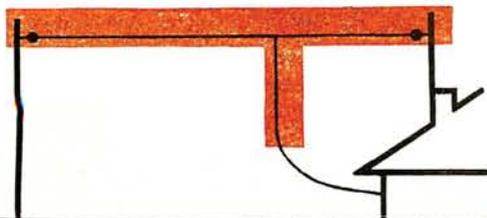

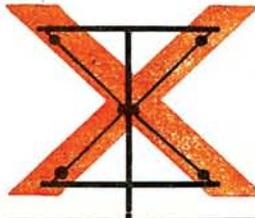Working h.f. from a restricted site? Then you will find these two compact antennas for the h.f. bands interesting and worth the small effort required to construct them. Your bank balance will not suffer either



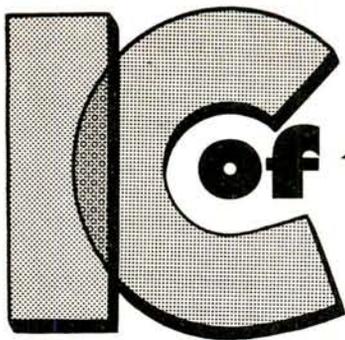

of the month

Brian DANCE M Sc

National Semiconductor LM10 Op Amp and Voltage Reference

Monolithic operational amplifiers have been employed in a large variety of applications and in many cases a common type such as the 741 is quite adequate. For some applications, however, there are good reasons for using a more expensive type of operational amplifier featuring special parameters that the more common types cannot equal.

One example of a high performance operational amplifier is the fairly new National Semiconductor device type LM10. This will operate from a total supply voltage as low as 1.1V and a supply current of only 270µA. It is thus very suitable for use in portable equipment powered by a battery: indeed, it can be operated from a single dry cell near to the end of its life. The low supply current required by the LM10 ensures that maximum cell life is obtained from the battery.

The internal circuit of the LM10 device is shown in Fig. 1 in block form together with its connections. It can be seen that the device contains not only an operational amplifier, but also a 200mV reference voltage source, together with its own comparator amplifier, which acts as a buffer for the reference voltage source to prevent any current taken from the reference output from interfering with the reference voltage.

The LM10 is available as a series of devices with slightly different type numbers, but all having the same internal circuit. The LM10, LM10B and LM10C versions can be operated from any supply voltage between 1.1V to 45V total, although it is wise to regard the maximum as 40V to allow for a margin of safety. If balanced supplies are employed, the maximum is about +20V lines. The maximum differential input voltage is quoted as ±40V; the input voltage may exceed the supply voltage provided that the voltage from the input to any other terminal of the device does not exceed this maximum differential input voltage. Lower cost versions, LM10BL and LM10CL have a maximum total voltage supply limit of 7V, although it is again wise to regard 6V as the upper limit. The LM10 can be operated with its chip at temperatures as high as 150°C, whereas the more economical LM10B and LM10BL can only be operated at chip temperatures up to 100°C. The LM10C and LM10CL have a maximum chip temperature specified as 85°C.



All LM10 devices incorporate thermal overload protection circuitry. This means that if the temperature rises towards the point at which thermal damage could occur, the output current is automatically reduced by the circuit so that damage is prevented. However, it is unwise to use the device under conditions that are likely to cause the thermal overload circuitry to operate, since such high temperatures will render devices more likely to failure.

Basic Parameters

The input offset voltage of the LM10C and the LM10CL is typically 0.5mV (maximum 5mV) which is better than the corresponding values of 2mV and 6mV

respectively quoted for the LM741C. However, when one considers the input currents, the performance is ten to a hundred times better than the 741C. For example, the input offset current of the LM10C and LM10CL is only 3nA maximum, whereas that for the 741 is 300nA. The corresponding values for the LM10 and LM10B are even smaller, the typical offset current being quoted as 0.25nA and the maximum 1.5nA.

A further advantage of the LM10 series of devices over more conventional operational amplifiers is that the output potential from the devices can swing to within 15mV of that of the power supply lines. Thus one can obtain output voltage swings of about 40V using the LM10 series, with the exception of the LM10BL or LM10CL.

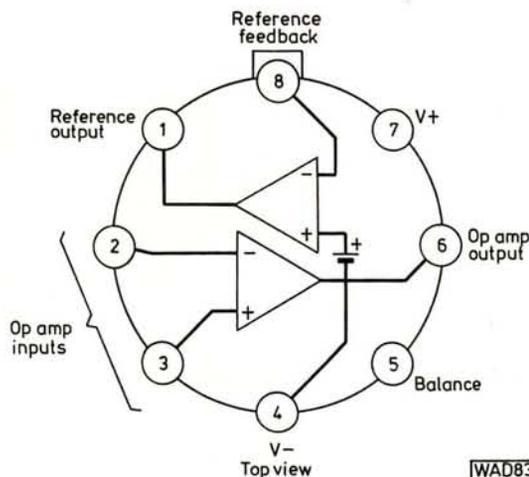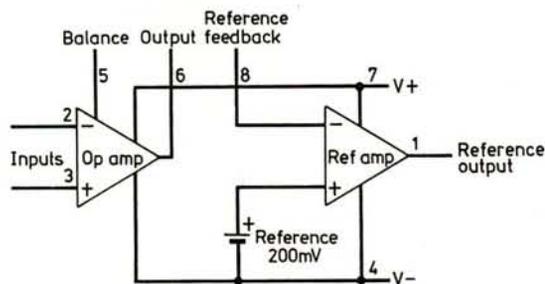

WAD838

Fig. 1: The LM10 series connections and basic internal circuit

The 200mV internal reference voltage source employs the bandgap of silicon as the voltage standard. Special techniques are employed to compensate for the effect of temperature changes on the reference voltage: typical voltage drift of the reference source being quoted as 0.003%/°C for the LM10CL.

Variations of power supply current required against operating temperature are shown in Fig. 2.

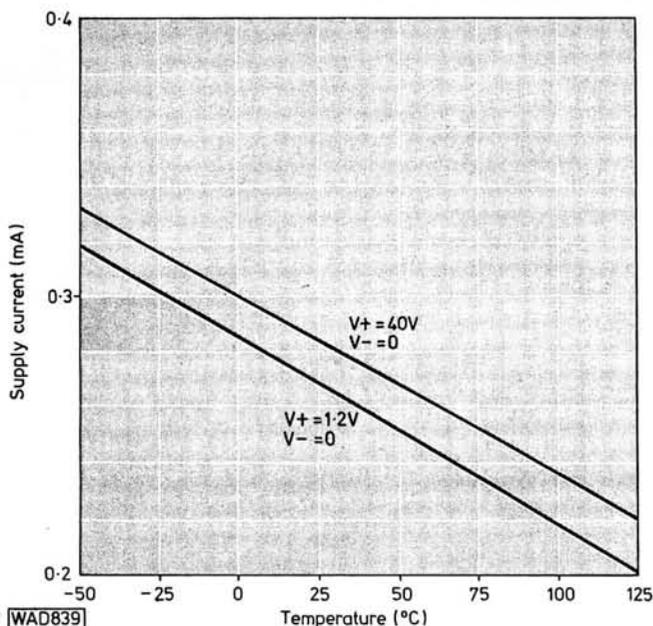


Fig. 2: Variation of supply current with temperature

Circuit Applications

LM10 series of devices have been designed for use in a wide variety of applications, such as voltage and current regulators (from low voltages to some hundreds of volts) providing greater precision than earlier monolithic devices: thyristor control circuits; transmitters for analogue signals, etc. Detailed information is available on the data sheet for the LM10, National Semiconductor Notes AN211 entitled "New Op Amp Ideas" and TP-14 entitled "Low Voltage Techniques." The following examples have been chosen to illustrate the wide variety of possible uses to which the versatile LM10 can be put.

Light Detector

The circuit of Fig. 3 employs the LM10 in a "floating mode" without any ground voltage reference. The photodiode is connected directly between the inverting and non-inverting inputs of the LM10; the output of the device is directly connected to the positive supply line so as to disable one half of the internal output stage. When the non-inverting input at pin 3 is positive with respect to the inverting input, no current flows in the internal output stage. As the potential at pin 3 falls, whilst light falls onto the photodiode, current passes from the positive line to pin 6.

The internal reference circuit provides the bias from pin 1 which determines the switching threshold of the circuit. At the switching point, the voltage across the photodiode equals the offset voltage of the operational amplifier; this is quite small and leakage current in the diode is negligible. A few hundred microvolts across the photodiode will produce the full short circuit current in the LM10.

The circuit of Fig. 3 employs R3 to provide hysteresis. Hysteresis is an effect which, in this case, renders the light level for switching to the conducting state slightly greater than that for switching back to the non-conducting state. The presence of some hysteresis ensures that the circuit does not keep switching between the two states for very small fluctuations in the light level. The values shown provide about 1mV of hysteresis for a 5V output swing,

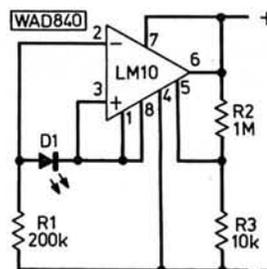


Fig. 3: A light detector using the LM10

although this disappears at frequencies above 10Hz owing to loss of gain. This circuit is not intended for fast operation, as the LM10 is fully frequency compensated. High accuracy should not be expected at switching frequencies exceeding 100Hz.

Logarithmic Light Sensor

The circuit of Fig. 4 also employs a photodiode to sense the presence of light, but the output is linearly related to the logarithm of the current passing through the photodiode and hence to the logarithm of the light level. This enables variations in light level over four decades (10 000 to 1) to be accommodated with good resolution at low light levels. The circuit is balanced at the middle of the range at which point R3 should be chosen so that the current through it is equal to the current through the photodiode, with the light level corresponding to the desired middle of the range. The output current varies from 1mA to 5mA over the working range set by the value of R3.

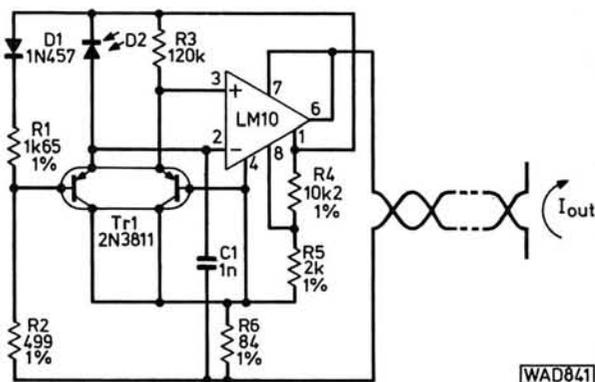


Fig. 4: A logarithmic light sensor circuit. This has a response similar to the human eye as far as variations in intensity are concerned

The logarithmic conversion characteristic of this circuit is temperature compensated by the resistor R6 which should be made of fine copper wire wound on a suitable former. The reference feedback circuit from pin 1 to the comparator input of pin 8 determines the voltage between pins 1 and 4; the latter is equal to the 200 mV reference multiplied by $(R4 + R5)/R5$ or 1.22V with the values shown. The setting of this reference output from pin 1 to 1.22V provides a current through R2 which is proportional to the absolute temperature, (owing to the presence of the forward biased junction of D1), and this "level-shift" voltage has a temperature coefficient matching that of R6. The capacitor C1 will prevent instability if a photodiode with a high capacitance is employed.

Meter Amplifier

The circuit of Fig. 5 shows how the LM10 can be used to increase the sensitivity of a 0-100μA meter to provide a

full scale deflection of 10mV or 100nA. The total current drain of this circuit from the power cell is less than 500µA; this corresponds to a life of some 3 to 6 months with an "AA" size cell or over a year with a "D" cell. Readers may feel an ON/OFF switch is unnecessary!

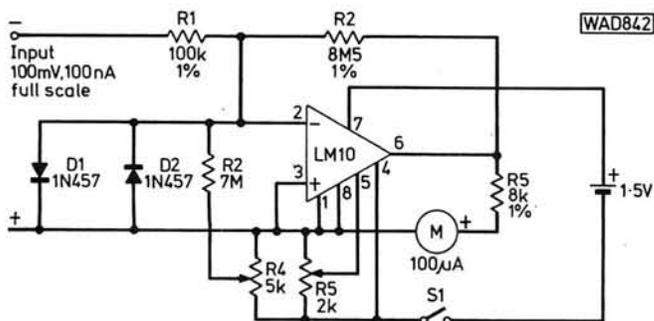


Fig. 5: A 10mV, 100nA meter circuit using the LM10

A particular advantage of this circuit is that its accuracy can be maintained over a temperature range of 15°C to 55°C. Offset voltage errors are nulled by adjusting R5, the zero setting control. The bias current can be balanced out using R4. As these trimming adjusters operate from the reference voltage output from pin 1, the settings are stable against variations of power supply voltage from the cell.

Input clamping diodes D1 and D2 protect the circuit from large overloads. The limited output swing provided by the LM10 provides protection for the meter during overload conditions. If the meter amplifier circuit is used to construct a multi-range meter, the internal reference voltage from pin 1 can also be employed in resistance measurements, eliminating the frequent adjustments required for setting of multi-range meters on resistance ranges as the cell voltage falls.

Electronic Thermometer

An electronic thermometer for the range -55°C to +150°C is shown in Fig. 6. The LM134 sensor develops a current which is proportional to the absolute temperature. The LM10 provides the required amplification and voltage

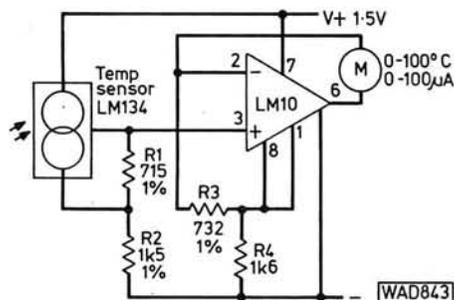


Fig. 6: An electric thermometer

offset so that direct readings in either °C or °F can be obtained. R2 is used to set the zero temperature and R3 sets the width of the temperature range that the circuit can accommodate. Some errors may occur in this circuit if the cell voltage falls below 1.5V, since the LM134 characteristics are unspecified below 1.5V.

Microphone Amplifier

For audio applications the frequency response of the LM10 device is somewhat limited, but it is possible to obtain a gain of about 10 at frequencies up to 10kHz. In

order to obtain a higher overall gain, for use as a microphone amplifier, the circuit of Fig. 7 employs the reference voltage amplifier as an audio preamplifier stage with a gain of 100. The output from pin 1 of this preamplifier stage is coupled by R3 and C1 to the inverting input of the operational amplifier. The values of R7 and R3 set the gain of this operational amplifier stage at 10 and at this low gain frequency response is level up to 10kHz.

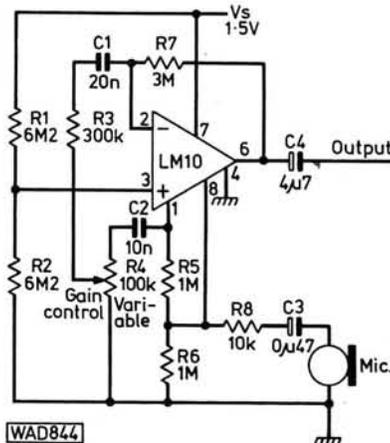


Fig. 7: A microphone amplifier with a gain of 60dB using one i.c.

The overall gain of the circuit is 1000 (60dB) with a 10kHz bandwidth when no load is connected to the output, falling to a 5kHz bandwidth with a 500Ω output load. The input impedance is 10kΩ. The circuit has been designed so that no steady current flows through the gain control, as this reduces noise when the control is operated. However, a slightly simpler circuit could have been designed using R5 as the gain control with a steady bias current (less than 75nA) flowing through it.

Laboratory PSU

A general purpose laboratory type power supply unit using two LM10 devices is shown in Fig. 8. The output is fully adjustable from 0V to 50V, this output voltage being equal to the value of R3 in ohms divided by 10000. A three-stage emitter follower circuit (TR3 to TR5 inclusive) is employed to provide the output current of up to 1A.

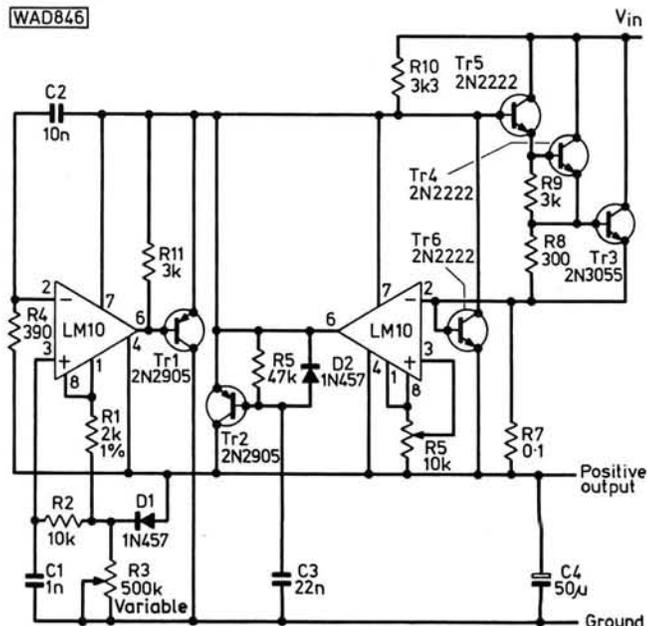



Fig. 8: A laboratory power supply providing 0V to 50V at outputs of up to 1A

continued on page 57

* Special
Offer

PWL
PWL
PWL
PWL

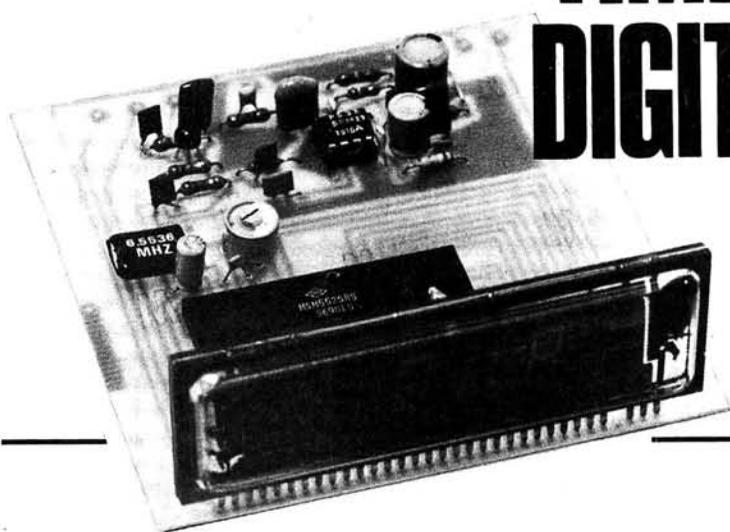'TIMESTEP' DFC4 DIGITAL FREQUENCY COUNTER KIT



A digital readout adds a touch of class to a receiver as well as giving a more accurate and easily read indication of frequency. Our special offer this month is a complete kit of parts to enable you to add a 3½ digit readout with a large bright phosphorescent display to your a.m. or f.m. receiver.

The module can also be used as a frequency counter and is used in our interesting cover project, the modulated waveform generator, to provide an accurate readout of the carrier frequency.

The kit is supplied complete with all components for the counter module, which is constructed on a single p.c.b. The mains transformer and other components for the power supply are also supplied with the kit.

The DFC4 will measure frequency up to 150MHz and can cope with 22 different i.f. offsets for a.m. and f.m. transmissions. The sensitivity is 1mV a.m. and 10mV f.m. and the kit comes with full instructions and hints on interfacing it to your receiver.

Do not delay in placing your order for this versatile kit, fill in the coupon now.

HERE'S HOW TO ORDER

Fill in both coupons with your name and full postal address in BLOCK LETTERS and send them with your crossed cheque or postal order(s), made payable to IPC Magazines Ltd. (your name and address on the back please) to: Practical Wireless, Dept. PWL11, Rochester X, Kent ME99 1AA. Only available while stocks last to readers in England, Scotland, Wales and Northern Ireland. Not available in Eire, Channel Islands or overseas. Orders are normally despatched within 28 days, but please allow time for carriage. You will be notified if a longer delay is expected. Closing date is 23rd April, 1982, subject to availability.

To: PRACTICAL WIRELESS

Dept PWL11, Rochester X, Kent ME99 1AA. Please send me the DFC4 Counter Kit(s) as indicated @ £12.50 each, including P&P.

I enclose P.O./Cheque No..... Value.....

Number of DFC4 Counter Kits required

Name.....

Address.....

Tel. No. (Home or Work)

Number of DFC4 Counter Kits required

Name.....

Address.....

From PRACTICAL WIRELESS
Dept PWL11, Rochester X, Kent ME99 1AA

CUT ROUND DOTTED LINE

AMATEUR RADIO EXCHANGE



The New Year is a time for good resolutions, so here are a couple which we have made for your benefit.

1. Brenda G8SXY will continue to serve her celebrated coffee to all customers whether buying, selling or just browsing.

2. Bernie G4AOG will also be brewing up... in his case some exciting new flavours for our product range... and, right now, in addition to the expected full selection of radio equipment by ALL the leading makers, you will find...

• A really comprehensive range of Amateur TV transceivers and converters, both slow and fast-scan, with some items exclusive to us... and we're going to build on it.

• TRIO Test Equipment – fully professional in specification, but at prices which are still attractive to the Amateur market... and, if the interest is there, again we will build on it.

What will we think of to keep us ahead of the pack in 1983?

**YAESU'S
LATEST AND GREATEST**

THE FT-ONE



at very special prices

£895 plus your old FT-902DM or

£995 plus your old FT-101ZD/3



FRG-7700

Yaesu's latest receiver with FM right across the band now offers all these optional extras *Memory facility *FRT-7700 Aerial Tuning Unit at only **£37.85** *Four VHF converters running from 50MHz up to 170MHz.

BASIC RECEIVER £319 inc. VAT and FREE HELISCAN AERIAL
Converter specifications * Phone for Prices

FRV-7700A	118-130MHz	130-140MHz	140-150MHz
FRV-7700B	118-130MHz	140-150MHz	50-60MHz
FRV-7700C	140-150MHz	150-160MHz	160-170MHz
FRV-7700D	118-130MHz	140-150MHz	70-80MHz

NEW

ATV-2 TV TRANSCEIVER

Available only from us, this has been developed from the very popular ATV-1 TV Transmitter and it represents a real triumph of miniaturised solid-state technology.

So simple to go on the air, transmitting or receiving high-definition fast-scan video... Camera or VCR in at one end, 70cm antenna and normal domestic TV out of the other, connect to 12v, and there you are... who needs the BBC?

What's more, it's made for us in Britain by WOOD & DOUGLAS, who are building up a tremendous reputation internationally for high-quality design and construction.

Just look at all these features:

- 2-channel input from video camera or recorder in B/W or colour (switchable on front panel)
- Separate gain controls on both input channels
- Pre-set, adjustable video and modulation controls on rear panel
- Built-in receive converter – just connect direct to UHF TV for instant ATV reception
- Built-in diode changeover for Tx/Rx
- Microphone socket for announcement of video Tx on 70cm (switchable between audio and video)
- Video transmitter gives full 3w PSP output • Spurious better than 50dB down
- Unit housed in steel case and constructed on high-quality fibreglass PCB
- Full range of matching accessories available soon

Just look at the price ONLY £119

ATV-1 still available for Tx only (with diode c/o for Rx converter) at just **£87**.



EXCLUSIVE

LICENSED CREDIT BROKERS • Ask for written quotation.
INSTANT HP AND 6-MONTHS NO-INTEREST HP TERMS AVAILABLE
FOR LICENSED AMATEURS AND BANK/CREDIT CARD HOLDERS



Credit card sales by telephone

STOP PRESS!! Some price increases notified by manufacturers, but we will hold advertised figures while stocks last.

All prices include VAT, but p&p/carriage are extra.
Please allow 14 days for delivery.

2 NORTHFIELD ROAD, EALING, LONDON, W13 9SY.

Tel: 01-579 5311 Closed Wednesday, but use our 24-hour AnsaFone service. So easy for Overseas visitors. Northfields is just seven stops from Heathrow on the Piccadilly Line.

136 GLADSTONE STREET, ST. HELENS, MERSEYSIDE. Tel: 0744 53157

Our North West branch run by Mike (G8EWU).
Just around the corner from the Rugby ground.

THE **PW** 'WINTON' Stereo Tuner

Part 5
E. A. RULE

This month in Part 5 of the Winton Tuner we will deal with the wiring details. It is very important to follow these instructions carefully in order to avoid introducing unnecessary faults into the project.

Mounting the TV Unit

The TV unit was originally intended to be soldered directly into a p.c.b. of a TV receiver but this is not possible in the *PW* tuner. The method used may seem crude but in practice is very reliable and enables the unit to be removed for any service needed with ease. First, the four fixing screws and solder tags are fitted to the chassis but not tightened. The TV r.f. unit is then placed into its correct position and the solder tags adjusted in their position until each one can be soldered to the TV unit case. Once soldered, the fixing screws can be tightened up. To remove the unit it is only necessary to remove the screws, the tags will stay on the unit in the correct positions for refitting. Once mounted, the TV antenna socket can be soldered to the input pin on the side of the unit. Fig. 16 shows how the unit is mounted.

Wiring

The full wiring details are shown in Table 1. It is important to note that this describes the correct sequence of connections, and the actual route the wires should take. A suitable size wire to use is 7/0.2mm (0.22mm²). Once the wiring is finished it can be tidied up with cable ties (RS type 543-428 are suitable). Where decoupling capacitors are shown between the earth pins and chassis, keep the leads to the capacitors as short as possible. These capacitors are for radio frequency decoupling and should be fitted even though they appear to be decoupling a "short."

Use the minimum amount of solder required to obtain a good joint and let the solder "flow" so that dry joints are avoided. Tracing faults in r.f. circuits is one of the most difficult jobs, without adding any due to intermittent "dry" joints. Extra care taken with the p.c.b. soldering (and for that matter all soldering) will avoid hours of frustration later.

The soldering iron used should have a small bit as this will help in avoiding "solder bridges" between the copper tracks. The use of a strong magnifying glass to look at each and every joint after soldering will be found well worthwhile and is something the author always does.

Ferrite Antenna

The ferrite antenna is mounted in two plastic clips which are in turn mounted onto the rear panel of the chassis. The ferrite rod is fitted into these clips with the m.w. coil L6 (the longest coil) towards the f.m. antenna socket. The wires from the coil connections to the a.m. p.c.b. are passed through the grommet positioned next to the a.m. antenna socket. The most suitable wire for connecting up the ferrite rod coils is 7/0.1mm (0.055mm²) if available, but the 7/0.2mm can be used although not so flexible. The wires should be left as single conductors, i.e., don't twist the groups together as this will increase the capacity between them and may make the antenna trimmers difficult to adjust.

A small amount of slack should be left at the ferrite rod end of the wires so that the coils can be adjusted for optimum position on the rod during final adjustment. The actual connections are shown in Fig. 14. It is important to note that each coil has its own earth lead to the a.m. unit, do not be tempted to use a common lead for this as unwanted signal pick-up could result.

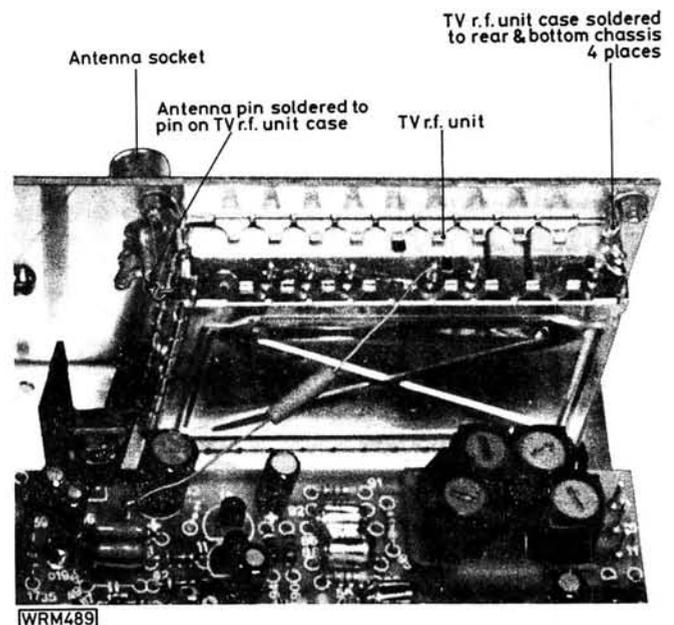


Fig. 16: The mounting of the TV r.f. unit

Fig. 14: The connections for the ferrite rod antenna looking at the tag ends of the coils


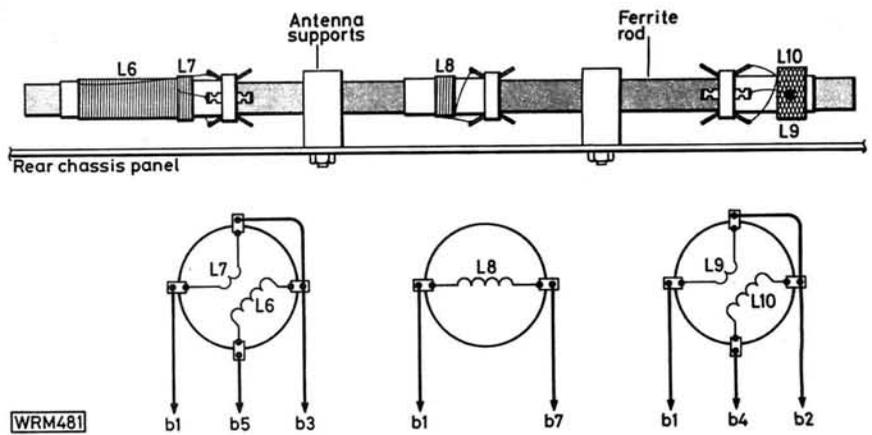


Fig. 15: Connections to the TV r.f. unit

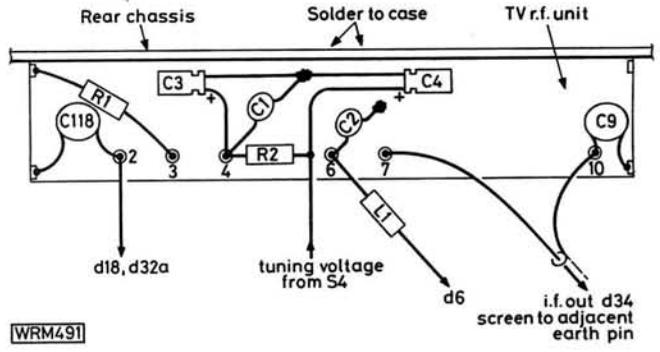

Most of the wiring is gathered up after completion into a "loom" and the route that the wires take is most important. There are four routes.

The front route follows the front of the unit from end to end approximately 40mm behind the front plate.

The rear route runs from end to end along the line of the rear edge of the a.m. board.

The cross (x) route joins the first two routes along the line where the digital board meets the a.m. board.

The direct route simply indicates that a wire goes from one point to another directly and is not gathered into a loom.

Before getting down to wiring, a few oddments should be done. Capacitor C112 (470nF) goes from pin c31 to nearby earth solder tag. Capacitor C10 (100nF ceramic) from pin "to C10" on the i.f. board to earth solder tag. A short green wire should be soldered from the earthed solder tag behind the digital board to the earth pin next to pin 5. On the front panel a wire should go from the solder tag above the four push switches to one side of S16 to 19 and the wiper A of S14.

The three-button switch should have all its bottom pins trimmed off and a spacer fitted at each end with a 6BA screw. It is then fitted to the front flange of the chassis with 6BA screws.

WRM491

Meters

The meters should only be glued in place when the unit is completely assembled and the front plate fitted; for wiring purposes they should be merely put in their correct place.

Mains Transformer

The mains transformer is fitted to the chassis with three large cable ties, with the buckle behind the small holes. Think carefully about the disposition of wires here as things are quite cramped. The fuseholder and cable clamp fitting are straightforward, but make sure the mains lead earth is long enough to reach an earth solder tag.

Wire	From	To	Via	Route/Notes
Yellow	S14-1	S15 left centre	—	Front
Yellow	S14-3	c14	R107	Front
Yellow	S14-4	c15	R108	Front
Yellow	S14-5	c13	R106	Front
Brown	c8	S16 "B"	—	Front
Brown	c9	S17 "A"	—	Front
Brown	c10	S18 H/S	—	Front
Brown	c11	S19 T/O	—	Front
Green	R56 pin 2	b8	S4 rear connections	Front x Rear
Blue	d38	d39	—	Direct
Blue	Point "Z" on AM board	to "Z"	—	Direct
Green	R56 pin 3	d20	—	Front
Blue	R56 pin 1	d19	—	Front
Brown	b32	d13	—	Front
Black	d16	S2 left rear	—	Front
Black	S2 left centre	"to S2" IF board	—	Front
Yellow	d24	S3 left centre	—	Front
Grey	d27	S3 left front	—	Front

Wire	From	To	Via	Route/Notes
White	d21	S3 left rear	—	Plus another 50mm wire on S3 left rear for tuning meter negative. Meter fitted later Front
Orange	d29	S1 left rear	—	
Red	d6	b22	c22	Rear L1 from TV tuner also to d6
Orange	b23	d17	FM Tuner B1 S1 left centre	Rear x Front
Red	d28	I.e.d. K	S1 left front	Front. Wire to I.e.d. 125mm long. K is longer lead. Use heatshrink sleeves on I.e.d.
Blue	d12	I.e.d. A	—	Front
White	c3	c21	—	Direct
White	c12	c20	—	Direct
White	d36	c19	15Ω ½W at C19 end	Rear
White	d32	c16b (1.5kΩ)	—	Direct
Black	C61 -ve	d4	—	Direct
Red	C61 +ve	d3	—	Direct
Red	d3	S16 right top	c1	Rear x Front
Orange	S16 centre right	d5	—	Front x Rear
Yellow	b24	d32a	c9	Rear
Yellow	d32a	d18	TV tuner pin 2	Rear and right end
Grey	c7	junction R2/C4 TV tuner	Right centre	Front and right end
Grey	S4 centre left	junction R3/C7 FM tuner	—	Front x Rear
Purple	d14	a.g.c. pin FM tuner	—	Front x Rear
Blue	d35	b29	—	Rear
Brown	d25	b27	—	Front x Rear
Green	d26	b28	—	Front x Rear
Blue	b14	S16 (standby) top left	c18	Rear x Front
Twin coaxial cable screens	b17 b21 b18	d9 d11 d16	— — —	Rear Rear Rear
Single coaxial	Antenna socket on chassis	Antenna phono plug on tuner	—	Direct. Fit also wire from earth solder tag on socket to black socket below
Twin coaxial cable	b16 b20 b18	pin 4 din o/p pin 1 pin 2	— — —	Rear Rear Rear
Black	b15	c16a	R110	Rear
White	b13	c17	R111	Rear
Single coaxial screen	FM Tuner IF Out plug IF Out plug	d31 pin E	— —	Rear Rear
Single coaxial screen	FM Tuner F Out plug F Out plug	c5 adjacent earth pin	— —	Rear Rear
Single coaxial screen	c3 c2	b26 NC	— —	Rear Rear
Fit meters now. See note headed "meters"				
White (already fitted)	S3 rear	Tuning meter negative	—	—
Orange	d22	Tuning meter +ve	—	Front
Red	b30	Signal strength meter +ve	—	Direct
Black	b31	Signal strength meter -ve	—	Direct
Single coaxial screen	d34	TV tuner pin 7 pin 10	— —	Rear Rear
Now fit the mains transformer, fuseholder and mains lead. See notes				
Red	d1	transformer	—	These wires are already fitted to the mains transformer
Black	earth above D15	transformer	—	
Red	d37	transformer	—	

Wire	From	To	Via	Route/Notes
Brown	transformer	fuseholder front tag	—	Sleeve joint to prevent shock
Brown	mains lead	fuseholder rear tag	—	Sleeve joint to prevent shock
Green/Yellow	mains lead	earthed solder tag by transformer	—	
Blue	mains lead	transformer	—	Sleeve joint

Fit the ferrite rod in two plastic clips. Coils are referred to as follows: LWC — long wave coil, MWC — medium wave coil, CC — coupling coil. The coupling coil has only two tags. The long and medium coils have their tags numbered by their "clock" position when viewed from the tag end and referenced to the paint mark at "12 o'clock".

Green	b1	LWC 4	MWC 2 and CC1	Do not twist the following wires but leave as loose as possible to reduce stray capacitance. If a.m. performance is critical smaller wires may be used.
Red	b3	MWC 8 and 10		
Black	b2	LWC 8 and 10		
Yellow	b4	LWC 2		
White	b5	MWC 4		
Grey	b7	CC2		
Brown	b6	AM antenna socket		


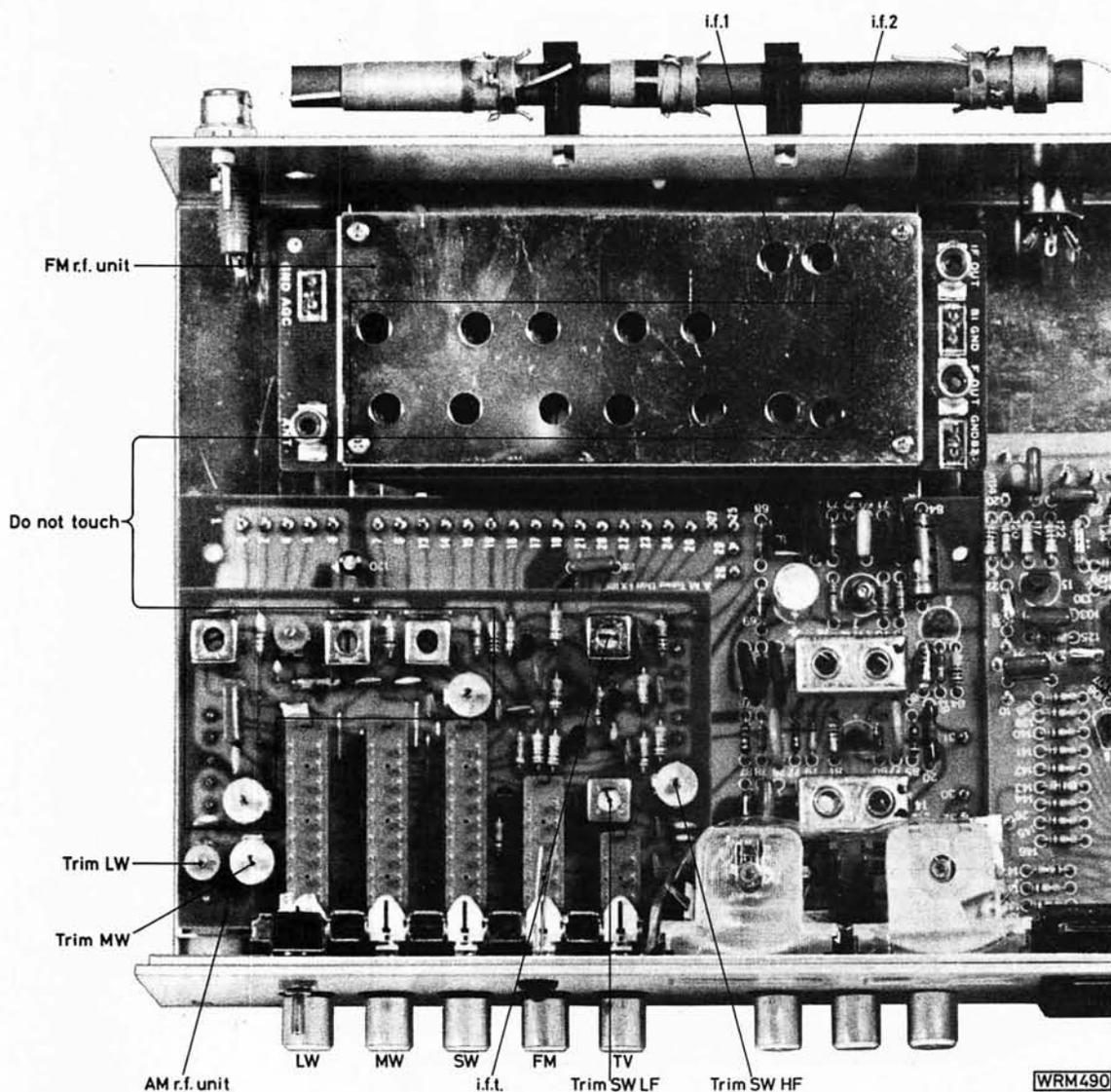


Fig. 17: The f.m. and a.m. r.f. units with their respective tuning adjustments marked

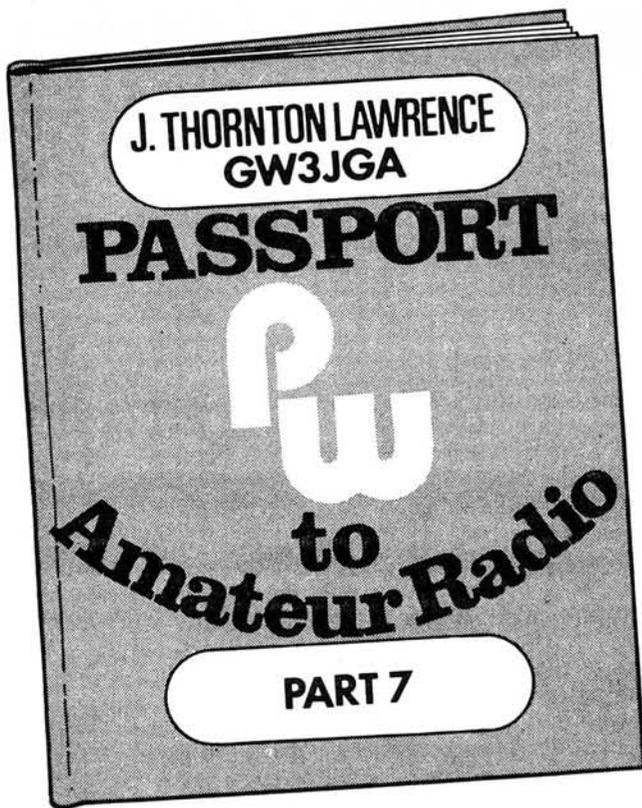We will deal with the setting up instructions for the tuner next month, as they have had to be held over due to space problems.



In this part of the series we will be looking at transmitters and types of modulation.

Transmitters

To state the obvious, the purpose of the transmitter is to generate a radio frequency signal for transmission to a distant receiving station. In addition, the transmitted signal must conform to the Amateur Sound Licence requirements in terms of power, frequency, accuracy and stability, absence of spurious emissions, etc., particularly when keyed or modulated by the information to be sent. Full details of these requirements are given in the Home Office publication *How to become a radio amateur*.

A block diagram of a simple c.w. transmitter (emission type A1A) for 160m, 1.8–2.0MHz, is shown in Fig. 47. It consists of a variable frequency oscillator followed by a buffer amplifier and a power amplifier.

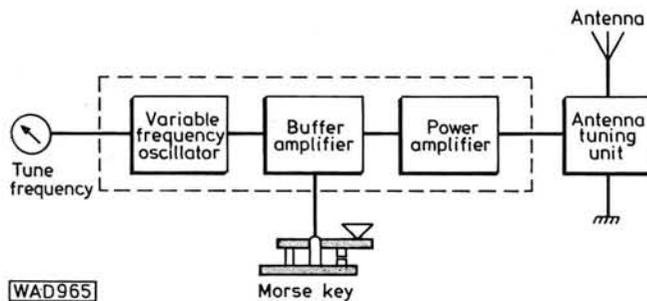


Fig. 47: Block diagram of a c.w. transmitter

It is usual for the oscillator to be operated in Class A or B, the buffer amplifier in Class B and the power amplifier in Class C. The various classes of operation refer to the conditions under which the valve or transistor operates and these are summarised and shown graphically in Fig. 48.

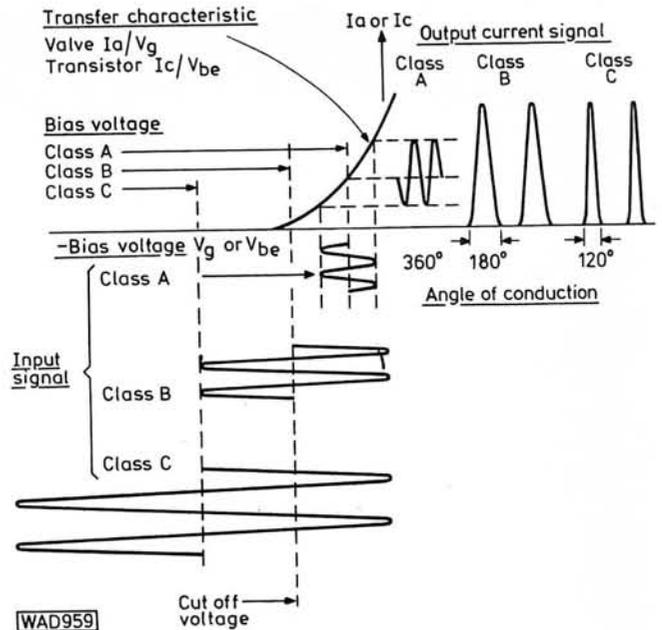


Fig. 48: Operating conditions for Class A, B and C

Classes of Amplifier Operation

In **Class A**, the transistor or valve is biased to near the centre of its linear operating range and the signal amplitude is insufficient to cause operation outside this range. Class A amplifiers have a low efficiency, typically 50 per cent or less (less than half the input power is converted into useful output), but they do not significantly distort the signal or generate harmonics.

In **Class B**, the valve or transistor is biased to the cut-off point and the input signal drives the device into full conduction for half of the cycle of input signal (180°) and beyond cut-off during the other half. The efficiency is higher than Class A, being 60–65 per cent for c.w. (continuous radio frequency wave operation).

A Class B amplifier stage with a single valve or transistor distorts the signal passing through it, producing mainly second harmonic distortion. In a Class B audio frequency amplifier two valves or transistors are required. These operate in push-pull, one handling one half-cycle and its partner the other, so eliminating the distortion.

A single valve or transistor Class B amplifier can be used for r.f. purposes in a transmitter because of the "flywheel" effect of the output tuned circuit. This type of amplifier has a reasonably linear transfer characteristic (the output signal is proportional to the input signal) and therefore an amplitude-modulated r.f. signal can be amplified with little distortion, an important property which is essential in single sideband transmitters, as we shall see later.

In a **Class C** amplifier, the valve or transistor is biased well beyond cut-off and the input signal is required to have a larger amplitude in order to drive the device into conduction. Conduction only occurs for about one-third of a cycle of the input signal (120°) and the efficiency can be in the region of 70 per cent.

The output of the device contains a high proportion of harmonics and the output circuit must be correctly tuned to the fundamental frequency to reduce the possibility of harmonics being radiated. The Class C amplifier has a non-linear transfer characteristic and is therefore unsuitable for amplifying an amplitude-modulated input signal, although we will see later that it can be used to amplitude modulate a carrier wave.

A Class C amplifier can be employed intentionally as a harmonic generator or frequency multiplier by increasing the bias still further so that the device is only conducting for a quarter of a cycle (90°) of the input signal.

In this condition, the output is rich in harmonics and by making the output circuit resonant at the desired harmonic, power can be obtained at this frequency. For example, the input could be at 7MHz and the output tuned to the second harmonic (14MHz), with further amplification for transmitting on the 14MHz band, or the third harmonic selected for transmitting on the 21MHz band. In Fig. 48 the bias conditions are shown for a valve I_a (anode current)/ V_g (grid voltage) characteristic and for a transistor I_c (collector current)/ V_{be} (base-emitter voltage) characteristic.

Simple CW Transmitter for 160m

The circuit of the transmitter illustrated in the block diagram (Fig. 47) is given in Fig. 49.

The v.f.o. is a series-tuned Colpitts oscillator. The oscillator feedback is obtained from a capacitive tap (the junction of C3 and C4). A simple memory "aid" is "C" is for Colpitts and capacitive tap and "H" is for Hartley and an inductive tap. The frequency stability of the oscillator depends mainly on the coil and the tuning capacitor C13 having good mechanical stability and Tr1 being coupled in such a way that any change in its internal capacitance has little effect on the frequency.

This is done by arranging that C3 and C4 are effectively across Tr1 and are large enough to swamp any small changes that might occur.

The output from Tr1 is fed to the tuned circuit L2 and C5 which has a coupling winding L3 feeding Tr2. The bias

for Tr2 is provided by R5 and R6 with decoupling by C6. The output from Tr2 is fed to the tuned circuit L4 and C7 with a coupling winding L5 feeding the base of Tr3. Note that Tr3 is normally cut-off and only conducts when driven with an input signal. The emitter biasing resistor R8 provides extra biasing voltage when the stage is operating giving the correct Class C conditions. The output is fed to a suitable impedance matching point on L6 which, with C14, resonates at the output frequency. Output coupling to the antenna tuning unit is provided by an adjustable coupling coil L7.

Keying and the Keying Filter

The transmitter is keyed on and off by connecting the Morse key in the emitter circuit of Tr2. When the key is "up" no current will flow through Tr2 and there is no output. With the key "down" normal output is obtained.

Keying a transmitter by abruptly starting and stopping the carrier wave results in spurious signals being radiated and these are received as "key clicks" over a wide range of frequencies. To overcome this problem the transmitter must turn on and off less quickly and a key click filter, L8, C9 and R9 is included for this purpose. Inductor L8 restricts the rate of rise of current through Tr2 when the transmitter is keyed on, and C9 the fall of current when keyed off, as shown in Fig. 50. The values of L8, C9 and R9 are often chosen experimentally, but the values given are typical.

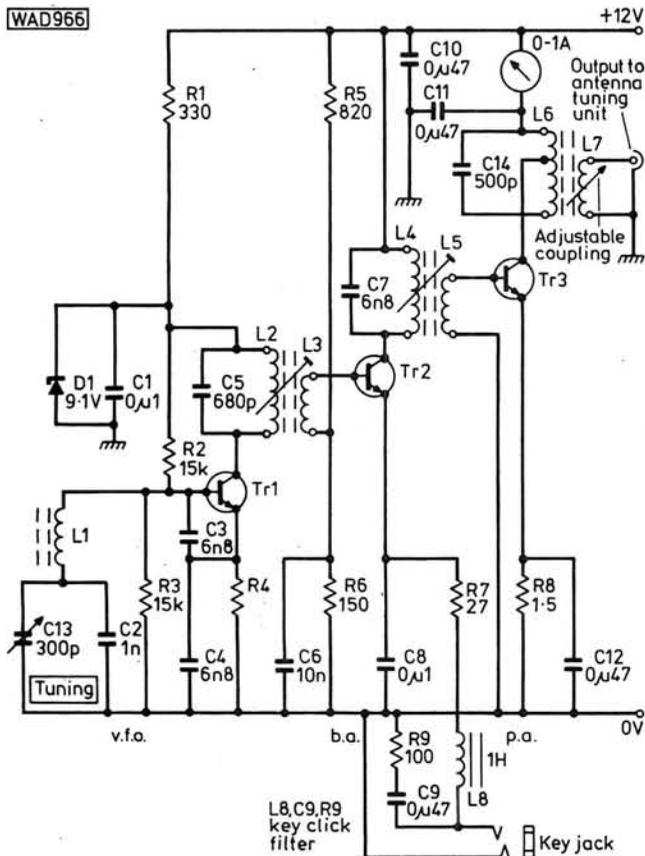


Fig. 49: The circuit diagram of the c.w. transmitter of Fig. 47

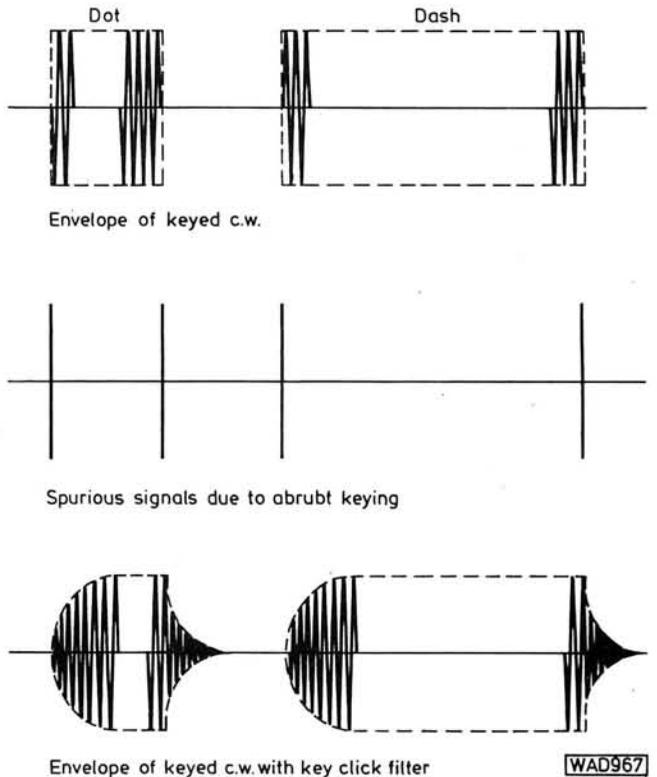


Fig. 50: Signal envelopes with and without key click filter

Modulation

To transmit voice information by radio wave it is necessary for the microphone output signal to vary or modulate the r.f. carrier wave in such a way that will allow the a.f. signal to be extracted at the receiver. The two basic

methods are amplitude modulation (a.m.) and frequency modulation (f.m.), each method having its particular advantages and disadvantages.

Amplitude Modulation

Amplitude modulation is produced by mixing the modulating signal with the carrier wave in a non-linear device or amplifier. Modulation can be carried out at high power levels in the output stage of the transmitter or at low power in an earlier stage providing the subsequent amplifiers are linear (Class A or B).

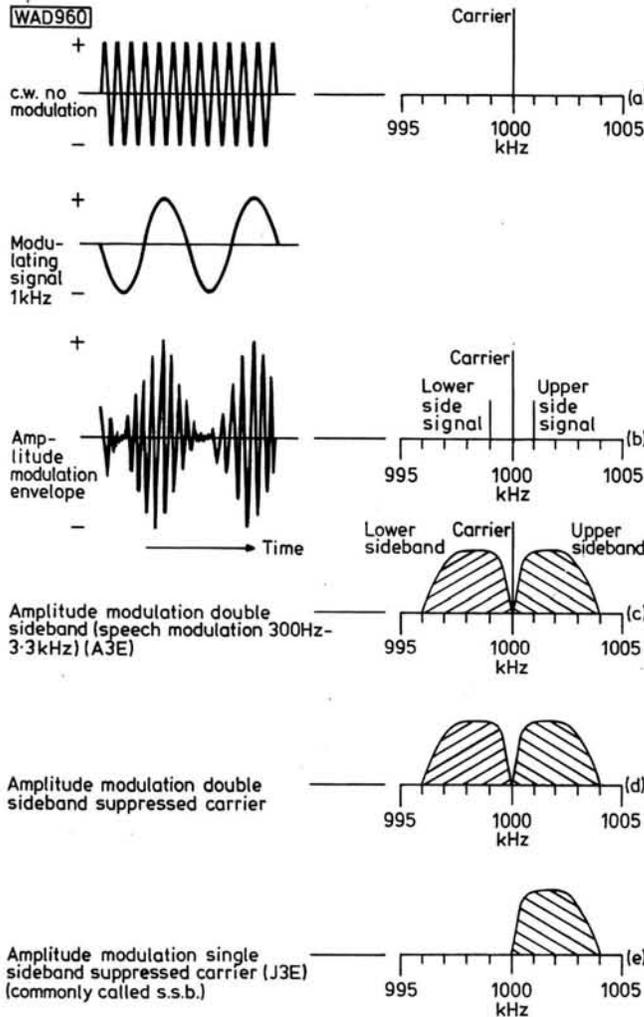


Fig. 51: Examples of a.m. envelopes showing sidebands

Amplitude modulation is shown in two ways in Fig. 51(a), (b) and (c). On the left is a representation of the carrier wave, the modulating signal and the resultant modulation envelope as would be seen on a conventional oscilloscope. The graphs on the right show the same conditions but with the frequency along the base-line. When two frequencies are fed into a non-linear stage, the output will contain a number of signals in addition to the original input signals. The main ones are the "sum" and "difference" frequencies, as shown below.

Input signals f_1 and f_2

Output signals $f_1, f_2, f_1 + f_2, f_1 - f_2$.

If the carrier frequency is 1000kHz (f_1) and the modulating frequency is 1kHz (f_2) then two side-

frequencies are generated, the higher one at 1001kHz ($f_1 + f_2$) and the lower one at 999kHz ($f_1 - f_2$). It is the sum of the carrier and the two side-frequencies which forms the modulation envelope shown in Fig. 51(b).

The speech signal from the microphone consists of a band of frequencies between about 300Hz and 3.3kHz varying in frequency and amplitude with the voice patterns. Modulation by a speech signal results in two sidebands, the upper sideband and the lower sideband. These sidebands, which carry the a.f. modulation information, are mirror images of each other. The carrier wave remains constant irrespective of whether modulation is present or not and although it carries no information its presence is required at the receiver for the demodulation process.

Since the carrier wave conveys no intelligence it is possible to dispense with it altogether as shown in Fig. 51(d) (thus saving a great deal of transmitter power), provided it is generated again, locally at the receiver for demodulation purposes. Unfortunately this carrier must be in the correct phase relationship with the sidebands or serious distortion will result. A double-sideband suppressed-carrier transmission is very difficult to tune in and requires a sophisticated receiver for satisfactory reception. However, if the carrier and one of the sidebands are removed and the remaining sideband transmitted then this exact phase relationship is no longer essential and the carrier can readily be inserted at the receiver.

As the two sidebands contain identical modulation, removing one of them does not result in loss of information and effects a further saving of transmitting power. This type of transmission shown in Fig. 51(e) is known as single sideband suppressed carrier or emission type J3E (A3J) and commonly abbreviated to just s.s.b.

Single Sideband (J3E)

Single sideband has several advantages for the radio amateur:

1. Saving in transmitter power or the ability to run the equivalent of higher power for the same rating of output amplifier.
2. No carrier radiated so it does not cause the usual heterodyne interference.
3. Requires only half the usual bandwidth.
4. Less affected by transmission path disturbances.

Amplitude Modulated Transmitter

Amplitude modulation A3E (A3) can be performed at high signal levels in the output stage of the transmitter by applying the modulating audio voltage in series with the supply voltage as shown in Fig. 52(b). To achieve adequate amplitude modulation of a transistor transmitter it is

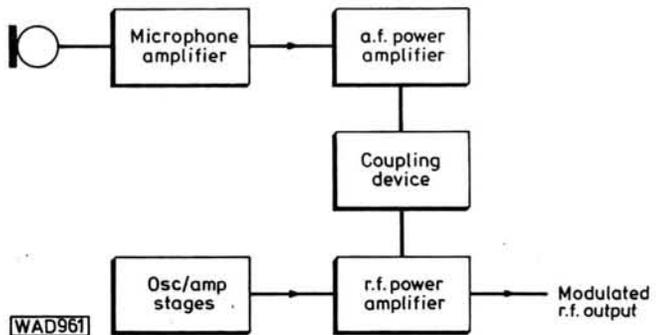


Fig. 52(a): Block diagram of a.m. (A3E) transmitter

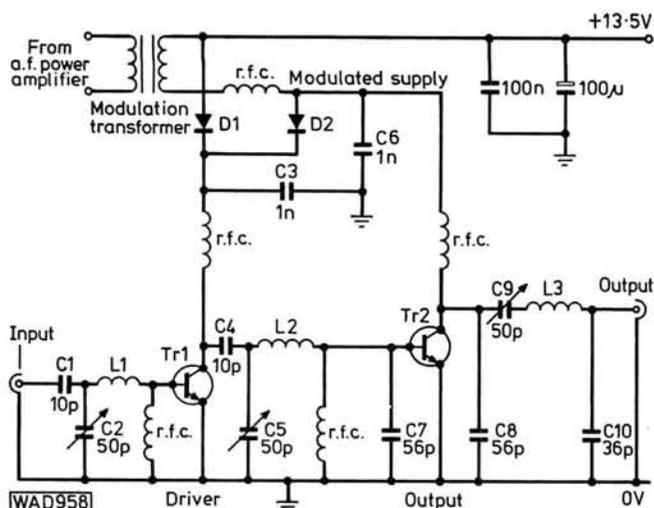


Fig. 52(b): Output stage of 144MHz a.m. transmitter

usually necessary to modulate the supply to the driver stage in addition to the output stage. In the circuit shown, diode D2 conducts and D1 cuts off when the modulating voltage swings positive and so provides extra drive to the output stage on positive modulation peaks.

If the output stage transistor was drawing 30 watts d.c. input power then approximately 15 to 20 watts of audio power would be required for full modulation.

SSB Transmitter (J3E)

The s.s.b. (J3E) signal is usually generated either by a phasing method, shown in Fig. 53(a), or by the use of a balanced modulator and filter shown in Fig. 53(b).

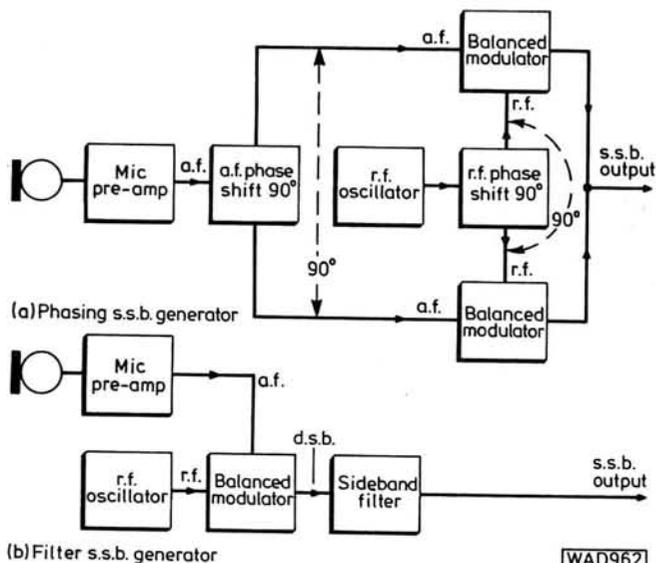


Fig. 53: Two methods of generation of an s.s.b. signal

In the phasing method, the a.f. signal is processed in a phase-shifting circuit which generates two signals having a 90° phase relationship over the audio frequency band, 300Hz to 3.3kHz. The r.f. signal is also phase shifted by 90° and fed with the a.f. signals to two balanced modulators with a common output. The result is that the carrier is removed and one sideband is cancelled out. Upper or lower sideband can be selected by reversing the a.f. or r.f. inputs to the modulators.

In the filter method, the r.f. signal is modulated in a balanced modulator to provide a double-sideband suppressed-carrier signal and then one of the sidebands is selected by a high-grade crystal filter to produce an s.s.b. signal. The filter method is the simpler of the two, but requires an expensive or very carefully home-made crystal filter.

Balanced Modulator or Mixer

The balanced modulator can take many forms but in essence it is a balanced circuit in which the r.f. input signal is cancelled or "nulled" out.

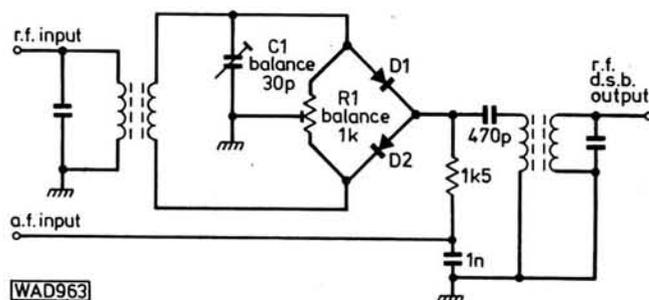


Fig. 54: Diode bridge modulator

The simplest form is a diode bridge arrangement shown in Fig. 54. Here the r.f. input is fed to a bridge circuit where the centre of the diodes is a null point. Resistor R1 and capacitor C1 enable the bridge to be accurately balanced to provide adequate suppression of the carrier. An a.f. signal input causes D1 and D2 to conduct alternately, on each half-cycle, unbalancing the bridge and producing a double-sideband suppressed-carrier signal at the output.

Simple SSB (J3E) Transmitter

The block diagram in Fig. 55 shows a simple s.s.b. transmitter for use on one band 14–14.35MHz. In this transmitter the s.s.b. signal originates from a 9MHz crystal oscillator feeding into a balanced mixer and then to a crystal filter. The 9MHz s.s.b. signal is mixed with a variable frequency oscillator (v.f.o.), tuning

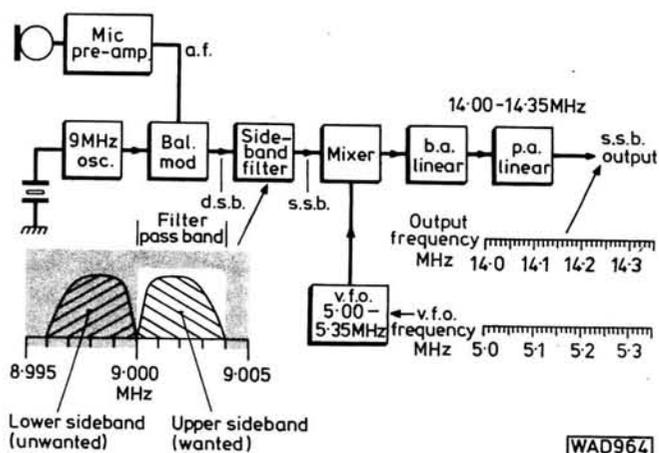


Fig. 55: Block diagram of a single band s.s.b. transmitter

5.0–5.35MHz. The sum of the two frequencies 14–14.35MHz is selected at the output. This signal is amplified in a linear buffer amplifier and then a linear power amplifier to give the required s.s.b. power output. Operation on other bands would be possible by changing the v.f.o. frequency.

It is essential that, once the amplitude modulated s.s.b. signal is generated, subsequent amplification must be linear or severe distortion will result. Class C amplifiers are unsuitable for this purpose.

Linear Power Amplifier

A typical linear power amplifier, for use on one h.f. band, is shown in Fig. 56(a). The valve is biased to operate in Class B for good linearity combined with high efficiency.

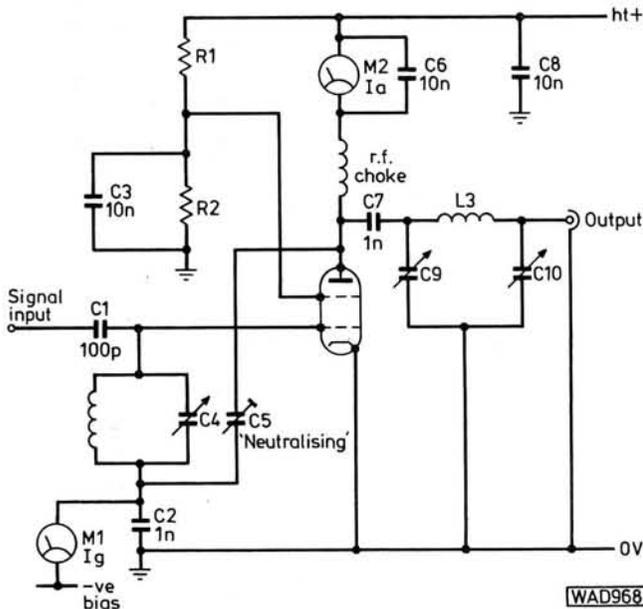


Fig. 56(a): Linear power amplifier

The s.s.b. signal is applied to the input tuned circuit and the control grid. The output signal at the anode is developed across the r.f. choke L2 and fed via C7 to the output tuned circuit L3, C9 and C10. This output circuit is called a "pi" network (similar in shape to the Greek letter pi, π). In operation, C9 tunes the output circuit to resonance and C10 effectively provides a variable capacitive tapping point on the tuned circuit and enables the output of the transmitter to be correctly matched to the load.

Neutralisation

There is usually some stray capacitance existing between the anode and grid of the valve both in the valve itself and in the wiring. Signal feedback through this capacitance affects the grid and anode tuning and may cause self-oscillation. A neutralising capacitor C5 feeds a small amount of r.f. signal from the anode to the opposite end of the grid tuned circuit and neutralises the effect of the anode-grid capacitance. The circuit is rearranged in Fig. 56(b) to show that the neutralising capacitor forms part of a "bridge" circuit. To set C5, the h.t. is temporarily disconnected, an input signal is applied and C4 adjusted

for maximum drive indicated on M1. With C10 at maximum C9 is rotated and any variation on M1 noted. Capacitor C5 is then adjusted for negligible variation of M1, indicating correct neutralisation.

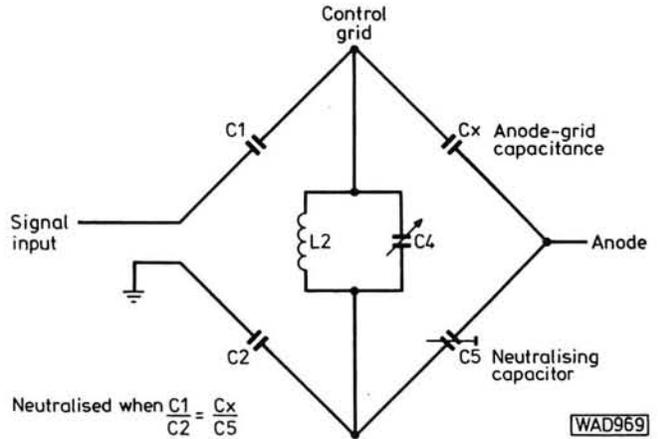


Fig. 56(b): Equivalent circuit of Fig. 56(a)

Upper and Lower Sideband


In the s.s.b. transmitter shown in Fig. 55 the upper sideband was selected by the relative placing of the 9MHz oscillator and the filter passband.

Selection of the lower sideband could be obtained by moving the 9MHz oscillator to the high-frequency side of the filter passband so that the lower sideband would fit within the filter passband.

By convention, amateur transmissions use the lower sideband on the 1.8, 3.5 and 7MHz bands and upper sideband on 14MHz and above.

In practice, two quartz crystals would be employed in the 9MHz oscillator having frequencies differing by about 3kHz correctly placed on each side of the filter passband and switched to give upper or lower sideband operation.

With regard to Class B and Class C r.f. amplifiers, remember that there are no essential physical circuit differences between the two types; the difference is in the operating conditions, namely the bias supply voltage and the amplitude of the r.f. input signal. However, Class B (and Class A) amplifiers are more critical to any stray feedback which may be present in the device or wiring and therefore may need neutralisation, as described, before correct tuning and operation can be obtained.

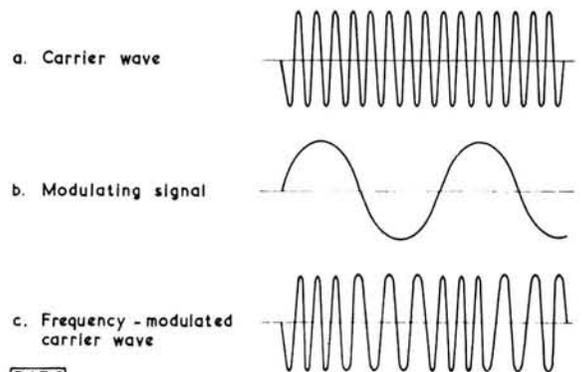

RAE 8

Fig. 57: Frequency modulation of a carrier wave

Frequency Modulation

Frequency modulation is shown graphically in Fig. 57, where (a) represents an unmodulated r.f. carrier wave, (b) an a.f. modulating signal and (c) a frequency modulated carrier wave.

In this diagram it can be seen that the frequency of the carrier wave is increased and decreased in direct relationship with the modulating signal. The amount of frequency change (deviation) depends on the amplitude of the modulating signal, and the number of times per second the frequency changes is equal to the modulating frequency. For example, suppose that an r.f. carrier wave of frequency 1000kHz is frequency modulated by a 1kHz signal, the deviation being 2.5kHz above and below the centre frequency, 1000 times per second (1kHz rate). If the amplitude of the 1kHz modulation signal is reduced to half, then the deviation will be reduced to half, i.e. 1.25kHz above and below the centre frequency, but still 1000 times per second (1kHz rate), as before.

Direct frequency modulation is performed in the oscillator circuit itself, usually by using a variable capacitance diode to modulate the oscillator frequency as shown in Fig. 58.

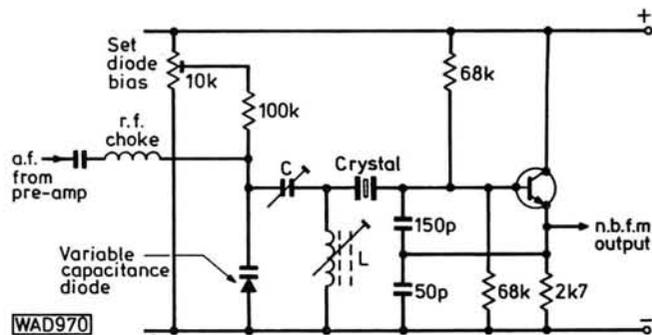


Fig. 58: A typical n.b.f.m. oscillator circuit

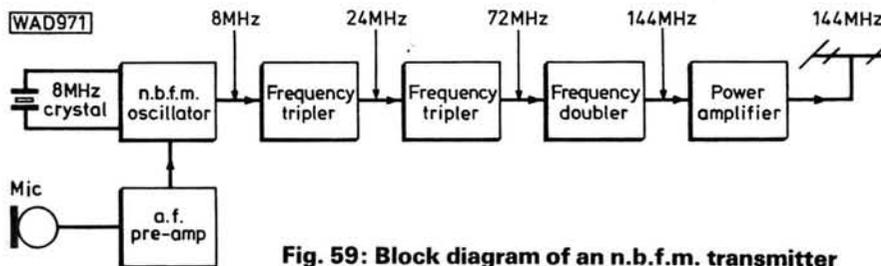


Fig. 59: Block diagram of an n.b.f.m. transmitter

(b) The transmitter output stage operates at a constant power level which allows the use of lower rated components, e.g. transistors and capacitors.

(c) Any class of amplification can be used and chosen for best efficiency or low spurious emissions, etc.

(d) Interference with television broadcast and audio equipment is significantly reduced as f.m. is not demodulated by the usual rectification methods.

Phase Modulation

Indirect frequency modulation, or phase modulation as it is more popularly known, is performed by modulating the r.f. carrier such that the phase of the carrier is changed corresponding to variations in the amplitude of the modulating signal.

In this method the frequency remains fixed and modulation is applied using a phase-shifting circuit, which can either be in the oscillator stage or following it. The effect is to either add or subtract frequency variations from the fixed carrier.

For amateur radio purposes, particularly on the 2-metre band, narrow band frequency (or phase) modulation (n.b.f.m.) is frequently used. In this mode the deviation is usually restricted to about 2.5kHz. A block diagram of a typical 2-metre n.b.f.m. transmitter is shown in Fig. 59.

In this transmitter the crystal oscillator frequency is nominally 8MHz and the frequency is multiplied 18 times in three frequency multiplier stages ($\times 3$, $\times 3$, and $\times 2$) giving a final frequency in the 144–146MHz band. It follows that any frequency deviation at the oscillator will also be multiplied 18 times and for a final deviation of 2.5kHz the oscillator deviation will only need to be $2500/18\text{Hz} = 139\text{Hz}$.

Basically, a crystal oscillator has good frequency stability but, by including in the crystal circuit a reactance which can be varied by the modulating signal, the crystal can be "pulled" off frequency and adequate deviation obtained for n.b.f.m. transmission.

The use of n.b.f.m. has several advantages:

(a) Modulation can be applied at low power, no high power modulator is required.

Crystal Oscillators

Quartz crystal oscillators are employed in transmitters, receivers and frequency measuring equipment wherever a stable, accurate oscillator is required.

A plate cut from quartz crystal has the property of generating an alternating voltage between its opposite faces when made to vibrate by mechanical means. Conversely it will vibrate when an alternating voltage is applied across it. The natural mechanical resonant frequency of the quartz plate is determined to a large extent by its dimensions, and when electrically connected in an oscillator it behaves as a series-tuned circuit having a very high LC ratio and a very high "Q" (>10 000). See Fig. 61.

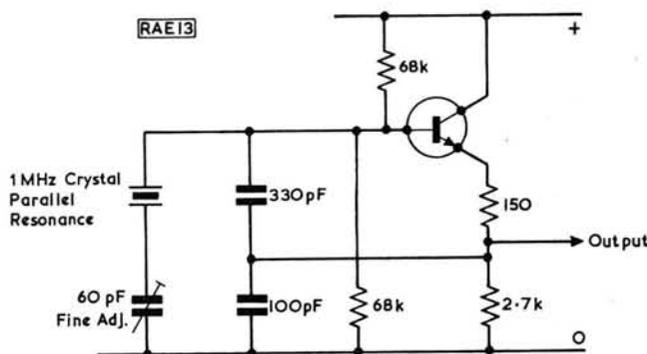


Fig. 60: A basic crystal oscillator circuit

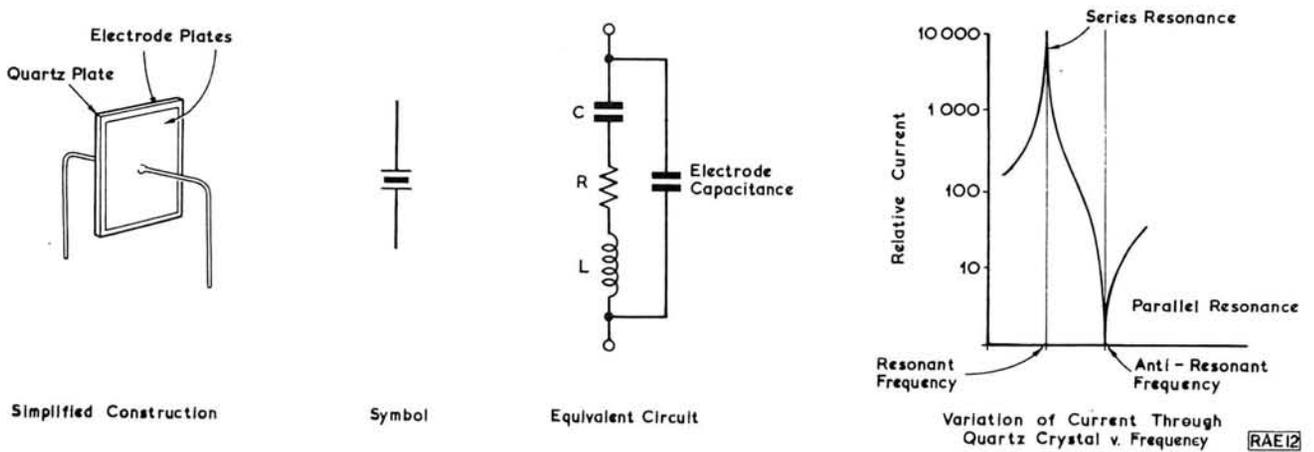


Fig. 61: Features of a quartz crystal

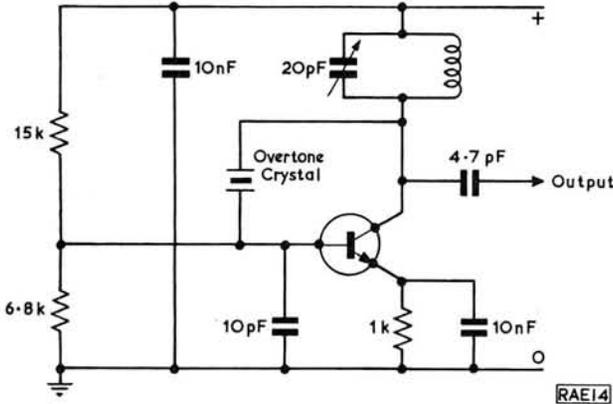


Fig. 62: An overtone crystal oscillator circuit

The crystal exhibits a series resonant frequency and a parallel resonant frequency; these are extremely close together: only a few hundred hertz apart at 10MHz. Crystals are calibrated in frequency for one or the other mode of resonance depending on the circuit requirements. An oscillator circuit for a crystal operating in parallel resonance is shown in Fig. 60.

Under normal room temperature conditions, the frequency of this oscillator would remain constant within a few parts per million (few hertz per megahertz).

Crystals can be manufactured for very high frequencies (100MHz and beyond) using multiple vibration of the crystal; these are known as overtone crystals and are used in series resonance. A typical circuit is shown in Fig. 62.

Next month we will consider transmitter measurements.

MODS No. 13

▶▶▶ continued from page 25

The new switch will now perform two separate functions depending on when it is operated. Setting it to position "A" before powering-up sets the band edges when the power is applied and in this instance gives us the European band and channel spacing. If you now set the switch to position "B" while the power is being applied to the rear of the set, regardless of whether it is turned on or not, you will alter the channel spacing and not the band edges. In other words, you will now have European band edges coupled with US channel spacing, thus making it usable in Australia. Similarly, setting the switch to "B", then powering-up and then resetting the switch to "A" will give you US band edges and European spacing.

It is important to remember that it is the position of the switch before power is applied that sets the band edges and the position afterwards that sets the channel spacing. If you can obtain a miniature s.p.d.t. switch that has a centre off position, such as RS No. 317-005, then the centre position will give you the option of the Japanese band limits and channel spacing, i.e. neither of the diodes will be in circuit.

Unfortunately there is not enough space this month for me to include the "Wanted" section but please continue to write in if you have any mods that you would like to pass on or if you have a request for a mod. The address is: R. S. Hall, Room 301, Hatfield House, Stamford Street, London SE1.

73's
Sam G8TNT

IC of the Month

▶▶▶ continued from page 44

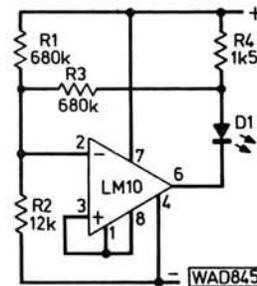


Fig. 9: A battery status indicator

TR3, a 2N3055 transistor, must be fitted to a suitable heat sink. The circuit contains a built-in current regulator for protection.

Battery Indicator

The simple circuit of Fig. 9 can be used to indicate the state of a 9V battery. The l.e.d. D1 begins to dim as the voltage falls below 7V and becomes extinguished at about 6V. If the warning of falling voltage is not required, R3 can be removed and the value of R1 halved so that switching to the extinguished condition occurs suddenly.

Availability

The LM10 is available from Watford Electronics, 35 Cardiff Road, Watford, Herts.

3-BAND SHORT-WAVE CONVERTER

1.6-6 MHz

4-15 MHz

7-30 MHz

PART 1

R. F. HAIGH

Short wave listening on the amateur and broadcast bands is a fascinating pastime, but a sensitive and selective receiver, which is easy to adjust and free from spurious responses, is essential.

The converter design presented here precedes the facilities of second conversion, i.f. detector and audio output stages, of an ordinary m.w. portable transistor receiver to provide general coverage of the h.f. bands between 1.6 and 30 MHz.

With the i.f. strip within the existing receiver already working, alignment of the converter presents no real problems. Although a little care and patience is required, a signal generator is not necessary. A b.f.o. (beat frequency oscillator) unit is incorporated to enable amateur s.s.b. and c.w. signals to be resolved.

Circuit Description

The complete circuit of the converter is given in Fig. 1. The dual gate MOSFET transistor Tr1 functions as a first mixer stage, with received signals from the r.f. front end coils, L1 and L2, taken to gate 1 and the local oscillator input applied to gate 2.

The mixer stage output is taken from the drain and developed across L3, the primary of the 1.6 MHz i.f. transformer. The secondary, L4, couples the converter unit to the m.w. receiver via a short length of coaxial cable.

A second field effect transistor, Tr2, acts as the local oscillator, the output from this stage being applied to Tr1 through the 10 pF capacitor C9. A padder capacitor is inserted in series with the oscillator coil tuned winding, L6, in order to enable the stage to track at 1.6 MHz above the received signal frequency. Coil L5 is the feedback winding which must be connected in the correct sense.


Band selection is effected by S1, a 4-pole, 3-way switch bank. Only one set of r.f. and oscillator coils, together with associated trimmer and padder capacitors, are shown on Fig. 1, in the interests of clarity. (Refer to Table 1 for the values of components marked with an asterisk.) It should be noted, therefore, that individual trimmers C1* are wired across the tuned windings of each of the r.f. coils, and each oscillator coil has a separate padder capacitor C6*. The r.f. and oscillator coils are tuned by ganged variable capacitors C2 and C8.

The 10 kΩ potentiometer, R1, functions as a simple form of r.f. gain control. Without this facility, very strong amateur s.s.b. transmissions cannot be resolved.

A beat frequency oscillator, b.f.o., is included, so that c.w. and s.s.b. can be rendered intelligible. The tuned winding of the b.f.o. coil, L8, is connected to the collector of Tr3, and feeds back to the base via L7. The b.f.o. stage has to work in conjunction with the i.f. amplifier in the

receiver used with the converter. Accordingly, the 220 pF capacitor C16 tunes L8 to within the standard i.f. range of 450 to 470 kHz, and the dust iron core is used to set the b.f.o. precisely at the receiver i.f. frequency. Fine adjustment of the b.f.o. is by means of the 15 pF variable capacitor C18, and the output is taken from the collector of Tr3 via the 10 pF capacitor C17.

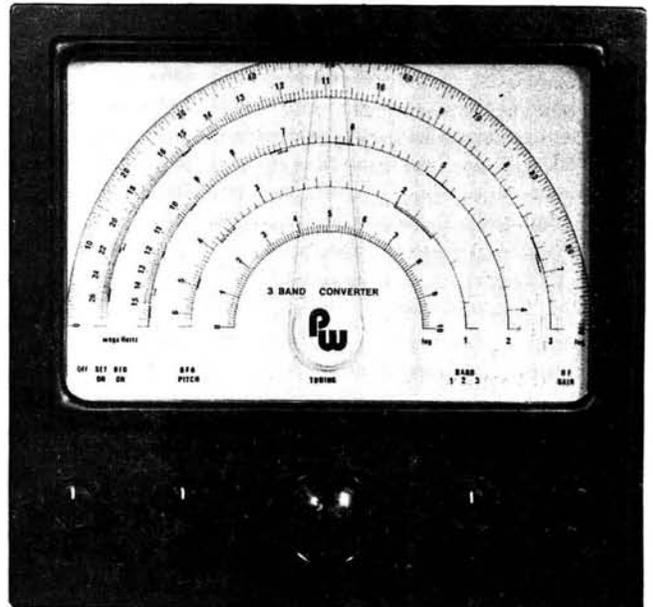Zener diode, D1, and resistor, R9, ensure a stable supply voltage for the b.f.o. unit, as fluctuations have a significant effect on the frequency of oscillation of Tr3. The converter oscillator stage is also supplied from the stabiliser circuit. Pre-set potentiometer R8 is used to optimise the drain voltage of Tr2, and its adjustment is not critical.



Power supply switching is performed by a 4-pole, 3-way rotary switch, S2, giving OFF, CONVERTER ON and CONVERTER AND B.F.O. ON positions.

Components

No difficulty should be encountered in obtaining any of the components, and most of them are available from suppliers advertising in *PW*. A brief note on some of the items may, however, prove helpful.

The ganged tuning capacitors, C2 and C8, must be good quality air spaced components, but the actual type and value are not critical. A large "E" type 500 pF

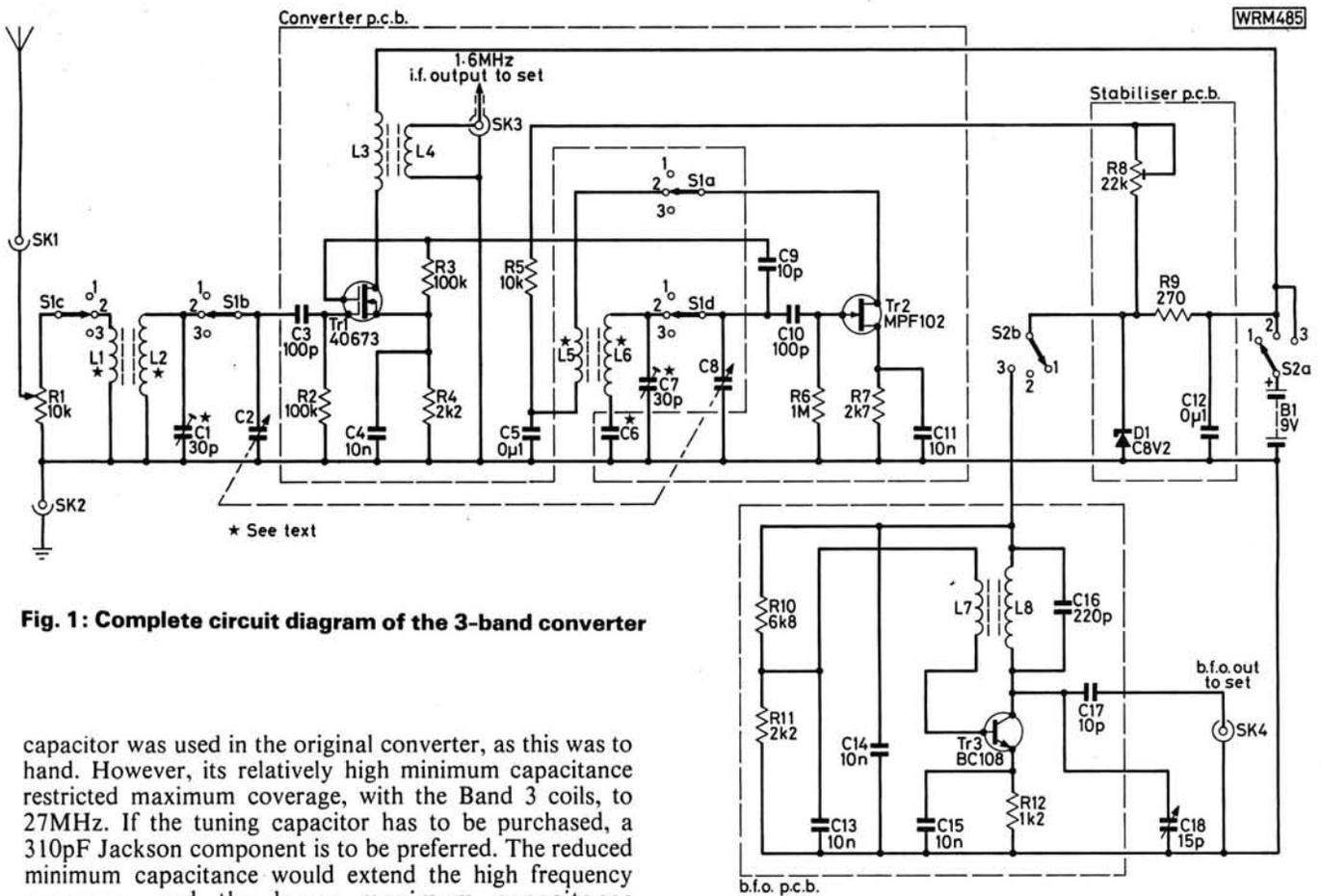


Fig. 1: Complete circuit diagram of the 3-band converter

capacitor was used in the original converter, as this was hand. However, its relatively high minimum capacitance restricted maximum coverage, with the Band 3 coils, to 27MHz. If the tuning capacitor has to be purchased, a 310pF Jackson component is to be preferred. The reduced minimum capacitance would extend the high frequency coverage, and the lower maximum capacitance would impart a useful reduction in the tuning rate. With the specified coils, there would still be an overlap on all three bands, thus ensuring continuous coverage. If the variable capacitor has integral trimmers, these must be removed. Chassis mounting, rotary, air spaced trimmers were fitted in the original unit, but the type used are no longer readily available. Philips "beehive" trimmers, or the more modern polypropylene dielectric rotary trimmers, would be ideal. The standard 10mm diameter formers with dust iron cores can be obtained from Electrovalue.

All of the fixed capacitors used for r.f. coupling, tuning and padding are 5 per cent tolerance polystyrene components, and two capacitors have to be connected in parallel to give some of the non-standard C6* padder values.

The 6:1 ratio reduction drive, drive drum, spindle couplers and tension spring are all manufactured by Jackson Brothers, and can be obtained from Watford Electronics. If any difficulty is encountered obtaining nylon drive cord, thin nylon curtain cord is an acceptable substitute.

Inductor Construction Details

All coils are home wound on standard 10mm formers with dust iron cores. Full winding details are given in Table 1.

Locate the coils at the base of the former or it will not be possible to completely withdraw the dust iron core and the amount of inductance variation will be curtailed. All turns are wound in the same direction and held in position by a liberal application of Balsa cement.

Anchoring the start and finish of the winding to pegs pushed into the former mounting holes is a good way of keeping the turns in place until the cement hardens. With the exception of L7 and L8, the coils consist of a coupling, or feedback winding, wound over the main tuned winding.

The cushioning effect of a thin strip of paper masking tape laid over the main winding will help to secure the turns of the coupling coil until adhesive can be applied to lock them in position.

If about 150mm of wire is left at the start and finish of the windings, it is possible to connect the coils directly into circuit. However, the 38 s.w.g. wire used for some of the coils is really too fine for this, and it is desirable to provide some means of anchoring the leads close to the windings.

CONSTRUCTION RATING Intermediate

BUYING GUIDE

All components required for this project are readily available from advertisers in *PW*. Jackson Bros. tuning capacitors and drives are available from Watford Electronics


APPROXIMATE COST £35

TABLE 1

RF COILS	No. of turns			Notes
	Antenna	Tuned	Padder	
	L1	L2		
Band 1 1.6-6MHz	7	45		38 s.w.g. close wound
Band 2 4-15MHz	4	18		26 s.w.g. close wound
Band 3 7-30MHz	2	9		26 s.w.g. tuned winding spaced over 7mm

OSC. COILS	Feedback	Tuned		
	L5	L6	C6*	
Band 1	6	27	330pF	38 s.w.g. close wound
Band 2	3	14	970pF	26 s.w.g. close wound
Band 3	3	8	2nF	26 s.w.g. tuned winding spaced over 6mm

IF, BFO COILS	L3	L4		
	L7	L8		
1.6MHz IF	120	20		38 s.w.g. L3 pile wound. L4 wound over L3
450-470kHz BFO	30	150		38 s.w.g. pile wound

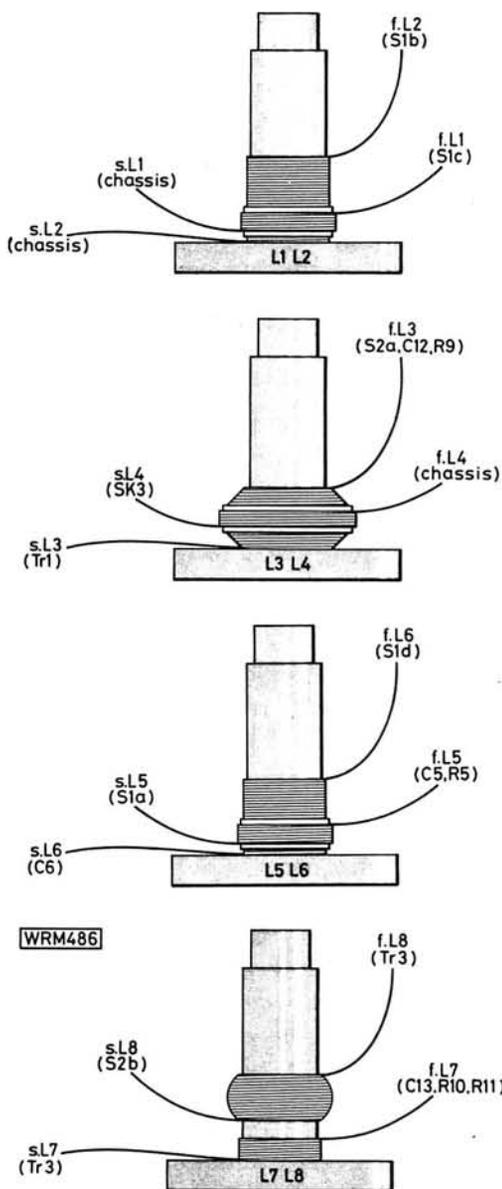

S = start of winding, F = finish of winding. All turns are wound in the same direction

Slightly undersize holes are drilled in small squares of 5mm Perspex sheet, and these are reamed out until a tight push fit is obtained on the coil formers. Veropin terminal pins are pressed into holes drilled at the corners of the squares, and the coil leads are soldered to these. Paxolin or plain Veroboard could be substituted for the Perspex.

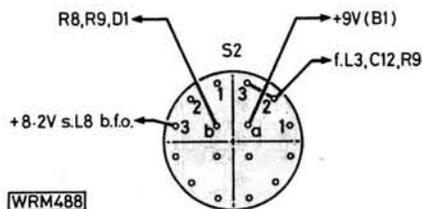


Fig. 2: Connections to ON/OFF switch S2. Position 1 OFF, 2 CONVERTER ON and 3 CONVERTER AND BFO ON

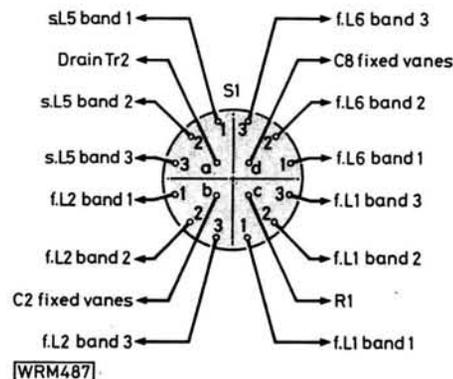


Fig. 3: Connections to band selector switch

★ components

Resistors

$\frac{1}{4}$ W 5% Carbon film

270 Ω	1	R9
1.2k Ω	1	R12
2.2k Ω	2	R4, 11
2.7k Ω	1	R7
6.8k Ω	1	R10
10k Ω	1	R5
100k Ω	2	R2, 3
1M Ω	1	R6

Linear potentiometer

10k Ω	1	R1
--------------	---	----

Pre-set miniature horizontal

22k Ω	1	R8
--------------	---	----

Capacitors

Disc ceramic

10n	4	C11, 13, 14, 15
0.1 μ F	1	C12

Polystyrene

10pF	2	C9, 17
100pF	1	C10
220pF	1	C16
See Table 1	—	C6

Air spaced twin gang variable

(See text for value)	1	C2, 8
----------------------	---	-------

Trimmers

15pF Jackson C804	1	C18
3–30pF (See text)	6	C1*, 3–7*

Semiconductors

Transistors

40673	1	Tr1
MPF 102	1	Tr2
BC 108	1	Tr3

Diodes

BZY88C8V2	1	D1
-----------	---	----

Inductors

(Refer to table for details)	8	L1–8
------------------------------	---	------

Miscellaneous

Coil formers, 10mm with dust-iron cores (8); 26 and 38 s.w.g. enamelled copper wire; 4-pole 3-way rotary switch, type CK (2); Ball drive 6:1 ratio Jackson 4511 (1); Drive drum 137mm dia. Jackson 5017 (1); Nylon cord, tension spring, 6mm spindle and bush; Belling Lee co-axial plug and socket (2); 4mm insulated terminals (2); 175 x 125 x 63mm standard aluminium box (1); p.c.b. (3); control knobs (5).

Next Month

Part 2 of this article will conclude with the mechanical construction of the 3-band s.w. converter and provide comprehensive setting-up and alignment details.

Full details of the interface with suitable m.w. receivers will be given.

THE CB CODE OF PRACTICE

READ YOUR LICENCE—It tells you what you can and cannot do. The conditions have deliberately been made simple with few restrictions. It is up to you to develop this service as you wish for the benefit of all. This means having consideration for one another and recognising that no-one has preferential rights at any time or place or on any channel. NATCOLCIBAR, the Parliamentary CB Working Party, and representatives of industry have in consultation with the Home Office prepared this simple code of practice. If you work to it, you will help the system to help you.

HOW TO OPERATE

1. **LISTEN BEFORE YOU TRANSMIT.** Listen with the Squelch control turned fully down (and Tone Squelch turned off if you have Selective Call facilities) for several seconds, to ensure you will not be transmitting on top of an existing conversation.
2. **KEEP CONVERSATIONS SHORT** when the channels are busy, so that everyone has a fair share.
3. **KEEP EACH TRANSMISSION SHORT** and listen often for a reply—or you may find the station you were talking to has moved out of range or that reception has changed for other reasons.
4. **ALWAYS LEAVE A SHORT PAUSE BEFORE REPLYING** so that other stations may join the conversation.
5. **CB SLANG ISN'T NECESSARY**—plain language is just as effective.
6. **BE PATIENT WITH NEWCOMERS AND HELP THEM.**

EMERGENCIES AND ASSISTANCE

7. **AT ALL TIMES AND ON ALL CHANNELS GIVE PRIORITY TO CALLS FOR HELP.**
8. **LEAVE CHANNEL 9 CLEAR FOR EMERGENCIES.** If you have to use it (for instance to contact a volunteer monitor service) get clear of it as soon as you can.
9. **IF THERE IS NO ANSWER ON CHANNEL 9,** then call for help on either channel 14 or 19 where you are likely to get an answer.
10. **IF YOU HEAR A CALL FOR HELP, WAIT.** If no regular volunteer monitor answers, then offer help if you can.
11. **THERE IS NO OFFICIAL ORGANISATION FOR MONITORING CB AND NO GUARANTEE THAT YOU WILL ALWAYS BE IN REACH OF A VOLUNTEER MONITOR.** CB IS *NOT* A SUBSTITUTE FOR THE 999 SERVICE.

CHOICE OF CHANNEL

12. **RESPECT THE FOLLOWING CONVENTIONS:**

Channel 9: Only for emergencies and assistance.

Channel 14: The calling channel. Once you have established a contact, move to another channel to hold your conversation.

Channel 19: For conversation among travellers on main roads. (Remember, if you are travelling in the same direction as the station you are talking to, not to hog this channel for a long conversation.) Give priority to the use of this channel by long distance drivers to whom it can be an important part of their way of life.

Other: You may find that particular groups in particular areas also have other preferred channels for particular purposes.

SAFETY

13. **USE COMMONSENSE WHEN USING CB** and do not transmit when it could be risky to do so. For example, don't transmit:

- a. When fuel or any other explosive substance is in the open—e.g. at filling stations, when petrol or gas tankers are loading or unloading, on oil rigs, or at quarries.
- b. When holding a microphone may interfere with your ability to drive safely.
- c. With the antenna less than 6 inches from your face.

INTERFERENCE

14. **INTERFERENCE** can be caused by any form of radio transmission. Avoid the risks. Put your antenna as far away as possible from others, and remember that you are not allowed to use power amplifiers. In the unlikely event that your CB causes interference, co-operate in seeking a cure using the suggestions from a good CB handbook. Moving the set or antenna a few feet may cure the problem.

the YL COLUMN

Elaine HOWARD G4LFM

Well here I am again, pen flying over the paper in an attempt to get some coherent thoughts into the magazine this month. So many things that deserve a mention have happened since I last wrote this column that I don't really know where to start.

Most of my news is all tied up with last autumn's Wireless Day at Chalk Pits Museum. Whilst operating mobile on my way there early that Sunday morning I managed to have a QSO with Constance G8LY. Many of you will have heard of Constance as she has been on the bands for many years now and is known to amateurs both old and new. We don't often have the chance to work each other as my home QTH is in what could be called a "radio black hole"! Constance told me one other lady to look out for was Violet G4ESR who would be at the Wireless Day.

Violet Bryan is a "white stick" operator who has two of the most beautiful guide dogs I have ever seen. Not normally being one of this country's dog lovers I was almost persuaded to change my mind after meeting Cindy and Sheba. They were very well behaved all day and didn't even mind being taken round by me whilst Violet and I explored the various stands.

I must say thank-you to those of you who have written to me over the months. If you have been wondering why the YL column doesn't appear every month it's not through lack of material, it's an "occasional" series—but all contributions are always welcome. It is very encouraging to hear from new licensees or not so new, everyone seems to have something to contribute.

Where were all the YL amateurs in the London area during the Breadboard Exhibition November 11–15? In the three days that I was operating the special event station GB8BB I worked 161 stations, and not one YL amongst them! Even reading through the log book for the whole five days not one lady's name appears—perhaps next year.

One QSO I did have that sticks in my memory was with Jonathan G6GJG, his callsign arrived in the post early Saturday morning and about his sixth contact was GB8BB. A new licence holder and just 14 years of age!

I have heard that there were a lot of YL RAE passes from last May's exam, so there should be a lot of G6s on the air. I must admit that I haven't heard many yet, but there's still plenty of time. Many ladies are learning the Morse very quickly, passing the test, then trading in their old callsigns without them ever being printed in the Call Book. Not a

bad achievement I think, and YLs on the h.f. bands are even more a rarity than on v.h.f., as some will no doubt have found out by now.

I will finish up with some of the comments that have arrived on my desk in some of the letters, if only to show that I do read them! Sheila G8KPL wrote telling me about the stations she worked during a lift, and right back in last July she had worked 91 QTH squares and was well on the way to the magic 100. Perhaps by now she will have completed that, but she was working EA stations on both side-band and f.m. modes of operation. Anne G4MBA has a good motto, if you can't beat them—join them, her husband is G4EDJ and has been licensed for over six years. Due to working during the day Anne has joined the local "Early Birds" net, from 6.30 to 7.30 in the mornings on 160m a.m.

Jeff Herbert sent me the results of the Colchester Radio Club 2m contest. It was held over three months and the number of stations worked were collected from members at the fortnightly club meetings. Scoring was simple, one point per simplex contact, repeater and mobile contacts were void. The final results were G8OVQ Jack with 251 points, and Jane G8WQY (who now has a G4 call) came second with 244 points. Jeff says that the club has four ladies in their membership, all with G4 callsigns and, who knows, that number may have risen since his letter.


Lastly, but not least, G6AIS wrote just saying what an enjoyment amateur radio is, and that next it is the Morse and a G4 callsign. "Now I press on with the Morse so that once more I can travel the world as I once did in working days, and call to mind the lovely places, islands with coral beaches, great cities full of beautiful architecture, and dusty bazaars with teeming multitudes and most of all blue skies and sunshine, and all this from a comfortable chair in my little Radio Room." What a lovely idea.

73s to you all until it's my turn to write again.



"How high are you, and do you suffer from wind?"
"About 5ft 8in and only when I eat beans!"

... heard on 2m by Ms A. C. Allen, G4HRH

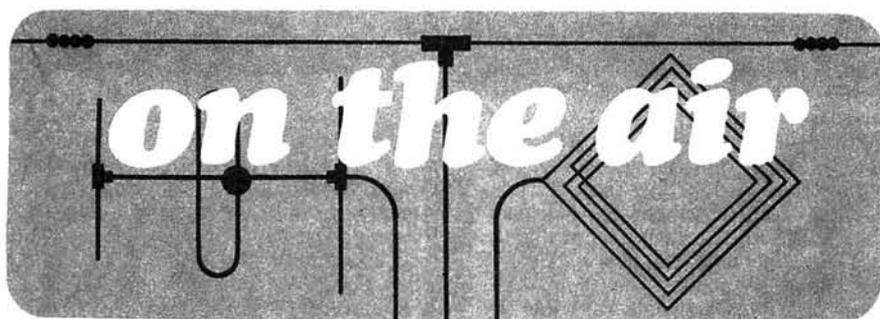

Amateur Bands

by Eric Dowdeswell G4AR

Reports to: Eric Dowdeswell G4AR
Silver Firs, Leatherhead Road,
Ashted, Surrey KT21 2TW.
Logs by bands in alphabetical order.

Greetings all, and a Very Happy New Year. May all your RAE's be happy ones. I hope that not too many of you were lumbered with CB rigs that you didn't want, considered by many dotting relatives to be a "natural" as a Christmas gift for the radio-minded offspring.

As some of you may know the 1.8 to 1.9MHz section of the 160m amateur band has been released to US amateurs by the FCC for c.w., a.m. and s.s.b. modes, with power inputs up to 1kW on an exclusive basis with the exception of certain restrictions to safeguard Loran navigational stations in eastern Canada. The US chain of Loran-A stations has been closed down to the joy of amateurs over there who have suffered incomprehensible restrictions on operation since 1949, with limitations on power varying with the time of day or night and from state to state.

Amateur operation in the segment 1.9 to 2.0MHz remains in some doubt even though the whole band 1.8 to 2.0MHz was earlier expected to be released with full privileges. With the advent of several other countries on to 160m in recent times, the band should become even more interesting with this news from the States. Many multiband h.f. transceivers now include Top Band, with a consequent increase in the amount of s.s.b. operation to be heard. In the past DXing has been inclined to be concentrated on c.w. at the low frequency end of the band.

The main problem on Top Band, especially for the transmitting amateur, is getting a suitable antenna system going, especially when one realises that the quarter wave wire is over 40 metres long. For DX working the antenna should be vertical over an extensive ground plane. In the event the wire is kept vertical as far as possible and then the remaining wire allowed to go off horizontally, or sloping, to the nearest support. In this case the wire is fed at the bottom and can go straight to the receiver usually. For transmitting a balun is advisable.

While a 40 metre-long wire is low impedance at the shack end on 160m it

may be a good idea to check with the receiver's manual as to the set's input impedance on this band as, in some cases, it may very well be different from the other h.f. bands. Anyway, as you may be sick of reading in this column, an antenna tuning unit should always be used with such a wire. The wire may be shorter if physically necessary, but resonated by the a.t.u.

An 80m centre-fed antenna with tuned feeders will work well on 160m if the a.t.u. is suitably modified for Top Band. Every effort must be made when transmitting on Top Band to get as good an earth system as possible, to the extent of laying down radial wires under the vertical portion of the antenna. This may take the form of wires a quarter wave long radiating from a central earth rod or even a buried galvanised water tank discarded by a builder. In practice the wires can be any old length to suit the QTH with as many as possible.

The far end of each wire ought to be soldered to a copper earth rod driven into the ground. This is not so impracticable as it sounds as the small-bore copper pipe used for domestic heating systems is quite cheap and offcuts are even cheaper and quite adequate.

To bury the wires I use the plywood end-cheek from an empty cable reel, freely given by almost any electrical dealer! Just run it along the lawn pushing it in for a depth of about three inches, repeating the process to push the wire into the slot. Use any old copper wire, bare, insulated or whatever with old coaxial cable eminently suitable. Don't worry about scars across your favourite lawn as they will disappear in a very short time! All joints must be soldered and then taped against corrosion. A butane hand torch is very useful when working beyond soldering iron range.

Hello Clubs

To those hard-working secs and PROs whose efforts have doubled the clubs' membership in the last year, well done! Rest assured, it will more than double again in the coming year! So let that be a lesson. I note the odd club where debate has centred around whether CBers should be accepted as members. Can there possibly be any argument on this point?

Every club needs a continuous injection of new blood if it is to survive and here it is for the asking. Legal and illegal CBers are far from the idiot, drooling, incomprehensible "breakers" the American

films would have us believe. So let them be most welcome, in every club.

Wimbledon & District RS Second and last Friday of every month with the venue at St Johns Ambulance Hall, Kingston Road, Wimbledon, London SW19. Ted Allen G3DRN, boss of the RSGB's QSL bureau, is the new secretary and busy arranging the new season's programme. He can be found at 30 Bodnant Gardens, Wimbledon SW20 0UD.

Crawley ARC Formal meetings normally held at the Ifield Trinity United Reformed Church with informal gatherings at members' QTHs. A code class is being run by Ken Franklin G3JKF who can tell you more on Crawley 28080 with Vernon and Dot Davis the ones to ask about club details, on Crawley 26316.

Cambridge & District ARC Every Friday round about 7.30 in the Visual Aids Room of the Coleridge Community College, Radegund Road, Cambridge, just off Coleridge Road. In the Tower Room will be found the club stations for v.h.f. and h.f., operating under the call G2XV. A very special welcome is on hand for any CBers says David Wilcock G2FKS, 19 Cavendish Avenue, Cambridge CB1 4UP (CB1!) or on 0223 247220.

Bolsover ARS Relatively new group meets every Wed at 8pm at The Angel, Bolsover, with Morse tuition starting half an hour earlier, courtesy G3MOK. Coming events include a talk on meteor scatter techniques plus a visit to the local Radio Hallam. Contact David Brocklehurst G8KIF, 33 Chestnut Drive, Clowne, near Chesterfield S43 4JG or ring 0246 811666.

Milton Keynes & District ARS January gathering will reveal all on receivers and test equipment at the Lovatt Hall, Silver Street, Newport Pagnell at 8pm on the second Monday, which is a regular date every month. Feb's meeting will deal with photo acoustics. It's D. O. White G3ZPA, Rose Cottage, Shenley Brook End, near Bletchley, Bucks MK5 7AF.

Glenrothes & District ARC The Club Room at Provostland, Leslie, Fife, at 7.30 every Wednesday but also, unusually, at the same time on the third Sunday with talks, lectures or a demonstration. Nobody has been inveigled into the sec's job at the moment so Chairman John Halliburton GM4AQO at 72a Ramsay Road, Kirkcaldy, Fife, will help out with club information, which is also 0592 266287.

Exmoor RC New sec reporting in is David Jones G6CHZ, Loughrigg, East Street, South Molton, Devon, with meetings at this QTH every Thursday at 8pm active with club station G8SSS. Near future plans call for RTTY facilities.

Mid-Warwickshire ARS Note new meeting times for the club, 8pm on the first and third Tuesdays at 61 Emescote Road, Warwick, instead of Mondays. So says Mary Palmer G8RZR of 12 Edmondson Close, Woodloes Park, Warwick, club secretary.

Borders ARS In fact covers both sides of the border, meeting on the first and third Fridays, with the new committee about to come up with a programme for

the coming year. Alex McCreadie GM8YPI, 16 Fancove Place, Eyemouth, Borders or Eyemouth 50492 has all the answers.

Cannock Chase ARS Nominated as the member who had done the most for the club in the past year. Larry Arkley G4HMV has been awarded the G3ABG trophy, named after the late John Morris. Meetings every Thursday at the Bridgtown War Memorial Club, Union Street, Bridgtown, Cannock, says PRO J. Gregory, 22 Tower View Road, Great Wynley, S. Staffs WS6 6HE or Cheslyn Hay 416419.

Barry College RS New sec is John Share GW3OKA of 3 Uplands Crescent, Llandough, Penarth, S. Glam or 702455, who, in the 70s did ditto with the Wirral DX Assoc and the Wirral RS. After some blush-making comments on the new-look *PW* John says club considers *PW* as best market place for new members. Needless to say all such will be welcomed with open arms. (See note later.)

Torbay ARS Has club stations G8IUI and G3NJA now all cock-a-hoop after getting top spot on 1.8MHz in NFD and 10th place overall. Meetings Fridays 7.30 at Bath Lane, Torquay, rear of 94 Belgrave Road, are informal but you'll need your tie apparently for the formal do on the last Saturday of every month, same time and place. RAE course runs at the Torquay Tech College says sec Hugh Davies G4DZH.

Cheshunt & District RC An excellent printed guide to the club and its activities awaits prospective members with an invite to attend for up to four weeks before being pestered to join! Full details of club officials and phone numbers all help to put the newcomer at her/his ease. Other clubs please copy! So, it's every Wednesday at 8pm, Church Room, Church Lane, Wormley, Herts, with Jan 6 being devoted to nattering but the 13th is all about radio equipment with the 27th offering video tapes on an Introduction to Amateur Radio and SSB HF Field Day 1981. Why not ring Bob Gray G6CNV on Dane End 203 if you'd like to go along.

Southdown ARS Has club station G3WQK quite active with meetings first Mondays at 7.30 at the Chaseley Home for Disabled Ex-servicemen at Southcliff, Eastbourne, E. Sussex. Excellent club mag adds interesting items on mobile STD in DL-land and those Euro-pips from the paging system in DL and F just below 88MHz on Band II. Drop a line or ring R. E. Holtham G4EKS, 2 Benbow Avenue, Eastbourne or 32777.

Maidstone ARS A steadily growing membership is blamed on the publicity in *PW*! Good lectures are a big factor of course, witness Jan 8 when Rowley Shears G8KW of KW Electronics will be presenting his new range of equipment. On Jan 22 a Mr Gibson will be talking on the RSGB's amateur radio insurance scheme. It's first and third Fridays around 8pm at the YMCA Sportscentre, Melrose Close, Cripple Street, Maidstone, Kent, which includes the beginners' classes with more formal meetings on the other Fridays. On Tuesdays there are informal question and answer sessions, also

at 8pm. However, Graham Edy G4AXD is waiting to tell you more at 29 Beech Road, East Malling, Maidstone, Kent which also hides West Malling 841021, strange to relate.

Wakefield & District RS Alternate Tuesdays. UGH! but you can work it out from meetings on Jan 12, a talk on crime prevention with the emphasis on vehicle security, and Jan 26 when there is a junk sale. Place is Holmfield House, Denby Dale Road, Wakefield, at 8pm. All visitors are most welcome says sec R. Sterry G4BLT, 1 Wavell Garth, Sandal Magna, Wakefield, or ring Wakefield 255515.

Stevenage & District RS Still meets first and third Thursdays at the staff canteen, British Aerospace Dynamics, Site B, Gunnels Wood Road, at 8pm. Membership has increased by 30 in last couple of months so you'll have to get there early if you're going to get a seat! Contact Steve Clarke G8LXY at 126 Putteridge Road, Luton, for all the gen on meetings etc. Just to keep up your interest there is a computer evening on Jan 7 so take yours along, while on the 21st G3WTV will chat on the QSL bureau, with an early date on Feb 4 when G4HED deals with the Morse code.

Hastings Electronics & Radio Club Club mag *Vital Spark* says club meets third Weds at the West Hill Community Centre, Hastings, for formal gatherings, with Mondays being computer nights and Fridays social nights at the Club Room, 479 Bexhill Road, St Leonards-on-Sea. Jan 20 is down for a talk on meteor scatter techniques but membership sec Paul Brown G8OXD, 7 Scutes Close, Hastings, will fill in the details.

Mid-Sussex ARS Marle Place Further Education Centre, Leylands Road, Burgess Hill, W. Sussex, at 7.30pm with AGM on Jan 28. Magazine *Mid-Sussex Matters* raises very important issue of careless talk on our bands, particularly on v.h.f. and u.h.f. where personal movements are frequently discussed quite openly with other amateurs. After all, amateur band receivers are freely available to one and all, and we don't want to tell others when we will or will not be at home! If you are interested in the club drop a line to Jack Brooker G3JMB, 20 Farnham Avenue, Hassocks or ring him on 4965. Sorry, should have added that meetings are on second and fourth Thursdays of the month.

Conwy Valley ARC With a programme of speakers until June next, at Green Lawns Hotel, Colwyn Bay, second Thursdays at 7.30pm. Highlight will be a visit by members of British Telecoms Radio Interference Branch, but contact sec J. N. Wright GW4KGI, Eleven, Bryn Derwen, Abergele, which also answers to 823674.

Radio Society of Harrow Meets Friday evenings 8pm in the Roxeth Room of the Harrow Arts Centre, High Road, Harrow Weald, Middx., with members enjoying spacious accommodation and ample seating, licensed bar at special prices plus coffee and biscuits. What else could one want? Full v.h.f. and h.f. band facilities through club station G3EFX on informal evenings. On Jan 8 talk and

demo on Brit Telecoms radiophone and paging systems with a film show on the 22nd, other Fridays being informal. More from Chris Friel G4AUF who will respond on 01-868 5002.

West Kent ARS Alternate Fridays, again UGH!, at the Adult Education Centre, Monson Road, Tunbridge Wells, Kent, with informal meetings at each following Tuesday at the Drill Hall, Victoria Road, TW. But it looks like Jan 8 when G8CAA talks of System X and beyond (sci-fi or simply telephones?) with a lovely junk sale on the 22nd. Club mag *QLF* tells us how to use an iambic keyer properly, much of which was new and useful to me, so obviously I've been making hard work of it! Why not ring Brian Castle G4DYF on Sevenoaks 56708 for the latest on the club.

Braintree ARS It's the Braintree Community Centre, Victoria Street, Braintree, first and third Mondays and around 7.45pm will do. Editor of club mag *BARSCOM* is Bob Willicombe who, with XYL Norma, is all set to take the RAE 'ere long, spurred on by the success of 15-year-old son David. So, who's turn is it for the rig tonight? Ask Norma for more details at 355 Cressing Road, Braintree, Essex.

Barry College RS Again. Late news is that due to great influx of new members meeting times have been increased and are now first and second Thursdays at the College Annex, Weycock Cross, Barry, with lectures and opportunities to buy and sell equipment. Space has been found for the demonstration of amateur radio and allied interests. One for diary is the Barry Mobile Rally on May 23 at the Barry Memorial Hall.

Ipswich RC Reminder of the East Suffolk Wireless Revival annual event to be held on May 30 this year at same venue, adjacent to the Suffolk Show ground. Club meetings second and last Wednesdays in the Clubroom of the Rose and Crown, 77 Norwich Road, Ipswich. Rooms are detached from the public bars so nothing to stop juniors coming along. Talks and lectures are backed by code classes plus active participation in field events by club stations G4IRC and GB2IRC. Jack Toothill G4IFF, 76 Fircroft Road, Ipswich or 0473 44047 can enlarge on the details. Should mention Jan 27 when Henry Massey G8YXP, lecturer at the Suffolk College, will explain the RAE.

Bournemouth RS Suppose I'd better mention this club since I imagine most of the *PW* staff are members, or ought to be if they are not! New venue since I last heard from them is the Kinson Community Centre, Pelhams, Millhams Road, Kinson, Bournemouth, first and third Fridays at 8pm. Secretary Arthur Bagley G4EKE of 8 Larks Rise, Ferndown, Wimborne, Dorset, awaits the postman with your enquiries about events and membership. Or you can always give him a bell on 0202 877945.

North Bristol ARC Just in time. Fridays 7.30pm at the Self-Help Enterprise Centre, Braemar Crescent, Northville, Bristol 7, where a warm welcome awaits prospective members, says Hon. sec. Ted Bidmead G4EUV, 4 Pine Grove,

MAIL ORDER

FROM



by two way
FREEPOST

MORSE KEYS		
HK 707	Straight Up/Down keyer	£11.44
BK 100	Semi-automatic mechanical bug	£17.88
MK 702	Up/Down keyer on marble base	£22.43
MK 702	Manipulator	£22.43
MK 704	Squeeze paddle	£14.38
MK 705	Squeeze paddle on marble base	£22.43
EKM 1A	Morse code practice oscillator	£8.63
MK 1024	Automatic memory keyer	£135.13
EK 150	Semi/Automatic keyer	£74.75

LINEAR AMPLIFIERS		
2M10-80P	144MHz 10W input/80W output with 9dB preamp	£138.00
2M25-150P	144MHz 25W input/150W output with 9dB preamp	£184.00
2M10-150P	144MHz 10W input/150W output with 9dB preamp	£209.88
2M3-150P	144MHz 3W input/150W output with 9dB preamp	£209.88

G. WHIP Mobile Antennas		
Tribander 10-20 Slide		
		£25.88
L.F. Coil 40/80/160 MTS		£6.56
L.F. Whip Telescopic		£4.26
Multimobile 10-20 Auto		£30.48
M/Mobile Coil 40/80/160		£6.56
M/Mobile Whip Telescopic		£4.26
Flexiwhip 10M Mast		£18.11
F/Whip Coils 40/80/160		£6.56
Base Standard		£6.00
Base Heavy Duty		£6.50
Extendarod		£12.00

SHURE MICS		
201	Hand ceramic omnidirectional high impedance	£14.49
202	Hand ceramic noise reducing high impedance	£15.18
401A	Hand controlled magnetic high impedance	£16.56
401B	Hand controlled mag. low impedance (200 ohms)	£16.56
444	Desk adjustable height controlled magnetic	£32.43
526T	Desk controlled response transistor preamp	£39.33

DAIWA		
CNA 1001 Auto ATU 200w RMS		£128.00
CNA 2002 Auto ATU 1Kw RMS		£185.00
CN 620A RF Power Meter 1.8 to 150 Mhz 1Kw		£49.99
CN 630 RF Power Meter 140-450 Mhz 200w		£69.00
SR11 Scanning Receiver		£49.00

STILL HELPING WHERE IT HURTS				
Here's a list below to make buying easier for you - Work it out yourself - You'll see - It really is easy!				
"And guaranteed for two years"				
	<i>List</i>	<i>Price</i>	<i>Deposit</i>	<i>12 Payments</i>
<i>Product</i>				
Yaesu FT 902DM	£885	399		£40.55
Yaesu FRG 7700/S	£329	£139		£15.89
Yaesu FRG 7700/M	£409	£180		£19.01
Yaesu FT 101ZD/FM	£665	£300		£30.41
Yaesu FT 101ZD/AM	£650	£275		£31.29
Yaesu FT 101Z/FM	£590	£250		£28.27
Yaesu FT 101Z/AM	£575	£225		£29.15
Yaesu FL 2100Z	£425	£185		£20.08
Yaesu FT1	£1295	£600		£57.91
Yaesu FT 480R	£379	£185		£16.18
Yaesu FT 707	£569	£230		£28.27
Yaesu FT 290	£249	£120		£10.82
Standard C78	£219	£99		£10.04
Standard C58	£247	£107		£11.69
ICOM 730	£574	£250		£27.00
ICOM 720A	£883	£400		£40.26
ICOM 290	£366	£166		£16.67

If you don't like easy payments call us anyway for price.

MICROWAVE MODULES	
MMT 432/28S	£149.00
MMR 432/144R	£184.00
MMT 28/144	£199.00
MMT 144/28	£99.00
MMC 28/136	£27.90
MMC 28/156	£27.90
MMC 28/144	£27.90
MMC 144/any IF	£27.90
MMC 144/28LO	£29.90
MMC 70/any IF	£27.90
MMC 432/28S	£34.90
MMC 432/144S	£34.90
MMC 1296/any IF	£32.20
MMC 050/500	£69.00
MMA 28 preamp	£14.95
MMA 144V preamp	£34.90
MMV 1296/28	£32.20
MML 144/100 linamp	£142.60
MML 432/100 linamp	£228.85
MML 144/25 linamp	£59.00
MML 432/50 linamp	£119.00
MM2000	£169.00
MMS 1	£115.00

UNADILLA/REYCO	
Antenna Traps-	
Precision moulded coil forms stainless - hardware - Aluminium tube irridit finish - Coated aluminium wire. Fully waterproofed.	
Available 7/14/21 MHz	£12.99

W2AU BALUN	
3.5/30 MHz 2.5 Kw with Lighting Arrestor - Suitable Veas, Yagis, Doublets, Quads etc.	
	£12.99

STANDARD	
C8800 2m, Tcwr	£252.00
C7800 70cms Tcwr	£275.00

TRONIXPSU	
British made, 5 amp constant, 7 amp surge, fully regulated and protected.	
	£27.90

FDK Multi 700EX	
	£199.00
FDK Multi 750E	
	£299.00

Send 50p for our bumper bundle literature

No Quibble Guarantee
Same Day Despatch
All Items Advertised

Choose your AMTECH here		
Amtech 100 Mobile Match		£16.95
Amtech 200 Random Wire ATU 10-160m 200w pep		£29.95
Amtech 300 Random and Coax Fed ATU 300w pep		£43.95
Amtech CW 250 - The most outstanding CW filter available		£24.90
Amtech Channelguard - A plug in device to eliminate those unwanted stations	Decoder	£15.25
	Sender	£7.25
Amtech FM7: FM Demodulator for FRG 7		£11.90

ANTENNAS	
Wide range in stock including JAYBEAM - HYGAIN - GOTHAM - TELECON - HOKUSHIN etc.	
Bantex 5/8 whip complete antenna	£8.99
Bantex 1/4w whip complete antenna	£3.50

YAESU CONVERTERS 7700 Series	
Model A	£63.00
Model B	£69.00
Model C	£65.00
Model D	£66.00

ROTATORS	
Skyking SU 4000	£92.00
Hirschmann 250	£35.00
Emoto 502CXX	£139.75
KR 400RC	£92.85
AR 40	£59.00
KR 950 2A	£50.00
Rotor Bearing	£12.00

*All items VAT and carriage paid.

ICOM IC 730. All bands 10-80m including 30m, 17m and 12m. 100w RF out and 40w AM. Twin VFO, digital readout, 3 speed tuning down to 10Hz. Dial lock, RIT, N.B. and Switchable Preamp. See list for H.P. details.	

SWR/RF POWER METERS	
SWR 25 3.5/170 MHz	£12.94
LEADER LPM 885-HF 1Kw	£58.00
HANSON 3.5/150MHz 200w	£28.75
REECE UHF 74 144/432	£16.28
HANSON FS 500H	
1.8/60MHz 2Kw	£67.85
OSKAR SWR 200	
3.30 MHz 2Kw	£40.00

Goods by return post.
(All items in stock at time of going to press).

AMCOMM SERVICES

194 NORTHOLT ROAD, SOUTH HARROW, MIDDX.
Telephone: 01-864 1166, 01-422 9585
Opposite South Harrow Tube Station on Piccadilly Line

Showroom Opening Hours
Tuesday to Saturday 9-5.30
Sunday by Appointment

All items over £100
available on easy terms
at List Price

NO POSTAGE REQUIRED

**AMCOMM SERVICES (PW1),
FREEPOST,
HARROW HA2 OBR.**

Please send me.....

at.....enclosed cheque/P.O. for

.....or charge my VISA/ACCESS

Nr.....

Name.....

Address.....

..... Post Code

SPECIAL!

THE CB ANTENNA THAT WORKS WELL ON 10 METRES

Hy-Gain SILVER ROD 1/2 WAVE OMNIDIRECTIONAL BASE STATION ANTENNA

The Silver Rod omnidirectional 40-channel Base CB Antenna has short, curved radials for easy installation in even the tightest spaces. RF energy is fully decoupled from coax and support for low SWR and maximum talk power.

Features rugged aluminium construction. Vertically polarized. The Silver Rod develops its 3.8dB transmitting gain through pattern compression, creating a lower angle of radiation.

Matching transformer provides DC ground, resulting in lower residual noise level – as much as 20dB below an ordinary antenna.

- 17'8" tall with short, curved, space-saving radials for full 1/2 wave performance
- RF energy is decoupled from coax and support for low SWR
- Rugged aluminium construction featuring taper swaged tubing
- 4dB gain derived from pattern compression and low radiation angle
- DC ground for draining precipitation static
- Supplied with 10m instructions added.

(Mounting mast not included)

SPECIAL PRICE

£20.00

inc. VAT
Securicor Delivery £5.00.

RADIO SHACK LIMITED
188 BROADHURST GARDENS,
LONDON, NW6 3AY
TELEPHONE 01-624 7174
TELEX 23718

Just around the corner from West Hampstead Station
on the Jubilee Line.

M&B RADIO


INVERTED VEE DIPOLES ONLY £32.00

MULTIBAND 10-11-15-20-40-80 meters

■ 2kW Handling Power

■ Heavy Duty Stranded Non-corrosive
& Plastic Coated

■ Total Length 26 meters

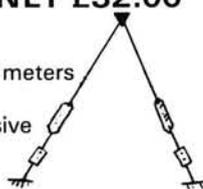

RADIATION DETECTOR ONLY £2.70

COMPLETE WITH INFORMATION


■ Metal Cased

■ Quartz Fibre Type

■ Contains 3 Lenses

■ Only the Size of a Pen

DETECT RADIATIONS BEFORE IT IS TOO LATE

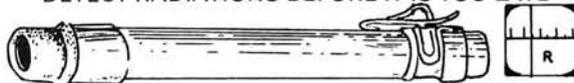

BOSCH 2.5kV 40uF Capacitors

£8.00 VAT & P&P extra

LED Displays SND70 1/4 in. common cathode

25p VAT & P&P extra

12 VOLT 4 pole continental type relays

50p VAT & P&P extra

WAVEGUIDE type 16 ft. sections copper type

£5.00 VAT & P&P extra

WAVEGUIDE square flanges

£2.75 VAT & P&P extra

MINIATURE type uniselector

£1.50 VAT & P&P extra

MINI-REGULATED PSU's 5-0-5 volts, 7.5-0-7.5 1.5 amp.

£3.50 VAT & P&P extra

ORDERS SENT ON RECEIPT OF ORDER

M&B RADIO 86 BISHOPSGATE STREET
LEEDS LS1 4BB
TEL (0532) 35649

MYERS ELECTRONIC RESEARCH

Synchronous Detection Radio Receiver Module

- ★ All RF processing by Plessey SL 600/1600 range
- ★ Demodulates any AM signal in the range 200kHz to 20MHz
- ★ May be used as an IF strip or a complete receiver
- ★ Ultra fast 'intelligent' AGC with audio levelling
- ★ 1 mA 'S' meter output
- ★ Tantalum & monolithic ceramic capacitors and 1% resistors throughout
- ★ screen printed earth plane board
- ★ Advanced all IC design
- ★ User selectable sig/noise or sig level muting
- ★ DC operated audio gain and muting level
- ★ Ultra stable performance – non critical supply volts or temperature
- ★ Easily modified for SSB/CW
- ★ May be used as direct conversion receiver

£1.00 in the post brings complete data package (circuitry – user notes – IC data)

The size of the module is 8.5 by 10cm

COMPLETE TESTED MODULE£54.95

KIT FORM MODULE£39.95

(Both inclusive of VAT and post and packing)

As described in detail in last months P.W.

MYERS ELECTRONIC RESEARCH
Customer Services Division,
145a Ashley Road, Hale,
Altrincham, Cheshire WA14 2UW.

Northville, Bristol BS7 0SL, bemoaning the continuing absence of Chairman Ernie G2DWI due to a spell in hospital. Get well soon. OM.

DX Time

Jim Dunnett of Prestatyn, Clywd, spends a lot of time with his SRX-30 and Creed 78 page printer on the RTTY frequencies printing out such as Y34YO on 7MHz, EC2X1, N1NBK, UK2BAB, 4N7NS and 4X6CV on 14MHz, and KA9EDK, KB9IS, VE2JR on 21MHz. Many Americans on 28MHz were supplemented by TR8WR and YB2AG. In the c.w. mode Jim found FY7YE, HK0BKX on San Andres, KP4KK/DU2, and MIC on 21, with XE2KF and ZS1XR on 28MHz. 10m band has been good for Jim of late, often finding it chock full of stations.

In Gower, Swansea, the CR100 of **Philip Morris** aided by a 40 metre-long wire and a 40m dipole ranged between 10 and 160m on s.s.b. Working backwards, he found EA8AK and EA9EU plus 4X4NJ and W2HCW on 160m s.s.b. ZL2BT, 4S7MX, FP0GAQ and 6W8HL on the 80m band. Catches of note on 40m were ZD7HH and P41C while 20m produced J28DM and lovely KC4USV, ending with FK8DH, YJ8NMP and 5W1DQ on 15m and FR0FLO on 10m.

From **David Warr** (Weymouth) comes news of the Safari Net around 21-290 MHz starting at 1830Z enabling him to log some fine catches like FP0GAP on St Pierre Is with GAQ at the same QTH. HS1ANN, J3AH, KH6CF, S83H, TR8BJ, G3AAE/VP9 and 7P8BX. On 10m, David found HV3SJ, 5H3TN and 9Q5FL. The 20m band produced VP2KAL, 3X1Z and 8R1RBF with sole VU2NKR of note on 40m. David uses a newly-acquired FR-50B and a ZL-special cut for the 15m band.

John East of Highworth, Wilts, is still breaking records with his remarkable HAC three-transistor t.r.f. receiver acquiring a coil for the 10 and 15m bands finding such as KX4S, VU2RYL, JH8BJG on 15m and JX7FD, ST2FF, VU2UGI and 8P6T on the 10m band with a 9 metre-long wire. The old 20m coil provided CO7AM, FK8CR, KX6QX on the Marshall Is., Y11BGD who wants cards to PO Box 5864 Baghdad, 3X1Z and 8R1RFB, all in spite of a bout of flu. Needless to say, John gets clobbered by every passing CBER!

From Wadhurst in E. Sussex comes **Rob Gibson** and his FRG-7 plus fan dipoles for 10, 15 and 20m in the loft. Nevertheless, he managed 5H3TC, 6Y5SH, C6ANU, FP0GAQ, G3MUV/CE0, JD1BAE on very rare Ogasawara Island, P29FV, VK9NYG on the Cocos Is and VP8ADR in the Falklands on 10m. Some good ones on 15m included 4S7VJ/5N21 for a strange one, 5R8AL, 6W8KA, A22DC, HM1KR, TR8DX and VP8ADR. The 20m band gave up AH8A on American Samoa, KH6DQ, VK9NS, VR6TC and Y11BGD.

Jon Kempster of Berkhamsted, Herts, BRS45205, is now safely ensconced in his new school where his studies include computers. His log shows such as SV0BV/SV5 who wants cards to PO Box 564, Athens, VP2NFW, VP2KAA, 8P6MH, and K6HNZ/CT3 for 14MHz. On 21MHz he caught S85H, VP9AD, 5Z4NQ, FR0FLO and HB0BHA with 28MHz showing up with N6KT/HK0, 6W8AR, D4CBC, FG7AR/FS7, SV1IA/8 reputedly on Corfu, and VY1CJ in the Yukon for a strange one.

BRS48544 is **John Hayes** of Edmon-ton, London N9, who sports an FRG-7700 and FRT-7700 a.t.u. plus Datong FL2 filter and a long wire. He warns that the STOAT on 10m is a phoney. John says much of his DX was logged using headphones. What else? His long list held such as C5AEG, C31MF, EP2TY, HM0K, J3AH, MIC, P29NAB, SV1DX, TA1AB, V2AS with cards to PO Box 550, St Johns, Antigua, plus V3ME, VK9NYG, VP5WJR, VS6IC, XT2AU, all on 10m s.s.b. On 15m PZ1AN showed up with YA1CP, G4HZI/P/5N21 (whew!), and UM8MAA. Goodies on 20m were AP2SQ, KL7LI, and VP9V. Lower down on 40m, John copped JX7FD, KG4KK, 8P6KK. And C5ACJ came up on 80m.

The Trio R-1000 and 20 metres of wire in the loft have kept **Archie McGrath** (Ramsgate) busy, mainly on 21 and 28MHz copying s.s.b. such as VP2KAC, FP0GAQ (QSL to K8CJK), VP2VD, AA1Q, HV1CN and YB2BJM on 21 and J28DL, ZS6LW, TA1SC plus HP6T working on 28. From Edinburgh, **Anne Edmondson** BRS47285 finds time to drop a line on her activities, which seem to be concentrated on getting ready for the RAE, but gets carried away a bit when digging too deep into the RSGB's *VHF/UHF Manual!* Although expected to be chopped in the current economy drive, a local RAE course has now got under way so Anne is very pleased. She was angry with herself recently, missing CO2OM and KC4ST on the Arabian Net, by falling asleep, but it was 0430! However, in more social hours Anne was able to log AJ1L, FP0GAQ, JY5ZM, V2AU (Antigua), YK1AA, 5N0FCA and 6Y5MJ on her Realistic DX200 and 9 metre-long indoor wire on 20m.

Dave Coggins (Knutsford, Cheshire) and I are both nutters when it comes to wildlife, so we seem to have more to say on that than on amateur radio! He's hoping to send his Labrador up his highest tree with one end of his 40 metre-long wire in her mouth! One way, I suppose. Dave ranges from 10 to 160m on his FRG-7700 and matching a.t.u. plus a 2-element delta beam on 15m and 20/40m W3EDP, finding G3MUV/CE0 on Easter Is., JT1KAI in Mongolia, KH6DX, UK0FAP on Sakhalin Is., and 8R1J on 10m, with amazing goodies like FK8DH, FR0FLO, HK0FBF, KL7U, TI9FAG on Cocos Is., VU2YK, YJ8RG, ZD7HH, ZS6BPL and 5N9ACO/8 all on the 40m band. Much the same on 80m where it was FP0GBG, HC1MD/5, HP3FL (PO Box 76, David, Panama), N6YK/VP2A, OE2VEL/KH6, XE1AE and ZL2BT. Still onwards, or is it

downwards, to 160m for EA3VY, OH0BH, and OH0NA on c.w., and a good one in 4X4NJ, an old timer on Top Band, plus many Europeans.

In General

From Crowthorne in Berkshire **Allan Stevens** seems to have got hooked on the 2m racket listening to repeaters and things on his new Wolfson 1200, but I don't suppose it will last! Foreseeing the rapid exhaustion of the current G6 + 3 calls Allan is wondering what the next series will be and reckons the "M" or 2A to 2Z blocks ought to cause a few pile-ups if they were to be introduced. At least it would make the humble "G" feel wanted, for a change.

An interesting letter from house-bound BRS42979 **Peter Lincoln** of Aldershot, Hants, who thought that my comments on the limited value of reports from SWLs seemed to relegate them to second-class members in the hobby. This is not so, of course, but merely a practical approach to an unfortunate trend in amateur radio. Peter is only 36 but already retired through ill-health. He is not entirely without knowledge of the electronics world and I have perhaps encouraged him to have a go at the RAE, for which he can take the exam at home, as well as the code test if necessary. He may have problems with neighbours when it comes to transmitting, but I'm sure the RAIBC will be able to assist, come the great day.

Adrian Oates G4MOU of Chester may be redundant and not so young but he won't lie down! He remembered amateur radio from his early days so sat and passed the RAE last December and has now overcome his nervousness on the air with c.w. He has also turned to another past achievement, that of printing, and handles QSL cards among other lines. Good luck OM, you deserve it.

D. L. Broadley (Frome, Somerset) read of Bill Rendell's exploits in rejuvenating an old HRO, so dragged out one he had acquired in Aden in 1950, changed every resistor and fixed capacitor and was staggered by the results. He added a digital frequency readout module after cutting a suitable slot in the panel, no mean task! So he is all set to send me the odd log very soon, I hope. It's all your fault, Bill!

From Armagh, N. Ireland, **H. Irwin** GI8ROJ sent me a copy of a letter countersigned by GI4FFL, GI8RLE and GI5MPS, addressed to our esteemed Editor, in which they support my "totally justified comment" in the September issue of *PW* concerning repeaters on the v.h.f. and u.h.f. bands. Hope the Editor finds time and space to publish it in toto. At least I know now that I'm not alone in my views!

Cheers for now, and don't forget the 15th of the month deadline for any information intended for publication. Once again VERY HAPPY NEW YEAR to each and every one of you, and keep those letters and club reports coming.

Medium Wave Broadcast Band DX

by Charles Molloy G8BUS

Reports to: Charles Molloy G8BUS
132 Segars Lane, Southport PR8 3JG.

George Boorer (ZL3PN) who lives in Timaru New Zealand has sent me a copy of his article *Listening to the Eclipse of the Sun* which appeared in the September issue of *Break In* of the NZART. The article describes some radio experiments conducted by George during a total eclipse of the sun which occurred on February 5th 1981 and the part that is of interest to us is his monitoring of an aviation beacon. "My FRG-7 was left running on an aviation beacon just above 1600kHz. This beacon is located not too far from Timaru, is very strong at night, but not receivable in daytime during summer," writes George.

Then follows a sequence of events starting at 0830 when the beacon was just detectable, by 0920 it was S9, by 0930 the broadcast band (medium wave) was full of stations "a mini-night on the broadcast band in mid-summer during daylight." By 1000 all the broadcasters had gone. 1015 saw the return to normal sky conditions and by 1030 the beacon was not detectable. "February 5th 1981 had started again. The D layer was back in place."

A striking experiment that demonstrates clearly how much we depend on solar radiation for our radio communications. It will be 1999 before we have an eclipse of the sun in the UK but there is no need to wait that long. As sunset approaches every day the medium wave gradually fills with stations. Why is this and what is the D layer?

Medium Wave Propagation

During the daytime any signals to be heard on the medium wave will have reached the receiver by means of the ground wave. This ground wave follows the curvature of the earth and the distance it will travel depends on the nature of the terrain over which it passes. Signals will travel further (are attenuated less) over water than over land. I had an example of this last summer while holidaying in SW Scotland. My local radio station BBC Radio Merseyside came roaring in on a car radio near Stranraer but was inaudible at Carlisle. One path was over the sea, the other over land.

What about the sky wave? In daylight the lowest layer of the ionosphere that is of interest to us is the D layer. It is a region of rarified gas some 60km to 90km above the earth's surface which is kept in an electrified condition (ionised) by ultra violet light from the sun. The D layer absorbs signals in the medium wave band.

As darkness approaches the D layer disappears and signals from medium wave stations now penetrate higher into the ionosphere where they are bent back to arrive at the earth at distances up to 2000km from the transmitter. This is the maximum distance for a single hop for E layer reflection. When the signal comes back to earth it can be reflected back to the ionosphere for a second hop and so on.

In short, it is the D layer that prevents daytime DXing on the medium wave. At night or during an eclipse of the sun, the D layer disappears and then we are in business.

Breakthrough

"All over the lower part of the medium wave broadcast band I am plagued with Morse signals from Radio Scheveningen that are so strong that they even drown the stronger signals such as BBC2" writes P de Man (PEIDM). Our reader lives near Leyden in Holland only a short distance away from the coastal station at Scheveningen.

What seems to be happening is that very strong signals from the coastal transmitters, on frequencies lower than the medium wave, are forcing their way past the selective tuned circuits in the radio receiver. As the receiver is tuned away from the l.f. end of the band it becomes more difficult for this breakthrough, as it is called, to occur, hence the problem is confined to the low frequency part of the medium wave band.

What can be done about it? A directional antenna such as a medium wave loop could be used to null out the offending QRM. Tune the loop to the station you are listening to and rotate it until the QRM disappears. The snag with this cure is that broadcasts in the same direction as the QRM, or its reciprocal, will also be nulled out. In a similar way one can make use of the directional properties of the receiver's internal ferrite rod antenna (if one is fitted). Simply rotate the receiver till the QRM disappears.

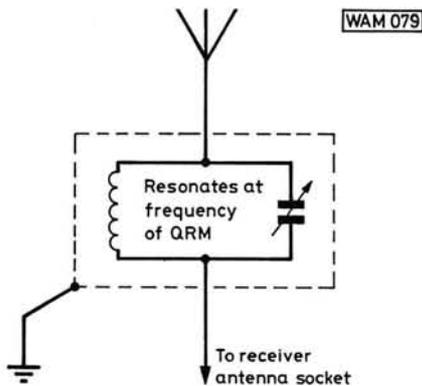


Fig. 1: Wavetrapp

Can you use a filter? asks our reader. Yes you can. Provided the receiver does not have an internal antenna of its own you can insert a wavetrapp in series with the lead from the external antenna. The

wavetrapp is just a parallel tuned circuit (Fig. 1) which is adjusted to resonate at the frequency of the QRM. The values of the inductor and variable capacitor will have to be found by trial and error but a long wave antenna tuning inductor and a 470pF variable would be a good starting point. The wavetrapp should be placed inside a metal box which is connected to earth. It is easy to adjust the trap. Turn its tuning knob until the QRM is reduced or disappears. Has anyone experience of suppressing breakthrough?



A pennant from Radio Bilbao which is on 990kHz

France Inter Time Signals

My reference to the one second pulses on the two megawatt French long wave station on 164kHz in the October issue prompted an interesting and informative reply from reader M. A. Kirk of Geneva. To quote from his letter, "The French time code is transmitted by phase modulation and was demonstrated at the TELECOM-75 exhibition in Geneva in 1975. Since March 1980 France Inter's 2MW 163.84kHz transmitter has been carrying the signal for 24 hours a day except for a few hours for maintenance on the nights of Tuesdays and Wednesdays—the information is phase modulated and a logic 1 is represented by two 25ms pulses at 100ms intervals and a logic 0 by a single 25ms pulse. The code is the same as that used by the DCF77 transmission at Mainflingen."

According to the *World Radio and TV Handbook 1981* page 533, Mainflingen (West Germany) gives "coded transmission of the number of minutes, hour, day, day of week, month and year". So, not only does our 2MW broadcast transmitter radiate second pulses, it also contains coded information giving the date and time as well. If you have not yet heard this transmission then tune to 164kHz (1829m), switch on the b.f.o. and you can't miss it.

Readers' Letters

Regular readers will remember the problem that some m.w. DXers have had with the DX160 communications receiver. It has its own ferrite rod antenna for use on the medium wave and this may be mounted internally or externally at the rear of the receiver. This of course prevents one using a medium wave loop with this receiver nor is it feasible to try the usual dodge of mounting the receiver at the centre of the loop and rotating the loop and receiver together, relying on induction between the two. The set is too bulky and heavy for that. Remembering that the ferrite rod antenna is also directional **Ted Jones** (Woking) bought a four wheel trolley. "With the DX160 on top and placed by the window I can manoeuvre the trolley for nulling out stations on medium wave." An ingenious and practical solution.

Using a Grundig Satellit 1400 with internal antenna **Simon Hamer** of New Radnor managed to pick up Oslo University Radio on 1314kHz after sign-off of NRK Stavanger. The time was 2303 on 7th October. Simon recognised the theme tune of the station as it had been played by *Sweden Calling DXers* the previous

day. According to *Sweden Calling DXers* both Oslo and Trondheim universities have been using it and Bergen University Radio has applied to use it during March 1982.



Dial Search

This is the name of a rather useful booklet produced by **George Wilcox** of Eastbourne. It is a listeners' check list of European radio stations and is in three parts. There is a list in frequency order of what can be heard, including the language used, on each channel of the Geneva Plan which covers the medium and long waves. There is a section on v.h.f. and there is a map based on Eastbourne which gives the bearing of a large number of European broadcasters. The map shows the direction to point your radio for the best reception of any of the locations marked on it. Instructions are given that enable the reader, with the aid of a protractor, to change the bearings so that they apply to any other location in Europe.

Dial Search will help listeners to find British and European broadcasters on the long wave, medium wave and v.h.f. It costs £0.80 plus £0.20 postage in the UK or six IRCs abroad and is obtainable from **George Wilcox**, 9 Thurrock Close, Lower Willington, Eastbourne BN20 9NF.

Short Wave Broadcast Bands

by Charles Molloy GBBUS

Reports: as for medium wave DX, but please keep separate.

The 120 metre tropical band seldom attracts much attention mainly I think because it is so difficult. Few DXers have ever heard anything on 120 metres and a word of warning for those who may be tempted to try comes from reader **M. Jansen** of Hoek in the Netherlands. Stations heard on 120 but not identified could be second harmonics from broadcasters on the medium wave. A second harmonic is a spurious emission from a transmitter on twice the normal frequency and a third harmonic is a spurious on three times the fundamental. Broadcasting stations do their best to suppress harmonics but it is difficult to prevent the radiation of a few watts of harmonics from a high power station. Our reader has found several harmonics on 120 metres while testing a new homebrew receiver which he has built especially for the tropical bands. If you suspect you are listening to a harmonic then search for the fundamental on the medium wave. Second harmonics on 120m would come from stations transmitting between 1150kHz and 1250kHz and third har-

monics from stations between 767kHz and 833kHz. Divide the frequency of the suspected harmonic by 2 or 3 to find the fundamental.

Control Points

Our reader in the Netherlands goes on to say that it is possible to DX on the tropical bands during daylight. "Here in Holland many serious DXers receive Indonesian stations on both the 60 and 90 metre bands during the afternoon in wintertime around 1400-1500 hrs GMT." Yes it is the same here in the UK and the reason is that it is only necessary to have darkness on part of the path from transmitter to receiver; the part between the control points. This of course raises the question, what are the control points?

Fig. 1, which is not to scale, shows how a signal travels from a distant transmitter, via the ionosphere, to our receiver. In the case of the frequencies used for the tropical bands it is necessary for the two control points to be in darkness otherwise the radio signal will not be returned to earth. The control points shown assume that the signal is reflected. In practice it is refracted and follows the curved dotted line below the control points, but the principle is the same.

Signals coming from the East will fade in before sunset at the receiver and will fade out after sunrise at the transmitter. Signals from the West will fade in before darkness reaches the transmitter and they will fade out after sunrise at the receiver. The effect is more pronounced in midwinter than at other times of the year. The

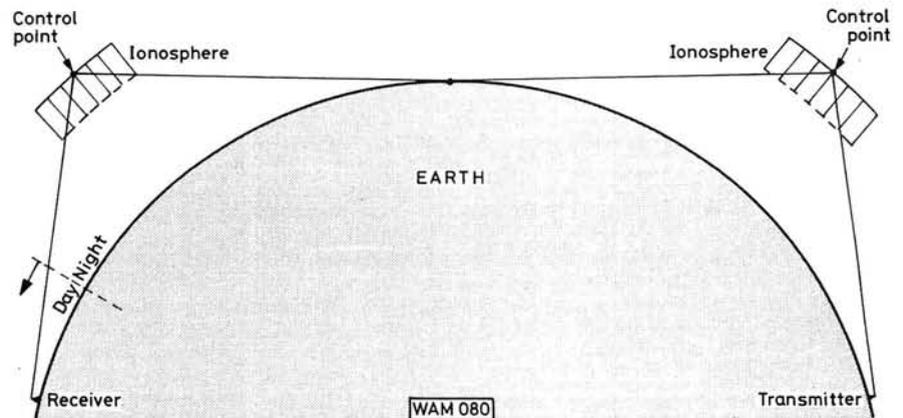


Fig. 1

sun is at a lower altitude, it ascends and descends at a shallower angle, twilight is longer and the period when DX can be heard in daylight is longer.

How far away are the control points? For the E layer (medium wave DX) the maximum distance for single hop reflection is 2000km and the control point obviously is at half this distance which is 1000km. For the F layer single hop reception cannot exceed 4000km and the corresponding control point is 2000km.

It is roughly true to say, when DXing on the medium wave or on the tropical bands, that there must be a path of darkness between TX and RX and it is only in mid-winter that any error becomes apparent. It is on the higher frequencies where the control points have to be in daylight that one really has to take account of them. The path from the UK to South America for example is open on the 19m and 25m bands for several hours after UK sunset because the control points, unlikely as this may seem, are still in daylight.

Pacific Service Frequencies and at 0215GMT on the Australian and NW Pacific Service at 0915GMT. "DX reports must be accompanied by four International Reply Coupons if QSL Verification cards are required" writes the station who go on to say that "interesting information about the areas in which we are received and the people who listen, is also appreciated." The station does not operate a general mailing list but requests for frequency and programme details are welcomed.



QSL Card from New Zealand



Colin Brooke's QSL from WVVH

Radio New Zealand

Broadcasts from Radio New Zealand seem to have a fascination for listeners in the UK. Indeed it is an achievement to pick up RNZ at all as the transmitters are low power, only 7.5kW, and the broadcasts are not beamed to Europe. Local time in NZ is 13 hours ahead of us (they are on summertime at the moment) and since the best time for reception in the UK is around breakfast time one gets the feeling of listening into the future, to events of the day to come.



Pennant from Radio New Zealand

RNZ have sent me a copy of their current schedule of short wave services which covers the period 25 October 1981 to 6 March 1982:

Pacific Service

1700-2030GMT	11.675MHz
2045-0530GMT	17.86MHz
0540-1115GMT	11.945MHz
1700-2005GMT	9.54MHz

Australian and NW Pacific Service

2015-0715GMT	15.485MHz
0730-1115GMT	11.96MHz

RNZ has a DX programme called *New Zealand Calling* which lasts for half an hour and is broadcast on the first and third Monday of each month on the

PW reader **Simon Hamer** of New Radnor has become a regular listener. "Thanks to your help, RNZ has been coming in regularly since I first logged it on Sunday 20 September". The receiver is a Grundig Satellit 1400 and 20 metre long wire and the best frequency is 15.485MHz at 0715. "I find RNZ's Book Review Programme aired at 0730 on Sundays very interesting" concludes Simon who thinks the station is a very welcome visitor to New Radnor. From Waltham Cross comes another report of RNZ on 15.485, this time at 0440 with a commentary of a rugby match. The receiver used by **T. W. G. Elsenham** is a vintage CR-100 which he has modified and he uses it with the outdoor TV antenna.

Readers' Letters

Another letter from New Zealand, this time from 16 year old **Martyn Barnes**, who is a student at college. He lives at Lower Hutt which is located NE of Wellington. His receiver is a new Sanyo stereo cassette/radio M7700K. "Its small size however does not seem to diminish its ability to receive stations on its two short wave bands. It tunes through the 120 metre band up to the 13m band". DX heard on the tropical bands includes Radio Colosal in Colombia on 4.945MHz, Solomon Islands on 5.02MHz and Radio Vanuatu at Port Vila (formerly New Hebrides). The frequency of the latter was not mentioned but Radio Vanuatu broadcasts on 3.945MHz and 7.26MHz. Welcome on board Martyn, hope to hear from you again.

Colin Brookes moved from Blackpool to RSA in 1979 and he says it took some months to readjust, as the transmitter directions and times are totally different. Colin gets fair reception from Brasil on 15.28MHz and 17.81MHz, R. Nacional Bogota in Colombia on 11.79MHz but so far HCJB has eluded him. WVVH Hawaii comes in well and he wonders if this might be the station heard by Alan Proctor (September issue).

Broadcasts Heard

A fine log of interesting DX comes from **Jim Edwards** who lives at Bryn near Wigan. With his R-1000, 60 metre-long wire and a.t.u. he pulled in Radio Clube Rondonopolis Brasil with a weak signal at 0100 on 2.48MHz in the 120m-band (quite a catch). ABC Melbourne on 6.15MHz at 2100, Ibadan Nigeria on 6.05MHz at 2205, Gansu China on 6.155 at 2200, Xinjiang China on 6.12 at 2310 and Action Radio Guyana on 5.95 at 0255 in English. **Rich Lewis**, Louth in Lincolnshire, uses the well known FRG-7 with a 19 metre-long wire and he reports hearing Seoul in the Republic of Korea on 6.48MHz at 2003. **Paul Clements** (Seaford) used an Eddystone 730/10 with a 6 metre-long wire outside the window to listen to Radio Internation Brasil on approx 17.86MHz at 2100.

Reader **A. N. Mead** is a newcomer to the short waves. He recently purchased a Realistic DX200 which he uses with a 25 metre-long wire. In the first few days he picked up Radio Nacional Brasil on 16.128MHz at 1945, Israel on 15.415 at 2100, HCJB the Voice of the Andes in Ecuador on 21.48 at 2130, Radio Nigeria on 15.12 at 0630 and All India Radio on 11.155 at 2045.

Practical Wireless, February 1982

G4JDT
HARVEY

EAST LONDON HAM STORE

G8NKV
DAVE

H. LEXTON LIMITED 191 FRANCIS ROAD LEYTON E.10
TEL 01-558 0854 TELEX 8953609 LEXTON G

RADIO & ELECTRONIC ENGINEERS

ENGINEERS ALWAYS AVAILABLE ON THE PREMISES

MAIN (UK) SERVICE CONTRACTOR TO HITACHI SALES (UK) LTD

EXCLUSIVE TO US IN THE UK. 1kW input 600W ssb 350FM 2MTR LINEAR!!

BUILT-IN POWER SUPPLY, ELECTRONIC WARM UP, VARIABLE INPUT ATTENUATOR. ADAPTS EXCITERS FROM 2W-25W. RADIAL BLOWER. LED'S FOR READY, TX, OVERLOAD, PTT & RF VOX with VARIABLE DELAY CHOICE OF EIMAC TUBES. 4x150A OR 4Cx250B OR 4Cx250R. ELECTRONIC PLATE CURRENT FUSE - NO THERMAL DAMAGE OF P.A. TUBE POSSIBLE. SIZE: H.88mm, W.318mm, D.375mm. FROM £300.00

D 70C	70cms.	10W in - 200W out	£489	All these linears have adjustable inputs and outputs and they are all fully protected. ALSO AVAILABLE:- 18db Gasfet masthead preamplifier which suits the output of these linears and which is also powered by them via the antenna co-ax.
D 200S	2mtr.	1kW p.e.p. ssb. (650 FM)	£599	
D 200	2mtr.	500W p.e.p. ssb. (400 FM)	£475	
D 200C	2mtr.	350W p.e.p. ssb. (150 FM)	£300	



ICOM PORTABLES
IC2E FM 2m £169.00
IC202 SSB £169.00
IC402 70cm £242.00
All accessories available - see below
AVAILABLE SOON
IC 4E 70CM

ICOM MULTIMODES



IC251 2m £495.00
IC451 70cm £366.00
IC290 2m £366.00

ICOM FM MOBILES



IC24G £165.00
IC25E £259.00

ICOM HF TRANSCEIVERS

IC730 200W £586.00
IC2KL 500W linear £839.00
IC2KLPS Power supply £211.00
A.T. 500 Auto A.T.U. Due in soon.

ICOM 720A G/C



GENERAL COVERAGE TX ALL BANDS
IC720A 200W £883.00
PS15 Power Supply £99.00
PS20 P/S with speaker £130.00
IC730 200W HF £586.00
MANY ACCESSORIES FOR ABOVE AVAILABLE

JAYBEAM ANTENNAS

8Y/2M 8 ELE YAGI £15.50
10Y/2M 10 ELE YAGI £33.00
PBM 10/2M 10 ELEMENT PARABEAM £39.00
8XY/2M 8 ELE X YAGI £31.00
X6/2M/X12/70CM DUAL BAND CROSSED £41.40
MANY OTHERS IN STOCK

ICOM ACCESSORIES

BP5 IIV Pack £30.50
BP4 Empty case for 6XAA £5.80
BP3 STA Noard Pk £15.50
BP2 6V Pack £22.00
BC30 Base charger £39.00
DC1 12V adaptor £8.40
WM9 Mic speaker £12.00
CP1 Mobile Charging load £3.20
LC1/2/3 cases £3.50
ICML1 10W Mobile booster for 2E £49.00
BC30 Base charger £39.00
MML1 10W Booster £49.00

TRIO/KENWOOD

TS830S HF Transceiver £690.00
TS130S HF Transceiver £520.00
TR8400 UHF Mobile £320.00
TR9500 UHF Multimode £445.00
TR7800 VHF mobile £285.00
TR7850 HP FM 2m POA
TR7730 2m FM TBA
TR9000 £370.00
TR2500 Portable Due In £245.00
PS30 20 1 amp PSU £85.00
Many Trio/Kenwood accessories available

YAESU/SOMMERKAMP

FT1	POA
FT902DM	POA
FT1012	POA
FT101ZDFM	POA
FT101ZDAM	POA
FT707 200W PEP	£569.00
FP707 PSU	£125.00
FL707 ATU	£85.00
FV707DM VFO FC + FT	£203.00
(FT707 + F1707 + FL707 SPECIAL PRICE POA)	
FT277ZD Soko all extras inc.	£753.00
FT7670X	£619.00
FT902DM Soko	£935.00
FC902 ATU	POA
FV901DM VFO	POA
SP901 Speaker	POA
Y0901P Scope	POA
FTV901 Transverter	POA
FT208 VHF	£209.00
FT708 UHF	£219.00
FT290 Multimode	£249.00
FRG7700+ Opt memory	POA

All accessories available

MICROWAVE MODULES

MMA 144V 2m Preamp £34.90
MML 144/25 RF AMP £59.00
MML 144/40 £77.00
MML 144/100S New with Preamp £129.95
MMT 432/144 2-70 Transverter £184.00
MMT 28/144 10m Transverter £99.00
MM2000 RTTY Receiver £169.00
MMI Morse Talker £115.00
MM 4000 RTTY
SEE IT WORKING AT OUR SHOP
£269.00 + keyboard.
Full range stocked.

STANDARD

C8800 2 mtr mobile £250.00
C7800 70cm mobile £270.00
C78 70cm portable £239.00
C58 2 mtr port. SSB/FM £219.00
CH68 Mounting tray £19.95
CLR Carry case £6.95
Battery charger £7.95
Set Nicads £11.00
CBP 58 25W linear CBP 78 10W linear
Due in soon, new standard mobile 2 mtr Multimode.

ROTATORS ETC

DIAWA
DR7600X £135.00
DR7600R £144.00
DR7500R £105.00
CN620 1-8 150MHz Pwr/swr £52.00
CN2002 2-5 kW PEP auto ATU £190.00
KENPRO
KR250 £44.85
KR400RC £90.00
CHANNEL MASTER 9502 £50.00
CN620 1-8 150MHz Pwr/swr £52.00
CN2002 2-5kW PEP auto ATU £190.00
CARRIAGE FREE MAINLAND

SWAN/CUBIC

102BX 235W + PS5 £800.00
103BX WARC 235W £1000.00
PS6 Power Supply £145.00
150MX Digital SP £561.00
15002 Linear £406.00
ST2A ATU TBA
ST3A ATU TBA

CUSHCRAFT AMATEUR ANTENNA

HF, A3 20/15/10 3 ele beam 8dB	ARX 2 Ringo Ranger 6dB vertical	£165.00	£28.00
ATV3 20, 15, 10 Trapped vertical	CS100 Speaker	£38.30	£13.00
ATV5 10, 15, 20, 40, 80 Trapped vertical	A144-4 ele Yagi	£83.69	£18.25
214B 14 ele boomer 15-2db	A144-7 ele Yagi	£55.77	£22.82
	A144-1 11 ele Yagi		£28.94
	ARX2B Ringo Mk11		£33.00
	ARB2K Conversion kit RINGO		

FULL RANGE OF A.S.P. MOBILE ANTENNAS IN STOCK

144+10T+Yagi OSCAR
144+20T+Yagi,
For vertical and horizontal Oscar specials

RECEIVERS ALL ON SPECIAL OFFER

R1000 Kenwood
FRG7700 Yaesu
FRG7700 Memory
Search II 2 metre
Soundmaster 150Kc - 470MHz Digital display
SSB/AM/FM etc.
ALL POA ARE ON SPECIAL
* 01-556 1415 *

CB
27/82

NOW STOCKING dnt 40 channel CB rigs + Handhelds + Base Station, we don't only sell these but we have an in car fitting service if needed and a full service back up. These sets are designed in Germany and built by a German Company.

ALL ACCESSORIES AVAILABLE - PLUGS SKTS CO-AX 2MTR COLINEAR £31.50, 70CM COLINEAR £31.50



PRICES INCLUDE VAT AT THE PRESENT RATE OF 15%
OPEN MON-FRIDAY 9:00-5:30. SATURDAY 10:00-3:00. INSTANT HP FACILITY AVAILABLE
EASY ACCESS M2-M11-M1 NORTH CIRCULAR ROAD-EASY PARKING

BARCLAYCARD

VISA

ILP TOROIDALS UNBEATABLE VALUE FOR MONEY!

New production capacity at Canterbury has increased our range, decreased our prices, improved our special customer design service. Choose from toroidal transformers in a range of 98 types.



Order using the FREEPOST coupon below.

Trade enquiries are welcome.

Supplied with rigid mounting kit with centre bolt, steel and neoprene washers: GUARANTEED 5 YEARS

TYPE	SERIES No	SECONDARY Volts	RMS Current	PRICE inc VAT	PRICE ex VAT
30 VA 70 x 30mm 0.45 Kg Regulation 18%	X1010	6+6	7.50	£5.28	£4.48
	X1011	9+9	7.77	+£1.10 P/P	+£0.87 P/P
	X1012	12+12	7.77		
	X1013	15+15	7.77		
	X1014	18+18	7.77		
	X1015	22+22	7.77		
	X1016	25+25	7.77		
50 VA 80 x 30mm 0.9 Kg Regulation 13%	X2010	6+6	4.16	£5.83	£4.93
	X2011	9+9	7.77	+£1.10 P/P	+£1.10 P/P
	X2012	12+12	7.77		
	X2013	15+15	7.77		
	X2014	18+18	7.77		
	X2015	22+22	7.77		
	X2016	25+25	7.77		
80 VA 90 x 30mm 1 Kg Regulation 12%	X3010	6+6	6.64	£6.51	£5.47
	X3011	9+9	4.44	+£1.43 P/P	+£1.43 P/P
	X3012	12+12	4.44		
	X3013	15+15	4.44		
	X3014	18+18	4.44		
	X3015	22+22	4.44		
	X3016	25+25	4.44		
120 VA 90 x 40mm 1.7 Kg Regulation 11%	X4010	6+6	10.00	£7.55	£6.38
	X4011	9+9	6.66	+£1.43 P/P	+£1.43 P/P
	X4012	12+12	6.66		
	X4013	15+15	6.66		
	X4014	18+18	6.66		
	X4015	22+22	6.66		
	X4016	25+25	6.66		
160 VA 110 x 40mm 1.9 Kg Regulation 8%	X5011	9+9	8.89	£9.92	£8.44
	X5012	12+12	8.89	+£1.43 P/P	+£1.43 P/P
	X5013	15+15	8.89		
	X5014	18+18	8.89		
	X5015	22+22	8.89		
	X5016	25+25	8.89		
	X5017	30+30	8.89		

TYPE	SERIES No	SECONDARY Volts	RMS Current	PRICE inc VAT	PRICE ex VAT
75 VA 110 x 45mm 2.7 Kg Regulation 7%	6X017	12+12	9.38	£11.83	£10.06
	6X013	15+15	7.50	+£1.73 P/P	+£1.73 P/P
	6X014	18+18	6.25		
	6X015	22+22	5.11		
	6X016	25+25	4.50		
	6X017	30+30	3.75		
	6X018	35+35	3.21		
300 VA 110 x 50mm 7.6 Kg Regulation 6%	7X013	15+15	10.00	£13.66	£11.66
	7X014	18+18	8.33	+£1.73 P/P	+£1.73 P/P
	7X015	22+22	6.87		
	7X016	25+25	6.00		
	7X017	30+30	5.00		
	7X018	35+35	4.28		
	7X019	40+40	3.75		
500 VA 140 x 60mm 4 Kg Regulation 4%	8X016	25+25	10.00	£18.17	£15.53
	8X017	30+30	8.33	+£2.05 P/P	+£2.05 P/P
	8X018	35+35	7.14		
	8X019	40+40	6.25		
	8X020	45+45	5.55		
	8X021	50+50	5.00		
	8X022	55+55	4.54		
675 VA 140 x 75mm 5 Kg Regulation 4%	9X017	30+30	10.41	£25.10	£21.54
	9X018	35+35	8.92	+£2.20 P/P	+£2.20 P/P
	9X019	40+40	7.81		
	9X020	45+45	6.94		
	9X021	50+50	6.25		
	9X022	55+55	5.68		
	9X023	60+60	5.11		

IMPORTANT: Regulation — All voltages quoted are FULL LOAD. Please add regulation figure to secondary voltage to obtain off load voltage.

The benefits of ILP toroidal transformers

ILP toroidal transformers are only half the weight and height of their laminated equivalents, and are available with 110V, 220V or 240V primaries coded as follows.

For 110V primary insert "0" in place of "X" in type number.

For 220V primary (Europe) insert "1" in place of "X" in type number.

For 240V primary (UK) insert "2" in place of "X" in type number.

How to order Freepost:

Use this coupon, or a separate sheet of paper, to order these products, or any products from other ILP Electronics advertisements. No stamp is needed if you address to Freepost. Cheques and postal orders must be crossed and payable to ILP Electronics Ltd. cash must be registered. C.O.D. — add £1 to total order value. Access and Barclaycard welcome. All UK orders sent post free within 7 days of receipt of order for single and small quantity orders. Also available at Electrovaive, Maplin, Marshalls, Technomatic and Watford Electronics.

ILP Electronics Ltd., Graham Bell House, Roper Close, Canterbury, Kent. CT2 7EP.

Please send me the following ILP modules PW/2/82

Total purchase price

I enclose Cheque Postal Orders Int. Money Order

Please debit my Access/Barclaycard No. _____

Name _____

Address _____

Signature _____

Post to: ILP Electronics Ltd. Freepost 2, Graham Bell House, Roper Close, Canterbury CT2 7EP, Kent, England.
Telephone (0227) 54778 Technical (0227) 64723 Telex 965780

ILP TRANSFORMERS (a division of ILP Electronics Ltd)

STAY AHEAD. STAY WITH US

MORSE TUTOR

The uniquely effective method of improving and maintaining Morse Code proficiency. Effectiveness proven by thousands of users world-wide.



- ★ Practise anywhere, anytime at your convenience.
- ★ Generates a random stream of perfect Morse in five character groups.
- ★ D70's unique "DELAY" control allows you to learn each character with its correct high speed sound. Start with a long delay between each character and as you improve reduce the delay. The speed within each character always remains as set on the independent "SPEED" control.
- ★ Features: long life battery operation, compact size, built-in loudspeaker plus personal earpiece.

Price £49.45

ACTIVE RECEIVING ANTENNAS

Datong active antennas are ideal for modern broadband communications receivers — especially where space is limited.



- ★ highly sensitive (comparable to full-size dipoles).
- ★ Broadband coverage (below 200 kHz to over 30 MHz).
- ★ needs no tuning, matching or other adjustments.
- ★ two versions AD270 for indoor mounting or AD370 (illustrated) for outdoor use.
- ★ very compact, only 3 metres overall length.
- ★ professional performance standards.

Prices: Model AD270 (indoor use only) £42.55
Model AD370 (for outdoor use) £56.35
Both prices include mains power unit.

VERY LOW FREQUENCY CONVERTER

If your communications receiver gives poor results below 500 kHz Model VLF is the answer.

- ★ Connects between antenna and receiver input.
- ★ Converts signals between DC and 500 kHz to the range 28 to 28.5 MHz with low noise and high sensitivity.
- ★ Crystal controlled for high stability.
- ★ Quality construction in diecast aluminium box (size 112 x 62 x 31mm), SO239 connectors, LED indicator, in/out switch.
- ★ Operates from internal 9 volt battery or external supply (5-15 volts DC).

Price: only £25.30

Our full catalogue plus further details of any product are available free on request.

All prices include VAT and postage and packing.

Goods normally despatched within 3 days subject to availability.



**DATONG
ELECTRONICS
LIMITED**

Spence Mills, Mill Lane,
Bramley, Leeds LS13 3HE
England.
Tel: (0532) 552461



Auto Marine



Your Official Yaesu Dealer in Greater Manchester for the North West.

Distributor of Jaybeam Antennas.

Main Cushcraft Dealer. Agent for TAL, Western, LAR, Microwave Modules, Western, Revco, Mosley, Drae, Shure.

MOSLEY

We carry a full range of station equipment including SWR and Power Meters, Connectors, Co-Axial Cables and Switches, Rotators, Power Supplies and a Full Stock of RSGB Books and Maps.



Our prices are competitive. Just send SAE for our catalogue and price list. Special package deal for new licensees setting up station.



Credit Card and Hire Purchase facilities with written quote on request. Telephone answering machine after hours. Open Tuesday to Saturday. Monday by appointment.



**AUTO MARINE
DEVELOPMENT COMPANY**
60 ORLANDO STREET,
BOLTON
Phone (0204) 21059



VHF Bands

by Ron Ham BRS15744

Reports to: Ron Ham BRS15744
Faraday, Greyfriars, Storrington,
Sussex RH20 4HE.

I have always believed that all aspects of radio communication are both essential and exciting and looking back over 35 years, at the systems I've seen, I ask myself, where else but in the world of amateur radio could one find a choice of 15 wave-bands to work on, some 6 different modes of operation and at least 4 types of atmospheric disturbance to influence the signals and add the sporting element to working DX.

Solar

Up in Ayrshire, **A. W. Rhead**, a member of the British Astronomical Association and frequent solar observer, has been experimenting with v.l.f. for some years and sending his results to a co-ordinator in the USA who runs a v.l.f. experimenters' news-letter. Like **Comdr Henry Hatfield** in Sevenoaks, Mr Rhead records the signal of MSF on 60kHz and compares his results with solar activity. From Bristol, **Ted Waring** reports that he counted 36 sunspots on October 20, 39 on the 31st and 50 on November 3. Henry also counted large numbers of sunspots and there is little doubt that these were responsible for the solar noise storm which began mildly on the 2nd, reached a high level on days 5, 6, 7, 8, 9 and 10 and gradually faded with a little noise and a few bursts each day until the 14th. In addition to this storm, which Henry and I recorded at 136 and 143MHz respectively, we also received several small bursts of solar noise, almost daily, between October 19 and 31.

The largest individual burst of solar radio noise that we have recorded for some time began at 1305 on the 15th and lasted for 10 minutes. It is surprising how events like these can just suddenly occur.

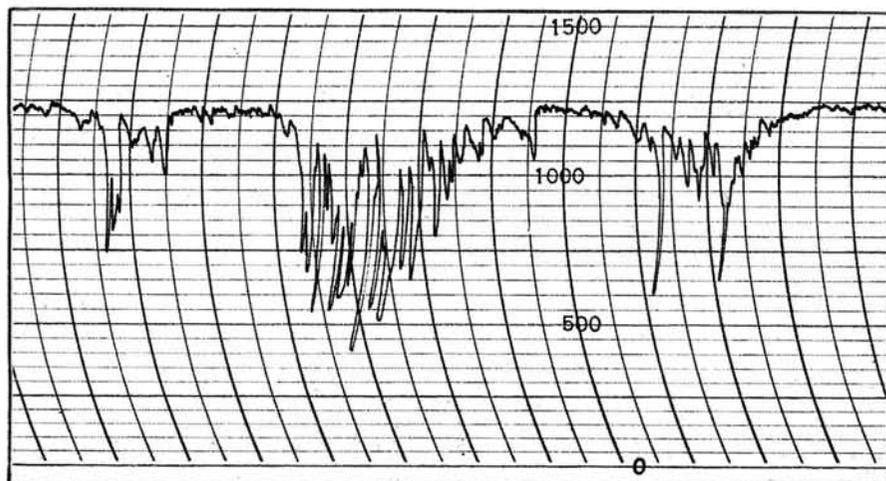


Fig. 1: Ten minute solar burst recorded at 140MHz by the author at 1305 on November 15

The 10m Band

I found the 10m band generally good between October 19 and November 15 with strong signals from Japan, in the mornings on 21 days and from Canada and the USA in the afternoons on 23 days. As far as my station is concerned signals from Australia were sparse throughout the period. At 0912 on October 30, I received a strong signal from 14-year-old SM2MTB while he was working a German station and around 0900 on November 5, I heard YU6GAS from the University of Titograd. At 1400 on October 19, **Harold Brodrigg**, St Leonards-on-Sea, Sussex, heard the young voice of 15-year-old Ari 4X6BP, working into the USA and when asked about DX conditions in Israel, Ari replied with a list of his QSOs with stations in South and Central America. "This young man must have a great future as a DXer" writes Harold who also noted that utility stations and harmonics from lower frequency broadcast stations were coming in as high as 45 to 50MHz on most days between October 20 and November 3. **Jon Kempster** BRS45205, Berkhamsted, using an FRG-7, an inverted "L" antenna and an a.t.u. has been listening to several American stations and trying to keep up with the c.w. Keep trying Jon, it will add a great deal to the pleasure you already get from your set.

"My new Tandy Patrolman 50 is great for listening on the 30-50MHz band for signals via the "F2" layer" writes **Wenlock Burton** from Victoria, Australia, who, between October 1 and 17, received signals from American and Hawaiian paging systems and Mexican and Russian mobiles between 34 and 40MHz. On several days, especially November 9 and 11, I heard strong echoes on the signals from European stations which of course may have been due to the prevailing solar activity.

10m Beacons

"What with new beacons and seasonal changes there is always something of interest" writes Ted Waring on November

10, who heard the beacons DF0AAB, VS6HK, WD4HES and ZS5VHF for the first time during his daily observations between October 15 and November 9. Between October 4 and 27, **Geoff Haynes** G3CWL, using a Ten-Tec RX10 receiver and a G3WPO 10m converter at his home in Leatherhead, Surrey, consistently heard signals from DL0IGI, 5B4CY, A9XC, VP9BA and YV5AYV. Then although this situation continued when he listened from his QTH in Falmouth, 240 miles west of Leatherhead, between October 29 and November 3, Geoff noticed a marked improvement in the reception of the European beacons DF0AAB, DK0TE, HG2BHA and LA5TEN, because, where he seldom heard these in Leatherhead he received them at good strength, almost daily in Falmouth. A good observation Geoff, you have proved the point that the reception of h.f. beacon signals does vary over relatively short distances. During the 28 day period between October 19 and November 15, I logged signals from the 10m beacon stations in Australia VK2WI on 5 days, Bahrain A9XC on 27 days, Bermuda VP9BA on 26 days, Caracas YV5AYV on 17 days, Cyprus 5B4CY on 26 days, Germany DL0IGI on 27 days, Hong Kong VS6HK on 14 days, Hungary HG2BHA on 9 days and, like Henry Hatfield, a new beacon UZABJ 28.272MHz on November 5, 6, 9, 12 and 13. The reports from both Henry and Ted Waring show similar results to mine but with the addition of the Canadian and South African beacons VE2TEN and ZS6PW which they both frequently heard. Another similar log came from **Arthur Swatton**, Westcliff-on-Sea, Essex, who also heard the German beacon DF0AAB.

The 6m Band

My phone rang at 1430 on November 10 and I was pleased to hear **Barry Ainsworth**, G4GPW, from nearby Lancing say "the 6m band is wide open, I have just worked VE1AST, cross-band between 10 and 6m s.s.b. and heard strong c.w. signals from WS 1, 2 and 3". Around 1400 on the 13th, I received strong s.s.b. signals from KA1MP and WB2CUS on 50MHz while they were working cross-band with 10m stations in England and Germany respectively.

RTTY

Although the majority of my RTTY listening is limited to short periods in the early morning and at midday I logged 200 stations between October 19 and November 15 spread over 28 countries, CN, DJ, EA, F, G, GW, HA, HB9, I, LA, LX, OE, ON, OK, OZ, PA, PY, SM, SV, T1, UA, VE, VK, W, YO, YU, YV and Y3. Among the interesting two-way QSOs I copied on 20m (14.090MHz) were I3FWY and W3AE at 0846 on October 19, DF9NW and EA3CVT at 1401 on the 23rd, I0DAO and OZ7XE at 1612 on the 24th, DJ1IJ and KD4SC, DK2DR and WA1ZEZ and DL7GE and WA1ZEZ around 0830 on the 26th,

DF3HE and DJ5QU at 0837 on the 28th, ON6ZM and OZ1CLE, PA3AXZ and EA6HH and UA3HR at 0934, 1400 and 1928 respectively on the 29th, DF2IC and LA5IV at 1400 on the 30th, F9KP and UA3HR and DF2IC and G3ASM at 0837 and 1334 on the 31st. Then on November 1 EA6HH and WB3HAZ at 0856, G3PFZ and ON4ZU around 0845 on the 2nd, EA3CVT and PA3BJD and 11KMF and 13XCE around 1425 on the 4th, F8DP and 11KMF at 0920 on the 5th, F6DXZ and IOEMV at 1355 on the 10th, GW4LWD in Cardiff and our Breadboard '81 exhibition station GB2PW at 1352 on the 12th and HB9BX and DL6BBJ around 1410 on the 13th. Among the 13 RTTY signals I received on 15m was SV1DU in Athens at 1814 on October 25 and the 6 copied on 10m were mainly in Canada, Italy and the USA. Between November 11 and November 14 the RTTY section of the *Practical Wireless* station at Breadboard '81, using the special event call-sign GB2PW, worked 31 stations in 15 countries. At 1442 on the 11th, I copied F6DXZ telling Geoff, our Editor operating at the time, that he would like to work him again under his own call G3GSR.

New readers with RTTY to TV converters should watch out for a rapid repetition of the letters RYRYRYRY or the figures 46464646 because these often precede a CQ or reply call-signs and offer a good chance to latch on to a QSO.

Microwaves

"The morning was spent making use of test equipment to test both transmitters and receivers in the microwave range" writes John Tye G4BYV, Dereham, who attended the Microwave Round Table meeting at Martlesham on October 18. The afternoon session was devoted to two lectures, one by Bill Thorpe on equipment for 29GHz and the other by Mike Walters on 23cm antennas.

On August 7, John, using his home-brew gear worked PA2HJS on 9cm (3.456GHz), a distance of 384km.

What about some microwave reports readers, with all those *PW* dishes sold there must be some new activity about.

Tropospheric

Apart from a few hours on October 23 and 24, the atmospheric pressure, measured on my Short and Mason barograph (have you seen the new Heathkit one) remained below 30.0in

(1015mb) from midnight on October 19 to midday on the 31st when it began to rise and by midnight it was 30.15 (1020mb). It continued to rise reaching 30.3 (1026mb) at midnight on November 2 where it remained until 0600 on the 4th when it began to rise still further, reaching 30.5 (1032mb) by midnight on the 5th and apart from a slight drop on the 11th and 12th, it stayed high until the 15th. Although the pressure was high, v.h.f. conditions were not as good as they should have been. On November 2, Roland Jeffery G6DSA, using a FT225RD and an 8-element Yagi, belonging to his father G8SIG, worked stations on 2m in Guernsey, France and Spain, EI8AAB on the 5th and EA1TA on the 6th.

Once the pressure went up I could hear signals, almost daily between October 31 and November 15, from the Bristol Channel repeater GB3BC R6 with only a roof-mounted dipole feeding my receiver. At 0500 on November 3, I heard an EA calling on R3 and judging by the strength, I am sure it was through the Brighton repeater GB3SR and on the 14th and 15th there were several repeater signals coming up on each channel.

Band II

Both Simon Hamer, Presteigne and Ian Kelly, Reading are keen Band II DXers and during the improved conditions between October 31 and November 5, Simon received signals from broadcast stations in Belgium, France, West Germany, BBC Radios London, Manchester, Solent, Sheffield and ILR Chiltern, Capital, LBC and Thames Valley between 88 and 100MHz. Ian also received signals from France and from a Dutch speaking station called "Radio Marina", BBC Radios Medway, Oxford and Solent and ILR Capital and LBC. For Band II DX, Simon uses a Pioneer SX450 and a Grundig Melody Boy and Ian uses a Realistic Modulette 929 music centre and both have wideband pre-amplifiers and a variety of home-brew antennas to meet their needs. "The best days were October 31 and November 2, when 7 and 12 continental stations were heard respectively. The majority of signals were absolutely excellent in mono" writes Ian and during the evening of November 1, Simon counted 8 editions of BBC Radio 3. Ian listened to the Disco Programme *Soiree Club* on most evenings and Simon also enjoyed a variety of music programmes from the abundance of French stations. Like Simon, I noticed a good bit of continental interference between 88-104MHz on November 1.

I am always pleased to hear from overseas readers, because it gives us a chance in the UK to learn more about the type of DX and propagation encountered in other parts of the world as well as an insight into the technical problems which have to be overcome.

Although the amount of sporadic-E is

News Items

"The U.K. Horizontal FM Group has been very active over the past few months and is growing in strength," writes their Secretary, Arthur Dorsett, G8YLH, Dogmersfield, Hants. The committee have decided that there will no longer be a net controller on activity nights. The calling frequency is now 144.675MHz and G8YLH will stand by on this channel to help any station in difficulty. Any station wishing for information about the group should call G8UAV on 144.650MHz.

The group also hold a Sunday morning net at 1030 on 145.350MHz to the Dutch novice stations (PD), also to EI on 145.575MHz at 1100. Arthur would like to give a word of thanks to one of my readers, Jon Kempster BRS45205 for the trouble he has taken to provide the group with some really excellent s.w.l. reports.

Congratulations to Tim Norris, Barnham, Sussex, who passed the RAE in May and now has the call-sign G6FKY. Tim became interested in radio in 1965, at the age of 12 and through the years listened on a variety of ex-Army and RAF receivers and now has a HC1400 and colinear for 2m and a Trio 1000 and long wire antenna for general use and a loft dipole for 10m. Tim worked an ON via the Kent repeater soon after he was licensed and an EA, he thinks via the Torquay repeater on R2 at 1439 on November 3.

Congratulations to the leading stations in the WAB VHF contest held on September 19 and the following information was kindly sent by the organiser, Del Roberts, Multi-operator section, 1st G4LAB/P and 2nd G6SW/P. Single operator, 1st G4HCQ, 2nd G8YBR and 3rd G8WJO and the mobile section was won by G4FQO/M.

Congratulations to George Grzebieniak on passing the RAE and now sporting the call-sign G6GGE which he received on November 5. George is now QRV on SSTV as well as 2m, 70 and 23cm and is looking forward to working some real DX on all bands.

Anyone interested in an expensive but rather special DX Diary for 1982, published in Finland, should write to Keith Hamer, HS Publications, 7 Epping Close, Mackworth Estate, Derby DE3 4HR, for details.

Congratulations to 15-year-old Roland Jeffery, in Cheshire, who passed the RAE in May and now has the call-sign G6DSA and along with G8WWY is helping to run a RAE course at Woodford Lodge Comprehensive School. Roland, a member of the Mid-Cheshire Amateur Radio Society, is push-bike mobile with a TR2300 and a home-brew $\frac{1}{4}$ wave ground plane antenna which works well from his bike.

small during the winter months I did see bursts of the RS-KH test card from Czechoslovakia at 1330 on October 20, test cards scribed Budapest from Hungary, CST 01 from Czechoslovakia and the plain one from Poland at 0850 on the 22nd, Grunten and Poland at 1315 on the 23rd. I also saw ORF FS1 and a film

TV

by Ron Ham BRS15744

Reports: as for VHF Bands,
but please keep separate.



THE CQ CENTRE

10 MERTON PARK PARADE 543 5150
(Adj Merton Hall Rd)
KINGSTON RD SW19

A sincere welcome to all Radio Amateurs and short wave listeners. We would like to thank all our customers who supported us at Leicester, and the organisers of the show.

CB became legal on the 2nd November, and we will be stocking a quality range of transceivers and accessories at our usual realistic prices – this we feel will be the gateway for many to the world of amateur radio.

On the amateur front we shall be continuing our wide range of new and second hand equipment including all the popular names – Yaesu – Trio – Icom – FDK – Microwave Modules – Jaybeam etc and we are still urgently seeking second hand equipment to purchase, working or not – try us last for a sensible price. Free 5/8 drill mount antenna (British made) with every new or second hand VHF rig.

Always in stock are the HB9CV beam and Slim Jim antennas, at £7.50 and £6.50 respectively, but due to changes in postal regulations it is not practical to mail order these singly. An extensive range of aerial equipment in stock – everything you should need, such as poles (1 + 2 inch), wall brackets (T + F), chimney lashing kits, clamps, guy rings and wire, tensioners and masts etc.

Please note that we are open till 8 pm Wednesdays and Fridays, 6 pm otherwise including Saturday, so call in or ring, for helpful advice.

Equipment may also be sold on a sale or return basis, for a nominal charge.

Latest lines include the Microwave Modules morse talker and the new 11/8 mobile aerial (7.5dB).

HF – VHF – UHF

CB – AMATEUR – PMR – MARINE

ACCESS – BARCLAYCARD – HP (6 MTHS INTEREST FREE)

73's from Bob, Ian and Paul at

LONDON'S BRIGHTEST & NEWEST EMPORIUM . .

PACKER COMMUNICATIONS

2 METRE ATU

IMPROVE YOUR VSWR, POWER OUT AND RECEIVED SIGNALS with an ATU 145 antenna tuning unit as featured in Practical Wireless of July 1981. **£19.95**



2 METRE WAVEMETER

REMEMBER You need a wavemeter to comply with the conditions of your licence. Our WM-2 keeps you legal. **£22.45**



TVI? We think that our UL-8 high pass filter is the best you can buy, but why not judge for yourself? For Ham and CB use. **£6.85**

For a full list of all our filters please send a S.A.E.

P-40. The no-compromise CB AND 2 METRE Mobile antenna. Hi grade steel whip 5/8 on 2m, 1.3m on CB (within HO spec). **£29.45** (plus £4.95 carriage)

Unit 4,

Station Industrial Estate,
Coniston, Cumbria.
Phone:- 09664 678.



WOOD & DOUGLAS



Your Winter Project could be:-

Project	Code	Kit	Assembled
70 cms Transmitter (0-5W)	70FM05T4	23.10	38.10
70 cms Receiver	70FM05R5	48.25	68.25
70 cms Synthesiser	70SY25B	60.25	84.95
70 cms Pre-Amplifier	70PA2	5.95	7.90
70 cms Converter	70RX2/2	20.10	27.10
70 cms 0-5W Synthesiser Package	70PAC2	128.00	163.00
70 cms 10W Power Amp/Pre-Amp	70PA/FM10	34.65	48.70
2M Transmitter (1-5W)	144FM2T2	22.25	36.40
2M Receiver	144FM2R2	45.76	64.35
2M Synthesiser	144SY25B	59.95	78.25
2M 1-5W Synthesised Package	144PAC	105.00	138.00
2M 10W Linear	144LIN10B	26.95	35.60
2M 10W Power Amplifier	144FM10B	25.95	33.35
2M Miniature Pre-Amplifier	144PA3	6.95	8.10
2M Low Noise Pre-Amplifier	144PA4	7.95	10.95
2M RF Switched Pre-Amplifier	144PA4/S	14.40	18.95
Toneburst	TB2	3.85	6.20
Piptone	PT2	3.95	6.90
Kay Tone	PTK1	5.95	8.20
Regulator	REG1	4.25	6.80
Microphone Pre-Amplifier	MPA1	2.95	5.40
CW Filter	CWF1	4.75	6.40
Reflectometer	SWR1	5.35	6.35

Full details will be forwarded on receipt of a large SAE. Non-technical enquiries only can be taken during the day on 07356 5324. Technical enquiries between 7-9 pm on either 07356 5324 or 0256 24611. Kits when stock will be return of post when humanly possible otherwise allow 28 days. Assembled items 20-40 days. Stock is held also at Amateur Radio Exchange in Ealing and J. Birkett in Lincoln.

(Prices include VAT at the current rate, please add 70p for postage.)

9 HILLCREST, TADLEY
BASINGSTOKE, HANTS RG26 6JB

NORTHERN COMMUNICATIONS

AMATEUR • COMMERCIAL • MARINE

AND NOW FOR SOMETHING REALLY NEW!




Send for details

-12V DC earth
144-146 MHz or
VHF Marine.

15 x 19 x 5 cms.
Mobile bracket
+ Int speaker inc.

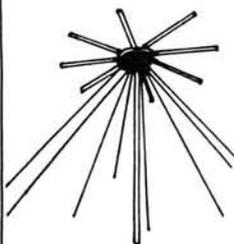A VHF monitor receiver with **VFO** plus **12** optional scanning channels for **£46.00** inc. VAT. Crystals **£2.25** each. Carriage free.



NORCONE 512 (66-512 MHz)
It's here! A no compromise, precision made full 16 element disccone antenna made in Britain. Standard S0239 connector, with cover. Supplied with 1" diameter, 30" mounting support mast and complete instructions.

An ideal partner for the SX200N "Bearcat" and other scanning receivers. It may also be used for transmission and in particular where antenna space is limited.

Full coverage of 70.144.432MHz Amateur bands plus Aircraft, Marine and Commercial bands.

£25.95 p.p. £1.75

MK-1. In line vertical mounting kit for 1" to 2" mast.

£2.45 p.p. £0.75

MK-2.

Chimney lashing kit, including hardware and lashing wire. **£2.95** p.p. £1.00

CK-1. Low loss coaxial cable kit, 10 metres, with connectors and fixing clips. **£3.75** p.p. £0.75

ZL-12 COMPACT YAGI

13db gain, compact 2 metre Yagi. 10'6" boom, lightweight rugged design. Hundreds of this award winning antenna already in use. Send for details.

£28.75 p.p. £1.75

ZL-8 SUPER COMPACT YAGI

9db gain, super compact 2 metre Yagi. 6'0" boom, lightweight rugged design. Ideal for limited spaces and portable operation. Send for details.

£17.95 p.p. £1.75

SX200N HOT NEWS!

Scanning Receiver NEW MODEL!

New model of this superb unit now with: Plug in modules - for easy service. Increased AF Output - for better reception. Improved Image Rejection - to cut out unwanted signals. Increased Selectivity - to cut out adjacent channels. Plus many more interesting features.

As reviewed in this issue. Frequency range 26MHz-514MHz!

£264.00 inc. VAT. Carriage £1.50

SPECIAL OFFER!

SX200N + Norcone 512. Complete inc. VAT. and delivery. **£285.00**

BEARCAT 220FBE (AM/FM)



New U.K. specifications with AM capability on all ranges. Built in PSU or 12V operation. Superior BEARCAT selectivity Superior BEARCAT performance.

ONLY £259 inc. VAT. Carriage £1.50

SPECIAL OFFER!

BEARCAT 220FB + Norcone 512. Complete inc VAT and delivery **£280**

STANDARD C78 UHF PORTABLE

Amazing new 70 cms Transceiver. Send for details. **£209.00**

Prices include VAT @ 15%

299-303, Claremount Road, Halifax HX3 6AW, West Yorkshire. G3UGF.
Tues-Sat. 9.45am-5.30pm.
Telephone (0422) 40792.
24 hour Ansafone Service.



COMMUNICATION CENTRE OF THE NORTH

The largest range of communications equipment available in the North. Full range of receivers, transceivers, antennas, power supplies, meters. Ali tubing - wall brackets etc.

We are the only official TRIO stockists in the North West. Full range of equipment on display. Guaranteed after sales service.

We can offer a full range of receiver from the SR9 2m **£46.00** to the Drake R7 at **£989** and the NRD515 at **£1,090**.

We are now stocking a range of top quality CB equipment and accessories.

MK II MULTITUNER. In 1977 we introduced our latest design in antenna tuners. This has now been exported to over 75 countries and recommended on Overseas World Broadcasts including HCJB. Will match practically any antenna to most receivers.

£35.00 inc. VAT & POST

Part Exchanges welcome. Second hand lists daily. Send S.A.E. for details of any equipment. HP terms. Access/Barclaycard facilities. Open 6 days a week. 24 Hour Mail Order Service.

Phone 0942-676790.

STEPHENS JAMES LTD.

47 WARRINGTON ROAD, LEIGH, LANCS. WN7 3EA.

SLIMLINE TELESCOPIC MAST

The SM30, a purpose designed telescopic tiltover mast with a slim unobtrusive silhouette, structured for single winch operation and either wall or post mounting. Extending from about 15ft up to 31ft it lowers down to about 3ft for easy access. It can be self supporting with many small or medium sized aerials or guyed for larger HF or VHF types.


NOTE THESE FEATURES

- ★ SLIM UNOBTUSIVE SILHOUETTE.
 - ★ TELESCOPIC AND TILTOWER FOR EASY AERIAL TWEAKING.
 - ★ WALL OR POST MOUNTING.
 - ★ SIMPLE ONE WINCH OPERATION.
 - ★ SAFETY UP LATCH TO RELIEVE CABLE.
 - ★ HOT DIP GALVANIZED FOR PROTECTION.
 - ★ ENGINEERED TO B.S.I. STANDARDS.
 - ★ OPTIONAL ROTOR HEAD UNITS (extra).
- TAKE THE STRAIN OUT OF AERIAL RIGGING AND GIVE YOUR SIGNALS A HEAD START WITH THE ALTRON SM30

Prices
SM30WM (Wall mounted) **£215.50**
SM30PM (Post mounted) **£225.00**
OPTIONAL RT1 1 1/2" Reducer tube **£11.50**
RH1 Rotor Head **£28.50**
MOBILE TRAILER AT1 for SM30 or others **P.O.A.**
Prices are incl. of VAT and U.K. Carr. C.W.O.

WE DESIGN. WE MAKE. WE SUPPLY DIRECT. You get unbeatable value. WE ARE THE ONLY MANUFACTURERS OF THIS MAST ... AND OTHER ALTRON PRODUCTS.

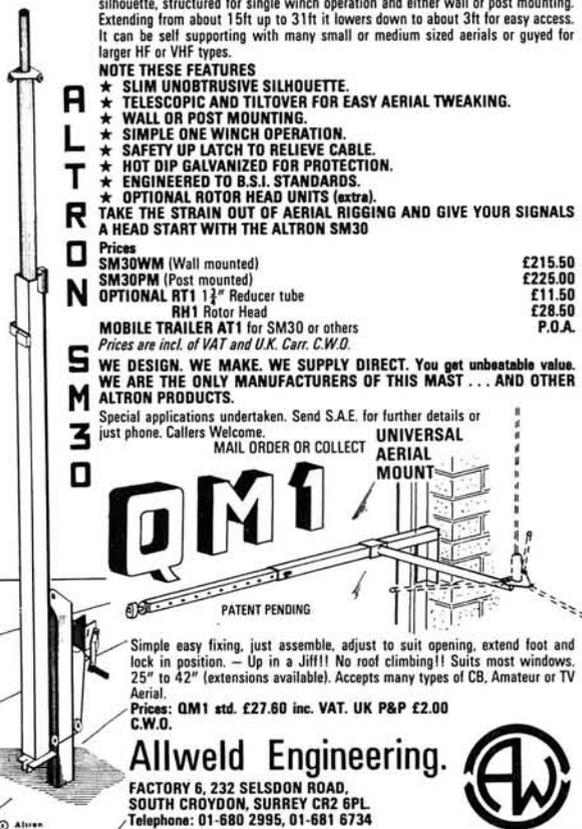Special applications undertaken. Send S.A.E. for further details or just phone. Callers Welcome. MAIL ORDER OR COLLECT



Simple easy fixing, just assemble, adjust to suit opening, extend foot and lock in position. - Up in a Jiff! No roof climbing!! Suits most windows. 25" to 42" (extensions available). Accepts many types of CB, Amateur or TV Aerial.
Prices: QM1 std. £27.60 inc. VAT. UK P&P £2.00 C.W.O.

Allweld Engineering.

FACTORY 6, 232 SELSDON ROAD, SOUTH CROYDON, SURREY CR2 6PL
Telephone: 01-680 2995, 01-681 6734



about gliders at 0855 on the 25th. Austria again at 0810 on the 26th and RSKH at 0845 on the 27th. Sometimes bursts of sporadic-E occur while an "F2" disturbance is in progress but it is easy to distinguish between the two. The majority of these signals were on Ch. R1 49.75MHz because such disturbances rarely go above 50MHz at this time of year.

"Not quite sporadic-E time yet, it should start between November 14 and 20, so I am testing my home-made Band I filters" writes Australian reader **Wenlock Burton** on November 2, who adds "There has been quite a bit of trop lately with the good weather". I look forward to hearing more Wenlock.

Tropospheric

When tropospheric conditions are good, Wenlock Burton often receives pictures, Fig. 2, at his home in Melbourne, from one of Australia's privately owned commercial TV stations, BTV6 (Ballarat and Western Victoria TV Ltd) in Ballarat. According to the 1980 edition of the *World Radio TV Handbook* there are some 29 such stations and their call-signs are coded. The first two letters 'BT' are an abbreviation of the name of the licence, the 3rd letter 'V' indicates the state 'Victoria' and the number '6' signifies the channel. In Australia Ch. 6 is 175.25MHz.

Between October 12 and 16, Wenlock also received pictures from stations BCV8 (Victorian Broadcast Network Ltd), MTN9 (Murrumbidgee TV Ltd) GTV9 (General TV Corporation Pty. Ltd) and HSV7 (Herald Sun TV Pty Ltd).

At 2120 on October 31, the atmospheric pressure having risen sharply, was steady and during a brief opening I received strong colour pictures from BRT Belgium on Ch. E10. The station was showing an episode of *Tales of the Unexpected*, in English with Belgian sub-titles. This was followed at 2138 with their weather report, 2139 came their NIEUWS (news) and sport mainly VOETBALL (football) followed at 2155 by a list of the following day's programmes and a clock showing 2259, one hour ahead of GMT. Finally a test card scribed BRT VTV.1 appeared accompanied by the time pips for 2300 and the station closed down. I also saw a monochrome film on Ch. E8 but this died out around 2230 GMT. This opening began to ebb and flow with changing weather, but as the pressure remained high, at 30.2in (1022mb), I received a weak signal of a football match at 2204 on November 1 and a weak picture at 1340 on the 2nd from Belgium on Ch. E10. At 0900 on the 3rd, I received strong pictures from the IBA transmitter at Lichfield on Ch. B8, strong colour test cards from BRT VTV.1 and RTBF-1 at 1400 and the *Muppets* with Shirley Bassey, in English with Belgian sub-titles on Ch. E10. Around the same time, **Tim Norris**, Barnham, using a converted Bush TV161, watched the French station TF1 from Caen on Ch. 21. At 2230 on Oc-

tober 31, **George Garden**, Bracknell, received a test card from Belgium on Ch. 28 and put this down to the two huge high pressure systems, which he saw on the weather report, over France and Germany. George has now invested in a JVC CX-610GB colour set and is looking forward to more good DX. In Chippenham, **Brian Renforth** received excellent pictures from France, TDF FR3 on Ch. 42, on October 30, TDF test cards on Chs. 39, 42 and 46 from Rennes on November 5 and several French stations, including Teletext transmissions from FR3 Ch. 42, on the 6th. I again received pictures from Belgium on Ch. E10 for short periods around 1955 on the 6th and 1344 on the 9th.

Amateur Television

"I can now report that the ATV repeater, VK3RTV, has been given its complete control system," writes Wenlock Burton, from Australia, who tells me that the functions are touch-tone commanded and a standard touch-tone keyboard is required. The user v.d.u. (TT1) is accessed by sending 300 baud Kansas City AFSK on the audio uplink frequency, "same as sending RTTY" says Wenlock.

Between 2000 and 2300 on November 7, **Roy Humphreys** G6AIW, from the Worthing Amateur TV group, set up his portable TV gear, home-brew 10W transmitter on 435MHz with 2m talk back and an 18-element parabeam, on the South Downs and successfully transmitted pictures to stations in Oxford and Derby and fellow club member, **Robin Stephens** G8EXU, has been experimenting with inter-carrier sound which he transmitted with his video for a couple of hours to Roy on November 9. The Worthing group gave much pleasure to the residents of the St Giles Home for the Disabled in Lancing when the Worthing Amateur Radio Club put on a special station at the home between 1100 and 1630 on November 7.

» QSL «	
FROM A.L.V. STATION	
ON6PM-T	
U.S.A. LIEGE	QTH 1800Z
We are happy to confirm: (OUR-YOUR)	
QSO - REPORT	
Date:	REPORTS: VIDEO: R
At:	SOUND:
Remarks:	
THANK YOU and VT 73 from:	
OPERATOR of the Station:	
PRESENTATOR:	
CAMERA: 1st	2nd
VISITORS:	

"Although I have a full licence (h.f.-v.h.f. etc) I am QRV on the 2m band only, but also on ATV 70cm as the announcer of the station ON6PM/T. We transmit every Saturday between 1500

and 1700 GMT, sound 439.75MHz and vision 434.25MHz and listen on 145.575MHz for reports" writes **Jose Robat** ON7TP, Bressoux, Belgium. Jose sent one of their ATV QSL cards, Fig. 1, which would sure look good on the shack wall and on the reverse side are 6 pictures, graded 0-5, indicating the quality of the report.

F2 TV

"At 1145 GMT today I discovered a smeary Soviet test card on Ch. R1, its image continually disintegrating and then reforming. At times there were multiple images" writes **David Appleyard** from Uppsala, Sweden on November 6. Join the club David, that's "F2" propagation and very well described. Around 1200 on the 7th, David noted a similar jumble of bars and patterns on Ch. E2 48.25MHz and writes "The disturbance persisted and at 1255 Arabic letters were discernible across the bottom half of the screen". David also saw a smeary, un-readable clock just before 1300 and then for about 10 minutes, large Arabic letters on a white centre piece with dark borders top and bottom were shown at intervals of about 2 minutes. David, using his 8in National receiver with its own rod antenna, suggests that this signal was coming from Dubai.

From Chippenham, Brian Renforth has been watching the "F2" signals on Chs. E2 and R1 and noted the typical Russian test card on October 16, Dubai with Arabic caption at 1400 on the 17th and a test card with squares, possibly Ghana, on the 27th. "A good start to my 16th birthday" said Brian as he identified tanks on display with CCCP on them at 0900 and Dubai test card at 1240 on the 28th.

"Today there has been a lot of TSS "F2" on Ch. R1" writes **Keith Hamer**, from Derby on October 31, who also sends 3 pictures, Figs. 3, 4, 5, of typical "F2" signals received by **Garry Smith** and himself between October 15 and 18. These pictures come from as far afield as China and as Keith says "look at the characters" (in Fig. 5).

I have seen that broken Russian test card around 0900 on several days, in fact, I logged multi-image, smeary and mostly un-identifiable signals on Chs. E2 and R1 on October 19 and then, almost every morning from October 26 to November 15. At 0930 on October 27, I saw what I thought was someone teaching in front of a giant chequered board and a multi-image announcer at 0835 on the 28th. Around 1350 on November 2, I saw what looked like an announcer answering the phone and at 1200 on the 6th David Appleyard saw the image of a woman dancing reproduced several times on the screen. "It is interesting that multiple TV reception on Ch. R1 re-appeared on November 1" writes **Harold Brodribb** who nearly resolved a picture on the 1st but did catch a glimpse of a test card on other days. "I couldn't identify it" said Simon Hamer



Fig. 2: Ballarat test card received by Wenlock Burton in Australia

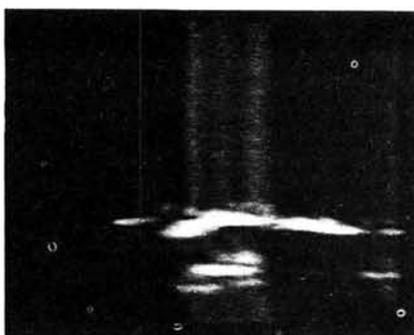


Fig. 3: Arabic TV caption received by Keith Hamer via F2

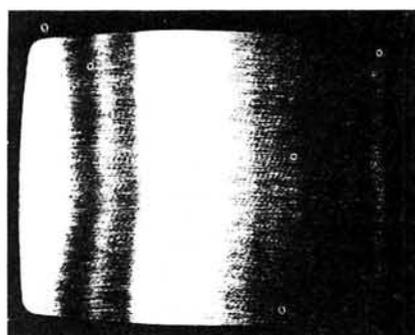


Fig. 4: Typical F2 patterns received by Garry Smith



Fig. 5: F2 signal possibly China received by Keith Hamer



Fig. 6: Gibraltar Band III TV received by Fred Pilkington in Spain



Fig. 7: Gibraltar caption received by Fred Pilkington

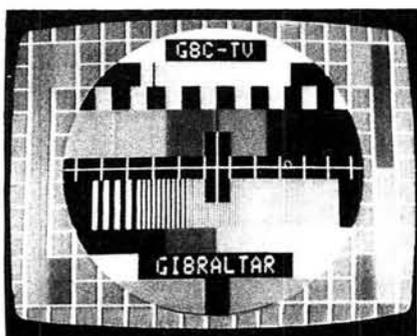


Fig. 8: Gibraltar test card received by Fred Pilkington in Spain

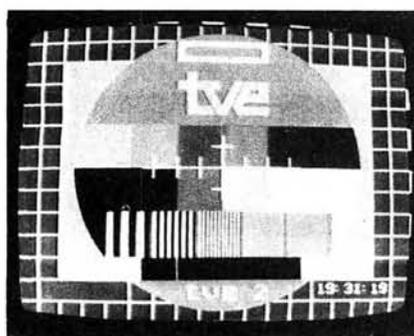


Fig. 9: Spanish TV test card received by Fred Pilkington whilst on holiday



Fig. 10: Spanish TV test card received by Fred Pilkington

who tried to grapple with the mixture on R1. Keep trying everyone, each bit of information helps.

Gibraltar

"I have recently been on vacation in the Malaga area on the Costa del Sol" writes Fred Pilkington G3IAG, Newport market and while there he used a home brew 220MHz beam and did some experimenting with reception of television from Gibraltar, 55 miles away. The excellent results, Figs. 6, 7, 8 came from the translator on top of the Rock, Ch. E11 217.25MHz. While in Spain, Fred kindly took 2 pictures of test cards from the Mijas u.h.f. transmitter, Figs 9, 10 and one from the regional station, Andalucia, Fig. 11.

Equipment

One of our readers since 1952, W. H. Collier, Newport, Wales, asks about suitable receivers for DXTV so I suggest you take a look around your shops for small screen portable sets made by JVC, National Panasonic, Plustron, Sanyo and Sony because these usually tune through v.h.f. Bands I and III and u.h.f. Make sure the dials on the set you choose are marked in Chs. 2-4, 5-12 and 21-69. I am always pleased to hear about any make of set which covers these ranges.

The DXTV-RX Group are organising a telephone warning network for openings caused by Aurora, tropospheric or sporadic-E. Several members have joined the network and any reader wishing to



Fig. 11: Spanish TV test card received by Fred Pilkington

take part should contact the secretary, George Grzebieniak, 35 Binns Road, Chiswick, London W4.



Lee Electronics Ltd

TELECOM ANTENNAS - YAESU MUSEN - ICOM - F.D.K. - STANDARD Etc.

TELECOMM TC9000 Mk II CB RIG



£99.95

inc. VAT
&
Postage


FEATURING

- ★ Priority Channel
- ★ Delta Tune
- ★ Noise Blanker
- ★ Squelch
- ★ Volume
- ★ Accessory Switch for optional sec-call etc.
- ★ P.A. Output
- ★ Hi-Low Power


The New TC9000 is here with added Priority Channel & Acc Switch & rear socket for sec-cal etc.

This is a top of the line set exceeding the M/T1320 spec. Come in and TRY IT and see the rest of our range of products.

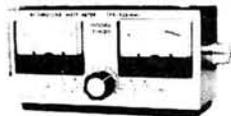TELECOM ANTENNAS - YAESU MUSEN - ICOM - F.D.K. - STANDARD Etc



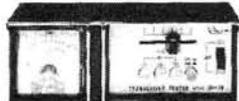T-435: VHF/UHF swr and power meter with 2/20/120 watt through line power measurement **£34.95** inc. VAT. P&P 75p.



UH74 SWR and power meter switchable HF, 2m and 432MHz with remote head at **£16.39** inc. VAT. P&P 75p.



SWR25: This ever-popular twin SWR and Power meter covers 3.5-150MHz at **£12.00** inc. VAT. P&P 50p.

HELICAL ANTENNAS

- 2m with BNC plug **£4.50**
- 2m with PL259 plug **£4.50**
- 2m for Trio etc. **£4.25**
- 2m with AR240 screw **£4.25**
P&P 25p

COAX SWITCHES

★ NEW SA-450 ★

High quality coax switch housed in a diecast box with SO239s
Frequency 3.5-500MHz
Loss 0.02dB
Weight 450gms
Max power 2.5kW
Impedance 50ohm



£9.77

CT-1 Coax toggle, 3 SO239s **£9.77** inc. VAT. P&P 25p.



CT-2 Coax toggle, 2 SO239s, 1 PL259 **£6.85** inc. VAT. P&P 25p.

TS-120 Coax slide switch, 3 SO239s **£6.75** inc. VAT. P&P 25p.



DL-30 Dummy load 25W DC-150MHz **£6.35** inc. VAT. P&P 25p.
T-100 100W Dummy load DC-500MHz **£20.12** inc. VAT. P&P 25p.
T-200 150W Dummy load DC-500MHz **£35.60** inc. VAT. P&P 25p.

NEW PRICE
T200
£33.60

2 METRE FM/SSB Portable/Mobile

C58



£239.50

- ★ L.C.D. display for low battery consumption
- ★ 100Hz/1KHz/25/12.5KHz/5KHz
- ★ Five programmable memories
- ★ Rit control for accurate ssb resolution
- ★ Effective noise blanker
- ★ Repeater and reverse repeater off set
- ★ A full one watt R.F. power
- ★ Automatic or manual tone burst
- ★ Full scanning facilities
- ★ Large range of optional accessories
- ★ Up/Down scan control on the microphone
- ★ Now available 25 watt amp **£79.95**

All MICROWAVE MODULES and DATONG products available

**400 EDGWARE ROAD
LONDON W2
01-723 5521 Tlx: 298765**

Normal Postal
Delivery 5 Days



INSTANT H.P. (with Bank Card)
& P/EX. WELCOME

Send 25p for
full details
of our range.

Sinclair ZX81 Personal Comp the heart of a system that grows with you.

1980 saw a genuine breakthrough – the Sinclair ZX80, world's first complete personal computer for under £100. Not surprisingly, over 50,000 were sold.

In March 1981, the Sinclair lead increased dramatically. For just £69.95 the Sinclair ZX81 offers even more advanced facilities at an even lower price. Initially, even we were surprised by the demand – over 50,000 in the first 3 months!

Today, the Sinclair ZX81 is the heart of a computer system. You can add 16-times more memory with the ZX RAM pack. The ZX Printer offers an unbeatable combination of performance and price. And the ZX Software library is growing every day.

Lower price: higher capability

With the ZX81, it's still very simple to teach yourself computing, but the ZX81 packs even greater working capability than the ZX80.

It uses the same micro-processor, but incorporates a new, more powerful 8K BASIC ROM – the 'trained intelligence' of the computer. This chip works in decimals, handles logs and trig, allows you to plot graphs, and builds up animated displays.

And the ZX81 incorporates other operation refinements – the facility to load and save named programs on cassette, for example, and to drive the new ZX Printer.



New BASIC manual

Every ZX81 comes with a comprehensive, specially-written manual – a complete course in BASIC programming, from first principles to complex programs.

Kit: £49.⁹⁵

Higher specification, lower price – how's it done?

Quite simply, by design. The ZX80 reduced the chips in a working computer from 40 or so, to 21. The ZX81 reduces the 21 to 4!

The secret lies in a totally new master chip. Designed by Sinclair and custom-built in Britain, this unique chip replaces 18 chips from the ZX80!

New, improved specification

- Z80A micro-processor – new faster version of the famous Z80 chip, widely recognised as the best ever made.
- Unique 'one-touch' key word entry: the ZX81 eliminates a great deal of tiresome typing. Key words (RUN, LIST, PRINT, etc.) have their own single-key entry.
- Unique syntax-check and report codes identify programming errors immediately.
- Full range of mathematical and scientific functions accurate to eight decimal places.
- Graph-drawing and animated-display facilities.
- Multi-dimensional string and numerical arrays.
- Up to 26 FOR/NEXT loops.
- Randomise function – useful for games as well as serious applications.
- Cassette LOAD and SAVE with named programs.
- 1K-byte RAM expandable to 16K bytes with Sinclair RAM pack.
- Able to drive the new Sinclair printer.
- Advanced 4-chip design: micro-processor, ROM, RAM, plus master chip – unique, custom-built chip replacing 18 ZX80 chips.



Built: £69.⁹⁵

Kit or built – it's up to you!

You'll be surprised how easy the ZX81 kit is to build: just four chips to assemble (plus, of course the other discrete components) – a few hours' work with a fine-tipped soldering iron. And you may already have a suitable mains adaptor – 600 mA at 9 V DC nominal unregulated (supplied with built version).

Kit and built versions come complete with all leads to connect to your TV (colour or black and white) and cassette recorder.



uter-



Available now- the ZX Printer for only £49.⁹⁵

Designed exclusively for use with the ZX81 (and ZX80 with 8K BASIC ROM), the printer offers full alpha-numerics and highly sophisticated graphics.

A special feature is COPY, which prints out exactly what is on the whole TV screen without the need for further instructions.

At last you can have a hard copy of your program listings – particularly

useful when writing or editing programs.

And of course you can print out your results for permanent records or sending to a friend.

Printing speed is 50 characters per second, with 32 characters per line and 9 lines per vertical inch.

The ZX Printer connects to the rear of your computer – using a stackable connector so you can plug in a RAM pack as well. A roll of paper (65 ft long x 4 in wide) is supplied, along with full instructions.

16K-byte RAM pack for massive add-on memory.

Designed as a complete module to fit your Sinclair ZX80 or ZX81, the RAM pack simply plugs into the existing expansion port at the rear of the computer to multiply your data/program storage by 16!

Use it for long and complex programs or as a personal database. Yet it costs as little as half the price of competitive additional memory.

With the RAM pack, you can also run some of the more sophisticated ZX Software – the Business & Household management systems for example.

How to order your ZX81

BY PHONE – Access, Barclaycard or Trustcard holders can call 01-200 0200 for personal attention 24 hours a day, every day.

BY FREEPOST – use the no-stamp-needed coupon below. You can pay

by cheque, postal order, Access, Barclaycard or Trustcard.

EITHER WAY – please allow up to 28 days for delivery. And there's a 14-day money-back option. We want you to be satisfied beyond doubt – and we have no doubt that you will be.

To: Sinclair Research Ltd, FREEPOST, Camberley, Surrey, GU15 3BR.

Qty	Item	Code	Item price £	Total £
	Sinclair ZX81 Personal Computer kit(s). Price includes ZX81 BASIC manual, excludes mains adaptor.	12	49.95	
	Ready-assembled Sinclair ZX81 Personal Computer(s). Price includes ZX81 BASIC manual and mains adaptor.	11	69.95	
	Mains Adaptor(s) (600 mA at 9 V DC nominal unregulated).	10	8.95	
	16K-BYTE RAM pack.	18	49.95	
	Sinclair ZX Printer.	27	49.95	
	8K BASIC ROM to fit ZX80.	17	19.95	
	Post and Packing.			2.95

Please tick if you require a VAT receipt

TOTAL £

*I enclose a cheque/postal order payable to Sinclair Research Ltd, for £

*Please charge to my Access/Barclaycard/Trustcard account no.

*Please delete/complete as applicable.

Please print.

Name: Mr/Mrs/Miss

Address:

FREEPOST – no stamp needed. Offer applies to UK only.

PRW02

sinclair ZX81

6 Kings Parade, Cambridge, Cambs., CB2 1SN.
Tel: (0276) 66104 & 21282.

S.E.M.
BOX 6, CASTLETOWN, ISLE OF MAN.
TEL: MAROWN (0624) 851277

S.E.M. ACTIVE MULTIFILTER

Will improve ANY receiver on ANY mode. Gives "passband tuning" and "Variable selectivity". Switched Hi-pass, Lo-pass, peak or notch. Selectivity 2.5KHz-20Hz tunable from 2.5KHz to 250 Hz. PLUS another notch which can be used in any switch position and covers 100Hz to 10KHz. TRY ONE ON 14 DAYS APPROVAL. **£57.00** ex stock.

S.E.M. EZITUNE

"In my fifty years on the air, this is the most useful gadget I've ever seen". Connects in aerial lead, produces S 9+ (1-170MHz) noise in receiver. Adjust A.T.U. for minimum noise. You have now put an exact 50 ohms load onto your transceiver. Fully protected, you can transmit through it, to save your P.A. and stop QRM. **£25*** ex stock.

S.E.M. TRANZMATCH

The most VERSATILE Ant Matching system. Will match from 15-5000 Ohms BALANCED or UNBALANCED at up to 1kW. Link coupled balun means no connection to the equipment which can cure TVI both ways. SO239 and 4mm connections for co-ax or wire feed. 160-10 metres TRAN Z MATCH **£65.00**. 80-10 metres **£58.00**. EZITUNE built in for **£19.50** extra. (See above for details or Ezitune). All Ex-stock.

THE SENTINEL AUTO MK II 2 or 4 metre PRE-AMPLIFIER

These include NEW PROTECTION circuit to give MAXIMUM LEGAL through power rating. Completely new third generation DUAL GATE MOSFET pre-amp giving 1dB N.F. and 20dB gain with GAIN CONTROL and OFF switch (straight through when OFF). The High Q tuned circuits for high selectivity.

Size: 1 1/2" x 2 1/2" x 4" **£25.00*** ex stock. Without RF Switch **£15.**

SENTINEL STANDARD Mk II 2 or 4 metre PRE-AMPLIFIER

Same as the AUTO less R.F. switch 12V 5mA. **£15.00*** ex stock.

PA3

ONE cubic inch miniature 2 metre pre-amplifier. Same circuit as above. **£7.95** ex stock. 70cms versions **£4.00** extra. Marine Band ex stock. Other frequencies to order.

SENTINEL 2 METRE LINEAR POWER AMPLIFIER/PRE-AMPLIFIER

These units use the latest techniques and transistors for highest reliability and performance. Infinite SWR PROTECTED devices. ULTRA LINEAR, all modes. R.F. switched. Same POWER GAIN at lower drive powers. Supply 13.8V nominal. SO239s. Three models:

- SENTINEL 35** Twelve times power gain. 3W IN 36W OUT. 4 amps. Max. drive 5W. 6" x 2 1/2" front panel, 4 1/2" deep. **£57.50** ex stock.
 - SENTINEL 50** Five times power gain. 10W IN 50W OUT. Max drive 16W. Same size as the Sentinel 35. **£69.50** ex stock.
 - SENTINEL 100** Ten times power gain. 10W IN 100W OUT. Max drive 16W. Size: 6 1/2" x 4", front panel, 3 1/2" deep. 12 amps. **£126.50** ex stock.
- All available less pre-amp for **£8.00** less.

SENTINEL H.F. WIDEBAND PRE-AMPLIFIER 2-40MHz 15dB gain. Ideal for 15 and 10 metres and OSCAR OR AN ACTIVE AERIAL 9-12V. Size: 2 1/4" x 1 1/4" x 3". Two versions. **1. STANDARD** Performance as above. **£10.00*** ex stock. **2. AUTO** Same performance as above with a change over relay r.f. operated by your transceiver for direct connection in your aerial co-ax. **£16.93*** ex stock.

FREQUENCY CONVERTERS

SENTINEL DUAL GATE MOSFET 2 METRE CONVERTERS

N.F. 2dB Gain 30dB. I.F.s 2 metres: 2-4MHz, 4-6MHz, 28-30MHz. 4 metres: 28-28.7MHz, 9-12V. 15mA. **£24.73** ex stock.

SENTINEL X 2 METRE CONVERTER Same as above plus mains power supply. **£28.80** ex stock. 70cms to 28-30MHz **£28.80** ex stock. **SENTINEL L.F. CONVERTER** 10KHz-2MHz IN 28-30MHz OUT. 9-12V. 5mA. **£20.80** ex stock. **SENTINEL TOP BAND CONVERTER** 1.8-2.3MHz IN 14-4.5MHz OUT. 9-12V 5mA **£20.80** ex stock. **S.E.M. IAMBIC KEYS** The ultimate auto key using the CURTIS custom LSICMOS chip. Tune and sidetone switching. **£30.00** ex stock. TWIN PADDLE TOUCH KEY **£12.50**.

*Means Belling Lee sockets, add £1.90 for SO239s or BNC sockets. Ring or write for more information. Place orders or request information on our Ansaphone at cheap times.

12 MONTHS COMPLETE GUARANTEE

Prices include delivery. C.W.O. or credit card number for same day service.

NEW CASIO FP-10 MINI PRINTER

(RRP £49.95)



AN INCREDIBLE

£44.95

Compatible with the FX-501P, FX-502P, FX-601P, FX-602P and FX-702P.

This 5x7 dot matrix electric discharge mini printer stores up to 30 characters and prints up to 20 per line, at the fast speed of 2 lines per second. Four AA size batteries will print from 6000-9600 lines approximately, depending on type. The rechargeable pack, NP-4M (£6.90) will print approximately 13,000 lines. The AC adaptor, AD-4150 (£5.00) will also recharge the NP-4M in situ.

Dims: 43.5H x 157.5W x 82.5D (1 1/4" x 6 1/4" x 3 1/4") Weight 372g (13.1oz). **CASIO FX-602P.** 512 program steps. With FREE MICROL PPP (£9.95) **£74.95**

CASIO FX-702P. Pocket calculator/computer. Input can be varied from 1680 program steps with 26 memories, to 80 steps with 226 memories, all non-volatile. Up to 10 programs can be stored. Scientific and statistical functions. (RRP £134.95) with FREE MICROL PPP, **£119.95.**

MICROL PROCOS 702P Professional Computing Solutions on tape **£24.95.**

DISCOUNTS ON SOFTWARE WHEN YOU BUY HARDWARE FROM US

Catalogue of Casio calculators, keyboards and watches and further information on the 602P or 702P and PROCOS on request (14p stamp).

Price includes VAT, P&P. Delivery normally by return. Send cheques, P.O. or phone your Access or Barclaycard number to:-

TEMPUS

Dept PW, 38 Burleigh Street, Cambridge, CB1 1DG. Tel: 0223 312866

MODULAR ELECTRONICS

95 HIGH STREET SELSEY, Nr CHICHESTER, SUSSEX. TEL: SELSEY (024361) 2916

DISTRIBUTOR FOR SOLID STATE MICROWAVE (THOMPSON CSF) RF PRODUCTS

GB0CS

Type	P/out	Gain	Volts	Freq.	Price
2N3886	1w	10dB	28	175MHz	£1.01
2N4427	1w	10dB	12	175MHz	£1.17
2N3553	2.5w	9dB	28	175MHz	£1.28
2N5913	2w	7dB	12	470MHz	£1.77
SO1127	4w	12dB	12	175MHz	£2.68
2N6080	4w	12dB	12	175MHz	£5.19
SO1143	10w	10dB	12	175MHz	£7.80
2N6081	15w	8.5dB	12	175MHz	£8.22
2N6082	25w	5.7dB	12	175MHz	£8.49
2N6084	40w	4.5dB	12	175MHz	£13.90
SO1428	45w	6.5dB	12	175MHz	£14.60
SO1416	70w	6.7dB	12	175MHz	£26.58
SO1477	100w	6.0dB+	12	175MHz	£31.50
2N5550	10w	5.2dB	13.6	175MHz	£8.98
2N5591	25w	4.4dB	13.6	175MHz	£8.73
2N5944	2w	9dB	12	470MHz	£7.47
2N5945	4w	8dB	12	470MHz	£8.49
SO1135	5w	7.5dB	12	470MHz	£6.72
SO1136	10w	6dB	12	470MHz	£8.56
2N5946	10w	6dB	12	470MHz	£12.02
SO1088	25w	6.8dB	12	470MHz	£20.24
SO1089	40w	4.3dB	12	470MHz	£27.83
SO1434	50w	6.0dB	12	470MHz	£28.10

Ex Equip 2N5070 2-30MHz 25wPEP **£2.88**
 2N5645 Mot. 12v 470MHz 4W out. **£4.50**
 2N5914 RCA 12v 470MHz 2w 7dB **£4.60**
 2188LY Mul. Studless BLY38 2w 470MHz **£3.45**
 61387 RCA Studless Sim C1-12 CTC **£3.45**
 Free data sheets with all purchases which include typical circuits etc.

LOW NOISE SMALL SIGNAL SEMICONDUCTORS.
 BFR90 Mul. T Pack. 2.5dB N/F 1GHz **£2.82**
 BFR91 Mul. T Pack. 2.5dB N/F 1.2GHz **£3.45**
 BFR34a T Pack. 4dB N/F GHz **£2.25**
 BFT66 Low Interm. T072 **£2.59**
 SO306 "O" MOS MOSFET **£2.60**
 40673 RCA MOSFET **£0.92**
 BFR90 UHF MOSFET Equip 3SK88 **£1.30**

UNELCO Cased RF Mica Caps. Following PFS
 10/20/30/40/50/60/70/80pF **£1.61**; 100/150/180/250pF **£1.73**; 1000pF **£1.84**.
 PTFE Sheet 0.25mm 300mm Square **£2.30**
 PVE 951-170-12v Aerial Relays. SPST. Good to 1296MHz.
 Silver Plated. RG43 Type **£10.70**

Barclaycard or Access on orders above £10.
POST and PACKING ADD 50p TO ALL ORDERS.
 Orders sent 1st Class Post where weight permits.
SAME DAY DISPATCH ON ALL IN STOCK ITEMS.
 Minimum invoiced order to approved customers **£15.00.**
 ALL PRICES NOW INCLUDE VAT AT 15%.

ITT 10.7MHz XTL Filters 25KHz **£8.05**
 HP 5082-2800 Hot Car. Diodes. **£1.12**
 HP 5082-2835 Hot Car. Diodes. **£0.98**
 HP 5082-3080 Pin Switch Diodes **£0.98**
 Motorola MC12013L + 10 Prescaler IC with full data/instructions **£11.50**
 BB103 Varicap Diodes **£0.50**
 TIP33 **£0.58**; 2N918 **£0.50**; BF180 **£0.50**; BF115 **£0.50**;
 2N5179 **£0.82**; BFY90 **£1.15**; ST2110 BSX20/2N2369a **£0.30**.

TRIMMERS
 Tetter PTFE 1-10pF 44p. DAU PTFE Film 1 to 9pF or 1.5-18pF 34p. Surplus 2.5-25pF 22p.

SPRAGUE (Grade 1) Mica Trimmers (500v) for R.F. Amps. 2.5-7pF 81p. 4-20pF 88p. 7-40pF 86p. 16-100pF 98p. 25-150pF 109p. 40-200pF 115p.

HEATSINKS single sided ideal for RF amps. Redpoint 6M1 2.6 deg/w **£2.20**

FINISHED MADE UP AND TESTED EQUIPMENT
PA2 Preamplifier for 2 meters, using the latest UHF stripline MOSFET the BFR90. 1 1/2" square for fitting in the rig. 50Q in/out imp. Only **£8.05** with instructions.
PAU2 432MHz Preamp. stripline using the BFR34a 14dB gain N/F < 2dB **£8.63**.

LINEAR AMPLIFIER MODULES. without Ch/Over. Size 55x92mm with thermal interface. 50Q.
 PM2-10 0.4w in 10w out. 13.8v **£18.40**
 PM2-15 1.5w in 15w out. 13.8v **£19.55**
 PM2-25 4w in 25w out. 13.8v **£20.99**
 CPM LINEAR AMPS with full RF Changeover size 82x102mm preamp can be fitted in RX.
 SPEC. AS FOR PM Series. Specify CPM type and add **£7.48** to PM series prices.

PRESCALER BOARD ÷ 10 Size 55x93mm with input amplifier (2x BFR34a) sens. 40mV 432mc uses MDT MC120121 I/C. 500MHz typ 600MHz. Only **£23.00**. 5v neg E supply

It's easy to complain about advertisements.

The Advertising Standards Authority.
If an advertisement is wrong, we're here to put it right.
 A.S.A. Ltd., Brook House, Torrington Place, London WC1E 7HN.

AMATEUR ELECTRONICS UK

Your number one source for
YAESU MUSEN



FT-101ZD Mk III

YAESU's FT-101ZD with FM is the most popular HF rig on the market thanks to its very comprehensive specification and competitive price. Incorporates notch filter, audio peak filter, variable IF bandwidth plus many other features.

FT-480R High technology all-mode 2metre mobile



The most advanced 2 metre mobile available today- USB, LSB, FM, CW full scanning with priority channel, 4 memory channels, dual synthesized VFO system.

FT-707 All solid-state HF mobile transceiver

As factory appointed distributors we offer you- widest choice, largest stocks, quickest deal and fast sure service right through-



The definitive HF mobile rig, digital, variable IF bandwidth, 100 watts PEP SSB, AM, CW (pictured here with 12 channel memory VFO). Latest bands.

FRG-7 General coverage receiver



The set with the world-wide reputation. YAESU's famous FRG-7 out-performs many a more expensive set. Rugged and reliable, it features high sensitivity and Wadley loop stability - a delight to use for the established amateur and new SWL alike.

FRG-7700 High performance communications receiver



YAESU's top of range receiver. All mode capability. USB, LSB, CW, AM and FM 12 memory channels with back up. Digital quartz clock feature with timer. Pictured here with matching FRT-7700 Antenna tuner and FRV-7700 VHF converter.



FREE SECURICOR DELIVERY



Amateur Electronics UK
508-516 Alum Rock Road · Birmingham 8
Tel: 021-327 1497 or 021-327 6313
Telex: 337045
OPEN: 9.30 - 5.30 Tues - Sat CLOSED: All day Mon



The **NEW** and **LEGAL**
PLANET 2000
FM CB Transceiver

CALL OR WRITE FOR DETAILS

36p in stamps brings you our latest price list / literature and credit voucher for £3.60

MASTER ELECTRONICS NOW!

The PRACTICAL way!

This new style course will enable anyone to have a real understanding of electronics by a modern, practical and visual method. No previous knowledge is required, no maths, and an absolute minimum of theory.

You learn the practical way in easy steps mastering all the essentials of your hobby or to start or further a career in electronics or as a self-employed servicing engineer.

All the training can be carried out in the comfort of your own home and at your own pace. A tutor is available to whom you can write personally at any time, for advice or help during your work. A Certificate is given at the end of every course.

You will do the following:

- Build a modern oscilloscope
- Recognise and handle current electronic components
- Read, draw and understand circuit diagrams
- Carry out 40 experiments on basic electronic circuits used in modern equipment
- Build and use digital electronic circuits and current solid state 'chips'
- Learn how to test and service every type of electronic device used in industry and commerce today. Servicing of radio, T.V., Hi-Fi and microprocessor/computer equipment.



New Job? New Career? New Hobby? Get into Electronics Now!

FREE!
COLOUR BROCHURE



POST NOW TO:

Please send your brochure without any obligation to

I am interested in:

PW/2/821

NAME _____

ADDRESS _____

- COURSE IN ELECTRONICS as described above
- RADIO AMATEUR LICENCE
- MICROPROCESSORS
- LOGIC COURSE

OTHER SUBJECTS _____

BLOCK CAPS PLEASE

British National Radio & Electronics School Reading, Berks. RG1 7BR

RST

VALVE MAIL ORDER CO.
Climax House
159 Fallsbrook Road, London SW16 6ED
SPECIAL EXPRESS MAIL ORDER SERVICE

AZ31 1-10	EM87 1-60	PY81 0-84	6AN5 4-74	607 2-20
CL33 2-00	EN91 3-50	PY82 0-80	6AN8A 3-45	607A 1-45
DY86/7 0-84	EY86 0-84	PY83 0-70	6AQ5 0-96	65C7 1-50
DY802 0-84	EY88 1-75	PY88 0-88	6AR5 1-98	65J7 1-60
EB8CC 3-36	EY500A 0-84	PY500A 1-80	6AS6 4-98	65K7 1-30
E180F 8-40	EZ80 0-84	PY800 0-84	6AS7GA 6-75	65L7GT 2-68
E180F 14-47	EZ81 0-84	PY801 0-84	6AT6 0-85	65N7GT 1-60
EB8C80 0-20	GY501 2-75	QQV02-6 14-06	6AU5GT 4-32	65S7 1-80
EB91 0-82	GZ32 1-25	QQV03-10 5-80	6AU6 1-08	65G7M 2-50
EBF80 0-50	GZ33 4-00	QQV03-20A 17-50	6AW8A 3-39	6U8 0-80
EBF89 0-85	GZ34 2-50	QQV06-40A 15-00	6B7 1-50	6V6GT 1-60
EC91 7-56	GZ37 4-00	£55.10	6B8 1-75	6X4 1-20
ECC33 3-50	KT61 3-50	QV03-12 4-46	6BA6 1-00	6X5GT 0-85
ECC35 3-50	KT66 10-00	R18 4-25	6BA7 5-12	7C5 2-95
ECC81 0-88	KT77 8-00	R19 1-20	6B6 1-08	7C6 2-25
ECC82 0-72	KT88 12-00	SP41 6-00	6B6 1-52	7S7 1-25
ECC83 0-88	N78 9-00	SP81 2-00	6B6 1-65	12AT6 1-20
ECC85 1-20	OA2 2-00	U19 13-75	6B6 3-72	12A7 0-88
ECC88 1-90	OB2 2-55	U19 13-75	6B7 4-00	12A7 0-88
ECC91 8-93	OC3 1-92	U25 1-16	6B8 1-75	12AB 2-19
ECF80 1-08	OD3 1-92	U26 1-44	6B8 1-75	12BE6 2-43
ECM35 2-00	PC86 1-40	U37 9-00	6B8 1-75	12B7 2-70
ECH42 1-15	PC88 1-40	UABC80 1-25	6B7 1-52	12BY7A 2-70
ECH81 1-20	PC92 1-28	UBF89 1-20	6B2 2-37	12HG7 4-17
ECL90 1-00	PC97 1-20	UCH42 1-20	6C4 0-98	30FL1/2 1-12
ECL82 1-00	PC900 1-20	UCH81 2-32	6C6 1-75	30P4 1-20
ECL83 1-50	PCF80 1-00	UCL82 1-04	6C86A 2-49	30P19 1-20
ECL86 1-20	PCF82 1-00	UCL83 1-44	6CD6GA 5-07	30PL13 1-80
EF37A 3-50	PCF86 1-60	UF89 1-44	6CL6 £3.72	30PL14 1-80
EF39 2-75	PCF801 1-60	UL41 2-50	6CH6 10-40	75C1 2-35
EF41 2-00	PCF802 1-90	UL84 1-20	6CV4 7-58	85A2 2-39
EF42 2-00	PCF805 1-60	UY41 1-25	6D5 1-75	90C1 2-44
EF50 1-50	PCF808 1-60	UY85 1-04	6D05 5-94	150B2 3-02
EF54 5-00	PCH200 1-60	VR105/30 1-92	6EA8 2-94	150C2 1-92
EF55 2-50	PCL82 1-60	VR150/30 1-92	6EH5 1-85	150C4 2-39
EF80 0-80	PCL83 2-00	Z759 16-80	6F6 1-75	57Z8 27-50
EF86 1-52	PCL84 1-00	Z803U 7-90	6G6 1-75	866A 15-27
EF91 1-80	PCL85 1-08	2D21 3-50	6H6 1-50	807 3-75
EF92 5-81	PCL86 1-08	3B28 14-35	6HS6 3-77	811A 18-33
EF183 0-80	PCL805 1-08	4CX250B 45-00	6J5 2-50	812A 18-33
EF184 0-84	PD500 3-80	SR4GY 3-50	6J6 3-50	813 79-26
EH90 1-40	PFL200 1-80	5U4G 1-52	6J7 2-50	866A 15-27
EL32 1-50	PL36 1-20	5V4G 1-52	6JB6A 4-56	872A 21-47
EL33 3-50	PL81 1-20	5Y3GT 0-85	6K4N 1-25	931A 15-78
EL34 2-20	PL82 1-20	5Z3 1-50	6K6GT 1-30	2050 6-96
EL36 1-60	PL83 2-22	5Z4GT 1-50	6K7 1-50	5763 3-75
EL81 3-50	PL84 1-40	UYD12 1-56	6K9 1-75	9814A 3-72
EL84 1-00	PL504 1-40	6A87 1-50	6K6 1-75	5842 12-09
EL86 2-50	PL508 1-80	6AH6 4-71	6LD6 6-36	6080 6-85
EL91 7-14	PL509 3-20	6AK5 3-60	6LGG 2-50	6146A 10-64
EL95 1-32	PL519 3-20	6AL5 0-82	6L7 2-00	6146B 8-12
EL360 8-50	PL802 2-96	6AM6 1-80	6LQ6 6-72	6853B 12-73
EM81 1-00	PY33 1-10			6973 3-87

Open daily to callers: Mon-Fri 9 a.m. - 5 p.m.
Valves, Tubes and Transistors - Closed Saturday
Terms C.W.O. only - Tel. 01-677 2424-7.
Quotations for any types not listed S.A.E.

Prices excluding VAT add 15%
Post and packing 35p per order

Telex 946708

Prices correct when going to press

ROBOT '800' SUPER TERMINAL

Quite simply the best & most complete Terminal ever built for Amateur Radio. Full Send/Receive RTTY ASCII & CW. Character & Test Pattern generation SSTV.



Please send 19p stamp for a complete information package.

AERO & GENERAL SUPPLIES

Building 33, East Midlands Airport,
Castle Donington, Derby DE7 2SA.
Tel: (0332) 812446

LOOK! LOOK! LOOK!

Due to popular demand, we have decided to continue manufacturing Frequency Display Units, for the FRG7, the SSR 1 Century 21 & SRX 30 Receivers.

Price £44.77p inc. of VAT postage & packing.

NEW PRODUCT. CB CB CB

The PERSUADER SPEECH PROCESSOR at £38.18p inc. VAT postage and packing.

S.A.E. For further information to:

BROOKES ELECTRONICS LTD.,
2A, Leicester Street, Norwich NR2 23AS.

Tel: 0603 24573


C.W.O. VISA AND ACCESS

Step-by-step fully illustrated assembly and fitting instructions are included together with circuit descriptions. Highest quality components are used throughout.

Sparkrite


BRANDEADING ELECTRONICS

NOW AVAILABLE IN KIT FORM

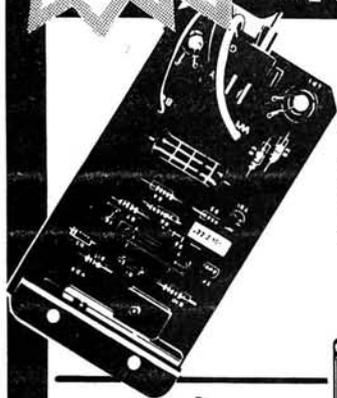



SX1000 Electronic Ignition

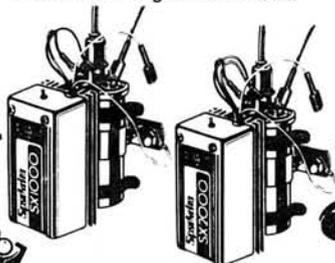- Inductive Discharge
- Extended coil energy storage circuit
- Contact breaker driven
- Three position changeover switch
- Over 65 components to assemble
- Patented clip-to-coil fitting
- Fits all 12v neg. earth vehicles




SX2000 Electronic Ignition

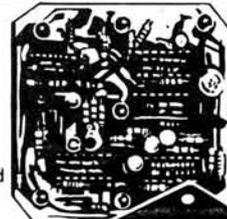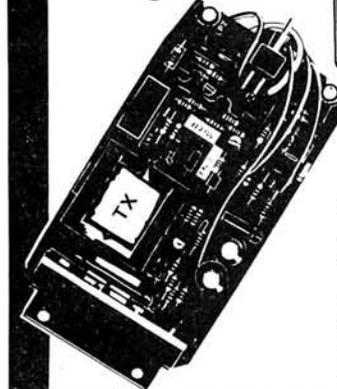- The brandleading system on the market today
- Unique Reactive Discharge
- Combined Inductive and Capacitive Discharge
- Contact breaker driven
- Three position changeover switch
- Over 130 components to assemble
- Patented clip-to-coil fitting
- Fits all 12v neg. earth vehicles



MAGIDICE Electronic Dice

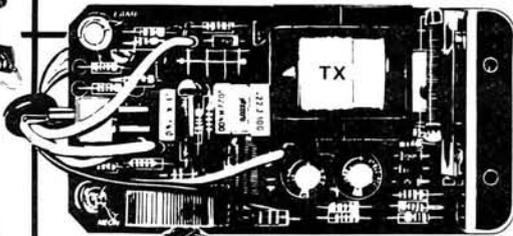
- Not an auto item but great fun for the family
- Total random selection
- Triggered by waving of hand over dice
- Bleeps and flashes during a 4 second tumble sequence
- Throw displayed for 10 seconds
- Auto display of last throw 1 second in 5
- Muting and Off switch on base
- Hours of continuous use from PP7 battery
- Over 100 components to assemble
- Supplied in superb presentation gift box



TX2002 Electronic Ignition



- The ultimate system ● Switchable contactless. ● Three position switch with Auxiliary back-up inductive circuit.
- Reactive Discharge. Combined capacitive and inductive. ● Extended coil energy storage circuit. ● Magnetic contactless distributor triggerhead. ● Distributor triggerhead adaptors included.
- Can also be triggered by existing contact breakers.
- Die cast waterproof case with clip-to-coil fitting ● Fits majority of 4 and 6 cylinder 12v neg. earth vehicles.
- Over 150 components to assemble

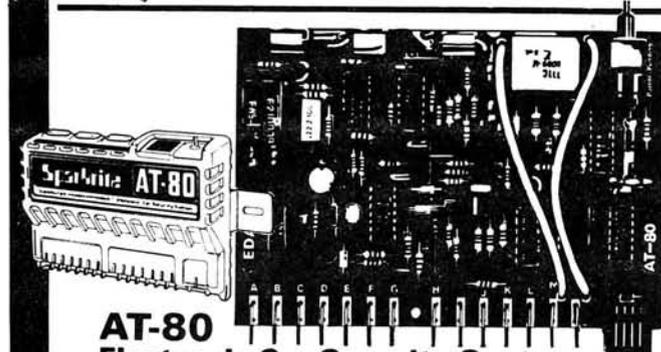


AT-80 Electronic Car Security System

- Arms doors, boot, bonnet and has security loop to protect fog/spot lamps, radio/tape, CB equipment
- Programmable personal code entry system
- Armed and disarmed from outside vehicle using a special magnetic key fob against a windscreen sensor pad adhered to the inside of the screen ● Fits all 12V neg earth vehicles
- Over 250 components to assemble

VOYAGER Car Drive Computer

- A most sophisticated accessory. ● Utilises a single chip mask programmed microprocessor incorporating a unique programme designed by EDA Sparkrite Ltd. ● Affords 12 functions centred on Fuel, Speed, Distance and Time. ● Visual and Audible alarms warning of Excess Speed, Frost/Ice, Lights-left-on. ● Facility to operate LOG and TRIP functions independently or synchronously.
- Large 10mm high 400ft-L fluorescent display with auto intensity. ● Unique speed and fuel transducers giving a programmed accuracy of + or - 1%. ● Large LOG & TRIP memories. 2,000 miles. 180 gallons. 100 hours. ● Full Imperial and Metric calibrations. ● Over 300 components to assemble.
- A real challenge for the electronics enthusiasts!

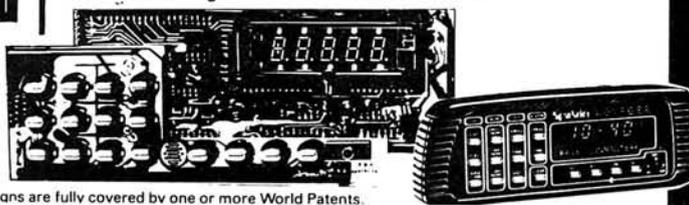

All EDA-SPARKRITE products and designs are fully covered by one or more World Patents.

EDA SPARKRITE LIMITED 82 Bath Street, Walsall, West Midlands, WS1 3DE England. Tel: (0922) 614791

Please allow 28 days for delivery

NAME _____ PW/2/82
ADDRESS _____

I ENCLOSE CHEQUE(S)/POSTAL ORDERS FOR

£ _____ KIT REF. _____

CHEQUE NO. _____
24hr. Answerphone
PHONE YOUR ORDER WITH ACCESS/BARCLAYCARD
SEND ONLY SAE IF BROCHURE IS REQUIRED

	SELF ASSEMBLY KIT	READY BUILT UNITS
SX 1000	£12.75	£27.95
SX 2000	£19.95	£43.75
TX 2002	£29.95	£62.95
AT. 80	£24.95	£49.75
VOYAGER	£49.95	£84.75
MAGIDICE	£12.95	£19.95

PRICES INC. VAT. POSTAGE & PACKING

BRANDEADING BRITISH ELECTRONICS
CUT OUT THE COUPON NOW!


A GREAT DAY OUT..

Enter the fascinating world of woodworking

Whatever your interest, skill or ambition in this traditional craft, you will find every facet of working in wood reflected here. Timber and tools, machinery and materials, plans and planes, clocks and clamps, dowels and drills, fitting and furniture, abrasives and adhesives – everything for everybody who ever works with wood.

See the widest range of machinery, tools, accessories and materials and how you can use them to improve your skills. See them in action, compare them and choose the ones which meet your needs and complement your style of woodworking.

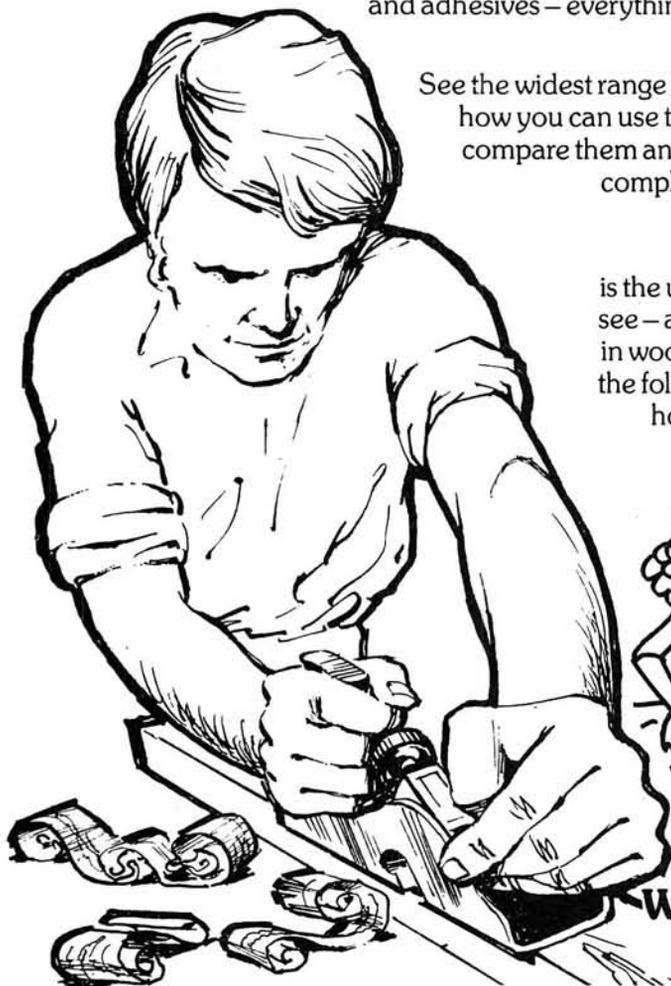THE CRAFT MARKET PLACE
is the unique centrepiece of this exhibition. Here, you can see – and buy if you wish – a wide range of beautiful items in wood showing what has been achieved by just some of the followers of the craft of woodworking. See for yourself how this absorbing hobby can also be profitable!



WEMBLEY CONFERENCE CENTRE

February 4-7, 1982

February 4-6, 10 am – 7 pm February 7 (Sunday), 10 am – 6 pm

Admission prices: Adults – £1.80
Children under 16 and Senior
Citizens – £1.00

Party rates: (groups of 20 or more)

Adults – £1.30 Children – 80p
(plus one free ticket per 20 tickets sold
for the organiser or teacher)

To get your party rate tickets
phone in advance to: The
Exhibition Manager, Practical
Woodworking Exhibition on
(01)-643 8040, or apply at the door.

PRACTICAL WOOD WORKING EXHIBITION

**Bring yourself –
and the family – and join in all the action!**

... sponsored by
Practical Woodworking
– full details in
the February
issue!

BUILD A PAIR OF MICRO MONITORS!

Just a few hours easy and interesting work and you'll have a superb pair of compact loudspeakers for about half the price of equivalent 'assembled' models.
The Wilmslow Audio Micro Monitor will stand comparison with any speaker of similar size (at any price!). Don't take our word for it - call for a demonstration!



The Micro Monitor kit contains all the components needed - a pair of cabinets in flat-pack form - accurately machined for easy assembly, all drive units, crossover networks, acoustic wadding, grille foam, velcro, nuts and bolts, etc. No electronic or woodworking knowledge required - simple, foolproof instructions supplied. The cabinets can be stained, painted or finished with iron-on veneer. Dimensions of assembled cabinet: 32x24x20cms. Suitable for amplifiers of 20 - 50 watts.

Price: **£103.95** per pair including VAT. Carriage and insurance £5.95



☎
0625 529599

35/39 Church Street, Wilmslow, Cheshire SK9 1AS



Lightning service on telephoned credit card orders!
Please allow 7 days for delivery.



MIGHTY NINETY PACKS ALL 90p Ea. Inc. VAT.

BUY SIX PACKS AND GET A SEVENTH PACK FREE!
POSTAGE 15p PER PACK

MN1	300 1/2 watt pre-formed resistors.	MN23	300 nuts, screws, washers, etc.
MN2	200 1/2 and 1/4 watt resistors.	MN31	15 assorted trimmer caps.
MN3	100 1 and 2 watt resistors.	MN32	13 30pF beehive trimmers.
MN4	50 wire wound resistors.	MN34	25 min. glass reed switch.
MN5	100 metal oxide resistors.	MN40	50 polystyrene capacitors.
MN6	12 assorted potentiometers.	MN42	10 BC107 transistors
MN7	25 assorted pre-set resistors.	MN43	10 BC108 transistors
MN8	50 assorted electrolytic caps.	MN44	10 slide switches sp/co.
MN9	100 assorted ceramic caps.	MN45	35 asstd. diodes - zener, rect., switching, signal.
MN10	100 mixed caps, poly, ceramic, elect, mica, etc.	MN51	10 - 2" red led.
MN13	20 assorted transistors.	MN53	20 0-1 mfd 25V ceramic disc.
MN14	40 1N4148 diodes.	MN54	20 0-01 mfd 25V ceramic disc.
MN20	1 240-110 to 12 volt 100mA transformer.	MN56	10 14 pin low profile I.C. socket.
MN22	8 - 2" LED's with clips 4 red, 2 yellow, 2 green.	MN57	10 16 pin low profile I.C. socket.
		MN58	2 x CA723 voltage reg.
		MN64	5 press-to-make min switches.

Microwave Modules as described in Practical Wireless "Exe". Project (Wessex Alarms) complete with horn. **£8.00** + 50p postage.

CHORDGATE LTD (Dept C)

75 Faringdon Road, Swindon, Wilts. Tel. (0793) 33877
OFFICIAL ORDERS SCHOOLS AND COLLEGES WELCOME
Retail premises at above address.

SPECIAL OFFERS IN NEW EQUIPMENT

SWAN ASTRO 150 HF Transceivers (RRP £613)
£525 incl VAT. Carriage £7.

NEC CQP 2200E 2M FM Transceivers (6 Channel)
£125 incl VAT. Carriage £2.
£90 incl VAT. Carriage £2.

Used CQP 2200Es

WE STOCK YASEU - SHURE - WELTZ - Cubic/Swan - Microwave Modules etc.

Quality crystals for 2 metres HC25/U **£1.65** each incl. VAT.

S0 TX 12-0833 RX 44-7666 R4 TX 12-0916 RX 45-0000
S23 TX 12-1312 RX 44-9583 R5 TX 12-0937 RX 45-0083
R0 TX 12-0833 RX 44-9666 R6 TX 12-0958 RX 45-0166
R3 TX 12-0895 RX 44-0895 R7 TX 12-0979 RX 45-0250
R8 TX 12-1000 RX 45-0333 R9 TX 12-1020 RX 45-4166

VALVES EL84/6BQ5 70p each incl. VAT. **EF184/6EJ7 80p** each incl. VAT. Please add 20p for post and packing for any quantity.
WE STOCK COMPONENTS, HARDWARE, CABLES, ANTENNAS Etc.
NEC SWAN/CUBIC FDK YAESU MICROWAVE MODULES

DAVTREND WELTZ etc.

William Munro (Invergordon) Limited

100 High Street, Invergordon, Ross-shire IV18 0DN
Tel: 0349 852351 Access Barclaycard Telex: 75265

Technical Training in Radio, Television and Electronics

ICS have helped thousands of ambitious people to move up into higher paid, more secure jobs in the field of electronics—now it can be your turn. Whether you are a newcomer to the field or are already working in the industry, ICS can provide you with the specialised training so essential to success.

Personal Tuition and Guaranteed Success

The expert and personal guidance by fully qualified tutors, backed by the ICS guarantee of tuition until successful is the key to our outstanding record in the technical training field. You study at the time and pace that suits you best and in your own home. In the words of one of our many successful students: "Since starting my course, my salary has trebled and I am expecting a further increase when my course is completed."

City and Guilds Certificates

Excellent job prospects await those who hold one of these recognised certificates. ICS can coach you for:

Telecommunications Technicians
Radio, TV Electronics Technicians
Technical Communications
Radio Servicing Theory
Radio Amateurs
Electrical Installation Work
Also MPT Radio Communications Certificate

Diploma Courses

Colour TV Servicing
Electronic Engineering and Maintenance
Computer Engineering and Programming
Radio, TV and Audio, Engineering and Servicing
Electrical Engineering, Installations and Contracting

Qualify for a New Career

Home study courses for leading professional examinations and diploma courses for business and technical subjects:—

G.C.E.	Engineering	Purchasing
60 subjects	Farming	Sales
at "O" &	Heating	Storekeeping
"A" levels	Industrial	Work Study
Accountancy	Management	
Air	Mechanical	
Conditioning		
Building		

POST OR PHONE TODAY FOR FREE BOOKLET.

ICS To: International Correspondence Schools

SINCE 1890
Dept. 276R Intertext House, London
SW8 4UJ or telephone 622 9911

Subject of Interest

Name

Address

Telephone Number



When replying to Classified Advertisements please ensure:

- (A) That you have clearly stated your requirements.
 - (B) That you have enclosed the right remittance.
 - (C) That your name and address is written in block capitals, and
 - (D) That your letter is correctly addressed to the advertiser.
- This will assist advertisers in processing and despatching orders with the minimum of delay.

Receivers and Components

AUTOMATIC MORSE DECODER - low cost easy build 9v circuit. Accepts audio input or practice key. Gives continuous readout on 12 character alphanumeric display. Send £3.95 plus large S.A.E. for fully detailed 17 page construction data. Parts and P.C.B. available. MacRitcie (Micros), 100 Drakies Avenue, Inverness IV2 3SD.

BRAND NEW COMPONENTS BY RETURN

HIGH STABILITY RESISTORS
 1/4W Carbon Film E12 Series 1R-10M. (E24 2R-6M2) 1p
 1/2W, 1W & 1W Metal Film E12 Series 10R-2M2-2p
METAL FILM 1/4W 1% E12 series 10R to 1M0-3p
CAPACITORS:
MULLARD Min. Ceramic E12 100V 2% 1.8pf. to 47pf.-3p
 2% 56pf. to 330pf.-4p. 10% 390pf. to 4700pf.-4p
Plate Ceramic 50V Wkg. Vertical Mounting.
 E12 22pf. to 1000pf. & E6 1K5pf. to 47Kpf.-2p
Miniature Polyester 250V Wkg. Vertical Mounting.
 .01, .015, .022, .033, .047 & 068 Mfd.-4p
 0.1-5p. 0.15 & 0.22-6p. 0.33 & 0.47-8p
 0.68-11p. 1.0-15p. 1.5-20p. 2.2-22p

ELECTROLYTIC. Wire Ended (Mkda/Volts).

0.47/50	5p	22/25	6p	100/25	7p	470/25	11p
1.0/50	5p	22/50	6p	100/50	8p	470/40	16p
2.2/50	5p	47/16	6p	220/16	8p	1000/15	15p
4.7/50	5p	47/25	6p	220/25	8p	1000/25	25p
10/50	5p	47/50	6p	220/50	10p	1000/40	35p
22/16	6p	100/16	7p	470/16	11p	2200/16	20p

TANTALUM BEAD SUBMINIATURE ELECTROLYTICS.

0.1, 0.22, 0.47, 1.0, 2.2 = 36V & 4.7 = 6.3V-14p
 4.7/16V & 25V-15p. 10/16 & 22/16-20p. 10/25-25p
 10/35V, 22/16V, 47/6.3V, 68/3V & 100/3V-30p
 15/25, 22/25, 47/10-35p, 47/16-80p, 220/16-£1.20
Polystyrene 63V Wkg. E12 Series Long Axial Wires.
 10 pf. to 820 pf.-3p. 1000 pf. to 10,000pf.-4p

TRANSISTORS.

BC107/8/9	10p	BC182L	8p	BF197	10p
BC147/8/9	10p	BC184L	8p	BFY50/51/52	15p
BC157/8/9	10p	BC212L	8p	BFX88	25p
BC547C/8C/9C/7p	8p	BCY70	15p	2N2926	7p
BC557C/8C/9C/7p	8p	BF195	10p	2N3055	50p

8 Pin D.I.L. i.c.'s 741 Op/amp.-18p. 555 Timer-24p
 Holders 8 Pin-9p. 14 Pin-12p. 16 Pin-14p. 18 Pin-16p. 28 Pin-25p. 40 Pin-30p.

DIODES (p.i.v./amps).

75/25mA	1N4148	2p	1250/1A	BY127	10p
100/1A	1N4002	4p	400/3A	1N5404	14p
800/1A	1N4006	6p	60/1.5A	S1M1	5p
1000/1A	1N4007	7p	30/150mA	AAY32	12p

ZENER DIODES.

E24 Series 3V3 to 33V 400mW-8p. 1W-14p
L.E.D.'s 3 mm. & 5 mm. Red-10p. Green, Yellow-14p
 Grommets for 3 mm.-13p. Holders for 5 mm.-2p

FUSES. 20 mm. Glass. 100mA to 5A. Q.B.-3p. A/S-5p
VOLTAGE REGULATORS. 5V, 8V, 12V, 15V 100mA-35p
 5V, 8V, 12V, 15V, 18V & 24V 0.5A-60p. 1A-65p

PRESET POTENTIOMETERS

50mW & 1/4W 100R to 1M0-7p.
PAIRS BATTERY SNAPS PP3-5p. PP9-10p

THE C. R. SUPPLY CO.

127, Chesterfield Road, Sheffield S8 0RN.
 V.A.T. Inclusive Prices, Postage 15p
 (FREE over £5.00)

SMALL ADS

The prepaid rate for classified advertisements is 32 pence per word (minimum 12 words), box number 60p extra. Semi-display setting £10.70 per single column centimetre (minimum 2.5 cms). All cheques, postal orders etc., to be made payable to Practical Wireless and crossed "Lloyds Bank Ltd". Treasury notes should always be sent registered post. Advertisements, together with remittance should be sent to the Classified Advertisement Manager, Practical Wireless, Room 2337, IPC Magazines Limited, King's Reach Tower, Stamford St., London, SE1 9LS. (Telephone 01-261 5846).

NOTICE TO READERS

Whilst prices of goods shown in advertisements are correct at the time of closing for press, readers are advised to check with the advertiser both prices and availability of goods before ordering from non-current issues of the magazine.

WE REPAIR/RESTORE valve type communication receivers with a one year guarantee. For a free quote telephone Corby 61697. Vintage British Radio Components Co., 22 Thurso Walk, Corby, Northants.

NOSTALGIA THE VINTAGE WIRELESS COMPANY COLLECTING 1920 to 1950

Receivers, valves, components, service data, historical research books, magazines, repairs and restorations. A complete service for the collector and enthusiast of vintage radio.

S.a.e. with enquiries and for monthly newsheet.
THE VINTAGE WIRELESS COMPANY, 64, Broad Street, Staple Hill, Bristol BS16 5NL. Tel. Bristol 565472.

VALVES. Radio, TV, Industrial transmitting, dispatched to all parts of the world by post. 6000 types in stock. Quotation SAE: Cox Radio (Sussex) Ltd., The Parade, East Wittering, Sussex. 2023 (024366).

CRYSTALS MADE TO ORDER within 6 weeks. 4-105MHz, wires or pins. £3.90 each inclusive. Hartley Crystals, Green Lane, Milford, Godalming, Surrey GU8 5BG.

BULK OFFERS

All new full spec. devices. No rubbish. SAE list. Prices per 100. Minimum order £10. Post £1. No VAT.

4001B	£3	POLYESTER CAPS, 100V ITT:
4007A	£9	-1 £2.50; -22 £3; -33 £3.50; -47 £4;
4011B	£9	-68 £5.50; 1-0 £6.
4017A	£20	0-1W presets, horiz. mntg:
4035B	£22	470R, 2K2, 4K7, 10K, 22K, 47K,
4503B	£25	100K. All £3/100.
4511B	£35	Tants: 0-1/35, 1-5/35, 2-2/16, all £4;
LM380N	£8	709 14 DIL
74LS112	£8	PC ELECTRONICS, 2, Thornhill,
709 14 DIL	£8	Romsey Road, Whiteparish,
C106F (No Tab)	£15	TBA120C
TBA120C	£15	Salisbury SP5 2SD.
MC357	£3	

BOURNEMOUTH/BOSCOMBE. Electronic components specialists for 33 years. Forresters (National Radio Supplies) late Holdenhurst Rd. now at 36, Ashley Rd., Boscombe. Tel. 302204. Closed Weds.

CRYSTALS Brand new high-precision. You benefit from very large stocks held for industrial supplies. All normal freq standards, baud rates, MPU, and all magazine projects inc:

HC39/U: 1-0, £3.75; 2.5625 MHz, £3.50; HC18/U: 4-0, 5-0, 6-0, 7-0, 8-0, 9-0, 10-0, 10-7, 12-0, 15-0, 16-0, 18-0, 20-0, 38-6667 MHz, £3.35. Selected freqs stocked in Glider, Marine and 27 MHz bands. Any freq made to order in 8 weeks from £4-10. 2-3 week service available.

FILTERS Your best source for 6 and 8 pole and monolithics for AM, CW, SSB, FM, on 455 kHz, 1-6, 9-0, 10-7, 21-4 MHz, etc.

Prices inc. VAT and UK post. SAE lists.

P. R. GOLLEDGE ELECTRONICS
 G3EDV, Merriott, Somerset, TA16 5NS.
 Tel: 0460 73718

BALLARD'S OF TUNBRIDGE WELLS have moved to 54 Grosvenor Road, no lists. S.A.E. all enquiries phone Tunbridge Wells 31803.

UOSAT ★ OSCAR

Complete program in Basic with comprehensive notes.

- ★ Reference orbits ★ Azimuth ★ Elevation
- ★ Range ★ Rise/set Times ★ Sub Sat Track
- ★ Full Sat Data ★ Doppler Period Measurement
- ★ Can also be used to calculate HF Beam Headings ★

Cheques for £10 to:

D. O'Neill,
 41 Barnton Road,
 Dumfries.

VHF CONVERTER 45-220MHz, 28-30MHz, tuneable IF £8. TVDX VHF-UHF converter. Receive VHF signals on UHF TV set £10.80. SAE data, lists, H. Cocks, Cripps Corner, Robertsbridge, Sussex. Tel. 058083-317.

FREE COMPONENT GRAB BAGS. Details, and Price list: SAE T.H.D. Electronics (Dept P.W.), 90 Longford, Yate, Bristol.

Aerials

COPPER AERIAL WIRE 14swg hard drawn 70' £5.34. 140' £8.84 inc. VAT. Postage £1.75 T.M.P. Electronics, Supplies, Britannia Stores, Leeswood, Nr. Mold. N. Wales.

G2DYM ANTI-INTERFERENCE ANTI-TVI TRAP DIPOLES TRANSMITTING & S.W.L. MODELS
 Data Sheets Large SAE. Aerial Guide 50p. Indoor and Invisible Aerials £3.50.
 Callers welcome Tel: 03986-215
G2DYM, Uplowman, Tiverton, Devon.

Books and Publications

UNIQUE T.V. REPAIR MANUALS and other books. SAE brings newsletter, price lists, etc. AUS, P.W., 68, Montgomery Street, Larkhall, Lanarkshire ML9 2AD.

WORLD RADIO TV HANDBOOK The world-famous guide to broadcasting schedules, indispensable for serious listeners - £10.49 or state Access/Visa number. Pointsea Research, 25 Westgate, North Berwick, East Lothian.

Record Accessories

STYLI for Music Centres etc. Free list for S.A.E., includes other accessories. FELSTEAD ELECTRONICS, Longley Lane, Gatley, Cheshire SK8 4EE.

Courses

COURSES - RADIO AMATEURS EXAMINATION. City and Guilds. Pass this important examination and obtain your licence, with any RRC Home Study Course. For details of this and other courses (GCE, professional examinations, etc.) write or phone - **THE RAPID RESULTS COLLEGE, DEPT JX1.** Tuition House, London SW19 4DS. Tel: 01-947 7272 (9am-5pm) or use our 24 hr Recordcall Service: 01-946 1102 quoting Dept. JX1.

Services

OSCILLOSCOPE repair and calibration. Quick service, competitive rates. W.I.R. Electronics 01-367-6816.

G.T. TECHNICAL INFORMATION SERVICE
 76 CHURCH ST., LARKHALL, LANARKS.
Any published full size service sheet – still only £1 + s.a.e.

Repair data your named T.V. £6.50 (with circuits £8.50)

Giant collections exploded diagrams of domestic equipment (many representative circuits) most leading manufacturers – 2 huge binders for £26.50 with free 1 year's updating service.

S.A.E. for free newsletter, price lists, any quotation, bargain offers, unique T.V. publications. 2 big catalogues list thousands service sheets/manuals plus £4 vouchers for £2 + large s.a.e. Complete British Colour TV circuits, etc. in 3 huge binders only £39.50.

Phone: 0698 883334 anytime. Callers 4-6 pm weekdays, Sat. 11-1.

**30,000 SERVICE SHEETS IN STOCK
 COLOUR MANUALS ALSO AVAILABLE**

TV Monos, Radios £1.25 – Tuners £1.25 – Tape Recorders, Record Players, Transistors from £1.25 – Car Radio £2.00 + S.A.E. – Stereograms, Radiograms from £1.25 – Also Colour available. – State, if circuit will do, if sheets are not in stock. All TV sheets are full length 24 x 12", not in Bits & Pieces. All other Data full lengths. Free Fault Finding Chart or TV Catalogue with order. Crossed P.O.s returned, if sheets not in stock. S.A.E. please.

£2 OLD Valve Radio
C. CARANNA
 71, Beaufort Park, London NW11 6BX
 01-458 4882 (Mail Order)

SERVICE SHEETS, Radio, Television, Stereo, etc., from 50p. Catalogue 25p. S.A.E. with orders, enquiries. Hamiltons, 47 Bohemia Road, St. Leonards, Sussex.

BELL'S TELEVISION SERVICES for Service Sheets on Radio, TV etc. £1.25 plus S.A.E. Colour TV Service Manuals on request. S.A.E. with enquiries to B.T.S., 190 Kings Road, Harrogate, N. Yorkshire. Tel. (0423) 55885.

SERVICE SHEETS, Radio, TV etc., 10,000 models. Catalogue 25p, plus S.A.E. with orders, enquiries, TELRAY, 5 Henderson Street, Preston PR1 7XP.

Personal

CHRISTIAN SINGLES HOLIDAYS. Weekend houseparties. Friendship contacts nationwide. C.F.F. Dept/B89, Edenthorpe, Doncaster.

Wanted

ELECTRONIC COMPONENTS PURCHASED. All types considered – Must be new. Send detailed list – Offer by return – WALTONS, 55A Worcester Street, Wolverhampton.

TWO ECLL80 VALVES. Savage "Ronada". Margaret Road, Liverpool, L23 6TR.

WANTED PW, MAY-JUNE, JULY 1963 Good price paid. Ring Southend 76211.

For Sale

NEW BACK ISSUES OF "PRACTICAL WIRELESS" available 90p each, post free. Cheque or uncrossed P/O returned if not in stock – BELL'S TELEVISION SERVICE, 190 Kings Road, Harrogate, N. Yorks. Tel. (0423) 55885.

TRIO 9R-59DE COMMUNICATION RECEIVER, boxed with handbook, little used. Offers. Jebb, 72 West Street, Dunstable, Beds.

EDDYSTONE EC10 short-wave receiver 0.5-30MHz SSB/AM £65. 01-578 0539.

**TELEVISION COMPUTER
 RADIOCOMMUNICATIONS
 & RADAR SERVICING**

**TWO YEAR full-time Modular
 Diploma course to include a high
 percentage of practical work.**

- ELECTRONIC PRINCIPLES
- MONO TV & CCTV
- COLOUR TV & VCR
- MICROELECTRONICS & DIGITAL TECHNIQUES
- MICROPROCESSORS & COMPUTERS
- RADIOCOMMUNICATIONS & RADAR

Each of the above Modules are 13 weeks in duration. Individual Modules can be arranged for applicants with suitable electronics background.

Tuition fees (UK & Overseas) £1575 per year (i.e. £525 per Module).

Next session starts January 4th.

Prospectus from:

**LONDON ELECTRONICS
 COLLEGE**

Dept: PP, 20 Penywern Road,
 London SW5 9SU. Tel: 01-373 8721.

ORDER FORM PLEASE WRITE IN BLOCK CAPITALS

Please insert the advertisement below in the next available issue of Practical Wireless for

insertions. I enclose Cheque/P.O. for £.....
 (Cheques and Postal Orders should be crossed Lloyds Bank Ltd. and made payable to Practical Electronics).

NAME.....

ADDRESS.....

Send to: Classified Advertisement Manager
PRACTICAL WIRELESS
 Classified Advertisements Dept., Room 2337
 King's Reach Tower, Stamford Street,
 London SE1 9LS. Telephone 01-261 5846
 Rate:
 32p per word, minimum 12 words. Box No. 60p extra.

Company registered in England. Registered No. 53626. Registered Office: King's Reach Tower, Stamford Street, London SE1 9LS.

Educational - cont.

TECHNICAL TRAINING

Get the training you need to move up into a higher paid job. Take the first step now—write or phone ICS for details of ICS specialist homestudy courses on Radio, TV, Audio Eng. and Servicing, Electronics, Computers, also self-build radio kits. Full details from:

ICS SCHOOL OF ELECTRONICS
Dept. 277R Intertext House, London SW8 4UJ
Tel. 01-622 9911 (all hours)
State if under 18

COLOUR TV SERVICING

Learn the techniques of servicing Colour TV sets through new homestudy course approved by leading manufacturers. Covers principles, practice and alignment with numerous illustrations and diagrams. Other courses for radio and audio servicing. Full details from:

ICS SCHOOL OF ELECTRONICS
Dept. 277R Intertext House, London SW8 4UJ
Tel. 01-622 9911 (all hours)
State if under 18

CITY & GUILDS EXAMS

Study for success with ICS. An ICS homestudy course will ensure that you pass your C. & G. exams. Special courses for: Telecoms, Technicians, Electrical Installations, Radio, TV & Electronics Technicians, Radio Amateurs, Full details from:

ICS SCHOOL OF ELECTRONICS
Dept. 277R Intertext House, London SW8 4UJ
Tel. 01-622 9911 (all hours)
State if under 18

Miscellaneous

ALUMINIUM TUBES FOR AERIALS. Various sizes available. Nerva Metals. 01-904 4647.

PRE-PACKED. Screws, nuts, washer, solder tags studding. Send for price list. A1 Sales (PW), P.O. Box 402, London SW6 6LU.

SUPERB INSTRUMENT CASES by Bazelli, manufactured from PVC Faced Steel. Hundreds of people and industrial users are choosing the cases they require from our vast range. Competitive prices start at a low £1.05. Chassis punching facilities at very competitive prices. 400 models to choose from. Suppliers only to Industry and the Trade. **BAZELLI**, (Dept No. 25), St. Wilfrid's Foundry Lane, Halton, Lancaster LA1 6LT.

THE SCIENTIFIC WIRE COMPANY

PO Box 30, London E 4
Telephone 01 531 1568

ENAMELLED COPPER WIRE

SWG	1 lb	8 oz	4 oz	2 oz
8 to 29	2.76	1.50	0.80	0.60
30 to 34	3.20	1.80	0.90	0.70
35 to 39	3.40	2.00	1.10	0.80
40 to 43	4.75	2.60	2.00	1.42
44 to 47	5.90	3.40	2.39	2.00
48 to 49	15.96	9.58	6.38	3.69

SILVER PLATED COPPER WIRE

14 to 30	6.50	3.75	2.20	1.40
----------	------	------	------	------

TINNED COPPER WIRE

14 to 30	3.85	2.36	1.34	0.90
----------	------	------	------	------

Prices incl. P&P and VAT. Orders under £2 add 20p.

SAE for list of Copper/Resistance Wire.

Dealer enquiries welcome.

Reg. Office 22, Coningsby Gardens.

CENTURION BURGLAR ALARM EQUIPMENT. Send SAE for list or a cheque/PO for £11.50 for our special offer of a full sized signwritten bell cover, to: Centurion, Dept PW, 265 Wakefield Road, Huddersfield, W. Yorkshire. Access & Barclaycard. Telephone orders on 0484-35527.

RECHARGEABLE BATTERIES

PRIVATE & TRADE ENQUIRIES WELCOME
FULL RANGE AVAILABLE. SAE FOR LISTS. £1.45 for Booklet "Nickel Cadmium Power" plus Catalogue. Write or call, Sandwell Plant Ltd, 2 Union Drive, BOLDMERE, SUTTON COLDFIELD, WEST MIDLANDS. 021 354 9764. AFTER HOURS 0977 84093
* NEW SEALED LEAD RANGE AVAILABLE *

PARAPHYSICALS JOURNAL (Russian Translations): Psychotronic Generators, Kirlianography, Gravity Lasers, Telekinesis. Details: SAE 4x9" Paralab, Downton, Wilts.

WAVEGUIDE, FLANGES & DISHES. All standard sizes & alloys stock. Special sizes to order. Call Earth Stations, 01-228 7876. 22, Howie Street, London SW11 4AR.

GLADSTONE RADIO, 66 Elms Road, Aldershot GU11 1 LP Closing March '82. Send two second class postage stamps (unused) for lists of components, speakers etc., at knock out prices.

ANTENNA FAULT?

LOSING DX? Poor reports? Check with an Antenna Noise Bridge, MEASURE resonance 1-150MHz and radiation resistance 2-1000 ohms, ANSWERS, £15.70.

V.L.F.7 EXPLORE 10-150MHz, Receiver £16.50. RARE DX UNDER QRM? DIG it OUT with a Tunable Audio Notch Filter, between your receiver and speaker, BOOST your DX/QRM ratio, 40dB notch, hear WEAK DX, £13.80. Each fun-to-build kit includes all parts, printed circuit, case, instructions, postage etc, money back assurance so GET yours NOW.

CAMBRIDGE KITS

45 (PB) Old School Lane, Milton, Cambridge.

ELECTRONIC KITS. Largest range of kits in the U.K. Everything from stroboscopic lights to transmitters, at unbeatable prices. Send S.A.E. for free catalogue to: EASTLING ELECTRONICS (KITS), 64B Hawthorne Road, Winton, Bournemouth.

MORSE CODE TUITION AIDS

Cassette A: 1-12 w.p.m. for amateur radio examination. Cassette B: 12-25 w.p.m. for professional examination preparation. Each cassette is type C90. Morse Key and Buzzer unit for sending practice. Price each Cassette (including booklets) £4.75. Morse Key and Buzzer £4.75. Prices include postage etc. Overseas Airmail £1.50 extra.

BARCLAYCARD (VISA) NUMBER ACCEPTED

MHEL ELECTRONICS (Dept 2), 12 Longshore Way, Milton, Portsmouth PO4 8LS.

CORDLES TELEPHONES, build your own simple and inexpensive units. Send £3.00 for plans to J. F. Ashley, Birley Grange Cottage Farm, Baslow Road, Cutthorpe, Derbyshire.

BURGLAR ALARM EQUIPMENT. Ring Bradford (0274) 308920 for our catalogue or call at our large show-rooms opposite Odsal Stadium.

QUALITY PERSONAL CALLSIGN TIES. Callsign - offwhite 3mm symbols on navy, wine or green background. Minimum order is two ties on same background, £9.70 the pair incl. 5/6 weeks delivery. - CWO to Garrison Radio, Catterick Garrison, N. Yorks. DL9 3JD. Tel. 0748-833311.

PCBs FOR PRACTICAL WIRELESS PROJECTS

Jan. 79	Sandbank Metal Detector	RO35	£3.81
Mar. 79	Soundlite Converter	WK001	£6.63
Jan. 80	A F Speech Processor	WR068	£2.68
Jan. 80	Wide Band RF Pre Amp	WR067	£1.00
June 80	Nimbus Base Station Adaptor	WR083	£2.90
Aug. 80	Model Railway Converter	WR085	£2.47
Sept. 80	Transceiver Power Unit	WR095	£1.00
Sept. 80	Beginners 2 Meter Converter	WAD634	£1.38
Feb. 81	PW Morse Tutor	WR081	£3.70
Feb. 81	Tape Slide Controller	Set of 3	£7.50
Mar. 81	Active Antenna	WAD784	£1.20
April 81	PW Helford 6V Stabiliser	WAD804	£1.00
April 81	Boat Engine Hours Counter	WAD788	£2.70
May 81	PW Stour	WAD834	£2.90
June 81	Car Audio Amp	WAD847	£1.35
July 81	Auto Cut-Out Power Supply	WAD853	£1.90
July 81	Stour	WR123	£4.40
July 81	Stour	WR124	£4.40
July 81	Stour	WAD830	£2.75
July 81	Stour	WR125	£5.50
Aug. 81	Exe. Micro Wave Transceiver	WR126	£3.90
Sept. 81		WR131	£2.50
Oct. 81	Sleep Timer	WR122	£2.60
Oct. 81	Stour	WR127	£3.80
Oct. 81	Stour	WR128	£4.50
Oct. 81	Stour	WR129	£4.50
Oct. 81	Stour	WR130	£4.50
Dec. 81	PW Winton Tuner	WR134	£5.95
Dec. 81	PW Winton Tuner	WR136	£4.50
Dec. 81	Crystal Calibrator	WR135	£1.70

Full range of RS components available.
Please phone for quote.


Please note our new address:
C. BOWES ELECTRONICS LTD.,
28 Stockport Road, Cheadle, Cheshire
Tel: 061-491 1644 ext. 5.
PLEASE SEND CASH WITH ORDER.

PROGRESSIVE RADIO

ALL ORDERS DESPATCHED BY RETURN POST

NICADS. 'AA' size 95p, 'C' 2AH £2.80p, 'D' 1.2AH £2.40p, 'D' 4AH £3.80p.
UNIVERSAL NICAD CHARGER, charges 'AA', 'C' or 'D' cells, up to 4 of each type £9.25p.
SWITCHES. Min. toggles, SPST 8x5x7mm 42p. DPDT 8x7x7mm 55p. DPDT off 12x11x9mm 77p. HEAVY DUTY-DPDT 240VAC 10 Amp 35p. PUSH TYPE, push on 16x6mm 15p, push to break version 17p. MERCURY (TILT) SWITCH, 1" x 1/2" 35p. NSA1198 8 1/2 digit multiplexed displays. com. cath. with data sheet £1.45p.
SPECIAL OFFER TIL209 Red LED's 10 for 75p. 0.2" LEDs, red, yellow, green 10p each.
MICROPHONE OFFERS: P.A./C.B. hand held mikes with thumb switch + curly lead, 1. 600Q dynamic £3.95p, 2. 600Q noise cancelling type £7.25p, 3. CB power type with volume control £7.95p. EM103 Electret Condenser Mike, 600Q, Omni, 50-1600Hz, aluminium case 172 x 22mm with battery £7.25p.
ANTEX SOLDERING IRONS: Models C15, CX17 and X25 all £4.45 each.
STABILISED POWER SUPPLY, 240 vac input 13.8 volts at 3/5 Amps DC output. £12.25p + 87p P-P.
JUMPER TEST LEAD SETS. 10 pairs of leads with insulated crocs each end 90p.
40KHZ TRANSDUCERS, RX/TX £3.50 pair.
STC BREAK GLASS FIRE ALARM UNITS, new with mounting box £1.50p.
MINIATURE SOLID STATE BUZZERS. 2 voltages available, 6 or 12VDC 75p each, Loud 12 volt buzzers 65p.
Cash with order please, official orders welcome from schools etc., please add 30p postage and packing. VAT inclusive. New catalogue at printers. Sorry for delay. All S.A.E.'s sent are being held until catalogue is ready.

31, CHEAPSIDE, LIVERPOOL L2 2DY

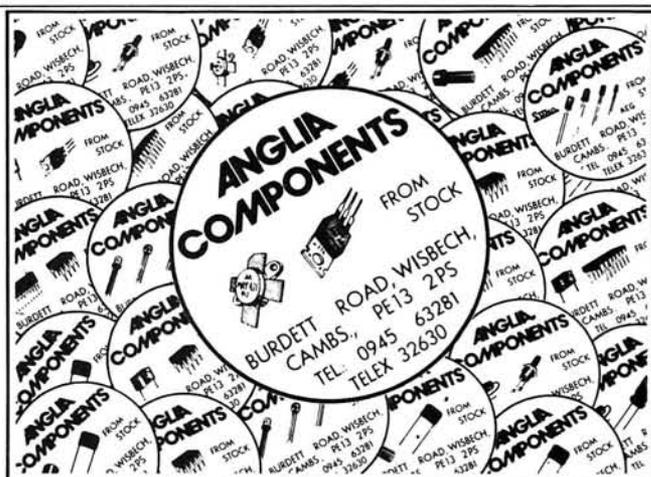



TITAN TRANSFORMERS AND COMPONENTS

DEPT. PW, CENTRAL HALL CHAMBERS
DUNCOMBE STREET, GRIMSBY
SOUTH HUMBERSIDE DN32 7EG

Mail order. Prices include 15% V.A.T.
Send for our catalogue
Please allow 28 days for Delivery.

12/24V RANGE PRI 220/240V			
SEC. $\begin{matrix} \text{0} & \text{12V} & \text{24V} \\ \text{0} & \text{12V} & \text{24V} \end{matrix}$			
TYPE	AMPS	PRICE	P/P
242	0.3 0.15	1.70	0.40
213	10.50	2.65	0.87
71	2 1	2.77	1.10
18	4 2	3.98	1.43
68	3 1.5	3.46	1.43
85	5 2.5	6.06	1.43
70	6 3	6.67	1.43
108	8 4	8.03	1.43
72		8.66	1.73
116	12 6	9.31	1.90
17	16 8	11.46	2.05
115	20 10	13.69	2.05
187	30 15	19.23	2.35
232	40 20	27.61	4.50
226	60 30	35.35	4.00

30/60V RANGE PRI 120/220/240V			
SEC. $\begin{matrix} \text{0} & \text{24V} & \text{30V} & \text{60V} \\ \text{0} & \text{24V} & \text{30V} & \text{60V} \end{matrix}$			
TYPE	AMPS	PRICE	P/P
124	1 0.5	3.30	1.43
126	2 1	6.36	1.43
127	4 2	7.86	1.73
125	6 3	11.78	1.90
123	8 4	14.72	2.20
40	10 5	17.10	2.20
120	12 6	19.44	2.35
121	16 8	27.70	2.65
122	20 10	32.05	4.00
189	24 12	37.02	5.00

CASED AUTOTRANSFORMERS			
240V LEAD IN 115V 2PIN SOCKET OUT			
TYPE	VA	PRICE	P/P
56W	20	6.60	0.87
64W	80	8.43	1.43
4W	150	10.86	1.73
69W	250	13.17	1.90
67W	500	20.46	2.20
84W	1000	30.24	2.55
95W	2000	54.83	5.00
73W	3000	76.67	6.50

15/30V RANGE PRI 220/240V			
SEC. $\begin{matrix} \text{0} & \text{12V} & \text{15V} & \text{30V} \\ \text{0} & \text{12V} & \text{15V} & \text{30V} \end{matrix}$			
TYPE	AMPS	PRICE	P/P
112	1 0.50	2.84	1.10
79	2 1.0	3.29	1.10
3	4 2	6.18	1.43
20	6 3	7.19	1.73
21	8 4	8.52	1.73
51	10 5	10.57	1.90
117	12 6	11.94	2.05
88	16 8	16.14	2.20
89	20 10	18.54	2.35
90	24 12	20.57	2.55
91	30 15	23.63	2.65
92	40 20	33.21	4.50


48/96V RANGE PRI 120/220/240V			
SEC. $\begin{matrix} \text{0} & \text{24V} & \text{48V} & \text{96V} \\ \text{0} & \text{24V} & \text{48V} & \text{96V} \end{matrix}$			
TYPE	AMPS	PRICE	P/P
430	1 0.5	4.69	1.43
431	2 1	7.84	1.43
432	4 2	12.94	2.05
433	6 3	14.62	2.20
434	8 4	20.04	2.45
435	10 5	28.75	2.65
436	12 6	36.16	4.00
437	16 8	39.47	4.00

LINE ADJUSTMENT AUTOTRANSFORMERS			
0 200 210 220 230 240 250			
TYPE	VA	PRICE	P/P
415C	50	2.31	0.87
416C	100	3.46	0.87
417C	200	4.00	1.10
418F	350	6.26	1.43
419F	500	6.74	1.73
420E	750	8.33	1.90
421F	1000	11.64	2.05

25/50V RANGE PRI 120/220/240V			
SEC. $\begin{matrix} \text{0} & \text{20V} & \text{25V} & \text{50V} \\ \text{0} & \text{20V} & \text{25V} & \text{50V} \end{matrix}$			
TYPE	AMPS	PRICE	P/P
102	1 0.50	3.29	1.43
103	2 1.0	4.09	1.43
104	4 2	7.65	1.73
105	6 3	9.09	1.90
106	8 4	12.24	1.90
107	12 6	15.15	2.20
118	16 8	22.46	2.55
119	20 10	27.05	2.55
109	24 12	32.44	4.50

AUTOTRANSFORMERS			
240/220-115V 65VA-10KVA			
TYPE	VA	PRICE	P/P
25	65	3.90	1.10
64	80	4.82	1.10
67	150	6.21	1.43
69	250	7.54	1.43
53	350	9.73	1.90
67	500	11.70	2.20
83	750	13.51	2.05
84	1000	18.31	2.35
95	2KVA	34.36	5.00
73	3	64.74	5.00
57	5	97.85	6.50
101	10	179.05	10.00

MAINS ISOLATORS (SAFETY SCREEN)			
PRI 120/220/240V SEC 60V 50V 0V 50V 60V			
TYPE	VA	PRICE	P/P
149F	60	8.40	1.73
150F	100	9.71	1.73
151F	200	13.84	2.05
152F	250	16.69	2.20
153F	350	20.77	2.55
154F	500	26.03	2.65
155F	750	36.75	5.00
156F	1000	47.42	6.00

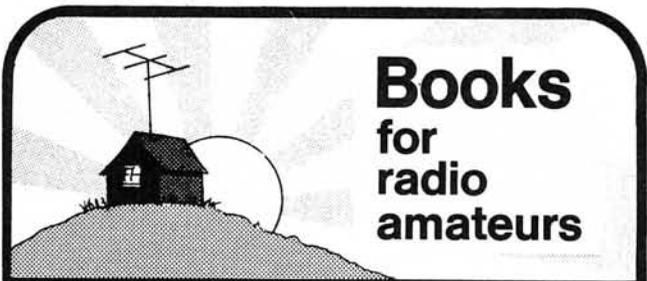

Books for radio amateurs

RSGB Publications

- A Guide to Amateur Radio (18th edn, paperback).....£3.07
- A Guide to Amateur Radio (18th edn, hardback).....£6.32
- Amateur Radio Awards (2nd edn).....£3.41
- Amateur Radio Operating Manual (new 2nd edn).....£4.96
- Amateur Radio Techniques (7th edn).....£6.16
- OSCAR - Amateur Radio Satellites.....£4.50
- Radio Amateurs' Examination Manual (9th edn) (1982-85 syllabus).....£3.12
- Radio Communication Handbook (5th edn) Vol 1.....£10.20
- Radio Communication Handbook (5th edn) Vol 2.....£9.06
- RSGB Amateur Radio Call Book (latest 1982 edn).....£4.71
- Test Equipment for the Radio Amateur (2nd edn).....£5.86
- Television Interference Manual (2nd edn).....£1.95
- VHF/UHF Manual (3rd edn).....£8.70
- World at their Fingertips.....£4.28
- Logbooks**
- Amateur Radio Logbook.....£2.45
- Mobile Logbook.....£1.14
- Receiving Station Logbook.....£2.68
- Wall maps**
- Great Circle DX Map.....£2.12
- IARU QTH Locator Map of Europe.....£1.34
- QTH Locator Map of Western Europe.....£1.34

Other Publications

- A Course in Radio Fundamentals (ARRL).....£3.24
- Active Filter Cookbook (Sams).....£12.69
- All About Cubical Quad Antennas (RPI).....£2.92
- Amateur Television Handbook (BATIC).....£2.39
- Antenna Anthology (ARRL).....£3.28
- ARRL Electronics Data Book.....£3.58
- Beam Antenna Handbook (RPI).....£4.11
- Beginner's Handbook of Amateur Radio (Sams).....£8.26
- Better Short Wave Reception (RPI).....£3.33
- Care & Feeding of Power Grid Tubes (Varian).....£2.98
- CMOS Cookbook (Sams).....£9.59
- Design of VMOS Circuits (Sams).....£7.95
- FM & Repeaters for the Radio Amateur (ARRL).....£3.67
- Hints and Kinks for the Radio Amateur (ARRL).....£3.11
- How to Program and Interface Your 6800 (Sams).....£12.74
- IC Converter Cookbook (Sams).....£11.28
- Knowing your Oscilloscope (Sams).....£6.32
- Microcomputer Primer (Sams).....£13.98
- Practical Antennas for the Radio Amateur (SCLEBI).....£8.02
- Radio Frequency Interference (ARRL).....£2.67
- RTTY the Easy Way (BARTG).....£1.14
- Shortwave Listeners Guide (Sams).....£4.44
- Single Sideband for the Radio Amateur (ARRL).....£3.32
- Solid-state Basics (ARRL).....£3.89
- Solid-state Design for the Radio Amateur (ARRL).....£5.56
- The ARRL Antenna Book.....£3.94
- The Cheap Video Cookbook (Sams).....£5.47
- The Complete Handbook of Slow Scan TV (Tab).....£5.76
- The 8080A Bugbook (Sams).....£9.59
- Understanding Amateur Radio (ARRL).....£4.06
- World Atlas (RACI).....£1.91
- 80m DXing (CTI).....£3.03
- 6809 Microcomputer Programming (Sams).....£10.89
- 8085A Cookbook (Sams).....£11.28

Prices include postage, packing and VAT where applicable. Postal terms: cheques/POs with order (not stamps or book tokens). Goods are obtainable (less P & P) at RSGB HQ, 10am-4pm, Monday - Friday.

The RSGB is the national society representing all UK radio amateurs and membership is open to all interested in the hobby, including listeners. The Society also publishes a complete range of books, log books and maps for the radio amateur. Contact the membership services section for more information about amateur radio, the RSGB and its publications.



Radio Society of Great Britain
35 Doughty Street, London WC1N 2AE
Telephone 01-837 8688

MAIL ORDER ADVERTISING

British Code of Advertising Practice

Advertisements in this publication are required to conform to the British Code of Advertising Practice. In respect of mail order advertisements where money is paid in advance, the code requires advertisers to fulfil orders within 28 days, unless a longer delivery period is stated. Where goods are returned undamaged within seven days, the purchaser's money must be refunded. Please retain proof of postage/despatch, as this may be needed.

Mail Order Protection Scheme

If you order goods from Mail Order advertisements in this magazine and pay by post in advance of delivery, PRACTICAL WIRELESS will consider you for compensation if the Advertiser should become insolvent or bankrupt, provided:

- (1) You have not received the goods or had your money returned; and
- (2) You wrote to the Publisher of PRACTICAL WIRELESS summarising the situation not earlier than 28 days from the day you sent your order and not later than two months from that day.

Please do not wait until the last moment to inform us. When you write, we will tell you how to make your claim and what evidence of payment is required. We guarantee to meet claims from readers made in accordance with the above procedure as soon as possible after the Advertiser has been declared bankrupt or insolvent.

This guarantee covers only advance payment sent in direct response to an advertisement in this magazine not, for example payment made in response to catalogues etc. received as a result of answering such advertisements. Classified advertisements are excluded.

VIDEO TRANSMITTER BOARD

Ready built - Crystalled & Aligned - Video In - 1/2 Watt RF out. - 13-8V DC - One Compact Board (110mm x 50mm) **£54 + 75p p&p**

ATV UP CONVERTOR

Suitable for domestic TV **£19.95 + 50p p&p**

Available soon - 2W and 10W 70cms linear amplifiers.

Terms: Cash With Order. Please send a s.a.e. for further details.

R. M. WEBB TELEVISION SERVICES
57 New Street, Burton-on-Trent
Tel: (0283) 65092.

WATFORD ELECTRONICS

33/35, CARDIFF ROAD, WATFORD, HERTS, ENGLAND
TEL. WATFORD (0923) 40588. TELEX 8956095

ALL DEVICES BRAND NEW. FULL SPEC. AND FULLY GUARANTEED. ORDERS DESPATCHED BY RETURN OF POST. TERMS OF BUSINESS: CASH/CHEQUE/P.O. OR BANKERS DRAFT WITH ORDER. GOVERNMENT AND EDUCATIONAL INSTITUTIONS OFFICIAL ORDERS ACCEPTED (TELEPHONE ORDERS BY ACCESS NOW ACCEPTED Minimum £10.00 please). TRADE AND EXPORT INQUIRY WELCOME. P & ADD 50p TO ALL ORDERS UNDER £10.00. (excluding VAT). OVERSEAS ORDERS POSTAGE AT COST.

VAT Export orders no VAT. Applicable to U.K. Customers only. Unless stated otherwise, all prices are exclusive of VAT. Please add 15% to the total cost including p & p.

We stock many more items. It pays to visit us. We are situated behind Watford Football Ground. Nearest Underground/Br. Rail Station: Watford High Street. Open Monday to Saturday 9 a.m. - 6 p.m. Ample Free Car Parking space available.

POLYESTER RADIAL LEAD CAPACITORS: 250V;
10n, 15n, 22n, 27n 6p; 33n, 47n, 68n, 100n 7p; 150n, 220n 10p; 330n, 470n 13p; 680n 19p; 1µ 23p; 1.5µ 40p; 2µ 46p.

ULTRASONIC TRANSDUCERS
395p per pair.

ELECTROLYTIC CAPACITORS (Values in µF): 500V: 10 52p; 47 78p; 63V: 0.47, 1.0 1.5, 2.2, 3.3, 8p; 4.7 9p; 6.8, 10, 22, 33 15p; 47 12p; 100 19p; 1000 70p; 50V: 47 12p; 68 20p; 220 24p; 470 32p; 2200 90p; 40V: 4.7, 1.5, 2.2, 9p; 3300 92p; 4700 120p; 25V: 1.5, 6.8, 10, 22, 33, 47 8p; 100 11p; 150 12p; 220 15p; 330 22p; 470 25p; 680, 1000 34p; 2200 50p; 3300 76p; 4700 92p; 16V: 40, 47, 100 9p; 125 12p; 220 13p; 470 20p; 680 34p; 1000 27p; 1500 31p; 2200 36p; 3300 74p; 4700 79p.

TAG-END TYPE: 70V: 4700 245p; 64V: 3300 198p; 2200 139p; 50V: 3300 154p; 2200 110p; 40V: 4700 160p; 25V: 10,000 320p; 15,000 345p.

TANTALUM BEAD CAPACITORS:
35V: 0.1 1µ, 0.22, 0.33 15p; 0.47, 0.68 1.0, 1.5 16p; 2.2, 3.3 18p; 4.7, 6.8 22p; 10 28p; 16V: 2.2, 3.3 16p; 4.7 6.8, 10 18p; 15 36p; 22 30p; 33, 47 40p; 100 75p; 220 88p; 10V: 15, 22 26p; 33, 47 35p; 100 55p.

POTENTIOMETERS: Caron Track 0.25W log & Linear Valves. 470Ω, 680Ω 1K, 2K (Lin only) Single 29p
5KΩ to 2MΩ Single gang 78p
5KΩ to 2MΩ Single with D/P switch 29p
5KΩ to 2MΩ Dual gang 98p
1W Wirewound 50Ω-20K 115p

POLYESTER (MYLAR) CAPACITORS:
100V: 1nF, 2n, 4n, 4n7, 10n 6p; 15nF, 22n, 30n, 40, 47 7p; 56, 100n, 200 9p; 500V: 470nF 12p.

SLIDER POTENTIOMETERS:
0.25W log and linear values 60mm track
5KΩ 500KΩ Single gang 70p
10KΩ 500KΩ Dual gang 110p
Self-Stick graduated Alum. Bezels 40p

CERAMIC CAPACITORS 50V
Range: 0.5pF to 10nF
15nF, 22nF, 33nF, 47nF 5p 100nF 7p

PRESET POTENTIOMETERS:
0.1W 50Ω-2.2M Min. Vert. & Horiz. 7p
0.25W 100Ω-3.3M Horiz. larger 10p
0.25W 250Ω-4.7M Vert. 10p

POLYSTYRENE CAPACITORS
10pF to 1nF, 8p 1-5nF to 12nF, 10p.

OPTO ELECTRONICS
LEDs plus clip 13 3 4 Digit LCD 550
T.C.O. Res 7 13 4 Digit LCD 120
TIL211 Grn 18 OCP 70
TIL212 Yel 18 ORP12 76
2" Red 14 2N5777 45
2" Green or Yellow 18 (Infra Red Emitter) 45
Rectangular LED's LD271 46
with Green, Yellow TIL32 52
with bezel 29
7 Seg. Displays Red SFH205 91
3" C Cath 99 TIL78 60
3" C Anod 99
3" ± 1 Red or Grn 150
5" C Cath 115 100KHz 270
5" C Anod 115 455KHz 370
6" C Cath 180 1MHz 295
8" Orange 275 1.008M 395
Burgraph 10 seg. 225 1.6MHz 395

RESISTORS—5% carbon, High Stab. Miniature, Low Noise.
Range Val. 1-99 100+
0.25W 202-4M7 E24 2p 1p
0.5W 202-5M1 E12 2p 1p
1W 202-10M E24 5p 3p
25 Metal Film 100-1M E24 6p 4p
1% 0.5W 51Q-1M E24 10p 8p
N.B. 100% price applies to Resistors of each type not mixed values.

CRYSTALS
LM10 395 RC4136D 69
702 75 LM301A 26
709C 8 pin 35 LM308T 85
710* 48 LM311H 70
733 78 LM318 240
741 8 pin 14 LM324 50
747C 14 pin 78 LM339 120
748C 8 pin 36 LM348 90
753 8 pin 185 LM349 115
815 159 LM379 415
9400CJ 350 LM380 75
AY-1-0212 675 LM381N 145
AY-1-0213 660 LM382 120
AY-1-1320 225 LM386 99
AY-1-5050 99 LM387 120
AY-1-5051 160 LM389 99
AY-3-1270 840 LM733 75
AY-3-8500 390 LM1458 60
AY-3-9110 720 LM390 60
AY-5-1224 235 LM3909N 120
AY-5-1230 450 LM3911 125
AY-5-1317A 639 LM3914 220
AY-5-8100 735 LM3915 240
CA3011 110 LM3916 225
CA3014 157 LM13600 135
CA3018 186 MS24A 280
CA3020 186 M52AA 625
CA3023 191 M253AA 1150
CA3028A 80 MC1300A 88
CA3035 235 MC1304P 260
CA3036 115 MC1310P 150
CA3043 275 MC1494 694
CA3045 385 MC1495 694
CA3046 71 MC1496L 92
CA3048 214 MC1596 225
CA3059 195 MC1710 79
CA3075 213 MC3302 190
CA3080E 65 MC3340P 120
CA3089E 215 MC3401 52
CA3090AQ 375 MC3403 89
CA3123 150 MC3405 150
CA3130 90 MFC6040 97
CA3140 48 MK5309B 65
CA3189 295 MMS303 635
ICL7106 795 MMS307 1275
ICL7107 975 MMS5526 820
ICL8038CC 340 NE543K 210
ICM7205 1150 NE544 185
ICM7215 1050 NE555 18
ICM7216A 1950 NE556DB 65
ICM7216B 1950 NE560 325
ICM7216C 1950 NE561 398
ICM7217A 790 NE562B 410
ICM7217B 80 NE564 420
ICM7218 80 NE565 120
ICM7219 48 NE566 120
LC130 495 NE567 150
LD130 452 NE567V 450
LF355 85 NE570 450
LF356 90 NE571 420

VEROBOARDS: 0.1" VQ Board 150p
Clad Plain DIP Board 330p
Vero Strip 144p
2 1/2 x 3 1/2 73p 52p
2 1/2 x 5 83p
3 1/2 x 3 1/2 83p
3 1/2 x 5 95p
3 1/2 x 7 95p
4 x 17 426p
Pkt of 100 pins 50p
Spot face cutter 118p
Pin insertion tool 162p

COMPUTER
214L 300n 99 7400 11
2114L 200n 130 7401 11
2532 32K 525 7403 14
2708 200 7404 14
2746 5V 7405 16
2746 5V 7406 28
2746 5V 7407 28
2746 5V 7408 28
4116-16K 85 7408 16
4315 CMOS 795 7409 16
6502 450 7410 14
7411 20 110 40
7412 20 111 55
7413 20 112 70
7414 32 118 80
7415 25 119 90
7416 25 120 75
7417 20 121 30
7418 20 122 45
7419 20 123 50
7420 22 124 25
7421 22 125 40
7422 22 126 40
7423 22 127 40
7424 22 128 40
7425 22 129 40
7426 22 130 40
7427 22 131 40
7428 22 132 40
7429 22 133 40
7430 22 134 40
7431 22 135 40
7432 22 136 40
7433 22 137 40
7434 22 138 40
7435 22 139 40
7436 22 140 40
7437 22 141 40
7438 22 142 40
7439 22 143 40
7440 22 144 40
7441 22 145 40
7442 22 146 40
7443 22 147 40
7444 22 148 40
7445 22 149 40
7446 22 150 40
7447 22 151 40
7448 22 152 40
7449 22 153 40
7450 22 154 40
7451 22 155 40
7452 22 156 40
7453 22 157 40
7454 22 158 40
7455 22 159 40
7456 22 160 40
7457 22 161 40
7458 22 162 40
7459 22 163 40
7460 22 164 40
7461 22 165 40
7462 22 166 40
7463 22 167 40
7464 22 168 40
7465 22 169 40
7466 22 170 40
7467 22 171 40
7468 22 172 40
7469 22 173 40
7470 22 174 40
7471 22 175 40
7472 22 176 40
7473 22 177 40
7474 22 178 40
7475 22 179 40
7476 22 180 40
7477 22 181 40
7478 22 182 40
7479 22 183 40
7480 22 184 40
7481 22 185 40
7482 22 186 40
7483 22 187 40
7484 22 188 40
7485 22 189 40
7486 22 190 40
7487 22 191 40
7488 22 192 40
7489 22 193 40

COPPER CLAD BOARDS
Fibre Single- Sided Double- SRBP
Glass sided sided 9.5" x 5"
6" x 6" 90p 110p 95p
6" x 12" 150p 200p

COMPUTER
90 28 74181 140 4028 58 4162 99
91 45 74182 75 4029 77 4163 99
92 30 74184 95 4030 50 4174 99
93 30 74185 99 4031 170 4179 99
94 30 74188 290 4032 125 4194 105
95 50 74190 70 4033 165 4408 790
96 45 74191 70 4034 195 4409 790
97 120 74193 65 4035 95 4410 725
98 100 74194 75 4036 275 4411 695
99 105 74195 65 4037 115 4412 800
00 74196 65 4038 110 4413 800
01 74197 65 4039 290 4419 280
02 74198 99 4040 59 4422 770
03 74199 99 4041 78 4433 770
04 74201 99 4042 60 4435 850
05 74202 99 4043 60 4440 999
06 74203 99 4044 65 4440 999
07 74204 150 4045 170 4451 350
08 74205 150 4046 75 4490 500
09 74206 150 4047 75 4500 675
10 74207 150 4048 55 4501 28
11 74208 150 4049 30 4502 90
12 74209 150 4050 30 4503 90
13 74210 150 4051 78 4504 105
14 74211 100 4052 78 4506 65
15 74212 55 4053 78 4508 265
16 74213 55 4054 125 4510 68
17 74214 55 4055 125 4511 68
18 74215 55 4056 125 4512 75
19 74216 55 4057 125 4513 99
20 74217 55 4058 125 4514 99
21 74218 55 4059 480 4515 198
22 74219 55 4060 90 4516 75
23 74220 55 4061 1225 4516 75
24 74221 55 4062 995 4517 415
25 74222 55 4063 38 4518 42
26 74223 55 4064 38 4519 42
27 74224 55 4065 38 4520 78
28 74225 55 4066 38 4521 78
29 74226 55 4067 38 4522 78
99 74296 55 4137 38 4592 78
00 74297 55 4138 38 4593 78

FERRIC CHLORIDE
1 lb 195p + 50p p&p

COMPUTER
90 28 74181 140 4028 58 4162 99
91 45 74182 75 4029 77 4163 99
92 30 74184 95 4030 50 4174 99
93 30 74185 99 4031 170 4179 99
94 30 74188 290 4032 125 4194 105
95 50 74190 70 4033 165 4408 790
96 45 74191 70 4034 195 4409 790
97 120 74193 65 4035 95 4410 725
98 100 74194 75 4036 275 4411 695
99 105 74195 65 4037 115 4412 800
00 74196 65 4038 110 4413 800
01 74197 65 4039 290 4419 280
02 74198 99 4040 59 4422 770
03 74199 99 4041 78 4433 770
04 74201 99 4042 60 4435 850
05 74202 99 4043 60 4440 999
06 74203 99 4044 65 4440 999
07 74204 150 4045 170 4451 350
08 74205 150 4046 75 4490 500
09 74206 150 4047 75 4500 675
10 74207 150 4048 55 4501 28
11 74208 150 4049 30 4502 90
12 74209 150 4050 30 4503 90
13 74210 150 4051 78 4504 105
14 74211 100 4052 78 4506 65
15 74212 55 4053 78 4508 265
16 74213 55 4054 125 4510 68
17 74214 55 4055 125 4511 68
18 74215 55 4056 125 4512 75
19 74216 55 4057 125 4513 99
20 74217 55 4058 125 4514 99
21 74218 55 4059 480 4515 198
22 74219 55 4060 90 4516 75
23 74220 55 4061 1225 4516 75
24 74221 55 4062 995 4517 415
25 74222 55 4063 38 4518 42
26 74223 55 4064 38 4519 42
27 74224 55 4065 38 4520 78
28 74225 55 4066 38 4521 78
29 74226 55 4067 38 4522 78
30 74227 55 4068 38 4523 78
31 74228 55 4069 38 4524 78
32 74229 55 4070 38 4525 78
33 74230 55 4071 38 4526 78
34 74231 55 4072 38 4527 78
35 74232 55 4073 38 4528 78
36 74233 55 4074 38 4529 78
37 74234 55 4075 38 4530 78
38 74235 55 4076 38 4531 78
39 74236 55 4077 38 4532 78
40 74237 55 4078 38 4533 78
41 74238 55 4079 38 4534 78
42 74239 55 4080 38 4535 78
43 74240 55 4081 38 4536 78
44 74241 55 4082 38 4537 78
45 74242 55 4083 38 4538 78
46 74243 55 4084 38 4539 78
47 74244 55 4085 38 4540 78
48 74245 55 4086 38 4541 78
49 74246 55 4087 38 4542 78
50 74247 55 4088 38 4543 78
51 74248 55 4089 38 4544 78
52 74249 55 4090 38 4545 78
53 74250 55 4091 38 4546 78
54 74251 55 4092 38 4547 78
55 74252 55 4093 38 4548 78
56 74253 55 4094 38 4549 78
57 74254 55 4095 38 4550 78
58 74255 55 4096 38 4551 78
59 74256 55 4097 38 4552 78
60 74257 55 4098 38 4553 78
61 74258 55 4099 38 4554 78
62 74259 55 4100 38 4555 78
63 74260 55 4101 38 4556 78
64 74261 55 4102 38 4557 78
65 74262 55 4103 38 4558 78
66 74263 55 4104 38 4559 78
67 74264 55 4105 38 4560 78
68 74265 55 4106 38 4561 78
69 74266 55 4107 38 4562 78
70 74267 55 4108 38 4563 78
71 74268 55 4109 38 4564 78
72 74269 55 4110 38 4565 78
73 74270 55 4111 38 4566 78
74 74271 55 4112 38 4567 78
75 74272 55 4113 38 4568 78
76 74273 55 4114 38 4569 78
77 74274 55 4115 38 4570 78
78 74275 55 4116 38 4571 78
79 74276 55 4117 38 4572 78
80 74277 55 4118 38 4573 78
81 74278 55 4119 38 4574 78
82 74279 55 4120 38 4575 78
83 74280 55 4121 38 4576 78
84 74281 55 4122 38 4577 78
85 74282 55 4123 38 4578 78
86 74283 55 4124 38 4579 78
87 74284 55 4125 38 4580 78
88 7428

H.A.C SHORT-WAVE KITS

WORLD-WIDE RECEPTION

CONSTRUCT YOUR OWN T-TWIN

TRANSISTOR RECEIVER

for use with headphones or small speaker.

Students - this receiver is ideal for your radio project. Simple to construct - sensitive selective.

£19.00

for the complete Kit.

All orders despatched within 7 days. Send stamped and addressed envelope now for free descriptive catalogue of kits and accessories.

SORRY, NO CATALOGUES WITHOUT S.A.E.

"H.A.C."
SHORT-WAVE PRODUCTS
P.O. Box No. 16, 10 Windmill Lane
Lewes Road, East Grinstead, West
Sussex RH19 3SZ.

HART KITS

WINTON TUNER

Complete designer approved kits (including pre-aligned AM front end) will be available from us for this excellent design. Phone or write for your free copy of lists.

WINTON AMPLIFIER

We have taken over the supply of kits for this high performance 'PW' design. Size and appearance match above tuner. Reprints of all articles describing design 85p VAT and post free.

VFL 910 VERTICAL FRONT LOADING CASSETTE DECK

Very high quality cassette mechanism as used in our Linsley Hood cassette recorder kit. Wow and flutter .09%. Memory counter. Sendust alloy head. 12V DC. Frequency generating feedback servo motor. Oil damped eject. £31.99 + VAT.

SF925 FRONT LOADING SOLENOID CONTROL CASSETTE DECK

Having full solenoid control of all functions this deck has numerous uses, most obvious is microcomputer drive, particularly since there is a facility to read the tape in the fast modes. Deck is full hi fi quality and is fitted with memory counter, Hall IC for auto stop and stereo R/P head. Price only £38.90 + VAT.

HART TRIPLE E PURPOSE TEST CASSETTE TC 1

Sets up tape speed, head azimuth and VU level all without test instruments. Fantastic value at only £2.70 + VAT.

CASSETTE HEADS

We hold large stocks of cassette heads ranging from mono to 4 track for domestic and industrial use including the fabulous HS16 sendust alloy super head at £8.20 + VAT. Remember your tape machine is only as good as its head. A worn head will lose the high frequency information on the tape and a very worn head will chew up the tape as well. Full technical spec of all heads is in our lists.

Write or phone for your copy of our free lists.

HART ELECTRONIC KITS LTD

Penylan Mill,
Oswestry, Shropshire SY10 9AF.
Tel: 0691 2894
Telex: 35661 HARTELG.

FAMOUS LOUDSPEAKERS

MAKE	model	size	watts	ohms	price
Seas	Tweeter	4in	50	8	£9.50
Goodmans	Tweeter	3½in	25	8	£4.00
Audax	Tweeter	4in	30	8	£6.50
Seas	Mid-Range	4in	50	8	£7.50
Seas	Mid-Range	5in	80	8	£12.00
Seas	Mid-Range	4½in	100	8	£12.50
Audax	Woofers	10in	50	8	£12.00
Audax	Woofers	8in	40	8	£14.00
Rigonda	Full-Range	10in	15	8	£5.00
Goodmans	Audio	12GP	60	8	£20.00
Goodmans	D12	12in	90	8/15	£27.50
Goodmans	Audio	12P	50	15	£20.00
EMI	450	13x8	10	3/8	£9.50
EMI	Bass	13x8	20	15	£12.50

BATTERY ELIMINATOR MAINS TO 9 VOLT DC

Stabilised output, 9 volt 400 m.a. UK made with terminals. Overload cut out. 5 x 3½ x 2½in. Transformer Rectifier Unit. Suitable Radios. Cassettes. £4.50.

BAKER LOUDSPEAKERS

Model	Ohms	Inch	Watts	Type	Price	Post
Major	4, 8, 16	12	30	Hi-Fi	£14	£2
Deluxe Mk II	8	12	15	Hi-Fi	£14	£2
Superb	8, 16	12	30	Hi-Fi	£24	£2
Auditorium	8, 16	12	45	Hi-Fi	£22	£2
Auditorium	8, 16	15	60	Hi-Fi	£34	£2
Group 45	4, 8, 16	12	45	PA	£14	£2
Group 75	4, 8, 16	12	75	PA	£22	£2
Group 100	8, 16	12	100	PA	£24	£2
Group 100	8, 16	15	100	PA	£32	£2
Disco 100	8, 16	12	100	Disco	£24	£2
Disco 100	8, 16	15	100	Disco	£34	£2

EMI MINI MODULE KIT 3-way

Loudspeaker System, EMI 5in Bass, 5in Middle, 3in Tweeter, with 3-way Crossover and Ready Cut Baffle. 15 x 8½in. Full assembly instructions. Response = 60 to 20,000 cps 12 watt RMS. 8 ohm. £10 ea. £18.50 pair. Postage £1.50.



R.C.S. LOUDSPEAKER BARGAINS

3 ohm, 4in, 5in, 6x4in, 7x4in, £1.50; 8x5in, 6½in, £3; 8in, £3.50. 8 ohm, 2in, 2½in, 3in, 5in, £1.50; 8in, £4.50; 10in, £5; 12in, £6. 15 ohm, 3½in, 5x3in, 6x4in, 7x4in, £1.50. 25 ohm, 3in, 5x3in, 7x4in, £1.50; 120 ohm, 3½in, dia, £1.50.

LOW VOLTAGE ELECTROLYTICS

1, 2, 4, 5, 8, 16, 25, 30, 50, 100, 200mF 15V 10p.
500mF 12V 15p; 25V 20p; 50V 30p;
1000mF 12V 20p; 25V 35p; 50V 50p; 1200mF/76V 80p.
2200mF 6V 25p; 25V 42p; 40V 60p; 2000mF/100V £1.20.
2500mF 50V 70p; 3000mF 25V 50p; 50V 65p.
3300mF 63V £1.20; 4700mF 63V £1.20; 2700mF/76V £1.
4700mF 40V 85p; 1000 mF 100V £1; 5600mF 76V £1.75.

HIGH VOLTAGE ELECTROLYTICS

8/450V 45p 8x8/450V 75p 50+50/300V 50p
16/350V 45p 8x16/450V 75p 32+32+32/25V 75p
32/350V 75p 20x20/450V 75p 100+100/275V 65p
50/350V 80p 32x32/350V 50p 150+200/275V 70p
50/500V £1.20 32x32/500V £1.80 220/450V 95p

MANY OTHER ELECTROLYTICS IN STOCK

TRIMMERS 10pF, 30pF, 50pF, 5p, 100pF, 150pF, 15p.
CONDENSERS VARIOUS, 1pF to 0.01mF, 3p.
PAPER 350V 0.1 7p; 0.5 13p; 1mF 150V 20p; 2mF 150V 20p
400V-0.001 to 0.05 5p; 0.1 15p; 0.25 25p; 0.47 35p.
MICRO SWITCH SINGLE POLE CHANGEOVER 30p.
SUB-MIN MICRO SWITCH, 30p. Single pole change over.
TWIN GANGS 120pF 50p; 500pF £1.
GEARED TWIN GANGS 25pF 95p; 365pF £1;
365 - 365 - 25 - 25pF £1. Single Gang 500pF £1.50.
NEON PANEL INDICATORS 250V. Red 1½ x ¼ 45p.
ILLUMINATED ROCKER SWITCH. Single pole. Red 65p.
RESISTORS. 100 to 10M, ¼W, 1W, 20% 2p; 2W, 10p.
HIGH STABILITY. ¼W 2% 10 ohms to 1 meg. 5p.
Ditto 5%. Preferred values 10 ohms to 10 meg. 3p.
WIRE-WOUND RESISTORS 5 watt, 10 watt, 15 watt 20p.
CASSETTE MOTOR, 6 volt £1.00.
CASSETTE MECHANISM, 6v or 12v Stereo Head £5.
BLANK ALUMINIUM CHASSIS. 6 x 4-£1.45; 8 x 6-£1.80
10 x 7-£2.30; 12 x 8-£2.60; 14 x 9-£3.00; 16 x 6-£2.90;
16 x 10-£3.20. All 2½in. deeps 18 swg
ANGLE ALI. 6 x ½ x ¾in. 18 swg. 25p.
ALUMINIUM PANELS, -18 swg. 6 x 4-45p; 8 x 6-75p;
14 x 3-75p; 10 x 7-95p; 12 x 8-£1.10; 12 x 5-75p;
16 x 6-£1.10; 14 x 9-£1.45; 12 x 12-£1.50; 16 x 10-£1.75.
BLACK PLASTIC construction box with brushed aluminium
facia size 6½ x 4½ x 2" £1.50. Many other sizes.
BRIDGE RECTIFIER 200V PIV ¼ amp 50p. 2 amp £1.00.
4 amp £1.50. 8 amp £2.50. DIODES 1a, 10p; 3a, 30p.
TOGGLE SWITCHES SP 30p, DPST 40p, DPDT 50p.
MINIATURE TOGGLES SP, 40p; DPDT, 60p.

BSR 172 BUDGET SINGLE PLAYER ideal for disco or small three-speed Hi-Fi system with stereo cartridge cueing device and bias compensator. Post £2 £20

BSR STEREO CARTRIDGES SC7 £2; SC12 £3.
Sonotone 9TA-£2.50; 9TA-HC £3.50; V.100 Magnetic £7.

MAINS TRANSFORMERS

5-8-10-16V. ½ amp £2.50 80p 17-0-17V 2 amps £4.50 £2
6V ½ amp £2.00 £1 18V 6a Twice £11.00 £1
6-0-6V 1½ amps £3.50 £1 20V 1 amp £3.00 £1
9V 250mVA 1 amp £1.50 80p 20-0-20V 1 amp £3.50 £1
9V 3 amp £3.50 £1 20/40/60V 1 amp £4.00 £2
9-0-9V 50ma £1.50 80p 25-0-25V 2 amps £4.50 £1
10-0-10V 2 amps £3.00 £1 28V 1 amp twice £5.00 £1
10-30-40V 2 amps £3.50 £1 30V 1½ amp £3.50 £1
12V 100ma £2.00 80p 30V 5 amp and £4.50 £2
12V 3 amps £3.50 £1 17-0-17V 2a £4.00 £1
15-0-15V 2 amps £3.75 £1

Radio Component Specialists
337, WHITEHORSE ROAD
CROYDON, SURREY, U.K. TEL: 01-684 1665
Post 65p Minimum. Callers Welcome. Closed Wed.
Same day despatch. Access-Barclay-Visa. Lists 25p

INDEX TO ADVERTISERS

A.H. Supplies	15	Lowe Electronics	3 & 2
A.J.H. Electronics	10	M & B Radio	68
Aero & General	86	M. H. Electronics	92
Allweld Engineering	78	Maplin Electronic Supplies	Cover IV
Amateur Electronics	85	Marco Trading	38
Amateur Radio Exchange	46	Microwave Modules	28
Ambit International	12	Modular Electronics	84
Amcomm Services	67	Monolith Electronics	
Anglia Components	92	Munro, W.	89
Antex Electronics	Cover III	Myers Electronics	68
Auto Marine Development Company	74	Neosid	8
Bi-Pak	10 & 11	Northern Communications	78
Birkett, J.	96	O'Neil, D.	
Black Star	13	P.C. Electronics	90
Bowes, C.	92	P.M. Components Ltd.	14
Bredhurst Electronics	Cover II	P.R. Gollidge Electronics	90
British National Radio & Electronics School	13 & 86	Packer Communications	77
Brookes	86	Partridge	63
Bull, J.	15	Photo Acoustics Ltd.	38
C.H.J.	96	Powell, T.	14
C.Q. Centre	77	Progressive Radio	92
C.R. Supply	90	R.S.T. Valve Mail Order	86
Cambridge Kits	92	Radio Component Specialists	95
C. Carana	91	Radio Shack	68
Catronics	27	Radio Society of Great Britain	93
Chordgate	89	Sandwell Plant Ltd.	92
Colomur Electronics Ltd	10	S.E.M.	84
Datong	74	Sinclair Research Ltd.	82, 83
E.D.A.	87	Sota	27
Electrovalve	15	South Midlands Communications Ltd.	16, 17
Electronic Mail Order Ltd.	14	Stephens-James Ltd.	78
G.T. Technical Information Service	91	Tandy Corporation (UK) Ltd.	9
Garex Electronics	63	Technomatic Ltd.	96
Gemini Communications	63	Telecom	8
Greens Telecom	8	Tempus	84
G2 Dym Aerials & Projects	90	Thanet Electronics	4, 5, 27
H.A.C. Shortwave	95	The Scientific Wire Co.	92
Hart Electronics	95	Titan Transformers	8, 93
Heathkit	13	Waters & Stanton	6, 7
Henry's Radio	14	Watford Electronics	94
I.C.S. Intertext	89, 92	Webb, R.M.	93
I.L.P.	74	Williams A.R. (Security Aids)	12
Intel	12	Wilmslow Audio	89
Lee Electronics	81	Wood & Douglas	77
Leeds Amateur Radio	18	The Vintage Wireless Co.	90
Lexton, Harvey	73	Zycomm Electronics	37
London Electronics College	91		

TTLs		74390 100p	74393 100p	LINEAR I.C.s		ML920 800p	8C187 30p	BFY51/2 30p	TIP31C 62p	2N2222A 30p	2N6059 325p	BRIDGE RECTIFIERS	
7400	11p			AN103	200p	MM57160 820p	BC212/3 11p	BFV56 33p	TIP32A 68p	2N2362A 30p	2N6107 65p	1A 50V 19p	
7402	12p			AY1-0212	600p	NE531 250p	BC217 12p	BFY90 80p	TIP33C 62p	2N2484 30p	2N6247 190p	1A 100V 20p	
7404	12p	4000 CMOS		AY1-1313	688p	NE555 20p	BC237 15p	BRY39 45p	TIP33A 90p	2N2646 45p	2N6254 130p	1A 400V 25p	
7405	18p	4000 15p		AY1-1320	320p	NE558 50p	BC327 16p	BSX19/20 24p	TIP33C 114p	2N2904/5 30p	2N6290 65p	1A 600V 30p	
7406	25p	4001 18p		AY1-5050	140p	NE570 425p	BC338 16p	BU105 190p	TIP34A 115p	2N2906A 30p	2SC1172 150p	2A 100V 35p	
7407	25p	4006 65p		AY3-8910	700p	NE564 420p	BC461 18p	BU108 250p	TIP34C 160p	2N2907A 30p	2SC1306 150p	2A 400V 45p	
7408	14p	4007 18p		AY3-8912	650p	NE565 130p	BC47/7B 30p	BU109 225p	TIP35A 225p	2N3053 40p	2SC1957 90p	3A 200V 60p	
7410	15p	4010 40p		AY5-1224A	240p	NE566 165p	BC516/7 40p	BU126 150p	TIP36A 270p	2N3054 65p	2SC1969 195p	3A 600V 72p	
7411	20p	4011 16p		AY5-1315	600p	NE567 140p	BC547B 16p	BU180A 120p	TIP36C 340p	2N3055 48p	2SC2028 120p	4A 100V 95p	
7413	25p	4012 20p		AY5-4007D	520p	NE571 425p	BC548C 9p	BU205 200p	TIP41A 65p	2N3442 140p	2SC2029 250p	4A 400V 100p	
7414	35p	4013 35p		CA3028A	120p	NE574 250p	BC549C 18p	BU208 200p	TIP41C 78p	2N3553 240p	2SC2078 200p	6A 50V 80p	
7416	25p	4016 30p		CA3019	80p	NE5534A 250p	BC578 18p	BU406 145p	TIP42 70p	2N3584 250p	3N128 120p	6A 100V 100p	
7417	25p	4017 50p		CA3046	72p	500p	BC599C 18p	BUY69C 350p	TIP42C 82p	2N3643/4 48p	3N140 120p	6A 400V 120p	
7420	17p	4020 60p		CA3048	225p	RC4136 70p	BCY70 18p	BUY80 350p	TIP54 160p	2N3702/3 12p	3N141 110p	10A 400V 200p	
7421	30p	4022 70p		CA3059	300p	RC4151 200p	BCY71/2 22p	MJ2501 225p	TIP120 130p	2N3706/7 14p	3N204 120p	25A 400V 400p	
7425	28p	4023 24p		CA3080E	72p	SD135/6 64p	BD139 58p	MJ265 90p	TIP122 120p	2N3773 300p	4036/2 75p	ZENERs	
7427	25p	4024 40p		CA3086	48p	S5668 260p	BD140 60p	MJ3001 225p	TIP122 120p	2N3819 250p	4038/2 75p	2.7V-33V 400mW 9p	
7430	15p	4025 20p		CA3089E	225p	SFF96364 800p	BD189 60p	MJE340 60p	TIP122 120p	2N3819 250p	4040/8 90p	1W 15p	
7432	25p	4026 130p		CA3090A	375p	SL490 350p	BD232 95p	MJE2955 100p	TIP4055 70p	2N3820 50p	4040/9 100p	TRIACS	
7437	27p	4027 32p		CA3130E	90p	SN76477 175p	BD233 75p	MJE3055 70p	TIS93 30p	2N3823 70p	4041/10 300p	3A 400V 60p	
7441	70p	4029 75p		CA3140E	50p	SP8515 750p	BD241 70p	MPF102 45p	ZTX108 12p	2N3866 90p	4041/11 300p	6A 400V 75p	
7442A	36p	4030 40p		CA3160E	100p	TA7205 250p	BD242 70p	MPF105 40p	ZTX100 15p	2N3902 700p	4059/4 120p	6A 500V 88p	
7445	60p	4032 125p		CA3161E	140p	TA7206 250p	BD247 70p	MPF105 40p	ZTX1502 18p	2N3905/6 20p	4067/3 75p	8A 400V 95p	
7447A	45p	4034 160p		CA3162E	450p	TA7222 200p	BD4672 40p	MPSA12 30p	ZTX504 30p	2N4037 65p	4087/2 100p	8A 500V 75p	
7448	45p	4040 60p		CA3189E	300p	TA7310 200p	BF2448 35p	MPSA13 50p	VN46AP 75p	2N4123/4 27p		8A 400V 95p	
7454	17p	4042 55p		CA3240E	120p	TA7310 200p	BF2568 70p	MPSA20 50p	VN66 80p	2N4125/6 27p		12A 400V 85p	
7472	30p	4043 60p		CA3280G	200p	TAA621 275p	BF2578 35p	MPF102 45p	VN10KM 30p	2N4421 30p		16A 400V 110p	
7473	30p	4046 80p		DAC1408-8	200p	TBA641BX1 300p	BF259 36p	MPSA43 50p	2N689 25p	2N4871 60p		16A 500V 130p	
7474	20p	4047 75p		HA1388	270p	TBA801 90p	BF329 36p	MPSA56 32p	2N698 45p	2N5087 27p	OA47 8p	12A 500V 100p	
7475	38p	4049 80p		ICL7106	850p	TBA810 100p	BF339 36p	MPSA70 50p	2N708 30p	2N5089 27p	OA90/91 9p	16A 500V 130p	
7476	30p	4050 30p		ICL8038	300p	TBA820 100p	BF340 35p	MPSU07 30p	2N918 45p	2N5172 27p	OA95 9p	3A 400V 100p	
7483A	45p	4051 60p		ICM87555	80p	TBA950 300p	BF345 40p	MPSU07 30p	2N930 30p	2N5194 90p	OA202 10p	8A 600V 140p	
7485	90p	4052 80p		IC7120	400p	TCA9109 110p	BF384/5 40p	TIP29A 40p	2N1613 25p	2N5245 40p	IN914 4p	16A 100V 180p	
7486	22p	4053 60p		IC7130	400p	TCA9210 350p	BF386 30p	TIP29C 55p	2N1711 25p	2N5298 65p	IN916 7p	16A 400V 110p	
7490A	25p	4059 500p		LF347	180p	TCA9220 350p	BF389 180p	TIP30A 48p	2N2102 70p	2N5401 60p	IN4148 4p	16A 400V 180p	
7492A	30p	4060 90p		LF351 48p	48p	TCA940 175p	BF450 30p	TIP30C 60p	2N2160 350p	2N5457/8 40p	IN4A003/4 6p	BT106 110p	
7493A	30p	4066 35p		LF353 100p	100p	TOA1004A 300p		TIP31A 55p	2N2219A 30p	2N5460 60p	IN4A005 7p	C106D 45p	
7495A	50p	4067 400p		LF356P 95p	95p	TOA1008 320p				2N5485 44p	IN4A006/7 6p	MCR101 36p	
7496	45p	4068 18p		LF357 120p	120p	TOA1010 320p				2N5875 250p	IN5401/3 14p	SPD2 24V 2A 70p	
74100	85p	4069 20p		LM10C 425p	425p	TD1022 600p				2N6027 48p	IN5404/7 19p	2N3525 130p	
74107	27p	4070 20p		LM301A 75p	75p	TD1024 120p				2N6052 300p	IS920 9p	2N4444 130p	
74121	30p	4071 20p		LM311 27p	27p	TD1034B 250p						2N5060 34p	
74122	45p	4076 60p		LM318 200p	200p	TD1170 300p						2N5064 40p	
74123	48p	4077 40p		LM319 225p	225p	TD2A002V 325p							
74125	40p	4078 20p		LM324 45p	45p	TD2A020 320p							
74126	40p	4081 20p		LM3352 140p	140p	TL071/81 45p							
74128	40p	4093 40p		LM339 65p	65p	TL072/82 75p							
74132	45p	4098 90p		LM348 75p	75p	TL074 130p							
74136	32p	4099 90p		LM358P 75p	75p	TL084 110p							
74141	65p	4503 50p		LM377 175p	175p	TL094 200p							
74145	70p	4507 40p		LM380 75p	75p	TL170 60p							
74147	100p	4510 65p		LM381AN 180p	180p	TL430C 70p							
74148	75p	4511 50p		LM382 120p	120p	UAA170 170p							
74150	80p	4518 50p		LM386 95p	95p	UA2240 300p							
74151A	45p	4520 70p		LM387 120p	120p	UDN6118 320p							
74153	45p	4528 75p		LM389 95p	95p	UDN6184 320p							
74154	70p	4534 500p		LM393 100p	100p	ULN2003 100p							
74157	50p	4543 100p		LM394 300p	300p	UPC575 400p							
74159	100p	4553 290p		LM709 36p	36p	UPC592H 200p							
74160	60p	4560 180p		LM710 350p	350p	UPC1558H 300p							
74161	60p	4572 30p		LM725 100p	100p	XR2206 300p							
74162	60p	4584 50p		LM733 100p	100p	XR2207 400p							
74163	60p			LM741 18p	18p	XR2211 600p							
74164	65p			LM747 70p	70p	XR2215 675p							
74165	60p			LM748 35p	35p	ZN414 70p							
74166	70p			LM7917 200p	200p	ZN419C 225p							
74170	160p			LM3302 140p	140p	ZN423E 150p							
74172	300p			LM3900 65p	65p	ZN424E 135p							
74174	70p			LM3909 95p	95p	ZN425E 360p							
74175	70p			LM3911 130p	130p	ZN427E 625p							
74190	70p			LM3914 210p	210p	ZN1034E 200p							
74191	70p			LM3915 225p	225p								
74192	70p			LM3916 225p	225p								
74193	70p			LM13800 125p	125p								
74196	60p			M51513L 300p	300p								
74197	60p			M51516L 500p	500p								
74221	75p			MB3712 250p	250p								
74283	75p			MC1310P 150p	150p								
74284	200p			MC1458 40p	40p								
74285	200p			MC1495L 350p	350p								
74365	55p			MC1496 70p	70p								
74366	55p			MC3340P 120p	120p								
74367	55p			MC3403 120p	120p								
74368	55p			MK50398 750p	750p								

COMPONENTS AT REALISTIC PRICES

A random selection from our large range. Lists Enclosed with First Order.

ELECTROLYTICS Rad. Lead. (Voltages stocked to 350V)
 1.0/50 5p, 2.2/40 5p, 4.7/35 5p, 10/50 6p, 22/16 6p, 47/10 6p, 100/40 9p, 220/10 7p, 470/40 15p, 1000/10 12p, 1000/63 Tag end can. 50p.

POLYSTYRENE CAPACITORS (Axial Lead)
 15p/125, 47/125, 68/30, 100/25, 150/63, 220/160, 470/25, 680/125 etc. etc. 3p each

RED COATED RADIAL POLYSTYRENES
 180p/63, 330/63, 560/63, 680/63 4p each

MINIATURE 500V CERAMIC DISCS "p" (50V & 250V Discs also stocked)
 2 2pf, 10pf, 47pf, 100pf, 220pf, 470pf, 680pf, 1000pf etc. etc. 4p each

SILVER MICA
 5.6p/350, 27/350, 47/120, 150/63 8p, 220/750, 270/350 10p, 470/250 15p, 4700/500 25p.

HIGH VOLTAGE DISCS
 27p/2KV 6p, 100/3.5KV 10p, 150/4KV 11p, 470/3KV 14p, 500/16KV 25p, 1000/1KV 6p, 4700/4KV 15p, 01/1KV 8p, 01/3KV 12p, etc. etc.

CAPACITORS 50V to 10KV
 Miniature Polypropylene 6p, Polyester 4p, Polycarbonate 10p.

TANTALUM BEAD CAPS
 .1/35, 2/2/35, 33/35, 47/35, 68/35, 1/35 10p, 2.2/16, 3.3/16, 4.7/16 12p, 4.7/35, 6.8/25 14p, 6.8/35 15p, 10/16, 22/63 18p, 22/10 20p, 22/16 25p, 33/10, 47/6 25p, 47/16 40p, 100/16 65p. (Also other values on lists).

MISCELLANEOUS
 5 pin DIN chassis skts. 180° 10p, 1uF/220V Mains Filter IIT 40p, 15KV Potted Silicon Diode Similar BY176/BY476 55p, 100K Stan. HOR P/SET 5p etc.

FLAMEPROOF CERAMIC WIRE WOUND RESISTORS
 4.7 ohm 7w 12p, 120 ohm 3w 8p etc.</

YOU'RE LOOKING AT 31 ANTEX SOLDERING IRONS!

The secret is in the range of bits for each model, from 19mm down to 0.5mm! No screws to seize up — push-on bits which cover the elements to save time and energy.

The new range of Antex irons come with or without safety plugs fitted. They are tougher than ever, and about twice as efficient as conventional designs.

Specify low wattage, low leakage Antex Irons now.



Our products are widely distributed by wholesalers and retailers throughout the UK. Please try your local dealer. Please send literature and price list to:

Made in England


ANTEX (Electronics) Ltd.
Mayflower House, Plymouth, Devon.
Tel: (0752) 667377/8 Telex: 45296

Name Address

..... Telephone

PW/2/82

MAPLIN make it easy...

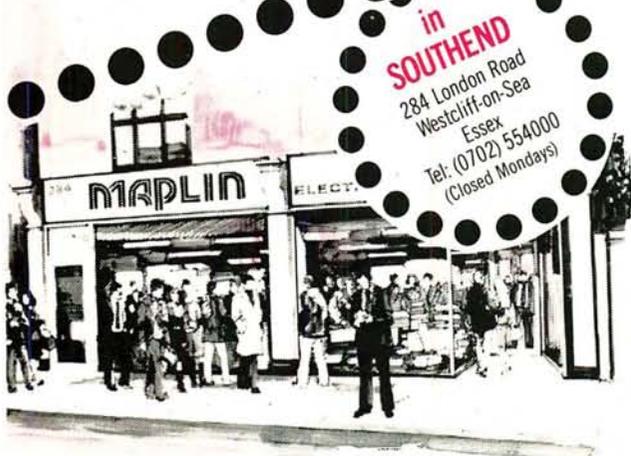

in
SOUTHEND
284 London Road
Westcliff-on-Sea
Essex
Tel: (0702) 554000
(Closed Mondays)



in
HAMMERSMITH
159-161 King Street
Hammersmith
London W6
Tel: 01-748 0926
(Closed Mondays)

For personal service visit one of our stores.
Our new store at Hammersmith is conveniently situated near the end of the M4 and the North and South Circular Roads. There is excellent street parking on meters a few steps away and Hammersmith Underground Station is nearby. Call in and see us soon.



in our
CATALOGUE

320 big pages packed with data and pictures of over 5,500 items

Over 100,000 copies sold already!
Don't miss out on your copy.

On sale now in all branches
WH Smith price £1.

In case of difficulty check the coupon below.

by
MAIL ORDER
A fast service
You can rely on

- * Same day service on in-stock lines
- * Very large percentage of our stock lines in stock
- * All prices include VAT
- * Large range of all the most useful components
- * First class reply paid envelope with every order
- * Quality components—no rejects—no re-marks
- * Competitive prices
- * Your money is safe with a reputable company

On price, service, stock, quality and security it makes sense now more than ever to make **MAPLIN** your first choice for components every time!

make it easy... with MAPLIN

The
Maplin Matinée
Amazing value for
only £299.95 plus £99.50
for cabinet if required
(Carriage Extra)

Easy to build....
selling for up to £1,000.
Send for our new book giving
full construction details. Order as XH55K.
Price £2.50 inclusive.



Post this coupon now.

Please send me a copy of your 320 page catalogue. I enclose £1.25 (incl. 25p p&p). If I am not completely satisfied I may return the catalogue to you and have my money refunded. If you live outside the U.K. send £1.68 or 12 International Reply Coupons.

Name _____
Address _____

PW/2/82

MAPLIN ELECTRONIC SUPPLIES LTD.

All mail to: P.O. Box 3, Rayleigh, Essex SS6 8LR. Tel: Southend (0702) 554155 Sales: (0702) 552911