

JULY 1984

Australia \$1.80, New Zealand \$2.20, Malaysia \$5.50

£1.00

TELEVISION

SERVICING·PROJECTS·VIDEO·DEVELOPMENTS

BERNARD
\$1.80
RELY STY

The Ferguson TX100 Chassis



Also:

**Video Recording on Tape
Spectrum-Monitor Interface
Servicing: Grundig 2 × 4 Super
Electronic Circuit Breaker
VCR Clinic ● TV Fault Finding**

N J ELECTRONICS

82 - 84 STORFORTH LANE TRADING ESTATE
HASLAND
CHESTERFIELD
S41 0SN

TEL. (0246) 209079

INTEGRATED CIRCUITS

BTT 822	1.90	TBA 120B	0.78
CA 3089	1.20	TBA 120C	0.75
ETT 6016	1.95	TBA 120SA	0.75
ETTR 6016	1.95	TBA 120U	0.75
MC 1307P	1.70	TBA 231	1.65
MC 1310P	1.20	TBA 396	1.70
MC 1327P	1.10	TBA 395	1.70
MC 1330P	1.50	TBA 480	0.99
MC 1349P	1.10	TBA 510	1.20
MC 1351P	1.20	TBA 520	1.50
MC 1352P	1.50	TBA 530	1.45
MC 1358P	1.20	TBA 540	1.70
ML 236E	3.00	TBA 550	1.80
ML 237B	1.80	TBA 560C	1.90
SAA 1021	3.80	TBA 570	1.10
SAA 1024	2.40	TBA 750	1.50
SAA 1025	4.40	TBA 800	1.10
SAA 1124	2.40	TBA 810S	0.90
SAA 1130	4.30	TBA 820	1.20
SAA 5040	7.50	TBA 890	3.50
SAS 560	1.80	TBA 920	2.00
SAS 570	1.80	TBA 950	2.65
SAS 660	2.30	TBA 990	1.60
SAS 670	2.30	TBA 1440	2.70
SL 901B	5.00	TCA 270S	1.90
SL 917B	6.20	TCA 270SQ	1.90
SN 29848	2.25	TCA 640	2.60
SN 57108AN	1.95	TCA 650	2.40
SN 76001AN	1.60	TCA 660	2.80
SN 76003	2.20	TCA 740	2.90
SN 76013N	2.50	TCA 800	2.00
SN 76023N	2.20	TCA 830S	1.60
SN 76131N	1.35	TCA 940	1.80
SN 76226DN	1.60	TCA 4500A	2.00
SN 76227N	1.20	TDA 1003	2.40
SN 76532	2.00	TDA 1004A	2.00
SN 76550	0.29	TDA 1044	2.50
SN 76546	1.80	TDA 1170	2.80
SN 76660	0.90	TDA 1180	2.80
SN 76666N	1.10	TDA 1190	2.00
SN 76707	1.70	TDA 1327	1.70
TA 7061AP	3.60	TDA 1412	1.00
TA 7063AP	3.50	TDA 2010	1.80
TA 7066P	3.90	TDA 2522	2.40
TA 7072P	2.90	TDA 2523	2.20
TA 7074P	3.30	TDA 2530	2.20
TA 7108P	2.44	TDA 2532	2.70
TA 7117P	3.20	TDA 2540	2.20
TA 7120P	1.61	TDA 1365	5.75
TA 7129AP	3.20	TDA 2541	2.30
TA 7130P	1.38	TDA 2560	2.05
TA 7137P	2.00	TDA 2571	2.10
TA 7139P	2.75	TDA 2581	2.80
TA 7146P	2.00	TDA 2582	2.60
TA 7157P	3.20	TDA 2593	2.70
TA 7171P	3.20	TDA 2600	5.95
TA 7172P	3.30	TDA 2600	5.95
TA 7176AP	3.00	TDA 2611A	1.15
TA 7193P	5.20	TDA 2640	1.80
TA 7202P	3.30	TDA 2653	2.10
TA 7203P	3.30	TDA 2680	2.10
TA 7204P	2.16	TDA 2690	2.20
TA 7205P	1.40	TDA 2690	2.20
TA 7208P	2.70	TDA 3560	5.10
TA 7210P	5.60	TDA 3561	6.50
TA 7222P	1.70	TDA 3562	6.50
TA 7223P	3.50	TDA 3950	2.40
TA 7227P	5.10	TDA 4600	2.65
TA 7310P	1.70	UPC 41C	3.50
TA 7313P	2.80	UPC 393C	1.90
TA 7609P	4.00	UPC 554C	2.30
TA 7611AP	2.90	UPC 555H	0.80
TA 75902P	2.03	UPC 556H3	1.70
TAA 320A	1.30	UPC 557H	0.92
TAA 470	2.30	UPC 566H3	3.50
TAA 550	0.39	UPC 574J	0.55
TAA 691	1.95	UPC 575C2	3.00
TAA 700	1.65	UPC 577H	3.50
TBA 120A	0.75	UPC 585C	1.49
TBA 120AS	0.75	UPC 741G	0.95
		UPC 1009H	2.41
		UPC 1017G	2.50
		UPC 1018C	1.19
		UPC 1023H	0.63

UPC 1024H 0.63

UPC 1025H	3.70
UPC 1026C	1.60
UPC 1028H	2.40
UPC 1031H2	2.40
UPC 1032H	1.50
UPC 1035C	2.50
UPC 1037H	1.62
UPC 1042C	2.60
UPC 1043C	2.60
UPC 1156H	2.40
UPC 1158H	0.78
UPC 1161C3	1.58
UPC 1163H	0.98
UPC 1167C2	1.58
UPC 1168C	2.75
UPC 1170C	1.75
UPC 1171C	1.62
UPC 1176C	2.43
UPC 1177H	2.60
UPC 1178C	2.14
UPC 1180C	3.00
UPC 1181H3	1.62
UPC 1182H	2.70
UPC 1183H	2.30
UPC 1185H2	3.50
UPC 1186H	0.98
UPC 1187V	1.70
UPC 1188H	3.60
UPC 1190C	2.00
UPC 1191V	1.70
UPC 1197C	1.70
UPC 1198H	1.41
UPC 1200V	1.97
UPC 1204C	1.63
UPC 1208C	2.00
UPC 1211C	4.00
UPC 1212C	1.34
UPC 1213C	1.53
UPC 1215V	2.70
UPC 1216V	1.99
UPC 1217G	3.59
UPC 1218H	3.00
UPC 1222	2.00
UPC 1223	3.70
UPC 1225	3.00
UPC 1226	2.49
UPC 1227	2.00
UPC 1228H	0.90
UPC 1230H	3.60
UPC 1238V	1.90
UPC 1245	2.20
UPC 1250	2.40
UPC 1350C	4.50
UPC 1353C	2.80
UPC 1356C2	3.00
UPC 1358H	3.00
UPC 1360C	3.50
UPC 1363C	3.50
UPC 1366C	3.00
UPC 1367C	3.00
UPC 1368H	4.00
UPC 1370C2	4.00
UPC 1373H	1.11
UPC 1377C	4.50
UPC 1378H	4.00
UPC 1382C	1.97
UPC 1384C	5.70
UPC 1447W	0.98
UPC 1470H	0.90
UPC 2002V	2.80

DIODES

BA148	0.18
BA159	0.10
BB103	0.20
BB105B	0.20
BY127	0.11
BY133	0.11
BY176	1.35
BY184	0.40
BY187	0.69
BY190	0.60
BY210-800	0.29
BY223	0.95
BY226	0.27
BY227	0.31
BY295	0.25
BY296	0.25
BY298	0.25
BY299	0.25
BYX10	0.21
BYX36-600	0.50
BYX71-350	0.50
BYX71-600	0.99
BYX55-600	0.33
BR100	0.35
OA47	0.10
OA90	0.08
OA91	0.08
SKESF	1.40
IN60	0.08
IN4001	0.05
IN4002	0.05
IN4003	0.05
IN4004	0.06
IN4005	0.07
IN4006	0.07
IN4007	0.07
IN4148	0.03
IN5402	0.13
IN5404	0.15
IN5406	0.17
IN5408	0.18
Y969	0.87

BRIDGE RECT.

B40	0.80
BY164	0.50
BY179	0.70
W005	0.25

TRANSISTORS

AC127	0.30
AC128	0.30
AC153K	0.30
AC176	0.36
AC186	0.30
AC187	0.30
AC188	0.30
AD149	0.88
AD161	0.45
AD162	0.45
AF139	0.48
AF239	0.60
AU113	3.40
BC107	0.15
BC108	0.15
BC109	0.15
BC116	0.13
BC140	0.30
BC141	0.30
BC142	0.22
BC143	0.27
BC147	0.12
BC148	0.12
BC149	0.12
BC154	0.11
BC157	0.11
BC158	0.11
BC159	0.11
BC170	0.13
BC171	0.12

BC172	0.13
BC173	0.12
BC174	0.12
BC182L	0.12
BC183L	0.12
BC184L	0.12
BC207	0.12
BC212L	0.09
BC213L	0.11
BC237	0.10
BC238	0.12
BC250	0.11
BC251	0.11
BC252	0.12
BC253	0.11
BC301	0.31
BC302	0.31
BC303	0.33
BC307	0.13
BC308	0.13
BC327	0.11
BC328	0.13
BC337	0.11
BC338	0.13
BC350	0.12
BC365	0.30
BC413	0.11
BC460	0.48
BC461	0.52
BC462	0.53
BC463	0.53
BC527	0.13
BC528	0.13
BC546	0.12
BC547	0.12
BC548	0.12
BC557	0.12
BC558	0.12
BD131	0.30
BD132	0.36
BD135	0.30
BD136	0.30
BD139	0.33
BD140	0.60
BD150A	0.70
BD207	0.90
BD221	0.40
BD228	0.35
BD233	0.53
BD234	0.38
BD238	0.38
BD239	0.42
BD253B	0.65
BD416	0.42
BD534	0.33
BD595	0.55
BD596	0.55
BD681	0.58
BD807	0.50
BDX32	1.70
BF127	0.30
BF137	0.30
BF180	0.29
BF181	0.27
BF182	0.28
BF185	0.32
BF194	0.12
BF195	0.11
BF196	0.13
BF197	0.16
BF198	0.16
BF199	0.18
BF200	0.34
BF240	0.16
BF245	0.30
BF256L	0.40
BF258	0.27
BF259	0.32
BF264	0.40
BF273	0.11
BF274	0.11
BF337	0.32
BF338	0.32
BF355	0.56
BF458	0.48
BF459	0.51
BF479	0.26
BF50	0.24
BF51	0.23
BF52	0.23
BU105	1.60
BU108	0.98
BU124	1.60
BU126	1.60
BU137	1.40
BU204	1.40
BU205	1.40
BU208	1.55
BU208A	1.90
BU208D	2.30
BU326	1.80

BU407	1.40
BU426V	1.70
BU526	1.62
E1222	0.35
FT3055	0.65
MJE340	0.50
MJE520	0.45
R2008B	1.70
R2009	1.90
R2010B	1.90
R2540	2.10
SP8385	2.10
TIP29	0.38
TIP30A	0.34
TIP31A	0.34
TIP31C	0.48
TIP32A	0.34
TIP32C	0.48
TIP33B	0.75
TIP41A	0.46
TIP41C	0.58
TIP42A	0.45
TIP42C	0.68
TIP2955	0.74
TIP3055	0.55
2N3055	0.73

ZENERS

400MW	0.10
1.3W	0.18

THYRISTORS

15/80	2.50
15/85	2.50
BR101	0.40
BR103	0.62
BR139	0.56
BR149	0.65
BR155	0.60
BT100	1.10
BT106	1.55
OT112	1.85
OT121	1.55
2N4444	1.55

REGULATORS

78 Series	0.60
79 Series	0.80
78L Series	0.42
79L Series	0.70

FUSES


20mm Anti Surge	(10 pack) 1.20
1 1/2" Anti Surge	(10 pack) 2.30
20mm Q Blow	0.50
1 1/2" Q Blow	0.70
Most Values	Stocked

CAPACITORS

.1 1000V	0.40
.1 1250V	0.48
.22 1000V	0.50
.22 1250V	0.60
.47 1000V	0.70
Also stocked:	
Tants, Discs,	
Polys, Plates,	
Electrolytics.	
Please ring for	
details.	

SWITCHES

G8 Plastic	0.85
G8	

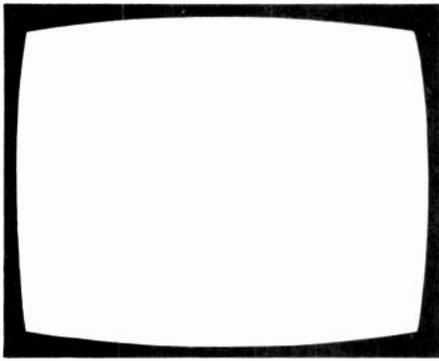

TELEVISION

July
1984

Vol. 34, No. 9
Issue 405

COPYRIGHT

©IPC Magazines Limited, 1984. Copyright in all drawings, photographs and articles published in *Television* is fully protected and reproduction or imitation in whole or in part is expressly forbidden. All reasonable precautions are taken by *Television* to ensure that the advice and data given to readers are reliable. We cannot however guarantee it and we cannot accept legal responsibility for it. Prices are those current as we go to press.

CORRESPONDENCE

All correspondence regarding advertisements should be addressed to the Advertisement Manager, "Television", King's Reach Tower, Stamford Street, London SE1 9LS. Editorial correspondence should be addressed to "Television", IPC Magazines Ltd., King's Reach Tower, Stamford Street, London SE1 9LS.

SUBSCRIPTIONS

An annual subscription costs £11 in the UK, £12 overseas (by surface mail). Send orders with payment to Quadrant Subscription Services Ltd., Oakfield House, Perymount Road, Haywards Heath, Sussex, RH16 3DH.

BINDERS AND INDEXES

Binders (£4.50) and Indexes (45p) can be supplied by the Post Sales Department, IPC Magazines Ltd., Lavington House, 25 Lavington Street, London SE1 0PF. Prices include postage and VAT. In the case of overseas orders, add 60p.

BACK NUMBERS

Some back issues are available from the Post Sales Department, IPC Magazines Ltd., Lavington House, 25 Lavington Street, London SE1 0PF at £1.20p inclusive of postage and packing.

QUERIES

We regret that we cannot answer technical queries over the telephone nor supply service sheets. We will endeavour to assist readers who have queries relating to articles published in *Television*, but we cannot offer advice on modifications to our published designs nor comment on alternative ways of using them. All correspondents expecting a reply should enclose a stamped addressed envelope. Requests for advice on dealing with servicing problems should be directed to our Queries Service. For details see our regular feature "Service Bureau". Send to the address given above (see "correspondence").

this month


- 473 Leader**
- 475 Electronic Circuit Breaker** *Ged Whitney, G8RSI*
Save on fuses and get an instant indication when dealing with that bane of service engineers, intermittent fuse blowing.
- 476 All at Fours and Sevens** *Les Lawry-Johns*
Many of the faults this month seem to involve certain voodoo numbers. Plus a visit from Mr. Nick Payne and his set.
- 477 Next Month in Television**
- 479 Letters**
- 480 Video Recording on Tape** *Eugene Trundle*
To record a video signal on tape economically for domestic purposes is a considerable problem. The reasons for bandwidth limiting and the use of f.m. are explained, along with the way in which the sidebands can be restricted.
- 484 VCR Clinic**
Notes on VCR faults and servicing from Derek Snelling, John Coombes, Philip Blundell, Tech. (C.E.I.) and Michael J. Cousins, T.Eng. (C.E.I.).
- 486 Teletalk** *Malcolm Burrell*
Comments on various faults and aspects of the contemporary servicing trade.
- 488 Spectrum-Monitor Interface** *John de Rivaz, B.Sc.(Eng.)*
A circuit to convert the Sinclair Spectrum microcomputer's YUV output signals to RGB drives for a monitor, using an SL901B i.c. plus a minimum amount of peripheral circuitry.
- 489 Teletopics**
News, comment and developments.
- 492 Servicing the Grundig 2 x 4 Super, Part 1** *Mike Phelan*
This machine is available at bargain prices and provides superb performance. The power supply and various basic fault conditions are dealt with in this first instalment.
- 494 The Ferguson TX100 Chassis**
The latest chassis in the Thorn/Ferguson TX series is designed to drive just about every type of tube and to interface with almost any video/audio/control requirements. A flexible, high-performance chassis to supersede the TX9 and TX10.
- 496 TV Fault Finding**
Reports on TV faults and servicing problems from Mick Dutton, John Coombes, Malcolm Burrell and Tony Thompson.
- 497 TV Test Pattern Generator, Part 3** *Tony Jenkins, G8TBF*
Preliminary constructional details.
- 498 Long-distance Television** *Roger Bunney*
Reports on DX conditions and reception, and news from abroad. Plus details of a helical aerial for satellite reception at 714MHz.
- 501 Service Bureau**
- 502 Test Case 259**

OUR NEXT ISSUE DATED AUGUST WILL
BE PUBLISHED ON JULY 18

MANOR SUPPLIES

NEW MKV PAL COLOUR TEST GENERATOR FOR TV & VCR.

TEST DEMONSTRATIONS AT 172 WEST END LANE

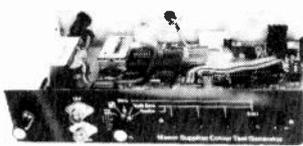

- ★ 40 different patterns and variations.
- ★ Broadcast transmission accuracy (fully interlaced sync pulses with correct picture blanking).
- ★ EBU colour bars, BBC colour bars, whole rasters & split bars (specially useful for VCR service), white, yellow, cyan, green, magenta, red, blue and black.
- ★ Chequerboard.
- ★ Mono outputs with border castellations, cross hatch, grey scale, vertical lines, horizontal lines and dots.
- ★ UHF modulator output plugs straight into receiver aerial socket.
- ★ Additional video output for CCTV & VCR.
- ★ Facilities for sound output.
- ★ Easy to build kit, standard parts. Only 2 adjustments. No special test equipment required.
- ★ Mains operated with stabilised power supply.
- ★ All kits fully guaranteed with back-up service.
- ★ Also available with VHF Modulator.


Price of Kit **£80.50**
 De Luxe Case (10" x 6" x 2 1/4") **£8.50**
 Optional Sound Module (2MHz or 5.5MHz) **£4.50**
 Built & Tested in De Luxe Case including Sound Module **£120.75**

SPECIAL TEST REPORT 'TELEVISION' DEC. 1982

Post/Packing £2.50
 All above prices include VAT 15%

PAL COLOUR BAR GENERATOR (Mk4)

4TH SUCCESSFUL YEAR

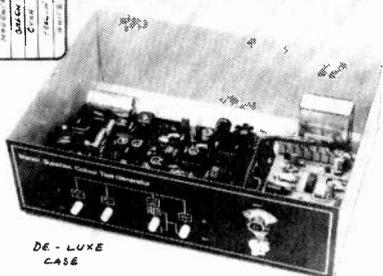

DE-LUXE CASE

- ★ Output at UHF, applied to receiver aerial socket.
- ★ In addition to colour bars R-Y, B-Y etc.
- ★ Cross-hatch, grey scale, peak white and black level.
- ★ Push button controls, battery or mains operated.
- ★ Simple design, only five i.c.s on colour bar P.C.B.

PRICE OF MK 4 COLOUR BAR GENERATOR KIT **£34.50**. DELUXE CASE **£8.50**. BATT HOLDERS **£3.20**. MAINS SUPPLY KIT **£4.80** (Combined P&P **£2.20**).

MK 4 DE LUXE (BATTERY) BUILT & TESTED **£66.70 + £2.20 P & P**.
 MK 4 DE LUXE (MAINS) BUILT & TESTED **£78.20 + £2.20 P & P**.
 VHF MODULATOR (CHI to 4) FOR OVERSEAS **£6.60**.
 EASILY ADAPTED FOR VIDEO OUTPUT & C.C.T.V.
 (ALL PRICES INCLUDE 15% VAT)

MANOR SUPPLIES TELETEXT ADAPTOR KITS

MK 1 (Texas XMII) remote control **£158.70** p.p. **£3.00**.
 MK2 (Mullard) infra red remote control **£198.40** p.p. **£3.00**
 Further details on request. Tel 01-794 8751/7346

Goods available if in stock immediately over shop counter (Mail order between 3 days and 1 week from receipt of order).

TV SERVICE SPARES

BACKED BY TWENTY YEARS EXPERIENCE & STAFF OF TECHNICAL EXPERTS

TELEVISION MAGAZINE PROJECT PARTS COLOUR PORTABLE TV MONO PORTABLE TV, SMALL SCREEN MONITOR ETC.

THORN TX10 TYPE REMOTE & TUNING CONTROL PANEL **£10.80** p.p. **£1.50**.
 PHILIPS UHF MODULATOR (AUDIO & VIDEO INPUT) **£17.25** p.p. **£1.00**.
 SAW FILTER IF AMPLIFIER PLUS TUNER COMPLETE AND tested for T.V. SOUND & VISION **£32.80** p.p. **£1.20**.
 THORN TX9, TX10 SAW FILTER IF PANEL **£9.80** p.p. **80p**.
 PAL DECODER KIT FOR RGB MONITORS **£31.00** p.p. **£1.00**.
 SPECIAL OFFER TEXAS XMII TELETEXT DECODER NEW & TESTED, AT REDUCED PRICE **£46.00** p.p. **£1.60**.
 TELETEXT 23 BUTTON DE-LUXE HANDSET WITH 5 YDS. CABLE **£7.80** p.p. **£1.20**. XMII STAB. POWER SUPPLY **£4.40** p.p. **£1.20**.
 CROSS HATCH UNIT KIT, AERIAL INPUT TYPE, INCL. T.V. SYNC AND UHF MODULATOR. BATTERY OPERATED. ALSO GIVES PEAK WHITE & BLACK LEVELS. CAN BE USED FOR ANY SET **£13.80** p.p. **80p**. (ALUM CASE **£2.90** DE LUXE CASE **£7.85** p.p. **£1.40**).
 ADDITIONAL GREY SCALE KIT **£3.35** p.p. **45p**.
 UHF SIGNAL STRENGTH METER KIT **£23.00** (VHF version also available). ALUM CASE **£2.90** DE LUXE CASE **£8.50** p.p. **£1.80**.
 CRT TESTER & REACTIVATOR PROJECT KIT FOR COLOUR & MONO **£32.20** p.p. **£2.80**.
 BUSH Z718 BC6100 SERIES IF PANEL **£5.75** p.p. **90p**.
 BUSH A816 IF PANEL (SURPLUS) **£1.90** p.p. **90p**.
 DECCA 80, SERIES, IF, FRAME T.B. **£5.75** each p.p. **£1.40**.
 DECCA 80, LINE SCAN UNIT salvaged **£11.50** each p.p. **£2.00**.
 GEC 2040 Convergence panels, Decoder panels **£2.88** each p.p. **£1.80**.
 GEC 2040 IF PANELS **£3.22** p.p. **£1.60**.
 GEC 2110 CONVERGENCE PANELS **£5.75** p.p. **£1.80**.
 PYE 691-7 CDA PANELS. Makers tested stock **£6.90** p.p. **£1.45**.
 PYE 725 T.B. Unit. Makers tested stock **£23.00** p.p. **£2.80**.
 THORN TX9 PANELS ex factory for small spares. Includes I.C.s & Semiconductors etc. **£5.75** p.p. **£2.00**.
 THORN TX9 PANELS salvaged ex factory for spares incl. LOPT & mains transformers **£11.50** p.p. **£2.80**.
 THORN TX9 PANELS ex factory salvaged complete cond **£23.00** p.p. **£2.80**.
 THORN TX10 T.B. PANELS salvaged ex factory **£17.25** p.p. **£3.00**.
 THORN 3000 LINE T.B., PCB POWER PCB **£5.75** each p.p. **£1.30**.
 THORN 8000/8500 IF/DECODER PANELS salvaged **£3.70** p.p. **£1.80**.
 THORN 8000/8500 FRAME T.B. PANELS salvaged/spares **£2.88** p.p. **£1.40**.
 THORN 9000 SERIES TOUCH TUNE REMOTE CONTROL UNIT PLUS ULTRASONIC TRANSMITTER HANDSET **£19.32** p.p. **£1.84**.
 THORN 9000 IF/DECODER PANELS Salvaged **£5.75** p.p. **£1.60**.
 PHILIPS G8/G9 IF/DECODER Panels for small spares **£1.75** p.p. **£1.40**.
 G8 Decoder panels salvaged **£4.25**. Panels for spares **£2.00** p.p. **£1.40**.
 G9 Scan Panel. Basic PCB in fibreglass **£16.68** p.p. **£1.80**.
 G11 Frame Panels **£20.70** p.p. **£2.00**.
 GRUNDIG 8630 Series Varicap Tuners **£5.75** p.p. **£1.00**.
 VARICAP, U321, U322, ELC 1043/06 ELC 1043/05 **£7.82** p.p. **80p**; G.I. type (equiv. 1043/05) **£4.00** p.p. **60p**. MAKERS VARICAP CONTROLS Pye CT200 4PSN **£8.60**, BUSH 4PSN **£5.50**, Decca 4PSN **£6.70** p.p. **80p**.
 SPECIAL OFFER ELEVEN POSITION VARICAP CONTROL UNIT UHF/VHF **£2.10** p.p. **£1.00**.
 BUSH "Touch Tune" Varicap Control Z179, Z718 types **£4.40** p.p. **95p**.
 VARICAP UHF-VHF ELC 2000S, ELC2060 **£11.30** p.p. **90p**.
 VARICAP VHF MULLARD ELC 1042, PHILIPS **£7.95** p.p. **80p**.
 UHF/625 Tuners, many different types in stock. DECCA Bradford 5 position, MULLARD 4 position **£2.88**, JAP Rotary **£5.50** p.p. **£1.80**.
 T.V. SOUND IF Panels **£7.82** p.p. **£1.00**.
 LOPT TESTER Service Dept approved **£17.82** p.p. **£1.20**.
 LOPTS NEW & GUAR. P/P Mono **£1.35p**, Colour **£1.50p**, Bobbins **80p**.
 BUSH 161 to 186 (twin panel) **£6.80**
 BUSH, MURPHY 774 series **£9.80**
 BUSH, MURPHY A816 series **£9.80**
 FERG., HMV, MARCONI, ULTRA
 950, 1400, 1500, 1580, 1590, 1591 .. **£6.80**
 THORN 1600, 1615, 1690, 1691 .. **£10.50**
 GEC 2000 to 2038 series **£7.80**
 GEC series 1 & 2 **£9.20**
 INDESIT 20/24EGB **£8.80**
 ITT/KB VC 200, 300 **£8.80**
 MURPHY 1910 to 2414 (twin panel) **£6.80**
 PHILIPS 170, 210, 300 SERIES **£8.80**
 PYE, INVICTA, EKCO, FERR.
 368, 169, 569, 769 series **£8.80**
 SPECIAL OFFER
 DECCA 20/24, 1700, 2000, 2401 ... **£4.40**
 GEC 2114/Junior Fineline **£3.25**
 PYE 40, 67 **£2.00**
 KB VC ELEVEN (003) **£2.00**
 KB VCI **£3.25**
 R.B.M. A823 **£5.60**
 R.B.M. Z179 **£11.30**
 R.B.M. T20, T22 **£11.30**
 R.B.M. T20, T22 Bobbin **£6.44**
 DECCA Bradford (state Mod No.) **£10.15**
 DECCA 80, 100 **£10.15**
 GEC 2028, 2040, 2100 **£6.70**
 GEC 2110 Series **£12.20**
 ITT CVC 5 to 9, CVC20 **£11.30**
 ITC CVC25, CVC30 series **£10.15**
 PYE 691-697 **£11.50**
 PYE 713, 715 **£7.85**
 PYE 725 (90°) 731 to 741 **£10.60**
 PHILIPS G8 **£10.15**
 PHILIPS G9 **£11.70**
 PHILIPS 570, 571 **£7.85**
 THORN 3000/3500 SCAN, EHT ... **£7.85**
 THORN 8000/8500/8800 **£14.80**
 THORN 9000 to 9600 **£14.80**
 THORN 9800 **£21.90**

OTHERS AVAILABLE, PRICES ON REQUEST. ALSO F.O.P.T.S.
 TRIPPLERS Full range available. Mono & Colour.
 Special Offer: Thorn 1400 5 stick EHT Tray **£1.72** p.p. **65p**.
 TRANSDUCTORS suitable for G8, A823, Bradford etc. **£1.72** p.p. **60p**.
 6-3V CRT Boost Transformers for Colour & Mono **£5.80** p.p. **£1.20**.
 CALLERS WELCOME AT SHOP PREMISES
 THOUSANDS OF ADDITIONAL ITEMS, ENQUIRIES INVITED
 LARGE SELECTION TESTED COLOUR PANELS POPULAR MODELS
 Telephone 01-794 8751, 794 7346

MANOR SUPPLIES

172 WEST END LANE, LONDON, N.W.6.

NEAR: W. Hampstead Tube Stn. (Jubilee) Buses 28, 159, C11 pass door
 W. Hampstead British Rail Stns. (Richmond, Broad St.) (St. Pancras, Bedford)
 W. Hampstead (Brit. Rail) access from all over Greater London.

Mail Order: 64 GOLDERS MANOR DRIVE, LONDON N.W.11.

ALL PRICES INCLUDE VAT AT 15%
 (CLOSED FOR HOLIDAYS JULY 9th TO JULY 21st)

TELEVISION & VIDEO SERVICING

(FULL-TIME & EVENING COURSES)

- ELECTRONIC PRINCIPLES
- TELEVISION SERVICING
- VIDEO CASSETTE RECORDER SERVICING

High percentage of practical video servicing provided

Courses from 3 weeks to 15 months.
College Diploma & BTEC Awards.

(Also full-time day courses in Computing Technology & Robotics).

Free prospectus – please state whether interest is in day or evening training.

LONDON ELECTRONICS COLLEGE
20 Penywern Road, Earls Court,
London SW5 9SU.
Tel: 01-373 8721.

**CAMPION
THOMPSON**
ELECTRICAL WHOLESALE

Ring
0562 743735
for
Big Profits . . .

. . . on the lowest priced TV's


Buy from the largest stock of used TV's in the U.K. More than 6,000 sets including high class refurbished colour sets, tested and un-tested mono sets. Many recent models, all from big name manufacturers including Philips and Pye G11.

. . . on domestic appliances

New products, end of line clearances and manufacturers' seconds, all at knock down prices.

**Big names,
big quantities,
big profits for you!**

Visit our showroom or phone us now.

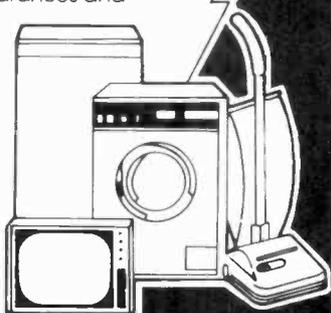

Campion Thompson Ltd.,
Campion House,
Franchise Street,
Kidderminster,
Worcestershire, DY11 6RE
Tel (0562) 743735 (4 lines)



FREE CAREER BOOKLET

Train for success in Electronics Engineering, T.V. Servicing, Electrical Engineering—or running your own business!

ICS have helped thousands of ambitious people to move up into higher paid, more secure jobs in the fields of electronics, T.V., electrical engineering—now it can be your turn. Whether you are a newcomer to the field or already working in these industries, ICS can provide you with the specialised training so essential to success.

Personal Tuition and 80 Years of Success

The expert and personal guidance by fully qualified tutors, backed by the long ICS record of success, is the key to our outstanding performance in the technical field. You study at the time and pace that suits you best and in your own home.

You study the subjects you enjoy, receive a formal Diploma, and you're ready for that better job, better pay.

**TICK THE FREE BOOKLET YOU
WANT AND POST TODAY**

ELECTRONICS ENGINEERING

A Diploma Course, recognised by the Institute of Engineers & Technicians as meeting all academic standards for application as an Associate.

T.V. & AUDIO SERVICING

A Diploma Course, training you in all aspects of installing, maintaining and repairing T.V. and Audio equipment, domestic and industrial.

ELECTRICAL ENGINEERING

A further Diploma Course recognised by the Institute of Engineers & Technicians, also covering business aspects of electrical contracting.

RUNNING YOUR OWN BUSINESS

If running your own electronics, T.V. servicing or electrical business appeals, then this Diploma Course trains you in the vital business knowledge and techniques you'll need.

Name

Address

ICS

ICS
Dept. EGS74
160 Stewarts Road,
London SW8 4UJ.



01-622 9911
(all hours)

P. V. TUBES

HAVE MOVED

Just phone your order through, we do the rest.



Telephone: Accrington (0254) 36521
Accrington (0254) 32611
Telex: 635562 Griffin G (For P.V.)

SUPPLIERS OF TELEVISION COMPONENTS

104 ABBEY STREET, ACCRINGTON, LANCS BB5 1EE.

TRADE COUNTER OPEN MON-FRI 9 a.m.-5 p.m. SAT 9.30 a.m.-5 p.m. TRADE COUNTER CLOSED WEDNESDAY p.m.

VARICAP TUNERS		SWITCHES & ACCESS.		DID YOU KNOW WE'VE GOT		PHILIPS KT3 SPECIFICS		SPECIFIC COMPONENTS		
ELC1043-05	8.40	On/off gen. purpose 4A	75	LOTS OF NEW THINGS!		KT3 posistor	1.50	Philips G8 knobs sm/kg	50	
ELC1043-06	8.40	G8 on/off	1.38	Decca speaker 16R	4.50	Mains electrolytic 225/25 380V	2.50	90° transductor	2.60	
ELC2003	16.50	G11 on/off	1.58	8R	3.75	Selector unit Mod. 933	13.42	Thorn 1591 speakers sm	4.10	
Philips G8/G9	10.50	G11 on/off remote	1.58	B+K tube bases Dynascan		On/off switch Mod. 933	3.20	kg	4.50	
Philips G11 (U321)	8.50	Gen. purpose rotary	66	No. 3	9.50	Tripler	10.65	Thorn 1500 controls	59	
U322	7.20	Thorn Tx 9/10	1.06	No. 6	11.08	Luminance chroma panel	24.00	390K frame 470K line contrast 1k5	each	
U341	9.50	G/C 2040	98	No. 8	10.08	2003 IF module	14.95	Focus control Thorny/GEC	1.83	
Thorn 1691	17.90	Thorn 1501 push	2.90	No. 10	10.08	U321 IF module	13.50	Thorn 9000 focus unit	5.95	
Rank T20	13.00	Thorn 1691 with vol. cont.	2.89	No. 23	13.86	R.G.B. panel	10.30	Thorn 9000 focus cont.	5.95	
PUSH BUTTON ASS.				L5 7"x3" speaker		4.25	Sound panel	8.50	Thorn 8500 focus unit	4.75
Decca 4 way	6.88	Rank drive buttons	35	C12 computer cass.	30	Power panel	10.60	Thorn Tx10 focus cont.	9.00	
6 way	7.50	1 1/2" x 1/2", 2" x 1/2", 2" x 1"	15	C18 computer cass.	33	Mains input panel	14.30	Decca bridge trans.	1.97	
GEC 2110 6 way	7.98	GEC 2110 tuner neons	14	51" floppy disc s/s s/d	1.61	Line sync panel	10.20	Decca 30 width cont.	50	
GEC 51m 6 way	6.50	Thorn 3500 A1 beam	70	3R fused res. GEC	50	Mark II chroma panel	16.50	Decca 2M2 HT cont.	25	
GEC/ITT/PYE 7 way	14.50	GEC 2110 A1 cont. R/B/G	58	15R fused res. G9	55	Sound module	8.50	Rank T20 focus cont.	2.20	
Pye 4 way (713/15)	9.00	ITT CVCS on/off	1.24	G11 line in coil	2.95	LOPT	9.70	Pye 731 HF choke	6.50	
Pye 6 way (207/715)	16.00	EAGLE MULTIMETERS		G11 line scan panel	5.30	Focus unit	3.50	Delay lines DL20, DL60, DL700, DL50	2.20	
Pye 697 repair kit	9.00	KEW 7N	5.25	G11 pot G2 R.G.B.	5.30	K30 SPECIFICS		CRT tube base	70	
Pye 725-735	11.00	KEW 14	7.95	G11 line scan panel	54.00	K30 LOPT	17.50	EHT final anode cap	53	
Philips G8 (early)	13.50	KEW 20	14.50	G11 power panel	37.50	K30 focus unit	2.90	6.3V CRT boost trans.	5.80	
Philips G8 (late)	13.90	EM5	11.95	G11 timebase panel	37.50	K30 EHT lead	5.90	Focus rod	1.25	
Rank A823	10.75	EM20A	15.95	G11 bridge trans.	97	Selector unit 1002 (early)	11.20	Focus holder	2.00	
Rank T20A	9.75	EM10	13.95	G11 EW correc. coil	1.95	TMS 1000 panel 1234	13.00	AFC unit G8	8.82	
Hitachi 4 way	10.75	EM50	17.95	G11 final anode lead	1.50	Euro decoder panel 1234	46.00	IF gain module	9.00	
Philips G11 unit	23.00	MM50	27.95	G11 focus unit	5.80	Pure supply 1234	23.50	C.O.A. panel	20.00	
Philips KT3	14.50	MM10	39.95	G11 39R 3W resistor	6.00	A1 gun switches	70	G8 rear conv. panel	23.00	
Philips KT30	10.30	MMT20	17.95	G11 RGB 10G diodes	50	On/off switch	2.60	SPARK GAPS		
ITT CVC 8/9 (mod)	12.00	MM150	74.95	Labgear CM7091 UHF/VHF colour bar	116.00	Selector unit 1002 (late)	9.90	Decca 100	52	
ITT 6 way with VCR	8.90	T1206	6.95	Televerta up converta	37.20	Hand set 1201	14.50	0.75 pf	1.50	
Thorn 8800 6 way round	7.50	MMC100	17.95			Hand set 1234	14.50	0.01 pf	32	
Thorn 9000 unit	10.60					Diode ZTX 33B	90			
Thorn 9000 switchback	2.90					DL 20 delay line	2.20			
SERVICE AIDS		ANTEX SOLDERING EQUIPMENT		SUNDRY EQUIPMENT		Solda Mop Strnd.		74	Specific Video Leads (please state models)	4.25
SERVISOL Freeze-It	1.02	C15W Iron 240V	4.41	Test Lead Set	4.20	Sidecutters sm.	1.20	Universals Video Lead Kit	6.00	
SUPER SERVISOL	92	C240 Element	1.80	Degaussing Coil Stick	17.00	Long Nose Pliers	1.20	EHT Cable	per mtr 25	
SERVISOL Foam Cleanser	89	Bits 102	90	Signal Injector	4.00	SM Torch	42			
SERVISOL Plastics Seal	1.00	821	90	Elect. Circuit Tester	1.50	Quick Set Adhesive	75			
SERVISOL Silicone Grease	1.08	CS17W Iron 240V	4.41	5A Choc Bloc (12)	40	Sm. Neon Screwdriver	40	PLUGS		
SERVISOL Tubes Silicone Grease	1.64	CS240 Element	2.25	Fuse Wire 5A, 15A, 30A	05	Lg. Neon Screwdriver	65	Phono Plugs	12	
SERVISOL Aero Klene	84	Bits 1101	90	4-way 13A Mains Conn.	5.00	Min. Screwdrivers	15	DIN Plugs 3 pin	22	
SERVISOL Aero Duster	1.10	1106	90	Safe Block (mains)	7.00	I.C. Inserters	1.18	4 pin	22p	
SERVISOL Excel Polish	88	XS25W Iron 240V	4.59	13A Plug Top (box 10)	4.80			5 pin	20	
SERVISOL Video Head Cleanser	82	XS240 Element	2.25	Portable Oscilloscope	155.00			Car Aerial Plug	18	
Super 40	1.50	Bits 50	90	Probes (x10)	10.90			2.5mm Jack Plug	14	
Fire Extinguisher 640G	2.50	51	90	Probes (x1)	10.90	DATA BOOKS (Zero VAT)		3.5mm Jack Plug	14	
Heat Sink Compound 25G	1.08	Temp. Controlled		CRT Tester/Rejuven.	172.00	TVT 80 A-Z only	3.75	Stand Jack Plug	20	
Silicone Rubber Tube 110G	2.98	30W Iron CSTC	10.50	KHP30 Meas. Probe 30KV	32.00	TVT 80 2N-2S only	4.00	Stereo Jack Plug	36	
Soldka Mop standard reel	74	40W Iron XSTC	10.50	Bell Wire (100m)	5.00	TVT 80/80 A-Z/2N-2S (pair)	7.50	Battery Plug Thorn TV's	28	
ELECTROLUBE PRODUCTS		Unit for above TCSU1	32.64	Mains Cable (circular 100m)		LIN IC Books (data only not equiv.)		Coax Plugs	each 18	
Electrolube Adhesive	62	Stand	2.00	(2 core)	10.75	LIN1	5.95	ten 1.80		
Electro-Mech lubricant	1.49	MLXS Auto Repair Kit	6.30	(3 core)	13.25	LIN2	5.95	PL259	40	
Elect. cleaning solvent	1.62			Factory recon. Avo meters	99.00	2M Fly Lead	70	Reducers for PL259	16	
Freezer	1.49	WELLER		Avo Batteries	2.20	4M Fly Lead	1.20	Line Connectors	16	
Foam cleanser	1.12	Heat gun	12.00	Vero Board	2.59	10M Fly Lead	1.90			
Heat transfer compound	1.14	Heat gun tips (pair)	57	Isolating trans. 500vA 240V	40.00	Figure 8 Mains Lead	62	CASSETTE DRIVE BELTS		
Silicone compound	1.94	3/16" Iron tips 25W (MT5)	57	Solder 500g	7.00	Computer to TV	97	35m 35 46mm 37 57m 37		
Special contact fluid (Snorkell)	3.20			D.I.Y. Solder	6.50	7 pin din to 5 pin din	98	66m 39 71m 43 76m 43		
Permagard	1.52			Solder Sucker	81	5 pin din to 5 pin din	98	90m 43 110m 59		
Elec. mech. lubricant pen	74			Nozzles						
VIDEO		LABGEAR		OFFICIAL ORDERS ACCEPTED FROM SCHOOLS, LOCAL AUTHORITIES ETC.		P.V. MICROCOMPUTER CENTRE				
Video care kits	3.50	CM7061 Power Unit 12V	10.70	WE HAVE A FULL RANGE OF AERIALS AND ACCESSORIES FROM TRADE COUNTER		Why not pay us a visit and see our range of Micros, Software Books and Peripherals. Please ring for prices.				
VHS E30 video tape	3.06	CM7062 Reg. Power Unit 12V	11.67	AERIAL EQUIPMENT		Spectrum 16K		Vic 20 Sharp		
VHS E60 video tape	4.00	CM7060 MHA 10db 12V W/B	9.39	Plastic Tape	50	48K	Commodore 64	Oric	We are also authorised dealers for the BBC Micro and accessories.	
Scotch E120 video tape	5.00	CM7065 VHF/UHF MHA W/B 12V 13.66		F.M. Plugs	25					
Scotch E180 video tape	4.50	CM7067 UHF 12V MHA (Specify A-B or C/D)	10.21	Set Top Aerial	2.30					
Beta L500 video tape	4.50	CM7068 UHF 12V MHA High Gain (Specify A-B or C/D)	15.19	Loop Aerial	1.00					
Beta L750 video tape	5.80	A-B or C/D)	15.19	Mast Amp/Power Unit WB	18.00					
Philips VCC 240	6.20	CM7053 Behind Set UHF Amp. (Mains)	12.13	Aerial Isolator Kit	2.08					
Philips VCC 360	8.30	CM7054 Behind Set UHF Amp. (Battery e.g. Caravans)	9.92	Attenuator 6dB, 12dB, 18dB	1.80					
Philips VCC 480	10.21	CM7043 Second Set Amp. UHF	11.54	27MHz Filter 50dB	2.10					
Philips VCC 1700	15.10	CM7093 Behind Set UHF Amp. 3 Sets	14.54	Cable Clips 7mm	per 100 1.18					
VIDEO HEADS		CM7063 Dist. Amp. VHF/UHF 17db/output 12V	20.10	Single Outlets	80					
3HSS VHS	32.50	CM7108 VHF/UHF 8+1 Dist. Amp.	41.20	Surface Splitter	1.70					
4HSS VHS	32.80	CM9700 27mhz CB Suppress.	3.86	A Splitter	70					
PS3B Beta/Sony	42.00	CM6011 Outdoor Splitter (2 way) W/B	7.46	ICOM Coax	15.00					
VIDEO RECORDER HEADS		CM9003 Flush Single Outlet	1.40	Coax Plugs	per 10 1.80					
Philips V2000	52.00	CM9010 Flush Twin Outlet	1.86	1" U Bolts	30					
Philips 1700	52.00	CM9034 UHF Group Filters with DC Through Pass (state A/B/CD)	6.97	J Bolts	25					
Video lamps	1.30	CM6006 6 Way Passive Splitter	10.97	ANTIFERENCE						
Video lamp holders	3.30	CM7042 TV Games Combin.	2.68	SB11 Splitter	1.91					
VCR DRIVE BELTS		CM9009 Flush TV/FM Outlet	2.90	COB11 Outlet	80					
22.5 mm	80	CM7091 Col. Bar Gen.	116.00	TRR/USP Transformer	2.83					
50.5 mm	82			CS200 Combiner/Splitter	3.03					
52.5 mm	84			CS1000 Combiner/Splitter	6.15					
71 mm	86			PU1240 Power Unit	11.00					
80 mm	88			UP1300 MHA	8.25					
100 mm	1.54			XS2U Xtraboost	11.63					
109 mm	1.56			4 way VHF/UHF Amp	33.75					
127 mm	1.60			6 way VHF/UHF Amp	42.00					
147 mm	2.10			XG8 High Gain Aerial A-B-CD-WB	16.00					
161.5 mm	2.14									
Video head cleaner	90									
AUDIO HEADS AND MOTORS		STATIONERY (Zero VAT)								
Mono record/playback	4.32	Service Call Pad (100)	1.20							
Stereo playback	4.79	Repair Ticket (100)	3.90							
Stereo record/playback	4.99	Job Card (100)	2.50							
Stereo record/playback (Dolby)	6.90	Rental Payment Card (50)	3.50							
Stereo record/playback (glass face)	10.95	Rental Agreements (100)	3.50							
Mono/stereo erase	2.25	H.P. Agreements (100)	3.50							
Electronic/rotation clockwise motors		Maintenance Agreement (100)	3.50							
6V MD6515	4.95									
9V MD9516	4.95									
12V MD12517	4.95									

PLEASE ORDER FROM LATEST COPY OF MAG. TO AVOID PRICE INCREASES

P. V. TUBES

PLEASE NOTE OUR NEW ADDRESS - COME AND SEE US
 104 ABBEY STREET, ACCRINGTON, LANCs BB5 1EE.
 Tel: 0254 36521/32611 Telex: 635562 Griffin G (For P.V.)

HOW TO ORDER
 ADD 65p per order P+P (U.K.). Heavier parcels e.g. cable, service aids, degauss, coils please allow £1.20 P+P (U.K.). Export orders charged at cost. First Class Mail is used whenever possible. Add 15% VAT to total except where it states zero rate.

Goods are despatched on the day we receive your order. If for any reason we are out of stock we will try to inform you as quickly as possible. We try our best to give a speedy, fair and efficient service. As our regular customers know, orders telephoned in before 4 p.m. will be despatched the same day. V.A.T. invoice on request. Give us a ring - we'll give you service. Please ask if what you need is not listed - we will try to help. Prices are subject to change without notice.

SEMICONDUCTORS

AC107	36	BC557	8	BF337	41	R20108	1.92
AC126	30	BC558	9	BF338	41	R2265	1.50
AC127	32	BCY72	13	BF355	56	R2322	67
AC128	32	BD115	45	BF362	68	R2323	62
AC128K	48	BD116A	65	BF363	72	R2461	1.50
AC141K	38	BD124P	79	BF371	30	R2540	2.80
AC142K	38	BD131	50	BF392	36	RCA16334	99
AC176	36	BD132	49	BF422	34	RCA16029	99
AC176K	36	BD133	60	BF423	46	RCA16039	99
AC186	41	BD135	38	BF435	35	RCA16092	99
AC187	38	BD136	38	BF457	36	RCA16040	99
AC187K	38	BD137	38	BF458	43	RCA16041	84
AC188	36	BD138	36	BF459	43	RCA16334	99
AC188K	39	BD139	36	BF460	86	RCA16335	99
AD143	82	BD140	44	BF462	88	RCA16799	99
AD161	54	BD144	1.70	BF469	46	RCA16957	2.88
AD162	54	BD150	60	BF470	66	TIC45	10
AD161/62 MP	1.15	BD159	85	BF597	10	TIC46	10
AF106	49	BD166	52	BF757	54	TIL32	60
AF114	89	BD179	70	BF758	54	TIL78	46
AF118	1.20	BD182	1.20	BRK39	27	TIP29C	48
AF121	75	BD183	75	BRF40	30	TIP30A	47
AF124	46	BD201	85	BRF79	85	TIP30C	43
AF125	46	BD202	91	BRF90	1.74	TIP31C	55
AF126	46	BD203	80	BF142	39	TIP32C	42
AF127	38	BD204	99	BF143	39	TIP33B	75
AF139	58	BD222	46	BFW10	60	TIP34B	1.06
AF178	1.54	BD223	56	BFX29	40	TIP41C	47
AF239	60	BD225	47	BFX84	42	TIP42C	50
AL102	2.00	BD232	68	BFX85	30	TIP47	70
AU106	2.50	BD233	60	BFX86	30	TIP120	65
AU107	2.00	BD234	63	BFX88	46	TIP2955	93
AU113	2.00	BD235	60	BFY50	30	TIP3055	60
BC107	20	BD236	65	BFY51	30	TIS91	21
BC108	20	BD237	57	BFY52	24	TU106/02	1.80
BC109	20	BD238	65	BFY90	95	2N696	21
BC114	12	BD243	85	BR100	34	2N918	82
BC115	17	BD244	85	BR101	21	2N2904	51
BC116A	16	BD410	79	BR103	83	2N2905	28
BC117	30	BD434	74	BRCA4443	94	2N3054	60
BC118	24	BD437	86	BRCA4444	98	2N3055	60
BC119	36	BD438	94	BRX46	40	2N3072	11
BC139	28	BD507	52	BRX39	56	2N3703	10
BC140	32	BD508	55	BRX55	45	2N3705	10
BC141	26	BD509	56	BRX56	57	2N3706	10
BC142	30	BD510	60	BSW67	68	2N3708	17
BC143	31	BD278A	81	BT100	1.85	2N5294	46
BC147	13	BD517	60	BT101	1.20	2N5296	46
BC148	9	BD520	75	BT102/500	1.20	2N5298	69
BC149	16	BD526	82	BT106	1.60	2SB337	1.86
BC157	12	BD535	82	BT107	1.69	2N5496	53
BC158	16	BD536	91	BT108	1.69	2N6107	75
BC159	15	BD696A	1.49	BT109	99	2N6109	81
BC160	25	BD697	1.24	BT116	1.21	2SA715	1.98
BC161	28	BD695	1.39	BT119	3.66	2SC495	1.10
BC170B	15	BD698	1.50	BT120	3.66	2SC496	1.31
BC171	15	BD707	95	BT151/800	1.20	2SC643A	1.50
BC172	15	BDX32	2.10	BU104	2.00	2SC1096	1.72
BC173	12	BF115	38	BU105	1.58	2SC1172	2.20
BC174	10	BF117	36	BU108	1.80	2SC1173Y	1.69
BC177	27	BF125	26	BU124	1.90	2SC1306	2.73
BC178	26	BF127	47	BU126	1.75	2SC1307	3.00
BC182L	9	BF154	23	BU204	1.50	2SC1449	1.67
BC183L	14	BF158	18	BU205	1.42	2SC1520	60
BC184L	12	BF160	27	BU206	1.80	2SC1678	2.67
BC186	18	BF167	24	BU208	1.60	2SC1909	2.90
BC187	18	BF173	22	BU208A	1.65	2SC1953	1.44
BC204	10	BF177	52	BU208/02	2.10	2SC2028	1.82
BC208	13	BF178	46	BU326A	1.75	2SC2029	2.60
BC209	10	BF179	28	BU407	1.70	2SC2078	2.90
BC212	9	BF180	39	BU426	3.07	2SC2091	1.34
BC212L	13	BF181	39	BU500	2.30	2SC2166	2.73
BC213	13	BF182	36	BU526	2.46	DEC1	2.20
BC214	10	BF183	29	BU508	3.20	DEC2	2.20
BC237	14	BF184	36	BU806	1.40	THY15/80	2.20
BC238	14	BF185	36	BU807	2.94	THY15/85	2.20
BC251A	18	BF194/394	16	BUW84	1.45	BU2088	2.20
BC252	12	BF195	16	BUW91A	3.84	BUW81A	3.84
BC261	18	BF198	16	BUX84	1.50		
BC262	18	BF197	16	E1222	40		
BC300	50	BF198	16	MCR101	45		
BC301	53	BF199	21	MCR220	1.50		
BC303	33	BF200	35	ME0411	29		
BC307	20	BF224	25	MJE340	68		
BC308	25	BF225	20	MJE520	50		
BC327	99	BF241	25	MJ3000	1.98		
BC327	99	BF256	55	MFS492	35		
BC328	18	BF257	28	MR614	45		
BC337	18	BF258	25	MR854	55		
BC338	18	BF259	35	MR475	2.46		
BC461	30	BF262	84	MR479	2.60		
BC547	13	BF263	75	ON447	99		
BC548	13	BF271	24	ON448	99		
BC548	13	BF271	24	OT112	1.81		
BC549	8	BF273	24	OT121	1.91		
BC550	7	BF336	36	R20088	1.90		

INTEGRATED CIRCUITS

AN2140	3.91	SN76003N	2.49	TBA990	1.90	UPC1168C	1.28	AA119	9
AN240	3.84	=SN76013N		TBA14406	2.44	UPC1176C	1.46	BA102	17
AN318	3.96	SN76023N	2.00	TCA160	1.20	UPC1177H	1.56	BA115	13
AN262	2.45	SN76110N	1.15	TCA760	2.30	UPC1178C	1.28	BA145	17
AN301	5.15	SN76115N	2.27	TCA270SQ	2.50	UPC1180C	1.84	BA148	17
ANT150	3.87	SN76131N	2.00	TCA800	3.10	UPC1181H	1.82	BA154	6
AN6340	7.85	SN76226DN	2.00	TCA830	2.44	UPC1182H	2.95	BA155	14
AN6341	4.45	SN76227N	1.18	TCA830S	1.75	UPC1183H	1.38	BA156	15
AN6341N	5.10	SN76532N	1.50	TCA900	2.20	UPC1185H	3.66	BA317	28
AN6344	7.85	SN76533N	1.70	TCA910	2.20	UPC1188H	2.20	BA318	4
BA521	2.80	SN76033N	2.49	TCA940	1.95	UPC1190G	1.20	BA319	4
BA536	3.00	SN76544N	2.36	TDA440	2.20	UPC1197C	1.05	BA319	4
CAS55	46	SN76650N	1.05	TDA1002	1.95	UPC1200V	1.18	BA319	4
CAS56	84	SN76660N	80	TDA1003A	5.50	UPC1211V	2.70	BA319	4
CA741	25	SN76666N	80	TDA1004A	3.35	UPC1212V	1.34	BA319	4
CA748	45	SN76530A	1.47	TDA1006A	2.80	UPC1215V	1.66	BA319	4
CA7065	1.80	STK015	6.25	TDA1009	3.90	UPC1216V	1.20	BA319	4
HA1124	1.85	STK032	13.25	TDA1010	1.54	UPC1217G	1.13	BA319	4
HA1151	3.89	STK043	11.05	TDA1037	4.79	UPC1218H	1.80	BA319	4
HA1322	2.85	STK433	5.85	TDA1037	2.95	UPC1223C	2.20	BA319	4
HA1342	2.49	STK435	9.08	TDA1044	4.44	UPC1225H	2.00	BA319	4
HA1306N	2.80	STK436	5.58	TDA1060A	4.44	UPC1226V	1.50	BA319	4
HA1366WR	2.80	STK437	7.85	TDA1062	1.56	UPC1227C	1.20	BA319	4
HA1392	3.95	STK459	8.20	TDA1083	1.88	UPC1228H	5.4	BA319	4
HA11219	2.48	STK441	6.10	TDA1170S	3.90	UPC1230H	3.95	BA319	4
LA031P	3.21	STK461-465	9.60	TDA1190	3.50	UPC1238V	1.18	BA319	4
LA032P	2.90	SW153	2.74	TDA1200	2.95	UPC1245V	1.35	BA319	4
LA1102	3.37	TA7050P	95	TDA1200A	2.12	UPC1353C	4.15	BA319	4
LA250	3.57	TA7051P	95	TDA1270	3.95	UPC1365C	6.38	BA319	4
LA400	3.05	TA7063P	2.20	TDA1327	1.70	UPC1366C	2.08	BA319	4
LA422	3.28	TA7074P	1.00	TDA1352B	1.90	UPC1367	2.08	BA319	4
LC7130	5.83	TA7108P	3.43	TDA1412	1.20	UPC1378H	2.70	BA319	4
LC7120	5.87	TA7120P	2.43	TDA1415	1.40	UPC1358H	1.88	BA319	4
LC7137	5.50	TA7129AP	3.78	TDA1470	4.87	UPC1360C	2.20	BA319	4
LM1011	3.25	TA7130P	9.63	TDA1770	4.80	UPC1363C	2.16	BA319	4
LM1340T	75	TA7141P	1.95	TDA2002	2.90	UPC1366C	1.84	BA319	4
LM1303N	2.83	TA7146P	4.67	TDA2003	1.20	UPC1368H2	2.15	BA319	4
MB3712	1.95	TA7193P	5.67	TDA2004	2.52	UPC1370C2	2.58	BA319	4
MC1307	1.99	TA7171P	1.85	TDA2006	1.78	UPC1382C	1.08	BA319	4
MC1310P	1.60	TA7172P	1.85	TDA2010	2.00	UPC1384	3.78	BA319	4
MC1327	1.70	TA7173P	1.85	TDA2140	5.95	UPC1447H	58	BA319	4
MC1351P	2.83	TA7176P	2.50	TDA2150	2.22	UPC41C	2.80	BA319	4
MC1330P	9.00	TA7202P	4.27	TDA2190	4.78	UPC5743	38	BA319	4
MC1349	1.99	TA7204P	3.77	TDA2020	4.86	UPC577H	2.46	BA319	4
MC1350	1.50	TA7205AP	3.72	TDA2030	2.80	UPC585C	1.28	BA319	4
MC1352	1.75	TA7208P	3.40	TDA2521	4.17	TDA 1011	4.00	BA319	4
MC1358P	1.50	TA7210P	4.60	TDA2522	2.40	11A 4112	75	BA319	4
MC1495L	3.00	TA7222P	2.42	TDA2523	3.48	IC/Transistor equivalent leaflet £2.25 for the pair		BA319	4
MC13002	3.90	TA7223P	3.74	TDA2524	2.25			BA319	4
MC14011BCP	96	TA7227P	6.98	TDA2525	3.84			BA319	4
MC14049UB	43	TA7228P	5.98	TDA2530	2.70			BA319	4
MC7742									

WE WILL ONLY SUPPLY TOP QUALITY, BRANDED COMPONENTS. REPUTATION COUNTS WITH US

G.G.L. COMPONENTS
108 SCOTLAND ROAD, CARLISLE, CUMBRIA CA3 9EY
PHONE (0228) 20358/139693

BUY WITH

E.M.T. TRAYS

INTEGRATED CIRCUITS	TYPE PRICE (£)	TYPE PRICE (£)	TYPE PRICE (£)	TYPE PRICE (£)	TRAN-SISTORS	TYPE PRICE	TYPE PRICE	LINE O/P TR.
AN103	1.95	LA4031P 2.45	TBA890 2.95	STK036 12.67	UPC1216V 2.00	BC548 10	BR100 18	RBM T20/22A 12.20
AN214	2.25	LA4032 2.34	TBA920Q 1.50	STK043 11.33	UPC1217G 3.35	BC557 10	BR101 32	RBM Z718 18/20/22
AN217	2.44	LA4101 1.88	TBA950/2X 2.65	STK050 20.75	UPC1218H 2.75	BC558 10	BR103 55	THORN500/2800 5.90
AN240	2.20	LA4400 2.80	TCA270S 1.30	STK070 21.95	UPC1222 2.05	BD124P 55	BT106 1.15	THORN500-5S 4.95
AN253	1.93	LA4420 1.94	TCA2800 1.95	STK077 8.56	UPC1223 3.40	BD131 33	BT116 1.30	THORN3000/3500 7.75
AN264	1.77	LA4422 2.75	TCA940 1.56	STK078 8.45	UPC1225 3.10	BD132 33	BU126 1.78	THORN8000 4.00
AN315	1.66	LA4430 1.93	TDA1002A 1.50	STK082 9.75	UPC1226 2.55	BD201 80	BU204 1.50	THORN9000/8800 5.90
AN318	6.95	MC1327A 1.00	TDA1003A 2.80	STK086 12.89	UPC1227 2.10	BD202 70	BU205 1.42	THORN1500-5S 4.95
AN337	4.41	MC1358P 1.60	TDA1004A 2.70	STK415 9.66	UPC1230H 3.45	BD203 70	BU206 1.35	THORN1690/1 9.00
AN360	4.15	MC1330P 90	TDA1035 3.20	STK433 7.25	UPC1245 1.99	BD204 83	BU208A 1.40	THORN1815 9.75
AN7110	1.93	ML231B 1.95	TDA1044 3.10	STK437 7.77	UPC1250 2.45	BD222 50	BU208A/021.70	THORN TX10 12.50
AN7114	2.23	ML232B 1.70	TDA1170 1.80	STK439 7.86	UPC1350C 4.50	BD232 50	BU326A 1.48	PYE 731/713 (110) 10.20
AN7115	2.37	ML237 2.50	TDA1412 90	STK441 9.52	UPC1356C2 3.60	BD233 37	BU407 1.12	PYE 725 (90) 10.20
AN7120	2.43	ML238 4.22	TDA2190 3.20	STK443 11.33	UPC1358H 3.05	BD234 40	BU500 1.80	ITT CVC 1-9 9.00
AN7140	2.10	TA7072P 2.75	TDA2200 2.95	STK459 9.55	UPC1363C 3.20	BD235 32	BU526 2.00	DECCA 80 8.50
AN7145	3.25	TA7108P 2.10	TDA2522 1.80	STK463 10.88	UPC1365C 5.05	BD236 43	BUW81A 3.20	DECCA 100 8.50
AN7150	2.89	TA7120P 3.05	TDA2523 2.25	STK501 8.88	UPC1366C 2.85	BD237 40	R2008B 1.45	ITT CVC 20 7.75
HA1137	2.30	TA7129P 2.00	TDA2530 2.10	UPC41C 2.95	UPC1367C 2.85	BD238 39	R2010B 1.45	ITT CVC 25/30/32 8.00
HA1144	2.39	TA7130P 1.20	TDA2532 2.20	UPC554C 1.30	UPC1368C 3.76	BD410 50	R2540 2.35	ANTI-SURGE FUSES
HA1151	1.97	TA7139P 2.80	TDA2540 1.95	UPC565H3 2.10	UPC1370C2 3.80	BD434 50	TIP31C 46	A/S20MM 80MA 2.75
HA1156	1.97	TA7157P 3.00	TDA2550 1.70	UPC567H 3.00	UPC1373H 1.20	BD437 09	TIP32C 47	100, 160, 200MA 1.70
HA1166	2.65	TA7171P 3.40	TDA2581 1.25	UPC585C 1.40	UPC1377H 3.80	BD438 78	TIP33B 80	315, 400, 500, 630, 800MA 1A, 125, 16, 200 1.20
HA1197	2.30	TA7172P 3.40	TDA2590 2.20	UPC1009H 2.15	UPC1384C 5.50	BD707 11	TIP41C 48	800MA 1A, 125, 16, 200 1.20
HA1199	2.30	TA7176AP 2.90	TDA2593 2.30	UPC1017G 2.55	UPC2002H 2.20	BDX32 11	TIP42C 48	2A, 3.15, 4, 5A 1.35
HA1202	1.75	TA7193P 4.20	TDA2600 5.50	UPC1018C 1.15		BDX49 12	TIP2956 70	2, 3.15, 4, 5A 1.35
HA1211	1.87	TA7202P 3.00	TDA2611A 1.50	UPC1025H 3.30		BDX58 11	TV106/021.60	DY80 72
HA1306	2.97	TA7203P 3.00	TDA2640 1.80	UPC1026C 1.45		BDX58 11	TV106/021.60	DY80 72
HA1319	2.99	TA7204P 1.80	TDA3560 5.10	UPC1028H 2.15		BDX58 11	TV106/021.60	DY80 72
HA1322	2.10	TA7205AP 1.60	SAS560S 1.83	UPC1031H 2.40		BDX58 11	TV106/021.60	DY80 72
HA1325	2.30	TA7208P 2.20	SAS570S 1.90	UPC1032H 0.85		BDX58 11	TV106/021.60	DY80 72
HA1338	2.78	TA7210P 5.60	SAS580 2.40	UPC1035C 2.50		BDX58 11	TV106/021.60	DY80 72
HA1339	2.80	TA7222P 1.70	SAS590 2.40	UPC1042C 2.40		BDX58 11	TV106/021.60	DY80 72
HA1342A	2.33	TA7223P 3.15	SL901B 4.80	UPC1043C 2.45		BDX58 11	TV106/021.60	DY80 72
HA1366	2.30	TA7227 4.65	SN76226DN 1.05	UPC1156H 2.45		BDX58 11	TV106/021.60	DY80 72
W/W/R	2.30	TA7310P 1.70	SN7603N 2.05	UPC1168C 2.70		BDX58 11	TV106/021.60	DY80 72
HA1368	2.20	TA7313P 2.10	SN76013N 1.80	UPC1170C 1.55		BDX58 11	TV106/021.60	DY80 72
HA1371	2.57	TA7313P 2.10	SN76023N 1.80	UPC1176C 2.15		BDX58 11	TV106/021.60	DY80 72
HA1374	2.56	TBA120AS 70	SN76110N 90	UPC1177H 2.20		BDX58 11	TV106/021.60	DY80 72
HA1377	3.80	TBA120AS 70	SN76226DN 1.05	UPC1178C 2.20		BDX58 11	TV106/021.60	DY80 72
HA1386	4.20	TBA120U 1.00	SN76227N 1.00	UPC1180C 3.05		BDX58 11	TV106/021.60	DY80 72
HA1397	4.15	TBA395 1.25	SN76660N 65	UPC1181H 2.20		BDX58 11	TV106/021.60	DY80 72
HA11211	2.43	TBA396 85	STK0039 6.45	UPC1182H 2.35		BDX58 11	TV106/021.60	DY80 72
HA11221	2.77	TBA520 1.30	STK0040 5.95	UPC1183H 2.35		BDX58 11	TV106/021.60	DY80 72
LA1201	1.88	TBA530 1.00	STK0050 7.50	UPC1185H2 3.30		BDX58 11	TV106/021.60	DY80 72
LA1230	2.30	TBA540 1.27	STK0111 7.35	UPC1188H 3.30		BDX58 11	TV106/021.60	DY80 72
LA1365	2.25	TBA550 1.40	STK0114 7.65	UPC1190C 3.10		BDX58 11	TV106/021.60	DY80 72
LA2200	2.25	TBA560Q 1.60	STK015 7.15	UPC1198H 3.30		BDX58 11	TV106/021.60	DY80 72
LA3122	2.10	TBA750Q 2.45	STK016 7.45	UPC1200V 1.90		BDX58 11	TV106/021.60	DY80 72
LA3301	1.97	TBA800 80	STK020 9.05	UPC1208C 1.85		BDX58 11	TV106/021.60	DY80 72
LA3350	1.93	TBA810AS 1.15	STK032 11.32	UPC1211C 4.05		BDX58 11	TV106/021.60	DY80 72
LA4031	1.66	TBA820 1.40	STK035 12.67	UPC1215V 2.50		BDX58 11	TV106/021.60	DY80 72

TYPE	PRICE
BY127	10
BY133	15
BY164	40
BY179	80
BY210/800	30
BY223	86
BY27M	23
BYX10	20
BYX55/600	26
BYX71/600	78
OA90	07
1N4001-7	07
1N5401-8	12
BZ261-range	18
BZ290-range	11

TYPE	PRICE
DIODES	
ANT-SURGE FUSES	
NEW VALVES	
DIODES	
ANT-SURGE FUSES	
NEW VALVES	

TYPE	PRICE
SUNDRIES	
PYE IF GAIN MOD	7.85
E/W COIL G11	1.65
VA1104	70
PY500A	1.90
G8 TRANSDUCTOR	2.25
G8 ON/OFF SW.	1.40

TYPE	PRICE
TV ELECTROLYTICS	
DECCA 30(400/400)350V	2.55
DECCA 80(100/400)350V	2.90
(800)250V	2.90
PHILIPS G8(600)300V	2.00
PHILIPS G9(2200)63V	1.15
PHILIPS G11(470)250V	2.20
PYE 691/7(200-300)350V	2.10
RBMA823(2500/2500)30V	1.10
THORN3500(175/100/100/400)350V	2.25
THORN3500(1000)70V	85
THORN9000(400)400V	2.75

TYPE	PRICE
PUSH BUTTONS/TUNERS	
DECCA/TIT 4W	6.45
DECCA/TIT 6W	7.95
PYE201 6W	15.80
PHILIPS G8S/L	13.90
PHILIPS G8S/Q	12.00
HITACHI 4W	8.50
ITT CVC5 7W	9.40
ITT CVC8/9	12.80
PHILIPS G11 (TIP SW.)	25.80
1043/05TFK	8.30
U321 TFK	7.95
U322 TFK	7.40

Available also a range of 25A/B/C/D Transistors. Please or write for lists.

ORDERING
Please Add 50p For P/P U.K. Add 15% VAT To This Total. Export Orders - Cost. DELIVERY BY RETURN ON ALL STOCK ITEMS.


INCREASE YOUR PROFITS IMPROVE YOUR SERVICE WITH RELIABLE COST EFFECTIVE TEST EQUIPMENT

LEADER LCT-910A C.R.T. TESTER-REJUVENATOR

Our top selling instrument is designed to readily test the various characteristics and rejuvenation of both colour and B/W C.R.T.s.

- Tests for shorts and leakage between electrodes.
- Tests cathode emission characteristics.
- Separately checks condition of guns.
- Removal of shorts and leakage between electrodes.
- Checks heater warm-up characteristics.
- Rejuvenation of low emission cathodes with automatic timing.
- Super rejuvenation with manual control.
- Complete with tube base adaptors.

Size: H 230mm W 330mm D 120mm.

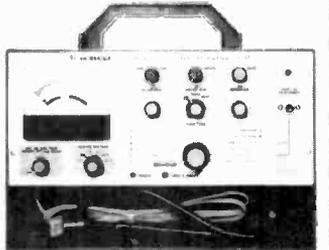

PRICE £186 + £27.90 VAT

THE VERY LATEST SC110A LOW POWER, FULLY PORTABLE OSCILLOSCOPE.

The new Thandar SC110A represents a break-through in oscilloscope development. The SC110A is ONLY TWO INCHES thick and weighs under two pounds, yet retains the standard features and controls of a bench oscilloscope.

FITS IN A BRIEFCASE

Full Sized Performance

- 10 MHz bandwidth
- 10 mV per division sensitivity
- Full trigger facilities are provided including TV frame, or TV filtering
- Runs on 4 to 10V DC via disposable batteries, re-chargable cells, or AC adaptor
- Size 255mm x 148mm x 50mm.

PRICE £165.00 + £24.75 VAT

Accessories: Carry Case £5.95 + £0.89 V.A.T.
 x 1 Probe £7.50 + £1.13 V.A.T.
 x 10 Probe £8.50 + £1.28 V.A.T.
 x 1 x 10 Switched Probe £10.50 + £1.58 V.A.T.
 AC Adaptor £6.95 + £1.04 V.A.T.

LEADER HIGH VOLTAGE METER EHT PROBE

Measures up to 40 K.V. D.C. with SAFETY BUILT IN METER

PRICE £28.00 + £4.49 VAT

BK'S REVOLUTIONARY DYNAMIC 'LOPT' TESTER

Revolutionary L.O.P.T. tester. Operates in dynamic mode which actually tests the L.O.P.T. under high voltage conditions without de-soldering or removal.

Size 75x100x40 mm. Supply 240V AC

PRICE £25.99 + £3.30 VAT

CRT TESTER-REJUVENATOR

BK'S C.R.T. TESTER-REJUVENATOR Tests and rejuvenates blue, green & red guns separately. Fitted with delta and P.I.L. sockets. Compact size 120x65x60 mm. Supply 240V AC

PRICE £32.00 + £4.80 VAT

HAMEG HM 203-4 20MHz DUAL TRACE OSCILLOSCOPE

SPECIFICATION:

- BANDWIDTH DC-20MHz
- SENSITIVITY CH1, CH2 2mV-50V/DIV
- TIMEBASE 40ns to 0.2S CM
- TRIGGER DC-40MHz Auto-Normal-TV
- CALIBRATION OUTPUT
- CH1 ADD AND INVERT FACILITY
- ALT/CHOP SWITCH
- LARGE RECTANGULAR SCREEN 8 x 10 cms.
- BUILT IN SEMICONDUCTOR COMP. TESTER
- SIZE 285mm x 145mm x 330mm.
- SUPPLY 110-125-220-240V AC 50-60Hz

2 YEAR WARRANTY

WITH COMPONENT TESTER


PRICE £264.00 + £39.60 VAT

Optional probes as above

U.K. Post Paid, Export orders welcome, please deduct V.A.T. and enquire for Overseas carriage cost. Barclaycard/Access orders welcome, or Cheque, Bank Draft, etc., with order please. Large S.A.E. for technical leaflets of complete range. Delivery normally within 7 days.

EAST CORNWALL COMPONENTS

ZENER DIODES		UPC1181H		MULTIMETER SPECIAL		MULTISECTION ELECTROLYTICS		VDRs, etc.	
400mW Plastic 3V-75V 8p each, 10/75p		UPC1181H	1.60	Russian type U4324 - (20,000 Ω P.V.)		THORN	850 100-300-100-15/300V	1.80	E295Z
1.3W Plastic 3V-200V 10p each, 10/10p		UPC1185H2	3.70	DC Volts: 0.6, 1.2, 3, 12, 30, 60, 600, 1200		1400	100-100-100-150/320V270	3.20	017
1.5W Flange 4.7-47V £1.40		UPC1212C	1.35	DC Curs: 3, 6, 15, 60, 150, 300, 600, 900		1500	150-150-150-100/300V	1.50	027
2.5W Plastic 7.5-75V £1.26 each		UPC1230H	3.90	AC Volt: M/A, 0.06, 0.6, 6, 60, 600, 3000		3000	1000/63V	0.56	E298DC
20W Stud 7.5-75V 87p each		UPC1367C	4.25	AC Curr: M/A, 0.3, 3, 30, 300, 3000		8000	1500/350V	1.70	E298ED
		UPC1378H	4.40	DC Resistance: 0.2, 5, 50, 500, 5000K		8000	2500-2500/63V	1.25	E298E
		UPC2002H	2.80	level dB: -10 to +12		8000	700/250V	2.10	A/258
		UPC2002H	2.80	Supplied with rechargeable batteries.		1000/70V	1000/70V	0.58	A/260
		UPC2002H	2.80	Price £12.00 incl. of p/p & VAT		9000	400/400V	0.25	A/262
		UPC2002H	2.80			9000	400/400V	0.25	A/265
		UPC2002H	2.80			9000	400/400V	0.22	A/266
		UPC2002H	2.80			9000	400/400V	0.22	A/267
		UPC2002H	2.80			9000	400/400V	0.22	A/268
		UPC2002H	2.80			9000	400/400V	0.22	A/380
		UPC2002H	2.80			9000	400/400V	0.22	

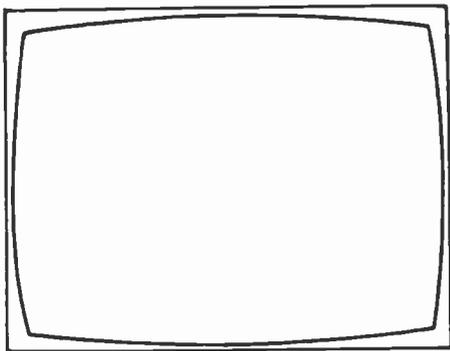

TELEVISION

EDITOR

John A. Reddihough

ADVERTISEMENT MANAGER

Roy Smith
01-261 6671

CLASSIFIED ADVERTISEMENTS

Barbara Blake
01-261 5897

COVER PHOTO

Our thanks to THORN EMI FERGUSON Ltd. who provided the photograph of their new TX100 chassis on this month's front cover.

READERS' PCB SERVICE

We have received notification from Readers PCB Services Ltd. (TV) of their intention to close the service down. Stocks of some of the boards that have been available are still held and those interested should enquire (for details see page 389, May 1984).

CORRECTIONS

The suggestion that tuner control units in the Philips G8 chassis (page 433 last month) can be replaced without removing the back is incorrect. Our apologies.

TV Test Pattern Generator Part 1, May. The right-hand half LS393 row counter in Fig. 2 should have been shown as IC3, not IC9. The clear pin of IC15 (pin 1) should have been included - it's connected to the 5V line. In Part 2 (June) BR1 should be shown as type KBL02 and IC2 as type 7805 in the components list.

Digital TV

In this digital age it's perhaps inevitable that TV sets should increasingly use digital techniques. The process started some while back with teletext, sophisticated tuning systems and remote control arrangements. It's taken a major step forward with the introduction of ITT's Digivision receiver in the UK. This carries out all signal processing between demodulators and the video, audio, field and line output stages in digital form.

This calls for considerable extra circuitry of course, though the component count is reduced since most of the circuitry required is contained in six v.l.s.i. chips. The whole operation is controlled by a sophisticated device (type MAA2000) which is referred to as the central control unit. It contains an eight-bit microcomputer (8049), an eight-bit/128 word EAROM (electrically alterable read-only memory), a decoder for remote control commands, a keyboard scanner for front panel controls (maximum 32 keys), a LED channel number display drive, a phase-locked loop to provide tuning at v.h.f. and u.h.f., a crystal-controlled oscillator and an interface section to drive the bus line that links it to the rest of the digital circuitry. The memory's capacity is sufficient to contain the tuning data for up to 30 channels and the factory programmed data for tube drive and timebase control (there's only one preset potentiometer in the set, for h.t. adjustment).

The video signal from the i.f. strip is AD converted by a device called a video coder unit (MAA2100). This also carries out RGB matrixing, beam current limiting, black-level clamping, c.r.t. cut-off control, brightness setting, white balancing and DA conversion to drive the RGB output stages. It works in conjunction with the MAA2200 video processor unit which is basically a digital colour decoder capable of NTSC or PAL operation. Two v.l.s.i. chips are used in the sound channel, an MAA2300 AD/DA converter and an MAA2400 audio signal processor. The luminance signal is handled in 7-bit form, the colour-difference signals in 6-bit form and the audio signals in 14-bit form. The MAA2500 deflection control unit receives 7-bit video and 3-bit bus control information and provides line drive pulses plus field output and EW modulator drives.

This group of six v.l.s.i. chips is complemented by an MEA2600 master clock pulse generator which operates at 17.73MHz (four times the colour subcarrier frequency) and an MEA2900 tuner interface i.c. to complete the Digivision line up.

A sophisticated system such as this tends to be expensive, at least initially with low volume production of the i.c.s. ITT have invested some £20 million in developing the system. It will therefore be used in up-market models to start with.

The introduction of the Digivision Model D1000 raises a number of interesting questions. Is there real advantage in going digital and how long will it be before others follow the same path for example. These need to be considered in the light of the fact that the Digivision system is undergoing considerable development. It's at present at quite an early stage in fact. Future developments already scheduled include the use of line and field stores, also digital horizontal convergence correction and digital geometry correction via feedback from the tube's faceplate. Digital horizontal convergence correction works by stretching the RGB scanning lines. The things that will really make a difference however are the line and field stores.

A field store will make it possible to display still pictures and provide selective enlargement (zoom), also picture-within-a-picture. It will probably be some time however before such a store can be produced at the sort of price that will make it feasible for use in TV sets - other than luxury models. Whilst it's nice to think that such features can be provided, one can't help wondering how much use they would get in practice. The whole point of television surely is to watch programmes as they develop. The line store is a more interesting prospect since it will make it possible to increase the number of lines displayed fairly economically, giving a much improved picture. The plan is to use a 2.2k byte RAM with a one and a half line storage capacity and interpolation to double the number of lines. This calls for 10MHz bandwidth RGB output stages, high resolution tubes and a line output stage able to operate at 32kHz.

The Model D1000, whilst having the advantage of digital signal processing, is unfortunately not adaptable for subsequent addition of these future developments. It seems to have been launched to test the market and gain experience of digital TV set operation in the field. For the present one could say that digital signal processing is a nicety. An analogue receiver correctly adjusted will give as good a display and be a lot cheaper. If and when digital TV chips become cheap, they will come into widespread use. Other semiconductor manufacturers are developing such chips, though ITT's decision in 1977 to go digital has put them ahead for the present. In practice it takes quite a time for technology to reach the point where it's suitable for use in mass-produced domestic products. We've seen in the past the gradual way in which analogue i.c.s have taken over from discrete circuitry in TV receivers. Even now the process is not complete - there are still sets with discrete audio and field output stages for example. It might also have been assumed that the SAW and ceramic filters would by now be universal, but you still find many a discrete coil in current chassis. Digital TV may become the standard eventually, but not for a good few years.

POST A PART ELECTRONICS

236 FURTHERWICK ROAD,
CANVEY ISLAND, ESSEX
Telephone 0268 690868
Telex 99305 ROSSER G.



TRADE COUNTER NOW OPEN

ORDERS DESPATCHED SAME DAY
ADD 60p P&P, THEN 15% VAT.
ADD POSTAGE FOR OVERSEAS ORDERS.
ORDERS WITH AEROSOLS, PLEASE ADD 25p PER CAN.

Thorn 100 20W (3500) R751 Safety Resistor	75p
Pye 713 Speaker 5" x 7" 701	1.00
Pye 713 Complete Tube Base Panel with Focus Slider & Leads	2.75
Pye 713 Control Knobs	4 for 50p
Tube Base Socket ITT CVC32	45p
Tube Base Socket Thorn 3000/8000 etc	50p
IC Inserter 16 Pin	50p
Large IC Extractor	50p
Crystal 4.43MHz	65p
EHT Lead & Cap for Split Diode Lopt	90p
Anode Cap	47p
Sanyo Anode Cap Assy + Lead. 12TCD-CT-1G	65p
DeGausse Thermistors PT37P. ITT/GEC	35p
DeGausse VDR E299D/HP230 3000/8000	25p
Capacitors Set of 4	1.90
Double Fuse Holder on Small Pax Board 20mm type	1.00
Single Fuse Holder on Small Pax Board 20mm type	50p
Direct Panel Mounting 20mm Fuse Clips	(pair) 15p
Single Fuse Holder on Small Pax Board. As per early 3000 mains input	6p
EHT Cable	Metre 25p
I3A Plugs	12 for 4.80
BF259 with Heatsink	14p
TP110 with Heatsink	40p
L129/130/131 Coil	25p
3MHz Ceramic Filter	25p
DL700 (Philips) Chroma Delay Line	1.00
DL50 Chroma Delay Line	1.00
19006A Lum Delay Line	1.00
3K5/9K Lum. Delay Line	65p
Plastic Cover for 3K5 SP8385	5p
TX9 Back Ground Control 10K	15p
FX9 Gain Control 100R	15p
1500 Metal Chassis Supports Pair	40p
Thorn 8K5 Focus Pot	2.40
Thorn 4000 Focus Pot	2.75
Thorn 1801 9W (3K5) R752	30p

SERVICE AIDS

Ambersil MS4 Silicone Grease	12oz 2.15
Ambersil Freezer	12oz 1.99
Ambersil Amberlube	6oz 1.89
Ambersil Ambertron	16oz 1.99
Ambersil Anti-Static Screen Cleaner	7oz 1.99
Ambersil Anti-Protective Lubricant	14.1oz 2.15
Ambersil Ambersilens Foaming Cleaner 13oz	1.26
Ambersil Circuit Lacquer	14oz 2.15

THICK FILM RESISTOR UNITS

3500 Thorn (5 Pin Connection) video	1.70
4000 Thorn (4 Pin Connection)	1.90
725/731 Pye (6 Pin Connection)	2.20
713 Pye (6 Pin Connection)	2.20

FUSES

20mm		1 1/4"	
50MA	10 for 70p	250MA	10 for 65p
315MA A/S	10 for 50p	750MA	10 for 65p
500MA	10 for 50p	7A	10 for 50p
1A	10 for 50p	10A	10 for 50p
2.5A	10 for 1.00	20A	10 for 50p
3.15A	10 for 1.00	50A	10 for 50p

Thorn Mains TX 3000/3500	7.50
Thorn Mains TX 8000/8500	10.00
Thorn S.O.P.T 8000/8500	3.50
Thorn Scan TX 3000/3500	6.00
Thorn EHT TX 3000/3500	6.00
Thorn LOPT 9600	12.00
Thorn LOPT 1615	7.25
Thorn LOPT 1590/91	7.25
Thorn LOPT 1690/91	7.25
Thorn LOPT 8000	9.80
Thorn LOPT 8500	9.80
Thorn LOPT TX9	9.85
Pye LOPT 713	10.00
Pye LOPT 725	9.85
Pye LOPT 731	10.18
Philips LOPT G9	8.80
Philips LOPT G11	13.75
GEC LOPT 3113	7.40
Diode Split LOPT AT2076/35	14.75
Sanyo LOPT AM-WM-21	6.75
Sanyo LOPT AM-WM-4	7.30
Philips LOPT G8	7.80
Sanyo LOPT (CW21) 4-2751-44700	5.00
ITT LOPT CVC5-9	9.60
ITT LOPT CVC30	8.75
ITT LOPT CVC45	9.75
Baird 8750	10.25
Baird 8752	10.25
Korting AZ9100	10.25
Korting B92-170	10.25
Korting AZ2101	10.25
Korting AZ2103	10.25
Korting ZTR1001	10.25
Siemens V1156	11.75
Siemens V1823	11.75
Zanussi BS2222	10.25
Zanussi BS2223	10.25
Salora FR0057	10.25
Salora FR0029	10.25

300 Mixed Resistors	1.50
300 Mixed Capacitors	1.50
150 Mixed Electrolytics	2.00
100 W/W Resistors	1.00
20 Mixed Conv Pots	1.00
40 Mixed Pots	1.50
20 Mixed Sliders	1.00
40 Mixed Presets	60p
20 Mixed VDR & Thermistors	1.00
20 Mixed Ferrite Cores	50p
100 Mixed Ceramic Discs	1.00
20 Mixed Valve Bases	1.00

AC128	39	BC172	9	BC559	8
AC131	40	BC174B	23	BC595	8
AC138	40	BC177	24	BCX33	22
AC141K	39	BC182L/B	12	BCX54	11
AC142K	38	BC183L	12	BD115	49
AC153	39	BC184L	13	BD131	30
AC176	33	BC187	24	BD132	46
AC178K/	33	BC204	15	BD133	59
AC128K	93	BC208	9	BD139	36
AC188	38	BC212L	9	BD140	38
AD142	1.18	BC213L	12	BD144	1.70
AD143	1.08	BC237	12	BD150	50
AD149	98	BC238B	8	BD163	98
AD161	32	BC238L	8	BD201	74
AD162	32	BC250A	15	BD203	78
AD263	1.05	BC251	8	BD204	99
AF127	45	BC252A	20	BD222	48
AF139	38	BC294	37	BD225	52
AF293	41	BC301	32	BD232	52
BC107	15	BC303	31	BD233	60
BC108	15	BC307	10	BD234	60
BC109	15	BC308	8	BD237	55
BC115	16	BC309	14	BD238	65
BC117	21	BC327	18	BD241	59
BC125	26	BC328	18	BD244	85
BC126	23	BC337	17	BD278A	81
BC139	27	BC338	17	BD386	88
BC141	34	BC347	17	BD433	71
BC142	30	BC394	8	BD437	83
BC143	31	BC454	8	BD532	1.20
BC147	12	BC465	8	BD589	1.20
BC148	12	BC456	10	BD677G	1.35
BC149	12	BC460	40	BD707	95
BC153	16	BC463	22	BD708	95
BC1540R	16	BC546	8	BDX10	93
BC154YL	16	BC547	12	BDY20	1.09
BC157	12	BC548	12	BDY82	99
BC158	12	BC549	8	BF137	20
BC159	15	BC557	10	BF153	20
BC171	9	BC558	10	BF154	25

INTEGRATED CIRCUITS

BRC1330	1.40	SN76013ND	1.26	TOA2002	2.80
BRC2064	1.00	SN76023N	1.80	TDA2030	2.10
BRC/M/200	1.00	SN76033N	2.00	TDA2522	2.10
BRC/M/300	1.00	SN76115	2.00	TDA2530	2.61
CA3060	1.58	SN76131N	1.58	TDA2540	3.50
LM1303P	1.48	SN76226N	1.25	TDA2581	3.00
ML231B	2.20	SN76227N	1.30	TDA2591	1.96
ML239B	2.00	SN76530P	1.30	TDA2611A	1.95
ML239B	2.96	SN76622N	1.00	TDA2640	2.90
ML1327AP	1.25	SN76660N	80p	TDA2690A	1.00
MC1358P	1.30	SN76666N	75p	TDA3580	6.00
MC1455P	18p	SN76744	1.92	TDA9503	3.48
MC14516B/CP	60p	TA7117P	1.90	TCEP100	2.90
SAA1025	7.20	TA7109AP	2.00	TEA1009	1.95
SAA1124	4.50	TAAG11	1.40	MC14426P	4.80
SAA5010	6.00	TBA120B	1.20	MC14514	4.50
SL432	1.80	TBA120C	1.20	UA758PC	2.66
SL1430	2.50	TBA120CQ	70p	UA1008A	2.60
SN15846N	60p	TBA120S	70p	JLN2165	1.25
SN74123N	65p	TBA120U	1.00	JLN2216A	1.25
SN74154N	1.40	TBA395	1.00	UFC1365C	5.75
SN76001N	1.40	TBA480Q	1.40	TC9488P	1.40
SN76110N	1.14	TBA510	1.90	SC9511P	1.40

Thorn 8/8K5 ex equip panels	untested	Thorn 3/3K5 ex equip panels	untested	Thorn 4000 PSU panel	ex-factory
PSU	2.88	PSU	3.75	Thorn 3K5 beam limiter board	2.50
FTB	3.75	LTB	3.75	new	1.75
Decoder	4.00	Video	2.50	Thorn 3K5 PSU bottom board	2.75
		Chroma	2.00	PC206 new	2.75
		IFB	2.75	Thorn 3K5 IF panel new	3.00
		Conv. 3K	1.75	Thorn 3/3K5 EHT & scan TX +	3.00
		Conv. 3K5	3.00	R2008B on alum chassis ex-	1.80
		Autovox Decoder FG/01	new	Thorn 8/8K5 damaged FTB for	1.25
		boxed	5.00	spares	1.25
		Thorn 4000 Convergence panel	ex-factory	Thorn 8/8K5 damaged decoder	2.25
		ex-factory	3.75	for spares	2.25

UHF TV Aerial for portable	50p	Coax Plugs	10 for 1.65
Indoor Aerial Parabolic Type Reflector	7.25	Band Change Switch Assy. Pye	40p
To Help Combat Ghosting Problems	2.50	Flush Mounting TV/FM Diplexer	1.00
Line Connectors	38p	Switched Flush Fitting Aerial Outlet	1.00

10 Spark Gaps	1.00
10-16 pin Quil IC Socket	90p
20 Assorted TV Knobs	1.00
10-16 pin Quil to Dil IC Socket	90p
100 Mixed Diodes	1.00
50 Mixed Mica Washers	65p
300 Mixed Resistors & Capacitors	1.50
10-16 pin Dil to Dil IC Socket	1.00
50 Electrolytics & 50 Capacitors	1.00
50 Mixed Poly Capacitors	1.00
30 Mixed Neons & Bulbs	1.00

BF167	24	BFR62	28	NKT276	20
BF173	28	BFR81	29	NKT453	1.65
BF179	32	BFR87	25	OT112	1.92
BF180	33	BFR90	1.74	OT121	2.08
BF181	30	BFR91	2.08	RI038	80
BF184	30	BF142	30	RI039	80
BF185	49	BF143	30	R2008B	1.40
BF194	16	BFX38	40	R2010B	1.10
BF195	16	BFY50	30	R2030	70
BF196	16	BFY51	34	R2265	1.30
BF197	15	BFY52	34	R2305	80
BF199	19	BRC116	1.50	R2322	50
BF223	15	BRC1893	1.43	R2443	25
BF224	18	BU105	1.00	RCA16446	1.25
BF225	19	BU126	1.10	RCA16599	1.20
BF226	20	BU207	1.05	RCA16600	1.40
BF240	9	BU208	1.15	RCA16799	1.13
BF241	21	BU208A	1.15	RCA18800	1.42
BF242	10	BU326A	1.30	RCA16902	1.38
BF243	20	BU407	1.70	SI299	2.25
BF244	28	BU408	2.76	S28000	1.25
BF245	28	BU500	2.30	S6080A/B	3.50
BF271	25	BU526	2.46	T6050V	1.30
BF274	11	BU807	2.94	T6052V	1.30
BF337	29	C1129	9	T9003V	1.25
BF338	34	C1172B	9	T9101V	1.45
BF352	40	ES386	54	T9063V	1.30
BF356	50	E9003	28	T9064V	1.10
BF391	21	E9005	25	T9039V	1.10
BF404	16	ME0404	10	TIC45X	50
BF422	47	ME412	10	TIC46	48
ME6002	10	TIC106C	40		
MJ2501	2.36	TIP29	42		
MJ3001	2.21	TIP30	42		
MJ182	47	TIP31	35		
MJE240	50	TIP32	43		
MJE520	50	TIP33	61		
MJE2955	1.40	TIP41	42		
MJE3005E	1.50	TIP42	45		
NKT241W	8	TIP110	61		
NKT241G	8	TIS91	25		
NKT241Y	8	ZTX550	30		

Pye 78+161	50p	EHT TRAYS	
Pye 147+260	50p	Thorn 3000	5.50
Thorn 56+1K+47+12	1.24	Thorn 8000	3.50
Thorn 50+40+1K5 60p	1.24	Thorn 8500	6.00
Thorn 128+16+1K7+	50p	Thorn 9000	7.90
116+462+126	50p	Thorn 9600	6.00
Thorn 120+72+300	50p	Thorn 900/950	1.50
RBM 250+14+58	63p	Thorn 900/950	1.50
(TV161)	63p	Pye 713 4 lead	5.83
Pye 3R5+15+45 (713)	90p	Pye 713 5 lead	5.97
Philips 2R2+682	90p	Pye 725	6.35
Philips 47R	52p	Decca Bradford	5.00
Thorn 350+20+148+	1.40	Baird 8750	7.10
1K5+317	92p	Korting AZ9100	7.10
Thorn 6+1+100	1.20	Philips G8 (520)	6.50
Thorn 3000 Metal	1.45	Philips G8 (550)	6.50
Thorn 8/8500 Plastic	1.45		

MULTISECTION CAPACITORS			
100+150+150	200+200+100	350V 55p	
220+47	350V 50p	200+200+75+25	
200+150+50 350V 60p	50+50+8	350V 00p	
200+200+100	100+50+100 350V 55p	100+150+50 350V 55p	
32+32+16	32V 52p	2500+2500 (Thorn) 8K	
100+50+150 350V 50			

Electronic Circuit Breaker

Ged Whitney, G8RSI

Some time ago I had the misfortune to encounter that bane of all service engineers' lives, the phantom fuse blower. The set in question was a Tandberg CTV3 and the fault was incredibly intermittent – the mains and/or h.t. rail fuses would blow at odd times irrespective of temperature or the time the set had been on test. At last, after a small fortune in fuses and near mental breakdown after replacing all the more likely parts, the fault revealed itself. I went to answer the phone – downstairs from the workshop – when “bang”! The set had failed in a big way... Curiously, the owner was on the phone at the time.

For Tandberg fans everywhere, the cause was the 0.91µF line scan correction capacitor C532 (of course). I also had to replace the line output transistor Q526, the mains bridge rectifier diodes CR701-4, the surge limiter resistor R702, the chopper transistor Q735, one of the chopper driver transistors Q734, the power supply efficiency diode CR735, the mains fuse F701 and the 230V h.t. line fuse F727.

During a similar tussle with a TX9 I decided to be smart (?) and use my G8 method. This consists of a 22Ω or 30Ω 10W wirewound resistor connected across the fuseholder in question. It works very well – with G8s. Splat! went the 22Ω resistor, hump! went the set, and I retired for a good strong brew.

The TX9 next devoured a 2A thermal cutout. I was going through the replace the obvious, ditch the rest then hang yourself routine when I got around to replacing the line driver transistor. Bingo! One more cured, and professor Quatermass spared a phone call.


Circuit Description

To assist with such problems, the circuit shown in Fig. 1 was devised. T1 is a current sensing transformer whose output is fed to a voltage-doubling rectifier (D5-6) whose output is in turn applied to a voltage comparator stage (of

sorts) based on Tr1. When the voltage at the slider of VR1 exceeds the forward voltage across D7/8 and the base-emitter forward voltage for Tr1, i.e. approximately 2V, Tr1 conducts. As a result Tr3 and, by regenerative action, Tr2 switch on. They hold each other in the conductive state until the reset switch S1 is closed to remove Tr2's base-emitter bias. With the switch circuit Tr2/3 in operation, Tr4 conducts to operate the relay. The latter removes the supply to the set, lighting the indicator instead. The use of the regenerative switch ensures that the circuit is held on when the excess current through T1 ceases.

Construction and Use

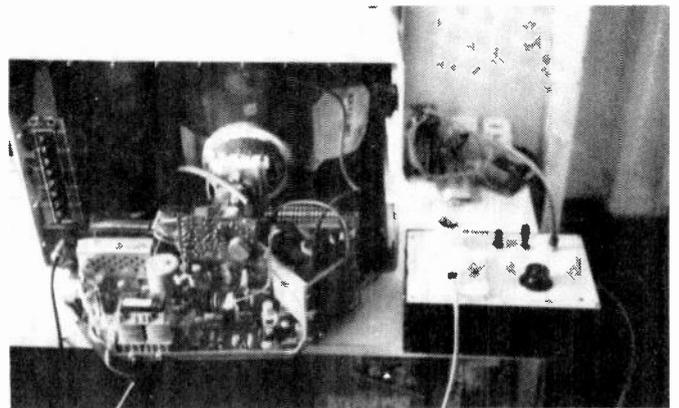The relay is not critical. A suitable type is the RS 348-784 (two pole changeover with 475Ω coil). The current sensing transformer consists of a Philips G8 heater transformer which, for the prototype, was rescued from the bin... The 6.3V secondary winding was completely removed – it can be sawn off using a hacksaw or, as in my case, the C type cores can be removed if loose (they fell



The circuit breaker in use with a Thorn TX9 chassis.

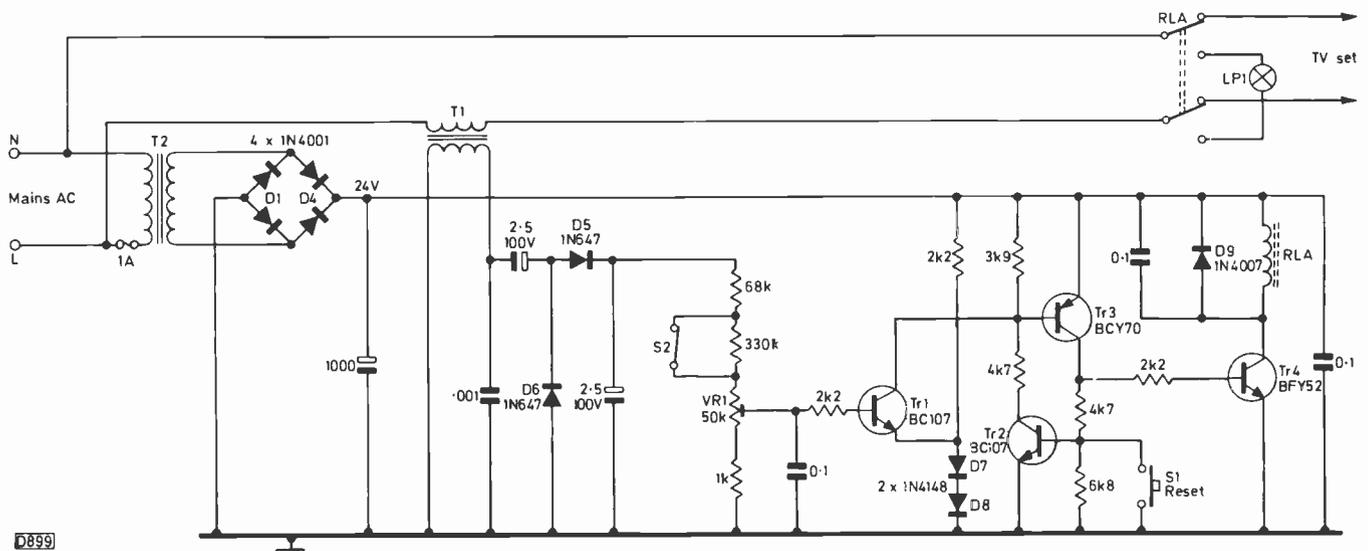


Fig. 1: Circuit diagram of the circuit breaker. Mains transformer T2 has an 18V 1A secondary winding.

out inside the set!). The original primary winding is retained to feed the voltage doubler circuit. The new sense winding consists of 14 turns of 7/36 PVC wire wound close over the outside of the retained mains winding. When complete, the whole core assembly can be secured with epoxy adhesive and held in a vice overnight. Construction of the unit is not critical though the usual safety precautions should be taken, i.e. no exposed live parts. Alternative transistor types could of course be used.

With VR1 and its series resistors of the values shown,

the maximum capacity is some 300W. Calibration was carried out using various sized bulbs, calculating the trip current from these. The setting varies from chassis to chassis of course. Set VR1 so that the circuit breaker just trips, then back it off a bit. The range at the high current end can be increased by opening S2 to reduce the voltage available at VR1. A three-way switch with extra resistors could be used for greater flexibility. The limiting factor is the relay's contact rating (10A with the suggested relay).

All at Fours and Sevens

Les Lawry-Johns

Have you ever thought about the numbers four and seven? Frankly, I'd never given them a thought until the other day, when a series of sets came in and the coincidence left me wondering. It's not every day that we're kept so busy at present however, so we rolled up our sleeves and prepared to do battle.

The KT3

The first set in line was a Philips KT3. It was reported not to work at all. So we dived straight at the right side power board and accused the 4.7Ω wirewound surge limiter of being open-circuit, thus removing the supply to the chopper. It was and a new resistor put things right without further delay.

The 9800

The second set was an Ultra 6749 (Thorn 9800 chassis). Apart from a degaussing click when it was first switched on there didn't seem to be much happening. So we asked the mains rectifier thyristor whether it was being supplied at its anode. It was. So the MR510 series diode was o.k. There were no signs of life at the other two legs of the thyristor however, and this led us to suspect the start-up circuit. We looked at the upper power board where the start-up circuit, transistor VT810 etc., lives. The start-up pulses are fed to the thyristor via R814 on this panel. R814, 470Ω. It was open-circuit of course, replacement restoring normal working.

Fancy That!

The next one began to make me think. It was a Bush set (Rank A823 chassis) with a faulty tripler. It had damaged the associated chassis-connected resistor. It's value? 470Ω. Then we had an IIT set, CVC5 chassis, suffering from poor focus. This was cleared by replacing the resistor that feeds the focus stick. Value? 4.7MΩ.

An amplifier suffered from short-circuit 2N3055 output transistors. As a result the emitter resistors had been damaged. 0.47Ω. I was afraid to lift the old Thorn 1500 on to the bench because I knew without a shadow of doubt what the cause of the loss of sync was going to be. R44 of course: 47kΩ.

Voodoo Numbers

While I was glad that the jobs were all simple for a

change, I was wondering when I'd encounter something without these voodoo numbers being involved.

So this chap struggled in carrying a CVC9. "Ah ha!" I thought. Tuner selectors no doubt. It wasn't. The problem was no results. We found that the h.t. fuse feeding the line output stage had blown. Naturally our first check was on the boost reservoir capacitor under the line output transformer. It was short-circuit. 0.47μF...

The Ferguson TX90

We haven't encountered many of these little sets so far. This one came in with the complaint of very poor sound. The nature of the fault suggested that the demodulator coil L104 was way off tune, and the presence of a 390pF polystyrene tuning capacitor in parallel with it was cause enough for us to replace this item. The sound then boomed out loud and clear, with only a trace of buzz which a touch on the core of L104 cleared.

Whilst looking at the circuit my eye was caught by the RGB output stages. Each transistor has three parallel 47kΩ resistors as its load, i.e. there are nine of them in this part of the circuit alone. There are four 47kΩ resistors in parallel in the boost regulator circuit, also four 270Ω resistors in series. The field output stage bias is provided by four 6.2kΩ resistors in series. We're told that this is all in the interests of reducing the total number of different components required in order to keep within the capabilities of the production line equipment. At least the equipment doesn't insist on components in the 47 series...

Mr. Neck Pain

At last the numbers game seemed to have come to an end. A rather strange gentleman next brought in a Pye CT218/1 (717 chassis). Although he was a strapping big fellow he started on about himself at great length, in this irritating sing-song voice, until I abruptly asked him what the hell was wrong with his set.

"Ah yes. I had trouble carrying it in you see because of my bad back. Haven't been to work for a long time because of it. Must see someone about it but I can't afford it. So I'm hoping the repair won't cost too much because my children will be visiting me this weekend and would like the television. My wife left me a couple of years ago, so I only see them every other weekend. Don't know why she left me. I've always worked hard. I'm supposed to be building a wall for this chap but my back won't let me. He keeps on about it..."

"Could I have your name please?"

"Oh yes. It's Nick Payne. That's right, Nick Payne. I told this chap that I couldn't build his wall this week. He got quite nasty about it. Said he'd been waiting for six months. But I can't help it if my back's bad.

"Do you build walls and things for a living then?" I asked, like a fool.

"Oh no. I'm a railway guard. Just do building work in my spare time. When I can that is, but I can't when my back's playing up."

"Well now, what's wrong with the set?"

"Well it sort of breathed a few times, then it went off. When I say breathed, it sort of fluttered - like it's been doing each time before it blew the fuse. I kept replacing the fuse, then put a stronger one in. Now it doesn't blow the fuse, it doesn't go at all, if you see what I mean Mr. Lorryjohns.

To cut a long story short he wanted the set there and then because of his children. So I lent him one for the weekend.

"Thank you Mr. Lorryjohns. Now could you carry it to my car? Because of my back you see."

The 18in. Pye

At last I was left to battle it out with the 18in. Pye. This and its close relative (Philips 570) are quite well known to me, so I didn't have any real misgivings. I checked the voltage-regulator thyristor with the ohmmeter. No shorts, but the 3.5Ω wirewound surge-limiter (part of the rear resistance assembly) was open-circuit. Check carefully for h.t. shorts. None. So I fitted a 3.9Ω, 17W wirewound across the defective dropper section, then checked the mains fuse. This should have been a 1.6A anti-surge type. It was 3.15A. I decided on a middle course and fitted a 2.5A fuse.

Crossing my fingers I switched the set on. It behaved quite nicely, and there was just over 150V at the end of the dropper. Then the over-voltage glow switch started to flash, indicating that the h.t. was pulsing. Time to switch off. While I was still looking in the back however there was this brilliant flash. Nearly blinded me as the mains fuse blew to pieces. Now there are only two things that commonly perform this caper. One is the mains filter capacitor, the other a shorted bridge rectifier diode. The filter was in order but two of the diodes in the bridge were short-circuit. Two new BY127s and a 1.6A fuse were fitted. Check again for shorts, avert eyes and switch on.

The set once more came on nicely enough. Then started to pulse. Next the fuse blew. This time the line output transistor was short-circuit. I replaced it with a BU208A (for convenience), and for good measure also replaced the BT106 thyristor. "That'll do it" I thought. Thought wrong. The glow switch still flickered as the h.t. pumped.

I checked the resistors in the thyristor control circuit, also one or two suspect capacitors. All perfect. But then the set did start up perfectly. So I wouldn't find a faulty part no matter how hard I looked. Something then stirred in my sluggish mind. I looked at the BR101 that triggers the thyristor. A gate controlled switch. Search for but can't find one. Why? The reason I don't keep something in stock is usually because time has proved that something else does the job. In this case a BRY56. Check connections and fit it. Bull's-eye!

The set behaved impeccably and now waits for Mr. Pain in the Neck to return my loan set, which so far he hasn't done. Perhaps he can visualise his bill.

next month in

TELEVISION

● SERVICING THE SONY KV2000UB

A comprehensive fault finding guide for this popular Sony set, covering both the Mk. I and Mk. II versions, by David Botto. Features of the set include a chopper power supply, GCS line output stage and discrete component colour decoder.

● STEREO TV SOUND

It looks as if four totally different stereo TV sound systems could be in use world-wide in a few years' time. There's more than meets the eye to the problem of adding a second sound channel to a TV transmission. It's not just a question of bandwidth: various interference problems make such systems difficult to engineer. David Looser explains.

● TV FAULT MECHANISMS

Several factors contribute to the development of faults in TV sets. These include weak points in circuit design, the use of underrated components, mechanical problems with component mounting, poor layout and inadequate quality control. It's a great help with servicing to be aware of these points. Tony Thompson explains how faults tend to develop in a chassis.

● VINTAGE HI-FI SOUND UNIT

Adding a decent push-pull audio output stage makes a great difference to sound quality. The problem is how to cater for the heater and h.t. current requirements. This plug-in unit provides a neat solution based on a couple of ECL80s. A Chas E. Miller vintage feature.

● TEST REPORT

The increasing number of transmissions, wanted and unwanted, that crowd the bands present problems for the aerial rigger. The ideal solution is to use a spectrum type meter. Eugene Trundle reviews the Urahm EP730FM panoramic field strength meter.

PLUS ALL THE REGULAR FEATURES

ORDER YOUR COPY ON THE FORM BELOW:

TO

(Name of Newsagent)

Please reserve/deliver the August issue of TELEVISION (£1), on sale July 18th, and continue every month until further notice.

NAME

ADDRESS


FOR FULL DETAILS ATTACH THIS SLIP TO YOUR LETTERHEAD AND SEND TO:
EAGLE INTERNATIONAL, PRECISION CENTRE, HEATHER PARK DRIVE, WEMBLEY, MIDDLESEX HA0 1SU

THE FANTASTIC EAGLE
TRADE-IN
OFFER!

10

BETWEEN
NOW AND
JULY 31st.

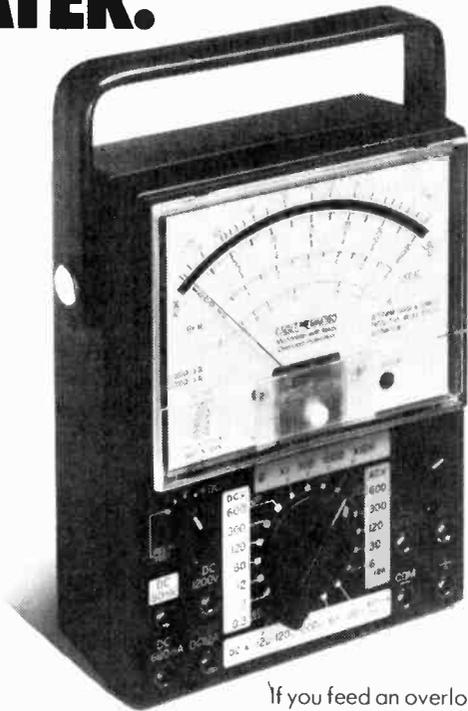**IN THE
EVENT OF
AN OVERLOAD
MOST METERS
WILL CUT OUT.
THIS ONE WILL CUT
BACK IN 5 SECONDS
LATER.**



If you feed an overload to most meters they will do just that—overload.

Even if it's only the fuse that's blown rather than the meter, it's still an annoying interruption to getting on with the job—assuming, of course, that the engineer has got a spare fuse.

The MM 150 however, is no ordinary multimeter.

When it is fed an overload a buzzer sounds and a warning light strikes. And the MM 150 goes one better. Internally, a clever relay disconnects the meter for five seconds giving the engineer time enough to disconnect the probes and check his mode/range selection.

We call this feature our Overload Protection Device.

Considering how much money and inconvenience it will save you, you may call it just plain common sense.

Needless to say, we back it as fully as we know how. With the Eagle 2-year guarantee.

For full details call Eagle on 01-902 8832.

EAGLE



CHROMOVAC

**QUALITY
REBUILDS**

**SPECIAL
OFFERS
THIS MONTH
ONLY**

Get on the hot-line today!

SUPERIOR QUALITY TUBES

051

DELTA RE-BUILDS

428 8777

most types of Inline Re-builds or
new ex-stock

★ 2 YEAR WARRANTY
★ 4 YEAR OPTIONAL

Delta Rebuilds

Up to 19"	£24
Up to 22"	£28
Up to 26"	£32
110° up to 22"	£32
110° up to 26"	£34
Low focus	£30
A47 342 New	£32

Delta only. Less 7½% 5+
Less 10% 10+ and over

Inline Rebuilds

Up to 22"	£40
Up to 26"	£45
Bonded Coil	+£5

ALL SIZES OF
NEW MONO TUBES
AT COMPETITIVE
PRICES

IN LINE TYPES EX-STOCK SELECTION NOT REBUILDS

370 HFB	£45	560 DMB	£62
370 HUB	£45	AXT 56-001	£62
420 CSB	£45	560 ATB	£65
420 EDB	£45	660 AB	£65
420 EZB	£45	A67-701	£65
420 ERB	£45	670 CZB	£65
510 UFB/A51-590	£55	H6817	£65
A51-570	£55		
A51-210	£55		
510 VSB	£60		
AXT 51-001	£60		
560 DYB	£62		
560 EGB	£62		
560 CGB	£62		

QUANTITY
DISCOUNT
AVAILABLE
Ask for details

★ OUR TECHNICAL DEPT. WILL ADVISE YOU ON
PROBLEMS YOU MAY ENCOUNTER ON FITTING
INLINE TUBES

DELIVERY: Ex stock items immediate dispatch on receipt of order.
Others allow 14 days.

CARRIAGE
£5 Singles. 2-3 £10. 4 £12
10 £15. 10+ Carriage paid
EXCLUSIVE OF VAT
TERMS
Cash with order

THE COMPANY WHO PUT HIGH STANDARDS FIRST

CHROMOVAC

CHROMOVAC LTD. UNIT 7, BEAR BRAND COMPLEX,
ALLERTON ROAD, WOOLTON, LIVERPOOL 25

Ask for MR BUTTERWORTH ON: 051-428 8777

Letters

RECEIVER NOISE

In "All About Field Strength" (April) it's suggested that a diode envelope detector produces a better signal-to-noise ratio than a synchronous demodulator. This doesn't agree with accepted theory nor with my own findings during research on teletext distortion. A synchronous demodulator effectively rejects one of the quadrature noise components, reducing the noise output power by half without affecting the signal.

With reference to the intermodulation distortion that occurs under overload conditions, I can confirm that forward acting a.g.c. systems can aggravate the situation. This causes a shift in the 6dB point on the i.f. response curve relative to 39.5MHz. As Brown and Glazier show in Telecommunications Volume 1 (pages 69-70), with a vestigial sideband signal this increases the second harmonic distortion.

G.E. Lewis, Senior Lecturer, Radio and TV Courses, Department of Electronics and Electrical Engineering, Canterbury College of Technology.

Harold Peters comments: Mr. Lewis is right of course – synchronous demodulators themselves are less noisy than diodes. It's the sets in which they are used that are noisier, as I was careful to say in my article. Customers complained about this. Whilst at Pye Ltd., Lowestoft in 1974 I measured the post-detector signal-to-noise ratio of close on a hundred sets of our own manufacture, together with a score from other UK and Japanese manufacturers. Fig. 1 in my article is based on the results. It ties up with subjective evaluation by our field liaison men, who used the then standard BREMA five-point impairment scale.

What came of it all? Nothing really. The diode has now vanished from the detector scene, and the once critical public seems to be quite content with the quality displayed by second generation copies seen through a well worn VCR.

REDIFFUSION Mk. 1 CHASSIS

The question of teletext lines on the picture with sets that use the Rediffusion Mk. 1 chassis was mentioned in Service Bureau last month. The official modification to overcome this problem is as follows. Change C612 from 16 μ F to 47 μ F (63V wkg) and R607 from 1.5k Ω to 3.3k Ω (0.5W 5%). These components are in the field output stage flyback damping network and are mounted on the output transformer (T601). Change R433 (15k Ω) to 12k Ω (0.5W 5%). This resistor is in the field oscillator timing network, on the timebase panel.

The thermistor mentioned (TH430) is in my experience a very common cause of ragged verticals and line flickering with these sets.

R. T. Rees, Senior Engineer, Just Rentals, Tonypany, S. Wales.

ALTERNATIVE GCSS

One of the problems those who handle Sony KV1810s have is that the gate-controlled switch devices used in

chopper and line output stages have to be replaced from time to time. They're expensive, costing about £10 each. We've recently come across a satisfactory replacement that's a lot less expensive (about £3). This is the SG264A gate-controlled switch used as the diode modulator driver in the Sony KV2704 (circuit reference Q808, part number 8-726-420-00). Sony don't recommend this as a replacement but we've found it to be one hundred per cent satisfactory – in fact we've been using it for over eighteen months without a single call back!

Our discovery of this solution to the problem has been a great help to us as we are only a small firm but have quite a few KV1810s out on rental. This tip may help other small shops in a similar position.

A. Christou, London N21.

THE GREAT PLUGTOP MYSTERY

I think we poor, hard pressed engineers sometimes tend to miss the obvious. Consider the mechanical arrangement of the 13A plug top. The live lead is taken to one side of the fuse mounting bracket while the neutral goes straight to its pin. This gets quite a considerable wagging each time the plug is inserted and removed. The live connection on the other hand is mechanically insulated by the fuse and holder. Solved!

G.C.C. Wride, Cheltenham, Glos.

SPECTRUM NO COLOUR

The no colour problem mentioned in the letters column last month when using the Sinclair Spectrum microcomputer with Grundig receivers also occurs with the Sony Model KV1820. In this case changing the value of R333 from 3.3k Ω to 4.7k Ω provides a complete cure.

Brian Francis, Tech. (C.E.I.), Plympton, Plymouth.

FOR DISPOSAL

I have for disposal a Philips Videomatic TV set Model 17TG306U which incorporates v.h.f./f.m. radio. It seems a pity to scrap this set, which is in excellent condition and working order. Anyone wanting the set will have to collect it.

L. Kinane, 38 West Lea Avenue, Harlow Hill, Harrogate, N. Yorks.

UNSOLDERING COMPONENTS

Mr. Treeby (letters, May) and others may be interested in the method used some years ago in the service department of one of our leading setmakers for removing components from a printed board, though not all service engineers may agree with doing the job in this way. The print side of the board was sprayed with a non-stick oil-based fluid from an aerosol – a Duckhams product. I've been unable to obtain this but find Three-in-One oil satisfactory – brush it on, taking the oil across the board to the nearest edge. You then melt the solder of the component to be removed, blowing the solder off with a compressed air jet. Lift the component out, clean off the oil and loose solder with a cloth and brush, brush over with grease removing solvent spirit, blow off dry, examine for any loose solder particles, then fit the new component.

The ITT CVC9 chassis' i.f. board, with those edge connectors, could be changed in four minutes. A very good method for removing i.c.s, but it won't work with another well known setmaker's double-sided print boards.

One last point: put a piece of cardboard down wind of the job – those molten solder blobs go a long way.

G.C. De Fraine,
Hartley, Nr. Dartford, Kent.

Video Recording on Tape

Eugene Trundle

Magnetic tape is far from being ideal as a recording medium for moving pictures. Compared with the relative simplicity of the first recording system, cine film, the practical difficulties involved in getting TV pictures on to and off tape are great indeed. The evolution of video recording techniques has been long and hard, the performance currently available from domestic VCRs and their professional counterparts representing a magnificent engineering achievement. One of the greatest hurdles in the path of the pioneers was the problem of accommodating the large bandwidth of a video signal within the constraints of the tape system. It's upon this aspect that we shall concentrate here.

For a reasonably detailed picture that's free from shading effects, a wide video bandwidth is required. Low frequencies define large objects, "backgrounds" and the overall brightness of the televised scene, the high frequencies representing sharp edges and fine detail. For a broadcast quality picture a bandwidth extending from virtually d.c. to over 5MHz is required, but no domestic tape system approaches the upper limit of this range – about 2.5MHz is the norm for the luminance component of the signal, this being extended by a further 1MHz or so in some machines when a monochrome signal is being handled.

This reduced bandwidth is necessary to limit the volume of tape required per hour of programme and keep the size of the cassette within reasonable limits. The less information recorded, the less storage space required, though it's possible to squeeze a greater playing time from a given size of cassette as the V2000 format and the VHS-LP mode show.

Tape Limitations

Having limited the luminance bandwidth we're left with a second, much more difficult problem that relates to the nature of the head-to-tape interface and the magnetic signal transfer system we're using. The recording head is of course inductive, which means that its impedance rises with frequency. If a 1V drive is required at 25Hz, a signal drive of many kV would be required at 2.5MHz to achieve the same flux density in the tape! This is a gross simplification, but it makes the point.

The same law works in reverse for playback. The playback head's output is proportional to the *rate of change* of the flux density in the tape. For an equal-energy recorded signal spectrum, the output from the head will be directly proportional to frequency: it will halve with each halving of the signal frequency recorded on the tape. Hence the well known 6dB/octave curve shown in Fig. 1.

Our 25Hz-2.5MHz example embraces almost 17 octaves (an octave is a doubling of frequency). Thus at 25Hz the output will be at $17 \times 6 = 102$ dB down on the level at 2.5MHz. Now 100dB is a voltage ratio of 100,000:1, so

even if we get an output of 1V from the head at 2.5MHz the output at 25Hz will have dropped to 10 μ V. One of the basic rules of a tape recording system is that 60dB or so is the best signal:noise ratio obtainable. So our 10 μ V, 25Hz signal will be buried under 1mV of noise – back to the drawing board!

Modulation

To make video recording practical, a carrier must be used for the signal – this is a common enough solution where the initial signal is not suited to the medium through which it's to be passed. If we use a carrier at say 4MHz, the upper sideband with our 25Hz-2.5MHz signal will be 4.6-6.5MHz, which is less than an octave. A full double-sideband signal represents 1.5-6.5MHz, which is just over two octaves. We've thus overcome the octave problem, and by using record/playback equalisation something approaching a flat overall response can be achieved.

What sort of modulation system should we use? The main possibilities are f.m., a.m. or p.c.m. (pulse code modulation). The latter two can be quickly dismissed. A.M. would be impossible due to its sensitivity to noise and the need for an a.c. bias waveform to overcome the nonlinearity of the tape/head transfer characteristic. P.C.M. would be ideal, but the very high bit rate required for good definition pushes the bandwidth requirements way beyond the capabilities of a domestic system, though professional digital VCRs have been demonstrated. This leaves f.m. as the obvious choice – with a lot going for it! Above a certain threshold, an f.m. system has a much greater immunity to noise than an a.m. one; and when it comes to recording a second signal (chrominance) simultaneously, the f.m. carrier provides an ideal source of a.c. bias for this.

Having settled upon the use of f.m. for our video modulation, we must optimise the noise performance by introducing a pre-emphasis system. The higher video frequencies occupy a disproportionate bandwidth in relation to the energy they contain: by boosting them prior to modulation and then restoring the balance by depressing them after demodulation, we get a useful reduction in overall system noise. Standard v.h.f./f.m. radio transmissions use this technique. It's taken a step further in most audio and video recording systems by using nonlinear pre-emphasis, i.e. the degree of h.f. boost is made proportional to signal amplitude – this is the basis of Dolby and similar noise-reduction systems.

FM Parameters

Returning to our f.m. system, we next have to decide upon the parameters to adopt – carrier frequency, deviation and modulation index. Each of these has to be a compromise – cost, performance and tape economy are

the trade-off factors. We'll take carrier frequency first.

To reduce the octave range, the higher the frequency the better. For a given writing speed (video head to tape velocity) however there's a definite upper limit. At the point where a recorded signal cycle on the tape is equal to the head gap, the output falls to zero. This is known as the extinction frequency (f_{ex}). In current domestic VCRs the head gap is about 0.3μ and with a writing speed of 5m/sec f_{ex} occurs at about 15MHz. This may seem to be very acceptable, but at $0.5f_{ex}$ (7.5MHz in this case) the response is 3dB down on the peak output (see Fig. 1) and is falling rapidly. Other losses occur at these higher frequencies – due to tape self-demagnetisation, head losses, gap effect, etc. – and these all combine to prevent a usable response much beyond $0.5f_{ex}$. So the band we have available extends to say 8MHz. If we set our f.m. carrier at half this frequency, about 4MHz, there will be equal room for upper and lower sidebands.

At this point let's consider some basic aspects of frequency modulation. The unmodulated carrier f_c sits centrally in the allocated channel, the modulating signal f_m being used to vary the carrier's frequency. The required result is obtained by employing a voltage-controlled oscillator whose maximum deviation is the amount by which the carrier frequency can be shifted by the modulating signal. This maximum deviation varies with different applications. For CB radio it's 2.5kHz; for v.h.f./f.m. radio broadcasting it's 75kHz. With the VHS video recording system the maximum deviation is 1MHz. It's worth emphasizing the difference between deviation and swing. Because an audio signal contains positive and negative excursions, it will move the f.m. carrier above and below the centre frequency. Hence the total swing is twice the deviation. For a video recording however, the centre frequency corresponds to the sync tip level. So the video signal can move the carrier frequency in one direction only – in practice upwards. Deviation and total swing are in this case the same.

Maximum deviation occurs when the modulating signal is at maximum amplitude – “peak programme” for sound systems, peak white for video. Thus deviation is proportional to the amplitude of the modulating signal. If this amplitude changes rapidly – due to high frequencies in the modulating signal – the rate of deviation will also be rapid. This has considerable effects on the sideband structure, as we shall see.

Modulation Index

The relationship between the modulating frequency and carrier deviation is known as the modulation index (M). Put simply, $M = \text{carrier frequency deviation} / \text{modulating frequency}$. In an entertainment channel the modulating frequency is continually changing with the sound or picture, so the modulation index is also changing. It will be at a minimum at the highest modulating signal frequency. As with deviation, the modulation index varies with

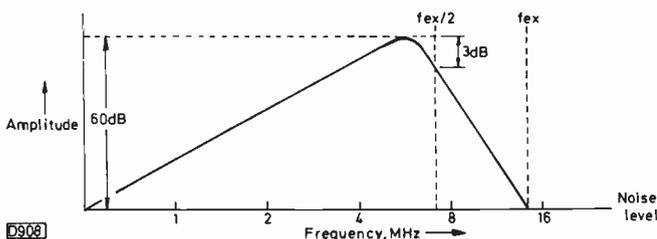


Fig. 1: The 6dB/octave curve, a plot of playback head output against frequency for an equal-energy tape recording.

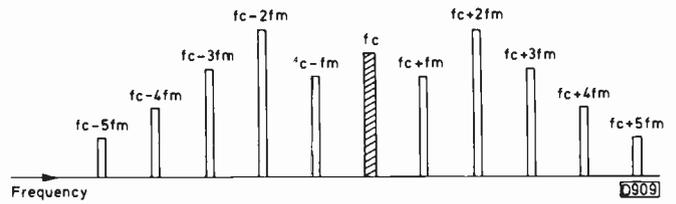


Fig. 2: F.M. system sideband distribution. The relative amplitudes of the individual sidebands depend on the nature of the modulating signal and the modulation index.

different systems. For v.h.f./f.m. radio the highest audio modulating frequency is 15kHz and the deviation limit is 75kHz. Putting these figures into our equation gives $75/15 = 5$, the minimum modulation index for this system. With our video recording system the highest signal frequency is around 2.5MHz while the maximum deviation is 1MHz. So M comes out at $1/2.5 = 0.4$. We shall soon see the significance of this low minimum modulation index.

Sidebands

All modulation systems generate sidebands. Their extent and nature depends on many factors. Simplest to understand is an a.m. system, in which just one pair of sidebands is produced by a modulating frequency, spaced at each side of the carrier frequency by a distance corresponding to the modulating signal's frequency. When more than one modulating frequency is present, corresponding additional sidebands are produced. A sideband group is thus formed as a symmetrical cluster at each side of the carrier frequency. The sideband limits are set by the highest modulating frequency present – for double-sideband transmission, as used for MW radio etc., the total bandwidth is $2f_m$.

With frequency modulation the situation is more complex. An f.m. system generates an infinite number of sidebands, stretching off into the distances at each side of f_c , spaced at f_m intervals from the carrier (see Fig. 2). In practice the number of these sidebands is limited by the bandwidth and signal/noise ratio of their path. What's of significance however is the number of these sidebands required to recreate the original signal adequately after demodulation. This depends on the energy carried in each individual sideband, and this energy distribution is governed by the modulation index. At $M = 5$ (the v.h.f. radio case) we need a total of 14 sidebands ($f_c \pm 7$) for acceptable reproduction, so the receiving bandwidth (the radio's i.f. channel) must be about 200kHz. That the energy distribution changes with M is demonstrated by considering a modulation frequency of 7.5kHz. Here $M = 75/7.5 = 10$, calling for 26 sidebands for adequate reception, again accommodated within a 200kHz window.

Sidebands beyond the “significant” range contain negligible energy and are discarded. For calculation of a practical system bandwidth, a general rule of thumb is $B = 2(f_d + f_m)\text{Hz}$, where B is the bandwidth, f_d the maximum deviation frequency (carrier displacement) and f_m the maximum modulating frequency. This represents a compromise between channel width and noise on the one hand, and theoretically perfect reception on the other.

When M is reduced below 0.5, the maximum deviation becomes less than half the maximum modulating frequency and virtually all the sideband energy is concentrated in the first sideband on each side of the carrier frequency. This suits our VCR scheme well in view of the limited bandwidth available. From the formula given

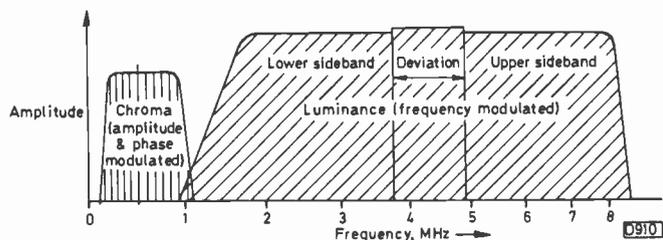


Fig. 3: Typical colour-under VCR recording frequency distribution.

above we get $B = 2(1 + 2.5) = 7\text{MHz}$, i.e. a luminance bandwidth of 3.5MHz each side of f_c . This is a spread of sidebands from say 1MHz to 7MHz, resulting in the familiar diagram shown in Fig. 3, where the f.m. deviation range is given against amplitude.

The reality is shown in Fig. 4. This is a spectrum analysis of the off-tape f.m. signal for a standard colour bar signal. It shows the f.m. deviation range, with the lower luminance sideband sinking to zero at around 1MHz and, on the left, the "chroma cluster". Note that a colour bar signal is less "busy" than a test pattern or a detailed picture. The latter would give rise to more "meat" in the sidebands.

Folded Sidebands & Harmonic Interference

When f_c is relatively low, it's important that no significant sideband spacing exceeds f_c itself. If this should happen the lower sideband will go below zero frequency. The energy in it can't just disappear – it will fold back into the real spectrum, sitting at a point representing the mirror image of its "ghost" – see Fig. 5. Another possible source of spurious sideband energy is harmonic distortion of the carrier waveform. A second harmonic of the carrier will appear at $2f_c$, modulated by f_m . The sidebands thus generated, especially $2f_c - f_m$, will fall within the system bandwidth. Fortunately odd harmonics of f_c give rise to sideband components beyond the spectrum of interest – which is as well in view of the basically squarewave output obtained from the i.c.-based and astable modulators used in VCRs. Third harmonic distortion of the first order lower sideband will give rise to a component at $3(f_c - f_m)$. This can beat with f_c – see Fig. 6.

Such spurious sideband effects will, if present, cause beat patterns or moiré effects on the reproduced picture.

Such spurious sideband effects will, if present, cause beat patterns or moiré effects on the reproduced picture.

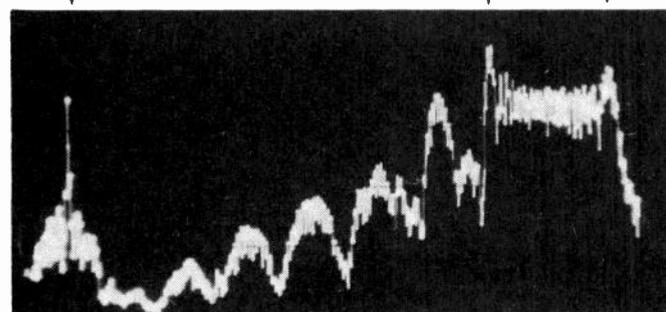


Fig. 4: Luminance and chroma signals and sidebands for colour bars on playback. This is for the Betamax system but others are similar. The modulator's deviation range can be clearly seen, along with the lower sideband energy distribution. The highly saturated colour bars give rise to considerable energy around the 687kHz down-converted colour subcarrier. Photo courtesy Sony (UK) Ltd.

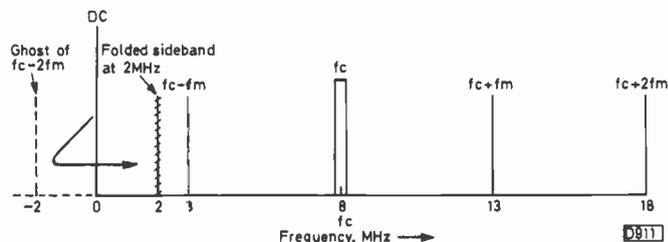


Fig. 5: Formation of a folded sideband, drawn to show the effect of a high-amplitude 5MHz signal modulating an 8MHz carrier.

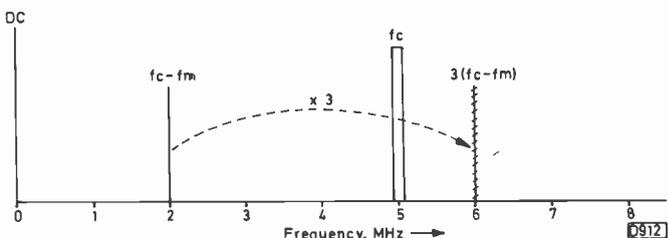


Fig. 6: Harmonic distortion of a modulated carrier: the third harmonic of the first lower sideband here gives rise to an interfering signal at 6MHz (f_c 5MHz, f_m 3MHz).

Increasing the carrier frequency solves many of the problems associated with sideband beats, because the interfering signals move away from the carrier (and thus out of the practical passband) at twice the rate at which f_c is increased. Professional VTRs use the "high-band" technique to take advantage of this. They also avoid in-band beat effects by using the heterodyne technique for f.m. modulation and demodulation. Typically the modulator takes the form of a voltage-controlled oscillator running at 50MHz. Its output is mixed with a 60MHz CW source to produce, after filtering, a very "clean" 10MHz f.m. carrier. During replay the 10MHz carrier and its sidebands are mixed with a 60MHz CW carrier to produce an f.m. signal at 70MHz. Filters before and after the 70MHz demodulator ensure the absence of beat effects. This elaborate system is capable of very linear and distortion-free operation.

No such luxuries as high-band operation and heterodyne f.m. can be afforded with a domestic machine however. These must depend on baseband frequency limitation and careful design of the filters and modulator to avoid the worst effects of sideband jangling – they do very well within the constraints imposed by cost considerations.

In most machines a switched luminance filter increases the bandwidth for monochrome operation, allowing the low-order f.m. sidebands into the 0-1MHz spectrum otherwise reserved for the colour-under signal. This greatly enhances the monochrome definition – in fact with the effect of the VCR's replay crispening circuit and the limitations imposed by the colour tube's shadowmask, it's often very difficult to tell off-air and off-tape monochrome material apart.

This "horizontal" elbow room is matched by a potential for "vertical" expansion of the recording f.m. signal – some but by no means all machines take advantage of this. As is well known, the f.m. luminance signal acts as the a.c. recording bias for the superimposed chroma signal when a colour programme is being recorded. Because of this, the f.m. carrier amplitude (luminance writing current) must be critically controlled to avoid driving the tape into magnetic saturation with heavily saturated colours (due to its f.m.

state, the luminance signal itself is immune to such limiting). When there's no chroma signal, we can gain extra benefit in noise performance by increasing the writing current, driving the tape to saturation on both half cycles of the f.m. carrier waveform. This can be done by linking the record colour-killer line to the record f.m. output or driver stage to bump up the writing current by 6dB or so.

Practicalities

This may all be very fascinating, but the serviceman may well ask whether it's a matter for the designer rather than himself. Apart from it being necessary nowadays to know the principles of how equipment works, it does become our business when a filter goes wrong and patterning or moiré effects appear on the screen.

To isolate the problem area, you need a known good prerecorded tape and another VCR with which it can be established whether the trouble is caused by a record or playback fault. For record problems a composite signal is required, containing both colour and an h.f. luminance component – the test card has these, but is not as good as a special pattern from a generator.

Most VCR signal filters consist of LC networks in a pi or ladder arrangement. In the case of a low-pass filter, the parallel capacitor components can come "off-earth", vastly increasing the upper cut-off frequency. More likely, an open-circuit filter will have been bridged by some well-intentioned soul.

Once you know what's going on, oscilloscope fault finding is not too difficult, with an r.f. signal generator hooked to the video input or a composite test pattern

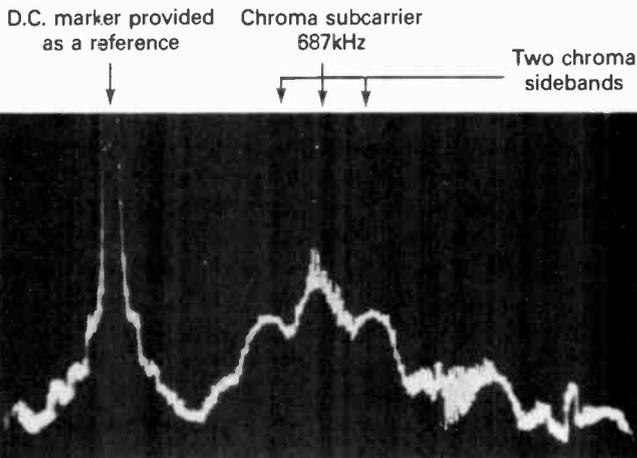


Fig. 7: Spectrum of a colour-under signal. This spectrum goes up to about 1.7MHz and shows the chroma subcarrier and its sidebands neatly contained within a total bandwidth of about 1MHz. Photo courtesy Sony (UK) Ltd.

input. In bad cases, vestiges of the chroma signal will be seen during record at the input to the luminance f.m. modulator. During playback, unwanted beat patterns should be eliminated by filters before and after the demodulator. If necessary, both should be checked.

Don't forget the chroma band restriction filter – excessive chroma bandwidth will also lead to patterning effects on luminance transitions and coloured areas of fine detail, due to beating between the outer skirts of the luminance and chroma sidebands. A photo of the chroma subcarrier and its skirts is shown in Fig. 7. It was taken during playback of a chroma-only colour bar pattern formed by removing the luminance signal during record.

CAPACITORS 91 5 x .0047/1500 AB23 Chassis 1.50 92 10 x 220MFD 16V Elect 0.50 93 10 x .047MFD 400V Mul Pol 0.50 94 5 x 4.7/100V C514 T3500 1.25 95 5 x 47/1000 Dublier 3.00 97 10 x 0.1/2000V W/E 2.00 98 5 x 1/250 Supp ITT etc. 1.50		68 Grundig 3010/1500 3.00 69 Thorn 3500 7.50 70 Thorn 8500 5.40 71 Philips G8 6.30 Elect 0.50 72 Pye 731 4.50 89 10 x Anti Track EHT Cap 2.00		179 TDA2532 2.00 180 TDA2540 1.05 181 TDA2541 2.67 182 TDA2580 3.28 183 TDA2571 2.15 184 TDA2591 0.98 185 TDA2593 2.23 190 TDA2800 4.00 191 TDA2811 1.24 192 TDA2840 2.35 210 ETR8016 2.28 211 ETR8016 2.28 212 BT78018 2.28 220 SL901B Int Circuit 5.00		030 GEC 2100 Hybrid 4.00 032 Thorn T x 9 Chass. 14.50 033 Philips KT3 8.00 034 RRI T24 Chass. 14.00 035 Sanyo CTP5101 9.50 037 Split Diode EHT Lead 1.35		SPECIFIC COMPONENTS 351 Thorn 1591 Speaker 2.00 352 Thorn 1600 Dropper 0.50 353 T x 10 Preset Drawer 3.00 354 T x 10 CRT Base Assy 4.00 355 3" Round BR Speaker 1.00 358 5 x Tho/3500 200 Conv. Pot. 1.00 359 5 x Tho/3500 50R Conv. Pot. 1.00 380 5 x TCE3500 A1 Rectifier 0.75 382 T9000 Rem. Receive Assy 5.00 383 T3500 Mains TX 5.00 384 T8500 Mains TX 7.50 385 T8500 (Plastic) Cut Out 1.50 370 Pye 731 Thick Film Resis. 1.50 371 Pye 713/731 Vis. Gain Mod. 6.50 372 Pye 731 3R3 50W Metal cld. 1.29 373 100k x3 Drawer Pset Alt Pye 731 2.00 378 Grundig 5010/8010 Vid Mod. 4.00 384 5 x 10R Phil. G8 Conv. Pot. 2.40 385 5 x 15R Phil. G8 Conv. Pot. 2.40 386 5 x Phil. G8 2k x2 Lin. Bright. 2.50 387 5 x Phil. G8 10k Log. Colour 2.50 388 5 x Phil. G8 47k Log. Vol. 2.50 389 G8 Plastic Mains Switch 0.75		390 G8 Metal Mains Switch 1.23 391 G8 Line Stor/Eq. 2.25 392 G8 R/G Symetry Coil 3.33 397 20 x 315A A/S 20mm Fuse 1.50 398 20 x 800MA A/S 20mm Fuse 1.50 399 20 x 25A A/S 20mm Fuse 1.40 400 20 x 2A A/S 20mm Fuse 1.40 401 20 x 1A A/S 20mm Fuse 1.40 402 20 x 125A A/S 20mm Fuse 1.40 403 5 x RRI T20 Tube Base 4.25 410 Phil. G11 E/W Load/ Coil 1.50 411 Phil. G11 Bridge TX 1.50 412 Philips G11 Speaker 1.00 413 10 x TDA2800 IC Holder 1.50 415 PALKT3 Speaker 1.50 435 5 x Decca 30 10R Fusible 0.50 436 5 x Decca 30 3R9 Modulohm 1.75 437 Decca 30 47k Vol + Switch 1.25 453 5 x 5R Universal Conv. Pot. 1.00 454 5 x 20R Universal Conv. Pot. 1.00 455 5 x 100R Universal Conv. Pot. 1.00 456 5 x 470R Universal Conv. Pot. 1.00 457 10 x 100k Tun/Pres TCE etc. 3.00 458 10 x 100k Tuner Preset G8 3.00 459 ELC1043/05 Tuner 6.00		460 ELC1043/06 Tuner 6.00 461 U321 New Tuner 7.95 462 U322 New Tuner 7.95 463 98003 Posister 0.99 464 98009 Posister 0.99 465 Mull.DL50 Delay Line 0.95 466 5 x VA1104 2.70 469 Cut Out Metal GEC 2100 1.00 470 5 x GEC2100 3 Lag Thermist. 1.00 479 5 x Gen. Purp. Ro- tary Switch 3.80 480 5 x Gen. Purp. Push/ Switch. 3.75 481 20 x Neons GEC etc. 2.25 482 5 x Univ. Aerial Skt. Kit 5.50 483 10 x Metal Coax Plug 1.70 484 Focus Unit T20 Type 1.25 485 Foc/Unit Thorn 8500 Type 1.25 486 4.43Mhz Crystal 0.40 488 10 x Ring Type Spk/ Gap 1.50 496 TX10 Chass. Focus Unit 7.00 497 De-Soldering Pump 3.50 498 1 x 10 Trimming Tool 1.00	
EHT TRAYS 50 ITT CVC 5/9 3.00 51 Decca 1730/1830 5.00 52 Decca 80 Series 4.50 53 GEC 2040 Hybrid 3.00 54 T1500 5 Stick 3.50 55 Thorn 9000 7.00 56 Thorn 1400 2.00 57 Philips G9 3.50 58 Universal ITT Type 4.50 59 5 x TV11 EHT Rec for PTV's 1.00 80 3 x TV46 EHT Rec Z718 1.00 61 ITT CVC 46 4.00 63 RRI T179 3.00 64 Pye 691/897 3.50 65 Pye CT200 4 Lead 3.50 66 Pye CT200 5 Lead 4.50 67 Korting 90 DGR Hyb 5.00		INTEGRATED CIRCUITS 140 5 x TDA440 3.00 141 5 x TBA120AS 1.80 142 5 x TBA540 4.00 143 5 x TBA540Q 4.00 145 5 x TBA580 3.50 146 5 x TBA81GS 3.00 147 5 x TBA9200 4.50 148 5 x TBA990 3.25 149 5 x TBA5200 4.00 150 5 x TBA530 4.25 151 5 x TBA950 4.50 154 10 x TCA270SQ 4.00 155 5 x MC1327Q 2.50 160 TDA1170 1.35 161 TDA1190 1.90 162 TDA1008A 1.45 164 TDA1035 1.83 166 TDA1044 2.23 168 TDA1190 1.90 167 TDA1142 0.90 172 TDA2002 1.80 173 TDA2020 2.50 174 TDA2030 2.15 178 TDA2523 2.35		LINE OUTPUT TX 001 Philips G8 7.50 002 Decca 30 Series 7.00 003 Decca 100 Series 6.50 004 ITT CVC 25/30/32 7.00 005 Philips G9 7.50 006 RRI T20 9.92 007 RRI A823 7.00 008 RRI Z718 18" 18.95 009 RRI Z718 20/22/26" 18.95 010 RRI A774 Mono 10.87 011 Thorn 1890/91 7.00 012 Thorn 1615 6.50 013 ITT CVC 46 6.50 014 Phil TX Chass. 5.00 015 RRI Ranger 1/2 5.00 016 ITT CVC 5/9 8.50 017 Philips E2 Chass. 5.00 018 Thorn 9000 12.80 019 Thorn 9500/9800 8.50 020 Polish 181 Mono 6.00 021 Thorn 3500 Scant 4.50 022 Thorn 8500 11.00 023 Thorn 1590/91 8.50 024 Thorn 1500 15KV 4.80 025 GEC 2040/2100 Hybrid CTV 4.00 026 Bush 161 Mono 5.00 027 GEC Single Std Mono 5.00 028 Pye 691 (wired) 5.00		PUSH BUTTON UNITS 110 Pye 713 4 Way 7.87 111 Pye 715 6 Way 11.95 112 Phil G8 Square 12.75 113 Phil G8 Sloping 14.88 114 Thorn 9000 2.50 115 Thorn 1615 4 Way 7.87 116 Decca 6 Way 8.95 117 Decca 4 Way 6.50 118 GEC 2110 6 Way 7.95 119 GEC 2136/7 Tapered 7.95 120 ITT CVC5 9.25 121 ITT CVC8 11.45 122 ITT 6 Way with V.C.R. 7.95 123 RRI A823 etc. 7.95 124 Hitachi 4 Way 7.95 125 RRI T20 6 Way 6.95		SMOOTHING CAPACITORS 80 220/400 CVC32/ T20 1.20 81 200+300 Pye 691 2.00 82 600/300 Phil G8 1.50 83 175+100+100 T3500 1.50 84 2000/100 Volt 0.50 85 470 Mfd G11 1.50 86 400+400 Decca 30 2.50 87 200+200+75+25 FTT CVC5/9 1.50 88 400/400V Tho 9000 1.50 89 4700/25 Thorn 1590/ 91 0.80		TRANSISTOR/DIODES 230 10 x AC128 1.50 235 50 x BC213L 2.50 250 10 x BD124 9.00 251 10 x BD131 1.80 270 10 x BU108 8.50 271 10 x BU208 7.50 272 10 x BU326 10.00 273 5 x BU205 3.75 290 25 x 2N3055 (Texas) 7.50 281 10 x 2N2905 (Equiv BC161/303) 0.50 290 10 x BT106 9.00 Thyristor 3.00 292 5 x BT119 4.50 293 5 x BT120 4.50 335 50 x BY127 Diodes 3.00 340 25 x TIP41A 6.50 341 25 x TIP41C 7.00			
<p>All components are A1 quality from prime manufacturers, and are dispatched by post same day as order received together with any refund due. All goods should be delivered within 4 working days.</p> <p>Please add 15% VAT and 90p P & P</p>													
<h1>QUICK SAVE T.V. SPARES</h1> <p>MUXTON HOUSE, MUXTON, TELFORD, SALOP. REG. OFFICE ONLY. CALLERS STRICTLY BY APPOINTMENT. UK ONLY. PLEASE QUOTE STOCK NO.</p>													

VCR Clinic

Reports from Derek Snelling, John Coombes, Philip Blundell, Tech. (C.E.I.), and Michael J. Cousins, T.Eng. (C.E.I.)

Timer Troubles

The complaint that a machine "won't make a timed recording" or that "the timer doesn't work" usually involves more detective work than fault finding. The only timer faults I've had have been with a Ferguson 3V22 where the stretched capstan belts caused failure to load, similar problems with the Panasonic NV7000, and off-tune Ferguson 3V29/30s. These were not actual timer faults of course: they were the result of the cold-start conditions that occur with a timed recording. If the cause of the trouble is not one of the above conditions, set the timer a couple of minutes ahead and check its operation – this is almost always correct. The next step is to see how the user sets the timer and to spot his error. As a guide, I've come across the following mistakes.

Setting for a twelve-hour clock when a 24-hour clock is fitted. Trying to set for a 24-hour clock when a twelve-hour clock is fitted. The timer set correctly but the clock set to the wrong day. On Ferguson machines, interpreting 130 as one hour and thirty minutes instead of 130 minutes. On the Hitachi VT8000/8300, setting the timer correctly then altering the switch-on time without resetting the length of recording (this reverts to twelve hours as soon as the start time is altered). Using a tape with the record protect tab removed (this is usually detected and indicated by most machines). Not setting the minutes of the start time on a Ferguson 3V35/36 (zero minutes was wanted) – this meant that the machine wouldn't allow the stop time to be set.

To be fair, manufacturers try to make timers foolproof. Many eject the cassette when the record tab has been removed for example, while on others the timer light flashes. Similarly if all the necessary information has not been fed into the timer, or the operate switch hasn't been set to the correct position, the timer light or the word timer will flash. The meanings of these indications are explained in the instruction books of course – but who reads them?

D.S.

Toshiba V31B

We've taken delivery of some Toshiba V31B VCRs during the last month or two. Only one fault has appeared so far, but it's occurred on four different machines – failure of the mains fuse for no apparent reason. In three cases the replacement fuse held, but in the other one two fuses went open (due, we think, to a faulty twin-plug adaptor). Has anyone else come across this fuse blowing problem and its cause – if there is one?

D.S.

Mitsubishi HS700

Another case of fuse blowing concerned a Mitsubishi HS700. The symptoms were no clock or channel change due to the absence of the standby 14V rail – F902 had gone open-circuit. The fuse can be reached after removing a plastic part labelled "remove to gain access to fuses", but as I tend to ignore labels I first attempted to get at the fuse internally, which is not easy. After changing the fuse the machine was tried out, whereupon the fuse again blew. The front on this model has a screen that covers most of

the control area: a careful check showed that it had come loose at one point, shorting R858 to chassis. Refixing the screen stopped the fuse blowing.

D.S.

Ferguson 3V29/30

A problem that's beginning to become common on early versions of the Ferguson 3V29 and 3V30 concerns the motor drive amplifier board mounted behind the control panel at the front of the machine. On later versions of these models the panel is combined with another one, so you won't find it behind the control panel. The fault is failure of the drum and/or capstan motor to rotate, usually intermittently. This gives the symptom that the machine fails to start or switches off when going. The cause is dry-joints on the transistors on this panel. Q236 is particularly suspect, but if in doubt resolder the lot.

D.S.

Horror Stories

A Sanyo VTC5000 came in with the complaint that there was no output from the r.f. output socket, not even the test signal. When the machine was switched on we found it to be dead. On removing the top the r.f. converter was seen to be disconnected: one of the phono plugs had touched the supply pin, shorting the always 9V rail with the result that fusible resistor R5207 had gone open-circuit. On replacing this and reconnecting the converter the original fault condition was present – it was cured by fitting a replacement converter. A phone call to the customer revealed that he'd tried checking the plugs inside in case they were loose and had forgotten to reconnect them before sending the machine in for attention . . .

That was nothing in comparison with the story of a Ferguson 3V22. A man had phoned to ask how much it would cost to have a new head fitted. He subsequently brought the machine in. Now we're always suspicious of people who bring in a machine for a specific job. After all, how do they know what's faulty? And if they do know, how come they can't repair it? Anyway the machine was put on the bench and switched on. Quick replay of a tape showed that the head could indeed be faulty, but on removing the top a series of horrors was revealed.

First, a bridge rectifier was dangling on four long wires by the mains transformer – the wires went to the place where the proper bridge rectifier should have been on the power supply panel. Then a light was noticed, also tucked away by the transformer. It was a bulb taped to two long wires that went off to where the cassette lamp should have been connected. A quick check showed that the cassette lamp and its holder were missing. Further checks showed that one of the video heads was broken, as was one of the record/playback switches, while all the guides had been screwed down fully.

Out of interest we checked the serial number against our records and found that the machine was one we'd sold in 1980. This was intriguing because the mechanics now fitted were of the later type introduced after August 1981. How all this had happened I don't know and probably never will. My guess is that the machine had been sent to

another "repairer" where it had sat for several months and been robbed right and left for spares, and had finally been thrown together from anything that could be found when the customer had insisted on having his VCR back!
D.S.

Ferguson 3V35/36

We've had several cases where the customer has complained of a jammed cassette in Ferguson 3V35/36 machines. What happens is that the cassette is inserted without the operate button being on. As the machine won't load, the customer pushes the cassette a bit harder. It then rides over the load switch which usually bends and jams in the screw holes under the cassette.
D.S.

Ferguson 3V29

A Ferguson 3V29 switched off after a few seconds operation in playback. With the top removed the cause of the problem was obvious – the head drum wasn't rotating. I've had this before, caused by a dry-joint on the motor drive amplifier board, but tapping this failed to bring any improvement. As all the motor drive transistors are mounted on the board I decided to start here. A quick check at one of the i.c.s revealed that the 12V rail was present, so meter checks were made on the transistors. All were o.k. Further checks with the machine on then revealed that one coil to the drum motor had no voltage on it. Tracing this back brought to light something I should have seen right away – there are two supplies to the board, the 12V rail for the i.c.s and a 13V rail for the drum motor. The latter was at 4V due to a defective regulator on the power board – transistor Q5 and zener diode D14 had to be replaced (the transistor had a hole blown in it!).
D.S.

Anyone see this?

Here's something odd. On April 20th a colleague noticed that the clocks on the two ITV teletext magazines differed by ten seconds. Did anyone else notice this? Has anyone an explanation?
D.S.

Sharp VC9300

This machine would play for three seconds after which the reel, capstan and head motors would simultaneously stop, leaving the tape threaded around the drum. If the play button was then pressed, the machine would play the tape perfectly to the end. The clue to the fault was a faint scraping noise from the underside of the deck just before the motors stopped. It was coming from the threading motor, the trouble being that the after-load switch was not always making contact. As a result, the microcomputer cut the power when the loading motor had been on for six seconds without the after-load switch closing.
P.B.

ITT 480 (Philips VR2020)

Here's a saga for you! The reported fault was a poor picture, but when I tried the machine it wouldn't play. The head was visibly going slow: after a few seconds the blocked rotor signal would be given and the machine would unthread. A replacement servo panel didn't help, and we then discovered that the head position pulses were missing. No current was passing through the optocoupler

LED due to the reel rotation LED being open-circuit (the three optocoupler LEDs are connected in series).

The next day we found that there was no E-to-E picture due to the U322 tuner not oscillating. A replacement put that right and it was then noticed that one of the clock digits was missing – due to a faulty CD4511.

The poor picture (on its own recordings only) was cured by fitting a new drum – the picture had looked as if it was covered in small squares. Next, after running perfectly all afternoon, the picture blanked out on playback. If the mute circuit was overridden by connecting pins 10 and 11 of the diagnostic plug, the resulting picture looked as if only one head was working.

The f.m. going into the luminance playback module was o.k., a replacement module restoring the picture. This time the fault was due to the TDA2740 i.c. As I write this the machine is running on soak. Is two days enough? . . .
P.B.

Hitachi Disc Player

We've had a couple of cases of the disc being jammed in the player. There's a hole in the bottom of the player to enable a jammed disc to be removed. In both instances the latch that holds the disc broke and the force required to remove the disc bent the metal runners connected to the caddy rail assembly. As a result, the caddy rail assembly had to be replaced as a complete unit.
J.C.

Sharp VC8300

If the cassette is ejected after insertion, check the drum belt which could be broken, stretched or off.
J.C.

Sharp VC2300

The trouble was "functions dead" with the tape trapped in the laced up position. All the mechanisms in these machines are driven electromagnetically, so the cassette can't be ejected even after the tape has been hand cranked back into the cassette. We found that there was 14V going to the 9V regulator transistor Q914 on the servo board but no output. A quick check showed that the transistor (type 2SA770) was open-circuit. Just to add to the confusion, there's another Q914 on the power board.
M.J.C.

Mitsubishi HS302B – and JVC

The fault was intermittent poor playback (as if one head was going low) accompanied by white streaks. When the covers had been removed I was amazed at the debris inside – bits of torn tape boxes, and nuts and bolts that had no connection with the machine. I came to the conclusion that the family's children had used the machine as a post box. When the foreign bodies had been removed, the mechanism and heads were given a good clean. After this the playback was good, so the machine was left for some time on soak test. Eventually the playback went low and streaky.

The f.m. playback waveform was scoped and, as expected, one output was very low. The problem was to decide whether the fault was to do with the preamplifier i.c. (IC201, AN6320N) and its associated circuitry or the heads/rotary transformer. Heat and freezer suggested that the i.c. was suspect, and when a replacement was obtained and fitted the machine ran for some hours before the fault reappeared. The real culprit turned out to be C204

(4,700pF) which couples the output from one head to pin 5 of the preamplifier i.c.

Since this fault I've had the same trouble with a couple of JVC HR7350s. The offending capacitors here are C272 and C273 (both 0.022 μ F). **M.J.C.**

JVC HR7700

A machine that obviously escaped JVC's quality control appeared in our workshop recently. The complaint was no sound on playback. On checking with a known good tape, sure enough there was no sound. The voltages on the audio board indicated that the machine thought it was in

the audio record mode. The commands for record, audio dub or playback come from the mechacon board, which was of the later type. It was found that the audio dub command was present at some 15V, putting the machine in the audio record mode even during playback. Checking through the circuitry produced no logical reason for some 15V being present at audio dub pin 23 on the mechacon board, but perseverance revealed that there was a leak between the print tracks leading to connectors 237 and 238. Connector 238 is the "not cue set" line, which is at approximately 25V regardless of the position of the cue switch. Scraping between the print restored the audio dub line to 0V, with the sound now normal. **M.J.C.**

Teletalk

Malcolm Burrell

TV servicing can be enjoyable. There's satisfaction to be had from restoring something to working order. But there's a difference between doing it for fun and doing it for a job. Many seem to have come into the profession years ago when it was the thing to "get a good trade" after leaving school. It might have been car mechanics, being a draughtsman or builder, but at one time TV was considered to be a good thing to get into. Unfortunately the wages and conditions nowadays leave a lot to be desired.

Those of us who for some misguided reason want to get good pictures and have developed a flair for this probably all too often feel those eyes watching us and hear the unspoken question "why does he spend so long on the job?" It seems that productivity and the need to maximize profit are considered to be more important than achieving reliability and just the right colour.

Whilst talking to someone recently I ventured the suggestion that much servicing was "just a con". The reply I was given was that some people want to be conned. This often seems to be so. For example, it's amazing how just before Christmas you seem to get a flood of calls of the sort that "it's not been right for months", "after two hours the sound fades" and "we wanted it right for Christmas"! If you're a field engineer the chances of putting such matters right are not very good – unless you take up residence. But if you call and make the right noises the customer is usually quite happy.

The wage problem has to be seen against the background that some firms go in for conning the public in a big way. I could go on about the case I was told about recently – of an engineer who was asked to look at a portable VCR brought in because the pictures were poor. He cleaned the heads – and got his £3 an hour. The job didn't take more than ten minutes, but the customer received a bill for £120, stating that a new set of heads had been fitted. Apparently the customer was happy – but how was he to know? In another case someone paid maintenance on a Telefunken set for ten years. The firm was happy to collect the money but reluctant to fit a new tube. It was simply boosted from time to time.

One has to acknowledge however that making honest servicing pay is difficult. Suppose that in one or two years' time someone with a Ferguson set fitted with the TX90 chassis pops in with a peculiar fault that takes four or five hours to find and put right. Could you really present an economic bill when maybe only an odd resistor had

changed value? Suppose that six months later the line output transformer failed, then maybe a new tube was required some months after that. It would be cheaper to buy a new set. Have we reached the point where most faults outside the guarantee period have become uneconomical to deal with?

Field Servicing

Field servicing has one or two advantages. You may sometimes get home early, you're relatively free – and just occasionally you might get to chat up someone really nice! There are loads of disadvantages however. For a start, because the nice man from Blogg's fixed the next door's telly in ten minutes flat you're regarded as not up to much if you have "to get the map out" to discover why the set's dead.

Most people take TV for granted nowadays. This applies to servicing as well. "My husband – he's a plumber – says it can't be much. Probably the picture valve." You sometimes want to say that if he knows so much about it why doesn't he fix the set himself?

You can leave the wrong impression behind in the rush to get from one job to the next. If you know the sets with which you're dealing, it's quite easy to come to a quick decision most of the time. You change say "R23" knowing that in 99 per cent of cases this will cure the fault. You even get to the stage where you've forgotten what R23 actually does! Field servicing becomes a matter of tearing from one place to the next and going through the motions. A great many faults don't even present themselves for diagnosis. Given that "the colour goes after three hours", you have a quick tap around, then check the reference oscillator adjustment and the tuning. In 75 cases out of 100 you won't have to go back again.

This tends to get rather boring. So much so that it comes as a relief to do a stint at the bench and deal with some awkward faults that require a logical approach. Perhaps this is why I tend to get furious when I see the field approach used in the workshop to get a high throughput. You know the sort of thing: switch on, get picture, can't be much wrong, quick twiddle then back to the car magazine.

Problems with Plastics

I had a problem with a Thorn 8500 chassis not long since: the brightness tended to fluctuate, and it seemed that the slider of the brightness control was intermittent. It transpired that the problem was due to the tag at one end of the control. Since the tag at the opposite end was unused, could I connect the wire to this and turn the control upside down? Removing the control panel assem-

bly, I was amazed to find that the plastic bracket that holds the control in place was disintegrating. I managed to effect a satisfactory repair, but wondered why the plastic should be in such a condition in a position where there's little stress.

Such problems are not uncommon on elderly sets. The on/off switch brackets on these and other sets frequently give up, and mounting by means of self-tapping screws in plastic cabinet fronts causes a lot of problems. The GEC C2110 series is notorious – either the switch falls inside or the push-button bank comes away. Repairs are often possible by removing the old mounting flanges and fitting long 6BA screws with spacers – provided there's no risk of them touching the chassis metalwork.

More drastic damage can suddenly occur. The plastic cabinet of a GEC set split almost in two one night. Not long ago a customer with a Thorn TX set found that the aerial socket had become loose – its mounting to the plastic chassis frame had broken.

Remember those little tuning ferrules used with RBM tuners? Nice and pliable when new, they became brittle and fell off after a few years' use. There are also component failures – for example the line output transformer used in the Philips 210 series chassis.

The use of plastics has caused a lot of problems in the past, maybe because ageing effects were not fully understood. One hopes that plastics technology has improved. The Thorn TX90 is a good set for example, but with so much plastic used in its construction one can't help wondering whether it might self-destruct after some eighty years' service.

It's fair to expect ten years' use from a modern TV set. How much longer should you be able to expect if it's been properly serviced?

The Reconditioned Set Market

Secondhand colour TV sets seem to be on offer at ever lower prices. A few years ago I looked into a shop where signs above a number of clean and well-appointed colour sets, at high prices, declared that they were fitted with reconditioned tubes. I've recently heard of "reconditioned" colour sets being on sale "from £35". This would be the price of a reconditioned tube alone. How is it all possible?

I once had cause to complain about a hybrid GEC colour set that had been sold a week or so previously with a three month guarantee. When it came back I found that there was enough dirt inside to grow potatoes in. The fault, no sync, was caused by the sync separator's 56k Ω collector load resistor having burnt up. In the process it had damaged the flywheel line sync drive coil. Not an expensive repair, especially with so many scrap panels available, but with a bit of attention to known stock faults the trouble could have been avoided. I was promptly told that these ex-rental sets were being "got rid of". The same set came back as a chargeable repair shortly afterwards. "Too old, not worth it" I said, and was quickly rapped across the knuckles again! Surely if you want to keep your customers the sets you sell should come up to a reasonable standard?

Even if you don't advertise the sets as reconditioned, the customers will tend to assume that they have been. A lot can be done without too much trouble. Inspection will reveal charred print and resistors and swollen capacitors, and you should know the things to look out for on particular chassis. Does the on/off switch feel right or does

it have a feeble click? Tube boosting is a dubious business and seldom lasts very long.

The law of the secondhand set jungle is to sell at ridiculous prices whilst making a handsome profit. In other words you use cheap labour to get the sets going then flog them in the hope that they won't go wrong during the guarantee period. An engineer I once knew maintained that technicians should always adopt a logical approach, and that the practice of bodging would degrade their skills. His worst fears seem to be coming to pass in this cut-price field.

Brightness Fault

My friend Len popped in one day with his Pye T173 portable (Philips TS7 chassis). "It's the brightness control" he said. The control worked, but you couldn't get sufficient brightness – only the highlights were visible. I'd not worked on one of these sets before, and first suspected inadequate first anode voltage. A quick check revealed that this assumption was wrong, but the tube's grid was at only 25V instead of 65V at maximum brightness. Furthermore the voltage at the slider of the brightness control increased as the control was moved from minimum to the mid-position, decreasing slightly as maximum was approached. I also noticed that the voltage at the top of the control varied. Obviously something was pulling the voltage down. The prime suspect was the slider's decoupler C188, but this proved to be blameless. With some trepidation I checked with the tube's base removed. Fortunately the result was the same.

After running out of further ideas I disconnected the slider and measured the voltage there. The same thing happened, so the control was clearly leaky. As I didn't have a direct slider replacement, the track was removed from the control for inspection – it's quite easy to do this. The cause of the leakage was then apparent – a film of carbon had formed at the bottom between the track and the wiper's track. Cleaning and reassembly provided a complete cure.

That KV1810 Again

My Sony KV1810 Mk. II is beginning to show its age but had been working well enough when I lent it to someone. It was returned in a damp van and when I switched it on all I got was a puff of smoke. This had come from R608, which is in series with the start-up gate-controlled switch Q602 and had gone open-circuit. The fuse had held and, as it turned out, the demise of R608 was a bit of a red herring.

The chopper drive circuitry was checked whilst powered by an 18V battery, with no mains input – the correct procedure with this set. Scope checks showed that the monostable circuit and the chopper driver transistor were working, but there was nothing at the gate of the chopper GCS Q603. I began to suspect the driver transformer, but a meter check proved that it was o.k. By chance I put the scope's probe on the transformer connections and got a waveform, so there was obviously a break in the print. Meter checks brought me to the connections to Q603 itself: the pads for the gate and cathode connections had lifted fractionally and cracked.

Repairing the print and applying a mains supply via a variac brought the set back to life. R608 had failed because with the set connected to the mains but no output from the chopper the start-up circuit can't switch off.

Spectrum-Monitor Interface

John de Rivaz, B.Sc. (Eng.)

The interface circuit described in the following article was devised after purchasing a Sinclair Spectrum microcomputer. To obtain the best display I decided to use a monitor with RGB inputs rather than employ a TV set and link the two at u.h.f. Using an RGB link avoids the modulation/demodulation and PAL encode/decode processes and the degradation they introduce. Unfortunately, inspection of the microcomputer revealed that RGB signals are present only within the ULA chip. YUV signals are available however, and pins on the microcomputer's multipin connector at the back are listed as being connected to these signals. An oscilloscope check revealed only low-level rubbish at these points, and on further investigation it was found that the internal wire links that connect the signals to the connector had been omitted. Installing the necessary links gave us YUV outputs at the connector and we then had the problem of converting these to RGB drives for the monitor. The V signal was alternating line by line, PAL fashion, and pulses of alternating polarity were present in the position oc-

cupied by the burst signal in a standard PAL waveform.

Being familiar with the Rank A823 chassis, I decided to use the SL901B i.c. that's employed for chroma signal demodulation and matrixing in the decoder of this chassis. The first problem was to find a way of using this chip with unmodulated signals. A look at the circuit (see Fig. 1) showed that if the U and V input pins (4 and 21) are earthed one half of each balanced synchronous demodulator will be rendered inoperative, enabling the other half to be used as a differential amplifier. These amplifiers have quite high gain, so the large outputs from the Spectrum had to be reduced. This is fortunate, as it enables the bias levels to be set correctly.

Obtaining sync pulses from the Y signal was straightforward. The signal from the Spectrum has positive-going sync pulses. An npn transistor (Tr1) with no bias produced negative-going pulses which are fed via an emitter-follower (Tr2) to provide a low-impedance output for the monitor.

The rest of the circuitry external to the SL901B is

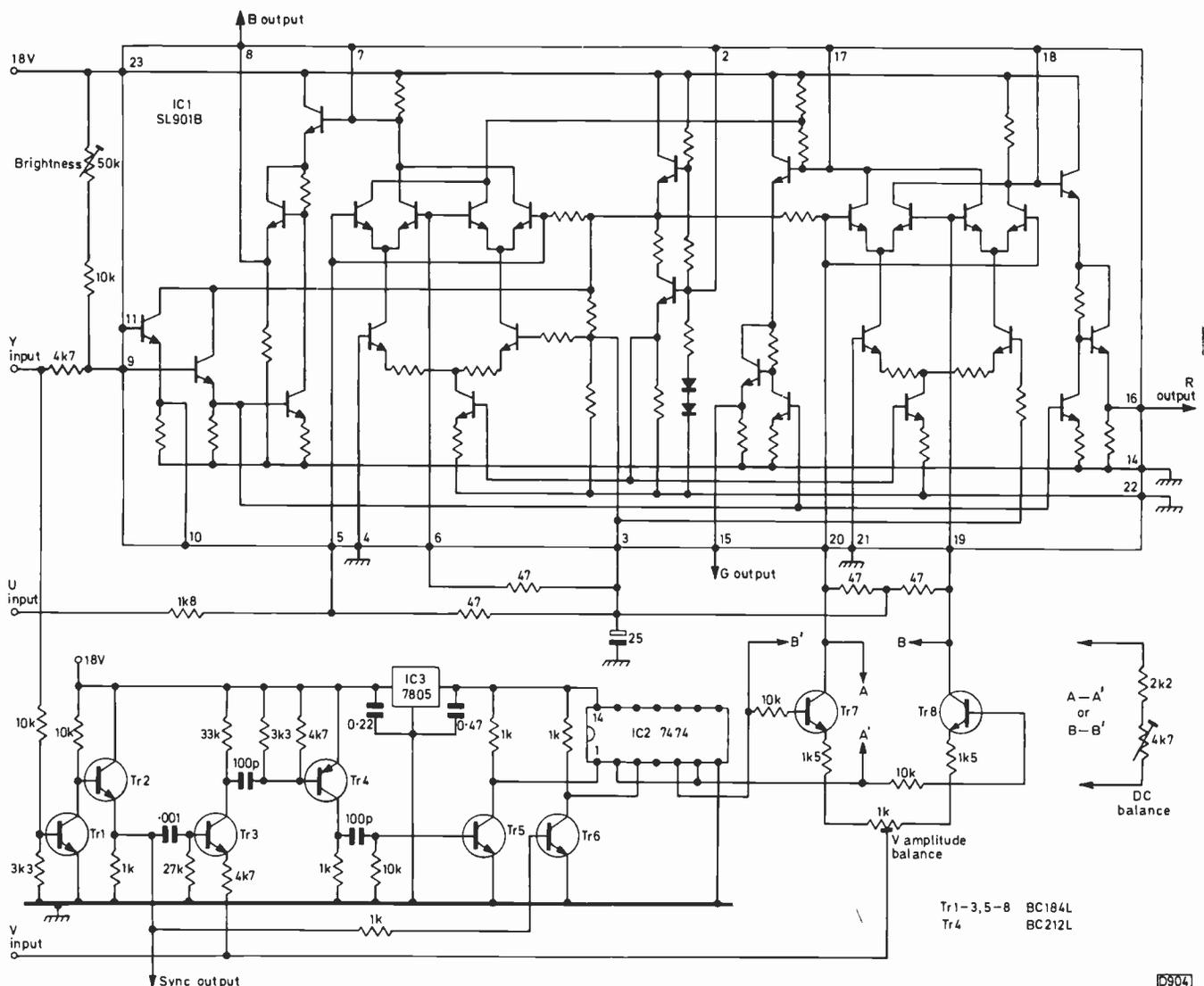


Fig. 1: Spectrum-monitor interface circuit for RGB drive.

concerned with removing the V signal PAL swings. This is done by feeding the V signal to pins 19 and 20 of the i.c. on alternate lines, via the switching transistors Tr7 and Tr8. The latter are switched on and off by the outputs from a D-type flip-flop in the 7474 i.c. For ident synchronisation, Tr3 is switched on during the burst periods by differentiated line sync pulses, thus passing the "V bursts" present at its emitter. The ident signal thus obtained is further processed by Tr4 and Tr5 and is then applied to the flip-flop's clear input – the flip-flop's clock input is driven by sync pulses after inversion by Tr6. To get the circuit working, some adjustment to the value of the resistance in Tr4's base circuit was required.

A d.c. balance control is necessary to prevent the switching waveform appearing at the output. Depending on component tolerances, this may have to be connected between either AA' or BB'. A V amplitude balance control is also provided. These controls can be set up by

getting the Spectrum to produce colour bars (there's a programme for this in the Spectrum manual), using an oscilloscope or observing the result on the screen. Brightness is controlled by applying d.c. bias to the SL901B's luminance input pin. The signal circuits are d.c. coupled throughout.

The signals from the Spectrum contain some computer noise, so it's not advisable to use speed-up capacitors to increase the picture sharpness.

The monitor I adapted was intended for use with TTL RGB signals, i.e. either on or off. The Spectrum has two levels of brightness however as well as colours. The TTL chip at the monitor's input was therefore removed, giving input via emitter-followers. These were biased by a preset brightness control which was disconnected. The monitor incorporates an 18V line which feeds a 12V regulator. It's derived from the line output stage and was used to supply the interface circuit.

Teletopics

MAJOR RENTALS MERGER

British Electric Traction, parent company of Rediffusion, has reached an agreement to sell the Rediffusion TV rentals operation to Granada. The combined TV rental group would have an estimated 19 per cent of the market. There are over 850 Rediffusion and Granada rental branches and it's expected that 100 or so would be closed following the merger. Job losses are put at some 700. The rental market has not been a happy one recently, with the increasing tendency to own both VCRs and TV sets outright. Added to this, Granada manages to make appreciably greater profits from its outlets than Rediffusion. From Granada's point of view benefits will come from economies of scale and the cash flow that investment in VCRs in recent years will produce in the future. BET is to retain the Rediffusion setmaking capacity.

PHILIPS' VHS POLICY

Philips' VCR policy keeps changing. Having decided to manufacture VHS machines, it was initially announced that the only W. European market in which these would be sold would be the UK. A new announcement states that Philips' VHS machines are to be distributed throughout W. Europe from the autumn. What next?

MONITORS AND RECEIVER-MONITORS

The growing use of home computers and video games has brought with it an increasing demand for monitors and receiver-monitors for display purposes. To meet this demand, several companies specialising in monitors and ancillary computer equipment have been set up in recent times while most TV setmakers have either introduced or plan to introduce monitors and/or receiver-monitors. Many users of home computers and video games units link their equipment to the TV display unit via the aerial socket. The disadvantages of this include drift (computer/games modulators are not exactly on a par with those used by the broadcasters!), patterning and bandwidth limitations. Similar problems arise with VCRs and discs. In all cases an RGB or composite video link gives greatly improved results.

The Ferguson Model MC01 14 in. receiver-monitor,

which is based on the TX90 chassis, is due for release at the end of August at a suggested price of around £229. In addition to the aerial socket there are separate DIN sockets for composite video and RGB inputs – linear or TTL (on/off) RGB inputs are accepted. To cater for the different composite video signal levels from different equipment, a preset video gain control is included. An added benefit of having separate input sockets is that several items can be connected to the receiver-monitor simultaneously. The MC01 senses the signal selected and switches over automatically. There's automatic sensing of sync polarity with RGB inputs, and sound signals can be fed into the MC01 with both RGB and composite video inputs. A 3.5mm headphone socket is also provided, and a specially designed battery adaptor with automatic adjustment for 12V/24V d.c. operation is available. The latter gives a typical running time of eight hours when used with a standard 40AH battery.

Because there's no standard connector for home computers, a range of leads to connect to most popular units is being made available through Ferguson dealers. A further range of leads provides connection with the Ferguson Videostar range of VCRs.

Ferguson will also be introducing a 12in. monochrome monitor, Model MM02, for business and home computer enthusiasts. This has an 80 character per line capability – the standard for word processors and some computers, as opposed to the 40 characters per line standard used for teletext and many low-priced computers. Technical features of the monitor include dynamic focusing to maintain clarity right across the screen, video rise and fall times of better than 20nsec for clean character edges (the average domestic TV receiver has video rise and fall times of around 100nsec), picture geometry better than 2 per cent and flywheel sync for good character verticals in the presence of noise and interference. The flyback time of only 8µsec means that up to 100 characters per line can be displayed if necessary. The tube has a P31 green phosphor screen which gives clear characters with minimal eye strain (tubes with alternative phosphors can be fitted, subject to negotiation). A further feature is multistandard (US/UK/Continental) operation to enable the monitor to handle a wide range of software/hardware. The price is expected to be less than £80.

Ferguson will also be introducing a cassette recorder, Model 3T31, designed specifically for use with microcomputers. The suggested price is £29.

An Advisory Service has been set up by Ferguson to aid

dealers and users with queries on computer-monitor compatibility and upgrading from one home computer to another. The telephone number is 01-807 3060.

ITT's first receiver-monitors were mentioned in this column last March. Several additions to the range have since been made. The 14in. RL2315, which has a suggested price of around £299, accepts u.h.f., composite video and RGB (both linear and TTL) inputs, with separate DIN sockets for the video signals and an easy to operate VCR/video/RGB switch. For those who require larger screen sizes, the CT2600/R is fitted with a 22in. tube and the CT2700/M has a 26in. tube. These two models use BNC sockets for the composite video and RGB inputs and in addition have an audio channel. The dot resolution is 420 with the 14in. tube, 540 with the 22in. tube and 630 with the 26in. tube.

Most new TV chassis have either as standard or as an optional extra a SCART socket to enable composite video and RGB inputs to be fed in. This 21-pin socket is also known as a Euroconnector or peritelevision socket.

CETEX

On the TV side the trend at this year's Consumer Electronics Trade Exhibition was towards isolated chassis fitted with SCART sockets to provide video and audio input/output connections, while the first models to be fitted with the new FS type tubes were shown. FST sets were included in the Mitsubishi, Panasonic, Philips, Pye and Toshiba exhibits. Philips and Panasonic were amongst the larger setmakers showing small screen monitors. Centrepiece of the ITT stand was the new Digivision Model D1000 – see separate note. The latest portables in the Philips range, two 12in. models (one with remote control) and a 14in. model, are fitted with the new TX3 chassis. On the video side, JVC were showing their Video Movie camcorder Model GRC1, the recorder section being to the VHS-C standard. This extraordinarily compact piece of equipment is just 13in. long and weighs less than 5lb. The Ferguson version is the 3V41. Price is around £1,000. JVC also introduced their first VCR featuring the hi-fi sound system – Model HRD725EK (Ferguson 3V42). These are top-loading machines with two speed operation. The Konica CV is claimed to be the world's smallest and lightest colour camera, and can be used with most VCRs. The compact design has been achieved by mounting the $\frac{1}{2}$ in. Cosvicon tube vertically in the camera's handle: the optical system consists of a 3:1 manual zoom lens, through-the-lens viewfinder and a mirror/prism arrangement to deflect light on to the tube's faceplate.

TUBE SIZE SPECIFICATION

The tradition of specifying tube sizes by the overall diagonal measurement in inches is to be phased out. The change follows an international agreement amongst tube makers to use the visible picture diagonal as the standard measurement for screen size, and pressure from trading standards officers who have argued that the present practice infringes the Trade Descriptions Act (Philips were fined a nominal sum when a test case was brought last year). The packaging for sets fitted with standard types of tube is now supposed to show the diagonal visible screen size in centimetres in brackets, with the word "visible" or the letter "V", following the inch measurement. For example, a 16in. set should be described as 16in. (38cm V) or 16in. (38cm Visible). This interim arrangement is

expected to last for two or three years. The aim with the new FS tubes is to use centimetres only, though inch sizes are being widely quoted at present.

DIGIVISION IS HERE!

CETEX saw the UK launch of the ITT Digivision system in the form of their 26in. Model D1000. The set is unique to date in that after detection the signals are AD converted and processed in digital form, under the control of an eight-bit microprocessor central control unit, then DA converted to drive the deflection output circuits, the c.r.t. drive and the audio output stages (the set is stereo capable of course). The basic system was described in our November 1981 issue. Model D1000 is a full-specification set with infra-red remote control, teletext, 15W audio output per channel from twin three-speaker systems with double chamber bass reflex loading, and sockets for AV and RGB inputs and headphone/audio outputs.

From the servicing point of view, how do you set up a receiver with only one preset potentiometer? Adjustment is done digitally with a service computer, which ITT call an "electronic screwdriver". The service computer is linked to the receiver via a socket and issues commands to the MAA2000 central control i.e., allowing the service engineer to change the data stored in an EROM. When re-programming is complete, control is returned to the MAA2000. The c.r.t. drive conditions, the timebases and picture geometry can all be set up in this way. The SP010 service computer does not come cheap however – it costs £125. To offset this ITT have announced a special introductory offer: with each Digivision set purchased, the dealer will receive a £25 voucher towards the cost of a service computer.

POLAROID-TOSHIBA 8mm VIDEO DEAL

The US photographic products group Polaroid is to market an 8mm portable video system produced by Toshiba. It's due for release in the USA this summer.

DBS UP-DATE

The government has announced that legislative changes will be introduced to enable a DBS service to the UK to start in the late 80s. The cost will be around £400m and the service will be operated by a consortium comprising the BBC, ITV companies and outside operators. There are likely to be three channels, one for films and the other two with mixed BBC/ITV programming.

Where is the money to come from? The BBC is to be barred from using extra cash obtained through licence revenues, while the ITV companies will be unable to count losses against their annual levy. The government seems to think that the consortium will be able to raise the required risk capital: as an inducement it will be given a three-year monopoly, while the IBA will be authorised to extend the franchises of ITV companies participating in the scheme. It's understood that the BBC will have a 50 per cent stake in the venture, with the ITV companies having a 30 per cent stake and the rest held by one or more outside companies. At the end of the three-year monopoly, the IBA will be able to advertise for participants in a competitive DBS service.

Agreement has been reached between the Luxembourg government and a private consortium to establish a satellite TV distribution company called Societe Luxembourgeoise des Satellite. The plan is to beam 16 TV channels over Europe, mainly for cable networks but

also as a DBS service. The project is called Coronet and the satellites will use the Luxembourg orbital position (19°W). It's hoped to launch two medium-power satellites late next year. Financial backing is being sought in several European countries, including the UK.

HITACHI HIRWAUN

Radical changes have been introduced by Hitachi at the Hirwaun TV factory in an effort to build up production and change the loss making plant into a profit earner. The labour force is to be reduced by 500, from 1,300 to 800, and the production lines will be modernised. As in Toshiba and Sanyo's UK plants, there will be a single-union agreement with the EEPTU. A "company members board" is to be set up to settle disputes without resort to strike action or lock-outs, and a "single status" employment policy will be introduced, i.e. a single canteen, common working hours and uniform etc. A seven per cent wage increase has been agreed.

THOMSON IN UK

TV sets and VCRs produced by the French government owned consumer electronics firm Thomson are to be marketed in the UK by Heron Electronics Ltd. Thomson is Europe's second largest consumer electronics manufacturer (after Philips), with substantial interests in W. Germany - its subsidiaries include Saba, NordMende and Telefunken.

POCKET COLOUR TV SET

The Japanese electronics concern Seiko has demonstrated a pocket colour TV set with a 2in. screen. Marketing is expected to begin in Japan and the USA later this year. The set has a liquid crystal display and weighs 450 grams. A price of around \$500 has been suggested. Seiko's wrist-watch sized monochrome TV set, which also has an LCD, was introduced in December 1982 and will be superseded by the new colour set. Some 70,000 of the monochrome sets have been sold.

VCR SERVICING COURSES

Steve Beeching is planning to run a further series of his VCR servicing courses this autumn. Enquiries should be sent to the Newark Video Centre, 108 London Road, Balderton, Newark, Notts.

NEW PLESSEY TV TUNING SYSTEM

The Plessey SP5000 i.c. is now in volume production: used in conjunction with a varicap tuner, it forms a complete phase-locked loop frequency-synthesis tuning system intended primarily for TV and cable TV applications. External circuitry is reduced to a minimum by incorporating a 1GHz prescaler, a multimodulus divider, storage register, crystal reference oscillator with divider chain, phase comparator and drive circuitry in the single chip, which requires only a 5V, 50mA supply. The circuit can select frequencies from 30MHz to 1.024GHz in 62.5kHz steps.

The SP5000 is controlled by a four- or eight-bit microprocessor which also decodes the remote control and keyboard commands. Plessey offer a series of PIC1655 microprocessors for this purpose to ensure that all common broadcast and cable TV requirements can be met. The microprocessor also controls a memory i.c. if program storage is required, and can drive two seven-segment displays directly for channel or programme number.

The SP5011 and SP5012 i.c.s are in production for cable TV use, offering up to eight options of up or down conversion to frequencies appropriate for connection to a TV receiver's aerial input: these are fixed frequency options of the SP5000, with an aluminium mask variant, so that no microprocessor is required.

Further details are available from Plessey Semiconductors Ltd., Cheney Manor, Swindon, Wilts SN2 2QW.

TELETON'S MOVE

Teleton Electro (UK) Co. Ltd. has moved from Westcliff-on-Sea, Essex to Hatfield, Herts. The new address is 154 Great North Road, Hatfield, Herts AL9 5JN, telephone number 070 727 2841.

VCR PROTECTION

An ingenious device has been introduced by Videotek Ltd., Unit 20/21, Royal Industrial Estate, Jarrow, Tyne and Wear NE32 3HR for the protection of unattended VHS VCRs. The device is in the form of a cassette which can be loaded into the machine. It's locked on partial insertion and can be removed only after being unlocked - 1,000 key patterns are available. The built in tremor switch triggers a 98dB alarm if the machine is moved or disturbed. The retail price is around £24.95.

SET TOP AERIAL WITH AMPLIFIER

Electronic Mailorder (Bury) Ltd., 62 Bridge Street, Ramsbottom, Bury, Lancs have introduced a combined set top aerial and amplifier at £9.70 plus 30p post and packing. The amplifier is a tuned type that may require adjustment - this is easily done by means of a small trimmer in the aerial base. The amplifier runs off eight HP3/AA type batteries which will last for about a year if the amplifier is switched off after use.

SATELLITE TV COMPANY

A new UK company, Satellite TV Antenna Systems, has been set up to develop and manufacture satellite communications equipment. The technical director is Steve Birkil, who has designed what the company refers to as a "radically new" receiver for which a number of orders have already been taken. Production has started at the company's factory in Builth Wells, Powys: initial production will be mainly for the US market, though European orders are also expected.

SLOW-SCAN CCTV SURVEILLANCE SYSTEM

The latest introduction by Frowds Ltd. (4 Northarbour Road, Cosham, Portsmouth, Hants PO6 3TJ) is Surveyorscan, a slow-scan TV system for operation via the telephone network. It was designed and developed by British Telecom and is being manufactured under licence and marketed by Frowds. Surveyorscan gives the user an unattended surveillance capability to virtually any site worldwide via the normal dial-up telephone network. Up to four cameras can be used to obtain still pictures at one or several different sites, the system also providing remote control of the cameras. The pictures can be displayed sequentially or all four together on a single monitor. Other features include movement detection where changes in pictures are noted, automatic activation of alarms, and remote control of such on-site facilities as gate locks, sirens, etc. The system is easy to operate and can be installed quickly and simply.

Servicing the Grundig 2 × 4 Super

Part 1

Mike Phelan

It's perhaps fortunate for some of us that the V2000 system hasn't turned out to be as successful as it might have been: even late model V2000 VCRs are now available at very low prices. If you intend to use your VCR for recording TV programmes, which after all is the primary purpose of such machines, the Grundig 2 × 4 Super, at present available for less than £200 from some outlets, must represent one of the best buys ever. The picture quality is superb, the dynamic track following giving noise-free shuttle search, slow motion and freeze frame.

Features

The machine is a front loader, with an attractive chocolate brown and gold finish. The front panel is uncluttered, with two groups of pushbuttons. Those on the left are a numerical keypad for entering data, plus controls for making timed recordings. The eight buttons in the centre are for the tape transport functions. The nomenclature here is a little odd, "stop" being still/pause and "tape" what we'd normally regard as stop.

Below this are two flaps covering more buttons. Those on the left are search and store for tuning (Bands I, III or u.h.f.). The other group are "go to", "slow" and "APF". The latter winds the tape either way until the beginning of a recording is found, then goes to still frame. There's also "time left", which we'll explain shortly. Although green, the clock display uses LEDs. When the machine is switched on, the clock data is replaced with either "CASS" (no tape in the machine) or "P TIME". In spite of the rather amusing definitions I've heard for this, it's how far along the tape is in hours or minutes. Also displayed is the length of the tape inserted, e.g. 1, 2, 3 or 4 hours (per side). When "TIME LEFT" is pressed, "P TIME" is subtracted from this.

There's no record switch. To record, you have to type in the channel followed by "PROG/DAY" and "START/STOP". You cannot record unless the clock has been set – done by typing in hours and minutes then pressing "CLOCK". If a mistake is made in entering data, the display shows "F"! Five timed recordings can be made over a 99 day period, from 32 channels. If you attempt to enter more time than there is on one side of tape the display shows "FULL".

At the rear of the machine there are sockets for video/audio input/output, remote and camera. The infra-red remote receiver clips on the side of the cabinet and is controlled by a very slim hand-held unit. If you have one of the current Grundig TV sets, one hand unit will control both the VCR and the set via an adaptor that replaces the remote receiver.

Mechanical Arrangements

To remove the top of the machine, take out two screws at the rear. All is then revealed – the mechanical construction is up to the usual Grundig standard. Six modules of identical size are plugged into the mother board at the bottom of the cabinet. From the left these are the power

supply, chrominance, luminance, servo, DTF and audio panels. The tuner and i.f. modules reside to the right of these in cans. The tuner is the usual Grundig type used in their TV chassis until recently.

In front of this group of modules is the self-seek board, then the keyboard module which is attached to the front of the cabinet. This contains the two microcomputer i.c.s that look after the mechanical and clock functions. The tape deck is on the right and can be removed after taking out three screws. Behind it is the motor connection board containing the direct drive head motor circuit, autostop, reel and loading motor drive circuits. To gain access to the deck, unclip and draw forward the cabinet front, then remove the "tea tray" – the massive screening can above the deck. It's no small thanks to this can that we've never had one of these machines with last night's supper all over the mechanics!

Although the Grundig machine is cassette compatible with the Philips V2000 series machines it uses a C-wrap rather than an M-wrap system. The motor that turns the loading ring also ejects and loads the cassette, using a very ingenious gear system with a rack and worm. The capstan motor is very small, the reel motors are very large and the drum motor is of the direct drive Hall-effect type. There's but one solenoid, for the reel brakes.

The Power Supply

Now for the problems, which are fortunately not many. We'll start with the power supply – see Fig. 1. This is a fully isolated self-oscillating chopper circuit of the Siemens type, with a BU208A chopper transistor and a TDA4600 control i.c. It's reasonably reliable, but the TDA4600, BU208A and the base drive coupling capacitor C401 must all be replaced together if any of them should fail. If this should happen the usual result is a completely dead machine, but if the 1.25AT mains fuse has failed the bridge rectifier should be checked for shorts. In the event of a dead machine also ensure that the start-up voltage (about 8V) from D418/R418 is present at pin 9 of the i.c. Once the circuit has come into normal operation the i.c. is supplied by D419/C419.

A common fault is that C401 goes leaky, the power supply switching on and off at approximately 1Hz intervals, sometimes clearing after a minute or so. Replace C401, the BU208A and the i.c. to be safe. The BU208A must be coated in heatsink grease and the nuts must be *tight*.

When working on the power supply, C435 and C485 should first be discharged – they both charge to 150V with no chassis leakage path and a nasty surprise can be had some minutes after switching off!

On the secondary side of the chopper transformer most of the supplies pass through the relay, which should energise at switch on (at the front panel switch) and de-energise fifteen seconds later if no functions have been selected. If the relay fails to operate, check that transistor T443 (near the bottom) has been turned on. If there's no base bias, R443 (390Ω) is probably open-circuit – it's not present on early panels. This bit of circuitry bypasses the

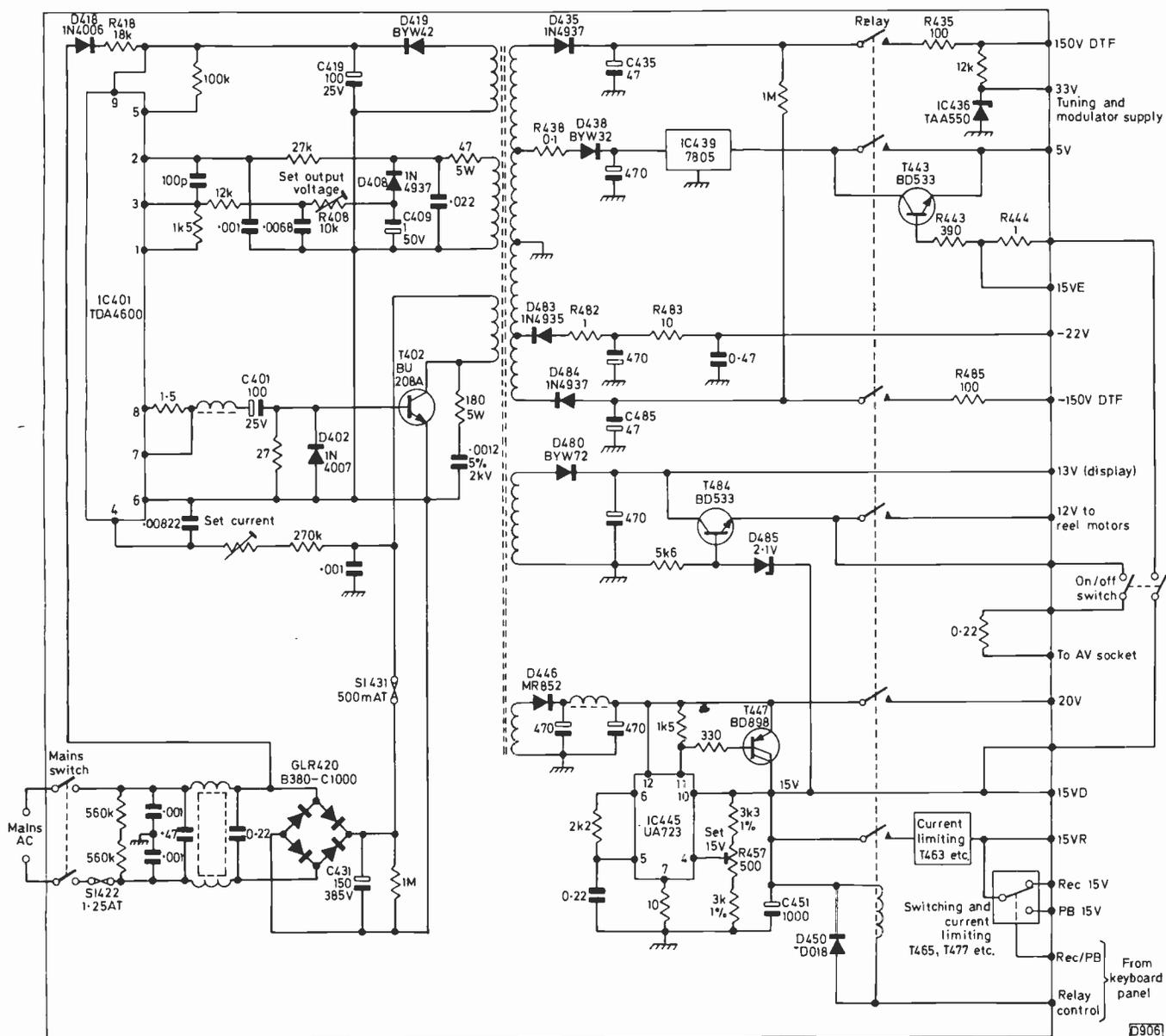


Fig. 1: The power supply – simplified circuit.

relay to provide the 5V supply for the microcomputer i.e. IC439 sometimes goes short-circuit, burning out the 0.1Ω surge limiting resistor R438 which again is not present on early machines.

Loss of the 15V supply shows up with the stop LED illuminated and the orange LED at the on/off switch barely visible. In almost every case you'll find that transistor T447 (BD898) is either dry-jointed or that one or more of its legs have broken off. This is the power transistor on the large heatsink at the front.

Loss of power to the reel motors – symptoms are slow or no fast wind and looping tape on playback – is caused by the 2.1V zener diode D485 at the top edge of the panel being open-circuit or dry-jointed. If the power transistor (T484) below it runs very hot, check the reel motor drive i.e. – more on this later.

The most common fault of all is failure of either of the 100Ω safety resistors in the 150V lines (R435 and R485). Symptoms are complete loss of DTF, i.e. noise bars on the slip-ring brushes above the head. If R435 is open-circuit there'll also be loss of tuning voltage – and the modulator output will be down at about ch. 21. Replace

both resistors and remove C484 and C437 (if fitted).

The primary side of the power supply – up to the relay – can be checked with only the mains connected, but extreme care is required.

The Keyboard Module

If the power supply is o.k. but the relay fails to operate, there's probably a fault on the keyboard module (see Fig. 2). As previously mentioned, the two microcomputer i.c.s are to be found here. They operate from different supplies and have different clock rates, so they cannot "talk" to each other directly. A shift register (IC270) and associated bits are used to transfer information either way.

In the case of no relay operation, check that pin 7 of IC280 goes high at switch on and that pin 16 of IC285 goes low. If the latter stays high, IC285 is probably faulty. Before you replace it, check the diode (D450) across the relay winding in the power supply. If pin 7 of IC280 doesn't go high, check the supplies and clocks at both microcomputer i.c.s. Dry-joints are common on this panel, especially along the bottom where the ribbon cables connect.

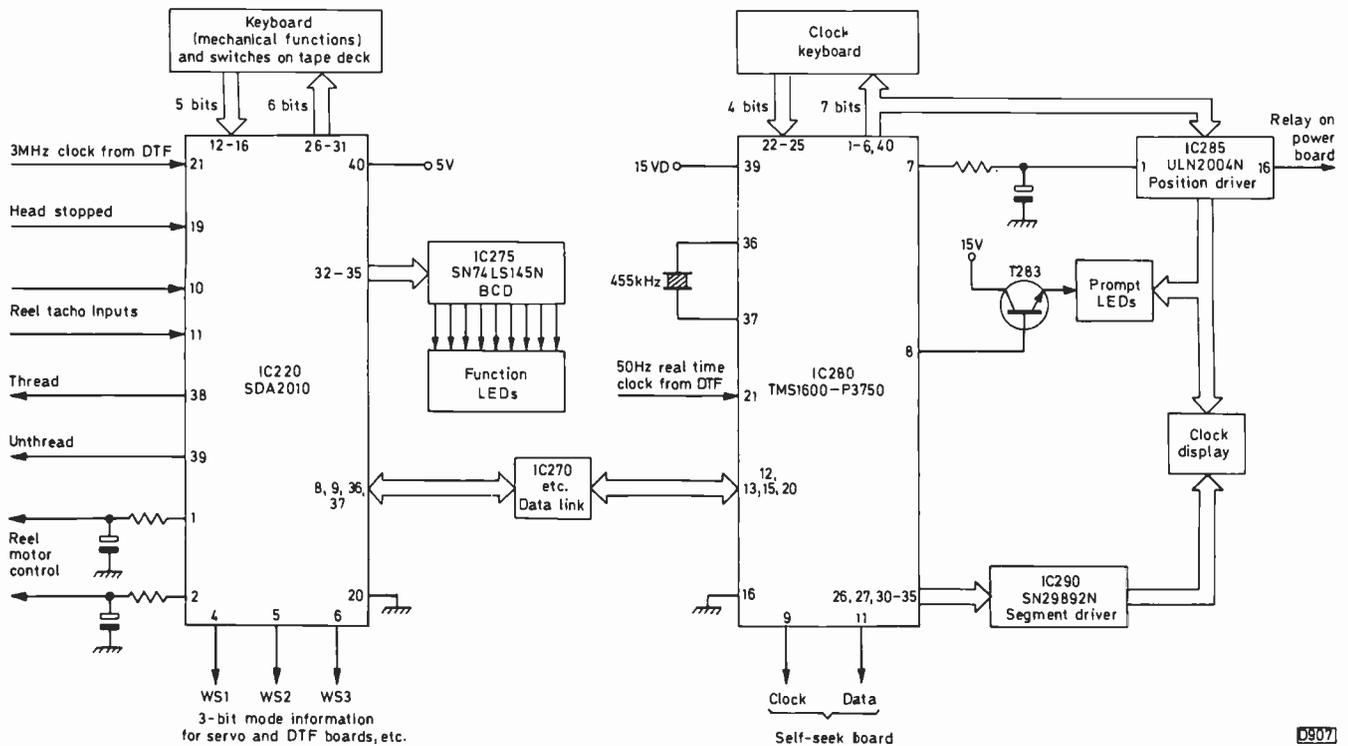


Fig. 2: The keyboard module – simplified block diagram.

We've occasionally had no switch on due to failure of IC220. The three WS outputs have also caused problems. These tell the servo, DTF etc. which mode the machine is in – if one bit is wrong you can get all sorts of strange results, like record in slow motion etc. More on the WS codes when we come to the servo board.

Sometimes the seven-segment displays give trouble: internal leakage can result in segments being lit that shouldn't be, or segments being dim or missing. R284-R293 always look cooked on machines that have had much use.

Next month we'll look at the signals section.

The Ferguson TX100 Chassis

In the past a new chassis from Thorn has usually involved the introduction of something radically different by way of circuitry or overall chassis arrangement. Think of the switch-mode power supply in the 3000 series, Syclops in the 9000 and so on. The theme of the new TX100 chassis however is evolution. It's been developed as a flexible, basic high-performance chassis to replace the TX9 and TX10 – flexible and basic in the sense that it's able to drive a wide range of tubes and is capable, with interfacing panels, of meeting all likely requirements over the next few years. Such requirements include remote control and teletext (of course); viewdata; frequency-synthesis tuning; RGB, composite video and stereo sound inputs; and SECAM colour capability for export models. The need to operate with cable and satellite signals has been taken into account in the design, and provision is made on the board for fitting the components required for stereo TV reception. The chassis may not look particularly innovative at first sight, but the design is elegant from a production viewpoint in the range of its capabilities.

Physically the new chassis is compatible with the TX9. This makes it possible to use existing chassis/cabinet mouldings. The new chassis is mains isolated however, which was never the case with the various versions of the TX9. As a result, for safety it was necessary to ensure that the chassis is not plug compatible with the TX9.

At a time when tube technology is in a state of change,

it's desirable that a new chassis should be capable of driving tubes of various types. The TX100 can drive tubes with 90° or 110° deflection angles in screen sizes 14-26in. and with neck diameters of 22.5, 29 and 36mm, also the new generation of FS (flat, square) tubes and the higher resolution types that are likely to be increasingly used. This has been achieved by making it simple to introduce modifications in the scanning areas of the chassis – alternative line output transformers and field output i.c.s and component changes by means of links. The EW correction circuit is on a subpanel fitted to 110° sets only.

The chassis has been designed to interface with the latest digital peripheral circuitry for tuning, remote control and text facilities. The SCART/Peritelevision input socket is an optional extra mounted on a panel with interfacing circuitry. It enables RGB, composite video and audio signals to be fed into the receiver, making the chassis capable of handling home text and graphic displays from computers or sophisticated games, also satellite TV and interactive cable signals.

Block Diagram

A block diagram of the basic chassis is shown in Fig. 1. The chopper power supply is of the Siemens self-oscillating type as used in later versions of the TX9, but in this case providing mains isolation. The safety cover over the

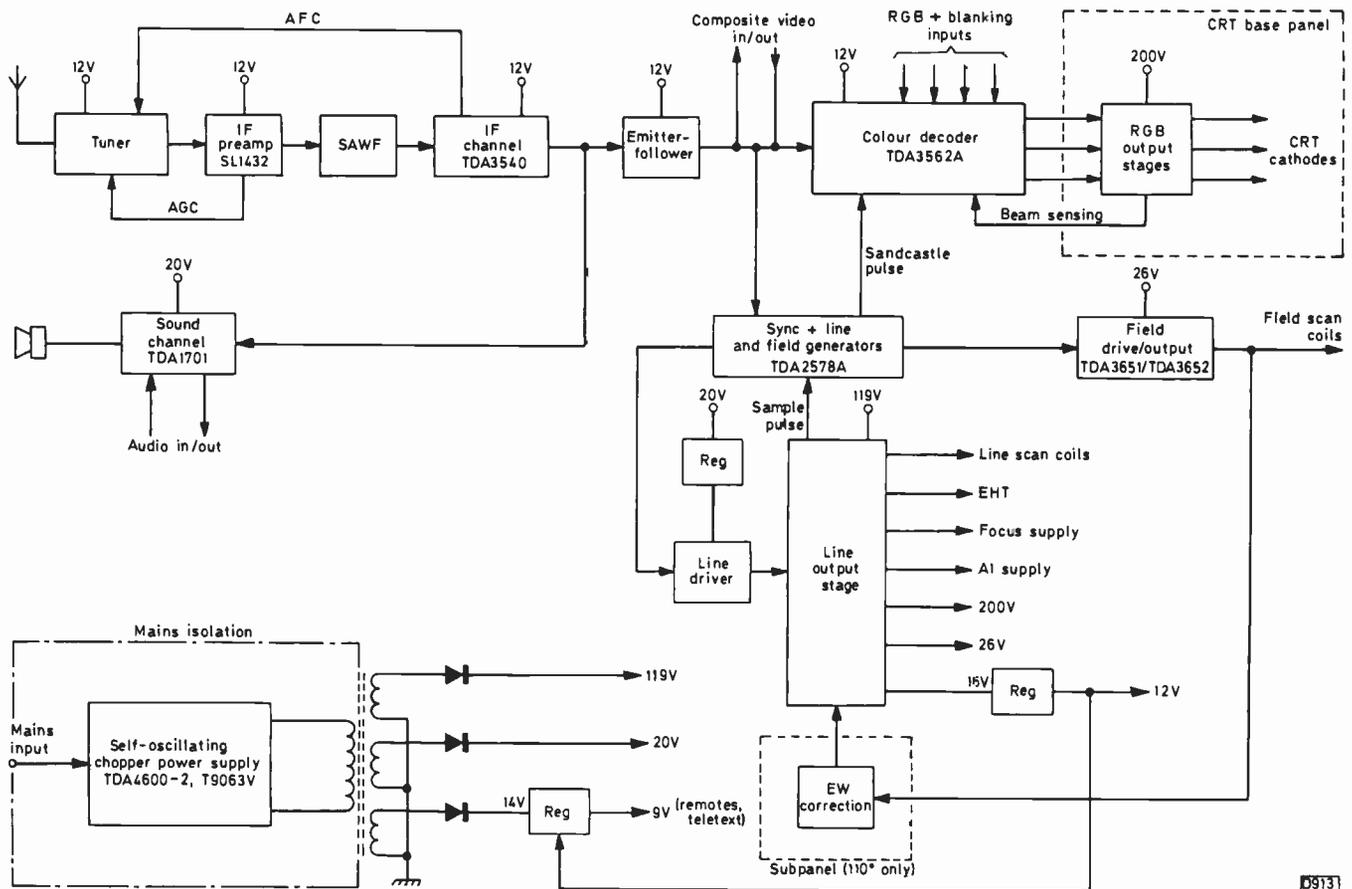


Fig. 1: Block diagram of the Ferguson TX100 chassis. A relay in the 119V line gives remote standby.

live section is colour coded – red for sets produced to drive 110° tubes, yellow for standard 90° tubes and blue for mini-neck (22.5mm) 90° tubes. The control i.c. is a TDA4600-2 and the chopper transistor a T9063V: a thyristor is used in the start-up circuit.

The i.f. strip is basically the same as with the TX9/10, though an improved i.f. i.c. has been adopted (TDA3540). An emitter-follower at the output of the i.f. strip facilitates interfacing. The TDA3562A decoder i.c. differs from the TDA3561 used in late versions of the TX10 in incorporating black level correction. Each RGB output stage incorporates a beam sensing circuit that provides feedback for this purpose. Only a single feedback connection is required as the i.c. samples the black currents of the three guns sequentially line by line. At first sight the RGB output stages look like the now conventional class AB circuits. The beam sensing circuits enable the circuitry to be subtly rearranged however. The first transistor in each channel is a conventional class A voltage amplifier with a high-value (15kΩ) load resistor to reduce dissipation. This is followed by an emitter-follower transistor to give optimum transient response on the positive-going edges of the video waveform. The transistor included for black-current sensing also acts as an emitter-follower to provide a discharge path for the tube capacitance on the negative-going edges of the video waveform. The new circuit provides good high definition and grey-scale performance.

The sync/timebase generator and field driver/output i.c.s are the same as those used in later versions of the TX10, though the TDA3651 replaces the TDA3652 in 90° chassis. The line output transistor, transformer, tuning capacitor and other components also vary for 90° and 110° operation. An unusual circuit in this area is the line driver stage (see Fig. 2). This is a low-voltage stage using a

BC372 Darlington transistor. A 15V regulator is incorporated and the supply to the driver transformer is altered for 90/110° operation, an example of the timebase flexibility we've referred to above.

Model Numbering

Sets using the new chassis will be added to the Ferguson range this autumn. They will be easy to spot as a new system of model numbering is to be introduced. The first two digits will indicate the screen size. This will be followed by A to indicate that a 90° tube is fitted or B for a 110° tube. The final digit indicates either 1 a standard set, 2 a set with remote control, 3 a teletext equipped set, 4 a set with teletext and stereo sound and 5 a component set. So 20A1 will indicate a standard 20in. set with a 90° tube. We shall also have to get used to referring to this as a Ferguson rather than a Thorn chassis.

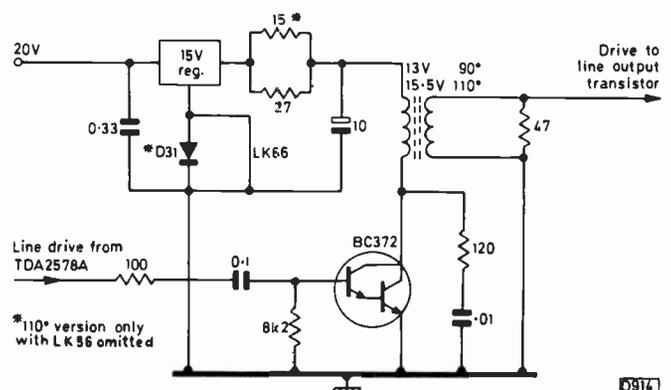


Fig. 2: The low-voltage line driver stage.

TV Fault Finding

Reports from Mick Dutton, John Coombes, Malcolm Burrell and Tony Thompson

Thorn TX9 Chassis

The problem with this set (PC1044 main panel, i.e. chopper version) was field roll, approaching double speed. It was cured by replacing the oscillator timing capacitor C206 (0.47 μ F) connected to pin 9 of the TDA1170S field timebase i.c. **M.D.**

Fidelity 20in. CTVs

A problem with these models is that the tuner presets are very touchy. There are two different types: thumbwheel controls or rotary potentiometers with a special adjuster that has a built-in gearbox to make adjustment easier. It's the latter type that seems to cause most problems. We had one set that was particularly sensitive on the first preset on BBC-1. This wasn't due to the tuner potentiometer assembly however but to very slight misadjustment of the video detector coil L1. **M.D.**

Philips KT3/K30 Chassis

Something I've often had recently is one colour dropping out as a result of corrosion on the pins of the decoder i.c., where it plugs into its base. It's possible to clean the pins, but a more permanent cure is to solder the i.c. direct. The same problem can also be responsible for running colour. **M.D.**

Thorn TX9 Hint

A TX9 Moviestar portable came in recently with the complaint of fuse blowing, something that's been mentioned in these pages before. Whilst testing we found that we were accumulating quite a tidy pile of small black fuses. This is wasteful. I eventually tried hooking the cutout from a Thorn 3000 chassis in place of the mains fuse. This blew quite readily from time to time until the cause of the fault was located after which the correct fuse was fitted. **M.B.**

Hitachi Models CPT1471/1473

The STR6020 chopper i.c. (IC901) bolted to the chassis is a prime suspect that can cause various faults on these sets. The trouble we had with two of them was a slight intermittent picture break-up accompanied by a sound rather like internal arcing. A couple of other sets would work normally then suddenly return to standby, the sudden loss of e.h.t. making it seem as if a flashover was responsible. **M.B.**

Pye 731 Chassis

The complaint with an Ekco Model CT262 (Pye 731 series chassis) was that the "picture goes off". Not very enlightening! We soak tested the set for several hours over three days but the fault wouldn't put in an appearance for us – despite efforts at prodding around. The set was then returned but came back a few days later, when it again performed faultlessly for hours on end. Whilst I was out my customer liaison/bookkeeper/soak tester/wife noticed

that it went off "just for a few seconds – no sound or picture, just snow and loud hissing, as though the aerial had been disconnected". At last a clue. With this problem the i.f. gain/selectivity module is always suspect on these sets. But I'd already tapped and prodded around, and even flexing the panel didn't help.

I then noticed the wire link that carries the tuner's output to the module. It was this link that was the trouble, due to being positioned so close to the tuner's screening can that an intermittent short was occurring. Why it happened so intermittently, and why tapping had no effect, remains a mystery. I've not come across another of these sets where the link was so critically close: possibly a replacement tuner with an oversized screening can had at some stage been fitted. **T.T.**

Thorn 1500 Chassis

The problem with a set fitted with the Thorn 1500 chassis was excessive height. Adjustment of the height control only made things worse, including the linearity. Voltage checks around the PCL805 field timebase valve revealed grossly excessive voltage at the anode of the triode section of the valve. We expected to find a low-value feed resistor, but in fact the filter capacitor C89 (1 μ F) was open-circuit. **T.T.**

Pye 725 Chassis

The complaint with a Dynatron set fitted with the Pye 725 chassis was low, distorted sound, worsening the longer the set was left on. The audio output stage showed no signs of distress – nothing overheating – so I suspected the TBA750Q intercarrier sound chip, which can sometimes be responsible for this fault. A replacement made no difference, as I should have known since freezing the original one had not affected the fault. Voltage checks then revealed that the chip's supply pin was at only about 6.5V instead of 11.5V. The feed resistor is R218 (560 Ω), and though it looked o.k. it had risen in value, replacement clearing the fault. **T.T.**

Thorn 3000 Chassis

Like many engineers, I get a lot of trouble with the first anode supply switches used in these sets. They are of the metal kind, the body of the switch being earthed via print lands on the panel. What actually happens is that the switches leak internally, taking the first anode supply to earth. The switch can of course be replaced – but only if you happen to have one with you, and I rarely seem to be in that position. Or you can remove the switch entirely, linking the print with stout, single-strand copper wire; or sever the print in such a way that the body is no longer earthed. I don't personally favour the latter approach: I think that once a switch has given trouble it's likely to be impaired and should be removed – and don't forget that any switch dealt with in this way would have a metal body with up to 1kV on it just waiting for some unsuspecting service engineer... It's best I think to link the supply permanently with copper wire.

The problem I had recently on one of these sets was very bad field linearity. I tried all the usual things but drew a blank. In the end, because of a hunch rather than any scientific reasoning, I changed the field output stage h.t. feed resistor R442 (58Ω). It's a wirewound component mounted on the field/audio board, at the top rear. It read all right out of circuit, though the problem would I suppose have been apparent had I checked the voltage across it – probably an instance of familiarity breeding contempt...

If you've got one of these sets fitted with the later type of power board and it keeps going dead for no apparent reason, check the two top fuses: lift them and measure the resistance, since you may be misled by voltage checks. If one of the fuses is open-circuit the set can continue to

function, but with the intermittent dead effect.

One last point on this chassis. When the dead set symptom can be cured by pressing the cut-out, this item is not above suspicion. In fact the cut-out is often responsible for the fault nowadays, years of running having burnt away the contact areas until at least one of them has a hole clean through it. You can confirm this by taking the cut-out apart. Don't attempt to reuse it: fit a replacement.

T.T.

Thorn 1615/1715 Series

If the problem is bent verticals at the top and bottom of the picture, check for a dry-joint on the tube base – on the earth lead to the Aquadag c.r.t. earthing spring. J.C.

TV Test Pattern Generator

Part 3

Tony Jenkins, G8TBF

This month we'll deal with the assembly of the PCBs. The layout of the logic board is shown in Fig. 9: this is the most complex board and in order to reduce construction time and errors has plated through holes. It needs to be soldered on the inside only and hasn't any through board links. When an i.c. is soldered on to this type of board the solder tends to run into the through holes, making subsequent extraction more difficult. We therefore recommend that extra care is taken when constructing the board and the use of i.c. sockets or soldercon terminals for the ZNA234E and EPROM i.c.s. Several ceramic and electrolytic capacitors provide local decoupling – see Fig. 9. These should be soldered in last of all.

The encoder and power supply boards are single-sided

types and construction is straightforward. An i.c. socket is suggested for the TEA1002. Layouts next month.

A set of the three PCBs will be available in late July at £27 inclusive of VAT and postage/package from Coombe Martin Electronics, King Street, Coombe Martin, North Devon, EX34 0AD. Please note that the boards will not be available individually.

A set of the three pre-programmed EPROMs will be available from JRW Developments, 13 Baulk Lane, Worksop, Notts, S81 7DF at £29 inclusive of VAT, postage and packing.

In next month's concluding article we'll describe the construction of the complete instrument in a suitable case and provide setting up instructions and fault finding hints.

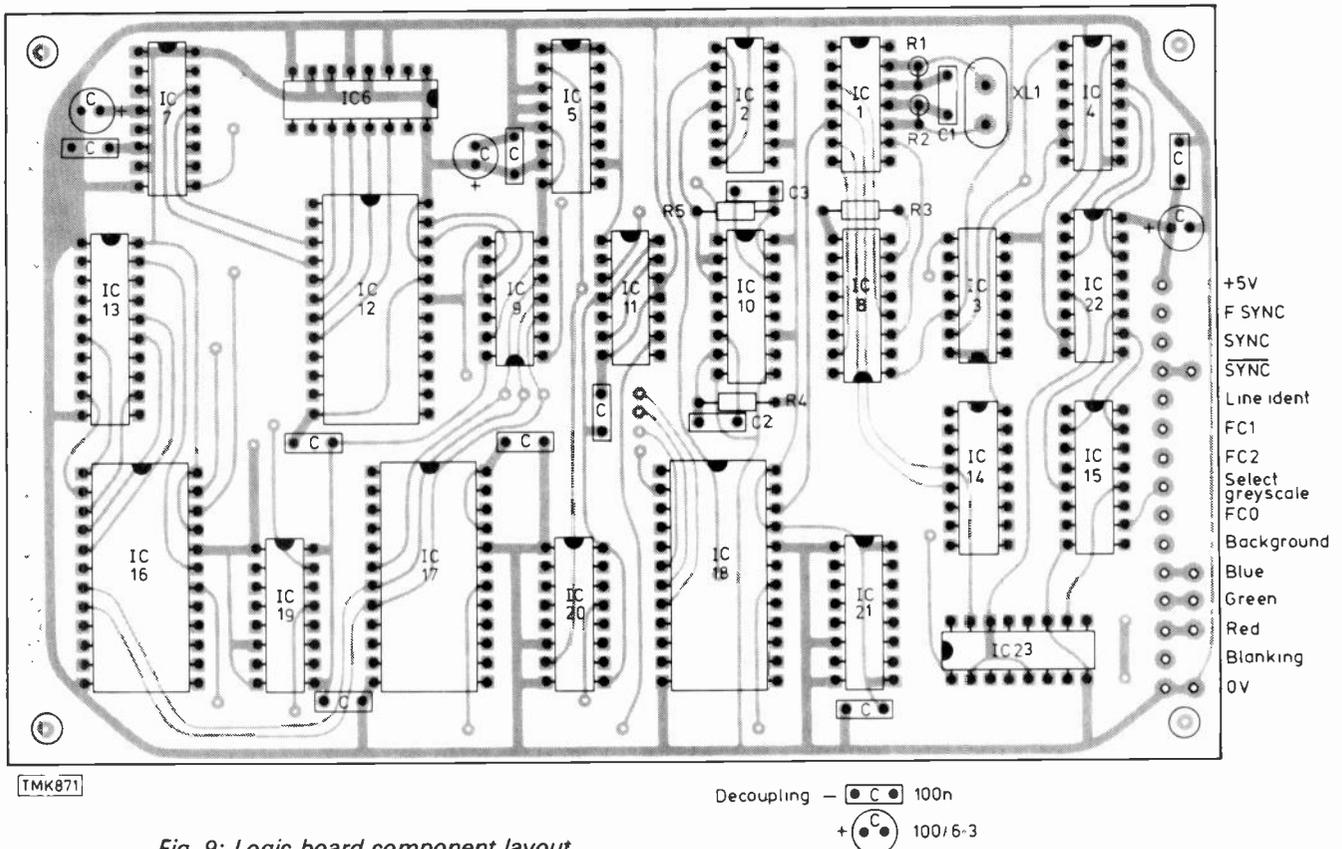


Fig. 9: Logic board component layout.

Long-distance Television

Roger Bunney

April was a great improvement on March, which had been unusually quiet. When Sporadic E activity perks up during April it usually means a good season ahead: the signs are certainly auspicious. Ionospheric conditions have been disturbed by solar flares however. These produced magnetic storms and blackouts from 24-28th April – the largest disturbances for several years. This resulted in auroral activity on the 25th and 26th. The m.u.f. rose prior to the 24th, Cyril Willis (Ely) logging Zimbabwe ch. E2 vision during the late afternoon via trans-equatorial skip. SpE propagation in Band II was noted on the 28th. The main loggings of the month were as follows:

- 8/4/84 RTVE (Spain) chs. E2, 3, 4.
- 15-16/4/84 Short-duration Band I SpE signals throughout the day.
- 17/4/84 CST (Czechoslovakia) R1.
- 20/4/84 RAI (Italy) IA; ZTV (Zimbabwe) E2 (TE).
- 22/4/84 RTP (Portugal) E2; RAI IA, IB.
- 23/4/84 TSS (USSR) R1.
- 24/4/84 ZTV E2 (TE).
- 25-26/4/84 Unidentified auroral signals in Band I during the evening – characteristic “rumbling” noises, hum on vision and poor sync.
- 27/4/84 TSS R1.
- 28/4/84 RAI IA, IB; EPT E3 (see below); Italian cordless phones at 49MHz!
- 1/5/84 TSS R2.
- 3/5/84 CST R1; many short-duration Band I signals during the morning.
- 5/5/84 Many short-duration SpE signals throughout the morning, with DFF (E. Germany) ch. E4 and signals on chs. R1 and 2 logged.

The Greek ch. E3 signal logged by Cyril Willis on the 28th lasted for over an hour, from 1830, the EPT identification appearing at 1900. The signal had no vertical test signals and tends to confirm a previous suspected Greek logging. There's no official Greek ch. E3 listing however. Well done Cyril!

MS activity was not particularly noteworthy, though the Lyrids shower arrived on schedule, with numerous dense bursts especially on the 22nd.

A static high-pressure system dominated the second half of the month, giving record temperatures and sun. For those in the south however the tropospheric conditions failed to produce a good opening, due in part to a gentle breeze on most days. Conditions were better farther north, a good opening being experienced in Scotland. Reception began to improve on the 22nd, with signals from the east and south east being widely logged. By the 24th, DXers along the east and north east coasts were receiving signals from Swedish, Norwegian and Danish transmitters in Band III and at u.h.f., the peak days being the 24/25th. Iain Menzies (Aberdeen) reported Band III and the u.h.f. spectrum jammed on the 24/25th, with W. German stations on all channels and from all three networks. Cyril Willis noted only “several W. German u.h.f outlets” on the 25th, while here at Romsey only French and Benelux stations were logged.

For once the north did best. While a circulatory breeze was present in the south, most days in Aberdeen produced fog banks that rolled in from the North Sea. The good conditions in the north continued until the 28/29th, producing signals from Norway, Sweden and Denmark in Band III and at u.h.f. During the first few days of May however the high-pressure system moved, rain fell and conditions returned to normal.

At least three of the new French Canal Plus transmitters – Lille, Paris and Rouen – are now on test, with daily transmissions from approximately 0900 to 1800. Excellent signals have been received from Lille – a grey scale and the PM5544 pattern (identification TDF and CENEX-BCH). Paris is somewhat weaker, while Rouen has a very distinctive pattern (see photograph).

A smaller tropospheric opening occurred on the 13/14th. This was particularly noticeable in the south, with signals from W. Germany and the Benelux countries.




Many thanks to the following for their reports: Tony Privett (Basingstoke), Iain Menzies (Aberdeen), Cyril Willis (Ely), Paul Barton (Harrogate), Gareth Foster (London) and Hugh Cocks (E. Sussex).

News Items

USA: The Broadcast Television Sound Committee (BTSC) has adopted a standard that could result in stereo TV sound transmissions before the end of the year, subject to FCC approval. Zenith's proposal for coding was selected following several years of tests and the evaluation of three basic systems.

Kampuchea: Test transmissions from a ch. A10 (system M) transmitter at Phnom Penh started in January. Regular transmissions are expected to start early next year.

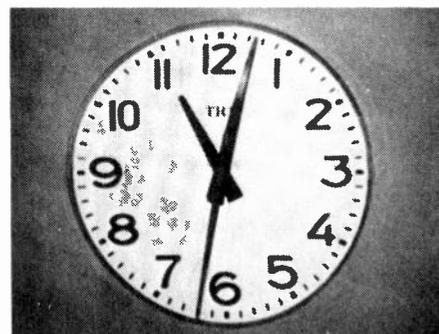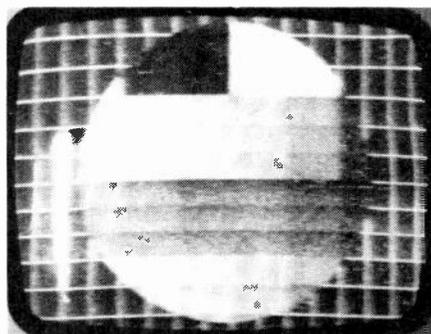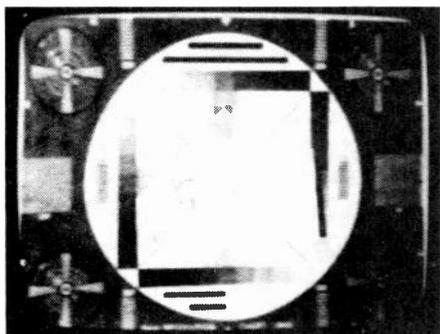France: The Canal Plus service is to be inaugurated on November 1st in the Paris, Lyons and northern regions.



Left: The RETMA test card used by G1APD (Southampton) – ATV reception in Romsey at 437MHz. Centre: Canal Plus on test from Rouen, received at Romsey. Right: Clock used by TRT (Turkey).

Descramblers to connect via a SCART socket will be available after payment – adaptors for older sets without such a socket will be available.

New DX Publication

Simon Hamer has written a useful nine-page (A5) booklet entitled "TV-DXing for Beginners". It covers the basics of DX-TV reception, signal propagation, channel allocations and methods by which a standard u.h.f. TV set can be used for the purpose. Enquiries should be sent (include a s.a.e.) to the North England Radio Club International, 4 Bryn Bank, Wallasey, Merseyside L44 1AU.

Transmitter News

AFNTV is operational in Holland on ch. A80 (between E70/71), at 20kW e.r.p. with horizontal polarisation and a 40m mast. This provides a strong signal in Rotterdam.

The Polish transmitter network has been increased as follows: Siedlce R1 50kW e.r.p., Przemysl R24 300kW, Opole R40 500kW, Siedlce R52 300kW (all TVP-1), Przemysl R41 300kW (TVP-2).

Regional programming will be carried by the following Norwegian transmitters from September: Greipstad E2; Bjerkreim E6; Lyngdal E9.

Satellites

ARABSAT is to be launched in November to provide services (DBS and point-to-point) to the Arabic countries at 2.5GHz. It will have 25 output transponders... Thames Television/Granada TV are planning a satellite service via ECS to compete with Sky Channel... The general trend at 4GHz in the USA is for increased downlink EIRP levels, now reaching 37dBW compared to the first generation 34dBW. As a result, TVRO terminals can operate with 6ft diameter dishes. At 12GHz Anik-C provides up to 48dBW on its downlink to the eastern USA, allowing 3.5ft dishes to be used. Plans are for future EIRP levels of up to 55dBW so that 2ft dishes can be used.

Pirate FM Radio

Several unlicensed, commercial f.m. radio stations have been in operation recently, mainly in the London area. The transmitter is normally sited atop a block of flats or at some similar vantage point with a radio link from the studio. Gareth Foster reports that Radio Jackie is using 209MHz for its link and Skyline Radio 203MHz. Other operators are likely to use this spectrum for the same purpose. The idea is to avoid seizure of the relatively much more expensive studio equipment: the transmitter may be moved around from day to day to avoid detection by the DTI/BT Radio Services.

Aerial Mounting Problems

Ian Moody comments that the boom of his Antiference XG14 u.h.f. array is exactly the correct length for a ch. E4 dipole and wonders whether it could be used for this purpose. I don't think that such a dual use would be feasible even with correct matching, but this does raise an interesting subject. If the boom is mounted so that it's parallel with a Band I aerial and the distance between the two is less than one wavelength (at Band I), there will be a degree of absorption. This will increase as the separation between the two is reduced. The moral is to avoid

SOUTH WEST AERIALS



As the leading UK aerial mail order company, we carry a comprehensive range of equipment for domestic, fringe, DXing and distribution systems. Satellite equipment (TVRO) is also available.

We also supply aerials/equipment for all bands, from large aerials to small filters – and all the bits in between. Aerials for the new 50MHz amateur band are just available.

We are active DXers – your guarantee of honest and accurate advice – efficient equipment at competitive prices.

We've listed just some of our weak signal/DXing UHF aerials below – prices include VAT, packing and Securicor carriage.

Faba. Gold anodised multi-element high gain (17dBd), the legendary XC391 (available Grps A,E,W) £59.85	Triax. Unix 44. Gold anodised multi-element (14dBd), (Grps A,K,E,W) £33.00
Jaybeam. JEX8 multi-element (14.5dBd) £26.70	Unix 92. Golden anodised perfection, high gain (17dBd) (Grps. A,K,E,W) £49.55
JBX21 High gain multi-element (18.5dBd) (available Grp. A,B,C/D) £54.00	BB Grid. Wideband 4 bay bowtie £22.80
Walsley. Budget high gain (18dBd) multi-element HG36 (Grps. A,B,C/D) £34.35	Twin Grid kit, 15.3dBd gain £54.60
Colour King. Wideband 4 bay bowtie (12.5dBd) £26.10	Quad Grid kit. THE ULTIMATE weak signal system 18.8dBd gain £81.10

NB. Grid kits include low loss combining filter, clamps, cross support masts.

(allow 7-10 working days for delivery of stock items)

SOUTH WEST AERIALS IS UNIQUE – TRY OUR COMPREHENSIVE CATALOGUE AT 54p. Please include an SAE with all enquiries, customer reception consultancies and for our own VHF aerial leaflets. (Access/Barclaycard welcome).



SOUTH WEST AERIALS
11, Kent Road, Parkstone,
Poole, Dorset, BH12 2EH.
Tel. 0202 738232



TV LINE OUTPUT TRANSFORMERS

PRICES INCLUDE VAT & CARRIAGE

Delivery by return of post.

RANK BUSH MURPHY A774 with stick rectifier 9.78 A816, T16, T18, Z712, Z715 10.35 T20, T22, T26, Z179, A823 11.50 Z718 Basic unit 13.50 T24e, T24h split diode P.O.A.	ITT: VC200, VC205, VC207 7.50 VC300, 301, 302, 400, 401, 402 9.20 CVC1, CVC2 (FORGESTONE) 11.50 CVC5, CVC7, CVC8, CVC9 series 8.50 CVC20, CVC30, CVC32, CVC45 8.50 CVC40 split diode 16.74 FT110, FT111. P/no AT2063/02 11.50
DECCA: 1210, 1211, 1511 11.50 1700, 2001, 2020, 2401, 2404 7.50 CS1730, 1733, 1830, 1835 8.50 30, 70, 80, 90, 100 Series 8.50	PYE: 169, 173, 569, 368 series 8.50 CT200, CT200/1, CT213 series 10.35
FERGUSON, THORN: 1590, 1591 9.20 1690, 1691, built in rect. 9.78 1600, 1615, 1700 series 11.20 1790 mono portable 9.20 3000, 3500, 8000, 8500, 8800 P.O.A. 9000, 9200, 9300 series 12.00 9500, 9600, 9650 series 10.99 9800, TX9, TX10 series P.O.A. MOVIESTAR 3781, 3787 12.00	PHILIPS: 170, 210, 300 series 8.50 320 series 9.78 TX, T8 mono series P.O.A. KT2, KT3 series colour 9.20 G11 series split diode P.O.A.
FIDELITY: FTU12 mono 10.35 CTV14R, CTV14S colour 15.83	BINATONE: 9909 mono 13.04 GRUNDIG: most models in stock NORDMENDE: FC125, Z206, Z306 11.50 SANYO: CTP5101, TJ series 11.50 SHARP: C1851H, C2051H 12.32 TELETON: TH14 mono 13.68 TOSHIBA: C800, C800B 19.45 TANDBURG: 190, CTV2-2, CTV3-3 P.O.A. TELEFUNKEN: most models in stock LINE OUTPUT TESTER 16.79
G.E.C. 2047 to 3135 mono 7.50 1201H, 1501H, 2114, 3133, 3135 9.20 DUAL & SINGLE hybrid col. 10.00 SINGLE STD solid state 12.00 SINGLE STD split diode P.O.A.	Tidman Mail Order Ltd., 236 Sandycombe Road, Richmond, Surrey. Approx. 1 mile from Kew Bridge. Phone: 01-948 3702 Mon-Fri 9 am to 12.30 pm & 1.30-4.30 pm Sat 10 am to 12 noon.
INDESIT: 24EGB hybrid 9.50 12LGB, 12SGB mono portables 10.35	
WINDINGS TYNE: main winding 6.80 RBM: T20, T22, T26, Z179 6.33 WALTHAM: W125 eht winding 2.37 KORTING: hybrid winding 6.90	

mounting arrays so that a boom is in parallel with a close proximity aerial element of similar dimension.

A similar problem occurs when say two aerials rather than a single wideband aerial are used to cover a certain

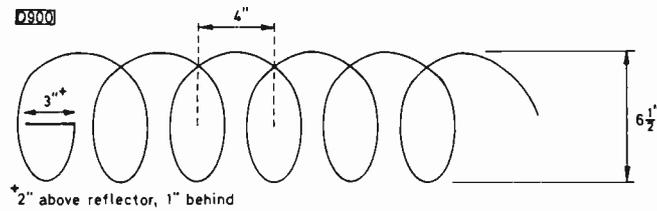


Fig. 1 (above): Helix details.


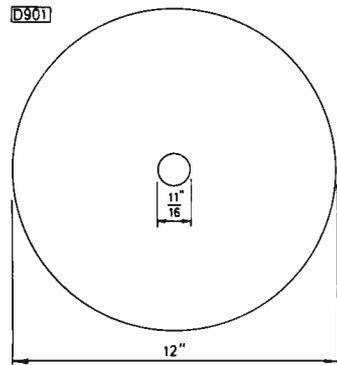


Fig. 2 (left): Reflector dimensions.

Fig. 3 (below): Details of the matching section.

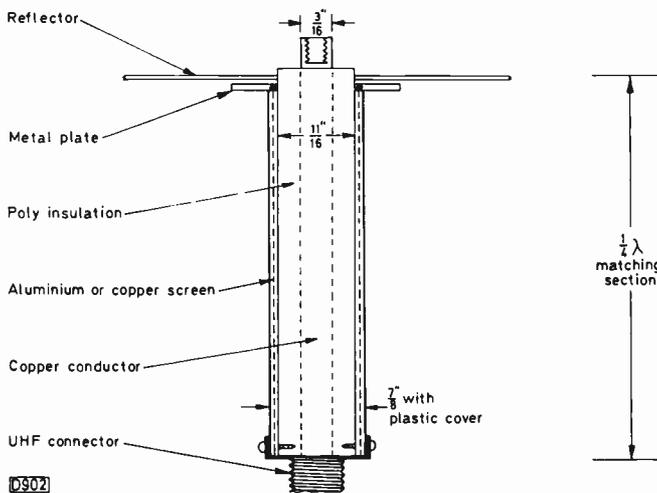

D902

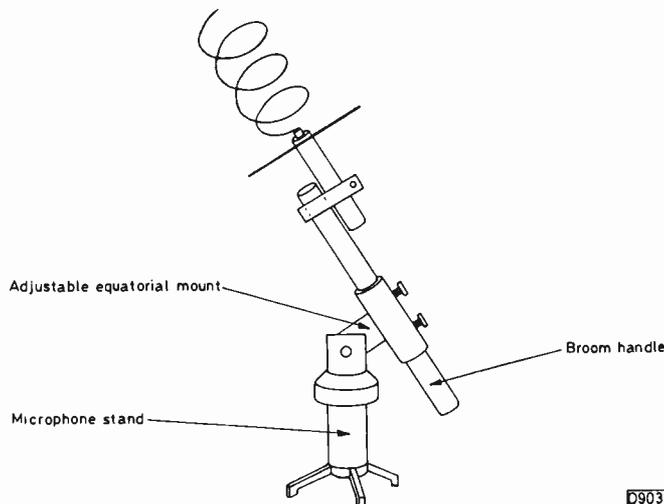


Fig. 4: The helical aerial mounted on its stand.

band and are mounted close together. Two narrower bandwidth aerials will be more efficient – provided they are mounted a wavelength or more apart. This can be a problem – a wavelength is 17ft in the case of ch. E3! The higher the gain, the worse the problem, as a study of stacking information will show. The minimum tolerable distance for stacked arrays is usually quoted as being 0.75λ , one wavelength being suggested as the best compromise. In many cases therefore a single wideband array will be more efficient despite its lower gain. Any observations?

Interference

I've recently encountered a new type of interference that presented itself as heavy patterning with a synchronised white square throughout most of Band I. It was traced to a Sinclair ZX81 on program payout, and despite being nominally on ch. 35 there was sufficient radiation to reach a Band I aerial at a distance of over 70 yards. Fitting a replacement coaxial lead with efficient screening between the ZX81 and the TV set reduced the problem.

Dave Lauder's DX-TV Newsletter recently reported an interesting case of teletext breakthrough with a DX-TV receiving installation. In this case the problem was overcome by fitting ferrite toroids to the aerial feeder and mains lead supplying the teletext receiver. Dave comments that computers etc. could produce similar problems and that fitting ferrite toroids to all connections should provide a cure. Ambit have a wide range of toroids – use v.h.f. types (i.e. dust iron) such as the T50-10, T37-12 and T50-12. The large ferrite toroids used as braid breakers can be obtained from amateur radio suppliers – in this case two similar toroids should be placed together and the mains cable or whatever wound through the centre several times. Let us know of any similar problems – or solutions!

Simple Helical Aerial

Chandra de Silva (Colombo, Sri Lanka) has built a simple helical aerial (see Figs. 1-4) at virtually no cost for the reception of the 714MHz signals from the Ekran satellite (Stationar-T) at 99°E. This satellite transmits the Moscow-1 service with a 24MHz wide f.m. video channel, 6.5MHz sound subcarrier and right-hand circular polarisation, and is well received in Sri Lanka, India and the Gulf. Unfortunately it's over the horizon in W. Europe.

The helical element consists of six turns of 3/8in. aluminium tubing, with 4in. spacing between turns (looking clockwise from the connection end). The latter is bent to give a spacing of just over 2in. between the end of the helix and the aluminium reflector. The matching section consists of a metal tube with a thick 50Ω coaxial inner that passes to an SC239 connector.

The main problem at the feed point is to obtain matching to the cable. Typically the feed impedance is some 130-140Ω. This requires a 102Ω quarter-wave section to match to 75Ω, or an 83Ω quarter-wave section to match to 50Ω. It might be better to make a direct connection at the feed point to a low-noise transistor amplifier such as that shown in the April issue (page 303) – a tapped coil could be used at the input for optimum noise matching.

The aerial has a beam width of about 36° (-3dB points) and a gain of 11dBi (8.8dBd). Comments and findings from anyone constructing an aerial of this type would be welcome.

D903

Service Bureau

Requests for advice in dealing with servicing problems must be accompanied by a £1.00 postal order (made out to IPC Magazines Ltd.), the query coupon printed below and a stamped addressed envelope. We can deal with only one query at a time. We regret that we cannot supply service sheets nor answer queries over the telephone.

RANK T20 CHASSIS

There's an odd effect on this receiver: the verticals at the top and bottom flare outwards, with some vertical compression. The EW pincushion control affects only the main portion of the display, not the top and bottom.

We've come across this effect on several occasions on various chassis and have usually found the cause to be loss of inductance in the EW loading or bridge coils – these are 5L1 and 5L5 in the T20 chassis. Inspect them for signs of overheating, broken or damaged ferrite etc. and replace as necessary.

PHILIPS KT3 CHASSIS

There's misregistration of the colour with respect to the luminance, seen most clearly with saturated colours. Colour from a left-hand object spills about 4mm across to the right. Otherwise the colours are correct, there are no blinds and all is well.

The colour fit can be improved by realignment of the chroma coupling circuit on panel U3430. Use a test pattern – Ch. 4 is ideal. Screw the core of the 2.2MHz trap U194 right down then back half a turn. Then tune the bandpass circuit U195 for best transition between the green and magenta bars without producing ringing. The effect of this is to widen the chroma response without spoiling the pulse response of the luminance channel.

HITACHI CNP190

I'm having difficulty with this fault due to its intermittent nature. About two or three times a night the picture contracts all round by about three inches, with loss of colour and sound. The problem doesn't seem to be temperature dependent and the picture may return to normal either suddenly or slowly. In the latter case the picture will expand and contract several times before settling down.

The likelihood is that the h.t. voltage is falling from time to time – this can be confirmed by leaving a meter connected across the 120V rail. Suspect components are the zener diode CR40 (HZ-7), the set h.t. potentiometer R911 and the three transistors (TR41/3/4) in the series regulator circuit.

RANK T20 CHASSIS

There's an unusual fault on this set – the picture contracts at the sides at points of high brightness. Any ideas?

We suggest you start by checking diodes 4D9 and 4D10, since these affect the breathing performance. If all is well, check the earthing of the c.r.t.'s Aquadag coating then if necessary set up the line output stage fifth harmonic tuning as detailed in the manual.

HITACHI NP6C CHASSIS

We're having trouble with the 2SC1942 chopper transistor used in this chassis. After a few days of normal operation the set goes dead. If left for a while it will come on again. This happens several times then the transistor goes, severely blowing the 800mA chopper circuit fuse. A BU208A used as a replacement lasted for about a week before going in the same way.

In our experience a BU208A is not suitable in this position and a 2SC1942 will have to be used. To prevent it blowing up again, replace the two HM9102 thick-film modules T901/2 in the power supply and check this area carefully for dry-joints. Also ensure that the two 22Ω resistors R925/R936 in the chopper transistor's base circuit have not changed value.

THORN 1590 CHASSIS

The field hold control is at one end of its track and the frame slips at intervals. Are there any "stock items" to go for?

If the l.t. supply is exactly right at 11.6V, and the field hold control and its series resistor R79 haven't changed value (this does happen), the most likely culprits are transistor VT15 on the output side of the multivibrator circuit and the field sync isolating diode D24.

RANK T20/22 SERIES

There seems to be some difficulty in supplying replacement overvoltage crowbar thyristors for these sets. Advertisers don't appear to stock the S2062D.

There's nothing very critical about 7THY2: a Thorn BRC4443 can be used in this position with no problems.

SONY KV1820UB

The initial trouble was intermittent start-up. At switch on the sound would come up but a few seconds later, before the picture appeared, the set would go dead (apart from the indicator neon being lit). Switching on and off would produce the same sequence, but after a few attempts normal operation would be obtained. The fault has subsequently become solid, with the set refusing to start, though if left for ten minutes or so the earlier sequence will occur, with the addition of a brief multi-coloured flash at screen centre as the set goes dead.

It's very common for these symptoms to be caused by an internally open-circuit gate in the line output device (Q901). This diagnosis will be confirmed if Q901 has h.t. at its anode and line drive at its gate. If there's no h.t. at Q901's anode when the fault is present, check the efficiency diode D806 for being short-circuit, then concentrate on the power supply. Check for voltage at the mains bridge rectifier's reservoir capacitor C606, then check the operation of the chopper transistor Q607.

QUERY COUPON

Available until 18th July 1984. One coupon, plus a £1.00 (inc. VAT) postal order, must accompany EACH PROBLEM sent in accordance with the notice above.

TELEVISION JULY 1984

RANK A823A CHASSIS

The problem is very bad patterning on the colour – it's not present on a monochrome picture. The decoder and i.f. panels have been replaced and the cause is not r.f. interference – it doesn't happen with a similar set.

A common cause of this problem is indifferent decoder panel earthing. This depends on contact between the panel earth print and the metal chassis bar. Ensure that both surfaces are clean and that the panel securing screws are tight. If this fails to cure the fault, check the i.f. panel earthing and that of the earth braids of the interconnecting leads. If necessary carry out decoder alignment as laid down in the manual, paying particular attention to the settings of the harmonic rejectors 3L12/13/14 and the items associated with the oscillator crystal (3TC1 and 3L1).

TEST CASE

259

Each month we provide an interesting case of television servicing to exercise your ingenuity. These are not trick questions but are based on actual practical faults.

All was tranquil in the workshop one Tuesday morn. The field engineers had left on their rounds, the phone was quiet, and our Jack-of-all-trades was dividing his attention equally between a recalcitrant VCR and the engineering announcements on Channel 4. Suddenly this somnolent scene was disturbed by a flood of light from the screen of a soak-testing ITT colour set – one of the CVC20 type. The job card showed that it stood accused of a "bright blank raster after thirty minutes". Just so!

Two checks with the Avo were made straight away. These showed that the first anode voltage was normal but that there was virtually zero voltage at the cathodes. This established, the set was put on the operating table, the VCR and TV programme being forgotten in the excitement – we had to tackle the fault before it disappeared, as experience had taught us it might.

Our first suspicion was that the 225V supply to the RGB output stages might be missing, but the heat rising from the collector load resistors indicated otherwise. The three BF458 output transistors were obviously hard on, with about 8V at each emitter. It didn't take long to find that this was because the TCA800 demodulator/matrixing chip was driving them to saturation, with over 9V coming from pins 3, 5 and 7. It became plain at this point that the job wasn't going to be a two-minute affair, so the c.r.t.'s heater feed was disconnected. Turning off the tube in this way would remove the strain on the tube, the tripler and the line output transformer. At the same time the decoder

panel was refitted on the print side of the panel to give easier access for our Sherlock Holmes.

The TCA800 is a straightforward chip. The luminance signal together with a d.c. bias voltage is fed in at pin 1. We confidently expected to find an outlandish voltage here, but it was almost exactly as specified at 1.9V. Voltage measurements were then made at the other relevant pins: these were a bit low at the clamp reservoir capacitor pins 2, 4 and 6, while there was about 1.6V instead of 1.8V at the pulse input pin 8. All other voltages were within a few per cent of normal. So after checking that the earth pin 16 was firmly grounded the chip itself was changed.

The new TCA800 produced the same results, and continued to do so when reduced to Arctic-like conditions with freezer. Back round the pins, with readings as before. Check that the clamp reservoir capacitors are grounded. Yes. R553 which is in series with the drive to the red output stage was then disconnected, bringing relief to this output stage. This proved that the trouble was at the chip side of things, though the primary cause could lie elsewhere...

The cause of the trouble was traced after a bit of scoping. If you should consult the block diagram of the TCA800 i.c. given in the service manual, the next step we took, don't be fooled by the absence of a connection that should have been shown but isn't. We'll explain this and the cause of the fault next month.

ANSWER TO TEST CASE 258

— page 447 last month —

Last month we were deep into the decoder of a Grundig Model 2222GB with no colour. We'd discovered that the basic cause of the fault was an unlocked reference oscillator, and had eliminated various possible causes. The set follows conventional practice, with the crystal reference oscillator controlled by a phase-locked loop. The heart of this is a discriminator that compares the oscillator's output with the burst signal. The discriminator produces an error voltage which biases a varicap diode in the oscillator circuit, pulling it into phase lock. Not when the discriminator diodes are leaky however! The items concerned are Di863 and Di868, type AA119. Being germanium devices, their leakage resistance is difficult to specify. These two had very different reverse readings however. The decoder seemed happy enough when a matched pair of OA90s was fitted, so we left it at that – after setting up the loop.

Finally the business of the test card clue to the colour-killer operation. As with a number of chassis, the 4.43MHz filter in the luminance channel is switched. The switch is within the TBA970 luminance chip: it's used to open-circuit the filter on a monochrome signal. The fact that the fourth frequency grating (4MHz) on the test pattern could be seen revealed that the trap was not in operation. We can't rely on the next grating (4.5MHz) for this, as not all shadowmask tubes can resolve it.

Published on approximately the 22nd of each month by IPC Magazines Limited, King's Reach Tower, Stamford Street, London SE1 9LS. Filmsetting by Trutape Setting Systems, 220-228 Northdown Road, Margate, Kent. Printed in England by The Riverside Press Ltd., Thanet Way, Whitstable, Kent. Distributed by IPC Magazines Ltd., Lavington House, 25 Lavington Street, London SE1 0PF. Sole Agents for Australia and New Zealand – Gordon and Gotch (A/sia) Ltd.; South Africa – Central News Agency Ltd. Subscriptions: Inland £11, overseas (surface mail) £12 per annum, payable to Quadrant Subscription Services Ltd., Oakfield House, Perrymount Road, Haywards Heath, Sussex RH16 3DH. "Television" is sold subject to the following conditions, namely that it shall not, without the written consent of the Publishers first having been given, be lent, resold, hired out or otherwise disposed of by way of Trade at more than the recommended selling price shown on the cover, excluding Eire where the selling price is subject to currency exchange fluctuations and VAT, and that it shall not be lent, resold, hired out or otherwise disposed of in a mutilated condition or in any unauthorised cover by way of Trade or affixed to or as part of any publication or advertising, literary or pictorial matter whatsoever. ISSN 0032-647X.

TV LINE OUTPUT TRANSFORMERS

FAST RETURN OF POST SERVICE

RANK BUSH MURPHY	PHILIPS
Z146 A640 dual std mono 7.00	170 series dual std mono 7.00
Bush A792, A793	210 300 series mono 7.00
single std mono 7.00	G8 & G9 series colour 8.00
A774 single std mono 7.00	PYE 169-173-569-368 7.00
A816 solid state mono 9.00	EKCO RV305-769-725-741 8.00
DECCA	WALTHAM 125 9.00
MS1700 2001 2020 2401 mono 7.00	REWIND SERVICE - available for most continental types, i.e. Kuba, Luxor, Korting, Tyne, Berry Skantic, K80 £15.00 inc pp, VAT. Old lopt required.
MS2404 2420 2424 mono 7.00	WINDINGS
CS1730 1733 colour 8.00	SOVEREIGN 14" colour overwind 15.00
CS1830 1835 colour 8.00	SONY 1320UB overwind 15.00
'30' series Bradford colour 8.00	RANK BUSH MURPHY
80 series colour 8.00	T20a T22 Pry & Sec 6.00
100 series colour 8.00	Z718 series primary 6.00
FERGUSON HMV MARCONI	Z718 series EHT overwind 7.00
1600 8.00	ULTRA THORN
G.E.C.	1690 1691 EHT overwind 7.00
2047 to 2105 7.00	1590 6.00
2000 to 2064 dual std mono 7.00	PYE
DUAL STD hybrid colour 8.00	691 to 697 EHT overwind 4.00
SINGLE STD hybrid colour 8.00	691 to 697 primary 5.00
Indesit 20EGB 24EGB mono 9.00	
KB - ITT	
VC200 VC205 VC207 mono 7.00	
CVC5 CVC7 CVC8 CVC9 col. 8.00	
CVC20 series colour 8.00	
CVC30 CVC32 series colour 8.00	
CVC45 8.00	

All lopts and windings are new and guaranteed

Open Mon.-Fri. 9 to 5.30 pm
Delivery normally by return.

PAPWORTH TRANSFORMERS

80 Merton High Street,
London SW19 1BE

S.A.E. all enquiries
Barclaycard and
Access welcome



01-540 3955

For orders placed at the post office
Trans cash 505 4856

ELECTRON GUNS TV TUBE COMPONENTS

If you are Rebuilding or Manufacturing TV tubes - We are the leading suppliers of Electron Guns and TV Tube Components to the TV Tube Industry. We specialise in all aspects of Electron Mount Technology.

Our product range includes more than 250 gun types for Colour, In Line, Mono and Display Tubes along with Mount Parts, Bases, Getters, Seal-offs, and all other associated items for TV Tube Production.

A Full Technical Back-up and Advisory Service is available to all customers World-wide.

Please request our current catalogues and Data Information.




GRIFTRONIC EMISSION LTD
NEW ROAD,
STUDLEY,
WARWICKSHIRE B80 7LJ
ENGLAND.

Telephone: 052-785 2684 or 2639 Telex: 336924 Grifem G.

TELEPART

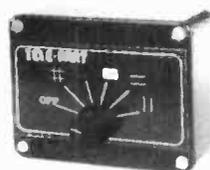13 WORCESTER ST.,
WOLVERHAMPTON,
WV2 4LJ
Tel: (0902) 773122
Telex: 336810



Telepart Pattern Generator

- * Exceptionally light and durable
- * Pocket size for outside service
- * PP3 battery power source
- * Five different test patterns for colour and mono TV
- * Cross hatch grid
- * Dot matrix
- * White raster
- * Horizontals
- * Vertices

A lightweight, extremely portable and versatile pattern generator for black/white and colour T.V. alignment and service at the customers home. At the turn of a switch, the generator can provide five essential test patterns for correct installation, fast checks and repairs. Pattern stability is first class and compares favourably with other more costly bulky generators only suitable for bench work. The generator is pocket size measuring 10x7.5x4 cm and weighs only 190 grams.

PRICE £14.95 (Subject to V.A.T.) POST & PACKING £1.15

New from Newnes

SERVICING DIGITAL CIRCUITS IN TV RECEIVERS

R Fisher

Specifically for colour television engineers, this book is an in-depth guide to digital circuits used in current TV receivers. The early chapters deal with digital techniques and their specific applications like teletext and videotex, their respective decoders being described in detail. Remote control systems, digital tuning and other digital circuits are also covered. A glossary of terms is included which will be useful to both engineers and students.

Softcover 288 pages £13.95

BEGINNER'S GUIDE TO COLOUR TELEVISION

Third Edition

Gordon J King — revised E Trundle

Colour TV has been greatly developed since it was first introduced in the UK in 1967. This new edition has been re-written to include, as well as the basic introduction to the subject, an up to the minute account of such innovations as satellite and cable, flat panel receivers, 3-D displays and "digitization" of TV signals.

Softcover 192 pages £4.50

Also of interest

BEGINNER'S GUIDE TO TELEVISION

Sixth Edition

Gordon J King — revised E Trundle

An introduction, with the minimum of mathematics, to the techniques and equipment used in television broadcasting, recording and reception.

Softcover 240 pages £4.50

BEGINNER'S GUIDE TO RADIO

Ninth Edition

Gordon J King

An introduction to radio principles and practice - ideal for radio and telecommunications technicians and students. Gordon King has updated the text to take account of recent technological changes.

Softcover 272 pages £4.50

Order now from your Bookseller or direct from

Newnes Technical Books

Borough Green, Sevenoaks, Kent TN15 8PH

ECONOMIC DEVICES, PO BOX 228, TELFORD TF2 8QP

16029	1.56	2SC1061	0.54	2SD898B	2.67	AN320	4.97	BC171	0.10	BD186	0.38	BF137	0.11	BLY49	2.00	BY203/20	0.18
16181	1.13	2SC1066	1.00	40408	0.45	AN322	4.30	BC172	0.09	BD188	0.06	BF152	0.20	BR100	0.20	BY206	0.17
16182	1.13	2SC1104	2.60	40594	1.39	AN331	2.99	BC172B	0.24	BD175	0.29	BF153	0.52	BR101	0.37	BY207	0.22
16334	0.80	2SC1106	4.12	40595	1.39	AN337	1.39	BC173	0.15	BD177	0.39	BF154	0.23	BR103	0.45	BY210-400	0.24
16335	0.72	2SC1114	5.61	40636	0.86	AN340P	1.06	BC174B	0.24	BD179	0.44	BF157	0.23	BR88B	0.56	BY210-600	0.27
16446	0.89	2SC1124	1.10	40871	1.39	AN355	3.36	BC177	0.18	BD181	0.90	BF158	0.16	BRC-M-300	1.50	BY210-800	0.30
16800	1.25	2SC1151A	4.29	40872	1.39	AN362	1.47	BC178	0.23	BD182	0.90	BF159	0.16	BRC116	0.80	BY223	0.85
16799	0.16	2SC1152	4.25	60857	1.10	AN5111	1.10	BC179	0.23	BD183	0.90	BF160	0.20	BRC1330	1.60	BY224-400	0.90
16801	2.06	2SC1157	4.12	74LS132	0.72	AN5132	3.94	BC182	0.08	BD184	1.10	BF167	0.30	BRC300	1.82	BY225-100	0.79
16802	1.03	2SC1162	0.95	74LS138	0.85	AN5250	3.33	BC182B	0.23	BD187	0.40	BF173	0.30	BRC4443	1.12	BY226	0.28
16803	4.81	2SC1172	1.92	74LS157	0.79	AN5435	2.80	BC182L	0.09	BD189	0.35	BF177	0.50	BRC4444	1.12	BY227	0.44
16905	1.35	2SC1195	2.03	74LS161A	1.18	AN5610	6.75	BC182LB	0.12	BD190	0.59	BF178	0.36	BRC5296	0.70	BY228	0.54
17074	6.00	2SC1213	0.75	74LS196	1.25	AN5613	3.72	BC183	0.09	BD201	0.54	BF179	0.32	BRC6109	0.75	BY255	0.97
17127	3.91	2SC1226	1.32	74LS200	0.25	AN5620X	4.63	BC183L	0.09	BD202	0.54	BF180	0.32	BRC82	0.98	BY298	0.25
17375	1.43	2SC1306	0.85	74LS244	1.65	AN6320N	3.89	BC183LB	0.23	BD203	0.54	BF181	0.29	BRC83	0.98	BY299	0.25
1N4001	0.05	2SC1307	1.35	74LS300	0.29	AN6342	1.36	BC184	0.09	BD204	0.54	BF182	0.30	BRC84	0.98	BY476A	0.76
1N4002	0.05	2SC1316	3.40	74LS367	1.05	AN6344	4.68	BC184L	0.09	BD207	1.00	BF183	0.35	BRCC4	0.54	BYW56	0.70
1N4003	0.05	2SC1364	0.49	74LS373	1.55	AN6363	10.20	BC184LB	0.23	BD208	1.00	BF184	0.39	BRX49	0.45	BYX10	0.28
1N4004	0.06	2SC1383	1.39	74LS447	1.05	AN6551	0.56	BC186	0.24	BD222	0.44	BF185	0.35	BRX39	0.50	BYX55-350	0.40
1N4005	0.07	2SC1398	0.51	74LS73	0.39	AN6552	0.52	BC187	0.18	BD225	0.44	BF194	0.15	BRX55	0.60	BYX55-600	0.25
1N4006	0.06	2SC1410	2.17	74LS74	0.39	AN7145	2.04	BC204	0.14	BD228	0.57	BF195	0.12	BRX56	0.38	BYX71-350	0.67
1N4007	0.07	2SC1413	3.68	74LS75	0.52	AN7150	2.22	BC207	0.12	BD229	0.63	BF196	0.15	BSR59	1.17	BYX71-600	0.85
1N4148	0.03	2SC1505	0.56	74LS86	0.49	AN7151	2.05	BC212	0.10	BD231	0.45	BF197	0.14	BSS38	0.30	BYX94	0.18
1N4448	0.12	2SC1578	6.67	74LS90	0.75	AN7156	2.05	BC212B	0.23	BD232	0.44	BF198	0.15	BSTBD1409	2.48	BYW56	1.09
1N5401	0.12	2SC1817	3.25	74LS92	0.75	AN7158	2.34	BC212L	0.09	BD234	0.38	BF199	0.15	BSTBD1405	4.37	BZV15-C12	0.72
1N5402	0.13	2SC1870	1.25	74LS93	0.75	AN7218	1.49	BC212LB	0.23	BD235	0.43	BF200	0.33	BSTC0146	2.25	BZV15-C12R	0.72
1N5403	0.14	2SC1878	1.49	74LS95B	0.85	AP58076	4.25	BC213	0.09	BD236	0.45	BF216	0.32	BSTC0236	2.25	BZV15-C24	0.72
1N5404	0.15	2SC1810	1.49	7805 TO-220	0.63	AS5805	1.43	BC213L	0.09	BD237	0.38	BF218	0.32	BSTC0246	4.51	BZV15-C24R	0.72
1N5408	0.18	2SC1815	0.41	7805 TO-3	1.05	AU106	1.96	BC213LB	0.23	BD238	0.29	BF222	0.50	BSTC1233	3.91	BZV15-C30R	0.72
1N914	0.05	2SC1829	2.01	7806	0.66	AU110	1.95	BC214	0.08	BD239	0.44	BF224	0.15	BSTC3146	0.71	BZX61 Range	0.16
1S44	0.06	2SC1875	4.77	7808	0.54	AU113	2.12	BC214L	0.12	BD240	0.36	BF237	0.59	BSTC0143	2.79	BZX70-C11	0.54
1S5012A	0.73	2SC1891	3.35	7812 TO-3	0.54	AV102	2.65	BC214LB	0.23	BD240D	0.47	BF240	0.15	BSTC0643	3.08	BZX70-C12	0.54
1S921	0.09	2SC1929	2.25	7812 TO-220	1.05	AV105K	1.89	BC225	0.24	BD241	0.45	BF241	0.15	BSTC0643	2.66	BZX70-C15	0.54
2582	1.94	2SC1942	5.70	7815	0.55	AY106	1.98	BC227	0.09	BD242	0.45	BF244	0.23	BSW68	0.38	BZX70-C30	0.54
2N1302	0.24	2SC1945	4.11	7818	0.55	BA102	0.90	BC228	0.09	BD243	0.44	BF245A	0.33	BX19	0.30	BZX70-C47	0.54
2N1303	0.34	2SC1953	1.75	7824	0.55	BA1310 (IC)	1.70	BC238A	0.11	BD243A	0.50	BF255	0.18	BX20	0.30	BZX79 Range	0.89
2N2218	0.28	2SC1957	0.86	AC107	0.86	BA1320 (IC)	1.22	BC238B	0.08	BD244	0.44	BF256	0.25	BX21	0.45	BZX79 Range	0.89
2N2219A	0.39	2SC1959	0.36	AC117	0.39	BA1330 (IC)	1.82	BC251A	0.12	BD244A	0.77	BF256C	0.38	BSY52	0.45	BZY93-C12	0.99
2N2222	0.34	2SC1962	1.75	AC123K	0.39	BA145	0.17	BC252	0.12	BD245C	0.88	BF257	0.30	BSY79	0.46	BZY93-C18	0.99
2N2646	0.75	2SC1969	2.92	AC128	0.28	BA154	0.08	BC258	0.22	BD246C	0.74	BF258	0.29	BT100A	1.46	BZY93-C24	0.99
2N2904	0.32	2SC2027	2.67	AC138	0.88	BA155-01	0.12	BC261A	0.20	BD253	0.95	BF259	0.30	BT106	1.20	BZY93-C24R	0.99
2N2905	0.39	2SC2028	1.91	AC141	0.28	BA156	0.12	BC262	0.20	BD278A	0.80	BF262	0.51	BT108	1.31	BZY93-C30	0.99
2N2906	0.34	2SC2029	1.49	AC142K	0.39	BA157	0.12	BC262	0.17	BD278B	1.96	BF263	0.51	BT109	1.31	BZY93-C47	0.99
2N3063	0.24	2SC2057	1.07	AC151	0.25	BA159	0.12	BC294	0.45	BD318	2.08	BF264	0.33	BT112	2.25	BZY93-C68	0.99
2N3064	0.90	2SC2073	1.40	AC153	0.30	BA182	0.17	BC301	0.30	BD375	0.38	BF271	0.30	BT113	2.25	BZY93-C7V5	0.99
2N3065	0.55	2SC2078	1.25	AC153K	0.36	BA222 (IC)	1.26	BC302	0.30	BD377	0.23	BF273	0.18	BT116	1.52	ZTK33	0.39
2N3065H	0.77	2SC2091	0.59	AC176	0.17	BA294/2	1.15	BC303	0.34	BD379	0.89	BF274	0.18	BT119	1.80	ZK18	2.47
2N3442	1.05	2SC2122A	4.85	AC176K	0.40	BA301 (IC)	0.92	BC307	0.09	BD380	0.89	BF324	0.16	BT120	1.60	C106D	0.46
2N3702	0.12	2SC2141	1.89	AC179	0.25	BA302	1.00	BC307A	0.14	BD410	0.44	BF336	0.27	BT121	2.25	C1129	0.52
2N3703	0.12	2SC2166	1.35	AC183	0.85	BA311 (IC)	0.96	BC308	0.12	BD412	5.70	BF337	0.36	BT122	2.25	CA1310E	2.45
2N3704	0.12	2SC2216	0.82	AC186	0.30	BA312 (IC)	0.90	BC308A	0.09	BD418	0.78	BF338	1.80	CA294	1.80	CA310E	3.18
2N3705	0.12	2SC2233	2.20	AC186K	0.50	BA313 (IC)	1.28	BC309	0.15	BD433	0.32	BF355	0.36	BT123	2.25	CA304E	2.23
2N3706	0.12	2SC2271	3.84	AC187	0.35	BA316	0.07	BC317A	0.07	BD434	0.29	BF362	0.54	BT126	2.25	CA306D	1.50
2N3707	0.14	2SC2278	1.03	AC187-01	0.40	BA317	0.47	BC323	0.92	BD435	0.42	BF363	0.54	BT128	2.25	CA308E	1.17
2N3711	1.14	2SC2335-KIT	7.61	AC187K	0.39	BA318	0.80	BC327	0.15	BD436	0.42	BF371	0.45	BT128P	2.79	CA3089	3.35
2N3711	0.85	2SC2526	1.70	AC188	0.33	BA328 (IC)	0.80	BC328	0.10	BD437	0.41	BF391	0.36	BT129	2.25	CA309E	1.30
2N3772	1.55	2SC2551	0.90	AC188-01	0.40	BA333 (IC)	1.24	BC337	0.08	BD438	0.44	BF393	0.90	BT151-800R	1.47	CA3090	1.25
2N3773	1.86	2SC2570	1.95	AC188K	0.39	BA401 (IC)	0.58	BC338	0.10	BD441	1.29	BF417	1.20	BT151 500R	2.80	CA309A	2.80
2N3819	1.20	2SC2570A	0.95	AC133K	0.59	BA511 (IC)	1.91	BC360	0.30	BD442	0.56	BF418	1.70	BT8019	2.20	CA3131E	2.03
2N3823	0.28	2SC2644	4.38	AC194K	0.59	BA521 (IC)	1.88	BC368	0.22	BD507	0.54	BF422	0.26	BT8218	2.80	CA3132E	2.83
2N3904	0.58	2SC2671	1.99	AD140	0.96	BA532 (IC)	1.88	BC440	0.99	BD508	0.54	BF423	0.26	BT802A	4.22	CAH78023N	6.00
2N3906	0.58	2SC2728	0.96	AD142	0.96	BA536 (IC)	2.72	BC441	0.40	BD509	1.29	BF435	0.49	BT821A	4.44	CBF16848N-07	1.41
2N4101	1.10	2SC372	1.27	AD143	0.96	BA539A (IC)	2.65	BC454	0.32	BD510	0.45	BF450	0.38	BT821A	5.44	CD4001	2.00
2N4240	3.00	2SC373	1.05	AD145	1.45	BA543 (IC)	3.00	BC455	0.32	BD518	1.36	BF451	0.26	BT822A	2.70	CD4002	0.24
2N4443	1.35	2SC383	1.20	AD149	0.81	BAV10	0.18	BC460	0.28	BD519	1.36	BF457	0.37	BU105	1.86	CD4008	0.96
2N4444	1.12	2SC386	0.45	AD161	0.30	BAV18	0.10	BC461	0.42	BD529	0.38	BF458	0.35	BU106	2.25	CD4011	0.23
2N4914	0.85	2SC411	1.99	AD262	0.30	BAV19	0.10	BC462	0.27	BD530	0.80	BF459	0.35	BU108	1.90	CD4012	0.24
2N5084	0.04	2SC458	0.55	AD262	0.95	BAV20	0.10	BC463	0.58	BD533	0.80	BF460	0.54	BU108S	1.90	CD4013	0.37
2N5293	0.45	2SC495	0.83	AF114	2.24	BAV21	0.17	BC464	0.58	BD534	0.36	BF469	0.27	BU110	2.52	CD4016	0.37
2N5294	0.45	2SC508	3.36	AF115	0.79	BAX12	0.10	BC465	0.58	BD535	0.44	BF470	0.28	BU111Y	1.78	CD4017	0.74

ECONOMIC DEVICES, PO BOX 228, TELFORD TF2 8QP

ESM532C	4.18	LM1303P/N	1.50	MPSU05	0.70	SAA5010	4.90	SN74190	1.81	T6029V	4.41	TBA395	1.35	TDA1230	2.93	TD49503	2.80
ESM632C	4.18	LM1310P/N	1.25	MPSU10	0.70	SAA5012	6.50	SN7420N	0.30	T6032V	0.89	TBA395Q	1.80	TDA1235	3.52	TD49513	2.40
ESM732C	4.18	LM3085N	0.77	MPSU55	0.90	SAA5020	5.25	SN7430	0.28	T6033V	0.73	TBA396	1.80	TDA1270	2.84	TE538	1.25
ETT8016	2.85	LM3173CK	1.30	MPSU56	0.30	SAA5030	7.50	SN7440N	0.24	T6035V	0.06	TBA400	2.17	TDA1327A	1.85	TE626	0.36
FTD9016	2.16	LM339N	0.08	MPSU80	1.20	SAA5040A	14.75	SN7473	0.56	T6036	0.44	TBA440P	1.55	TDA1327B	1.85	TE626	1.35
FND500	5.25	MR3407	1.25	MR510	0.30	SAA5050	8.50	SN7474N	0.72	T6037	1.91	TBA480	1.42	TDA1330	1.00	TEA1002	3.15
FT3055	1.85	LM340T5	0.75	MR812	0.80	SAA681B	1.80	SN7490AN	0.93	T6041V	0.86	TBA480Q	1.97	TDA1365	6.35	TEA1009	5.96
GF758	0.82	LM340T12	0.75	MR914	0.46	SAA700	3.00	SN75110N	0.75	T6044V	0.86	TBA500PQ	1.45	TDA1412	0.95	TEA1020S/P	0.34
GF759	1.82	LM340T5	0.75	MSSD7002	0.85	SAB1009B	4.53	SN76001ANQ	2.25	T6045	1.09	TBA510	1.55	TDA1420	1.48	TEA1067	0.46
GF781	0.78	LM342N	0.56	MVS240	0.52	SAB1049P	3.66	SN76003N	2.81	T6049	1.10	TBA510S	1.60	TDA1470	2.63	TIC106C	0.55
GH3F	1.85	LM3940N1	1.84	MVS480	0.30	SAB3011	7.34	SN76013N	3.63	T6052V	0.76	TBA520	1.87	TDA1512	2.20	TIC106M	0.50
HA11211	2.30	MVS67CN	1.30	MVS480-02	0.55	SAB3012	5.34	SN76013NDG	2.25	T6059	0.46	TBA520Q	1.35	TDA1670	3.85	TIC160B	0.85
HA11215	4.00	LM748	1.65	ME545B	2.95	SAB3013	3.20	SN76013NDG	0.07	T6059	1.05	TBA530	0.86	TDA1770	5.56	TIC44	0.85
HA11225	3.90	LM8360	2.78	ME545B	3.80	SAB3021	7.18	SN76023N	2.35	T8001V	1.89	TBA530Q	0.86	TDA1905	1.25	TIC45	0.70
HA11226	7.56	LM8361	2.78	ME5534N	1.40	SAB3022B	12.34	SN76023ND	1.04	T9003V	0.86	TBA540	0.98	TDA1908	2.95	TIC47	0.70
HA11229	2.51	M1024	2.55	ME555	0.34	SAB3022B	11.18	SN76033N	2.33	T9005V	2.16	TBA540Q	1.15	TDA1910	2.38	TIP120	0.98
HA11235	3.80	M1025	4.70	ME556	0.75	SAB3024	4.77	SN76105N	2.36	T9010V	0.87	TBA550	1.95	TDA1940	2.54	TIP110	0.48
HA1124	4.70	M1124	2.54	ME560N	3.16	SAB3209	4.75	SN76110N	1.13	T9011V	1.27	TBA550Q	2.25	TDA1950	2.54	TIP112	0.80
HA11244	4.32	M1130	4.06	ME565N	1.20	SAB3210	2.93	SN76115AN	1.46	T9013V	5.81	TBA560C	0.86	TDA2002	1.20	TIP117	0.86
HA11245	3.90	M191	5.74	ME645B	3.80	SAB4209	12.75	SN76131	1.74	T9014V	1.52	TBA560CQ	1.15	TDA2003	1.05	TIP120	0.73
HA11251	3.30	M193	18.55	ME646N	3.80	SAF1031	2.30	SN76226N	1.20	T9016	0.92	TBA570	1.55	TDA2004	2.52	TIP121	1.00
HA1137W	2.57	M51102L	4.02	ME650N	3.94	SAF1032	5.80	SN76227N	0.68	T9022N	0.39	TBA570A	1.56	TDA2006	1.25	TIP126	0.98
HA1138	3.58	M5115P	4.34	ME645B	3.80	SAF1039	11.86	SN76228N	2.97	T9034V	1.25	TBA570Q	1.35	TDA2010	2.79	TIP127	1.30
HA11414	2.50	M51231P	2.79	MP1106	4.00	SAS5010	7.82	SN76231	2.31	T9035V	1.26	TBA625A	1.97	TDA2020	2.75	TIP2955	1.70
HA1144	6.38	M5124P	4.38	DA200	0.10	SAS560	1.80	SN76242	4.75	T9039V	6.15	TBA625B	1.97	TDA2030	1.65	TIP29A	0.41
HA1156	1.23	M5134-9341	3.75	DA202	0.10	SAS560S	2.97	SN76243	4.75	T9051V	2.55	TBA625C	1.97	TDA2140	1.44	TIP29B	0.57
HA11580	7.80	M51394P	6.25	DA47	0.10	SAS560T	2.85	SN76252	2.51	T9053V	1.83	TBA641A12	3.75	TDA2150	5.63	TIP29C	0.40
HA1180	3.45	M5142P	4.38	DA90	0.07	SAS570	1.81	SN76360	1.97	T9054V	0.92	TBA641BX1	1.80	TDA2151	1.75	TIP3055	0.85
HA1186	3.08	M5143P	6.06	DA91	0.08	SAS570S	0.00	SN76390	2.80	T9057V	0.83	TBA651	1.80	TDA2160	3.64	TIP30A	0.41
HA1187	5.13	M5144P	3.42	DA95	0.08	SAS570T	2.50	SN76396	2.63	T9063V	2.94	TBA673	1.80	TDA2161	1.80	TIP30B	0.63
HA11711	16.13	M51513L	2.06	DC28	0.96	SAS580	4.41	SN76510N	0.95	TA5814	1.35	TBA700Q	2.19	TDA2190	3.11	TIP31B	0.35
HA11713	6.70	M51515BL	3.10	DC29	1.95	SAS5800	2.82	SN76530P	1.90	TA7020P	4.36	TBA720	2.85	TDA2510	1.82	TIP31C	0.63
HA11714	7.05	M51516L	3.40	DC36	0.96	SAS590	4.55	SN76532N	1.80	TA7027	4.36	TBA730	1.75	TDA2520	2.15	TIP32B	0.35
HA11715	7.95	M51517L	2.90	DC36	1.16	SAS5900	2.32	SN76533N	1.56	TA7050	1.58	TBA750Q	1.46	TDA2521	2.15	TIP32C	0.66
HA11718	6.79	M5152L	1.00	DC44	0.40	SAS680	2.50	SN76540N	1.80	TA7051	1.58	TBA780	1.55	TDA2522	2.81	TIP33C	1.25
HA11724	15.80	M51522	4.00	DC46	0.40	SAS680Q	1.20	SN76544	1.60	TA7080AP	0.80	TBA780	3.00	TDA2523	2.75	TIP34	1.07
HA11725	16.80	M5191P	4.49	DC75	0.40	SAS680S	1.20	SN76545	4.55	TA7061AP	0.78	TBA800	0.00	TDA2524	4.50	TIP41A	0.39
HA1180	4.88	M5192	2.00	DN188	1.70	SAS6810	1.20	SN76546	3.15	TA7069	2.84	TBA810AS	1.46	TDA2525	2.96	TIP41B	0.28
HA1203	1.56	M53273P	0.92	DN236	2.50	SAS670	2.50	SN76546N	3.15	TA7070P	1.52	TBA810S	1.46	TDA2530	2.19	TIP41C	0.44
HA1306	1.74	M53274P	1.20	DT112	0.98	SAS670Q	1.20	SN76549	2.35	TA7071	3.35	TBA810T	1.46	TDA2531	2.51	TIP42A	0.39
HA1322	1.74	MA06	0.97	DT121	0.70	SAS670S	1.20	SN76550	0.30	TA7072P	1.35	TBA820	0.83	TDA2533	2.09	TIP42B	0.71
HA1339	1.76	MA8001	0.74	PD144	2.83	SAS6710	1.20	SN76551	1.35	TA7073P	4.05	TBA820M	1.65	TDA2540	1.95	TIP42C	0.44
HA1342	1.80	MB3705	1.62	PT1017	2.43	SAS6800	2.30	SN76570	2.80	TA7074P	1.95	TBA890	1.85	TDA2541	1.95	TIP47	0.65
HA1350	2.97	MB3712	2.65	PT2014	2.76	SAS6810	1.30	SN76600	1.10	TA7076Q	4.95	TBA900	2.25	TDA2545	3.16	TIP48	0.83
HA1365	3.85	MB3713	1.30	PT6042	1.82	SBA550B	1.95	SN76611	2.35	TA7089N	1.41	TBA920	1.50	TDA2560	1.97	TIP49	3.20
HA1366WR	1.82	MB3730	2.94	R1038	1.99	SBA750	1.46	SN76620	2.35	TA7089P	1.36	TBA920Q	2.10	TDA2571A	2.81	TIS43	1.21
HA1367	3.20	MC13002	4.86	R1039	1.99	SC948P	1.90	SN76622	1.50	TA7092P	3.85	TBA940	1.70	TDA2575A	2.95	TIS90	0.22
HA1368	1.69	MC1303P	0.96	R2008B	1.20	SC9503	1.50	SN76623	0.62	TA7093P	1.64	TBA950	1.55	TDA2576A	2.58	TIS91	0.26
HA1368R	1.86	MC1307P	1.90	R2009	1.20	SC9504P	1.46	SN76630	2.31	TA7132P	5.34	TBA970	2.08	TDA2577	5.31	TL071CP	2.02
HA1370	2.97	MC1310P	1.25	R2001B	1.20	SC9511P	1.90	SN76640	3.85	TA7138P	1.40	TBA970Q	2.98	TDA2581	1.95	TM51000NL	10.78
HA1377	2.88	MC1327P	1.20	R2029	1.20	SCR957	1.20	SN76650N	1.24	TA7139	0.37	TBA990	1.65	TDA2582	1.98	TM53748NS	11.86
HA1389	1.62	MC1330P	1.23	R2030	1.20	SG2644	4.38	SN76651	1.35	TA7120P	3.50	TBA990Q	1.95	TDA2580	2.80	TM54116	1.87
HA1389R	1.62	MC1349P	1.20	R2257	1.16	SG613	7.88	SN76660N	2.25	TA7122B/P	0.54	TBA231	2.33	TDA2581	2.80	TV106	1.20
HA1392	2.88	MC1350P	1.10	R2265	1.95	SG629	6.28	SN76665S	1.35	TA7124P	2.00	TC4001	1.29	TDA2581Q	2.80	TV8010B	2.70
HA1397	2.97	MC1351P	0.75	R2305	1.07	SG6533	9.37	SN76666N	0.98	TA7130P	1.15	TC4053BP	1.62	TDA2583	2.24	U05G	1.03
HA1398	2.88	MC1352P	1.01	R2306	1.23	SI-1020N	4.76	SN76705	3.38	TA7136AP	1.15	TC1A150	3.94	TDA2584	2.80	U143M	2.80
HA1406	1.80	MC1357P	1.95	R2322	1.26	SI-1125HD	10.36	SN76705N	3.99	TA7137P	0.85	TC1A160B	1.62	TDA2600	5.00	U3700	0.55
HA17723	5.40	MC1358P	1.55	R2323	1.23	SI-1130N	6.70	SN76707N	3.99	TA7141AP	3.51	TC1A270Q	1.55	TDA2610	2.53	U3700C	0.44
HF4050AF	2.25	MC14001	7.15	R2348	1.82	SKB2/08	0.78	SN76709	4.65	TA7146P	8.04	TC1A270S	1.95	TDA2611A	1.25	UA723CA	5.02
HD4801A05	15.60	MC14011	0.23	R2354A	1.82	SKE2F/104	1.26	SN76709N	4.95	TA7148P	6.51	TC1A270SQ	1.65	TDA2611AQ	2.55	UA758PC	3.06
HM6231	7.71	MC14013	0.37	R2354B	1.82	SKE2G/204	0.95	SN76730	4.23	TA7149P	2.10	TC1A290A	2.05	TDA2612Q	4.25	UA787P3C	1.87
HM6232	7.71	MC14018CP	0.37	R2441	1.23	SKE2G/304	0.95	SN76810N	0.62	TA7153P	4.53	TC1A420A	1.90	TDA2620	1.96	UA1030	2.04
HM6233	7.71	MC1402S	0.54	R2443	0.80	SKE4F/102	1.26	SN76920N	2.63	TA7161P	5.66	TC1A440	1.95	TDA2630	2.34	UA180	1.15
HM9102	2.92	MC14049UBC	0.52	R2461	2.10	SKE4F/106	0.66	SN94041	3.45	TA7162P	4.25	TC1A4500A	1.65	TDA2631	2.48	ULN1265	3.25
HM9104	2.94	MC1438R	0.95	R2471	0.92	SKE4F/206	2.18	SN94042	3.95	TA7169	4.80	TC1A530	1.80	TDA2640	2.25	ULN2204	7.00
HT4207	1.87	MC14493P	2.56	R2507	1.16	SKE4F/208	0.68	SP8385	0.50	TA7171P	2.53	TC1A630	2.63	TDA2643	6.23	ULN2216F	1.95
IS689	1.87	MC14510BAL	3.15	R2540	1.80	SKE4G/202	0.87	ST4A41C	2.27	TA7172P	1.20	TC1A650	1.85	TDA2651	2.95	UPC1001H	2.50
IT7203	0.20	MC1712	3.52	R2615	0.80	SL1310	2.85	STK0029	3.42	TA7176P	4.44	TC1A660B	2.65	TDA2652	7.05	UPC1009C	5.74
K1747P	2.95	MC7724CP	3.17	RC4195NB	1.96	SL1327E	1.20	STK0039	4.00								

AA117	0.09	BC182	0.06	BD232	0.31	BU111	1.40	OCP71	1.80	TIP32	0.24	IN.914	0.02	2SB337	1.20	VALVES	PCL85	0.55	LM390	0.25	BRIDGE		
AA119	0.09	BC182L	0.06	BD237	0.21	BU126	0.70	ORP12	1.00	TIP32A	0.24	IN.4001	0.04	2SB405	0.22	DY87	0.53	PCL86	0.55	NE565	0.15	RECTIFIERS	
AA132	0.09	BC183	0.06	BD238	0.24	BU204	0.75	ORP60	1.20	TIP33	0.59	IN.4002	0.04	2SC480	0.21	DY802	0.45	PCL805	0.55	NE566	0.40	1A/50V	0.18
AC107	0.20	BC183L	0.06	BD433	0.28	BU205	0.70	ORP61	1.20	TIP34	0.50	IN.4003	0.04	2SC495	0.00	ECC82	0.40	PFL200	0.85	BYX55/	0.80	1A/100V	0.18
AC126	0.17	BC184	0.06	BD437	0.28	BU208	0.75	R2008	0.80	TIP41A	0.22	IN.4004	0.04	2SC573	0.40	ECC83	0.43	PL36	0.80	350	0.30	1A/200V	0.19
AC127	0.15	BC184L	0.06	BD535	0.38	BU208A	1.20	R2008B	0.80	TIP42A	0.25	IN.4005	0.04	2SC1181	1.00	ECC84	0.40	PL504	0.95	BYX55/	0.80	1A/400V	0.21
AC128	0.15	BC184	0.06	BD536	0.38	BU208D	1.20	R20108	0.80	TIP42C	0.25	IN.4006	0.04	2SC1172Y	1.50	ECC85	0.40	PL508	1.90	600	0.30	1A/600V	0.23
AC128K	0.23	BC212L	0.06	BD537	0.40	BU426	0.85	SAS560	1.10	TIP47	0.40	IN.4147	0.82	2SC1279	0.24	ECH81	0.49	PY81	0.70	BYX55/	0.80	1A/800V	0.20
AC141K	0.23	BC213	0.06	BD538	0.40	BU406	0.85	SAS570	1.10	TIP48	0.40	IN.5400	0.09	2SC1306	1.00	ECH84	0.52	PY88	0.40	600	0.30	2A/200V	0.36
AC142K	0.22	BC213L	0.06	BDX32	1.00	BU407	0.75	SN78013N	1.40	TIP49	0.40	IN.5402	0.10	2SC1307	1.00	ECL80	0.57	PY500A	1.00	BYX55/	0.80	2A/400V	0.42
AC153K	0.23	BC214	0.06	BDX65	0.80	BU408	1.00	SN78023N	1.40	TIP110	0.57	IN.5403	0.11	2SC1520	0.25	ECL82	0.59			800	0.32	2A/800V	0.54
AC176	0.18	BC214L	0.06	BF180	0.16	BU500	1.10	SN78033N	1.50	TIP112	0.54	IN.5404	0.11	2SC2029	1.20	ECL84	0.57			500	0.29	2A/800V	0.58
AC176K	0.20	BC237	0.07	BF181	0.16	BU526	0.80	SN78226	0.90	TIP115	0.45	IN.5405	0.12	2SC2078	1.20	ECL86	0.49	BZY88 Range	2V7 to 39V 0.08	500	0.31	3A/400V	0.70
AC187	0.15	BC238	0.07	BF183	0.20	BY126	0.08	SN78227	0.80	TIP117	0.56	IN.5406	0.13	2SC2122A	2.00	EF80	0.31	1.3V Zeners		500	0.31	3A/400V	0.80
AC187K	0.20	BC300	0.16	BF184	0.20	BY127	0.08	SN78110N	0.70	TIP125	0.47	IN.5407	0.13			EF85	0.34	BZX61 Range	2V7 to 39V 0.12	800	0.36	6A/200V	1.00
AC188	0.17	BC301	0.18	BF185	0.20	BY133	0.08	SN78115	0.70	TIP128	0.56	IN.5408	0.13			EF89	0.43	Met		800	0.30	6A/400V	0.80
AC188K	0.23	BC302	0.18	BF194	0.05	BY184	0.22	SN78227	0.80	TIP127	0.47	IN.5408	0.13			EF89	0.43			800	0.30	25A/100V	1.80
ACY18	0.40	BC303	0.18	BF195	0.05	BY176	0.85			TIP265	0.72					EF89	0.43			800	0.30		
ACY19	0.40	BC327	0.06	BF196	0.06	BY179	0.35	T28000	0.52	TIP265A	0.72					EF89	0.43			800	0.30		
AD142	0.80	BC362	0.06	BF199	0.06	BY182	0.32	TAG06-60	0.42	TIP265B	0.72					EF89	0.43			800	0.30		
AD149	0.45	BC337	0.06	BF200	0.16	BY184	0.32	TAG52-1		TIP265C	0.72					EF89	0.43			800	0.30		
AD181	0.22	BC328	0.06	BF257	0.18	BY187	0.32	200		TIP305A	0.34					EF89	0.43			800	0.30		
AD182	0.22	BC357	0.06	BF258	0.18	BY196	0.20	TAG4443	0.76	TIP305B	0.34					EF89	0.43			800	0.30		
AF124	0.25	BCY32	1.50	BF259	0.18	BY208	0.11	TAG4444	0.76	TIP305C	0.34					EF89	0.43			800	0.30		
AF125	0.25	BCY33	1.50	BF259	0.18	BY207	0.11	TAAS50	0.16	TIP305	0.34					EF89	0.43			800	0.30		
AF127	0.25	BCY34	1.50	BF257	0.20	BY223	0.72	TAA550	0.16	TIP305	0.34					EF89	0.43			800	0.30		
AF136	0.22	BCY42	0.20	BF238	0.20	BYX10	0.15	TBA120S	0.45	TIP305	0.34					EF89	0.43			800	0.30		
AF239	0.22	BCY56	0.16	BF282	0.30	CA270	0.40	TBA395	0.80	TIP305	0.34					EF89	0.43			800	0.30		
AL112	0.70	BCY70	0.16	BF422	0.21	CA3086	0.25	TBA396	0.80	TIP305	0.34					EF89	0.43			800	0.30		
AL113	0.80	BCY71	0.16	BF458	0.19	CA3088	0.25	TBA397	0.80	TIP305	0.34					EF89	0.43			800	0.30		
AS215	1.00	BCY72	0.16	BF458	0.19	CA3089	0.25	TBA398	0.80	TIP305	0.34					EF89	0.43			800	0.30		
AS217	1.00	BD115	0.26	BFX29	0.20	CA3240	0.90	TBA399	0.80	TIP305	0.34					EF89	0.43			800	0.30		
AU110	1.10	BD124P	0.50	BFX84	0.20	C1080	0.23	TBA400	0.75	TIP305	0.34					EF89	0.43			800	0.30		
AY102	1.80	BD124	1.10	BFX85	0.20	MC1327	0.70	TBA401	0.75	TIP305	0.34					EF89	0.43			800	0.30		
AY106	1.80	BD128	0.26	BFX87	0.15	MJ2500	1.00	TBA402	0.75	TIP305	0.34					EF89	0.43			800	0.30		
BA145	0.10	BD132	0.25	BFY50	0.14	MJ2501	1.10	TBA403	0.75	TIP305	0.34					EF89	0.43			800	0.30		
BA148	0.10	BD135	0.25	BFY51	0.14	MJ2955	0.85	TBA404	0.75	TIP305	0.34					EF89	0.43			800	0.30		
BA154	0.08	BD136	0.20	BFY52	0.14	MJ3000	1.15	TBA405	0.75	TIP305	0.34					EF89	0.43			800	0.30		
BA157	0.12	BD137	0.20	BFY53	0.14	MJ3001	1.15	TBA406	0.75	TIP305	0.34					EF89	0.43			800	0.30		
BB101	0.13	BD138	0.20	BFY54	0.25	MJE29A	0.30	TBA407	0.75	TIP305	0.34					EF89	0.43			800	0.30		
BB103	0.16	BD139	0.20	BFY57	0.25	MJE30A	0.30	TBA408	0.75	TIP305	0.34					EF89	0.43			800	0.30		
BB106B	0.10	BD140	0.20	BR10	0.14	MJE340	0.25	TBA409	0.75	TIP305	0.34					EF89	0.43			800	0.30		
BB205B	0.24	BD144	0.50	BSX19	0.15	MJE350	0.30	TBA410	0.75	TIP305	0.34					EF89	0.43			800	0.30		
BC107	0.07	BD150	0.30	BSX20	0.15	MJE520	0.30	TBA411	0.75	TIP305	0.34					EF89	0.43			800	0.30		
BC108	0.07	BD157	0.30	BSX21	0.16	MJE2956K	0.80	TBA412	0.75	TIP305	0.34					EF89	0.43			800	0.30		
BC109	0.07	BD158	0.30	BSX28	0.16	QA47	0.08	TBA413	0.75	TIP305	0.34					EF89	0.43			800	0.30		
BC115	0.10	BD166	0.30	BSX29	0.16	QA50	0.08	TBA414	0.75	TIP305	0.34					EF89	0.43			800	0.30		
BC118	0.11	BD175	0.30	BZK78	0.18	QA91	0.84	TBA415	0.75	TIP305	0.34					EF89	0.43			800	0.30		
BC140	0.19	BD177	0.30	BT106	0.90	QA200	0.87	TBA416	0.75	TIP305	0.34					EF89	0.43			800	0.30		
BC141	0.19	BD179	0.32	BT109	0.90	QA202	0.87	TBA417	0.75	TIP305	0.34					EF89	0.43			800	0.30		
BC142	0.19	BD181	0.46	BT116	0.80	OC28	1.00	TBA418	0.75	TIP305	0.34					EF89	0.43			800	0.30		
BC143	0.19	BD201	0.33	BT119	1.00	OC29	1.00	TBA419	0.75	TIP305	0.34					EF89	0.43			800	0.30		
BC147	0.08	BD202	0.30	BSX29	0.16	OC35	1.00	TBA420	0.75	TIP305	0.34					EF89	0.43			800	0.30		
BC148	0.08	BD203	0.42	BU104	1.00	OC36	0.50	TBA421	0.75	TIP305	0.34					EF89	0.43			800	0.30		
BC149	0.08	BD204	0.42	BU105	0.80	OC71	0.30	TBA422	0.75	TIP305	0.34					EF89	0.43			800	0.30		
BC157	0.08	BD222	0.21	BU108	1.00	OC72	0.50	TBA423	0.75	TIP305	0.34					EF89	0.43			800	0.30		
BC159	0.08	BD225	0.21	BU110	1.10	OC200	1.00	TBA424	0.75	TIP305	0.34					EF89	0.43			800	0.30		

IN.914	0.02	2SB337	1.20	VALVES	PCL85	0.55	LM390	0.25	BRIDGE		
IN.4001	0.04	2SB405	0.22	DY87	0.53	PCL86	0.55	NE565	0.15	RECTIFIERS	
IN.4002	0.04	2SC480	0.21	DY802	0.45	PCL805	0.55	NE566	0.40	1A/50V	0.18
IN.4003	0.04	2SC495	0.00	ECC82	0.40	PFL200	0.85	BYX55/	0.80	1A/100V	0.18
IN.4004	0.04	2SC573	0.40	ECC83	0.43	PL36	0.80	350	0.30	1A/200V	0.19
IN.4005	0.04	2SC1181	1.00	ECC84	0.40	PL504	0.95	BYX55/	0.80	1A/400V	0.21
IN.4147	0.82	2SC1172Y	1.50	ECC85	0.40	PL508	1.90	600	0.30	1A/600V	0.23
IN.5400	0.09	2SC1279	0.24	ECH81	0.49	PY81	0.70	BYX55/	0.80	1A/800V	0.20
IN.5401	0.10	2SC1306	1.00	ECH84	0.52	PY88	0.40	600	0.30	2A/100V	0.35
IN.5402	0.10	2SC1307	1.00	ECL80	0.57	PY500A	1.00	BYX55/	0.80	2A/200V	0.36
IN.5403	0.11	2SC1520	0.25	ECL82	0.59			800	0.32	2A/400V	0.42
IN.5404	0.11	2SC1989	1.30	ECL84							

UNDER NEW MANAGEMENT

TRITELL EDMONTON LONDON

SPECIAL RE-OPENING OFFERS

EVERYTHING REDUCED TO LOW, LOW PRICES

Now in stock Philips G11 and ITT Solid State, Decca 80 and 100 series, Pye Solid State.

Trading as:

CENTRAL TV, 01-807 4090

HUSSAIN CENTRAL TV

No. 1 distributor in U.K.

Special sale for this month only

G8 520 26" £6. 520 22" £9. G8 550 26" £10. 550 22" £20. G9 £18. Thorn 26" £5. Thorn 22" £12. Thorn 8500 £20. GEC Hybrid £4. GEC Solid State £20. Pye Hybrid £4. Pye Solid State £20. Chelsea £20. ITT Hybrid £15. Decca Hybrid £15. Also latest stock G11, ITT, Decca 80 and 100 series.

VHS Videos plus Cameras available

Guaranteed all T.V.'s are untouched off the floor. Buy now while stocks last.

**Ring us today 021-622 1023 or 021-622 1517
48/52 Pershore St., Birmingham City Centre.**

TEL-X BLACKBURN

TELEVISION DISPOSALS

TEL-X BLACKBURN have now moved into larger premises and now offer you a more wider selection of TV's.

Here are a few examples:

	Off the pile from	Workers from
DECCA	£15.00	£25.00
GEC S/S, all types inc. remotes	£20.00	£30.00
THORN 8000	£20.00	£30.00
PYE 18"	£20.00	£30.00

Other makes are available. - Min. 4 sets.

WORKING SETS ON DISPLAY

TEL-X BLACKBURN

Unit P3,
Roe Lee Industrial Estate,
Whalley New Road,
Blackburn, Lancs.
Tel. 0254 679984

IRISH TV NOTICE (SUMMER SALE)

We can supply in good working order Bush, Pye and Ferguson from £60, Philips G.8. From £80, Decca from £90, B/White £25, Re-Gunned C.R.T.s from £40 (We have our own Re-Gunning plant). 500 sets to choose from. Fresh stocks weekly. Phone now for full price list to Ireland's largest distributor of used TVs to the trade.

*ALL PRICES INCLUDE V.A.T.
We can deliver to any part of Ireland.*

TELE SPARES LTD.

Unit 113, Elm Road,
Western Industrial Estate,
Dublin 12, Ireland.
Telephone: Dublin 521211/521756.

TUNERS + TUNERS

- ★ If you repair sets regularly – phone us today and we will dispatch immediately – no need to send cash 'up front'.
- ★ All tuners dispatched by first class post for receipt by you the next day.
- ★ All popular tuners/tuner repairs supplied 'off the shelf'.
- ★ Unusual types repaired same day as received (subject to spares availability).

TELEPART

13 Worcester Street,
Wolverhampton, WV2 4CJ.
Phone: (0902) 773122.

VIDEO CASSETTE RECORDER SERVICING COURSE

3 WEEKS FULL-TIME
(Sept. 17th to Oct. 5th)

Intensive course intended for qualified television service engineers.

The course combines the advantages of industrial & academic training & includes a high percentage of practical work.

Full details:

LONDON ELECTRONICS COLLEGE,
(Dept V6)
20 Penywern Road,
London SW5 9SU.
Tel: 01-373 8721

HOCKLEY DISCOUNT TELEVISIONS

MIDLANDS NEWEST WHOLESALERS

FRESH STOCK WEEKLY

Bush from£6.00
G8 520 from£5.00
G8 550 from£10.00
G.E.C. Solid State£20.00
Pye Solid State£18.00
Pye Chelsea£20.00
I.T.T. Hybrid£18.00
Decca Hybrid£12.00

Also latest stock G11, B.R.C. 9000, Decca 80 & 100 Series
I.T.T. CVC30, 45 etc.

WORKING SETS FROM £18.00
100's OF WORKING SETS AVAILABLE
RING US NOW

021-551-2233

**94 Soho Hill,
Hockley,
Birmingham B19 1AE.**

Opening hours 9 - 7 Monday - Saturday
Sundays by appointment.

BI-PAK

VALUE PACKS

Pak No.	Qty	Description	Price
VP1	300	Assorted Resistors Mixed Types	£1.00
VP2	300	Carbon Resistors 1/4 Watt Pre-Frmed	£1.00
VP3	200	1/4 Watt Min Carbon Resistors Mixed	£1.00
VP4	150	1/4 Watt Resistors 100 ohm - 1M Mixed	£1.00
VP5	200	Assorted Capacitors All Types	£1.00
VP6	200	Ceramic Caps Miniature - Mixed	£1.00
VP7	100	Mixed Ceramics Disc. 10pf - 56pf	£1.00
VP8	100	Mixed Ceramic Disc. 60pf - 0.15p	£1.00
VP9	100	Assorted Polyester/Polystyrene Caps	£1.00
VP10	60	C280 Type Caps Metal Foil Mixed	£1.00
VP11	100	Electrolytics - All Sorts	£1.00
VP12	60	Bead Type Polystyrene Min Caps	£1.00
VP13	50	Silver Mica Caps Ass. 56pf - 500pf	£1.00
VP14	50	Silver Mica Caps Ass. 180pf - 4700pf	£1.00
VP15	50	High Voltage Disc. Ceramic 750v - 8Kv Mixed	£1.00

BI-PAK'S OPTO SPECIAL

A selection of large and small sized LED's in various shapes, sizes & colours, together with 7 Segment Displays both anode & cathode plus photo transistors, emitters and detectors, Cadmium Cell ORP12 and Germ. photo transistor OCP71 included. In all a total of 25 Opto pieces valued over £12 Normal Price.

Order No. VP57
Our Super Value
Price Just
£5.00



VALUE PACKS

Pak No.	Qty	Description	Price
VP28	10	Rectangular 2" Green LED'S	£1.00
VP29	30	Ass. Zener Diodes 250mW - 2W Mixed Vts. Coded	£1.00
VP30	10	Ass. 10W Zener Diodes Mixed Vts. Coded	£1.00
VP31	10	5 Amp SCR's TO-66 50-400v Coded	£1.00
VP32	20	3 Amp SCR's TO-66 Up To 400v Uncoded	£1.00
VP33	200	Sil. Diodes Switching Like IN4148 DO-35	£1.00
VP34	200	Sil. Diodes Gen. Purpose Like OA200/BA13/16	£1.00
VP35	50	1 Amp IN4000 Series Sil. Diodes Uncoded All Good	£1.00
VP36	8	Bridge Rects. 4 x 1 Amp 4 x 2 Amp Mixed Vts. Coded	£1.00
VP37	8	Black Instrument Type Knobs With Pointer 1/2 Std	£1.00
VP42	10	Black Heatsinks To Fit TO-3, TO-220 Ready Drilled	£1.00
VP43	4	Power-Fin Heatsinks 2 x TO-3 2 x TO-66 Size	£1.00
VP44	1	Large Power Heatsink 90 x 60 x 35 mm Drilled For Up To 4 TO-3 Devices	£1.00
VP45	50	BC107/B Type NPN Transistors Good Gen. Purpose Uncoded	£1.00
VP46	50	BC177/B Type PNP Transistors Good Gen. Purpose Uncoded	£1.00
VP47	10	Silicon Power Trans. Similar 2N3055 Uncoded	£1.50

SILICON BRIDGE RECTIFIERS

Comprising 4 x 1/2 Amp rectifiers mounted on PCB.
VRM - 150 vits
IFM - 1.5 Amps

Size: 1 inch square
10 off £1.00
50 off £4.50
100 off £7.50

ORDER NO: 4R1 B Rect.

VP38 100 Silicon NPN Transistors - All Perfect. Coded Mixed Types With Data And Eqvt. Sheet No Rejects. Fantastic Value **£3.00**
VP39 100 Silicon PNP Transistors - All Perfect. Coded Mixed Types With Data And Eqvt. Sheet No Rejects. Real Value**£3.00**

IC BARGAINS

VP40	30	Assorted 74 Series TTL I.C.'s Gates, Flip-Flops & M.S.I.'s + Data Book. All New, Normal Retail Value Over £5.00. Our Price	£2.50
VP41	30	Assorted CMOS I.C.'s CD4000 Series. Pack Includes 00/09/12/14/18/21/25/25/28/30/35/44/68 AY/AE Types Plus Data Sheet Value Over £8.00. Normal retail	£2.50

RATCHET SCREWDRIVER KIT

Comprises 2 standard screwdriver blades 5 & 7mm size. 2 cross point size 4 & 6. 1 Ratchet handle. 5-in-1 Kit £1.45 each. O/No 329B

HYBRID LED COLOUR DISPLAYS



Red, Green, Yellow - 3/5/6 inch Mixed types and colours
NUMERIC & OVERFLOW
Common Anode/ Cathode. GaAsP/ GaP.

Brand New, Full Data incl.
10 pieces (our mix)£4.00
Normal Retail Value Over £10.00
Order No. VP58

VALUE PACKS

Pak No.	Qty	Description	Price
VP16	50	Wirewound Res. 9W (avg) Ass. 1 ohm - 12K	£1.00
VP17	50	Metres PVC Covered Single Strand Wire Mixed Colours	£1.00
VP18	30	Metres PVC Covered Multi Strand Wire Mixed Colours	£1.00
VP19	40	Metres PVC Single/Multi Strand Hook-Up Wire Mixed	£1.00
VP20	6	Rocker Switches 5 Amp 240v	£1.00
VP21	20	Pcs. 1 - 2 & 4 mm Plugs & Sockets Matching Sizes	£1.00
VP22	200	Sq. Inches Total, Copper Clad Board Mixed Sizes	£1.00

VALUE PACKS

Pak No.	Qty	Description	Price
VP23	20	Assorted Slider Pots. Mixed Values	£1.00
VP24	10	Slider Pots. 40 mm 22K 5 x Log 5 x Lin	£1.00
VP25	10	Slider Pots. 40 mm 47K 5 x Log 5 x Lin	£1.00
VP26	20	Small 125° Red LED'S	£1.00
VP27	20	Large 2° Red LED'S	£1.00

TRANSISTOR CLEARANCE

All Sorts Transistors. A mixed Bag NPN-PNP Silicon & Germ. Mainly Uncoded You To Sort Pack Includes Instructions For Making Simple Transistor Tester. Super Value. Order No VP60 **£1.00**

Send your orders to Dept. T7
BI-PAK PD BOX 6
3, BALDOCK ST
WARE HERTS



Use your credit card. Ring us on Ware 3182 NOW and get your order even faster. Goods normally sent 2nd Class Mail. Remember you must add VAT at 15% to your total order. Postage add 75p per total order.

MANTEL

Manchester's No. 1 in Ex-Rental TVs
Over 2,000 TVs in stock
Special Offer on Working Colour TV's

All sets are Serviced with repolished cabinets ready for sale

Philips G8 550s	22/26	£45
Philips 18"		£40
Philips G8 520s	22/26	£35
GEC S/State	from	£35
Thorn 17" 8000		£30
Decca 30	18/20/22/26	£30
Japanese	from	£30
Many other makes available from £25		

Discount on quantity

Ex Equipment Panels & Tubes Available

Deliveries may be arranged to the North and Scotland.

Ring for quote. Callers welcome.

Some Examples of UNTESTED TVs available

Thorn	10 for	£125
Philips	6 for	£90
Bush	6 for	£80
GEC	6 for	£60
Decca	6 for	£60
Mono TVs avail. s/s		£4 each
New TV trolley stands.		
All sizes		£4.95
All Prices subject to V.A.T.		

419 Barlowmoor Road, Chorlton, Manchester 21 2ER.
Tel: 061 861 8501

TELEVISION TUBE SHOP LTD

NEW MONO TUBES

A31-120W/300W	17.00
A31-510W	17.00
A34-100W	18.50
A38-160W	18.00
A44-120W	25.00
A50-120W	19.00
A61-120W	21.00
230DB4	25.00
240DB4	22.00
310EUB4	19.95
310FXB4	17.50
310GNB4A	26.50
340CB4/RB4	26.00
RIGONDA 6"	14.00

OTHER TYPES STOCKED - RING FOR QUOTE
MULLARD COLOUR TUBES STOCKED P.O.A.
 Please allow 7 days for delivery.

ALL TUBES TESTED BEFORE SALES AND FULLY GUARANTEED.

TELEVISION TUBE SHOP LTD

52 BATTERSEA BRIDGE ROAD,
 LONDON, SW11.

Tel: 228 6859/223 5088

CARRIAGE: Mono £3, Colour £10.

SATELLITE RECEIVING EQUIPMENT

1.9M, 2.5M and 5M Harrison Dishes
 Sat-Tec R5000 4GHz Receivers
 Avcom COM-2B 4GHz Receivers
 California Amplifier 4GHz LNAs
 Chaparral Feed Horns

Demonstrations by appointment only

Dealers wanted

HARRISON ELECTRONICS

22 Milton Road,

Westcliff-on-Sea, Essex SS0 7JX.

Telephone: Southend (0702) 332338

"NORTH LONDON WHOLESALE'S" TV SALES

Example of working set prices:

GEC Hybrid £15, Decca 30 £24, 22" Philips 520 £25,
 22" Philips 550 £35, Thorn 3000 £25,
 19" Thorn 8500 £30, Twin Chip Bush £24.
 Thorn 8800 £39. Mono from £4 etc.

Prices for other models or non-workers on request.

Re-gunned tubes available. 5 mins. M.1.

Please telephone us for details on:-

WATFORD 45590

CENTREVISION MANUFACTURERS SECONDS

Beta Video top make boxed
from **£149 + VAT**

VHS Sharp Video from **£175 + VAT**
Ex-rental TV. ITT remote CD752 Stand
+ Meter **£120 + VAT**. A1 working.

Thorn 8800 Remote **£45 + VAT**
GEC Solid State from **£25 + VAT**

Hybrids at give-away prices.

Also:

Tubes, Parts, Stands etc,
plus working sets.

Sloper Road, Cardiff.
Telephone: 0222 44754

Opposite Cardiff City Football Ground

TELETRADERS

Forde Road, Brunel Industrial Estate,
Newton Abbot, Devon
Telephone: (0626) 60154

**The Best Quality Sets Available
Anywhere**

All First Class working order and excellent
cabinets.

Philips G8 550	£40
Philips G11	£85
GEC Solid State	£35
Thorn 3500 Electronic 22"	£35
Thorn 9000	£60
Thorn 8800	£45
Thorn 9800	£55

**Full spares back-up of tubes and panels -
send for list e.g. PL509 £1, PY500 £1**
Bulk terms to other wholesalers

☆☆☆

THE NO. 1 WHOLESALE IN THE SOUTH

ALL SETS HAVE BEEN ENGINEERED AND ARE IN PERFECT WORKING ORDER

*PRICES AVAILABLE ON THESE
SETS NOW!!!*

PYE CHELSEA's
PYE 721s, 731s, 725s
PHILIPS 520s, 550s
BUSH T20, T22, T24s
(Remote Control)

THORN 8000 & 8800s
THORN 9000, 9200,
9600
(Remote Control)

Special Offer

SALORA 22"

£35 inclusive
Massive reductions for bulk
Minimum 5 Sets

Big reductions for export orders over
100 sets

COLOUR TELEVISION & MUSIC CENTRE

35 Stafford Road,
Weston Super Mare
Avon.

Opening hours: 9-6 Mon-Sat, Sundays by
appointment

(Weston Super Mare 413537)

(Note new address)

(15 minutes past Bristol Southward
on M5)

VIDEO HEADS

MONOLITH
electronic products

RECORDER Head Price
Model No. £ + VAT

AKAI
VS9300 29.95
VS9500 29.95
VS9700 29.95
VS9800 29.95

BUSH
BU6900A 38.95

FERGUSON
3V00 29.95
3V16 29.95
3V22 29.95
3V24 29.95
3V30 29.95

GRUNDIG
SUR4004 72.45
2000GB 63.00

RECORDER Head Price
Model No. £ + VAT

HITACHI
VT3000E 38.69
VT5000ER 38.69
VT8500E 38.69

JVC
HR3300 29.95
HR3660EK 29.95
HR7200EK 29.95

PANASONIC
NV2000 29.95
NV2010 29.95
NV366B 38.13
NV777B 63.64

RECORDER Head Price
Model No. £ + VAT

PHILIPS
1500 54.07
1502 54.07
N1700 59.50
N1702 59.50
N2000 59.50

SANYO
5000 47.24
5300 47.24
5600 47.24

RECORDER Head Price
Model No. £ + VAT


9300 47.24

SONY
C5 38.95
C6 38.95
C7 38.95
8000UB 38.95
8000E 38.95
8080 38.95
8080E 38.95


TOSHIBA
V5250B 38.95
V5470B 38.95

DRIVE BELT KITS

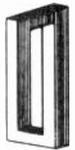Kit Price
Model No. £ + VAT
8000 4.50
8080 4.25
C7 & J7 4.25
HR3330 4.50
HR3360 4.50
HR3600 4.50
HR3660 4.50
NV300 4.25
NV7000 4.00
V7540 4.50



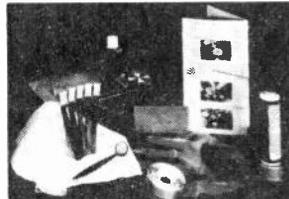UNIVERSAL VIDEO HEAD REPLACEMENT KIT £8.25



KIT CONTAINS: Eccentricity gauge, handling gloves, cleaning fluid, 5 cleaning tools, air blast, inspection mirror, antistatic cloth, screwdriver, replacement instructions, motor speed disc, service label.

£5 OFF

ON ORDERS OVER £100

PLEASE ADD VAT + £1.50 P&P PER ORDER

MOST DELIVERIES EX-STOCK BUT PLEASE ALLOW UP TO 28 DAYS.

Ask for our **FREE AUDIO HEAD REPLACEMENT GUIDE** and full catalogue



● Audio + Video Heads ● Motors ● Parts

THE MONOLITH ELECTRONICS CO. LTD

5-7 Church Street, Crewkerne, Somerset TA18 7HR, England
Telephone Crewkerne (0460) 74321
Telex 46306 MONLTH G

SUPPLIER TO MOST OF THE U.K.'s LEADING DISTRIBUTORS AND SERVICE ORGANISATIONS

VISIONTEL

FIRST CHOICE FOR BEST QUALITY EX-RENTAL TVs
EXCELLENT WORKING SETS FROM ONLY

£25

(EXCLUDING VAT)

CLEANED · POLISHED READY FOR THE SHOWROOM

OR

SILLY PRICES FOR SETS 'OFF THE PILE'

LOW PRICES · FRIENDLY SERVICE FOR CURRENT STOCK DETAILS
TELEPHONE US ON 01-328 3787
OR COME ALONG TO
55 KILBURN HIGH ROAD, NW6

20AX APOLLO 30AX

PHONE FOR TRADE PRICES ON PIL TUBES

Fast Mail Order service to any part G.B. Delivery 2-3 days. Just phone for a quotation. Delivery Manchester area free same day. Two year guarantee. Fitting while you wait or in your home £20.

18"	A47 - 342 x 343	470 BEB22 (£45.00)	£37.00
19"	A49 - 120 x 192 x		£37.00
20"	A51 - 220 x 110 x 161 - 510	JKB22 (£45.00)	£38.00
22"	A56 - 120 x 123 x 140 x 410		£38.00
25"	A63 - 120 x		£39.00
26 x	A66 - 120 x A67 - 120 x 140 x 150/200		£39.00
20AX	56-510		£48.00
30AX	56/66-540		£48.50
20" - 22" SOLID STATE COLOUR TVs FULLY SERVICED & SOAK TESTED. VERY RELIABLE WITH GOOD TUBE £61.00, WITH NEW TUBE £83.00 inc DELIVERY			

061 799 0854 24 hour answering service.

43 Clarke Cres, Little Hulton, Nr. Manchester M28 6XM.

MAIL ORDER ADVERTISING

British Code of Advertising Practice

Advertisements in this publication are required to conform to the British Code of Advertising Practice. In respect of mail order advertisements where money is paid in advance, the code requires advertisers to fulfil orders within 28 days, unless a longer delivery period is stated. Where goods are returned undamaged within seven days, the purchaser's money must be refunded. Please retain proof of postage/despatch as this may be needed.

Mail Order Protection Scheme

If you order goods from Mail Order advertisements in this magazine and pay by post in advance of delivery, Television will consider you for compensation if the Advertiser should become insolvent or bankrupt provided:

- (1) You have not received the goods or had your money returned; and
- (2) You write to the Publisher of Television summarising the situation not earlier than 28 days from the day you sent your order and not later than two months from that day.

Please do not wait until the last moment to inform us. When you write, we will tell you how to make your claim and what evidence of payment is required.

We guarantee to meet claims from readers made in accordance with the above procedure as soon as possible after the Advertiser has been declared bankrupt or insolvent.

This guarantee covers only advance payment sent in direct response to an advertisement in this magazine not for example, payment made in response to catalogues etc. received as a result of answering such advertisements. Classified advertisements are excluded.

The World of . . .

"TELEPANELS"

52 Mount Pleasant Road, Chigwell, Essex. Telephone 01-729 0506.

COMPARE OUR PRICES!

COMPARE OUR SERVICE!



	IF	TUNER	DECODER	G8/G9 DECODER IF COMBINED	LINE OUTPUT	POWER	CONVERG	FRAME	VIDEO	6 WAY TUNER SWITCH BANK
PHILIPS G.8	5.00		7.00	15.00	14.00	8.00	5.00	5.00		3.50
THORN 3000/3500	2.00	5.75	4.00		8.00	8.00	5.00	6.00	5.00	1.75
GEC 2110	10.00		5.00		12.00	6.00	5.00	5.00	5.00	5.00
PYE 731	8.00		10.00		18.00	10.00	7.00	8.00		

TRIPLERS FOR ALL MODES £3.00 SPEAKERS £1.50

P+P 1 PANEL £1.50 2 PANELS OR MORE £3.00

CASH
WITH
ORDER - PLEASE

POST OFF YOUR CHEQUE NOW! & YOUR PANELS SENT BY RETURN OF POST!!!

A.B.C. TRADE SALES

COLOUR T.V.'s

Philips G8, Pye, Decca 30's,
Thorn's 3000's, 3500's, 8000's

Prices start from £12 - Working sets from £20

Hundreds of Mono T.V.'s from £2.00

Jap. sets from £30.00

Special prices for quantity

9,000 sq. feet Warehouse

83 SHOWELL ROAD, BUSHBURY,
WOLVERHAMPTON, STAFFS.

Tel. Wolverhampton 722637

COLOUR TELEVISIONS

PYE CHELSEA - 6 button

PYE 723

PHILIPS G8 550 THORN 8000, 8800

THORN 9000, 9200, 9600 Remote Control

Working panels and tubes available.

REBUILT TUBES

Delta - In Line - PIL.

SOUTHBRIDGE TV CENTRE

120, Selhurst Rd., London, S.E.25.

Tel: 01-771 3535.

COMPLETE VIDEO System
HOME AND PORTABLE

ONLY £699

TRADE TERMS AVAILABLE

This superb NEC System is now available from Fineplan Video at an unbelievable low price. Over 3 hours recording is possible on an L750 Beta Video Tape. You may never again see a full size complete system offered at this price.

NEC TC 1060E COLOUR VIDEO CAMERA
6X2-speed power zoom lens. Macro. TV view-finder. Auto iris with manual override. Colour temp. and white balance controls. Boom microphone. Fingertip control of recorder functions.

NEC PVC 1040E PORTABLE VIDEO RECORDER
Forward/reverse picture scan. Audio dub. Still frame. Frame advance. Back space edit. 8-mode remote control. Video/audio and RF input/output. Weight 4.8Kg

NEC TT 1040 TUNER TIMER 12 channel tuner. 5 event 14-day timer. Power failure backup. Built-in mains adaptor/battery charger. Battery is included in system.

Delivery UK Mainland £8. Other area delivery charges quoted on request.

NEC

EXPORT MODELS ALSO AVAILABLE

Accessories: Separate AC adaptor/charger. Car leads. Conversion lens. Filters. Tripods. Lights. Copy kits. Extension cables. Microphones. L750 Beta tapes £4.95.

The Videocentre

Fineplan Video Services

5 Masons Avenue, Harrow, Middx. Tel: 01-863 0666 (Opposite Harrow & Wealdstone Stn)
10am-6.30pm including Saturday and Wednesday 10am-2pm.
PROPRIETOR FINEPLAN SECURITIES LIMITED

LONDON'S LARGEST TELEVISION
WHOLESALER . . .

with over 4½ thousand sq. feet.

"TELEMANN"

8-10 RHODA STREET,
(Off Bethnal Green Road)
LONDON E.2. FREE CAR PARK
TEL: 01-739 2707

ALL MAKES IN STOCK AND GUARANTEED
COMPLETE

The only wholesaler with a
guaranteed single price. If the sets
work or not our price is the same!
Free delivery to the London area.

Telephone 01-739 2707 -
NOW!

Philips VCR 1700 with new boxed
1½ hour cassette and mains lead
£45. Single standard mono's £3.

PHILIPS 22" (Model 520) Parcel of ten £15
PHILIPS 22" (Piano Key 550) Parcel of ten £20
JAPANESE MODELS 18"-20" £30

FREE DELIVERY TO THE LONDON AREA!

EMCO - EUROSONIC - GRUNDIG - TELETON + ALL BRITISH MAKES
ETC. ETC. ● ALL SPARES READILY AVAILABLE ●

IMMEDIATE CREDIT AVAILABLE - TRADE ONLY

If you are a trader simply phone for the part you require and we will send it - no quibble - no hold up for status check. Satisfy us over the phone that you are a trader and we will supply almost any TV component by return "off the shelf". e.g. LOPTX - EHT trays - droppers - OSC coils - switches - cans - smoothers - I.C.'s, etc. etc.

**YOU CAN BE 95% SURE WE CAN SUPPLY ANY
TV COMPONENT BY RETURN
IF YOU NEED SPARES FAST - RING NOW!**

ACCESS AND BARCLAYCARD ACCEPTED.

Applies to U.K. only.

TELEPART (W'TON)

THE TELECENTRE, WORCESTER ST.,
WOLVERHAMPTON (0902) 773122

SETS & COMPONENTS

PANELS

**GOOD WORKING
POST PAID NO VAT**

Make	Power Supply	Line Panel	T.Base Panel	Decoder D	IF Tripler	Convergence	
Thorn 3500	£12.00	£9.50	£6.50	£5.00	£3.00	£4.00	£5.00
Thorn 8500	£6.00	-	£9.50	£11.00	-	£4.00	£5.00
Philips G8	£12.00	£11.00	£6.50	£11.00	£9.00	£4.00	£5.00
GEC S/S	£6.50	£11.00	£6.50	£8.50	£11.00	£4.00	£5.00
Bush	£6.50	£6.50	£6.50	£11.00	£6.50	£4.00	£5.00
Decca							
Bradford	£6.50	£6.50	£6.50	£8.50	£6.50	£4.00	£5.00

+ ITT spares. BUSH or PHILIPS state model.

TUBES

£29.00

INCLUSIVE, REGUNS TWO YEAR
GUARANTEE, QUANTITY
DISCOUNTS

£14.50

SIX MONTH GUARANTEE
SLIGHTLY USED

A56-120 A51-110 A49-191 A47-342 or 343 A44-270-1
A66-120 A67-120 (All 26" add £5)

IN-LINE 51-161 From £35 plus 100's more
Delivery £5 per tube. British Isles.
No need to spend £5 returning old tube
if you buy from us.

U-VIEW TUBES,

29 Warmsworth Road,
Doncaster, Yorkshire DN4 0RP.
Tel: 0302-855017.

Callers ring first: Open every day including Sunday

TELEVISION

No other consumer magazine in the country can reach so effectively those readers who are wholly engaged in the television and affiliated electronic industries. They have a need to know of your products and services.

The prepaid rate for semi display setting £6.00 per single column centimetre (minimum 2.5 cms). Classified advertisements 35p per word

**THORN
COLOUR TVs**

Most models. Excellent condition. Working or untested.

- ★ Philips 550/660
- ★ Decca 1051/1052
- ★ Pilot (JVC) etc.

Phone or call for competitive prices.
Regular supply.

REPOSSESSED TV CENTRES LTD.,
335-341 Stockport Rd., Longsight, Manchester.
Tel. 061-273 2854.

CANVEY COLOUR TUBES

Unit 3, Charfleets House, Charfleets Industrial Estate, Canvey Island, Essex.
Tel: Canvey Island (0268) 690577

CURRENT PRICE LIST

DELTA TUBE TYPE FROM £27.50 to £31.50
INLINE TUBE TYPE FROM £35.00
MONO TYPES P.O.A.

ALL PRICES EXCLUSIVE OF VAT.

All Tubes Guaranteed for 2 YEARS and Reprocessed
to Original Manufacturers Specifications.

WOODSDALE COMPONENTS

**RANK BUSH MURPHY
TRANSFORMERS**

Line Output	
Z718 (T703A, T706A)	
New (Complete)	£20.50
Less Focus Module and Rectifier	£10.50
T20, T22 (T705A)	£9.00
T26 (T705B)	£9.50
Switch Mode	
T114A/B	£8.00

Genuine RBM Units.

AERIALS

UHF Aerials P & C Wideband 4 Bay
Bowtie (12.5 dB) £20.00
Above with built-in Broadband amp.
(27dB) plus stabilised power
supply £45.00

Prompt Postal Service.
Add 15% VAT to all prices.
DISCOUNT for QUANTITIES.

34 Field End Road, Eastcote,
Pinner, Middlesex. HA5-2QT.
Tel: 01-868 5580.

N. Skehan

Agents Office. Callers by appointment only.

TELEVISION

Trade & Retail supplies of
s/h colour & mono TVs.
Most makes available,
workers or non-workers

SOUTHPARK DISTRIBUTORS

Unit 4 Rubastic Road,
Brentpark Industrial Estate,
Southall, Middx. UB2 5LL.
01-574 4631, Ext 28

COLOUR T.V.s

THE BEST IN LONDON
200 + TVs WEEKLY

LOADS SMALL SCREEN
WORKING SETS TO
ORDER — ALL MAKES

WINDSOR WHOLESALE
TEL: 01-968 8771.

THE TV WAREHOUSE

Your local trade & retail suppliers of
CTV's special clearance of older
models.

THE TV WAREHOUSE,
Watling Street (A5),
Hockliffe, Beds.

Tel: Leighton Buzzard 210686.

SUFFOLK TV TUBES

1 Park Road, Hackbridge, Nr. Wallington, Surrey SM6 7ER
Tel. 01-669 7825/7826

Are pleased to announce they are now rebuilding customers Japanese and British In Lines including P.I.L. with the fitting of coils as necessary.

E.g. A51-570X A51-161X A56-610X
A56-500X A66-500X A51-500X
A37-552X A37-557X AXT37-001

560 DYB 22 TC03 560 EGB 22 TCO1
A56-540X etc. now available.

Many more tubes available ex stock.

Delta's available ex stock, glass not required.

Computer and VDU CRT's rebuilt as required.

BRITAIN'S LARGEST INDEPENDENT MANUFACTURER

REBUILDERS SINCE 1958.

SERVICE PAGES

(minimum 12 words), box number 70p extra. All cheques, postal orders etc., to be made payable to Television, and crossed "Lloyds Bank Ltd". Treasury notes should always be sent registered post. Advertisements, together with remittance, should be sent to the Classified Advertisement Dept., Television Room 2612, IPC Magazines Limited, Kings Reach Tower, Stamford Street, London SE1 9LS. (Telephone 01-261 5846).

COLOUR TV PANELS Fully Tested & Working

	IF	CDA/ Video	Decoder	LTB	Line Board	Power
GEC 2040	3.50	3.50	4.00	5.00	-	-
DECCA 13/30	3.00	-	7.00	5.00	-	4.00
BUSH A823	4.00*	-	10.00*	5.00*	2.50	4.00
THORN 8/8j	-	-	10.00	5.00	-	5.00
PYE 205	3.00	3.50	5.00	10.00	-	-
THORN 3/3j	5.00	5.00	5.00	8.00	-	10.00
G8	6.00	-	8.00	7.00	15.00	5.00

*Please specify prefix A or Z.

Please add 15% VAT to above prices, then add post + packing.
Post + Packing: 1 panel £1.50; 2 panels £2.25; 3 panels £3.00 etc.

Hybrid panels do not include valves.

Terms cash with order.

Also a vast selection of modern working and non-working TVs at low prices. Please ring for current stock.

GOLCAR T.V. SERVICES (formerly LAVITE LTD.)

Old C of E School, Church Street, Golcar, Huddersfield. Tel.: 0484 643273

Callers by appointment only.



- * Britains most reliable source of quality TVs.
- * Hundreds of working polished TVs.
- * New adjustable TV stands.
- * Pye 18" Chelsea's working & polished £35.00 in quantity.

Krystal Marketing Ltd.,
Breedon Cross Storage,
Dale Road, Selly Oak,
Birmingham B29 6AQ.

Phone 021-471 3023
Telex 335540-G
Ask for Les

TRADE COLOUR TV'S ALWAYS 200 IN STOCK

Phillips G8 from £10
Bush Twin Chip from £8
Pye Chelsea from £15

Avo repairs prompt service scopes etc.

Colour TV's in good working order from £35.

E.G. Phillips G8's 22" £35.

Ring us for spares and type availability anytime.

Also Videos, V2020 and V2023's etc.
ALL STOCK CHANGES WEEKLY

(0934) 514047/512792/27560

P&R SUPPLIES, Unit 5,

Worle Industrial Estate,

Weston-Super-Mare. Exit 21 M5.

COLOUR BAR GENERATOR

Pal Colour Generator with 11 patterns plus sound.
Grey scale, Colour Bars, Red, Green & Blue Raster,
Crosshatch, Dots, Chequer Board, Black Raster, White
Raster, Half Black & White £75.90.



BLACK AND WHITE GENERATOR

Crosshatch, Peak White, Dots, Half Black & White and
Grey Scale £18.50
In Circuit Transistor Tester £14.25
Capacitance Meter measures 10pF to 1µF complete with
moving coil meter £14.75

Prices include P&P & VAT.

C.M.J. ELECTRONICS

Unit 8, 16 Union Mill Street, Horseley Fields,
Wolverhampton WV1 3DW.
Tel: (0902) 871563

TURN YOUR SURPLUS capacitors, transistors, etc. into cash. Contact COLES-HARDING & CO, 103 South Brink, Wisbech, Cambs. 0945 584188. Immediate settlement.

TV VALVES

COLOUR VALVES PY500/A-65p, PL509/519-£1.50.
MONO VALVES ECC82, EF85, EF183, EF184, DY87,
DY802, PCF80, PCF802, PCL82, PCL83, PCL84, PCL85/
805, PCL86, PCC84, PCC89, PC92, PC97, PC85, PC88,
PFL200, PL36, PL534, PY800, PY88 ETC.
MONOCHROME VALVES ALL 35p EACH.
ALL VALVES EX-EQUIPMENT & TESTED.
P&P 50p Per order, Access/Visa Cards welcome.
ELECTRONIC MAILORDER, 62 Bridge St.
Ramsbottom, Lancs, BL0 9AG. Tel. (070682) 3036.

GENERAL TELEVISION TRADE SALES FACTORS

3-5 UNION ST.
DONCASTER

Telephone:
(0302) 68416

Regular weekly supplies of good quality TVs, all with excellent cabinets, we look after our sets, we don't knock them about, as you'll see if you call, suitable for re-sale or rent. Working or off the pile. We're always happy to see you, whether its for one TV or one hundred and one.

MONDAY TO SATURDAY 9 to 5.30

GOOD SETS
GOOD SERVICE
CALL & SEE US YOU
WON'T BE DISAPPOINTED
Special Prices on Philips G8's &
Other Lines

STANDS, LEGS,
SLOTMETERS, PANELS,
TUBES ETC.



PHONE
NOW
(0302) 68416

RANK
SABA
KORTING
THORN
EKCO
ETC.

PHILIPS
PYE, JAPANESE
DECCA, GRUNDIG
GEC, ITT

EXCELLENT MOTORWAY ACCESS FROM MOST PARTS
VIA M1 OR A1
WE'RE ONLY A SHORT DRIVE AWAY

TELE-MASTER

We are a good reliable supplier of
QUALITY colour T.Vs.
We can DELIVER
Try use for SIZE (18"-26")
PHILIPS, PYE, DECCA, BUSH

TELE-MASTER

Rotherham (0709) 863614
24hr Answering Service

TELEVISION TUNER REPAIRS ALL TYPES

BRITISH, EUROPEAN
JAPANESE ETC.

MEN-TU ELECTRONICS LTD.
SALTERNS LANE,
FAREHAM, HANTS.

Tel: 0329-235116

SATELLITE TV RECEIVER

Receives 4GHz band. Ideal for demon-
stration terminal in U.K. 100 degree
Kelvin LNA. £392 + VAT (+ Carr).
LNA/down converter PCB's stocked for
the constructor. SAE data.

HUGH COCKS TV SERVICES,

Cripps Corner, Robertsbridge,
Sussex TN32 5RY. Tel. 058083 317.

EX RENTAL C.T.V.'s & REGUN TUBES

RBM, THORN, DECCA, PYE GEC,
GRUNDIG, ITT, PHILIPS G8, G9, G11,
JAPANESE
From £10

Also all modules from £4 untested.

STARLITE ELECTRONICS,
80 Como St., Romford, Essex.
Telephone Romford 752537
London Code 3.

Thorn 3000/3500
Thorn 9000
UNIVERSAL
1 year guarantee

TRIPLERS
£4.50 inc. p&p

The UNIVERSAL TRIPLER can be used in most
G.E.C., I.T.T., Pye, Rank, Decca & Continental
sets.

WING ELECTRONICS

15 Waylands, off Tudor Rd, Hayes End, Middlesex

Trent Tubes

31 RADCLIFFE ROAD,
WEST BRIDGFORD, NOTTINGHAM
THE QUALITY REBUILDER

PHONE 0602 813329

ALL TUBES CARRY A 2 YEAR GUARANTEE

EXTENDABLE TO 4 YEARS

ALL SIZES OF STD DELTA'S £26.50

A51-161, etc. £35.00

A56/66-510 (20AX) £40.00

A56/66-540 (30AX) £49.00

560 OZ B22 £41.00

JAPANESE TYPES OUR SPECIALITY

1000's MORE TYPES AVAILABLE

VDU MONO INDUSTRIAL TYPES PLEASE PHONE

* STOCKISTS *
PETERBOROUGH: TAMWORTH:
H. DONMOR, 0733 71809 Mercia Ltd., 0827 52202
HEMSFORD:
Redivision Ltd., 0543 877153

PL802 Valve New£5.00
PL802 Solid State Plug in replacement Module£4.50
BT106 Thyristor£0.75 BU126 Transistor£0.75
2SC643AY Transistor£0.70 R2008B Transistor£0.80
R2010B Transistor£0.80 SL901B Integrated Circuit£4.00
VAT INC. ADD £0.50 P&P

ACORD ELECTRONICS LTD
UNIT 2-3 ENTERPRISE PARK
SLYFIELD, GUILDFORD GU1 1RB

SECOND HAND Colour TV spares and tubes. Most
makes. Telephone Southport (0704) 74411. Anytime.

**T.V. SPARES, PANELS
AND MANUALS**
PHILIPS · GRUNDIG

TELEVIEW 01-994 5537
194, Acton Lane, London W.4.

RANK BUSH MURPHY TV PANELS

Repair, exchange, sales service, prompt effi-
cient service. All chassis covered. New PCB
available to replace burnt T20 line Panel. We
charge only £16 to repair switch mode power
supply. Ring Monday to Saturday and ask for
Mr. Kheli.

T. K. Panels Service,
31 Bronte Paths, Stevenage, SG2 0PG.
Tel. (0438) 61567.

TELEVISION

LEGAL NOTICE

TRADE MARK 1132859 consisting of SONATA

and registered in respect of "Radio and television
instruments and apparatus; sound recording and
sound reproducing apparatus and instruments; parts
and fittings included in Class 9 for all the aforesaid
goods" was assigned on 13 September 1982

by **Jacobson Van Den Berg & Co (UK)
Limited of Jacoberg House, 231 The Vale,
London W3 7RN**

to **Empire Stores (Bradford) Limited of 18
Canal Road, Bradford BD9 4XB.**

**WITHOUT THE GOODWILL
OF THE BUSINESS IN WHICH THE MARK
WAS THEN IN USE.**

AERIALS

AERIALS AND ACCESSORIES

North Londons Specialist Aerial Supplier
Wholesale and Mail Order.

VHF/UHF antennas, masts, brackets, cable, amplifica-
tion and distribution equipment etc. All types of aerial
hardware and software supplied. Single and multipoint
systems planned and installed.

Send 50p for our new 1983 catalogue and price list.

S.C.S. AERIALS

(Aerial Distributors)

26-28 Port Vale, Hertford, Herts. SG14 3AB.
Tel: 0992 50478.

2 METRE PARABOLIC DISHES

Glassfibre Construction
Suitable for 4 and 12 GHz £290

Polar Mounts and Feed Supports Available.

Send S.A.E. for Details

SP ANTENNA SYSTEMS,
3 Woolpack Corner, Biddenden,
Ashford, Kent TN27 8BU
Tel: 0580 291090

AERIAL SYSTEM COMPONENTS: everything you
need to install multi-outlet systems. Terrific range of
filters, diplexers, amplifiers, outlets, cable etc. Use the
gear the trade uses and save pounds. Free planning/
advice. Catalogue 50p (refundable). **WRIGHTS**
AERIALS, 43 Greavesike Lane, Micklingor,
Rotherham.

AERIAL BOOSTERS

Next to the set fitting

B45H/G-UHF TV, gain about 20db, Tunable over the complete
UHF TV band. **PRICE £8.70.**

AMPLIFIED SET TOP AERIALS for UHF TV, trebles the gain.
PRICE £9.70.

All Boosters we make work of a PP3/006p/6F22 type battery or
8v to 18v D.C. P&P 30p PER ORDER.

ELECTRONIC MAIL ORDER, 62 Bridge Street, Ramsbottom,
Lancs BLD 9AG. Tel. (070682) 3036
Access/Visa Cards Welcome SAE Leaflets

CLEARVIEW AERIALS

Clearview have pleasure in announcing a full and
comprehensive range of signal amplification equip-
ment. For example: low noise electronically remote
controlled masthead pre-amp 1.6db noise. CH. 17-69.
Set side amplifiers, distribution amplifiers, notch filters
4 in 1 or 2 in 1 etc. Combiners for 2 UHF aerials 3db
gain or 4 6db gain. Trade and retail.

Send large SAE for our comprehensive catalogue

CLEARVIEW AERIALS,

173 Kings Road,
Kingston Upon Thames, Surrey.

COURSES

CONQUER THE CHIP... Master modern electronics
the PRACTICAL way by SEEING and DOING in
your own home. Write for your free colour brochure
now to **British National Radio & Electronics School,**
Dept. C4, Reading, Berks RG1 1BR.

WANTED

WANTED. Service manuals R.B.M. T20-6. 01-776
0284.

NOEL EDMONDS

"Late Late Breakfast Show"

Is urgently looking for any bizarre funnies/
bloopers on Film or V.T. (any format). If you
have a gem please contact:

B.B.C. T.V. CENTRE
Wood Lane, W12
Telephone 01-578 1969
(Reverse Charges)

WANTED. We will clear any amount of colour sets
from small Rental Companies, Hotels, etc. Please
phone P & R Domestic Electrical Clearance Supplies,
Weston Super Mare (0934) 514047.

WANTED

T.V.s, VIDEOS,
HI FI, AUDIO

£100,000 TO SPEND

If you have a surplus, we
would be delighted to make
an offer.

Contact:

Mr Fred Tuck
(0934) 413537

OSCILLOSCOPE TUBE type Hitachi 5U PI (F). New
for second hand. **HODGE.** Tel. 0460 40645.

WANTED ALBA T1014 semi-portable B/W TV.
Phone (0632) 562562.


HOME SECURITY

ALARMS

FREE CATALOGUE!

Our Great New Illustrated
Catalogue is Packed with
Information on Superb
Quality, Professional Burglar
Alarm Equipment.

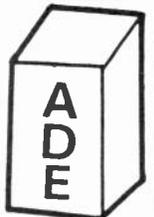IT TELLS YOU ALL YOU
NEED TO KNOW
**TRADE ENQUIRIES
WELCOME.**



NO CHARGE FOR POST & PACKING
SEND S.A.E. OR TELEPHONE NOW
FOR YOUR FREE COPY!
Prop. J. Chadwick

A.D. ELECTRONICS
SECURITY MANUFACTURERS
217 Warbreck Moor,
Aintree, Liverpool L9 0HU
Tel: 051-523 8440

SERVICE PAGES

SERVICE SHEETS

TELEVISION SERVICE SHEET SPECIALISTS

Thousands of British, European, and Japanese models in stock.

Colour **£2.00** Mono **£1.50** (post free)

Manual prices on request.

Send stamped envelope for free catalogue and enquiries

SANDHURST TV SERVICES (MAIL ORDER)

49C Yorktown Road, Sandhurst, Camberley, Surrey GU17 7AG

30,000 SERVICE SHEETS IN STOCK. COLOUR MANUALS ALSO AVAILABLE

TV Monos, Radios, **£3.00**. Tuners **£3.00**. Tape Recorders, Record Players **£3.00**. Transistors **£3.00**. Car Radios **£3.00** + SAE. Stereograms & Music Centres **£3.00**. Radiograms **£3.00**. Also Colour available. State if circuit will do if sheets are not in stock. Circuits **£3** - colour. All TV Sheets are full length 24 x 12 not in Bits and Pieces. All other Data full lengths. All Sheets **£3** except colour. SAE please. Old Valve Radios **£3** + SAE 9 x 3. Ensure payment with order.

C. CARANNA, 71 BEAUFORT PARK, LONDON NW11 6BX.

(MAIL ORDER)

BELL'S TELEVISION SERVICES for service sheets on Radio, TV, etc. **£1.50** plus S.A.E. Service manuals on colour TV and Video Recorders, prices on request. S.A.E. with enquiries to B.T.S., 190 Kings Road, Harrogate, N. Yorkshire. Tel. (0423) 55885.

TANATON ELECTRONIC LTD.

1A Courtenay Place, Walthamstow E17

Service sheets + manuals new pack of 10. Mixed radio/TV music centres **£5.00**. 3K5 convergence PCB blank **£2.50**. 8K5 power PCB blank **£1.50**. Mixed bag components R.C. TR **£2.00**. Mixed bag coloured stereo knobs **£1.50**. 2N3055 unmarked, 20 for **£1.50**. High speed switching diodes ESM 181-800R, 10 for **£1.50**.

Cheque or postal order made payable to:
Tanaton Electronic Ltd.

Add 60p P+P.

TECHNICAL INFO SERVICES 76 Church St - Larkhall - Lanarks Giant TV & VCR DIAGRAM MANUALS

Brit CTVs 3 vols **£45**
Vol. 1 Decca G.E.C. ITT **£17**
Vol. 2 Philips Pye Redif. **£17**
Vol. 3 Rank Bush Thorn **£17**
Foreign CTVs (now updated) 2 vols **£32**
Mono (Stand + Port) 2 vols **£32**
Early VCR (VHS/Philips) **£17**
VCR later models inc. Betamax **£17**
Domestic Equipment Exploded Diagrams in 2 huge binders for **£32**

New T.V. Rep. Manuals **£7.50** each
1983 Brit. CTV or Foreign CTV 4
Complete set of 15 TV Rep Mans for **£105**

Unique T.V. Repair course **£9.50**
The only practical radio servicing and repair course **£9.50**

Large SAE brings FREE 50p magazine inc. service sheet/details of unique T.V. publications. Any quotation plus price lists, etc.

Full size service sheets **£2** + I.s.a.e.
CTVs/Music Centres **£3** + I.s.a.e.

Worlds largest collection of service manuals 1930 to date. From **£4.50** to **£35** each.

e.g. Autovox/G8/A823 **£7.50** each
Integrated TV repair system **£195**.
Contains over **£250** normal prices.

**FOR FAST QUOTES
RING 0698 883334**

**TO ADVERTISE
IN THIS SPACE
RING
MANDI
01-261 5846**

FOR SALE

THORN 9600. Fault guide program 48K spectrum **£4.50** p & p inc. S. WARLAND, 163 Victoria Street, Gillingham, Kent. Medway 576135.

N1700 SPARES, including heads, circuit units, tuner, motors, miscellaneous items. Telephone 074632-406.

TRADE TELEVISION SUPPLIES, now available at Bournemouth: from **£15** (minimum 5 sets). Some working sets available **£25**. Telephone Bournemouth 38081.

BOOKS AND PUBLICATIONS

"**RADIO AND TELEVISION SERVICING**" books, new editions for the last 6 years always in stock. Prices on request: **BELLS TELEVISION SERVICES**, 190 Kings Road, Harrogate, N. Yorkshire. Tel. 0423 55885.

COMPLETE FULL-SIZE SETS any published service sheets **£2** + LSAE except CTVs/Music Centres from **£3** + LSAE. Manuals from 1930 to latest. Quotations, free 50p magazine, price lists, unique technical publications for sale. Repair data/circs almost any named TV/VCR **£8.50** by return. **TIST**, 76 Church Street, Larkhall, Lanarks ML9 1HE. Phone (0698 883334).

RADIO & TELEVISION servicing books 1974-1982. Mint condition inc. rare 75/76 vol **£100**. Tel. Durham 719400.

**PLEASE MENTION TELEVISION
WHEN REPLYING TO BOX NUMBERS**

MISCELLANEOUS

BURGLAR ALARM EQUIPMENT. Latest discount catalogue out now. Phone C.W.A.S. ALARM 0274 731532.

BUSINESS/PROPERTY FOR SALE

COMPLETE TUBE REGUNNING PLANT. Electric ovens. In good working order. Free training available. Tel: 0582 410787.

FOR SALE. A66-510X, A66-120X used, seen working. Offers: Barter 01-776 0284.

JAPANESE COLOUR TVs, Panasonic, Hitachi, Mitsubishi, Toshiba, Sharp. Fully refurbished - to trade only. J. M. PEARSON TELEVISION 0484 863489.

PRACTICAL TELEVISION 220 copies 51-72. Practical Wireless 1957 only. Offers: Yatton 832472.

340 NEW individually boxed speakers, 5" ceramic 3Ω **£200**. Will quote for lower quantities. Tel. Bishop Auckland (0388) 604669.

SPECIAL T.V. CLEARANCE

DISCOUNT FOR VAN
LOAD DIRECT
FROM SOURCES

MAKES	COMPLETE NON-WORKERS	WORKING
Philips G8s, 2 Chip Bush/Murphy	£14	£26
Thorn 3000, 3500	£13	£22
Thorn 8800, 9000, 9600, 9800, Touch tune sets, etc	£25	£40
Bush T20s, Philips G11s	£90	£70
GEC Solid State, all types	£19	£28
Pye 18", 22"	£17	£28
Japanese Hitachi, National Panasonic	£15	£28
ITT CVC5/8/9	£14	£28
Decca Bradford	£10	£25
GEC/Pye - Hybrid	£5	£10

Mono in batches of 20 at **£2** each Other Makes Available on Request
Discount for Quantity

SPECIAL OFFER! SPARE TV PANELS AVAILABLE AT COMPETITIVE RATES, Philips G8s 26" - **£5** TESTED, OR UNTESTED, FOR ALL MAKES. PLEASE RING Thorn 3500 26" - **£5** FOR A PRICE LIST OF PANELS, OR SEND SAE OF PANELS REQUIRED FOR PRICE.

**M.S. ELECTRONICS, Unit 1, Warwick Street,
Earlsdon, Coventry (0203) 714213**

NB. To give prompt service, telephone to order in advance to avoid disappointment.

**REBUILT COLOUR TUBES
DELTA TYPES**

Example Prices

All sizes up to 22" — £28.00
All sizes up to 26" — £32.00

*All In Line P.I.L. Mono
Gaming Machine C.R.T.s*

20 AX £38.00 **Fast U.K. Delivery** 30 AX £48.00

Call or Phone:

RE-LIFE T.V. TUBES
PLANE STREET,
OLDHAM, LANCs.
061-665 2668

*Big reductions on Contract Orders
Home or Overseas.
Wholesalers Required
in certain parts of the U.K.*

**TO ADVERTISE IN THIS SPACE
RING
MANDI
01-261-5846**

**A.B.D.
TELEVISION LTD.**

100's Colour TV's in stock in excellent
condition—working sets for the trade.

Fresh stocks weekly
Untested — complete
(Majority working)

Mono TV's	£2
Bush 22"-26" CTV Solid State	£5
Hybrid Decca - ITT	£12
Philips G8 - 550	£18
G.E.C.	£20

Philips G11, Bush T20, ITT CS 600
Prices on quotation

Many other makes to choose from
Refurbished Sets — Showroom Condition
Ready to Retail

BRC 9000	£50
Bush T20	£75
ITT CS 600	£85

WE ARE OPEN SEVEN DAYS A WEEK
Unit 3 & 3A, Meadow Trading Estate,
Meadow Lane,
Nottingham, NG2 3HQ.
Nottingham (0602) 864627

GRUNDIG, working colour from £40.00. Recondi-
tioned panels from £4.00. Remote control handsets
wanted. Reconditioned telequipment oscilloscopes.
Repairs, spares, manuals. OCHRE MILL, 0785
814643.

TRADE ONLY

YORKSHIRES LATEST OUTLET:
Ex Rental Change Over TV's
Colour from £15.00
Mono from £ 2.00

**TELEFIX
PROVIDENCE WORKS**
Ellinthorpe Street,
Wakefield Road, Bradford 4.
Telephone: 0274 480281 or 733373

NORTHERN IRELAND DEALERS


We have the best value in secondhand televisions. And our low,
low prices are second to none. Philips 550, Decca 100/80/302, Pye
741 series and many other makes available.

*Prices: Non workers (complete) from £20.
Guaranteed workers from £38.*

*We deliver bulk orders anywhere in Northern Ireland.
New loads arriving regularly so phone now for latest stocks.*

SM ELECTRONICS

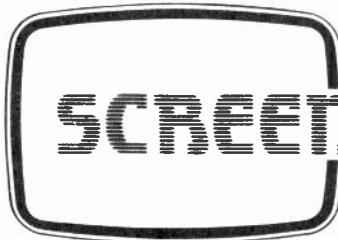11 Sandholes Road, Cookstown N. Ireland.
Tel: Cookstown (NI) 06487/64277.




Bursting with Stock!

SPECIAL CLEARANCE
of G8 22 inch from £14.50, G8 26 inch from £15.00

Guaranteed - Complete Sets from £10.00
Trade Workers from £25.00
Panels By Post from £3.00
Mono's from £1.00
Stands — Aerials — Accessories Etc.

WORKING SETS
Phone us first for quantity,
we can give an
UNBEATABLE PRICE!!!
OPEN 5 DAYS —

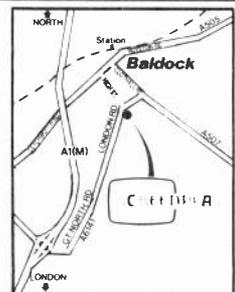Phone:
Baldock 894905, Hitchin 31644
SECTION THREE, UNIT FOUR, SERL COMPLEX,
LONDON ROAD, BALDOCK, HERTS.



Order form

Please insert the enclosed advertisement in the next available issue of **Television**

Heading

Signature

Date

No. of ins..... Chq/PO

Classified Advertisement

Department, Room 2612,
King's Reach Tower,
Stamford Street,
SE1 9LS.

NAME AND ADDRESS

.....

.....

.....

.....

7/84

● TELEBEST ●

We Specialise in Working Sets
In Retail Condition

**BUSH DECCA G.E.C. GRUNDIG
PHILIPS THORN etc**

From 25 + VAT

**HUNDREDS OF NON
WORKERS AVAILABLE**

**MANY SWITCH ONS WITH
EX. CABS.**

GRUNDIG 26" Min. of 5 **28.75 inc**
BUSH 2 CHIP Min. of 5 **16.00 inc**
G8 520 white cabs. Min. of 5 **16.00 inc**
GEC s/s wood cabs. Min of 5 **25.00 inc**

Phone **PAUL** on **01-514 1333**
For Stock Availability

**841 Romford Road,
Manor Park,
London E12.**

WETSTED TUBES PRESENTS AN UNBEATABLE OFFER

£26 ALL DELTAS ONE PRICE

£40 ALL P.I.L. ONE PRICE

* SPECIAL CRT POLISHING SERVICE
WHILE U WAIT **Only £5**

* ALL DELTA SIZES FROM STOCK

* DISCOUNT FOR ORDERS OF 5 CRTs OR
OVER

* FREE DELIVERY WITHIN 20 MILE
RADIUS OF MAIDSTONE

Ring Now

Maidstone 872400

or visit our factory.

**Unit 32, Branbridges Ind Est.
East Peckham, Kent.**

* Agents required in South

Prices do not include VAT

EAST ANGLIA SUPPLIES

Fully working colour TVs from £25.00
plus VAT straight from our retail shelves.
Most makes are available and small regular
orders are welcome. Personal services
guaranteed and if we can help you boost
your rental or retail trade we would be
delighted.

*Free delivery available
(only petrol charged).*

Contact John, Dave or Steve at
Barry T.V. Services
on Cambridge 69215
or Ely 61462

When replying to
Television Classified
Advertisements
please ensure:

- That you have clearly stated your requirements.
- That you have enclosed the right remittance.
- That your name and address is written in block capitals, and
- That your letter is correctly addressed to the advertiser.

This will assist
advertisers in
processing and
despatching orders
with the
minimum of delay.

N.W. ELECTRONICS

25 YEARS SUPPLYING THE TRADE

New low. Summer prices

HIGH QUALITY COLOUR TV's

PHILIPS 520	£ 15
PHILIPS 550	£28
GEC 2010 Plastic or Wood	£25
HITACHI 19" Push Button	£35
SANYO	£35
BUSH 2 CHIP	£ 15
BUSH 1 CHIP	£ 10
THORN 9000	£45
BUSH 718	£35
BUSH T22 Exc. Cond	£65

**OTHER MODELS IN STOCK INCLUDE:
SONY, ITT, PYE, MITSUBISHI, etc.**

MONO TV's

**MANY MONO TV's FROM
£2 EACH**

WORKING TV's TO ORDER

**EXCELLENT CABINETS -
READY TO SELL OR RENT**

BUSH 2 CHIP	£29
PHILIPS G8 550	£43
PHILIPS G11	£85
BUSH T20, T22	£ 75
GEC 210 Plastic or Wood	In lots of 50 £50 Each £38
BUSH 718	£45
ADJUSTABLE STANDS	EACH £3

LATER MODELS: PHONE FOR QUOTATION

WHITE GOODS

HOOVER TWINS	FROM £7
HOTPOINT 1460	FROM £10
AUTO's	FROM £15

SPARES! SPARES! TV PANELS

	1F	DECODER	LINE-UP	POWER	CONVERG	VIDEO	FRAME TR
BUSH 2 CHIP	1.00	8.00	6.00	3.00	3.00	5.00	5.00
3000/3500	2.00	4.00	8.00	8.00	5.00	5.00	6.00
GR	5.00	7.00	14.00	8.00	5.00	5.00	5.00
GEC 2110	10.00	5.00	12.00	6.00	5.00	5.00	5.00
BUSH 718	8.00	15.00	25.00	3.00	5.00	5.00	15.00
BUSH T20	8.00	15.00	20.00	20.00	5.00	5.00	15.00

P&P 1panel £1.50. 2 panels £2.00. 3 panels £2.50 etc. Quick Despatch-CWO Please

CASH ONLY - DELIVERY CAN BE ARRANGED
YOU CAN REACH US EASILY FROM ANYWHERE

(0274) 688458

Unit 12, Wharfedale Road **OPEN MON-SAT 9-5.30**
M606 Euroway Estate **Don't forget! We are open**
Bradford **all day Saturday!**

<p>All diodes at 10p or less in this list 20 of one type £1.00</p> <p>OA 47 8p OA 90 8p IN 60 5p IN 541 5p IN 914 3p IN 2069a 10p IN 2070 10p IN 4001 3p IN 4002 3p IN 4003 4p IN 4004 4p IN 4005 4p IN 4006 4p IN 4007 5p IN 4148x40 10p IN 4448x40 10p IN 4742 10p IN 4722 10p IN 4751 10p IN 5235 10p IN 5254 10p IN 5349 10p IN 5392 10p IN 5393 10p IN 5928B 10p IAV 30 10p IM 72Z55 10p IR 106a 20p IR 3051 10p IS 164 10p IS 921 10p IS 3011a 10p IS 3072a 10p IS 5024a 50p IS 5030 50p ITT 210 10p ITT 921 10p ITT 923 10p ITT 1075 10p ITT 2001 10p ITT 2002 10p ITT 4150 10p ZE 1.5 10p ZF 3 10p ZF 3.3 10p ZF 4.3 10p ZF 10 10p ZF 11 10p ZF 12 10p ZF 15 10p ZF 33 10p ZF 43 10p ZF 47 10p ZF 82 10p ZPD 3.9 10p ZPD 4.7 10p ZPD 5.6 10p ZPD 10 10p ZPD 47 10p ZPY 8v2 10p ZPY 12 10p ZPY 16 10p ZPY 24 10p ZPY 43 10p ZPY 47 10p ZPY 56 10p ZTE 2 10p ZTK 22 10p ZTK 33 10p ZTK 33a 10p ZW 13 12p ZW 27 10p ZW 4.3 10p ZW 310 10p ZX 68 30p ZY 47 10p ZY 72 10p AA 113 10p AA 119 8p AA 144 10p BA 102c 10p BA 157 8p BA 159 8p BA 173 8p BA 182 8p BA 201 8p BA 202 8p BA 243 8p BA 248 8p BA 316 5p BA 318 5p BAV 10 10p BAV 21 10p BAW 21 10p BB 103 10p BB 105A x12 10p BB 105B x12 10p BB 105G x12 10p BB 121a 10p BRC 83c13 10p BZX 46c22 15p BZX 61 9-1 6p BZX 61c110 10p BZX 61c20 10p BZX 61c30 10p BZX 61c220 10p BZX 70c6v2 8p BZX 70c12 20p BZX 70c33 8p BZX 79c3v9, 4v7, 5v1, 5v6, 6v2, 6v8, 7v5, 11, 12, 30, 47 10p each BZX 83c4v3, 5v6, 8v2, 12, 13, 24, 27, 33 10p each BZX 84c6v8 x10 30p BZX 85c8v2 10p BZX 88c0v7, 3v9, 4v3, 6v2, 8v2, 12 10p each 1A/1600V 10p CV 8617 10p</p>	<p>Min 12 volt Relays 75p</p> <p>Y 716 10p Y 729 30p Y 730 10p Y 827: 6A/1KV 20p Y 860 30p Y 933 30p Y 969 50p Y 997 30p R 1038 40p R 1039 40p R 2009 80p R 2010b 50p R 2029 40p R 2210 60p R 2257 60p R 2265 50p R 2305 50p R 2306 50p R 2322/2323 pair 80p R 2323 15p R 2396 50p R 2461 80p R 2030 50p R 2443=BD124 40p R 2737 40p R2738=TIP41 30p R2775=TIP41c 40p R3129=TIP47 40p S 2008b 80p</p> <p>BU 105/04 80p BU 108 10p BU 124 50p BU 126 80p BU 180a 65p BU 204 70p BU 205 10p BU 206 10p BU 207 10p BU 208 80p BU 208 on heat sink 70p BU 208A 10p BU 208D 90p BU 222 10p BU 326 10p BU 407 60p BU 426V 60p BU 500 10p BU 508A 10p BU 526 75p BU 807 10p BUX 84 50p BUW 84 30p BUY 71 10p</p> <p>TIC 106a 30p TIC 116m 40p TIC 116n/Y 1003 35p TIC 126N 40p TIC 206m 30p TIC 225S 40p TIC 226E 40p TIC 226m 30p TIC 236m 30p TICV 106D 10p (TO92 case 2A/400V) 10p TIP 29 20p TIP 30 35p TIP 30A 35p TIP 30B 40p TIP 30C 45p TIP 31 30p TIP 31A/RCA 16334 35p TIP 32 25p TIP 33B 50p TIP 33C 70p TIP 34A 70p TIP 34B 60p TIP 34C 70p TIP 35B 50p TIP 35C 70p TIP 35D 80p TIP 36 50p TIP 36C 70p TIP 41B 40p TIP 41D 70p TIP 42/BRC 6109 30p TIP 48 40p TIP 49 30p TIP 57 30p TIP 100 30p TIP 102 30p TIP 112 30p TIP 115 50p TIP 117 50p TIP 120 35p TIP 125 35p TIP 130 30p TIP 131 25p TIP 136 30p TIP 140 50p TIP 147 50p TIP 640 50p TIP 645 50p TIP 2955 35p T 6032 30p T 6036 40p T 6040 40p T 6047 40p T 6049 40p T 6051 40p T 6052 40p T 9004 40p T 9005 40p ZTX 102c 10p ZTX 107 10p ZTX 108c 10p ZTX 109k 5p ZTX 213 5p ZTX 341 10p ZTX 342 10p</p> <p>SPECIAL OFFER CVC 21 Chassis complete £35 Computer Transformer 20v/2.5A; 20v/1.5A; 17v/5A; 19v/5A; 28v/0.5A £3</p>	<p>ZTX 384 10p ZTX 451 10p ZTX 550 10p MJ 2253 60p MJE 3040 60p MJE 2209 10p SP 8385 50p</p> <p>Voltage Regulators +5V/UA78P05SC 30p -5V/LM79M05CPC 25p -8V/79M08c 30p +6V/78M06c 30p +10v/78LA10 20p LM 337 30p LM 342/18 30p LM 340T 5.0 50p -12V/MC 7912 20p +12V/LM 340T12 50p +15V/78M15 15p +18V/MC78M18 20p +24V/78M24 30p MC 7724cp 40p MC 7824 40p TIS 90 10p TIS 91 20p TIS 92 20p TIS 93 20p</p> <p>CB Radio transistor 16119 2A/40v.50Meg 5 for £1.</p> <p>U 19885 40p U 3832 15p U 3845 15p MR 508 10p MR 501 10p MR 502 10p BCW 71R 30p BYF 1202 10p BYF 1204 10p BYF 3126 40p BYF 3214 40p BYX 10 6p BYX 36/600 35p BYX 38/300 25p BYX 55/350 10p BYX 55/600 (Bead) 10p BYX 71/350 20p BYX 71/600 50p BYX 72/300 20p BYV 95B 10p BYV 95C 12p BYV 96D 10p BYZ 106 10p BPW 41 15p BYW 56 2A/1000v G11 8p BZY 93c75 50p BZV 15/18 30p BZV 15/30 30p BZV 70c6v2 10p BZX 79.3v 10p Bush thyristor RCA 76122 £1 ITT computer booklet 2020 £2 G8 20 turn 100K pot 35p Transformer 240v/20v-500Ma 75p Viewdata torroids £6 CVC 20 tube base £2 Mitsumi tape motor 75p Sanyo tape motor 75p Swiss made 250rpm/240V motor very small 75p Mono scan coil 110" small neck £1.50 Infra red led £1.50 LD57CA 15p Mono scan coil £3 G 8 transductor £1 AT 4041/41 transductor £1 2K5 Lin pot with 40mm spindle 20p 1982 Hitachi Ae isolator 50p Mullard FM decoder 1401 £1 Philips service pack, flat films, 57 condensers 56nf-2.2uf £2 VHF 3 Transistor rotary tuner DX-TV £1 15K-20 turn pots 20p Thorn panel 6x100 pot + changeover switch (Irish) 50p Battery converter TA 75 for colour TV. 12/24v Thorn 3787 £6 Thorn 3500 2A cut out 75p</p> <p>Stereo GEC amp 20 watt + pre-amp with 4 pots + mains power unit with circuit £6</p> <p>SPECIAL OFFER Decca-TTT etc. FEO4/1/250AC/4 Mains filters (grey type) x 4 £1</p> <p>BRIDGES SKB 2/08 L5A 30p KBL 005 30p KBL 02 30p KBP 04 30p W02 15p W04 15p W05 20p GEC remote panel. Main transformer 3/c SAA 1025/SN 74141/TBA 231 £6 AT 2076/55 GEC split diode £10 Mullard AT 2048/11 LOPTI £2.50</p>	<p>PHILIPS DIY HOME SECURITY ALARMS KITS Send for details. Prices £54 to £112.</p> <table border="1"> <tr> <td data-bbox="816 190 1039 481"> <p>10 Mixed TV & radio speakers £5 + £2 post</p> <p>8Ω 4" speakers £1 4700/10v x 10 50p 68/16 x 10 50p 150/16 x 10 50p 47/25 x 10 50p 220/25 x 10 50p 1/250 x 10 50p 8000/30v 50p 470/40v x 10 £1 22/100v x 10 £1 100/350v 70p 400/350v 70p 47/500v 25p 1/600v 25p .022/1kv 10p</p> </td> <td data-bbox="1039 190 1262 481"> <p>Philips GP422.4CH (£40 cost) £6</p> <p>Stereo Dynamic Cartridge</p> <p>12 Volt Aerial Changer over Relays £1</p> <p>GEC Hitachi V/Cap tuner, after 1979 Series £13 6 Push Button Unit for GEC 2100 Series £12 Replacement for Touch Button Unit £12</p> </td> <td data-bbox="1262 190 1486 481"> <p>Mullard Broadband R.F. power modules</p> <p>VHF. BGY33 £15 UHF. BGY22E £5 PT4236C £5 PT9783 £5</p> </td> </tr> </table> <p>Various Tools and Accessories</p> <p>Philips Freeze £1.00 Foam Cleaner £1.00 Contact Cleaner £1.00 G11 Neon Switch £1.00 GPO 5 way plug 25p 12v screwdriver tester with lead + croclip 25p Mains timer, 13 amp - up to 2 hours: easy to use, plugs into socket £3.00 Sellotape PVC Electric Insulation 25mm x 20M 70p Telescopic aerials (radio) £1.00 UHF Radio Aerial 50p Xcelite pliers £3.90 Xcelite snips £5.00 Xcelite cutters £3.90 GKN Supascrow kits £2.50 VU meter 45p Pull up large aerial 75p "V" TV aerial £1.00 Soldering iron 6v/23w £2.50 Weller solder iron 15 watt/25 watt £5.00 Portable TV aerial 75p Phillips snips £2 2 way baby alarm/intercom with long leads £5 Phillips universal battery tester/charger, fuse/bulb tester £2 Vol/ohm test meters 1000 ohm/volt To Clear £4 Eisenmann NICAD CHARGER 5.5V/150 ma £2 12V Nicad pack. "AA" £2.50 Hitachi TP 007 Battery pack 7.2v/1.6A £7 Hitachi Silver Oxide Battery G13 UCC357 IEC SR44 1.5V "AA"/1.25V Nicad 60p "AA"/1.25V Nicad £1 "C" Nicad £2 "D" Nicad £3 Duracell PP3 60p Duracell "C" 50p 70ML Silicone Sealer (clear) £1 1/2" x 1/2" microphone/speaker 50p Continental 2 pin plug with 5ft mains lead (black & blue) 5 for £1 7" Ferrite rod with LW/MW coils £1.75 Xcelite 5" bent nose plier £3.50 De-solder pump + 2 nozzels £5.20 Plastic box for i.c.s with anti-static pad 6"x3"x4" 75p Can of handy oil "mobil" 40p Flat Red LED 12p 500gm 60/40 solder reel £7 Clearweld glue pack 30p Dual v/u meter -20 - +10db £1 15 service manuals, Thorn 3504 & 3448, etc £2.50 3 x C90 Cassettes 70p Can Freezer £1.75 K30 thermistor 232266298009 75p</p> <table border="1"> <tr> <td data-bbox="816 1310 1039 1500"> <p>75R/25 Watt 25p 18R/11 Watt 25p 120R/17 Watt 20p</p> <p>Front End Music Center. VHF/MW/LW 13"x34" £3 Output Stage for music center £5 SONY 1400KV Chroma Panel £6 SONY 1400KV Tuner unit £3.50 SONY 1400KV Touch button unit £3.50 Texas Viewdata Decoder VDP 12/80 Issue 3 with all IC's £10.00</p> </td> <td data-bbox="1039 1310 1262 1500"> <p>100 Fuses £2.00 100 W/W Res. £1.50 BF 199 20 for £1 BC 547 100 for £4 10 x 20 Turn 100k pots. Rank £2 Thorn 9 volt power supply regulated £3.00 BF 470 20 for £2 Metal BD 124 10 for £8 20 Slider Knobs 70p 6 Mixed UHF Aerial Isolating Sockets, some with long leads. Fit ITT, GEC, Philips, Pye £1.00</p> </td> </tr> </table> <p>Quantity Reductions</p> <p>BY204/4 25 for £1.00 BY206 25 for £1.00 BD132/238 20 for £2 W005 bridge 20 for £2 G11 touch button red 6 for £1 BY210/600 25 for £1.00 BY298 3 amp/fast/R 20 for £1.50 BD239 20 for £2.00 MR856 25 for £1.50 BU126 10 for £6.00 BU205 10 for £8.00 BU105 10 for £6.00 2SC2122A 10 for £8.00 BF458 10 for £1.00 BD136 10 for £1.25 BF224 20 for £1.40 OA90 40 for £1.00 BYX10 100 for £4.00 KT3 multiceps 10 for £7.50 50 High voltage ceramic condensers £1.50 Mixed Mounting Kit for Power Transistors 50p 300 Condensers £1.50 300 Resistors £1.50 150 Electrolytics £2.00 15 Bulbs 40p Video lamps 20 for £5, 200 for £25 Antistatic Discloth 5 for £1 100 Diodes £1.50</p> <p>Mixed Packs</p> <p>TO66 12 Power Trans RCA 16182 NPN Replacement for BD124 and Mounting Kits £1.00 50 Mixed AC series Transistor £4.50 15 Panel mount rocker switch 250V/10A £1.50 25 Panel Mount Bulbs & Neons £1.50 25 LED red/yellow/green £1.50 20 Convergence Pots £1.20 20 Large LED Red £1.00 20 Small LED Red £1.00 10x20 Turn 100K Pots £1.00 100 Transistor £2.50 20 Convergence Pots 80p 100 Sockets £1.00 10 Thermistors 50p 20 Slider Pots £1.00 30 Presets 50p 15 VDR + thermistors, degaussing, HT, etc. £1.00 40 glass reed switch £1 10 press to make switch 70p 40 Pots £1.50 10 Gun Switches 50p 5 Tube Bases £1.00 1,000 Diodes, Condensers, Resistors on Bandolier £3.00 Lucky Dip 600 gram £1.00 Jungle Bag 5Kg £5.00 20 Knobs £1.00 40 Pots, 1/2"+6mm spindles for audio/TV/£3 £1.00 20mm Fuse Holders £1.00 Chassis Mount 10 for £1 IN4001/6 100 mixed £2.50</p>	<p>10 Mixed TV & radio speakers £5 + £2 post</p> <p>8Ω 4" speakers £1 4700/10v x 10 50p 68/16 x 10 50p 150/16 x 10 50p 47/25 x 10 50p 220/25 x 10 50p 1/250 x 10 50p 8000/30v 50p 470/40v x 10 £1 22/100v x 10 £1 100/350v 70p 400/350v 70p 47/500v 25p 1/600v 25p .022/1kv 10p</p>	<p>Philips GP422.4CH (£40 cost) £6</p> <p>Stereo Dynamic Cartridge</p> <p>12 Volt Aerial Changer over Relays £1</p> <p>GEC Hitachi V/Cap tuner, after 1979 Series £13 6 Push Button Unit for GEC 2100 Series £12 Replacement for Touch Button Unit £12</p>	<p>Mullard Broadband R.F. power modules</p> <p>VHF. BGY33 £15 UHF. BGY22E £5 PT4236C £5 PT9783 £5</p>	<p>75R/25 Watt 25p 18R/11 Watt 25p 120R/17 Watt 20p</p> <p>Front End Music Center. VHF/MW/LW 13"x34" £3 Output Stage for music center £5 SONY 1400KV Chroma Panel £6 SONY 1400KV Tuner unit £3.50 SONY 1400KV Touch button unit £3.50 Texas Viewdata Decoder VDP 12/80 Issue 3 with all IC's £10.00</p>	<p>100 Fuses £2.00 100 W/W Res. £1.50 BF 199 20 for £1 BC 547 100 for £4 10 x 20 Turn 100k pots. Rank £2 Thorn 9 volt power supply regulated £3.00 BF 470 20 for £2 Metal BD 124 10 for £8 20 Slider Knobs 70p 6 Mixed UHF Aerial Isolating Sockets, some with long leads. Fit ITT, GEC, Philips, Pye £1.00</p>
<p>10 Mixed TV & radio speakers £5 + £2 post</p> <p>8Ω 4" speakers £1 4700/10v x 10 50p 68/16 x 10 50p 150/16 x 10 50p 47/25 x 10 50p 220/25 x 10 50p 1/250 x 10 50p 8000/30v 50p 470/40v x 10 £1 22/100v x 10 £1 100/350v 70p 400/350v 70p 47/500v 25p 1/600v 25p .022/1kv 10p</p>	<p>Philips GP422.4CH (£40 cost) £6</p> <p>Stereo Dynamic Cartridge</p> <p>12 Volt Aerial Changer over Relays £1</p> <p>GEC Hitachi V/Cap tuner, after 1979 Series £13 6 Push Button Unit for GEC 2100 Series £12 Replacement for Touch Button Unit £12</p>	<p>Mullard Broadband R.F. power modules</p> <p>VHF. BGY33 £15 UHF. BGY22E £5 PT4236C £5 PT9783 £5</p>						
<p>75R/25 Watt 25p 18R/11 Watt 25p 120R/17 Watt 20p</p> <p>Front End Music Center. VHF/MW/LW 13"x34" £3 Output Stage for music center £5 SONY 1400KV Chroma Panel £6 SONY 1400KV Tuner unit £3.50 SONY 1400KV Touch button unit £3.50 Texas Viewdata Decoder VDP 12/80 Issue 3 with all IC's £10.00</p>	<p>100 Fuses £2.00 100 W/W Res. £1.50 BF 199 20 for £1 BC 547 100 for £4 10 x 20 Turn 100k pots. Rank £2 Thorn 9 volt power supply regulated £3.00 BF 470 20 for £2 Metal BD 124 10 for £8 20 Slider Knobs 70p 6 Mixed UHF Aerial Isolating Sockets, some with long leads. Fit ITT, GEC, Philips, Pye £1.00</p>							

SENDZ COMPONENTS

TO ORDER SEE BACK PAGE

Thorn Spares		BY 210/400	5p
9000 tube base and panel	£1.50	BY 210/600	8p
9000 Front Panel	£5	BY 210/800	10p
9000 Front Panel (remote)	£8	BY 223	£1
8800/9000 remote unit U705 receiver	£6	BY 224/600: 4.8A/600v bridge	50p
9000 Frame panel	£8	BY 226	15p
9000 Cyclops panel	£1.50	BY 227	15p
8000/8500 timebase panel	£8	BY 228	20p
8000/8500/9000 chroma panel	£15	BY 229/400	30p
8800 convergence panel	£6	BY 234	10p
8500 convergence panel	£6	BY 237	5p
4000 Frame panel	£5	BY 238	15p
4000 Chroma	£20	BY 254	10p
4000 Power supply	£3	BY 255	30p
1600 Mains lead, switch		BY 298	10p
3500 6 push button + cable form	£1.50	BY 299	10p
T605 1vNPN T066 80v/6A	10p	BY 406	8p
9000 Sound output panel	£1	BY 527	20p
3500 Focus unit	£1.50	BY 407a	10p
4000 thick film.		BY 602	10p
00S1-010-E003	£1	F 247	10p
00S1-012-E002	£1	XX K1 3102	50p
00S1-012-0108	£1	XX K1 3123	50p
00S1-018D	£1	Hitachi 2A/1500V metal case wire end	20p
3500 Mains Trans	£4	Line Transformers	
3500 2amp thermal cutout	75p	G8 Trans. Philips	£6
3500 IF panel	£2	G11 Split Diode	£12.00
3500 Frame panel	£3	CVC820 Split Diode ITT	£10.00
3500 Video panel	£5	Thorn B/W AD5308F + Stik + Lead	£1.50
3500 Line panel	£3	GEC 2040	£3.00
3500 A1 Diode	20p	GEC 2110	£7.00
Export 3500 IF panel	£2	Mullard AT 2036	£1.50
Remote unit, 11c, transformer, relay + 5 volt unit	£2	Pye 169 Line Trans	£3.00
IC board with set of SN74LS	£1	Pye mono	£3.00
4000 Tube base	£4	Rank mono T704A	£3.50
3500 A1 pots	50p	CVC32 ITT	£7.50
Beam limiter panel	£1.50	GEC Portable G10T2041	£3.00
3500 Power panel complete	£1	GEC Portable G10T2046	£3.00
3 way regulated adaptor 240V 6V/7.5V/300mA	£3.50	EHT Split Diode Leads	£1.00
Rank/Toshiba preh unit 0354	£9.50	EHT Cable/Metre	20p
2 banks of 3 PB unit. Pye 731	£2	Ex panel "14" Fidelity portable	£5
4 Push button unit preh	£1.00	Triplers	
6 Push button VHF/UHF for v.cap. GEC-Decca type	£7.00	11 TEZ Rank	£3.00
7 Push button for CVC5 ITT	£8.00	G9 Philips	£4.00
KT3 12 Push button unit	£2.00	GEC 2110	£4.00
KT3 (Export) 12 P.B.U.	£2	9000 Thorn	£6
6 Push button Unit Thorn	£1.00	9500 Thorn	£4.50
6 Push button unit for GEC 2040 and ELC 1043/05	£6.00	2040 GEC	£3.50
Hearing aid unit	£3	GEC TFM25 Tripler	£2.00
6 Push button unit PYE 713	£7.00	Universal Tripler	£6.00
7 Lamps for P.B./Unit	10p	TVK 76/9	£3.00
Mains Droppers		G8 Philips	£4.50
Pye 731 3+56+27R	50p	Decca 80 100	£4.50
Pye 3RS/15R/45R	50p	Grundig TVK 52	£2.50
Thorn 50/17/1K5	£1.00	11TBQ Pye 731	£3.00
120/20/20/48/117	£1.00	11THY	£4.00
270/10/6 for Thorn 4000	50p	D22 for Pye 18" colour portable	£4.00
18/320/70/39	£1.10	LP 1193/63	£4.00
Thorn 50-40R-1K5	50p	BG 100/41	£3.25
Ae Socket & Lead		BG 100/61	£3.25
GEC, ITT, Philips, Pye	25p	KT3 BG200/43	£3.50
7x3 1/2 Thorn	£1	T/Text ultrasonic rec'r panel	£14.00
Rank Toshiba Tube Bases	30p	Video cassette lamps on lead.	
Speakers		12-14V.	50p or 3 for £1.00
6x4 G11	25 ohm	GEC 8 touch unit assy complete with all I.C.'s + pots	£4.00
5x24	3 ohm	G11 E.W. coils	£1.00
5x3	80 ohm	G11 Transient Suppressors	
5x3	50 ohm	245V	10 for £1.00
5x3	35 ohm	G11 Scan Coils	£5.00
5x3	15 ohm	G11 100K tuner pots	12 for £1
6x4	15 ohm	KT3 IF panel	£6.00
7x3	70 ohm	KT3 line OSC transformer	£1
5x3	8 ohm	KT3/K30 infra-red receiver head	£3
7x3	16 ohm	K30 drawer unit with IC's (home)	£10
5" dia	16 ohm	K30 drawer unit with IC's (export)	£10
5" dia	8 ohm	KT3 AE Sockets	25p
6" dia	4 ohm	KT3 receiver panel	£8
6" dia	3 ohm	KT3 line driver transformer	50p
2" dia	8 ohm	Decca 80/100 IF panel	£5
3" dia	8 ohm	NPN PNP 80V 6 Amp TO66 O.P. Trans.	pair 25p
KT3 speaker		5 button touch tuner BBC1/2	
3" dia	15 ohm	ITV1/2 video with ic SAS 560T/570T	£7.00
Diodes		Control panel 5 sliders + mains lead	£1.50
BY 127	10p	G11 8 touch button unit replaces old 6 P.B.U.	£24
BY 133	10p	Tube base + base unit for 820 Euro chassis	£4.00
BY 134	10p	GEC Line O/P Trans. & Rec Stick for Portable	£3.00
BY 164	50p	CVC 20/25/30/35/40 decoder panel	£10
BY 176	25p	CVC 20/25/30/35/40 decoder panel (untested)	£5
BY 179	40p	CVC 40/45 IF panel	£5
BY 184	25p	40K Transducer	50p
BY 187	10p	PHILIPS NES11N	£1.20
BY 190	10p	LM337M Reg.	30p
BY 196	30p	20 GEC Black Spark Gaps	£1.00
BY 198	10p	G11 Line Driver Transformer	35p
BY 204/4	8p	BTW 30/50	
BY 206	8p	G770/HV34 6KV	3 for 8p
BY 208/800	8p	BTW 92/800R	£3
International Rectifier EHT Diodes	20p	6A/1000V Stud Diodes	20p
6A/600V Stud Diodes	20p	25A473 PNP C/P	10p

Complete new GEC portable chassis M1201H/M1501H with P.B.U./v.cap/LOPTI £10

Field + Jungle panel for GEC 3133/3135 £1.50

GEC 2110 line panel with transformer £7.00

GEC 2110 tuner unit + IF Panel £12.00

Pye/Chelsea Line op panel £12.00

Pye 713 IF panel and tuner £7.00

Pye 7-3 Chroma £10.00

Pye/Chelsea Timebase panel with LOPTI £10.00

Pye 731 Frame Panel £5.00

Pye 731 Convergence Panel £5.00

Pye 731 line O/P panel with transformer + tripler £12.00

Pye 731 Chroma £10.00

Pye 731 IF panel + tuner £10.00

Pye 607/205 Line panel with transformer £10.00

Pye CDA/205 panel £6.00

GEC portable chassis + LOPTI 2114 New Thorn 1613/1713 chassis 9.75

Hills 520 multimeter + case. 20,000Ω/volt, fuse diode protected + logic test facility. 10meg/1200 volt £19.50

NEW MULLARD TELETEX

Decoder Panel (VM6230) £15.00

Panel 6101 £15.00

Panel 6330 £15.00

G8 Tuner Unit + Panel £8.00

G8 Convergence Panel (late type) £12.00

G8 Line O/P Panel £12.00

G8 Power Supply £6.00

G8 6 Sloping PBU £12.00

G8 IF + Chroma £12.00

G8 Chroma £6.00

G11 IF Detector £3.00

G11 Selector gain module £3

Complete CVC 825 Chassis (both panels) £40.00

AEC V/Cap Resistor Unit UHF with IC SAS660 SAS670 £3.00

Z714 RANK IF Panels 6MHz 1 I.C. SLA37F £3.00

L2909B RANK IF Panels Export 5.5MHz 2 I.C.'s TBA1205B TCA2705Q £2.50

Z743 RANK IF Panel Export 5.5MHz 3 I.C.'s TBA750+SC9504P+SC9503 £1.50

Pye G11 Front panel with transducer, pots, tuner pots, 6 pb switch+lead £5.00

GEC V/cap VHF/UHF tuner and IF + sound O/P PC 706B3 (Export) £12.00

GEC Line O/P PC 659B3 £10.00

GEC Power Supply (Export) £10.00

G11 dynamic correction panel £6

CVC 20 Front panel with sliders + mains input panel £4

CVC 40 PUSH BUTTON ASSY with sliders: complete with lamp assy + pots £14

CVC 5 Mains on/off + 5 pots £2

GEC Convergence panel £11

Universal Focus. Fits Pye, Thorn and Decca Units.

Large Type 75p

Decca Small 75p

KT3 Focus Unit 75p

K30 Focus Pot 75p

CVC 32 Focus Unit 75p

Focus Rod 25p

G11 focus £2.00

ITT Small for use with Split Diode 50p

TV11 50p

Renov TV12SP 50p

TV13 50p

TV14 50p

TV18 60p

TV20 £1.00

TV45 50p

Thorn 14/1500 rec stick 5p

16 Button Key Pad 1 to 0 + * + # + 4 blank (Cherry) £3.00

Condensers

470/16 6p

1500/16 20p

3300/16 20p

10000/16 25p

15000/16 25p

3300/18 20p

47/25 5p

470/25 5p

680/25 5p

1000/25 Radial 10p

1500/25 10p

3300/25 25p

4700/25 25p

5000/25 25p

3500/30 20p

470/35 6p

2200/35 25p

100/40 5p

220/40 5p

400/40 20p

1250/40 20p

1500/40 20p

2500/40 25p

1000/50 25p

1250/50 25p

2000/50 20p

3000/50 25p

3300/50 25p

Infra Red and Ultrasonic G11 Teletext Decoder Panel £1.50

RANK & ITT Mains Remote On-Off Switch (720R) £1.50

RANK & ITT Mains Remote Switch 2865 ohm £1.50

RANK & ITT Remote Switch 2800 ohm £1.50

G11 Mains Switch 50p

4 amp Mains Switch 30p

GEC Mains Switch 4 amp 30p

KT3 Mains switch £1.00

THORN Rotary Mains Switch 75p

G8 Mains Switch 24p

Thyristor 600/4 amp C106/2 20p

G11 Preh Red LED P/Buton for C.H. Change RANK TOSHIBA Transducers TPC-2011 £50p

CVC 5 Mains on/off + 250K + 100K + 500K + 50K + 500K Pot on Panel £2.00

Thorn 12 or 24 volt battery converter for portable colour T/V £12.00 Post £1

20n/2KV 15p

0.0082/2500 15p

150/3500 10p

1800/4KV 5p

4.7n/5KV 10p

170/8KV 10p

180/8KV 10p

210/8KV 10p

1000/10KV 10p

210/12KV 10p

1000/12KV 10p

1200/12KV 10p

Multi-Caps

Thorn 3500

175/100/100/350v £1.75

KT3/200/25/25/385v £1.00

300+300+150+100+50MFD 350V £2

47/220/350v 60p

150/150/100/100/320v £2.00

2500/2500/63v 50p

470/470/250v 50p

150/200/200/300v 70p

400/400/200v £1.70

300/100/100/16/275v £1.50

100/200/325v 40p

150/150/100/375v £1.50

750/250/250/300v 2.00

1500/2000/30v 50p

Jelly pot Thorn 00D4/013 £3

150/150/100/100/320v £2.00

100/300 + 300/200/100/16/275v £2.00

300+300/300 £2.00

225+25/380 £1.50

200/100/100/350v 70p

500/500/25v 50p

150/150/100/300v 75p

200/150/100/300v 1.00

ITT Panels

ITT 8 & 6 Push Button Unit £1.00

CMA 10 £2.00

CMA 11 £2.00

CMA 30 £2.00

CMA 40 £1.50

CMA 10/2 £5.00

CMA 16 £4.00

CMA 38 £8.00

CMA 45 £1.50

CMA 47 £1.00

CMA 52 £15

CMA 57 £6.00

CMA 58 £8.00

CMA 59 £8.00

CMA 67 £3.75

CMA 67/2 £4.00

CMA 68 £4.00

CMD 12 £10

CMD 32 £5.00

CMD 33 £5.00

CMD 40 £5.00

CMD 41 £5.00

CMA 25 £2.00

CMA 26 £2.00

CMA 31 £1.50

CMA 40 £2.00

CMA 40 £2.00

CMA 10 £1.50

CMA 31 £1.00

CMA 12 (untested) £4.00

CMA 30 (untested) £4.00

CMA 20 £1.50

CMA 21 £1.50

CMA 40 £1.00

CMA 45 25p

CMA 10 £2.00

CMA 30 £4.00

CMA 30 £2.00

CMA 40 £2.00

CMA 12 £10.00

CMA 14 £8.00

CMA 30 £7.00

CMA 40 £7.00

CMA 45 £7.00

CMA 30 £5.00

GMA 90 £5.00

GMC 120 £2.50

GMR 64 £5.00

TMN 2 £2.00

VCA 20 £10

VCA 21 £10.00

VMC 26 £3.00

VMC 34 £5.00

VMC 44 + 45 £4.00

VMC 51 £5.00

Hand Sets

Transducer Hand Set Insert, crystal, transducer, SAA 1124 & lead £3.50

8 C.H. Ultrasonic GEC Full Remote C2014H/C219H £15.00

New Replacement for G11 Ultrasonic Full Remote £15.00

Thorn 4000 insert with 7 buttons £5.00

Decca RC 11 £14.00

Decca RC 12 £14.00

G11 Infra-red full teletext £19.00

C11 Ultrasonic full teletext for G2bc 674/02 and G22c 66/02 £16.00

Philips, 2 button £8.00

Rank, Infra-red £10.00

Dynatron-Full remote CTV 62, 63, 64 £19.00

Philips full remote KT3, 16C92B/20C934, 7228/7324; K12 26C 747/1ST 66K 1826 £12.00

G11, Full remote top button assy. £12.00

G11, Full remote repair service (exchange unit) £12.00

Philips infra red full remote 9 channel for 60 CP2605 £6.00

Philips infra red full remote 12 channel for 60 CP2605 £12.00

KT3/K30 T/Text £15.00

KT3/K30 Full remote £15.00

KT3 Power supply £4.00

Tuner Units	
GEC or Hitachi 6 push button unit	£12
GEC 2110 V/Cap	£6
ELC 1043/06 (AEG)	£6
ELC1043/05 Mullard	£6.00
ELC1043 (Ex Panel)	£3.75
ELC1042	£5.00
ELC2000	£7.00
ELC2004	£10.00
ELC2006	£10.00
GEC Tuner V/Cap Hitachi After	
1979 ET548	£10.00
U322 (UHF)	£4.00
V314 (VHF)	£5.00
U321	£7
U341 UHF	£7.00
ELC1043/05 Thom	£5.90
Small V/Cap Mitsumi	
UHF	£4.00
VHF	£3.00
Portable & rotary Tuners Sanyo & Mitsumi UHF	£5.00
6003 Bush V/Cap Tuner	£10.00
NSF-UHF/VHF Varicap (old type)	£10.00
Mosfit UHF/VHF (new type)	£10.00
SONY 1400KV Tuner unit	£3.50
Thorn Tuner PANEL with 6x100K pots + cursors NO TUNER	£1.00
U321 on panel FTT 40	£6.00
Tuner unit VHS Sylvania GTR	£2.50
Videoon MTS 900	£2.50
Thorn 3500 tuner panel with ELC 1043/05 + pots	£7.00
Mullard Video Modulator.	
Application, video tape recorders, TV cameras, video games, closed circuit TV, C.C.L.R. system. Data supplied.	£10.00
VT 100 Sound Tuner Kit. TV. Viosound. The latest design in low noise fitted with DNR, RF output and audio	£30.00
Sylvania UHF VHF F6013 (Fits Rank)	£6.00
Sylvania F6003	£6.00
Sylvania UHF F4720B	£6.00
Sylvania VHF 900	£6.00
Decca Bradford Tuner 5 Button	£4.00
Small Tuner DX 175-220MHz	
Auto Changeover	£5.00
9000 Thorn Tuner on Panel	£7.00
D.P.D.T. switch Black knob: Chassis or PCB mount	4p each or 40 for £1.00

SENDZ COMPONENTS

63 Bishopsteignton, **Shoeburyness, ESSEX SS3 8AF**

SAME DAY SERVICE
All items subject to availability.
No Accounts : No Credit Cards
Postal Order/Cheque with order
Add 15% VAT, then £1 Postage

Add Postage for overseas
Callers: To shop at 212 London Rd., Southend. Tel. 0702-332992

Open 9-11/2-30.6. G.V.M.T + school orders accepted on official headings add 10% handling charge.

THORN 1400 4P.B. Mech. Tuner	
THORN 1500 4P.B. Mech. Tuner	
THORN 1590 4P.B. Mech. Tuner	
THORN 3500 4P.B. Mech. Tuner	
THORN 8000 4P.B. Mech. Tuner	
THORN 8500 4P.B. Mech. Tuner	
All new & boxed. £4.00 each	
Delay Lines	
DL20A	80p
DL600	£1.00
G8 (Old Type)	£1
DL700	£1.00
UDL11	30p
KT 3 Luminescence	75p
Luminescence Delay Line (CVC 45)	
10x630ma fuse	25p
10x2A fuse	50p
10x3.15 fuse	50p
Co-Ax Joint	15p
Co-Ax Belling Lee Plug	15p
Co-Ax Splitter	£1.00
UHF Modulator CCIR	£3.00
Infra Red Emitting Diode	20p
NE286H Small Neon Lamps	
GEC	5p
Mullard 5 Watt Amps. LP1162	
New	75p
T.V. Tubes	
12" A31/300 Hitachi	£10
15" A38/170W Hitachi	£8
18" Hitachi PIL tube with scan coils	£25
Integrated Circuits	
AC76003	£1.50
AM25LS23PC	10p
BAV40	40p

BRC-M-200	40p
BRC-M-300	50p
BRC 1330	75p
BTT822	£1.00
BTT6016	£1.20
BTT6018/ML237B	£1.50
BTT6218	£1.50
BTT8124	£1.00
BTT8224	£1.00
CA270AE	50p
CA270CW	50p
CA270CE	50p
CA920AE	£1.00
CA1310	50p
CA3065Q	50p
CA3089Q	50p
CA3094AE	50p
CA3123	40p
CA3146	£1.00
CA3189	50p
CBF16848	40p
CD4510	30p
DM7492	50p
HA1196	40p
HA1370	£2.00
HA11223	40p
HEF4001	10p
HEF4011AF	10p
HEF4053B	30p
M913	£2.00
MI024=SAA	£2.00
MI025=SAA	£2.00
MC476p	£1.00
MC1307	75p
MC1330	75p
MC1349	50p
MC1352	£1.00
MC1358	£1.00
MC14002	15p
MC14013	25p
MC14016	25p
MC14066	15p
MC14069	15p
MC14514	10p
MC1748	80p
MCM2114	75p
MEM4956	£1.00
ML231	£2.50
ML232	£1.20
ML236E	£1.50
ML237B	£4.00
ML238B	£4.00
ML239	£3.00
MM5387	£1.00
MM5611	£1.00
MM5840	75p
N64100	£1.00
NE545B (Dolby)	75p
NE555P	60p
NE555	60p
LL-1	30p
OPT600	30p
OPT601	30p
SAA611	£1.00
SAA661	£1.75
SAA1020	£4.00
SAA1021	£4.00
SAA1024	£2.50
SAA1025	£2.50
SAA1073	£3.00
SAA1074	£3.00
SAA1124	£3.00
SAA1130	£2.50
SAA1174	£3.00
SAA1176	£3.00
SAA1250	£3.00
SAA1272	£3.00
SAA1276	£3.00

SAA5000	£1.50
SAA5000A	£1.50
SAA5012A	£5.00
SAA5020	£3.50
SAA5030	£5.00
SAA5040	£3.50
SAA5040A	£4.40
SAA5050	£3.50
SAF1032p	£2.50
SAF1039	£2.00
SAS560	£2.00
SAS570	£2.00
SA5660	£1.00
SAS670	£1.00
SL901B	£5.00
SL918	£6.20
TA7122	£1.15
TAA320A	
TAA470	£1.50
TAA570	75p
TAA611B	£1.50
TAA621	£2.00
TAA661	£1.75
TAA641	£1.50
TA7117	50p
TA7120P	50p
TA7315AP	50p
TA7607AP	40p
TA7609P	50p
TBA120A	40p
TBA120AS	50p
TBA120SA	40p
TBA120B	40p
TBA120SB	40p
TBA120SQ	£1.00
TBA120U	75p
TBA120C	40p
TBA1441	£1.00
TBA231	75p
TBA395Q	50p
TBA396Q	£1.00
TBA396	75p
TBA4400P	£1.00
TBA4400C	£1.00
TBA480Q	£1.00
TBA510	£2.00
TBA510Q	£2.00
TBA520	£2.00
TBA530	£2.00
TBA540	£1.00
TBA550Q	£2.50
TBA560CQ	£2.00
TBA570	£1.50
TBA625	50p
TBA641	£2.00
TBA651	£2.00
TBA673	£1.00
TBA720A	£1.50
TBA750Q	£1.50
TBA780	50p
TBA800	£1.50
TBA810AS	60p
TBA810S	60p
TBA820	60p
TBA890	£1.00
TBA900	£1.50
TBA920	£1.50
TBA920Q	£1.50
TBA950	£1.50
TBA990Q	£1.00
TMS1000NL	£4.00
TMS1943	
(clockchip)	£1.00
TMS9980	£4.00
TMS9901	£1.00
TMS2716JL	£1.00
TMS3529	£1.00
TMS4014	70p
TX-012	£1.00
TMS9902	£1.20
UPD2114C 4K RAM	
400ns	75p
ULN2216	75p
SN29848	50p
SN29770BN	£1.00
SN29771BN	£1.00
SN29772BN	£1.00
SN7402N	£1
SN7472N	£1
SN74107	£1.00
SN74167	70p
SN7472N	20p
SN75108AN	£1.00
SN76001	£1.00
SN76003	£1.00
SN76013ND	£1.50
SN76018	£1.00

SN76008	£1.00
SN76023N	£1.50
SN76033	£1.50
SN76110N	£1
SN76115AN	50p
SN76131	50p
SN76141N	£1.00
SN76226	£1.00
SN76227N	60p
SN76228N	£1.00
SN76270	£1.00
SN76532N	50p
SN76544N	£2.00
SN76545	£3.50
SN76546	£1.00
SN76550	30p
SN76552	30p
SN76570	£1.00
SN76620	50p
SN76650	50p
SN76660N	40p
SN76620AN	50p
SN76666	£1.00
SN76705N	£1
SN76707N	75p
SN76708AN	75p
SN76720	£1.00
UA783P3C	40p
BT100A/02	40p
BT138/10A	70p
BT146	30p
TBA540Q	£1.50
TCA270	£1.00
TCA270Q	£1.00
TCA640	£1.00
TCA660	£1.00
TCA270S	£1.00
TCA270SQ	£1.00
TCA740	£1.00
TCA800	£2.00
TCA830	£1.00
TCEP100	£2.25
TCE120CQ	£1.00
TDA400Q	£1.00
TDA1003A	£1.00
TDA1010	£1.00
TDA1060A	£1.50
TDA1072	£1
TDA1151	30p
TDA1170	£2.00
TDA1190	£1.00
TDA1327A	£1.00
TDA1412	50p
TDA2003	£2.00
TDA2004	£2
TDA2010	£1.00
TDA2140	£3.50
TDA2522	£1.00
TDA2530	£1.50
TDA2532	£1.00
TDA2540	80p
TDA2541	£1.00
TDA2571AQ	£2.50
TDA2575A	£2.50
TDA2581	£2.50
TDA2590	£1.00
TDA2593	£1.00
TDA2560	50p
TDA2600	£5.00
TDA2611	£1.00
TDA2653	£1.00
TDA2002	£1.00
TDA2640	£2.00
TDA2680	£1.00
TDA2690	£1.00
TDA2593	£1.00
TDA3190	£1.00
TDA3500	£2.00
TDA3560	£3.50
TDA3571Q	£1.50
TDA9403	£3.00
TDA3651AQ	£3
SN74LS125AN	30p
SN74LS248	50p
SIL4516	50p
SN16861NG	50p
SN16862AN	£1.00
SN16964AN	50p
SN29764AN	£1.00
UA721	40p
UA7300	40p
RGP30G	10p
MPSA44	10p
MPSA13	10p
MJ13005	30p
MJES1T	25p
MJE340	28p
MJE660	25p
MJE661	25p
MJE3055	£1.00

MJE2801	30p
MJE2955	50p
MJE13005	30p
Sanikron Diode	
SKE2G2/04	30p

Transistors	
AC106	15p
AC121	15p
AC124	15p
AC128	15p
AC137	15p
AC151	15p
AC131	15p
AC138	15p
AC152	15p
AC153K	15p
AC142K	15p
AC169	15p
AC176	15p
AC176K	15p
AC178K	15p
AC179	15p
AC186	15p
AC187K	15p
AC188	15p
AC188K	15p
ACY21	25p
AD143	50p
AD149	50p
AD161/162	pair 40p
AF139	25p
AF181	£1.00
AF239	25p
AF367	25p
AL102	£1.75
BC161	30p
BD507	30p
BD509	30p
BD510	30p
BD517	30p
BD519	30p
BD534	30p
BD535	30p
BD544D	30p
BD562	30p
BD610	40p
BD646	50p
BD676A	30p
BD678	30p
BD681	25p
BD807	20p
BD826	20p
BD948	30p
BDX75	20p
BDX32	£1.25
BF115	20p
BF121	20p
BF127	