

RADIO & ELECTRONICS WORLD

ISSN 0262-2572

AUSTRALIA
CANADA \$2.95c
EIRE £1.31½p
NEW ZEALAND \$2.20c
HOLLAND F7.15

THE COMPLETE COMMUNICATIONS MAGAZINE

85p



Meteosat Reception: How to 'tune in' to the weather

ICOM Vs TRIO Battle of the Titans



**HIGH QUALITY
SYNTHESISER
CONTROLLER**

CIRCUIT SPECIAL
including the latest in CAD
- Circuit Modeller

PROJECTS

- Wideband LCD-DFM
- RF/RGB TV Interface
- FRG7700 Memory Expansion

FEATURES

- Optical Astronomy
- Amateur Radio World

History Repeats Itself!

Smartly bound, completely updated and revised, copies of R&EW projects.

Price
£1.20
each



We've got them covered

- The Autobridge
- Lab Quality PSU
- 2m Power Amplifier
- Multiband Up Converter
- CB Selcall
- UOSAT receiver
- MSF clock.

We've been thinking of producing reprints of the most popular R&EW projects for some time now, but wanted to present them in an attractive fashion without making them too expensive.

When we saw the new Bindit machine we knew we had the answer.

R&EW Project Reprints are bound using the Bindit machine - completely updated and revised projects, perfectly bound between attractive covers.

We think that the Bindit System is such an effective way of collating documents that we feel many offices, schools, colleges etc., might like to know more about the system. For further information fill out the coupon below and send it to **Epping Technical Associates Ltd., 94 Theydon Grove, Epping, Essex,** or circle

Make your cheques and postal orders payable to **Radio & Electronics World** clearly stating which reprints you would like (all previous articles from October issue onwards in complete form are available) and send your orders to:
R&EW Project Reprints, 200 North Service Road, Brentwood, Essex, CM14 4SG.

Please send me further details of Bindit and accessories.

Name:

Address:

Postcode:



Prices include VAT, postage and packing



ACTING EDITOR

Paul Coster

EDITORIAL ASSISTANT

Janet Capon

ART EDITOR

Sally Bennett





ADVERTISEMENT MANAGER

John White

RADIO & ELECTRONICS WORLD

JUNE 1983

CONTENTS

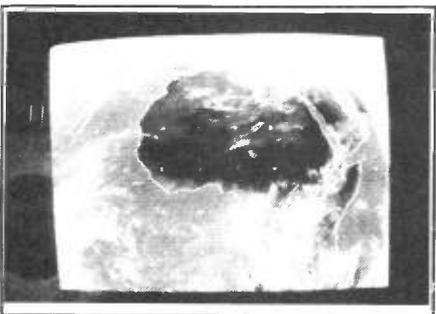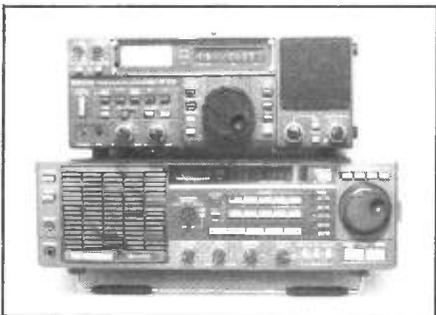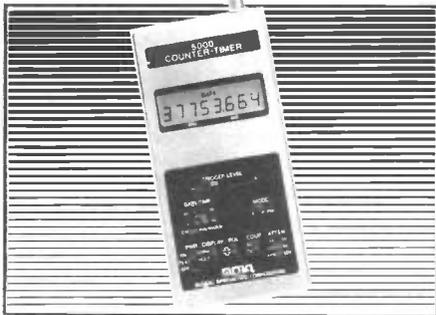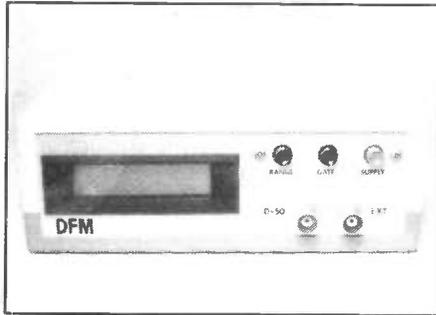

Editorial & Advertising
(0277) 213819
117a High Street,
Brentwood, Essex,
CM14 4SG.

Projects

RF/RGB TV Interface	- A switchable converter	8
Synthesiser Control System	- For 70cm and 2m bands	13
Universal Counter	- Data Brief 1	19
Wideband LCD-DFM	- Meters frequencies	26
2m Update	- More on our transverter	35
FRG7700 Memory Expansion	- Money-saving mod	36
Muting Preamplifier	- Data Brief 2	55
100W Power Amplifier II	- Constructional details	67

Features

NEC Rally	- A personal view	21
Optical Astronomy	Light in the dark	31
Zilog Z8000	- Held over from last month	39
AI File	- My fair lady?	52
Weather Satellite Reception	- An appetising introduction	57
Amateur Radio World	- AMSAT adventures	61
Data File	- A different OTA	72
Notes From The Past	- Early correspondence	80

Reviews

AMS1	- Audio measuring system	24
GSC 5000	- Latest counter/timer	42
ICR70/R2000 Receivers	- Icom or Trio?	46
Circuit Modeller	- CAD for CPM	62

News


Bulletin Board	- Hold the front page	7
Events	- Where it's at	21
Next Month's R&EW	- Order yours now	22
R&EW Book Service	- Best buys	45
Video News	- Pete's page	66
Short Wave News	- Across the waves	76
DX-TV	- Distant channels	76
New Products	- Bigger and better	82
Parts Profile	- Components catalogued	90

See page 89 for details of subscriptions and back orders.

Accounts	Jack Burrows FCA	REW	(0277) 232628
Design	Martin Sheehan	TEL	Roland Perry
& Production	Helen White		
Computing	Jonathan Burchell	Technical	(0277) 213819
Projects	Adrian Barnes	Enquiries	Keith Collins

COMPONENTS FOR COMMUNICATORS

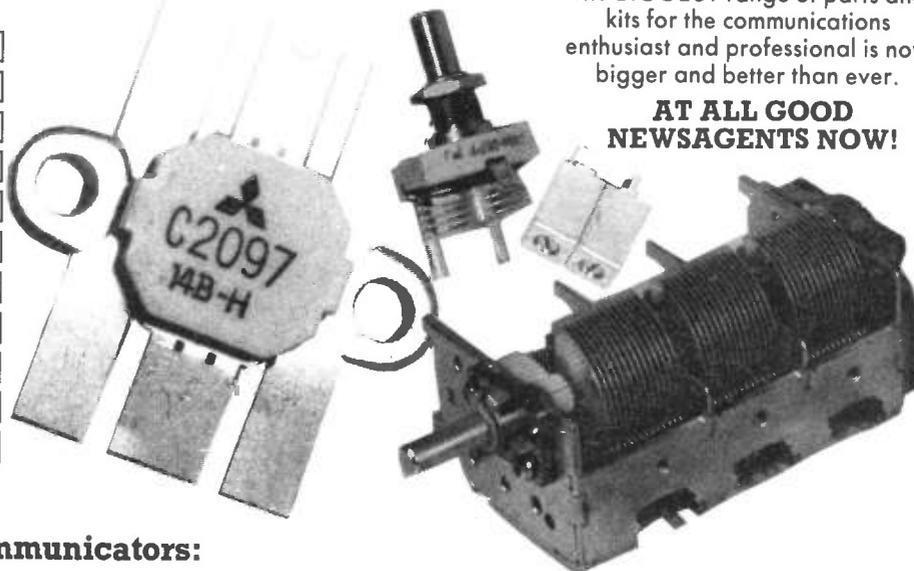- Coax Relays for RF
- Crystal Filters
- Crystals
- Ceramic Filters
- Ceramic Resonators
- Coils for RF
- Coils for IF
- Coils for Oscillators
- Transistors for RF
- MOSFETS for RF
- Connectors for RF



**ambit's
Spring Catalogue
is out (March 1st)!**

The BIGGEST range of parts and kits for the communications enthusiast and professional is now bigger and better than ever.

**AT ALL GOOD
NEWSAGENTS NOW!**

Communications for communicators:

ambit INTERNATIONAL, 200 North Service Road, Brentwood, Essex CM14 4SG

Telephone (Consumer Sales/Enquiries) 0277-230909 — Telephone (Industrial Sales/Enquiries) 0277-231616 — Telex 995194 AMBIT G
Data 24hrs (RS232/300baud) 0277-232628 — REWTEL. ● Prices exclude VAT except where otherwise shown. ● Postage and Packing 60p per pre-paid order. ● Orders submitted using Ambit Stock Codes will be processed first. ● Orders for in-stock items despatched same day (up to 4pm receipt). ● Hours — (consumer sales) 8am-7pm Mon-Sat: (Industrial) 8am-6pm (Mon-Fri). ● Retail sales 9am-6pm Mon-Sat — Industrial sales 'Take-away' by arrangement. ● Industrial accounts available on application: 2 trade, 1 bankers ref.




Richardson Electronics (Europe) Ltd.

FOR VALVES,
RF TRANSISTORS AND
SEMI-CONDUCTORS,
CALL THE REEL PEOPLE
YOUR SINGLE SOURCE
FOR AMERICAN VALVES

BRANDS BY ALL LEADING
MANUFACTURERS

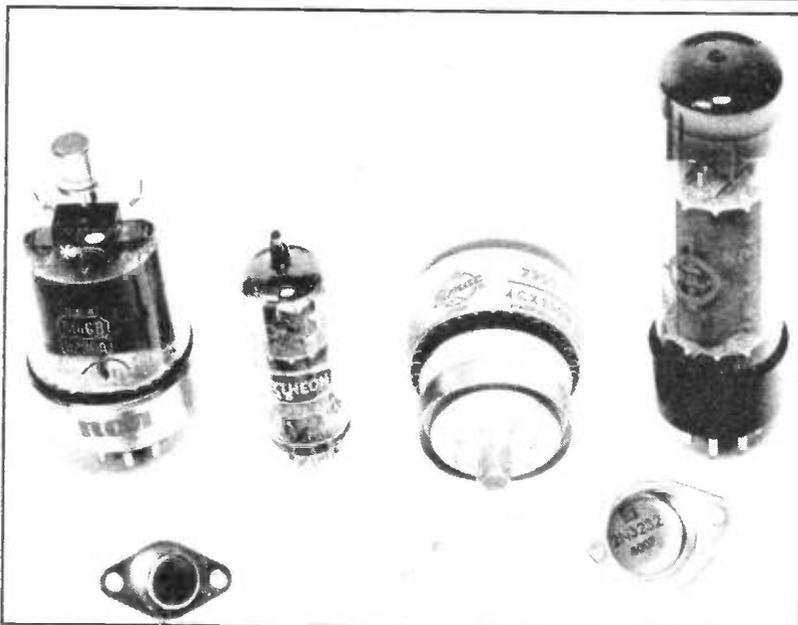Richardson Electronics (Europe), Ltd.
Dean Road, Outer Circle Road
Industrial Estate
Lincoln, England LN2 4DV
Telephone: 0522-42631
Telex: 56175 REEL UK



Write, call or Telex Allan McCrone for further details.

Northampton Communications

6MTR - 2MTR - 70CM CONVERSIONS//TRANSVERTERS FOR CB RADIOS

2 MTR TRANSVERTER KIT	£ 68.95
RX UNIT KIT ONLY	£ 38.95
HARDWARE FOR ABOVE (i.e: case, switches, etc)	£ 9.95
COMPLETE ASSEMBLED UNIT	£ 98.95
TX UNIT ONLY FOR RX UNIT	£ 30.00
6 MTR CONVERSION KIT	£ 59.80
ASSEMBLED UNIT inc. RADIO	£129.95
70 CM RX UNIT KIT	£ 44.95
70 CM TX UNIT KIT	£ 48.95

Available soon repeater shift for all kits.
Above equipment works on all modes ie: AM,FM,SSB, & CW.

HOT LINE PROBLEM SERVICE (Technical)
Northampton (0604) 38202

TUESDAY & THURSDAY 14.00 hrs. to 17.00 hrs.
ASK FOR: EVAN G8 KHC or COLLIN G3 VMU


Trade enquiries by headed letter only please
Attn. G. Austin G6 NYH.

All TX Kits above are sold subject to purchaser holding
current Amateur Radio TX Licence.

Northampton Communications Limited
76 Earl Street, Northampton.
Telephone: (0604) 33936

ELECTRONI-KIT

FX-COMPUTER

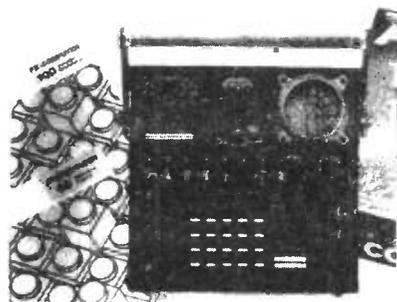

Teach-Yourself Computer and Electronics Construction Kit

A complete introduction to the "How, Why and What" of Computers and Electronics in the most practical way ever devised

THE KIT IS BATTERY-OPERATED AND COMPLETELY SELF-CONTAINED. NO TELEVISION OR OTHER EQUIPMENT IS REQUIRED. VERY EXTENSIVE MANUALS ARE INCLUDED

Ministry of Science and Technology, Japan —
Prize Winning Product

The **FX-COMPUTER** is the ideal introduction to the study and understanding of computers and electronics. The kit offers remarkable versatility because the components are interchangeable and circuits are constructed by simply plugging specified components into the board provided in accordance with the instruction manuals. You quickly understand the principles involved and new circuits can be easily devised, built and dismantled. No soldering or wiring is involved, no tools are required; the components themselves complete the circuits.

No previous knowledge is required — very extensive educational manuals have been provided by English experts in computers and electronics. Working through the manuals you will soon be able to write programmes and "run" them and understand how computers work.

The following are just a few of the programmes in the Computer Manual (there are too many to list here) and also a few of the projects in the Electronics Manual:

How to instruct the Computer and Store Information into Memories Use of different Instructions and Programming Techniques. Adding, subtracting, multiplying, dividing, averaging, counting down, etc. etc. in Decimal and Hexadecimal. Converting Hexadecimal to Decimal, storing Random Numbers. Games: Tennis, Catch-the-Rat, Gun Fight, Slot Machine, etc. Using the Computer as a Musical Organ, storing and playing back tunes, etc. **OVER 100 PROGRAMMES SHOWN IN THE COMPUTER MANUAL PLUS EXPLANATIONS AND DEMONSTRATIONS OF ALL TECHNICAL TERMINOLOGY.**

Electronic Components and How they Work batteries, conductors, resistors, capacitors, diodes, transistors, lamps, photo electric devices (CdS cell is included in the kit), oscillators, burglar alarms, control systems, organ, lie detector, etc., etc. **OVER 65 PRACTICAL WORKING PROJECTS SHOWN IN THE ELECTRONICS MANUAL.**

All this is in ONE kit, costing about the same as the cheapest "Basic" ordinary Computer

The price is only £69.95 plus £3.00 P&P
(overseas rates quoted on request)

TRADE & EDUCATIONAL ENQUIRIES WELCOMED

Send cheque/PO/Access/Barclaycard to
DEPT. REF. Electroni-Kit Ltd

It's not JUST a computer!

**ELECTRONI-KIT LTD.
388 ST. JOHN STREET
LONDON, EC1V 4NN (01-278 0109)**



Constructor Series Speakers

IT'S
SO EASY

Have fun, save money, building a Kef design with a Wilmslow Audio CS Total kit.

No electronic or woodworking knowledge necessary and the end result is a proven top-quality design that you'll be proud of.

Each kit contains all cabinet components, accurately machined for easy assembly, speaker drive units, crossovers, wadding, grille fabric, terminals, nuts, bolts, etc.

The cabinets can be painted or stained or finished with iron-on veneer or self adhesive woodgrain vinyl.

Easy foolproof assembly instructions supplied. Set of constructor leaflets sent free on receipt of large S.A.E.

Prices: CS1 (As 101)	£110 pr. inc. VAT, plus carr./ins. £ 5.50
CS1A (simplified LS3/5A)	£103 pr. inc. VAT, plus carr./ins. £ 5.50
CS3 (as 103.2)	£129 pr. inc. VAT, plus carr./ins. £10.00
CS5 (as Carlton II)	£192 pr. inc. VAT, plus carr./ins. £15.00
CS7 (as Cantata)	£250 pr. inc. VAT, plus carr./ins. £18.00



0625 529599

35/39 Church Street, Wilmslow, Cheshire SK9 1AS



Lightning service on telephoned credit card orders!



QUALITY CRYSTALS—AT COMPETITIVE PRICES. POPULAR FREQUENCIES IN STOCK

2 METRE STOCK CRYSTALS. Price £1.96 for one crystal. £1.74/crystal when two or more purchased

	HC6/U	HC6/U	HC25/U	HC25/U	HC25/U	HC6 & 25/U
	30pF TX	30pF TX	30pF and 40pF RX	20pF and 30pF RX	25pF and 20pF TX	SR RX
R0	4-0277	8-0555	12-0833	14-9888	18-1250	44-9666
R1	4-0284	8-0569	12-0854	14-9916	18-1281	44-9750
R2	4-0291	8-0583	12-0875	14-9944	18-1312	44-9833
R3	4-0298	8-0597	12-0896	14-9972	18-1342	44-9916
R4	4-0305	8-0611	12-0916	15-0000	18-1376	45-0000
R5	4-0312	8-0625	12-0937	15-0027	18-1406	45-0083
R6	4-0319	8-0638	12-0958	15-0055	18-1437	45-0166
R7	4-0326	8-0652	12-0979	15-0083	18-1468	45-0250
S8	—	—	12-1000	14-9444	18-1500	44-8333*
S9	—	—	12-1020	14-9472	18-1531	44-8416*
S10	—	—	12-1041	14-9500	18-1562	44-8500*
S11	4-0354	8-0708	12-1062	14-9572	18-1593	44-8583
S12	—	—	12-1083	14-9555	18-1625	44-8666*
S13	—	—	12-1104	14-9583	18-1656	44-8750*
S14	—	—	12-1125	14-9611	18-1687	44-8833*
S15	—	—	12-1145	14-9638	18-1718	44-8916*
S16	—	—	12-1167	14-9667	18-1750	44-9000*
S17	—	—	12-1187	14-9694	18-1781	44-9083*
S18	—	—	12-1208	14-9722	18-1812	44-9166*
S19	—	—	12-1229	14-9750	18-1843	44-9250*
S20	4-0416	8-0833	12-1250	14-9777	18-1875	44-9333*
S21	4-0423	8-0847	12-1270	14-9805	18-1906	44-9416
S22	4-0430	8-0861	12-1291	14-9833	18-1937	44-9500
S23	4-0437	8-0875	12-1312	14-9861	18-1968	44-9583

SR = Series resonance *HC25 only

The above list includes crystals for the following equipment R0 to R7 and S8 to S23 for following: Belcom FS1007, FDK TM56, Multi-11 Quartz 16 and Multi 7, Icom IC2F, 21, 22A and 215, Trio Kenwood 2200, 7200, Uniden 2030 and Yaesu FT2FB, FT2 Auto, FT224, FT223 and FT202. **4 METRE CRYSTALS** for 70-26MHz in HC6/U at £2.25. TX 8-78250MHz. RX 6-74668 or 29-78MHz in stock.

70cm CRYSTALS in stock 8-0222 in HC6 £1.85. Pye Pocketfone PF1, PF2, PF70 and Wood and Douglas £4.50 a pair or TX £2.25, RX £2.50, SU8(433-2) RB0, RB2, RB4, RB6, RB10, RB11, RB13, RB14 and RB15.

CONVERTER CRYSTALS in HC18/U at £2.95. In stock 22-000, 38-666, 42-000, 70-000, 96-000, 101-000, 101-500, 105-666 and 116-000MHz.

TONE BURST AND I.F. CRYSTALS in HC18/U at £2.25 in stock. 7-168MHz for 1750Hz and 10-245MHz for 10-7MHz I.F.'s

FREQUENCY STANDARDS in stock £2.75. HC6-200kHz, 455kHz, 1000kHz, 3-500kHz, 5-000MHz and 10-000MHz. HC13 100kHz. HC18 1000kHz. 7-000MHz, 10-700MHz, 48-000MHz and 100-000MHz.

MADE TO ORDER CRYSTALS

Fundamentals Frequency range	Price	Overtone Frequency range	Price
6 to 30kHz	£23.00	3rd OVT	21-00 to 65-00MHz £4.55
30 to 80kHz	£15.00	5th OVT	60-00 to 110-00MHz £5.10
80 to 159kHz	£10.98	5th OVT	110-00 to 125-00MHz £7.00
160 to 999kHz	£7.96	5th, 7th & 9th OVT	125-00 to 150-00MHz £8.00
1 to 1-5MHz	£10.76		150-00 to 250-00MHz £9.60
1.5 to 2.5MHz	£5.08		
2.5 to 4-0MHz	£4.76	Delivery	2-0 to 125-0MHz 2 to 3 weeks
21 to 25MHz	£4.55		1-0 to 2-0MHz 3 to 4 weeks
25 to 30MHz	£6.50		Other frequencies 6 to 8 weeks

Unless otherwise requested fundamentals will be supplied for 30pf load capacitance and overtones for series resonant operation.

HOLDERS:—PLEASE SPECIFY WHEN ORDERING—else HC25/U supplied for XTLS above 3MHz. HC13/U 6-200kHz. HC6/U & HC33/U 170kHz-170MHz. HC18/U & HC25/U 2-250MHz

DISCOUNTS: The above prices are for small quantities, price on application for 10+ units to same frequency/spec. or bulk purchases of mixed frequencies. We supply FREE xtals for use in UK repeaters.

COMMERCIAL CRYSTALS: available on fast delivery and at competitive prices. Please send for list stating interests.

EMERGENCY SERVICE: for XTALS 1 to 125MHz. The surcharges apply to each crystal not each order and are subject to VAT. Days refer to working days. 4 days +£12, 6 days +£7, 8 days +£5, 13 days +£3.

CRYSTALS-SOCKETS HC6 & HC25 £0.20 each. Minimum order charge £1.50

TERMS: Cash with order post Inc. to UK Ireland. Cheques & P.O.'s to QSL Ltd Bank drafts in pounds sterling

A stamped addressed envelope with ALL enquiries please.

PRICES ARE EX VAT. PLEASE ADD 15%

Telephone: 01-690 4889 24Hr Ansafone: Erith (03224) 30830
 Telex: 8813271 GECOMS—G (Attention QUARTSLAB)
 Cables: QUARTSLAB, London




QuartSlab
 MARKETING LTD
 P.O. Box 19
 Erith Kent DAB 1LH

Now Available the brand new **1983** edition of the

WORLD RADIO TV HANDBOOK

(37th EDITION)

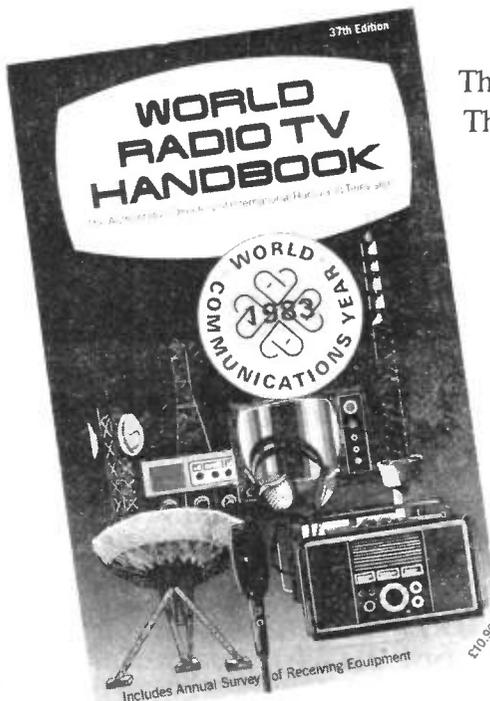

The *only* authoritative directory of International Broadcasting!
 The standard reference of DXer's, SWL's and professionals!

- ☆ Special articles will include:
 - ★ Larry Magne's in depth tests on latest SW receivers, including some brand new models.
 - ★ Top U.S. DXer Jerry Berg gives an experienced reader's views on using WRTH.
 - ★ Plus various stories and features of interest to listeners around the world.
- ☆ Completely updated reference section with frequencies, times languages, addresses, and details of all known SW, and most MW stations.
- ☆ UK price only £10.95 (Please add £1 if to be sent by post. Please allow 14 days for delivery).

☆ Listing by frequency of the worlds SW/MW/LW stations, and *essential* information for the active listener.

W.R.T.H. will be published 1st February, 1983
 Available from your bookseller or direct from:

UK TRADE, Fountain Press, 65, Victoria Street, Windsor, Berkshire, Windsor: 56959

BULLETIN BOARD

Visible Agreement

Britain's position as a world leader in developing optical fibre communications has been given a further boost by agreements signed towards the end of March under which British Telecom will exchange its expertise with Standard Telephones and Cables (STC) to benefit telephone users making international calls.

STC will pay for research work carried out in British Telecom's Research Laboratories at Martlesham, Suffolk, which will also supply the company with special microchips.

For some years, British Telecom and STC have been working on agreed complementary research programmes concerned with the stringent requirements of undersea submarine cable systems. Now that commercial optical systems are being developed, these co-operative programmes are to be formalised.

There are two agreements, both relating to optical fibre communications used in the undersea cables which will span the world's oceans.

In one, British Telecom and STC will share the results of their research work applicable to optical submarine cable systems.

This will help to put STC — Britain's only firm making submarine cable systems — into a strong competitive position in the world's markets. And it will mean rapid commercial application for Telecom's investment in optical research.

In the other agreement, British Telecom's research laboratories will supply to STC high-reliability, long life silicon integrated circuit chips for use in the underwater electronic equipment associated with the cable.

'Slovak News


The Czechoslovak five-year industrial plan for 1981 to 1985 emphasizes the further development of electrical engineering and envisages a 40 to 50 per cent increase in production. The electrical engineering industry is to create conditions for increasing the export capacity of Czechoslovak engineering and other products, for reducing import needs, and for much wider international division of labour, especially between the socialist countries.

★ ★ ★ Nota Bene ★ ★ ★

Scanning through the industrial press, this news item from 'Micro Bulletin' caught our eye — probably it had something to do with the title: "Zilog sues Nippon Electric".

NEC must be beginning to wish it had never heard of the Z80: David Shirley of Computer Information Centre relates that his US partner, NNC Electronics, which supplies CiC with processor boards, took a trial consignment of 300 NEC "Z80"s, some of which were to go into boards for the CiC Executive 30. The chips seemed OK until the firms switched to faster, 120 nanosecond access memory, whereupon they "went haywire". The memory supplier insisted that the memory worked fine with other Z80s: the fault had to be in the CPU. Exhaustive logic analysis by a customer showed the chips some 20% below spec, with one or two serious logic faults — so the customer complained bitterly to Zilog. Zilog disowned the chips — but recognised the bugs as ones which had appeared in an interim design between the Z80 and the Z80A: now Zilog has a strong suspicion just which blueprints NEC got hold of. "What a wonderful story!"

SNIPPETS

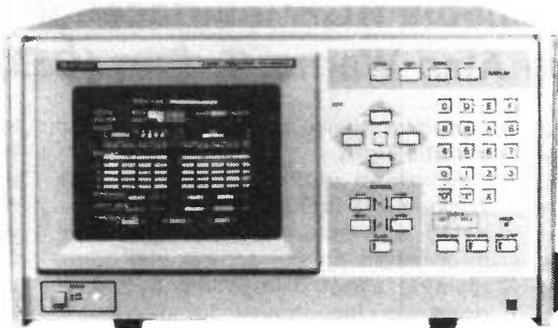

WE At National...

Wessex Electronics Ltd of Bristol has been appointed by National Panasonic (UK) Ltd to market National measuring and testing equipment. Among the products Wessex will be distributing is a 20MHz, 32 channel logic analyser. The VP.3620A is a dedicated unit catering to a wide range of industrial needs. It contains a logic state analysing function for self-contained microprocessor operation analysis and a logic timing function for the evaluation of peripheral operations. With its multifunction capability, National's logic analyser is also able to display the traced data in disassembled mnemonic mode corresponding to each microprocessor in use.

Marconi Mobiles

Marconi Mobile Radio has received another order from the British Home Office for the 770H base station. 65 sets are to be supplied, bringing total Home Office orders for this equipment to more than £250,000.

Centronics For Atari

Centronics Data Computer have recently supplied six thousand model 739 mini printers to ATARI. The order was placed on the basis of an immediate requirement that could not be met by any other printer supplier.

The Centronics Model 739 is a highly reliable low cost dot matrix printer providing extensive paper handling capabilities as well as near letter quality proportional printing. It is extremely rugged, and can print true lower case descending characters, underlines and high resolution graphics.

Distributor Of '82

Texas Instruments has named Macro as its Distributor of the Year for 1982. Despite already being TI's biggest distributor, Macro increased its TI business by some 55%. The company has been TI's biggest distributor for nine years, and is the largest distributor of TI semiconductor components in Europe.

Harris And Tex

Texas Instruments and Harris Corporation have entered into an alternative sourcing agreement covering the design, manufacturing and marketing of gate array and standard cell semi-custom circuits with a standard user-friendly design interface.

DEC 1000

Just three years after the start of operations, Digital Equipment's Remote Diagnosis Centre in Basingstoke has announced its 10000th Customer as Glasgow Royal Infirmary, in the eastern district of the Greater Glasgow Health Board (GGHB).

The biochemistry department of Glasgow Royal infirmary has a PDP-11/44 system which has been in use for nearly two years. This succeeded a PDP-11/34 originally installed in 1977.


The department use the PDP-11/44 for data management and collating results from analyses performed on (primarily) blood samples.

Telephones

Explained—by TI?

Alexander Graham Bell described it in the late 1870s as "this grand system, whereby a man in one part of the country may communicate by word of mouth with another in a distant place". Telephone communication, a century old, is now — with digitisation — moving into its second major phase of development.

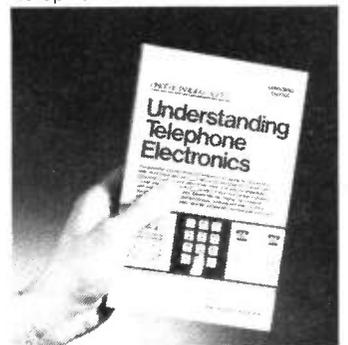"Understanding Telephone Electronics" takes the reader step-by-step from the simplest explanation of telephonic principles through to an intermediate level of telecomms learning. The book covers the technologies incorporated in dialling, ringing, transmission, signalling, switching, digital techniques, modems and cordless telephones.





RF/RGB TV INTERFACE

**A single board switchable RGB interface for the Ferguson TX9.
Design by Alan Warne, T. Eng (CEI) FSERT.**

In the January **R&EW**, we presented a method for converting domestic televisions into dedicated RGB monitors, enabling a higher quality display, or colour graphics. To obtain the best possible bandwidth, the signals were applied via a set of amplifiers to the cathodes of the colour display tube, and the preceding tuner, SAW and video amplifier were removed. The author's original intention was to manufacture a monitor for RGB external displays only, since to incorporate off-air television signals would have re-

quired extensive switching and other modifications.

Following publication of that first conversion, the designer was inundated with letters requesting further information on the project and complaining about dismantling part of a good working receiver for modification. As one letter stated "I can convince the wife and family to have a second colour television for computing, so long as they can watch their television programmes as well!"

The design work for that unit was

based on the earlier TX9 chassis, type PC1001. Since that time, two further updates have taken place — the PC1040 and, latest in the line, the PC1044 which uses a switched mode power supply. Both of the later versions have facilities for adding teletext, since they employ the Mullard TDA3560 luma chroma processor with separate data inputs.

It is a well known fact that PAL signal decoding reduces the video bandwidth to less than 6MHz in a standard television receiver, whereas the standard television tube can produce signals with bandwidths greater than 6MHz depending on the type of tube. This is the reason better quality pictures are produced with direct RGB rather than by using the PAL decoder.

Design

Retaining the TDA3560 allows PAL decoding to be carried out on the incoming television signal, but further RGB signals are applied to the IC, superimposed over the off-air picture (such as Teletext). A further facility exists so that incoming signals to the IC may be disabled and only RGB text displayed. In this mode the RGB signals pass in and out of the IC with negligible bandwidth limitation, but can be switched between off-air pro-

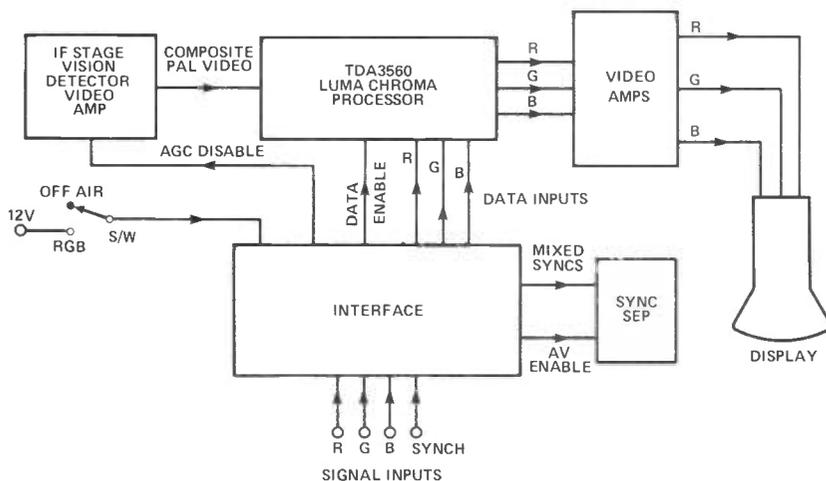


Figure 1. Block diagram showing connections for the interface.

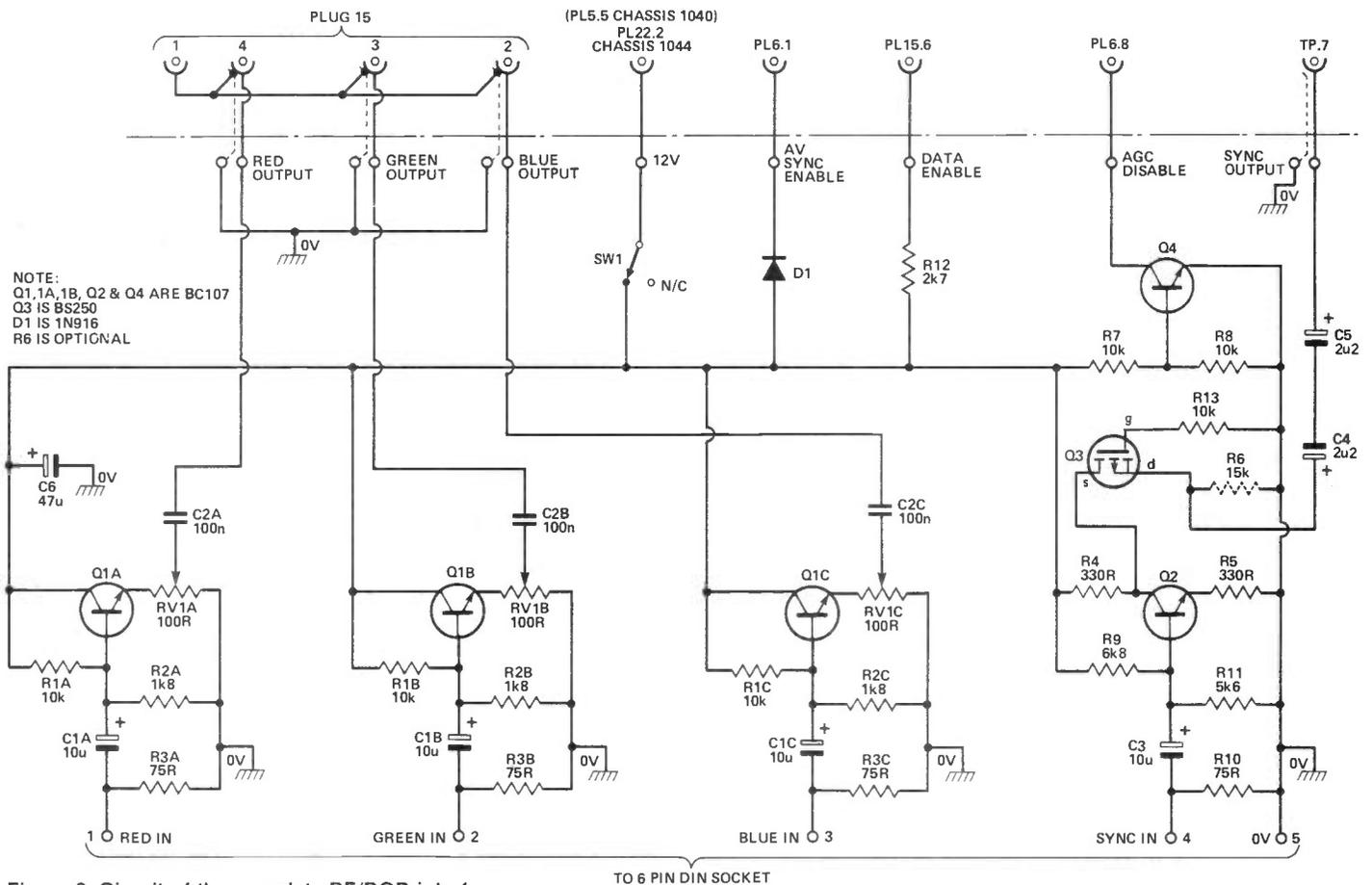


Figure 2. Circuit of the complete RF/RGB interface.

grammes or RGB inputs by controlling the data enable pin. As shown in Fig. 1, the TDA3560 will allow external RGB signals from Teletext or Viewdata equipment, but can also accept external data from computers if interfaced correctly. At the push of a switch, off-air TV programmes or external data can be displayed.

The chassis compatible with our switched RGB can be identified by the type of luma chroma IC which is located in the centre of the printed board under the neck of the CRT. Signals from most computers have a video signal amplitude of 0.7 volts peak-to-peak Red, Green and Blue. However, mixed sync signals are 2 volts peak-to-peak negative going, and require 75R termination at the monitor input. Between these, the TDA3560 will accept direct RGB signals at 1 volt peak-to-peak at a maximum input impedance of 150R.

Construction

All components selected for the interface are mounted on a single-sided PCB. Input signals may be connected via BNC plugs and sockets, keeping the input leads as short as possible. Alternatively, connections are made using a 6-pin DIN plug and socket —

Circuit Description

The interface consists of three identical emitter follower stages for Red, Green and Blue Q1 A, B and C. Each stage is fitted with a preset emitter resistor for setting up signal levels RV1 A, B and C (Fig. 2).

When using data inputs on the TDA3560, the receiver contrast control is non-operative and emitter preset controls are adjusted to give a contrast level which is compatible with off-air pictures when the receiver is switched over. Mixed synchronising signals are connected to an inverter stage, Q2, to give a positive-going output. A VMOS FET Q3 couples these signals via C4 and C5 to the TX9 sync input. When TV is selected Q3 is switched off, isolating computer

syncs from television syncs. The data enable pin on the TDA3560 requires a high to enable, which is given by R12. D3 then switches the TX9 sync separator into AV sync mode to improve the sync performance.

It was found in practice that when data enable had been selected, spurious signals from off-air programmes were visible at low level. This was unacceptable, and Q4 is used as a switch to short out the AGC line and prevent it. A 12 volt power source is required to power the board and this supply is readily available from the TV chassis via an on/off switch. When voltage is applied, off-air programmes are disabled and data and sync inputs are enabled.


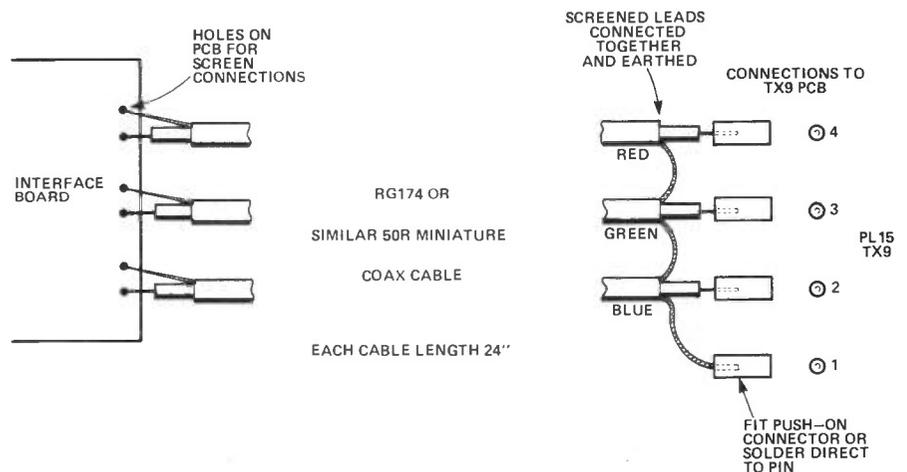


Figure 3. Wiring the interface to the TX9 PCB.

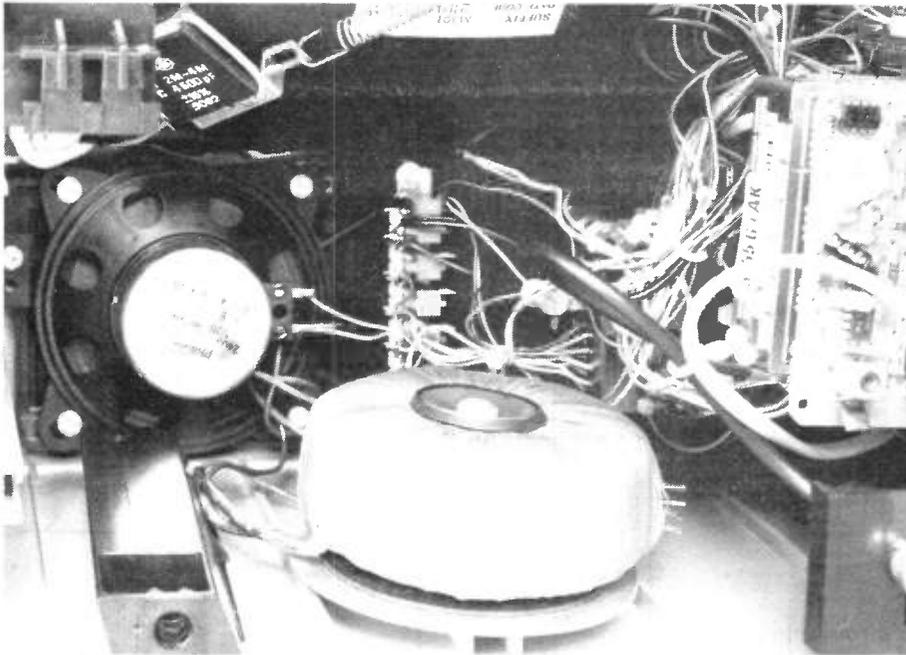

Positions for the board and transformer.


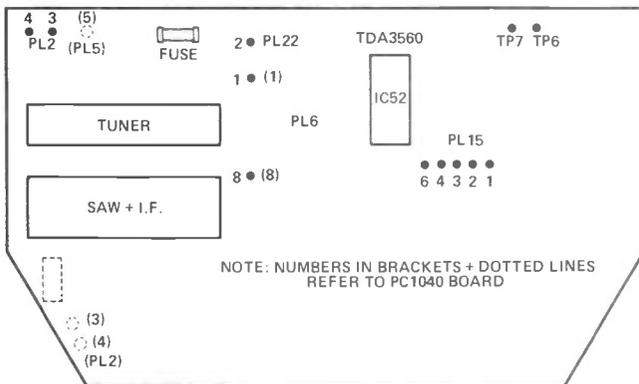


Figure 4. Connections on the TX9 printed boards.

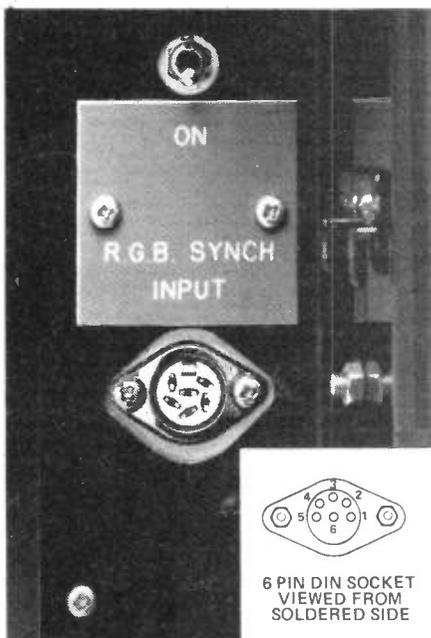

A small panel is fitted below the on/off switch. The inset gives pin designations for the DIN socket.

the popular home computer's RGB connector.

Red, Green, Blue and sync output signals are connected to the receiver chassis using miniature co-axial cable (RG174 50R), which should have the screened outers earthed at both the interface and chassis ends (Fig. 3). Other interconnecting leads must be multi-stranded conductors (16/0.2mm), PVC covered. Figure 4 indicates the connecting points when using either PC1040 or PC1044 printed board. All connections to the PC1044 are push on, enabling the interface to be fitted within minutes. When using PC1040, with the exception of +12 volt, all connections are push on. The 12 volt lead does not have a convenient pin available and must be soldered into PL5.5 with the existing lead still in place. The PCB is mounted together with the DIN socket and on/off switch onto the aluminium side panel. An isolated mains supply must be used

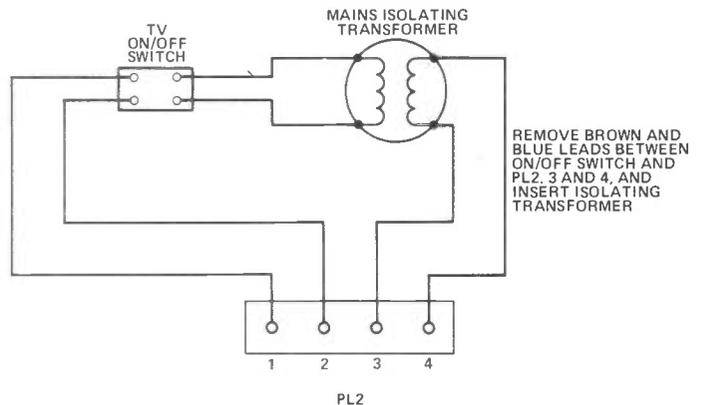


Figure 5. The TV on/off switch can be used to supply the isolating transformer.

PARTS LIST

Resistors

R1A,B,C,7,8 10k
R2A,B,C 1k8
R3A,B,C,10 75R
R4,5 330R
R6 (optional) 15k
R9 6k8
R11 5k6
R12 2k7

Potentiometers

RV1,2,3 100R min preset

Capacitors

C1A,B,C,3 10u 25V tant

C2A,B,C 100n 50V ceramic
C4,5 2u2 25V tant
C6 47u 25V tant

Semiconductors

D1 1N4148
Q1A,B,C,2 BC107
Q3 BS250

Miscellaneous

SK1 6 pin DIN socket
T1 see text
SW1 SPST toggle (if required)
PCB, RG174 50R coaxial cable

A complete kit of parts, consisting of PCB, components, aluminium PCB mounting bracket, 14" transformer plate and bolt, DIN socket switch and cables (does not include mains isolating transformer) is available for £36.00 including post & packing. PCB's can be bought separately for £5.00 inclusive. Orders cheques and enquiries to A V Warne Electronics, 113 Queens Road, Vicars Cross, Chester.

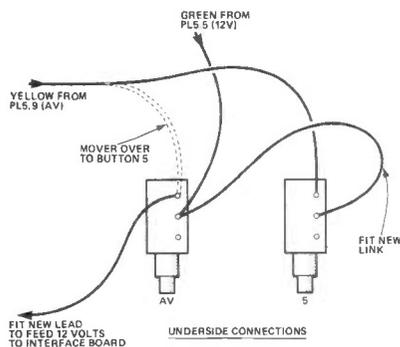


Figure 6. Alternative switching between RF and RGB using the AV button.


with this modification and a toroidal transformer is best suited for the application. When converting a 14" receiver, an 80 VA transformer is suitable and can be fixed with a single bolt to another aluminium plate. Alternatively, if a remote PCB is already in use, the transformer may be mounted directly on the rear. When a 20" or 22" large screen set is converted, a 120 VA transformer should be used and will fit on a right angled bracket behind the tuner draw.

All interconnecting cables from the interface board, including co-ax, should be 24" long.

An alternative for switching TV/RGB can be the channel select button marked "AV", which is neater and cheaper than using a separate switch on the rear panel. **Figure 6** shows how the present AV facility is moved to the next button, to retain AV when using a video recorder, and the now spare button relabelled and used for RGB switching.

Testing

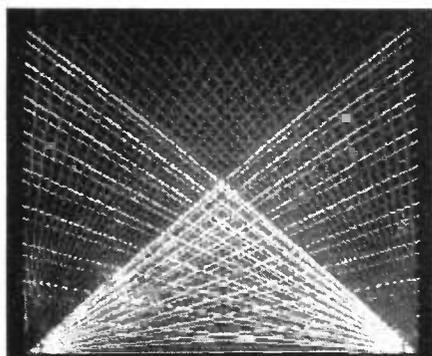Linear signals were fed to the RGB input and a greyscale wedge displayed using a Philips pattern generator and RGB decoder. Each preset on the



Demonstration of the improved definition provided by RGB inputs.

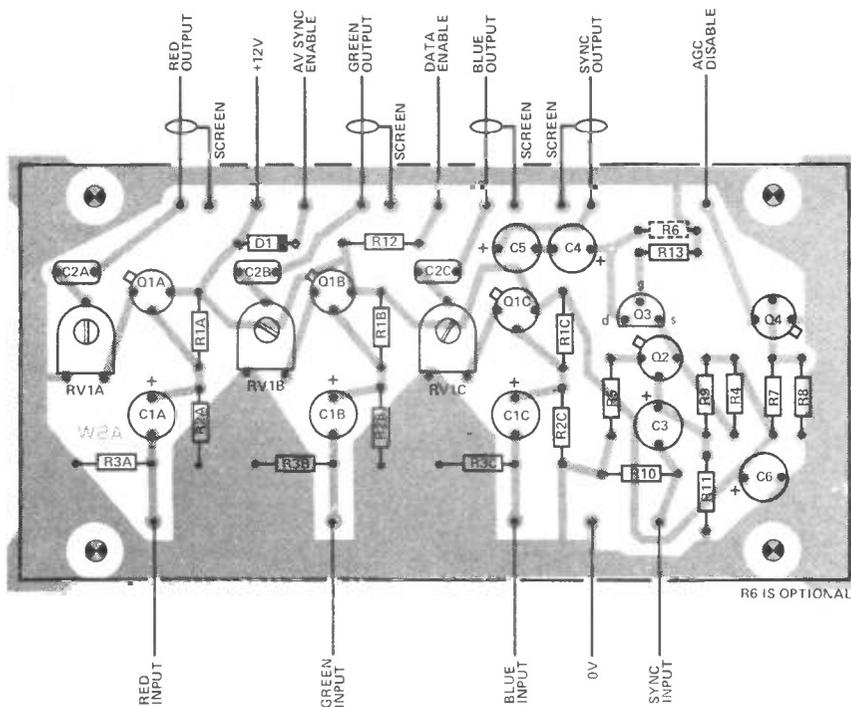


Figure 7a. Component overlay of the completed PCB.

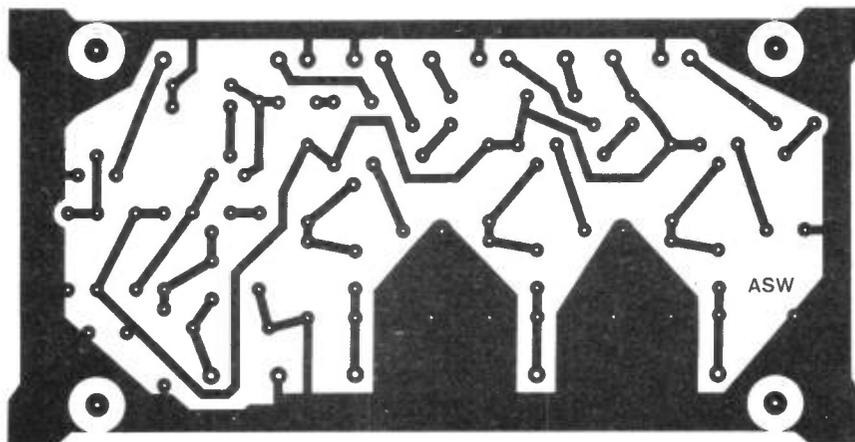


Figure 7b. Foilside of the above PCB overlay.

interface board RV1 A, B and C was set to provide a good greyscale with adequate contrast compatibility when switching over to TV. When using a computer to drive the interface, signal levels were higher at about 4 volts TTL and each preset was turned down by a small proportion giving excellent results.

Conclusion

Many home and commercially manufactured computers offer direct RGB output signals as well as UHF signals, but there is no comparison between the

two methods of interface. Direct RGB is superior and must be employed by the more discerning user who needs a good quality display at low cost. Alternative interfaces may be produced using opto-isolating techniques, which avoid the use of a mains isolating transformer, but due to the bandwidth limitations of devices currently available and the manner in which they operate, problems arise in producing a linear transfer of data. The method utilised in the present design, avoids such problems neatly and reliably.

■ R&EW

Amateur RADIO

For all two-way radio enthusiasts

AMATEUR RADIO MAGAZINE IS NOW AVAILABLE ON SUBSCRIPTION—PHONE KAREN SMITH AT BICESTER (08692) 44517 FOR DETAILS

Amateur RADIO ONLY 90^p

What Radio? Price chart

RSGB's David Evans questioned

Pass the RAE

Transverters vs black boxes

Centre-fed aerials explained



Two top multimodes - tested by Angus McKenzie G3 OSS

THE SPECIALIST MAGAZINE FOR ALL RADIO AMATEURS—FEATURING THE BEST IN TWO-WAY RADIO EVERY MONTH.

★ REVIEWS

★ NEWS & REPORTS

★ EQUIPMENT ANALYSIS

★ CONSTRUCTION PROJECTS

★ SHORTWAVE COLUMN

★ PASSING THE RAE

★ SPECIAL ARTICLES ON ANTENNAE PROPAGATION ETC

★ CONTRIBUTORS

INCLUDE ANGUS MCKENZIE · REV


GEORGE DOBBS · JOHN HEYS · PAT

HAWKER · AND NIGEL GRESLEY

PLUS

FREE CLASSIFIED ADS!



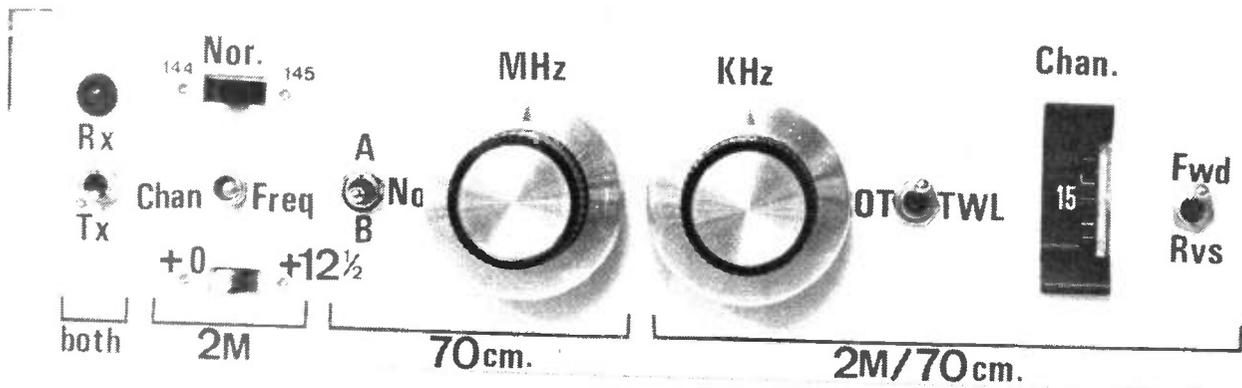

SYNTHESIZER CONTROL SYSTEM

- Operates on 70cm and 2m bands.
- 8-digit direct drive 7 segment LCD display
- Motorola 145151 synthesizer running at 68-74MHz (70cm) and 44-49MHz (2m).
- ROM code converter.
- 400 channel capacity.
- 25kHz spacing

A comprehensive transmitter /receiver synthesizer system for the 70cm and 2m bands.

Design by Ian Chapman.

Our synthesizer was developed when it became apparent that the FM activity on the 70cm band (in the London area) had increased to a point where the channel capacity of the author's rig could no longer meet operational needs. So, rather than invest several hundred pounds in a new rig, an interesting project would be the conversion of the set to synthesizer operation, thereby obtaining up to 400 channels at 25kHz spacing.

Instead of generating a basic frequency at 12 to 14MHz and employing a series of frequency multipliers for both transmitter and receiver, it was felt better to opt for the highest practicable VCO frequency, consistent with ease of conversion. After studying the circuitry of the mobile, it was decided that the VCO should operate between 68 and 74MHz, thus requiring a multiplication of six times in both the transmitter and receiver, and making the modification of the two multiplier units relatively straightforward.

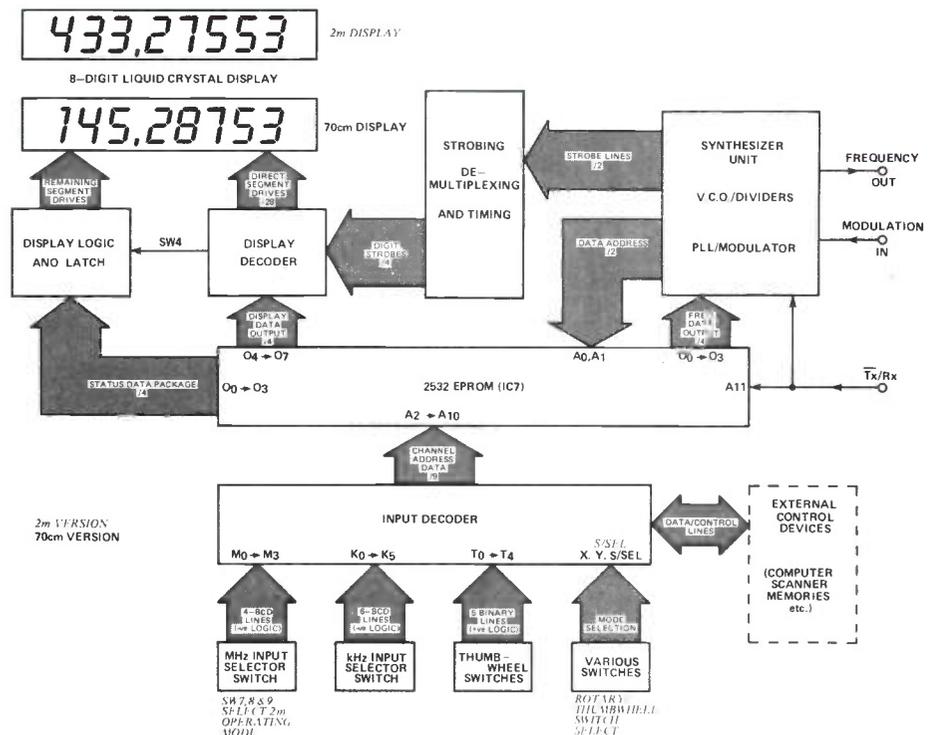


Figure 1: Synthesizer Control block diagram.

SYNTHESIZER CONTROL

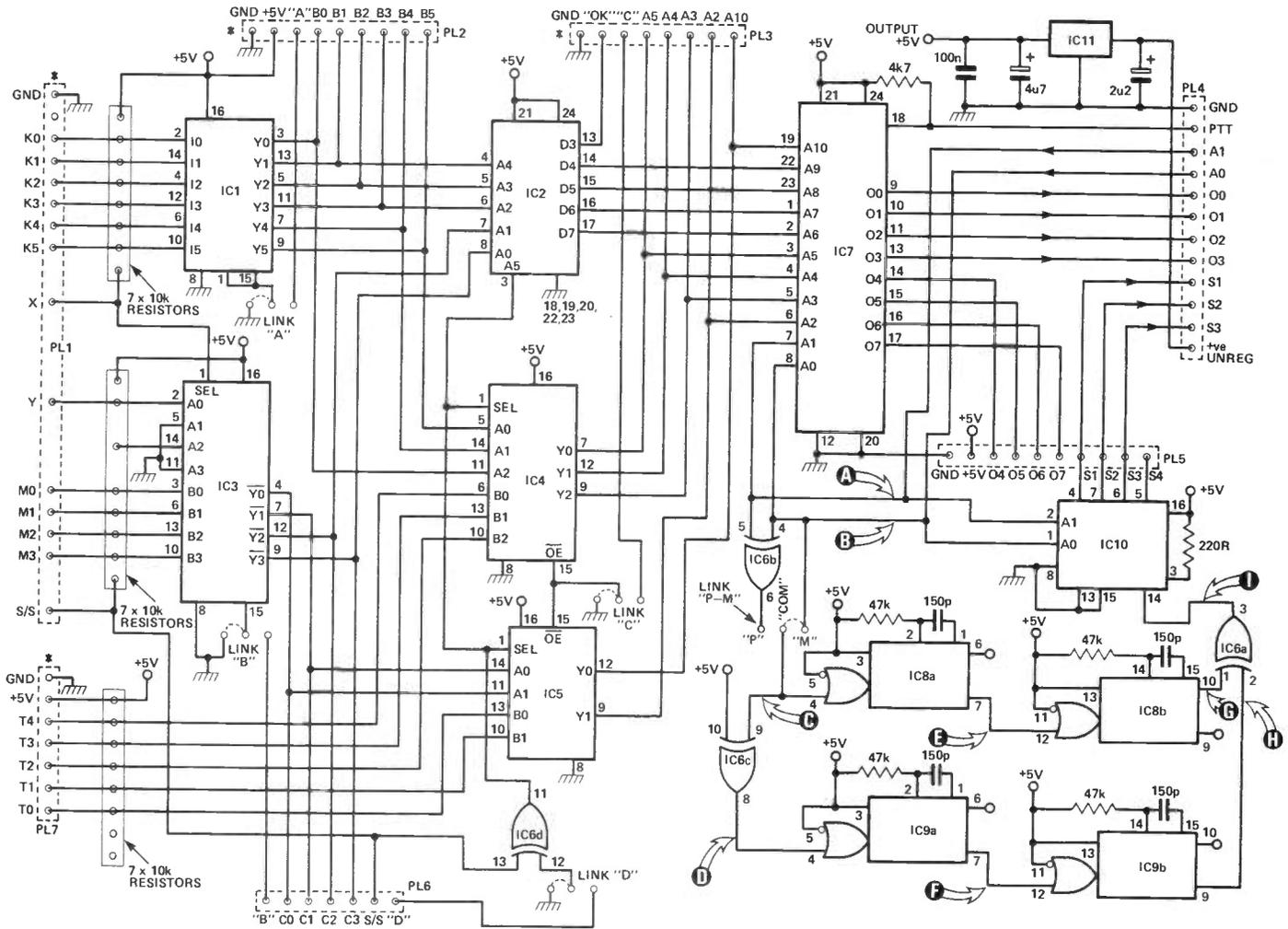


Figure 2: Synthesizer Control circuit diagram.

NOTE:
 IC11 IS 74LS366
 IC2 IS 2716
 IC3 IS 74LS258
 IC4 & 5 ARE 74LS257
 IC6 IS 74LS86
 IC7 IS 2532
 IC8 & 9 ARE 4528
 IC10 IS 74LS256
 IC11 IS 7805

Circuit Description

Referring to the block diagram shown in Fig. 1 and the circuit diagram in Fig. 2, it can be seen that the 2532 data outputs are used by two devices — the synthesizer unit, and the display. Thus the lower 4 bits of the output (00 — 03) are dedicated to outputting the data for synthesizer frequency control, whilst the upper 4 bits (04 — 07) carry the data outputs for the corresponding display decoder.

The 2532 is addressed by three binary information sources. The Motorola synthesizer IC requires 12 bits of binary data, and these are clocked out of the EPROM as three 4 bit chunks using two strobe lines holding a binary address, which are connected to the A0 and A1 inputs of the EPROM. A RECEIVE/TRANSMIT line is also needed on A11 to provide an IF offset on the frequency data, and, if necessary, a frequency change for split frequency operation. The other nine address lines (A2 — A10) hold a binary code corresponding to the channel selected, which comes from the switch interface circuit (see later).

The strobing n A0 and A1, which comes from the synthesizer board, is in the form of a binary count from 0 to 3, generated by an oscillator counter pair on the frequency synthesizer board (Motorola), and has a count period of approxi-

mately 1½mS during which data is strobed not only into the synthesizer, but also into the display decoder (04 — 07), the data output being synchronous with the A0/A1 addressing from the synthesizer unit.

Channel selection for the synthesizer is derived from two 40-way CB type rotary switches with BCD outputs (see Fig. 3). The common contacts of these switches are grounded, and pull-up resistors are connected to the appropriate input pins of IC1 and IC3, so that inverse binary coded decimal data (negative logic) is obtained from both switches. One rotary switch (S1) is used to input the MHz band to work in, and on rotating clockwise, counts 0-9 four times. The other rotary switch (S2) increments the frequency in 25kHz steps, working from 43X.00 to 43X.975, where X is the MHz band that has been selected on S1. Thus, any frequency of the form 43X.YYY in 25kHz steps can be set up, where X is set on switch S1, and YYY is set on switch S2.

Since this method of setting frequency can be cumbersome when moving between commonly used channels, other options are available. A three way switch (S3) is provided which, when in the centre position allows direct input of frequency as described above, but, when

displaced from the centre, allows access to two completely independent groups of 40 channels, which can be anywhere in the 70cm band, in 25kHz steps. In this mode, S1 has no effect, but S2 moves through the 40 pre-programmed channels. One bank of 40 channels is accessed when S3 is down, the other when S3 is up. Thus, up to 80 favourite channels can be programmed into these positions for instant access, whilst still retaining full frequency agility when S3 is in the centre position.

One further option is available as a result of this design. It is often useful to be able to switch rapidly between two channels, where one is commonly used and the other is less commonly used. This design allows for another 32 channels to be pre-programmed as regular channels (eg, calling channels, repeater channels and working channels), and allows these to be quickly selected without disturbing the rotary switch S2, by the operation of S4, and then by using the switches S5/S6 which can be a thumbwheel type and a toggle switch or any other suitably coded switches. A binary switch is preferable, as it allows access to all 32 possible channels, but a BCD switch can be used, although it will limit the number of available channels to 20. Operation of the two-way switch S4 decides whether the

channel is set up on the rotary switches (S1 and S2), or on the multi-way switch (S5/6). As a result, two frequencies are immediately available, one on S5 and the other on the rotary switches S1 and S2, and switching between them is effected by operating S4.

The switch decoder for the synthesizer comprises 5 integrated circuits (LSTTL), IC1 to IC5, and converts the binary coded decimal from the rotary switches (S1 and S2), which occupies 10 data lines, into binary as needed by the synthesizer EPROM IC7, for which only 9 data lines are needed. It also allows for the extra 80 channels to be accessed with the three-way switch S3, and adds the facility to have independent channels available on S5 (see Figs 2 and 3).

The 40-way switch S2 produces 6 data lines (coded k0 to k5, k0 being least significant). The data presented is *negative logic* and comprises a binary representation of the tens digit of the position of the switch (0-3) on k4-k5. A BCD representation of the last digit of the switch position appears on k0 to k3. Thus the data appears on these lines as 0 to 39, inverse logic. The data is first inverted by IC1, which is a tristatable inverting buffer (74LS366). The tristate ability allows for the future addition of an independent controller (for example, a frequency scanner or computer). The outputs from the tristate inverter IC1 and the OE on Pins 1 and 15 are brought out to an external connector PL2 when LINK "A" is set appropriately.

In order for an external device to take control, it is necessary for IC1 Pins 1 and 15 to be taken high and then data can be supplied via the data lines B0-B5 (see Fig. 2). For the basic unit, however, the tristate input is linked low at link "A" to force IC1 to output all the time.

The coding of the 40-way switches is such that K0, K4 and K5 assume all possible states (when switch S2 is turned, K0 alternates 0,1,0,1,..., and after each 10th turn, K4 and K5 change in the sequence 00,01,10,11,00...). Thus, these 3 bits are already pure binary, and do not need any adjustment. However, the other three bits, K3, K2, K1, only assume certain states (k3,k2, k1:000,001,010,011,100 = 5 combinations out of a possible 8). To code them in true binary, therefore, these bits need correction. They are fed into an EPROM (IC2) with a special program "burnt" into it (see Fig. 5). A 74188 Bipolar PROM was used in the original design, but later replaced by the 2K EPROM as it was felt that in due course a considerable saving a power consumption could be effected by the use of CMOS EPROM devices. This program will be discussed fully shortly.

The MHz 40-way switch S1 produces 6 data lines, but only the lowest 4 are used, as it is only necessary to count from 0 to 9: the tens digit is neglected and the unused two bits are left unconnected. The lower 4 bits are fed into a quad 2 line to 1 line inverting tristatable multiplexer, a 74LS258 (IC3). The data lines are again brought out to a connector PL6 so that an external device can read from or place data onto this bus via C0 - C3. The output enable line from pin 15 of the multiplexer IC3 is linked low at link B on the basic unit, to force IC3 to output, but by repositioning link "B" it can be brought out to "B" on PL6, so that an external device can tristate the bus and place data on it. Assuming that IC6 Pin 11 is high, and the data is routed through the multiplexer and inverted, so that it becomes positive logic. By examining the binary coding for each bit, it can be seen that whereas M0 and M1 assume all states, and can be left unaffected, M2 and M3 only assume three of the possible four states (00,01,10) and so need correcting: these are also routed to the EPROM (IC2).

At the EPROM, 5 lines enter. The three "K" lines can take 5 states, and the two "M" lines can take 3 states. Thus, the total number of

combinations possible is $3 \times 5 = 15$, which can be coded into 4 binary bits ($2^4 = 16$). With an appropriately programmed EPROM, therefore, 5 lines can be compacted into 4 by assigning a unique 4-bit code to each 5-bit combination. The codes assigned range from 0000 to 1110. The four active outputs of the EPROM 04 - 07 are then routed to the address lines of IC7, the synthesizer EPROM, A6 to A9.

The other lines from the rotary switches that are already binary, and which are not routed to the EPROM IC2 are input to a non-inverting multiplexer. This consists of two 74LS257s (tristatable quad 2 line to 1 line multiplexers IC4

and IC5) configured as a 10 line to 5 line multiplexer. When the select lines (Pins 1 of IC4/5) are low, the data from the rotary switches (S1 and S2) is routed through to the address lines A2 to A5 and A10 of the 2532 EPROM. The outputs from the multiplexers are also brought out to an external connector PL3, along with the output enable line "C", so that, if required for a scanning facility, an external device can take control of the system by driving the enable line "C" high and putting its data on the lines A5 to A2 and A10. In the basic system, the tristate line is linked low at link "C", to force the multiplexers to pass data normally.

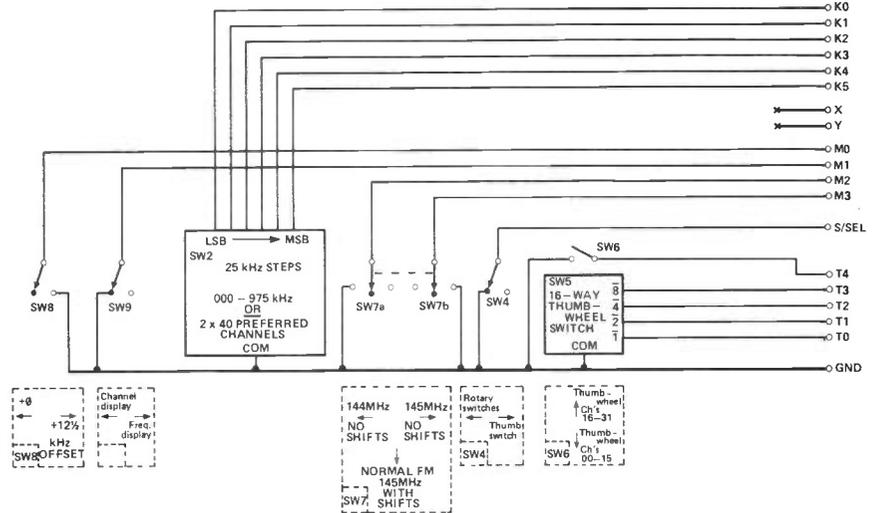


Figure 3a: 2m data switching.

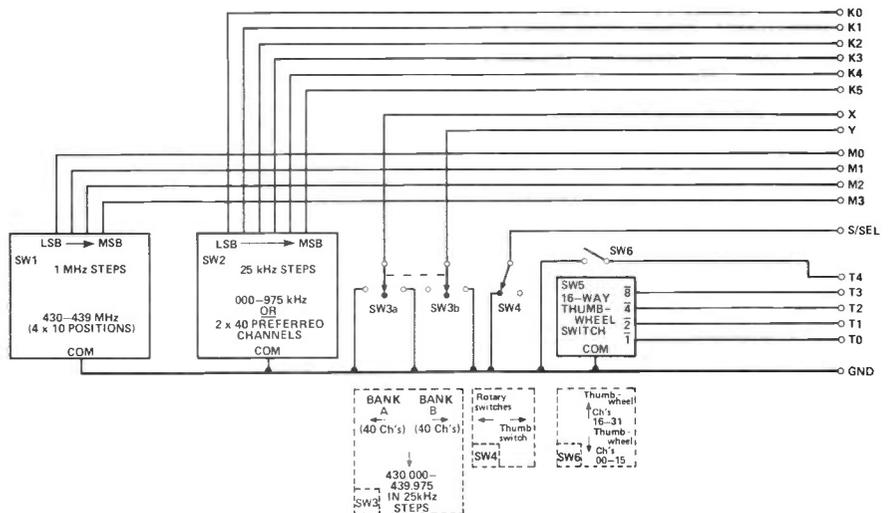


Figure 3b: 70cm data switching.

Design

The design philosophy was to create a basic system which used readily available components and offered sufficient flexibility for other devices (such as a scanning controller, a read/write memory or a computer) to be interfaced with only very minor circuit changes. A modular design evolved, and as a result many different display formats can be catered for. Also, the design can be modified for

use on other frequency bands, particularly 2 metres, where channels at 12.5kHz spacing can be accommodated and displayed. By carefully designing the hardware, a system has been devised that is simple to use for the inexperienced operator, yet powerful enough to equal many of the Japanese 'black boxes' on the market.

Since it is inadvisable to use an IF as low as 10.7MHz in a receiver covering the entire 70cm band (due to the

inherent poor image rejection), 21.4MHz was chosen. An EPROM chip was then programmed for 70cm, using this IF and containing the channels described in **Fig. 5**.

The block diagram in **Fig. 1** shows the complete synthesizer system. The frequency multiplier stages for both transmitter and receiver are not described since the design of these follows standard practice. If low power consumption is a requirement, then the EPROMs can be replaced with their CMOS equivalents. Some of the 74LS devices do not as yet have direct CMOS equivalents.

The ROM used in this synthesizer design is the source of much of the flexibility of the system, as its programming determines, (for any given channel selection):

1. The transmission frequency.
2. The receive frequency, and the IF offset.
3. The output shown on the digital display, with any special display if desired.
4. Any indication of a frequency shift when using split-frequency working. (eg, repeaters).

In choosing a ROM, several considerations had to be taken into account:

At least 400 channels were needed to be able to access the entire 70cm amateur band in 25kHz steps. Thus, 9 address lines were needed for this ($2^9 = 512$ channels). Three other address lines had to be provided — two for clocking the frequency data into the synthesizer IC and for indicating TRANSMIT/RECEIVE status, and so a total of 12 address lines are used. For this reason a 4K x 8 or larger ROM is necessary.

The device used had to be standard, easily programmable, and alterable, so an EPROM was chosen. At the time of writing, few facilities were available for programming the 8K x 8 EPROM (the 2764), and so the 2532 or 2732 had to be used. As will be described later, the use of this EPROM means that special interfacing to BCD coded switches is needed, but this in turn means that all of the 512 channel selections available in the EPROM can be accessed.

The system had to be compatible with a receive-only design since the TRANSMIT/RECEIVE line is not then needed, the standard 2K x 8 (2716) is the ideal choice for a programme EPROM. For this to be possible using the same PCB, the 4K x 8 EPROM used in the transceiver design had to be pin compatible with the 2716. This limits the choice of EPROM to the Texas 2532, NOT the Intel 2732. Then, to use a receive-only design with the 2716, the

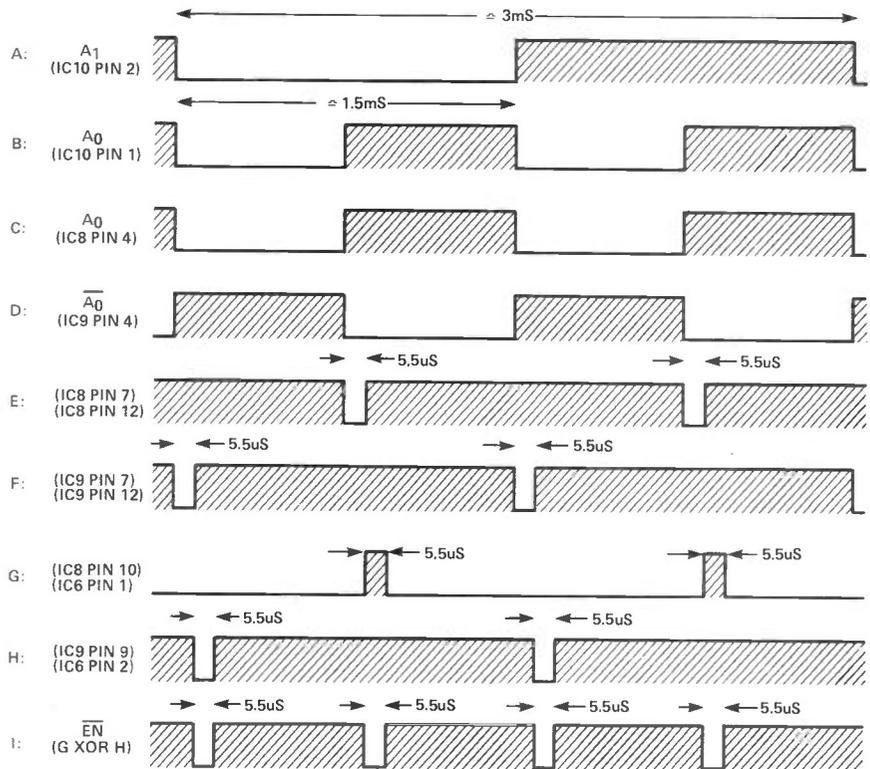


Figure 4: System timing diagrams.

TRANSMIT/RECEIVE line (connected to CE on the 2716) should be permanently strapped to the ground line.

System Operation

A typical example of the use of this system is putting out a call. If the calling channel (SU20 — 433.500 MHz) has been programmed as one of those selectable on S5, then the rotary switches are free to set up another channel: for example, a simplex channel to move to after the CQ call is answered. S4 can be operated to select the calling channel, set up on S5, and the CQ call put out. When a reply is received, the desired simplex channel can be rapidly checked using S4, to ensure that it is still clear, the message to change to the simplex channel can be passed on the calling channel, and then both stations can change frequency for the contact. The only switch operation needed is S4 to change frequency. Note that, even if the proposed simplex channel is not free, the frequency can be adjusted up or down in 25kHz steps with the rotary switch S2. Clearly, this system can be very efficient. If a new frequency had to be selected using S1 and S2 each time it were necessary, the process of changing channel would be much more laborious, particularly when operating

mobile.

When a frequency shift on transmit is needed, such as with repeater operation, it is useful to have the channels set up in three ways, as normal "forward" repeater channels (+1.6 MHz shift on transmit), simplex channels (no shift on transmit), and "reverse" repeater channels (-1.6MHz shift on transmit). To do this, three distinct channel selections are necessary. This is easily arranged using the facilities of the unit and has been found to work very successfully.

Note that, even when the transmit and receive frequencies are the same, the VCO outputs from the synthesizer will be different, due to the IF offset needed on receive.

For operation in different modes from the basic "dial-up frequency" way of entry, the system operates in another way. The three-way switch S3 is a double pole, centre-off type switch that is connected to the IC3 multiplexer (see **Fig. 2**). The select line on the multiplexer (Pin 1) is pulled up by the resistor when S3 is in the centre (off) position, forcing the data from S1 onto the outputs, however, if S3a is displaced from its centre position, the select line is forced low, and the other data is forced on the outputs. The upper 3 bits of this alternative data is hard-wired on Pins 5, 14 and 11 of IC3 to be the combination 010, which will emerge

after inversion as the combination 101, which is the one legal combination on these lines not used by S1 and is free for use to access other channels. This corresponds to the code for either 10 or 11 decimal, depending on the state of the lowest bit. Thus, for both 10 and 11, there exist 40 channels that can each be accessed with the 40-way switch S2. S3b determines the state of the lowest bit — if the switch is set to “band A”, pin 2 of IC3 is pulled high by the pull-up resistor; if the switch is set to “bank B”, then pin 2 is forced low. Thus 80 extra channels are provided by the “X” and “Y” lines, which can be dialed up using S3. This completes the range of codes from S1 (0000 to 1011).

The thumbwheel switch combination (S5 and S6) provides further channel options. Since the inputs to the EPROM IC2 can take 15 states, and four binary lines can take 16 states, there is one remaining output state left. This is 1111 or 15 in decimal. This cannot be accessed unless one of the address lines (A5) on the 2516 EPROM is taken high. When this occurs, the combination 1111 is output on the data lines, regardless of the states of the other address lines. Thus, if a switch S4 is connected to this line, pulling the input high with a switch position will cause the remaining address combination on the synthesizer EPROM to be accessed. At the same time, S4 is connected to the select lines (pins 1) on the two tristating multiplexers IC4 and IC5. When S4 is switched to ground, the data is routed normally, from the rotary switches S1 and S2, and the EPROM is free to take the 15 normal states. If, however, S4 is opened, IC2 output is forced to 1111 and entirely new and different data is enabled into the multiplexer from the other input, permitting 32 further channels ($2^5 = 32$) to be accessed. The data on this line could come from a hexadecimal thumbwheel switch (range 00 to 15) and a simple switch S6, in which case all 32 channels are available on lines T0, T1, T2, T3 and T4. Alternatively, a standard BCD thumbwheel switch could be used, together with S6, in which case 20 channels are available. The code used should provide a positive logic output, although negative logic can be catered for by programming the synthesizer EPROM differently.

The EPROM IC2 used in this decoder is specially programmed for the job of decoding the BCD data into binary combinations. Any program which assigns the codes 0000 to 1110 to each input combination uniquely will suffice, but different versions will result in incompatibility and so one “standard” form has been chosen (see Fig. 5).

ADDRESS LINES A6 → A10
ARE ALL AT LOGIC ‘LOW’
(0) FOR THIS CODING.

FOR ALL OTHER ADDRESS
INPUT COMBINATIONS,
OUTPUTS SHOULD BE CODES
TO ‘1111’ (ALL HIGH).

OUTPUT O3 IS A STATUS FLAG
AND SHOULD REMAIN ‘0’
THROUGHOUT OPERATION.
A ‘1’ OUTPUT ON THIS LINE
INDICATES AN ILLEGAL
CODE ERROR

0 = LOGIC ‘LOW’
1 = LOGIC ‘HIGH’
X = ‘DON’T CARE’
(all values)

ADDRESS						OUTPUT DATA				
A5	A4	A3	A2	A1	A0	O7	O6	O5	O4	O3/ OK
0	0	0	0	0	0	0	0	0	0	0
0	0	0	0	0	1	0	1	0	1	0
0	0	0	0	1	0	1	0	1	0	0
0	0	0	0	1	1	1	1	1	1	1
0	0	0	1	0	0	0	0	1	0	0
0	0	0	1	0	1	0	1	1	1	0
0	0	0	1	1	0	1	0	0	1	0
0	0	0	1	1	1	1	1	1	1	1
0	0	1	0	0	0	0	1	0	0	0
0	0	1	0	0	1	0	0	1	1	0
0	0	1	0	1	0	1	1	1	1	0
0	0	1	0	1	1	1	1	1	1	1
0	0	1	1	0	0	1	1	1	1	1
0	0	1	1	0	1	1	1	1	1	1
0	1	0	0	0	0	1	0	0	0	0
0	1	0	0	0	1	1	1	0	1	0
0	1	0	0	1	0	0	1	1	0	0
0	1	0	0	1	1	1	1	1	1	1
0	1	0	1	0	0	1	1	1	1	1
0	1	0	1	0	1	1	1	1	1	1
0	1	0	1	1	0	1	1	1	1	1
0	1	0	1	1	1	1	1	1	1	1
0	1	1	0	0	0	1	1	0	0	0
0	1	1	0	0	1	1	0	1	1	0
0	1	1	0	1	0	0	0	0	1	0
0	1	1	0	1	1	1	1	1	1	1
0	1	1	1	0	0	1	1	1	1	1
0	1	1	1	0	1	1	1	1	1	1
0	1	1	1	1	0	1	1	1	1	1
1	X	X	X	X	X	1	1	1	1	0
A5	A4	A3	A2	A1	A0	O7	O6	O5	O4	O3
(3)	(4)	(5)	(6)	(7)	(8)	(17)	(16)	(15)	(14)	(13)

Figure 5: EPROM (IC2) program.

An additional output is available from the 2516 EPROM on O3. This line, termed “OK”, is a debugging tool. So long as valid BCD data from the rotary switches appears on its input lines, the EPROM with flag “OK” with a logic “0” on O3. This indicates that the system is behaving itself. If, for any reason, an “ERROR” state is flagged in the form of a logic “1”, it is clear that something is amiss with the hardware or the BCD switches.

When external devices are to be attached to the board busses (eg, a scanning controller, read/write memories, a computer), the four links “A”, “B”, “C” and “D” should be changed from the “INT” position to the “EXT” position. In the “internal” position a ground is held on the enable line of the device outputting data onto the respective busses. Thus, the output device is allowed continuous access to the bus in question. If the link is moved to the “external” position, the ground is removed from the enable line of the bus driver in question, and this enable line is brought out onto an external connector so that it can be controlled by an outside device. When the outside device wishes to force data onto the

bus, it drives high the enable line on the bus concerned, tristating it and so allowing data to be pushed onto it. When normal control of the bus is wanted, the outside device grounds the enable line.

In a basic board, links “A”, “B”, “C” and “D” can be wired permanently to ground. However, if it is felt that the “external” option is one that may be wanted, four miniature DIL switches could be fitted on the board to make changeover easy.

In the context of external control, another use of the “OK” line comes to light. When, for example, a computer is the external controller, it will be placing binary data onto the busses as required. If, for any reason, non-BCD data is output, a spurious and undefined condition could arise. However, the “OK” line flags this condition, allowing action to be taken (for example, gating out the transmit line). Since the “OK” line could be very useful, it is brought out onto external connector PL3.


With the link in the “M” position (for the Motorola synthesizer), A0 is used as the fundamental timing pulse (see timing diagram). A0 is used since it is the output which changes state each

time the address on lines A0 and A1 lines changes. This output is then split between two sets of monostables. One line is taken to a monostable IC8a with a period of about 5 μ S which is set to trigger off the positive-going edge of the input signal. IC8a will trigger from alternate changes of address. The other line from the exclusive-OR output is inverted by another exclusive-OR gate and presented to another monostable with a similar period to that of IC8a. This also triggers off a positive edge, which was a negative-going edge before inversion through IC6. Thus, this second monostable, IC9, will trigger off those changes other than those that cause IC8a to trigger. As a result, both monostables between them trigger off every address change. The delays on both of these cause the strobe pulse to occur conveniently about 5 μ S after the transitions, thereby allowing the display driver time to set up and stabilise. When each monostable times out, further monostables (IC8b and IC9b) are triggered to determine the data input period (also set to around 5 μ S). Thus, a "time window" is provided, well into the data entry time, to strobe the display decoder whilst the data on the lines is stable. The outputs from the two monostables are combined with another of the exclusive-OR gates available in IC6, producing an output at pin 3 which goes to logic "0" during the entry period (the Q output of IC8b and the Q output of IC9b are supplied to the exclusive-OR gate so that the output at IC6 pin 3 is of the correct polarity). This output is connected to the enable (E) input of the 74LS256 (IC10). As a result, data is gated onto the outputs only during the given display data input time, thus resolving any timing problems that would otherwise occur.

In this way, the data output and addressing signals from the synthesizer EPROM are arranged to suit the display driver, completing the interfacing between the input switching, the synthesizer EPROM, and the display.

Channels And Devices

In the prototype design, the channels available were assigned in a way that proved to be very effective (see Fig. 5). The band was accessible in 25kHz steps as described. One bank of 40 channels (S3 to BANK "A") contained all the usual simplex channels (SU16 — SU55). The other bank (S3 to BANK "B") was used for all the repeater channels (forward and reverse shift — simplex was selected when the channel was dialled up directly on S1 and S2). The 32 thumbwheel switch S5/S6

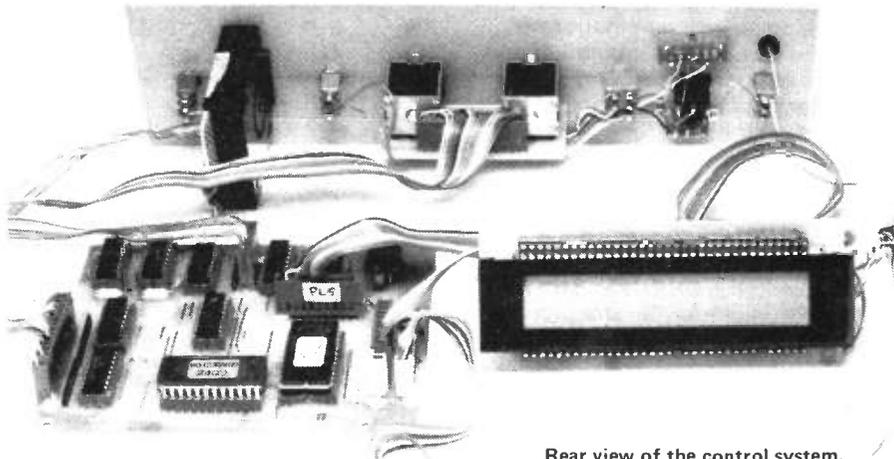

Rear view of the control system.

channels were programmed with all the locally used channels: simplex, calling, and repeater channels.

The data for the display driver has to be presented in the correct format and with the correct timing. From the discussion of the EPROM used it is clear that the data for the display is clocked out of the EPROM on the upper 4 data lines 04 — 07 of the EPROM, following the strobing on the A0 and A1 lines, as described earlier. The display driver requires 4 data lines to be strobed in, and so the data lines can be connected directly to the display decoder. However, the display driver also requires four individual strobe lines, as opposed to two binary coded lines, and the timing on these lines is critical. As a result, there has to be some decoding and retiming of the lines to the display decoder to strobe in the data. This is accomplished by four ICs (see Fig. 2). The first, a 74LS256 (IC10) is a dual 4-bit addressable latch, which is used as a 2 line to 4 line demultiplexer, to decode the addressing from the synthesizer IC. For use in this mode the CLR and D_B lines are grounded and the D_A line is pulled high. As a result, the device will decode the addresses on A0 and A1, pulling high the appropriate output Q_{xa}, provided that the E line is held low. If E is taken high, then all the outputs are forced low (inactive). The Q_a outputs are the lines used in this mode — the Q_b outputs are not connected. The enable line is used to provide the correct timing for the display decoder IC. For the display driver concerned (7211B) the data strobe line must only be strobed after the data has settled down on the input lines. Thus, it is only permissible for the strobe lines to the display driver IC to be high for some of the time whilst the data is present, and therefore the enable line is used to delay the strobe until the time is right. The timing is provided by a 74LS86 (TTL quad exclusive-OR gate IC6) and

two 4528Bs (CMOS dual monostables, IC8 and IC9).

Options

Either the 144MHz or the 145MHz band can be selected. If the three-way switch S7 is set to '144' then the 144MHz band will be stepped through in 25kHz steps by rotating the 40-way switch S2, with no frequency shifts (transmit frequency = receive frequency).

If the 3-way switch S7 is set to '145' then the 145MHz band will be stepped through in 25kHz steps by rotating the 40-way switch S2, also with NO frequency shifts (ie, NOT repeater mode).

If the 3-way switch S7 is set to 'NOR' then the normal band will be stepped through in 25kHz steps by rotating the 40-way switch S2: the 145MHz band with repeater shifts when appropriate: +0.6MHz on transmit between 145.000 and 145.1875; no shift from 145.200 to 145.5875; -0.6MHz on transmit between 145.600 and 145.7875 (2m repeaters) and no shift from 145.800 to 146.000 (satellites).

A +12.5kHz offset can be placed on transmit and receive using switch S8 — this allows the new 'interwoven' channels to be used. This offset applies to all but 'thumbwheel switch' mode.

The two-way switch S9 allows the selection of either a frequency or a channel number on the display. Set to 'FREQ', a display such as '145.550' is seen: set to 'CHAN', a display such as 'S-22' or 'P-05' (R5) is seen.

If 'thumbwheel switch' mode is selected on switch S4, then 32 channels are available on the 16 way thumbwheel switch S5 and the switch S6. These are set in the 'standard' 2532 EPROM to be a selection of common repeater and simplex channels.

Next month we conclude the project with construction and display details.

■ R&EW

A 10MHz universal counter system

The frequency meter featured in this issue uses the Intersil ICM7226, a versatile IC worthy of closer inspection. The pin-out is given in **Fig. 1**, and below is a description for each pin.

Pin 1: *Control*. If a selected digit line is connected via a diode, various control functions will be enabled, according to **Table 1**. These allow, amongst other things, the display to be blanked, or tested, or the switching in of an external oscillator, eg, a 10MHz source phase-locked to Droitwich. The 1MHz select allows the use of a 1MHz crystal with the same multiplex rate. However, the resolution will be one digit less.

Pin 3: *measurement-in-progress out*

Pin 5: *store out*

Pin 32: *reset out*

These provide the various timing pulses as outputs for controlling other devices.

Pin 4: *Function*. This will, upon connection of various digit lines (**Table 1**), switch the counter into its various modes. In 'Time Interval' and 'Frequency Ratio' the two inputs, pin 2 and pin 40 are used. Otherwise only pin 40 is used.

Pins 8-16 (except 12): are the segment BCD output of the count being displayed, used in the frequency meter to control an LCD driver. The data is multiplexed at a rate of 500Hz.

Pins 8-16 (except 12): are the segment outputs for an 8 digit CA multiplexed display. There is an interdigit blanking time of $\approx 6\mu s$ to prevent ghosting.

Pin 19: *Reset*. Connecting this pin to 0V will reset the whole counter.

Pin 20: *Ext d.p. input*. When enabled (D8 to pin 1) the connection of a digit line will light the appropriate decimal point.

Pin 21: *Range*. There are four internal ranges available, depending on which digit line is connected, with the D1 line giving 10ms gate, and the D4 line giving 10s.

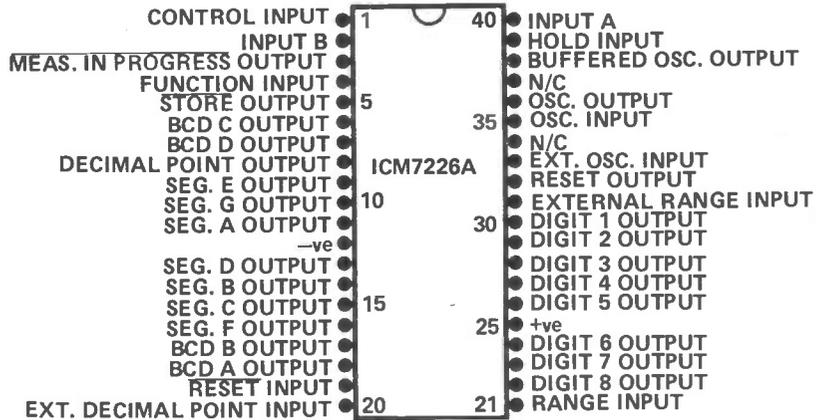


Figure 1. Pin designations for the 7226A.

However by connecting D5, an external range can be applied to pin 31.

Pins 22-30 (except 25 = +V): are the digit lines, and it will have been realised that these are used for many operations. They also connect to the CAs of the displays, D1 being the least significant digit (on the right looking from the front).

Pin 33: *External osc in*. If enabled with D1 to pin 1, an external oscillator signal can be fed into this pin, and if for example one of the Plessey high speed dividers up to 1.5GHz is used, a 2.5MHz frequency will give the correct reading.

Pins 34,37: are not committed and should be connected either to +V or 0V for best stability.

Pin 35,36: are the oscillator pins, normally used with a 10MHz crystal.

Pin 38: *Buffered osc out*. This gives the crystal output, and is capable of driving one TTL load (LS), without loading the main oscillator. However, capacitive loading

should be kept to the absolute minimum. With reference to the description of pin 33, the 'osc out' could be divided by 4 using a 74LS74 to give the 2.5MHz signal which is then fed back into pin 33.

Pin 39: *Hold input*. This should normally be tied to 0V, but if switched to +V the display will freeze with the last reading. This same switch will blank the display if D4 is connected to pin 1 at the same time.

A test circuit is given in **Fig. 3**, which will demonstrate most of the capabilities of the device. The inputs should be TTL level, and should not exceed the supply by more than 0V3.

When in 'frequency ratio' mode, Fa (pin 40) should be greater than Fb (pin 2).

For single or 'one-shot' time interval measurements, input A, then input B, must have a high to low transition to 'prime' the counter, prior to any measurements being taken using external circuitry. For repetitive signals this occurs automatically.

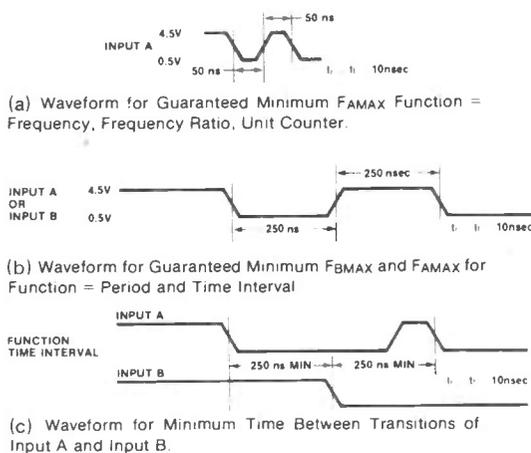


Figure 2. Waveforms for guaranteed minimum frequencies when used as a counter (a), tuner (b) and during AB transitions (c).

	FUNCTION	DIGIT
FUNCTION INPUT PIN 4	Frequency Period Frequency Ratio Time Interval Unit Counter Oscillator Frequency	D1 D8 D2 D5 D4 D3
RANGE INPUT PIN 21	.01 Sec/1 Cycle .1 Sec/10 Cycles 1 Sec/100 Cycles 10 Sec/1k Cycles	D1 D2 D3 D4
External Range Input PIN 31	Enabled	D5
CONTROL INPUT PIN 1	Blank Display Display Test 1MHz Select External Oscillator Enable External Decimal Point Enable Test	D4&Hold D8 D2 D1 D3 D5
EXTERNAL DECIMAL POINT INPUT, PIN 20	Decimal Point is Output for Same Digit That is Connected to This Input	

Table 1. Control functions for selected digit lines.

THE NEC RALLY

A personal view, by Stephen Ibbs.

It is refreshing to see the RSGB moving to the NEC for their rally. The well-known problems of space, access, and parking, associated with 'Ally Pally' were immediately resolved, but at what cost? Listening to the locals travelling back from the show revealed some interesting thoughts...

Clearly many people appreciated the move to the new venue as a breaking away from the old London Wireless Club image that still lingers rightly or wrongly. Two London amateurs told me they preferred it at 'Ally Pally', because it was the local London rally for them, and blow the rest of the country — friendly bunch, Radio Hams!

The entrance fee of £2, admittedly including parking, seemed somewhat high, but this did at least enable a feeling of more room, and the space to breathe. When will exhibition organisers place just a few seats around the place so that weary travellers can rest without having to buy food first. The catering was, I thought, awful. Catering firms presumably have to pay a large

fee to get the NEC franchise and I felt they were taking their revenge out on us with the now traditional soggy roll and thimble of coffee. Some exhibitors were determined to recoup their stall fee in their sales and items of second-hand equipment were being offered at absurd prices. However, other stalls were also offering some excellent bargains, and I was able to stock up on ceramic capacitors and get 2 dynamic microphones at excellent prices. The Wood and Douglas stand was doing a brisk trade in their new amplifier kit, and it was nice to put a face to June, their superb telephone receptionist. Anybody who has phoned W & D will know what I mean.

One section of the hall had been given over to various societies — RAIBC, RAYNET, RN, RAF etc, and I spent an enjoyable time learning about their various interests. The RAIBC stand had a talking frequency meter that must be a real boon to white-stick operators, and it is refreshing to see how amateurs *do* help each other get

over disabilities.

The prize for the best exhibit must surely go to the brilliant 10GHz transceiver display by the Midland Microwave Society. This contraption, which was mounted on 'chip' board, (pun intended by them), had a brass cold water tap attached, what looked like a watering can funnel, and various bits of plumbing — useless but eye-catching, a comment suitable for many 'essential' bits of paraphernalia I suspect.

Conclusion

For certain sections of the amateur fraternity this must have been a good rally. Signposting for the various lectures should have been better, and I would have preferred more second-hand stalls, a 'flea market' and a 'bring and buy'. I hope it stops in the Midlands to bring the RSGB to the country as a whole, and if the catering can be improved, it will be entered in next year's diary for me at least.

■ R&EW

EVENTS: MOBILE RALLIES

June 1983


May 10-12th	Cable '83 Online Conference	Wembley Conference Centre	Northwood (09274) 28211
May 10-12th	Tomorrow's World Micro City 1983	Bristol Exhibition Complex	Bristol (0272) 292156
May 22nd	B.A.T.C. Amateur TV	Posthouse, Leicester	G8CJS (0532) 670115
May 22nd	RS Welsh Amateur Mobile Rally	Barry College of Further Education	GW4FOM R. Rowles Cardiff 565656
May 25th	Lincoln Short Wave Club Annual General Meeting	City Engineers Club	G5FZ, G6C01
May 29th	East Sussex Wireless Revival	Civil Service Sports Ground Ipswich	J. Tootill GLIFF (0473) 44047
June 5th	Spalding & DARS Mobile Rally	Springfields, Spalding	I. Buffham G3TMA

In the Next Issue of R&EW

The Complete Communications Magazine

DTMF Decoder

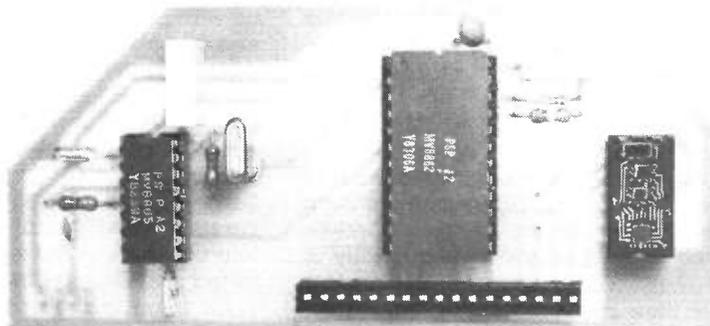A Dual Tone Multi-Frequency signalling system, which acts as an excellent receiver for control/data transfer via the telephone lines.



Digital Capacitance Meter

To complement this month's high quality LCD frequency meter, we asked the designer to come up with a unit of the same standard for measuring capacitance. The project he produced exceeded all expectations, and we present it next month.

HF RECEIVER DESIGN II

The second part of this informative series analyses the complexities of receiver performance, with an in-depth explanation of the many confusing parameters encountered.



RADIO AMATEUR'S TEST CARD

An extremely interesting and useful project for DXers everywhere (. . . but the exact details we're keeping secret until next month).

Plus:
SSB for the SX200N – a neat add-on.
Z8 Backplane – an essential interface.
Datong Automatic Notch Filter – reviewed and explained.

*July edition
On Sale 2nd June*

PROJECT PACKS


100W POWER AMPLIFIER

Ultra high quality, high power audio power amplifier. Over 100W into 8 ohms, very low distortion - <0.01% at 1kHz into 8 ohms THD, low signal to noise ratio > 96dB.

Complete kit of parts including; custom designed case, with all panels preformed and drilled, high quality finish to front panel, 250VA torrodial transformer, amplifier board and components, protection board and components, heat-sinks, all nuts, bolts, connecting cable etc.

Stock No.
41-00508

Price
£185.00

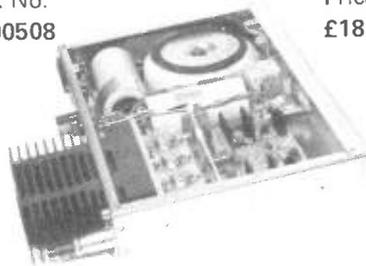

All prices include VAT @ 15% Please allow 21 days for delivery. Postage & Packing 60p per order.

100W PA BOARD

Kit of parts for 100W power amp board. PCB, all components and output transistor bracket.

Stock No.
41-00504


Price
£41.95

LOUDSPEAKER PROTECTION BOARD

Kit of parts for loudspeaker protection board, PCB and all components.

Stock No.
41-00505

Price
£ 9.65

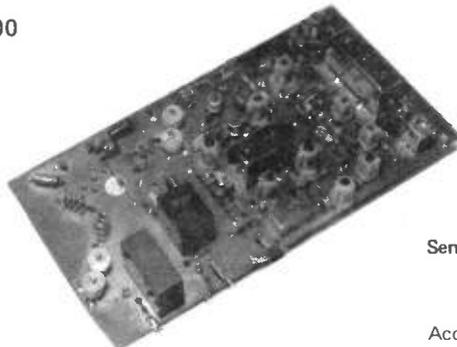

FRG7700 Memory Add On

SR5303U 40 way channel switch.

Stock No.
53-00303

Price
£ 4.54

2m Transverter

Up dated version as described this month. For use with most HF transceivers- converts 28MHz to 144MHz on both receive and transmit. Up to 10W output. Complete electronics kit inc., double sided PCB, all components pre-aligned filters, Xtal and heatsink for output transistor.

Stock No.
41-00305

Price
£56.83

Send your order to **Ambit International**
200, North Service Road,
Brentwood, Essex CM14 4SG
Tel: (0277) 230909

Access/Barclaycard Welcome.

PROJECT BOARDS

High quality fibre glass printed circuit boards for R&EW projects and data briefs.


ISSUE	DESCRIPTION	STOCK NO.	PRICE
JUNE	LCD DFM Main Board	41-20603	£7.24
	LCD DFM Display	41-20604	£1.81
	500kHz Pre Amp	41-20605	£0.92
	200MHz Prescaler	41-20606	£0.92
	600MHz Prescaler	41-20607	£0.92
	KB4438 (Undrilled)	41-20602	£0.67
MAY	Rew Vox	41-20405	£0.87
	Audio Limiter	41-20501	£3.79
	!R Volume Control	41-20503	£2.48
	100W Power Amp	41-20504	£5.25
	PA Protection Board	41-20505	£1.40
	Rewbichron 2 Logic Board	41-20506	£6.07
Rewbichron 2 Display Board	41-20507	£3.79	
APRIL	FM IF Amp	41-20401	£2.41
	18W PA	41-20404	£4.83
MARCH	Bargraph Display Driver(Undrilled)	41-20301	£1.38
	Bargraph Display (Undrilled)	41-20302	£0.93
	Airband Memory	41-20303	£3.45
	2M Transverter	41-20305	£9.60
	Noise Generator	41-20306	£4.35
FEBRUARY	Modem	41-20201	£6.83
	Audio Attenuator (Undrilled)	41-20202	£0.72
	CW Filter	41-20205	£2.76

All prices include VAT @ 15% please allow 21 days for delivery. Postage & Packing 60p per order.
Send your order to **Ambit International**, 200 North Service Road, Brentwood, ESSEX CM14 4SG.
Tel: (0277) 230909. Access/Barclaycard Welcome.

SEND YOUR ORDER TO:

ambit INTERNATIONAL

200, NORTH SERVICE ROAD
BRENTWOOD, ESSEX
CM14 4SG
Telephone : (0277) 230909

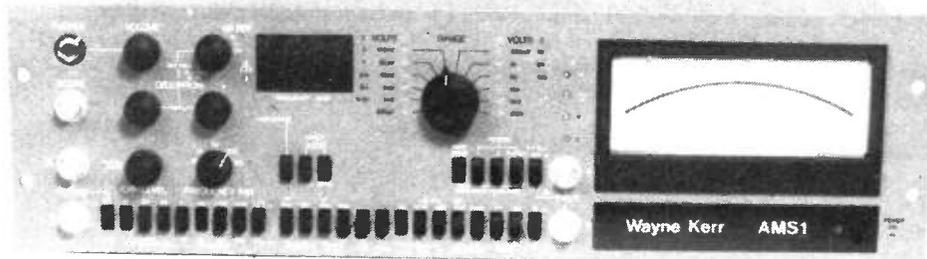

AMS 1

AUDIO MEASURING SYSTEM

A comprehensive piece of test equipment from Wayne Kerr, reviewed by our Audio Engineer, David Strange.

Basically, the AMS1 consists of an oscillator and a meter, with a large amount of sophisticated electronics in between, which may be selected to carry out the wide range of measurements required by the audio engineer.

The tests accommodated by the AMS1 are: Frequency Response, Level (including programme and noise), Wow and Flutter, Rumble, Distortion and Phase. The measurements may be monitored by oscilloscope and headphones from sockets arranged on the front panel.

Quad Stab Osc

The oscillator is a quadrature type, stabilised by a thermistor. This, unfortunately affords no long term amplitude stability, but was probably not deemed a problem because there is no absolute calibration of output level. Instead, the output may be continuously varied by a potentiometer, with three push buttons to enable attenuation in two 30dB steps and a switch at

the back of the potentiometer giving an additional 20dB step. Overall the level may be varied across the range -90dB to +20dB, ref to 0dB (0.775). When checked against the meter section of the test set, the oscillator steps were in disagreement by about 0.2dB.

As well as the normal sinewave output from the oscillator, a clipped square-wave version is also selectable. The frequency range of the oscillator is 15Hz to 150kHz selected in 4 decade steps by pushbuttons and continuously varied within each step by a more or less uncalibrated potentiometer. The frequency is read from a 4 digit 7 segment display with a rather slow rate of sampling. Setting a specific frequency, for say distortion measurements, proved to be very difficult because of the second or two inertia in the system.

On the subject of the frequency counter, it may also be used to measure the frequency of an incoming signal — useful when checking the long term drift or speed variation of a tape

recorder. Here the frequency variation would be noted and the percentage drift calculated accordingly.

Metering The Functions

The meter is, of course, used as an indicator for a number of instrument functions besides level. Dealing with level first, we find five different measuring methods at our disposal:

1. Volts true RMS
2. Volts RMS
3. DIN 45405 (for CCIR noise measurement)
4. BS 4297 (for programme measurement)
5. ANSI C16.5VU (for programme and noise)

To perform the measurements to these characteristics, not only are different time constants required, but also different arithmetic functions. Before the signal gets processed this far, it is first amplified. Despite having the appearance of possessing two inputs the amplifier is unbalanced and the inputs commoned for all functions of

OSCILLATOR (Parallel A and B outputs with ON/OFF switch)	
Frequency Range:	15Hz to 150kHz in 4 decade ranges
Output level:	25µV to 7.75V (-90dB to +20dB ref 775mV)
	Frequency and Output Level may be monitored using Check Freq and Check Level functions
Output flatness:	Normal range (-70dB to -20dB) 15Hz to 30kHz ± 0.2dB 15Hz to 150kHz ± 0.5dB -20dB position (-90dB to 0dB) 15Hz to 30kHz ± 0.5dB 15Hz to 150kHz ± 1.5dB (-80dB to 0dB)
Output impedances:	50 ohm nominal
Sine wave distortion:	15Hz to 20kHz less than 0.01% (typically 0.005%)
Square wave output:	Normal range (1mV to 5Vpk-pk) Rise time to 90% < (1% of period - 1.5µs)
Wow and flutter carrier oscillator:	3150Hz (3000Hz optional) ± 3Hz
LEVEL MEASUREMENT (From selected A or B input or Oscillator output)	
Range:	300µV to 100V FSD on Vrms range - 92dB to +42dB on dB range (ref 775mV)
Measurement:	Switchable between true rms Volts or dB, on a linear centre zero dB scale
Frequency response:	15Hz to 30kHz ± 0.2dB 10Hz to 150kHz ± 0.5dB (300µV range ± 1dB)
Input impedances:	1M ohm or 600 ohm (switchable)
Frequency counter:	4 digits - may be used to measure incoming frequency or oscillator frequency
Programme Measurement	
Ballistics switchable between PPM characteristics (BS4297) and VU characteristics (ANSI C16.5 1954). (Other parameters as per Level Measurement Section above for frequencies in the range 20Hz to 20kHz).	


NOISE MEASUREMENT (A or B input)	
Indication:	True rms Volts, Quasi-peak dB (CCIR Rec 468-2) or VU characteristic (ANSI C16.5 1954)
Frequency response:	Wideband (10Hz to 150kHz ± 0.5dB). Two further positions, to accommodate plug in option filters to CCIR, DIN, IEC, and NAB standards (other parameters as per Level and Programme measurement sections above)
WOW AND FLUTTER MEASUREMENT (A or B input)	
Range:	0.03% to 10% FSD with 3150Hz or 3000Hz carrier
Residual reading:	< 0.003%
Input level range:	50mV to 100Vrms. (Warning light indicates if signal too small)
Standards:	To CCIR Rec 409-2 (Weighted and Unweighted)
RUMBLE MEASUREMENT	
Range:	- 92dB to + 42dB (ref 775mV)
Indication:	dB to DIN 4549 (Weighted and Unweighted)
DISTORTION MEASUREMENT (A or B input)	
Range:	0.03% to 100% FSD (0.1% min at 16kHz)
Frequencies:	80Hz, 1kHz, 5.6kHz, 16kHz (switchable)
Input level range:	100mV to 4.5Vrms (100K ohm input impedance) 3.5V to 100Vrms (12K ohm input impedance)
Inherent distortion:	Less than 0.005%
Residual noise:	Less than 0.007% relative to 100mV (Less than 0.015% at 16kHz)

NARROW BAND FILTERS	
For measurement of signals masked by noise (eg, Crosstalk)	
Frequencies:	80Hz, 1kHz, 5.6kHz, 16kHz switchable (other parameters as per Level Measurement section above)
PHASE MEASUREMENT (A input relative to B input)	
Range:	± 120° (on centre zero meter scale) with phase invert
Input Level Range:	50mV to 5Vrms. (Warning Light indicates if signal is outside this range)
Resolution:	2°
POWER MEASUREMENT	
Range:	1mW to 1kW into external 8 ohm load on linear scale
MONITOR FACILITIES	
dc output	1V at FSD
Scope output	1Vrms at FSD
Phones output	Adjustable, for high or low impedance headphones
SUPPLY VOLTAGE	115 or 230V ± 10% ac 50-60Hz
TEMPERATURE RANGE	Operating 0 to 40°C Full specification 10 to 30°C
WEIGHT	4.9Kg.
DIMENSIONS	(Overall inc knobs) 483mm x 134mm x 250mm

Table 1: Technical specifications.

WIDEBAND LCD-DFM

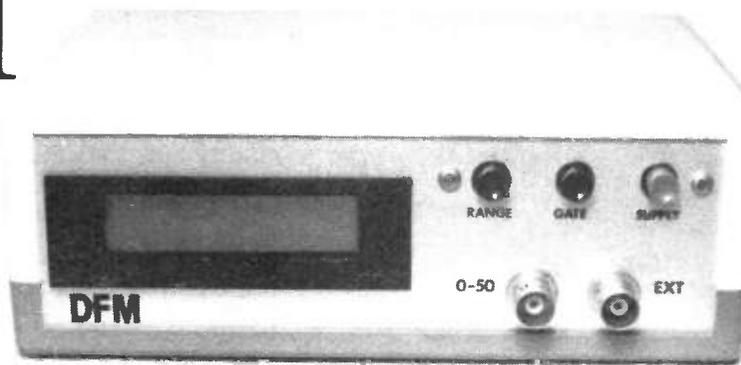An 8-digit portable frequency meter, designed by Stephen Ibbs G4LBW, to cover the range DC-600MHz.



The frequency meter featured in the November '81 issue of **R&EW** used the Intersil 7216, which directly drives an 8-digit LED display, and whilst a battery pack was incorporated, its size made it primarily a piece of bench equipment. However, it had the advantage of three switchable ranges and a means of measuring capacitance. There are occasions, when a smaller portable unit is desirable and problems are encountered with LED displays, because even if multiplexed, they draw quite a lot of current. The answer lies in using LCD displays, and recent developments have made the design of a small frequency meter possible.

A new technique of triplexing liquid crystal displays was tested utilising the ICM 7231A. Previously each segment had to be connected separately — an 8 digit display with decimal points required 65 connections (including the backplane). By triplexing, each digit only requires 3 segments lines, the whole display controlled by three control lines, making a total of 27 connections, and this includes one annunciator (a chevron with the display specified) and one decimal point, per digit. This in turn means that one 40 pin IC can drive a display and still have other pins available for inputting and controlling data.

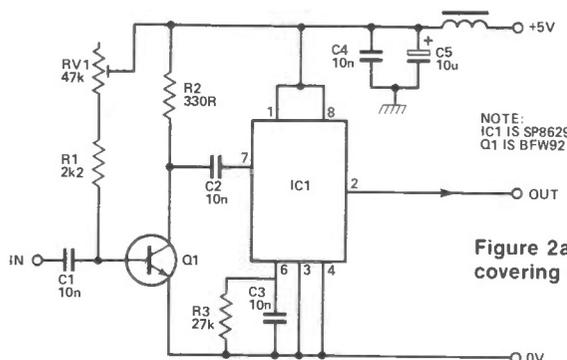


Figure 2a. One of the preamp/prescalers covering the 200MHz range.

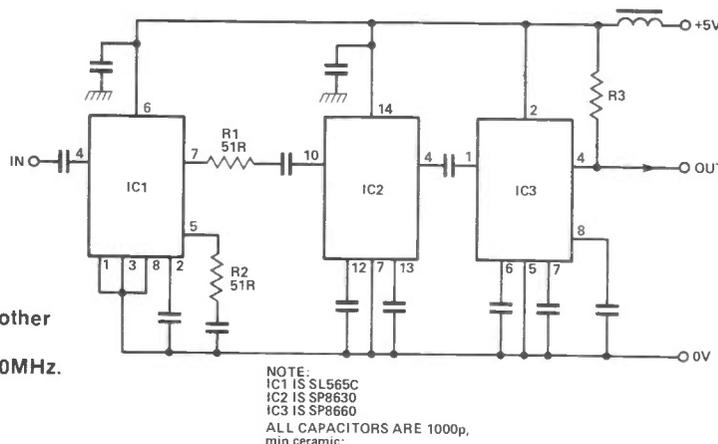


Figure 2b. The other prescaler, which operates up to 600MHz.

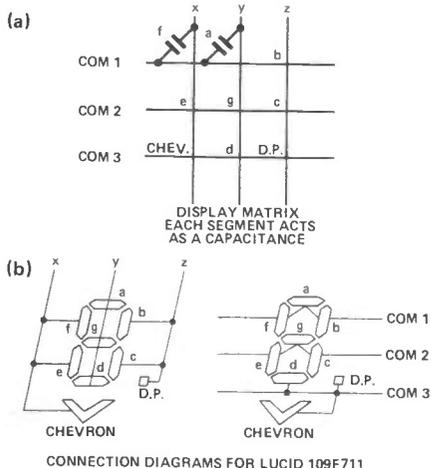


Figure 1. Display wiring as represented by a cross-matrix (a) and the actual segments (b).

A New Approach

The best way to understand the triplexing technique is to consider the display as a matrix (Fig. 1a). As the common line and the x segment line intersect, the 'f' segment lights. The voltages on the lines decide which segment lights. Fig. 1b shows the connections for the specified LUCID display to help faultfinding (eg if the 'b', 'c', and the 'dp' segments fail to work it is the z segment line of the digit which is suspect).

The LCD driver IC decodes the 4 bit BCD data arriving at pins 32-35, which is presented in multiplex form by the ICM7226A, a frequency meter IC that performs all the 7216 functions, but also provides BCD output. The IC has 4 gate times, but only two are used, as

the 10ms gate (pin 30) was not felt to be very useful in frequency meter applications, and the 10s gate (pin 27) is normally too long to wait for portable applications.

The BCD output data is multiplexing through all the digits, each digit's data coinciding with a 'high' on the appropriate line D1 to D8. This control information needs to be encoded into a 3 bit binary code to be fed into the A0, A1, A2 pins of the 7231, which is accomplished by the 4532. One other piece of information will enable the 7231 to perform properly, a low-going pulse to the CS pin to latch the data, decode it, and then send it to the digit being addressed by the 'A' lines (37-39). This proved to be a problem in the design stage because, at first, the GS

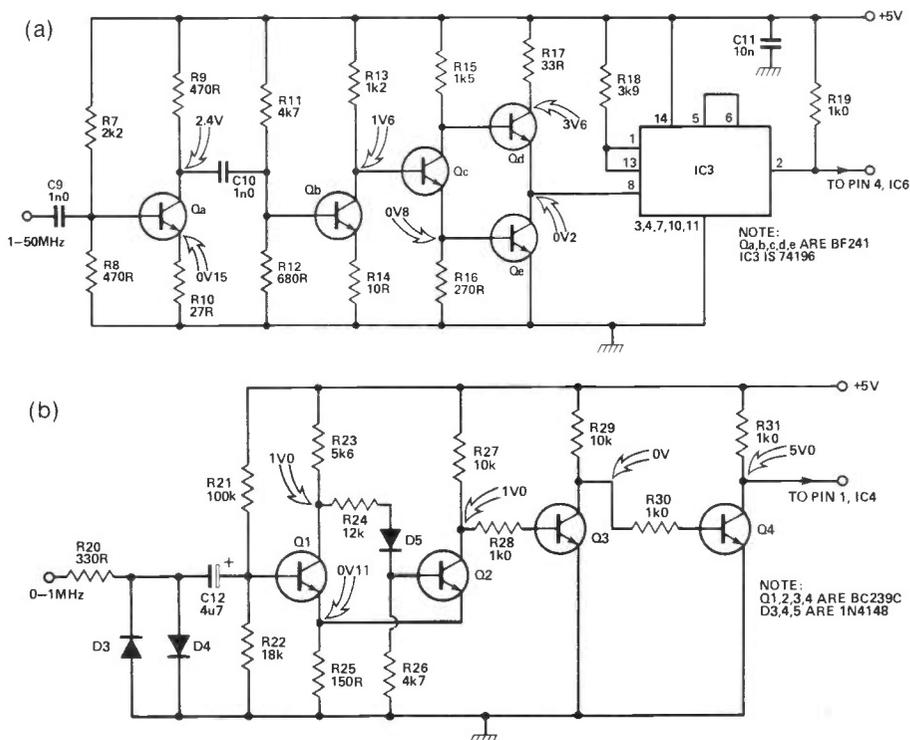


Figure 3. The HF prescaler (a) and LF amplifier (b) which appeared in the November '81 issue of R&EW.

output of the 4532 was used. Eventually, however, the Eo output was tried. This pin goes high when all the inputs are low and the E1 (pin 5) is high. Fortunately this occurs after each digit has been addressed (a delay actually incorporated into the IC's design to prevent inter-digit ghosting when driving an LED display direct). When inverted, this works a lot better than pin 14. The inclusion of C3 (22-1000pF) is to stabilise the display.


Pin 2 of the 7231 is labelled Vdisp,

and this allows control of the display peak voltage, most easily accomplished by incorporating a preset, RV1, to vary the voltage on the pin. This will cause the display either to blank (+ve), or become so strong that it will ghost (0v). However, such an arrangement is fine if the display and IC do not fluctuate by more than $\pm 5^\circ\text{C}$. The circuit shown in Fig. 7d can be used to provide temperature compensation. The extra resistor and transistor are easily incorporated on the PCB.

Figure 4. bypassing the 74LS196 using a DPDT switch (top right).

NAND		
A	B	OUT
0	0	1
0	1	1
1	0	1
1	1	0

TRUTH TABLE

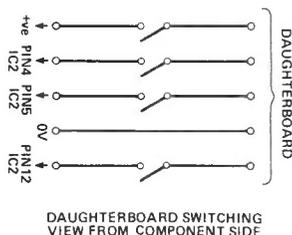

Circuit Description

The 1-50MHz preamp/prescaler was taken from the R&EW meter already mentioned, with the exception that the BF241 was used instead of the BF274. A wire link connects the preamp to the prescaler IC, because if signals below 10MHz are being measured, the 74LS196 can be bypassed via a switch (Fig. 4) to avoid the signal being divided by ten, thereby giving better resolution.

The signal goes via a logic switching network. The truth table of the NAND gate is given in Fig. 5. If one of the inputs is high, signals (inverted) will pass through the gate. Thus R7 holds IC5d open, allowing signals to pass through. R8 holds IC5b closed, its output remaining high. This in turn opens IC5a, allowing the signal to pass through to the 7226. A 5-pin plug has been incorporated on the PCB, because it will be seen that if pin 12 was made to go low, and pin 5 high, signals from an external source can be fed to pin 4 and on to the counter. A small series of boards have been designed to fit onto the PCB plug (in position x), and when plugged in, they automatically switch the levels, and disable the output of the 50MHz preamp. It only takes a few seconds to open the case and plug on a new board, soldering the coax, but the author recognised that many would want a daughter board permanently plugged in, but switchable, so if the PCB plug is placed in position 'y', a multipole switch can be added to connect the board and achieve the necessary signal and supply connections. The 0V being common to all, only a 4 pole switch is needed, wired as shown in Fig. 6. The use of a switch is particularly recommended for the 600MHz prescaler board because this draws a lot of current and it is good to be able to disconnect the +ve supply line when not in use. (The prescaled buffered output of the 50MHz preamp is also available at IC5 pin 8).

The 10MHz frequency reference is provided by X1 with trimming by TC1. A regulated +5V is needed by all the ICs, most easily achieved using a 3-terminal regulator with C4 and C5 included to aid stability.

The 300kHz-50MHz preamp was fully described in the Nov. 81 issue so will only be summarised here. Qa and Qb provide the amplification and Qc, d, e the level shifting to TTL. The IC acts as the divide-by-10, and if the S version of the 74196 is selected frequencies up to 100MHz can be processed. The LS version in the prototype worked up to about 45MHz.

The low frequency amp (1 - 500kHz) was also described in the same issue with Q1 being the amplifier, Q2 acting as a switch, and Q3 and Q4 shifting the output to TTL level square waves.

The 200MHz pre-amp has a choke and two capacitors for decoupling. The BFW92 is used in common emitter mode, and the preset should be adjusted to give half-supply voltage at the collector. The signal is then capacitively coupled to the input of the divide-by-10 SP8629, the output emerging at pin 2. The unit will randomly count, and this can be stopped by inserting a resistor between pin 7 and earth; though this will reduce the sensitivity. The IC is actually guaranteed to 150MHz but the prototype measured accurately up to 240MHz.

The 600MHz preamp needs no adjustment and uses the recently introduced Plessey IC, the SL565C wide gain amplifier (guaranteed to 1GHz). The output feeds the input of the two divide-by-ten ICs, the first being the SP8630 (up to 600MHz), the second being the 8660, which, whilst only guaranteed to 200MHz, does provide TTL output. This module will also randomly count, and resistors to the IC inputs will stop this, but reduce the sensitivity.

Both the 200MHz and the 600MHz boards measured the 12MHz oscillator stage of a 2M transceiver with ease, but the lower limit is somewhat dependent on the wave shape.

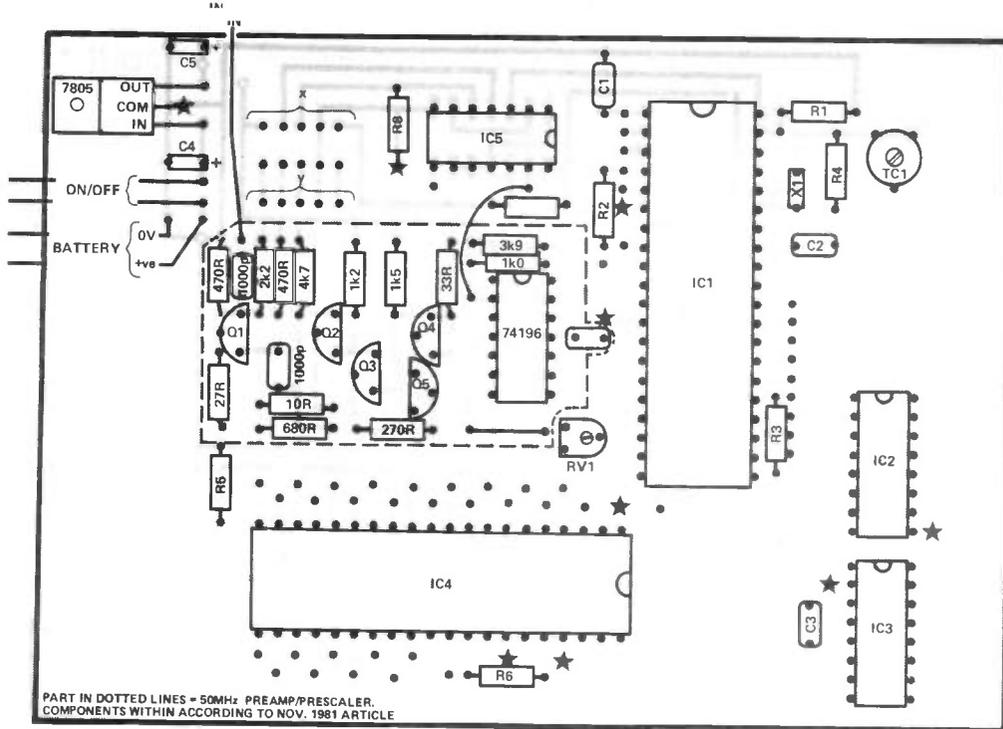


Figure 8a. Component placing on the double sided PCB.

★ = SOLDER LINK BOTH SIDES

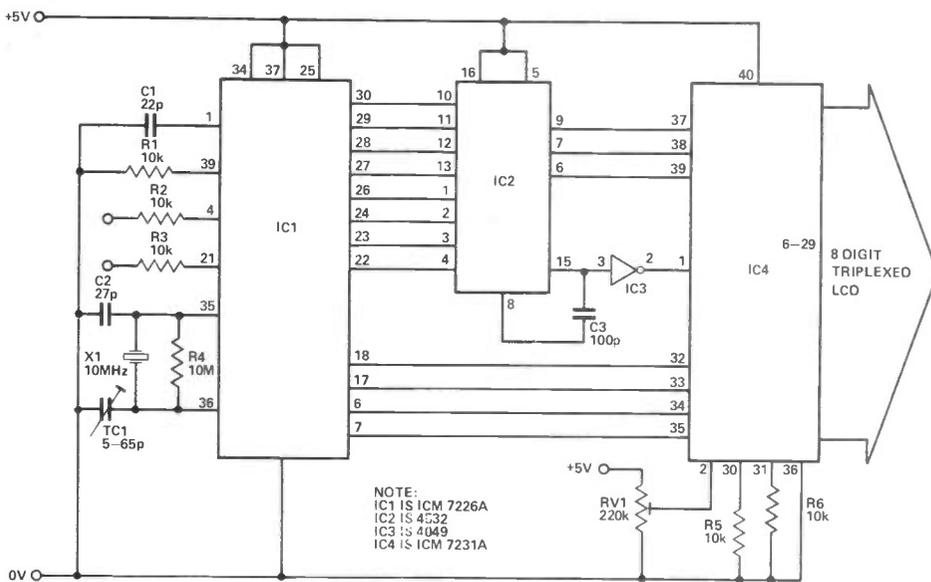


Figure 7a. Main circuit of the LCD-DFM.

Figure 7c. Logic switching for additional boards using the 74HC00.



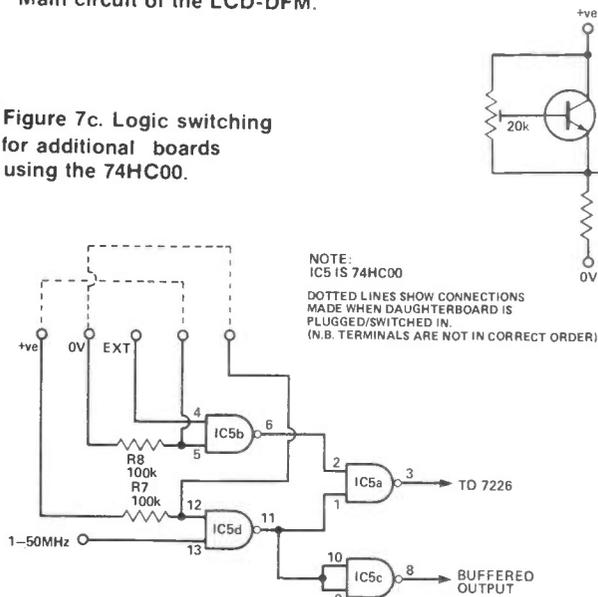
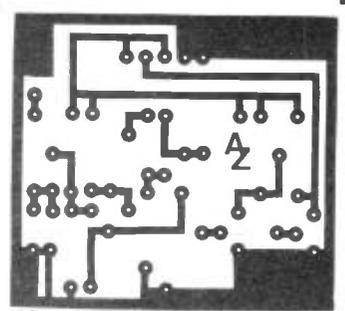



Figure 7d. Temperature compensation circuit (optional).

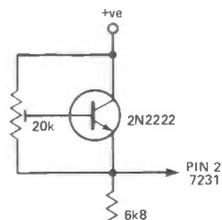


500kHz Pre-amp. © Baskin-Indev, Ltd 1983

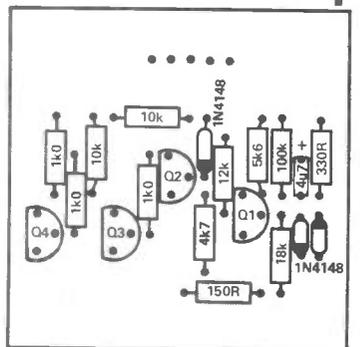

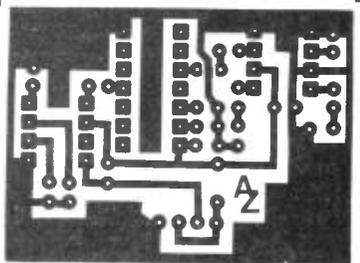
Foil pattern and component overlay for 500kHz pre-amplifier



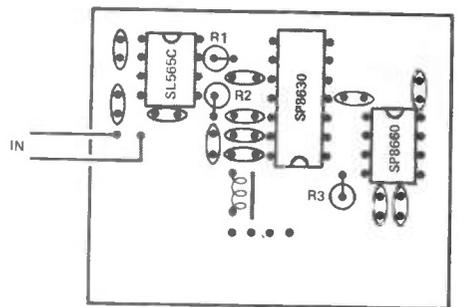600MHz Prescaler © Baskin-Indev, Ltd 1983




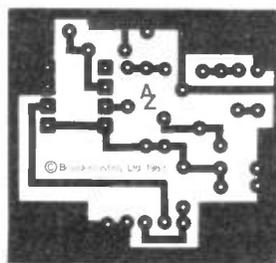Foil pattern and component overlay for 600MHz prescaler.



200MHz Prescaler

Foil pattern and overlay for 200MHz prescaler

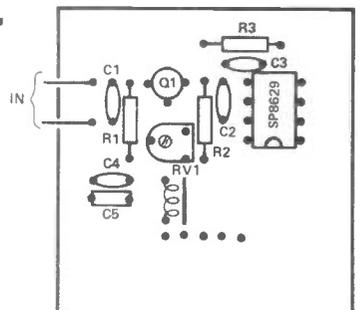

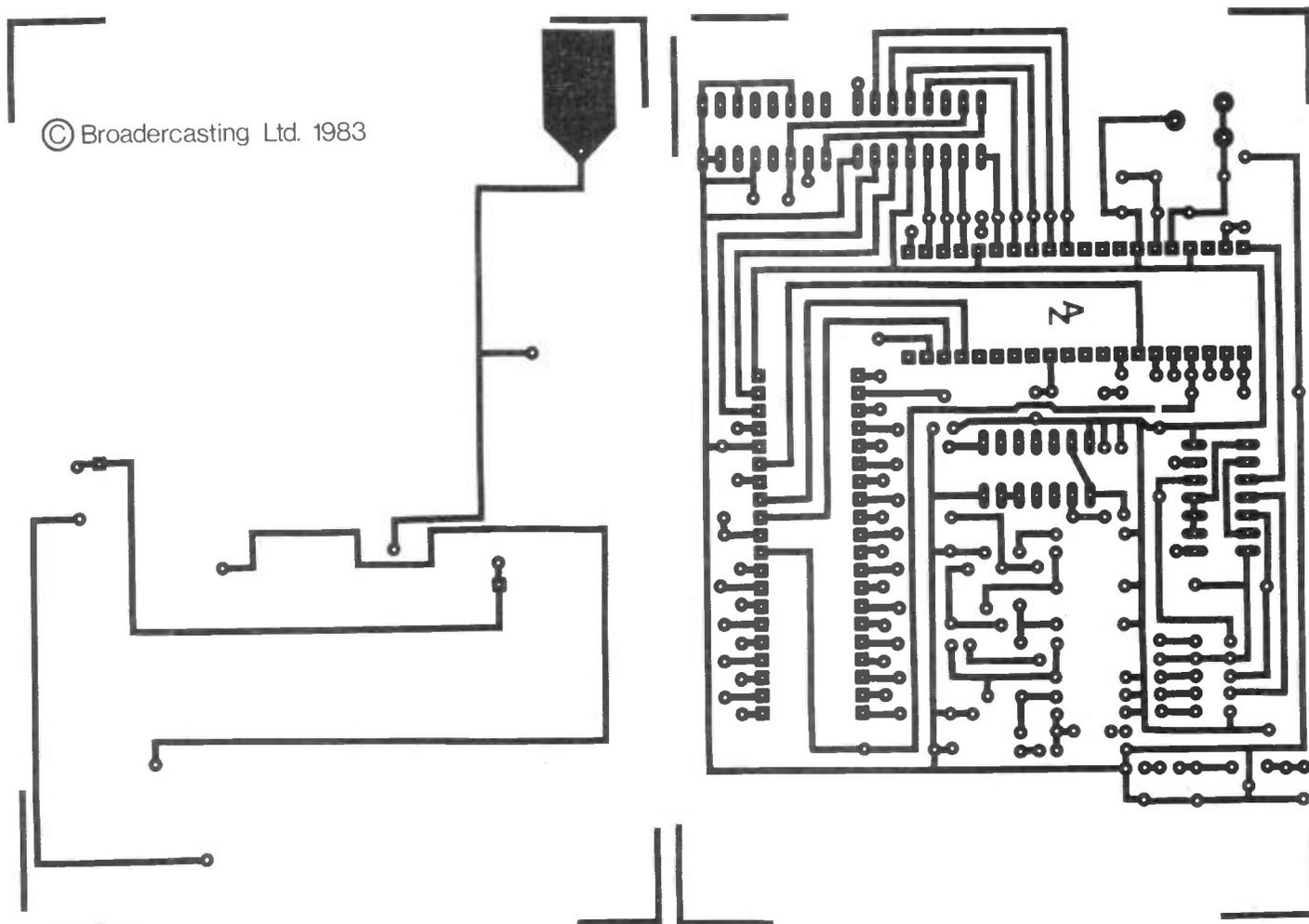


Figure 8b. The two sides of LCD-DFM board (includes pads for 50MHz prescaler).

PARTS LIST (Main Board)

Resistors

R1,2,3,5,6	10k
R4	10M
R7,8	100k

Potentiometers

RV1	min cermet 220k
-----	-----------------

Capacitors

C1	22p
C2	27p
C3	100p
C4	15V tant 200n
C5	10V tant 10u

Semiconductors

IC1	ICM7226A
IC2	4532
IC3	4049
IC4	ICM7231A
IC5	74HC00
IC6	7805

Construction

A double-sided PCB was designed, shown in **Fig. 8b**. Through-board solder-links need to be made at the points marked on the overlay, and the 0v side of R8 should be soldered on both sides as should the common line of the regulator. Please note that the track from IC1 pin 4 to IC4 pin 30 should have a small break in it (this will be explained later). The wire link from the supply has been deliberately included, rather than

using a PCB track, to enable the regulator section to be tested before connecting it to the expensive circuitry.

Veropins were used for all lead connections except the display, and if the daughter board is to be left mounted, insert 8 pins for the switch leads. Sockets were used for the large ICs, and the regulator was mounted with the metal tab in contact with the small PCB heatsink. This is then bolted down

before soldering the pins to avoid strain on the legs. Pin 4 of the 7226 has been left uncommitted for readers who wish to use the other facilities as indicated in the data file. In the prototype this is wire linked to D1 (30) to provide the frequency meter function. This wire link can, instead, be replaced by a PCB track on the component side if desired. If the other facilities are to be used, constructors may like to join the track break mentioned earlier. The

effect of this will be to illuminate one of the annunciator chevrons below the display — the particular chevron changing as the function changes, to show which has been selected.

An SUE switch bank was installed to control the gate times, prescaler switching, (if included) and supply, and a 20mm spaced, three-way bracket was selected because in the future it is possible to change it to a 10mm, five-way bracket, and insert two other switches (for reset, pin 19 to earth, and the enabling of an external oscillator reference for greater accuracy, pin 30 to pin 1 via a diode and 10k resistor). Two BNC sockets were mounted, one for the 1-50MHz preamp, the other connected to the daughter board.

Testing

Test the regulator section, and if +5V appears at the output, switch off, and insert the wire link. Set the trimmer and preset to mid-travel, and switch on again, whereupon the display should light up. Adjust RV1 to get a good contrasting display with no ghosting. The unit may be reading randomly, but by applying a signal to the preamp, input, a stable reading should be obtained. The trimmer is then adjusted to display the correct frequency. Otherwise the 10MHz reference oscillator can be set up by placing the meter next to a receiver tuned to WWV (10MHz), and zero-beating.

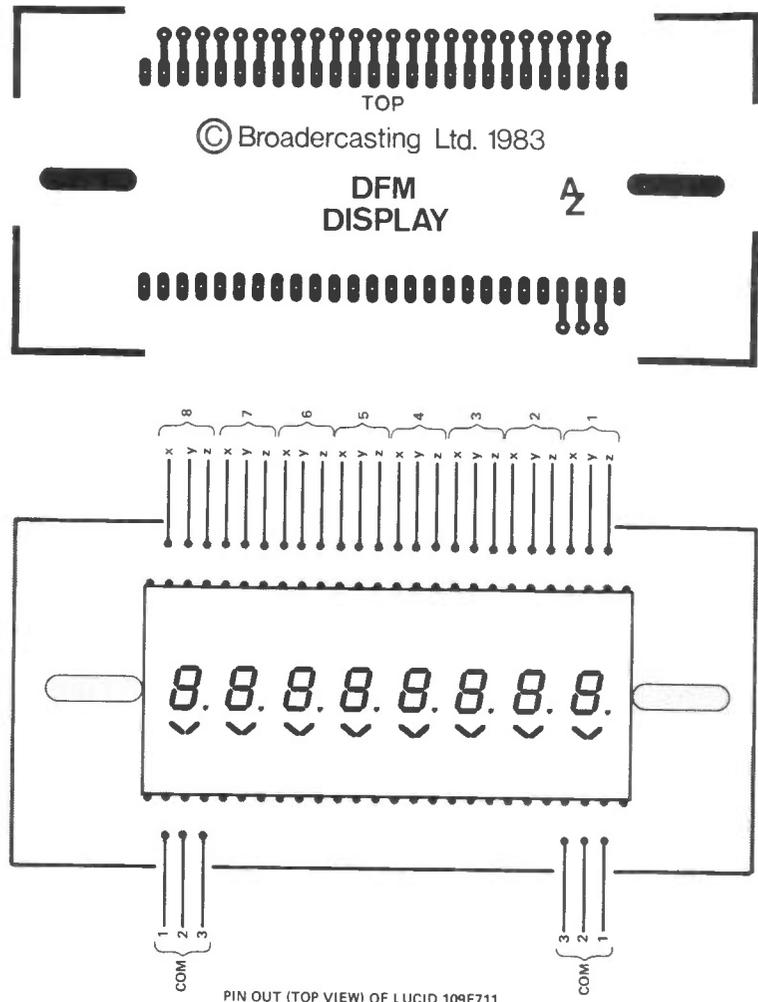



Figure 9. PCB foil pattern (above) and overlay (below) for the 8-digit display.

In Use

The supply switch has a second pole that can be used to switch in an external Ni-Cad charger (with two sockets on the rear panel) when the unit is switched off. This would avoid removing the batteries which can then be stuck down with double-sided sticky pads.

The meter does not display the decimal points simply because to cater for all the possible combinations of prescalers and gate times made the switching far too complicated. A decimal point can be activated by connecting the appropriate digit line to pin 31 of the 7231, normally held low by R6. A pad has been provided on the PCB for this purpose.

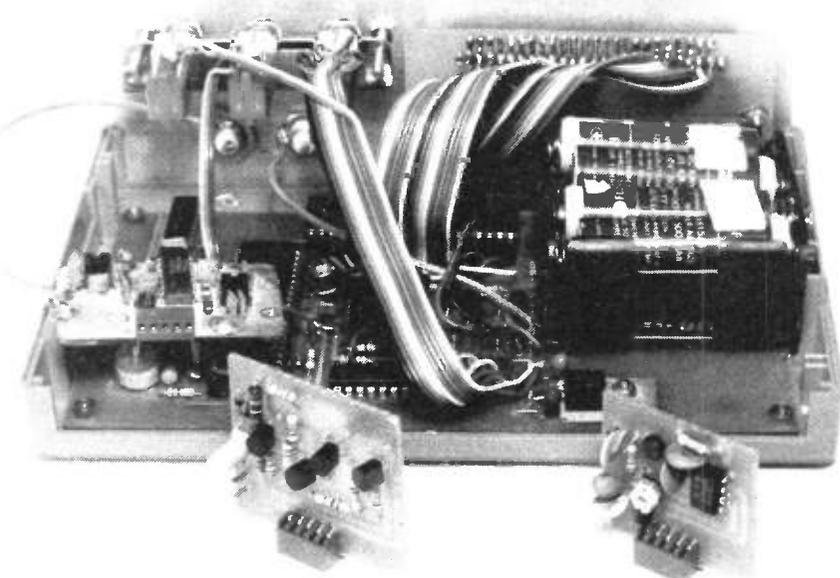My thanks to Alan, G6NXO and Geoff, G6LYE for their help and advice with this project.



The completed Digital Frequency Meter, as viewed from behind the display. The two boards in the foreground are the 200MHz and 600MHz prescalers.

WORLDWIDE

Scientists are constantly expanding our knowledge of space using a wide range of advanced optical and electronic technology. James S.B. Dick looks at some of the hardware employed by such modern-day astronomers.

Archaeological sites such as Stonehenge, the calendars of the Mayas, and Chinese eclipse records dating back to 4000 BC, show that Astronomy was widely studied long before civilisation came to Europe. The bright star Sirius would have been watched until it occupied a certain position in the sky after sunset — the Egyptians then knew the Nile floods were due. Astronomy is still used to compare the motion of the Earth against high-accuracy atomic clocks. Once the heavens had been mapped, simple observations provided knowledge of longitude and latitude on the Earth — of great importance to mariners before the advent of inertial and radio-based navigation systems. However, time and location are again being measured from 'celestial' sources — artificial satellites (such as GOES and NAVSTAR) are now being used to provide time, position and velocity information accurate to microseconds and metres.

While Astronomy has provided mankind with a time system, curiosity about his environment has made him look out at the stars, not with the aim of utilising them in mundane problems, but to explore. Although his interest in the stars may have been intense, man was ill equipped to observe them in an objective, scientific way. Indeed, it is only in recent years that the passion for exploration and observation has been provided for.

The Light Fantastic

The accurate, quantitative measurement of light is called photometry. By measuring the amount of light emitted by a star at different wavelengths, the temperature, approximate size and likely chemistry of that star can be determined.

A telescope is pointed at the star and then the collected light passes through a wavelength-selective filter onto a sensitive detector called a photomultiplier (PMT). Inside, photons from the star hit a cathode made of an alkali metal and eject electrons from the surface layer. The electrons are accelerated to the nearest positive electrode (one of the "dynodes") and collide with its surface. Each electron impact releases more (≈ 10) electrons, which are accelerated to the next dynode and so on. The end result is that one or two of the photons that liberated electrons at the photo-emissive cathode are responsible for an avalanche of perhaps one million electrons onto the anode. Typical anode currents are often quoted as 1 A/uW of incident light — the Sun's intensity is about 200mW/cm² — though the maximum current allowed in the tube is usually about 1mA.

Instead of measuring the current as a function of intensity, the modern technique is "photon counting". With this method, the avalanches caused by individual photons are

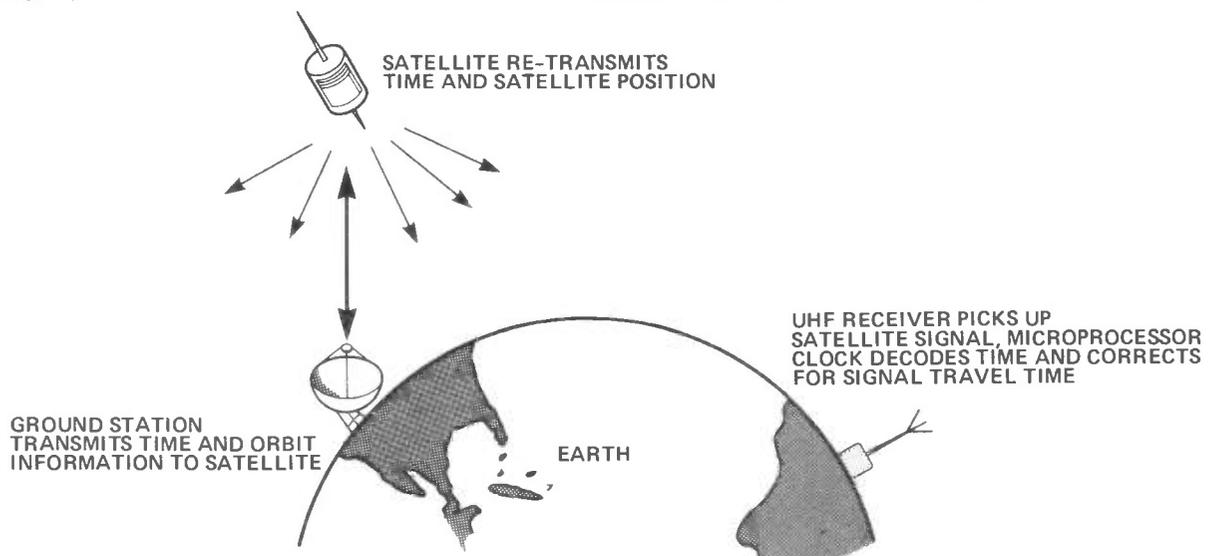


Figure 1. The principle elements involved in satellite time services.

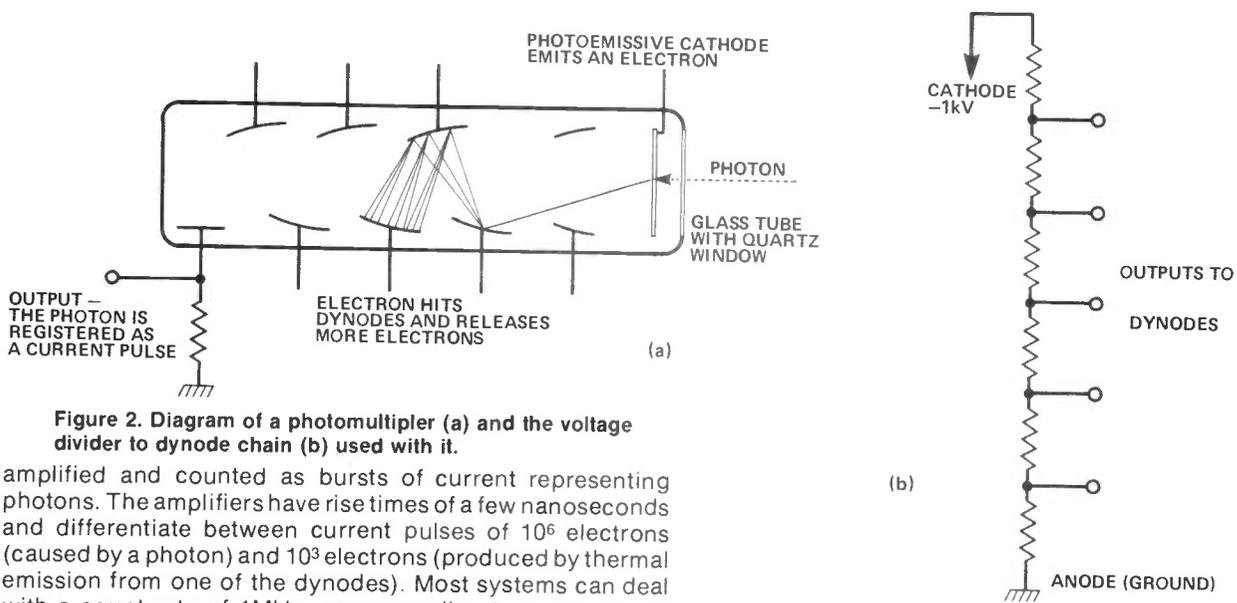


Figure 2. Diagram of a photomultiplier (a) and the voltage divider to dynode chain (b) used with it.

amplified and counted as bursts of current representing photons. The amplifiers have rise times of a few nanoseconds and differentiate between current pulses of 10^6 electrons (caused by a photon) and 10^3 electrons (produced by thermal emission from one of the dynodes). Most systems can deal with a count rate of 1MHz, corresponding to a star on the 'naked-eye limit', seen through a filter (optical passband 200 nm) with a telescope of 1.5m aperture. The pulses are counted by hardware (TTL "HS" series) counters which are read and cleared under computer control. The computer then supplies the astronomer with real-time feedback and stores the data on, perhaps, magnetic diskette and paper "hard-copy" for later analysis. To measure one star in five colours may take twenty minutes — each measurement on the star is normally done twice and the intensity from the sky is measured so that it may be subtracted from that of the star.

While Astronomers can digitise the vast amount of data held on photographic plates, by using a scanning densitometer, it is more convenient to use a two-dimensional electronic detector. The state-of-the-art utility here is the charge coupled device (CCD). These were first invented in 1970 and took only four years to go into production. Although they may be used as analogue delay lines and signal processors, only their optical processes will be discussed.

Essentially, within the CCD, a slab of p-type semiconductor has a matrix of electrodes placed on its top surface. When these electrodes are positively charged, a potential well forms beneath them and free electrons collect as a "charge packet" in the well. If the CCD is exposed to light, electrons freed by the incident photons gradually fill the wells. If a picture is focussed onto the CCD substrate, each well may be thought of as a picture element — the CCD is then an array of such elements. To read out the picture, a process known as charge coupling is used. Looking at Fig. 6, the well under the 10 volt electrode is deeper than the others and will be the site of charge storage. Increasing the voltage on the third electrode to 10 volts will create another well and charge will be shared. If the potential on the second electrode is decreased, the charge packet will be totally transferred. Hence, correctly phased voltages applied to the electrodes cause a movement of the charge packet just beneath the

Worth A Thousand Words

The photometry system just described provides information concerning the luminosity of a point of light. However, galaxies and other "extended objects" are best viewed as a picture. Early observers had to be accurate artists — sketches were made with pencil and paper — until photography took over and became one of astronomy's workhorses. Modern plates may be 30cm x 30cm and show a 6° square of sky, recording objects a million times fainter than the eye can see.

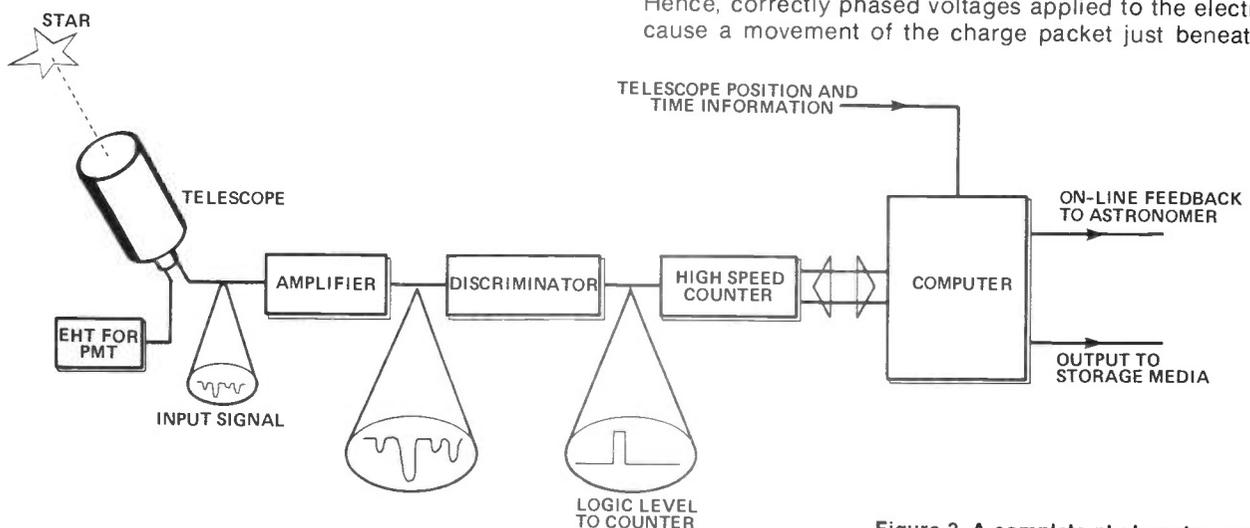


Figure 3. A complete photometry system.

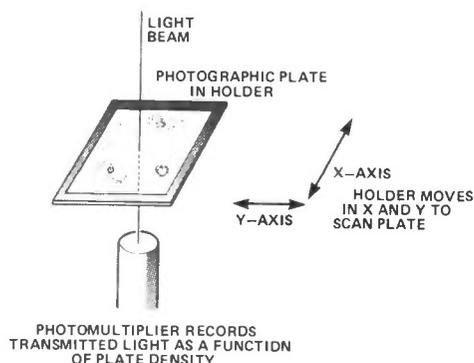


Figure 4. Representation of a scanning densitometer.

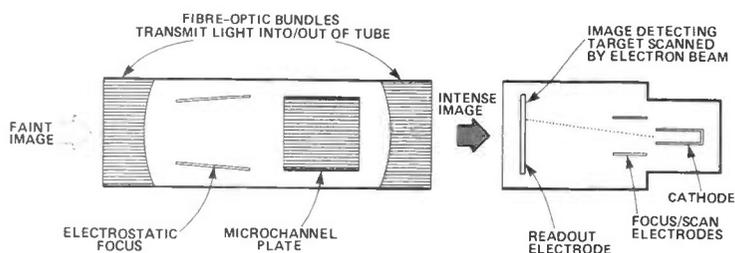


Figure 5. Microchannel plate and Vidicon for focussing and detecting images.

surface of the semiconductor, towards the readout gate. To transfer the picture from the CCD to a computer for analysis, successive rows of electrodes are clocked and their charge packets read out.

CCDs have some faults, however. Thermal emission of electrons is reduced by cooling the chip and irregularities in electrode spacing (typ $\pm 3\%$) are reduced by electron-beam techniques during manufacture. If a well is over-illuminated, more charges are created than can be held in the well. The surplus charges spill into nearby wells (ie, adjacent picture elements) — "blooming" causes a "white out" over a portion of the picture. Front face imaging of the CCD creates problems because of interference and absorption effects caused by the polysilicon surface layer. An alternative is to illuminate the device through the substrate which is chemically thinned to around 10 μ m (spectral coverage from 300 nm to 700 nm is obtained, although manufacturing yield is significantly decreased). Due to the CCD's high efficiency (about 50%) in detecting photons, compared with a photomultiplier, they are an effective tool.

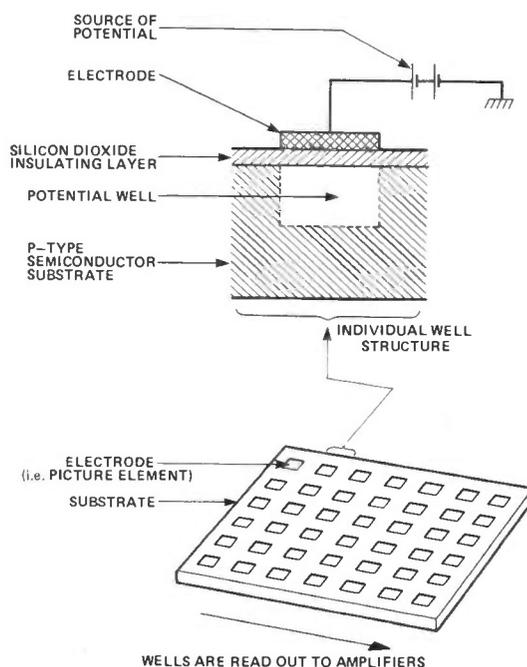


Figure 6. The CCD imaging array, with one cell enlarged to show electrode connections.

In order to guide the telescope onto a faint object, intensified TV systems are commonly used. A single stage microchannel plate intensifier is placed in front of a vidicon. Here, the image falls onto a fibre-optic bundle, whose other end is a photosensitive cathode. An electrostatic lens focusses the emitted electrons from the cathode onto a bundle of hollow glass tubes (a few microns in diameter), whose insides have a dynode-type effect. The accelerated electrons exit from the microchannel plate and hit a phosphor where they generate light. This is carried down another fibre optic bundle to the front surface of the camera tube. The image, intensified typically by a factor of 10,000 is then televised in the normal way and fed to a monitor in the telescope control room.

Drives, Encoders And Trackers

In addition to detecting objects, it is necessary to access and track them. The position of stars in the sky is defined in terms of "right ascension" and "declination" — the celestial equivalent of longitude and latitude on the Earth. The telescope is moveable in the two axes of right ascension and declination. One method of determining the telescope position is to mount absolute encoders on the drive shafts. These are circular discs, optically encoded with information (usually in Gray code). Gray code is similar to binary except that one bit changes at each increment or decrement. While absolute encoders are large and expensive, the telescope's position is defined mechanically and is therefore non-volatile.

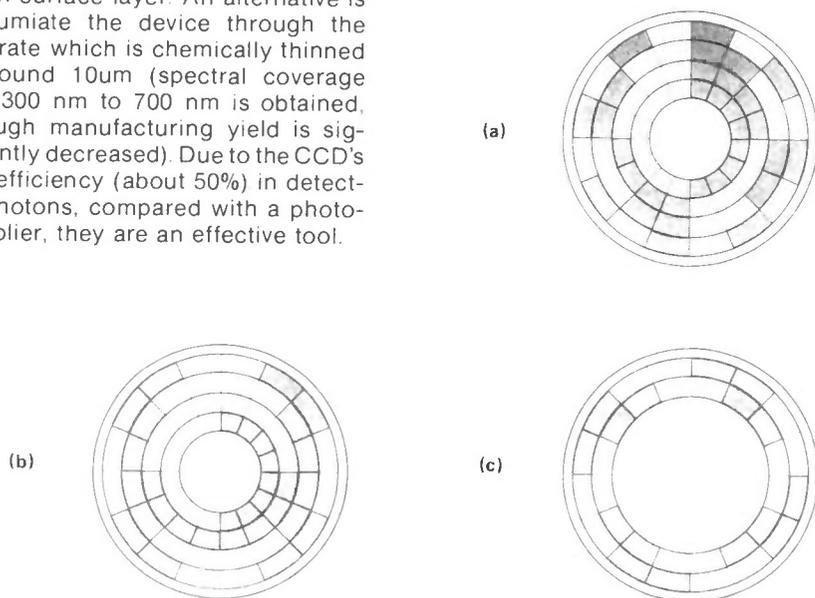


Figure 7. Digitising reference discs, absolute encoders for Binary (a) and Gray codes (b) and an incremental system (c) encoder disc.

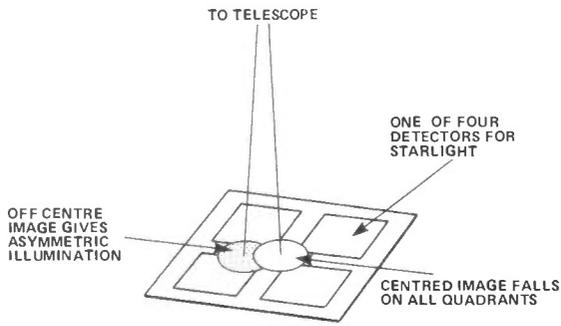


Figure 8. A quadrant star tracker.

Incremental encoders, with a resolution of 48,000 steps per resolution, — an accuracy of ± 0.0075 degrees — can be obtained at less cost and are physically smaller (15cm diam x 10cm deep). The position of the telescope is initially determined from a datum point and the subsequent pulses from the encoder's detector are used to alter that position.

Noise is a frequent cause of problems — encoder pulses are missed by the counters or spurious spikes add phantom pulses. The encoder system has to be kept on continuously if minor movements of the telescope, while parked, are to be counted. Once the telescope has been 'sighted' on a star, the drive system has to be capable of keeping the star in the centre of the field-of-view. While an accurate drive rate helps, the effect of telescope flexure and atmospheric refraction tend to decentre the star. The cure is to use an electronic eye as direct feedback — the Star Tracker. Light from a star (frequently a nearby star) is taken to a crude two dimensional detector; the simplest case may only have four picture elements. If the star is centred, equal quantities of light will fall into the quadrants — any asymmetry is monitored by the telescope control computer which then corrects the drive rate accordingly.

Earlier trackers used a single detector (photomultiplier, perhaps) with a chopping vane to segment the image into halves — the amplitude of the resultant AC signal being the feedback mechanism. More sophisticated trackers use the video output from the aforementioned acquisition camera. The video lines, corresponding to the centre of the field, display the star's profile in two dimensions.

Telescope drives were originally clockwork — a falling weight and governor linked to gears. Later, electric motors

were used and their rotation monitored by a tachometer, whose output controlled the supply to the motor in a servo-loop. Even some small (0.5m aperture) telescopes are driven in declination — speed is not critical here because motion is only involved when moving between stars or for minor tracking adjustments. Continuous tracking is not required because the stars "move" only in right ascension axis.

Modern telescopes depend upon stepper motors, which move through a fixed angle each time a pulse is applied. The rate is simple to control via digital electronics, as it is directly proportional to the applied pulse rate. Stepper motors are expensive however, so synchronous motors are often used, particularly by amateur Astronomers. These are similar to stepping motors except that they are designed to run at a fixed frequency — typically $\pm 10\%$ variation is allowed. A standard, small synchronous motor may run at 250 RPM for 50 Hz input and 300 RPM for 60 Hz. However, the necessity of a mains supply often prevents the amateur from taking his telescope into the country in search of dark skies. One solution is to run an inverter from a 12 volt battery. The frequency of the inverter is derived from a crystal oscillator and long-term tracking can be excellent. A variable track speed is provided by a frequency synthesiser — a multiple of a fixed frequency being derived from a voltage controlled oscillator. The output frequency is given by $n \times f_{CLK}/10^4$. An alternative to the synthesiser is the pre-settable down-counter. A counter is made to count down from an all-zero condition to a value, m, which is selected by thumbwheel switches. The output is given by

$$f_{OUT} = f_{CLK}/(M-m),$$

where M is the maximum counting value plus one. This is fed to a flip-flop to produce a symmetric signal to the inverter transformer. **Table 1** shows that reasonable linearity between m, the dialled frequency, and f, the actual frequency, is obtained over a $\pm 20\%$ range centred on 50Hz.

Switch-selected value	Output frequency (Hz)
2500	33
3000	35
4000	42
5000	50
6000	62
7500	100

Table 1. Comparison of dialled frequency, m, and actual frequency, f.

A Brighter Future

The technological future for astronomy is bright. Improvements in CCD technology will provide better photon detection efficiency and reduce the flaws. Multiple mirror telescopes — their many surfaces accurately controlled by multiprocessor servo-loops — will let astronomers view fainter and therefore more distant objects. The increased use of accurate telescope control systems on all sizes of telescopes ensures quicker object - acquisition and eliminates the many minutes often spent searching for stars. Once the telescope, and the instrument it carries, are computer controlled, the observer may sit in a control room — perhaps several thousand kilometres away — and run his experiment. No more will there be the need for long journeys to observation sites. The increased output from Earth-bound telescopes and space-borne instruments is rapidly expanding mankind's knowledge of the universe.

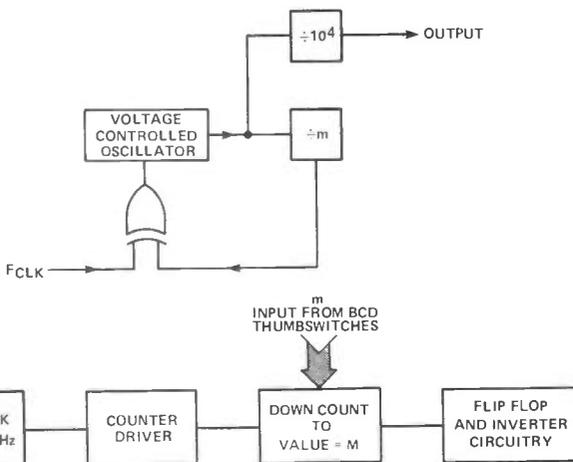


Figure 9. Basic frequency synthesiser and down-counter block.

FRG7700

MEMORY EXPANSION



John Mills describes a modification to considerably increase the FRG7700's memory facilities

Many users of the FRG7700 receiver from Yaesu must have at some time thought of buying the optional memory unit, but may have been dissuaded by the high cost of the Yaesu version. Owners with the unit already fitted will probably have wished for more than the present 12 memory channels. For both of these reasons the author decided to look more closely at the workings of the 'black box' to find a suitable solution.

and bandswitch positions are 'read' and converted into digital data.

2. When the 'memory write' button is selected this data is stored in ICs Q30-35.

3. When 'memory read' is selected, the unit examines the stored data, and using its own internal PLL VFO, it generates the same VFO and frequency band information as was originally manually selected. At the same time, the settings preset on the main VFO and bandswitch are disabled.

The memory ICs used in the unit are 256 x 4 static random access units. Up to 256 data locations are available via the address inputs A10 to A17 (J02). As will be seen from diagram 2, the memory switch S5A/B selects various address combinations up to a max of only 12.

Herein lies the key to this article, replace S5A/B with a 40 way CB type switch and you have instant access to 40 memory channels. Although this does not change the initial purchase

cost of the unit, it does reduce the cost/memory channel from around £7.50 to £2.25.

At this stage the following points should be considered before proceeding further:

1. Extensive dismantling of the Rx is required and
2. Any warranty claims may be invalidated.

Step By Step

To fit the new switch follow the steps carefully and do not miss out any:

1. Disconnect the Rx totally from the AC mains.
2. If a memory unit is fitted remove from the Rx. Take care when removing the plugs, they are all numbered but pull on the body not the wires to remove them.
3. Remove the top/bottom covers. (Disconnect the plug to the backup battery holder).
4. Disconnect all connections to the main PCB — PB2169. Again take care

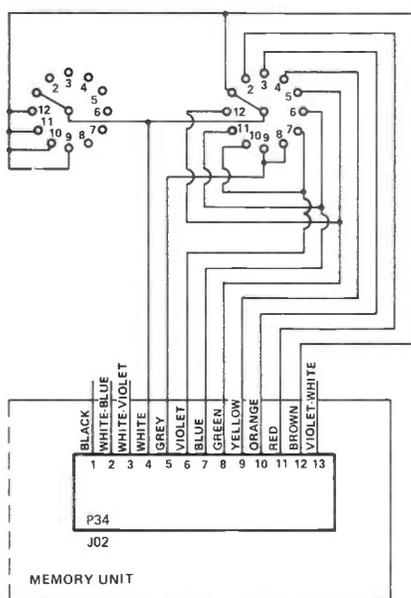


Figure 1: Existing memory switch wiring.

Rx Operations

The FRG7700 is not computer controlled — and this explains the relative complexity of the memory unit. It is not the intention of this article to go into complex electronic descriptions (see the feature published back in December 81/January 82 for more specific details of both the FRG7700 and the Trio R1000), but in essence however operation is as follows:

1. The manually set VFO frequency

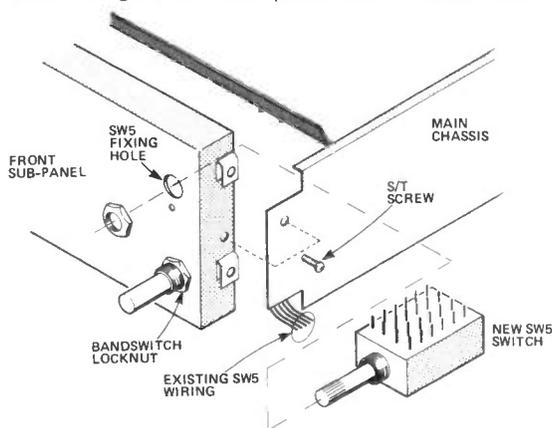


Figure 3: Wiring of new memory switch.

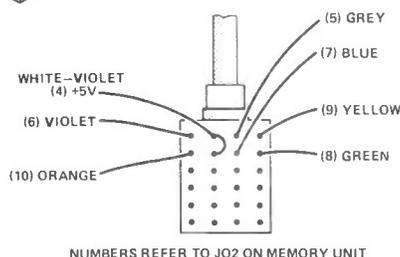


Figure 2: Exploded view of receiver chassis.

NUMBERS REFER TO J02 ON MEMORY UNIT

to pull the plug bodies not the wires. Two wires from the backup battery must be unsoldered from the main PCB — note carefully the polarity and location of these connections.

5. The frequency display is supported by a foam backed metal plate secured by two screws, remove this panel and screws carefully. Remove the small PCB with the AM/PM LEDs held by a S/T screw to the left of the display.

6. Remove all front panel knobs. These simply pull off except for the VFO tuning knob and band select knob which are held by small grub screws. Note the position of the band selector knob as this is not indexed on the shaft. After removing the VFO knob, remove the small X-head screws exposed underneath to remove the plasti-chrome skirt.

7. Remove the main PCB, take extra care not to damage the vacuum fluorescent frequency display, easing the main PCB gently back and upwards.

8. Remove the front panel by removing the two top and two bottom CSK screws.

Now it gets trickier.

9. Refer to **Fig. 2** and remove the locknuts on the band select switch. Remove the S/T screw holding the R/H side of the front sub-panel to the main chassis.

10. Undo the locknut on S5 (diagram 3).

11. Carefully push S5 back out of the front sub panel as far as it will go. S5 will probably be restricted by a cable

harness strap which is fitted to the bush of S5. If S5 cannot be removed easily, carefully unwrap the harness to release the wiring loom. At this point it may help if the front sub panel is carefully separated from the main chassis by one or two inches max. (See **Fig. 2**).

12. As the wiring to S5 runs up from below the chassis, ease the switch and wiring out and through the gap between front and main chassis panels.

13. Refer to **Fig. 1** and check the colours shown against P34 (pins 4 to 12) from the memory unit appear on S5. If your Rx has different coding to that shown then write in your own colours to correspond with **Fig. 1**. Remove all wires to S5. The wires from A16 and A17 are not used and should be stored within the main cable harness.

14. Enlarge the hole previously occupied by S5 to 9MM. Be careful not to allow metal drillings to fall in the Rx.

15. Wire the switch as shown in **Fig. 3**.

16. Carefully fit the switch into S5 position ensuring the pins are upwards and that the lug on the switch locates into the existing location. Fit the washer and locknut provided and tighten carefully.

17. Re-assemble the Rx in reverse order to the previous steps.

18. Check correct operation before fitting any existing memory unit.

19. Refit memory unit and check operation is as before.

The receiver now provides 40 switch selected memory channels. Some of the new switch positions may line up with the existing front panel markings

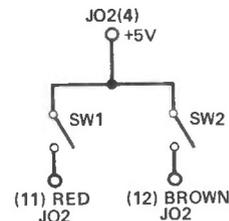


Figure 5: Switch wiring for 120 channel expansion.

but with frequency readout available the lack of 40 marked positions should not prove a problem. For the more adventurous reader, the memory can be expanded by a further 120 (3 x 40) channels if required. Refer to **Fig. 5** for wiring details. In this requirement the two unused address lines A16 and A17 are connected to $\pm 5V$ by switches to select further memory locations. Some mental ability is required, with S1,2 'off' 40 frequencies are selected by S5. Switch on S1 to select a further 40, S2 a further 40 and lastly both S1 and S2 together to provide the last 40. Taking the full 160 channel capability this reduces the cost/chan down to 56P.

The author would like to thank Alec from Amcomm Services, Harrow, for the loan of a memory unit to aid this article. Amcomm also state that they will honour any warranty claims on Rx's bought from them that have the above mods fitted.

Note: The only part required for this conversion is S5, the SRS 303UCB switch.

■ R&EW

R&EW PANEL SIGNS

Giving that professional look to the front panel of your latest creation can be a bit of a problem.

Dry rub down lettering can be used for control markings and scales but unless used with skill the results can be less than flattering.

The R&EW label system solves the problem by providing a set of symbols and scales that are printed on the reverse side of a thin, clear plastic sheet.

Identify the word/symbol you require, cut around it, peel the backing paper off and stick it in place on your project.

The results are perfect every time.

Three different sets of panel markings are available, black wording, white wording and a set of scales.



The wording sets contain over 1000 words covering 300 terms — the dial set contains one large horizontal tuning scale, frequencies and 12 control panels.

Any one will cost you only £1.50, but buy two and we'll give you the third one free that's just £3.00

for the complete set of R&EW Panel Markings.

All prices include VAT and post and packing.

Send your order to:
R&EW PANEL SIGNS
117A High Street
Brentwood
Essex CM14 4SG

VOLUME SWELCH RF GAIN

MEMORY AND PERIPHERAL INTERFACING

Continuing the second lesson of the Zilog Z8000 course, we introduce aspects of hardware design and timing circuits. The lesson concludes with some questions on all the material covered.

HARDWARE DESIGN CONSIDERATIONS

Memory Refresh

In the case of dynamic devices, memory interfacing requires correct setting of the refresh register: enable bit on and rate large enough. The LDCTL instruction, executable in system mode, allows refresh to be loaded from one of the Z8000's 16-bit registers. A hexadecimal value of 9E00 will produce refresh each 60 clock periods which, at 4MHz, will satisfy the worst-case needs of typical 16K dynamic RAMs. The table below lists the delay in clock cycles between refreshes for other possible refresh register values. Recall that bits one through eight hold the row value, and nine through fourteen hold the rate.


		LOWER NIBBLE OF UPPER BYTE															
		0	1	2	3	4	5	6	7	8	9	A	B	C	D	E	F
UPPER NIBBLE OF UPPER BYTE	0	NO REFRESH															
	1	NO REFRESH															
	2	NO REFRESH															
	3	NO REFRESH															
	4	NO REFRESH															
	5	NO REFRESH															
	6	NO REFRESH															
	7	NO REFRESH															
	8	256	4	8	12	16	20	24	28								
	9	32	36	40	44	48	52	56	60								
	A	64	68	72	76	80	84	88	92								
	B	96	100	104	108	112	116	120	124								
	C	128	132	136	140	144	148	152	156								
	D	160	164	168	172	176	180	184	188								
	E	192	196	200	204	208	212	216	220								
	F	224	228	232	236	240	244	248	252								

		UPPER BYTE								LOWER BYTE							
		UPPER NIBBLE				LOWER NIBBLE											
E	RATE	ROW ADDRESS								0							
		AD ₉	AD ₈	AD ₇	AD ₆	AD ₅	AD ₄	AD ₃	AD ₂	AD ₁	AD ₀	AD ₁₅	AD ₁₄	AD ₁₃	AD ₁₂	AD ₁₁	AD ₁₀

Figure 15
Refresh Control Register

Memory and I/O Spaces

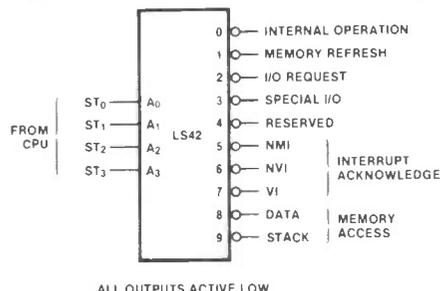In order to segregate memory and/or I/O spaces, the ST3:0 lines must be decoded. The simplest needs can be satisfied by decoding the first ten ST combinations. This precludes distinguishing program stack and data stack memory or running slave operations unless further decoding is added.



ALL OUTPUTS ACTIVE LOW

Figure 16
ST 3:0 Decoding

Address/Data Bus Design

Another system requirement is proper *buffer design* between the Z8000 and external memory, peripherals, or other Z-Bus devices. It is sufficient to point the data bus toward the processor *only* during read operations and to float it during acknowledged bus requests.

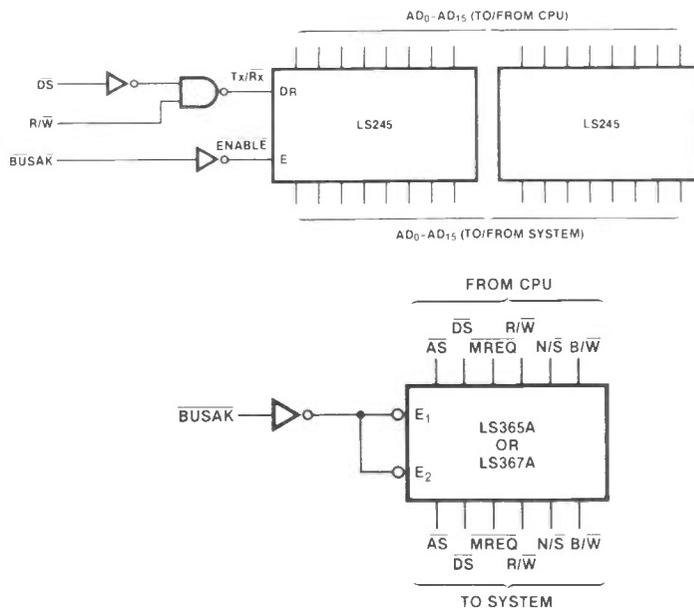


Figure 17
Buffering Address/Data
and Status Signals

The status buffer shown will need pull-up resistors on both sides.

Demultiplexing addresses from the AD15:0 lines can best be accomplished with transparent latches when designing with standard memories. \overline{AS} , as intended, provides the latching signal and \overline{BUSAK} must be observed.

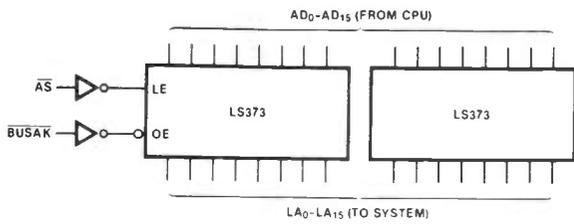


Figure 18
Address Latches

Multiplexing Latched Addresses into 16K x 1 RAMs can be accomplished by synchronizing \overline{MREQ} to the CPU clock and then feeding the address bits alternately to the seven chip-address inputs during row (RAS) and column (CAS) address times defined by the circuitry shown below. The 16th address bit is used to select alternate banks of 16K words, if needed, while the lowest bit controls CAS to byte banks within each word bank.

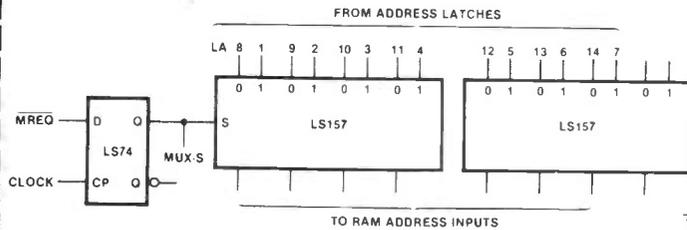


Figure 19
Address Multiplier

RAS and CAS generation can be achieved in several ways. The scheme below continues the logic given above to generate row and column selects compatible even with slow 16K RAMs. It also produces an optional \overline{WAIT} output and properly utilizes A0 only for byte writes.

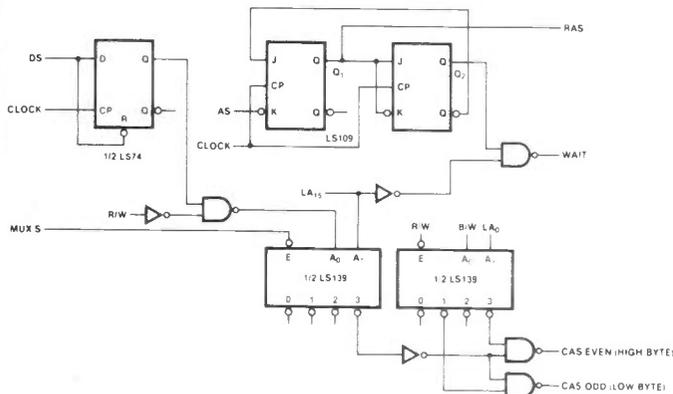


Figure 20
RAS and CAS Generation

There is another, more natural alternative, using Zilog 6132, 4K x 8 pseudo-static RAMs (See Fig. 21).

Any attempt to segregate memory spaces using the ST outputs must carefully consider the particular setup, access and other times crucial to proper operation of the memory devices selected. It may, for instance, be necessary to delay \overline{AS} to these devices so that control circuitry has adequate time to enable and disable appropriate memory areas, according to the desired partitioning.

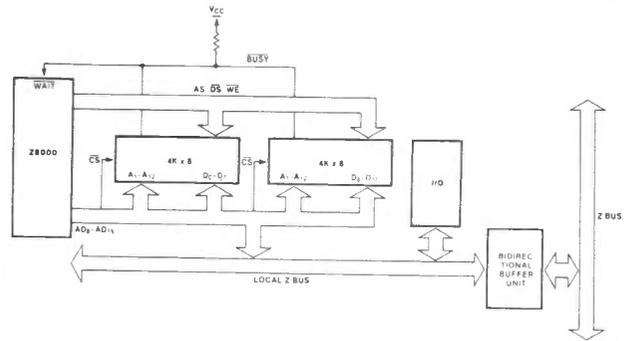


Figure 21
Z8000 - 6132 Interface

The \overline{STOP} Input

The \overline{STOP} input is a useful feature of the Z8000 apart from slave processing. A single-step circuit can, for instance, be designed.

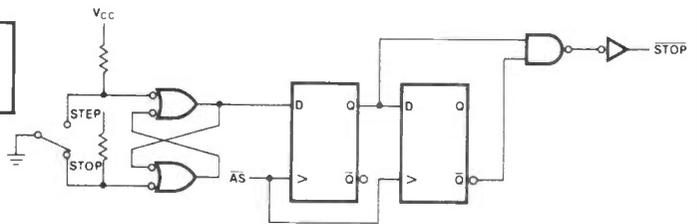


Figure 22
Single-Step Circuit

\overline{STOP} currently puts the processor into a continual (rate insensitive) series of memory-refresh cycles. This increases heat dissipation in memory devices for the duration of the \overline{STOP} . The debounced input is latched in the first flipflop by \overline{AS} while the second flipflop remembers the complement of the last switch position. This guarantees a low on \overline{STOP} during T3 of each instruction's final machine cycle, as required by the Z8000's \overline{STOP} timing (See Fig. 24).

The Clock

Finally, the clock circuitry shown in the previous lesson can be filled out to include both Z8000 and TTL drive capability.

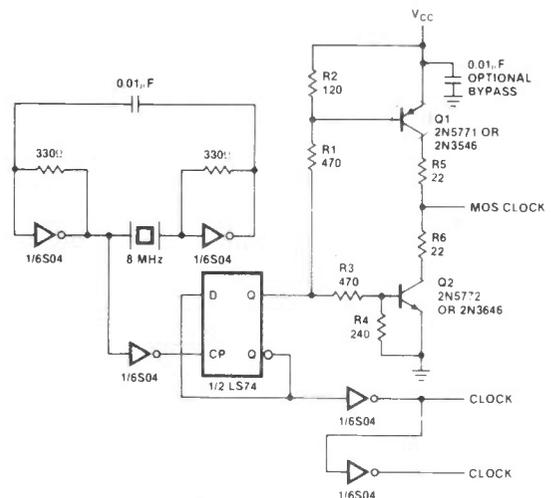


Figure 23
Clock Driver Circuitry

It is worth noting that the Z8000, like most MOS processors, will accept higher than nominal clock rates at higher supply voltages. This can be useful in critical

applications where the speed advantage at a higher voltage outweighs the power dissipation penalty.


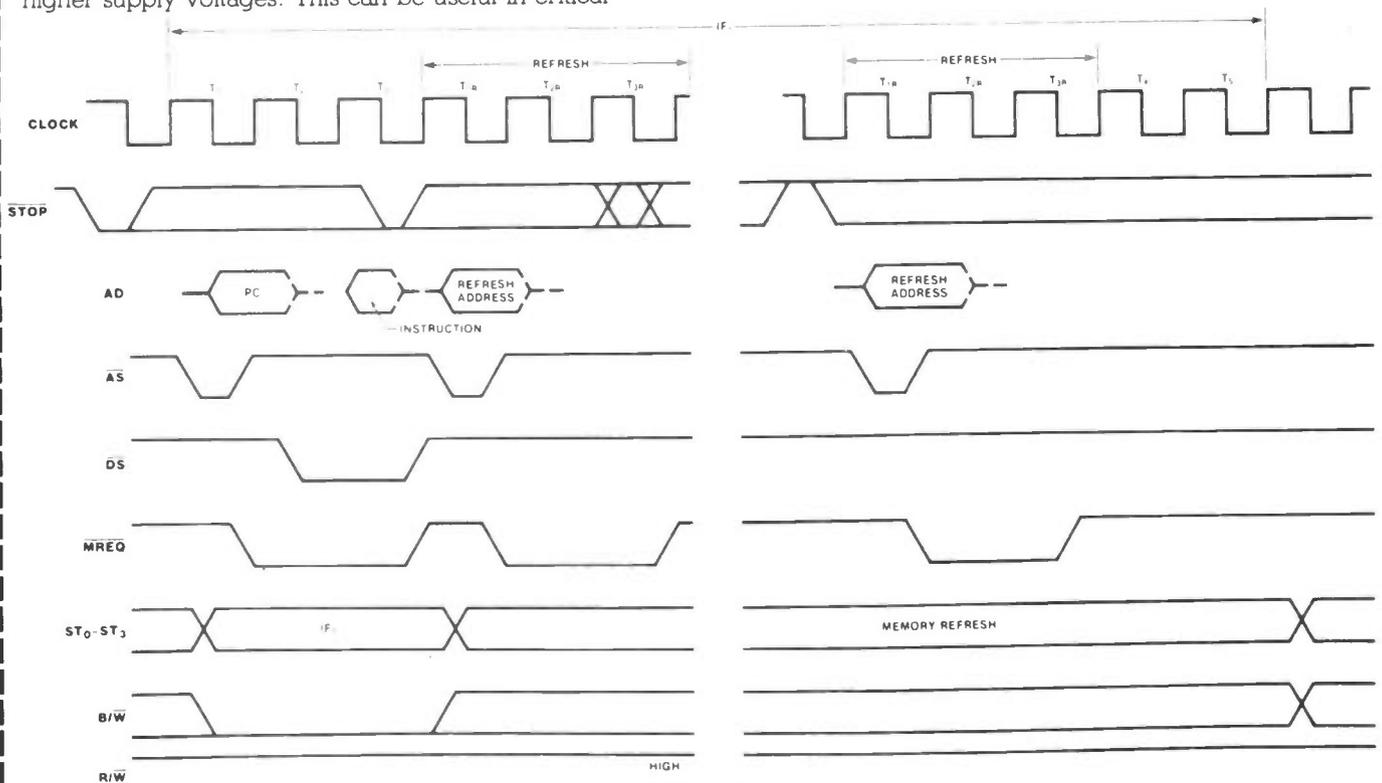
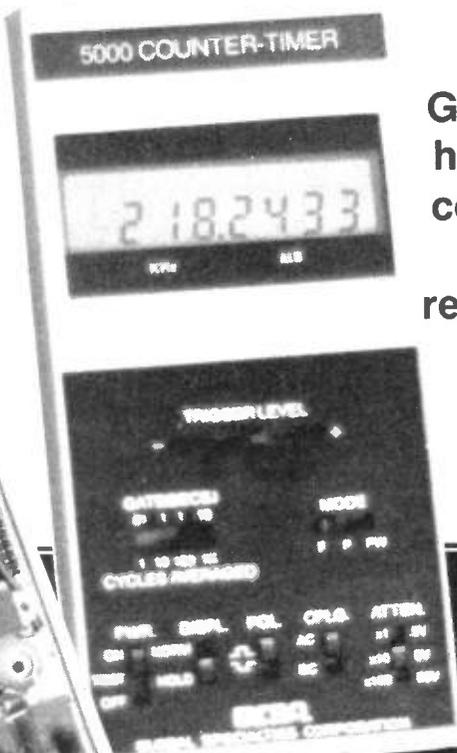


Figure 24
STOP Timing

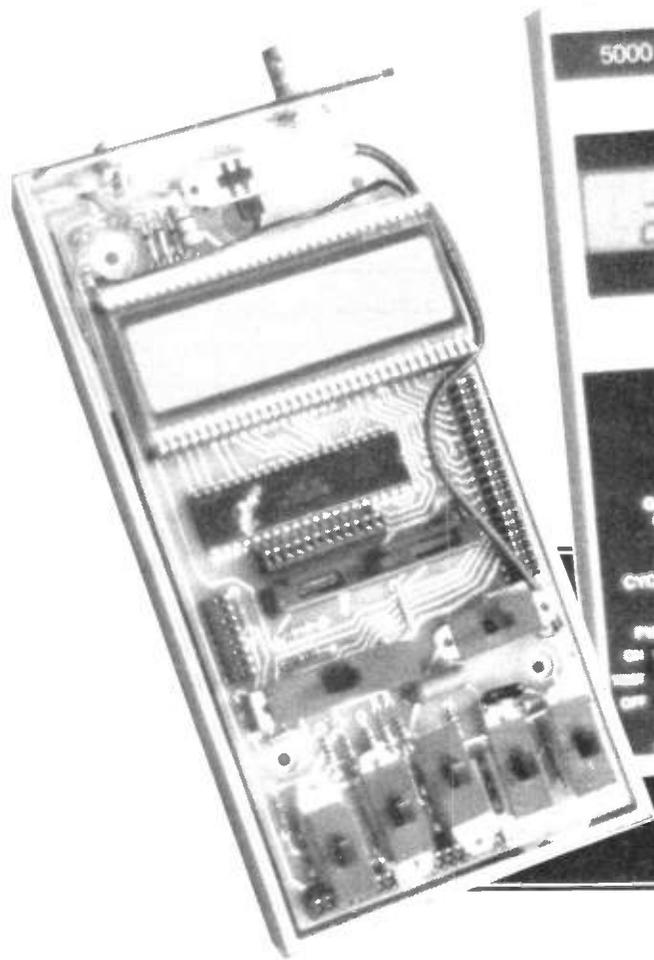QUESTIONS

- The CPU clock is not one of the primary Z-Bus signals because:
 - A. Memory and I/O transfers are not synchronous to system clock.
 - B. Address strobe synchronizes address emission and latching during memory and I/O accesses.
 - C. Data strobe synchronizes data transfer and latching.
 - D. All of the above.
- Proper memory access demands that a memory controller look at least at which of these signals?
 - A. \overline{AS} and \overline{DS}
 - B. \overline{AS} , \overline{DS} and R/\overline{W}
 - C. \overline{AS} , \overline{DS} , R/\overline{W} and B/\overline{W}
 - D. \overline{AS} , \overline{DS} , R/\overline{W} , B/\overline{W} and $A0$.
- Bus direction in Z8000 systems should be determined with R/\overline{W} and \overline{DS} so that the bus normally points:
 - A. Toward the Z8000 except during read cycles.
 - B. Toward the Z8000 except during write cycles.
 - C. Away from the Z8000 except during write cycles.
 - D. Away from the Z8000 except during read cycles.
- The ST lines by themselves can be used to create as many as:
 - A. Six memory spaces
 - B. Three memory spaces
 - C. Five memory spaces
 - D. Four memory spaces.
- Which one of the following statements is true?
 - A. In order to work on a Z-Bus system, peripherals *must be* word organized.
 - B. Peripherals used on a Z-Bus system *must be* byte organized.
 - C. On a Z-Bus system peripherals *may be* byte organized if they read from and write to the appropriate half of the bus according to $A0$.
 - D. On a Z-Bus system peripherals *may be* byte organized if they read from and write to the appropriate half of the bus according to \overline{AS} .
- Which of the following is *not* one of the basic cycles of which all Z8000 instructions are composed?
 - A. Memory
 - B. I/O
 - C. Execution
 - D. Internal
- The time that memory and peripherals have to respond before data strobe goes away can be extended by pulling the:
 - A. \overline{WAIT} line low
 - B. \overline{STOP} line low
 - C. \overline{BUSRQ} line low
 - D. $ST3:0$ lines low
- By using the N/\overline{S} and ST lines, as many as six memory spaces may sensibly be distinguished by a Z8000 system. How many I/O spaces can be distinguished?
 - A. Six
 - B. Four
 - C. Three
 - D. Two



GSC recently launched a hand-held DFM/Timer to complement their bench-top range. Robert Aldy reports on its capabilities as a field instrument.

5000 COUNTER/TIMER

One of the most useful pieces of test equipment, in addition to an oscilloscope, is a frequency meter/counter-timer. There are many DFM's on the market, but they are mostly designed for lab use only. Even the so-called 'portables' are usually bench types with the addition of a battery pack. Not so the latest model from Global Specialities corporation — the hand-held

5000. Its small size and battery power pack (Nicaid or alkaline), make it ideally suited to general purpose field applications as well as for lab use (an AC adaptor/nicaid charger is available as an option).

Functions And Displays

The 5000 provides for measurement of frequency, period and pulse width. All the controls are slide switches, with the exception of the trigger level control, which is a slide pot (more of this later). These switches select input attenuation, AC/DC coupling, trigger polarity, normal display or hold, mode

and gate time.

The centre position of the power switch selects a self test function. This tests the internal logic against the meter's crystal reference and a table included in the manual shows the reading the meter should indicate when self testing. The manual also goes into some detail to describe how to calibrate the meter against an external reference.

The display is an eight digit 0.43" LCD type. The contrast between figures and background is good and easy to read. In addition, the display also includes annunciators to indicate over-

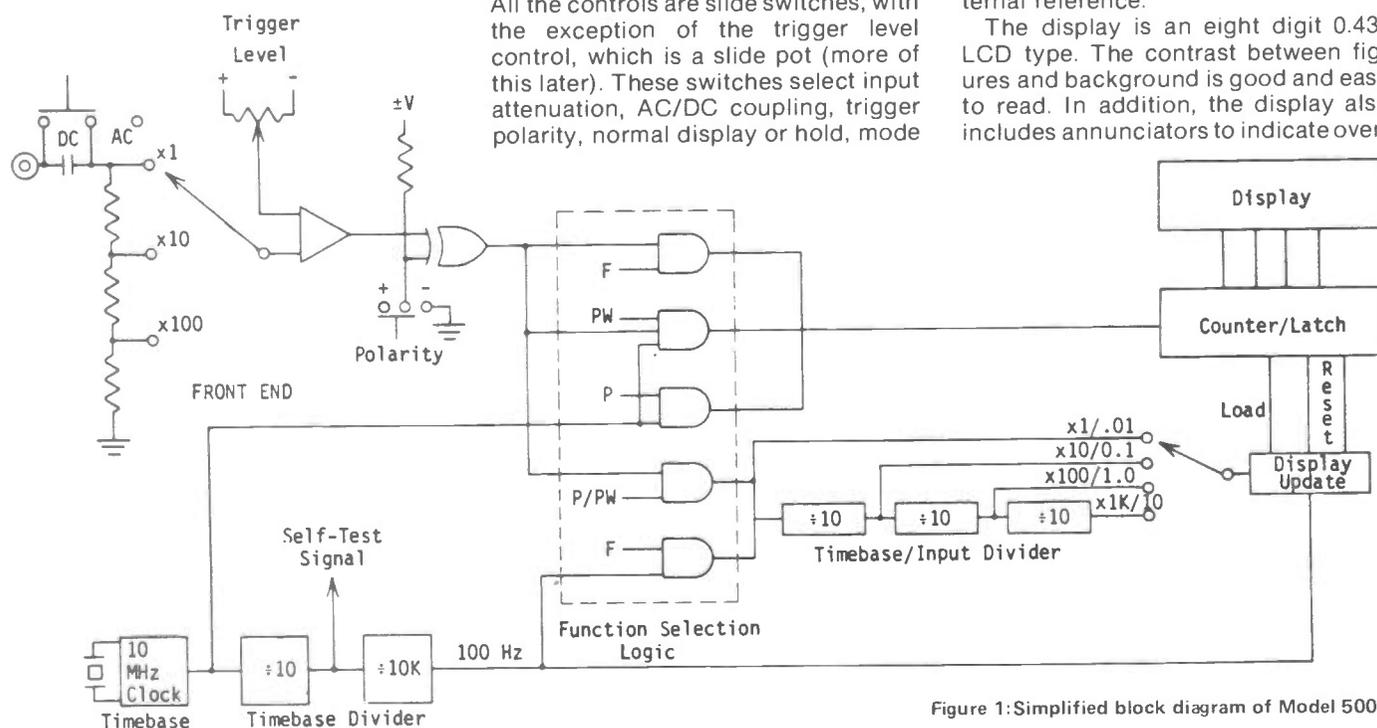


Figure 1: Simplified block diagram of Model 5000.

flow (OFL), low battery (BATT) and GATE. In frequency mode, 'GATE' indicates that the instrument is in the process of counting, whereas in period and pulse width mode it comes on when the signal has crossed the trigger threshold and goes off after the selected number of cycles have been completed. A pulse stretcher circuit on the GATE annunciator allows it to be used to set up the trigger level even on narrow pulses.

Frequency measurements are quoted at 0.1Hz to 40MHz, but typically extend to 50MHz. The resolution permits displays from 100Hz to 0.1Hz depending on the selected gate period (0.01, 0.1, 1 or 10 seconds). Irrespective of the gate setting, the frequency is always displayed in kHz. For fast, accurate measurement of low frequencies it is far better to use the period mode, and converting the result to frequency by invoking the reciprocal (ie, $f=1/T$).

Measurement Modes

In the period mode the 5000 measures the time over which the signal is above the trigger threshold of the input. This period measurement can be averaged over 1,10,100 or 1000 cycles depending on the setting of the gate switch. Periods from 50ns to 10 seconds are possible, but the time is always displayed in microseconds, making it a little inconvenient to read when measuring long periods. The pulse width mode measures the mark time or space time of the input signal depending on the position of the polarity (slope select) switch. Measurements range from 25ns to 10 seconds and as in the period mode the average can be taken over 1,10,100 or 1000 cycles. Again, time is displayed in microseconds. In all modes, resetting

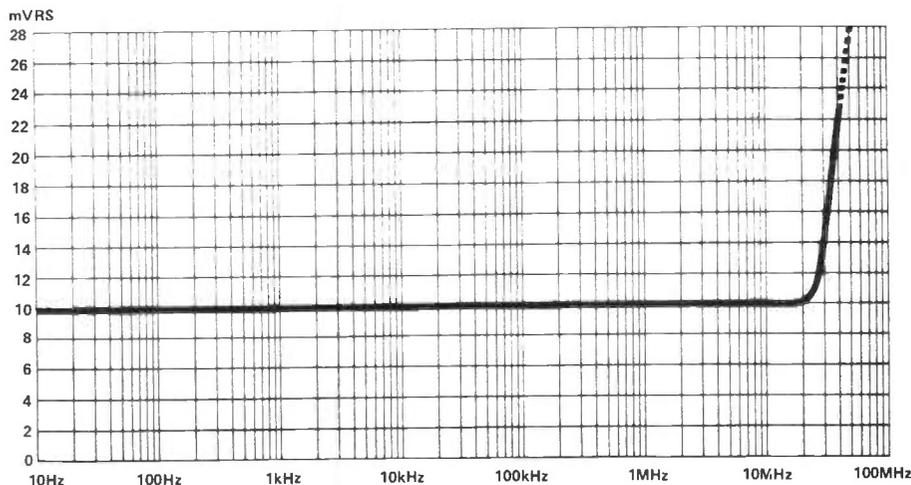


Figure 2: Sensitivity versus frequency—sinusoidal input.

the meter can be achieved at a given time by switching over and back any of what the manual calls 'the Master Reset functions', namely gate, mode or polarity.

In addition to the three primary modes, the display can be set to "NORMAL" or "HOLD". Generally, the 'Normal' position will be used and in this case the display is updated continuously. The time between the end of one count and the start of the next being a constant 230mS which-ever range is used.

The 'Hold' position provides a useful addition to the basic functions. It allows for the measurement of a signal over a single gate period; the display is then held indefinitely until a reset is applied. This means measurements can be made of random or infrequent signals and, in fact, the meter can be left unattended to record the next event.

The trigger polarity and AC/DC coupling functions are self explanatory.

Input attenuation can be switched between x1, x10 and x100 and is used to prevent the 5000 from being overdriven. It also effectively expands the range of the trigger level control. The input is overdriven when the attenuated signal is greater than $\pm 0.5V$ (DC plus AC peak). Thus the maximum input signal that can be applied before overdriving is $\pm 50V$, achieved with the attenuator set to x100. If the instrument is overdriven, the signal is clipped but may still give an accurate reading of frequency and period. For pulse width, the trigger threshold is particularly

Input

Impedance - 1M + 25p
 Sinewave sensitivity - 30mV RMS-
 1kHz to 30MHz
 50mV RMS-
 DC to 50MHz
 Coupling - AC or DC
 Attenuator - x1, x10, x100
 Trigger Polarity +ve or -ve edge.

Reference

10MHz crystal oscillator

Modes

Frequency - 0.1Hz to 40MHz
 - 4 gate times 0.01/0.1/1/10s
 (Display in kHz)
 Period - 50ns to 10s
 - 4 ranges 1/10/100/1000 cycle
 (Display in us)
 Pulse width - 25ns to 10s
 4 ranges 1/10/100/1000
 (Display in us)

Display

8 digit 0.43" LCD
 Annunciators - indicate overflow
 (OFL)
 - low battery (BATT)
 - 'GATE'
 Battery life - 7 hours continuous
 with alkaline batteries



important and this measurement is likely to become inaccurate.

Logical Operations

The simplified block diagram of the model 5000 (Fig. 1), shows the implementation of the main functions, and in particular, how the gate switch is used to switch in different parts of the timebase divider chain to perform the averaging facility. Note also how the trigger polarity is effected using an Exclusive-OR gate, which incidentally is one of the logic functions implemented with the new 74HC series high speed CMOS to save power.

The instruction manual for the instrument is very explicit and comes complete with a full circuit diagram. There is a useful section on applications and it is refreshing to see a full description on how to re-calibrate the meter, rather than the usual negative attitude of 'return to the manufacturers for re-calibration'. There is even a section describing how to change the voltage level at which the low battery warning comes on. This can be used to give a longer advance warning that battery voltage is dropping. To give this extra warning time, a resistor has to be removed from the circuit board, but it is

not until the case is removed that it becomes apparent that this is not as easy as first thought. The circuitry is mounted on three closely stacked circuit boards and the only way to identify the required component is to compare each board with a diagram showing part of the track layout. Since the diagram is not very clear, a mistake could easily be made. Another criticism which may be levelled at the manual, is that there seems to be some confusion about the meter's specifications. Depending on which page you read, battery life under continuous use can be either 7 or 11 hours — a considerable discrepancy. Similarly, for period measurement, the specification reads '... from 50ns' as well as, '40ns'. The statement of input sensitivity is also confused. Fig. 2 shows input sensitivity versus frequency, with the graph clearly indicating a sensitivity of 10mV RMS upto 20MHz, rising steeply thereafter. The specifications at the front of the manual state a figure of 30mV RMS. Under test, the result indicated the former figure to be more likely, at least with the review meter. It could be said that there is nothing like hedging your bets, but its still pity, since these small points spoil on

otherwise well written manual.

In The Field

Using the meter is made easy by the simple 'no fills' approach to the design. The input is connected via a BNC socket. A 0.8m coax lead, fitted with BNC plug and miniature quick-clip probes, is supplied. When measuring large signals there is no problem using the controls, but when the signal amplitude is near the limit of the meter's capabilities, the trigger level needs very careful adjustment to achieve a correct reading. This is where the slide pot trigger adjustment was found to be sadly lacking. Slide pots may be justified from an aesthetic point of view on hi-fi gear, but when used to make fine adjustments in measurement and control they are an unmitigated disaster. Perhaps the manufacturers will heed this point and put a rotary trigger adjustment on their next model.


Overall, the 5000 functions well and is a likeable instrument, despite a few minor irritations. The robust construction, both internal and external, should ensure it will stand up to a good deal of rough treatment, making it ideal for field work.

■ R&EW

The SCOPEX SG315

A new range of test capabilities

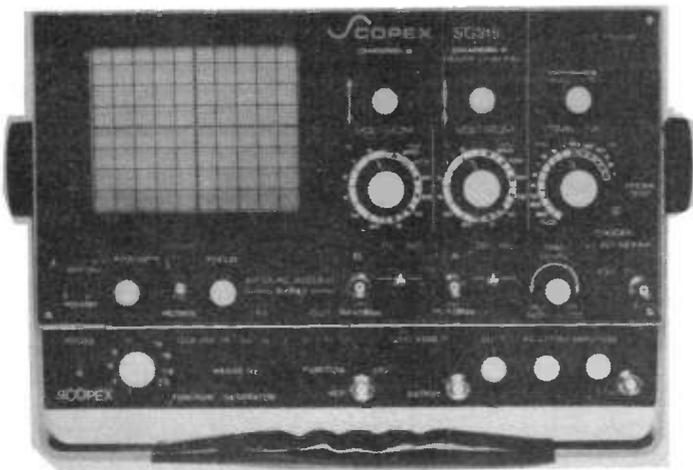Combined Oscilloscope and Function Generator in one Precision Instrument



SCOPEX Instruments Limited
Pixmore House, Pixmore Avenue, Letchworth,
Herts. SG6 1HZ Tel: (04626) 72771 Telex: 825644

The Scope

15 MHz bandwidth
5 mV sensitivity

Timebase range
1 μ s-100 ms/cm

8x10 cm screen
vertical display
A+B, B invert

X-Y display,
X deflection
through A channel
for max.
sensitivity

Normal, TV and ext.
trigger

**The Function
Generator**
0.2 Hz - 250 KHz

Sine

Square

Triangular

DC offset variable

Duty cycle variable

Output 20v,
600 ohms

20 dB attenuator
plus variable

VCF input

TTL sync output

Function Generator can be supplied separately for you to fit to any Scopex Dual Trace scope, just state type when ordering, FG4, FG14/25.

Function Generator also available in an instrument case, FG1.

Prices:

SG315 — £295+VAT. Price includes Probes and Mains Plug and carriage UK mainland.

Function Generator for mounting on Scopex Dual Trace Scopes:

FG4, FG14/25 — £69+VAT

Function Generator: FG1 — £79+VAT

**NEW!
SG315**

R&EW BOOK SERVICE

ZX81 BASIC BOOK

By Robin Norman

1982; 168pp; 215 x 130; Paperback.

Stock No: 02-11785 Price: 5.95

If you have a ZX81, or are thinking of buying one, this book will tell you all you need to know to get the best from it. This book covers the basic 1K version, the additional facilities offered by the 16K expansion RAM, and how to use the ZX Printer. There are 14 original programs for you to run on the machine (for 1K and 16K versions), and for those confused by computer jargon (and who isn't?) there is a glossary of technical terms. Robin Norman assumes no initial computing know-how, and his undemanding writing style is a perfect beginner's introduction.

THE SPECTRUM BOOK OF GAMES

By M James, S M Gee, & K Ewband

1983; 146pp; 155 x 235mm; Paperback

Stock No: 02-20479 Price: 6.50

Here is a selection of twenty-one exciting, high quality games written specially for the ZX Spectrum. These games make full use of the Spectrum's facilities, and are fully tested and crash-proofed.

Among those included are variant of popular arcade games such as Spectrum Invaders, Rainbow Squash and Mighty Missile; board games such as Capture the Quark; a compelling adventure game Treasure Island; a conversational game in which the Spectrum answers you back; and a commando game for you to test your skill. Each program is presented to appeal to all Spectrum owners, no matter how old or young, whether you are completely new to computing or fairly experienced.

Each program is accompanied by an explanation of how to play the game and how the program works, including tips on how to modify or 'personalize' it for your own special use.

Normally games of this quality are only available individually on cassette. This book therefore gives you remarkable value.

THE SPECTRUM PROGRAMMER

By S M Gee

1983; 142pp; 155 x 235mm; Paperback

Stock No: 02-20258 Price: 6.50

The appearance of the Sinclair ZX Spectrum in 1982 was a major event in personal computing. This book takes the Spectrum user in easy stages from his first steps in programming to a good level of competence.

Early chapters give a brief history of the ZX range, and give advice on how to set up the machine and use the keyboard. Subsequent chapters describe one's first steps in BASIC, looping and choice, handling text and numbers, and functions and subroutines. There are three chapters on graphics and sound while the final chapters is devoted to logic and other advanced topics.

The book includes many programming examples, and most chapters contain at least one complete program listing, mainly for games applications. It is clearly and logically written, and will be invaluable to all spectrum users, in the home, education and small business.

INTRODUCING SPECTRUM MACHINE CODE

By Ian Sinclair

1983; 152pp; 230 x 155mm; Paperback.

Stock No: 02-20827 Price: 8.50

GET MORE SPEED AND POWER FROM YOUR ZX SPECTRUM! Many of the things you want, like fast moving graphics for games, cannot be achieved with slow-acting, high level languages such as BASIC. Also, actions which have not already been provided for by your Spectrum's in-built BASIC interpreter are just impossible. For instance, you won't be able to use ZX81 cassettes, you cannot renumber a whole set of lines quickly you cannot send serial printer signals to the cassette output, etc. All these, however, and many others can be accomplished by programming the Spectrum directly in machine code. Sooner or later, all microcomputer users feel the need to get to grips with machine code.

Unlike most books on machine code, this has been written specially for the beginner who is carefully shown what to do in easy stages, step by step. A knowledge of machine code will enable you to really master your Spectrum and open up a fascinating range of extra facilities you would hardly have thought possible!

THE ZX SPECTRUM AND HOW TO GET THE MOST FROM IT

By Ian Sinclair

1982; 130pp; 155 x 235mm; Paperback

Stock No: 02-20185 Price 6.50

This book is written for the Sinclair SPECTRUM user who is a beginner or has used other machines, particularly the ZX81. It covers the setting up and operation of the machine in detail but from the viewpoint of the beginner, highlighting the difficulties and illustrating how the machine responds to incorrect commands. The beginner is guided through the difficult early stages until he or she feels confident enough to start designing and entering BASIC programs. The book has also been designed to be used as a reference guide for the more experienced user.

ZX81 USER'S HANDBOOK

By T J Terrell & R J Simpson

1982; 138pp; 215 x 135mm; Paperback.

Stock No: 02-12234 Price: 5.95

The ZX81 is a fascinating machine that has brought the power of the computer within everyone's reach. But the user is often bewildered by the many facilities offered by the ZX81, and after mastering some simple BASIC programming, finds himself asking questions about the machine:

What is a string and how is it used?
How can I create moving graphics?
How can I interface external hardware?
Why use machine code?

The ZX81 User's Handbook sets out to answer these and many more questions, covering the structure of the ZX81, binary and hexadecimal arithmetic, flow charts, logic, graphics, the Z80A microprocessor work and machine code.

Original programs illustrate these topics (all running on the standard 1K version), and a glossary of over 100 terms is included.

PROGRAMMING WITH GRAPHICS

By Garry Marshall

1983; 120pp; 155 x 235mm; Paperback.

Stock No: 02-20215 Price: 6.50

Computer graphics is a fascinating field. It has also become highly topical, as so many of the new personal computers have high-resolution graphics.

This book provides an up-to-date treatment of the subject, covering the three major methods of graphics production. After introductory chapters describing the background to graphics and the principles of its production, there are three chapters devoted to block, pixel and line graphics. The final chapter considers topics such as colour, movement and three-dimensional drawing, and the Appendix summarises the graphics facilities of various micros.

The book is readily understandable by the non-mathematical user, and has the great advantage over most books on this subject of being machine independent. It will therefore be of great interest to all personal computer users who use or wish to use graphics, whether in the home, in education or in business.

R&EW BOOK ORDER FORM R&EW

Stock No.	Please supply the following books:	Quantity	Price £.p

Postage is included in the book prices shown. Packing is charged at a flat rate of 60p. Please quote stock no(s). of book(s) ordered.

NAME Total: 0.60
ADDRESS

POSTCODE

I herewith enclose a cheque PO* no. value

made payable to **Radio & Electronics World.** *delete as appropriate

Please debit my **ACCESS*/BARCLAYCARD*** no.

Signature





ICR70/R2000

RECEIVERS REVIEWED

William Poel tells you what's going on inside the latest communications receivers.

Loyal readers of **R&EW** will remember the comparative review of the R1000/FRG7700 we published back in 1981. In the short space of time since that review, advances made in the general receiver art have been substantial. Not so much in the areas of signal handling (there are some who grumble that anything since an HRO has been a retrograde step as far as the ability to handle large signals and keep the unwanted products to a minimum is concerned) but in the areas of control and 'function' management. In other words, the invasion of the micro-processor, which means that radio engineering will never be quite the same again — traditionalists might like to muse upon the concept of using servo motors to drive the knobs on their favourite AR88.

The R70 is a significant product for ICOM, who for some reason best known to themselves have wilfully managed to keep out of the HF receiver business until now. Mind you, they've had a fair bit of practice, so it's not surprising that the essence of this receiver is a distillation of their existing HF designs used in transceivers such as the IC720. The R2000 is a very

different kettle of fish, setting out to be a general coverage and broadcast receiver. It is a very worthy successor to the R1000, although on first impression it must be said that the R70 has more 'communications' appeal. And so it should, bearing in mind the cost differential.

We shall be very cautious about direct comparisons here. The last time we were forthright and suggested that the FRG7700 could be favourably compared with an NRD515, we failed to include the comment that the comparison was similar to that between a Ford and a Jaguar. So, in the present comparison, the R2000 is the GTXLR 'go faster' model, and the R70 is the laid back 10 litre job. Neither should cause undue distress to the owner of an NRD515, which remains in a league of its own.

Synthesize Or Bust

It's a brave receiver designer that tries to stand firm in the march of progress by insisting that non-synthesized local

oscillators are where it's at. Redoubtable characters at Plessey still fly the flag for air spaced tuning capacitors and direct generation of the LO, whilst you could just as easily use the output of the phase detector (adjusting the filter time constants!) to drive a servo on the tuning capacitor — we have yet to hear of anyone doing this seriously enough to want to tell **R&EW** about it.

Both receivers provide fully synthesised steps without interpolation VFOs. The R2000 provides 50Hz, 500Hz and 5kHz, with 200 steps per revolution, but the R70 provides 10Hz, 100Hz and 1kHz with 100 steps per revolution. Purists will warm to the promise of vernier precision on the R70, although the R2000 isn't actually any more tricky to handle — except perhaps if you use a razor sharp CW filter system. The R70 provides only one 'memory', in the shape of the now conventional system of a second VFO. The R2000 grasps the opportunity of the MPU control and goes to town with 10 memories plus a full memory/band scan feature. The full versatility of this feature is best illustrated in conjunction with VHF converters and satellite watching.

Naughty, But Nice

Such things may well have AR88/HRO fans snorting in disgust, but these features need not degrade any other aspect of the performance, so why not just enjoy them? The memories store both the frequency and the mode, and when scanning, the mute operates to hold the scan on busy channels in the FM mode. It's all good fun, and whilst the signal handling may not be of the best, these extras are common enough to persuade owners of older receivers to trade up — or add on an R2000 to help keep as many ears open at once as possible. By careful choice of memory frequency, it's an ideal means of keeping track of HF conditions with the minimum of fuss.

The R70 has more immediately identifiable possibilities for the computer person, since ICOM have been good enough to provide a bigger I/O socket, plus enough of a description of the connections to enable those so inclined to control the whole receiver using an external computer, as we'll shall be exploring shortly. The R70 offers pass-band tuning, and this is one thing that even communications purists cannot deny has great utility in the confusion of modern HF communications. It's worth taking a closer look at PBT, since this is something that can be retrofitted (by the brave) to most dual conversion receivers, and the results really will be immediately detectable.

Any meaningful description of the circuit of either of these receivers requires reference to the detailed circuit diagrams, and whilst we just managed to squeeze in the R1000, FRG7000 and even the NRD515, both of the present receivers have advanced the art of complexity past the point at which it is possible to absorb the manufacturer's block diagrams, let alone the detailed circuit diagrams. The Japanese passion for illustrating block diagrams using every semiconductor as an excuse for another box has now gone too far, so we've simplified that of the R70 to help understand the way these receivers work (*Fig. 1*).

Once Around The Block

As usual, Trio have a more concise and readable approach which doesn't need much additional comment from us. One of the several noteworthy parts of the R2000 circuit is the use of the CMOS 8049 MPU, since quite apart from power consumption considerations, it's essential to keep the RF

noise to a minimum. It's a shame that most non-Japanese micro manufacturers have not yet fully grasped the enormous significance of CMOS MPUs in the real mass marketplaces.


Both receivers employ essentially the same overall configurations, except for the items already noted. The R2000 uses a different set of numbers in VCOs and IFs — but herein lies the major difference from the communications standpoint, since the R2000 doesn't put all its selectivity up front, but keeps the first and second IFs wide enough to account for the fact that the first LO steps in 25kHz increments, the 2nd LO is fixed, and the 50Hz interpolation occurs at a ratherly gingerly 400kHz-ish, resulting from the division of the VCO in the IC2 PLL loop by 100 in IC3. This means, if there's a strong signal less than 25kHz away from the weak one you want to hear, then they all get to the last IF filter before meaningful filtration occurs. The 3rd mixer may well decide that it's had enough before that can occur.

The R70 uses the textbook procedure and puts a 15kHz bandwidth crystal filter right up front at 70.4515MHz — the first LO is the only

variable oscillator (excepting the pass band tuning system). As anyone with a brief practical acquaintance with PLL synthesis will have discovered, you don't get 10Hz resolution at 100MHz by direct methods, dual modulus or not. The R70 achieves 10Hz steps through the use of multiple mixings and divisions. A shortage of details on the ICs involved precludes us from making a proper analysis of what is going on, but whatever it is, it's so grossly complex that we'd rather bypass this technology and use the mental energy to work with the MC14515X series of synthesiser devices that we know and love. The convoluted machinations of this scheme achieve their objectives by generating the 10Hz at a sufficiently low frequency to make for practical loop design.

And The Rest

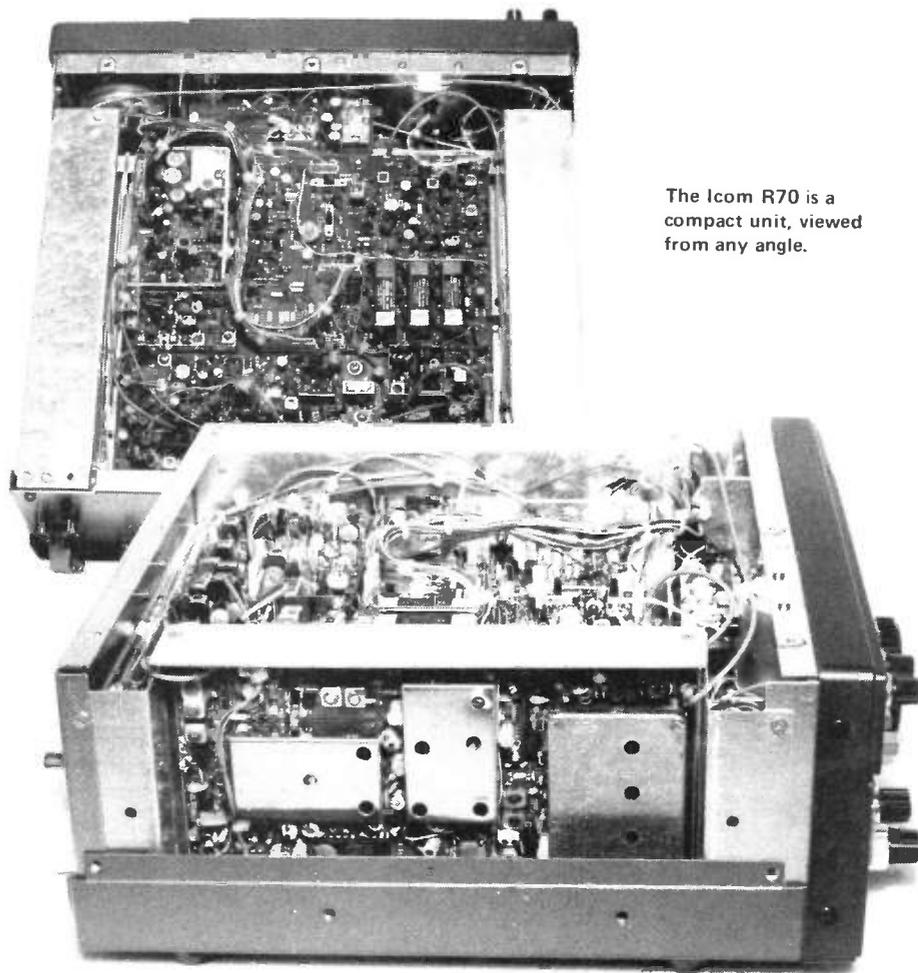The noise blanking systems in both receivers work well, with the additional refinement of the R70 having a wide/narrow facility to take into account the longer 'woodpecker' noises (wide — referring to the pulse width rather than



The Icom R70 is a compact unit, viewed from any angle.

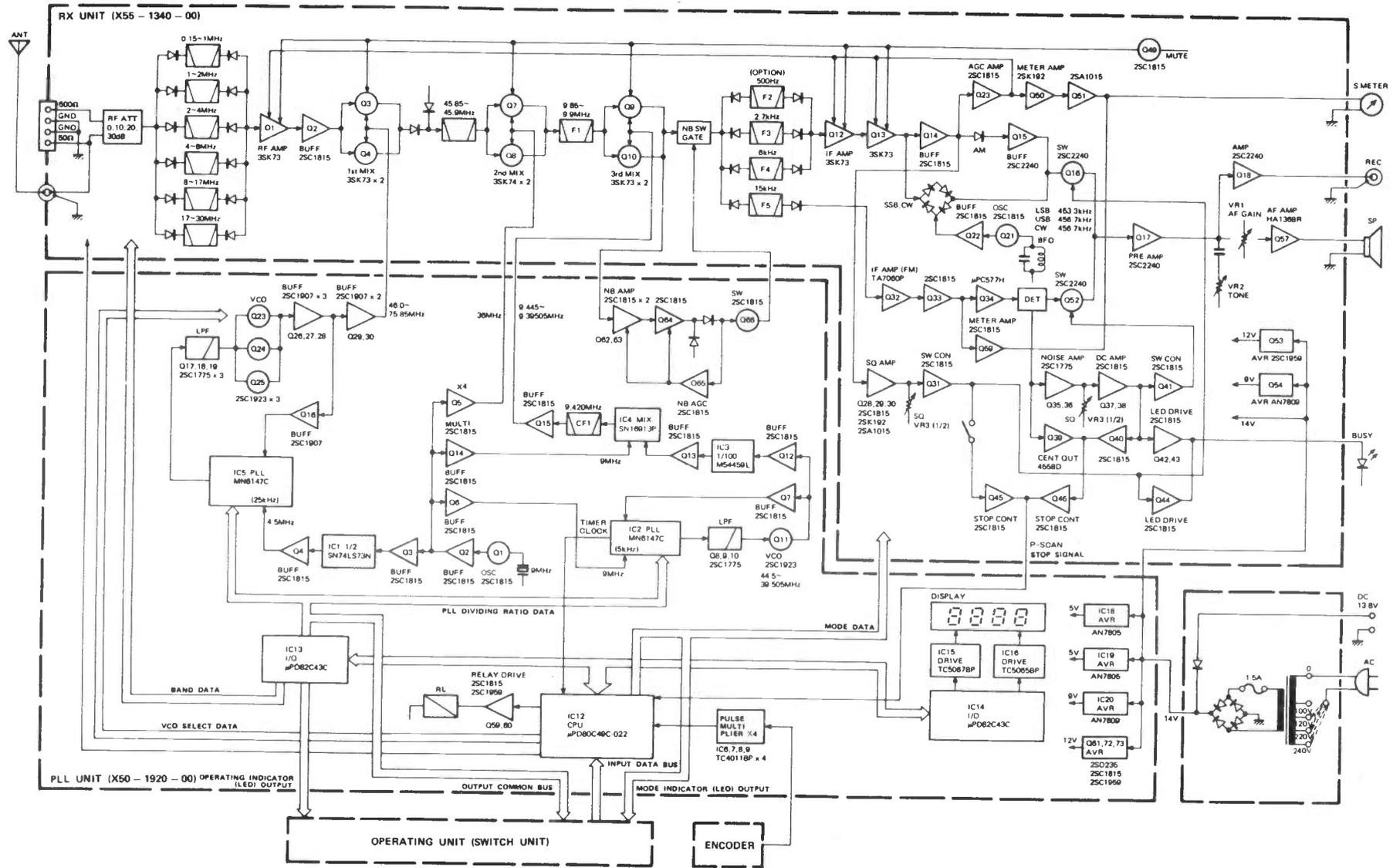


Figure 1: Block diagram of the R2000, showing both the HF and PLL sections.


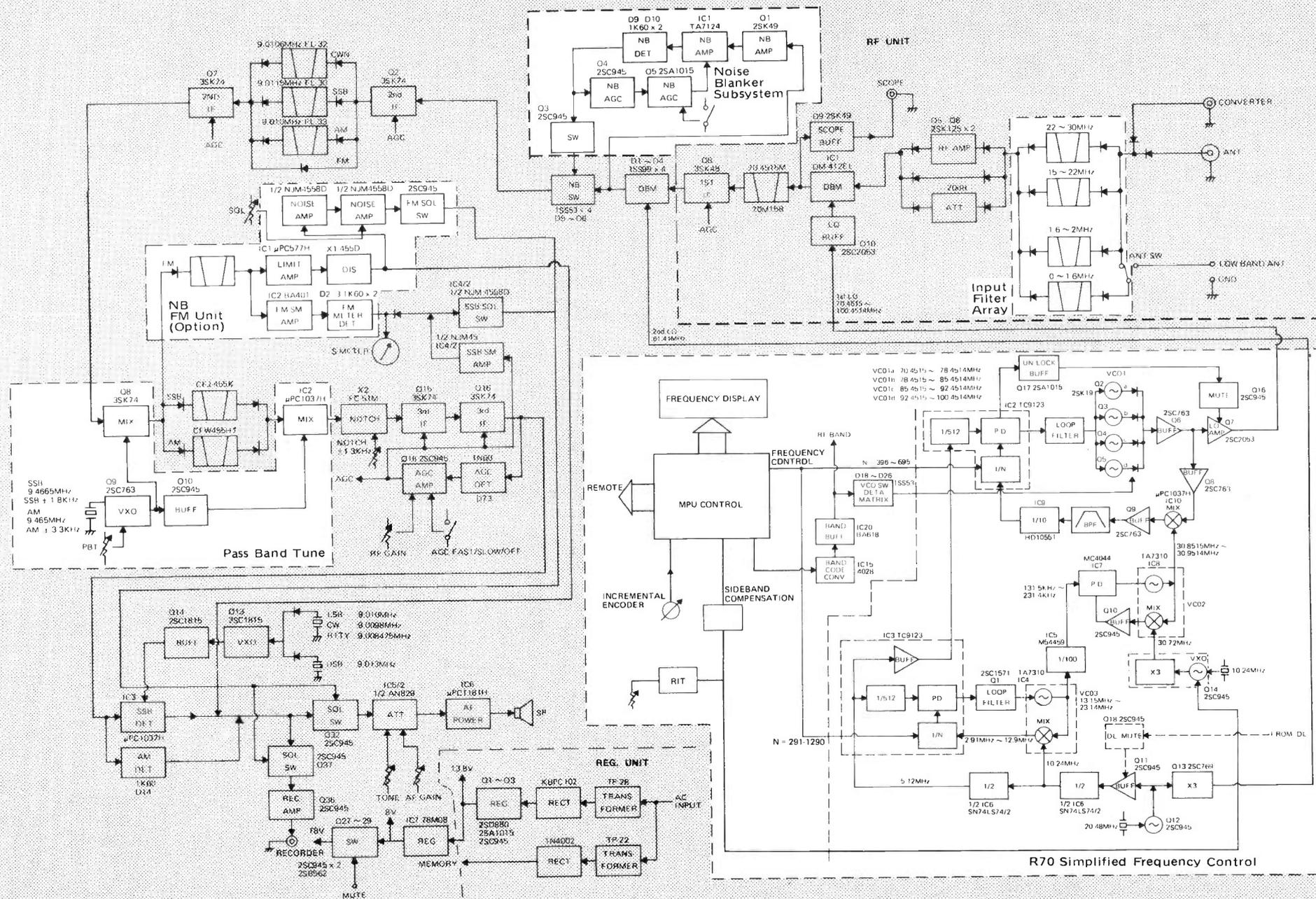


Figure 2: The Icom R70 block diagram, with the main areas highlighted.

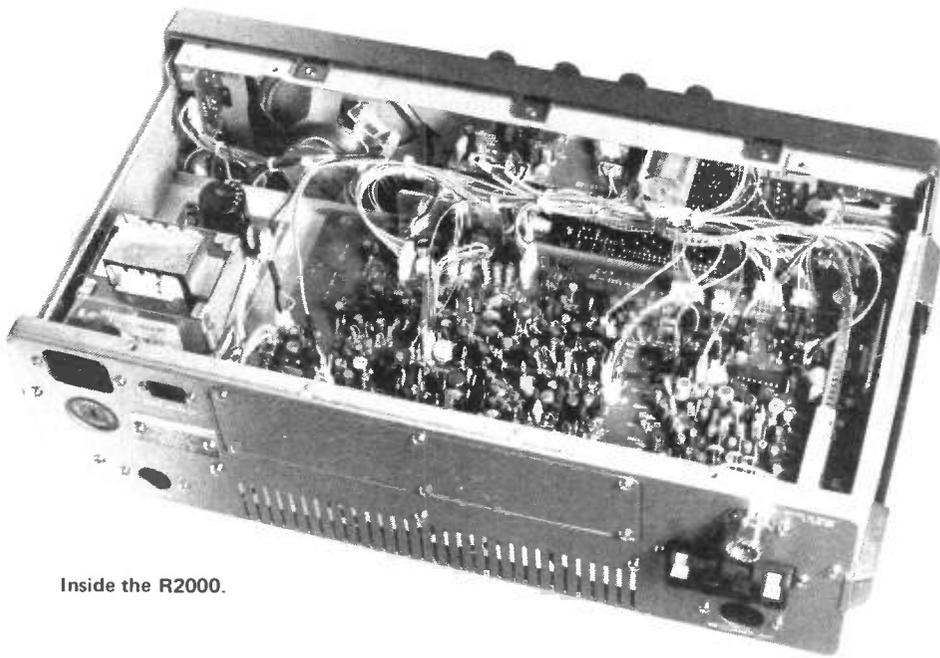

Inside the R2000.

anything to do with selectivity), as well as ignition and similar shorter impulse noises. Likewise both receivers include FM facilities (it's an option on the R70), which works perfectly well in both cases — the adoption of squelch on all

modes is very welcome, if a somewhat sudden departure from previous HF receiver practice.

RF gain works on the AGC loops in both cases, providing compensation on S meter readings in the approved


manner. In fact, these two receivers seem to have remembered just about everything anyone might possibly have thought about when conceiving an 'ultimate' HF receiver system. Those of you who like to sit and muse upon such things should not, however, give up in despair that there's nothing left to do, since the truly vast numbers of parts in these receivers stem from the very introspective Japanese 'not invented here' mentality which denies them access to some of the bits that US and European designers are prepared to include.

There's scope for simplifying the designs, and turning them into something a good deal more modular. But there is still a very real danger that the erstwhile designer will be so disheartened by the enormity of what messrs ICOM and TRIO have laid on him, that he will not bother to try and keep abreast of design trends any longer. Don't do it!

We'll be taking the designs apart, a bit at a time, to examine the latest in HF Rx design philosophy and suggest alternatives — and hope that some of it finds its way into the designs of our readers.

■ R&EW

WHO STOCKS HELICAL FILTERS FOR VHF/UHF?

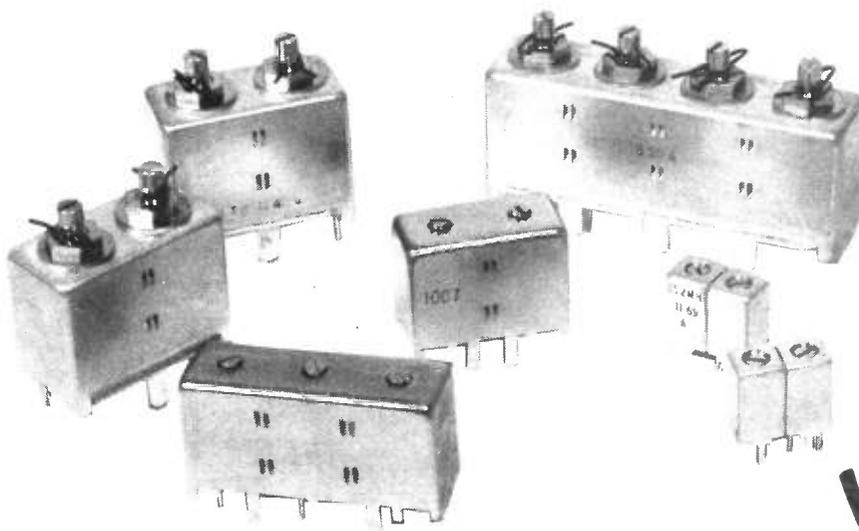

WE DO!

aim

ambit industrial marketing

200 North Service Road, Brentwood, Essex CM14 4SG
 Telephone (Consumer Sales/Enquiries) 0277-230909.
 Telephone (Industrial Sales/Enquiries) 0277-231616
 Telex 995194 AMBIT G
 Data 24hrs (RS232/300baud) 0277-232628 — REWTEL.

- Prices exclude VAT except where otherwise shown.
- Postage and Packing 60p per pre-paid order.
- Orders submitted using Ambit Stock Codes will be processed first.
- Orders for in-stock items despatched same day (up to 4pm receipt).
- Hours — (consumer sales) 8am-7pm Mon-Sat: (Industrial) 8am-6pm (Mon-Fri).
- Retail Sales 9am-6pm Mon-Sat *Industrial Sales 'Take-Away' by arrangement.
- Industrial accounts available on application: 2 Trade, 1 Bankers Ref.

The Logic Probes

Spend Less

LP-1 Logic Probe

The LP-1 has a minimum detachable pulse width of 50 nanoseconds and maximum input frequency of 10MHz. This 100 K ohm probe is an inexpensive workhorse for any shop, lab or field service tool kit. It detects high-speed pulse trains or one-shot events and stores pulse or level transitions, replacing separate level detectors, pulse stretchers and pulse memory devices.

Ali for less than the price of a DVM

£31.00*

LP-2 Logic Probe

The LP-2 performs the same basic functions as the LP-1, but, for slower-speed circuits and without pulse memory capability. Handling a minimum pulse width of 300 nanoseconds, this 300 K ohm probe is the economical way to test circuits up to 1.5 MHz. It detects pulse trains or single-shot events in TTL, DTL, HTL and CMOS circuits,

replacing separate pulse detectors, pulse stretchers and mode state analysers

£18.00*

Test More

LP-3 Logic Probe

Our LP-3 has all the features of the LP-1 plus extra high speed. It captures pulses as narrow as 10 nanoseconds, and monitors pulse trains to over 50 MHz. Giving you the essential capabilities of a high-quality memory scope at 1/1000th the cost.

LP-3 captures one shot or low-rep events all-but-impossible to detect any other way.

All without the weight, bulk, inconvenience and power consumption of conventional methods

£49.00*

The New Pulser DP-1

The Digital Pulser, another new idea from G.S.C. The DP-1 registers the polarity of any pin, pad or component and then, when you touch the PULSE button delivers a single no-bounce pulse to swing the logic state the other way. Or if you hold the button down for more than a second, the DP-1 shoots out pulse after pulse at 1000 Hz. The single LED blinks for each single pulse, or glows during a pulse train. If your circuit is a very fast one, you can open the clock line and take it through its function step by step at single pulse rate or at 100 per second. Clever! And at a very reasonable price.


£51.00*

GLOBAL SPECIALTIES CORPORATION



Unit 1, Shire Hill Industrial Estate,
Saffron Walden, Essex CB11 3AQ.
Telephone: Saffron Walden (0799) 21682.
Telex: 817477.

Name _____ Address _____									
I enclose Cheque P.O. for £ American Express card no. _____ FOR IMMEDIATE ACTION — The G.S.C. 24 hour 5 day a week service. Telephone (0799) 21682 and give us your Barclaycard Access American Express number and your order will be in the post immediately.	I enclose my Barclaycard Access card no. _____ Exp. date _____ For FREE catalogue tick box								

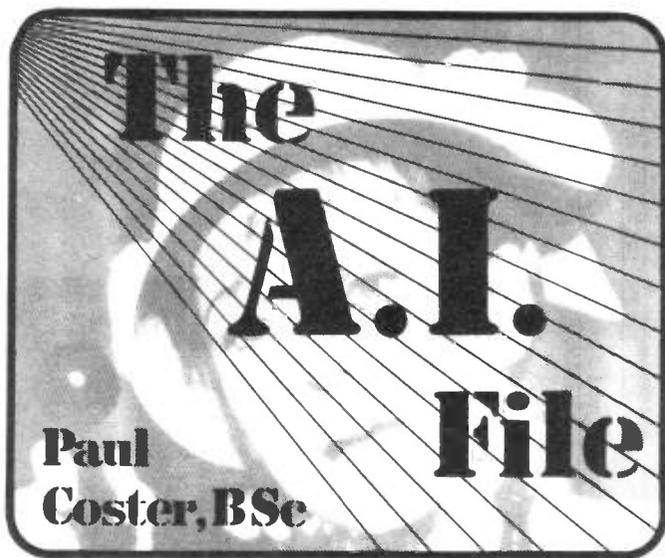

The sixties saw the birth of a number of programs which could converse and answer questions in English. One of the more famous of these 'human mimics', ELIZA, is analysed this month, to exemplify some of the shortcomings associated with conversational programs.

Followers of this series have probably, by now, acquired a somewhat sceptical outlook on Artificial Intelligence. This is not necessarily a bad thing, since all too often wild claims are made for programs supposedly exhibiting human traits such as creativity and intelligence. To the author's knowledge, no system exists at the present time which transcends the limitations imposed by its algorithmic roots — many machines can *act* in a human fashion, but there is always an underlying logic which says 'if A then B (or NOT B)', and in the final analysis a digital signal can only be high or low.

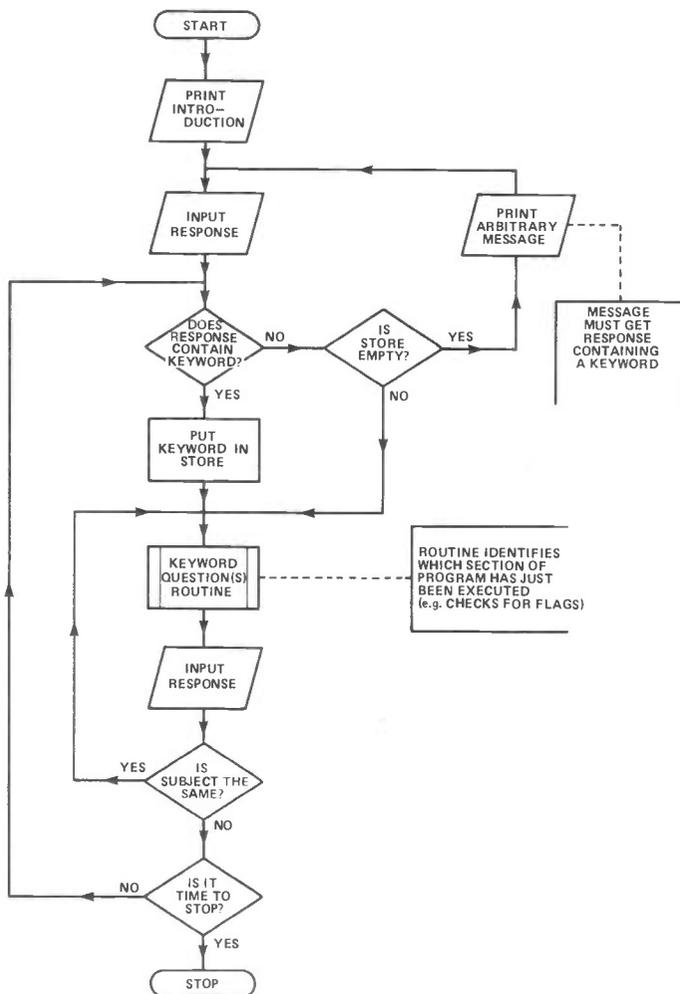


Figure 1. Flowchart reflecting the structural basis of programs which respond to questions using a key word searching routine.

- 1 My husband made me come here
- 2 *Your husband made you come here*
- 3 He says I'm depressed a lot of the time
- 4 *I am sorry to hear that you are depressed*
- 5 It's true. I am unhappy
- 6 *Do you think that coming here will help you not to be unhappy*
- 7 I need some help, that's for sure
- 8 *What would it mean to you if you got some help*
- 9 Perhaps I could learn to get along with my mother
- 10 *Tell me more about your family*
- 11 My mother looks after me
- 12 *Who else in your family looks after you*
- 13 My father
- 14 *Your father*
- 15 You are like by father in some ways
- 16 *What resemblance do you see*
- 17 You are not very aggressive, but I think you don't want me to notice that
- 18 *What makes you think I am not very aggressive*
- 19 You don't argue with me
- 20 *Why do you think I don't argue with you*
- 21 You are afraid of me
- 22 *Does it please you to think I am afraid of you*
- 23 My father is afraid of everyone
- 24 *What else comes to mind when you think of your father*
- 25 Bullies
- 26 *Does that have anything to do with the fact that your husband made you come here*

Table 1. Example of ELIZA's (italics) question and answer abilities (adapted from Weizenbaum, 1966).

The Turing Test And Other Fables

With this fact in mind, it's surprising to note that prior to the appearance of conversational programs onto the AI scene, a British scientist called Alan Turing had proposed a test for establishing whether a machine could 'think'. It comprised a game involving the machine and two people, assigned the letters 'A', 'B' and 'C' respectively. Each of B and C is isolated in a room with a computer terminal — their only means of communication. Person C's task is to ask questions of A and B in order to determine which is the machine and who is the person. The task confronting A and B is then to prevent C from discovering whether they are machine or person. Turing suggested that if C was ever unable to identify A and B reliably, then machine A must be capable of thought.

The Turing Test, though seemingly well designed, merely served to motivate a wave of AI research into producing a system to 'beat the test'. In effect, the goal became to develop a machine that could convince the person operating it that he or she was conversing with *another person*, rather than a machine. The problem with this line of reasoning becomes apparent when it is realized that programs *do* currently exist which can fool their operators into believing they are speaking to some mysterious person or intelligence 'behind' the machine; the point being that the programmers responsible for these technological miracles would never consider them capable of thought. In other words, the programs' creators know the sort of responses that will be elicited by a given question — can you consistently and accurately predict the way someone else will answer a particular set of questions? Creating a machine which *appears* to think is quite a different matter from coming up with one that *does* think (although we'll leave you to ponder the question as to how to differentiate between a person who *is* thinking and someone *pretending* to think).

Eliciting ELIZA

Having exposed the distinction between acting intelligently and possessing intelligence, we can move on to examining a specimen of the former — Joseph Weizenbaum's ELIZA. **Table 1** shows a typical conversation session with ELIZA. More importantly, it reveals certain key points about the program's *modus operandi*. In the first two lines, ELIZA responds to the statement 'My husband made me come here', by merely transforming the pronouns 'my' to 'your' and 'me' to 'you', then repeating the statement. This process of repeating a question by 'reflecting' it back at the person you are talking to, is a common enough occurrence in everyday conversation, with intonation providing the interrogative form.

Another of ELIZA's techniques is to latch onto particular key words in a statement and respond with a comment or observation. For example, the word 'depressed' in line 3 appears again in line 4. The same is true for 'unhappy' (5 and 6), 'help' (7 and 8 — qualified as 'some help'), 'aggressive' (17 and 18), 'argue' (19 and 20) and so on. A variation on this is obtained by the use of a collective noun instead of the one supplied. In line 8 ELIZA asks 'What would it mean to you if you got some help', to which the reply 'Perhaps I could get along with my mother' is given. Now, rather than posing a question based around the word 'mother', ELIZA employs the collective noun 'family', thereby exhibiting a further aspect of its structure — a database including examples of nouns which form part of a collective group.

A 'clever' extension of the noun-collective noun transition, is shown in lines 15 and 16. Here the statement 'You are like my father' contains the preposition 'like', meaning 'similar to'. The response, utilising the words supplied, would be 'In what ways am I like your father', but this has quite a complex construction. So, ELIZA employs the noun derived from the transitive verb 'resemble' and asks the question 'what resemblance do you see'. The point to notice is that this question could apply equally to any 'You are like...' sentence.

Who brought you here?

The Police

What trouble did you have with the Police

Cops don't do their job

What do they do then?

Cops arrest the wrong people

They arrest the right ones at times

The law should get those Italian crooks

Are you Italian?

My background is British, but I was born in this country

Do you know any Italian crooks?

I try to avoid the underworld

Are you afraid of the underworld

The Mafia are the worst gangsters

Are you connected with the Mafia?

You know, they know me

How do they know you?

They spy on me

Why do they do that?

They want to get false evidence to frame me

What is it they have against you?

They are out to get me

What for?

I have incriminating evidence against the Mafia

Are you sure of this?

You don't believe me

I am doing my best

Table 2. An extreme case of paranoid schizophrenia, as modelled by PARRY; shown in italics (adapted from Colby, 1972).

Problem Corner


Perhaps the most interesting feature of the **Table 1** interaction is contained in lines 24-26. Having just responded to a statement concerning the subjects' father (line 24), ELIZA is confronted by the one-word answer, 'Bullies'. Without recourse to some other information, the machine's response cannot relate to line 25 directly, so ELIZA refers back to some previous subject. It still manages to ensure the link isn't unnatural, by asking whether the subject of line 25 is related to that in line 1. This is a rather more refined technique than simply continuing the dialogue with a new and unrelated topic, but it amounts to the same thing. There are programs, however, which unashamedly resort to the latter. **Table 2** shows an extract from a session with one such program, called PARRY, which may be excused its disjointed and convoluted conversational style, since it was designed to act in a manner similar to someone suffering from paranoia. And if, after reading through the interview, you think it's easy to tell that a machine was behind the responses, then consider the amusing fact that similar extracts fooled psychiatrists in America, who could not distinguish between diagnosed paranoiacs and PARRY.

■ R&EW


Muting system with AF amplifier

The KB4438 from Toko is a low noise, low distortion dual channel pre-amplifier circuit, specifically designed to follow a stereo decoder in FM tuner applications. It features sufficient gain to overcome the insertion loss of high quality pilot tone filters and de-emphasis circuits, yet still produces up to 3.2V RMS output. Other features include a muting facility of around 80dB, a slow turn-on controlled by an RC network. To this may be added a separation figure of 80dB; channels balanced to within ± 0.5 dB.

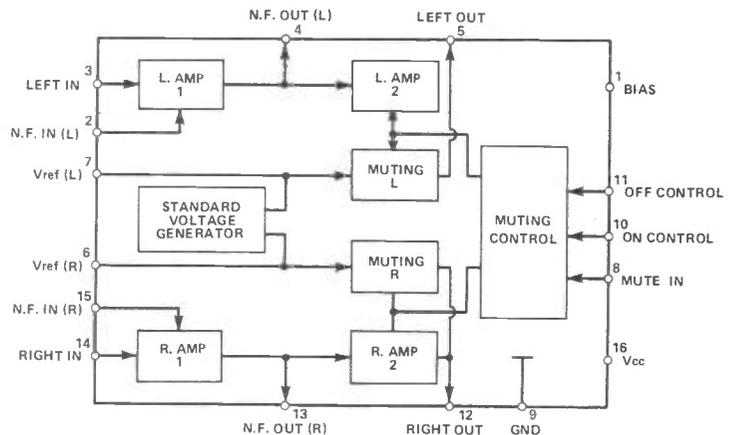The IC may also be used in other applications as a straightforward pre-amplifier by leaving out the pilot tone filters and de-emphasis capacitors from the applications board shown.




KB 4438 block diagram

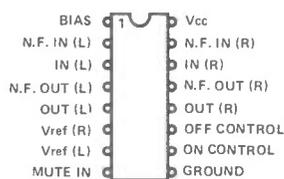


ABSOLUTE MAXIMUM RATINGS

- DC SUPPLY (Vcc) 16V
- POWER DISSIPATION 540mW
- TEMP RANGE: OPERATING -30°C TO +70°C STORAGE -55°C TO +125°C

Pin out for the KB 4438

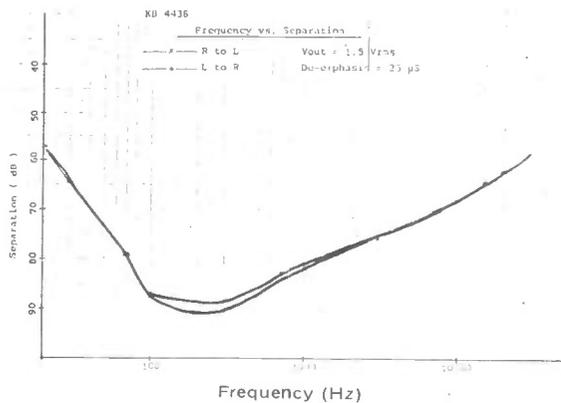

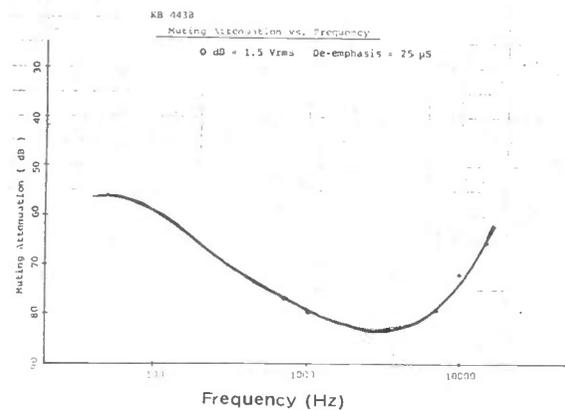Graph to show frequency versus separation.




Graph to show muting attenuation versus frequency.

PARAMETER	SYMBOL	MIN.	TYP.	MAX.	UNIT	CONDITIONS
No Signal Current	ICC	7.0	11.0	16.0	mA	Input signal off
Voltage Gain	GV	23		24	dB	
Channel Balance	C.B.			+0.5	dB	
Output Voltage	Vout	3.0	3.2		V RMS	Distortion 0.1%
Signal To Noise Ratio	S/N	87	96		dB	De-emphasis 25uS
Channel Separation	Sep	72	80		dB	De-emphasis 25uS
Distortion	THD		0.01	0.05	%	
Muting Attenuation	M.ATT	72	80		dB	Mute on, De-emphasis 25uS
Muting Transient Level	MDC.OUT	-20		-20	MV.DC	Input signal off
Muting Time	MT(1)		0.15		SEC.	Time from on to off
Muting Time (Power on)	MT(2)	1.0	1.6	2.5	SEC.	
Transient Level	on out		30	100	MV.	At power on
Transient Level	off out		30	100	MV.	At power off
S/N At Muting On	Mon. S/N	96	109		dB	At mute on
Muting On Level	MUT.S	1.20	1.35	1.50	V	


VCC = 13V, Ta = 25°C, RL = 6k8, VOUT = 1.5VRMS, De-emphasis = 25uS. Unless otherwise noted.

Table 1: Electrical Characteristics.

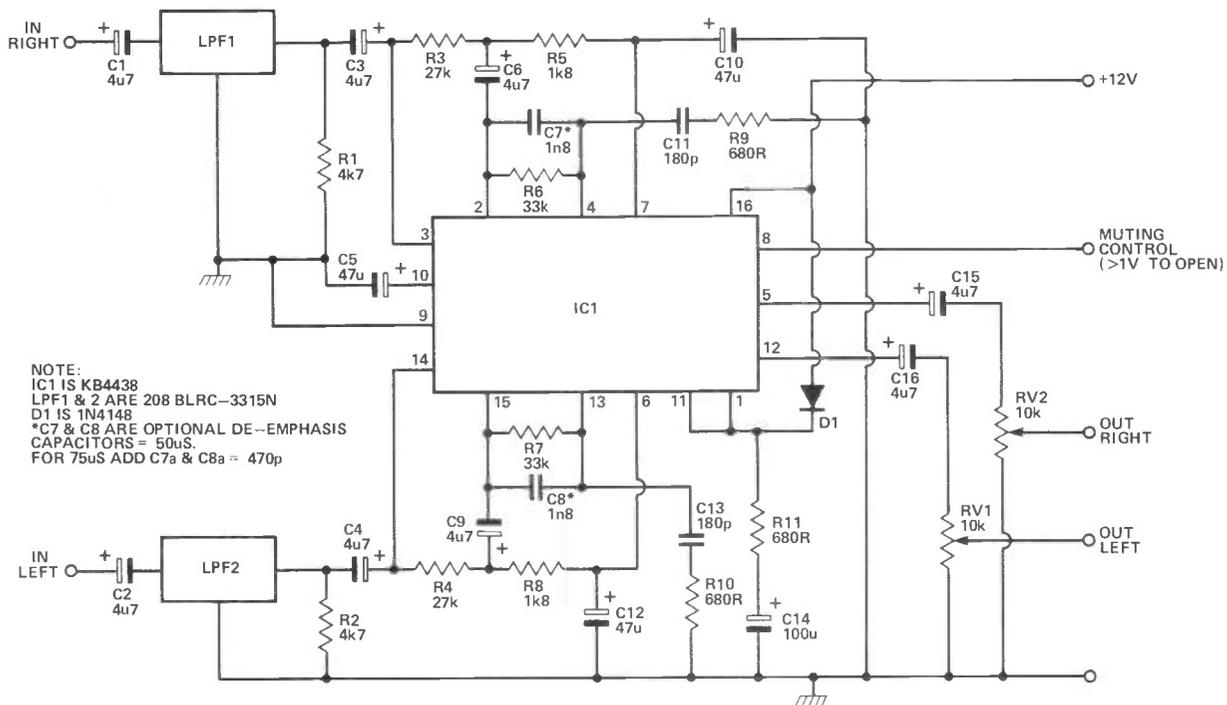



NOTE:
 IC1 IS KB4438
 LPF1 & 2 ARE 208 BLRC-3315N
 D1 IS 1N4148
 *C7 & C8 ARE OPTIONAL DE-EMPHASIS
 CAPACITORS = 50uS.
 FOR 75uS ADD C7a & C8a = 470p

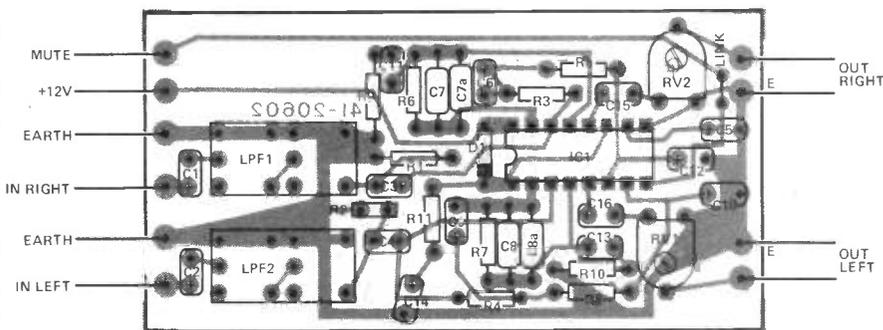Circuit diagram for the board layout shown incorporating pilot tone filtering and de-emphasis components.



Component Overlay.

PCB Foil

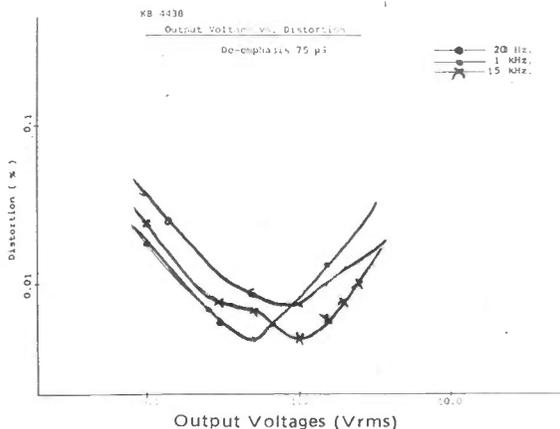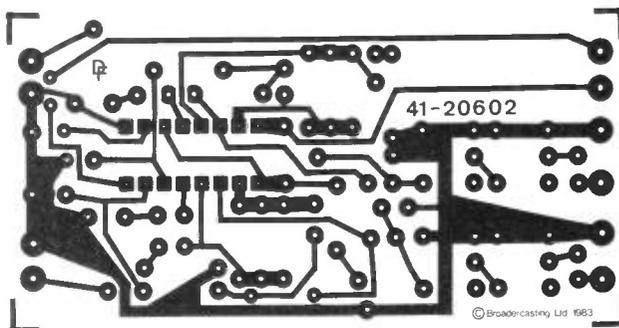


Graph to show output voltages.

S/N Ratio	96dB
Low Distortion	0.01%
High Muting Att.	80dB
High Separation	80dB
High Channel Balance	±0.5dB
Low Pop Noise	
Switch on Delay Facility	

Table 2: Specifications.

WEATHER SATELLITE RECEPTION

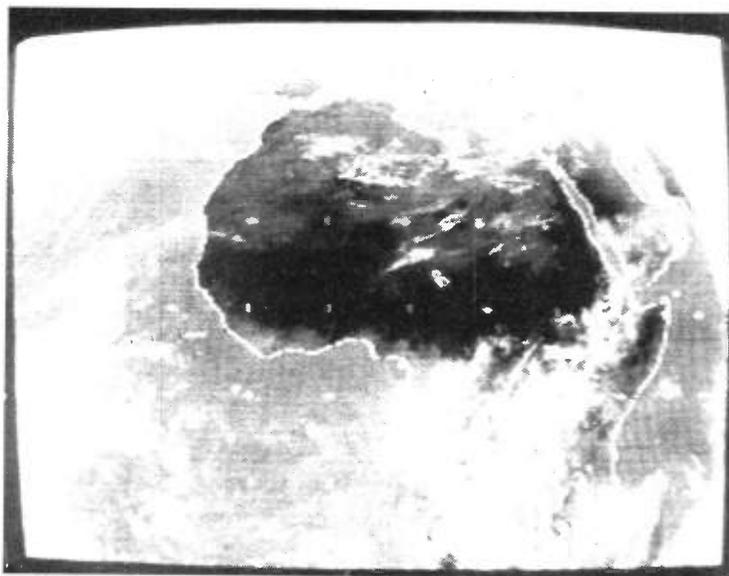A practical approach, originated by Matjaz Vidmar YU3UMV, in VHF Communications magazine



The background to the METEOSAT weather satellites was described by Terry Weatherly in the August 1982 issue of **R&EW** (with additional notes March 1983), and at that time, the facilities for the enthusiast to construct and operate an effective ground station were relatively limited. However, we are pleased to announce that a recent series in the German-based publication, 'VHF Communications' has changed the picture somewhat. Those of you who attended the RSGB national exhibition at Birmingham will have had the chance to see the results of this system on the **R&EW** stand.

The main problem for the enthusiast has been getting a decent viewable picture — and whilst many have tried to live with a variety of surplus facsimile equipment, it's not been hitherto possible to emulate the effects you see on the TV weather forecast each night. The system to be described is a realisation of everything the keen

satellite watcher has asked for.

The big attraction of METEOSAT over earlier weather satellite systems is the fact that it is stationary in the sky, and broadcasts a computer enhanced series of images. The TV signal is a standard form of slow scan image transmission, broadcast as an FM signal (on 1691/1694.5MHz). Viewing techniques have tended to adopt a variety of mechanical means (do you remember the article that featured a converted windscreen wiper motor?) with two serious drawbacks — definition is indifferent as a result of poor gray scale resolution, and conversion to differing speed standards is tricky.

Most **R&EW** readers should not be unduly frightened by the RF processing side of satellite reception, and most of us can probably provide a 'back of an envelope' solution to a digital scan conversion system — but translating such blocks into practise has been an important area which has only really

come into its own with the dramatic drop in the price of the 64k DRAM.


One further problem that seems to surround METEOSAT for those not 'in the know' is the fact that most features either assume too much knowledge of the system and fail to cover the detailed specification, or they are written for the casual interest of the reader. As the author of this piece has discovered, the only comprehensive way to 'get into' METEOSAT is to read all the references, and if this feature causes you to want get deeper into the subject, then there is no alternative than to peruse the articles listed at the end.

Standards

Working on the assumption that a good many readers may already have access to weather satellite equipment (using a variety of non-ideal output media!), this series starts with consideration of the APT digital scan converter.

The choice of solution is based on memory size. The resolution selected was 256x256 (lines x pixels), which effectively produces a picture that uses all the available resolution on a domestic grade TV tube. The 64 level Gray scale resolution (radiometric) has been selected to provide the best overall definition, and this is further enhanced in an optional Grayscale to pseudo-colour converter. Purists may feel that this is cheating, but the infra red images are quite accurately represented by a scale from red to blue, and the visual effects are very soporific — no man-made visual effects box can outdo nature at her best.

The modulation technique is FM, with a maximum deviation of 9kHz, and an FM subcarrier at 2.4kHz which is amplitude modulated to a maximum of 80% (white) with frequencies in the range 0-1.6kHz. The overall maximum transmission bandwidth is 26kHz, with a 1.6kHz video bandwidth. The generic term "APT" refers to "Automatic Picture

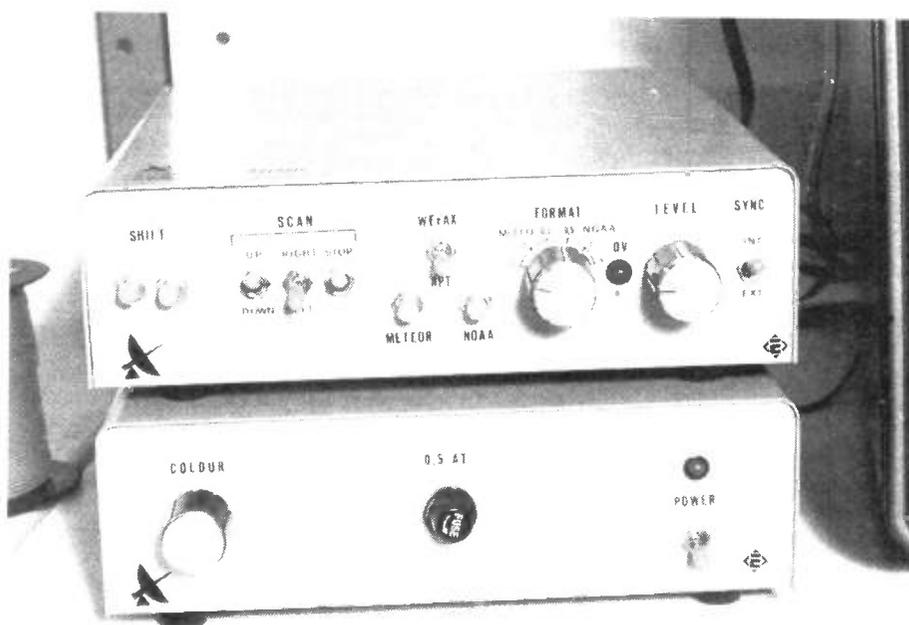

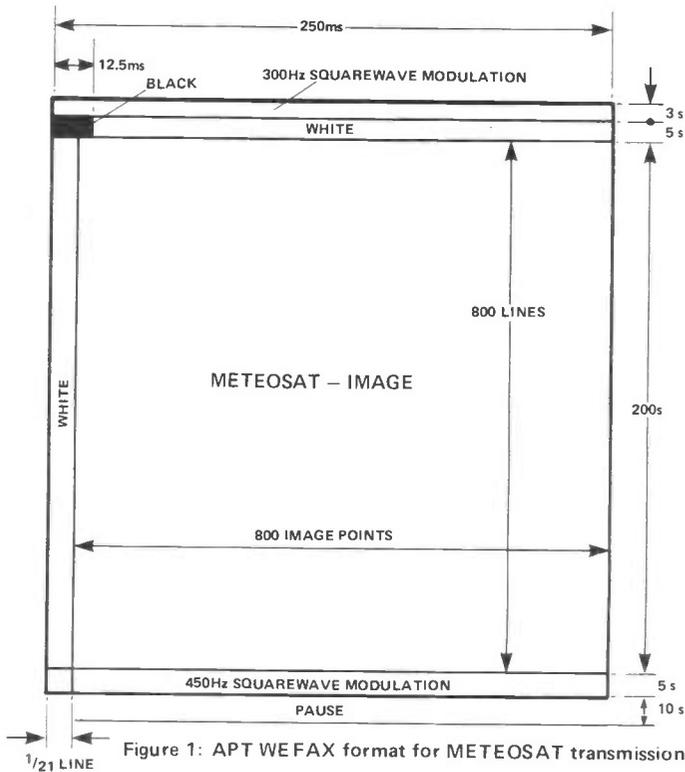


Figure 1: APT WEFAX format for METEOSAT transmissions.

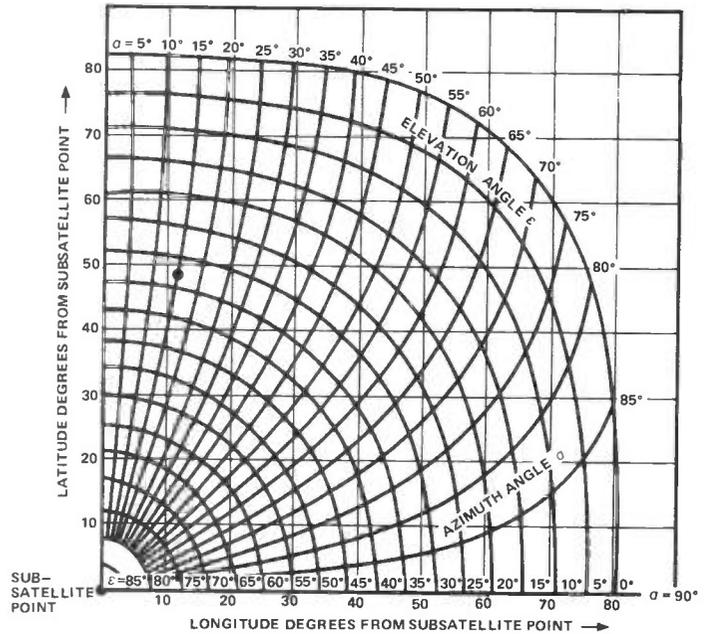


Figure 2: Azimuth and elevation angles can be taken from this diagram.

Transmission', which in METEOSAT's case means: 240 lines per minute, 840 pixels per line, 40 of which are in the form of a leading edge (Fig. 1). The 300Hz starting tone occurs at the top of the frame in the figure, since the picture will appear from the bottom of the screen and climb up to completion, 800 lines later.

The TIROS and NOAA series orbiting satellites use a different format, whereby the Infra red and visible images are transmitted simultaneously side-by-side on the same video lines (Fig. 3). The images are separated by burst frequencies of 832Hz and 1040Hz, allowing the user to select either the dual image (at 120 lines per minute) or blank either the IR or visible image and receive the resultant at 240 lines per minute.

Hardware and theory for getting the 1.6GHz signal down to baseband are adequately covered in the references at the end of this feature: but an area where there is scope for further development is the 137MHz IF sub-system. The R&EW 144MHz UOSAT receiver system described by Graham Leighton has been successfully adapted by a number of satellite watchers, and we have had several effusive letters

from the delighted users.

So we shall be revisiting the UOSAT receiver system in an issue or two's time to tidy up loose ends, put in a much wider filter for correct reception and provide a description of the adaption specifically to this application. Also NOAA and TIROS requirements will be considered.

The System

Figure 4 is the block diagram of the system for use with the scan converter. There are basically two sections involved in the image processor: the first demodulates and digitises the baseband signal from the 2.4kHz subcarrier, and the next section stores and displays the results. A further facility is provided in the shape of an input side chain for use with the high resolution (HRPT) digital images from the NOAA and METEOSAT series satellites, and this must be used in conjunction with a frame synchronizer, which will be covered in a separate feature.

The baseband signal is first filtered and demodulated before being sampled and converted in the section module, which provide the necessary TV signals to operate a composite or UHF input. In view of the excellent

definition available with the system, purists will prefer to go directly into the video circuits where possible.

Pressure on space prevents further coverage in this issue, but next month we will run through each of the circuits involved. Those who can't wait should get the issues of VHF Communications listed here, since if you intend to go to all the trouble of getting your own met satellite ground station, then you should equip yourself with all the necessary background information and reading.

.....
 Modifying the DL6HA 001/28 Dual-Gate MOSFET Converter for Reception of Weather Satellites and other Space Vehicles. T. Bittan, G3JVQ
 1972/3 167-168

More Details on Reception of the European Weather Satellite METEOSAT. R. Lentz, DL3WR
 1978/4 230-240

A System for Reception and Display of METEOSAT Images. R. Tellert, DC3NT
 1979/3 130-140

1979/4 194-202

1980/1 14-22

1980/2 73-87

1980/3 169-178

1980/4 194-210

A Simple Converter for Reception of Weather Satellites in Conjunction with 2m FM Receivers H. Kulmus, DJ8UZ
 1980/4 211-214

A System for Reception and Display of METEOSAT Images Part 7-9. R. Tellert, DC3NT
 1981/1 43-50

1981/2 110-118

1981/3 152-166

A Receive Converter for the Geostationary Weather Satellites METEOSAT - GOES -

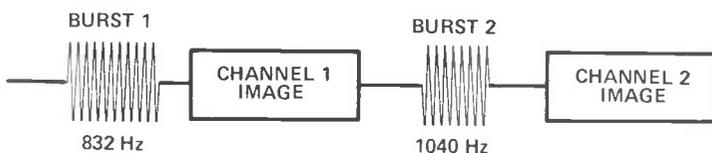


Figure 3: A NOAA6 video signal line.

GMS Part 1: The SHF-Module, B. Roessle, DJ1JZ

1981/4 207-213

Antennas for Reception of Orbiting Weather Satellites in the 137MHz Band T. Bittan, G3JVQ/DJ0BQ

1981/4 214-218

Forecasting the Reception Times of Orbiting Satellites, T. Bittan, G3JVQ/DJ0BQ

1981/4 219-220

A Receive Converter for Weather Satellites METEOSAT GOES, GMS Part 2: The local Oscillator Module, B. Roessle, DJ1JZ

1982/1 24-30

A Digital Storage and Scan Converter for Weather Satellite Images, Part 1, Matjaz Vidmar, YU3UMV

1982/4 194-208

Remember — **R&EW** is now the UK representative for VHF Communications, if you have had any problems concerning subs., parts etc., please write to us with an SAE (mark the envelope VHF Comms) and we will endeavour to sort these problems out. Regrettably we cannot take responsibility for problems that have occurred before our takeover.

■ R&EW


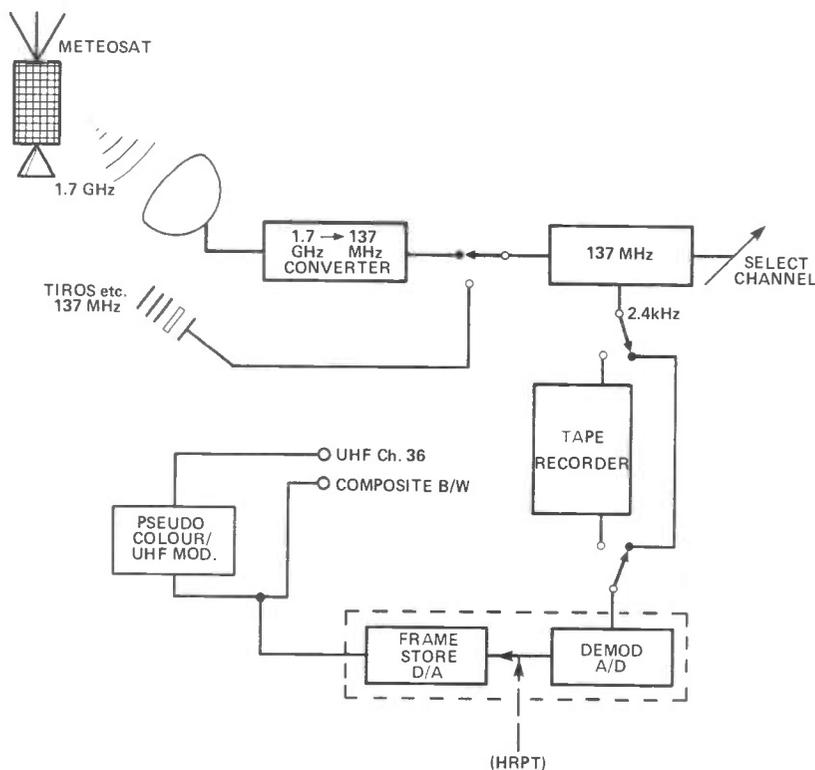


Figure 4: A complete METEOSAT ground station system.

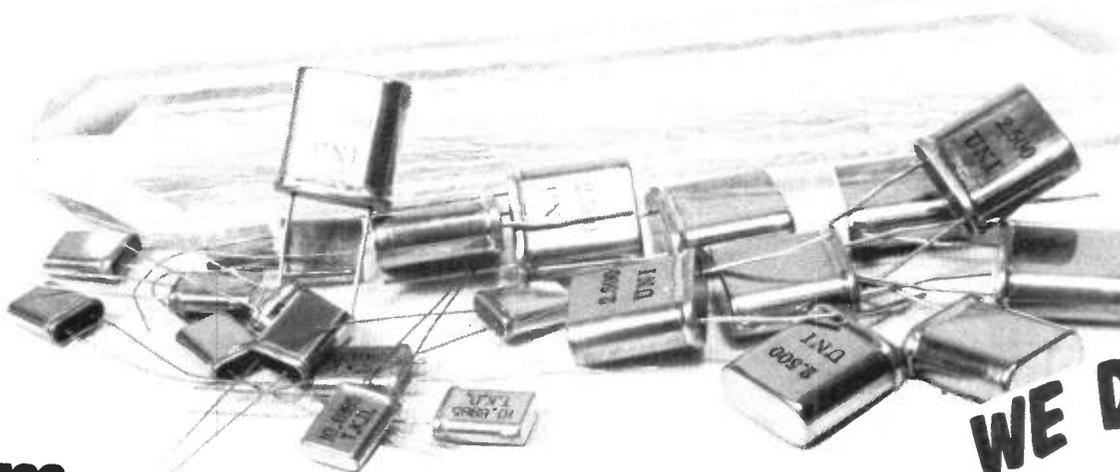Who Stocks Quartz AND Ceramic Resonators for all Applications?



WE DO!

aim

ambit industrial marketing

200 North Service Road, Brentwood, Essex CM14 4SG
 Telephone (Consumer Sales/Enquiries) 0277-230909.
 Telephone (Industrial Sales/Enquiries) 0277-231616
 Telex 995194 AMBIT G
 Data 24hrs (RS232/300baud) 0277-232628 — REWTEL.

★ Including the latest 1MHz CERAMIC RESONATOR

- Prices exclude VAT except where otherwise shown.
- Postage and Packing 60p per pre-paid order.
- Orders submitted using Ambit Stock Codes will be processed first.
- Orders for in-stock items despatched same day (up to 4pm receipt).
- Hours — (consumer sales) 8am-7pm Mon-Sat; (Industrial) 8am-6pm (Mon-Fri).
- Retail Sales 9am-6pm Mon-Sat *Industrial Sales 'Take-Away' by arrangement.
- Industrial accounts available on application: 2 Trade, 1 Bankers Ref.

Soundex Professional Audio Products

Peak Programme Meter Systems, Drive Amplifiers, Meter Movements,
Audio Measuring Sets, On-Air and Rehearsal Lights



BROADCAST SPECIFICATION SOUND MONITORING EQUIPMENT

from

ambit
INDUSTRIAL MARKETING

Soundex have for many years been designing and producing high performance Peak Programme Meter driver amplifiers and associated products

Our products are renowned for quality, performance and economy and are widely used by the BBC, IBA, British Telecom and top broadcasting and recording studios throughout the world

The range comprises Free-Standing PPM Systems, PPM Measuring Sets and Driver Amplifiers meeting BS 5428, DIN 45406 and IEC 268 specifications in addition to low cost units of high performance

Separate Meter Movements are offered in a range of sizes and a choice of 1 to 7, -12 to +12dB including dual pointer types

Other products include a free-standing Audio Frequency Sound Measuring Set to CCIR 468-2, a free-standing PPM Measuring Set to BS 5428 and IEC 268 specifications together with a range of On-Air and Rehearsal Lights

Literature giving full technical specification, dimensional drawings and installation data for individual products is available on request

aim

200, NORTH SERVICE ROAD, BRENTWOOD, ESSEX, CM14 4SG
Telephone: (0277) 231616 Telex: 995194 AMBIT G
DATEL (0277) 232628 RS232 300 BAUD

AMATEUR RADIO WORLD

Compiled by Arthur C. Gee, G2UK

Satellites again head the list of interesting events in the Amateur Radio World. The Russians sent another one up — ISKRA 3 — on the 18th November last. It was launched by hand from the Salyut 7 manned space laboratory, in the same way as the previous ISKRA. It was in a similar low orbit, so its life expectancy was short. In fact, by the end of the month, it was only being heard occasionally and has since ceased altogether. It transmitted telemetry and a code store was in operation at times. A fifteen to ten metres transponder was in operation and used by a number of stations. It is reported that the Russians are proposing to put twenty or so similar satellites into space in the near future, so interest in this sphere of amateur space activity should continue unabated for some time to come yet.

The launch of AMSAT's Phase III satellite is now scheduled for June 3rd. This replaces the one lost when the Ariene L5 failed. If successful this time, it will open a completely new phase in amateur radio communication, as it will be in a quite different orbit from previous Oscars and is a far more sophisticated spacecraft.

Burst Into Life

From time to time rumours abound that previously 'deceased' satellites have "come alive again"! Oscar 7 has been said to be sending out telemetry signals again, but nothing definite has been produced as 'hard copy'. It would have been in continuous sunlight at the time and as it failed in July 1980 through nicad battery failure, it could be that these batteries have now gone 'open circuit' and its solar panels were able to


Another satellite, which sends the code signal "1051", over and over again and signs after a dozen or so "1051"s with "55" has appeared on 29.401 MHz, the frequency of the beacons on the Russian RS 1 and 2, which were thought to be defunct. It is said that it is RS 2 and that it is only switched on when it is within range of Moscow. It is thought to be RS 2, because RS 2 has adequate solar panels, giving it a positive power balance, whereas RS 1 had batteries of low capacity giving a negative power balance. The other satellites are working well, including UOSAT, which has had its Digita-ler switched on at times.

"Mandrake", writing in the "Sunday Telegraph" reported that the Falkland's servicemen's seasonal phone calls home, at Christmas had not been very successful. A suggestion that it would have been better to have used amateur radio facilities for this, in the same way as the USA radio amateurs are able to with their 'patching' technique for their overseas Forces, fell on unsympathetic ears at the Ministry of Defence. British radio amateurs are not allowed by their Licence terms to participate in "third-party" traffic. A M. of D. spokesman said, "If it is illegal, we would not want to be part of it". "Mandrake" puts the blame on Tony Hancock for the credibility gap. The status of the amateur radio operator has never recovered from Tony's "The Radio Ham" all those years ago. "Mandrake" may well be right!

Turning A Blind Ear

Following a report from an official of the Home Office that nine stations were traced and closed down for illegal broadcasting in 1981, a "Wireless World" reader has a letter in the January 1983 issue, quoting a blatant example of continued infringement of the radio regulations by a mini-cab firm in his area. He concludes his letter by suggesting to the Home Office that if they only managed to trace nine cases and need a lead on this matter, they could do worse than "ask the amateurs" — a view this scribe heartily endorses!

From the "Trinity House Gazette" for December last, we learn that Larry Walker, the assistant keeper at Portland Bill Lighthouse, used to operate an amateur radio station at the Eddystone Lighthouse before it ceased to be a manned station. From Portland his latest contacts have been with amateurs in Goose Green (VP8LP) and with Pebble Island in the Falkland Islands. He reports that in the early hours of 5th October last, the Goose Green station received a call from an Argentine station, who very soon went off the air when he realised to whom he had been talking! During the Argentine occupation, assistant keeper Reg Silvey of the Imperial Lighthouse Service, living in Port Stanley, kept up transmissions from "underground" locations even though Cape Pembroke Lighthouse was unworkable.

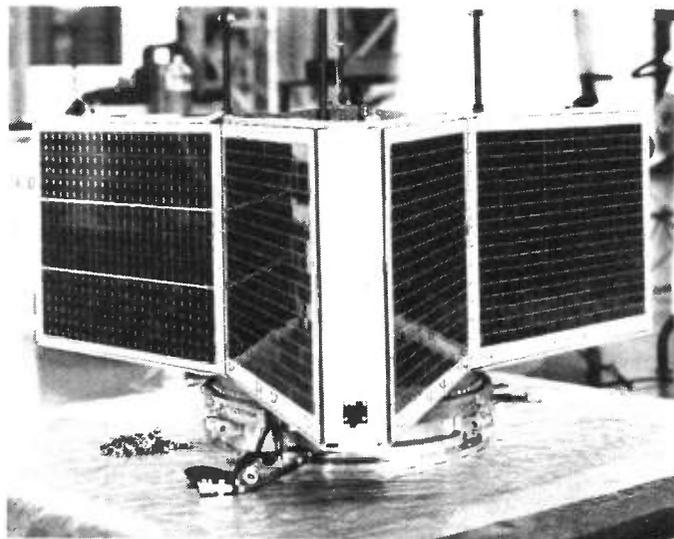

News Review

The "new bands" are beginning to pick up a bit, particularly 10 MHz now that USA and Canada have been given permission to use this band. West Coast and VE stations have been worked in the late evening.

■ R&EW

As you read this, it is anticipated that the replacement for AMSAT's Phase III satellite will have been launched.

CIRCUIT MODELLER

Steve Kirby BSc, York Electronics Centre, evaluates a new software package which enables designers to 'prototype' using a micro.

If you've ever wanted to iron out the bugs from your latest design at the drawing board stage, before ever applying a soldering iron, 'Circuit Modeller' may be the answer. This newly released numerical circuit modelling program will allow you to 'try out' your circuit on a microcomputer before putting it on a breadboard. The package runs on any Z80 based computer with 64K of RAM and at least one floppy disk running under the CPM operating system. In addition, a printer capable of being set to 132 column width is useful for graphical output.

Too Big To Handle

For many years IC designers have had to use computer modelling to debug their circuits, as IC's are so expensive to build in small prototype quantities (around £50,000 for even a single wafer's worth!). Mathematical modelling programs were sophisticated enough to let the designer draw the circuit out on a graphics terminal, using a light pen to select components from a 'catalogue' of standard resistors, capacitors and transistors etc, each with its own mathematical analogue. Programs such as SPICE (written at Berkeley University, California) then worked out the circuits' DC

voltages and currents using complex non-linear models which closely imitate the behaviour of real components. Using this information, a simpler small signal linear model can be constructed and used to predict gain and phase frequency responses from any selected input quantity, to any output, as well as finding frequency dependent input and output impedances.

What's A Linear Model?

A linear model of a circuit is a way of using simple mathematical equations to describe how that circuit behaves in response to a stimulus. The model is made up of linear components. These have strictly linear responses to inputs, that is, the effect (eg current for a resistor) is directly proportional to the cause (voltage across the resistor). This can be expressed as: output = $K \times$ input. With a linear component, if you double the input the output is also doubled.

Some components are naturally linear; resistors, non-polarised capacitors and air-cored inductors (Fig. 1). Operational amplifiers can behave non-linearly in an open loop circuit, but with the large amounts of

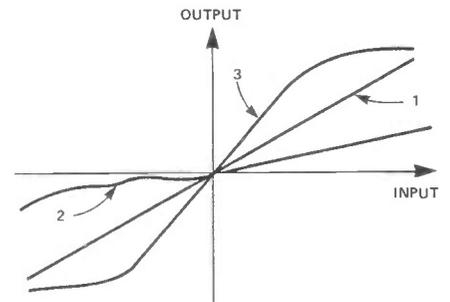


Figure 1. Curves representing the three different component types. Number 1 is for linear components (eg, resistors), number 2 for polarity sensitive components (eg, electrolytic capacitors) and number 3 represents non-linear devices such as op-amps.

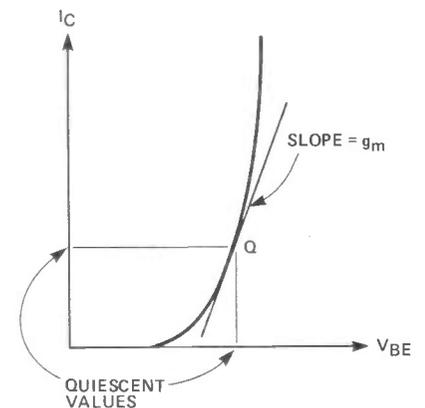


Figure 2. Finding the slope of the I_c - V_{BE} characteristic at point Q.

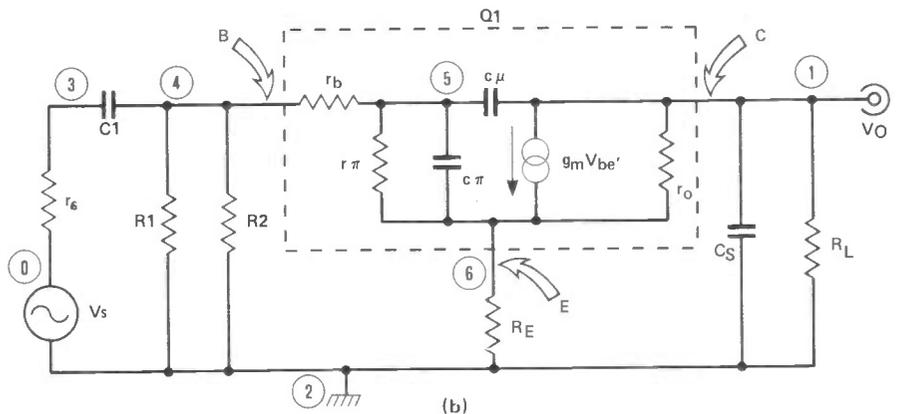
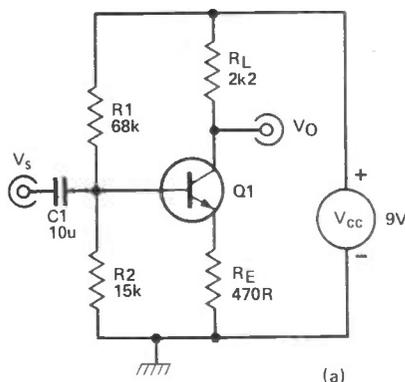


Figure 3. A single transistor amplifier (a) and the linear model (b) which represents it.

negative feedback usually used they are almost ideal linear gain stages. Other components are linear only for a certain polarity of inputs (eg, an electrolytic capacitor behaves very non-linearly if you apply the DC biasing voltage the wrong way around. Ferrite or iron-cored inductors have almost linear responses until the magnitude of the current through them becomes large enough to cause saturation of the magnetic material.

The most important class of non-linear components are transistors and diodes. A transistor's collector current is exponentially related to the base emitter voltage, as given by $I_c = I_s \times \text{Exp}(V_{BE}/V_T)$, which is a very good approximation to the experimental behaviour of most transistors. (I_s is a constant and V_T is the so called thermal voltage, KT/q , directly proportional to absolute temperature T , and about 26mV at 25°C). This extremely non-linear behaviour can only be fitted into the pattern for passive components if a small enough change in the base emitter voltage, from its average quiescent value, is used as the input. Then the output collector current can be "linearised" using the slope of the $I_c - V_{BE}$ characteristic at the quiescent point (Q on Fig 2). By differentiation, the slope can be found from I_c/V_T and is in amps output per volt input, called the "transconductance" (denoted by g_m). Using small subscripts to denote very small (Δ 1% typically) changes in the variables, the formula may be written as $i_c = g_m \times v_{be}$.

This is just what we need for finding a frequency response, the AC input can be made small enough so that it does not disturb the DC quiescent conditions, and all the non-linear semi-conductors can be replaced by models that accurately "mimic" them at their working point. Models of bipolar transistors, JFETs, diodes and MOSFETs are all given in the CM theory manual.

A Case In Practice

To show the way of using linear models with CM, consider the single transistor amplifier in Fig. 3a. We want to know what the small signal frequency response (gain and phase) is, from the voltage source input to the collector voltage output. A quick calculation shows that I_c is approximately 2mA, so g_m is 0.077V/A. Fig. 3b is the small signal equivalent linear model of Fig. 3a. You may have noticed that some peculiarities have appeared, and the supply voltage has disappeared! To the

small AC signals, the large decoupling capacitors in the power supply look like a short circuit to ground, and as we are only interested in small signal changes in current through the resistors, the DC quiescent currents are omitted — V_{cc} is at ground potential for small signals. The 'driving power' for the output comes from the floating current source $g_m \cdot v_{be}$.

The input voltage source, V_s , has an output resistance modelled by R_s (say 10R). The transistor linear model is within the dotted line. The resistor, r_o , models the bulk silicon and connection resistances between the external base lead and the internal active base, and is very important in high frequency or low noise circuits. It is the voltage v_{be} across the lower limb of the potential divider resistor r_π which controls the collector current source $g_m \cdot v_{be}$, implementing the small signal model equation.

The base current i_b is β_s times less than i_c , (β_s is the small signal AC current gain at quiescent current I_c and r_π is:

$$r_\pi = \frac{v_{be}}{i_b} = \frac{v_{be}}{i_c/\beta_s} = \frac{\beta_s}{g_m} \quad \therefore r_\pi = 3246\Omega$$

The slope of the I_c/V_{CE} characteristic is modelled by the collector emitter resistor r_o (Fig. 4). At high frequencies (say Δ 1MHz) very small junction and packaging capacitances have large effects on the transistor's gain. These effects are modelled by C_π , C_u and C_s . Typical values for these components are $C_u=2p$, $C_\pi=5p$, $r_b=100R$, $r_o=100k$. This type of transistor model is called the "hybrid pi" after the two part hybrid pi model parameters (ie, the "famous" H_{FE}).

Circuit Modeller expects you to find the DC quiescent currents and turn the real circuit into a linear model yourself. In many cases the quiescent par-

ameters are not too time consuming to calculate, or the parameters could just as well be measured on a breadboard; the circuit acting as an analogue computer solving its own equations! The model has an input voltage node (0 by CM convention), output (1), ground (2). Only node 0 is constrained to a given voltage (V_s), so there are five free nodes and at each of them we can use Kirchoff's current law and say the algebraic sum of all current into the node is zero. A bit of fairly tedious algebra gives us the five equations in Fig. 5, one for each free node. These equations fall into a five-by-five pattern — for N unknown voltage nodes you

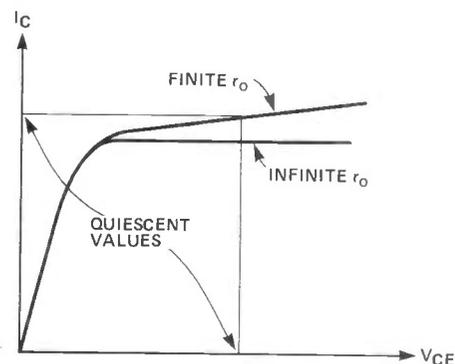


Figure 4. Graph showing the I_c/V_{CE} characteristics is modelled by R_o .

need N equations and an array (N x N) of coefficients. At this point (given a free week or two) you could solve the equations for the unknown voltages, using the algebraic symbols. A slightly quicker method is to substitute in numerical values for all the complex impedances (for a particular input frequency) and solve it using matrix algebra and techniques such as Gaussian elimination. However, with Circuit Modeller this is all done automatically in a few seconds. The "number crunching" inner core of the

$$\begin{aligned} 0.V1 & - \frac{(1+j\omega C_1).V3}{r_s} + j\omega C_1.V4 + 0.V5 + 0.V6 = \frac{v_s}{r_s} \\ 0.V1 & + j\omega C_1.V3 - \frac{(j\omega C_1+1)}{R_1} \frac{+1}{R_2} \frac{+1}{r_b}.V4 + \frac{1}{r_b}.V5 + 0.V6 = 0 \\ & + j\omega C_\mu.V1 + 0.V3 + \frac{1}{r_b}.V4 - \frac{(1+1+j\omega(C_p+C_\mu)).V5}{r_p} + \frac{(1+j\omega C_p).V6}{r_p} = 0 \\ & + \frac{1}{r_o}.V1 + 0.V3 + 0.V4 + \frac{(1+j\omega C_\pi + g_m).V5}{r_\pi} - \frac{(1+j\omega C_\pi + g_m+1).V6}{R_E r_o} = 0 \\ & -(j\omega(C_\mu+C_s)+1) \frac{+1}{r_o} \frac{+1}{R_L}.V1 + 0.V3 + 0.V4 + (j\omega C_\mu - g_m).V5 + \frac{(g_m+1).V6}{r_o} = 0 \end{aligned}$$

Figure 5. Using Kirchoff's current law to equate the five free nodes.

NEW	Create new model (clears old model).
ADD	Add components to the model.
EDIT	Edit (or delete) existing components in model.
PRINT	Print out values and node connections of model components.
LOAD	Load a model previously saved on disc.
SAVE	Save the current model on a named disc file.
GAIN	Obtain gain and phase at a given frequency.
ZIN	Obtain input and output impedances.
PLOT	Plot graph on printer of log gain and phase against log freq.
BW	Find the centre freq. and bandwidth of amplitude response.
SEARCH	Search for a frequency at which a given gain occurs.
OPTION	Set options for graph phase (+/- 180° or full scale).
SYMBOLS	Change the symbols used in plotting graph.
?	To obtain help if you're stuck.

Table 1. Complete listing of the Circuit Modeller commands.

programs are all written in optimised Z80 machine code running hundreds of times faster than an interpreted BASIC version. CM solves purely for the gain and phase of the output (V(1)-V(2))/input (V(0)-V(2)), but by using a unity gain controlled voltage source (CVS), as a mathematical floating voltmeter, you can pick off the voltage between any pair of nodes as the output, and similarly use another CVS controlled from input nodes (0) and (2) as a floating signal generator.

So, Circuit Modeller can take the grind out of complex mathematical calculations, whilst at the same time getting over the problem of limited memory on microcomputers. It does this by a combination of clever programming, limiting the size of circuit that can be handled and providing only a linear model frequency response analysis. CM can work on circuits with up to 32 nodes, made up with a maximum of 101 each of capacitors, resistors and inductors, 31 mutual inductors and 31 voltage or current sources.

What Can CM Do

It is best to look at CM's facilities by actually modelling different types of circuit. CM is full 'menu-prompted', so it is very easy and quick to learn. The single transistor amplifier linear model mentioned earlier would be entered as in Table 2

The features contained in CM are also worth explaining. Node 0 is always the input driven by an ideal voltage source, whose other terminal is connected to pin 2 (node 1 is the output). Current and voltage sources, whose magnitude are controlled by the voltage between a pair of nodes, are available and can be used both in active device models, and to have floating input drives or output pickups (eg, the frequency response of the current in

the 100R base resistance could be made the output by having a voltage source controlled by nodes 4 and 5 driving nodes 1 and 2-the present node 1 should be changed to node 7 using the ADD command. Now we can ask for a gain at a particular frequency by typing the command keyword GAIN. CM will print out the gain (within a range of ± 600dB) at any specified frequency from well below sub-audio to near infra-red frequencies!

The most commonly used CM feature is the PLOT of log gain in dB and phase against log frequency. CM asks for an upper and lower frequency and

? NEW	(clear any existing model and accept new values)
*RO 10,0,3	(resistor between nodes 0 and 3, 10 ohms)
*RK 15,4,2	(15K resistor, RK used for value in kilohms)
(etc.)	
*CU 1,3,4	(CU used for capacitor in microfarads)
*CP 5,5,6	(CP used for capacitor in picofarads)
(etc.)	
*CS	
gm (A/V) ? 0.069	
Rout ? 100E3	(Exponents can be used for brevity)
current flows towards node number ? 6	
current flows from node number ? 1	
controlling voltage positive terminal node number ? 5	
controlling voltage negative terminal node number ? 6	
* (return)	
	(now CM asks you if you want the model saved on disc file, this can be later re-loaded with the LOAD command)

Table 2. Statements typed on the computer to enter the model of figure 3.

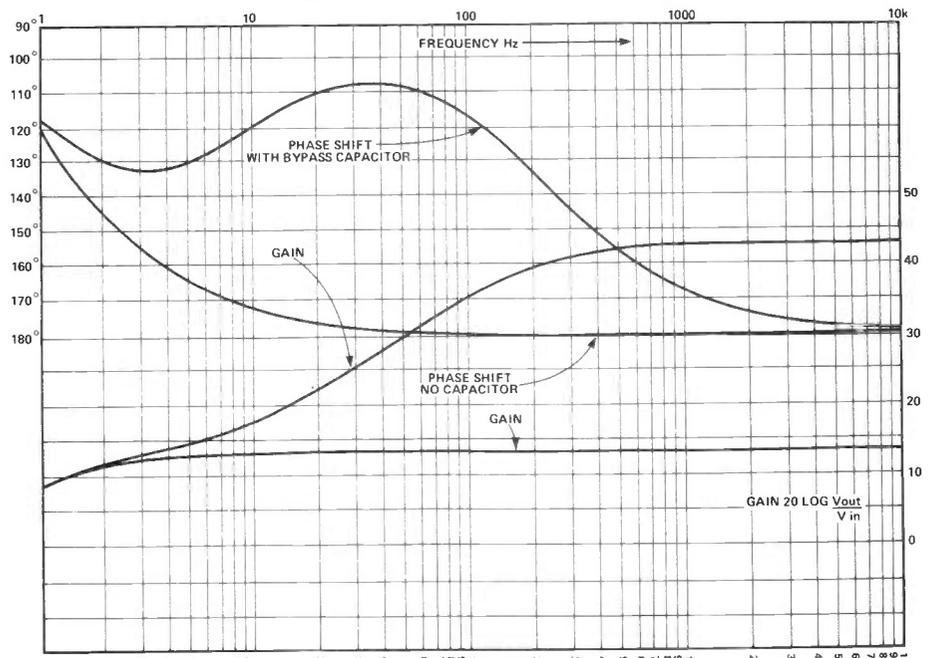


Figure 6. Plot of log gain (dB) against log frequency (Hz) of figure 3.

the number of steps to be plotted. After some calculation (the model above took 40 seconds for 50 steps from 1Hz to 10MHz) the graph is plotted out on the device expected to be a 132 column line printer (see **Fig. 6**). The dB axis is scaled automatically over the full range of calculated gains, which is a bit of a nuisance if you want it calibrated in 10dB steps. The phase can be calibrated to either a $\pm 180^\circ$, or full calculated range using the OPTION command. The component connections and values are listed on the printer by the PRINT command. The wide band gain of 4.7(13dB) and the input coupling capacitor induced 1.4Hz high pass break frequency can be clearly seen, as can the effect of the transistor junction capacitances in the output excess phase shift above 300kHz (note the phrase "wraps around" when in excess of 180°). The effect of bypassing the emitter resistor can be found by using the ADD command to put a 50u capacitor in parallel with RE, and re-running PLOT (see **Fig. 8**).

The ZIN command finds the complex input and output impedances at nodes 0 and 1, at a given frequency: (11,170-j159,000)ohms input, (2,194 + j0.297) ohms output impedance for the above circuit at 0.1Hz. You stay in each of the command program sections until a single return is typed so the same command can be re-run very quickly. For example, the ZIN command loops back and asks for another frequency at which to calculate impedances.

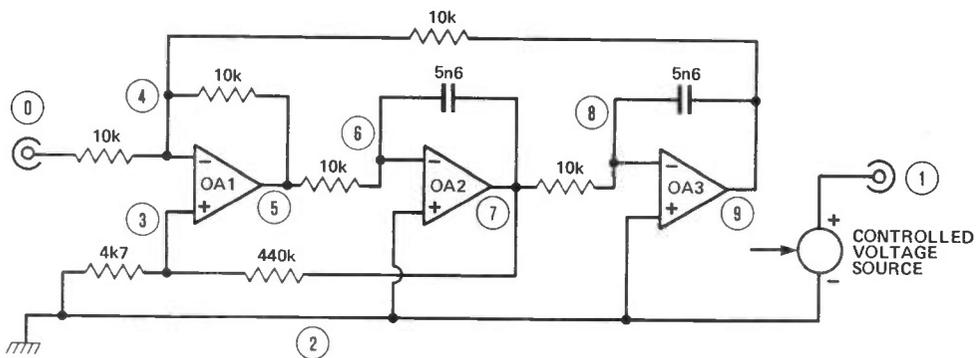


Figure 7. State variable bandpass filter circuit.

There are built-in models of common operational amplifiers (eg, 741 and TL081) or you can 'build' your own. The model has a specified differential input resistance, voltage gain, output resistance and single pole break frequency. These were used to plot the response of the circuit in **Fig. 7**, a state variable bandpass filter. The high, low and bandpass output (**Fig. 8**) were obtained by using EDIT to connect the control terminals of the output voltage source to ground and the outputs of op-amps 1,2 and 3 in turn.

You can find the frequency at which a particular gain occurs using the SEARCH command. This works iteratively from an initial 'guess' value you give, and will only converge for gains on a sloping part of the response. A second type of automatic search, the BW command, can find the centre frequency and upper and lower -3dB

points of bandpass type circuits (including LC tuned filters containing mutual inductors) again working from an initial 'guess' (best found using PLOT) for the centre frequency. BW gave the centre frequency of the circuit in **Fig. 3** as 2.85kHz, upper 2.885kHz and lower 2.798kHz, bandwidth 86.6Hz.

To leave space in the memory for the large array of circuit equation coefficients the active part of the program, which implements a particular command, is only brought in from disk when needed. This 'overlay' system means there are some disk transfer delays, though they are not too noticeable in practice.

Summing Up

Two manuals are supplied with CM, both being blessedly short. A 17-page operating manual quickly and simply describes how to use CM with many examples, and a theory manual briefly outlines linear circuit theory and mathematical modelling and gives a partial explanation of how CM works. The manuals are clearly written and printed and include an index for quick reference.

Circuit Modeller itself is a useful tool, which matches up to the author's claims. Within the limitations of a small signal linear model it can perform useful circuit analyses and save significant amounts of time, especially in filtering circuits. The user is responsible, however, for ensuring that the linear model used is suitable for the real circuit being designed and built. I found it best to use CM in conjunction with a few hand calculated analytical equations, and compare the predicted performance with that measured on the scope ... no I won't be selling my soldering iron just yet!

■ R&EW

Circuit Modeller is produced by Harcourt Systems and marketed by Seasim Control Limited (01-346-9271).

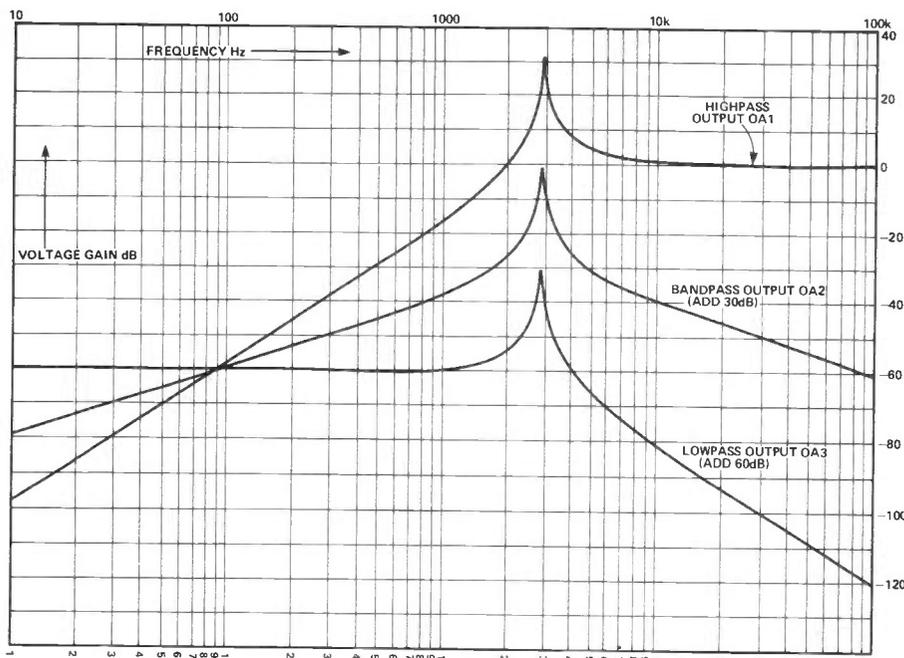


Figure 8. Plot of voltage gain against frequency for the figure 7 circuit.

Peter Luke reveals the shape of cameras to come and casts his eye over a varied range of new recorders.

Flat screen TV sets, that would herald the end of the cathode ray tube with its power hungry heater and fragile collection of electrodes, are still some way off from a production line reality. A similar revolution in camera technology is, however, here with us today in the shape of the Hitachi VK-C2000E.

Outwardly the new camera looks little different from 'ordinary' cameras, although it's smaller than most. The reason for this small size is that the bulky vidicon/saticon/tricon tubes of the current generation of cameras has been replaced by a MOS image sensor. The advantages of a semi-conductor image sensor are manifold — low power consumption, robustness and an almost infinite life are perhaps the more obvious — but it is only until recently that adequate definition has been available from such devices.

A MOS image sensor is made up of a grid of light sensitive elements, each element in any row being connected to a CCD type shift register. The information from each point in a row can thus be output serially and the serial data stream from each row then added to similar information from other rows in the familiar order of a TV scanning frame. That's a very simple overview of the operation of the MOS element, not taking into account the requirements of encoding information as to the hue of any picture point (we'll go into more detail in a future issue of **R&EW**). Even this brief explanation of the system shows, however, that the other bulky and power hungry elements of conventional cameras — the scan coils — can also be dispensed with.

So much for the technical aspects of the camera — what about its specification and performance?

Gathering MOS

Ergonomically the camera is a delight, with an adjustable shoulder brace that allows the camera to fit snugly over the shoulder to provide a convenient and stable filming position.

For an £800 camera, the controls are perhaps rather spartan. A white balance control, auto fade in/out and a

standby switch about cover them. There's a lot to be said for keeping things simple however, and the camera is delightfully easy to operate.

In terms of performance, the camera offers a quality that is not matched by many more conventional designs. Resolution is claimed at 450 lines — not many recorders will be able to take full advantage of this though — while the accuracy with which the camera reproduced colours was impeccable.

Perhaps the most notable feature however, was the lack of any 'comet-tailing' that is the scourge of most domestic 'tube-based' cameras. In fact the lack of lag on the Hitachi is only matched by broadcast standard cameras.

The camera will be available in the UK later this year and anyone considering the purchase of a top-of-the-range conventional camera, should take a look at the Hitachi first. It is definitely the shape of things to come.

Newcomers

Sanyo's VTC 6500 means the company now have a representative in the fashionable front-loading market. At £450 the recorder looks to be good value, offering as it does a 14 day, 8 event timer plus IR control and a

healthy complement of trick video facilities.

JVC can now offer their VHS-C format system as a £1000 odd camera/recorder package. The six month wait since the announcement of the model looks to have been worth while.

Mitsubishi have two new recorders in the shops. One, the HS 320, is a fairly conventional mains based machine though it comes with a fairly comprehensive range of facilities including Dolby noise reduction and an 'elapsed time' tape indicator — some day all tape indicators will be like this. The other machine, HS 700, is billed as a transportable in that it is a cross between a mains based machine and a portable (battery powered) machine. As one manufacturer has already had a fairly disastrous experience with such a hybrid, it's difficult to see how this model will find a market niche for itself — still at £450 it's not too expensive.


Philips have joined the ranks of those offering portables with their VR2220. It's a bit late in the day though, and the VHS and Beta camps are already further down the 'small is beautiful road'.

On the subject of smaller and smaller, Sony have demonstrated a recorder/camera combination that makes use of full size Beta cassettes. The system uses a 'half-size' head drum yet maintains compatibility with the format by extending the tape path. This approach looks on the surface to be more attractive than the non-standard — though compatible — VHS-C cassettes.


To round off this tip-toe through the new releases, it's good to note that the excellent NV-100 portable from Panasonic (reviewed in the March 83 issue of **R&EW**) is appearing in a number of different guises.

Two camera companies with very good reputations, Canon and Olympus, have adopted the NV-100 and are now pushing it through their networks of photographic dealers. The days of the cine camera do indeed seem to be numbered.

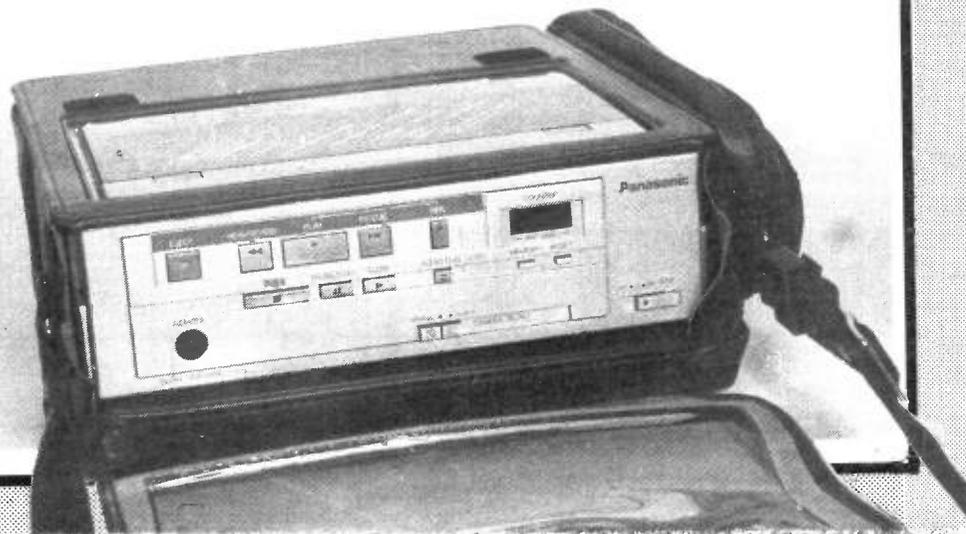Panasonic's NV-100 is now appearing under the banners of both Canon and Olympus



100W POWER AMPLIFIER

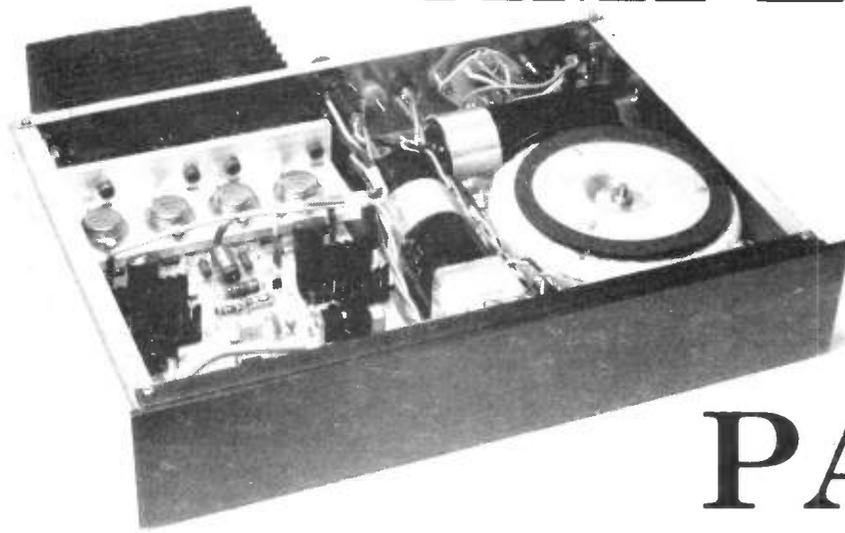

PART II

The second and concluding part of our amplifier project, designed by Steven Marshall and Derek Frost, deals with construction and installation.

Last month we discussed the design of the power amplifier, including a description of the circuit and overlay diagrams. This month we continue with the construction and conclude by explaining how to integrate two amplifiers into your present system.

Construction

Begin by fitting Q7 and Q8 with their respective heatsinks, not forgetting to use a good smear of heatsink compound and lock washers, but do not tighten finally as yet. The temperature sensing transistor, Q3, should now be mounted next to the heatsink of Q8. The flat surface of Q3 must make good thermal contact with the surface of the heatsink. Therefore, before soldering, apply a blob of heatsink compound to the junction. Solder in, ensuring that Q3 remains flat, if necessary, bending the leads slightly after soldering. This is the most important part of the early construction and must be correct to ensure good thermal tracking for the output stage.

Continue by mounting the other components on the board, with, as ever, care over orientation of transistors, diodes and capacitors.

The wirewound resistors (R26,27,28, 29,30,31 + 32) and R33, the 2 watt carbon resistor wound with L1, should be mounted with an airspace between resistor body and board of at least 1/8" to allow for cooling. This is particularly important in the case of R27 and R28 which can get very hot when driving low impedance loads.

At this point, check the solder side of the board for solder bridges or dry joints,

and double check component orientation on the top side. A mistake here could prove to be very expensive!

Next, study the diagram showing the power transistor mounting, which is **not** according to normally accepted practice, ie, there is an airspace between the PCB and heatsink bracket, to allow circulation of air all around the bracket. Note also that the two NPN power transistors are mounted in reverse with respect to each other, and the same is true for the PNP pair. This is to avoid a long connecting track between the two

base connections. We found it helped to mount the transistors and To3 insulating washers with the usual liberal smearing of heatsink compound, to the bracket, then drop the eight mounting bolts through, holding all in place with sellotape. The whole assembly may then be turned over for fitting the plastic bushes into the aluminium bracket and then finally, the PCB and nuts with shakeproof washers just fingertight at this stage.

With a multimeter set to a high resistance range, check that the power

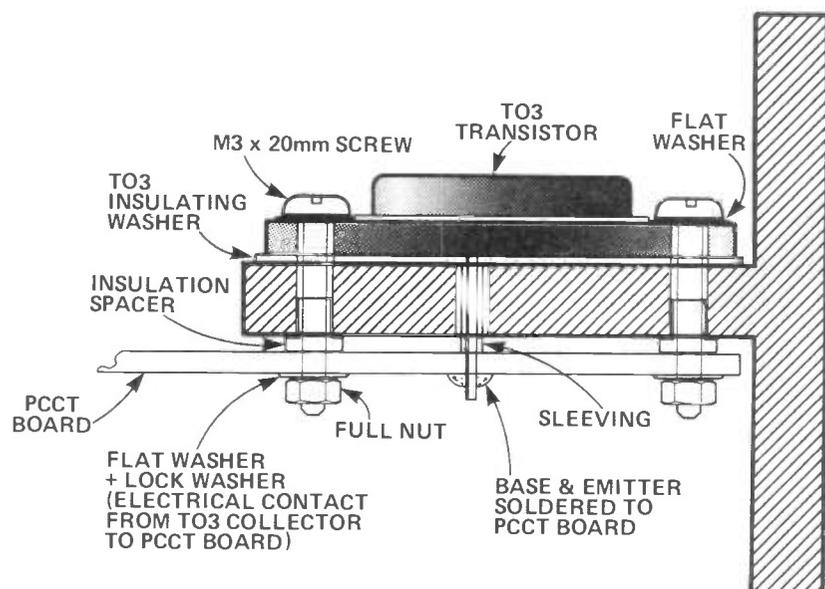


Figure 1: Heatsink bracket section showing power transistor mounting.

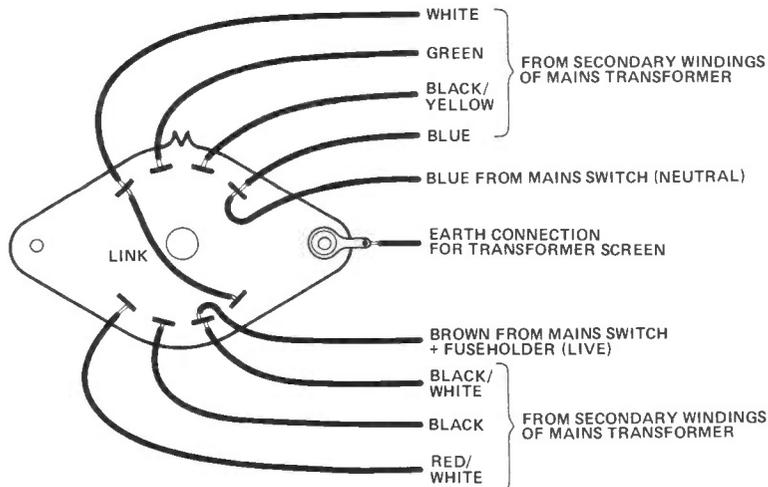


Figure 2: Rear view of voltage selector showing connections.

transistor cases are open circuit with respect to the aluminium bracket. If so then tighten the nuts and repeat the check, soldering the transistor leads if all is OK.

The discovery of a short between case and bracket will mean dismantling and checking for burrs on the bracket drilling or reversed transistors etc. (Do not solder output transistors before tightening mounting bolts or curing short circuits). The PCB is now complete and may be put aside. Construction of the protection board is straightforward if the overlay is followed and, as before, all components correctly orientated. The majority of components are vertically mounted due to the size of the relay and ideally, should be mounted with the relay fitted but not soldered until assembly is completed. This completes the board construction and assembly of the metalwork may begin with a trial assembly of all parts of the casing with the exception of the front panel.

The next stage is to assemble the rear panel assembly with sockets, fuseholders, etc. Remembering that the input socket is insulated from the case with two small bushes.

The phono socket should be fitted with the piece of audio coaxial cable,

since it will be difficult to install after the back panel and chassis are assembled.

The two heatsinks should now be bolted to the aluminium bracket with the four socket headed bolts and a good coating of thermal compound. The back may now be dropped over the heatsink in the second slot from the board end, and the whole assembly slid into the chassis. After fixing the back with self tapping screws, the two holes in the chassis should line up with those in the bottom of the heatsink. If so, insert two M5 pan head screws into the heatsinks through the chassis and tighten up. Fit support pillars to PA board and install those for the protection board.

Next, fix the mains switch bracket to the chassis and then the switch to the bracket. At this point, the mains wiring from socket to switch and switch to voltage selector may be completed. Followed by installation of the transformer. Follow the diagram for connections of the primaries to the selector very carefully after passing all primary leads through a piece of sleeving. Double check afterwards since the

selector is obscured by one of the smoothing capacitors.

Bolt the bridge into place, followed by the smoothing capacitors, and lastly the protection board, adjusting the positions of transformer and capacitors if required, so that they do not touch each other, then tighten everything up.

Wiring may now begin, following closely the colour coding and layout shown, to ensure stability and low noise.

The indicator LED should have its three leads connected and sleeved and the plug installed at the other end of the leads. Insert it into the front panel so that it is flush with the front and cement into place with a small dab of adhesive, impact (**not** superglue, which will attack the finish of the front panel). When the glue has dried off, preferably overnight, the front panel may be fitted and screwed carefully into place, at which point you are ready to begin testing.

One small word of warning. When interboard wiring is complete, but before

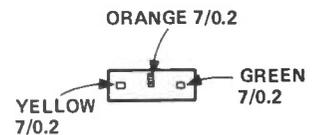


Figure 4: Rear view of indicator LED showing connections.

connecting the transformer secondaries to the bridge rectifier. It is a good idea to switch on the mains supply and check that the correct AC voltages are appearing at the secondary connection leads (ie, 40.0.40 volts approx). A fault would indicate an incorrectly assembled mains voltage selector which **must** be corrected before proceeding further (22000u capacitors make a very loud bang when treated to an excess of voltage!) If all is well, connect the transformer to the bridge.


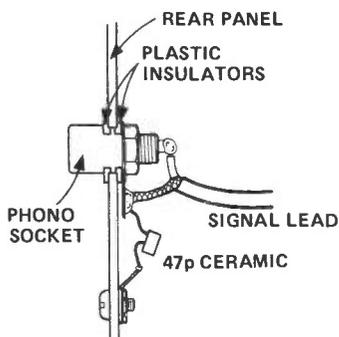


Figure 3: Rear panel section showing phono socket and plastic insulators.

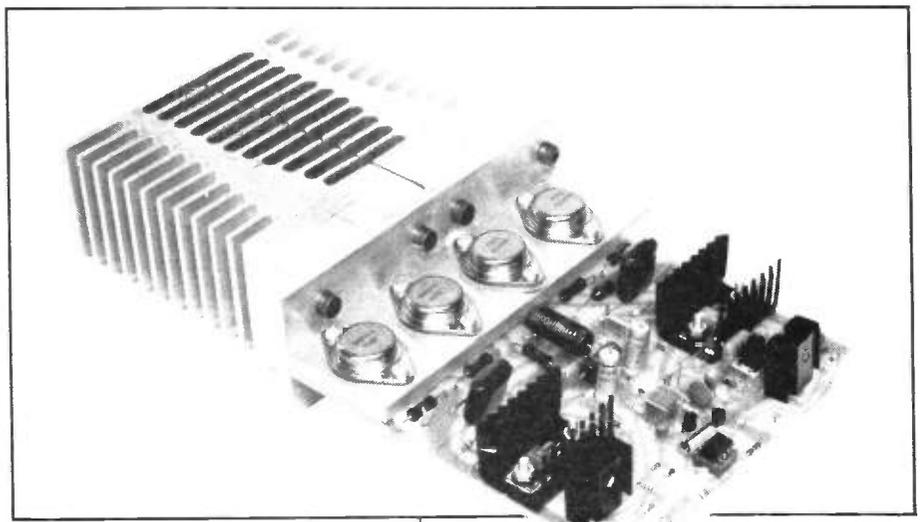

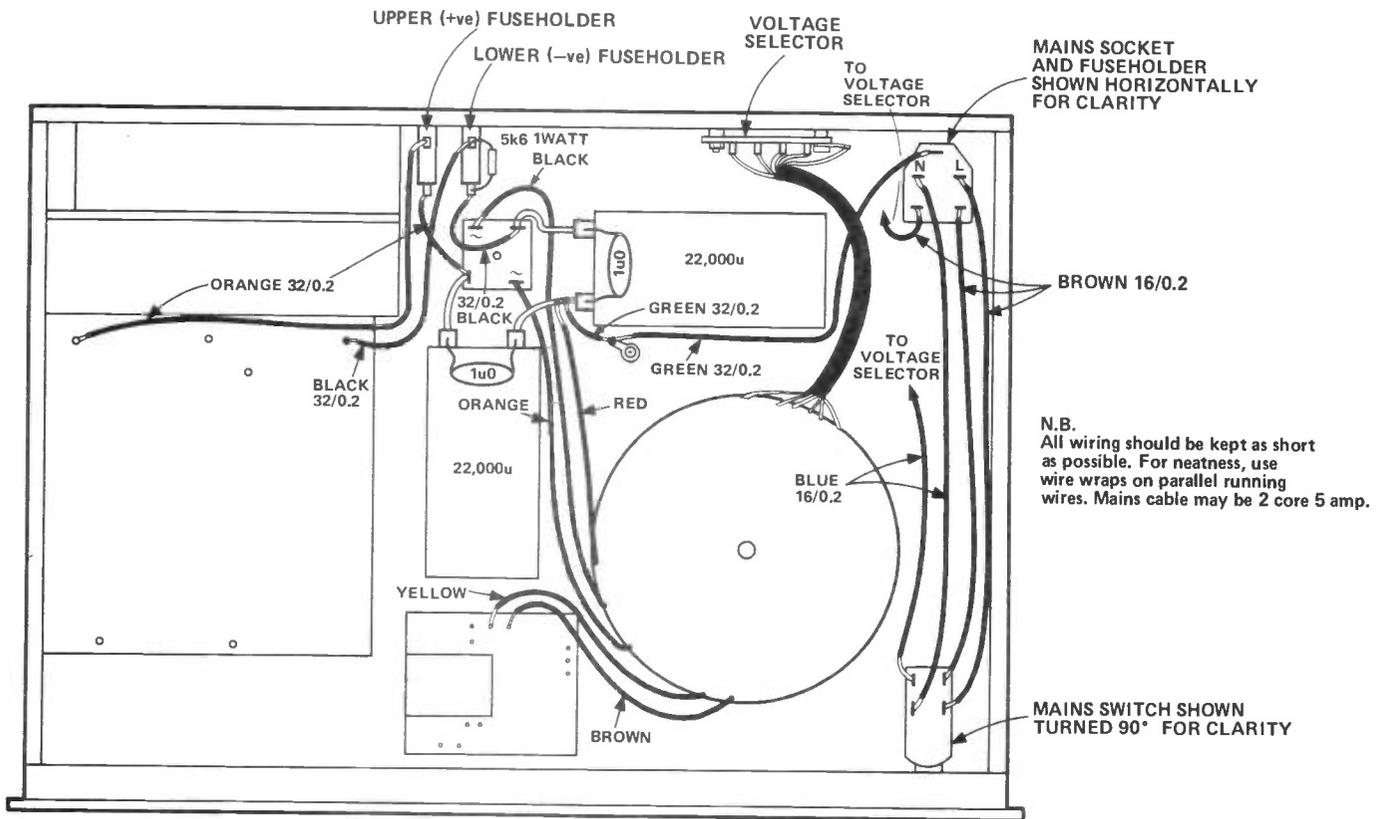


Figure 5: Main amplifier power supply wiring.

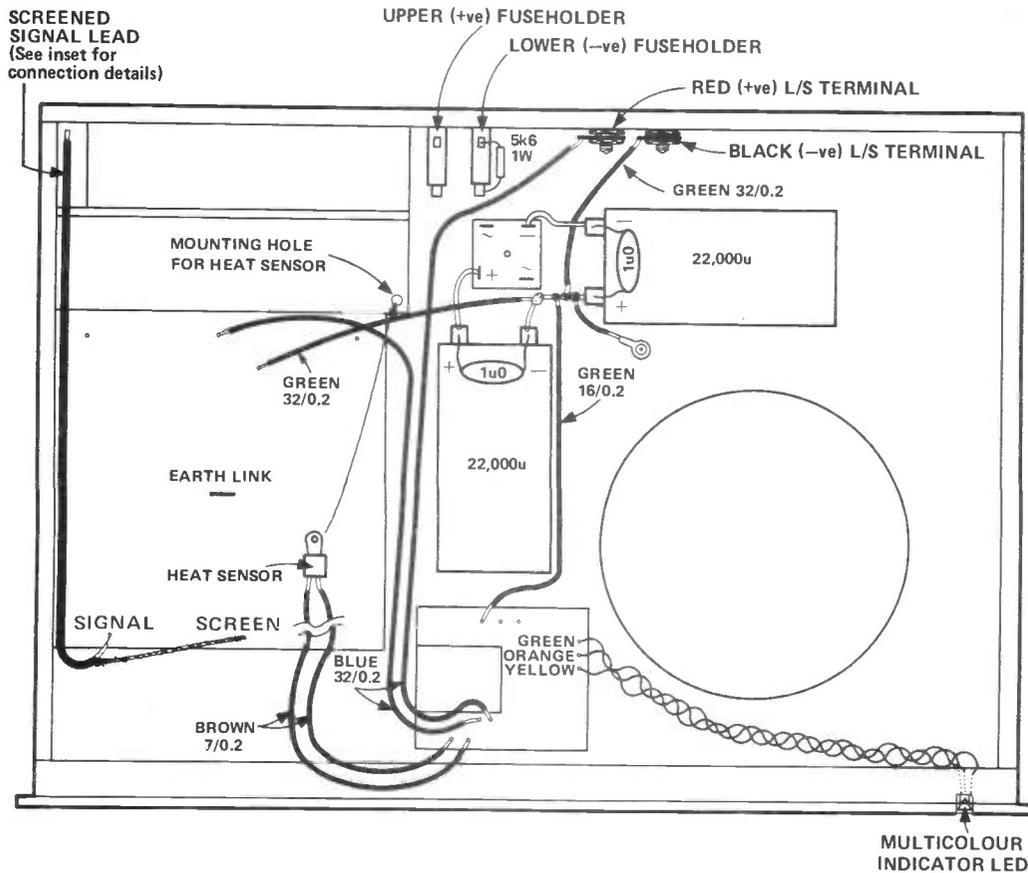


Figure 6: Main amplifier signal wiring. ▶

Setting Up

Begin by removing both supply line fuses (if fitted), turning RV1 fully anticlockwise, and setting voltage selector at 240V. Connect a 1 watt 1k Ω resistor across the upper(positive) fuseholder and a 1 watt 1k Ω resistor across the lower fuseholder in parallel with 5k6 1W already in this position. This will serve to current limit the amplifier temporarily in the event of a fault.

Switch on mains power, whereupon the LED on the fascia should glow red initially, and turn green after 8-10 seconds.

Check that the DC voltages on the amplifier side of both fuseholders are \pm 24 to 26 volts. Monitoring the positive supply voltage at the same point, gradually turn RV1 clockwise, when the voltage at the half way point should drop to 20 to 21 volts. Return RV1 to zero (fully anti-clockwise). This indicates that the amplifier is working and quiescent current is adjustable.

Owners of an oscilloscope and signal generator may confirm this by injecting a 1kHz signal at 300mV, to give an output of approx 10V.

Capacitors of this size retain sufficient charge to destroy a good sized screwdriver or soldering iron bit for some time, so proceed by disconnecting the mains, then discharging both capacitors with a 1-2 watt 100 ohm resistor. Remove the 1k Ω and 1k Ω resistors previously added for current limiting, insert the lower (-ve) fuse, and connect a meter set to 100-200mA f.s.d across the +ve fuseholder, observing the correct polarities.

Switch on the amplifier and check for the LED to change from red to green. With RV1 still fully anticlockwise (this ensures that the output transistors are turned off) the amplifier should draw approx 40mA.

The output stage quiescent current should now be set to 20mA per device pair (40mA total), by turning RV1 slowly clockwise. This is in addition to the initial current — if initial current is 38mA then set final current to 78mA or if 42mA then set to 82mA.

This should all be done with no load or signal and amplifier at ambient temperature of 20°C approx. Replace +ve fuse, then check that voltages on amp board agree with those on circuit diagram.

In Use

The amplifier is nominally rated at 100 watts, but a brief look at the specification from last month's article will indicate that it is capable of vastly more than that. If you are using 4-ohm loudspeakers, that is, the impedance curve drops to 4 ohms or less, don't forget that the delivery is in excess of 200 watts — even 2 ohms can be coped with, and in this case 240 watts continuous is supplied. This means there are large currents flowing, so the loudspeaker leads must be able to carry them.

An ideal place to situate the power amps is under, or very close to, the loudspeakers, connected by the shortest possible lengths of heavy (at least 15 amp, preferably 30 amp) cable, or any of the super quality audio cables if you already have some. Remember to ensure that all connections are very tight and secure, and you'll be in for the listening experience of a lifetime!

■ R&EW


Accurate Digital Multimeters at Exceptional Prices

28 RANGES, EACH WITH FULL OVERLOAD PROTECTION

SPECIFICATION MODELS 6010 & 7030

- 10 amp AC/DC
- Battery: Single 9V drycell. Life: 200 hrs
- Dimensions: 170 x 89 x 38mm.
- Weight: 400g inc. battery.
- Mode Select: Push Button.
- AC DC Current: 200 μ A to 10A
- AC Voltage: 200mV to 750V
- DC Voltage: 200mV to 1000V
- Resistance: 200 Ω to 2M Ω
- Input Impedance: 10M Ω
- Display: 3 1/2 Digit 13mm LCD
- O/Load Protection: All ranges

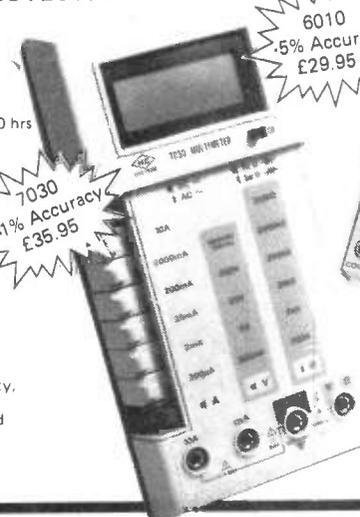OTHER FEATURES: Auto polarity, auto zero, battery low indicator, ABS plastic case with tilt stand, battery and test leads included, optional carrying case.



6010
0.5% Accuracy
£29.95

7030
1% Accuracy
£35.95

NEW ANALOGUE METER WITH CONTINUITY BUZZER AND BATTERY SCALE

NEW
HM102 BZ
£13.00

NEW HM 102 BZ SPECIFICATION

- DC Voltage: 0-25, 1, 2.5, 10, 25, 100, 250, 1000 volts 20,000 ohms/volt.
- AC Voltage: 0-10, 25, 100, 250, 1000 volts 10,000 ohms/volt.
- Decibels: -20 to +22dB
- DC Current: 0-50, 500 μ A, 0-5, 50, 500mA
- Ohmmeter: 0-6 Megohms in 4 ranges. 30 ohms Centre Scale
- Power Supply: One 1.5V size 'A' battery (incl)
- Size & Weight: 135 x 91 x 39mm, 280gr.




HM 101 POCKET SIZE MULTIMETER SPECIFICATION

- DC & AC Voltage: 0-10, 50, 250, 1000 volts, 2000 ohms/volts
- Decibels: -10 to +22dB
- DC Current: 0-100mA
- Ohmmeter: 0-1 Megohm in 2 ranges, 60 ohms Centre Scale
- Power Supply: One 1.5V size 'A' battery (incl)
- Size & Weight: 90 x 60 x 29mm, 92gr. incl. battery
- Price: £5.50

Add 15% to your order for VAT. P&P is free of charge. Quantity discount for trade on application.

ARMON ELECTRONICS LTD.

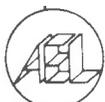

Cottrell House, 53-63 Wembley Hill Road, Wembley, Middlesex HA9 8BH, England

Telephone 01-9024321 (3 lines)

TELEX No 923985

XTAL'S

MANUFACTURER IN AND EXPORT OF PIEZO-ELECTRIC CRYSTALS

We have a two working day service ! small orders accepted !



BOERENKRIJGLAAN 40 3180 WESTERLO
TEL. (0)14-54.78.63 TLX. 72470 XTAL BELGIUM

MASTER ELECTRONICS NOW!

The PRACTICAL way!

You will do the following:

- Build a modern oscilloscope
- Recognise and handle current electronic components
- Read, draw and understand circuit diagrams
- Carry out 40 experiments on basic electronic circuits used in modern equipment
- Build and use digital electronic circuits and current solid state 'chips'
- Learn how to test and service every type of electronic device used in industry and commerce today. Servicing of Radio, T.V., Hi-Fi and microprocessor/computer equipment.



New Job? New Career? New Hobby?
Get into **Electronics** Now!

FREE!
COLOUR BROCHURE

Please send your brochure without any obligation to

NAME

ADDRESS

.....

BLOCK CAPS PLEASE

POST NOW TO:

**British National
Radio & Electronics School**
Reading, Berks. RG1 1BR
REW6/817

I am interested in

COURSE IN ELECTRONICS as described above

RADIO AMATEUR LICENCE

MICROPROCESSORS

LOGIC COURSE

OTHER SUBJECTS

RADIO DIRECTION FINDER

MODEL DF

Model DF is a revolutionary Radio Direction Finder which immediately indicates the direction of an incoming radio signal while it is being received on your existing NBFM communications receiver.

Any narrow band FM receiver or transceiver in the range 20 to 200 MHz is suitable and provided the signal is received as NBFM, even AM and SSB signals will give a reading.

FEATURES

- ★ Works with any existing narrow-band FM receiver or transceiver without modification. The only connections required are to the external speaker and antenna jacks.
- ★ Gives a clear directional readout on a circular array of sixteen bright green LEDs.

- ★ Easy to use and install.
- ★ Only a single coaxial cable needed between display unit and antenna combiner.
- ★ Broadband from 20 to 200 MHz, operating frequency determined by the chosen antennas and receiver.
- ★ Magmount option for combiner unit.

APPLICATIONS in which Model DF is already being used successfully include: finding PMR transceivers with stuck microphones, locating pirate transmitters, tracking mobile transmitters of various kinds, location of anti-social CB or amateur radio users (see review in "Citizens Band", January, 1983), retrieving stolen transceivers. Existing customers include both professionals and hobbyists.



COMBINER UNIT MAIN UNIT

SYSTEM DETAILS

A complete system comprises display unit and antenna combiner plus four antennas mounted at the corners of a square spaced apart by 0.05 to 0.3 wavelengths.

For fixed station use, four dipoles are suitable while four magnetically mounted quarter wave whips are ideal for mobile use. Depending on the choice of antenna, the system will operate from 20 to 200 MHz. Suitable magmount quarter wave whips are available from Datong for VHF use.

- * Basic System (model DF display unit with Model DFA1 combiner) £149.00 + VAT (£171.35)
- * DF System as above, but with mobile version of combiner, Model DFA2 (as DFA1 but fitted with magmount and 4 metre coaxial download terminated with PL259 plug) £159.00 + VAT (£182.85)

Complete Mobile DF System (Model DF display unit, Model DFA2 combiner, and four Model MA1 quarter wavelength magmount antennas cut for 145 MHz) £214.00 - VAT (£246.10)

* Antennas not included.

OTHER PRODUCTS

Datong specialise in designing and manufacturing unique products for the amateur radio, CB and radio communications markets. Other products include a range of highly selective audio filters for receiver improvement, active receiving antennas, a Morse Code training aid, speech processing systems for transmitters, low cost selective call systems, a Morse code "typewriter", a broadband r.f. preamplifier, a synthesised converter for receiving 0 to 30 MHz on a two metre SSB receiver.

Our products are not necessarily the cheapest, but in terms of performance at the price they represent excellent value.



Our catalogue or specific data sheets are available free on request. We deal both direct and through selected amateur radio dealers.

Write to dept. **REW**
DATONG ELECTRONICS LTD.
Spence Mills, Mill Lane,
Bramley, Leeds LS13 3HE
Telephone: 0532 552461

The CA3080 Operational Transconductance Amplifier (OTA) can be used in a host of voltage or current controlled applications.

Ray Marston explains how.



The CA3080, is a special type of operational amplifier, capable of being controlled by an external current. **Fig. 1a** shows the basic symbol and formulae for a conventional op-amp, which is essentially a voltage-amplifying device. It has differential input terminals and produces an output voltage of $A(e1 - e2)$, where A is the open-loop voltage gain of the op-amp (typically 100,000), and $e1$ and $e2$ are the signal voltages at the non-inverting and inverting input terminals respectively. The open-loop voltage gain of the op-amp is fixed, and it also has a high input impedance and low output impedance.

Figure 1b shows the basic symbol and formulae of the CA3080 OTA, which is essentially a voltage-to-current amplifier. Like a conventional op-amp, it has differential-voltage input terminals but, as indicated by the constant-current symbol at its output, these input voltages produce an output in the form of a high-impedance current with a value of $g_m(e1 - e2)$, where g_m is the transconductance or 'voltage-to-current gain' of the device. In practice, the g_m value can be controlled by, and is directly proportional to, the value of an external bias current fed into an I_{bias} terminal. In the CA3080, this current can be varied from 100nA to 1mA, giving a 10,000:1 gain-control range.

An OTA is a very versatile device. It can be made to act like a conventional voltage-amplifying op-amp by simply wiring a suitable load resistance to its output terminal — its output current is converted to a proportional voltage. The total current consumption of the CA3080 OTA is double the value of I_{bias} , which may be as low as 100 nA, enabling the device to be used in true micro-power applications. The magnitude of I_{bias} can easily be controlled by an external voltage and a series resistor, enabling the OTA to be used as a voltage-

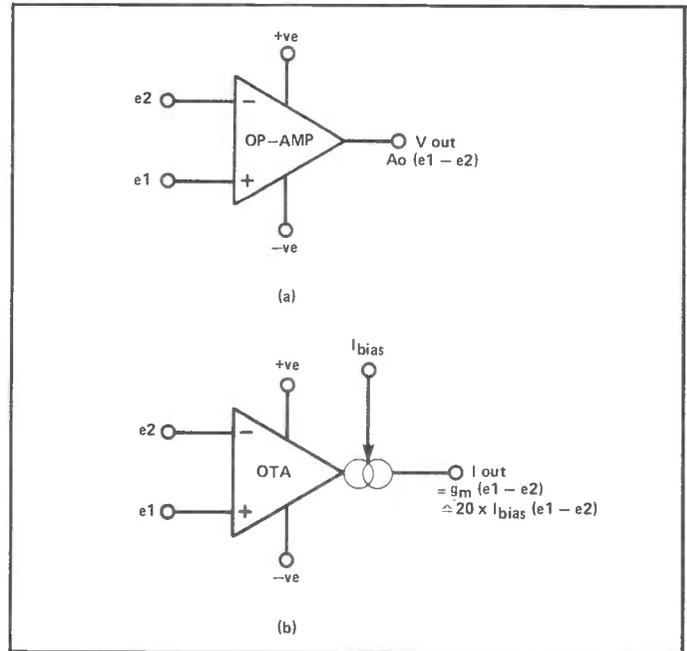


Figure 1. A conventional op-amp (a) is a fixed-gain voltage-amplifying device. An OTA (b) is a variable-gain voltage-to-current amplifier.

controlled amplifier (VCA), oscillator (VCO) or filter (VCF). **Fig. 2a** shows the connections of the 8-pin dil 'E' version and **Fig. 2b** shows its internal circuit.

CA3080 Basics

The CA3080 is a fairly straightforward device, made of nothing more than one differential amplifier and four current mirrors. Each of these comprise a 3-terminal circuit that, when provided with an external bias current into its input terminals, produces an in-phase current of identical value at its output terminals. When a current mirror (CM) source and CM sink are connected as shown in **Fig. 3** and powered from split supply rails, they generate a differential ($I_{source} - I_{sink}$) current in any external load that is connected to the 0V rail.

Figure 4 shows how the differential amplifier and four current mirrors are interconnected in the CA3080 to make a practical OTA. Bias current I_{bias} controls the emitter current, and thus the g_m , of the Q1-Q2 differential amplifier via CM 'C'. The collector currents of Q1 and Q2 are mirrored by CMA

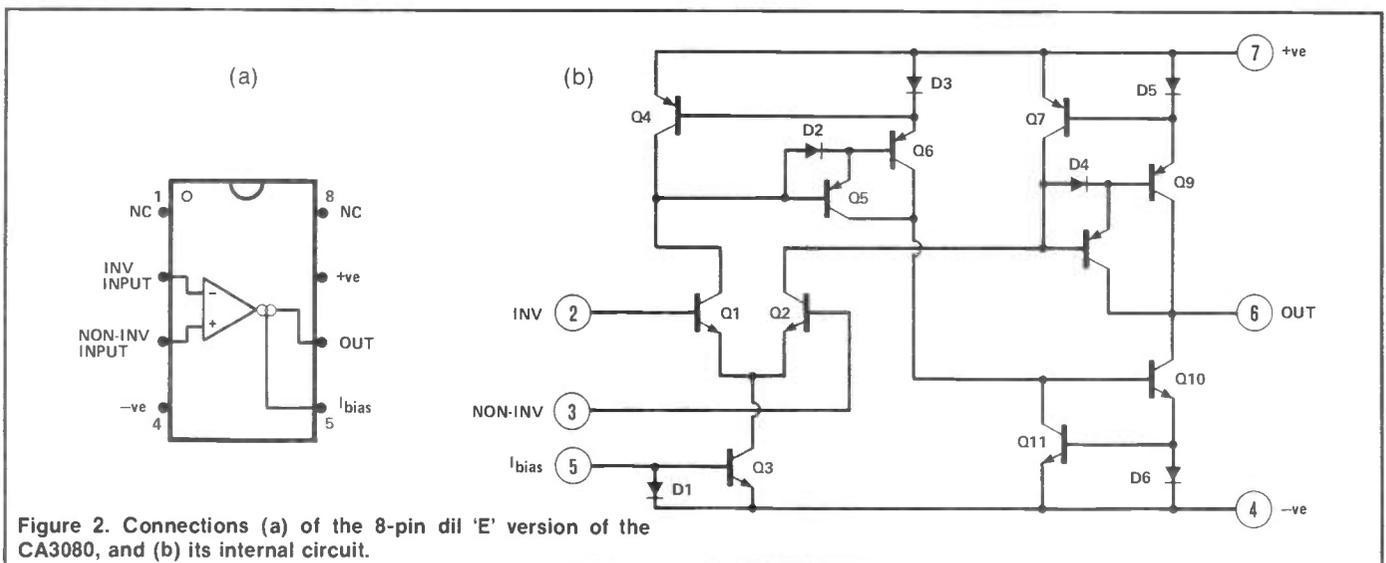


Figure 2. Connections (a) of the 8-pin dil 'E' version of the CA3080, and (b) its internal circuit.

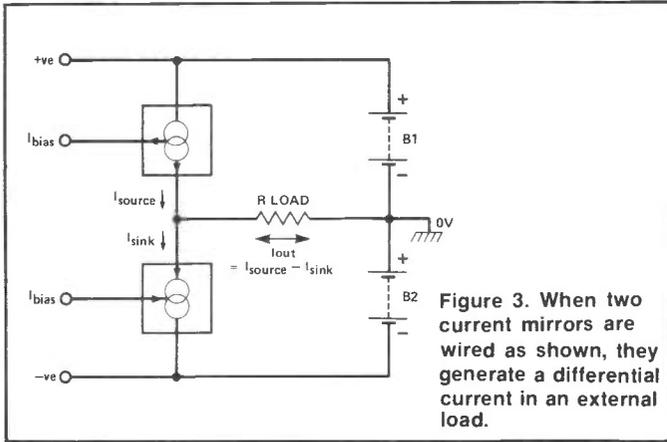


Figure 3. When two current mirrors are wired as shown, they generate a differential current in an external load.

and CMB and fed into the bias and sink terminals (respectively) of CMD, so that the externally available output current of the circuit is equal to $I_b - I_a$.

If you refer back to **Fig. 2b**, which shows the internal circuit of the CA3080, you should be able to work out the functions of the individual elements with little difficulty. Q1 and Q2 form the differential amplifier, with D1-Q3 making up CMC of **Fig. 4**, and CMD comprises D6-Q10-Q11. Current mirrors CMA (Q4-Q5-Q6-D2-D3) and CMB (Q7-Q8-Q9-D4-D5) are slightly more complex, using Darlington pairs of transistors, plus speed-up diodes, to improve their performances.

Some Finer Points

All of the major operating parameters of the CA3080 are adjustable and depend on the value of I_{bias} . The maximum (short circuit) output current, for example, is equal to I_{bias} and the total operating current is double the I_{bias} value. The input bias currents drawn by pins 2 and 3, when the IC is operating in the linear mode, each roughly equal $I_{bias}/200$, the precise values depending on the current gains of Q1 and Q2 within the chip.

The transconductance (g_m) and the input and output resistance (impedance) values also vary with the I_{bias} value. **Fig. 5** shows typical parameter values when the IC is driven from split 15 volt supplies at an ambient temperature of $+25^\circ\text{C}$. Thus, at a bias current of $10\mu\text{A}$, g_m is typically $200\mu\text{mho}$, and input and output resistances are 800k and 700M respectively; at 1mA bias, the values change to 20mmho , 15k and 7M respectively.

The available output voltage swing of the IC depends on the values of I_{bias} and an external load resistor connected to the output (pin 6) of the device. If the load impedance is infinite, the output can swing to within $1V_5$ of the positive supply rail and to within $0V_5$ of the negative rail. If the impedance is not infinite, the peak output voltage swing is limited to $I_{bias} \times R_L$. Thus, at $10\mu\text{A}$ bias with a 100k load, the available output voltage swing is $\pm 1V$.

The slew rate (and bandwidth) of the IC depend on the value of I_{bias} and any external loading capacitor connected to pin 6. The slew rate value, in volts/us, equals I_{bias}/CL , where CL is the loading capacitance value in pF, and the I_{bias} value is in μA . With no external loading capacitance connected, the maximum slew rate of the CA3080 is about $50V/us$.

Basic Circuits

The CA3080 is a very easy IC to use. Its pin-5 I_{bias} terminal is internally connected to the pin-4 negative supply rail via a base-emitter junction, so the biased voltage of the terminal is about 600mV above the pin-4 voltage. I_{bias} can thus be obtained by simply connecting pin-5 to either the common rail or the positive supply rail via a current-limiting resistor of suitable value.

Figure 6 shows a simple but instructive way of using the CA3080 as a linear amplifier with a voltage gain of about 40dB . The circuit acts as a direct-coupled differential amplifier. It operates from split 9-volt supplies, so $17V_4$ is generated across bias resistor R1, which thus feeds roughly $500\mu\text{A}$ into pin-5 and causes each IC to consume another 1mA from its supply rails.

At a bias current of $500\mu\text{A}$ the g_m of the CA3080 is approximately 10mmho . The output of the **Fig. 6** circuit is loaded by a 10k resistor (R2), and thus gives an overall voltage gain of $10\text{mmho} \times 10\text{k} = 100$, or 40dB . The peak current that can flow into this 10k load is $500\mu\text{A}$ ($=I_{bias}$), so the peak available output voltage is $\pm 5V$. The output is also

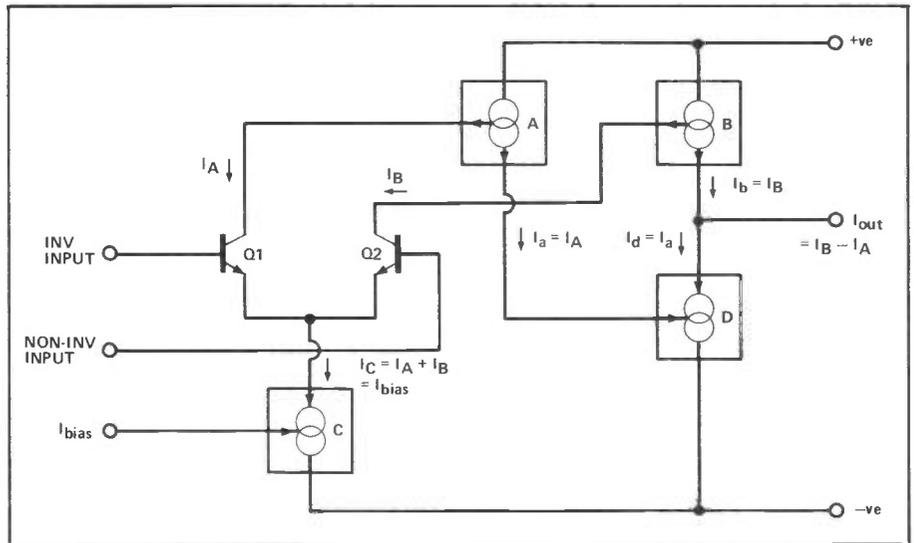


Figure 4. The CA3080 comprises one differential amplifier and four current mirrors.

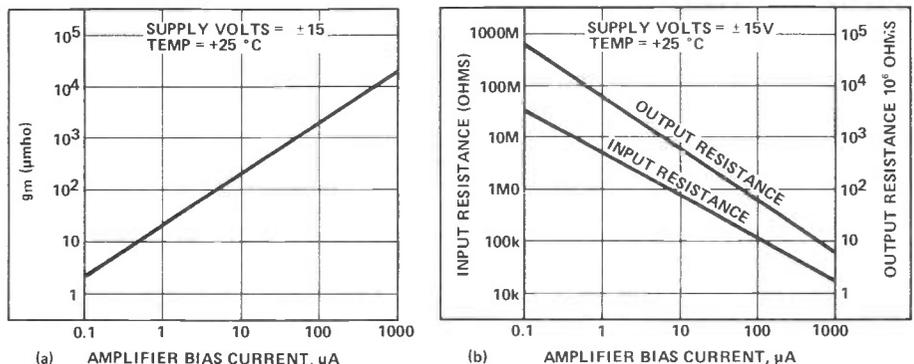


Figure 5. The transconductance (a) and the input and output resistances (b) of the CA3080 vary with the bias current value.

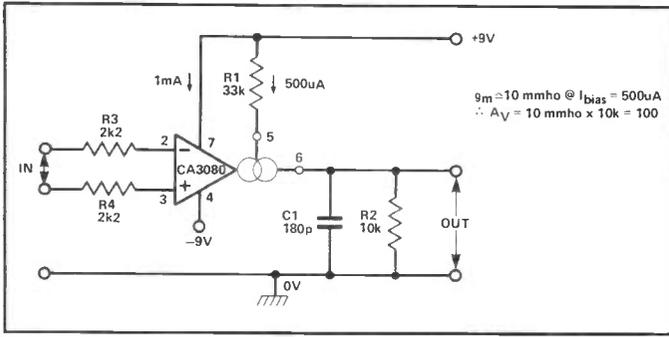


Figure 6. Differential amplifier with 40dB voltage gain.

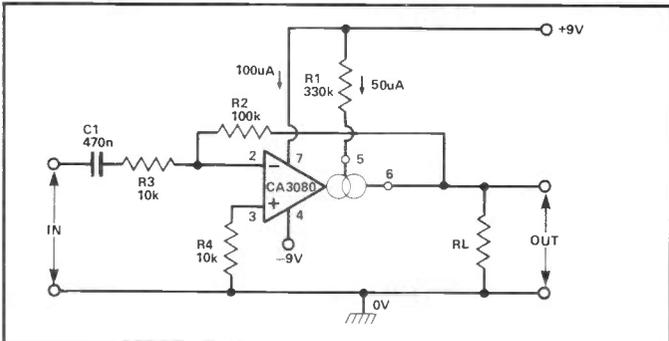


Figure 7. 20dB micro-power inverting amplifier.

loaded by 180 pF capacitor C1, giving the circuit a slew-rate limit of $500\mu\text{A}/180\text{pF} = 2.8\text{V}/\mu\text{s}$. The output impedance of each circuit equals the R2 value (10k).

Note in this circuit that the IC is used in the open-loop mode, and that if the slew rate of the chip is not externally limited via C1 the IC will operate at its maximum bandwidth and slew rate. Under this condition the CA3080 may be excessively noisy, and pick up radiated EMF signals.

In the Fig. 6 circuit, the differential inputs are applied via series resistors R3 and R4, which simply help equalise the source impedance of the two signals and thus maintain the DC balance of the IC.

The voltage gain of the circuit depends on the value of I_{bias} , which in turn depends on the value of the supply rail voltage. The voltage gain of the CA3080 can be made almost independent of the I_{bias} and supply voltage values by using conventional op-amp techniques, as shown by the 20dB AC-coupled inverter circuit of Fig. 7, which consumes a mere 150 uA from its split 9-volt supply rails.

Figure 7 is wired like a conventional op-amp inverting amplifier, with its voltage gain (A_v) determined primarily by the R2/R3 ratio (= 10, or 20dB). This gain equation is, however, only valid when the value of an external load

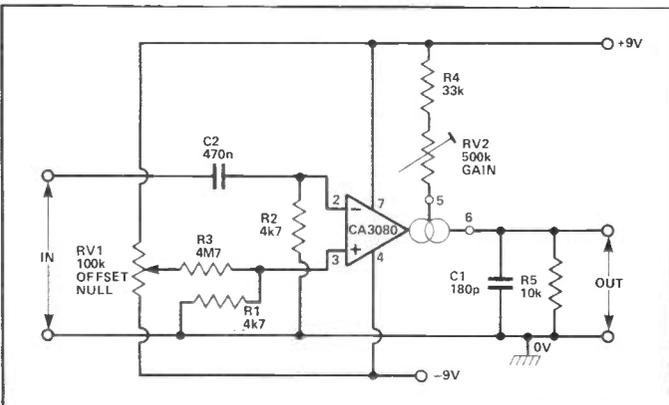


Figure 8. Variable-gain (x5 to x100) AC amplifier.

resistor, R_L , is infinite, since the output impedance of this design is equal to $R2/A_v$, or 10k, and any external load causes this impedance to give a potential divider action that reduces the output of the circuit.

In Fig. 7, the main function of I_{bias} is to determine the total operating current of the circuit and/or the maximum available output voltage swing. With the component values shown, I_{bias} has a value of 50uA, causing the circuit to consume a total of only 150 uA. When R_L is infinite, the output is loaded only by R2, which has a value of 100k, so the maximum available output voltage is $\pm 5\text{V}$. If R_L has a value of 10k, on the other hand, the maximum output voltage limits at $\pm 0.5\text{V}$. This circuit can thus be designed to give any desired values of voltage gain and peak output voltage. Note that, since the IC is used in the closed loop mode, external slew rate limiting is not required.

If the CA3080 is to be used as a high-gain DC amplifier, or as a wide-range variable-gain amplifier, input bias levels must be balanced to ensure that the output correctly tracks the input signals at all prevailing I_{bias} values. Fig. 8 shows how suitable bias can be applied to an inverting AC amplifier in which the voltage gain is variable from roughly x5 to x100 via RV2, and the offset balance is pre-set via RV1. The circuit is set up by adjusting RV2 to its minimum (maximum gain) value and then trimming RV1 to give zero DC output with no AC input signal applied.

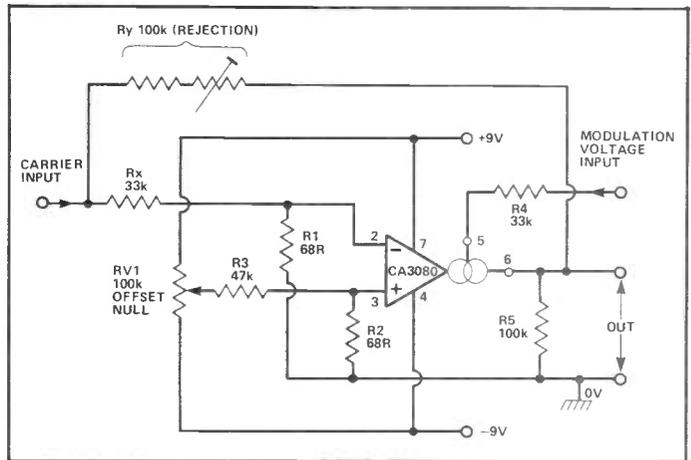


Figure 9. Ring modulator or 4-quadrant multiplier.

Voltage-Controlled Gain

In practice, the most important uses of the CA3080 are in true micropower amplifier and oscillator applications, and in applications in which important parameters are controlled by an external voltage. In the latter category, one important application is as a voltage-controlled amplifier (VCA) or amplitude modulator, in which a 'carrier' signal is fed to the input of the amplifier, and its output amplitude is controlled or modulated by another signal fed to the I_{bias} terminal. Fig. 9 shows a practical circuit for a ring-modulator or 4-quadrant multiplier, in which the output signal polarity depends on the polarities of both the input signal and the modulation voltage. Operation of the circuit is such that, when the modulator input is tied to the zero volts rail, the inverted signal currents feeding into R5 from the output of the OTA are exactly balanced by non-inverted signal currents flowing into R5 from the input signal via R_y , so that zero output is generated across R5. If the modulation input goes +ve, the output of the OTA exceeds the current of the R_y network, and an inverted gain-controlled output is obtained. If the modulation input is -ve, on the other hand, the output current of R_y exceeds that of the OTA, and a non-inverted gain-controlled output is obtained. Thus, both the phase and amplitude of the output

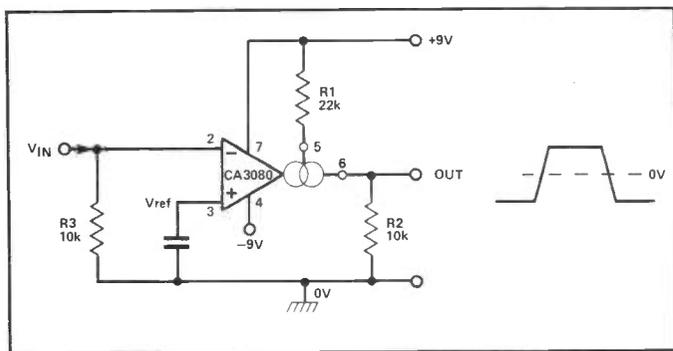


Figure 10. Fast inverting voltage comparator.

signal of this 4-quadrant multiplier circuit are controlled by the modulation signal. The circuit can be used as a ring modulator, by feeding independent AC signals to the two inputs, or as a frequency doubler by feeding sine wave signals to the two inputs.

Note that, with the R_x and R_y values shown, the circuit gives a voltage gain of $\times 0.5$ when the modulation terminal is tied to the +ve or -ve supply rail; the gain doubles if the values of R_x and R_y are halved. Also note that in practice a voltage follower buffer stage must be interposed between the output terminal and the outside world.

Comparator Circuits

The CA3080 can easily be used as a programmable or micro-power voltage comparator. Figure 10 shows the basic circuit of a fast, programmable, inverting comparator, in which a reference voltage is applied to the non-inverting input terminal and the test input is applied to the inverting terminal. The circuit action is such that the output is driven high when the test input is below V_{ref} , and is driven low when test is above V_{ref} (the circuit can be made to give a non-inverting comparator action by transposing the input connections of the IC).

With the component values shown, the I_{bias} current of the Fig. 10 circuit is several hundred μA , and under this condition the CA3080 has a slew rate of about $20V/\mu s$ and thus acts as a 'fast' comparator. When the test and V_{ref} voltages are almost identical, the IC acts as a linear amplifier with a voltage gain of $g_m \times R_2$ (about 200 in this case). When the two input voltages are significantly different, the output voltage limits at values determined by the I_{bias} and R_2 values; in Fig 10, the output limits at roughly $\pm 7V$ when R_2 has a value of $10k$, or at $\pm 700 mV$ when R_2 has a value of $1k$.

Figure 11 shows how the above circuit can be modified so that it acts as an ultra-sensitive micro-power comparator which typically consumes a quiescent current of only $50 \mu A$

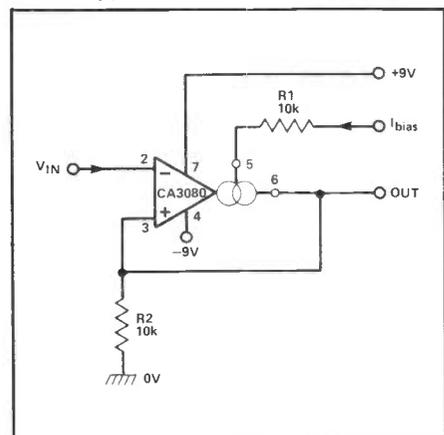


Figure 12. Programmable Schmitt trigger.

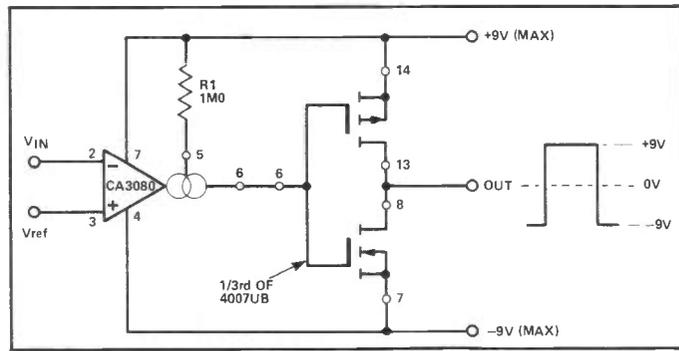


Figure 11. Non-inverting micro-power voltage comparator.

but gives an output voltage that swings fully between the two supply rails and can supply drive currents of several mA. Here, the CA3080 is biased at about $18 \mu A$ via R_1 , but has its output fed to the near-infinite input impedance of a CMOS inverter stage made from one section of a 4007. The CA3080-plus-4007 combination gives the circuit an overall voltage gain of about $130dB$, so input voltage shifts of only a few micro-volts are sufficient to switch the output from one supply rail to the other.

Schmitt Trigger Circuits

The simple voltage comparator circuit of Fig. 10 can be made to act as a programmable Schmitt trigger by connecting the non-inverting 'reference' terminal directly to the output of the CA3080, as shown in Fig. 12. In this case, when the output is high, a positive 'reference' value of $I_{bias} \times R_2$ is generated; when V_{in} exceeds this value, the output regeneratively switches low and generates a negative reference voltage of $I_{bias} \times R_2$; when V_{in} falls below this value, the output regeneratively switches high again and once more generates a positive reference voltage of $I_{bias} \times R_2$. Thus, the trigger thresholds (and also the peak output voltages) of this Schmitt circuit can be precisely controlled or programmed via either I_{bias} or R_2 .

Astable Circuits

The Schmitt trigger application can be modified as an astable multivibrator or square-wave generator circuit by simply connecting its output back to the non-inverting input terminal via an R-C time-constant network. With the addition of a few other components, an output waveform with variable mark/space ratio can be produced, as shown in Fig. 13. Here C_1 alternately charges via D_1 - R_3 and the left half of RV_1 , and discharges via D_2 - R_3 and the right half of RV_1 , to give an M-S ratio that is fully variable from 10:1 to 1:10 via RV_1 .

■ R&EW


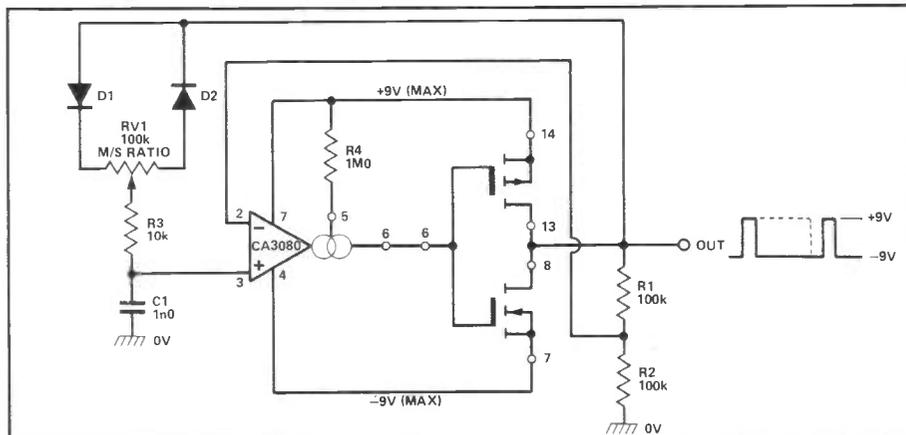


Figure 13. Variable mark-space ratio astable.

SHORT WAVE NEWS FOR DX LISTENERS

Frank A. Baldwin

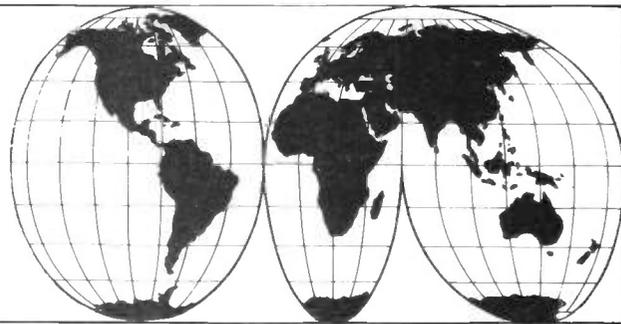All times in GMT, **bold figures** indicate the frequency in kHz.



In last month's rendition, we dealt with a review of some of the easier-to-receive Latin American stations operating on the 60 metre band (**4750 to 5060**). The present instalment continues this review, commencing with some of the Brazilian transmitters regularly logged here in the UK. Some of our beginner SWL readers may care to visit the frequencies designated from around 2200 onwards.

Adjust the dial to **4835** where may be found signals from Radio Nacional in Boa Vista operating from 0900 to 0400 and identifying as "Radio Difusora Roraima", it has a power of 10kW. Then there is Radio Jornal do Brasil in Rio de Janeiro on **4875** from 0900 through to 0530 with a 10kW transmitter; Radio Clube do Para, Belem on **4885** to the schedule 0800 to 0300 at 10kW; Radio Bare in Manuas on **4895** working away from 0800 (Sun-

day from 0900) to 0400 with a 5kW signal and identifying as "Radio Super Bare".

Turn your attention now to that part of your receiver dial indicating the frequency **4905** where you may log Radio Relogio in Rio de Janeiro on the air to the to the schedule 0800 to 0300. You cannot mistake this one for the reason that it broadcasts time-signals which overlay current programmes, the second pulses being quite distinctive. The power is 5kW.

The nearby channel of **4915** will almost certainly provide signals from Radio Anhanguera in Goiania if conditions are right. It operates from 0900 (Sundays from 1000) to 0400 and has a power of 10kW; or there is Radio Dragao do Mar in Fortaleza which can be located on **4925** where it is scheduled from 0800 to 0900 and from 2130 to 0300 with a 5kW transmitter although

there is a difficulty here with the co-channel Brazilian Radio Difusora Taubate, Taubate operating from 0830 to 0300 with a power of 1kW. Both stations are often reported so it will be apparent that the station identification must be clearly heard before an entry is made into the logbook.

ON **5025** operates the often reported Radio Borborema in Campina Grande, scheduled from 0800 to 0430, it identifies as "A Princesa do Sul" and has a power of 1kW whilst on **5035** we have Radio Aparecida with a 2.5kW signal operating from 0900 to 0300.

The last Brazilian at this high end of the band is Radio Clube do Para in Belem which is on the air from 0700 to 0300 with a power of 10kW.


Turning our attention now to some of the Colombians on the 60 metre band, we commence

with Radio Guatapuri in Valledupar which may be tuned at that point of the dial marked **4815**. Identifying as "Radio Favorita", it has a power of 10kW and is scheduled on the air around-the-clock.

Neiva in Colombia may be heard on **4855** where it is scheduled from 1100 to 0530 although it has been reported as closing at 0400 on occasions. The power is 1kW.

Then there is a particular favourite of mine in the form of Radio Super in Medellin on **4875** which is often logged in the early mornings whilst I drink a cup of welcome tea! It is scheduled around-the-clock and has a power of 2kW — the station, not the tea!

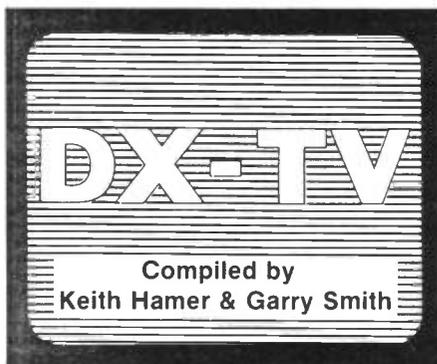To wind up the Colombian scene on this band there now remains Radio Caracol in Neiva on **4945** on a 24-hour basis at 2.5kW; Radio Santa Fe in Bogota



Enhanced tropospheric reception conditions returned yet again during February — in fact on two occasions around the middle of the month. There hasn't been such an abundance of openings since the early 70's so perhaps we're making up for lost time.

Other reception during the month was due mainly to Meteor Shower (MS) activity although an aurora was noted on the 4th with the characteristic rumbling and sleigh-bell sounds present on the various Band I channels.

Czechoslovakia (CST) and Austria (ORF) were the most commonly identified television services received throughout the month via MS. The distinctive "RS-KH" test card (see **R&EW**, April 1983) from CST was seen on the 4th, 7th, 8th, 9th, 10th, 11th, 15th, 16th, 21st, 22nd, 24th and 28th on

channel R1. The Austrian "ORF FS 1" PM5544 was seen on most days together with occasional glimpses of the Telefunken T05 monoscopic test card. The Swedish "TV 1 SVERIGE" PM5544 was noted on channel E3 on the 2nd, 6th, 17th, 23rd and 28th while the Norwegian PM5544 was seen on the 6th, 20th and 21st. Other countries noted via MS included Spain(RTVE), Russia(TSS) and Poland(TVP) which were all identified during test transmissions or news programmes. A late-evening tropospheric lift on the 15th provided West German reception throughout Band III and UHF with the East German first network appearing near closedown at 2157GMT on channel E6 with the "ak" news symbol, clock caption and programme schedule for the following day. Similar conditions on the 18th and 19th produced Dutch, Belgian, French and a few West German stations. The signal strengths were high and good enough to sustain snow-free colour pictures of entertainment quality for several hours on both days.

Notes For Beginners

By the time this column is read, the 1983 Sporadic-E season should be underway permitting the reception of

television signals from as far away as Russia, Jordan, Spain and Iceland. Reception occurs on several channels throughout Band I between 48MHz and 70MHz. To receive these signals a VHF tuner is required in place of the UHF type normally fitted to British sets. Varicap tuners are the best and can be obtained relatively cheaply from Sendz Components or Manor Supplies. The ELC 1042 type covers only Bands I and III whereas the ELC 2000 and ELC 2060 versions are multi-band with the added bonus of UHF and an extended Band I coverage up to approximately 90MHz for "out of band" Eastern European channels. Existing powering arrangements may be used, that is, a stabilised 30V supply for the tuning potentiometers and a 12V supply for the tuner itself. It should be noted that a band switch will be necessary and great care is essential with regards to isolation. A large-screen receiver is likely to have a live chassis irrespective of mains polarity. A small-screen mains/battery portable is likely to have an isolated chassis but the service manual should be consulted if there are any doubts.

There are various receivers on the market which already have facilities for Bands I and III. The channels are normally marked 2-4 (Band I) and 5-12 (Band III). The Plustron TVR 5D is one

on **4965** with the same schedule and power and finally Radio Cinco in Villavicencio on **5040** also with a 24-hour schedule but with a power of 3kW.

To complete the review of the so-called 'easy' stations operating from Latin America there now remains another old favourite of mine — La Voz Evangelica in Tegucigalpa, Honduras which may be logged on **4820**

where it is scheduled from 1030 to 0300 and from 0500 to 0600 in Spanish and from 0300 to 0500 in English. These latter programmes are religious in content but do make the station identification a relatively easy matter for the beginner making a start at the LA game.

Next month some of the not-so-easy stations will be reviewed.

Around The Dial

United Arab Emirates

Dubai on **21655** at 1213, OM and YL in an Arabic dramatic production — even complete with the cries of a baby — in an External Service presentation. Dubai is on this frequency from 0700 through to 1715.

Egypt

Cairo on **9475** at 2023, YL with songs together with some typical Arabic music during the Domestic Service schedule which is on this channel from 1800 to 2345.

Cairo on **11665** at 2028, local-style songs and music in the "Voice of the Arabs" Service to the Middle East, North and Central Africa, South Asia and Europe from 1900 to 0030 on this frequency. Trumpet fanfare at 2030 followed by OM with station identification and a newscast in Arabic.

Canada

Montreal on **6045** at 0644, OM with the French programme for Africa, the Middle East and Europe, scheduled from 0630 to 0645.

Netherlands Antilles

Bonaire on **9175** at 0623, YL with announcements at the end of the English programme for the North American West Coast, listed on this channel from 0530 to 0625.

Czechoslovakia

Prague on **7345** at 2018, OM and YL with an English programme for Europe, timed from 2000 to 2030. It was all about the local music and folk songs, complete with several samples.

Prague on **6055** at 0623, OM presenting the news and comment feature in the French transmission to Europe, scheduled from 0600 to 0630.

Iraq

Baghdad on a measured **3367** at 2044, OM with a talk in the Persian transmission to Iran which is aired on this frequency from 1600 to 1900 and from 2000 to 2300.

Nigeria

Lagos on **7255** at 0628, OM's with a chorus of African chants, drums, OM and YL with announcements in the French programme for West Africa, on this channel from 0600 to 0700. QRM from the overlaying Radio Sofia.

Poland

Warsaw on **6135** at 1447, YL with a talk in the Danish transmission for Europe, scheduled from 1430 to 1500.

Warsaw on **6095** at 0636, OM with a talk in Polish in a programme for Poles abroad — I nearly wrote Poles apart — this session being timed from 0600 to 0700.

Warsaw on **7270** at 0640, OM with listeners' letters and replies during an English programme to Europe, scheduled from 0630 to 0700.

East Germany

Radio Berlin International on **6080** at 2140, OM with a newscast in English during a programme in that language timed from 2130 to 2215 on this channel.

Spain

Madrid on **21595** at 0647, some of the colourful and distinctive music of Spain during a transmission intended for Spaniards in Australia, the Near and Middle East, scheduled from 0600 to 0930 (not Sunday).

Madrid on **11760** at 2042, OM with a newscast of both local and world events during the English service to Europe, timed from 2000 to 2100.

Switzerland

Berne on **6165** at 0643, a YL yodelling some yodels — made my throat ache — during the German, French and Italian programme for Africa and Europe, featured on this channel from 0600 to 0645.

Berne on **3985** at 0652, Swiss music in typical style during a music programme for Europe, scheduled from 0645 to 0700.

Libya

Tripoli on **6185** at 0651, YL with a song, some local-style music, YL announcer in the Domestic Service which operates at this point on the dial from 0500 through to 2330.

Kuwait

Radio Kuwait on **11990** at 1140, OM with songs in Arabic together with the music in a programme of the Domestic/External Service, on this channel from 0400 to 1505.

example and this particular set will resolve the UK and Western European sounds systems.

For initial experiments with Sporadic-E propagation the aerial used for DX can be a fairly simple affair especially as the signals can attain very high strengths. A simple dipole with each rod 50 inches in length will suffice and should be mounted horizontally and externally where possible. The enthusiast can then progress to the luxury of a more ambitious aerial system such as a rotatable 3 or 4-element beam for weak-signal work. The use of a pre-amplifier is tempting but should be avoided, especially at Band I frequencies, since it can overload

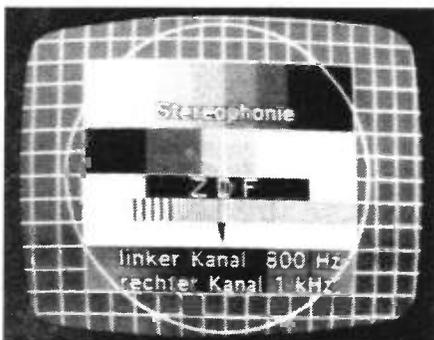


Figure 1: West German FuBK test card carrying a stereo TV sound test transmission.

in the presence of strong signals. A bandpass filter may be necessary to avoid interference from CB. To ensure that the DX system is functioning the receiver can be tuned throughout Band I to check that signals are arriving satisfactorily from local and semi-local BBC-1 transmitters. Reception will be displayed as a pattern of white lines because the 405-line system uses positive vision modulation rather than the negative modulation system used by the UK 625-line services and Continental VHF and UHF networks.

During the Sporadic-E season (which lasts from early May until mid-September) a check for reception throughout Band I should be made as often as possible during the day because signals can come and go within a matter of minutes. Sometimes a Sporadic-E opening will last the whole day, occasionally from about 0600 until 2400, or even later. It should be noted that there may be several days during the season when signals are totally absent. Full details about getting started with DX-TV were given in the September 1982 edition of **R&EW**.

Service Information

Sweden: Severiges Radio have introduced a new transmitter on channel

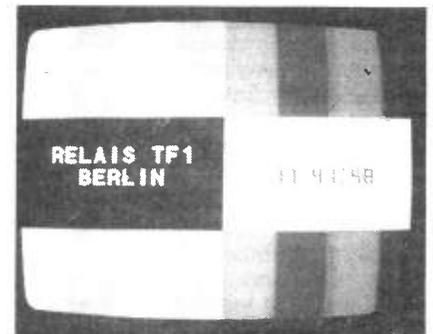


Figure 2. (SLIDE) Test pattern radiated by the French TV first network (TF 1) relay station operating in West Berlin. Photo by courtesy of Juergen Klassen, West Germany.

E41 at Finnveden with an ERP of 1000kW for their first network. The transmitter was previously operating on E4 with an ERP of 3kW.

East Germany: Links via Poland and the Gorizont satellite are providing Russian army personnel stationed in certain parts of the DDR with television programmes from the USSR. The East German authorities are rapidly extending the TSS-1 network on UHF channels as well as E12 and E4. The latter channel is causing some concern in West Germany as TSS transmissions

Sweden

Stockholm on **6065** at 0655, OM with a talk during the Swedish transmission to Africa and Europe, this being a relay of the Domestic 1st Programme, on this channel from 0430 to 0830.

Stockholm on **9615** at 1208, OM presenting a newscast in the German programme for Europe, timed here from 1200 to 1230.

Norway

Oslo on **6015** at 0658, OM with station identification as "This is Radio Norway International" in both English and Norwegian, interval signal then a newscast in the Norwegian programme to Africa, the Middle East, Europe and South America, scheduled from 0700 to 0745.

South Yemen

Aden on **6005** at 1952, OM with songs in Arabic with local orchestral backing in the Domestic Service which is scheduled on this frequency from 0300 to 0630 (Friday from 0630 to 1100) and from 1100 to 2200. Logged often of late.

Benin

Cotonou on **4870** at 0610, YL with a newscast in vernacular in the Home Service which is on this channel from 0400 (Saturday from 0550) to 0800 and from 1300 (Saturday from 1100) through to 2400. The power is 30kW.

South Africa

RSA Johannesburg on **25790** at 1204, OM with a newscast in the French programme to Central Africa and Europe, timed from 1200 to 1300.

Turkey

Ankara on **15220** at 1210, OM with a song complete with local orchestral backing in the transmission for Turks abroad. The "Voice of Turkey" is on this channel with this programme from 0700 through to 1700.

Mauritania

Nouakchott on **4845** at 0607, OM with quotations from the Holy Quran. The schedule is from 0600 (Sunday from 0800) to 0900 and from 1758 (Saturday and Sunday from 1700) to 2400. The power is 100kW.

China

Radio Peking on **7780** at 2010, OM with a talk during the Portuguese presentation to Africa and Europe, scheduled from 2000 to 2100.

Radio Peking on **7800** at 2006, European-style music in the French programme for Africa and Europe, timed from 1930 to 2030.

Radio Peking on **11600** at 1425, YL with a talk all about Chinese history during an English programme for South East Asia being presented on this channel from 1400 to 1500.

South Korea

Seoul on **7550** at 2100, OM with station identification in Russian as "Govorit Seoul" (Here is Seoul) and the following Russian programme for the USSR. The inevitable jammer arrived a minute later, identifying in morse as UB.

Romania

Bucharest on **17850** at 1153, YL with a song during the French programme for Africa and Europe, scheduled from 1130 to 1200. YL with station identification, interval signal and carrier off at 1155.

Sri Lanka

Colombo on **4902** at 2120, the chanting of monks on a full-moon day. This is the Home Service 1 which irregularly operates on this frequency from 0000 to 0300 and from 1000 to 1745 in Sinhala. On full-moon days the schedule is extended from 1000 through to 2400. The power is 10kW.

Now Hear This

Voz de Sao Vicente, Cape Verde on a measured **3931** at 2115, when radiating a talk in Creole. This one operates from 1200 to 1400 and from 1800 to 2400 Monday to Friday inclusive; Saturday from 1200 through to 2400 and on Sunday from 0900 through to 2400. The power is

Iran

Tehran on **3779** at 2040, YL with a talk in Persian in the Domestic 1st Programme which closes at 2130 but can be heard from around 1930 onward at my QTH.

Tehran on **15260** at 1135, OM's with a rousing marching chorus in Persian then OM with announcements, exhortations and the rest. All in the Domestic Service 1st Programme which is on this channel from 0630 through to 1615.

Vatican

Vatican City on **6190** at 2039, OM and YL with the English programme directed to Africa from 2030 to 2045.

Seychelles

Mahe on **15405** at 1158, European-style light music. OM with announcements at the end of the Arabic programme for North East Africa and the Middle East, scheduled from 1100 to 1200. Off abruptly at 1200 without the National Anthem.

10kW and the languages used are Portuguese and Creole. Not an easy one to log owing to the surrounding — and often covering — commercial interference. It announces as "Voz de Sao Vicente" and it is sometimes heard by DXers both in the UK and Europe. ■ R & EW

are now interfering with BR-1 (Bavarian Television) programmes from Ochsenkopf. The new service is known as 'Fernsehen der Sowjet-Armee' (FSA).

Spain: There is a new television service operating in the Basque country called Euskal Telebista (ETB). The studios are based at Durango and the main UHF transmitters are located at Durangesado (channel E33), Bilbao (E35), Vitoria (E42) and Jaizkibel (E51). The Philips PM5544 test card is used with the identification "ETB" in the upper black rectangle.

Afghanistan: Until recently, PAL colour was used with 625 lines scanning but

following the invasion by Russia, links have been provided to the Eastern-bloc system called "Intersputnik". A new transmitter has been specially installed to radiate programmes using the USSR colour system, SECAM.

Denmark: There are plans to introduce a second network in an effort to combat competition from planned communal television systems. Denmark's Radio are also investigating the possibility of commencing a regional television service.

Faeroe Islands: Television broadcasting is presently limited to private stations which mainly radiate programme material supplied by Denmark's Radio. A national network is planned for the islands with transmitters at Torshavn and Suduroy.

Bulgaria: Bolgharska Televizia are currently bringing into service a number of high-power transmitters. Details of channel allocations are not available at the moment.

Poland: TVP-2 are now radiating programmes from a new outlet on channel R26 with 1000kW ERP. Its location is unknown.

Czechoslovakia: Soviet television programmes from TSS-1 are now being relayed via three low-power transmitters.

The Bratislava outlet operated by

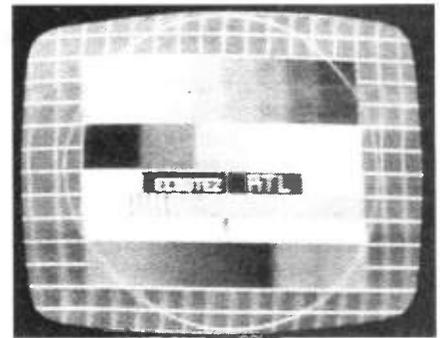


Figure 4. The FuBK test card radiated by Radio-Tele-Luxembourg and received on channel E27.



Figure 3. Identification caption received from Belgian Television.

CST is reported to be back in service following a fire which caused severe damage.

Hungary: Magyar Televizio (MTV) have commenced a teletext service similar to the BBC's CEEFAX system.

We are indebted to the EBU (Belgium), Gosta van der Linden (Netherlands) and Alexander Wiese (West Germany) for the above information.

■ R & EW

Design Engineers

Satellite Communications

Major expansion of our Space Division has created numerous opportunities for engineers to be involved in some of the most technologically challenging work on meteorological and communications satellites.

Qualified Hardware and Software Design Engineers of various levels of experience are required for posts which vary from Engineering Manager/Group Leader to membership of a Design Team. Disciplines include:

Spacecraft Systems
Communications Systems
Microwave Systems and Equipment
Radar and Signal Processing
Electronic Circuit Design
Mechanical, Thermal and Dynamics Design
Power Supplies Switch-Mode

Salaries and benefits will reflect the importance we attach to the positions and relocation assistance is available if required.

Please write or telephone stating your qualifications, recent experience and area of interest to Jack Burnie, Marconi Space & Defence Systems Limited, Browns Lane, The Airport, Portsmouth, Hants. Tel (0705) 674019 Ref: BL 34.

(All posts are open to men and women)

Marconi
Space & Defence Systems



NOTES FROM THE PAST

With the results of the April survey beginning to emerge, it's interesting to note Centre Tap's comments on readers' correspondence in the past.

Of the many readers who wrote on the type of articles they like in *Radio Constructor*, and its general policy, all praised its wide range of subjects and many say they would like to see an even wider field. A South Australian reader, Mr. E.M.P. Wells, suggests we might emulate the Australian *Radio and Hobbies* magazine. For British readers unfamiliar with this magazine, I might mention that up to half its contents are given over to articles of scientific interest. Occasionally such subjects as astronomy are covered, but in these days of radio-equipped sputniks perhaps the latter is not really so remote from our hobby after all.

We would like to hear of readers' experiences on the efficient frequency range of transistors and also their employment in hi-fidelity circuits. He does not like ultra-miniaturisation (matchbox sets, etc) but readily appreciates that other readers do. One of the chief reasons for his interest in transistors is on account of the exorbitant cost of batteries "down under". Readers who do see copies of Australian magazines are invariably horrified at the prices of all radio gear, many items costing more than double the list price in UK and then gaily advertised as bargains. If you are thinking of emigrating to Australia, take as much gear as you can carry.

He also asks about projection TV. Am afraid, OM, interest over here has largely languished chiefly on account of cost, and with many others I personally feel that the "eventual" TV receiver will be in the form of a flat picture to be hung on the wall or stood on the mantelshelf.

Reely

To get round to other correspondents. From P.M. (Gainsborough) comes a complaint. He writes; "Recently you said you were open to receive readers' criticisms. Here is one, and an important one, I think. Insist that all set designers stick to coils of well-known and easily obtainable makes. This business of so many turns of 32 s.w.g. enamelled on a 1/2in former is both irritating and expensive. It is almost impossible nowadays to buy either the wire or a former without a lot of trouble. In any case you have to buy far more wire than you need and the rest of it is usually waste. Even if the gauge happens to be right for the next winding job, the specification is sure to call for either silk or cotton-covered. Because of this silly practice I have already collected half-a-dozen reels which, as far as I can foresee, are useless. In any case the ready-made coils are cheaper than buying the wire. Otherwise the magazine is all right but more articles on refinements such as magic eyes, tuning meters, remote control, noise suppression, etc, would further improve it".

Fireside Listening

Recently I wrote of matchbox receivers, and some interesting correspondence with readers has ensued. An outstanding application of the idea comes from Mr. O. G. Kerslake who

builds miniature receivers into tiny radiograms which form a part of 3-D stage sets which he surrounds with a gilt picture frame for hanging on walls.

He built up the scene with dolls house furniture. The radio located behind the picture scene really works and can be heard clearly at the far end of the room. The clock which tells the correct time is the dial and movement from a small wrist watch; the mirror forming the overmantel is one of the type used in birdcages. The figure sitting in the scene could be a cut-out of your wife or girl friend — failing possession of either of these you could fall back on a pin-up personality.

The usual plaques or model scenes are dead and of little interest, but you can use a working model which might well be based on real life or be an actual scene from your own drawing room, complete with carpet and rug. Other working parts might well be included by imaginative readers. For instance, I would suggest that a "live" fire could be simulated by a peanut bulb behind red celluloid set inside a grate. A small piece of suspended foil would rotate automatically by the heat, giving apparent life and movement to the fire. The purist might even add a little Eureka wire element so heat comes off as well!

The great thing, of course, is to keep everything in the correct proportion to ensure naturalness and reality.


As far as the radio side is concerned, a moving coil headphone earpiece (or even an old m/c microphone) will serve as the loudspeaker, and with the advent of transistors and deaf-aid components a set which would really fit into the "radiogram" cabinet might well be designed. Alternatively, a little judicious cheating is permissible with the larger components hidden behind the breast of the fireplace or even at the back of the scene. There is still time to get one ready as a Christmas present for a special friend. A small ceiling light could be fitted. Thus one could shave in the mirror while listening for the time-signal and weather report.

What's My Line

A.G. of Ewell asks, in a cheery letter: "I have often been amused by some of the sub-headings you use. They remind me of the sub-titles used for the small news items on the front page of the London *Evening News*. You wouldn't happen to be the same chap, would you?" The answer, I am afraid, is no, but on A.G.'s recommendation I am considering applying for the job when it falls vacant.

Finally R.M. of Dorking, another of the Old Timer school, writes: "How thankful I am that I kept up my interest in the technical side of radio. The TV programmes are so dull (except for sport and outside broadcasts) that I should be bored to death if I couldn't get some fun out of constructing, adjusting and experimenting, which is more than most licence-holders get. As for the plays—most of them are feeble, especially those written 'specially for TV' — a phrase I've learned to dread. Produced for any form of entertainment for which an admission fee is charged, the customers would want their money back — and if they didn't get it they would be justified in wrecking the theatre".

THE microdot

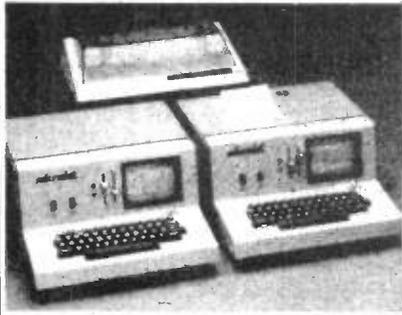

Forget all those messy wires, the MICRODOT now offers a totally integrated communications system.

Write for full details to . . .

POLEMARK Ltd
Lower Gower Road
Royston, Herts SG8 5EA
Tel. Royston (0763) 47874

CW/RTTY COMMUNICATIONS TERMINAL

STANDARD FEATURES INCLUDE

- * Integral high resolution video monitor
- * Professional keyboard with many special functions
- * Real-time clock (constantly displayed)
- * Transmit and receive both CW (morse) and RTTY (teleprinter)
- * Users callsign programmed in
- * Receive CW speed tracking and display
- * Self checking facility
- * Char. by char. or 'page' transmission modes
- * Stylish two tone metal cabinet

OPTIONAL FEATURES


- * Printer interface board (Centronics compatible)
- * On-board 40 column printer (12V)
- * External 80 column printer (SEIKOSHA GP100A)

LOW COST PROFESSIONAL TEST INSTRUMENTS



Hand Held
Analogue and
Digital
Multimeters

16 Models
from £18.75

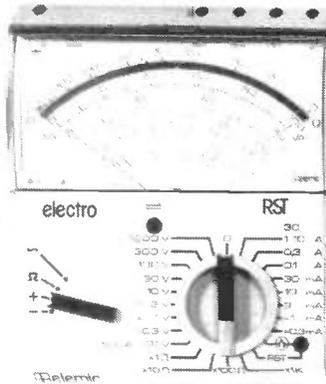

- ★ FREQUENCY METERS
- ★ ANALOGUE MULTIMETERS
- ★ DIGITAL MULTIMETERS
- ★ FUNCTION GENERATOR
- ★ OSCILLOSCOPES
- ★ POWER SUPPLIES
- ★ LOGIC PROBE
- ★ SCOPE PROBES

Write or phone for illustrated test instrument catalogue and price list

Black Star Ltd.
9A, Crown Street
St. Ives, Huntingdon
Cams. PE17 4EB
Tel: (0480) 62440 Telex 32339



Is this scene unfamiliar?

If so, you are obviously missing out on the monthly thrill of receiving a hand-delivered copy of R&EW.



Turn to page 89
in order to rectify this situation..
and become a REWSUB!

£1 OFF FOR REWCARD HOLDERS
Subscriptions ordered before the end of June, and including a REWCARD number, will be charged the reduced rate.

SUPPLIERS & SERVICES INDEX

Modular Power

Power Supplies and dc-dc converters
WE STOCK FOR YOU
ASK US FIRST!
PHONE: (0992) 719458

THIS SPACE ONLY
£20.00



ACORN
Atom & BBC

Your local Fruit and Nut

NORTHERN COMPUTERS
 Churchfield Rd, Frodsham,
 Warrington WA6 6RD.
0928 35110

Save money on drawer sets with the **BITSABOX**



12 drawer white sandwich perch set for your bits and pieces. Drawer size 140 x 50 x 37mm.

ONLY £2.20
 +90p P&P

Cheques/PO to: DMW Boxes
 81 Somerset Road London E17
 Prop R E Davidson
 PERSONAL CALLERS & TRADE ENQUIRIES WELCOME


ANGLIA COMPONENTS



BURDETT ROAD, WISBECH,
 CAMBS., PE13 2PS
 TEL: 0945 63281

CONTACT JOHN WHITE
0277 . 213819

ASCII Keyboards

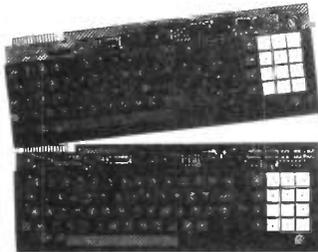

- Upper & Lower Case plus Control
- Autorepeat (Model 777)
- Low Power Consumption
- Parallel Data Output
- Metal Mounting Frame
- Suitable for Tuscan, Tangerine etc.
- Shift & Alpha Lock


Model KB756A	56 key	£44.50
KB710	Numeric Pad	£ 7.50
KB771	72 key	£57.50
KB777	77 key	£65.00

Accessories available include:-

Metal Case	£15.95
Edge Connector	£ 2.25
DC to DC Converter	£ 5.50

(for operation off single 5V supply)

High Performance Monitor

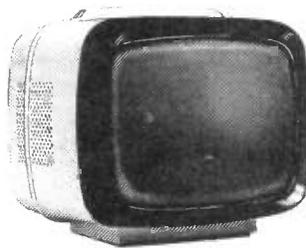

MONITOR

- 12" Green P31 Phosphor
- Toroidal Transformer
- MULLARD C.R.T.
- Composite Video Input
- 80 Character
- Ideal for Apple, B.B.C.
- Line Capability
- Micro, Gemini, Nacrom, Tuscan, Newbrain etc.
- 24MHz Video Bandwidth
- 240V AC Input
- MODEL 101 £89.50



- 80/40 Column
- Expansion Port for CPM, Floppies, Winchester and up to 2M Bytes RAM
- 640/256 Pixel Graphics
- 280 with 32K RAM
- Printer Port
- Ideal with above Monitor
- MODEL A £229.00

ZX Spectrum Series 2 - CP48 32K Memory Extension

Gives total of 48K. Simply fits internally with no soldering. Similar to competitors but only £20.95. Also if fitted by us £29.95.

U.K. Orders add 15% VAT on order total. Overseas orders add £6.50 to cover part cost postage and documentation.

FULL DATA SHEETS ON REQUEST

Citadel Products Ltd
 Dept. REW, 50 High Street, Edgware
 Middlesex, HA8 7EP. Tel: 01-951 1848

NEW PRODUCTS

See The Light

Hellermann Deutsch Ltd., a member of the Bowthorpe Holdings PLC Group of companies, are launching a Fibre Optic Connector — the new TC2 series.


The TC2 incorporates the unique 'BI-TERM' feature, allowing the Connector to be assembled using either the Pot Polish or cleave fibre termination procedure.

Its features are: easy accessibility for ferrule cleaning, alignment sleeves can be replaced in the field. Interface sealing to avoid ingress of dust or moisture, combined bulkhead or jam nut mounting styles as standard, termination of fibres by 'pot or polish' or 'cleave' method, and a comprehensive assembly kit for simple assembly.

Developed for the 50/125um., range of single fibres; average insertion loss is 1dB. The TC2 Connector is designed to allow ferrules and alignment sleeves

to be replaced at a minimal cost where a faulty termination is made, thereby avoiding costs normally incurred in discarding the whole Connector.

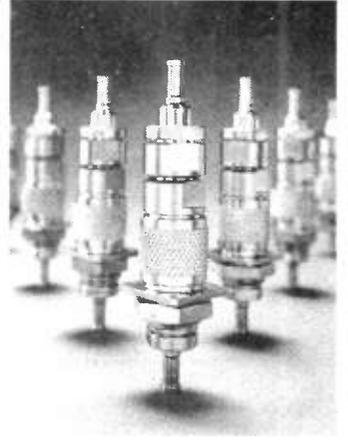For information:
 Hellermann Deutsch Ltd.,
 Technical Sales Dept.,
 EAST GRINSTEAD.



Plain, Portable Printer

Rapid Terminals now offer a plain paper, portable printer manufactured by Digital Equipment Corporation. Known as the DECwriter Correspondent (LA12), it is a 150 character per second dot matrix printer that measures only 46.5 x 14.4 x 39.4cm. In addition to the usual EIA standard RS232C, RS423 and CCITT-V28 serial interfaces, the LA12 also incorporates an acoustic coupler, approved to work on British Telecom modems, which will connect to a host computer over standard telephone lines.

The LA12 employs friction feed and will accommodate any paper up to 8.5 inches wide. A tractor feed option is available for use with fan fold paper.

Each character is printed within a 9 x 9 dot matrix with true descenders. Character spacing can be varied between 5 and 16.5 characters per inch, the latter

allowing a full 132 characters to be printed on 8.5 inch wide paper. Line spacing is 2 to 12 lines per inch.

For international use, the LA12 incorporates a universal power supply and character sets for ten languages. The full 128 ASCII character set can be printed using the LA12's QWERTY standard keyboard. In addition, the keyboard can be changed to numeric data entry mode using a single keystroke (an indicator shows if the numeric code is selected).

The LA12 is flexible when communicating with a host computer. Two models (C and D) are available, both having the EIA serial I/O port operating at 50 to 9600 baud. The Model C also includes an acoustic coupler.

The acoustic coupler operates at 300 baud. It is compatible with both Bell 1035 and CCITT-V21 specifications. The coupler 'muffs' are adjustable for different size telephone handsets accommodating most standard telephones.



Rapid Recall Ltd.
 Rapid House,
 Denmark Street,
 HIGH WYCOMBE,
 Bucks.
 HP11 2ER.

Beckman Measures Up

A low-cost version of the successful T-series handheld digital multimeters has been introduced by Beckman Instruments. At only £43.45 (plus VAT), it is the lowest priced professional quality instrument currently on the market.

The T90 offers six resistance ranges from 200R to 20M plus a separate diode test function, five DC voltage ranges from 200mV to 1000V (0.8% accuracy), two AC voltage ranges of 200V and 600V (1.5% accuracy) and five DC current ranges from 200uA to 2A. There is no AC current range.

All functions and ranges are selected by a single rotary switch, the meter being fitted with an on/off switch. The 3½ digit liquid crystal display, features automatic decimal point and polarity, plus overload and low battery indication.

The T90 will operate continuously for 200 hours from a



standard 9V battery. Size is 150 x 90 x 30mm and weight only 285g, including battery. A selection of accessories is available. Beckman Instruments Ltd., Mylen House, 11 Wagon Lane, SHELDON, Birmingham, B26 3DU.

PT's F1 HF Rx

Phase Track announces a new and advanced HF broadcast receiver. It discards synthesiser techniques, because of their poor performance. In place of which, is an application of synchronous demodulation.

In its specific application to BBC World Service reception the limited channel capability is no drawback and the use of crystal control gives the receiver a high standard of performance, in such a compact form.

The carrier recovery technique is the result of a considerable amount of practical investigation. Momentary carrier fades hardly affect the fly-wheel synchronisation system, making it almost immune to interference.

practical the application of single sideband techniques to the

reception of AM signals. This system has been made possible by the greater production accuracy of specially developed thick film circuits.

The LINIPLEX F1, HF receiver is available from Phase Track Ltd at £500 (ex works) and includes a universal mains adaptor, spare antenna plugs, spare fuses, a 4M super-flexible wire dipole antenna, adjusting tool and fully comprehensive Operation and Maintenance Manual. It is guaranteed against defective components or bad workmanship for a period of 1 year from the date of purchase. Available from Harrods, London, in April at about £800. Phase Track Ltd., 132 Queens Road, READING, Berks, RG1 4DG.



CALL IN AND SEE FOR YOURSELF

AUDIO ELECTRONICS

ALL PRICES INCLUDE VAT

TEST EQUIPMENT CENTRES ALL MODELS ON DISPLAY OPEN SIX DAYS A WEEK

RETAIL • MAIL ORDER • EXPORT • INDUSTRIAL • EDUCATIONAL

DIGITAL MULTIMETERS (UK C/P Free)



ALL MODELS 3 1/2 DIGIT UNLESS STATED



Model	Specifications	Price
HAND HELD	With free carry case	
KD25C	13 range 0.2A DC 2 meg ohm	£24.95
KD30C	16 range 10A DC 2 meg ohm	£29.95
KD30C	26 range 10A AC/DC 20 meg ohm	£34.95
KD55C	28 range 10A AC/DC 20 meg ohm	£39.95
6010+	22 range 10A AC/DC 20 meg ohm	£34.40
7030+	As 6010 but 0.1% basic	£41.30
KD615	16 range 10A DC 2 meg plus Hfe tester	£39.95
189M	30 range 10A AC/DC 20 meg plus Hfe tester	£69.95
HAND HELD AUTO RANGE		
DM2350	21 range 10A AC/DC 20 meg ohm (Miniature)	£49.95
HD30	16 range 0.2A AC/DC 2 meg ohm	£41.95
HD30/B	As above plus cont. buzzer	£44.50
HD31	22 range 10A AC/DC 2 meg ohms plus cont. buzzer	£58.95
	+Optional carry case £2.95	

BENCH MODELS

TM353	27 range LCD 2A AC/DC	£86.25
TM355	29 range LED 10A AC/DC	£86.25
TM351	29 range LCD 10A AC/DC	£113.85
2001	28 range LCD 10A AC/DC plus 5 range Cap. Meter with case	£108.00
TM451	4 1/2 digit LCD every facility (0.02%)	£171.00
1503a	4 1/2 digit LCD every facility (0.05%)	£171.00
1503Ha	0.03% basic version of above	£189.00
	+Optional carry case £6.84	

ALWAYS BARGAINS IN EQUIPMENT FOR CALLERS

FREQUENCY COUNTERS



PFM200A	200 MHz hand held pocket 8 digit LED	£67.50
B110A	8 digit LED bench 2 ranges 100 MHz	£77.00
B610B	9 digit LED bench 2 ranges 600 MHz	£113.85
B000B	9 digit LED 3 ranges 1 GHz	£178.00
TF040	8 digit LCD 40 MHz	£126.50
TF200	8 digit LCD 200 MHz	£166.75
	+Optional carry case £6.84	
	Prescalars - Extended range of most counters	
TP600	600 MHz	£43.00
TP1000	1 GHz	£74.00

SIGNAL GENERATORS (220/240v AC)



FUNCTION	All sine/square/triangle/TTL etc	
TG100	1 Hz - 100 KHz	£90.00
TG102	0.2 Hz - 2 MHz	£166.75
PULSE		
TG105	Various facilities 5 Hz - 5 MHz	£97.75
AU010	Multiband Sine/Square	
LAG27	10 Hz to 1 MHz	£90.85
AG202A	20 Hz to 200 KHz (List £94.50)	£83.50
RF		
SG402	100 KHz to 30 MHz (Last few)	£59.95
LSG17	100 KHz to 150 MHz	£79.35

ELECTRONIC INSULATION TESTER

YF 501 500 V/0-100m with carry case £63.00

MULTIMETERS (UK C/P 65p)

C7081	50K/V 21 ranges. Range doubler 10A DC	£15.95
SPECIAL PRICE		
ETC5000/5001	21 ranges, 50K/V. Range doubler 10A DC.	£16.50
TMK500	23 ranges 30K/V. 12A DC plus cont. buzzer.	£23.95
NM56R	20K/V. 22 range pocket	£10.95
EU102	14 range 2K/V pocket	£5.95
B30A	26 range 30K/V. 10A AC/DC overload protection, etc.	£23.95
360TR	23 range 100K/V. Large scale 10A AC/DC plus Hfe	£36.95
AT1020	18 range 20K/V. Deluxe plus Hfe tester	£17.50
ST303TR	21 range 20K/V plus Hfe tester	£16.95
YM 360TR	19 range 20K/V plus Hfe tester	£13.95

VARIABLE POWER SUPPLIES (UK C/P £1.00)

PP241	0/12/24V. 0/1A.	£35.00
PP243	3 amp version	£59.95
PS 1307S	8/15V 7 amp twin meter	£24.95

DIGITAL THERMOMETER

TH301 LCD -50 C to +750° with thermocouple £68.43

AC CLAMP METER


ST300 D/300A 0/600 VAC. 0/1 Kohm 9 ranges With carry case (UK C/P 65p) £28.50

LOGIC PROBES

LP10 10 MHz £28.50
LDP075 50 MHz with carry case and accessories £71.30

AUDIO • RF • FUNCTION • PULSE

OSCILLOSCOPES

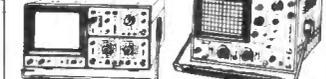

Full specification any model on request. SAE by post.		
HM Series HAMEG: SC THANDAR:		
CS Series TRIO: 3 Series CROTECH		
SINGLE TRACE		
3030	15 MHz 5mV. 95mm tube plus component tester C/P £3.00	£177.10
SC110A	Miniature 10 MHz battery portable (Post free)	£171.00
HM103	15 MHz 2mV. 6 x 7 display plus component tester C/P £3.00	£181.70
	+Optional carry case £6.84 AC adaptor £6.69 Nicads £12.50	
DUAL TRACE (UK C/P £4.00)		
HM203/4	Dual 20 MHz plus component tester	£303.60
CS1562A	Dual 10 MHz (List £321.00)	£269.50
3131	Dual 15 MHz + component tester	£276.00
CS1566A	Dual 20 MHz All facilities (List £401.35)	£349.50
HM204	Dual 20 MHz plus component tester sweep delay.	£419.75
CS1820	Dual 20 MHz with extra facilities (List £508.30)	£485.00
OPTIONAL PROBE KITS		
X1	£7.95	X10 £9.45
X1 - X10	£10.50	X100 £16.95
HIGH VOLTAGE METER		
Direct reading 0/40 KV		
20K/Volt. (UK C/P 65p)		£23.00
DIGITAL CAPACITANCE METER		
0.1 pf to 2000 mfd LCD 8 ranges		
DM6013	£52.75 (Carry case £2.95)	
TRANSISTOR TESTER		
Direct reading PNP. NPN. etc.		
TC1 (UK C/P 65p)		£21.95

AUDIO ELECTRONICS

Cubegate Limited
301 EDGWARE ROAD, LONDON W2 1BN. TEL: 01-724 3564
ALSO AT HENRY'S RADIO,
404/406 EDGWARE ROAD, LONDON W2. TEL: 01-723 1008


FREE CATALOGUE! SEND LARGE SAE (UK 20p)

ALL PRICES INCLUDE VAT
Order by Post with CHEQUES/ACCESS/ VISA or you can telephone your orders. All orders despatched within 5 days unless advised.

Self-Binder

FOR RADIO & ELECTRONICS WORLD

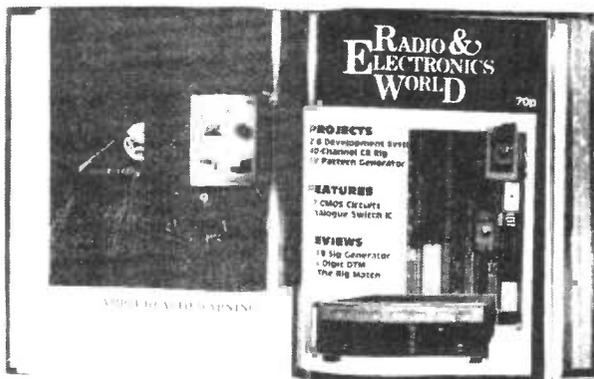The "CORDEX" Patent Self-Binding Case will keep your issues in mint condition. Copies can be inserted or removed with the greatest of ease. Royal Blue finish, gold lettering on spine.



The specially constructed Binding Cords are made from Super Linen of great strength, very hard twisted and twice doubled. They are attached to strong RUSTLESS springs under tension, and the method adopted ensures PERMANENT RESILIENCE of the Cords. Any slack that may develop is immediately compensated for and the Cords will always remain taut and strong. It is impossible to overstretch the springs, as a safety check device is fitted to each.

Price in UK £3.90 including postage, packing and VAT.
Overseas readers please add 30p

Available only from:
R&EW Publications,
45 Yeading Avenue,
Rayners Lane,
Harrow, Middlesex HA2 9RL

NEW PRODUCTS

Stolec Stoppers


Stolec, a UK based company with subsidiaries in the USA and Japan, are offering a range of new filters and suppression devices for removing RFI interference.

The range covers currents from 1 — 100 Amps, single and three phase.

Stolec can also offer a fast custom design service through their associate company, Roxburgh Suppressors Ltd., of Rye, East Sussex.

For further information please contact:

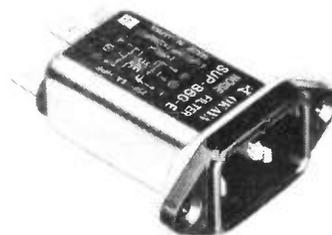*Stolec Ltd.,
Unit 1,
Haywood Way,
Ivyhouse Lane,
HASTINGS,
East Sussex.*



Neons On Parade

BOSS Industrial Mouldings Ltd, as sole UK Distributors for Philips Miniature Neons, have introduced a range of blue and green fluorescent neons. These have AC striking voltages of 100V and 94V respectively, and life expectancy of greater than 20,000 hours. Both neons are available either as individual discrete components or with an appropriate butt welded special film resistor suitable for 220-250V operation at temperature up to 130°C.

*BOSS Industrial Mouldings Ltd.,
James Carter Road,
MILDENHALL,
Suffolk,
IP28 7DE.*




Whiteley's Into Toroids

A new range of toroidal transformers has been launched by Whiteley Electronics Limited of Mansfield.

The transformers, which are suitable for a variety of power and audio applications, are available in VA ratings of 20 to 400 and a range of core sizes from 25 to 150mm (OD). The manufacturers offer advice to customers on the most practical and cost effective units for particular applications.

Though Whiteley have been making laminated core transformers for more than 40 years, this is the first toroidal type to be manufactured by them. The Company use the toroidal transformers in their production of audio and other electronic equipment.

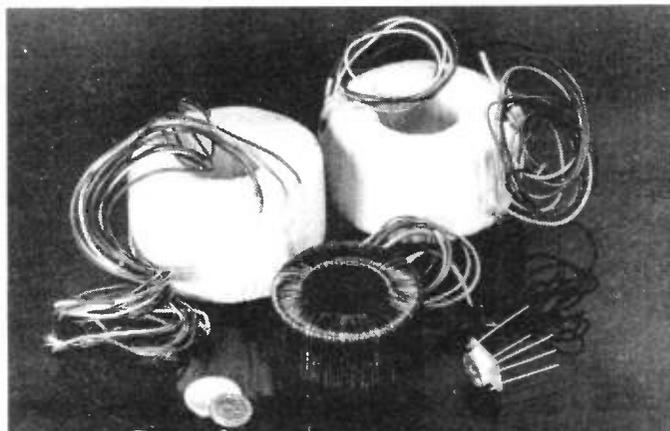*Whiteley Electronics Ltd.,
Victoria Street,
MANSFIELD,
Notts,
NG18 5RW.*



Dynamic Duo

Duckhams have made two further additions to their range of industrial aerosols. They are a Dry Film Release Agent and Lubricant and an Electrical Cleaning Spray — 'D11' and 'D12'.

'D11' — a dry film release agent and lubricant is a new concept in dry-film, non-stick surfacing. 'D11' will deposit a thin, smooth white layer on metal, plastic, rubber and wood. Of high adhesion and chemical resistance, the deposit is intended for all types of extrusion, compression and injection moulding.

'D12' — an all-purpose electrical cleaning spray for all electronic components used in industry as well as in computers and marine, automotive and machine electrics etc. Compatible with all plastics, metals and lacquer, 'D12' is non-toxic and non-flammable and is safe to use while machines are in motion.

Its powerful spray means contaminant is flushed away with



the minimum of waste, while instant evaporation and the absence of both oil and silicon ensures a residue-free surface results.

Alexander Duckham & Co. Ltd.,
Summit House,
WEST WICKHAM,
Kent,
BR4 0SJ.



FORCEful Mobiles

Cody Electronics, the exclusive UK distributors for the Force range of VHF and UHF hand portables announce the addition of the new Force UHF mobiles to their range of Force Communications Equipment.

A steel case and die-cast rear metal frame protects the Force Mobile radiotelephone from vibrations and the effects of poor weather conditions. The unit is suitable for virtually all business, industrial, public service and farming applications.

Operating on the frequency range 420 — 470MHz, the unit has 2 to 8 channels and RF Power Output of 15/25 watts. A high performance receiver ensures maximum rejection of ignition noise, adjacent channel

signals and power-off transmitters. The radio has an audio output and there is provision for adjusting the RF Power to meet the requirements of low power systems.

Options available include CTCSS as a plug-in module and five tone signalling in the following formats: ZVE1, CCIR and EEA. The Force is supplied complete with fist microphone mounting hardware and can also be used as a Base Station Unit.

Frank Cody Electronics Ltd.,
Star House,
Gresham Road,
STAINES,
Middlesex,
TW18 2AN.

SELECTRONIC

Radio, TV and Radio Communication
Specialists

934MHz UHF Radio Equipment

An easily installed radio system, with uses for small businesses, from home to small boats and a useful home to car two-way private radio system. Range available from this equipment — mobile to base 10 - 15 miles; base to base up to 100 miles (conditions permitting).


We have in stock the full range of Reftec equipment, i.e. Mobile Transceiver MTR 934/1 plus full range of aerials and fittings, etc.

- ★ STOCKISTS OF AMATEUR RADIO EQUIPMENT:
Yaesu, Trio, F.D.K. Tonna, Jaybeam, Revco etc.
- ★ REPAIR & MODIFICATIONS BY EXPERIENCED
& QUALIFIED STAFF.
- ★ CREDIT TERMS AVAILABLE

For further information please ring:
Mike Machin on (0268) 691481.


Tandy
AUTHORISED DEALER

203, HIGH STREET,
CANVEY ISLAND

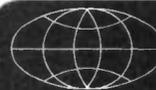

Intermedial Ltd.

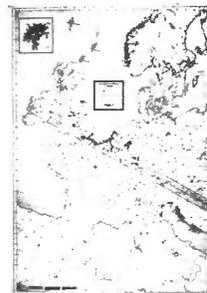
3, Beech Avenue, Eastcote, Ruislip, Middx. HA 4 8UG, Tel. 01 8664641



PRECISION LOCATORSET

With the accuracy of a computer program (tolerance less than .5%), this map and ruler cannot be compared with ordinary locator maps.

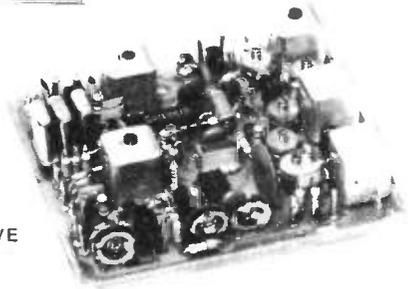- Ruler can be fixed at QTH •Size 30 x 42½ inches, scale 1:3 million •Printed in 4 colours on washable plastic •Metal top and bottom strips •Approved for contests •Full directions •Dispatched in sturdy cylinder. £11.50



PLL TRANSCEIVE V.F.O.

Converts any surplus radio telephone into a continuously variable F.M. transceiver. Microphone is connected to unit and a stable 2 metre F.M. signal is available for driving the amplifier stages. On receive the unit produces a local

oscillator signal 10.7MHz below signal frequency. •600KHz repeater shift •Suitable for other I.F.'s •Extension for digital display •Kit includes all components (exc 3 Xtals and varco) •8 pages of directions. £14.90 (directions only £0.95)

XTALS 46.56MHz 46.36MHz 43.00MHz £11.50

C.W.O. All prices incl. VAT, p&p (within U.K.)



THE **AUTOSCAN 5000** IS UNIQUE

IT'S PROBABLY THE ONLY SCANNING CB RIG IN BRITAIN TODAY - AND BRITISH DESIGNED AND BUILT TOO.

THIS IS THE START OF A NEW GENERATION OF QUALITY RIGS AND HAS ALREADY RECEIVED WIDE ACCLAIM FROM USERS AND REVIEWERS ALIKE - FAR OUTCLASSING OTHER PRODUCTS IN DESIGN, PERFORMANCE AND LOOKS.'

IF YOU ARE A SERIOUS BREAKER YOU WILL BE CURIOUS ABOUT THE AUTOSCAN 5000. FIND OUT MORE FOR YOURSELF AND HOW YOU CAN TRY ONE BY WRITING FOR OUR BROCHURE TO THE MANUFACTURERS:

MAGPIE ELECTRONICS LTD., FREEPOST, ANDOVER, HANTS.

SP10 2BR (NO STAMP NEEDED) OR TEL: 0264 66361

NEW PRODUCTS



Counting Benches

A new low-cost bench-top frequency counter offering a wide range from 5Hz to 650MHz has been introduced by GSC.

The new Model 6000 incorporates an 8-digit LED display and simple pushbutton controls with LED indicators for selecting the input, gate time and lowpass filter.

Two front-panel BNC inputs are provided: one covering the range 5Hz to 100MHz with a 1M input impedance and the other for signals between 40MHz and 650MHz with a 50R impedance. Gate times of 0.1, 1.0 and 10 seconds are available, and a

switchable low-pass filter provides 3dB/octave roll-off at 60kHz for audio and ultrasonic measurements.

The standard Model 6000 incorporates a 3.579545MHz temperature-compensated crystal oscillator with an accuracy of ± 1 part in 10^6 .

The instrument is compact (76 x 254 x 178mm) and lightweight (1.6kg), and features a flip-up leg for benchtop use.

Global Specialties Corporation, Shire Hill Industrial Estate, SAFFRON WALDEN, Essex, CB11 3AQ.

Please mention

RADIO & ELECTRONICS WORLD

when replying to advertisements

TALK TO THE WHOLE WORLD

Study now for the **RADIO AMATEUR'S EXAMINATION**

We have had 40 years successful experience in training men and women for the G.P.O. Transmitting licence.



FREE R.A.E. brochure without obligation from:-

British National Radio & Electronics School
READING, BERKS. RG1 1BR

Name

Address

REW6/822

BLOCK CAPS PLEASE

A Clean Sweep


For the first time, Datong have developed an Automatic Notch Filtering system for use with any receiver. Presented in a new aluminium case (measuring only 150 x 90 x 42 mm). Model ANF gives the user a powerful tool to remove tune-up whistles and heterodyne type interference - it connects in series with the receiver's loudspeaker.

The Datong ANF continuously scans the audio frequency range from 270Hz to 3.5kHz. Whenever a whistle or heterodyne is detected, model ANF automatically locks onto it, and notches it out. It will clear any interference from the DX you are working, in typically 1 second or less. The notch is extremely deep, typically better than 40dB at 3.5kHz, and should the interfering signal drift. Model ANF will track it automatically.

The notch can be moved manually if the user wishes, but due to the sharpness of the filter notch, the ANF has automatic frequency control (AFC) in the manual notch position. This unique facility prevents the user having to search for the best notch position.

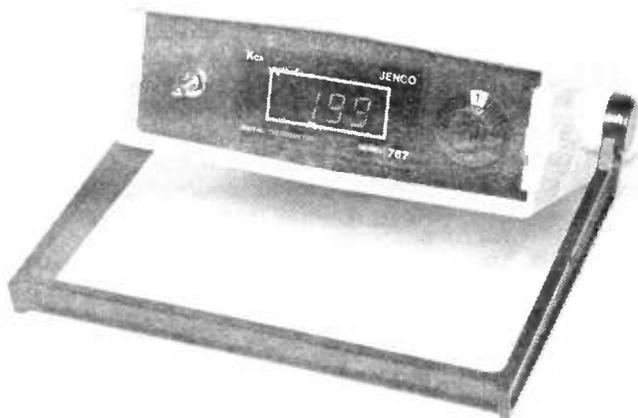Model ANF is able to detect and lock onto whistles up to 6dB below the level of other signals. It contains its own 2 watt audio power amplifier and requires an external 12 V DC supply. The price of the unit is £67.85 (including VAT) and it can be obtained from the Manufacturer direct or through Datong dealers. *Datong Electronics Ltd., Spence Mills, Mill Lane, Bramley, LEEDS. LS13 3HE.*





Centemp Temp Sense

Centemp Instrument Company have added a range of bench mounting digital thermometers to their range of temperature measuring instruments. Available in base metal thermocouple calibrations J, K and T, the 199 series features an analogue output of 1mV/°C resolution. Accuracy is quoted as ± 0.1%. Competitively priced at £189

excluding VAT the 199 series comes complete with two metres of mains lead.

For further details please contact:

Centemp Instrument Co.,
62 Curtis Road,
HOUNSLOW,
Middlesex.
TW4 5PT.


Bigger Exposure

In the past, ultra-violet units with a large exposure area have always been expensive. The UV415 from Decon Laboratories is a new unit with an exposure area of 45 x 24cm, but a price of only £97.

The light source is four 15W actinic blue fluorescent tubes backed up by a reflector and controlled by a six minute electro-mechanical timer. This is housed in a sturdy matt black cabinet which has a foam pad attached to its lid to ensure even distribution of pressure over the


glass plate.

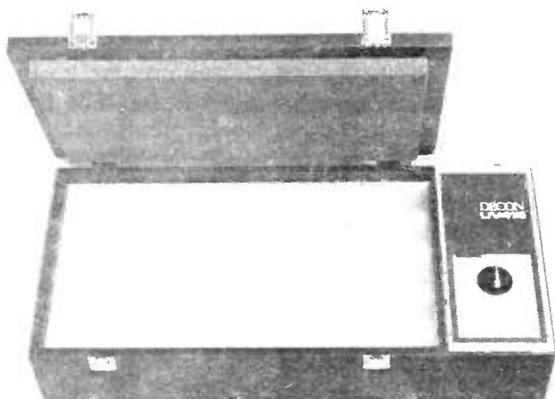To complement this unit Decon Laboratories are also introducing a new range of high quality, spray coated photosensitive copper boards. These are available in four standard tinax bases. The developer for these boards is granular and is packed in small sachets which make up 1/2 L solution.
Decon Laboratories Ltd.,
Conway Street,
HOVE,
Sussex.
BN3 3LY.



GAREX (G3ZV1) SX200-N

THE SUPREME
SCANNER

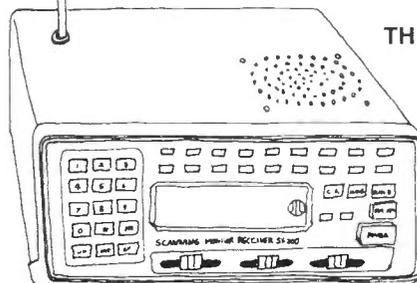

COMPARE THESE FEATURES

- * SPECIALLY DESIGNED FOR EUROPEAN MARKET
- * MICROPROCESSOR CONTROLLED 32,000 CHANNELS
- * AM & FM ALL BANDS
- * WIDER COVERAGE: 26-58, 58-88, 108-180, 380-514MHz; includes 10m, 4m, 2m & 70cm Amateur bands.
- * 5kHz & 12½kHz FREQUENCY INCREMENTS
- * 16 MEMORY CHANNELS WITH DIRECT ACCESS
- * 2 SPEED SCAN/SCAN DELAY CONTROL
- * 2 SPEED SEARCH UP AND DOWN
- * SEARCH BETWEEN PRESET LIMITS UP AND DOWN
- * 3 SQUELCH MODES inc. CARRIER & AUDIO
- * RELAY OUTPUT FOR Aux. CONTROL
- * INTERNAL SPEAKER
- * EXTERNAL SPEAKER & TAPE OUTPUT
- * LARGE GREEN DIGITRON DISPLAY BRIGHT/DIM
- * AM-PM CLOCK DISPLAY
- * 12V DC, 230V AC OPERATION
- * 12 MONTH WARRANTY FACTORY-BACKED SPARES & 'KNOW-HOW' AND THE ALL-IMPORTANT PRE-DELIVERY CHECK BY GAREX THE

MAIN SERVICE & SALES AGENTS £299.00 inc VAT Delivered

NEW *** REVCONE *** ***NEW***
A new top quality 16-element, all British made, VHF/UHF broadband fixed station aerial from Revco. Ideally suited to SX200 and other VHF/UHF Receivers.
PRICE £24.95 inc

SR-9 monitor: 2m FM with 144-146MHz full coverage VFO + 11 xtal controlled channels, ideal for fixed, M, P use. 12V DC operation £47.50
Marine Band SR-9, 156-162MHz, same spec. and price.

CRYSTALS FOR NR-56, SR-9, SR-11, HF-12, TM-56B All 2m channels from 0(145.00) to 33(145.825). Also 144.80, 144.825, 144.85 Raynet at £2.46 (+20p post per order). Over 40 popular marine channels at £2.85 (+20p post).

RESISTOR KITS a top-selling line for many years. E12 series, 5% carbon film, 10Ω to 1M, 61 values, general purpose rating 1/4W or 1/2W (state which)

Starter pack 5 each value (305 pieces)	£ 3.10
Standard pack 10 each value (610 pieces)	£ 5.55
Mixed pack, 5 each 1/4W + 1/2W (610 pieces)	£ 5.55
Giant pack, 25 each value (1525 pieces)	£13.60

NICAD RECHARGEABLES physically as dry cell: AA(U7) £1.30; C(U11) £3.35; PP3 £5.55. Any 5+: less 10%, any 10+: less 20%.

CRYSTAL FILTER 10.7MHz, 12½kHz spacing, ITT 901C £6.90
10.7MHz, 25kHz spacing, type 914B or 909B £6.90

HT TRANSFORMER multi-tap mains pri.: 5 secs. 35V 200mA, 115V 150mA, 50V 500mA, 150V 300mA, 220V 300mA £5.50

PYE RADIOTELEPHONE SPARES (s.a.e. full list) Ex. equip., fully guaranteed. Cambridge AM10
10.7MHz 1F. £3.65 2nd mixer £3.45 455KHz block filter 12½kHz £9.40 dirto 25kHz £3.45 455KHz AM IF £4.95 Audio bd. £1.95
WESTMINSTER W15/W30 AM Rx RF 68-88MHz or 148-174MHz £6.95 10.7MHz 1F (inc. 12½kHz xtal filter) £8.25 2nd Osc £2.10
455KHz 1F £5.65 455KHz block filter (12½kHz) £7.35 Squelch £1.45 QQ206-40a (quick-heat) RF tested £11.95 Aerial relays £1.50
PYE SPARES ARE OUR SPECIALITY - COMPLETE UNITS ALSO AVAILABLE

GAREX FM DETECTOR and squelch conversion for Pye R/T equipment Ready assembled, full instructions. Tailor-made, easy-fit design, replaces existing squelch board, with minimum of modifications. For AM Cambridge £6.30; for Vanguard AM25B (Valve RX) £6.10; for Transistor Vanguard AM25T £6.95

MAIN DISTRIBUTOR OF REVCO AERIALS & SPECIAL PRODUCTS
(trade enquiries welcome)




PRICES INCLUDE UK P&P and 15% VAT



GAREX ELECTRONICS

7 NORVIC ROAD, MARSWORTH, TRING, HERTS HP23 4LS
Phone 0296 668684. Callers by appointment only.

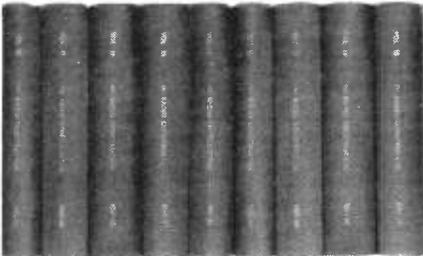BARGAIN OFFER ANNUAL BOUND VOLUMES RADIO & ELECTRONICS CONSTRUCTOR



Each of these handsome bound volumes contain more than 150 practical articles in their 700-800 pages of text, published in 12 monthly issues of R&EC.

12 monthly issues to August 1978 (Vol. 31), 1979 (Vol. 32), 1980 (Vol. 33).

* **Volume 33** contains Ian Sinclair's Databus Series — **How Microprocessors Work** Selection & Bussing, CPU Registers; Addressing Memory The Accumulator; Inputs & Outputs; Interrupts; Status Register; Signed Binary Arithmetic; Computing Languages.

ONLY £4.95 each inclusive of post and packing.

Subjects cover - Amplifiers, Amplifier Ancillaries, Calculators, Electronics, 'In Your Workshop', Receivers, Receiver Ancillaries, Television, Test Equipment etc. etc.

12 monthly issues to July 1974 (Vol. 27), 1975 (Vol. 28), 1976 (Vol. 29), 1977 (Vol. 30).

ONLY £3.95 each inclusive of post and packing.

Please send remittance payable to 'RADIO & ELECTRONICS WORLD' stating volumes required to:—

DATA PUBLICATIONS
45, Yeading Avenue,
RAYNERS LANE, HARROW
Middlesex HA2 9RL

FOR SALE. GSC 2001 Function generator, and Maxi-100 frequency counter. Virtually unused. £80 each. Phone 05402-677.

OSCILLOSCOPE. Solartron Solarscope, type CD64 3S, 1961, any test, delivery possible. £30 o.n.o. Telephone: London (01) 947-8365.

SCARBOROUGH. Derwent Radio for Communications receivers, new, second hand. Good trade-in. Thousands of components, books, magazines. 5 Columbus Ravine, Scarborough. Tel: 0723-65996.

OSCILLOSCOPE. Telequipment D52 dual beam + manual + new probe kit (worth £15). V.G.C. £90 o.n.o. Phone: 021-236-3583.

ZX81 & SPECTRUM SOFTWARE. Q.R.A. Distance/Bearing and Log. Complete with full contest score, graphic map of both Southern & Northern Europe all on one programme, only £4.95 inc. P&P Alan Parrott, 72 Godstone Road, Kenley, Surrey, CR2 5AA.

FOR SALE. Pair Hi-Fi stereo headphones, Howland West Audio CIS-550. £10.00 o.n.o. Box No. 36.

NATIONAL PANASONIC. Auto stop stereo cassette deck RS-260USD. £35.00 o.n.o. Box No. 37.

RACAL RA17. Professional communications receiver. 0.5 to 30MHz. Very good condition. £145.00. G8JDE, QTHR, Telephone: 095-279-375.

COMPONENTS. Redundant stock now available. Very competitive prices, S.A.E. for list. Datong Electronics Ltd., Spence Mills, Mill Lane, Bramley, Leeds, LS13 3HE.

TRIO TR2400. Synthesised handheld 2M transceiver, case, nicads and charger. V.G.C. £135. LOW linear amp. £15. 13.8V p.s.u. £12. M.M. 2M to 10M receive converter £12. Trio JR500 ur bands H.F. receiver, requires attention, £12. WANTED: 2M, 30W linear amp plus preamp. 6 or 8 element yagi and rotator. Telephone: Luton (0582) 31075.

NEW BARGAINS. Quality L.C.D. Watch pens. Take 'Parker' refills, £3.99. Qartz L.C.D. Watches, £3.99. Murphy stereo cassette recorders (portable) £39.99. P&P 45p. Send 45p & 9" x 4" s.a.e. for illustrated lists (components, kits, etc.) Wand Electronics, 95 Albert Road, Levenshulme, Manchester. Tel: 061-225-7684.

INTERESTED IN RTTY? You should find the **RTTY Journal** of interest. Published in California, USA, it gives a wide outlook on the current RTTY scene. RTTY-DX; DXCC Honour Roll; VHF RTTY News; and up to date technical articles are included. Specimen copies 35p from The Subscription Manager, RTTY Journal, 21 Romany Road, Oulton Broad, Lowestoft, Suffolk NR32 3PJ.

POWER SUPPLIES TRIPLE OUTPUT. Lambda Linear +5V 3A ± 12 to 15V 1/2A £25 each. Also TV Monitor 15 inch high resolution picture or Data, cased £45.00. Ring 0279-504212.

WANTED. Loan or buy. Service manual, Rigonda. M.A. Haddy, 33 Bolton Lane, Bradford, Yorkshire, BD2 1DR.

AERIAL BOOSTERS. Improve weak radio and television reception, (indoor types) from £7.00. S.A.E. Leaflets. Electronics Mailorder, Ramsbottom, Lancashire, BLO 9AGR.

DIGITAL WATCH REPLACEMENT PARTS. Batteries, displays, backlights, etc. Also reports, publications, charts, S.A.E. for full list. Profords, Copners Drive, Holmer Green, Bucks. HP15 65GF.

PRINTED CIRCUIT BOARDS NAME-PLATES AND LABELS. Designed and manufactured. Short and long runs. Prototype PCB's. Artwork and photographic services. We'll try to beat any genuine quotation, G.N. Slee, 78 Derry Grove, Thurnscoe, Rotherham, South Yorkshire, S63 0TP. Tel: (0709) 895265.

LIST-A-RIG. A service offered by G3RCQ Electronics to introduce buyers and sellers of used amateur equipment. Buying? It's free, just send an s.a.e. Selling/Wanted? Send s.a.e. for details on how to join the fast-growing list. List-a-rig is sent and updated daily; no waiting, no deadlines. LIST-A-RIG (REW) 65 Cecil Avenue, Hornchurch, Essex, RM11 2NA.

JOIN THE INTERNATIONAL SW LEAGUE. Free services to members including QSL Bureau, Amateur and Broadcast Translation, Technical and Identification Dept., — both Broadcast and Fixed Station, DX Certificates, contests and activities for the SWL and transmitting members. Monthly magazine *Monitor* containing articles of general interest to Broadcast and Amateur SWLs, Transmitter Section and League affairs, etc. League supplies such as badges, headed notepaper and envelopes QSL cards, etc. are available at reasonable cost. Send for league particulars. Membership including monthly magazine etc. £11.00 per annum UK, overseas rates on request. Secretary 88, the Barley Lea, Coventry, W. Midlands.

CLASSIFIED ADVERTISEMENTS

Advertisements must be prepaid and all copy must be received by the 4th of the month for insertion in the following month's issue. The Publishers cannot be held liable in any way for printing errors or omissions, nor can they accept responsibility for the **bona fides** of Advertisers.

Underline words required in **Bold** type. Your name, address, and/or telephone number, if to appear, must be paid for. Telephone numbers count as two words. Please use **BLOCK CAPITALS**. Advertisements are accepted on the understanding that the details stated comply with the conditions of the Trade Description Act, 1968. — Cancellations must be notified by telephone or in writing by the 6th of the month preceding publication. Replies to Box Numbers should be addressed to: Box No. - **RADIO and ELECTRONICS WORLD**.

Where advertisements offer any equipment of a transmitting nature, readers are reminded that a licence is normally required. **Rate: 12p per word. Minimum charge £2.00** **Box No. 30p extra**

Send your copy to **RADIO & ELECTRONICS WORLD, Classified Ads., 45 Yeading Avenue, Rayners Lane, HARROW, Middlesex. Tel: 01-868-4854.**

QSL CARDS. Printed 50 for £9.90, 100 for £11.55, 500 for £23.35. State preferred background colour and send copy and payment to: Gainsborough Studio, P.O. Box 3, Liverpool, L10 4YY.

FANTASTIC OFFER. 200 assorted top specification IC's in manufacturers' tubes plus 10 red LED's and 2 opto-isolator IC's (worth £2.50 alone) plus 44 page Catalogue No. 19 with many thousands of mechanical and electronic bargains. Price: £6.00 including VAT and postage. J.A. Crew & Co., Spinney Lane, Aspley Guise, Milton Keynes, MK17 8JT.

TRIO R1000 receiver, 200kHz — 30MHz Complete, leads, manuals, etc. Original packing. Very little use. £275.00 plus free 40 channel CB Phone: Telford 606451 evenings.

THE BRITISH AMATEUR ELECTRONICS CLUB. For all interested in electronics. Four Newsletters a year: library of technical books and magazines: help for members by experts: annual exhibition. Subscriptions only £4.50 per year, UK & Eire, if joining before 1st July 1983. Details from the Hon. Sec., J.G. Margetts, 113 South Road, Horndean, Hants., PO8 0ER.

ULTRA-VIOLET EXPOSURE UNITS.

Print your own photo-etch PCBs and enjoy the freedom of being able to change your circuits without ruining hours of artwork. UV-300 unit (240 x 150mm/2 x 8 watt) — £35.00 + VAT. UV-800 unit (240 x 350mm/4 x 15 watt) — £85.00 + VAT. The UV-800 is controlled by ZN1034 precision timer. Prices include UK postage. Available direct from the manufacturers: ELECTRONIC ASSISTANCE LTD., Unit 1, Brynberth Industrial Estate, Rhayader, LD6 5EN (Tel. 0597-810711).

OSCILLOSCOPE C.R.T. TUBES. Dual-beam, boxed. G.E.C., Centronic types. £42.50 each inc. P&P Details, specs., Coventry (0203) 463999.

Take me to your Newsagent!

Newsagents often run out of copies of R&EW simply because it is the best value for money electronics magazine around. To make sure you don't miss a single issue, why not fill out the coupon and your newsagent will reserve a copy of every month's magazine ready for you to pick up at your leisure. Fill out the coupon NOW and drop it in when you pick up your morning paper.

NEWSAGENT: Please reserve me a copy of the **JUNE 1983**
RADIO & ELECTRONICS WORLD
and every succeeding issue until further notice.

NAME:
ADDRESS:

Back Numbers

Back issues of R&EW are available from: R&EW Back Numbers Dept., 45, Yeading Avenue, Rayners Lane, HARROW, Middlesex HA2 9RL. Tel: 01 - 868 - 4854. All issues, with the exception of January 1982, are still available. All orders must be prepaid, the cost of each issue being £1.00 inclusive of postage and packing. Photocopies of specific articles can be provided. The month(s) in which the article appeared must be stated. Due to the high staffing costs involved in providing this service we regret that we must charge £1.00 per article. Again, all orders must be prepaid.

Overseas Agents: *Holland Electronics, 071 - 218822, Postbus 377, 2300 A. J. Leiden.*
U.S. Project Pack Agents, Box 411, Grenville, New Hampshire, NH030408. U.S.A.

Subscriptions

If you want to be sure of getting your copy of Britain's most informative Radio/Electronics magazine, **PLAY SAFE & SUBSCRIBE.**

Fill in the form below and send to: R&EW Subscription Dept., 45, Yeading Avenue, Rayners Lane, HARROW, Middlesex. HA2 9RL. Tel: 01 - 868 - 4854

I would like to subscribe to Radio & Electronics World for a year (12 issues). Please start my subscription from the issue.

SUBSCRIPTION RATE	UK	£13.00 per 12 issues
	Overseas	£13.50 per 12 issues

I enclose a cheque/postal order/International Money Order* to the value of £.....

Please debit my Access/Barclaycard* account No.

for my order of £.....

*Delete as applicable.

Signature:.....

Please use **BLOCK CAPITALS** and include postal codes.

NAME (Mr/Mrs/Miss).....

ADDRESS

.....

.....

.....

POST CODE.....

PARTS PROFILE

DFM

Resistors

10k(5off).. 10M.. 100k(2off)..

Potentiometer

220k Min Cermet..

Capacitors

22p.. 27p.. 100p.. 15V tantalum.. 10V tantalum..

Semiconductors

ICM7226A.. 4532.. 4049.. ICM7231A.. 74HC00.. 7805..

Miscellaneous

TC15-65p trimmer.. X110MHz crystal.. 40 pin IC sockets.. 8-digit disc connectors.. 6 digit bezel.. P switch(3off).. 3 way bracket Verobox.. PlayLUCID IC9F711 and edge CBs.. 2 pole push-push SUE (20mm).. knobs.. BNC sockets..

RGB

Resistors

10k(6off).. 1k8(3off).. 75R(4off).. 330R(2off).. 15k.. 6k8.. 5k6.. 2k7..

Potentiometers

100R min preset(3off)..

Capacitors

10u 25V tant(4off).. 100n 50V ceramic(3off).. 2u2 25V tant(2off).. 47u 25V tant..

Semiconductors

1N4148.. BC107(4off).. BS250..

Miscellaneous

6 pin DIN socket.. T1.. SPST toggle.. RG174 50R coaxial cable.. solder.. PCB..



PLEASE SEND ME THE ABOVE, TICKED COMPONENTS FOR USE IN R&EW PROJECTS.

* I ENCLOSE £.....

* PLEASE DEBIT MY *ACCESS/BARCLAYCARD ACCOUNT

NO.:

SIGNATURE

NAME:

ADDRESS:

.....

.....

* PLEASE DELETE AS APPROPRIATE


Advertisers' Index

AMATEUR RADIO	12
AMBIT INTERNATIONAL	4,54,60,59
ARMON PRODUCTS	70
AUDIO ELECTRONICS	83
BINDIT	I.F.C.
BLACKSTAR	81
BNR+ES	71,86
BULGIN	O.B.C.
CITADEL	82
DATONG	71
ELECTRONIKITS	5
EUROPEAN CRYSTALS	71
FOUNTAIN PRESS	6
GAREX	87
G.S.C.	51
INTERMEDIAL	85
MAGPIE ELECTRONICS	86
MARCONI	79
NORTHAMPTON COMMUNICATIONS	5
P.M.S.	I.B.C.
POLEMARK	81
QUARTSLAB	6
RICHARDSON ELECTRONICS	4
SCOPEX	44
SELECTIONS	85
WILMSLOW AUDIO	5

PUBLISHED BY BROADCASTING LIMITED C.1983
 Subscription (INLAND) £13.00 (OVERSEAS) £13.50. Printed in England by LSG Printers & Design
 Distributed by SM Distribution, London, SW9

All reasonable precautions are taken by R&EW to ensure that the information given by our advertisers is reliable. However, we cannot guarantee or accept legal responsibility for it. Information and prices are correct at time of going to press. Reproduction of contents is possible, with permission from the Editor. Budget or short rate starts to which terms are allowable, provided the source is given.

PROM 1

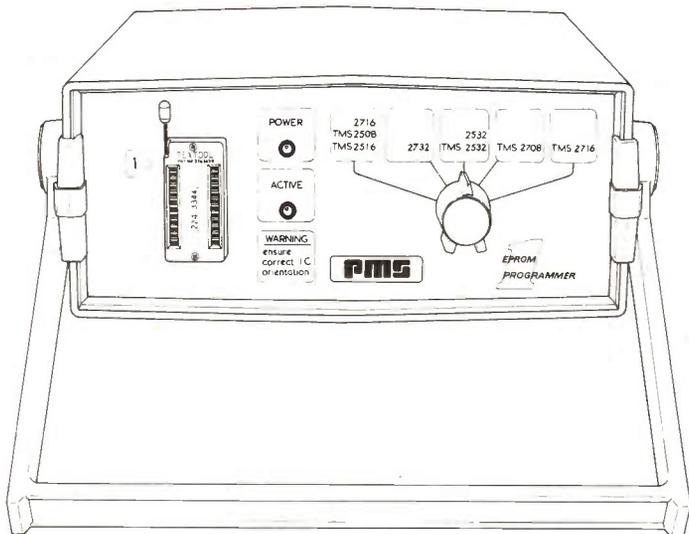

Intelligent EPROM Programmer

The new PROM 1 from P.M.S. offers the user an intelligent, easy to use EPROM Programmer, capable of programming a wide range of common EPROM types. The unit has its own CPU with a 4K memory buffer and communicates to the user's Computer/Terminal over a standard R.S.232 link. Full on-screen editing facilitates easy modification of machine code programs.


The PROM 1 offers the following functions:-

1. Disk to Buffer. Allows a file to be copied from disk into the PROM 1's internal 4K buffer.
2. Buffer to Disk. Allows contents of buffer to be stored on disk.
3. EPROM to Buffer. Allows contents of EPROM to be stored in Buffer.
4. Buffer to EPROM. Programmes EPROM with current contents of the Buffer.
5. Display Buffer. Displays contents of the Buffer on screen and allows full screen editing of the buffer contents.
6. Check EPROM Status. Checks the status of the EPROM plugged into programmer socket i.e. EPROM type and whether it is blank, equal to or not equal to the buffer.

The PROM 1 can be used with just a terminal but functions 1 and 2 will not apply. The unit is supplied with full operating instructions, including CP/M routines for system configuration.

R.R.P. £349.00

ZENITH data systems

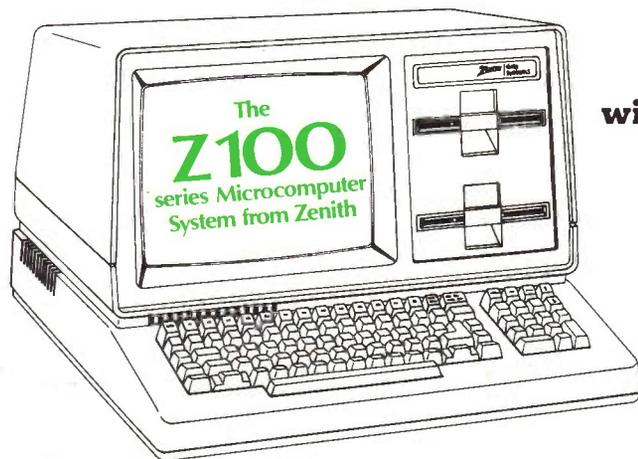

The 16-bit Micro with 8-bit compatibility and colour graphics

Features 8088 and 8085 processors, 128K user RAM expandable to 768 kb, 2 x 320kb drives, 2 serial ports, 1 parallel port, light pen socket and 4 - S100 bus slots for add on options. Disk controller supports 4 - 8" drives and 4 - 5.25" drives. High resolution graphics (640 x 225 pixels, 8 colours). Supplied with MSDOS, CP/M 85, 16-Bit Microsoft Colour Basic with FULL GRAPHICS implementation and complete documentation. The Z-100 comes in two basic forms:-

- Z-120-22 With integral monitor (as illustrated) and 1 colour plane ram set fitted£ 2,590
- Z-100-22 Low profile version with full colour RAM set£ 2,576



Twin 8" Drives (as illustrated), suitable for the Zenith Z-100 series computer with no extra interfacing. Capacity 1.2 Mb per drive£ 1,050
 Colour Monitor. Zenith ZVM-134 high resolution 13" RGB monitor - Special introductory offer price£ 400
 Zenith ZVM-121 12" green screen monitors£ 85

Send for our current list of Ex-demo and second user equipment at low low prices.

PMS
Developments

22 Tarsmill Court Rotherwas Hereford HR2 6JZ
 Tel: Hfd 265768, 50848 (STD 0432)

BULGIN MULTIRANGE CONTROL KNOBS

A UNIQUE BLEND



*More combinations of size,
finish, cap, skirt, push fit, collet etc.*

*now available from **Ambit International***

200 North Service Road, Brentwood, Essex CM14 4SG

Circle No. 200