

NEW IMPROVED

AUSTRALIA
HOLLAND
NEW ZEALAND
NORTH AMERICA \$2.95
D71699

Radio & Electronics

For all aspects of practical amateur radio **World**

Simply the Best

SPORADIC - E PROPAGATION


TILT OVER AND EXTENDING MAST CONSTRUCTION DETAILS

DATA FILE CONCLUDING AUDIO POWER AMPS



HIGH QUALITY DIRECTIONAL COUPLER PROJECT

COMPUTING TRANSMISSION LINE VALUES

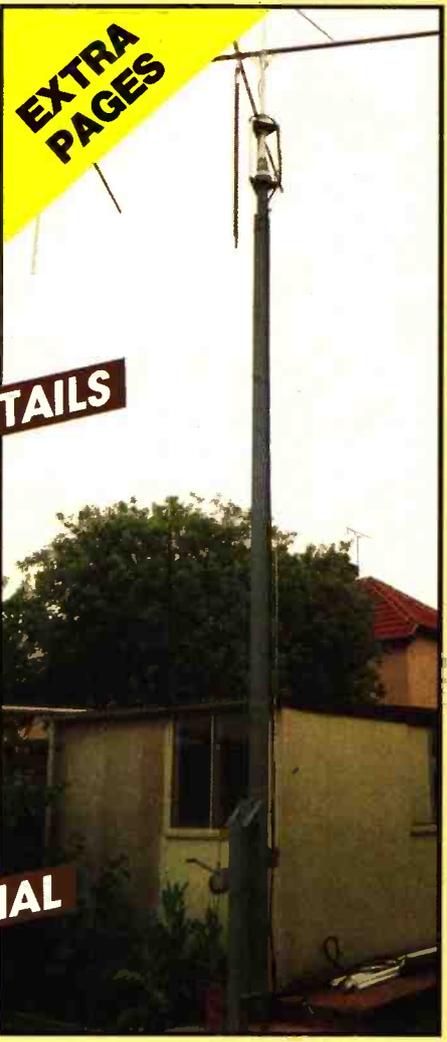BUILD THE 6QV06-40A VALVE LINEAR AMPLIFIER



EXTRA PAGES

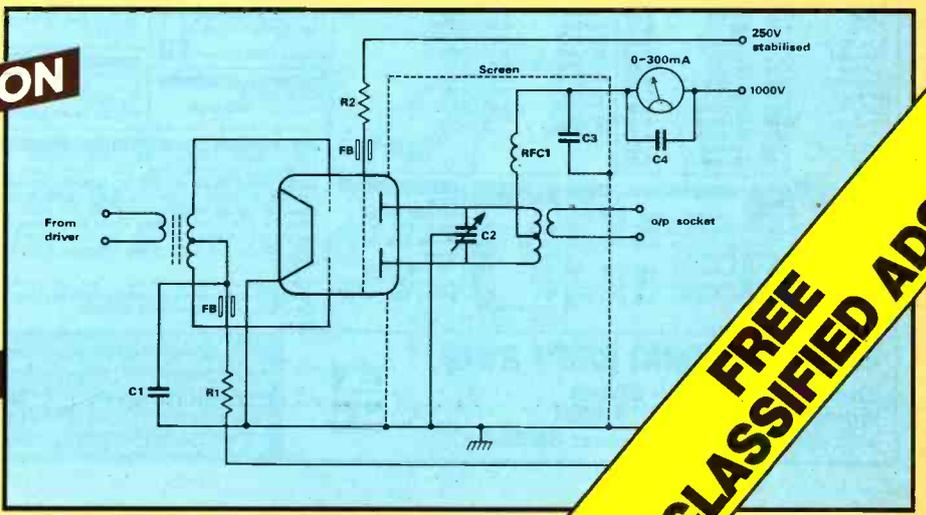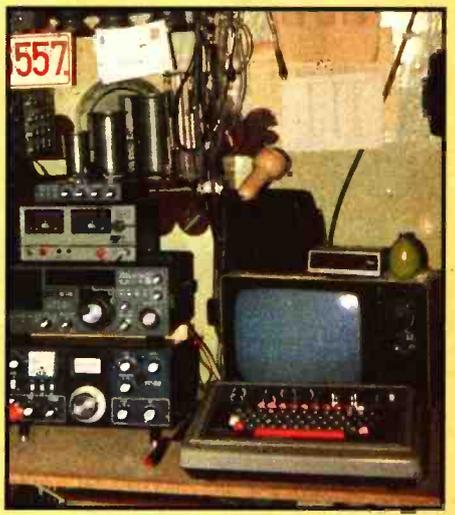

FREE CLASSIFIED ADS



Table of electronic components including TRANSISTORS, DIODES, VALVES, and various types with prices.

ZENER DIODES table listing various diode types and their prices.

RESISTOR - CARBON FILMS 5% table listing resistor values and prices.

RESISTOR KITS table listing kit contents and prices.

RESISTORS - WIREWOUND generally 5% table listing resistor specifications.

TERMINAL BLOCKS AUGUST SPECIAL table listing terminal block types and prices.

MULTIMETER SPECIAL table listing multimeter models and prices.

PANEL METERS table listing meter types and prices.

FUSEHOLDERS table listing fuse holder types and prices.

CHART RECORDERS table listing recorder models and prices.

POWER SUPPLY table listing power supply units and prices.

FUSES - Prices per 10 table listing fuse specifications.

EUROPEAN ADAPTERS table listing adapter types and prices.

IC SOCKETS table listing socket types and prices.

D CONNECTORS table listing connector types and prices.

VOLTAGE REGULATORS table listing regulator types and prices.

LED'S table listing LED types and prices.

IC SOCKETS table listing socket types and prices.

ORDERING: All components are brand new and to full specification. Please add 45p postage/packing (unless otherwise specified) to all orders then add 15% VAT to the total.

MARCO TRADING (DEPT RW8) The Maltings, High Street Wem, Shropshire SY4 5EN Tel: 0939 32763 - Telex: 35565



Radio & Electronics World

CONTENTS

CONSTRUCTION PROJECTS

- 16 High Quality Directional Coupler – A SWR coupler for frequencies above 432MHz
- 31 QWV06-40A Linear Amplifier – Coaxing 100 watts from a double beam tetrode
- 48 40ft Tilt-Over and Extending Mast – Made from readily available materials
- 67 One Night's Work – Adaptations to an electric typewriter
- 70 BBC Micro Volume Control – How to connect your micro to your hi-fi
- 74 TV and Video Interface – Providing a direct connection

FEATURES

- 21 Radio Rallies – A visit to some recent rallies
- 24 Twenty Questions – Based on the RAE
- 25 Sporadic-E Propagation – An unpredictable phenomenon
- 36 Data File – The second part on Audio Power Amplifiers
- 45 BBC Micro Morse Tutor – A simple Morse teaching program
- 55 Improving Resistors – A new look at resistors
- 58 DTI Green Paper – A summary of the discussion document
- 60 Data Communication – A brief description
- 62 Computing Transmission Lines – A program to calculate a matching impedance

REGULAR FEATURES

- 4 Product News
- 13 News Desk
- 68 Amateur Radio World
- 71 Point of Contact
- 73 Dates for your Diary
- 79 ATV on the Air
- 81 Corrections and Mods
- 82 DX-TV Reception Reports
- 86 Short Wave News

SERVICES

- 65 Newsagents Order Form
- 66 Amateur Radio Subscription Order Form
- 75 Radio Amateurs Handbook Order Form
- 81 Next Month in R&EW
- 87 Subscription Order Form
- 89 Back Issues Order Form
- 90 Free Classified Ads
- 91 Free Classified Ads Order Form
- 94 Advertising Rates and Information
- 94 Advertisers Index

Editor DENNIS PADFIELD G1AJQ

Advertisement Manager NICOLA DYER
Advertisement Executive ANNE BRADY

Subscriptions 01-684 3157

Accounts CLARE BRINKMAN

Publisher PETER WILLIAMS
General Manager ALAN GOLBOURN

ON SALE: Second Thursday of the month preceding cover date

NEXT ISSUE: Cover date September 1984 on sale 9 August 1984

PUBLISHED BY: Radio & Electronics World Magazines, Sovereign House, Brentwood, Essex CM14 4SE, England (0277) 219876

PRINTED: In England

ISSN: 0262-2572

NEWS TRADE SALES BY: Seymour Press Ltd, 334 Brixton Road, London SW9 7AG Tel: 01-733 4444

SAFETY IN THE SHACK

Some of the constructional projects described in *R&EW* refer to additions or modifications to equipment. Any alteration or addition to the circuit may invalidate the guarantee.

We prefer that each constructional project contains its own power supply or battery. A constructional project will occasionally describe how the power supplies of any equipment may be used to supply the circuit of that project. Ensure that the power unit in the equipment is adequate to provide the additional load current. In all cases, check that the equipment mains fuse is correctly rated.

Safety in the shack, please at all times.



The new 13 metre satellite earth station antenna, known as System 2, under construction by Marconi Communication Systems Ltd for Mercury Communications Ltd at the Isle of Dogs in London

COVER PICTURES

- Left: 40ft Extending Mast courtesy of G6TNC
- Top right: High Quality Directional Coupler
- Centre right: DATA COM courtesy of OWC6557 and John G6MOK
- Bottom: QWV06-40A Linear Amp circuit diagram

Whilst every care is taken when accepting advertisements we cannot accept responsibility for unsatisfactory transactions. We will, however, thoroughly investigate any complaints.

The views expressed by contributors are not necessarily those of the publishers.

Every care is also taken to ensure that the contents of *Radio & Electronics World* are accurate, we assume no responsibility for any effect from errors or omissions.

Audit Bureau of Circulations membership approved pending first audit
© Copyright 1984
Radio & Electronics World Magazines

PRODUCT NEWS

Featured on these pages are details of the latest products in communications, electronics and computers. Manufacturers, distributors and dealers are invited to supply information on new products for inclusion in Product News. Readers, don't forget to mention **Radio & Electronics World** when making enquiries

BENCH POWER SUPPLY INCLUDES DELAY

New from Thurlby is a 15V 4A version of the PL Series of laboratory bench power supplies. Designated the PL154, the new supply operates in constant voltage or constant current modes from a few milliamps to 4 amps continuous.

A new feature is switchable current limit delay which makes peak currents up to 7 amps available to circuits with fluctuating loads.

Twin digital meters give a highly accurate display of voltage and current levels to a resolution of 10mV and 1mA respectively.


Remote sense terminals

are provided to allow precision to be maintained at high current, and a separate dc output switch enables voltage and current levels to be set before connecting the supply to the load.

The PL154 is part of a wide range of digitally metered bench power supplies from Thurlby which includes single, dual and triple output models.

The PL154 is available from Thurlby Electronics Ltd and their distributors. Price in the UK is £145.00 plus VAT.

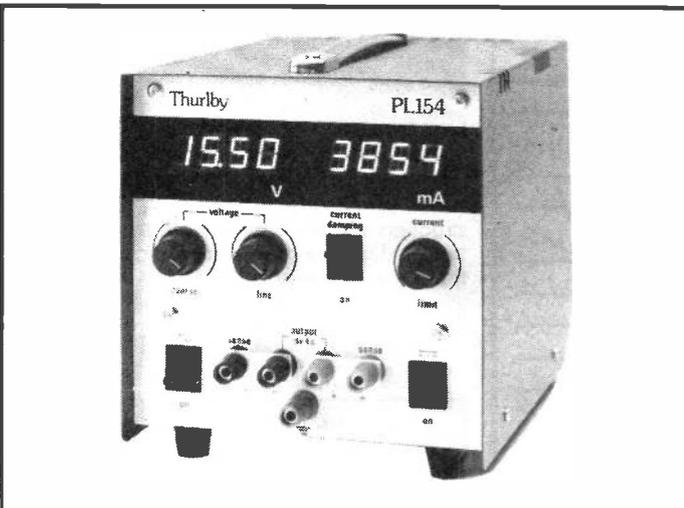Thurlby Electronics Ltd, New Road, St Ives, Huntingdon, Cambridgeshire PE17 4BG. Tel: 0480 63570



GAS-TIGHT INSULATED TERMINALS


Oxley has extended its range of insulated terminals to include both stand-off and lead-through versions designed to provide optimum sealing against gasses and liquids.

These new components, known as CEEL[®] terminals, differ from the standard Barb[®] range by having an enlarged middle section to the spill and

a silicone rubber sealing ring recessed into the PTFE insulator bush.

After assembly, this enables increased pressure to be applied to the silicone rubber and the chassis to ensure a gas-tight seal.

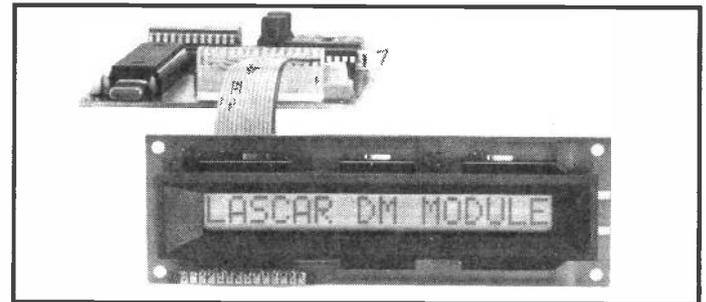CEEL[®] terminals are available in 5A and 15A versions with rated voltages of, respectively, 3KV and 4KV, and mounting hole diameters of 3.96mm and 6.35mm.



DOT MATRIX EVALUATION SYSTEM

A Dot Matrix Evaluation System now available from Lascar Electronics is claimed to save hundreds of man-hours and thousands of pounds in development costs. It allows use of Dot Matrix Displays by users without specialised microprocessor knowledge.

The system is available at a special offer price of £49.95 (+ p&p and VAT) and comprises a 16-character line display complete with bezel and panel mounting kit, a microprocessor-based controller module, inter-connecting cable and a full instruction manual. A 5V dc supply is all that is required to have an LCD Dot Matrix Display system up and running in minutes.

The controller module contains a pre-programmed EPROM which contains the initialisation programme plus

15 standard 'messages'. On-board hexadecimal and programme switches allow custom messages and programmes to be developed. These can then be saved, either by implementing a 'power down-mode' or by reprogramming the EPROM.

Expansion of the system is easily attained as all controls, data lines etc are brought out to a 32 way double-sided edge connector.

The programme messages can also be switched to the display by contact closure or open collector transistor output.

The EVAL-1 Evaluation system will allow many potential new users of Dot Matrix Displays to fit them to their instruments in the minimum time and cost.

Lascar Electronics Ltd, Module House, Whiteparish, Salisbury, Wiltshire SP5 25J. Tel: 07948 567. Telex 447876.

The spills are precision formed from brass and are finished with heavy silver plating.

Assembly is easy and rapid and is effected by inserting the bush into the mounting hole and then pressing the metal spill firmly and slowly into the bush until the positive detent action locks the assembly in place.

Simple tools are available to facilitate this operation.


Leakage rate of correctly sealed terminals is less than 10⁻³ microlitres per second of helium at one atmosphere differential pressure at 20°C ie 15lb per square inch.

CEEL[®] terminals meet the 56 day damp heat climatic category of IEC68 (IEC68: 55/200/56).

Operating temperature range is -55°C to +200°C.

Insulation resistance is greater than 2 x 10⁶ megohms.

PRODUCT NEWS

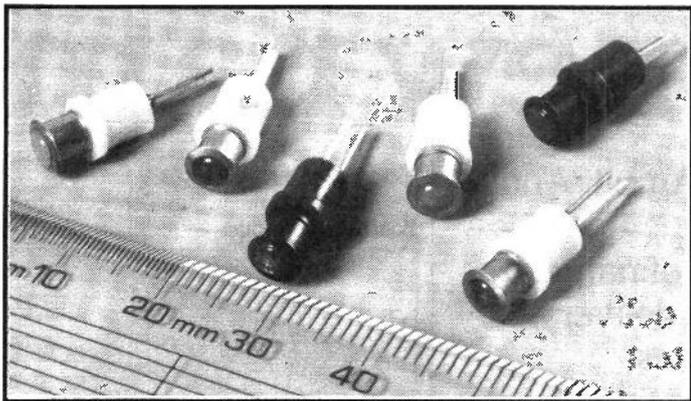

NEW WIDE ANGLE SOLID STATE INDICATORS

A range of wide angle viewing press-fit solid state indicator lamps, the SSI/5 series is available from Oxley.

Approved for military applications against DEF/STAN 59-61/90/195, these lamps are available in red, green and amber versions. They are ruggedly constructed and feature the patented Barb[®] self-locking body outline which allows rapid assembly to panels drilled with 5mm holes.

They are supplied with high dispersion grade PTFE bushes; the bush together with the self-locking mounting providing an excellent seal tested to one atmosphere (15 pounds per square inch equivalent to 33.5 feet or

10 metres of sea water) with a leakage rate of less than 1 millilitre per hour under standard laboratory conditions for sealing against gasses, vapours and liquids.

Terminations can be either tin-lead or silver plated and versions with a black PTFE bush and black anodised aluminium bodies are available for improved visual contrast.

Nominal operating current for the red lamps is 20 milliamps and for the green and amber versions: 40 milliamps.

Nominal luminous intensity is 1.4mcd for the red lamps; 1.5mcd for the green and amber lamps.

Oxley Developments Co Ltd, Priory Park, Ulverston, Cumbria LA12 9QG. Tel: 0229 52621.

A HOT STORY FROM WEST HYDE!

Problems of heat dissipation can be particularly hard to solve on small electronic instruments, where forced ventilation is impractical, and external heat sinks both mar the aesthetic appearance of a product, and add significantly to the cost. Two new case ranges from West Hyde meet this problem head on, and incorporate heat dissipation properties into the case bodies themselves.

The first type of case is panel-mounting to DIN standard 43700 dimensions. Lengths of U-shaped aluminium extrusion are linked together in a number of ways to produce cases in twelve standard sizes. The use of an aluminium profile results in a case with an ideal strength/weight ratio, and allows several useful features to be designed in.

As well as slots to carry PCBs or chassis, the extrusion includes T-slots to accept nuts or hex-head bolts with which hot components such as plastic-package semi-conductors can be mounted. Further external slots take rotating fixing pawls, which allow an instrument to be installed in a panel entirely without access at the rear.

The West Hyde DIN case has a semi-matt black epoxy powder paint finish to assist heat radiation, and a clip-in front panel concealing all assembly screws.

The second case range is intended for free-standing or wall-mounting applications, and is formed from a hollow extrusion in various sizes and lengths.

Being made from a single extrusion, the 'Sink Box' has extreme rigidity and is inexpensive to produce and simple to assemble.

As well as two rows of internal PCB slots, the extrusion incorporates a row of deep fins on one face around a central T-slot, to maximise heat dissipation. Two further T-slots on the opposite outer face allow brackets to be fitted for wall mounting, belt mounting, or to attach the Sink Box within a second enclosure.

The case has a black anodised finish as standard, with matching aluminium end panels and optional moulded nylon bezels.


Both these ranges are available ex-stock from: West Hyde Developments Ltd, Unit 9 Park Street Ind Estate, Aylesbury, Bucks HP20 1ET. Tel: Aylesbury (0296) 20441

FUME EXTRACTION FOR SOLDERING IRONS

Now available in the Climavent range of soldering fume extraction equipment are low-cost suction adaptors which can be attached to conventional soldering irons for efficient extraction of fumes at source.


Introduced as a cost-saving facility, these attachments will allow industrial companies to make full use of their existing soldering appliances when installing a fume extraction system. The range of adaptors available covers all known makes of soldering irons.

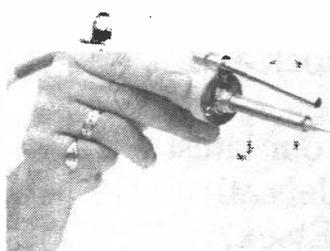The metal suction nozzle of the Climavent adaptors is positioned on the soldering appliance to remove soldering fumes at the point of work, for optimum operator protection. The fumes collected at the nozzle are transferred by a lightweight tubing connection to high velocity extractors in the fume extraction system.



Solder fume extraction systems can be supplied by Climavent Ltd to suit any factory layout for the protection of from two to 450 operatives. Based on a high-vacuum suction ring main arrangement with tubing connections to each soldering appliance, the systems will ensure that the presence of colophony (solder/flux fumes) within the operator's breathing zone is undetectable.

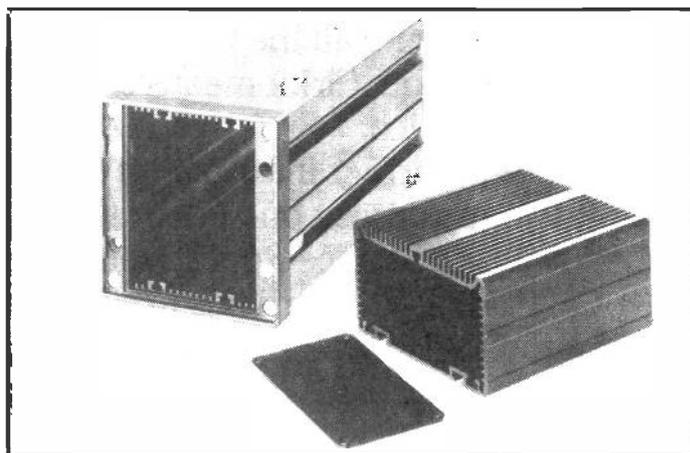Available from: Climavent Ltd, 326 Haydock Lane, Haydock Industrial Estate, St Helens, Merseyside WA11 9UY. Tel: 0942 726164



WAVE GUIDE FILTERS

Now available from M M MICROWAVE Ltd, a member of the Micro Metalsmiths Group of Companies, is a new fully illustrated shortform catalogue detailing their extensive range of waveguide filters.

M M Microwave design, manufacture and test a wide range of radar and telecommunications components

and sub systems. The company is approved to Defence Standard 05-24 and facilities include a fully equipped research and development department and a comprehensive computer aided design library.

This allows engineers to optimise design without having to evaluate prototypes. In addition, high precision computer controlled machining

Cirkit. A new name

This year Ambit will stop being Ambit. And become Cirkit.

Cirkit is more than just a change of name. It means a better service for you. Faster delivery.

A bigger range of the best and latest products with well over 10,000 different items available.

Everything for the home and industrial user.

A whole new Cirkit range of constructional kits, graded for the student, expert and enthusiast.

Modules to build for everyone.

Cirkit is a go ahead company that believes in giving service to its customers.

There's a technically skilled staff to help you.

We keep in touch with the manufacturers and we know what's going on.

As soon as new products are available, Cirkit has them.

Cirkit means a bigger catalogue. A better company to deal with.

And a wider than ever range of products that's growing all the time.

For you, Cirkit means a bigger stock and better service.

For further information send for our latest catalogue or visit one of our three outlets at:

200 North Service Road, Brentwood, Essex, CM14 4SG; 53 Burrfields Road, Portsmouth, Hampshire, PO3 5EB; Park Lane, Broxbourne, Hertfordshire, EN10 7NQ.

To: Cirkit Holdings PLC, Park Lane, Broxbourne, Hertfordshire.
I enclose 80p. Please send me your latest catalogue and 3 x £1 discount vouchers!
If you have any enquiries please telephone us on Hoddesdon (0992) 444111.

Name _____

Address _____

Telephone _____

Area of Special Interest _____


Cirkit

Bigger Stock. Better Service.

REW8

Computer Products

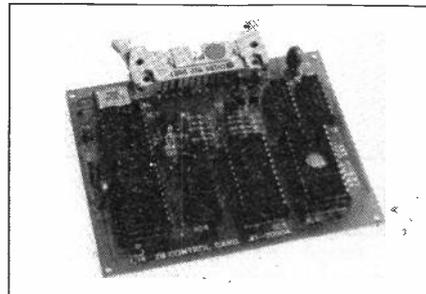A complete range from Connectors to Board Level product



C12 Computer Cassette	21-00012	0.55
BBC to Centronics Printer	03-10019	7.25
BBC to 25 way D Male	03-10021	4.50
25 way D Socket	10-25200	1.90
25 way D Plug	10-25100	1.30
Cover for 25 way D	10-25322	0.93
20 up Eprom Eraser	40-82100	31.25
Z80 A Industrial Controller	40-82000	49.95
6802 Industrial Controller	40-68020	49.95
6502 Industrial Controller	40-65020	49.95
Z8 Basic/Debug Controller	41-00904	50.00

Nicad Batteries & Chargers

Minimum life 600 (300 PP3 size) full charge/discharge cycles. Batteries must be charged from a constant current source only. All batteries are supplied only with a residual charge and should be charged before used.

AA	1.2V	500mAH	01-12004	0.80	0.74
C	1.2V	2.2AH	01-12024	2.35	1.99
D	1.2V	4.0AH	01-12044	3.05	2.85
PP3	8.4V	110mAH	01-84054	3.70	3.50
CH1/22 PP3 Charger 11mA for 16 hours			01-00159		4.30

CH8/RX Multi-purpose Charger 01-02204 9.40

Will recharge AA, C, D and PP3 size cells with automatic voltage selection. Will recharge following combination: 6x D, 6x AA, 6x C, 2x PP3, 2x D+2x C, 2x D+2x AA, 2x D+1x PP3, 2x C+2x AA, 2x C+1x PP3, 2x AA+1x PP3.

Battery Adaptor 01-12001 0.96

Sold in pairs: one to convert AA size to C size and one to convert C to D size. Both may be used together to convert an AA to D size.


Semiconductors

Linear IC's

LM301AN	DIL version	61-03011	0.44
LM308CN	DIL version	61-03081	0.65
LM311CN	Popular comparator	61-00311	0.46
LM324	Low power quad op amp	61-03240	0.67
LM339N	Low power quad comparator	61-03390	0.68
LM346	Programmable quad op amp	61-00346	3.72
LF347	Quad Bi-FET op amp	61-00347	1.82
LM348	Quad 741 type op amp	61-03480	1.26
LF351	Bi-FET op amp	61-03510	0.49
LF353	Dual version of LF351	61-03530	0.76
LM380N	IW AF power amp	61-00380	1.00
NE555N	Multi-purpose low cost timer	61-05550	0.45

for a better service.

NE556N	Dual version of the 555	61-05560	0.50
uA741CN	DIL low cost op amp	61-07411	0.22
uA747CN	Dual 741 op amp	61-07470	0.70
uA748CN	741 with external frequency comp	61-04780	0.40
HA1388	18W PA from 14V	61-01388	2.75
TDA2002	8W into 2 ohms power amp	61-02002	1.25
ULN2283	1W max. 3-12V power amp	61-02283	1.00
MC3357	Low power NBFM IF system and detector	61-03357	2.85
ULN3859	Low current dual conversion NBFM IF and detector	61-03859	2.95
LM3900	Quad norton amp	61-39000	0.60
LM3909N	8-pin DIL LED flasher	61-39090	0.68
KB4445	Radio control 4 channel encoder and RF	61-04445	1.29
KB4446	Radio control 4 channel receiver and decoder	61-04446	2.75
ICM7555	Low power CMOS version of timer	61-75550	0.98
ICL8038CC	Versatile AF signal generator with sine/square/triangle OPs	61-08038	9.50
TK10170	5 channel version of KB4445	61-10170	1.87
HA12002	Protection monitor system for amps, PSUX, TXs etc	61-12002	1.22
HA12017	83dB S/N phono preamp 0.001% THD	61-12017	0.80
MC14412	300 baud MODEM controller (Eduro/US specs)	61-14412	6.85

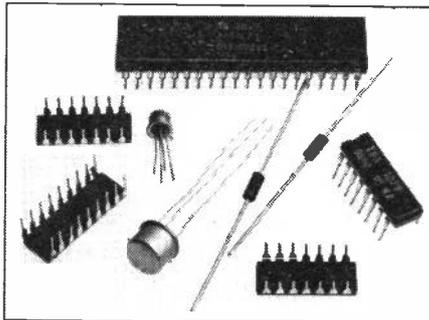

Microprocessor & Memories

Z80A	Popular and powerful 8-bit CPU	26-18400	3.40
Z80AP10	2 port parallel input/output	26-18420	2.95
Z80A CTC	4 channel counter/timer	26-18430	2.90
Z8671	Z8 Micro comp. and Basic	26-08671	17.50
6116-3	16K (2kx8) CMOS RAM 200nS	26-36116	6.68
Z6132-6	32K (4kx8) quasi RAM 350nS	26-06132	15.00
4116-2	16K (16kx1) 150nS	26-24116	1.59
2764	64K (8kx8) 450nS	26-02764	9.50
2732	32K (4kx8) 450nS	26-02732	5.70

Voltage Regulators

7805	5V 1A positive	27-78052	0.40
7812	12V 1A positive	27-78122	0.40
7815	15V 1A positive	27-78152	0.40
7905	5V 1A negative	27-79052	0.49
7912	12V 1A negative	27-79122	0.49
7915	15V 1A negative	27-79152	0.49

Transistors

BC182	General purpose	58-00182	0.10
BC212	General purpose	58-00212	0.10
BC237	Plastic BC107	58-00237	0.08
BC238	Plastic BC108	58-00238	0.08
BC239	Plastic BC109	58-00239	0.08
BC307	Complement to BC237	58-00307	0.08
BC308	Complement to BC238	58-00308	0.08

BC309	Complement to BC239	58-00309	0.08
BC327	Driver/power stage	58-00327	0.13
BC337	Driver/power stage	58-00337	0.13
MPSA13	NPN Darlington	58-04013	0.30
MPSA63	PNP Complement to MPSA13	58-04063	0.30
J310	JFET for HF-VHF	59-02310	0.69
J176	JFET analogue switch	59-02176	0.65
3SK51	Dual gate MOSFET-VHF amp	60-04051	0.60
3SK88	Dual gate MOSFET-Ultra lo noise	60-04088	0.99
TIP31A	Output stage	58-15031	0.35
TIP32A	Complement to TIP31A	58-15032	0.35
VN66AF	VMOS Power FET	60-02066	0.95
IN4001	Rectifier diode	12-40016	0.06
IN4002	Rectifier diode	12-40026	0.07
IN4148	General purpose silicon	12-41486	0.05

Silicon Controlled Rectifiers

BRY55-100	100V .8A	52-55100	0.50
C106DI	400V 4.0A	52-00106	0.70
C122DI	400V 8.0A	52-00122	1.45

3mm Diameter LEDs

V178P	Red	15-01780	0.15
V179P	Green	15-01790	0.16
V180P	Yellow	15-01800	0.18

5mm Diameter LEDs

CQY40L	Red	15-10400	0.12
CQY72L	Green	15-10720	0.15
CQY74L	Yellow	15-10740	0.15


Infra-Red LEDs

CQY99	Emitter	15-10990	0.56
BPW41	Detector	15-30410	1.51

Tri Colour LED

V518	Orange-Green-Yellow	15-05180	0.60
------	---------------------	----------	------

Capacitors

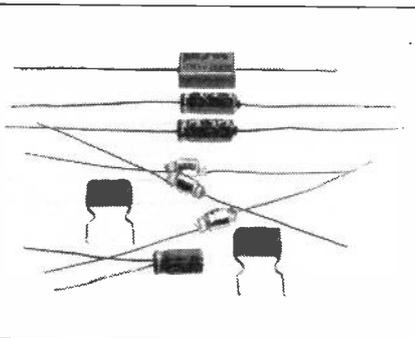

Aluminium Electrolytics Radial PCB Mounting

10u	16V	05-10606	0.24
47u	16V	05-47606	0.28
47u	25V	05-47607	0.28
470u	6.3V	05-47705	0.36
470u	16V	05-47706	0.48

Tantalum Beads

1uf	35V	05-10501	0.18
10uf	16V	05-10601	0.28
47uf	6.3V	05-47601	0.45
47uf	16V	05-47602	0.92

Monolithic Capacitors

1n	04-10204	0.39
10n	04-10304	0.42
100n	04-10404	0.45


Low Voltage Disc Cermaic

1n	04-10203	0.20
10n	04-10303	0.20

Polyester (C280)

10n	04-10305	0.18
47n	04-47305	0.24
100n	04-10405	0.24
470n	04-47405	0.51
1uF	04-10505	0.66

R F Components

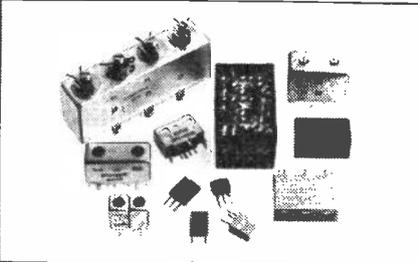

Filters

CFU/LFB CFW/LFH SERIES

Miniature 455kHz filters. I/P and O/P impedance 2K.

	-6dBW	-40dBW		
LFB6/CFU455H	6kHz	18kHz	16-45512	1.95
LFB12/CFU455F	12kHz	26kHz	16-45515	1.95
LFH6S/CFW455HT	6kHz	14kHz	16-45525	2.45
LFG12S/CFW455FT	12kHz	22kHz	16-45528	2.45
CFM2455A Mechanical IF Filters for 455kHz			19-45530	0.77

Crystal Filters 2 Pole Types

10M15A	10.7 Centre Freq.	20-10152	2.10
10M08AA	10.695 Centre Freq.	20-11152	3.49

Inductors

We offer the complete Toko range of fixed and variable inductors. Over 500 coils from audio to V.H.F. See catalogue for details.

Soldering Irons (Antex)

CS240	Iron 240VAC 17 Watts	54-22300	5.20
XS-240	Iron 25W 240V High heat capacity	54-22500	5.40
SK6	Presentation pack of one XS-240 with ST4 stand	54-22510	7.20
MLXS	Handy 12V 15W soldering iron complete with crocodile clips and solder	54-20004	5.60

Please add 15% VAT to all advertised prices and 60p post and packing. Minimum order value £2 please. We reserve the right to vary prices in accordance with market fluctuation.

PRODUCT NEWS

facilities maintain tight tolerances for critical applications, and sophisticated fabrication and evaluation techniques guarantee performance to the highest specifications.

The shortform catalogue details bandpass, bandstop and microwave integrated circuit filters over the frequency range 2GHz to 100GHz. Available with Tchebyshev, maximally flat or linear phase designs, the filters cover a wide range of bandwidth and rejection values.

The catalogue also includes diagrammatic references for Design Engineers and a standard filter specification sheet for specific enquiry/order information.

M M Microwave Ltd, Ings Lane, Kirkbymoorside, York, North Yorkshire YO6 6DW. Tel: (0751) 31955

TELETEXT AND PRESTEL ADAPTORS

GEC (Radio and Television) Limited are to relaunch their Teletext and Prestel adaptors which not only upgrade a standard television set into receiving these functions, but also convert any television set into remote control capability.


Two versions of these machines have been developed for the UK and overseas markets: one which operates in black and white and the other which operates with colour text and graphics. In addition, the Prestel adaptor is available with either numeric information input or full alphanumeric capability.

This unique product is already proving of great interest to the deaf and hard of hearing. Not only does it offer remote control facility, it also means that for the first time they can record programmes with subtitles.

Special arrangements have been made by GEC with the RNID to give preferential terms to registered deaf people through the GEC network of local dealers.

The price of the Teletext adaptors are: Black and white text (MRP) £114.80. Colour £129.30

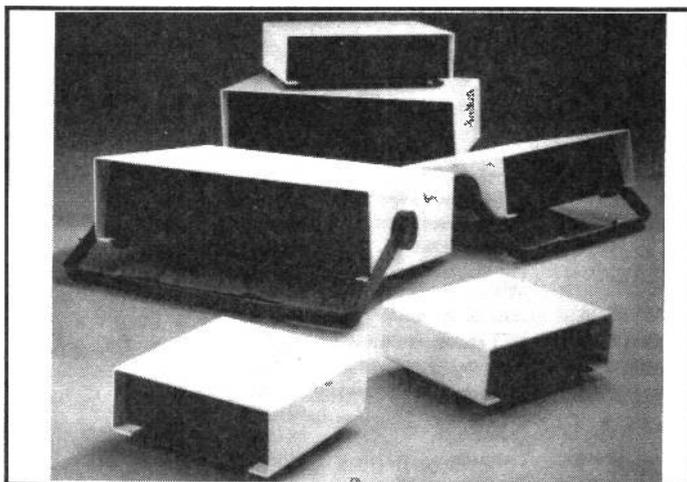GEC (Radio and Television) Ltd, Byfleet Industrial Estate, 2 Canada Road, Byfleet, Surrey. Tel: Byfleet 53134



NEW 'G' CASE

BICC-Vero Electronics has introduced its new range of 'G' cases which provide the latest in soft-line modern styling and are ideal for housing peripheral equipment or portable instrumentation.

They provide all round accessibility for mounting components, wiring and servicing. An integral chassis forms the mounting plate for components, front and rear panels and the cover. The front and rear panels are each secured through the chassis by two screws, which do not intrude onto the panel area thus there are no unsightly fixings visible and the whole panel areas are free for mounting components.

The cover, which comprises the top and sides, slides onto the chassis and fits closely over the front and rear panels. This is secured in position by four further screws which each pass through foot mouldings and tighten onto the

chassis to provide a minimum of assembly operations. The cover also forms a cowl over the front panel, which protects projecting components such as switches and provides a degree of shading for illuminated components such as neons and LCDs.

The new 'G' cases are available in three sizes, of which the largest two can be supplied with a comfortable carrying handle. This handle combines the function of portability with an adjustable tilt feature, as it can be folded back and locked at any angle to suit the user. The range is available as standard finished in epoxy textured paint in an attractive combination of sea-foam and bitter chocolate and a choice of other colours is available subject to a minimum order quantity.

BICC-Vero Electronics Ltd, Hedge End Industrial Estate, Flanders Road, Hedge End, Southampton SO3 3LG. Tel: 04892 81424/5




REMOTELY CONTROLLED ROTATOR UNIT

A substantially built rotatable mounting with remote direction control gets the best out of television, CB or FM radio aerials, or can be used to mount security cameras. Known as the type 200 XL, it is available from Semiconductor Supplies, Sutton, Surrey, by mail order for only £49.45 inclusive.

Television security cameras or other equipment weighing up to 45Kg (100lb) can be mounted and rotated by mains power over 365 degrees. Speed of movement is one revolution per 65 seconds. The weatherproof case is made of metal castings.

Dimensions: Rotator - 290 x 120 x 150 mm (h x w x d). Control box - 80 x 197 x 160 mm.

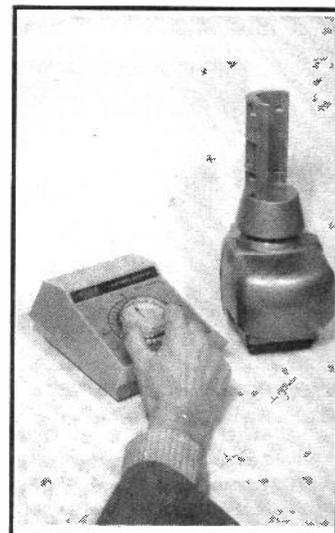Semiconductor Supplies International Ltd, Sutton, Surrey. Tel: 01-643 1126



PUSH-ON/TAB CONTACTS AND HOUSINGS

Now available from BICC-Vero Electronics is its Finclik range of push-on/tab contacts and housing for applications in the domestic appliance and automotive industries and for use by business, gaming and vending machine manufacturers.

The Finclik system consists of reeled 6.3mm receptacle and tab contacts and a range of nylon male and female housings. The contacts are machine applied to wires and then inserted into the housings from the rear. An integral spring lance latches behind a shoulder in the housing and prevents 'backing out'.

PRODUCT NEWS

The contacts are available in brass, tin plated brass and phosphor bronze as required. Wire sizes accommodated by the receptacle are 0.5 to 2.5sq mm and 3 to 6sq mm. Wire ranges covered by the tab are 0.75 to 2.5sq mm and 3 to 6sq mm.


The male and female housings are in nylon 6/6 and have a melting/distortion temperature level of 105°C. They are available in single, 2, 3, 4, 6

and 8 way versions for free hanging applications.

The 6 and 8 way sizes are also available in board mounting versions.

The entire system is readily available ex-stock and has been enthusiastically received in the market place.

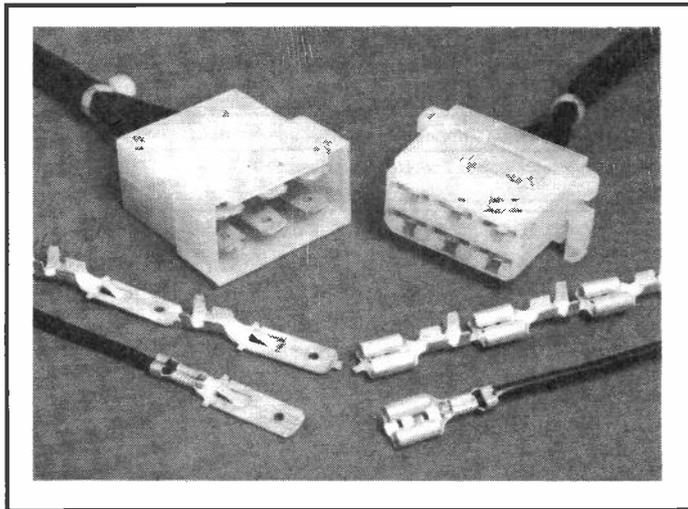*BICC-Vero Electronics Ltd,
Hedge End Industrial Estate,
Flanders Road, Hedge End,
Southampton SO3 3LG*



BIB COMPACT DISC CLEANER

Bib announce the introduction of their first accessory product for the Compact Disc, which is a cleaning kit, comprising a bottle of special formula cleaning liquid, applicator cloths and a special purpose high quality chamois leather polisher. All these items are packed in a convenient storage wallet for dust free protection.


Bib recommend regular use of this product, as essential to maintain high quality production of C-D discs. It is necessary to keep the surface of Compact Discs free from

finger prints, dust and dirt and other contaminants, as these prevent the laser optical system operating correctly, resulting in distortion and poor performance.

Bib also state that the same kit is suitable for cleaning video laser discs.

Attractively packaged in fully descriptive blister card, this kit has a recommended retail price of only £2.99 including VAT.

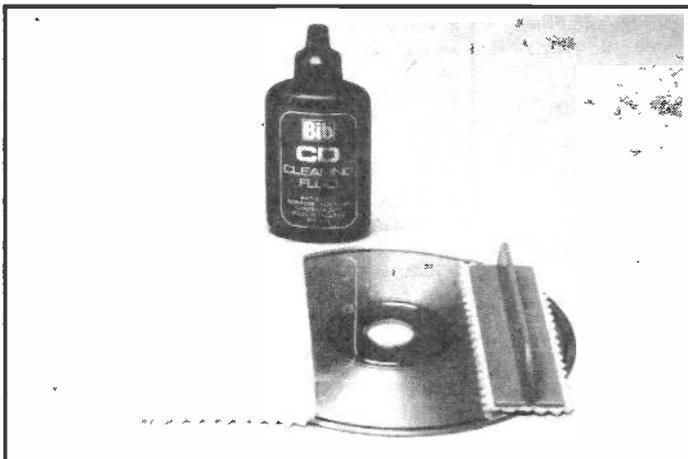Bib Audio/Video Products Limited, Kelsey House, Wood Lane End, Hemel Hempstead, Herts HP2 4RQ. Tel: (0442) 61291



PORTABLE 1 GHZ FREQUENCY COUNTER

Fieldtech Heathrow announces the arrival of a new 1 GHz frequency counter designated the Sencore FC71. The FC71 meets the demands for portable frequency counting applications for avionics, broadcast, two-way communications, and general servicing.

The FC71 is the first, portable, 1 GHz frequency counter to provide consistent longterm accuracy measurements for more than 9 hours on one battery charging. The FC71 uses a unique method to hold 0.5 part-per-million accuracy (0-40 degrees C) all the way to 1 GHz.

The instrument allows accurate measurements wherever needed: e.g. Broadcast towers; 2 way radio repeater stations; aircraft for testing of nav/comm equipment. It's the first portable counter that's really practical because it provides the technician or engineer with a full day's testing on one battery charge.


The FC71 provides extra tests not found on other

counters. Its single-input Frequency-Ratio calculator tests frequency multiplier and divider stages. Sencore's exclusive Crystal Check function tests any crystal for fundamental frequency operation.

The FC71 can be used as a 'talker' for any IEEE 488 Bus system, allowing its frequency measurements to be sent to a computer. The FC71 sends its full 8-1/2 digit frequency readings down the bus, along with the correct range labels: Hz, KHz, MHz, or multiply or divide symbols for the ratio function. All FC71s come equipped with a special connector on the back that mates with the Sencore IB72 IEEE Interface Bus Adapter. The IB72 contains all the circuits necessary to interface the FC71 with the IEEE 488 bus circuits.

The FC71 sells for only £640.

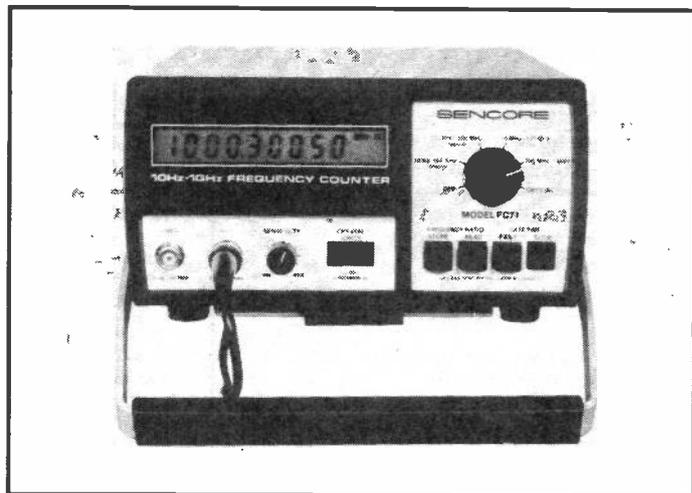*Fieldtech Heathrow Limited
Huntavia House
420 Bath Road
Longford
Middlesex
UB7 0LL
Tel: 01 897 6446.*



REGULATORS FROM GOTHIC CRELLON

The MC78T00 series from Motorola is a new family of three terminal, 3.0A positive voltage regulators available in a range of output voltages from 5V to 24V. Gothic Crellon are now able to supply the range ex-stock.

Besides being offered in a wide variety of voltage options, these devices offer improved performance characteristics over existing regulators with superior load and line regulation, output

voltage tolerance and ripple rejection specifications.

Additionally, these devices are specified for thermal regulation which is an indication of the careful thermal layout of the IC and the integrity of the die bond to the package heat sink.

These monolithic devices employ internal current limiting, thermal shutdown and safe-area compensation. The series is offered in both metal and plastic packages and in two operating temperature ranges.

R WITHERS COMMUNICATIONS

584 HAGLEY ROAD WEST, OLDBURY, WARLEY
B68 0BS (QUINTON, BIRMINGHAM)

Tel: 021-421 8201/2 (24 HR ANSWERPHONE)



RWC SPECIAL OFFERS



INSTANT FINANCE AVAILABLE TO ALL LICENCED AMATEURS SUBJECT TO STATUS. VIA LOMBARD TRICITY + N-WALES TRUST

NEW TRANSCEIVERS & RECEIVERS - BEST BUYS P & P


Kenpro handheld 140-150 MHz 2 watts H/Power out includes Nicad pack & charger £159.95 £2.00
ALL AVAILABLE KENPRO ACCESSORIES IN STOCK

Hamaster FM 2025-25w 2mtr mobile	£179.00	£4.00
FDK Palm II-Ex Demo 6CH 2mtr H/H	£119.00	£2.50
FDK Palm II-Ex Demo 6CH 70cm H/H	£119.00	£2.50
Blazetone FM200-15w 2mtr PRT Shift	£129.00	£3.00
Century 210-AM-FM-SSB Digital		
PLL SW Receiver 0-30mhz	£199.00	£5.00
Kenwood/Trio TR3500 UHF/H/H	£199.00	£2.50
Kenwood/Trio TR 7950 45W Mobile	£319.00	£5.00

SPECIAL

10 METRE FM

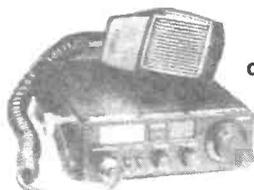UNMODIFIED £33.00
with RPT shift £58.00
All parts available separately HURRY
ONLY 30 left! Some seconds available, please phone



£47.50 COMPLETE

TRIED 10-FM?

Complete mod kit for LCL 2740 DNT M40 inc 2 x XTALS, 2 x c's XTAL filter full instructions @ £12.95 inc post.

ACCESSORIES

PART OF OUR EXTENSIVE RANGE ON OFFER

P & P

500mhz 7 Digit Mini Frequency Counter	£59.98	£2.00
40mhz 7 Digit version of above	£39.98	£2.00
Spring Silly Price Rotator Offer 50KG - Kopek Straight Through Rotator	£38.95	£2.00
Oskerblock SWR 200 maximum power 2kw. Normal price £59.95 -3.5-144MHz only	£39.95	£2.50

Phone for special 70cm packages

FT708R

1W/200mw FM portable

£189

FT-790R 1W/200mw multimode

All the features of the FT-290R on 70 cms Incredible value at

70cms

£259



10 memories
Keyboard entry
A must at only

JOIN THE INTEREST ON 70!

STOP PRESS

Come and see the FT736 - fantastic!



FT730 70cm 10W FM mobile

£239

FULL YAESU RANGE ALWAYS IN STOCK + MATCHING ACCESSORIES

ANTENNAS - REMEMBER IT'S THE ANTENNA THAT MAKES THE STATION!

Sun KG-144 Triple 5/8 Base	£29.95	£3.00	EXCELLENT RANGE OF 70cm MOBILE + ANTS IN STOCK
Hoxin 8/8 Mobile 88	SPECIAL £16.50	£2.00	+ All Tonna & Jaybeam in stock
Sun Double 5/8 KG5 Mobile	SPECIAL £11.50	£2.00	FREE
Hoxin DC Grounded	SPECIAL £10.50	£2.00	Advice on your Antenna requirements
			2mtr HB9CV £6.99 £2.00
			70cm HB9CV £5.99 £2.00
			10mtr HB9CV £29.50 £3.50

NEW

BRAND NEW CCTV CAMERA

Made in USA



General Electric

- * Ideal Amateur TV/Slow Scan
 - * 240v AC 50hz 625 Line
 - * BNC Video Output
 - * Top Quality Professional Unit
 - * Choice of Lens
 - * 12 months Warranty
 - * Ideal Internal Security (without Lens)
- ONLY £79.00 P&P £3.00**
(Normal Retail over £200.00)
Choice of Lens from £20.00 Limited Quantity Available

NEW

MAIN DISTRIBUTOR FOR GW MORSE KEYS

- * Solid Brass (Polished) 'made in GW LAND'
- * Hand Made
- * Solid Slate Base
- * Personal Call Sign Plate Available.



ONLY £34.50 Plus £2.50 PP

SAE Details Dealers wanted

REVCO RS2000 MKI & II GEMSCAN 70

The Scanner you can BUY



Why Wait? Listen NOW!

RWC EXCLUSIVE

- * 70 Memories
- * AM-FM (Narrow Band)
- * 60-179mhz Continuous (depending on Model) + 380-520mhz
- * Modifiable 60-520mhz continuous (Out Soon)
- * Large Clear Red LED Readout
- * Push Button Keyboard (No plastic Film)
- * Various Models at Prices to suit your Pocket

From **ONLY £259.00*** P&P £3.00

- (* Depending on coverage Required)
- * GAS-FET Front End Model Available
- * 12v DC + Mains PSU Built in
- * Plus many many more facilities

RWC HAVE THE TECHNOLOGY!!

NOW, listen to all sorts of interesting activities!

THE NEW PORTABLE ANTENNA THEY ARE ALL TALKING ABOUT!



Due to increased production - 2Meter Travelling Jim
Now Only £7.95

£1.00 Post & Packing.

We are confident you will be happy with your Travelling Jim, if you are not you can return the Antenna (Within 7 days) for full refund.

NEW
kit available @ **£4.75** +75p P+P



Overseas customers welcome. We speak German & Japanese. Import/Export no problem. Please telephone during working hours or

Telex 334303 TXAGWM-G

Don't Forget We stock almost all Power Transistors/Modules for amateur radios which we import ourselves proving we mean business when it comes to service back-up! — Phone us for your requirements. Part exchange welcome. Please send a SAE for any information you require and our latest s/h list. Full demonstration facilities. Please visit our shop, Junction 3, M5, 2 mins along the A456 towards Birmingham. We promise your visit will be worthwhile

PRODUCT NEWS

MULLARD POWERMOS

Gothic Crellon are now stocking a range of Mullard POWERMOS devices (BUZ Series) in both plastic and metal international standard packages offering high current and voltage stability.

Typically POWERMOS offers a combination of fast switching times and high cut-off frequencies. Maximum drain source voltages vary across the range of devices from 50V to 500V and max-

imum continuous drain current is between 2.5A and 32A. Maximum continuous power dissipation is 75W for the plastic packages (TO-220) and ranges from 78W to 125W in the metal range (TO-3).

The POWERMOS range has been designed for easy connection in parallel to increase performance if required.

*Gothic Crellon Ltd, 380 Bath Road, Slough, Berks.
Tel: 06286 4300.*

'SLOPEFRONT' LCD MULTIMETER

A new low-cost LCD Multimeter now available from Lascar Electronics is of totally British design. A unique feature is the angled display which makes the instrument extremely easy to use, whether hand held or laid flat on a bench. The elegantly styled case is moulded in ABS, making the DP2020 equally suitable for laboratory or rugged field use.


Six full functions are available - dc volts, ac volts, dc amps, ac amps, resistance and diode check - a total of 21 measurement ranges.

Complete protection against accidental overload is built into the meter.

A large LCD readout gives clear unambiguous readings and allows over 2,000 hours use from a standard PP3 battery.

The DP2020 is available from stock at a price of £24.95 + VAT. Substantial discounts are available to organisations with large numbers of service technicians.

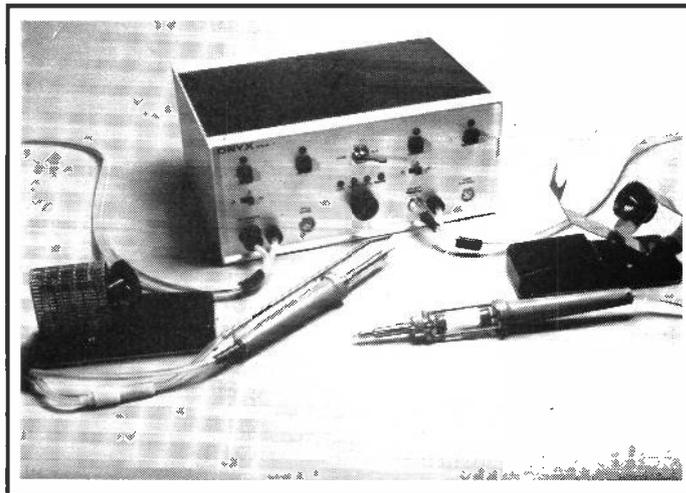*Lascar Electronics Limited, Module House, Whiteparish, Salisbury, Wiltshire SP5 2SJ.
Tel: Whiteparish (07948) 567.
Telex 477876.*



REWORK STATION FROM GREENWOOD ELECTRONICS

Greenwood Electronics has introduced a new, totally self-contained rework station, the Oryx HSR1, which requires neither external air, nor vacuum, supply lines.

Designed to be simple to operate, the HSR1 offers advanced features including soldering/desoldering temperature selection for different PCB materials, independent ON/OFF and earthing control of the soldering and desoldering irons and fume extraction during soldering. A unique desoldering iron facilitates quick and accurate desoldering and avoids the potential damage to the pcb tracks and adjacent components that can occur with conventional desoldering equipment.

The HSR1 consists of five major units: the TC84 temperature controlled soldering iron, the unique SR84 vacuum solder removing iron, the main control unit and two demountable magnetic base safety stands for the irons.

The TC84 is fitted with a fume extractor. This vacuum line from the main unit can be switched from the TC84 to the SR84 as required. A comprehensive range of long life, iron plated tips is available for the TC84 and interchanging tips is a simple operation.

The SR84 desoldering iron is, like the rework station itself, a new development. It features a hollow tip which allows the operator extremely precise control over the desoldering operation and facilitates very clean, neat reworking. It has been designed to overcome the problems associated with conventional desoldering

equipment - such as burning, damage to the PCB tracks and to adjacent components.

The temperature of the tip can be set to its optimum for the type of board being reworked, a four position switch control being provided on the main unit which gives settings for paper and fibre-based PCBs. The unique Oryx design of filters and interchangeable tips makes the SR84 both easy to use and easy to maintain.

The main unit contains the temperature selector for the irons, independent ON/OFF and earthing switches for each iron, the vacuum pump and switched front panel mounted DIN sockets for foot control of the vacuum line and 'power out' (12Vdc) for powering a hand held type P1 PCB drill - available as an optional extra.


A feature of the main unit is the independent electrical control over the two iron circuits. This allows the HSR1 to be used for soldering only, desoldering only, or both operations sequentially. Also, the vacuum line is only fed to one iron at a time, a switch on the front panel controlling its routing.

Considerable attention has been paid to safety and the HSR1 is designed to meet all the relevant UK and European safety requirements.

Power requirements of the HSR1 are 240Vac, 140 watts maximum.

Dimensions are: 305mm (w) x 228mm (d) x 136mm (h). Total weight is 8.5Kg. Price: £495 (ex VAT).

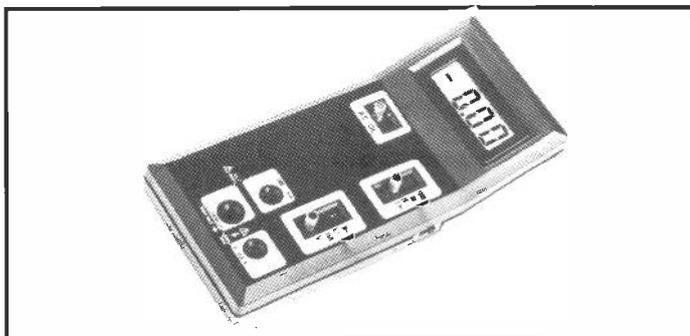Greenwood Electronics, Portman Road, Reading, Berks. RG3 1NE. Reading (0734) 595844.



DIGITAL HUMIDITY & TEMPERATURE METER

The model RHT 200 is a lightweight hand held instrument designed for fast and easy determination of relative humidity and temperature. The instrument covers the ranges 10% to 95% RH and -10° to +60°C, to a resolution of 0.1% and 0.1° respectively. Readout is by large liquid crystal display (LCD).

The capacitive RH sensor consists of a non-conductive foil which is covered on each side with a layer of gold. Temperature sensing is by semiconductor. Both sensors are mounted in a tubular hand held probe which is connected to the instrument by one metre of flexible self-coiling cable.

Powered by one small 9 volt battery (PP3 or equivalent) the RHT 200 is completely portable and controls are limited to an ON/OFF slide switch and another to select RH/TEMP mode.

To complete the package a good quality carrying case is provided which has compartments for the unit and probe. A mains charger unit with rechargeable cell is available if required.

The weight of the instrument and probe is only 300 grammes and the overall dimensions of the unit and carrying case are 260 x 145 x 45mm.

Channel Electronics (Sussex) Ltd, PO Box 58, Seaford BN25 3TB. Telephone: 0323 894961.



ENFIELD ELECTRONICS

208 Baker Street, Enfield,
Middlesex. EN1 3JY. Tel. 01-366 1873



TRANSISTORS				TTL			
AC125 30p	BC183C 12p	BF198 14p	TIP29C 45p	2N1304 80p	7417 28p	7447 75p	7486 35p
AC126 30p	BC183L 12p	BF199 14p	TIP30A 40p	2N1305 80p	7420 28p	7448 55p	7489 140p
AC127 30p	BC183LB 12p	BF200 35p	TIP30B 50p	2N1307 70p	7422 28p	7450 21p	7490 37p
AC128 30p	BC184 12p	BF224B 20p	TIP30C 45p	2N1308 80p	7425 28p	7451 20p	7491 45p
AC132 30p	BC184B 12p	BF258 35p	TIP31 40p	2N1613 35p	7426 28p	7452 21p	7492 40p
AC141 30p	BC184L 12p	BF259 35p	TIP31A 40p	2N2222A 30p	7427 30p	7454 21p	7493 41p
AC142 30p	BC186 12p	BF259 35p	TIP31B 40p	2N2369A 28p	7403 18p	7428 30p	7494 21p
AD162 45p	BC212A 14p	BF595 35p	TIP32A 40p	2N2646 68p	7404 18p	7430 26p	7495 25p
BC107 30p	BC212B 14p	BF595 35p	TIP32C 40p	2N2904A/5A 30p	7406 32p	7432 26p	7497 60p
BC108 30p	BC213 12p	BF595 35p	TIP32E 40p	2N2906A 60p	7407 32p	7433 35p	7497 60p
BC109 12p	BC214 12p	BF595 35p	TIP32F 40p	2N2907A 30p	7408 25p	7437 30p	7498 41p
BC109B 14p	BC214B 14p	BF595 35p	TIP32G 40p	2N2926G 12p	7408 25p	7438 30p	7475 40p
BC109C 14p	BC214L 14p	BF595 35p	TIP32H 40p	2N2926R 12p	7409 25p	7440 23p	7476 35p
BC109D 14p	BC214M 14p	BF595 35p	TIP32I 40p	2N2926T 12p	7410 18p	7441 51p	7476 35p
BC109E 14p	BC214N 14p	BF595 35p	TIP32J 40p	2N2926V 12p	7411 25p	7442 40p	7477 35p
BC109F 14p	BC214P 14p	BF595 35p	TIP32K 40p	2N2926W 12p	7412 25p	7443 71p	7478 35p
BC109G 14p	BC214Q 14p	BF595 35p	TIP32L 40p	2N2926X 12p	7413 25p	7444 58p	7479 35p
BC109H 14p	BC214R 14p	BF595 35p	TIP32M 40p	2N2926Y 12p	7414 37p	7445 71p	7480 81p
BC109I 14p	BC214S 14p	BF595 35p	TIP32N 40p	2N2926Z 12p	7416 28p	7446 71p	7485 75p
BC109J 14p	BC214T 14p	BF595 35p	TIP32O 40p	2N2926AA 150p			
BC109K 14p	BC214U 14p	BF595 35p	TIP32P 40p	2N2926AB 150p			
BC109L 14p	BC214V 14p	BF595 35p	TIP32Q 40p	2N2926AC 150p			
BC109M 14p	BC214W 14p	BF595 35p	TIP32R 40p	2N2926AD 150p			
BC109N 14p	BC214X 14p	BF595 35p	TIP32S 40p	2N2926AE 150p			
BC109O 14p	BC214Y 14p	BF595 35p	TIP32T 40p	2N2926AF 150p			
BC109P 14p	BC214Z 14p	BF595 35p	TIP32U 40p	2N2926AG 150p			
BC109Q 14p	BC214AA 14p	BF595 35p	TIP32V 40p	2N2926AH 150p			
BC109R 14p	BC214AB 14p	BF595 35p	TIP32W 40p	2N2926AJ 150p			
BC109S 14p	BC214AC 14p	BF595 35p	TIP32X 40p	2N2926AK 150p			
BC109T 14p	BC214AD 14p	BF595 35p	TIP32Y 40p	2N2926AL 150p			
BC109U 14p	BC214AE 14p	BF595 35p	TIP32Z 40p	2N2926AM 150p			
BC109V 14p	BC214AF 14p	BF595 35p	TIP32AA 40p	2N2926AN 150p			
BC109W 14p	BC214AG 14p	BF595 35p	TIP32AB 40p	2N2926AO 150p			
BC109X 14p	BC214AH 14p	BF595 35p	TIP32AC 40p	2N2926AP 150p			
BC109Y 14p	BC214AJ 14p	BF595 35p	TIP32AD 40p	2N2926AQ 150p			
BC109Z 14p	BC214AK 14p	BF595 35p	TIP32AE 40p	2N2926AR 150p			
BC110A 14p	BC214AL 14p	BF595 35p	TIP32AF 40p	2N2926AS 150p			
BC110B 14p	BC214AM 14p	BF595 35p	TIP32AG 40p	2N2926AT 150p			
BC110C 14p	BC214AN 14p	BF595 35p	TIP32AH 40p	2N2926AU 150p			
BC110D 14p	BC214AO 14p	BF595 35p	TIP32AI 40p	2N2926AV 150p			
BC110E 14p	BC214AP 14p	BF595 35p	TIP32AJ 40p	2N2926AW 150p			
BC110F 14p	BC214AQ 14p	BF595 35p	TIP32AK 40p	2N2926AX 150p			
BC110G 14p	BC214AR 14p	BF595 35p	TIP32AL 40p	2N2926AY 150p			
BC110H 14p	BC214AS 14p	BF595 35p	TIP32AM 40p	2N2926AZ 150p			
BC110I 14p	BC214AT 14p	BF595 35p	TIP32AN 40p	2N2926BA 150p			
BC110J 14p	BC214AU 14p	BF595 35p	TIP32AO 40p	2N2926BB 150p			
BC110K 14p	BC214AV 14p	BF595 35p	TIP32AP 40p	2N2926BC 150p			
BC110L 14p	BC214AW 14p	BF595 35p	TIP32AQ 40p	2N2926BD 150p			
BC110M 14p	BC214AX 14p	BF595 35p	TIP32AR 40p	2N2926BE 150p			
BC110N 14p	BC214AY 14p	BF595 35p	TIP32AS 40p	2N2926BF 150p			
BC110O 14p	BC214AZ 14p	BF595 35p	TIP32AT 40p	2N2926BG 150p			
BC110P 14p	BC214BA 14p	BF595 35p	TIP32AU 40p	2N2926BH 150p			
BC110Q 14p	BC214BB 14p	BF595 35p	TIP32AV 40p	2N2926BI 150p			
BC110R 14p	BC214BC 14p	BF595 35p	TIP32AW 40p	2N2926BJ 150p			
BC110S 14p	BC214BD 14p	BF595 35p	TIP32AX 40p	2N2926BK 150p			
BC110T 14p	BC214BE 14p	BF595 35p	TIP32AY 40p	2N2926BL 150p			
BC110U 14p	BC214BF 14p	BF595 35p	TIP32AZ 40p	2N2926BM 150p			
BC110V 14p	BC214BG 14p	BF595 35p	TIP32BA 40p	2N2926BN 150p			
BC110W 14p	BC214BH 14p	BF595 35p	TIP32BB 40p	2N2926BO 150p			
BC110X 14p	BC214BI 14p	BF595 35p	TIP32BC 40p	2N2926BP 150p			
BC110Y 14p	BC214BJ 14p	BF595 35p	TIP32BD 40p	2N2926BQ 150p			
BC110Z 14p	BC214BK 14p	BF595 35p	TIP32BE 40p	2N2926BR 150p			
BC111A 14p	BC214BL 14p	BF595 35p	TIP32BF 40p	2N2926BS 150p			
BC111B 14p	BC214BM 14p	BF595 35p	TIP32BG 40p	2N2926BT 150p			
BC111C 14p	BC214BN 14p	BF595 35p	TIP32BH 40p	2N2926BU 150p			
BC111D 14p	BC214BO 14p	BF595 35p	TIP32BI 40p	2N2926BV 150p			
BC111E 14p	BC214BP 14p	BF595 35p	TIP32BJ 40p	2N2926BW 150p			
BC111F 14p	BC214BQ 14p	BF595 35p	TIP32BK 40p	2N2926BX 150p			
BC111G 14p	BC214BR 14p	BF595 35p	TIP32BL 40p	2N2926BY 150p			
BC111H 14p	BC214BS 14p	BF595 35p	TIP32BM 40p	2N2926BZ 150p			
BC111I 14p	BC214BT 14p	BF595 35p	TIP32BN 40p	2N2926C0 150p			
BC111J 14p	BC214BU 14p	BF595 35p	TIP32BO 40p	2N2926C1 150p			
BC111K 14p	BC214BV 14p	BF595 35p	TIP32BP 40p	2N2926C2 150p			
BC111L 14p	BC214BW 14p	BF595 35p	TIP32BQ 40p	2N2926C3 150p			
BC111M 14p	BC214BX 14p	BF595 35p	TIP32BR 40p	2N2926C4 150p			
BC111N 14p	BC214BY 14p	BF595 35p	TIP32BS 40p	2N2926C5 150p			
BC111O 14p	BC214BZ 14p	BF595 35p	TIP32BT 40p	2N2926C6 150p			
BC111P 14p	BC214CA 14p	BF595 35p	TIP32BU 40p	2N2926C7 150p			
BC111Q 14p	BC214CB 14p	BF595 35p	TIP32BV 40p	2N2926C8 150p			
BC111R 14p	BC214CC 14p	BF595 35p	TIP32BW 40p	2N2926C9 150p			
BC111S 14p	BC214CD 14p	BF595 35p	TIP32BX 40p	2N2926CA 150p			
BC111T 14p	BC214CE 14p	BF595 35p	TIP32BY 40p	2N2926CB 150p			
BC111U 14p	BC214CF 14p	BF595 35p	TIP32C0 40p	2N2926CC 150p			
BC111V 14p	BC214CG 14p	BF595 35p	TIP32C1 40p	2N2926CD 150p			
BC111W 14p	BC214CH 14p	BF595 35p	TIP32C2 40p	2N2926CE 150p			
BC111X 14p	BC214CI 14p	BF595 35p	TIP32C3 40p	2N2926CF 150p			
BC111Y 14p	BC214CJ 14p	BF595 35p	TIP32C4 40p	2N2926CG 150p			
BC111Z 14p	BC214CK 14p	BF595 35p	TIP32C5 40p	2N2926CH 150p			
BC112A 14p	BC214CL 14p	BF595 35p	TIP32C6 40p	2N2926CI 150p			
BC112B 14p	BC214CM 14p	BF595 35p	TIP32C7 40p	2N2926CJ 150p			
BC112C 14p	BC214CN 14p	BF595 35p	TIP32C8 40p	2N2926CK 150p			
BC112D 14p	BC214CO 14p	BF595 35p	TIP32C9 40p	2N2926CL 150p			
BC112E 14p	BC214CP 14p	BF595 35p	TIP32CA 40p	2N2926CM 150p			
BC112F 14p	BC214CQ 14p	BF595 35p	TIP32CB 40p	2N2926CN 150p			
BC112G 14p	BC214CR 14p	BF595 35p	TIP32CC 40p	2N2926CO 150p			
BC112H 14p	BC214CS 14p	BF595 35p	TIP32CD 40p	2N2926CP 150p			
BC112I 14p	BC214CT 14p	BF595 35p	TIP32CE 40p	2N2926CQ 150p			
BC112J 14p	BC214CU 14p	BF595 35p	TIP32CF 40p	2N2926CR 150p			
BC112K 14p	BC214CV 14p	BF595 35p	TIP32CG 40p	2N2926CS 150p			
BC112L 14p	BC214CW 14p	BF595 35p	TIP32CH 40p	2N2926CT 150p			
BC112M 14p	BC214CX 14p	BF595 35p	TIP32CI 40p	2N2926CU 150p			
BC112N 14p	BC214CY 14p	BF595 35p	TIP32CJ 40p	2N2926CV 150p			
BC112O 14p	BC214CZ 14p	BF595 35p	TIP32CK 40p	2N2926CW 150p			
BC112P 14p	BC214DA 14p	BF595 35p	TIP32CL 40p	2N2926CX 150p			
BC112Q 14p	BC214DB 14p	BF595 35p	TIP32CM 40p	2N2926CY 150p			
BC112R 14p	BC214DC 14p	BF595 35p	TIP32CN 40p	2N2926CZ 150p			
BC112S 14p	BC214DD 14p	BF595 35p	TIP32CO 40p	2N2926D0 150p			
BC112T 14p	BC214DE 14p	BF595 35p	TIP32CP 40p	2N2926D1 150p			
BC112U 14p	BC214DF 14p	BF595 35p	TIP32CQ 40p	2N2926D2 150p			
BC112V 14p	BC214DG 14p	BF595 35p	TIP32CR 40p	2N2926D3 150p			
BC112W 14p	BC214DH 14p	BF595 35p	TIP32CS 40p	2N2926D4 150p			
BC112X 14p	BC214DI 14p	BF595 35p	TIP32CT 40p	2N2926D5 150p			
BC112Y 14p	BC214DJ 14p	BF595 35p	TIP32CU 40p	2N2926D6 150p			
BC112Z 14p	BC214DK 14p	BF595 35p	TIP32CV 40p	2N2926D7 150p			
BC113A 14p	BC214DL 14p	BF595 35p	TIP32CW 40p	2N2926D8 150p			
BC113B 14p	BC214DM 14p	BF595 35p	TIP32CX 40p	2N2926D9 150p			
BC113C 14p	BC214DN 14p	BF595 35p	TIP32CY 40p	2N2926DA 150p			
BC113D 14p	BC214DO 14p	BF595 35p	TIP32CZ 40p	2N2926DB 150p			
BC113E 14p	BC214DP 14						

NEWS DESK

Cellular radio prices

British Telecom Radiophone today announced the details of its prices for the new Cellnet cellular radio service which is scheduled to start operating early in 1985.

The new car radiophone, to be called the Telecom Topaz, will cost £1350. Installation will cost around £100 depending on the make of car. The phone will be manufactured by NEC in Japan.

Telecom Topaz features a 16-memory store, a ten-digit display of the number dialled, hands-free operation, electronic security lock and last number recall.

In addition, British Telecom Radiophone also announced its intention to place orders with Motorola and Mobira for cellular radiophones, for use in the car and as hand-held portables.

The new products from Motorola and Mobira are expected to cost between £1350 and £2000 for car radiophones, and between £2000 and £2500 for the hand portables. All prices exclude VAT.

As a special service to existing radiophone customers, British Telecom Radiophone will be offering a trade-in deal for people switching over to Cellnet.

From April 1 next year, customers who own either of British Telecom's automatic car radiophones, Sapphire and Emerald, will be able to switch to Telecom Topaz for only £850 - a discount of £500 - provided they have been using the service for at least one year.

Sales of Cellnet equipment will be handled by British Telecom Radiophone's retail division which has a nationwide network of dealers selling the existing range of British Telecom radiophones.

The opening of the Cellnet service will mean the introduction of a new range of products, the first of which is Telecom Topaz.

Telecom Topaz charges (excluding VAT) start at £1350 for the equipment (approx £92 per quarter for a five-year lease). Connection to the Cellnet system costs an initial



£60 plus a quarterly subscription of £75. Call charges range between 8p and 25p per minute according to the timing of the call.

Sales enquiries for British Telecom Radiophone products should be made to Al Tingey on 01-730 1570. The Marketing Manager is David Pugh on 01-730 1412.

British Amateur Television Club

Amateur TV enthusiasts in Central Scotland who would be willing to participate in financial support or construction of a 24cm ATV Repeater for the area are asked to contact Norrie, GM4BVU, 3 Townhill Road, Earnock, Hamilton, ML3 9UX.



Prestel for Australia

Prestel, British Telecom's world-beating viewdata system based on GEC computers, has recorded another major international success by winning the prestige Australian public service contract.

The all-British system has been chosen by Telecom Australia for its new Viatel service which will start early next year.

The contract for GEC computers and Prestel software was won against stiff international competition. It is worth £2 million initially with more to follow as Viatel develops and expands.

More than 1,000 Prestel-type terminals are already operating on private Australian networks and local firms will be able to supply terminals, TV-set adaptors and personal computers to work with Viatel.

The Australian decision means that 10 countries have now purchased national videotex systems from GEC-Prestel - more than all other international competitors combined.

Three GEC 4190 mini-computers will be installed at the Melbourne headquarters Australia's Viatel service which will start public operations in February 1985. Each computer is capable of handling 2,000 simultaneous calls.

Unlike most other countries, Australia has decided to omit the normal public trial stage.

New business opportunities created in mobile radio

The Department of Trade and Industry has published a consultative document on the future of the radio frequencies known as Band I (41-68 MHz) and Band III (174-225 MHz), which will cease to be used for 405-line black and white television services from the end of 1984.

This move will create one of the largest single additions to the spectrum available for mobile radio in Great Britain, and is bound to attract much business interest.

A summary of this document is given on page 58.

RSGB news

Some Raynet members in East Anglia participating in Intex, the national home defence exercise held recently, were actively canvassed by a group who claimed that such participation would be an infringement of national and international radio regulations.

Fortunately the situation was clarified by reference to DTI and participating members were reassured by information issued very rapidly from HQ.

It is probably worth restating that Raynet exists purely to provide a communication resource to the community at large in times of national and local need.

It is open to all radio amateurs and SWLs, whether they be RSGB members or not. It is not a political organisation, nor does it wish to promote any particular political point of view.

Members and groups are free to decide for themselves their level of support for any user service. In particular they are free to decide their

level of support for CEPOs in work related to peace time, disaster, or to home defence training.

The Chinese Radio Sports Association, which represents radio amateurs in the People's Republic of China, has applied for membership of the IARU. CRSA was originally founded in 1964 but it became inactive soon after that date because of the suspension of amateur radio in China until early 1982. Amateur radio in China is still club-based, with no licences for individual stations having yet been granted: there are at present three club stations, BY1PK near CRSA headquarters (box 6106, Beijing), BY4AA at the Shanghai branch (box 205, Shanghai) and BY8AA at the Sichuan branch (box 6106, Beijing).

There are at present 30 authorised operators, and other applicants are being trained at present.

Another application for membership of the IARU has been received from the

Vanuatu Amateur Radio Society, which represents amateurs in the Republic of Vanuatu. The society was founded in May 1980, at which time the country was known as New Hebrides and was jointly administered by France and the United Kingdom. There are 25 amateurs in Vanuatu, of which 18 are members of VARS, and the country's licensing authority is reported to have a very favourable attitude to the hobby.

VARS has a headquarters station with the callsign YJ8DX, and the callsign YJ8ES is used by the Society's branch on Espiritu Santo Island.

The Department of Trade and Industry is at present considering ways of restricting the use of illegal 27MHz CB equipment without adversely affecting the operation of licensed radio amateurs on the 28MHz band.

European Space Agency astronaut Huber Ocolls from the Netherlands may become

the first European amateur in space. He is due to fly on one of the USA space shuttle missions during 1985. Although he is not yet licensed, he intends to obtain his ticket prior to launch. The Dutch National Society, VERON, is apparently to make an official request to NASA for him to use equipment similar to that used by W5LFL.

Packet Radio is another area of rapid growth within amateur radio which is gaining popularity in the UK. Packet data exchanges between two individual amateurs is quite legal. As such, it is just another form of data transmission which is quite permissible under the terms of the UK licence. The initial confusion was because of the third party message facilities associated with packet radio at present being used by many amateurs in North America. Needless to say, as with any other form of data transmission, identification of transmissions should always comply with UK licence regulations.



Bernie - please mention that we're closed on Mondays and open Wednesdays!

HOW TO RECEIVE

For the best prices, always choose A.R.E. Buy mail order, phone order, or personal purchase - we give you the lot, including Brenda's coffee. And we've always got more than our ads can carry! A special welcome to new licensees - let our expert staff help sort out your equipment needs.

ALL PRICES INCL. VAT

HF TRANSCEIVERS		£
0490	YAESU FT757GX	685.00
0130	YAESU FT102	685.00
0100	YAESU FT980	1265.00
0380	YAESU FT77	486.00
2021	ICOM IC745	839.00
2005	ICOM IC751	1099.00
1450	TRIO TS930S	1150.00
1530	TRIO TS430	752.10

VHF TRANSCEIVERS		£
1000	YAESU FT230	259.00
	ICOM IC27E	329.00
5779	FDR750X	319.00
1932	TRIO TM201A	269.00

VHF MULTIMODE TRANSCEIVERS		£
0810	YAESU FT290F	269.00
	YAESU FT480R	395.00
1020	YAESU FT726R	739.00
2396	ICOM IC271E	649.00
	ICOM IC290D	499.90
1980	TRIO TS9130	442.52

2M HANDHELD FM TRANSCEIVERS		£
0700	YAESU FT208R	198.00
0930	YAESU FT203R	149.00
2480	ICOM IC2E	179.00
2475	ICOM IC2E	239.00
1680	TRIO TR2500	237.82

2M/70cm TRANSCEIVERS		£
1020	YAESU FT726R	739.00
1934	TRIO TW4000	469.00

70cm HANDHELD TRANSCEIVERS		£
0710	YAESU FT708R	179.00
1780	TRIO TR3500	256.45
2490	ICOM IC4E	229.00
2476	ICOM IC04E	T.B.A.

70cm MULTIMODE		£
0890	YAESU FT790R	249.00
2440	ICOM IC471	735.00
2450	ICOM IC490E	549.00

HF RECEIVERS		£
2250	ICOM IC7R0	565.00
2249	ICOM IC7R1	649.00
1090	YAESU FRG7700	369.00
1100	YAESU FRG7700M	435.00
1820	TRIO R2000	421.36
1800	TRIO R600	263.12
5573	SONY ICF7600D	179.00

VHF RECEIVERS		£
5650	JIL SX200	299.00
	JIL SX400	598.00
5641	AOR 2001	325.00
	REVCO SCANNER	258.00
5610	BEARCAT 2020	289.00
5780	ATC720 HANDHELD	159.00
5781	RX40 HANDHELD	142.00
	REVCO HANDHELD	248.00
5573	SONY ICF7600D	179.00

ANTENNA TUNERS		£
5320	ICOM AT500	399.00
2310	ICOM AT100	285.00
0510	YAESU FC757	231.50
0140	YAESU FC102	179.00
1555	TRIO AT250	273.01
0420	YAESU FC700	98.90
	AMTEC 300	49.00
1460	TRIO AT930	145.00
5080	WELZ AC38	73.95

RECEIVER ANTENNA TUNERS		£
1170	YAESU FRT7700	46.00
	GLOBAL AT1000	46.00

TELE READERS CW & RTTY/AMTOR		£
5280	TONO 530	299.00
5420	TASCOCORP610E	179.50
	TONO 5000	795.00
5270	TONO 9100	695.00
4780	12 VOUGREEN AMBER	89.00
4900	ICS AMTOR	265.00

POWER SUPPLIES		£
0500	YAESU FP757	149.50
0505	YAESU FP757HD	162.50
0410	YAESU FP700	125.00
2110	ICOM ICPS15	119.00
2392	ICOM ICPS25	89.00
2006	ICOM ICPS35	149.00
5820	BNOS 25 AMP	138.00
5810	BNOS 12 AMP	95.45
5800	BNOS 6 AMP	52.00
4680	ORAE 4 AMP	34.00
4710	ORAE 25 AMP	110.00

LINEAR AMPLIFIERS		£
5741	ALINCO ELH230D	69.00
	ALINCO ELH230G	59.00
5742	ALINCO ELH260D	114.95



INSTANT HP AVAILABLE
WRITTEN DETAILS ON REQUEST



24-HOUR PHONE ORDER SERVICE

**ALL OFFERS SUBJECT TO AVAILABILITY
PRICES CORRECT AT TIME OF GOING TO PRESS**

To use ARE's Rapid Despatch Mail Order Service just quote the Stock Number together with your Access or Visa Card number. Your goods will be on their way within 24 hours, subject to availability.

If the particular item you're looking for is not listed here, call us on 01-992 5767 or 092 52 29881 - Brenda & Bernie pride themselves on being able to supply anything connected with amateur radio.

All orders over £100 are sent carriage free. For 24-hour Securicor delivery, add £6.00. For orders below £100 add £2. or £1 for books. Beam Antennas are sent by Securicor only.




GENERAL COVERAGE RECEIVER KIT FCR 130

This is a complete kit which allows you to build and learn as you go. Suitable for anyone who has an interest in radio and can manage a soldering iron. It really is within the scope of most beginners. You don't have to be a 'semi-professional amateur' to understand how it works as we supply very comprehensive and complete instructions, written in plain language. Well spaced components so its OK for fat fingers! The receiver tunes, in 3 bands from 1 to 30 Mhz. Solid aluminium tuning and control knobs and base panel. Black anodised front panel. Nice to build . . . nice to look at . . . nice to own.

Model FCR 130 Receiver kit **ONLY £75.30 inc VAT. Post & Packing £2.40**

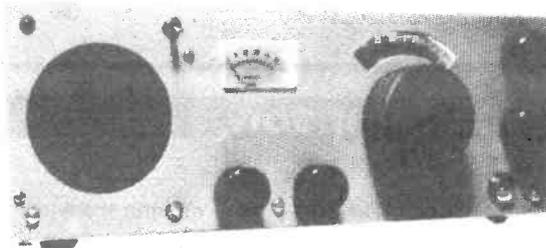- ★ 30:1 Geared analogue tuning
- ★ 3 Band switch with spare position
- ★ Tape record socket
- ★ Headphone socket
- ★ Signal Meter
- ★ Internal speaker + On/Off sw.
- ★ A.F. Gain and Tone Control
- ★ AM, CW, SSB



COMMUTECH (Devon) LTD Chapel Street, Holsworthy, Devon EX22 6AR Tel: (0409) 253504

THE BEST FROM A.R.E.



SX 400

Undoubtedly the finest VHF UHF receiver yet developed. Extremely professional in its design. Fully programmable. scan facility. memory facility.

£598 INC VAT.

SONY ICF 7600D

Sony's latest approach to pocket-size communications receivers. Covering from 153 Kc through to 30 MHz. All mode operation including SSB and FM on broadcast band. Keyboard entry for frequency access. Memory facility. Scan facility. A truly portable communication receiver. AC power supply included.

£179
INC VAT.



ICOM IC-R71

The best communications receiver of professional standards yet to be offered to the amateur fraternity. Tunable from 100 Kc to 30 MHz, all mode with FM option. Memory facility. Optional infra-red remote control unit.

£649 INC VAT.



**OK-Brenda says
we're closed on
Mondays and open
Wednesdays!**



CLOSED—Mondays · OPEN—Wednesdays

FULL DETAILS. TUES, WED, FRI 9.30-5.30 · THURS 9.30-6.00 · SAT 9.30-5.00.



LONDON
373 UXBRIDGE ROAD,
ACTON
LONDON W3 9BH
TEL 01 992 5765 6

NORTHERN
38 BRIDGE STREET
FAIRFAX TOWN, NEWTON WILLOWS
MIDSEYSDALE, WAIP 9BA
TEL 092 5229881

more on your wavelength

High Quality Precision Directional Coupler

by Derrick Simpson

In the course of work on the development of an antenna system the need to be able to measure voltage standing wave ratio at 432MHz and higher frequencies prompted a look at commercially available directional couplers. The cost of these was enormously high, certainly out of reach of the pocket of most radio amateurs.

It was found that the basic concept was very simple and that the high cost is almost entirely due to the high mechanical precision necessary in order that the accuracy, reliability and repeatability could be achieved and maintained over long periods of time.

SWR meter

A directional coupler in some form or other is used in every instrument and is commonly called a SWR meter. It is a device that is capable of separating the forward or incident voltage from the reverse or reflected voltage, which occur in a transmission line, co-axial or parallel carrying radio frequency energy that is not perfectly terminated.

Note: A line that is infinitely long can be considered as perfectly terminated if all the energy fed into it is totally absorbed, dissipated in the loss resistance along its length.

The circuit and the electrical form of the directional coupler is as shown in *Figure 1*, and may be recognised by some. It consists of a central line somewhat larger in diameter than the two smaller lines coupled to it, but maintaining the characteristic impedance of the co-axial line of 50ohm.

The smaller lines are diametrically opposite one another on each side of the main line. These secondary lines also have their characteristic impedance set at 50ohm so that the measuring equipment will also see a matched line. In use we very often find that one end of the secondary lines are in fact terminated

with 50ohm dummy loads. This ensures that there is a standard that is common to all the measurements made, and can always be referred to.

The physical dimensions of the directional coupler are determined by the size of the flange on the 'N' type socket used and the necessity to make the instrument with a 50ohm characteristic impedance. The formula used to calculate the sizes of the lines is given in the appendix.

Standing waves

At this point it may be helpful to consider how standing waves form and how they relate to the measurements made and to what is happening in the transmission line.

The sine wave of the voltage being propagated in a line towards a short circuit, produces an incident wave


moving from left to right (refer to *Figure 2*).

Since there can be no voltage sustained across the short circuit assuming no losses, an equal voltage is reflected and is propagated back down the line with such a phase that the voltage at the short is always zero.

It is also true that the current is a maximum into the short circuit and that the current wave is also reflected in the same way. This is important because it does not matter whether the voltage or current is measured as the result is the same.

Diode voltmeter

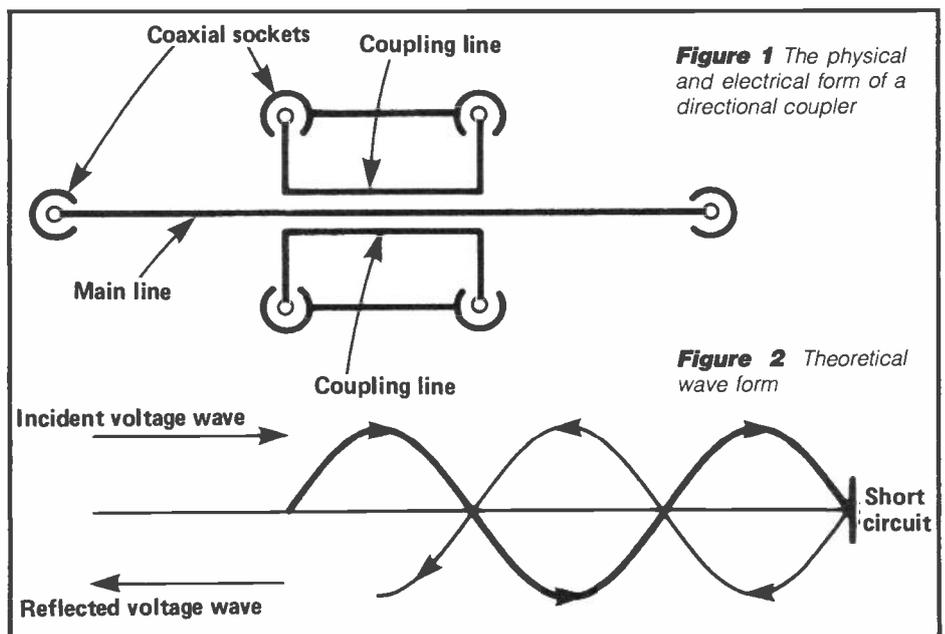The conception of two independent waves existing on the line and travelling in opposite directions at the same time is correct, but it is not sufficient for all problems.



DIRECTIONAL COUPLER

For example, a simple diode voltmeter (see Figure 3) connected across such a line could not separate the two waves but would give a reading that would be dependent upon the magnitude and the relative phase of the two voltages existing on the line at that point.

If the voltmeter was moved then it would be found to give a different reading depending upon its position on the line.

For instance, if both reflected and incident voltages were in phase at the point of measurement, then the meter would show a reading of twice the incident voltage. Conversely, if both voltages were out of phase by 180° , then the meter would show zero voltage.

So it can be seen that a reading can be taken simply by moving the diode voltmeter along the line.

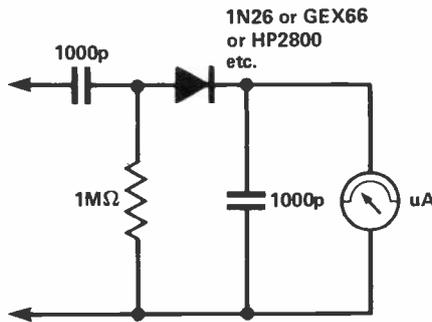


Figure 3 Circuit of a simple diode voltmeter

totally reactive, in so much as reactances dissipate no power. All that can be done is to measure the values of forward and reflected voltages or currents and allow them to be expressed as a ratio.

However, this information can be very valuable because it can be used to determine the load impedance, if the conditions under which the measurement is taken are precisely defined. One of these is that the directional coupler can be connected directly to the antenna terminals without the use of any intervening co-axial cable, so that a measurement can be taken determining the complex impedance of the terminations.

To make further measurements would need a slotted line, but these are necessary if the load is to be totally defined.

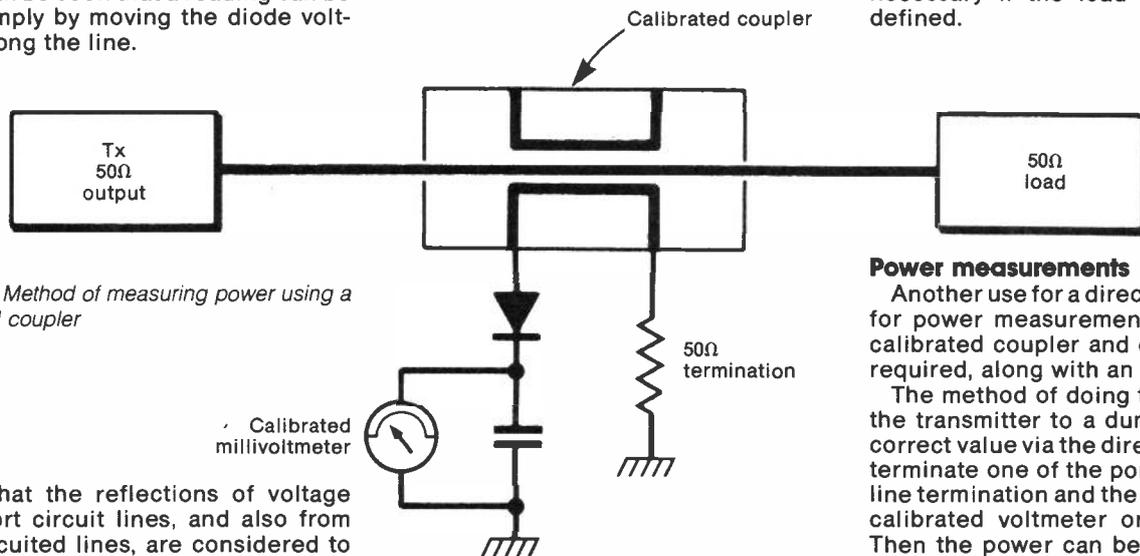


Figure 4 Method of measuring power using a directional coupler

Note that the reflections of voltage from short circuit lines, and also from open circuited lines, are considered to be total reflection modified only by the losses inherent in all transmission lines; the losses having the effect of making the measured voltage reflected lower by the amount of loss in the line.

Care should be taken when measuring the reflected voltage at the transmitter end because the measurement must take into account the loss incurred from transmitter to the load, and add the loss from the load back to our measurement point at the transmitter. In other words, the cable loss reduces the forward voltage and also reduces the reflected voltage. The same also applies to the current.

Between the extremes of open and short circuited lines the terminating impedance may have any values of resistance and reactance. Therefore, if the termination has a resistive component then power will be absorbed in that resistance and the reflected power will decrease in magnitude, the actual value depending upon the amount of power fed into the line and the loss of the line.

Therefore it can be seen that if the load is purely resistive, but is not the correct value to terminate the line fully, there will be a standing wave on the line that is a function of the forward power minus the power absorbed in the load.

This is a measure of how closely the cable impedance and the load impedance match. For a resistive load the

forward and reflected voltages are in phase with one another, but if there is a reactance associated with the load impedance, then the phase angle of the reflected voltage will vary between plus 90° and minus 90° with respect to the forward voltage. The phase angle is therefore dependent upon the magnitude and the sign of the associated reactance.

Unfortunately a directional coupler, like the diode voltmeter, cannot distinguish between loads that are purely resistive and loads which are partially or

Power measurements

Another use for a directional coupler is for power measurement and for this a calibrated coupler and dummy load are required, along with an RF voltmeter.

The method of doing this is to couple the transmitter to a dummy load of the correct value via the directional coupler, terminate one of the ports with a 50ohm line termination and the other end with a calibrated voltmeter or millivoltmeter. Then the power can be found by using Ohm's Law and multiplying the result by the coupler loss factor for that frequency (see Figure 4).

Construction

In order to construct this directional coupler it must be said that a fair amount


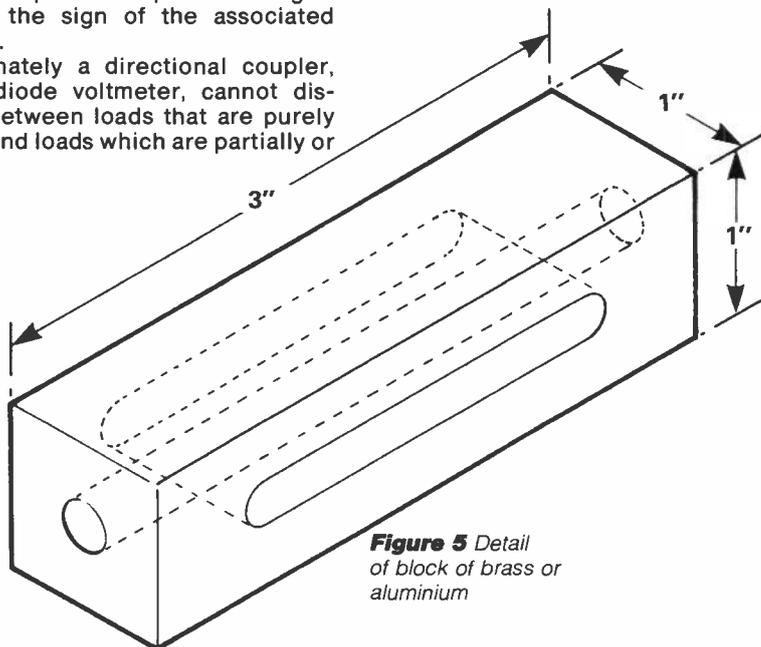


Figure 5 Detail of block of brass or aluminium

WELZ

"MADE TO MEASURE"

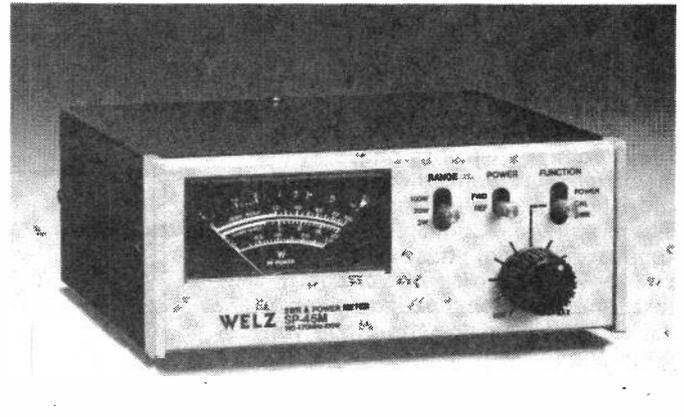USED BY PROFESSIONALS AND AMATEURS THROUGHOUT THE WORLD



SP-15M 1.8~150 MHz
200 W max.

SP-45M 140~470 MHz
100 W max.

Full-Flat Response SWR & Power Meter

- Slim & compact body, usable in mobile, marine, handy & base stations.
- WELZ's exclusive new three-transformer type directional power sensor using ferrite cores.
- Three ranges (2.5/20/200 W) Forward/Reflected Power and SWR measurements.
- Full scale meter indication at 2.5 W power range.
- 1.5 W SWR sensitivity.
- Connectable with matching network AC-35M or AC-38M (as shown in picture).


- WELZ's new exclusive wide range (140~470 MHz) directional power sensor.
- Three ranges (3/20/100 W) Forward/Reflected power and SWR Measurements.
- Full scale meter indication at 3.0 W power range.
- 3W SWR sensitivity.

£41 inc VAT

£59.75 inc VAT

ANTENNA TUNER using SP-15M & AC-35M/AC-38M

SPECIFICATIONS

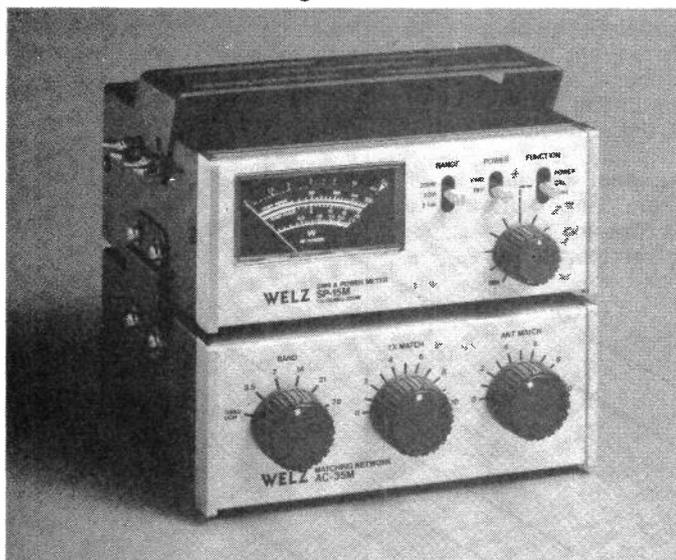

	SP-15M	SP-45M
Frequency Range (MHz)	1.8-150	140-470
Power Measurement (W) CW	0-200	0-100
Accuracy (power measurement) at full scale	±10%	
Power Range (W)	2.5/20/200	3.0/20/100
Measurement Function	Forward/Reflected Power, Calibration & SWR	
Insertion Loss (dB)	0.2	0.5
SWR Measurement	1:1 - 1:∞	
SWR Sensitivity (W)	1.5	3.0
Impedance	50 ohms	
Connectors	SO-239	
Dimensions (mm)	160 (W) X 65 (H) X 145 (D)	
Weight (g)	950	

AC 38 ATU £73.95 Carriage £2 extra per item

Send for details of complete range of Welz products.

WATERS & STANTON ELECTRONICS


Head Office: 18-20 Main Rd, Hockley, Essex. Southend (0702) 206835 & 204965
Branch: 12 North Street, Hornchurch, Essex. (04024) 44765.

DIRECTIONAL COUPLER

of precision engineering and lathe work is necessary, but this is a must if meaningful use is to be made of the information gained by the measurements that can be performed by this device.

Some of the parts must be manufactured to an accuracy of plus or minus

Figure 6 Centre conductor

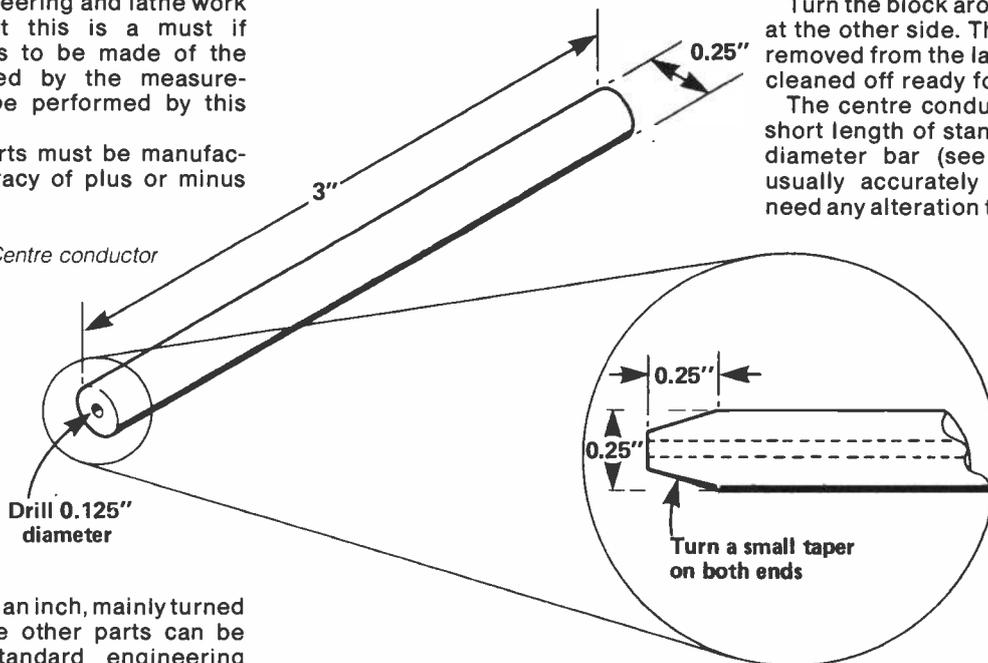

Turn the block around and do the same at the other side. The block can now be removed from the lathe and sharp edges cleaned off ready for the next step.

The centre conductor is made from a short length of standard brass .250 inch diameter bar (see *Figure 6*). This is usually accurately sized and will not need any alteration to its diameter but be

one-thousandth of an inch, mainly turned parts; most of the other parts can be finished to a standard engineering tolerance of plus or minus one-hundredth of an inch.

The body of the coupler is machined from a block of brass (see *Figure 5*) or aluminium 3 inches long and 1 inch square. It is set up on the cross slide using a lathe as a boring machine. A pilot hole .250 inches in diameter is drilled through the block as accurately as possible.

Next, using a long series drill, without removing the block from the lathe cross slide or moving the cross slide in any way (experienced machinists may adjust the cross slide in order to correct an out of true of the pilot hole as it exits the block), fit a boring bar with a cutter set for .265 inches and take a slow cut. Keep taking fine cuts until .565 inches is arrived at.

The final bore diameter must be .575 inches \pm .001 inches if a 50ohm line is to be achieved. When the bore is finished turn the block through 90°.

Make sure that the block is square to the chuck and reclamp to the cross slide ensuring that the height of the block is not altered in any way from the previous operation.

Fit a cutter holder into the headstock and mount slot drill or four flute milling cutter of .227 inches diameter. Carefully mill a slot 1.181 inches long, deep enough so that it cuts through into the bore. This must be done in one cut and with very great care.

If a lathe with a power cross slide is available then this will present little difficulty.

careful not to damage its surface when handling; use soft jaws in the vice and in the lathe chuck when drilling and turning the ends.

Two brass plates 1/8 inch thick, three inches by one inch are drilled as per the drawing and the holes threaded as marked (*Figure 7*). Carefully mark out using a centre punch on hole centres. Use a sharp drill and be careful to avoid snatching if using a press drill.

The body of the coupler should be drilled and tapped to take the fastening screws for the 'N' type sockets. 4 BA screws could be used and the holes opened out in the socket flange to 3/4 inches. The other holes are drilled

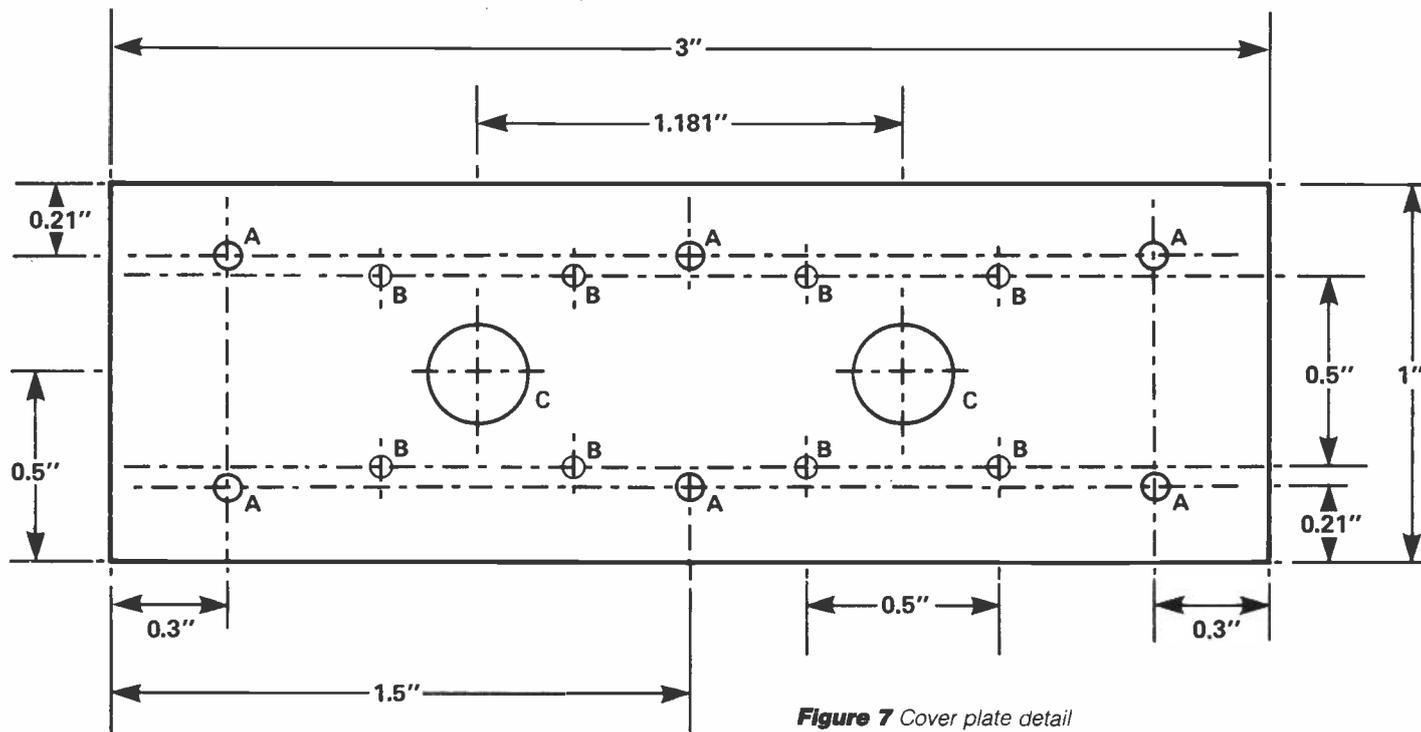


Figure 7 Cover plate detail

DIRECTIONAL COUPLER

$\frac{5}{64}$ inch and tapped to take a 6 BA bolt.

All the sockets are modified by turning off the raised part on the back of the flange. On most 'N' and BNC sockets this will release the pin in the centre. It will be found that there are two teflon washers supporting the pin and the rear one should be discarded. On some types of BNC socket the rear teflon washer must be turned down so that it fits into the .250 inch hole in the mounting plate.

Once all the parts have been sorted out a dummy assembly run can be tried and any mechanical adjustments can be made. Parts should be marked so that they can be reassembled later to be put back in the same place.

The centre conductor should have the pins from the 'N' type socket soldered in place and any excess solder cleaned off. Care should be taken to ensure that the pins are straight and in line with the centre conductor, otherwise problems could occur when trying to mate the 'N' type plugs at the sockets. This can now be set aside ready to be fitted later.

The modified BNC sockets can now be fastened permanently to the brass plates and then all the screw threads and the excess pin length can be removed from the BNC sockets. (Care should be taken if your BNC sockets have the long teflon support for the centre pin because there must be at least $\frac{1}{8}$ inch of pin showing through the teflon in order to allow the pickup line to be fitted).


The pin on the BNC socket should be flush with the surface of the brass mounting plate, as should the screw threads which protrude through the mounting plate. This can most easily be achieved by rubbing the assembly against fine carborundum paper laid on a glass plate, to ensure a flat surface and a good finish. All traces of grit and dust particles must be removed before any further assembly can take place.

Two lengths of copper wire .098 inches in diameter and 2 inches long (allowing plenty for cutting to size) are used for the pick-up loops.

It is very important that the dimensions of the pick-up loops are adhered to, because unless there is access to calibration facilities, the coupling loss and balance will not be known precisely. Adjustment of balance can be made with simple test equipment and this will be described in Appendix A.

A simple jig should be made in order to help make the loops. A piece of plate about $\frac{1}{8}$ inch thick has to have two holes drilled in it .114 inches in diameter and 1.181 inches apart. The copper wire should be bent into a flattened 'U' shape (Figure 8), the ends should pass through both holes, and the wire should lay flat against the plate between the holes. The height of the pick-up loops should be .310 inches measured by placing the loop legs upwards on a flat surface and scribing a mark across the legs with a height gauge set for .310 inches. Cut the legs and file flat to the mark made.

Once this has been done four copper

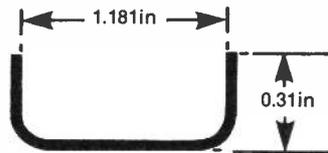

Material: 0.098in diameter copper wire
2 required

Figure 8 Coupling loop

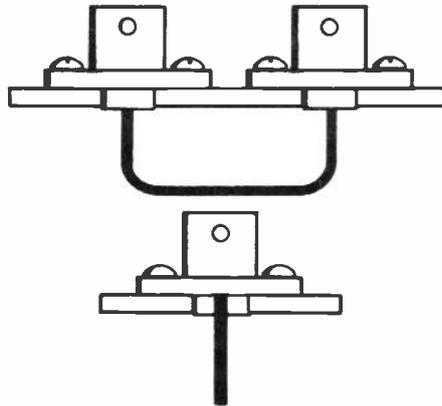


Figure 9 Detail of coupling connections

or brass ferrules are needed so that the coupling loops can be soldered onto the BNC socket pins and kept square. They must not lean to either side or be twisted to one side or the other (Figure 9). The ferrules are made from copper or brass shim stock cut into a strip $\frac{1}{4}$ inch wide and wrapped around a spare piece of .098 inch diameter copper wire a couple of times to form a tube $\frac{1}{4}$ inch long and .098 inches inside diameter. Solder the loops using a hot soldering iron and the minimum amount of cored solder.

The BNC mounting plates can now be fitted onto the body and secured lightly with the fastening screws. The loops should protrude into the bore of the body by the diameter of the wire (Figure 10).

This will produce a coupling loss of about -35dB at 144MHz dropping to -26 dB at 432MHz and about -17dB at 1296MHz, cut off being about 3.5GHz with a coupling of -6dB or less (but could still be useful).

Continue assembly by fitting the 'N' type sockets and centre line. When these have been fitted the screws can be tightened securely and varnish applied to prevent them from coming loose.

Appendix A

The finished directional coupler can be adjusted so that both the pick up lines have the same coupling loss. If the details have been followed closely then the out of balance will not exceed 2dB and hopefully we should be able to do better than .25dB.

Some test equipment is needed but apart from a good 50ohm termination load, a 50ohm dummy load and an avometer with a diode probe will suffice. The source of RF can be a transmitter for 70cm. It is not necessary that the diode probe be calibrated: all that is needed is

an indicator of the voltage developed.

The 50ohm dummy load termination must be able to handle all the power that the transmitter can produce. Set up the coupler as shown in the drawing (see Figure 4) and switch the transmitter on. Measure the voltage produced at the transmitter end of the coupling line with a 50ohm terminator at the other end of the line. Swap sides and compare the voltage measured with the other side. The voltages measured should be exactly the same. If they are then the coupler is ready to use.

The likelihood of both lines producing the same voltage is remote, so one line will have to be adjusted slightly in order to alter the pick-up a little. Move the line in to increase the pick-up. This could be done by bending the flat part of the loop slightly using snipe-nosed pliers. A better method of very fine adjustment can be used by putting several 1 thou thick copper shim stock under the socket mounting plate on the side with the higher voltage measurement (a convenient source for copper shim material is the outer from Pope h100 co-axial cable).

Appendix B

If the constructor has access to a good attenuator of at least 40dB range adjustable in 1dB steps, capable of working at 500MHz or more and of handling the RF power that will be used, then it is quite easy to measure the coupling loss at 432MHz.

Set up the equipment as shown in Figure 11. With the attenuator set to 35dB and using a Tee connector measure the voltage across the 50ohm load, then without disturbing anything measure the voltage at the end of the coupling lines.

Reduce the attenuation until the measured voltage is the same as the first measurement. If required the measuring detector could be a receiver or spectrum analyser etc. Because the coupler lines are all 50ohm and indeed should be terminated in 50ohm so a length of 50ohm coaxial cable can be used between the coupler and whatever detector is used without incurring errors.

It would only be necessary to add the

The formula used for calculating the impedance of the main line is:

$$138 \times \text{Log}^{10} D/d$$

Rearranging to give ratio of D to d from Zo

$$** \text{Zo} = 50 \text{ Ohm}/138 = .3623$$

$$** \text{Ratio of } D/d = .3623^{10} = 2.30:1$$

$$** d = .25 \text{ inch} \times 2.30 = .575 \text{ inch}$$

$$** \text{Line inner diameter} = .250 \text{ inch}$$

$$** \text{Line outer diameter} = .575 \text{ inch}$$

DIRECTIONAL COUPLER

Figure 10 Detail shows the coupling loops protruding

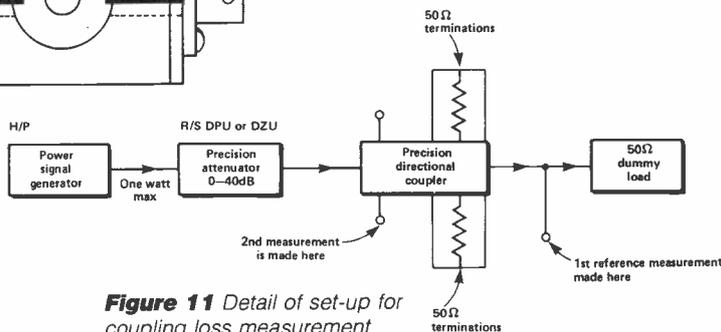
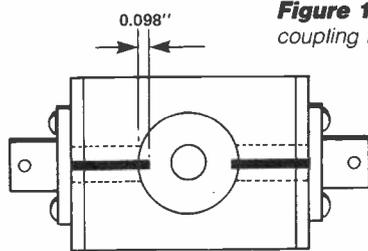


Figure 11 Detail of set-up for coupling loss measurement

insertion loss of the co-axial cable used to the insertion loss of the coupler at the frequency used for the measurement.

The physical dimensions of the lines used in this directional coupler are determined by the requirement that the device has a characteristic impedance of 50ohms.

Note the number of dB's of attenuation removed. This figure is then the coupling loss in dB at the frequency that the measurement was made, and if repeated at say 150, 300, 450, 1000 and 1500MHz, a curve showing the coupling loss against

frequency can be drawn and this graph can be very useful for some applications.

Once the coupler is finished and calibrated we can now use it in order to measure VSWR very accurately, certainly to within 5% or better at 1296 MHz. It must be remembered that both lines are for all intents and purposes exactly the same, so that it does not matter which line is used to measure forward or reflected voltage.

The pick up coupling is the same in any case, but for the maximum accuracy the same diode detector should be used to

make both forward and reflected measurements.

The coupler should be fitted at the antenna when making VSWR measurements, or if this is not possible then the length of the connecting cable must be an electrical multiple of a half wavelength at the frequency in use and be measured very accurately at that.

Don't forget that the length of the cable must include the plugs and sockets and also about one third of the length of the coupler itself. The terminating loads are 1/2W line terminations and are available from Greenpart or Schuner. These are highly recommended since they are good to well over 1.5GHz and are relatively inexpensive.

The same procedure is used for the secondary line sizes but 276 is substituted for 138, the result gives an approximation of dimensions. It should be remembered that the exact impedance of the secondary lines will vary slightly with variations in the wire diameter, cavity size and also the coupling to the main line.

Therefore the line impedance must be measured in order to say precisely what the actual characteristic impedance is.

For the directional coupler described using the given dimensions, and obtaining the coupling factor specified, the secondary line impedance will be within a few per cent of 50ohms.

RADIO RALLIES

BY STEPHEN IBBS

Two rallies have been held in the Midlands recently, one at Drayton Manor Park, and the other at Elvaston Castle (near Derby). It is interesting to compare these two and see how they serve the amateur and his/her family looking for a day out.

The Drayton rally was held on the 20th May, and the weather was good but not brilliant. I arrived at about 8.15am to help a friend set up a stall, and was relieved to find that they have at last moved the three marquees to a new site further away from the main entrance. It had always been a dice with death wandering around the rally because of cars streaming in, and this move was an excellent and necessary improvement. However, the recurring criticism of Drayton is that they always try to cram too many stalls into the tents. One more marquee with the same number of firms would ensure much more room, and less irritability from crowds unable to move.

The stewards tend to be rather over-zealous, or officious, depending on your view-point, and though the rally was not due to open until 11am, it was clear that most stall holders were ready for business well before time... not that this had any effect on the stewards, who delighted in keeping the crowds out,

until finally somebody saw sense. There were a great many bargains to be had at Drayton.

Clearly, the bottom has dropped out of the secondhand market for certain items... eg Pye equipment, and these were being snapped up by those not susceptible to the flashing lights of the latest Japanese offerings.

The big advantage of Drayton is, of course, the fun-fair and zoo for the rest of the family. There is an excellent system whereby children can pay £2.50 and then go on as many rides as they like, all day. This enabled Shelagh (G4TCD) and myself to wander round at our leisure, wishing we could afford to buy lots of things.


The Elvaston rally was held on the 10th June, and the weather was glorious. Here we had to pay 40p car parking... compared with Drayton's £1 per adult plus car parking... a very pleasant surprise, but what sort of day could the children expect? As things turned out, it was marvellous. There were beautiful grounds to explore, the castle and its exhibitions, as well as fun-fair rides, traditional fair-organ, WW2 lorries and jeeps, dog-handling displays, and a special childrens' show arranged by the rally organisers. Their efforts were

greatly appreciated, in what I think must be the best rally I have ever attended. Scouts were on hand to direct the very spacious parking facilities, a PA system was working through the day to announce the various attractions etc, and the refreshments were of a very high standard, with a radio ham wandering around in full chef's gear (plus shorts), directing operations.

With all these distractions it was difficult at times to concentrate on the job in hand... spending the hard-earned pennies. There were a lot of attractive goodies on offer, particularly on the well-organised 'bring-and-buy' stand. There were a lot of stalls out in the open, and the marquees only had stalls around the edges (unlike Drayton which also squeezes in a double row along the centre), and this made so much difference in terms of comfort.

Drayton will always be popular because of its well established side-attractions, but its organisers would do well to remember the thousands of amateurs who object to being kept out, then squashed in to marquees holding too many stalls.

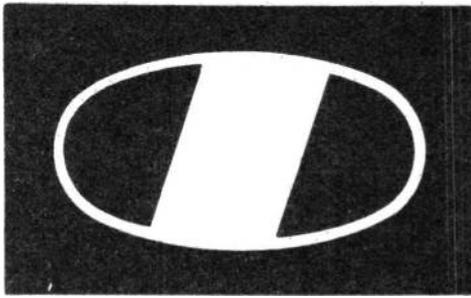Finally, many congratulations to the Elvaston organisers... long may it continue.



ICOM

FOR THE SWL...

IC-R70, £565.

The R70 covers all modes (when the FM option is included), and uses 2CPU-driven VFOs for split frequency working, and has 3 IF frequencies. 70MHz, 9MHz and 455KHz, and a 100dB dynamic range. It has a built-in mains supply. Other features include input switchability through a pre-amplifier, direct or via an attenuator, selectable tuning steps of 1KHz, 100Hz or 10Hz, adjustable IF bandwidth in 3 steps (455KHz). Noise limiter, switchable AGC, tunable notch filter, squelch on all modes, RIT, tone control. Tuning LED for FM (discriminator centre indicator). Recorder output, dimmer control.

The R-70 also has separate antenna sockets for LW-MW with automatic switching, and a large, front-mounted loudspeaker with 5.8W output. The frequency stability for the 1st hour is ± 50 Hz, sensitivity – SSB/CW/RTTY better than 0.32 uv for 12dB (S + N) ÷ N, Am – 0.5 uv. FM better than 0.32 for 12dB Sinad. DC is optional.

Ever since its introduction the IC-R70 has proved to be a popular and reliable HF receiver making your listening hours a pleasure. Please contact us for further details on this excellent set.



IC-R71E, £649.

For those who like the easy life, the R71E has the option of an infra-red remote control unit, making it a very sophisticated rig indeed, here are some details.

100 KHz – 30 MHz all mode (with FM option).

Quadruple conversion superhet. IF frequencies 70MHz, 9MHz and 455KHz with continuous bandpass tuning and notch filter. Virtually immune from adjacent channel interference with 100db dynamic range. Adjustable AGC, noise blanker and switchable pre-amplifier. Direct keyboard into twin VFO's with 32 programmable memories. 5 year lithium memory backup cell. Memory and band scan with auto-stop. Tuning rates 10Hz, 50Hz and 1 KHz with 6 digit readout. AC mains operation. Auto squelch tape record function.

OPTIONS:- Synthesized voice readout, infra-red remote controller, 12 V DC kit, mobile mounting bracket, two CW filters 500 and 250 Hz, FM unit, computer interface, headphones.



You can get what you want just by picking up the telephone. Our mail-order dept. offers you: free, same-day despatch whenever possible, instant credit, interest-free H.P., telephone Barclaycard and Access facility and a 24 hour answering service.

Please note that we now have a new retail branch at 95, Mortimer Street, Herne Bay, Kent. Give it a visit, BCNU.



TWENTY QUESTIONS

A self-test for those who are studying for the City and Guilds 765 Radio Amateurs Examination. Otherwise it can be used to 'brush-up' the memory and revive knowledge that is rusty

Compiled by Dennis Hayes

The City and Guilds 765 Radio Amateurs Examination takes approximately 3 hours and contains two separate papers which have to be answered during the period of the examination.

One hour is allowed for the first paper (765-1-01) which has 35 multiple choice questions covering licensing conditions and transmitter interference. A short break is allowed before commencing the second paper (765-1-02) containing multiple choice questions about operating practices, procedures and theory. This paper has 60 questions and the time allowance is 1½ hours.

The Amateurs Handbook (published in three parts and included in the December 83, January & February 84 issues of **Radio & Electronics World**) is a useful source of information and is recommended reading for the intending candidate. Page 20 of Part 1 of this book gives a comprehensive guide to other sources of information.

Although the following quiz is not as extensive as the City and Guilds examination and does not give a preview of the questions actually set, it may provide a useful indication of your state of readiness if you answer the quiz questions over a self-timed interval.

Now try the quiz, then look at the answers (on page 70).

Questions

1. Which of the following organisations is entitled to request assistance from a licensed amateur radio station during an emergency (disaster relief operation)?

- (a) Emergency County Planning Officer
- (b) St John Ambulance Brigade
- (c) The DHSS
- (d) British Red Cross Society
- (e) Police Force

2. An amateur radio station may use any class of emission provided it is within the amateur frequency bands. (True or False?)

3. The Morse Test includes sending----

words, averaging 4 letters per word, in 4 minutes.

(True or False?)

4. What is the maximum number of corrections and uncorrected errors that are allowed in the Morse Sending Test?

	Correction	Uncorrected Errors
(a)	2	2
(b)	1	3
(c)	4	0
(d)	3	4

5. The Morse Test involves receiving ---- words, averaging 5 letters per word and --- five figure groups in --- minutes.

6. Related to Question 5. A word with more than one letter incorrectly received counts as --- errors.

7. The maximum number of errors in receiving plain language and figures during the Morse Test is:

	Plain Language	Figures
(a)	1	1
(b)	2	1
(c)	3	2
(d)	4	2

8. What speeds of transmission are permitted for RTTY?

	Bauds
(a)	40
(b)	45.5
(c)	49
(d)	47.5

9. When using telegraphy it is particularly important to ensure that interference due to ---- is eliminated.

10. The amateur must notify the authority when he is testing for the presence of harmonics or other spurious emissions in his transmission. (True or False?)

11. If the station is temporarily operated elsewhere the call - sign must be amended.

(True or False?)

12. The input power requirement for an

equipment is 550W. A suitable rating for its supply fuse would be:

(a) 13A (b) 3A

13. The ohmic value of a resistor with colour coded bands of yellow, brown, orange is:

(a)	31,000
(b)	41,000
(c)	25,000
(d)	6,000

14. The input level of 100 mW to an amplifier of equal input and output impedances produces an output of 10 W. The power gain of the amplifier (in dB) and its output level (in dBW) is:

	Gain (dB)	Output Level (dBW)
(a)	20	10
(b)	17	7
(c)	14	4
(d)	10	10

15. If the maximum deviation of an FM signal is 3KHz either side of the carrier when the modulating frequency is 100Hz, the modulation index is:

(a) 5 (b) 3 (c) 100 (d) 30

16. When a 14.1MHz carrier is frequency modulated at 1KHz, first and second sideband pairs will be produced at:

1st	2nd
(a) 14,087 & 14,103KHz	14,094 & 14,106KHz
(b) 14,098 & 14,102KHz	14,096 & 14,104KHz
(c) 14,101 & 14,099KHz	14,102 & 14,098KHz

17. A pre-emphasis circuit restricts the bandwidth of an FM signal and a clipper attenuates the lower frequencies. (True or False?)

18. A Lissajous figure can be displayed when comparing two low frequency sinusoidal signals and the oscilloscope pattern will depend on:

(a) signal amplitudes (b) phase relation (c) frequencies (d) a,b,c

19. The Lissajous figure will be stationary when a constant ratio exists between (a) phase (b) frequency (c) both.

20. An antenna designed for operation on 435MHz has the same gain as another designed for operation at 145 MHz. Are they equally effective?

(a) No (b) Yes

SPORADIC-E PROPAGATION


by Keith Hamer
and Garry Smith



Throughout Europe there are literally hundreds of broadcast radio and television transmitters operating in Bands I and II within the 40 to 110MHz spectrum. Many outlets are low-power relays but there are dozens of main transmitters with effective radiated powers (ERPs) of between 10 and 100 KW. These can be easily received in the UK with the aid of Sporadic-E propagation.

The established DX enthusiast will already be aware of those countries and transmitters which are readily received, and those which are more elusive, requiring patience and technical expertise. The newcomer has to start from basics and it is hoped that this article will provide an insight as to which countries can be expected during good conditions and how to identify reception.

It shouldn't be assumed that a large aerial and sophisticated equipment will automatically guarantee an endless selection of extra TV and radio programmes on a permanent basis. One of the thrills of DX reception is the uncertainty and surprise element of what may be received, since it is atmospheric conditions which have the upper hand in the matter. TV-DXers with years of experience still find the sight of a foreign test card or clock caption on their screens fascinating, especially when the signal has originated several hundred miles away.

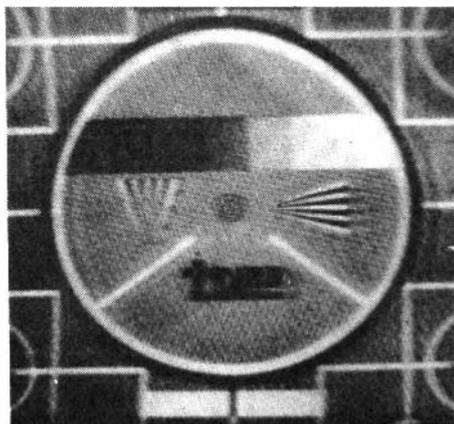

Spanish test card

Sporadic-E reception

Under normal conditions signals radiating from a high power transmitter cannot be satisfactorily received beyond the optical horizon. This is approximately 80 to 100 miles from the transmitting site and is due to the curvature of the Earth. Signals will leave at a tangent and continue into space after passing through the E-layer, situated some 75 miles above the surface of the Earth. At certain times of the year patches of ionised gasses within the E-layer become capable of reflecting signals at VHF frequencies back to the Earth.

Since reflection takes place a skip distance is involved. This is typically 700 miles, but occasionally the signal is reflected again producing multi-skip reception. Sometimes reflection will take place at a more acute angle, thus producing a very short skip of 250 miles or less. Such instances are, however, rare.

Sporadic-E ionisation occurs mainly between mid-May and early September, when DX reception can be an almost daily event. However, Sporadic-E activity can occur at other times of the year, although it is less frequent and less dramatic than the summer period. 'Openings', as they are termed, are completely random and can present themselves at any time of the day or night.


On some days activity can be non-existent or last for only a few minutes, while on others there may be several openings. Occasionally an opening can last for much of the day with signals arriving from every direction.

Openings are more common on the lower VHF frequencies. Consequently

there will be fewer instances of signal propagation on the FM radio band compared with Band I television channels. During very intense activity the maximum usable frequency (MUF) will occasionally rise above the 2-metre amateur band and permit Band III TV reception, albeit on the lower channels such as E5 and E6. However, on at least one occasion the MUF rose sufficiently to allow Soviet TV to be seen on all its Band III channels including R12 at 223.25MHz. Details of channel frequencies are given in the table.

Signals propagated via Sporadic-E ionisation can vary in strength and quality even over a period of seconds, although the higher the frequency at which reception takes place the more stable and slow-fading it tends to be. Television signals propagated on the lower Band I channels are often very strong, attaining levels of several mV, but they can suffer from reduced bandwidth effects, producing smeary and distorted video.

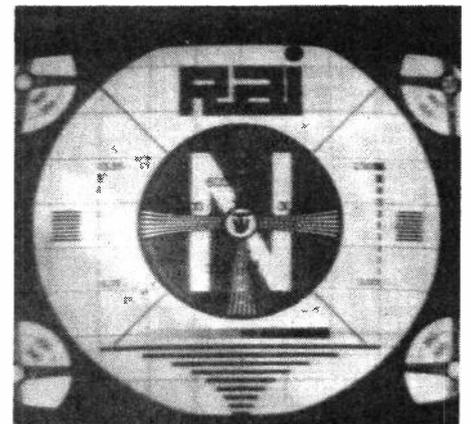Colour and sound are more easily resolved on the higher Band I channels



Italian test card

SPORADIC-E

due to improved signal stability and quality. Where the FM radio band is affected via Sporadic-E the signal characteristics often resemble those of tropospheric propagation.

Initial experiments in Sporadic-E reception should be conducted during the summer, to take advantage of frequent openings and high signal levels. This means that fairly simple receiving apparatus can be employed. A dipole can be used for both TV and FM radio reception, with each rod cut to 50 inches for the centre of Band I or 30 inches for the FM band.

Aerials should be mounted horizontally and some method of rotation is desirable since a horizontal dipole is directional. Height is not of great importance because signals propagated via Sporadic-E arrive at an angle but, local shielding should be taken into account.

For more serious and regular experiments most enthusiasts progress to the luxury of a multi-element beam covering the appropriate channels. The use of masthead amplifiers should be avoided, no matter how tempting these may be. Signal levels in Band I can attain many mV without amplification, and using such a device may introduce cross-modulation and other spurious effects.

Equipment requirements

A typical domestic FM radio receiver will suffice for the reception of Western

European FM stations where the frequency range 88 to 108MHz is used. Eastern bloc countries have their own FM band situated between 64 and 73MHz, with the exception of Yugoslavia where standard Western European allocations have been adopted. One solution to Eastern bloc FM reception is to use a scanner such as the SX200-N.

This would also allow monitoring of the various Italian private radio station transmitter links operating between 45 and 60MHz. These carry popular music programmes and are usually present during reception of television signals from Italy on channels IA and IB. As a bonus, foreign TV sound can be monitored with such a scanner.

For television reception via Sporadic-E, a receiving system capable of covering the necessary frequencies is an obvious essential. With the exception of France, who use 625 lines with positive vision modulation and AM sound, all other European services use 625 lines with negative video and FM intercarrier sound. In fact they are very similar to our own system except that the sound spacing differs and they utilise Bands I and III as well as UHF. The intercarrier sound spacing is 6.0MHz in the UK and Eire, 6.5MHz in Eastern-bloc countries and 5.5MHz in Western Europe (including Yugoslavia), Africa and the Middle East.

Certain domestic television receivers already possess a multiband tuner as


standard. These are mainly imported models from manufacturers such as Grundig, Luxor and Telefunken. A few domestic video cassette recorders have multiband facilities. The Sanyo 930-00 and the Hitachi VT 11E (DS) are two examples. By simply connecting a suitable aerial and setting the bandswitch selector to Band I, DX signals can be tuned in with the VCR.

There are many small-screen portable TV sets which cover the appropriate European channels. Prospective purchasers should look for tuning scales marked 2-4 and 5-12; this will indicate Western European E channels 2 to 12. Some portables have switching for Continental and UK sound standards and colour receivers catering for both PAL and SECAM transmissions are readily available.

For the keen experimenter a multiband tuner could be fitted to an existing receiver although modifications and additions of this type demand a certain level of competence on the part of the individual. The usual safety precautions must be observed when dealing with domestic receivers since these employ live-chassis techniques.

Battery/mains portables are normally equipped with an integral mains isolating transformer, thus making modifications more attractive from the aspect of safety.

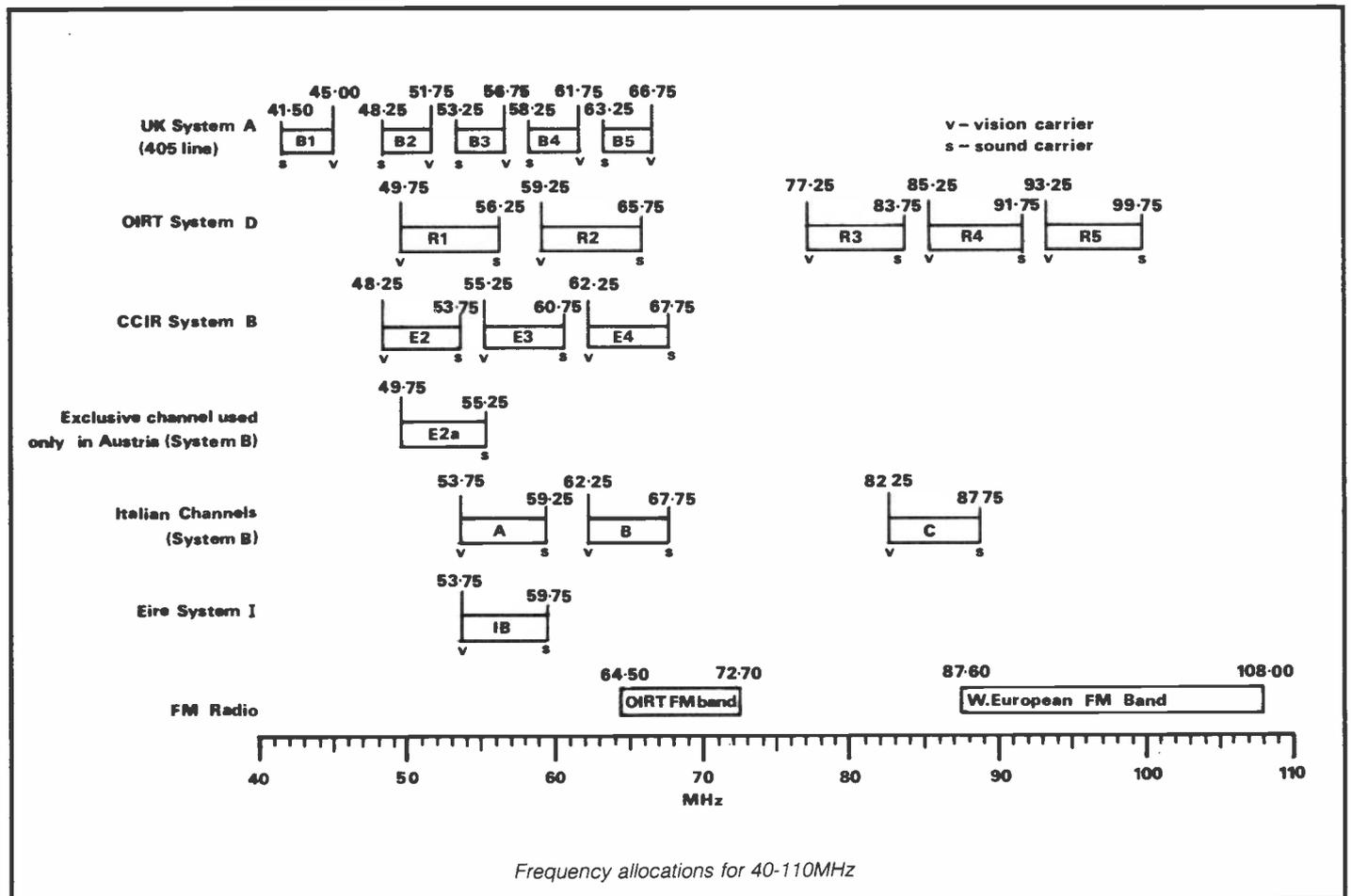Inexpensive varicap tuners suitable for Band I experiments are available



SPORADIC-E



from mail-order companies such as Sendz Components. Most have only the basic Band I coverage of 47 to 68MHz but others provide an extended coverage well into the FM radio spectrum. The ELC 2060 is an example and covers OIRT channels R3, R4 and R5.

Simple modifications of this type will provide vision-only signals, but it is not considered too much of a disadvantage. The intercarrier sound IFs could be realigned to the appropriate sound spacing of 5.5MHz or 6.5MHz if required, although many circuits use fixed ceramic filters and these would have to be changed.

The more intrepid experimenter could build the multiband DX-TV converter described in the August 1983 issue of **R&EW**. This can be used with an unmodified receiver.

Identifying TV signals

Programme content and presentation quality both contribute in providing signal identification in the absence of captions and test cards. The experienced DXer finds his 'sixth sense' offers assistance too. Familiarising oneself with the positions of various channels in Band I is advisable and is a relatively easy task, especially if the local BBC-1 transmitters are still on the air to act as markers.

Reference to the channel allocations in the table should help. Once their relative positions have been established, with practice it should be easy to differentiate between E and R channels.

Some countries do not use all channels in Band I and by a process of elimination it is possible to work out which service is being received. For instance, Rumania does not appear on channel R1 and Denmark does not transmit on channel E2.

The general direction from which a signal originates can often give a valuable clue, although on rare occasions signals can be reflected within the E-layer and arrive from a totally different direction than that of the transmitter. Neighbouring countries may be present, especially during intense openings. Yugoslavian signals usually accompany Italian transmissions, and if these are present it is often worthwhile to be on the look out for double skip signals from Jordan.

The accompanying sound channel can provide more clues, but unless one is conversant with foreign languages it may be best to leave well alone, although it does tend to add a touch of glamour to the reception.

Test cards provide a positive form of identification. Most television services use an electronically generated colour pattern and nearly all incorporate some form of identification. Norway even displays the time and the transmitter location on their test card; other services simply include station initials. On Russian test cards there are lots of unusual numbering systems and small lettering in the Cyrillic alphabet.

Test cards in Europe are radiated prior to programmes but there is a growing

trend to display sample teletext pages. Unfortunately these all look alike, especially on weak signals. Identification captions and clocks are other possible means of identifying services, but not all clocks carry identification.

However, clock captions can give an indication as to the country of origin even without identification. A check should be made of the time. Is it GMT +1 hour or GMT +4 hours? If it's the latter and on an E channel then the signal is almost certainly an 'exotic', probably from the Middle East.

Weather maps can be a useful guide to identifying a signal. By noting which area of the map is receiving the most attention it is often possible to pin-point the source of reception.

Some services regularly use subtitling in the lower portion of the picture, especially with imported programmes and feature films. Scandinavia, Yugoslavia and Rumania frequently show subtitled programmes. While spoken foreign languages may be difficult to understand it is surprising how quickly one recognises them when in subtitle form.

Several European countries such as West Germany, Switzerland and Italy now incorporate station identification in the corner of the picture in an attempt to prevent piracy. These inserts frequently change position but they do provide yet another means of identification.

Most countries use some form of digital information known as vertical interval test signals (VITS) within the frame bar. These differ between services and also from studio to studio within a particular service. As the VITS tend to change periodically they cannot be relied upon to provide definite identification on a permanent basis. The frame amplitude of the receiver may have to be reduced in order to display these test pulses.

The style of dress and sometimes the complexion of presenters can offer an overall clue to the country of origin, although the sighting of a big beefy battleaxe doesn't always indicate Soviet TV. Early morning TV from Russia is easy to spot: it's normally a diet of keep-fit classes followed by a concert, poetry or a military parade.

In other Eastern bloc countries services are more Westernised in their approach, with cartoons and advertising. This is especially true of Hungarian TV. Spanish TV tends to feature bullfighting very regularly – in fact, it's their version of 'Match of the Day'. Popeye cartoons, Tom and Jerry dubbed in Spanish, The Avengers and a few 'heavy' drama programmes are also typical offerings.

The DX-TV enthusiast will have to search for Icelandic TV if it's late-night test cards he's after. Programmes do not start until approximately 2000GMT and closedown is never more than about three hours away. Consequently, the test card is radiated for lengthy periods, even throughout the night on some occasions. A late evening opening to this area could mean trans-Atlantic DX since there will

SPORADIC-E

be little chance of signals being swamped by European stations, especially during the early hours.

When to tune in

As mentioned previously, Sporadic-E reception can occur at any time of the day or night, the only limiting factor being the hours of transmission. Since Western Russia is GMT +3 hours (CET +2 hours) test transmissions may be present as early as 0400 CET with programmes at 0600. Several other countries usually commence test transmissions shortly after. Italian reception is common during the main season and in 1983 it was seen virtually on a daily basis with a blank raster followed by the test card at 0800.

There is often a decrease in activity towards mid-morning. Spain is a frequent visitor around noon showing test cards, some of which include transmitter location details. Regional programmes in Spain are radiated at 1300.

Many European services devote mornings to schools television followed at lunchtime by lengthy news bulletins and magazine programmes. At such times identifying stations can often prove a headache, especially for the newcomer to DX-TV. During afternoon periods, Spain and Portugal may close down some of the transmitters and, if conditions are good to the south, there is the possibility of double-hop or even triple-

hop reception, perhaps from Ghana or Nigeria.

There is a tendency for intense openings to manifest themselves during the late afternoon or early evening and the FM radio band can become extremely active with signals from the south-east. Albanian TV on channel IC often appears during such activity. The 'magic' time for exotics seems to be between 1815 and about 1930 with the possibility of Jordanian signals appearing.

Western Russia is well populated with Band I transmitters and their current affairs programme 'BPEMЯ' is a familiar sight at 1900, preceded by a clock caption showing 2100 hours local time. It is not uncommon for Soviet transmissions to end at about 2130 CET but some other Eastern-bloc countries radiate programmes until approximately 0100.

Successful reception

We have concentrated mainly upon reception of television signals propagated via Sporadic-E ionisation since Band I frequencies are regularly affected. Many would-be experimenters often feel that reception of this nature is too technically demanding for them to undertake and that large receiving arrays and ultra-sensitive receivers are necessary.

The authors' thoughts were similar

some 15 years ago but success is assured even for beginners. New enthusiasts usually see Soviet, Italian and Spanish TV programmes within a few days of starting during the main summer season. This year's Sporadic-E may be the quietest yet as regards local interference problems since few 405-line VHF transmitters are operating at full strength. The whole of the band will eventually be re-organised to incorporate the 6 metre amateur band and various other communication services, a development which will be peculiar to the United Kingdom.

Further reading

The following two books should prove to be of interest to radio and television enthusiasts:-

Radio Stations Guide - Apart from covering long wave, medium wave and short wave stations, this book also lists European FM transmitters in ascending order of frequencies.

Guide to World-Wide Television Test Cards-Edition 2 - A comprehensive book featuring test cards and identification captions to help DX-TV enthusiasts identify reception.

Both books are available from *HS Publications, 17 Collingham Gardens, Derby DE3 4FS*. Further details are available by sending a stamped-addressed envelope.

AA117 5p	BC328 5p	BFX85 20p	TIP112 54p	2N3773 100p	BVX70/500 31p	DY802 45p	4042 59p	7482 70p	74LS367 52p	HA-1368 190p	TBA990 60p
AA117 40p	BC328 40p	BFX85 15p	TIP113 45p	2N3819 25p	BYX71/600 80p	ECR22 45p	4043 57p	7483 45p	LM321 90p	LA-201 150p	TC420 40p
AA117 150p	BC328 150p	BFX85 15p	TIP117 56p	2N3866 68p	BYX71/600 80p	ECR23 43p	4044 57p	7486 25p	LM321 100p	LA-1265 170p	TC480 80p
AA117 15p	BC328 15p	BFX85 15p	TIP120 43p	2N4031 25p	OA47 6p	ECR24 40p	4047 65p	7489 100p	LM380 60p	LA-3301 180p	TC490 80p
AA117 15p	BC328 15p	BFX85 15p	TIP121 47p	2N4036 25p	OA90 4p	ECR25 40p	4048 49p	7490 35p	LM380 60p	LA-3350 150p	TC490 80p
AA117 15p	BC328 15p	BFX85 15p	TIP122 47p	2N4317 25p	OA91 4p	ECR26 40p	4049 49p	7491 35p	LM380 60p	LA-4311 140p	TC490 80p
AA117 15p	BC328 15p	BFX85 15p	TIP125 47p	2N4443 75p	OA200 7p	ECR27 40p	4050 49p	7493 35p	LM380 60p	LA-4032 190p	TC490 80p
AA117 15p	BC328 15p	BFX85 15p	TIP126 56p	2N4444 75p	OA202 7p	ECR28 40p	4051 62p	7495 40p	LM380 60p	LA-4051 250p	TC490 80p
AA117 15p	BC328 15p	BFX85 15p	TIP127 56p	2N5061 20p	IN914 2p	ECR29 40p	4052 61p	7497 80p	LM380 60p	LA-4101 140p	TC490 80p
AA117 15p	BC328 15p	BFX85 15p	TIP128 47p	2N5294 30p	IN4001 4p	ECR30 40p	4053 61p	74107 30p	LM380 60p	LA-4102K 32p	TC490 80p
AA117 15p	BC328 15p	BFX85 15p	TIP2955 34p	2N5296 30p	IN4002 4p	ECR31 40p	4054 57p	74111 52p	LM380 60p	LA-4102K 32p	TC490 80p
AA117 15p	BC328 15p	BFX85 15p	TIP3054 38p	2N6106 40p	IN4003 4p	ECR32 40p	4055 90p	74116 52p	LM380 60p	LA-4420 150p	TC490 80p
AA117 15p	BC328 15p	BFX85 15p	TIP3055 38p	2N6107 40p	IN4004 4p	ECR33 40p	4056 85p	74119 85p	LM380 60p	LA-4430 150p	TC490 80p
AA117 15p	BC328 15p	BFX85 15p	TIP3056 38p	2N6108 40p	IN4005 4p	ECR34 40p	4057 72p	74122 40p	LM380 60p	LA-4430 150p	TC490 80p
AA117 15p	BC328 15p	BFX85 15p	TIP3057 38p	2N6109 40p	IN4006 4p	ECR35 40p	4058 72p	74123 40p	LM380 60p	LA-4430 150p	TC490 80p
AA117 15p	BC328 15p	BFX85 15p	TIP3058 38p	2N6110 40p	IN4007 4p	ECR36 40p	4059 25p	74125 40p	LM380 60p	LA-4430 150p	TC490 80p
AA117 15p	BC328 15p	BFX85 15p	TIP3059 38p	2N6111 40p	IN4008 4p	ECR37 40p	4060 25p	74126 40p	LM380 60p	LA-4430 150p	TC490 80p
AA117 15p	BC328 15p	BFX85 15p	TIP3060 38p	2N6112 40p	IN4009 4p	ECR38 40p	4061 25p	74127 40p	LM380 60p	LA-4430 150p	TC490 80p
AA117 15p	BC328 15p	BFX85 15p	TIP3061 38p	2N6113 40p	IN4010 4p	ECR39 40p	4062 25p	74128 40p	LM380 60p	LA-4430 150p	TC490 80p
AA117 15p	BC328 15p	BFX85 15p	TIP3062 38p	2N6114 40p	IN4011 4p	ECR40 40p	4063 25p	74129 40p	LM380 60p	LA-4430 150p	TC490 80p
AA117 15p	BC328 15p	BFX85 15p	TIP3063 38p	2N6115 40p	IN4012 4p	ECR41 40p	4064 25p	74130 40p	LM380 60p	LA-4430 150p	TC490 80p
AA117 15p	BC328 15p	BFX85 15p	TIP3064 38p	2N6116 40p	IN4013 4p	ECR42 40p	4065 25p	74131 40p	LM380 60p	LA-4430 150p	TC490 80p
AA117 15p	BC328 15p	BFX85 15p	TIP3065 38p	2N6117 40p	IN4014 4p	ECR43 40p	4066 25p	74132 40p	LM380 60p	LA-4430 150p	TC490 80p
AA117 15p	BC328 15p	BFX85 15p	TIP3066 38p	2N6118 40p	IN4015 4p	ECR44 40p	4067 25p	74133 40p	LM380 60p	LA-4430 150p	TC490 80p
AA117 15p	BC328 15p	BFX85 15p	TIP3067 38p	2N6119 40p	IN4016 4p	ECR45 40p	4068 25p	74134 40p	LM380 60p	LA-4430 150p	TC490 80p
AA117 15p	BC328 15p	BFX85 15p	TIP3068 38p	2N6120 40p	IN4017 4p	ECR46 40p	4069 25p	74135 40p	LM380 60p	LA-4430 150p	TC490 80p
AA117 15p	BC328 15p	BFX85 15p	TIP3069 38p	2N6121 40p	IN4018 4p	ECR47 40p	4070 25p	74136 40p	LM380 60p	LA-4430 150p	TC490 80p
AA117 15p	BC328 15p	BFX85 15p	TIP3070 38p	2N6122 40p	IN4019 4p	ECR48 40p	4071 25p	74137 40p	LM380 60p	LA-4430 150p	TC490 80p
AA117 15p	BC328 15p	BFX85 15p	TIP3071 38p	2N6123 40p	IN4020 4p	ECR49 40p	4072 25p	74138 40p	LM380 60p	LA-4430 150p	TC490 80p
AA117 15p	BC328 15p	BFX85 15p	TIP3072 38p	2N6124 40p	IN4021 4p	ECR50 40p	4073 25p	74139 40p	LM380 60p	LA-4430 150p	TC490 80p
AA117 15p	BC328 15p	BFX85 15p	TIP3073 38p	2N6125 40p	IN4022 4p	ECR51 40p	4074 25p	74140 40p	LM380 60p	LA-4430 150p	TC490 80p
AA117 15p	BC328 15p	BFX85 15p	TIP3074 38p	2N6126 40p	IN4023 4p	ECR52 40p	4075 25p	74141 40p	LM380 60p	LA-4430 150p	TC490 80p
AA117 15p	BC328 15p	BFX85 15p	TIP3075 38p	2N6127 40p	IN4024 4p	ECR53 40p	4076 25p	74142 40p	LM380 60p	LA-4430 150p	TC490 80p
AA117 15p	BC328 15p	BFX85 15p	TIP3076 38p	2N6128 40p	IN4025 4p	ECR54 40p	4077 25p	74143 40p	LM380 60p	LA-4430 150p	TC490 80p
AA117 15p	BC328 15p	BFX85 15p	TIP3077 38p	2N6129 40p	IN4026 4p	ECR55 40p	4078 25p	74144 40p	LM380 60p	LA-4430 150p	TC490 80p
AA117 15p	BC328 15p	BFX85 15p	TIP3078 38p	2N6130 40p	IN4027 4p	ECR56 40p	4079 25p	74145 40p	LM380 60p	LA-4430 150p	TC490 80p
AA117 15p	BC328 15p	BFX85 15p	TIP3079 38p	2N6131 40p	IN4028 4p	ECR57 40p	4080 25p	74146 40p	LM380 60p	LA-4430 150p	TC490 80p
AA117 15p	BC328 15p	BFX85 15p	TIP3080 38p	2N6132 40p	IN4029 4p	ECR58 40p	4081 25p	74147 40p	LM380 60p	LA-4430 150p	TC490 80p
AA117 15p	BC328 15p	BFX85 15p	TIP3081 38p	2N6133 40p	IN4030 4p	ECR59 40p	4082 25p	74148 40p	LM380 60p	LA-4430 150p	TC490 80p
AA117 15p	BC328 15p	BFX85 15p	TIP3082 38p	2N6134 40p	IN4031 4p	ECR60 40p	4083 25p	74149 40p	LM380 60p	LA-4430 150p	TC490 80p
AA117 15p	BC328 15p	BFX85 15p	TIP3083 38p	2N6135 40p	IN4032 4p	ECR61 40p	4084 25p	74150 40p	LM380 60p	LA-4430 150p	TC490 80p
AA117 15p	BC328 15p	BFX85 15p	TIP3084 38p	2N6136 40p	IN4033 4p	ECR62 40p	4085 25p	74151 40p	LM380 60p	LA-4430 150p	TC490 80p
AA117 15p	BC328 15p	BFX85 15p	TIP3085 38p	2N6137 40p	IN4034 4p	ECR63 40p	4086 25p	74152 40p	LM380 60p	LA-4430 150p	TC490 80p
AA117 15p	BC328 15p	BFX85 15p	TIP3086 38p	2N6138 40p	IN4035 4p	ECR64 40p	4087 25p	74153 40p	LM380 60p	LA-4430 150p	TC490 80p
AA117 15p	BC328 15p	BFX85 15p	TIP3087 38p	2N6139 40p	IN4036 4p	ECR65 40p	4088 25p	74154 40p	LM380 60p	LA-4430 150p	TC490 80p
AA117 15p	BC328 15p	BFX85 15p	TIP3088 38p	2N6140 40p	IN4037 4p	ECR66 40p	4089 25p	74155 40p	LM380 60p	LA-4430 150p	TC490 80p
AA117 15p	BC328 15p	BFX85 15p	TIP3089 38p	2N6141 40p	IN4038 4p	ECR67 40p	4090 25p	74156 40p	LM380 60p	LA-4430 150p	TC490 80p
AA117 15p	BC328 15p	BFX85 15p	TIP3090 38p	2N6142 40p	IN4039 4p	ECR68 40p	4091 25p	74157 40p	LM380 60p	LA-4430 150p	TC490 80p
AA117 15p	BC328 15p	BFX85 15p	TIP3091 38p	2N6143 40p	IN4040 4p	ECR69 40p	4092 25p	74158 40p	LM380 60p	LA-4430 150p	TC490 80p
AA117 15p	BC328 15p	BFX85 15p	TIP3092 38p	2N6144 40p	IN4041 4p	ECR70 40p	4093 25p	74159 40p	LM380 60p	LA-4430 150p	TC490 80p
AA117 15p	BC328 15p	BFX85 15p	TIP3093 38p	2N6145 40p	IN4042 4p	ECR71 40p	4094 25p	74160 40p	LM380 60p	LA-4430 150p	TC490 80p
AA117 15p	BC328 15p	BFX85 15p	TIP3094 38p	2N6146 40p	IN4043 4p	ECR72 40p	4095 25p	74161 40p	LM380 60p	LA-4430 150p	TC490 80p
AA117 15p	BC328 15p	BFX85 15p	TIP3095 38p	2N6147 40p	IN4044 4p	ECR73 40p	4096 25p	74162 40p	LM380 60p	LA-4430 150p	TC490 80p
AA117 15p	BC328 15p	BFX85 15p	TIP3096 38p	2N6148 40p	IN4045 4p	ECR74 40p	4097 25p	74163 40p	LM380 60p	LA-4430 150p	TC490 80p
AA117 15p	BC328 15p	BFX85 15p	TIP3097 38p	2N6149 40p	IN4046 4p	ECR75 40p	4098 25p	74164 40p	LM380 60p	LA-4430 150p	TC490 80p
AA117 15p	BC328 15p	BFX85 15p	TIP3098 38p	2N6150 40p	IN4047 4p	ECR76 40p	4099 25p	74165 40p	LM380 60p	LA-4430 150p	TC490 80p
AA117 15p	BC328 15p	BFX85 15p	TIP3099 38p	2N6151 40p	IN4048 4p	ECR77 40p	4100 25p	74166 40p	LM380 60p	LA-4430 150p	TC490 80p
AA117 15p	BC328 15p	BFX85 15p	TIP3100 38p	2N6152 40p	IN4049 4p	ECR78 40p	4101 25p	74167 40p	LM380 60p	LA-4430 150p	TC490 80p
AA117 15p	BC328 15p	BFX85 15p	TIP3101 38p	2N6153 40p	IN4050 4p	ECR79 40p	4102 25p	74168 40p	LM380 60p	LA-4430 150p	TC490 80p
AA117 15p	BC328 15p	BFX85 15p	TIP3102 38p	2N6154 40p	IN4051 4p	ECR80 40p	4103 25p	74169 40p	LM380 60p	LA-4430 150p	TC490 80p
AA117 15p	BC328 15p	BFX85 15p	TIP3103 38p	2N6155 40p	IN4052 4p	ECR81 40p	4104 25p	74170 40p	LM380 60		

ATTENTION 10 METRE OPERATORS!

especially for the 10 Metre users who have converted CB rigs

The AKD 10 Metre Linear Amplifier

- ★ 25 Watts FM out for 4 Watts in
- ★ 50 Watts PEP on SSB
- ★ About 10 Watts out for ½ Watt in (13.8V)
- ★ Automatic RF sensing
- ★ Fully protected output
- ★ Relay switching employed
- ★ Requires nominal 12 volts @ 5 amps (15 volts maximum)
- ★ In-line fused
- ★ 2 year guarantee (including output device)
- ★ British made



£25.50
Incl VAT, p&p

10 Metre RF Switched, In-Line Pre-Amp.

- ★ 3SK45 Dual Gate Fet, 15 dB gain
- ★ Fail safe, will handle 10 watts through power
- ★ 2 year guarantee




£14.50
Incl VAT, p&p

★★★★★

Also available, the AKD range of RF INTERFERENCE FILTERS – high performance, sleek appearance.

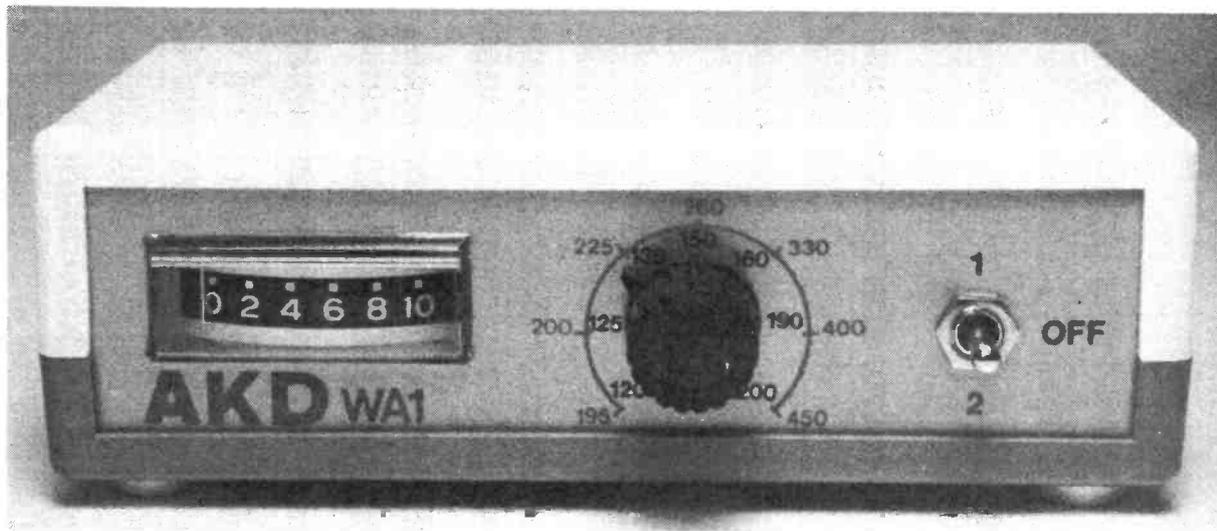Used by British Telecom, Granada, ITT, Thorn-EMI and other prominent companies.



A WAVEMETER FOR VHF/UHF

The AKD WA1 Absorption Wave-meter covers 120-450 MHz in two ranges. It is extremely sensitive and comes complete with a small aerial. It requires a PP3 battery.

£24.95 inclusive
of postage & VAT

Direct from the Manufacture – or from your local Amateur Radio dealer.
Trade enquiries welcome

*** AKD * ARMSTRONG KIRKWOOD DEVELOPMENTS**
62 Marcourt Road, Stokenchurch, High Wycombe, Bucks, HP14 3QU
Tel. 024-026-2360

The QQV06-40A

as a linear amplifier

by Brian Dale

In this article Brian Dale discusses the gentle art of coaxing in excess of 100 watts from the QQV06-40A double beam tetrode. Although not a constructional article as such, nevertheless it provides sufficient information to construct a linear amplifier based on his experience of constructing half a dozen such amplifiers in as many years:

Having wet his feet on the band, the newcomer to 2 metres will often decide that he requires more power. Technically this is not very difficult for several manufacturers produce ranges of linear amplifiers with output ratings from ten to nearly 200W.

All of these are capable of giving excellent results. However, when the cost of the complete system is analysed, particularly for higher powers, the newcomer may well have second thoughts. The combined cost of a 100W amplifier and the associated power supplies will almost certainly exceed £200 and if higher powers are contemplated, considerably more.

Frequently, therefore, thoughts turn to a 'home brew' solution.

Designs for 2 metre 100W solid-state linear amplifiers have appeared from time to time in the amateur press. A costing exercise, however, will frequently reveal that, given the expense of high power VHF transistors, there is little financial advantage over purchase and, furthermore, one mishap will make the project hopelessly uneconomic.

The next consideration is for the use of those old fashioned generators of heat, light and RF valves.

Choice of valves

Here there is a choice. The high power alternative is to use a ceramic tetrode such as the 4CX250, but the cost of this plus the special valve base, blower and the high voltage power supply unit will almost certainly run far higher than the solid-state option previously rejected.

The other choice is to consider the use of a medium power double tetrode such as the well tried QQV06-40A, which is capable of an output well in excess of 100W in SSB service, relatively inexpensive and, provided that reasonable precautions are taken, quite straightforward to construct and operate.

With regard to the economic aspects, these valves are regularly advertised at prices from £6 to £60 but it is frequently possible to purchase ex-equipment samples for considerably less at rallies and radio club junk sales.



The remaining costly item for such an amplifier is the HT mains transformer. This again is best found at a rally or a junk sale. The power requirements are quite modest and a 350-0-350V or 375-0-375V, 125mA transformer should be quite capable of powering an output well in excess of 100W. A small ex-broadcast receiver transformer giving 250-0-250V and sundry heater windings will provide bias and heater supplies.

The QQV06-40A is a VHF double tetrode with a total anode dissipation rating of 40W for which most handbooks quote the use of a maximum anode

voltage of 750V for CW and 600V for amplitude modulation operation, giving a carrier output of up to 90W. The latter, however, gives the clue to the power possibilities in SSB operation.

During 100% amplitude modulation peaks, the anode voltage reaches twice its steady value and the peak output power is one and a half times the unmodulated carrier level. It would therefore appear that the valve is capable of withstanding anode voltages up to 1200V and of giving a peak output power in the order of 130-140W.

Experience gained in the construction

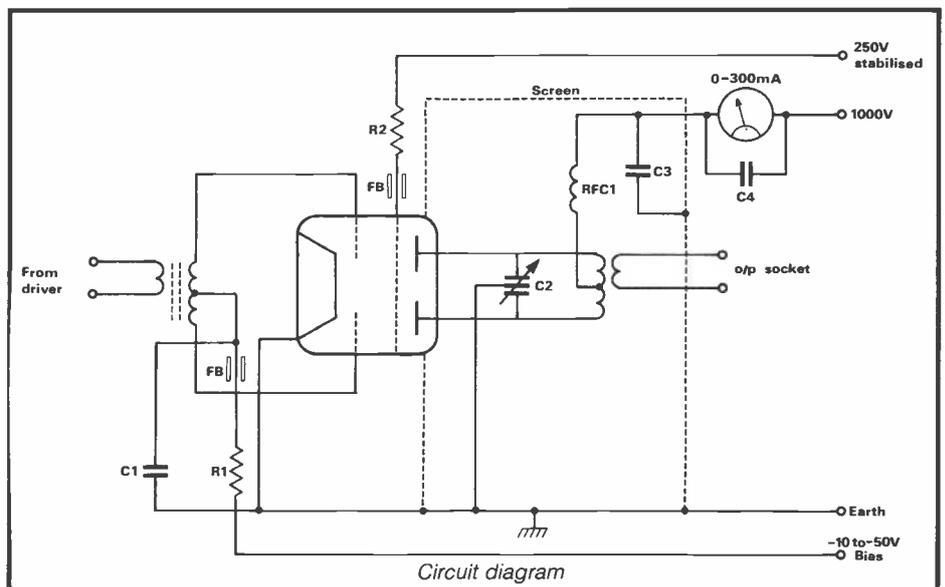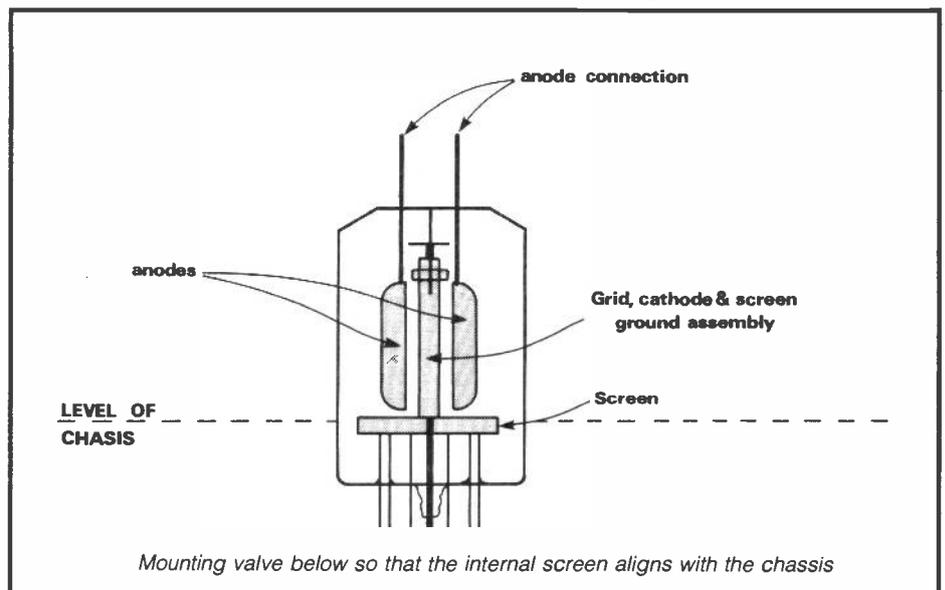

QQV06-40A

of several QQV06-40A linear amplifiers over the past few years indicate that such output powers are quite possible and practical. Some particular examples of these valves do not seem too happy at the 1200V HT level, but all seem reasonably content at around 1000V.

Many excellent articles have been written about the design of QQV06-40A amplifiers for use at the normal rated voltages. However, when the voltages are increased, the stage gain increases to something in excess of 20dB and in consequence more care has to be taken to ensure that stability is maintained.

The first stage in construction at which stability must be considered is in the physical layout. There must be maximum isolation between input and output circuits and in consequence these must be separated by either a shield or the chassis. This requirement has also been recognised by the valve designers who have fitted an internal shield between the base of the valve and the electrodes.

To ensure maximum shielding effect the valve holder must be mounted below the chassis or shield at a level which ensures the internal screen is exactly level with the chassis or screen. Furthermore the cutout through which the valve is mounted must be sufficiently large to accept the valve but without more than about 1mm clearance.

The valveholder mounted, it is then convenient to consider wiring those electrodes which must be earthed. These may be earthed individually to a single earth point on the chassis, but I have found that greater stability can be obtained by cutting a strap from an old 50gm tobacco tin, shaped such that it will join all earthed electrodes and reach down to the chassis to which it is firmly bolted (Figure 3).

The grid circuit

Most conventional published circuits show a grid circuit comprising a coil and split stator capacitor. This may be perfectly satisfactory at lower voltage levels but experience has shown that better stability is obtained if the split

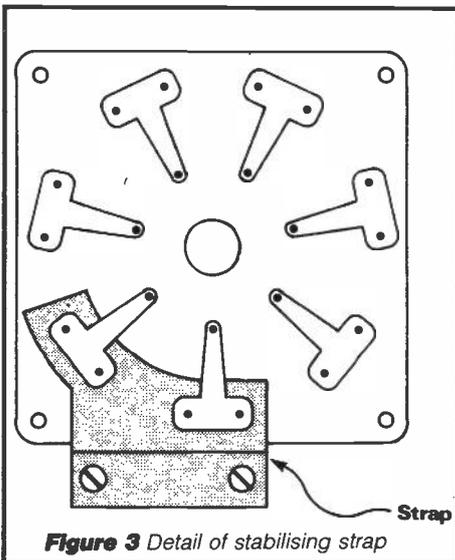


Figure 3 Detail of stabilising strap

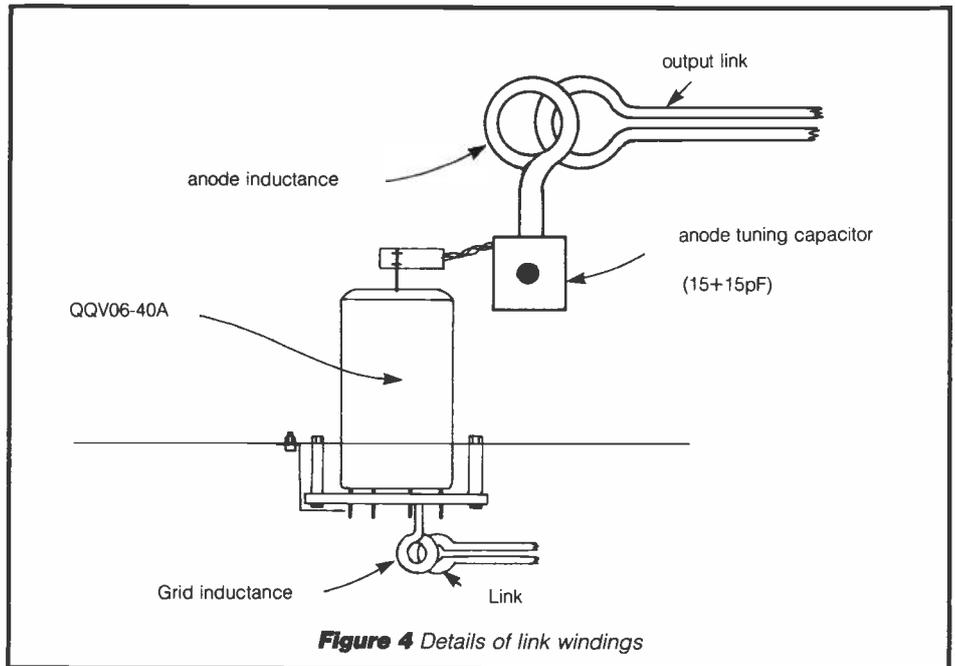


Figure 4 Details of link windings

stator capacitor is omitted and the grid inductance is resonated by the input capacity of the valve.

This is a simple operation if a grid dip oscillator is used. A coil of about six turns of 18 gauge wire is wound around a pencil, connected across the two grids and the resonant frequency determined. If the frequency is too high, squeeze the turns together; if too low, stretch the coil. If resonance cannot be obtained, remove a turn or substitute a larger coil as appropriate.

When resonance is achieved, solder a 100ohm wire wound resistor (which will later be connected to the bias supply) and the bypass capacitor to the centre point of the coil.

As a further precaution, slip a couple of ferrite beads onto the resistor lead. A wire wound resistor should be used for the resistive element and also acts as a radio frequency choke.

The screen circuit

Similarly, the screen grid should also be fed through a wire wound resistor with a couple of ferrite beads on the lead.

Under no circumstances should a bypass capacitor be fitted for to do so would upset the internal neutralisation of the valve.

The anode circuit

The anode circuit may comprise either tuned lines or a coil and split stator capacitor. There is little to choose between them. The tuned lines are reputed to be slightly more efficient, but on the other hand the coil-capacitor arrangement takes far less space. I have invariably used the latter system and found no cause for complaint.

The components used have usually been a 15 x 15pF or a 10 x 10pF split stator capacitor with a 3 turn, 1 inch inside diameter, 1½ inch long coil. The dimension of this inductance should be checked during construction and before

connecting the power supplies. With valve in position and the capacitor about half enmeshed, check the resonance of the combination in the same way as described for the grid circuit.

The link winding should be a single turn of well insulated wire. For this, I use a length of TV low loss coax with the outer insulation and braiding removed.

In an early linear a link of PVC insulated wire was used. After several months operation, during a 2 metre contest (Murphy's Law again), a loud bang and a flash announced that the insulation had failed. On inspection it was found that the insulation had melted. As the temperature within the case was quite moderate, it can only be surmised that heating due to losses within the PVC had caused the insulation to melt and eventually fail.

Power supplies

All power supplies for a QQV06-40A linear may be obtained from a single 350-0-350 or 375-0-375V transformer with a 6.3V heater winding, although, if available, it is preferable to use a separate transformer to power heater and bias supplies.

The high voltage output is obtained by fitting a bridge rectifier across the whole secondary winding. With a 350-0-350V winding this will give a peak of 990V whilst a 375-0-375V winding will give 1060V. This is smoothed by three 100µF capacitors in series, each in parallel with a suitable balancing resistor. The resultant value is 33µF at 1350V working which is more than adequate for the task. A suitable capacitor is R S Components stock number 103-890. Using these capacitors in conjunction with a 375-0-375V transformer, my power unit gives an off-load voltage of 1050V and on 200mA load is about 60 or 70V less – quite adequate regulation for the purpose.

A lower voltage for the screen supply may be obtained from the centre tap of

COMPUTER WAREHOUSE

1000's OF BARGAINS FOR CALLERS

THE 'ALADDIN'S' CAVE OF COMPUTER AND ELECTRONIC EQUIPMENT

HARD DISK DRIVES

Fully refurbished **DIABLO/DRE** series 30 2.5 Mb disk drives.
DEC RK05, NOVA, TEXAS compatible
 Front load. Free stand or rack mount
 Exchangeable type (via lid removal)
 ma3020 PSU unit for 2 drives **£125.00**
DIABLO/DRE 44-4000A/B 5+5 ex stock from **£995.00**
 1000's of spares for S30, 4000, 3200, HAWK ex stock.
 Plus in house repair, refurbishing service.
 Call for details or quotation.

EX STOCK INTEGRATED CIRCUITS

D8085AH-2	D8086	D8257-5
D8202	D8271	AM2764-3DC
74LS86	74LS112	74LS373
7407	2102-6	4116-3

CALL SALES OFFICE FOR PRICES

HOT LINE DATA BASE

DISTEL ©

THE ORIGINAL FREE OF CHARGE dial up data base.
 1000's of stock items and one off bargains.
ON LINE NOW - 300 baud, full duplex CCITT tones, 8 bit word, no parity.
01-679 1888

COMPUTER 'CAB'

All in one quality computer cabinet with integral switched mode PSU, Mains filtering, and twin fan cooling.
 Originally made for the famous **DEC PDP8** computer system costing thousands of pounds. Made to run 24 hours per day the PSU is fully screened and will deliver a massive +5v DC at 17 amps, +15v DC at 1 amp and -15v DC at 5 amps. The complete unit is fully enclosed with removable top lid, filtering, trip switch, 'Power' and 'Run' LEDs mounted on Ali front panel, rear cable entries, etc. etc. Units are in good but used condition - supplied for 240v operation complete with full circuit and tech. man. **Give your system that professional finish for only £49.95 + Carr. Dim. 19" wide 16" deep 10.5" high. Useable area 16" w. 10.5" h. 11.5" d. Also available LESS PSU, with FANS etc. Internal dim. 19" w. 16" d. 10.5" h. £19.95. Carriage & insurance £9.50.**

COOLING FANS

Keep your hot parts **COOL** and **RELIABLE** with our range of **BRAND NEW** professional cooling fans.
ETRI 99XU01 Dim. 92 x 92 x 25 mm. Miniature 240 v equipment fan complete with finger guard. **£9.95.**
GOULD JB-3AR Dim. 3" x 3" x 2.5" compact very quiet running 240 v operation. **NEW £8.95**
BUHLER 69 11.22. 8-16 v DC micro miniature reversible fan. Uses a brushless servo motor for extremely high air flow, almost silent running and guaranteed 10,000 hr life. Measures only 62 x 62 x 22 mm. Current cost £32.00. **OUR PRICE ONLY £12.95** complete with data.
MUFFIN-CENTAUR standard 4" x 4" x 1.25" fan supplied tested EX EQUIPMENT 240 v at £6.25 or 110 v at £4.95 or **BRAND NEW 240v** at £10.50. 1000's of other fans EX Stock. Call for Details. Post & Packing on all fans £1.60

SAVE £250 SUPER PRINTER SCOOP



BRAND NEW CENTRONICS 739-2

The "Do Everything Printer" at a price that will NEVER be repeated. Standard **CENTRONICS** parallel interface for direct connection to **BBC, ORIC, DRAGON** etc. Super print quality with full pin addressable graphics and 4 type fonts plus **HIGH DEFINITION internal PROPORTIONAL SPACED MODE** for **WORD PROCESSOR** applications. 80-132 columns, single sheet, sprocket or roll paper handling plus much more. Available **ONLY** from **DISPLAY ELECTRONICS** at the ridiculous price of **ONLY £199.00 + VAT** Complete with full manual etc. Limited quantity - Hurry while stocks last.
 Options: Interface cable (specify) for BBC, ORIC, DRAGON or CENTRONICS 36 way pig £12.50. Spare ribbon £3.00 each. BBC graphics screen dump utility program £8.60. Carriage and Ins. £10.00 + VAT

BUDGET RANGE VIDEO MONITORS

At a price YOU can afford, our range of **EX EQUIPMENT** video monitors defy competition!! All are for 240v working with standard composite video input. Units are pre tested and set for up to 80 col use on BBC micro. Even where **MINOR** screen burns may exist - normal data displays are unaffected.
1000's SOLD TO DATE
9" HITACHI very compact fully cased, dim. 21 cm H x 21 cm W x 22 cm D. Black and white screen **£44.95**
12" KGM 320-321, high bandwidth input, will display up to 132 columns x 25 lines. Housed in attractive fully enclosed brushed alloy case. **B/W only £32.95**
GREEN screen £39.95
24" KGM large screen black & white monitor fully enclosed in light alloy case. Ideal schools, shops, clubs etc. **ONLY £55.00**
14" BRAND NEW Novex COLOUR type **NC1414-CL**. Many exacting features such as RGB TTL and composite video input, **GREEN TEXT** key, internal speaker and audio amp. Even finished in BBC micro matching colours. Fully guaranteed. **ONLY £199.00**
 Carriage and ins on ALL videos £10.00

TRANSTEL PRINTERS

EX NEWS SERVICE compact, quality built 50 column matrix printer. Standard 5 bit serial, **BAUDOT CODE** current loop interface for connection to computer or radio receiver via simple filter network to decode and print most world-wide **NEWS, TELEX** and **RTTY** services. Supplied tested and in good condition with data, large paper roll and 50 and 75 baud xtals. **ONLY £49.95** Carr. £6.00

GE TERMIPRINTER

A massive purchase of these desk top printer - terminals enables us to offer you these quality 30 cps printers at a **SUPER LOW PRICE** against their original cost of over £1000. Unit comprises of full **QWERTY**, electronic keyboard and printer mech with print face similar to correspondence quality typewriter. Variable forms tractor unit enables full width - up to 13.5" 120 column paper, upper - lower case & standard **RS232** serial interface, internal vertical and horizontal tab settings, standard ribbon adjustable baud rates, quiet operation plus many other features. Supplied complete with manual. Guaranteed working **£130.00** or untested **£25.00**, optional floor stand £12.50 Carr & Ins £10.00

DUAL 5" DISK DRIVES

Current, quality, professional product of a major computer company, comprising 2 x 40 track **MPI** or **Shugart FULLY BBC COMPATIBLE** single sided drives in a compact, attractively styled, grey ABS structured case with internal switched mode PSU. The PSU was intended to drive both drives and an intelligent **Z80** controller with over 70 i/c's. The controller has been removed leaving ample space and current on the +, -5, +12 and -12 supply for all your future expansion requirements. Supplied tested with 90 day guarantee in **BRAND NEW** condition with cable for **BBC micro**. Ex Stock at **only £259.00** + £10.00 carr. Limited Quantity Only

TELETYPE ASR 33

DATA I/O TERMINALS
 Industry standard combined **ASCII 110** baud printer, keyboard and 8 hole paper tape punch and reader. Standard **RS232** serial interface. Ideal as cheap hard copy unit or tape prep. for **CNC** and **NC** machines. **TESTED** and in good condition. **Only £235.00** floor stand 10.00 Carr & ins £15.00

PROFESSIONAL KEYBOARD OFFER

An advantageous purchase of brand new surplus allows a great **QWERTY**, full travel, chassis keyboard offer at fractions of their original costs.
ALPHAMERIC 7204/60 full **ASCII** 60 key, upper, lower + control key, parallel TTL output plus strobe. Dim 12" x 6" +5 & -12 DC **£39.50**
DEC LA34 Uncoded keyboard with 67 quality, **GOLD**, normally open switches on standard **X, Y** matrix. Complete with 3 LED indicators & i/o cable - ideal micro conversions etc. **pcb DIM 15" x 4.5" £24.95** Carriage on keyboards £3.00

SEMICONDUCTOR 'GRAB BAGS'

Mixed **Semis** amazing value contents include transistors, digital, linear, I.C.'s triacs, diodes, bridge recs, etc. All devices guaranteed brand new full spec, with manufacturer's markings, fully guaranteed.
50+ £2.95 100+ £5.15
TTL 74 Series A gigantic purchase of an "across the board" range of 74 TTL series I.C.'s enables us to offer 100+ mixed "mostly TTL" grab bags at a price which two or three chips in the bag would normally cost to buy. Fully guaranteed all I.C.'s full spec. **100+ £6.90 200+ £12.30 300+ £19.50**

DATA MODEMS

Join the communications revolution with our range of **EX TELECOM** data modems. Made to most stringent spec and designed to operate for 24 hrs per day. Units are made to the **CCITT** tone spec. With **RS232** i/o levels via a 25 way 'D' skt. Units are sold in a tested and working condition with data. Permission may be required for connection to **PO** lines.
MODEM 2B "Hackers Special" fully fledged up to 300 baud full duplex, **ANSWER** or **CALL** modes. **AUTO ANSWER**. Data i/o via standard **RS232 25 way 'D'** socket. Just 2 wire connection to 300's line. Ideal networks etc. Complete with data, tested, ready to run at a **NEW SUPER LOW PRICE** of **ONLY £65.00 + VAT + Carr.**
MODEM 20-1 Compact unit for use with **MICRONET, PRESTEL** or **TELECOM GOLD** etc. 2 wire direct connect 75 baud transmit 1200 baud receive. Data i/o via **RS232 'D'** socket. Guaranteed working with data **£69.95**
MODEM 20-2 same as 20-1 but 75 baud receive. 1200 baud transmit **£70.00**
TRANSDATA 307A 300 baud acoustic coupler **RS232 i/o £95.00**
NEW D8L2123 Multi Standard modem selectable V.130-300 V.23 75-1200, V23 1200-75 full duplex. Or 1200-1200 half duplex modes. Full auto answer via modem or CPU. LED status indicators. **CALL** or **ANS** modes. Switchable **CCITT** or **BELL 103 & 202**. Housed in ABS case size only 2.5" x 8.5" x 9". **£286.00 + VAT**
 For further data or details on other **EX STOCK** modems contact sales office.
 Carriage on all modems £10.00 + VAT.

THE BENEFITS OF INSURANCE

Almost four months ago, on the 29th of February 1984, we, **DISPLAY ELECTRONICS** were unfortunate enough to have a serious fire at our main location, reducing a substantial part of our stock, warehouse and offices to a pile of ashes and rubble. **HOWEVER**, we had seen the adverts about the "Benefits of Insurance" and some years ago had taken comprehensive insurance cover to protect against an event such as this.
 The day after the fire we did not even have a single pen to write with, to say nothing of the non-existent showroom and burnt out warehouse with direct access to the stars via our now non-existent roof!!
 The loss of stock and damage to the premises has resulted in losses in excess of £400,000 pounds in real money - no price can value time and effort.
 We are still, although working under great difficulties, **VERY MUCH** in business. We owe this to supreme efforts by all our staff - perhaps knowing their jobs could have been at stake, stock being located at several different locations, help from business colleagues and our bank.
 To these people, I say a very loud **THANK YOU**.
 To both the mighty **PRUDENTIAL** and **GENERAL ACCIDENT** insurance Companies who from the date of our fire have **NOT** even offered or paid **A SINGLE PENNY** in compensation or have not even offered an ounce of moral support...
 To both the mighty **PRUDENTIAL** and **GENERAL ACCIDENT** insurance Companies who only answer our requests for help and information with "We are still looking at reports..." I say **"STRONG STUFF THIS INSURANCE????"**
 David Fisher, Managing Director, **DISPLAY ELECTRONICS**

66% DISCOUNT

ELECTRONIC COMPONENTS EQUIPMENT
 Due to our massive bulk purchasing programme which enables us to bring you the best possible bargains, we have thousands of I.C.'s, Transistors, Relays, Cap's, P.C.B.'s, Sub-assemblies, Switches, etc. etc. surplus to our requirements. Because we don't have sufficient stocks of any one item to include in our ads, we are packing all these items into the **"BARGAIN PARCEL OF A LIFETIME"**. Thousands of components at giveaway prices! Guaranteed to be worth at least 3 times what you pay. Unbeatable value!! Sold by weight.
2.5kls £4.25 + pp £1.25 **5kls £5.90 + £1.80**
10kls £10.25 + pp £2.25 **20 kls £17.50 + £4.75**

EX STOCK DEC CORNER

BA11-MB 3.5" Bax, PSU, LTC	£385.00
DH11-AD 16 x RS232 DMA interface	£210.00
DLV11-J 4 x EIA interface	£310.00
DUP11 Sych. Serial data i/o	£650.00
DZ11-B 8 line RS232 mux board	£650.00
LA36 Decwriter EIA or 20 ma loop	£270.00
LAXX-NW LA180 RS232 serial interface and buffer option	£130.00
LAX34-AL LA34 tractor feed	£85.00
MS11-JP Unibus 32 kb Ram	£80.00
MS11-LB Unibus 128 kb Ram	£450.00
MS11-LD Unibus 256 kb Ram	£850.00
MSC4804 Qbus (Equiv MSV11-L) 256 kb	£499.00
PDP11/05 Cpu, Ram, i/o, etc.	£450.00
PDP11/40 Cpu, 124k MMU	£1850.00
RT11 ver. 3B documentation kit	£70.00
RK05-J 2.5 Mb disk drives	£650.00
KLBJA PDP 8 async i/o	£175.00
MIB6 PDP 8 Bootstrap option	£75.00
VT50 VDU and Keyboard - current loop	£175.00

1000's of **EX STOCK** spares for **DEC PDP8, PDP8A, PDP11** systems & peripherals. Call for details. All types of Computer equipment and spares wanted for **PROMPT CASH PAYMENT**.

QQV06-40A

adjust the position of the output link. For this, an RF power meter should be placed in series with a dummy load.

Position the link about halfway into the PA coil. Without drive applied, set the anode current to about 35mA and then apply sufficient CW or FM drive to raise this to about 100mA on resonance. Note the reading on the RF meter. Switch off the HT voltages, earth the PA coil with a screwdriver and push the link another 1/8 to 1/4 inch into the coil.

Remove the screwdriver, switch on the HT voltages, check the PA tuning and again note the power output. If it has increased, repeat the process. If it has decreased, move the link in the opposite direction. Continue until maximum output is obtained. This should be in the order of 60W.

If it is found that with the link fully in, there is still insufficient coupling, substitute a link of greater diameter.

Operating conditions

The operating conditions of the QQV06-40A amplifier are set by the anode dissipation of the valve which is 40W. Thus in FM operation, as the amplifier will be operating for periods of several minutes at a time and assuming an efficiency of about 60%, the maximum input power should be about 100W, ie 100mA anode current.

In CW operation, however, the valve is

only operating in 'key-down' conditions for about one third of the time, and it might be thought that the input could be increased in proportion.

This, however, is not so, for this would be exceeding the safe cathode emission of the valve. 200mA would be within this limit, at which level the output would be in the order of 120W.

In both CW and FM operation, efficiency, cooling and valve life will be improved if maximum bias is applied with the drive level increased accordingly. In either case, several milliamps of grid current will be flowing.

For SSB operation, adjust the bias for 30-35mA standing anode current under no-drive conditions, and set the drive level such that speech peaks cause the grid meter to just flicker upwards. At this drive level the anode current meter will probably be kicking to about 150-180mA. This does not indicate, however, that the input is 150-180W, for these peaks are of such short duration that the PA meter is unable to follow.

Similarly, the RF output meter will only be following the average output level, which can vary widely with the type of meter, the characteristics of the voice and the level of processing employed.

As a very broad rule of thumb, on unprocessed speech the RF output meter will normally indicate in the order of 30-40% of peak output.

The thought of exceeding published valve ratings may well give rise to concern regarding valve life. In my experience, however, such worries are groundless, for the QQV06-40A valve in use in my present linear has been used in this and previous linears for the past six years, and I know of several operators whose experience is similar.

PARTS LIST

- R1, R2, R3 37Kohm
- R4 47Kohm, 2W
- R5 8.2Kohm, 11W
- R6, R7 37Kohm, 5W
- R8 6Kohm, 15W (see text)
- R9 1000 ohm W/W Pot
- R10 100 ohm
- F1 5A
- C1-C9 100µF, 450V wkg
- C8 330µF, 63V wkg
- T1 350-0-350V or 375-0-375V, 125mA
- T2 250-0-250V, 60mA
- LP1 6V, 0.3A
- SW1 SPST 240V 5A
- SW2 SPST 240V 5A
- V1 VR150/30
- V2 VR105/30

Rectifiers associated with T1 - 1500V PIV

Rectifiers associated with T2 - 750V PIV

TRANSISTORS

BC107/8/9	- 12p	BC184L	- 8p	BFY50,51,52	- 20p
BC147/8/9	- 10p	BC212,212L	- 8p	BFX88	- 15p
BC157/8/9	- 10p	BC327,337,337L	- 10p	BSX19	- 14p
BC547/8/9	- 7p	BD135,136	- 25p	BSX20	- 15p
BC557/8/9	- 7p	BD137,138,139	- 25p	2N2926	- 7p
BC182L	- 8p	BF195,7	- 10p	2N3055	- 50p
BC183	- 8p	BCY70	- 15p	TIP31A,32A	- 25p

ELECTROLYTIC CAPACITORS. (Mfds/Volts)

1/25, 1/50, 2.2/25, 2.2/50, 4.7/25, 4.7/50, 10/16, 10/25, 10/505p
22/16, 22/25, 22/50, 47/16, 47/25, 47/50, 33/10 - 6p, 100/16, 100/257p
100/50 - 12p, 100/100 - 14p, 220/16 - 8p, 220/25, 220/5010p
470/16, 470/25 - 11p, 470/35 - 12p, 470/40 - 15p, 1000/1615p
1000/35 - 22p, 1000/40 - 35p, 2200/10 - 8p, 2200/2535p

Carbon Film resistors 1/4W 5% E24 series 0.51R to 10MO 1p

100 off per value - 75p, even hundreds per value totalling 1000 £7.00

Metal Film resistors 1/4W 10R to 1MO 5% E12 series - 2p, 1% E24 series 3p

Mixed metal/carbon film resistors 1/2W E12 series 1R0 to 10MO 1 1/2p

Miniature polyester capacitors 250V working for vertical mounting

01, 015, 022, 033, 047, 068 4p. 01 5p. 015, 022 6p. 0.33 & 0.47 8p

Mylar (polyester) capacitors 100V working E12 series vertical mounting

1000p to 8200p - 3p. 01 to 068 mfd - 4p. 0.1 5p. 0.12 & 0.15 6p

Subminiature ceramic plate capacitors 100V wkg vertical mounting. E12 series

2% 1.8 pf to 47 pf - 3p. 2% 56 pf to 330 pf - 4p. 10% 390p - 4700p 4p

Polystyrene capacitors 63V working E12 series long axial wires

10 pf to 820 pf - 3p. 1000 pf to 10,000 pf - 4p. 12,000 pf 5p

DIODES (p.i.v./amps)

75/25mA 1N4148 2p. 800/1A 1N4006 6p. 400/3A 1N5404 14p. 115/15mA OA91 6p
 100/1A 1N4002 4p. 1000/1A 1N4007 7p. 60/1.5A S1M1 5p. 100/1A bridge 25p
 400/1A 1N4004 5p. 1250/1A BY127 10p. 30/45mA OA90 6p. 30/15A OA47 8p
 Zener diodes E24 series 3W3 to 33V 400 mW - 8p. 1 watt 12p
 L.E.D's 3 & 5mm Red 10p. Green, Yellow 14p. Grommets 3mm - 1 1/2p, 5mm 2p
 20mm fuses 100mA to 5A Q/blow 5p. A/surge 8p. Holders p.c. or chassis 5p
 High speed p.c. drills 0.8, 1.0, 1.3, 1.5, 2.0mm - 22p. Machines 12V d.c. £6.00
 HELPING HANDS 6 ball joints and 2 croc clips to hold awkward jobs £4.50
 AA/HP7 Nicad rechargeable cells £1.50 pair. Universal charger unit £6.00
 Glass reed switches with single pole make contacts - 8p. Magnets 12p
 Ranges of tantalum electrolytic caps at competitive prices.
 All prices are inclusive of VAT. Postage 20p (free over £5). Lists Free.

THE C. R. SUPPLY CO

127 Chesterfield Rd, Sheffield S8 0RN

Return posting

WOOD & DOUGLAS

* NEW CATALOGUE * NEW PRODUCTS * NEW TELEPHONE NUMBER * NEW PRICES *
 OUR FULL current product range is listed below but keep in touch at rallies and exhibitions throughout the Summer for our latest developments for you the active amateur.

Package Prices	Kit	Package Prices	Kit
1. 500mW TV T/mit (70FM05T4 + TVM1 + PF433).....	35.00	8. 2M Linear/Pre-amp 25W (144PA4/S + 144LIN25S).....	42.00
2. 500mW TV T/ceive (As 1 + TVUP2 + PSI 433).....	60.00	9. 70cms Synth 10W T/ceive (R5 + SY + AX + MOD + SSR + 70FM10).....	150.00
3. 10W TV T/mit (As 1 + 70FM10 + BDX33).....	65.00	10. 2M Synth 10W T/ceive (R5 + SY + SY2T + SSR + 144FM10A).....	120.00
4. 10W TV T/ceive (As 2 + 70FM10 + BDX33).....	30.00	11. 2M Crystal Cont'd 10W T/ceive (R5 + T3 + BPF + 144FM10 + SSR).....	85.00
5. 70cms 500mW FM T/ceive (70T4 + 70R5 + 1.5W O/P).....	75.00	12. 70cms Linear/Pre-amp (70LIN10 + 70PA2/S).....	45.00
6. 70cms 10W FM T/ceive (As 5 + 70FM10).....	105.00		
7. 2M Linear/Pre-amp 10W (144PA4/S + 144LIN10B).....	40.00		

70cms EQUIPMENT	CODE	ASSEM-BLED	KIT	2M EQUIPMENT	CODE	ASSEM-BLED	KIT
Transceiver Kits and Accessories				Transceiver Kits and Accessories			
FM T/mitter (0.5W)	70FM05T4	48.00	28.75	FM Transmitter (1.5W)	144FM2T3	39.35	26.30
FM Receiver (with PIN RF c/o)	70FM05R5	65.40	45.80	FM Receiver (with PIN RF c/o)	144FM2R5	65.50	47.20
T-mitter 6 Channel Adaptor	70MCO6T	21.30	14.25	Synthesiser (2 PCB's)	144SY25B	78.75	60.05
Receiver 6 Channel Adaptor	70MCO6R	25.20	17.90	-ditto- Multi/Amp	SY2T	27.80	20.65
Synthesiser (2 PCB's)	70SY25B	88.00	62.25	Bandpass Filter	BPF 144	6.50	3.30
-ditto- Transmit Amp	A-X3U-08F	34.15	22.10	PIN RF Switch	PSI 144	7.55	5.35
-ditto- Modulator	MOD 1	8.95	5.50	Power Amplifiers (FM/CW Use)			
Bandpass Filter	BPF 433	6.50	3.30	1.5W to 10W (No c/o)	144FM10A	24.15	18.50
PIN RF Switch	PSI 433	7.55	5.35	1.5W to 10W (Auto-c/o)	144FM10B	38.71	28.25
Converter (2M or 10M i.f.)	70RX2/2	27.10	20.10	Linears			
TV Products				1.5W to 10W (SSB/FM) (Auto c/o)	144LIN10B	38.40	28.50
Receiver Converter (Ch 36 Output)	TVUP2	27.50	22.80	2.5W to 25W (SSB/FM) (Auto c/o)	144LIN25B	40.25	29.95
Pattern Generator (Mains PSU)	TVPG1	42.25	36.50	10W to 25W (SSB/FM) (Auto c/o)	144LIN25C	44.25	32.95
TV Modulator (For Transmission)	TVM1	9.85	5.75	Pre-Amplifiers			
Ch 36 Modulator (For TV Injection)	TVMOD1	9.80	5.50	Low Noise, Miniature	144PA3	8.60	7.40
Power Amplifiers (FM/CW Use)				Low Noise, Improved Performance	144PA4	12.86	8.40
50mW to 500mW	70FM1	18.45	12.80	Low Noise, RF Switched, Full c/o	144PA4/S	24.30	15.30
500mW to 3W	70FM3	23.45	17.80	GENERAL ACCESSORIES			
500mW to 10W	70FM10	41.45	33.45	Toneburst	TB2	6.70	4.25
3W to 10W	70FM3/10	23.95	18.30	Piptone	PT3	7.50	4.45
10W to 40W	70FM40	65.10	52.35	Kaytone	PTK3	8.75	6.05
Combined Power Amp/Pre-Amp (Auto c/o)	70PA/FM10	56.60	40.15	Relayed Kaytone Regulator (12V, low differential)	REG1	6.95	4.40
Linears				Solid State Supply Switch	SSR1	5.85	3.70
500mW to 3W (Straight Amp, no c/o)	70L13/LT	27.90	19.90	Pre-Amplifier	MPA2	6.10	3.50
3W to 10W (Auto c/o)	70L13/10E	41.05	30.15	Reflectometer	SWR1	6.35	3.50
1W to 7W (Auto c/o)	70LIN10	44.25	32.50	CW Filter	CWF1	8.55	5.80
Pre-Amplifiers				TV Filter (Boxed)	HPF1	5.95	—
Bipolar Miniature (14dB)	70PA2	8.10	6.50	FM TV MODULES			
MOSFET Miniature (14dB)	70PA3	9.65	7.50	50mW 420MHz Source (Video Input)	UFM01	26.95	19.80
RF Switched (30W)	70PA2/S	24.25	15.25	50MHz i.f. Processor	VIDIF	54.25	38.95
GaAs FET (16dB)	0PA5	20.10	12.80	Varactor Multiplier (Boxed)	WDV400/1200	63.95	—
GM EQUIPMENT							
Converter (2M i.f.)	6RX2	28.40	20.80				

Further details on our product range will gladly be forwarded on receipt of an A5 size SAE. Technical help is available by phone (NEW NUMBER) during normal office hours. Kits are usually available by return of post but please allow 28 days for unforeseen delays. Please add 75p to your total order for postage and handling. Credit card orders are gladly accepted, please give us a call.

ANYONE CAN SEE A KIT... REPUTATION SELLS OURS

Unit 13, Youngs Industrial Estate
 Aldermaston, Reading RG7 4PQ
 Tel: 07356 71444; Tx: 848702



DATA FILE

Ray Marston presents a further selection of practical IC audio power amplifier circuits in this concluding part of his special 2-part feature.

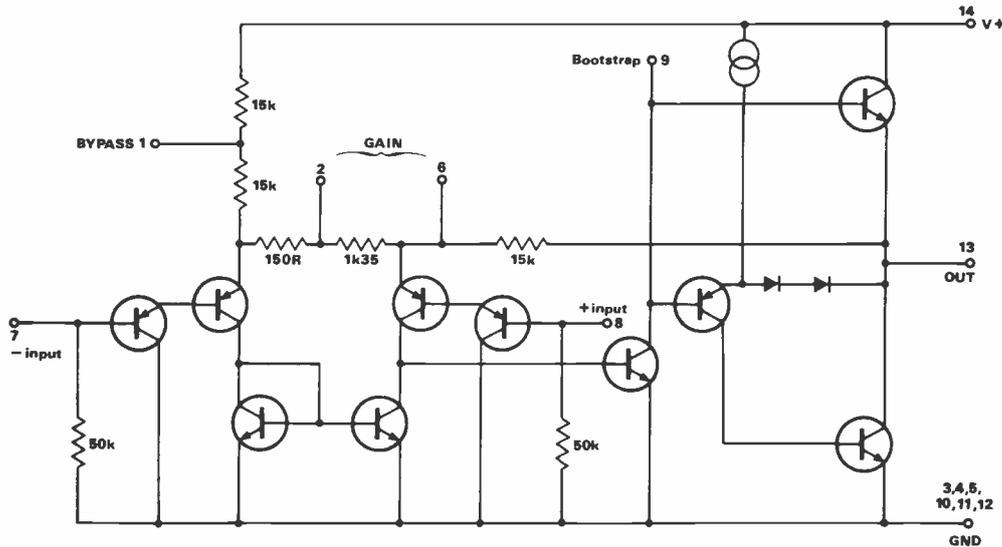


Figure 1a Internal circuit and pin connections of the LM390 1 watt battery-operated audio power amplifier

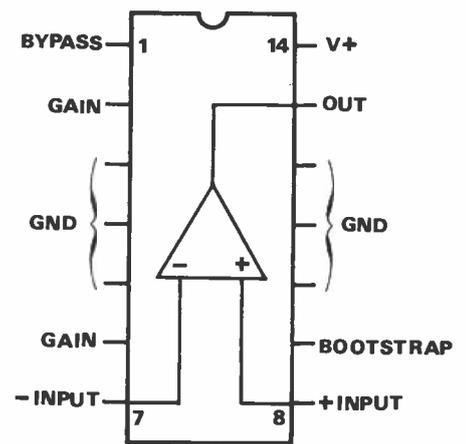


Figure 1b Pin layout of LM390

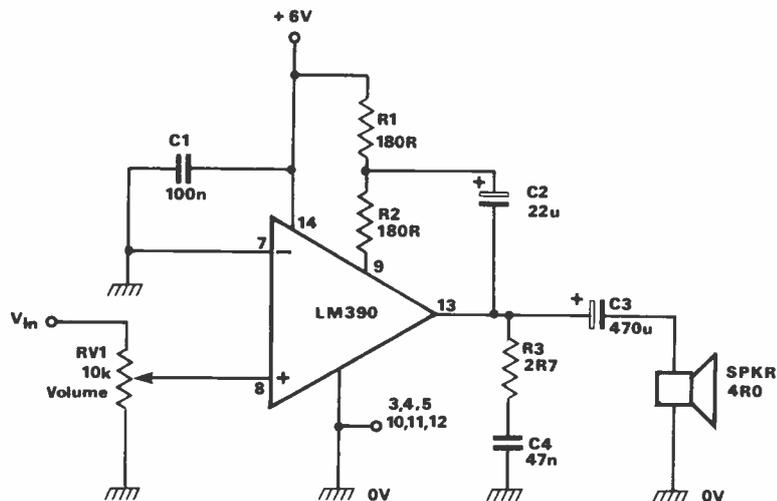


Figure 2 LM390 1 watt amplifier with $A_v=20$

LM390 circuits

The LM390 is described in the manufacturer's literature as a '1 watt battery operated audio power amplifier', and is optimised for operation with 6V to 9V power supplies (10V maximum): specifically, the IC can feed 1W into a 4R0 load when powered from a 6V supply.

Figure 1a shows the internal circuit and pin connections of this IC, which is internally very similar to the LM388 (described last month) but has its output stage modified to give the maximum possible output voltage swing. The device is housed in a 14-pin DIL package with an internal heatsink connected to pins 3-4-5 and 10-11-12 (Figure 1b).

The overall voltage gain of the LM390 is internally set at x20, but can be increased to x200 by wiring a shunt capacitor between pins 2 and 6. The IC inputs are ground referenced, and the output stage automatically self-biases to a quiescent value of half-supply volts when the output stage of the IC is suitably dc-biased via external resistors wired between pins 9 and 14.

Figures 2 to 6 show some practical applications of this IC. Figure 2 shows one way of using the LM390 as a 1W amplifier driving a 4R0 load from a 6V supply. Here, R1 and R2 are wired in series between the positive supply line and pin 9 of the IC, to give dc biasing to

the output stage of the IC. Note that the R1-R2 junction is boot-strapped from the output of the IC via C2, to raise the ac-impedance of R2 to a value far greater than its dc value.

The overall voltage gain of the LM390 is internally determined in the same way as in the LM388, and thus equals x20 in the Figure 2 circuit.

Figure 3 shows how the gain can be increased to x200 by simply wiring C5 between pins 2 and 6.

Figure 4 shows an alternative way of using the LM390. Here, dc current is fed to pin 9 of the IC via the speaker and R1. Note here that R1 is boot-strapped via C2, and that this circuit therefore gives a

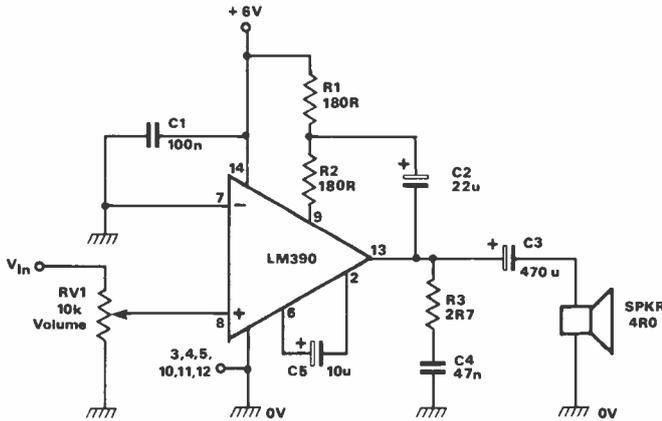


Figure 3 LM390 1 watt amplifier with $A_v = 20$

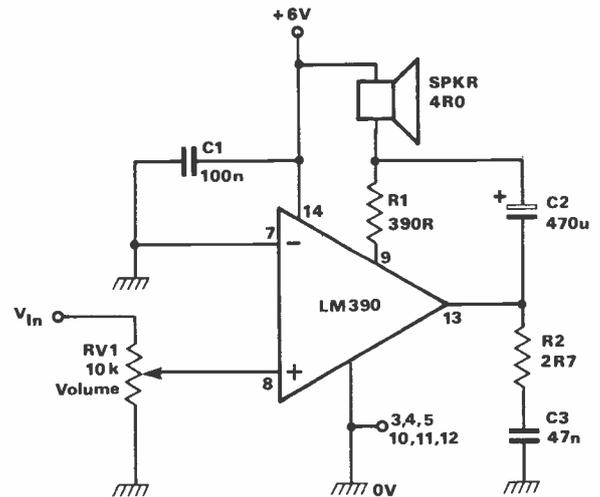


Figure 4 LM390 1 watt amplifier with $A_v = 20$ and load returned to +ve supply


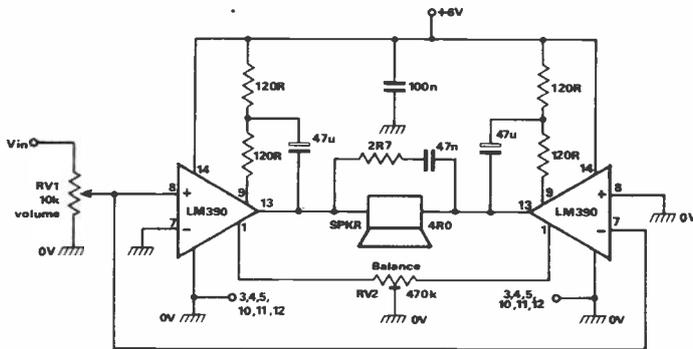


Figure 5 LM390 bridge amplifier delivers 2.5 watts into 4R0 load

Figure 6 LM390 based intercom

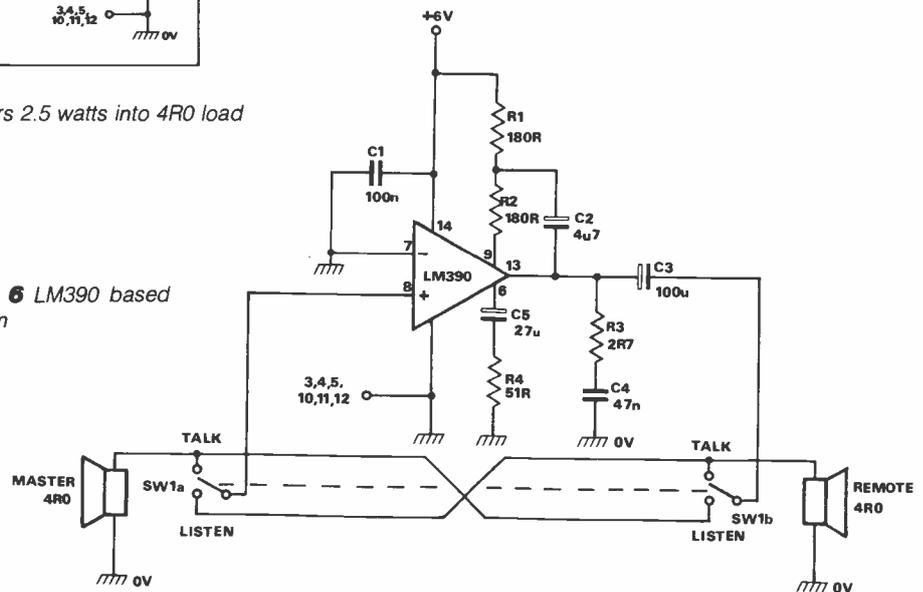

performance similar to that of *Figure 2*, but does so with a saving of two components.

Figure 5 shows how to connect a pair of LM390 ICs in the bridge configuration, to provide 2.5W of drive to a direct-coupled 4R0 load when using a 6V supply. Pre-set pot RV2 is used to balance the quiescent outputs of the two ICs and thus minimise the quiescent current consumption of the circuit.

Finally, *Figure 6* shows how to use a single LM390 IC to make a simple 2-way intercom circuit. Note here that C5-R4 are used to provide the IC with an overall voltage gain of $\times 300$ ($= 15K/51R$).

Before leaving the LM390, note that

this IC has a fairly poor ripple-rejection performance, and if any problems are met in this respect they can usually be overcome by wiring a 10μF (or larger) capacitor between pin-1 and ground. Also note in *Figures 2* to *6* that the 2R7 resistor and 47nF capacitor wired in series across the output of the IC form a Zobel network, to enhance circuit stability, and may be eliminated in some applications.

LM383 Circuits

The LM383 (*Figure 7*) is described in the manufacturer's literature as an 8W audio power amplifier IC. This device is specifically designed for use in auto-

mobile applications, in which the 'running' supply voltage has a nominal value of 14.4V, and at this voltage the IC can in fact typically deliver 5.5W into a 4R0 load or 8.6W into a 2R0 load. In reality, the IC will operate with any supply voltage in the range 5V to 20V, can supply peak output currents of 3.5 amps, and has a current-limited and thermally-protected output stage.

The LM383 is housed in a 5-pin package, as shown in *Figure 7*, and is a very easy device to use.

Figure 8 shows how to wire the device as a 5.5W amplifier for use in automobiles. Here, the closed-loop voltage gain is set at $\times 100$ via the R1-R2-C3

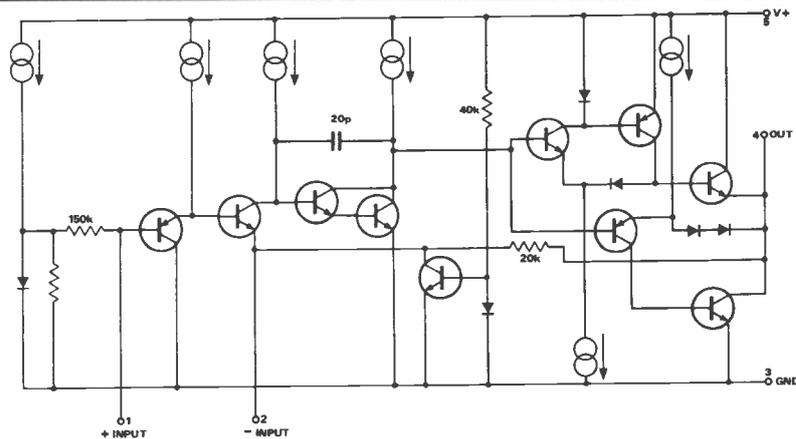


Figure 7 Internal circuit and pin connections of the LM383 8 watt audio power amplifier IC

feedback network, and the IC is operated in the non-inverting mode by simply feeding the input signal to pin-1 via C1. Capacitors C2 and C4 are used to ensure the high-frequency stability of the IC, and it is vital that C4 be wired as close as possible between pins 3 and 4.

Figure 9 shows how a pair of LM383 ICs can be connected as a 16W bridge amplifier for use in automobiles. Pre-set pot RV1 is used to balance the quiescent output voltages of the two ICs and to thus minimise the quiescent operating current of the circuit.

LM2002 (TDA2002) circuits

The LM2002 (Figure 10) is described as an 8W audio power amplifier IC, and is actually a direct equivalent of the popular TDA2002 IC.

Like the LM383, the LM2002 is specifically designed for use in automobile applications, in which it can typically deliver 5.2W into a 4R0 load or 8.0W into a 2R0 load. The LM2002 can in practice operate with any supply voltage in the range 5V to 20V, can supply peak output currents of 3.5 amps, and has a current-limited and thermally-protected output stage.

The LM2002 is internally very similar to the LM383, but uses a slightly less efficient output stage, with a consequent slight reduction in the available output power into a given load. The device is housed in a 5-pin package, as shown in Figure 10, and is a very easy device to use.

Figure 11 shows how to wire the LM2002 as a 5.2 W audio amplifier for use in automobiles, with a closed-loop voltage gain set at x100 via R1-R2-C3. Note that C4 and R3 help ensure the high frequency stability of the IC, and it is vital that these components are wired as close as possible between pins 3 and 4.

Figure 12 shows how to wire a pair of LM2002 (or TDA2002) ICs as a 16W bridge amplifier for use in automobiles. Balance control RV1 is set to give minimum quiescent operating current.

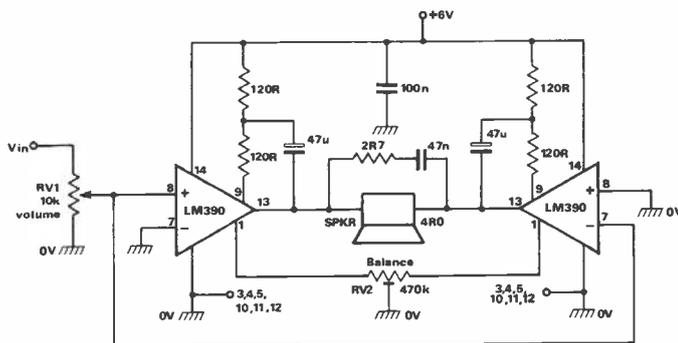


Figure 8 LM383 5.5 watt amplifier for use in automobiles

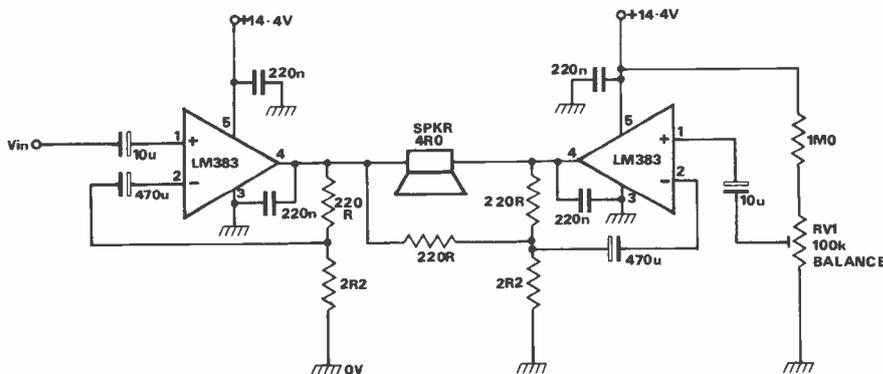


Figure 9 LM383 16 watt bridge amplifier for use in automobiles

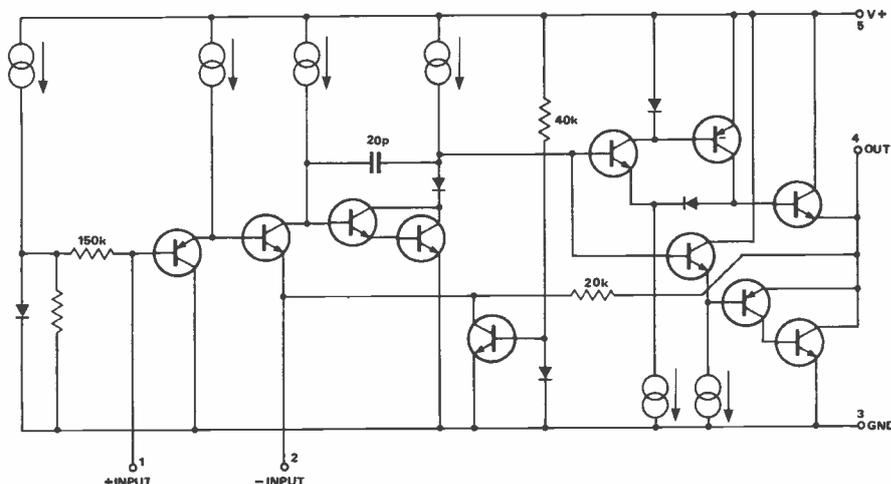


Figure 10 Internal circuit and pin connections of the LM2002 (TDA2002) 8 watt audio power amplifier IC

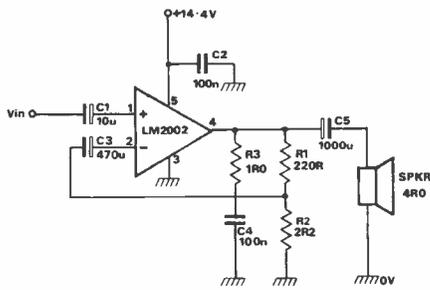


Figure 11 LM2002 5.2 watt amplifier for use in automobiles



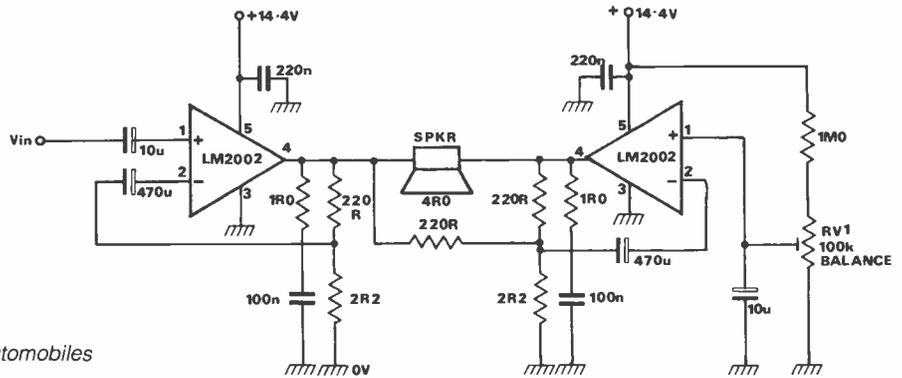


Figure 12 LM2002 16 watt bridge amplifier for use in automobiles

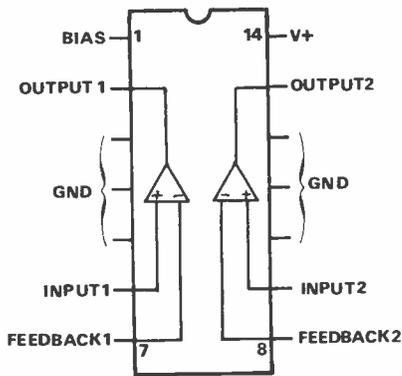

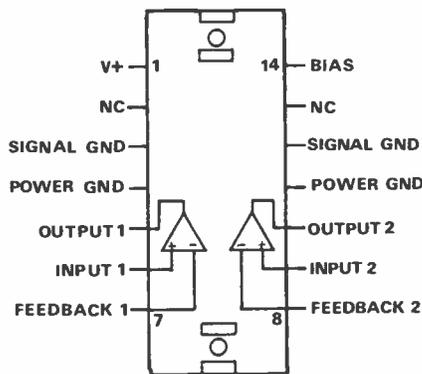LM377 DUAL 2WATT AMPLIFIER
LM378 DUAL 4WATT AMPLIFIER



LM379 DUAL 6WATT AMPLIFIER


V+	LM377	LM378	LM379	MAX O/P POWER PER CH. INTO:	
				8R0	16R
12V	LIMIT TO 2.5W PER CHANNEL	LIMIT TO 5W PER CHANNEL	LIMIT TO 6W PER CHANNEL	1.6W	1W
16V				2.2W	1.5W
18V				3W	1.8W
20V				3.8W	2.4W
22V				4.6W	2.8W
24V				5.4W	3.6W
26V				6W	4.2W
28V				7W	5W
30V				—	5.5W

Figure 14 Approximate performance characteristics of the LM377/378/379 dual amplifiers

Figure 13 Outline and pin notations of three popular 'dual' amplifiers

	IC1		
	LM377	LM378	LM379
V+ (max)	18V	24V	28V
P _{OUT} / Ch	2W	3W	4W
e _{IN} (max)	80mV	100mV	115mV
A _v approx	50	50	50
Z _{IN}	22k	22k	22k

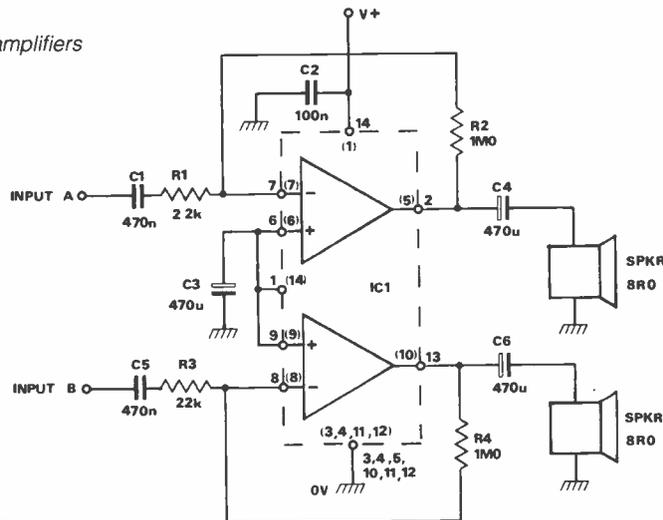TYPICAL PERFORMANCE OF THE INVERTING STEREO AMPLIFIER



NOTE:—LM379 PIN NUMBERS ARE SHOWN IN PARENTHESES

Figure 15 Simple inverting stereo amplifier using the LM377, LM378, or LM379 dual amplifier ICs

LM377/378/379 circuits

National Semiconductors produce a range of 'dual' power amplifier ICs for use in stereo amplifier and bridge-configured mono amplifier applications. The best known of these devices are the LM377 dual 2W, the LM378 dual 4W, and the LM379 dual 6W amplifiers. Figure 13 shows the outlines of these devices, and Figure 14 shows the approximate performance characteristics of the three ICs.

The LM377/378/379 range of ICs all have similar internal circuits, with high-impedance differential input stages and fully-protected output stages, and differ primarily in their voltage/power ratings

and in their packaging styles. It should be noted that the input stages of these ICs are intended to be dc-biased to half-supply volts, and a bias generator is built into the ICs for this purpose.

The LM377/378/379 range of ICs are very easy to use. Figure 15 shows the connections for making a simple inverting stereo amplifier powered from a single-ended power supply. Here, the amplifier is biased by connecting each non-inverting input pin to the BIAS terminal (pin-1 on the LM377 or LM378, or pin-14 on the LM379), and the closed-loop voltage gain of each amplifier is set at approximately x50 by the ratio of R₂/R₁ or R₄/R₃. The table shows the typical

performance of this circuit.

Figure 16 shows how the above circuit can be modified for use as a non-inverting amplifier. The voltage gain of each half is again set at roughly x50, in this case via the ratio of R₄/R₃ or R₆/R₅, and the non-inverting input terminals are biased via the internal network of the IC.

Figure 17 shows how the above 'non-inverting' amplifier circuit can be modified for use with split power supplies. Note in this case that the internal BIAS generator is ignored, and that the non-inverting input of each amplifier is dc-coupled to the ground 'half-supply' point via volume control RV1.

Figure 18 shows a highly effective way

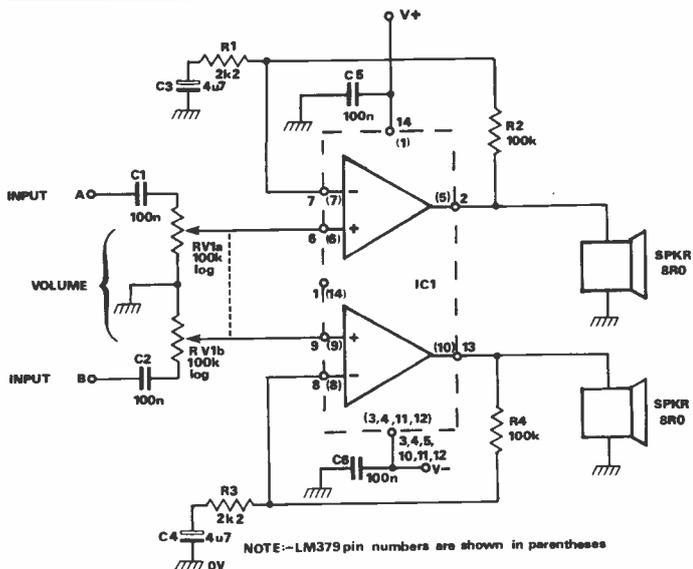


Figure 16a Non-inverting stereo amplifier using a single-ended supply

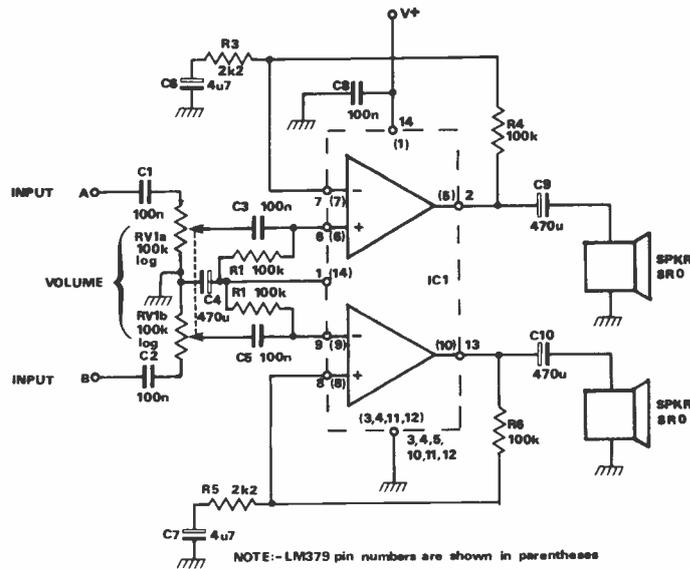


Figure 17a Non-inverting stereo amplifier using a split supply

V+	IC1	P _{OUT}
18V	LM377	2W/Ch
24V	LM378	3W/Ch
28V	LM379	4W/Ch

Figure 16b Power ratings

V+	V-	IC1	P _{OUT}
+9V	-9V	LM377	2W/Ch
+12V	-12V	LM378	3W/Ch
+14V	-14V	LM379	4W/Ch

Figure 17b Power ratings

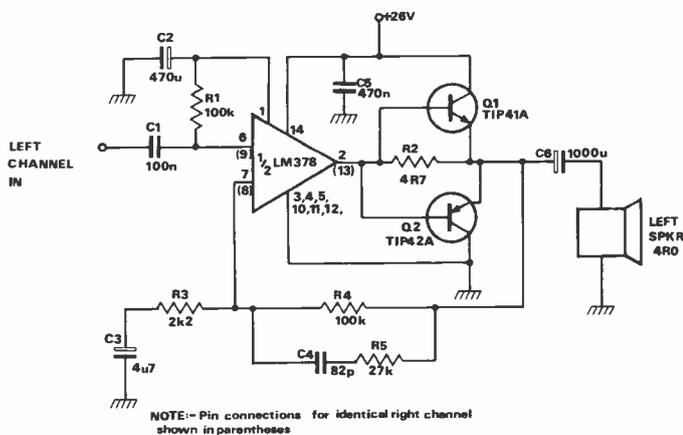


Figure 18 One channel of a 15 watt per channel stereo amplifier using a single-ended supply

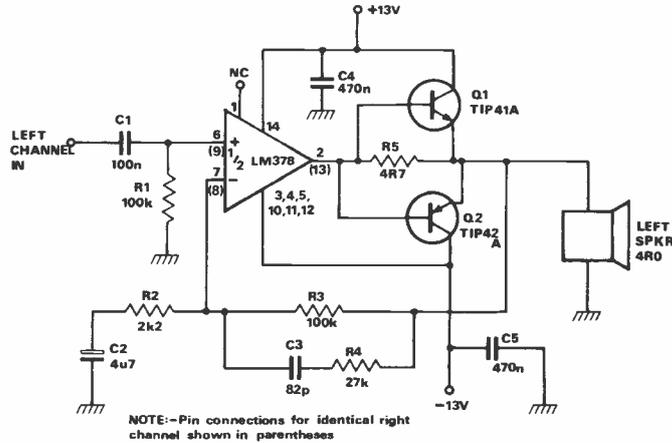


Figure 19 One channel of a 15 watt per channel stereo amplifier using a split supply

of boosting the available output power of one half of the LM378 to 15W. This remarkably simple circuit generates a typical THD of only .05% or so at an output power level of 10W. At very low power levels, Q1 and Q2 are inoperative and power is fed directly to the speaker via R2: at higher power levels Q1 and Q2 act as a normal complementary emitter follower and provide most of the power drive to the speaker. R2 and Q1-Q2 are effectively wired into the negative feedback network of the circuit, which consequently generates negligible cross-over distortion.

Figure 19 shows how the above circuit can be adapted for use with a split power

supply. This circuit produces negligible output dc-offset, thus enabling the speaker to be direct-coupled to the output of the circuit.

Finally, Figure 20 shows how the two halves of a LM377, LM378 or LM379 can be used to make a bridge-configured 'mono' amplifier which can feed relatively high power levels into a direct-coupled speaker load.

The LM1877 IC

The LM1877 dual 2W power amplifier IC is an improved pin-for-pin replacement for the LM377, and should be used in place of the latter IC whenever possible. The LM1877 gives an improved perform-

ance in terms of very low cross-over distortion, very high input impedance, and a high slew rate, but has a slightly poorer ripple-rejection performance, and typically consumes a higher quiescent current than the LM377.

In the remainder of this article, Ray Marston gives very brief descriptions of a few popular audio power amplifier ICs, complete with one or more 'application' circuits for each IC.

The TBA810S

This IC can supply several watts of audio power output, and is particularly well suited for use in automobile

GREAT OFFERS FROM SCARAB SYSTEMS

And now, from U.K.'s leading radio software house, come two professionally produced items which are a *must* for the radio amateur.

Split screen Spectrum RTTY (48K only)

This exciting program and special interface board allows you to compile your answer while still in receive mode. **£37.50** (fully assembled and tested.)

MPTU-1 tone encoder/decoder

This phase lock loop circuit is 100% reliable and extremely sensitive. **£69.70** (all plugs supplied).



SCARAB SYSTEMS

39 Stafford St, Gillingham, Kent. ME7 5EN Tel: (0634) 570441

Please send me:

Spectrum split screen 48K £37.50 MPTU-1 RTTY/AMTOR terminal unit £69.70

Free Details of other equipment and programs

I enclose a cheque/postal order for

I wish to use my Access/Visa

Name

Address

Telephone

Signature

REW I understand that, if I am not fully satisfied, I can return the equipment with full reimbursement.



VELLEMAN-KITS

High quality range of electronic kits for serious amateurs, qualified engineers and training schools and colleges

NEW INTERFACE SYSTEM FOR SINCLAIR ZX81 and SPECTRUM COMPUTERS:

K2615	Motherboard for ZX81	£25.69
K2616	Motherboard for Spectrum	£25.69
K2609	DC Output board	£19.01
K2610	A/D Converter	£28.26
K2611	Opto coupler input board	£20.66
K2614	Centronics interface	£30.83
K2618	D/A converter	£24.66

NEW KITS NOW AVAILABLE


K2594	Zero Cross Programmable timer	£11.41
K2598	Car Amplifier	£15.41
K2600	2 Amp dimmer	£5.32
K2601	Stroboscope	£10.79
K2602	4 channel running light with music modulator. £20.55	
K2606	LED audio power meter	£12.48

SEND FOR FREE ILLUSTRATED POSTER OF COMPLETE RANGE AND LIST OF STOCKISTS from address below:



VELLEMAN (UK) LTD.

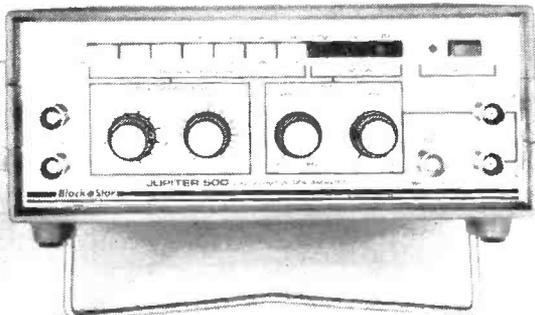P.O. Box 30, St Leonards on Sea
East Sussex TN35 7NH
Tel: 0424 753246



FUNCTION GENERATOR 0.1Hz - 500kHz

- * Sine, Square, Triangle, TTL
- * Accuracy typically 1% of output
- * Typically 0.02Hz - 700kHz
- * 7 switched ranges with coarse and fine frequency controls
- * $\pm 30V$ output capability
- * Variable DC offset
- * External A.M. facility
- * External sweep facility
- * Short circuit protection all outputs

JUPITER 500 (inc. P & P and VAT) £128.80


Colour leaflet with specifications and prices available from:

BLACK STAR LTD, (Dept REW) 9A Crown Street, St. Ives, Huntingdon, Cambs. PE17 4EB, England. Tel: (0480) 62440 Telex: 32339



Designed and manufactured in Britain

Black★Star

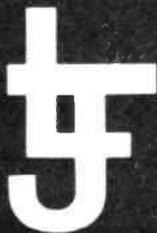

**Microsystems
for Education
and Training**


With the pace of technological growth accelerating a greater need for highly trained Design and Technician Personnel is being generated.

In recognition of this growing need L.J. Electronics offer a range of microsystems designed to aid understanding through hands-on experience. Robustly made to a high standard, all L.J. equipment is supported by fully comprehensive instruction manuals that provide details on hardware, software and experiments.

L.J. Microsystems form the basis of a completely structured course that can be divided into the following areas:


- Microelectronic Systems
- Microprocessor Systems
- Robotics

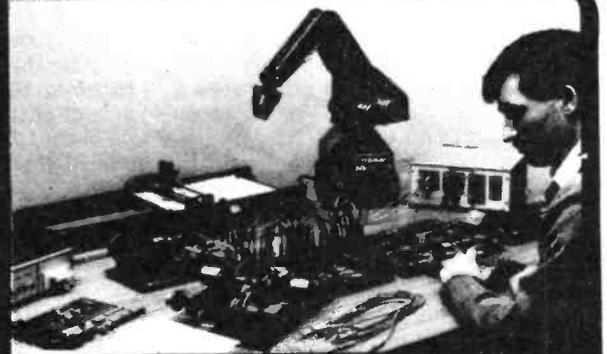To find out more about L.J. Microsystems send for our catalogue:



L.J. Electronics Ltd.

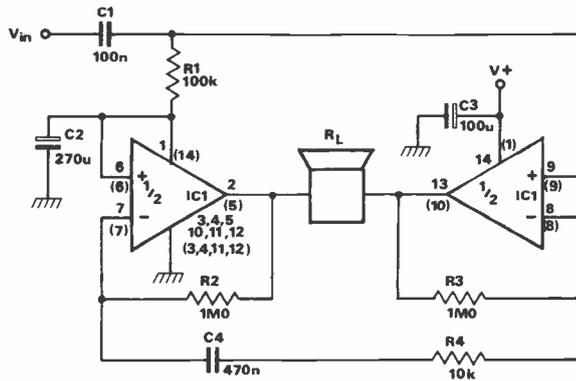Francis Way, Bowthorpe Industrial Estate, Norwich NR5 9JA.
Telephone: (0603) 748001 Telex: 975504.



NOTE:- LM379 Pin numbers are shown in parentheses

Figure 20 Bridge amplifier circuit using dual-amplifier ICs

IC1	V+	RL	P _{OUT}
LM377	14V	8R0	4W
LM378	22V	16R	8W
LM379	28V	16R	12W

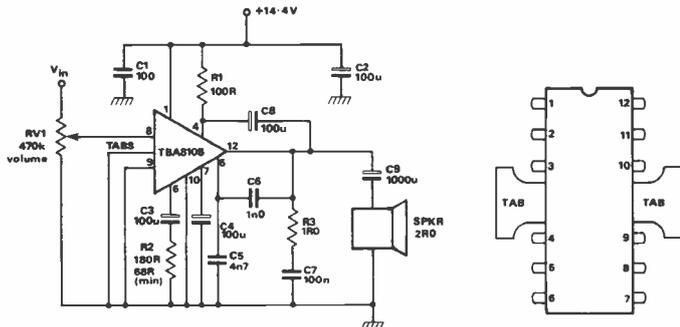


Figure 21 TBA810S 7 watt amplifier for use in automobiles

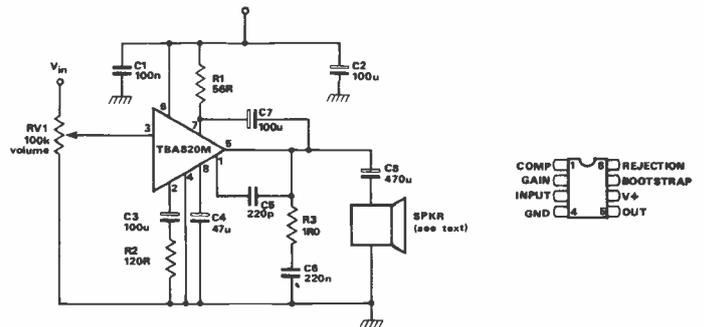


Figure 22 TBA820M low-power audio amplifier circuit

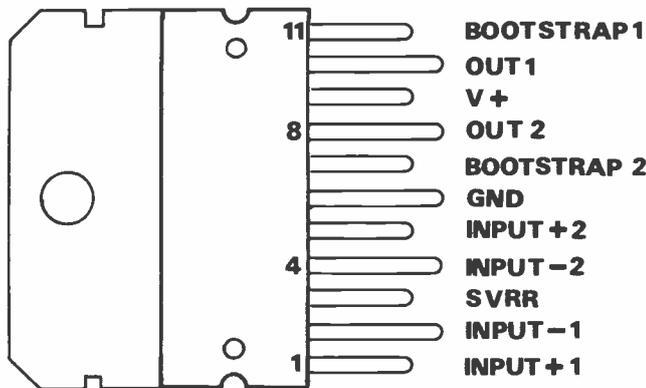


Figure 23a Pin layout

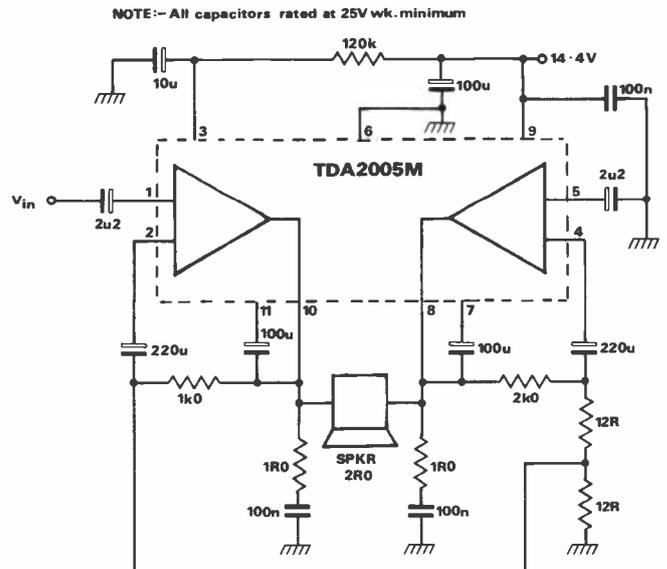


Figure 23b TDA2005M 20 watt power booster for use in cars

applications. The device features protection against supply polarity inversion and high-voltage supply transients. **Figure 21** shows a practical applications circuit: voltage gain is determined by R2; R1 is an output biasing resistor and is boot-strapped via C8; R3-C7 is a Zobel network.

The TBA820M

This is a low-power amplifier capable of generating a few hundred milliwatts in a 4R0 to 16R0 speaker load, and is housed in an 8-pin DIL package. The IC can operate from supply voltages as low as 3V, and features low quiescent current, good ripple rejection, and low cross-over

distortion. **Figure 22** shows a practical applications circuit, in which the voltage gain is determined by R2, and R3-C6 form a Zobel network. This circuit can use a maximum supply voltage of 16V with a 16R0 speaker, 12V with an 8R0 speaker, or 9V with a 4R0 speaker.

The TDA 2005M

This is a 20W audio power booster specifically designed for use in automobiles, and is fully protected against output short circuits etc. The IC actually houses two power amplifiers which are internally connected in the bridge configuration to provide the high power output (into a 2R0 load) from the 14.4V

(nominal) power supply of an automobile. The IC is housed in an 11-pin package. **Figure 23** shows a practical applications circuit. Note that all capacitors must be rated at 25V minimum.

The TDA2006

This is a high-quality amplifier that can be used with either split or single-ended power supplies, and which typically generates less than 0.1% distortion when feeding 8W into a 4R0 speaker load. The IC is housed in a 5-pin TO220 package that has an electrically insulated heatsink tab, which can consequently be bolted directly to an external heatsink without need of an insulating washer.

DATA FILE

TO220 package

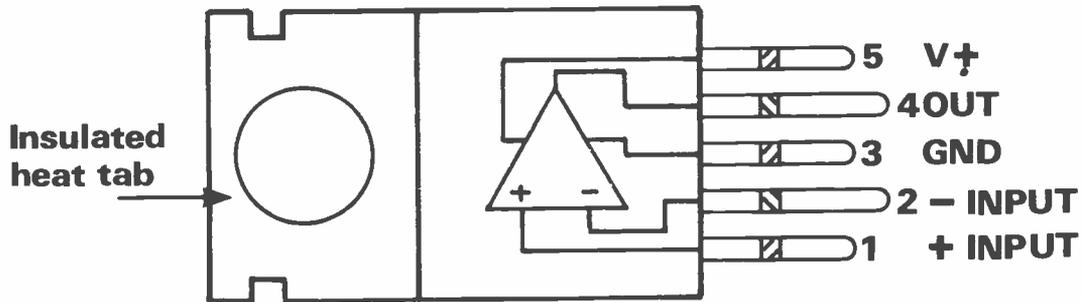


Figure 24 Outline and pin connections of the TDA2006 and TDA2030

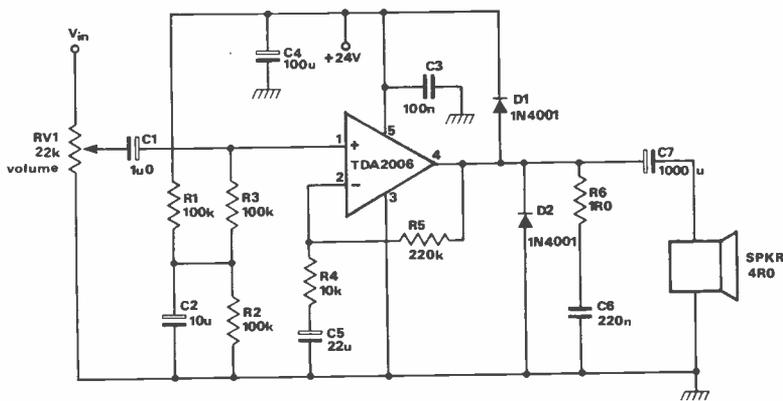


Figure 25 TDA2006 8 watt amplifier with single-ended supply

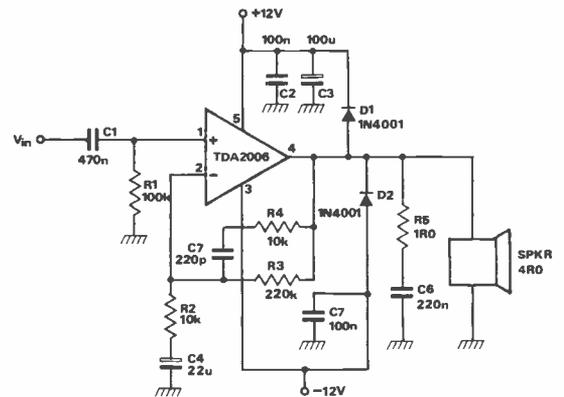


Figure 26 TDA2006 8 watt amplifier with split power supply

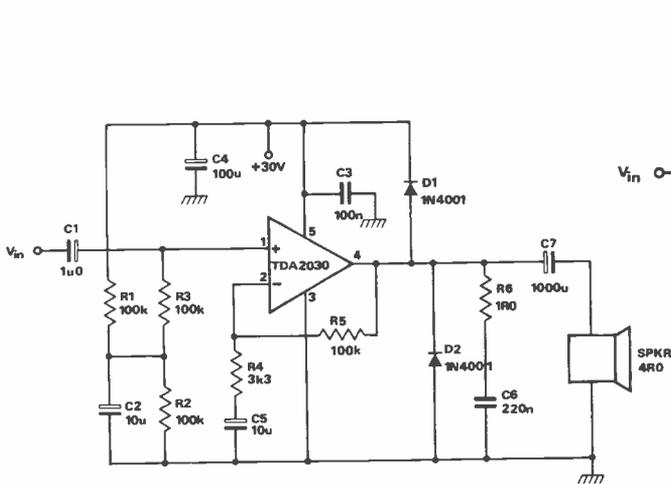


Figure 27 TDA2030 15 watt amplifier with single-ended supply

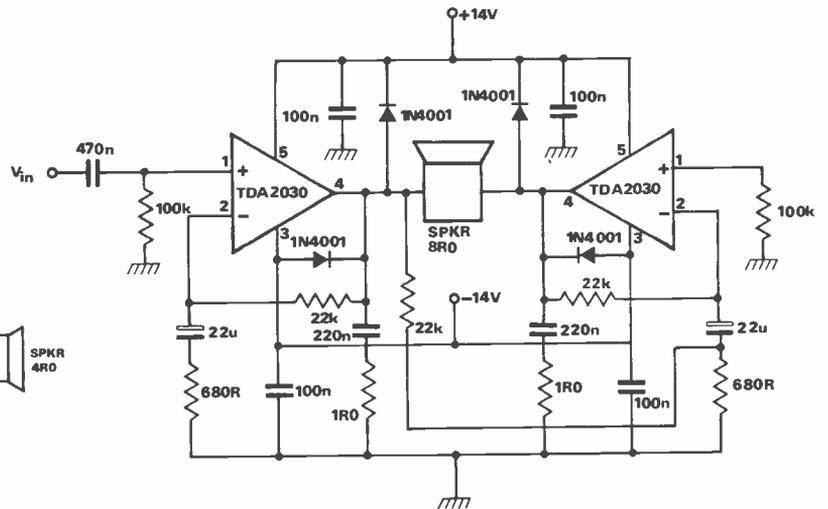


Figure 28 TDA2030 24 watt bridge amplifier with split supply

Figure 25 shows how to use the TDA2006 with a single-ended supply. The non-inverting input pin is biased at half-supply volts via R3 and the R1-R2 potential divider, and the voltage gain is set at x22 via R5/R4. D1 and D2 protect the output of the IC against damage from back EMF voltages from the speaker, and R6-C6 form a Zobel network.

Figure 26 shows how to modify the above circuit for use with split power supplies. In this case the non-inverting

input is tied to ground via R1. This circuit also shows how high-frequency roll-off can be applied to the amplifier via C5-R4.

The TDA2030

This very popular IC can be regarded as an upgraded version of the TDA2006, and is housed in the same 5-pin TO220 package with insulated heat tab. It can operate with single-ended supplies of up to 36V ($\pm 18V$, split). When used with a +28V single-ended supply, it gives a

guaranteed output of 12W into 4R0 or 8W into 8R0. Typical THD is .05% at 1KHz at 7W output.

Figure 27 shows how to connect the TDA2030 as a 15W amplifier using a single-ended +30V supply and a 4R0 speaker load and a voltage gain of 30dB. Finally, Figure 28 shows how to wire a pair of these ICs as a split-supply 'bridge' amplifier that can deliver 24W into a 4R0 speaker load with a typical THD of less than 0.5%.

BBC MICRO MORSE TUTOR

This is a Morse tutoring program for the BBC Micro that has a maximum sending speed of about 20wpm. The limitation on speed lies in the sound generator chip, which cannot make a sound shorter than 1/20 second.

Since the BASIC is running a lot faster than this there is no advantage to be gained in using machine code.

Data structure

The 36 characters (26 letters and 10 digits) are held in the integer array A% as sequences of 1's and 3's - the comparative values of the dots and dashes - and the number of dots and dashes in each character is held in the array L%.

When a character is sounded, the information is converted to a string and examined bit by bit.

This is preferable to using a string array which would waste an incredible amount of memory, although memory itself is not a problem.

The zero is placed first of the numbers in accordance with the sequence in the ASCII code, rather than last as is normal in Morse.

Timing

The real time clock in the BBC runs in Hz (1/100 second) but the sound chip runs in units of 1/20 second - 5Hz. This is therefore the minimum duration of a dot.

by M LAVOCAH

The conversion factor between these two timings is DUR%.

When a sound statement is reached the CPU passes this to the sound chip and is then free to carry on with the next statement while the sound chip makes the noise.

Therefore when pausing between dots and dashes we must first pause for the time it takes to make the sound, and then pause for the gap itself.

The program

PROCinit selects the mode of operation. First of all you select between sending phrases or random characters. (PA% 1,2)

If you select phrases, you then have to type in a phrase before the computer sends it back to you. Knowing what's coming isn't too much of a problem, but you could always get a friend to type something in or else hit the keys at random.

This has the advantage (?) that the Morse sent contains a disproportionate amount of 'hard' letters.

If you choose to receive random characters, you can then choose between letters only, numbers only, both, or a particular range of letters (G 1,2,3,4).

The characters are tokenised as follows:

Space	0
A - Z	1 - 26
0 - 9	27 - 36

When picking random letters, two variables are used:

R% base of range
Q% length of range
eg R% 1, Q% 26 is the alphabet.

As it stands the program runs in an endless loop; when you get bored, press ESCAPE. It's all legal due to the REPEAT...UNTIL FALSE syntax.

The noises

The syntax of the SOUND statement is SOUND channel, loudness, pitch, duration. The pitch can be altered at your discretion, high numbers giving a high pitch. The duration (and hence the speed) can also be varied, but only down to 5Hz.

Some of you may have already noticed the extra sound statement in line 370, which provides a bit of background interference. For more difficult reception, make this noise louder and the Morse itself quieter. A louder noise is given by a more negative loudness parameter, up to -15.

```
L.
10 REM (c) M.LAVOCAH APR'84
20 MODE7
30 PROCdata
40 PROCinit
50 IF PA%=2 THEN REPEAT:PROCphrase:UNTIL FALSE
60 REPEAT:PROCrandom:UNTIL FALSE
70 END
80 :
90 DEF PROCrandom
100 TIME=0
110 FOR PASS%=1 TO HZ
120 C%=0%*RND(1)+R%
130 REPEAT
140 PROCchar:PROCcorrect
150 UNTIL COR%=1
160 PRINT"CORRECT:";CHR$(ANS%)
170 NEXT
180 T=TIME:PRINT"ELAPSED TIME ";INT(T/100);" SECS"
190 PRINT"CHARACTERS PER MINUTE:";INT(HZ*6000/T)
200 ENDPROC
210 :
220 DEF PROCphrase
230 INPUT"WHAT IS THE PHRASE "P$:I%=LEN(P$)
240 CLS:PRINT"PRESS ANY KEY TO START":G=GET
250 TIME=0
260 FOR PASS%=1 TO I%
270 C%=ASC(MID$(P$,PASS%,1))
280 IF C%<32 THEN C%=0
290 IF C%>64 THEN C%=C%-64 ELSE C%=C%-21
300 IF C%<0 THEN C%=0
310 PROCchar:PROCpause(4*DUR%)
320 NEXT
330 T=TIME:PRINT"TIME ";T:PRINT"PRESS ANY KEY":G=GET
340 ENDPROC
350 :
360 DEF PROCchar
370 NZ=L%(C%):A%=STR$(D%(C%)):SOUND&10,-5,4,20
380 FOR A%=1 TO NZ
390 B%=VAL(MID$(A%,A%,1))
400 B1%=B%*DUR%/5:IF B1%=0 THEN B%=8 ELSE SOUND 1,-15,PITCH%,B1%
410 PROCpause(DUR%+B%*DUR%)
420 NEXT
430 ENDPROC
440 :
450 DEFPROCcorrect
460 COR%=0:*FX 12,0
470 IF C%<27 THEN ANS%=C%+64 ELSE ANS%=C%+21
480 G%=GET
490 IF G%=ANS% THEN COR%=1
500 ENDPROC
510 :
520 DEFPROCpause(F)
530 T%=TIME:REPEAT UNTIL TIME>=T%+F
540 ENDPROC
550 :
560 DEF PROCinit
570 PRINT"MORSE TUTOR":PRINT
580 PRINT"DURATION OF DOT IN CS(TRY 5) ";
590 REPEAT:INPUTDUR%:UNTIL DUR%<15 AND DUR%>4
600 PRINT"PITCH (50-150) ";
610 REPEAT:INPUT PITCH%:UNTIL PITCH%>300 AND PITCH%<200
620 PRINT:PRINT"RANDOM LETTERS(1) OR A PHRASE(2) ?"
630 REPEAT:PA%=VAL(GET$):UNTIL PA%=1 OR PA%=2
640 IF PA%=2 THEN ENDPROC
650 PRINT"HOW MANY CHARACTERS ";
660 REPEAT:INPUTH%:UNTIL H%<100 AND H%>5
670 PRINT"LETTERS(1) NUMBERS(2) BOTH(3) SELECTED LETTERS(4) "
680 REPEAT:G=VAL(GET$):UNTIL G>0 AND G<5 AND G=INT(G)
690 IF G=2 THEN R%=27:Q%=10 ELSE R%=1
700 IF G=1 THEN Q%=26
710 IF G=3 THEN Q%=36
720 IF G=4 THEN PRINT"FIRST LETTER":REPEAT:INPUTR$:R%=ASC(R$)-64:UNTIL R%<26:P
PRINT"LAST LETTER":REPEAT:INPUTL$:L%=ASC(L$)-64:UNTIL L%<26:Q%=L%-R%+1
730 CLS
740 ENDPROC
750 DEFPROCdata
760 DIM L%(36),D%(36)
770 FOR A%=1 TO 36
780 READ L%(A%),D%(A%)
790 NEXT
800 ENDPROC
810 :
820 REM ABC,DEF,GHI,JKL
830 DATA 2,13,4,3111,4,3131
840 DATA 3,311,1,1,4,1131
850 DATA 3,331,4,1111,2,11
860 DATA 4,1333,3,313,4,1311
870 REM MNO,PQR,STU,VWX,YZ
880 DATA 2,33,2,31,3,333
890 DATA 4,1331,4,3313,3,131
900 DATA 3,111,1,5,3,113
910 DATA 4,1113,3,133,4,3113
920 DATA 4,3133,4,3311
930 :
940 REM NUMBERS
950 DATA 5,33333,5,13333
960 DATA 5,11333,5,11133
970 DATA 5,11113,5,11111
980 DATA 5,31111,5,33111
990 DATA 5,33311,5,33331
```

PHONE
0474 813225
3 LINES



P.M. COMPONENTS LTD
DEPT REW SELECTRON HOUSE, WROTHAM ROAD
MEOPHAM GREEN, MEOPHAM, KENT DA13 0QY

TELEX
966371
PM COMP

INTEGRATED CIRCUITS

AN124	2.50	MC1358	1.58	STK439	7.95	TBA560Q	1.45	TDA2530	1.95
AN214Q	2.50	MC1495	3.00	TA7061AP	3.00	TBA570	1.00	TDA2532	1.95
AN240P	2.80	MC1496	1.25	TA7108P	1.95	TA7108P	1.00	TDA2540	1.25
AN612	2.15	MC145106P		TA7120P	1.85	TA7120P	1.50	TDA2541	2.15
AN7140	3.50	MC1723	7.95	TA7130P	1.50	TBA691R	2.50	TDA2560	2.15
AN7145	3.50	SA455A	3.50	TA7227P	2.25	TBA820C	1.45	TDA2571	2.95
AN7150	2.95	MC3357	2.75	TA7176AP	2.95	TBA800	0.85	TDA2593	2.95
BA521	3.35	ML231B	1.75	TA7203	2.85	TBA810A	1.65	TDA2600	5.50
CA1352E	1.75	ML232B	2.50	TA7204P	1.15	TBA810P	1.05	TDA2610	5.50
CA3086	0.48	MSM5807	8.75	TA7205AP	2.15	TBA820M	0.75	TDA2611A	1.95
ET7601E	2.50	PLL02A	5.75	TA7222AP	1.80	TBA820Q	1.45	TDA2640	2.60
HA1335A	2.95	SA455A	3.50	TA7227P	2.25	TBA890	2.50	TDA2680A	2.75
HA1377	3.50	SA1025	7.25	TA7310P	1.80	TBA920	1.65	TDA2690	2.45
HA1156W	1.50	SAAS010	6.35	TA7313AP	2.95	TBA950/2X		TDA2695	3.95
HA1551	2.95	SAS560S	1.75	TA7321P	2.25	TBA970	2.15	TDA2700	3.95
LA1230	1.15	SAS570S	1.75	TA7609P	3.15	TBA970	2.15	UPC575C2	5.70
LA4102	2.95	SAS580	2.85	TA7611AP	2.95	TBA1441	2.15	UPC1025H	2.50
LA4250	2.95	SL901B	4.85	TA7611AP	2.95	TCA270	1.10	UPC1028H	1.95
LA4420	1.95	SL917B	6.65	TA7611AP	2.95	TCA270SQ		UPC1032H	1.50
LA4430	2.50	SL1310	1.80	TAA621AXI	3.50	TC4705Q		UPC1158H	2.75
LA4400	4.15	SL1327	1.10	TAA661B	3.20	TC4705Q		UPC1181H	1.15
LA4422	2.50	SL1327Q	1.10	TAA661B	3.20	TC4705Q		UPC1182H	1.25
LC7120	3.25	SN76033N	1.95	TA700	1.70	TC4705Q		UPC1185H	2.95
LC7130	3.50	SN76033N	1.95	TB230B	2.95	TC4705Q		UPC1185H	3.95
LC7131	5.50	SN76033N	1.95	TBA120C	1.15	TC4705Q		UPC1350C	2.95
LC7137	5.50	SN76033N	1.95	TBA120T	1.05	TC4705Q		7805	0.65
LM324N	0.45	SN76110N	0.89	TBA120U	1.00	TC4705Q		7815	0.65
LM380N	0.95	SN76115N	1.25	TBA231	1.25	TC4705Q			
LM380T	2.95	SN76131N	1.30	TBA2395	1.50	TC4705Q			
M5151L	2.95	SN76226D	1.15	TBA336	0.48	TC4705Q			
M5152L	1.50	SN76227N	1.05	TBA440N	2.55	TC4705Q			
MB3712	2.00	SN76533N	1.65	TBA480Q	1.25	TC4705Q			
MC1307P	1.00	SN76544N	1.95	TBA510	2.50	TC4705Q			
MC1310P	1.00	SN76550N	1.00	TBA510Q	2.50	TC4705Q			
MC1327	0.95	SN76550N	1.15	TBA520Q	1.10	TC4705Q			
MC1327Q	0.95	SN76660N	0.90	TBA530	1.10	TC4705Q			
MC1330P	1.10	STK014	7.95	TBA530Q	1.10	TC4705Q			
MC1349P	1.20	STK015	7.95	TBA540	1.25	TC4705Q			
MC1350P	0.95	STK445	7.95	TBA540Q	1.35	TC4705Q			
MC1351P	1.50	STK443	7.95	TBA550Q	1.95	TC4705Q			
MC1357	2.35	STK437	7.95	TBA560C	1.45	TC4705Q			

NEW BRANDED CATHODE RAY TUBES

A1865/20	65.00	DG13.2	45.00	M38-120W	65.00
A44.120	25.00	DH3.91	45.00	M38-120WA	65.00
AW36.11	25.00	DH7.11	95.00	M38-121GR	65.00
CME822W	19.00	DH7.91	45.00	M38-121GHR	65.00
CME822GH	25.00	DP7.5	35.00	M38-121LA	65.00
CME1428GH	45.00	DP7.6	45.00	M38-121WA	65.00
CME1523GA	39.00	DP7.11	45.00	M38-122GH	65.00
CME1523W	39.00	DN13.78	35.00	M38-122GW	65.00
CME1431GH	39.00	F15-101LC	46.00	M38-140LA	65.00
CME1431W	39.00	F16-101GM	55.00	M38-141GH	65.00
CME202GH	45.00	F16-101LD	55.00	M38-142GR	65.00
CME2325W	45.00	F21-130GR	55.00	M38-340P31	65.00
CME3126GH	45.00	F31-101LD	55.00	M38-341GR	65.00
CME3128W	45.00	F22-11LD	53.00	M38-341P31	65.00
CME3128W	45.00	F31-101GM	65.00	M38-344P39	65.00
CME3132GH	45.00	F31-10GR	65.00	M40-120W	65.00
CME3132GH	45.00	F31-10LC	65.00	M42-120GM	65.00
CME3155W	45.00	F31-10LD	65.00	M43-12L/G01	65.00
CRE1400	25.00	F31-12LC	65.00	M44-120LC	65.00
CV429	89.00	F31-12LD	65.00	M44-120GR	65.00
CV1450	35.00	F31-13GR	65.00	M47-25GR/22	65.00
CV1526	19.00	F31-13LD	65.00	M50-120GH	65.00
CV2368	15.00	F31-13GR	65.00	M50-120GR	65.00
CV2191	19.00	F41-123LC	160.00	M50-120GV	65.00
CV2193	15.00	F41-141LG	160.00	M50-120LC	65.00
CV2328	65.00	F41-142LC	185.00	M61-120LC	75.00
CV5119	85.00	M7-120W	19.00	M61-120W	75.00
CV5320	85.00	M14-100GM	45.00	S6A	59.00
CV3368	59.00	M14-100KA	45.00	SE4/D-P7	45.00
D9-110GH	39.50	M14-100LC	45.00	SE42BP31AL	55.00
D9-120	45.00	M17-151GVR	175.00	SE42BP31	55.00
D10-210GH	45.00	M17-151GR	175.00	SE52AP31AL	55.00
D10-210GH/88B	65.00	M19-100GY	55.00	SE5F31	55.00
D10-210GH/72	65.00	M19-100W	45.00	193	65.00
D10-210GM	59.00	M19-101GR	55.00	T948N	65.00
D10-210GV	35.00	M19-103W	55.00	T948H	65.00
D10/293GY/90	55.00	M23-110GH	55.00	V3191	59.00
D13-27GH	49.50	M23-111W	55.00	V4150LC	55.00
D13-30GH	49.50	M23-111GH	55.00	V4254B	65.00
D13-33GH	49.00	M23-111LD	55.00	V4254H	65.00
D13-47GH/26	55.00	M23-112GM	55.00	V4283W	65.00
D13-47GH/34	55.00	M23-112GV	55.00	V5002LD	65.00
D13-47GH	55.00	M23-112W	55.00	V5004GR	59.00
D13-51GH/34	85.00	M23-112KA	55.00	V5004LD	59.00
D13-51GH/26	85.00	M23-112LD	55.00	V5004LG	59.00
D13-51GM/26	55.00	M23-112W	55.00	V6005GH	65.00
D13-550GH/01	55.00	M24-120GM	59.00	V6007DP31	59.00
D13-550GH	65.00	M24-120GR	59.00	V6007GW	65.00
D13-600GM	59.00	M24-120LC	59.00	V6008GH	59.00
D13-610GH	59.00	M24-120WAF	59.00	V6008W	65.00
D13-610GM	59.00	M24-121GH	55.00	V6009WA	59.00
D13-611GH	59.00	M24-121LC	59.00	V6009WA	59.00
D13-611GM	59.00	M28-11LA	49.00	V6048F	59.00
D13-630GH	59.00	M28-12GH	55.00	V6048J	49.00
D14-120GH/08	65.00	M28-12LC	55.00	V6052GH	65.00
D14-121GH/H4	75.00	M28-13LC	49.00	V6052GR	65.00
D14-122GH	55.00	M28-13L	49.00	V6064B	55.00
D14-122GM	55.00	M28-13GR	49.00	V6064CL	55.00
D14-122GR	55.00	M28-13WA	49.00	V6068GH	55.00
D14-122GV	55.00	M28-131GR	55.00	V6070P31	49.00
D14-122GW	55.00	M28-131GR	55.00	V7016A	65.00
D14-122W	55.00	M28-133GH	55.00	V7030	59.00
D14-122W	55.00	M31-100GH	55.00	V7273GH	65.00
D14-122W	55.00	M31-100GM	55.00	V7301/67A	59.00
D14-122W	55.00	M31-182GR	55.00	V7035A	49.00
D14-122W	55.00	M31-182GR	55.00	V7037GH	45.00
D14-122W	55.00	M31-183W	55.00	V8004GR	65.00
D14-122W	55.00	M31-184W	65.00	V8006GH	65.00
D14-122W	55.00	M31-184GH	65.00	V8010A	65.00
D14-122W	55.00	M31-184GH	65.00	V8011A	15.00
D14-122W	55.00	M31-185GH/VR	69.00	V8012A	15.00
D14-122W	55.00	M31-186W	69.00	2BP1	9.00
D14-122W	55.00	M31-190GH	55.00	3BP1	13.50
D14-122W	55.00	M31-190GR	55.00	4EP1	30.00
D14-122W	55.00	M31-190LA	55.00	3H/OBM	55.00
D14-122W	55.00	M31-190W	55.00	5BP1	9.00
D14-122W	55.00	M31-191GH	55.00	5BP1F	30.00
D14-122W	55.00	M31-191GR	55.00	5BP1S	30.00
D14-122W	55.00	M31-191W	55.00	5CP1	10.00
D14-122W	55.00	M31-192W	55.00	6EP1/3	39.00
D14-122W	55.00	M31-195GH	59.00	13BP1	13.50
D14-122W	55.00	M31-210GH	59.00	13BP4	17.50
D14-122W	55.00	M31-220W	59.00	17DWP4	25.00
D14-122W	55.00	M31-270GY	65.00	32J/1085	69.00
D14-122W	55.00	M31-271P31	65.00	88D	15.00
D14-122W	55.00	M31-271W	65.00	99B	15.00
D14-122W	55.00	M36-12W	75.00	130	15.00
D14-122W	55.00	M36-141LA	75.00	1273	39.00
D14-122W	55.00	M36-141LG	75.00	1564	15.00
D14-122W	55.00	M36-141W	75.00	1844	45.00
D14-122W	55.00	M36-170LG	75.00	5545GM	75.00
D14-122W	55.00	M38-100G (220/400V)	65.00	9442E1	80.00
D14-122W	55.00	M38-101GH	65.00	95447GM	75.00
D14-122W	55.00	M38-103GR	65.00	95449GM	75.00
D14-122W	55.00	M38-113GR	65.00	779631	79.50

SEMICONDUCTORS

AA12	0.25	BC172C	0.10	BD179	0.72	BF355	0.37	R2010B	1.70
AC126	0.45	BC173B	0.10	BD182	0.70	BF362	0.38	R2322	0.58
AC127	0.20	BC174	0.09	BD201	0.83	BF363	0.38	R2323	0.68
AC128	0.28	BC174A	0.09	BD202	0.85	BF371	0.20	R2540	2.48
AC128K	0.32	BC177	0.15	BD203	0.78	BF394	0.19	RCA1633A	1.90
AC141	0.28	BC178	0.15	BD204	0.70	BF457	0.32	SKE5F	1.45
AC141K	0.34	BC182	0.10	BD222	0.48	BF458	0.38	TIP29	0.40
AC142K	0.30	BC182L	0.10	BD225	0.48	BF467	0.68	TIP29C	0.42
AC176	0.22	BC183	0.10	BD232	0.35	BF495	0.23	TIP30C	0.43
AC176K	0.31	BC183L	0.09	BD233	0.35	BF597	0.25	TIP31C	0.42
AC187	0.25	BC184LB	0.09	BD234	0.35	BF599	0.23	TIP32C	0.42
AC187K	0.26	BC204	0.13	BD236	0.45	BF640	0.23	TIP33B	0.75
AC188	0.25	BC207B	0.10	BD237	0.40	BF641	0.28	TIP34B	0.75
AC188K	0.37	BC208	0.13	BD238	0.40	BF681	0.25	TIP41A	0.45
AD142	0.79	BC212	0.09	BD241	0.40	BF688			

PHONE
0474 813225
3 LINES

P.M. COMPONENTS LTD
DEPT REW SELECTRON HOUSE, WROTHAM ROAD
MEOPHAM GREEN, MEOPHAM, KENT DA13 0QY



TELEX
966371
PM COMP

A SELECTION FROM OUR STOCK OF BRANDED VALVES

A1714 18.50	E283CC 10.00	EF95 1.00	HAA91 1.00
A1998 11.50	E288CC 13.50	EF97 0.90	HAB1C80 0.90
A2087 11.50	EB10F 18.50	EF98 0.90	HBC90 0.75
A234 14.95	E1148 1.00	EF183 0.65	HBC91 0.80
A2593 6.50	E1524 1.00	EF184 0.65	HF93 0.75
A2900 11.50	EA50 1.00	EF730 1.80	HF94 1.00
A3042 24.00	EA76 1.95	EF731 3.50	HK90 1.50
A3283 20.00	EA79 1.95	EF732 3.50	HL2K 3.50
AC/HL/DD	EA81 0.80	EF800 11.00	HL23DD 4.00
AC/TH1 4.00	EA83 0.70	EF805S 13.50	HL41 3.50
ACT72 59.75	EA89 1.50	EF806S 14.50	HL42DD 3.50
AC/VP2 4.00	EA91 2.50	EF812 0.65	HL90 0.70
AC/SPEN	EA92 1.50	EF1200 1.50	HL92 1.50
	EA93 3.50	EH90 0.72	H133/DD 3.50
	EA94 0.52	EK36 0.72	EL21 6.00
	EA95 3.95	EL32 0.95	EL33 4.00
	EA96 3.95	EL33 4.00	EL34 2.25
	EA97 3.95	EL34 Mullard	
	EA98 3.95	EL36 3.95	KR63 45.00
	EA99 3.95	EL37 9.00	KT8C 7.00
	EA99 3.95	EL38 4.75	KT3C 3.50
	EA99 3.95	EL39 4.75	KT36 2.00
	EA99 3.95	EL41 3.50	KT44 4.00
	EA99 3.95	EL42 2.00	KT45 4.00
	EA99 3.95	EL43 6.95	KT61 4.00
	EA99 3.95	EL44 2.50	KT63 2.00
	EA99 3.95	EL45 0.70	KT66 OSRAM
	EA99 3.95	EL46 4.75	KT66 OSRAM
	EA99 3.95	EL47 10.50	KT66 OSRAM
	EA99 3.95	EL48 0.85	KT56 USA 6.90
	EA99 3.95	EL49 1.50	KT56 GEC
	EA99 3.95	EL50 1.50	KT56 GEC
	EA99 3.95	EL51 1.50	KT56 GEC
	EA99 3.95	EL52 1.50	KT56 GEC
	EA99 3.95	EL53 1.50	KT56 GEC
	EA99 3.95	EL54 1.50	KT56 GEC
	EA99 3.95	EL55 1.50	KT56 GEC
	EA99 3.95	EL56 1.50	KT56 GEC
	EA99 3.95	EL57 1.50	KT56 GEC
	EA99 3.95	EL58 1.50	KT56 GEC
	EA99 3.95	EL59 1.50	KT56 GEC
	EA99 3.95	EL60 1.50	KT56 GEC
	EA99 3.95	EL61 1.50	KT56 GEC
	EA99 3.95	EL62 1.50	KT56 GEC
	EA99 3.95	EL63 1.50	KT56 GEC
	EA99 3.95	EL64 1.50	KT56 GEC
	EA99 3.95	EL65 1.50	KT56 GEC
	EA99 3.95	EL66 1.50	KT56 GEC
	EA99 3.95	EL67 1.50	KT56 GEC
	EA99 3.95	EL68 1.50	KT56 GEC
	EA99 3.95	EL69 1.50	KT56 GEC
	EA99 3.95	EL70 1.50	KT56 GEC
	EA99 3.95	EL71 1.50	KT56 GEC
	EA99 3.95	EL72 1.50	KT56 GEC
	EA99 3.95	EL73 1.50	KT56 GEC
	EA99 3.95	EL74 1.50	KT56 GEC
	EA99 3.95	EL75 1.50	KT56 GEC
	EA99 3.95	EL76 1.50	KT56 GEC
	EA99 3.95	EL77 1.50	KT56 GEC
	EA99 3.95	EL78 1.50	KT56 GEC
	EA99 3.95	EL79 1.50	KT56 GEC
	EA99 3.95	EL80 1.50	KT56 GEC
	EA99 3.95	EL81 1.50	KT56 GEC
	EA99 3.95	EL82 1.50	KT56 GEC
	EA99 3.95	EL83 1.50	KT56 GEC
	EA99 3.95	EL84 1.50	KT56 GEC
	EA99 3.95	EL85 1.50	KT56 GEC
	EA99 3.95	EL86 1.50	KT56 GEC
	EA99 3.95	EL87 1.50	KT56 GEC
	EA99 3.95	EL88 1.50	KT56 GEC
	EA99 3.95	EL89 1.50	KT56 GEC
	EA99 3.95	EL90 1.50	KT56 GEC
	EA99 3.95	EL91 1.50	KT56 GEC
	EA99 3.95	EL92 1.50	KT56 GEC
	EA99 3.95	EL93 1.50	KT56 GEC
	EA99 3.95	EL94 1.50	KT56 GEC
	EA99 3.95	EL95 1.50	KT56 GEC
	EA99 3.95	EL96 1.50	KT56 GEC
	EA99 3.95	EL97 1.50	KT56 GEC
	EA99 3.95	EL98 1.50	KT56 GEC
	EA99 3.95	EL99 1.50	KT56 GEC
	EA99 3.95	EL100 1.50	KT56 GEC

PCF82 0.60	QU37 11.50	UF85 1.20	2D21 0.95	6AT6 0.75	6N7GT 2.50	30FL13 1.10
PCF84 0.65	QU38 12.50	UF41 1.15	2D21W 2.50	6AT8 1.75	6P15 1.50	30FL14 1.25
PCF86 1.20	QV05-25 1.75	UF42 1.15	2E26 7.95	6A4U 2.00	6P25 4.00	30L1 0.45
PCF87 0.40	QV06-20 29.50	UF80 0.80	2J42 93.00	6AU6 0.95	6P28 2.00	30L15 0.80
PCF200 1.80	QV2-250C	UF89 2.50	2K25 24.95	6AV6 0.75	6G7 1.20	30L17 0.60
PCF201 1.80		UL41 3.50	2K25 Ray 75.00	6AW8A 2.50	6G7GT 1.20	30P4MR 1.00
PCF800 0.40	QVQ8-100	UL64 0.95	2K26 95.00	6B8G 1.50	6S4A 1.50	30P12 1.00
PCF801 1.35	145.00	UL65 3.50	3A108A 9.00	6BA6 0.95	6S7 1.10	30P18 0.60
PCF802 0.60	QY3-125 49.50	UL77 8.00	3A109B 12.00	6BA7 4.50	6SA7GT 1.00	30P19 1.50
PCF803 1.25	QY4-250 65.00	UL8 9.00	3A110B 11.00	6BA8A 3.50	6S7GT 1.50	30PL1 2.00
PCF806 1.00	QY4-400 71.95	UL8 9.00	3A110B 12.00	6BD4 1.50	6S7GT 1.20	30PL13 0.50
PCF808 1.25	R10 4.00	UL8 9.00	3A114K 11.50	6BD5 1.50	6SH7 1.20	30PL14 1.75
PCF809 1.25	R16 12.00	UL8 9.00	3A147J 7.50	6BD6 1.00	6SJ7GT 1.20	31USA 5.50
PCF810 1.00	R17 2.50	UL8 9.00	3A167M 10.00	6BE5 0.72	6SK7 0.80	33A/158M 19.50
PCF811 1.00	R18 2.50	UL8 9.00	3A2 3.95	6BF5 1.60	6SK7GT 1.20	
PCF812 1.00	R19 2.50	UL8 9.00	3A3 3.95	6BG6G 3.00	6SL7GT 0.85	44A/158M 19.50
PCF813 1.00	R20 1.20	UL8 9.00	3A4 1.10	6BH8 1.90	6SN7GT 0.85	
PCF814 0.75	R21 2.50	UL8 9.00	3A5 1.10	6BH8A 1.50	6SQ7 0.80	35A 4.50
PCF815 0.80	R22 1.20	UL8 9.00	3A72 3.35	6BJ6 1.20	6SS7 1.95	35L6GT 2.00
PCF816 0.85	R1169 55.00	UL8 9.00	3A72 3.35	6BK4 4.00	6U4GT 1.75	35W4 0.70
PCF817 1.60	R1169 55.00	UL8 9.00	3A72 3.35	6BK4 4.00	6U4GT 1.75	35Z3 1.85
PCF818 0.85	R1169 55.00	UL8 9.00	3A72 3.35	6BK4 4.00	6U4GT 1.75	38E7 4.50
PCF819 0.85	R1169 55.00	UL8 9.00	3A72 3.35	6BK4 4.00	6U4GT 1.75	40K06 5.00
PCF820 0.85	R1169 55.00	UL8 9.00	3A72 3.35	6BK4 4.00	6U4GT 1.75	60B5 1.60
PCF821 0.85	R1169 55.00	UL8 9.00	3A72 3.35	6BK4 4.00	6U4GT 1.75	50C5 0.95
PCF822 0.85	R1169 55.00	UL8 9.00	3A72 3.35	6BK4 4.00	6U4GT 1.75	50C6DG 1.15
PCF823 0.85	R1169 55.00	UL8 9.00	3A72 3.35	6BK4 4.00	6U4GT 1.75	60Y16 2.06
PCF824 0.85	R1169 55.00	UL8 9.00	3A72 3.35	6BK4 4.00	6U4GT 1.75	62AG 19.50
PCF825 0.85	R1169 55.00	UL8 9.00	3A72 3.35	6BK4 4.00	6U4GT 1.75	61STP 2.00
PCF826 0.85	R1169 55.00	UL8 9.00	3A72 3.35	6BK4 4.00	6U4GT 1.75	75B1 2.50
PCF827 0.85	R1169 55.00	UL8 9.00	3A72 3.35	6BK4 4.00	6U4GT 1.75	75C1 2.50
PCF828 0.85	R1169 55.00	UL8 9.00	3A72 3.35	6BK4 4.00	6U4GT 1.75	80A 3.00
PCF829 0.85	R1169 55.00	UL8 9.00	3A72 3.35	6BK4 4.00	6U4GT 1.75	85A2 1.50
PCF830 0.85	R1169 55.00	UL8 9.00	3A72 3.35	6BK4 4.00	6U4GT 1.75	90AV 10.00
PCF831 0.85	R1169 55.00	UL8 9.00	3A72 3.35	6BK4 4.00	6U4GT 1.75	90C1 2.70
PCF832 0.85	R1169 55.00	UL8 9.00	3A72 3.35	6BK4 4.00	6U4GT 1.75	90CG 13.50
PCF833 0.85	R1169 55.00	UL8 9.00	3A72 3.35	6BK4 4.00	6U4GT 1.75	91AG 9.00
PCF834 0.85	R1169 55.00	UL8 9.00	3A72 3.35	6BK4 4.00	6U4GT 1.75	10D2 1.25
PCF835 0.85	R1169 55.00	UL8 9.00	3A72 3.35	6BK4 4.00	6U4GT 1.75	10F7 0.75
PCF836 0.85	R1169 55.00	UL8 9.00	3A72 3.35	6BK4 4.00	6U4GT 1.75	95A1 6.50
PCF837 0.85	R1169 55.00	UL8 9.00	3A72 3.35	6BK4 4.00	6U4GT 1.75	108C1 1.50
PCF838 0.85	R1169 55.00	UL8 9.00	3A72 3.35	6BK4 4.00	6U4GT 1.75	150B2 6.95
PCF839 0.85	R1169 55.00	UL8 9.00	3A72 3.35	6BK4 4.00	6U4GT 1.75	150C2 1.50
PCF840 0.85	R1169 55.00	UL8 9.00	3A72 3.35	6BK4 4.00	6U4GT 1.75	150C3 2.15
PCF841 0.85	R1169 55.00	UL8 9.00	3A72 3.35	6BK4 4.00	6U4GT 1.75	155UG 26.00
PCF842 0.85	R1169 55.00	UL8 9.00	3A72 3.35	6BK4 4.00	6U4GT 1.75	274A 15.00
PCF843 0.85	R1169 55.00	UL8 9.00	3A72 3.35	6BK4 4.00	6U4GT 1.75	1858T 1.50
PCF844 0.85	R1169 55.00	UL8 9.00	3A72 3.35	6BK4 4.00	6U4GT 1.75	1858T 1.50
PCF845 0.85	R1169 55.00	UL8 9.00	3A72 3.35	6BK4 4.00	6U4GT 1.75	1858T 1.50
PCF846 0.85	R1169 55.00	UL8 9.00	3A72 3.35	6BK4 4.00	6U4GT 1.75	1858T 1.50
PCF847 0.85	R1169 55.00	UL8 9.00	3A72 3.35	6BK4 4.00	6U4GT 1.75	1858T 1.50
PCF848 0.85	R1169 55.00	UL8 9.00	3A72 3.35	6BK4 4.00	6U4GT 1.75	1858T 1.50
PCF849 0.85	R1169 55.00	UL8 9.00	3A72 3.35	6BK4 4.00	6U4GT 1.75	1858T 1.50
PCF850 0.85	R1169 55.00	UL8 9.00	3A72 3.35	6BK4 4.00	6U4GT 1.75	1858T 1.50

WIREWOUND RESISTORS
PREFERRED VALUES

4 Watt	4R7-1K8 0.16
	2K2-6K8 0.16
7 Watt	R47-4K7 0.18
	5K6-12K 0.19
	15K-22K 0.20
	1R-10K 0.20
11 Watt	15K-22K 0.24
	1R-10K 0.26
17 Watt	15K-22K 0.28

BASES ETC.

B7G 0.15	14 Pin DIL 0.15
B7G Skirted	14 Pin DIL/Q 0.15
B8G 0.30	16 Pin DIL 0.30
B9A 0.20	16 Pin DIL 0.17
B9A Skirted	OCTAL 0.35
GANS 0.27	
B108 0.16	B9A PCB 0.15
B13B 0.50	B5 0.75
B13B 0.14	B9G 0.38


ZENER DIODES

BZX61 0.15
6V2 7V5 8V2 10V 11V 12V 13V 15V 16V 18V 20V 22V 24V 27V 30V 33V 36V 39V 47V 51V 56V 68V 75V

BZY88 0.07
2V7 3V 3V3 3V9 4V3 4V7 5V1 5V6 6V2 6V8 7V5 8V2 9V1 10V 11V 12V 13V 15V 18V 20V 24V 27V 30V

THERMISTORS	BATTERIES
VA1040 0.23	7V Power Mike batteries
VA1056S 0.23	TR175 £2.25 ea
VA1104 0.46	other prices on request
VAT8650 0.70	
VA1097 0.25	

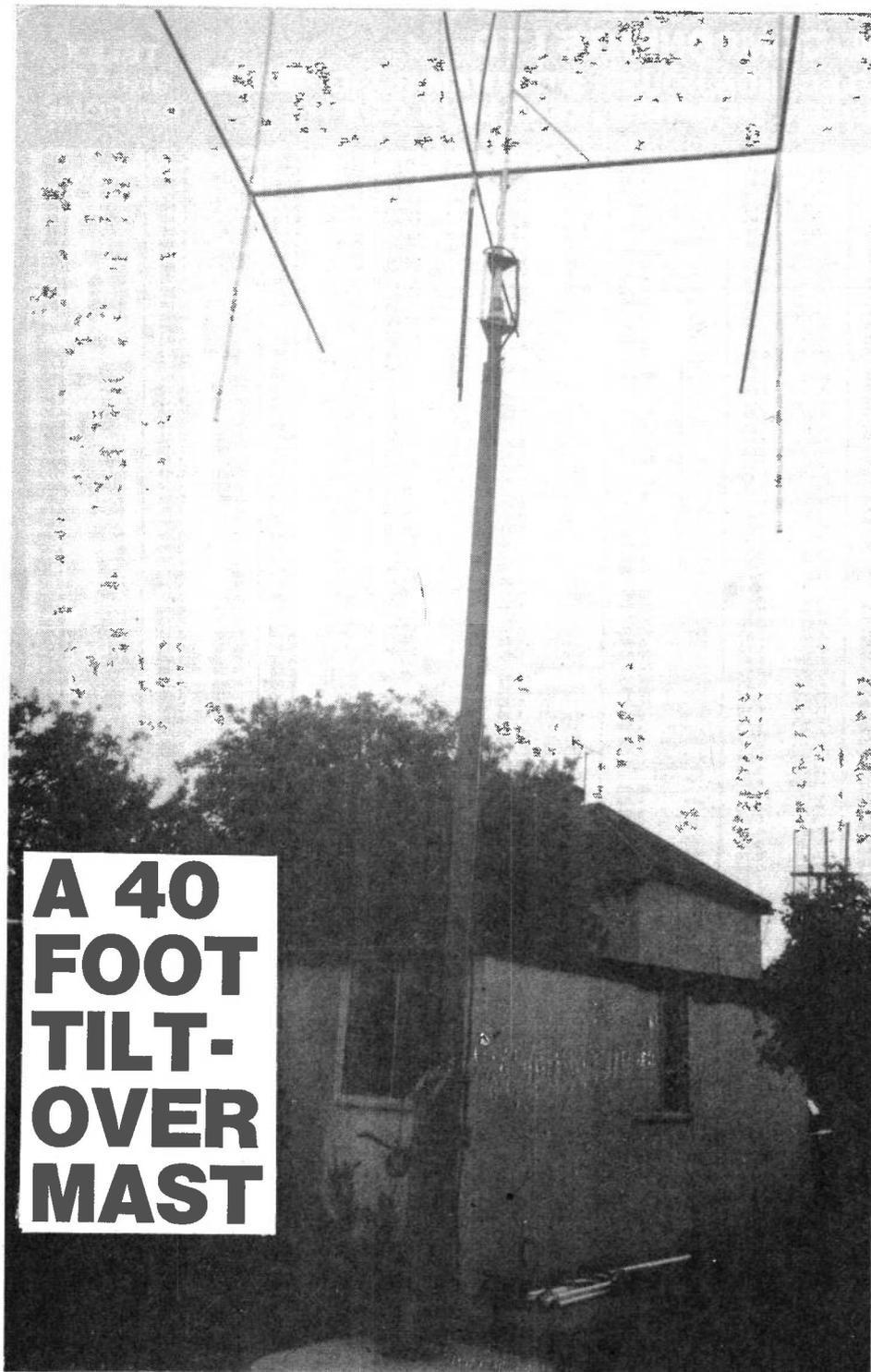CALLERS WELCOME
★ ENTRANCE ON A27
50 YDS SOUTH OF MEOPHAM GREEN
CAR PARKING AVAILABLE
Open Monday-Friday 9am-5.30pm
★ 24 HOUR ANSWERPHONE SERVICE ★
ACCESS AND BARCLAYCARD ORDERS WELCOME
★ MANY OTHER ITEMS AVAILABLE ★
UK ORDERS P&P 50p PLEASE ADD VAT AT 15%
EXPORT ORDERS WELCOME CARRIAGE/POST AT COST



A 40 FOOT TILT-OVER MAST

and a few hundredweight of cement for the base. This was bought ready-mixed and barrowed to the hole at a very reasonable price.

The result was a first-class mast which extends to forty feet unguyed, and is extremely easy and simple to tilt and raise. I set about it in the following way.

First I applied through the usual channels for planning permission. A word of advice here: *always* call it a *mast*, not a tower!

While this is taking place, contact as many of your local metal stockists as possible to obtain prices and delivery dates. It is worth shopping around as prices can vary considerably.

Foundations

You need to dig a hole 4 foot 6 inches square by 2 foot 6 inches deep. This will take the cement for the base. Bang in two lengths of angle-iron on each side at an angle of 45 degrees and to a depth of three feet. These will help to make a good anchorage. If you bond them with heavy wire and connect it to the groundpost it will serve as a useful ground plane (detail shown in *Figure 1*).

The main mast and groundpost are constructed from 100 x 100 x 4mm RHS tube. The inner sliding mast is made from 70 x 70 x 2.9mm RHS. No guy-wires or ropes are needed.

All the necessary brackets, pulleys, etc can be made in a day by a skilled person, but if you don't feel confident about it, your local blacksmith will knock them up for you. Welding and assembly will take about two days for a skilled worker, but the average ham will probably spend a couple of weeks of spare time labour.

Observe the small sump hole at the bottom. When the groundpost is constructed it is set firstly into this small hole with a bag of ready-mixed cement. Check for true vertical with a spirit level and allow two days for it to set before the bulk cement is barrowed in.

Three and a half tons of cement are required for this, and your local barrow-mix firm is probably your best answer here...

After filling, leave for two weeks before any additional strain is put on it. This will give you time to get on with the rest of the construction.

The diagrams (*Figure 2a, b and c*)

How many of us have gazed up in awe and stood green-eyed and wished for the same thing? How many of us have turned the pages of the magazines and wistfully eyed the advertisements for tilt-over masts, only to decide that the cost is prohibitive?

Here is a mast which will cost you just over £100 to build.

All you will need are the materials, which are not expensive, plus the determination to get down to the job – yes, some hard work *is* involved but it isn't beyond anyone's capability. My mast was constructed in a very short time and I used a standard hacksaw, a drill, and a few other simple tools. The only 'extras' were the use of an arc-welder

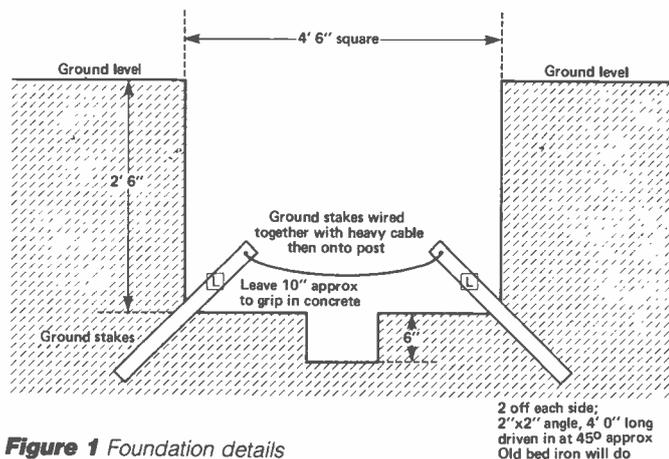


Figure 1 Foundation details

TILT-OVER MAST

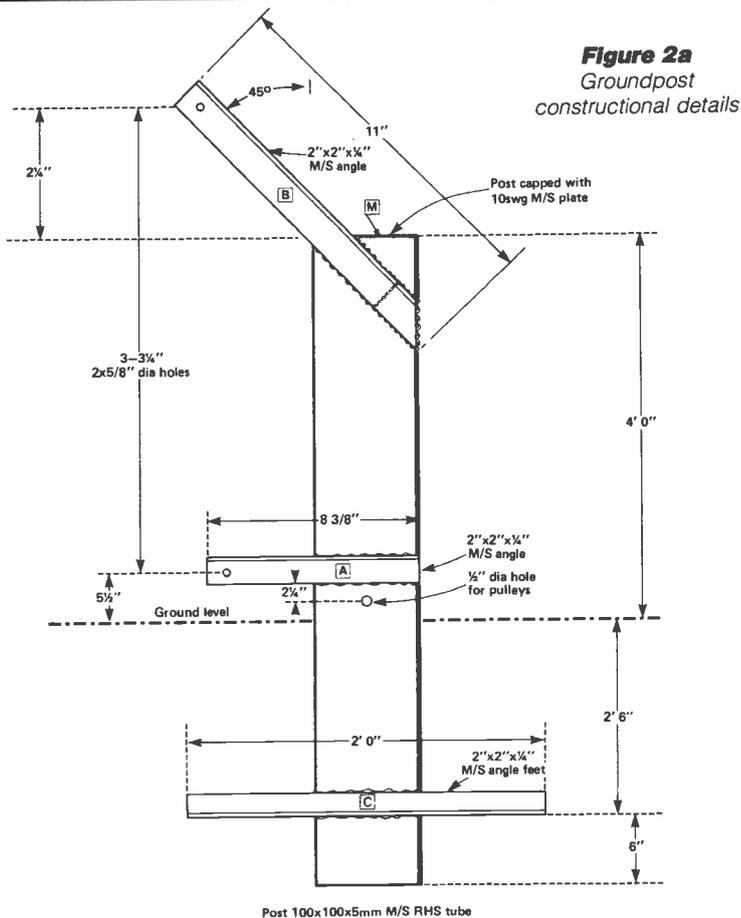


Figure 2a
Groundpost
constructional details

clearly show the dimensions and constructional details of the ground post. The hatching shown on the angle-iron indicates welding (for the uninitiated!).

On this subject it should be mentioned that unless you can weld it is better to get in a professional to do it. It goes without saying that the welds must be very good in view of the weights and strains involved, so perhaps it would be a good idea to do all the measuring and cutting first and have everything prepared so that you can call in a welder to do the whole job at once. It won't be that expensive, by the way.

Pulleys

If you don't feel confident to make these you will have to buy them, but *don't* go to a boatbuilders – they will charge the earth. Local bearing shops will often have them at more reasonable prices. Measurements are given in the following diagrams.

In any case most of the odd bits you will need may be found quite cheaply at scrapyards or from your local blacksmith. The pull needed to raise the mast from 90 degrees to the vertical is in the region of 1500 pounds, decreasing of course as the mast rises, so your pulleys and wire must be of very sound quality to say the least...and you can understand from this poundage why the welding has to be of top quality!

Little difficulty should be encountered in the construction providing the measurements are adhered to. Note the

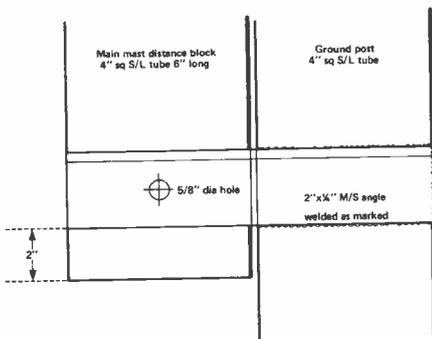


Figure 2b
Detail showing
retention of bottom
of mast to groundpost

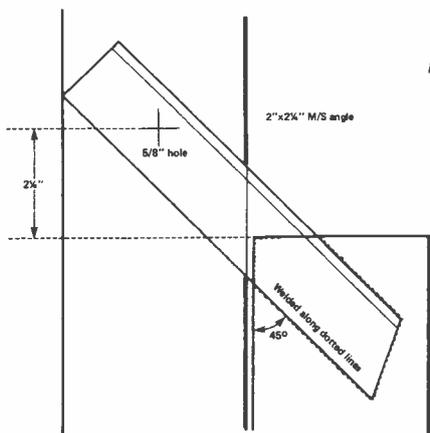


Figure 2c
Pivot point detail


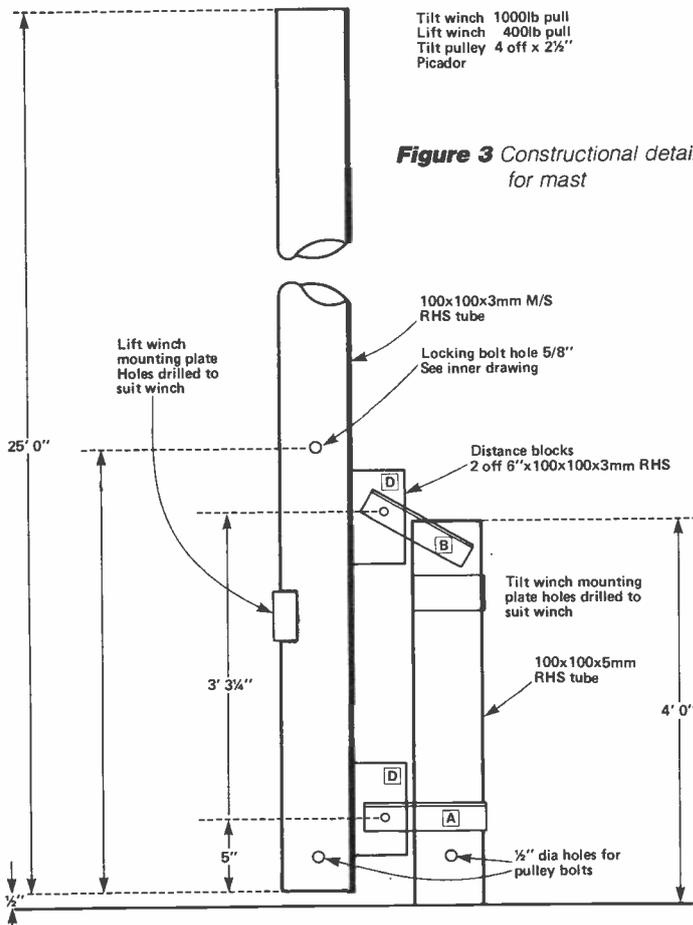


Figure 3 Constructional detail
for mast

Tilt winch 1000lb pull
Lift winch 400lb pull
Tilt pulley 4 off x 2 1/2"
Picador

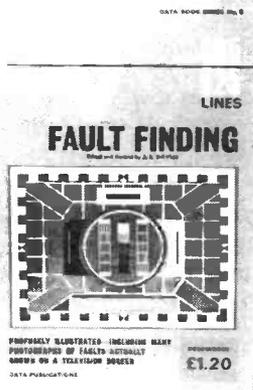REPAIR THAT OLD BLACK & WHITE TV with the aid of the best seller "TV FAULT FINDING"



Over 100 illustrations, including 60 photographs of a television screen after the appropriate faults have been deliberately introduced.

Comprehensive Fault Finding Guide cross-referenced to methods of fault rectification described at greater length in the text.

5th Edition
Edited by J R Davies
132 pages

(more than 200,000 copies sold)

Price **ONLY** £1.50 (inc p&p)

Available only from:

DATA PUBLICATIONS

45 Yeading Avenue, Rayners Lane, Harrow, Middx HA8 9RL

G8KBQ AVCOMM LIMITED G6HKT

25 Northload Street, Glastonbury, Somerset BA6 9HB
Tel: 0458 33145

25pf Beehive trimmer caps.....	5/40p
250pf min. variable caps. 1/4" spindle.....	50p
0.5 - 6pf tubular trimmers.....	30p
5 - 28pf tubular trimmers.....	35p
45pf + 45pf C808 split stator caps.....	£1.50
5 x 1 3/4 Ribbed ceramic coil formers for Atu's.....	£2.50
1000pf 10KV caps (ideal 2M linears).....	50p
Electret mic inserts, 600 OHM.....	35p
12-way tag strips.....	35p
240V AC RED neons.....	30p
Pack 5 1/4" coilformers - cans.....	35p
Pack asstd. solder tags.....	20p
Pack insulated stand off's.....	30p
Pack 10 cabinet feet.....	25p
Dummy load resistor packs 520HM 200W in silver sand.....	£2.75
Black collet knobs, 1/4" spindle.....	35p
1 1/4" inline fuseholders.....	10p
PCB through plating rivets.....	100/20p
Universal 1/4" drive couplings.....	35p
125uF 350V elect. caps, 10 for.....	£4.00

APRIL '84 LISTS, CONTAINING MANY BARGAINS 30p. ALL GOODS BY RETURN. P&P 35p up to £5, above post extra.

ELECTRONICS C.O.A.D "ANALYSER"

PERFORMANCE ANALYSIS OF LINEAR CIRCUITS using the BBC MODEL B SPECTRUM 48K and NEWBRAIN micros.

Simulates Resistors, Capacitors, Inductors, Transformers, Bipolar and Field effect Transistors, and Operational Amplifiers in any circuit configuration.

Performs FREQUENCY RESPONSE ANALYSIS on Circuits with up to 16 Nodes and 60 Components, for Phase and Gain Loss, input Impedance and Output Impedance.

Ideal for the analysis of ACTIVE and PASSIVE FILTERS, AUDIO, WIDEBAND and RF AMPLIFIERS, LINEAR INTEGRATED CIRCUITS etc, etc...

"ANALYSER" can greatly reduce or even eliminate the need to breadboard new designs. USED BY INDUSTRIAL AND UNIVERSITY R & D DEPARTMENTS WORLD WIDE.

LOW COST...VERY EASY TO USE

For further details write or phone **NUMBER ONE SYSTEMS**

Department REW, 9A Crown Street, St Ives
Huntingdon, Cambs UK, PE17 4EB

Tel: 0480 61778 Telex: 32339

Bredhurst
electronics

BREDHURST ELECTRONICS
HIGH ST, HANDCROSS, W. SX.
(0444) 400786 RH17 6BW



MAIL ORDER
AND RETAIL
MON-FRI 9-12.30/1.30-5.00
SAT 10.00-4.00pm

THE COMMUNICATIONS CENTRE OF THE SOUTH —

HF TRANSCEIVERS

	£ (c&p)	
TRIO TS930S	1195.00	(-)
YAESU FT980	1329.00	(-)
ICOM IC751	1099.00	(-)
ICOM IC745	839.00	(-)
TRIO TS430S	779.00	(-)
TRIO TS830S	758.00	(-)
YAESU FT102	719.00	(-)
YAESU FT757GX	719.00	(-)
TRIO TS530SP	669.00	(-)
TRIO TS130S	576.00	(-)
YAESU FT77	479.00	(-)

ANTENNA TUNER UNITS

ICOM IC-AT500 auto	399.00	(-)
ICOM IC-AT100 auto	285.00	(-)
TRIO AT250 auto	277.00	(-)
YAESU FC757 auto	248.00	(-)
YAESU FC102 High Power	185.00	(-)
TRIO AT230	143.00	(2.00)
TRIO AT130	98.95	(1.50)
YAESU FC700	103.00	(1.50)
WELZ AC38	73.95	(1.50)
YAESU FRT7700 Short Wave Listening	48.25	(1.00)

HF RECEIVERS

ICOM R71	649.00	(-)
ICOM R70	565.00	(-)
TRIO R2000	436.00	(-)
TRIO VC10 VHF Converter for R2000	117.00	(-)
YAESU FRG7700M with memory	455.00	(-)
YAESU FRG7700 without memory	385.00	(-)
YAESU FRT7700 antenna tuner	48.25	(-)
YAESU FRA7700 active antenna	43.95	(-)
TRIO R600	272.00	(-)

VHF RECEIVERS

JIL SX200N	299.00	(-)
AOR AR2001 25-500MHz	345.00	(-)
FDK ATC720 Handheld Airband	179.00	(-)
FDK RX40 Handheld 141-179 MHz	142.00	(-)

2M FM TRANSCEIVERS

TRIO TM201A 25W Mobile	279.00	(-)
ICOM IC27E 25W Mobile	299.00	(-)
YAESU FT230R 25W Mobile	269.00	(-)
TRIO TR2500 Handheld	246.00	(-)
FDK Multi 725X 25W Mobile	239.00	(-)
YAESU FT208R Handheld	209.00	(-)
ICOM IC2E Handheld	179.00	(-)
ICOM IC02E Handheld	239.00	(-)

2M MULTIMODE TRANSCEIVERS

TRIO TS780 2M and 70cm base	850.00	(-)
YAESU FT726R 2m fitted (70cm optional) base	775.00	(-)
ICOM IC271E 25W base	649.00	(-)
ICOM IC290D 25W Mobile	499.00	(-)
TRIO TR9130 25W Mobile	458.00	(-)
FDK Multi 750XX 20W mobile	349.00	(-)
YAESU FT290R Portable	279.00	(-)

70cm TRANSCEIVERS

TRIO TW4000A Mobile 2M/70cm	488.00	(-)
TRIO TM401A 12W Mobile	310.00	(-)
TRIO TR3500 Handheld	265.00	(-)
YAESU FT790R Multimode portable	259.00	(-)
ICOM IC4E Handheld	229.00	(-)
YAESU FT708R Handheld	189.00	(-)

POWER SUPPLIES

YAESU FP757GX	145.00	(1.50)
YAESU FP700	145.00	(2.50)
TRIO PS430S	119.00	(2.50)
TRIO PS20	59.95	(2.00)
ICOM PS15	119.00	(2.50)
ICOM PS20	176.00	(2.50)
DRAE 4 amp	34.00	(-)
6 amp	53.50	(-)
12 amp	110.00	(-)
BNOS 6 amp	92.95	(-)
24 amp	138.00	(-)
40 amp	98.45	(-)
24 amp	276.00	(-)

NEW AKD WAVEMETER (VHF) £24.95

SPEAKERS

TRIO SP230 (TS830, 530)	43.47	(1.50)
TRIO SP430 (TS430)	30.99	(1.50)
TRIO SP120 (TS130, 120)	27.99	(1.50)
YAESU SP102 (FT102)	55.00	(1.50)
TRIO SP40 Mobile speaker	14.98	(0.75)
YAESU SP55 Mobile speaker	16.00	(0.75)

WORLD CLOCKS

TRIO HC10 Digital	71.95	(2.00)
ICOM Gold Globe Clock — LCD readout	54.95	(2.00)
YAESU QTR 24D — Analogue quartz	34.50	(2.00)

ANTENNA BITS

Hi-Q Balun 1:1 5kW pep	9.95	(0.75)
W2AU Unadilla 4:1 Balun	18.99	(1.20)
7-1 14/21/28 MHz Unadilla Traps — pair	18.99	(1.20)
7-1MHz RAL-TRAPS — Epoxy — pair	8.95	(1.50)
Self Amalgamating Tape 10m x 25mm	3.95	(0.75)
T-piece polyprop Dipole centre	1.50	(0.30)
Polyprop Strain Insulators	0.50	(0.10)
Small ceramic Egg Insulators	0.75	(0.10)
Large ceramic Egg Insulators	0.75	(0.10)
75 ohm Twin Feeder light duty	0.16	(0.04)
300 ohm Twin Feeder	per metre	0.14
UR67 Low loss coax — 50ohm	per metre	0.67
UR76 50 ohm coax — dia 5mm	per metre	0.25
UR70 70 ohm coax	per metre	0.30
4mm Polyester Guy Rope, strength 400kg	per metre	0.16

WELZ SWR-POWER METER

SP15M SWR-Power HF/2M 200W	41.00	(1.00)
SP45M SWR-Power 2M/70cm 100W	59.75	(1.00)
SP250M SWR-Power HF/2kw	57.75	(1.00)
SP350M SWR-Power HF/2M/70cm 200W	73.95	(1.00)

COAXIAL SWITCHES

SA450 2 Way Diecast SO239 (500MHz)	12.50	(0.75)
SA450N 2 Way Diecast N plug (500 MHz)	15.50	(0.75)
CH20A 2 Way Welz SO239 (900 MHz)	20.75	(1.00)
CH20N 2 Way Welz N plugs (900MHz)	37.00	(1.00)

GOODS NORMALLY DESPATCHED WITHIN 24 HRS — PRICES CORRECT AT TIME OF GOING TO PRESS — E&OE

TILT-OVER MAST


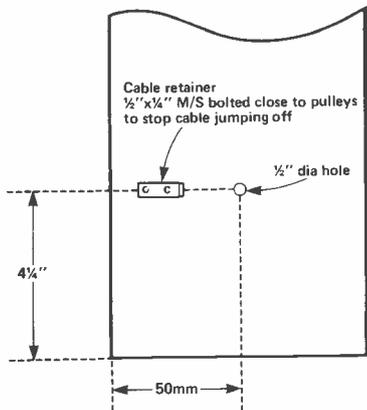
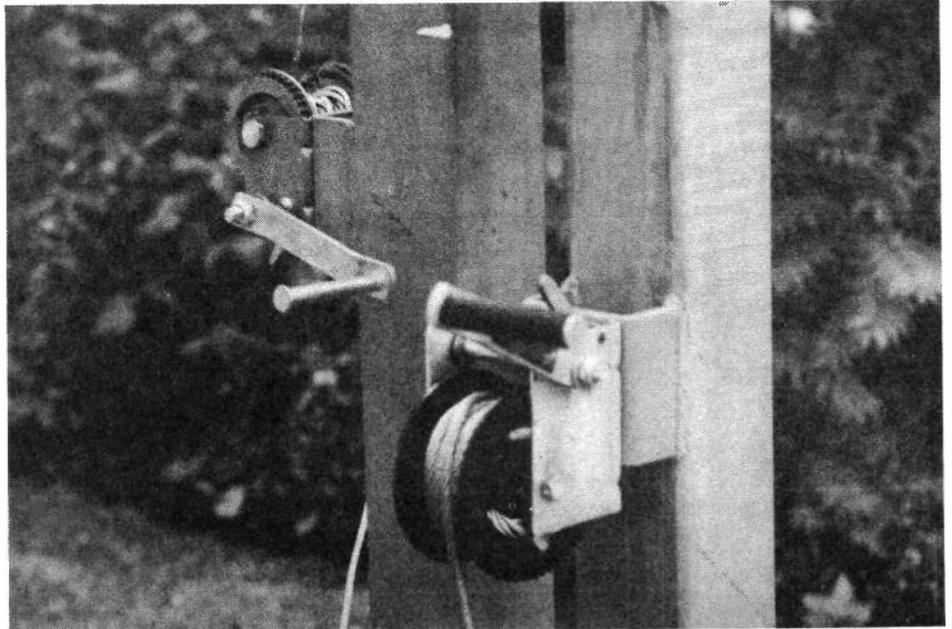
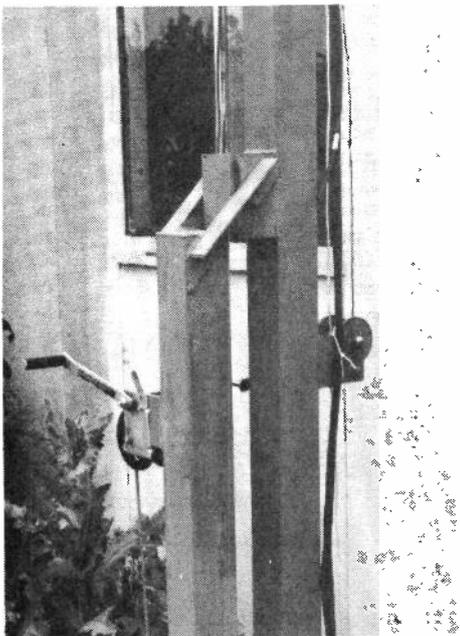


Figure 4a

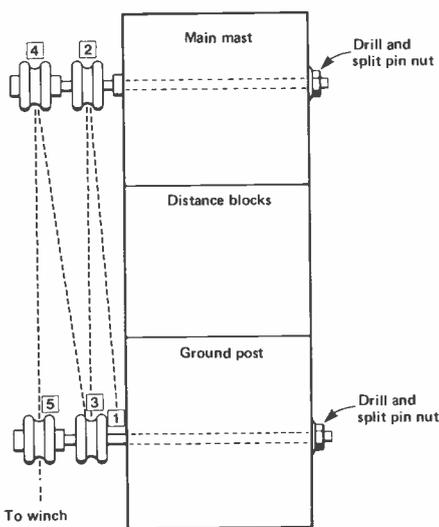

Pulleys 4 off 2 1/2" dia Picador with "Oilite" bushes
 2 off 6 1/2" x 1/2" H/T M/S bolts and nuts
 Cable is 6mm stainless steel
 Anchor with eye at point 1 Pass over pulley at point 2
 then 3 then 4 then 5 and up to tilt winch
 Cable length required is 25' approx

Figure 4b

half-inch clearance between the ground level and the mainmast. The following diagram shows the details of the bottom pulley mounting of the mainmast in detail.

Basic principles

Figure 3 shows the position of the two winches. As can be seen the principle of tilting the mast follows the orthodox methods. The pictures show the tilt pulley mounting details.

Tilt pulley mounting details

You will need four 2 1/2 inch dia. Picador pulleys with Gilite bushes and 2 x 6 1/4" x 1/2" H/T M/S bolts and nuts. Approximately 25 feet of 6mm stainless steel cable is also needed. Anchor the cable with its eye at point 1, pass it over the pulley at point 2, then over 3, 4 and 5, and then up to the tilt winch. As shown in Figure 4b.

Counterweights

It was found that counterbalancing was needed in order to facilitate raising the main mast. Approximately 300lbs are required and it is possible to obtain old 56lb weights from your local coalman.

The weights do not need to be attached to the mast directly, but by a chain, so that when the mast tilts to about 10 degrees from the vertical the slack is taken up and the weights rise as the mast tilts further.

If the weights are fixed directly to the mast there is the danger that it will snap shut and 'flick' the mast top and cause damage.

Guide plate

Clearly, the inner mast cannot be allowed to 'sit' within the main mast and wobble. The method of stabilising this is again quite simple. Figure 5a shows the view from the bottom of the mainmast, looking upwards, and the guide plate in position.

The diagonal mounting prevents any

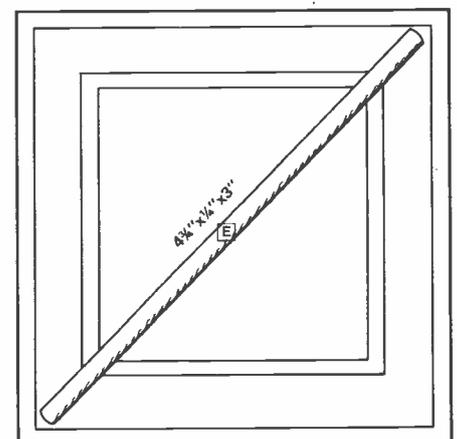


Figure 5a Guide plate details

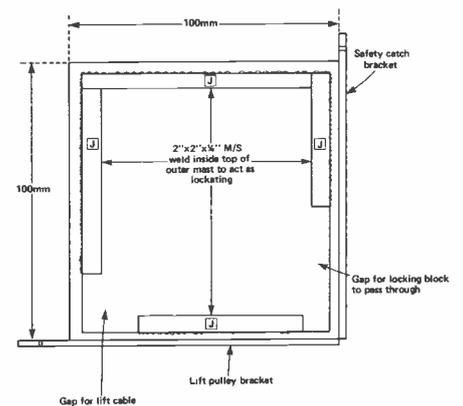


Figure 5b Inner mast locating plate details

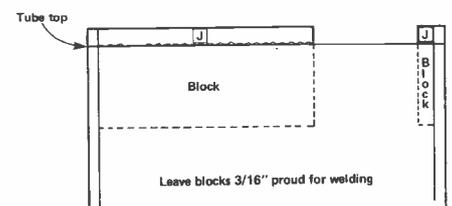


Figure 5c Welding details

TILT-OVER MAST

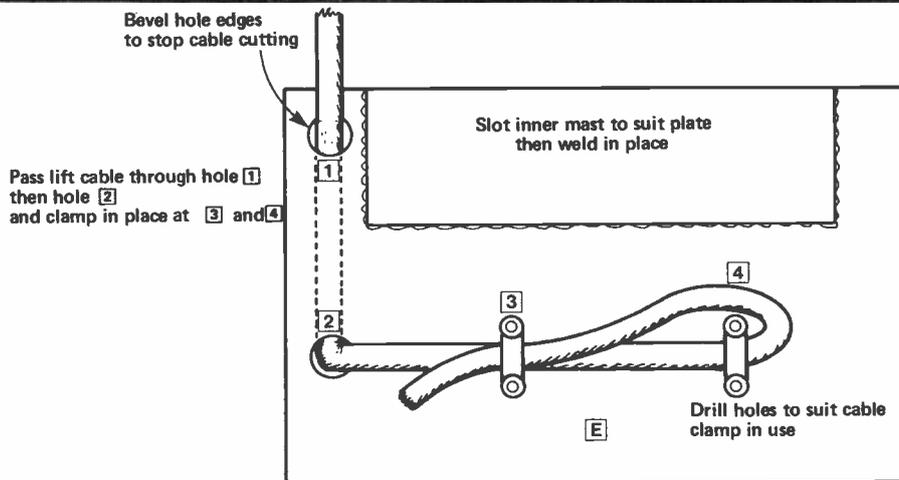


Figure 5d Inner mast lifting cable fixings

Bottom guide and rope anchor plate F/S cable is 6mm stainless steel 50' 0" approx


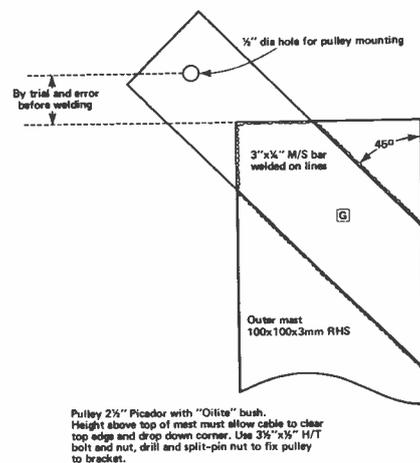


Figure 6 Pulley mounting detail

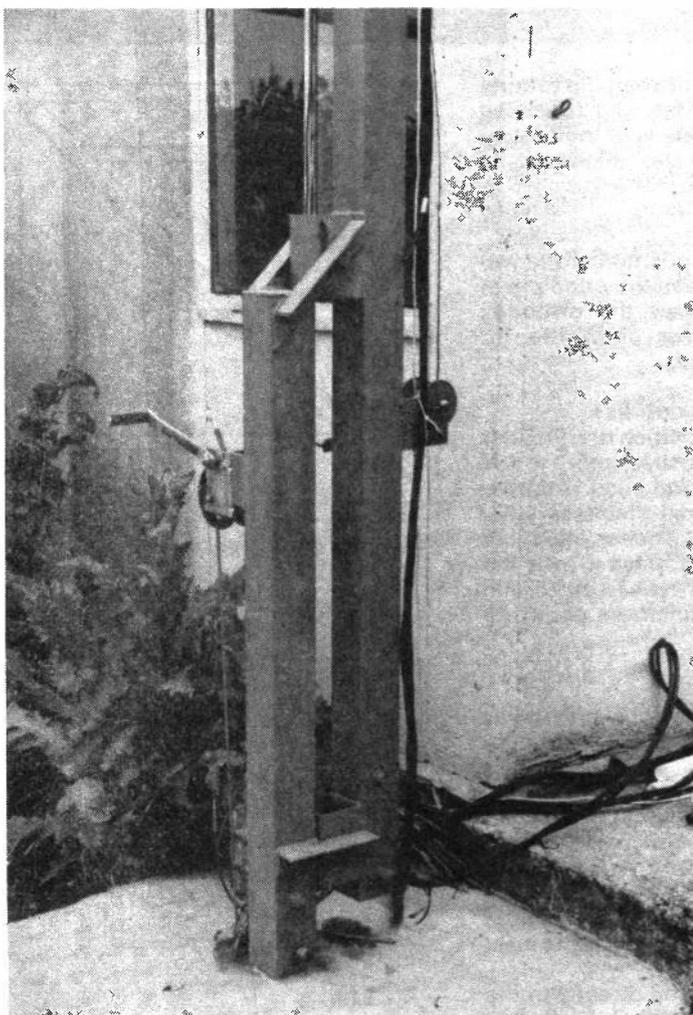

2 off 3/16" M/S plate to fit inside mast, weld to tube and top of mast

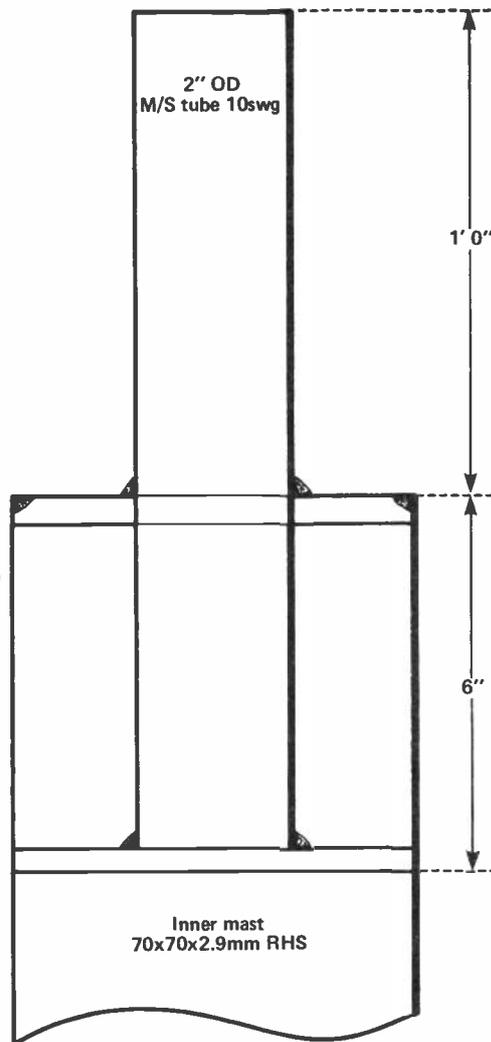


Figure 7a Rotator mounting tube detail

motion except up or down and is perfectly adequate for the task. The plate measures 4 3/4" x 1/4" x 3". The inner mast is slotted to take the plate before it is welded into position.

Holes are drilled in the guide plate for the stainless steel cable which will raise the inner mast. These may be of a size appropriate to the diameter of cable used. About 50 feet of 6mm cable is required.

Pass one end of it through holes 1 and

2, then clamp it in place at holes 3 and 4 as shown in *Figure 5d*.

The diagrams are self-explanatory and call for little comment beyond noting the remarks about positioning the blocks. Observe too the gaps for the locking block and the lift cable.

Observe the caution to use trial and error tactics before welding the 3" x 1/4" bar in order to ensure the pulley is mounted in the best position for alignment of the lifting cable. As shown in

Figure 6, the actual position is not difficult to obtain, but one must ensure that the cable does not graze on the inner wall of the main mast, and that an even strain is imparted.

This fitting shown in *Figure 7a* is to take standard 2" dia. antenna mounting arrangements. Construction is simple and no problems should be encountered.

Winches

No details of winches have been shown

TILT-OVER MAST

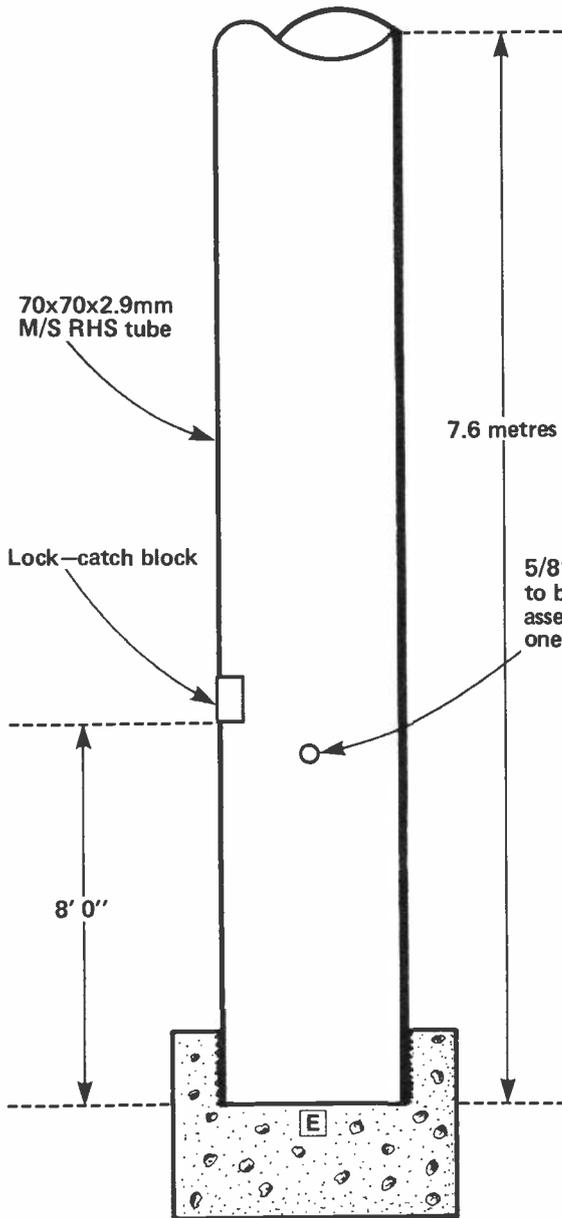


Fig 7b Inner mast constructional detail

as these are readily obtainable from local trailer makers. Again, avoid your boatyard or ship's chandlers because their prices are often astronomical.

The luffing and telescoping cables may also be found at the trailer maker. If you bear in mind the weights and stresses involved in raising the mast you should have no problems in finding the right winches for the job.

Hints and tips

Obviously the first job is to dig the hole and to make the groundpost. Take the trouble to doublecheck all measurements before you cut or drill or do anything else.

Give the groundpost two coats of red oxide undercoat and three coats of black bitumastic. When this is finished, set it in the hole in the manner already described, and start building the mainmast. This can be painted in the same way. You will have a couple of weeks for

this job as the groundpost requires this time to set solidly in the cement.

The rest of the mast can now be tackled and should be quite straightforward.

An additional refinement is to fit a 4' to 5' length of tube to a bracket about 15 feet up the mainmast. This is hinged by nut and bolt so that it hangs down when the mast is lowered and supports its weight.

No detail of the cord used for the safety latch has been shown either, as tough cord is readily obtainable from many sources.

The weight and balance of the safety latch is shown in Figure 8, and is of course sufficient to enable it to fall back into place when the block on the inner mast has passed it on the way up. But if any doubt should be experienced it is a simple matter to incorporate a mild spring.

Conclusion

Naturally the best bit has been left to

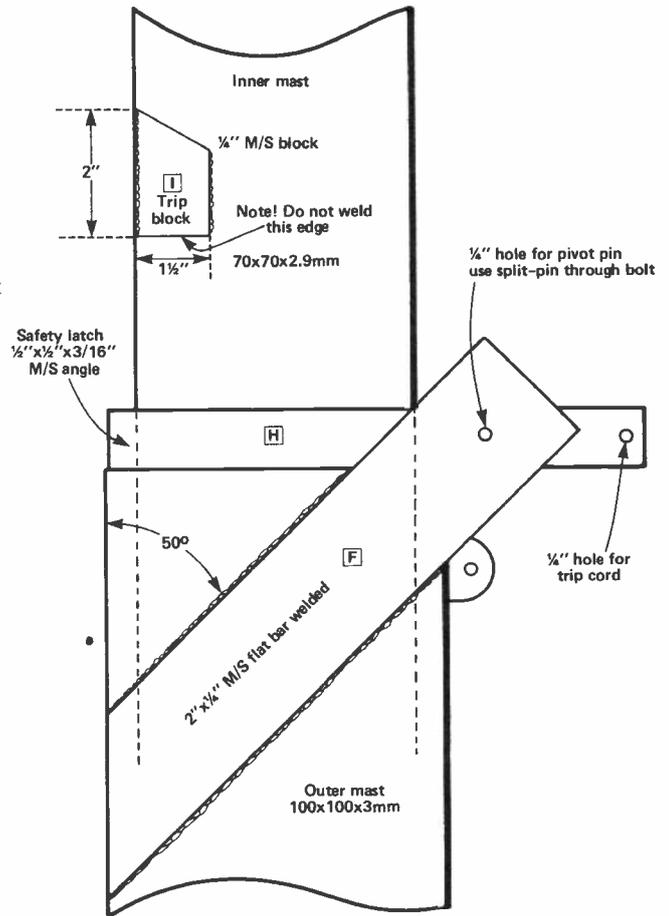


Fig 8 Safety latch detail

the end. How do you lift the mainmast on to the groundpost? The best way (and probably the only way) is to get a few tough guys from the club to come round and help. A Saturday morning is not usually the best time as most local amateurs seem to be busy then.


Although the mainmast weighs nearly 400lbs it is by no means a daunting task to get it in place.

One little extra might be to make up a plastic cover to snugly fit over the inner mast at the junction of the mainmast to prevent water from getting in. A child's bucket and a little ingenuity are all you need for this task.

So there you have it! And the cost? Bearing in mind that I was able to tackle the greater part of the work myself, it came to between £85 and £100.

If you employ a welder then you must expect it to cost a little more, but then, a commercial mast will cost you anything from £285 to £300... Have fun!

DOT MATRIX PRINTERS

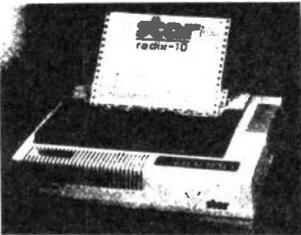

ALL PRINTERS HAVE CENTRONIC PARALLEL INTERFACE UNLESS OTHERWISE STATED. ALL PRINTERS HAVE HI-RES, DOT ADDRESSABLE GRAPHIC MODE. PLEASE SEND SA FOR FULL DETAILS.

EPSON FX 80 160 CPS 10" wide fric. & pin feed	£344 - VAT	£395
FX 100 160 CPS 15" wide fric. & tract feed	£431 - VAT	£495
RX80 FT 100 CPS 10" wide fric. & tract feed	£261 - VAT	£299
RX80T 100 CPS 10" wide tractor feed	£234 - VAT	£269
LO1500 200 CPS Letter quality printer		
8143 RS 20 Interface for FX and RX printers	£29 - VAT	£33
8148 RS202 Interface with 2K buffer, son roll	£60 - VAT	£69
Ribbon Cartridge for RX80 FX80 & MX80	£7 - VAT	£7
Ribbon Cartridge for FX100 & MX100	£12 - VAT	£13
STAR Gemini 10X 120 CPS 10" wide fric. & tract feed	£200 - VAT	£229
Gemini 15X 120 CPS 15" wide fric. & tract feed	£245 - VAT	£289
Delta 10 150 CPS 10" wide fric. & tract feed	£327 - VAT	£375
Delta 15 150 CPS 15" wide fric. & tract feed	£395 - VAT	£459
Radix-10 200 CPS NLO 16K Buffer Par & serial interface downloadable characters incredible value at	£431 - VAT	£495
Radix-15 15" wide version of Radix-10	£518 - VAT	£595
SEIKOSHA GP100A 50 CPS 10" wide tractor feed	£156 - VAT	£179
GP250X 50 CPS 10" wide tractor feed cer. & par	£196 - VAT	£225
GP100VC 300 CPS 10" wide VIC 20 & 64 interf	£174 - VAT	£199
GP500A 50 CPS 10" wide tractor feed	£187 - VAT	£215
GP550A 50 CPS 10" wide tractor feed correspondence quality	£234 - VAT	£269
GP100AS Serial interface ideal for Spectrum with microdrive	£174 - VAT	£199
SHINWA CP80 80 CPS 10" wide friction & tract feed Spare ribbon cartridge for CP80	£187 - VAT	£215
	£6 - VAT	£6
RITEMAN Compact 120 CPS 80 col fric. & tract feed	£200 - VAT	£229
CANON PW1080A 160 CPS 10" wide 27 CPS NLO 24 x 16 matrix	£283 - VAT	£325
PW1155A 160 CPS 15" wide 27 CPS NLO 24 x 16 matrix	£347 - VAT	£399
COLOUR PRINTERS Seikosha GP700A 7 colour 50 CPS printer	£347 - VAT	£399
Canon PJ1080A 7 colour 40 CPS inkjet printer	£391 - VAT	£449
CPP40 40 column 4 colour battery operated	£118 - VAT	£135

ALL OUR PRINTERS HAVE 1 YEAR WARRANTY

BBC MICROCOMPUTER SYSTEM

WE ARE AN OFFICIAL BBC COMPUTER DISTRIBUTOR
DEALER ENQUIRIES ARE WELCOMED

Acorn Electron £199 INC VAT

WE SUPPLY FREE 30 HOUR BASIC BOOK AND A DUST COVER WITH EACH COMPUTER

This is the best microcomputer currently on the market 32K RAM 32K ROM 8 modes of operation full colour full-size keyboard internal expansions such as disc interface speech synthesizer Econet interface in short it is a personal computer capable of expanding into a small business system

BBC Microcomputer Model B	£348 - VAT	£399
BBC Mod B - disk interface	£409 - VAT	£469
BBC Mod B - Econet interface	£389 - VAT	£447
BBC Mod B - disk and Econet interfaces	£450 - VAT	£517
BBC 100K disk drive	£230 - VAT	£264
BBC dual 800K disk drive	£699 - VAT	£803
Torch Z80 disk pack including Z80 2nd processor 64K RAM and CPN operating system - Free Perfect Software	£696 - VAT	£799
BBC Terminal receiver (Augs)	£96 - VAT	£112
BBC cassette recorder and lead	£26 - VAT	£29
Disk interface kit (free fitting)	£84 - VAT	£96
Mod A to Mod B upgrade kit	£70 - VAT	£80
Fitting charge for A to B upgrade kit	£20 - VAT	£23
16K memory upgrade kit	£30 - VAT	£34
Games paddies	£11 - VAT	£12
12" Monochrome monitor incl cable	£89 - VAT	£102
14" Colour monitor incl cable	£199 - VAT	£222
User guide	£10 - VAT	£10
Econet interface (free fitting)	£60 - VAT	£69
Speech interface (free fitting)	£47 - VAT	£54
BBC disk manual - formatting disk	£30 - VAT	£34
Parallel printer cable	£10 - VAT	£11
BBC word processor (vtrw)	£52 - VAT	£59
BBC Fourth language cassette	£15 - VAT	£17
BBC Lisp language cassette	£15 - VAT	£17

APPROVED ECONET SERVICE CENTRE
WE STOCK A LARGE RANGE OF SOFTWARE FOR BBC MICRO INCLUDING ACORN'S OFFICIAL BBC SOFTWARE LONGMAN'S SOFTWARE PLEASE SEND LARGE STAMPED ADDRESSED ENVELOPE FOR FULL DETAILS

TORCH Z80 2nd PROCESSOR For only £347 + VAT

Torch 2nd Processor Z80 is supplied with perfect writer (a powerful Word Processor) perfect speller (spelling checking program - I should have used one for making this advert!) Perfect Filer (A Database Program) Perfect Calc (Spread Sheet) It includes 64K memory (Almost 60K available to user) Fits inside BBC Computer

Z80 2nd Process - Perfect Software	£347 - VAT	£399
Z80 Processor - Perfect Software - Dual 800K Disk Drives	£695 - VAT	£799

GUARANTEED LOWEST PRICES

100% BBC COMPATIBLE MITSUBISHI AND TEAC SLIMLINE DISK DRIVES



These drives are supplied ready cased with all the necessary cables formatting program and User Guide
There are some very useful utilities included on formatting disc e.g
• DISASSEMBLER This is 6502 machine code disassembler
• DUP To copy and rename a file on disc
• FORMAT Formatting program for 40 & 80 tracks
• FREE This utility provides a disk usage analysis
• NDMJMP Enables you to display and modify any part of BBC memory
• MERGE Merge a number of text files into one file
• RELOCATE Downloads a basic program to £80
• SQUIMP Screen dump for EPSON in all graphic modes
• VERIFY Verifies every sector on a disk
• MENU A flexible menu program

Single drive 100K 40 trks single sided	£147 - VAT	£169
Dual drive 200K 40 trks single sided	£286 - VAT	£329
Single drive 200K 40 trks double sided	£173 - VAT	£199
Dual drive 400K 40 trks double sided	£330 - VAT	£379
Single drive 400K 80 trks double sided	£199 - VAT	£229
Single drive 400K 40/80 trks switchable DS	£217 - VAT	£249
Dual drive 800K 80 trks double sided	£382 - VAT	£439
Dual drive 800K 40/80 trks switchable DS	£408 - VAT	£469

All above drives are low power slimline (0.3 A typ at 12v and 0.4 A at 5v per drive). Normally extra power supply is not required the BBC Computer power supply is designed to drive two low power drive (IT IS NOT DESIGNED TO DRIVE INTERNAL ROM BOARD)


40 Track SS/DD diskettes (10 Box)	£18 - VAT	£20
40 Track DS/DD diskettes (10 Box)	£23 - VAT	£26
80 Track SS/DD diskettes (10 Box)	£28 - VAT	£32
80 Track DS/DD diskettes (10 Box)	£30 - VAT	£34

ALL ABOVE DISKETTS ARE CERTIFIED EITHER MEMorex OR DETALIFE

YOUR CONTACTS AT AKHTER ARE

DEALER/BULK ENQUIRIES	HAMAYUN MUGHAL
TELEPHONE ORDERS	PAULA HAYES
DEALER ORDERS	TONY GLOVER
BUSINESS SYSTEMS ENQUIRIES	DENNIS SUTCH
EXPORT ENQUIRIES	MAHAMAD EDIB
ECONET SYSTEM TECHNICAL ENQUIRIES	ALAN LAFFOLEY
ACCOUNTS	CARON ANDREWS
DESPATCH	PAUL SWIFT
REPAIRS	JOHN MAULE

BUSINESS SYSTEMS

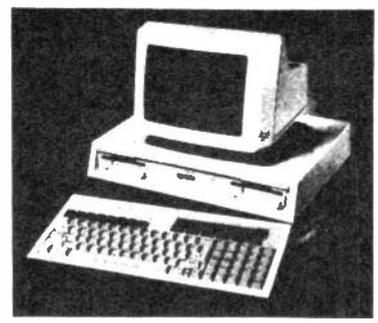

APRICOT - SIRIUS - SANYO IBM - TEXAS - TORCH

APRICOT 'Portable Executive Computer' 16 Bit Micro 256K RAM up to 1.44 megabytes floppy disk storage 3 1/2" Sony disks Portable brief case styling Modem with auto dialler (optional) hard disk optional vast software library (compatible with Sirius 1)
Apricot with Single Drive and Monitor £1690 - VAT
Apricot with Double Drive and Monitor and Free Printer or 2nd Monitor £1890 - VAT

SANYO PROFESSIONAL COMPUTER
16 Bit Micro 128K RAM expandable to 256K Single or Double Disk Drive built in full colour graphics (640 x 200 pixels in 8 colours) IBM compatible Free software. Sanyo MBC 550 128K RAM single drive and free software including Wordstar and Calcstar £749 - VAT
Sanyo MBC555 128K double drive and free software including Wordstar Calcstar Infostar Datastar etc £999 - VAT
SIRIUS 1 Sirius 1 Computer with 128K RAM and 1 1/2 megabyte Floppy disc storage including CP M 86 MS DOS and Microsoft Basic £2195 - VAT

Sirius 1 Computer with 256K RAM and 2 1/2 megabyte Floppy disk storage including C/M 86 MS DOS & Microsoft Basic £2895 - VAT

TORCH
CP500 COMPUTER with colour monitor includes Twin 400K disks Torchnet Operating System (free perfect software (perfect writer, perfect speller, perfect calc, perfect filer) Torchmail Plus (Electronic Mail) Torch Mars (Financial modelling with graphics) Torchnet (Viewdata Access System) Executive Aid (Menu System)
Data! 600 (Link to outside mainframe services i.e Telecom Gold) £2950 - VAT

TEXAS INSTRUMENTS PROFESSIONAL COMPUTER
TI 502 Dual 320K Drives 256K RAM Up to 10 megabyte on board storage possible TI speech command hardware option brings a new level of user friendliness to computing. Allows voice operated keyboard control (Optional) Price £2650 - VAT


MAINTENANCE CONTRACTS ARE AVAILABLE.

DAISYWHEEL PRINTERS



JUKI 6100 20 CPS Bi-Directional Logic seeking 10 12 15 CP1 - PS Spacing 2K buffer, bi setting Daisywheel Singer sheet feeder unit Tractor Unit RS 232 Interface Spare Daisywheel	£349 - VAT	£395
	£217 - VAT	£249
	£52 - VAT	£59
	£17 - VAT	£19
BROTHER HR-15 13 CPS Bi-directional 10 12 15 CP1 - PS Keyboard Unit Single Sheet Feeder Unit Tractor Unit	£344 - VAT	£395
	£139 - VAT	£159
	£217 - VAT	£249
	£95 - VAT	£109
DAISY STEP 2000 20 CPS Unidirectional 10 12 15 CP1	£260 - VAT	£299
SMITH CORONA TP1 12 CPS 10 12 CP1 unidirectional	£208 - VAT	£239


PROFESSIONAL MONITORS

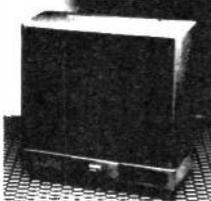

* SANYO
* MICROVITEC
* FIDELITY
* PHOENIX

SANYO DM8112 12" Green screen 18 MHz Hi-Res	£86 - VAT	£99
DM2112 12" Green screen 15 MHz Monitor	£66 - VAT	£75
CD3125 14" RGB Normal Res. Colour Monitor	£173 - VAT	£199
CD3117 14" RGB Medium Res. Colour Monitor	£286 - VAT	£329
CD3115 14" RGB High Res. Colour Monitor	£391 - VAT	£449
MICROVITEC CUB 1431 MS 14" RGB Normal Res. Colour Monitor	£173 - VAT	£199
1451 MS 14" RGB Medium Res. Colour Monitor	£321 - VAT	£369
1441 MS 14" RGB High Res. Colour Monitor	£417 - VAT	£479
FIDELITY Colour Monitor CM14 14" RGB RGBY Composite sound col	£187 - VAT	£215
PHOENIX Phoenix High Res 12" Green Monitor	£66 - VAT	£75
Phoenix High Res 12" Amber Monitor	£69 - VAT	£79

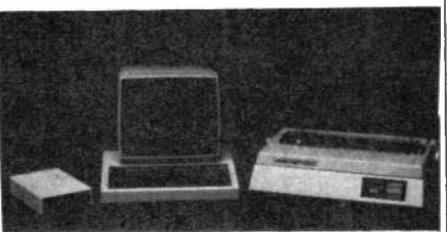COMPLETE WORDPROCESSING SYSTEMS INCLUDING DAISYWHEEL PRINTER From £695 + VAT



SYSTEM 1 BBC Micro model B Wordwise Phoenix monitor Smith Corona TP1 Daisywheel Printer Cassette Recorder + all the necessary cables and documentation £656 - VAT £799.25

SYSTEM 2 BBC Micro model B - Disk Interface, Phoenix Monitor 100K Single Disk Drive Wordwise Smith Corona Daisywheel Printer - all the necessary cables and documentation Price only £895 - VAT £1029.25

SYSTEM 3 BBC Micro model B - Disk Interface Phoenix Monitor Dual Disk Drives 200K Wordwise Smith Corona Daisywheel Printer - all the necessary cables and documentation Price £999 - VAT £1148.85

SYSTEM 4 BBC Micro model B - Disk Interface Sanyo High Res Green Monitor Wordwise (or view) Juki 6100 Daisywheel Printer Single 400K Disk Drive - all the necessary cables and documentation £1049 - VAT £1206.35

SYSTEM 5 BBC Mod B Micro - Disk Interface Sanyo High Res Green Monitor Wordwise (or view) Juki 6100 Daisywheel Printer Dual Disk Drive 800K - all the necessary cables and documentation Price £1195 - VAT £1374.25

SYSTEM 6 Sanyo 16 Bit IBM pc Compatible Micro 128K RAM Single Disk Drive 160K Wordstar Calc Star Sanyo High Res Green Monitor Juki 6100 Daisywheel Printer - all cable and documentation Price Only £1145 - VAT £1316.75

SYSTEM 7 Sanyo 16 Bit IBM pc Compatible Micro 128K RAM Dual Disk Drive 360K Wordstar Calc Star Mailmerge Infostar Spellstar Datastar Sanyo High Res Green Monitor Juki 6100 Daisywheel Printer - all necessary cables and documentation Price £1395 - VAT £1604.25

SYSTEM 8 All the components of System 6 but with Sanyo High Res Colour Monitor and Wordstar with Colour Facilities Price £1445 - VAT £1667.75

SYSTEM 9 All the components of System 7 but with Sanyo High Res Colour Monitor and Wordstar with Colour Facilities Price £1695 - VAT £1949.25

WE CAN ALSO SUPPLY PACKAGES WITH COMPONENTS OF YOUR OWN CHOICE. PLEASE PHONE (0279) 412639 AND ASK FOR HAMAYUN MUGHAL FOR A PRICE.



AKHTER COMPUTER GROUP

28/29 BURNT MILL
HARLOW, ESSEX. CM20 2HU U.K.
Tel. HARLOW (0279) 443521 Telex: 818894 AKHTER G

ORDERING INFORMATION:

We accept official orders from UK Government and Education establishments. Carriage is Free. Normal delivery. If express delivery is required please add £8.00 + VAT per parcel. We accept telephone orders on Barclay and Access Card please ring (0279) 443521 (10 lines) All cheques made payable to "AKHTER INSTRUMENTS"



N.B. ALL VAT INCLUDED PRICES ARE THE CORRECT PRICES. EXCL. VAT PRICES HAVE BEEN ROUNDED UP TO NEAREST POUND.

OPENING HOURS: MON-FRI 9am-6.30pm, SAT 10am-5pm
We welcome callers, no parking problems.

IMPROVING RESISTORS

by Dr CJD Catto

There are occasions when it is worth winding a resistor oneself, for example when an odd value or high wattage low resistance is required. If a precision component is needed, it is advisable to make a four-terminal device, ie by bringing out the current and voltage leads separately. This is best done by spot-welding a pair of voltage tapping points, as shown in *Figure 1*.

Manganin is a convenient material to use for a low value, low temperature-coefficient resistor. It is a good idea to wind a loose non-inductive coil (see *Figure 1*): if the wire is on a former, differential expansion can make the wire act as a strain-gauge, and spoil the low temperature-coefficient of resistance.

There is also the thermal EMF between the manganin and the copper circuit wires, but this is only a few microvolts per °C, and its effect can be made negligible by using a symmetrical layout, with junctions isothermal. For higher powers, the wire can be suspended in a gently-stirred oil-bath.

Alternatively, a temperature-controller can be employed, as shown in the block diagram of *Figure 2*. The full circuit diagram is given in *Figure 3*, and its operation is described below.

Resistance wires made of copper-manganese or quaternary alloys¹ and certain film resistors have a temperature coefficient that passes through zero at some temperature. The circuit shown in *Figure 3* has been used to maintain a

four-terminal resistor R_1 at its zero-TC point, despite changes in the current I_1 passed through it.

The auxiliary heater R_2 brings the block in which R_1 is embedded up to temperature, but the fan F_1 permits efficient extraction of heat if I_1 is increased.

The feedback loop using the thermistor bridge $T_1P_1R_3-7$ and the op-amp N_1 followed by the heater/fan combination ensures that the temperature settles rapidly. The speed of the fan motor is controlled by varying the load presented to the transformer-rectifier inserted in series with the ac supply and the motor. T_1 is mounted in the middle of the block, close to both R_1 and R_2 , to minimise thermal overshoot, and a thermocouple junction T_2 is used to check the temperature.

It is important to bed R_1 in a resilient but thermally-conductive material (eg Redpoint Thermpath) to minimise

strain-gauge effects. The potential-tapping points $v+v-$ are symmetrically disposed, to minimise thermocouple effects.

The somewhat odd supply rails were chosen to fit in with the rest of the equipment, of which this circuit was but one part.

Readers will no doubt be able to simplify the circuit arrangements but, as in any analogue circuit dealing with small signals, it is worth keeping the ac and hum-bearing components separate from the 'precision' side as far as possible.

In the application described, R_1 was employed as the current-sensing resistor of an electromagnetic lens supply with a stability of the order of a tenth of one part per million!

Reference 1: GWC Kay & TH Laby 'Tables of Physical and Chemical Constants' 14th Edn, Longman 1975, pp 105-106.



Figure 1 Voltage tapping points

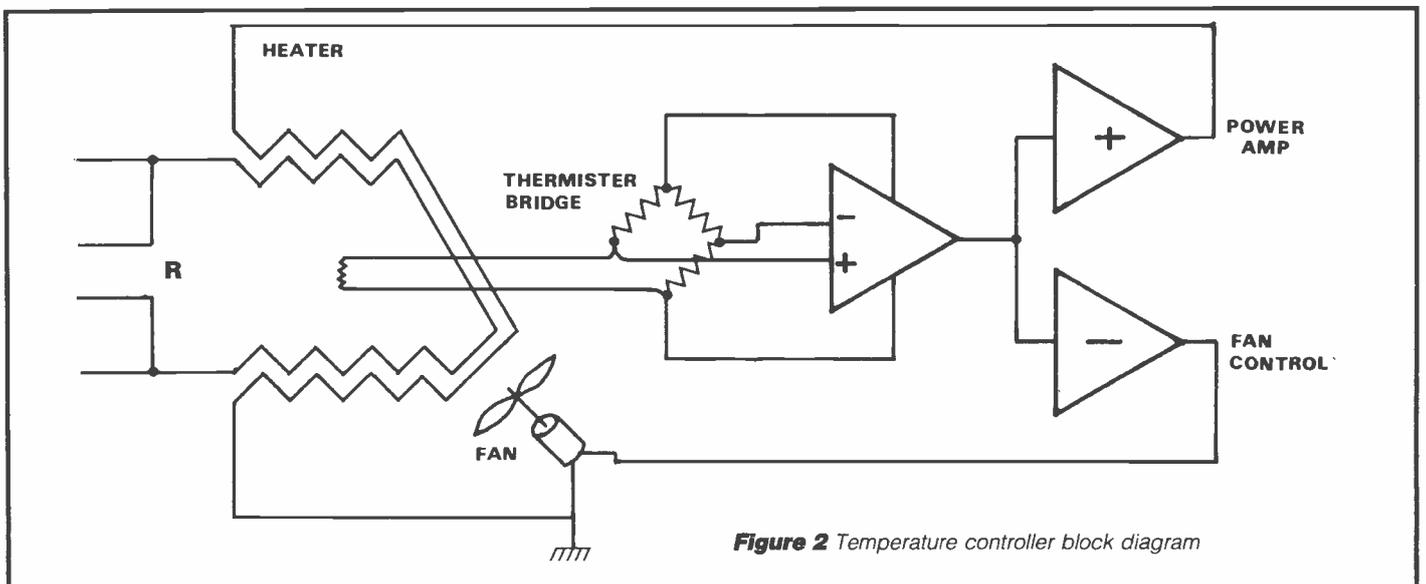


Figure 2 Temperature controller block diagram

IMPROVING RESISTORS


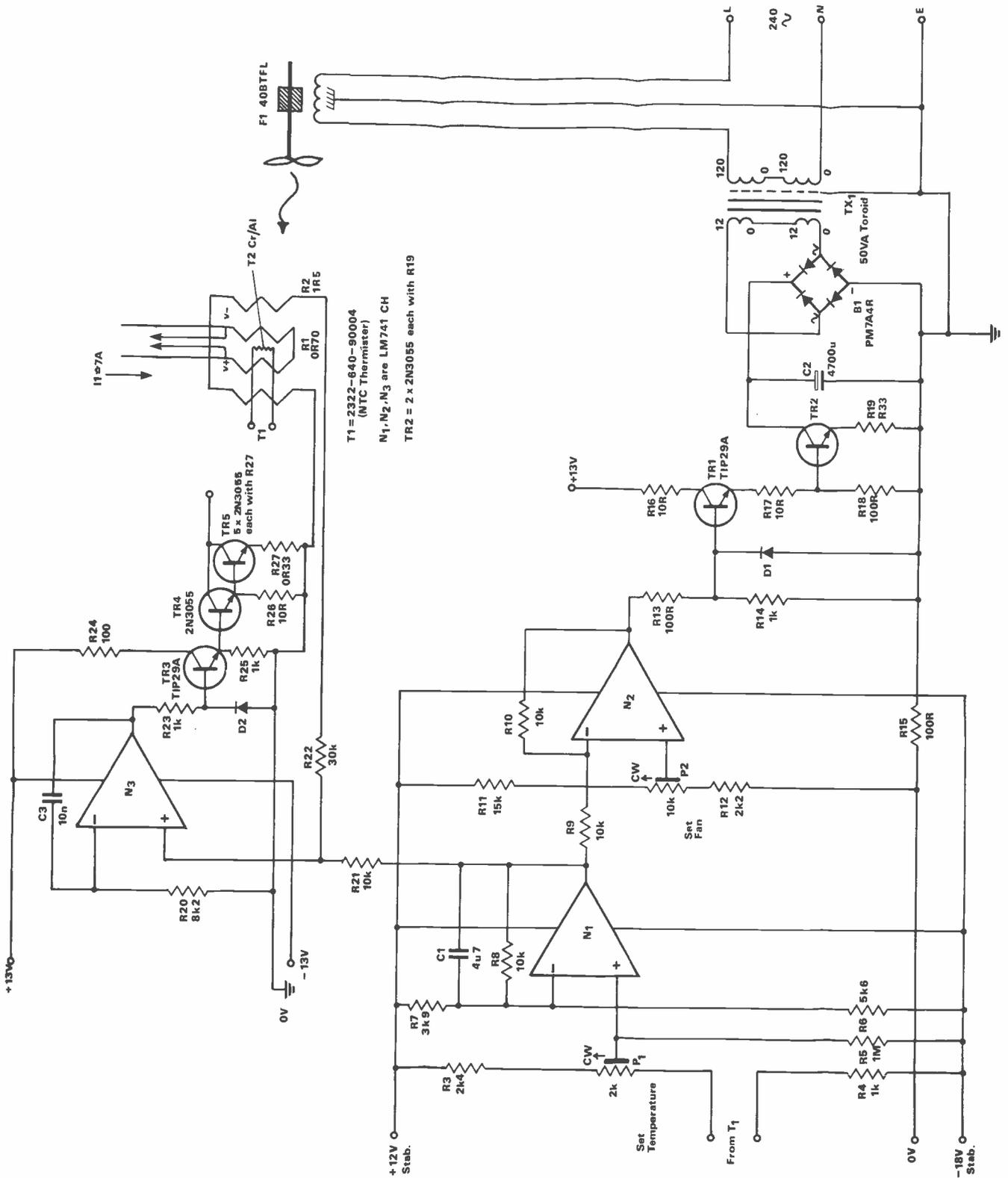


Figure 3 Temperature control circuit

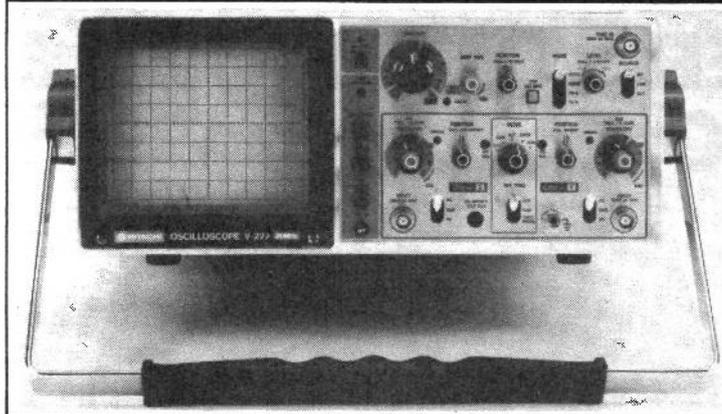

Hitachi Oscilloscopes

performance, reliability, value and immediate delivery!



Hitachi Oscilloscopes provide the quality and performance that you'd expect from such a famous name, with a newly-extended range that represents the best value for money available anywhere.

V-212	20MHz Dual Trace	V-209	20MHz Mini-Portable
V-222	20MHz (illustrated)	V-509	50MHz Mini-Portable
V-203F	20MHz Sweep Delay	V-1050F	100MHz Quad Trace
V-353F	35MHz Sweep Delay	V-134	10MHz Tube Storage
V-422	40MHz Dual Trace	VC-6015	10MHz Digital
V-650F	60MHz Dual Timebase	VC-6041	40MHz Digital

Prices start at around £300 plus vat including 2 probes and 2 year warranty. We hold the range in stock for immediate delivery.

For colour brochure giving specifications and prices ring (0480) 63570
Thurlby-Reltech, 46 High Street, Solihull, W. Midlands, B91 3TB

RADIO & ELECTRONICS WORLD

PCB's

Jan '84	
FAX receiver	£4.65
FAX processor	£4.35
8211	£0.99
7665	£0.99
Cymar Q meter	£2.65
Zener diode checker	£0.99
Feb '84	
Real time clock	£2.45
NiCad charger	£1.65
Crowbar protection	£0.99
Step attenuator	£1.30

PCB'S

March '84	
LM380 Audio amplifier	£0.99
April '84	
10.7MHz oscillator	£0.99
455Hz oscillator	£0.99
May '84	
Signal generator	£1.90
Frequency meter	£4.30
S meter display	£0.99
S meter control	£1.90
FAX receiver	£22.28

KITS

FAX processor (including programmed EPROM)	£34.54
8211	£2.88
Crowbar protection	£3.43
LM380 Audio amplifier	£3.21
10.7 MHz oscillator	£3.22
455kHz oscillator	£1.82
Signal generator	£9.65
(includes case)	
July '84	
VLF converter	£1.60
Teletypewriter Interface	£1.45
All kits include printed circuit board, though are available without, please enquire	

EDWARDSCHILD LTD

We accept Access & Barclaycard/Visa. All prices include VAT & P+P

Tel: (0277) 216433
453a, Becontree Ave
Dagenham
Essex, RM8 3UL




C. M. HOWES

COMMUNICATIONS
FUN TO BUILD KITS BY MAIL ORDER

139 Highview, Vigo, Meopham,
Kent DA13 0UT

Tel: Fairseat (0732) 823129

Enjoy the satisfaction of building your own quality equipment with one of our kits. All kits come with a ready drilled and tinned PCB that has the component locations screen printed on it for easy assembly, all board mounted components, and full, clear instructions. We like to think that our documentation sets our kits apart from the rest. Building is straightforward and fun, so choose a worthwhile project from our expanding range:-

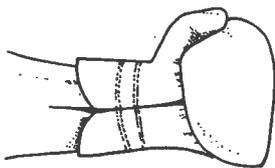

ADD SOME PUNCH!

AP3 AUTOMATIC SPEECH PROCESSOR

Add more "punch" to your signal with this excellent processor. This is the unit described by Dave, G4KQH in the September edition of "Ham Radio Today". We have sold hundreds and hundreds of these, with many customers coming back to buy a second, third or even fourth unit for use with their other rigs. They work well and sound good.

- *Automatically adjusts to the level of your voice to give precise clipping levels.
- *Four selectable clip levels in approx. 6dB steps.
- *Automatically turns itself off when not in use.
- *9 or 12 Volt operation, onboard voltage regulator.
- *Suitable for high or low impedance mics (will even work with an IC251 etc. with a simple mod, we can give you details).
- *Simple to build, with only one adjustment for output level to make.
- *Full instructions, parts list, circuit etc.

KR £14.80, assembled PCB module £19.80

DcRx DIRECT CONVERSION COMMUNICATIONS RECEIVER

This kit is reviewed in the May issue of "Shortwave Magazine" by G3RJV. The article says a lot more than we can in this space. Suffice to say these are very popular with both beginners and experienced operators.

- *Single band versions for 3.5, 10 and 14MHz.
- *12 Volt operation.
- *1 Watt output into an 8 ohm 'speaker' or 'phones.
- *Only one adjustment to make to align the module.
- *All coils ready wound for repeatable results.
- *Balanced FET mixer, FET VFO.

The unit only requires a couple of 50pF tuning capacitors by way of external components to function. We can supply suitable air-spaced devices at £1.50 each while stocks last. **DcRx Kit £13.95, assembled PCB module (aligned) £18.90.** Don't be put off by the low price, this receiver works well and is capable of world-wide reception.

PA/15 2M LINEAR AMPLIFIER 15 Watt

Do you have a 2M hand-held that could do with a boost? Suitable for mobile or base station use this unit will give a 10dB gain with any hand-held having up to 1/2 Watts output. Easy to build, with preformed inductors for simplicity, this unit is also suitable for 1 Watt SSB rigs. An RF switched (or PTT operated) change-over unit is available type C01, see below.

PA2/15 Kit £18.90, assembled PCB module £22.80

PA2/30 2M LINEAR AMPLIFIER 30 Watt

This unit gives approx 8dB gain for use with an IC202, FT290 etc. It puts out a clean signal with margin against overdriving with these popular radios. The PA2/30 includes preformed inductors and PTFE output trimmers for good performance. 13.8 Volt operation. The C01 change-over unit can be used with this item.

PA2/30 Kit £22.90, assembled PCB module £26.90

C01 RF or PTT SWITCHED CHANGE-OVER UNIT

This unit is designed to switch a linear, preamp, or both in and out of line. Suitable for all bands 160 to 2M, with an RF sensitivity of 1/2W for switching. Will switch up to 100W RF output from a linear, 25W max from the rig. Suitable for many uses apart from switching our PA Series Linears.

KR £8.90, assembled PCB module £11.90 (includes a switched bias output on TX and provision for a TX LED indicator).

XM1 CRYSTAL CONTROLLED FREQUENCY MARKER

This very useful piece of test equipment is reviewed in the June issue of "Amateur Radio". A good quality design, this calibrator will help you meet the amateur licence frequency measurement requirements, it can also be used to calibrate almost any receivers' dial. Check that digital display is telling the truth, they often don't! The XM1 has marker outputs at 1MHz, 100kHz, 25kHz and 10kHz intervals, these are usable from longwave up to 70cm. This design features a pulsed ident facility that enables you to distinguish markers from off-air signals on crowded bands. A worthwhile addition to the shack.

KR £15.60, assembled PCB module £19.60

ST2 CW SIDE-TONE UNIT or PRACTICE OSCILLATOR

The ST2 provides a nice soundig sinewave note, either from your key, or from the output of your rig by RF sensing. The unit will work with positive or negative keying, up to 15 volts, and by direct connection to the antenna feeder of an HF or 2M rig up to 25W. The unit can also function with a pick-up antenna without direct connection as long as it is near enough to the radiating piece of wire string or whatever. With inline connection the unit will work with QRP rigs of as little as 1/2W output on the HF bands.

KR £8.20, assembled PCB module £8.90

If you would like further information on any product, simply drop us a line enclosing an SAE, we have an information sheet on each item. We aim to keep everything in stock and delivery within 7 days.

PLEASE ADD 60p P&P to your total order value

73, Dave, G4KQH, Technical Manager

SUMMARY OF GREEN PAPER ON MOBILE RADIO

Land mobile radio services, especially those in densely populated areas, have suffered from congestion of radio channels for a number of years with frustrating consequences for users and industry alike. But relief – in the form of the release of broadcasting Bands I and III for land mobile radio services – is at hand. This release of frequencies will double the amount of spectrum currently available for mobile radio services.

At the beginning of 1985 the 405-line television services in the United Kingdom will close down and the radio frequencies (known as Bands I and III) will become available for land mobile radio services. The growth of land mobile services (radiotelephone systems and other forms of mobile radio communication) has been inhibited for some years because of the shortage of suitable radio spectrum.

The release of Bands I and III will constitute one of the biggest ever additions to land mobile spectrum in the United Kingdom. At least 1000 channels should be available in London in Band III alone – a substantially larger block of spectrum than that to be used for the two cellular radiotelephone systems to be operated by Racal Vodafone, formerly Racal Millicom, and TSCR.

In spite of the restrictions imposed by the shortage of spectrum, the use of mobile radio has grown at a rate of eight per cent per annum or more for many years. If this were maintained, the number of mobile radios in use would more than double in 10 years.

The relief to the current congestion would, therefore, be only temporary unless the spectrum were used efficiently. The Government believe that multi-channel trunked radio systems, which offer considerable gains in spectrum efficiency, will make the best use of the available radio channels.

Individual users providing their own communication services are unlikely to justify the allocation of the blocks of channels necessary to achieve trunking gains and the Government have therefore identified service providers – companies offering communication services to others – as the likely major operators in Bands I and III.


If the approach that the Government suggest is adopted, it should be possible to meet the demands for mobile radio spectrum until the end of the century.

Opportunities

The release of such a large block of radio spectrum will permit an enormous increase in the use of mobile radio, in terms of the numbers of people having access to it and the range of services offered, and will lead to the creation of new jobs in both the manufacturing and the service industries.

Most radio communication in the UK is local in character. The spectrum in Band III will make it possible to set up a network of local and regional systems meeting this need.

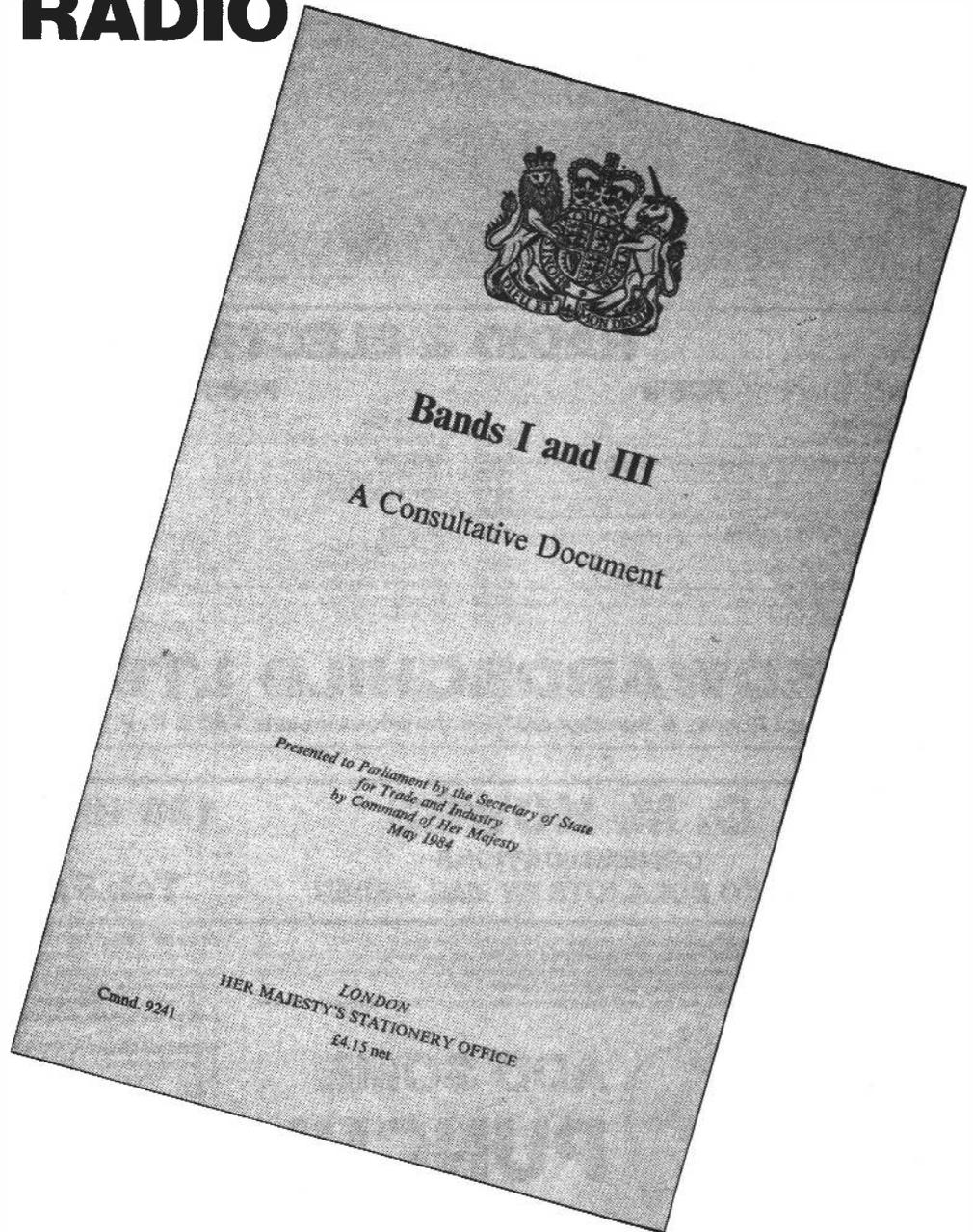The demand for mobile radio services will probably mean that the first systems are established in the London area and in the other main conurbations. In these



areas, where the mobile radio bands are generally overcrowded, the systems will benefit both new and established users.

The former will be able to obtain an immediate service from a company operating in the new bands; the latter will have the option of transferring to one of the new services.

The size of the new systems has to be decided, but it is clear that there will be opportunities for large operators to bid for substantial blocks of 20 channels or more to provide trunked services and message handling facilities.

An operator of this scale would be capable of meeting the mobile communications requirements of even the largest existing private mobile radio systems.

The size of such an operator may suggest a need for it to accept certain obligations regarding access to the system by others: the Government will wish to consider any views that are expressed on this question.

Smaller operators should also be able to bid for more modest frequency allocations, with the prospect of expansion if they were successful.

Competition

The Government's belief is that the introduction of new competing services will be the best way of ensuring that the consumer's needs are met.

Within the new bands, competition, and the ability of successful companies to obtain additional radio channels, will

MOBILE RADIO

lead to the development of a range of radio services that reflects the range of consumer demands.

These services will also provide some additional competition to the newly established cellular radiotelephone operators. In this way the consumer will have a choice in the quality of service he obtains and the price he pays.

The question of competition with the cellular radiotelephone systems will be an important one. By 1989 the cellular operators will have achieved virtually national coverage. Before then it should be possible to judge whether there is a need for a further national radiotelephone system.

The existence of further systems would add to the competition in the provision of this type of service, and small and medium-sized systems in Band III will offer a local alternative to the cellular systems. The use of fully interconnected services on a substantial scale would, however, make significant inroads on the overall capacity on Band III to accommodate future mobile radio services.

There may also be implications for the development of the cellular systems which are undertaking major and high investments and are subject to special licence conditions and public interest obligations. A related question will also be the continuation of the existing VHF

radiotelephone service operated by British Telecom.

New technology

The availability of the new block of spectrum should act as a stimulus to the development of new radio technologies. The Government propose that part of Band III should be used exclusively for the introduction of new and advanced communication systems, eg single side band and time division code multiplexing, since these offer the means of meeting future growth in demands for radio communication.

Companies with an interest in developing advanced communication systems may wish to put forward proposals for using this part of the band.

Operators

The Telecommunications Act 1984 provides that from July 1 1984 the Director General of Telecommunications should be available to advise the Secretary of State on what mobile radio services are required and how effective competition in their provision can best be ensured.

The selection of the operators in different areas, and decisions as to the number and size of operators will require careful consideration. The Government hope that the Director General will assist in reaching the necessary decisions.

The issues

The key issues addressed in the consultative document and on which the Government invite views are:

- a) – what services should new systems be expected to provide?
- what size should the systems be initially?
- how many systems should be licensed in each area?
- what obligations and conditions should be attached?
- b) – how should the candidates be selected?
- should restrictions be imposed on who is allowed to apply, in particular on public telecommunications operators and on manufacturers?
- c) – should the Government license further national radiotelephone systems?
- should local services be permitted to provide full interconnection with the PSTN and if so what conditions should be imposed to avoid excessive demands on the spectrum?

There may be other issues that those commenting will wish to raise, but these are the ones the Government see as crucial to the introduction of fully competitive services benefiting all areas of Great Britain.




**ATU KITS
CAPACITOR KITS
BALUNS
AERIAL FEEDER-
SPREADER KITS**

**TAU SYSTEMS LIMITED
SKELMERSDALE, ENGLAND**

**Phone
0695-24662**

TAU Old Fashioned Radio Engineering enables our Aerial Tuner Units to perform at an unsurpassed High Level, by virtue of being Infinitely Variable they will tune almost any Transceiver/ Aerial.

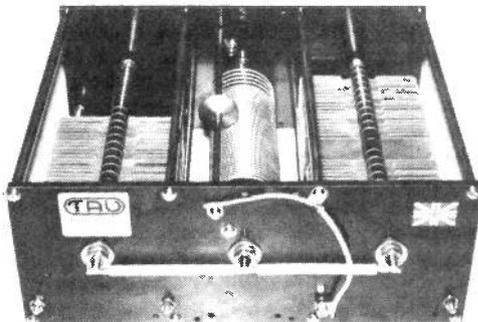The best Transceiver in the World is only as good as the Aerial System its obliged to operate through – Realise its Full Potential with a Tau ATU.



ULTIMATE SPC SUPER-TRANSMATCH ATU

The Laws of Physics haven't changed over the years.

Get back to Basic Principles and enjoy complete Signal Readability and Full Strength – courtesy of:-

TAU SYSTEMS LTD – NOBODY MATCHES UP TO US!

ALL COMPONENTS ARE BRAND NEW, TO FULL SPECIFICATION AND GUARANTEED FOR ONE YEAR FROM DATE OF PURCHASE NO CHARGE FOR POSTAGE OR PACKING. Just add 15% for VAT and send your cheque/cash/ postal order to us for a by return service.

VIDEO CONNECTING LEADS & KITS

VL10 Video Kit – Universal – any video to any video.....	£6.00
VL01 UHF plug to UHF plug..... 1.2 metres.....	£1.95
VL02 BNC plug to BNC plug..... 1.2 metres.....	£3.30
VL03 BNC plug to UHF plug..... 1.2 metres.....	£2.00
VL04 BNC plug to Phono plug..... 1.2 metres.....	£1.60
VL05 UHF plug to Phono plug..... 1.2 metres.....	£1.50
VL06 Phono plug to Phono plug..... 1.2 metres.....	£1.00
VL07 'F' plug to 'F' plug..... 3 metres.....	£3.00
VL08 'F' plug to 'F' plug..... 1.2 metres.....	£2.40
VL09 Video Kit – 2 metres Video Cable terminating in Phono plug at each end, 2 pieces Phono to UHF adaptor, 2 pieces Phono to BNC adaptor.....	£3.40

COMPUTER TAPE. TOP QUALITY CASSETTES FOR THE HOME COMPUTER

C10 £0.90 each – £3.50 pack of 5	C15 £1.00 each – £4.00 pack of 5
AUDIO TAPE BASF C90 LH Extra. Packs of 5.....	£4.00

AUDIO LEADS & TV FLY LEADS

AL 01 Co-Ax plug to Co-Ax plug white..... 2 metres.....	£1.15
AL 32 Co-Ax plug to Co-Ax plug white..... 4 metres.....	£1.80
AL 33 Co-Ax plug to Co-Ax plug white..... 10 metres.....	£3.45
AL 34 Co-Ax plug to Co-Ax socket white..... 2 metres.....	£1.25
AL 03 2 pin Din plug to 2 pin Din plug grey..... 3 metres.....	£0.85
AL 04 2 pin Din plug to 2 pin Din plug grey..... 10 metres.....	£1.40
AL 05 2 pin Din plug to 2 pin Din socket grey..... 3 metres.....	£0.85
AL 06 2 pin Din plug to 2 pin Din socket grey..... 5 metres.....	£1.00
AL 07 2 pin Din plug to 2 pin Din socket grey..... 10 metres.....	£1.40
AL 12 5 pin Din plug to 5 pin Din plug grey..... 1.2 metres.....	£0.90
AL 13 5 pin Din plug to 5 pin Din plug mirror Image..... 1.2 metres.....	£1.25

DIGITAL MULTIMETER 10MT013

LCD – Max Indication 1999 – Measurements:- DC Volts; AC Volts; DC Amps (Max 10 amps); Resistance; Diode and hFE – Battery powered (PP3) – Battery included – Test leads included – many other features – full instructions. Complete.....

£50.00

A full list of what is available will be sent with each order. Stamped addressed envelope all enquiries.

ORDER TODAY – YOUR GOODS TOMORROW – FROM:-

**McLELLAND
DATATEXT**

**Unit 3A, Bankfield Industrial Estate, Kitson Road, Leeds LS10 1NT
Telephone 0532 455169; Telex 556282**

DATA COMMUNICATIONS



How to get started

In the 1980s, data communication by amateur radio takes many forms: RTTY, AMTOR, Packet Radio, mailboxes and digital repeaters are just a few examples. This article from *Datacom*, the journal of the British Amateur Radio Teleprinter Group, describes some of the more popular techniques, and outlines how BARTG can help individual amateurs to get started.

Different forms

RTTY, AMTOR and Packet Radio are all examples of digital data communication, allowing text or computer data to be transmitted to a distant point by radio.

RTTY (*Radio Teleprinter*) is the oldest and simplest of these modes, whereby messages typed at a teleprinter keyboard at one end of the radio link appear as printed characters at the other end, in the same manner as the familiar office telex machine. In fact, many amateurs still use surplus telex machines, but nowadays these are being replaced in many stations by home microcomputer systems with visual display units (VDUs), which are much cleaner and quieter and more flexible.

AMTOR (*AMateur Teleprinter Over Radio*) is a computer-driven data communication system, incorporating auto-

matic error detection and correction facilities, dramatically reducing errors caused by interference. The main characteristic of AMTOR is that messages are broken down into 3-character blocks, and the receiving station acknowledges successful receipt of each block before the transmitting station sends the next one. Messages are transmitted at about the same speed as RTTY, and almost all the errors appearing at the receiving end are due to typing mistakes!

Packet Radio is a more complex mode, intended for high integrity data links. The main features of Packet Radio are its very low undetected error rate, message transfer speeds about 15-20 times faster than RTTY or AMTOR, and the capability automatically to route messages to specified destinations. Packet Radio also allows several independent QSOs to be conducted at the same time on a single frequency, thus conserving valuable spectrum space.

The basic requirements

All of these modes of data transmission have very similar basic requirements. At the transmitting end, message characters are encoded into streams of bits (binary digits, or elements), which can

have two states: by convention, a binary '1' is usually called the *Mark* state, and a binary '0' is called the *Space* state. These bits are fed into a Tone Generator, such that a *Mark* produces a high audio frequency tone, and a *Space* produces a low audio frequency tone. It is these tones which modulate the transmitter.


At the receiving end, the high and low audio tones appearing at the loudspeaker or headphone output of the receiver are routed to a Terminal Unit (TU). The TU detects the tones and converts them back to *Mark* and *Space* signals to drive the teleprinter or computer.

Character codes

The sequence of *Mark* and *Space* bits used to represent each character is agreed internationally. Several different codes are used, depending on the mode.

In standard RTTY, each character is represented by 5 data bits, plus Start and Stop bits, as defined in the International Telegraph Alphabet (ITA) No 2. Also used in RTTY are the Murray and Baudot codes, which are similar to ITA2.

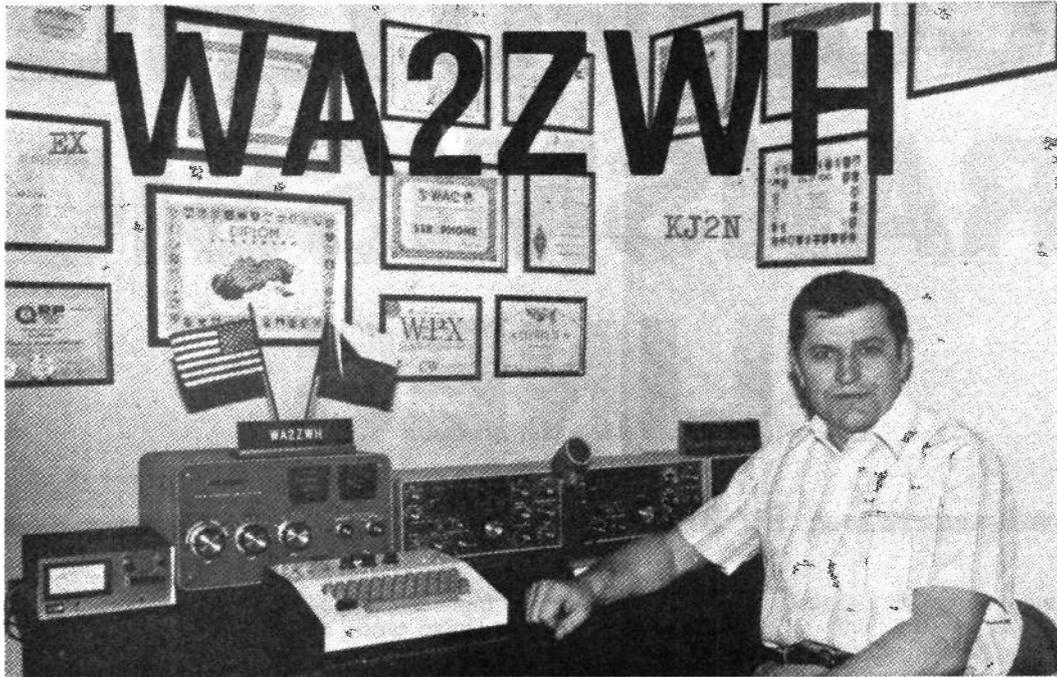A further code sometimes used in RTTY is the International Telegraph Alphabet No 5. This has 7 data bits per character, and is more or less the same



as the American Standard Code for Information Interchange (ASCII, pronounced 'askee'), used in almost all home computers.

AMTOR uses a special 7-bit code defined in CCIR Recommendation 476. The main characteristic of this code is that all valid characters contain a combination of 4 *Mark* bits and 3 *Space* bits. This fact is made use of at the receiver – if a received character contains this combination of *Marks* and *Spaces* it is assumed to be valid, but if not it is rejected. AMTOR uses synchronous transmission, and message characters do not have Start or Stop bits.

Packet Radio uses ASCII for message characters, together with special control characters for packet framing, routing and error checking. The way in which these characters are used is defined in the recently agreed AX.25 protocol, which closely resembles the High Level Data Link Control (HDLC) protocol used in commercial packet networks.

Speeds

For ITA2, the two speeds in general use are 45.45 and 50 baud. The former is by far the most popular on the HF bands, because of the worldwide availability of surplus American equipment. However, the increasing availability of 50 baud telex machines in Europe means that there is now a trend to this speed, particularly at VHF.

For ITA5/ASCII, the most usual speeds are 110, 300, 600 and 1200 baud.

For AMTOR, the speed is always 100 baud. However, because of the error detection techniques used in this mode, about half the time is taken up by handling control codes, so the effective message rate is about the same as 50 baud RTTY.

Most present day Packet Radio networks operate at VHF/UHF, allowing

high data rates, typically 1200 baud. However, Packet Radio is still in its infancy, and it is likely that other standards will emerge in due course.

The signal

As mentioned above, the usual way of sending a data signal is by modulating the transmitter with the *Mark* and *Space* tones. In practice, these tones are used to produce frequency shift keying (FSK). The most common method is standard FSK, whereby the *Mark* tone appears as one radiated frequency and the *Space* tone is 170Hz below this frequency. The 170Hz shift is standard for all lower speeds, with 425Hz and occasionally 850Hz being used at the higher speeds.

At VHF, use of Audio Frequency Shift Keying (AFSK) of an FM transmitter is popular. The standard frequencies are 1445Hz for *Mark* and 1275Hz for *Space*.

Where to find data signals

Data signals are to be found on virtually all bands from 160m to 70cm. FSK is the only mode used on the HF bands, but both FSK and AFSK are used at VHF. The most popular frequencies in use today are:

RTTY: 3.590, 14.090, 144.600, 145.300 and 432.600MHz

AMTOR: 3.588, 14.075 and 144.590MHz

RTTY repeaters operate on 70cm.

The equipment

The equipment required to operate RTTY can be very simple. The cheapest approach is to buy a teleprinter for a few pounds and to connect this to a home-made Tone Generator (for transmission) and a Terminal Unit (for reception). BARTG publishes a book entitled *RTTY the Easy Way*, which contains full circuit

and constructional details of suitable units, together with full information on how to connect them together and set them up. As an alternative to a mechanical teleprinter, the home micro can be used instead, and several trade suppliers provide suitable RTTY programs for the more popular machines.

To run AMTOR, a more ambitious setup is needed. This can be a complete 'black box', or alternatively there are kits available containing the necessary control hardware and software, for interfacing to an existing teleprinter or micro.

A similar situation exists in the world of Packet Radio, which requires a complex Terminal Node Controller (TNC) to handle the transmission and reception of packets. Again, TNCs are available as 'black boxes' or as kits.

BARTG

The British Amateur Radio Teleprinter Group was formed in 1959, and exists to encourage and promote interest in all modes of data communication. The Group publishes a regular magazine covering technical matters, contest news, tutorials for beginners and general gossip. Other services include a Sunday RTTY news bulletin, contest sponsorship, and the supply of specialist components and books.

Most important, the Group offers advice and assistance to individual members to get their systems working. The current annual membership subscription is £5. No application form is necessary – simply send the £5 (cheques etc made payable to 'BARTG'), together with a note of your name, address and callsign (or a QSL card) to Mr John Beedie, G6MOK, 161 Tudor Road, Hayes, Middlesex UB3 2QG. Tel: 01-561 0010.

Published by kind permission of the British Amateur Radio Teleprinter Group.

COMPUTING TRANSMISSION LINES

By Brian Kendal, G3GDU

Whenever a radio signal is passed along a wire, that wire, together with its environment forms a transmission line which has a characteristic impedance – and losses.

In most equipment, wiring is kept short and, in consequence, losses are minimal. Sometimes, however, particularly at the higher frequencies, even the shortest connections are significant in terms of wavelength and losses can only be minimised by matching the impedance of these connections to their associated circuits.

When designing and constructing aerials, it may often prove necessary to insert a quarter wave matching section of some unusual impedance. Often this is achieved by paralleling lines of standard impedance, such as using two lengths of 300ohm ribbon to make a 150ohm section, but if the required impedance is known, it is often quite simple to manufacture an accurate section from materials at hand.

A more common example is in the construction of VSWR meters. Many of these use the case as the screen of the transmission line.

Consequently the selection of the correct diameter of wire between the input and output connectors can ensure that the correct impedance is maintained.

The insertion of the meter in an aerial circuit will not then upset the VSWR previously attained nor affect the loading on the transmitter.

In each of these and many more cases, it is quite possible to calculate the necessary parameters with pencil, paper and a book of log tables.

Recently, however, when working on a problem which required this type of calculation, it occurred to me that a program for calculating the parameters of the most common forms of transmission lines would form a most useful addition to my program library.

The formulae for the calculations were found in the *Radio Data Reference Book* by G Jessop G6JP, published by

the RSGB. This gives the basic impedance calculations for seven types of transmission line.

One of these formulae is unfortunately ambiguous, so it was decided to omit this from the program until it could be confirmed from an alternative source.

The program may be considered to comprise seven sections, the menu and calculations for each of the six different types of transmission line.

The menu (lines 10 to 210)

This is the section of the program in which the various options are listed and the appropriate calculation selected.

This description is for the BBC Model B Micro, but could be adapted for other popular machines.

The first line of significance is '30 MODE 6'. Prior to writing this program, it had been decided that wherever possible, simple diagrams of the selected transmission line should be given.

MODE 6 was chosen as an appropriate low definition mode which could also be output to the printer without a graphics screen dump routine. On line 70, the gap between the words 'USING' and 'AIR' is to prevent the latter word being split onto two lines and also improve the presentation of the display. This technique has also been used elsewhere in the program.

Some readers may be unfamiliar with the style of line 210. This is a single line statement which equates exactly to: PRINT 'SELECT REQUIRED CALCULATION' INPUT A

The succeeding line, 220 is also a complex statement, this being the equivalent of:

IF A = 1 GOTO 230
IF A = 2 GOTO 650 etc.

However, only six valid alternatives exist but it is possible for 0 or a higher number than six to be keyed in. This would confuse the computer and cause it to initiate an error message. To prevent this, the line is completed by:

ELSE GOTO 10

which, if an invalid selection is made,

loops the program back to the beginning.

At this point it might be worthwhile to explain the PRINT statements which appear throughout the program. It is well known that this causes a blank line.

In some cases, however, it appears as 'PRINT' or 'PRINT"', these causing the computer to output two or three blank lines. Some computers, such as the ZX81, will not accept this statement and it will be necessary to include a separate 'PRINT' statement for each blank line required.

Calculations

The second part of the program starts with a CLS in order to remove the menu from the screen. This is followed by a simple diagram. In this, the parallel lines are built up from 'underlines' and the arrow heads on lines 270 and 300 are the 'raise the power' symbol whilst that on line 290 is a lower case 'V'.

The three parameters for a parallel

TRANSMISSION LINE FORMULAE PARALLEL STRIPS (SLAB LINES)

$Z = 377 a/b$ if $a < b$

where a is the spacing and b is the width of the line

PARALLEL WIRE

$Z = 276 \text{ LOG } D/d$ if $d < D$

where d is the diameter of the wire and D the spacing

WIRE PARALLEL TO INFINITE PLANE

$Z = 138 \text{ LOG } D/d$ if $d < D$

where d is the diameter of the wire and D the spacing

WIRE PARALLEL TO TWO INFINITE PLANES

$Z = 138 \text{ LOG } [(4D)/(2\pi)]$ if $d < D$

where d is the diameter of the wire and D the spacing

CIRCULAR COAXIAL

$Z = 138 \text{ LOG } (1.178D/d)$

where d is the diameter of the inner wire and D the side length of the outer

COMPUTING TRANSMISSION LINES

```

10 REM THIS PROGRAM CALCULATES THE CHARACTERISTIC IMPEDENCE OF VARIOUS
TYPES OF TRANSMISSION LINES
20 REM BY BRIAN KENDAL, G3GDU
30 MODE6
40 CLS
50 PRINT
60 PRINT
70 PRINT "IMPEDENCE OF TRANSMISSION LINES USING
AIR DIELECTRIC"

80 PRINT
90 PRINT "1. PARALLEL STRIPS"
100 PRINT
110 PRINT "2. PARALLEL WIRE"
120 PRINT
130 PRINT "3. WIRE PARALLEL TO INFINITE PLATE"
140 PRINT
150 PRINT "4. WIRE BETWEEN TWO INFINITE PLATES"
160 PRINT
170 PRINT "5. CIRCULAR COAXIAL"
180 PRINT
190 PRINT "6. SQUARE COAXIAL"
200 PRINT
210 INPUT "SELECT REQUIRED CALCULATION",A
220 ON A GOTO 230,650,1040,1460,1900,2010 ELSE GOTO 10
230 CLS
240 PRINT
250 PRINT "PARALLEL STRIPS (SLAB LINES)"
260 PRINT "
-----"
270 PRINT "
a          If a<<b"
280 PRINT "
-----"
290 PRINT "
^         ^"
300 PRINT "
|         |"
310 PRINT "
-----"
320 PRINT
330 INPUT "DO YOU REQUIRE a, b OR Z",B#
340 IF B#="a" GOTO 380
350 IF B#="b" GOTO 450
360 IF B#="Z" GOTO 570
370 GOTO 330
380 PRINT
390 INPUT "INPUT a",a
400 PRINT
410 INPUT "INPUT b",b
420 PRINT
430 PRINT "THEN a = "(b*z)/377
440 PRINT
450 INPUT "PRESS C FOR FURTHER CALCULATION OR M FOR MENU",X#
460 IF X#="C" GOTO 230
470 IF X#="M" GOTO 10
480 GOTO 450
490 PRINT
500 INPUT "INPUT a",a
510 PRINT
520 INPUT "INPUT Z",z
530 PRINT
540 PRINT "THEN b = "(377*a)/z
550 PRINT
560 GOTO 450
570 PRINT
580 INPUT "GIVE a",a
590 PRINT
600 INPUT "GIVE b",b
610 PRINT
620 PRINT "THEN Z = "(a*377)/b "ohms"
630 PRINT
640 GOTO 450
650 CLS
660 PRINT
670 PRINT "PARALLEL WIRE"
680 PRINT "
<TWIN LINE>"
690 PRINT
700 PRINT "LET d BE WIRE DIAMETER AND D THE SPACING"
710 PRINT
720 INPUT "DO YOU REQUIRE d,D OR Z",W#
730 CLS
740 IF W#="d" GOTO 770
750 IF W#="D" GOTO 880
760 IF W#="Z" GOTO 960
770 PRINT
780 INPUT "INPUT d",d
790 PRINT
800 INPUT "INPUT Z",z
810 PRINT
820 PRINT "THEN d = "(z/276)*((2*d)/(1+(z/276)))
830 PRINT
840 INPUT "PRESS C FOR FURTHER CALCULATION OR M FOR MENU",U#
850 IF U#="C" GOTO 650
860 IF U#="M" GOTO 10
870 GOTO 840
880 PRINT
890 INPUT "INPUT d",d
900 PRINT
910 INPUT "INPUT Z",z
920 PRINT
930 PRINT "THEN D = "(d*(10^(z/276)))/z
940 PRINT
950 GOTO 840
960 PRINT
970 INPUT "INPUT d",d
980 PRINT
990 INPUT "INPUT D",D
1000 PRINT
1010 PRINT "Z = "(276*(LOG((2*D)/d))) " ohms"
1020 PRINT
1030 GOTO 840
1040 CLS
1050 PRINT
1060 PRINT "WIRE PARALLEL TO INFINITE PLATE"
1070 PRINT
1080 PRINT "
o"
1090 PRINT
1100 PRINT "
-----"
1110 PRINT "d = DIAMETER OF WIRE AND D = SPACING"
1120 PRINT
1130 PRINT
1140 INPUT "DO YOU REQUIRE d, D OR Z",S#
1150 IF S#="d" GOTO 1180
1160 IF S#="D" GOTO 1290
1170 IF S#="Z" GOTO 1380
1180 PRINT
1190 INPUT "INPUT D",D
1200 PRINT
1210 INPUT "INPUT Z",z
1220 PRINT
1230 PRINT "THEN d = "(D/10^(z/138))
1240 PRINT
1250 INPUT "PRESS C FOR FURTHER CALCULATION OR M FOR MENU",R#
1260 IF R#="C" GOTO 1140
1270 IF R#="M" GOTO 10
1280 GOTO 1250
1290 PRINT
1300 INPUT "INPUT d",d
1310 PRINT
1320 INPUT "INPUT Z",z
1330 PRINT
1340 PRINT "THEN D = "(d*(10^(z/138)))
1350 PRINT
1360 GOTO 1250
1370 GOTO 1360
1380 PRINT
1390 INPUT "INPUT d",d
1400 PRINT
1410 INPUT "INPUT D",D
1420 PRINT
1430 PRINT "THEN Z = "(138*LOG(D/d)) "ohms"
1440 PRINT
1450 GOTO 1250
1460 CLS
1470 PRINT
1480 PRINT "WIRE PARALLEL TO TWO INFINITE PLATES"
1490 PRINT
1500 PRINT "
-----"
1510 PRINT "
^         ^"
1520 PRINT "
o         o"
1530 PRINT "
-----"
1540 PRINT "
-----v"
1550 PRINT
1560 PRINT "WIRE OF DIAMETER d PLACED CENTRALLY
BETWEEN TWO INFINITE PLAT
ES SPACED D"
1570 PRINT
1580 INPUT "DO YOU REQUIRE d, D OR Z",O#
1590 IF O#="d" GOTO 1620
1600 IF O#="D" GOTO 1730
1610 IF O#="Z" GOTO 1820
1620 PRINT
1630 INPUT "INPUT D",D
1640 PRINT
1650 INPUT "INPUT Z",z
1660 PRINT
1670 PRINT "THEN d = "(4*D)/(PI*(10^(z/138)))
1680 PRINT
1690 INPUT "PRESS C FOR FURTHER CALCULATION OR M FOR MENU",N#
1700 IF N#="C" GOTO 1460
1710 IF N#="M" GOTO 10
1720 GOTO 1690
1730 PRINT
1740 INPUT "INPUT d",d
1750 PRINT
1760 INPUT "INPUT Z",z
1770 PRINT
1780 PRINT "THEN D = "(PI*d*(10^(z/138)))/4
1790 PRINT
1800 GOTO 1690
1810 GOTO 1800
1820 PRINT
1830 INPUT "INPUT d",d
1840 PRINT
1850 INPUT "INPUT D",D
1860 PRINT
1870 PRINT "THEN Z = "(138*LOG((4*D)/(PI*d))) " ohms"
1880 PRINT
1890 GOTO 1690
1900 CLS
1910 PRINT
1920 PRINT "CIRCULAR COAXIAL"
1930 PRINT
1940 PRINT "INNER CORE DIAMETER d AND SCREEN
DIAMETER D"
1950 PRINT
1960 INPUT "DO YOU REQUIRE d, D OR Z",K#
1970 IF K#="d" GOTO 1990
1980 IF K#="D" GOTO 1290
1990 IF K#="Z" GOTO 1380
2000 GOTO 1960
2010 CLS
2020 PRINT
2030 PRINT "
-----"
2040 PRINT "
|         |"
2050 PRINT "
|         |"
2060 PRINT "
|         |"
2070 PRINT "
|         |"
2080 PRINT "
|         |"
2090 PRINT "
|         |"
2100 PRINT "
|         |"
2110 PRINT "
|         |"
2120 PRINT "
|         |"
2130 PRINT "
|         |"
2140 PRINT "INNER WIRE DIAMETER d, OUTER CASE SIDE D"
2150 PRINT
2160 INPUT "DO YOU REQUIRE d, D OR Z",J#
2170 IF J#="d" GOTO 2210
2180 IF J#="D" GOTO 2320
2190 IF J#="Z" GOTO 2400
2200 GOTO 2160
2210 PRINT
2220 INPUT "INPUT D",D
2230 PRINT
2240 INPUT "INPUT Z",z
2250 PRINT
2260 PRINT "THEN d = "(1.178*D)/(10^(z/138))
2270 PRINT
2280 INPUT "PRESS C FOR FURTHER CALCULATION
OR M FOR MENU",I#
2290 IF I#="C" GOTO 2010
2300 IF I#="M" GOTO 10
2310 GOTO 2280
2320 PRINT
2330 INPUT "INPUT d",d
2340 PRINT
2350 INPUT "INPUT Z",z
2360 PRINT
2370 PRINT "THEN D = "(d*(10^(z/138)))/1.178
2380 PRINT
2390 GOTO 2280
2400 PRINT
2410 INPUT "INPUT d",d
2420 PRINT
2430 INPUT "INPUT D",D
2440 PRINT
2450 PRINT "THEN Z = "(138*LOG(1.178*D/d)) "ohms"
2460 PRINT
2470 GOTO 2280
2480 END

```

COMPUTING TRANSMISSION LINES

strip line are line spacing (a), line width (b) and impedance (Z). Line 330 asks which of these is required.

In an INPUT statement, the computer expects the answer to be a number and will not accept a letter. It will, however, accept a 'string variable', so the requirement can be satisfied by the term 'B\$'.

The formula for parallel strip lines is $Z = 377 \times (a/b)$

when b is much larger than a.

This expression can also be transposed to give either 'a' or 'b' in terms of the other two parameters.

Lines 340 to 360 select the appropriate calculation and line 360 is a simple method of repeating the question should an invalid selection be made.

In the first of these calculations, the known parameters are input on lines 390 and 410, and the calculation is performed on line 430.

Line 450 invites either a further calculation or a return to menu, this being achieved at lines 460 and 470 with Line 480 as a 'backstop' in case of an invalid selection.

The alternative transpositions of the formula are handled in the same way in Lines 490 - 560 and 570 - 640, the only difference being that the selection of further calculation or menu is achieved by looping back to Line 450 with a GOTO statement.

With one exception, each section of

the program works in the same way, the only difference being the graphics and the formulae. The single exception is for 'Circular Coaxial' for which the formula is the same as that for 'Wire Parallel to an infinite Plate'.

For this, it seemed superfluous to repeat the calculation, so after selecting the required parameter, the program was looped back to the appropriate part of the earlier section.

Testing and using the program

The best, in fact the only way to test a program is to run it, so, after having input the program, key 'RUN'.

On the screen should appear a menu giving six options. First, however, check the invalid selection routine by keying '7', '8', or '9'. The screen should just flicker and the input number disappear.

Now check the first option: 'Parallel Strips'. Press '1' and the screen should change to a diagram in the upper part of the screen with the question below: 'DO YOU REQUIRE a, b OR Z'.

Select 'a' and the words 'INPUT b' will appear. Input a number (say 10) and 'INPUT Z' will be printed beneath. Input another number (say 100) and below will be written:

'THEN a = 2.65251989'

and further down the screen:

'PRESS C FOR FURTHER CALCULATION OR M FOR MENU'.

Press 'C' and the previous calculation will be deleted and the diagram plus 'DO YOU REQUIRE a, b OR Z' will return.

This time select 'b' and use the result of the previous calculation with the value of Z as before.

If the formula has been correctly entered, the answer should be the original 'b'. If all is well, again repeat using 'a' and 'b' to calculate 'Z'.

Using this technique, each section may be checked and if all is well, the program may be used with confidence.

Postscript

This program was written for the BBC 'B' OS 1.2 computer. As only about 5K of memory is used, it should also be suitable for the BBC 'A'. For other makes of machine, it is possible that the graphics may not prove suitable. If so, 'MODE 6' on line 30 and the lines describing the graphics throughout the program could be removed without any effect on the calculations.

Minor alterations may also be necessary due to variations in the dialect of these machines.

A final and very important point to remember is that all the calculations have assumed an air dielectric. Should any other material be used, the value of Z calculated should be multiplied by $1/\sqrt{K}$ where K is the dielectric constant of the material.

REG WARD & CO. LTD
AXMINSTER, DEVON

Largest Amateur Radio Stockist in the South West

YAESU	ICOM	TRIO
FTOHE HF TX	IC751 AF TX	TS930S HF TX
FT980 HF TX	IC745 HF TX	TS830S HF TX
FT102 HF TX	IC730 HF TX	TS530S HF TX
FT77 HF TX	IC290D 2M TX	TS430S HF TX
FT757 HF TX	IC490 70CM TX	TS130S HF TX
FT290 2M M/M TX	IC271 2M B/STX	TR9130 2M M/M
FT790 70CM MM TX	IC27 2M FM	TR7930 2M FM
FT480 2M MM TX	IC2E 2M H/H	TW201 2M FM
FT726 2M/70CM BS TX	IC02E 2M H/H	TW401 70CM FM
FT208 2M H/H	IC4E 70CM H/H	TW4000 2M/70CM FM
FT708 70CM H/H	IC04E 70CM H/H	
FT203 2M H/H	ICR70 RX	TR2500 2M H/H
FT230 2M FM	ICR71 RX	TR3500 70CM H/H
FM730 70CM FM		
FRG7700 RX		

Above normally always in stock plus full range of accessories. Prices on request.

Complete range of ancillary equipment by Microwave Modules. Mutek, Datong, Drae, Welz, BNOS, Hansen, Hinouno, Kempro. Aerials by Jaybeam, Mini, TET, Hygain G Whip

Western Parade West St
Axminster Devon EX 13 5NY
Telephone: Axminster (0297)34918
Open: Mon-Fri 9.00-5.30
(Weds 9.00-1.00) Sat 9.00-5.00
Access Instant Credit Barclaycard

Radio & Electronics World —
For all aspects of practical amateur radio

Don't take a chance on being able to get your copy

AVOID DISAPPOINTMENT
Place a regular order with your newsagent

Should you have any difficulties obtaining a copy, phone (0277) 219876 or write to Circulation Department, **Radio & Electronics World**, Sovereign House, Brentwood, Essex CM14 4SE

NEWSAGENT ORDER FORM

Radio & Electronics World

The communications, electronics & computers magazine

To (name of newsagent)

Please order a copy of **Radio & Electronics World** for me every month

NAME.....

ADDRESS.....

.....

.....

Newstrade distributors: Seymour, 334 Brixton Road, London SW9 7AG. Tel: 01-733 4444

Amateur RADIO

For all two-way radio enthusiasts


THE PERFECT COMPLEMENT TO
RADIO & ELECTRONICS WORLD

DON'T MISS YOUR COPY

With regular features like Current Comment, DX Diary, Straight and Level, Angus McKenzie's equipment review, SWL, Rally Calendar and Free Classified Ads, and a host of special features in each issue, make sure you place a regular order for **Amateur Radio** with your newsagent or take out a post free subscription now, while the offer lasts

SUBSCRIPTION BENEFITS

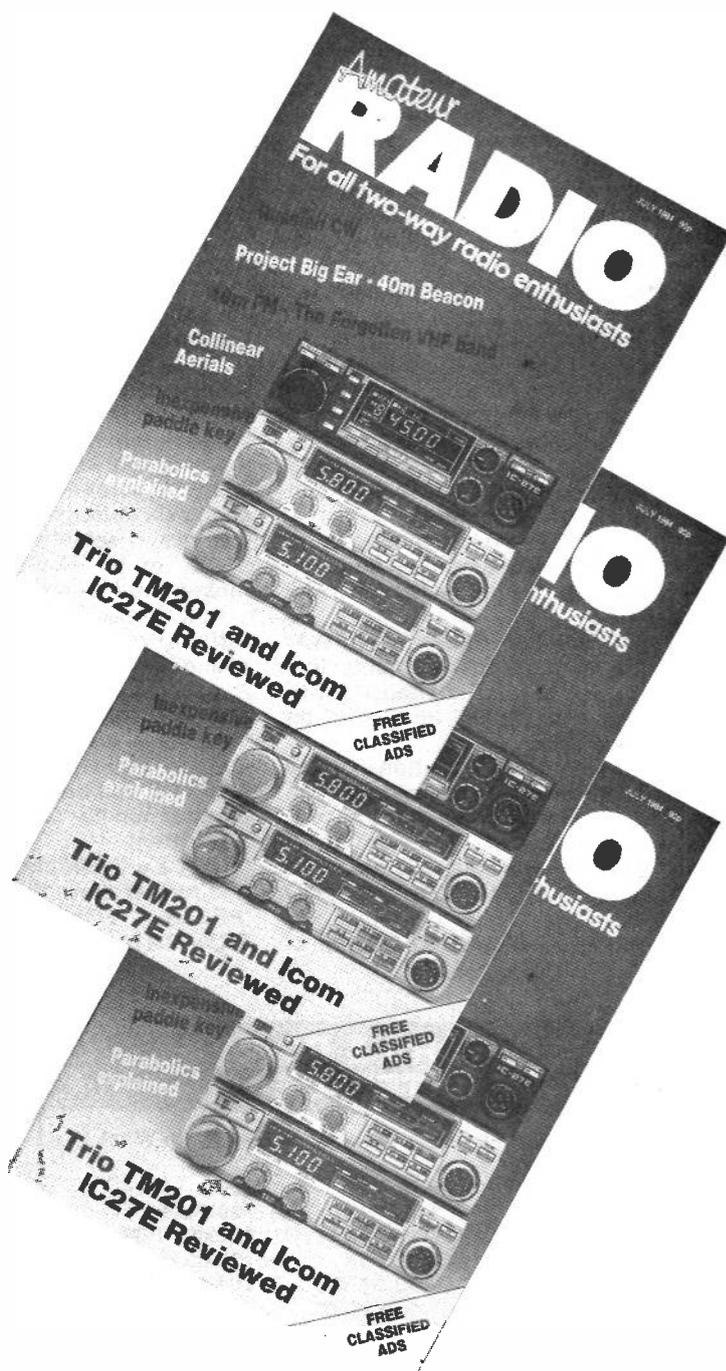- ... delivery to your door by publication date each month
- ... inflation proof – price guaranteed for 12 months



On sale NOW at your newsagent

AMATEUR RADIO SUBSCRIPTION ORDER FORM

To: Subscription Department • Amateur Radio •
513 London Road • Thornton Heath •
Surrey • CR4 6AR. Tel: 01-684 3157

PLEASE SUPPLY: (tick box) for 12 issues, all rates include P & P

Inland £10.80
World-Surface £11.65
Europe-Air £16.30
World-Air £24.40

NAME

PAYMENT ENCLOSED: £

Cheques should be made payable to Amateur Radio. Overseas payment by International Money Order, or credit card.

ADDRESS

CREDIT CARD PAYMENT  

..... Postcode

Signature RE0884

ONE NIGHT'S WORK

The Brother EP44 is a very useful typewriter and printer, but if one does a lot of listing or typing it is advisable to use a power pack.

Not all 6V supplies are suitable, as the printer solenoid causes a current pulse of several amperes, and if the power source does not have a low impedance, the input voltage falls to a point where the data is corrupted.

The makers supply a suitable mains unit, but unless this is left permanently switched on, the plug to the printer must be withdrawn when not in use so that the internal batteries will keep the memory refreshed.

To avoid this inconvenience, I decided to use rechargeable batteries, coupled to a 12V dc supply which I already had. The circuit is shown in *Figure 1*.

Four cells are used, giving a nominal 4.8V-5V, but provided they are kept well charged the working voltage is about 5.5V and the printer operates on 32 column listings, which are the most demanding as regards power supplies.

The circuit is very simple, comprising four 1/2C cells (1.2AH) in series, charged by a constant current using a BD136 regulated to about 100mA. A green LED gives a reference voltage between input and base, and also indicates that the circuit is operating.

Optionally, a switch can be fitted to cut out the charging, or, as shown by dotted lines on *Figure 1*, to give a trickle charge. The whole unit is housed in a suitable box, the transistor being mounted on an aluminium strip, more for convenience than for a heatsink (*Figure 2*).

A lead with an output connector to fit the EP44 is required: note that the centre socket of the connector is *negative* and the outer sleeve is *positive*.

Typing aid

This device is an aid to typing, as it was found that the LCD display viewing angle is such that one must lean over the keyboard to read it. A wedge prism is made to fit over the display (*Figure 3*). This gives a greatly improved viewing angle. The prism can be cut and filed from 1/4 inch perspex, and polished with fine wet and dry paper and metal polish.

Small pieces of card or thin plastic are glued to the ends as supports. The top surface should be roughly parallel with the keyboard, and it is fitted as shown in *Figure 4*.

The dimensions are not critical: within limits, the greater the angle of the prism, the further back one can sit and view the display, but the design shown seems satisfactory.

EP44 EXTRAS

by A M Tucker

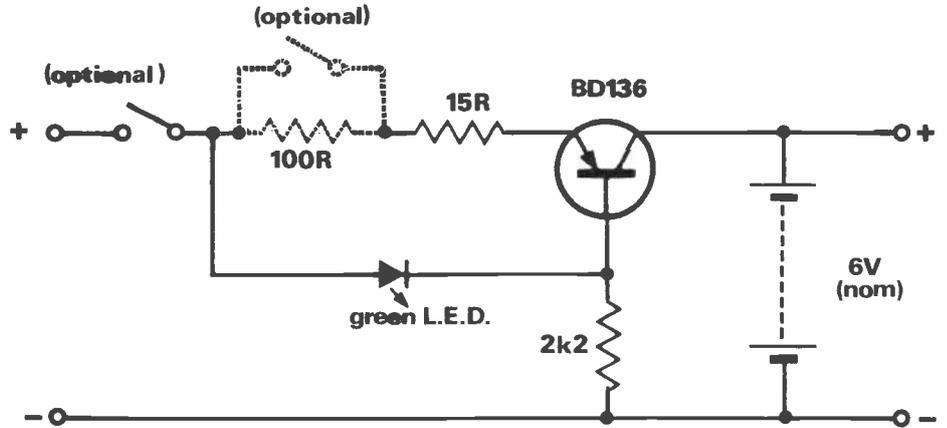


Figure 1 Circuit diagram

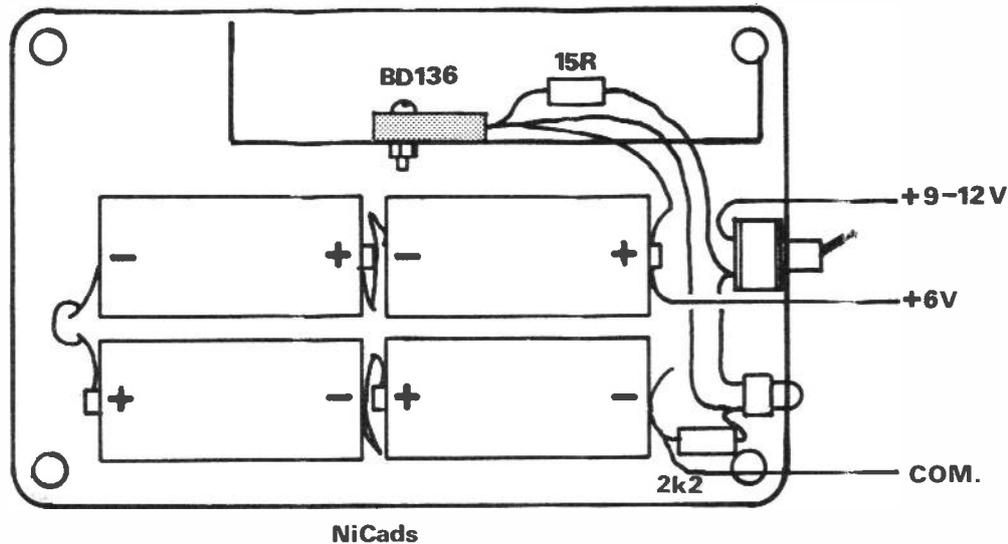


Figure 2 Component layout

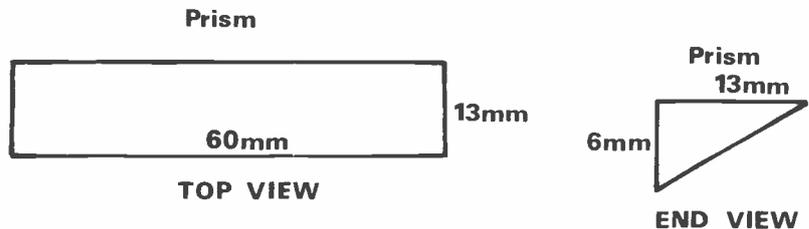


Figure 3 Prism constructional detail

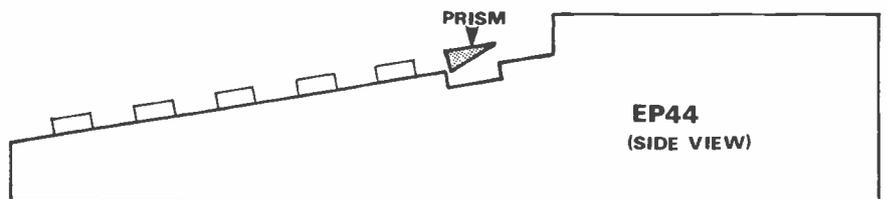


Figure 4 Prism location

AMATEUR RADIO WORLD

Compiled by Arthur C Gee G2UK

Greenwich Mean Time Centenary

The Greenwich Mean Time Centenary was celebrated by radio amateurs by the operation of two stations with the call-signs GB0GMT and GB1GMT respectively. These stations were operated by the St Dunstan's College ARS throughout June. Contacts made will be confirmed in due course, by a special QSL card supplied by the National Maritime Museum.



The measurement of 'Time' goes back to antiquity – possibly as far back as 1500 years BC. The activities of man have, from the creation, been regulated by the natural time scale provided by the daily rotation of the earth giving periods of light and dark, ie day and night.

The first man-made time recorders kept a record of the position of the sun in the sky during its daily apparent passage from sunrise to sunset and even today, the time scale adopted for general use must approximate to solar time.

In the 19th century, there were observatories in many countries making observations for the determination of time. Attempts were made to co-ordinate these activities and in 1884 an international conference was held in Washington DC, USA, at which it was agreed that the meridian of Greenwich, England, should be standard reference meridian for the measurement of time – hence the origin of Greenwich Mean Time.

The measurement of time is now a most sophisticated scientific discipline. It has come a long way from sundials to caesium beam atomic clocks, with their split second accuracy. Chod Harris, VP2ML, gives a very good description of 'WWV,' the Time and Frequency Radio Station at Boulder, Colorado, in his 'DX' column in the April last *73 Magazine*.

Readers interested in this topic should read it. Chod makes a case for every amateur radio station operator interested in DX having one very accurate clock in the shack, set at UTC. Whilst we

don't go quite so far as he makes out in his column, we do agree that a really accurate clock is a boon in the shack.

The writer acquired several years ago one of Cambridge Kits' MSF Radio Clocks. This is a real 'radio clock,' in that it receives radio signals from the British Time Signal radio station at Rugby on 60KHz and displays them in real time on a digital display unit.

This gives absolutely accurate time and whilst occasional severe electrical interference or very poor propagation conditions may at times distort the display – when the error is quite obvious.

UOSAT-2 back in action

No doubt, by the time this appears in print, most readers will have heard the good news that UOSAT-2 is back in action, transmitting telemetry data again – after ten weeks silence.

Problems arose on the morning after launch, when UOSAT-2 did not respond to repeated commands from the Surrey University Satellite Command Station. Then began a long series of checks to establish the cause of the trouble, made all the more difficult by the fact that according to the telemetry so far recorded, there was nothing wrong at all! Daily attempts to gain command continued to prove unsuccessful.

Then, over the weekend of May 12, radio amateurs at the Stanford Research Institute, California, using a very sensitive radio receiving station located in Greenland, picked up faint signals on 1.2GHz. These indicated that the command receiver of UOSAT-2 was switched on. This important discovery confirmed not only that the spacecraft was still operating, but also that it was in its predicted orbit.

Armed with this encouraging information, Neville Bean and Roger Peel, of the University of Surrey UOSAT Project team, made a further attempt on Monday 14 May, to recover command of UOSAT-2.

Attempts using 144MHz were unsuccessful but, on the next orbit, commands using 438MHz resulted in the main data beacon being powered-up! The signals from the beacon are again as strong as they were immediately following launch and the telemetry indicates all seems pretty okay. The battery voltage is 14.6 volts, which is as it should be and the temperature of the satellite is between -5 to 0 degrees centigrade, ie within expected values. More tests can now be initiated, to see if the cause of the shutdown can be ascertained.

Computerisation of licensing

The licensing of radio amateurs is now being administered by the Post Office on behalf of the Department of Trade and Industry, who remain responsible for all the other aspects of the amateur radio service.

Ever since the first radio amateurs were licensed in the UK, the licensing system has been carried out by manual means.

Due to the significant increase in the number of licensees recently, the manual system has been unable to cope, so it was decided to go over to a central computer system.

To assist in this changeover, all UK licensees are being sent a request from the Post Office to confirm their name, address etc.

If this applies to you, be warned, do read the notes on the back of the letter sent with it before you complete the form, or you may make mistakes!

News

During the discussions following the recent AMSAT-UK AGM, suggestions were made that a feasibility study be made into the possibility of funding and launching a radio communication satellite within the ambit of AMSAT-UK.

The Irish Department of Communications recently released the 'new' HF amateur radio bands for use by Irish radio amateurs. These are 10.100MHz to 10.150MHz; 18.068MHz to 18.168MHz and 24.890MHz to 24.990MHz.

The Bulgarian Everest Expedition has used amateur radio for its means of communication. Due to poor propagation conditions, it is reported that communication via OSCAR 10 may be used at times.

Around the 23rd April last, a large group of sunspots began to appear over the limb of the sun. As it came more into 'view,' it was apparent that it was to be one of the largest groups seen for many years.

This was somewhat unexpected, as we are at present in a sunspot minimum period. The group subsequently produced some of the highest solar flux levels ever recorded. Very high levels of absorption, aurora and magnetic disturbances were experienced.

Secondary solar activity peaks such as this one have been observed before in sunspot cycles. It is possible this one may improve propagation conditions for HF communication during several months ahead.

BI-PAK BARGAINS

HIGH QUALITY MODULES FOR STEREO, MONO & OTHER AUDIO EQUIPMENT

O/No.	POWER R.M.S.	MAX SUP. VOLTAGE	PRICE
AL 30A	10 Watts	30V	£4.95
AL 60	25 Watts	30-50V	£5.92
AL 80	35 Watts	40-60V	£8.75
AL 120	50 Watts	50-70V	£15.22
AL 250	125 Watts	50-80V	£20.60

Stabilised Power Supplies — Output current 2.5 Amps

O/No.	AC Input Price
SPM 120/45	40-48V £8.05
SPM 120/55	50-55V £8.05
SPM 120/65	60-65V £8.05

Stereo Pre-Amplifier
O/No. Supply Vtg. Price
PA 100 30/55V £18.50

Mono Pre-Amplifiers — Operating Vtg. 40-65V

O/No.	Price
MM 100 Suitable for Disco Mixer	£14.75
MM 100G Suitable for Guitar Pre-Amp Mixer	£14.75

Magnetic Cartridge Pre-Amplifier
O/No. MPA30. Sup Vtg. 20-30V. Price £4.29

Monographic Equaliser
GE 100 MKII 10 Channel
OUR PRICE ONLY £20.00
Full Specifications and Data available on request. Please send self-addressed envelope.

PRECISION MORSE KEYS

Well designed beginners key. Fully adjustable. Dims: Base 82mm x 45mm. O/No. VP 122. **£1.85**

ANTENNA SWITCH 2 and 3 WAY

Co-axial switch for one transceiver to two antennae or one antenna to two transceivers. Dims: 86 x 55 x 32mm (Body). O/No. VP 113 **£4.50**
As above but 3-way. O/No. VP 114 **£4.75**

HIGH PASS FILTER/SUPPRESSOR

CB/TV. High pass filter. Reduces unwanted signals picked up by antenna. Dims: 45 x 25 x 17mm. O/No. VP 115 **45p**

LOW PASS FILTER

Designed to reduce harmonics on the VHS and TV band. Cut-off frequency: 30MHz. V.S.W.R.: Less than 1.2 to 1. Insertion loss: -0.2dB @ 27MHz. Impedance: 50ohms. Dims: 80 x 55 x 40mm. O/No. VP 116 **£2.75**

ANTENNA COUPLER

Transceiver/car radio antenna coupler. With co-axial cables. One co-axial terminates in antenna plug and the other in PL259 plug. Dims: 67 x 46 x 30mm. O/No. VP 117 **£2.00**

TAPE RECORDER SWITCH

Unit to control motor of tape recorder. 1.8m cord and 2.5mm plug attached. On/Off switch. Dims: 55 x 20 x 20mm. O/No. VP 127 **£1.00**

DC-DC POWER SUPPLY

DC to DC adaptor. Plugs into car cigar lighter aperture. Output 3, 4.5, 6, 7.5, 9, 12V @ 800mA. Has universal output spider plug, also 9V battery snap and polarity reversing facility. O/No. VP 119 **£2.45**

SPEAKER PROTECTOR

Limits voltage to speaker or to the permissible max., by automatically introducing a resistor in series with speakers. When excessive voltage is reduced the unit resets itself. Electronic voltage-sensing relay circuit. Spring terminals. Cut-off level adjustable from 10W-120W. Full instructions included. Dims: 85 x 74 x 25mm. O/No. VP 118 **£9.95**

ELECT & PIEZO BUZZERS

PIEZO
Miniature round piezo-electric buzzer White plastic Low consumption
Frequency: 4kHz approx.
Output 70dB (A) @ 1 typ
Power 12Vdc 4mA
Dims: 22 (dia) x 11.5mm
Fixing Centres: 26.5mm
O/No. VP 107 **95p**

PIEZO
Piezo buzzer White plastic 90mm leads. For use on a.c. mains Frequency: 3.5kHz approx.
Output 85dB (A) @ 1m typ
Power 240Va c. 5mA
Dims: 32 (dia) x 14mm
Fixing centres: 38mm
O/No. VP 108 **£1.15**

ELECTRONIC
Miniature electronic buzzers Solid state Ivory plastic 150 leads. Frequency: 500 Hz approx.
Dims: 22 x 16 x 15mm
Output: 82dB (A) @ 1m typ
Fixing centres: 26mm
3V 25mA: O/No. VP 82 **6V 25mA: VP 83**
9V 25mA: O/No. VP 84 **12V 25mA: VP 86**
80p each

SUB-BOX

A neat swivelling disc provides close tolerance substitution resistors of 36 preferred values from 5ohms to 1Kohm. Simply fix clips into circuit and swivel until optimum result is achieved.
O/No. VP 112 **£4.75**

MINIATURE VICE

Miniature plastic and metal vice with strong suction base for portability. Single action to secure or release suction. Plastic jaws with rubber pads 20mm wide, open out to 40mm. Dims: 85 x 65 x 60mm approx.
FANTASTIC VALUE
O/No. VP 95 **ONLY £1.60**

LEARN A LINGO! PILLOW SPEAKER

Slim under pillow unit. 80hms 2" speaker 1.5m lead with 3.5mm mono jack plug. Black. Dims: 65 (dia) x 17mm. O/No. VP 88 **£1.25**

METRIC & BRITISH MEASURES

Steel tapes in sturdy ABS plastic case. Silk wrist strap. These yellow coated convex tapes have inch and metric graduations. Automatic push-button return.
2m long x 13mm wide O/No. VP 89 **£1.00**
3m long x 13mm wide O/No. VP 90 **£1.50**
5m long x 16mm wide O/No. VP 91 **£2.00**

BATTERY TESTER

Tests all types of battery including standard, NICAD, Alkaline etc. Takes all standard sizes including 6V lantern batteries and watch/hearing aid cells. Also tests fuses and lamps by means of internal 9V (PP3) battery. Can also be used to recharge NICAD batteries by means of external 3.12V d.c. power supply (not included). Full instructions provided. Dims: 185 x 103 x 30mm. O/No. VP 101 **£7.00**

FM MONITOR

FM monitor for 2 metre band. All metal. Attached earphone. PL259/SO239 connectors. 144MHz 10W maximum. Dims (body) 55 x 30 x 23mm. O/No. VP 120 **£4.20**

DUMMY LOAD

50 ohms 30W UHF co-axial plug fitting (PL259). O/No. VP 121 **£5.20**

PICK-UP COIL

Large telephone pick-up coil for high sensitivity. Suction pad to stick to telephone. 30cm lead to 3.5 jack plug. Connects direct to cassette recorder. Dims: 32 (dia) x 17mm (body) 36mm (dia) sucker. O/No. VP 87 **£1.00**

VALUE PACKS

Pak No.	Qty	Description	Price
VP1	300	Assorted Resistors Mixed Types	£1.00
VP2	300	Carbon Resistors 1/2 Watt Pre-Formed	£1.00
VP3	200		£1.00
VP4	150	1 Watt Resistors 100 ohm 1M Mixed	£1.00
VP5	200	Assorted Capacitors All Types	£1.00
VP6	200	Ceramic Caps Miniature - Mixed	£1.00
VP7	100	Mixed Ceramic Disc 1pf - 56pf	£1.00
VP8	100	Mixed Ceramic Disc 56pf - 015pf	£1.00
VP9	100	Assorted Polyester/Polystyrene Caps	£1.00
VP10	60	C280 Type Caps Metal Foil Mixed	£1.00
VP11	100	Electrolytics - All Sorts	£1.00
VP12	60	Bead Type Polystyrene Min Caps	£1.00
VP13	50	Silver Mica Caps Ass. 5pf - 150pf	£1.00
VP14	50	Silver Mica Caps Ass. 180pf - 4700pf	£1.00
VP15	50	High Voltage Disc Ceramic 750v - 8kv Mixed	£1.00
VP16	50	Wirewound Res. 9W (avg) 1 ohm - 12k	£1.00
VP17	50	Metres PVC Covered Single Strand Wire Mixed Colours	£1.00
VP18	30	Metres PVC Covered Multi Strand Wire Mixed Colours	£1.00
VP19	40	Metres PVC Single/Multi Strand Hook Up Wire Mixed	£1.00
VP20	6	Rock Switches 5 Amp 240v	£1.00
VP21	20	Pcs Pls. 1 - 2 & 4 mm Plugs & Sockets Matching Sizes	£1.00

VP22	200	Sq Inches Total Copper Clad Board Mixed Sizes	£1.00
VP23	20	Assorted Slider Pots Mixed Values	£1.00
VP24	10	Slider Pots 40mm 22K 5 x Log 5 x Lin	£1.00
VP25	10	Slider Pots 40mm 47K 5 x Log 5 x Lin	£1.00
VP26	20	Small 125v Red LED'S	£1.00
VP27	20	Large 7v Red LED'S	£1.00
VP28	10	Rectangular 2 Green LED'S	£1.00
VP29	30	Ass. Zener Diodes 250mW 2W Mixed Vts Coded	£1.00
VP30	10	Ass. 10W Zener Diodes Mixed Vts Coded	£1.00
VP31	10	5 Amp SCR'S TO-66 50-400v Coded	£1.00
VP32	20	3 Amp SCR'S TO-66 Up To 400v Uncoded	£1.00
VP33	200	Sil Diodes Switching Like IN4148 OD 35	£1.00
VP34	200	Sil Diodes Gen Purpose Like OA200V SAK1316	£1.00
VP35	50	1 Amp IN4000 Series Sil Diodes Uncoded All Good	£1.00
VP36	8	Bridge Rects 4 x 1 Amp 4 x 2 Amp Mixed Vts Coded	£1.00
VP37	8	Black Instrument Type Knobs With Pointer 1" Std	£1.00
VP42	10	Black Heatsinks To Fit TO-3 TO-220 Ready Orled	£1.00
VP43	4	Power-Fin Heatsinks 2 x TO-3 2 x TO-66 Size	£1.00

TRANSISTOR CLEARANCE
All Sorts Transistors. A mixed bag NPN-PNP Silicon & Germ. Mainly Uncoded You To Sort Pack includes Instructions For making Simple Transistor Tester. Super Value.
Order No. VP60 **£1.00**

BI-PAK SOLDER — DESOLDER KIT

Kit comprises: O/No. VP 80
1 High Quality 25 Watt General Purpose Lightweight Soldering Iron 240v mains incl. 3/16" (4.7mm) bit.
1 Quality Desoldering Pump High Suction with automatic ejection. Knurled anti-corrosive casing and Teflon nozzle. 1.5 metres of De-Soldering braid on plastic dispenser.
2 yds (1.83m) Resin Cored Solder on Card
1 Heat Shunt too tweezer Type
Total Retail Value over £12.00
OUR SPECIAL KIT PRICE £9.95

BI-PAK PCB ETCHANT AND DRILL KIT

Complete PCB Kit comprises
1 Expo Mini Drill 10,000RPM 12Vdc. incl. 3 collets & 3 x Twist Bits
1 Sheet PCB Transfers 210mm x 150mm
1 Etch Resist Pen
1 1/2 pack FERRIC CHLORIDE crystals
3 sheets copper clad board
2 sheets Fibreglass copper clad board
Full instructions for making your own PCB boards
Retail Value over £15.00
OUR BI-PAK SPECIAL KIT PRICE £9.95
ORDER NO. VP 81

TECASBOTY THE ELECTRONIC COMPONENTS AND SEMICONDUCTOR BARGAIN OF THE YEAR!

This collection of Components and Semiconductors for the hobbyist is probably the most value-packed selection ever offered, it consists of Resistors, carbon and wirewound of various values. Capacitors: All types, sorts and sizes including electrolytics. Potentiometers — single, dual, slider and preset. Switches, Fuses, Heatsinks, Wire, P.C.B. Board, Plugs, Sockets etc., PLUS a selection of Semiconductors for everyday use in popular Hobby Projects. These include: SCR's, Diodes, Rectifiers, Triacs & Bridges as well as a first class mix of Transistors and I.C.'s. In all, we estimate the value of this in current retail catalogues to be over £25! So, help yourself to a great surprise and order a Box TODAY for ONLY at BI-PAK. Remember, stocks are limited so hurry! You can call us on 0920-3182/3442 and order just **£6.50** with your Barclaycard or Access Card — 24hr Answerphone Service NOW. Order No. VP 85.

OUR GREAT NEW 1984 CATALOGUE

Presented with a Professional Approach and Appeal to ALL who require Quality Electronic Components, Semiconductors and other Accessories ALL at realistic prices. There are no wasted pages of useless information so often included in Catalogues published nowadays. Just solid facts i.e. price, description and individual features of what we have available. But remember, BI-PAK's policy has always been to sell quality components at competitive prices and THAT WE STILL DO. We hold vast stocks "in stock" for fast immediate delivery, all items in our Catalogue are available ex stock. The Catalogue is designed for use with our 24 hours "ansaphone" service and the Visa/Access credit cards, which we accept over the telephone. To receive your NEW 1984 BI-PAK Catalogue, send 75p PLUS 25p p&p to:-

BI-PAK Send your orders to Dept REB BI-PAK PO BOX 6, WARE, HERTS. SHOP AT 3 BALDOCK ST. WARE, HERTS. TERMS CASH WITH ORDER. SAME DAY DESPATCH ACCESS BARCLAYCARD ALSO ACCEPTED TEL (0920) 3182. CIRD 388 7006 ADD 15% VAT AND 75p PER ORDER POSTAGE AND PACKING

BBC MICRO VOLUME CONTROL

by Alan Pickard

The BBC Microcomputer has a small internal loudspeaker which produces an audio output at a reasonable volume, under software control. A pre-set situated on the main PCB underneath the keyboard PCB enables the volume to be adjusted. This control could be 'brought out' to the rear of the case for more accessible adjustment, although this is probably not worth the effort as the level would not need to be changed significantly in normal use. Volume adjustment with reference to the pre-set level can also be achieved via the appropriate SOUND command parameter. If desired, the existing speaker could be connected to a changeover switch (or jack socket) and a better quality speaker of the same impedance utilised. This however would be limited by the low power capability of the internal amplifier.

Direct or decoupled connection to the audio amplifier of a television is not recommended, unless the mains input to the set is via an adequate isolation transformer, and the modifier has sufficient knowledge of the equipment and is experienced in working with TV chassis. Also remember that the manufacturer's guarantee may be invalidated by modifications to the equipment.

The most useful enhancement of the audio facility would be to connect the output directly into an external amplifier, eg domestic audio system. This is fairly simple to carry out and is described as follows.

Connections to the computer

The audio section of the computer is made up of a number of op amps, the final stage having the internal speaker connected. An output suitable for connection to an external amplifier is already provided at the output of the 'pre-amplifier' stage as shown in *Figure 1a*. This is brought out to the edge of the main PCB situated underneath the keyboard and

Figure 1a


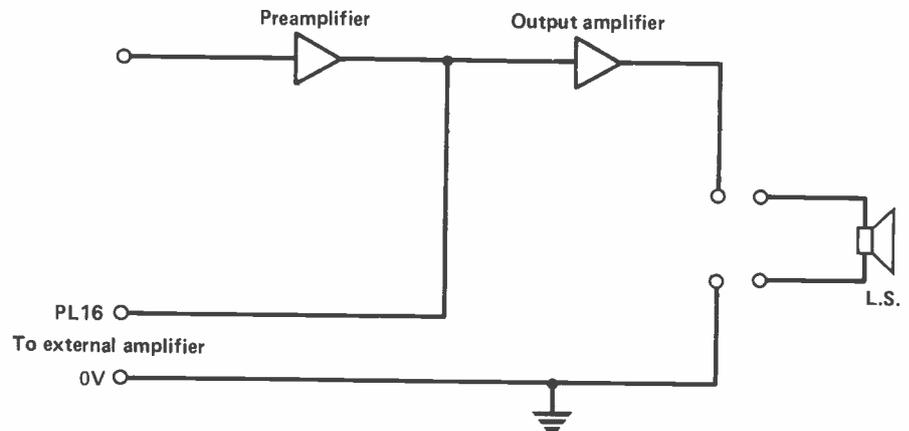


Figure 1b

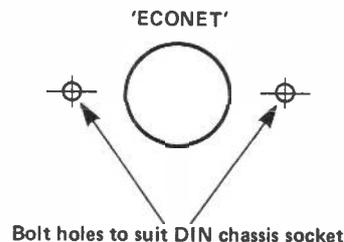

adjacent to the power supply unit. Unfortunately PL16 and the associated 0V point are merely solder filled, through-plated holes (no solder pins), and it is rather awkward soldering on to these almost inaccessible points. However, it can be done providing care is taken to ensure that the plastic case, power supply cables and insulation and motherboard are not damaged, and this is easier than removing the motherboard! Small screened cable is recommended, which may then be run along the edge of the motherboard from PL16/0V to the rear of the machine. A3 (or 5) pin DIN chassis socket can then be

fitted to the 'Econet' aperture, which will necessitate the drilling of two holes in the plastic case as shown in *Figure 1b*. If twin (screened) cable is used, this enables instant connection to both channels of a stereo amplifier, but an appropriate link would suffice.

All that is now required is a suitable cable, eg 3 (or 5) pin DIN plug which will enable connection to the input of a stereo amplifier.

This facility will considerably enhance such sound effects as those found in Starfire, Space Invader, Envelbeeb programs, etc, but should not be used to annoy (or frighten) the neighbours!

ANSWERS TO TWENTY QUESTIONS

- All except (c)
- False. The frequency bands, power limitations and related classes of emission are specified.
- The missing number and errors in the statement are in italics 'The Morse Test includes sending 36 words averaging 5 letters per word in 3 minutes'.
- (c)
- The missing numbers in the statement are in italics 'The Morse Test involves receiving 36 words averaging 5 letters per word and 10 five-figure groups in 1½ minutes'.
- 2 errors.
- 4 errors in plain language, 2 errors in figures, ie (d)
- (b)
- Key clicks.
- False. Details of these tests must be recorded in the Station Log.
- True. The prefix letters of the callsign are varied according to UK country of location, eg G for England, GD for Isle of Man, etc.
- The suffix 'A' is also added for location or 'P' for pedestrian or 'M' for vehicle/vessel.
- (b)
- (b)
- (a)
- (d)
- (c)
- False. Pre-emphasis attenuates the lower audio frequencies and, in relation to the noise distribution across the frequency band, creates a better energy distribution and S/N ratio. The clipper limits the peak amplitudes of the audio and prevents over-deviation.
- (d)
- (b)
- (b). If the 435MHz antenna is one third of the size of the other it will receive one third of the energy and if the gains are equal the performance is not. If it has three times as many elements, the performance will be similar.

POINT OF CONTACT

The general interests of some of our readers and of club networks are shown below. If you have similar interests why not establish a contact at the time and on the band indicated.

If you or your club wish to be included in this scheme, would you please complete and return the form below and send to: **Radio & Electronics World**, Sovereign House, Brentwood, Essex CM14 4SE.

MOST IMPORTANT — include a **telephone number** — if you have a particularly interesting contact so that we can contact you for details for publication.

VK5QV ex G3KGH

Usually available Mondays, Wednesdays and Fridays from: 0800 GMT on 14MHz. Uses phone. Equipment FT101Z, FL2100Z, Theta 7000, TH6, Oric 1. Special interests: working 'G' stations. Would like to contact someone from Gravesend.

GU4XGU ex GU6NAE

Usually available daily from 0800 to 0855; 1250 to 1325; and 1925 to 2200. Uses phone, CW, and RTTY. Equipment Icom IC 290H, KW 2000A, IC2E, LCL 2740 converted to 10m FM, Vic 20 with an MPTU-1 terminal unit. Special interests: operation on VHF, RTTY, and reception of amateur satellites.

G4JHI

Usually available Monday to Friday from 1730, Saturday anytime and Sunday morning on 2, 15, 20, 80 and 160 metres and occasionally on 10, 30, and 40 metres. Uses J3E/A1A on HF, and F3E on VHF.

Equipment Trio TS530, FT480R plus MM 100W linear. Special interests: RS satellites, DX, WAB, local net working.

CLUB NETS

Escape

Ex-Service Communications Association. Usually available Monday, Wednesday and Sunday mornings at 0700 GMT and Monday, Wednesday and Sunday evenings at 1900 GMT. Modes used are CW and SSB on frequencies of 14020/14185/14255; 21020/21185/21255; 7005/7085; 3730/3790/3570. RTTY contact from the early Autumn. National CB channel is 34.

The following list of nets has been supplied by South Essex Amateur Radio Society.

Sunday

G5SN net starting at 0930 on 3.7MHz SSB.

The Royal Naval Amateur Radio Society net starting at 0930 on 3.660MHz SSB.

The Northern net starting at 1030 on 7.85MHz.

The Amplitude Modulation Preservation Society net starting at 1430 on 1980KHz on AM and SSB, with G4GVO in the chair.

Kent and Essex Round Robin on the first Sunday of each month starting at 1830 on 1950KHz with Basil G3LID or George G4INO in the chair.

Monday

CW net on 1950KHz starting at 2000, all are welcome.

Thursday

RAYNET Call out on 144.875 FM at 2030 GMT with Joe G3AJS as controller.

Friday

SEARS 2 metre CW net starting at 2030 on 144.410.

10 metre FM net on 29.600MHz (calling frequency) at 2130.

Weekdays

The Shaving Club starting at 0715 on 1927KHz with Arthur G3KPT in the chair.

Daily

On 1978KHz at 0930, Frank G5WL and Frank G3BLI wel-

come a call from anyone for a chat.

We apologise for any errors, but the information above is correct as far as we know. Please send any corrections to the Editor.

SPECIAL EVENT STATIONS

GB2ABC

The Abergavenny and Nevill Hall Amateur Radio Club will be running a special event station at the Abergavenny and Border Counties Show on 28th July. The station will be operating on SSB on all bands to 146MHz and FM on 2 metres. Further details from GW3SSY on 0873 78674.

GB2PYF

The Abergavenny and Nevill Hall Amateur Radio Club will be operating a special event station at the Pen-y-Faal Hospital Fete. The station will be using SSB on all bands upto 146MHz and FM on 2 metres. Further details from GW3SSY.

POINT OF CONTACT

Name/Club..... Address
 Postcode
 Telephone No Call Sign Date licensed
 Type of Licence A..... B.....
 Bands usually preferred.....
 Operating days M T W T F S S Times.....
 Equipment.....
 Phone/CW.....
 Special interests eg DX,AMSAT etc.....

 Most interesting contact made to date.....

RE0884

We are pleased to accept Points of Contact not on our form

— DATES FOR — — YOUR DIARY —

Dates for your diary is updated every month.

Club secretaries and organisers are requested to send information of forthcoming events as early as possible

to **Radio & Electronics World**, Dates for your diary, Sovereign House, Brentwood, Essex CM14 4SE

Date	Function	Location	Contact
15 July	DF Hunt	Wirral and District AR Club	G Scott G8TRY
	DF Hunt on 160 & 2m	Dunstable Downs AR Club	Phill Morris Dunstable 607623 I Mitchell G4NSD
17 July	QRP Operating by C Page	Biggin Hill AR Club	
18 July	Computer Night	S Bristol AR Club	Brian GIDBH
21 July	Radio & Electronics Fair	Royal Victoria Hall, S Borough	W Kent AR Society
22 July	Anglian Mobile Rally	Stanway School	Colchester Radio Amateurs
22 July	Home Counties Mobile Rally	McMichael Sports and Social Club, Belles Hill, Stoke Poges	
29 July	Scarborough AR Rally	The Spa, Scarborough	
5 August	Woburn Rally		
7 August	High Power Transmitters	Chelmsford AR Society	
17 August	DF Hunt on 2 & 10m	Dunstable Downs AR Club	Phill Morris Dunstable 607623
19 August	HAMFEST 84	Flight Refuelling Social Club, Merley Park Road	RAIBC & Flight Refuelling AR Society
27 August	DF Hunt	Southgate AR Club	G40BE (QThr with SAE)
5 Sept	Sattelite Communication	Fareham & District AR Club	Brian Davey G4ITG
8-9 Sept	International Amateur TV Contest	British Amateur TV Club	G Shirville G3VZV
9 Sept	Telford Mobile Rally	Telford Shopping Centre	G8DIR/G8 UGL G3 UKV
16 Sept	Vange AR Society Mobile Rally	Nicholas School, Basildon	Mrs D Thompson
19-23 Sept	The Personal Computer World Show	Olympia 2	
23 Sept	Lincoln HAMFEST	Lincolnshire Show-Ground	Lincoln SW Club G5FZ/G6COL
23 Sept	National Car Boot Sale	Shuttleworth Collection, Old Warden, Beds	Dunstable Downs Radio Club
7 Oct	Gt Lumley Annual Rally	Gt Lumley Community Centre	Gt Lumley AR Society G40CQ
13 Oct	Midlands VHF Convention	BT Training College, Stow, Staffs	Peter Burdem G3UBX
17-25 Jan 85	Amateur TV Winter Cumulative Contest	British Amateur TV Club	G Shirville G3VZV
	CHANGE OF VENUE		
	Worthing & District AR Club	Lancing Parish Hall, South St, Lancing	

Computer & TV Video INTERFACE

by Alan Pickard

The BBC Micro has the ability to provide a video output via socket SK2. This is standard on the Model B, but can easily be provided on the Model A by fitting the appropriate BNC socket.

This video output provides a more direct connection of the output from the video processor after amplification and dispenses with the necessity of passing through a UHF modulation stage and subsequently a demodulation stage. This signal can then be fed in to a monitor or after the vision detector stage in a television, resulting in a better quality, higher resolution display (having avoided any slight degradation of the signal by a stage of modulation and then demodulation).

What is involved

The universally adopted standard for 'line level' video is 1V peak-to-peak into 75ohm impedance.

Modifying a television circuit involves feeding in the video output from the computer to the point where the vision detector stage output is normally fed. This input should be via a 75ohm coaxial cable and must present a 75ohm terminating impedance to the input circuit.

In most cases a certain amount of additional circuitry will be required to match the 75ohm, 1V positive input signal such that the impedance, amplitude and polarity required by the video stages of the receiver are correct.

Points to check

Before deciding to attempt a 'video in' modification to a black and white television, the following points should be observed.

This modification should only be attempted if you have sufficient knowledge to understand the manufacturer's circuit diagram and have previous experience of working on TV chassis. If the set is within its guarantee period, the guarantee may be invalidated by the modification.

Ensure that the chassis of the set is not connected to either the mains live or the mains neutral lines. To be compatible with connection to a micro (ie safe) the mains input to the set should be via a step down isolating transformer such that the video stages are supplied with low supply voltages of the order 12-24V dc.

In the case of a 'hot chassis' set (live or neutral connected to chassis), or low voltage supplies derived from mains

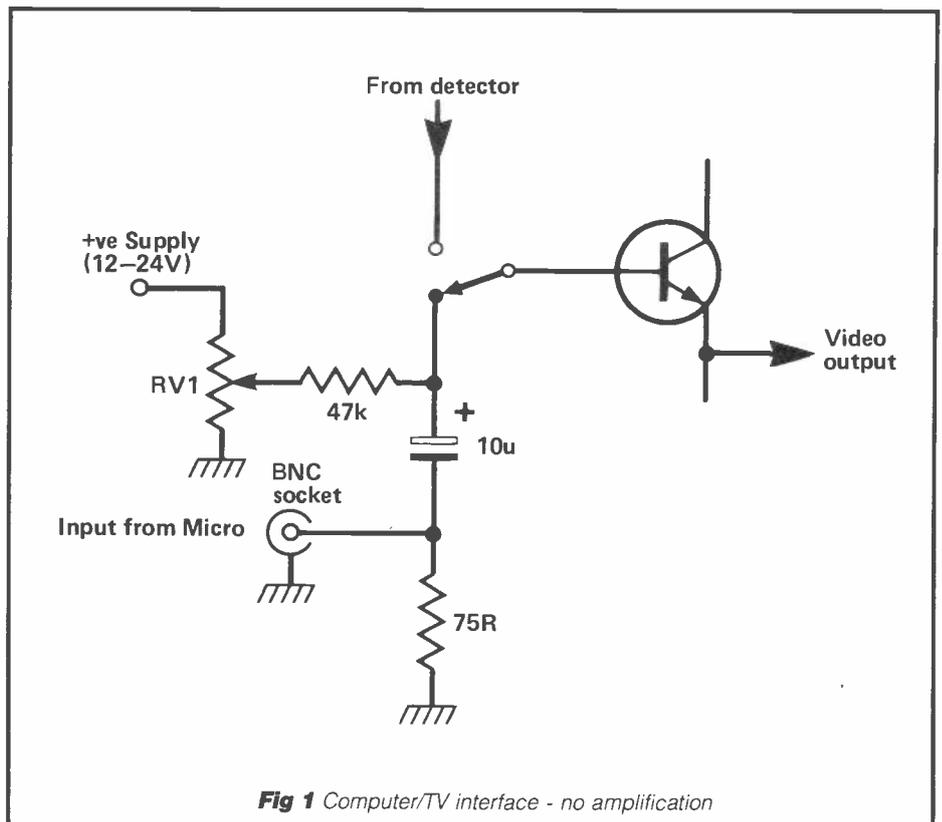


Fig 1 Computer/TV interface - no amplification

dropper resistors, do not attempt modification. The best way of establishing whether or not the set is safe to modify is by consulting the manufacturer's circuit diagram.

In all cases check that the mains fuse to the TV set is correctly rated.

Computer/TV interface

Figure 1 illustrates how to connect a video input (output from micro) to the first video amplifier stage (after the detector stage). These few components would be all that were required for input matching, if the first video amplifier stage in the television stage was designed for 1V positive input (75ohm): in other words, if it is not required to change amplitude or polarity of the incoming video signal.


In some cases however, the 1V video input will not be of sufficient amplitude to drive the video stages fully (resulting in the display not 'locking'). In this case an amplification stage will be required as shown in Figure 2. This consists of a

common base amplifier which provides a low impedance input to the first video amplifier and does not invert the signal. Amplitude is adjusted from 1-3V via RV1, and RV2 sets the bias voltage. The polarity of C2 depends on RV1 and RV2 settings.

If the television set requires a positive-going video input (see waveform), then the circuit in Figure 3 will provide the required amplification and inversion of the signal. RV1 adjusts the bias on the following video amplifier stage and RV2 sets and gain.

The above notes are intended to be a guide only to conversion, but it should enable the successful connection of a video signal. For stable operation, the wiring to the switch should be kept as short as possible. In order to be able to switch easily from 'video in' mode to 'UHF TV' mode, the fitting of the changeover switch as indicated on the diagrams is recommended. Also, connection to the television set should be via a BNC socket.

COMPUTER & TV VIDEO INTERFACE

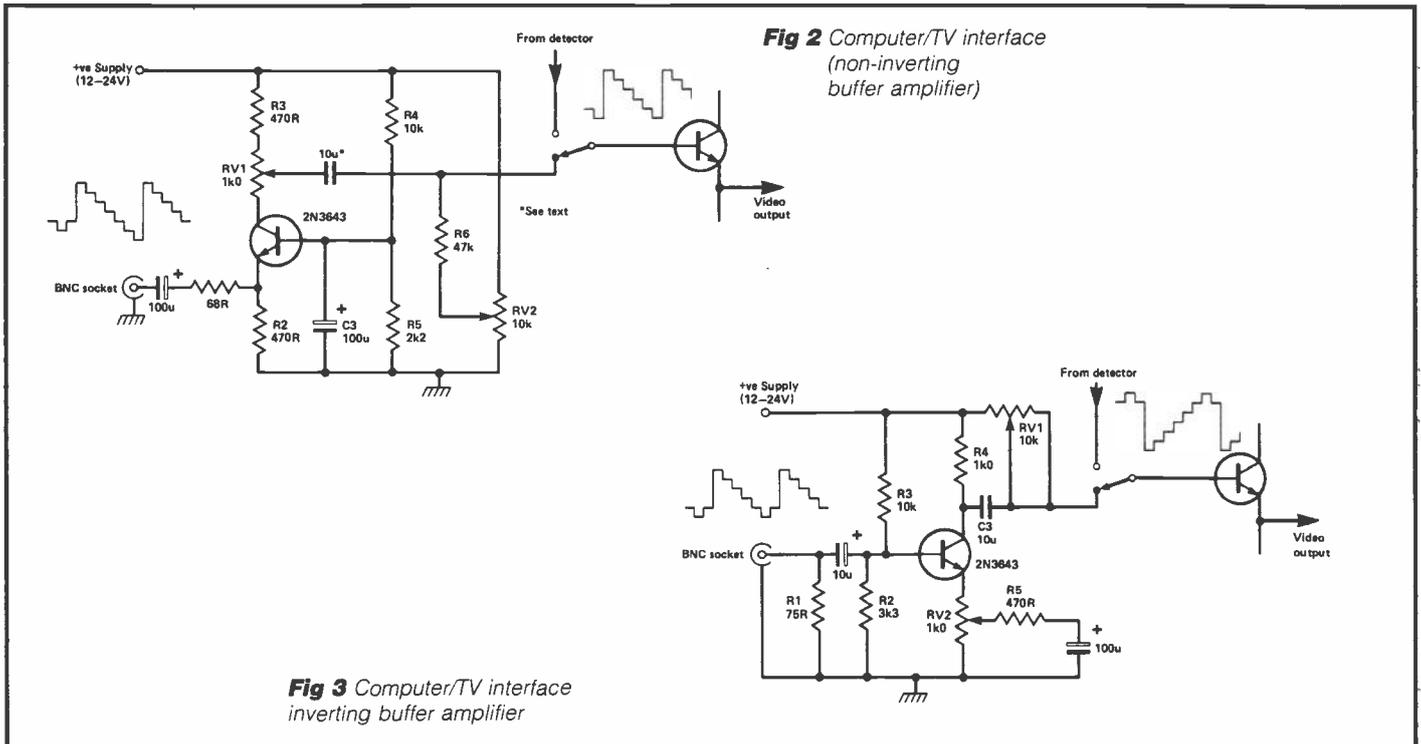

The 2N3643 transistor may be difficult to obtain, but I have used a BC118 successfully. A 2N3904 is probably also suitable, the requirements being similar operational frequency (around 200MHz)

and a gain of around $100 h_{fe}$. Although the conversion work requires a reasonable amount of time and effort, it is well worth it as the improved quality of the direct video


display will demonstrate. As well as providing a crisper display and therefore reducing eyestrain, the use of Mode 0 for text (word processing, etc) is more realistic.

THE 3-PART RADIO & ELECTRONICS WORLD

AMATEURS HANDBOOK

is now available as a complete set for only £2.50 (including post and packing)

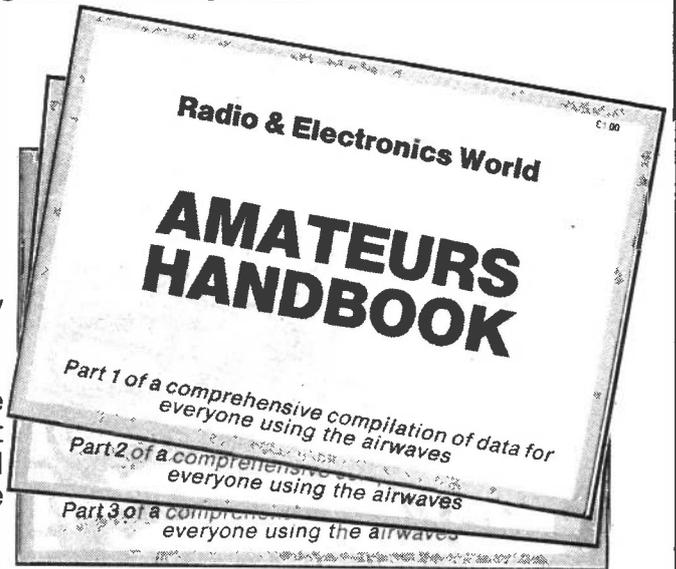The Handbook is an informative guide to the world of the amateur radio enthusiast. It contains a multitude of useful facts and figures designed to benefit both the novice and the licensed amateur.



To: Radio & Electronics World · Sovereign House · Brentwood · Essex · CM14 4SE

NAME.....
 ADDRESS.....

 Postcode.....

PLEASE SUPPLY:
 1 set of R&EW AMATEURS HANDBOOK

PAYMENT ENCLOSED: £2 — 50 Cheques should be made payable to Radio & Electronics World: Overseas payment by International Money Order, or credit card.

CREDIT CARD PAYMENT VISA
 Signature.....



South Midlands

* FREE FINANCE • 2 YEAR GUARANTEE

BRANCHES AT: SOUTHAMPTON, LEEDS, CHESTERFIELD

'YAESU' FOR H.F. EQUIPMENT – 'SMC' AT YOUR SERVICE

FT-ONE 'THE ULTIMATE' TRANSCEIVER



FT ONE	Transceiver HF All Mode.....	£1569.00
KEYT901	Curtis Keyer.....	£28.50
DCT1	DC Power Cable.....	£10.85
RAMT1	Non volatile memory.....	£14.49
FMU1	FM unit.....	£44.99
XF8.9K★	Filter 300Hz or 600Hz or 6KHz each.....	£19.35



FT707 THE BUY OF THE YEAR

**100W PEP
8 BAND HF
SSB/CW/AM
£425!‡**



T707‡	Transceiver 100W 10-80M (8 bands)	£425.00
707	Mains ext. power supply/speaker	£125.00
707DM	Digital VFO	£130.00
V707R	Transvertor (NB main frame only).....	£29.35
1B707	Relay switching box.....	£16.25
1B2	Mobile mounting bracket.....	£18.25
1T707	Workshop Manual FT707.....	£13.00

S
M
U
C
P
E
S
R
P
E
S
C
A
I
V
E
L
R



FT102 THE "WORKHORSE" BASE



FT102#	Transceiver 9 band.....	£719.00#
SP102	External speaker.....	£55.00
FC102	Antenna coupler.....	£185.00
AMFMUT102	AM/FM unit option.....	£49.00

SUPER VALUE – VALVE FINALS



FT77 THE IDEAL MOBILE

Employing all the latest engineering and manufacturing techniques the FT77 is intended to offer the essential modern operating features in the most economical, reliable and compact HF transceiver available.




FT77	8 Band Rx/Tx 100W output	£479.00
FT77S	8 Band Rx/Tx 10W output	£449.00
FP700	Matching AC PSU.....	£145.00
FC700	Matching antenna tuner	£103.85
FV700DM	Digital VFO unit.....	£209.00
MKT77	Marker unit.....	£10.85
FMUT77	FM unit.....	£28.55
AMUT77	AM unit.....	£24.00

S
T
I
U
M
P
P
E
L
N
I
D
S
O
I
U
T
S
Y



FT980 "COMPUTER COMPATABLE"

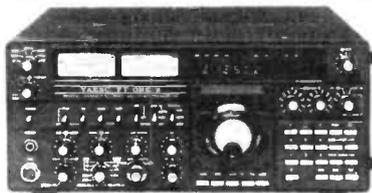

FT980	Transceiver General Coverage Rx.....	£1329.00
SP980	Ext. speaker with audio filter.....	£61.55
XF455.8MCN	300Hz CW filter (455KHz 8 pole).....	£49.00
XF8.9HC	600Hz CW filter.....	£29.50
XF8.9GA	6KHz AM filter.....	£29.50
FIF★★	Computer interface (see FT757GX units)	
D410004	Interconnect lead FT980-FC757AT.....	£26.99
TST980	Technical Supplement FT980.....	£8.50



FT757GX THE BIGGEST SELLER

Every item normally sold as an extra is provided as standard, including AM and FM modes, a 600Hz narrow CW filter, iambic keyer with dot-dash memory, 25KHz marker generator, IF shift and width filters, effective noise blanker and AF speech processor..... all at no extra charge.



FT757GX	transceiver General Coverage Rx.....	£719.00
FC757AT	Automatic antenna tuner.....	£245.00
FP757GX	Switch mode PSU (50pc duty).....	£145.00
FP757HD	Heavy duty PSU (100pc duty).....	£179.00
FIF80	Computer interface for PC8001 NEC..	£105.00
FIF65	Computer interface for Apple II.....	£54.00
FIF232C	Computer interface RS232C.....	£59.00

S
U
P
E
R
S
E
R
V
I
C
E

SMC SERVICE

Free Securicor delivery on major equipment. Access and Barclaycard over the phone. Biggest Branch agent and dealer network Securicor B' Service contract at £5.00. Biggest stockist of amateur equipment. Same day despatch wherever possible.

FREE FINANCE

On many regular price items SMC offers Free Finance (on invoice balance over £120). 20% down and the balance over 6 months or 50% down and the balance over a year. You pay no more than the cash price!! details of eligible items available on request.

GUARANTEE

Importer warranty on Yaesu Musen products. Ably staffed and equipped Service Department. Daily contact with the Yaesu Musen factory. Tens of thousands of spares and test equipment. Twenty-five years of professional experience. ● 2 Year warranty on regular price Yaesu products.

SMC STOCK CARRYING AGENTS WITH DEMONSTRATION FACILITIES

Neath John GW4FO1 (0639) 52374 Day (0639) 2942 Eve Bangor John G13KDR (0247) 55162 Stourbridge Andrew G4BJY (0384) 390916

Communications Ltd

MAIN DISTRIBUTOR: FACTORY BACKED

BUCKLEY, STOKE, GRIMSBY, JERSEY, EDINBURGH.



YAESU FOR VHF EQUIPMENT – 'SMC' YOUR SUPPLIER

FT290R & FT790R MULTIMODE



★432MHz
PORTABLE
SSB/CW/FM
£259!★

S U P P L I E R S	FT690R	Multimode Transceiver 6m	£259.00
	FT290R	Multimode Transceiver	£279.00
	FT790R★	Multimode Transceiver 70cm	£259.00★
	SMC2.2C	2.2Ah Nicads 'C' size	per set £21.60
	SMC8C	220mA Charger (13A Style).....	£9.20
	MMB11	Mobile Mount.....	£28.19
	CSC1A	Carrying case	£4.45
	FL6010	6m 10W Amplifier	£49.00
FL2010	2m 10W Amplifier	£66.55	

FT 726R MULTIMODE UHF, VHF, HF



FT726R	TRANSCIVER MAIN FRAME ONLY	£619.00
FT726R(2)	Transceiver c/w 2m	£775.00
21/24/28	HF module	£209.00
50/726	6m module	£195.00
430/726	70cms module	£259.00
SAT726	Full duplex module	£99.95
XF455MC	600Hz CW filter	£41.85

FT208R & FT708R HANDHELDS

KEYBOARD ENTRY SCANNING – L.C.D.

4 bit CPU provides:- ten memories, up-down manual tuning. Scanning of; memory, band or between limits (busy and clear), autoscan restart, programmable repeater splits, and European standard synthesiser steps. The keyboard also offers 16 tone D.T.M.F. tones and the unit is supplied with NiCad pack, helical and soft case.

**S
U
P
P
L
I
E
R
S**



FT208R	2M Handheld 2.5W	£209.00
FT708R★	70cm Handheld 1W	£189.00★
SMC.89AA	Charger (slow) 13A style	£8.05
NC7	Charger (base)	£34.65
NC8	Charger (quick) and Power Unit	£56.75
PA3	DC adaptor and charger	£16.00
FNB2	NiCad Battery Pack	£23.00
FBA2	Battery pack sleeve	£3.65
SMC.FLC5	Heavy duty case	£25.30
MMB10	Mobile bracket	£8.45

FT230R & FT730R FM MOBILES



FT230R	2m Transceiver 25w	£269.00
FT730R★	70cm Transceiver 10w	£239.00★
MMB15	Mobile mounting bracket	£14.65

★SEVENTY CMS. SUPER SAVER

FT203R & FT703R HANDHELDS

"THUMBWHEEL" TINY HANDHELD

Ultra compact 65W x 34D x 153H mm, synthesised handheld. Computer aided design and component insertion with chip capacitors and resistors has produced this modern marvel: 2.5W RF (10 Bv) (3.5W RF) (12V). It has VOX (for use with YH-2 lightweight headset, and built in 'S'/PO meter. Supplied with tone burst, helical and appropriate case.

**S
U
P
P
L
I
E
R
S**



FT203R	c/wFBA5, CSC6 etc.	£155.00
FT203R	c/w FNB3, CSC6 etc	£175.00
FT203R	c/w FNB4, CSC7 etc	£185.00
FBA5	7.2/9V Cell case only (6 x 'AA')	£6.85
FNB3	10.8V NiCad Pack (425mAH)	£33.50
FNB4	12.0V NiCad Pack (500mAH)	£38.25
CSC6	Soft case (FBA5 or FNB3 fitting)	£6.00
CSC7	Soft case (FNB4 fitting)	£6.85
YH2	Headphone/Microphone option	£14.50
MH-12A 2b	Speaker/Microphone option	£17.69
MMB21	Mobile mounting bracket	£8.00
SMC8.9AA	Charger (slow) 13A style	£8.05
NC15	Charger (quick) and Power Unit	£49.95

FRG7700 COMMUNICATIONS RX



FRG7700	Receiver 0.15-30MHz AM/CW/SSB/FM	£385.00
FRG7700M	Receiver c/w 12 channel memory	£445.00
MEMG7700	Memory option	£75.00
FRT7700	Antenna tuner/switch	£48.25
FRA7700	Active antenna	£43.95
FF5	Low pass filter 500KHz	£11.25
FRV7700	VHF Convertors, 6 models, each 3 bands. From £84.50-£94.25 each	

LEEDS
SMC (Leeds)
257 Otley Road
Leeds 16, Yorkshire
Leeds (0332) 782326
9-5.30 Mon-Sat

CHESTERFIELD
SMC (Jack Tweedy) Ltd
102 High Street
New Whittington, Chesterfield
Chesterfield (0246) 453340
9-5 Tues-Sat

BUCKLEY
SMC (TMP)
Unit 27, Pinfold Lane
Buckley, Clwyd
Buckley. (0244) 549563
9.30-5.30 Tues-Sat

STOKE
SMC (Stoke)
76 High Street
Talke Pits, Stoke
Kidsgrove (07816) 72644
9-5.30 Tues-Sat

GRIMSBY
SMC (Grimsby)
247A Freeman Street
Grimsby, Lincs
Grimsby (0472) 59388
9.30-5.30 Mon-Sat

JERSEY
SMC (jersey)
1 Belmont Gardens
St Helier, Jersey
Jersey (0634) 77067
9-6pm Mon-Sat

EDINBURGH
SMC Scotcomm,
23 Morton Street
Edinburgh EH15 2HN
Tel: 031 657 2430
10-5 Tues-Fri, 9-4 Sat


HEAD OFFICE
&
MAIL ORDER

S.M. HOUSE, RUMBRIDGE STREET, TOTTON, SOUTHAMPTON, SO4 4DP, ENGLAND
Tel: Totton (0703) 867333. telex: 477351 SMCOMM G. Telegram: 'Aerial', Southampton

NEW! Britain's biggest & best monthly magazine for sea fishermen

Containing a wealth of information and advice from which every sea angler will be able to learn.

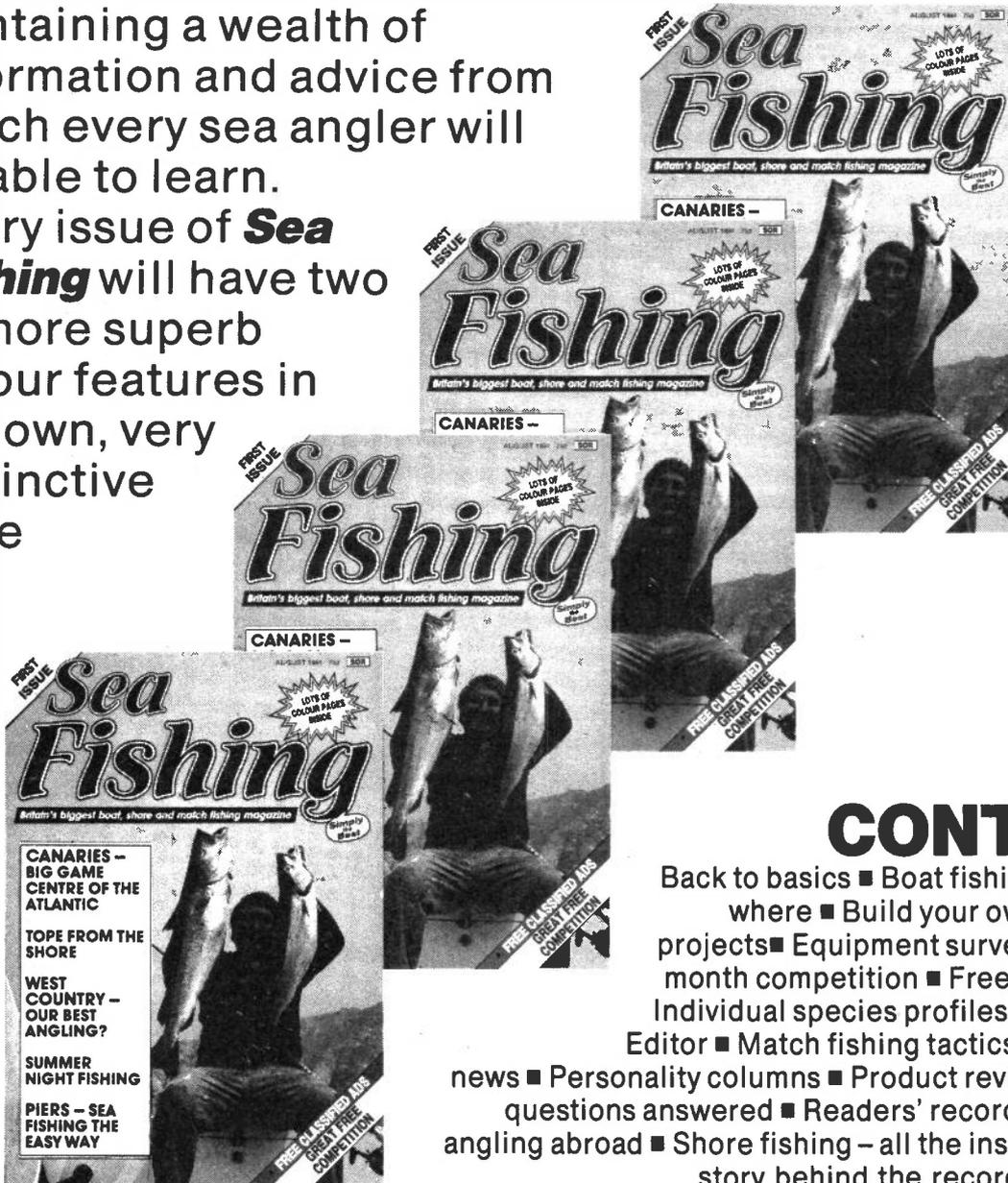Every issue of **Sea Fishing** will have two or more superb colour features in our own, very distinctive style



CONTENTS

Back to basics ■ Boat fishing – how, when, where ■ Build your own dinghy ■ DIY projects ■ Equipment surveys ■ Fish of the month competition ■ Free competitions ■ Individual species profiles ■ Letters to the Editor ■ Match fishing tactics ■ New product news ■ Personality columns ■ Product reviews ■ Readers' questions answered ■ Readers' record fish lists ■ Sea angling abroad ■ Shore fishing – all the ins-and-outs ■ The story behind the record ■ Tide tables

**ON SALE
AT YOUR
NEWSAGENTS
FROM
19th JULY**

SEA FISHING SUBSCRIPTION ORDER FORM

TO: Subscription Department · Sea Fishing · 513 London Road · Thornton Heath · Surrey · CR4 6AR. Tel: 01-684 3157

PLEASE SUPPLY: (tick box) for 12 issues, all rates include P & P

Inland	World-Surface	Europe-Air	World-Air
£12.20 <input type="checkbox"/>	£13.10 <input type="checkbox"/>	£18.95 <input type="checkbox"/>	£26.10 <input type="checkbox"/>

PAYMENT ENCLOSED: £ -

Cheques should be made payable to Sea Fishing. Overseas payment by International Money Order, or credit card.


CREDIT CARD PAYMENT Signature.....

NAME ADDRESS.....

Postcode.....

ATV on the Air

Presented by Andy Emmerson, G8PTH

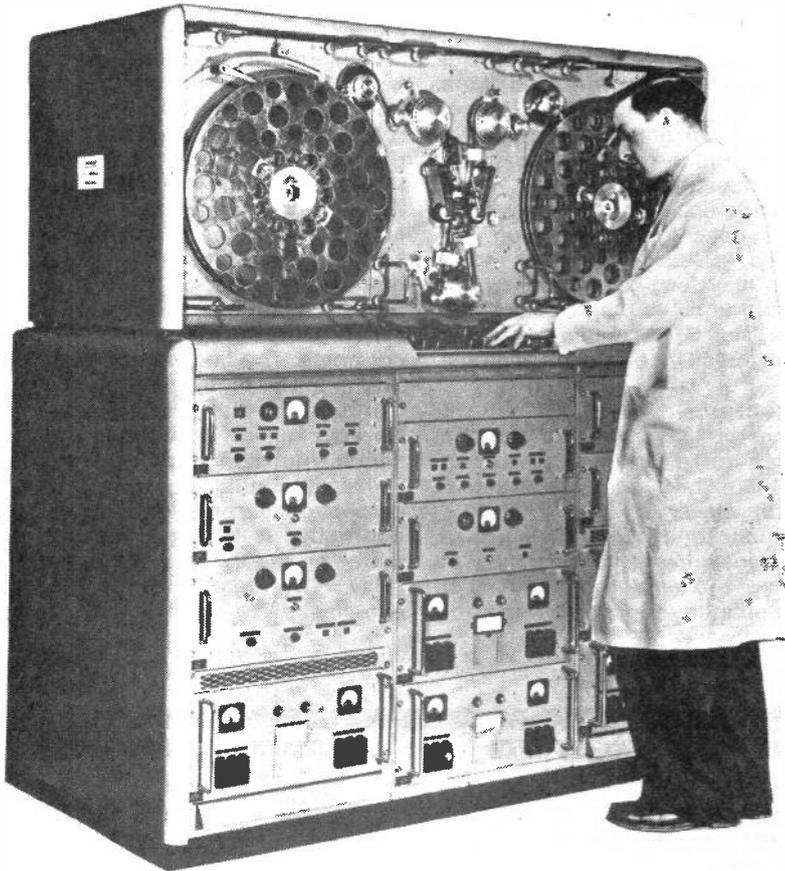

Every shack should have one. This is VERA, the Vision Electronic Recording Apparatus, developed by the BBC in the 1950s. It recorded video and audio on giant reels of tape, and makes a Philips 1500 look really compact. (Picture courtesy 3M)

The topics for this month are connectors and feeders, which means they are applicable to all modes of amateur radio, not just TV, but I hope you will not stop reading just for that. All the information I pass on is based on hard-won experience and is generally the sort of thing you won't find in the handbooks!

BATC convention

The thoughts were inspired by the British Amateur Television Club's annual exhibition and day out. It was a success – it was well attended and there were more trade stalls than before.

Anyone searching for a camera or monitor should have come away satisfied, though the really cheap cameras sold very early (like £5 for a non-working modern Sanyo $\frac{2}{3}$ in model). It was nice to see the odd Pye Lynx or two – these seem to go on for ever – and there were several colour cameras at sub-£200 prices.

Monitors seemed to be over-priced, though, and I did not see many selling. Several of the traders had new products,

such as Fortop and Wood & Douglas. Solent Scientific had a dinky little 10mW test transmitter for 24cm, which was demonstrated by its deviser G8CMQ as a creepy-peepy (the video equivalent of a handy-talky). It would also be useful for checking out your receiver after a period of inactivity.

The Worthing Repeater Group had a superb display of 'how they built their repeater' from a junked cash register (well, the logic at least)! L-Wave and LMW Electronics had some nice microwave bits and pieces and added a high-tech note to the proceedings.

To the point...

Grant Dixon, in presenting this year's Grant Dixon award, pointed out that we had a duty to pass on the knowledge we gained for the benefit of others. Mike Walters, G3JVL, did just that in a packed lecture on 23cm techniques. I certainly learned something new and was reminded of other points I had myself learned from bitter experience, so it

might be worth repeating them here.

It is of course true that antennas, connectors and feeders do as much work in your system as the actual transmitter and receiver themselves. At 70cm, and even more so at 23 and 24, signals are too precious to lose in sub-standard feeders and connectors.

The choice of the right antenna is important and it is worthwhile sorting out if you want high gain whether you can live with the narrower beamwidth you will end up with. Multiple antenna systems may mean that they are not all beamed exactly on the same point on the horizon, and long aerials must be kept accurately horizontal to avoid firing above (or below) the horizon.

Cabler's choice

Just as important is the feeder. Heliax type cables obviously offer the lowest loss but they are expensive to buy and so are the special connectors! Add to this their inflexibility and size and I think you are better off with more 'normal' types of coax. G3JVL made the important point that semi air-spaced cables could act as water pipes if not properly sealed and the braiding can also act as a capillary wick for moisture. So do tape up the ends of cables with self-amalgamating tape and try to avoid installing cables on humid days – the moisture can later condense out inside the cable. Remember that BNC connectors are *not* waterproof, so use N-type exclusively outdoors.

When it comes down to a choice of coax, there isn't really a choice now. Half-inch cables are reasonable but avoid RG-8, especially the sort sold to CBers. It has a low braid density, which allows half the RF to escape before it reaches the other end of the feeder. UR-67 is adequate but H-100 is lighter in weight and has much improved low-loss characteristics. It is sold at all rallies nowadays and costs little more than new UR-67.

Contaminated cables

Avoid buying second-hand cable like the plague. It looks such a bargain but it is positively evil how coaxial cables age invisibly. I say invisibly, though a trained eye can tell old cable. The outer sheath tends to get harder and more brittle and the inner dielectric goes yellow. The braiding tarnishes to a black colour and is almost impossible to clean or solder. What has happened is that vinyl (from which they make the sheathing) is not naturally a very flexible material and so plasticisers are added to make it more workable.

Over time, however, these additives may leach out and start to contaminate the braiding and dielectric. Exposure to the elements and sunlight hastens this effect and gradually the plasticisers migrate to the central polythene, raising its dielectric constant and power factor and hence VSWR and attenuation.

Having lost its plasticiser the outer vinyl starts to go brittle and cracks, allowing in moisture which corrodes the braid. RF is inhibited from flowing through the braid, attenuating the return

ATV ON THE AIR

current path and allowing the forward signal to radiate from the centre conductor. Less signal reaches the aerial from the transmitter and as less signal can be reflected, the 'match' as read on a VSWR meter looks better as the cable ages. But clever lads like you and me are not so easily fooled now.

Of course, cable like this is useless, even if it has been stored unused, and it often appears at rallies at bargain prices. But don't be caught.

People who have looked at H-100 cable may feel it is difficult to work with, and at first sight this is true. It is not as flexible as 'normal' coaxes, and the sheath needs a good knife to cut it. On the other hand its toughness means it resists scratching and splitting. The braiding and copper foil are fiddly to dress and the copper centre conductor is quite thick, and all these factors add up to make it awkward to prepare the cable for fitting a plug.

Connecting you now

First of all, you must use the right connectors and the Greenpar are the type to use, for two reasons. Firstly, the centre conductor will fit the centre pin without filing down (which is taboo) and secondly because the Greenpar design has a ferrule for contacting the braid, rather than relying on fanning out strands of the braiding.

Do not slit the plastic sheath

lengthwise; just cut around the cable and remove a length of sheath. Remove the braid and foil as well, and after sliding the shell of the connector down the cable (I know, I forget this too sometimes!), force the ferrule between the foil and braiding. If it refuses to go use a hairdrier to warm up the sheath and make it more supple; the ferrule will slide down now and after things cool down they will grip the ferrule even better.

Turning to connectors (both BNC and N type) I must admit I am very fond of the type made by Greenpar and Coline. These use a ferrule to contact the braiding and hold the centre pin captive. The older designs (Mil Spec), if not properly made up, can allow the centre pin to slip back inside the plug (on BNCs). This at least causes an open circuit and may lead to a short circuit when the pin touches the braid. Having blown up a 'Blue Brick' in this way I have now thrown out all my non-captive plugs!

More expense!

Reverting to G3JVL wisdom and the way we risk our equipment by cutting corners, Mike had some instructive thoughts on relays.

Most stations tend to use some form of relay for transmit/receive switching at the bottom of the aerial feeder. Many of these use plated phosphor-bronze for

contacts which eventually gets pitted and oxidised. If operated by miniature push-rods these must be capable of conducting heat out of the relay contact chamber (if the relay feels warm when passing power this is a good sign)! The ideal relay also has auxiliary detector contacts, and a well designed system uses these to detect that the relay has thrown before passing RF through the relay. Switching 'live' RF is a recipe for an early death of the relay – and transmitter.

Even more worrying is the poor isolation performance of some relays. Mike said that he would like a preamp or receiver to see no more than 1mW of RF, though 10mW might not be lethal. Most relays are fine at two metres and even 70cm, but give perhaps only 22dB isolation at 24cm. If you intend to run 100W on transmit, such a relay is clearly quite inadequate.

I must admit this quite shocked me and sent me rushing for my calculator when I got home. The bottom line is that if you intend to run high power on 24 you must use one of the better Japanese or German relays. These also ground the contact not connected. Otherwise you will have to build your own, or find some aerospace surplus goodies. The only alternative is to put a second relay in series on the Rx side of the main Tx/Rx relay. Oh dear, sounds like more expense!

HART

LINSLEY HOOD 300 SERIES AMPLIFIER KITS.

Ultra high quality, Mosfet output, Hi-Fi amplifier kits by this famous designer. Two models of identical appearance are available, one giving 35 watts per channel output, the other 45. Careful design has made these amplifiers capable of superb sound quality. The delicacy and transparency of the tone quality enables them to outperform, on a side by side comparison, the majority of commercial amplifiers. Building is very easy as almost all components are fitted on easily removed printed circuit boards. Subsequent setting up needs only a simple multimeter to obtain the full specified performance. Both kits come with very comprehensive building instructions.

35 Watt Complete Kit - **£79.50** 45 Watt Complete Kit - **£83.50**
Reprints of Original Articles from 'Hi-Fi' News **£1 no Val.**

LINSLEY HOOD CASSETTE RECORDER CIRCUITS

Complete record and replay circuits for very high quality low noise stereo cassette recorder. Circuits are optimised for our HS16 Super Quality Sendust Alloy Head. Switched bias and equalisation to cater for chrome and ferric tapes. Very easy to assemble on plug-in PCBs. Complete with full instructions.

Complete Stereo Record/Play Kit - **£25.20**
VU Meters to suit - **£2.30 each**
Reprints of original Articles **75p no Val.**

HART TRIPLE-PURPOSE TEST CASSETTE TC1

One inexpensive test cassette enables you to set up VU level, head azimuth and tape speed. Invaluable when fitting new heads. Only **£4.66** plus VAT and 50p postage.

Tape Head De-magnetiser. Handy size mains operated unit prevents build up of residual head magnetisation causing noise on playback. **£4.54**

Full details of the entire range of HART products is contained in our illustrated lists. Ask for your FREE copy NOW. Enquiries for lists are also welcome from overseas but please let us have three IRCs to cover the cost of surface post or 5 IRCs for airmail.

In a hurry? A telephone order with credit card number placed before 3pm will be despatched THAT DAY!
Please add part cost of post, packing and insurance as follows

INLAND
Orders up to £10 - 50p
Orders £10 to £49 - £1
Orders over £50 - £1.50

OVERSEAS
Postage at cost plus £2
documentation and handling

LINSLEY HOOD 100 WATT POWER AMPLIFIER

Our complete kit for this brilliant new design is the same size as our Linsley-Hood Cassette Recorded 2 Kit includes all parts for two power amplifiers with large heatsink area, huge power supply and speaker protection circuit. Total cost of all parts is **£114.46** but our special introductory price for all parts bought together is only **£105.50**.

'ALPS FF317U FM FRONT END'

Beautiful, precision made High Quality variable capacitor tuned FM Front End with Dual-gate MosFet, 2-AM Gangs and 3:1 reduction gear.
FM range 87 to 109MHz 12v 30mA Max AGC and AFC. OUR PRICE ONLY **£3.99** INCLUDING VAT AND POSTAGE (Circuit if required 35p).

'MULLARD UHF TV FRONT ENDS'

Compact Varicap tuned modules. U322 is used in 'ELEKTOR' teletext decoder. U321 £9.24 inc vat. U322 £9.76 inc vat.

COMPLETE STEREO TUNER MODULE

Three band LW/MW/FM Stereo Tuner fully assembled on PCB 165 x 85mm. Supplied with Ferrite rod aerial and band switch fully wired. Facility provided to drive tuning meter and stereo LED. Only needs 12v DC supply. FM sensitivity. 2.5uV. Price only **£7.99** inc. VAT and post.

HIGH-SPEED DIGITAL CASSETTE RECORDER

A really super buy for the computer enthusiast. These decks, made by Burroughs, are the real thing using a capstanless cassette mechanism to record and replay data at 10 and 30 inches per second. The read after write head uses an NRZ system with separate tracks for clock and data. Power supplies of 5v, -12v and +12v are required. The front panel is fitted with a grey Perspex cassette carrier, eject button and two indicator lights. Control circuits contain 39 ICs on 3 PCBs. Front panel is 137mm square and the unit is 200mm deep. These are offered in good ex-equipment condition at a fraction of their original cost, **ONLY £44.50** inc vat and postage.
Data inc circuits and layouts of PCBs **£3.50**

HIGH QUALITY REPLACEMENT CASSETTE HEADS



Do your tapes lack treble? A worn head could be the problem. Fitting one of our replacement heads could restore performance to better than new! Standard mountings make fitting easy and our TCI Test Cassette helps you set the azimuth spot-on. We are the actual importers which means you get the benefit of lower prices for prime parts. Compare us with other suppliers and see! The following is a list of our most popular heads, all are suitable for use on Dolby machines and are ex-stock.

HC20 Permalloy Stereo Head. This is the standard head fitted as original equipment on most decks. **£5.11**
HM90 High Beta Permalloy Head. A hard-wearing, higher performance head with metal capability. **£8.08**
HS16 Sendust Alloy Super Head. The best head we can find. Longer life than Permalloy, higher output than Ferrite, fantastic frequency response. **£9.01**
HQ551 4-Track Head for auto-reverse or quadrophonic use. Full specification record and playback head. **£9.79**
MA481 Latest version Double Mono (2/2) record/Play head. Replaces R48. **£5.90**
SM166 Standard Mounting 2/2 Erase head. Compatible with above or HQ551 4 Track head. **£5.90**
ME151 Non Standard Mounting 2/2 Erase head. **£4.25**
H524 Standard Erase Head. Semi double gap, high efficiency. **£1.50**
H561 Metal Tape Erase Head. Full double gap. **£4.90**
RS7106 Audio Visual Head. (1/2 plus top 1/4). **£10.82**
Please consult our list for technical data on these and other Special Purpose Heads.

'STEREO AMPLIFIER MODULE'

Ready built and tested quality power amplifier module complete and ready to use. Mains input 220/240v with power to spare for tuner and tape deck. Size 190 x 110 x 65mm

TUNER AND PRE-AMP MODULE

Matching unit to above. Contains Long, Medium and Short wave AM tuner. Stereo FM tuner and pre-amp with switched inputs for tuners, tape and pickup. Complete with flywheel drive and cord assembly. Size 400 x 220 x 60mm.
Special offer for both items only **£16.90**

All prices exclude VAT unless stated

Please Note: New Phone Number: **(0691) 652894**
Personal callers are always very welcome but please note that we are closed all day Saturday



HART

HART ELECTRONIC KITS LTD
PENYLAN MILL
OSWESTRY, SHROPSHIRE
SY10 9AF

CORRECTIONS AND MODS

Whilst every effort is made to ensure that there are no mistakes with our diagrams, the occasional error does occur. We appreciate our readers' co-operation in notifying them to us.

VHF/UHF FREQUENCY METER (May 1984 issue)


Due to an error the foil pattern was printed in mirror image in last month's issue.

It has also been noted that some of the ICs are static sensitive so care should be taken with handling.

VR1 should have read 100K and not 100R.

YAESU FC102 REVIEW (July 1984 issue)

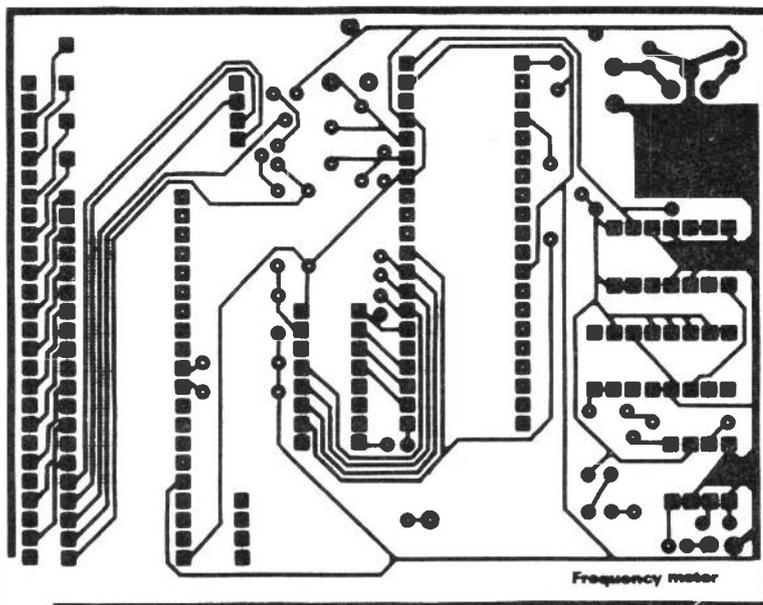It appears that part of the review could be misinterpreted, so we advise our readers to read their instruction manuals thoroughly before using.



EXT ISSUE • NEXT ISSUE • NEXT ISSUE • NEXT

NOISE

James Dick takes a look at what we call noise

AM RAD

An experimental signal generator described by Paul Wesley Warren

DISTANCE AND BEARING PROGRAM

Steven Pocock describes his simple program

PLUS all the usual features!

New Products • News • Reception Reports . . .

DON'T MISS the September issue – on sale **9th August**

To be sure of your copy of *Radio & Electronics World*, complete the newsagent order form in this issue or take out a subscription

EXT ISSUE • NEXT ISSUE • NEXT ISSUE • NEXT

DX-TV RECEPTION REPORTS

Compiled by Keith Hamer and Garry Smith

Sporadic-E is on the way. That was the message during April when several pre-season openings were noted at considerable strength and duration. The first of these was noted on the 8th with a football match from Spain on channels E2, E3 and E4 in the early afternoon. Other programmes followed and the opening lasted until 1530.

Another opening occurred on the 22nd with strong and consistent signals from Italy on channel IA for well over an hour from 1000 BST. The programme was a religious service and at times it appeared on channel IB. Italian signals appeared again during a lengthy opening which was first noticed at 1920 on the 28th. Fortunately there were no problems with identification. The normally small 'anti-pirate' inscription of 'RAI' was in much larger letters towards the top right-hand corner of the picture. You couldn't miss it!

Signals from the east were noted on April 23. The opening was already in progress at 1340 when the receivers were switched on. A cinemascope feature film was noted and, judging by the captions, it was of Polish origin. To confuse the issue, some captions in the Cyrillic alphabet were seen after the film on channel R1, with a newsreader or announcer in uniform appearing a little later.

A new channel R1 transmitter has opened in Poland at Siedlce close to the Russian border and one wonders if this may be a joint Polish/Russian service. Several other enthusiasts noted this transmission.

Due to tropospheric activity in Band III and at UHF towards the end of the Easter period, quite a few elusive stations were picked up. At least one enthusiast saw Polish Band III stations. Here in Derby the main highlight was RTL Luxembourg on channel E7 with the test card. Normally reception on E7 is very difficult due to the local menace (Lichfield

channel B8), but fortunately the transmitter had been switched off for several days.

DX log for April

The following log should give newcomers to DX-TV an idea of just what can be received:

2/4/84:

SRG (Switzerland) on channel E3 with the '+PTT SRG 1' FuBK test card from the Uetliberg transmitter; CST (Czechoslovakia) channel R1 radiating the EZO-type test card from Ceske Budejovice.

3/4/84:

CST R1, R2 on EZO test card.

4/4/84:

TVE (Spain) E3 with the GTE colour test card; CST R2 on test pattern; MTV-1 (Hungary) with a multiburst/frequency gratings pattern on channel R1.

6/4/84:

TVE E3 on GTE test card with several sightings via meteor shower (MS); CST R2 on test card.

8/4/84:

TVE E2, E3, and E4 during the early afternoon with football followed by other programmes until 1530.

9/4/84:

TVE E3 on colour test card; NRK (Norway) on E4 with the PM5534 test card including the identification 'Norge Kongsberg'.

10/4/84:

TVE E3 on a bar test pattern with indecipherable identification; the GTE test card was also seen; TVP (Poland) R1 on the PM5544 with a dark background; CST R1 on EZO test card; ORF (Austria) on channel E2a with the PM5544 test card and 'ORF FS 1' identification. This was

also noted in Band III on channel E5 via MS.

12/4/84:

Unidentified PM5544 test card on channel R2 but thought to have been of Hungarian or Czechoslovakian origin.

13/4/84:

TVE colour test card on channel E3.

22/4/84:

RAI (Italy) from 1000 BST onwards with a religious service until 1100 via Sporadic-E (SpE). This programme was also noted on channel IB; TSS (Russia) or TVP on R1 with a cinemascope feature film during the early afternoon via SpE.

24/4/84:

SR-1 (Sweden) on E2 with the 'TV 1 Sverige' PM5544; several West German stations noted via enhanced tropospheric conditions at UHF including the Hessischer Rundfunk test card and 'hr 3 FFTM' identification on their FuBK on channel E37.

25/4/84:

West German trop signals including WDR-1 (Westdeutscher Rundfunk) from the Langenberg transmitter on channel E9; mystery colour bars noted on E5 at 0825 via weak trop.

26/4/84:

RTL (Luxembourg) on E7 with the 'RTL Plus' PM5544 test card; SWF-1 (Südwestfunk) on channel E9 from Hornisgrinde in West Germany with the FuBK test card and 'SWF BADN' identification.

28/4/84:

RAI on channel IA with programmes from 1900 BST via Sporadic-E propagation.


30/4/84:

TVE E3 on a bar pattern which included the transmitter identification 'RTVE Gamoniteiro'. This pattern was featured in the August 1982 edition of *R&EW*.


Reception reports

Kevin Jackson (Leeds) logged a few unusual transmissions towards the end of April via the improved trop conditions. The 8KW NDR (Norddeutscher Rundfunk in West Germany) outlet at Sylt on channel E41 was seen radiating a test card similar to the one shown in the July 1984 issue of *R&EW*.

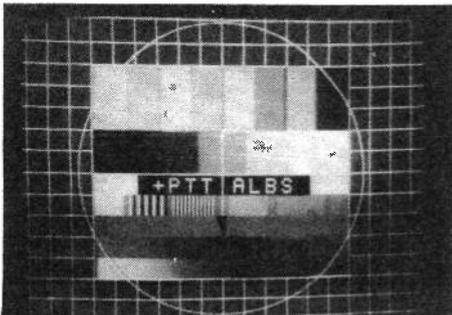
Kevin's best DX event was on the 26th when a Polish Band III station appeared



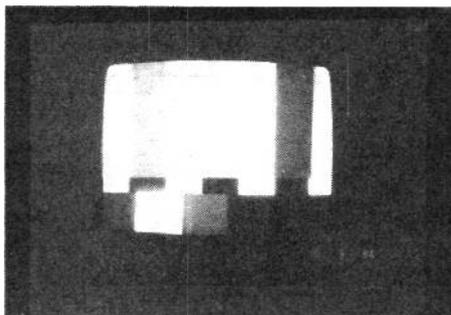FuBK from Albis, Switzerland. Photo courtesy of Gosta van der Linden



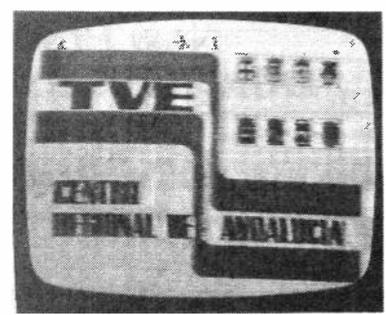AFN-TV Berlin. Photo courtesy of Jürgen Klassen



TVE identification from Andalucia, Spain

DX-TV RECEPTION REPORTS

on a clock caption followed by an identification caption and programmes. Transmissions came from the channel R6 outlet at Olstzyn, a distance of 1438Km.

Adrian Patton of Grimsby has commented on the growing problem of interference in his area from a nearby cordless 'phone installation'. He's also experiencing problems from a home computer. This produces negative images throughout Band I. Has anyone a suggestion regarding a remedy? Incidentally, Adrian wouldn't mind a chin-wag with any local DX-TV or amateur radio enthusiasts particularly at weekends. He may be contacted by dialling 0472 887950.

Wigan enthusiast Tony Cater has discovered a possible pirate radio link just below channel E21. The identification 'KFM 24 hours a day' has been heard and transmissions come from the Manchester area. An out-of-band amateur station has also been noted from the

same direction.

Andy Webster (Billinge, Wigan) noted patterning over RTE (Eire) on channel IH. Further investigations revealed an electronically generated chessboard pattern not unlike the old Zimbabwe type. The signal, at approximately 210MHz, later switched to a picture showing an amateur enthusiast and some of his equipment, but there was no sign of a signal on the 70cm amateur band. Towards the end of the month, Andy noted Sporadic-E activity on channel R1 with possibly the new Polish transmitter at Siedlce.

Over the Easter holiday Clive Athowe of Blofield near Norwich refurbished his DX shack. It now resembles an executive suite with fitted carpets and armchairs. He's also forwarded an executive-style log - it's a computer print out! Band III meteor shower goodies include CST (Czechoslovakia) on channel R6 from Pardubice on April 8th radiating the test



card, and TVP (Poland) from Gdansk or Krakow showing the dark PM5544 test card on channel R10.

The E2 outlet at Gwelo in Zimbabwe appeared on the 20th with programmes accompanied by Italian channel IA signals. Gwelo appeared again on the 24th but this time with the 'ZBC TV' PM5544 test card. Sporadic-E was active on several occasions. The Russian '0249' monoscopic test card came up on R1 for about thirty minutes during the morning of April 24. Signals from Spain on channel E2 were also noted via SpE during the month with a bullfight showing all the gory detail!

DX-TV on video

Adrian Patton has taken us to task over our recent claim that the Hitachi VT 11E video cassette recorder has multi-band facilities. He owns such a machine but it is UHF-only.


There are apparently several versions

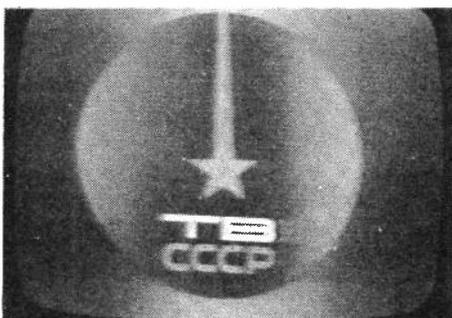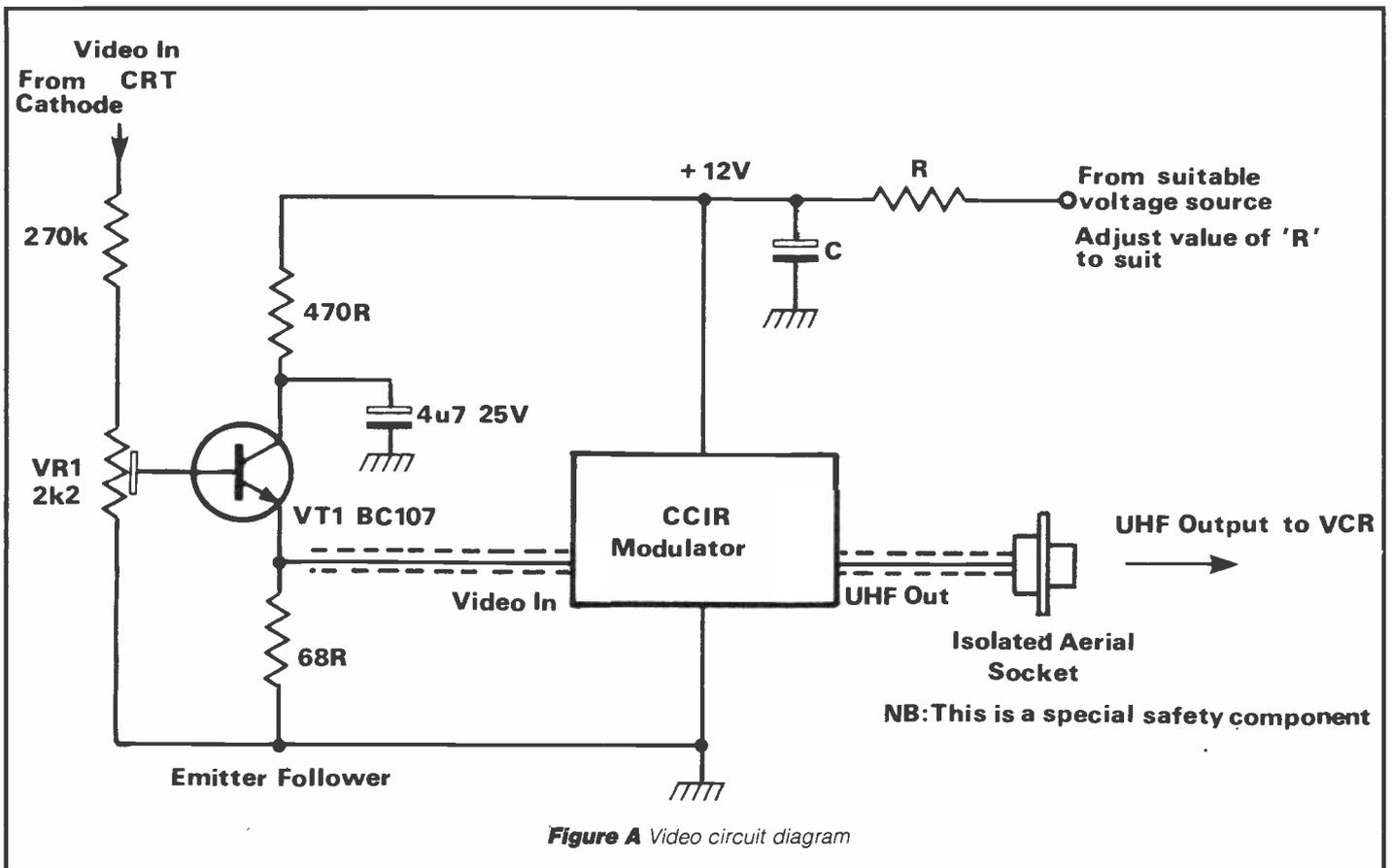

Russian identification caption on channel R1



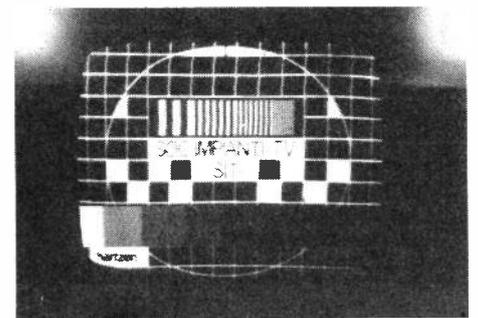Pirate TV aerials at Bergamo Northern Italy



Test card from Italian pirate station

DX-TV RECEPTION REPORTS

of this particular model. The VT 11E (DS) has multi-band facilities plus the PAL/SECAM switch which we referred to. The VT 11E (BS) however is UHF-only, although according to our service information the standard VT 11E does possess multi-band facilities. This is all very confusing and we wonder if the manufacturers know themselves!

While on the subject of video recorders, from time to time we are asked how Bands I and III DX can be recorded using a UHF-only VCR. One solution is to use a VHF to UHF converter to extract the signal at video.

The live chassis found in most receivers presents a problem but an attractive method which we have used for several years overcomes this.

It involves the use of an expensive UHF modulator with the video tapped off at the cathode of the crt. The reason for using the modulator is simple: it can be positioned inside the set with the signal leaving at UHF via an isolated UHF aerial socket. This is of the same type as found on most recent TV receivers.

The idea was originally suggested by Hugh Cocks of satellite TV fame and the simple circuit is shown in *Figure A*. The modulator is available from Sendz Components. The 12V supply may be conveniently obtained from virtually any low-voltage point within the receiver, for instance, the cathode of the sound

output valve. Adjustment to VR1 should be made for optimum results with signals of various strengths.

Service Information Netherlands:

AFN-TV officially commenced broadcasting on April 5 from the American Forces base at Soesterberg. The transmitter has an ERP of approximately 20KW and operates on channel A80, which would be equivalent to a European channel between E70 and E71.

The horizontally polarised transmitting aerial is located on a 40-metre mast. Programmes from AFN-TV Soesterberg consist of video recordings and are different from those radiated by the station in West Germany where material is received from America via satellite.

Norway:

NRK are expected to start a regional television service in September. Programmes will be produced by NRK at Sørland in Kristiansand and radiated via three main outlets. These will be Greipstad on channel E2 (60KW), Bjerkreim E6 (15KW) and Lyngdal E9 (30KW). A regional news programme will be broadcast on weekdays between 1745 and 1755 local time.

Belgium:

On February 20th, BRT TV2 program-

mes began from a 10KW ERP outlet in Brussels on channel E25. It replaces the E25 transmitter at Wavre which collapsed some time ago.

TELE-2 programmes on channel E49 originate from the Profondeville outlet which has an ERP of 50KW.

In the Brussels area the French satellite service known as TV5 is rebroadcast on channel E56 in PAL colour on the CCIR-H standard.

France:

Canal Plus commenced broadcasting on April 20 using the VHF Band III channel 1 (176MHz. vision, 182.5MHz sound).

Scrambled programmes will be radiated between 1000 and 1200 local time with non-scrambled material from noon until 1800.

The official starting date for Canal Plus is November 1, 1984. Six hours of programmes each day are scheduled but they will be mainly scrambled with only 45 minutes per day of de-scrambled material.

Test transmissions for Canal Plus on channel 1 have started in the area around Paris. The channel corresponds to the old channel F8a.

This month's Service Information was kindly supplied from various sources via Gösta van der Linden in Rotterdam, Netherlands.

YOUR RADIO AMATEURS EXAM SUCCESS

Study at home – pass first time with RRC's Complete Home Tuition Service

- Self-contained courses, regularly updated for The City & Guilds Radio Amateurs Exam ● Fully inclusive fees ● No costly, time consuming text books to buy ● Everything you need in booklet lecture form
- Regular tests ensure you are fully prepared ● Enrol at any time ● Timetable to suit you ● Continued tuition at no extra cost if you don't pass first time

FREE PROSPECTUS & ADVISORY SERVICE

Write or phone today for full details, and a FREE copy of our prospectus, without obligation to:



THE RAPID RESULTS COLLEGE

Dept. JY11, Tuition House, London SW19 4DS

Tel: 01-947 7272 (9am-5pm) – or use our 24-hour Recordacall Service: 01-946 1102 quoting Dept. JY11



Name _____
(BLOCK CAPITALS PLEASE)

Address _____

Postcode _____

My interest is _____



THE RAPID RESULTS COLLEGE



SAT ELECTRONICS

PROFESSIONAL 2M VHF POCKET SCANNER

**LIMITED SUPPLIES!!!
SO HURRY**



**£54.95
EX VAT**

A 10cm auto-scanning receiver. XTAL controlled double superheat with squelch. LED indication of channel and auto/manual scan SW. Contains crystals for 9 repeater outputs and the mobile calling channel. So you don't miss a thing on 2M. Powered by built in 6V nicad pack and can be run off an external 6V supply, for charging and use. Comes complete with rod antenna, earphone and carrying case. Can also be re-crystalled for use between 130 Mhz and 170 Mhz

Marine Band version available soon

SAT ELECTRONICS

164 Washway Road, Sale, Cheshire M33 1RH

Tel: 061 905 1040

Please add 15% VAT P&P inc

a.m.

ELECTRONICS LIMITED

REGULATORS

LM317T Plastic TO220 variable	£1.00
LM317 Metal TO3 variable	£2.00
7812 Metal 12v 1A	£1.00
L036 TO3 Metal 12v L037 15v	ea. 50p
7805/12/15/24 plastic	40p
7905/12/15/24 plastic	50p
CA3085 TO99	50p
LM723 14 dil or TO99	50p

EPROMS/MEMORIES

2764-300ns INTEL/FUJITSU	£6.50
2732A-3 Ex-eqpt.	£2.50
2102 500ns AMD	80p 10/£6.00
MC6810P	£1.05

POWER TRANSISTORS

TIP141,142,147 £1 ea. TIP112,125,42B	2/£1
TIP35B £1.30 TIP35C	£1.50
2N055 Motorola	50p 5/£2.00
2N055 Ex eqpt tested	5/£1.00
MJE3055, MJE2955 equiv.	ea. 50p

DISPLAYS

zFutaba 4digit clock fluorescent display	
FLT-02-8 also 5-LT 16 8J	£1.50
Futaba 8 digit calculator fluorescent display	
9CT-01-3L	£1.50
LCD Clock display 0.7in digits	£3.00
Large Clock display 1in digits	£3.00
7 seg 0.3in display comm. cathode	50p

MISCELLANEOUS

QUARTZ HALOGEN LAMPS

A1/216 24v 150w	£2.25
H1 12v 55w (car spot)	£1.25

WOUND POT CORES

with adjuster unused	
RM7 LA4245	3/£1.00
RM8 LA4344	2/£1.00

TOK KEY SWITCH 2 POLE 3 KEYS

ideal for car/home alarms	£3 100+£2.00
12v 1.2w small wire ended lamps fit AUDI/VW	
TR7 VOLVO	10/£1.00
14v 0.75w MES lamps	8/£1.00
Heat shrink sleeving pack	£1.00
PTFE sleeving pack asstd colours	£1.00
250 mixed res. diodes, zeners	£1.00
Mixed electrolytic caps	100/£2.00
ITT CASS. RECORD/PLAY AMP.+cct.	£2.00
Stereo cassette deck	£5.00
Stereo cass R/P head	£2.50
Mono head £1 Erase head	50p
Thermal cut-out 50°C, 77°C or 85°C	50p
Thermal fuse 121°C 240v 15A	5/£1.00
Vero pins fit 0.1in Vero	100/50p
Double sided PCB pins	100/50p
TO220 Micas + bushes	10/50p 100/£2.00
T03 Micas + bushes	10/50p
RELAYS 240v AC coil PCB mounting	
2 pole changeover £1 3pole c/o	£1.00
Varley 24v dc 4p c/o relay	80p
Fig 8 mains cassette leads	3/£1.00
KYNAR wire wrapping wire 2oz reel	£1.00
PTFE min. screened cable	10m/£1.00
TOKIN MAINS RFI FILTER 250v 15A	£3.00
TDK MAINS RFI FILTER 115v 15A	£1.00
IEC CHASSIS PLUG/6A RFI FILTER	£3.00
Epoxy potting compound 500g	£2.00
Mercury tilt switch small	£1.00
Min. rotary sw.4p c/o 1/8in shaft	2/£1.00

Thorn 9000 TV audio o/p stage	2/£1.00
10m7 CERAMIC FILTER	50p 100/£20
6m CERAMIC FILTER	50p
240v AC FAN 4.6in SQUARE NEW	£4.00
240/115v AC FAN 4.6in SQ NEW	£7.00
12v DC brushless fan reversible	
2.5in sq 2in deep QUIET	£9.00
BELLING-LEE 12way block L1469	4/£1
POTENTIOMETERS short spindle	
2k5 10k 2m5 Lin	5/£1
500k 1in 500k log long spindle	4/£1
40KHz ULTRASONIC TRANSDUCERS EX-EQPT. NO DATA	Pair/£1
STICK-ON FEET	20/£1
T03 TRANSISTOR COVERS	10/£1

RECTIFIERS

120v 35A stud	40p
12FR400 12A 400v small stud	4/£1.50
BY127 1200v 1.2A	10/£1.00
1N5401 100v 3A	10/£1.00
BY254 800v 3A	8/£1.00
BY255 1300v 3A	6/£1.00
1A 800v bridge rectifier	4/£1.00
6A 100v bridge	50p
10A 100v bridge	£1.25
15A 100v bridge	£1.25
25A 200v bridge	£2.00ea. 10/£18
25A 400v bridge	£2.50

SCRs

2N6399A 10A 600v	£1.00
BTX95 800v 15A	£1.20
35A 800v stud	£2.00
70A 500v large stud	£3.00
MCR106 equiv. 4a 400v	40p ea 100/£20.00
2N5061.8A 60V.8A 60v TO92	4/£1 100/£10.00
TICV106D.8A 400v TO92	3/£1 100/£15.00

TRIACS

TXAL228 8A 400v isol. tab	2/£1.00
20A 500v isolated ex eqpt tested	£1.50

CONNECTORS

'D' 9way £1 15way £1.25 25way	£2
37way £2 50way	£2.50
(Ex Eqpt price per pair) covers	50p ea
D9 PCB PLUG 90 deg.	£1.50
AMPHENOL (Centronics) 36 way plug + skt ex eqpt	£2.50
0.1in double sided edge connector 32way ideal ZX81/SPECTRUM	£1.50
0.1in d/sided pcb plug 24+25 way	£1.50
2 pole sub min connectors ideal radio control RS 466/472/488/343 5 pairs	£2

IDC CONNECTORS

25 way 'D' socket	£2.00
20 way socket (BBC user port)	£1.00
26 way socket (BBC printer)	£1.50
34 way socket (BBC disc drive)	£2.00
40 way socket	£2.00

IDC CARD EDGE CONNECTORS D/S EX-EQPT

34 way (fits disc drive PCB)	£3
40 way (fits Centronics 739 PCB)	£3
50 way	£3.50

WIRE WOUND RESISTORS

W21 or sim 2.5W 10 OF ONE VALUE for £1	
1R0 2R0 2R7 3R9 5R0 4R7 10R 12R 15R 18R 20R	
27R 33R 36R 47R 100R 120R 180R 330R 390R	
470R 560R 680R 820R 1K 1K2 1K3 1K8 2K7 3K3 10K	

W22 or sim 6 watt 7 OF ONE VALUE for £1	
R22 1R5 9R1 10R 12R 20R 33R 51R 56R 62R 120R 180R 270R 390R 560R 620R 1K2 2K2 3K3 3K9 10K	

W23 or sim 9 watt 6 OF ONE VALUE for £1	
R22 1R0 3R0 6R8 56R 62R 100R 270R 1K8 10K W24/ or sim 12 watt 4 of one value for £1	
R50 2R0 10R 18R 68R 47R 75R 82R 150R 200R 270R 400R 620R 820R 1K	

PHOTO DEVICES

Slotted opto-switch OPCOA OPB815	£1.30
2N5777	50p 100/£26 1000/£190
TIL81 TO18 Photo transistor	£1
TIL38 Infra red LED	2/50p
OPI2252 Opto isolator	50p
Photo diode	50p 6/£2
MEL12 (Photo Darlington base o/c)	50p
RPY58 LDR	50p
TO18 LDR	50p
LEDs Red 3mm or 5mm	12/£1 £5/100
Green + yellow 3/5mm	10/£1 £6/100
Flashing red 5mm	50p
Bicolour red/green 5mm or rect.	50p 5/£2

DIODES

1N4151 sim 1N414B	100/£1.25
1N4148	100/£1.50
1S3740 Germanium	100/£2.00
1N4004 or SD4 1A 300v	100/£3.00
1N5401 3A 100v	10/£1.00
BA157 1A 400v Fast recovery	100/£2.50
BA159 1A 1000v Fast recovery	100/£3.50

MULTI TURN PRESETS

10R 20R 100R 200R 500R	
2K 5K 22K 50K 100K 200K	40p

IC SOCKETS

8pin 12/£1, 14pin 10/£1	
18/20pin 7/£1 100/£12 1k/£80,	
22/28pin 25p, 24pin 25p 100/£20 1k/£100,	
40pin 30p, 16 pin 12/£1 100/£6	

TRIMMER CAPACITORS small

Grey 1.5-6.4pF, Green 2-22pF 6 for 50p,	
Yellow 2-16pF	

SOLID STATE RELAYS NEW 10A 250v AC zero voltage switching control voltage 8-28v DC

DC	£2.50
VARIAC 0 to 270v 12A new uncased	£20
VARIAC 0 to 130v 6A new uncased	£6

POLYESTER/POLYCARB CAPS

10n ax. 100/£2, 22n radial 100/£2.50, 47n rad. 100/£2.50	
1u 250v Polyester C280	5/£1 100/£10
1u5 P/carb 15mm rad	100/£5.00
2u2 160v rad 28mm	100/£10
470n 250v AC X rated rad	4/£1
100n 250v AC X rated rad 20mm	4/£1
33n 250v AC X rated rad 15mm	10/£1

BEAD THERMISTORS

GLASS BEAD NTC Res @ 20	80p
250R 1K2 50K 220K 1M4	
R53 THERMISTOR	£2.00

BEAD TANTALUM CAPS

47u 3v, 10u 6V3, 68u 6v	12/£1 100/£6
2u2 20v	8/£1 100/£8

SMALL AXIAL CERAMIC CAPS 50V

15p 18p 22p 27p 33p 47p 68p 82p 470p 1n 10n(25v)	100/£3
--	--------

STEPPER MOTOR 4 PHASE 2 9v WINDINGS

	£4.50 10/£35
--	--------------

KEYTRONICS

332 LEY STREET ILFORD, ESSEX
Shop open Mon-Sat 10am-2pm
TELEPHONE: 01-553 1863

MIN ORDER £2.50 OFFICIAL ORDERS WELCOME
UNIVERSITIES · COLLEGES · SCHOOLS · GOVT DEPARTMENTS
P&P AS SHOWN IN BRACKETS (HEAVY ITEMS)
50p OTHERWISE (LIGHT ITEMS)

ADD 15% VAT TO TOTAL


ELECTRONIC COMPONENTS BOUGHT FOR CASH



SHORT WAVE NEWS FOR DX LISTENERS

BY Frank A Baldwin

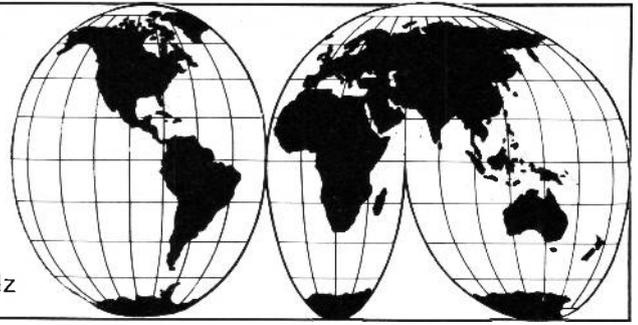All times in GMT, **bold** figures indicate the frequency in KHz



AROUND THE DIAL

With the 'season' in full swing for the best chance of reception in the UK of signals from Latin America, I bring to your attention the Republic of Peru and in particular some of the out-of-band stations that have recently been reported.

Peru is in west South America with the capital, Lima, being some 13Km from the chief port of Callao. The country is bounded in the west by the Pacific Ocean and divided by two ranges of the Andes with high altiplano in between.

The western range features two high volcanoes, El Misti and Huascaran, whilst in the east are the West Amazon rain forests.

The population is mostly Indian, the Inca capital being at Cuzco on the high altiplano, the Inca Atahualpa being captured and treacherously executed by Francisco Pizarro and his band of adventurers – the so-called Conquistadors, who eventually fought amongst themselves. All that sets the scene, now we deal with the DX.

The details listed here are correct according to the latest information that I possess, although I should mention that some of the frequencies are apt to vary on occasions – this habit being part of the LA DX game. Where a time is stated (not a transmission period) it indicates when heard.

Logging some of these Peruvians will prove to be far from an easy matter. Apart from their relatively low powers, there is the ever present problem of the commercial QRM which abounds around most of the channels listed. For these reasons alone the successful reception by a UK based enthusiast would represent a DX feat of no mean order.

In frequency order for ease of operating, we commence with –

Radio El Sol de Los Andes, Cuatunumi, Santa Cruz on **4254.5**. The only other details

known about this one is that it announces as being on **4225** and has also been heard on **7073.5**.

Radio Frecuencia Juvenil, Cajabamba, Cajamarca, on **4361**, operating a schedule from 0000 to 0400.

Radio Inca del Peru, Los Banos del Inca, Cajamarca, on **4494** – not to be confused with Radio Inca del Peru based in Lima.

Radio Los Andes is located in Tayacaya, Huancavelica, where it is scheduled around-the-clock, the frequency being **5300**.

Radio San Francisco, Ayacucho, is timed on the air from 2300 to 0330 on **5301**.

Radio Nueva Acobamba, Acobamba, Huancavelica, is on **5325** where it operates from 1100 to 0230.

Radio La Voz del Noroiente, Jaen, Cajamarca, on **5340** is scheduled from 1100 to 0200.

Radio Vision, Juanjui, San Martin, is on **5360** schedule unknown.

Radio Pucara, Jaen, Cajamarca, is on **5560** from 2300 to 0200.

Radio Yucan, Cutervo, Cajamarca, is on a reported **5617** from 1110 through until 0007.

Radio Bambamarca, Bambamarca, Cajamarca, is on **5656** from 2100 to 0300.

Radio Acunda Mariscal Morales, Chota, Cajamarca, is reported on **5657** from 2000 to 0400.

Radio San Miguel, San Miguel de Pallaques, Cajamarca, is on **5707** from 0045 to 0250.

All of the foregoing was retrieved from my computer memory bank but much of it was originally obtained from *Short Wave News*, the journal of the Danish Short Wave Clubs International with additional information from the *World Radio Handbook*, 38th Edition, to whom acknowledgements are made.

Next month I will be dealing with some more of the Peruvian transmitters.

African stations are listed first and these will provide some hours – or even days – of endeavour and enjoyment for those readers interested in the short wave world.

AFRICA

Cameroon

Radio Douala on **4795** at 2052, OMs with songs in vernacular complete with drums and other local instruments – very rhythmic. R Douala is on the air from 0425 to 0800 and from 1630 to 2300 with a power of 100KW.

Yaounde on **4850** at 2055, OMs and YLs with local songs in vernacular and OM with announcements in French. The schedule is from 0430 to 0700 and from 1630 to 2400. This is the National Service in English and French.

Chad

Radio Chad, N'djamena, on a measured **4904** at 1910, OM with a talk in French, drums in typical African style. OM with station identification at 1930 in French. The schedule is thought to be from 0500 to 2100, Saturday until 2200 although I have not confirmed this period. N'djamena is probably better known as Fort Lamy; it is the capital of the Chad Republic sited at the confluence of the Shari and Logone rivers. It is the centre of the caravan trade and somewhat isolated. The power is 100KW.

Egypt

Cairo on **11665** at 0015, chimes time-check, OM with station identification and the news in Arabic in a programme of the Domestic/External Service, scheduled on this channel from 1900 to 0030.

Kenya

Nairobi on **4934** at 0334, OM with recitations from the Holy Quran in the Eastern Service programme timed from 0250 to 0630 and from 1420 to 2010

(General Service on Sunday only until 2110).

Libya

Tripoli on **11815** at 2003, OM with a talk in Arabic in a 'Voice of the Greater Arab Homeland' programme, timed on this frequency from 1800 to 2100 and from 2300 to 0330. English to North America in a Radio Jamahiriya presentation is timed on this channel from 2100 to 2250 although the timings of these programmes are apt to vary from day to day.

Nigeria

Radio Nigeria, Lagos, on a measured **4932** at 2103, OM with a newscast of both African and world events. This is the Educational Service which is on the air from 0400 to 2300.

Sao Tome

Radio Nacional on a measured **4807** at 2026, music in the fast rhythmic local style, OM with announcements in Portuguese. This one is scheduled from 0530 to 2300 (Saturday until 2400) and the power is 10KW. Sao Tome has recently come to life again after an absence of about eighteen months. Similarly, Chad mentioned above went silent in 1979 but re-emerged earlier this year.

Senegal

Dakar on **11895** at 0612, OM with a newscast in French, a short interlude of some orchestral music then OM & YL alternate with announcements during a French programme for West and Central Africa, daily from 0600 to 0800.

AMERICAS

Argentina

Radio Rivadavia, Buenos Aires, on a measured **5882** at 0150, a commentary in Spanish describing the events during an exciting, apparently, futbol (football) match between two local teams.

A GREAT MAGAZINE FOR ALL ASPECTS OF PRACTICAL AMATEUR RADIO



Packed with more editorial features than any other magazine plus more pages of readers small ads

ALSO . . .

. . . Product reviews . . .
 Communications & electronics news . . .
 Reception reports — shortwave, DX-TV, ATV . . .
 Construction projects — what to build for your rig, your computer & your enjoyment . . .
 New technology . . .
 Educational articles . . .
 Coming events . . .
 Readers letters . . .
 Technical & practical questions answered . . .
 Latest equipment reviews . . .
 and all the latest news in the Amateur Radio World . . .
 Keep in touch with up to date developments - TAKE **R&EW** every month and stay informed.

SUBSCRIBER BENEFITS

Take out a **POST FREE (UK) Sub while offer lasts**

- Delivery to your door by publication date each month
- Inflation proof — price guaranteed for 12 months

On sale NOW at your newsagent and at equipment dealers

RADIO & ELECTRONICS WORLD SUBSCRIPTION ORDER FORM

To: Subscription Department • Radio & Electronics World • 513 London Road • Thornton Heath • Surrey • CR4 6AR. Tel: 01-684 3157

NAME

ADDRESS

.....

Postcode.....

PLEASE SUPPLY: (tick box) for 12 issues, all rates include P & P

Inland £10.80 World-Surface £11.65 Europe-Air £17.50 World-Air £28.50

PAYMENT ENCLOSED: £ —

Cheques should be made payable to Radio & Electronics World. Overseas payment by International Money Order, or credit card.

CREDIT CARD PAYMENT

.....

Signature..... RE0884

SHORT WAVE NEWS

R Rivadavia is on the air Monday to Friday inclusive from 2100 to 0200 but extended to 0400 on football events, Saturday from 2300 to 0400.

Brazil

Radio Emisora Rural, Santarem, on **4765** at 0048, OM with a sporting commentary in Portuguese, the signal surprisingly riding over that of the R Moscow relay in Havana. R Em Rural is on the air from 0800 to 0300 at 10KW.

Radio Nacional da Amazonia, Manaus, on **4845** at 0026, OM with a local pop song in Portuguese, OM with announcements. The schedule is from 1300 to 0800, the power 250KW.

Radio Baré, Manaus, on **4895** at 0039, YL with a ballad in Portuguese complete with guitar backing. R Baréis on the air from 0830 to 0130 with a power of 1KW.

Radio Cultura do Para, Belem on **5045** at 0053, a programme of recorded local pops, OM announcer. The schedule is from 0700 to 0300 with a power of 10KW.

Radio Nacional da Amazonia, Brasilia, on **11780** on 0125, OM announcements in Portuguese, YL with a pop song, OM with station identification at 0130. This one radiates from 0800 to 1600 and from 1800 to 0200 with a power of 250KW.

Radio Globo, Rio de Janeiro, on **11805** at 0120, OM with a sports commentary then OM with promos. R Globo operates from 0800 to 0400 with a power of 10KW.

Radio Clube de Pernambuco, Recife, on **11865** at 0125, OM a talk in Portuguese, announcements then promos. RC de Pernambuco is scheduled from 0900 to 0400 with a power of 1KW.

Colombia

Radio Guatapuri, Valledupar, on **4815** at 0320, OM with a local pop song, OM with announcements in Spanish. The schedule is from 1000 to 0500 with a power of 10KW.

Radio Sutatenza, on **5095** at 0323, OM with announcements in Spanish then a programme of recorded local pops. On the air from 0900 to 0400 at 50KW.

Ecuador

CRE Guayaquil on a measured **4656** at 0136, OMs with a discussion in Spanish and several mentions of Guaya-

quil. Radio Dif del Ecuador (CRE) operates from 2300 to 0400 with a power of 5KW.

Radio Luz y Vida, Loja, on a measured **4851** at 0339, OM with a local pop song in Spanish, OM announcements. Sometimes on a 24-hour schedule but normally from 1045 to a variable 0400. The power is 5KW.

Peru

Radio Ondas del Titicaca, Puno, on a measured **4922** at 0019, OM with a talk in Spanish about Peruvian affairs, several place names being mentioned. Slightly muffled speech and some echo-effect probably due to studio conditions. This one operates in Spanish or Aymara - the local Indian language - to the schedule 0945 to 0300 with a power of 1KW.

Venezuela

Radio Valera, Trujillo, on **4840** at 0315, OM with station identification, promos in Spanish then into a programme of local pops. R Valera is on the air from 1000 to 0400 with a power of 1KW.

Radio Capital, Caracas, on **4850** at 0012, OM with the station identification, announcements and local pops. The schedule is from 1000 to 0500 and the power 1KW. Recently reactivated, this one has been off the air since 1978.

Radio Barquisimeto on **4990** at 0339, OM announcements in Spanish, OM ballad - rather sorrowful at that! The schedule is from 1000 to 0400 with a power of 15KW.

ASIA

China

Radio Beijing on **9900** at 2014, YL with a talk during the Standard Chinese transmission directed to Europe and North and West Africa and timed from 2000 to 2100.

India

AIR (All India Radio) Delhi on **9665** at 1957, OM with announcements, frequencies and times of transmissions then YL with a newscast during the English programme for the UK and Western Europe, scheduled from 1845 to 2230. Also logged in parallel on **9755**.

AIR Delhi on **11620** at 1317, OM with a talk in the Sinhalese programme to

Asia, timed from 1300 to 1330.

Iran

Teheran on **9770** at 2030, trumpet call, OMs with a military marching song then OM and YL alternate with a newscast in Persian (Farsi). Schedule on this channel is unknown. Also logged in parallel on **9022**.

Israel

Jerusalem on **11655** at 0120, OMs and YLs with a discussion about local politics during an English presentation to the Americas and Europe, scheduled from 0100 to 0125.

Jerusalem on **9815** at 2004, OM with news comment in the English programme to Africa, Europe and North America, schedule from 2000 to 2030 - a more reasonable time than the above for many readers perhaps.

North Korea

Pyeongyang on **9360** at 1823, YL with announcements, local music and songs in the French programme to Europe, timed from 1700 to 1850.

Saudi Arabia

Riyadh on **5875** at 0254, interval signal, national anthem, OM station identification in Arabic at sign-on of the Domestic Service General Programme which is on this channel from 0255 to 0500 and from 1000 to 2300.

Sri Lanka

Colombo on **11800** at 1734, local-style music and YL with a song during the Urdu transmission to East Africa and the Middle East scheduled from 1645 to 1745.

OM with station identification and news in the English programme to the same target areas and timed from 1745 to 1815.

Turkey

Ankara on **9695** at 2120, YL with a song, local-type music during the Turkish programme for Turks abroad, featured from 1600 to 2200 on this frequency.

Yemen Arab Republic

San'a on **9780** at 2020, OM with some songs in Arabic complete with local orchestral backing during the all-Arab transmission on this channel from 0300 to 0700 (to 1000 on Friday) and from 1100 to 2110.

EUROPE

Austria

Vienna on **11660** at 1858, interval signal, OMs with the station identification in French, German and English, frequencies, then into the German transmission for Europe, North Africa, the Middle East and South and West Africa, scheduled from 1900 to 2000.

Spain

Madrid on **11880** at 2040, YL with a news comment on both local and world events in the English presentation for Africa, timed from 2030 to 2130.

Greece

Radio Macedonia on **12000** at 1004, YL with folk songs and music, YL with announcements in Greek. The schedule is from 0355 (Sunday from 0425) to 2305.

Malta

Deutsche Welle (Cologne, West Germany) relay on **11795** at 1417, YL with announcements during the German programme for Europe, the Middle East, South and South East Asia, timed from 1400 to 1600. A news comment followed.

Portugal

Lisbon on **11800** at 1506, OM with a football commentary in the Portuguese programme for India and the Middle East, scheduled from 1400 to 1600.

CLANDESTINE

National Voice of Iran on **5915** at 1932, OM with a talk in the Persian programme with several mentions of Ayatollah Khomeyni. The Persian (Farsi) language is used from 1730 to 1745, 1800 to 1815 and from 1930 to 1945. Seda-ye Melli-ye Iran is pro-Soviet (transmissions emanate from the Baku transmitters) anti-US but hostile to Khomeyni although originally they were pro-Khomeyni.

NOW HEAR THESE

Abidjan, Ivory Coast, on **11920** at 0600. Radio Amazons, Iquitos, Peru, on **5060** at 0345. At 5KW the schedule is from 1000 to 0500. Melbourne on **11790** from 1500 to 1600 and from 2000 to 2030 on this channel. Also have a try for signals from the standard frequency and time signal stations.


NEW IMPROVED

Radio & Electronics World


The communications, electronics & computers magazine

BACK ISSUE SERVICE


All issues from October 1981 onwards are still available, with the exceptions of January 1982 and February 1982. All orders must be pre-paid, the cost of each issue being £1.00 inclusive of postage and packing. A contents index spanning the issues from October 1981 to September 1983 is available on receipt of a stamped addressed envelope. To ensure that you don't miss any future issues, we suggest that you place a regular order with your newsagent or complete the subscription order form found in this issue.

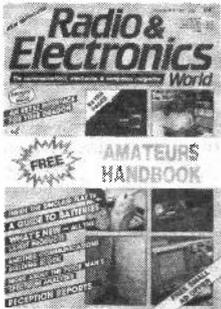

DECEMBER 1983
Designs — Poor Man's Spectrum Analyser Part 2; Communications Building Blocks Part 2; A 4001/4011 Tester; Continuity Tester. *Features* — Inside the Sinclair Flat TV, An in-depth probe; A Circuit Designers Guide to Batteries; Data File on Op-Amps Part 1; Metal Detectors in Warfare; Data Brief 1-LM1821S Video IF PLL Synchronous Detector; Data Brief 2-SL6270 Gain Controlled Audio Amplifier; An RS232C Interface for Your Dragon 32. *Reviews* — ALDEN Weather Chart Recorder Kit; Digithurst MicroSight 1.

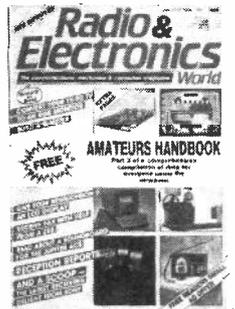

JANUARY 1984
Designs — Communication Building Blocks (Active Antennae); FAX Receiver; RGB Interface for the Ferguson TX-90; A Couple of Voltage Detectors; LCD Capacitance Meter; Cymar Q-meter (An aid to winding coils); Zener Diode Checker; A Drinker's Delight; LCD Display Option for the Rewbichron II. *Features* — A Novel Receiver (Sony); Capacitors for Coupling, De-coupling and Filtering; Data File on Op-Amps Part 2; Farewell to Test Card F; A Soundboard for the Jupiter Ace; Data Brief — MC1377 Colour Signal Encoder.

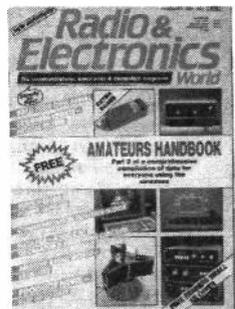

FEBRUARY 1984
Designs — Switched Mode Power Supplies — Crowbar Protection Circuit; Switched Step Attenuator; Universal NiCad Charger; Communications Building Blocks (IF Amplifiers); Real Time Calendar Clock. *Features* — Data File on Op-Amps; Six Antennas from Three Wires (Double your directions without doubling your cost); Designers Update (Helical Filters); Moving Pictures from Wax — Phonovision; Computers, Communications and Applications; Data Brief — Low cost, wide range varicap diodes.



MARCH 1984
Designs — Modifying the Pye PF1 Pocketfone Receiver; Communications Building Blocks (IF Amplifiers); One Night's Work (Audio-Amp); 200W PEP Transmatch. *Features* — Sony ICF 7600D Receiver; Data File on Op-Amps; UOSAT-B; AKD Absorption Wavemeter; Data Brief — Hitachi HA 1197 AM Tuner; Oscar 10 and its Orbit Parameters; Programmable Sound Generator (the AY8910 family); Random Morse Computer Program; ICOM World Clock.



APRIL 1984
Designs — One Night's Work (IF Oscillator); HF Linear Amplifier; The Piano Key — only £5 for Perfect Morse; Peak-Reading LED RF Wattmeter; Speech and the Computer — Make the Beeb Micro Talk!; 2 Metre Tiger Antenna. *Features* — Hall Effect Devices — Exploiting Magnetism's Effect on Conductors; Data File — CMOS Bilateral Switches and Multiplexer/Demultiplexer ICs; Data Brief-TD 2002A Linear IC



MAY 1984
Projects — One Week's Work (VHF/UHF Frequency Meter); Spectrum Analyser Update; Assembling a Logic Probe Signal Generator; 2 Metre J-Stick Aerial; SX-200 Relative S-Meter. *Features* — Data File — 4046B Phase-Locked Loop CMOS IC; Hamey HM203-4 Oscilloscope review; A Beginners Guide to Meteor Scatter Propagation; High & Low Measurements — A Guide to Measuring Outside the Conventional Ranges



JUNE 1984
Projects — Microprocessor Controlled Dot Matrix Printer; One Night's Work — Replacement Plug-in Module for 2532 EPROM; A low-cost Frequency Standard; Radio Frequency Bridge; Modifying the RGB Interface for the Ferguson TX90. *Features* — High Speed Data Transmission; Trio-Kenwood TS-430S Transceiver; ZX Spectrum Data Transmission Program; Data File — National Semiconductors LM Range of Dual Audio-Preamplifier ICs; Data Brief — MC 1648 (SL 1648) Voltage Controlled Oscillator; HP41CX Calculator Review



JULY 1984
Projects — VLF converter, a unit for the very low frequency; Teleprinter Terminal Interface; Multifunction Test Instrument, a versatile piece of test equipment; Building the Fortop TVT-437; Improving Indoor Aerials, getting better reception without an aerial amplifier; Logic Probe for CMOS and TTL's. *Features*; Amplicon Digital Panel Printer; Oscar 10; Yaesu FC102 Review; Data File — audio power amplifiers; Images of the World, a new publication review.

RADIO & ELECTRONICS WORLD

TO: Back Issues Department • Radio & Electronics World • Sovereign House • Brentwood • Essex • CM14 4SE

NAME:

ADDRESS:

POST CODE:

BACK ISSUE ORDER FORM

PLEASE SUPPLY: (state month and year of issue/s required) [NOTE: January & February 1982 issues not available]

.....
..... at £1.00 each


PAYMENT ENCLOSED: £ —

Cheques should be made payable to **Radio & Electronics World**. Overseas payment by International Money Order or credit card

CREDIT CARD PAYMENT:

.....

SIGNATURE

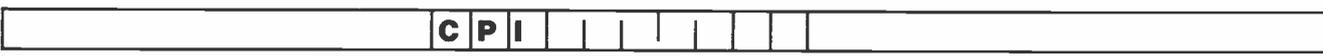

FREE CLASSIFIED ADS

FREE CLASSIFIED ADS CAN WORK FOR YOU

We are pleased to be able to offer readers the opportunity to sell your unwanted equipment or advertise your 'wants'.

Simply complete the order form at the end of these ads, feel free to use an extra sheet of paper if there is not enough space on the order form. We will accept ads not on our order form.

Send to: **Radio & Electronics World**, Sovereign House, Brentwood, Essex CM14 4SE.

DEADLINE AND CONDITIONS

Advertisements will be inserted in the first available issue on a first come first served basis. We reserve the right to edit and exclude any ad. Trade advertisements are not accepted.

FOR SALE

■ Ham int Major M588 USB, LSB, AM, FM, 26.515 to 27.855MHz, 5KHz shift. Zetagi BV131, 200W linear amp. Eurosonic 178 power/SWR Mod/FS meter-matcher. Zetagi P27, RF preamp. All superb condition, only eight months old. Current owner now licenced. £130 or exchange HF receiver in good condition. Tel: Camborne 0209 718021

■ Yaesu FT101E, good condition, with 600Hz filter, fan, and fist mic. £285. Yaesu YC601 digital frequency display (fits all Yaesu 101 and 401 series TRCVs) £75 (perfect condition). Maurice (G6IMV), 18 Mossvale Grove, Washwood Heath, Birmingham, B8-3QJ.

■ Yaesu FT707 and FC707 ATU. Mike bracket original boxes and manuals, extra bands K-tone fitted all mint cond £450 the lot. Pete Stevenson, 6 Netherhouse Place, Commanhead, Glasgow, G34-0DT Tel: 041-771-7611

■ Zenith R7000 £350 mint, exchange 35mm Nikon camera, video recorder, WHY. C Haynes, 13 Lionel Road, Eltham, London SE9 6DQ. Tel: 01-850-1543

■ Swop Stereo, cost £750 for transceiver. sorry no cash, on the dole. Just taken licence. Also radio controlled model aircraft cost £200 WHY. Full details. Tel: 051 489 2668

■ Eddystone 830/X R3 £30. Audioline 341 FM/CB £25. Rama ext SP £5. RD6 resistance box 152 to 1MHz £15 ono. 2x, 6µF, 500V capacitors £1.00 pair. 1400µf, 400V capacitor 50p. 1800 µF, 250V both BX Daly. 1-3500µf, 30Vdc capacitor 20p. Dual O/P 16µf, 350v capacitor. Also 6x Newmarket 404 transistors 10p ea. Pye radio telephone POA and various other bits + pieces POA. Bob Jones. Tel: 0685 74061

■ Colour printer/X-Y plotter, Type CGP-115, four-colour pen mechanism, selectable 40/80 character width printing, relative and absolute graphic modes, extras, £110 onvo. Tel: Mike GM4UKG, QTHR, Inverkeithing (0383) 416688.

■ Trio R600, mint condition, four months old, receiver used very little £230 ono. Global at 1000 ATU, good condition £20. T Corbett, Sunnyside, New Road, Coedpoeth, Wrexham, Clwyd, North Wales. Tel: Wrexham 757435 (after 6pm).

■ Scopex 14D-10 double trace CRO. Bandwidth 10 MHz. Absolutely as new condition. Cost £289, accept £150. Complete with manual and muff. Tel: Reading 883799

■ IC2E, Spkr Mic, BP4 battery case +6 Nicads, DC1, 12V adaptor, mobile charging lead, cases, all standard accessories £140. 20W PA, suits 2E, £20. Rx converter, 2m input, 10m output, £10. Wanted, FT290. Dan Glover (G6RMA QTHR). Tel: (0322) 524938 (evenings only)

■ SWL report forms designed for maximum information about your listening post. Give real meaning to your DX reports. Derek Rout, 3/137 Champion St, Christchurch, New Zealand.

■ Pye Tx/Rx 1.6/3.9 KHz, 50W, spares, manual. As new, offers. BC221 freq meter, charts, PSU vgc £40. Dane test oscillator 0.1 10000Hz, dual quad output, vgc £40. Serviscope with new spare valves £40. Airmec VTVM, Type 219, vgc £35. Marconi VTVM, TF899, vgc £20. Metrix MX202B, VOM, vgc £45. Racal SSB adaptor RA218 less crystals, as new, offers. Valves QV08/100, QF41, 723A/B, KT66, 11E3, QU37, 3C45, 5R4GY, 6CH6, CRTs DG-18-14A, RMT59. Shack clearance. Tel: 0502 715419

■ Complete 80M through 70cms station. TS130V transceiver, MMT144/28, MMT432/28, VFO120, DFC230, YK885N, RF switching module and all interconnecting cables. Demonstration available. Prefer not to split. £710 onvo. Carriage at cost or local delivery. Phone or write to Graeme G6CSY QTHR at Orpington (0689) 29230 evenings.

■ 2m FM amplifier by Catronics Ltd, 11.5W in, 40W out plus spare new 11.5 in 40 out transistor and circuit etc £25. Hardly been used. 2m speech processor with internal 9V battery, also multi plug

to fit Yaesu transmitter, as new £15. Tel: Nelson 68548

■ Realistic 5 band DX200 receiver £75 ono. A Parr, 3 Groes Lwyd, Abergele Clwyd. Tel: 0745/822176

■ Ex EMI research lab's parabolic four foot dish with tripod mount. Part motorised low windage sited in Hampshire £125. Buyer collects phone Looe (05036) 4339 G8MRB

■ Realistic DX160 Comm Receiver 50KHz to 30MHz coverage in 5 bands. Separate speaker, amateur and broadcast bands. Mains or 12Vdc operation. Little used. A1 condition. Boxed £50.00 ono. 10M to 2M receive converter to listen to 2M amateur band. £10.00. C Walker G4XSE Tel: Bishop's Waltham (Hants) 3511

■ Armstrong AF208 chassis with full data and speaker. Radiomobile car radio model 1085XT with speaker. Also Bush radio type AC11. Long medium short waves. Needs dial panel. All in good working order. Offers please or exchange for small short wave radio, such as Mohican GC-14, Codar T28, or any similar type. WHY. Arthur Hyde, 54 The Causeway, Pagham, Bognor Regis, Sussex PO21 4PG. Tel: Pagham 3256

■ Pye Cambridge 5W VHF mobile transceiver. Easily modified to 2 metres £15. Carriage extra. 'Artificial Satellite Observink' by H Miles. The best book available for information on orbital predictions, telemetry, radio tracking and visual observation of satellites. Brand new, £5.50. K H Law, 11 Springhill Road, Saffron-Walden, Essex CB11 4AH. Tel: 0799 21388

■ Yaesu FRG 7700, good condition, bargain at only £210. Tel: Yeovil 29313 (evenings)

■ Yaesu FT480R as new condition, boxed with manual etc £260 ono. Nakamichi cassette deck model 350 boxed as new £60 ono. Rank, Bush, Murphy, colour monitors, Ex-BBC, working £50 each or all ten for £450. Tel: Guildford 0483-571134 (evening-weekends)

■ Labgear LG300 CW transmitter, covers amateur bands. Also Woden UM2 power supply and modulator. Neither in working order but could be made workable. Ideal for valve enthusiast, circuit diagrams also available. £70 the lot. Buyer must collect. A Mackay, 20 Broom Covert Rd, Swinfen Hall, Lichfield, Staffs. Tel: Shenstone 480909 (after 6.30pm)

■ Code Master CW/RTTY Decoder + Morse tutor, CWR 610E £120.00 (G4UVJ). Tel: Canvey Island 697978 (QTHR).

■ Help yourself to a pass in the RAE. Where ever you live the Dover YMCA Radio Club help you. Write now for information to RAEC, Dover YMCA, 2 Leyborne Road, Dover CT161SN. Our oldest student passed the RAE and CW at age of 87 years. Don't wait that long. P J Pennington, 146 Elms Vole Road, Dover, Kent. Tel: 0304 20300

■ Oric 48K plus Oric chess and other software £95 (or swop for Spectrum 48K). Heathkit RAI amateur bands receiver £45 ono. Tel: Loughborough 268136 (after 7pm).

■ Shack clear out. Grommets mixed sizes 100+ £1.00 bag. Washers, non-metallic, with 1/8in and 1/4in holes different sizes rubber/fibre/insulation 2,000 £7.00. Three tone buzzers, will work on 9V to 12V fixed to PCB, 3in x 1/4in, beautifully made, box of 40 £2 each. Pots all 22K Lin small size, 10 for £1. Packs res/cap/trans/100+ £2.50. Polypropylene tube light, strong, 200lb breaking strain, 100 yard rolls £1. Fuzz boxes £9. D Martin, 29 St Johns Close, Leatherhead, Surrey.

■ Cossor 1035 'Scope good condition with manual £15. Mono DX-TV chassis audio video in/out £10, Pye, Bush, EMO, Philips CTV spares/panels, Philips/Pye portable TV. Chassis all cheap to clear or exchange - what have you? Mains transformers HT & LT. Also to clear. Mr A Bouskell, 129 Lyminster Road, Sheffield, S Yorks S6 1HY. Tel: (0742) 311191

■ Hameg scope HM203-4 as new £250. Realistic scanner 2003 60 channel. Unused £190. Realistic speaker £5. Revco discone aerial unused boxed £30. Home built bench power supply 0-30V 2amp £25. Workshop clearance, wire small drill, bits and peices etc £15. All collect or plus carr. Edwards, 2 Beach Road, Burton, Bradstock, Bridport, Dorset DT6 4RF. Tel: 0308 897625

■ For sale. DX200 communications receiver, vgc. 1.8-30MHz + long wire antenna and full instructions. Good for SWL beginner £68 ono. Philips black and white portable television, excellent 20in screen vgc £68 ono. Hitachi radio portable FM/MW/LW, very smart, £13 + case + earphone. Nice present. Laurence Mendes, The White House, Chapel Lane, Mickleton, GL55 6SD. Tel: 038 677 727/798.

■ Creed 75 page printer with stand, paper winder, 6S tape reader, Creed 80-0-80 power supply, lots of paper rolls & tape, all in wkg condition. Buyer collects £25.00 the lot. Ring after 7pm week days. Tel: Mike (G8ATK) 0252 715765.

■ Computer printer for sale. TTL level input. Uses ordinary 8 1/2in wide paper. C/W power unit, built-in interface, software (tape and printout). Modified Creed 7B. Can be seen working on my Acorn Atom. £50 buyer collects. Also four 2708 EPROMS, offers? Or will exchange for a 2716 or 2532. N J Tubbs, 35 Burns Road, Pound Hill, Crawley, Sussex. RH10 3AT. Tel: Crawley 513354 (evenings).

■ Closed circuit TV camera with b/w monitor for sale. Two sets available each with 6 1/2metres cable, £65 per set. Stereo reel-to-reel recorder (Cossor), 2 speed, track transfer, etc. Complete with stereo microphone, £40. Microphone mixer £5. Fifteen 5in floppy disks (used) £1 each. Three storage boxes for 5in disks £1.50 each. Buyer collects large items or pays carriage extra to price asked. All items must go!! Dennis Lyons. Tel: Shipton-under-Wychwood (0993) 830248 or Nuneaton (0203) 385614 (answer service).

■ Yaesu FT290R. MuTek, carry case, rubber duck and 25W linear, all mint. £250 ono. Yaesu 70cm FT790R and FL7010 linear brand new, used 5hrs only, £270 ono. All equipment only used in shack. J Beam 12XY 70cm new, in box £20. Advance 10A, 13V power supply £20. Phone 0728 2952. House move forces reluctant sale.

■ Realistic PRO2001 scanning receiver 16560 freqs. Complete with discone antenna and VHF/UHF portable antennae. £90.00 ono. Also Realistic DX200 comms. Receiver £65.00 ono. Both in mint condition complete with handbooks and original packing. Also Lowe TX40 CB TX/RX complete with SWR meter, matcher and AR2 antenna. £30.00. Tel: 0302 841530.

■ National NC81C Ham bands receiver, metal tubes, rare 1937 USA Rx, working, £75. QST's 1926 to 1948, approx 150, offers. All following new, boxed, CDE BT1A rotator, £85. AR30 £40. Mirage B108 linear, 144MHz 80Watts + remote relay £85. Mics, Yaesu YD148 desk dual Z, £15. Sure 401A, HI-Z, £10. Trio MC35S, HI-Z, £10. Mobile mounts, TS130, FT707, £10 each. Kenpro bearing KS-065, £15. FT707 linear relay, £15. FF501DX filter, £12. AEC SWR50A SWR/Watt £11. Phone: 0202 510400.

■ Sony CRF-320 HF + general coverage receiver sell £325, or swap 2 metre multimode. Tel: (Glasgow) 041-551-9117 evenings.

■ Sony IFC 7600D radio. New May 1984. Controls rather small for my fingers. Cost £170 asking £140. Tel: Worthing 49978.

■ SX200N scanning Rx with PSU VGC £190 ono. KW2000A complete with PSU - LS good condition with shure 444 mike £180 ono. Approx 230 Rx and Tx valves mostly new, offers. Twin meter SWR, new £10. Letters only please. Buyer collects or carriage extra. D Bemister 69 Woodfield Drive, Gidea Park, Romford, Essex.

NEW IMPROVED

Radio & Electronics

The communications, electronics & computers magazine **World**

SMALL ADS

Complete, full-size sets, any published service sheets £2 + large SAE — except CTV's/Music Centres from £3 + large SAE. Manuals from 1930 to latest. Quotations, free 50p magazine, price lists, unique technical publications, for large SAE. Repair data/circls almost any named TV/CVR, £9.50 by return.

TISREW

76 Church Street, Larkhall, Lanarkshire ML9 1HE
Phone: 0698 883334

CHESHIRE

DW ELECTRONICS G3 XCF

Amateur Radio Supplies
71 Victoria Rd, Widnes
Tel: 051-420 2559
Open Mon-Sat 9.30-6 (closed Thurs) Sun 9.30-12
We supply Yaesu, ICOM, Tonna, Jaybeam, Microwave Modules, Datongs etc

KENT

AMTRONICS (TONBRIDGE) G4 SYZ

THE AMATEUR RADIO SPECIALISTS IN KENT

IT'S AMATEUR RADIO from AMTRONICS
8 Tollgate Buildings
Hadlow Road, Tonbridge, Kent
Tel: (0732) 361850
FDK, AZDEN, YAESU, JAYBEAM, FORTOP, DATONG, etc.

Thanet Electronics



95 Mortimer St, Herne Bay

Tel: 02273-69464

Open: Mon, Tues, Wed 9-5
Thurs 9-1, Fri, Sat 9-5.30

All mail order & service enquiries to head office, 143 Reculver Rd, Tel: 02273-63859

LONDON

BONEX LTD

RF component specialists Toko coil & Inductors

102 Churchfield Road

London W3 6DH

Tel: 01 992 7748

NORFOLK

Eastern Communications



31 Cattle Market Street

NORWICH

(0603) 667189

MON-FRI 9.30-5.30
SAT 9.30-5.00

MAIL ORDER



ACCESS BARCLAYCARD

COUNTY GUIDES

FROM ONLY £13.16 PER MONTH

Take advantage of this simple, economical and rewarding method of advertising by filling in the form below.

Agents Wanted To Sell Computer Software for most Computers. We now have the Dialog Electronics Part 1 in stock. Also have in stock Pools Winner and Coursewinner. We can supply Business software, games and Computer ad on's. **Phone (0288) 4179** up to 9pm most nights for your free list and details about our agents.

BILLINGTON VALVES

Send 35p for our July 84 catalogue, including a huge range of top quality, valves and bases, or SAE for quotation. We purchase valves, any quantity, vintage on modern, very high prices paid for PX25, DA30 valves.

Billington Valves, Irwin Drive, Horsham RH12 1NL
(Mail order only)

BCNU AT THE SUSSEX MOBILE RALLY

10.30 to 5.00pm on SUNDAY 15th JULY 1984. Brighton Raceground, Racehill, BRIGHTON. It's the winner for Radio Amateurs! Free car parking and many attractions for the whole family. Usual trade stands. All under cover.

RTTY SOFTWARE

CBM64, VIC20, ATOM, DRAGON 32/64, TANDY COLOR COMPUTER
Advanced machine code programs with split-screen type-ahead operation, any baud rate, saveable memories etc.

AMTOR

Superb full-feature system for Dragon 32/64 at one third the cost of current alternatives.

MORSE DECODER & SENDER

MORSE TUTOR: BASICODE KIT

Available for Dragon 32/64. Large SAE for software/hardware details.

Grosvenor Software (REW)

22 Grosvenor Road, Seaford, Sussex
Tel: (0323) 893378

Radio & Electronics World

You can be assured that readers know where they can go in your area to purchase

COUNTY GUIDE

RATES

BOXES ad sizes

20mm x 59mm single
40mm x 59mm double

Total prepayment rates	Ad space	3 issues	6 issues	12 issues
	single	£47.00	£88.00	£158.00
	double	£94.00	£176.00	£316.00

RADIO & ELECTRONICS WORLD COUNTY GUIDE ORDER FORM

TO: Radio & Electronics World · Sovereign House · Brentwood · Essex
CM14 4SE · England · (0277) 219876

print your copy here

NUMBER OF INSERTIONS REQUIRED

Single County Guide 3 £47.00... 6 £88.00... 12 £158.00...
Double County Guide 3 £94.00... 6 £176.00... 12 £316.00...

PAYMENT ENCLOSED

£ —

Cheques should be made payable to Radio and Electronics World. Overseas payments by International Money Order

Conditions — Payment must be sent with order form. No copy changes allowed. Ads accepted subject to our standard conditions, available on request.

Registered No 2307667 (England)

C P I

CATALOGUE OF ALLSORTS
 Electronic, telephones, new BT sockets, burglar alarm equipment etc
 Send 40p and SAE to:
CABELEC
 14 Tillman Close, Greenleys,
 Milton Keynes MK12 6AQ. Dept REW.

THE VINTAGE WIRELESS COMPANY
 1914 - 1960
 Radios, amplifiers, service sheets, valves, vintage components, books new & used, repairs & restorations, mail order only.
Tudor House
 Cosham Street, Mangotsfield,
 Bristol BS17 3EN
 0272-565472

RADIO CANADA
 Peking, Australia, voice of America. A Vega 206 (6x SW/MW/LW). Pulls these and dozens more. £23.45. Year's guarantee. Return dispatch.
CORRIGAN RADIOWATCH,
 Building 109, Prestwick Airport KA9 2RT

Turn your surplus IC's Transistors etc into CASH. Immediate settlement. We also welcome the opportunity to quote for complete factory clearance.
 Contact:
Coles, Harding & Co, 103 South Brink
Wisbech, Cambs. Tel: 0945 584188

RTTY
THE EXPANDING MODE
 Build your own terminal unit to interface your micro to a receiver or transceiver.
 PL1 PLLT.U. . . . Kit..... £13.50
 built module..... £18.50
 FP1 Power supply & pre-filter Kit £11.25
 built module..... £14.65
 Software also available - please enquire
 For full catalogue send s.a.s.e. to
 Please add VAT to all prices
PNP Communications (REW)
 62, Lawes Avenue, Newhaven
 East Sussex BN9 95B
 Telephone (0273) 514465

RESISTOR PACKS FOR ALL PROJECTS
 1/4watt carbon film resistors 5% 1 ohm to 10M E24 series. Packs of 10 each value (1690 resistors) **£10.00** Your choice of quantities/values 125 for **£1.00**. VAT and Post Free.
GORDON HALLETT
 20 Bull Lane, Malden Newton,
 Dorchester, Dorset DT2 0BQ.

EUROLEC VIDEO SERVICES
 01-669 2611 Telex 893819 Eurolec G
Address for correspondence only:
 35 Sandy Lane South,
 Wallington, Surrey SM6 9RF
 We have a quantity of Phillips VCR cassettes, both new and ex-library. Please write or phone for details
 NTSC/PAL Transfers. Please write or phone for details

J A CREW & CO
SPINNEY LANE, ASPLEY GUISE,
MILTON KEYNES
Tel: (0908) 583252
(Mail order only)
 1000 resistors 1/4 1/2 watt £2.50; 100+ capacitors 95p. 50 electrolytics 95p; LED's red 50p/6, yellow/green 50p/4; 50 assorted branded transistors £1.95; 50+ diodes, SCR's & bridge rectifiers £1.60; BC108 £8/100, panel neons £2.50/10; TIP 50 £1.20/4; BY164 bridge 1.4A 25p; Opto-isolators 60p/5; Mains filter 5A (List £6+) £2.85; 40 pin low profile DIL sockets 50p/2; 6 volt BI-PIN bulbs 50p/10; 12 volt low profile relays SPCO 5 A rating £1.25. Add £1 p&p to all orders under £12. 44 page catalogue packed with thousands of other bargains, mechanical and electronic, price 50p.

4 PLASTIC BOXES £2
 1. Thick black, four screw top, size 90mm by 70mm deep 26mm.
 2. Thick black four screw top, size 150mm by 84mm, deep 43mm.
 3. Thin white flick on top, size 81mm by 64mm, deep 26mm.
 4. Thin semi-clear white top, size 81mm by 64mm, deep 64mm.
 ONE OF EACH TYPE (sample) **£2.00** plus P&P 30p.
ELECTRONIC MAIL ORDER
 62 Bridge Street, Ramsbottom, Lancs. BLO 9AG.
 Tel: (070 682) 3036. - ACCESS/VISA

R & S Radio (G4OWY)
 Amateur radio equipment bought, sold and exchanged. List of available items sent on request.
Telephone anytime on 0305-786930

ALPHA KEYS
 Precision engineered keys for the connoisseur. Twin or Single paddle. One of the lightest and smoothest movements ever.
CAVITY WAVEMETERS
 For the UHF/VHF operator, one wavemeter to cover 144 mhz to over 2500 mhz. Can measure rf as low as 50 mill watts with suitable meter.
COAXIAL RELAY KITS
 The cavity block is pre-machined to take either BNC or N type sockets. Two types of cavity available. Alum. type for HF, Brass for the higher frequency.
 Send large SAE for more information to:
PAUL SERGENT, G4ONF
 6 Gurney Close, Costessey, Norwich NR5 0HB
 Tel: (0603) 747782

Ant Products
All Saints Industrial Est
Baghill Lane, Pontefract West Yorkshire
Telephone (0977) 700949
TIGER LY9 70 Cms Antenna
 New from Ant Products, a superb addition to the range of renowned antenna, the Tiger LY9 for 70 cms. A light weight antenna with a heavy weight signal. Offering a high 11db gain on a 58 inch boom length. Great for vertical or horizontal mounting. Supplied in matched pairs for the ultimate Oscar station complete with all hardware for mounting with elevation control. Precisely adjustable for angle in order to get the best performance. Also including matching unit for circular polarisation. Right or left hand can be chosen with equal efficiency. Last but not least our famous two year guarantee and full back up service.
Write now for full details enclosing a SAE plus 25p in stamps

This space could be yours for as little as **£23.25** per month. Call the advertising department now on 0277 219876, or complete the coupon opposite.

Radio & Electronics World
 The communications, electronics & computers magazine

SMALL ADS

This method of advertising is available in multiples of a single column centimetres — (minimum 2cms). Copy can be changed every month.

RATES
 per single column centimetre:
 1 insertion £9.65, 3 — £9.15, 6 — £8.65, 12 — £7.75.

RADIO & ELECTRONICS WORLD SMALL AD ORDER FORM

TO: Radio & Electronics World · Sovereign House
Brentwood · Essex CM14 4SE · England · (0277) 219876

PLEASE RESERVE.....centimetres by.....columns

FOR A PERIOD OF 1 issue..... 3 issues..... 6 issues..... 12 issues.....

COPY enclosed..... to follow.....

PAYMENT ENCLOSED:..... £ — Cheques should be made payable to Radio & Electronics World Overseas payments by International Money Order

CHARGE TO MY ACCOUNT.....

COMPANY

ADDRESS

SIGNATURE **TELEPHONE**.....

C P I

ADVERTISERS INDEX

AKD.....30	Data Publications.....50	CM Howes Communications.....57	Reltech Instruments.....57
Akhter Instruments.....54	Display Electronics.....33		Reg Ward & Co.....65
Amateur Radio Exchange.....14, 15		Keytronics.....85	
Avcomm Ltd.....50	East Cornwall Components.....26		Scarab Systems.....42
	Edwardschild Ltd.....57	Marco Trading.....Inside Front Cover	South Midlands Communications.....76, 77
Bi-Pak.....69	AM Electronics.....84	McLelland Electronics Ltd.....59	C R Supply Co.....35
Black Star Ltd.....42	L J Electronics.....42	Microwave Modules.....Outside Back Cover	Tau Systems.....59
Bredhurst Electronics.....50	SAT Electronics.....84	Mutek Ltd.....Inside Back Cover	Thanet Electronics.....22, 23
Brian Reed.....38	Enfield Electronics.....12		
	Garex Electronics.....38	Number One Systems.....50	Velleman (UK) Ltd.....42
C-Scope International.....38	Grandata Ltd.....29		Ward Electronics.....72
Cirkit.....6, 7	Hart Electronics.....80	PM Components Ltd.....46, 47	Waters & Stanton.....18
Commutech (Devon) Ltd.....15	Hemmings Electronics Ltd.....72	Rapid Results College.....84	R Withers Communications.....10
Cricklewood Electronics.....63			Wood & Douglas.....35



ADVERTISING RATES & INFORMATION

ABC membership approved pending first audit Jan-Dec 1984

DISPLAY AD RATES		series rates for consecutive insertions			
depth mm x width mm	ad space	1 issue	3 issues	6 issues	12 issues
61 x 90	1/8 page	£91.00	£86.00	£82.00	£73.00
128 x 90 or 61 x 186	1/4 page	£160.00	£150.00	£145.00	£125.00
128 x 186 or 263 x 90	1/2 page	£305.00	£290.00	£275.00	£245.00
263 x 186	1 page	£590.00	£560.00	£530.00	£475.00
263 x 394	double page	£1140.00	£1070.00	£1020.00	£910.00

COLOUR AD RATES		colour rates exclude cost of separations	series rates for consecutive insertions			
depth mm x width mm	ad space	1 issue	3 issues	6 issues	12 issues	
128 x 186 or 263 x 90	1/2 page	£420.00	£395.00	£375.00	£335.00	
297 x 210	1 page	£810.00	£760.00	£730.00	£650.00	

SPECIAL POSITIONS	
Covers: Bleed: Facing Matter:	Outside back cover 20% extra, inside covers 10% extra 10% extra [Bleed area = 307 x 220] 15% extra

DEADLINES		*Dates affected by public holidays			
issue	colour & mono proof ad	mono no proof and small ad	mono artwork	on sale thurs	
Sept 84.....	12 Jul 84.....	18 Jul 84.....	20 Jul 83.....	9 Aug 84.....	
Oct 84.....	15 Aug 84*.....	21 Aug 84*.....	23 Aug 84*.....	13 Sept 84.....	
Nov 84.....	13 Sep 84.....	19 Sep 84.....	21 Sep 84.....	11 Oct 84.....	
Dec 84.....	11 Oct 84.....	17 Oct 84.....	19 Oct 84.....	8 Nov 84.....	

CONDITIONS & INFORMATION			
<p>SERIES RATES Series rates also apply when larger or additional space to that initially booked is taken. An ad of at least the minimum space must appear in consecutive issues to qualify for series rates. Previous copy will automatically be repeated if no further copy is received. A 'hold ad' is acceptable for maintaining your series rate contract. This will automatically be inserted if no further copy is received. Display Ad and Small Ad series rate contracts are not interchangeable.</p>	<p>If series rate contract is cancelled, the advertiser will be liable to pay the unearned series discount already taken.</p> <p>COPY Except for County Guides copy may be changed monthly. No additional charges for typesetting or illustrations (except for colour separations). For illustrations just send photograph or artwork. Colour Ad rates do not include the cost of separations.</p>	<p>Printed — web-offset.</p> <p>PAYMENT All single insertion ads are accepted on a pre-payment basis only, unless an account is held. Accounts will be opened for series rate advertisers subject to satisfactory credit references. Accounts are strictly net and must be settled by publication date.</p> <p>FOR FURTHER INFORMATION CONTACT Radio & Electronics World, Sovereign House, Brentwood, Essex CM14 4SE. (0277) 219876</p>	<p>Overseas payments by International Money Order. Commission to approved advertising agencies is 10%.</p> <p>CONDITIONS 10% discount if advertising in both Radio & Electronics World and Amateur Radio. A voucher copy will be sent to Display and Colour advertisers only. Ads accepted subject to our standard conditions, available on request.</p>

£600 + for the receiver performance of a £250 portable? There's a better way!

Fitting a preamplifier to Icom's IC 271 will degrade the dynamic performance of the transceiver to a level very similar to that offered by a FT290 fitted with our SLNA 145sb! Fitting our RPCB 271ub replacement front-end on the other hand will give you the same sensitivity (to within a small fraction of a dB) as the IC 271/Icom AG20 preamp combination, but with about 20dB better spurious-free dynamic range! The superiority of our approach will be best seen during contests and openings, where with our board you'll be able much more easily to hear the weak dx amongst the strong locals (assuming they have clean signals in the first place!), instead of a bandful of unpleasant noise! It does seem pointless to waste the excellent potential performance of this transceiver by fitting a preamp when there's a better way of going about it.


Incidentally, we did have a few teething problems with the interfacing of the RPCB 271ub to the IC 271. R+ was getting into Icom's mic preamp IC producing rather unpleasant ssb audio on transmit. This has now been cured, and of course where our customers have had problems we've been happy to put them right. We do care!

Stephen G4 SJP

P.S.

Our new TVHF 230c 2m to all 9 amateur hf bands transverter should be available in limited quantities at first by the time this appears in print. See it (and us) at the major rallies, or give a ring for more info.

RPCB 271ub
£89.90 + 1.50 inc. vat.

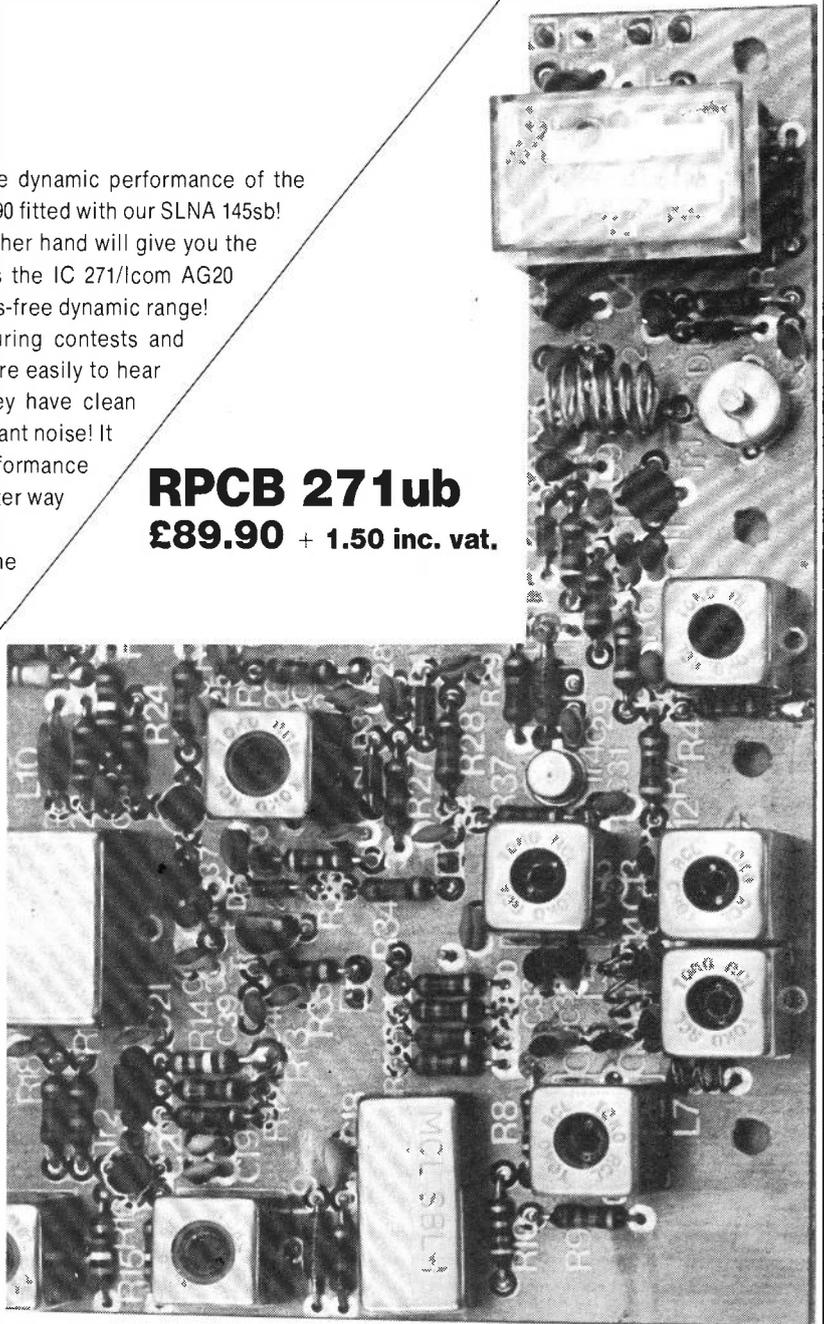

muTek limited — the rf technology company

Dept RW, Bradworthy, Holsworthy, Devon EX22 7TU (040924) 543






MICROWAVE MODULES LTD

NEW!

MML 144/200-S: 144 MHz 200 WATT LINEAR AMPLIFIER

NEW!

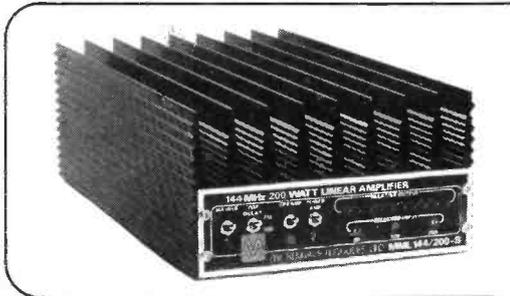

FEATURES

- * 200 watts Output Power
- * Linear All Mode Operation
- * Suitable for 3, 10 & 25 watt Transceivers
- * Ultra Low-Noise Receive Preamp — Front Panel Selectable
- * Relative Output LED Bar Display
- * Equipped with RF Vox & Manual Override
- * LED Status Lights for Power, Transmit, Preamp on and input level

£245 inc VAT (p&p £4.50)

144 MHz HIGH PERFORMANCE RECEIVE CONVERTER: MMC 144/28 HP

NEW!



FEATURES

- * Excellent strong signal handling characteristics
- * Gasfet RF amplifier
- * High level double-balanced mixer
- * Harmonic-free, regulated oscillator

Input frequency range: 144-146 MHz
Output frequency range: 28-30 MHz
Typical gain: 20 dB minimum
Noise figure: 2 dB
3rd order intercept point: + 19 dBm (output)

Image rejection: 60 dB
Input/output impedance: 50 ohm
Power requirements: 13.8V at 75mA
Power connector: 5 pin DIN socket
RF connectors: SO239 or BNC, please specify

Size: 110 x 60 x 31 mm (4 3/8 x 2 3/8 x 1 1/4")

£42.90 inc VAT (p&p £1.25)

1296 MHz GaASFET PREAMPLIFIER — MMG1296

NEW!

This GaASFET 1296 MHz preamplifier is constructed on high-quality Teflon glass-fibre pcb and includes a microstripline filter which provides excellent rejection to mixer image frequencies and out of band signals. It has a power gain of 15dB and a noise figure of 1.2dB. The power requirements are 13.8V at 35mA and the unit is fitted with 50 ohm BNC sockets.



£59.95 inc VAT (p + p £1.25)

MMC50/28S — 6M CONVERTER

This new Converter has switched oscillators to provide coverage of 50-54 MHz on a 28-30 MHz receiver. The design utilises MOSFETS in the RF amplifier and mixer stages, and the local oscillator is regulator controlled.

INPUT RANGES: 50-52 MHz **OUTPUT RANGE:** 28-30 MHz
 52-54 MHz
OVERALL GAIN: 30dB **NOISE FIGURE:** 2.5dB

£34.90 inc VAT (p + p £1.25)

NEW!

OUR ENTIRE RANGE OF PRODUCTS WILL BE EXHIBITED AND ON SALE AT MOST OF THE 1984 MOBILE RALLIES BY OUR OWN SALES TEAM, COME AND TAKE A CLOSER LOOK

ALL MICROWAVE MODULES PRODUCTS ARE FULLY GUARANTEED FOR 12 MONTHS (INCLUDING PA TRANSISTORS)



WELCOME

MICROWAVE MODULES(REW)

BROOKFIELD DRIVE, AINTREE, LIVERPOOL L9 7AN, ENGLAND

Telephone: 051-523 4011 Telex: 628608 MICRO G

CALLERS ARE WELCOME, PLEASE TELEPHONE FIRST

HOURS:
MONDAY-FRIDAY
 9-12.30, 1-5.00
 E. & O.E.