

RADIO & ELECTRONICS CONSTRUCTOR

DECEMBER 1979
Volume 33 No. 4

Published Monthly
(3rd of preceding Month)

First Published 1947

Incorporating The Radio Amateur

Editorial and Advertising Offices
57 MAIDA VALE LONDON W9 1SN

Telephone 01-286 6141 Telegrams Databux, London

© Data Publications Ltd., 1979. Contents may only be reproduced after obtaining prior permission from the Editor. Short abstracts or references are allowable provided acknowledgement of source is given.

Annual Subscription: £7.50, Eire and Overseas £8.50 (U.S.A. and Canada \$20.00) including postage. Remittances should be made payable to "Data Publications Ltd". Overseas readers, please pay by cheque or International Money Order.

Technical Queries. We regret that we are unable to answer queries other than those arising from articles appearing in this magazine nor can we advise on modifications to equipment described. We regret that queries cannot be answered over the telephone, they must be submitted in writing and accompanied by a stamped addressed envelope for reply.

Correspondence should be addressed to the Editor, Advertising Manager, Subscription Manager or the Publishers as appropriate.

Opinions expressed by contributors are not necessarily those of the Editor or proprietors.

Production— Web Offset.

CMOS OSCILLATORS — Using CMOS logic gates as pulse generators — by R. J. Caborn 206

RECENT PUBLICATIONS 209

NEWS AND COMMENT 210

AMPLIFIER CLIPPING MONITOR — Suggested Circuit — by G. A. French 212

THE OSCAR PHASE III — A Progress Report by Arthur C. Gee 215

S.W. AERIAL TUNING UNIT — by R. A. Penfold 216

SHORT WAVE NEWS — For DX Listeners — by Frank A. Baldwin 220

DIGITAL TANTALISER — by I. M. Attrill 222

ADDRESSING MEMORY — Databus Series No. 5 by Ian Sinclair 228

IN NEXT MONTH'S ISSUE 231

LONG TIME LOW C — by E. A. Parr 232

BREADBOARD '79 — A Preview 235

VMOS POWER DEVICES — Part 1 by John Baker 238

BOOK REVIEW 240

RADIO TOPICS — by Recorder 241

READER'S HINTS & TIPS — In your Workshop 243

REGENERATION
Electronics Data No. 52 iii

Published in Great Britain by the Proprietors and Publishers, Data Publications Ltd, 57 Maida Vale, London W9 1SN.

The *Radio & Electronics Constructor* is printed by Swale Press Ltd.

THE JANUARY ISSUE
WILL BE PUBLISHED
ON 5th DECEMBER

MAPLIN

ELECTRONIC SUPPLIES




PRINTED CIRCUIT DRILLS

Miniature 12V DC drills designed for drilling pcb's. Small drill: Order as BW03D Price £8.75 Large drill: Order as BW02C Price £10.63



ANTI-STATIC MAT & GUN

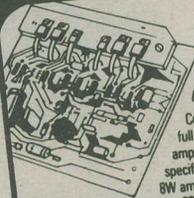Turntable mat removes static from discs while they are playing. Order as LX10L Price £2.95 Gun removes static charge from discs. After use dust no longer clings and may be easily brushed off. Order as LX04E Price £4.99



AMP KITS

Complete kits of parts with full instructions to make hi-fi amplifiers with excellent specifications. 8W amp kit: Order as LW36P Price £3.83 50W amp kit: Order as LW35Q Price £13.73 150W amp kit: Order as LW32K Price £14.89



HEADPHONES

High quality stereo headphone with large padded headband and slider volume controls. Order as WF14Q Price £7.99



CONDUCTIVE PAINT

Repair pcb's, car demisters, etc., with this silver paint. Phial contains 3gm. Order as FY72P Price £2.69



MCKENZIE POWER SPEAKERS

High quality, high power speakers. 12in. 50W 8Ω Order as XQ79L Price £18.79 12in. 50W 16Ω Order as XQ80B Price £18.79 12in. 80W 8Ω Order as XQ81C Price £26.92 12in. 80W 16Ω Order as XQ82D Price £26.92 15in. 150W 8Ω Order as XQ83E Price £57.80 15in. 150W 16Ω Order as XQ84F Price £57.80



MINIATURE VICE

Small modellers vice in tough plastic with metal faced jaws. Clamps to bench. Jaws width 41mm, maximum opening 30mm. Order as FY53H Price £2.78



20,000 OHM/VOLT MULTIMETER

A 20,000 ohms per volt multimeter at an incredibly low price. DC volts 5, 25, 125, 500, 2,500; AC volts 10, 50, 250, 1,000; DC amps 0 to 0.05mA, 0 to 250mA; Resistance 0 to 50k, 0 to 5M ohms; Decibels -20 to +22dB. Complete with test leads, battery and instruction leaflet. Order as YB83E Price £13.70



ELECTRET MICROPHONES

Super quality genuine electret microphones operating on 1.5V battery (HP7-type) supplied. Cassette type with miniature jack plug. Order as YB33L Price £3.84 Omnidirectional low-cost with standard jack plug. Order as YB34M Price £3.75 Unidirectional 600Ω with standard jack plug. Order as YB35Q Price £9.75 Unidirectional 600Ω/50kΩ dual with standard jack plug (pictured). Order as WF34M Price £16.77



WIRING TOOLS

Miniature box-jointed wiring pliers with insulated handles and return spring. Order as BR68A Price £4.52 Miniature box-jointed side-cutters with insulated handles, return spring and precision cutting edges. Order as BR70M Price £4.45 End-action wire strippers, fully adjustable, insulated handles. Order as BR76H Price £5.85



CLOCK MODULE

Module requires only transformer and two push switches to operate 4-digit, 0.7in red LED display. Alarm and radio outputs. Battery back-up when mains fail. Sleep and snooze timer. Seconds display. Just add speaker for alarm tone. Full details on page 267 of our catalogue. Order as XL14Q Price £8.41



MEGAPHONE

High quality megaphone with differential microphone. Requires eight HP11 batteries (not supplied). Shoulder strap for portable operation. Order as XQ72P Price £47.61




DEMAGNETISER

Tape head demagnetiser with curved probe ideal for cassette tape heads. Cures hiss due to permanently magnetised heads. Amazing low price. Order as FO62S Price £4.15



CAR AERIAL BOOSTER

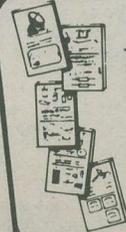High gain car aerial booster for long, medium, short and VHF bands. Negative earth cars only. Very easy to fit - just plugs in plus one wire to +12V. We have measured gains of 20dB at 90MHz! Order as XQ37S Price £5.93



TEACH YOURSELF ELECTRONICS

There is no better way of learning basic electronics than by practical experience and this set of books is undoubtedly the very best basic course for doing just that. Set of five Basic Electronics books. Order as XQ10L Price £7.89

MULTIMETER & TRANSISTOR TESTER

Superb high sensitivity multimeter and transistor tester in one. Sensitivity 100,000 ohms per volt DC. Ranges DC volts 0.5, 2.5, 10, 50, 250, 1,000; AC volts 5, 10, 50, 250, 1,000; DC current 0.01, 0.025, 0.5, 5, 50, 500mA, 10A; AC current 10A; Resistance 5k, 50k, 5M, 50M ohms; Decibels -10dB to +62dB. Complete with test leads, three leads for transistor tester batteries and instruction leaflet. Order as YB87U Price £39.30



TURNTABLES

Autochanger complete with stereo ceramic cartridge and circuit to make a complete low-cost record player ideal for the young pop fan. Order as XQ00A Price £16.30 Single-play rim-drive turntable with stereo ceramic cartridge. Order as XB23A Price £24.79 Single-play belt-drive turntable 'S'-shaped tone arm. Order as XB25C Price £30.63



TRANSISTOR TESTER

Accurate transistor tester measures dynamic gain, identifies unknown transistors, also ideal for matching transistors into pairs. Order as LWF5F Price £12.28



QUICKTEST

A safe and quick way to connect to the mains. Just snap the wires under the sprung keys and close the lid. Completely safe both open and closed. Order as YB21X Price £6.29

All prices include VAT and postage and packing, but if total under £6 please add 30p handling charge. Prices guaranteed until January 11th 1980. Export customers deduct 13% and export postage will be charged extra at cost.

Please use order code. All items in stock at time of going to press.

FOR FULL CATALOGUE DETAILS SEE BACK COVER

MAPLIN

ELECTRONIC SUPPLIES LIMITED

All mail to PO Box 3, Rayleigh, Essex SS6 8LR. Telephone: Southend (0702) 554155 Shop: 284 London Road, Westcliff on Sea, Essex (closed on Monday). Telephone: Southend (0702) 554000

<p>MOTORS 1.5-6VDC Model Motors 22p. Sub. Min. 'Big Inch' 115VAC 3 rpm Motors 32p. 12VDC 5 Pole Model Motors 37p. 8 track 12V Replacement Motors 55p. Cassette Motors 5-8VDC ex. equip. 70p. Geared Mains Motors (240V) 2.5 rpm 75p. 115VAC 4 rpm Geared Motors 95p.</p>	<p>JUMPER TEST LEAD SETS 10 pairs of leads with various coloured croc clips each end (20 clips) 90p per set.</p>	<p>PANEL METERS Ferranti 0-600VAC 3.5" square £2.95. Japanese type 60 x 47 x 33mm clear plastic type; 50 micro, 100 micro, 1Ma, 2 amp, 25 volts, 300 VAC, 'S', 'VU', all £5.25 each. Larger type 110 x 82 x 35mm; 50 micro, 100 micro £6.35 each.</p>	<p>AEROSOL SERVICE AIDS, SERVISOL Switch Cleaner 226gm 60p. Freezer 226gm 70p. Silicone Grease 226gm 70p. Foam Cleanser 370gm 60p. Plastic Seal 145gm 60p. Excel Polish 240gm 47p. Aero Klene 170gm 55p. Aero Duster 200gm 70p.</p>	<p>TOOLS SOLDER SUCKER, plunger type, high suction, teflon nozzle, £4.99 (spare nozzles 69p each). Good Quality snub nosed pliers, insulated handles, 5" £1.45. Antex Model C 15 watt soldering irons, 240VAC £3.95 Antex Model CX 17 watt soldering irons, 240VAC £3.95. Antex Model X25 25 watt soldering irons, 240VAC £3.95. Antex ST3 iron stands, suits all above models £1.65. Antex heat shunts 12p each. Servisol Solder Mop 50p each. Neon Tester Screwdrivers 8" long 43p each. Miyarna IC test clips 16 pin £1.95.</p>
<p>SEMICONDUCTORS C106D 400V 2.5A SCR 20p. 2N5062 100V 800mA SCR 18p. BX504 Opto Isolator 25p. CA3130 95p. TBA800 50p. 741 22p. 741S 35p. 723 35p. NE555 24p. LM3400 40p. AD161/2 70p. 2N3055 38p. ZN414 75p. BD238 28p. BD438 28p. IN4005 10 for 35p. TIL305 alpha numeric displays £2.50. TIL209 Red Leds 8p each. 0.5" 7 segment Led display. Comm. Cathode, green, full spec. 85p each.</p>	<p>TRANSFORMERS All 240VAC Primary (postage per transformer is shown after price). MINIATURE RANGE: 6-0-6V 100mA, 9-0-9V 75mA and 12-0-12V 50mA all 79p each (15p). 0-6V. 280mA £1.20 (20p). 12V 500mA 99p (22p). 12V 2 amp £2.75 (45p). 15-0-15V 3 amp Transformer at £2.85 (54p). 30-0-30V 1 amp £2.85 (54p). 20-0-20V 2 amp £3.65 (54p). 0-12-15-20-24-30V 2 amp £4.75 (54p). 20V 2.5 amp £2.45 (54p).</p>	<p>CAR STEREO SPEAKERS Shelf mounting in black plastic pods with 5" 5 watt speaker available in 4 or 8 ohms only £3.95 per pair.</p>	<p>SURPLUS BOARDS No. 1. this has at least 11 C106 (50V 2.5A) plastic SCR's, one relay a unijunction transistor and tantalum capacitors £1.95. No. 2. I.F. Boards, these are a complete I.F. board assembly made for car radios, 465Khz, full set of I.F.'s and oscillator coils, trimmers etc., 40p each. No. 3 Board with two BDY60 Power Transistors, 45p each.</p>	<p>SWITCHES Sub. miniature toggles; SPST (8 x 5 x 7mm) 52p. DPT (8 x 7 x 7mm) 62p. DPT centre off 12 x 11 x 9mm 77p. PUSH-SWITCHES, 16 x 6mm, red top, push to make 14p each, push to break version (black top) 16p each. G.P.O. Telephone handsets £1.95p. Electrolytic Caps, can type, 2,200mfd and 2,200mfd 50VDC 35p each.</p>
<p>PROJECT BOXES Sturdy ABS black plastic boxes with brass inserts and lid. 75 x 56 x 35mm 54p. 95 x 71 x 35mm 65p. 115 x 95 x 37mm 75p.</p>	<p>TRIAC/XENON PULSE TRANSFORMERS 1:1 (gpo style) 30p. 1:1 plus 1 sub. min. pcb mounting type 60p each.</p>	<p>MURATA MA401 40KHz Transducers. Rec./Sender £3.50 pair.</p>	<p>POWER SUPPLIES SWITCHED TYPE, plugs into 13 amp socket, has 3-4.5-6-7.5 and 9 volt DC out at either 100 or 400mA, switchable £3.45. HC244R STABILISED SUPPLY, 3-6-7.5-9 volts DC out at 400mA max., with on/off switch, polarity reversing switch and voltage selector switch, fully regulated to supply exact voltage from no load to max. current £4.95.</p>	<p>MICRO SWITCHES Standard button operated 28 x 25 x 8mm make or break, new 15p each. Roller operated version of the latter, New 19p each. Light action micro, 3 amp make or break 35 x 20 x 7mm, 12p each. Cherry plunger operated micro, 2 normally open, 2 normally closed, plunger 20mm long (40 x 30 x 18mm) 25p each.</p>
<p>AMP MULTIWAY IN-LINE PLUGS AND SOCKETS, 3 way 35p, 6 way 45p, 12 way 55p, per pair.</p>	<p>MICROPHONES Min. tie pin. Omni, uses deaf aid battery (supplied), £4.95. ECM105 low cost condenser, Omni, 600 ohms, on/off switch, standard jack plug, £2.95. EM507 Condenser, uni, 600 ohms, 30-18KHz., highly polished metal body £7.96p. DYNAMIC stick microphone dual imp., 600 ohms or 20K, 70-17KHz., attractive black metal body £7.75p. EM506 dual impedance condenser microphone 600 ohms or 50K, heavy chromes copper body, £12.95. CASSETTE replacement microphone with 2.5/3.5 plugs £1.35. INSERT Crystal replacement 35X10mm 40p. GRUNDIG electric inserts with FET preamp, 3-6VDC operation £1.00.</p>	<p>ELECTRICAL ITEMS 13 amp 3 pin plugs plastic 27p, rubber 62p. 13 amp rubber extension sockets 42p. 12 way flexible terminal blocks; 2 amp 20p, 5 amp 24p, 10 amp 33p, 15 amp 47p. Standard batten (BC lampholders 27p).</p>	<p>AMPHENOL CONNECTORS (PL259) PLUGS 47p. Chassis sockets 42p. Elbows PL259/SO239 90p. Double in line male connector (2XPL259) 65p. Plug reducers 13p. PL259 Dummy load, 52 ohms 1 watt with indicator bulb 95p.</p>	<p>PUSH BUTTON UNITS 6 way, 3 DPDT, 3 4 pole c/o 55p. 8 way, 5 DPDT, 3 4 pole c/o 70p. RANK ARENA magnetic cartridge pre-amplifier modules, new with connection details £1.95p.</p>
<p>CHANGEOVER REED SWITCH 2 1/2" Long 35p. Glass Mercury Switch 1 1/2" x 3/8", long leads, 35p.</p>	<p>LIGHT DIMMER 240VAC 800 watts max. wall mounting, has built in photo cell for automatic switch on when dark £4.50</p>	<p>PUSH BUTTON TV TUNERS UHF, not varicap, transistorised new £2.25</p>	<p>BUZZERS MINIATURE SOLID STATE BUZZERS, 33 x 17 x 15mm white plastic case, output at three feet 70db (approx), low consumption only 15mA, four voltage types available, 6-9-12 or 24VDC, 80p each. LOUD 12VDC BUZZER, Cream plastic case, 50mm diam. x 30mm high 63p. GPO OPEN TYPE BUZZER, adjustable works 6-12VDC 27p. 12VDC siren, all metal, rotary type, high pitched wail, £7.50.</p>	<p>TAPE HEADS Mono cassette £1.75. Stereo cassette £3.90. Standard 8 track stereo £1.95. BSR MN1330 1/2 track 50p. BSR SRP90 1/4 track £1.95. TD10 tape head assembly - 2 heads both 1/4 track R/P with built in erase, mounted on bracket £1.20.</p>
<p>MULTIMETERS NH55 2,000 o.p.v. IKV AC/DC. 100ma DC current, 2 resistance ranges to 1meg. £5.95. MODEL 72606 20,000 opv 1,000 volts AC/DC., 250ma DC current, resistance 3 ranges to 3meg, dimensions 127 x 90 x 32mm, mirror scale £11.75p. HANSEN AT210 100,000 opv 1.2KV AC/DC., 12 amps AC/DC current, resistance to 200 meg in 4 ranges, capacitance 200pf-0.2mfd, 1,00pf-1mf., decibel range, internal safety fuse, dimensions 160 x 105 x 50mm, an excellent meter, £34.50p.</p>	<p>RIBBON CABLE 8 way single strand miniature 22p per metre.</p>	<p>TELEPHONE PICK UP COIL Sucker type with lead and 3.5mm plug 62p.</p>	<p>TERMS: Cash with Order (Official Orders welcomed from colleges etc). 30p postage please unless otherwise shown. VAT inclusive. S.a.s. for illustrated lists.</p>	<p>STEREO FM/GRAM TUNER AMPLIFIER CHASSIS, VHF and AM. Bass, treble and volume controls, Gram. 8-track inputs, headphone output jack, 3 watts per channel with power supply. £14.95 and £1.20 p&p (CCT supplied).</p>
<p>MORSE KEYS Beginners practice key £1.05. All metal fully adjustable type. £2.60.</p>	<p>SPEAKERS 5" Round 8 ohms 5 watts £1.35. 6" round 6 watt 8 ohms with cambic surround £2.75. Elac 8" 8 ohm long throw speaker, 18 watts twin cone £4.75. Mid-Range 5" speaker 850-7khz 20 watts £1.45.</p>	<p>RELAYS Plastic Encap. Reed Relay, 0.1 matrix. 1kΩ coil, 9-12VDC normally open, 35p. Miniature encapsulated reed relay 0.1 matrix mounting, single pole make, operates on 12VDC 50p each. Continental series, sealed plastic case relays, 24VDC 3pole change over 5 amp contacts, new 65p. Printed circuit Mtg., Reed relay, single make, 20mm x 5mm, 6-9VDC. coil, 33p each. Metal Cased Reed Relay, 50 x 45 x 17mm, has 4 heavy duty make reed inserts, operates on 12VDC 35p each. Magnets 1/2" long 1/4" thick with fixing hole, 10 for 40p.</p>	<p>STEREO FM/GRAM TUNER AMPLIFIER CHASSIS, VHF and AM. Bass, treble and volume controls, Gram. 8-track inputs, headphone output jack, 3 watts per channel with power supply. £14.95 and £1.20 p&p (CCT supplied).</p>	<p>STEREO FM/GRAM TUNER AMPLIFIER CHASSIS, VHF and AM. Bass, treble and volume controls, Gram. 8-track inputs, headphone output jack, 3 watts per channel with power supply. £14.95 and £1.20 p&p (CCT supplied).</p>

PROGRESSIVE RADIO

31 CHEAPSIDE, LIVERPOOL 2.

ALL ORDERS DESPATCHED BY RETURN POST

How to make a hobby

The opportunities in electronics, today, and for the future are limitless – throughout the world. Jobs for qualified people are available everywhere at very high salaries. Running your own business, also, in electronics – especially for the servicing of radio, TV and all associated equipment – can make for a varied, interesting and highly remunerative career. There will never be enough specialists to cope with the ever increasing amount of electronic equipment coming on to the world market.


We give modern training courses in all fields of electronics – practical D.I.Y. courses – courses for City & Guilds exams, the Radio Amateur licence and also training for the new Computer Technology. We specialise only in electronics and have over 40 years experience in the subject.

All the training can be carried out in the comfort of your own home and at your own pace.

A tutor is available to whom you can write at any time for advice or help during your work.


and a career.

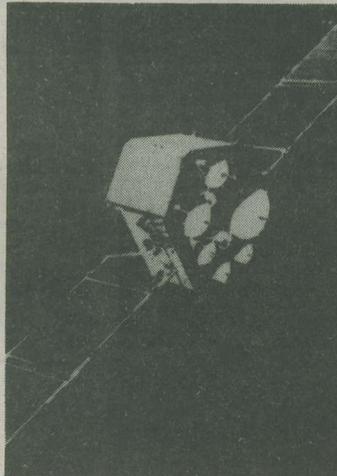- COURSES AVAILABLE
- CITY & GUILDS CERTIFICATES IN TELECOMMUNICATIONS AND ELECTRONICS.
- RADIO AMATEUR LICENCE.
- COMPUTER TECHNOLOGY WITH HOME TRAINING COMPUTER.
- DIGITAL ELECTRONICS.
- BEGINNERS PRACTICAL COURSE.
- RADIO AND TELEVISION SERVICE.
- AND MANY OTHERS.



All students enrolling in our courses receive a free circuit board originating from a computer and containing many different components that can be used in experiments and provide an excellent example of current electronic practice.

Free 32 page
Colour Booklet.

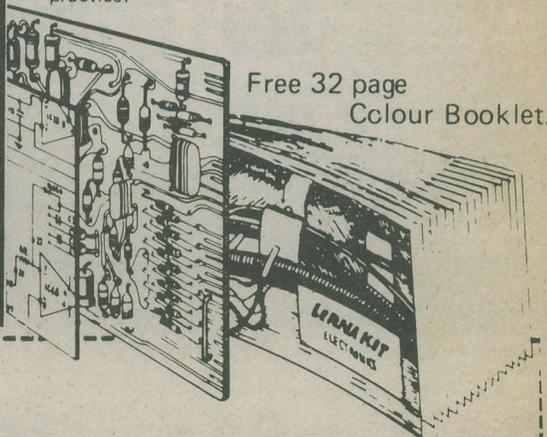

REA12

NAME

ADDRESS

Block Caps Please

Post now, without obligation, to:-

**BRITISH NATIONAL RADIO and
ELECTRONICS SCHOOL**

P.O. Box 156, Jersey,
Channel Islands.

Britain's Best Breadboard Buy at Breadboard '79

**FREE
ENTRY TICKET
WORTH £1.00
WITH EVERY PURCHASE**

All over Britain, hobbyists are discovering Britain's Best Breadboard Buys. At the London Breadboard exhibition '79 on Stand Nos. F1, F2 and G1, G2, CSC will be exhibiting their full range of breadboards.

Here is your chance to obtain a special ticket for Breadboard '79 worth £1.00 absolutely FREE.

Cut out the coupon below and take it along to one of our listed dealers, and make a purchase of any of our breadboards and receive your special FREE ticket — see you at Breadboard '79.

Take the coupon to any of these main dealers:

LONDON

Rastra Electronics Ltd., 279-281 King Street, Hammersmith, London W6

Cubegate Ltd., Audio Electronics, 301 Edgware Road, London W2 1BN

Technomatic Ltd., 17 Burnley Road, London NW10 1ED

Precision Instrument Labs., Instrument House, 727 Old Kent Road, London SE15

MANCHESTER

Shudehill Supply Co., 53 Shudehill, Manchester M4 4AW

BUCKINGHAMSHIRE

West Hyde Development, Unit 9, Park Street Industrial Estate, Aylesbury, Bucks HP20 1ET

Best Electronics (Slough) Ltd., Unit 4 Farnburn Ave., Slough, Bucks SL1 4XU

KENT

Lawtronics, 13a High Street, Edenbridge, Kent TN8 5AX

NEWCASTLE

Aitken Bros., 35 High Bridge, Newcastle upon Tyne

SCOTLAND

Marshalls, 85 West Regent Street, Glasgow G2

F. Brown & Co., 45 George IV Bridge, Edinburgh EH1 1E3


LEEDS

Leeds Amateur Radio Club, Cookridge Street, Leeds 1


HERTFORDSHIRE

BI PAK, 3 Baldock Street, Ware, Herts

CONTINENTAL SPECIALTIES CORPORATION

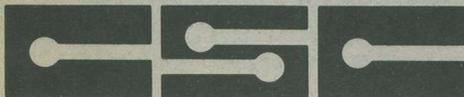

CSC UK LTD. EUROPE, AFRICA, MIDEAST
Dept 16CC2 Shire Hill Industrial Estate Units 1
and 2, Saffron Walden, Essex CB11 3AQ
Tel: Saffron Walden (0799) 21682. Telex: 817477

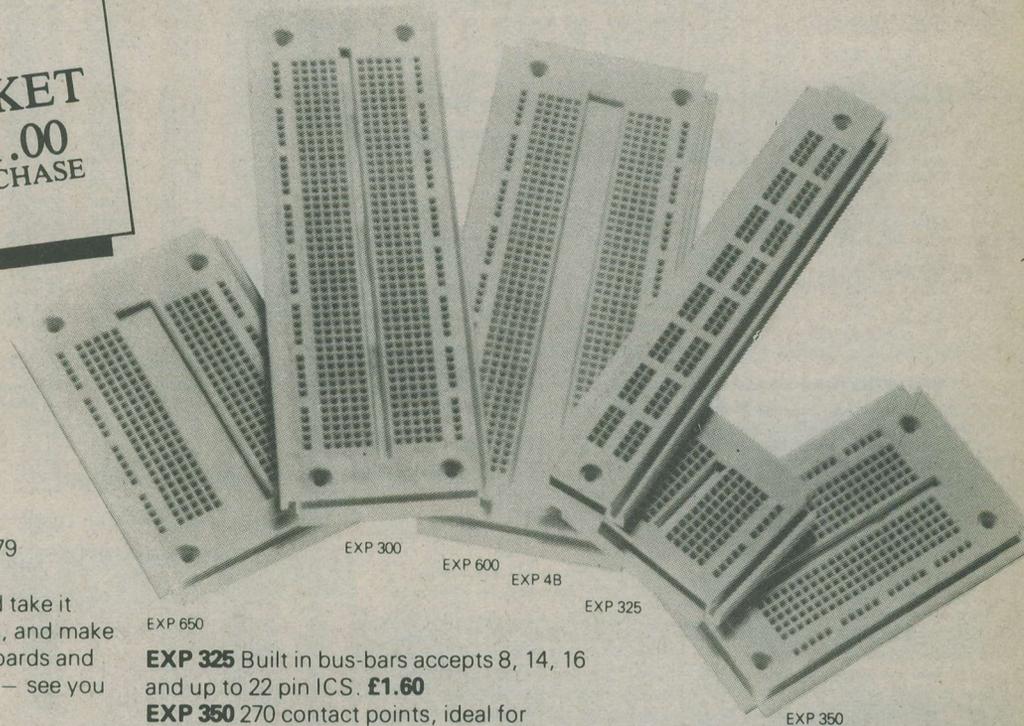

EXP 650

EXP 300

EXP 600

EXP 4B

EXP 325

EXP 350

EXP 325 Built in bus-bars accepts 8, 14, 16 and up to 22 pin ICs. **£1.60**

EXP 350 270 contact points, ideal for working with up to 3 x 14 pin DIPS. **£3.15**

EXP 650 For microprocessor chips. **£3.60**

EXP 4B An extra 4 bus-bars in one unit. **£2.30**

EXP 300 The most widely sold breadboard in the UK; for the serious hobbyist. **£5.75**

EXP 600 6" centre channel makes this the Microprocessor Breadboard. **£6.30**

PB6 Professional breadboard in easily assembled kit form. **£9.20**

PB100 Kit form breadboard recommended for students and educational uses. **£11.80**

The above prices do not include P&P and 15% VAT

The Experimentor System

4 ways to order Experimentor Systems

- EXP 300PC which includes one item.
A matchboard pre-drilled PCB — £1.32
- EXP 302 which includes three items.
Three 50-sheet scratchboard workpads — £1.68
- EXP 303 which includes three items.
Two matchboards and an EXP 300 solderless breadboard — £8.60
- EXP 304 which includes four items.
Two matchboards and EXP 300 breadboard and a scratchboard workpad — £9.30

This coupon entitles the holder to a free ticket worth £1.00 to Breadboard '79, with the purchase of any listed breadboards

1 EXP 325 £2.70	Qty. Req'd.	2 EXP 350 £4.48	Qty. Req'd.
3 EXP 650 £5.00	Qty. Req'd.	4 EXP 4B £3.50	Qty. Req'd.
5 EXP 300 £7.78	Qty. Req'd.	6 EXP 600 £8.38	Qty. Req'd.
7 PB6 £11.73	Qty. Req'd.	8 PB 100 £14.72	Qty. Req'd.

Experimentor System

1 EXP 300PC £2.38	Qty. Req'd.	2 EXP 302 £2.79	Qty. Req'd.
3 EXP 303 £11.04	Qty. Req'd.	4 EXP 304 £11.85	Qty. Req'd.

Boxed prices include P&P and 15% VAT

If no dealer in your area contact CSC direct.

Continental Specialties Corporation, (U.K.) Limited, Dept 16CC2
Unit 1, Shire Hill Industrial Estate, Saffron Walden, Essex Tel: (0799) 21682

NAME

ADDRESS

FREE catalogue tick box

I enclose cheque/PO for £
or debit my Barclaycard, Access, American
Express card

No. Exp. date
or Tel: (0799) 21682 with your card number and
your order will be in the post immediately.

GREENWELD

443G Millbrook Road Southampton SO1 0HX

All prices include VAT at 15% — Just add 30p post

£1 BARGAIN PACKS

K101—16 BC2398 N.P.N. Low Noise	£1.00
K102—15 BC349B N.P.N. Low Noise	£1.00
K103—10 BC546B N.P.N. 80 Volt	£1.00
K104—18 BC182B N.P.N. 60 Volt	£1.00
K105—50 IN4148 Silicon Diode	£1.00
K106—18 BC184L N.P.N. Low Noise	£1.00
K107—18 BC213L P.N.P. General Purpose	£1.00
K108—8 2N5060 30N .8A SCR	£1.00
K109—15 BC114 N.P.N. Low Noise	£1.00
K114—15 XK6116 (BF241) N.P.N. 200 MHz	£1.00
K115—18 SP1218 (2N3702) P.N.P. Gen. Purpose	£1.00
K117—10 BF450 P.N.P. T.V. IF Amp.	£1.00
K118—16 ME4101 N.P.N. 80V Low Noise	£1.00
K124—50 .02uF Disc Ceramics	£1.00
K125—200 1k 5% 1/4W. CF Resistors	£1.00

1,000 RESISTORS £2.50!!

New stock just arrived — Carbon Film 2% and 5%, 1/4W and 1/2W, all brand new, but have pre-formed leads, ideal for PC mntg. Enormous range of popular mixed values for just **£2.50/1,000, £11/5,000 £50/25,000.**

LINEAR IC BARGAIN

We have just received a large consignment of popular linear IC's that have failed the manufacturers stringent tests. However, on checking through a few hundred we have found that quite a large proportion tested in a simple oscillator circuit are functional, so are offering them in packs as follows:

TYPE	PACKAGE	%GOOD	QTY	PRICE
702	14DIL	65	25	£1.20
709	8DIL	75	20	£1.20
709	14DIL	50	30	£1.20
710	TO99	30	40	£1.20
710	14DIL	30	40	£1.20
720	14DIL	80	20	£1.20
741	TO99	40	25	£1.20
748	TO99	70	15	£1.20

Connection-data is supplied. One of each pack, **£8.50**

3W AMP MODULE

Ready built and tested, this handy amplifier will prove very useful around the workshop. Just requires 17V ac source (and 8R spkr) as bridge rect and smoothing cap are mounted on the PCB. The 4 transistor circuit provides enough sensitivity for most applications. Supplied complete with circuit diagram and wiring details. Only **£1.75**. Suitable transformer **£2.20**.

TRANSFORMERS

PA 100V line speaker type. Pri tapped 0.625W — 10W in 5 steps. Sec 4 or 8 ohm **£1.75 10/£15 100/£110**
Mains pri, 3 sec windings, 8, 25 and 40V, each at 100mA. A selection of voltages from 8 to 73V is therefore obtainable. 57x48x36mm with flying leads. **£1.50**
Mains pri, sec 40V @ 250mA **£1.75**

CLOCK CASE BARGAIN

Z472 Oval format, overall size 130x68x87mm deep, with built in stand. Rear panel drilled to accept 4 switches and alarm **60p**

Send SAE for latest 8 page Bargain List with 60 more packs on — plus lots of other goodies!

THE AMAZING GREENWELD CATALOGUE

FEATURES INCLUDE:

- 50p Discount Vouchers
 - Quantity prices for bulk buyers
 - Bargain List Supplement
 - Reply Paid Envelope
 - Priority Order Form
 - VAT inclusive prices
- PRICE **30p** + 15p POST

VERO OFFCUTS

Packs of 100 sq ins of good size pieces about 4 x 3" in the following types:

K541 0.1" copper clad	£1.50
K542 0.15" copper clad	£1.60
K544 0.1" plain	£1.50

Also pieces 2 1/2 x 1" — 10/£1.20 100/£9
17x3 3/4" x 0.1" sheets — 10/£16.50

Large range of Standard Veroboard and boxes/cases in stock. Details in catalogue, **45p**

SCOOP! Verobox type 2522, unused but has 3 1/2" holes in one end and 1 1/2" hole the other, so instead of £3.96, we are selling these at **£1.85**

SWITCHES

Push-button banks — 20 types listed on Bargain List No. 8, free with cat (45p) or send SAE. Samples:
W473 3 interlocking 4PCO + 2 independent, **70p**
W481 5 interlocking 4PCO **70p**
Both types supplied with free knobs!
W106 DPCO slide switch 23x15x7mm **10/£1.20; 100/£9**
W107 SPCO min slide switch with 2 wires attached. **10/80p 100/£6.**
W508 SPCO 5A microswitch with 29mm lever 20x12x6mm **38p 10/£3.00**
W302 Rocker switch on/off 10A white. **22p 10/£1.80.**
W305 Rocker SPCO, centre off, 10A rating, white **30p 10/£2.30 100/£19.**

AERIALS

X901 Telescopic 8 sections 970mm long extended, 175mm collapsed. Swivel joint. 2BA fixing hole in base. **75p**
X904 Ferrite rod 140mm x 9mm LW/MW/coupling coils, each independently moveable **64p**
X905 As above, but LW/coupling coil together on moveable former **55p**

BUZZERS & MOTORS

Z401 Powerful 6V DC, all metal construction. 50mm dia x 20mm **70p**
Z402 Miniature type, 3-9V, only 22x15x16mm. Very neat **65p**
Z450 Miniature 6V DC motor, high quality type 32mm dia x 25mm high, with 12mm spindle. Only **£1**
Z451 12V high torque motor 30mm dia x 40mm high, with 10mm spindle. **65p**
Z452 6V DC motor with gearbox giving final shaft speed 700 rpm. Spindle is threaded OBA. Ex-equip **£1**
Z453 As above, but 300 rpm and unthreaded spindle **£1**.

VU METERS

Voo2 Twin type. 2 meters 40x40mm and driver board, supplied with circuit and connexion data. **£3.50**
Voo3 New type, just in. Twin type moulded in one piece, 80x40mm (No driver board but suitable circuit supplied) **£2.50**

MARCO TRADING

To introduce our new list some of the prices below are much less than our new list price. These special prices are valid until the end of the month in which they appeared.

To obtain a free copy of our 35 page list simply send a 20p postage stamp or a large SAE. This advertisement shows only a small part of our range. (Our new list includes CMOS, Tant Beads, Electrolytics, Disc ceramics, etc.)

TRANSISTORS

AC128	24p	BC213	9p	BF115	32p	BFY77	10p
AD149	58p	BC213L	9p	BF127	38p	BR101	30p
AD161	42p	BC214	9p	BF159	25p	BRV39	32p
BC107	8p	BC214B	9p	BF166	22p	BSY52	30p
(TO5 leg)		BC214B	9p	BF167	32p	BU105/02	£1.50
BC108	9p	BC214L	9p	BF178	24p	BU124	£1.82
BC109	9p	(TO5 lead)	8p	BF178	24p	BU126	£1.50
BC125	10p	BC268A	25p	BF182	29p	BU204	£1.50
BC126	10p	BC301	42p	BF183	29p	BU205	£1.35
BC147B	7p	BC307B	10p	BF194	10p	BU206	£1.75
BC149	8p	BC308A	10p	BF194A	12p	BU208	£1.75
BC153	10p	BC309	10p	BF195	10p	GET872	15p
BC161	42p	BC441	36p	BF195C	12p	GET881	15p
BC177	18p	BC460	36p	BF200	28p	OC45	25p
BC178	18p	BC547	12p	BF224J	15p	OC71	28p
BC182	9p	BC558A	13p	BF241	12p	OS72	32p
BC182L	9p	BCY42	30p	BF257	28p	OC76	36p
BC183	9p	BCY70	17p	BF259	29p	TIP29A	44p
BC183B	9p	BCY71	18p	BF262	29p	TIP31A	36p
BC183L	9p	BCY72	15p	BF263	30p	TIP32A	40p
BC184	9p	BD116	54p	BF337	30p	TIP32C	70p
BC184L	9p	BD131	35p	BFT41	11p	TIP33A	65p
BC212	9p	BD132	35p	BFX84	22p	TIP41A	45p
BC212B	9p	BD135	34p	BFX89	50p	TIP42A	65p
BC212L	9p	BD136	34p	BFY50	20p	TIP3055	85p
BC212LA	9p	BD183	75p	BFY51	20p	TIS43	34p
		BDY20	£1.05	BFY52	20p	2N3055	48p

400m/w ZENER DIODES Low Price

3V, 3V3, 3V6, 3V9, 4V3, 4V7, 5V1, 5V6, 6V2, 6V8, 7V5, 8V2, 9V1, 10V, 11V, 12V, 13V, 13V5, 15V, 16V, 18V, 20V, 22V, 24V, 27V, 30V, 33V.
Price: **8p each 100 any mix £8.00**

1 watt ZENER DIODES

3V3 to 200V Full range
Price: **15p each 100 any mix £12.50**

BRIDGE RECTIFIERS

1.5Amp 50V	32p
400V	43p
800V	58p
2.0Amp 50V	35p
700V	44p
400V	50p
6.0Amp 50V	70p
200V	78p
400V	85p
10.0Amp 50V	£1.87
400V	£2.79
600V	£3.54
25.0Amp 50V	£1.95
400V	£2.99
600V	£4.50

I.C. SOCKETS

8 DIL	10p
14 DIL	13p
16 DIL	15p
18 DIL	18p
20 DIL	22p
22 DIL	23p
24 DIL	24p
28 DIL	28p
40 DIL	40p

0.1W SUB. MINIATURE PRE-SETS

100Ω to 1Meg Vertical or Horizontal.
Price: **6p each. 100 any mix £4.50**

ROTARY TOTS

LOG: 4K7, 10K, 22K, 47K, 100K, 220K, 470K, 1M, 2M2 **27p each**
LIN: 470Ω, 1K, 2K2, 4K7, 10K, 22K, 47K, 100K, 220K, 470K, 1M, 2M2 **10 for £2.50**
(Mixed your choice)

RESISTORS Low Noise 5% High Stability

1/4W at 40C, 1/3W at 70C. E12 series only i.e. 2.2Ω, 2.7Ω, 3.3Ω, 3.9Ω, 4.7Ω, 5.6Ω, 6.6Ω, 8.2Ω, 10Ω etc.

All at **2p each**, 10 of one value for **15p**, 1,000 mixed in 100's **£8.00**
Our well known "Special Development" pack. Special Price: **£6.00**
(This pack consists of 10 off each value 2.2Ω to 2M2. 730 resistors)
1W resistors available. E12 series only. 2.2Ω to 10M **5p each**
2W resistors available. E12 series only. 10Ω to 10M **8p each**

DIODES

0A47 10p, 0A81 14p, 0A90 10p, 0A91 10p, 0A200 5p, 1N4148 4p, 1S44 7p, 1N914 (Formed Leads) 3p, 1N4001 5p, 1N4004 6p, 1N4007 7p, 1N5392 11p, 1N5401 16p, 1N5404 18p, 1N5408 27p.

Many, many more items in stock including our new range of 63V polycarbonate close tolerance capacitors. In 63V we are now able to offer 1%, 1%, 2% and 5%. In 440V the range is still the same. Full details in our FREE list.

SPECIAL OFFERS

Power Amplifier Sanyo STK015 Brand New Full Spec etc. 10 Watts into 8Ω. Free spec sheet with every order. Our price: **£2.50 each**.
Radio Spares Edge Meter Type MR100 (259-562). All new and boxed. RS price over £4.00 each. Our price: **£2.50 each**.

Send your orders to:

**DEPT. DP12, MARCO TRADING,
THE OLD SCHOOL, EDSTASTON,
Nr. WEM, SHROPSHIRE SY4 5RJ
Tel: Whixall (094872) 464/465**

Please add 25p postage and packing to each order and add 15% VAT to your total order. Export add NO VAT but add postage Air/Sea at cost.



SEMICONDUCTORS

DEPT. RC12, PO Box 6, Ware, Herts.
Visit our Shop at: 3 Baldock Street, Ware, Herts.

TEL: 0920 3182
TELEX: 817861

TRANSISTORS

Type	Price	Type	Price	Type	Price	Type	Price
AC126	£0.21	BC148	£0.08	BC550	£0.18	BU105	£1.84
AC127	£0.21	BC149	£0.08	BC555	£0.18	BU105/02	£2.24
AC128	£0.18	BC157	£0.12	BC557	£0.18	BU204	£1.81
AC129K	£0.30	BC159	£0.12	BC558	£0.18	BU205	£1.81
AC130	£0.23	BC167	£0.14	BC559	£0.14	BU208/02	£2.68
AC131	£0.23	BC168	£0.14	BD116	£0.58	MJE2955	£1.04
AC132	£0.25	BC169	£0.10	BD121	£0.75	MJE3440	£0.89
AC141K	£0.35	BC170	£0.10	BD124	£0.81	MPE102	£0.35
AC142	£0.23	BC171	£0.10	BD131	£0.40	MPF104	£0.35
AC176	£0.21	BC172	£0.10	BD132	£0.40	MPF105	£0.40
AC176K	£0.30	BC173	£0.10	BD135	£0.44	MPSA05	£0.23
AC179	£0.29	BC177	£0.18	BD136	£0.40	MPSA06	£0.23
AC180	£0.23	BC178	£0.18	BD137	£0.40	MPSA55	£0.23
AC180K	£0.32	BC180	£0.29	BD138	£0.41	OC22	£1.73
AC181	£0.23	BC181	£0.10	BD139	£0.41	OC23	£1.73
AC181K	£0.32	BC182L	£0.10	BD140	£0.41	OC24	£1.55
AC182	£0.21	BC183	£0.10	BD155	£0.92	OC25	£1.18
AC187K	£0.32	BC183L	£0.10	BD175	£0.89	OC28	£1.15
AC188	£0.21	BC184	£0.10	BD176	£0.89	OC28	£1.15
AC188K	£0.32	BC207	£0.13	BD177	£0.78	OC29	£1.09
AD140	£0.69	BC208	£0.13	BD178	£0.78	OC35	£1.03
AD142	£0.69	BC209	£0.14	BD179	£0.86	OC36	£1.03
AD143	£0.86	BC212	£0.10	BD203	£0.92	OC70	£0.27
AD149	£0.89	BC217	£0.12	BD204	£0.92	OC71	£0.17
AD161	£0.40	BC218	£0.10	BDY20	£0.82	OC71	£0.17
AD162	£0.40	BC219	£0.10	BF457	£0.43	TC144	£0.33
AD161	£0.40	BC221	£0.10	BF458	£0.43	TC145	£0.40
AD162MP	£0.81	BC222	£0.10	BF459	£0.44	TC29A	£0.48
AF124	£0.35	BC223	£0.10	BF594	£0.36	TIP29B	£0.48
AF125	£0.35	BC238	£0.18	BF595	£0.36	TIP29C	£0.51
AF126	£0.35	BC251	£0.17	BF939	£0.26	TIP30A	£0.46
AF127	£0.37	BC251A	£0.18	BF940	£0.29	TIP30B	£0.46
AF139	£0.40	BC302	£0.32	BF979	£0.32	TIP30C	£0.50
AF186	£0.58	BC302	£0.17	BF979	£0.32	TIP31A	£0.46
AF239	£0.47	BC303	£0.32	BF980	£0.32	TIP31B	£0.48
AL102	£1.38	BC304	£0.44	BF980	£0.32	TIP31C	£0.50
AL103	£1.38	BC327	£0.18	BF982	£0.25	TIP32A	£0.46
AL104	£1.81	BC328	£0.17	BF982	£0.25	TIP32B	£0.46
AU110	£1.61	BC337	£0.17	BF985	£0.28	TIP32C	£0.50
AU113	£1.61	BC338	£0.17	BF986	£0.29	TIP41A	£0.50
BC107A	£0.09	BC440	£0.35	BF987	£0.25	TIP41B	£0.52
BC107B	£0.10	BC441	£0.35	BF987	£0.25	TIP41C	£0.55
BC107C	£0.12	BC480	£0.44	BF987	£0.25	TIP42A	£0.50
BC108A	£0.08	BC481	£0.44	BF988	£0.25	TIP42B	£0.52
BC108B	£0.11	BC477	£0.23	BF988	£0.25	TIP42C	£0.55
BC108C	£0.12	BC478	£0.23	BF988	£0.25	TIP2955	£0.69
BC109A	£0.09	BC479	£0.23	BF988	£0.25	TS43	£0.25
BC109B	£0.10	BC547	£0.12	BF988	£0.25	TS59	£0.20
BC109C	£0.12	BC548	£0.12	BF988	£0.25	UT15	£0.23
BC147	£0.08	BC549	£0.12	BRY39	£0.51	ZTX107	£0.11

74 SERIES TTL ICs

Type	Price	Type	Price	Type	Price	Type	Price
7400	£0.10	7426	£0.26	7470	£0.26	74105	£0.43
7401	£0.12	7427	£0.27	7472	£0.23	74105/02	£0.27
7402	£0.12	7428	£0.29	7473	£0.28	74110	£0.41
7403	£0.12	7430	£0.12	7474	£0.28	74111	£0.66
7404	£0.12	7432	£0.25	7476	£0.28	74118	£0.92
7405	£0.12	7433	£0.34	7477	£0.28	74119	£1.35
7406	£0.25	7437	£0.25	7480	£0.50	74121	£0.27
7407	£0.25	7438	£0.24	7482	£0.78	74122	£0.44
7408	£0.14	7440	£0.13	7483	£0.55	74123	£0.46
7409	£0.14	7441	£0.57	7484	£1.01	74136	£0.59
7410	£0.12	7442	£0.62	7485	£0.78	74141	£0.63
7421	£0.19	7443	£0.80	7485	£1.45	74145	£0.63
7422	£0.17	7444	£0.80	7486	£0.25	74150	£0.98
7423	£0.27	7445	£0.74	7490	£0.36	74151	£0.55
7424	£0.57	7446	£0.69	7491	£0.73	74153	£0.55
7425	£0.28	7447	£0.55	7492	£0.40	74154	£0.94
7426	£0.12	7448	£0.84	7493	£0.34	74155	£0.57
7427	£0.12	7450	£0.10	7494	£0.86	74156	£0.57
7428	£0.12	7451	£0.12	7495	£0.86	74157	£0.57
7429	£0.18	7453	£0.12	7496	£0.57	74160	£0.58
7430	£0.24	7454	£0.12	74100	£0.97	74161	£0.71
7431	£0.21	7460	£0.12	74104	£0.44	74162	£0.71

CMOS ICs

Type	Price	Type	Price	Type	Price	Type	Price
CD4000	£0.18	CD4015	£0.87	CD4026	£1.38	CD4043	£1.01
CD4001	£0.17	CD4016	£0.48	CD4027	£0.78	CD4044	£0.84
CD4002	£0.18	CD4017	£0.86	CD4028	£0.78	CD4045	£1.61
CD4006	£1.05	CD4018	£0.97	CD4029	£0.97	CD4046	£1.49
CD4007	£0.19	CD4019	£0.48	CD4030	£0.55	CD4047	£1.00
CD4008	£1.05	CD4020	£1.03	CD4031	£2.30	CD4048	£0.48
CD4009	£0.18	CD4021	£0.96	CD4035	£1.15	CD4049	£0.48
CD4010	£0.55	CD4022	£0.94	CD4037	£1.09	CD4054	£1.26
CD4011	£0.17	CD4023	£0.17	CD4040	£1.01	CD4055	£1.15
CD4012	£0.18	CD4024	£0.74	CD4041	£0.87	CD4056	£1.55
CD4013	£0.48	CD4025	£0.17	CD4042	£0.82	CD4069	£0.19


LINEAR ICs

Type	Price	Type	Price	Type	Price	Type	Price
CA3011	£0.92	CA3140	£0.80	MC1350	£1.61	709P	£0.29
CA3014	£0.75	IM301	£0.33	MC1352	£1.61	72110C	£0.46
CA3018	£1.54	IM304	£1.84	MC1469	£3.39	72710	£0.34
CA3020	£1.95	IM308	£1.15	MC1496	£1.03	UA711C	£0.36
CA3022	£0.92	IM309	£1.72	NE536	£3.05	72711	£0.36
CA3035	£1.61	IM320 5v	£1.72	NE550	£1.09	UA723C	£0.52
CA3036	£1.15	LM320 12	£1.72	NE555	£0.27	UA711C	£0.27
CA3042	£1.72	LM320 15	£1.72	NE555	£0.89	72741	£0.27
CA3046	£0.80	LM320 24	£1.72	NE555	£1.88	72741P	£0.23
CA3052	£1.84	M380	£0.97	NE566	£1.38	UA747C	£0.89
CA3054	£1.26	M381	£0.96	NE567	£1.38	72747	£0.89
CA3075	£1.26	IM3900	£0.66	UA702C	£0.52	UA748	£0.40
CA3089	£1.72	MC1303L	£0.97	72102	£0.52	72748	£0.40
CA3090	£4.14	MC1304	£2.18	UA703	£0.28	748P	£0.40
CA3123	£1.18	MC1310	£1.09	UA709	£0.28	SN76013N	£2.01
CA3130	£2.08	MC1312	£2.18	72709	£0.52	SN76023	£2.01

THYRISTORS

Volts No:	Price	Type	Price
50 THY1A/50	£0.29	Z1X108	£0.11
100 THY1A/100	£0.32	Z1X109	£0.11
200 THY1A/200	£0.36	Z1X300	£0.13
400 THY1A/400	£0.43	Z1X500	£0.14
600 THY1A/600	£0.51	2N1613	£0.23
800 THY1A/800	£0.66	2N1711	£0.23
50 THY3A/50	£0.32	2N1889	£0.51
100 THY3A/100	£0.34	2N1890	£0.51
200 THY3A/200	£0.37	2N1891	£0.51
400 THY3A/400	£0.48	2N2147	£0.88
600 THY3A/600	£0.57	2N2148	£0.81
800 THY3A/800	£0.74	2N2160	£1.15
50 THY5A/50	£0.41	2N2192	£0.44
100 THY5A/100	£0.51	2N2193	£0.44
200 THY5A/200	£0.57	2N2194	£0.44
400 THY5A/400	£0.65	2N2217	£0.25
600 THY5A/600	£0.79	2N2218	£0.25
800 THY5A/800	£0.93	2N2218A	£0.25
		2N2219	£0.23
		2N2219A	£0.26
		2N2904	£0.23
		2N2904A	£0.24
		2N2905	£0.20
		2N2905A	£0.23
		2N2906A	£0.18
		2N2907	£0.23
		2N2907A	£0.25
		2N2926	£0.10
		2N2927	£0.09
		2N2928	£0.11
		2N2929	£0.09
		2N2929A	£0.09
		2N2930	£0.09
		2N2930A	£0.09
		2N2931	£0.09
		2N2931A	£0.09
		2N2932	£0.09
		2N2932A	£0.09
		2N2933	£0.09
		2N2933A	£0.09
		2N2934	£0.09
		2N2934A	£0.09
		2N2935	£0.09
		2N2935A	£0.09
		2N2936	£0.09
		2N2936A	£0.09
		2N2937	£0.09
		2N2937A	£0.09
		2N2938	£0.09
		2N2938A	£0.09
		2N2939	£0.09
		2N2939A	£0.09
		2N2940	£0.09
		2N2940A	£0.09
		2N2941	£0.09
		2N2941A	£0.09
		2N2942	£0.09
		2N2942A	£0.09
		2N2943	£0.09
		2N2943A	£0.09
		2N2944	£0.09
		2N2944A	£0.09
		2N2945	£0.09
		2N2945A	£0.09
		2N2946	£0.09
		2N2946A	£0.09
		2N2947	£0.09
		2N2947A	£0.09
		2N2948	£0.09
		2N2948A	£0.09
		2N2949	£0.09
		2N2949A	£0.09
		2N2950	£0.09
		2N2950A	£0.09
		2N2951	£0.09
		2N2951A	£0.09
		2N2952	£0.09
		2N2952A	£0.09
		2N2953	£0.09
		2N2953A	£0.09
		2N2954	£0.09
		2N2954A	£0.09
		2N2955	£0.09
		2N2955A	£0.09
		2N2956	£0.09
		2N2956A	£0.09

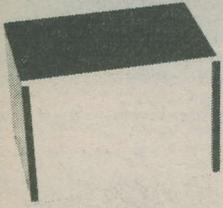DO YOUR PROJECTS LACK THE PROFESSIONAL LOOK?



**IF SO,
TRY OUR HB RANGE**

Instrument cases to give any project a professional look. The four separate top, bottom and end panels are made of black p.v.c. coated steel. Front panel and top and bottom trim are satin anodised aluminium for a neat finish; back panel is in plain aluminium. The whole case, including screws, comes in a flat package and may be assembled in minutes.

DIMENSIONS IN INCHES


Model	Width	Depth	Height	Price
HB1	9	6	3	£4.87
HB2	9	6	4½	£5.27
HB3	9	6	6	£5.63
HB4	12	8	3	£5.98
HB5	12	8	4½	£6.80
HB6	12	8	6	£7.26

ALUMINIUM BOXES

Aluminium box with lid and screws.

Model	Length	Width	Height	Price
AL1	3	2	1	52p
AL2	4	3	1½	62p
AL3	4	3	2	72p
AL4	6	4	2	81p
AL5	6	4	3	94p
AL6	8	6	2	£1.27
AL7	8	6	3	£1.43

(Dimensions in inches)

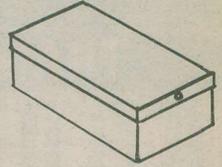


INSTRUMENT CASES

BC Range consists of black P.V.C. coated steel top cover with bevelled front edge, u-shaped aluminium chassis and two fixing screws.

Model	Length	Width	Height	Price
BC1	6	4½	2	£1.61
BC2	6	4	3½	£1.74
BC3	8	5½	2½	£1.99
BC4	10	6½	3	£2.60

(Dimensions in inches)

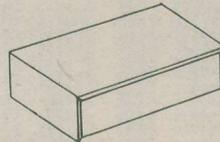

SHEET ALUMINIUM

Gauge	4 x 6	6 x 9	8 x 12
16	29p	57p	£1.02
18	20p	42p	69p
20	17p	32p	52p

AXIAL CAPACITORS

1/25v	4p	125/10v	7p
2.2/63v	4p	150/25v	6p
3.3/50	4p	180/25v	6p
4.7/40v	4p	220/16v	8p
10/25v	4p	220/25v	8p
15/16v	5p	220/63v	9p
22/10v	5p	330/10v	9p
22/16v	5p	330/25v	9p
22/25v	5p	330/63v	12p
33/35v	5p	470/6.3v	9p
33/50v	5p	470/16v	12p
47/25v	5p	470/40v	15p
47/16v	5p	680/6.3v	12p
47/50v	6p	1000/6.3v	15p
50/25p	5p	1000/16v	20p
100/10v	5p	1500/25v	20p
100/16v	5p	2200/10v	20p
100/63v	8p	3300/16v	25p

4700/10v 25p

TTL

7400	10p	7438	19p	7494	43p
7401	12p	7440	12p	7495	37p
7402	12p	7441	50p	74107	20p
7404	12p	7442	38p	74121	26p
7405	12p	7446	51p	74122	34p
7406	25p	7447	43p	74123	42p
7408	14p	7450	12p	74132	48p
7409	14p	7451	12p	74141	56p
7410	10p	7470	26p	74151	38p
7411	15p	7472	22p	74153	38p
7412	16p	7474	23p	74154	60p
7414	42p	7475	24p	74160	45p
7416	22p	7476	19p	74164	60p
7420	12p	7485	50p	74174	55p
7421	20p	7486	21p	74175	55p
7427	20p	7489	£1.25	74192	48p
7430	13p	7490	32p	74193	48p
7432	17p	7491	30p	74194	43p
7437	18p	7492	30p	74196	48p
		7493	25p		

Single sided, copper clad, printed circuit board. 2½ x 8½
4½ x 9
Price: 10p
Price: 25p

25 Mixed Rubber Grommets Price 16p

16mm screw-on cab. feet. Set of four
Price: 5p

14mm square self adhesive feet. Set of four
Price: 15p

Din Plugs 5 pin 180° Price 10p

Din Sockets 5 pin 180°. Standard metal type
Price: 10p

Magnetic earpieces with 3.5mm plug
Price: 12p

Reed Switches Price: 5p
Wire Neons 90 volts Price: 4p

75mm diam. 15 ohm Speaker
Price: 60p

125mm x 78mm Oval 50 ohm Speaker
Price: 75p

Latchswitch 2p 2w Price: 10p

DPDT Slide Switches Price: 12p

Green Phono Plugs Price: 6p

Bridge Rectifiers

W005 50v 1A Price: 25p

W04 400v 1A Price: 28p

Red L.E.D.s 2 inch Price: 8p

Green L.E.D.s 2 inch Price: 12p

Ceramic Filters 6MHz, SEF 6.0MB Price: 20p

Colour T.V. Crystals 4.433619MHz Price: 90p

PP3 Battery connecting leads Price: 6p

20mm chassis mounting fuse holders Price: 6p

20mm Panel Mounting F/H Price: 17p

DL500 Displays Common Cathode

.5 inch displays Price: 75p

1p 12w Rotary Switches Price: 41p

RADIAL CAPACITORS

.47/50v	4p	220/50v	9p
1/50v	4p	220/63v	9p
2.2/25v	4p	330/10v	8p
10/40v	4p	330/25v	8p
10/50v	5p	330/50v	9p
15/16v	5p	330/63v	9p
22/25v	5p	470/6.3v	8p
22/50v	6p	470/16v	9p
33/63v	6p	470/25v	10p
47/16v	6p	1000/16v	20p
47/35v	6p	1000/25v	21p
100/35v	6p	1000/35v	23p
220/16v	8p	2200/10v	23p
220/40v	8p	3300/6.3v	24p

TRANSISTORS

AD161/2		BC182LB	9p	BF194	12p
MP	75p	BC183A	10p	BF195	12p
BC107	9p	BC207B	11p	BF198	15p
BC108A	10p	BC212L	10p	BF200	25p
BC148	7p	BC213LB	10p	BF750	15p
BC149C	8p	BC308	10p	TIP32B	45p
BC149S	9p	BC338	10p	2N2906	16p
BC171B	10p	BC547	11p	2N2907	18p
BC172'b	10p	BD183	90p	2N3055	45p
		BF137	11p		

C280 POLYESTER CAPACITORS 250v

.01uF	4p	.068uF	5p	.33uF	8p
.015uF	4p	.1uF	5p	.47uF	8p
.022uF	4p	.1uF 400v	7p	.68uF	12p
.033uF	4p	.15uF	6p	.68uF 630v	10p
.047uF	4p	.22uF	6p	1.0uF	15p

CAN CAPACITORS

1250/50v	50p	10,000/10v	60p
2500/35v	70p	15,000/10v	60p
		15,000/16v	75p

DIODES

BZY88c 6v2	7p	BZY88c 22v	7p
BZY83c 6v2	7p	BZY79c 68v	7p
BZY88c 7v5	7p	IN914	3p
BZY88c 8v2	7p	IN4148	2p
BZX79c 9v1	7p	IN4150	3p
BZY88c 15v	7p	IN4004	5p
BZY88c 20v	7p	IN4005	6p

OA91 4p

SUB-MIN PRESETS

Horizontal: 100Ω 220Ω 470Ω 1k, 1k5, 2k2, 4k7, 10k, 22k, 47k, 100k.
Vertical: 470Ω 2k2, 4k7.
All price: 5p

All prices include V.A.T. and post and packing. Send for free pamphlet on all our instrument cases, boxes and components. Discount on boxes and instrument cases only, as follows: Orders over £10 5%, over £20 10%, over £30 15%.


**HARRISON BROS. P.O. Box. 55, Westcliff-on-Sea,
Essex. SS0 7LQ. Telephone: Southend-on-Sea (0702) 32338.**

Technology for sale.

The Mark III FM Tuner

DIY Hi-Fi will never seem the same again. Ambit's Mark III tuner system is electrically & visually superior to all others. Some options available, but the illustrated version with reference series modules: £149.00 + £18.62 VAT

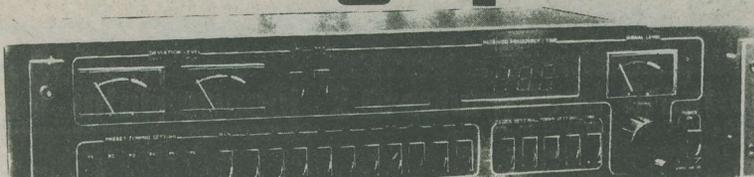With Hyperfi Series modules £185.00 + £23.12



Features of the system:

- * Precision construction & design of all parts
- * Time frequency display
- * State of the art performance with facilities for updates, using modular plug in systems.
- * Deviation level calibrator for recording
- * All usual tuner features

Digital Dorchester All Band Broadcast Tuner: LW/MW/SW/SW/SW/FM stereo

A multiband superhet tuner, constructed using a single IC for RF/IF processing - but with all features you would expect of designs of far greater complexity. The FM section uses a three section (air gang) tuned FET tunerhead, with ceramic IF filters and interstermination; AM employs a double balanced mixer input stage, with mechanical IF filters - plus a BFO and MOSFET product detector for CW/SSB reception. Styled in a matching unit to the Mark III FM only tuner, employing the same degree of care in mechanical design to enable easy construction. MW/LW reception via a ferrite rod antenna.

Electronics only (PCB and all components thereon) £33.00 + £4.95 VAT
 Complete with digital frequency readout/clock-timer hardware £99.00 + £14.85 VAT
 Complete with MA1023 clock/timer module with dial scale £66.00 + £9.90 VAT
 Hardware packages are available separately if you wish to house your own designs in a professional case structure. Please deduct the cost of electronics from complete prices.

LW MW FM LCD Digital Frequency Display - July PW feature

Update your old radio, or build this into a new design. Or use it as a servicing aid - this low power unit with LCD display reads direct frequency in kHz/MHz, or with usual AM/FM IF offsets for received frequency. Low power LCD means no RF! - 15-20mA at 9v even with the divide by 100 prescaler. FM resolution is 100kHz, AM 1kHz. Sensitivities better than 10mV
 Complete kit £19.50 + £2.93 VAT, built and tested module £27.00 + £4.05VAT



Ambit stocks and distributes a wide range of frequency counter LSI for all types of DFM-part two of the catalogue contains details of the MSMS523/4/5/6 range, and the versatile MSL2318 divide by ten or hundred prescaler IC. The DFM1 combined counter for AM, FM SW and direct/clock/stopwatch/timers - details available, but SAE please!

PW SANDBANKS PI METAL LOCATOR

Maintaining our professional approach to home constructor kits, we offer the pulse induction "Sandbanks". Now with injection molded casing for greatly improved environmental sealing. £37.00+£5.55vat

VHF MONITOR RX WITH PLESSEY IC

4/9 channel version of the PW design but using standard (fundx9) crystals, and TOYO 8 pole crystal filter with matching transformers. Coil sets from our standard range to cover bands from 40 to 200MHz. Complete module kit £31.25 + £3.90vat

MICROMARKET

		OSTS: overflow:	
6800P	650p	8212	230p
6820P	600p	8216	195p
6850P	275p	8224	350p
6880	400p	8228	478p
68S2	365p	8251	625p
8080	630p	8255	540p

RADIO and AUDIO MODULES: Consistently the most advanced

FOR FM
 EF5801-3-4 series: 6 stage varicap tuning, all with oscillator output
 5801 Dual gate MOSFET RF stages, bipolar mixer £17.45 + 2.61VAT.
 5803 Dual gate RF/mixer stages, amplified LO out £19.75 + 2.96VAT
 5804 'Hyperfi' series, with internal PIN diode arc, and ultra wide range tuning system £24.95 + 3.74VAT
 EF5402 4 stage varicap tuner with TDA1062 and LO output. Uses FET/IC input, PIN acg £10.75 + 1.61VAT

FOR 30-200MHz
 The EF series are available on special order to cover bands (usually approx 20% of the centre frequency) in the range described. Details in our price list.
FOR FM IFs at 10.7MHz
 7030 single 6 pole linear phase filter IF with HA1137E10.95 + 1.64VAT
 7130 two 6 pole linear phase filter IF with CA3189E £16.25 + 2.44VAT
 7230 Hyperfi IF, switched bandwidth, AGC IF preamp, linear phase ceramic filters with diode switched narrow filter £24.95 + 3.74VAT

DECODERS FOR MPX (STEREO)
 Various types, guaranteed the world's biggest and best ranges
LARSHOLTZ FM TUNERSSETS
 7252 MOSFET front end combined with CA3089 IF £26.50 + 3.97VAT
 7252 JFET front end, combined with IF and decoder £26.50 + 3.97VAT
FM/AM tuning synthesiser, see details elsewhere in this advertisement

COMPONENTS FOR RADIO/COMMUNICATIONS/AUDIO/TV etc.

As usual, Ambit brings you the latest and best, a small selection of which is shown in this advertisement. The Ambit catalogues contain information on most of the devices mentioned here - and an order for the new part three will ensure you stay up to date with latest developments. Data photocopying service described in pricelist info.

RADIO ICs for FM var	SL1600 series	Audio preamps	vat
CA3089E	1.94 29	LM3811	1.81 27
CA3189E	2.45 37	LM382N	1.65 25
HA1137W	2.20 33	KB4436	2.53 38
HA11225	2.20 33	KB4438	2.22 33
SN76660N	0.75 11	TA0A1028	3.50 53
		TA0A1029	3.50 53
		TA0A1074	3.75 56
RADIO ICs for AM/FM	SL1610 series	Audio power	vat
TDA1090	3.35 50	TEA2000	0.75 11
TDA1083	1.95 29	TEA810AS	1.09 16
TOA1220	1.40 21	LM380N	1.00 15
IF AMPLIFIERS	SL1620 series	ULN2283 <th>1.00 15</th>	1.00 15
KB4406	0.50 07	ULN2283	1.00 15
MC1350	1.20 18	TA2A2002	2.99 45
see comms ic also		TA2A2002	2.99 45
COMMUNICATIONS	SL1630 series	TA2A2020 <th>2.99 45</th>	2.99 45
KB4412	2.55 38	MC3567	3.12 47
KB4413	2.75 41	MC1496	1.25 19
SD6000	3.75 56	NE544	1.70 25

OSTS: Remember all OSTs stocks are obtained from BS9000 approved sources - your assurance that all devices are very best first quality commercial types. Some LPSN TTL is presently in great demand, so please check by phone before ordering

TL: Standard AND LP Schottky

		All prices listed in pence *	
7400	13 20	7472	28
7401	13 20	7473	32 38
7402	14 20	7474	37 38
7403	14 20	7475	38 40
7404	14 24	7476	37 38
7405	18 26	7478	38
7406	38	7480	48
7409	17 24	7481	86
7410	15 24	7482	69
7411	20 24	7485	104 99
7412	17	7486	40
7413	30	7488	205
7414	51	7490	300
7415	24	7491	76 110
7416	30	7492	38 78
7417	30	7493	32 99
7420	16 24	7494	78
7421	29 24	7495	65 99
7423	27	7496	58 120
7425	27	7497	185
7426	27	741XX series	
7427	29	74107	32 38
7428	35	74109	63 38
7430	17 24	74110	54 54
7432	25	74111	68
7437	40 24	74112	68
7438	33 24	74113	38
7440	17 24	74114	38
7441	74	74115	198
7442	70 99	74118	83
7443	115	74120	115
7444	112	74121	25
7445	94	74122	46
7446	94	74123	46
7447	82 99	74124	46
7448	56 99	74125	37
7449	99	74126	44
7451	17 24	74129	74
7453	17 24	74132	73 78
7454	17 24	74136	40
7455	35	74138	60
7460	17	74139	60
7463	124	74141	56
7470	28		

CD 4000

4000 17 4522 149
 4001 17 4528 102
 4002 17 4532 125
 4006 109 4538 125
 4007 18 4532 150
 4008 80 4539 110
 4009 58 4543 174
 4010 58 4549 399
 4011 17 4554 153
 4012 17 4558 117
 4013 55 4560 218
 4014 95 4562 330
 4016 52 4566 159
 4017 80 4568 281
 4018 80 4569 303
 4019 60 4572 25
 4020 90 4584 63
 4021 82 4585 100
 4022 90
 4023 17
 4024 76
 4025 17
 4026 180
 4027 95
 4028 72
 4029 100
 4030 58
 4032 120
 4040 83
 4042 85
 4043 95
 4044 80
 4046 130
 4048 60
 4049 55
 4050 55
 4051 65
 4052 95
 4053 65
 4055 135
 4056 513
 4059 163
 4063 109
 4068 53
 4069 20
 4070 20
 4071 20
 4072 20
 4073 20
 4076 90

MORE FROM THE GENERAL AMBIT CATALOGUE RANGES:

Varicap tuning diodes for AM/FM/TV: 1-9 v AM tuning (Cr 15:1) from TOKO-
 KV1211 double matched 175p 26p vat
 KV1210 triple matched 245p 37p vat
 KV1215 triple snap-apart 245p 37p vat
 MVAM115 single 15v 105p 16p vat
 MVAM125 single 25v 105p 16p vat
 MVAM2 double 25v 148p 22p vat
 BB204/104 double FM 40p 6p vat
 BA102 single AFC etc 30p 4p vat
 BA121/TT210 single afc etc 30p 4p vat
 BB105B single UHF 40p 6p vat
PIN DIODES, BANDSWITCH
 BA479 PIN attenuator 35p 5p vat
 TDA1061 P-form atten. 95p 14p vat
 BA182 Bandswitch 21p 3p vat
 All RF semiconductor stocked in depth. Please ask for quantity pricing details.

TOP GRADE LEADS BY AEG: PRICES ARE EXC. VAT (add 15%)

512Z Red Green Yellow Orange
 5mm 14p 15p 20p 10p
 1mm 13p 15p 18p 19p
 2x5x15 17p 20p 20p 24p
FUTABA FLOURESCENT VACUUM DISPLAYS FOR CLOCKS etc
 5LT02 clock display (static drive) with AM/PM flags £9 + 1.35
 5LT03 DFM display for MSMS525 LSI counter £9.45 + 1.42 vat
 6LT06 5 digit DFM display (G1 AY58100) mpxed £9.75 + 1.42 vat

TOKO COILS, FILTERS, CHOKES, etc for AM/FM/TV comms-

TYPE Size: 5mm 7mm 10mm (please add VAT @15%)
 AM IF 55p 33p 30p Various for ICs, transistor etc.
 FM IF 55p 33p 33p Various for ICs, transistor etc.
 SW coils 33p Two impedance series
 OSC coils 55p 33p 33p For LW/MW/SW
 TV vif/iff 35p

Various coils in the range 20kHz to 300MHz - see TOKO catalogue

CERAMIC and MECHANICAL FILTERS (inc MURATA TYPES)
 CFT450B/CFT455C 60p; CFX014-180p; CFX4455C-85p
 CFT475C-60p; CFU407C-85p
 MURATA CFU45H and CFU455C ceramic block filters 1.95ea
 MURATA CFM455 series ladder filters, D, E, F, G, H bandwidths available now £20.15, £28.6kHz; E8.35 ea (metal encapsulated)
 SFD455B, SFD4705, SFD472B 85p ea
 CFM2 series mechanical elements types A,B,C,D (4-10kHz bandwidth) -65p ea. (As used in RCME feature)

MULTIPLEX/PILOT TONE FILTERS, FM IF FILTERS (see cat and)

CFSE10.7/SFE10.7 - stereo FM IF ceramic filters (sim FM4 etc) 50p
 CFSB10.7/SFE10.7M - mono bandwidth ceramic FM IF filters etc 70p
 SFE10.7M - ultra linear phase stereo ceramic IF filter 70p
 CD10.7 - 10.7MHz ceramic discriminator (for CA3089 etc) 70p

Current news: A PCB for the Mullard DC tone and volume control system is now available £3 + 0.45 VAT. HMOS PA modules for 60-100W - kit £14 + £2.10VAT, heatsink £4.10+0.61. FM radio control system crystals £3.75 pair inc VAT (Sept on). MK50366N: static drive clock/timer IC £3.78 + 0.57 VAT. 12kHz channel spacing 8 pole 10.7MHz XTAL filter by TOYO type H4402 £15.50 + £2.32VAT. A further updated pricelist is now available, and we would like to remind you that enquiries can only be answered if accompanied either by an official business letterhead, or an SAE. STOP PRESS: TOKO's new split-apart triple AM tuning diodes are in stock £2.45 + 37p VAT, (KV1215). SBL1 diode DBM 1.500MHz £4.25+0.64p.

Terms: CWO please. Account facilities for commercial customers OA. Postage 25p per order. Minimum credit invoice for account customers £10.00. Please follow instructions on VAT, which is usually shown as a separate amount. Overseas customers welcome - please allow for postage etc according to desired shipping method. Access facilities for credit purchases. Catalogues: Ambit. Part 1 45p. Part 2 50p 90p pair. TOKO Euro shortform 20p. Micrometals toroid cores 40p. All inc PP etc. Full data service described in pricelist supplements. Hours/phone: We are open from 9am - 7pm for phone calls. Callers from 10am to 7pm. Administrative enquiries 9am to 4.30pm please (not Saturdays). Saturday service 10am to 6pm.



AMBIT catalogues are guaranteed to contain the most up-to-date and best informed comment on modern developments and advances in the field of radio and audio. There is no competitive publication that even approaches the broad range of parts/information on modern techniques.
2 Gresham Road, Brentwood, Essex.
 TELEPHONE: 0277 216029

TRADE COMPONENTS

PAY A VISIT — THOUSANDS MORE ITEMS BELOW WHOLESALE PRICE. CALLERS PAY LESS ON MANY ITEMS AS PRICES INCLUDE POSTAGE. PRICES INCLUDE VAT AND ADDITIONAL DISCOUNT IN LIEU OF GUARANTEE. GOODS SENT AT CUSTOMERS RISKS UNLESS SUFFICIENT ADDED FOR REGISTRATION OR COMPENSATION FEE POST.

OFFERS CORRECT AT 1/11/79 APPLICABLE TO ORDERS RECEIVED DURING NOVEMBER

VALVE BASES

Printed circuit B/G	7p
Chassis B7-B7G	11p
Shrouded Chassis B7G-B8A	13p
B12A tube. Chassis B9A	13p
Speaker 6" x 4" 5 ohm ideal for car radio	£1.00
4 3/4" diam. 30 Ω	£1.75. 4" diam. 80
2 1/2" diam. 8 Ω	75p or 32
£1.07	
TAG STRIP—6-way 2 1/2p	5 x 50pF or 1000 +
9-way 4 1/2p Single 2p	300pF trimmers 35p

Car type panel lock and key 65p

Transformer 9V 4A £3.30

Aluminium Knobs for 1/4" shaft. Approx. 5/8" x 7/8" with indicator Pack of 5 95p

BOXES — Grey polystyrene 61 x 112 x 31mm, top secured by 4 self tapping screws 57p clear perspex sliding lid, 46 x 39 x 24 mm 10p

ABS, ribbed inside 5mm centres for P.C.B., brass corner inserts, screw down lid, 50 x 100 x 25mm orange 65p; 80 x 150 x 50mm black 97p; 109 x 185 x 60mm black £1.52.

DIECAST ALI superior heavy gauge with sealing gasket, approx 6 1/2" x 2 3/8" x 1 3/8" £1.55; 3 3/4" x 2 3/8" x 1 3/8" 99p.

VARIABLE CAMM PROGRAMMER 10, 12 or 15 pole 2 way, 50VAC motor — series with 1mfd, or 3k 10W or 15W pygmy bulb for mains operation. Ex equipment £3.10.

SWITCHES

Pole	Way	Type	
1	2	Flush Wall Wh. Rocker	35p
6	2	Slide	24p
2	1	Rotary Mains	14 1/2p
2	Alternating	Micro with roller	30p
2	2	Sub-Min Toggle	62p
2	1	Toggle	40p
1	2	Sub-Min Toggle	67p
2	Alternating	2A Mains Push (3/4" hole)	43p
1	3	Slide	10p

S.P.S.T. 10 amp 240v. white rocker switch with neon. 1" square flush panel fitting 39p

1 pole 2-way 10 amp oblong clip in mains rocker appliance switch 36p

Standard thumb-wheel switch 0-9 in 1248N or B.C.D. or Comp. 1242 also 2p co 85p

Standard Lever Key switch D.P.D.T. locking plus D.P.D.T. and S.P.S.T. Heavy Duty non latching 73p

1 pole 2-way Micro; button, roller, lever or hair-trigger 15p

Push to make 15p To break 17p

4-bank of 2PCO independent 40p

5-bank of 2x2PCO, 4PCO, 6PCO, interlock plus 2PCO independent 48p

6-bank of 4x4PCO+6PCO+2PCO interlocking. 58p

COMPUTER & AUDIO BOARDS/ASSEMBLIES

VARYING CONTENTS INCLUDE ZENER, GOLD BOND, SILICON, GERMANIUM, LOW AND HIGH POWER TRANSISTORS AND DIODES, HI STAB RESISTORS, CAPACITORS, ELECTROLYTICS, TRIMPOTS, POT CORES, CHOKES, INTEGRATED CIRCUITS, ETC.

3lb for £2.30 7lb for £4.30

1k horizontal preset with knob 10 for	40p
3" Tape Spools	5p
1" Terry Clips	5p
12 Volt Solenoid	40p

ENM Ltd. cased 7-digit counter 2 1/2 x 1 3/4 x 1 1/4" approx. 12V d.c. (48 a.c.) or mains £1.10

Auto charger for 12v Nicads, ex-new equipment £3.95

Miniature 0 to 5mA d.c. meter approx 7/8" diameter £1.25

RS Yellow Wander Plug Box of 12 40p

18 SWG multicore solder 3 1/2p foot

SAPHIRE STYLII. 10 different; dual and single point, current and hard to get types. My mix £1

RESISTORS

1 1/2-1 watt 1 1/2p 10 same value 10p

1 watt 1 1/2p

1 or 2% same price Up to 15W w/wound 10p, 10 same value 75p

RELAYS

RS/Alma reed relay, 1K12v or 3k Ω 18-30v d.c. coil, normally open 36p

12v d.p.c.o. heavy duty octal 600 Ω 4 p/co min sealed 75p. Base 10p. D.I.L. 3.7-12V S.P. £1.00

POTS

Wirewound 38p. Log or Lin rotary 22p, or slide 30p. With switch 40p, Dual 45p Dual switch 55p 1.5m Edgetype 10 for 40p.

Skeleton Presets

Slider, horizontal or vertical standard 5p or submin 4p

THERMISTORS and V.D.R.'s

CZ1/2/6/11/14. KR22. KT150. VA1005/6/8/1010/1033/4/7/8/9 1040/1053/5 1106/6/7/1074/6/7 1108/2/6/1091/6/7/8 1100/3/8/8602. Rod with spot blue/fawn/green. E299DDP120 / 218 / 224 / 338 / 340 / 350 / 352. YF020 E220ZZ/02 KR150 E23 glass bead YG150-S534 bead KB13 E299 DHP230, 116-121 401 (TH7, VA1104, OD10) R53 Glass All 7p each

JAP 4 gang min. sealed tuning condensers 40p

ELECTROLYTICS — Hundreds more in catalogue Value/Voltage

Tant Bead .22, 47/35v 6p. .1, 1/35v, 47/6.3v 8p. 22/20v, 3.3/16v 9p. 4.7/16v, 10/3v 10p. 3.3/35v 4.7/35v 12p. 10/2.5v 13p. 22/16v 16p.

Wire End

63v 2.2, 4.7, 10, 33, 5p. 2.5 3p. 22, 6p. 47, 7p. 220 8p. 100 9 1/2p. 470 17 1/2p. 1000 29p.

25v 6p, 6.4, 10, 12, 16, 22, 25, 30, 33, 40, 47, 50, 64 4p. 100, 150, 160, 330 6p. 220 7p. 250, 300, 470 8p. 1000 11 1/2p. 22/16, 10/50 4p. 100/10, 47/16 5p. 100/16, 100/35, 220/16 6p. 470/6.3, 470/16 8p. 1000/16 10p. 2200/10 20p. 4700/10 30p. 15/160 7p. CANS, 250/300, 45p. 300/450 90p. 100/275 14p. 2000/100 82p. 1000/100 70p. 8 + 8/450 9p. 10,000/16 50p.

RS 100-0-100 micro amp null indicator

Approx. 2" x 3/4" x 3/4" £1.85

INDICATORS

Bulgin D676 red, takes M.E.S. bulb 38p

12 volt, or Mains neon, red pushfit 23p

R.S.-Scale Print, pressure transfer sheet 12p

CAPACITORS: Ceramic up to .01 2p, to .1 5p, to .68 8p. Silvermica up to 5000PF 5p, to .01 21p. Poly, etc up to .1 2p, to .2 3p, to .47 5p, to .68 7p: .1, .22/900v 15p. .3/600v 4p. 1mFd up to 250v 10p. 2.2mFd up to 100v 14p. 4/16v 25p. 6.8/63, 25/50 19p. 8/20v 40p. CAN 1/350 12p. 8/660vac £2. 3/660vac £1.75. 5/150 70p.

Pulse Tube: 8-12kV, 10, 47, 56, 82, 320pF 2p each.

Hundreds of others in Catalogue

SONNENSCHNEIN/POWERSONIC DRI-FIT RECHARGEABLE SEALED GEL (Lead Antimony) BATTERY, 6V 1 amp.hr. (3 3/4" x 2" x 7/8") £2.70

6 amp. hr. (4 1/2" x 2" x 3") £4.25

Ex-equipment, little used.

CONNECTOR STRIP

Belling Lee L1469, 4 way polythene. 9p each

1 1/2 glass fuses 250 ma or 3 amp (box of 12) 20p

Bulgin 5mm Jack plug and switched socket (pair) 40p

Reed Switch 28mm body length 5p

PP9 Battery Leads 8p

Aluminium circuit tape, 1/4 x 36 yards—self adhesive. For window alarms, circuits, etc. 95p

TV MAINS DROPPERS

5 assorted multiple units for 45p

100pF air-spaced tuning capacitor £1.30

5 1/4" x 2 1/4" Speaker, ex-equipment 3 ohm 65p

2 Amp Suppression Choke 10p

3 x 2 1/2 x 1 1/2 PAXOLINE 5 for 35p

4 1/2 x 1 1/2 x 1 1/2 PAXOLINE 10 for 15p

Nylon clip on MES bulb holder 4p

VALVE RETAINER CLIP, adjustable 5 for 15p

Sub-miniature Transistor Transformer 35p

Valve type output transformer 90p

POT CORES with adjuster

LA2508-LA2519 43p per pair

16 Watt Power Amp. Module

35v 1A power required, giving 16 watt

RMS into 8 Ω £3.45

REGULATED TAPE MOTOR

Grundig 6V approx., 3" x 1 1/2", inc. shock absorbing carrier, or Jap 9V, 1 1/2" diam. £1.05

20mm chassis fuse holder 5p

Fane 8 ohm 3" sq. heavy duty communications speaker £1.60

RS neg. volt regulator 103, 306-099 (equiv. MPC900) 10A, 100 watt 4-30 volt. Adjustable sort circuit protection. Sacrifice at £2.00

ACOS DUST JOCKEY Automatic record cleaner £1.30

Digital count unit. Counts in steps of 1, 2, 5 or 10 with total limit switch (2 x D.I.L. BCD), reed relay remote output. Mains power supply, relay and delay unit. UNUSED. Displays on 2 Minित्रon. 7 segments sold separately. £5.60

AUDIO LEADS 3 pin din to open end, 1 1/2yd, twin screened, 45p

5 pin din 180° to 2-phono, 4ft., 70p

3 pole jack plug to tag ends, 4ft., 70p

RELAY 6 amp changeover. Mains coil 200v A.C. F.S.D. level Meter 1 1/2" x 1 1/2" £2.60

McMurdo 4 or 8 way plug and socket ex-equipment 50p

RELAY 6V Capacity 6V 450 m.a.h. at 10 hour rate. Ex-new equipment £3.75

"Makaswitch" 1p 10-way wafer 15p

Wood cased 8-12V buzzer £2.60

2.5A r.f. thermo-couple and meter 2 1/2" square £3.86

Crouzet 30-minute timer-programmer, multi-variable -contacts £7.80

ACOS DUST JOCKEY Automatic record cleaner £1.30

AUDIO LEADS 3 pin din to open end, 1 1/2yd, twin screened, 45p

5 pin din 180° to 2-phono, 4ft., 70p

3 pole jack plug to tag ends, 4ft., 70p

RELAY 6 amp changeover. Mains coil 200v A.C. F.S.D. level Meter 1 1/2" x 1 1/2" £2.60

McMurdo 4 or 8 way plug and socket ex-equipment 50p

RELAY 6V Capacity 6V 450 m.a.h. at 10 hour rate. Ex-new equipment £3.75

"Makaswitch" 1p 10-way wafer 15p

Wood cased 8-12V buzzer £2.60

2.5A r.f. thermo-couple and meter 2 1/2" square £3.86

BRIAN J. REED

161 ST. JOHNS HILL, BATTERSEA, LONDON SW11 1TQ


Open 10 a.m. till 7 p.m. Tuesday to Saturday. VAT receipts on request.

Terms: Payment with order Telephone: 01-223 5016

APEL POWER SUPPLIES

STABILIZED POWER SUPPLIES WITH ELECTRONIC SHORT CIRCUIT PROTECTION


AL.212 P

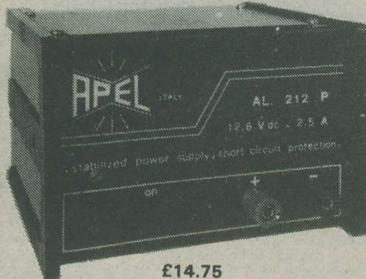

£14.75

INPUT VOLTAGE	220 V ac ± 10% 50-60 Hz
OUTPUT VOLTAGE RANGE	12,6 V dc
OUTPUT CURRENT MAX	2,5 Amp
LOAD REGULATION	<0,3% 0-2,2 Amp
RIPPLE	<5mV 2,2 Amp
DIMENSIONS (mm)	W140 × H90 × D140
WEIGHT	1,490 Kg.

AL.315 P

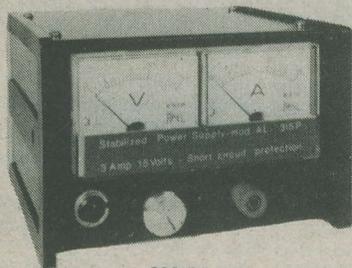

£29.50

INPUT VOLTAGE	220 V ac ± 10% 50-60 Hz
OUTPUT VOLTAGE RANGE	1,7-15 V. dc
LOAD REGULATION	<0,2% 0-2,8 Amp
DIMENSIONS (mm)	W140 × H90 × D155
RIPPLE	3mV 2,8 Amp
WEIGHT	2,330 Kg.

AL.330 P



£46.50

INPUT VOLTAGE	220 V ac ± 10% 50-60 Hz
OUTPUT VOLTAGE RANGE	3,4-30 V. dc
OUTPUT CURRENT RANGE MAX	3 Amp
LOAD REGULATION	< 5% 0-2,8 Amp
RIPPLE	10mV 2,8 Amp
DIMENSIONS (mm)	W270 × H90 × D155
WEIGHT	4,250 Kg.

STOCKISTS

Alpha Sound Service,
50 Stuart Road, Waterloo, Liverpool L22 4QT.
England.

Anson Electronics,
1133 Hessle High Road, Hull, England.

Amateur Radio Shop,
13 Chapel Hill, Huddersfield, HD1 3ED.
England.

Brent Electronics,
Seaview Street, Cleethorpes,
Lincolnshire, England.

J. Birkett,
26 The Strait, Lincoln, England.

Bradford Consultants Limited,
25 Regent Parade, Harrogate,
Yorkshire, England.

F. Brown & Co. Ltd.,
44/46 George IV Bridge Street,
Edinburgh, Scotland.

N. R. Bardwell Limited,
Sellers Street, Sheffield, England.

Casey Brothers,
235 Boundary Road,
"Saint Helens,"
Lancashire, England.

Electronic Services Limited,
33 City Arcade, Coventry CU11 HX, England.

A. Fanthorpe Limited,
6 Hepworth Arcade, Silver Street,
Hull, England.

G. W. M. Radio,
Portland Road, Worthing, Sussex.

Leeds Amateur Radio,
27 Cookridge Street,
Leeds LS2 3AG, England.

Target Electric Limited
16 Cherry Lane, Bristol, England.

New Cross Radio,
6 Oldham Road, Manchester,
England.

Progressive Radio,
93 Dale Street, Liverpool L2 2JD.
England.

R. E. Pitt Electrical Services Limited,
60/64 Bath Buildings, Mont Pelier,
Bristol, England.

Peats Electronics,
Parnell Street, Dublin.

R. F. Potts,
68 Bobbington Lane, Derby, England.

Brian A. Pearson Limited,
66 Moncur Street, Glasgow, Scotland.

R M E Supplies Limited,
143 Stockwell Street, Glasgow, Scotland.

Stephan James Limited,
Warrington Road, Leigh, Lancashire.

Stewarts Radio,
4 Chance Street, Blackpool, England.

The Radio Shop,
16 Cherry Lane, Bristol BS 3NG,
England.

Q. C. Trading,
1 St. Micheals Terrace, Woodgreen M22 4FT,
England.

AL.1 P5



£78.00

INPUT VOLTAGE	220 ± 10% 50 Hz
OUTPUT VOLTAGE RANGE	1 + 15 V. dc
OUTPUT CURRENT MAX	5 Amp
LOAD REGULATION	< 0,1% 0-4,5 Amp
RIPPLE	< 2mV 4,5 Amp
DIMENSIONS (mm)	W210 × H155 × D250
WEIGHT	5,100 Kg.

AL.212 PS



£18.00

INPUT VOLTAGE	220 V ac ± 10% 50-60 Hz
OUTPUT VOLTAGE RANGE	12,6 V dc
OUTPUT CURRENT MAX	2,5 Amp
LOAD REGULATION	<0,3% 0-2,2 Amp
RIPPLE	<5mV 2,2 Amp
DIMENSIONS (mm)	W140 × H90 × D140
WEIGHT	1,490 Kg.
AMPEROMETER	

AL.315 P2



£54.00

INPUT VOLTAGE	220 V ac ± 10% 50-60 Hz
OUTPUT VOLTAGE RANGE	± 1,7 + 15 V dc
OUTPUT CURRENT RANGE MAX	3 Amp
LOAD REGULATION	< 0,2% 0-2,8 Amp
RIPPLE	< 3mV 2,8 Amp
DIMENSIONS (mm)	W270 × H90 × D155
WEIGHT	4,140 Kg.

Stan Willets Limited,
37 High Street, West Bromwich.

M/S Waltons,
55a Worcester Street,
Wolverhampton WV2 4LL, England.

Distributed in the UK.
and Ireland by:

PEAT'S WHOLESALE LTD.

Chapel Lane, Parnell St, Dublin 1, Ireland.

PHONE 741746-740678-722845. TELEX 31787.

STEVENSON

Electronic Components

CMOS				
4020	50p	4050	25p	
4022	50p	4060	80p	
4023	13p	4066	30p	
4024	40p	4068	13p	
4001	13p	4025	13p	4069 13p
4002	13p	4026	90p	4070 13p
4007	13p	4027	28p	4071 13p
4009	30p	4028	45p	4072 13p
4011	13p	4029	50p	4081 13p
4012	13p	4040	55p	4093 36p
4013	28p	4041	55p	4510 60p
4015	50p	4042	55p	4511 60p
4016	28p	4043	50p	4518 65p
4017	47p	4046	90p	4520 60p
4018	55p	4049	25p	4528 60p

FULL DETAILS IN CATALOGUE!

TTL				
7473	20p	74141	55p	
7474	22p	74145	55p	
7475	25p	74148	90p	
7476	20p	74150	55p	
7485	55p	74151	40p	
7486	20p	74154	65p	
7489	13p	74157	40p	
7490	25p	74164	55p	
7492	30p	74165	55p	
7493	25p	74170	100p	
7494	45p	74174	55p	
7495	35p	74177	50p	
7496	45p	74190	50p	
74121	25p	74191	50p	
74122	35p	74192	50p	
74123	38p	74193	50p	
74125	35p	74196	50p	
74126	35p	74197	50p	
74132	45p	74199	90p	

OPTO				
LED's	0.125in	0.2in	each	100+
Red	TIL209	TIL220	9p	7.5p
Green	TIL211	TIL221	13p	12p
Yellow	TIL213	TIL223	13p	12p
Clips	3p	3p		
DISPLAYS				
DL704	0.3 in CC		130p	120p
DL707	0.3 in CA		130p	120p
FND500	0.5 in CC		100p	80p

SKTS					
8pin	8p	18pin	14p	24pin	18p
14pin	10p	20pin	16p	28pin	22p
16pin	11p	22pin	17p	40pin	32p
3 lead TO18 or TO5 socket. 10p each					
Soldercon pins: 100:50p 1000:370p					

PCBS				
VEROBOARD				
Size in.	0.1in	0.15in.	Vero	Cutter 80p.
25 x 1	14p	14p		
2.5 x 3.75	45p	45p		
2.5 x 5	54p	54p	Pin insertion tool 108p	
3.75 x 5	64p	64p		
3.75 x 17	205p	185p		
Single sided pins per 100 40p 40p				
Top quality fibre glass copper board. Single sided. Size 203 x 95mm. 60p each.				
'Dalo' pins. 75p each.				
Five mixed sheets of Alfac. 145p per pack				

RESISTORS				
Carbon film resistors. High stability, low noise 5%.				
E12 series. 4.7 ohms to 10M. Any mix.				
0.25W	each	100+	1000+	
0.5W	1p	0.9p	0.8p	
	1.5p	1.2p	1p	
Special development packs consisting of 10 of each value from 4.7 ohms to 1 Meg-ohm (650 res) 0.5W £7.50. 0.25W £5.70.				
METAL FILM RESISTORS				
Very high stability, low noise rated at 1/2W 1%. Available from 51ohms to 330k in E24 series. Any mix.				
0.25W	each	100+	1000+	
	4p	3.5p	3.2p	

PLEASE WRITE FOR YOUR FREE COPY OF OUR 80 PAGE CATALOGUE OF COMPONENTS. CONTAINS OVER 2500 STOCK ITEMS.

LINEAR				
LF356	80p	NE531	98p	
LM301AN	26p	NE555	23p	
LM308	60p	NE556	60p	
LM318N	75p	NE567	100p	
LM324	45p	RC4136	100p	
LM339	45p	SN76477	230p	
LM378	230p	TB8000	70p	
LM379S	410p	TB810S	100p	
LM380	75p	TDA1022	620p	
LM3900	50p	TL081	45p	
LM3909	65p	TL084	125p	
LM3911	100p	ZN14	80p	
MC1458	32p	ZN425E	390p	
MM57160	590p	ZN1034E	200p	

TRANSISTORS					
AC127	17p	BCY72	14p	ZTX500	16p
AC128	16p	BD131	35p	2N697	12p
AC176	18p	BD132	35p	2N3053	18p
AD161	38p	BD139	35p	2N3054	50p
AD162	38p	BFY40	35p	2N3442	135p
BC107	8p	BFY50	15p	2N3702	8p
BC108	8p	BFY51	15p	2N3703	8p
BC108C	10p	BFY52	15p	2N3704	8p
BC109	8p	MJ2955	98p	2N3705	9p
BC109C	10p	MPSA06	20p	2N3706	9p
BC147	7p	MPSA56	20p	2N3707	9p
BC148	7p	TIP29C	60p	2N3708	8p
BC177	14p	TIP30C	70p	2N3820	44p
BC178	14p	TIP31C	65p	2N3904	8p
BC179	14p	TIP32C	80p	2N3905	8p
BC182	10p	TIP2955	65p	2N3906	8p
BC182L	10p	TIP3055	55p	2N4058	12p
BC184	10p	ZTX107	14p	2N5457	32p
BC184L	10p	ZTX108	14p	2N5459	32p
BC212	10p	ZTX300	16p	2N5777	50p
BC212L	10p				
BC214	10p				
BC214L	10p				
BC477	19p	1N914	3p	1N4006	6p
BC478	19p	1N4001	4p	1N5401	13p
BC548	10p	1N4002	4p	BZ88 ser.	8p
BCY70	14p	ITT Full spec. product.			
BCY71	14p	1N4148	-£1.40/100. £11/1000		

CAPACITORS				
TANTALUM BEAD				
0.1, 0.15, 0.22, 0.33, 0.47, 0.68, 1 & 2.2uF @ 35V				each
4.7, 6.8, 10uF @ 25V				8p
22 @ 16V, 47 @ 6V, 100 @ 3V				13p
				16p
MYLAR FILM				
0.001, 0.01, 0.022, 0.033, 0.047, 0.068, 0.1				3p
				4p
POLYESTER				
Mullard C280 series				
0.01, 0.015, 0.022, 0.033, 0.047, 0.068, 0.1				5p
0.15, 0.22				7p
0.33, 0.47				10p
0.68				14p
1.0uF				17p
CERAMIC				
Plate type 50V. Available in E12 series from 22pF to 1000pF and E6 series from 1500pF to 0.047uF				2p
RADIAL LEAD ELECTROLYTIC				
63V 0.47 1.0 2.2 4.7 10				5p
				7p
				13p
				20p
25V 10 22 33 47				5p
				8p
				10p
				15p
				23p

CONNECTORS				
JACK PLUGS AND SOCKETS				
	screened	unscreened	socket	
2.5mm	9p	13p	7p	
3.5mm	9p	14p	8p	
Standard	16p	30p	15p	
Stereo	23p	36p	18p	
DIN PLUGS AND SOCKETS				
	plug	chassis socket	line socket	
2pin	7p	7p	7p	
3pin	11p	9p	14p	
5pin 180°	11p	10p	14p	
5pin 240°	13p	10p	16p	
1mm PLUGS AND SOCKETS				
Suitable for low voltage circuits. Red & black. Plugs. 6p each Sockets: 7p each.				
4mm PLUGS AND SOCKETS				
Available in blue, black, green, brown, red, white and yellow. Plugs: 11p each Sockets: 12p each				
PHONO PLUGS AND SOCKETS				
Insulated plug in red or black				9p
Screened plug				13p
Single socket	7p	Double socket		10p

SOLDERING IRONS
ANTEX X25 (25W) or ANTEX CX (17W) 390p each
Reel of solder (39.6M) 240p each

LOUDSPEAKERS
56mm dia. 8ohms. 70p 64mm dia. 64ohms. 75p
64mm dia. 8ohms. 75p 70mm dia. 8ohms. 100p
Magnetic earpiece including 2.5 or 3.5mm plug. 15p each
Crystl earpiece including 3.5mm plug. 30p each

SWITCHES
Subminiature toggle. SPDT 70p. DPDT 80p.
Standard toggle. SPST 34p. DPDT 48p.

Slide switches (DPDT) miniature or standard 15p.
Push to make switch. 15p. Push to break switch. 20p.
Wavechange switches: 1P12W, 2P6W, 3P4W, 4P3W. 43p

CONTROL KNOBS
Ideal for use on mixers etc. Push on type with black base and marked position line. Cap available in red, blue, green, grey, yellow & black. 14p.

MISCELLANEOUS
Connection cable available in single or stranded packs of eight colours. Single Stranded
8 metre pack 18p 18p
40 metre pack 85p 80p

BATTERY CLIPS
Battery clips for PP3 with lead. 6p each.
Battery clips for PP9 with lead. 10p each.
Miniature crocodile clips in red or black. 8p each.
Red or black probe clips. 20p each.
Murata Ultrasonic Transducers. 180p each. 350p pair.

PANEL METERS
High quality 2" wide view meters. Zero adjustment. Back illumination wiring. Available in 50 uA, 100 uA, 500 uA, 1mA, 100 mA, 500 mA, 1A. £4.75 ea. VU meter similar style. £1.40 ea.

SLIDE POTENTIOMETERS
Good quality 60mm travel slider with 80mm fixing centres. Available from 5k - 500K in log and linear. 55p each. Suitable black knobs 6p ea. Coloured knobs 10p ea.

We now offer one of the widest ranges of components at the most competitive prices in the U.K. See catalogue for full details. We welcome callers at our shop in College Rd, Bromley, from Mon-Sat, 9am-6pm (8pm on Weds and Fridays). Special offers always available. We also provide an express telephone order service. Orders received before 5pm are shipped same day. Contact our sales office now with your requirements. TELEPHONE: 01-464 2951/5770.

Quantity discounts on any mix TTL, CMOS, 74LS and Linear circuits. 100+ 10%, 1000+ 15%. Prices VAT inclusive. Please add 30p for carriage. All prices valid to April 1980. Official orders welcome.



BARCLAYCARD & ACCESS WELCOME

ORDERS DESPATCHED BY RETURN POST

Mail orders to: STEVENSON (Dept RE)

76 College Road, Bromley, Kent BR1 1DE.

ALL PRICES INCLUDE 15% V.A.T.



CMOS OSCILLATORS

by
R. J. Caborn

Using CMOS logic gates as pulse generators.

CMOS logic circuits frequently require low frequency oscillators or pulse generators, these being used for such purposes as producing clock pulses or causing light-emitting diodes to attract attention by flashing on and off. It then becomes desirable to use CMOS logic gates themselves in the oscillator circuit.

The amplification required for oscillation may be provided by two CMOS inverters in tandem, as shown in Fig. 1(a). The output is in phase with the input, and if the output is coupled back to the input by way of a frequency controlling RC network, an oscillator will result. NAND gates with 2 inputs (as in the CD4011) and 2-inputs NOR gates (as in the CD4001) are usually easier to obtain than CMOS inverters, and they can be used as inverters by connecting their inputs together. Fig. 1(b) shows two NAND gates connected as inverters, whilst Fig. 1(c) shows two NOR gates similarly connected.

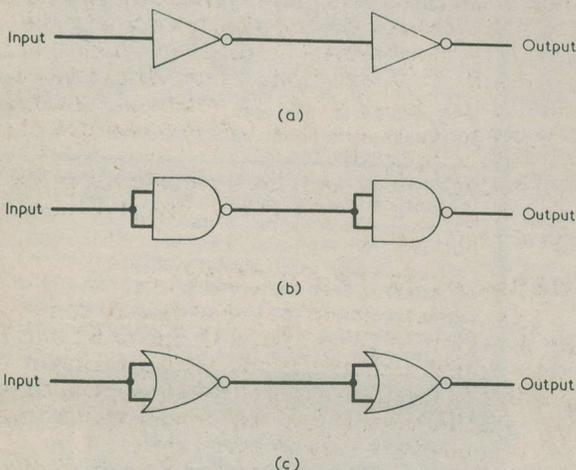


Fig. 1(a). Two CMOS inverters connected in tandem. The output is in phase with the input (b). NAND gates may be employed to act as inverters (c). The inverters may also consist of NOR gates

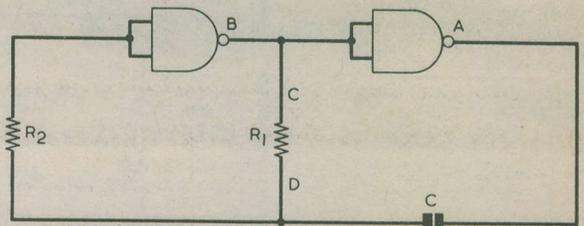


Fig. 2. Recommended CMOS oscillator circuit. NAND gates are shown here, but the circuit will function equally well with inverters or NOR gates

RC NETWORK

Several CMOS oscillator circuits with RC frequency control have appeared in this and other journals, but what is possibly the best for low frequency and audio frequency applications is that shown in Fig. 2. Before discussing how this circuit functions it is necessary to briefly consider two aspects of a CMOS inverter, or of a NAND gate or a NOR gate connected as an inverter.

Fig. 3 gives a transfer characteristic for a CMOS inverter at a supply voltage of 10 volts. The output voltage stays at 10 volts for an input voltage change of zero to about 2 volts, after which it starts to fall. At the other end of the curve, the output voltage stays at zero for an input voltage between about 8 and 10 volts. The curve of Fig. 3 is typical only, and the device will still be within specification if the output commences to fall at any input between 1 and 3 volts, or to rise above zero level at any input between 7 and 9 volts. This spread means that frequency calculations for an RC controlled CMOS oscillator can only be of an approximate nature.

The second aspect of a CMOS inverter which has to be considered is the presence of the "hidden" protection diodes at each gate input. The normal

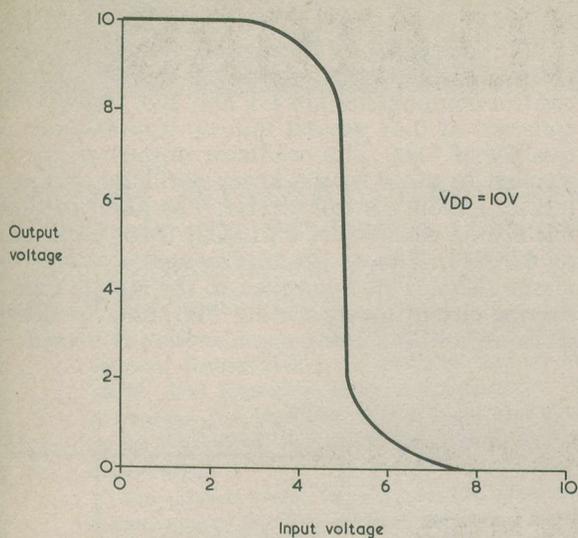


Fig. 3. Typical transfer characteristic for a CMOS inverter

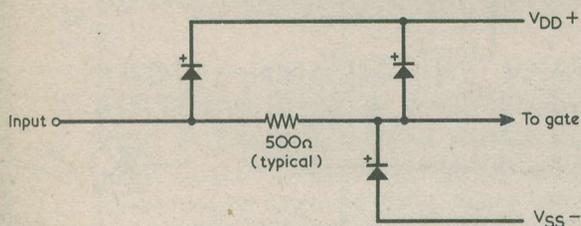


Fig. 4. CMOS logic gates have diode input protection circuits

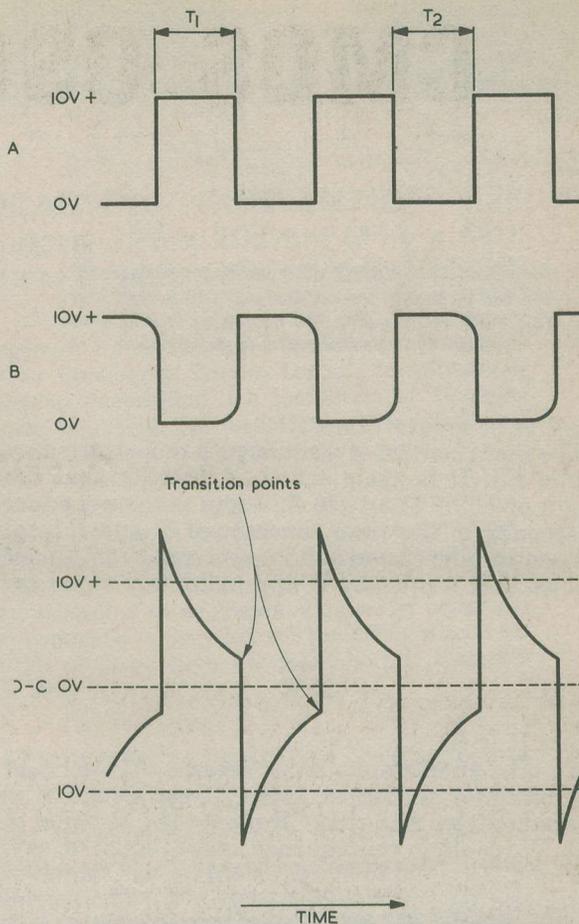


Fig. 5. Waveforms appearing in the oscillator circuit of Fig. 2. The bottom waveform shows the voltage at point D with respect to point C

gate input protection circuit is shown in Fig. 4, and the diodes conduct to protect the gate if the input is taken more than 0.6 volt positive of the positive rail, or more than 0.6 volt negative of the negative rail.

Representative curves for the oscillator of Fig. 2 are given in Fig. 5, the upper two curves showing the voltages at points A and B respectively. A 10 volt supply is assumed. The third curve shows the voltage at point D with respect to point C. If we commence our examination at an instant half-way along the T1 section of the curves, we have point A high and point B low. Capacitor C in Fig. 2 is discharging into R1, and the voltage at its left-hand terminal is applied to the input of the left-hand inverter via R2.

As the input of the left-hand inverter goes more and more negative it reaches the curved section of the inverter transfer characteristic, and the inverter output, at point B, commences to go positive. It continues to go positive until it arrives at the curved section of the transfer characteristic of the right-hand inverter, whereupon both inverters become capable of linear amplification. There follows a very rapid changeover, and it results in point A going low and point B going high.

The changeover starts at the "transition point" in the bottom waveform of Fig. 5, at which point the left-hand terminal of capacitor C is negative of

its right-hand terminal. When point A goes low, the left-hand terminal of the capacitor is then taken *negative* of the negative supply rail by, typically, about half the supply voltage. At the start of the next half-cycle, therefore, the capacitor is discharging both through R1 and through R2 and the appropriate input protection diode (or diodes) of the left-hand inverter input. The discharge path through R2 ceases when the left-hand terminal of the capacitor is less than 0.6 volt negative of the negative supply rail.

The cycles then continue as illustrated in Fig. 5, each half-cycle being a mirror image of the half-cycle preceding it.

OSCILLATOR FREQUENCY

The oscillator frequency is obviously controlled by the values of the capacitor C, and of R1 and R2. Since transfer characteristic spread makes it impossible to calculate oscillator frequency accurately, simplifications can be made which make calculations very easy to carry out.

The range of suitable values in R1 and R2 can lie between the limits of some 10kΩ and 1MΩ. If R2 is given a value which is equal to or greater than R1 it is found in practice that it has only a small effect on oscillator frequency, and its presence can be ignored. So the final step in calculating component values is simply to remember that R2 must be

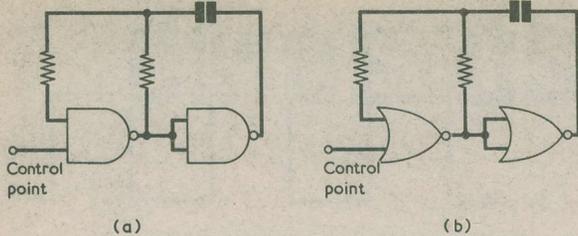


Fig. 6(a). This NAND gate oscillator may be inhibited by taking the control point to a logic low
 (b). With NOR gates the oscillator is inhibited when the control point is taken high

equal to or greater than R1.

The main control of frequency is then exerted by C and R1. It is again found in practice that the length of T1 or T2 in Fig. 5 is approximately equal in seconds to the time constant of C and R1 expressed in microfarads and megohms. From this it follows that frequency is approximately equal to

$$\frac{1}{2CR}$$

where R is R1.

To take an example, let us assume that we want the oscillator to run at 10Hz. If the equation is worked out, we find that CR must then be equal to 0.05. We could in consequence have C equal to, say, 1μF and R1 equal to 50kΩ (0.05MΩ), or C equal to 0.1μF and R1 equal to 500kΩ (0.5MΩ). The second choice would be the better because an 0.1μF capacitor is usually cheaper and less bulky than a 1μF capacitor. Since we are working approximately only, R1 could be 470kΩ. The remaining step is merely to make R2 of Fig. 2 470kΩ or, say, 1MΩ.

Where a frequency is required more precisely, the values calculated as just described make a useful starting-off point. The value of R1 can then be finally trimmed until the required oscillator frequency is given.

INHIBITING

If the oscillator inverters consist of NAND gates or NOR gates, the oscillator can be readily inhibited or enabled. In the circuit shown in Fig. 6(a), which employs NAND gates, one of the inputs of the left-hand gate is taken to a control point. The oscillator will only run if the control input is taken to a high logic level. The oscillator is inhibited if the control input is taken low.

The reverse occurs with the two NOR gates of

Fig. 6(b). In this case the oscillator is enabled when the control input is low and is inhibited when the control input is high.

A simple 1-second bleeper circuit is given in Fig. 7. In this diagram the upper oscillator frequency control components are C1 and R2, giving a time constant of 0.47 second and an approximate frequency of 1Hz. The oscillator output at pin 4 is applied to pin 8 of the lower oscillator, giving an inhibit-enable control at 1Hz. The lower oscillator has a time constant of 0.01 (C2) times 0.047 (R4), or 0.00047. The oscillator frequency is therefore about 1kHz. This is applied to the simple speaker driving circuit incorporating TR1, and the bleeper gives an audible 1kHz signal which is present for

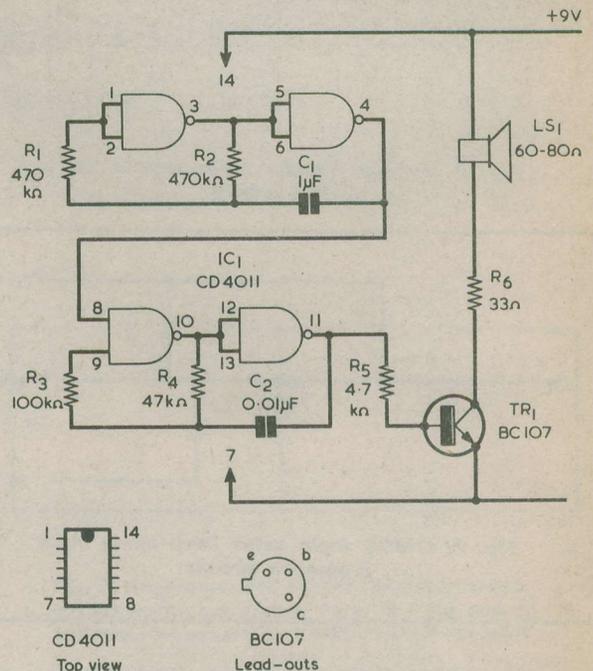


Fig. 7. A 1-second bleeper circuit incorporating a CD4011. All the resistors may be 1/2 watt 5%. The function of R6 is merely to limit collector current in TR1

about 0.5 second and absent for about another 0.5 second in each cycle. If the bleeper is required to give pulses at almost exactly 1Hz, R2 may be replaced by a 390kΩ resistor in series with a 220kΩ pre-set potentiometer. The potentiometer is then set up as accurately as possible for 1 second operation.

BACK NUMBERS

For the benefit of new readers we would draw attention to our back number service.

We retain past issues for a period of two years and we can, occasionally, supply copies more than two years old. The cost is 65p, inclusive of postage and packing.

Before undertaking any constructional project described in a back issue, it must be borne in mind that components readily available at the time of publication may no longer be so.

RECENT PUBLICATIONS



7TH INTERNATIONAL BROADCASTING CONVENTION (IEE Conference Publication 166). 364 pages, 295 x 205mm (11½ x 8in). Published by the Institution of Electrical Engineers. Price, U.K. £15.00, overseas £18.50.

This book comprises 82 technical papers presented by leading engineers at the 7th International Broadcasting Convention held at Wembley Conference Centre, London, in September 1978. The sponsors were the Electronic Engineering Association, the Institution of Electrical Engineers, the Institute of Electrical and Electronics Engineers, the Institution of Electronic and Radio Engineers, the Royal Television Society and the Society of Motion Picture and Television Engineers.

The papers cover virtually all technical aspects of current and projected radio and television broadcasting, and the authors represent bodies based not only in the U.K. but also in the U.S.A., Canada, Japan, Australia, Federal Republic of Germany, Republic of Ireland, Republic of South Africa, Denmark, the Netherlands, Belgium and Italy.

Although this notice has been subject to delay, the value to engineers engaged in advanced transmission development work of the information contained in the book still remains vastly in excess of the charge made for it. The book may be obtained from the Institution of Electrical Engineers, Marketing Department, Station House, Hitchin, Hertfordshire, SG5 1RJ.

RADIO AMATEURS' EXAMINATION MANUAL, EIGHTH EDITION. By G. L. Benbow, G3HB. 120 pages, 248 x 184mm (9½ x 7in). Published by the Radio Society of Great Britain. Price £1.85.

The trend in technical examination these days is towards multiple-choice questions with which a correct answer has to be picked from a number of alternatives. This approach certainly makes the job of examination paper markers considerably easier but, since the person sitting the examination is presented with one answer among several which has to be correct, the examination can hardly be as searching as the older type in which the candidate faced a blank piece of paper. In the same way that Napoleon preferred officers who were lucky our institutes are apparently beginning to favour examinees who also possess that attribute.

At any event, the Radio Amateurs' Examination has now changed over to multiple-choice questions and this fact, combined with alterations in the R.A.E. syllabus, has caused the appearance of this new 1979 edition of "Radio Amateurs' Examination Manual". As with all R.S.G.B. publications which this reviewer has seen, presentation of text and diagrams is excellent. The book commences with the procedure of becoming a radio amateur transmitter and then deals with the technical information which the R.A.E. applicant will need to know. There are four appendices, of which the last gives two practice R.A.E. multiple-choice question papers with, on the final page of the book, correct answers.

Apart from its value to budding radio amateurs, most of the volume forms a useful textbook in its own right. If desired, "Radio Amateurs' Examination Handbook" may be obtained direct from the Radio Society of Great Britain, 35 Doughty Street, London WC1N 2AE, at £2.16 including post and packing.

"HOW IT WORKS" – TELEVISION. By David Carey. 52 pages, 170 x 115mm. (6¾ x 4½in). Published by Ladybird Books Ltd. Price 30p.

To attempt in some 6,000 words to explain the manner in which television works, and to include in those 6,000 words accurate descriptions of scanning, transmission and reception, audio detection, amplitude modulation, studio practice, O.B. practice and colour reproduction is a challenge to daunt any technical journalist. David Carey succeeds in meeting the challenge and, what is more, presents his text in a manner which can be understood by the children for whom Ladybird Books are, presumably, mainly produced. The colour illustrations by B. H. Robinson assist considerably.

What is primarily to be commended is the fact that the text does not gloss over or give misleading short-cuts with technicalities but presents these accurately. The book is curiously dated in several places, as in the references to "Light", "Home" and "Third" on page 35, and to 405 lines on page 32, but this does not detract overmuch from its value. The book will certainly be genuinely instructive for any youngster who wishes to find out how the television picture appears on his domestic screen.


EDUCATIONAL SOLAR CELL FROM FERRANTI

Ferranti Electronics Limited have developed and produced a Silicon Solar Cell specifically for educational use.

The cell, designated the ESC3 series, is 3ins. in diameter and is capable of producing 0.9A at 0.5V under good sunlight conditions. Physical protection is provided by a tough moulded case and by a Fresnel lens which also acts as a light collector. Power take off is from metal pins on the rear of the case. Accidental short circuiting of the output will not damage the cell, and any number of cells can be arranged in series/parallel combinations to provide increased output values.

In addition to providing an educational aid for schools, colleges and universities it can provide the DIY enthusiast with a power source for operating functional models and electro/mechanical devices.

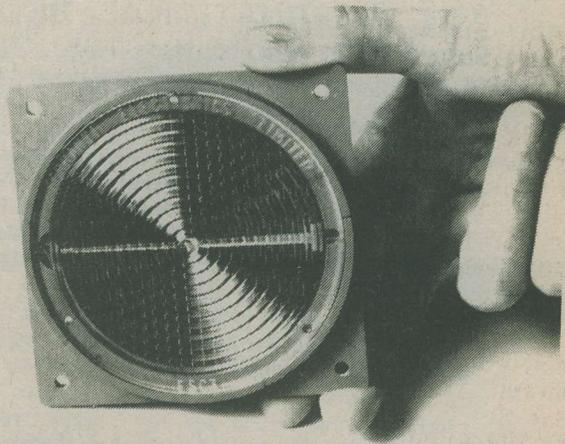Further information can be obtained on application to: Ferranti Electronics Limited, Fields New Road, Chadderton, Oldham, Lancs, OL9 8NP.



The Ferranti ESC3 Solar Cell which will produce 0.9A at 0.5V under good sunlight conditions. Ferranti Electronics Limited have developed the cell specifically for educational use, although there are obvious DIY applications

NEW INDUSTRY LINKED DEGREE COURSE

A new 4½ year degree course in Electronic/Electrical Engineering has been devised jointly by Bath University and GEC-Marconi Electronics Limited. The course covers a broad spectrum of electronic/electrical engineering and yet allows for specialised study to a greater than normal depth. It is intended for students of high calibre and will lead to a Master of Engineering degree (M.Eng).

Bath University already has an excellent reputation for its electronic and electrical degree courses

and always draws a very high level of candidates for them. The University has entered enthusiastically into the joint study which also has the support of the Engineering Industries Training Board in the form of a grant.

The course will start in September 1980. Applications to enter the course should be made to the School of Electrical Engineering, Bath University, Claverton Down, Bath, from where full details may be obtained.

TWO NEW DIGITAL MULTI-METERS FROM LASCAR

Lascar Electronics, the Essex based manufacturers of Digital Panel Meters And Counters have moved to larger premises in

Basildon.

At the same time two new digital multi-meters have been introduced. Both have LCD read-outs for clarity

and long battery life, and are claimed to be considerably lower cost than imported products of similar specification.

The LMM-100 is suitable for field or bench use, has 25 different ranges, a basic accuracy of 0.1% and is priced at £69.95 + VAT.

The LMM-200 is a compact hand-held instrument, with 15 different ranges, a basic accuracy of 0.5% and a 200 hour battery life. It is priced at £34.95 + VAT and should have wide appeal in many different applications.

Another ten instruments will be introduced over the next year. Eventually the range will include frequency counters, counter-timers, thermometers and other general purpose instruments. All will feature LCD read-outs for extended battery life and high portability.

Lascar Electronics are now at Unit 1, Thomasin Road, Burnt Mills Industrial Estate Basildon, Essex.



COMMENT

NEW DC TURNTABLE FOR THE PROFESSIONAL USER

Lee Engineering Limited of Napier House, Bridge Street, Walton-on-Thames, Surrey KT12 1AP have introduced into the UK the QRK Electronics GALAXY, a new DC Turntable designed for the professional user. It has a D.C. Motor with an electronic speed control which provides for plus or minus 10% speed variation on both 33 $\frac{1}{3}$ and 45 RPM. The turntable which is instant starting, provides for slip cueing without a loss in speed and it has back cueing with no drag.

Direct speed readout on LED's of the RPM is located on the front panel. Switching is digital with remote start/stop for operator convenience. Bob Sidwell, President of QRK of Fresno, California, says this is the first new turntable designed and manufactured for the professional user in the U.S.



since the original outer rim drive table which QRK introduced in 1944.

The turntable costs approximately £350.00.

FIRST UK '3-CHANNEL' SURROUND-SOUND BROADCAST

The first experimental transmissions of an improved stereo-compatible system of 'surround-sound' broadcasting developed by IBA engineers have been made on the Independent Local Radio station 'Radio Victory' at Portsmouth.

On Sunday, September 23, 1979 a two-hour concert recorded by IBA and Radio Victory engineers at Chichester Cathedral last July was broadcast in surround-sound on Radio Victory's VHF/FM service on 95.0MHz.

The surround-sound system uses a 3-channel matrix transmission system that has been developed at the IBA engineering centre at Crawley Court, Winchester to improve stereo-compatibility beyond that found possible with '2-channel' and '2 $\frac{1}{2}$ -channel' systems.

These experiments are part of an IBA investigation into surround-sound techniques with particular reference to the 'ambisonics' techniques of the National Research Development Corporation.

Continuing IBA work has underlined the advantages of a full '3-channel' system using a new IBA matrix, particularly in respect of the excellent compatibility for listeners using conventional mono or stereo equipment. The penalties imposed by such a system may be a slight reduction of coverage area and non-compatibility with the earlier 'surround-sound' systems.

IBA engineers stress that these '3-channel' experiments are not yet at a stage where it is possible to recommend a 'surround-sound' standard for national or international use.

Readers will only be too well aware, from their own experience, how costs are rising in all directions which, of course, also applies to this magazine and we regret that, with this issue our cover price has had to be increased by 5p. We know that our high standards are greatly valued and we shall continue to maintain them.

We have in the pipeline many highly interesting and worthwhile projects which will continue to make this magazine a 'must' for so many.

LONG LIVE SHORT WAVE

Rather belatedly, we give news of a record, entitled as above, produced by Mitch Murray, one of this country's leading songwriters and record producers.

On side one, after some introductory music from "Toys for Big Boys", one of Mitch Murray's songs, there follows an introduction and information on frequencies, propagation and the Radio Spectrum. This is succeeded by identification of Facsimile Telegraphy, RTTY, Slow Scan etc. Satellites, Decoding Single Side Band, Receivers, Aerials are among other topics dealt with. There is also a talk by Henry Hatch, of BBC World Radio Club fame, on the DX hobby.

Side two consists entirely of station identifications, more than thirty of them from Australia's "Waltzing Matilda" to Voice of America's "Yankee Doodle Dandy".

This unique LP is a first class introduction to the DX hobby and is a useful accessory for SWL enthusiasts. The record is priced at £3.50, inclusive of postage, and is obtainable from Trans-Island Productions Ltd., P.O. Box 24, Douglas, Isle of Man.



"Sir, according to my 'light charge' alarm unit, there's a brigade of horsemen coming up the valley."

SUGGESTED CIRCUIT

AMPLIFIER CLIPPING MONITOR

By G. A. French

Whilst solid-state a.f. amplifiers have many practical advantages when compared with valve amplifiers, they tend to suffer from one single disadvantage. This disadvantage arises when the amplifier goes into overload. If a valve amplifier overloads the resultant distortion increases gradually, whereas overload in a solid-state amplifier results in a very sharp rise in distortion which is, also, subjectively unpleasant. Solid-state a.f. amplifiers almost always employ a totem-pole output stage and the sudden increase in distortion arises when the positive and negative output voltage swings become too large to be handled by the output transistors. The result is that signal voltage peaks become flattened, and the effect is referred to as "clipping".

Due to the widely varying amplitude of most types of music it is possible for a solid-state amplifier to be set up such that the majority of the music signal is given virtually distortion-free reproduction with only occasional peaks being clipped. The clipping effect may even pass unnoticed by listeners with less musical ears although it can cause anguish to listeners with experience of good quality audio reproduction. In cases where amplifiers are operated at very high output levels, as occur in discos and musical festivals, occasional or even frequent clipping can occur and may not be audibly evident to the operator of the amplifier if he is close to one or more of the loudspeakers in the system. With domestic high fidelity systems, the operator will want to avoid clipping

on high volume peaks but, if the clipping is only slight and occasional, may not realise that it is occurring.

The solution to all these problems is to add to the amplifier concerned a monitor which gives a visual indication when clipping occurs, or when the output signal voltage level is just below the level at which clipping will take place. This article describes a very simple clipping level monitor circuit which can be added to most conventional solid-state mains-powered amplifiers and which causes a light-emitting diode to be illuminated when the output signal level exceeds a predetermined value. It should be stressed that the circuit requires changes in components or component values to suit particular amplifiers and that it may require

some experiment on the part of the constructor. The circuit should only be used by readers who are reasonably familiar with a.f. amplifier operation and who have the ability to make connections into an existing amplifier without causing any damage thereby.

BASIC CIRCUIT

The basic circuit of the clipping monitor appears in Fig. 1, and here it is assumed that the amplifier has positive and negative supply rails giving a voltage between 20 and 40 volts, that the supply is capable of providing the few extra milliamps required by the monitor circuit and that the amplifier clips when the output signal voltage approaches the negative rail by less than 1.2 volts. If the amplifier has a conventional totem-pole output circuit, the

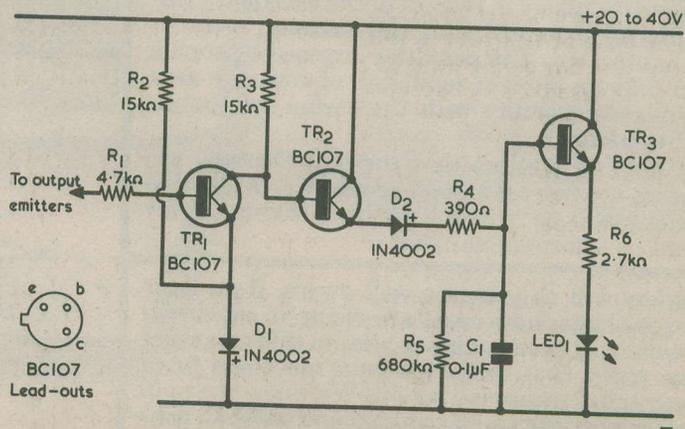


Fig. 1. The basic circuit of the clipping monitor. The single silicon diode in the emitter circuit of TR1 causes the l.e.d. to light up when the output emitters have a voltage which is less than 1.2 volts positive of the negative rail

output will be available at the junction of the two output transistors, frequently at the emitters of two emitter followers, and its voltage will be central between the two supply rails under quiescent conditions. The output then normally couples to the loudspeaker via a large-value electrolytic capacitor. In this article we shall, for convenience, refer to the output point as "the output emitters" although, in practice, the output may be at the junction of two collectors, or at the junction of an emitter and a collector. Where there are small series resistors to prevent thermal runaway, or a small series choke, the output point is considered to be on the speaker side of these components.

The amplifier output point couples to the base of TR1 via R1, which has a very high value compared with the loudspeaker impedance and should have no effect whatsoever on amplifier performance. At all signal output voltages which cause the left-hand end of R1 to be positive of the negative rail by greater than about 1.2 volts, TR1 is turned on and its collector voltage is only slightly positive of the negative supply rail. The 1.2 volt voltage delay is due to the forward voltage drop of 0.6 volt in silicon diode D1, and the similar forward voltage drop in the base-emitter junction of TR1.

If the output voltage takes the left-hand end of R1 to less than the voltage delay TR1 turns off. The base of emitter follower TR2 is very quickly taken to the positive supply rail by R3, causing C1 to charge via diode D2 and current limiting resistor R4. TR3 is another emitter follower which now appears on its base causes its emitter to go positive and light up LED1. If TR1 now turns on again its collector at once goes to a low voltage above the negative rail, taking the base of TR2 with it. This does not cause any discharge in C1, however, because D2 now becomes reverse-biased, and no current can flow through it and the emitter-base junction of TR2 (which acts like a zener diode at its reverse breakdown voltage).

C1 now commences to discharge through R5 and the base of TR3, whereupon LED1 extinguishes more slowly than would be the case if C1 were not present. Without C1 in circuit the l.e.d. would give only a momentary flicker if TR1 were turned off by, say, a single short transient signal at clipping level. C1 ensures that the l.e.d. remains alight for a longer time so that a much more noticeable effect is given. The

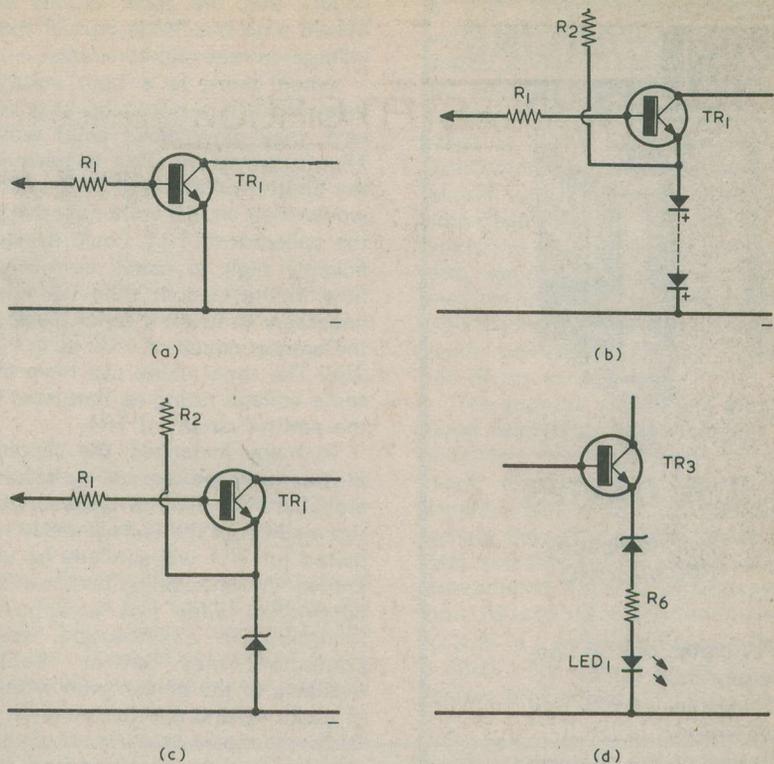


Fig. 2(a) If D1 and R2 are omitted, and the emitter of TR1 is connected direct to the negative rail, the voltage delay at TR1 base is 0.6 volt only

(b). A higher voltage delay is given by connecting two or more silicon diodes in the emitter circuit

(c). In cases where a large number of silicon diodes would be required, a zener diode may be employed instead

(d). When there is a high voltage delay it may be necessary to add a zener diode in the emitter circuit of TR3

capacitor also provides a greater brightness level in the l.e.d. when TR1 is turned off by a series of negative half-cycle signal peaks, since the l.e.d. remains at least partly illuminated between the peaks. The time constant of the circuit, taking into account TR3 base current, is roughly 0.04 second, which is the length of a cycle at 25Hz.

All the resistors may be 5% or 10% types, and R2 to R5 inclusive should have a rating of $\frac{1}{4}$ watt. At supply voltages below 30, R1 may be $\frac{1}{4}$ watt and R6 $\frac{1}{2}$ watt. Above 30 volts R1 should be $\frac{1}{2}$ watt and R6 1 watt. Where only gain-selected BC107's are available, the three transistors can be BC107B or BC107C, although their gain figures are not in practice particularly critical. LED1 can be any l.e.d. of any desired colour. With a supply of 30 volts there is a 2mA flow in both R2 and R3 and about 10mA in R6 when the l.e.d. is fully alight.


VOLTAGE DELAYS

In Fig. 1 it was assumed that clipping occurred when the amplifier output negative peaks were less than about 1.2 volts

positive of the negative rail. However, different amplifiers will have different clipping levels and the voltage delay provided in the emitter circuit of TR1 has to be set up to suit the particular amplifier with which the clipping monitor is to be used.

In Fig. 2(a) there is no voltage delay component in the emitter circuit, and R2 of Fig. 1 is not needed. The monitor will then cater for amplifiers which clip when negative voltage peaks are less than about 0.6 volt positive of the negative rail. Two or more silicon diodes, which may all be 1N4002 or similar, are used in Fig. 2(b). The voltage delay between the base of TR1 and the negative rail is then approximately equal to 0.6 volt multiplied by the number of diodes plus the 0.6 volt given by the base-emitter junction of TR1. Four diodes would, for instance, give $4 \times 0.6 + 0.6$, or 3 volts delay. For delay voltages above this level, it would be preferable to use a single zener diode of the appropriate voltage, as in Fig. 2(c). Diodes in the BZY88 series would be suitable. R2 should then be reduced to $7.5k\Omega$ $\frac{1}{4}$ watt, to

UNDERSTANDING TELEVISION

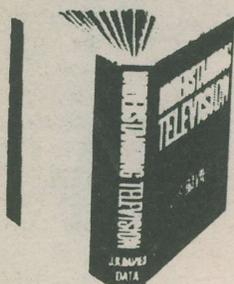

by

J. R. DAVIES

Over 500 pages
300 diagrams

- Principles of 405 line reception
- Principles of 625 line reception
- Nature of the television signal
- Receiver tuner units
- A.F. and video amplifiers
- Deflector coil assemblies
- Automatic gain and contrast control
- Receiver aerials
- The cathode ray tube
- Receiver i.f. amplifiers
- Vertical and horizontal timebases
- Synchronising
- Power supply circuits
- Introduction to Colour TV

£3.95 P. & P. 80p

To: DATA PUBLICATIONS Ltd., 57 Maida Vale London W9

Please supply copy(ies) of "Understanding Television" Data Book No. 17. I enclose cheque/crossed postal order for

Name

Address

BLOCK LETTERS PLEASE

ensure that the zener diodes are biased onto the flatter part of their voltage-current characteristic.

When there is a high voltage delay there is a possibility that the l.e.d. may glow dimly even when TR1 is turned on. This is because the emitter potential of TR3, which would then be 1.8 volts negative of the collector of TR1, could be sufficiently high to cause current to flow in the l.e.d. It then becomes necessary to insert a zener diode in the emitter circuit of TR3, as in Fig. 2(d). The zener diode can have the same voltage rating as that used in the emitter circuit of TR1.

In many instances, the clipping output voltage for a particular amplifier may not be known, with the result that the voltage delay required for TR1 will similarly be unknown. Whilst clipping level can be determined with test equipment, including an oscilloscope, such equipment may not be readily available to the person who wishes to make up and use the monitor. A fairly reasonable assessment of clipping level can be obtained from the amplifier specifications remembering that, from Ohm's Law, voltage squared is equal to power in watts multiplied by resistance in ohms. To take an example, let us suppose that we have an amplifier which operates with a 30 volt supply and which is stated to have a maximum r.m.s. output power of 16 watts into 4Ω . The product of 16 and 4 is 64, which is equal to the r.m.s. output voltage squared. The maximum r.m.s. output voltage for the amplifier is thus 8 volts. If we multiply this by 1.4, we find that the corresponding peak voltage is 11.2 volts. It is fairly safe to assume from this that the amplifier will start approaching overload when its peak output voltage significantly exceeds 11.2 volts. The next process is to

measure the quiescent output voltage between the output emitters and the negative rail, and this could be, say, 14 volts. The voltage delay for the clipping monitor could then be set at 14 minus 11.2 (= 2.8) if it is to respond to negative peaks of 11.2 volt or more. In practice, the delay could be set at 2.4 volts by using three diodes in the circuit of Fig. 2(b), or at 1.8 volts by using two diodes. Subsequent checks, consisting of deliberately running the amplifier close to or into overload, will indicate whether the clipping monitor is capable of detecting occasional negative peak excursions which go up to distortion level.

This approach has to be of an approximate nature but should nevertheless enable the monitor to indicate output signal levels which approach or are at the clipping level. The example purposely employed "easy" figures to assist in demonstrating the procedure, but the work involved in calculating the peak output voltage is quite easy if a pocket calculator is employed.

Since the amplifier concerned will almost certainly be one of a pair in a stereo system, another monitor circuit will need to be fitted also in the second amplifier. This can have the same voltage delay as was considered desirable for the first amplifier.

SUPPLY VOLTAGES

The circuit of Fig. 1 is, as was stated, suitable for amplifiers having a positive and negative supply of 20 to 40 volts. The monitor is then connected as shown in Fig. 3(a).

More powerful amplifiers have positive and negative rails on either side of a central zero voltage rail. When the voltages are suitable the clipping monitor may be powered by the zero voltage rail and the

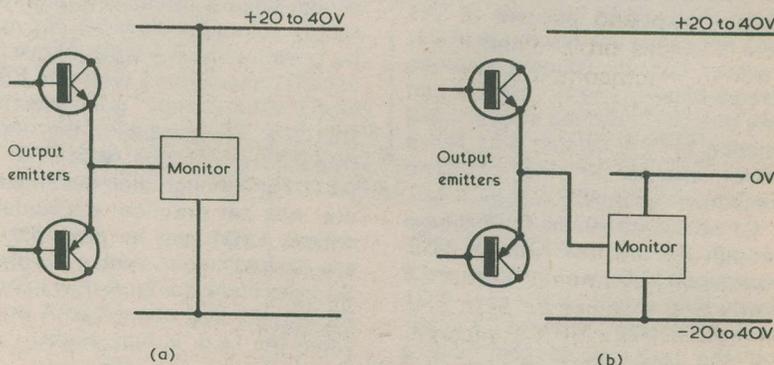


Fig. 3(a). With amplifiers having two supply rails the monitor is connected as shown here

(b). This method of connection may be employed when the amplifier has a central zero voltage rail

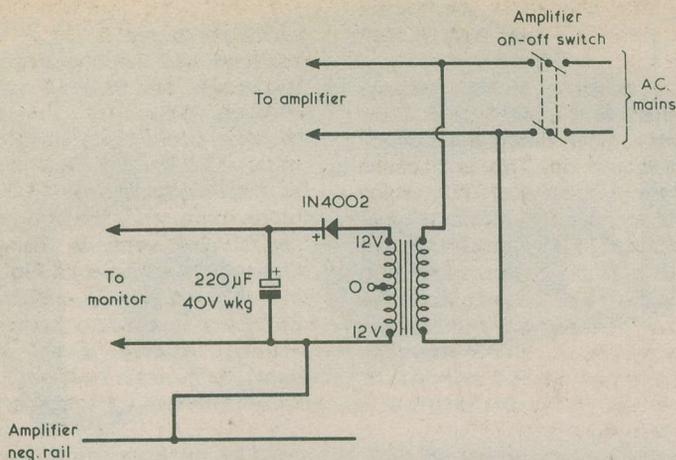


Fig. 4. The monitor can be powered by an inexpensive supply incorporating a low-cost mains transformer. The same supply can also be used for the second monitor in a stereo system

negative rail, as in Fig. 3(b). Amplifiers in this category have a relatively very wide output voltage swing, and with these R1 should be increased in value to 10k Ω 1 watt. If the supply voltages available

from the amplifier are in excess of 40 volts, or if it cannot provide the small extra current required by the monitor, it would not be unduly uneconomic to provide the monitor with its own power supply, as in Fig.

4. The mains transformer can be any small type offering a rectified output voltage in the range of 20 to 40 volts. A miniature transformer having a 12 - 0- 12 volt secondary rated at 50mA or more would be satisfactory, for instance, and this would provide a rectified and smoothed output of around 33 volts. The single power supply could also supply the second clipping monitor in a stereo system. Note that the negative rail of the supply is made common with the negative rail of the amplifier.

The monitor circuit will function quite well with much smaller a.f. amplifiers having supply voltages down to as low as 9 volts. The monitor circuit can be connected across the supply rails, as in Fig. 3(a), and some of the resistor values are reduced. For 9 to 20 volt operation, R2 and R3 should be changed to 8.2k Ω , R4 to 220 Ω and R6 to 1.8k Ω . The values of R1 and R5 remain unchanged.

THE OSCAR PHASE III

A Progress Report By Arthur C. Gee

In March 1980, the latest of AMSAT's Orbiting Satellites Carrying Amateur Radio, will be launched from Kourou, French Guiana. AMSAT-III A, as it is called, will be a much more sophisticated than previous amateur radio satellites and will give its amateur radio users a new experience, because at the highest point of its orbit, it will be available to the entire hemisphere below it and users will have continuous access up to ten hours per orbit.

AMSAT Phase III is a high altitude, long life satellite, which will be launched as a secondary payload, aboard an Ariane mission. The European Space Agency will provide the launch opportunity from a site in Kourou, near the coast of French Guiana. It will be first put into an elliptical orbit with a projected inclination of 17 degrees, an apogee of 35,000 Km and perigee of 200 Km. After a few weeks in this orbit, when it has stabilised and the onboard microcomputer has determined that the satellite is in the proper orientation to the sun, to the earth and its proper position in its orbit, a one-shot onboard perigee kick motor will fire. This will lift the perigee to its projected 1500 km altitude and raise the inclination to 57 degrees. This orbit will have a period of approximately 660 minutes and a longitude increment of about 165 degrees west per orbit. The kick motor is a solid propellant motor which will burn for 20 seconds. These parameters are the anticipated ones — the final ones will no doubt be slightly different from these.

This orbit will favour the Northern Hemisphere at first, as the apogee after the perigee kick motor firing will occur at about 26 degrees North latitude. Over the course of the first two years, the latitude of

the apogee will drift gradually northward to its highest point: 57 degrees North latitude. From this time on the apogee will drift southward until after another year or so it will occur over the equator. From this point on, the Southern hemisphere will be favoured and the second of the AMSAT Phase III missions will have been launched, again initially favouring the northern hemisphere. Throughout its lifetime however, the AMSAT Phase III series satellites will be accessible throughout the world at some point during the day; those regions falling under the illumination at apogee will simply have greater access time.

AMSAT Phase III-A will carry a Mode B transponder. Its uplink will be in the 70 cm band and the downlink in the 2 metre band. The passband will accommodate SSB, CW, SSTV, RTTY and whatever digital modes are approved for use through the satellite. There will be several Special Service Channels that will deal exclusively with such matters as data exchange, education, scientific study, officially authorised traffic and general telemetry and codestore information, and an engineering beacon for more sophisticated management purposes will be at the very edges of the passband. To access the satellite, a user will need about 1000 watts e.r.p. on 70 cms — but high gain antennas to achieve this effective radiated power economically are feasible as near apogee (plus or minus 3 hours) AMSAT Phase III-A will move very slowly and through a comparatively small arc; tracking will be a fairly simple matter.

S.W. AERIAL TUNING UNIT



by
R. A. PENFOLD

*Improves receiver performance
over 1.6MHz to 30MHz*

An aerial unit (or a.t.u.) is one of the simplest accessories for a short wave receiver and yet it can provide quite significant and worth-while improvements in performance. It has two beneficial effects, these being an increase in signal strength and an attenuation of spurious responses.

Since an a.t.u. is a passive device a claim that it increases signal strength may seem unlikely, since such a claim gives the impression that the unit provides active amplification. In practice it does not, and what it does do is to improve the coupling between the aerial and the receiver input which, in most receiver installations, is inefficient over at least some if not most of the frequencies covered. The a.t.u. simply ensures that as much of the aerial signal energy as possible is coupled into the receiver. Normally, it can provide an increase of two or three "S" units when an ordinary long wire antenna is employed with a receiver having the usual low impedance aerial input circuit.

The reduction in spurious responses applies mainly with superhet short wave receivers. The aerial tuning unit is made resonant at the frequency of the desired signal, thereby giving additional

COMPONENTS

Capacitors

VC1 365pF variable, Jackson type "O" (see text)
VC2 356 variable, Jackson type "O" (see text)

Inductor

L1 see text

Switches

S1 d.p.d.t. toggle
S2 1-pole 12-way rotary, with adjustable end stop

Sockets


SK1 insulated wander plug socket
SK2 insulated wander plug socket
SK3 insulated wander plug socket

Miscellaneous

Metal instrument case (see text)
3 control knobs
4 cabinet feet
Wire, nuts, bolts, etc.

input tuned filtering and reducing the effect of image and similar responses.

Fig. 1. The pi-network circuit employed in the aerial tuning unit

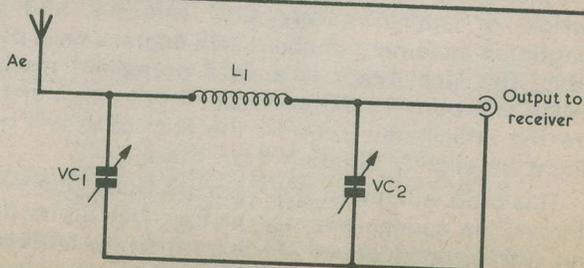

CIRCUIT OPERATION

The conventional arrangement for an a.t.u. is the well-known pi network circuit shown in Fig.1. This is a form of matching circuit which, if correctly set up, provides an input impedance which correctly matches the source impedance of the aerial (which, like any other signal source, must have a source impedance) and which also matches the input impedance of the receiver. The aerial impedance varies considerably at different frequencies and, if a wide range of frequencies is to be covered, it is impossible for a single aerial to have a source impedance equal to the input impedance of the receiver at all of these. Optimum signal transfer occurs when source impedance is equal to input impedance.

The input impedance of the a.t.u. can be made variable by adjusting VC1, and the output impedance may be altered by VC2. A further factor is that VC1 and VC2 in series provide a tuning capacitance which is connected across the coil. If, therefore, the two variable capacitors are adjusted such that the consequent tuned circuit is resonant at the desired frequency and also provides the required input and output impedances it follows that the tuning unit must provide maximum transfer of signal energy from the aerial to the input of the receiver.

The working circuit of the a.t.u. described here appears in Fig.2, and it differs mainly from that of Fig.1 by making the inductance variable by means of switch S2, which selects sections of the complete coil. A variable inductance is necessary if the unit is to carry out the threefold requirement of being resonant at the desired frequency and, at the same time, of presenting the correct input and output impedances.

A refinement is the inclusion of S1(a)(b), which can be switched so that the unit is bypassed. This feature can be very useful when setting up the a.t.u., as it provides an instant check on the effect of the unit.

The two variable capacitors are Jackson type "O" single gang air-spaced components having a maximum value of 365pF. It is not essential to use these particular capacitors and any other air-spaced variable capacitors having a maximum value in the range of 300pF to 500pF will be equally satisfactory. Solid dielectric variable capacitors should not be employed as these do not have the required performance at short wave frequencies.

CONSTRUCTION

The author's a.t.u. is housed in a metal instrument case having dimensions of 152 by 118 by 51mm. This is a case type BC1, available from Harrison Bros., P.O. Box 55, Westcliff-on-Sea, Essex, SS0 7LQ. Any other metal case of about the same dimensions, or slightly larger, should be equally satisfactory. The input and output sockets, an earth socket, and switch S1(a)(b) are mounted on the rear panel of the case, whilst the two variable capacitors and the coil tap switch S2 are fitted to the front panel. VC2 is to the left of the switch and VC1 is to its right. The spindles of all three components are at the same horizontal level and they are laid out in symmetrical manner as illustrated in the photograph of the front panel.

The Jackson 365pF variable capacitors have three mounting holes in the front plate which are tapped 4BA. Three corresponding 4BA clear holes

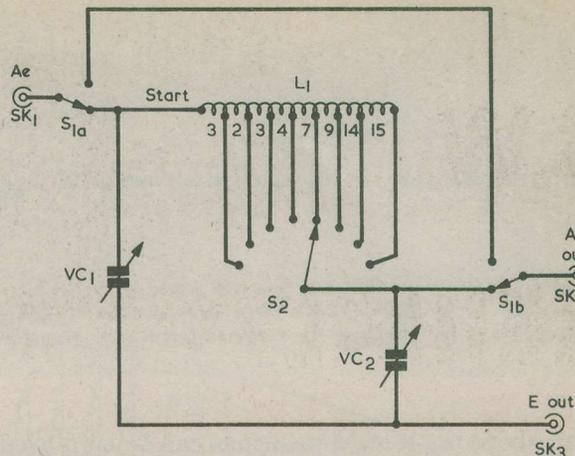


Fig. 2. The practical a.t.u. circuit requires variable inductance in addition to variable capacitance, and this is provided by tapings in the coil which are selected by S2. The numbers indicate the number of turns in each section of the coil


have to be drilled in the front panel for each capacitor and they may be marked out in the following manner. Take a piece of paper, cut out a hole of $\frac{1}{4}$ in. diameter in its centre and pass the hole over the spindle of the capacitor. Mark on the paper, with a pencil, the positions of the three 4BA tapped holes. Then use the paper as a form of template to mark out the 4BA clear holes required in the front panel of the unit. Drill out the holes, together with the central hole for the capacitor spindle. The capacitor is then mounted by three short 4BA bolts, with spacing washers (which could be 2BA nuts) between the inside surface of the front panel and the front plate of the capacitor. Short bolts are essential because their ends must not protrude more than fractionally beyond the capacitor front plate as they could then damage the fixed or moving vanes.

The coil is home-constructed and, because of the large variables in the circuit, is not as critical in its construction as would be, say, the aerial input coil of a short wave receiver. The former used in the prototype is a plastic tube about 72mm. long and 25mm. in diameter. It was originally part of a reel on which Multicore solder was supplied. Any reasonably strong tube made of plastic material



The three sockets and the bypass switch, S1(a)(b), are mounted on the rear panel of the case

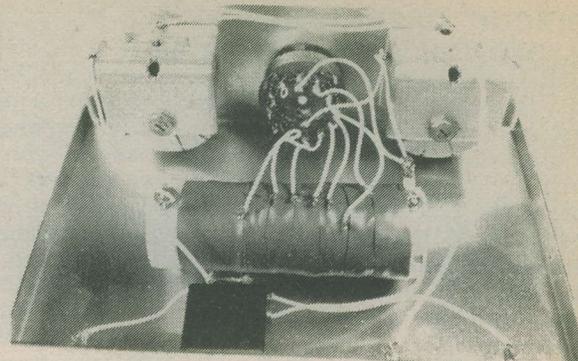The wiring between the coil taps and switch S2



with about the same dimensions can be employed. An alternative is a length of 1in. diameter timber, such as a piece cut from a broom handle. Provided that it is dry this will have more than adequate insulation resistance for the present purpose.


A 6BA solder tag is mounted at each end of the former to provide anchoring points for the ends of the coil. If a plastic tube is employed, a 6BA clear mounting hole is drilled in it opposite each solder tag. With a wooden former, the mounting will be carried out with woodscrews. The coil is wound with enamelled copper wire of around 26 to 30 s.w.g., 28 s.w.g. wire being employed for the coil used in the prototype. A length of $5\frac{1}{2}$ metres of the wire will be more than sufficient. The coil is wound in sections, the turn numbers being indicated in the circuit of Fig.2. Each section has a length of about 6 to 7mm., with the result that sections with a small number of turns have the wire fairly well spaced out whilst those with a large number of turns have the wire very nearly close-wound.

Strip the enamel from the winding wire at one end and solder this to one of the solder tags. Wind on the first section, which has 3 turns. The winding proper may start about 5mm. in from the solder tag, and a narrow band of p.v.c. insulation tape is then used to hold the section in place on the former. A small loop is made in the wire and the next sec-

tion, with 2 turns, is wound on and secured in place with tape. A loop is again made in the wire. This procedure is continued with further sections of 3, 4, 7, 9, 14 and 15 turns, the free end at the last section being cut to length, stripped of enamel and soldered to the second solder tag. Note that it is important for all the turns on the coil to be wound in the same direction. Mark the former in any convenient way, say by a piece of coloured tape, so that the coil start end, with the 3 turns section, may be identified.

Next carefully scrape away the enamel from the wire loops between the sections and tin these with solder. The completed coil is then mounted in the case as shown in the photograph of the interior, with the coil start nearer VC1. It is this end of the coil which connects to the fixed vanes of VC1. The coil former is spaced off from the case surface by two spacing washers about 10mm. long.

Wiring is then carried out as illustrated in Fig.3. S2 is a single pole 12-way switch with adjustable end stop set for 8-way operation. Before connecting to its tags, check with a continuity tester or by visual inspection the eight outer tags which the switch brings into circuit. With some switches the relative positioning of these tags and the central tag may differ from that shown in Fig.3. The wiring should be kept reasonably short and direct, and care should be taken to avoid dry joints, particularly at the tapping points in the coil. The wire connecting together the moving vanes tags of VC1 and VC2 is not essential, since the bodies of these two capacitors are connected together via their mounting to the front panel, but it is in general good practice to fit the wire.

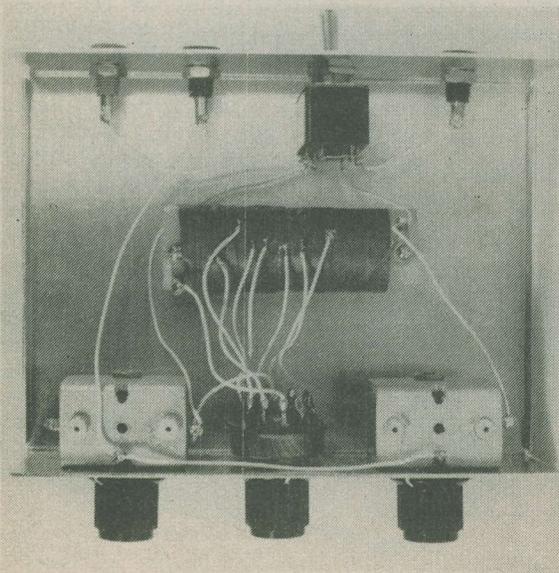

Looking down into the case with the lid removed. The general view is the same as that in the wiring diagram of Fig. 3

USING THE UNIT

A 2-way cable is used to connect SK2 and SK3 of the a.t.u. to the receiver aerial and earth terminals. It is not essential, or even desirable, to use a coaxial cable here, and ordinary unscreened wire is perfectly suitable. If the receiver earth terminal connects to an external earth this connection is retained.

The unit will match any long wire aerial of about 10 metres or more in length to a receiver having a normal input impedance in the range of 50Ω to 600Ω .

Setting up is considerably eased if the receiver has a tuning meter or an "S" meter. S2 is then tried at various settings, with VC1 and VC2 being adjusted at each setting in an attempt to peak the received signal as indicated by the meter. Switching the unit in and out by means of S1(a)(b)

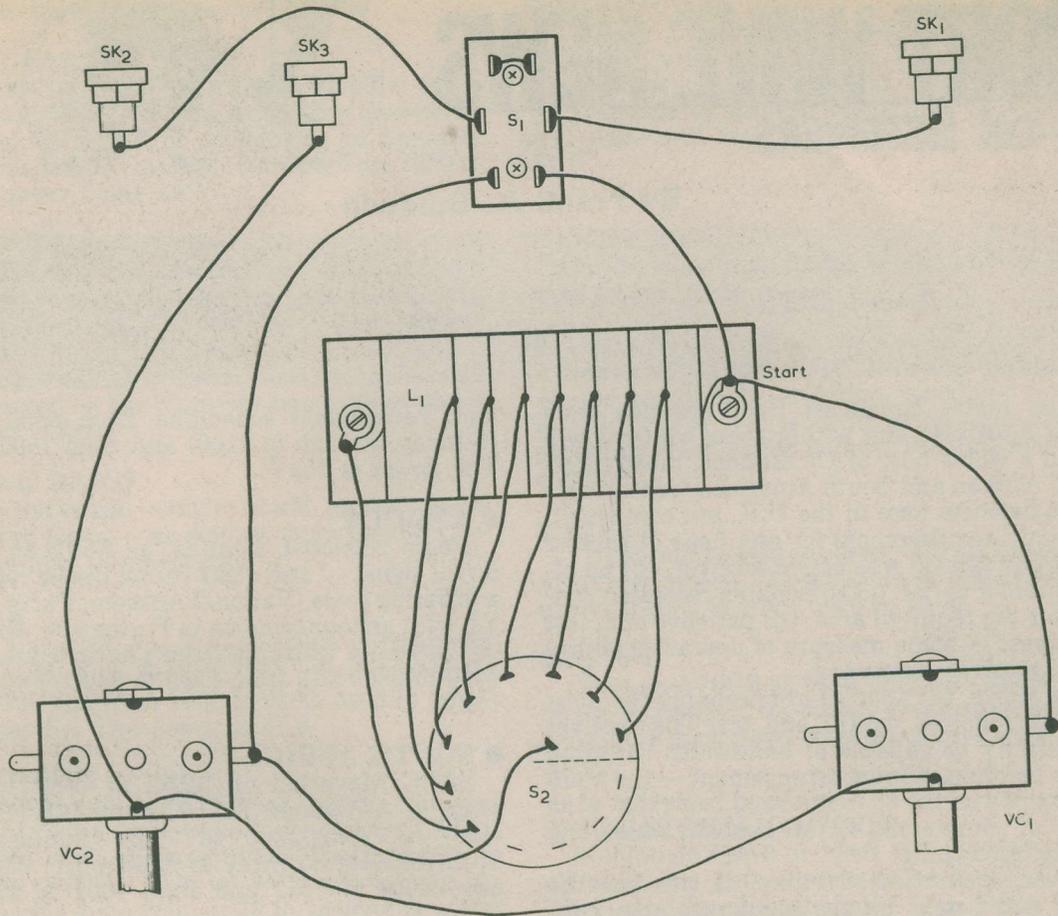



Fig. 3. Wiring up the aerial tuning unit. The wires should be kept reasonably short and direct

will show that if any improvement is introduced by the tuning unit. If the receiver does not have a signal strength meter the tuning unit can be set up for maximum volume using a *weak* signal, with the receiver a.g.c. switched off if possible. It will be impossible to set up the a.t.u. by volume indications when using a strong signal with the a.g.c. switched

in, as the a.g.c. will mask any improvements in signal strength. The a.t.u. will not always provide an increase in signal strength since there may already be an adequate match between the aerial and the receiver on some short wave bands. In these cases, the controls can either be set up for maximum results, or the unit can be bypassed by means of S1(a)(b).

If extensive listening is to be carried out over a wide range of frequencies, it would be worth-while fitting logging scales around the knobs for S1(a)(b) and the two variable capacitors. The optimum settings for these controls for each band can be found initially and noted. Resetting the controls when changing bands will then be much simpler and quicker.

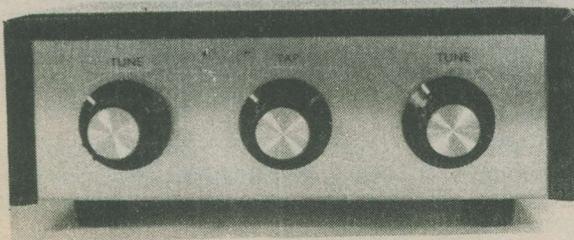In general, the lower the reception frequency, the greater the number of coil turns which has to be switched into circuit by S2. It should be possible to use the aerial tuning unit successfully at any frequency within the short wave spectrum of about 1.6MHz to 30MHz.



Switch S2 is mounted at the centre of the front panel with VC1 to its right and VC2 to its left

SHORT WAVE NEWS

FOR DX LISTENERS



By Frank A. Baldwin

Times = GMT

Frequencies = kHz

The 90 metre Broadcast Band extends from 3200 to 3400kHz and within these confines will be found a whole host of Dx stations, mostly low-powered African and South American transmitters as far as listeners here in the U.K. are concerned.

The main requirements for any hope of success on this band are (a) a selective receiver, (b) an efficient outdoor aerial, (c) reasonable reception conditions for the required area, (d) patience and, last but not least — some measure of operating ability with the receiver concerned.

Of the above, (a) and (d) are probably the most important, followed by (b) and (c). The receiver should ideally be capable of bandwidth variation and/or a bandpass tuning arrangement — the main bar to progress on the 90 metre band being that of an 'overlay' of commercial QRM, beneath which one must 'dig' for results.

However, from time to time, if one has the patience and listens on the band regularly, conditions prevail such that some African and Latin American stations may be logged by almost anyone around at the appropriate time — but these ideal occasions are few and far between.

Just recently we have been 'observing' the band during what may be termed normal conditions and what follows are the results obtained.

● MOZAMBIQUE

Radio Mozambique, Maputo, on 3210 at 1832, light orchestral music, YL with a ballad in Portuguese. This is the 'A' programme in Portuguese, scheduled here from 0255 to 0530 and from 1630 to 2210 (except for an English programme from 1800 to 1815). The power is 100kW.

● LIBERIA

Monrovia on a measured 3227 at 1958, OM with a talk in vernacular. This is the Home Service, scheduled from 0600 to 0800 and from 1805 to 2220, the power being 10kW.

● MALAGASY

Tananarive on a measured 3287.5 at 2006, OM and YL with a duet in vernacular mixed with heterodyne QRM. The schedule is from 0300 to 0600 and from 1300 to 2100 and is the Home Service in French and Malgache. The power is 100kW.

● NIGERIA

Lagos on a measured 3326.5 at 2000, YL with identification and a newscast in English. New frequency, schedule unknown at present — testing?

● BURUNDI

Bujumbura on 3300 at 0410, OM with (news?) in vernacular. This is the Home Service 1 in French

and Vernaculars scheduled from 0330 to 0600 (Sunday through to 2100) and from 1500 to 2100. The power is 25kW.

● ANGOLA

Radio Nacional, Luanda, on 3375 at 0400, interval signal — and eight chime theme repeated in a differing scale, National Anthem, Party Anthem, YL with announcements in Portuguese when opening the daily transmissions. The schedule is from 0400 to 0800 and from 1530 to 2400. The power is 10kW.

● SOUTH AFRICA

SABC Meyerton on 3250 at 1953, local folk songs in Afrikaans. The schedule (All Night Service) is from 2200 to 0300 (Sunday 0400), Springbok Radio (May to September) 0300 (Sunday 0400) to 0552 and from 1662 to 2200. The power is 100kW.

● MALAWI

Blantyre on 3380 at 2004, OM with announcements in vernacular followed by a church service. The schedule is from 0245 to 0520 (April to October until 1110) and from 1745 to 2210 (April to October from 1300). The power is 100kW.

● ZIMBABWE-RHODESIA

RBC Salisbury on a measured 3396 at 2008, YL's in operatic chorus. This is the General Service scheduled from 0355 to 0530 and from 1530 to 2200. The power is 20kW.

● CONGO

RTVC Brazzaville on a measured 3264 at 1838, YL with announcements in French followed by a musical interlude. This is a new frequency, probably a move from 3232 where the schedule was from 0400 to 0700 and from 1700 to 2300, the power being 4kW.

● IRAQ

Baghdad on a measured 3242.5 at 2003, YL with the programme in Kurdish (Home Service), scheduled from 0258 to 0855 and from 1230 to 2200. In Turkmen from 0900 to 1225. The power is 50kW.

● ECUADOR

Radio Iris, Esmeraldas, on 3380 at 0338, local-style pops, YL song in Spanish. The schedule is from 1100 to 0300 (closing time is variable) and the power is 10kW.

Radio Zaracay, Santo Domingo, on 3390 at 0350, OM with a song in Spanish, local-style dance music. The schedule is from 1000 to 0500 (closing

time is variable) and the power is 10kW.

● GUATEMALA

La Voz de Nahuala, Nahuala, on **3360** at 0334, local music similar to Samba but with a loud drum beat predominating, OM announcer in Spanish. The schedule is from 1100 to 1300 and from 2230 to 0430, the power being 1kW.

● VENEZUELA

Radio Universidad, Merida, on **3395** at 0355, OM with a love song followed by announcements in Spanish. The schedule of this one is from 1000 to 0400 and the power is 1kW.

All of the foregoing however does not include all that was logged on the 90 metre band — see under **Now Hear This**.

60 METRE BAND

As this particular article would appear to be aimed at the Dxer — as distinct from the SWL — we migrate now to this band.

● CONGO

Pointe Noire on a measured **4843** at 1944, OM with a harangue in French. The schedule is from 0400 to 1200 and from 1500 to 2100, usually relaying Brazzaville. The power is 4kW.

● CAMEROON

Radio Bertoua on **4750** at 0430, National Anthem and announcements in French by OM on opening the daily transmissions. The schedule is from 0430 to 0730, 1630 to 2200 and there is an English programme from 1830 to 1845. The power is 20kW.

Radio Garoua on **5000** (yes, the frequency is correct) at 1938, local-style music, OM with announcements in French, all mixed with MSF. Also logged on the listed **5010** at 0439, OM with religious chants. They would appear to be using both channels but not simultaneously.

● NIGERIA

Lagos on **4990** at 0436, YL with the programme review in English. This is the National Service which is in English and vernaculars, scheduled from 0430 to 1000 and from 1700 to 2305. The power is 20kW.

● COLOMBIA

Emisora Nuevo Mundo, Bogata, on **4755** at 0410, local-style dance music, OM with vocal in Spanish. This transmitter is on the air around the clock, the power being 1kW.

● HONDURAS

La Voz Evangelica, Tegucigalpa, on **4820** at 0418, OM and YL in English, YL with hymns. The schedule of this one is from 1030 to 0500 with programmes in English from 1500 to 1600, 0300 and 0400 and from 0415 to 0430. The power is 5kW.

OTHER BANDS

On the remaining bands some items of interest were logged, such as —

● LEBANON

Beirut on **21610** at 1932, Arabic music in the Arabic programme for Africa, scheduled from 1900 to 2000. For those interested, the English programme for Africa is from 1830 to 1900 on this channel.

● LIBYA

Tripoli on **15100** at 1949, OM in Arabic, local songs and music. The schedule on this channel, entirely Arabic, is from 0800 to 2200.

● EGYPT

Cairo on **17690** at 1430, OM with identification in the opening of the Hindi programme for South and South East Asia, scheduled here from 1530 to 1630.

● EQUATORIAL GUINEA

Malabo on **6250** at 1948, OM and YL with announcements and news items in Spanish. This is the Home Service scheduled from 0500 to 2300. There is an English programme listed from 2030 to 2100, the evening Spanish transmission being from 1900 to 2030 and from 2100 to 2300. The power is 10kW.

● CHINA

CPBS Peking on **7335** at 2000, YL with identification and opening announcements, 'East is Red', in the opening of the Domestic Service 1 Programme scheduled on this channel from 2000 to 2300. Also logged in parallel on **7504**.

NOW HEAR THIS

FR3 Cayenne, French Guyana, on **3385** at 0340, light orchestral music, OM announcements in French, YL song in French. The schedule is from 0900 to 1200 and from 2100 to 0200 but on Saturday (when logged) closing time is variable. The power is 4kW.

GREAT CIRCLE DX MAP

The Radio Society of Great Britain have recently published a second edition of their famous Great Circle DX Map.

This colourful wall map shows the true bearings from the UK of countries throughout the world, and is thus invaluable for radio enthusiasts with directional antennas. Amateur radio prefixes are included, and the map is plastic laminated for extra durability.

760 by 620mm, Price £1.50 (£1.99 inc p&p) from RSGB
35 Doughty Street, London WC1N 2AE.

DIGITAL TANTALISER



By I. M. Attrill

Match your timing skill against this ingenious electronic game

This amusing electronic game is a development of a circuit which was published some years ago in *Radio & Electronics Constructor* ("The 'Tantaliser' — An Electronic Game", by G. A. French, October 1975 issue). In the earlier circuit an l.e.d. flashed on and off continually, and it was required that a push-button be pressed during the periods when the l.e.d. was extinguished. This allowed a capacitor to acquire a small charge. If the button was pressed when the l.e.d. was alight the capacitor discharged at a much higher rate. The voltage across the capacitor was monitored by a voltmeter and the purpose of the game was to achieve as high a voltage as was possible in a given period of time, or to take the voltmeter indication up to full-scale deflection.

DIGITAL CIRCUIT

The present circuit employs a basically similar approach for the charge and discharge of the capacitor. The l.e.d. indicator flashes on and off at a fairly slow rate of around 0.6Hz. There is a push-button on the front panel of the unit and it is again intended that this be pressed when the l.e.d. is extinguished. Where the design now differs from the previous one is that there is a digital readout instead of the simple voltmeter arrangement used in the previous design. A 2-digit counter commences to count at the start of the game and ceases only when the voltage across the capacitor has reached a pre-determined level. As a result, a skilful player will be able to stop the digital count at a low number, whereas a less skilful player may only be able to do so after a higher count has been displayed. Of course, the aim is to obtain the lowest possible final score on the counter.

It is not possible to cheat by merely holding the push-button depressed continuously as the capacitor discharge rate is higher than the charge rate. Thus it is important to avoid having the button pressed when the l.e.d. is alight, as any charge previously acquired by the capacitor will be more rapidly lost again.

The game can be made slightly more difficult by switching the l.e.d. to a second, faster, flashing rate, once the player has become competent at the game with the lower flashing rate selected.


This game obviously tests the reactions of the player, since in order to do well it is necessary to activate the push-button very quickly after the l.e.d. indicator has switched off. However, a good sense of timing is also needed, because it is not possible to succeed at the game by waiting for the indicator light to switch on again before releasing the push-button. However fast one's reactions may be, this would inevitably leave a short period with the l.e.d. on and the button depressed, leading to very slow progress for the reason stated earlier. It is necessary for the player to anticipate the switching on of the l.e.d. indicator, so that he or she can release the push-button momentarily before the l.e.d. turns on. This gives a steady progress towards completion of the game without any "back tracking", and therefore gives a good low score.

This game is also a good test of concentration because, during the half minute or so that the game usually lasts, it is necessary to concentrate carefully and continuously on the game. A slight loss of concentration almost invariably leads to the push-button being depressed at the wrong time and ground being lost in consequence.

GENERAL ARRANGEMENT

The general arrangement of the unit is shown in the block diagram of Fig.1. The l.e.d. indicator is driven by a low frequency oscillator which produces a square wave having a 1:1 mark-space ratio, and the l.e.d. lights up when the oscillator output is low. As well as lighting the l.e.d. the oscillator output is taken via a time constant circuit and the push-button to the storage capacitor. When the push-button is pressed in the required manner, the voltage across the capacitor increases.

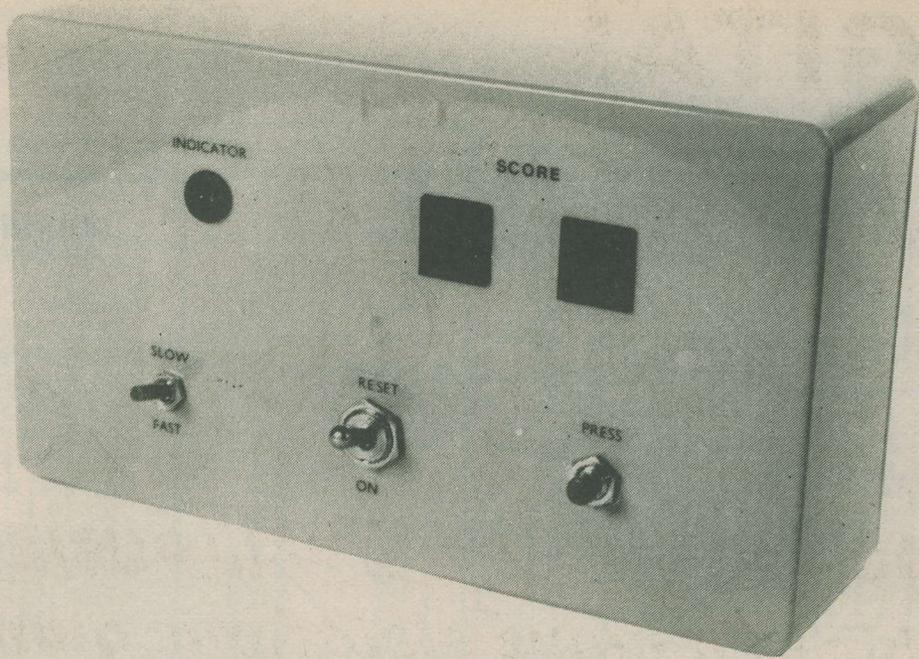At the start of the game the clock oscillator feeding the 2-digit counter commences operation,



The front panel of the digital "Tantaliser". This offers a challenge to test skill in timing and visual reaction

and the count starts from zero. Clock frequency is approximately 2Hz. The voltage across the storage capacitor is applied to a voltage detector and, when it reaches the required level, the voltage detector inhibits the counter. The "frozen" count which is then displayed is the player's score.

FULL CIRCUIT

The full circuit of the "Tantaliser" game appears in Fig.2. The oscillator driving the l.e.d. is a 555 multivibrator, and the l.e.d. and series resistor R4 are connected between its output and the positive rail so that the l.e.d. is turned on when the output is low. Timing components R2, R3 and C2 give a

flashing rate of approximately one flash every 1.7 seconds, and R3 is made large in relation to R2 so that a mark-space ratio of virtually 1:1 is obtained. When S1 is closed, R1 is shunted across R3, reducing the timing resistance and nearly doubling the oscillator frequency.

C3 is the storage capacitor and, when the 555 output is high, it charges via R5 when push-button S2 is pressed. D2 becomes forward biased if S2 is pressed when the 555 output is low, causing R6 to be effectively in parallel with R5. In consequence, the discharge rate is much greater than the charge rate.

The voltage detector uses operational amplifier

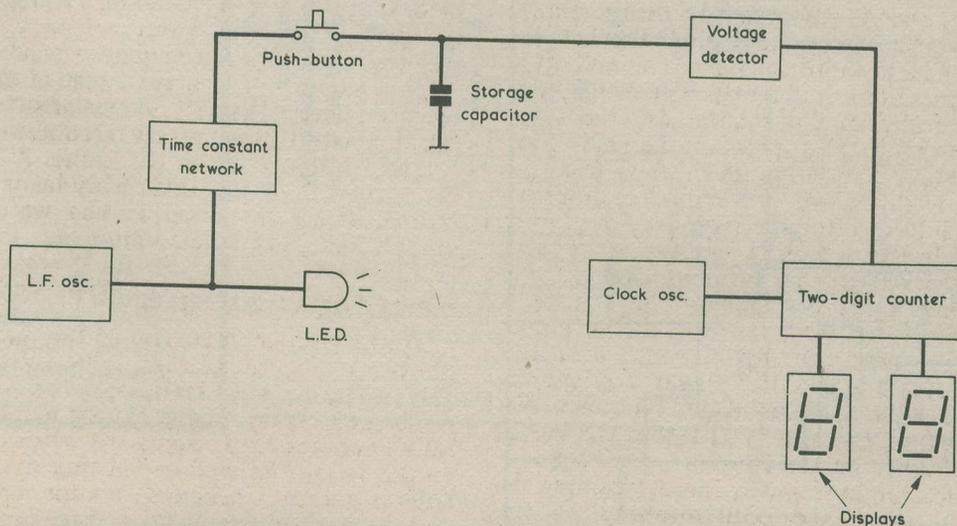


Fig.1. Basic line-up of the "Tantaliser" game. The low frequency oscillator produces a square wave which lights the l.e.d. when the output voltage is low. The purpose of the game is to manipulate the push-button such that the storage capacitor becomes charged sufficiently to trigger the voltage detector. The latter then stops the two-digit counter

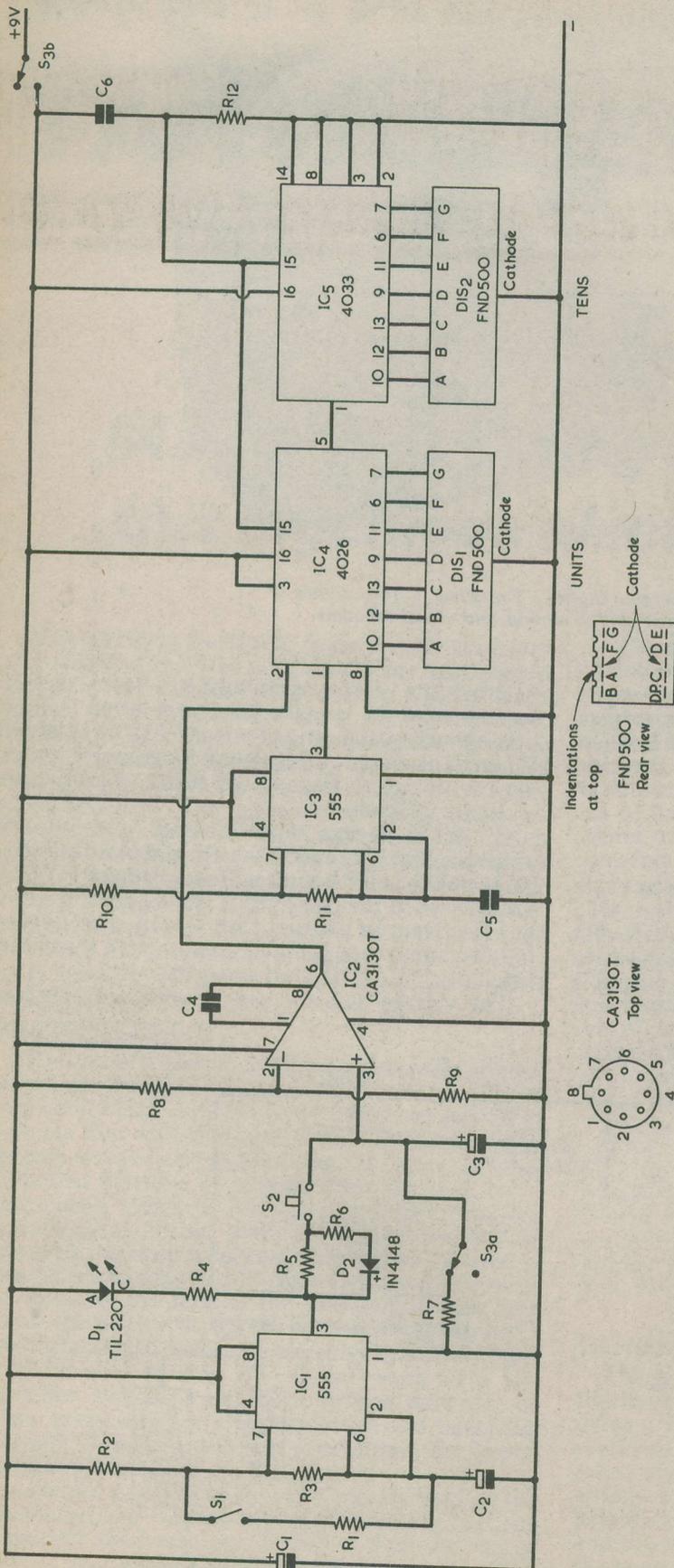


Fig. 2. The full circuit of the unit. C3 is the storage capacitor and the short-circuit across it, via R7, is removed when switch S3 is set to the "On" position to start the game. C6 and R12 ensure that IC4 and IC5 are reset to zero and the count then commences

COMPONENTS

Resistors

(All $\frac{1}{4}$ watt 5%)

R1 560k Ω

R2 2.7k Ω

R3 470k Ω

R4 1k Ω

R5 560k Ω

R6 56k Ω

R7 10 Ω

R8 4.7k Ω

R9 4.7k Ω

R10 1M Ω

R11 1M Ω

R12 100k Ω

Capacitors

C1 100 μ F electrolytic, 10V. Wkg

C2 2.2 μ F electrolytic, 63V. Wkg

C3 10 μ F electrolytic, 10V. Wkg

C4 22pF ceramic plate

C5 0.22 μ F polycarbonate or type

C280

C6 0.1 μ F type C280

Semiconductors

IC1 555

2 CA3130T

IC3 555

IC4 4026

IC5 4033

D1 i.e.d. type TIL220 or similar

D2 1N4148

Displays

DIS1 FND500 (see text)

DIS2 FND500 (see text)

Switches

S1 s.p.s.t. toggle

S2 push-button, press to make

S3 d.p.d.t. toggle

Miscellaneous

Plastic case (see text)

Veroboard, 0.1in. matrix



2-off 16-way i.c. holders

9-volt battery type PP7 or PP9

Battery connectors

Panel-mounting bush (for D1)


Nuts, bolts, wire, etc.

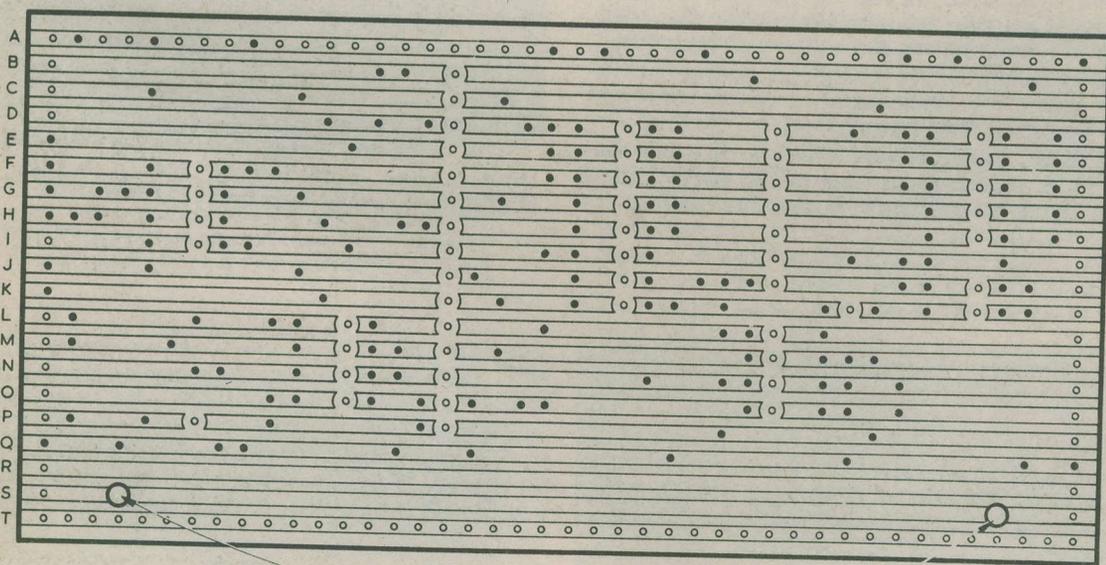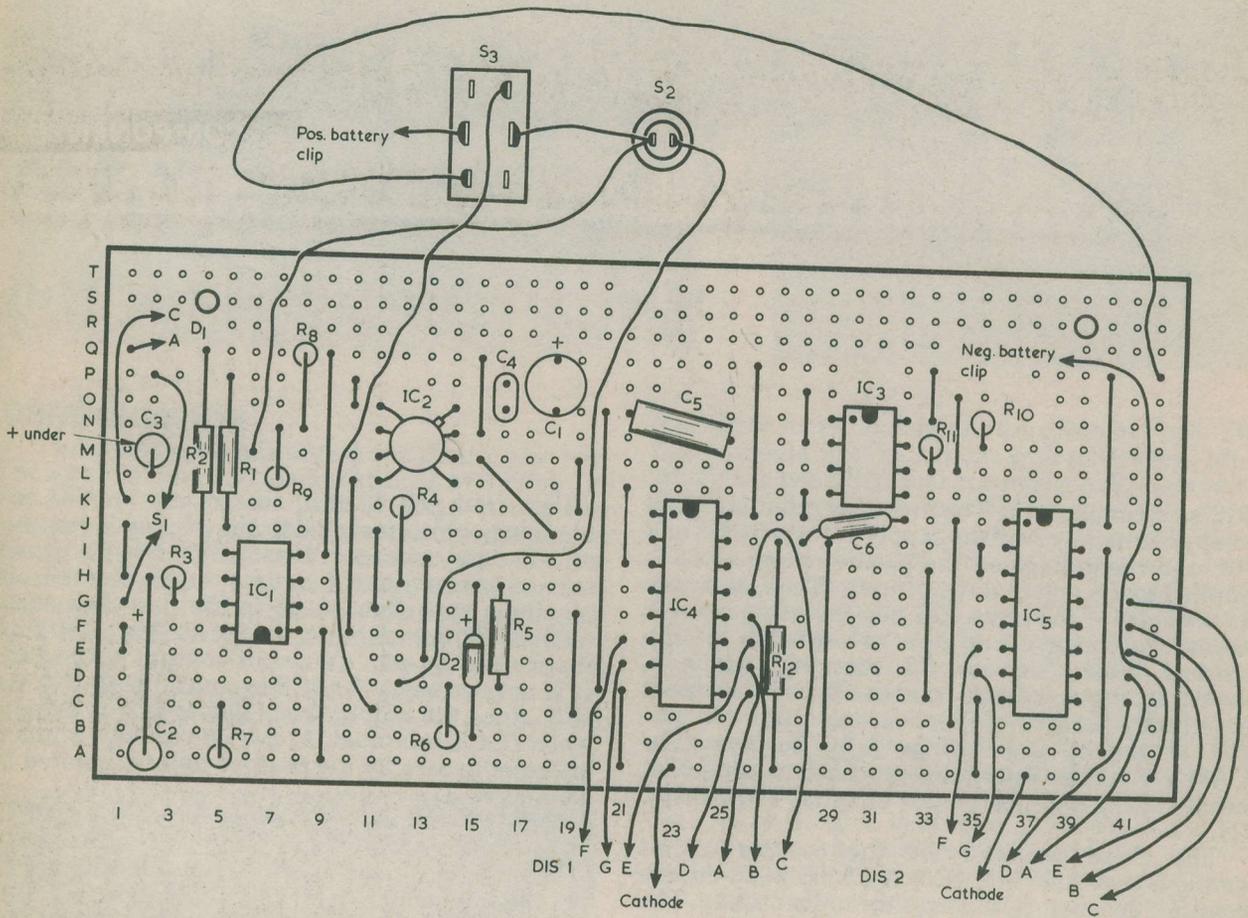

6BA clear

Fig.3. The wiring and layout of components on the Veroboard panel. IC4 and IC5 are fitted in i.c. holders and should be the last components to be fitted to the board

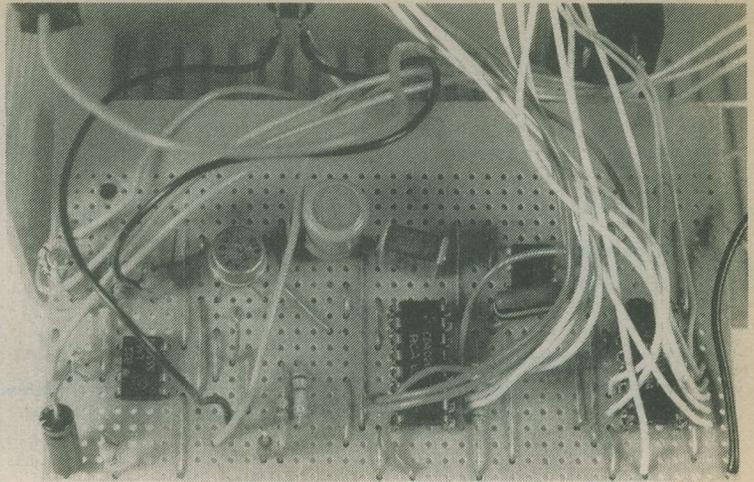The unit employs five integrated circuits and these, with most of the discrete components are assembled on a Veroboard panel



IC2 as a comparator. The inverting input is biased to approximately half the supply voltage by R8 and R9, and the voltage on the positive plate of C3 is applied to the non-inverting input. When, as occurs at the start of the game, the non-inverting input is negative of the inverting input so also is the op-amp output. When, due to C3 charging, the non-inverting input voltage rises and becomes even marginally positive of the inverting input, the output of the op-amp swings fully positive. The CA3130T has no internal compensation capacitor, necessitating the use of the external component, C4.

The clock oscillator for the counter circuit employs a second 555, IC3. A CMOS 4026 decade counter/decoder, IC4, drives the units display. The 4026 will couple directly to an efficient common cathode 7-segment l.e.d. display, and FND500 displays are employed in the prototype. A clock enable input on pin 2 is available with the 4026, and this is connected to the output of IC2. When IC2 output goes positive at the successful conclusion of a game the clock input of IC4 is inhibited and the count is then halted.

A CMOS 4033 device is used to drive the tens display. This is basically similar to the 4026, and it can also drive an efficient 7-segment display. It


differs from the 4026 in that it can provide zero blanking, which means that the display is switched off when the counter is at zero. This has the advantage of conserving the battery supply by not displaying a superfluous zero in the first digit of the readout. The clock signal for the 4033 is taken from the divided-by-ten "carry out" output of the 4026. It is not necessary for IC2 to control both IC4 and IC5, since the output from IC4 to IC5 is stopped when IC4 is inhibited. At switch-on, both counters are reset to zero by the positive pulse generated by C6 and R12.

On-off switching is provided by S3(b), and C1 gives all the supply decoupling that is necessary. When the unit is switched off, S3(a) discharges C3 via the low value current limiting resistor R7, so that the circuit is ready to commence a fresh game when it is next switched on.


Current consumption depends to a large extent on the number of display segments which happen to be turned on, and the current drain is normally within the range of 40 to 80mA. A fairly large 9 volt battery such as a PP7 or PP9 is needed for economical running.

The FND500 7-segment display is available from Messrs. Tom Powell, 306 St. Paul's Road, Highbury Corner, London, N.1.

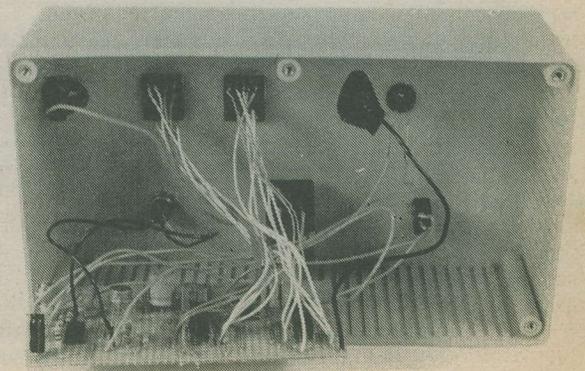The Veroboard panel is wired up to the components on the front panel before it is finally mounted to the rear panel of the case




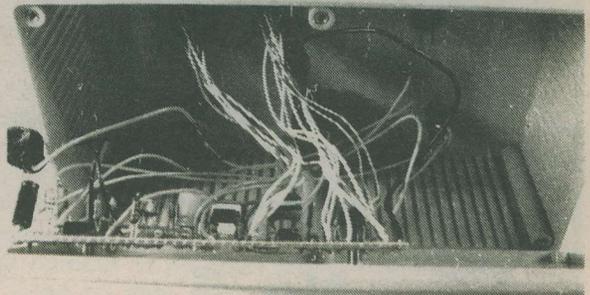Here, the Veroboard panel is secured in place. After the battery has been fitted, the rear panel is mounted in position on the case



CONSTRUCTION

The prototype is assembled in a plastic case having approximate outside dimensions of 190 by 110 by 60mm. Any plastic case of about this size or larger should be capable of accommodating the parts. The lid of the case becomes a removable rear panel and the Veroboard component panel is mounted on it. The displays, the l.e.d. indicator, and the three switches are mounted on the front panel, as can be seen in the accompanying photographs. The exact front panel layout is not critical and any sensible arrangement can be used.

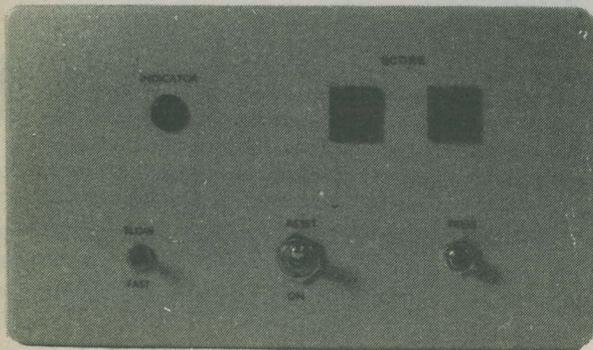

In the prototype the flashing l.e.d. is situated upper left on the front panel. To its right are the two 7-segment displays. Below, S3 is mounted centrally with S1 to its left and S2 to its right

The two displays each require a rectangular cut-out measuring 15mm. wide by 16mm. high. The cut-outs can be made by first drilling a central hole about 13mm. in diameter and then filing this out to the correct size and shape with a miniature flat file. Alternatively a fretsaw or coping saw could be used. The displays can be glued in place using a good quality adhesive such as an epoxy type or they can be made a tight push fit into the cut-outs. The decimal points of the displays are not used in the present application but they will assist in indicating which way up the displays should be mounted. Also, the indentations in the displays should be at the top. The specified FND500 displays have built-in display filters, incidentally.

The remaining components are assembled on a piece of 0.1in. matrix Veroboard having 42 holes by

20 copper strips, and details are given in Fig.3. The board should first be cut out with a hacksaw, after which the two 6BA clear mounting holes should be drilled. The layout requires a relatively large number of breaks in the copper strips and these should be made next. The link wires and components are then soldered in place. It is advisable to use i.c. holders for IC4 and IC5, since these are CMOS devices which can be damaged by high static voltages. The two i.c.'s should be fitted to these holders when all other wiring has been completed, and until that time should be left in their protective packaging. Care must also be taken with IC2, which has a MOS input stage, and this i.c. should also be left in its protective packaging until it is time for it to be fitted to the board. It should be the last component to be soldered into position, and the soldering iron must have a reliably earthed bit.

The completed component panel is wired up to the components on the front panel by means of thin flexible p.v.c. covered wires. The wiring is finally completed by connecting the two battery clips and the lead which connects between S2 and S3. The component board is then mounted on the rear panel of the case on the extreme left hand side, as viewed from the rear. This leaves a suitable space for the battery on the right, and the latter may be held in place by a simple home-made clamp. Spacing washers about 6mm. long should be fitted over the two 6BA mounting screws which secure the component board to the rear panel, these spacing the component board underside away from the panel. Without these washers the board would be strained and could crack when the mounting nuts and bolts were tightened up.

After giving the unit a thorough check for wiring errors a battery may be connected, and it is then ready for use.

It should be noted that if a player is very slow at completing the game the counter will cycle through a complete count and commence from zero once again. The actual score is then equal to the number displayed plus 100. Alternatively, the game can simply be considered as lost if the player fails to complete it before the count goes back to zero. ■

A few copies of the October 1975 issue containing the original 'Tantaliser' article by G. A. French, are still available price 65p, inclusive of postage (a free piece of veroboard is also contained in the issue).



really explains *microprocessors*

series
No. 5

By Ian Sinclair

Addressing Memory

In this fifth article in our 12-part series on microprocessors we examine the various methods employed for addressing memory.

You remember that, in part 4, we went over the ways in which the normal 1,2,3 count of the program register could be interrupted by jumps or by calling data out of memory? In this part we're going to look at these processes in more detail, because the way we can use a microprocessor very much depends on what methods we can use for memory addressing. Because memory addressing methods are important, what appears to be a bewildering variety of methods has been devised, and at first sight they all look pretty much alike.

IMMEDIATE ADDRESSING

Taking the simplest type of memory addressing first, immediate addressing means that the address of the data is the next address in the program. Immediate data is part of the program, so that when a program instruction is "immediate", then the next program byte is the data. For example, the instruction called "load immediate" will be followed in the program by a byte which is the number to be loaded into the accumulator. More of this follows in part 6; for the moment we can forget the immediate instructions, because they have no effect on the smooth flow of the program.

Two important types of memory addressing are DIRECT absolute addressing and IMPLIED addressing. There's also a method called INDIRECT addressing which is rather less common and which we'll leave out of this section. Because there are different methods of carrying out these address in-

structions, however, it often looks as if there are more types of addressing than really exist — some differences are so slight that they hardly merit separate descriptions. The addressing problem, remember, is that any address consists of two bytes, but the accumulator can hold only one byte at a time. Direct memory addressing looks straightforward. A typical direct memory addressing instruction would have a 1 byte instruction code followed by the two bytes which give the memory address. Some CPU's require the address bytes to be loaded in with the high order (the first byte of the number) first, others, notably the 6502 as used in KIM-1, require the reverse order. Whatever method of load-

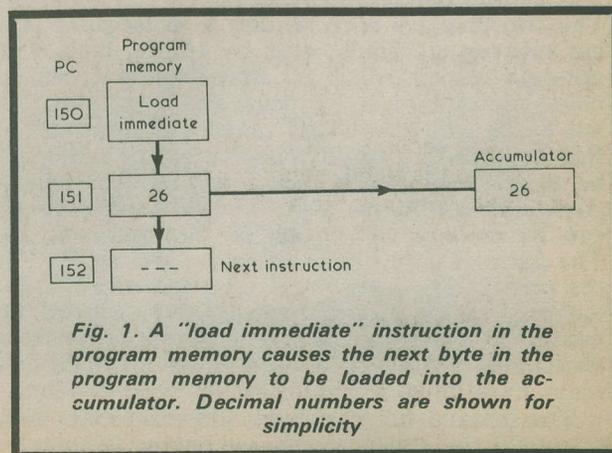


Fig. 1. A "load immediate" instruction in the program memory causes the next byte in the program memory to be loaded into the accumulator. Decimal numbers are shown for simplicity

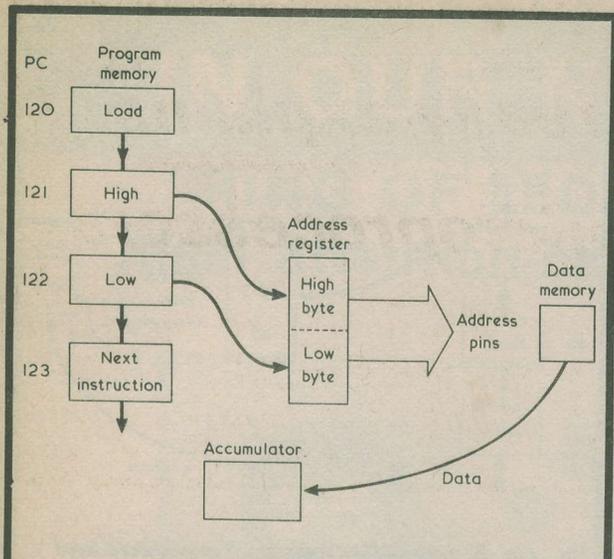


Fig. 2. Direct addressing. The instruction code is followed by two bytes which are assembled into a 16-bit number in an address register. This is then gated to the address pins, causing data to be released from the memory with that address. The data on the data lines is gated into the accumulator, completing the instruction

teen address lines. When fewer than sixteen address lines are used, the CPU is said to have paged memory access — for example if only ten lines were used the “memory page” would have $2^{10} = 1024$ addresses. The rest of the normal 65536 addresses are obtained by using other signals (such as bits from the program counter) as the “page numbers”.

Single byte memory instructions also restrict the range of addresses to a page of $2^8 = 256$ words. This would be unsatisfactory for some types of instruction, but acceptable for others, such as jump, because not many programs need to jump over a large number of program steps. The methods that are used to deal with paged memory are a bit beyond the scope of this series, however. What we want to look at for the moment are some of the methods of memory access, direct or implied, which are commonly used.

One very common method is what is called program-relative displacement; it is a two-byte instruction in which the first byte is the instruction code and the second is a pure number. The instruction is the byte which sets up the CPU ready for the number that follows. The number is a number of **program steps** added to the number that is already stored in the program counter. This number is called the **displacement**. Suppose, for example, that we are at program step number 21 (decimal), and the jump instruction byte is followed by 56 (decimal). The effect is then to add 56 to 21 giving 77 (decimal), so that the next program step we want is 77 (decimal). The number 77 (in binary, of course) would then be transferred to the data counter (or address register) so as to fetch the byte which is stored at that address. We’ve used the decimal numbers here rather than binary because they’re easier to follow, but the numbers which are handled by the program are, of course, binary numbers. This is a procedure for a jump, but we can also use this type of add-to-program-count method to find an address in memory to deposit or recover a byte of data.

ing is used in the program, the two byte number is the address of the memory which has to be read or loaded by the instruction. The word “direct” is a good reminder of what is done — the address of the memory is the byte pair directly following the instruction byte.

Implied addressing is rather more cunning. The memory address is loaded into the data counter, and the read or write instruction simply specifies the data counter — so switching the address lines to the data counter. If more than one register can be used for this purpose, the instruction byte will specify which register is used to store the address. The advantage of this method is that the address does not have to be specified right away — it can be loaded into the data counter (or whatever register is used) later, after all the rest of the program has been completed. The address can also be a number which is calculated during the program and loaded into the data counter.

Indirect addressing, incidentally, is a roundabout business in which two bytes of program contain an address which is loaded into the data counter. This address in memory contains one byte of another address, with the next byte in the address which is one greater (for example, addressing No. 59 for the first byte, with the second in 60). This second address is where the data is to be found. It has its advantages but not many programmers make much use of indirect addressing, and not all CPUs permit indirect addressing.

ADDRESS LINES

Not all CPUs allow direct addressing as we’ve described it either. Some instructions use only one byte, so that a full two byte address cannot be specified; a few CPUs have less than the normal six-

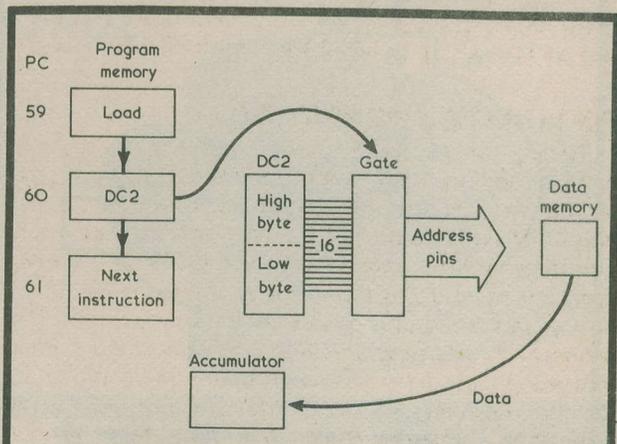


Fig. 3. Implied addressing. A two-byte address is stored in a data counter, DC2 in this example. The instruction to load, implied, followed by the code address of the data counter causes the number stored in DC2 to be gated to the address pins so that it fetches data from that memory address into the accumulator

NEGATIVE NUMBER

Do I hear an objection? It looks rather as if we could only add a number on, going to an address number higher than the one the program has reached. Don't you believe it — we can add a *negative* number, so that the program goes *back* a number of places equal to the number byte following the instruction. Now there's another objection — nobody has ever told you how a binary number can be labelled as + or -. Not now, folks, but definitely later.

The advantage of program-relative displacement (splendid phrase, isn't it?) is that it doesn't depend on any particular address being available. Let me explain that. Suppose we have a program starting at address 1, and at address 15 (decimal) there is a displacement of 10 (decimal), sending the counter to 25 (decimal). If now we need this row of memory addresses for some other program, we don't need to alter our program in any way — it can be fed in at any other address, and when the jump part of the program occurs, it's still a jump of ten places. If by contrast, the instruction had been one which forced the CPU to move to step number 25, that instruction would need to be changed if we moved the program to another patch of memory.

There's a disadvantage, though. For a reason that should become clearer later on when we discuss signed binary numbers, we can only displace the program counter by +127 or -128 places. For a lot of work, this isn't a serious restriction; and if we really need to get hold of an address more than these numbers away from the program count then there are other ways.

The type of program displacement we've just described is called direct program-relative displacement

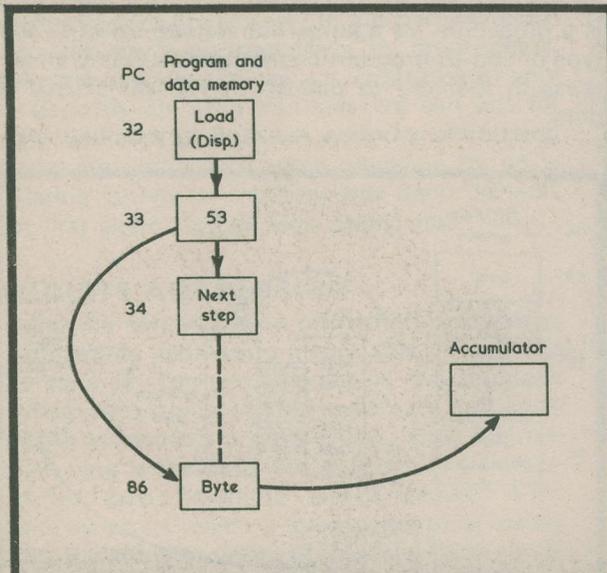


Fig. 4. Program-relative addressing. When the program-relative load instruction is used, the next byte in memory is added to the number which is in the program counter register, and the sum is used as a memory address. The address number must be fairly close (128 steps or less) to the step in program where this instruction is used

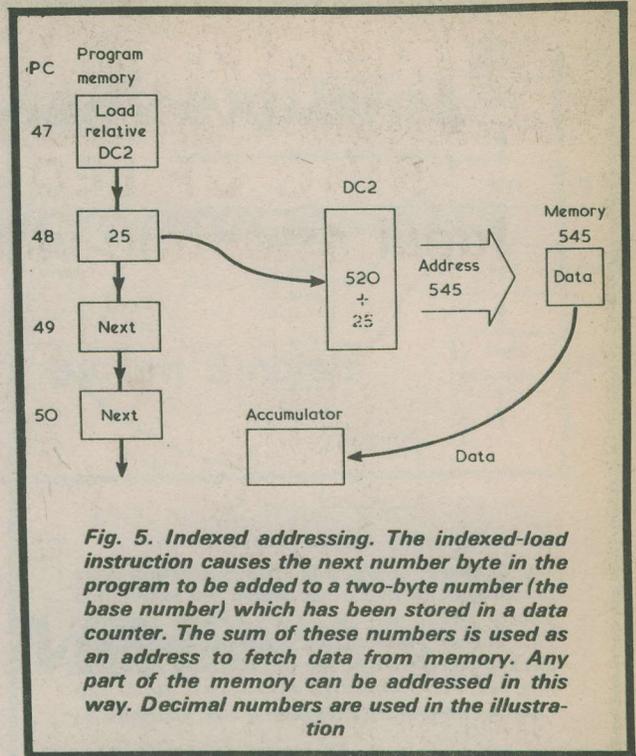


Fig. 5. Indexed addressing. The indexed-load instruction causes the next number byte in the program to be added to a two-byte number (the base number) which has been stored in a data counter. The sum of these numbers is used as an address to fetch data from memory. Any part of the memory can be addressed in this way. Decimal numbers are used in the illustration

ment — because the number of steps to be added to the program counter comes directly after the jump instruction. There's another type of program-relative displacement called *indexed* which involves a rather more roundabout method. When we use this sort of jump, the first byte, as usual, sets up the CPU ready for the next byte. The next byte once again is the number of steps to be displaced, but this displacement is not added to the number in the program counter. The program counter is held waiting, while this number is added to a number in the data counter and the total of these two is the address which is used in the instruction.


INDEXED DISPLACEMENT

Now that may look a rather elaborate way of adding a displacement, but it has its advantages. For example, while you're writing a program you may very well not know how many places you want to jump until the program is finished. Using indexed displacement, you can leave the decision until later, then enter the number into the data counter which is specified after the jump instruction. The step forward from this is true indexed addressing. In this memory addressing system, an address number stored in memory is added to the number in the data counter, or in some other register. The advantage of this system is that a much wider range of memory addresses can be accessed; in some types of CPU, for example, this is the only way of getting from one page of memory to the next.

All microprocessor CPUs can use this program-relative displacement systems, and some have interesting variations. One such variation is indexed displacement with increment. In this scheme, the jump instruction specifies a memory address in

IN OUR NEXT ISSUE

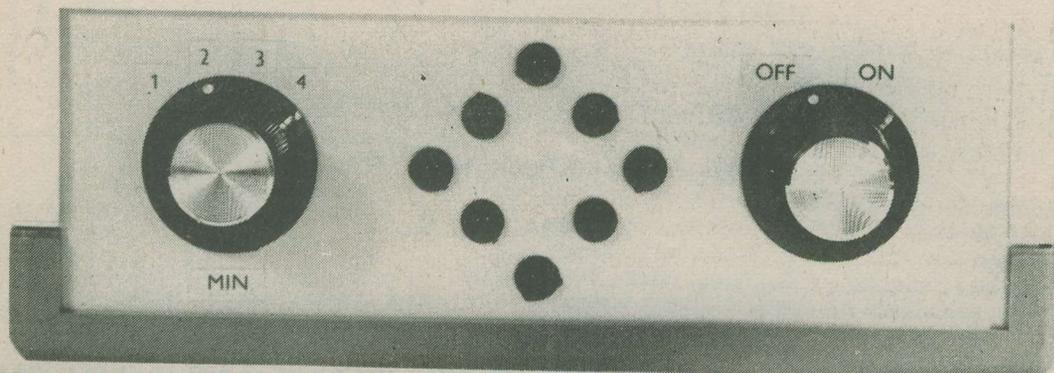"RING OF LEDS" PRINT TIMER
Ideal attention-catching presentation



UNIQUE DISPLAY indicates 8 segments of timing period

15 METRE DELTA BEAM

A "DX-grabbing" antenna which requires little outside space. Costs only a few pounds, this driven delta will work real DX and is equivalent to a 3-element Yagi in performance.

The antenna is very simple to construct and can be airborne in a couple of hours. The results should satisfy the most critical DX chaser.

IN YOUR WORKSHOP

SHORT WAVE NEWS

NEWS & COMMENT

ELECTRONICS DATA


Controlled
Voltage Gain

USING CMOS 555's

The CMOS 555 has now become available on the home constructor market. Known more properly as the ICM7555, it is a fully pin-compatible with the well-established bipolar 555 i.c., but draws a much lower supply current. It is suitable for supply voltages from 2 to 18, and its output can drive both t.t.l. and CMOS devices. The trigger and threshold pins have much higher input impedances than do the corresponding pins in the 555.

ULTRASONIC REMOTE CONTROL

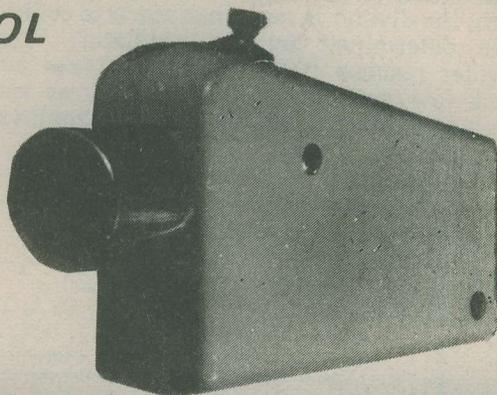- ★ Sequential on-off switching
- ★ Exceptionally low receiver consumption
- ★ Portable hand-held transmitter



RADIO & ELECTRONICS CONSTRUCTOR

LONG TIME LOW C

By E. A. Parr

50 MINUTE PARKING METER REMINDER USING THE FERRANTI ZN1034 TIMER.

For timing periods of up to a few minutes, the ubiquitous 555 timer i.c. reigns supreme. Unfortunately, the period is given by the formula:

$$T = 1.1RC,$$

which means that for periods above about 5 minutes the timing resistance goes into hundreds of kilohms, giving problems with leakage, and the capacitance goes into thousands of microfarads, resulting in problems with leakage, poor tolerance and cost.

FERRANTI ZN1034

The Ferranti ZN 1034 was designed to overcome these problems in a rather novel way. Its main internal connections are shown in Fig. 1. Basically, it consists of an oscillator and a 12 stage divider. The oscillator runs at a frequency determined by a timing resistor and capacitor. The 12 stage divider divides the oscillator frequency by 4096. When the chip is triggered (by a negative pulse on pin 1 or by application of the supply) output Q at pin 3 goes high; the divider is reset then starts to count up at a rate determined by the oscillator. When the divider reaches 4096 the control takes output Q back low again. This approach allows very long timing periods to be given for quite small values of

R and C. With pins 12 and 11 linked, the period is given by:

$$T = 2700RC.$$

With 500k Ω between pins 11 and 12 the period is:

$$T = 7500RC.$$

Another useful feature of the chip is the inclusion of a 5 volt shunt regulator on pin 5. This allows the timer to be run on a wide range of supply voltages from 5 volt d.c. up to (with suitable external components) 440 volts a.c.

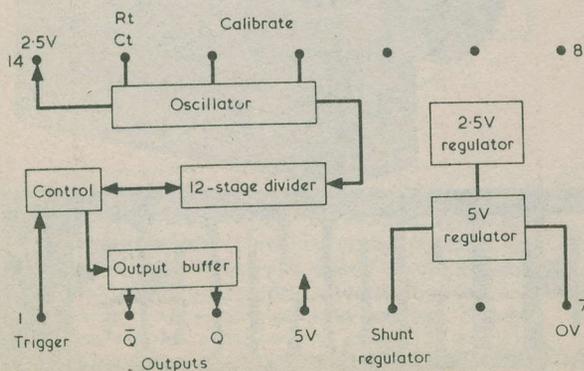


Fig. 1. The main internal functions of the ZN1034

COMPONENTS

Resistors

(All fixed values $\frac{1}{4}$ watt 5%)

R1 100k Ω

R2 470 Ω

R3 470 Ω

VR1 47k Ω pre-set potentiometer, 0.1 watt, horizontal

Capacitors

C1 10 μ F electrolytic, 10 V. Wkg.

C2 0.1 μ F ceramic disc or type C280

C3 10 μ F electrolytic, 10 V. Wkg.

C4 0.1 μ F ceramic disc or type C280

Semiconductors

IC1 ZN1034 in 14 pin d.i.l.

TR1 BC107

Switch

S1 see text

Battery

B1 9 volt battery type PP3

Buzzer

Audible alarm — see text

Miscellaneous

Veroboard, 0.1 in. matrix

Case — see text.

The output is taken from the not-Q output, which is low during the timing period and high when the timing is complete. The output turns TR1 on at the end of the timed period, sounding the audible alarm.

The timer is operated with pin 1 connected to the zero volt rail, and this initiates the timer when the supply is turned on. Switch S1 thus starts the timer. C3 decouples the battery and was found necessary because of the extra current drawn by the audible alarm.

CONSTRUCTION

The prototype was designed for pocket use, hence size was a problem. (The large values of capacitance necessary with a 555 would have needed large pockets!) The circuit was built on a small piece of 0.1 in. Veroboard with the layout shown in Fig. 3. This should be self-explanatory.

The case for the prototype caused some searching, until a domestic calculator died in a rather terminal manner. With the keyboard sawn off and the end made good with modeller's plasticard and plastic putty, it made an ideal case complete with battery compartment and connector! As an added bonus, the switch S1 was provided by the jack socket on the calculator side. Removal of the jack plug starts the timer, and the alarm is silenced by re-inserting the plug. This gives greater protection against inadvertent operation than a normal on-off switch, which could easily be knocked in a pocket.

When the circuit is first built, C1 should be 0.1μF. This will give a timing period of the order of 40 seconds, allowing correct operation to be checked and the circuit de-bugged.

CALIBRATION

With all the timing components at their nominal value, the calculated timing range is 45 to 67.5 minutes. In practice, tolerances in value, particularly with C1, may cause the desired timing period (50 minutes or 1 hour) to be outside the range of VR1. This discrepancy can be taken up by employing a different value for R1, as determined in the calibration process.

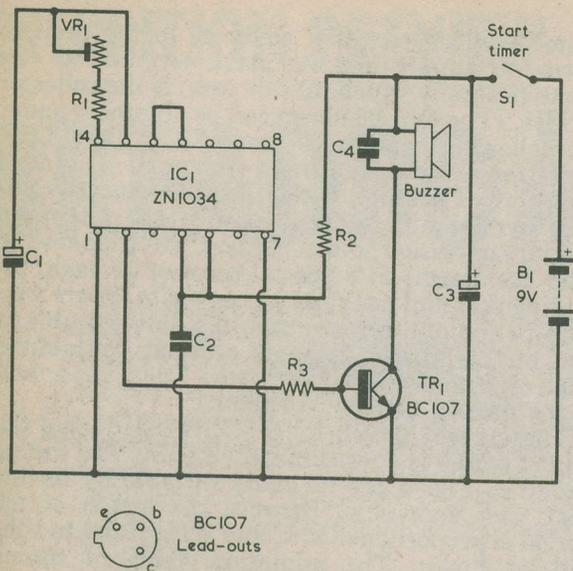


Fig. 2. The circuit of the parking meter reminder timer. This causes the buzzer to sound after 50 minutes

PARKING METER REMINDER

The author has used the ZN1034 in a number of applications, the most interesting of which is a parking meter reminder. This was designed to sound a miniature buzzer at the end of a 50 minute period, and the unit had to be small enough to fit in a pocket and run off a 9 volt battery. The circuit is shown in Fig. 2. The same circuit can also be employed to function as a 1 hour timer.

IC1 is the ZN1034, and R1 and C1 are timing components with fine adjustment being given by VR1. The circuit is powered by a 9 volt battery type PP3, and the internal shunt regulator on pin 5 is used to provide the 5 volt supply on pin 4. Resistor R2 is the dropper resistor and C2 a decoupling capacitor.

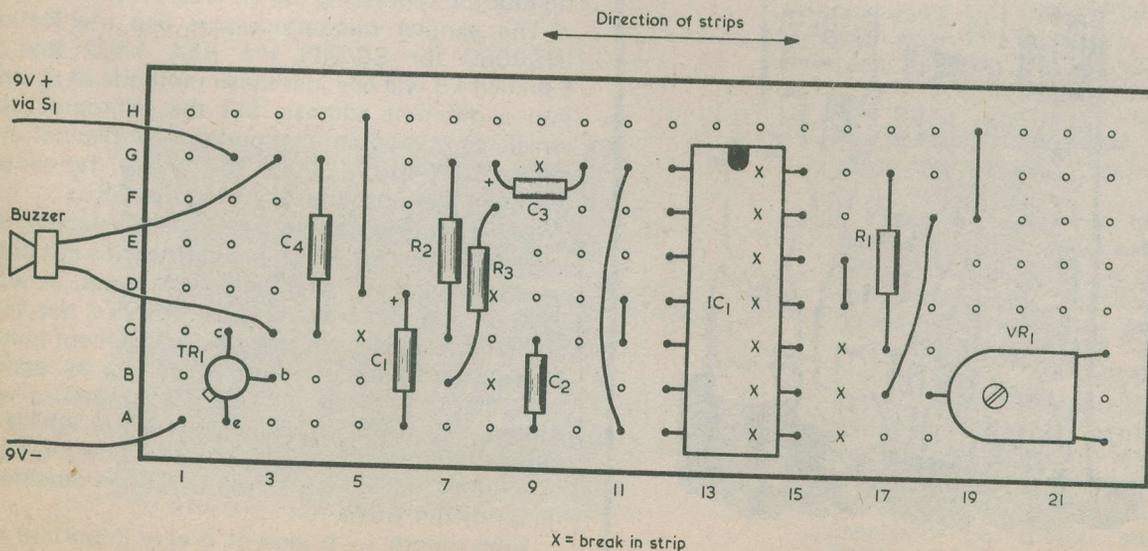


Fig. 3. The component side of the Veroboard assembly employed in the prototype

The calibration is a simple, but somewhat lengthy, procedure. With C1 at its correct nominal value of $10\mu\text{F}$, turn VR1 to its minimum resistance position and start the timer. Note the time which elapses before the buzzer sounds. The setting for VR1 (and the possible altered value in R1) can then be calculated.

Let us suppose the timer sounds after 45 minutes and we are aiming for a 50 minute period. 45 minutes corresponds to $100\text{k}\Omega$, and therefore 50 minutes corresponds, in kilohms, to 100 multiplied by 50 and divided by 45, or $111\text{k}\Omega$. The total value of R1 and VR1 is thus $111\text{k}\Omega$, and VR1 is then adjusted to insert $11\text{k}\Omega$. If we were aiming at a period of 60 minutes, the total value required in R1 and VR1 would be 100 multiplied by 60 and divided by 45, or $133\text{k}\Omega$. VR1 would then be adjusted for $33\text{k}\Omega$.

AUDIBLE ALARM

The audible alarm employed in the prototype was a miniature Solid State Electronic Buzzer type DM-03. This has approximate dimensions of 33 by 16 by 17 mm., draws a maximum current of 17mA at 9 volts and produces a rich clear sound when ac-

tuated. Its red terminal connects to the positive source of supply and its black terminal to the negative supply which, in this case, is the collector of TR1. (The DM-03 alarm can be obtained, under the following conditions, from Field Tech Ltd., Spitfire Road, Heathrow Airport, London, Hounslow, TW6 3AF. Field Tech Ltd. normally impose a minimum order charge of £10 but, as a special concession to our readers, are prepared to offer the alarms at a special price of £1 each, including post and packing, for *cash with orders only* for a period of 3 months from the date of publication of this article. Readers ordering the alarms must refer to *Radio & Electronics Constructor* and to the present article. — Editor.)

The current drawn by the ZN1034 during the timing period is approximately 8.5mA. The timing circuit of Fig. 2 can be made variable by having VR1 user accessible. Because the length of the period is proportional to R, any scale fitted to VR1 will be linear. The minimum value of timing resistance is $4\text{k}\Omega$, and the author has made a very useful timer covering 7 to 105 minutes by making C1 $33\mu\text{F}$, R1 $4.7\text{k}\Omega$ and by using a $100\text{k}\Omega$ multi-turn potentiometer in the VR1 position.

Databus Series No. 5

ADDRESSING MEMORY

(Continued from page 230)

which the displacement is stored, but *also* increments the address number so that each repeated


jump goes to a different memory address. This is a very smart method of making sure that different numbers are fed in each time there is a jump. The fancy name for this type of system is auto-incremented indexed program relative displacement. If no displacement is added, and no increment, then this "indexed" system is just the implied method of addressing which was described earlier.

The simpler microprocessors like the National INS8060 (or SC/MP) the REA 1802 and the Fairchild F8 will use just these methods of stepping into a different address, but the microprocessors which are used in computing, as distinct from machine control, need the more far-ranging methods like absolute direct addressing.

Convenient as program-relative displacement is for small programs which are in RAM, it's not entirely satisfactory for machine-control work, in which most of the memory is ROM. There's not much point, for example, in adding a displacement number to a program number, and so getting an address which is an address in ROM if you need to write data out to RAM. In the simpler CPUs which use only program relative displacement, indexing has to be used to provide addresses which are outside the range of the ROM.

Next month — a look at a very important data register, the accumulator.

(To be continued)

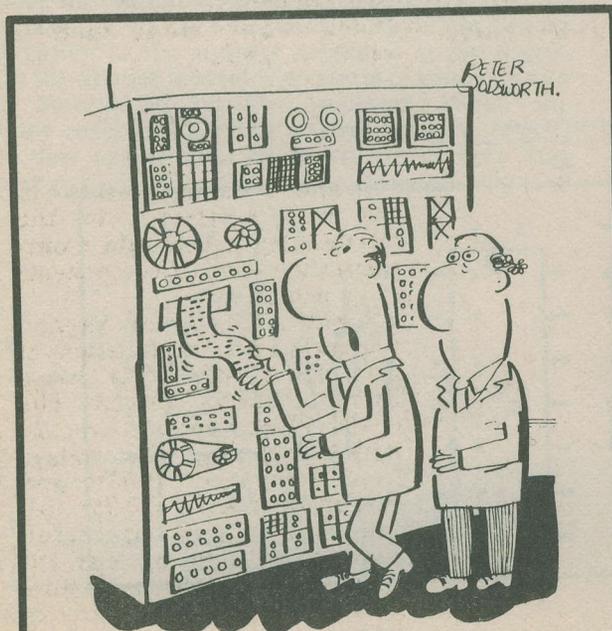

"It wants to know when Pay-day is".

EXHIBITION PREVIEW

BREADBOARD '79

Following upon the great success of last year's **Breadboard 78**, which attracted more than 10,000 visitors, the organisers, **Trident International Exhibitions Ltd.**, have booked the Royal Horticultural Halls at Elverton Street, Westminster from Tuesday 4th December to Saturday 8th December for an even bigger exhibition — **Breadboard 79**.

Breadboard 79 will contain more than 90 exhibition stands accommodating UK, and overseas, manufacturers and suppliers of components, tools and test equipment. The stands will feature microcomputer systems, analysers, logic test accessories, hi-fi kits, modulators etc., as well as a varied range of construction kits and TV games.

There will also be a number of competitions and demonstrations in which visitors can participate.

We give brief details of some of the items to be exhibited which will be of special interest to our readers.

Ambit International will include among the many items on their stand the DFM3 shown in the photograph. The DFM3 was introduced in response to many requests for received frequency displays for portable operation.

The DFM3 incorporates a 5 digit LCD, giving direct frequency display on the following ranges:

VHF with 10kHz resolution up to 200MHz typ (limited by prescaler — theoretical maximum is 399.99MHz).

Direct reading the above range without IF offset.

LW/MW with 100Hz resolution for the Marine DF channels.

LW/SW with 1KHz resolution for up to 39.999 MHz.

The IF offsets include all standards around 450-470kHz for AM, plus 2MHz and 10.7MHz for shortwave in addition to the 450-470kHz ranges. VHF offsets are based around 10.7MHz.


The unit is supplied for panel

mounting as a double deck system, with the rear section being devoted to input shaping and prescaler operations. The front section carrying the main IC and display can be used independently in the AM mode only, providing facilities for portable DF receivers where the total current drain of 4mA is essential.

The display is static, thus creating no strobing interference, and enabling the last digit stage to be incorporated in a simple frequency stabilizer sensor system.

Made in England by Ambit International
Price ready made module £44.90 + VAT.

* * * *

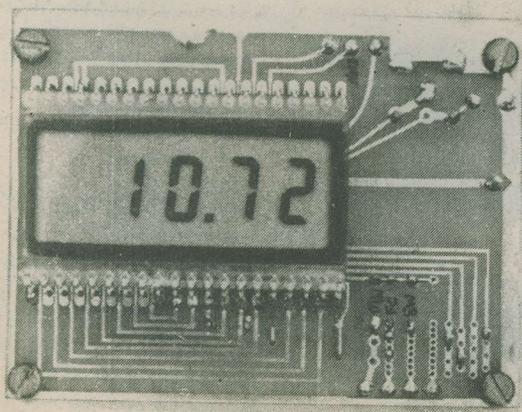

Ambit continue receiver frequency display line with the DFM3

A brief mention of just two of the new additions to the **Stevenson Electronic Components** range of components to be exhibited.

First a range of rugged general purpose multimeters of very high quality yet as always very reasonably priced. The model illustrated has over 20 ranges including DC voltage from 100mV to 1000V and current from 50µA to 0.25A. All ranges are well protected against voltage or current overload. An interesting feature is its ability to read directly transistor parameters such as hFE and I_{ceo}.

The meter comes complete with probes, batteries, and a


comprehensive manual, and is priced at £12.95 (inc VAT).

A second new line represents an article which in these days of digital electronics is increasingly difficult to find, but for which in many applications there is no substitute. A range of 2" moving coil panel meters with an attractive modern appearance and a tough acrylic face. The window is slightly raised so that the meter may be mounted behind a rectangular cutout in the panel. Alternatively bolts are provided at the rear for front mounting.

There is a wide choice of ranges including a VU meter and an illumination kit is available which is easily installed. Price is £4.75 for the meter and 50p for the illumination kit.



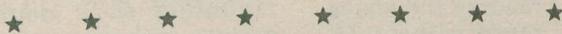The HT-320 multimeter from Stevenson Electronic Components




At Breadboard 1979, **Continental Specialties Corporation (U.K.) Ltd.** is featuring its extensive range of prototyping boards and accessories for circuit designers, as well as several new ranges of low-cost digital troubleshooting and test aids for the development, production or service environment.

Among the new products on show is the CSC Experimentor family of modular solderless bradboards, designed to provide a quick, simple method of realising electronic circuits. The Experimentor breadboards can be used in conjunction with the unique 'Scratchboard' worksheet concept to provide rapid documentation of circuit designs, and Experimentor 'Matchboard' pre-drilled, pre-etched printed-circuit boards are available if a permanent circuit is required.

New low-cost test instruments on show include the MAX-100 frequency counter and associated prescaler; the miniature MAX-550 frequency counter, which operates at up to 550MHz; the Model 2001 sweepable function generator, which can produce sine, square or triangle waves at up to 100kHz.

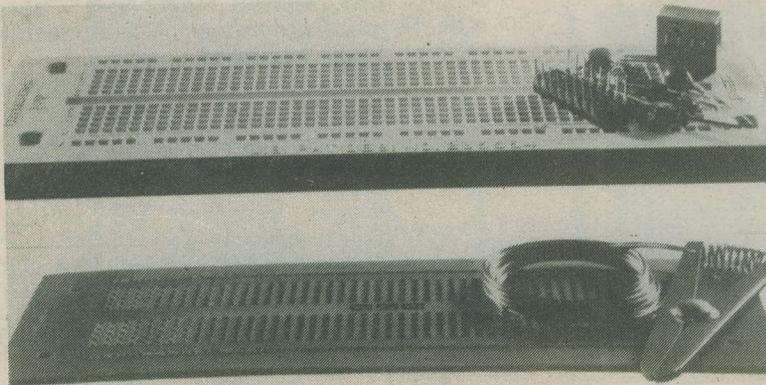CSC is also showing a range of circuit-powered digital troubleshooting equipment, including logic probes, digital pulsers, logic monitors and logic test kits.



The continental Specialties Corporation Experimentor system of solderless bradboard and, underneath, the matchboard pre-drilled

EXHIBITORS

- Ace Mailtronix Ltd.
- Acorn Microcomputers Ltd.
- Alcon Instruments Limited
- Ambit International**
- Amtron UK Limited
- Aura Sounds
- Bernard Babani (Publishing) Ltd.**
- Bi-Pak Semiconductors**
- Boss Industrial Mouldings Limited
- T. J. Brine Associates
- The British Amateur Electronics Club**
- Carston Electronics Ltd.
- Charcroft Electronics Ltd.
- Chordgate Limited
- Chromasonic Electronics
- Chromatronics
- Clef Products
- Commodore Systems Division
- The Component Centre
- Compshop Ltd.
- Continental Specialties Corporation**
- Crael UK Ltd.
- Crimson Elektrik
- Crofton Electronics Limited
- De Boer Elektronika
- Electronic Organ Constructors Society
- Electronics Today International
- Electroni-Kit Ltd.
- Electrovalue Ltd.
- Everyday Electronics
- Expo (Drills) Limited
- Falcon Acoustics Ltd
- GMT Electronics
- Hart Electronics
- Havant Instruments Ltd.
- Henry's Radio
- Lektrokit Limited
- Light Soldering Developments Limited
- LINDY-Klaus Lindenberg KG
- Lotus Sound
- Manx Electronics
- M.C. Marketing
- Magnum Audio Ltd.
- Maplin Electronic Supplies Ltd.**
- A. Marshall (London) Ltd.
- Medelec Ltd.
- Microdigital Ltd.

One of Maplins
range of synthesisers




Exhibitors (continued)

N.I.C. Models
The Newbear Computing Store
OK Machine & Tool (UK) Ltd.
P.I.L. Ltd.
T. Powell
Powertran Electronics
Practical Computing
Practical Electronics
Sentinel Supply
Stevenson Electronics Components
Strutt Electrical & Mechanical
Engineering Ltd.
Transam Components Ltd.
TUAC Ltd
Two Plus One Components Ltd.
Vero Electronics Ltd.
Watford Electronics
West Hyde Developments Ltd.

One of the major exhibitors at Breadboard will be **Maplin Electronic Supplies**. This company is looking forward to being able to attend this exhibition as it provides such a golden opportunity to greet all their customers and exchange views. This year's change of venue to the Agricultural Halls will be a great asset as they offer a lot more room for the public to browse and play with or buy any of the many items on show. Maplin will have a full arena of exhibits.

Their range of project kits will be on display with special attention being given to the organ and synthesizer (see photo) for which professional musicians will be in attendance giving continuous demonstrations with Mr. John Parker on the organ and Mr. Mike Beecher putting the new 5600 synthesizer through its paces.

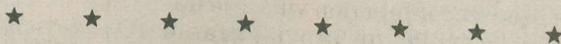
In addition many of the lines shown in this company's large catalogue will be on sale along with their range of leaflets.



Due to the success of last year's show, **BI-PAK Semiconductors** are very pleased to be taking part in the second London Breadboard Exhibition. The name BI-PAK is now well known, not only to enthusiasts, but right across the electronics industry having been in the forefront of the distribution market for some fourteen years.

Over those years their growth has been considerable and yet they still manage to keep in touch with customers' requirements for quality components at competitive prices and maintain a same day service.

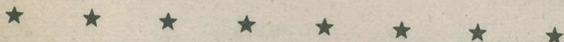
They will again be demonstrating and exhibiting their full range of Bi-Kits and high quality audio modules, including some new additions. Also there will be a large selection of semiconductors and components on sale.



Bernard Babani (Publishing) Ltd will be displaying their entire range of publications.

The series of titles is one of the largest available and covers practically every aspect of radio and electronics with subjects to interest all enthusiasts from the complete beginner to the highly experienced. All their books offer extremely good value, being inexpensive paperbacks ranging in price from 25p to £2.75.

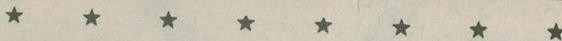Their new 1980 eight page descriptive catalogue covering all their books will be available **FREE** to all visitors to their Stand.



The British Amateur Electronics Club (B.A.E.C.) is the only national amateur electronics club in this country, and its importance is widely recognised in the world of amateur electronics, including exhibitors at Breadboard '79.

Members keep in touch and help each other through the quarterly B.A.E.C. Newsletters and several exhibitors will be offering special concessions to B.A.E.C. members. The B.A.E.C. Stand will be the place to go for friendly discussions on amateur electronics and a chance to play with elec-

VMOS POWER DEVICES—Part 1

By John Baker

The first of two articles describing applications for the new VMOS power transistors

VMOS power field-effect transistors are not a new development but they have only been in existence for a few years and it is only recently that they have become available to the amateur experimenter. Previous f.e.t. types have been mainly suitable for low power applications, such as high impedance buffer amplifiers, low noise pre-amplifiers and similar functions. Devices such as the 2N3819, 2N3820, etc., have maximum dissipation figures of a few hundred milliwatts, and at first sight could conceivably be considered suitable for medium power applications, such as in the output stages of portable radios. In practice, however, they are unsuitable for such applications since their drain-to-source resistance when made fully conductive is unlikely to be less than about $100\ \Omega$ and could be as much as several times this figure. An f.e.t. audio output stage, employing devices of this type, would obviously give very poor efficiency even when driving a high impedance loudspeaker.

VMOS devices, or "vertical" f.e.t.'s as they are sometimes called, have the structure shown in the representative cross-sectional diagram of Fig. 1. The current flows vertically between the drain and the source, rather than horizontally as is the case with an ordinary JUGFET or MOSFET. It is the unusual VMOS structure which enables VMOS devices to handle high powers and currents.

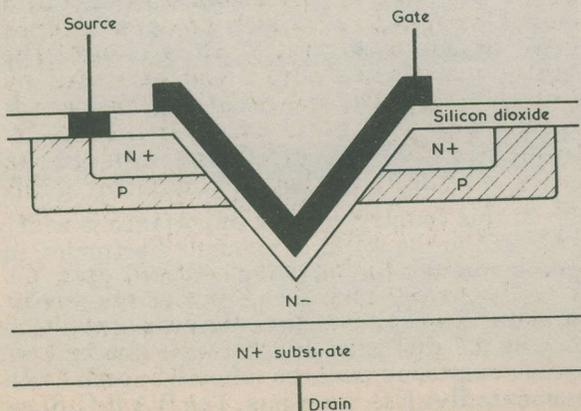


Fig. 1. A cross-section illustrating the internal

AVAILABLE TYPES

At the time of writing, three medium power VMOS devices are readily available to the amateur user, these being the VN46AF, VN66AF and VN88AF, all of which are manufactured by the Siliconix Corporation. They may be obtained from Maplin Electronic Supplies. The main difference between these three devices are their maximum drain-to-source voltage ratings, which are 40 volts, 60 volts and 80 volts respectively. They are all in a TO-220 encapsulation, have a maximum drain-to-source current rating of 2 amps and a maximum power dissipation of 12.5 watts.

These VMOS devices are enhancement f.e.t.'s rather than the depletion types which are more often encountered. A depletion f.e.t. is normally in the on state, and its gate must be reversed biased with respect to its source in order to turn off the device or bias it for linear operation. An enhancement mode f.e.t. is much more like an ordinary bipolar transistor in that it is normally turned off, and its gate must be forward biased with respect to its source if it is to be turned on. For a drain-to-source current of 1mA, the VMOS devices require a forward bias of between 1.8 and 2 volts. Like ordinary f.e.t.'s, these transistors are voltage rather than current operated, and they have very high input impedances. The drain-to-source saturation voltage with a gate bias of 10 volts and a drain current of 1 amp is 3 volts maximum (4 volts maximum for the VN88AF).

ADVANTAGES

VMOS f.e.t.'s have several advantages over bipolar power transistors, the most obvious being their very high input impedance. This makes it possible for the device to provide an output current of an amp or more whilst being driven from a high impedance circuit, since no significant input current is drawn by a VMOS transistor. In consequence, a single VMOS device can often be employed where two or three bipolar transistors connected in a Darlington configuration would be needed. This fact can offset one disadvantage of VMOS transistors, which is their slightly higher cost (at the time of writing) when compared with most bipolar power devices.

Another advantage with VMOS transistors is the fact that they do not have the minority carrier storage time effect associated with bipolar transistors, since they are majority carrier devices. In practice this means that they have a very fast switching speed, the actual figures for the devices mentioned here being 2 nanoseconds typical and 5 nanoseconds maximum. Typical FT is 600MHz.

A third advantage of VMOS transistors is that they do not suffer from thermal runaway and secondary breakdown. Bipolar transistors are subject to thermal runaway because they have a positive temperature coefficient; as they increase in temperature they conduct more heavily, thereby producing increased power dissipation and further temperature rise. Unless appropriate steps are taken, this regenerative process can easily continue until the transistor is destroyed. Secondary breakdown can be regarded as a form of localised thermal runaway within a transistor, and it limits the maximum voltage-current combination that can be safely handled. VMOS devices have a negative temperature coefficient, so that increased temperature causes a reduced current flow. Thus, a sort of negative feedback action prevents thermal runaway and secondary breakdown.

There are disadvantages to VMOS transistors which are, once more, applicable at the time of writing. The main disadvantage is that the saturation voltage is higher than that of a bipolar transistor, whereupon they become slightly less efficient in some applications. Another disadvantage is that, in the power range being considered here, only n-channel devices are available at present. It is probable that future developments will overcome these problems.

TOUCH SWITCH

The remainder of this present article will be devoted to two circuits incorporating a VMOS transistor, and the first of these is shown in Fig. 2. The diagram shows a very simple touch switch which demonstrates the main properties of a VMOS device.

It is assumed that, when power is first applied to the circuit, C1 is in a discharged state. TR1 is, as a result, turned off. Only leakage current will flow in the load and at most this should be only $10\mu\text{A}$. The leakage currents in several prototype circuits were all much less than $1\mu\text{A}$; too low, in fact, for the author to detect at all.

The switch can be set to the on state by touching the upper set of contacts. C1 then charges up to the supply rail voltage through the skin resistance of the operator, biasing TR1 into the on state. The circuit will remain in this state until C1 gradually discharges into TR1 gate and through its own leakage resistance, or until the operator touches the lower set of contacts to provide a discharge path through his skin resistance. The input resistance of TR1 and the leakage resistance of C1 will both be extremely high, and it is found in practice that the circuit seems to stay in the on state indefinitely.

The touch contacts do not need to be particularly efficient in terms of low contact resistance with the skin of the finger which touches them, as a high resistance here will merely increase the time taken for the circuit to switch from one state to the other, rather than preventing the circuit from working at all. On the other hand it is important to ensure that there is a very high resistance between the contacts since even a minute leakage current would be sufficient to prevent the circuit from functioning correctly. For the same reason there must be very high resistance in the wiring to the transistor gate lead-out, and the capacitor must be a good quality plastic foil component.

The touch switch circuit works well with loads drawing current up to about 100mA. At these currents there is no significant voltage drop across TR1 when it is turned on.

CMOS TIMER

An obvious field of application for VMOS devices is as an output switching device driven by CMOS logic. An example is given in the CMOS timer of Fig. 3. Here, two gates of a CMOS 4001 quad 2-input NOR i.c. are connected to act as a monostable multivibrator which produces a timed positive output when switch S1 is closed. The length of the positive output can be varied by means of VR1. The range of timing periods available will vary to a small extent due to tolerances in the value of C2 and variations in transfer characteristic between different NOR gates, but it should be of the order of less than 1 second to slightly in excess of 1 minute.

At the end of a timing period, with S1 open, C1 will be discharged and the output at the second gate, at pin 4, will be low. Both the inputs, at pins 1 and 2, of the first gate will therefore also be low, and the first gate output, at pin 3, will be high. If S1 is momentarily closed, pin 1 of the first gate will be taken high causing pin 3 to go low. Since C2 is discharged, pins 5 and 6 of the second gate will also be taken low, and its output will go high, maintaining

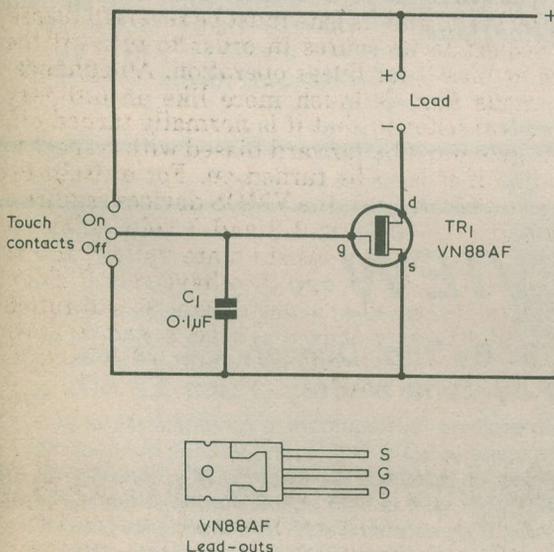


Fig. 2. A very simple touch switch incorporating a VMOS transistor. If leakage resistances are kept very high the circuit remains almost indefinitely in the on or the off state

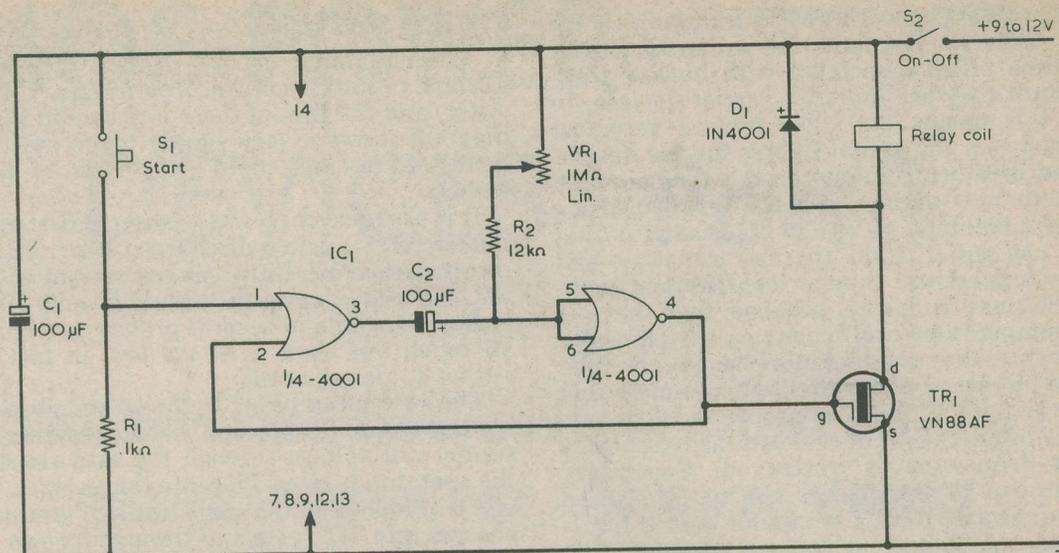


Fig. 3. A timing circuit in which the output of a CMOS gate couples directly to the gate of the VMOS transistor. The loading placed on the CMOS output is negligibly low

the low output at pin 3 of the first gate. The high output of the second gate turns on TR1 and causes the relay, whose coil is in its drain circuit, to energise.

C2 commences to charge via R2 and VR1. When its right hand plate is sufficiently positive the output of the second gate starts to go negative, taking pin 2 of the first gate negative also. The overall gain in the two gates results in a fairly rapid transition to the original state in which the output at pin 3 of the first gate is high and pin 4 of the second gate is low. The timing period is then over, with TR1 turned off and the relay de-energised.

The low current output of a CMOS gate is not sufficient to energise a relay directly, and a VMOS transistor is an ideal device for converting a CMOS

output voltage to a high load current. Indeed, a CMOS output could actually drive more than a hundred VMOS transistors.

As with the touch switch of Fig. 2, the VMOS transistor of Fig. 3 can readily provide output load currents up to 100mA. This enables relays with quite low coil resistances to be used.

NEXT MONTH

In next month's concluding article, we shall discuss the use of VMOS devices in the output stages of a.f. amplifiers and in other applications.

(To be concluded)

BOOK REVIEW

ADVENTURES WITH ELECTRONICS. By Tom Duncan. 64 pages, 245 x 190mm (9¾ x 7½in). Published by John Murray. Price £2.50.

This hard cover book presents simple constructional projects for beginners, a particular feature being that no soldering is required. The assemblies are made up on S-DeC's, and various methods are employed for making connections which would normally be soldered. For instance, if a transistor lead-out is to be extended a piece of 22 s.w.g. tinned copper wire is held against the lead-out by passing 1mm bore rubber or plastic sleeving over the two. If an earphone with stranded leads is to be connected to the S-DeC, the neat trick of opening out one leg of a paper clip is recommended. The opened-out part of the clip is passed into the S-DeC hole and the stranded lead is held in the remaining section.

After an introductory passage the book proceeds to a few simple circuits and then describes fifteen projects. These include a rain detector, a burglar alarm, an electronic metronome and an f.e.t. radio. The book carries on to two short sections covering the working of radio and the testing of transistors, and concludes with a list of the parts required for the projects. The components may be purchased individually or as a complete kit for the book.

"Adventures With Electronics" is printed in red and black, and has an imaginative approach which will particularly appeal to the younger reader.

Radio Topics

By Recorder



Now that everybody is going mad about microprocessors, it becomes desirable for all of us to get at least a smattering of knowledge about some of the things which go on in the realm of what the media keep referring to, annoyingly, as the "silicone chip". The extra "e" added to the correct word "silicon" conjures up horrible visions of chunks of unhealthy looking potato fried up in silicone grease.

One of the mildly eccentric points about microcomputer i.c.'s is the numbering of inputs and outputs. Instead of numbering these in the order 1, 2, 3, 4, 5 and so on, the first input is numbered zero, giving the series 0, 1, 2, 3, 4, etc.

2 TO THE NOUGHT

Perhaps this makes sense when we consider binary numbers. We may in reading about microprocessors encounter the number 1111111, which consists of seven binary digits. This is obviously 1 less than 10000000 which, when we count the number of digits (8) we may erroneously assume to be 2 to the power of 8, or 256. The number 1111111 must therefore be 1 less, or 255.

But we would be wrong because 10000000 is not 2 to the power of 8, but is 2 to the power of 7, which is equal in decimal to 128. Why is this? It is because the least significant digit in the number, the one at the extreme right, does not represent 2 to the power of 1, it represents 2 to the power of zero.

Let's try it with smaller binary numbers. 100 in binary is 4 in decimal, and is obviously equal to 2 squared or 2 to the power of 2. If we count the number of digits, from right to left, we do not use the series 1, 2, 3 but, instead, the series 0, 1, 2 to arrive at the correct power of 2. With the binary number 1000, the digits, counting from right to left, number 0, 1, 2, 3. So 1000 is 2 to

the power of 3, or 2 cubed, or 8 in decimal.

The same state of affairs exists in decimal. 100 in decimal is 10 to the power of 2, as can be determined by counting the digits from right to left, using the sequence 0, 1, 2.

NUMBER DOODLES

Whilst on the subject of numbers, some mild and harmless amusement can be obtained from doodling with pocket calculators. As an example, key in any number from 1 to 9 inclusive, and then multiply this by 3. Multiply again by 7, then by 11, then by 13 and then finally by 37. After this, press the "equals" button.

The numbers 11 and 101 multiplied together in any order produce palindromic number (numbers which read the same in both directions) until you take the number of

Most people know the result of keying in 7734 and then turning the calculator upside-down. Another number which can be treated in the same manner is 58008.

POWER SUPPLIES

The illustration shows the smart lines of the TPS 21 bench power supply now available from Gresham Lion Limited, Gresham House, Twickenham Road, Feltham, Middlesex, TW13 6HA.

Output voltage on all types is adjusted by a high-accuracy 10-turn potentiometer mounted on the front panel, and this allows setting to be carried out to within 5mV. Similarly, current trip adjustment is made using a single turn "Cermet" potentiometer. In the range, the TPS 20 power supply offers a single variable voltage from 0 to 30 volts with current limiting up to 1 amp and a separate 5 volt 1 amp output. The TPS 21 gives two 0-30 volt outputs up to 1 amp, together with a 5 volt 3 amp output. Variations on the TPS 21 are the TPS 21D, which has i.e.d. digital displays instead of meters, and the TPS 23A with variable current limiting up to 2 amps. The two remaining power supplies in the range are the TPS 25 with a single 0-40 volt output and variable current limiting up to 1 amp, and the TPS 28 which offers a single variable 0-60 volt output at 2 amps maximum, or tracked 0-30 volt positive and negative outputs, again up to 2 amps maximum.




Bench power supply type TPS 21. This is one of a new range of precision power supplies manufactured by Gresham Lion Limited

multiplications too high. For instance, try keying in 11 times 11 times 101 times 101 equals. The result will stand another multiplication by 11 before the number becomes too large.

I can't guarantee that all calculators will give the desired answer to the next little doodle, but it's worth trying. Key in 9.876543 and then divide it by 8. The result, with simpler calculators, should be 1.2345678.

CAM SWITCHES

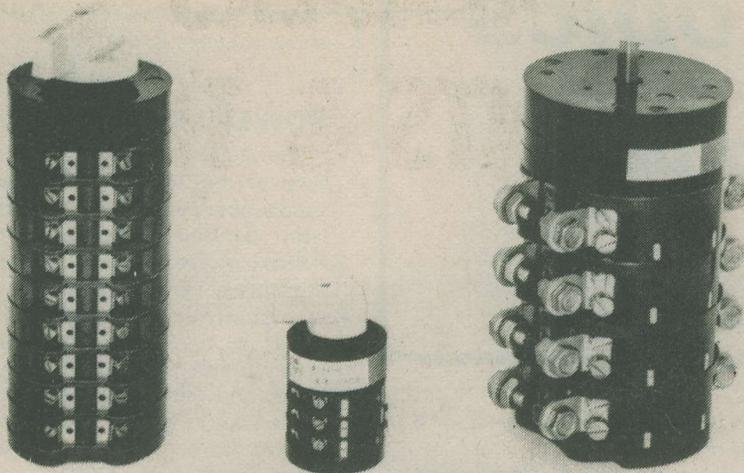The cylindrical components with terminals in the second photograph are husky rotary cam switches marketed by J & N Wade (Switches) Limited. Meeting most European specifications, these switches feature a positioning cell which determines the switching angle (30, 45, 60 or 90 degrees) and also sets the start and stop positions of the switching function. Either one or two double-make,



Cam switches of 16 and 25 amp rating available from J & N Wade (Switches) Limited. These versatile and rugged units can be adapted to control a wide range of high current switching circuits

double-break contacts are available, and the switch design enables the user to employ up to 72 contacts by using, for example, a three-column unit having a single operating handle.

The switches are available for mains, on-off, changeover, step control, starter, motor reversing, voltmeter, ammeter, wattmeter and group control applications. Spring return functions are available on many of the switches and a range of series-parallel units is also available.

The switches are described as 16 amp (type K) and 25 amp (type A) units. Voltage ratings are up to 660 volts, and thermal current ratings range from 16 to 200 amps, or 2,000 amps with contacts in parallel. Further details may be obtained from J & N Wade (Switches) Limited, Limberline Road, Hilsea Industrial Estate, Portsmouth, PO3 5JQ.

IMMERSION SWITCH

I have just received a sample of the new Immersion Heater Time Switch manufactured by Smiths Industries Limited, and a very neat little item it is, too. Intended for operation from 220 to 250 volt 50Hz mains supplies, it is capable of switching on an off resistive loads up to a maximum of 16 amps. In its nominal application as an immersion heater time switch it can offer savings in electricity since it automatically provides just the right amount of water heating in each day. There is no need to rely on memory. The switch can, of course, be used for switching resistive loads other than immersion heaters.

The switch measures 2 3/4 in. square by 2 1/4 in. deep, and can be fitted directly into any flush conduit fixing or surface mounted switch

box. It is supplied complete with mounting screws and bracket and can be purchased from electrical retailers.

The timing mechanism incorporates a plastic ring, calibrated in hours from 1 to 24, which is driven by the internal synchronous clock so that it rotates once every 24 hours. Near the periphery of the ring are two concentric circles of holes, these being spaced out at quarter hour intervals. A metal peg is inserted at the appropriate hole in the inner circle to give switch-on, and a second peg is fitted to another hole in the outer circle to provide the switch-off function. Four additional pegs are provided, enabling the controlled item to be switched on and off two or even three times a day. A lever at the front of the switch can be manually actuated to switch the load on or off (apart from a period up to ten minutes after a timing operation, during which the lever action is inhibited) and the timer will then automatically take over the subsequent switching off or on at the appropriate time. Indeed, the timer can have only one peg inserted, whereupon it simply switches on or off at a predetermined time.

EARTH STATION

Now fully operational at Madley, Herefordshire, is the £6M Madley I satellite communication ground station commissioned by the Post Office. The inauguration took place in April and the prime contractor was Marconi Communications Systems Limited.

Initially Madley I is being used with the Indian Ocean Intelsat IVA satellite and provides a large capacity for telephone, telex and television traffic. The station has facilities for

further expansion and it is foreseen that it will be used with the next generation of international telecommunication satellites, Intelsat V, whereupon the system channel capacity will be doubled. In terms of quantity of equipment Madley I, with its 32 metre antenna, is one of the largest satellite earth stations operating in the Intelsat system. In all, 55 chains of receiving equipment, 14 chains of transmitting equipment and 10 high power amplifiers give Madley I the capability to communicate with about 40 countries simultaneously, and Marconi Communication Systems is already manufacturing equipment to extend this capacity.

As prime contractor, Marconi Communications Systems is coordinating the efforts of an international team of sub-contractors including Mitsubishi Electric Corporation, Japan, for the antenna sub-system and Comtech, in the U.S.A. for the low noise amplifiers.

The complete Madley I station is built up in modular fashion from a number of individual sub-systems. The largest of these is the steerable 32 metre parabolic antenna which is mounted on a building housing the steering and control equipment. Also in this building are the high power transmitter amplifiers with their associated control logic, and low noise cryogenically cooled broadband receivers.

In the Post Office central building is installed the Marconi Ground Communication Equipment. This consists of s.h.f. branching, s.h.f./i.f. downconverters, demodulators, modulators and base-band equipment. Also in the building is the cross-site make-up amplifier operating at the s.h.f. receiver frequency, fixed station test facilities and all associated control and monitoring equipment. (S.H.F., incidentally, stand for Super High Frequencies of 3,000 to 30,000MHz.)

Peripheral systems, such as public address, air conditioning, fire detection and weather recording facilities have all been supplied.

It should be mentioned that Marconi has a long record of achievement in the technology and construction of communication earth terminals. For the Post Office the company designed and equipped the Intelsat A stations at Goonhilly 2 and 3, and in September of 1978 handed over Goonhilly 4. Marconi Communication Systems remain the only British Company to have supplied complete communication satellite earth stations.

In your workshop-shop

READERS' HINTS & TIPS

Smithy discusses hints sent in by readers

"Knock Knock!"

Smithy sighed wearily.

"Who's there?"

"Two people: Killer and Mugger."

"Killer who and Mugger who?"

Dick grinned expansively.

"Killer Hertz and Mugger Hertz!"

Smithy grunted irritably. It had been a tiresome day. On the "For Repair" rack were no fewer than four colour television receivers which had been collecting dust over the last week awaiting replacement parts from their manufacturers' service departments. Accompanying them were two black and white television receivers which were similarly awaiting replacement parts from the manufacturers' service departments. Also on the rack was a multi-knobbed silvery music centre for which a replacement part had actually arrived from the manufacturer's service department that very morning, the only snag being that it was for the wrong model.

Smithy drew some comfort from the fact that he and Dick had at least cleared the rest of the stock on the "For Repair" rack. The last item had been an inexpensive cassette recorder with an intermittent fault on "Playback". They had struggled for a fruitless and frustrating two hours of the afternoon in their search for the source of the intermittent, tapping components and flexing the printed board without a single sign of success. It was eventually Dick who noticed that the intermittent fault became evident only when the "Playback" button on the "Record-Playback" switch was pressed in at a certain angle. This finally led to the discovery of a cold joint at one of the switch tags. After the wasted two hours, the intermit-

tent fault was cured in less than ten seconds by a touch of the soldering iron and the expenditure of three millimetres of resin cored solder.

READERS' HINTS

"Come on Smithy, cheer up." called out Dick from his side of the Workshop.

Smithy looked over at his assistant and then glanced at his watch.

"You must admit," he stated, "that it hasn't been one of our better days. Oh well, there's no use moping about it, I suppose. You can press on home early if you like, as there won't be anything else to do today."

But Dick seemed reluctant to depart.

"D'you remember," he asked casually, "when we were doing that cassette recorder, you asked me to have a look in your bench drawer for an insulated rod which you could use to poke at the components?"

A pained expression passed over the Serviceman's face.

"I don't think 'poke' is quite the right word to use. I employ that little rod to gently tap the components."

"You were poking them all right near the end, when you were getting all het up about that intermittent," retorted Dick. "Anyway, while I was looking in your drawer I noticed that you had quite a large sheaf of letters in there, all clipped together with a whacking great paper clip. I was wondering ..."

His voice trailed away expectantly.

"Sheaf of letters?" repeated Smithy frowning. Suddenly his expression changed and his eyes lit up. "Why, of course! Those are the letters with hints sent in by readers, and they've been gradually accumulating over the months. There should be quite a pile there by now."

He opened the drawer and took out the letters.

"Yes," he went on cheerfully. "We've got quite a selection here. Certainly enough for us to have a good readers' hints session. Shall we do just that?"

"Yes please!"

"Right. Well, you come over here and I'll have a go at them."

As Dick carried his stool across the Workshop and set it up alongside Smithy's, the Serviceman looked through the letters. He extracted one from the sheaf.

"Here's a good one for starters," he announced. "And it's from a reader who uses a home-constructed short-wave preselector with plug-in coils. The ones he uses are the Denco miniature types which plug into a B9A valveholder. As you will very probably know, these coils are supplied in aluminium cans which can be used as screens for the coils, and in his preselector he first fits the coil he wants to use and then screws the screen over it." (Fig. 1.)

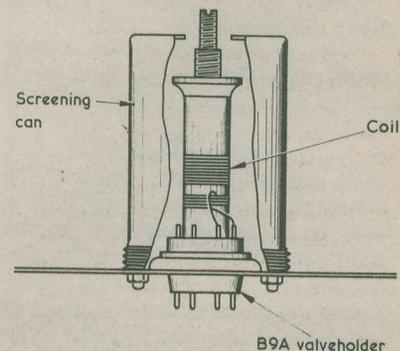


Fig. 1. Denco plug-in coils are supplied in an aluminium container with a screw-on lid. If the lid is secured under the valveholder into which the coil is plugged, the container may then be screwed into it to form a screening can

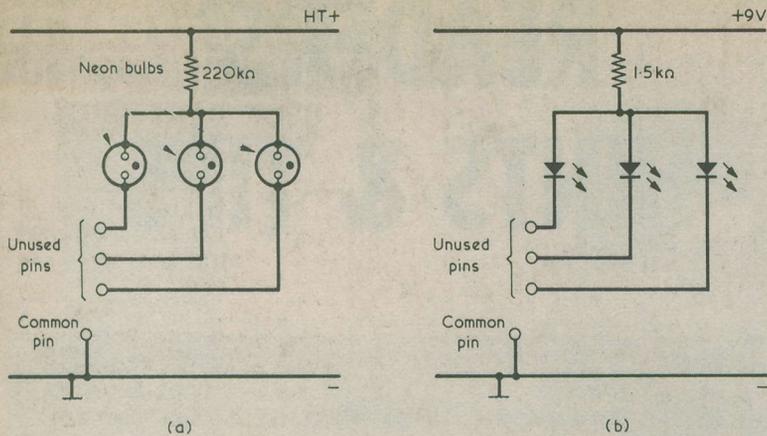


Fig. 2(a). The three neon bulbs are wired to the B9A valveholder so that each lights up when one of three separate coils is plugged in. The series resistor has a value suitable for h.t. voltage of around 150 to 200 volts

Fig. 2(b). With semiconductor equipment having a low supply voltage, light emitting diodes may be employed instead of neon bulbs

"Yes?"

"The snag is that he doesn't always know which coil happens to be plugged in without having to uncrew the can again! And so he uses an electrical method of indicating which coil is in use. There are three coil ranges and he has modified the coils by adding to each a bridge wire which connects between a common pin at chassis potential and a disused pin. The disused pin is different with each coil. The result is that whichever coil is inserted completes a circuit between chassis and a neon indicator coupled to the h.t. positive rail. I should add that his preselector is a valve job with a high voltage h.t. supply." (Fig. 2(a).)

"Does that mean you can't use the idea with a low voltage transistor preselector?"

"Not at all. With a low voltage preselector the bridged pins could just as readily turn on i.e.d.'s." (Fig. 2(b).)

"Why, of course they could," said Dick excitedly. "And, whether the indicators were neons or i.e.d.'s, they could all be mounted on the front panel of the preselector to give a really effective and striking indication of the range which is in use. I've just thought of something else. With i.e.d.'s you could use three different colours for the three ranges; red, green and yellow!"

"Okay, okay," said Smithy, holding up his hand. "Don't get all carried away. There's one point I should make to anyone who considers adding the bridging wire to the Denco coil pins."

"What's that?"

"The pins are mounted in polystyrene, which melts very readily with heat, and so the soldering iron should be applied and withdrawn very quickly. A good plan is to first plug the coil into an odd B9A valveholder, fit the bridging wire to the pins and then solder it quickly. After that, give the coil a good few minutes to allow the polystyrene to reset hard again before removing it from the valveholder." (Fig. 3.)

ETCHANT TRAYS

"That bridging wire idea is a good hint to begin with," said Dick enthusiastically. "What's the next one, Smithy?"

"It's a method for making up trays for etching printed circuit boards," replied Smithy slowly, as he read a new letter. "There are two diagrams attached to the letter, so you'd better have a look at these."

He removed a sheet of paper from the letter and passed it over to his assistant. (Figs. 4(a) and (b).)

"What's the advantage of these trays?"

"The main advantage is that they cost nothing at all," stated Smithy. "As you know, it's often recommended that a photodeveloping tray be used for printed circuit etching, but trays of that nature are not so easy to come by nowadays, and they can also be quite pricey, too. What this letter suggests is that suitable etchant trays can be made up with the plastic available from discarded washing-up liquid bottles,

plastic milk bottles or similar circular containers. First of all the neck and base of the bottle are cut off, after which a cut is made down the resultant cylinder, giving a rectangle of plastic sheet. If necessary, this can be cut down again to give a final rectangle of the desired size. Next, you draw lines on the rectangle as shown in the first diagram, and then fold or crease along the lines. Follow this by folding the sheet to the shape illustrated in the second diagram and, using an office paper stapler, staple together the multiple layers of plastic material at the corners. The staples must be high enough up the walls of the tray which has now been formed to be above the surface of the etchant."

"What size of tray can you make up with this idea?"

Smithy studied the letter.

"The average washing-up liquid bottle will make a tray measuring about six by six inches with three-quarter inch walls," he stated.

"Furthermore, a series of smaller trays could be made, to fit one inside the next. As a result, an appropriately sized tray can be selected for whatever board is to be etched, with a consequent saving on etchant. Finally, trays made up in this way are neat and durable, and will survive the etching of many a printed circuit board."

He turned to a further letter.

"Snap!"

"What did you say?"

"I said snap!" chuckled Smithy.

"Believe it or not, but the very next letter I've picked up describes another home-made plastic bath for etching printed circuits. Let me read from the letter. 'The bath which I now use, and have used very successfully for two years, is made from one of those boxy-shaped plastic bottles in which supermarkets commonly sell half-gallons of lemon squash. The plastic from which these are made is translucent and reasonably tough but is quite

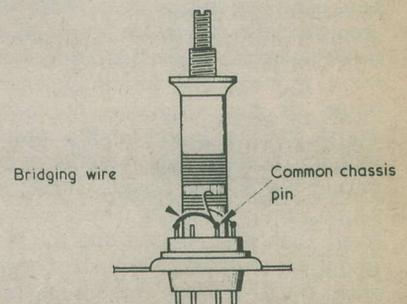


Fig. 3. The bridging wire is soldered to the appropriate coil pins in the manner shown here

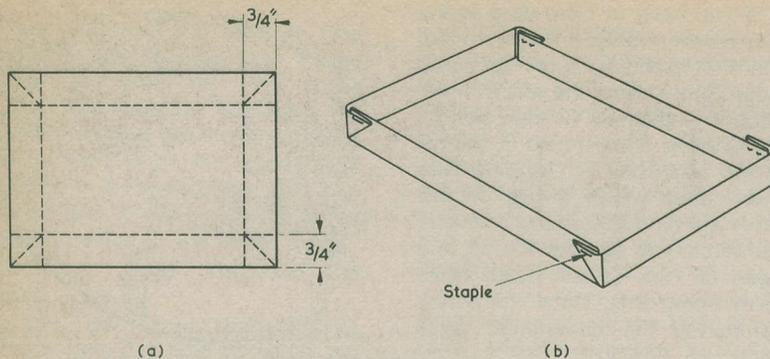


Fig. 4(a). A rectangle of plastic cut from a plastic container is marked up as illustrated
 (b). The plastic is then folded up to form a tray, the corners being secured by staples

easy to cut with a sharp knife."

"I think I know the sort of bottle that's being referred to," said Dick, frowning, "but I'm not entirely certain."

"The reader has drawn a sketch of the bottle after it has been converted to a bath."

Smithy handed Dick a sketch which had been attached to the letter. (Fig. 5.)

"Oh, I know the type of bottle that's meant now," said Dick. "Go on, Smithy."

"Okeydoke," replied Smithy equably. "The bottle is used laying on its side, and a rectangular aperture measuring, say four by five inches is cut centrally in the upper face. This hole is significantly smaller than the maximum which could be cut out, so that there is an overhang all round the inner surface, giving the advantage that accidental spillage of the contents is very unlikely. This home-made bath still has the screw cap on it, which makes it very easy to empty and wash out when it becomes dirty. Another point is that the handle, which is also left on, provides a convenient place to attach a cord which can be looped over a simple crank on the spindle of a slow-speed electric motor. This allows the contents of the bath to be gently agitated whilst etching is in progress."

"Blimey," said Dick appreciably, "that's a cunning approach. There's one thing, though. Won't the overhanging edges make it difficult to remove the printed board after etching?"

"Our correspondent has covered that point too," grinned Smithy. "All that has to be done is to thread a piece of plastic covered wire about a foot long through a suitable hole in the bath. The board may then be removed by this wire."

He paused for a moment.

"I think it's worth giving a word of warning here," he continued. "Ferric chloride etching solution is a pretty active chemical and like all active chemicals it should be handled with care."

"Dissolving ferric chloride crystals can sometimes cause the creation of heat, and so the process of dissolving should not be carried out in a plastic tray or bath, although it is of course in order to store a cool and fully prepared ferric chloride solution in a suitable plastic container."

"That seems sensible enough," commented Dick. "Is that the finish of that letter?"

"No," stated Smithy, "there's a second hint in it. This also has to do with printed circuits and it deals with a good and cheap etch resist. The letter says that the cheapest and best etch resist the writer has yet come across is a preparation sold as engineer's marking out liquid. This is a spirit based lacquer which is usually blue in colour, and it is widely used in metal working to provide a coloured background on

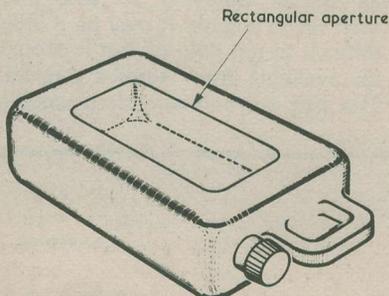


Fig. 5. A home-made bath for printed circuit etching is made from a supermarket lemon squash container

PEATS for PARIS
ELECTRONIC COMPONENTS
RADIO & TELEVISION
For the convenience of Irish enthusiasts we supply:
 Radio & Electronics
 Constructor Data Books
 Panel Signs
 Transfers
Also a postal service
PEATS
 the world of electronics
 25 Parnell Street, Dublin 1. Telephone 749972

MORSE IMPROVEMENT

C90 Cassettes (A) 1-12 w.p.m. with simple exercises. Suitable for R.A.E. preparation. (B) 12-24 w.p.m. computer produced professional level operator material including international symbols.

Price each: complete with instruction and exercise booklets **£4.75** including postage. Morse Key and Buzzer Unit suitable for sending practice and DIY tape preparation.

Price **£4.75** including postage
 Overseas Airmail **£1.50** extra.

MHEL ELECTRONICS (Dept. R)
 12 Longshore Way, Milton,
 Portsmouth (UK), PO4 8LS

GAREX

V.H.F. Receivers SR-9 for 2-metres F.M., fully tunable 144-146MHz, 2-speed slow-motion dial, also 11 xtal controlled channels. Compact, sensitive, ideal for fixed or mobile listening. Built-in L.S., 12v D.C. operation **£47.15 inc. VAT**. Crystals, if required: **£2.60** each. All popular 2m. channels in stock. **Marine band version (156 162MHz) £47.15 (xtals £2.90)**. Mains psu for above **£11.95**. **Pocket VHF Receiver** 12 channel xtal controlled complete with nicad and charger. 4MHz bandwidth in range 140-175MHz **£57.95**. Amateur and Marine xtals in stock, prices as SR-9.

Amplifier module new, fully assembled 6W IC unit, 12v D.C. Low impedance (4-8 Ω) input and output for extn. speaker amplification, with circuit **£2.75**.

Neons min wire end **70p/10; £4.50/100**

Slide switches min DPDT **20p ea; 5+: 16p**

Resistor Kits E12 series, 22 Ω to 1M Ω

57 values, 5% carbon film, 1/8W or 1/4W Starter pack, 5 each, value (285) **£3.10**

Mixed pack, 5 each 1/8W + 1/4W (570) **£5.55**

Standard pack, 10 each (570) **£5.55**

Giant pack, 25 each (1,425) **£13.60**

BNC Cable mtg socket 50 Ω 25p;

5+: **20p;** PL259 UHF Plug & Reducer **75p;**

5+: **67p;** SO239 UHF Socket panel mtd. **60p;** 5+: **50p;** Nicad rechargeables

physically equiv. to zinc-carbon types: AAA (U16) **£1.80;** AA(U7) **£1.30;** C(U11) **£3.35;**

PP3 **£5.55**. Any 5+: less 10%. Any 10+ less 20%.

We stock V.H.F. & U.H.F. mobile aeri-als.
 s.a.e. details.
 Access — Barclaycard

PRICES INCLUDE UK POST, PACKING & VAT
 Mail order only Sole Address:

GAREX ELECTRONICS
 7 NORVIC ROAD, MARSWORTH.
 TRING, HERTS HP23 4LS
 Cheddington (STD 0296) 668684

which scribed lines stand out clearly. It should not be confused with 'marking blue', a non-drying paint sold in toothpaste type tubes which is used for quite different purposes. The correct marking out liquid can be put on the cleaned copper surface of the board with a paint brush or a pen to form the tracks, or it can be applied all over and then scratched away, when dry, at the places where it is not wanted. The lacquer dries in a few moments and etching may then be carried out straightaway. After etching is complete, the lacquer can be removed with a paper towel wetted with methylated spirit."

"That sounds like just the thing for printed circuit buffs," commented Dick. "How d'you get hold of this marking out liquid?"

"That's not quite so easy," said Smithy, as he continued to read the letter. "It seems that the liquid is sold in large bottles only, which are much too big to provide the small quantities required for amateur printed circuit work. On the other hand, the liquid should be available in any good engineer's tool shop, and it may well be possible to obtain an odd ounce or two in an old ink bottle from a small local engineering company. Even this small quantity would be adequate for dozens of printed boards."

"Does the marking out liquid have a trade name?"

"Let me see now," said Smithy, as he continued to look through the letter. "Ah yes, here we are. A very widely used brand of the liquid is sold under the name 'Spectra Color', and this should help you to identify it if you should go around hunting for it."

"'Spectra Color', eh?" repeated Dick. "I must remember that for any future printed circuit jobs I start off on. Any more hints, Smithy?"

AWKWARD SCREWS

Smithy picked up another letter. "Here's a neat little one," he chuckled. "It's a solution to the perennial problem of getting screws started in awkward places."

He pointed to a sketch in the letter. (Fig. 6).

"If you have to offer up a screw in an awkward place," he continued, "you first put two turns of cored solder tightly round the screw in the direction indicated in the sketch. The screw is then placed in the required position by holding the solder, after which a tug on the solder will tend to turn the screw in. If possible, you can put the tip of a finger on the screw head while you're doing this. Once the screw has started the screwdriver takes over."

"Hey, that's crafty!"

"It *is* neat, isn't it?" agreed Smithy. "Now let's see what I've got next."

Smithy picked up several letters and looked through them carefully. After a little thought, he arranged them in a new order.

"Come on, Smithy, I'm getting all impatient!"

"Sorry to hold you up. The reason I'm sorting these letters out is that they come from one reader who has sent in a number of hints. However, these break down largely into three main ideas. Right, I'll get started on the first. This is an idea for replacing drive belts in reel-to-reel tape recorders and cine projectors. Our correspondent states that having paid prices from £2.50 to nearly £6 for replacement belts and, in some cases, not being able to obtain belts at all for some imported jobs, he got so fed up that he decided to see if he could make up his own belts. And here is one of the belts he actually made himself."

Smithy took out a belt from the letter envelope and handed it to Dick. (Fig. 7).

Dick picked it up and stretched it experimentally.

"It seems to have quite a bit of elasticity in it," he remarked. "The two ends are tied together with cotton thread. Here, hang on a minute this isn't a solid material — it's got a hole down the middle."

"That's right," confirmed Smithy. "It's plastic sleeving and it's known as 'Symel' Sleeving. As with that etch resist lacquer it may be a little difficult to get hold of, but it should be available from surplus dealers. The size our correspondent uses is

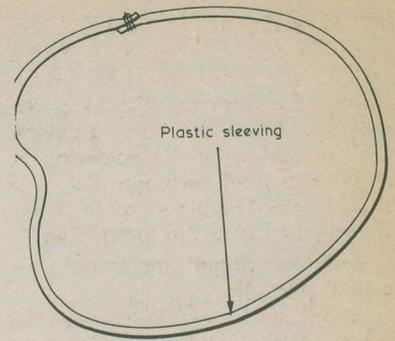



Fig. 7. A driving belt made up from tough plastic sleeving. The belt will be found a suitable replacement in many reel-to-reel tape recorders

1½ mil bore with ½ mil wall thickness. A length of 25 yards can be obtained for quite a moderate sum and this can be cut up and made into a considerable number of belts. The sleeving is cut to the length required for the replacement belt and the two ends are tied together with several turns of thin strong thread. The sleeving will run over the smallest pulley likely to be encountered, and it has even been used successfully in replacements for square section drive belts. A further advantage occurs with tape recorders which have to be partially stripped down to fit a replacement belt. All that is required with the 'Symel' sleeving is to thread it through and get someone to hold it in position while you tie the ends together."

"That's certainly an idea I've never heard of before," commented Dick. "What's the next hint?"

"It's a holding device for soldering small components," said Smithy. "All it consists of basically is a crocodile clip soldered on to the end of a piece of fairly heavy copper wire about 6 to 10 inches long. If desired, the teeth of the clip can be filed down so that they don't mark the item to be held. The free end of the copper wire is secured in a vice or movable clamp, and the wire can be bent into any position. The item

Fig. 6. An idea for starting screws in awkward places. Pulling the solder turns the screw through several revolutions, after which the screwdriver may be brought into use

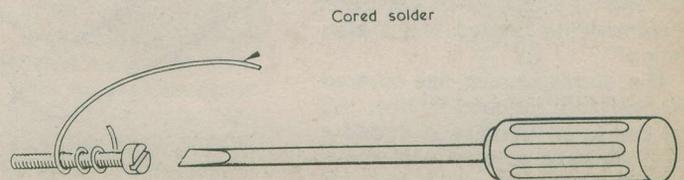

to be soldered is held in the crocodile clip, leaving both hands completely free to hold wires against the item for soldering. An example of how the holding device can be used is for the soldering of wires to a gram cartridge plug in a pick-up arm. There's a sketch of the holding device in the letter. See?"

Smithy's finger indicated the sketch. (Fig. 8).

"Stap me," said Dick eagerly. "That's just the sort of thing we need in this place. I'll make up one of these holding gadgets first thing tomorrow."

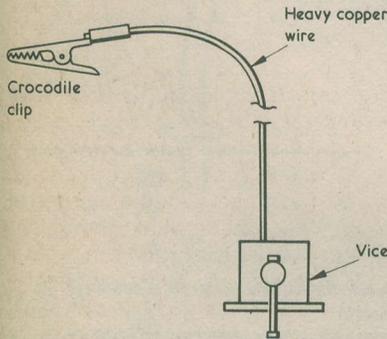


Fig. 8. A "third hand" for holding components during soldering. The copper wire can be bent to place the crocodile clip in any desired position

"It will certainly be jolly useful," agreed Smithy. "Now here's the third hint and it is concerned with mains units for transistor radios. Instead of making up a mains supply you simply obtain one of the pocket calculator mains adaptors which are on offer very cheaply these days. The letter writer states that he bought one rated at 7.5 volts d.c. at 50mA for less than a

pound. These adaptors are intended for charging the batteries of pocket calculators, and they include a mains transformer and a rectifier. Now, there is of course no guarantee that a calculator adaptor will be suitable for a particular radio and so there's some risk that you may not be able to use the adaptor for this purpose after you've bought it. So far as hum is concerned, the electrolytics across the radio supply rails should provide sufficient smoothing in most cases. The calculator adaptors usually have the d.c. output carried by a 2-core wire terminated in a jack plug. The radio can then be fitted with a suitable jack socket which isolates the internal battery when the plug is inserted. It is essential that you check the output polarity of the calculator adaptor by means of a meter before wiring up the jack socket." (Fig. 9).

"That sounds to me," said Dick slowly, "as though the idea should only be used by people who understand the technicalities involved."

"That's right," agreed Smithy. "But against this has to be balanced the fact that these calculator mains adaptors can be picked up at giveaway prices. Now let's have a look at the next hint. Which, incidentally, brings us to the end of our present batch."

LEAD ANCHORING

Smithy took up the final letter in the sheaf on his bench and read it carefully.

"Ah", he remarked, "what we have here is an idea for anchoring leads which connect to Veroboard assemblies. Now, external connections to Veroboards are usually made with flexible insulated wires and these can pass through the appropriate holes in the boards and be soldered to the copper underneath. Alternatively, Veropins can be

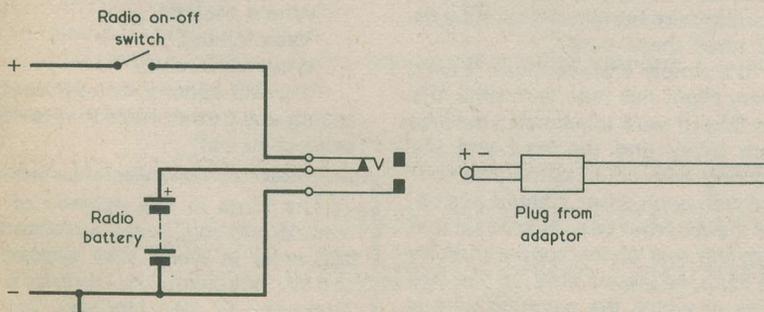


Fig. 9. Using a low-cost pocket calculator mains adaptor to power a small radio. It is necessary to find the polarity and voltage available at the adaptor output plug before using it with the receiver. Not all calculator adaptors may be suitable for this application

ELECTRONIC CONSTRUCTORS

SAVE MONEY!

★ With our BARGAIN PARCEL . . . ★

Contains:
10 x BC107, 10 x BC108, 10 x BC109, 3 x 8FY51, 3 x BC172, 3 x BC170 and 10 Mixed Values - ELECTROLYTICS: 10 Mixed Values - CERAMIC CAPS: 20 Mixed Values - FIXED CAPS: 10 DIODES GERMANIUM - Sim. OA91; 10 DIODES SILICON - Sim. IN914; 2 x 741 IC's. 1 2gms PHIAL CYNOACRYLAITE ADHESIVE. VAT inc. in price (all items are brand new).

Plus a Surprise Gift worth 50p

Send £5 plus 50p p&p

(Cheque, Postal Order, Money Order) to

★ SIGTRONIC ELECTRONICS ★

27 Malvern Street, Stapenhill

Burton-on-Trent, Staffs. DE15 9DY

Tel: (0283) 46868 special orders

THE

MODERN BOOK CO.


Largest selection of English & American radio and technical books in the country

19-21 PRAED STREET

LONDON W2 1NP

Tel: 01-402 9176

MORSE MADE EASY

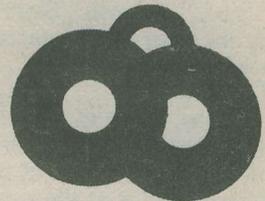

BY THE G3HSC RHYTHM METHOD!

These courses which have been sold for over 23 years, have been proved many times to be the fastest method of learning Morse. You start right away by learning the sounds of the various letters, numbers, etc., as you will in fact use them. Not a series of dots and dashes which later you will have to transkate into letters and words.

Using scientifically prepared 3 speed records you automatically learn to recognise the code, RHYTHM without translating. You can't help it. It's as easy as learning a tune 18 WPM in 4 weeks guaranteed.

The Complete Course consists of three records as well as instruction books. For Complete Course send £5.50 (overseas surface mail £1 extra).

THE G3HSC MORSE CENTRE
Box 8, 45 Green Lane, Purley, Surrey.

I enclose £5.50 or s.a.e. for explanatory booklet.

Name

Address

soldered to the board and the external leads soldered to these. Both of these methods are perfectly acceptable, but Veropins are to be preferred if the leads connecting to the board will be subjected to any physical movement, as would occur if they were leads going to a battery connector. Even with a Veropin there is still a weak point, this appearing where the wire leaves the rigid solder joint at the pin itself."

"That's true," agreed Dick. "I've bumped into several cases where wires have fractured at their Veropin solder joints."

"The answer to the problem," said Smithy, reading through the letter, "is to physically anchor the wires at the edge of the Veroboard. What is required for each lead are two adjacent holes in a single copper strip near the edge of the Veroboard, assuming that the Veroboard circuit layout allows this. Cuts are made in the strip on either side of the two adjacent holes. Next, a piece of single core insulated connecting wire has its ends bared for about half an inch at one end and about an inch and a half at the other end. Like this."

Smithy passed over a sheet attached to the letter. (Fig. 10 (a).)

"I'm with you so far. Go on, Smithy!"

"Then," said Smithy, "you pass the half inch bared end through one of the Veroboard holes and solder it to the copper."

"Right!"


"Next," resumed Smithy, "you pass the lead to be secured under the wire." (Fig. 10(b).)

"Check!"


"Finally," stated Smithy, "you pull the one and a half inch wire end fairly tight with a pair of pliers and quickly solder it at the second hole in the copper." (Fig. 10(c).)

"Right!"

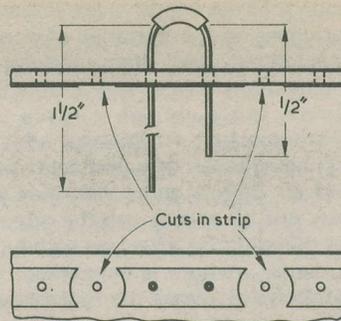
"And that's it," said Smithy. "Cut off the excess wire on the copper"




(a)

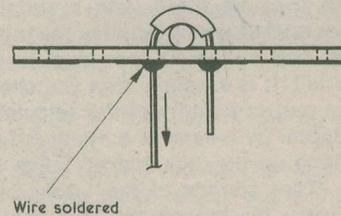

(c)

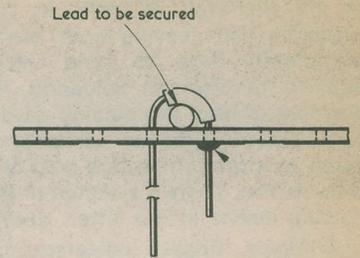

(b)

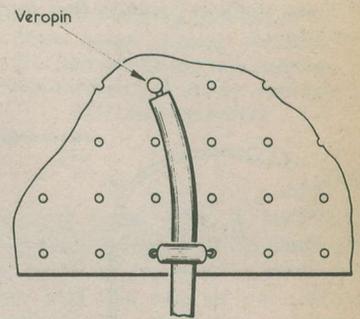

(d)

Fig. 10 (a). First step in anchoring a lead at the edge of a piece of Veroboard

(b). The short end of the wire is soldered at the Veroboard hole through which it passes

(c). The long end is pulled tight with a pair of pliers, and it is also soldered to the Veroboard copper strip

(d). Top view illustrating how the lead is secured in position near the edge of the Veroboard. There is now no risk of the lead breaking at the point where it leaves the solder joint at the Veropin

side of the Veroboard and the lead is then held securely at the edge of the board. Easy, isn't it?" (Fig. 10(d).)

"I'll say," agreed Dick warmly. "Just a minute, though."

"What's wrong?"

"At the start you said that the copper strip is cut at the two holes on either side of the two which the securing wire is soldered to. Why do you need these cuts?"

"It's simply a precaution. There's a very slight risk that, with time, the two lots of wire insulation could be worn away and the lead and the securing wire could come into contact with each other. Should this occur the external wire is still isolated from the rest of the copper strip by the cuts on either side of the two holes at which the securing wire is soldered. The precaution is, admittedly, in the ultra-cautious category if no other connections are made to the strip concerned, but it is worth carrying out, nevertheless."

Smithy picked up the letters,

tidied them up and clipped them together again.

"Well," said Dick, "this has been a really good hint session."

"It certainly has," agreed Smithy. "It's always of interest and value to know what other people are thinking about, and the ideas they use to make life easier. Knock knock!"

Dick looked startled.

"Who's there?"

"Wee Willie!"

"Wee willie who?"

"We will eagerly look forward to seeing any further hints that readers send in to us!"

The hints in this episode of "In Your Workshop" were submitted, in the order in which they appear, by D. W. Mephram, H. Kennedy, F. Dickens, C. M. Lindars, W. H. Spindler and T. F. Jones.

As Smithy states, further hints for this feature are welcomed. Payment is made for those that are published.

SAVE MONEY!

*** NOW ON ***
CASSETTE TAPES

ACADEMY C60 - Super-Low Noise/Hi-output, Cassette Tapes (Ferric Oxide) 2 x 30 mins, Recording/Playing time - 5 for **£3.00** P&P included

A.T.Z. C60 - 'Chromium Dioxide' very Low Noise/Hi-output, Cassette Tapes of high quality 2 x 30 mins, Recording/Playing time: 5 for **£5.00** P&P included


Buy now at lower than pre-Budget prices

SIGTRONIC ELECTRONICS

27 Malvern Street, Stapenhill
Burton-on-Trent, Staffs. DE15 9DY

**BREAD
BOARD**

1979

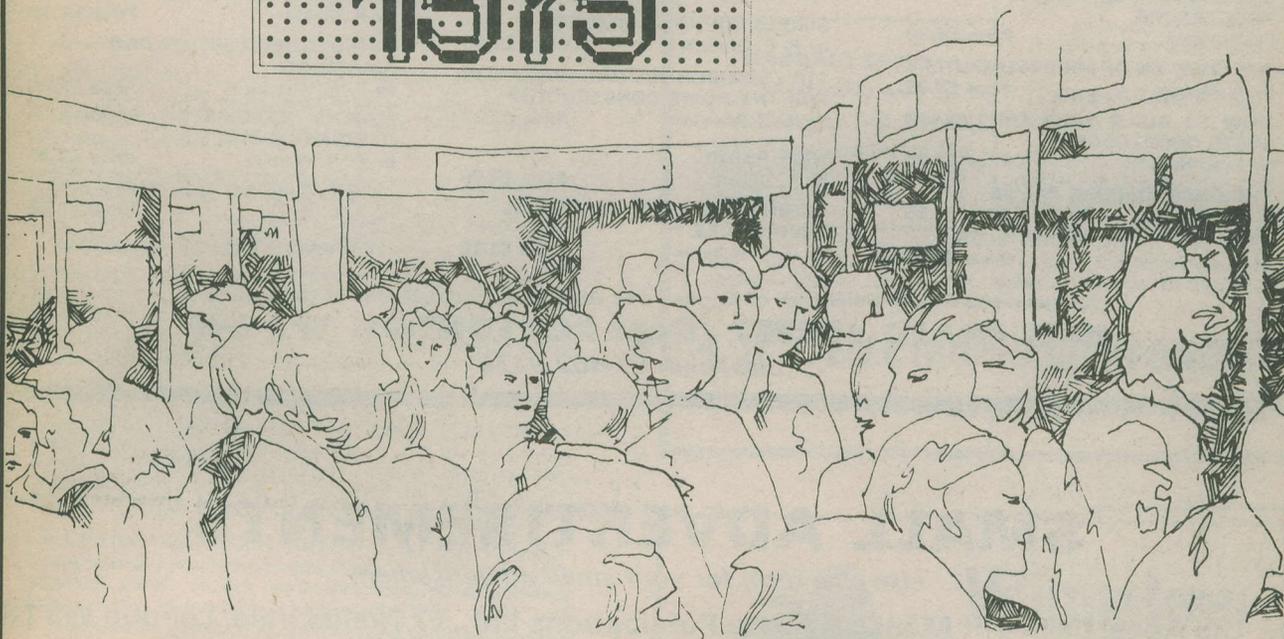

There's a lot going on at Breadboard!

Seventy exhibitors showing and selling everything that the hobby electronics enthusiast could want! Demonstrations of electronic organs – computer kits – audio gear.

Radio Station S22 broadcasting throughout the show. See your voiceprint! Get your own weather details direct from Tiros M! Test your reactions – and your strength.

Careers in Electronics – get the advice and information that could start you off on a rewarding and interesting career.

It's worth going to Breadboard!

**Royal Horticultural Halls Elverton Street
Westminster London SW1**

December 4-8th 1979

Admission £1 (students 70p)

THE MODERN BOOK CO

PROJECTS IN RADIO AND ELECTRONICS by I. R. Sinclair, Price £2.50

ELECTRONIC PROJECTS IN THE HOME
by O. Bishop Price £2.50

ELECTRONIC PROJECTS IN AUDIO
by R. A. Penfold Price £2.50

OP-AMPS THEIR PRINCIPLES & APPL.
by J. B. Dance Price £2.50

PRINTED CIRCUIT ASSEMBLY
by M. J. Hughes Price £2.10

ELECTRONIC SECURITY DEVICES
by R. A. Penfold Price £1.65

UNDERSTANDING DIGITAL ELECTRONICS
by Texas Inst. Price £4.00

UNDERSTANDING MICRO-PROCESSORS
by Motorola Price £4.30

THE FIRST BK OF MICROCOMPUTERS
by R. Moody Price £3.35

HOW TO BUILD YOUR OWN SOLID STATE OSCILLOSCOPE
by F. G. Rayer Price £1.70

THE OSCILLOSCOPE IN USE
by I. R. Sinclair Price £2.85

AMATEUR RADIO TECHNIQUES
by P. Hawker Price £3.80

THEORY & PRACTICE OF MODEL RADIO CONTROL
by P. Newell Price £4.50

REPAIRING POCKET TRANSISTOR RADIOS
by I. R. Sinclair Price £2.55

MAKING & REPAIRING TRANSISTOR RADIOS
by W. Oliver Price £2.30

WORLD RADIO TV HANDBOOK
by J. M. Frost Price £9.25

PROJECTS IN RADIO & ELECTRONICS
by I. R. Sinclair Price £2.50

ELECTRONIC PROJECTS IN THE HOME
by O. Bishop Price £2.50

SIMPLE CIRCUIT BUILDING
by P. C. Graham Price £2.20

110 SEMICONDUCTOR PROJECTS FOR THE HOME CONSTRUCTOR
by R. M. Marston Price £3.20

HAM RADIO
by K. Ulyett Price £5.00

BEGINNER'S GUIDE TO DIGITAL TECHNIQUES
by G. T. Rubaroe Price £1.10

UNDERSTANDING SOLID-STATE ELECTRONICS
by Texas Inst. Price £1.80

A SIMPLE GUIDE TO HOME COMPUTERS
by S. Ditlea Price £4.00

HOW TO BUILD A COMPUTER-CONTROLLED ROBOT
by T. Loofbourrow Price £5.30

THE CATHODE-RAY OSCILLOSCOPE & ITS USE
by G. N. Patchett Price £4.00

HOW TO GET THE BEST OUT OF YOUR TAPE RECORDER
by P. J. Guy Price £1.90

A GUIDE TO AMATEUR RADIO
by P. Hawker Price £1.70

RADIO CONSTRUCTION FOR AMATEURS
by R. H. Warring Price £2.80

MAKING TRANSISTOR RADIOS A BEGINNER'S GUIDE
by R. H. Warring Price £2.90

1979 THE RADIO AMATEUR'S H/B
by A. R. R. L. Price £7.86

★ PRICES INCLUDE POSTAGE ★

We have the Finest Selection of English and American Radio Books in the Country
19-21 PRAED STREET (Dept RC) LONDON W2 INP
 Telephone: 01-402 9176

SMALL ADVERTISEMENTS

Use this form for your small advertisement

To: The Advertisement Manager, Data Publications Ltd., 57 Maida Vale, London W9 1SN
 Please insert the following advertisement in theissue of RADIO & ELECTRONICS CONSTRUCTOR

➔			

15 words at 12p
=£1.80

ALL WORDING
IN
BLOCK LETTERS
PLEASE

I enclose remittancebeing payment at 12p a word. MINIMUM £2.00.
 Box Number, if required, 30p extra.

NAME.....
 ADDRESS.....

Copy to be received four weeks prior to publication.
 Published on the 3rd of every month, forward dated.

SMALL ADVERTISEMENTS

Rate: 12p per word. Minimum charge £2.00

Box No. 30p extra

Advertisements must be prepaid and all copy must be received by the 4th of the month for insertion in the following month's issue. The Publishers cannot be held liable in any way for printing errors or omissions, nor can they accept responsibility for the *bona fides* of Advertisers. Where advertisements offer any equipment of a transmitting nature, readers are reminded that a licence is normally required. (Replies to Box Numbers should be addressed to: Box No. —, *Radio and Electronics Constructor*, 57 Maida Vale, London, W9 1SN.

SOLAR CELLS: Bits, books and bargains. Send 95p for Solar Cell booklet and Data Sheets or stamp for list. — Edencombe Ltd., 34 Nathans Road, North Wembley, Middlesex HA0 3RX.

CONSTRUCTORS 200 mixed components £4. 30W soldering irons £2.60. Full refund guarantees. Lists 15p refundable. Mail only. Components bought. Sole Electronics, 37 Stanley Street, Ormskirk, Lancs.

COMPLETE REPAIR INSTRUCTIONS for any requested TV, £5 (with diagrams £5.50). Any requested service sheet £1 plus s.a.e. S.a.e. brings free newsletter, details unique publications, vouchers and service sheets from 50p. AUSREC, 76 Church Street, Larkhall, Lanarkshire.

CONSTRUCT METAL DETECTORS: 1. £120 pulse discriminator (£12 construction cost). 2. £60 model (£6 con/cost). 3. £30 BFO (£3 con/cost). For all three together, written guaranteed d.i.y. plans, send £2. (Dept. RC), J. Lucas, 2 College Road, Grays, Essex. (Established 1973).

CLEARING ELECTRONICS LABORATORY. Numerous quality components available (95% new), inc: punched panels, boxes, wafer-switches, potentiometers, metal-oxide resistances, semiconductors, tools, etc. Unrepeatable — so hurry! Send £5 for a valuable selection worth at least £20. Money refund guarantee. M. J. Evans, 7 Shap Drive, Warndon, Worcester, WR4 9NY.

FOR SALE: Inverter, 12V d.c. to 240V a.c. Suitable running electric shaver, camping, boating, etc. £5.50. Box No. G355.

JOIN THE INTERNATIONAL S.W. LEAGUE. Free services to members including Q.S.L. Bureau, Amateur and Broadcast Translation, Technical and Identification Dept. — both Broadcast and Fixed Stations, DX Certificates, contests and activities for the SWL and transmitting members. Monthly magazine, *Monitor*, containing articles of general interest to Broadcast and Amateur SWLs, Transmitter Section and League affairs, etc. League supplies such as badges, headed notepaper and envelopes, QSL cards, etc., are available at reasonable cost. Send for League particulars. Membership including monthly magazines, etc., £6.00 per annum. (U.K. and British Commonwealth), overseas 612.00. Secretary ISWL, 1 Grove Road, Lydney, Glos., GL15 5JE.

P.C.B. DESIGN. Outline drawings, layouts, projects, for the constructor. Cost according to circuit complexity. D. G. Harrington, 25 Poynter Road, Bush Hill Park, Enfield, Middlesex.

FOR SALE: *Fundamentals of Radio Servicing* by B. W. Hicks, published by Hutchinsons Educational, £2.20 post paid. *Handbook of Satellites and Space Vehicles* by R. P. Haviland, £3.50 post paid. — Box No. G366.

INTERESTED IN OSCAR? Then join AMSAT-UK. Newsletters, OSCAR NEWS Journal, prediction charts, etc. Details of membership from: Ron Broadbent, G3AAJ, 94 Herongate Road, Wanstead Park, London, E12 5EQ.

(Continued on page 253)

COMPONENT PACKS

PU1: 50 untested, unmarked t.t.l. i.c.'s (mostly 7400 series) **65p**
 PU2: Untested, unmarked silicon diodes, some germanium. Pack of 200 (approx.). **65p**
 PU4: Resistors, mixed values, various wattages. Good selection of values. Approx 100. **65p**
 PT1: Tested, marked selection of popular diodes. Contains: 25 x 1N914, 10 x 1N4002, 5 x BY127 **125p**
 PT4: Stranded connecting wire. Five colours each 5 metres. **65p**
 PT5: As pack PT4 but solid conductor. **65p**

... AND MORE

PT12: Pack of five reed switches **50p**
 PT13: Four 10kΩ mono slider pots **85p**
 PT14: Ten pots, assorted values and types. Good selection but no guarantee of any particular value. Hence only **85p**
 PT15: 100 square inches of copper clad s.r.b.p. board **65p**
 PT16: Hardware. Assorted nuts, bolts, washers etc. Approx 100 pieces, count by weight **65p**

SPECIAL XMAS OFFER

Buy £5 worth of the above packs, and receive one pack of your choice. FREE. Offers ends 31-12-79

BARGAIN SPOT

Whilst stocks last

Money refunded if unavailable
 2,200µF 25V electrolytic **38p**
 AD142 Transistor **30p**
 S.P.S.T. Toggle switch **29p**


CABLE AND WIRE

	Price per metre
Single Microphone Cable	10p
Mains, 3A 3 core	15p
Twin Lighting Flex	6p

Mail order only. All prices include VAT. Please add 20p for postage (except component packs). Full list available on receipt of large s.a.e.

T. & J. ELECTRONIC COMPONENTS

98 Burrow Road, Chigwell, Essex IG7 4HB

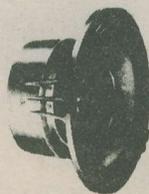

Wilmslow Audio

THE firm for speakers!

SEND 30p FOR THE WORLDS BEST CATALOGUE OF SPEAKERS, DRIVE UNITS KITS, CROSSOVERS ETC. AND DISCOUNT PRICE LIST

AUDAX • AUDIOMASTER • BAKER • BOWERS & WILKINS • CASTLE • CELESTION • CHARTWELL • COLES • DALESFORD • DECCA • EMI • EAGLE • ELAC • FANE • GAUSS • GOODMAN'S • I.M.F. • ISOPON • JR • JORDAN WATTS • KEF • LEAK • LOWTHER • MCKENZIE • MONITOR AUDIO • PEERLESS • RADFORD • RAM • RICHARD ALLAN • SEAS • STAG • TANNON • VIDEOTONE • WHARFEDALE • YAMAHA • SHACKMAN • TANGENT

WILMSLOW AUDIO DEPT REC

SWAN WORKS, BANK SQUARE, WILMSLOW CHESHIRE SK9 1HF

Discount HiFi Etc. at 5 Swan Street

Tel: 0625-529599 for Speakers, 0625-526213 for HiFi

CELEBRATE XMAS WITH US



FREE

WITH THE FIRST ORDER OPENED THIS MONTH — Worth:—
£15 — An MF200 Pocket Camera with Flash; Value £9.95
(Ideal for Christmas)

BARGAIN BASEMENT!

SAVE! SAVE! EEEEE's
NOT NEW! but in tip-top condition
— ONE ONLY —
AN OLYMPIA, MODEL CD60
Electronic Calculator with 7 digit green
display 4 functions and wrist strap
for carrying
OUR PRICE ONLY £6.25 - P&P 40p
Don't confuse this with cheap calculators
(This one was made in Germany!)

SUPER VALUE! — SUPER VALUE!
Again not new — but in excellent condition
— TWO ONLY — **TEXET, MODEL 890**
Electronic Calculators British made
with 8 digit red l.e.d. display and with 4 functions
and memory & many other features.
OUR PRICE ONLY £3.55 each - P&P 40p
(Ideal for Christmas presents!)

The above calculators represent really good value
for money and also have been checked and tested
by our engineer
Write stating preference and we will confirm availability
by return.

PACK X101

Contains 35 — mixed capacitors —
All good usable values, i.e.,
1,500pf / 0.01uf / 0.15uf / 0.4 uf
etc. **48p per pack or 2 packs
for only 82p**

PACK X102

Contains 50 — Germanium Diodes —
Similar to OA90/91. Only **42p per
pack or 2 packs for only 77p**

PACK X103

Contains 30 — mixed transistors —
Some new and branded — NPN &
PNP — Silicon and Germanium
(Most usable)
Great value at only **65p per pack
or 2 packs for only £1.10**

PACK X104

Contains 50 — Silicon Diodes —
Similar to 1N4148, a real bargain at
48p per pack or 2 packs for 80p

PACK X105

Contains 50 — Mixed Wattage
Resistors. Really super value at only
45p per pack or 2 packs for only 80p

PACK X106

Contains 20 — Electrolytic Capacitors —
Ideal for transistor circuits. Values like
10mfd / 50mfd / 220mfd / 100mfd
at **£1 per pack or 2 packs for £1.70**

PACK NOS: X107-X108-X109-X110-X111-X112 (still available) See November Issue, R&E Constructor for price


SIGTRONIC ELECTRONICS, 27 Malvern Street, Stapenhill, Burton-on-Trent, Staffs. DE15 9DY. Telephone: (0283) 46868 after 6 p.m. for all
Special Orders and Quotations. All prices include VAT. Add 37p to order for P&P — Cheques/Giro Cheques/P.O.'s accepted.

Random Electronic


EASY DICE

Build your own 'EASY DICE' from the 5 intergrated
circuits and full components supplied, including box
and descriptive instructions.

Complete
or
Kit

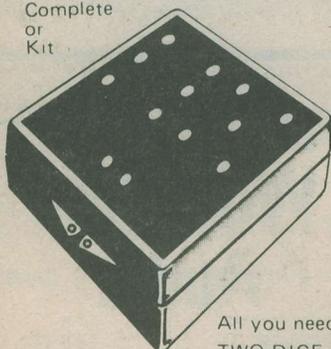

P.C.B.
Layout

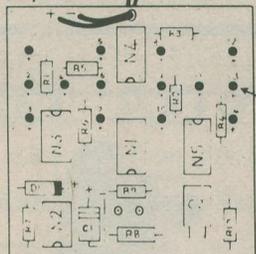

All you need is a soldering iron
TWO DICE FACES TOUCH CONTROL...

- a *Self Assemble Dice **£3.95**
- b *Ready built Dice **£4.75 (INCL. P+P)**

Order now from **Fringewood Electronics Ltd**
1 Hatton Court Ipswich Suffolk (0473 210151)

Amount enclosed £

Name

Address

please state amount required in appropriate box a b

RADIO MODELLER

ELECTRONIC BOOKS

● MODEL RADIO CONTROL

Detailing both Theory and Practice, this book,
by leading authority Paul Newell, has become
the standard reference work. A brief historical
survey leads up to a detailed description of
proportional systems, with over 100 il-
lustrations, including theoretical circuits and
p.c. layouts for an advanced digital system.
134 pages

Price **£3.35**

U.K. Packing
& Postage **32p**

ON SALE NOW
at all leading shops
or direct from:—

**RADIO MODELLER
BOOKS DIVISION,
High Street,
Sunningdale,
Berkshire SL5 0NF.**

theory and
practice of

MODEL RADIO CONTROL

development of a stem
proportional system and
digital system design
practical examples and
full circuit details

Mail Order Protection Scheme

The publishers of this magazine have given to the Director
General of Fair Trading an undertaking to refund money
sent by readers in response to mail order advertisements
placed in this magazine by mail order traders who have
become the subject of liquidation or bankruptcy proceedings
and who have failed to supply goods or refund money. These
refunds are made voluntarily and are subject to proof that
payment was made to the advertiser for goods ordered
through an advertisement in this magazine. The arrange-
ment does not apply to any failure to supply goods adver-
tised in a catalogue or direct mail solicitation.

If a mail order trader fails, readers are advised to lodge a
claim with the Advertisement Manager of this magazine
within 3 months of the appearance of the advertisement.
For the purpose of this scheme mail order advertising is
defined as:

"Direct response advertisements, display or postal
bargains where cash has to be sent in advance of goods
being delivered."

Classified and catalogue mail order advertising are ex-
cluded.

SMALL ADVERTISEMENTS

(Continued from page 251)

RADIO, ELECTRONICS, TELEVISION BOOKS.

Largest variety. Lowest prices. Write for list. Business Promotion Bureau, 376 Lajpat Rai Market, Delhi 110006, India.

FOR SALE: U.S. Signal Corps signal generator. 100kHz to 32MHz. Mains operated. £15. Telephone: Tunbridge Wells 28607.

FOR SALE: Bush cassette tape recorder, battery driven. Microphone, etc. Excellent condition. £10 plus postage. Box No. G375.

THE RADIO AMATEUR INVALID & BEDFAST CLUB is a well established Society providing facilities for the physically handicapped to enjoy the hobby of Amateur Radio. Please become a supporter of this worthy cause. Details from the Hon. Secretary, Mr. H. R. Boutle, 14 Queens Drive, Bedford.

FOR SALE: "Challenge of the Stars" by Patrick Moore and David A. Hardy £2.00. "Destroyers" by Antony Preston £4.00. Box No. G376.

WANTED: FAX equipment, manuals, service sheets, etc. G2UK, 21 Romany Road, Oulton Broad, Lowestoft, Suffolk. NR32 3PJ.

COLLECTORS' ITEMS. Nearly 50 copies of Radio Society of Great Britain's *Bulletins* covering period 1945 to 1949. In reasonable condition. Offers to: Box No. G377.

FOR SALE: C15 10MHz SCOPE. Complete with probes and accessories, plus spare parts. Excellent condition, hardly ever used. £50.00. Telephone: 051-334 4574.

AERIAL BOOSTERS — B11 VHF/FM Radio — B11A VHF 2 Metre Radio — B45 UHF Television. Price £5. S.A.E. for leaflets, Electronic Mailorder Ltd., Ramsbottom, Bury, Lancs. BL0 9AG.

FOR SALE Gent's wrist watch, £20. Nurse watch, £12. Box No. G382.

WANTED: Telford Communications TC10 "Multimode" 2 metre transmitter. Details and price please to Box No. G383.

VHF/FM TRANSMITTER KIT. New silicon chip design means low price (beats anyone else) and better performance. Very small. Fully tuneable 88-108MHz. Instructions etc., all included. **INTRODUCTORY OFFER** £1.95 plus 30p P&P. (Unlicensable). M. Henry, 30 Westholme Gardens, Ruislip, Middlesex.

POSTAL ADVERTISING? This is the Holborn Service. Mailing lists, addressing, enclosing, wrapping, facsimile letters, automatic typing, copy service, campaign planning, design and artwork, printing and stationery. Please ask for price list. — The Holborn Direct Mail Company, Capacity House, 2-6 Rothsay Street, Tower Bridge Road, London, S.E.1. Telephone: 01-407 6444.


FOR SALE: Metal Detector £10. S.a.e. for lists. Box No. G384.

FOR SALE: Copies of *Radio Constructor*, W.W., P.W., P.E., 1956 on, from 5p plus post. S.A.E. enquiries. 1 Hazel Grove, Yelverton, Devon, PL20 6DX.

FOR SALE: Non-working video tape recorders, complete £50, incomplete £30 plus £6 carriage. Closed circuit cameras £45. Commodore Pet computer £500. Stereo cassette mechanisms £10 and £15. 25 2W zeners 50p. Box No. G385.

WANTED: WB. HF1016 speaker. State price. Burton, 24 Holly Road, Birmingham, B16 9NH. (Telephone: 021-454-2046).

(Continued on page 255)

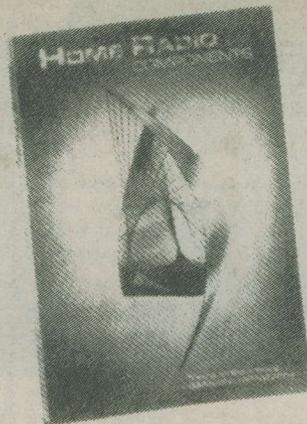

FIRST and STILL BEST

We've been producing our Electronics Components Catalogue for **over 20 years**. During that time we've learned a lot, not only in the art of catalogue production but in building a business that serves the needs of constructors. Little wonder that we have a reputation **second to none** for our catalogue — **and** for the service that backs it up. Experience both for yourself. Just send £1.30 with the coupon and a catalogue will come by return of post.

- About 2,500 items clearly listed and indexed.
- Profusely illustrated throughout.
- 128 A-4 size pages, bound in full-colour cover.
- Bargain list of unrepeatable offers included free.
- Catalogue contains details of simple Credit Scheme.

HOME RADIO (Components) LTD.

Dept. RC., 234-240 London Road, Mitcham, Surrey CR4 3HD
Phone: 01-648 8422

POST THIS COUPON
with cheque or P.O. for £1.30

Please write your Name and Address in block capitals

NAME

ADDRESS

HOME RADIO (Components) LTD., Dept. RC
234-240 London Road, Mitcham, Surrey CR4 3HD

Regd. No. 912966, London





From
Kam
Circuits
a new p.c.b.
battery
operated
Mini-
Drill

Available with or without a portable stand this new powerful precision drill will enable you to drill holes in p.c.b.'s, metal, wooden panels or anywhere that small holes are needed. Bit sizes 0.6mm, 1.0mm and 1.5mm. Power supply 4 × UM3 batteries. Price without stand £19.02 (inclusive of p.p. and VAT). Stand price £8.63 (inclusive of p.p. & VAT).

Write for technical brochure now:



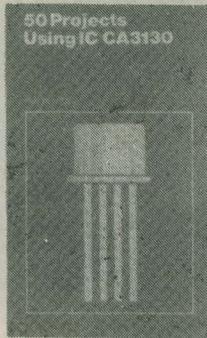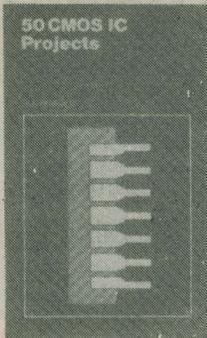Kam Circuits Limited
Porte Marsh Road, Calne, Wilts. SN11 9BW
Telephone: (0249) 815262 Telex: 444218



DIRECT READER SERVICE

RADIO & ELECTRONICS BOOKS

17. Solid State Power Supply Handbook	85p	35. Fun and Games with your Electronic Calculator	75p
18. 50 Projects Using IC CA3130	£1.25	36. 50 (FET) Field Effect Transistor Projects	£1.25
19. 50 CMOS IC Projects	£1.25	37. 50 Simple L.E.D. Circuits	75p
20. A Practical Introduction to Digital IC's	95p	38. How to Make Walkie-Talkies	£1.25
21. How to Build Advanced Short Wave Receivers	£1.20	39. IC 555 Projects	£1.75
22. Beginners Guide to Building Electronic Projects	£1.25	40. Projects in Opto-Electronics	£1.25
23. Essential Theory for the Electronics Hobbyist	£1.25	41. Radio Circuits Using IC's	£1.35
24. Constructors Manual of Electronic Circuits for the Home	50p	42. Mobile Discotheque Handbook	£1.35
25. 79 Electronic Novelty Circuits	£1.00	43. Electronic Projects for Beginners	£1.35
26. 52 Projects Using IC741	95p	44. Popular Electronic Projects	£1.45
27. How to Build Your Own Electronic and Quartz Controlled Watches & Clocks	85p	45. IC LM3900 Projects	£1.35
28. Two Transistor Electronic Projects	85p	46. Electronic Music and Creative Tape Recording	£1.25
29. How to Build Your Own Metal and Treasure Locators	£1.00	47. Practical Electronic Calculations and Formulae	£2.25
30. Electronic Calculator Users Handbook	95p	48. Radio Stations Guide	£1.45
31. Practical Repair and Renovation of Colour TVs (Reprinting)	£1.25	49. Electronic Security Devices	£1.45
32. Handbook of IC Audio Preamplifier and Power Amplifier Construction	£1.25	50. How to Build Your Own Solid State Oscilloscope	£1.50
33. 50 Circuits Using Germanium, Silicon and Zener Diodes	75p	51. 50 Circuits Using 7400 Series IC's	£1.45
34. 50 Projects Using Relays, SCR's and TRIACS	£1.25	52. Second Book of CMOS IC Projects	£1.50
		53. Practical Construction of Pre-Amps, Tone Controls, Fitters & Attenuators	£1.45
		54. Beginners Guide to Digital Techniques	95p

POSTAGE: 20p PER BOOK. IF MORE THAN 3 BOOKS ORDERED: 10p PER BOOK

To: Data Publications Ltd., 57 Maida Vale, London W9 1SN

Please send me within 21 days copy/copies

Book Nos:

.....

I enclose Postal Order/Cheque for £

Name

Address

.....

(Block Letters Please)

(We regret this offer is only available to readers in the U.K.)

SMALL ADVERTISEMENTS

(Continued from page 253)

SIGNAL INJECTORS (AF/RF) £2.50 with full instructions. Pin points faults in radios/amps. quickly. Or send s.a.e. for list of low priced test equipment. Bobker, 29 Chadderton Drive, Unsworth, Burv, Lancs.

DIGITAL MULTIMETER Doram. Cost £68. Also similar multimeter. (Watford) £55. Offers, 4 Riversley Road, Gloucester, GL2 0QT.

WANTED: Large and small quantities of transistors, I.C. s displays, etc., etc. Call any Saturday to: 306 St. Paul's Road, London N.1. Telephone: 01-359 4224.

X-BAND SPECTRUM ANALYSER for sale or exchange for good multimeter. Telephone Swindon 751112.

PERSONAL

JANE SCOTT FOR GENUINE FRIENDS. Introductions to opposite sex with sincerity and thoughtfulness. Details free. Stamp to: Jane Scott, 3/Con North St. Quadrant, Brighton, Sussex, BN1 3GJ.

SPONSORS required for exciting scientific project Norwich Astronomical Society are building a 30" telescope to be housed in a 20" dome of novel design. All labour being given by volunteers. Already supported by Industry and Commerce in Norfolk. Recreational. Educational. You can be involved. Write to: NAS Secretary, 195 White Woman Lane, Old Catton, Norwich, Norfolk.

FOR HELP with (elementary) Computer, statistical or technical mathematics, send query, s.a.e., paper, P.O. for 50p to: Box No. G380.

IF YOU HAVE ENJOYED A HOLIDAY on the Norfolk Broads, why not help to preserve these beautiful waterways. Join the Broads Society and play your part in determining Broadlands future. Further details from: — The Hon. Membership Secretary, The Broads Society, "Icknield," Hilly Plantation, Thorpe St. Andrew, Norwich, NOR 85S.

CHI-KUNG for mental/physical health. Discover "Chi" — the life-force/bio-electricity in your body. Send stamp for your Free Literature. The Chi-Kung Society (REC39), 64 Cecil Road, London E13 0LR.

BROADLANDS RESIDENTIAL CLUB for elderly people. Are you recently retired and looking for a home? We have a delightful top floor room overlooking Oulton Broad, facing south. Write to: The Warden, Broadlands Residential Club, Borrow Road, Oulton Broad, Lowestoft, Suffolk.

BUILD YOUR OWN

P.A. GROUP & DISCO SPEAKERS by R. F. C. Stephens
Save money with this practical guide. Plans for 17 different designs, Line source, I.B., Horn and Reflex types, for 8"-18" drive units. £3.95 post free (\$8 overseas).

THE INFRA-BASS LOUDSPEAKER by G. Holliman
(full constructional details for versions using 15", 12" and 10" drive units.) £2.95 post free (\$6 overseas).

THE DALESFORD SPEAKER BOOK by R. F. C. Stephens
This book is a must for the keen home constructor. Latest technology DIY designs. Plans for I.B., and Reflex designs for 10-100 watts. Also unusual centre-bass system. £2.20 post free (\$5 overseas).

VAN KAREN PUBLISHING
5 Swan Street, Wilmslow, Cheshire

A CAREER IN RADIO

Start training **today** and make sure you are qualified to take advantage of the many opportunities open to the trained person. ICS can further your technical knowledge and provide the specialist training so essential to success.

ICS, the world's most experienced home study college, has helped thousands of ambitious men to move up into higher paid jobs — they can do the same for **you**.

Fill in the coupon below and find out how!

There is a wide range of courses to choose from, including:

CITY & GUILDS CERTIFICATES

Telecommunications Technicians'
Radio TV Electronics Technicians'
Electrical Installations Technicians'
Electrical Installation Work
Radio Amateurs'

MPT Radio Communications Cert.

**EXAMINATION STUDENTS —
GUARANTEED COACHING
UNTIL SUCCESSFUL**

TECHNICAL TRAINING

ICS offer a wide choice of non-exam courses designed to equip you for a better job in your particular branch of electronics, including:
Electronic Engineering & Maintenance
Computer Engineering/Programming
Radio, TV & Audio Engineering & Servicing
Electrical Engineering, Installations & Contracting

COLOUR TV SERVICING

Technicians trained in TV Servicing are in constant demand. Learn all the techniques you need to service Colour and Mono TV sets through new home study course approved by leading manufacturer.

POST THIS COUPON OR TELEPHONE FOR FREE PROSPECTUS

I am interested in

Name Age

Address

Occupation

ICS

Accredited
by CACC
Member of
ABCC

To
International Correspondence Schools
Dept P278 Intertext House, LONDON
SW8 4UJ or phone 01-622 9911 (anytime)

REVOR OPTICAL & TECHNICAL

6 SICILIAN AVENUE
LONDON W.C.1
Tel. 01-836 4536

£14.91

**POST
FREE**

4" dia. lens

FLEXIBLE MAGNIFIER

WITH CAST IRON BASE,
PRECISION GROUND AND
POLISHED LENS, CHROME PLATED
FRAME AND FLEXIBLE TUBE.
IDEAL FOR HOBBIES, AND
DETAILED WORK WHICH REQUIRES
BOTH HANDS FREE.

CALLERS WELCOME

(Subject to price ruling at the time of issue)



RADIO & ELECTRONICS CONSTRUCTOR

Single Copies

Price 55p each, p&p 15p

Issue(s) required

Annual Subscription

Price £8.00 inland, £9.00 overseas (including Eire)

post free, commence with.....issue

Bound Volumes:

Vol. 27. August	1973 to July	1974	Price £3.00, post & pkg £1.05
Vol. 28. August	1974 to July	1975	Price £3.20, post & pkg £1.05
Vol. 29. August	1975 to July	1976	Price £3.50, post & pkg £1.05
Vol. 30. August	1976 to July	1977	Price £3.70, post & pkg £1.05
Vol. 31. August	1977 to August	1978	Price £5.20, post & pkg £1.05
Vol. 32. September	1978 to August	1979	In course of preparation

CORDEX SELF-BINDERS

With title, 'RADIO & ELECTRONICS CONSTRUCTOR' on spine,
maroon only

Price £1.95, post & pkg 45p

With no title on spine, maroon

Price £1.95, post & pkg 45p

With no title on spine, green

Price £1.95, post & pkg 45p

Prices include V.A.T.

DATA BOOK SERIES

DB5 TV Fault Finding, 132 pages Price £1.20, P. & P. 22p

DB6 Radio Amateur Operator's Handbook,

New edition in course of preparation

DB17 Understanding Television, 504 pages Price £3.95, P. & P. 80p

DB19 Simple Short Wave Receivers Price 80p, P. & P. 22p
140 pages

STRIP-FIX PLASTIC PANEL SIGNS

Set 3: Wording — White — 6 sheets Price £1.00, P. & P. 9p

Set 4: Wording — Black — 6 sheets Price £1.00, P. & P. 9p

Set 5: Dials — 6 sheets Price £1.00, P. & P. 9p

Prices include V.A.T.

I enclose Postal Order/Cheque for.....in payment for.....

NAME

ADDRESS

(BLOCK LETTERS PLEASE)

Postal Orders should be crossed and made payable to Data Publications Ltd.

Overseas customers please pay by International Money Order.

All publications are obtainable through your local bookseller

Data Publications Ltd., 57 Maida Vale, London W9 1SN

PLEASE MENTION THIS MAGAZINE WHEN WRITING TO ADVERTISERS