



Save £20 on a DataStation development kit. See page 16

ELECTRONICS WORLD



DECEMBER 2003 £3.25

Planar resistors' stress

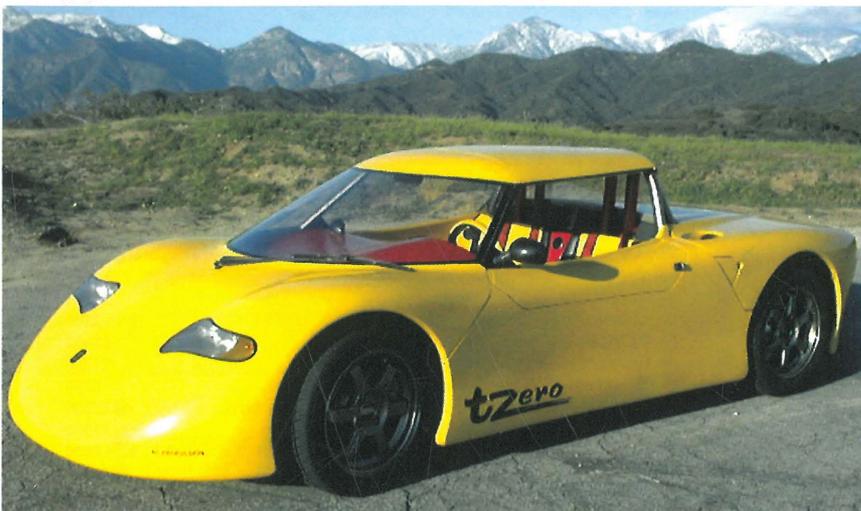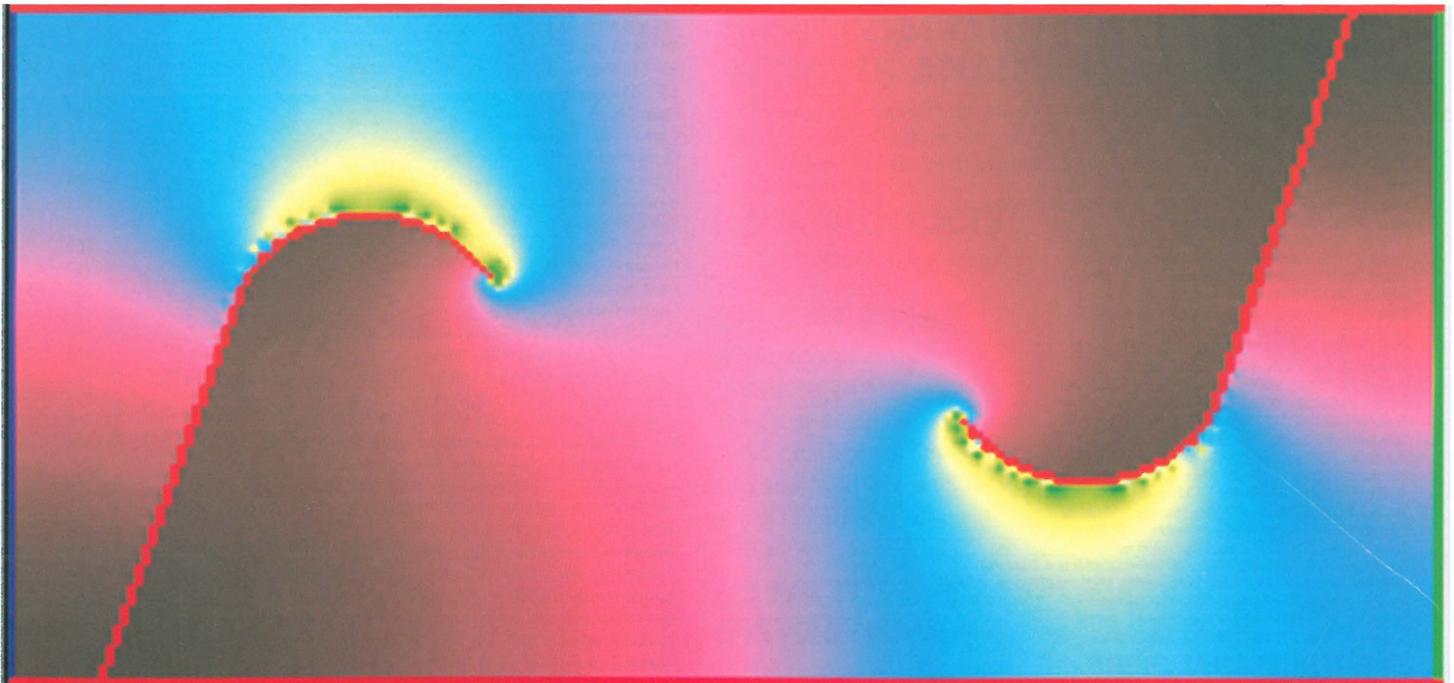

**laptop batteries out-perform
specialist traction batteries**

**MOSFET
auto bias**

**Intro to
network analysis**

Circuit ideas:

Inductance multiplier

Simple code lock



Audio Precision – system 1 – Dual Channel Audio Test System	£2200
ENI 550L Amplifier (1.5 to 400MHz) 50 Watts	£2500
Hewlett Packard 3314A Function Generator 20MHz	£750
Hewlett Packard 3324A synth. function/sweep gen. (21MHz)	£1950
Hewlett Packard 3325B Synthesised Function Generator	£2500
Hewlett Packard 3326A Two-Channel Synthesiser	£2500
H.P. 4191A R/F Imp. Analyser (1GHz)	£3995
H.P. 4192A L.F. Imp. Analyser (13MHz)	£4000
Hewlett Packard 4193A Vector Impedance Meter (4-110MHz)	£2900
Hewlett Packard 4278A 1kHz/1MHz Capacitance Meter	£3500
H.P. 53310A Mod. Domain Analyser (opt 1/31)	£3950
Hewlett Packard 8349B (2 - 20 GHz) Microwave Amplifier	£2000
Hewlett Packard 8508A (with 85081B plug-in) Vector Voltmeter	£2500
Hewlett Packard 8904A Multifunction Synthesiser (opt 2+4)	£1750
Hewlett Packard 89440A Vector Signal Analyser (1.8GHz) opts AY8, AY4, AYB, AY7, IC2	£9950
H.P. ESG-D3000A 3GHz Signal Gen	£6995
Marconi 6310 – Prog'ble Sweep gen. (2 to 20GHz) – new	£2500
Marconi 6311 Prog'ble sig. gen. (10MHz to 20GHz)	£2995
Marconi 6313 Prog'ble sig. gen. (10MHz to 26.5GHz)	£3750
R&S SMG (0.1-1GHz) Sig. Generator (opts B1+2)	£2500
Rhode & Schwarz UPA3 Audio Analyser	£1500
Rhode & Schwarz UPA3 Audio Analyser	£2250
Fluke 5700A Multifunction Calibrator	£12500
Fluke 5800A Oscilloscope Calibrator	£9995

OSCILLOSCOPES

Gould 4068 150MHz 4 channel DSO	£1250
Gould 4074 100MHz - 400 Ms/s - 4 channel	£1100
Hewlett Packard 54502A - 400MHz - 400 MS/s 2 channel	£1600
Hewlett Packard 54520A 500MHz 2ch	£2750
Hewlett Packard 54600A - 100MHz - 2 channel	£675
Hewlett Packard 54810A 'Infinium' 500MHz 2ch	£2995
Intron 2020 - 20MHz. Dual channel D.S.O (new)	£450
Iwatsu SS 5710/SS 5702 - from £125	
Kikusui COS 5100 - 100MHz - Dual channel	£350
Lecroy 9314L 300MHz - 4 channels	£2750
Meguro MSO 1270A - 20MHz - D.S.O. (new)	£450
Philips 3295A - 400MHz - Dual channel	£1400
Philips PM3392 - 200MHz - 200Ms/s - 4 channel	£1750
Philips PM3094 - 200MHz - 4 channel	£1500
Tektronix 2213/2215 - 60MHz - Dual channel	£300
Tektronix 2220 - 60MHz - Dual channel D.S.O	£850
Tektronix 2221 - 60MHz - Dual channel D.S.O	£850
Tektronix 2235 - 100MHz - Dual channel	£500
Tektronix 2245A - 100MHz - 4 channel	£700
Tektronix 2430/2430A - Digital storage - 150MHz	from £1250
Tektronix 2445 - 150MHz - 4 channel +DMM	£850
Tektronix 2445/2445B - 150MHz - 4 channel	£800
Tektronix 2465/2465A/2465B - 300MHz/350MHz 4 channel	from £1250
Tektronix 7104 - 1GHz Real Time - with 7A29 x2, 7B10 and 7B15	from £1950
Tektronix TDS 310 50MHz DSO - 2 channel	£750
Tektronix TDS 420 150 MHz 4 channel	£950
Tektronix TDS 520 - 500MHz Digital Oscilloscope	£2500

SPECTRUM ANALYSERS

Advantest 4131 (10kHz - 3.5GHz)	£3000
Advantest/TAKE DA RIKEN - 4132 - 100kHz - 1000MHz	£1350
Ando AC 8211 - 1.7GHz	£1500
Avcom PSA-65A - 2 to 1000MHz	£750
Farnell SSA-1000A 9kHz-1GHz Spec. An.	£1250
Hewlett Packard 182T Mainframe + 8559A Spec.An. (0.01 to 21GHz)	£2000
Hewlett Packard 853A Mainframe + 8559A Spec.An. (0.01 to 21GHz)	£2500
Hewlett Packard 3582A (0.02Hz - 25.5kHz) dual channel	£1500
Hewlett Packard 3585A 40 MHz Spec Analyser	£3000
Hewlett Packard 3585B 20 Hz - 40 MHz	£4500
Hewlett Packard 3561A Dynamic Signal Analyser	£3500
Hewlett Packard 8568A -100kHz - 1.5GHz Spectrum Analyser	£3500
Hewlett Packard 8590A (opt 01, 021, 040) 1MHz-1.5MHz	£2500
Hewlett Packard 8592B 9 KHz - 22 GHz	£7995
Hewlett Packard 8594 9 KHz - 2.9 GHz	£4500
Hewlett Packard 8596E (opt 41, 101, 105, 130) 9kHz - 12.8GHz	£9950
Hewlett Packard 8713C (opt 1 E1) Network An. 3 GHz	£6000
Hewlett Packard 8713B 300kHz - 3GHz Network Analyser	£5000
Hewlett Packard 8752A - Network Analyser (1.3GHz)	£4995
Hewlett Packard 8753A (3000kHz - 3GHz) Network An.	£3250
Hewlett Packard 8753B+85046A Network An + S Param (3GHz)	£6500
Hewlett Packard 8754A - Network Analyser 4MHz -1300MHz)	£1500
Hewlett Packard 8756A/8757A Scaler Network Analyser	from £900
Hewlett Packard 8757C Scalar Network Analyser	£3500
Hewlett Packard 70001A/70900A/70906A/70902A/70205A - 26.5 GHz Spectrum Analyser	£7000
IFR A7550 - 10kHz-GHz - Portable	£1750
Meguro - MSA 4901 - 30MHz - Spec Analyser	£600
Tektronix 492P (opt 1,2,3) 50kHz - 21GHz	£3500
Willtron 6409 - 10-2000MHz R/F Analyser	£1250
Tek 496 (9kHz-1.8GHz)	£2500

All equipment is used - with 30 days guarantee and 90 days in some cases.

Add carriage and VAT to all goods.

1 Stoney Court, Hotchkiss Way, Binley Industrial Estate
Coventry CV3 2RL ENGLAND

Radio Communications Test Sets

Hewlett Packard 8920B (opts 1,4,7,11,12)	£6750
Hewlett Packard 8922M + 83220E	£2000
Marconi 2955	£1250
Marconi 2955B/60B	£3500
Marconi 2955R	£1995
Motorola R2600B	£2500
Racal 6103 (opts 1, 2)	£5000
Rohde & Schwarz SMFP2	£1500
Rohde & Schwarz CMD 57 (opts B1, 34, 6, 19, 42, 43, 61)	£4995
Rohde & Schwarz CMT 90 (2GHz) DECT	£3995
Rohde & Schwarz CMTA 94 (GSM)	£4500
Schlumberger Stabilock 4015	£3250
Schlumberger Stabilock 4031	£2750
Schlumberger Stabilock 4040	£1300
Wavetek 4103 (GSM 900) Mobile phone tester	£1500

MISCELLANEOUS


Ballantine 1620A 100Amp Transconductance Amplifier	£1250
EIP 545 Microwave Frequency Counter (18GHz)	£1000
EIP 548A and B 26.5GHz Frequency Counter	from £1500
EIP 575 Source Locking Freq.Counter (18GHz)	£1200
EIP 585 Pulse Freq.Counter (18GHz)	£1200
Fluke 6060A and B Signal Gen. 10kHz - 1050MHz	£950
Genrad 1657/1658/1693 LCR meters	from £500
Gigatronics 8541C Power Meter + 80350A Peak Power Sensor	£1250
Gigatronics 8542C Dual Power Meter + 2 sensors 80401A	£1995
Hewlett Packard 339A Distortion measuring set	£600
Hewlett Packard 436A power meter and sensor (various)	from £750
Hewlett Packard 438A power meter - dual channel	£1750
Hewlett Packard 3335A - synthesiser (200Hz-81MHz)	£1750
Hewlett Packard 3457A null meter 6 1/2 digit	£850
Hewlett Packard 3784A - Digital Transmission Analyser	£2950
Hewlett Packard 37900D - Signalling test set	£2500
Hewlett Packard 34401A Multimeter	£500
Hewlett Packard 4274A LCR Meter	£1750
Hewlett Packard 4275A LCR Meter	£2750
Hewlett Packard 4276A LCZ Meter (100MHz-20KHz)	£1400
Hewlett Packard 5342A Microwave Freq.Counter (18GHz)	£850
Hewlett Packard 5385A - 1 GHz Frequency counter	£495
Hewlett Packard 6060A and B Electronic Load 300W	from £750
Hewlett Packard 6622A - Dual O/P system p.s.u	£950
Hewlett Packard 8350B - Sweep Generator Mainframe	£1500
Hewlett Packard 8642A - high performance R/F synthesiser (0.1-1050MHz)	£2500
Hewlett Packard 8656A - Synthesised signal generator	£750
Hewlett Packard 8656B - Synthesised signal generator	£995
Hewlett Packard 8657A - Synth. signal gen. (0.1-1040MHz)	£1500
Hewlett Packard 8657B - 100MHz Sig Gen - 2060 MHz	£3950
Hewlett Packard 8657D - XX DQPSK Sig Gen	£3950
Hewlett Packard 8901B - Modulation Analyser	£1750
Hewlett Packard 8903A, B and E - Distortion Analyser	from £1000
Hewlett Packard 11729B/C Carrier Noise Test Set	from £2500
Hewlett Packard 53131A Universal Frequency counter (3GHz)	£850
Hewlett Packard 85024A High Frequency Probe	£1000
Hewlett Packard 6032A Power Supply (0-60V)-(0-50A)	£2000
Hewlett Packard 5351B Microwave Freq. Counter (26.5GHz)	£2750
Hewlett Packard 5352B Microwave Freq. Counter (40GHz)	£5250
Keithley 220 Programmable Current Source	£1750
Keithley 228A Prog'ble Voltage/Current Source IEEE.	£1950
Keithley 237 High Voltage - Source Measure Unit	£3950
Keithley 238 High Current - Source Measure Unit	£3750
Keithley 486/487 Picoammeter (+volt.source)	£1350/£1850
Keithley 617 E Electrometer/source	£1950
Keithley 8006 Component Test Fixture	£1750
Marconi 6950/6960/6960A/6970A Power Meters & Sensors	from £400
Philips 5515 - TN - Colour TV pattern generator	£1400
Philips PM 5193 - 50 MHz Function generator	£1350
Philips PM 6654C System Timer Counter	£750
Rohde & Schwarz FAM (opts 2,6 and 8) Modulation Analyser	£2500
Rohde & Schwarz NRV/NRVD Power meters with sensors	from £1000
Tektronix AM503 - AM503A - AM503B Current Amp's with M/F and probe	from £800
Wayne Kerr 3245 - Precision Inductance Analyser	£1750
Bias unit 3220 and 3225L Cal.Coil available if required.	(P.O.A)
Wayne Kerr 3260A + 3265A Precision Magnetics Analyser with Bias Unit	£5500
W&G PCM-4 PCM Channel measuring set	£3750

3 COMMENT


Too much regulation?

5 NEWS

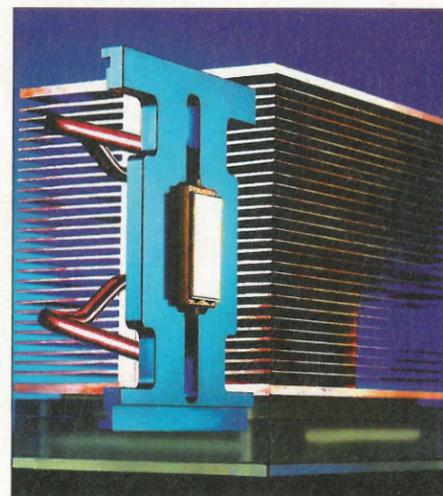- Bacteria makes electricity from sugar
- Optocouplers will use silicon
- Super magnet breaks field record
- Soothing the hot spots



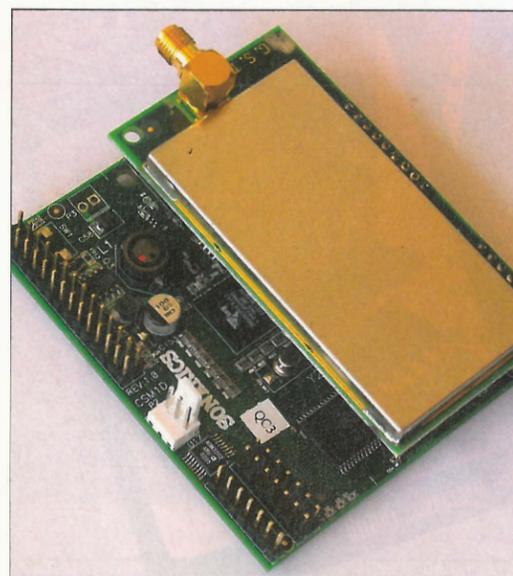- Capacitive coupling is fast
- IEE merger backed by Government
- DAB radio reference design



- Credit cards get smart
- European 65nm CMOS disclosed
- Digital TV too complicated, says DTI
- Light emitting handbag

12 REDUCING THE STRESS IN PLANAR RESISTORS

Leslie Green explains how best to mount resistive elements on PCBs

17 AUTOBIAS FOR MOSFET OUTPUT STAGES

If you think biasing for vertical d-MOSFETS in a class AB output stage is not very critical, let Edmund Stuart put you right.

21 TIME MACHINE 2

John Morrison concludes his article on accurate time measurement on a budget.

24 AN INTRODUCTION TO NETWORK ANALYSIS

Software based circuit simulators are all very well but John Ellis thinks he can give you a better insight into the usefulness of these tools.

29 NEW PRODUCTS

The month's top new products.

34 CIRCUIT IDEAS

- Simple code clock
- Staircase waveform generator
- Voltage-controlled capacitance/inductance
- An inductance multiplier
- A simple driver circuit for stepper motor
- Cut relay power to a quarter

46 CAPACITOR & AMPLIFIER DISTORTIONS

Cyril Bateman concludes his latest distortion series with tests on resistors and op-amps.

54 LETTERS

- Wideband buffers
- Walt Disney University
- In the defence of Mr Miller
- Volks radio receivers
- Attracting younger readers
- Detention Green
- Cyril's quiz answer
- EMC misconception
- Help wanted

60 WEB DIRECTIONS

Useful web addresses for electronics engineers.

READER OFFER

Buy a discounted, software configurable serial I/O card, courtesy of **Observant Electronics**. Extended due to popular demand!

OLSON[®]

UK's NO.1 IEC CONNECTION



CALL OUR SALES HOTLINE
020 8905 7273

   
24 HOUR DELIVERY SERVICE
OLSON ELECTRONICS LIMITED
OLSON HOUSE, 490 HONEYPOT LANE, STANMORE, MIDDX HA7 1JX
TEL: 020 8905 7273 FAX: 020 8952 1232
e-mail: sales@olson.co.uk web site: <http://www.olson.co.uk>

EDITOR
Phil Reed
p.reed@highburybiz.com

CONSULTANT
Ian Hickman

CONTRIBUTING EDITOR
Martin Eccles

EDITORIAL E-MAILS
EEditor@highburybiz.com

EDITORIAL ADMINISTRATION
Caroline Fisher
01322 611274
EAdmin@highburybiz.com

GROUP SALES
Reuben Gurunlian
01322 611292

ADVERTISEMENT E-MAILS
r.gurunlian@highburybiz.com

CLASSIFIED FAX
01322 616376

PUBLISHING DIRECTOR
Tony Greville

ISSN 0959-8332
SUBSCRIPTION QUERIES
Tel (0) 1353 654431
Fax (0) 1353 654400

Disclaimer
We work hard to ensure that the information presented in *Electronics World* is accurate. However, *Electronics World's* publisher - Highbury Business Communications - will not take responsibility for any injury or loss of earnings that may result from applying information presented in the magazine. It is your responsibility to familiarise yourself with the laws relating to dealing with your customers and suppliers, and with safety practices relating to working with electrical/electronic circuitry - particularly as regards electric shock, fire hazards and explosions.


Too much regulation?

I've been following the letters in the last few months concerning EMC and CE marks. Reader consensus seems to be about 50-50 on whether in fact there is a conspiracy or not. My own opinion is that I am sure the regulations do some good - but is it too little for the cost to the consumer. Does the consumer get his/her money's worth? I don't think so. Putting aside industrial, military and transport electronics for a moment, my own experiences are that the things that traditionally cause interference still do. If I want to listen to AM radio, I must make sure I'm nowhere near my TV or fluorescent lighting. If I'm using a sensitive microphone amplifier, I must make sure there is not a refrigerator on the same power circuit. My mobile phone (only spewing a few watts at very high frequency) will interfere with anything audio I own. And so it goes on - so regulations for the aforementioned interferers don't seem to work or they are not worth the paper they are printed on.

When it comes to industrial gear - in particular when life is at risk if anything went awry - I can see some sense. Although quite what it is that comes out of a CD/MD/DVD player that can affect an aircraft I can't imagine. But most flights these days ban them. And all this when the jury is still out on links to cancer from overhead power lines and transmitters. Something's not making sense.

If you read last month's leader, you'll know I went to Rhodes on holiday. Whilst there I spied a fascinating pole mounted power distribution system. Looking closely and also working out roughly the load on what appears to be a 125A feeder - I suggest that the latest IEE regs were not followed. But does it really matter? The pole has been there for years and there was no evidence of overload or indeed any other problems. So, does it matter that we sometimes don't follow the advice of the gurus? In this instance obviously not.

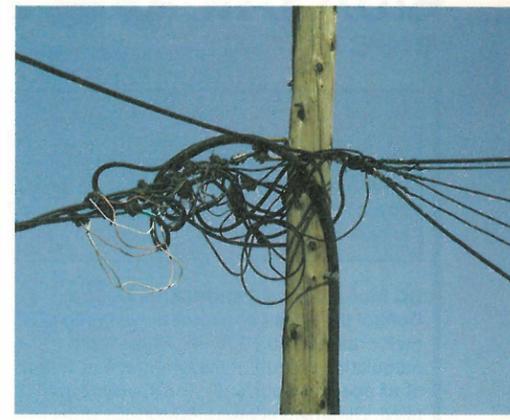Wireless
Last month I suggested that G3 franchise holders ought to sell to the business fraternity and low and behold, Motorola have just announced that they are working on a network card that will hook into a Wi-Fi network if available and if not - seek out



a G3 connection. Well done. Perhaps the porn industry won't be the 'killer app' for G3 after all.

Welcome
I'd like to welcome Caroline Fisher to our little EW team. Caroline has taken over from Jackie and will be your first point of contact for all things administrative. So, for those of you who were wondering if you'd ever get a response from us - hopefully you will soon!
Phil Reed

New editorial and advertising address
The Highbury Business Communications office previously at Cheam, Surrey has moved to Swanley in Kent. All correspondence intended for the editorial and advertising departments should be addressed to:
Electronics World,
Highbury Business Communications,
Nexus House,
Azalea Drive,
Swanley,
Kent, BR8 8HU
The switchboard phone no. is 01322 660 070
Advertising sales (Reuben Gurunlian)
Tel 01322 611292
Fax 01322 616 339

Electronics World is published monthly. Orders, payments and general correspondence to **Jackie Lowe, Highbury Business Communications, Nexus House, Azalea Drive, Swanley, Kent, BR8 8HU**
Subscriptions: Wyvern Subscription Services, Link House, 8 Bartholomew's Walk, Ely Cambridge, CB7 4ZD. Telephone 01353 654431. Please notify change of address.
Subscription rates
1 year UK £38.95 O/S £64.50
US\$100.62 Euro 102.55
Newstrade: Distributed by COMAG, Tavistock Road, West Drayton, Middlesex, UB7 7QE Tel 01895 444055.

USA mailing agents: Mercury Airfreight International Ltd Inc, 10(b) Englehard Ave, Avenel NJ 07001. Periodicals Postage Paid at Rahway NJ Postmaster. Send address changes to above.
Printed by Polestar (Colchester) Ltd,
Filmsetting by G&E 2000
A1 Parkway, Southgate Way, Orton Southgate, Peterborough, PE2 6YN


HIGHBURY
Business Communications
A SUBSIDIARY OF HIGHBURY HOUSE COMMUNICATIONS PLC



Quasar Electronics Limited
 PO Box 6936, Bishops Stortford,
 CM23 4WP
 Tel: 0870 246 1826
 Fax: 0870 460 1046
 E-mail: sales@quasarelectronics.com

Add £2.00 P&P to all UK orders. 1st Class Recorded - £4.
 Next day (insured £250) - £7. Europe - £5. Rest of World - £10.
 We accept all major credit/debit cards. Make cheques/PO's
 payable to Quasar Electronics Limited.
 Prices include 17.5% VAT. MAIL ORDER ONLY.
 Call now for our FREE CATALOGUE containing details of
 over 300 electronic kits, projects and modules.



QUASAR 0871 CREDIT CARD SALES 717 7168 electronics

Motor Drivers/Controllers

Here are just a few of our controller and driver modules for AC, DC, unipolar/bipolar stepper motors and servo motors. See website for full details.

DC Motor Speed Controller (5A/100V)

Control the speed of almost any common DC motor rated up to 100V/5A. Pulse width modulation output for maximum motor torque at all speeds. Supply: 5-15VDC. Box supplied. Dimensions (mm): 60Wx100Lx60H. Kit Order Code: 3067KT - **£12.95**
 Assembled Order Code: AS3067 - **£19.95**

NEW! PC / Standalone Unipolar Stepper Motor Driver

Drives any 5, 6 or 8-lead unipolar stepper motor rated up to 6 Amps max. Provides speed and direction control. Operates in stand-alone or PC-controlled mode. Up to six 3179 driver boards can be connected to a single parallel port. Supply: 9V DC. PCB: 80x50mm. Kit Order Code: 3179KT - **£9.95**
 Assembled Order Code: AS3179 - **£16.95**



PC Controlled Dual Stepper Motor Driver

Independently control two unipolar stepper motors (each rated up to 3 Amps max.) using PC parallel port and software interface provided. Four digital inputs available for monitoring external switches and other inputs. Software provides three run modes and will half-step, single-step or manual-step motors. Complete unit neatly housed in an extended D-shell case. All components, case, documentation and software are supplied (stepper motors are NOT provided). Dimensions (mm): 55Wx70Lx15H. Kit Order Code: 3113KT - **£15.95**
 Assembled Order Code: AS3113 - **£24.95**

NEW! Bi-Polar Stepper Motor Driver
 Drive any bi-polar stepper motor using externally supplied 5V levels for stepping and direction control. These usually come from software running on a computer. Supply: 8-30V DC. PCB: 75x85mm. Kit Order Code: 3158KT - **£12.95**
 Assembled Order Code: AS3158 - **£26.95**



Controllers & Loggers

Here are just a few of the controller and data acquisition and control units we have. See website for full details. Suitable PSU for all units: Order Code PSU203 £9.95

Rolling Code 4-Channel UHF Remote

State-of-the-Art. High security. 4 channels. Momentary or latching relay output. Range up to 40m. Up to 15 Tx's can be learnt by one Rx (kit includes one Tx but more available separately). 4 indicator LED's. Rx: PCB 77x85mm, 12VDC/6mA (standby). Two and Ten channel versions also available. Kit Order Code: 3180KT - **£41.95**
 Assembled Order Code: AS3180 - **£49.95**



Computer Temperature Data Logger

4-channel temperature logger for serial port. °C or °F. Continuously logs up to 4 separate sensors located 200m+ from board. Wide range of free software applications for storing/using data. PCB just 38x38mm. Powered by PC. Includes one DS1820 sensor and four header cables. Kit Order Code: 3145KT - **£22.95**
 Assembled Order Code: AS3145 - **£29.95**
 Additional DS1820 Sensors - **£3.95 each**



NEW! DTMF Telephone Relay Switcher

Call your phone number using a DTMF phone from anywhere in the world and remotely turn on/off any of the 4 relays as desired. User settable Security Password, Anti-Tamper, Rings to Answer, Auto Hang-up and Lockout. Includes plastic case. 130x110x30mm. Power: 12VDC. Kit Order Code: 3140KT - **£39.95**
 Assembled Order Code: AS3140 - **£69.95**



Serial Isolated I/O Module

PC controlled 8-Relay Board. 115/250V relay outputs and 4 isolated digital inputs. Useful in a variety of control and sensing applications. Uses PC serial port for programming (using our new Windows interface or batch files). Once programmed unit can operate without PC. Includes plastic case 130x100x30mm. Power: 12VDC/500mA. Kit Order Code: 3108KT - **£54.95**
 Assembled Order Code: AS3108 - **£64.95**



Infrared RC Relay Board

Individually control 12 on-board relays with included infrared remote control unit. Toggle or momentary. 15m+ range. 112x122mm. Supply: 12VDC/0.5A
 Kit Order Code: 3142KT - **£41.95**
 Assembled Order Code: AS3142 - **£69.95**



PIC & ATMEL Programmers

We have a wide range of low cost PIC and ATMEL Programmers. Complete range and documentation available from our web site.

Programmer Accessories:
 40-pin Wide ZIF socket (ZIF40W) **£16.00**
 18V DC Power supply (PSU201) **£6.95**
 Leads: Parallel (LEAD108) **£4.95** / Serial (LEAD76) **£4.95** / USB (LEADUAA) **£4.95**

NEW! USB 'All-Flash' PIC Programmer

USB PIC programmer for all 'Flash' devices. No external power supply making it truly portable. Supplied complete with 40-pin wide-slot ZIF socket, box and Windows Software. Kit Order Code: 3128KT - **£49.95**
 Assembled Order Code: AS3128 - **£54.95**



Enhanced 'PICALL' ISP PIC Programmer

Will program virtually ALL 8 to 40 pin PICs plus a range of ATMEL AVR, SCENIX SX and EEPROM 24C devices. Also supports In System Programming (ISP) for PIC and ATMEL AVRs. Free software. Blank chip auto detect for super fast bulk programming. Requires a 40-pin wide ZIF socket (not included). Kit Order Code: 3144KT - **£54.95**
 Assembled Order Code: AS3144 - **£69.95**



ATMEL 89xxx Programmer

Uses serial port and any standard terminal comms program. 4 LED's display the status. ZIF sockets not included. Supply: 16-18VDC. Kit Order Code: 3123KT - **£29.95**
 Assembled Order Code: AS3123 - **£34.95**



NEW! USB & Serial Port PIC Programmer

USB/Serial connection. Ideal for field use. Header cable for ICSP. Free Windows software. See website for PICs supported. ZIF socket not incl. Supply: 18VDC. Kit Order Code: 3149KT - **£29.95**
 Assembled Order Code: AS3149 - **£44.95**



Most items are available in kit form (KT suffix) or assembled and ready for use (AS prefix).

www.quasarelectronics.com

Secure Online Ordering Facilities • Full Product Listing, Descriptions & Photos • Kit Documentation & Software Downloads



UPDATE

Bacteria makes electricity from sugar

Sugars can be converted to electricity with an efficiency higher than previously known, claim researchers at the University of Massachusetts Amherst.


Professor Derek Lovley has discovered a micro-organism that is capable of stable, long-term electricity production by oxidising carbohydrates - but it is early days. "I don't want to give the impression that it's 'Back to the Future,' where we stuff a banana in the engine and go," said Lovley, "but it's a pretty good leap from where microbial fuel cells were before."

Lovley's cell produces 600mV at between 600 and 800µA.

The organism, *Rhodofex ferrireducens*, transfers electrons directly onto an electrode as it metabolises sugar, producing carbon dioxide as a by-product.

"There's been a lot of interest in microbial fuel cells trying to convert sugar into electricity," Lovley said. "But in the past, they've converted ten percent or less of the available electrons, and we're up over 80 per cent. And previous attempts to convert carbohydrates to electricity have required an electron shuttle, or mediator, which is typically toxic to humans."

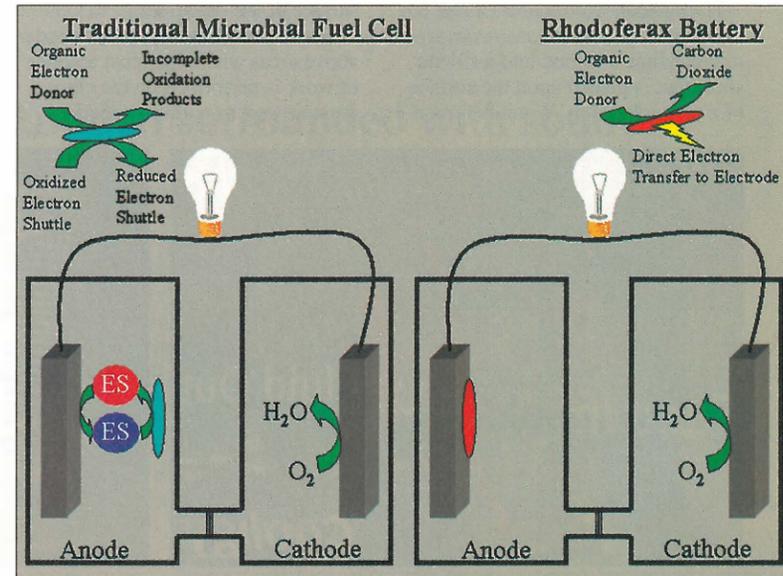
This organism doesn't require a mediator because it attaches directly to the surface of the electrode, said Lovley: "That's one of the big advances. People have done it without a mediator before, but their recovery of energy was less than one per cent. In the end, the electrons in the fuel cell are



transferred to oxygen, so what we are really doing is putting a wire in between the microbe and the oxygen and harvesting this electron flow that otherwise would just go directly to oxygen."

Rhodofex was isolated at the university from aquifer sediments in Virginia. "We found that it had the unique ability to oxidise sugars with the reduction of iron oxides," Lovley said. "This was of interest to us because last year we reported another group of iron reducers, known as *Geobacter*, could transfer electrons to electrodes. We reasoned that *Rhodofex* might be able to do the same thing, which proved to be the case."

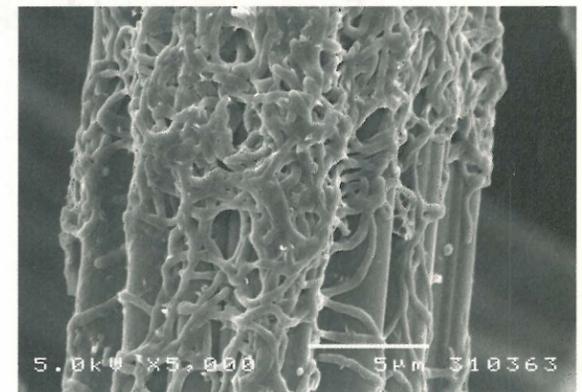In theory, a cup of sugar in a fuel cell could produce 60W for 17 hours.



The organism *Rhodofex* shown on an electrode.

Opcouplers will use silicon


Silicon - great for ICs, but terrible at emitting light. That view may soon change as STMicroelectronics plans to sell optocouplers made using conventional silicon.

The French/Italian chip firm has demonstrated light emitting silicon, and says the efficiency is better than more expensive gallium arsenide.

Moreover, the devices could be integrated with power electronics and control circuits, reducing the number of packages in applications such as motor control.

ST's emitters avoid using silicon's indirect bandgap by embedding rare earth elements, such as erbium, into a layer of silicon dioxide. When charge is injected into the SiO₂ layer it excites the erbium. Photons are released, in erbium's case, at around 1.5µm.

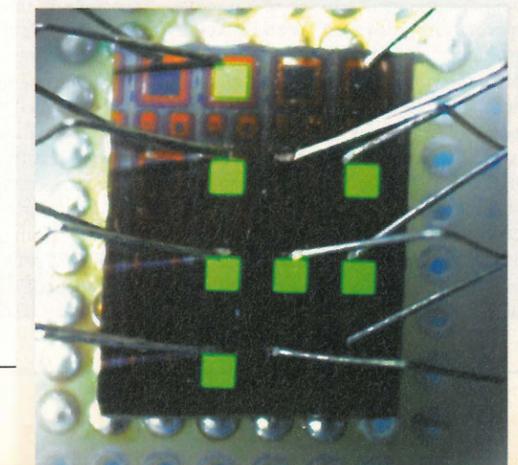Power output is claimed to be 1mW per mm² of silicon. More photons are emitted, at a set current, than conventional LED materials such as AlInGaP and AlInGaN, claimed ST.



STMicroelectronics has produced light from silicon by doping with rare-earth materials. This is not new, many research teams have done it before but, unlike most attempts, ST's devices are easily visible - as Electronics World witnessed during a visit to the development labs in Catania, Sicily. The emitters have been used to construct working all-silicon opto-isolators.

Soothing the hot spots

Technology developed at Stanford University in the US has been applied to the cooling of microprocessors, which could exceed 100W next year.

The system, from a firm called Cooligy, uses a series of microchannels etched into a silicon sheet that is placed upon the surface of a processor chip. Water is forced

through the channels by an "electrokinetic" pump, said the firm.



The advantage of this technique, versus heat sink and fan cooling, is it copes better with hot spots on the surface of the processor.

"These hot spots, typically found above areas where the most amount of work is performed on the chip, must be kept to within a specified

temperature to ensure high performance and reliability," said the firm.

It claims to be able to remove up to 1,000W/cm².

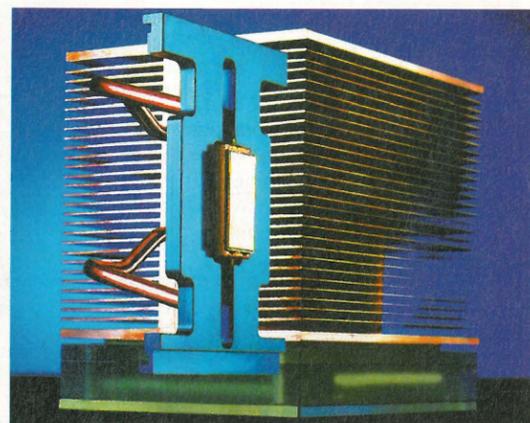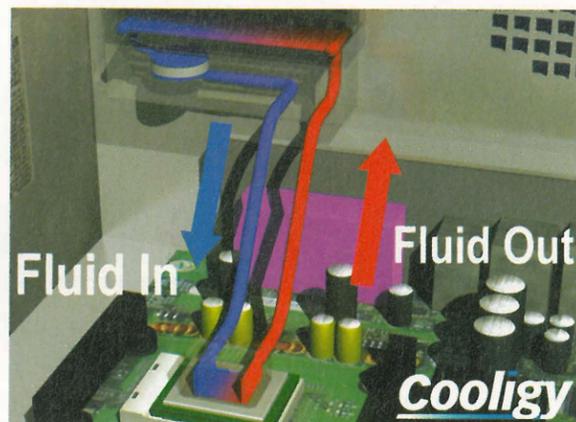Cooligy said its heat sinks would be attached to the processor die at the point of packaging. It expects to start supplying test systems to computer manufacturers this year.



The photos show the microchannel heat collector attached to a mounting plate that connects the heat collector to the CPU. Fluid flows through the collector, back to a radiator that transfers heat to the air, then into a pump located below the radiator. The pump moves the fluid back through the microchannel heat collector, completing the sealed loop.

Super magnet breaks field record

A superconducting magnet has generated a magnetic field of 25 Tesla for the first time.

In the experiment, carried out at the US National High Magnetic Field Laboratory, a 5T high temperature superconductor (HTS) 'insert' coil was positioned in an existing 20T magnet.

The HTS insert coil broke at least seven world records, claims the lab, including the highest field generated in a superconducting magnet and highest increment of field in an HTS insert of useful size. These records were previously held by Japanese industrial scientists.

"This is a critical and essential technological breakthrough for high temperature superconducting

materials for state-of-the-art magnets," said project leader, Dr Justin Schwartz.

The lab worked with New Jersey-based Oxford Superconducting Technology.

"The drive for ever higher fields in commercial NMR spectroscopy magnets was a compelling motivation for Oxford's investment in this achievement, and we look forward to using the technological advances demonstrated in our high field business," said Dr Ken Marken, project leader at Oxford.

Oxford supplied long-lengths of Bi-2212 superconducting wire for the program and both organisations "spent much time on conductor development, conductor

characterisation, coil winding studies, and the testing of coils," they said.

Capacitive coupling is fast

Scientists at Sun Microsystems have invented a technique for passing high speed data between chips without using a direct electrical connection.

In fact the method uses capacitive coupling between closely spaced pads to transfer data from one die to another. Sun says that in tests a single channel could reliably send data at 1.35Gbit/s.

In fact the firm has manufactured test chips with 16 channel links, capable of transferring data at 21.6Gbit/s. At this speed the bit error rate was better than 10⁻¹⁰, claimed the firm.

Links made between chips in this way are a factor of 60 times denser than using wires.

The technique was invented by Ivan Sutherland, a senior engineer at Sun who also invented the micropipeline method of asynchronous logic.

A transmitter is an inverter directly driving the pad, measuring around 35x35µm. The receiver's pad makes up the other half of the capacitor, which feeds to back to inverters.

The smallest pads that gave reliable transmission measured 25x25µm, said Sun.

IEE merger backed by Government

The proposed merger between the Institution of Electrical Engineers (IEE), the Institute of Mechanical Engineers and the Institute of Incorporated Engineers has been backed by the Government.

"This vitally important development reflects the fact that there is an increasing convergence between the disciplines within engineering, and I am sure it will unify and strengthen the profession as a whole," said Lord Sainsbury, minister for science.

"Such an institution would undoubtedly have a stronger voice and therefore be more successful at promoting and representing the

engineering sector."

The IEE itself has indicated that the merger is more likely to happen than not. The previous president of the Institution, Professor Mike Sterling, said earlier this year: "Most of the comment and questions concentrated on how to proceed rather than whether we should."

All three organisations are carrying out consultation with members. A final vote on the proposed merger will be carried out in the autumn.

"Both members and their employers would find such a body more relevant to the first decade of the 21st century," said Sterling.

Digital TV too complicated, says DTI

A study published by the Department of Trade and Industry has warned that many UK consumers are not able to use digital TV systems.

The Government's E-commerce Minister, Stephen Timms, said: "Today's digital TV equipment is confusing and difficult to use."

According to consulting firm Generics, which carried out the DTI's research, over seven per cent of the UK population cannot use a digital set-top box or TV, even for simple everyday viewing. This compares to under three per cent for analogue TVs.

"The UK leads the world in take up of digital TV, and we must not squander the opportunity to make the most of this advantage. This report provides a wake-up call to the industry," said Timms.

Dr Jeremy Klein, Generics project leader, outlined the problem: "We now have a pretty good idea of where the problems lie. Compared with analogue TV, digital TV provides many more useful features; but you can only access those features by using the remote control and on-screen displays.

"Our research indicates that unless improvements are made, then about two million people will not easily be able to use digital TV in its current form."

Much of the technology for digital set-top boxes comes from the PC world. "That's fine if you've had experience of PCs, but not everyone has. Some people simply cannot

understand how to work the equipment and are scared that they will make mistakes," said Klein.

"It's fine to press the red button", claimed Kay Sinclair, Generics' product design expert, "but it's what happens next that confuses people."

London surrounded with sound

A five-channel, surround sound audio broadcast trial has started in London, with UK firms providing the receiving equipment.

Radioscape is supplying much of the core broadcast equipment, based on the digital audio broadcasting (DAB) standard. Receivers come from Radioscape and Imagination Technologies.

The six month pilot scheme sees Capital Radio broadcasts using Microsoft's Windows Media Audio 9 format, which can squeeze 5.1 audio into a 128kbit/s Internet protocol

stream. If you are in an interactive service and you want to go back to the top menu, then every broadcaster does it a different way, she said.

Manufacturers should get together and set design and use standards, the Government said.

NTL Broadcast is proving the multiplex for the trial using L-band (1.4GHz) transmission.

"The high quality and compression efficiencies of Windows Media 9 Series make 5.1-channel surround sound over DAB a reality," said Simon Mason, head of new product development at NTL Broadcast.

The Radioscape receivers are two PCI-bus cards. Imagination is supplying DAB receivers that output the five channel data to a PC via USB cable.

2.4GHz band not congested

A Radiocommunications Agency report shows that the 2.4GHz band remains relatively free from activity in the UK, despite warnings it would be saturated by wireless LAN and Bluetooth.

The report, from Mass Consultants, said "the use of 2.4GHz services appears to be very widespread, although the recorded levels of activity were generally low, both in terms of signal strength and the proportion of the time

that signals were present".

The firm carried out private sector monitoring in Cambridge and public sector tests in schools, hospitals and Heathrow Airport. All areas were covered extensively by wireless LAN.

In fact the main contributor to the band was microwave ovens, while movement detectors were commonly found at low signal strengths.

No cases of wireless LAN congestion were observed, said the firm. No out of band emissions were observed and power levels were within the designated limits.

Light emitting handbag

Bag specialist Bree and Bayer Polymers have teamed up to produce a prototype self-illuminating handbag.

"We had been toying with the idea of illuminating the dark insides of handbags for quite some time, but lacked an elegant solution," said Philipp Bree.

Eckard Foltin, head of Bayer's creative centre, had meanwhile been looking for

another use for the firm's dashboard and headlining illuminating electroluminescent (EL) technology.

The two met, and the result is a bag with a 7 x 16 EL film embossed with the Bree

logo that lights up two compartments at the touch of a button.

"In less than five years, interior light will be just as common in handbags as mobile telephones are today," said Bree.



European 65nm CMOS disclosed

Philips and Belgian research organisation IMEC have released details of the 65nm CMOS process they are jointly developing.

"The completion of fabrication of 65nm CMOS devices with good electrical performance marks the second milestone within the strategic partnership between Philips and IMEC," said IMEC.

65nm is the next step after 90nm, the most advanced CMOS process in production.

The organisations formed an alliance at the beginning of 2000 to explore processing and integration steps in CMOS. Work on 65nm began in early 2002 after achieving the first milestone: 90nm CMOS.

The 65nm technology is based on a scaled version of planar 90nm bulk CMOS.

Devices feature 45nm gate length, equivalent oxide thickness of 1.4nm, 100nm thick polysilicon gates and sub-20nm junction depths. "Gate dielectric recipes were optimised through plasma nitridation of ultra-thin oxides for reduction of gate leakage and suppression of boron penetration," said IMEC. "Shallow source/drain engineering was performed using ultra-low energy implantation in combination with germanium pre-amorphisation and fluorine co-implantation (PMOST) and fast ramping high-temperature spike anneals."

Low-temperature deposition techniques were introduced in the back-end for spacer, silicide blocking and pre-metal dielectric layers to avoid excessive dopant

diffusion and de-activation.

Finally a two-step nickel salicidation was integrated to improve control of line width effects as well as reduced junction leakage and contact resistance.

Drive currents of $790\mu\text{A}/\mu\text{m}$ for NMOST and $355\mu\text{A}/\mu\text{m}$ for PMOST were obtained at $V_{\text{dd}}=1\text{V}$ and an off-state current of $100\text{nA}/\mu\text{m}$.

Devices exhibit good short channel effects control. "The achieved electrical performance, which compares favourably with results from other companies, demonstrates that a successful step has been made in the joint exploration of the 65nm technology at IMEC and Philips Research," says Dr Carel van der Poel, senior v-p of Philips Research.

Credit cards get smart

UK consumers are beginning to receive credit and debit cards containing secure microcontrollers as part of the national Chip and PIN programme.

The replacement of magnetic stripe cards has begun in earnest, in a bid to cut the UK's annual fraud bill of £425m.

Replacing the country's 122 million cards, 850,000 shop terminals and 40,000 cash machines will cost the UK banks around £1.25bn.

Chip and PIN was trialed through the summer in Northampton with over 200,000 cards being issued and 1,000 retailers set up with card readers. In a

survey, four fifths of users were said to be in favour of the scheme.


"I am encouraged that the lessons learnt in the trial will be taken forward as the scheme is rolled out across the country, so that the majority of plastic card transactions will be chip and PIN by 2005," said Hazel Blears, minister for crime reduction and policing. "As well as fighting fraud, Chip and PIN has also proved to be an efficient, secure and customer-friendly system."

APACS, the Association for Payment Clearing Services, has set a deadline of 2005 for a complete switchover to the smartcards. By the end of this year 20 per cent of UK cardholders will be using the cards.

In 2002 the UK banks lost £425m to card fraud, the majority of which was to counterfeiting (£148m). Card-not-present fraud cost £110m, while theft using stolen or lost cards cost £108m.

Sonarics Labs has unveiled a DAB radio reference design. Called CSM1, the design is based around Analog Devices' \$5 Blackfin general purpose DSP. Running on this, Sonarics' software implements DAB Band III and L-Band decoding, MP3 playback from a flash card and digital sound recording. The evaluation module in the picture is available for £199 (\$299) and is 76 x 66 x 15mm. Sonarics estimates the parts would cost \$25 in production.

www.sonarics.com

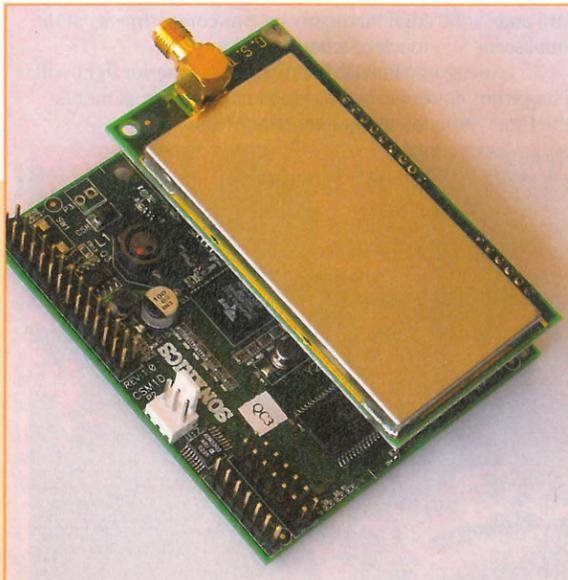

Superlattices transducer

Improved ultrasound transducers could spring from theoretical computer-based studies at the University of Arkansas.

"We can design new materials based on our predictions," said researcher Igor Kornev.

Using a computer model first described in 2000, Kornev and fellow researcher Laurent Bellaiche looked at hypothetical ferroelectric superlattices made of layers of lead zirconate titanate (PZT) with different titanium compositions.

In particular, superlattices with between one and six layers of 44 per cent titanium PZT alternating with layers of 52 per cent titanium PZT.

The average titanium composition of these is 48 per cent - the composition at which normal - disordered - PZT exhibits a huge piezoelectric response.

With six layers of each, the superlattice exhibited a phase transition not previously seen in any piezoelectric material.

This transition created an even larger piezoelectric response than the phase transition known in the disordered material.

In addition, they found that the superlattice can be stuck in a higher energy state than the ground state, which implies commonly used and assumed statistical laws are not always valid, said the team.

"These superlattices are thus important not only for technological applications but also from a fundamental physics point of view" Kornev said.



S.V.G.A II

NEW! SVGA II now has a slimline case, 9 display outputs at 640*480, 800*600 & 1024*768. Colourbars, crosshatch, dot, black, red, green, blue, white and flashing white patterns. Test and set-up computer monitors without a PC. 15 way D type output, runs on 8-12V DC adapter and be built in a couple of hours. **New lower kit price of only £29.50.**

Can be supplied in PC Bone or Black case. Software upgrade available for original SVGA generator.



MULTIGEN VIDEO GENERATOR

From the Author of SVGA generator and Videogen comes a new all in one unit. Ten display outputs in PAL, NTSC & VGA of testcard, colourbars, grayscale, crosshatch, centering, red, green, blue, white and flashing white. PAL 625 lines 50Hz - NTSC 515 lines 60 Hz, Composite & 5 Video outputs - VGA 640*480 60 Hz, 15 way D - AUDIO 1 KHz Phono output. Unit can be powered via 8-12V DC adapter, 2 AA alkaline or rechargeable batteries that are recharged via adapter.

Full kit of parts to build the Multigen, £58 or £62 including 1.6A/hr NiMH Batteries.

Based on a 50 mips Ubicom/Scenix micro running software routines to create fully interlaced test patterns. An Analogue devices AD722 chip performs the RGB conversion giving a 1Volt signal into 75 ohm termination. A DC/DC converter power supply enables just 2 AA cells to power the Multigen. Audio tone output is a sine wave generated by a Wien bridge oscillator circuit with a buffered output. The kit comes with a high quality double sided PCB with ready programmed micro and AD722 chip ready soldered. All components including case, self adhesive overlay, drill template and full construction details are supplied in the kit. Only soldering of components to PCB and drilling, filing of plastic end panels is required to construct Multigen. The unit can be built in three to four hours. Visit our Website for circuit diagrams, layout details and actual screen shots of the different patterns produced.

Note: Micro can be re-programmed onboard for future software upgrades.

Now available in PC Bone or Black case, please state when ordering.

Please add £2 postage to all orders. £3 for overseas orders. Send cheque, Postal Orders or International Money Orders to:

J Harding, 43 Jonathan road, Trentham, Stoke-on-Trent, Staffs, ST4-8LP England.

Coming soon. D-GEN a PAL 512*288 digital pattern generator with 3:4 / 16:9 Testcards & Scart RGB output.

For more information on these two kits and future products, send S.A.E or.

Visit our website "<http://www.videocorner.co.uk>" or Email us at "roy@videocorner.co.uk"



Easy-PC for Windows

World Beating Value in PCB Design Software


from
£97

High performance Windows based PCB Design Capture, Simulation and Layout software at prices you'd expect from your local computer store!



NEW! in Easy-PC 7

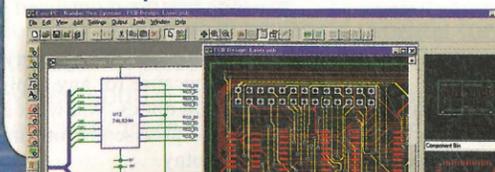- Library Databook
- Step and repeat plotting
- Swap Connection Mode
- Dimensioning
- Copy to Metafile plus much more.....



Stop press... by customer demand, now with Tsien Boardmaker 2 design import...

Number One Systems delivers true 32 bit Windows software applications including features that a few short years ago would only have been available in software tools priced in the thousands!

Test drive Easy-PC and Easy-Spice for yourself and be prepared to be amazed at the super value...

Call for a brochure, price list and demo CD on +44 (0)1684 773662 or email sales@numberone.com

No1 Number One Systems

Number One Systems
Oak Lane, Bredon
Tewkesbury, Glos GL20 7LR
United Kingdom

or download from
www.numberone.com

Better audio and smaller PCs from VIA

PC component maker has introduced a new audio chip, aimed at home entertainment PCs.

Called Eight-TRAC Audio, the device complies with AC'97 revision 2.3, supports 8 channel outputs, and up to 20-bit resolution with 96kHz sampling rates.

Hardware down-mixing allows PC users to play 6-channel audio with two or four speakers and the analog mixer circuitry includes stereo processing to provide 3D surround sound effect for stereo media. A high-quality headphone amplifier is also included on the chip.

Automatic jack detection allows users to connect a record or playback

audio device to any jack. The chip will detect this and the user can then configure the correct I/O to the jack in use through the PC.

VIA also announced a smaller PC motherboard format.

The successful 17 x 17cm mini-ITX PC motherboard format was initially promoted by the firm 18 months ago and it is now mooted a full-function PC on a 12 x 12cm board - dubbed nano-ITX.

It is aimed at "the next generation of smaller, quieter, digitally intelligent home, office, mobile, industrial and commercial devices", said VIA.

www.via.com.tw

VIA Eight-TRAC Audio chip

AC97 rev 2.3 compliant
96kHz sampling
20-bit ADC and 20-bit DAC
>95dB signal/noise
7.1 ch outputs
96kHz S/PDIF output
Direct CD input to S/PDIF output
Integrated headphone amp
3.3V or 5V analog power
3.3V digital power
48-Pin LQFP package

Laptop batteries can out-perform specialist traction batteries when it comes to electric vehicles.

Laptop batteries can out-perform specialist traction batteries when it comes to electric vehicles.

Californian firm AC Propulsion recently revamped its tzero prototype car to make the 'super Light

version'. A move from lead-acid batteries to lithium-ion (Li-ion) saved 230kg and tripled the vehicle's energy capacity.


Power comes from 6,800 65 x 18mm diameter (18650 size) Li-ion

cells - as used in laptop battery packs. "The market for big cells is small so they cost too much," said company president Tom Gage. "The small cells for the tzero cost less, in total, than the nickel-metal hydride battery in the Toyota RAV4 electric vehicle, and they hold twice the energy."

Gage look into getting 'vehicle' cells made. "We got a quote from one battery company for a Li-ion pack made from 100 much larger cells," he said. "Their price was ten times higher, and neither the energy or the power were as good as we get from the small cells. If you want to start building electric cars right now, as we do, you have to have a commercial battery. Right now, 18650s are the only game in town."

Tzero weighs 900kg and will drive 250 miles in 75-80mph traffic. "On any type of standardised drive cycle it will go over 300 miles," said Gage. Its best 0-60mph time is 3.6s.

www.acpropulsion.com

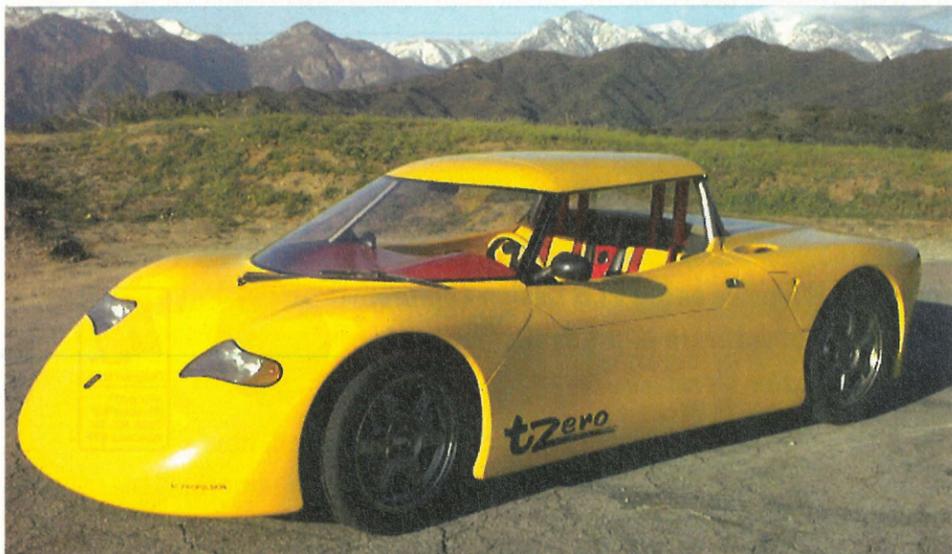

Carbon shines perfect light

Carbon nanotubes are "ideal photon emitters", said researchers at the US University of Rochester.

"The emission bandwidth is as narrow as you can get at room temperature," said professor Lukas Novotny of the university's optics department.

Precise, discrete, wavelengths are emitted by the tubes, unlike the wider band output of most materials at room temperature.

The team was using confocal microscopy, illuminating a single nanotube with a focused laser beam to see what was re-emitted by fluorescence.

"The emission wasn't just perfectly narrow, it was steady as far as we could measure," said researcher Todd Krauss.

Molecules, said Rochester, usually emit their photons for a certain time and then cease, only to resume again

later. The tubes that Krauss and Novotny measured remained steady to the limits of their instrumentation. "This is very exciting because for any application in quantum optics, you want a steady and precise photon emitter," said Novotny.


Narrow steady emissions could help with the development of single photon emitters - used in quantum cryptography.

Correction

The UK's most powerful computer, HPCx, is not located in Oxfordshire as we reported in the September edition of EW, but Cheshire, and is part of Daresbury Laboratory near Warrington. More information about this facility can be found at: www.cse.clrc.ac.uk/hp/cx/index.shtml

PROTEUS

The Complete Electronics Design System

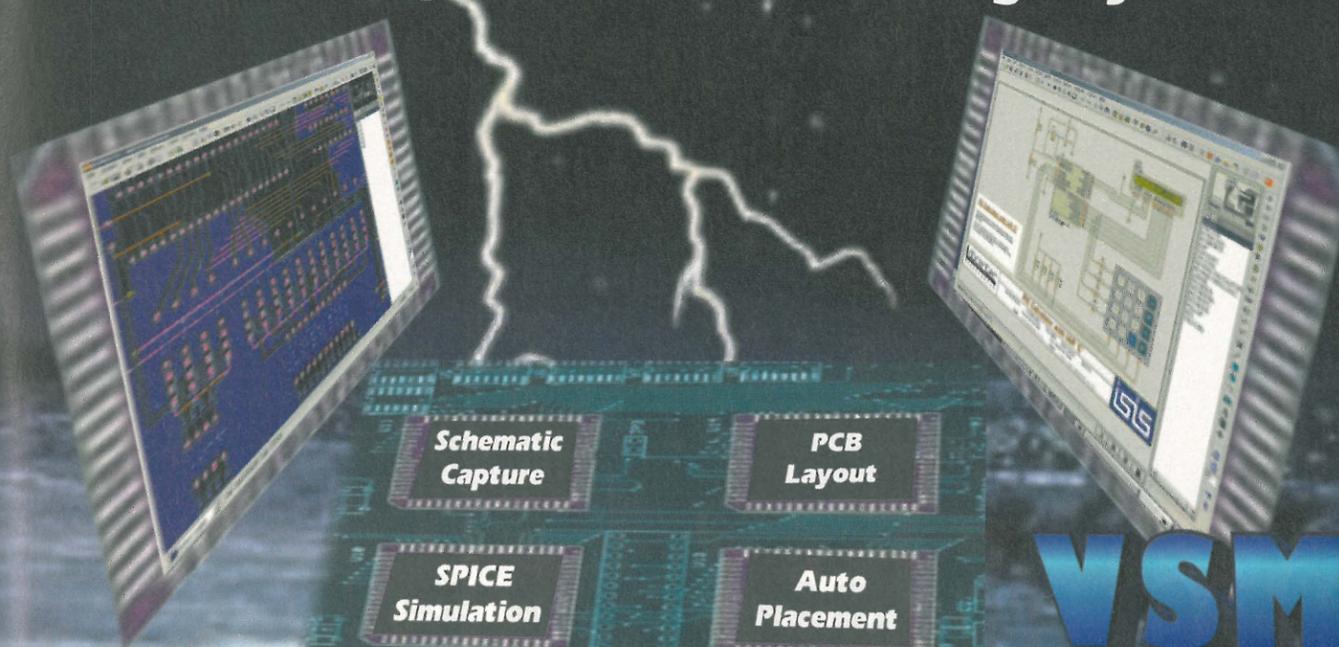

VSM
Virtual System Modelling

- ### Schematic & PCB Layout


 - Powerful & flexible schematic capture.
 - Auto-component placement and rip-up/retry PCB routing.
 - Polygonal gridless ground planes.
 - Libraries of over 8000 schematic and 1000 PCB parts.
 - Bill of materials, DRC reports and much more.

New Features in Version 6

 - Drag and drop toolbars.
 - Visual PCB packaging tool.
 - Improved route editing.
 - Point and click DRC report.
 - Multiple design rules (per net).
 - Multiple undo/redo.
- ### Mixed Mode SPICE Circuit Simulation

 - Berkeley SPICE3F5 simulator with custom extensions for true mixed mode and interactive simulation.
 - 6 virtual instruments and 14 graph based analysis types.
 - 6000 models including TTL, CMOS and PLD digital parts.
 - Fully compatible with manufacturers' SPICE models.

- ### Proteus VSM - Co-simulation and debugging for popular Micro-controllers
- Supports PIC, AVR, 8051, HC11 and ARM micro-controllers.
 - Co-simulate target firmware with your hardware design.
 - Includes interactive peripheral models for LED and LCD displays, switches, keypads, virtual terminal and much, much more.
 - Provides source level debugging for popular compilers and assemblers from Crownhill, IAR, Keil, and others.

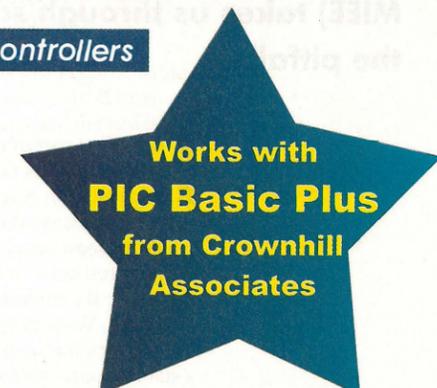

labcenter
Electronics
53-55 Main Street, Grassington. BD23 5AA

Tel: 01756 753440
Fax: 01756 752857
Contact us for
Free Demo CD

www.labcenter.co.uk
info@labcenter.co.uk

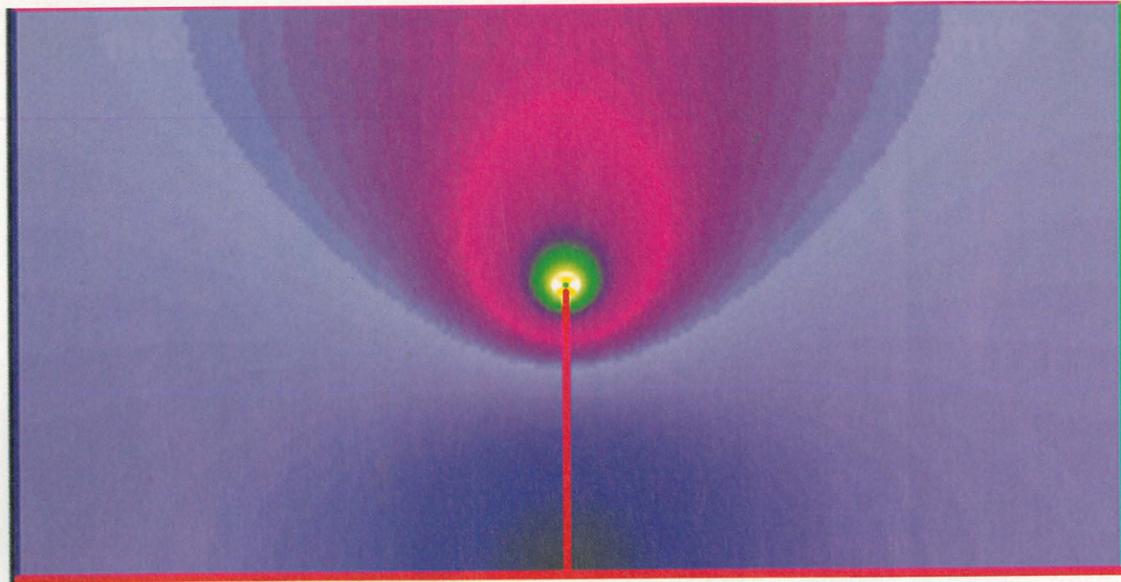


Fig. 1. Gradient plot of a plunge cut.

Reducing the stress in planar resistors

A well-designed resistor should have a flow pattern that is smooth and gradual. And choosing which track pattern would be most suitable for high stability resistors is also very important. Leslie Green (CEng MIEE) takes us through some of the pitfalls

In the first part of this article, the measure 'stress ratio' was introduced to give a quantitative rule for choosing which track pattern would be most suitable for high stability resistors. In this last part of the article the subject of trimming is discussed. Without careful trimming, all the work that went into designing a stable resistor pattern would be wasted; the trimming range is

required to be so great that it has a strong influence on the final stress ratio in the trimmed resistor.

The stress ratio is so important to this discussion that it is repeated again below:

$$\text{Stress Ratio} = \frac{\text{Peak Electric Field Strength}}{\text{Mean Active Field Strength}}$$

Regions in the distribution which have a field strength of less than 5% of the peak field strength are not taken into account when calculating the mean field strength, hence the term 'mean active field strength'.

Trimming

The problem with the resistor design so far is one of accuracy. It is very difficult to control the material of the film and its thickness accurately. Without some form of trimming the resistor would typically have a tolerance of around $\pm 19\%$. Given that trimming techniques consist of making cuts in the film, it is more natural to express this as a one sided tolerance of the form $+0\% -30\%$. The resistor is then trimmed up to the desired value.

You might think that there is an error in the above paragraph because from $\pm 19\%$ you might have expected to go to $+0\% -38\%$. The answer is that large percentages don't behave in a nice additive way.

Trimming is of major importance to manufacturers and users alike; it makes the difference between a good, stable resistor, with excellent voltage withstand properties, and a poor resistor not having these qualities.

Trimming Techniques

The best possible way to trim a resistor is to uniformly thin down the film. Remember that the resistance of the film is inversely proportional to its thickness. Unfortunately this is not as easy to achieve in practice, as it is to consider theoretically. Possible techniques include surface abrasion, wet etching or gaseous-phase dry etching. These are all difficult and expensive processes, particularly when you consider that a *dynamic trim* is the optimum method. By dynamic trim I mean that the resistor is being measured whilst it is being

trimmed. Otherwise you can imagine having to guess how long to leave the resistor in the etching tank to achieve the desired amount of trimming. Amongst these three trimming techniques, as far as I know, only dry etching is currently being used commercially.

And now we go from the very best techniques to one of the worst. One of the worst ways to trim a resistor is to put a laser cut partly through the middle, perpendicular to the current flow. This is shown in Fig. 1.

With electrodes on either side this rectangular element we should have a resistance of two squares. By cutting half way through it at the middle, the resistance is increased to 2.454 squares. This is horrible in terms of the peak electric field intensity, as the gradient field plot of Fig. 1 shows. The stress ratio is 7.09.

The straight cut at right angles to the current flow is known as a plunge, a plunge cut or a P-cut. It is not only lousy in terms of the resulting stress ratio. It is also difficult to get accurate trimming, because the percentage resistance change per micron of cut length increases as you cut further into the film.

Laser Cutting

Laser trimming of resistive films is a detailed technology in its own right. The laser is not a continuous beam, as you might have expected, but is a series of short bursts of intense energy at a low duty cycle.

Each short pulse evaporates the material in a small circular region, but the edges of the 'cut' are not distinct. The laser beam has a finite focus in terms of its intensity, so that there is a small region around the edge of the hole where the resistive material has been overheated but not evaporated.

As you can imagine, this region is not an ideal place for high current densities. It is also more likely to drift in resistance value, and if it is contributing more than its fair share of resistance to the overall resistance, then the resistor will not be as stable as it should be.

To get a cut line in the resistor, the beam is stepped to a new position, designed to overlap the previous position by as much as 90%. This gives a clean cut, also called a *kerf*, in the film. Another problem associated with this cut is micro-fractures¹. The resistive material is being heated sufficiently to evaporate it; although only a small amount of material is

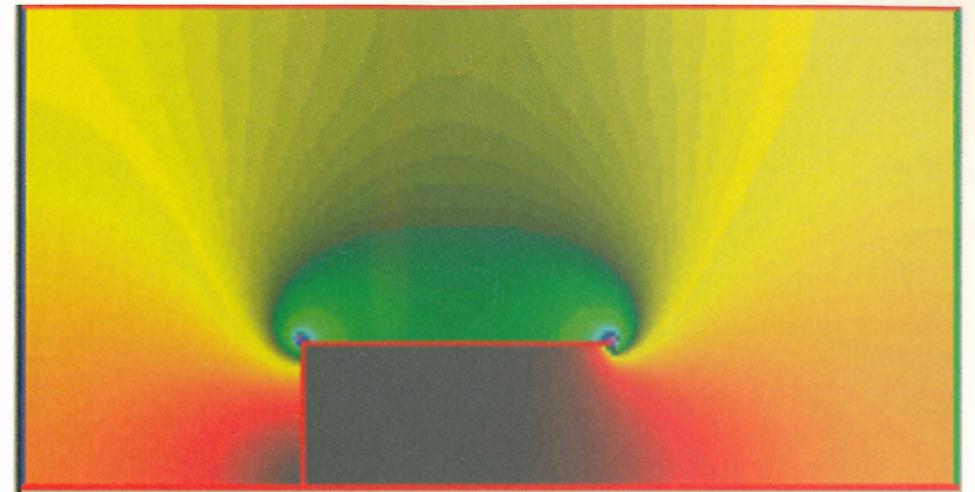


Fig. 2. Gradient field plot of an L-cut.

being removed, the surrounding area still gets heated significantly. This results in micro-fractures spreading away from the lased path. These fractures will spread with time and are one cause of the resistance increasing after the trimming operation.

For this reason the manufacturer has to use predictive trimming to set the value lower than the final required value, so that the resistor will drift up to the correct value a few tens of hours after the trimming is complete.

Another problem with the laser trimming technique is that a narrow laser cut in a relatively large sheet of resistive material allows significant distributed capacitance across the resistor². When used in an attenuator, such a resistor cannot be compensated to give a response that is flat to within a few percent.

Symmetry

It is evident from the previous plot that the field is mirror symmetric about the central cut. This symmetry is useful in terms of the accuracy of the finite element analysis. Because of the symmetry, it is actually only necessary to simulate half of the resistor. In this way there are twice as many simulation elements used in each direction, giving 4x the resolution in terms of the number of elements.

It is a general principle of any sort of computer simulation to take advantage of symmetry whenever possible, to either improve accuracy or reduce the simulation time. Unfortunately the L-cut of Fig. 2, which is used because it is easier to get a fine trim than with the P-cut, wrecks the symmetry. However,

throughout this article I have not made use of any available symmetry, in order to make the resistor designs easier to understand.

The resistance is increased by taking the cut parallel with the current flow, forming an L shape. This pattern has a resistance of 2.45 squares and a stress ratio of 3.48. The L-cut therefore gives a considerably better stress ratio for the same resistance as the P-cut. The only possible drawback is that the length of the cut is longer.

Now the cut on the film has been shown as being very narrow. This would apply to a laser cut, typically around 25µm, on a relatively large thick film resistor. On a resistor of 0603 size, the simulated cut would appear considerably wider. This would reduce the distributed capacitance and the field stress ratio.

For a larger thick film resistor another method is to use an air abrasion cut. This is wider than a laser cut and therefore reduces the stress ratio and the distributed capacitance; the penalty is increased cost because the machine is slower.

Obviously what we would like to do is to remove whole strips of the resistive material parallel to the current flow. This just is not feasible with a laser because the trim time would be enormous and the resistor would overheat. Clearly, since the length of cut determines the trim time and therefore the trim cost, this has to be balanced against the achievable accuracy and stress ratio achieved.

The User's Problem

You may not be designing the resistor, but you do need to understand what can happen in routine production. If you approve

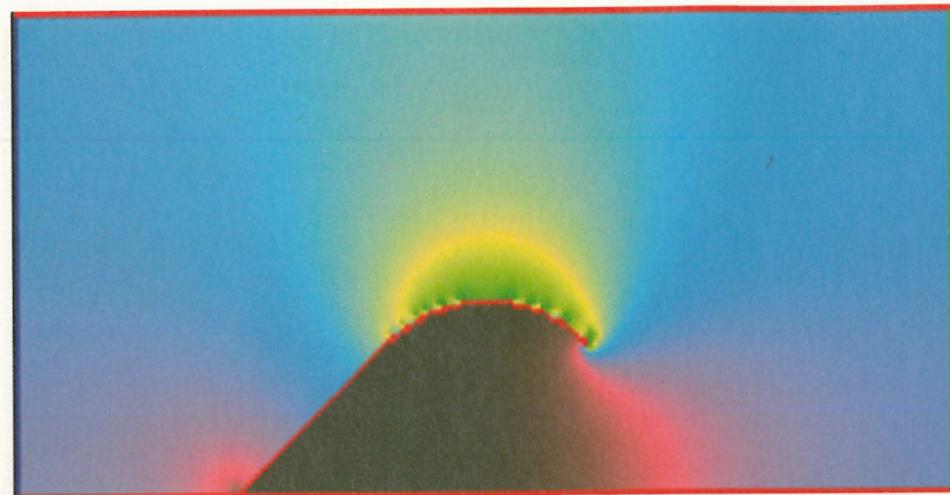


Fig. 3. Above gradient plot of a lazy-J cut.


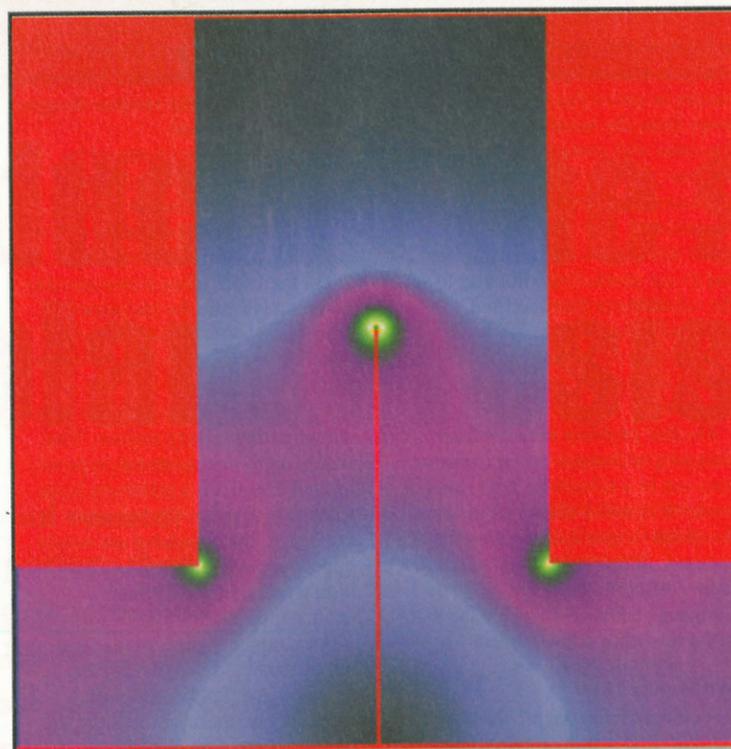


Fig. 4. Gradient plot of a top hat pattern. The orange area is the (insulating) substrate.

Fig. 5. Below gradient plot of a serpentine trim.

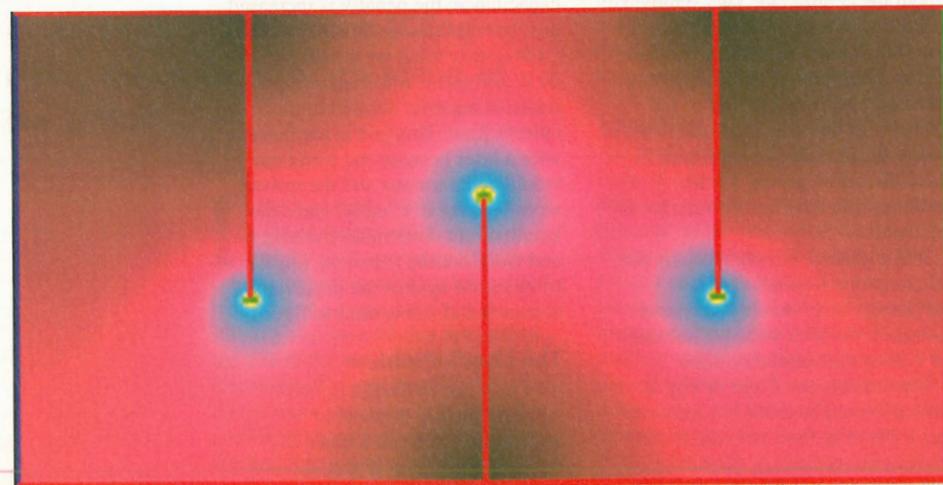

the design of custom resistors based on one sample batch, you can get caught out. Suppose the prototype batch happened to have high sheet resistivity. This would mean that the resistors would not need to be heavily trimmed. Thus any distributed capacitance effects and voltage breakdown effects would not necessarily be evident. Then, when you are in routine production, you get a batch where the sheet resistivity is low and all the nasty problems surface. This is why a user would need to consider what the manufacturer was doing in the design of the resistor.

Other Cuts

The L-cut can be enhanced by a P-cut at the 'open' end. When the plunge does not intersect with the L, a fine trim is achieved and the stray capacitance across the cuts is reduced.

If the plunge intersects the L, the path becomes continuous; a section of resistive material is isolated and it becomes a box cut.

Looking at the stress patterns on the P-cut and the L-cut, it is clear that all the problems come at the sharp corners. Looking back in this article at how the stress in the square corner problem was solved, a new cut is suggested. This consists of a sloping line which ends in a curved path. We could call this new cut a lazy-J as shown in Fig. 3.

The resistance is 2.52 squares and the stress ratio is 2.59. This makes it better than the L-cut. To get a finer trim, a sloping line should be cut up from the outside towards the open end of the arc. If this cut were continued, the shape of the cut would be a mirror symmetrical round-topped triangle. The fine trim cut also helps to reduce capacitance across the cuts, by reducing the potential difference across them.

Dynamic Circuit Trimming

The previous trimming techniques have been to get the final resistor to a predetermined value. Another possibility is to trim a circuit to a defined operating point by adjusting a resistor appropriately. This might be done for a hybrid circuit, for example, where it would be unacceptable to use a pot.

Because we are trying to emulate the range of a pot, the trimming range of the resistor needs to be considerably increased. In this case the top hat and serpentine cut can be used.

Figure 4 is one form of 'top hat' trim; it is good for making larger resistance changes, but it suffers badly from the electric stress problem, with a stress ratio of 6.16 in this simulation. Another method of getting greatly increased resistance is the serpentine trim of Fig. 5. This is just a series of interlocked plunge cuts.

This example has a resistance of 4.75 squares, which is a considerable 'trim' from the starting value of 2 squares. Again the stress ratio is very poor at 7.22. A better method is to use a lazy-J serpentine cut, shown in Fig. 6.

Figure 6 has a resistance of 5.30 squares and a stress ratio of 3.75. This new cutting pattern is therefore considerably better than the old serpentine cut. The top hat pattern is considerably more difficult to improve. First the basic shape of the corners is changed by pushing them inwards, as was done earlier on the single corner section. Then the top of the cut needs to be made circular as shown in Fig. 7.

This gives a resistance of 7.24 squares with a stress ratio of 3.45. The circular cut on the end of the plunge needs some explanation. This is not as infeasible as it might at first appear. Once the plunge is past the 'brim' of the top-hat, the change of resistance with cut depth is easily predictable. The fringing part of the field is relatively constant because the height of the hat can be made much larger than the cut depth.

It is therefore also true that the circular artefact on the end will have a relatively constant effect on the resistance and so it is possible to predict when to start the circular part of the cut. A fine trim can be done by a P-cut into the side of the hat, some distance above the circular cut.

Link Cutting

An even better way of getting large trims without affecting the stability of the resistor is to use link cutting. In one method the resistive film is used to form short links that bypass larger loops or ladders. When the link is cut, the current has to pass through the longer loop, thereby increasing the resistance.

These methods are very prone to the problems of stress in corners and can in fact be enhanced by the corner smoothing techniques mentioned earlier.

The key advantage of these link cutting methods is that the resistive

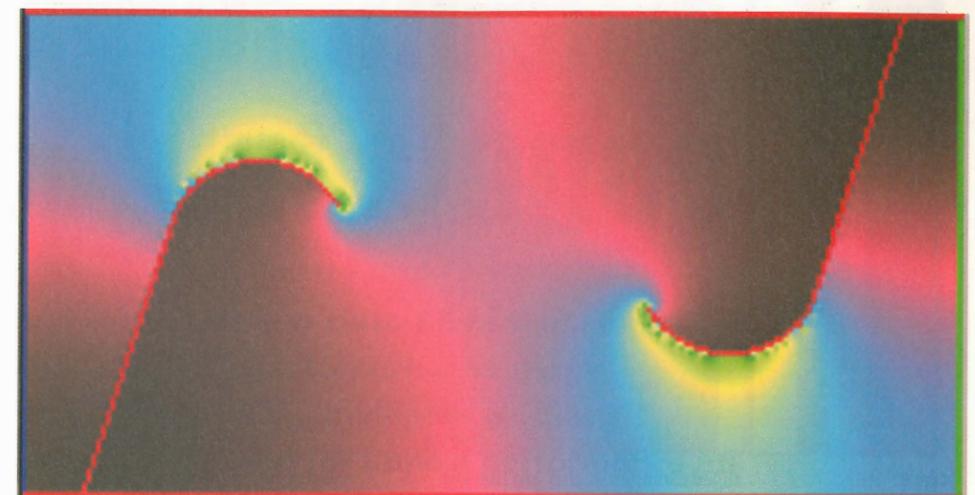


Fig. 6. Gradient plot of an improved trim method, a lazy-J serpentine trim.

film is completely cut away. Thus the resistive material which has been overheated around the edge of the cut is no longer used to carry current.

Another method to overcome the trimming problem is to have strips of conductive material under the resistive bar, following the equipotential lines as shown in Fig. 8. These conductive strips can be connected to each other with laser cuttable strips and the resulting pattern will have a stress ratio approaching 1.

Notice that this is an equipotential plot; the gradient plot would show nothing because the gradient is the same throughout. The capacitance of the bars will not be as significant as

you might at first imagine, simply because there is very little potential difference between them.

Conclusion

There are many factors that affect the stability of a planar resistor. The initial shape of the resistor is important in order to give a low stress ratio and therefore the optimum performance from a given technology. Trimming a resistor with a laser is problematic. As far as the film integrity is concerned, the laser cut should be as narrow as possible. This minimises the heating of the film and therefore reduces the micro-cracks that form around the cut. The

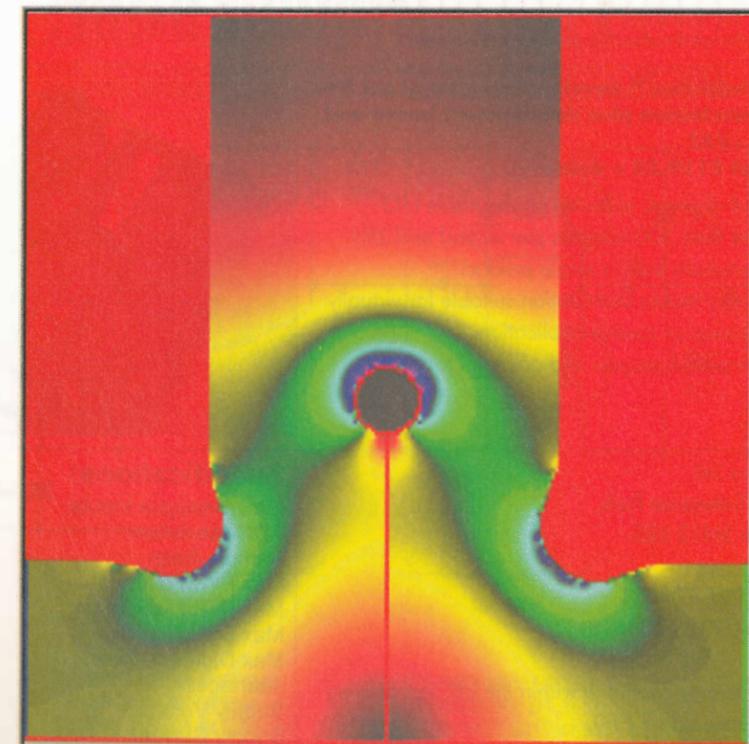


Fig. 7. Gradient plot of an improved top-hat trim.

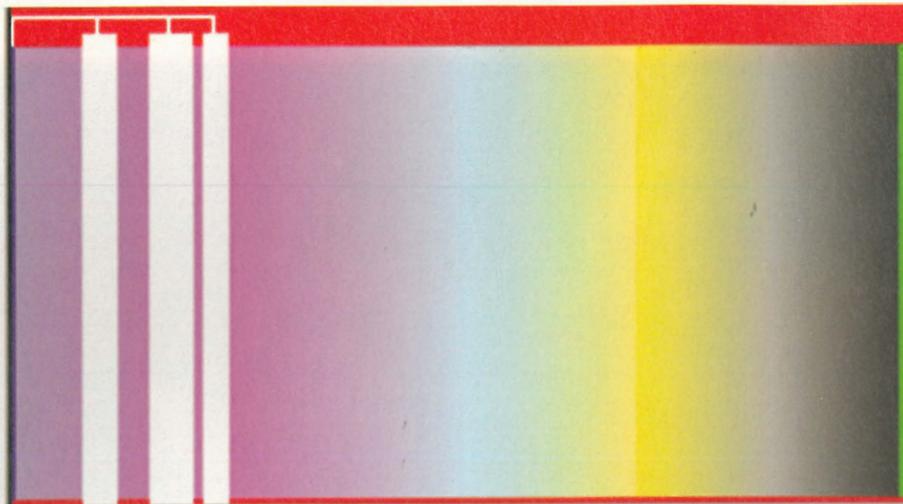


Fig. 8. Equipotential plot of the ultimate in stress-free trimmed resistors. The white strips are conductive material either over or under the resistive film.

disadvantages of this are that the parasitic capacitance across the cut is higher and the stress ratio is worse. It is very easy for the micro-fracture problem to be an order of magnitude, or more, larger than the effect due to the stress ratio. Thus the stress ratio has greater importance when the micro-fracture problem is dealt with. The micro-fracture problem and the overheating of the film around the edges of the laser cut are both dealt with by 100% cuts of individual current paths. This allows the benefits of the stress ratio improvements to be realised. It is not possible to verify the performance of a custom designed

resistor based on a prototype that happens to have high sheet resistivity. The fact that it has not been heavily trimmed means that its voltage withstand capability, long term stability, 1/f noise and AC performance will be superior to a future part which is made from a lower resistivity material. A possible solution to this problem is to get the manufacturer to trim such a part up to the maximum possible adjustment range. This will make the resistor the wrong value by up to 30%, but may give a more representative sample in terms of the adverse effects mentioned previously. The 2-dimensional field patterns in

planar films are very beautiful to look at when seen in full colour. Unfortunately the gradient patterns are at their most beautiful when the stress ratio is the worst. Thus a truly beautiful resistor design has a very plain looking gradient plot. A well-designed resistor has a flow pattern that is smooth and gradual. Sharp lines and angles need to be avoided. If you look at the equipotential plot, you can see where the current is flowing; it always flows at right angles to the equipotential lines. This is an area where artistic ability can improve electrical performance. Thus a beautiful resistor has technical as well as artistic merit. Interested readers can download demo field plotting software from www.logbook.freemove.co.uk

References

1. Mechanism and Control of Post-Trim Drift of Laser-Trimmed Thick-Film Resistors by J.Shah & L.Berrin: IEEE Transactions on Components, Hybrids and Manufacturing Technology. Vol. CHMT-1, No.2, June 1978, pp 130-136.
2. Parasitic Capacitance Effects of Planar Resistors by S.Demurie & G.DeMey: IEEE Transactions on Components, Hybrids and Manufacturing Technology. Vol. 12, no.3, September 1989, pp 348-351.

Electronics World reader offer:

Save £20 on a DataStation™ development kit and get free delivery!* Get a DataStation plus development board and cable for just £99 +VAT (Normally priced at £119.50 + delivery).

DataStation™ is a 16 channel, software configurable I/O module offering more than 500 samples per second and 391 different I/O configurations from a single product. This unrivalled flexibility makes DataStation suitable for virtually any PC driven monitoring or control application. Please send your completed coupon and payment to:


EW Reader Offer

Observant Electronics Ltd.
Unit F2b, Avonside Enterprise Park,
Melksham, Wiltshire SN12 8BS

Alternatively call 01225 704631
or fax your order to 01225 708618.

*Note: free delivery is only available within the UK. For delivery outside of the UK please add £2.50.

Offer valid until 28th November 2003

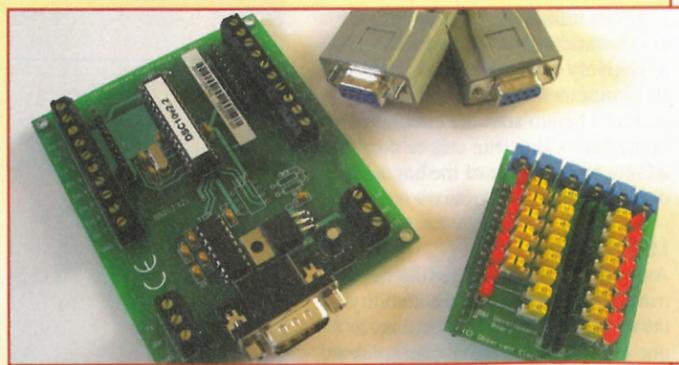

Specifications:

Max Analogue Inputs:	6
ADC resolution:	8 or 12-bit selectable
Sample Rate:	> 500 samples per second
Max PWM outputs:	2
Max PWM resolution:	10 bits
Max Digital inputs:	16
Max Digital outputs:	16
Interface:	RS-232
Supply Voltage:	7 to 35v dc
Supply Current:	15mA typical
Dimensions:	99 x 82 mm

Autobias for mosfet audio output stages

It's said that biasing vertical d-mosfets in a class-AB output stage is less critical than biasing their bipolar counterparts. So many designers are content with the classical V_{BE} multiplier as bias generator. However, the accuracy needed for utmost performance (in terms of cross-over distortion and quiescent dissipation), cannot be provided by such a circuit, even when it is thermally coupled to one of the output devices. Edmond Stuart explains

Several factors may contribute to the lack of accuracy:

- 1) Mismatch between relative temperature coefficients of mosfets and bjts as consequence of the variability of the gate threshold voltage as well as the temperature coefficient of V_{GS} .
- 2) Thermal delay and attenuation of the coupling between output device and sensing element.
- 3) Drivers - if included - that operate at a different temperature.
- 4) Long-term drift of threshold voltages as a result of ageing¹.
- 5) Errors in adjusting the bias level

for each individual amplifier.

So it seems natural to replace the V_{BE} multiplier - which in fact provides a kind of error feed forward² - by a control loop based on feedback of the bias current itself. In the past, several attempts has been undertaken in this direction, but none of them seem to me suitable for high-end applications, as they are intrusive also on other parts of the amplifier. This could raise distortion^{3,4}, complicate HF compensation^{5,6} or be incompatible^{3,4,5} with a complementary source follower arrangement (which I prefer), or


could be too complex⁷. Nevertheless, reference 5, ingenious in its own right, inspired me to a re-design that overcomes these shortcomings.

The new design comprises three sections: a bias current sensor, an isolator and an integrator. Each of them will be discussed below in detail.

Bias sensor

The bias sensor's purpose is to detect any deviation from the nominal bias level without being influenced by the current distribution over the output transistors, i.e. independently of the

Fig. 1. Circuit diagram of the autobias generator connected to a typical mosfet output stage

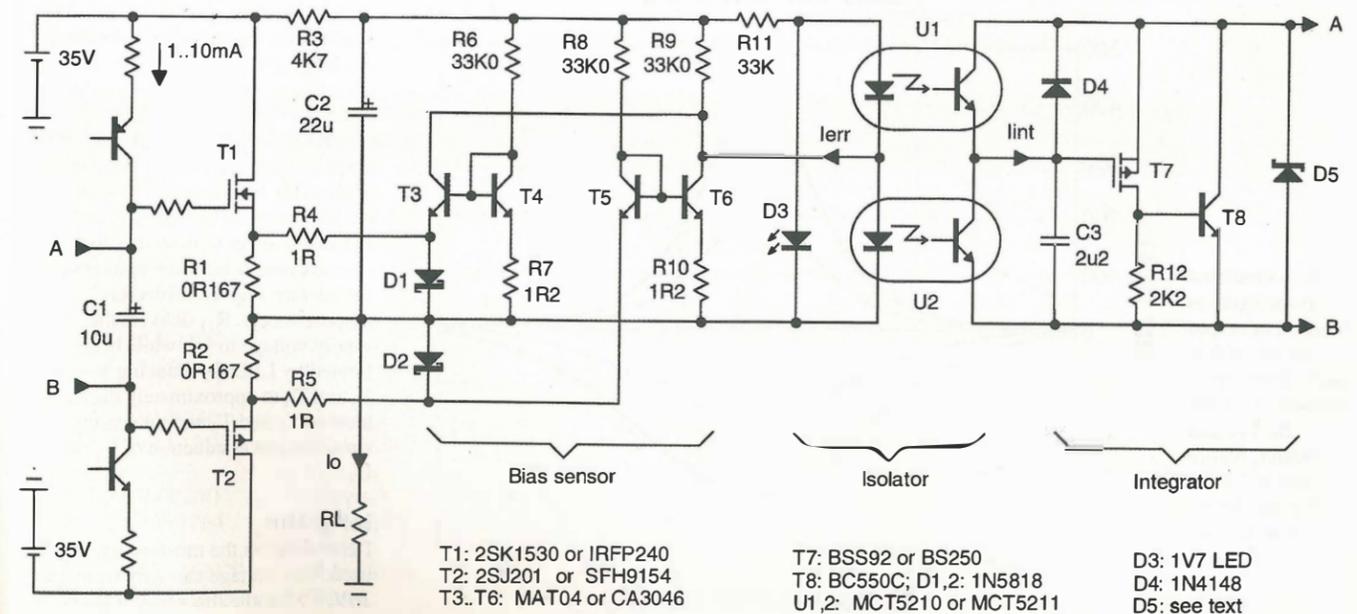

T1: 2SK1530 or IRFP240
T2: 2SJ201 or SFH9154
T3..T6: MAT04 or CA3046

T7: BSS92 or BS250
T8: BC550C; D1,2: 1N5818
U1,2: MCT5210 or MCT5211

D3: 1V7 LED
D4: 1N4148
D5: see text

current delivered to the load (R_L). This is accomplished by sensing the voltages across the source resistors of the output stage and passing them to a non-linear network, comprising two current mirrors (transistor pairs $T_{3,4}$ and $T_{5,6}$ respectively). Two equal reference currents are supplied to the inputs of the mirrors via R_6 and R_8 . Since the voltage across each source resistor adds an off-set to V_{BE} of T_3 and T_6 , the currents reflected by them will be lower than the reference.

Under quiescent conditions, this offset is such that each mirror reflects only 50% of the reference current. As dictated by the laws of physics, this condition is met if the offset voltage is 18mV (at room temperature). Together with R_1 and R_2 , this 18mV defines the quiescent current of the output stage (e.g. 100mA if

$R_1=R_2=0.18\Omega$). To maintain this condition the reflected currents are summed together and subtracted from a third reference current supplied by R_9 . The resulting difference, I_{ERR} , tells us whether the output stage is under, correct or over biased, thus I_{ERR} can be used as a feedback signal, Fig. 2.

Next, what happens in the presence of small or medium signals? This is illustrated by the middle curve of Fig. 3. It shows the relationship between error signal and output current at the nominal bias level. As one can see, the crux is that the error signal stays very close to zero. Apparently, the non-linear behaviour of the mosfets, in particular in their weak and moderate inversion region, matches the characteristics of the bias sensor quite well. The other curves show the error signal if the output stage is forced to

an under - or over-biased state. Beyond output currents of ca. 0.6A the error signal is pinched off. This looks like a disadvantage, but it turned out to be beneficial, as explained below.

Finally, what happens in the presence of large signals? Suppose T_1 carries a large current and T_2 is turned off. In this case the reflected current in T_3 is zero, while in T_6 it is 100%. Summed together and subtracted from the third reference, the resultant error signal is again zero. This is exactly what we want, as an output stage operating in class B provides no information about the quiescent current, thus the error signal has been pinched off in order to preserve the charge of the integrator's capacitor (C_3).

Since music has a high peak/average ratio - some 20dB - the average signal level - even at maximum volume - is well within the capture range of the bias sensor. Sine waves at full power give no trouble either, as the relative time traversing the capture region is long enough to let the control loop do its work. However, a large square wave pushes the output stage continuously in class B and no error signal is produced at all, leaving the integrator in an undefined state.

Isolator

To avoid any adverse interaction between common mode and differential signals at the gates (node A and B), an isolator has to be inserted somewhere inside the servo loop. Putting it between bias sensor and integrator greatly simplifies the circuit, as the integrator can now simply use the bias voltage as supply. Given the bipolar nature of the error signal, two opto-couplers (U_1, U_2) are needed, one for charging, the other for discharging C_3 . They are specified for operating at low currents (<1mA). Apart from their primary task (isolation), they serve one more purpose: masking the tiny deviations of the error signal, as can be seen at the middle curve of Fig. 3. The reduced transfer ratio at very low currents from which any opto-coupler suffers (see Fig. 4), meets this purpose nicely. R_{11} delivers the supply voltage to U_1 , while being limited by LED D_3 reducing V_{CE} of T_3 and T_6 to approximately the same level as T_4 and T_5 and preventing simultaneous conduction of U_1 and U_2 .

Integrator

Depending on the mosfets actually used, bias voltage can vary from 2 to 10V. To handle this range it leads

almost automatically to the kind of topology, as shown in Fig. 1. In spite of its simplicity, this integrator, or to be more precise - integrating shunt regulator, exhibits a dynamic output impedance that is low enough (<2 Ω) to cope with AC currents from the driver stage. In order to exclude interaction at AF, integrator capacitor C_3 is rated such that the unity gain frequency of the servo loop falls below the audio spectrum, somewhere between 1 and 10Hz, depending on the transfer ratio of the opto-couplers. D_4 discharges C_3 during switch off and protects the gate of T_7 . For reliable operation, low leakage at the integrator input is essential, so D_4 should be protected from light. Zener diode D_5 is rated at the maximum expected bias voltage plus a small margin and should be adapted to fit a particular design. If some component fails or if nasty test signals have been applied, this diode protects the output stage against excessive common mode currents.

Accuracy

The bias level is very sensitive to mismatches of the transistor pairs and reference currents. Base-emitter voltages T_3, T_4, T_5 and T_6 respectively should match at least within 0.5mV. A quad transistor like a MAT04 or CA3086, selected on low V_{os} , meets this requirement. For the same reason, R_6, R_8 and R_9 should match at least within 0.5% as well as the equivalent emitter series resistors; hence R_7 and R_{10} are rated slightly higher than R_4 and R_5 . Since a MAT04 is equipped with small reverse connected diodes between base and emitter, Schottky diodes D_1, D_2 are added to protect them.

Now we come to a moot point: the voltage of 18mV across R_1 and R_2

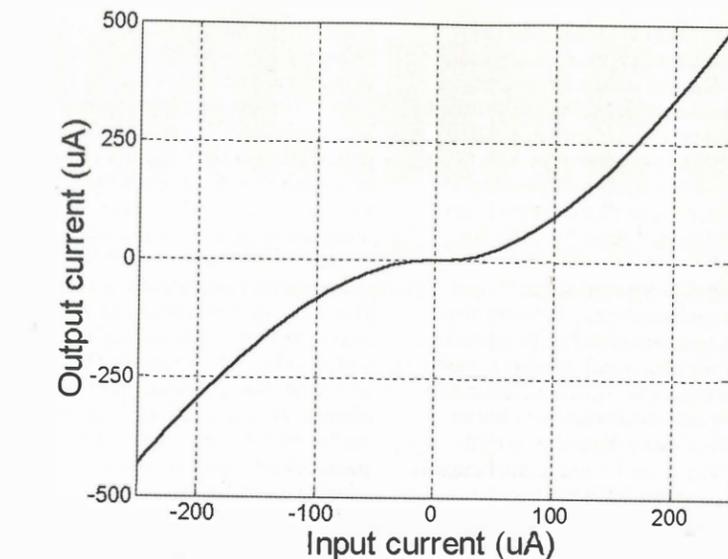


Fig. 4. Transfer function of the isolator.

which all relies upon, varies linearly with the absolute ambient temperature*. Of course, it varies much less than the junction temperature of the output devices and thermal runaway is precluded, but still it is not constant. It is not yet clear to me whether this should be regarded as flaw or feature, as one could argue that the decreased transconductance of mosfets at elevated temperatures just needs an increased bias level. Interestingly, a bias control IC from Linear Technology⁶ shows the same temperature dependence, which could not be explained by an inherent shortcoming of the basic circuit. So I concluded that this property has been added on purpose. Asking why, Linear Technology was unable to give a satisfactory explanation. If anybody could shed light on this

* $V_{BE} = V_T \ln 2$, where $V_T = kT/q$, the thermal voltage (25.86mV at 300K).

matter, please let me know.

Experimental results

To see if the circuit is generally applicable, I tested it on several combinations of mosfets, all capable of delivering 12 to 20A, but of different types and brands. To minimise temperature effects, measurements were done at a reduced supply voltage of 2x16V, the mosfets mounted on a large heatsink with forced air cooling and at a frequency of 1kHz. Static measurements were done at an even lower voltage, 2x7.5V. Since these were very time consuming, I have done this only in case 1 and 2.

In the first instance, dynamic behaviour of bias current was observed by means of an oscilloscope, but changes at various output levels were hardly visible and difficult to quantify, except in case 1, which showed an increase of 5% at maximum output power. Instead, I

Fig. 2. Simulated error signal as function of bias current ($I_{REF}=1mA$, $R_{1,2}=0.167\Omega$, $R_L=\infty$).


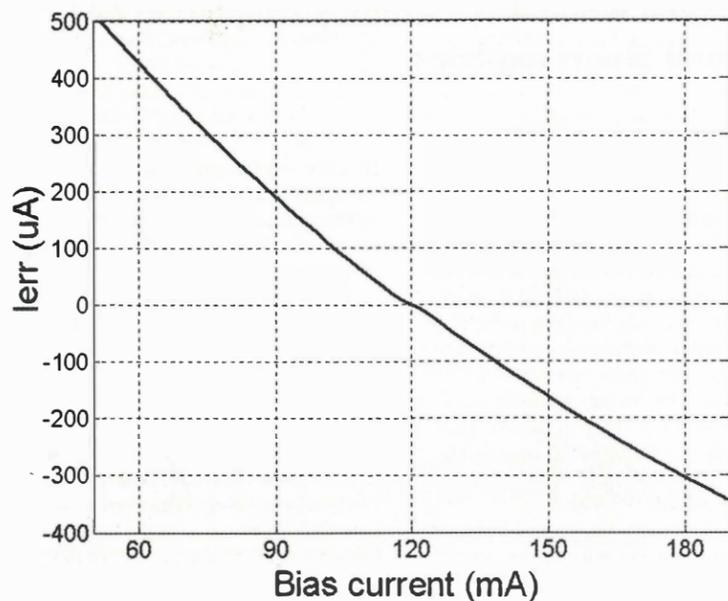


Fig. 3. Simulated error signal as function of output current at bias levels (from top to bottom) of 60, 90, 120, 150 and 180mA. Notice that at 120mA this signal stays close to zero.

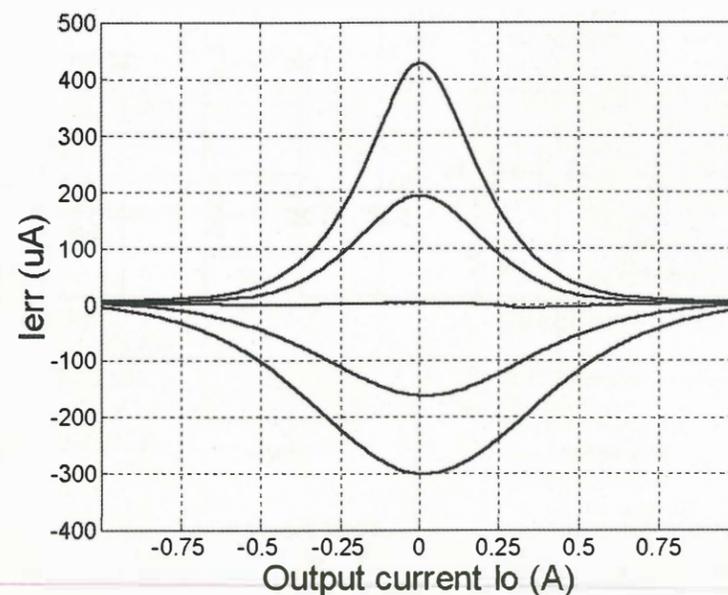

Ripple amplitude of the error signals measured at $V_O = 8V_{pp}$ and 1kHz as well as estimated ripple on bias voltage (V_{RPL}) at 20Hz.

Case	Type	Manufacturer	R_L (Ω)	I_{ERR} (μA_{eff})	I_{INT} (μA_{eff})	V_{RPL} (mV _{eff})
1	IRFP240	Int. Rectifier	4	15.9	3.3	12.9
	IRFP9240	Idem	∞	62.4	157.0	568
2	2SK1530	Toshiba	4	4.9	<0.1	<0.4
	2SJ201	Idem	∞	3.2	<0.1	<0.4
3	IRFP240	Intersil	4	14.2	1.3	4.7
	FQA12P20	Fairchild	∞	5.0	<0.1	<0.4
4	IRFP240	Intersil	4	7.2	0.2	0.8
	SFH9154	Fairchild	∞	5.6	<0.1	<0.4
5	FQA19N20	Fairchild	4	11.6	0.7	2.5
	FQA12P20	Idem	∞	5.1	<0.1	<0.4

The Electronics World Book Service offers access to our team of specialist publishing experts. We can order any book or CD-ROM currently in print from *War And Peace* to the *Reference Data for Engineers*. All books are delivered free of charge within the UK unless otherwise stated. Contact us at the numbers below:
 Telephone: **01737 812727** or **01737 812676**
 Fax: 01737 813526
 Email: salesteam@boffinbooks.demon.co.uk

HIGH SPEED DIGITAL DESIGN
 Howard W Johnson & Graham Martin
 Re-issue
 Focusing on the field of knowledge lying between digital and analog circuit theory, this text sets out to help engineers working with digital systems shorten their product development cycles and help fix their latest design problems. It covers signal reflection and crosstalk.
 820 pages ▲ HB
 Code PEAR 0 13 395724 1 **£44.99**

RF CIRCUIT DESIGN: THEORY & APPLICATIONS
 Reinhold Ludwig; Pavel Bretchko
 This practical guide introduces RF circuit design fundamentals while emphasizing a circuit based approach. It provides MATLAB routines to carry out simple transmission line computations and uses a PC-based commercial RF circuit simulation tool to demonstrate actual circuit behaviour.
 Oct 1999 ▲ 656 pages ▲ HB
 Code PEA 0 13 095323 7 **£35.99**

VERILOG DEVELOPER'S LIBRARY
 Bob Zeidman
 Verilog is one of the most used hardware description languages. This text contains a library of useful code for those users who do not want to recreate identical code for common tasks.
 Jul 1999 ▲ 450 pages ▲ PB
 Code PEA 0 13 081154 8 **£79.99**

PASSIVE COMPONENTS FOR CIRCUIT DESIGN
 Ian Sinclair
 Designed for technician engineers and anyone involved in circuit design, this text provides an introduction into a key area of analogue electronics. It covers all component types capable of power amplification, including: resistors, capacitors, transformers, solenoids and motors.
 Nov 2000 ▲ 301 pages ▲ PB
 Code H80 7506 4933 X **£23.50**

ELECTRONIC SERVICING AND REPAIRS
 Trevor Linsley
 Updates the previous text taking into account changes in the City and Guilds courses 2360 and 2240. Also features *hardware* topics, testing and fault diagnosis, PLCs and CAD software, and new chapters. Health and safety; electronic component recognition; electronic circuit assembly techniques; electronic semiconductor devices; electronic circuits in action; testing electronic circuits; digital electronics; electrical circle theory; electronic systems; communication systems; security systems; sensors and transducers.
 3rd edition ▲ Aug 2000 ▲ 261 pages
 Code HB 0 7506 5053 2 **£18.99**

DIGITAL LOGIC DESIGN
 Brian Holdsworth & Woods
 This undergraduate text on digital systems covers first and second year modules and HND units, and can also be used as a reference text in industry. Updated topics in the fourth edition include: EBCDIC, Grey code, practical applications of flip-flops, linear and shaft encoders and memory elements.
 4th edition ▲ Aug 2002 ▲ 448 pages
 Code HB 0 7506 4582 2 **£19.99**

NEWNES INTERFACING COMPANION: COMPUTERS, TRANSDUCERS, INSTRUMENTATION AND SIGNAL PROCESSING
 Tony Fischer-Cripps
 Provides the fundamentals of electronics, transducers, computer architecture and interfacing techniques needed to use a simple PC or PLC-based system for the collection of data previously only obtainable from expensive dedicated equipment.
 Aug 2002 ▲ 320 pages ▲ HB
 Code HB 0 7506 5720 0 **£24.99**

NEWNES RADIO AND RF ENGINEERING POCKET BOOK
 Steve Winder & Joseph J Carr
 With a mass of information and data for students, radio and telecommunications engineers, RF circuit designers, radio hobbyists and technicians, this guide covers all aspects of radio and communications engineering from low frequencies to microwaves, with an emphasis on mobile communications.
 3rd edition ▲ Jul 2002 ▲ 352 pages ▲ HB
 Code HB 0 7506 5608 5 **£16.99**

ELECTRONIC PROJECTS FROM THE NEXT DIMENSION: PARANORMAL EXPERIMENTS FOR HOBBYISTS
 Newton Braga
 A guide to making and using paranormal research electronics. It describes practical electronic circuits to be used in experiments involving instrumental transcommunication (ITC), the electronic voice phenomenon (VP), and paranormal experiments involving ESP, auras, and Kirlian photography. White and pink noise generators for use in instrumental transcommunication (ITC) experiments; Kirlian photography; plasma experiments; extrasensory perception testers; magnetic fields sensors.
 Nov 2000 ▲ 256 pages ▲ PB
 Code H80 7506 7305 2 **£28.50**

BASIC AC CIRCUITS
 Clay Rawlins
 A step-by-step approach to AC circuits for beginners, providing thorough coverage of theory and practice. The text provides individualized learning goals covering electronics concepts, terms and the mathematics required to understand AC circuit problems.
 2nd Edition ▲ Oct 2000 ▲ PB
 Code H80 7506 7173 4 **£34.50**

INTERFACING WITH C
 Mike James & Howard Hutchings
 An exploration of interfacing personal computers using C. An introduction to C; loops and data conversion; data acquisition using C; essential mathematics; convolution; digital filters; Fourier transforms; correlation; Kalman filters; data conversion; investigating the spectral and time-domain performance of z-transforms using computer-managed instruction; introducing audio signal processing using C; standard programming structures. Dewey: 005.71262
 2nd edition ▲ Dec 2000 ▲ 308pages
 Code HB 0 7506 4831 7 **£20.50**

SELF ON AUDIO
 Douglas Self
 This work offers a collection of *Electronics World* articles, including self-build projects. It aims to demystify amplifier design and establish empirical design techniques based on electronic design principles and experimental data.
 Jul 2000 ▲ 256 pages ▲ PB
 Code H80 7506 4765 5 **£28.50**

ROBOTICS, MECHATRONICS, AND ARTIFICIAL INTELLIGENCE: EXPERIMENTAL CIRCUIT BLOCKS FOR DESIGNERS
 Newton C Braga
 This work simplifies the process of finding basic circuits to perform simple tasks, such as how to control a DC or step motor, and provides instruction on creating moving robotic parts, such as an "eye" or "ear".
 Nov 2001 ▲ 317 pages ▲ PB
 Code HB 0 7506 7389 3 **£21.99**

EMBEDDED MICROPROCESSOR SYSTEMS: REAL WORLD DESIGN
 Stuart Ball
 Providing an introduction to the design of embedded microprocessor systems, this edition covers everything from the initial concept through to debugging the final result. It also includes material on DMA, interrupts and an emphasis throughout on the real-time nature of embedded systems.
 3rd edition ▲ Nov 2002 ▲ 368 pages ▲ PB
 Code HB 0 7506 7534 9 **£35.00**

POWER SUPPLY COOKBOOK
 Marty Brown
 Providing an easy-to-follow, step-by-step design framework for a wide variety of power supplies, including linear, switching and quasi-resonant switching. There is also discussion of design topics such as magnetics, feedback loop compensation design and EMI/RFI control in straightforward terms.
 2nd edition ▲ Jun 2001 ▲ 336 pages ▲ HB
 Code HB 0 7506 7329 X **£24.99**

MIXED-SIGNAL AND DSP DESIGN TECHNIQUES
 Walt Kester
 Mixed-signal processing implies the use of analogue and digital in the same system; this is a specialized type of signal processing that requires a high level of experience and training. This book focuses primarily on signal processing hardware - how it works, how to interface it, and design it.
 Oct 2002 ▲ 336 pages ▲ PB
 Code HB 0 7506 7611 6 **£39.99**

BUILD AND UPGRADE YOUR OWN PC
 Ian Sinclair
 This third edition of *Build and Upgrade Your Own PC* is based around building and upgrading to the very latest systems running processors with speeds over 2.0 Ghz and ultrafast buses. It also covers upgrading to Windows XP and Windows Me.
 3rd edition ▲ Jul 2002 ▲ 335 pages ▲ PB
 Code HB 0 7506 5758 B **£22.50**

PRACTICAL ELECTRONICS HANDBOOK
 Ian Sinclair
 A collection of all the key data, facts, practical guidance and circuit design basics needed by a spectrum of students, electronics enthusiasts, technicians and circuit designers. It provides explanations and practical guidance, and includes new sections on SHF techniques and intruder alarms.
 5th edition ▲ Feb 2000 ▲ 571 pages ▲ PB
 Code HB 0 7506 4585 7 **£16.99**

ANALOG CIRCUIT TECHNIQUES WITH DIGITAL INTERFACING
 Trevor Wilmshurst
 Aimed at junior undergraduates, this textbook offers comprehensive coverage of analogue electronic circuit design with two full chapters devoted to the use of SPICE in circuit simulations, programmes leading to Eng MSc Electronic conversion type courses.
 Mar 2001 ▲ 320 pages ▲ PB
 Code H80 7506 5094 X **£19.99**

ELECTRONICS FOR SERVICE ENGINEERS
 Joe Cieszynski & Dave Fox
 From simple mathematics and circuit theory to transmission theory and aeriols, this text provides the range of knowledge required to service electronic and electrical equipment. Questions and worked examples illustrate the concepts described in each chapter.
 Mar 1999 ▲ 294 pages ▲ PB
 Code H80 7506 3476 6 **£20.99**

UNDERSTANDING AUTOMOTIVE ELECTRONICS
 W B Ribbens
 Covering the most recent technological advances in operation and troubleshooting of electronic systems and components, including low-emission standards, on-board diagnostics and communications, digital instrumentation, and digital engine control. A practical text, suitable for the automotive technician, student, enthusiast, or professional who wants to upgrade his or her background in electronic systems found in the automotive.
 6th ed. Dec 2002
 Code HB 0 7506 7599 3 **£24.99**

DESIGNING EMBEDDED INTERNET DEVICES
 Brian DeMuth & Eisenreich
 This guide to designing internet access and communications capabilities into embedded systems takes an integrated hardware/software approach, using the Java programming language and industry-standard microcontrollers. The CD-ROM has Java source code and a version of the text.
 Aug 2002 ▲ 320 pages
 PB & CD-ROM
 Code HB 1 878707 98 1 **£35.00**

FABRICATING PRINTED CIRCUIT BOARDS
 Jon Varteresian
 Engineers are often faced with the need for small quantities of a certain board design for construction of a small number of devices. This book describes the process of making a printed circuit board, from the conversion of a schematic diagram into a board layout to the making of the board itself.
 Jul 2002 ▲ 251 pages ▲ PB
 Code HB 1 878707 50 7 **£21.99**

REFERENCE DATA FOR ENGINEERS: RADIO, ELECTRONICS, COMPUTERS AND COMMUNICATIONS
 Mac E Van Valkenburg
 Written by professionals for professionals, this title is a complete reference for engineers, covering a broad range of topics. As well as addressing radio technology data, this reference volume covers digital electronics, computers and communications.
 9th edition ▲ Aug 2001 ▲ 1568 pages
 HB & CD-ROM
 Code H80 7506 7291 9 **£90.00**

PRACTICAL RF HANDBOOK
 Ian Hickman
 A hands-on-guide for engineers, technicians, students and enthusiasts working in RF design, this comprehensive text covers all the key topics in RF, including: analogue design principles; transmission lines; transformers; couplers; amplifiers; oscillators; modulation; and antennas.
 3rd edition ▲ Feb 2002 ▲ 289 pages
 150 line drawings ▲ PB
 Code HB 0 7506 5369 8 **£19.99**

NEWNES TELEVISION AND VIDEO ENGINEER'S POCKET BOOK
 Eugene Trundle
 This text provides a pocket tool for service engineers. It presents a range of essential information in a compact form, covering television reception, satellite and cable television, video recorders, colour camera technology, teletext and fault-finding.
 3rd edition ▲ Oct 1999 ▲ 512 pages ▲ HB
 Code HB 0 7506 4194 0 **£17.99**

PIC IN PRACTICE: AN INTRODUCTION TO THE PIC MICROCONTROLLER
 David W Smith
 An exploration of the PIC microcontroller, designed to be used at a variety of levels. It introduces the reader to the range of tasks the PIC can perform and makes use of readily available components. The PIC used in the examples is the re-programmable EEPROM 16C84/16F84.
 Apr 2002 ▲ 261 pages ▲ PB
 Code HB 0 7506 4812 0 **£14.99**

If you are ordering by credit card, need further information, or would like to use our search facilities call **01737 812727** Fax **01737 813526**. The order/helpdesk open from 9am to 5pm, or leave your order on our out of hours answerline or email us at salesteam@boffinbooks.demon.co.uk
 When placing orders please quote
 • Name • Address (home & delivery) • Daytime telephone number • Debit/Credit card number • Expiry date
 • Details of order. Please note that prices may change, but are correct at time of going to press.
 Boffin Books Ltd., 24 Walton Street,
 (Walton-on-the-Hill, Tadworth, Surrey KT20 7RT, UK

ELECTRONICS WORLD ORDER FORM

Please order or search the following:

Code	Description	Qty	Price
POSTAGE & PACKING FREE IN THE UK*			TOTAL
Name	Daytime Tel		
Address	Postcode		
Delivery address (if different)	Postcode		
I enclose a cheque/postal order value £ payable to 'Boffin Books Ltd'			
Please debit my Access/Visa/Switch/Delta card Issue number (Switch only)			
Card Number	Expiry Date		
Signed	email:salesteam@boffinbooks.demon.co.uk		

*Postage charges outside the UK available upon request or email to salesteam@boffinbooks.demon.co.uk
 Send order form to: **Boffin Books Ltd., 24 Walton Street, Walton-on-the-Hill, Tadworth, Surrey KT20 7RT, UK**

An introduction to network analysis

Computerised circuit simulators are useful tools, but they are not infallible. Here, John Ellis provides an insight into how network analysis works, with the aim of giving you a better idea of how to assess the usefulness of the results of circuit simulations. In the second part of this article, John will also outline how you can produce your own basic simulation tools.

Today, circuit simulation is such an integral part of electronic design – whether for integrated circuits, discrete designs or even printed circuit boards – that the underlying principles are not often considered. This is an indication that the design process, and technology, is commercial, competitive and industrialised where the principles have become secondary to designing new circuits or products that put transistors to use.

Specialist software has become available to enable circuits with thousands or millions of transistors to be simulated with relative ease. The price that is paid for this commercialisation is that the simulation software also has a price tag. To an extent, only companies can afford to pay for them.

Yet the principles of simulation are quite straightforward. It is possible to write programs on a PC to address some of the simpler tasks without too much difficulty – particularly for small-signal analyses. Transient analyses over large voltage swings causing saturation are more difficult.

The SPICE – Simulation Program with Integrated Circuit Emphasis – program¹ is perhaps the most widely used simulator. Although a public domain program, Berkeley lists charges of \$150 for version 2 listings and \$250 for version 3 on their web site – at least as of May 2000. Commercial versions make it easier to use, but are similarly, or more expensively, priced.

This set of articles introduces the simulation task from circuit specification to methods for solving the equations, and illustrates the solutions for some example circuits. As such the principles described are not new: the purpose of this article is to provide an overview of the simulation process.

Furthermore, the program methods here are, it has to be emphasised, quite basic and do not equate to a full commercial simulator. A commercial simulator will have a graphical user interface, or GUI, accepting a circuit diagram for the input which is drawn more or less as normal. With the simulator described here, you will have to enter the equations for the nodes manually.

A commercial simulator will have robust algorithms which will deal with extreme non-linear behaviour in transistors. For example, while the basic exponential equations can be handled without much difficulty, in saturation, the gain rapidly collapses, making the collector-base junction become far more significant than in the

normal active mode. The algorithms here are somewhat basic, but respond to short time-stepping.

In this article, I have limited discussions to resistors, capacitors and the well-known SPICE -type of model of the bipolar transistor. Bipolars form the bulk of most discrete circuit designs, but MOSFETs are dominating the transistor and IC market in many areas and perhaps should be considered in a separate article.

The bipolar SPICE model has served very well for many years since its introduction (*op cit*). It continues to describe the types of transistor used in amplifiers, such as the BC547, BD139 and 2N3055 (epi) devices quite well. It is today regarded as somewhat lacking for very high speed transistors, such as used in the mobile phone industry, which have f_T s of 10GHz or more, but it is to its credit that it has withstood the test of time for so long.

How to simulate a circuit

There are several steps to simulating a circuit. First, the circuit has to be described in terms of its components. Then, expressions are required for each of those components to describe the electrical behaviour in terms of voltages and currents. Lastly, the resulting set of equations has to be solved in a self-consistent manner.

Starting with the circuit diagram, every interconnection point, or node, is given a number. Often the circuit is also specified as a 'net list'.

In the SPICE model, a node is simply listed as a number with the related node numbers given as appropriate to the component, followed by a letter for the component type – such as R for resistor – and finally its value. The result is a set of nodes with the components described between each, leading to a set of equations describing the electrical behaviour with, usually, one unknown voltage per node. Hence the number of equations required is dictated by the number of interconnections in the circuit.

There are two approaches to simulation that provide complementary information about a circuit. These are the frequency-domain and time-domain methods. In the simulation world, the approaches do not give equivalent information.

The frequency-domain method is based on an AC small-signal model, while the time-domain approach uses discrete time steps. The frequency-domain method gives the frequency response of a circuit, but no absolute values. This is because all equivalent impedances are by definition

fixed and do not change with voltage.

The time-domain approach will provide large-signal behaviour, distortion characteristics, and transient information for – in principle – any arbitrary input waveform. The frequency-domain method is useful for checking whether an amplifier has a flat response, or whether there are some peaks or other surprises in its performance, while the time-domain solution will provide absolute distortion and other information, but for a pre-defined input waveform.

Time-stepped simulation will thus provide the most detailed analyses of circuits. For long complex wave-forms though, it may take a while as there would be many calculations to make. For example if the response over a 1 second period were needed, but time steps of 1µs were required for accuracy, at least 1 million calculations would have to be made.

In some simulations, the time steps taken need to be varied according to the changes occurring in a circuit, so that where nothing much changes the time steps can be widened, and *vice versa*. This usually requires an iterative approach, possibly with 'trial and error' so that if a time step is taken which is too large to resolve accurately, finer time steps can be taken from the previous solution.

Component descriptions

Resistors. Resistors are almost too trivial to mention, but there are some considerations to make concerning the formulation of the model. In a circuit, two nodes N_1 and N_2 with a resistor between them, Fig. 1, have a description for the current which is just

$$i = \frac{V_2 - V_1}{R} \quad (1)$$

where V_1 and V_2 are the voltages on the nodes and R is the resistance. Current is taken to flow in the direction 'there' to 'here', so if node 1 were 'here', the current is as given in equation 1.

Capacitors. Capacitors are described in two ways, either as an impedance, for the frequency-domain analysis, or using a differential, for time-domain analysis. The impedance method uses the expression

$$Z_c = \frac{1}{2\pi f C} \quad (2)$$

Here, Z_c is the impedance of the capacitor, f the frequency, and C is the capacitance.

The differential uses

$$i = C \frac{dV}{dt} \quad (3)$$

where C is the capacitance and dV/dt is the rate of change of voltage across it with respect to time. In Fig. 2, on nodes N_1 and N_2 , for example, the rate of change of voltage with time is

$$\frac{dv}{dt} = \frac{(V_2 - V_1)_t - (V_2 - V_1)_{t-1}}{dt} \quad (4)$$

where t is the time at the current time step; $t-1$ is the previous time step, and dt is the difference between the time steps. The current is then

$$i = C \times \frac{(V_2 - V_1)_t - (V_2 - V_1)_{t-1}}{dt} \quad (5)$$

Because the previous time-step solution leaves the capacitor with a charge on it, it is a little simpler to write equation 5 thus

$$i_c = \frac{C(V_2 - V_1)}{dt} - \frac{Q_{t-1}}{dt} \quad (6)$$

where Q_{t-1} is the charge on the capacitor at the previous iteration ($t-1$).

Inductors. I have not simulated any inductors here, but it is perhaps possible to describe inductors in a similar fashion to the capacitor. The small signal approach is very easy and uses

$$Z_l = 2\pi f l \quad (7)$$

For the transient simulation, instead of a stored charge, there is a stored magnetisation which for want of any better symbol I designate by H . Then for a change in current the induced voltage

$$V = -L \frac{di}{dt} \quad (8)$$

Following the same time steps as for the capacitor

$$V = -L \frac{i_t - i_{t-1}}{dt} \quad (9)$$

and the stored magnetisation

$$H = L \frac{i_{t-1}}{dt} \quad (10)$$

so

$$V = -\left(L \frac{i_t}{dt} - \frac{H_{t-1}}{dt}\right) \quad (11)$$

For any change in current, H will change, and if the current were to become constant, there could still be a stored energy represented by H . At the next time step H is updated by $V dt$ – rather than $i dt$ for the capacitor charge – which for a constant current will not alter H . This correctly gives an induced voltage if, for example, the current were to be switched off.

Note that the current must be referenced towards the node to obtain the correct signs.

Transistor models

Transistors are rather more complicated. The most widely used model is the bipolar algorithm used since the early 1970s for SPICE. Actually, SPICE is a circuit solving environment, while the individual components are described using device models.

The bipolar transistor model is based on the Ebers-Moll formulation but extended by Gummel and Poon². There are several equations to describe a transistor, which account for the various physical effects which occur. These can be found in SPICE manuals, or the SPICE code from Berkeley, and are discussed in bipolar device books^{3,4}. In the following discussion, SPICE model really means 'the bipolar model used in SPICE'.

In a basic SPICE bipolar formulation, around forty parameters describe the transistor. Each transistor will have its characteristics described by a set of SPICE parameters known as the SPICE model. Most manufacturers provide the SPICE model values for their transistors.

In addition to the SPICE parameters, each transistor requires an additional set of variables to describe the particular device's operating conditions. For example, the SPICE model will provide a fixed value of emitter and collector resistance internal to the device – basically the silicon limiting resistances – and a saturation current for the junctions.

A particular transistor will need to refer to these fundamentals, which will vary for each type of transistor

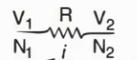


Fig. 1. Resistor from point of view of node 1.

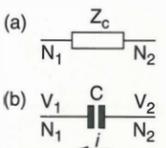


Fig. 2. Two views of a capacitor. Component (a) is for small-signal analysis while (b) is for transient analysis.

used, but also to the voltages on the device such as V_{be} and V_{cb} , which may be different for each particular transistor.

Formulating in C

Using C for the simulation program, the two sets of data required to describe a transistor can be accessed easily using pointers.

Pointers can be set up to refer to the model file and particular variables by defining double precision pointers *trmodel[n] and *trvar[n], where n is a number equal to or larger than the maximum number of transistors required. Alternatively, double-deferred pointers can be set up for a true 'unlimited' simulation.

Now, for a particular transistor m the model pointer, trmodel[m], is set to point to the model file, from which the forty or so SPICE parameters are referenced. Thus more than one transistor may refer to the same SPICE file.

The individual variables however, must be set separately for each transistor which are referenced from the pointer base trvar[m], where m is again the number of the particular transistor in the circuit. Thus a three-transistor circuit using two types of transistor will require two SPICE files.

If the first and last transistor were a BC547, trmodel[0] and trmodel[2] should point to the same BC547 model file but trmodel[1] points to a BC557 file. Individual parameters are referred to by name, which is actually pre-defined as an index. To accomplish this, each SPICE parameter is equated to an integer number, in sequence. For example, r_e might be set to 20, meaning that the SPICE model parameter 'RE' is the 20th parameter from the model base trmodel[#].

The parameter is accessed using trmodel[0][re]. Then, the individual variables will be accessed using a similar set of references such as trvar[0][vbe].

A snag is that it is not always easy to remember, at first, which parameters are individual transistor variables – like the operating voltages – and which are model parameters – like I_{sat} , r_e , r_b . Both are needed to describe a transistor in a circuit.

It was not the intention to describe the SPICE equations in this article. However, some discussion to illustrate the type of calculations SPICE performs is worthwhile.

The fundamental expression for collector current for a given base-to-emitter voltage V_{be} is

$$I_c = I_{sat} \left(\left(\exp \frac{V_{be}}{n_f \times V_{th}} \right) - 1.0 \right) \quad (12)$$

where I_{sat} is the saturation current for the device, V_{th} is the thermal voltage kT/q , (k is Boltzmann's constant, q the magnitude of the charge on an electron and T is absolute temperature) and n_f is the ideality term.

For some first-order simulations, using the transistor in the forward active region, this may suffice. In fact, this is why I always refer to a transistor as a voltage controlled device. Strictly, it is, despite the term 'current mirror' used as a current amplifier.

SPICE adds similar expressions to equation 12 for the collector-to-base voltage to reflect the second junction.

There are also additional terms for the collector to base diode – reflecting the extrinsic collector to base diode – and reverse gain.

The basic operation is fairly symmetrical in terms of applied voltages though the forward and reverse parameters will usually lead to quite different results between forward and reverse bias. This basis for transistor modelling was proposed by Gummel and Poon (*op. cit.*), who included a modification for I_c , q_b , to describe gain fall-off at high currents from high level injection.

Base current comprises four terms. The first is the forward current from equation 12 divided by the forward gain parameter β_F . The second is a low-current term while the third and fourth are terms for the collector to base diode. The third is the collector reverse current as described for the collector – the collector to base diode currents are the same but opposite signs – divided by the reverse gain and the fourth the low current gain characteristic. The collector and base current account for some dozen or so parameters.

Once the DC operating point is established, the capacitances are determined from equations describing the junction capacitances and transit times. These control the frequency response.

The two components making up a capacitance in a junction are the depletion capacitance, which varies with bias voltage with a power law usually between the ideal half (square root) and a less ideal one quarter. The depletion capacitance uses a standard expression

$$C_j = \frac{C_{j0}}{\left(1 - \frac{V_j}{V_{j0}} \right)^{m_j}} \quad (13)$$

where m_j is the power, V_j the applied voltage, V_{j0} the built-in voltage and C_{j0} the capacitance for zero bias. The parameters V_{jx} , M_{jx} and C_{jx} where x is for E and C, for the emitter or collector, are supplied in the SPICE model file. An integrated circuit transistor also has a third junction to the substrate, designated by S.

For high reverse biases, V_j is negative and thus decreases the capacitance while for forward bias the term V_j/V_{j0} approaches 1. To stop a numerical overflow as well as generating an unrepresentatively large capacitance, a term F_C limits the effective bias to a fraction, maybe 90%, of V_{j0} . This parameter, as with all the others, is characterised to give the best fit to the transistor by the manufacturer.

At the same time, however, there is an increasing capacitance arising from stored charge – current carriers – within the transistor. This is expressed in terms of forward transit time (all carriers take the transit time to cross) and increases in proportion to the current and is the so-called diffusion capacitance. The net junction capacitance is the sum of the depletion and diffusion capacitances.

There are terms for the base and collector junction capacitances, and terms for the transit time as a function of temperature. The collector to base capacitance is split into two terms separated by the effective base resistance, and all of these terms add up to the forty or so in the model.

The transistor equivalent circuit is quite relevant to the

discussion on the model. There are two shown in Fig. 3(a) and (b) for the standard and small-signal models respectively. The main difference between these is that the small-signal model contains equivalent resistances for the input and output impedances, which are not included in the standard model.

The small-signal model requires these impedances to be determined from the differentials of the DC equations. It will provide relative gain as a function of frequency. The large-signal model will calculate the currents and voltages for each time step and does not need to know these 'effective' resistances.

In effect the large-signal model is a series of incremental small signal model changes and will accommodate the 'large signal' behaviour automatically.

In these equivalent circuits, V_{be} and V_{cb} are the applied base to emitter and collector to base voltages respectively. Internal resistances of the transistor are described by r_{bb} , representing the external to intrinsic base resistance.

The resistance arises because the base current has to flow laterally in the base. It is a measure of the resistance of the base region, Fig. 4. Sometimes this is called 'rbb', but the SPICE equivalent circuit usually refers to it as 'rbb'. SPICE uses two terms called 'RB' and 'RBMIN' to account for the change in r_{bb} with bias.

Resistance 'RB' is the value of the base resistance under zero bias, normally its maximum value, while 'RBMIN' is the lowest value that r_{bb} can have. An expression relates r_{bb} to 'RB' and 'RBMIN'.

Resistances 'RE' and 'RC' represent the fixed resistances associated with the contacts and diffusion resistances, and 'ro' the output resistance which relates roughly to the Early voltage in the large-signal model. Collector-to-base capacitance is split into two which are lumped into the intrinsic (c_{bc}) and extrinsic or external base (c_{bcx}) contact.

To illustrate the difference between the small and large signal models consider a BC547B biased at 2mA. The DC conditions may have $V_{be}=0.64V$ for both models, and $i_b=6.7\mu A$. A small change in V_{be} (say 1mV) leads to a change in base current of 25nA.

The large signal model will calculate the new base current for a given voltage at a particular time step, whereas the effective input impedance is a resistor of $1.0/25nA$ or 4kΩ. This input impedance is h_{ie} , which is just the small signal change of base current for a small change in base voltage.

The value of h_{ie} used in the small signal model has to be

determined for the particular bias point of the transistor. The input impedance h_{ie} is dependent on the transistor bias, as is h_{fe} , the forward gain; g_m , the forward transconductance and c_{diff} , the diffusion capacitance. So for any small signal model these must be first calculated from a static or DC solution and either then perturbing these by a small amount to determine the small-signal parameters (numerical differentiation), or evaluating the differential directly.

A DC solution is also required for the transient model in order to establish the starting conditions. So it follows that a DC solution is a first step once the circuit has been defined for either simulation.

A DC solution

The DC problem is easier to consider as it uses a very basic equivalent circuit that has no capacitors in it as shown in Fig. 5.

The base and collector currents are shown as current sources. Resistors R_E and R_C can be lumped in with the emitter and collector load resistances. This reduces the number of unknowns in each transistor circuit to essentially two: the base current and base voltage. Formulation of the equations to write the emitter voltage in terms of I_e is necessary though. This is $(1+h_{fe})i_b$, and R_E , and the base voltage ($V_E=V_B-V_{be}$), and similarly for the collector to base voltage.

The DC solution generally has to be iterated to obtain the self-consistent solution which meets both the circuit requirements and SPICE model equations for those bias points.

One way to solve the DC problem is, having set the model for each transistor in the circuit, to guess the bias voltages V_{be} , V_{cb} , and gain. Then, the SPICE model is called which provides the collector and base currents for those bias conditions.

For the next step, these values are stored temporarily. Writing the matrix in terms of gain and the base and collector voltages being 'known' quantities, the circuit conditions are calculated. This leads to a collector and base current being defined which is closer to the circuit values than perhaps the original SPICE calculation.

Now the calculations are iterated. The collector current from the circuit simulation is compared with the current from the SPICE simulation. If the current from SPICE is lower than the circuit current, the base-emitter voltage is increased; and if higher, reduced.

The new collector-base voltage corresponding to the circuit conditions is used, basically adjusting for the new base voltage. Then another loop comprising a SPICE calculation followed by a circuit simulation is executed. Again the currents are compared and will eventually converge providing the base voltage adjustments are set accordingly. This approach is a type of relaxation method with a search test included.

One iterative method is to use a pure 'binary search' whereby the base voltage is adjusted up or down by a difference value which is then halved, so that the adjustments become smaller as the convergent value is approached, for each input condition. This should reach any desired accuracy within a finite number of iterations,

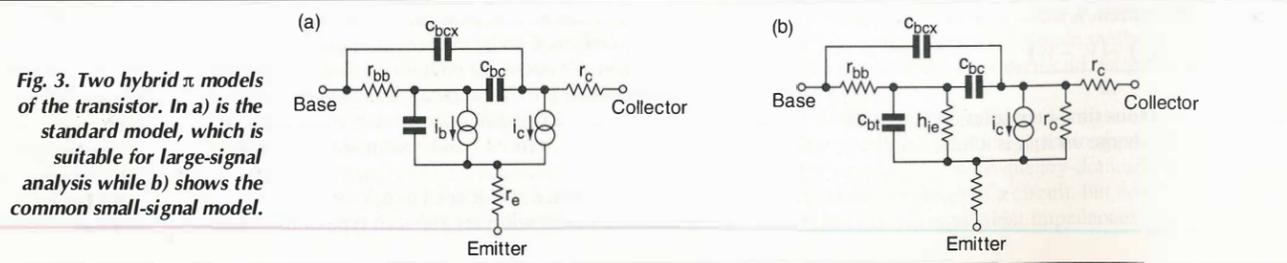


Fig. 3. Two hybrid π models of the transistor. In a) is the standard model, which is suitable for large-signal analysis while b) shows the common small-signal model.

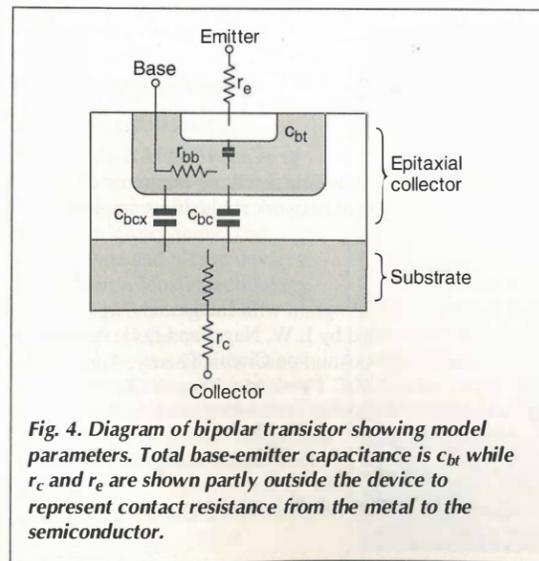


Fig. 4. Diagram of bipolar transistor showing model parameters. Total base-emitter capacitance is C_{bt} while r_c and r_e are shown partly outside the device to represent contact resistance from the metal to the semiconductor.

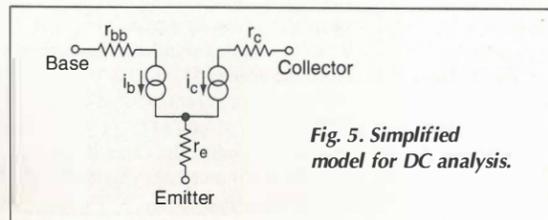


Fig. 5. Simplified model for DC analysis.

typically 8, giving 2^8 reduction from the original difference. Another is to use the fact that the collector current is exponentially dependent on base voltage and adjust the base voltage by the voltage

$$dV_{be} = V_{th} \log \frac{I_{c(C)}}{I_{c(S)}} \quad (14)$$

Here, $I_{c(C)}$ is the current determined from the circuit and $I_{c(S)}$ the SPICE model current. Component dV_{be} is added to the base voltage so that if the SPICE calculation is below the circuit current the voltage will increase V_{be} . This is usually able to resolve the two conditions within four or five iterations, but will take more at high or low currents when the exponential law of the junction changes, unless this is also tracked through successive iterations to provide a better predictive adjustment.

At this point we can consider the small-signal model.

Small-signal model

The small-signal AC analysis technique begins by determining the impedance of each component in the model. A 'frequency response' will require the gain and phase to be calculated for a number of discrete frequencies over a band of interest.

Each solution is calculated using an AC (sinewave) signal so that components such as capacitors can be represented by an impedance at that frequency. By carrying out a number of these simulations over the desired range the bandwidth of a circuit can be determined, along with any untoward frequency response being highlighted.

Complex numbers. In any reactive component, the voltage will be out of phase with the current. The current and voltage can be represented by an x - y graph where y is current and x voltage. The resultant impedance is the vector sum of the voltage and currents as shown in Fig. 6 for a capacitor, where the current leads the voltage.

Other textbooks may plot the current on x and voltage as $-jy$, but the important point is the phase relationship. I prefer to keep voltage on x as the independent variable. Arguably for a capacitor the current is the independent variable.

Impedance of a capacitor is Z_c as given in equation 2. In a composite circuit containing resistors and capacitors, the impedance has to be obtained from the vector resultant. For a single resistor and capacitor, this is trivially the square root of the individual impedances squared. For several components, this approach rapidly becomes unwieldy.

It has been known for a long time that complex numbers can be mapped onto an x - y graph where y represents the imaginary term, resulting in an exactly equivalent vector

diagram to the simple impedance graph just mentioned. But now any number of impedances can be handled by following the rules of adding complex numbers.

Each impedance is then represented by a complex number comprising a real and imaginary term, represented by $x+jy$ where j is the square root of -1 . The rules of complex number arithmetic are straightforward if not quite as simple as ordinary arithmetic. Really, complex numbers make calculations easy.

A capacitor is represented by $1/(j\omega C)$, or $-j/(\omega C)$ to be more useful. This maps the capacitor onto the imaginary axis in the $-$ direction.

To illustrate the use of complex numbers a basic resistor-capacitor low-pass filter circuit as shown in Fig. 7 is simulated. Writing the nodal equations there are just V_{in} and V_{out} , effectively one unknown. Across the resistor and capacitor junction is the resistor current

$$i_r = \frac{V_{in} - V_{out}}{R} \quad (15)$$

and the capacitor current

$$i_c = \frac{V_{out} - V_{out}}{Z_c} = -\frac{V_{out}}{Z_c} \quad (16)$$

Note that we consider the node at V_{out} with all currents written entering the node as shown in Fig. 7 such that we can write the sum of all currents to be zero. This is only Kirchhoff's current law.

In this example we could also have written $i_r=i_c$, but note that i_r and i_c have 'directions'. If we use $i_r=i_c$ the directions are the same, but writing $i_r+i_c=0$ requires that the current flows are towards each other.

In more complicated circuits with several components connected to one node it is appropriate to consider all currents entering that node and equating them to zero.

Summing these currents and setting them to zero gives

$$V_{out} \left[-\left(\frac{1}{R} + \frac{1}{Z_c} \right) \right] + \frac{V_{in}}{R} = 0 \quad (17)$$

This expression has the form which will be used in all subsequent simulations. In this case V_{in} is known and is moved to the right-hand side to give

$$V_{out} \left[-\left(\frac{1}{R} + \frac{1}{Z_c} \right) \right] = -\frac{V_{in}}{R} \quad (18)$$

Using ordinary numbers, the only way we can combine the two impedance terms is by the vector sum. Using complex numbers we can add them directly. The complex version of a resistor is $(R, 0)$ where the two terms represent the real and imaginary parts, in that order, while the complex impedance of the capacitor is $(0, Z_c)$.

In the above equation we have inverse impedances.

Defining the complex impedances

$$z_{r(real)} = R \quad (19a)$$

$$z_{r(imag)} = 0 \quad (19b)$$

$$z_{c(real)} = 0 \quad (20a)$$

$$z_{c(imag)} = \frac{-1}{2\pi f C} \quad (20b)$$

we can write

$$V_{out} \left[-\left(\frac{1}{z_r} + \frac{1}{z_c} \right) \right] = -\frac{V_{in}}{z_r} \quad (21)$$

In the second part of this article, I will go into more detail about how the concepts of network analysis are implemented in software. ■

References

1. SPICE, Simulation Program with Integrated Circuit Emphasis, introduced by L.W. Nagel and D.O. Pederson, 16th Midwest Symposium on Circuit Theory, April 1973
2. H.K. Gummel and H.C. Poon, 'An Integral Charge Control Model of Bipolar Transistors', *Bell System Technical Journal*, 49, 827, 1970.
3. P. Ashburn, 'Design and Realisation of Bipolar Transistors', Wiley, 1988
4. D. Roulston, 'Bipolar Semiconductor Devices', McGraw-Hill, 1990.

NEW PRODUCTS

Please quote *Electronics World* when seeking further information

Fast Ethernet switches

Zarlink Semiconductor has announced availability of fast Ethernet switching chips aimed at supporting high-speed multimedia applications such as streaming video and VoIP (voice over Internet protocol). The six-device ZL50408 family consists of eight-port Fast Ethernet switches with a Gigabit uplink, as well as five and nine-point switches. Available in managed or lightly managed options, the switches provide full wire-speed forwarding at layer two and classification at layers two through four. The Gigabit uplink versions - the ZL50408/407 devices - are expandable to 16 ports. The family provides fine-granularity rate control - down to 16kbit/s increments - on both ingress and egress ports. The switches support QoS and access features, such as congestion management at the input and output of each port, patent-pending port security and filtering, IEEE's 802.1X Extensive Authentication Protocol, 4K VLAN (virtual local area network), 4K IP multicasting, advanced statistics monitoring, and link aggregation with the capability to trunk ports across chips.

Zarlink
www.zarlink.com
Tel: +44(0) 1793 518000



SAPMO1 series are: drain-source voltage 150V; gate-source voltage $\pm 20A$; and pulsed drain current $\pm 80A$. Maximum power dissipation is 150W at 25°C.

Allegro
www.allegromicro.com
Tel: +33(0) 4 50512359

Prober retrofit kit for wafer ID

Cognex has announced the In-Sight 1700 series prober retrofit kit. The kit features the 1700 series wafer readers, which read alphanumeric and 2D matrix codes for the tracking wafers through the production process. The kit comes with all

Transistors for fet drivers


Complementary dual bipolar and Mosfet parts have been introduced by Zetex in its

hardware, software, and installation instructions. The wafer reader's algorithms and electronically-controlled lighting improve wafer ID efficiency by reducing no-reads on hardmarked, softmarked, or even super-softmarked codes that have been degraded by process effects. The ability to read new compact code standards, while still being able to read older bar codes, enhances prober versatility, said the firm. Ethernet communication allows for remote setup, data access, and process monitoring on the test floor.

Cognex
www.cognex.com
Tel: +33(0) 1908 206033

4A PCB connectors stack up together

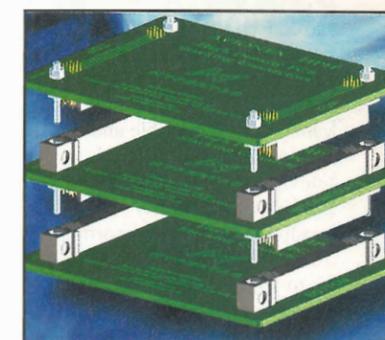Hypertac Interconnect has added a stacking option to its standard range of HPH high-density PCB connectors. A minimum gap of 9mm between PCBs can be achieved by using a low-profile unshrouded pin carrier male and standard female connector, in comparison to full height




version of 16mm. Stainless steel hardware with optional polarising is available on all variations to discriminate mating connectors from one another, whilst providing a guiding system for correct mating, even in blind applications. The connectors are self-jigging when used in multi-position applications. The guiding hardware is pressed in to specifically placed mounting holes with the connector fitting around this. Both the insulator shroud and extended guides provide protection against contact damage during manufacturing.

Hypertac
www.hypertac.com
Tel: +33(0) 8450 8033

3mm x 2mm x 1mm micro leaded package. Used in push-pull circuit topologies,

the transistor pairings create low cost, high performance power gate drivers. Providing the requisite high pulse current and fast switching, the ZXTD4591AM832 offers a 40V rated NPN and PNP combination collector current of 2.5A and a maximum voltage of 500mV. Specified up to 2A, the gain of the two transistors is also high, respectively 200 and 160 at 1A collector current. The Mosfet equivalent ZXMC3AM832 package houses complementary 30V Trench Mosfets that combine low on-resistance with enhanced rise and fall times

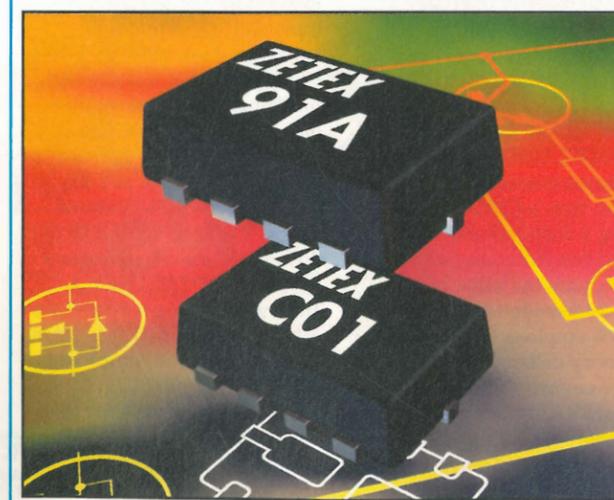Zetex
www.zetex.com
Tel: +44(0) 161 622 444



Heat compensated audio transistors

The Sanken SAPMO1 series of temperature-compensated audio transistors are available from Allegro MicroSystems. The 150V p-type and n-type devices use Sanken's Mosfet technology to offer highly accurate and responsive temperature compensation through the use of on-chip diodes. In addition, they feature built-in push/pull circuitry that eliminates the need to trim the idling current in audio amplifiers using external components. Absolute maximum ratings for the

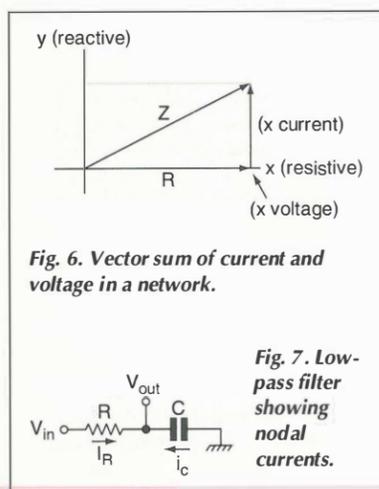


Fig. 6. Vector sum of current and voltage in a network.

Fig. 7. Low-pass filter showing nodal currents.

NEWPRODUCTS

Please quote **Electronics World** when seeking further information

Stereo headphone DAC has low power

Wolfson Microelectronics has introduced the WM8759, a low-power 24-bit stereo DAC with integrated headphone driver. It is suited for use in the next generation of portable and home music players, and digital televisions. The WM8759 provides up to 50mW headphone power, supporting 16- to 24-bit word data inputs at up to 192kHz sampling rate. Operating on split analogue/digital power supplies, the device allows power consumption down to 20mW on 2.7V supplies, less than 10µA in standby, but supporting large output power from the headphone driver. The device has been rated at 100dB signal-to-noise ratio (SNR), "A" weighted at 48kHz with -88dB THD driving a line load and -72dB THD driving 16Ω headphones. The WM8759 includes a hardware control interface for selection of audio data formats, a serial interface port, digital interpolation filters, and multi-bit sigma delta modulators.

Wolfson Microelectronics
www.wolfsonmicro.com
Tel: +44(0) 131 272 7000



Fibre access with redundant architecture

Data Device Corporation has introduced a series of 2Gbit/s Fibre Channel network interface controllers (NICs). The FC-75000 Fibre Access NIC features a dual redundant architecture with autonomous failover or dual independent channels, low memory to memory message latency, deterministic autonomous message scheduling, and built-in avionics upper layer protocols on conduction cooled PMC card making it ideally suited for the most rigorous military

applications. The series of conduction cooled Fibre Channel NICs operate over a wide -40 to +85°C temperature range.
DDC
www.ddc-web.com

40in. LCD for TV and display information

Torisan Sanyo has bought out an improved version of its 40in. TFT LCD module for television and public information display applications. The TM396WX-71N32 is lighter by 2.3kg and offers a response time of 8ms making it suitable for display of

television and other video format images without streaking or blurring. The panel offers a full colour display of up to 16.7 million colours with a resolution of 1280x768 (WXGA) and a contrast ratio of 600;1. Luminance of 500cd/m² combined with its contrast make it suitable for use in areas where the ambient light levels might wash-out other displays. Minimum backlight life is 50,000 hours, reducing lifetime costs when compared with alternatives such as plasma displays, claims the company. Plans exist to develop much larger and improved versions of TFT LCD module in the future for these applications.

Torisan Sanyo
www.displaze.com
Tel: +44(0) 1296 469770


DSL platform gets DSLAM 1.1 data path

Wintegra has added a DSLAM 1.1 data path software release as part of its DSL platform which is aimed at DSLAM chassis-based line cards and uplink cards. Using the fabless firm's internal packet processing engines the DSLAM 1.1 data path software release provides advanced data path features such as multicast, NAT, VLAN support and enhanced deep packet classification, all with scalable performance. It is factory hardened and provided as a shrink-wrapped package that is royalty free and requires no up-front NRE fees.

Wintegra
www.wintegra.com
Tel: +44(0) 1698 404885

Power Mosfet controller for 42V automotive systems

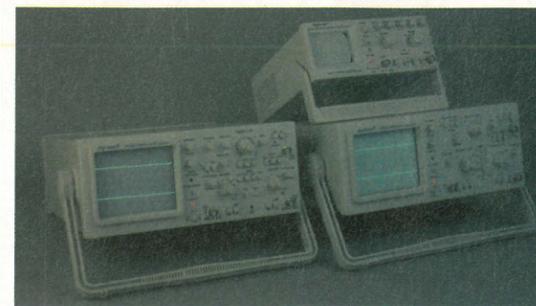The A3925 power Mosfet controller from Allegro MicroSystems is for use in 42V automotive applications involving high-power motors. It provides six high-current gate-drives capable of driving a wide range of power N-channel MOSFETs. Bootstrap capacitors provide a steady supply voltage over a varying battery input



Vann Draper is offering over 20% discount to readers of **Electronics World** on their new range of **digimess** analogue oscilloscopes, prices shown below include discount.

The range consists of a 10MHz single channel as well as 20, 40 and 60MHz dual channel types. Triggering modes are Auto, Norm and TV, with the 40 and 60MHz versions also including PP Auto triggering. Z axis inputs & input delay lines are provided on the 20, 40 and 60MHz types and all models are supplied with probes, mains lead, operating manual and a 1 year guarantee.

Model number	M010	M020	M040	M060
Price (inc vat & del)	£109.00	£289.00	£459.00	£649.00
B/W & no of CH's	10MHz single	20MHz dual	40MHz dual	60MHz dual
Accelerating voltage	1.3kV	2kV	14kV	14kV
Screen size 8 x 10	1 div = 6mm		1 div = 10mm	
Vertical (3%)	5mV - 5V/div		5mV - 5V/div	
Vertical mode	CH1	CH1, CH2, ALT, ADD, CHOP, INVERT CH2		
Horizontal (3%)	0.1S - 0.1uS/div		0.5S - 0.2uS/div	
Dims (cm) & wt	22x27x9, 3kg		32x42x13, 6.5kg	

To order, simply post the coupon to: **Vann Draper Electronics Ltd, Stenson House, Stenson, Derby DE73 1HL.** Or Tel 01283 704706 Fax 01283 704707
Email sales@vanndraper.co.uk Web www.vanndraper.co.uk

20% discount for EW readers
digimess oscilloscopes from £109.00 inc vat & del



Vann Draper Electronics Ltd

The test & measurement specialists

www.vanndraper.co.uk

Test equipment from Grundig, **digimess**, Kenwood, Hameg, Tektronix, Avo and more

Use this coupon for your order

Please supply me:
(Qty) ... (Model) ... (Price) ...
(Qty) ... (Model) ... (Price) ...

Name: _____

Address: _____

Tel No: _____

Total £ _____

Cheques payable to Vann Draper Electronics Ltd or debit my Visa, Mastercard or Switch card:

Card type: _____

Card No: _____

Expiry date: _____ Switch iss No: _____

Signature: _____

Overseas readers can still obtain this discount but carriage charges vary according to country. Please telephone, fax, email or write to Vann Draper.

16Mbit SRAM cuts size in half

Renesas Technology has a range of low power 16Mbit SRAMs with a chip size of approximately 32mm². The small die size is achieved through combining an SRAM

cell using a thin film transistor and a DRAM cell using a stacked capacitor. First devices in the range comprise the 16Mbit RILA1616R series (1.8V version) and RILV1616R series (3V version). Dubbed SuperSRAM, the memory cell uses a 0.15µm process and it is approximately half the size of the firm's CMOS SRAM using a conventional six-transistor structure (when employing the same process). Unlike pseudo static RAM which employs DRAM memory cells and is used in large-capacity applications, SuperSRAM does not require refreshing, said the company. As with conventional SRAM,

information stored in a memory cell is automatically maintained by means of the load transistor and driver transistor. Data retention current is 1µA at 25°C. Two external voltage versions of the SuperSRAM are available on a metal mask option basis: the 1.8V (1.65V to 2.3V) RILA1616R series and the 3V (2.7V to 3.6V) RLIV1616R series. Both are housed in two different types of package, a 52-pin TSOP (10.79mm x 10.49mm) with a 0.40mm pin pitch, and a 48-ball fine-pitch BGA (7.5mm x 8.5mm) with a 0.75 ball pitch.

Renesas
www.renesas.com
Tel: +44(0) 1628 585161



SPECIAL OFFERS

TEKTRONIX 2445A 4 Ch 150MHz Delay, Cursors etc. Supplied with 2 Tektronix probes **ONLY £425**

TEKTRONIX 2232 Digital Storage Scope. Dual Trace 100 MHz, 100nm with probes. £525
H.P. 54501A Digitizing Oscilloscope 100MHz, 4Ch £425
CIRRUS CRL254 Sound Level Meter with Calibrator, 80-120dB, LEO. £95
BECKMAN HD110 Handheld 3 1/2 digit DMM, 28 ranges with battery, leads and carrying case. £30
WAYNE KERR B424 Component Bridge. £50
RACAL 9300 True RMS Voltmeter 5Hz-20MHz usable to 60MHz 10V-36V. £50
RACAL 9300B as above. £75

H.P. 3312A Function Gen 0.1Hz-13MHz AM/FM Sweep/Tri/Gate/Burst etc. £300
FARNELL AMM255 Automatic Mod Meter 1.5MHz-20Hz Unused. £75
FARNELL DS61 Low Frequency Syn Sig Gen 0.001Hz to 99.99kHz, Low Distortion TTL/Square/Pulse Outputs etc. £95
H.P. 3310A Function Sine/Sq/Tri/Ramp/Pulse 0.1Hz-10MHz low distortion, TTL Output, Any. £125
H.P. 545A Logic Probe & 547A Logic Pulser and 547A Current Tracer. £90
FLUKE 77 Multimeter 3 1/2 digit Handheld. £60
FLUKE 77 SERIES II. £70
HEME 1000 LCD Clamp Meter with carrying Case. £60

Racal 9008 Automatic Modulation Meter AM/FM 1.5MHz - 2GHz **£95**

Datron 1061A High Quality 6 1/2 digit Bench Multimeter True RMS/4 wire/Current Converter **£225**

BLACK STAR ORION PAL/TV Colour Pattern Generator £75-£125
THURLBY/THANDER TG210 Function Generator, 0.002Hz-2MHz, TTL etc. £30-£35
THURLBY/THANDER P.S.U. PL320QMD, 0V-32V, 0A-2A Twice (late colours). £200

JUST IN

HP 8640A Signal Generator AM/FM 500kHz-512MHz £250
LEADER LB0523 Oscilloscope Dual Trace 35MHz. £140
GOLD OS300 Oscilloscope Dual Trace 20MHz. £95
NATIONAL PANASONIC VP7705A Distortion Analyser. £125
KENWOOD V1776 Millivoltmeter 2 Channel. £50
KENWOOD FL 140 Wow & Flutter Meter. £50
KENWOOD FL180A Wow & Flutter Meter Used. £75
BIRD 43 Watt Meter. £75
Elements for the above. £25

MARCONI 893C AF Power Meter, Sinad Measurement. Unused £100 Used £60
MARCONI 2610 True RMS Voltmeter Autorangin 5Hz-25MHz. £195
GOULD J3B Sine/Sq Osc. 10Hz-100kHz. Low distortion £75-£125
AVO 8 Mk6 in Ever Ready Case, with leads etc. £80
Others Avos. from £50
GOODWILL GV1427 Dual Ch AC Millivoltmeter 10mV in 12 Ranges Freq 10Hz-1MHz. £75
SOLARTRON 7150 DMM 6 1/2 digit True RMS. £150
SOLARTRON 7150 PLUS. £200

9901 Counters, Counter, 50MHz. £50
9902 Counter, 50MHz. £75
9903 Counter, 50MHz-560MHz, 9-digit. £50
RACAL 9343M, LCR Databridge. £200
Automeasurements of R, C, L, D. £125
HUNTRON T1MCR. £125
MARCONI T1MCR. £175

FARNELL AP60/150. £2000
FARNELL AP100. £2000
H.P. 6012B DC Power Supply 0-50A 1000V. £1000
FARNELL AP60/50 1KW Autoranging. £1000
FARNELL H60-50 0-60V 0-50A. £750
FARNELL H60/25 0-60V; 0-25A. £400
Power Supply HPS3010 0-30V; 0-10A. £140
FARNELL Dual PSU XA35-2T 0-35V 0-2A Twice QMD LCD Display. £180
FARNELL L30-2 0-30V; 0-2A. £80
FARNELL L30-1 0-30V; 0-1A. £60

Many other Power Supplies available.
Isolating Transformer 240V In/Out 500VA. £40

FARNELL DTV 12-14 OSCILLOSCOPE

DUAL TRACE 12 MHz TV COUPLING **ONLY £75**

FARNELL LFI 12-14 Sine/Sq OSCILLATOR 10 MHz - 1 MHz **ONLY £75**

OSCILLOSCOPES

TEKTRONIX TDS350 Dual Trace 200MHz 1G/S unused. £1500
TEKTRONIX TDS320 Dual Trace 100MHz 500M/S. £1200
TEKTRONIX TDS310 Dual Trace 50MHz 200M/S. £950
LEPROY 9400A Dual Trace 175MHz SG/S. £750
HITACHI VC6523 Dual Trace 20MHz 20M/S. £750
PHILIPS PM3092 2+2Ch 200MHz Delay. £600
PHILIPS PM3089 2+2Ch 100MHz. £800 As new. £550

TEKTRONIX TDS350 Dual Trace 200MHz 1G/S unused. £1500
TEKTRONIX TDS320 Dual Trace 100MHz 500M/S. £1200
TEKTRONIX TDS310 Dual Trace 50MHz 200M/S. £950
LEPROY 9400A Dual Trace 175MHz SG/S. £750
HITACHI VC6523 Dual Trace 20MHz 20M/S. £750
PHILIPS PM3092 2+2Ch 200MHz Delay. £600
PHILIPS PM3089 2+2Ch 100MHz. £800 As new. £550

TEKTRONIX TDS350 Dual Trace 200MHz 1G/S unused. £1500
TEKTRONIX TDS320 Dual Trace 100MHz 500M/S. £1200
TEKTRONIX TDS310 Dual Trace 50MHz 200M/S. £950
LEPROY 9400A Dual Trace 175MHz SG/S. £750
HITACHI VC6523 Dual Trace 20MHz 20M/S. £750
PHILIPS PM3092 2+2Ch 200MHz Delay. £600
PHILIPS PM3089 2+2Ch 100MHz. £800 As new. £550

JUST IN

H.P. 86312A PSU 0 - 20V/0-2A. £400
H.P. 86311B PSU 0 - 15V/0-3A. £400
H.P. 863090 PSU Dual 0 - 15V 0-3A/0-12V 0-1.5A. £750
H.P. 86328 PSU 0 - 20V/0-5A. £500
H.P. 8623A PSU Triple Output ranging from 0-20V 0-5A to 0-20V 0-4A. £850
H.P. Agilent 34401A DMM 6 1/2 digit. £400/£450
H.P. 3478A DMM 5 1/2 digit. £275
FLUKE 45 DMM Dual Display. £400
KEITHLEY 2010 DMM 7 1/2 digit. £950
KEITHLEY 617 Programmable Electrometer. £1250
H.P. 4338B Resistor. £1500
H.P. 4338C Resistor. £1500
H.P. 4338D Resistor. £1500
H.P. 4338E Resistor. £1500
H.P. 4338F Resistor. £1500
H.P. 4338G Resistor. £1500
H.P. 4338H Resistor. £1500
H.P. 4338I Resistor. £1500
H.P. 4338J Resistor. £1500
H.P. 4338K Resistor. £1500
H.P. 4338L Resistor. £1500
H.P. 4338M Resistor. £1500
H.P. 4338N Resistor. £1500
H.P. 4338O Resistor. £1500
H.P. 4338P Resistor. £1500
H.P. 4338Q Resistor. £1500
H.P. 4338R Resistor. £1500
H.P. 4338S Resistor. £1500
H.P. 4338T Resistor. £1500
H.P. 4338U Resistor. £1500
H.P. 4338V Resistor. £1500
H.P. 4338W Resistor. £1500
H.P. 4338X Resistor. £1500
H.P. 4338Y Resistor. £1500
H.P. 4338Z Resistor. £1500

SPECTRUM ANALYSERS

H.P. 8561B 50Hz - 6.5GHz. £5000
H.P. 8560A 50Hz - 2.9GHz Synthesised. £5000
H.P. 8594E 9kHz - 2.9GHz. £4500
H.P. 8591E 1MHz - 1.8GHz 75 ohm. £2750
H.P. 853A with 8559A 100kHz - 21GHz. £1750
H.P. 8558B with Main Frame 100kHz - 1500MHz. £750
H.P. 3585A 20Hz - 40MHz. £2500
ADVANTEST RA418 10kHz - 3.5GHz. £2750
EATON/Altech 757 0.001 - 22GHz. £750
MARCONI 2382 100Hz - 400MHz High Res. £2000
MARCONI 2370 30Hz - 110MHz. £500
H.P. 182 with 8557 10kHz - 350MHz. £500
H.P. 1411 Systems
8553 1kHz - 110MHz. £500
8554 500kHz - 1250MHz. £750
8555 10MHz - 18GHz. £1000
H.P. 8443 Tracking Gen/Counter 110MHz. £250
H.P. 8444 Opt 059. £750
B & K 2033R Signal Analyser. £650
H.P. 8754A Network Analyser 4MHz - 1300MHz. £1250
H.P. 3577A Network Analyser 5Hz - 200MHz. £3000
H.P. 53310A Modulation Domain Analyser Opt 001/003. £5000
ONO 50K1K Portable FFT Analyser. £1500
H.P. 8720C Microwave Network Analyser 50MHz-20GHz. £12500

RADIO COMMUNICATIONS TEST SETS

MARCONI 2955/2955R. £1000
Rohde & Schwarz CMT 0.1 - 1000MHz. £1500
Schlumberger 4040. £750

STEWART OF READING
110 WYKEHAM ROAD, READING, BERKS RG6 1PL
Telephone: (0118) 9268041 Fax: (0118) 9351696
www.stewart-of-reading.co.uk
Callers welcome 9am-5.30pm Monday to Friday (other times by arrangement)

USED EQUIPMENT - GUARANTEED. Manuals supplied.
This is a VERY SMALL SAMPLE OF STOCK. SAE or telephone for lists. Please check availability before ordering. CARRIAGE all units £16. VAT to be added to total of goods and carriage.

NEWPRODUCTS

Please quote *Electronics World* when seeking further information



bridge-open, all undervoltage conditions, and thermal shutdown. Operating temperature range is -40 to +135°C.

Allegro Microsystems
www.allegromicro.com

Buck bias regulator with 75V input

National Semiconductor is offering its smallest high-voltage buck bias switching regulator to satisfy housekeeping or bios power needs in next-generation communications, automotive -48V distributed and battery powered systems. The LM5007 is a buck bias regulator which steps down a high-voltage (up to 75V) primary-side power supply and produces a low voltage (10V typical) bias supply for secondary-side control devices. The device contains an 80V n-channel power Mosfet rated at

range. Direct control of each gate output is possible via six TTL compatible inputs. A different amplifier with two sample-and-hold outputs is integrated to allow accurate measurement of the low-side current in a 3-phase bridge. Two diagnostic fault outputs can be continuously monitored to protect the driver from short circuits to battery or supply,



0.7A peak that can be switched at high frequencies (up to 500kHz), allowing the use of a small output filter to complete a bias supply design that sources up to 0.5A continuous load current. The device is available in a 4 x 4mm 8-pin chip-scale package and an MSOP-8 package. According to the supplier, the control scheme

deployed in the LM5007 can eliminate the need for loop compensation while offering a very fast transient response using an ON-time that is inversely proportional to the input line voltage (V_{in}). This produces a relatively constant and easily filtered switching frequency. An intelligent current limit is implemented with a forced OFF-time, which is inversely proportional to V_{OUT} .
National Semiconductor
www.national.com
Tel: +44(0) 870 242171

Programmable output power module in slot

Lambda has expanded the output options for its Vega series with the addition of two wide-range programmable output modules. The W2 and W5 modules provide designers with a programmable output of 0.25V


GPS receiver with broad beam antenna

Sarantel has introduced SmartAntenna F02, its latest integrated antenna-receiver for global positioning applications. It combines the firm's omni-directional GPS antenna with Fastrax's Trax02/4 GPS receiver chipset. The antenna's GeoHelix design offers high levels of immunity to RF interference, simplifying the

integration process, said the supplier. It measures 32 x 32mm and 10.8mm deep, weighs under 30g, and consumes 100mW at 2.7V in continuous operation. According to Sarantel, Fast acquisition times are a feature of the 12 channel iTrax02/4 receiver, which has a 32MIPS DSP core and dedicated GPS search engine. The use of a


broad antenna beam width is designed to provide a more accurate GPS fix. The position fix is normally accurate to within 10 metres worldwide. The device's serial data interface (RS232) and 3.3V ground power connections are made via one standard 14-way header. It does not require a ground plane. Operating on the GPS L1-band (1575.42MHz) the GeoHelix antenna design is based on copper tracks, deposited on to a small ceramic cylinder, which are individually and automatically laser-trimmed for optimum frequency response. The antenna-receivers are fully mounted side-by-side in combined applications such as Bluetooth and GSM without loss of performance. A development kit is available which allows the more advanced user to make use of the pre-emptive real time operating

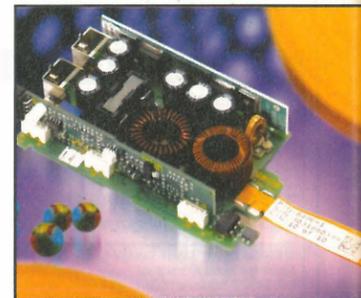Sarantel
www.sarantel.com
Tel: +44(0) 1933 670561



to 7V at 30A and 0.25V to 32V at 8.5A respectively. The modules occupy a single slot on the Vega chassis. They offer a choice of fixed or tracking overvoltage protection and can be fitted with fast-on or screw terminal output connectors. The modules also offer a choice of either resistance programming of the output, between 0 and 32kΩ, or voltage programming of the output, between 0 and 5V. Both programming types are available in four variants: inhibit with fixed current limit; inhibit with program current limit (0-5V); enable with fixed current limit; and enable with program current limit (0-5V). Power density is 0.35W/cm³ and there is no minimum load requirement.
Lambda
www.lambdae.com
Tel: +44(0) 1271 856666

THERE IS INTERESTING NEWS

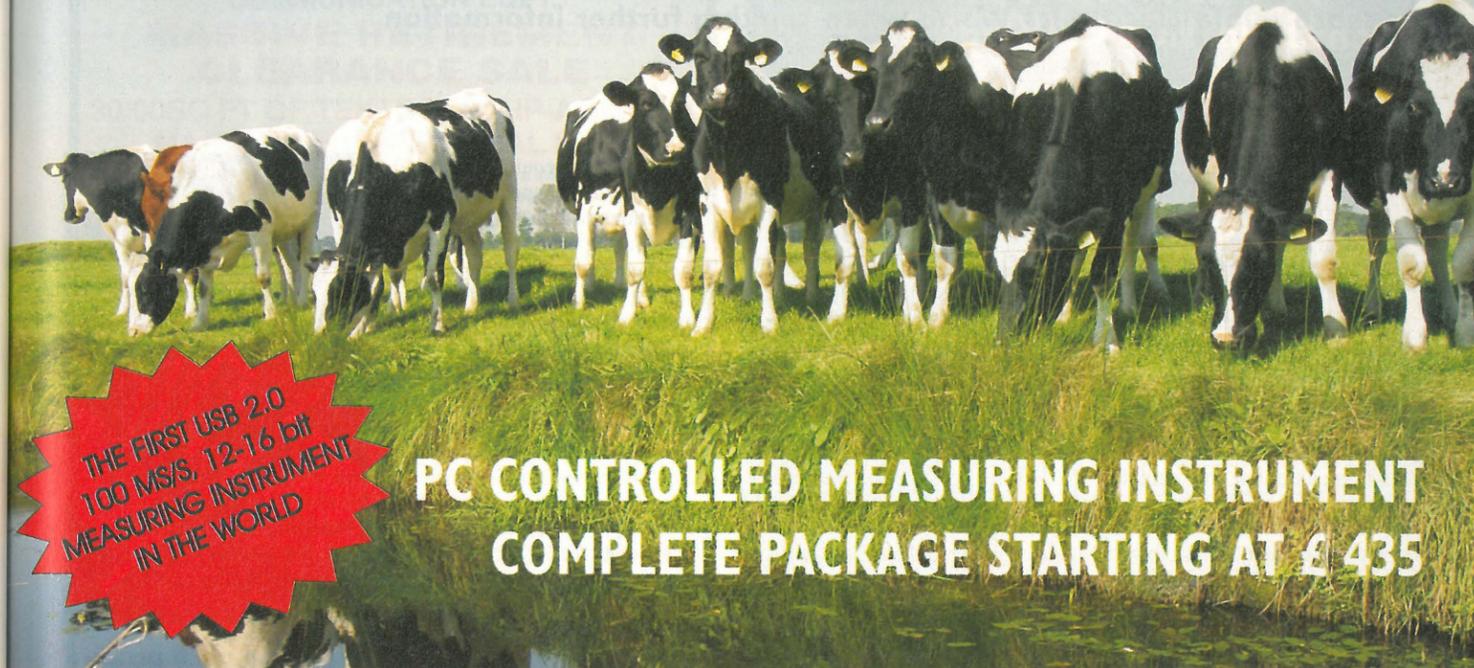

THE FIRST USB 2.0
100 MS/S, 12-16 bit
MEASURING INSTRUMENT
IN THE WORLD

PC CONTROLLED MEASURING INSTRUMENT
COMPLETE PACKAGE STARTING AT £ 435

OSCILLOSCOPE


FFT ANALYSER

VOLTMETER

RECORDER

The Handyscope 3 is a powerful and versatile two channel measuring instrument with an integrated function generator.

- ° USB 2.0 connection (USB 1.1 compatible)
- ° sample speed up to 100 MHz per channel
- ° 8 to 16 bit resolution (6 μ Volt resolution)
- ° 50 MHz bandwidth
- ° input sensitivity from 200 mV up to 80 Volt
- ° large memory up to 131060 samples per channel
- ° four integrated measuring devices
- ° spectrum analyser with a dynamic range of 95 dB
- ° fast transient recorder up to 10 kHz
- ° several trigger features
- ° auto start/stop triggering
- ° auto disk function up to 1000 files
- ° auto setup for amplitude axis and time base
- ° auto trigger level and hysteresis setting
- ° cursor measurements with 21 read-outs
- ° very extensive function generator (AWG) 0-2 MHz , 0-12 Volt

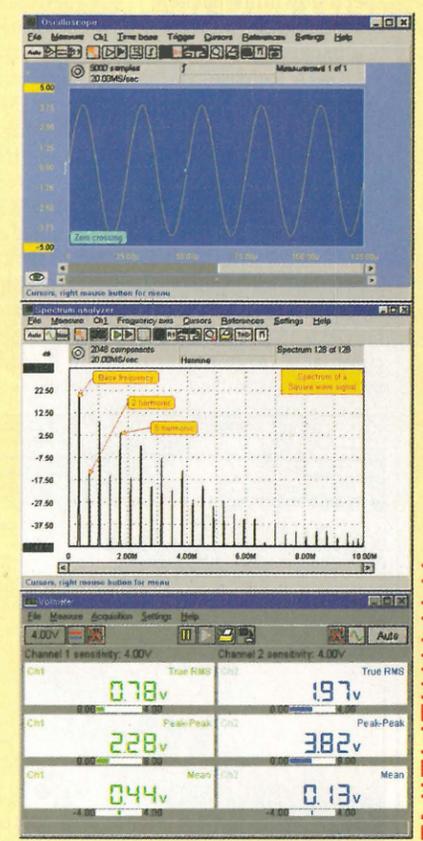

for more information, demo software, software, source code and DLL's visit our internet page: <http://www.tiepie.nl>

<p>TiePie engineering (NL) Koperslagersstraat 37 8601 WL SNEEK The Netherlands Tel: +31 515 415 416 Fax: +31 515 418 819</p>	<p>TiePie engineering (UK) 28, Stephenson Road, St. Ives Cambridgeshire, PE17 3WJ, UK Tel: 01480-460028 Fax: 01480-460340</p>
--	---

HANDYSCOPE HS3

WWW.TIEPIE.NL

NEWPRODUCTS

Please quote *Electronics World* when seeking further information

100-tap non-volatile potentiometers

Xicor is offering a family of 100-tap non-volatile digitally-controlled potentiometers that will accommodate a voltage swing of between 0V and 10V for an increased dynamic range, making the devices suitable for applications such as offset and bias voltage adjustments in high voltage amplifier and regulator designs. The X9319 family of potentiometers features 100-taps with 99-segmented resistors and is available in 10kΩ and 50kΩ total resistance options. Adjustments to the wiper position are made using an up/down interface and the position can be stored in the internal EEPROM for recall



during device power-up. According to the supplier, the up/down interface allows efficient wiper position calibration for reduced manufacturing cost in bias and control applications. Likely applications for this programmable device are high


profile systems requiring gain, reference voltage and bias calibrations such as common mode biasing in RF power amplifiers and gain adjustments in audio applications. Other target applications include signal conditioning circuits to set zero offset and span correction for sensors and adjustments in process controls requiring parameter retention.

Xicor
www.xicor.com
Tel: +44(0) 1993 700544

IDE improves data visualisation

Green Hills Software, the supplier of real-time operating systems and embedded software development tools, has released the latest version of its integrated development environment (IDE) for embedded developers. Multi IDE 4.0 features new data visualisation, workspace management and low-level and bare-board debugging features which support software development activities, ranging from connecting to, exercising and testing new boards through advanced application debugging and project management. The IDE has also been extended to improve developer productivity over more aspects of the software development process, says the supplier. The Workspace Manager provides a graphical interface for managing sequences of commonly used actions within the IDE. Also the Multi Editor supports complete cross reference-browsing capabilities without the need for a compiled or linked program and it locates function prototypes included in header files so the user can see the required function signatures while typing, without requiring any previous configuration. Multi 4.0 will support PowerPC, ARM, MIPS, x86/Pentium, 68K/Coldfire, V800 and StarCore processor families as well as native development for Windows, Solaris, HP/UX and Linux.

Green Hills Software
www.ghs.com

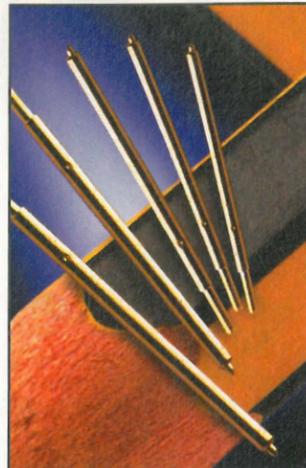

Ultra-fine pitch probe tests down to 0.5mm centres

The P706 from Peak Test Services is an ultra-fine pitch test probe for testing components at centres down to 0.5mm (0.02 inch). According to the supplier, the probe is specifically designed for testing boards using ball grid array, multi-chip modules and other fine-pitch packages. The P706 has a gold-plated 4-point crown measuring only 0.25mm in diameter, a working travel of 0.65mm and a spring force of 0.2N.

Peak Test Services
www.thepeakgroup.com
Tel: +44(0) 1462 475600

Isolated approach to POL converter design


Vicor has introduced its first in a range of isolated point-of-load (POL) power converters which is designed to sit on its factorised bus architecture. The power module supplier is responding to the need for more power rails driving widely ranging current levels on PCB designs with a new type of low current power regulator which can supply voltages ranging from 5V down to 1V scattered about the PCB at positions close to the point-of-load. Vicor's approach is to introduce a family of isolated point of load devices. It believes there is a problem with ground currents, generating unwanted noise with the more

3G Basestation design

PicoChip Designs has announced its first high speed downlink packet access design (HSDPA). This is a packet-based mode for WCDMA Release 5 which increases data rates to up to 14Mbit/s for intensive multimedia services and has been dubbed by some as next generation 3G or 3.5G. The "basestation on a CD" design platform includes tested algorithms and source code for WCDMA FDD and HSDPA. The design platform combines a high-performance processor optimised for

wireless, with a programming environment using standard ANSI C as well as system libraries. Based on the picoArray processor, it delivers 300GOPS and 30GMAC/s performance. In addition to WCDMA FDD and HSDPA, reference designs for TDSCDMA, 802.16 and other standards are under development. The system is also appropriate for any other advanced wireless technology.

Picochip
www.picochip.com

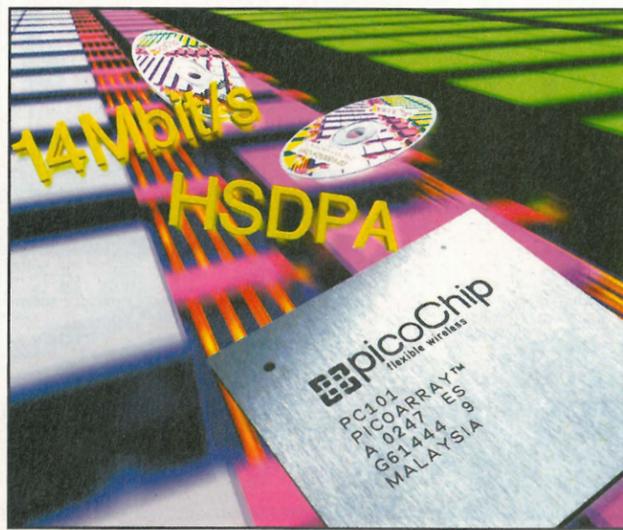

JOHN RADIO ELECTRONIC TEST AND COMMUNICATION EQPT.

MASSIVE RETIREMENT CLEARANCE SALE

30.00SQ FT OF TEKTRONIX-HP-AGILENT-MARCONI-PHILIPS-RACAL ETC.,

Over the rest of this year at our bulk Smithies Mill site sales by auction-Tender-Offer-all welcome private or trade-single or bulk items. Equipment sale floor 6000sq ft +25.000sq ft of adjoining buildings plus 9000sq ft will be slowly added from our Whitehall Works headquarter site.

Open weekdays 9am-5pm and Saturday mornings to 1:00pm

Closed dinner 1- 2pm

ALWAYS PHONE FOR APPOINTMENT FIRST.

Item lists-photos-site map-on

website www.johnsradio-uk.com www.johnsradio.com
email: johnsradio@btconnect.com

Location M62 Junction 27, A62 to Huddersfield, 1 mile Birstall Smithies Lights (6 roads) look to your left, site under factory chimney with aerials on top, road second left, Smithies Moor Lane, 100yds second entrance on left.

Johns Radio, Smithies Mill, Birstall Smithies Lights,
883-885 Bradford Rd, Batley, West Yorks WF17 8NN-8NS.

Phone - 01924 442905 - Fax - 01924 448170

Our normal sales, workshop, repairs and calibration will continue until clearance of all items.

Contact Patricia at Whitehall Works-84 Whitehall Rd East,
Birkenshaw, Bradford BD11 2ER.

Phone - 01274 684007 - Fax 01274 651160

NEXT SALE FRI-SAT DECEMBER 5-6


DETAILS www.tech-asset.co.uk

info@tech-asset.co.uk

The Simple Solution! FlexIt

AVR Controller Development System

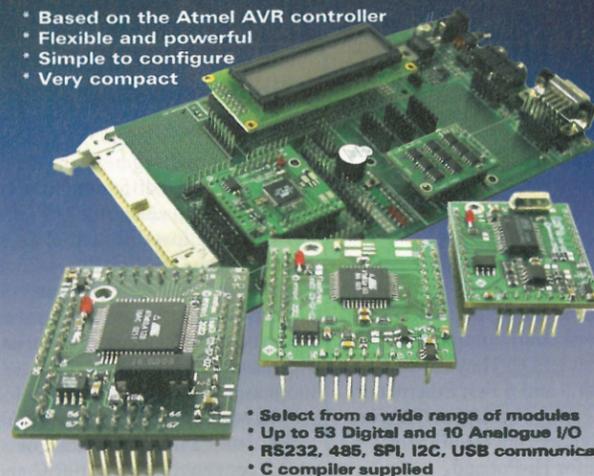- Based on the Atmel AVR controller
- Flexible and powerful
- Simple to configure
- Very compact



- Select from a wide range of modules
- Up to 53 Digital and 10 Analogue I/O
- RS232, 485, SPI, I2C, USB communication
- C compiler supplied
- Compatible with most AVR dev. tools
- In-system programmable
- Free Atmel debug simulator available
- Peripheral drivers and libraries supplied
- Increasing range of expansion modules
- Full website support

Check out FlexIt at www.ennovi.co.uk

ennovi Ltd
Dynamic Design

+44 (0)1425 478884
sales@ennovi.co.uk

Precision measurement
Embedded control
Intrinsic safety
Internet embedded systems
USB interface

A QUANTUM LEAP IN
EMBEDDED CONTROLLERS

Quick FIRE SUPERCONTROLLERS

Our range provides:-

- The fastest 68000 based Core up to 66 Mhz.
- Extensive I/O:- Serial, IrDA, SPI, I²C, Analogue, Timers/Counters, RTC, etc.
- Large Memory Capacity:- Flash, SRAM, DRAM.
- Supports:- Mono & Colour LCD's, Touch Panels & Keypads, Very Low Power.

ALSO LOW COST

DEVELOPMENT

- Target easily & quickly.
- Full ANSI 'C' compiler, assembler & linker all Windows32 based.
- Source Level Debug.
- Full Driver Support with Libraries.
- Real Time Multitasking OS with a free run time licence.
- Free Unlimited email support.

www.cms.uk.com

see our web site for full details

CAMBRIDGE MICROPROCESSOR SYSTEMS LTD



Unit 17-18 Zone 'D' Chelmsford Rd. Ind. Est.
Great Dunmow, Essex CM6 1XG
Telephone: 01371 875644
email: sales@cms.uk.com

Please quote *Electronics World* when seeking further information

traditional non-isolated device. Called the V-1 chip voltage transformation module (VTM), it achieves a response time of less than 1µs and delivers up to 80A in a volume of less than 0.25 cubic inch while converting 48V to 1.5V. The modules may be paralleled to deliver hundreds of amps at an output voltage settable from 1.0 to 1.8V DC, at full load. The firm's factorised power architecture is different to alternative intermediate bus architecture of other suppliers which feed non-isolated POL converters at lower bus voltages. Vicor maintains this approach is less efficient. The company says its VTMs have 1MHz bandwidth and can provide efficient bi-directional power flow with the load, limiting voltage excursions due to instantaneous load surges or dumps. The open loop output resistance, Rout, of the V048K015T80 VTM is approximately 1.3mΩ. The BGA package supports in-board mounting with a low profile of 0.16 inch (4mm) over the board. A J-leaded package option will support on-board surface mounting with a profile of 6mm

over the board. Outline dimensions are 32 x 21.5 x 6mm.

Vicor
www.vicoreurope.com

Oven controlled crystal oscillators for all synchronization

C-MAC Micro Technology has a range of single oven temperature-controlled crystal oscillators. The CFPO-D03 single oven TCXO series is suitable as a frequency source and time keeping reference for all synchronization systems, including GPS based equipment.



The device is designed to provide a holdover performance of better than 7µs over 24 hours in stable ambient conditions and a frequency stability better than 2 x 10⁻¹⁰ peak-to-peak over an operating temperature range from -20 to +70°C. Package size is 51.0 x 41.0 x 19.0mm.
C-MAC Micro Technology
www.cmac.com

Mixed signal test in PC format

National Instruments has announced a suite of 100Msample/s PXI instruments intended for the prototyping and test of mixed-signal devices and systems. It includes 100 and 50MHz digital waveform generator/analysers (NI PX16552 and NI PX16551), a 100Msample/s, 16-bit arbitrary waveform generator (NI PX1-5421), and a 100Msample/s, 14-bit high-resolution digitiser (NI PX1-51220). The modules are designed to be used with the 100MHz clock and frequency generator (NI PXI-5404) and 500MHz switching module (NI PXI-2593) which were announced earlier this year.

Designed to run with the firm's LabView 7 Express graphical development software and the interactive NI Digital Waveform Editor, the instruments will also integrate with third-party software simulation tools, such as standard VCD files from FPGA simulation packages for test execution in LabView, LabWindows/CVI or other development environments. The digitiser, arbitrary waveform generator and digital waveform generator/analysers are built on a synchronisation and memory core architecture developed by the firm for its mixed signal instrument modules. Onboard memory is up to 512Mbyte. In addition, the 5421 arbitrary waveform generator has a close-in spurious free dynamic range of 91dB. The digitisers capture signals with increased fidelity - 64 times the resolution of traditional 8-bit instrumentation, said the company. The digital waveform generator/analysers provide programmable voltage levels from -2.0 to 5.5V with the 10mV resolution necessary for testing devices that use different levels or for characterising how a given device performs under changing conditions.

National Instruments
www.ni.com

Unidirectional pressure transducer

Kulite is offering a unidirectional differential pressure transducer for measuring low differential pressures. This digitally corrected miniature pressure transducer is for use in air speed measurements using pitot tubes. It can also be used for flow measurements. The ET-3DC-312 has a full scale output of 5V DC, with a total error band of 0.5 per cent over 0 to 100°C and a bandwidth from DC to 2.5kHz. The device can withstand 100 per cent relative humidity, a peak linear vibration of 50g (sine 10 to 2,000Hz) and a mechanical shock of 100g. ■
Kulite
www.kulite.co.uk
Tel: +44(0) 1256 461646

Integrated connector modules

Pulse has introduced 12 integrated connector modules, for use in ADSL and cable modems, set-top boxes and video-on-demand equipment.

The modules combine magnetics with the RJ45 connector. The Starjack series is IEEE802.3 compliant and offers AutoMDIX compatibility with four parts



designed for 10baseT applications and eight for 10/100baseTX. The RJ45 module includes an optional resistor capacitor noise cancellation circuit with alternative shield configurations for improving system compliance to worldwide emc standards. The components are offered in single-port (1x1), tabdown configuration with or without LEDs. They are suitable for Cat 5 and 6 Fast Ethernet or UTP cable. The internal magnetics are 100 per cent electrically tested for Hi-Pot and functionality delivering at least 1.5kVrms (typically 2kVrms) isolation and they operate from 0 to 70°C.

Pulse
www.pulseeng.com
Tel: +44(0) 1483 401700

CIRCUIT IDEAS

Fact: most circuit ideas sent to *Electronics World* get published

The best circuit ideas are ones that save time or money, or stimulate the thought process. This includes the odd solution looking for a problem - provided it has a degree of ingenuity. Your submissions are judged mainly on their originality and usefulness. Interesting modifications to existing circuits are strong contenders too - provided that you clearly acknowledge the circuit you have modified. Never send us anything that you believe has been published before though. Don't forget to say why you think your idea is worthy. Clear hand-written notes on paper are a minimum requirement: disks with separate drawing and text files in a popular form are best - but please label the disk clearly. Where software or files are available from us, please email Caroline Fisher with the circuit idea name as the subject.

Send your ideas to: Phil Reed, Highbury Business Communications, Nexus House, Azalea Drive, Swanley, Kent, BR8 8HU
email ewcircuit@highburybiz.com

Simple code lock



This code lock makes use of toggle switches to generate a preset binary code that activates a solenoid to open the lock Fig. 1. The circuit is designed in such a way that any wrong switching will cause interruption of the power supply to the solenoid and will keep it deactivated. For convenience, the switches with their toggles up are assigned binary code '1', while switches with toggles down are assigned binary code '0'.

The '0' (toggle down) and '1' (toggle up) states of these switches are shown in Fig. 2. For switches with toggles up (state 1) to conduct current, terminals b-c are used. For switches, with toggles down (state 0) to conduct current, terminals a-b are used. The central terminals, 'b' of all these switches are connected to + terminal of the DC supply. It can be seen Fig. 1. that in order to energise relay 2, the toggles of the switches number 2, 3, 6, 7, 8 and 10 must be up (binary state 1), and the toggles of the switches number 1, 4, 5 and 9 must be down (binary state 0). With the relay 2 energised, the user's solenoid system is activated to open the lock. If any of these switch(es) is/are in a wrong state, relay 1 is energized and will interrupt the dc supply of relay 2, and the solenoid system is not activated at all.

The code, which I set in my circuit, was 0110011101 as shown in Fig. 1. But re-arranging these switches can set any code. Total combinations of a ten-digit binary code come out to be more than 1000. Each addition of a switch doubles

the number of combinations that could be set and thus, makes it more and more difficult to be assessed by someone else. It is advised to use more switches to make the combination more difficult.

Ejaz ur Rehman
Islamabad
Pakistan

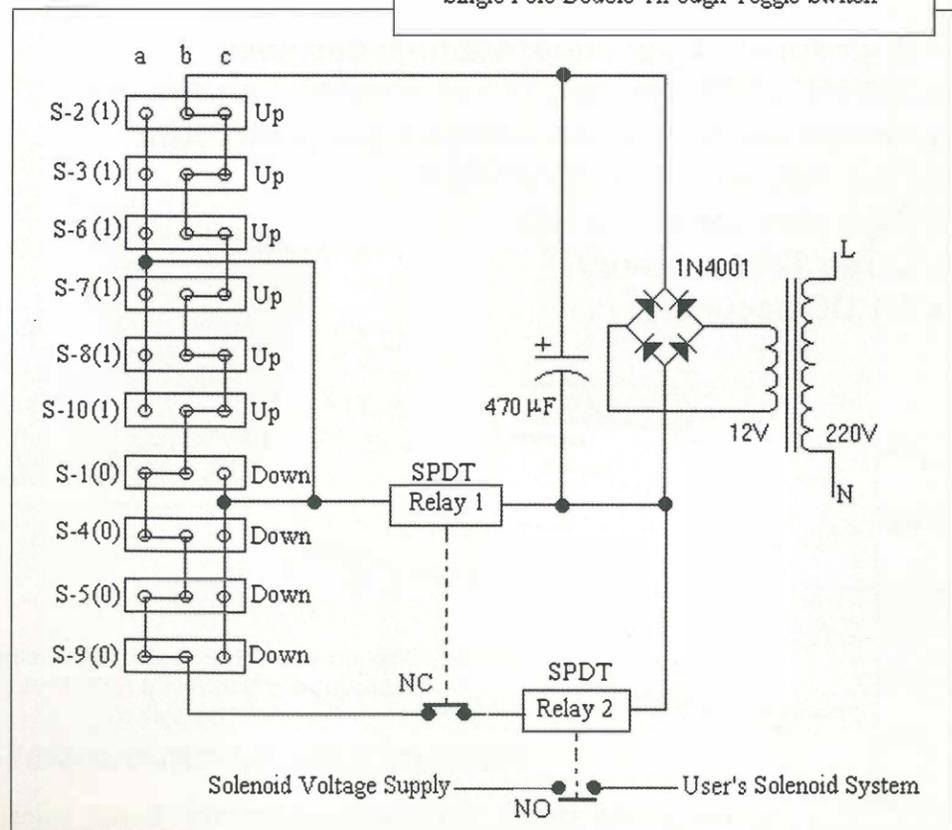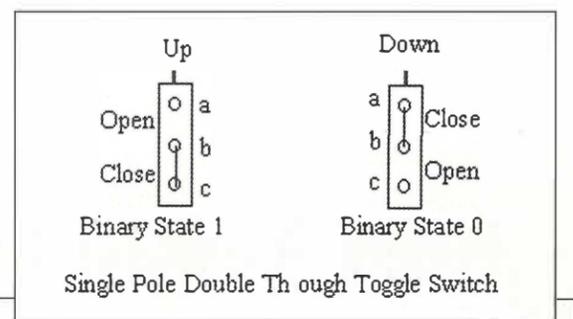

Staircase waveform generator

A 555 timer configured as an astable multivibrator drives the programmable staircase waveform generator shown in Fig. 1. This multivibrator can be reset using switch S₁.

Output from the multivibrator feeds a presetable decade up/down counter through the push switch S₄ and rotary switches S₅ and S₆.

On the 74192 counter, inputs CP_U and CP_D are the clock up and down

inputs respectively. The rotary switches are coupled to ensure that clock pulses feed only one of these inputs at a time. They are wired such that the unused clock input is pulled high.

Counter outputs are Q₀₋₃ and S₂ provides a reset facility. Push switch S₃ is added to allow parallel data to be loaded into the counter inputs D₀₋₃.

Terminal-count outputs TC_U and TC_D are normally high so the monitor

LEDs are off. When the counter is receiving clock pulses via CP_U and the count reaches 9, the TC_U output goes low on the next high-to-low transition of the clock, lighting LED₁. Output TC_U remains low until the CP_U input goes high again. Similarly, LED₂ lights when CP_D is clocked down to zero.


Outputs from the counter feed the decoder shown in Fig. 2. This decoder is configured as an digital-to-analogue converter.

Initially, the op-amps are adjusted for minimum offset. Diode D₁ doesn't start to conduct until its associated output rises above 0.7V. Diodes D₂ and D₃ clamp the output voltage at 1.4V.

The binary-weighted resistors follow the relationship:

$$R_n = \frac{R_f \times V_c}{V_o} = \frac{10k \times 1.4V}{1V} = 14k$$


Gain of the final op-amp can be

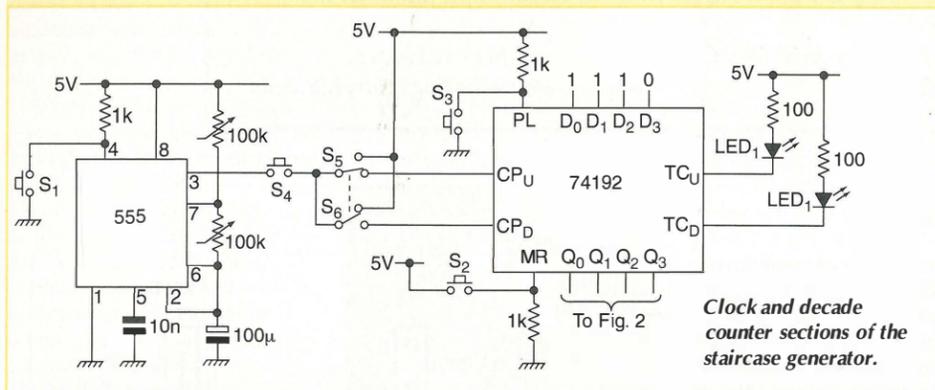

High Resolution PC Oscilloscope

- High speed, 5GS/s dual channel oscilloscope
- 50MHz, 80dB dynamic range spectrum analyser
- PicoScope & PicoLog software supplied FREE
- Plug into any desktop or laptop PC
- High resolution - 12 bits
- Large 128K memory
- 1% DC accuracy

PICO Technology Limited

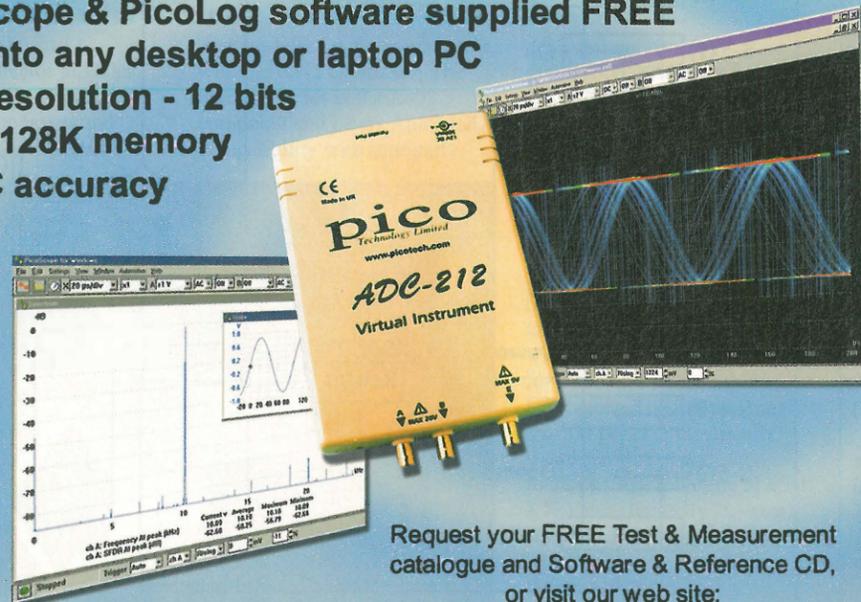

Request your FREE Test & Measurement catalogue and Software & Reference CD, or visit our web site:

www.picotech.com/scope139

Tel: +44 (0) 1480 396395 Fax: +44 (0) 1480 396296 E-mail: sales@picotech.com



NEW
Catalogue
Out Now




adjusted to give the desired staircase characteristic. By using S₃ and loading data into the counter, the output can be made to start from any preset value. The minimum voltage of the staircase can be set using potentiometer Z at the bottom of the resistor ladder.

Figures 3, 4 and 5 show the waveforms created with the components shown. Operation of the D-to-A converter is explained more fully in an article by me in the *Journal of the Instrument Society of India*, Vol. 18, 1988 p. 295. **V. Gopalakrishnan**

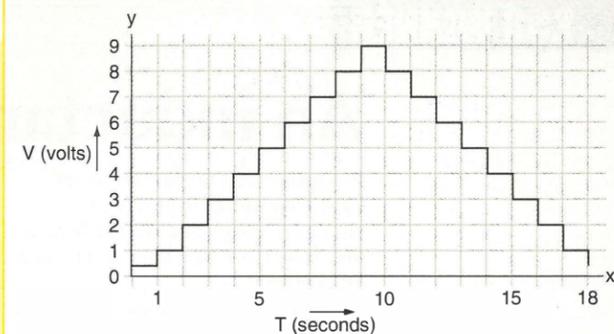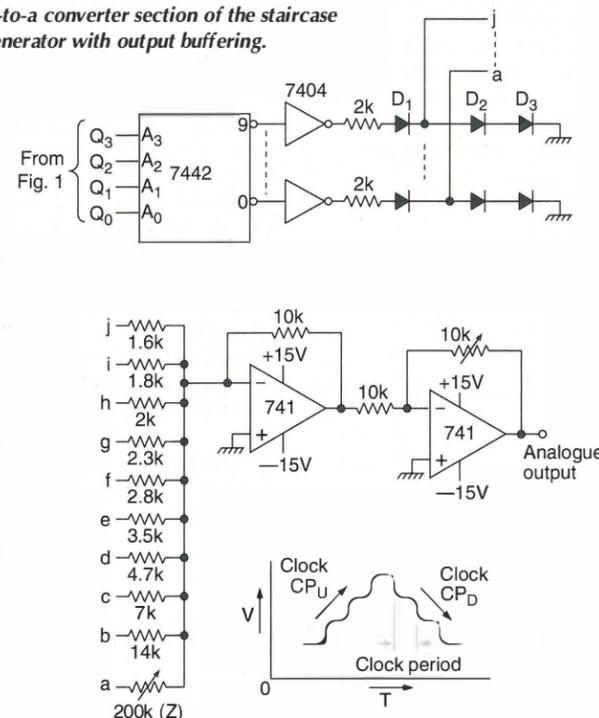
D-to-a converter section of the staircase generator with output buffering.



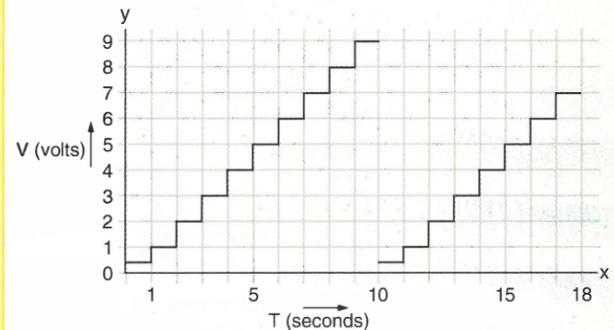Output waveform when the circuit is used for producing a triangular waveform.



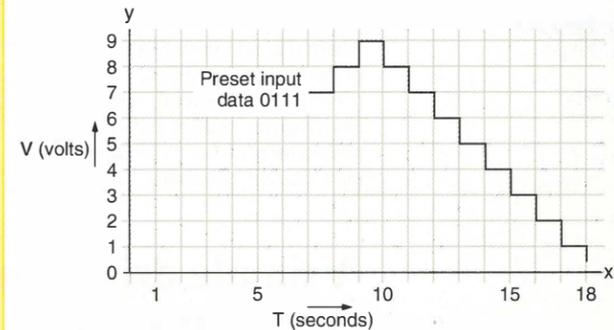Output waveform when the circuit is used as a staircase generator.



By loading the counter with preset data, the ramp can be made to start at any voltage.

Voltage-controlled capacitance/inductance

With a transconductance op-amp such as the XR13600, it is possible to use the transconductance, g, to produce a simulated capacitance or inductance, as shown in the diagram.

Such a circuit can be considered to have three modes of operation. Firstly, with Z₁=R and Z₂=R₁ the output resistance is given by:

$$R_{out} = \frac{R + R_A}{gR_A}$$

With Z₁=R₁ and Z₂→C, the inductance is given by:


$$L_{out} = \frac{CR_1}{g}$$

Finally, with Z₂=R₂ and Z₁→C, the capacitance is given by:

$$C_{out} = gCR_2$$

Here, g=19.2I_B, hence resistance, inductance and capacitance can be controlled by altering only voltage V_B.

Kamil Kraus
Rokycany
Czech Republic

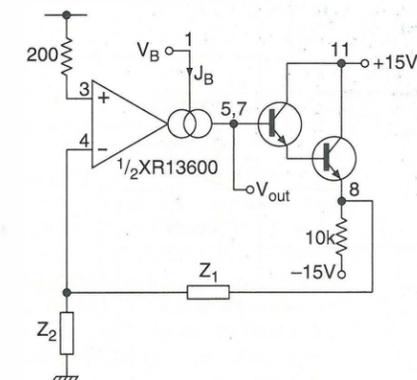

Using a transconductance op-amp, one simple circuit can act as a voltage-controlled resistance, capacitance or inductance.

An inductance multiplier

It is known that the application of large inductances in electronic circuits is always undesirable because they have large size, large weight and large price.

The proposed multiplier of inductance can be used in order to replace a large inductance coil by a small one. The circuit of the multiplier of inductance is shown in

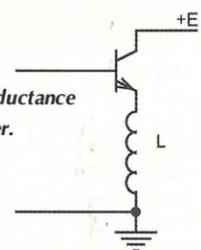


Fig.1. Inductance multiplier.

Fig.1. The equivalent inductance of the circuit is found to be

$$L_{eq} = (\beta + 1) L,$$

where β is the current gain coefficient of the bipolar transistor.

The proposed circuit can be used in low-frequency filters and other arrangements where a large inductance is necessary. For example,

it can be used in a low-frequency oscillatory circuit as it is shown in Fig.2. The oscillatory circuit consists of the 1nF capacitor and the equivalent inductance of the multiplier. The field-effect transistor is used to ensure the necessary bias current of the bipolar transistor. The output incremental resistance of the field-effect transistor is very large, so it does not shunt the circuit. The equivalent inductance of the multiplier is equal to 0.4H in this case, i.e. the equivalent inductance is 400 times larger than the inductance of the applied coil.

The frequency response of the

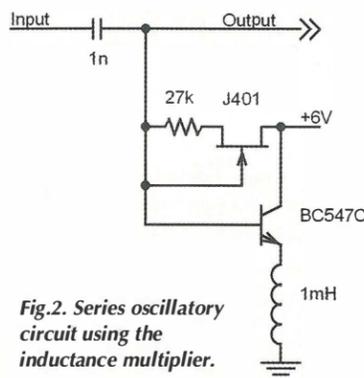


Fig.2. Series oscillatory circuit using the inductance multiplier.


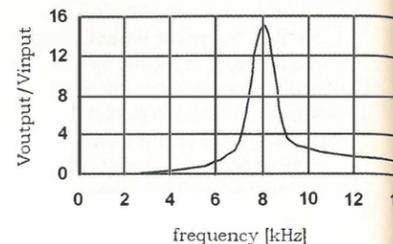


Fig.3. Frequency response of the oscillatory circuit.

oscillatory circuit is shown in Fig.3. It is easy to see that the output AC voltage is 15 times larger than the input AC voltage at the resonance frequency. Consequently the Q-factor is approximately equal to 15. It is also easy to check that the resonance frequency of 8kHz really corresponds to the inductance of 0.4 H and capacitance of 1nF. Therefore the application of the proposed circuit allowed getting a low resonance frequency of the oscillatory circuit without applying a large inductance coil.

S. Chekcheyev
Tiraspol
Moldova
Russia

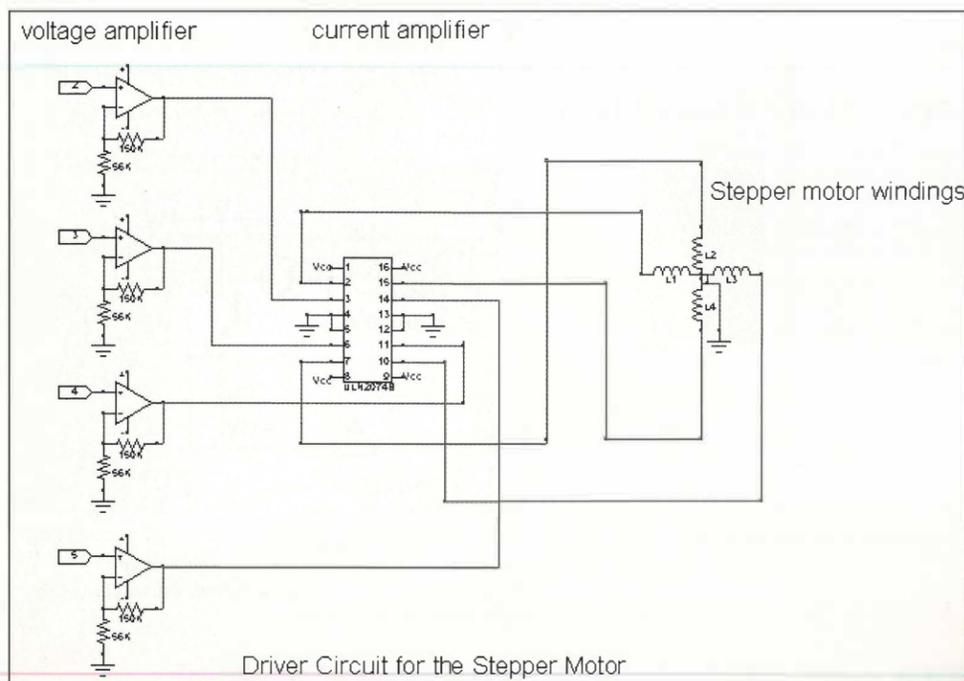A simple driver circuit for stepper motor and its control through a PC



In the circuit shown below a 12V, 1.5A, 10kg - cm torque stepper motor is interfaced to the PC via its parallel port. This is done in order to automate the motion of the stepper motor. This circuit is mainly IC based which makes it easy for construction, has fewer components and is also cost effective.

To move the stepper motor, a proper sequence of output bits from the PC parallel port (25 pin D connector) is obtained. The parallel port consists of 25 pins but we make use of only four data pins (2 to 5) and one ground pin (25) of the port 378 (hex) of LPT1. In the circuit only 4 of the 25 pins are shown. Pin 25, which is grounded, is not shown. For clockwise rotation output bit sequence 0001, 0010, 0100, 1000 is required. The voltage levels corresponding to logic 0 and logic 1 are insufficient for driving this stepper motor and hence need to be amplified. This is done by

Program for continuous rotation

```

/* contin.c */ #include <conio.h> #include <dos.h> void
cdelay(float); void cdelay(float); int a[4] = {1,2,4,8}; main() { int
n; float rpm; int calib = 18750; char ch; clrscr(); printf("\n Enter
speed in RPM ");
scanf("%f",&rpm);
printf("Please select the direction cw/ccw :- ");
ch = getch();
if(ch == 'c')
{
if((rpm >= 0.3) && (rpm < 8))
{cdelay(calib/rpm);}
else if(rpm > 8)
{printf(" Too fast ");}
else if(rpm < 0.3)
{printf(" Too slow ");}
}
else if(ch == 'a')
{
if((rpm >= 0.3) && (rpm < 8))
{cdelay(calib/rpm);}
else if(rpm > 8)
{printf("Too fast");}
else if(rpm < 0.3)
{printf("Too slow");}
}
}
void cdelay(float rpm)
{
int n = 3;
while(!kbhit())
{
outportb(0x378,a[n]);
delay(rpm);
n = n-1;
if(n < 0){n = 3;}
}
}
void ccdelay(float rpm)
{
int n = 0;
while(!kbhit())
{
outportb(0x378,a[n]);
delay(rpm);
n = n+1;
if(n > 3){n = 0;}
}
}

```

Program for Stepwise Movement

```

/* handcrl.c */
#include <conio.h>
#include <dos.h>
main()
{
char key, key1;
int a[4] = {1,2,4,8};
int i = 0;
while( (key = getch()) != '\r')
{
if(key == 0)
{
key1 = getch();
if(key1 == 72) /* extended code for up arrow key */
{
outportb(0x378,a[i]);
i = i+1;
if(i > 3)
{i = 0;}
}
else if(key1 == 80) /* extended code for down arrow
key */
{
if(i < 0)
{i = 3;}
outportb(0x378,a[i]);
i = i-1;
}
}
}
}

```

configuring the op-amps (741) in the non-inverting mode to provide a gain ~4. In the circuit diagram the power supply connections for the op-amp are not shown i.e. Vcc = +12V, Vee = -12V. The IC ULN2074B (Vcc +12V), a darlington transistor array, is used for current amplification.

The IC pins 4, 5, 12, 13 are connected to a heat sink and grounded. The voltage pulses obtained from this IC are then used to drive the stepper motor. Two programs in 'C' language control the

stepper motor. The first program (contin.c) is used when the motor needs to be continuously rotated and the second program (handcrl.c) moves the motor in a step-by-step manner. In the first program the motor can be moved at user selected speeds between 0.3 - 8.0rpm. The direction of motion, clockwise/counter clockwise is also user selectable by pressing the 'c'/'a' keys when prompted by the program. The calibration factor declared as a variable 'calib = 18750' in this

program is used to calibrate the speed of the stepper motor. This calibration factor may vary from PC to PC and needs to be determined before using the program. In the handcrl.c program the up arrow and the down arrow keys are used to rotate the motor in the counterclockwise or clockwise direction respectively, the motor moves by one step by pressing the key once.
S. Tauro, M.A.N. Razvi
Mumbai
India

A fast accurate differentiator

Op-amp based differentiators have a number of problems such as high output noise, ringing and instability, and severely limited speed of operation due to the finite open loop bandwidth of the op-amp. These limitations have effectively excluded their use in fast instrumentation and measurement systems.

The active differentiator circuit shown in Fig. 1, is inherently stable, has very low output noise and can deal with input signal slew rates up to about 1000V/μs with high accuracy and even beyond 5000V/μs with reduced accuracy. Fig. 2. shows the performance of the circuit. For the slew rate tests above 2000V/μs, the power supply voltages were increased from those shown in the circuit.

Q1 forms an emitter follower to buffer the input and to provide a low impedance source to the capacitor, C1. Q2 and R3 act as a current to voltage converter. The relatively high standing current in Q2 gives it an emitter input impedance of about 1.4 ohm, so most of the capacitor current flows into Q2 emitter with only a small amount flowing through R2. This common base stage Q2 gives very fast response to capacitor current changes. The 50 ohm collector output resistor, R3, was chosen to match a 50 ohm

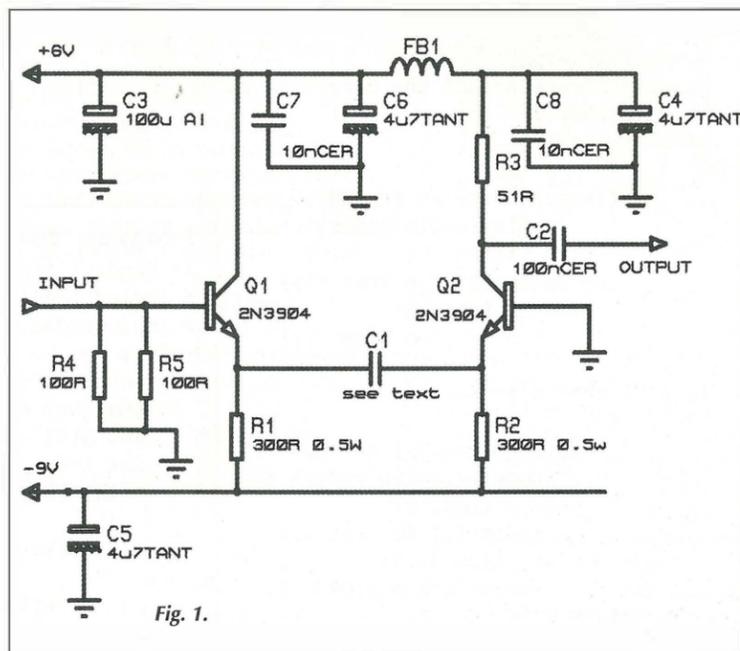


Fig. 1.

system for high-speed work, but could be made higher to achieve a larger output with only a small effect on speed performance.

The circuit output is given by

$$V_o = R3 * C1 * \text{Input slew rate}$$

Where the input slew rate is in V/s. The output is a scaled version of the

true differential of the input signal. For input signal slew rates of up to 25 V/μs, C1 should be about 1000pF. For slew rates greater than this, C1 should be reduced to ensure that Q1 can provide sufficient current into the capacitor without loading the source too much.


As the circuit does not rely on a high gain amplifier for its operation, output noise is very low. With the capacitor value at 1000pF, the 'no signal' output noise is less than 1mV peak to peak measured with a 350MHz scope.

It should be noted that, in contrast with RC passive differentiators, the circuit's output response is related to the actual differential of the input waveform. This means that the circuit can be used to measure accurately the linearity of ramp waveforms or observe small rapid changes in signals. With small values of C1, it can be used to generate very fast rise (~1ns), short duration pulses from slower input signals.

For good high frequency performance the circuit should be constructed using RF techniques on a ground plane. As the output is taken effectively across R3, the circuit is sensitive to noise on the positive supply rail and so it should be very well decoupled as indicated.

Alan Lloyd
Upton
Chester
UK

Fig. 2. Measured performance of differentiator.

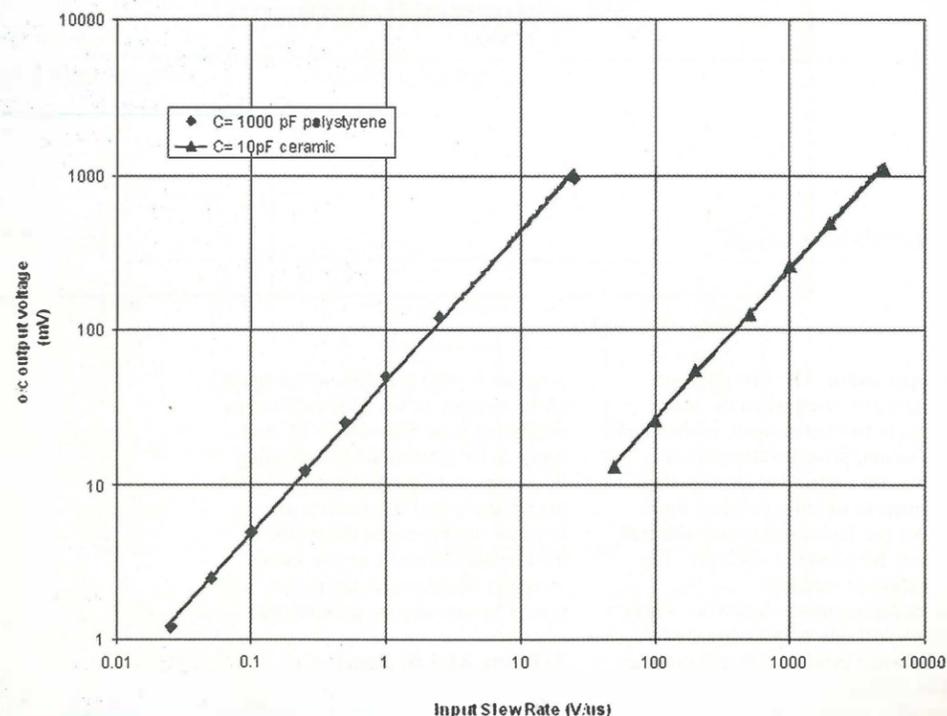

Unusual application of comparators as excellent high speed linear amplifiers

A comparator is essentially a high gain, high slew rate amplifier with excellent offset and drift characteristics. An internal compensating capacitor is not provided at the manufacturing stage to significantly improve the requirement of slew rate.

The comparator is an element of pulse width modulator, peak detector, delay generator, switch drivers, A/D converters etc. However one might not have seen the comparator being used as linear amplifier with excellent high frequency and good output drive capability.

In order to use the comparator as an op-amp, one has to externally provide the frequency compensation and choose the appropriate value of open collector pull up resistor.

The LM139/LM239 being the most popular and easy to use quad comparator, is chosen to show how it can be configured as a non-inverting amplifier. Similarly the LM111/LM211, another precision popular comparator, is used to show how it can be configured as an inverting amplifier. Standard connections are shown in Fig. 1. and Fig. 2.

Comparators do not have internal provisions for compensation by external components; therefore compensation must be applied externally at the input of the device. The R1, C1 network provides the external frequency compensation at the input. A small value of C2 is introduced across R3 to prevent very high frequency oscillation and to reduce the gain of the amplifier outside the frequency range of interest.

The feed back network R3 & R2 sets the closed loop gain at 1+R3/R2 in the case of a non-inverting amplifier and at -R3/R2 in the case of an inverting amplifier as shown in the Figs 1 & 2 respectively. For the values indicated the closed loop gain works out to 5 for both of the circuits.

The value of R4 tied to the +15V supply, not only affects the positive swing, but also the drive (current sourcing) capability. The higher the value of R4, the lesser the positive swing and the lesser the output drive capability. Therefore it is suggested

to use $R4 \leq 820$ ohms, so that the output can have a maximum linear swing of + or -13V when operated at + or -15V.

The circuits work very well both for low and high level signal. The amplifiers even respond linearly to a

square wave input of up to 100kHz easily and can safely drive a load greater than or equal to 2K at + or -13V.

V.Manoharan
Kerala
India

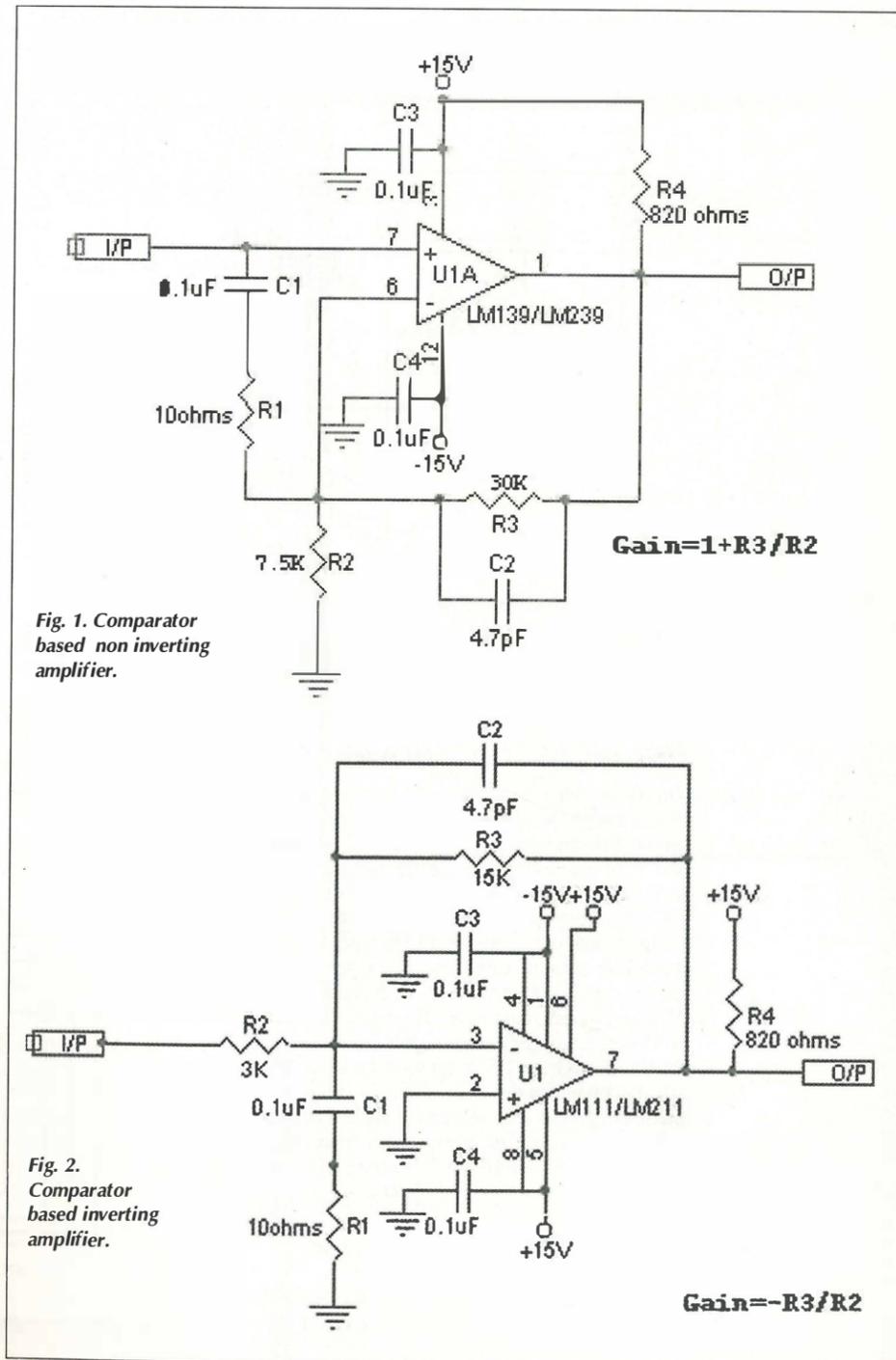


Fig. 1. Comparator based non inverting amplifier.

Fig. 2. Comparator based inverting amplifier.

Cut relay power to a quarter

Electro-mechanical relays are cheap and easy to use but unfortunately waste a large amount of power in their coil. Because of the magnetic hysteresis, the full drive voltage must be applied to excite the relay but only one half of this voltage is needed to keep it held.


The circuit shown takes advantage of this property and has been designed to fulfil the requirements of various supply voltages and control

polarities (figure a = positive control, figure b = negative control). V_{cc} is the supply voltage and the relay has an operating voltage of $2V_{cc}$. In the OFF state, capacitor C1 is charged to V_{cc} through D1, R1 and the conducting Mosfet (Tr1 at fig. a, Tr2 at fig. b). When switching to the ON state, Mosfets commute so that C1 is connected in series with the supply and the voltage across the coil rises to $2V_{cc}$ for a few milliseconds. When

C1 is discharged, the coil voltage drops to V_{cc} thus reducing the power consumption.

Relay's specifications exhibit a coil resistance that is about four times higher when the operating voltage is double (FINDER: $55\Omega@6V$, $220\Omega@12V$, $900\Omega@24V$) hence the power is cut to a quarter.

Paul GELINEAU
Mazières-en-Mauges
France

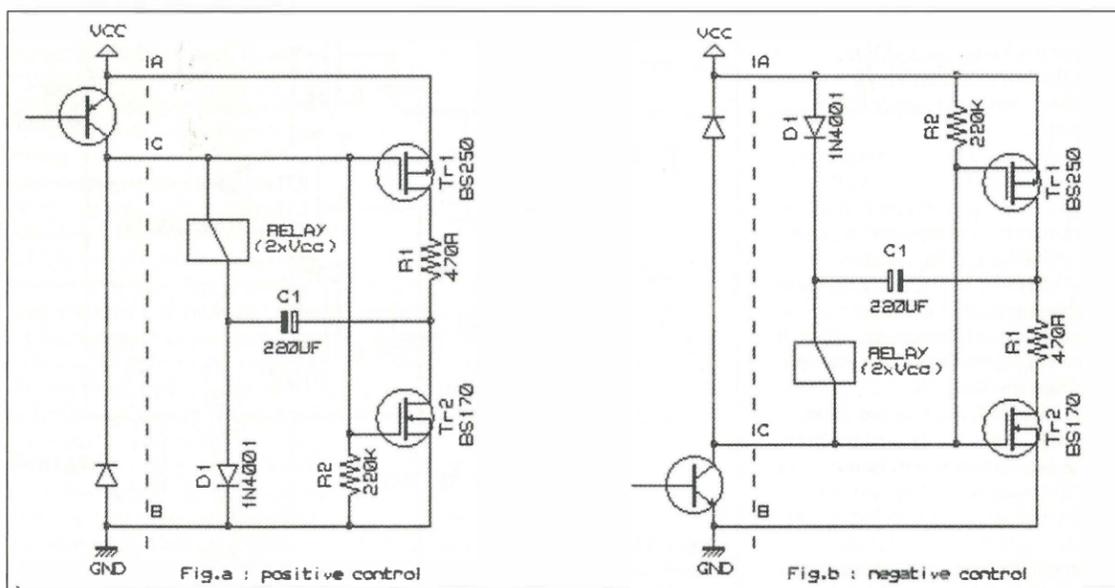


'None of the Above' decoder

This circuit idea can save a gate or two, which may help a design 'just fit' in available resources. It relies on the difference between V_{OL} (or V_{sat}) of the drivers and V_f of the diode being greater than the difference in V_f of an "on" and an "off" LED. Most individual LEDs go from dark to bright within 500mV, but there is significant V_f variation between types and colours, so beware when mixing them. The schematic shows the idea applied to turn a 1-of-10 decoder into a 1-of-12 with just one more gate. Of course, the same idea works for fewer (or more) outputs, such as Red/Yellow/Green LEDs for model traffic lights, or a standby/on indicator (a neat use for a common-anode bicolour LED, if only somebody made them!)

By the way, does anyone else remember destroying early Nixie decoder/drivers by turning all the outputs off?

Peter Horn
By email

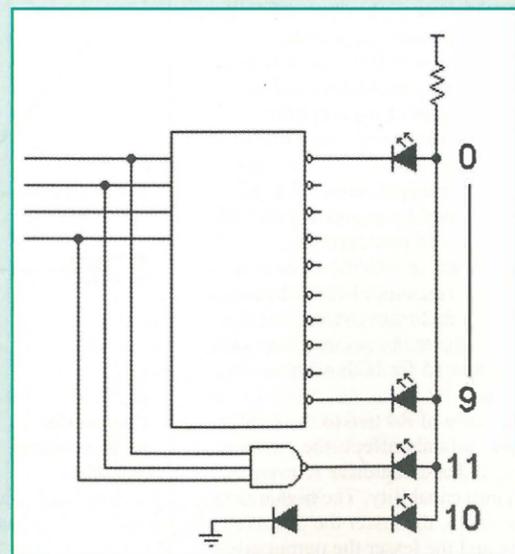

Electronics World reader offer:
x1, x10 switchable
oscilloscope probes,
only £21.74 a pair,
fully inclusive*

*Additional pairs as part of the same order, only £19.24 each pair.

Seen on sale for £20 each, these high-quality oscilloscope probe sets comprise:

- two x1, x10 switchable probe bodies
- two insulating tips
- two IC tips and two sprung hooks
- trimming tools

There's also two BNC adaptors for using the cables as 1.5m-long BNC-to-BNC links. Each probe has its own storage wallet.

To order your pair of probes, send the coupon together with £21.74 UK/Europe to **Probe Offer, Jackie Lowe, Highbury Business Communications, Nexus House, Azalea Drive, BR8 8HU**

Readers outside Europe, please add £2.50 to your order.

Specifications

Switch position 1	
Bandwidth	DC to 10MHz
Input resistance	1MΩ - i.e. oscilloscope i/p
Input capacitance	40pF+oscilloscope capacitance
Working voltage	600V DC or pk-pk AC
Switch position 2	
Bandwidth	DC to 150MHz
Rise time	2.4ns
Input resistance	10MΩ ±1% if oscilloscope i/p is 1MΩ
Input capacitance	12pF if oscilloscope i/p is 20pF
Compensation range	10-60pF
Working voltage	600V DC or pk-pk AC

Switch position 'Ref'
Probe tip grounded via 9MΩ, scope i/p grounded

Please supply the following:

Probes

Total _____

Name _____

Address _____

Postcode _____ Telephone _____

Method of payment (please circle)

Cheques should be made payable to Electronics World

Access/Mastercard/Visa/Cheque/PO

Credit card no. _____

Card expiry date _____ Signed _____

Please allow up to 28 days for delivery

Op-Amp and resistor distortions

In the last article of this series, Cyril Bateman uses his real-time distortion measuring system to explore means to reduce distortions in IC op-amp circuits and investigates distortions in resistors and potentiometers

Having completed the design for my very low distortion fixed output oscillator, part of the equipment for my original *Capacitor Sounds* series, I needed to provide a variable level output, able to develop an undistorted 6V test signal across my near perfect 1 μ F reference capacitor. My original potentiometer and non-inverting unity gain output amplifier design distorted badly driving a 3V signal into a 600 Ω resistive load. This problem was solved by using an NE5534AN op-amp as a variable gain inverting amplifier, with a 15.4k Ω input resistor and a 25k Ω conductive plastic potentiometer for feedback. This inverting, variable gain output stage and potentiometer,

added almost no measurable distortion driving a 600 Ω resistive load, but did distort with a capacitive load.

Clearly for my capacitor measurements, I needed to design a very low distortion, more powerful, buffer output stage. Searching my bookshelves and back issues of *Electronics World* I found nothing, but on the internet I found a short series of articles by Walt Jung, "Op-Amp Audio" originally published in the US magazine *Electronic Design* from September to December 1998¹. In this he suggests using a gain stage and separate output buffer. Apparently he had successfully used the Analog Devices AD811AN, a current feedback video amplifier, as an audio output buffer. Using an OPA134 gain stage with this AD811AN output, I could develop an undistorted 6V signal at 1kHz across my near perfect 1 μ F reference capacitor from a 100 Ω source impedance.

A similar test signal at 100Hz across larger capacitors needed more current than the AD811AN could provide. Further searching found a novel circuit for an exceptionally accurate, active feedback amplifier developed as input buffer for a 16 bit ADC, in *Electronic Design* April 2001². A similar arrangement could drive the more powerful output stage needed for my 100Hz test equipment³. Then, whilst busy developing circuits and measuring capacitor distortions, time did not permit exploring these solutions in more detail for general use. Now two years later, using my standalone distortion tester⁴, I could at last begin. Fig. 1

Active Feedback Amplifier

Many low level audio systems use unity gain, voltage following ICs as buffers between stages, it being often claimed such circuits can output up to 10V AC using ± 15 V supply rails, but measurable distortions are produced with much smaller signals. This novel active feedback amplifier, developed as a 16 bit input buffer, used both sections of a dual op-amp, the first amplifier section to drive the load as usual, the second stage to provide distortion cancelling active feedback instead of the usual feedback resistor. The idea being that having two errors of equal value but opposite sign, the feedback signal error would cancel the forward gain error². Fig. 2

Initial tests measuring the input-output voltage differential of an AD712JN using my differential scope probe⁵ confirmed that this arrangement did reduce errors. Intended for use as a unity gain buffer, I wondered whether it could

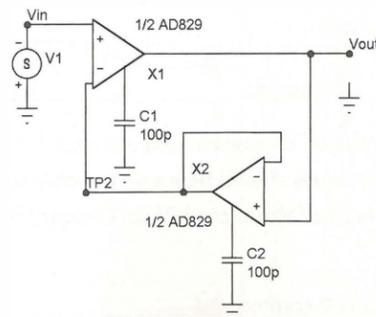


Fig. 2. The schematic from the "Active Feedback Amplifier Enables High-Performance A-to-D Conversion" article² found while accessing the *Electronic Design* web site.

be adapted for use in the gain of two buffer I now needed. A few initial measurements confirmed this arrangement could provide gain and improve performance. Initially it seemed an almost ideal distortion reducing panacea, except that some ICs I tried did not work at all well in my gain of two circuit.

Op-Amp distortion tests

Most op-amps provide very large open loop gain, typically 100dB at low frequency, allowing use of substantial feedback to reduce distortion. However this gain reduces rapidly with frequency such that by 1kHz, the open loop gain has reduced by 20dB and output distortion is increasing. With small audio signals and light loading this may not present a problem but with increasing amplitude and heavier circuit loading, problems do emerge. Capacitance to ground compounds these difficulties and can even result in oscillations.

The 'direct' input to my notch filter presents a high resistance in parallel with a 10.2nF capacitance, which with the 600 Ω to ground in my test PCB⁶ provides a difficult 575 Ω and parallel 10.2nF test load, exceeding that expected in an audio circuit. I decided to use this load to explore how popular audio op-amps behaved. Would using the second stage of a dual IC as an output buffer or the Walt Jung external buffer permit larger amplitude undistorted signals? To make certain of a stable performance at all signal levels, I decided to use my test PCB to measure distortion with a 1V test signal, then increase the signal in 1V steps to 6V or until the amplifier distorted. Fig. 3.

Single Amplifier circuit

For many years the TL072CP, MC4558TPI and NE5532AN dual amplifier ICs have been used in audio systems. With a DIL header to bypass U8 and taking the output from U7A using one half of a TL072CP, its unloaded second section simply voltage following the first section's output, I wanted to see what low distortion signals with a gain of two, could be driven into my test load. Fig. 4.

The other two ICs worked rather better, the MC4558TPI producing 0.00228% distortion at 4V, but the NE5532AN was seven times better, just 0.00032% distortion driving a 4V signal into this difficult test load, the best of these older op-amps. From earlier measurements I already knew the expensive AD797 could provide large amplitude low distortion

signals, so for this article I wanted to explore less exotic devices.

To minimise distortion with any IC it is essential to match as closely as possible the impedances 'seen' at its inverting and non-inverting inputs, otherwise, as explained in the Walt Jung papers, it will generate increased second harmonic distortion. The AD797 is able to produce exceptionally low distortion, but is sensitive to small impedance differences between its inverting and non-inverting inputs.

Although not claiming any particular distortion performance, in the past I found the BiFET AD712JN behaved well when driving adverse loads. Tested as above I measured 0.00162% distortion, rather better than the MC4558TPI and TL072CP but worse than the NE5532AN. A

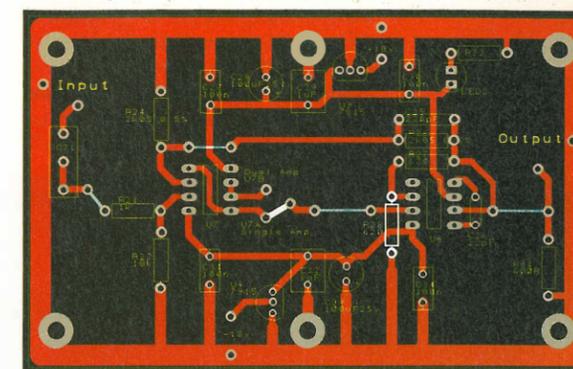


Fig. 3. The test PCB and component values used for this article. The link which changes from measuring the 'single' to 'dual' configurations is highlighted in white. Resistor R2B, highlighted in white, must be removed when using an NE5534AN or similar amplifier also the DIL header for U8. With a current feedback AD811AN for U8, resistor R2B is required, so should be refitted.

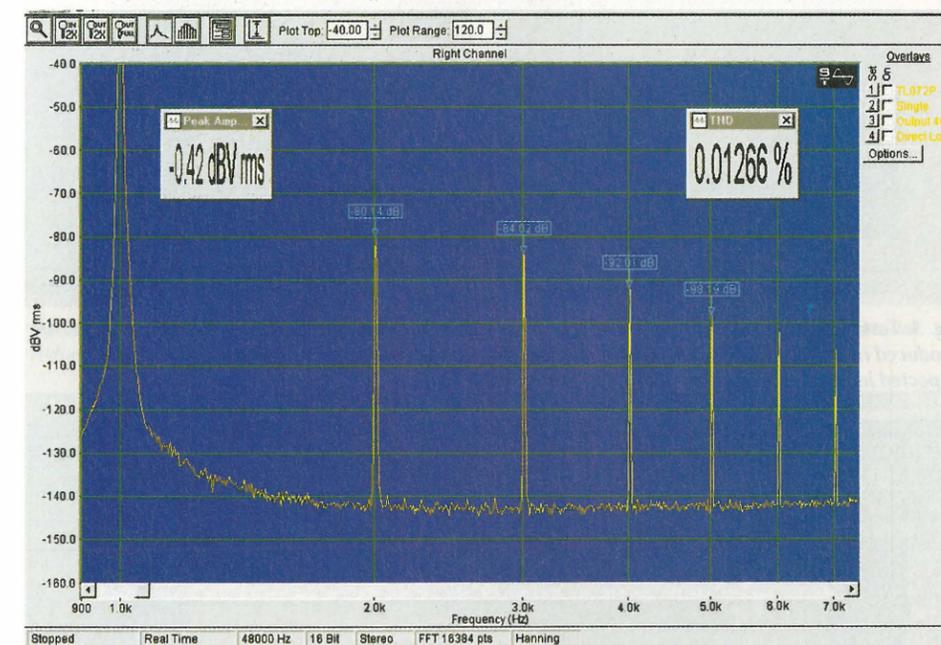


Fig. 4. Single amplifier distortion measured using the 'A' section of a TL072CP driving into my 575 Ω 10.2nF test load. For this IC the 4V nominal test voltage had to be reduced to 3.8V.

JFET input TLE2072CP measured 0.00142%, much better than the old TL072CP and slightly better than the AD712JN while an OP275G with its Butler Bi-polar/JFET input stage, intended for audio circuits, measured 0.00088% distortion. The Burr Brown FET input OPA2134CPA, part of their 'SoundPlus' range designed for low distortion audio, measured 0.00036% to equal the NE5532AN performance. Fig. 5.

Dual Amplifier

Having established a distortion baseline for a single stage amplifier driving 4V into my test load, would a gain of two version of the dual amplifier active feedback design, with output now taken from U7B, work any better? The heavy output

currents would be removed from the input gain stage, but being in the one package, would thermal or capacitive feedback present new problems, increase distortions or even result in oscillation?

I decided to start by trying the worst performing of the above amplifiers, for that should more clearly show any improvement, as reduced distortion or increased drive level. The TL072CP in this 'dual' arrangement could not provide increased drive, but distortion at 4V output reduced dramatically from 0.01266% to 0.00041%, almost equalling the best of the dedicated 600 Ω capable audio op-amps. Fig. 6. With such a dramatic improvement, I wondered how the other op-amps would perform using this circuit and

components by simply plugging in a different IC. Strangely the MC4558TPI, which had easily outperformed the TL072CP in my first tests, also improved but by a far smaller margin, from 0.00228% as a

single stage to 0.00062% in this dual circuit. However, this IC could now almost drive a low distortion 5V signal into my load.

The NE5532AN also improved from its original, equal best single stage

performance, to an amazing 0.00022% at 4V, almost halving the best single stage results. In addition it could now easily drive a full 5V low distortion signal into my test load. In like fashion the AD712JN also could drive a 5V signal at 0.00073% and a 4V signal with just 0.00032% distortion. **Fig. 7.** Whether a feature of the op-amps themselves or my test circuit, the TLE2072CP, OPA2134CPA and OP275G were unusable in this configuration, so after all it has failed to become the hoped for universal palliative. Exactly why some ICs performed so well in this circuit and others were unusable is not clear.

Perhaps using an external load bearing buffer op-amp as proposed by Walt Jung would work better. This two IC arrangement is more expensive and requires larger printed board area, but in small quantities it could prove less expensive than using say a single AD797. I decided to explore this option, using the identical test set up, test load and PCB test circuit by replacing the bypass DIL header with an IC. I knew the AD811AN worked well in this circuit position, but how would an NE5534AN perform?

Two amplifiers

Starting with a 1V test signal and increasing in 1V steps as before, I tried an NE5534AN as the output stage with various amplifier gain stages. With R28 removed, the NE5534AN output stage works as a unity gain voltage follower. Taking the output once more from U7A, the 'A' section of the first op-amp provided the gain of two. Its unloaded second section following the first section output but was otherwise inactive. Using the NE5532AN as the first amplifier, at each test voltage significantly less distortion was measured compared with the same NE5532AN used alone, whether as a single amplifier or in my dual configuration. Furthermore, with the drive signal into my test load increased to 6V I measured just 0.00017% distortion. At all lower test voltages, a similar or slightly lower distortion was measured, an amazing result. Clearly removing the output stage's thermally conducted heat from the gain stage was beneficial in reducing distortion. **Fig. 8.**

Even more amazing was that the TL072CP, which had performed less well on its own, with the NE5534AN output, was able to drive a 5V signal with only 0.00044% distortion, into the test load. The MC4558TPI also improved and was able to drive a 6V signal at 0.00031%. With this success I decided to refit R28 so I could use an

AD811AN output buffer to compare directly with these NE5534AN results.

The NE5532AN which had worked so well with the NE5534AN output buffer, partnered now with the AD811AN generated 0.00308%, ten

times more distortion than when measured as a single amplifier. Since this was the last but one combination of those tested and the final combination worked perfectly, this distortion must result from a

particularly unhappy combination of IC and test load characteristics. However, all other combinations I tried worked extremely well with this AD811AN and 5V output. The TL072CP improved to 0.00022%

Technical support

Full details of the 'Real Time' hardware test method and my original *Capacitor Sounds* low distortion oscillator, buffer amplifier, notch filter/pre-amplifier and DC bias assemblies, complete with parts lists, assembly manuals and full size printed circuit board drawings as .PDF files arranged for easy viewing of the figures, on screen or hardcopy, are provided in my CD.

This CD includes updated and much expanded re-writes with very many more figures, of my first series *Capacitor Sounds* articles, supported now by some ninety capacitor distortion measurement plots as well as all six articles from this new *Capacitor Sounds II* series.

Also included are PDF re-writes of my earlier *Understand Capacitors* series together with articles on how to diagnose failed printed board mounted capacitors and essential low cost capacitor measurement methods, more than twenty popular articles.

This final version of my CD, now with 'artwork' label, costs £15 Sterling inclusive of post & packing.

Readers who purchased an earlier CD, can now upgrade to this version for £5 Sterling, inclusive.

I can still supply sets of three professionally manufactured printed circuit boards, FR4 with legend and solder resist, also four gang potentiometers, as described in my original *Capacitor Sounds* articles.

One set of boards costs £27.50 but due to weight, post and packing is extra.

Four gang potentiometer if ordered together with PCBs costs £5.00.

Post packing UK and EU: £3.50
Rest of World: £7.50

Send cheques or postal/money orders in pounds Sterling only to:-

C. Bateman.
'Nimrod' New Road.
ACLE. Norfolk.
NR13 3BD.
England.

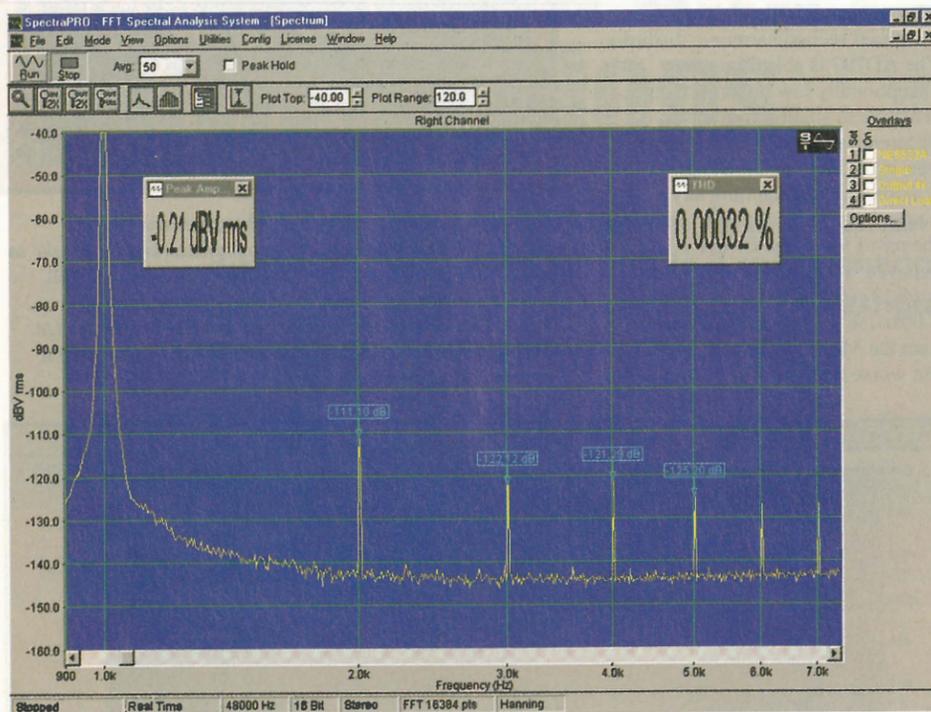


Fig. 5. Tested at 4V output, but otherwise exactly as Figure 4, this 'single' amplifier test of an NE5532AN produced remarkably little distortion driving this difficult test load, a heavier load than would be expected in any real world circuit or interconnect cable loading.

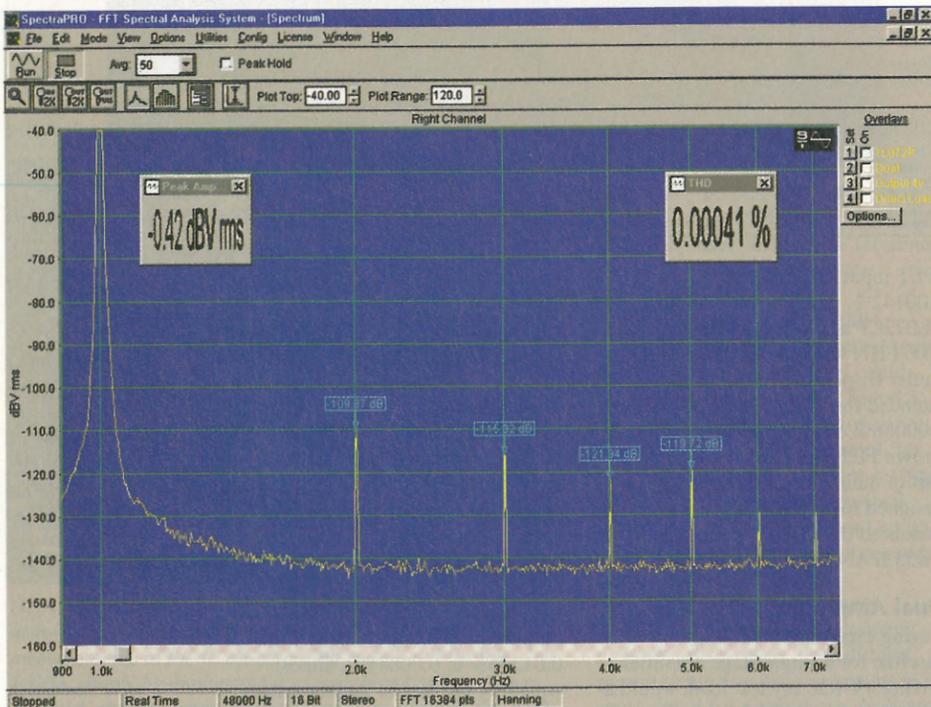


Fig. 6. The TL072CP of Figure 4, tested in the 'dual' amplifier circuit using its 'A' half for gain and 'B' half as a voltage follower driving the test load. Distortion has dramatically reduced from 0.01266% to 0.00041%.

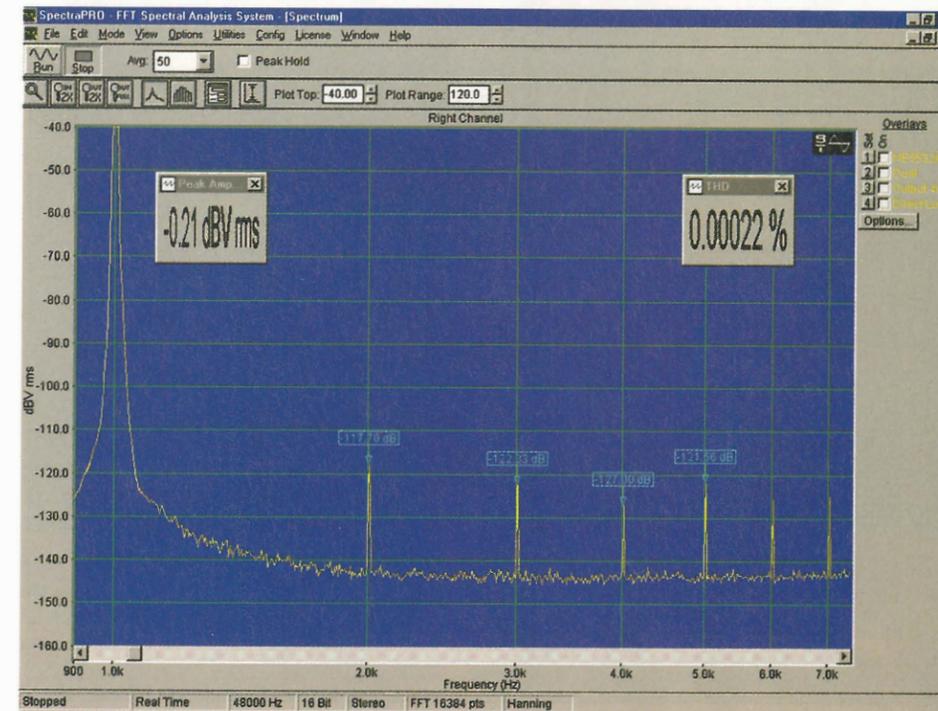


Fig. 7. Retesting the Figure 5 NE5532AN in the 'dual' amplifier test circuit as Figure 6, distortion has reduced again to 0.00022%, 50% less than the best 'single' amplifier of those tested

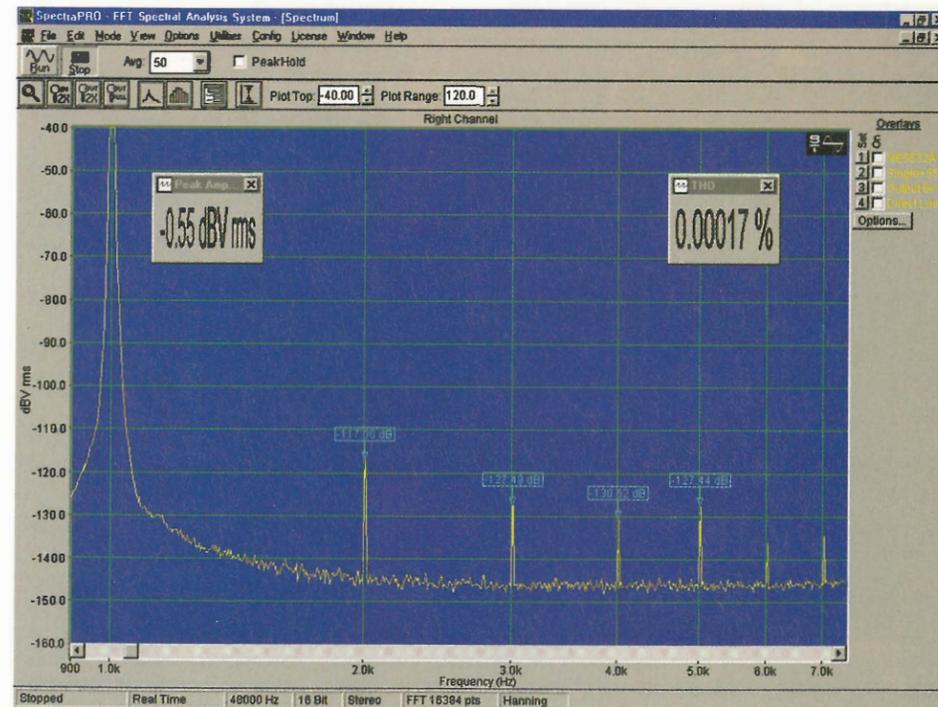


Fig. 8. Removing the DIL header and R28 to use two separate ICs rather than the 'dual' arrangement of Figures 6 & 7. Retesting the Figure 5 NE5532AN 'A' section with an NE5534AN for U8 removed the test load thermal effects, reducing distortion to just 0.00017%, halving that measured with the best performing 'single' IC

distortion, half that found when this IC was used with an NE5534AN. The OP275G and MC4558TPI improved more to 0.00016% and 0.00014% distortion respectively. Best of all, the OPA2134CPA with this AD811AN output, measured a remarkable 0.00010% at 5V output and could even

manage 0.00011% distortion at 6V output, approaching the distortion measuring limit of my equipment. **Fig. 9.**

Op-Amps - Conclusions

Clearly, while the dual amplifier arrangement worked well, following the Walt Jung advice¹ to physically

separate the gain and output driver stages can produce exceptionally low distortion figures into an adverse load, for many perhaps most combinations of gain and driver ICs.

Resistors

Many readers have written requesting advice about the resistor distortions, much publicised in magazines and internet discussion groups and based on subjective tests, not measurements. They were concerned about voltage and temperature coefficients and the effect of magnetic and non-magnetic leadwires.

I believe distortion from carbon composition and to a lesser extent carbon film resistors can be a problem, but expected modern laser spiralled 1% metal film resistors would not produce any measurable distortion with my equipment. Today no sensible audio design would use carbon composition or carbon film resistors.

Every resistor exhibits a temperature coefficient and a very small voltage coefficient, specified according to international standards and test methods. BS and CECC specifications demand 'true values', so test instrument uncertainties must be added to the component's measured values in any published claim. Consequently a resistor specified as 50ppm temperature coefficient, may in practise exhibit less than 30ppm deviation.

In circuit, resistor body core temperature will increase above local ambient according to the power dissipated. The body temperature of a typical 0.25W resistor with 25% rated loading, increases some 6°C above local ambient, but temperature coefficient with a steady temperature rise does not produce distortion. To generate distortion with an AC signal, resistor core temperature must track the AC signal. Every resistor has some mass and thermal inertia so its core temperature cannot instantly change. Metal film resistor temperature and voltage coefficients with modest AC signal loading generate little or no measurable second harmonic distortion, even with low frequency signals.

In past years when 5% carbon film resistors were standard, miniature high speed grinding wheels were used to cut a groove in the resistive film, to trim to value. The resultant spiral cut through the resistive element, into the surface of the exceptionally hard resistor core, usually had ragged edges and varying width. In places a poor grind could leave minute semi-conducting bridges across the cut, resulting in increased third harmonic distortion. Today 1%

tolerances require laser cutting equipment. Lasers cut clean, consistent, spirals, virtually eliminating this source of distortion.

The termination between lead wire and resistor element for almost all low wattage resistors relies on a pressure contact between the end cap and the resistor element. Unless adequate contact can be assured after soldering the resistor into circuit, this presents a potential source of third harmonic distortion. Some audio specialist companies have used non-magnetic end caps to counter the 'magnetic' discussions. To maximise the contact pressure it is essential the thermal expansion coefficients of end cap and resistor body are matched using a high tensile strength, elastic metal. For these reasons I prefer to use plated steel end capped resistors with tinned copper leadwires, believing any magnetic field effects due to the tiny currents in most resistors, flowing through this end cap, are preferable to third harmonic distortion from poor end contact pressure. My equipment can only stress a resistor to some 6V and read distortions above -120dB. To stand any chance of realistically measuring distortions in 1% metal film resistors, much larger pure test voltages, loading the resistor to perhaps 50% power and measurements down to -135dB or better are needed.

I no longer have any carbon composition resistors but do have a number of 20 year old, ground spiral, carbon film resistors. I decided to see whether my test equipment might find these produced more distortion than modern low cost 1% metal film types. Using a 6V test signal, I measured some 56kΩ with 1kΩ source impedance, 5.6kΩ also using 1kΩ source and finally some 560Ω resistors using 100Ω sources. Naturally resistor current through the 56kΩ parts was minuscule so it was no surprise to find all types, carbon film and metal film measured almost identically, near my equipment's basic distortion.

At 5.6kΩ I found one particular carbon film resistor measured 0.00011% compared with the metal film types at 0.00007%. At 560Ω, because the resistors were passing 10mA through current and dissipating 65mW, larger differences were noticed. I now found two carbon film resistors measuring increased distortion. One, a quarter watt part measured 0.00013% and a half watt 0.00010%. In comparison low cost 1% metal film resistors measured 0.00007% as did a 0.5% Welwyn RC55, near the baseline distortion of my equipment, at these settings.

Second harmonic for all four

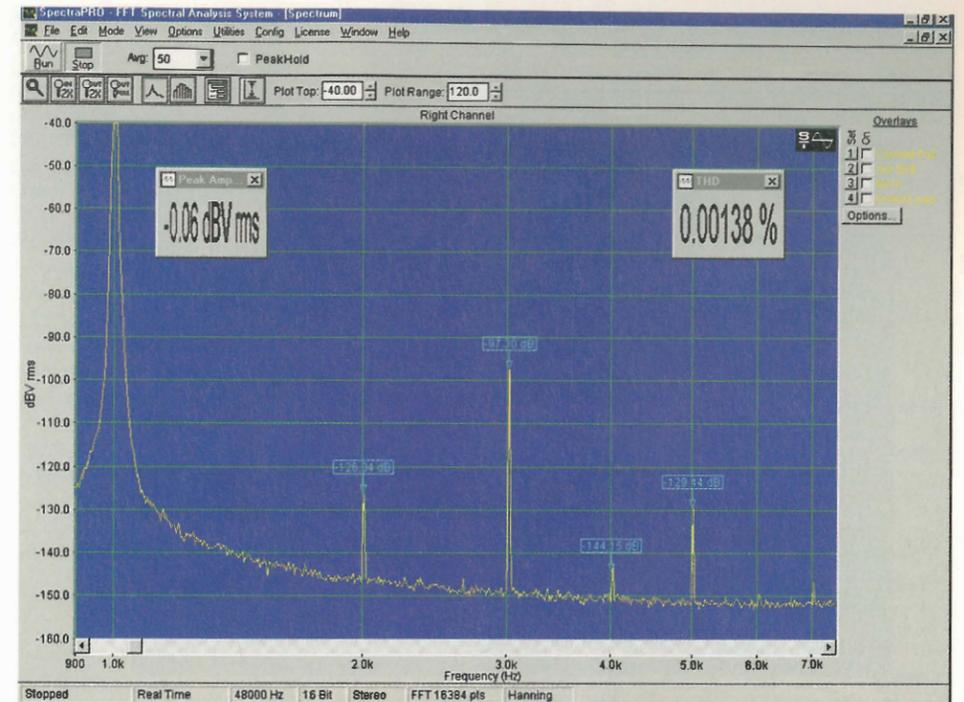


Fig. 11. This multi-turn cermet trimmer, set as a 5.6kΩ variable resistor and tested with a 6V signal from 1kΩ source impedance, generated this enormous -97dB third harmonic, 0.00138% harmonic distortion. Tested exactly the same a low cost carbon control produced 0.00129% while a conductive plastic control and 10-turn wirewound generated only 0.00009% and 0.00007%.

resistors measured -127dB, the metal film third harmonics measured -125dB while the carbon film third harmonics measured -118 and -120dB respectively, all higher harmonics remained below -140dB for all types. **Fig. 10.**

Fixed Resistors - Conclusions

Provided a resistor is loaded to 25% of its rated power or less, modern 1% metal film resistor distortion is small, typically less than 0.0001%, smaller than almost any other active or passive component, which may be used in an audio system.

Distortions found with the 1% metal film resistors used for this article are small and cannot be properly measured at 6V using my less than 1ppm distortion equipment.

Volume controls - trimmer resistors

Almost as many words have been written about noisy carbon volume controls as for distorting capacitors, but I have seen little about distortion from volume controls or pre-set trimmers. As seen in this series, third harmonic distortion in capacitors and resistors is usually caused by non-Ohmic contact resistances, surely the wiping contacts used in volume controls and pre-set trimmers must produce similar distortions. Recalling

the problems I had with my original oscillator variable output stage, I decided to explore further.

Unlike other variable resistor types, a multi-turn wire wound at AC will exhibit a reactive phase angle in addition to its claimed DC resistance value. Depending on its design, construction and the test frequency, it may appear either as inductive or capacitive. I tested my stocks and without exception all were capacitive at low frequencies, measuring typically 100pF, becoming inductive at higher frequencies. This reactance may cause problems in some circuits.

Using the 6V drive at 1kHz from my equipment, I first connected some 10kΩ potentiometers and multi-turn pre-set resistors to make 5.6kΩ variable resistors, passing some 1mA through each wiper. I used a 10-turn wirewound, a 20-turn cermet trimmer, a low cost carbon and a conductive plastic volume control. Not surprisingly the 10-turn wirewound measured 0.00007%, my equipment baseline distortion, the conductive plastic was almost as good at 0.00009%, the difference being a 5dB increase in third harmonic distortion. When I tried the low cost carbon volume control I expected and found increased distortions, now measuring 0.00129%, 14 times greater distortion than the conductive plastic volume

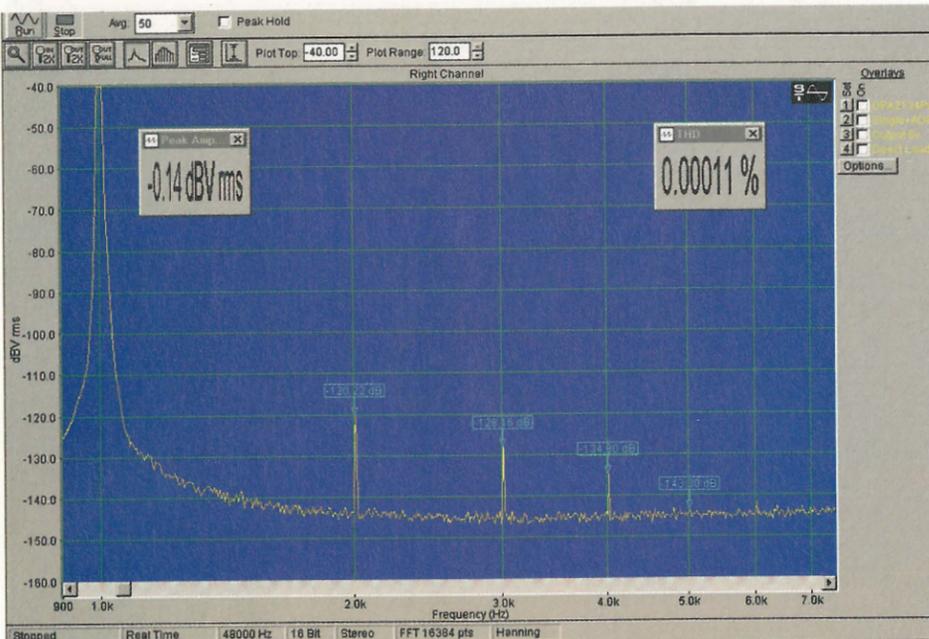


Fig. 9. Refitting R28 and using an AD811AN current feedback amplifier for U8, this Burr Brown OPA2134CPA, the joint best 'single' amplifier tested, reduced its distortion from 0.00036% at 4V output to this remarkable 0.00011% distortion at 6V output.

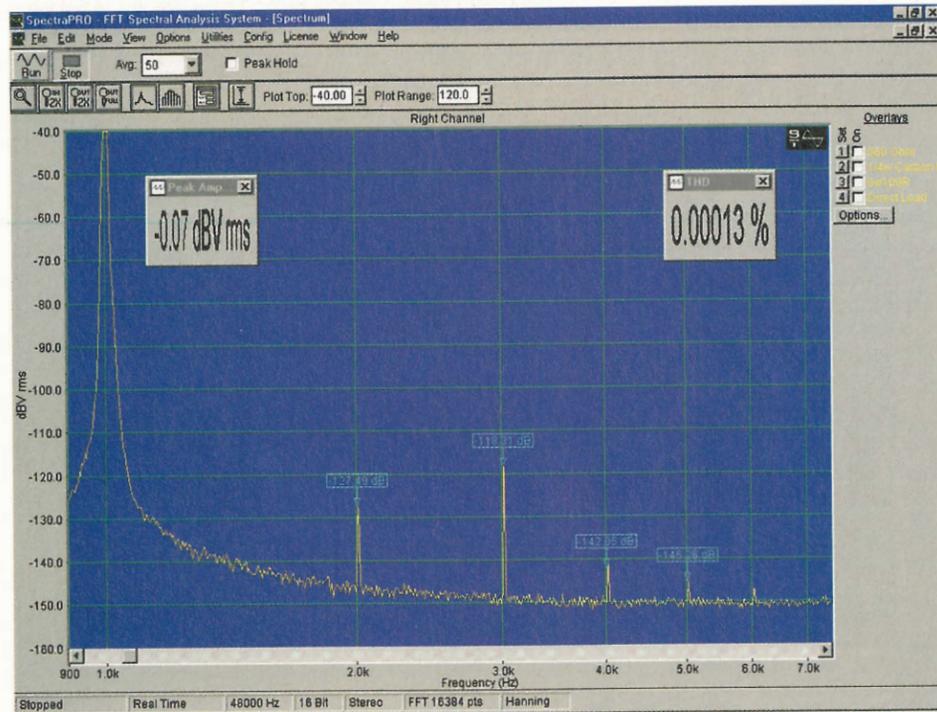


Fig. 10. This 20 year old 0.25 watt carbon film resistor made with a ground, not laser trimmed, spiral, produced 0.00013% distortion when loaded to 25% rated power. The second harmonic for a same make 0.5 watt resistor loaded to 12.5% rated power, measured 2.3dB better. Distortions from a modern laser spiralled, low cost 1% 0.5 watt metal film resistor, were too small to be measured.

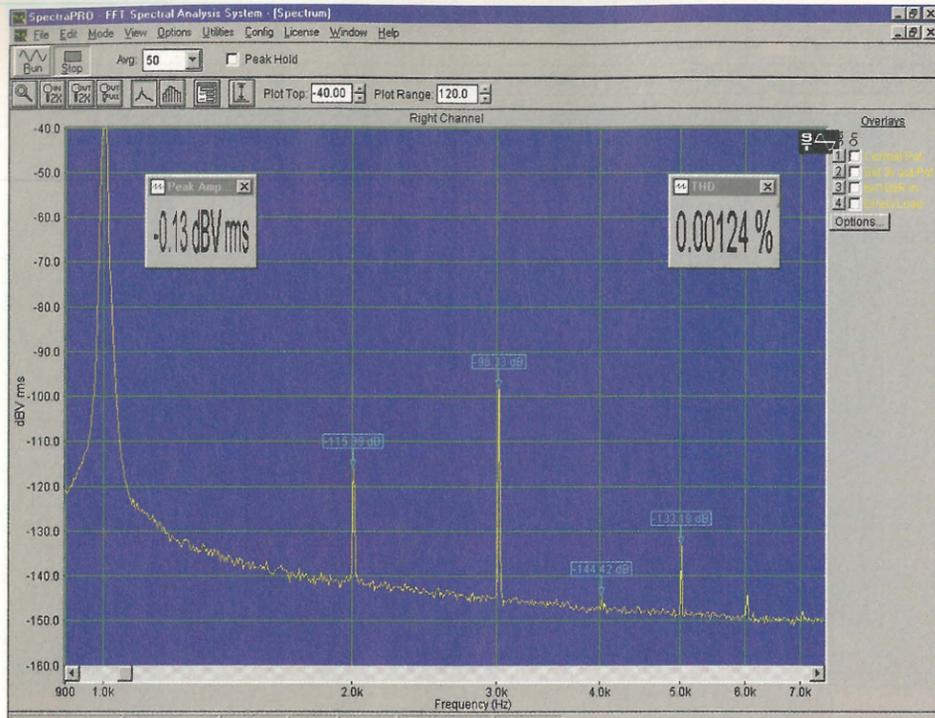


Fig. 12. Re-connected as potentiometers to output a 3V test signal drawing 225µA through their wipers, produced a similar pattern of distortion. The cermet control with 0.00124% distortion was worst; the low cost carbon was much better at 0.00039%, the conductive plastic and wirewound measuring just 0.00009% and 0.00005% respectively.

control. Second harmonic was -117dB, third -98dB, fourth -137dB and fifth -121dB.

Finally, the multi-turn cermet trimmer which measured an enormous 0.00138% distortion, worse even than the inexpensive carbon control. While the second and fourth harmonics remained near my measurement baseline, its -97dB third harmonic dominated distortion, more than 31dB worse than measured on the wire wound control. Fig. 11.

Used as a potentiometer

While the above test reasonably simulated use as a variable resistor, many potentiometers and pre-sets are used as potential dividers or volume controls. To simulate this requirement I connected my 6V test signal to one end terminal, the other end to ground, then set the wipers to measure a 3V output signal. To ascertain the effect of wiper contact linearity, each control was tested twice, once with my notch filter input switched to 'pre-amp' for a negligible 10µA wiper current, then switched to the 'direct' position, a 13.5kΩ resistance in parallel with 10.2nF capacitance, drawing some 225µA through the wiper.

With the 10µA wiper current, the

10T wire wound measured 0.00006%, the carbon and conductive plastic controls 0.00007%. The cermet trimmer third harmonic increased by 16dB to measure a distortion of 0.00037%. Clearly this increase results mainly from the cermet resistive element, not the wiper contact which was passing only 10µA of current compared with 600µA through its element.

Distortion was third harmonic at -109dB, second -120dB.

To determine how increased wiper current might be a factor, I re-measured each with the pre-amp switch set to 'direct', for 225µA wiper current. The wire wound and conductive plastic controls changed little, reading 0.00006% and 0.00009% respectively. The low cost carbon control measured 0.00039% distortion, indicating its wiper made reasonable contact, whereas the cermet trimmer measured very badly, at 0.00124% its distortion was dominated by a -98dB third harmonic. Fig. 12

Variable resistors and potentiometers - conclusions

Clearly to minimise distortion, the

lowest possible Ohmic values should be used and variable resistors, potentiometers and pre-set controls must be subject to the smallest possible through and wiper currents. Particular care must be taken to avoid passing capacitive load currents through the wiper contacts, which could result in unexpected tone control distortions.

For almost all applications, a conductive plastic control will produce low noise and distortion while avoiding any reactive loading problems which may result when using a wire wound control. When a cermet type control must be used, it is essential to make certain it is subjected only to small voltage drops with small currents passing through the element and none or very little current is drawn through the wiper.

Conclusions

This series has shown how using low cost self build equipment and simple test methods, one can easily measure the distortions generated by most components used in modern audio systems as well as complete amplifiers, in the hope many readers will replicate these measurement

methods. Gain understanding, especially of capacitor functions and help to eliminate many popular misconceptions. Improving our knowledge base by using real measurements to replace subjective opinion.

Contacts:

WinAudioMLS Pro <http://www.dr-jordan-design.de>
SpectraPlus232 <http://www.soundtechnology.com>

References

1. Op-Amp Audio. Walt Jung, *Electronic Design*, September to December 14, 1988. <http://www.elecdesign.com/content/3004,2800,1474&1518.html>
2. Active Feedback Amplifier Enables High-Performance A-to-D Conversion. Moshe Gerstenhaber & Chau Tran, *Electronic Design*, April 2, 2001
3. Capacitor Sounds. C. Bateman, *Electronics World*, January 2003
4. Capacitor Sounds II. C. Bateman, *Electronics World*, September 2003
5. Differential-in 100MHz scope probe. C. Bateman, *Electronics World*, December 2001
6. Capacitor Sounds. C. Bateman, *Electronics World*, September 2002

FFT Software

Throughout my *Capacitor Sounds* series, except the first two articles, I used the SpectraPlus232 software for my distortion plots. This software is easy to set up and has served well. However some readers have asked whether lower cost software might be used, since with a full set of options it becomes expensive.

I have now found two alternatives. Provided the reader can accept not having the on screen THD% display, all other facilities I used are provided by purchasing only the Spectra base module, almost halving the cost. The on screen THD% option can be purchased later.

My second alternative is "WinAudioMLS Pro", I evaluated version 1.66, a new version having its microphone correction ability updated for use with my test equipment, or a conventional microphone. It can be obtained from the Dr. Jordan web site.

As standard this software provides a THD+N display and cursor controlled readout of harmonic levels. It accepts the microphone correction file, essential when using my notch filter/pre-amplifier assembly. In addition to all the features needed for my measurements it also provides an MLS measuring facility. This

can be used to measure loudspeaker and room responses as well as the impedance and phase of low impedance components, especially those used in loudspeakers. All this for less cost than for the basic SpectraPlus232 module, makes this

software well worth your evaluation.

This software also has a range of additional cost upgrade options, but I found the base WinAudioMLS Pro version with their THD% option, sufficient for my needs.

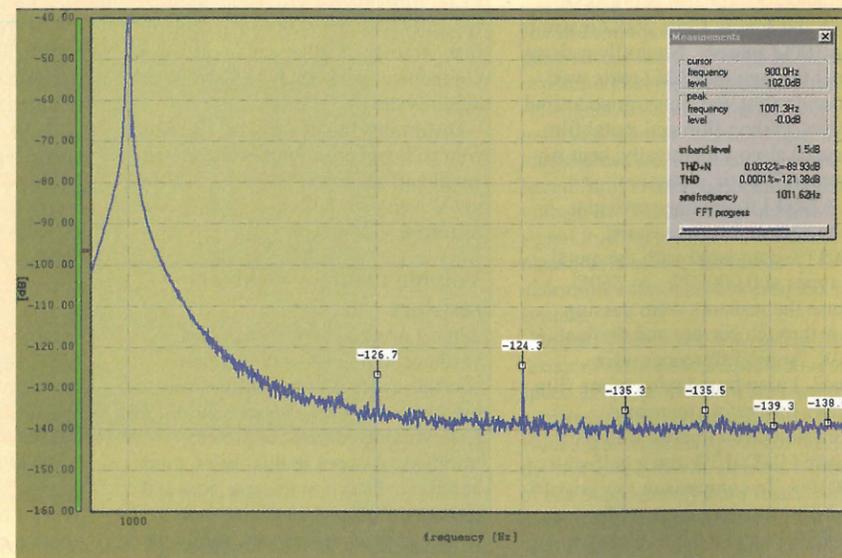


Fig 13. The Dr Jordan software, measuring a 511Ω resistor at 1V and 1kHz.

Complete and fax the coupon to: +44 (0) 1353 654400

I wish to subscribe for one year to **Electronics World**:

Price UK £38.95 O/S £64.50
 US\$100.62 Euro 102.55

Please tick preferred method of payment

I enclose a cheque payable to Highbury Business Communications Ltd

Please invoice me Purchase No

(NB Purchase order must be included to validate invoice)

Please charge my: Master Card/Visa/Amex/Diners
 Club/Switch/Delta (please circle)

Card No

Expiry Date

(Switch/Delta Only) Valid from / / Issue Number

Signature

Date

Name

Job Title

Company

Address

Postcode/Zip

Country

Telephone/Fax

E-mail

Please tick here if you do not wish to be contacted by other businesses either by

Mail Telephone Fax E-mail

Please return to: Highbury Subscription Services,

Link House, 8 Bartholomew's Walk, Ely,

Cambridgeshire CB7 4ZD, UK.

Email: wss@wyverncrest.co.uk

(Quote ref: EW1)

ELECTRONICS WORLD

HIGHBURY Business Communications

The world's leading electronics magazine, **Electronics World** is a technology-transfer magazine for the global electronics industry. It covers research, technology, applications, products and patents in areas such as audio, R.F., components, CAD design, circuit building, PC & Micro based products, tests & measurement, semiconductors, power sources and much, much more.....



Make sure you receive your regular monthly copy by subscribing today.....

LETTERS

to the editor

Letters to "Electronics World" Highbury Business Communications, Nexus House, Azalea Drive, Swanley, Kent, BR8 8HU
e-mail EWletters@highburybiz.com using subject heading 'Letters'.

Defence of Mr. Miller continued

I would like to clarify my June 2003 letter regarding Miller compensation, in light of Mr. Graham Maynard's and Mr. John Ellis's responses to said matter.

Mr. Maynard noted that Mr. Ellis published graphs of 2mV spikes for the PLIL case versus 25mV spikes for the Miller compensated case and suggested that I was unaware of such graph. Fortunately, I had not had any Guinness that day, so this suggestion is somewhat strained. He then made an elementary explanation as to why such behaviour might, for those

unskilled in such matters, result in degraded audible performance. Indeed, this was despite the fact that, by his own admission, he also suggested that such spikes would not have been measurable in a THD distortion test set-up. I certainly agree that 25mV is much larger than 2mV, however, I am unaware of any convincing or credible evidence that such microsecond width spikes would actually be audible, despite being visible on a scope. This is a view often held by the "golden ears brigade" which, arguable, is in an effort to extract rather large quantities of cash from the uninitiated.

Mr. Maynard also made an assertion that I considered Miller compensation "essential". It would appear that Mr. Maynard may have been on the Guinness himself whilst reading said article. I made no such claim. There are indeed, other very well known and very well used alternatives to Miller compensation. For example, a common technique in current feedback amplifiers¹ is to compensate by one capacitor from the high impedance gain stage output to AC ground.

Mr. Maynard also pointed out that he failed to notice the ambiguity in the simulation graphs. This will, hopefully be rectified by the following. It was, and is still, not clear as to the exact method as to how the graphs were made. As I noted, it is important to break the loop in the correct place. It is quite common for the inexperienced to perform loop analysis incorrectly, as a correct loop analysis is not necessarily trivial. For example Dr. Middlebrook² has studied this issue extensively. In summary, it can be quite difficult to break the loop without ensuring the correct loading on each side if the loop. There may be significant interactions. In addition, Mr. Ellis article did not specify exactly where the loop was broken, which can be quite crucial. The exact details of the loop gain measurement need to be specified in order to make any conclusions as to the validity of the results.

To continue, I certainly agree with Mr. Maynard that there are many without the experience to competently design amplifiers and may well use Miller compensation incorrectly. However, there are also many experts who have no such problem. In addition, there are also those that are prone to use such terms as "high amplitude transparency" intermixed with various Star Trek technical terms in an effort to mislead or obscure the real issues, or because that do not actually understand the real significance of these terms themselves.

Regarding Mr. Maynard's query on the MOSFET 1000 amplifier, which was, of course, and no surprise here I would gather, designed by myself. It used a trivial Miller compensation scheme utilising a mere 8 transistors for the complete driver design, excluding the output power mosfets. It achieved <0.005% THD at 20kHz at 8 Ohms. The only other compensation was the standard RC Zobel network and the standard parallel LR in series with the output.

I do agree with Mr. Maynard that some writers do indeed fail to consider many aspects of their subject matter. However, there are also those that have considerable experience, such that those with only a passing acquaintance often misunderstand the finer and more subtle points being presented by individuals who do have such experience. I also note that Mr. Maynard is not acquainted with myself, further information may be obtained by reference to my AnaSoft Web Director entry in this magazine:-)

In reply to Mr. John Ellis's response, I certainly agree with Mr. Ellis regarding the assertion that some amplifiers may well have been designed rather poorly with regard to slew induced distortion. However, his arguments and technical rationale in his letter are very well known and completely understood by many, many, professional amplifier designers and have been so for many years, indeed going way back to the likes of J. Linsley Hood and Peter

Baxendale, well known prior regulars to this magazine I might add. Mr. Ellis seems to be implying that all amplifier designers are not the full shilling. There is nothing new here at all. The reality is that this is a solved problem and a dead issue. As I suggested in my first letter, is relatively straightforward to design audibly perfect amplifiers with Miller compensation e.g. without the input overloading etc. Mr. Ellis appears to be comparing apples with oranges. That is, comparing a good PLIL amplifier, with a bad Miller compensated amplifier. Mr. Ellis also comments on the addition of a low pass filter to avoid slew limiting, so I will address this by noting that for reference, the MOSFET 1000 had a full power bandwidth of 200kHz, did not require, and had no input filter.

Mr. Ellis then addresses my comments on the loop gain analysis. Unfortunately, he still fails to address the fundamental criticism. Exactly how was the graph obtained? Where was the loop broken? What steps were taken to ensure that loading effects were accounted for correctly? He appears to be suggesting "...by performing the subtraction..." that one can determine a valid loop gain plot from a suitable subtraction of the 1 from the closed loop plot, as seen from the input signal. This is a very well known error, and was one of the issues that was being addressed in my original letter. The gain determined from the signal input is simply not the same gain as that around the feedback path. It is quite common for these two gains to be significantly different, such that the signal input derived loop gain shows stability, when in fact, the real loop gain as seen by the feedback loop, shows, and is, unstable.

Mr. Ellis then goes on to point out that he considers that the article was objective. While there was a passing nod to impartiality, it appeared to present the case from the advantage of the PLIL point of view. Furthermore, I clearly quoted two statements by Mr. Ellis, that were indeed contradictory, that is, his claim that their was an "improvement in linearity" for the PLIL, yet his results, further supported in Mr. Ellis' own table in his reply to my letter, showed worse linearity.

In closing, Mr. Ellis' claim that competent Miller compensated amplifiers are not standard practice is ludicrous. Indeed they are, and have been for well over 20 years, probably 30. I would estimate that there are 1000's of amplifier designs out there with golden ear specifications, using

Miller compensation. I would suggest that Mr. Ellis actually investigate what the facts actually are. His overall inferred implication that 100's of amplifier designers are clueless says much.

Kevin Aylward
Peterborough
UK

References:

- 1 "The current feedback myth"
- 2 Dr. Middlebrook,
<http://www.rdmiddlebrook.com/>

Wideband buffers

Many thanks to Dewald de Lange for his comprehensive article, 'Flat, wideband buffers' in EW October, 2003. He certainly clarified issues that have given me fits. If only I'd had this information 35 years ago when we all were building op-amps from bits and pieces!

Despite the continuing abundance of linear integrated circuits in a world gone digital, discretion is said to be the better part of valour, and often a design using discrete components has decided advantages over its monolithic counterpart. I would love to see more articles extolling the virtues of a simplistic approach to circuit design.

Jim Wood
California,
USA

Test failure

It appears that I would not be a likely recruit for C. Bateman & Co. I tried Cyril's cube-of-resistors puzzle (*Letters*, September 2003) and I must confess that it took me considerably longer than the required couple of minutes. To make myself feel better I showed it to three other engineers. Engineer 1 muttered something about having to see a man about a dog and departed. Engineer 2 rather irritatingly solved the problem in about five minutes. Some time later Engineer 3 alleged that I had been conceived out of wedlock and said that he would be able to do it with Kirchhoff's Laws and simultaneous equations but he hadn't the time. He reappeared the following morning with a solution similar to Engineer 2's. At this point, before hastily retreating, Engineer 1 asked what would happen if the resistors all had different values. I was able to work out the answer much quicker this time: the person who had posed the question would be in danger of having their own resistance determined by a mob armed with the

PCB help wanted

I seek the help of readers who may be familiar with my problem. To design my double-sided PCB's, I use a homemade program that in the end generates two drawings in bit-map format. Then, via the commercial program Paint Shop Pro version 4, I can print the layout of the component side and the solder side of a double-sided PCB. To register one drawing with respect to the other, I use markings on the four corners of each drawing. On one drawing the markings are open squares and on the other the markings are solid squares that fit exactly into the open squares. To register the drawings I put them face to face and I found that the markings do not register. When I put the drawings together face to back, in the same fashion as they come out of the printer, the markings do register. It turned out that vertical lines are not printed perpendicular to horizontal lines. Blaming my old ink-jet printer, I took the bit-map files to a print shop to have them printed on a state-of-the-art laser printer. Their printouts however showed the same defect. I would be very much obliged if somebody can explain to me what causes this error.

Chris Schuur
Nuenen
The Netherlands

electrician's Megger. (A clue for anyone still struggling: short together any points which are at the same potential.)

Pete Fry's letter remarked on school science lessons and reminded me of a question I used to ask sandwich-course students. I thought it would indicate their ability to apply theoretical knowledge to a practical situation. I got it from a MENSAs magazine. (As you have probably guessed by now, the magazine was someone else's.) Suppose that two metal balls have an identical weight, diameter, and surface finish. One ball has a lead core surrounded by aluminium, and the other an aluminium core surrounded by lead. How does one tell which is which without damaging the balls? I had to abandon this question when my son completed his 'A' level courses in maths, further maths, and physics without having been taught about moments of inertia. A university lecturer told me that this is now quite normal. This seems to me to leave a gaping hole in students' understanding of a world which contains numerous rotating objects, and to be a bad thing for a nation which relies increasingly on its technical ability and inventiveness.

On one more topic, I found the article "The Cathode" interesting, particularly the bit about the forming process for oxide-coated cathodes.

Walt Disney University

Perhaps Brian Corbett would like to tell us just what he means by a 'Mickey Mouse' degree. Or is it just an all purpose term of denigration he has picked up from the press and politicians? Perhaps he means 'media studies' and the like. If he does then I suggest a bit of a re-think might be needed.

Media studies courses were developed at the old polytechnics more than twenty years ago. The people who undertook the early courses are now in their forties and fifties, and many have gone on to successful careers in broadcasting. That was the great strength of polytechnics and similar institutions. They could develop worthwhile vocational courses without being forced to call them degrees. Abolishing the polytechnics took away that option.

In England we have a very poor understanding of exactly what we mean by vocational courses. Studies in law, medicine or veterinary medicine are not seen as vocational and are acceptable to the chattering classes as worthy of being called degrees.

Mathematics, physics, chemistry and biology will just about pass muster provided they are studied at a 'good' university. Studying engineering, electronics, computer science or applied anything, is a sure fire way to be seen as just about one step up from the 'drawers of water and hewers of wood'.

With this kind of snobbery around do we really need Brian Corbett casting around for someone to look down on?

Dr. Les May
Rochdale
Lancashire
UK

When I worked in T.V. servicing many years ago, the workshop had a box of tricks called a tube booster. This was sometimes able to rejuvenate cathodes which had lost their emission. If I remember rightly, the booster put an excessive current through the heater and a large

positive voltage on the control grid. Presumably the effect was similar to the forming process, removing the oxygen from any residual oxide on the cathode and leaving exposed barium behind. I can't help wondering if the success rate would have been higher if the tube had been

left for some time before being operated, so that the oxygen could be absorbed by the getter.
Hugh Mirams, G8UTW
 By email

Volks radio receivers - Germany 1930's

I read the *EW* August article on 'Radio Receivers of the Third Reich'. As I examined the schematic that was shown on page 17, I noticed how extremely primitive it is. This is one of the crudest receiver circuits that was commercially produced after 1929 (the year the superheterodyne came out in America). The Germans obviously intending to make a mass produced radio that was as cheap as possible, your article's propaganda about the Nazi censoring, notwithstanding. In any case I noticed that the output stage was directly connected to the speaker and that the power amp stage had a directly heated cathode, which combined would have made for a very noisy speaker - 50Hz tone from the AC line.

I was thinking, there was a method used in dynamic speakers called a 'hum-bucking coil'. This coil was wrapped around the field coil of the speaker. The hum from the speaker would induce a counter-EMF in the H-B coil and cancel out this 'waste noise'.

Could the Germans have used that in their radio receiver sets to nullify the 50 cycle power line hum from the lousy circuitry they used ???

Chad Castagna
 Woodland Hills
 California
 USA

Fluorescent Starter

October's *Circuit Ideas* on 'Fluorescent Starter Circuit' reminded me of working on lamp dimming circuits in the 1960s. We found that it was necessary to keep the heaters alive and used a double secondary transformer to heat the two cathodes and so dispensed with the starter. I seem to remember 9 volts but I have been using 6.3 volts in several fittings at home for over 30 years. These have given me nearly instant starting without flicker and usually the light gets too poor before the tube fails completely. Dimming circuits work well but must have a flywheel action to cope with the back EMF from the choke otherwise the dimming range is poor.

Albert Lardeur
 Chaldon
 Surrey
 UK

Dinosaurs and Crosstalk

R Harris makes serious errors in his letter "Dinosaurs" in the September issue of *EW*, p54.

Since in my June article I wrote; "... coarse grain arrays made up of a small number of powerful processors have discredited rather than promoted large scale (fine grain) array processors," he should not have written about failure of Transputer (powerful) arrays discrediting my promotion of an array of one million processors, because I had already said so.

Harris's second error is to write within the paradigm of separation between management and technocracy, with the technocracy subservient. We have just spent half a century demonstrating that such an arrangement fails, and I have written books and articles about its failure; see my book *Computer Worship*, (pub. Pitman 1973), or my article 'The New Bureaucrac', *Wireless World* December 1982 at <http://www.ivorcatt.com/31.htm>, or indeed my June 2003 article, which Harris is supposed to be commenting on. Harris, willy-nilly, writes as if it will always be thus; "... make the transition to management; technical side of the fence". The error some technocrats make is to assume, in their ignorance, that management is a challenge.

Compared with hi-tec activity, it is trivial, as I know from experience. Hi-tec activity contains within it all the challenges of management, so that the challenge of management is a subset of the challenges posed by high technology. That is the reason for the nervous rearguard by management against hi-tec, and the incessant propaganda that Harris parrots, that technocrats would not be able to manage. The recent major case of such propaganda was to try to blame an engineer for the collapse of GEC after Weinstock had systematically rooted out GEC's technical (a middle managerial) infrastructure, so that it was bound to collapse when the cold war 'defence' scam disappeared. The journalists who blamed an engineer were not technocrats.

In his letter, "Design for EMC", *EW* Nov.03, p53/54, Ian Darney recommends his faulty article in the August 1998 issue and his earlier article in May '01, in both of which he in turn recommended certain faulty software to calculate crosstalk in digital systems. Unfortunately both Ian Darney and those who supply the software betrayed their lack of grasp of the subject in Figure 11 in Darney's Aug '98 article. The software output proves

that he and they do not know that in the configuration shown, the crosstalk (noise) is flat topped, not the damped sine wave which they show. You can see this in the oscilloscope photographs I took of such cases and published in *IEEE Trans. Comp. Dec. 1967*. The whole industry has ignored my exciting discovery of the two modes of propagation and my rigorous proof, leading to simple graphs for reading off the maximum crosstalk amplitude for any configuration of printed circuit wires. These can now be found on the www via www.ivorcatt.com/34.htm.

As to "De-bounce II", the letter by Ronald Ogilvie on the same page, I have gone back to the letters etc. that he refers to. Certainly, Yong's circuit is nonsense. However, there is a second problem, which is 'The Glitch'. This hazard, also called 'synchroniser' or 'arbiter', has to be dealt with by circuitry which also solves de-bounce. In 1961, when I complained to a designer of the £5 million Ferranti Atlas Computer that it would crash because it lacked circuitry behind a mechanical switch to deal with the glitch, he replied that this did not matter because the computer was so unreliable anyway. Too get a feel for the money, my graduate salary was less than £1,000.

Later, I was the first to publish on 'The Glitch', see *IEEE Trans. Com. Feb.1966*, p108. Although the subject was and remains taboo, I published in the *IEEE* by giving it a misleading title. (Repeated in my self-published 1980 book *Digital Electronic Design vol. 2*, p281. Send large s.a.e. to me via *EW* for those 23 pages). It is also discussed in my book *Computer Worship*, p94, and was then picked up by the *Daily Telegraph*, 5 Feb.1974, "Computers sent mad by 'The Glitch'".

Later, Wormald claimed to have solved the insoluble problem of 'The Glitch', but he recanted when I went after him. His recantation, in *IEEE Trans. Com. Oct 1979*, ended; "... Obviously the situation needs understanding by a much wider circle of the computing fraternity than the small proportion of engineers who have been concerned so far." Since then, the problem has been ignored/suppressed for a further quarter century, so that computers can continue to crash. Chris Penfold was commissioned to write a play about the suppression, and wrote the script, but it was cancelled before shooting.

Ivor Catt
 St Albans
 Hertfordshire

Cyril's quiz answer

The answer to my quiz is all too simple provided you spot the importance of the circuit's symmetry. This is made easier by assigning resistor and junction node numbers, as in the amended figure.

Starting from point A, we have three same value resistors, each connecting to a pair of resistors of the same value, shown as junctions 2, 3, 4. One resistor of each pair then connects to one of the three resistors which lead out through point B, shown as junctions 5, 6, 7.




Hence each of the junctions 2, 3, 4, sees the same source and load currents, so these three junctions are equipotential points. In similar fashion, junctions 5, 6, 7 are also a set of three equipotential points, but have a different voltage from the first set. Hence we can short junctions 2, 3, and 4 together without any current flowing in the short. Likewise junctions 5, 6, and 7.

Equipotential points can be interconnected without contravening the 'Kirchoff' law as in the rearranged figure. Hence by inspection we have $1/3 + 1/6 + 1/3 = 5/6$ or 0.833 Ohms which is the answer.

If proof is needed, a Spice simulation can be made by adding a very small current sensing resistor R13, 0.0001 Ohms, as shown in the schematic which also clearly shows the above symmetry and node junctions, this R13 is much too small to affect the calculated values.

I have also attached MC6 simulations showing the overall circuit resistance of the original figure as 0.833 Ohms and two groups of equipotential points at 0.6V and 0.4V, using a 1V signal as stimulus.

Cyril Bateman
 Acle
 Norfolk
 UK.

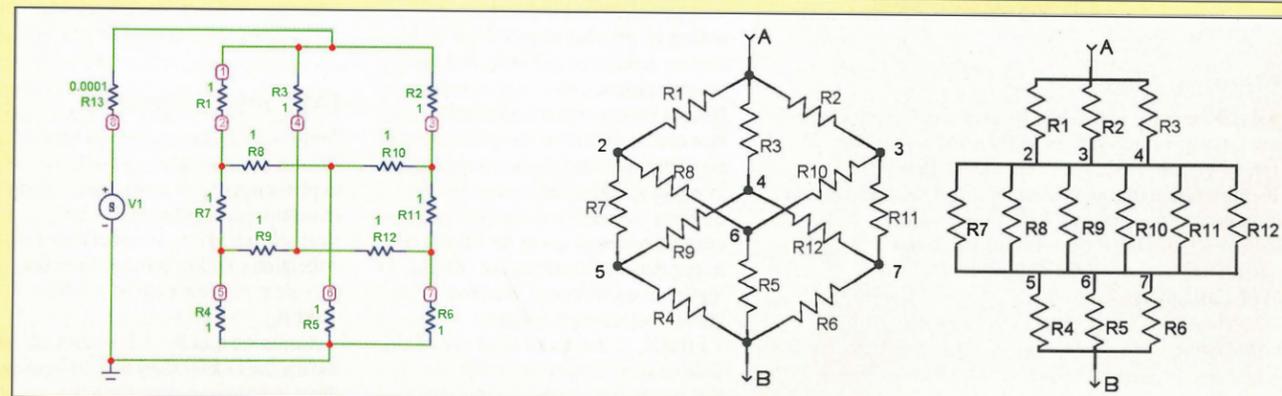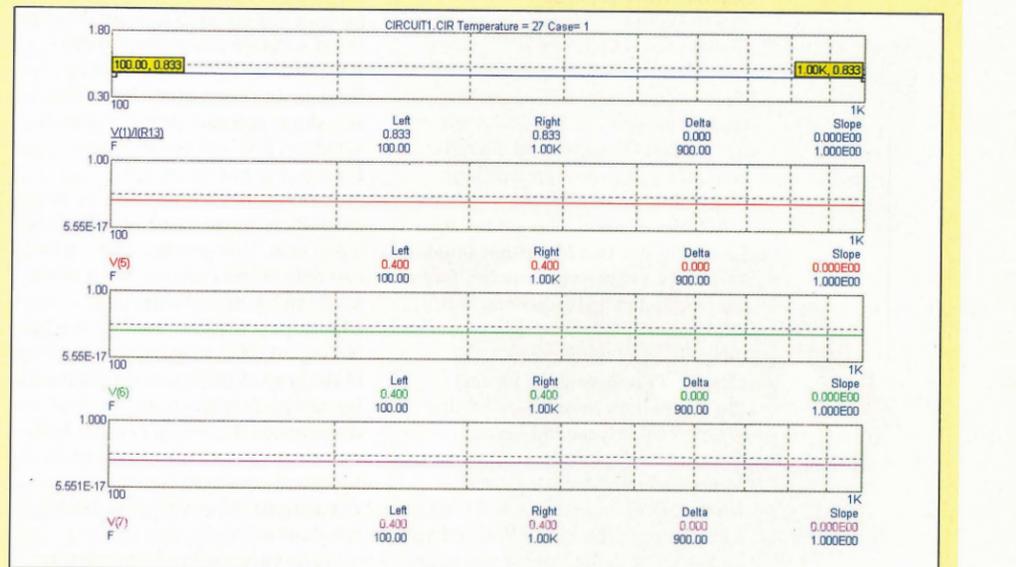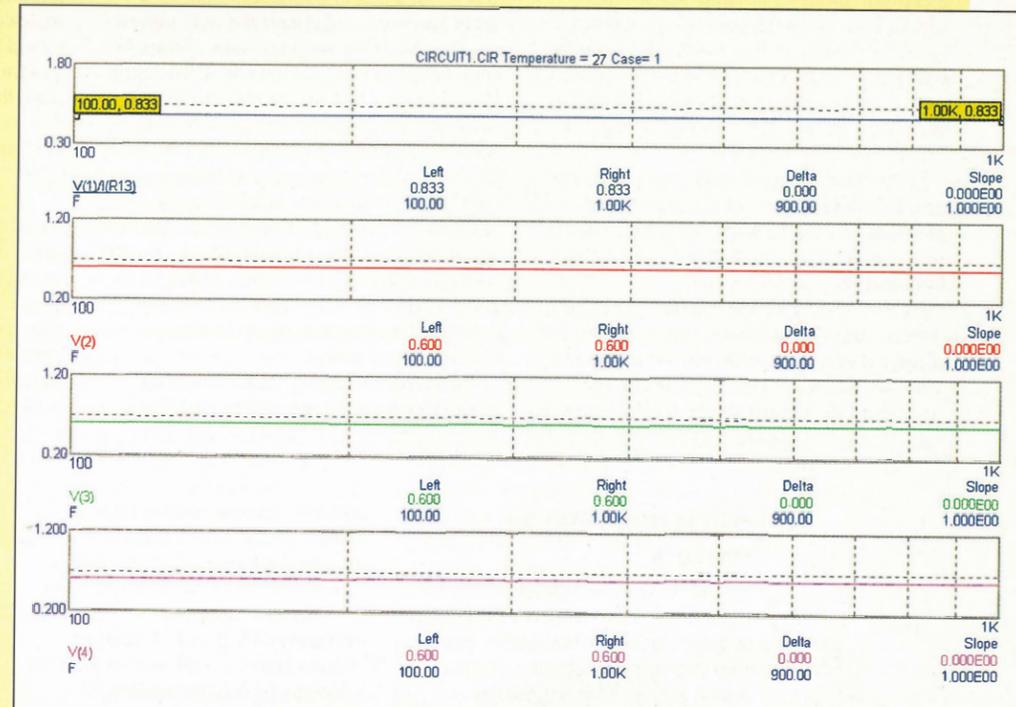


Wilmslow Audio
View Cart Checkout




THE CAUSE? SPECIAL EMPLOYMENT OFFERS
THE EFFECT? UNEMPLOYMENT AND FINANCIAL DISTRESS
THE SOLUTION? A COMMUNITY OF SUPPORTERS
THE RESULT? A COMMUNITY OF SUPPORTERS

WEB DIRECTIONS

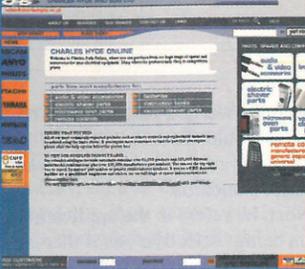

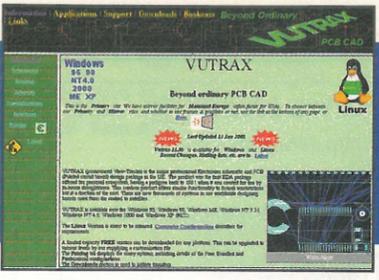To reserve your web site space phone Reuben Gurnlian
Tel: 01322 611292
Fax: 01322 616376



Put your web address in front of 18,000 electronic technicians.

Electronics World acknowledge your company's needs to promote your web site, which is why we are dedicating 2 pages in every issue to WEB ADDRESSES.

Image only will cost £150 + vat for a full year.


Image with colour screen shot will cost £350 + vat for a full year, this will include the above plus 3cm shot of your web site which we can reproduce if required.

To take up this offer or for more information telephone Reuben Gurnlian

tel 01322 611292

E-mail gurunlian@highburybiz.com

ANASOFT LTD
<http://www.anasoft.co.uk>

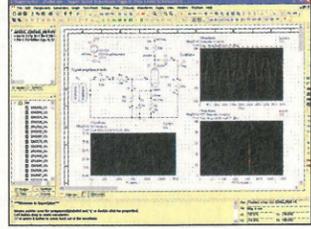

SuperSpice, the affordable, mixed-mode windows circuit simulator. Wrote by an analogue design engineer for those Teletubbies who like keeping things simple.

CHARLES HYDE & SON Ltd
<http://www.charleshyde.co.uk>



Search for both original and copy spare parts in our extensive database covering Akai, Alba, Bush, Ferguson, Goldstar, Hitachi, LG, Marantz, Matsui, Nokia, Saisho, Sanyo, Sony, Sharp, Thomson, Panasonic, Philips, Samsung, Tascam, Teac, Toshiba, Yamaha and many more. In addition huge ranges of Lasers, Loptis, Remote controls and Semiconductors may be accessed.

CHYGWYN
<http://www.chygywn.com>



ChyGwyn Limited offers electronic design and embedded software development for remote monitoring, embedded appliances, set-top boxes and similar devices. We are experts in customisation of Linux and write device drivers for custom hardware.

CONFORD ELECTRONICS
<http://www.confordelec.co.uk/index.shtml>

Lightweight portable battery/mains audio units offering the highest technical performance. Microphone, Phantom



Power and Headphone Amplifiers. Balanced/unbalanced signal lines with extensive RFI protection.

CRICKLEWOOD ELECTRONICS
<http://www.cricklewoodelectronic.co.uk>

Cricklewood Electronics stock one of the widest ranges of components, especially semiconductors including ICs, transistors, capacitors, all at competitive prices.

DB TECHNOLOGY
<http://www.dbtechnology.co.uk/>



EMC Testing and Consultancy. Anechoic chamber and open area test site.
● Compliance Tests
● Rapid, accurate pre-compliance tests.
● Fixes included. FCC Listed.
● Flexible hourly booking available.

DESIGNER SYSTEMS CO.
<http://www.designersystems.co.uk>




Electronic product design company with over a decade of experience promoting it's own product range and designing and manufacturing innovative products for client companies/individuals.



EasySync
<http://www.easysync.co.uk>

EasySync supplies a wide range of USB-RS232 and USB-RS422/485 converters. It also specialises in USB test and measurement devices.

FELLER UK
<http://www.feller-at.com>

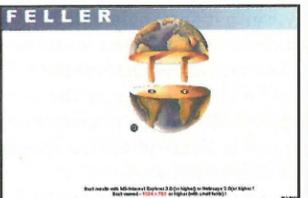

Feller (UK) Ltd. manufacture Fully approved cordsets (Moulded mains plugs and connectors) and Power Supply Cables for all industrial Countries to National and International Standards

FUTURE TECHNOLOGY DEVICES INTL. LTD.
<http://www.ftdichip.com>



FTDI designs and sells USB-UART and USB-FIFO interface i.c.'s. Complete with PC drivers these devices simplify the task of designing or upgrading USB peripherals


GREENWELD
<http://www.greenweld.co.uk>

Audio ● Batteries & Chargers ● Books ● Communications ● Computer ● Cable ● Capacitors ● Car Equipment ● Craft Goods ● Disco Equipment ● Enclosures ● Electrical ● Fuses ● Graphic supplies ● Hardware ● Instrumentation ● Kits ● Lighting Mechanical ● Optical ● Photographic ● Power supplies ● Transformers Resistors ● Semiconductors ● Software ● Soldering Irons ● Surplus goods ● Switches ● Relays ●



Telephone Accessories ● Tools ● Plus much more. Whether your interest is in electronics, model engineering, audio, computer, robots or home and leisure products (to name just a few) we have a wide range of new and surplus stock available.

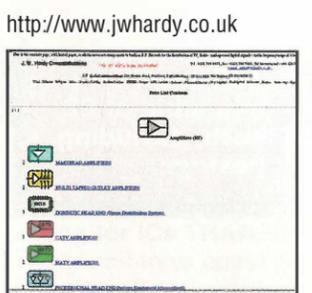J W HARDY COMMUNICATIONS
<http://www.jwhardy.co.uk>



R.F. Network Specialist. Shop online - for R.F.network components. We supply a full range of TV, radio reception equipment to receive analogue/digital signals from both terrestrial and satellite sources. We provide a free planning service for your R.F. networks, MATV, and SMATV etc

LOW POWER RADIO SOLUTIONS
<http://www.lprs.co.uk>

LPRS produces radio modules with embedded "easy-Radio" software protocols for short range radio applications. We also represent Circuit Design narrow band modules in the UK.

MATRIX MULTIMEDIA LTD
www.matrixmultimedia.co.uk
Matrix Multimedia publishes a number of



highly interactive CD ROMs for learning electronics including: Complete electronics course, Analogue filter design, and PICmicro(R) microcontroller programming (C and assembly).

NORCALL Ltd
<http://www.tetra-com.co.uk>

e-mail Norcall@aol.com Suppliers programmers and repairers of new and refurbished two-way radio equipment. Retuning and recrystallising service available. All types of batteries chargers and aerials supplied.

QUASAR ELECTRONICS
www.QuasarElectronics.com



Over 300 electronic kits, projects and ready built units for hobby, education and industrial applications including PIC/ATMEL programming solutions. Online ordering facilities. Tel: +44 (0) 870 246 1826 Fax: +44 (0) 870 460 1045 Email: sales@QuasarElectronics.com

RADIOMETRIX
<http://www.radiometrix.co.uk>



Radiometrix specialises in the design and manufacture of VHF & UHF, RF data modules. We offer a broad range of PCB mounted miniature transmit, receive and transceiver modules for OEM use. They comply with European harmonised standards EN300 220-3 and EN301 489-3 and are CE certified by an independent Notified Body.

SOFTCOPY
<http://www.softcopy.co.uk>

As a PC data base or hard copy, SoftCopy can supply a complete index of Electronics World articles over the past ten years. Photo copies of articles from back issues are also available.

TECHNICAL AND SCIENTIFIC SUPPLIES
<http://www.technicalscientific.com>

Suppliers of pre-1985 equipment and components.

- Test/Masurement equipment
- Valves and semiconductors
- Transducers and pressure gauges
- Scientific books and catalogues
- Manuals and data sheets

TELEVES
<http://www.televes.com>

Tel: 44(0) 1633 875821 email hbotas@televes.com Televes website was launched as an easier way to keep in contact with our World-wide Network of Subsidiaries and Clients. This site is constantly updated with useful information/news plus you can download info on our range: TV Aerials & accessories, Domestic and Distribution amplifiers, Systems Equipment for DTT and Analogue TV, Meters and much more.

TEST EQUIPMENT SOLUTIONS
<http://www.TestEquipmentHQ.com>



Test Equipment for rental or second user sale at the industry's lowest prices. All types of equipment from all leading manufacturers including general purpose, communications and industrial test. Items fully refurbished with 1 year warranty. Rental rebate given on purchases.



TELONIC
<http://www.telonic.co.uk>

Telonic specialists in laboratory AC & DC Power Supplies, Electronic AC & DC Loads, Electrical Safety Testing and complete test systems. Plus RF Filters, Attenuators, Diesel Engine Smoke Measurement, Quartz Crystal Microbalances. Tel +44 (0) 118 9786911

TOTAL ROBOTS
<http://www.totalrobots.co.uk>



Robot Kits and Control Technology products, including OOPic the first Object-Oriented Programmable Integrated Circuit. Secure on-line ordering and fast delivery.

TELNET
<http://www.telnet.uk.com>



Top quality second-user Test and Measurement Equipment eMail sales@telnet.uk.com

To reserve your web site space phone Reuben Gurnlian
Tel: 01322 611292 Fax: 01322 616376

ULTRA-CREA OY
http://www.ultra-crea.fi



Our business idea is to provide our customers complete service, i.e. design from the customer specification to the delivery of finished and tested products.


- Our offerings are as follows:
- RF transmission line filters from 100MHz to 3GHz
 - Special antennas to frequencies as above
 - Transmitter and Receiver modules
 - RF-subunits such as amplifiers, oscillators, directional couplers etc.

VUTRAX PCB DESIGN SOFTWARE
http://www.vutrax.co.uk



Vutrax electronic schematic and pcb design system for Windows 95/98, ME, NT, 2000, XP and Linux. Limited capacity FREE version downloads available, all upgradeable to various customised level.

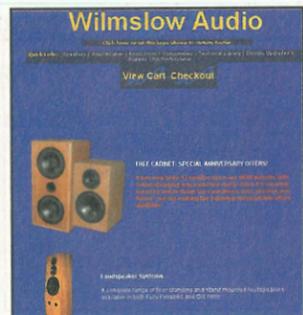WILMSLOW AUDIO
http://www.wilmslow-audio.co.uk



"UK's largest supplier of high quality loudspeaker kits and drive units. Comprehensive range of components and accessories, including damping products, connectors and grilles materials. Demonstration facilities available.

Ten year index: new update

TABLE OF CONTENTS
Click on a topic

Analogue Design
Audio
Avionics
Broadcasting
Communications
Components
Computers
Consumer Electronics
Control Electronics
Digital & DSP Design
History
Instrumentation & Test
Marine & CP
Medical
Miscellaneous
Opto-electronics
PC Interfacing
Projects
RF Design
Safety
Science & Technology
Security



Electronics World Magazine is published by Cumulus Business Media

Subscription hotline +44 (0) 1622 778000

Reprints of all the articles listed are available

This index is available on CD-ROM, containing masses of additional information

Photo copies of Electronics World articles from back issues are available at a flat rate of £3.50 per article, £1 per circuit idea, excluding postage.

Hard copy Electronics World index Indexes on paper for volumes 100,101, and 102 are available at £2 each, excluding postage.

www.softcopy.co.uk

Hard copies and floppy-disk databases both available

Whether as a PC data base or as hard copy, SoftCopy can supply a complete index of *Electronics World* articles going back over the past nine years.

The computerised index of *Electronics World* magazine covers the nine years from 1988 to 1996, volumes 94 to 102 inclusive and is available now. It contains almost 2000 references to articles, circuit ideas and applications - including a synopsis for each.

The *EW* index data base is easy to use and very fast. It runs on any IBM or compatible PC with 512K ram and a hard disk.

The disk-based index price is still only £20 inclusive. Please specify whether you need 5.25in, 3.5in DD or 3.5in HD format.

Existing users can obtain an upgrade for £15 by quoting their serial number with their order.

Ordering details


The *EW* index data base price of £20 includes UK postage and VAT. Add an extra £1 for overseas EC orders or £5 for non-EC overseas orders
Postal charges on hard copy indexes and on photocopies are 50p UK, £1 for the rest of the EC or £2 worldwide.

For enquires about photocopies etc please send an sae to SoftCopy Ltd.

**Send your orders to SoftCopy Ltd,
1 Vineries Close, Cheltenham GL53 0NU.**

Cheques payable to SoftCopy Ltd, please allow 28 days for delivery.

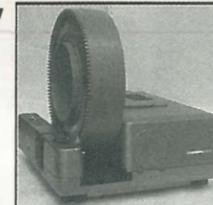**WATCH SLIDES ON TV
MAKE VIDEOS OF
YOUR SLIDES
DIGITISE YOUR
SLIDES
(using a video capture card)**



"Liesgang diatv" automatic slide viewer with built in high quality colour TV camera. It has a composite video output to a phono plug (SCART & BNC adaptors are available). They are in very good condition with few signs of use. For further details see www.diatv.co.uk £91.91+ vat = £108.00

Board cameras all with 512x582 pixels 8.5mm 1/3 inch sensor and composite video out. All need to be housed in your own enclosure and have fragile exposed surface mount parts. They all require a power supply of between 10 and 12v DC 150mA.

47MMIR size 60x36x27mm with 6 infra red LEDs (gives the same illumination as a small torch but is not visible to the human eye).....£37.00 + vat = £43.48
30MP size 32x32x14mm spy camera with a fixed focus pin hole lens for hiding behind a very small hole.....£35.00 + vat = £41.13

40MC size 39x38x27mm camera for 'C' mount lens these give a much sharper image than with the smaller lenses.....£32.00 + vat = £37.60

Economy C mount lenses all fixed focus & fixed iris

VSL1220F 12mm F1.6 12x15 degrees viewing angle.....£15.97 + vat = £18.76

VSL4022F 4mm F1.22 63x47 degrees viewing angle.....£17.65 + vat = £20.74

VSL6022F 6mm F1.22 42x32 degrees viewing angle.....£19.05 + vat = £22.38

VSL8020F 8mm F1.22 32x24 degrees viewing angle.....£19.90 + vat = £23.38

Better quality C Mount lenses

VSL1614F 16mm F1.6 30x24 degrees viewing angle.....£26.43 + vat = £31.06

VWL813M 8mm F1.3 with iris 56x42 degrees viewing angle.....£77.45 + vat = £91.00

1206 surface mount resistors E12 values 10 ohm to 1M ohm 100 of 1 value £1.00 + vat

1000 of 1 value £5.00 + vat

866 battery pack originally intended to be used with an orbital mobile telephone it contains 10 1.6Ah sub C batteries (42x22dia the size usually used in cordless screwdrivers etc.) the pack is new and unused and can be broken open quite easily.....£7.46+vat = £8.77




Please add 1.66 + vat = £1.95 postage & packing per order

JPG ELECTRONICS
Shaws Row, Old Road, Chesterfield, S40 2RB
Tel 01246 211202 Fax 01246 550959 Mastercard/Visa/Switch
Callers welcome 9:30 a.m. to 5:30 p.m. Monday to Saturday

FRUSTRATED!

Looking for ICs TRANSISTORS?

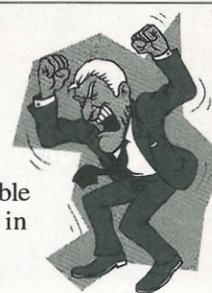A phone call to us could get a result. We offer an extensive range and with a World-wide database at our fingertips, we are able to source even more. We specialise in devices with the following prefix (to name but a few).



2N 2SA 2SB 2SC 2SD 2P 2SJ 2SK 3N 3SK 4N 6N 17 40 AD
ADC AN AM AY BA BC BD BDT BDV BDW BDX BF
BFR BFS BFT BFW BFX BFY BLY BLX BS BR BRX BRY BS
BSS BSV BSW BSX BT BTA BTB BRW BU BUK BUT BUV
BUW BUX BUY BUZ CA CD DX CXA DAC DG DM DS
DTA DTC GL GM HA HCF HD HEF ICL ICM IRF J KA
KIA L LA LB LC LD LF LM M M5M MA MAB MAX MB
MC MDA J MJE MJF MM MN MPS MP5A MP5H MP5U
MRF NJM NE OM OP PA PAL PIC PN RC S SAA SAB
SAD SAJ SAS SDA SG SI SL SN SO STA STK STR STRD
STRM STRS SV1 T TA TAA TAG TBA TC TCA TDA TDB
TEA TIC TIP TIPL TEA TL TLC TMP TMS TPU U UA
UAA UC UDN ULN UM UPA UPC UPD VN X XR Z ZN
ZTX + many others

Please ask for our Free CD Rom STOCK LIST.
WE STOCK A MASSIVE RANGE OF COMPONENTS!

Mail, phone, Fax, Credit Card orders & callers welcome.



Cricklewood Electronics Ltd
40-42 Cricklewood Broadway, London NW2 3ET
Tel: 020 8452 0161 Fax: 020 8208 1441
www.cricklewoodelectronics.co.uk
E-mail: sales@cricklewoodelectronics.com

ADVERTISERS INDEX

Beta Layout	63
Cambridge Microprocessor Systems Ltd	35
Cricklewood Electronics	63
Ennovi Ltd	35
Johns Radio	35
JPG Electronics	63
Labcente	11
Multigen	9
Observant Electronics	IBC
Olson Electronics	2
Pico Technology	38
Quasar Electronics	4
Stwarts of Reading	31
Telnet Ltd	IFC
Test Equipment Solutions	OBC
Tie Pie Engineering	33
Vann Draper Electronics Ltd	31
Westdev	9

PCB-POOL®

SERVICING YOUR COMPLETE PROTOTYPE NEEDS

- Prototypes at a fraction of the cost
- Industry standard quality
- Tooling and setup included
- Follow up series runs
- Any contour
- CAM / CAD consulting
- Fr4 1.6mm, 35µm Cu

PRICE EXAMPLE:
1 EUROCARD DS1P7H
+ Tooling
+ Photoplots
+ VAT
= £ 29.89*

€49

*Sterling rates may vary. Price = € 49



Freephone
0800-389 8560

Simply send your files and order ONLINE.
WWW.PCB-POOL.COM



Service Link

ARTICLES WANTED

BEST CASH PRICES PAID

FOR VALVES KT88, PX4 AND MOST AUDIO/OTHER TYPES.

Tel: 01403 784961

Billington Export Ltd.
Sussex RH14 9EZ
Fax: 01403 783519
Email: sales@bel-tubes.co.uk
Visitors by appointment

TOP PRICES PAID

For all your valves, tubes, semi conductors and ICs.
Langrex Supplies Limited
1 Mayo Road, Croydon, Surrey CR0 2QP
TEL: 020 8684 1166 FAX: 020 8684 3056

FOR SALE

RF DESIGN SERVICES

All aspects of RF hardware development considered from concept to production.

WATERBEACH ELECTRONICS

www.rlaver.dial.pipex.com
TEL: 01223 862550
FAX: 01223 440853

FOR SALE

PRINTED CIRCUIT BOARDS

DESIGNED & MANUFACTURED **agar** Circuits
• Prototype or production quantities
• Fast turn around available
• PCBs designed from circuit diagrams
• Almost all computer files accepted
• PCB assembly - mechanical assembly
• Full product design-manufacture-test-repair
Unit 5, East Belfast Enterprise Park
308 Albertrbridge Rd, Belfast BT5 4GX
TEL 028 9073 8897 FAX 028 9073 1802
info@agarcircuits.com

SERVICES

POWER SUPPLY DESIGN

Switched Mode PSU
Power Factor Correction
designed to your specification
Tel/Fax: 01243 842520
e-mail: eugen_kus@cix.co.uk
Lomond Electronic Services

WESTDALE ELECTRONICS

We would welcome the opportunity of quoting for your requirements.
If you have a problem with your semiconductors or relays, give us a call and we will locate them for you.
We also have access to inventory Stateside ie
Current, Obsolete, Mil, Spec
Call: Bryan on -
Tel/Fax: 0115 9402127

For a FREE consultation on how best to market your products/services to a professional audience ring
020 8722 6028

SERVICES

From Concept To Production 48 HOUR SERVICE

Electronic design and manufacturing services for the new millennium:

- Embedded monitoring & control
- PSTN telephones and test equipment
- Datacom interfacing, line driving etc
- Switch Mode & linear PSU and battery management
- Gas detection systems
- Printed Circuit Board design
- Technical documentation, schematic layout & language translation
- Wireless telemetry systems
- Audio & Video processing
- GSM telemetry via SMS or data (TCP/IP)
- DVD player control systems
- GPS positioning systems
- Specialist cable looms
- Small, medium & large scale manufacturing

Email: sales@designersystems.co.uk
Tel/Fax: +44 (0) 1872 223306

Designer Systems
Design & manufacturing in the UK

for more information see our web site @ <http://www.designersystems.co.uk>

PCBs Conv/PTH/Multi-Layer/Flexible • UK & Far East production
• CAD Layout • Electronic Design • Assembly (prototype & production)
• SMD m/c assy @ 18,500 cps/hr

Deliveries from **24 Hrs**

Prototype PTH PCBs from just **£40.00**

Tel: 01635 40347
Newbury Electronics Ltd
Faraday Road Newbury Berks RG14 2AD
Fax: 01635 36143
e-mail: circuits@newbury.tcom.co.uk
<http://www.newburyelectronics.co.uk>

Visit **www.pcbtrain.com**
The low cost source for prototype PCBs from 1 to 6 layers

WANTED

WANTED Surplus or Obsolete Electronic Components
Turn your excess stock into instant cash!
SEND OR FAX YOUR LIST IN STRICTEST CONFIDENCE
Will collect anywhere in the UK

Mushroom COMPONENTS

28 College Street, Kempston, Bedfordshire, MK42 8LU
Tel: 01234 363611 Fax: 01234 326611
E-mail: sales@mushroom.co.uk
Internet: www.mushroom.co.uk

Service Link

A thousand applications ONE SOLUTION!

Introducing **DataStation™** a 16 Channel, mixed-signal, software-configurable serial I/O controller.

Greater than 500 samples per second, 391 different I/O configurations from one single product!


With up to:

- 6 Analogue Inputs
- Selectable ADC resolution
- 2 PWM Outputs
- 16 Digital Inputs
- 16 Digital Outputs
- RS-232 interface

Typical Applications:

- Machine control
- Industrial automation
- Environmental monitoring
- Robotics

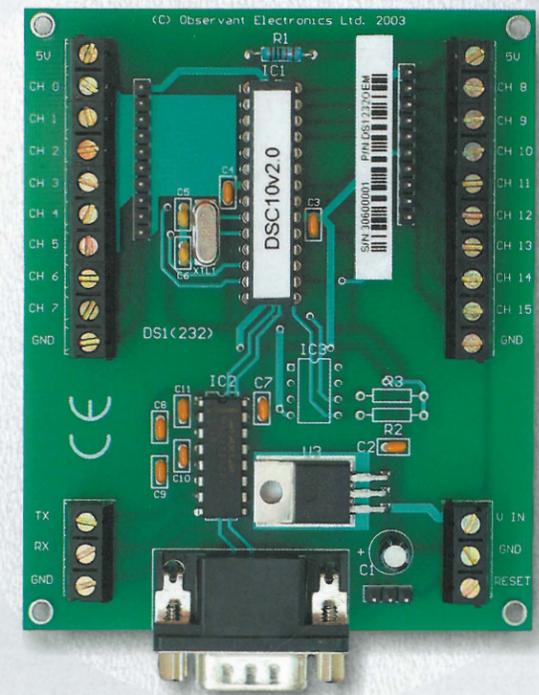This unrivalled flexibility allows designers to meet the needs of virtually any application with just one product, helping to reduce development costs and time-to-market significantly.



£89.00
plus VAT

(Significant discounts for higher volumes)

To find out more or buy online visit: www.ObservantWorld.com



Unit F2b, Avonside Enterprise Park,
New Broughton Road, Melksham,
Wiltshire. SN12 8BS. U.K.
Telephone: 01225 704631
Facsimile: 01225 708618
www.ObservantWorld.com
Email: enquiries@ObservantWorld.com

TEST EQUIPMENT SOLUTIONS

Quality Second User
Test Equipment
With 12 Months Warranty

The Industry's
Most Competitive
Test Equipment Rental Rates

AMPLIFIERS

	Sale (GBP)	Rent (GBP)
Amplifier Research 100L 10KHz-220MHz 150W RF Amplifier	9950	359
Amplifier Research 10W10008 1GHz 10W RF Amplifier	2950	89
Amplifier Research 1W1000 1GHz 1W RF Amplifier	950	48
ENI 5100L 400 MHz 100W Power Amplifier	8950	330
HP 83498 2-20GHz 15dB +20dBm Amplifier	2950	89
Kalmus KMS737LC 25W 10KHz-1GHz Amplifier	4750	143

DATA COMMS

	Sale (GBP)	Rent (GBP)
Fluke DSP4000 Cat 5e/6 LAN Cable Tester	3250	135
HP 18294A X21 Interface For HP Protocol Analyser	750	34
HP J2300D WAN Internet Advisor	2550	92
HP J3446C LAN Fast Ethernet Internet Advisor	3950	119
Inet SPECTRA 2 Port Multi-protocol Analyser - Prices From Tek 1503C Metallic TDR	4950	179
	2500	90

ELECTRICAL NOISE

	Sale (GBP)	Rent (GBP)
HP 346A 18GHz APC-3.5(m) Noise Source	1150	42
HP 346C 26.5GHz APC-3.5(m) Noise Source	1595	65
HP 89708/020 2GHz Noise Meter	7250	218

ELECTRICAL POWER

	Sale (GBP)	Rent (GBP)
8MI 100G POWERISA Single Phase Mains Disturbance Ana.	1950	95
8MI A-116 1-600A Current Clamp For 8MI 4800/100G	650	33
Dranetz PP4300 Power Quality Analyser	4950	179
Dranetz TR2022 10-1000A Current Clamp For PP4300	595	25

EMC

	Sale (GBP)	Rent (GBP)
Chase LFR1000 9KHz-150KHz Interference Meas Receiver	850	43
Electrometrics EM7600 10KHz-100MHz Transient Limiter	185	10
R&S E8100 20MHz-1GHz EMC Test Receiver	1950	59
R&S EPZ100 Panoramic Display For E8100	695	28
Schaffner NSG435 ESD Simulator	2950	89

FREQUENCY COUNTERS

	Sale (GBP)	Rent (GBP)
EIP 548 26GHz Frequency Counter	2750	99
HP 53131A 225MHz 10 Digit Universal Counter	850	31
HP 53131A/030 3GHz Universal Counter	1350	41
Philips PM6670 120MHz Frequency Counter/Timer	350	28
Philips PM6673 120MHz Frequency Counter/Timer	395	20
Racal 1992 1.3GHz Frequency Counter	1150	35
Racal 1998 1.3GHz Frequency Counter	695	35
Racal 9903 50MHz Frequency Counter Timer	295	24

FUNCTION GENERATORS

	Sale (GBP)	Rent (GBP)
HP 33258 21MHz Function Generator	2650	80
HP 8904A 600KHz Function Generator	1350	49
LeCroy 9109/9100-CP Arb Waveform Gen With Controller	1950	59
Philips PMS138 10MHz Function Generator	1500	54
Philips PMS193 50MHz Function Generator	1750	63
Tek AWG2021 125MHz 250MS/s Arbitrary Waveform Gen.	4950	149
Thandar TG1304 13MHz Function Generator	495	30
Wavetek 650 2MHz Variable Phase Synthesiser	4150	150

LOGIC ANALYSERS

	Sale (GBP)	Rent (GBP)
HP 16500A Logic Analyser Mainframe	1250	71
HP 16500C/03 Logic Analyser Mainframe With 32M Memory	2350	85
HP 16510A 100MHz Timing/25MHz State 80 Ch Logic Card	675	34
HP 16510B 100MHz Timing/35MHz State 80 Ch Logic Card	890	45
HP 1662A 500MHz Timing 100MHz State 68 Ch Logic Ana.	2900	87
HP 1662AS 500MHz Timing 100MHz State 68 Ch with DSO	4500	135

MULTIMETERS

	Sale (GBP)	Rent (GBP)
HP 34401A 6.5 Digit Digital Multimeter	650	33
HP 3458A 8.5 Digit System Multimeter	4850	175
Keithley 2400 200V Digital Sourcemeter	2500	751.8
Schlumberger 7150+ 6.5 Digit Precision Multimeter	395	29

NETWORK ANALYSERS

	Sale (GBP)	Rent (GBP)
Anritsu S331C 4GHz Scalar Network Analyser	5250	189
Anritsu S820A 20GHz Sitemaster Scalar Network Analyser	10950	414
HP 3552A Transmission Test Set	1450	75
HP 3577A 5Hz-200MHz Vector Network Analyser	4750	142
HP 4195A 500MHz Vector Network/Spectrum Analyser	8950	323
HP 4396A 1.8GHz Network/Spectrum Analyser	10950	395
HP 8712ES 1.3GHz Vector Network Analyser c/w S Param	9500	342
HP 8714C/1E1 300KHz-3GHz Vector Network Ana c/w TR	7250	218
HP 8753B/006 6GHz Vector Network Analyser	6500	195
HP 8753D/002/006/010 6GHz Vector Net Ana c/w S Param	17950	647
HP 8753ES 3GHz Vector Network Analyser c/w S Param	16950	508

Checkout our
Autumn 2003
Product Guide !!
Call Us Now for Your Copy



	Sale (GBP)	Rent (GBP)
HP 8757C Scalar Network Analyser	4500	162
HP 89441A - Various option sets available - CALL from	14000	504
R&S ZVC 20KHz-8GHz Vector Network Analyser	19500	702

OSCILLOSCOPES

	Sale (GBP)	Rent (GBP)
HP 54501A 4 Channel 100MHz 20MS/s Digitising Scope	1250	38
HP 54502A 2 Channel 400MHz 40MS/s Digitising Scope	1500	45
HP 54540A 4 Channel 500MHz 2GS/s Digitising Scope	3950	189
HP 54542C 4 Channel 500MHz 2GS/s Digitising Scope	4950	179
HP 54825A 4 Channel 500MHz 2GS/s Digitising Scope	7250	287
HP 54845A 4 Channel 1.5GHz 8GS/s Digitising Scope	10950	395
LeCroy LC534AL/GP01/64MBSM 4 Ch 1GHz 2GS/s Dig Scope	6500	234
LeCroy LC584AM 4 Channel 1GHz 8GS/s Digitising Scope	15350	553
Tek TDS3054/3FFT/3TRG 4 Channel 500MHz 5GS/s DPO	6250	188
Tek TDS350 2 Channel 200MHz 1GS/s Digitising Scope	1850	112
Tek TDS5208 2 Channel 500MHz 500MS/s Digitising Scope	3450	125
Tek TDS5540 4 Channel 500MHz 1GS/s Digitising Scope	4400	159

POWER METERS

	Sale (GBP)	Rent (GBP)
HP 11722A 2.6GHz Power Sensor Module	1250	45
HP 436A/022 RF Power Meter With GPIB	750	32
HP 437B RF Power Meter	1350	49
HP 438A Dual Channel RF Power Meter	1550	49
HP 8153A Light Wave Multimeter Mainframe	1750	63

HP Power sensors - Many available.....Call us

	Sale (GBP)	Rent (GBP)
HP E4412A 10MHz-18GHz 100mW Power Sensor	695	35
HP E4418A Single Channel RF Power Meter	1500	54
HP E4418B Single Channel RF Power Meter	1650	60
Marconi 6910 20GHz 100mW Power Sensor	350	18

POWER SUPPLIES

	Sale (GBP)	Rent (GBP)
Many different units available.....Call Us	85	9
HP 1122A Probe Power Supply	250	15
Kikusui PLZ150W 150W Electronic Load	595	25

PULSE GENERATORS

	Sale (GBP)	Rent (GBP)
HP 8082A 250MHz Pulse Generator	1450	53
HP 8110A/81103A 150MHz Pulse / Pattern Generator	4750	171
HP 8112A 50MHz Pulse Generator	2450	89
HP 8130A 300MHz Pulse Generator	5500	198

SIGNAL & SPECTRUM ANALYSERS

	Sale (GBP)	Rent (GBP)
Advantest R3361A 9KHz-2.6GHz Spectrum Analyser With TG	5750	173
Advantest R413ID 3.5GHz Spectrum Analyser	3950	143
Advantest R9211A 100KHz Dual Channel FFT Analyser	2950	89
Anritsu MS2602A/01 100Hz-8.5GHz Spectrum Analyser	7750	233
Anritsu MS6108 2GHz Spectrum Analyser	2650	80
Anritsu MS710A 23GHz Spectrum Analyser	5950	476
Anritsu MS710C 23GHz Spectrum Analyser	7500	225
HP 339A 110KHz Distortion Analyser	1250	38
HP 3562A 100KHz Dual Channel Dynamic Signal Analyser	3650	110
HP 35660A 102.5KHz Dual Channel Dynamic Signal Analyser	3250	98
HP 3585A 40MHz Spectrum Analyser	3950	119
HP 53310A 200MHz Modulation Domain Analyser	3950	119
HP 8563A/103/104/H09 22GHz Spectrum Analyser	10950	328
HP 8591A/010/021 1.8GHz Spectrum Analyser With TG	3950	119
HP 8594E/041 2.9GHz Spectrum Analyser	5000	180
HP 8901A/001 1.3GHz Modulation Analyser	950	48
HP 8903B/001/013/051 20Hz-100KHz Audio Analyser	1950	59

SIGNAL GENERATORS

	Sale (GBP)	Rent (GBP)
HP 83732B/1E1/1E5/1E8 0.01-20GHz Synth Sig Generator	22500	810
HP 8644B/002 2GHz High Performance Signal Generator	7500	270
HP 8648B 2GHz Synthesised Signal Generator	3500	126
HP 8656B/001 0.01-990MHz Synthesised Signal Generator	1250	38
HP 8657A 1GHz Signal Generator	1600	48
HP 8657B/001 2GHz Synthesised Signal Generator	3500	105
HP E44218 3GHz Signal Generator	5500	165
HP E4432A/1EM 3GHz Signal Generator	6950	251
HP E4433B/202/UNB/UN9/UND 4GHz RF Signal Generator	9950	300
Marconi 2022 Synthesised 1GHz Signal Generator	695	35
R&S SMY02 9KHz-2GHz Synthesised Signal Generator	3150	95

TELECOMS

	Sale (GBP)	Rent (GBP)
HP 37717C/UKJ PDH Transmission Analyser	2450	74
HP 37722A 2MBPS Digital Telecom Analyser	2950	135
HP 37732A 50BPS-2MBPS Telecom/Datacom Analyser	2950	135
HP 3788A/001 2MBPS Error Performance Analyser	1350	40
Marconi 2840A 2MB Handheld Transmission Analyser	1250	38
Trend AURORA DUET Basic & Primary Rate ISDN Tester	3250	98
Trend AURORA PLUS Basic Rate ISDN Tester	350	28
TTC 147 2MBPS Handheld Communications Analyser	3750	113
TTC Fireberd 4xxxx Interfaces - many types available...Call		
TTC Fireberd 6000A/6004/6005/6006 Comms Analyser	3950	143
TTC TIMS-45 TIMS Test Set For Fireberd 4000/6000	750	24
W&G DST-1 Handheld E & M Signalling Tester	750	24
W&G PCM-23 Voice Frequency PCM Tester	2450	89
W&G PCM-5/BN984/00.01/02/BN958.24 PCM Chan Meas Set	2500	75
W&G PFA-35 2MB/s Digital Transmission Analyser	3850	115

WIRELESS

	Sale (GBP)	Rent (GBP)
Anritsu ME4510B Digital Microwave System Analyser	10950	329
HP 11759C RF Channel Simulator	6950	209
HP 8920A/1/4/7/13/14/103 1GHz Radio Comms Test Set	3950	119
HP 8920B/1/4/13/14/51/102 1GHz Radio Comms Test Set	5950	179
IFR 1600S/16/20/21/22/35 1GHz Radio Comms Test Set	3950	143
Marconi 2955A/2957A 1GHz Rad Comms Test Set c/w AMPS	2750	99
Marconi 2955R 1GHz Radio Comms Test Set	3150	126
Marconi 2965/11 1GHz Radio Communications Test Set	5950	178
R&S CMU55/81/4/6/9/41/42/43/44/51/61/108/118/120 RCTS	6550	236
R&S CMU200/81/1/82/1/84/1/85/2/1/82/2/1/82/2 RCTS(tri-band)	21250	638
Wavetek 4201S Triband Digital Mobile Radio Test Set	3950	143
Wavetek 4202S/AM Triband Digital Mobile Radio Test Set	4500	135

If you don't see what you want, please CALL!

See our extensive online catalogue at www.TestEquipmentHQ.com

Flexible commercial solutions available on all products



FREE
Palm Zire shipped
with every order
over £5K

Prices shown are for guidance in £UK and are exclusive of VAT. Rental prices are per week for a rental period of 4 weeks. Free carriage to UK mainland addresses for Sales. This is just a selection of the equipment we have available - If you don't see what you want, please call. All items supplied fully tested and refurbished. All manuals and accessories required for normal operation included. Certificate of Conformance supplied as standard; Certificate of Calibration available at additional cost. Test Equipment Solutions Terms apply. E&OE.

01753 596000
Fax: 01753 59 6001

www.TestEquipmentHQ.com
email: info@TestEquipmentHQ.com