

20W QUALITY AMPLIFIER DESIGN

NOVEMBER 1966
Three Shillings


Wireless World

ELECTRONICS • TELEVISION • RADIO • AUDIO



JOHN F. KENNEDY SPACE CENTER, NASA
KSC LIBRARY

Aircraft Corona Noise

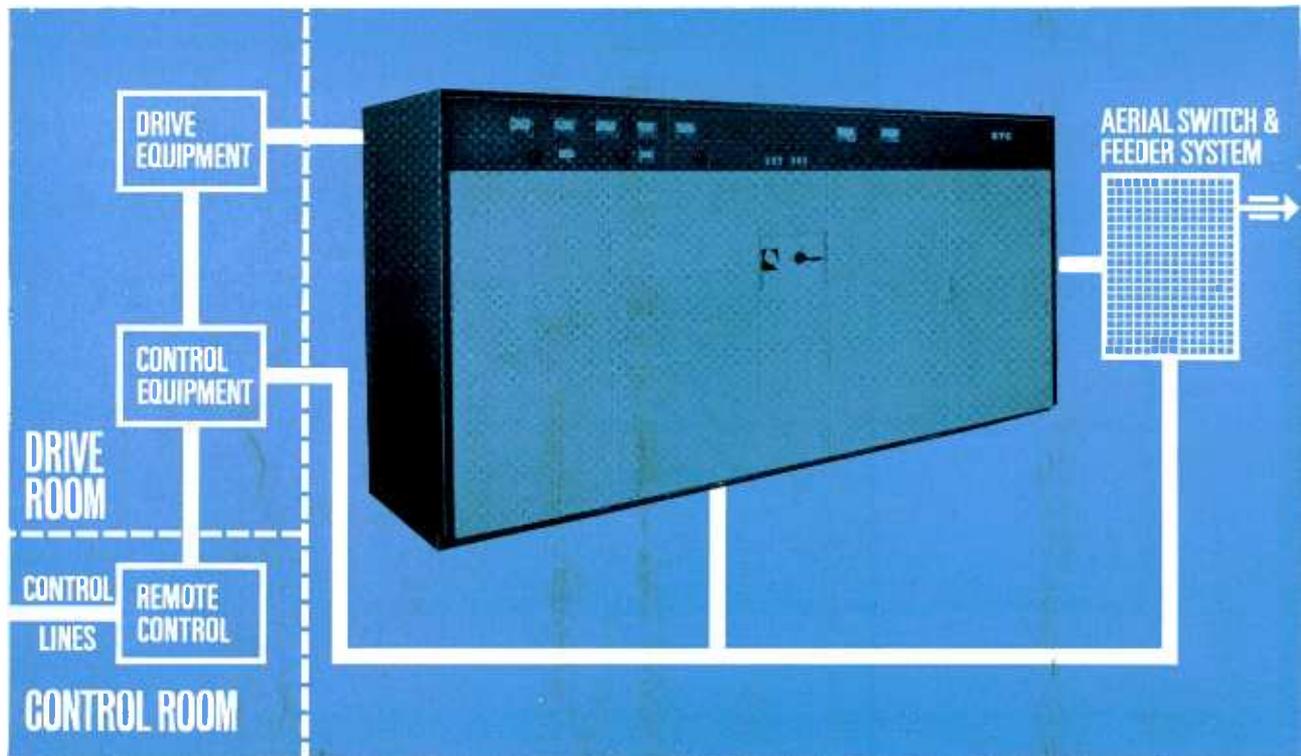

The QT.8-A STANFAST transmitter amplifier

The QT.8-A is the latest of the STC QT Series of automatic transmitter amplifiers for use in the STANFAST HF communication system. It operates in the frequency range 4—28Mc/s with a power output of 20kW for single frequency working or 30kW p.e.p. Being of the linear amplitude response type it is suitable for i.s.b. and d.s.b. telephony or for single or multichannel telephony. Its built-in automatic control and

tuning facilities enable the frequency to be set up locally or from a remote position making the amplifier suitable for unattended operation.

- Automatic tuning
- High reliability
- Automatic load correction
- Rapid fault location
- Solid state logic control circuits
- SWR monitoring
- Manual tuning facility provided

- ISB techniques effect bandwidth saving and power economy
- Negative feedback improves linearity and gain stability
- Requires front access only
- Meets CCIR requirements

For further details write, phone or telex Standard Telephones and Cables Limited, Radio Division, Oakleigh Road, New Southgate, London N.11.
Telephone: ENTEnterprise 1234.
Telex: 261912.

world-wide telecommunications and electronics

STC

"Wireless World"
Iiffe Electrical Publications Ltd.,
Dorset House, Stamford Street,
London, S.E.1

Managing Director:
W. E. MILLER, M.A., M.I.E.R.E.

Editor-in-chief:
W. T. COCKING, M.I.E.E.

Editor:
H. W. BARNARD

Technical Editor:
T. E. IVALL

Editorial:
F. MILLS
G. B. SHORTER, B.Sc.

Drawing Office:
H. J. COOKE

Production:
D. R. BRAY

Advertisements:
G. BENTON ROWELL
(Manager)
J. R. EYTON-JONES

© Iiffe Electrical Publications Ltd., 1966. Permission in writing from the Editor must first be obtained before letterpress or illustrations are reproduced from this journal. Brief extracts or comments are allowed provided acknowledgement to the journal is given.

VOLUME 72 No. 11
PRICE: 3s.

FIFTY-SIXTH YEAR
OF PUBLICATION

Wireless World

ELECTRONICS, TELEVISION, RADIO, AUDIO

NOVEMBER 1966

- 541 "Electronics and the Future"
- 542 High-performance Transistor Amplifier— by A. R. Bailey
- 547 Corona-generated Noise in Aircraft by C. E. Cooper
- 553 Titanium Cone Loudspeaker by E. J. Jordan
- 565 Power Sources Symposium
- 567 Hybrid Computers—2 by P. W. J. Van Eetvelt
- 572 "Microwaves à la Mode"
- 579 More about Farnborough

SHORT ITEMS

- 546 Laser Television Display
- 560 Thin Films in Electronics

REGULAR FEATURES

- | | |
|---|---------------------------------------|
| 541 Editorial Comment | 575 Letters to the Editor |
| 561 World of Wireless | 578 H.F. Predictions—
November |
| 562 November Conferences and
Exhibitions | 581 November Meetings |
| 563 Personalities | 582 New Products |
| 574 News from Industry | 588 Real and Imaginary
by "Vector" |

PUBLISHED MONTHLY (3rd Monday of preceding month). Telephone: Waterloo 3333 (70 lines).
Telegrams/Telex: Wiworld Iiffepres 25137 London. Cables: "Ethaworld, London, S.E.1."
Annual Subscriptions: Home £2 6s 6d. Overseas: £2 15s 6d. Canada and U.S.A. \$8.00. Second-class
mail privileges authorised at New York N.Y. BRANCH OFFICES: BIRMINGHAM: 401,
Lynton House, Walsall Road, 22b. Telephone: Birchfield 4838. BRISTOL: 11, Marsh Street, 1.
Telephone: Bristol 21491/2. COVENTRY: 8-10 Corporation Street. Telephone: Coventry
25210. GLASGOW: 123, Hope Street, C.2. Telephone: Central 1265-6. MANCHESTER:
260, Deansgate, 3. Telephone: Blackfriars 4412. NEW YORK OFFICE U.S.A. 300
East 42nd Street, New York 10017. Telephone: 867-3900.

silicon planar

**for audio, radio and hybrid
television applications**

Mullard now offer a comprehensive range of Silicon Planar Transistors for all new design requirements. These devices are outstanding in performance and are available at competitive prices.

Complete information is available to Design Engineers from:—

Mullard Limited · Entertainment Markets Division
Mullard House · Torrington Place · London · W.C.1
Tel: LANgham 6633 · Telex 22281

BC107

Low-frequency high-gain driver.

BC108

Low-frequency high-gain amplifier.

BC109

Low-noise high-gain A.F. amplifier.

BF115

V.H.F. mixer and oscillator for television.

BF167

'Integrated Screen' transistor for television I.F. amplifiers (A.G.C.)

BF173

'Integrated Screen' transistor for uncontrolled television I.F. amplifier stages.

BF180

Low-noise R.F. amplifier for U.H.F. and integrated tuners.

BF181

High-gain mixer and mixer/osc. for U.H.F. and integrated tuners.

BF184

High-gain I.F. amplifier for A.M., F.M. and television sound.

BF185

R.F. and I.F. amplifier for portable radios.

Mullard **Si** *planar*

WW-110 FOR FURTHER DETAILS.

Wireless World

ELECTRONICS, TELEVISION, RADIO, AUDIO

“Electronics and the future”

THIS is the title of the report on the industry by the Economic Development Committee for Electronics which covers its first two years' work. In it the 22-member committee* surveys the performance and prospects of each of the three main sectors of the industry, namely: capital goods, consumer goods, and components. Conclusions are drawn from its investigations on the problems facing the industry and recommendations made as to how they should be overcome.

The Committee concentrated on imports and exports, “partly because these throw light on the vitality and competitiveness of our industry compared with those of other countries, and partly because reducing imports and increasing exports are important economic objectives in themselves.” The conclusions on the whole are those which have been arrived at so often by other committees and individuals as, for instance, this one: “There will be a rapid expansion in the use of microelectronic circuits, which will require quick changes in policy by the [capital equipment] industry” or this one on consumer goods: “Output is static and exports are low in all but a few fields.”

The Committee's recommendations cover R. & D., Government-industrial relations, export subsidies, provision of international standards to facilitate exports, etc., but we are tempted to ask: “Where do we go from here?” About one-third of the 36-page report is devoted to statistics giving some interesting facts and figures on production and exports in each of the main sectors, but for whose benefit?


Where do the findings of this Government-appointed committee fit into the overall plans of, for instance, the industry's sponsoring body, the Ministry of Technology? True, both the E.D.C. and the Ministry of Technology occupy adjacent sections of Millbank Tower, in London, but to the outsider there seems little liaison between them.

Recently the Ministry of Technology has set up a Technical Advisory Committee on Electronics under the chairmanship of Ieuan Maddock, deputy controller in the Ministry, whose terms of reference include: “to identify within the field of electronics both research and development projects relating to systems, equipments, components and production technologies, the exploitation of which is important industrially and commercially. In relation to these projects to identify areas where effort and available facilities are considered to be too fragmented or on too small a scale.” From a perusal of the list of members† it is obvious that it includes top level men in the industry who, incidentally, have been appointed in their personal capacity and not as representatives of their companies.

Are there not too many Government committees investigating the activities of the industry and offering advice or making recommendations? Looking down the “corridors of power” the number of committees directly or indirectly concerned with the radio and electronics industry is legion. It is to be hoped that Mr. Maddock's committee set up by our sponsoring Ministry will not be just one more “taking minutes and wasting hours.” It is encouraging to see that the emphasis is “technical” for it is felt that all too often those who study our industry with a view to increasing its competitive power or strengthening its position know little, if anything, of the peculiarities of an industry based on a technology which is changing so rapidly.

* Under the chairmanship of Sir Edward Playfair until May this year but now led by Sir Donald Stokes, deputy chairman and managing director of Leyland Motor Corporation.

† R. J. Clayton, managing director, G.E.C. (Electronics); P. D. Hall, director, I.C.T.; D. S. Ridler, technical director, S.T.C.; P. E. Trier, director, Mullard; A. J. Young, managing director, English Electric Valve Co.; Dr. G. G. MacFarlane, director, R. R. E., Malvern; W. Makinson, National Research Development Corp.; J. H. Merriman, deputy engineer-in-chief, G.P.O.; J. R. Mills, Electronics and Instrumentation Division, Ministry of Technology; Dr. W. H. Penley, deputy controller, electronics, Ministry of Aviation; A. W. Ross, Director of Physical Research (Naval), Ministry of Defence; and Mrs. M. Swaffield, Electronics and Instrumentation Division, Ministry of Technology. (Secretary, Dr. J. R. M. Granville, R.R.E.)

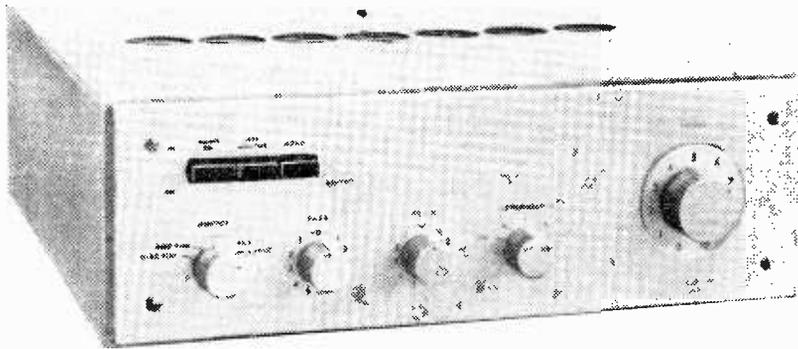

1.—DESIGN FOR A 20W POWER AMPLIFIER

HIGH-PERFORMANCE TRANSISTOR AMPLIFIER

By A. R. BAILEY, Ph.D., M.Sc.(Eng.), A.M.I.E.E.

OVER the past few years there has been a proliferation of designs for audio-frequency amplifiers, and the reader would be well justified in asking if any more were necessary. Unfortunately, transistor amplifier design has, for the most part, been inferior to that of the best valve amplifiers. Listener-fatigue is quite common and there are many inherent defects in circuits that can degrade performance without it being apparent from the specification of the amplifier.

Over two years ago the author was asked by a manufacturer to look into the design of transistor amplifiers and it has taken this length of time to come up with an answer that he feels can stand comparison with the best valve amplifiers available.

Part of the answer lies in the flood of relatively cheap planar epitaxial transistors that have just recently become available. The high current gain of these devices along with the high cut-off frequencies obtainable has greatly eased design problems. Even so there are design problems that seem to have been either overlooked or ignored in the past, particularly that of overload capability. These have been examined in some detail in producing the present circuit, and this is why some parts are definitely unorthodox.

Initial considerations

Before discussing the circuit finally produced, it may be advantageous to examine the reasons for discarding certain circuits. Many circuits appear promising at

first sight but further investigation shows inherent defects in their performance. A typical example is the π mode class AB system where the circuit is class A for small inputs but biases back to class B with full sine-wave drive. With an input waveform having a smaller ratio of peak-to-mean than a sine wave the circuit will bias back into class C under full drive conditions. As the bias conditions are modified to take care of these very square type of waveforms it can be shown that in the limiting case the bias becomes pure class A.

Similarly the pulse-width modulated amplifier appears to have many advantages, but in practice the spurious frequency generation produced in the demodulation process is excessive.*

Pure class A output stages give low distortion, but the heat dissipation becomes a serious problem and the heat sink size for the output transistors becomes excessive. In addition there is a far greater risk of breaking down output transistors in a class A stage by reactive loads. This is due to the greater transistor dissipation in this mode of operation.

Class B operation was therefore chosen using the normal series output connection so as to avoid the use of an output transformer. The drive to the output transistors is somewhat unusual in that a driver transformer is used. Purists may wince at the thought of using transformer drive but nevertheless a good transformer offers many advantages. The transformer removes the need for a phase-splitting transistor as this is done by balanced secondary windings. The low resistance of these windings greatly reduces the effect of leakage currents on the standing transistor currents. This gives very good temperature stability even when germanium output transistors are used.

Silicon or germanium ?

The complete circuit is shown in Fig. 1. Here it will be seen that the first stage is a conventional common emitter stage followed by a direct-coupled emitter-

Dr. A. R. Bailey, after taking his London B.Sc. degree at Bradford Technical College in 1953, stayed on to undertake research into precision three-phase a.c. voltage stabilizers under a D.S.I.R. grant. He then went into industry for a short time but returned to join the staff of the college, which became the Bradford Institute of Technology, where he is a lecturer in the Electrical Engineering Department. The Institute became the University of Bradford this month. Dr. Bailey is consultant to Radford Electronics Ltd.

* "Distortion and Power Output of Pulse Duration Modulated Amplifiers." E. C. Bell and T. Sergeant, *Electronic Engineering*, August 1965.

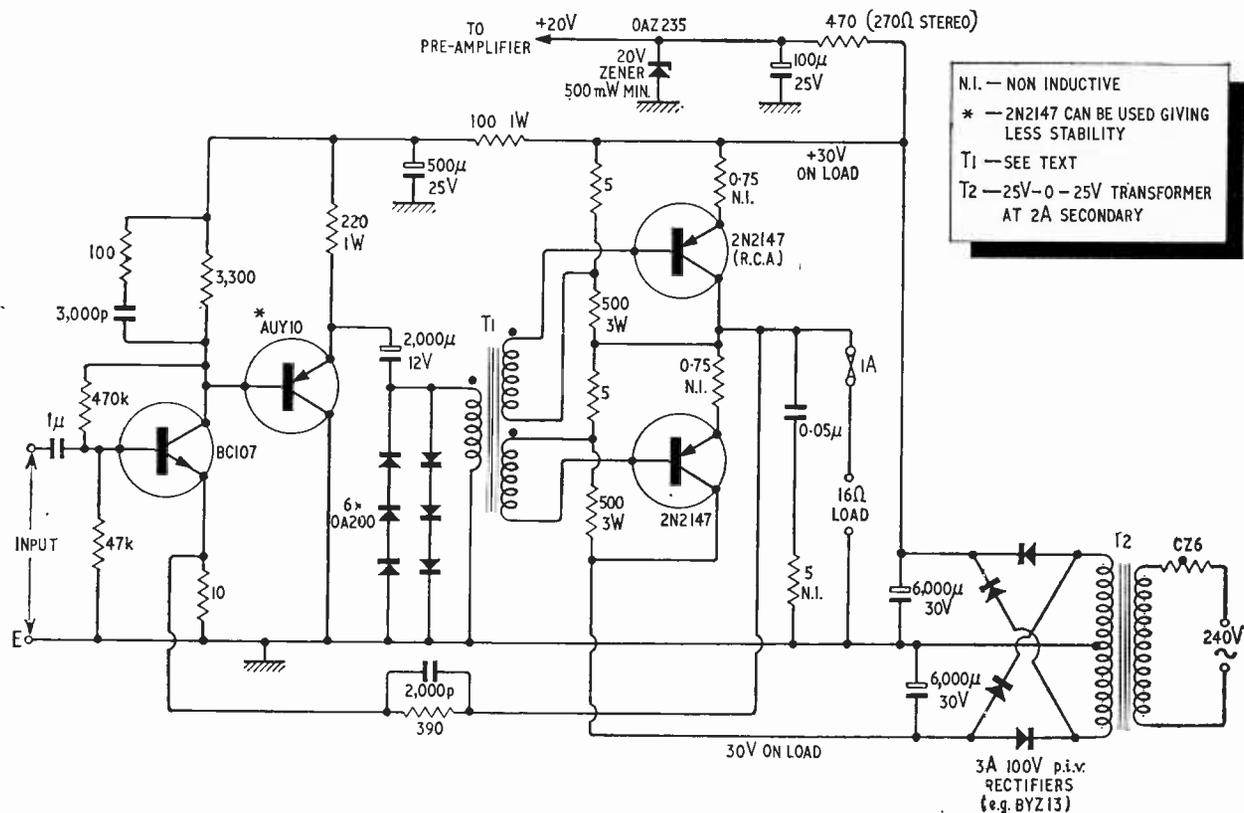


Fig. 1. Circuit of complete power amplifier.

follower. This drives the driver transformer and the output stage at low impedance, thus assisting the distortion and bandwidth properties of the amplifier.

The size of heat sink required for the output transistors depends on the ambient temperature range, the type of output transistor and the type of service considered. For example the most severe test is for germanium transistors tested under full load current conditions into a reactive load and at a high ambient temperature. Rather than deal with large heat sinks for arduous duty, the author feels that it is better to specify silicon output transistors where severe conditions are likely to be encountered. For normal domestic duty into loudspeaker loads the cheaper option of germanium transistors is perfectly satisfactory. In fact germanium transistors usually give far lower distortion due to their better linearity.

Two output circuits are therefore given, the silicon n-p-n circuit appearing in Fig. 2. The supply polarity is unchanged so that the same power supply will drive either configuration. The amplifier chassis is a perfectly adequate heat sink for the two circuits, although it is not wise to test the germanium circuit under odd load conditions for more than short periods.

Output stage protection

The protection of transistor amplifiers against load conditions is one of the factors that has restricted the use of these amplifiers in the past. Anyone who has experimented with power output stages will have discovered the extreme speed with which output transistors can be

destroyed. Indeed the author has a very large graveyard of power transistors that were sacrificed in trying to find a complete answer to the problem.

The protection system used in this amplifier is the best compromise that can be reached at reasonable cost. The author has not managed to blow up any transistors with the circuit given even under severe reactive loads, so 100% protection should be given to any accidental short-circuits of the loudspeaker leads. Performance

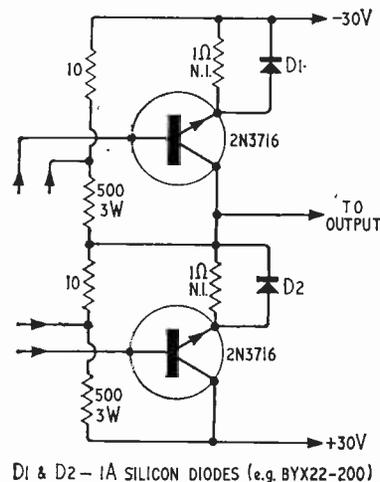


Fig. 2. Alternative output circuit for silicon power transistors.

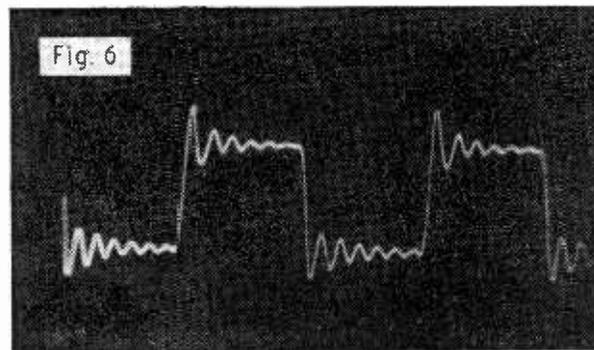
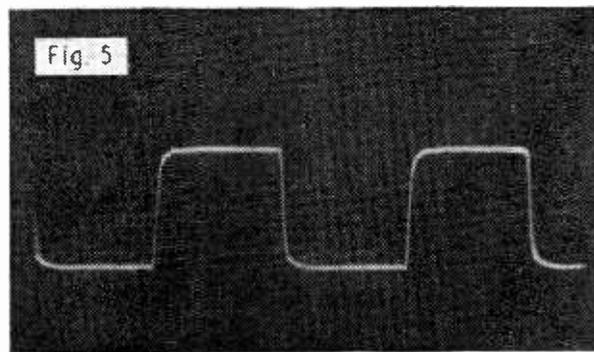
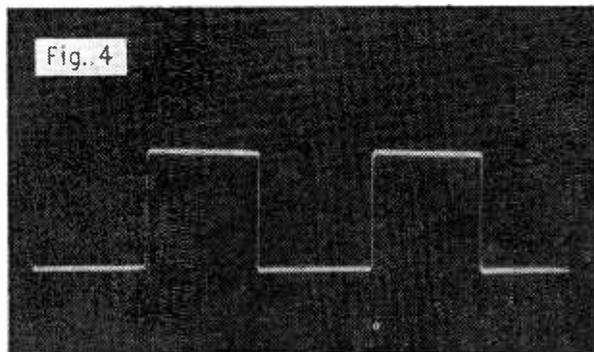
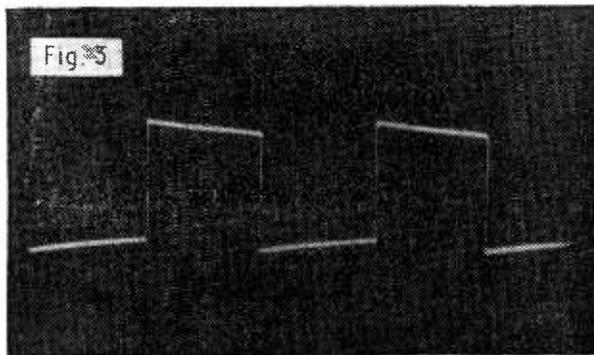


Fig. 3. Amplifier response to 100 c/s square wave with 16 Ω resistive load.

Fig. 4. Response to 1 kc/s square wave, 16 Ω resistive load.

Fig. 5. Response to 10 kc/s square wave with 16 Ω resistive load.

Fig. 6. Response to 10 kc/s square wave with pure capacitance load of 0.47 μ F.

with electrostatic speakers is also good, and no power transistors have been lost due to the low reactance of such speakers at high frequencies.

The protection is split into two parts. First, the power output transistors are arranged to give automatic current limiting at about 130 per cent of rated peak output current. This is produced by the diodes strapped across the primary of the driver transformer. The drive voltage to the output transistors is nearly directly proportional to the load current due to the voltage developed across the emitter resistors. Hence limiting the peak drive voltage automatically limits the peak output current available.

The second line of protection is that of conventional fusing. This fuse is in the speaker output lead, and is necessary to prevent over-dissipation of the output transistors, particularly at low frequencies. If the amplifier is driven hard into a short circuit, then the power dissipation in the output transistors will be high even with the limited current available. To prevent breakdown it is therefore necessary to remove the short circuit before the output transistor temperature rises to excessive limits. A standard quick-blow fuse gives quite adequate protection and blows in less than half a second under full-drive and short-circuit conditions. With the silicon transistors in the output this fuse may not be necessary, but it is felt advisable in view of the cost of power transistors.

Performance



The final performance of the amplifier is well up to the standards expected of the best valve amplifiers and it does not sound appreciably different. The transient response is perhaps slightly "cleaner" than the best valve amplifiers, but the difference is very slight indeed. There is no "transistor-sound" whatever, and very little listening fatigue even after long periods of listening. As the output stage runs effectively in class A for small inputs and the distortion rises slowly with drive, this effect might be expected. Far too many amplifiers run class B output stages at very low levels of quiescent current so as to economize on heat sink design. This gives rise to bad low-level distortion and consequent fatigue effects.

No attempt has been made to obtain very fast rise-times for the amplifier—after all the amplifier is designed to reproduce the audio frequency range rather than be a transmitter. The stabilizing networks are therefore designed to give the best overall balance between h.f. distortion and stability and the rise-time was left to look after itself. Even so the results are very good as can be seen from the square-wave tests shown in Figs. 3 to 6.


The droop on the 100 c/s square wave is due to the size of the amplifier input capacitor. This droop is not important as is shown by the frequency response in Fig. 7.

The higher frequency square-wave tests are very satisfactory, the rise-time turning out at about 3.5 microseconds. The more important factor of h.f. stability is shown to be adequate as the worst case of pure capacitive load (about 0.5 μ F in this case) gives fairly well damped oscillations. Unconditional load stability such as this is not common in valve amplifiers and is very unusual in transistor amplifiers.

The step-network in the collector of the first transistor cuts the loop gain at the high-frequency end of the spectrum and assists in the stabilization of the amplifier. The lower the frequency at which this cut starts, the better is the h.f. stability but the poorer is the h.f. distortion. The time-constants chosen in the circuit are about the optimum, as the distortion at full power output is only about 0.4% at 32 kc/s. The distortion characteristics are

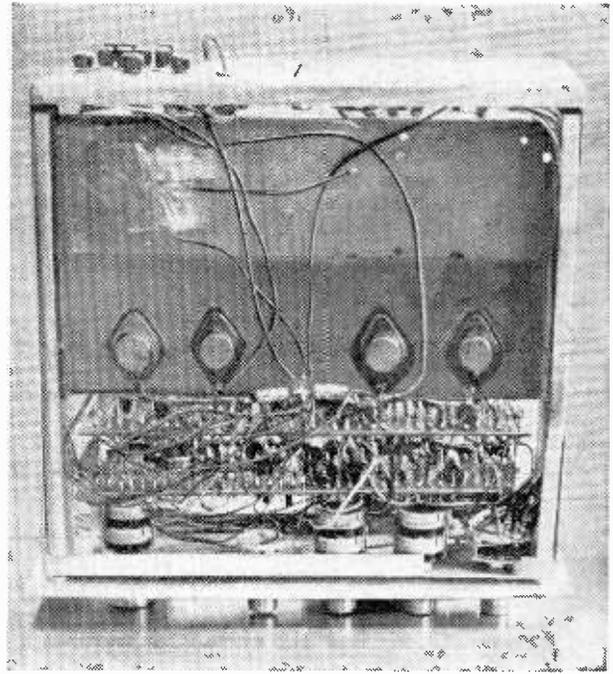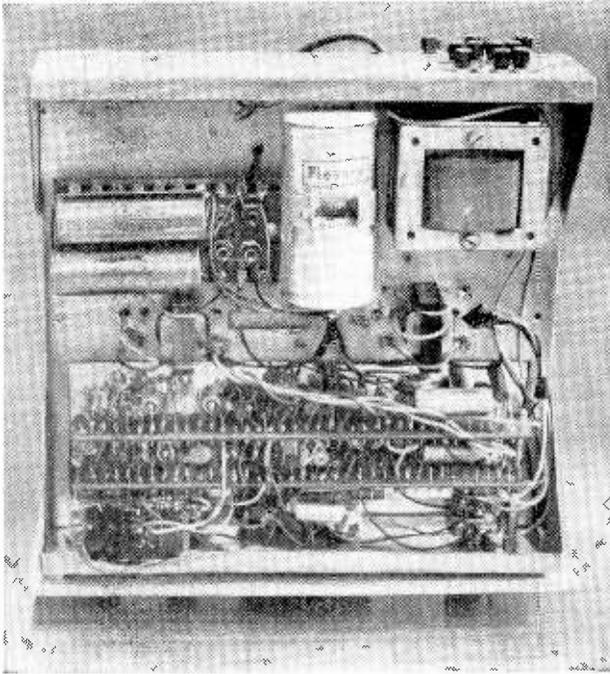


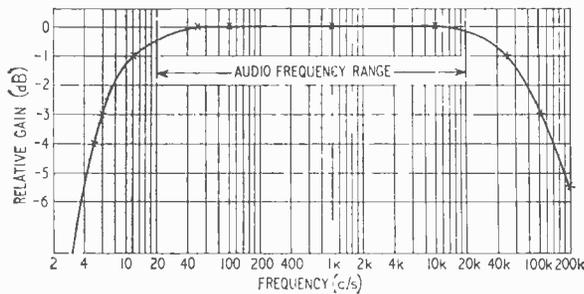Top and underside views of the complete chassis. Note the heat sink for the output transistors.



Left:—Fig. 7. Overall response of power amplifier.

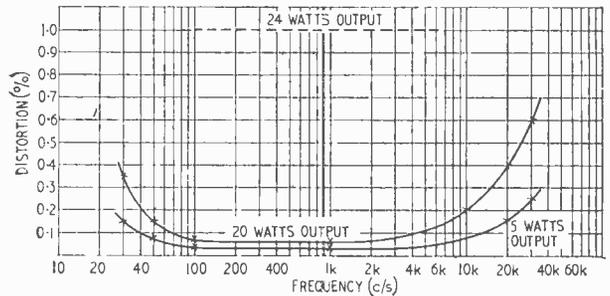Below:—Fig. 8. Distortion characteristics of cascaded amplifier and preamplifier, 16 Ω resistive load.



shown plotted in Fig. 8, where it is seen that full power output is obtainable up to over 40 kc/s. The distortion over the range of 20 c/s to 20 kc/s is very low compared with normal valve and transistor amplifiers which generally have rapidly rising distortion characteristics at the extremes of the audio range. Indeed quite a few amplifiers are unable to deliver full power output at 20 kc/s.

To obtain this performance it is necessary to have a well-regulated power supply so that the main h.t. is maintained under full drive conditions. After several attempts at various circuits it was decided to use an unregulated h.t. supply with a capacitor input filter. Provided that the transformer is of adequate size, then the regulation can be held to about five volts swing. This is quite adequate, and the complexity and cost of a regulated supply were felt to be unnecessary—particularly as two supply lines are involved.

Constructional notes

The driver transformer is wound with 200 turns of 30 s.w.g. d.s.c. trifilar wire on a $\frac{3}{4}$ in square core made of Radiometal. The author is not aware of any source of trifilar wire, so this means in practice that three wires are

SPECIFICATION

- Rated input for 20 W output into 16 Ω load: 500 mV.
- Distortion at rated power output at 1 kc/s: <0.1 %
- Load stability: unconditional.
- Hum and noise: >80 dB down on full output.
- Rise-time: <4 μs.
- Short-circuit load performance: proof against accidental drive into short-circuit loads for short time periods. For long overload periods there is a small region of continuous sine-wave driving level where the output transistors can be damaged by overdissipation. This is most unlikely to be met in practice, and with music or speech drive will not be significant.

wound on the core at the same time and as close together as possible. This method of winding gives an extremely low value of leakage inductance and in practice is negligible.

The emitter resistors of the output stage must be very low in inductance. A zig-zag of resistance wire is quite suitable, but a coil may double the distortion at 20 kc/s. For this reason commercial wire-wound resistors are not suitable as they stand. Even one foot of straight wire in the emitter circuit produces a noticeable effect on the distortion at 20 kc/s.

The size of the heat sinks for the output transistors will depend on the ambient temperature range and type of service. For laboratory use it would be advisable to use heat sinks having a thermal capacity of better than 3 deg C per watt, but this is felt to be unnecessary for music reproduction. Three inch squares of $\frac{1}{8}$ in blackened aluminium will be quite adequate, or alternatively the author's method of $\frac{1}{8}$ in blackened aluminium plate bolted to the amplifier main chassis enables the area to

be reduced below this figure. In this case, however, it is essential that thin mica washers and silicone grease are used for insulation to prevent short-circuits.

The thermal stability of the output stage is best checked with a millivoltmeter across one of the emitter resistors. This voltage should not rise above 100 millivolts when the amplifier is undriven after a period of operation into its correct load. If this value is exceeded there is the risk that thermal runaway will result, and this indicates that the heat sink size is inadequate.

Caution must be taken with the wiring so as to avoid spurious feedback effects. In particular, the output stage emitter and collector leads must be kept as short as possible, and the main h.t. decoupling and smoothing capacitors as close as possible. The shorter the leads carrying these heavy current class B waveforms the better. If care is taken with the wiring, then there is no reason why the specification given should not be met.

(Details of a pre-amplifier design will be published next month.)

LASER TELEVISION DISPLAY

AN experimental television display system using deflection and modulation of a laser light beam instead of an electron beam has been developed by a group of workers at the Zenith Radio Corporation, Chicago, U.S.A. The methods of deflection and modulation, which both depend on diffraction of a laser light beam in ultrasonic waves in a water cell, were outlined by Dr. R. Adler at the recent Sixth International Conference on Microwave and Optical Generation and Amplification sponsored jointly by the I.E.E. and I.E.R.E. at Cambridge (see also p. 572). A helium-neon gas laser, producing red light, is used. Deflection angles achieved are small, but are sufficient to allow 200 picture points to be resolved along a scanning line and a 3-Mc/s video signal to be displayed on a screen.

In the deflection system, the laser beam is directed into a water cell through which ultrasonic waves of length Λ are propagated by a transducer driven from an 18 to 34 Mc/s sinewave source. The light rays, of wavelength λ , strike the water wavefronts at a narrow glancing angle, θ . The acoustic waves produce an optical diffraction "grating" in the water composed of strata of different refractive indexes (i.e. strata of different densities resulting from the compressions and rarefactions set up by the transducer). The spatial period of this "grating" is, of course, Λ , the acoustic wavelength. A diffracted beam of light (composed of the in-phase diffracted rays) emerges from the cell, and this also is at an angle θ to the wavefronts. In this phenomenon, called "Bragg reflection" after Professor Bragg's famous work that led to X-ray crystallography, the angle θ at which the emerging light is at maximum intensity is given by $2\theta = \lambda/\Lambda = \lambda f/v$, where λ and Λ are as defined above, f is the frequency of the ultrasonic waves and v is the velocity of these waves in water. As can be seen from this law, variation of the ultrasonic frequency causes the angle of the emergent beam to vary, and it is this phenomenon which is used for scanning. The transducer drive frequency is, in fact, varied over the 18 to 34 Mc/s range mentioned above in a sawtooth function of time to give a line scan. Dr. Adler stated

that all the incident laser light could be diffracted with an electrical input of less than 1 watt.

For very small scanning angles the mechanism described above is satisfactory, but theoretically the water cell should be rotated with the deflection of the emergent beam, and to obtain the larger scanning angles needed for a television display this rotation is, in fact, necessary. In the Zenith system the effect of cell rotation is obtained by rotating the ultrasonic wavefronts as the transducer drive frequency changes, using a phased array of transducer elements. The number of resolvable light spots on a screen, N , which can be obtained by the system is given by $N = \Delta f \cdot \tau$ where Δf is the ultrasonic frequency change and τ is the transit time of the acoustic waves across the optical aperture.

Intensity modulation of the laser beam is obtained by a similar diffraction process in an acoustic cell, and this was first used by Scophony Ltd. in London before World War II, for modulating light from an arc lamp in a large-screen television system.* The basis of the method is that the intensity of the light beam diffracted by the acoustic cell is proportional to the amplitude of the ultrasonic waves in the water, so the video signal is used to amplitude-modulate the signal driving the cell transducer. The laser beam traversing the intensity modulating cell is made wide enough to encompass several picture elements, which travel across the beam at the velocity of the acoustic waves. As in the Scophony system, the horizontal beam deflection process nullifies the apparent motion of these elements and makes them stand still on the screen.

One of the British organizations working on deflection of laser beams is Mullard Research Laboratories. Both they and Zenith are interested in other applications besides television, such as information storage for electronic data processing systems.

* "Scophony Television System," *Wireless World*, 23rd July 1937, p. 78. Also "The Supersonic Light Control and its Application to Television with Special Reference to the Scophony Television Receiver," by D. M. Robinson, *Proc. I.R.E.*, August 1939.

Corona-generated Noise in Aircraft

MEASUREMENT AND CONTROL TECHNIQUES

By C. E. COOPER

EITHER by charging action in the Van de Graff manner, or by the mere fact of its irregular shape in existing atmospheric electrostatic fields, an aircraft in flight can produce locally intense dielectric stress in the layers of air immediately adjacent to its skin. With sufficiently high stress the air dielectric becomes ionized, and resultant current flow or "corona" can generate radio noise which, coupled into the aircraft's receiving aeriels, is quite capable of totally disrupting communication and radio navigation.

The effect is usually most serious on the lower-frequency systems, such as a.d.f. (automatic direction finding) which operates from 150 kc/s to 2 Mc/s. In this system, the processed outputs of a loop (or goniometer search coil) and an omni-directional or sense-finding aerial are used to operate servo motors which drive the loop towards a null and remotely indicate this null position. The system provides both relative heading and homing facilities, and in the presence of noise the dial indicator may either "hunt" erratically or even (much worse) indicate a false bearing.

The frictional, or tribo-electric, charging process results from the high-speed brushing of air or airborne particles past the aircraft skin. Charge magnitudes from this process can be substantially affected by the nature of skin finish materials, treatments and adulterants, but the highest charge rates occur where ice crystals are precipitating out from a very cold, moist atmosphere.

Charge magnitudes have been further extended by the widespread use of pure-jet engines, which gulp fantastic quantities of air (together with particle content and the occasional bird) past their internal surfaces, and so supplement charge generation from normal airflow over the aircraft skin. This tribo-electric charging by the engines is itself additional to that arising out of the combustion processes.

Fig. 1(a) shows a typical recording of charge rate during take-off and climb of a BAC 1-11 aircraft. The circumstances are of constant throttle setting, implying no local restrictions upon engine noise. Following take-off, charge rate rises rapidly to a maximum after some few minutes (and thousands of feet) of climb. As automatic processes reduce fuel consumption rate with increasing altitude and speed, charge rate also decreases, but more slowly than it rose, becoming virtually constant by some 15,000 ft of altitude. A marked step down can be seen where throttle setting is reduced at the top of the climb, some 26,500 ft in this case.

In Fig. 1(a) the greater part of the charge can be assumed to be due to combustion effects, with the climb being entirely through clear air, in which tribo-electric charging is at a minimum, though not non-existent. For comparison, Fig. 1(b) shows (to a different scale) the far more erratic variations in charge rate when the aircraft is in level flight through light precipitation conditions. In this case, with the jets throttled back, charge from combustion products is small.

However generated, charge becomes stored in the capacitance between the aircraft skin and some ill-defined outer field boundary, stressing the air dielectric between them. Such stress may be either supplemented or opposed, depending upon the polarity of any existing atmospheric potential gradient, as is experienced when


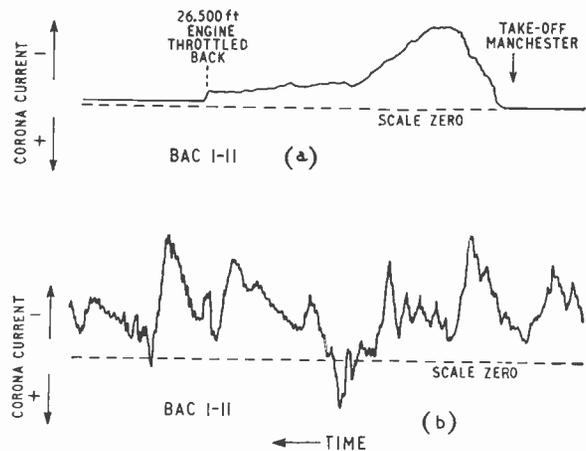


Fig. 1. Corona current measured during flights of BAC 1-11 aircraft: (a) following take-off in clear air; (b) level flight in conditions of ice precipitation.

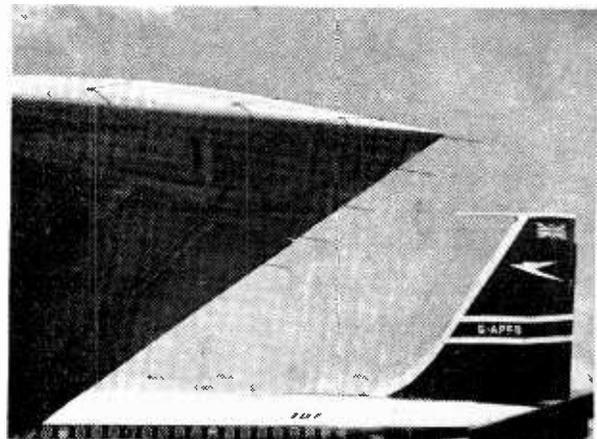

Dischargers on trailing edge and tip of a wing on a Boeing 707.

C. E. Cooper is general manager of Chelton (Electrostatics) Ltd., manufacturers of aircraft aeriels and aircraft static discharger systems. After working with Mazda on valve development he became a lecturer at South West Essex Technical College. He then joined Easco Electrical Ltd., becoming works technical manager. Before going to Chelton, he jointly formed two small service companies but later sold these interests "when lack of technical interest outweighed the financial advantages of company ownership".



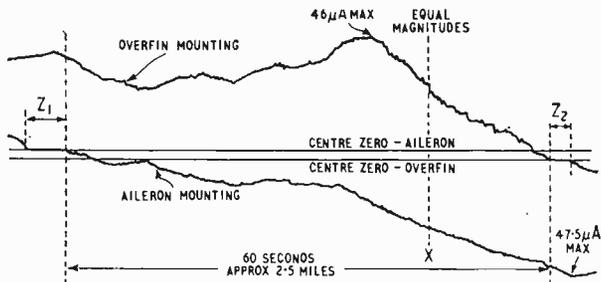


Fig. 2. Section of corona current recordings made at two extremities in an HS.125 twin-jet executive aircraft flying between charged clouds (altitude 9,000ft, air speed 150 knots). Each trace shows corona current through a single discharger mounted as shown. Z_1 and Z_2 indicate periods of zero discharge.

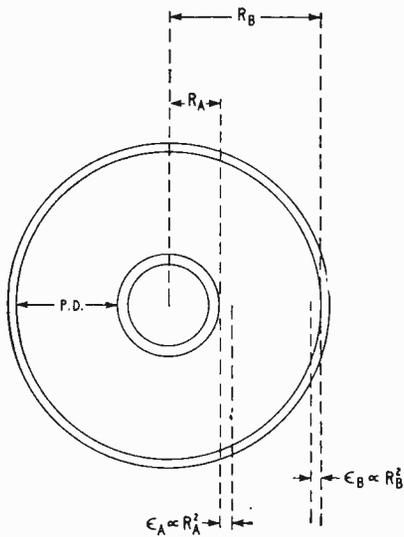

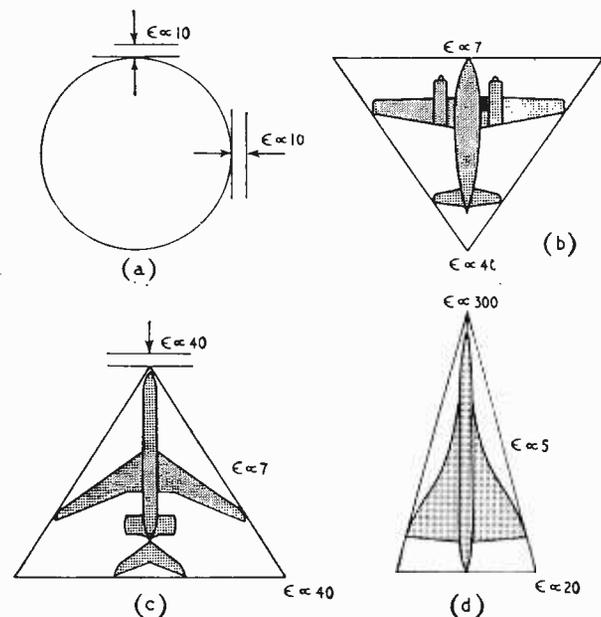Left: Fig. 3. Potential gradient between two concentric spheres A and B with radii R_A and R_B .



Below: Fig. 4. Potential gradient variations with different slopes: (a) circular disc; (b) older type of aircraft; (c) modern jet aircraft shape; (d) supersonic jet aircraft.

the aircraft changes height or flies between charged cloud formations.

The trace recording of Fig. 2 provides indirect indication of the variations of electrostatic field as measured at two different extremities of an HS.125 aircraft flying obliquely between charged cloud areas. During the sixty-odd seconds of this recording, stress changes from maximum at the tail fin to maximum in reverse polarity at one wing tip, passing through a stage at "X" of considerable and equal but opposite stresses at these two measuring sites. At this instant, the net aircraft charge accumulation is zero, but because of aircraft span in the spatial field, intense dielectric stress exists in air layers adjacent to the aircraft extremities. Since the overall effects are similar, though not identical, to those frictionally produced, they are initially considered as a third form of aircraft charging.

No aircraft system at present used suffers from the mere existence of charge, but since the charging processes are typically of constant-current form, p.d. between aircraft and boundary rises continuously until limited by some form of dielectric breakdown. In extreme circumstances, this could be a minor lightning flash, but, far more commonly, limitation occurs at much lower potential by the process of atmospheric ionization, permitting release of current back into the atmosphere at a rate balancing that of acquisition.

The ionization condition, and consequent radio noise generation, can be reached in seconds and continuously maintained from the rates of charge which have to be anticipated for possibly 5% of total short-stage flying time. Consideration of the function of devices used to control these effects requires an understanding of how gradient magnification occurs.

Potential Gradient Between Spheres

With p.d. between two concentric spheres A and B, as shown in Fig 3, then immediately adjacent to the two spheres the respective gradients ϵ_A and ϵ_B will be in proportion to the surface areas, i.e. to the squares of the radii. An increase of outer sphere radius (only) will therefore increase the disparity between ϵ_A and ϵ_B in greater proportion than that of the spacing increase. This in turn means that to maintain constant gradient ϵ_A by the inner sphere requires an increase of p.d. which is less than proportional to the spacing increase. For a sufficient disparity of dimensions, the radius of a small object virtually fixes its immediately adjacent gradient in proportion to applied p.d., regardless of the distance across which it is applied and hence also of the shape of the field outer boundary.

For a spherical object, gradient is of course the same across any fixed distance radially from any part of the surface, but for any non-spherical shape, a constant applied potential will produce different gradients adjacent to every different radius. In adapting this principle to aircraft circumstances, aerodynamic shapes are such that consideration must initially be restricted to two-dimensional forms. If potential applied between the flat circular disc (flying saucer?) of Fig. 4(a) and some distant boundary is such as to produce ten units of gradient adjacent to any place on the edge, changing to the almost equilateral triangle of Fig. 4(b) might produce some 7 units at the centre of each flat side, and perhaps 40 units at each apex, depending upon their tip sharpness. As shown, the triangle at (b) can contain the idealized outline of an older shape of aircraft; in (c) the triangle is reversed to contain a later aircraft shape. The significant difference is that, in the latter

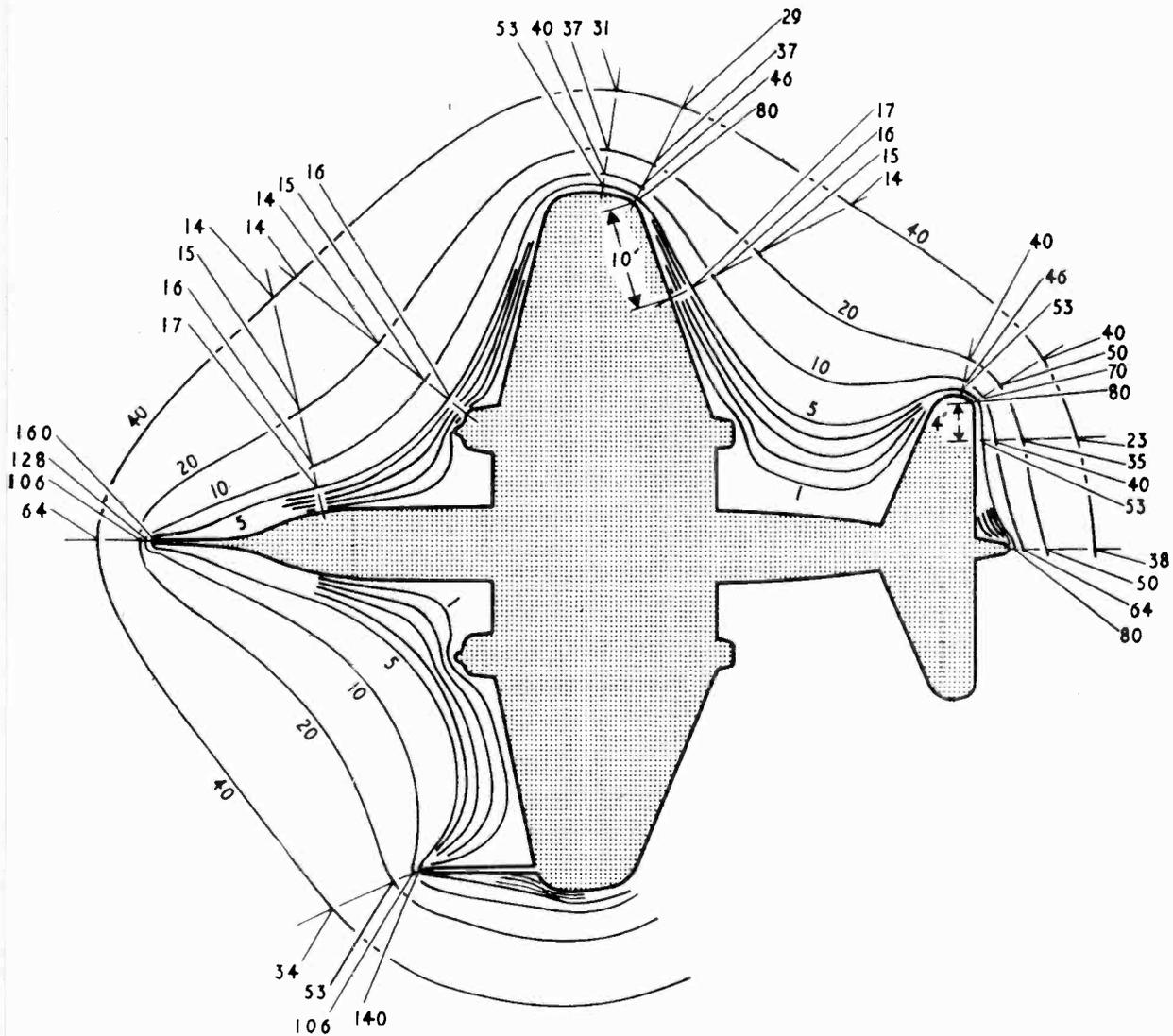


Fig. 5. Equipotential contours and derived gradients (groups of four figures) for the Canberra aircraft.

case, one of the high-gradient positions looks in the forward direction, imposing practical difficulties not present when high-gradient positions look only aft or athwart.

In all these shapes, the relative gradients indicated are still only the mean values over some arbitrarily chosen distance from the outline. Fig. 5 shows how these mean values vary with span of measurement for a Canberra aircraft. Gradients (in purely relative units) are derived from the equipotential contours, and each row of four figures averages the gradients out to contours 5, 10, 20 and 40 respectively. The projection of the nose and wingtip pitot tubes from the main bulk produces adjacent gradients which are higher than for any other part of the aircraft.

The figures marked are best regarded as the *local* mean gradients, as determined by aircraft shape out of the *general* mean gradient existing around the aircraft as a whole (p.d. between aircraft and surroundings).

Consider a p.d. applied between two spaced equal spheres; provided the gap between them is smallish

relative to sphere radius then gradient will be constant across the gap. Halving the gap by moving the spheres closer together will result in the mean gradient being doubled without changing its constancy of division. The same doubling of *mean* gradient could otherwise have been produced by bridging half the gap with a sharp-pointed spike, but in this case the gradient immediately adjacent to the point may be up to hundreds of times *above* the mean, balanced by a more moderate reduction *below* the mean across most of the gap.

The degree of gradient magnification depends mainly upon the point radius, but is also affected by stem thickness behind the point, and by its projection length from the main bulk of conducting surface. This process of magnification can be utilized to control the positions at which local gradient is highest, and hence at which corona will start for the lowest possible aircraft potential. Corona is gaseous ionization, occurring when sufficient p.d. exists between electrodes whose shape and spacing are such as to produce intense local increase of gradient

above the average across the gap. Thus corona occurs adjacent to both electrodes in a point-to-point gap, but at only one in a point-to-flat surface gap. It can also occur at both extremities of an isolated conductor in an otherwise linear field, which represents the HS.125 conditions at "X" in Fig. 2.

The radio interference produced by ionized gas or vapour in a neon tube is quite well known, but r.f. noise signals can be radiated from ionized gas without necessarily also producing visible light.

Noise signals are radiated directly from ionized gas, with a random frequency spectrum, and magnitudes tending to inverse relationship with frequency but often significant up to the v.h.f. band. After reception via a channel of finite bandwidth, the noise signals are comparable with a suppressed carrier modulated by white or random noise, producing a characteristic "hiss" after detection.

Where conditions produce a gradient only slightly above the ionization threshold, the corona discharge can have an interrupted or pulsed form, and this results in the received and detected noise having some predominant pitch of note. For increasing gradient around the threshold condition, this note typically changes from a "ticking" sound, through some very rough, guttural notes to a whistle of pitch eventually rising above audibility or response.

CONTROL METHODS

There is no effective method known to prevent the processes of charge acquisition by an aircraft, which, with a capacitance typically some hundreds of pF, will rise in potential at a rate of 100,000 volts per second from a charge rate of microamperes. Rates up to a milliamp or more have been recorded, still without including thunderstorm conditions. With potential rising at such rates, even the mythically smooth-outlined aircraft of publicity pictures must very quickly reach the condition where corona occurs from some or many parts of the aircraft.

Paradoxically perhaps, therefore, the simplest approach to noise control is to make corona occur more easily. This can be done by placing sharp projections at aircraft extremities to produce corona by large magnification of only quite low general gradient. With the corona path confined to dimensions comparable to the point radii, noise radiation is drastically reduced.

The numerous practical objections to an aircraft bristling with rigid sharp points have led to the development of the discharge tip shown in Fig. 6, which in various assemblies, has recently become virtually standard for almost all British and many other aircraft types. The tip comprises a small tuft of a hundred or so nichrome wires of about $\frac{1}{2}$ thou' diameter (51 s.w.g.), spread into a crown around a tiny plug inside a supporting tube. If allowed to bunch they would function only as single blunt point, so the flared polythene moulding is fitted to create turbulence in the airflow and so keep sufficient number of the wires separated to function as individual sharp points.

Release of corona via a very sharp point provides substantial, but still insufficient, reduction of r.f. noise generation, and the process is extended by inclusion of high series resistance. The actual value used is a compromise between greatest reduction of noise and the avoidance of undue restriction of the d.c. component of corona current. Major current restriction is provided by the gaseous corona path itself, with a slope resistance around $10^9 \Omega$ for the tip of Fig. 6. Series resistance

additions of up to some $50 M\Omega$ are therefore feasible without substantially restricting current. The series resistance appears both to reduce the ratio of noise-current-to-d.c. component, and also to act in conjunction with tip stray capacitance to reduce the length of path through which noise current flows, and so confine radiation principally to the ionized air. To have maximum effect series resistance needs to be concentrated as closely as possible to the corona point.

A complete discharger device is constructed with the corona-tip supported on a 9-inch tapered rod of glass-fibre, surface coated with high resistance material. Some 10 to 40 dischargers of this type are commonly grouped in trailing or semi-trailing positions near to the various outermost extremities of an aircraft.

To maintain the essential semi-trailing position for the corona tip, forward facing assemblies have been produced recently; these units are designed to mount on pitot heads or the lightning diverter probe often fitted at the apex of a radome. The three discharger tips on each unit are critically angled, with spiral resistance tracks around the mounting cone.

Simulation and measuring equipment.—To optimize design and demonstrate performance of discharger devices, the equipment shown in Fig. 7 was constructed in simulation of an aircraft wing section. The high voltage generator is of the Cockcroft-Walton type, with 20 stages providing an off-load rectified output of some 120 kV from the 5 kV 50 c/s available from the transformer, and adjusted by a Variac. The d.c. output voltage is measured by a 10-microamp meter in series with a long chain of five-hundred $20 M\Omega$ resistors contained within about 50 ft of coiled-up polythene tubing.

High voltage is applied to the wing section through

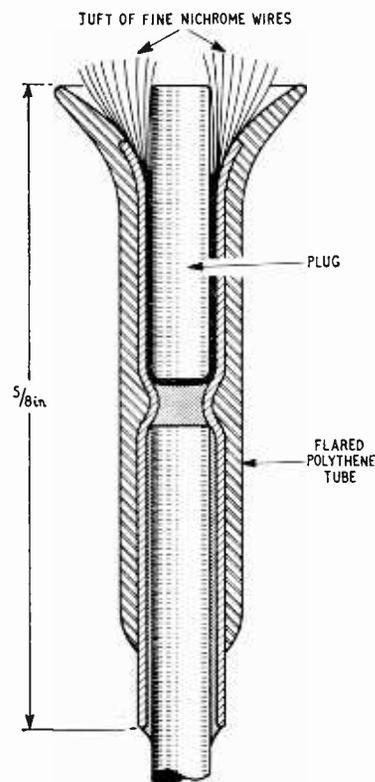


Fig. 6. Cross-section of tip of discharger fitted to aircraft.

a pair of microammeters set into the wing, separately measuring corona released directly via the wing or via lightly insulated inset tabs, on which dischargers under test are normally fitted. Measurements are generally in terms of the applied potential and other conditions which result in various standard values of corona current, ranging from threshold (taken as 1.0 μ A) up to 50 μ A. Comparative noise measurements are then made for the various conditions and currents.

Noise radiated during corona discharge is picked up by a capacitance type aerial, too small to approach resonance within the 0.5 to 5.0 Mc/s pass-band of the receiver aperiodic amplifier. This pass-band was chosen to overlap into the frequency ranges used for m.f. automatic direction-finding and h.f. communication, but subsequent interest has moved more towards the lower frequencies used by Decca and other long-range navigational systems.

Amplified r.f. output is conventionally rectified, passed via a calibrated attenuator to a transistor a.f. amplifier, and then switched to either a speaker or a noise meter. The whole receiving and measuring equipment is mounted in, or on, the wing section, since it all necessarily operates at the high potential of the wing.

The applied potential which will produce less than a microamp of corona from, say, an exposed bolt-head will produce perhaps 10 to 15 microamps from a typical discharger, but with a received noise level some 50 dB lower. Even this residual white noise will be less objectionable in form than the typically rough note due to corona from the bolt-head or similar minor projection.

Certain discharger designs show marked directional or polarization effects in their noise radiation, with fairly sharp nulls as the corona point is oriented. By optimization of this characteristic attempts have been made to secure even better than the 50 dB noise reduction mentioned, but there is considerable doubt over the possibility of maintaining or even knowing the true null positions in aircraft service. In fact, the noise level radiated by the discharger design shown has proved acceptable, and the major problem is to prevent even trifling corona current from starting elsewhere than at the dischargers.

The optimum installation is a complex function of discharger type, number and siting. It has to include such factors as air pressure differentials, exposure of sharp extensions during control-surface action, and the nature of the various normal projections, particularly aeriels. It is quite possible for an m.f. system to collect and suffer from noise radiated during discharge off the aerial of, say, a v.h.f. system not itself affected by the noise.

The field configuration which will exist around a particular aircraft is most readily determined to a sufficient degree of accuracy by a few two-dimensional plots on resistance analogue paper. This graphite-impregnated material has a fairly uniform resistance of about 3000 Ω per square (i.e. between opposite edges of a square of any dimensions). A representation of the aircraft shape, or some section of it, together with a surrounding field boundary,

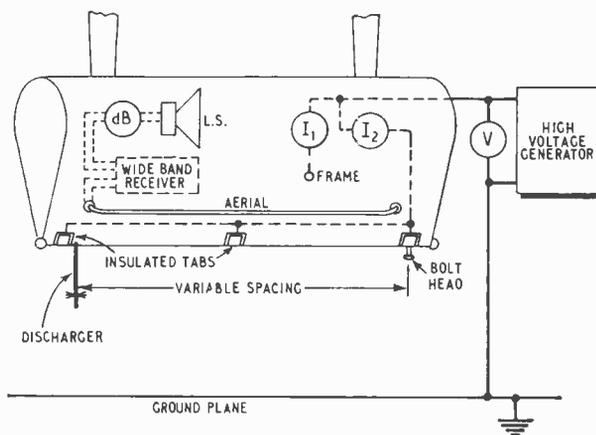


Fig. 7. Block diagram of test and measuring apparatus mounted inside simulated aircraft wing section.

are first outlined in wax pencil, and then edged or filled-in solid with brush application of a highly conducting paint (Fig. 8). The material used is a dispersion of metallic silver powder in methyl iso-butyl ketone, which air dries to a few ohms per square, a negligible value compared with the paper resistance. It should be noted that most of the so-called "metallic" paints are in fact non-conducting. Contact to the conducting areas can conveniently be made via pieces of aluminium foil, held in place by small strips of self-adhesive tape, and brushed over by the conducting paint.

For present purposes the shape of the field boundary is immaterial, provided its minimum spacing to aircraft shape is not less than about half the aircraft's largest dimension (in scale, of course). At this minimum spacing, the field pattern adjacent to aircraft shape is substantially unaffected by boundary shape. Potential now applied between the shape and the boundary will

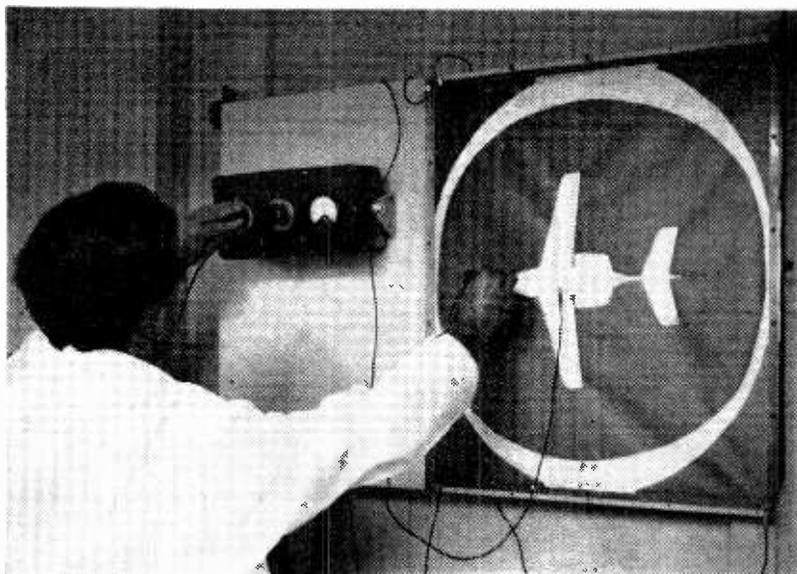


Fig. 8. Apparatus for plotting analogues of equipotential electric fields surrounding various shapes of aircraft.

distribute itself across the intervening resistance paper areas as an analogue of the electrostatic field which would exist around similar shapes in air, or any uniform dielectric. The potential distribution can be explored with a high-resistance voltmeter, but is far better done by forming a suitable bridge circuit, and exploring for null balance against a series of potentiometer settings to produce equipotential contours.

Instead of random exploration, it has been found easier to explore along a series of lines normal to their origin at the aircraft shape, as previously marked onto the resistance paper in wax pencil (i.e. non-conducting). It is better still to mark these lines along the quite readily estimated direction of maximum gradient away from their origins, and so achieve the highest sensitivity of off-balance indication.

Use of a d.c. (9V) supply for the resistance-paper bridge has been found useful in providing indication of the direction of probe movement needed to approach balance. The four-transistor d.c. amplifier used provides off-balance indication down to below a millivolt, with input resistance sufficiently high that an off-balance setting does not materially load the paper bridge to distort potential distribution.

Exploration is conveniently made by a probe formed of a ball-point pen tip (minus ink, of course) which can be rolled across the paper without need to lift and re-apply. Located balance positions are then marked on, again in wax pencil, although better accuracy is achieved by using a sharp-pointed probe for exploration, which

can then prick through the resistance paper to mark an underlying cartridge paper or similar. Joining up each series of equipotential positions provides contours as in Fig. 5 of correct shape but in purely relative terms, from which the relative gradients can be obtained by measurement either of the spacing out to a particular contour, or by interpolation to the contour reached by some constant spacing.

This last-mentioned is of most interest in order to provide the relative mean gradients effective over the length by which a discharger will project from the airframe. To obtain better accuracy across such a dimension, a final plot is made of each significant extension, using as field boundary one of the contours previously plotted, possibly with corrections to include effect of the third dimension, as estimated by comparison with plots in other planes. Since the contour boundary has true shape, there is no minimum spacing limit imposed, and the plot can be large scale.

In Fig. 9 the dotted line indicates the scaled dimension of discharger projection out from its mounting surface. Potential applied across the resistance paper from wingshape to contour boundary is set (by a series rheostat) to produce a convenient whole number of voltage at the discharger line where it most closely approaches the boundary, i.e. the position of highest gradient. Other gradients relative to the maximum can now be plotted for various distances away from that of maximum.

This information is then used in conjunction with that from graphs of discharger performance grouped at different spacings to produce an aircraft layout at graded spacings which will approach the ideal of equal current released by all dischargers at any given aircraft potential.

In-flight corona recordings are achieved by fitting special dischargers insulated from the airframe, each with a single wire brought in to a multi-channel strip paper recorder, with circuit completed to a common airframe connection. Each channel needs to be protected by shunt diodes against the excessive currents which will flow when in the vicinity of thunderstorm activity.

The measurement is one of fluctuating unidirectional current, with electrons normally leaving the discharger, i.e. the aircraft having negative polarity relative to its surroundings. As already indicated in Fig. 2, reverse direction of current flow is also possible, due to atmospheric gradients rather than aircraft charging. For this reverse polarity, the dischargers have closely similar threshold potential, but a rather higher slope resistance.

The area from which charge is released does not directly indicate the area or method of acquisition, but such information can, with experience, be derived from the pattern of corona variations with time and the differentials, if any, between corona in areas of known equal exposure.

To gain the necessary statistical information, an airline aircraft has for some months past been making corona recordings during its normal passenger flights over most of the European continent. Whenever practicable, the corona recordings are accompanied by taped observations of the ambient conditions, the radio noise level during discharges, and the overall effects upon particular navigational systems. The results of this programme are hoped to provide the first objective standards by which to make comparative assessments of the susceptibility of different aircraft designs in experiencing static charge effects, and of the value of various discharge systems in minimizing the effects.

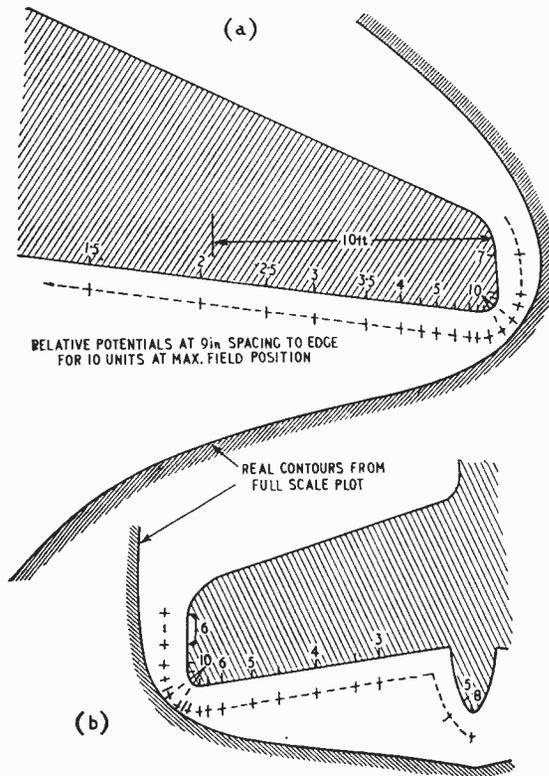


Fig. 9. Potential gradients at (a) wing and (b) tail of HS. 125 executive aircraft.

Titanium Cone Loudspeaker

EVOLUTION AND DESIGN

By E. J. JORDAN, Assoc.I.E.R.E.

SOME years ago a friend gave me a book which he had purchased for 6d from an old bookshop. It was McLachlan's "Elements of Loud Speaker Practice" published in 1935. It makes fascinating and, for the author, somewhat sobering reading, inasmuch as that in over 30 years there has been so little apparent progress in loudspeaker development. Among the many possible loudspeaker types described are the full range push-pull electrostatic loudspeaker and the Blatthaller loudspeaker, forerunner of the French Orthophase. The last chapter is headed "Recent Developments" and introduces firstly the concept of a large moving-coil loudspeaker used together with a horn loaded tweeter in conjunction with a crossover system, and secondly a moving-coil loudspeaker having a small auxiliary cone attached to the centre of the main cone to handle the high frequencies (Voigt, of course). The frequency response of the last-mentioned is comparable to that of many modern hi-fi loudspeakers and is reproduced in Fig. 1. For direct comparison the frequency response of a modern 12 in twin-cone loudspeaker is shown in Fig. 2.

Undoubtedly one of the main reasons for the slow progress has been that at the time the book was written


loudspeaker design thinking was well ahead of the availability of suitable materials and engineering techniques with which to implement the ideas. Modern technology has now provided us with a vast range of metals, ceramics and plastics that allow us to realize the principles established so long ago.

Once valve amplifiers had reached the stage where a few relatively low distortion watts were available, the single paper cone moving-coil loudspeaker emerged as by far the most satisfactory compromise between quality and economics, and continues so to be. With the progressive improvement of broadcasting and recording quality there came a demand for a wider frequency range than could then be obtained from the single paper cone and crossover systems, and double-cone systems were extensively developed. In addition to Voigt, Goodmans Industries were largely responsible for the sophistication of double-cone techniques. This is apparent in their famous "Axiom" range. Many companies developed excellent crossover systems and it is worth noting that, while widely varying techniques were used in tweeter design, the low frequencies were invariably handled by the ever faithful paper cone moving-coil loudspeaker.

The difficulty in obtaining a smooth

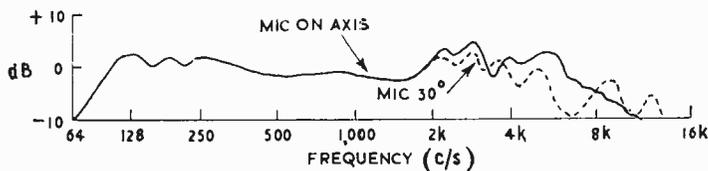
E. J. JORDAN, who recently joined Audio & Design Ltd., of Maidenhead, as a director, started his career in the service department of G.E.C. He then spent twelve years with Goodmans Industries and in 1964 became technical director of Jordan-Watts Ltd. of Hayes, Middx., where he produced the first "modular" loudspeaker.

extended high frequency response from a single cone was practical rather than theoretical. As we shall show later it is necessary to use a flared cone in order to obtain a good high frequency performance, but because of their poor strength/weight ratio paper flared cones were prone to non-linear flexing at low frequencies, resulting in harmonic and intermodulation distortion. Metal cones were tried on and off right from the start but the highly resonant nature of metal precluded these as a satisfactory material for many years. A significant breakthrough in this respect was made by Hugh Brittain of G.E.C. Research Laboratories by using a 6 in straight sided Duralumin cone having a plastics (p.v.c.) edge termination which, together with a controlled deformation in the cone body, largely overcame the resonance problems associated with metal. This resulted in a loudspeaker with a very acceptable frequency response and a harmonic distortion level which was so low that it has not yet been improved upon. Details of this were published in *Wireless World*, Nov-



Above:—Fig. 1. Response curve of twin diaphragm m.c. loudspeaker (Voigt) with tractrix horn about 4ft long and 4ft square at mouth (Reproduced from "Elements of Loud Speaker Practice"—McLachlan, 1935).

Right:—Fig. 2. Response, distribution and total harmonic distortion curves of 12 in twin cone m.c. loudspeaker in enclosure.

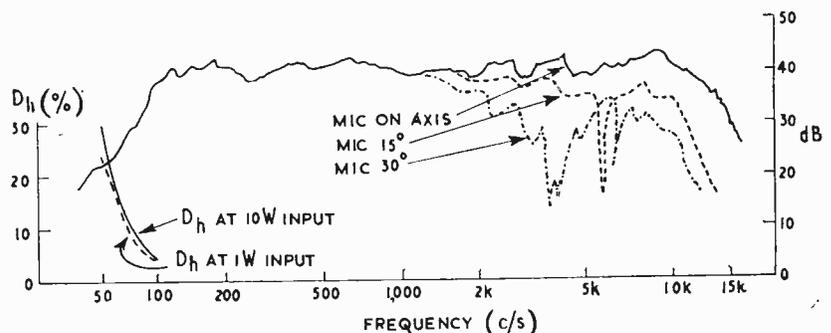

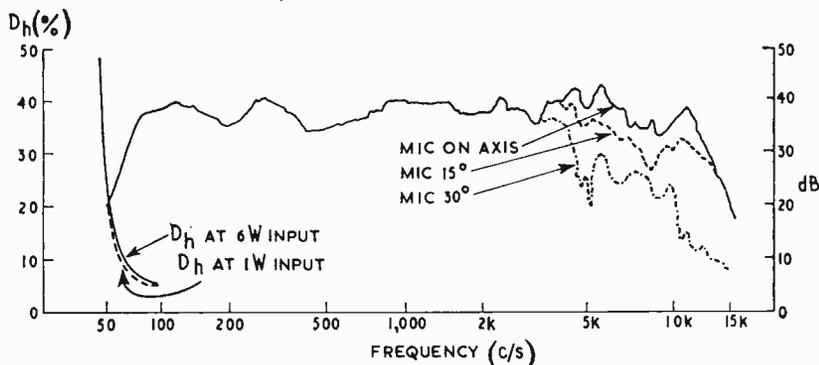


Fig. 3. Performance curves of 8 in hyperbolic paper cone m.c. loudspeaker.

ember-December 1952 and January 1953.

Shortly after this the author worked on the problems associated with flared cones and discovered that the distortion could be reduced to acceptable proportions by the use of (a) a very flexible surround, and (b) a flare following a hyperbolic law. The resulting loudspeaker, now known as the "Axiette," is still marketed by Goodmans. Its response curve is shown in Fig. 3.

Throughout these years the improvement in materials was most apparent in the realm of permanent magnets, which, for a given total flux were a fraction of the size of their pre-war counterparts. Plastics technology was forging ahead and most loudspeaker engineers were keeping a very close watch on this industry, hoping for a plastics panacea to the problems of cone design. This came—not, however, to the protagonists of cone loudspeakers but to the full-range electrostatic loudspeaker.

A direction in which remarkable advances have since been made has been the reduction in the overall size of loudspeaker systems. Theoretically efficiency may be traded for size for a given low frequency limit *reductio ad absurdum*. As usual, practical mechanical problems set a limit, but the vast majority of present-day hi-fi loudspeakers are very much smaller and less efficient than their earlier counterparts—an approach now made acceptable by the availability of domestic power amplifiers with outputs of up to 100 watts. This trend was started by Edgar Vilcher in the U.S.A. when he developed the "acoustic suspension system" which basically comprises a large massive bass cone loudspeaker fitted with a highly flexible suspension and housed in a small airtight enclosure. Implicit in this approach is the use of some

form of crossover system and separate radiators in the high frequencies.

The birth of the now well-known full-range electrostatic loudspeaker was announced in a series of articles in *Wireless World* in 1956 and a completely new standard in sound reproduction was established.

The most significant advantage of the electrostatic loudspeaker over existing loudspeakers was in its transient performance. The importance of transient response has been stressed often enough over the years by the pundits but it has been played down to a large extent by many manufacturers and grossly underrated by the hi-fi public generally. The reason for this may be due to the difficulties associated with making measurements of transient performance compared with simple frequency response curves.

Some indication of transient performance can be obtained from response curves¹. For example, the ability of the moving system to allow sufficient acceleration to adequately reproduce transient sounds is directly related to its high frequency performance. The worst aspect of transient performance, however, is the prolonged "ringing" that can follow a transient. Any transient is composed of a series of harmonically related overtones and any sharp resonances in the system which fall into this range of overtones are often not very apparent on the response curve except to the experienced observer, who can recognize them as tiny, near vertical changes of level. Even this is not entirely reliable because such effects can be produced by other causes. The situation is illustrated by reference to the two hypothetical response curves shown in Fig. 4. It is extremely likely that loudspeaker A would reproduce sounds with a far higher degree of

accuracy than loudspeaker B. Even though B has the flatter curve, the transient ringing associated with the small sharp changes could result in extreme colouration and very poor definition. Curve B could well be described as "angry."

The electrostatic loudspeaker is a perfect example of the above argument. Its measured response curve is unusual and certainly not level (Fig. 5), but it has the one outstanding quality that renders its shortcomings relatively unimportant, and this is the complete lack of colouration (or, in the words of the advertisements, "this loudspeaker lacks character"). It is a salutary lesson to listen to white noise on a loudspeaker comparator while switching between various high quality systems including the electrostatic loudspeaker. All the conventional cabinet systems have pronounced "vowel" sounds which are entirely absent from the e.s.l. (Incidentally, for purposes of educating the ear a good "live" white noise is the sound of car tyres on a wet road.)

All of which brings us back to about the present time. We have inherited a veritable fund of basic principles, the advantage of over 30 years of further development and an almost unlimited range of materials and techniques. Whither now? Faced with this situation, the author adopted the approach now to be described.

Design objective.—The problem was to recreate sound as accurately as possible within the confines of the listening area—in this case the domestic living room or lounge. As a starting point we will assume a medium room of 2,000 cubic feet. The programme material likely to make the greatest demands on the available sound power and frequency range is that provided by a full concert orchestra. We will assume the listening level to be such as to provide a peak intensity at the ears similar to that experienced in a typical seat in a concert hall, and finally we will let the low frequency limit be 30 c/s. For domestic reproduction this frequency is quite low enough since very few recordings extend as low as this and the room dimensions limit bass reproduction to a frequency given by:

$$f = \frac{560}{\text{longest dimension in feet}}$$

From the above information can be calculated the total acoustic power required in the room and hence the

volume velocity (diaphragm area \times excursion \times frequency) required from the loudspeaker (Appendix 1). It is necessary to choose a suitable ratio of diaphragm area to excursion. However, the choice of diaphragm dimensions must be determined in part by a number of other factors which we will now consider.

The loudspeaker diaphragm has to draw its energy from the electrical output of the amplifier and transfer it to the air in the form of sound waves. This transfer is profoundly affected by the impedance of the air load, which in turn is determined by the diaphragm dimensions and frequency. It is well known that the radiation resistance curve abruptly changes shape about the point where $kr=2^*$. This corresponds to the frequency where, assuming a circular diaphragm, the circumference is equal to 2 wavelengths.

Although the entire radiation resistance curve may be exactly represented as a Bessel function, it is usually considered adequate to use the two approximate expressions given in Appendix 2 dealing with the parts of the curve above and below the "knee" respectively.

Consider first those frequencies below the "knee." It can be shown that for the radiated power to be independent of frequency the diaphragm must be rigid and either have a mechanical impedance that is very much lower than the air load or a mechanical impedance that is dominantly mass (known as the condition of mass control). Either of these conditions are realizable in practice but the condition of mass control offers a number of advantages:

1. It renders the low frequency performance less dependent on room acoustics.
2. Performance is less critically dependent on the position of the loudspeaker in the room.
3. It makes domestically acceptable enclosure systems which are necessary in order to secure an adequate low frequency performance.

Above the "knee" of the curve a mass-controlled diaphragm will cause the radiated power to fall as frequency rises at the rate of 6 dB per octave. The polar response becomes progressively more narrow as frequency rises. These two factors obviously render a mass-controlled

rigid diaphragm unsuitable for high frequencies. There are two solutions to the problem. One is to provide a smaller diaphragm and use some form of mechanical or electrical crossover system. The other is to cause the existing diaphragm to reduce its effective diameter as frequency rises. The effect of this is also to reduce the mass of the diaphragm, and since at these frequencies the radiated power is proportional to the effective area and inversely proportional to the square of the mass it follows that the smaller the cone the higher will be the efficiency, the mass and the area being directly proportional to each other (see Appendix 3). Provided the correct ratio of diameter to frequency could be maintained both the radiated power response and the polar response could theoretically be independent of frequency.

Again it is seen that a choice has to be made and it is clearly seen in theory at least that the second arrangement is to be preferred, inasmuch as it does not introduce any abrupt discontinuities in the system. Any arrangement using multiple diaphragm crossover techniques is likely to suffer from three serious drawbacks. First, at the crossover frequency the radiated power is shared between two diaphragms of different size and hence different polar response. This means that there must be an abrupt change in the power response if the axial pressure response is to be maintained, or vice versa. Secondly, the electrical impedance looking into a loudspeaker system incorporating electrical crossover networks must inevitably exhibit considerable phase change about the crossover frequencies. Crossover frequency networks are designed to be matched by constant resistance at all of their terminations, a condition which is never fulfilled in practice. The effects of such a load applied to

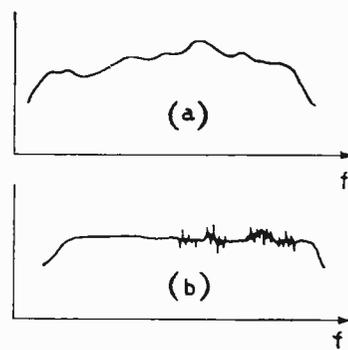


Fig. 4. Curve (b), although flatter, has the "angry" appearance associated with a poor transient response and is less acceptable than curve (a).

the output of an amplifier may in many cases considerably affect the phase of the negative feedback voltages, thereby degrading the performance of the amplifier. Thirdly, the inevitably resonant nature of the crossover system will introduce transient distortion of the type discussed above.

Accepting then the desirability of the "reducing diameter" approach we find that one of the simplest ways of achieving this in practice is to apply the driving force at the centre of the diaphragm only. It can readily be visualized that if the diaphragm were, for example, a stretched membrane of some low-loss material, at the higher frequencies ripples would spread out from the driving point and travel to the edge. If some damping media were applied to such a diaphragm the ripples would undergo severe attenuation as they moved outwards, so that the displacement at the point of application of the force was considerably greater than at any other point and most of the sound radiation would be from this central point. Clearly with such an arrangement as this the effective central working area would be a function of

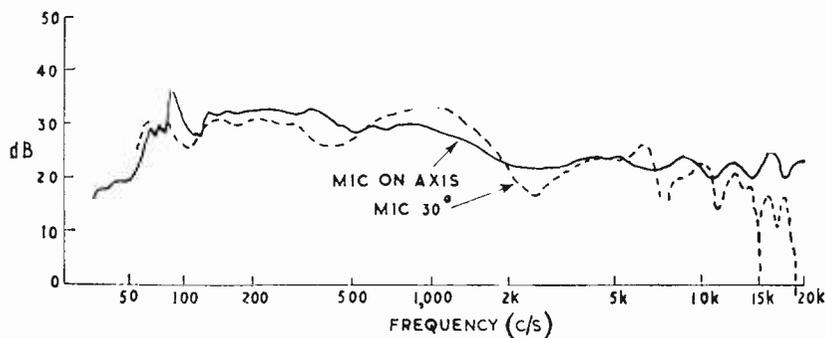


Fig. 5. Performance curves of full range electrostatic loudspeaker.

*Radiation resistance is the real part of the acoustic impedance of the air load. It is plotted vertically in normalized form $R_{r,1}/\pi r^2 \rho c$ against normalized frequency $kr (= 2\pi r/\lambda)$ plotted horizontally (where $R_{r,1}$ —radiation resistance in newton-seconds/metre, r —diaphragm radius in metres; ρ —density of air in kg/m^3 ; c —velocity of sound in m/sec λ —sound wavelength in metres; and $k=2\pi/\lambda$).

wavelength and therefore frequency, thus giving us the type of operation we require.

It is fairly obvious at this point that we have talked ourselves willy-nilly into a fair description of the operation of a single-cone loudspeaker at high frequencies. The single-cone loudspeaker, by its very nature, has intrinsically the right sort of characteristics necessary for full range sound reproduction, and even the poorest examples of this type of loudspeaker provide very acceptable results. This was appreciated, in principle if not in detail, 40 years ago, and, as we have already indicated, this loudspeaker has by far the most satisfactory all round performance for general purpose applications. Its performance has been limited at low frequencies for the want of a good suspension system. The problem at high frequencies is that of producing a cone of such form, material and dimensions as will operate to the precise requirements.

In fact it is no less a problem to define the "precise requirements" in material terms. There has been no tractable mathematical approach for dealing with this other than the author's own very limited contribution which gives no more than an indication of the relationship between the various physical parameters of the cone. This is outlined in Appendix 3. Fig. 6 shows how the effective cone diameter reduces as frequency rises due to cone flexure. The expressions in Appendix 3 show that in order to secure a level response the first mode of flexure must start at

the "knee" frequency and that a flared profile is necessary to provide the correct rate of area reduction with rising frequency. By the choice of suitable profiles the radiated power response may be made to rise or remain level or to fall. The high frequency limit of a loudspeaker is reached when the radiating area has been reduced to a point where its effective mass becomes equal to that of the voice coil. The last-mentioned provides a non-reducing factor in the total moving mass and above this frequency the efficiency falls. It may be mentioned at this stage that the further loss of efficiency at high frequencies is incurred by voice coil inductance, but from what has been said it will be seen that this can be compensated by means of the cone design. In practice, however, the more we make use of the facility of increasing efficiency as frequency rises the more restricted will be the ultimate high frequency limit. The overall high frequency efficiency over the frequency range above the "knee" is largely a function of the material from which the cone is made.

Apart from the considerations of the response curve a high overall high frequency efficiency is extremely desirable, inasmuch as it permits the use of damping techniques to avoid transient ringing. Any form of damping reduces overall efficiency and the greater the intrinsic efficiency of the cone the more freely can we apply damping media to improve the transient performance.

Generally speaking the higher the velocity of sound within the material

the greater will be the efficiency and therefore the more extended may be the high frequency response. Further, high sound velocities are usually associated with materials having a high strength/weight ratio. This is also the property necessary to eliminate the distortion associated with flared cones. As we have previously said, the strength/weight ratio of paper is not particularly high and, in addition, paper is a relatively inexact and unstable material in mechanical terms. The reasons why the single-cone approach has not received greater attention are now becoming apparent.

We now see that we are faced with the problem of determining the cone material, shape and dimensions with very little mathematical assistance, yet in order to secure a smooth extended high frequency response devoid of colouration it is imperative to be able to determine these factors very accurately and further to retain this accuracy throughout manufacture. The approach has therefore to be entirely experimental. The tooling necessary to produce cones of almost any form is very complex, and such experimental work demands that cone tools be made and discarded until the correct parameters are obtained. Naturally one cannot afford to be haphazard in this approach, and each cone form tested must result from a logical assessment of the performance of the previous one. Nevertheless this work is very time-consuming and very expensive and it is easy to understand why this problem has not been previously tackled with any degree of thoroughness, especially when one considers that all there is to show at the end is a single-cone loudspeaker with little or no "gimmick value."

Some 12 years after developing the hyperbolic paper cone 8 in loudspeaker, the author experimented with small aluminium cones, which led to the development of the Jordan-Watts module. This cone had a hyperbolic flare which closely approached a pure radius. The frequency response of this unit is shown in Fig. 7. It will be noted that the axial frequency response is fairly smooth and level but the off-axis response is falling towards the high end. This indicates that the mean hemispherical power response (m.h.p.r.) is falling. The shape of the mean hemispherical power response is of far greater importance than that of the axial pressure response.

It was not until three years later that the author had the opportunity to experiment with a variety of alternative flares, and he discovered that



Fig. 6. Indicating how the effective cone radius (r) may decrease with rising frequency.


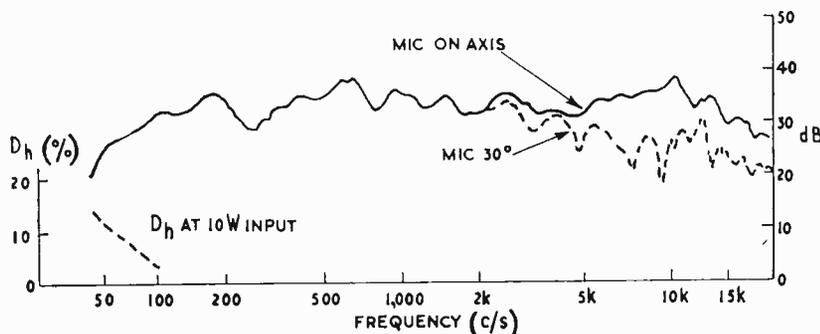


Fig. 7. Performance curves of 4 in. dia. aluminium cone having a hyperbolic profile approaching a radius.


although he could raise the m.h.p.r. it was at the expense of the high frequency limit. An acceptable compromise is shown in Fig. 8, which is the response of a unit similar to the previous one but employing an aluminium cone with a flare given by the law $y=0.75/x$. Although this curve does not appear to be as good as the previous one there was, on listening tests, considerably less colouration, and the improved transient performance gave the impression of a more extended top response. This range of experiments virtually exhausted the possibilities of aluminium as a cone material which, although it gave results considerably superior to those of paper cones, still left something to be desired, and again the search was on for a new material.

The clue was given in an advertisement by Imperial Metal Industries Ltd. describing titanium as having "a greater strength weight ratio than any other structural metal." Samples were immediately ordered and duly received. As a starting point one of the sample pieces was placed in the tool used for the previous aluminium cone and when pressure was applied the material immediately shattered; and the author's company was then faced with the agonizing prospect of having to find out how to tool for titanium before knowing if the metal was going to be satisfactory in any case. This was done, however, and the advantages of titanium became immediately apparent, and experiments were once again undertaken to determine the correct cone law. Shortly after this another breakthrough was made whereby it became immediately possible to obtain the correct flare in any material without any further tests.

This came as the realization that a stretched membrane displaced at its centre would follow a hyperbolic curve (Fig. 9). If the displacing force is oscillating the lines of stress and strain will lie along the natural hyperbolic curve and there will be no tendency whatever for the material to be displaced from this curve at any point. This is exactly the situation required in a loudspeaker cone to avoid unwanted "break-up," and not only shows the advantage of the hyperbolic law in principle but also tells us exactly how to achieve it in practice—i.e. a sheet of the proposed material, in this case titanium, is subjected to considerable tension, placed in an annular clamp and the centre displaced by a cylindrical tool. This is the technique now used in the manufacture of titanium cone loud-

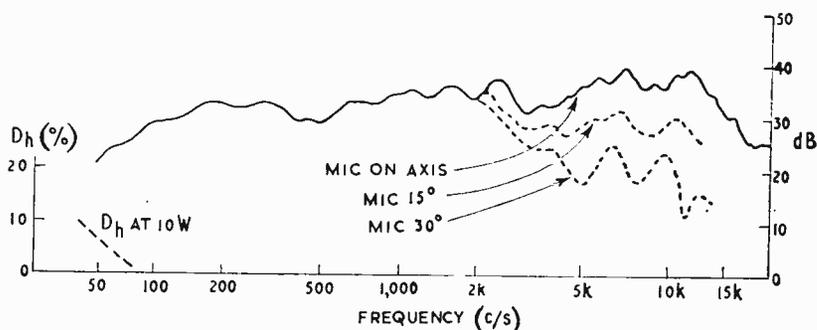

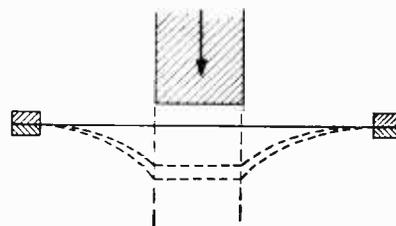Above: Fig. 8. Performance curves of 4in dia. aluminium cone having a hyperbolic profile given by $y = 0.75/x$.



Right: Fig. 9. Showing the formation of a hyperbolic form by displacement at the centre of a stretched membrane.

speaker modules and systems marketed by Audio & Design Ltd.

The metal titanium.—Out of interest readers may like to know that titanium is the fourth most abundant metal found in the Earth's surface. It is an element and the material used in loudspeaker cones is 99.9% pure. In addition to its exceptionally high strength/weight ratio it does not corrode and will withstand extremely high temperatures. It is produced in this country by Imperial Metal Industries (Kynock) Ltd., Birmingham, a subsidiary of I.C.I. It has become commercially available only during the past 10 years and, because of its properties, its principal applications are in the aerospace industry. In spite of the abundance of the crude ore the metal is expensive, owing to the very elaborate refining and milling processes required. The material is extremely difficult to work with and the rate of tool wear is high. In our application the grain size is of very great importance.

The coil.—The voice coil of the loudspeaker has to be as light as possible consistent with reasonable efficiency. Considerations of high frequency performance have led us to an actual cone (piston) diameter of about 4in. From this we have calculated (see Appendix 1) a peak displacement of $\pm \frac{1}{8}$ inch in order to provide the required low frequency radiated power level, assuming reflex loading. Thus, in order to provide a constant driving force either the coil must be $\frac{1}{2}$ in longer than the depth of the magnetic

gap or vice versa. In the interests of lightness the short-coil, deep-gap approach is used, and this incidentally also provides a higher magnetic efficiency.

Considerations of total magnetic flux and flux density led to the adoption of a magnetic gap diameter, and therefore coil diameter, of approximately 1½in. The coil itself comprises a $\frac{1}{2}$ in aluminium winding on an aluminium former of thickness 0.0015in. The winding is immersed into the centre of a $\frac{1}{2}$ in deep magnetic gap.

The mechanical attachment between the top of the coil former and the cone neck is of paramount importance and must be effected by means of a very thin layer of hard-setting adhesive. Any flexibility at this join will lead to three severe defects: (a) premature mechanical failure (the forces developed across the glue line are very considerable); (b) attenuation of the high frequency response and colouration due to the resonance resulting from the mass of the cone and the compliance of the adhesive; and (c) harmonic and intermodulation distortion at high frequencies due to the inevitable non-linearity of the compliance.

The flexible surround.—Since the cone is moving and the supporting framework is not, the cone must be supported at its edge by means of a flexible coupling which has to perform the following quite separate functions:

1. To permit complete freedom of the cone to move axially and to

restrict any sideways movement.

2. To provide an airtight seal between the edge of the cone and the enclosure. Further in this respect it must appear acoustically opaque to back-pressures emanating within the enclosure.

3. To provide a satisfactory termination to the cone at high frequencies in order to effect as much as possible the complete absorption of the incident flexure waves arriving at the cone edge. Failure to do this will result in reflected waves, leading to interference effects and colouration.

4. The rim must be intrinsically non-resonant.

5. The rim must be made of a material that does not age and is mechanically stable under all conditions of climate.

One technique employed by the author was to use a composite plastics rim, attached to which was an annular metal spring. This spring had two natural positions, a normal and an inverted cone frustum, i.e., it

would always attempt to spring either up or down away from the flat position. When attached to the plastic rim, it was held against its will in the flat position, and by carefully balancing the force of the spring against the rim stiffness a cone surround was obtained that offered almost zero stiffness to axial movement and complied perfectly with the first two of the above requirements. However, extreme difficulty was experienced in meeting requirement 4.

The problems were finally overcome by the use of an impregnated polyether foam. The method of impregnation, which is novel, is such as to produce the effect of a "tapered" transmission line between the edge of the cone and the chassis.

Restoring force.—In the interests of mechanical stability it is essential that the cone assembly be provided with a restoring force to ensure that the coil always moves relative to a fixed mean position in the centre of

the magnetic field. It is important for this restoring force *not* to be applied at the cone edge since this would incur cone flexing at low frequencies. The ideal position for the restoring force is at the rear of the cone where it acts also as a means of centring to maintain the coil in its correct axial position within the magnetic gap. If the axis of the cone is arranged in the horizontal position the location of the suspension system should be such as to support the cone and coil system at its centre of gravity (acknowledgement to Percy Wilson).


As a result of the restoring force the complete system will exhibit a resonance below which the condition of mass control will be no longer operative. The resonant frequency must therefore be near the lower limit of the required frequency range.

One very important requirement for the suspension system is that it must be completely linear over the full range of cone displacement. Failure to be so results in the very high harmonic distortion apparent in the extreme bass response of many loudspeakers. The suspension system itself must be mechanically stable, and this requirement led to the use of three tangentially disposed beryllium copper cantilevers (two of which are used to carry the voice coil current). The cantilevers are attached at their inner ends to a rigid insulating annulus surrounding the coil and attached to the coil via a "lossy" compliant medium the purpose of which is to ensure that the mass of the suspension system is decoupled from the coil at high frequencies.


Chassis.—In the loudspeaker described the entire moving assembly is built up on a removable top plate which in turn is screwed to four supporting members attached to the magnet system. The entire assembly is suspended in a vented housing via an insulating medium to avoid transmission of energy to the housing and mechanical resonances. The detachable moving assembly is readily replaced in the event of misuse or damage, as shown in the photograph. The entire assembly is produced under laboratory conditions in a state of clinical cleanliness.

Enclosure.—The titanium cone loudspeaker module was designed for reflex loading which, if correctly designed provides an extended low frequency performance having a very low distortion level within an enclosure of acceptable domestic dimensions.

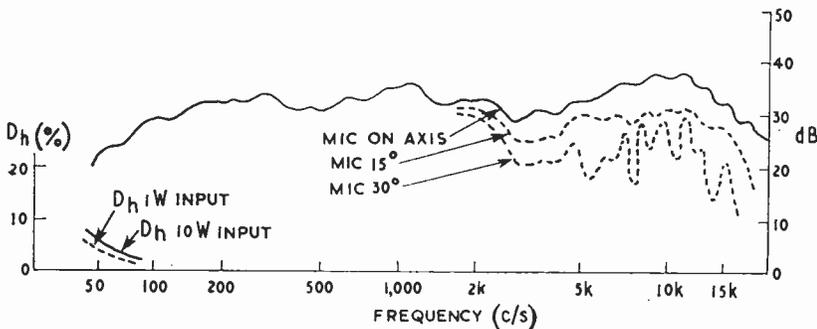It can be shown that for optimum performance the Q of the funda-



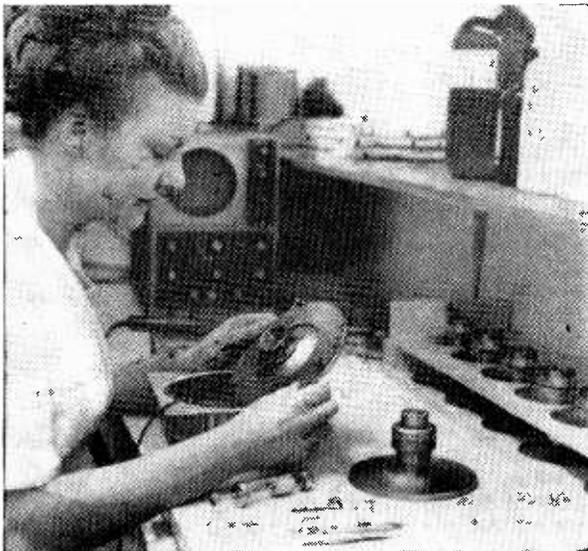Above: Fig. 10. Performance curves of 4in diameter titanium cone loudspeaker.



Left: Assembling a titanium-cone loudspeaker. The entire moving assembly is mounted on a detachable ring. The outer housing is vented.

mental cone resonance in free air should be 0.62^2 . If the internal volume of the enclosure is then such that the enclosed air stiffness is 1.62 of the suspension stiffness and the reflex vent is arranged to tune the enclosure to the free air resonance of the loudspeaker, the overall frequency response will be perfectly level down to that frequency. By an appropriate increase in enclosure size and retuning, the response can be extended to as much as an octave below this frequency with a response variation of not more than ± 3 dB.

A source of difficulty sometimes encountered with reflex loading is that at very low frequencies, i.e. below 20 c/s, the acoustic load applied to the cone falls very considerably and factors such as motor rumble can cause very considerable cone displacement. A solution to this problem has been found in the provision of a semi-flexible plastics diaphragm spanning the inside of the enclosure between the loudspeaker and vent. This has virtually no effect upon frequency down to the enclosure resonance, but below this it provides a progressively increasing stiffness controlled load.

Performance data.—The power response, axial pressure response, polar response and distortion are shown in the composite curve in Fig. 10. Unfortunately the author had insufficient time to secure facilities for transient testing but the performance in this respect can be demonstrated by white noise tests.

The question of Doppler distortion is often raised in reference to small full-range loudspeakers. There has recently been some dispute about the significance of this type of distortion, but accepting for the moment that its significance is proved, it is normally applied to small loudspeakers on the assumption that very large cone displacements are necessary to produce adequate radiated power at low frequencies. In our case this is not so since, owing to the efficiency of the type of reflex loading employed, the cone displacement of the loudspeaker described is no more than that encountered in the cone of a conventional 12in loudspeaker.

Final thoughts.—The most significant subjective advantages gained by the use of titanium as a cone material have been in the high frequency and transient responses. The author feels that at the moment there is no entirely adequate explanation for these subjective advantages in terms of the performance parameters normally discussed but that further light may be thrown upon the matter by an

examination of the property of mechanical hysteresis within the cone. It is reasonably obvious that titanium will have a lower hysteresis loss when subjected to alternating flexure than any other diaphragm material hitherto used, and in the not too distant future it is hoped to make a complete examination of the relationship between mechanical hysteresis and subjective and objective transient performance.

My thanks are due to Imperial Metal Industries Ltd. for their very considerable help and advice on tooling and their extensive tests to determine the optimum material characteristics for our purpose; to John Martin of Martin Watch Laboratories, Bracknell, for his development of the cone tooling described; and to my assistant Margaret Collett for her work on the experimental and production prototypes.

REFERENCES

1. "Loudspeakers" by E. J. Jordan, Page 49. Focal Press, London (1963).
2. As above, p. 154, eqns. 10.19 to 10.23.

APPENDIX I

Acoustic power P_r required to reproduce a full orchestra in a medium room (2,000 cu. ft.) at serious listening level (say 80dB) is 0.002 watts. Assume an l.f. limit of 40 c/s.

$P_r = v^2 R_{M,A} \cdot 10^{-7}$ acoustic watts
where v = r.m.s. velocity of cone
 $\therefore 0.002 = v^2 \cdot 2.18 \times 10^{-6} \times r^4 \times 40^2 \times 10^{-7}$

$$v^2 r^4 = \frac{0.002 \times 10^{-7}}{2.18 \times 10^{-6} \times 40^2}$$

$$\therefore v r^2 = 2.4 \times 10^3$$

From considerations of h.f. response discussed in text, r was found to be 6 cm.

$$\therefore v = \frac{2.4 \times 10^3}{36} \approx 67 \text{ cm/sec}$$

$$\therefore v_{peak} = 1.11 \times 67 = 74.5 \text{ cm/sec}$$

From which the peak-to-peak displacement at 40 c/s

$$\frac{74.5}{2 \times 40} = 0.94 \text{ cm} = 0.366 \text{ inch.}$$

(Symbols defined in footnote on p. 555).

APPENDIX 2

Approximate expressions for radiation resistance ($R_{M,A}$) above and below the curve "knee" are:

When $kr \ll 2$
 $R_{M,A} \approx 2.18 \times 10^{-4} f^2 r^4$ mech. ohms.

When $kr \gg 2$
 $R_{M,A} \approx 2.16 \times 10^5 r^2$ mech. ohms.
(Symbols defined in footnote on p. 555).

APPENDIX 3

Assume condition of mass control:—

$$P_r \propto \frac{F^2}{\omega^2 L_M^2} \cdot R_{M,A}$$

where L_M = cone mass.
When $kr \gg 2$, $R_{M,A} \propto r^2 \propto A$
For a given cone thickness:—

$$L_M \propto r^2$$

$$\therefore P_r \propto \frac{1}{f^2 r^4} \cdot r^2$$

If the effective cone radius were to remain independent of frequency, P_r would fall at 6 dB/octave. Including losses due to the voice coil inductance, this becomes 12 dB/octave. To compensate the above expression must vary as f^4 .

$$\therefore \frac{1}{f^2 r^4} \cdot r^2 \propto f^4$$

$$\therefore \frac{1}{r^2} \propto f^6$$

$$\text{or } \frac{1}{r} \propto f^3$$

but r is a function of $\left(\frac{c_c}{f}\right)$

where c_c is the velocity of flexural wave motion in the cone.

Then $\frac{c_c}{f}$ must vary as $\frac{1}{f^3}$

$$\text{or } c_c \propto \frac{1}{f^2}$$

In a straight-sided cone, $c_c \propto 1/f$ approx. Thus the above indicates the need of a flared cone.

Consider now the frequency at which the reduction of radius should start. This is given by

$$f = \frac{c_c}{l_c}$$

where l_c is length of cone side.
The frequency corresponding to $kr = 2$ is

$$f = \frac{c}{\pi r}$$

where c is the velocity of sound in air. These two frequencies should be coincidental

$$\therefore \frac{c_c}{l_c} = \frac{c}{\pi r}$$

$$\therefore \frac{c_c \cdot r}{l_c} = \frac{c}{\pi}$$

$$\therefore c_c \sin \theta = \frac{c}{\pi} = \text{const.}$$

where θ is the angle between the cone side and the axis.

While we are unable to calculate absolute values from the expressions, they do give a very good guide in experimental determination.

(Symbols defined in footnote on p. 555).

Thin Films in Electronics

SOME NOTES ON THE I.E.R.E.-I.E.E. CONFERENCE HELD EARLIER THIS YEAR

THE conference on thin film applications was organized because it was felt there was a need for us to take stock of the place of thin films in electronic engineering, the subject having generally taken a back seat compared to solid circuits.

One point that emerged from the conference was that the delegates were by no means all devotees of the thin film approach. Indeed, a speaker questioned the future of thin films since diffused integrated circuits were usable up to 300 Mc/s and above—apart from the obvious use of thin films as stable R s and C s in hybrid circuits. Perhaps this is the limited extent to which thin film circuits will be used, but much depends on the development of a usable and reliable thin film transistor. Another summed up the position by maintaining that thin film circuitry was not, as is often thought, competitive to diffused integrated circuits, but that the techniques were complementary.

COMPONENTS

Resistors.—A paper by Naylor and Fairbank (Ferranti) described results obtained from tantalum resistors and capacitors made by sputtering. It was stated that the use of the sputtering technique (in which tantalum atoms are “knocked” from a source to a substrate by bombardment with ions of an inert gas), rather than by thermal exaporation by heating or electron beams, resulted in better uniformity of film thickness.

Capacitors.—The two main advantages of thin film capacitors is that capacitance can be up to 1 pF for 0.001 in² with a high breakdown voltage and can remain voltage-independent. Tantalum pentoxide is attractive since for one thing its dielectric constant is 21 compared to 2-4 for the more usual silicon oxides. Capacitors with good h.f. performance can be made with tantalum pentoxide (Naylor & Fairbank) by making electrode resistivity low (rather than dielectric losses).

Inductors.—Little, relatively, was said on the subject of inductors, presumably because these are more difficult to adapt to thin film circuits than R s or C s. (For one thing, a conducting substrate near to the coil reduces inductance and increases losses.) But within limits inductors with values around 1 μ H are quite feasible, and a paper by Manfield and Windle (R.R.E.) indicated that inductances can be made up to 12 μ H with a tolerance spread of 0.05% and high Q values. (Desired Q values can be achieved by adjustment of the plating thickness.)

Active devices.—Much work in the field of thin film transistors using evaporated layers of CdS or CdSe (field effect types) has been done by P. K. Weimer, who is well known for his work. Unfortunately, erratic variations in device characteristics have held back progress. Tickle, Swystun and Treleaven (Saskatchewan University) showed that device characteristics were strongly dependent on film thickness. Batch fabrication was thus used to reduce effects of random variations in deposition.

D. J. Page (Westinghouse, U.S.A.) described a heterojunction transistor (or dielectric transistor) which was produced by preparing a dielectric diode on a silicon p-n

junction. Most of such CdS-Si devices showed an exponential emitter characteristics. It was felt that if base recombination could be reduced then useful devices may be evolved.

APPLICATIONS

Many examples of the use of thin film techniques were given, including magnetic film memories, cryoelectric or superconducting memories, galvanometric devices, ultrasonic transducers, strain gauges and microelectric circuits. A number of complete equipments have been produced besides many circuit building blocks which use hybrid microelectronic techniques. Holland and Chapman reported on the thin film modules used in Marconi television equipment (see p.58 February issue) and W. S. Whitlock (A.S.W.E.) discussed their use in radar receivers, using thin film inductors and capacitors in resonant circuits. According to the author, the thin film capacitor is something of an obstacle for narrow band receivers. The main difficulty appears to be the realization of high- Q LC circuits (>100) at frequencies around 30 Mc/s. Series resistance of leads and electrodes was felt to be a contributory factor to low Q , and to minimize this, changes in geometry and material were suggested.

Active filters.—Avoidance of large-value inductors for l.f. work is given by the use of active filters (see p. 129 March issue). Adjustment of component values was necessary, as tolerances were too wide—scribing resistors with diamond gave adjustment to $\pm 0.1\%$. Capacitor adjustment was provided by cutting the leads to small capacitors giving adjustment to about ± 2 pF. The authors concluded that hybrid microelectronics could be used for active filters in many applications.

Ultrasonic transducers.—A technique which has become well known in the last two or three years is that of vacuum deposition of CdS films for use as piezoelectric ultrasonic transducers and is due to the work of N. F. Foster (Bell Telephone). In the past, quartz has been used as the principal transducer material, but for frequencies above 100 Mc/s, the material thinness required is not practical for bonding.

To overcome this and other problems the evaporated layer or thin film transducer was developed. In essence, an electrode is evaporated onto the propagation medium, covered with evaporated CdS and finally a further electrode is deposited. With this method losses can be as low as 4 dB at 200 Mc/s and 12.5 dB at 1.5 Gc/s. Usually CdS is the material used for such transducers, but others have been tried, such as ZnS, CdSe and ZnO. Zinc oxide is the most attractive due to its greater electromechanical coupling coefficients and higher sound velocity. This last factor would mean that films would be thicker than those of CdS for the same λ . CdS films have been deposited by sputtering and efficiencies are similar to evaporated types, but the orientation is such that only longitudinal propagation is possible. Sputtered ZnO films have shown high efficiencies but the full potential has not been realized yet, partly due to lack of control of film orientation.

WORLD OF WIRELESS

Colour TV Service and Servicing

TO keep television dealers and their servicing staffs abreast of the latest developments associated with the proposed start of a colour television service next year Mullard arranged a discussion meeting at the end of September for a small cross-section of the trade. They were addressed by F. C. McLean, B.B.C. director of engineering; David Attenborough, head of BBC-2; A. J. Kenward, secretary of S.E.R.T. and R.T.E.B.; and S. E. Allchurch, director of B.R.E.M.A.

Mr. McLean, dealing with the technical aspects of the colour TV service, stressed that the public is likely to be more critical of quality in colour than in monochrome. He cited experience in the U.S.A. and gave it as his opinion that the slow start of colour there was not only that receivers were expensive but that the colour picture seen on an average receiver was so very variable.

Of the programme side Mr. Attenborough made the point that as 99% of viewers will be receiving the colour programmes on monochrome receivers for some time to come it is essential that the addition of colour should be "an enrichment of a good monochrome picture."

For the benefit of service technicians desirous of taking a course in colour TV servicing the Radio Trades Examination Board has prepared a list of nearly 60 colleges which are offering part-time courses. In answer to a questioner Mr. Kenward stated that the minimum equipment required for servicing colour receivers (additional to that on a well-equipped monochrome bench) is a pattern generator. Useful additions would be a sweep generator, PAL signal generator, degaussing equipment and c.h.t. measuring equipment.

There was the inevitable question regarding the introduction of colour on 405 lines in the v.h.f. band, but both Mr. McLean and Mr. Allchurch stressed that it would be a retrograde step, delay the start of a colour service and complicate receivers.

R.A.F. Engineer Branch

WITH the object of bringing before educationists the need of the Royal Air Force for young men of high calibre who are qualified in the applied sciences—particularly electrical, electronic and mechanical engineers—and the opportunities afforded in the Service, a two-day symposium was recently held at the R.A.F. College, Cranwell. Some 120 guests from the academic world attended.

During the symposium it was announced by the Minister of Defence for the R.A.F. (Lord Shackleton) that the Technical Branch will in future be known as the Engineer Branch. Within the Branch there will be a division between mechanical engineering and electrical engineering duties. The latter will cover communications, ground and airborne electrical and electronic equipment, instruments and surface-launched missiles.

The papers presented at the symposium and the tour of the college stressed the standard of technical training provided for cadets and specially for young post-graduates who enter the Service. The courses at the College vary from the 4½-year engineer cadet course to the engineer officer (graduate) course of eight months and the age of entries varies from 17½ to 45 years.

Correspondence Courses

FOR several months the Cleaver-Hume Group of Correspondence Colleges has been operating from its new headquarters at Aldermaston Court, Berks, but it was not officially opened until September 23rd when the ceremony was performed by Sir Arnold Lindley, chairman of the Government's Engineering Training Board.

The new centre, from which are regularly distributed the "lessons" for some 600 different subjects to over 100,000 students in the U.K., is also to be used at week-ends for seminars for selected students. Professor H. F. Trewman, for many years principal of the E.M.I. College of Electronics, is advisory principal at Aldermaston.

Among the members of the Cleaver-Hume Group is the British Institute of Engineering Technology which was founded in 1927. The B.I.E.T. brochure on the electronic engineering correspondence courses gives brief details of a radio and electronics construction course (the £20 fee covers the cost of a Radionic constructional kit and multimeter), several electronic engineering courses and a course on transistor circuitry.

H.R.H. The Duke of Edinburgh will officially open the Radio Communications Exhibition at Seymour Hall, London, W.1, at 12 noon on October 26th. The four-day exhibition, sponsored by the Radio Society of Great Britain, will be open daily from 1000-2100. Admission costs 3s. There will be some 30 exhibitors and there will be displays and demonstrations by Royal Signals, Royal Navy and the Post Office.

Experimental colour television transmissions using the PAL system are radiated daily from Monday to Friday at set times during the normal BBC-2 trade tests from Crystal Palace (channel 33), and the relay stations at Hertford and Tunbridge Wells (channels 64 and 44). The daily schedule is:—1400-1415 test card in black & white, 1415-1425 colour bars, 1425-1500 colour slides; this sequence is repeated from 1500-1700. On Wednesdays, Thursdays and Fridays there is a further series of tests from 1810-1900. Users of 625-line u.h.f. monochrome receivers may find it interesting to see these transmissions to assess the compatibility.



150 ft radio telescope of the National Research Council of Canada at Algonquin Radio Observatory, Lake Traverse, Ontario. The electronics system for controlling the steerable paraboloid was supplied by A.E.I. Electronics. The company's film "The Radio Sky", telling the story of radio astronomy, can be borrowed from A.E.I., 35 Grosvenor Place, London, S.W.1.

B.B.C. Research Scholarships.—The Engineering Division of the B.B.C. maintains six research scholars at United Kingdom Universities and is awarding one scholarship this year. The scholarships are intended to provide the opportunity to work for a higher degree, the subject chosen for post-graduate study being within those fields of physics or engineering which have an application to sound and television broadcasting. This year's scholar is G. C. Goddard, who graduated with an upper second class honours degree in electronic and electrical engineering from Birmingham University this year. He has been awarded a three-year scholarship to undertake research on "A method of increasing the data-handling capacity of underwater telemetry links" at Birmingham University, Department of Electronic and Electrical Engineering.



Philips' 75th anniversary is commemorated in the postmark on the first issue of a new Dutch airmail stamp.

BBC-2 in the North East:—The BBC-2 service from Pontop Pike will start on November 5th, on Channel 64 (sound 821.25 Mc/s, vision 815.25 Mc/s) with horizontal polarization. Test transmissions will begin on October 22nd and will normally consist of test card from 0900 to 1200 and 1400 to 1915 every day except Sunday. Some 1,700,000 people in the north-east of England will be in the service area of the u.h.f. transmissions.

Some radio altimeters which operate in the 420-460 Mc/s band have been causing serious interference to observations made at the Mullard Radio Astronomy Observatory at Cambridge. The interference is caused by the local oscillator in the altimeter receiver (which operates in the radio astronomy band 406-410 Mc/s) when the aircraft concerned is flying within radio line of sight of the Observatory. In a Board of Trade notice pilots of aircraft registered outside the United Kingdom carrying specified types of radio altimeter are requested not to operate them when flying within U.K. airspace.

The experiment kit for the 30-week series of television lectures "First steps in physics" is being produced by the Communications Division of S.G. Brown Ltd. The course, which is nationally networked by I.T.A., is produced by ABC Television in collaboration with the National Extension College, Cambridge. The series, which started on September 25th and is presented by Professor James Ring, of Hull University, is intended to prepare viewers, with little prior knowledge of the subject, for the G.C.E. "O" Level examination next June.

E.I.B.A.—Many companies and associations in the radio and electronics industry are listed among the donors in the annual report of the Electrical Industries Benevolent Association which assists "any deserving or necessitous person," excluding manual workers, who are or have been in any branch of the electrical industry. Among the associations listed are R.T.R.A., Radio Industries Club, R.E.C.M.F., VASCA, and B.V.A. During 1965 the Association's income went up by nearly £18,000 to over £123,000.

C.N.A.A. Degree Courses.—The Council for National Academic Awards, confers degrees "comparable in standard with those granted by universities" on students completing approved courses in education establishments which have not the power to award their own degrees. The council has recently issued a list of courses which lead to the award of its B.A. or B.Sc. degrees and the colleges providing them. It is obtainable from the C.N.A.A., 24 Park Crescent, London, W.1. The colleges providing electronics courses, as opposed to electrical courses with an electronic bias, are Staffordshire College of Technology, Northern Polytechnic (London) and Rutherford College of Technology (Newcastle-upon-Tyne).

The African Broadcasting Conference, which was convened by the International Telecommunication Union in Geneva in October 1964 but adjourned after a few days, resumed its work on September 19th, again in Geneva. The purpose of the Conference, attended by some 180 delegates from more than 60 countries was to draw up a medium-wave broadcasting plan for Africa and also examine the position as regards long-wave broadcasting on the African continent.

An information sheet, number 4002(4), detailing the 625-line vision signal waveform, has been issued by the Engineering Information Dept. of the B.B.C., Broadcasting House, London, W.1. It includes all the characteristics with waveforms showing the line and field synchronizing signals and an r.f. response curve for an ideal receiver.

Stereo Test Transmissions.—In addition to the increased frequency of stereo broadcasts announced a few months ago, the B.B.C. transmits test signals to facilitate channel identification and adjustment of cross-talk. A 250 c/s tone is transmitted in the left-hand channel only from about four minutes after the end of the Third Programme until 2355 every night.

A one-day course on counter design with silicon integrated circuits is being held at John Dalton College of Technology, Chester St., Manchester, on October 31st (Fee £3 15s including lunch). The lecturer is K. J. Dean of Letchworth College of Technology.

Because of increased attendance at meetings of the Surrey Radio Contact Club they are in future being held at the "Blue Anchor," South End, Croydon. Meetings will now be held on the third Tuesday of each month at 2000. At the meeting on November 15th an illustrated taped lecture on the American station W1BB will be given.

NOVEMBER CONFERENCES AND EXHIBITIONS

LONDON

- Nov. 9-11 Savoy Pl., W.C.2
Automatic Operation and Control of Broadcasting Equipment
 (I.E.E., Savoy Pl., W.C.2)
- Nov. 17-18 Savoy Pl., W.C.2
Small-angle Scattering of Electrons and X-rays
 (Inst. Phys. & Phys. Soc., 47 Belgrave Sq., S.W.1)

OVERSEAS

- Nov. 14-16 San Francisco
Engineering in Medicine & Biology
 (Dr. D. H. Lecroisset, Jet Propulsion Lab., Pasadena, Calif.)
- Nov. 15-18 Washington
Magnetism and Magnetic Materials
 (I.E.E.E., 345 E. 47th St., New York 10017)
- Nov. 19-25 Milan
Automation and Instrumentation Conference & Show
 (Federazione delle Assoc. Scientifiche e Tecniche, via Ripamonti 115, Milan 15/6)

PERSONALITIES

S. S. Carlisle, M.Sc., F.Inst.P., M.I.E.E., director of the British Scientific Instrument Research Association, is the 1966/67 chairman of the Control and Automation Division of the I.E.E. He graduated with first-class honours in electrical engineering at Queen's University, Belfast, in 1940. After post-graduate study he was awarded an M.Sc. From 1942 to 1946 he served with the Admiralty in the experimental department of H.M.S. *Excellent*, Portsmouth, where he was engaged on gunnery, radar and fire control development. Mr.



S. S. Carlisle

Carlisle joined the British Iron and Steel Research Association in London in 1946 as the head of the instrument section of the Physics Department. From 1953 to 1958 he was head of the South Wales laboratories of B.I.S.R.A., and was head of the Physics Department of B.I.S.R.A. in London from 1958 until 1963 when he was appointed director of the British Scientific Instrument Research Association. Mr. Carlisle is past-president of the Society of Instrument Technology; vice-chairman of the United Kingdom Automation Council, and U.K. delegate on the International Federation of Automatic Control Components Committee.

Professor A. L. Cullen, O.B.E., Ph.D., D.Sc.(Eng.), who has occupied the chair of electrical engineering at Sheffield University since it was created in 1955, has been appointed to the Pender Chair of Electrical Engineering at University College, London, where for nine years prior to his Sheffield appointment he was successively lecturer and reader in electrical engineering. Prof. Cullen, who was the 1965/66 chairman of the Electronics Division of the I.E.E., graduated at Imperial College, London, in 1940 and was for six years at the R.A.E., Farnborough. The last incumbent of the Pender Chair was **Dr. H. E. M. Barlow**, who is now on the board of directors of Marconi Instruments and **W. H. Sanders** (Electronics).

Air Marshall Sir Walter Pretty, K.B.E., C.B., Deputy Chief of the Defence Staff (Personnel and Logistics), Ministry of Defence from 1964 until his recent retirement from the R.A.F., has been appointed to the board of directors of Redifon Ltd. Trained at the R.A.F. College, Cranwell, Sir Walter, who was knighted in 1962, became deputy director of radar in the Air Ministry in 1944. The following year he was appointed chief signals officer, Fighter Command, R.A.F., and in 1948 became Director-General of Navigational Services at the Ministry of Civil Aviation. In 1953 he was appointed Director of Electronics Research and Development (Air) in the Ministry of Supply. In 1958 he was appointed Director-General of Organization at the Air Ministry and from 1961-64 held the appointment of Air Officer Commanding-in-Chief, Signals Command.

G. H. Metson, M.C., D.Sc., Ph.D., M.I.E.E., director of research at the Post Office for the past two years, has retired on health grounds and is succeeded by **W. J. Bray, M.Sc.(Eng.), A.C.G.I., D.I.C., M.I.E.E.** Dr. Metson, who is being retained as a consultant, joined the Post Office as a youth-in-training in the physics laboratory in 1925. Later he transferred to Northern Ireland, where he carried out research on magnetron oscillations and received his M.Sc. and Ph.D. at Queen's University, Belfast. During the war he served with the Royal Corps of Signals. In 1946 he was back at Dollis Hill in charge of the thermionics group set up to study the causes of valve failure. Dr. Metson became deputy director of research in 1962. His successor, Mr. Bray, who entered the Post Office Engineering Department in 1934 as an assistant engineer in the Radio Experimental Laboratories at Dollis Hill, was chosen in 1961 to lead the newly formed Post Office Space Communication Systems Branch. Since 1963 he has led a team



W. J. Bray

at Dollis Hill working on research connected with communication satellites and lasers. Prior to his concentration on satellite communications Mr. Bray was concerned primarily with ionospheric- and tropospheric-scatter.

Commander Hugh St. A. Malleson has been appointed a director of SGS-Fairchild Ltd. During 16 years naval service he qualified in signals and was experimental officer, H.M. Signal School, Admiralty; and Commander on



Cdr. H. St. A. Malleson

the staff of the Director of Radio Equipment, Admiralty. From 1950 to 1964 Commander Malleson was head of the Government and Industrial Valve Division at Mullard Ltd.

R. H. Davies, C.B.E., B.Sc., M.I.E.E., deputy general sales manager, of Ferranti Ltd. for the past nine months has succeeded **O. M. Robson, M.A., M.I.E.E.**, as general sales manager. Mr. Robson is retaining his seat on the board as sales director. Mr. Davies joined Ferranti Ltd. in 1946 after spending the later war years with the British Air Commission in Washington, D.C., on joint British/U.S. radar development. In 1947 he returned to the U.S.A. to become vice-president and general manager of Ferranti Electric Inc. (New York), a wholly owned subsidiary of Ferranti Ltd. He rejoined the parent company in 1963 but still remains a director of Ferranti-Packard Electric Ltd. in Toronto and Ferranti Electric Inc. in New York.

J. M. Brunskill was recently appointed plant manager of the Mullard Research Laboratories, Redhill, Surrey, which he joined as administrative assistant in 1952. He previously served for 13 years in the Royal Corps of Signals, reaching the rank of Major.

Maurice Esterson, B.Sc.(Eng.), A.M.I.E.E., is appointed deputy manager of the Microwave Tube Division of English Electric Valve Company. He joined E.E.V. in 1941 as a development engineer in the magnetron section and in 1960 became manager in charge of



M. Esterson

high-power klystrons. When E.E.V. bought their plant at Lincoln, Mr. Esterson was appointed the managing director's special representative for integrating the Lincoln organization with that at Chelmsford.

E.A.G. Davis, D.S.O., who joined the Marconi Marine Company in 1959 as marine superintendent in which capacity he acted as the company's adviser on navigational problems as related to electronic aids, has been appointed assistant general manager. In October 1962, he was appointed management executive and in 1964 became assistant to the general manager. During the war he served in the Royal Naval Reserve and was promoted to the rank of Commander. On leaving the service in 1946 Mr. Davis took up a Government appointment.

D. L. Phillips, M.M., B.Sc., A.M.I.E.R.E., has resigned from the managing directorship of Mills & Rockleys (Electronics) Ltd., printed circuit manufacturers of Skelmersdale, Lancs. Mr. Phillips was works manager of Technograph Electronic Products Ltd.



D. L. Phillips

before joining the Mills & Rockleys group in 1958 as a consultant to set up an electronics subsidiary. During the war he served in the R.A.F. as a technical signals officer and immediately prior to joining Technograph was with Plessey at their components division at Swindon. He is setting up a consulting service on printed circuits.

L. C. Jesty, who two years ago went to the U.S.A. to join the Westinghouse Corporation, has had the degree of D.Sc. conferred on him by the London University for his work in the field of "The science of visual communication and display." Dr. Jesty was educated at University College, Southampton, and joined the G.E.C. Research Laboratories, Wembley, in 1927, where he spent 18 years. He then went to Cintel as head of the advanced development department. In 1949 he joined Marconi's as chief of the television research group. Seven years later he joined the Sylvania-Thorn colour television laboratories at Enfield, Middx., where until 1962 he was in charge of colour television research.

Roy R. Roper, has joined Racal Instruments Ltd. as sales director. For the past year he has been a director of Weir Electronics and Weir Industrial Controls. For two years prior to that



R. R. Roper

he was general sales manager of Cossor Communications Company, having previously spent seven years with Solartron and five years as a development engineer on submarine communication systems with Standard Telephones & Cables. Mr. Roper, who is 36, started his career as a technician in the Post Office Engineering Department.

P. E. Leventhall, B.Sc.(Hons.), M.I.E.R.E., has joined Hudson Electronics Ltd. and International Marine Radio Company Ltd. (both S.T.C. subsidiaries) as technical manager and will be responsible for all development projects. He graduated in physics at Leeds University and has been chief engineer of Cossor Communications Ltd. for the last three years having previously been chief engineer of Murphy's radio-telephone division.

G. S. C. Lucas, O.B.E., F.C.G.I., M.I.E.E., has retired from A.E.I. Electronics of which he was director and group general manager. He started his career with the British Thomson-Houston Company (now part of A.E.I.) in 1915 and after serving his apprenticeship studied at the City & Guilds (Engineering) College. In 1925 he went into the B.T.H. research laboratory and in 1932, as head of the electrical development section, became responsible for electrical measurements and developments in the audio engineering field. Mr. Lucas was appointed an O.B.E. for his contribution to the development of centrimetric fire-control radar during the war. When the B.T.H. Electronics Engineering Dept. was set up in 1945 he was appointed manager. He became chief engineer in 1953, and has been director and general manager of A.E.I. Electronics, Leicester, since 1963.

OBITUARY

Sierd Sint Eriks, K.B.E., managing director of the Mullard Company and chairman of Philips Electronic and Associated Industries until his retirement for health reasons in 1964, died on September 27th, aged 66. Educated at Rotterdam University he came to England in 1929 as general manager of the Mullard Company before becoming responsible for all N.V. Philip's interests in the United Kingdom. He became chairman of Philips Electronic and Associated Industries in 1955 and was personally responsible for starting the Mullard Research Laboratories near Redhill shortly after the war. Mr. Eriks, who in 1961 was appointed an honorary K.B.E. "in recognition of his valuable services to British official interests," felt that the company should play its part in the education of future scientists and technicians and instigated a number of endowments, including the Mullard Radio Astronomy Observatory at Cambridge University, the Mullard Cryomagnetic Laboratory at Oxford University and various readerships in science at a number of other universities.

A. W. Martin, M.B.E., Assoc.I.E.E., technical director of E. K. Cole Ltd., died on September 23rd aged 59. He joined the company in 1926 becoming chief engineer in 1943 and technical director in 1952. During the war he was in charge of the company's radar development unit at Malmesbury, for which he was appointed an M.B.E. With the acquisition of E. K. Cole Ltd. by the Pye group Mr. Martin was appointed to the Pye board and assumed overall responsibility for the domestic sound radio and television engineering activities of the group. He was also chairman of Ekco Electronics Ltd.

Power Sources Symposium

SOME DEVELOPMENTS IN VARIOUS POWER CELLS, BOTH OLD AND NEW

A MEETING held at the same time as the Liberal Party Conference in Brighton, though not so much in the public eye, was the Fifth International Power Sources Symposium. This biennial symposium is organized by the Joint Services Electrical Power Sources Committee and has been previously known as the Battery Symposium. The change of title led one to believe that more prominence would be given to sources of power other than electrochemical batteries, but the number of papers dealing with "unconventional" or non-electrochemical sources was in fact less than in 1964.

The symposium was attended by about 400 delegates from about 20 countries and during the three days 40 papers were read.

As on previous occasions many papers were intended for electro or physical chemists. For example, several of these dealt with the structure and properties of lead compounds present in the positive paste of lead-acid cells, in particular the two modifications of lead dioxide (α and β). These have not yet been fully explored and much work continues using various techniques of analysis. In these notes, however, only those papers which are felt to be of more practical and direct interest to readers are dealt with.

Secondary cells

Lead-acid types.—In both lead-acid and silver-zinc battery systems the plates are usually made by pasting an oxide on to a supporting grid and then, in the case of negative plates, reducing it to a metal. This is obviously a wasteful process as the raw material is metallic lead which is converted to oxide powder and then reduced back to metallic lead at a later stage. This, together with the fact that it is difficult to control the porosity (high porosity is one requirement for high plate efficiency) in a plate made by pasting and reduction (and also the porous material often has a low mechanical strength), has prompted investigation of other methods of manufacture. Work on the use of metal powders was reported by Morrell and Smith (Lucas) who considered for various reasons that the most satisfactory method was that of mixing the powder with a soluble removable filler which does not prevent cold welding (e.g. sodium chloride crystals or sodium nitrate). It was concluded that satisfactory zinc plates can be made from strength and electrochemical aspects. Preliminary results on lead plates are also promising. However, much more work on the subject is needed since little is known about factors which control plate capacity and the processes taking place during plate discharge. The effect of filler size has yet to be investigated.

Sealed Ni-Cd types.—For many years interest and activity in the field of high performance power sources has been growing due, in part, to the advent of the transistor and also to the space effort. At the same time, though, the more well-known electrochemical

storage batteries are steadily being improved. Turner, Howden, Ovinaka and McHenry (Bell Telephone) described developments leading to an improved battery design, and new techniques in electrode and separator fabrication. A new separator material developed consists of Teflon and zirconium oxide particles. High porosity (60-80%) is obtainable—necessary for sufficient passage of oxygen from the positive to the negative plate. Dr. Turner considered that the inherent capability of Ni-Cd cells outmatched that of all other sealed rechargeable cells in terms of overall performance and cycle life (which can be >10 years). One paper, by Azulay and Kirkman (Alkaline Batteries Ltd.), contained many useful notes for the user, mainly on charging conditions and an interesting point was made concerning constant potential charging. Here, in a sealed cell, overcharge energy is dissipated as heat (as opposed to gas in an open cell). A rise in the battery temperature, consequently lowering the back e.m.f., would result in a higher end current for a fixed applied potential. This effect could result in a progressively rising overcharge

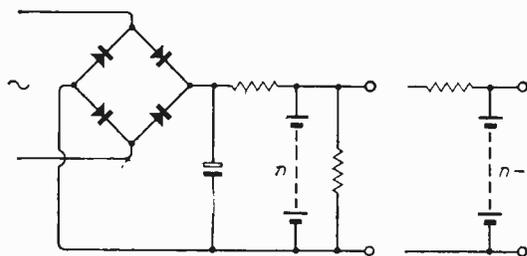


Fig. 1. Use of Ni-Cd cells as stabilizers.

current—or thermal runaway. Thus if the charging period is likely to be prolonged indefinitely the constant potential method should be avoided.

Another piece of advice was that storage of sealed cells should be done in the fully discharged state since, under certain circumstances, gassing could occur when subsequently placed on charge.

If the electrode pair in Ni-Cd cells is replaced by a pair containing the same active material in both electrodes [e.g. $\text{Cd}(\text{OH})_2$] or if the positive electrode is replaced by an electrode free from active material, a type of cell is obtained in which an equilibrium is reached between oxygen evolution and reduction, and only little energy can be stored in such cells. These can be used as stabilizer cells since the cell voltage changes by only a small amount within a certain range of current. These cells are, incidentally, reversible—i.e. current can flow in either direction. An example of their use was given by F. Peters (Varta, Germany)—see Fig. 1. Apart from stabilizing the output voltage against mains variations the cells also act as a capacitor (10,000-20,000 μF) giving a low a.c. resistance practically independent of frequency. Further stabilization can be obtained by adding $n-1$ cells

giving virtual independence of mains variations. Temperature coefficient of voltage is about 1 mV deg C⁻¹.

Primary cells

Leclanché type.—In almost all chemical and electrochemical reactions the reaction rate decreases with temperature. The Leclanché cell is no exception to this, the resistance and viscosity of the electrolyte becoming so high that cells are unfit for use at -23° C. Erämetsä and Karsila (Finland) reported on investigations of electrolytes which will operate down to -42° C (at this temperature output is down to 15% of that at +25° C). It was shown that cells using electrolytes based on lanthium chloride (with MgCl₂, NH₄Cl and H₂O) gave a slightly greater capacity than standard commercial cells and a considerably better capacity than cells based on lithium chloride and bromide. At -42° C the cell capacity compared with a lithium chloride cell.

Air Cells.—These are primary cells in which the oxygen of air is the active material (serving as the cathode depolarizer) consumed by the positive electrode of the cell. These have been known for a long time, a typical cell having zinc anodes, a KOH electrolyte and a porous carbon cathode depolarized by oxygen diffusing through it to the electrode surface. Interest in these is due to the high energy density and the relative low cost. They are, however, only suitable for low discharge rates (e.g., C/700).*

A new magnesium-air cell was described by Carson and Kent of the G.E. Company (U.S.A.), and is known as the Magair cell. It is capable of a much higher power operation than present air cells. The electrolyte used is common salt. The air cathodes in these cells are derived from those used in fuel cells and a catalyst (platinum black) is used. It is interesting to note that in the absence of oxygen the cell still produces power because the air electrode can still operate as a cathode, hydrogen now being evolved from the water in the electrolyte. In this condition a cell voltage of 0.3 to 0.6 V is obtained. Normally though, open circuit voltage is 1.6 V, dropping to 1 V at 60 mA cm⁻². At "moderate" production rates, the cost of such cells is expected to fall to about £3 per watt, which for a service life of 1,000 hours would provide electricity at a cost of nearly 1d per watt-hour—much cheaper than dry cells. Costs would be reduced further by using air electrodes without a platinum catalyst.

Solar cells

Further details of the UK3 satellite power system were presented in a paper by F. C. Tremble (R.A.E.). This satellite is the first to be built in the U.K. (by B.A.C.). The "solar" cells (made by Ferranti) are connected in two arrays, one supplying the load directly and the other charging the battery (Ni-Cd) for operation in dark periods. Battery charge is at constant current and then at constant voltage and at 40° C the charge is reduced to prevent overheating. Should battery voltage fall below 14 V it is disconnected from the load and put on trickle charge; should the voltage fall below 9 V, the battery is then assumed to be beyond revival and permanently disconnected. The load requirement is 5 W mean with a maximum of 15 W and this is supplied *via* ±6 and ±12 V rails regulated to 1%.

Each of the load panels comprises six sets of 40 cells

in series and each of the 14 battery panels consists of six sets of 48 cells in series. These panels are connected in parallel *via* protective silicon diodes. In all there are about 7,400 cells. (Originally, it was thought that due to the Starfish high-altitude nuclear bomb the flux, integrated over one year, would be equivalent to 10¹¹ electron cm⁻² at 4 MeV. But, the trapped radiation has decayed more rapidly than expected and is now thought that it will not exceed 10¹³ electron cm⁻². This would result in a cell current of 60 mA at 400 mV rather than nearer 52 mA.) Efficiency of the arrays, measured at 100 mW cm⁻² with a tungsten lamp, is about 8.9%.

Thermoelectric sources

A material becoming more popular for thermoelectric use is a Si-Ge alloy, and the design of sources using such was discussed by W. Thorpe (Ferranti). (Si-Ge has the advantage, among others, of high relative efficiency at high temperatures.) Methods of preparation were described and a typical output was 0.2 V at 11 A for a sample 0.44 cm² cross-sectional area and a temperature difference of 850 deg C. For higher current the area is increased and for higher voltages, units are placed in series. The number of alloyed connections can affect reliability and it was pointed out that by using an alloy with a higher Seebeck voltage—achieved by decreasing the impurity (phosphorous *n* type and boron for *p* type)—the number can be reduced, but a reduced efficiency must be accepted.

Fuel cells

A low temperature hydrogen-oxygen fuel battery was described by Gillibrand and Gray (Electric Power Storage Ltd.). The 30-cell battery provided an output of 1 kW at room temperature and was on load for 2,000 hours. Before such a battery would be commercially acceptable, however, the reliability of the cells and auxiliary equipment (electrolyte pump, cooling fan, valves and so on) would have to be improved. Faults in the experiment were found to be mainly due to mechanical failures—seals and joints usually.

Low temperature cells usually use hydrogen as fuel but often this can be undesirable. An alternative is to use a methanol-water mixture, and at 200° C with a catalyst this produces hydrogen and carbon dioxide. A battery using such methanol-air cells was reported on by Clow, Bannochie and Pettinger (Energy Conversion Ltd.). The cell design provided an output of 55 W at 0.675 V. A battery of cells was proposed to give an output of 6 kW.

Economics.—Fuel cell costs were compared with costs of other power sources in a paper by Harrison & Lomax (Electric Power Storage), although it was difficult to estimate future production costs. It is interesting to note that for a hydrogen fuel cell, as with a motor-generator, little cost reduction is obtained for efficiencies greater than 40%.

It was stated that for electric cars, although fuel cells could provide attractive power densities, it was unlikely that they ever will be economically suitable, unless for instance, the price of hydrazine could be reduced drastically. Capital costs of £100 per kW would increase the cost of the power source in the A.E.I. Mini-car to £1,000. For other applications, such as remote radio repeaters, fuel cells can be attractive, where convenience is of prime importance. A typical example of the high price paid for convenience is the dry battery as used in torches, where costs are given as about £9 per kWh!

*C/700 signifies a rate that will discharge the cell in 700 hours.

WHY THEY ARE NEEDED AND
HOW THEY WORK

HYBRID COMPUTERS

analogue + digital

2.—HARDWARE OF PARALLEL HYBRID MACHINES

By P. W. J. VAN EETVELT,* Dip.Tech.(Eng), Grad.I.E.E.

IN the previous article, by C. D. Dwyer, reference was made to the limitations of pure analogue computation systems and to the historical development of, and need for, hybrid techniques. It will thus be appreciated that the concepts of hybrid computation have been evolved over the past decade to a state where the commercial production of general-purpose hybrid computing systems is now technologically feasible. In the light of the applications experience gained on early systems it was realized that full emphasis must be placed on the needs of the computer user in the design of these general-purpose hybrid systems.

The object of the present article is to introduce what is known as parallel hybrid hardware. A parallel hybrid computer may be defined in its broadest sense as an equipment in which a pure analogue computer is linked via suitable interface equipment to pure digital logic elements that operate in parallel (see Fig. 1). In a subsequent article illustration will be provided by short descriptions of two commercial hybrid computation systems, and the use of such systems will be shown by their application to two specific problems.

In order to appreciate the capabilities of a parallel hybrid computer it is necessary to understand the operation and field of application of the elements from which it is constructed. These elements may be divided into four distinct groups as follows:—

1. Pure analogue elements.
2. Analogue elements incorporating digital control.
3. Analogue elements providing digital outputs.
4. Pure digital elements.

Let us now consider these groups of elements in more detail.

PURE ANALOGUE ELEMENTS

Present-day electronic analogue computers simulate systems by representing system variables in terms of voltages. In order to solve the equations describing the system, it is necessary to implement basic mathematical relationships between these voltages or machine variables. The basic mathematical operations which can be carried out on a pure analogue computer are as follows:

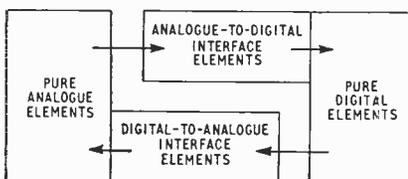


Fig. 1. Block schematic of a parallel hybrid computing system.

Analogue Element	Symbol	Function
Multiturn high resolution potentiometer	$x \rightarrow \lambda \rightarrow y = \lambda x$	Multiplication by a constant less than unity
Inverter	$x \rightarrow \rightarrow y = -x$	Inversion of input sign
Summing amplifier	$y = -(x_1 + x_2 + 10x_3 + 10x_4)$	Summation of several inputs
Relay mode controlled summing integrator	$y = -\frac{1}{T} \int_0^t (x_1 + \dots + 10x_4) dt$	Integration of the summation of several inputs
Bipolar quarter square multiplier	$x \rightarrow \rightarrow y \rightarrow \rightarrow z = xy$	Multiplication, division, etc., of inputs
Diode function generator	$x \rightarrow \rightarrow y = f(x)$	Generation of arbitrary functions
Relay comparator	$x \rightarrow \rightarrow y \rightarrow \rightarrow$	Comparison of two inputs to energize relay contacts

Fig. 2. Table of analogue computing elements.

multiplication by a constant; inversion; summation, i.e. generalized addition and subtraction; integration*; multiplication, division, etc.; nonlinear function generation; and variable comparison.

All these operations may be implemented in terms of machine variables by passive elements in association with operational amplifiers. In fact, electronic analogue computers are built around a complement of d.c. operational amplifiers.

*Electronic Associates Ltd.
†Differentiation can be implemented directly but is purposely avoided since the signal-to-noise ratio in the circuits can be unacceptable.

I will assume that readers are familiar with pure analogue computing equipment, but for reference purposes a table of analogue elements, symbols and their functional operation is given in Fig. 2. Logic graphical symbols used will correspond to those recommended by B.S. 530:1948, Supplement No. 5, as exemplified by previous articles on logic in *Wireless World*.

Referring to the bipolar quarter-square multiplier in Fig. 2, other types of multipliers do exist and have been used successfully in the field of analogue computers. The most notable is the servo multiplier, which has the advantage of enabling several inputs to be multiplied by a common single input. However, the servo multiplier is restricted by nature for low frequency applications, and is not usually found on hybrid computers, where the object is to solve problems at high speed.

The Fig. 2 table does not, of course, exhaust pure analogue elements nor indeed analogue techniques. It does, however, illustrate the basic capabilities of an analogue computer.

Modern general purpose analogue computers are built as an integrated unit comprising modular units mounted in a single, purpose-built console. These modular units are mounted directly behind the "patch bay" to avoid trunking, thus minimizing cross-talk, etc. The inputs and outputs to the modular units occupy a frontal position, allowing the use of patch panels. The patch panel usually occupies a central position on the computer console, and conveniently placed either side and below this are the computer mode control and readout facilities.

Mode control.—The modes of operation necessary on either analogue or hybrid computation systems are given in the table below.

Mode	State of Computer	Function
Pot-set	Computer reference voltage off	Setting of potentiometers representing input data
Initial-condition	Computer reference voltage on	Setting of integrator initial conditions etc.
Hold	All machine variables held at previously achieved value	Inputs to integrators isolated
Operate	Computing	Solution of problems
Static test	Special reference available at patch panel	Checking out of computer set up
Rate test	Fixed voltage applied to all integrator inputs	Checking out of integrator time constants
Slave	Mode control slaved by external console	Slaving of several computers

In past analogue computer systems all mode control was achieved by the use of relays. This, however, produces problems in high speed computation, since relays are subject to three limitations which become increasingly important at high speeds of operation:

1. Relays are electromechanical devices and the in-

herent electrical inductance and mechanical inertia produce time delays and limit speed of operation.

2. When several relay contacts throw in parallel the degree of simultaneity of contact is limited, and this causes "initialization" problems that increase with the size of computer installation.

3. Relay contact bounce introduces errors into a simulation which become increasingly important at high speeds of operation.

Thus a limitation is imposed on the speed of operation of relay mode controlled computation equipment, which limits the use of high speed subroutines, high speed iteration and other such techniques being used in current simulation problems.

All modern general purpose hybrid computing equipment utilizes the solid-state switch wherever possible to eliminate the above-mentioned limitations imposed by relays. The solid-state switch is not yet fully developed to the state where it completely replaces the relay, but it is sufficiently developed to enable it to perform important tasks in the field of hybrid computation.

Solid state switching implies the use of digital control which will now be described in the following section.

ANALOGUE ELEMENTS INCORPORATING DIGITAL CONTROL

The digital-analogue switch.—One of the requirements of hybrid computation is the necessity for high speed switching with switching times of the order of 1 μ sec or less. Since the fastest switching time which can be realized with electromechanical devices is several milliseconds, it is clear that electronic switching is essential. The d/a (digital-analogue) solid-state switch is a diode bridge assisted by bottoming transistors. The switching action is controlled by a binary logic signal such that a "1" causes conduction and "0" the non-conducting state. The d/a switch is connected directly to the summing junction of an operational amplifier at virtual earth. When the switch is non-conducting its input is switched to earth; thus the input impedance is independent of its state. When used to switch analogue input signals the switch is padded with a resistance which swamps that of the diode bridge itself. Thus transient variations of input impedance during switching are eliminated and also the summing accuracy is made compatible with the resistors commonly used as inputs.

The symbol adopted for the d/a switch does not indicate whether it is a straightforward solid-state switch


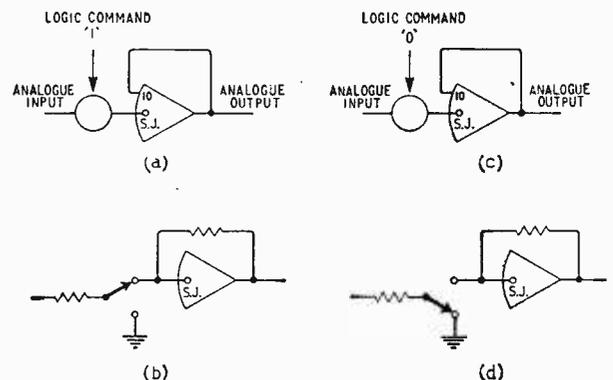


Fig. 3. Digital-analogue switch: (a) conducting state with (b) equivalent circuit; (c) non-conducting state with (d) equivalent circuit.

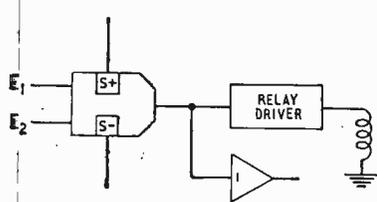

Left:— Fig. 4. Digital-analogue relay, driven by electronic comparator.

or whether it is padded as mentioned; this ambiguity is however clearly resolved, since when used as a computational element the d/a switch is always of the latter type and is best illustrated in association with an operational amplifier as shown in Fig. 3, which also illustrates the equivalent circuits for the conducting and non-conducting states.

The digital-analogue relay.—Where low-speed switching can be implemented the reed relay can be used to advantage, e.g. initialization subroutines. Modern hybrid computation systems make provision for this facility in the form of a d/a relay. This is a reed relay driven by a relay driver stage, the input of the relay driver stage being controlled by a logic command. This logic command may be derived from a logic comparator to be described later. Thus analogue signals may be compared and a decision based on this comparison made via the relay contacts. This is shown symbolically in Fig. 4.

Digital-analogue relay driven by comparator.—In Fig. 4, when $E_1 + E_2 \geq 0$, contact is made from the arm via the “+1” contact and when $E_1 + E_2 < 0$ via the “0” contact. This convention is consistent with the logic output of the comparator. The d/a relay is used where switching times of the order of 1 msec are sufficient.

Electronic mode controlled integrator.—The relay mode controlled integrator commonly used in analogue computation systems is totally unsuited to the needs of hybrid computation. The electronic mode controlled integrator was developed when the concept of high speed subroutines was utilized to solve complex problems in an efficient manner.

The operation of this type of integrator can be seen from Fig. 5. When the voltage at B is low, i.e. logic state “0,” the outputs of the two “AND” gates which it feeds, P and Q, are both logic “0.” Thus the base of the operational amplifier is isolated from the initial condition network and summing junction network, since their associated gates (solid-state switches) are non-conducting. The output of the d.c. operational amplifier thus remains at the value it achieved before B became low. Therefore when B is low the integrator assumes the “hold” mode. When B is high, i.e. logic “1,” the mode is determined by the logic input A. When this is high the initial condition gate is conducting and the “operate” gate non-conducting. A first order lag circuit is formed. The output of the amplifier thus achieves the initial condition value applied at the initial condition input as the limit or asymptote of an exponential rise. The time-constant CR is made as small as possible by making R small while not causing excessive base current to flow. Therefore when A and B are high the integrator assumes the initial condition mode. When A is made low and B remains high the initial condition gate ceases to conduct and simultaneously the operate gate conducts; thus an

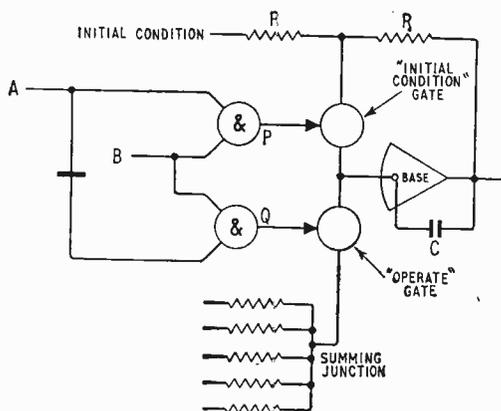


Fig. 5. Simplified schematic of electronic mode controlled integrator.

integrator is formed and the output of the amplifier is dependent on the time integral of the inputs. Therefore with A low and B high the integrator assumes the “operate” mode. A summary of these statements and the programming symbol are given in Fig. 6.

Track/store unit.—The implementation of high speed subroutines in hybrid computation systems leads to a requirement for storage of analogue sample values. This was originally achieved by utilizing an integrator and restricting it to the initial condition and “hold” modes. Thus in the initial condition mode the input signal is tracked and in the “hold” mode the finally achieved output is stored or held. The two main disadvantages of this method are that the inherent time-constant of the initial-condition network limits the rate at which an analogue signal may be tracked. This may be improved upon by using smaller capacitor values in association with the integrator. However, this leads to a second disadvantage in the “hold” mode since the drift rate of the integrator output is enhanced by the smaller capacitor value used. These disadvantages have now been overcome in an extremely efficient manner in the track/store unit.

The method of operation can be seen from Fig 7. When the voltage at A becomes high the solid-state switch S_n conducts and an inverter is formed. Since the logic signals A and P are both low the two CR networks C_1, r_1 , and C_2, r_2 are both earthed and thus are charged by the amplifier output. When A becomes low the switch S_n ceases to conduct and the monostable element output M becomes “1” for a predetermined duration (τ msec). Switch S_1 conducts simultaneously and thus the output is stored by C_1 . When the monostable returns to logic “0” after τ msec state P becomes high and thus the output is stored by both C_1 and C_2 . Resistances r_1 and r_2 are small values purely

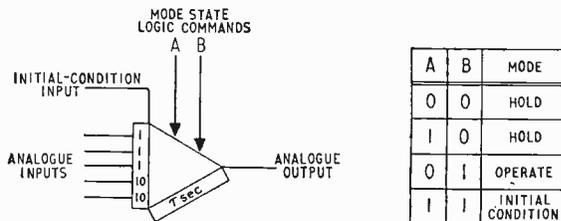


Fig. 6. Programming symbol and mode state table for electronic mode controlled integrator.

to limit the charging current derived from the amplifier output. C_1 is very much smaller than C_2 , so that C_1 assumes the output value at a rate very much faster than C_2 . The monostable is used to allow the charge on C_2 to reach the output value on C_1 before closing the switch S_2 in the store mode. The objective of the circuit may be clarified as follows. In the track mode the amplifier circuit tracks the input virtually instantaneously. In the store mode a CR circuit with a low time-constant, which has been able to achieve the final output, is used initially to store the amplifier output. After a predetermined time has elapsed say $\tau = 10 C_1 r_1$, the voltage on C_1 will have reached 99.99% of this value and thus may be used to store the finally achieved output value. Since C_2 is very much larger than C_1 , the drift rate in the store mode is rendered almost negligible. Typical figures which refer to a system to be described later are a 300 nsec track time-constant and a $100 \mu V$ per second drift rate in the store mode.

The programming symbol for a track store unit is shown in Fig. 8.

ANALOGUE ELEMENTS PROVIDING DIGITAL OUTPUTS

These elements are extremely important since they provide lines of analogue feedback which may be used to

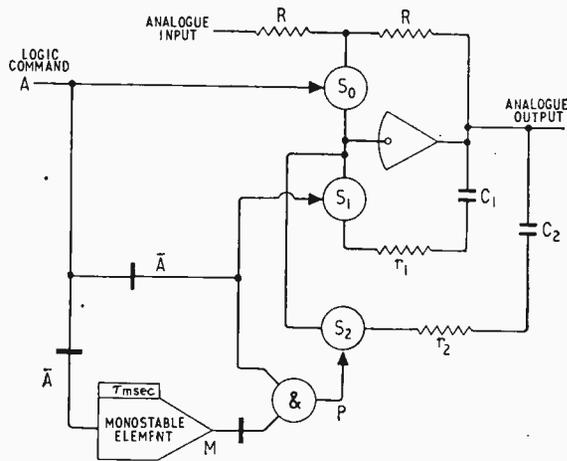


Fig. 7. Simplified schematic of track/store unit.



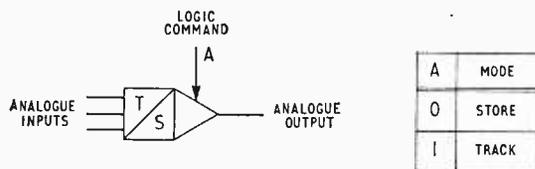


Fig. 8. Programming symbol for track/store unit.

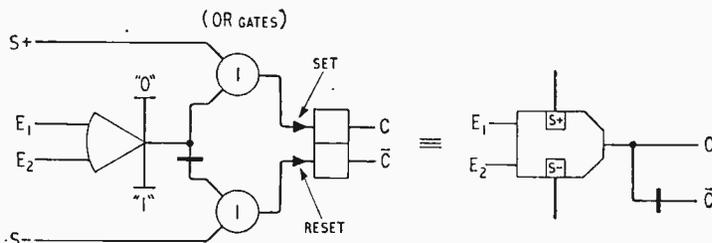

Left:- Fig. 9. High-speed electronic comparator.

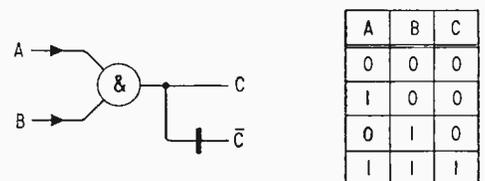Below:- Fig. 10. Two-input AND gate and truth table.



effect control decisions of the digital field of operations. Since the digital logic signals are in fact voltage levels, the simplest possible element in this group is the voltage limited trunk in which an analogue voltage is either hard- or soft-limited to produce the voltage levels required for the digital system. This is usually lower than used in analogue systems. Here, for example, if the digital logic signals are such that logic "0" = 0V and logic "1" = +5V we may arrange that an analogue signal which is negative produces a logic "0" and one which is positive produces a logic "1" via a voltage limited trunk. This element is only used when a crude form of comparator is needed and on most modern hybrid computation systems the electronic comparator has further useful features such as logic controlled latch facilities. Basically the electronic comparator is an operational amplifier in the high gain mode whose output is voltage limited to provide a logic signal of the right amplitude. The logical complement of this is derived using a single transistor inverter stage. These outputs are arranged to drive an asynchronous bistable multivibrator commonly referred to as a flip-flop, the output of which is the logical output. The drive circuit is arranged with OR-gate logic so that it is possible to override the analogue inputs to the comparator using logic inputs. The logic output may therefore be overridden or latched. Logic comparators are also produced so that the logic output may be used to drive a double-pole double-throw reed relay externally.

Logic comparators, as in Fig. 9, produce logic "0" when the sum of the inputs is negative and logic "1" when the sum of the inputs is positive. The analogue inputs may be overridden by the application of a logic "1" to logic inputs labelled S+ and S-. The output C can be made independent of the analogue inputs and can be forced to logic "1" or "0" by the application to logic "1" to S+ or S- respectively. The full programmer's symbol is shown in Fig. 9.

The table below represents the state of the logic output C with respect to the sum of analogue inputs and S+ and S-.

$E_1 + E_2$	$S+ \equiv '0'$	$S+ \equiv '1'$	$S- \equiv '0'$	$S- \equiv '1'$
≥ 0	1	1	1	0
< 0	0	1	0	0

The S+ and S- should not be made high simultaneously otherwise the output C is not clearly defined.

Finally, it is worthwhile mentioning the analogue-to-digital (a/d) converter. A/D converter equipment may be used to convert analogue signals to either parallel or serial digital signals. They are only usually incorporated in fully integrated hybrid systems when the

complexity of the problems justifies their economic inclusion.

PURE DIGITAL ELEMENTS

Before discussing the hardware involved in this section, it is important to appreciate the advantages of synchronous digital elements over asynchronous ones. Early attempts at the development of hybrid computation systems brought out the main deficiencies of individual computing elements.

One of the major problems experienced was due to the use of asynchronous digital elements which had three main deficiencies:—

1. Since asynchronous elements cannot be sequentially controlled by manual step pulses, rigorous check-out procedures were made difficult if not impossible.

2. Inherent noise caused digital element outputs to change state randomly, introducing non-predictable errors into the final solutions.

3. Lack of sequential control causes the outputs of digital elements to become misaligned or out of phase with respect to each other, and can result in asynchronism with the main simulation.

4. A time-event or timing diagram could not be drawn up to establish correct operating sequence.

These problems may be eliminated by the use of parallel digital elements which are controlled in time sequence by synchronizing pulses. This type of digital element is referred to as synchronous logic. The synchronizing pulses are derived from a master clock, which generates a high frequency periodic pulse train. The higher the frequency, in fact, the more closely synchronous operation approaches that of asynchronous elements. The bandwidth of the individual elements dictates the maximum clock frequency permissible and in modern hybrid systems this is of the order of 1-10 Mc/s.

All present day hybrid computation systems incorporate synchronous digital elements, eliminating the problems posed by asynchronous equipment.

Let us now look at the digital elements used in parallel hybrid computation systems.

The AND gate.—This is the simplest element to be considered and its symbol and associated truth table are shown in Fig. 10.

As a basic element the AND gate may be used to build up OR, NOR and NAND gates, parallel half-adders, full-adders, etc., provided its complementary output is made available.* Thus general purpose AND gates are always provided with their complementary output as shown by the programming symbol in Fig. 10.

The AND gate does not require synchronization, its output being almost simultaneously determined by its inputs.

The flip-flop is the other basic element required in parallel hybrid computation systems. It is, in fact, a bistable multivibrator.

General-purpose flip-flops are provided with a logic output and its complement. The output is controlled by three inputs, these being "set," "reset" and "enable." With the "enable" input high, i.e., logic "1," raising the "set" line high causes the output to go high on the next clock pulse, whereas raising the

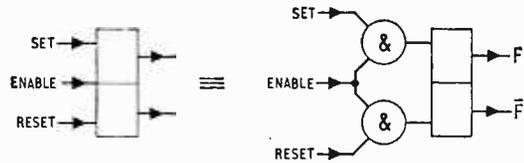


Fig. 11. Flip-flop with set/reset control. ($F=1$ when $set=1$; $F=0$ when $reset=1$. F does not change state if set and $reset=0$.)

"reset" line high causes the output to go low on the next clock pulse. If the "enable" line is low, the "set" and "reset" inputs are rendered inoperative.

All other pure digital elements are built up from these two basic elements. The units commonly incorporated in modern hybrid computation systems are as follows:—

General purpose shift-register.—A general purpose shift-register comprises a number of flip-flops arranged so that the set line of each flip-flop is connected to the output of the preceding stage. If a bit is loaded into one flip-flop stage, then enabling the shift-register and raising the shift line high causes the bit to be propagated from one flip-flop to the next at clock rate. The flip-flops may, however, be used separately or may be loaded in parallel when set connected as a shift register.


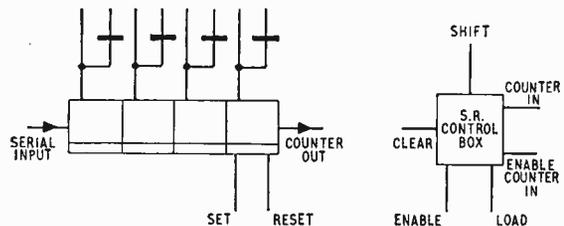


Fig. 12. General-purpose shift register with control box, usable as four independent flip-flops, 4-bit shift register or binary up-counter.


Monostable multivibrator with variable "period."—This unit functions as follows. When the input A is raised high the output becomes high simultaneously and remains high for a preset period capable of adjustment from 1 μ sec up to 100 sec with thumbwheel switches and vernier adjustment.

Fig. 13. Monostable multivibrator set up to give an "on" time of 50ms for a short input pulse at A.

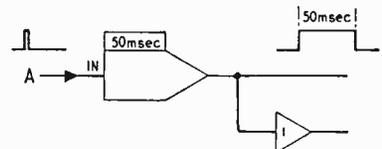

Logic level differentiators.—These may be of two types, i.e., leading-edge differentiators or trailing-edge differentiators. The output of these elements produces a momentary blip, one clock pulse wide when the input

Fig. 14. Differentiator, producing a blip as a result of a level change at point A.

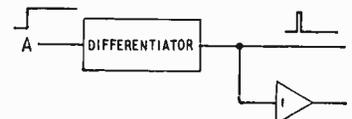

goes from low to high or high to low depending on which type it is. In practice differentiators are of the leading-edge type. When fed with a complementary output they function as trailing-edge differentiators.

*See, for example, "Logic Without Tears," by H. R. Henly, *Wireless World*, January 1965, pp. 44-49, and "Economic Logic," by the same author, October 1965, pp. 518-523.

“Microwaves à la Mode”

CAMBRIDGE CONFERENCE HIGHLIGHTS SOLID-STATE MICROWAVE OSCILLATORS AND AMPLIFIERS

DISCOVERER of the Gunn effect J. B. Gunn provided the keynote of the Sixth International Conference on Microwave and Optical Generation and Amplification, held in Cambridge in September, by the title of his paper “Microwaves à la Mode.” Although this paper was in fact a “guided tour” of oscillation mechanisms in bulk gallium arsenide (including, incidentally, an excellent cine film showing travelling electric-field domains), the title could well have stood for the whole field of solid-state microwave amplifying and oscillating devices, in which there has been such rapid development recently. At the last MOGA conference, in Paris in 1964, the subject was not included, but at the Cambridge conference about 25% of the papers were devoted to semiconductor devices. The remaining papers were divided between vacuum tubes such as klystrons, magnetrons and travelling-wave tubes and quantum devices such as masers and lasers.

Besides Gunn-effect (travelling-domain) devices, which have already been discussed in *Wireless World*¹, there are gallium arsenide (GaAs) devices in which travelling domains do not appear but transit-time and negative resistance effects are significant; junction devices such as avalanche, tunnel and varactor diodes; devices producing oscillation and amplification by means of magnetoresistive elements made of indium antimonide; and “acoustic” amplifiers based on a t.w.t. type of interaction between microwave mechanical waves and current carriers in piezo-electric materials such as cadmium sulphide². All these were represented at the conference.

Variety of oscillation modes

There seems to be some confusion about the use of the term “Gunn effect” in describing one group of devices. It is certainly confined to bulk-material, usually GaAs, (as distinct from junction) devices, but whether the term should be restricted to the exact phenomenon originally observed by Gunn, in which the applied potential was pulsed, or whether it may be extended to other oscillation modes in bulk materials subsequently discovered by other workers is very much an open question. Mr. Gunn himself, although giving an admirable lecture, only added to the confusion in the minds of the uninitiated by identifying seven different modes of operation in which travelling electric-field domains occur (quite apart from three non-domain modes!). These seven modes were divided into two classes: (a) modes in which the frequency was determined by the transit time of the drifting electrons and therefore by the length of the GaAs bar; and (b) modes in which an associated resonant circuit determined the frequency because the r.f. voltage in this circuit was large enough to control the nucleation, extinction or propagation of the travelling domains.

In this last-mentioned “resonant” class of modes came one of the highest power Gunn-effect microwave oscillators to be reported so far. This was an oscillator giving, in pulsed operation, 220 watts peak power at 1.1Gc/s, and was mentioned by Dr. D. G. Dow (Varian Associates;

U.S.A.) in a paper describing a whole range of experimental pulsed GaAs oscillators. Other high peak powers obtained were 64 watts at 2.2Gc/s and 1.5 watts at 7.65 Gc/s—the peak power in watts, P , being given approximately by the law $P=200/f^2$, where f is the frequency in Gc/s. The outputs measured were all at frequencies lower than the natural (transit-time) frequency of the GaAs bar; tuning ranges of up to 1.5:1 could be obtained; and efficiencies up to about 8% had been achieved. Dr. Dow said that the principal obstacle to successful application of GaAs microwave oscillators was at present the quality of the GaAs raw material and he mentioned that developments were in progress to improve the quality.

Other bulk-material phenomena

Microwave oscillations produced by GaAs bars biased on the positive-resistance region of the static I/V characteristic at a point below the normal voltage for Gunn travelling-domain oscillations were reported by W. K. Kennedy (Cornell University, U.S.A.) in a paper read by L. F. Eastman. The oscillators had been tuned from 7 to 9Gc/s by means of a waveguide cavity, and the maximum peak power observed had been 500mW, with an efficiency of 2.2%. GaAs elements had also been operated as reflection type amplifiers, with a power gain of 16dB over the 7-9 Gc/s range, the output power saturating at about 150mW. Eastman described his own experiments on using GaAs Gunn-effect diodes (natural frequencies; 500 to 3,500Mc/s) for noise generation in the microwave spectrum. In general this was done by operating the Gunn diodes into circuits of higher impedance than those of the GaAs elements.

In the field of piezo-electric semiconductor devices, it appears that the one-time high hopes for acoustic microwave amplifiers have not, in the event, been fulfilled. Workers in this field seemed to agree that the conventional transistor amplifier had now overtaken the acoustic amplifier at microwave frequencies, and that the major

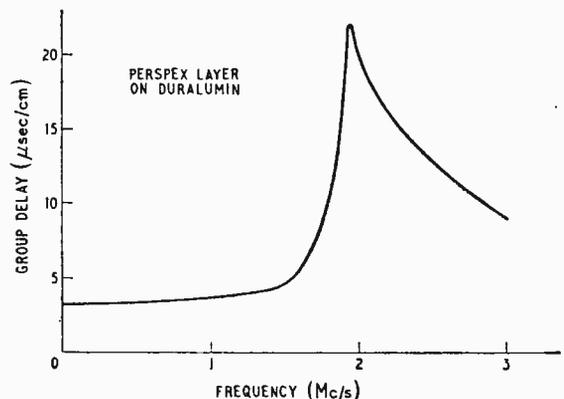


Fig. 1. Delay characteristic of experimental acoustic delay line using Rayleigh surface waves—one possible step towards microwave integrated currents.

1. “The Gunn Effect,” *Wireless World*, August, 1965, p. 416.
2. *loc. cit.* See also “Mechanical Microwaves,” *Wireless World*, January, 1965, p. 57.

trouble with cadmium sulphide acoustic amplifiers was the lack of consistency in the performance of CdS samples. (It was suggested that this might be due to a lack of homogeneity in the crystals.) Tests on crystals reported by G. Robertson (University College, London), using a thin light beam as a probe, showed marked variations in conductivity and acousto-electric coupling along the length of the material.

O. Cahen and E. Dieulesaint (Thomson-Houston, France) described a CdS acoustic microwave amplifying equipment in which the acoustic gain was 45dB at 700 Mc/s, but it turned out that, owing to losses in the thick quartz transducers and in the CdS, the overall electrical "gain" was -30dB! However, the authors said they were hoping to achieve net gain eventually by the use of thin-film transducers deposited on the CdS.

Microwave integrated circuits

In the meantime, it seems possible that these piezoelectric elements may prove useful as passive components in microwave systems, and a number of research organizations in the U.K. are studying possible applications very closely, particularly in the field of microwave integrated circuits. E. A. Ash (University College, London), for example, pointed out that whereas complete amplifiers for microwave integrated circuits could be fabricated on small silicon chips, no comparable progress had been made in the construction of the resonators, filters, etc., needed to interconnect the amplifiers. Since microwave integrated circuitry was primarily concerned with surfaces, he felt that the surface or Rayleigh acoustic wave was well adapted to this field of technology, particularly as there were now acoustic materials available with lower loss per wavelength (dB/ λ) than that of e.m. waveguide. As a result of using acoustic techniques instead of conventional e.m. waveguide components, considerable size reduction should be possible—as much as 10^5 times, in fact.

By way of illustrating the use of Rayleigh waves, Dr. Ash described an experimental delay line, such as might be used in pulse-compression radar, that had been constructed in his laboratory. This comprised an aluminium substrate, coated with a 0.3mm Perspex layer to allow dispersive waves to be obtained, with a transducer at each end. The delay characteristic is shown in Fig. 1. Similar work on the use of surface waves was reported by F. Mayo and C. P. Wen (R.C.A., Princeton, U.S.A.) and included descriptions of "two-dimensional" transducers evaporated on to the delay-line element.

Magnetoresistive elements

The use of the magnetoresistive properties of indium antimonide to give amplification, oscillation or attenuation at microwave frequencies was discussed by S. Kataoka and H. Naito (Japanese Government Electro-technical Laboratory, Tokyo) in a paper read by a colleague. The principle is that if d.c. is passed through an InSb magnetoresistive element which is subjected to the transverse magnetic field of a microwave signal (plus a constant, biasing magnetic field), a microwave e.m.f. is generated across the element as a result of the multiplying action between the current and the microwave magnetic field. If the element is placed in a cavity in a position where the transverse magnetic field is at maximum and the electric field at zero, the element, in principle, absorbs no signal power. In this way the direct current can be converted into microwave r.f. energy. A description was given of a device based on this principle for operating as an amplifier or an attenuator at 9,840 Mc/s. The cavity

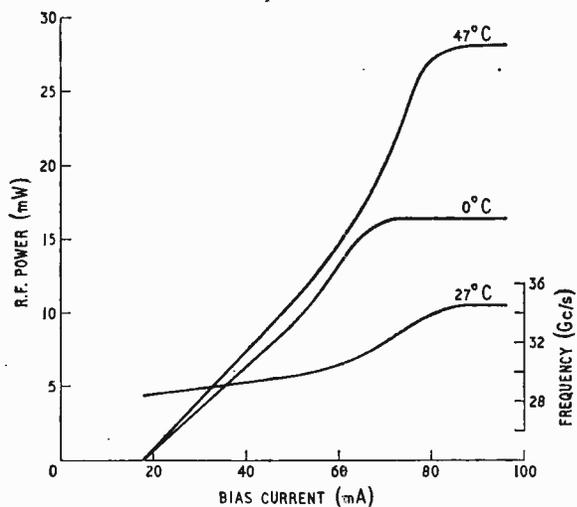


Fig. 2. Power output and frequency performance of a commercial GaAs avalanche diode at different bias currents. (Power measured at 0°C and 47°C; frequency at 27°C.)

contained the InSb element and a tuning piston, and there was a common channel for the d.c. input and the microwave output. Gain or loss was controlled by the direct current or the biasing magnetic field.

In the field of junction-diode, as distinct from bulk material, devices, one of the latest fields of interest is the operation of silicon and gallium arsenide diodes in the avalanche mode, by suitable d.c. biasing, to produce negative resistance effects which can be utilized for oscillation or amplification. In such devices the usable frequency range is related to the transit time of the current carriers through the space charge depletion layer of the diode, which, for example, would be a few microns thick for operation at 10 Gc/s. C. C. Shen and L. A. MacKenzie (Cornell University, U.S.A.) described some experiments using commercial gallium arsenide diodes with different doping levels in oscillation circuits. They stated that very wide operating frequency ranges had been achieved. One diode, for example, produced oscillations in the 2-4 Gc/s band in a coaxial system, in the 7-12 Mc/s band in X-band waveguide and at 50 Gc/s in millimetre waveguide. Results obtained with one diode, in terms of r.f. power output and frequency with varying d.c. bias current, are shown in Fig. 2. The authors had also examined the effects of temperature variation and had found that increasing temperature resulted in increasing power output (as shown in Fig. 2) but decreasing oscillation frequency.

Many of the devices described at the conference were very experimental, and it is hard to say at present which of them will prove successful in the microwave applications of the future and which will turn out to be little more than laboratory curiosities. It has been rightly observed, however, that this whole new field of bulk-material and transit-time phenomena is reminiscent of the arrival of velocity-modulated and crossed-field devices in the valve field several decades ago, and that the coming era of development, as then, will result in important new commercial devices with substantial frequency ranges and power outputs.

The MOGA conference was sponsored jointly by the I.E.E. and the I.E.R.E., and the proceedings are expected to be available in two or three months' time.


NEWS FROM INDUSTRY

COMPACT COMPUTER

OVER 20 million orders per minute can be processed by Myriad II, a new Marconi microelectronic parallel computer. A simpler version of Myriad I, it is a basic instrument using the techniques of modular construction, permitting extra units to be added to the computer with any or all of Myriad I facilities. Myriad II is also designed to be compatible with Myriad I in order that programmes may be interchangeable. This computer is contained in a desk and two cabinets. The control unit is mounted on top of the desk with additional equipment such as tape recorders, tape punches, magnetic drums and disc stores. It uses a 24-bit word, and an order code in simple single address form, the orders being obeyed sequentially. Two sizes of store unit are available with either 4,096 or 16,384 (24-bit) words, providing storage capacity up to a maximum of 32,768 words. The stores are coincident current, ferrite core types with a cycle time of 1.5 μ s, and access time of 0.5 μ s. If required, magnetic disc or drum stores with average access times of 85 and 10ms respectively can be added, and a maximum capacity of 2 million words is then available. It has been designed to form the centre of complex data handling systems, such as industrial process controls, and all types of traffic control, and systems can be provided for small control centres which can be built up as the degree of automation is increased. Myriad I remains more suitable for high-speed applications.

An independent company has been formed to manufacture quartz crystal units and is known as **Crystal Electronics Ltd.** of 1 Shore Road, Hythe, Southampton. All U.K. military crystal holder styles are available within the frequency ranges 50 to 150 kc/s, and 1 to 20 Mc/s. Additional types include the U.S. military crystal holder styles, and flying lead alternatives to the plug-in pin types. Quartz crystal for high grade filter applications will be supplied to customers' specifications. One of the company's principals, Mr. T. C. McKnight, who will supervise the technical process, has sixteen years' experience in the quartz crystal development industry.

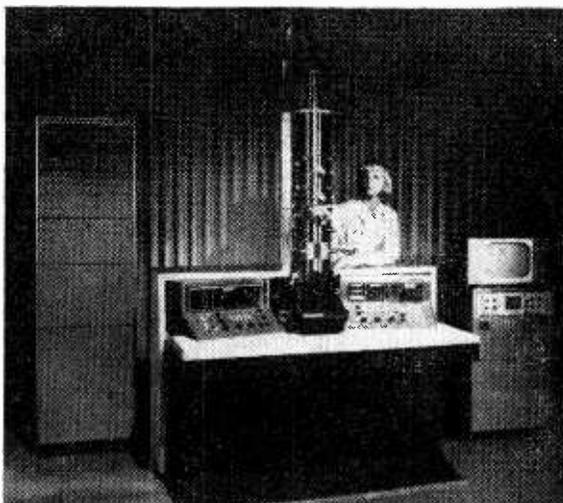The new 22,500 sq ft Hertfordshire factory for **Kerry's (Ultrasonics) Ltd.** and **P. G. Day (Electronics) Ltd.**, both subsidiaries of Kerry's Engineering & Electronics Ltd., was officially opened on the 26th September. This new headquarters of the two companies is at Hunting Gate, Wilbury Way, Hitchin, Herts. With full production, and inte-



The EMU-4 electron microscope by the RCA International Division, 30 Rockefeller Plaza, New York 20, N.Y., has automatic pumping operation for its vacuum system and an optional image intensifier device that "sees" the image via television and a light intensifier image tube, and displays it on a television picture monitor. Magnification is 200,000x with a resolution of 8Å. For spot size control down to 2 μ m there is double condenser operation.

gration of the Stratford, E.15, and the Basildon, Essex, departments, it is estimated that about 100 staff will be employed. Ultrasonic equipment developed and produced by Kerry is used in industrial cleaning, the machining of hard and brittle materials, spot, seam, and ring welding of metals, the welding of thermoplastics, and biochemical research. In the field of micro-circuit, semi-conductor, and integrated circuit production, ultrasonic welding equipment is available for welding aluminium conductors to gold film deposits on glass, and with the same equipment, copper, nickel and gold wires can be ultrasonically welded to rare and precious metal films deposited on glass or ceramic substrates.

The development of a new system for the **disc recording of video signals** is the objective of a newly formed company, **Video Records of Wolverhampton**. The video information is recorded on the photosensitized area of a 10 in disc.

A. N. Clark (Engineers) Ltd. of Binstead, Isle of Wight, manufacturers of telescopic masts, and **Precision Metal Spinings (Stratford on Avon) Ltd.**, specialists in the design and manufacture of microwave aerial dishes, have now joined the **Coubro & Scrutton** group of companies. With other members of this group, who are **Associated Aerials Ltd.**, and **R. T. Masts Ltd.**, **Coubro & Scrutton** can offer a comprehensive aerial service from l.f. to microwave frequencies, including masts, supporting structures, and installation facilities.

Three u.h.f. transmitters have been ordered by the B.B.C. from the **Marconi Company** for installation in 1968 at a cost of £300,000. They have been

designed for completely automatic un-attended operation except for occasional routine visits. From Caradon Hill in Cornwall, Sandy Heath, Beds, and North Yorks they will broadcast BBC-2 programmes and will be capable of handling colour. The 40kW vision transmitter employs an English Electric 4-cavity klystron valve and this section and its associated 8kW sound section transmit separately. Breakdown precautions take the form of multiplex facilities which provide automatic changeover to a combined sound and vision signal at reduced power on one section, should the other section fail.

A contract for a **computer-controlled traffic regulation system** for the City of Liverpool has been placed with the **Plessey Company**. The system, which covers the Mersey Tunnel approaches in the city centre, provides for the control of tunnel-bound traffic in such a manner that when there is a hold-up in the tunnel, the queues of vehicles in the approach roads are kept clear of main intersections to minimize interference with cross traffic. The system, employing an XL9 computer, utilizes buried inductive loop "presence detectors" at strategic intersections. It also provides for automatic emergency routing of appliances on the receipt of a warning of fire in any given sector of the city.

Texas Instruments Inc., **Fairchild Camera and Instrument Corporation**, and **SGS Fairchild** (Fairchild's European affiliate) have entered into a cross licensing agreement for patents held by each company in the field of semiconductor manufacture. The ten-year agreement covers world patents except those in Japan.

LETTERS TO THE EDITOR

The Editor does not necessarily endorse the opinions expressed by his correspondents

Organ Tuning

IN spite of Mr. Daniel's protestations (September issue), I still maintain that an average good tuner will avoid a too quick beat which would take place if the "temperament" was truly equal (i.e. $12\sqrt{2}$). We are of course talking about beats, where, in the case of a fourth they occur at exactly twice the rate of those caused in a fifth for each cycle of discrepancy from the pure (untempered) interval, and therefore a cycle here or there makes all the difference.

About eighteen years ago I tuned an electrophonic instrument to what I then called "mean beat tuning" (for want of a better name). It was an attempt to create a scale which is in my opinion the sort of scale a tuner would produce—which is very nearly a true progression, but not quite. The instrument when first tried in a shop containing a dozen or more organ builders of the old school, produced the unanimous exclamation "What have you done—this is the first time we have heard one of your machines sound something like a pipe organ."

I cannot quite see the relevance of $A=440$ c/s when middle C=261 c/s. If $A=440$, the C is 261.6256 c/s. However, I have performed the mathematical task of $261 \times (12\sqrt{2})^9$ and this works out to 438.9479. Oh yes, only a cycle or so, but several beats nevertheless, and these are the subtle differences I intended to convey in my letter. Helmholtz is alleged to have described equal temperament as a "hellish din" anyway, and added "give me my justly tuned harmonium." It is instructive to tune an organ to a pure scale. It makes one realise to what dissonancies our ears have become accustomed.

Regarding Mr. Douglas's comment upon the Compton Rotofon speaker, I would say that Doppler effects plus certain phase reversals are exploited, whereas the rotating speakers of some organs which I have seen, do not, at least to the same extent.

LESLIE E. A. BOURN,
Technical Director.

The John Compton Organ Co., Ltd.,
London, N.W.10.

The Engineer Shortage

MR. SCROGGIE'S thoughtful letter in your September issue is timely. Well may engineers puzzle over why engineering does not appear an attractive career to boys. The trouble is that all too few engineers do puzzle over it and even fewer attempt to put matters right.

The plain fact is that the public does not understand how vital engineering is to the country's future and consequently is not prepared to accord due recognition (including money) to engineers. The first difficulty for the public is the confusion about the term "engineer," for not only do professionals and artisans alike use the same name but there are so many divisions in engineering.

It was an awareness of the difficulties made by fragmentation that caused the Institutions to create the Council of Engineering Institutions so that they could, where necessary, speak with one voice. The Council, with the valuable support of the Ministry of Techno-

logy, is doing much to enlighten people, especially young people, about the work of engineers and its vital contribution to our way of life.

As to "prospects," action in the field of individual salaries, pensions and conditions of service is not the concern of the C.E.I., but of the Engineers' Guild Ltd. Roughly speaking the relationship of the Guild to the C.E.I. is comparable with that of the British Medical Association to the General Medical Council. If more engineers of Mr. Scroggie's persuasion would join us, the Engineers' Guild would be in a stronger position to introduce reason and logic into the assessment of engineering salaries.

Engineers' Guild,
London, W.1

J. K. RICKARD
(Hon. Sec.)

TV Research Today

"RADIOPHARE" asks why we have no one like Shoenberg to make dramatic innovations in television today. But is this the right question? A classical investigation of the theory of picture scanning¹ was published in U.S.A. in 1934, and the existence of a body of telecommunication research workers in the Bell Telephone Laboratories must surely be an important factor. After the British invention of interlaced scanning, the next big step was colour on a sub-carrier frequency-interlaced with the main video signal: first R. B. Dome, then the N.T.S.C. system, and finally the present European wrangle over SECAM, PAL, SEQUAM and so on.

The French went ahead with 819 lines (on which I have commented favourably: see "More Lines Instead of Colour?", *Wireless World*, May 1956, p. 239), but it appears that 819 lines is being squeezed out by 625. As there have been so few major television developments, should we really be distressed that Britain has not pulled another golden rabbit out of the hat?

For some years research workers in U.S.A., Britain, France, Russia and Australia (and possibly elsewhere) have been seeking means of reducing bandwidth, but the statistical structure of the typical picture is against us: it has such infinite variety. Some of the more promising schemes have been set up and tested by the B.B.C.² Too much is now known about picture-forming processes and about radio propagation for it to be easy to innovate. Turning to "Radiophare's" list of questions, I make the following comments:—

(1) Transmitters and receivers for quasi-optical frequencies. This in practice means laser technology, which is by no means neglected. Propagation is a very major question: is it worth pursuing a television system which would be available only on a piped basis and, therefore, only in densely populated districts? The natural field for the initial development of these techniques is in point-to-point telecommunication.

(2) Efficient wideband modulation methods. What does this mean if not "more efficient methods of packing information into the sideband?"

(3) More efficient methods of packing information into the sideband. This is the obverse of "bandwidth reduction," and the various schemes of colour television are

more or less successful examples of putting three pints in a one-pint pot without losing too much.

(4) Multiple interlace and bandwidth reduction. I have myself instigated a trial of frequency interlace³ and there is an extensive literature on bandwidth reduction. It is dangerous to say that anything is scientifically impossible, but equally dangerous to find oneself seeking to overcome some fundamental principle of nature such as the second law of thermodynamics. (Remember the Stenode receiver based on a denial of the existence of sidebands?) "Shannon theory" may be relevant, as was recently suggested in *Wireless World*⁴.

(5) Simple high-stability oscillators. I suspect that "Radiophare" means *cheap* high-stability oscillators, for use in receivers. Then I must ask two questions. (1) How much should a receiver manufacturer spend on how good an oscillator? (2) Are all present-day receivers equally unsatisfactory, or have some manufacturers already solved the problem?

(6) Local distribution of wideband video. What about Professor Barlow's work on waveguides? Again I assume that receiver cost is important, so p.c.m. is not likely to be practicable and there would be objections even to f.m.

(7) Improved resolution in camera pick-up tubes. I suspect that this could be provided if needed. What did the French do for 819 lines?

(8) & (9) Improved c.r.t.s and alternative forms of display. This is an interesting field because it does not appear to come into immediate collision with fundamental laws of nature. There are, however, some fairly basic limitations on c.r.t. brightness and focus because (a) the current-density in the spot is related to the current-density at the cathode and (b) the sharpness of definition of the spot is ultimately limited by the random (thermal-agitation) electron velocities transverse to the beam. I suspect that we could have a lot more if we paid for it, just as the performance and comfort of some expensive cars is a long way beyond that of the family car.

"If we paid for it" is the problem. It appears that since 1945 television has been regarded largely as a means of keeping afloat the domestic radio side of the industry. The *laissez-faire* economist would say simply that if the companies in the radio and television receiver industry cannot make a profit, they must either close down or make something else. The planning economist would say that if television is to be subsidized, we must know why. B.B.C. money comes from viewers and N.R.D.C. money from taxpayers, so does "Radiophare" honestly want to vote 10s worth of TV licence or a pennyworth of income tax to television research? Even if he does, is he right? Machine tools, computers, nuclear reactors, and space vehicles are other applicants for our research money and manpower, and all would claim to have export potential. So the decision is really a politico-economic one.

The worst thing would be to pour out money in the vague hope that it would somehow generate ideas. But on the other hand I suggested in my first paragraph that the presence of an active body of research workers could contribute to the

generation of information and ideas. The way out of the dilemma is to be reasonably generous with money whenever there is any sign of long-range ideas. Unfortunately the Science Research Council appears at present to be limiting the amount of money available for long-range and fundamental research, perhaps on the ground that Britain's present economic situation demands urgent rectification of our alleged weakness in technological development in spite of brilliance in fundamental research. None the less I believe that if anyone has an outstanding idea it is still just possible for him to get sufficient support to develop it.

D. A. BELL

The University of Hull.


1. Pierre Mertz and Frank Gray, "A Theory of Scanning and its Relation to the Transmitted Signal in Telegraphy and Television," *Bell S.T.J.*, Vol. 13 (1934), p. 464.
2. G. F. Newell and W. K. Geddes, "Tests of Three Systems of Bandwidth Compression of Television Signals," *Proc. I.E.E.*, Vol. 109B (1962), p. 311.
3. E. A. Howson and D. A. Bell, "Reduction of Television Bandwidth by Frequency Interlace," *J. Brit. I.R.E.*, Vol. 20, No. 2 (Feb. 1960), p. 127.
4. H. O. Codon, "Communication Theory and Colour Television," *Wireless World*, May 1966, p. 243.

Simple Receiver for Low-voltage Operation

THE receiver described in the October issue utilises three r.f. stages and one a.f. stage. While this is the best strategy from the point of view of sensitivity, it is not the approach that leads to the lowest current consumption, since most transistors only work well as r.f. stages when they pass about 1 mA collector current.

The diagram below shows a circuit which works well with as little as 300 μ A total battery current. Here the gain is concentrated in three a.f. stages. At the r.f. end, one high-beta transistor is used as a buffer between the tuned circuit and the detector diode. The tuned circuit may be connected directly to the base without appreciable loss of selectivity because of the high input impedance of the emitter follower. This arrangement provides an effective gain of around ten by dispensing with the usual step-down transformer to match the tuned circuit to the transistor. By itself, this is hardly enough, but the addition of a reaction winding of about three turns enables sufficient r.f. signal to be presented to the detector for reception of the Home, Light and Third programmes in the London area, using a ferrite rod aerial three inches long. The 100- Ω resistor in the base circuit of the first transistor was put there to reduce interference from the local television station. It could probably be omitted in most areas.

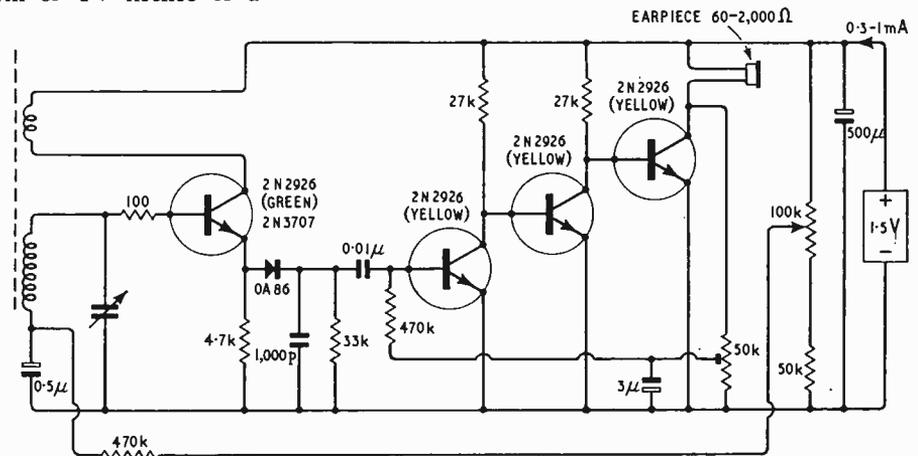The receiver is quite simple to operate, the only irri-



tating feature being that, if reaction is pressed to the limit, there is some backlash, and retuning is necessary after adjusting the reaction control. Earpieces with resistances between 60 and 2,000 Ω may be used; the current taken rises to about 1mA with a 60- Ω earpiece.
Croydon.
G. WAREHAM

Receiving Stereo Broadcasts

YOUR article under the above title in the September issue seems to paint a somewhat gloomy picture of the possibilities of stereo reception and, at the same time, appears to contain certain inaccuracies and a lack of appreciation of practical and operational requirements.

In the brief outline of the pilot-tone system, your author claims that, in a monophonic receiver, use is made of 90% of the available modulation. This is correct but surely results in a signal-to-noise deterioration of approximately 1 dB and not 4 dB as stated. It may well be that statistically the $L+R$ content of a typical stereo broadcast is some 3 to 4 dB down on the level of a comparable monophonic programme but this does not derive directly from a consideration of system limits. He goes on to say that for stereo reception the signal-to-noise ratio is worsened by about 22 dB but appears to accept the situation, without question, as a price to be paid. A simple qualitative explanation then, may not be out of place here. In a basic f.m. system the noise associated with the sidebands inherently increases rapidly as these sidebands become remoter from the carrier. (Hence the use of pre-emphasis in a monophonic broadcast.) The noise associated with modulation frequencies centred on 38 kc/s is thus relatively large. Although this is not heard directly because of its frequency range, it is translated down into the audio band by heterodyne action with the locally re-inserted 38 kc/s sub-carrier and at once becomes audible. It is, in fact, this latter noise, after normal de-emphasis, which accounts for the deterioration of signal-to-noise performance under stereo conditions.

It is not intended in this note to discuss decoders in detail, but concerning those employing a switching process it must be said that there is no need to use a 1:1 mark-to-space ratio rectangular waveform which, admittedly, does not yield adequate separation of the channels. On the contrary, sine wave switching with the angle of flow limited to less than 180° does, however, give excellent results.

Regarding the presence of a basic 38 kc/s signal in the audio outputs it will be appreciated that harmonics of this frequency are also present and thus twin-T filters may not of themselves provide adequate suppression. However, the 50 μ s de-emphasis network will attenuate the 38 kc/s component by over 20 dB and its harmonics even more, probably making the inclusion of any additional filter unnecessary.

Finally, let it be said that the writer is not unaware of the theoretical considerations in the general field of stereo broadcasting but feels that in certain circumstances their importance can be exaggerated when applied to domestic entertainment.

Let your would-be stereo listeners take heart. Let them provide themselves with decent aerials, good average receivers and decoders and enjoy this new facility.
London, S.E.19.
G. D. BROWNE

IT is true that, by itself, a 10% reduction in deviation would result in a 0.9 dB reduction in s/n ratio. But in the pilot-tone system, since the $L-R$ signal contributes to the deviation as well as the $L+R$ signal, the

$L+R$ or mono output will generally be less than it would be were the sub-carrier absent, by an amount depending on the lack of correlation between L and R channels. (Typically, the total loss would be about 4 dB*.) Thus it is fair to say that as a result of using the pilot-tone system, in which the main channel deviation is limited to 90% of 75 kc/s, the reduction in s/n ratio is 4 dB.

We are pleased that Mr. Browne raised a point on which we did not go into detail. However, it should be said that reducing conduction usually means reducing output also. For instance, reducing conduction from 180° to 40° would reduce output by 13 dB and reduce the post-detection correction from 4 dB to less than 1 dB†. Mr. Browne's "good average receivers" calls for comment. According to one company who adapt receivers for stereo reception, nearly all the latest British tuners are "quite incapable" of producing the necessary bandwidth and detector linearity!—ED.


* See "Stereo Broadcasting and Reception" J. G. Spencer and G. J. Phillips, *Radio and Electronic Engineer*, June 1964 (Appendix I), and "Determination of the effective depth of monophonic programme transmitted on the pilot-tone system" D. E. L. Shorter, *E.B.U. Review* Part A Feb. 1963.

† see "Stereophonic FM-Receivers and Adaptors" D. R. von Recklinghausen, *I.R.E. Trans.* vol. BTR-7, Nov. 1961, p. 67.

Television Distribution

YOUR contributor, "Radiophare," seems to live in a strange world. It is as though each home was on a separate satellite with no possibility of physical contact between them. Reality is different: most of us live in towns and cities where the distance between one home and the next is but 15 yards. Having got sound and vision signals to the first home in a city the problem is how to extend it to the next. Any of your readers, if faced with this problem in the course of an ordinary day's work, would, I am sure, do the obvious thing and run a bit of cable to it. If they were then asked to extend the signal to the next home they would repeat the process and so on to the boundaries. Given a little time for reflection they would realise that their problem was to design for the maximum efficiency and lowest cost of the unit shown in the diagram. I have no doubt that they would soon conceive an h.f. wired network.

Once the problem is seen in this light the idea of equipping every home as a satellite reception station appears as the absurdity which it is; being, indeed, only one degree less absurd than enabling every home to accept from a distance of 15 yards picture signals containing no redundancy. "Cathode Ray" has already put the suggestion for 1,000 or 2,000 lines into its proper perspective and I will only add that if "Radiophare" should ever find himself in a position to decree this

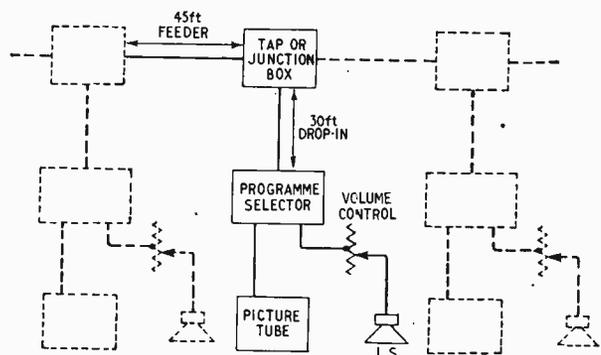

marvellous thing, he could do it most easily and cheaply with a wired distribution system.

I hope that he may learn to see the problem of broadcasting in this light as it will restore his pride in his own country which leads the world in wired distribution. In contrast to the elaborate demonstrations of electronic expertise which "Radiophare" would inflict on the long-suffering public, high-frequency wired systems bear the true hallmarks of good engineering; they are simple, reliable and cheap.

Rediffusion Ltd.,
London, S.W.1.

R. P. GABRIEL

The Diode-transistor Pump

I AM sorry about the misprint in the opening paragraph of Mr. Waddington's article in the July issue but even the corrected version ("Letters" p. 458, September) does not help me to understand why one should be so concerned about the slope sensitivity of the simple pulse-rate discriminator. At an input-to-output ratio of 10:1 the basic differentiator and clamp will depart from linearity by about 0.7%. If this point is arranged to correspond with an input frequency of 300 kc/s (for a nominal centre frequency of 150 kc/s) a 10 V step at the input will give an output of ± 0.25 V at very low distortion for a deviation of ± 75 kc/s. Since this level is some 40 dB above the maximum input sensitivity of most pre-amplifiers, the programme signal at the discriminator is not likely to be degraded by the audio circuits.

The performance of the basic circuit is, of course, ruined by adding an integrating capacitor and this component must either be isolated in the way Mr. Waddington has done or dispensed with altogether. A moving-

coil meter placed in series with the differentiator will sense the mean level of the output current pulses without the aid of a capacitor and for f.m. receiver application the 50 μ s de-emphasis function can be combined with the first stage of the pre-amplifier along with the equalizing networks for gramophone, tape and other inputs. The only point to watch here is the possibility of overloading the audio stages by the relatively large discriminator pulses.

Mention should be made of the f.m. receiver design by E. D. Frost¹ which includes an inherently linear pulse-rate discriminator of a centre frequency of 300 kc/s for stereo operation. This receiver appears to combine the best of all worlds and probably represents the proper basis from which future developments should proceed. There still remain many points of detail to interest the circuit designer but the case for high discriminator output is, I suggest, not one of them.






Lee-on-the-Solent,
Hants.

A. S. CHESTER

¹ Frost, E. D., 'Pulse-counting F.M. Tuner'—W.W. Dec. 65

The author replies:—

From Mr. Chester's comments, it is obvious that he only visualizes one use for a frequency/voltage converter, namely that of discriminator for an f.m. tuner. While I concede that only a few millivolts of input are required for the "general purpose pre-amplifier," the discriminator may, and most probably will in the future, be called upon to drive a stereo decoder. These in general require a higher input. The discriminator may also be used for a.f.c. and for this a large d.c. output is desirable. However, as I tried to show in my article, there are also many other applications of frequency/voltage converters where a large output voltage, coupled with good linearity, is an essential.

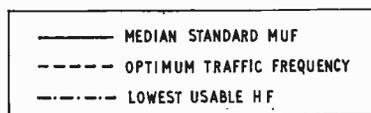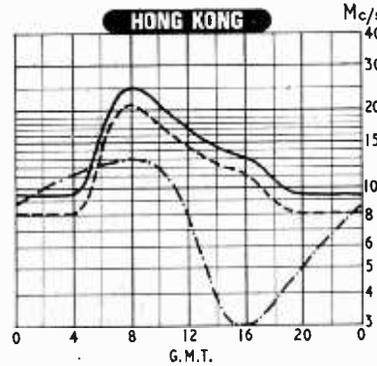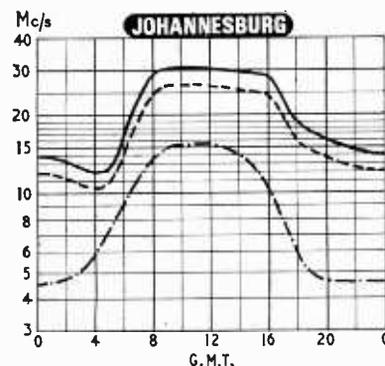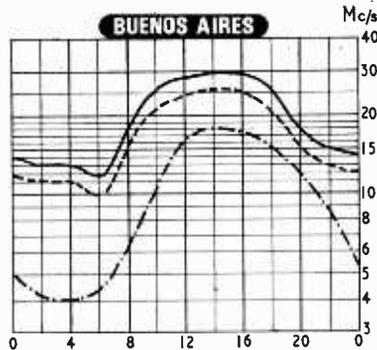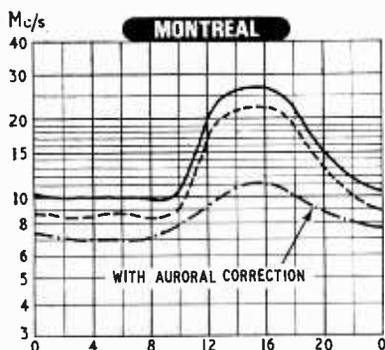

H. F. PREDICTIONS NOVEMBER

The higher daytime MUFs, characteristic of the winter months, are now becoming apparent for circuits predominantly in the Northern hemisphere. The Northern Auroral Zone passes roughly through Alaska, Hudson Bay, Iceland and Northern Norway. Radio paths passing through this zone are subject to additional absorption, and a correction is made for this in the calculation of the lowest usable frequency (LUF).

The prediction curves show the median standard MUF, optimum traffic frequency and LUF for reception in this country. Unlike the standard MUF, the LUF is closely dependent upon such factors as transmitter power, aerials, and the type of modulation. The LUF curves shown were drawn by Cable and Wireless Ltd. for commercial telegraphy and assume the use of transmitters of several kilowatts and aerials of the rhombic type.

More about Farnborough

NEW NAVIGATION AND GUIDANCE SYSTEMS AT 1966 S.B.A.C. EXHIBITION

LAST month we were able to do little more than mention a few of the interesting items seen at the Society of British Aerospace Companies' exhibition ("Avionics at Farnborough," October issue, p. 487). The following is a continuation of the report, in itemized form, and contains photographs of the new Cossor secondary radar transponder, the S.T.C. improved I.L.S. and the Marconi mobile ground radar outlined last month.

Television target simulator.—As part of a general programme of work on visual factors in flying aircraft, the Royal Aircraft Establishment were demonstrating a simulator using television technique for studying problems in low level flying—in particular the task of looking for objects on the ground. A background scene, which can be a photograph of natural countryside taken from the air or a highly complex artificial scene specially constructed for the job, is televised and displayed on a television monitor. A small square target is superimposed on the background, and this target may be varied in contrast and size either in steps or continuously in accordance with an exponential law. The contrasts in the background may also be varied, from a zero-contrast plain grey display, in conjunction with the exponential change of the target contrast. One recent study was on the contrast threshold of the eye. This, the minimum contrast at which the eye can see the target, is necessary for producing theoretical predictions of visual ability and has been investigated by many experimenters. In the past, plain backgrounds to the target have been used and the results have tended to prove optimistic when applied to the real-life situation. A demonstration on the simulator showed that much of this discrepancy could be explained by the existence of a textured background.

A further demonstration was concerned with the effect of noise on the television display. R.A.E. are interested in the levels of noise which affect a person's performance in a specific task. Again it has been found


that the complexity of the background used in the experiment has a direct bearing on the effect of noise, and also that quite obtrusive levels of noise may be tolerated by the observer in his task of searching for a small square target of near threshold contrast.

Television-aided missile guidance.—Components of an Anglo-French air-to-ground missile system called MARTEL, using television for observing the target area, were shown by Marconi, the developers of the television equipment. A sensitive television camera is fitted into the nose of a missile carried by a supersonic aircraft and, after the missile has been launched, the picture from this camera is transmitted back to the aircraft, where the pilot views the target area on a c.r.t. monitor. A joystick enables the pilot to control the field of view of the camera. Once the target has been selected, control signals within the missile adjust the flight path to bring the major axis of the missile into alignment with that of the television camera. The missile itself is being developed by Hawker Siddeley Dynamics in conjunction with Engins Matra of France, and flight trials using the television system have already taken place.

Missile "miss-distance" indication.—Parts of two electronic systems for

indicating the "miss-distance" of a guided missile relative to a practice target were displayed by Ekco Electronics. One system uses a radioactive source fitted to the missile, and the miss-distance is determined by a gamma-ray monitor carried in the target. Another system operates on an acoustic principle in which the peak amplitude of the shock wave generated by the missile is measured in the target. With both systems the information obtained in the target is telemetered to the towing aircraft, or to the ground, where it is processed to give miss-distance in digital form.


U.H.F. homer and transponder beacon.—The latest version of the MR343 tactical radar transponder beacon made by Rank Bush Murphy is fitted with a u.h.f. homer. The beacon is designed for parachuting to the ground with airborne assault forces, and as a secondary radar transponder operating in conjunction with Rebecca airborne interrogators it provides distance and homing signals for support aircraft. In the u.h.f. homer application, it provides a homing signal for aircraft fitted with homer equipment operating in the 225-240Mc/s range. The homer uses a crystal-controlled m.c.w. transmitter giving a 150mW peak power output. This is modulated at 3.5 kc/s and 1.7 kc/s by an electro-mechanical encoder, using a photo-

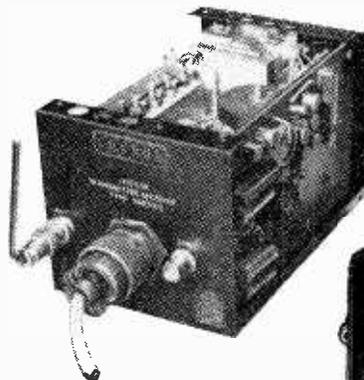

Left, Integrated-circuit airborne transponder of the Cossor SSR 2100 secondary radar and I.F.F. equipment (see October issue p.487).



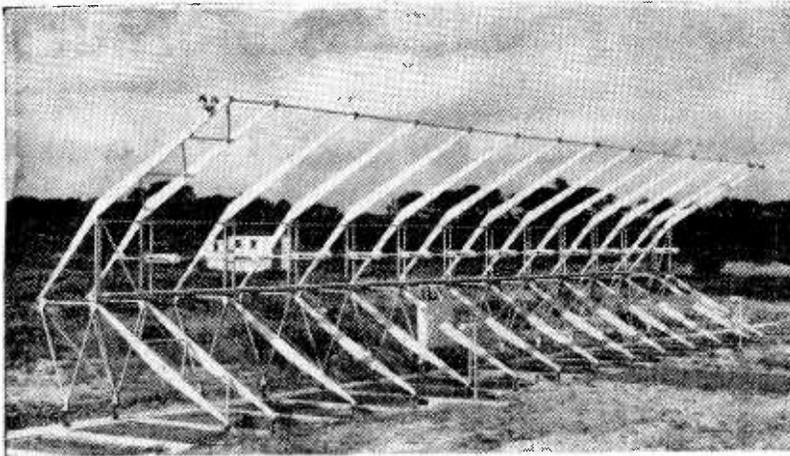Below, Tactical navigation beacon MR 343 made by Rank Bush Murphy, incorporating a u.h.f. homer facility.




The 85ft localizer aerial array of the S.T.C. improved I.L.S. equipment STAN.7/8/9 which meets (CAO's accuracy and reliability requirements for Category III operational performance (see October issue, p.487).

transistor, which can generate morse identification signals. Power is provided by a 12V nickel-cadmium battery.

Loran C (and A) receiver.—The Decca Navigator Company were showing a compact airborne receiver, using solid-state circuitry, designed to make available to an aircraft navigator the full position-fixing facilities of both the Loran C and the Loran A navigation systems. Loran C (on which Decca have patents) has not yet been widely used for aircraft navigation, but it is stated that flight trials have shown it to be a promising system. Like Loran A it is a hyperbolic pulse system giving a pair of time-difference measurements in the aircraft, but instead of operating on a radio frequency of 2 Mc/s it works

on 100 kc/s. This low frequency virtually eliminates aircraft altitude as a factor of range, and provides a greater ground wave range—which can extend to 1,200 nautical miles over water. Sky waves can be received at ranges up to 2,000 n.m.

Because of the difficulty of transmitting sufficiently short pulses for accurate position fixing, the time difference measurement is based on phase comparison of selected r.f. cycles within the pulses. For this reason the Loran C receiver includes an "indexing" system to ensure correct selection of identical r.f. cycles in all received pulses. Once the master and both slave stations have been acquired, tracking is automatic on both slaves, and either of the two readings can be displayed on demand. Digital outputs are provided

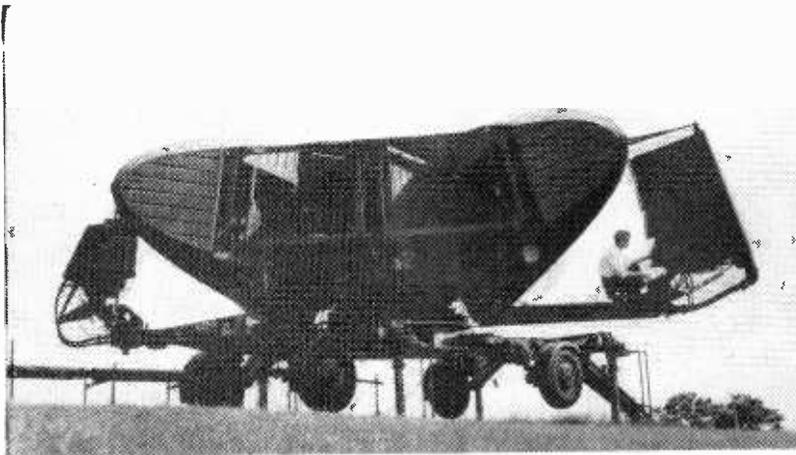

Surveillance radar unit of the Marconi mobile radar for air traffic control or ground controlled interception (see October issue, p.487).

to allow the use of an airborne digital computer for converting the hyperbolic information into latitude and longitude readings or for operating an orthogonal map display. Two versions of the receiver are available, one in a single package, and another comprising three units.

Microminiature airborne computers constructed from integrated circuits were displayed by Elliott and Ferranti. Such computers are designed to reduce the workload on the crew of modern high-speed aircraft by performing on-line routine tasks of data assimilation. Using time-sharing techniques, they accept inputs from navigation and other equipments, perform co-ordinate transformation and other data processing operations and feed information needed for navigation and aircraft monitoring to display units.

The Elliott computer, MCS 920M, is a general-purpose, parallel mode computer with a word length of 18 bits and a core storage capacity of 8,192 words, expandable to 65,536 words. For such on-line working it has four levels of interruption and order modification. The machine occupies a three-quarters short ATR case, weighs 27.5 lb and operates without forced-air cooling at ambient temperatures up to 70°C. Mean time between failures is said to be at least 2,000 hours in an airborne environment. Servicing is a matter of replacing disposable integrated circuit modules, of which there are only 38 types in the whole computer. Techniques adapted from this computer are to be used in an advanced "head up" display system, incorporating Elliott's ceramic c.r. tubes in the display unit, which the company are supplying to the U.S. Navy.

Ferranti's microminiature computers on show were the types FM 1600A and FM 1600B, both derived from the company's Poseidon naval-action data automation computer used in H.M.S. Eagle. The FM 1600A, the smaller of the two, is a 24-bit parallel machine with a 1 μsec core store. The central processor, the 4,096 words of core storage, the input/output logic and the power supplies are contained in a long three-quarters ATR case with a volume of 0.7 cu ft. The FM 1600B is also a 24-bit parallel machine, designed with a philosophy of extensive "software" making up for minimum "hardware." NOR logic elements are used. The add/subtract time is 12 μs and the multiplication time is 38-46 μs. A three-address programming system is used.

NOVEMBER MEETINGS

Tickets are required for some meetings: readers are advised, therefore, to communicate with the society concerned

LONDON

2nd. B.K.S.T.S.—“Baird and television” by T. H. Bridgewater at 7.30 at Central Office of Information, Hercules Rd., S.E.1.

3rd. I.E.E.—Appleton Lecture “The Cambridge one-mile radio telescope” by Prof. Sir Martin Ryle at 5.30 at Savoy Pl., W.C.2.

4th. I.E.E. & I.E.R.E.—Colloquium on “Character recognition” at 2.30 at Savoy Pl., W.C.2.

9th. I.E.R.E.—“Radio and radar aspects of meteorology” by C. E. Goodison at 6.0 at 9 Bedford Sq., W.C.1.

14th. I.E.E.—Discussion on “Market research in relation to electronics design” at 5.30 at Savoy Pl., W.C.2.

16th. I.E.E.—“Reflections from thin layers” by G. Millington at 5.30 at Savoy Pl., W.C.2.

16th. I.E.R.E. & I.E.E.—Colloquium on “Closed circuit television in medicine and biology” at 6.0 at Middlesex Hospital Medical School, Cleveland St., W.1.

16th. B.K.S.T.S.—“Titanium cone loudspeakers” by E. J. Jordan at 7.30 at Central Office of Information, Hercules Rd., S.E.1.

22nd. I.E.E., Television Soc., & B.K.S.T.S.—Colloquium on “Sound on film” at 9.30 at Savoy Pl., W.C.2.

23rd. I.E.E.—“Electronically assisted acoustics in concert halls” by J. Moir at 6.0 at Savoy Pl., W.C.2.

23rd. I.E.R.E.—“Psychological aspects of acoustics” by Prof. J. T. Allanson at 6.0 at 9 Bedford Sq., W.C.1.

23rd. I.E.E. Grads.—“Travelling wave masers” by J. C. Williams at 6.30 at Savoy Pl., W.C.2.

23rd. B.K.S.T.S.—“Special effects” by Bernard Marsden at 7.30 at Central Office of Information, Hercules Rd., S.E.1.

24th. Television Soc.—“Interference to television in the u.h.f. bands” by A. S. McLachlan at 7.0 at I.T.A., 70 Brompton Rd., S.W.3.

28th. I.E.E.—Colloquium on “The use of electromagnetic waves in distance measuring” at 2.30 at Savoy Pl., W.C.2.

28th. I.E.E.—“Elementary particles and resonances” by Dr. F. Heymann at 5.30 at Savoy Pl., W.C.2.

30th. I.E.E.—Discussion on “Transfer-function measuring instruments” at 5.30 at Savoy Pl., W.C.2.

30th. I.E.R.E.—“The development of a pay-television system” by Dr. G. L. Hamburger at 6.0 at the London School of Hygiene and Tropical Medicine, Keppel St., W.C.1.

ARBORFIELD

24th. I.E.R.E.—“Digital radar simulator for air traffic control” by D. Stoddart at 5.0 at Lecture Theatre, School of Electronic Engineering, R.E.M.E.

BASILDON

16th. I.E.R.E.—“Gas lasers” by H. Foster at 6.30 at Barstable Grammar and Technical School, Timber Log Lane.

BEDFORD

7th. I.E.E.—“The education and training of technician engineers” at 7.0 at Bridge Hotel.

BIRMINGHAM

28th. I.E.E. & I.P.O.E.E.—Forum on “Connections in electronic circuits” at 6.0 at M.E.B. Offices, Summer Lane.

BOURNEMOUTH

15th. I.E.R.E.—“Transistor, sinusoidal, stabilized inverters” by C. E. S. Ridgers at 7.0 at the College of Technology.

30th. I.E.E.—“Introducing integrated circuits” by P. Cooke at 6.30 at College of Technology, Lansdowne.

BRIGHTON

8th. I.E.R.E.—“Thin film microelectronics” by T. Cummins at 6.30 at College of Technology.

BRISTOL

3rd. I.E.R.E., I.E.E. & Inst. Prod. Eng.—“Recent developments in satellite telecommunications” by Dr. H. C. Husband at 7.0 at Victoria Rooms, Clifton, Bristol 8.

7th. I.E.R.E. & I.E.E.—“Television recording” by P. Leggat at 6.0 at Large Lecture Theatre, The University.

16th. Inst. Prod. Eng.—Viscount Nuffield Memorial Paper “A survey of microelectronics, including future developments” by Dr. I. M. Mackintosh at 7.0 at The University.

CAMBRIDGE

10th. I.E.R.E. & I.E.E.—“Some problems in the design of electrical filters” by J. K. Skwirzynski at 8.0 at University Eng. Dept., Trumpington St.

24th. I.E.E.—“Speech compression” by Dr. J. Swaffield at 8.0 at University Eng. Dept., Trumpington St.

CARDIFF

4th. Television Soc.—“Microelectronics” by Dr. S. Forte at 7.30 at Angel Hotel.

9th. I.E.R.E.—“Latest developments in radio astronomy” by Dr. P. Williams at 6.30 at Welsh College of Advanced Technology.

CHELMSFORD

28th. I.E.R.E.—“The Watkins-Gunn effect: negative resistance in semiconductor” by B. K. Ridley at 7.0 at the Technical High School, Patching Hall Lane, Broomfield.

COVENTRY

28th. I.E.R.E.—“Electronic exchanges” by E. S. Grundy at 7.15 at Lanchester College of Technology, Priory Street.

CRANFIELD

22nd. I.E.E.—“Lasers & associate devices” by Dr. McFarlane at 7.0 at the College of Aeronautics.

DAGENHAM

16th. I.E.E. Grads.—“Electronic telephone exchanges” by L. R. F. Harris at 6.45 at South-East Essex Technical College.

EDINBURGH

8th. I.E.E. & I.E.R.E.—“Scanning electron microscope and other electron probe instruments” by Prof. C. W. Oatley at 6.0 at Carlton Hotel, North Bridge.

24th. I.E.R.E. & I.E.E.—“Transducers in medical research” by Dr. D. C. Thomas at 6.0 at Carlton Hotel, North Bridge.

GLASGOW

7th. I.E.E. & I.E.R.E.—“Scanning electron microscope and other electron probe instruments” by Prof. C. W. Oatley at 6.0 at the University of Strathclyde, C.1.

KINGSTON, SURREY

2nd. I.E.E. Grads.—“Technical plans for starting colour on BBC-2 by J. Redmond at 7.0 at the College of Technology, Penrhyn Rd.

LEICESTER

9th. Television Soc.—“Steam radio—the birth of broadcasting” by The Hon. Rowland Wynn at 7.15 at Vaughan College, St. Nicholas Street.

LIVERPOOL

14th. I.E.E.—“Variable speed drives using semiconductor adjustable frequency inverters” by D. A. Jones at 6.30 at Electrical Engineering Labs., The University.

16th. I.E.R.E.—“Stereophonic broadcasting” by Dr. G. J. Phillips at 7.0 at the College of Technology, Byrom Street.

21st. I.E.E.—“Lasers” by J. C. North at 6.30 at Electrical Engineering Labs., The University.

LOUGHBOROUGH

15th. I.E.E.—“Field effect devices” by Dr. R. E. Hayes at 6.30 at Edward Herbert Building, University of Technology.

MALVERN

14th. I.E.R.E.—“There is more to colour than wavelength” by R. W. Brocklebank at 7.0 at the Abbey Ballroom.

NEWCASTLE-UPON-TYNE

9th. I.E.R.E.—“Lasers and their applications” by Dr. G. W. Wilson at 6.0 at the Inst. of Mining and Mech. Engrs., Neville Hall, Westgate Road.

OXFORD

8th. I.E.R.E.—“Circuit design using digital computers” by E. Wolfendale at 7.30 at Clarendon Laboratory, Parks Road.

9th. I.E.E.—“Micro-miniaturization” by R. G. Dixon at 7.0 at S.E.B., 37 George Street.

PLYMOUTH

15th. I.E.E. & I.E.R.E.—“Automatic driving of trains” by R. Dell at 7.0 at the College of Technology.

PORTSMOUTH

16th. I.E.E.—“U.K.3 satellite electronics” by W. M. Lovell at 6.30 at the College of Technology, Anglesca Road.

SHEFFIELD

2nd. I.E.E.—“Hybrid computers” by Dr. H. B. Williams at 6.30 at Sheffield Industries Exhibition Centre.

SOUTHAMPTON

8th. I.E.E.—Colloquium on “What’s new in integrated circuits” at 2.30 at the Lanchester Theatre, The University.

23rd. I.E.E.—“Satellite control” by E. G. C. Burt at 6.30 at the Lanchester Theatre, The University.

SWINDON

9th. I.E.R.E. & I.E.E.—“Ballistic missile early warning system” by B. S. Batt at 7.0 at the College.

WHITBY

7th. I.E.E.—“Semiconductor integrated circuits” by C. S. den Brinker at 7.0 at Botham’s Cafe, Skinner Street.

NEW PRODUCTS

equipment systems components



NUMERICAL CONTROL

FEEDBACK Limited who produce both servo and computer logic teaching equipment have now married both systems together to give an assembly which illustrates the principles of numerical control and can be constructed and understood by an average student during a single laboratory period. Described as a logic tutor the Feedback Logikit Primer LK.255 with the additional plug-in elements and the Digital Encoder SE.254 costs £200, and may be expanded to accommodate larger experimental developments for very little extra cost. Both d.c. and carrier servo systems can be controlled from the logic and, for authorities wishing to teach servo plus logic, under £450 will equip a laboratory unit. In the simplest form, a position control system can be constructed which responds to a numerical demand in the form of a 3-bit binary number set on three switches. A digital encoder is coupled to the output shaft, and this produces a Gray code to identify any of eight equal angular segments within a 360° rotation. The logic circuits made up by the constructor from simple plug-in elements convert the Gray code to natural binary and then compare the input demand with the encoder output. The differences (greater or less) in binary form are converted into an error signal suitable for the servo. This drives the encoder in the correct direc-

tion to reduce the differences to zero. Input demand, and the natural binary response are monitored continuously by a bank of indicator lamps. The student is thereby in no doubt of the accuracy and speed of the system response. The encoder SE.254, which is covered by a clear Perspex case, carries a mimic replica of the encoding disc, on the front. Its lamps and phototransistors are energized from the logic tutor by means of a long plug-in cable. The encoder can be used with any servo or other suitable mechanism which will respond to the error signal. It is specifically supplied with attachments to couple it directly to any Feedback servo system. Although the experiment illustrated in the photograph involves only a 3-bit number, the encoder will produce up to five bits (32) as well as generating continuous impulses for speed control experiments.

The experimental scope of the Logikit primer includes simple functions of several variables, theorem application, binary addition and subtraction, cyclic binary numbers, a parity chain, decimal to binary-decimal translation, the use of NOR and NAND logic elements for basic operations, binary comparisons, and others, all of which are included in the handbook. Feedback Ltd., Crowborough, Sussex.

WW 301 for further details

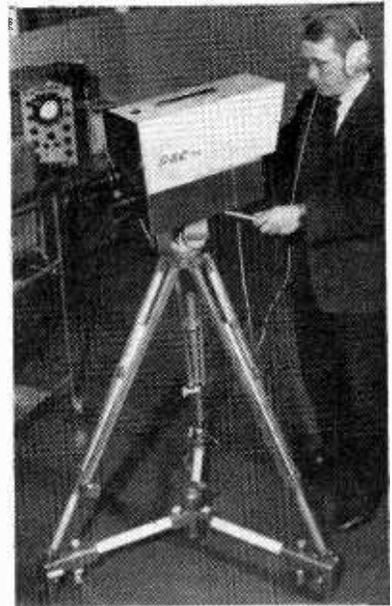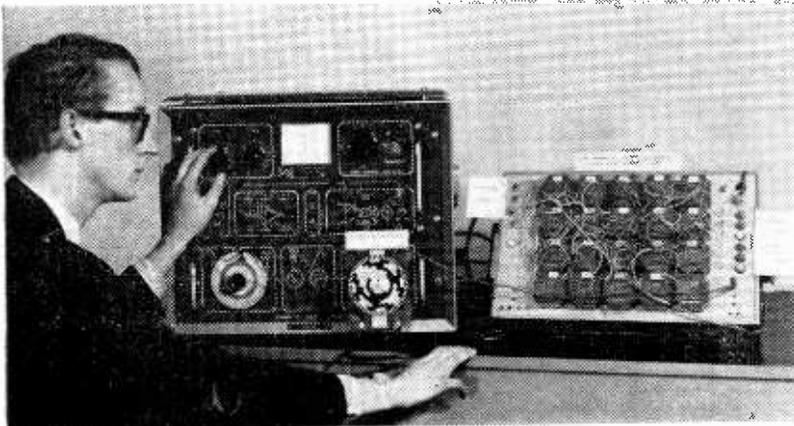

Television Studio Camera

A MAINS operated transistor TV studio camera, has been developed by G.E.C. Electronics' Communications Group, of Spon Street, Coventry. Known as the type VCT 2/S, it incorporates a 7 in electronic viewfinder which is easily removed for use separately as a picture monitor. The camera and viewfinder have separate power circuits. The camera can be supplied with a scanning/field standard of either 625/50 or 525/60 and transmits over a bandwidth of 10 Mc/s.


A vidicon tube is used in the camera, and a four-lens turret, which will take "C" mount or broadcast mount lenses, is fitted. A control knob at the side of the camera enables optical focus to be adjusted, or a remote control system can be fitted. The camera has a built-in sync pulse generator and all the principal circuits are contained in replaceable printed circuit modules, thus simplifying maintenance. To minimize the length of the signal cable from the vidicon tube, the video head amplifier module is mounted directly above the vidicon focus coil. A high signal/noise ratio of 36dB peak-to-peak with a 0.2 μA signal is obtained from the video head amplifier. The "target voltage," "beam current," "electrical focus" and "black level" camera controls are normally preset but can be linked to a camera terminal unit to permit adjustments to be carried out remotely. The viewfinder's electronic circuits are also contained in printed circuit modules to facilitate easy servicing.

WW 302 for further details

Delay Relays

TIME delays of 3 to 180 seconds can be obtained from series 200 and series 300 time delay relays by Relay Specialties Inc. Style 200 (9-pin miniature socket) and Style 300 (8-pin octal socket) are hermetically sealed in glass, flushed and gas filled, and both series are constructed to assure either on or off operation with single-pole, double-throw contacts. All relay components including ceramics, wire, glass, steel and silver contacts are inorganic, and free from moisture. Standard tolerances on time delays are $\pm 25\%$ with closer tolerances available. These relays, thermally operated by a separate heating circuit, have standard heater voltages of 6.3, 26.5 and 115 V a.c. or d.c. Contact ratings are 115 V a.c. 3A resistive, or 28 V d.c. 3A resistive. Operating temperature range is 65° to 100°C , and a minimum life of 100,000 operations is claimed for average operating conditions. Relay Specialties, 3 Godwin Avenue, P.O. Box 223, Fair Lawn, N.J., U.S.A.

WW 303 for further details

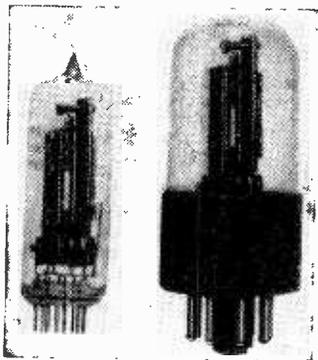

Dual Transistor



THE 2C444, a silicon planar dual transistor is available from SGS-Fairchild Ltd., Stonefield Way, Ruislip, Middlesex. This is a six terminal device giving low drift performance in d.c. amplifiers, and can be used in industrial applications, power supplies, video and cascade amplifiers. The 2C444 replaces two C444 transistors, and it is stated that this is the first industrial transistor to have guaranteed h_{FE} and V_{BE} matching. Planar construction, and low leakage, offer a range of guaranteed hybrid parameters that allows flexibility in designing equipment. Maximum drift $30 \mu\text{V}/^\circ\text{C}$, f_T is typically 350 Mc/s, and h_{FE} ratio 0.7 minimum.

WW 304 for further details

CRYSTAL FILTERS

TWO filter units, the PF1 and PF2, by Elliott Electronics, 3 Sandgate Avenue, Tilehurst, Reading, Berks, have been designed to improve the selectivity of existing receivers with i.f.s of 455 to 470 kc/s. They are also intended for incorporating into new receiver assemblies and single-sideband generators. The PF1 is available in two versions, PF1/RX with a symmetrical passband for receiver applications and PFL/SB with an asymmetrical passband, and sharp cut-off on the l.f. or h.f. side for sideband generation. Input and output transformers are tapped to match into valve or transistor circuits with impedances of 1 to $2\text{k}\Omega$, 10 to $40\text{k}\Omega$ or $100\text{k}\Omega$ upwards. The centre frequency can be 457, 465 or 470 kc/s $\pm 1\text{kc/s}$. Price £4 1s. The PF2 is a simplified filter in which there are no matching transformers and it has been designed to couple directly (without centre tapings) to standard i.f. transformers which are tuned to the centre frequency of the filter. The centre frequency can be 459, 467 or 472 kc/s $\pm 1\text{kc/s}$. The price is £3 2s.

WW 305 for further details

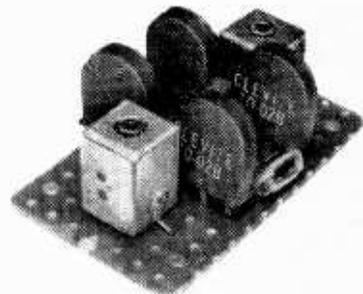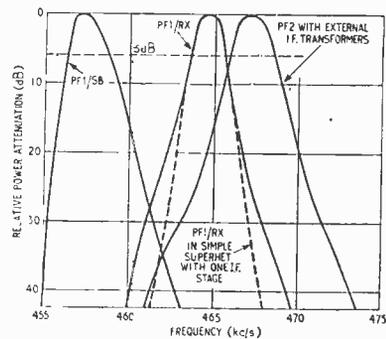

Reversible Counter

THE Hewlett Packard reversible electronic counter 5280A counts at rates up to 2 Mc/s, reverses in 250 ns and has a reverse counting rate of 1 Mc/s. The instrument is intended for the precise control of automatic processes, where the counter's ability to operate in a temperature range from 0° to 50°C will also be useful. With its accompanying 5285A universal plug-in unit it will count either of two input channels A or B, or count A upwards or downwards, depending on the polarity chosen for B, at the 2 Mc/s rate. It will count A+B and A-B, at rates up to 1 Mc/s. This last-mentioned mode has special value with laser interferometers and other kinds of transducers, to make precise measurements of length, or in X-Y positioning. Model 5280A will maintain accurate count, even if simultaneous signals should arrive at A and B channels in the A+B or A-B modes; an anti-coincidence circuit is built in. This instrument will perform tasks that include reading pulses in remote control or telemetering systems, comparing frequencies, and


measuring length, thickness, angular displacement, flow rate, liquid level and weight (with appropriate transducers). The controls include a polarity switch to reverse input signal direction-sensing and trigger level settings with ± 100 volt range. Readout is 6 digits in-line with \pm sign; 7th and 8th digits are optional, with no decrease in maximum counting or reversing rate. Overflow is indicated by a front panel neon light. The inputs present 1 megohm in parallel with 80 pF to the external circuit. Sensitivity is 100 millivolts r.m.s. or 1 volt pulse of $0.2 \mu\text{s}$ minimum width. Either a.c. or d.c. coupling may be selected. For recording or to control other equipment, Model 5280A has four-line binary coded decimal outputs as standard equipment. Model 5280A is priced at £558. The Model 5285A universal input plug-in unit is £172. Hewlett Packard Ltd., Slough, Bucks.

WW 306 for further details



THYRISTOR GATE SENSITIVITY METER

A GATE sensitivity meter is now available from Caltronics Limited of Hunting Gate, Hitchin, Herts. This thyristor gate sensitivity meter provides accurate and rapid measurement of the gate current-to-fire for a wide variety of thyristors. A Zener diode provides a stabilized anode-to-cathode voltage of 6 volts to the thyristor under test. The gating characteristics of the device under test are measured by applying half-wave rectified 50-60 c/s pulses between the gate lead and cathode of the device. A trigger network in the anode supply lead senses the turn-on point of the thyristor and energizes an electronic switch that removes the gating signal. A peak reading voltmeter circuit is utilized to give a direct indication of

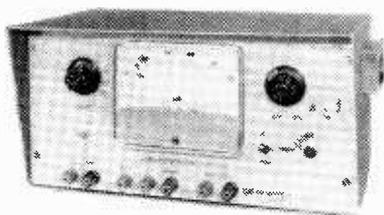


the current or voltage level at which the thyristor fires. The gate current-to-fire reading is obtained by driving the gate circuit through a set of precision resistors which form an adjustable 10-step current source. The gate voltage-to-fire reading is obtained by driving the gate circuit from an adjustable 3-step voltage source. Calibration potentiometers allow the sensitivity meter to be calibrated on both current and voltage. Terminals are provided for parallel remote operation of the instrument. Remote indication of the meter reading may be obtained from a pair of panel terminals which provide a 1 volt signal for full scale indication on the front panel meter. The full scale gate current ranges start at 0.010 mA, rising to 300 mA. The gate current accuracy is $\pm 3\%$ of full scale, and the full scale gate voltage ranges are 1, 3 and 10 volts with a gate voltage accuracy of $\pm 5\%$ of full scale. The analogue output is 0 to 1 V d.c. into a 1 M Ω load. The input power requirements are 220-240 V, 50-60 c/s single phase. The price is £195.

WW 307 for further details

Recording Tape Tester

TAPE testing assemblies which will test the full width of magnetic tape for "drop out" and other defects have been developed by Gresham Lion Electronics. Already available to tape manufacturers, it is now available to users of tape. A wide choice of tracking arrangements is offered, and a version for computer work provides a full width record head for $\frac{1}{2}$ in tape followed by a dual replay head stack with 7 and 9 tracks (type P.S. 79). Top or bottom edge tape guidance is provided by spring loaded ceramic guides, and head blocks are protected by an enclosed cover. Electrical and mechanical specifications can be drawn up to meet particular applications. The specification of one assembly—the seven and nine track replay head assembly for $\frac{1}{2}$ in tape—is as follows: the record head has a track width of 0.505 ± 0.001 in., a gap length of 0.0005 in (nominal). The resistance is 25 Ω , inductance 7 mH,

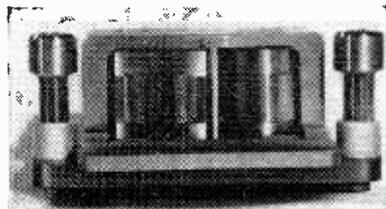

and saturation current 33 mA p-p. The replay head with 7 tracks has a track width of 0.030 ± 0.001 in (9 tracks 0.040 ± 0.001 in) and a gap length of 0.00025 in (9 track 0.00025 in); the resistance is 11.4 Ω (9 tracks 12.5 Ω) and the inductance is 5.6 mH (9 tracks 5.3 mH). Also being developed is a nine track assembly (T.S. 45) which will provide total surface checking of half an inch, high density tape (9 track, 3,200 flux reversals per inch). Gresham Lion Electronics Ltd., Lion Works, Hanworth Trading Estate, Feltham, Middx.


WW 308 for further details

Inductive Transducer

THE P/12/150 non-contact subminiature inductive transducer is 0.1 in diameter and 0.15 in long. Designed to be fully compatible with the range of Associated Engineering electronic units for measuring displacement and vibration, it can be used in temperatures from ambient up to 150°C, and in acceleration fields up to 2000g. It has a working range of 0.005 in, a resolution of 10 μ in and a frequency response from d.c. up to 10 kc/s, with extension to 60 kc/s for special applications. Asso-

Distress Beacon

BASED on the SARBE range of military beacons, the compact beacon BE355 is manufactured by Burndept Electronics Ltd., Erith, Kent. It will be of special value to yachtsmen and to business/private aircraft flying over the sea, or thinly populated areas. It will transmit on the v.h.f./u.h.f. distress frequencies 121.5 and 234 Mc/s. Power output is 100 mW mean and 200 mW peak. It will operate for 24 hours over the temperature range 0°C to 55°C with a 13.4 V mercury battery, which is butt

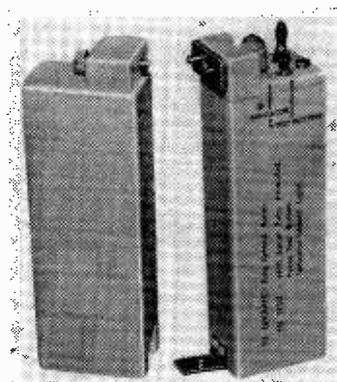



mounted to the radio. A larger battery is available for 48 hours transmission. Both beacon and battery are encased in cans of drawn aluminium and they weigh 25 ounces complete. A sealed retractable telescopic aerial is also contained within the beacon housing when not in use. A function check is carried out by button and indicator lamp. When the beacon is required, extending the aerial initiates the transmission of a wobbled signal two or three times per second. When not in use the BE355 is $5\frac{1}{4}$ in high, $3\frac{1}{2}$ in wide and $1\frac{1}{4}$ in deep. The price is expected to be about £33 to £40.

WW 309 for further details

ciated Engineering Ltd., Group Research and Development, Cawston, Nr. Rugby, Warwickshire.

WW 310 for further details

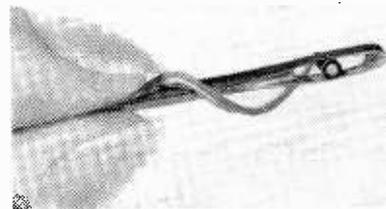

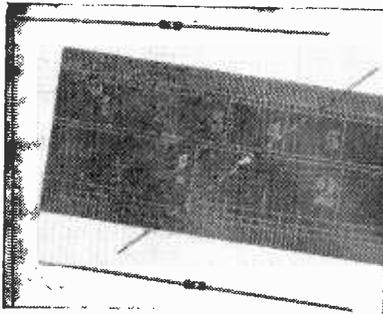

SUBMINIATURE RESISTORS

ERG Industrial Corporation has produced a range of subminiature precision metal film resistors with dimensions from 0.145 in x 0.045 in upwards. Style RE-0-125 (illustrated) is rated for $\frac{1}{8}$ W at 100°C. Temperature coefficients are from $\pm 0.0025\%/^{\circ}\text{C}$ upwards and initial resistance tolerances of $\pm 0.1\%$ are available. The operating temperature range is -55°C to $+165^{\circ}\text{C}$, and values between 2 Ω and 2 M Ω can be specified. Other styles with ratings from 1/20 W up to $\frac{1}{2}$ W at 100°C are available. Erg Industrial Corporation Ltd., Luton Road, Dunstable, Beds.

WW 311 for further details

A.F./R.F. Test Set

MODEL A 220 a.f./r.f. test set is an instrument manufactured by Amalgamated Wireless (Australasia) Ltd., and marketed in the U.K. by Livingston Laboratories. This receiver functions as a variable frequency generator, wide-band receiver, high impedance voltmeter, and modulation meter and it can be mains or battery powered for station or field operation. The generator provides frequencies from 100 c/s to 650 kc/s with a maximum output level of +13dBm at switch selected output impedances from 75 Ω to 1.2 k Ω . The generator output can be amplitude modulated up to 80% by an internal 820 c/s oscillator, or from an external source between 200 c/s and 3.4 kc/s. The wideband receiver function measures signal levels down to -80dBm over the frequency range 50 c/s to 250 kc/s with selectable balanced input impedances of 75, 150, 600, and 1,200 ohms. Provision is made for monitoring by headphones or a.c. recorder, measuring distortion, intermodulation products, and filter band-pass characteristics. The generator will withstand a short circuit across the output terminals for up to one hour without damaging the instrument. Instrument Division, Livingston Laboratories Ltd., Livingston House, Greycaine Road, North Watford, Herts.


WW 312 for further details

Film Resistor Networks

ENCAPSULATED cermet resistance networks made by Nexus Research Laboratory Inc. (U.S.A.) are available in a wide range of values, with standard tolerances of 1% and 0.5% and specially ordered resistance tolerances of 0.25% and 0.1%. They are intended particularly for users of operational amplifiers. Claimed advantages of these networks are small size, inherent reliability, and close thermal tracking of similar resistors fired on a common substrate. These networks are available to order, in special configurations including binary and b.c.d. related resistance ratios for use in digital/analogue interface converters. The thermal tracking (ratio between units on a common substrate) is ± 20 p.p.m./ $^{\circ}\text{C}$. Power dissipation

per substrate is 0.5 W. From Livingston Components Ltd., Livingston House, Greycaine Road, North Watford, Herts.

WW 313 for further details

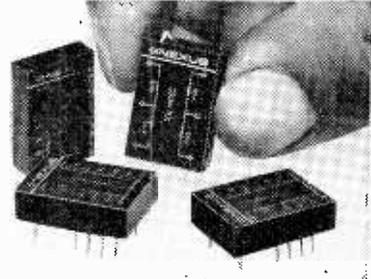

A.C.-D.C. Converter

IN modern data processing systems, a frequent requirement is the conversion of a.c. data signals to d.c. signals that will drive suitable indicating devices and recording equipment. The TP-663 a.c. to d.c. converter made in the U.S.A. by Technical Products Company, is such an instrument complete with self-contained regulated power supplies. Operator controls are not required, since the a.c. input voltage is converted directly to an average d.c. output. This instrument may be equipped with from one to eight channels. Two connectors are provided on the rear of the chassis for each channel. The two detectors (used in the conversion process) that are available with the converter are TP-663A and TP-663B. The TP-663A

provides a 70 dB dynamic range over a frequency range from 5 c/s to 20 kc/s, and a 60 dB dynamic range over the frequency range 4 c/s to 40 kc/s. The RP-663B provides a 70 dB dynamic range over the frequencies 4 c/s to 40 kc/s and 60 dB from 2 c/s to 200 kc/s. The TP-663A provides a response time of 0.5 s for 63% of final reading, while the TP-663B normally supplied with damping has a response time that is 0.2 s for 63% of the final reading. There is the option of faster response time with less damping. Marketed in the U.K. by Environmental Equipments Ltd., Denton Road, Wokingham, Berks.


WW 314 for further details

WIRING BOARDS

PRECISION printed-circuit boards known as ISEP-Veroboards are being made in eight sizes to fit the various sizes of 19 in ISEP sub-racks. Available from Electronic Services, S.T.C., Edinburgh Way, Harlow, Essex, the boards are supplied plain, or clad with narrow copper strips that connect entire rows of holes together horizontally to simplify component connection. Insulation between strips is at least 100 M Ω . Strips can be interlinked or severed between holes to provide many variations of component interconnections. Boards are protected by a flux preservative, and are suitable for cutting out, and punching at room temperature. Claimed advantages of ISEP-Veroboards include ease of access to components, and ease of adaptability to suit changing requirements. Specially designed terminal pins

to fit the board holes (which are spaced out on a 0.1 in matrix) are available, as well as a tool for inserting pins at the rate of 1,000 an hour, and a cutter for making breaks in the copper strip.


WW 315 for further details

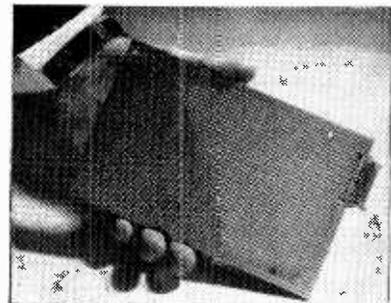

Vibration Monitor

ALTHOUGH primarily designed to measure vibration levels at the engine bearings of jet airliners, the Vibration Monitor developed by the Plessey Dynamics Group will find many applications in marine and other industrial fields, where vibration can lead to fatigue of basic materials, or where vibration levels are excessive and therefore unacceptable for reasons of safety, reliability or accuracy. The equipment consists of two units, a display unit containing a bank of up to 12 vertical scale indicating meters, and a remotely located amplifier unit containing an amplifier for each transducer channel. The

amplifiers, completely interchangeable and identical with each other, are of the integral subminiature type housed in a single semiconductor can. The voltage gain is 100dB up to 1 Mc/s, and response is flat to 2dB over the range 80 c/s to 200 c/s, falling to -23dB at 25 c/s to meet specified requirements. The gain of each amplifier can be varied by means of a preset adjustment. Maximum operating temperature rating is 75°C. The equipment is provided with a built-in self-checking function: a two position switch spring-loaded to the "normal" position, tests all channels simultaneously when held in the "test" position. Normal "no faults" operating gives a mid-scale reading on the indicator, whereas a short-circuited transducer gives no reading and an open circuit a full scale reading. Transducers, not included in the equipment, should be of a type conforming to ARINC 554 characteristics. Plessey Electrical Equipment Division, Eastern Avenue, Romford, Essex.

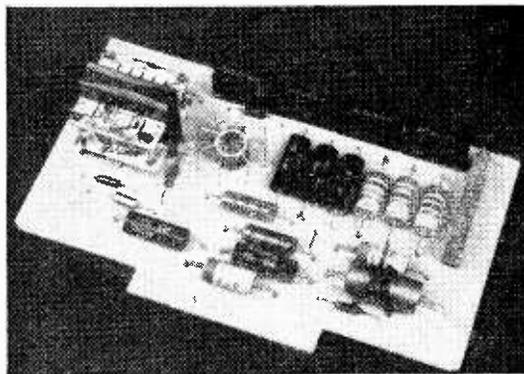


WW 316 for further details

Thin-Film Monitor

A NEW film thickness monitor from Genevac Limited, Pioneer Mill, Radcliffe, Manchester, is designed for measuring the total thickness and also the rate of deposition of vacuum-deposited thin films. This is achieved by collecting a portion of the evaporant stream on a quartz crystal mounted in a suitable position within the evaporator. Using the principle of the linear change of resonant frequency with increasing mass of the monitor crystal, the device indicates the change as a displayed d.c. voltage and likewise indicates the rate of change of this voltage. Feedback can be taken from the instrument and used to control the heat input to an evaporation source and hence the rate of deposition; also the end point

of the evaporation can be preset by using the instrument to operate an electro-mechanical shutter. The instrument can be used to control both laboratory and production depositions with a high degree of repeatability. The total mass deposited is indicated over four ranges of 1, 5, 10, 50 kc/s full-scale deflection. Provision is made for backing off to zero between consecutive depositions; the crystal requires cleaning at intervals of approximately 60 kc/s shift. The control unit is housed in two cases both 9in wide, 6in high and 6in deep; one case contains all the necessary power supplies and displays the mass deposited; the second case displays the rate of deposition. The electronic circuitry of the oscillator, which is in a separate unit, is placed close to the evaporator and connected to the monitor's quartz crystal through a coaxial vacuum seal.

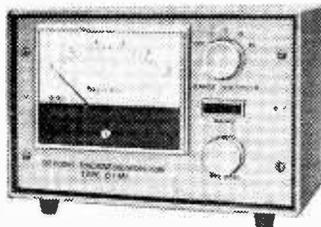

WW 317 for further details

INSTRUMENT CASE

MODERN style instrument cases are being manufactured by Vero Electronics Ltd., of Chandler's Ford, Hampshire. Plastic side frames incorporating handles are injection moulded in dove grey "Cyclocac" polymer, which, with four substantial aluminium extrusions offer a strong, rigid frame. The cover panels are aluminium, coated with p.v.c. (charcoal grey or green). Parts can be packed flat in kit form, and assembly takes about 15 minutes using a screwdriver. One size only is available at the moment to accommodate a unit 19 in wide x 7 in high, and 15 in deep.

WW 318 for further details


Crystal Oscillator

PLUG-IN crystal oscillators intended as medium stability frequency sources, are now available from the Marconi Co. Ltd. Each of the oscillators in this range possess a glass encapsulated quartz crystal, with the buffer output stage (solid-state) circuitry accommodated around it. Housed in aluminium tubes 1.125 in in diameter and mounted on international octal valve bases, type F3170 units cover the frequency range 1 to 115 kc/s. The seated height will vary between 3.125 in to 5 in, depending on the frequency of the unit. Type F 3171 units, mounted on B7G valve bases, cover the frequency range 115 kc/s to 100 Mc/s, and they can be housed in standard F3006 crystal ovens for enhanced frequency stability. With a seated height of 3.125 in, these units are provided with $\frac{1}{4}$ in diameter cylindrical aluminium covers. Frequency stability of both types is better than 1 part in 10^6 within the temperature range -20° to +70° C. The frequency of the units can be trimmed by an external capacitor located between a base pin and earth. The buffer output stage will maintain a

frequency stability of 1 part in 10^6 for a 10% variation in load impedance. The output impedance is $5\text{ k}\Omega \pm 10\%$ with an output of 2V peak to peak. A 6V supply is required. Marconi Co. Ltd., Chelmsford, Essex.



WW 319 for further details

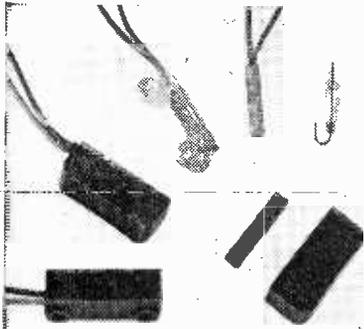

REED SWITCH

MOULDED reed switches of a new design are available from West Hyde Developments Ltd. The glass envelope is shielded by a brass sleeve, which in turn is completely encapsulated in a polypropylene moulding; it is thus claimed that the attendant risks to the normal fragile housing of such reeds are considerably reduced. It is stated that test switches have been working continuously for 5×10^{10} operations, at a rate of 100 operations/s. Applications for this moulded reed switch with hermetically sealed contacts include over and under speed monitors, flow and conveyor monitoring, routing control, counting, press tool protection and guards, position detection, timing, and proximity detectors. The switches will give operations either directly, or through plug-in diode-transistor-logic modules on B9A bases including relay drivers, monostable Schmitt triggers, and AND gates. West Hyde Developments Ltd, 30 High St., Northwood, Middlesex. WW 320 for further details

2-Way CdS/CdSe Cell

THE photoconductive cell PH50 made by Photain Controls Ltd. has an element consisting of a mixture of cadmium sulphide and cadmium selenide, with resistance variations from $2 M\Omega$ in the dark to $3 k\Omega$ at 100 lux. It will operate in the range 6 to 200 V d.c. with a permissible continuous power dissipation of 200 mW. The glass encapsulation allows it to operate over the temperature range $-30^\circ C$ to $+60^\circ C$. Since it is sensitive to both side and end illumination, it can be used in oil burner and flame failure controls, where a standard housing is required for mounting into the blast tube of a burner, whilst at the same time being suitable for end-on mounting on to the front plate of the boiler. Photain Controls Ltd., Randalls Road, Leatherhead, Surrey. WW 321 for further details


WIRELESS WORLD, NOVEMBER 1966




THE HOUSE OF BULGIN
AT YOUR SERVICE

A LARGE RANGE OF MOULDED SWITCHES

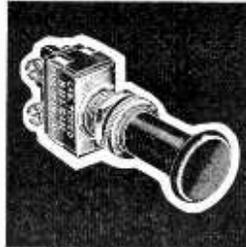Produced on our highly automated plant these switches are inexpensive, but completely reliable, giving a normal minimum life of 25,000 operations.



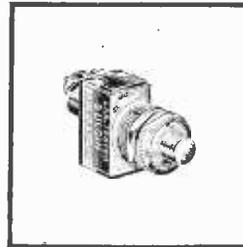
SM.445/TERM S.P.C.O.
Push-Pull Operation.




SM.365 S.P.M.B.
Push Operation.



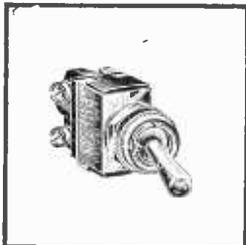
SRM.265 S.P.C.O.
Push Successional Action.



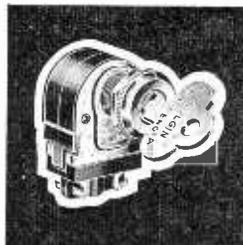
SM.265/TERM/PD S.P.C.O.
Toggle Operation.




SM.320 S.P.C.O.
Key Operation.

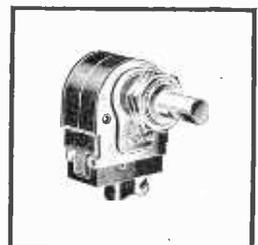


SM.253 S.P.M.B.
Semi-Rotary Operation.

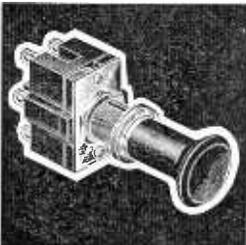


SM.446 S.P.C.O.
Push-Pull Operation.

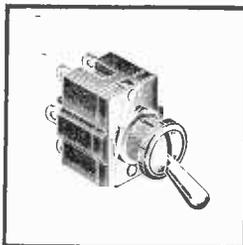

SM.327/PD D.P.C.O.
Toggle Operation.

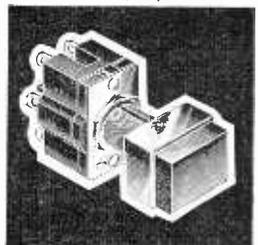

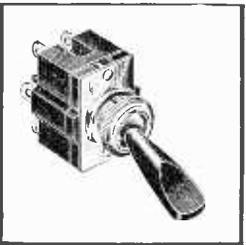
SRM.270/SQ D.P.C.O.
Push Successional Action.



SM.270/DB D.P.C.O.
Toggle Operation.



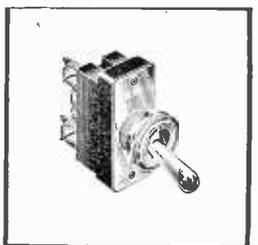S.780 D.P.C.O.
plus Centre OFF
Toggle Operation.



S.790 S.P.C.O.
plus Centre OFF
Toggle Operation.

Send for Technical details quoting this advert.

A. F. BULGIN & CO. LTD.
Bye Pass Rd., Barking, Essex.
Tel: R1Ppleway 5588 (12 lines)

MANUFACTURERS AND SUPPLIERS OF RADIO
AND ELECTRONIC COMPONENTS TO

ADMIRALTY	MINISTRY OF WORKS	B.B.C.
WAR OFFICE	MINISTRY OF AVIATION	G.P.O.
AIR MINISTRY	MINISTRY OF SUPPLY	I.T.A.
HOME OFFICE	RESEARCH ESTABLISHMENTS	N.P.L.
CROWN AGENTS	U.K.A.B.A.	D.S.I.R.

WW-123 FOR FURTHER DETAILS.

587

"Something Nasty in the Woodshed"

I T cannot have escaped your notice that just about everybody has been having a go at the great television controversy and getting all hot under the colour in the process. You will be relieved to learn, I intend to stand aloof from the hurly-burly (largely because nobody would take the slightest notice anyway). Instead, I would like to take the opportunity of reminding my One Regular Reader of the root cause of all this 405-625-colour wrangle.

Knowing that television broadcasting is allegedly dedicated to serving the best interests of the viewer, the otherwise uninformed foreign visitor might reasonably suppose that the ruckus has been brought about by a revolt on the part of the proletariat. But if inflamed mobs are storming Parliament House bearing banners inscribed "We demand the Black & White Minstrels in colour!" or "Give us 200 extra lines!" all I can say is that the newspapers are keeping awfully quiet about it.

Drawing blank in this quarter, our visitor might then turn his attention to our various national Aunt Sallys. The Government, perhaps? Well, certainly the Conservatives gave us some action. They very kindly pledged about £150M of our money to support a third service which the viewers didn't particularly want and most certainly couldn't afford. The Labour Government condoned this project, but in view of the national economic situation have taken the most rigorous steps to ensure that nobody can buy a new receiver to make use of the service. But, as everyone knows, no government has ever been known to act of its own volition, but only when someone is kicking it in the rear, so our hypothetical foreign visitor must look elsewhere for the culprit.

This brings the B.B.C., the I.T.A. and the programme companies under the bright lights for grilling. Here we have some circumstantial evidence, for the B.B.C. is already going ahead with the third service and promising colour, while the I.T.A. is going R G B with rage, envy and frustration. But stay. A moment's thought will produce the paradox that neither they nor the programme contractors really wanted another service or colour any more than elephants want wings. The B.B.C. took it on because it was told to, and because if it hadn't the opposition soon would have. If the roles had been reversed, the situation would have been a mirror image of the present one, in which the I.T.A. has to agitate for parity in the cause of preserving its programme ratings. Similarly, deep down in their cheque-books, the programme contractors and advertisers wish colour TV had never been invented, because it will undoubtedly cost much more but will sell no more soap powder or what have you. But if they don't go into colour they won't sell as much as they do now, so although they don't want it they must have it.

Personally, I don't think the commercial boys need get so het up as all that. It will be a long time before colour sets are in anything but a minority and they could well leave it to the B.B.C. to get the gremlins out before chipping in—after all, this worked on the black-and-white service. But that's a digression. The point to note is that neither the B.B.C., the I.T.A. nor the programme contractors started the agitation.

This leaves only one more suspect, namely the domestic radio industry itself. But what was the motivation?

The answer lies back in the early 1920's when sound broadcasting was born. The boom in domestic receivers and components which followed was completely unexpected. It happened because conditions were exactly right; there was the magic of conjuring voices from thin air; the fact that the cost of a crystal set did not overstrain even a modest pocket, and the circumstance that the home construction of simple receivers could bring a local kudos which was out of all proportion to the skill demanded. The situation was equivalent to the winning of a first dividend on the football pools.


Fair enough. But with the growth of the boom emerged the dangerous philosophy that it, like Tennyson's brook, would go on for ever, or even if it didn't, another first dividend would materialize in its place. The domestic receiver industry became addicted to pulling down its barns and building greater, regardless of the biblical warning concerning such conduct. Came the dawn, when, with overseas markets neglected and saturation point looming at home, the rosy dreams of yesteryear were ousted by nightmares about over-production.

Television was hailed as the saviour of the situation, but first dividends, like lightning, rarely strike twice in the same spot. This time the conditions were not precisely right. The price tag on the television receiver was too high, there was no crystal set equivalent and no home construction on a massive scale. The sales curve took a long time to get off the ground and when it did no vast fortunes were made in the domestic receiver industry. Nevertheless for some years television served to prevent the wolf from shouldering open the doors of many a factory.

But instead of using this period as a breathing space in which to rationalize the size of the industry to an off-peak demand, the receiver manufacturers have constantly attempted suicide, using the weapons of price-cutting and gimmickry. The public, too, has suffered; for example, the high-quality potential of the v.h.f./f.m. sound service has been nullified by cut-to-the-bone circuits and tinny 6in loudspeakers; in the television field, very few have ever seen a 405-line picture as it could be and should be and the accompanying sound reproduction leaves much to be desired.

The present appalling muddle has largely been brought about by the industry's frenzied lobbying to sustain an artificial level of demand. The u.h.f. television service has boomeranged to clonk the manufacturers on the side of the head with a dual-standard design requirement and Nature has very unsportingly refused to modify her laws of electromagnetic wave propagation to suit their desires. As for sales, there is patently no first dividend here even if there had been no credit squeeze. Colour? I don't think anyone is so wildly optimistic as to visualize an avalanche of colour receiver sales in the foreseeable future (and if the Earls Court Radio Show demonstrations were anything to go by, the hand of Providence is in that).

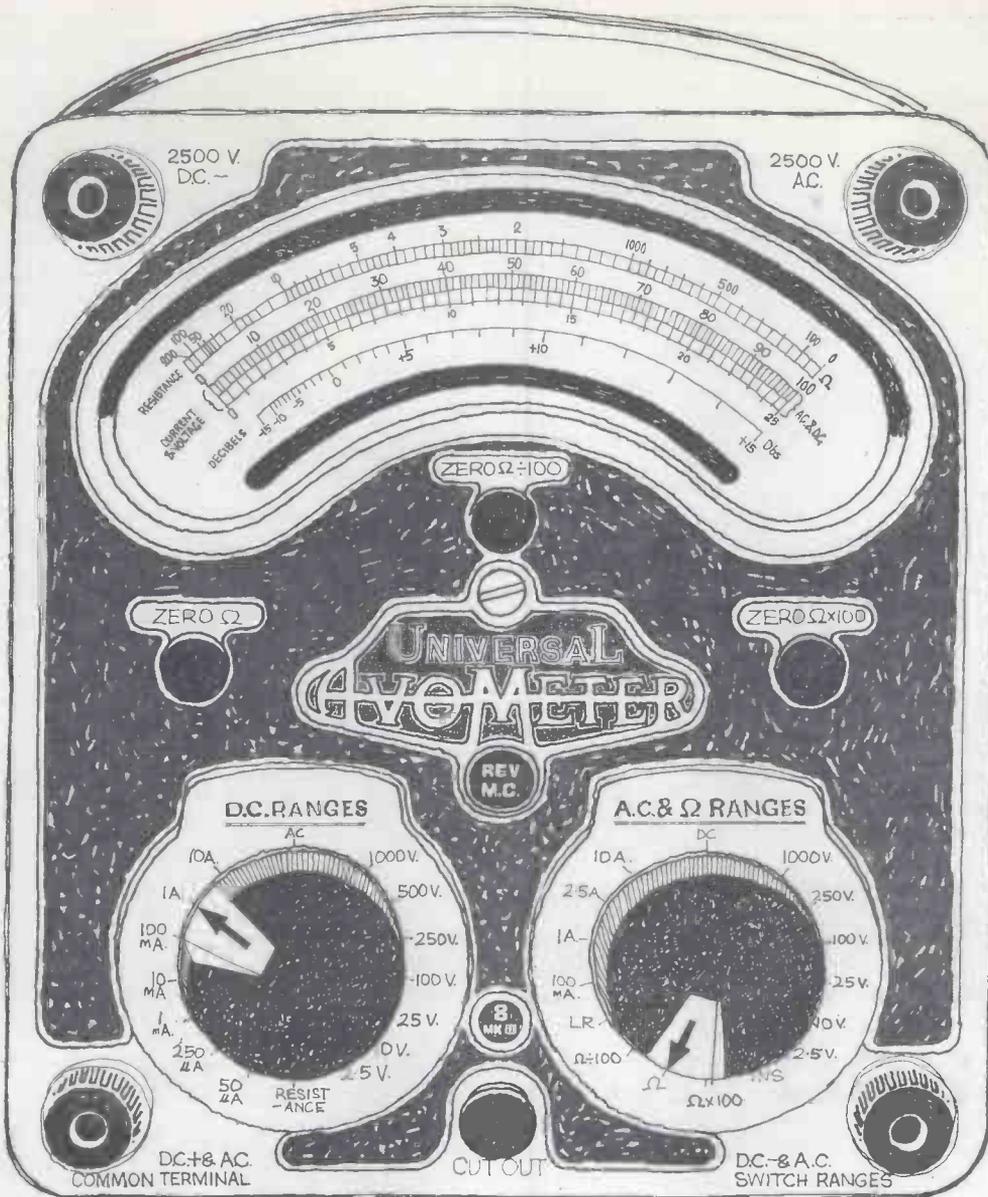So, to end on a cliff-hanger note, we leave the villain of the piece, the receiver industry, still struggling wildly to get out of a pit of his own digging, while the American take-over tiger purrs smilingly down over the rim. Will he perish miserably at the bottom or will he find the foothold of rationalization in the nick of time? If so, will he be devoured by the tiger?



'don't monkey with success'

That's what they told us when we wanted to glamorize the Avometer's looks to match its modern-as-tomorrow internal circuitry and meter movement. 'Avometer', they told us, is the household word for a high-sensitivity, accurate and super-rugged multirange meter. You, they told us, like the way Avometers handle, know you can trust their performance, have a genuine affection for them. OK, you win. Get your Model 8 Mk. III (illustrated) or Model 9 Mk. II (with International scales and symbols) from your local supplier or Avo Ltd., Avocet House, Dover, Kent. Telephone Dover 2626. Telex 96283.



AVΩ MEANS BASIC MEASUREMENTS ALL OVER THE WORLD

WW-003 FOR FURTHER DETAILS.



(Photograph by courtesy of the G.L.C.)

...and in your own armchair



Not so far-fetched with electrostatic loudspeakers and stereo broadcasts.

Properly handled, stereo radio is a vital step towards the closest approach to the original sound.


Watch the Radio Times for that "S".

For details of the QUAD range (including the multiplex decoder for stereo broadcasts) send a postcard to: The Acoustical Manufacturing Co. Ltd., Huntingdon. Tel: Huntingdon 2561/2.

QUAD

for the closest approach to the original sound

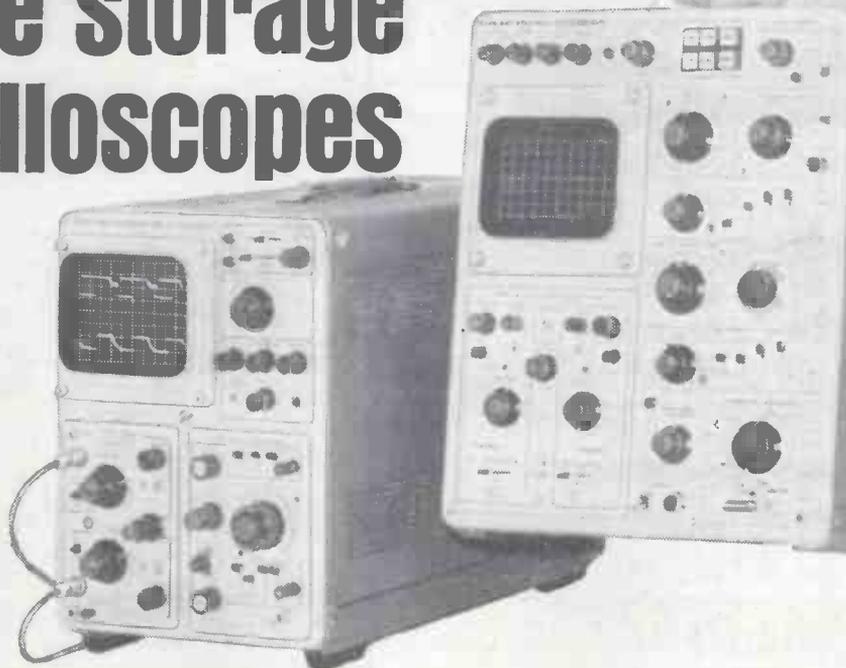2 split-screen bistable storage oscilloscopes



The exclusive Tektronix split-screen, bistable storage feature is now available in two oscilloscopes, the new DC-to-30 MHz Type 549 and the familiar DC-to-15 MHz Type 564.

Both offer the unique capability for simultaneous storage and conventional oscilloscope operation, plus general purpose convenience and plug-in versatility. These features and new, reduced prices for the Type 564/RM564 add up to the kind of value you can expect from Tektronix.

Tektronix Bistable Storage Offers

- Contrast of a stored trace independent of viewing time
 - Brightness of a stored trace independent of viewing time
 - Brightness of a stored trace independent of writing time
- There is much more you need to know. Fill in the Reader Enquiry Card, write, telephone or telex and we will send you complete specifications. The Prices shown are free of duty—subject to Treasury Direction.



Tektronix U.K. Limited

Beaverton House · Station Approach
Harpenden · Herts.
Telephone: Harpenden 61251
Telex: 25559

For Overseas Enquiries:—

EUROPE AND THE MIDDLE EAST: Tektronix Ltd., P.O. Box 36, St. Peter Port, Guernsey, C.I.

CANADA: Tektronix Canada Ltd., Montreal, Toronto & Vancouver.

AUSTRALIA: Tektronix Australia Pty. Ltd., 4-14 Foster Street, Sydney, N.S.W., Australia.

SWITZERLAND: Tektronix International A.G., P.O. Box 57, Zug, Switzerland.

UNITED STATES: Tektronix Inc., P.O. Box 500, Beaverton, Oregon, U.S.A.

STORAGE SCOPE		TYPE 549	TYPE 564	TYPE 564 Mod 08
WRITING SPEED	NORMAL	0.5 cm/μs	25 cm/ms	100 cm/ms
	ENHANCED	>5 cm/μs	>125 cm/ms	500 cm/ms
ERASURE		SPLIT SCREEN FULL SCREEN REMOTE/AUTO	SPLIT SCREEN FULL SCREEN	SPLIT SCREEN FULL SCREEN
PLUG IN TYPES		ACCEPTS LETTER AND 1-SERIES	ACCEPTS 2 AND 3 SERIES TIME BASES AND VERTICALS	
PRICE		£981	£363	£363

WW-005 FOR FURTHER DETAILS.

LITTLE KING MINI-POWER RELAYS

EX STOCK

12 & 24 VDC, 100 & 240 VAC

LITTLE space required

Screw-Fix Quick-Change
1.7 sq. in 2.0 sq. in.

KING size switching

2 KVA 1.5 KVA

10 million operations (proof tested to 27 million).

Power transfer=1 : 1,500.

Current gain=1,400 (coil to all contacts).
LK2C (2 pole screw-fix type)=10 amps./400 volts per pole (1,000 VA max.).



Plug 'em in

or fix 'em

**SCREW-FIX
TYPE
2, 3, & 4
POLE**

**QUICK-
CHANGE
TYPE
2 & 3 POLE**

RELAYS
SHOWN
ACTUAL
SIZE

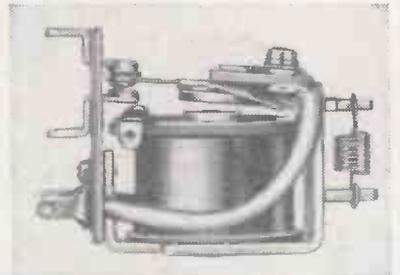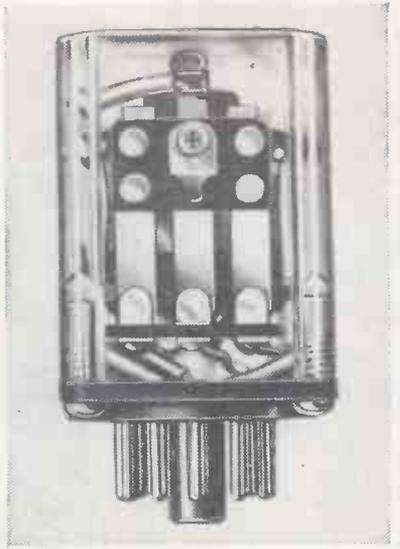

3,000 TYPE RELAYS DELIVERED NOW

EX STOCK



3000 TYPE

With coils from 0.1 ohm to 50,000 ohms. Any combination of contacts, light or heavy duty up to 36 springs (12 change-overs). Sensitivity: Approx. 10-40 milliwatts per contact set (light duty). Reliability: Up to 100 million operations on light duty contacts, one million on heavy duty. Variants available include: Plug-in, London Twin, Industrial 3 (10-30 A), Remanent, Latching, Solid State Timers (1 sec. to 15 mins.), Transistorised Relays.

**A.I.D., A.R.B., AND
ADMIRALTY APPROVED**

600 TYPE

Similar to the 3000 type, but smaller. Contacts for 300 mA to 5.A. Coils: Maximum. 10,000 ohms. Insulation: Up to 650V working.

MINI G.P.

S 1500 PO. Miniature general purpose relay. Miniaturised version of PO 600 type with identical specification. 3/4 x 1 1/4 x 2 1/4 in. (plus tags). Ideal for printed circuit work.

Ex Stock specially manufactured to meet general purpose requirements
Fitted with standard twin silver contacts for 150 v./0.6 A. a.c./0.3 A. d.c.
2 c/o., 4 c/o. and 6 c/o.—500Ω, 1,000Ω and 2,000Ω—6 to 110 v. d.c.

COIL Ω +5%	BOLD FIGS. ARE D.C. VOLTS. ITALICS ARE m/A ± 5%			
	CONTINUOUS RATINGS			
	DPDT	4PDT	6PDT	
500	Pull-in	6 12	8 16	9 18
	Circuit Min.	8 16	11 22	12 24
	Circuit Limit (3W)		40 80	
	Coil Max. (7W)		55 110	
1,000	Pull-in	8 8	12 12	12 12
	Circuit Min.	11 11	16 16	17 17
	Circuit Limit (3W)		55 55	
	Coil Max. (7W)		80 80	
2,000	Pull-in	12 6	16 8	18 9
	Circuit Min.	16 8	22 11	24 12
	Circuit Limit (3W)		80 40	
	Coil Max. (7W)		110 55	

A.D.S. RELAYS LIMITED

97 ST. JOHN ST., LONDON, E.C.1.

Tel.: CLerkenwell 3393. Cables: ADSRELAYS, London, E.C.1.





a mountain of meters for Mahomet

(or just one if that's all you want)

We mean no disrespect, of course. We are merely underlining the fact that a 'mountain of meters' does exist. Here at Anders there are the largest stocks of standard and non-standard meters in the United Kingdom. Our aim is to give off-the-mountain delivery of the greatest variety of meters to the greatest variety of meter users. If you want a meter—or quite a lot of meters—standard or special—you needn't wear out your patience or your sandals. You needn't even come to the mountain. Just pick up the telephone. . . .

□ Meters of all kinds from stock □ Meter calibration/Meter modification/Ancillary equipment □ Custom-designed meter circuitry and components □ Sole U.K. distributors of FRAHM vibrating reed frequency meters and tachometers and of the EKM range of portable voltmeters, ammeters and wattmeters.

ANDERS METER SERVICE

Anders Electronics Ltd • 103 Hampstead Road • London NW1
Telephone Euston 1639 *Ministry of Aviation Approved.*

WW-007 FOR FURTHER DETAIL



versatile!

The Erie 'Weecon' ceramicon range comprises sub-miniature rectangular plate capacitors in 5 sizes from 0.15 in. square to 0.5 in. square, suitable for operation in ambients up to 125°C.

'Weecon' versatility is based on a fully comprehensive capacitance range of 6 pf to 54,000 pf, with a minimum tolerance of $\pm 1\%$, available over 10 standard temperature compensating and 5 standard high permittivity dielectrics: there is the option of 100V or 200V working.

The high volumetric efficiency, performance and flexibility of the 'Weecon'

range makes it particularly suitable for compact systems such as communications, data processing, military equipment, test gear etc.

Erie's 'Weecon' range underlines their versatile and flexible approach to the demands of a fast moving and fast changing electronics industry. Past experience and forward research ensure that Erie are always abreast of current developments as they occur.

Weecon, ceramicon are Registered Trade Marks of Erie Resistor Limited.

Erie take a pride in Performance



Write for catalogue to:

ERIE RESISTOR LIMITED,

Gt. Yarmouth, Norfolk, England.

Telephone: Great Yarmouth 4911

Cables: Resistor Great Yarmouth Telex: 97421

CAPACITOR SELECTION IN LESS TIME AT LESS COST IN LESS SPACE



Developed by Hatfield Instruments Ltd. for use by design engineers for circuit tolerancing and in similar applications, the new Capacitor Decade Box Type 688/A provides a rapid means of capacitor selection over the range 100 pF to 1µF.

It is economical, dependable and occupies minimum bench space even when used in multiples, yet accuracy is better than 5% at any setting.

Write now for further information and we will gladly arrange for a Technical Representative to demonstrate this new unit.

ACTUAL SIZE

5½ x 1¾ x 2¾ in.
(14.1 x 4.1 x 7cm.)

BRIEF SPECIFICATION

- Ranges:**
Four decades giving steps of 100 pF, 1000 pF, 0.01 µF and 0.1 µF.
- Minimum Capacity:**
30 pF with all Switches set to zero.
- Accuracy:**
Better than 5% at any setting.
- Voltage rating:**
250 V d.c. (0.1 µF Decade
100 V d.c.)
- Weight:**
15 oz.—440 g.
- Finish:**
Green hammered enamel.

Miniature Decade Resistance Box



Ideal for rapid evaluation of resistor tolerances in transistor circuits, this unit is exactly the same overall size as the new Decade Capacitor Box (see left) and is accurate and well - screened. Two types are available, both offering four decades: Type 591/A-10 Ω, 100 Ω, 1k Ω and 10k Ω steps: Type 591/B-1 Ω, 10 Ω, 100 Ω and 1k Ω steps. Ask for complete information.

HATFIELD BALUN

HATFIELD INSTRUMENTS LTD., DEPT. W.W., BURREINGTON WAY, PLYMOUTH, DEVON
Telephone: Plymouth 72773/4
Telegrams: Sigjen Plymouth


BSR UA70

now with cueing device


BSR add yet another plus feature to the remarkable UA70 automatic/manual turntable unit by including an integral mechanical cueing device — and without increasing the price. This cueing device allows the pick-up arm to be raised or lowered at any selected point on a record during manual play. Raising the cueing lever lifts the pick-up arm which may then be positioned above the record at the chosen point. The stylus is lowered gently to the groove by returning the lever to the rest position.

Now, more than ever, the UA70, with its wealth of outstanding design features, fine engineering and high performance, provides the selective listener with a turntable unit of quality unsurpassed in this price range.

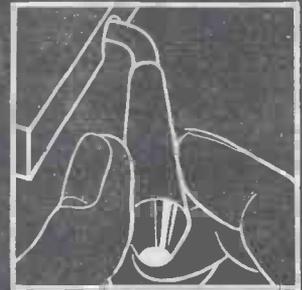£12.18.3 retail, including P.T. without cartridge.



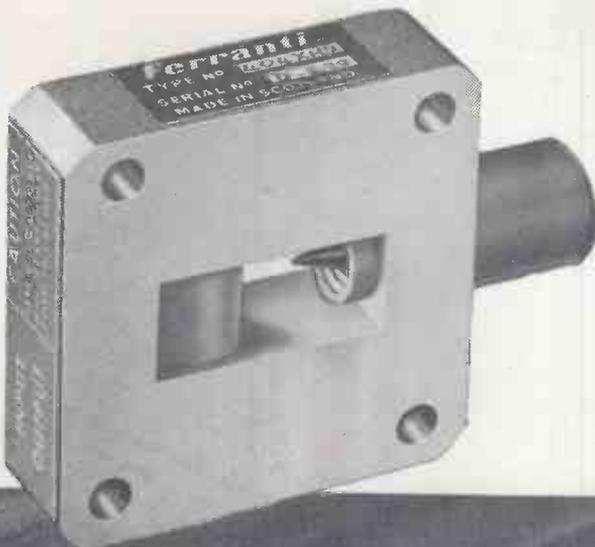THE WORLD'S LARGEST MANUFACTURER OF RECORD CHANGERS AND TAPE DECKS
BSR LIMITED, MONARCH WORKS, OLD HILL, STAFFORDSHIRE



FERRANTI

First into the Future


X-band Series 400XHD (8800 ± 30 Mc/s)
 J-band Series 100 HD1 (13300 ± 50 Mc/s)
 Lightweight—50 gm. ■ 25db Isolation ■ 0.3 db
 Insertion Loss ■ 1.2 V.S.W.R. ■ -26°C to $+50^{\circ}\text{C}$ ■ Rugged ■ Can be supplied for other
 X and J-band frequencies

FERRANTI
 lightweight
 isolators
 for airborne
 doppler
 radar




Write for further details to: FERRANTI LTD., KINGS CROSS ROAD, DUNDEE, SCOTLAND Tel: (ODU2) DUNDEE 87141

WW-011 FOR FURTHER DETAILS

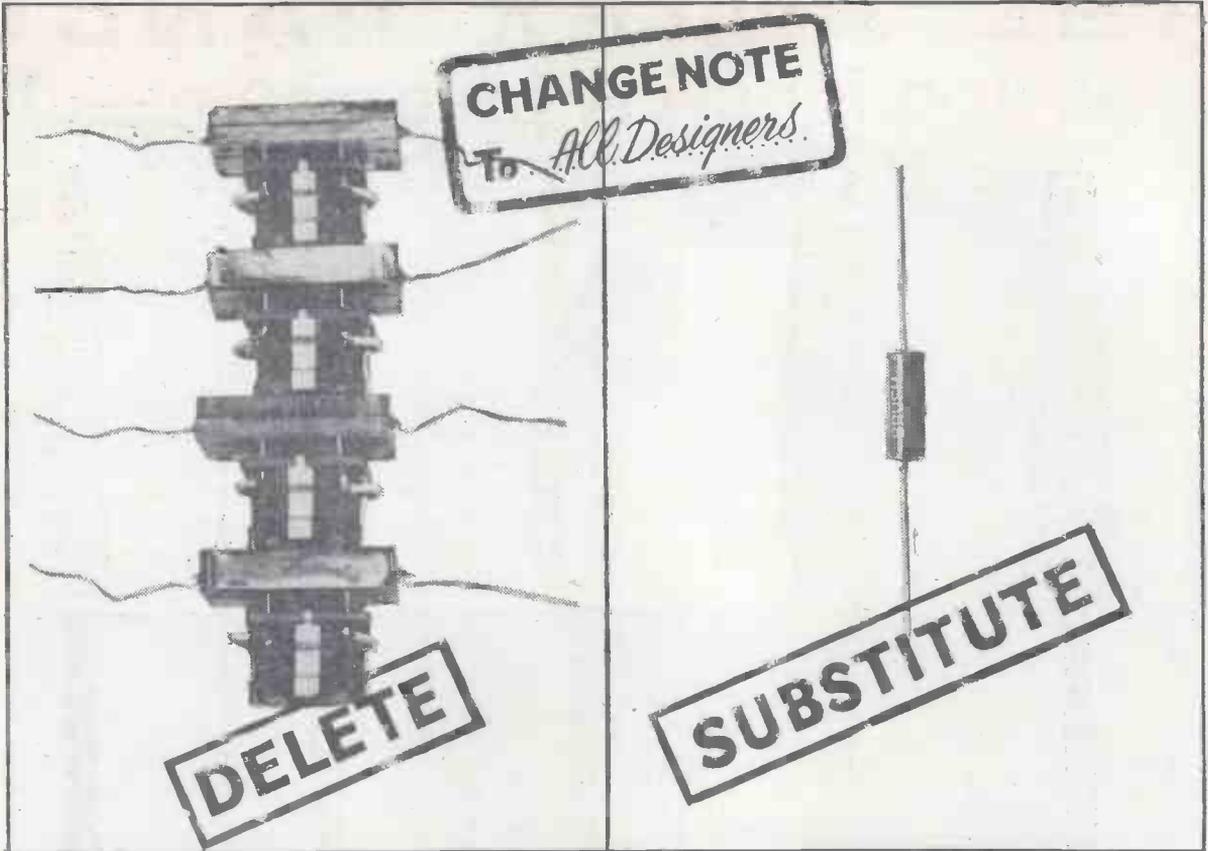


Why designers use Brush Cleviste filters

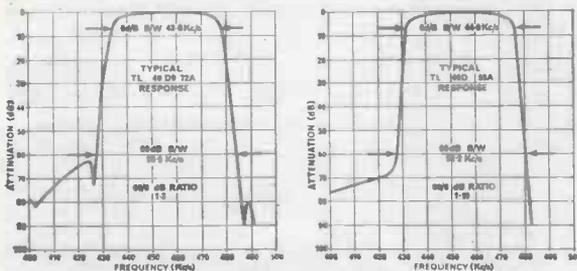
Brush Cleviste Bandpass Filters are NOW made in UK and are NOW down in price!



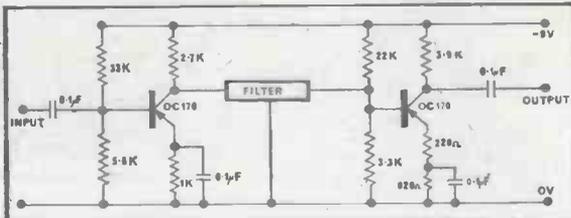Stability for both ranges is better than 0.2% for 5 years and $\pm 0.15\%$ from -20 to 65°C .



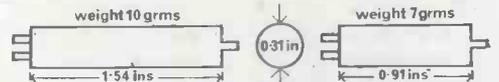Circuit suitable for filters requiring 2.5K terminating impedance is TL 2D5A, TL 4D8A, TL 6D11A, TL 8D14A, TL 10D16A



Abridged Description of the STANDARD range

Abridged Description of the MINIATURE range

Centre Frequency	455, 500 Kc/s	455, 500 Kc/s
	Alternative frequencies in the range 300 – 600 Kc/s are available on request	
Tolerance	$\pm 1 \text{ Kc} \pm 2 \text{ Kc/s}$ according to type	$\pm 2 \text{ Kc/s} \pm 3 \text{ Kc/s}$ according to type
Bandwidths (6dB) available	2 to 55 Kc/s	10 to 40 Kc/s
Terminations	1200 – 2500 Ω , according to type	1000 – 2000 Ω according to type
Insertion Loss	3 to 10dB (max) according to type	4 to 5dB (max) according to type
60dB ratio	1.4 to 2.5 (max) according to type	1.8 to 2 (max) according to type
Operating Temperature range	-40 to $+85^\circ\text{C}$	-40 to $+85^\circ\text{C}$

BC BRUSH CLEVITE COMPANY LIMITED

For full details write for bulletins 66006, 66007, 66009.

THE ANTEX RANGE

-an iron for every precision need!



F
40W. Models for 20 or 24V (mains models available shortly) $\frac{5}{16}$ " bit fitted—alternative bits available. 42/6d




ES
25W. Models for 12, 24, 110, 220 or 240V supply. $\frac{1}{8}$ " bit fitted—3 alternative bits available. 35/-



E
20W. Models for 24, 110, 220 or 240V supply. $\frac{1}{4}$ " bit fitted—8 alternative bits available. 35/-




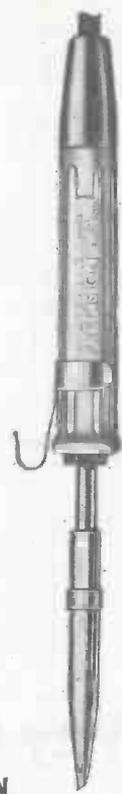
G
18W. Models for 110, 220 or 240V supply. $\frac{3}{32}$ " bit fitted — 3 alternative bits available. 32/6d



CN
15W. Models for 24, 110, 200, 220 or 240V supply. $\frac{3}{32}$ " bit fitted — 17 alternative bits available. 32/6d

HOURS of work reduced to SECONDS with the new ANTEX DE-SOLDERING TOOL

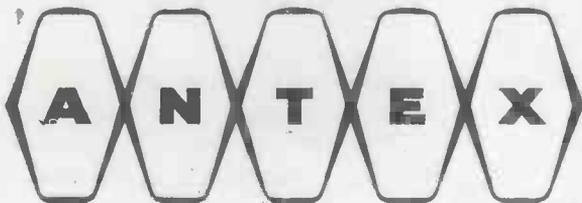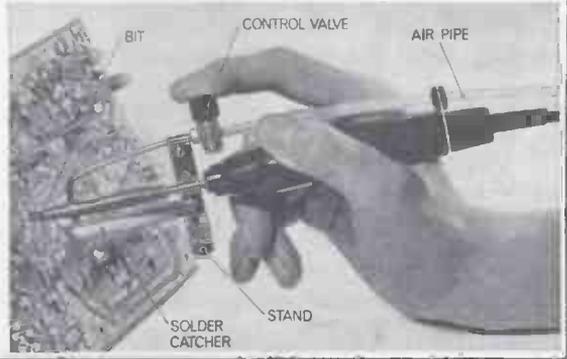Soldered joints can now be easily, speedily and neatly unsoldered. A self-cleaning nozzle, exclusive to the ANTEX de-soldering irons, sucks up molten solder into stainless-steel catcher. Operates by compressed air from airline or standard footpump. Type ESS for 240, 220, 110 or 24 volts. Type GSS for 240, 220 or 110 volts. Price complete with connecting tube, flexible lead and adaptors £4. 4. 0.



ANTEX LTD

Grosvenor House, Croydon,
Surrey, MUNICIPAL 2774

WW-013 FOR FURTHER DETAILS.

INCREASE THE SENSITIVITY OF YOUR OSCILLOSCOPE, VOLTMETER OR COUNTER



The TA401 is similar to the TA601 as illustrated

TA605
ACTUAL
SIZE

SPECIFICATIONS	TYPE TA401	TYPE TA601	TYPE TA605
GAIN	40dB \pm 0.1dB	60dB \pm 0.1dB	20, 30, 40, 50 and 60dB \pm 0.2dB
BANDWIDTH \pm 3dB	1c/s-3Mc/s	3c/s-1.2Mc/s	20-40dB, 1c/s-3Mc/s; 50dB, 2c/s-2Mc/s; 60dB, 4c/s-1.5Mc/s.
BANDWIDTH \pm 0.3dB	4c/s-1Mc/s	10c/s-300kc/s	20-40dB, 4c/s-1Mc/s; 60dB, 10c/s-300kc/s.
INPUT IMPEDANCE	>5M Ω < 40pF from 100c/s to 1Mc/s	>1M Ω < 50pF from 100c/s to 300kc/s	>5M Ω < 40pF from 100c/s to 300kc/s
INPUT NOISE	<15 μ V, zero source <50 μ V, 100k Ω source	<15 μ V, zero source <40 μ V, 100k Ω source	As TA401 and TA601 at 40dB and 60dB
POWER SUPPLY	PP3 battery, life 100 hours		PP9 battery, life 1,000 hours, or A.C. Power Unit
AVAILABLE OUTPUT	1V up to 1Mc/s, 300mV at 3Mc/s, into load of 100k Ω & 50pF		1.5V up to 2Mc/s 1V at 3Mc/s, into 100k Ω and 50pF
OUTPUT IMPEDANCE	100 Ω in series with 6.4 μ F		
SIZE & WEIGHT	3in. x 1 $\frac{3}{4}$ in. x 1 $\frac{1}{4}$ in. 7 oz.		2 $\frac{1}{2}$ in. x 4in. x 5 $\frac{1}{2}$ in. 2 $\frac{1}{2}$ lbs.
PRICE with battery and input lead	£17 0 0	£17 0 0	£27 0 0 (Optional A.C. Power Unit £7 10 0)

LEVELLE


PORTABLE INSTRUMENTS

Fully detailed leaflets are available on our complete range of portable instruments.

LEVELLE ELECTRONICS LTD.

PARK ROAD, HIGH BARNET, HERTS. Telephone: 01-449 5028

WW-014 FOR FURTHER DETAILS.

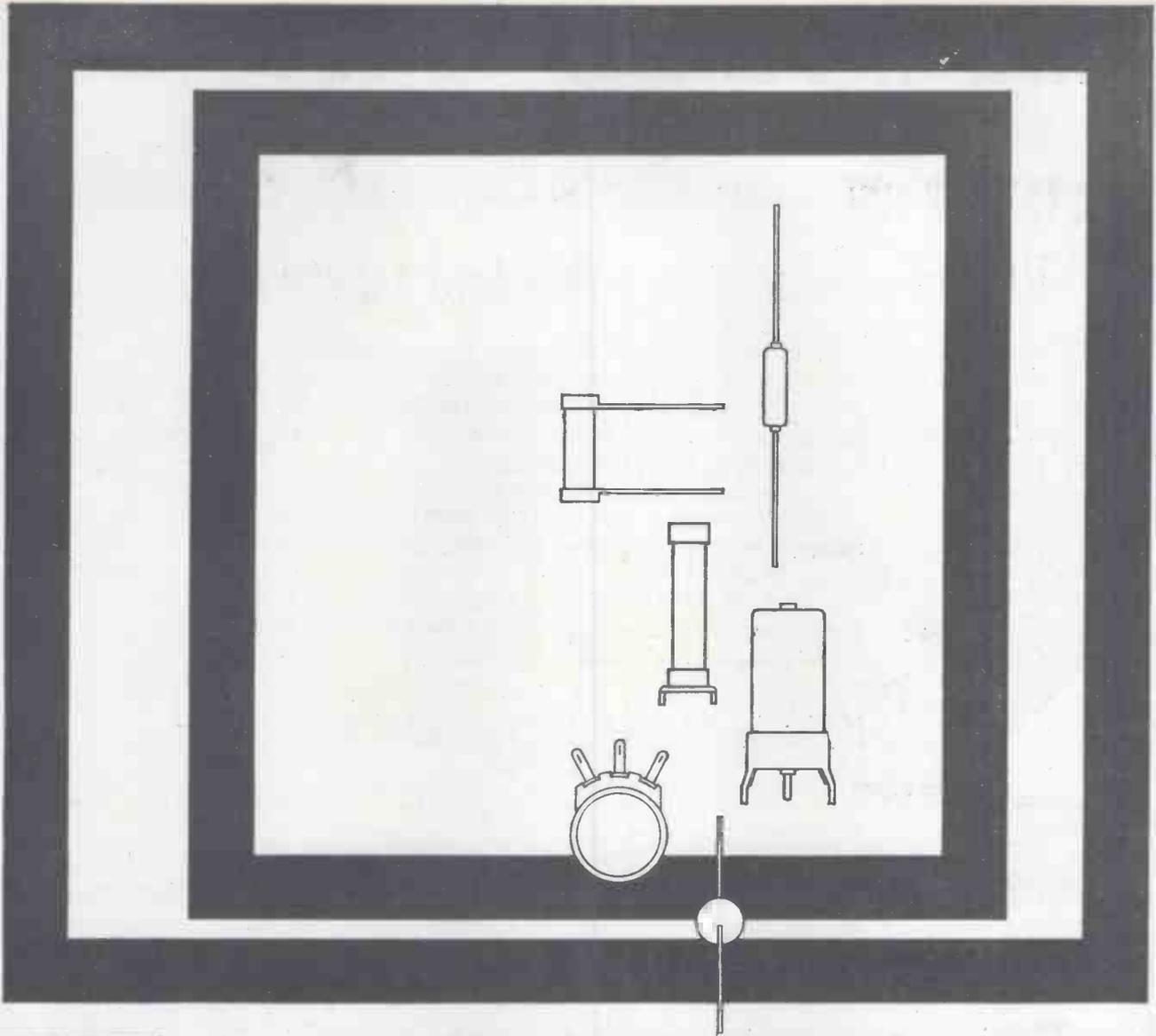
RFT
electronic

combines
progress
and quality

Exporters

HEIM - ELECTRIC

Deutsche Export und
Importgesellschaft mbH
102 Berlin, Liebknechtstrasse 14
German Democratic Republic

The whole is no better than its parts

RFT carbon film resistors are made on automatic production lines. High-performance automatic grinders ensuring tolerances of less than $\pm 2\%$ are an important constituent of modern production installations. This manufacturing accuracy is for the reliability and long service life of RFT resistors just as decisive as the use of high-grade materials and comprehensive tests.

This means that any piece of equipment with RFT components contains important quality factors. They ensure the reputation of the product and thus stimulate demand. Our customers reap the benefit.

The comprehensive RFT range encompasses

Resistors

Carbon film resistors, wire-wound resistors, potentiometers, rheostats.

Capacitors

Plastic capacitors, paper capacitors, metallised paper capacitors, electrolytic capacitors, high-voltage capacitors, interference suppression capacitors.

Sole Representatives:

Globus Commercial Enterprises (Britain) Ltd.

MAPPIN HOUSE, 156 OXFORD STREET, LONDON, W.1

Phone: Langham 0978

Telex: LDN 21853

Cable: Globus London W.1

WW-015 FOR FURTHER DETAILS.


New from Plessey—PR155 MF/HF receiver speaks for itself

Glossy superlatives are out, here are the facts...

- All transistor design for reliability and low power consumption.
- Modular construction using printed circuit cards for easy maintenance.
- Frequency range: 60 kc/s to 30 Mc/s, continuous coverage.
- Ease of operation: Two tuning controls.
- Scale length: 70" per megacycle.
- Resolution: Better than 100 c/s.
- Stability: ± 5 c/s short term, ± 30 c/s long term.
- Reception modes: CW, MCW, DSB, USB, LSB.
- Radiation: Less than $5\mu\text{V}$.
- AGC range: 120 dB—4dB output.
- Signal handling capacity: Better than 1V R.M.S. for low intermodulation.
- RF protection: 6V R.M.S. without damage.

Write for full technical information to:

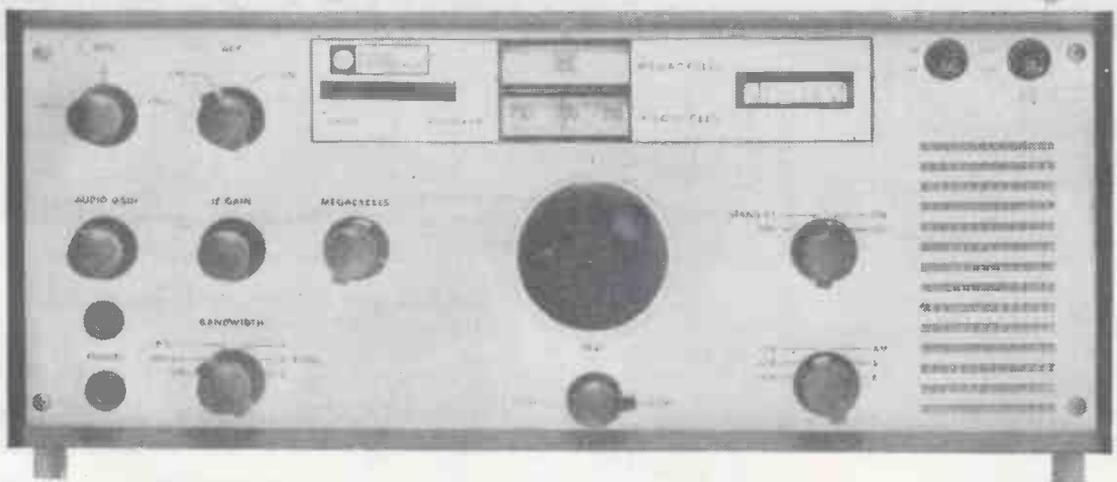The Plessey Company Limited, Radio Systems Division, Ilford, Essex, England
Telephone: Ilford 3040. Telex: 23166



PLESSEY Electronics



VALVES FOR: Radio and T.V. Retailers
T.V. Rental Groups
Trade Service
Radio Relay Companies
Audio Equipment
Electronic Equipment
Instrumentation
Computer Manufacturers
Aircraft, Marine and Radar
Communications Equipment
Public Corporations
Civic Councils
Educational Authorities
Hospitals and Medical Schools
Research and Development
Government Departments
**AIR REGISTRATION BOARD AND
MINISTRY OF AVIATION
APPROVED**

ALWAYS PHONE

Pinnacle

FIRST



01-692 7714

A NEW DIRECT LINE
ROUTED STRAIGHT TO
OUR INDUSTRIAL
ORDER DEPARTMENT

Pinnacle

PINNACLE ELECTRONICS LTD

ACHILLES STREET • NEW CROSS • LONDON S.E.14

Tel: Tideway 7285

WW-017 FOR FURTHER DETAILS.



... inside story

THE LINTON — here you can see exactly what you get for your money when you buy the Linton, compact twin speaker system from Wharfedale. Remember Wharfedale speaker systems are the finest in the world — and the best value for money too!
 For colour folder giving full details of the Linton write to Dept. W11. Selected by the DESIGN CENTRE LONDON.

Frequency range 40 c/s — 20,000 c/s
 Impedance—Suitable for 8 or 15 ohm amplifier
 Power handling capacity 10 watts rms (20 watts peak)
 Size 19" x 10" x 10" Weight 18 lb
 Finished in Zebrano, mahogany, walnut or teak veneers
 £18.12.7. (tax paid)

 RANK WHARFEDALE LIMITED IDLE BRADFORD YORKSHIRE

Tel: 612552/3
 Grams: 'Wharfedel' Bld.
 WW—018 FOR FURTHER DETAILS.



Wireless World

INFORMATION SERVICE FOR PROFESSIONAL READERS

To obtain further details of any of the coded items mentioned in the Editorial or Advertisement pages of this issue, please complete one or more of the attached cards entering the reference number(s). Your enquiries will be passed on to the manufacturers concerned and you can expect to hear from them direct, in due course. Cards posted from abroad require a stamp. These Service Cards are valid for six months from date of publication.

PLEASE USE CAPITAL LETTERS

Pour obtenir tout autre renseignement sur tout article mentionné dans l'Editorial ou dans les pages publicitaires de ce numéro nous vous prions de remplir une ou plusieurs des cartes ci-jointes en inscrivant le numéro ou les numéros de référence. Vos demandes de renseignement seront transmises aux fabricants Intéressés qui, entemps voulu, vous feront parvenir une réponse. Il est nécessaire d'affranchir les cartes postées l'étranger. Ces cartes de service sont valides pendant six mois à partir de la date de publication.

PRIERE D'UTILISER DES CARACTERES D'IMPRIMERIE

Weitere Einzelheiten über irgeendwelche Artikel, die auf redaktionellen oder Anzeigenseiten erschienen erhalten Sie, indem Sie eine oder mehrere der beigefügten Karten ausfüllen und die Kennnummer(n) angeben. Ihre Anfrage wird an den Hersteller weitergeleitet, und Sie werden dann direkt von ihm hören. Karten, die im Ausland aufgegeben werden, müssen frankiert werden. Diese Service-Karten sind für sechs Monate vom Ausgabebetrag gültig.

BITTE IN BLOCKSCHRIFT AUSFÜLLEN

Per ulteriori particolari in merito agli articoli menzionati nel testo o nelle pagine pubblicitarie di questo numero. Vi preghiamo di completare una o più delle schede allegate citando il numero o i numeri di riferimento. La Vostra richiesta sarà inoltrata ai fabbricanti interessati che Vi risponderanno direttamente. Le schede dall'estero devono essere regolarmente affrancate. Questo scontrino di servizio è valido per sei mesi dalla data di pubblicazione.

SI PREGA DI COMPILARE LE SCHEDE
STAMPATELLO

Con objeto de obtener más detalles de cualquiera de los artículos mencionados en las páginas editoriales o de anuncios de este número sírvase rellenar una o más de las unidas tarjetas citando el número o numeros de referencia. Sus consultas serán transmitidas a los fabricantes interesados de quienes tendrán noticias directamente a su debido tiempo. Las tarjetas enviadas desde el extranjero requieren franqueo. Estas tarjetas de servicio son validas durante 6 meses a partir de la fecha de publicación.

SÍRVASE ESCRIBIR CON LETRAS MAYUSCULAS

10-12 Watts - 5 kVA

DRAKE TRANSFORMERS

Mains Transformers

Chokes

Audio Output Transformers

Audio Input Transformers

Saturable Reactors

Coils

Current Transformers

Transistor Transformers

Inverter Transformers

Screened Microphone

Transformers

Wide Band R.F. Transformers



DRAKE TRANSFORMERS LTD., BILLERICAY, ESSEX

Billericay 1155

Integrity in Instrumentation



IN STRICT TRAINING

Essential to the consistent quality of Sifam instruments is the inflexible rule that only fully competent, Sifam-trained staff can take part in the manufacturing process.

This obviously precludes any kind of "sit-in" training for new and transferred employees; therefore Sifam have a pre-production training school staffed by full-time training officers. Although completely separated from the main factory, the school echoes its organisation and facilities—trainee employees are able to carry out practical work in instrument manufacture *as well as* acquire theoretical knowledge from films and lectures.

The result of this rigorous policy over training is that every employee works *consistently* to Sifam's high standards . . . which, in turn, helps to maintain the accuracy and reliability for which Sifam instruments are acclaimed.



SIFAM ELECTRICAL INSTRUMENT COMPANY LIMITED
WOODLAND ROAD TORQUAY DEVON ENGLAND
Telephone: TORQUAY 63822 Telegrams: SIFAM TORQUAY

TIMERS MICRO SWITCHES

IMMEDIATE DESPATCH



S5G

- ★ 1 MILLION OPS. 5 amp. c/o Sub-miniature Micro-switch.
- 2/5 each per 1,000.



VAQ

- ★ 10 amp. c/o PUSH BUTTON. Panel mounting. Buttons in six colours.
- 5/4 each per 500.



C-5

- ★ LOW TORQUE PRECISION ROTARY SWITCH.
- ★ 5 amp. c/o.
- ★ 1/2 million operations.
- 6/3 each per 1,000.



VV-15-1A

- ★ 15/10 amps. c/o.
- ★ 100,000 ops.
- 1/8 each per 1,000.
- Single Throw 1/6 each.



LIMIT SWITCH WL 10 FCA2

- ★ 10 amp. 2 circuit
- ★ CASED FOR USE UNDER ARDUOUS CONDITIONS. MECHANICAL HANDLING, MACHINE TOOLS, LIFT GEAR.
- ROLLER LEVER AS ILLUSTRATED.
- As low as 45/5 each



V-10-1B

- ★ 1 MILLION OPERATIONS.
- ★ 10 amp. c/o.
- ★ COMPARE OUR SPEC. & OUR PRICES WITH OTHER SIMILAR TYPES.
- Screw Terms 2/2 each per 1,000.
- V-10-1A Solder Tags 1/11 each per 1,000



VV-5GW-1A44

- ★ LIGHT FORCE
- ★ 4 gms. Wire actuator.
- ★ Designed for coin-operated mechanisms.
- 4/1 each per 1,000.

U.L. APPROVED (Appr. No. 32667) U.S. MIL. SPEC.
ALWAYS AVAILABLE FROM STOCK.

PROCESS TIMERS



611 T Delay Relay

- ★ 2 secs. to 25 secs. Delay.
- ★ 15 amp. c/o. micro-switch fitted.
- ★ LARGE RANGE OF A.C. & D.C. OPERATIONS.
- From 39/11 each.



SYT MINI-TIMER

- ★ DIAL RANGES 10 secs. to 6 hours.
- ★ Mains operation.
- ★ 5 AMPS. DOUBLE POLE, DOUBLE THROW SWITCHING INCORPORATED.
- Accuracy 1/2%.
- From £9.2.3 each.



STP Sub-Mini Process Timer

- ★ Plug-in Octal base.
- ★ Mains operation.
- ★ Built-in 2 amp. c/o switching.
- ★ 10 secs. to 1/2 hour.
- From £5.1.8 each.



PROXIMITY SWITCH—TL 2 GNA

- ★ FOR BATCHING, CONVEYORS, MACHINE TOOL CONTROL, PACKAGING, SORTING, etc.
- ★ SENSES FERROUS AND NON-FERROUS OBJECTS.
- ★ NEEDS NO MECHANICAL FORCE OR PRESSURE TO OPERATE.
- ★ SOLID STATE SENSING HEAD, plus Power Pack.
- From £6.14.5 each.

FLOATLESS LIQUID LEVEL CONTROLS


- ★ To control or record liquid levels.
- ★ Stainless Electrodes switching minute current to Master unit for:
- ★ Pumps, Motors, Alarms, etc.
- ★ No moving parts.
- Single and multi switching.
- From £4.19.7 each

LATEST DEVELOPMENT PROXIMITY HEAD YL-2GP-A
Mains operated . . . REQUIRES NO POWER PACK WHATSOEVER . . . AVAILABLE DECEMBER
 NORTHERN STOCKISTS AND DISTRIBUTORS: GORDON WILSON (AUTOMATION) LTD. BLACKBURN 59921

(Dept. W.W.7) **OMRON PRECISION CONTROLS**
 313 Edgware Road, London, W.2 **Tel.: Paddington 2370**

INSTRUMENTS FOR INDUSTRY

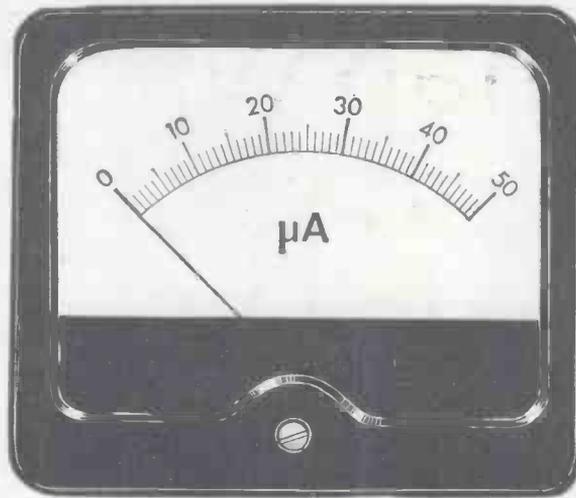One of our "up to the minute" instruments for "up to the minute" requirements, available for speedy delivery in a wide range of microammeters, milliammeters and voltmeters both DC and rectified AC.



This is an actual size illustration of our model "SQ 2" in black moulded case. Further information on this range, and other modern stylings, will be sent on request.

HARRIS ELECTRONICS (LONDON) LIMITED

138 Gray's Inn Road, W.C.1.

'Phone Terminus 7937

WW-022 FOR FURTHER DETAILS.



SME

The best pick-up arm in the world

Only S.M.E. Precision Pick-up Arms offer all these features • Choice of arm length Model 3009 (9in.) or Model 3012 (12in.) for still lower tracking error—of special importance with elliptical styli • Low inertia • High precision ball races and knife-edge bearings for minimum pivot friction • Linear offset chosen for lowest distortion • Automatic slow-descent with hydraulic control • Bias adjuster calibrated for tracking force • Exact overhang adjustment with alignment protractor • Precise tracking force from $\frac{1}{4}$ -5 grams applied without a gauge • Shielded output socket • Low capacity 4ft. connecting cable with quality plugs • Light-weight shell • Camera finish in satin chrome, gun-black and anodised alloy • Comprehensive instructions • Rational development—all improvements can be incorporated in any existing Series II arm.

For sales and service ring Steyning 2228.

S.M.E. LIMITED • STEYNING • SUSSEX • ENGLAND

WW-023 FOR FURTHER DETAILS.

The hard-to-find man is the man with advanced technical knowledge

In the field of Electronics today the greatest demand is for men to fill the positions of skilled technicians and support engineers. These are the 'hard-to-find' men for whom the way ahead to rewarding and interesting jobs lies wide open.

CREI HOME STUDY COURSES offer advanced technical education to the man who realises that technical knowledge must be current and up-to-date if progress is to be made in a world in which new ideas, new techniques and new applications develop almost overnight.

CREI COURSES ARE AVAILABLE IN:-

- Electronic Engineering Technology
- Automation & Industrial Electronic Engineering
- Nuclear Engineering
- Communications Engineering
- Aeronautical & Navigational Engineering
- Television Engineering
- Servomechanisms & Computer Engineering
- Space Data Systems
- Radar & Servo Engineering
- Mathematics for Electronic Engineers
- City & Guilds of London Institute: Subject 49 and Supplementary Studies Subject 300.

For further information write to:

G.R.E.I. (London) (Dept. WW73)
WALPOLE HOUSE, 173/176 SLOANE STREET, LONDON, S.W.1
Telephone: BELgravia 8662

(INTERNATIONAL DIVISION OF CAPITOL RADIO ENGINEERING INSTITUTE, WASHINGTON, D.C.)

PLEASE SEND ME (FOR MY INFORMATION AND ENTIRELY WITHOUT OBLIGATION) FULL DETAILS OF THE CITY & GUILDS PROGRAMME. (C. & G. SUBJECT 49)

1st yr. 2nd yr. 3rd yr. 4th yr.
 SUPPLEMENTARY STUDIES (SUBJECT 300)

NAME

ADDRESS

EDUCATIONAL AND TECHNICAL BACKGROUND

C.R.E.I. (LONDON) (DEPT. WW73)
WALPOLE HOUSE, 173/176 SLOANE STREET, S.W.1

PLEASE SEND ME (FOR MY INFORMATION AND ENTIRELY WITHOUT OBLIGATION) FULL DETAILS OF THE EDUCATIONAL PROGRAMMES OFFERED BY YOUR INSTITUTE

NAME

ADDRESS

ELECTRONICS EXPERIENCE

C.R.E.I. (LONDON) (DEPT. WW73)
WALPOLE HOUSE, 173/176 SLOANE STREET, S.W.1

CHASSIS and CASES

by *Smith's*
of
EDGWARE ROAD

H. L. SMITH & CO. LTD.
ELECTRONIC COMPONENT DISTRIBUTORS
287/289 EDGWARE ROAD, LONDON, W.2.
Tel: PADDington 5891/7595

We shall be pleased to quote for all your component requirements

BLANK CHASSIS

SAME DAY SERVICE

Of over 20 different forms made up to YOUR SIZE.
(Maximum length 35in., depth 4in.)

SEND FOR ILLUSTRATED LEAFLETS or order straight away, working out total area of material required and referring to table below, which is for four-sided chassis in 16 s.w.g. aluminium.


48 sq. in.	4/6	176 sq. in.	9/10	304 sq. in.	15/2
80 sq. in.	5/10	208 sq. in.	11/2	336 sq. in.	16/6
112 sq. in.	7/2	240 sq. in.	12/6	368 sq. in.	17/10
144 sq. in.	8/6	272 sq. in.	13/10	and pro rata.	
P. & P. 2/6		P. & P. 2/9		P. & P. 3/-	

Discounts for quantities. More than 20 sizes kept in stock for callers

FLANGES (1/4in., 3/8in.), 6d. per bend.

STRENGTHENED CORNERS 1/- each corner.

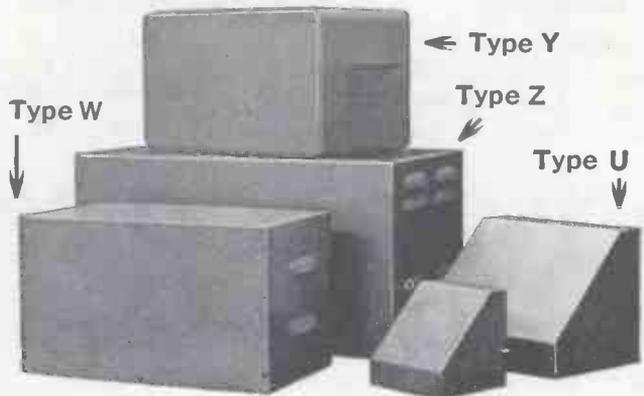PANELS: Any size up to 3ft. at 6/- sq. ft. 16 s.w.g.; (18 s.w.g. 5/3). Plus post and packing.



CASES

ALUMINIUM, SILVER HAMMERED FINISH

Type	Size	Price	Type	Size	Price
U	4 x 4 x 4*	10/-	Y	8 x 6 x 6*	26/6
U	5 1/2 x 4 1/2 x 4 1/2	15/6	Y	12 x 7 x 7	41/-
U	8 x 6 x 6	21/-	Y	13 x 7 x 9	46/-
U	15 x 9 x 9	44/6	Y	15 x 9 x 7	48/6
W	8 x 6 x 6	21/-	Z	17 x 10 x 9	66/-
W	12 x 7 x 7	34/-	Z	19 x 10 x 8 1/2	71/-
W	15 x 9 x 8	44/-			

Plus post and packing.

Type U has removable bottom or back, Type W removable front, Type Y all-screwed construction, Type Z removable back and front.

WW-025 FOR FURTHER DETAILS.



MINIFLUX  **MAGNETIC HEADS**

Specialists in components for magnetic recording.
Heads for tape · 8-16mm Film · Solid-state Record & Playback Amplifiers · Class D erase & bias Oscillators



MINIFLUX ELECTRONICS LTD.
8 Hale Lane. London N.W. 7.

WW-026 FOR FURTHER DETAILS.

MICROPHONES

their accessories

TRANSISTOR SOUND

and

'RADIOMIC' EQUIPMENT


top ranking quality for top ranking performance.

Full particulars from:

LUSTRAPHONE

St. George's Works, Regent's Park Road,
London, N.W.1 Tel: PRIMrose 8844

WW-027 FOR FURTHER DETAILS.

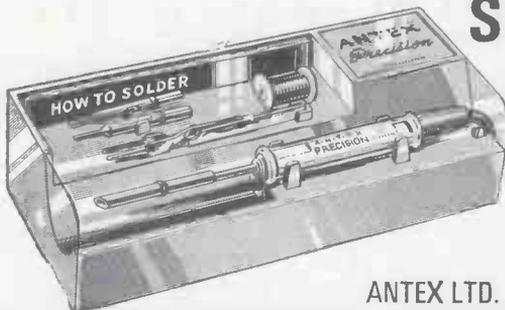

SOLDERING?—the complete answer!

Made by ANTEX — makers of the finest precision soldering irons in the world, this Soldering Kit contains *everything* you need for successful soldering. Unique plastic "tool-box" format (with space for iron stowage *with* plug) keeps everything where you want it.

ANTEX LTD. GROSVENOR HOUSE, CROYDON, SURREY. MUNICIPAL 2774/5

WW-028 FOR FURTHER DETAILS.

THE AUDIO FIDELITY STEREO-33

A High Fidelity, All Transistor Stereo Amplifier providing 10 watts R.M.S. on each channel

OUTPUT PER CHANNEL

10 watts R.M.S. into 15 ohm load.
15 watts R.M.S. into 3.75 ohm load.

TOTAL HARMONIC DISTORTION

0.1% at 10 watts R.M.S. } Into 15 ohm
1,000 c.p.s. } load.

DAMPING FACTOR 20.

FREQUENCY RESPONSE

±1½ db. 20-20,000 c.p.s.

HUM AND NOISE

-80 db.

CROSS TALK

-42 db. to -53 db.

MAINS INPUT SELECTION

100-110-120-200-210-220-240V.
50/60 c.p.s.

SEMI-CONDUCTORS (per channel)

AC107, OC44(3), OC81Z(2), OA5, OC127Z
AD140(2)

INPUT SENSITIVITIES

(for 10 watts R.M.S. into 15 ohms)

Pick-up Magnetic 3.5 mv. 33½ r.p.m.

7 mv. 78 r.p.m.

Pick-up Crystal/Ceramic 400 mv.

Microphone 5 mv.

Tape Head 2 mv.

Aux. (Radio, Tape, Ceramic P.U. etc.) 100 mv.


(Above sensitivities will be doubled when

output load is 3-4 ohms.)

BASS CONTROLS

+11 db. to -16 db. at 40 c.p.s.

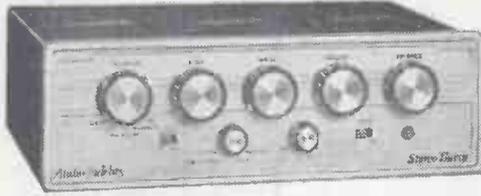Incorporation of the very latest Transistors has made possible the really outstanding performance figures of this brilliant design. Compare them with other leading makes currently available.



RETAIL PRICE 39 GNS

THE PRE-AMPLIFIER IS A COMPLETELY NEW DESIGN

IT MINIMISES THE NECESSITY OF MATCHED INPUTS AND COMPLICATED SWITCHING ARRANGEMENTS. IT ALSO PRODUCES CONDITIONS OF MINIMUM NOISE AT HIGHEST SENSITIVITIES.

TREBLE CONTROLS
+ 15 db. to - 15 db. at 10 kc/s.
EQUALISATION
Gram to standard R.I.A.A. characteristic. Tape head to standard C.C.I.R. characteristic.
SIZE 12½ x 4 x 8½ in.
WEIGHT 12½ lb.
FILTER (Steep Cut) 7 kc/s., 11 kc/s., 15 kc/s.
INPUT SELECTOR
33½ r.p.m., 78 r.p.m., AUX., Mic., Tape Head.
INPUT SOCKETS
Magnetic P.U., Crystal/Ceramic Pick-up. Aux., Tape Head/Microphone.

Designed for ease of fitting in cabinet or for free standing use. Tested for satisfactory operation in temperatures of up to 50°C. (120°F.).

Built to highest standards employing latest materials and techniques.

PLEASE SEND S.A.E. FOR LEAFLET
EXPORT ENQUIRIES INVITED

Designed and developed by the Audio Fidelity Group of Companies.

Manufactured and Distributed by **LINEAR PRODUCTS LTD. ELECTRON WORKS, ARMLEY, LEEDS.**

WW-029 FOR FURTHER DETAILS.

LIVE SOCKETS Instantly!

With Lexor DIS-BOARDS. Over 1,000 combinations in all types of fittings and finishes. Available from stock.

Brochure and price list from:
LEXOR DIS-BOARDS LIMITED, ALLESLEY OLD ROAD, COVENTRY. Telephone: 72614 or 72207



WW-030 FOR FURTHER DETAILS.

TRANSFORMERS COILS CHOKES

LARGE OR SMALL QUANTITIES
TRADE ENQUIRIES WELCOMED

SPECIALISTS IN
FINE WIRE WINDINGS

MINIATURE TRANSFORMERS
RELAY AND INSTRUMENT COILS, ETC.
VACUUM IMPREGNATION TO APPROVED STANDARDS

ELECTRO-WINDS LTD.

CONTRACTORS TO G.P.O., A.W.R.E., L.E.B., B.B.C., ETC.
123-5-7 PARCHMORE ROAD, THORNTON HEATH, SURREY
LIVINGSTONE 2261 EST. 1933

WW-031 FOR FURTHER DETAILS.

with the NEW Antex **PRECISION SOLDERING KIT**

This is what the ANTEX Kit contains:

- Model CN240 15W Precision Iron with 3/16" bit, (used in electronic workshops and factories all over the world)
- Two spare Interchangeable Bits (5/32" and 3/32")
- Reel of resin-cored Solder
- Handy Heat Sink ● Cleaning Pad

PLUS 36-page booklet on "How-to-Solder"—a mine of information for amateur and professional.

BRING YOUR WORKSHOP UP-TO-DATE with the new ANTEX KIT

Obtainable from radio and electrical shops everywhere.

49'6

ANTEX LTD. GROSVENOR HOUSE, CROYDON, SURREY. MUNICIPAL 2774/5

WW-032 FOR FURTHER DETAILS.

Genevac

VACUUM COATING UNITS



All purpose 6" & 12" Units

- ★ 1", 2", 3" or 4" Vacuum Systems
- ★ Fully fitted workchamber
- ★ 10^{-4} torr in 4 minutes with 4" system
- ★ 12v. 40A. LT Evaporation supply
- ★ 3000v. 100mV. Ion clean up supply



Accessories include Carbon Coating and Sputtering Equipment, Rotary Drives and 6-source Turret.

Complete Microcircuit and Thin Film Production Equipment is also available.

Full details on request.

GENEVAC LTD., Subsidiary of General Engineering Co. (Radcliffe) Ltd.

PIONEER MILL · RADCLIFFE · MANCHESTER
Tel.: Radcliffe 3041-2

Branch Offices:

LONDON	MIDLAND	SCOTTISH	MANCHESTER	LIVERPOOL
Tel.: WATERLOO 2248	Tel.: SHIRLEY 4508	Tel.: CALEDONIAN 5597	Tel.: BLACKFRIARS 0185	Tel.: CENTRAL 9532-3

WW-033 FOR FURTHER DETAILS.

THE PEMBRIDGE COLLEGE OF ELECTRONICS FOR TRAINING IN RADIO AND TELEVISION

FULL-TIME COLLEGE COURSE IN RADIO AND TELEVISION

Our Course, of sixteen months' duration, provides a fundamental training for radio and television engineers. It includes theoretical and practical instruction on transistor television receivers, U.H.F. television receivers and colour television.

Exactly half the time is spent on practical work and the course provides excellent practical experience on valve and transistor radio receivers and high-fidelity equipment and all well known makes of television receivers.

The Course is recognised by the Radio Trades Examination Board (R.T.E.B.) for the Radio and Television Servicing Certificate examinations.

Next Course commences 4th January, 1967.

To: **The Pembridge College of Electronics (Dept. P10)**
34a Hereford Road, London, W.2.

Please send, without obligation, details of the Full-time Course in Radio and Television.

Name _____

Address _____

CMP5


WW-034 FOR FURTHER DETAILS.

SUPERIOR PERFORMANCE

Celestion

Studio Series

LOUDSPEAKERS

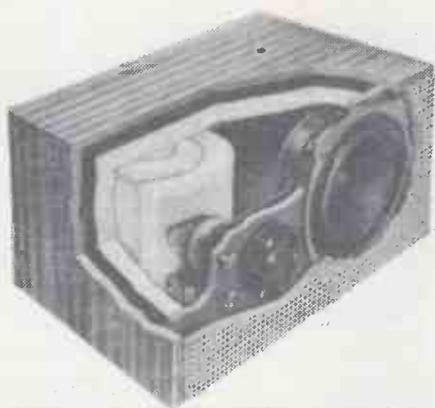

The Ditton 10

The Ditton 10 is a compact high fidelity reproducer measuring only 12 $\frac{3}{4}$ " x 6 $\frac{3}{4}$ " x 8 $\frac{1}{2}$ ". We, along with many thousands of satisfied users throughout the world, consider it to be the finest loudspeaker in its class—sales certainly substantiate this.

If you are in doubt ask your audio dealer to demonstrate the Ditton 10 against any other comparable system.

Brief Specification

Power handling capacity	10 watts R.M.S.
Overall frequency response	35-15,000 c/s
Impedance	15 ohms
Size	12 $\frac{3}{4}$ " x 6 $\frac{3}{4}$ " x 8 $\frac{1}{2}$ " (323mm x 171mm x 203mm)

Price £19.6.0. inc. P.T. plus 5/7d. surcharge.



CX2012

When installed in a suitably designed enclosure the CX 2012 12" Co-axial loudspeaker provides truly professional sound quality.


A highly compliant cone surround allows maximum linear movement and minimises harmonic distortion.

Sensitivity of the co-axially mounted, horn-loaded, compression high note unit may be adjusted by means of the "Brilliance" control provided.

Brief Specification

Power handling capacity	20 watts R.M.S.
Overall frequency response	30-18,000 c/s
Impedance	15/16 ohms

Price
£17.10.0.

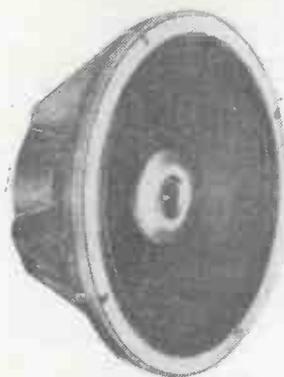

CX1512

A lower powered alternative to Model CX 2012, Model CX 1512 provides the high standards of performance demanded by professional users.

Price £12.5.0.

Brief Specification

Power handling capacity	15 watts R.M.S.
Overall frequency response	30-15,000 c/s
Impedance	15/16 ohms

SMALLER ENCLOSURES

Celestion research engineers have now evolved two new enclosure designs of only 2.5 cu. ft. to accommodate the above co-axial loudspeakers. Their external dimensions (using $\frac{3}{4}$ " timber) are only 30" x 17 $\frac{1}{2}$ " x 11 $\frac{1}{2}$ ". Full details are given on the colour brochure.

Celestion

Studio Series

CELESTION LTD

Ferry Works, Thames Ditton, Surrey. Tel: EMBerbrook 3402/6

GD408

WW-035 FOR FURTHER DETAILS.

Celestion Ltd., Ferry Works, Thames Ditton, Surrey.
Please send me full details of the Studio Series range of loudspeakers.

Name _____
Address _____
A 21 _____



LOUDSPEAKERS

A RADFORD loudspeaker is not just another loudspeaker. It is something very special.

Reporting on the 1966 Audio Fair HI-FI NEWS said of the STUDIO model "... Radford amplifiers provided signals for a pair of STUDIO speakers, and the latter gave a purity of sound on singing voices never heard before ..."

Similarly Donald Aldous commented in A.R.R. "The performance of this big loudspeaker reaches such a high standard of realism that it must be heard—no words can describe the quality."

Four types of loudspeaker are available as described below. Each model has been designed to obtain the maximum possible performance within a size and price classification. In each category the RADFORD loudspeaker will out-perform any other make.

BOOKSHELF

Uses two drive units, equalised and integrated by a ten element electrical network. Sealed enclosure loaded with a new sound absorbing material. Sensibly flat response from 60 Hz to 14 kHz. Size 21 x 12 x 8in. (53 x 30 x 20 cms.).

EXECUTIVE

This loudspeaker is identical with the Bookshelf model in respect of the drive units and integrating network; the difference being solely in the styling and size of the enclosure. The larger enclosure enables the low frequency response to be extended to 40 Hz. Delayed responses in the lower mid-range are also reduced due to the increased dimension from front to back. Sensibly flat response 40 Hz to 14 kHz. Size 25½ x 15 x 11½in. (65 x 38 x 29 cms.).

MONITOR

Three drive units are used in this loudspeaker. The enclosure is identical with that of the Executive.

The moderate size and exceptional performance of this system makes it very suitable for use as a monitor for broadcast and recording where the most accurate low distortion reproduction is essential. All the drive units have a high power capability within their frequency range, and due to the precise filtering, relatively high sound pressure levels may be generated over the whole frequency band when used with amplifiers of sufficient power output. Sensibly flat response 40 Hz to 14 kHz. Size 25½ x 15 x 11½in. (65 x 38 x 29 cms.).

STUDIO

This loudspeaker uses four drive units. In order to extend the flat response below 40 Hz the rear of the bass driver is loaded with an acoustic transmission line. Sensibly flat response 30 Hz to 25 kHz. Size 35 x 17¼ x 15in. (89 x 44 x 38 cms.).

Why not go to your dealer for a demonstration?

RADFORD ELECTRONICS LTD
Ashton Vale Road
Bristol 3

WW—036 FOR FURTHER DETAILS

M. R. SUPPLIES, Ltd.

(Established 1935)

Known for many years as the most reliable source of the following specialised material—always right up to date. Careful packing—immediate delivery. Prices nett.

THERMOSTATS. Open type. Made by Sunvic Controls for building in equipment. Variable from 30 to 80°. 3 degree diff. 15 amps A.C. Switching. 6/6 ea. (des. 2/6.)

EXTRACTOR FANS. Ring mounted all metal construction. T/E induction motor silent operation. 8" Blade, 10" max dia. 400 C.F.M. £5.15.0. (des. 5/-). Same model 10" Blade, 12" max dia. 500 C.F.M. £6.6.0. (des. 5/-).

ELECTRIC GRINDERS. 200/250 v. A.C. Fitted coarse and fine 3in. grindingwheels. Very handy for many domestic and industrial uses. Foot mounted, overall length 7in. £7/15/- (des. 2/6).

MINIATURE RUNNING TIME METERS (Sangamo). We have great demands for this remarkable unit and can now supply immediately from stock, 200/250 v. 50 c. synchronous. Counting up to 9,999 hours, with 1/10th indicator. Only 1½in. square, with cyclometer dial, depth 2in. Many industrial and domestic applications to indicate the running time of any electrical apparatus—easy to install. 60/- (post paid).

SMALL GEARED MOTORS. In addition to our well-known range (List GM 564), we offer small open type S.P. units, 200/250 v. A.C., 1, 6, 12, 24, 60 r.p.m., approx. 5in. long, with 1½in. shaft projection. Suitable for display work and many industrial uses. Only 69/6 (des. 3/-).

SYNCHRONOUS TIME SWITCHES (Our very popular speciality). 200/250 v. 50 c. for accurate pre-set switching operations. Sangamo 8.254, providing up to 3 on-off operations per 24 hours at any chosen time with day-omitting device (use optional). Capacity 20-amps. Compactly housed, 4in. dia. 3½in. deep. With full instructions, £5/18/6 (des. 3/-). Also same make, same duty. Domestic Model fitted with 13-amp. plug for easy installation, portable, £4/9/6 (des. 3/-). Other ratings of Time Switches available for special requirements—please enquire.

MINIATURE VARIABLE TRANSFORMERS (Philips). Remarkable and very popular offer from stock. Open type—panel mount, only 3½in. dia. Input 200/240 v. Output 0/240 v. 0.5 amp. continuous, £3/18/6 (des. 2/6).

AIR BLOWERS. Highly efficient units fitted induction totally enclosed motor 200/260 v. 50 c. 1 ph. Model 8D.26, 80 CFM (free air) to 11.5 CFM at 15 WG (size approx.) 6 x 6 x 7in. Outlet 2½in. square £3/10/- (des. 5/-). Model 8D27, 120 CFM (free air) to 40 CFM at 1.2 WG, 8 x 7 x 9in. outlet 2½in. sq., £11/15/6 (des. 5/-). Model 8D28, 260 CFM (free air) to 127 CFM at 1.5 WG 11 x 8 x 9in., outlet 3in. sq. £13/17/6 (des. U.K. 7/6).

SYNCHRONOUS ELECTRIC CLOCK MOVEMENTS (as mentioned and recommended in many national journals), 200/250v. 50 c. Self-starting. Fitted spindles for hours, minutes and central sweep seconds hands. Central one-hole fixing. Dia. 2½in. Depth behind dial only 1½in. With back dust cover, 29/6 (des. 1/6). Set of three brass hands in good plain style. For 5/7in. dial 2/6. For 8/10in. dial 3/6 set.


SYNCHRONOUS TIMER MOTORS (Sangamo). 200/250 v. 50 c/s. Self-starting 2in. dia. x 1½in. deep. Choice of following speeds: 1 r.p.m., 12 r.p.h., 1 r.p.h., 1 rev. 12 hours, 1 rev. per day. Any one 39/6 (des. 1/6). Also high-torque model (G.E.C.) 2½ x 2in. x 1½in., 6 r.p.m. 57/6 (des. 1/6).

IMMEDIATE DELIVERY of Stuart Centrifugal Pumps, including stainless steel (most models). Philips Variable Transformers (all models).

M. R. SUPPLIES, Ltd., 68 New Oxford Street, London, W.C.1
(Telephone: MUSeum 2958)

EDDYSTONE COMMUNICATION RECEIVERS

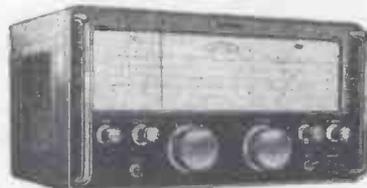For the professional or Amateur user who likes the Best.



840C
£66

Communication receiver at a moderate price. MANUFACTURING STANDARDS OF THE HIGHEST ORDER, 8 B8A valves Superheterodyne circuit. **FREQUENCY RANGES:**

Range 1 12.4—30 Mc/s
Range 2 5.2—12.0 Mc/s
Range 3 2.5—6.1 Mc/s
Range 4 1.12—2.58 Mc/s
Range 5480—1.150 kc/s

Ranges 4 and 5 include the international Distress Frequencies.

Model No.	Cash Price	Model No.	Cash Price
EC10.....	£48 0 0	EB35.....	£59 7 6
840C.....	£66 0 0	940.....	£133 0 0
	EA12.....		£185 0 0

Hire Purchase Terms gladly arranged. Owing to frequent changes in the HP regulations we are obliged to discontinue advertising these. Please write for current rates. A 4d stamp will bring you these and a full range of Eddystone Literature.

Carriage paid per passenger train. SATISFACTION GUARANTEED

SEND FOR LITERATURE TO

The Eddystone
Specialists

SERVICES LTD.


49/51 COUNTY ROAD
LIVERPOOL, 4



Telephone: AINTREE 1445

ESTAB. 1935

WW—037 FOR FURTHER DETAILS.

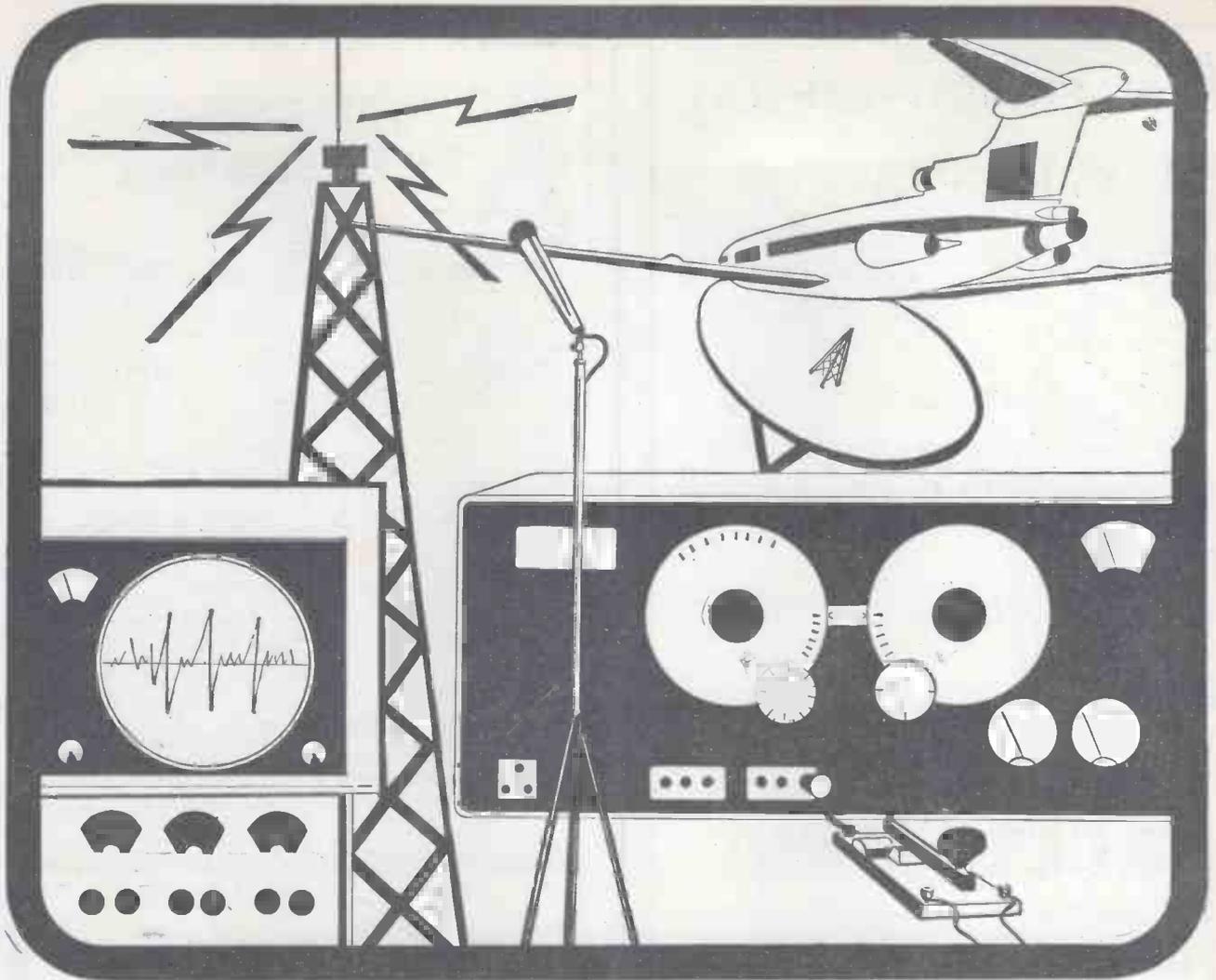

WHERE THE GOING IS TOUGH, THE NEED FOR QUALITY VITAL GOVERNMENTS AGREE ON TEONEX VALVES.

Governments all over the world have chosen TEONEX Valves for vital civil and military roles requiring compliance to E.V.S. or M.I.L. standards. In spite of rising demand for these valves from government departments the world over, increased production facilities have made it possible to offer the TEONEX range (incorporating the entire range of British-produced valves or their Continental equivalents) for use outside the U.K. only.


Price list and technical specifications may be obtained from:—

TEONEX LIMITED

2a Westbourne Grove Mews,
London, W.11
England.



Export Enquiries Only Please!

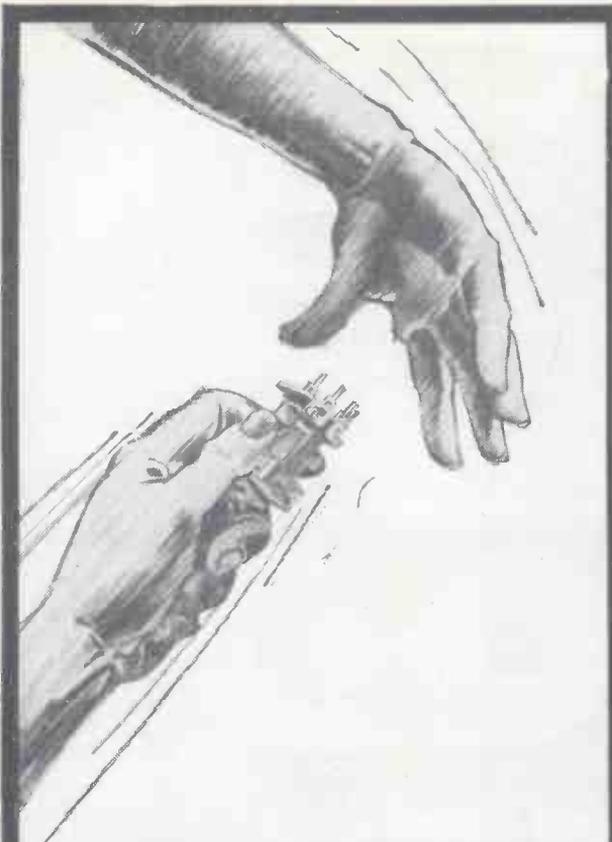

THE ETHER RELAY RACE!

Starters – many. Handicap – quality at the right price. Winners – Ether, because of their perfect changeover. Special Prize – awarded to Ether for bringing to the field two new low-cost miniature relays for either printed circuit or chassis mounting. Robustly designed and reliable for many applications such as domestic appliances or vending machines – but equally suitable for any application which requires inexpensive trouble-free relay performance.

Two-pole changeover types: up to 2A (240V a.c. or 24V d.c.)
 Single-pole double make and break: up to 3A (240V a.c. or 24V d.c.)
 Standard coil voltages: 6, 12, 18 and 24V d.c.
 Maximum operating power: 1W

Umpire – you, the user

“ TALK RELAYS WITH ETHER ”



ETHER

ETHER LIMITED, General Products Division, Caxton Way, Stevenage, Herts.
 Telephone: Stevenage 4422. Telex: Ether Stevenage 82319

WW—039 FOR FURTHER DETAILS.


G P 7



PRECISION PRESSINGS

Accurate components at competitive prices

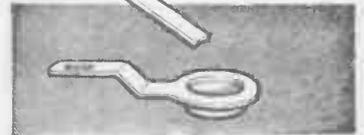produced by progressive tooling and multiform methods



JOHN SMITH LTD.

209 SPON LANE · WEST BROMWICH · STAFFS TELEPHONE: WES 2516 (3 lines)
 WOODS LANE · CRADLEY HEATH · STAFFS TELEPHONE: CR 69283 (3 lines)
 WW—040 FOR FURTHER DETAILS.



TRANSVERTERS


(TRANSISTORISED D.C. CONVERTERS)

the D.C. conversion specialists since 1935

2 KW. Peak Starting.
 750 W. Continuous.
 50-60-400 c/s. or D.C.
 from 12-24-50v. Battery.
 Up to 93% Efficiency. Polarity Reversal Protection. Square or Sinewave. Up to 300% Instant Overload Capacity. Manually Controlled Frequency. Reed Type Indicator. Remote Control Facilities.

Applications: Static "No-Break" Standby Power Supplies: For Vital System(s) Protection, e.g. V.H.F. Transmitters: Industrial Processes: Control-Alarm-Warning Systems: Mobile Use of Counters; Sig./Gen Recorders—U/V Sound. Oscilloscopes and Lab. Gear in Marine and Aircraft (K114).

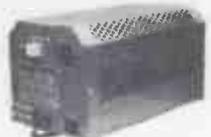
Range of models available. Please write to department with prices from £11-£94.10.0 C.10 for transverter leaflet



VALRADIO LIMITED
 BROWELLS LANE · FELTHAM · MIDDLESEX ENGLAND
 Telephone: FELTHAM 4837-4242

Valradio and Stereosonoscope are the registered trade marks of Valradio Ltd.

WW—041 FOR FURTHER DETAILS.

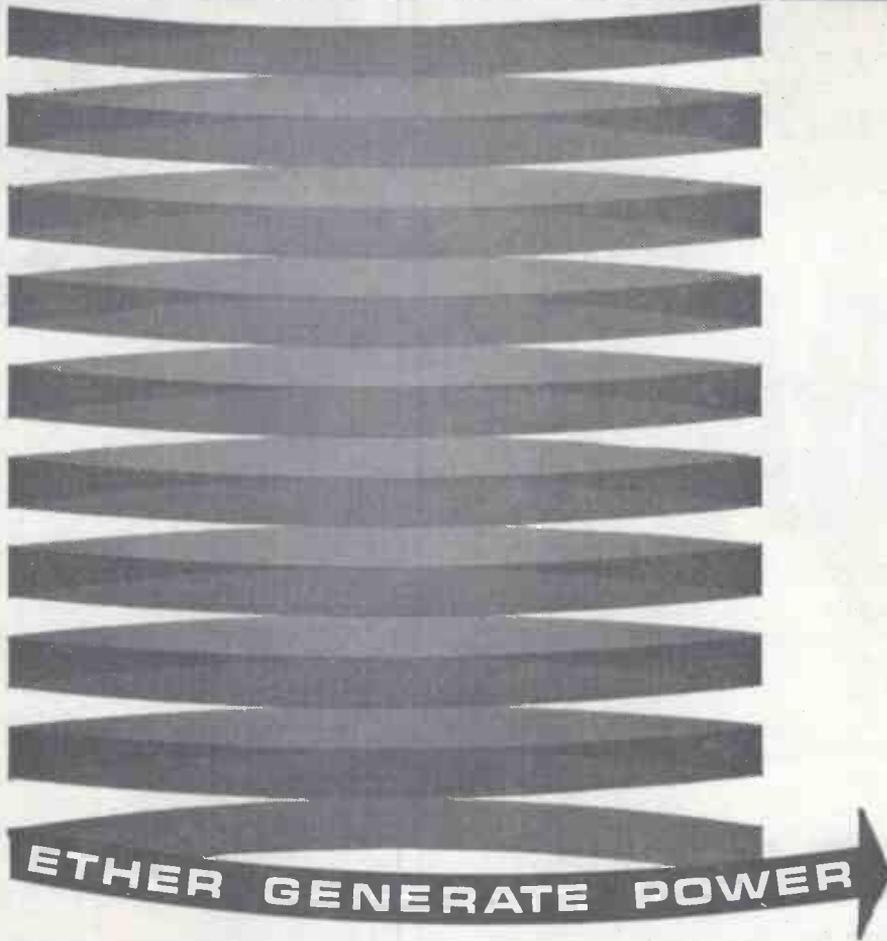


Switch-on with ETHER power supplies

Power supplies—an integral part of any electronic design—can be a headache. Consult Ether at the design stage of any project.

Specialist designs available in addition to a wide range of off-the-shelf equipment, all with power-in-reserve including:

High-stability units (single and multi-output) variable, plug-in and programmed equipment with wide choice of current and voltage ranges, a.c. voltage regulators, silicon or germanium units.

“TALK POWER WITH ETHER”

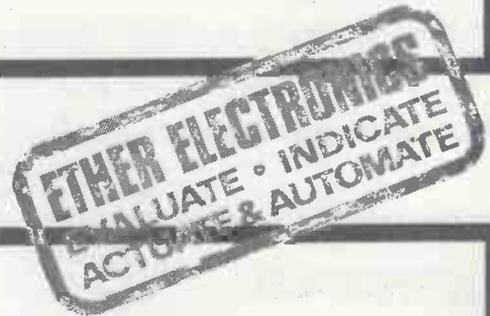

ETHER

ETHER LIMITED, General Products Division, Caxton Way, Stevenage, Herts. Telephone: Stevenage 4422. Telex: Ether Stevenage 82319

**YOU CAN
NOW BUY THE
WORLD'S FINEST
SPEAKER VALUE
DIRECT FROM**

R&A

The 700 Mark V Range

Specially designed to provide outstanding range, smoothness and uniformity of frequency response with freedom from self generated forms of distortion up to levels more than adequate for domestic listening. The speakers in this range all have a highly developed dual radiating system with optimum termination of both cones — voice coil impedance 15 ohms.



Power handling capacity in appropriate enclosures:—

- 780 Mk. V Price £3.19.7
8 in. 6 watts r.m.s. 12 watts peak. (inc.11/7 P.T.and P.&P.)
- 7100 Mk. V Price £4.14.3
10 in. 8 watts r.m.s. 15 watts peak. (inc.13/9 P.T. and P.&P.)
- 7120 Mk. V Price £4.18.6
12 in. 10 watts r.m.s. 18 watts peak. (No P.T. but Inc. P. & P.)


Send for full technical data sheet with suggestions for enclosures to:

REPRODUCERS AND AMPLIFIERS LTD.
Frederick Street, Wolverhampton England

LOUD SPEAKER MANUFACTURERS TO THE
RADIO INDUSTRY SINCE 1930

WW—043 FOR FURTHER DETAILS.

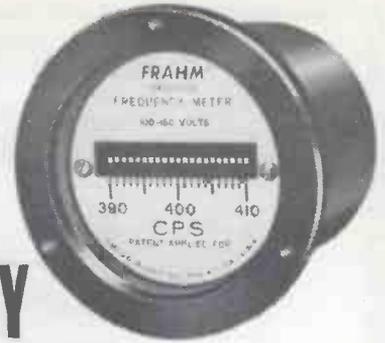**FRAHM
vibrating
reed
FREQUENCY
METERS**



are widely used as standards in many industries because:—

- 1) They are accurate (to $\pm 0.3\%$ or $\pm 0.1\%$ as specified)
- 2) They are not voltage or temperature sensitive, within wide limits
- 3) They are unaffected by waveform errors, load, power factor or phase shift
- 4) They will operate on A.C., pulsating or interrupted D.C., and super-imposed circuits
- 5) They need only low input power
- 6) They are compact and self-contained
- 7) They are rugged and dependable

FRAHM Vibrating Reed Frequency Meters are available in miniature, switchboard and portable forms, in ranges from 10 to 1700 cps. Descriptive literature on these meters, and on FRAHM Resonant Reed Tachometers, freely available from the sole U.K. distributors:—

ANDERS METER SERVICE

ANDERS ELECTRONICS LTD. 103 HAMPSTEAD ROAD LONDON NW1
TELEPHONE EUSTON 1639 *MINISTRY OF AVIATION APPROVED*
WW—044 FOR FURTHER DETAILS.



DIGITUBE TG121A

This Glow Discharge Indicator Tube was designed especially for transistorized electronic equipment.

- IT FEATURES:**
- SMALL SIGNAL INDICATION WITHOUT AMPLIFICATION
 - SMALL POWER CONSUMPTION AND THERMAL DISSIPATION
 - SMALL SIZE (DIAMETER 8MM., LENGTH 18MM.)
 - STABLE CHARACTERISTICS AND LONG LIFE
 - SELF RESET OF DISPLAY

PRICES:

1-99	—	8/3
100 up	—	7/10
1000 up	—	7/5

Available from stock

RASTRA Electronics Ltd.,
275/281 King Street, London, W.6. Tel: RIV 2960

WW—045 FOR FURTHER DETAILS.

**DO YOU STILL USE A HAMMER AND CHISEL
TO CUT A SQUARE IN SHEET METAL?**

Don't any more


We have a Hand-operated Tool now to cut any straight sided shape. Square R/Angles slots for Louvres. All you do is simply mark out your shape and follow the lines. You can also convert the Tool to a Punch-Louvre Forming and Riveting Tool.

**NO DISTORTION OF METAL
ON EITHER SIDE OF CUT**

Also a number of Bench Type folding machines
EXPORT ORDERS DESPATCHED IMMEDIATELY
AVONLEA TOOLS, WOODEND MILL, MOSSLEY, LANCASHIRE.
MOSSLEY 2687



WW—053 FOR FURTHER DETAILS.

RACKS, PACKS and laboratory equipment

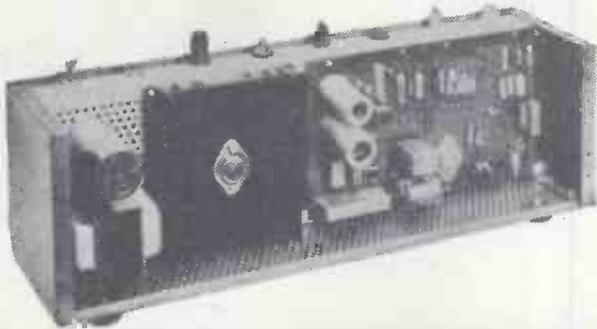

Chassis System

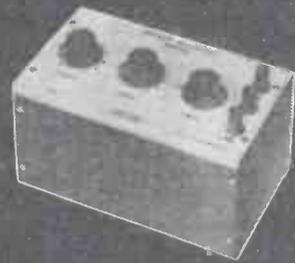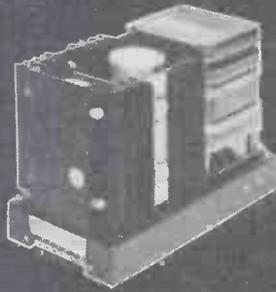The well-known Lektrokit construction system, consisting of a range of simple, inexpensive items from which electronic chassis can be built up, using only screws and nuts.



Rack System

Consists of a range of a few basic parts, from which fixed or mobile 19-inch racks can be assembled without the need for special tools or skills.

Transistor Stabilised Power Units


A range of five mains-operated power supplies with stabilised output voltage fully variable between 0 and 50V. Output currents $\frac{1}{2}$ A, 1A, 2A, 5A or 10A.

Transistor Stabilised Sub-Units

Six sub-units, for incorporation in customers' equipment. Pre-set stabilised output voltages 6-30V; output currents $\frac{1}{2}$ A, 1A, 2A, 3A, 5A or 10A.

Lektrokit Decade Resistors

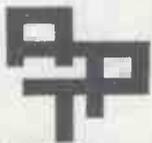
For industrial applications, and for universities, technical colleges and schools. Ranges 0-1.11 k Ω (1 Ω steps, accuracy $\pm 2\%$), or 0-1.11 M Ω (1 k Ω steps, accuracy $\pm 0.5\%$).



A-P-T ELECTRONIC INDUSTRIES LTD.

Chertsey Road, Byfleet, Surrey
Tel. Byfleet 41131/2/3/4 PABX
Grams. APTRAN, BYFLEET

GOODMANS HIGH FIDELITY

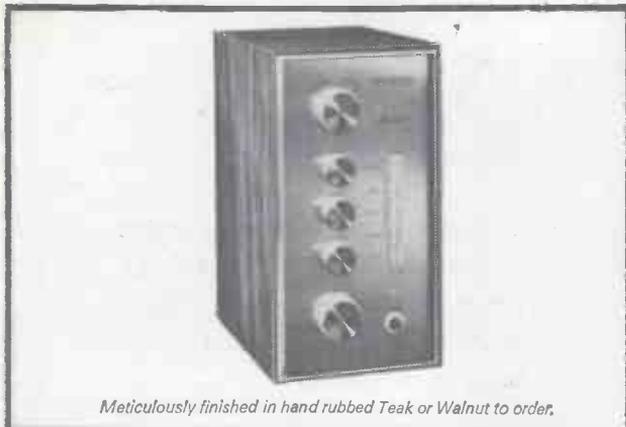

Meticulously finished in hand rubbed Teak or Walnut to order.

MAXAMP 30


The **FIRST** British All-Silicon Transistorised Stereo Amplifier

"An excellent example of fundamental re-thinking in compact stereo amplifier design. Simple to set up and operate . . . there is no doubt that the Maxamp 30—with its high output in a small compass—is the best value-for-money product in this class which is yet available in the U.K." **David Phillips and Donald Aldous "Audio and Record Review," April 1966.**

"... The Maxamp 30 must rate par with the best valve circuits . . . the amplifier passed its test with flying colours . . . the arrangement of the facilities provided could not be better . . . The quality of workmanship in the amplifier is above criticism . . ." **N. Hulley "HiFi News," July 1966.**

"Clearly a real advance has been made . . . the standard is a high and creditable one; to the listener it means clear, firm and well contained reproduction . . . this neat little amplifier is very much a success—a significant contribution to modern solid-state equipment." **Clement Brown "Records and Recording," May 1966.**

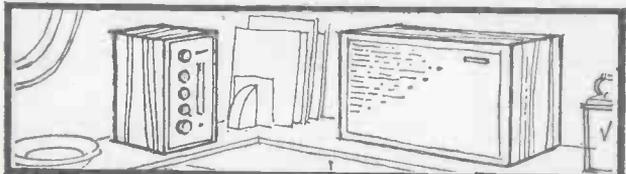"From the measurements taken it will be seen that the makers have been more than modest in their published specification. It is one of the quietest amplifiers I have used, has more than adequate reserve of power for all domestic conditions and a discreet elegance of design that reflect credit on all concerned." **John Gilbert "The Gramophone," July 1966.**



MAXAMP 30 can be used with any high quality loudspeaker, such as Goodmans MAXIM, MEZZO and MAGNUM-K systems (see opposite page). It is shown here with MEZZO.

Frequency response: 20 c/s to 20 Kc/s \pm 3db.

Total Harmonic Distortion: Less than 0.3% for 15 watts per channel into an 8 ohm load at 1000 c/s.

Loudspeaker Outputs: 4—8—15 ohms.

PRICE: £49.10.0

Send the coupon for a free copy of 8 page colour booklet.

Please send MAXAMP 30 booklet and 1966 Hi-Fi Manual together with name and address of my nearest Goodmans dealer.

Name _____

Address _____

WW11

GOODMANS INDUSTRIES • Axiom Works • Wembley • Middx • Tel: WEM1200
A Division of Radio Rentaset Products Ltd.

WW—047 FOR FURTHER DETAILS.

VARIABLE D.C. POWER UNIT WITH ACCUMULATOR PERFORMANCE FROM A.C. MAINS

EFFECTIVE
RESISTANCE
LESS THAN
.1 ohm.



TYPE
250V RU/30/20
250V RU/60/10
PRICE
£131-5-0

FEATURES

0-30 VOLTS Variable up to 20 AMPS.
0-60 VOLTS Variable up to 10 AMPS also available.
RIPPLE CONTENT negligible, IMPEDANCE and REGULATION equivalent to accumulator performance. SILICON RECTIFIERS. Inadvertent "SHORT" protection.
OVERLOAD CAPACITY 200% for short periods.

APPLICATIONS

Operating and Servicing transistorised equipment. 12 v. Mobile radio/tel operation, D.C. Motors, relays, industrial power, etc., from any point of A.C. WITHOUT THE USE OF ACCUMULATORS.

12 v. or 24 v. FIXED OUTPUTS up to 24 Amps. also available.
AVOID THE EXTRA EXPENSE OF SUPER REGULATION YOU MAY NEVER NEED. Prices £14-16-0 to £131-5-0.

Valradio

LIMITED

Please write to department C 3b.
for current literature.

BROWELLS LANE,
FELTHAM, MIDDX.
ENGLAND

Tel.: FEL 4837-4242

VALRADIO and STEREOSONOSCOPE are the registered trade marks of VALRADIO LTD.

WW—048 FOR FURTHER DETAILS.

FRACTIONAL HORSEPOWER ELECTRIC MOTOR MANUFACTURERS



THE HALL MARK
OF QUALITY MOTORS

REGISTERED
TRADE MARK

PROMPT & PERSONAL SERVICE

WRITE TODAY FOR DETAILS


COMTEX LTD

(DEPT. ww) 566 CABLE STREET,
LONDON, E.1, ENGLAND

Telephone: Stepney Green 1400

WW—049 FOR FURTHER DETAILS.

NEW CATALOGUE

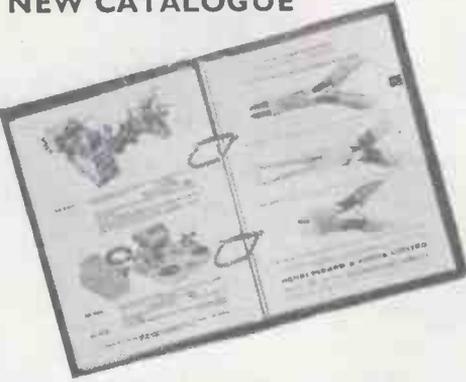

A Comprehensive, fully illustrated Catalogue of hand tools, and small machine tools, for miniature assembly and repair work.


Red plastic ring binder 5/- each
 Red card back cover 2/6 each
 Please send cash with order.

HENRI PICARD & FRERE LTD
ESTD. 1877
 MANUFACTURERS IMPORTERS & WORLD WIDE DISTRIBUTORS
 34/35 FURNIVAL STREET LONDON E.C.4
 BRANCH OFFICES IN SWITZERLAND FRANCE & GERMANY

POPULAR PROGRESS

WW-950 FOR FURTHER DETAILS.

GOODMANS HIGH FIDELITY

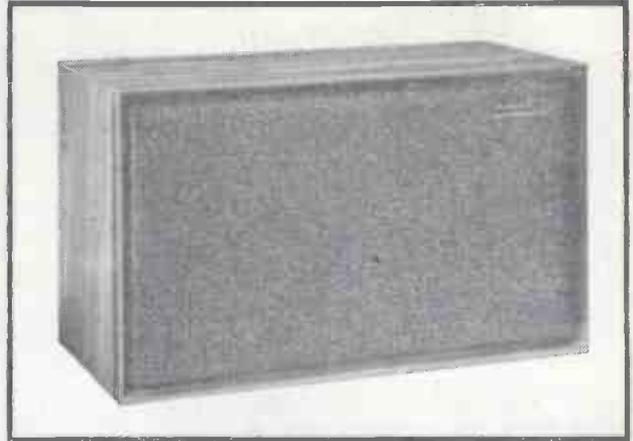

mezzo

HIGH FIDELITY BOOKSHELF LOUDSPEAKER SYSTEM

Handles 15 watts of power—yet measures only 10½" x 18½" x 8" deep—the MEZZO really will go on a bookshelf. The styling is restrained yet distinctive, making MEZZO an "easy" addition to any design-conscious furnishing scheme. The frequency range is a clear and clean 40—20,000 c/s with a control and smoothness accounted for by two new specially developed and patented loudspeakers. The 8" bass unit is of very advanced design and construction, and is particu-

larly notable for its very low distortion and extraordinary smoothness of performance. It is claimed to be the smoothest bass-reproducer of its size ever produced. The treble unit completes the quality picture to give an overall performance unrivalled in a reproducer of this size. The L.C. crossover network operates at 2,200 c/s. The distortion level is extraordinarily low. The perfectly controlled balance of the MEZZO sound makes it—The Loudspeaker to Live With.

SPECIFICATION

Dimensions 10½" x 18½" x 8" deep
 Range 40—20,000 c/s
 Power 15 watts
 Impedance Suitable for 8 ohm—15 ohm amplifiers
 Distortion—Less than 1% total harmonic at 55 c/s and above, for sound pressure level of 80 db at 6 ft.

PRICE £26.12.7. (inc. P.T.)

ORCHARD & IND LIMITED
 PRESENT A SELECTION OF

Loose Leaf Binders


Write for New Catalogue to:
 Head Office:
NORTHGATE · GLOUCESTER
 TELEPHONE: (0GL2) 22111 (5 LINES)
 TELEX: GLOUCESTER 43192

WW-051 FOR FURTHER DETAILS.

Also in Goodmans M range of Loudspeaker systems


MAXIM

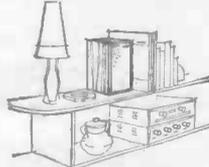8 watts 10½" x 5½" x 7½" deep same size as Maxamp 30, yet gives full range High Fidelity performance.
 £17.15.7. (inc. P.T.)



MAGNUM - K

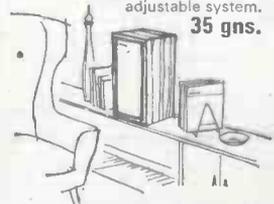25 watts 24" x 15" x 11½" deep. The champagne-class 3 way adjustable system.
 35 gns.



All 3 systems selected for the Design Centre. All meticulously finished in hand rubbed Teak or Walnut to order, and all can be used upright or horizontally.

See and hear them at your local Hi-Fi dealer. We will be pleased to tell you where your nearest stockist is.

Please send MAXAMP 30 booklet and 1966 Hi-Fi Manual together with name and address of my nearest Goodmans dealer.

Name _____
 Address _____

WW11

GOODMANS INDUSTRIES, Axiom Works, Wembley, Middx. Tel: WEM1200
 A Division of Radio Rentaset Products Ltd.

WW-052 FOR FURTHER DETAILS.

NEW PARTRIDGE TYPES

for the MULLARD 50w P.A. TRANSISTOR AMPLIFIER

Microphone input Transformer type TG4731	35/-
Driver Transformer type TG4732	42/6
Output Transformer type TG4733/100V.	65/-
Output Transformer type TG4733/15 ohms.	65/-

Partridge

Ask now for Data Sheet on these new transformers designed for the Mullard 50w and for details of other Partridge Types specified for leading published circuits.

PARTRIDGE TRANSFORMERS LTD.

Roebuck Road; Chessington, Surrey. Telephone: LOWER Hook 4353-4-5



WW-054 FOR FURTHER DETAILS.

Litesold

SOLDERING INSTRUMENTS

With re-styled moulded nylon handles

- SEVEN SIZES, FROM 10 WATTS to 55 WATTS
- REPLACEABLE BITS, COPPER AND PERMATIP
- EXCELLENT TEMPERATURE REGULATION
- COOL, UNBREAKABLE HANDLE
- RAPID HEATING
- SIMPLE SERVICING
- ALL VOLTAGES
- LOW COST




LITESOLD instruments are compact and nicely balanced. Bits are spring-collet mounted for firmness and easy removal.

Copper bits are standard, in sizes from 3/32in. to 13/32in. dia. PERMATIP bits are slightly slower, but eliminate bit face wear.

LITESOLD elements are encased in specially pre-oxidised wire for constant temperature regulation from new—less glamour but honest design, also apparent in the simple, unbreakable handle, with the element unit secured by two self-tapping screws (servicing couldn't be easier) and firm, spring-on clip. LITESOLD hollow-spindle construction prevents heat loss into the handle (which DOES stay cool) and improves performance. Useful LITESOLD accessories include HEAT GUARDS for elements, and BENCH STANDS.

Free details of the whole wide range of LITESOLD and ADAMIN soldering equipment in Brochure SP5. LIGHT SOLDERING DEVELOPMENTS LTD., 28 Sydenham Road, Croydon, Surrey. Tel.: CRO 8589 & 4559

WW-055 FOR FURTHER DETAILS.

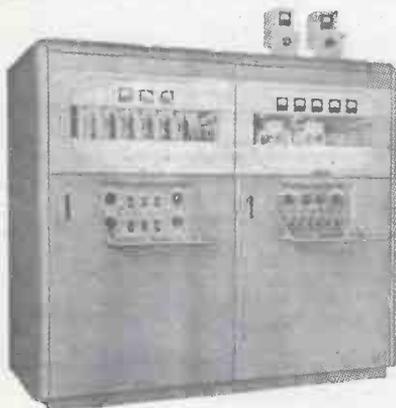

NOW UPGRADE YOUR TRANSMITTER CAPABILITY AT LOW COST!

15 & 50 KW H.F. (4-26 MB) TRANSMITTERS FOR CW, F.S. RTT, ARQ & FACSIMILE FEATURING:

- Linear amplification.
 - Forced air cooled EIMAC 3CX2500A3 tubes.
 - Servo drive mechanisms. Vacuum variable capacitors.
 - With F.S. Keyer, 10 channel crystal-controlled oscillator and variable master oscillator.
 - ISB/SSB/DSB amplification with suitable exciter.
 - Use on 50/60 cycle
 - 600 ohm balanced transmission line output.
 - Spare parts and installation engineering services available.
- Complete technical details on request.

THE MEDITERRANEAN COMMUNICATIONS EQUIPMENT CO. LTD.

P.O. BOX 54, GIBRALTAR

WW-056 FOR FURTHER DETAILS.



FERRANTI Space Vehicle Silicon Solar Cells

TYPES MS20 AND MS21

These are blue-sensitive, radiation resistant, n on p cells which have been specially developed for electric power generation on space vehicles such as ESRO 2 and UK3.

Full design performance data is available showing the variation of load characteristics in space at different radiation levels up to 10^{16} 1 Mev equivalent electrons/sq. cm. dosages and temperature ranges from -120 to $+120^{\circ}\text{C}$. In addition to guaranteeing the performance of complete satellite systems in known orbit radiation and temperature conditions, this data shows that FERRANTI cells possess the maximum known levels of radiation resistance for silicon solar cells, thus enabling known and maximum life to be obtained in orbital service.

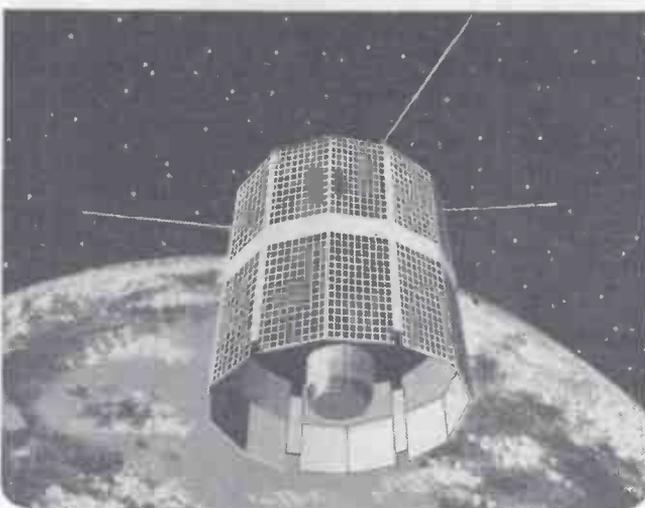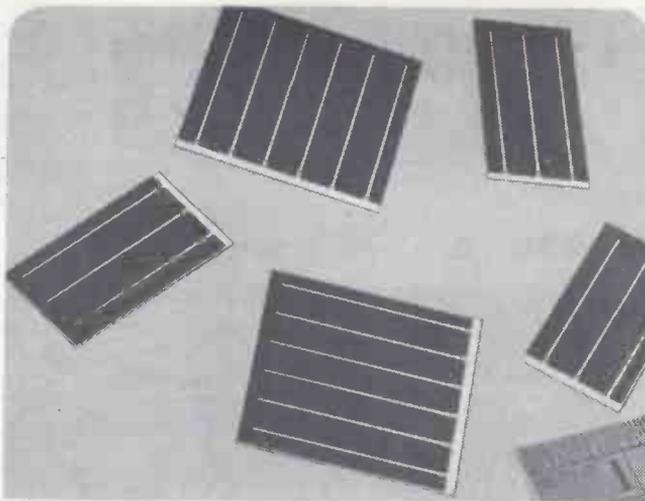This design data is available to system designers on request or via the complete satellite power system design service offered by the Ferranti Automation Systems Division.



RATINGS and CHARACTERISTICS

	Symbol	MS20		MS21		
		Min.	Max.	Min.	Max.	
Short Circuit Current	ISC	66	-	132	-	mA
Current at 300mV Load Point	I300	65	-	130	-	mA
Current at 400mV Load Point	I400	60	-	120	-	mA
Open Circuit Voltage	Voc	530	560	530	560	mV
Blue Spectral Response at 5000A relative to that at 8500A.		45	-	45	-	%
Infra-red Spectral Response at 10,000A relative to that at 8500A.		45	-	45	-	%
Ambient Operating Temperature		-80	+100	-80	+100	$^{\circ}\text{C}$

The illumination intensity is equivalent to 140mW/sq. cm. of Air Mass Zero and is obtained from an infra-red corrected Xenon arc lamp fitted with a Grubb Parsons filter type BA 123.

The Ferranti Automation Systems Division at Simonsway, Wythenshawe, Manchester, 22, telephone MERCURY 5291, undertake the manufacture of cell arrays and power supplies to suit individual satellite systems requirements.

FERRANTI

First into the Future

The following publications on Solar Cells are available on request:
 ESB21—SPACE VEHICLE SILICON SOLAR CELLS TYPES MS20 AND MS21.
 ESA27—RADIATION RESISTANT HIGH EFFICIENCY SILICON SOLAR CELLS.


Write now for details to: FERRANTI LTD, GEM MILL, CHADDERTON, OLDHAM, LANCASHIRE, ENGLAND
 Telephone: (061) MAIN 6661

FE28V


WW-057 FOR FURTHER DETAILS.



have a *name for it!

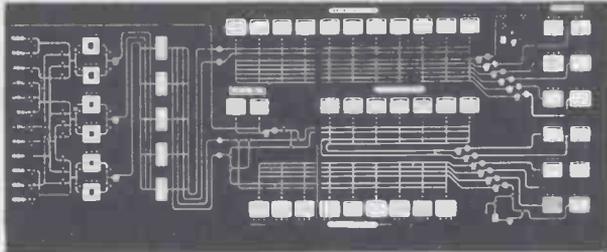

They call it
*
INDICATIVE INTEGRATION

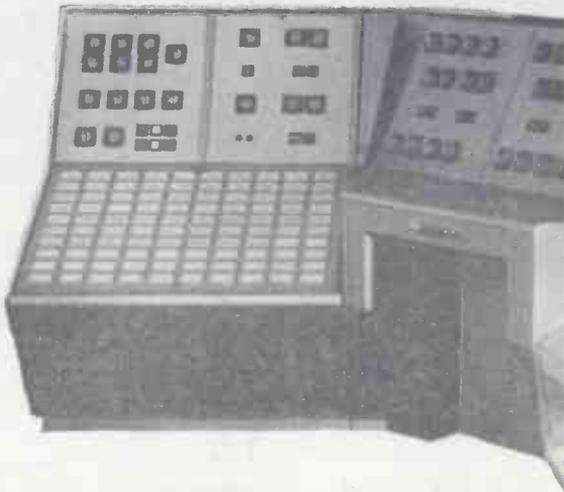

K.G.M. offer a greater variety of Digital Indicators than any other manufacturer. For years they have been designing and making Mimic Diagrams and Control Consoles. Their combination of know-how and manufacturing resources deserves its own title. Ask for the Indicative Integration brochure and see what we mean.

KGM
electronics limited
 BARDOLPH RD RICHMOND
 Phone: RICHmond 7171 Surrey

WW-058 FOR FURTHER DETAILS.




*sound mixers with details
to your specification....*

Elcom complete mixing equipment is designed around the well known Elcom Electronic Fader which provides noise free stepless fade.

A wide range of equipment is available from the transportable four channel Mono/Stereo battery/mains units to large multi-channel studio consoles.

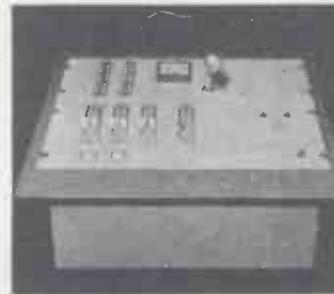Standard equipment can be provided at low cost with an unlimited combination of facilities to customers specification, and we are pleased to discuss specific requirements and submit quotations.



ELCOM

A member of the Painton group of Companies

For full details write or phone:
ELCOM (NORTHAMPTON) LTD.
WEEDON ROAD INDUSTRIAL ESTATE
NORTHAMPTON, Tel. Northampton 51873

WW-059 FOR FURTHER DETAILS.



ARE YOUR INSTRUMENTS ACCURATELY CALIBRATED?

The Bradley Calibrator 130B provides D.C. voltages up to 3,000 and A.C. voltages up to 511 at an accuracy of 0.2% for the rapid and easy calibration of all types of instruments.

This Calibrator provides a wide range of A.C. and D.C. precision voltage steps for testing of avometers, meter movements, transistor and valve voltmeters, oscilloscopes etc. All outputs have % error indication and are short circuit proof.

To enable you to test the 130B Calibrator yourself, we shall be glad to provide one on loan. In addition, the Bradley range includes precision current sources and programming facilities. May we send you full details of the Bradley range of calibrators? Write for the 'Calibration Equipment' booklet, publication No. 102.



G. & E. BRADLEY LIMITED


Electral House, Neasden Lane, London, N.W.10. Telephone: DOLlis Hill 7811
Telegrams: Bradelec London N.W.10. Telex: 25583



FABBRICA ITALIANA APPARECCHI RADIO
DIPARTIMENTO ELETTRONICA PROFESSIONALE
 MILAN (Italy)-Via G. B. Grassi, 93-Telephone: 306241/306841-Telex: 31295

PRODUCTION

- | | |
|---------------------------------|------------------------------------|
| ● Closed circuit television | ● Radar and ancillary equipment |
| ● Sound diffusion installations | ● Electronic military equipment |
| ● TV transmitters | ● Ancillary navigational equipment |
| ● Radio transmitter/receivers | ● Antennae and accessories |

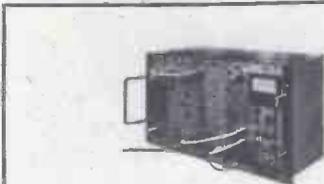

Transistorised television repeater P 3149



Direction unit for large sound diffusion installations



Transistorised telecamera P 4814

WW-061 FOR FURTHER DETAILS.

FREE TO AMBITIOUS ENGINEERS
 - THE LATEST EDITION OF ENGINEERING OPPORTUNITIES

Have you sent for your copy?
 ENGINEERING OPPORTUNITIES is a highly informative 156-page guide to the best paid engineering posts. It tells you how you can quickly prepare at home for a recognised engineering qualification and outlines a wonderful range of modern Home Study Courses in all branches of Engineering. This unique book also gives full details of the Practical Radio & Electronics Courses, administered by our Specialist Electronics Training Division—the B.I.E.T. School of Electronics, explains the benefits of our Employment Dept. and shows you how to qualify for five years' promotion in one year.

SATISFACTION OR REFUND OF FEE

Whatever your age or experience, you cannot afford to miss reading this famous book. If you are earning less than £30 a week, send for your copy of "ENGINEERING OPPORTUNITIES" today—FREE.

BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY
 (Dept. 303B), Aldermaston Court, Aldermaston, Berkshire

WHICH IS YOUR PET SUBJECT?

- Mechanical Eng..
- Electrical Eng..
- Civil Engineering.
- Radio Engineering.
- Automobile Eng..
- Aeronautical Eng..
- Production Eng..
- Building, Plastics, Draughtsmanship, Television, etc.

GET SOME LETTERS AFTER YOUR NAME!

- A.M.I.Mech.E.
- A.M.I.C.E.
- A.M.I.Prod.E.
- A.M.I.M.I.
- A.I.O.B.
- B.Sc.
- A.M.I.E.R.E.
- City & Guilds
- Gen. Cert. of Education
- Etc., etc.

PRACTICAL EQUIPMENT

- Basic Practical and Theoretic Courses for beginners in Radio, T.V., Electronics, Etc., A.M.I.E.R.E. City & Guilds
- Radio Amateurs' Exam.
- R.T.E.B. Certificate
- P.M.G. Certificate
- Practical Radio
- Radio & Television Servicing
- Practical Electronics
- Electronics Engineering
- Automation

INCLUDING TOOLS!

The specialist Electronics Division of B.I.E.T. NOW offers you a real laboratory training at home with practical equipment.

Ask for details.
B.I.E.T. SCHOOL OF ELECTRONICS



POST COUPON NOW!

Please send me your FREE 156-page "ENGINEERING OPPORTUNITIES"
 (Write if you prefer not to cut page)

NAME.....

ADDRESS.....

SUBJECT OR EXAM. THAT INTERESTS ME.....

THE B.I.E.T. IS THE LEADING ORGANISATION OF ITS KIND IN THE WORLD

WW-062 FOR FURTHER DETAILS.



Before you buy a
Timer/Counter
you must see the

ADVANCE
TC3



Measures frequency, period, phase angle, pulse width, time, resistance, or capacity.

The basic instrument, with PC1 plug-in module measures up to 10MHz at 10mV AC or DC coupled input with trigger level and slope selection.

PC2 plug-in extends frequency range to 100MHz at 50mV.

PC3 plug-in measures resistance and capacity values to 1%.

Seven decade variable time scale enables results to be multiplied into usable units, e.g., r.p.m., galls/hr., ft./secs.

the most versatile
British Timer/Counter
on the market

PRICES :

TC3, £600	PC2, £150
PC1, £50	PC3, £100


—but you can see this remarkable instrument, and try it, for nothing.
Ask for a demonstration.



ADVANCE ELECTRONICS LIMITED

Instrument Division, Roebuck Road, Hainault, Ilford, Essex. Telephone: 01-500 1000.

WW-063 FOR FURTHER DETAILS.

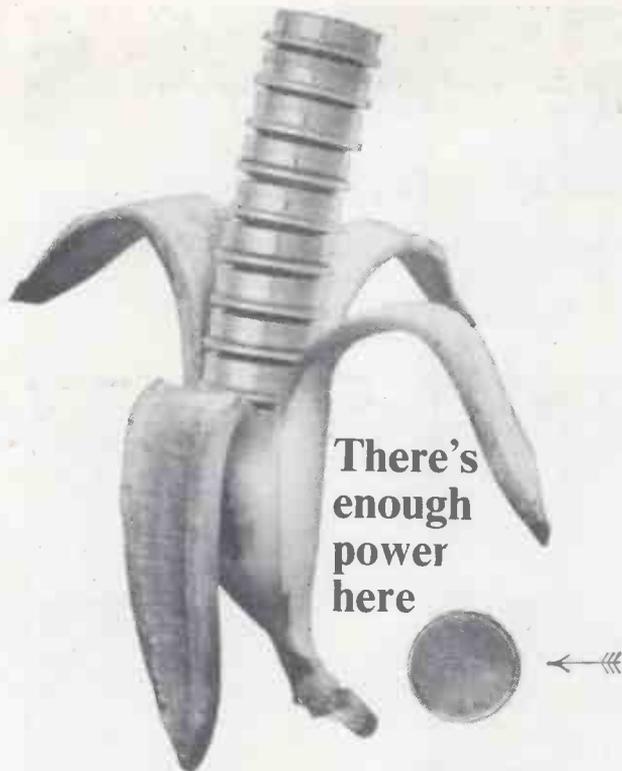

There's
enough
power
here

to run
a transmitter/receiver
for 12 hours—

and you can recharge it — again and again . . .

Now power is self contained. All kinds of instruments, tools, appliances are no longer dependent upon wires and cables. A small DEAC sealed nickel-cadmium accumulator (of the type illustrated) can supply power from 20 to 3,000 milli-ampere/hrs. where and when it is needed. Recharging is simple and direct and there is no deterioration in storage. Other types up to 23 ampere/hrs. are available.

Designers, think Deac. Full details are readily available. Send for them now by completing the coupon below.

➡ (For the record, a slice of banana can produce 20 calories of energy. This cell, the same size, is many thousands of times more powerful.)

Please send me details of your rechargeable accumulators.

NAME _____

ADDRESS _____

DEPT. _____

DEAC

DEAC (Great Britain) Ltd., Hermitage St., Crewkerne, Somerset.
Phone: Crewkerne 666. Grams: Tudorwerk Crewkerne.

M & P D2


WW—064 FOR FURTHER DETAILS.

N.C.BROWN LTD


MAIL ORDER DIVISION

pacesetters in storage equipment

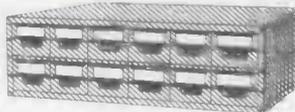36-DRAWER UNIT
'SPACE SAVER' 36A. Overall size 42" high, 24½" wide, 12" deep. 36 drawers. In best quality steel, stove enamelled dark green. **£12.0.0.**



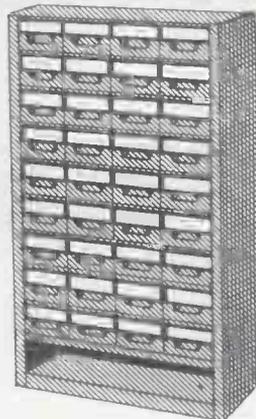12-DRAWER UNIT
POPULAR 12A
12 drawers in a compact nest measuring 9" high, 35" wide, 12" deep—an invaluable storage asset for the very economical price of only **£4.15.0.**



TO: N. C. BROWN LTD. Dept. E29
Heywood Lancs Tel. 69018
London: Dept. E29 5/6 Staple Inn, W.C.
Please send me a copy of your free illustrated catalogue.
Please send me a 36A drawer unit 12A drawer unit
Tick where applicable and send cash with order.

NAME _____

ADDRESS _____

WW—065 FOR FURTHER DETAILS.



KONTAKT
60

THE SPECIAL CLEANER
FOR INACCESSIBLE
CONTACTS

- ★ KONTAKT 60 cleans and protects all contacts
- ★ Eliminates high transition resistances
- ★ Prevents 'creep' currents
- ★ Does not affect plastic materials
- ★ In spray can with 5½ in. spray nozzle.

Other Kontakt products are:—

- 70 Protective Lacquer
 - 72 Insulating Spray
 - 75 Cold Spray for Fault Location
 - 80 Special Siliconized Polish
 - 100 Antistatic Agent for Plastics
- Write for full details of above complete range of Kontakt products to:—

SPECIAL PRODUCTS DISTRIBUTORS LIMITED

81 Piccadilly, London, W.1. GROsvenor 6482

WW—066 FOR FURTHER DETAILS.

RACAL Digital counters
combine versatility
with economy




SA.550 N.A.T.O. Codification 6625-99-971-8519

**Racal SA.550 100 Mc/s
Digital Frequency Meter**

Direct Frequency Measurements from signal levels as low as 100 mV are possible without tuning or interpolation. Measurement capability can be extended by the use of the active probe unit type SA.544.

- All Solid-State Design
- 8 Digit Inline Display
- 0-55°C. operating Ambient
- D.C. Logic Switching
- Digital Printout Facilities
- Internal or External Standard

The SA.540 Universal Counter Timer illustrated below is for time, period and frequency measurement up to 11 Mc/s.

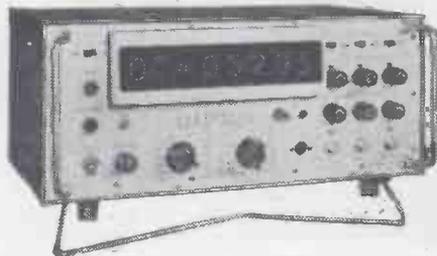

SA.540



Write for fuller details to:
Racal Instruments Ltd.,
Dukes Ride, Crowthorne, Berks
Tel: Crowthorne 2272/3 or
Bracknell 941 Telex

AI/A64



There's
enough
power
here



to operate
a hearing aid
for
8 hours—

and it's re-chargeable — again and again . . .

Now there's freedom for electrically powered tools, instruments and appliances. Neat, powerful DEAC sealed nickel-cadmium accumulators give manufacturers new scope for design, new potential for power that can come in pea-size packs (as well as a range of other sizes from 20 to 3,000 milli-ampere/hrs. capacity) with a notably flat discharge curve. Recharging is simple and direct, and there is no deterioration in storage. Other types up to 23 ampere/hrs. are available.

Talk to your designers about DEAC.

We have a folder full of vital information. Send for it now by completing the coupon below.



(For the record, a pea can produce .5 of a calorie of energy. This cell, the same size, is many thousands of times more powerful.)

Please send me details of your rechargeable accumulators.

NAME _____

ADDRESS _____

DEPT. _____

DEAC

DEAC (Great Britain) Ltd., Hermitage Street, Crewkerne, Somerset. Tel: Crewkerne 666. Grams: Tudorwerk Crewkerne.

M & P D1

WW—068 FOR FURTHER DETAILS.

TELEPRINTERS · PERFORATORS REPERFORATORS · TAPEREADERS EDITING & REPRODUCING SETS

Codes: Int. No. 2 Mercury/Pegasus, Elliot 803, Binary and special purpose Codes.



2-5-6-7-8 TRACK AND
MULTIWIRE EQUIPMENT



TELEGRAPH AUTOMATION AND COMPUTER PERIPHERAL ACCESSORIES

Picture Telegraph, Desk-Fax, Morse Equipment; Pen Recorders, Switchboards; Converters and Stabilised Rectifiers; Tape Holders, Pullers and Fast Winders; Governed, Synchronous and Phonic Motors; Teleprinter Tables and Cabinets; Silence Covers; Distortion and Relay Testers; Send/Receive Low and High



Pass Filters; Teleprinter, Morse, Teletext Paper, Tape and Ribbons; Polarised and specialised relays and Bases; Terminals V.F. and F.M. Equipment; Telephone Carriers and Repeaters; Multiplex Transmitters; Diversity,

Frequency Shift, Keying Equipment; Line, Mains Transformers and Suppressors; Racks and Consoles; Plugs, Sockets; Key, Push, Miniature and other Switches; Cords, Wires, Cables and Switchboard Accessories; Teleprinter Tools; Stroboscopes and Electronic Forks; Cold Cathode Matrices; Test Equipment; Oscilloscopes; Miscellaneous Accessories and Spares.

W. BATEY & COMPANY

Gaiety Works, Akeman Street, Tring, Herts.

Tel.: Tring 3476 (3 lines) Cables: RAHNO TRING
STD: OHH 282 TELEX 82362

WW—069 FOR FURTHER DETAILS.

Harmony in the home RECORD HOUSING



Folded Horn Enclosure £10.19.0.

Neilson Equipment Cabinet 18 gns

Housing Hi-Fi is our business . . . turntables, tape recorders, loudspeakers, tuners, amplifiers, records, tapes . . . there's a RECORD HOUSING cabinet to suit your equipment. Send for illustrated catalogue giving full details of over 20 different cabinets, plus stockists list (U.K. only) to:—

RECORD HOUSING (Dept. WW11)

Brook Rd, London, N.22. Tel: BOWes Park 7487.

WW—070 FOR FURTHER DETAILS.



for the first time
the reliability of metal oxide
film at 50 parts per million
temperature coefficient
electrosil NC resistors

Type	DEF 5115.1 Rating	Ohmic Range	Max DC Volts	Length (Ins.)	Diam. (Ins.)
NC.4	$\frac{1}{4}$ W	49.9 - 150K	200	0.281	0.098
NC.5	$\frac{1}{8}$ W	49.9 - 499K	250	0.416	0.148
NC.6	$\frac{1}{2}$ W	49.9 - 1 Meg	300	0.593	0.200

The Electro-sil NC resistor gives a lower temperature coefficient and tighter tolerances than ever previously available from a metal oxide resistor by a natural yield process.

Made by the unique Electro-sil glass-tin-oxide process, NC resistors introduce high-reliability into the high-precision resistor field. These resistors meet all conditions specified in pattern RFG7 of DEF 5115.1 and characteristic C of MIL-R-10509E.

- Very low and consistent noise level
- Impervious to moisture
- Wide operating temperature range
- Negligible voltage coefficient
- Excellent high frequency performance
- Extremely tight design tolerance

Send today for data sheet E2.05 which gives full details.



Electrosil Limited,
P.O. Box 37, Pallion,
Sunderland, Co. Durham.
Telephone: Sunderland 71481
Telex: 53273

STEREOSOUND

TRADE MARK

**IN-EXPENSIVE
HIGH FIDELITY!
THE
S.S.9**

now with optional
player unit
B.S.R. UA.70 or
GARRARD SP.25

**52Gns complete
with two speakers**

Made by STEREOSOUND the specialists in Stereo-
phonic Sound. Teak veneered cabinet with 81X watts
solid state stereo amplifier. Choice of player unit.
Space for cassette tape recorder or radio tuner. Two
matching loudspeakers, each with 9 in. elliptical high
fidelity unit and 4 in. tweeter. All for 52 gns. Ask
your Hi Fi specialist, radio retailer, or department
store to demonstrate.

Made by
STEREOSOUND Productions Ltd
Capital Works, Brighthouse. Tel.: 1755

London distributors:
HIGHGATE ACOUSTICS
71/73 Gt. Portland St., W.1. Tel.: Museum 2901



WW-072 FOR FURTHER DETAILS.

minitest MULTI-RANGE TEST SET

50uA movement 20,000 ohms per volt

for only **£7.17.6.** (Trade price)

(with leather case £8.12.6)

LOOK AT THESE FEATURES

- * D.C. sensitivity 20,000 ohms per volt
- * A.C. accuracy maintained up to 20 kc/s
- * A.C. sensitivity 2,000 ohms per volt
- * Additional decibel scale
- * D.C. accuracy $\pm 2\frac{1}{2}\%$ F.S.D.
- * Small size 5 $\frac{3}{4}$ " x 3 $\frac{3}{8}$ " x 2 $\frac{1}{8}$ "
- * A.C. accuracy $\pm 2\frac{3}{4}\%$ F.S.D.
- * Weight 18 ozs. * 20 ranges

Fits into the pocket. The Salford Minitest, a highly sensitive test meter for the measurement of A.C. and D.C. volts, current and resistance. The clarity of the scale is exceptional and the knife edge pointer ensures accurate reading. Housed in a tough Melamine cover, the movement is built into a pressed steel case which effectively screens it from external magnetic fields.

MINITEST	D.C. Amps	D.C. Volts	A.C. Volts
	0-1 Amp.	0-1,000	0-1,000
	0-100 mA.	0-250	0-250
0-	0-10 mA.	0-100	0-100
0-	200,000	0-25	0-25
0-	200,000	0-1 mA.	0-10
0-20 Megohms	0-50 uA.	0-2.5	0-2.5

All ranges are selected by a single twelve-position rotary switch. A separate slide switch is provided to change over from A.C. to D.C. ranges.



SALFORD ELECTRICAL INSTRUMENTS LIMITED
Peel Works • Barton Lane • Eccles • Tel: ECCles 5081 • Telex: 66711
London Sales Office: Brook Green, Hammersmith W.6. Tel: 01-603 9292
A Subsidiary of THE GENERAL ELECTRIC COMPANY LTD OF ENGLAND



Leaflet on request.

WW-073 FOR FURTHER DETAILS.

THE VARIAC* variable transformer is the most useful and versatile device ever developed for the control of a.c. voltage, or of current, power, heat, light, speed. It provides smooth continuous adjustment of output voltage from zero to line voltage and above, either hand-operated or motor driven.

Only Variac has Duratrak*—a patented track surface giving longer life, increased overload and surge capacity and maximum economy in maintenance.

There are over 600 Variac models and assemblies to suit virtually every possible requirement, ranging from small units for laboratory or instrument use to large ganged assemblies for high power 3-phase operation. The range includes low-voltage, high-frequency, dual-output and narrow-range types, open, covered, portable, metalclad and oil-immersed constructions, plus many special models. This is the largest range of variable transformers available today.

The technical superiority and dependability of Variac are the result of over 30 years of development and refinement since the introduction of the first Variac models—the *original* variable transformers.


**Variac* and *Duratrak* are registered trade marks*

Variacs are made in England by The Zenith Electric Co. Ltd. London, and exclusively distributed in the U.K., Eire and British Colonies by Claude Lyons Ltd,

Variac

REGD

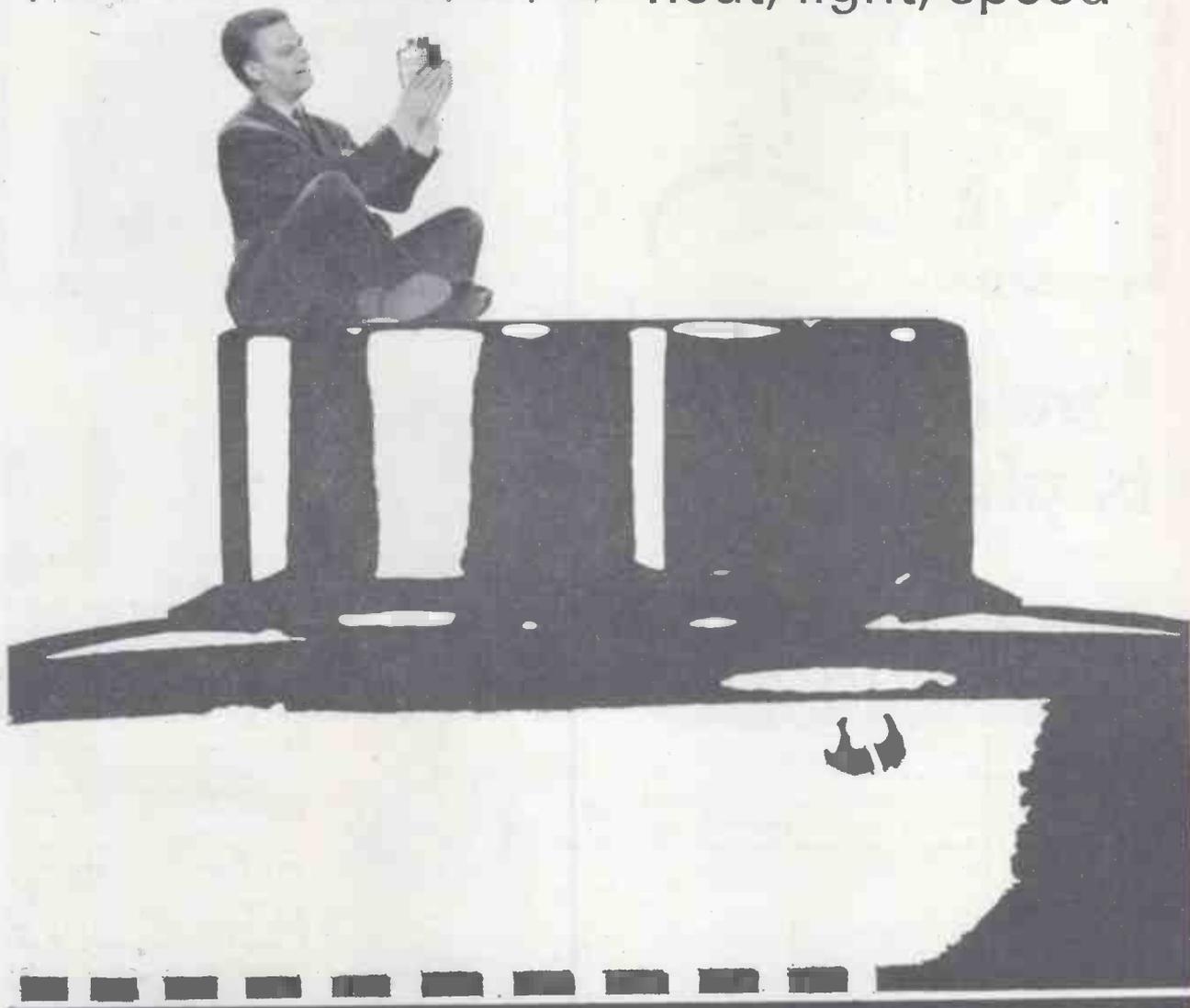the most useful and versatile device for controlling voltage, current, power, heat, light, speed



Write for comprehensive catalogue to Publicity Department, Hoddesdon


CLAUDE LYONS LTD

Valley Works, Hoddesdon, Herts Hoddesdon 67161 Telex 22724
76 Old Hall Street, Liverpool.3 MARitime 1761 Telex 62181

WW-074 FOR FURTHER DETAIL*

CL48

d'you
hear
there?..

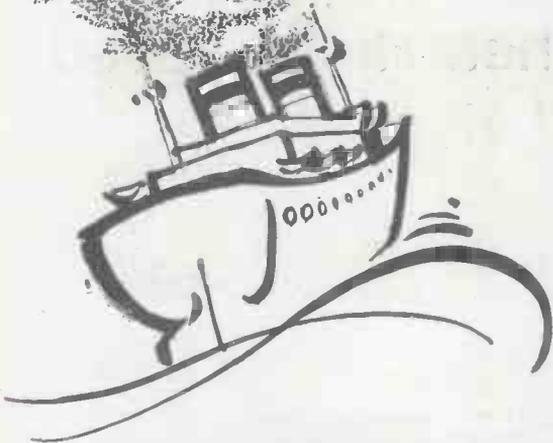

Public Address
is plain sailing
with

Pamphonic

We manufacture a comprehensive range of high quality equipment for trouble-free sound reinforcement aboard ship, where information and instructions must be heard clearly and distinctly. Our Technical Advisory Service is freely available to assist in the planning of sound systems suitable for the acoustic peculiarities in ships at sea.

Pamphonic for sound—naturally

Our Technical Advisory Service is freely available for your use.

Now Manufactured & Marketed by:-

PYE TVT LIMITED

GOLDHAMS LANE · CAMBRIDGE · P.O. BOX 41

Telephone: Cambridge 45115 · Cables: TeeVeeTee, Cambridge · Telex 81103

WW—075 FOR FURTHER DETAILS.


WHITELEY for acoustic hoods

All noisy environments such as factories, workshops, department stores and hotels require the facility of an acoustic hood which permits telephone conversations to be held without the interference of annoying background noises. Whiteley acoustic hoods are strongly made from resin bonded ply and finished in a cellulose enamel which makes these suitable for indoor or outdoor use.

Standard
Hood
Dimensions
25" high
20½" deep
24½" wide



Fitted with loudspeakers

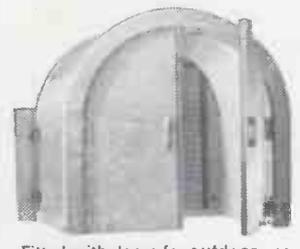

Fitted with doors for outdoor use

Also available with internal light and/or a storage shelf below hood

& directory holders



These attractive, and extremely functional directory holders will hold five directories neatly and securely, in individual swivel holders permitting easy identification and reference. The lower shelf provides additional storage space. The units are of cast alloy and are finished in an attractive grey epoxy resin enamel and constructed to strict G.P.O. design specifications.


Directory Holder Dimensions
17½" high x 13½" wide x 13½" deep

For further details please write or telephone.

WHITELEY ELECTRICAL RADIO CO. LTD
Mansfield · Notts. Telephone: Mansfield 1762-5

WW—076 FOR FURTHER DETAILS.

WB178

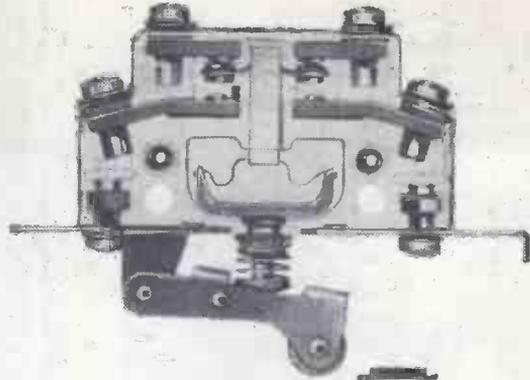

TRY THIS FOR SIZE

AND 10,000,000 SWITCHING OPERATIONS

Thorn Quick-Action Switch Units

Thorn Type S800 units will give up to 28,000 switching operations per hour dependent upon load and temperature. This rapid make and break action is fully maintained, without shimming. Despite the small dimensions, the units can be used for rated loads up to 16 amps, AC or DC. Service life is at least 10 million switching operations. In fact, the units have been bench tested to 40 million repeat cycles without failure.

Thorn Type S800 units are designed as standard components for universal application throughout the entire control-gear field, for incorporation in all types of switchgear. And, because they can be actuated through

a variety of tripping means, they serve as impulse generators for digital counters, warning systems, regulating and monitoring equipment, and as switching elements in small-scale contactors, toggle and diaphragm-operated switchgear, etc.

The units are totally enclosed in transparent, dustproof housings which enable the state of the contacts to be examined at any time without dismantling. Standard contacts are of hard silver. Shown is the S800 d. actual size.

For full details write to:




Thorn Special Products Ltd


Great Cambridge Road, Enfield, Middx. Tel: HOW 2477
A member of the Thorn Electrical Industries Ltd group of companies

Bullers CERAMICS

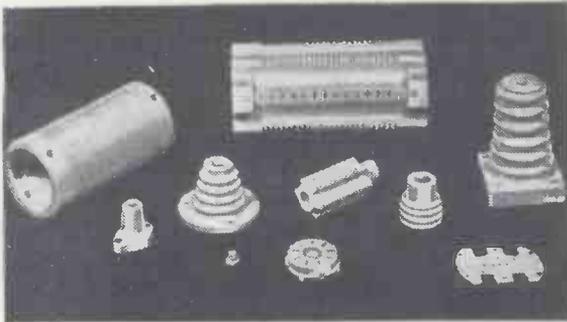for the **ELECTRONIC INDUSTRY**
(and Electrical Appliance Manufacture)



Frequelex—for high-frequency insulation.

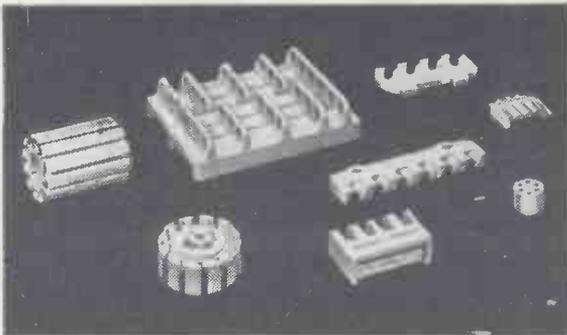

Refractories for high-temperature insulation.



Bullers porcelain for general insulation purposes.

Meticulous care in manufacture, high quality material, with particular attention applied to *dimensional precision and accuracy*, explain the efficiency and ease of assembly when using Bullers die pressed products. Write today for detailed particulars.

BULLERS LIMITED

Milton, Stoke-on-Trent, Staffs.

Phone: Stoke-on-Trent 54321 (5 lines)

Telegrams & Cables: Bullers, Stoke-on-Trent


London Office: 6 Laurence Pountney Hill, E.C.4

Phone: MANSion House 9971

WW—078 FOR FURTHER DETAILS.

5,000 catchy answers to one basic problem

(Here are some of them)

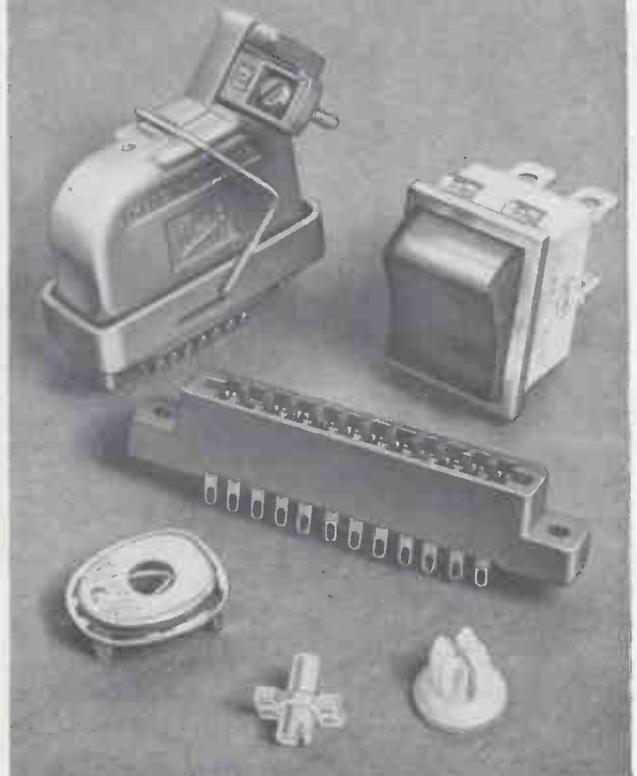

Whenever there's a problem of connection you'll find Carr Fasteners coming up with the answer. Currently they're working on 5,000 different answers and producing a total of 25 million parts a week. Most of them are small and simple, but what they lack in inches they make up for in ingenuity — so don't underestimate them. In fact you'll find them in anything from toys to furniture, from cars to electronic equipment. You could probably make use of them yourself.

CARR FASTENER CO LTD

the firm with the best connections

Stapleford, Nottingham Telephone Sandiacre 2661

Sales offices: Wembley, Birmingham, Sale, Glasgow

WW—079 FOR FURTHER DETAILS.

CARR FASTENER

UNITED CARBS GROUP

NOW—the PLESSEY 700 radio telephone with 19" rack mounting

(and it's even easier to install and maintain)


A radio telephone link is cheaper, and easier to install, than a good quality copper wire circuit at 3 miles.

For emergency uses, or over difficult terrain, line systems may be impossible or too costly to install. In any situation Plessey can provide fully line integrated radio telephone systems with these benefits—

low installation costs, less maintenance, greater reliability.

And now a rack mounted version with even greater access—the front panel hinges down for routine maintenance checks. Full subscriber and


exchange integration facilities are provided by plug-in circuit cards which can easily be changed to meet different requirements. 5 watt amplifier, party line operation, subscriber check metering and coin box operation can also be incorporated. The 700R operates in the frequency bands up to 470 Mc/s, is fully transistorised and can be powered by batteries, ac/dc converter, thermo-electric or solar converters. Plessey offers a comprehensive system planning, surveying and installation service. For further information, contact: AT&E (Bridgnorth) Limited, Bridgnorth, Shropshire, England. Telex: 33373.

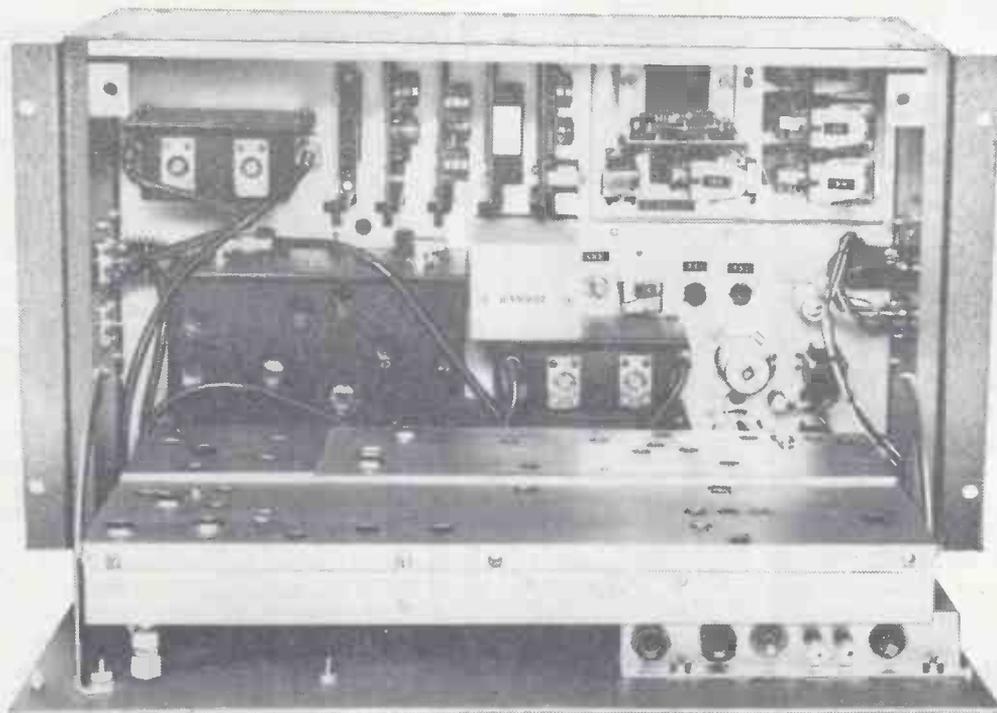

PLESSEY Electronics



*Expensive Units
at
well below cost*

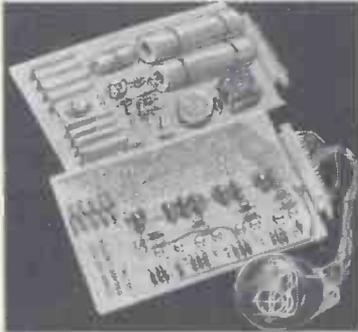


DECADE COUNTER AND DIGITRON DRIVE UNIT

A fundamentally stable divide by ten decade counter, thoroughly reliable and capable of directly driving a digitron type GR 10K. Designed on a printed circuit board measuring only 7½ in. x 5 in. several units can be "plugged" into a cabinet using standard guide rails and edge connectors, thus creating an efficient and reliable digital counter at reasonable cost.


Power requirements: Plus 150 v. at 4.5 mA. Minus 70 v. at 150 mA. Input requirements: Negative pulse not less than 100 mV. Max. freq. 40 Kc/s.

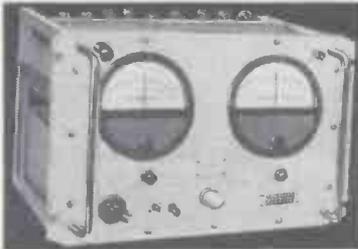Full details on request together with details of new low price D.C. output power supply units for transistor applications (as illustrated above).




SOLARTRON COMPONENT RESOLVER VP.748

Truly an instrument with fantastic capabilities, here, in one unit, is the means to monitor characteristics of loudspeakers, transformers, synchros and associated components; gas analysis. Frequency range 0.5 to 1,000 c/s. and voltage ranges from 50 mV. to 150 v. Large thermo-couple meters (6in.) provide Reference and Quadrature outputs and 1.0 pk/pk output for oscilloscopes is provided on the front panel. Power requirements 115 v. or 200-250 v. 50 cycles. Price £250.

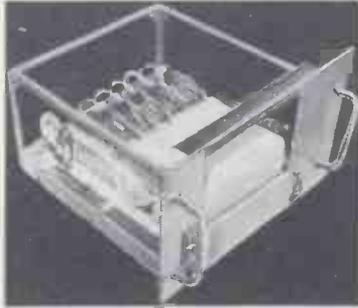

SEFRAM RAPIDGRAPH PEN RECORDER

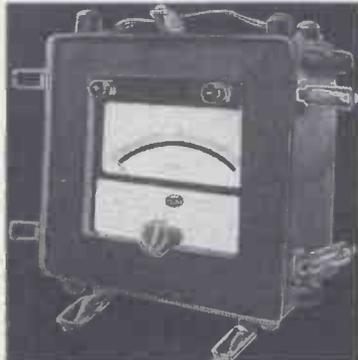Five Channel. Paper Speed. 1 through 100 mm./sec. in ten steps with 40 mm. chart/channel. Pen f/c max. D.C. 60 c/s. Pen sensitivity. 6mA at 2 v. for f.s.d. Event markers. Mains operated 240 v. 50 c/s. Size 19in. x 12in. x 18in. Weight 47 lbs. First class professional instrument in brand new condition at well under maker's list price. £270.



SANGAMO WESTON D.C. VOLTMETER TYPE AL5442

A precision instrument especially designed for use in Standards Laboratories for the calibration of D.C. volts 0-400 at 1,000 ohms per volt. This unit has been calibrated to B.S.89 P.R. limits and has been designed to the highest Ministry specification. Mirror scaled, this unit cost the Ministry well over £40. Price £17/10/-.

NOW READY— OUR NEW PLUGS AND SOCKETS CATALOGUE


Greatly enlarged 72 page second edition—send for a copy now!

LIND-AIR ELECTRONICS LTD

53 Tottenham Court Road, London, W.1

Telephone: LANgham 3653 (10 lines) Telex: 27931

WW—081 FOR FURTHER DETAILS.

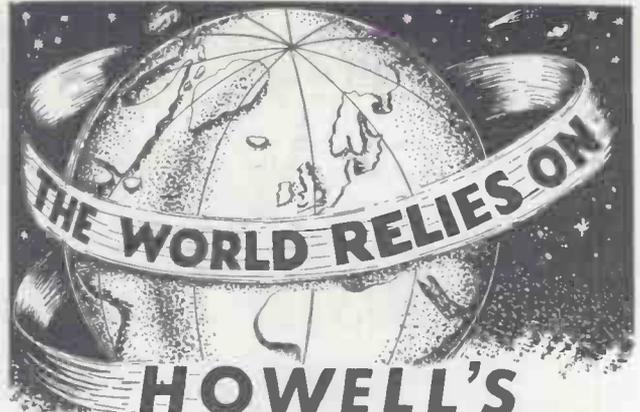

HOWELL'S TRANSFORMERS

MINISTRY OF AVIATION APPROVED INSPECTION.

TRANSFORMERS

STANDARD RANGE OR TO YOUR DESIGN
TOROIDAL — 'C' CORE — PULSE — MATRIX

CHASSIS— CABINETS & PRECISION METALWORK
ELECTRONIC ASSEMBLY

HOWELLS RADIO LTD.


MULBERRY STREET, MANCHESTER, 15

MOSS SIDE 2000-2434

WW—082 FOR FURTHER DETAILS.

COIL WINDING MACHINES

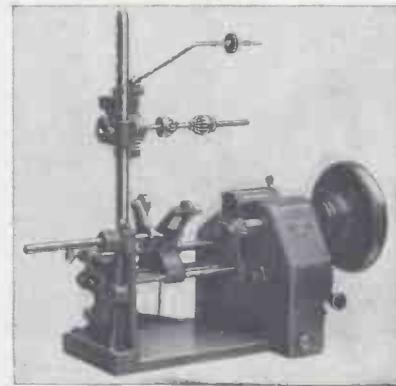for coils up to 6½" diameter to 6" long. 20-47 S.W.G.



Model "Q" standard.

The feed is fully automatic and the nut is in constant contact with the lead-screw. The reversal of the carriage is obtained by reversing the lead-screw rotation. Two lead-screws are used to give the large range of feeds and a lever on the carriage nut brings either into action. This lever has a neutral position which enables the carriage to be put at any position on the lead-screws. Ball bearing feed wheels are employed. This machine may be fitted for double coil and double end drive, also for "Pyramid Winding."

Enquiries are invited.

ETA TOOL CO. (LEICESTER) LTD.


29A, WELFORD ROAD, LEICESTER. Telephone 56386

WW—083 FOR FURTHER DETAILS.

PYE—the first name in
mobile radio put
BRITAIN two years
ahead with the—



PYE POCKETFONE

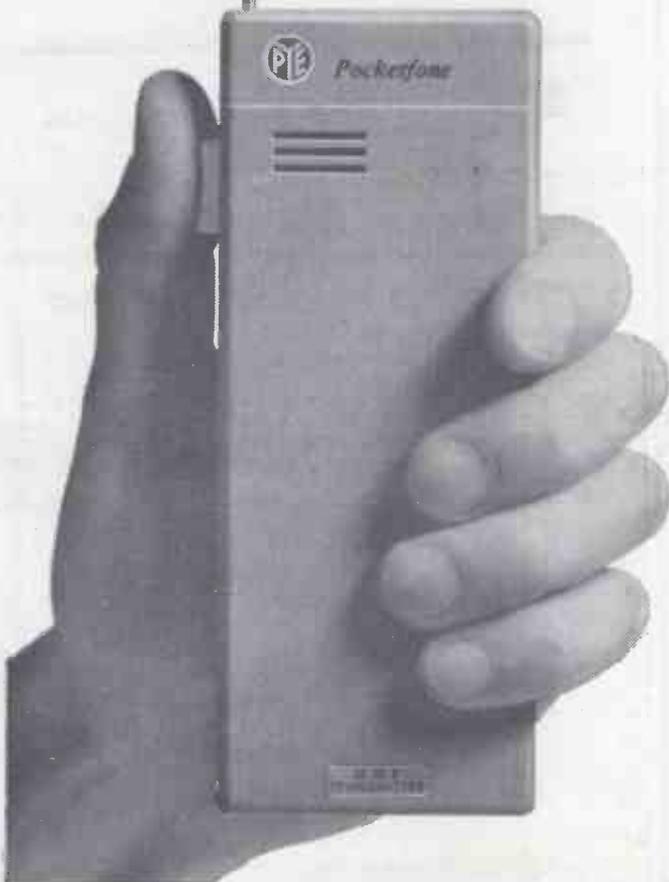

Pye Telecommunications Limited, winner of the Queen's Award in 1966 for exports of radiotelephone equipment to more than 100 countries, now place their world-wide sales and service organisation behind the Pye Pocketfone—the world's first u.h.f. pocket radiotelephone system.

Performance, reliability and impressive signal penetration in built-up areas have been proved under arduous service conditions by police and security services in Britain and overseas.

The Pye Pocketfone has a myriad applications in government, industry and commerce. Export orders emphasise Britain's two-year lead in this new and vital field of radio communication. Pye and Pye alone are organised and able to meet demands for any application—anywhere in the world.



PYE TELECOMMUNICATIONS LIMITED · CAMBRIDGE · ENGLAND · TELEPHONE CAMBRIDGE (OCA3) 61222 · TELEX 81166

WW—084 FOR FURTHER DETAILS

PS
C

Record it...and hear the play-back simultaneously on the Brenell Mk5 Type M




—and be sure it sounds superb!

Loudspeaker tape monitoring, enabling you to check and adjust your recording as it is being made, is only one of the assets of this outstanding recorder. All the features the discriminating recordist has come to expect from Brenell tape recorders are here—and many others, too. Four speeds (frequency response 40-20,000 c/s at 15 i.p.s.), mixing, superimposing, hinged deck, pause control, safety erase lock, 8½" dia. spools, etc. The price? 93 gns. For the stereo enthusiast there is the STB2, £150.

Write for illustrated leaflet WW11

The key to Brenell's leadership— The Mark 5 Series 3 Deck

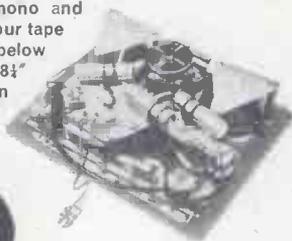Used on all Brenell models mono and stereo. Provision for 4 heads. Four tape speeds. Wow and flutter content below 0.10 at 7½ i.p.s. Fast rewind and 8½" dia. reel accommodation. (Version available to take up to 10½" NAB reels) Price £34.0.0.



Brenell

BRENELL ENGINEERING CO. LTD.
231-5 LIVERPOOL ROAD, LONDON, N.1. NOR 8271 (5 lines)
GD611

WW—085 FOR FURTHER DETAILS.

PROTECT ELECTRONIC EQUIPMENT AGAINST MALFUNCTION OR BURNOUT...



No. KV-115/220 AC

Sintronic CENSORVOLT AUTOMATIC VOLTAGE MONITOR

Guards primary power lines to prevent equipment abuse in
• RADIO-TELEPHONES • MARINE RADIOS • BROADCASTING TRANSMITTERS
• TELEPHONE & TELEGRAPH EQUIPMENT • AIRPORT RADIO INSTALLATIONS

Provides positive protection for all types of electronic equipment against high or low line voltage. Continuously monitors the primary line voltage and automatically disconnects the equipment when the line voltage reaches the preset cut-off point. Automatically reconnects the equipment when the line voltage returns to a safe level. Warning light and buzzer alarms.

Voltage damage or malfunction of electronic equipment can be costly . . . protect your electronic gear with Censorvolt.

Write Dep't. WW for complete information

BROADCAST / COMMUNICATIONS · DIVISION
Singer Products COMPANY INC
95 Broad Street, New York, N.Y. 10004 CABLE: EXREGNIS
WW—086 FOR FURTHER DETAILS.

Two important new ILIFFE technical books

Transistors for Technical Colleges

L. Barnes M.Sc., Tech. A.M.I.E.E.

This book is the ideal student's guide to practical design aspects of electrical engineering. An easy-flowing text takes the reader swiftly through a whole range of devices and circuits—including the Zener diode and the thyristor—and he is encouraged to design simple circuits by a graphical approach. Separate reference and symbol sections area also included.
25s. net, by post 26s. (limp covers), 192 pp. 87 illustrations.
42s. net, by post 43s. 1d. (case bound).

Feedback Circuit Analysis

S. S. Hakim, Ph.D., B.Sc., A.M.I.E.E.

What are the real effects of feedback on the amplifier's circuit performance? The author, an experienced lecturer on feedback circuit analysis, examines the classical theory, discusses its limitations—and advances his own, more generalized explanation. He also refers to the problem of stability in detail. Electronic graduates and engineers everywhere will find this book both fascinating and factual.

95s. net, by post 97s. 400 pp. 306 illustrations.

obtainable from leading booksellers

ILIFFE Books Ltd.

DORSET HOUSE STAMFORD STREET LONDON S.E.1.
WW—087 FOR FURTHER DETAILS.

THERE IS A **SHURE** ANSWER TO EVERY SOUND PROBLEM


COMMUNICATIONS 414A

Controlled magnetic hand microphone providing a clear, crisp, natural voice response of high intelligibility. Rugged and dependable, ideally suited for outdoor - indoor public address and communications. Frequency response 200 to 4,000 cps. High impedance and high output.



PROFESSIONAL RECORDING SM5A

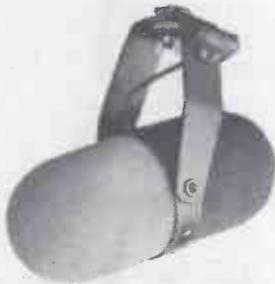Dynamic microphone for studio and location work. Cardioid directivity. Effectively rejects background noise and provides natural dialogue or vocal music pickup. Also suitable for scoring. Frequency response 50 to 15,000 cps. Perfectly balanced and dependable under all operating conditions.



AMATEUR RADIO 444

Designed for radio communications, providing optimum performance from single sideband transmitters as well as AM and FM units. Response cuts off sharply below 300 cps and above 3,000 cps, ensuring maximum speech intelligibility and audio punch to cut through noise and interference.



PROFESSIONAL ENTERTAINER 585SA

Dynamic microphone with an effective filter to protect against wind and "pop". Features fine reproduction of music and voice. Ideal for use with high quality sound systems and tape recorders. Eliminates squeal caused by feedback and overcomes poor acoustic conditions, indoors or outdoors.



SHURE

Setting the world's standard in sound.

Shure Electronics Limited, 84 Blackfriars Road, London SE1. Tel: WATerloo 6361.
WW-088 FOR FURTHER DETAILS.

+ + + MARCONI INSTRUMENTS

WIDE RANGE OF EQUIPMENT

FOR AUDIO + + IMPEDANCE +

+ FREQUENCY SWEEP + + + +

+ + FREQUENCY AND TIME +


+ + UHF MEASUREMENTS + + + +

DETAILS BY RETURN +

FREQUENCY & TIME


Counter/Frequency Meter TF 1417/2
Measures: Frequency up to 10 MHz,
Waveform Period up to 5 MHz,
Time Intervals down to 0.2 μ sec.
Price: £800

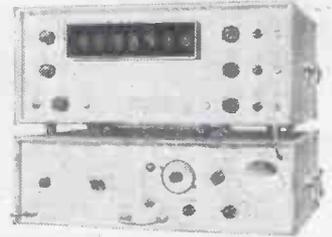Frequency Converter TF 2400/1
Heterodyne unit extending the range of
10 MHz counter. 10 to 510 MHz tuning
range, 20 kHz to 10 MHz as amplifier.
Price: £365




IMPEDANCE

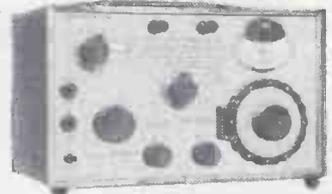Universal Bridge TF 2700
Measures: Inductance: 0.1 μ H to 110 H
Capacitance: 0.5 pF to 1,100 μ F.
Resistance: 0.01 Ω to 11 M Ω .
Price: £85



FREQUENCY SWEEP

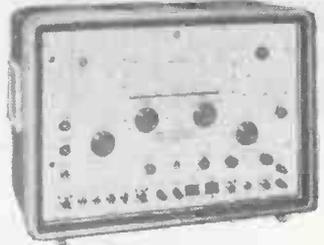20 MHz Sweep Generator TF 1099
Sweep Range: 100 kHz fixed to upper
limit variable up to 20 MHz. Compensated
probes for differential measurements.
Price: £325



MARCONI INSTRUMENTS LIMITED

WW-089 FOR FURTHER DETAILS.


OFFER IMMEDIATE DELIVERY

AUDIO EQUIPMENT

TF 2160 Series Attenuators
0 to 111 dB, D. C. to 550 kHz.
Prices: TF 2160 £120, TF 2161 £100,
TF 2162 £55



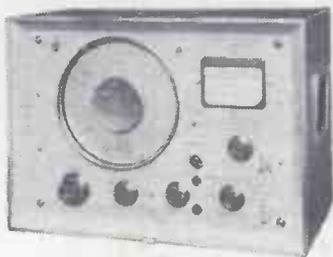Wide Range RC Oscillator TF 1370A
10 Hz to 10 MHz sinewave, 10 Hz to 100
kHz squarewave, Less than 1%
distortion, 31.6 V output up to 1 MHz.
Price: £275




MF Transmission Measuring Set TF 2333
Signal Source 30 Hz to 560 kHz,
Attenuator 70 dB in 1 dB steps,
Level Meter -70 dBm to +25 dBm.
Price: £335



Sensitive Valve Voltmeter TF 2600
1 mV f.s.d. to 300 V f.s.d., 50 Hz to
5 MHz.
Price: £121



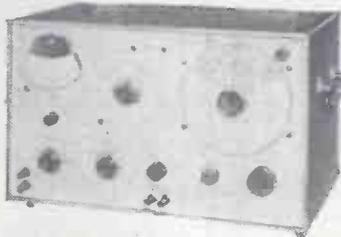
Wave Analyser TF 2330
(Selective Voltmeter), 20 Hz to 50 kHz
tuning range, 6 Hz bandwidth, 65 db
rejection at 40 Hz off tune, 30 μ V to
300 V voltage range.
Price: £550




RC Oscillator TF 1101
20 Hz to 200 kHz, Less than 0.5%
distortion, 0 to 20 V into 600 Ω .
Price: £145



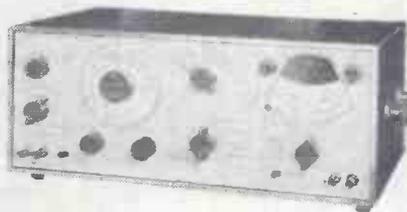Distortion Factor Meter TF 2331
20 Hz to 20 kHz tuning range.
Reads harmonics up to 100 kHz.
Measures distortion down to 0.01%.
Price: £240



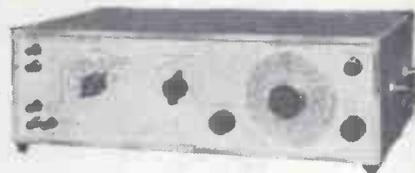
Tunable Rejection Filter TF 2334
Increases rejection ratio of TF 2330.
Can also be used for other purposes.
20 Hz to 20 kHz tuning range,
80 dB rejection ratio.
Price: £140



ST. ALBANS, HERTS. TEL: ST. ALBANS 59292. TELEX 23350


WW-090 FOR FURTHER DETAILS.

TC 326

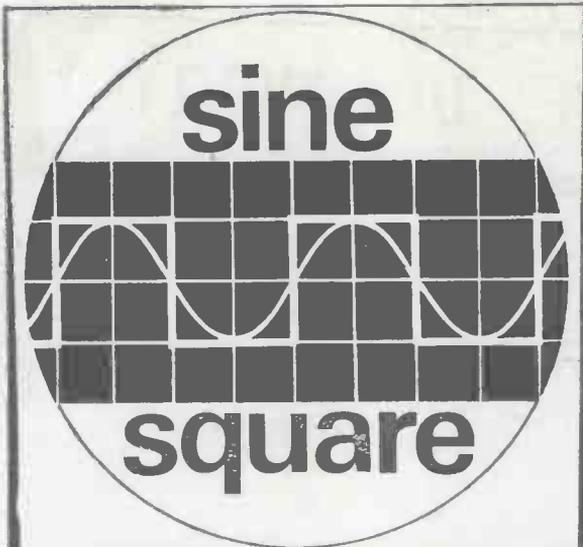

TYPES L.F. AND L.F.M. OSCILLATORS

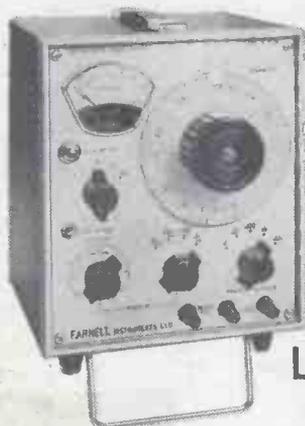- ★ Wide frequency range 1 c/s—100 Kc/s.
- ★ Sine or Square wave thermistor stabilised output.
- ★ Output continuously variable from 200 micro volts—12 volts peak to peak.
- ★ Fully transistorised circuits.
- ★ Suitable for mains or battery operation.



L.F.
£49

L.F.M.
£58

Sales Engineers in London area and all parts of the U.K.



FARNELL INSTRUMENTS LTD.
SANDBECK WAY, WETHERBY, YORKS. Tel. 2691/2/3/4

WW—091 FOR FURTHER DETAILS.



Eddystone SLOW MOTION DIALS

Catalogue No. 598 epicyclic dial

This full vision dial incorporates an epicyclic, ball-bearing drive mechanism of improved design

and giving a reduction ratio of approximately 10 to 1. The movement is smooth and free from backlash. Dial escutcheon measures 6" long by 4 1/4" wide, finished ripple black. Four lines are provided on the semi-circular scale for individual calibrations, the outer line being marked from 0 to 100 over 180°. Supplied complete with black instrument knob 2 1/4" diameter.



Catalogue No. 898 gear driven dial

A high grade assembly for precision instrument applications. Gear driven, flywheel-loaded mechanism, with a reduction ratio of 110 to 1, giving smooth, positive control.

instrument knob. Complete with fixing screws and mounting template.

Pointer travel is 7". A circular vernier scale, marked 0 to 100, is read in conjunction with the lowest line on the main scale, which has five lines for individual calibration. Overall dimensions 9 1/4" by 5 1/2". Diecast escutcheon finished glossy black to match 2 1/4" diameter



Eddystone Radio Limited

Eddystone Works, Alvechurch Road, Birmingham 31

Telephone Priory 2231 Cables Eddystone Birmingham Telex 33708

WW—092 FOR FURTHER DETAILS.

LTD/ED 8



NEW

ORRTRONICS 8 TRACK DELUXE STEREO AUTOMOBILE TAPE PLAYER

Enjoy your favourite music played continuously in superb stereo hi-fidelity. Fully transistorized—no fade, no static. Beautiful black and chrome case matches all interiors. Only 7" wide and 2 3/4" high. Can be quickly and easily installed in any car, truck, boat or airplane with a 12 volt system. Completely automatic operation.

Simply insert a sealed plastic magazine tape cartridge and it plays continuously until shut off. Long-playing tape cartridges are tamper-proof, unbreakable and totally resistant to heat and cold. Choose from a vast library of Orrtronic tape cartridges featuring all types of music by your favorite artists.

Write for free catalog and price schedule

MORHAN
EXPORTING CORPORATION

485 Broadway • New York, N.Y. 10013 • Cable: "Morhanex"

WW—093 FOR FURTHER DETAILS.

take your pick!




from IR semiconductor centers

Over 100 IR semiconductor devices are available from your dealer, many with free instruction manuals and project and experiment details.

Look for the floor-standing 'Semiconductor Center', or the counter-top 'Minicenter'.

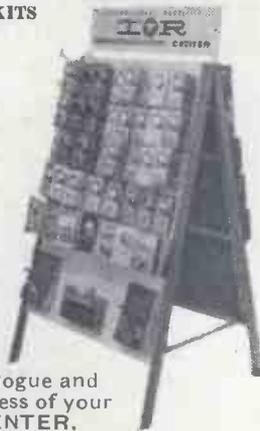- EXPERIMENTER SEMICONDUCTOR KITS
- MOUNTING KITS AND HEAT SINKS
- SILICON BRIDGE RECTIFIERS
- UNIUNCTION TRANSISTORS
- SELENIUM PHOTO CELLS
- INSTRUMENT RECTIFIERS
- AUTOMOTIVE RECEIFIERS
- SILICON SOLAR CELLS
- SILICON RECTIFIERS
- GERMANIUM DIODES
- THYRISTORS (S.C.R.)
- ZENER DIODES
- TRANSISTORS
- SELECIUM STACKS




Write for the free illustrated catalogue and price-list, also the name and address of your nearest IR SEMICONDUCTOR CENTER.

INTERNATIONAL RECTIFIER
HURST GREEN · OXTED · SURREY TEL: OXTED 3215

Dealers — write for details of how you can start your own IR SEMICONDUCTOR CENTER.



WW-094 FOR FURTHER DETAILS

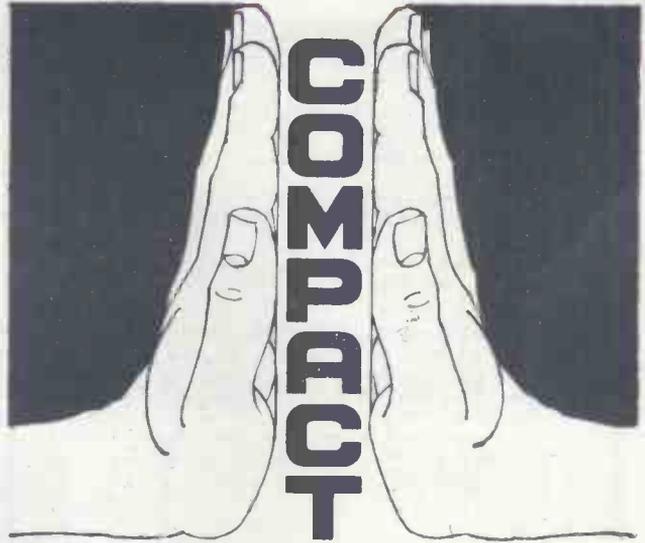

SOLID STATE AUDIO & ULTRASONIC TEST SET

AWA's (for Amalgamated Wireless Australasia, Ltd) model A211 is geared to meet any test requirements. Completely portable, this Audio and Ultrasonic Test-Set was designed to test broadcast, telephone and marine sonar sounding equipment. It provides all the facilities necessary to analyse and measure the characteristics of audio and ultrasonic networks in individual units, complete systems or separate stages within a single unit. Measurements can be made of the following characteristics:

- Output voltage versus input voltage as a function of frequency.
- Total power output versus input signal voltage as a function of frequency.
- Harmonic distortion and phase shift between input and output as a function of frequency and input/output level
- Noise output voltage signal input.

Put AWA equipment to the test.



AWA MODEL A211

For further information, contact your nearest AWA agent. Ask him for details on the complete line of AWA Test Equipment.

AMALGAMATED WIRELESS (AUSTRALASIA) LIMITED

P.O. Box 2516, Sydney, N.S.W., Australia

LIVINGSTON LABORATORIES LTD.
BRITAIN

CANADIAN MARCONI COMPANY
CANADA

WW-095 FOR FURTHER DETAILS.

AUDIO AMPLIFIER

12 Volt with 15 W. Output

Designed specially to give pleasing results on music and speech

Common emitter, class B output stages, with maximum efficiency choke coupling to 15 ohm speaker lines; temperature stabilised and direct coupled pre-amplifier stages with liberal feedback.

All output and input terminations are fully floating, thus enabling layman or skilled engineer to be equally confident in the simple matter of coupling up for use.

FULL DETAILS OF THIS AND EQUIPMENT BY RETURN OF POST



E. K. ELECTRONICS (I.A.) LTD: Brotherton, Knottingley, Yorks.

WW-096 FOR FURTHER DETAILS.

ULTRASONIC CONTROL

more versatile than photo-electric systems

**SELECTIVE
COMPACT
FLEXIBLE**

An exceptionally compact, versatile and flexible ultrasonic transmitter and receiver, which can be mounted in any position, available for mains or internal/external battery power. Selective circuit avoids possibility of random response to other ultrasonic sources. Wide range of applications in production monitoring, counting, alarm and control systems of all kinds, with the dual advantage over photo-electric systems that receiver response is unaffected by fog, grit, dust, steam, etc., and that the equipment will "see" even translucent objects. External equipment such as counters, alarms, indicators can be operated remotely by the receiver.

The versatility of the equipment is extended by the feature that two modes of operation can be used, direct or reflected.

Direct
Transmitter and Receiver aligned to face each other. Range up to 30 feet—internal relay contacts close when transmitter ultrasonic beam is interrupted.



Reflected
Transmitter and Receiver in close proximity and facing same general direction. Range up to 12 feet—transmitter relay contacts close when beam is interrupted and reflected to receiver.



- Size:** Transmitter { 4½ in. x 2 in. x 3 in.
Receiver
- Price:** Model BO/1 (Battery operated) 19 gns.
Model MO/1 (Mains operated) £26
(Set of TX and RX in each case)
- Supply:** Model BO/1 Ever Ready PP7.9V.
Model MO/1 240 V. 50 c/s A.C.
- Consumption:** Receiver 9 V. 2 mA. (15 mA. on full operation) Transmitter 9 V. 4 mA.


Nuray new from



Manufactured by **BEULAH ELECTRONICS LTD.**
A Member of the D.T.V. Group of Companies
Dept. WW, 126 Hamilton Road, London S.E.27

Tel.: Gipsy Hill 6166

WW-097 FOR FURTHER DETAILS.

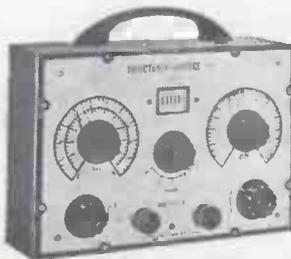

**INDUCTANCE
BRIDGE
MODEL 66**


NOMBREX TRANSISTORISED INSTRUMENTATION

- ★ Signal Generator 27 £10.16.9
- ★ Power Supply Unit 61 £6.14.6
- ★ C.R. Bridge 62 £9. 6.9
- ★ Audio Generator 63 £17. 1.9
- ★ Inductance Bridge 66 £18. 6.9

All prices include battery, post and packing. Prompt Delivery.

S.A.E. FOR TECHNICAL LEAFLETS

TRADE & EXPORT ENQUIRIES INVITED

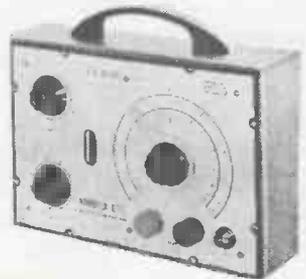


**C. R. BRIDGE
MODEL 62**

NOMBREX LTD. ESTUARY HOUSE, CAMPERDOWN TERRACE, EXMOUTH, DEVON. Phone: 3515

WW-098 FOR FURTHER DETAILS.

FOR the first time

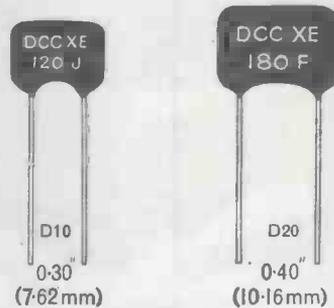

Dip-coated Silvered Mica Capacitors to humidity classification DEF-5312-H5 and BS.2132 Part 1: 1963-55/125-21... at dipped prices, too!

By means of a revolutionary new process, Dubilier have succeeded in producing *dip-coated* Silvered Mica Capacitors which, for the first time, meet DEF and BS humidity classification—and, moreover, at relatively low cost!

The capacitors are space and weight-saving—offer standard wire spacing for printed circuit boards. To dip into our store of knowledge on the subject—ring ACO^{rn} 8671.

Housing

Tough non-flammable thermosetting material.

Capacitance Range

At the preferred series values.

Type D10—15pF. to 1,000pF. at 350V d.c. peak.

Type D20—100pF. to 4,700pF. at 350V d.c. peak.
200pF. to 2,200pF. at 750V d.c. peak.

Capacitance Tolerance

±10%, ±5%, ±2%, ±1% and ±0.5% (or ±1pF. whichever is greater).

Temperature Range

−55°C. +125°C.

Insulation Resistance

< 25,000MΩ at 20°C.

Power Factor

At 100Kc/s to 1Mc/s.
< 0.1% above 100pF.

WW—099 FOR FURTHER DETAILS.

< 0.2% above 50pF. up to and including 100pF.

< 0.3% above 5pF. up to and including 50pF.

Stability

0.05% or 0.1pF. whichever is the greater.


Temperature Co-efficient

−10 to +50 p.p.m./°C. 20°C. to +125°C.

DUBILIER CONDENSER COMPANY (1925) LIMITED
Ducon Works, Victoria Road, North Acton,
London W.3. Telephone: ACO^{rn} 8671.


DUBILIER

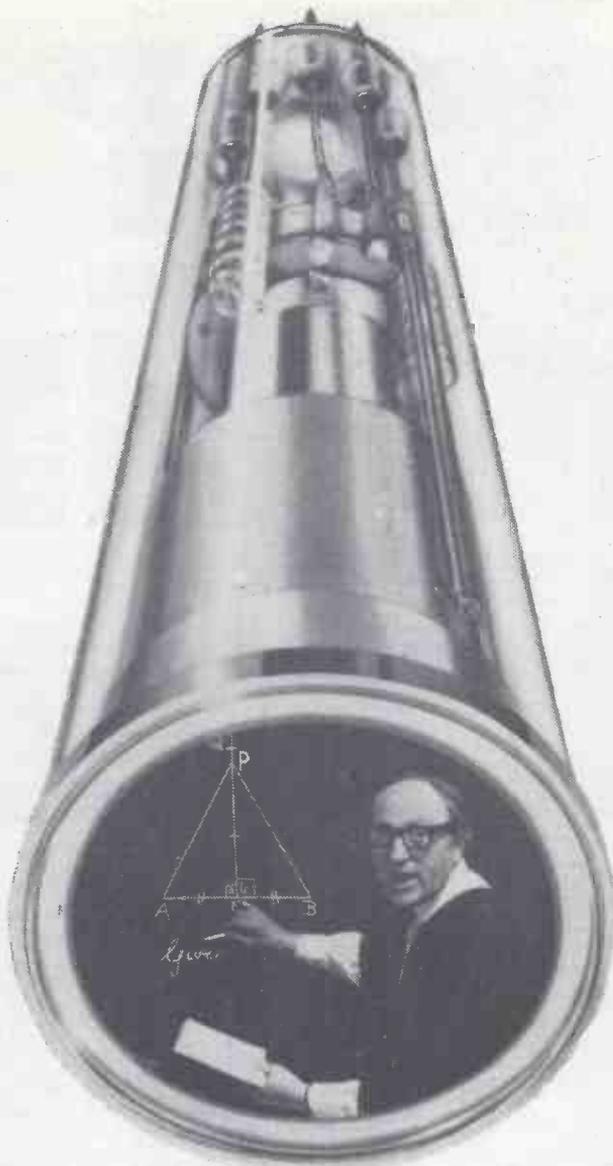Leaders in capacitor development for more than fifty years.



The new teacher

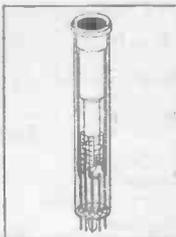English Electric Valves supply the vidicons for most of the closed-circuit TV cameras made in Britain, including those used in education. Their popularity with TV camera makers and users is because EEV vidicons give unusually high resolution, high sensitivity and short lag, besides being proved reliable. In many applications lives of more than 8,000 hours have been achieved. Such



reliability is essential if hundreds of school children are not to gaze at a blank screen halfway through the geometry lesson. EEV vidicons are available with two different values of heater current, 6.3V/600mA and 6.3V/95mA, and with either separate mesh or integral mesh construction. For further technical information and the name and address of your nearest stockist write to:

ENGLISH ELECTRIC VALVE COMPANY LIMITED
 CHELMSFORD, ESSEX, ENGLAND. TELEPHONE: CHELMSFORD 53491 TELEX: 99103
 WW-100 FOR FURTHER DETAILS.

AP275



the **ULTIMATE** in sophisticated amateur equipment

DAVCO DR-30 COMMUNICATIONS RECEIVER

Compact, high performance, all solid-state receiver for amateur applications featuring **FIELD-EFFECT TRANSISTORS**

Developed especially for the sophisticated amateur who knows enough to demand the finest. The DAVCO DR-30 is amateur-designed and professionally engineered to provide exceptional performance under extreme environmental conditions and combines advanced design with simplicity of operation. It provides all the latest state-of-the-art techniques in an ultra-compact unit (just 4" h x 7-1/8" w x 6" d). Every DAVCO DR-30 is hand-crafted, inspected on the line during production no less than 60 times and put through rigorous final testing before serial number and warranty are

awarded. The DR-30 utilizes Field-Effect Transistors in RF stages to assure greater sensitivity, superior image rejection and unbelievable freedom from cross-modulation or strong-signal overloading. You'll dig out the weak ones with ease, even when the ham down the block is on with his KW. Today's crowded bands demand DAVCO DR-30 performance. Ask the ham who is using one now, check the many plus features included at no extra cost and you'll discover why Davco is the leader in providing amateurs with the most advanced in solid-state electronics.

DAVCO DR-30
\$389⁵⁰
PRICE IN U.S.A.

• Complete ham-band coverage 80-10 meters and portion of 6 meters • Standard-equipment 9.5-10.5 Mc band provides WWV and 31 meter SWL band • Three position selectivity for optimum fidelity and QRM rejection • Crystal-controlled BFO; separate AM and Product detectors; AF and RF gain controls • Full AGC with selectable


decay time; S-Meter; illuminated dial • Fly-wheel tuning drive with high-ratio split gears; direct calibration on all bands • Tunable rejection notch filter; extremely effective noise limiter • Transmitter type VFO; crystal controlled first oscillator; built in crystal calibrator • Low power consumption, permitting 12V

battery operation when desired; AC supply available • Full transistorization, diode selectivity switching, plug-in module construction, highest quality components • Rugged, stable extruded aluminum chassis for extreme stability; textured grey metal cabinet; FULLY GUARANTEED.

For further information and illustrated brochure, write: **DAVCO ELECTRONICS, Inc.** P.O. Box 2677, 2024 S. Monroe St. • Tallahassee, Fla. 32304

WW-101 FOR FURTHER DETAILS.

VITALITY

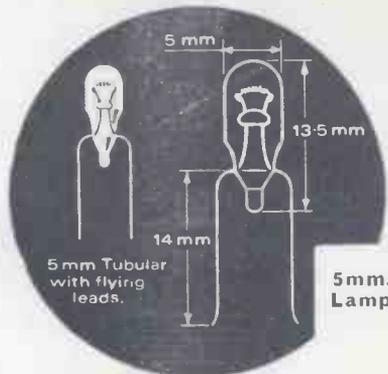


Highly dependable, this little lamp is extensively used wired direct to printed circuits or potted as an integral part of the equipment. In ratings from 0.75v. 0.17w. to 28v. 1.12w., it is designed for an average burning life of 1,000 hours.

Write for catalogue of standard ratings to:-

VITALITY BULBS LTD

MINIATURE AND SUB-MINIATURE LAMP SPECIALISTS
BEETONS WAY, BURY ST. EDMUNDS, SUFFOLK. TEL: 2077. STD. 0284/2071

WW-102 FOR FURTHER DETAILS.

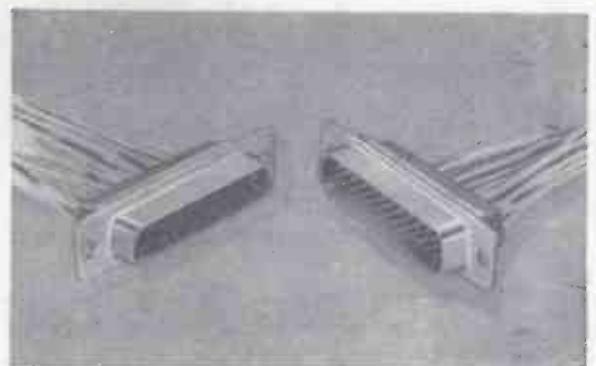

ROYAL-D PLUGS

D Subminiature series with crimp snap in contacts and "Little Caesar" Rear-Release System. 9 to 50 contacts with mixed coaxial layouts.

Cannon Electric
(Great Britain) Ltd.,
Lister Road,
Basingstoke, Hants.
Tel: Basingstoke 3171



Registered Trademark

CANNON

WW-103 FOR FURTHER DETAILS.

ONE OF A SERIES FEATURING VETERAN CARS—presented by the makers of today's most advanced mobile communications system



1897 Benz Single cylinder 3½ H.P. with Dog Cart body. Owned by Cmdr. Sir Hugh Dawson, Bt., CBE., RN.

CALLING ALL CARS—WITH BCC 81!

The BCC 81 is the perfect modern VHF transmitter-receiver for patrol cars, ambulances, taxis and the like. Extensive use is made of space-saving transistors—the whole unit fits neatly under the dashboard of almost any vehicle.

ECONOMICAL The BCC 81 has an extremely low current consumption, equal to just one instrument panel lamp on 'receive'.


RELIABLE The 81 set is backed by the full resources and the long-standing reputation of the British Communications Corporation.

TOP OF ITS CLASS An advanced design with single and six channel versions available with a 6-watt A.M. output make the BCC 81 unbeatable in its class.

BCC

BRITISH COMMUNICATIONS CORPORATION LTD.

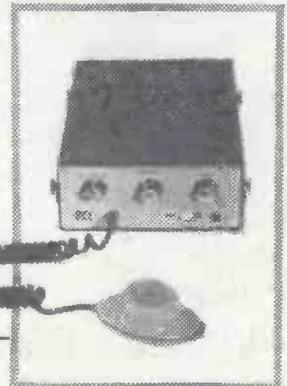EXHIBITION GROUNDS, WEMBLEY, MIDDLESEX.
Telephone: WEMbley 1212. Telegrams: BEECEEE WEMBLEY.



RADIO VALVE DATA

An invaluable reference book for everyone concerned with radio, television, telecommunications and electronic circuits. Now in its eighth edition it is completely revised and gives in tabular form the characteristics of approximately 7,000 types of British valves, transistors, semiconductors and rectifiers for radio, television, telecommunications and electronics circuits. Together with particulars of 300 cathode ray tubes for television applications.


To facilitate easy reference valves and semiconductors are now divided into two separate sections and transistors have been regrouped under four main headings. And, for the first time, drawings of valve base and transistor connections are given.

Have the facts on radio valves at your fingertips with RADIO DATA. No technical reference library is complete without one!

11" x 8 3/8" 230 pp. approx. 9s 6d net 10s 3d by post

RADIO VALVE DATA

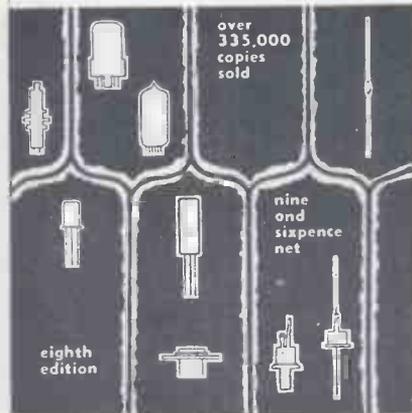CHARACTERISTICS OF SEVEN THOUSAND VALVES - TRANSISTORS - SEMICONDUCTOR DIODES & RECTIFIERS - CATHODE RAY TUBES



ILIFFE BOOKS LTD

DORSET HOUSE
STAMFORD STREET, S.E.1
Obtainable from leading booksellers

WW-105 FOR FURTHER DETAILS.

VITALITY




Miniature and Sub-Miniature Indicator Bulbs in sizes from 4.5mm

Catalogue from
VITALITY BULBS LTD
MINIATURE LAMP SPECIALISTS

BEETON'S WAY, BURY ST. EDMUNDS, SUFFOLK. TEL: 2071 STD 0204/2071

WW-106 FOR FURTHER DETAILS.


A.C. SOLENOID TYPE SCM.

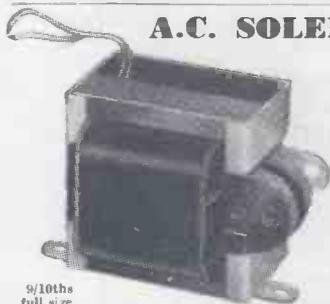

Continuous 3 oz. at 1/2 in.
Instantaneous to 2 lb.
Larger sizes available
Also—Transformers to
8 kVA 3 Phase

9/10ths full size
R. A. WEBBER LTD.
KNAPPS LANE, CLAY HILL, BRISTOL 5. PHONE 65-7228/9

WW-107 FOR FURTHER DETAILS.

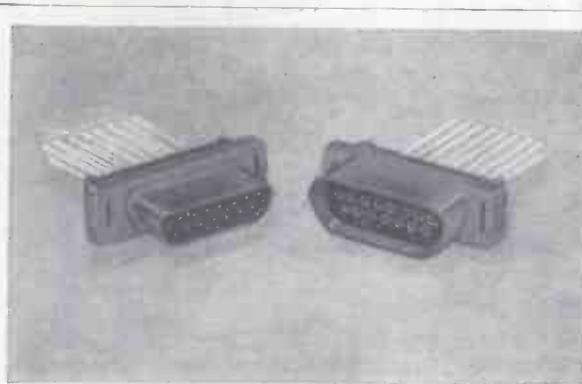

MICRO-D PLUGS

Versatile, highly reliable microminiature connectors designed for space and weight saving applications.

Cannon Electric
(Great Britain) Ltd.,
Lister Road,
Basingstoke, Hants.
Tel: Basingstoke 3171



Registered Trademark

CANNON

WW-108 FOR FURTHER DETAILS.

NINE


9 GOOD REASONS
for choosing the
SERVISCOPE* type

S51a

- Compact as a portable typewriter, only 8" x 7" x 15" overall.
- Weighs only 16 lbs; not just portable, but positively easy to carry.
- 5" (12 cm.) flat-faced PDA tube.
- Bandwidth 3 Mc/s (-3dB approx.). Sensitivity 100 mV/cm.
- 5% Time and Voltage calibration.
- Auto sync. and trigger level control.
- Proven performance, 10,000 S 51's in use throughout the world.
- Nation-wide maintenance and user advisory service available.
- **costs only £55** (U.K. price).

Ask for a descriptive leaflet, and a copy of the Telequipment short form catalogue, which describes briefly the entire range of Telequipment Serviscopes* and portable laboratory 'scopes.

*Serviscope is a registered trade mark

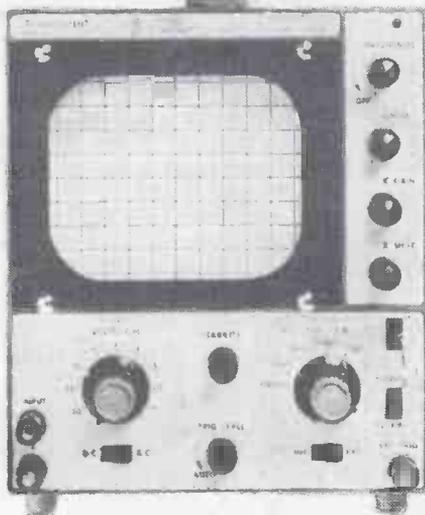

 **TELEQUIPMENT**

Telequipment Ltd Southgate · London N14 · Tel: FOX Lane 1166

WW-109 FOR FURTHER DETAILS.

"Wireless World"
Hiffe Electrical Publications Ltd.,
Dorset House, Stamford Street,
London, S.E.1

Managing Director:

W. E. MILLER, M.A., M.I.E.R.E.

Editor-in-chief:

W. T. COCKING, M.I.E.E.

Editor:

H. W. BARNARD

Technical Editor:

T. E. IVALL

Editorial:

F. MILLS

G. B. SHORTER, B.Sc.

Drawing Office:

H. J. COOKE

Production:

D. R. BRAY

Advertisements:

G. BENTON ROWELL
(Manager)

J. R. EYTON-JONES

© Hiffe Electrical Publications Ltd., 1966. Permission in writing from the Editor must first be obtained before letterpress or illustrations are reproduced from this journal. Brief extracts or comments are allowed provided acknowledgement to the journal is given.

VOLUME 72 No. 11

PRICE: 3s.

FIFTY-SIXTH YEAR
OF PUBLICATION

Wireless World

ELECTRONICS, TELEVISION, RADIO, AUDIO

NOVEMBER 1966

- 541 "Electronics and the Future"
542 High-performance Transistor Amplifier— by A. R. Bailey
547 Corona-generated Noise in Aircraft by C. E. Cooper
553 Titanium Cone Loudspeaker by E. J. Jordan
565 Power Sources Symposium
567 Hybrid Computers—2 by P. W. J. Van Eetvelt
572 "Microwaves à la Mode"
579 More about Farnborough

SHORT ITEMS

- 546 Laser Television Display
560 Thin Films in Electronics

REGULAR FEATURES

- | | |
|---|---------------------------------------|
| 541 Editorial Comment | 575 Letters to the Editor |
| 561 World of Wireless | 578 H.F. Predictions—
November |
| 562 November Conferences and
Exhibitions | 581 November Meetings |
| 563 Personalities | 582 New Products |
| 574 News from Industry | 588 Real and Imaginary
by "Vector" |

PUBLISHED MONTHLY (3rd Monday of preceding month). Telephone: Waterloo 3333 (70 lines). Telegrams/Telex: Wlworld Hiffepres 25137 London. Cables: "Ethaworld, London, S.E.1." Annual Subscriptions: Home £2 6s 0d. Overseas: £2 15s 0d. Canada and U.S.A. \$8.00. Second-class mail privileges authorised at New York N.Y. BRANCH OFFICES: BIRMINGHAM: 401, Lynton House, Walsall Road, 22b. Telephone: Birchfield 4838. BRISTOL: 11, Marsh Street, 1. Telephone: Bristol 21491/2. COVENTRY: 8-10 Corporation Street. Telephone: Coventry 25210. GLASGOW: 123, Hope Street, C.2. Telephone: Central 1265-6. MANCHESTER: 260, Deansgate, 3. Telephone: Blackfriars 4412. NEW YORK OFFICE U.S.A. 300 East 42nd Street, New York 10017. Telephone: 867-3900.

silicon planar

**for audio, radio and hybrid
television applications**

Mullard now offer a comprehensive range of Silicon Planar Transistors for all new design requirements. These devices are outstanding in performance and are available at competitive prices.

Complete information is available to Design Engineers from:—

Mullard Limited · Entertainment Markets Division
Mullard House · Torrington Place · London · W.C.1
Tel: LANgham 6633 · Telex 22281

BC107

Low-frequency high-gain driver.

BC108

Low-frequency high-gain amplifier.

BC109

Low-noise high-gain A.F. amplifier.

BF115

V.H.F. mixer and oscillator for television.

BF167

'Integrated Screen' transistor for television I.F. amplifiers (A.G.C.)

BF173

'Integrated Screen' transistor for uncontrolled television I.F. amplifier stages.

BF180

Low-noise R.F. amplifier for U.H.F. and integrated tuners.

BF181

High-gain mixer and mixer/osc. for U.H.F. and integrated tuners.

BF184

High-gain I.F. amplifier for A.M., F.M. and television sound.


BF185

R.F. and I.F. amplifier for portable radios.

Mullard **Si** *planar*

tune . . . set level . . . select AM or FM

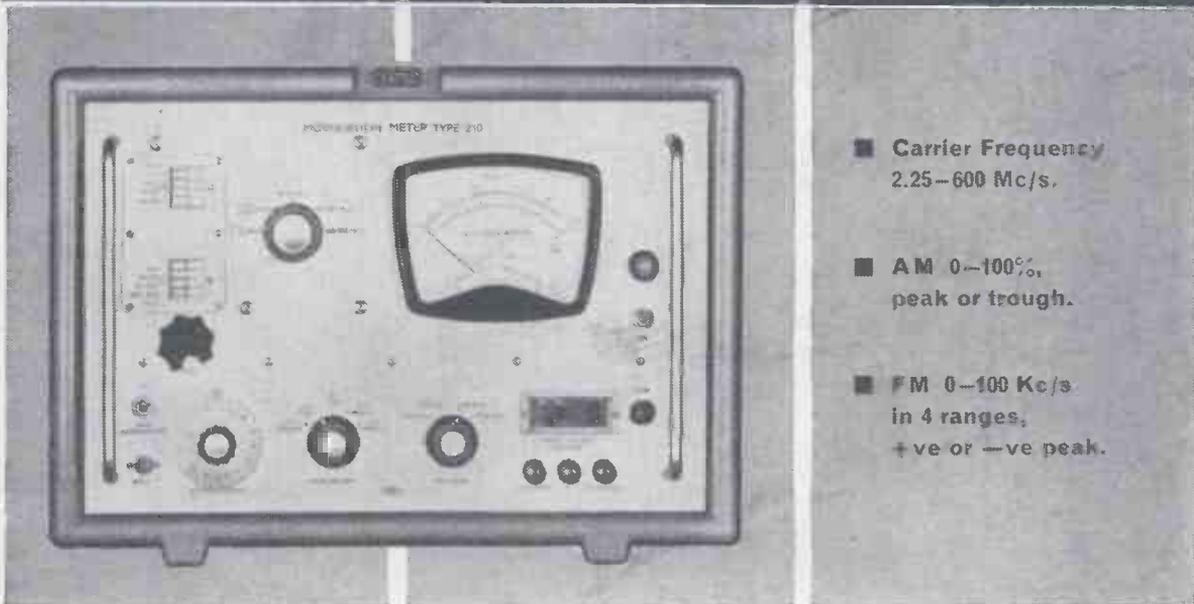for instant direct reading of Modulation Depth or Deviation



- Carrier Frequency
2.25–600 Mc/s.
- AM 0–100%,
peak or trough.
- FM 0–100 Kc/s
in 4 ranges,
+ve or –ve peak.

Throughout its extensive measuring range, the Airmec Modulation Meter Type 210A has the sensitivity to handle low signal input levels. It will accurately measure AM inputs from 7mV to 700mV, and FM inputs from 7mV to 10V.

Monitor outputs of both LF and IF are available at front panel terminals. The IF output is at 750 k/cs, and allows the modulation envelope of the input signal to be observed on an oscilloscope.

Limiting action is so effective that spurious frequency modulations on AM signals can be measured. Changes of mean carrier level when amplitude modulation is applied can also be measured to an accuracy of better than $\pm 1\%$

Airmec Modulation Meter Type 210A




Airmec for peak performance
—CONSISTENTLY

LABORATORY INSTRUMENTS DIVISION—
High Speed Counters, Signal Generators, Oscilloscopes, Wave Analysers,
Phase Meters, Ohmmeters, Valve Voltmeters etc.

AIRMEC LIMITED, HIGH WYCOMBE, BUCKS, ENGLAND
TELEPHONE: HIGH WYCOMBE 21201 (10 lines)

AP281

WW-111 FOR FURTHER DETAILS.

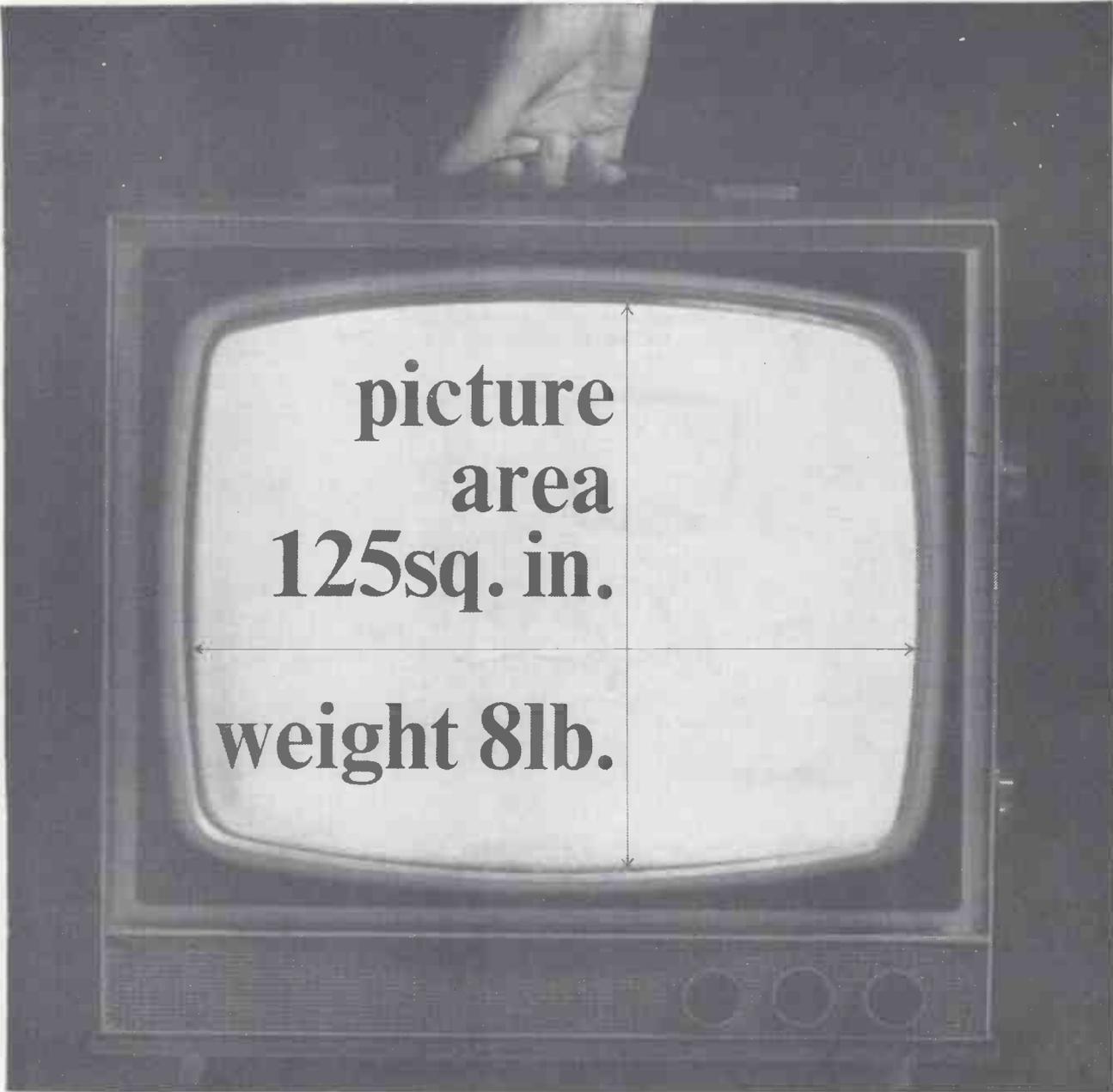

new

MAZDA

16in.

TV TUBE

—first choice for the big-screen 'second set'

The new MAZDA CME1601 [A40-11W] has been specifically designed to meet the demand for a high-performance 16" tube for the 'second set'. Its weight of 8 lbs., only half that of the 19" tube, and a length of less than 11", help to make the 'second set' compact and truly transportable. The big picture area of 125 sq. ins. is more than two-thirds that of the 19" tube. Light transmission is

65% and the high quality electron gun ensures excellent definition.

E.H.T. voltage rating is 12 to 17 kV. Built throughout to MAZDA's world-renowned quality standards, Type CME1601 is the only 16" tube made in this country.

For full technical information write to:

Thorn-AEI

Radio Valves & Tubes Ltd



7 Soho Square, London W.1
Telephone: GERrard 5233



Have a good look at your Associated Aerials array before it's installed


(There's one up there, somewhere, but nobody's seen it for years.)

Associated Aerials make aerial arrays and associated equipment for every kind of transmission and situation from compact RT aerials (for taxis and fire-brigades, for instance) to huge broadcasting networks. Omni-directional and directional aerials for remote territories; marine and ground-to-air; TV and communications; VHF, UHF.

Aerials that you can rely on.

Aerials for places that are so high, cold, wet or plain miserable that you don't want to see them again for a long, long time.

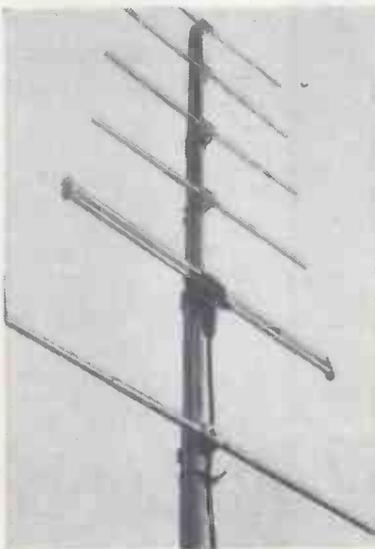Get details about Associated Aerials — the most easily forgotten aerials in the world.



For example, this is what the aerial up there on the mountain looked like when it was put up in 1961. It is a yagi aerial cut to a frequency of 165 Mc/s with excellent electrical characteristics, rugged mechanical construction to stand up to high winds and heavy ice loading, internal heating so that even severe icing cannot affect its performance.

Today, it looks the same; it works the same; it's just colder.

ASSOCIATED AERIALS LTD

Knight Road, Strood, Kent, England.
Telephone: Medway 78255
Telex: 96146

A COUBRO & SCRUTTON COMPANY



WW-113 FOR FURTHER DETAILS.




Marconi is advanced space communication

Britain's first overseas civil satellite communication ground station is being built by Marconi on Ascension Island for Cable and Wireless Limited. Marconi has also supplied Britain's first three military space communication stations.

Marconi space capability is based on long experience in all the elements required by communication systems via synchronous and random orbit satellites—computers for traffic handling and aerial direction, highly accurate aerial and servo control systems, ultra high frequency transmitters and extremely sensitive receivers. Marconi has a lifelong experience in planning, designing, manufacturing, installing and commissioning complete operational systems anywhere in the world.



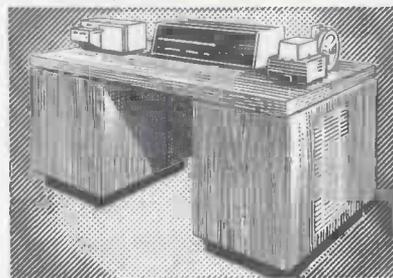Marconi Myriad computer—a vital part of many Marconi space communication systems.



Marconi space communications systems

AN 'ENGLISH ELECTRIC' COMPANY

The Marconi Company Limited, Space Communication Division, Chelmsford, Essex, England



WW-114 FOR FURTHER DETAILS.

LTD/PS1



Coubro & Scrutton

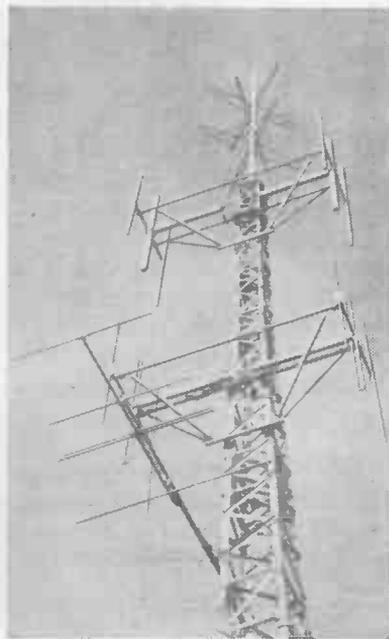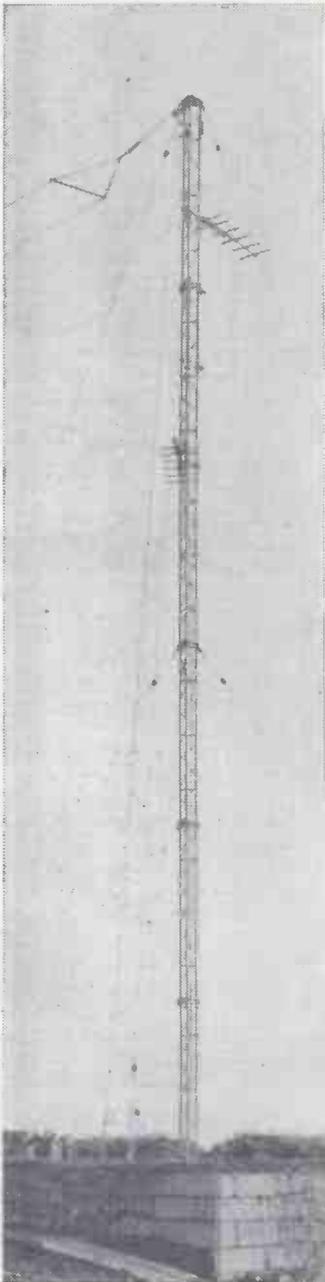design, supply and install all types of radio masts, towers and aerial systems in any part of the world



The Coubro & Scrutton Group of Companies


Telescopic Masts:	A. N. CLARK (ENGINEERS) LTD
VHF & UHF Aerials:	ASSOCIATED AERIALS LTD
Business R/T Masts & Aerials:	RT MASTS LTD
Towers, Masts & Aerial Systems:	COUBRO & SCRUTTON LTD

WW-115 FOR FURTHER DETAILS.

TELEX: 25850
 TEL: STD 01-252-4477
 430 BARKING ROAD, LONDON, E.13
 C.S.1

KEYSWITCH

RELAYS

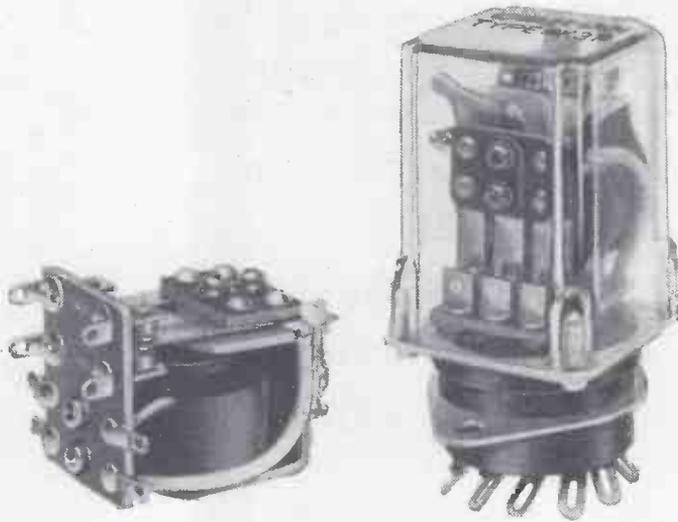

why say Keyswitch?


It's a difference of quality, often not visible until you look at performance data. Keyswitch miniature and sub-miniature relays are exhaustively tested . . . each one individually. All conform precisely to a very fine specification. Their reliability is proven. They have all the benefits of Keyswitch delivery — and that's quick, every time.

TYPE MK2 Illustrated approx. actual size. Inexpensive double-pole double-throw midget power relay. 99.9% pure silver contacts switch to 7.5A or 250V d.c./500V a.c. Operation and release 15-30 milliseconds. Universal coil range to 250V a.c./d.c. This relay can cost as little as 11/0.

TYPE MK3P Illustrated approx. actual size. 3-pole plug-in version with clear cover, and complete with socket. Contacts de-rated. This relay can cost as little as 17/8.

always to price ✕ **always to specification** ✕ **always on time**

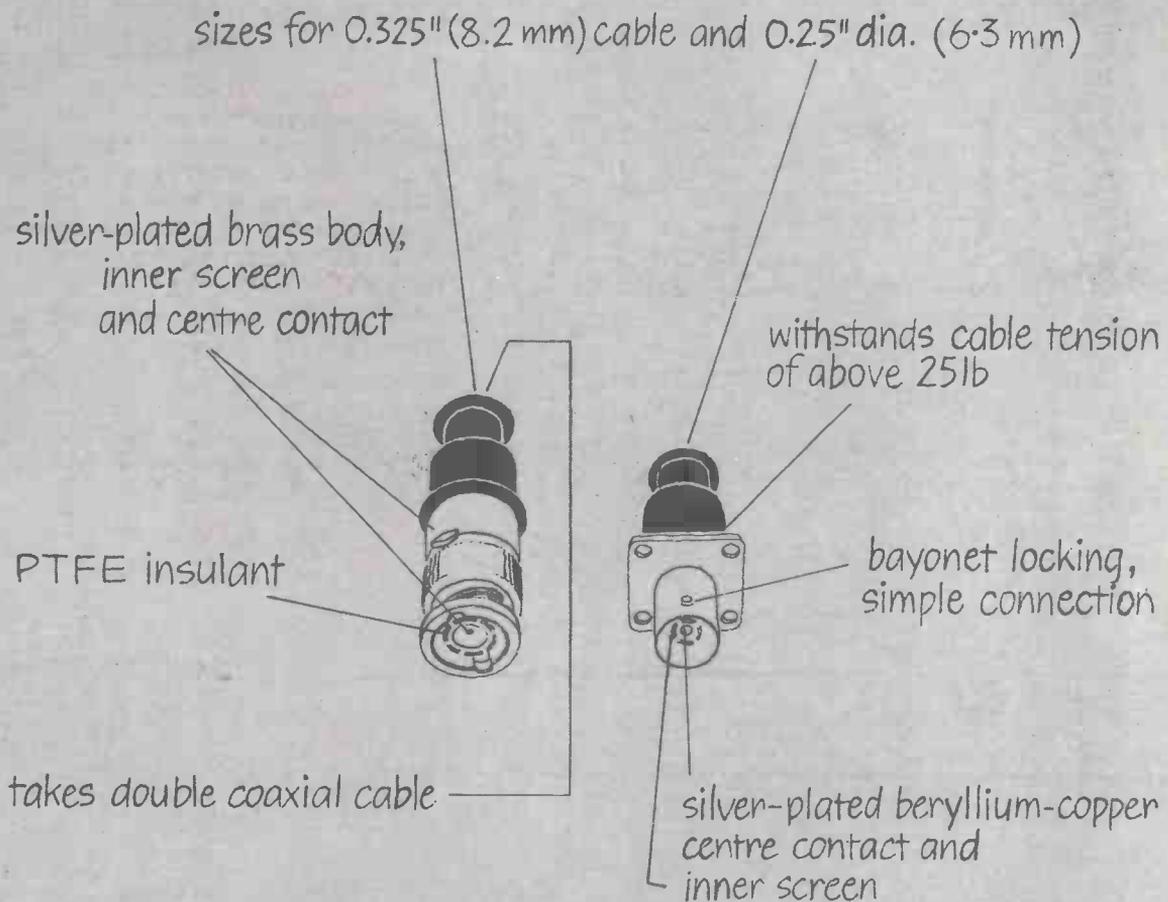KEYSWITCH RELAYS LIMITED · CRICKLEWOOD LANE · LONDON · NW2 · TELEPHONE: GLADSTONE 1152 · TELEX: 262754



NEW **DOUBLE** COAXIAL CONNECTOR


loop-free screening, lower shunt capacitance, effective noise cancelling. Free Plug, free socket, panel and bulkhead sockets available. Will mate with series L1637, pattern 15 B.N.C. connectors.

BELLING-LEE components

Write for leaflets P674 & P675 or telephone Miss Woolgar at Enfield 5393 Ext. 27

Belling & Lee Ltd. · Great Cambridge Road · Enfield · Middlesex · Telephone: Enfield 5393 · Telex: 263265

WW-117 FOR FURTHER DETAILS.

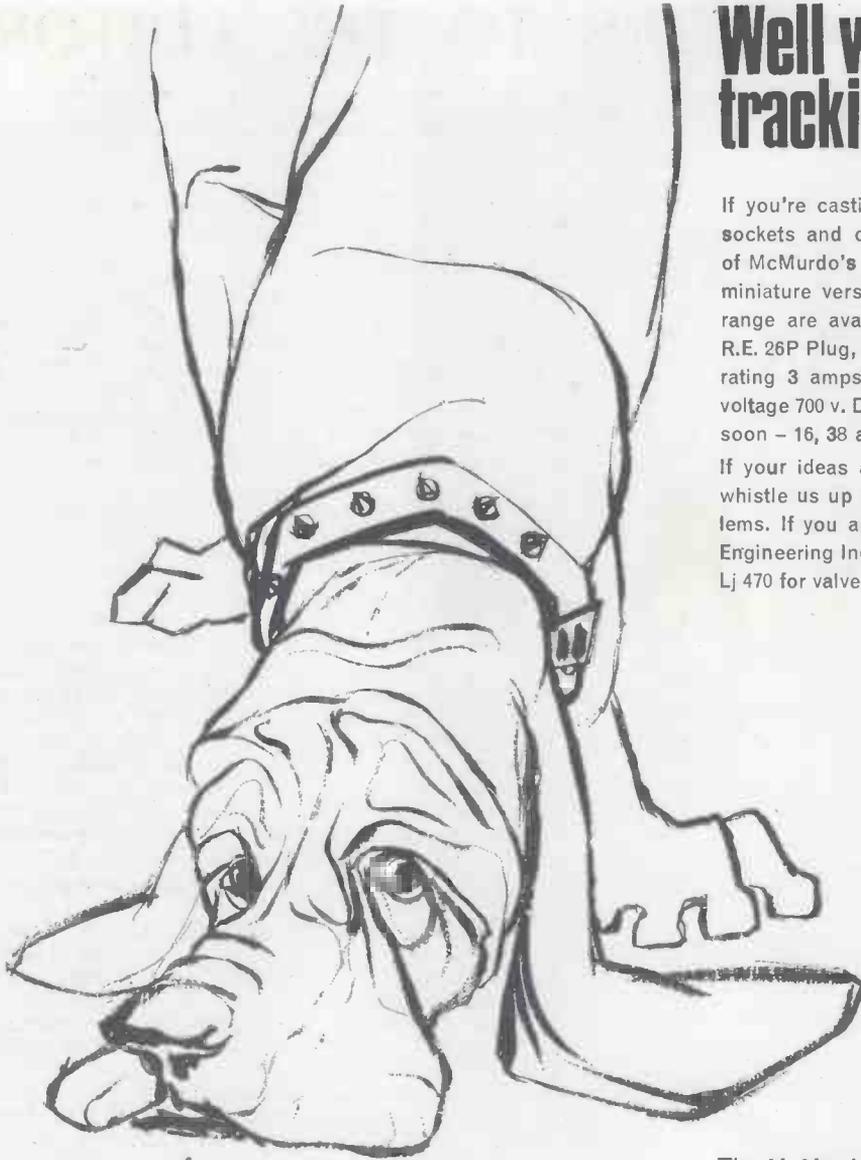

Well worth tracking down

If you're casting around for new ideas in sockets and connectors get on the scent of McMurdo's new REDETTE range. These miniature versions of the well-known Red range are available now in 26 way size - R.E. 26P Plug, R.E. 26S Socket. Max. current rating 3 amps. per contact, max. working voltage 700 v. D.C., other sizes in production soon - 16, 38 and 52 ways.

If your ideas are still at the design stage whistle us up to help you solve your problems. If you are a holder of the Electronic Engineering Index see Lj 400 for connectors, Lj 470 for valve holders.

The McMurdo range includes: CONNECTORS - rack and panel, line and jumper, printed circuit and audio range. VALVE HOLDERS - plug-in relay sockets, decal 10-pin valve holders. Crystal sockets. VOLTAGE SELECTORS.

Further details from:-


McMURDO ELECTRONIC COMPONENTS

THE McMURDO INSTRUMENT COMPANY LIMITED,
RODNEY ROAD · PORTSMOUTH · TEL: 35361 · TELEX: 86112

LUGTON & CO. LTD., 209/210 TOTTENHAM COURT ROAD, LONDON, W.1
SASCO, P.O. BOX NO. 20, GATWICK ROAD, CRAWLEY, SUSSEX.
KENYA Rigso Ltd., Victoria Garden, P.O. Box 195. NAIROBI.
MAURITIUS J. Mee Goupille & Co. Ltd., P.O. Box 6. PORT LOUIS.
NEW ZEALAND D. J. Reid (N.Z.) Ltd., C.P.O. Box 2830, AUCKLAND, C.I.

WW-118 FOR FURTHER DETAILS.

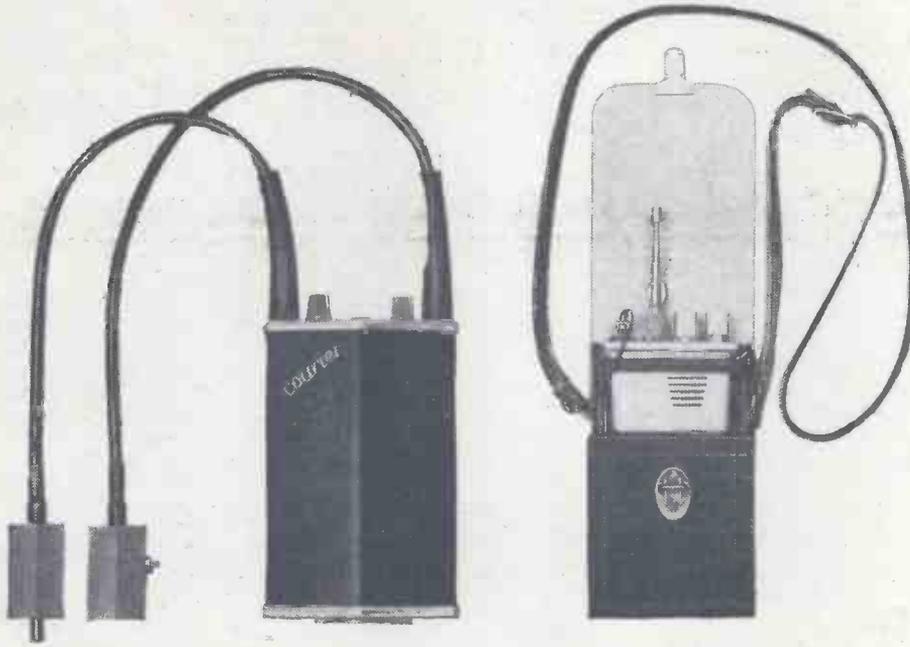there's nothing pocket-size about the performance of GEC's VHF pocket radiotelephones...



GEC fm Courier

A fully transistorised 3-channel transceiver designed to be inconspicuous in use, and allow full freedom of movement. It gives full operation fitted beneath clothing – microphone and earpiece-speaker units clip behind the lapels. Silicon transistors make the Courier extremely reliable, and suitable for a wide climatic range. Standard rechargeable battery gives 8-hour shift endurance.

An intrinsic-safety version is also available – the first pocket set to be granted an Intrinsic Safety Certificate for use in hazardous atmospheres.

The equipment meets G.P.O. Specification W.6346.

Service: F3 Telephony. Single or two-frequency simplex.
Frequency range (one, two or three channels): 71.5 Mc/s to 100 Mc/s, or 156 Mc/s to 174 Mc/s (25 kc/s spacing). (Other ranges to special order.)

Ambient conditions: Temperature -20°C to $+50^{\circ}\text{C}$.
Altitude up to 20,000 ft. a.m.s.l. Relative humidity 0 to 90%.
Dimensions of Transmitter/Receiver: $6\frac{7}{16}'' \times 4\frac{1}{8}'' \times 1\frac{3}{8}''$
Weight: With battery 23 oz. Less battery 16 oz.

Power Output: Nominally 500 mW or 400 mW.
Modulation Capability: ± 5 kc/s deviation (maximum).
Sensitivity: 15 dB signal/noise ratio for $1.5\mu\text{V}$ e.m.f.
Selectivity: Pass Band ± 7.5 kc/s at 6dB. Stop Band ± 23.5 kc/s at 65 dB min.

GEC am Courier

A fully transistorised 3-channel transceiver for pocket or hand-held operation.

Service: A3 Telephony. Single or two frequency simplex.

Frequency Range: 68-174 Mc/s Band.

Number of Channels: Maximum of 3 spaced within ± 250 kc/s of mean carrier frequency. (25 or 50 kc/s spacing.)

Dimensions: $6\frac{7}{16}'' \times 3\frac{1}{16}'' \times 1\frac{1}{2}''$ ($7\frac{1}{16}''$ over controls). (Including standard battery.)

Weight: 24 oz. (including standard battery).

R.F. Output Power: Adjustable 200 mW to 400 mW.

Modulation Capability: 100% (250 mW carrier). 90% (400 mW carrier).

Sensitivity: $2\mu\text{V}$ (e.m.f.) input modulated 30% at 1 kc/s for 13 dB signal to noise ratio and 150 mW output.

Selectivity: Pass band ± 7.5 kc/s at 6 dB. Stop band: ± 23.5 kc/s at 75 dB min. (2 signal method).

A.G.C. Characteristic: Rise in output less than 4 dB for signal change 2 V to 20 mV.


For full details of both Couriers, please contact us.



G.E.C. (ELECTRONICS) LIMITED
Communications Group

Spon Street, Coventry. Telephone: Coventry 22027

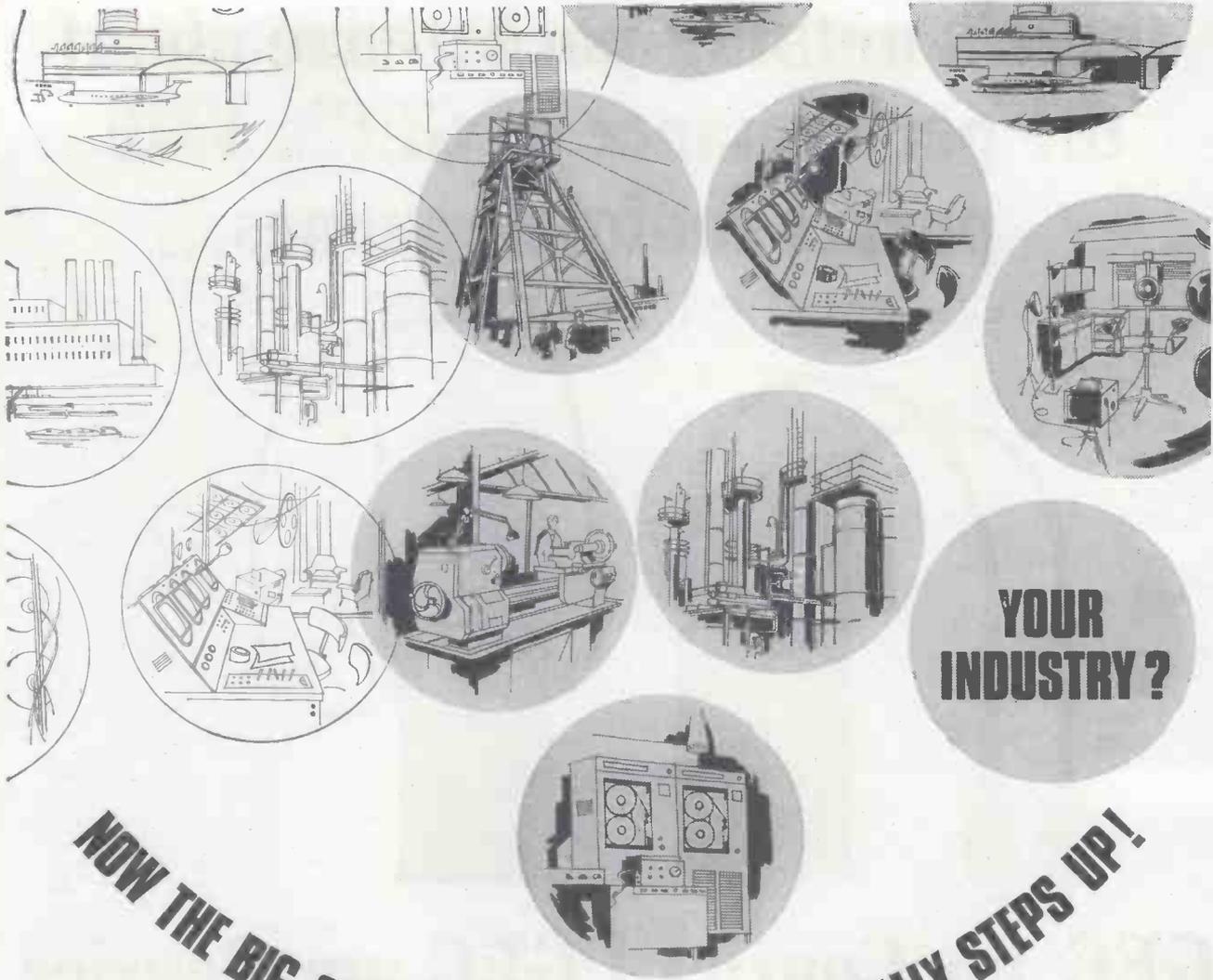A subsidiary of The General Electric Company Limited of England



**YOUR
INDUSTRY ?**


NOW THE BIG SWING TO ASTRALUX V.S.T. REALLY STEPS UP!

Everywhere Astralux Voltage Stabilising Transformers outperform and outdate conventional C.V.T. systems

HERE'S WHY ASTRALUX V.S.T. IS REPLACING C.V.T. IN INDUSTRY AFTER INDUSTRY:

Better Performance. That means improved Output Voltage Stability—output voltage maintained within $\pm 0.5\%$ for input voltage changes of $+10\% - 20\%$. Even when the voltage fluctuation is as great as $+10\%$ to -30% the V.S.T. will maintain the output voltage to within $\pm 1\%$. ● **Latest Materials.** High temperature (Class F) materials give optimum reliability and increased safety margins on operating temperatures. ● **Low external field.** The latest techniques in magnetic core design give improved performance, coupled with high efficiency, while still offering low external fields. ● **Stable Voltage—Stable Prices.**

ASTRALUX prices remain stable over long periods, so costing a job ahead is facilitated with this advanced system. ● **Over 10,000 models!** The ASTRALUX V.S.T. Standard Range consists of ten basic models with over a thousand variations on each. *No other manufacturer* offers such a choice, or can offer such economical prices. ● **Low Cost Specials.** You can order V.S.T. 'specials' at little more than the cost of standard units. Our design department will be happy to prepare prototypes to your specification, for incorporation into equipment under development. Free illustrated booklet giving full details of ASTRALUX V.S.T. from

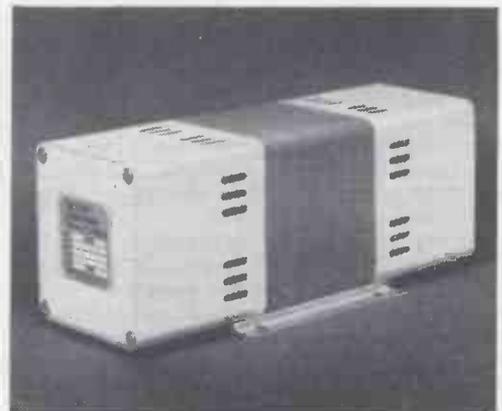

ASTRALUX dynamics limited THE FORMER DIVISION • BRIGHTLINGSEA • COLCHESTER • ESSEX • TEL: BRIGHTLINGSEA 417
WW-120 FOR FURTHER DETAILS.

—Vortexion quality equipment

The 120/200 watt amplifier can deliver its full power at any frequency in the range of 30 to 20,000 c.p.s. for which the response is accurate within 1 db with less than 0.2% distortion at 1,000 c.p.s. Noise level —90 db. It can be used to drive mechanical devices, i.e., synchronous capstan or projector motors, etc., for which the power is over 140 watts on continuous sine wave. A floating series parallel output is provided for 100-120 v. or 200-250 v., and additional matching transformers for other impedances are available. The input is for 1 mW. 600 ohms.

30/50 WATT AMPLIFIER

The Vortexion 30/50 watt Amplifier can deliver 50 watts of speech and music or over 30 watts of continuous sine wave and the main amplifier has a response of 30 to 20,000 c.p.s. within 1 db. at 0.1% distortion and outputs for 4, 7.5, 15 ohm and 100 volt line. Models are available with two, three or four mixed inputs which may be low impedance balanced line microphones, P.U. or Guitar inputs. Price £70 with 4 mixed inputs.




The 12-way electronic mixer has facilities for mixing 12 balanced line microphones. Each of the 12 lines has its own potted mumetal shielded microphone transformer and Input valve, each control is hermetically sealed. Muting switches are normally fitted on each channel and the unit is fed from its own mumetal shielded mains transformer and metal rectifier.

Also 3-way mixers and Peak Programme Meters.
Price £60.

4-way Mixers from £40/8/6.

2 x 5-way stereo mixers with outputs for echo chambers, etc., available.

120/200 WATT AMPLIFIER

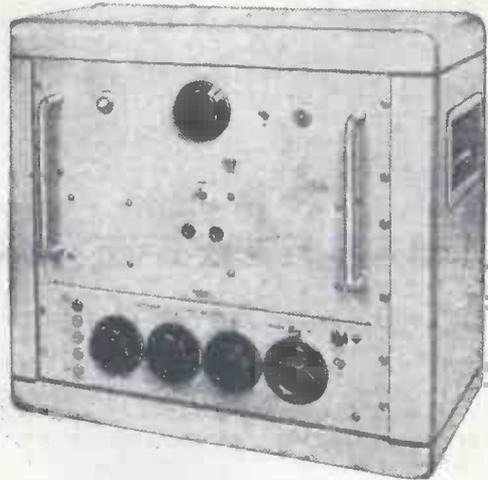


ELECTRONIC MIXER AMPLIFIER

This high fidelity 10/15 watt Ultra Linear Amplifier has a built-in mixer and Baxandall tone controls. The standard model has 4 inputs, two for balanced 30 ohm microphones, one for pick-up C.C.I.R. compensated and one for tape or radio input. Alternative or additional inputs are available to special order. A feed direct out from the mixer is standard and output impedance of 4-8-16 ohms or 100 volt line are to choice. All inputs and outputs are at the rear and it has been designed for cool continuous operation either on 19 x 7in. rack panel form or in standard ventilated steel case.

Size 18 x 7½ x 9½in. deep.

Price of standard model £49.

12-WAY ELECTRONIC MIXER

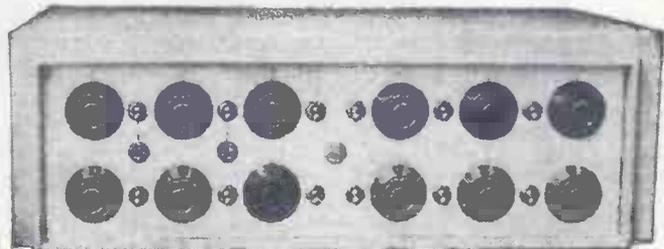

Price of standard model £98.

Full details and prices of the above on request


VORTEXION LIMITED, 257-263 The Broadway, Wimbledon, London, S.W.19

Telephone: LI Berty 2814 and 6242-3

Telegrams: "Vortexion London S.W.19"

It's **NEW!** **MODEL 633**

Guaranteed for 3 years

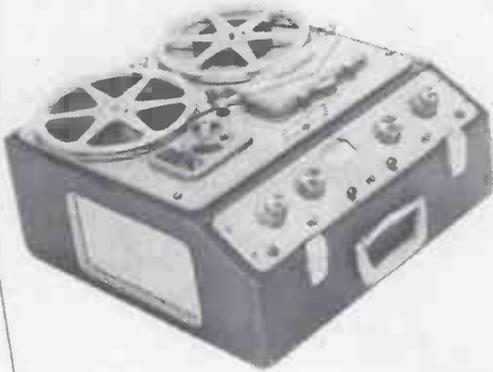

An instrument for the connoisseur...
Designed to a strict specification
Built to endure

- * Three operational speeds:
633— $1\frac{1}{8}$, $3\frac{1}{2}$ and $7\frac{1}{2}$ i.p.s.
633H— $3\frac{1}{4}$, $7\frac{1}{2}$ and 15 i.p.s.
- * Monitoring of recorded programme.
- * Comparison by "A-B" switching.
- * Switched bias control.
- * Level meter reads on both record and playback.
- * Mixing facilities with separate gain controls.
- * Modular construction to provide maximum service accessibility.
- * Separate record and replay heads.
- * Separate record and replay amplifiers.
- * Fully compensated input socket for magnetic pick-up.
- * Spot erase.
- * 3 watts undistorted output.

Model 633 120 gns.
Model 633H 125 gns.

Ferrograph

the incomparable tape recorder

The 633 is the latest addition to the Ferrograph range and is intended for the serious home recorder as well as the professional user. Each instrument is supplied with an abstract of actual performance in the form of a test certificate. Spare parts—as with all Ferrograph instruments—are guaranteed available for at least 10 years.

Interested? Then complete and post this coupon to:
THE FERROGRAPH CO. LIMITED
84 Blackfriars Road, London, S.E.1.


- Please send me the FREE-illustrated Ferrograph leaflets.
 - Please send me the comprehensive 64-page model 633 Ferrograph Manual, for which I enclose £1—refundable when I purchase my Ferrograph.
- (Tick items required in box at left)

NAME _____

ADDRESS _____

WW7



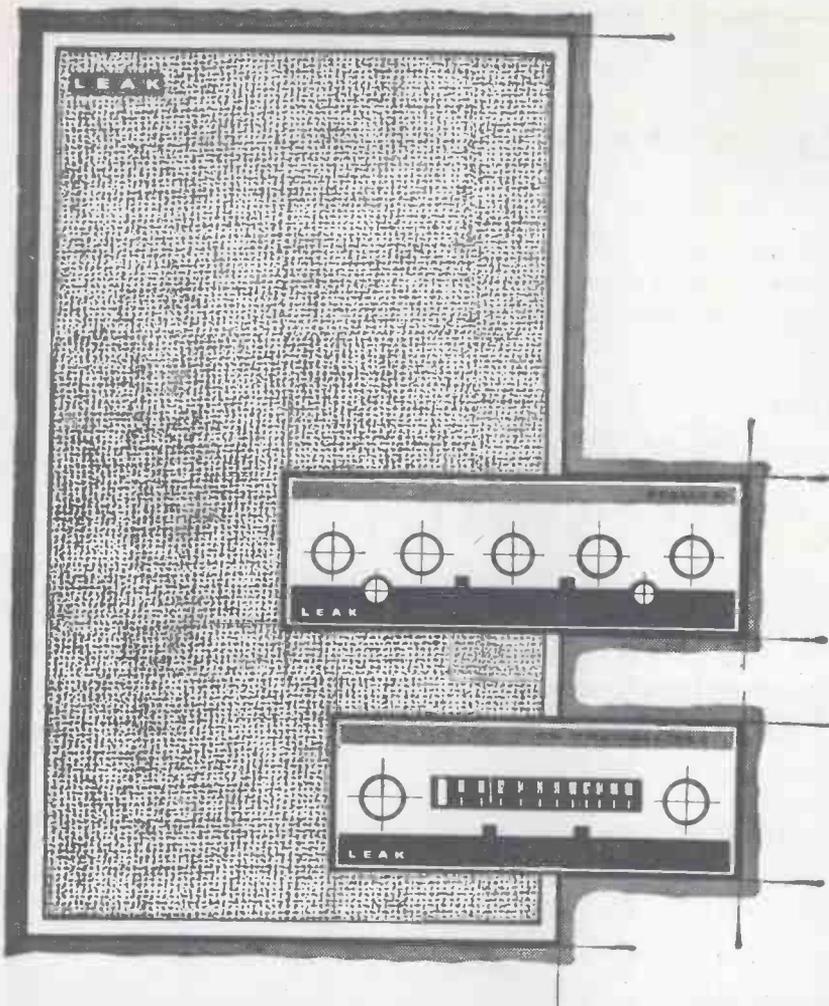

A TRIPLE FIRST FOR LEAK

A Successor to the famous "Trough-Line II"

F.M. "TROUGH-LINE III" price £31.14.6

"To sum up, the Leak Trough-Line II belongs to the very limited class of aristocrats in the tuner world."

HI-FI NEWS

Another Milestone in Audio Engineering . . .

STEREO 30 TRANSISTORISED AMPLIFIER price £49.10.0

"People sometimes ask why there is any necessity to change to transistors, the elimination of the output transformer is, in our view, sufficient reason now that

solutions of the problem of linearity in the response of the rest of the transistor circuit have been found. As additional bonuses we get smaller size, cooler running and the prospect of longer life."

"Last Autumn, during his presidential address to the British Sound Recording Association, H. J. Leak demonstrated a prototype high-quality transistor amplifier which gave results indistinguishable from those of his valve amplifiers."

WIRELESS WORLD EDITORIAL MAY, 1963

A Major Loudspeaker Invention:

THE "SANDWICH" price £39.18.0

"... This design must be regarded as a break-through of fundamental and far-reaching importance."

AUDIO AND RECORD REVIEW

If you are interested in Hi-Fi equipment combining faultless presentation with audio engineering to impeccable standards, offering studio quality reproduction at reasonable cost . . .

WRITE NOW FOR FULLY ILLUSTRATED AND DETAILED LITERATURE

LEAK

. . . the first name in High Fidelity since 1934

H. J. LEAK & CO. LTD., BRUNEL ROAD, WESTWAY FACTORY ESTATE, LONDON, W.3

Telephone: SHEpherds Bush 1173 (PBX). Telegrams: Sinusoidal, London, W.3

AND NOW-STEREO RADIO

By adding the Armstrong Stereo Radio Decoder to any of the current range of Armstrong Stereo Tuner-Amplifiers and Tuners you can receive the BBC's new series of stereo broadcasts. The quality is superb, the stereo is excellent, it's what we have all been waiting for.


Whether you already have one of our models or are about to buy one, the addition of the Decoder is simplicity itself. All stereo models were designed with this in mind. Simply plug it in, plug in the stereo beacon indicator and fix the decoder to the tuner in the space provided—the fixing holes are already there.

M5 STEREO RADIO DECODER £14.10.0

MAKES YOUR STEREO SYSTEM COMPLETE

Stereo now or stereo later, that's your choice with Armstrong Tuners. If you want only the VHF band then you need the 224 FM Tuner, but if you also want good quality medium waveband reception your choice would be the 223 AM-FM Tuner. In FM performance these tuners are identical. High sensitivity, wide bandwidth and an accurate centre-zero meter for spot-on tuning provide you with the best possible results from the BBC's FM broadcasts, whether stereo or mono.

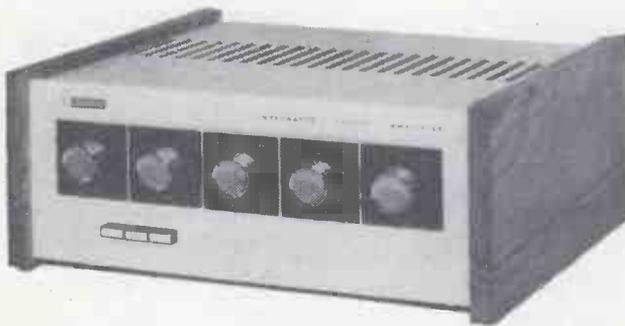To complete your system choose between the Armstrong 222 and 221. Both of these high fidelity amplifiers provide 10 watts per channel, more than enough for domestic use. 222 is designed for ceramic pickups, and the 221, as well as having certain other extra facilities, is also suitable for higher quality magnetic pickups.



224 FM TUNER	£25 2 3
223 AM-FM TUNER (illustrated right)	£31 9 0
222 STEREO AMPLIFIER	£28 15 0
221 STEREO AMPLIFIER (illustrated left)	£35 10 0
OPTIONAL CASE. Teak and vinyl hide	£3 10 0

(As illustrated. All models).

A self-powered decoder (M12, £15/7/6) suitable for older Armstrong models fitted with multiplex connections will be available shortly.

For full details and technical specifications of all models, post coupon or write, mentioning 11 WW66.

Armstrong Audio Limited, Warlters Road, London, N7

telephone North 3213



name

address

11 WW66.....

WW-125 FOR FURTHER DETAILS.



SINCLAIR STEREO 25

A stereo pre-amplifier control unit designed to ensure high fidelity at its best

A COMPLETE HI-FIDELITY STEREO ASSEMBLY INCLUDING POWER UNIT FOR ONLY £22.18.0

A very high standard of reproduction can be obtained using Sinclair items in conjunction with first-class ancillary equipment. All that is needed is one Stereo 25 pre-amp control unit (£9/19/6), two Z.12s (£8/19/-) and one PZ.3 Mains Power Supply Unit (£3/19/6) to possess the finest possible hi-fi stereo installation. As a very desirable optional extra, you could include the Micro FM (£5/19/6). The overall saving in cash will prove considerable and as a result you will have an installation second to none irrespective of price.

ORDER FORM AND OTHER SINCLAIR'S DESIGNS WILL BE FOUND on the NEXT TWO PAGES

sinclair

The Sinclair Stereo 25 pre-amp control unit has been designed specially to obtain the very finest results used in conjunction with two Sinclair Z.12s as described on the following pages. It can also be used for feeding into any other high quality stereo power amplifier. The best quality components, individually tested before acceptance, are used in its construction, ganged controls are carefully checked for matching, whilst the overall appearance of this very compact de-luxe pre-amp and control unit reflects the professional elegance which characterises all Sinclair designs. The front escutcheon panel is in solid brushed and polished aluminium

with beautifully styled solid aluminium knobs. Mounting the unit is simple, and the generous output of the PZ.3 is more than enough to power the Stereo 25 together with two Z.12s to provide stereo reproduction. Hi-fi enthusiasts seeking the ultimate in equipment for domestic listening will find all they want from this combination of Sinclair units, and with a Micro FM to provide the tuner, their installation will compare favourably with anything costing up to four times as much. The Sinclair Stereo 25 is easily fitted and it will grace any type of hi-fi furniture.

MAY BE USED WITH ANY HIGH QUALITY POWER AMPLIFIER

● TECHNICAL SPECIFICATION

Performance figures obtained with the outputs of the Stereo 25 fed to two Z.12s and the entire assembly powered by a PZ.3.

- SENSITIVITY for 10 watts into 1.5 ohms load per channel.
Mic.—2 mV into 50K ohms.
Pick-up—3 mV into 50K ohms.
Radio—20 mV into 4.7K ohms.
- FREQUENCY RESPONSE (Mic. and Radio) from 25 c/s. to 30 kc/s. ± 1 dB extending to 100 kc/s. ± 3 dB.
- EQUALISATION—Correct to within ± 1 dB on RIAA curve from 50 c/s to 20 kc/s.

- TONE CONTROLS
Treble +12dB to -10dB at 10 kc/s.
Bass +15dB to -12dB at 100 c/s.

- SIZE—6½in. X 2½in. X 2½in. overall, plus knobs

- FINISH—Front panel in brushed and polished solid aluminium with solid aluminium knobs. Black figuring on front panel.

BUILT, TESTED
AND
GUARANTEED

£9.19.6

FULL SERVICE FACILITIES AVAILABLE TO ALL SINCLAIR CUSTOMERS

SINCLAIR RADIONICS LTD., 22, NEWMARKET ROAD, CAMBRIDGE

Telephone 52996

WW—126 FOR FURTHER DETAILS.

Comment from around the world

AUSTRALIA

"Congratulations on your F.M. set. You certainly are the leaders in miniature electronics."

P.K., Vaucluse, N.S.W.

"The Micro-6 is tremendous and all 7 local stations here in Melbourne are easy to tune. I wish to congratulate you on your excellent design."

L.M.C., Bentleigh, Victoria.

"I've found your Micro-6 excellent. The volume is more than adequate, with fantastic tone."

S.M., Box Hill, Victoria

JAMAICA

"The reception and sound is superb (Micro-6), and I found the instructions very clear."

R.R., Kingstown,

NEW ZEALAND

"I have received your Z.12 amplifier. I am extremely pleased with its performance, and it is well worth the cost. Thank you for your prompt delivery."

B.R.L., Howick, Auckland.

SWAZILAND

"May I congratulate you on the Micro F.M. The performance of this tiny radio has amazed friends who just cannot believe it works until demonstrated. I am roughly thirty miles from the station in mountainous terrain, and without any extra aerial a good signal is produced."

D.J.B., Mhlambanyat,

SOUTH AFRICA

"Much to my delight, the tuner (Micro FM) performs splendidly, fully justifying the modest outlay called for. The tuner picks up all the F.M. programmes. I am now anxious to purchase two Z.12 amplifiers."

P.E.R., Florida, Transvaal,

UGANDA

"I am extremely pleased for having invested in this remarkable little box of power and it certainly lives up to its specification."

J.T.R., Kampala.

U.K.

"I am extremely pleased with the Z.12 amp. (connected to the tape head). The firm of Sinclair will always rate highly in my esteem."

B.C., Glasgow.

"The finish and general quality is very good (Micro-6). It is fantastic that a transistor radio can be so compact."

N.R.C., Bishop's Stortford.

35,000 CONSTRUCTORS CAN'T BE WRONG

Something like thirty-five thousand Micro-6 kits have been bought and assembled by constructors ranging in experience from beginners to experts, for in size, design and performance there is just nothing like it in the world. We have simply lost count of the number of enthusiastic letters received from Micro-6 constructors. This set, together with the Micro FM, have firmly established entirely new trends in radio design. They have set the pattern that constructors everywhere are following with success all over the world.

Start building
with Sinclair to-day

FULL SERVICE FACILITIES AVAILABLE TO ALL SINCLAIR CUSTOMERS • ALL ITEMS GUARANTEED

SINCLAIR

SINCLAIR RADIONICS LTD., 22 NEWMARKET ROAD, CAMBRIDGE

Telephone 52731

WW-127 FOR FURTHER DETAILS.

TWO SETS THAT HAVE CHANGED THE FACE OF RADIO



WITH BRUSHED AND POLISHED ALUMINIUM FRONT PANEL AND SOLID ALUMINIUM TUNING CONTROL

MICRO FM

7 TRANSISTOR
SUPERHET F.M.

The world's only combined
pocket-sized F.M. Tuner and
personal receiver

This unique, superbly engineered superhet FM will give you enormous satisfaction in building and using it. It is the only set in the world which can be used both as an FM tuner and as an independent FM pocket receiver just whenever you wish and its performance is fantastic used either way. Problems of alignment which have previously made it almost impossible for a constructor to complete an FM set have been completely eliminated in the Micro FM. It is ready

to use the moment you have built it. The pulse counting discriminator ensures best possible audio quality; sensitivity is such that the telescopic aerial included with the kit assures good reception in all but the very poorest reception areas. The Sinclair Micro FM will give you all you want in FM reception and the satisfaction of building a unique design that will save you pounds. Use it with your Z.12 assembly!

Technical Specification

THE SINCLAIR MICRO FM is a completely self-contained double-purpose F.M. superhet. It uses 7 transistors and 2 diodes. The R.F. amplifier is followed by a self-oscillating mixer and three stages of I.F. amplification which dispense with I.F. transformers and all problems of alignment. The final I.F. amplifier produces a square wave which is converted so that the original modulation is reproduced exactly. A pulse-counting discriminator ensures better audio quality. One output is for feeding to amplifier or recorder and the other enables the Micro FM to be used as an independent self-contained pocket portable. A.F.C. "locks" the programme tuned in. The telescopic aerial included is sufficient in all but the worst signal areas. Case size—2½ x 1½ x ¾ in. plus aerial.

- FASCINATING TO BUILD
- NO ALIGNING NECESSARY
- SUPER QUALITY AND SENSITIVITY

SINCLAIR MICRO FM

Complete kit of parts inc. transistors, case, front panel assembly, all parts, earpiece and instructions. **£5.19.6**



- BUILD IT IN AN EVENING
- AMAZING POWER, RANGE AND SELECTIVITY


Complete kit of parts inc. transistors, case, earpiece and instructions. **59/6**

MICRO-6

The smallest radio set
on earth

A minutely sized receiver which will slip into a waistcoat pocket without even showing. It is the smallest set in the world, yet the Micro-6 is completely self-contained including aerial and batteries and it virtually plays anywhere. Its clever six-stage circuit (2 R.F., double diode detector, 3 A.F.) ensures all you want in a radio today—power, range, quality and selectivity. A.G.C. counteracts fading from distant stations, bandspread brings in Luxembourg like a local station. There is a great pleasure to be had in building the Micro-6, and it makes a highly acceptable gift once others have seen its white, gold and black case and heard its amazing performance.

SINCLAIR

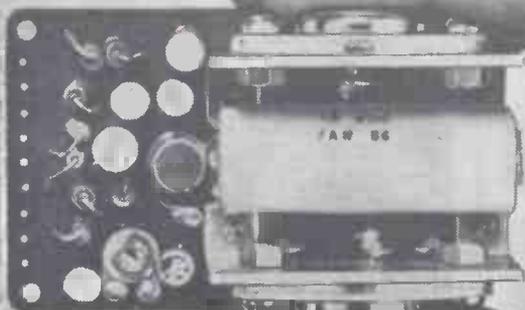

More power per square inch than any other amplifier in the world!

THE SINCLAIR Z.12 is a powerful high fidelity amplifier of exceptional compactness complete with its own high gain pre-amplifier and ready to connect to any input. Its great power gives an output equal to **SIX WATTS PER SQUARE INCH** of its total size—a standard of performance unsurpassed by anything in its class. And because of its exceptionally small size, robust construction and unique circuitry, you can now use quality amplification in applications never before possible. 8 special H.F. transistors are used in a circuit in which generous negative feedback and ultra-linear class B push-pull output achieve the highest possible standards of quality ●

The Z.12 will operate from 6 to 20 v. d.c. and when not using a battery, the P.Z.3 mains power supply unit will be found ideal ● Responses extend from 15 to 50,000 c/s ± 1 dB ● Input sensitivity 2 mV into 2 K ohms ● Signal to noise ratio is better than 60 dB and the output may be fed directly into any load from 3 to 15 ohms, or two 3 ohm speakers may be used in parallel ● The manual included with the Z.12 gives full details of matching tone and volume control circuits for mono and stereo together with multi-input switching facilities. For those requiring a completely assembled stereo pre-amp control unit there is the Sinclair Stereo 25, described on page 23L.

sinclair Z.12 COMBINED 12 WATT HI-FI AMPLIFIER AND PRE-AMPLIFIER



P.Z.3 POWER SUPPLY UNIT

In this special Sinclair design original circuitry based on advanced transistorised techniques is used to achieve phenomenally good smoothing, thus assuring ideal operating conditions for the Z.12 and Stereo 25 for which it was designed. Ripple is a barely measurable 0.05 v. The P.Z.3 will power two Z.12's and the Stereo 25 with ease. For A.C. mains. **79/6** 200/250 v., 50/60 c/s.

Ready-built, tested and guaranteed, with Z.12 manual.

89'6

Guarantee

Should you not be completely satisfied with your purchase when you receive it from us, your money will be refunded in full and at once without question.

- **SIZE**—3" x 1 3/4" x 1 1/4"
- **FANTASTIC POWER!**
12 WATTS R.M.S. CONTINUOUS SINE WAVE (24 W. PEAK)
15 WATTS R.M.S. MUSIC POWER (30 W. PEAK)
- **REQUIRES FROM 6 TO 20V.**
- **FOR HI-FI, RADIO TUNER, ELECTRIC GUITAR, P.A., ETC.**
- **HI-FI PERFORMANCE AT A FRACTION OF THE USUAL COST**

If you prefer not to cut this page, please refer to W.W.10 when writing your order.

—ORDER FORM—

To SINCLAIR RADIONICS LTD.,
22 NEWMARKET ROAD, CAMBRIDGE

Please send.....

for which I enclose


CASH/CHEQUE/MONEY ORDER for £ s. d

NAME

ADDRESS

WW.11

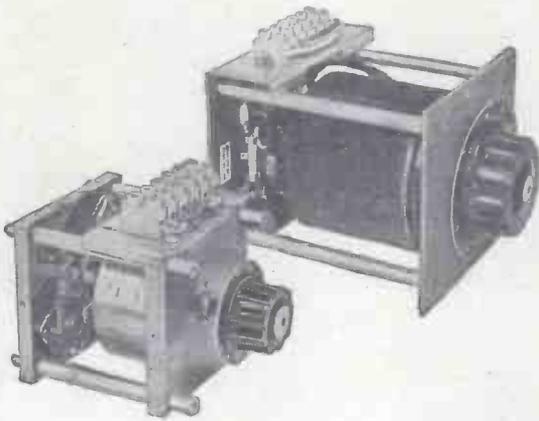COMPACT REGULATORS FOR INFINITELY VARIABLE SPEED CONTROL . . . Berco HSR range



A new range of motor Speed Controllers for building into machinery, machine tools, conveyors and processing machines of all kinds. This speed control is light, convenient to install and enables shunt-wound machine characteristics to be fully exploited. SR controllers provide good speed/torque regulation with infinitely variable smooth variation from zero to full speed—complete reliability—minimum maintenance. More compact and economical than mechanical variable speed drives. Good delivery. Suitable for motors up to $\frac{1}{2}$ H.P.

Please phone or write for List MT 1645D



The British Electric
Resistance Co. Ltd.
Queensway · Enfield · Middlesex
Telephone: HOWARD 2411
Telegrams: VITROHM Enfield

33b

WW-129 FOR FURTHER DETAILS



STOCKISTS



MODEL 8 MK. III



MULTIMINOR MK. IV

REPAIR SERVICE
7-14 DAYS

We specialise in repair, calibration and conversion of all types of instruments, industrial and precision grade to BSS.89.

Release notes and certificates of accuracy on request.

Suppliers of Elliott, Cambridge and Pye instruments.

LEDON INSTRUMENTS LTD

76-78 DEPTFORD HIGH STREET, LONDON, S.E.8

TEL.: TIDeway 2689

E.L.D. & G.P.O. APPROVED

CONTRACTOR TO H.M. GOVT

WW-130 FOR FURTHER DETAILS.


NEW! ROAMER SEVEN Mk. IV.

7 WAVEBAND PORTABLE OR CAR RADIO
AMAZING PERFORMANCE AND SPECIFICATION

★ NOW WITH PHILCO MICRO-ALLOY R.F. TRANSISTORS.

★ Fully tunable on all wavebands.
★ 9 stages—7 transistors and 2 diodes.
★ Cover M. & L. Waves. Traveller Band and three Short Waves to approx. 15 metres. Push-pull output for room-filling volume from rich toned 7in. x 4in. speaker. Air spaced ganged tuning condenser. Ferrite rod aerial for M. & L. Waves and telescopic aerial for S. Waves. Real leather look case with gilt trim and shoulder and hand straps. Size 9x7x4in. approx. The perfect portable and the ideal car radio. (Uses PP7 batteries available anywhere).

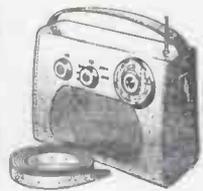★ Extra band for easier tuning of pirate stations, etc.
Total cost of all parts NOW ONLY £5.19.6 P. & P. 5/6.




Parts price list and easy build plans 3/-. (Free with kit).

NEW MELODY MAKER SIX

★ 8 stages. Six transistors and two diodes. Covers Medium and Long Waves and Extra Band for KABIER tuning of PIRATES, etc. Top grade 3in. Loud-speaker for quality output. Two R.F. stages for extra boost. High 'Q' 6in. Ferrite Rod Aerial. Approx. 350 Milliwatts push pull output. Handsome pocket size case with gilt fittings. Size 6 1/2 x 3 1/2 x 1 1/2. (Uses long-life PP6 battery). Carrying strap 1/6 extra. This amazing receiver may be built for only

£3.9.6 P. & P. 3/6.

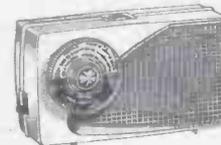

Parts Price list and easy build plans 2/-. (Free with kit.)

POCKET FIVE

★ 7 stages—5 transistors and 2 diodes. Covers Medium and Long Waves and Traveller Bands, a feature usually found in only the most expensive radios. On test, Home, Light, Luxembourg and many Continental stations were received loud and clear. Designed round super-sensitive ferrite rod aerial and fine tone 2 1/2in. moving coil speaker, built into attractive black and gold case. Size 5 1/2 x 1 1/2 x 3 1/2in. (Uses 1289 battery, available anywhere).

Total cost of all parts NOW ONLY 42/6 P. & P. 3/6.

Parts price list and easy build plans 1/6. (Free with Kit).

All components used in our receivers may be purchased separately if desired. Parts price lists and easy build plans available separately at prices stated. OVERSEAS POST 10/-.

ALL OTHER ITEMS AVAILABLE AS PREVIOUSLY ADVERTISED

RADIO EXCHANGE

61 HIGH ST., BEDFORD. 'Phone: 52367

Callers side entrance Barratts Shoe Shop. Weekdays 9-5 p.m. Sats. 9-12.30

WW-131 FOR FURTHER DETAILS.



**you cannot get a full orchestra
in your room – but you can get**

Chapman stereosound

You may think you are hearing things and so you are. All the instruments, once unheard, brought to life as if you were there amongst the musicians. The new Chapman stereosound gives you this distinct impression in the comfort of your own living room.

In attractively finished units the Chapman range of High Fidelity stereo tuners and amplifiers are all fitted with multiflex decoders for stereo broadcast reception. Send for further details to:



Derritron Radio Limited

Chapman Division, 24 Upper Brook Street, London W1

WW-132 FOR FURTHER DETAILS

DE-ICER, Controller Mk. 3. Contains 10 relays D.P. changeover heavy duty contacts, 1 relay 4P, C/O. (235 ohms coil). Stud switch 30-way relay operated, one five-way ditto, D.C. timing motor with Chronometric governor 20-30 volts 12 R.P.M.; geared to two 30-way stud switches and two Ledex solenoids, 1 delay relay, etc., scaled in steel case, size 4 x 5 x 7 in. £3 each, post 5/-.

GEARED MOTORS (Reversible).

28 v. 150 r.p.m., 25/-, post 2/6.

24 v. Open gears with governor approx. 10 r.p.m., 25/-, post 2/6.

24 v. D.C. 1.4 r.p.m., reversible with two micro switches inside gear box, silent operation, £2 each, post 5/-.

A.C. Motor 115v. 50 c/s 1/300 H.P., 3000 r.p.m. Capacitor 1 mfd. 25/-, post 3/-.

Dalmator SC5, 28 v. D.C. at 45 amps.; 12,000 r.p.m. output 750 W. (approx. 1 h.p.), brand new, £2/10/- each, post 7/6.

28 v. D.C., 200 r.p.m. (ideally suited for opening garage doors), current consumption approximately 6 amps. Price £3/10/-, postage 7/6.

AZIMUTH INDICATOR UNIT ID-260/GRD 115v. 50 c/s., complete with Azimuth Bearing Indicator and suitable for aerial direction control, 2in. tube with shield suitable for modulation percentage indicator or oscilloscope and 3in. speaker that can be utilised as a sidetone monitor. With all valves, in excellent condition, price £8/15/-, carriage 15/-.

CRD6 DIRECTIONAL ANTENNA for use with the above Instrument, £5 each, carriage £1.

CM23 COMPARTOR SIGNAL UNIT, £4/10/-, carriage 15/-.

CONDENSERS. 10 mfd. 1,000 v. 12/6, post 2/6. 8 mfd. 1,500 volts, 17/6, post 2/-.

8 mfd. 1,200 volts, 12/6, post 3/-.

8 mfd. 600 volts, 8/6, post 2/6.

0.25 mfd., 2 kv. 4/-, post 1/6.

Vacuum condenser 50 pf. 32 kv. 30/-, post 1/6.

6 pf. 20 kv. 22/6, post 1/6.

All the above are new in cartons.

HEADPHONES. DLR.5, 10/- pair, 2/6 post. No. 10 headset and microphone, 15/-, post 2/6.

AUTOMATIC PILOT UNIT Mk. 2. This complex unit of diodes and valves, relays, magnetic clutches, motors and plug-in amplifiers, with many other items, price £7/10/-, £1 carriage.

U.S.A. DESK MICROPHONE CRV/51018/A. Complete with 7 yards of screened cable and universal jack (adjustable), 10/- each, post 3/-.

AR88 SPARES: Vibrator Unit, 6 v. D.C. New 25/-, post 6/-.

Block Condenser 3 x 4 600 v. D.C. 25/-, post 4/-.

0.01 mfd. 400 v. D.C., 4 for 12/6.

Capacitor Air Trimmer, 2-20 pF., box of 3 10/-.

Ceramic I.O. Valve Holder, box of 5 7/6.

SIGNAL GENERATOR TS155c/UP (as new) price £75, carriage £1.

TS125A, with leads, etc., price £25, carriage 10/-.

ARC-27 TRANS-RECEIVER. 1,750 Channels, price £90 each.

AN/UPA39A, Video Coder-Decoder, price £45 each, carriage 10/-.

APNI ALTIMETER TRANS/REC. suitable for conversion 420 mc/s complete with all valves 28 v. D.C. Dynamotor and 3 relays, 11 valves, price £3 each, carr. 7/6.

RADIO TELEPHONE GR300 V.H.F. 75 Mc/s. two channels, complete with control box and 12 v. D.C. supply, as new, £50, carr. £1.

Control unit for the GR300, £3 each; also power supply unit 12 v. D.C., £3/10/-, carr. 10/-.

BLOWERS MOTORS. 115 v. A.C., 50 or 60 c/s., 1.80 h.p., 0.2 amps. 3,200 r.p.m., cont. duty, new in cartons £2/10/- each, post 5/-.

Smaller type blower 24 v. D.C., 15/-, post 2/6.

RELAYS SEMI ROTARY. 3 pole DT., contacts suitable for 10 amps. (silver), coil 12 volts D.C., new in cartons 12/6 each, post 2/6.

TRANS/RECEIVER UNIT Mk. 3. Freq. 2 to 8 mc/s., RT or CW., MCW., requires external power supply. Complete station £9, carriage 25/-.

Trans-rec. only £3/10/-, carr. 15/-.

RESISTORS. Variable 3 ohm. 10 amps., 25/-, post 4/-.

ROTARY TRANSFORMERS. 24 v. input, 175 v. at 40 ma. output 25/-, plus 2/- post. EICOR type, 12 v. input, 400 v. at 180 ma. output, 30/-, plus 4/- post. 12 v. input, 225 v. at 100 ma. output, 25/-, plus 3/- post. (All the above are D.C. only).

MICROPHONES Type T50. Fits the palm of hand with on/off switch and lead (Electro Dynamic) 35/- each, 2/6 post. Type T17 with lead and PL55 plug, 45/-, 3/- post.

CANADIAN C52 TRANS./REC. Freq. 1.75 to 16 mc/s. on three bands. R.T., M.C.W. and C.W. Crystal calibrator, etc., power input 12 volt D.C., new condition complete set £50, carr. £2/10/-.

Used condition in working order £25, carr. £2/10/-.

C52 receiver only (less outer case), £8/10/-, carr. 15/-.

Transmitter only £7/10/-, carr. 15/-.

Power unit C52 rec., new £3/5/-.

Used power units in working order £2/5/-, carr. 10/-.

TRANSFORMERS. 230 to 115 v., isolation 300 va, £4 each, plus 5/-.

230/115 auto 300 watts, £3, post 6/-.

230 v. pri. 24 v. at 2 amp., 22/6, post 5/-.

RDO RECEIVER has complete metering of both RF and Audio Circuits. Calibrated Accuracy: 1% approx. Video Output: 25mv into 50 ohms.

It utilizes the same plug in RF tuning units as the AN/APR-4 Receiver, and is ideally suited for monitoring and measuring signals in the 38-4,000 mc range. Receiver with three tuning units covering 38-1,000 mc/s. and Panoramic Adaptor. Price £150, carr. 30/-.

OSCILLOSCOPES. Type 1035, Cossor Mk. 1, in very good condition. £35, carr. £1.

Hartley type 13a, £25, carr. £1.

Type 1049 Mk. IV, excellent condition, price £50 each, carr. £1.

APN.1 CIRCSCALE METERS: 0-270 degrees, ideal for making rev. counters etc. Price 25/- each, post 3/-.

CT.53 SIGNAL GENERATOR. Freq. range 8.9-300 mc/s. with calibration chart. Output 1µV-100mV. internal square wave and sine wave modulation at 100 c/s, external modulation 50 c/s-10 Kc/s, 230 v. A.C. Complete with chart etc., price £27/10/-, carr. £1.

MARCONI CR100/2 RECEIVER. Freq. 60-30 mc/s., selectivity 100 db-30 db, complete with bandpass filter switch 100-300-1,200-3,000-6,000 c/s, 2 RF stages, crystal filter etc., 230 v. A.C. power supply. Price £30 each, carr. £1.

HRO RECEIVER. Model 5T. This is a famous American High Frequency superhet, suitable for CW., and MCW., reception crystal filter, with phasing control. AVC., and signal strength meter. Freq., range 50 kc/s. to 30 mc/s., with set of nine coils.



Receiver only in working order, £18/10/-, carr. 15/- each. Set of nine coils £12/10/-, available only with set. Power unit for HRO., 100/240 v. A.C., £2/15/-, carr. 10/-.

CONVERTERS. Type 8a, 24 v. D.C., 115 v. A.C. at 1.8 amps 400 cycles, 3-phase, £6/10/- each, post 8/-.

DALMOTORS (All ex equipment):

Actuator Type SR-43: 28 v. D.C. 2,000 r.p.m., output 26 watts, 5 inch screw thrust, reversible, torque approx. 25 lbs., rating intermittent, price £3 each, postage 5/-.

Model PM-4: 28 v. D.C. @ 3 amps, 4,500 r.p.m., output 40 watts, continuous duty complete with magnetic brake. Price £2 each, postage 4/-.

Model SR-2: 28 v. D.C. 7,000 r.p.m., duty intermittent, output 75 watts, price 25/- each, postage 4/-.

MOTORISED ACTUATOR: 115 v. A.C. 400 c/s. single phase, reversible, thrust approx. 3 inches complete with limit switches, etc. Price £2/10/- each, postage 5/- (ex equipment).

D.C. MOTOR: 27 v. D.C. with gear box, 4 r.p.m. Price 25/-, postage 3/- (ex equipment).

GEARED MOTOR: 28 v. D.C. approx. 200 r.p.m. complete with precision potentiometer, 40k plus or minus 3%, 2.5 watts linear plus or minus 0.25%. Price 30/-, postage 4/- (ex equipment).

TRANS/REC 510/A. This is a lightweight transmitter/receiver principally used for long range communications. Frequency, tunable 2-10 Mc/s. and has facilities for "VOICE" or "CW" working. The operator can set up 4 crystal controlled channels within this band and select the required frequency by means of a switch on the panel of the transmitter. Power requirements 1½ v. and 90-7½ v. The power output is approx. 0.2 watts for "VOICE" (unmodulated) and 0.5 watts for "CW." Suitable for mobile units or can be used as a base station with improved aerial system. In excellent condition. £15 each, carr. 10/-.

MARCONI TYPE TF-144G SIGNAL GENERATOR. Freq. 85 Kc/s.-25 Mc/s., internal and external modulation, power supplies 200/250 v. A.C. Price £25, carr. 30/-.

TSS35A/U, Hewlett Packard Co. Signal Generator: freq. on 4 bands 7-16 kc/s., 15-36, 34-80, 70-160 kc/s., with 400 cys. external mod., microvolts 0-10 and 0-20 Db., with a 2 inch cathode ray tube for visual indication. Power Supplies 115 v. A.C. Price £75 each, carriage £1.

MARCONI SIGNAL GENERATOR NO. 13. 2 bands, 20-40 mc/s and 40-80 mc/s. FM., AM., and CW. Mod. Freq. 300/1000/1600/3000 and external mod. Output voltage is 0.1-10. Power Supplies 110 v. or 250 v. A.C. Price £50, carriage £1.

MULTIPLIERS (CT54 valve voltmeter), £2/10/- each, post 3/-.

HS RELAYS. 1,700/1,700 ohm coil, 17/6 each. 500/500 ohm coil, 15/- each. Postage 2/-.

TACAN Trans/Receiver, same as ARN21, British made, STC, TR9171 complete with five 2C39As with associated valve-holders. As new price £25. Used condition £15, carriage £1.

CONTROL MOTORS. 115/115 v., 2 pole 60 cys., output 5 watts, the tachometer 115v. 1 ph., output volts per 1,000 v.=6 v., £3/10/-, carr. 4/- each. Type R110-2B-B. 115/115 v. 400 cys., £2/10/-, carr. 4/- each.

TELEPHOTO UNITS (Transceiver) Type CNP. Complete with tuning fork and power supplies 115 v. 50 or 60 cys., £30 carr. £2 each.

TELETYPEWRITERS. TT-4 TGXc-2. Also AN/PGC-1 and AN/PGG-2, £35, carr. £1 each.

UNISELECTORS (ex equipment):

8 bank 25 way, 75 ohm coil, price 35/- each, postage 4/-.

3 bank 25 way, with one homing bank, price 25/- each, postage 3/-.

RELAY PANEL: with 4 Leach relays, 28 v., 135 ohm coil, 4P. C/O, 10 amp. contacts, 4 relays, 28 v., 235 ohm coil, 3 pole C/O plus high speed relay, 16,000 ohm, 1 C/O. Price 30/- each, postage 5/-.

TELEPHONES (PORTABLE) TYPE "F." Suitable for all outdoor activities up to a range of 5 miles, in excellent condition. Price, complete with batteries, £5/10/- per pair, carriage 10/-.

B.44 MODULATION TRANSFORMER: Ratio 2:1 or as an output transformer 85:1. Price 25/- each (new in cartons), postage 3/6.

FUEL INDICATOR Type 113R: 24 v. complete with 2 magnetic counters 0 to 9999, with locking and reset controls mounted in a 3 in. diameter case. Price 30/- each, post 5/-.

MACHMETERS: Range 0:1 and 0:1.2, 6A/3384 and 5325 respectively, price 30/- each, postage 5/-.

ALTIMETERS: 40 to 60,000 feet, the ideal instrument for making a barometer, price £5 each, post 5/-.

BATTERY CHARGERS: 100-250 v. A.C. Input, 12 v. 15 Amp. Output (2-Range) charger complete with Sun-vick thermal switch for fast or trickle charge, price £12/10/- each, carr. 30/-.

HEWLETT PACKARD ADAPTOR, Model X281A: Wave guide to coaxial adaptor, freq. 8.20-12.40 km/c., size 1 x 1/4 in., price 30/-, post 2/-.

AVOMETER MODEL 7: As new, complete with case and leads, £15; secondhand condition £12/10/-.

Postage on both 7/6.

COMMAND RECEIVERS: 190-550 kc/s., as new, price £6/10/- each, post 5/-.

Model 3-6 mc/s and 6-9 mc/s., as new, price £5/10/- each, post 5/-.

BC-433-G COMPASS RECEIVER: Freq. 200-1,750 kc/s. in 3 bands, suitable for aircraft, boats, etc. Complete with 15 valves, power supply input 24 v. D.C. at 2 amps. Receiver only £5 each, control box for receiver £1 each, carr. 15/-.

Complete installations can be quoted for. Please write further details. List available 6d. S.A.E. for all enquiries.

W. MILLS

3-B TRULOCK ROAD, TOTTENHAM, N.17
Phone: Tottenham 9213

THE ELECTRONICS & SCIENTIFIC CENTRE

MAGNAVOX-COLLARO 363 TAPE DECKS

The very latest 3-speed model—1 $\frac{1}{2}$, 3 $\frac{1}{2}$, 7 $\frac{1}{2}$ l.p.s. available with either $\frac{1}{2}$ track or $\frac{1}{4}$ track head. Features include: Pause control; digital counter; Fast forward and rewind; new 4 pole fully screened induction motor; interlocking keys. Size of top plate 13 $\frac{1}{2}$ x 11 x 5 $\frac{1}{2}$ in. deep below unit plate. For 200/200 v. A.C. mains 50 c.p.s. operation. New, unused and fully guaranteed.

LIND-AIR PRICE
 $\frac{1}{2}$ track model £10/10/-
 $\frac{1}{4}$ track model £13/9/6
 Carriage and Packing 7/6 extra.

50V. SERVO SYSTEM

A unique offer of a pair of 50-volt, 50-cycle servos that enable remote indication of angular position to be made. These are ideal for monitoring Wind Direction in the comfort of the home, or the position of an aerial system for amateur broadcasting enthusiasts. The exact position of a roulette wheel could be "guessed" by a magician using our system. It should be noted that 50 v. is readily obtainable, by using the 200-250-volt tap on any mains transformer. Size of magnet motor 3 $\frac{1}{2}$ x 7in. Cost of pair, 75/-, plus 5/- P. & P.

SELECTOR DRIVE

A very interesting item with numerous applications consisting of an electro-magnet and brass tooth wheel. A switch wafers and contacts are coupled to this and arranged to be on for 10 pulses and off for the next 15. An auxiliary contact is normally on, but off for one in every 25 pulses; complete with suppressor resistors and a series contact to facilitate continuous operation. Absolutely ideal for window displays, switching lamps or models, 12 or 24 v. D.C. Brand New and boxed, 12/6, inc. P. & P.

SINCLAIR SUPER MINIATURES

Micro 6 miniature radio... £2 19 6
 Micro-FM (tuner/receiver)... £5 19 6
 £23 M.F.S. unit... £3 19 6
 7-23 12 watt amp and pre-amp, fully built... £4 9 6
 STEREO 25 pre-amp control control unit, fully built... £9 19 6
 P. & P. 3/6 each.

MODEL MAKER'S

Miniature D.C. Motor. Ideal for driving a gear system or can be used as a tachometer. Speed 10,900 r.p.m. at 230 mA. 6.3 v. D.C. Housed in black ebonite case size 1 $\frac{1}{2}$ in. x 1in. dia. Spindle 1in. long x 3/64in. dia. 9/6. P. & P. 2/6.

MULTIMETERS

C.1001. 20,000 Ω volt... £3 12 6
 P. & P. 3/6
 P.14. 1,000 Ω /volt... £2 2 0
 P. & P. 3/6
 N.H. 200. 20,000 Ω /volt... £6 0 0
 P. & P. 5/6
 B.40. 10,000 Ω /volt... £6 2 6
 P. & P. 6/-
 500. 30,000 Ω /volt... £9 19 6
 P. & P. 6/6
 Reconditioned AVO Mod. 7 £14 0 0
 P. & P. 7/6
 New AVO Meters from stock.
 MINILAB
 7 in 1 Tester... £6 19 6
 P. & P. 6/6

PLUGS, SOCKETS & CONNECTORS

New 72-page Catalogue now ready! Well over 160,000 different types of British and American manufacture. Standard Circular, Miniature Circular, Pygmy, Audio, Electrical, Miniature, Sub-miniature, Radio Frequency, etc., etc.
SEND FOR YOUR COPY NOW!

LIND-AIR Electronics Ltd. DEPT. **WV11**

53 TOTTENHAM COURT ROAD, LONDON W.1.

LAngham 3653

MANY MORE INTERESTING BARGAINS AVAILABLE AT THE SHOP

WW-133 FOR FURTHER DETAILS.

PROFESSIONAL ELECTRIC INSTANT HEAT SOLDER GUN

Ideal for model makers, home repairs, electronics, radio, TV, etc. Unique features include interchangeable tips, extension barrels, comfortable grip with trigger control. "U" shaped 3/16in. bit to minimise wear. Light beam is automatically directed on to end of bit when ON/OFF trigger is in use. 85 watt element with special ventilation. Complete with 2-pin, 5 amp. plug, 230-250 volts. Spares available. **49/6 +2/6 P.P.**

SUPER LIGHTWEIGHT PILOT'S HEADSET

COMPLETE WITH BOOM MICROPHONE
 Made to highest Military specifications, as used by Airlines. High imp. Complete with 5ft. cable. 75/-, P. & P. 2/6.

'SMITH' 1/10th second RECORDING STOPWATCH

UNREPEATABLE AT ONLY 77/6.
 Postage and Packing 2/6. Time those sporting events, records, films, etc., yourself with this excellent ex-service timer, offered at rock bottom bargain price. Pattern 3149, manufactured to stringent government specifications. Jewelled movement, 1/10th sec. recorder, 0-15 min. register and functions with three pressures (start, stop and return) on crown. 14 Days, Approval for Cash. 12 Months' Guarantee.

FANTAVOX STEREOGRAPHIC AMPLIFIER MODEL MG-333

The Stereo MG-333 is a compact and handsomely designed dual channel amplifier for use with stereo record players and AM or FM tuners. The amplifier operates from a power source of 105-125 (or 200-240) volts, 50/60 cycle AC, and is equipped with individual volume controls for each channel, a continuously variable tone control, and a stereo-monophonic mode switch. Price £8/19/6. P. & P. 6/6.

SYNCHRONOUS CLOCK MOTORS

G geared for 40 revolutions per hour, 230 v., 50 cycles. With mounting flanges. 29/6. P.P. 1/6.

TRANSISTORS

XA 101 1/8	SB 344 3/-	ACY 21 6/-
XA 102 1/8	V15/20P	AC 107
XA 104 1/8	V60/201P	AF 115 14/6
GET 3 2/-	V60/201P	AF 115 8/6
GET 103 4/-	MAT 100	AF 117 7/6
GET 104 4/-	MAT 120	ACT 20 5/-
OC 16 10/-	MAT 120	28014
OC 23 10/-	OC 45 1/9	28017 44/6
OC 45 1/9	OC 81 6/-	MAT 101
OC 81 6/-	OC 81D 6/-	MAT 101
OC 81D 6/-	OC 170 7/6	MAT 121
OC 170 7/6	OC 171 8/8	BC 107 8/6
OC 171 8/8	MA 383 3/-	BC 107 8/6
MA 383 3/-		P. & P. 1/-



High accuracy, wide range, low cost. These are among the many advantages of MINI TIME. Comprising a pocket size black moulded case with contrasting front panel and 3in. meter. MINI TIME is designed to measure the time interval between the opening and/or closing of contacts, or width of pulses in active circuits. Range: 1 milli-10 secs.

Send for explanatory leaflet to our Agents: Hird-Brown Ltd., Bolton; Sencorn Ltd., London; Jiveco, Paris; S.P.R.L. Pol Francois, Belgium; or direct to A. G. BROWN ELECTRONICS LTD., LOWER MILLS, BUSBY, GLASGOW, SCOTLAND.

WW-134 FOR FURTHER DETAILS.

TECHNICAL TRAINING by ICS IN RADIO, TELEVISION AND ELECTRONIC ENGINEERING

First-class opportunities in Radio and Electronics await the ICS trained man. Let ICS train YOU for a well-paid post in this expanding field. ICS courses offer the keen, ambitious man the opportunity to acquire, quickly and easily, the specialized training so essential to success. Diploma courses in Radio/TV Engineering and Servicing, Electronics, Computers, etc. Expert coaching for:

- * INSTITUTION OF ELECTRONIC AND RADIO ENGINEERS.
- * C. & G. TELECOMMUNICATION TECHNICIANS' CERTS.
- * C. & G. SUPPLEMENTARY STUDIES.
- * R.T.E.B. RADIO AND TV SERVICING CERTIFICATE.
- * RADIO AMATEURS' EXAMINATION.
- * P.M.G. CERTIFICATES IN RADIOTELEGRAPHY.

Examination Students Coached until Successful.

NEW SELF-BUILT RADIO COURSES

Build your own 5-valve receiver, transistor portable, signal generator and multi-tester—all under expert tuition.

POST THIS COUPON TODAY and find out how ICS can help YOU in your career. Full details of ICS courses in Radio, Television and Electronics will be sent to you by return mail.

MEMBER OF THE ASSOCIATION OF BRITISH CORRESPONDENCE COLLEGES.

INTERNATIONAL CORRESPONDENCE SCHOOLS

International Correspondence Schools (Dept. 222), Intertext House, Parkgate Road London, S.W.11.

NAME

ADDRESS
 Block Capitals Please

.....

..... 10.66

A WHOLE WORLD OF KNOWLEDGE AWAITS YOU!

WW-135 FOR FURTHER DETAILS.



Instruments for Laboratories Test & Service Workshops

- Low prices.
- Well-proven circuitry.
- Modern functional styling.
- Accurate and reliable performance.

3in. PORTABLE SERVICE OSCILLOSCOPE Model OS-2

Modern styling, lightweight and compact size, make this the ideal 'scope for service man, laboratory technician, amateur radio enthusiast or hobbyist. "Y" bandwidth 2 c/s-3 Mc/s. ± 3 dB. Sensitivity 100 mV/cm. TB 20 c/s-200 kc/s. in four ranges. Mumetal c.r.t. screen. Dimensions 5in. wide x 7½in. high x 12in. deep. Wt. 9½lb.

Kit.....£23.18.0 Assembled £31.18.0

Outstanding value in a low-priced 'Scope.



LOW-PRICED SIGNAL GENERATOR. Model RF-IU

Provides extended frequency coverage on 6 bands on fundamentals and harmonics. Ideal for the alignment and trouble shooting of RF, IF and audio circuits. Large easy-to-read dial. Pre-aligned coil and bandswitch assembly. RF output of at least 100 millivolts. 100 kc/s—100 Mc/s fundamentals, up to 200 Mc/s harmonics. 400 cycle audio signal with 4 v. output. Dimensions 9½in. wide x 6½in. high x 5 in. deep.

Kit.....£13.18.0 Assembled £20.8.0



LOW-PRICED SINE/SQ GENERATOR. Model AO-IU

This inexpensive generator covers 20 c/s-150 kc/s with a choice of sine or square waves, the latter up to 50 kc/s. This generator is ideal for checking the fidelity and distortion of audio amplifiers and radio receivers. Output voltage ranges: Sine-wave 0-100 mV., 0-1 v., 0-10 v. (Dist less than 1 per cent.). Square-wave 0-800 mV., 0-8 v., 0-80 v. Dimensions: 9½in. wide x 6½in. high x 5in. deep.

Kit.....£14.15.0 Assembled £21.5.0

LOW-PRICED RESISTANCE/CAPACITANCE BRIDGE. Model C-3U

This compact, self-contained R/C Bridge is A.C. powered, and will be found equally valuable in the Laboratory, service workshop production line, etc. Measures capacitance from 10 pF-100µF. Polarising voltages from 5-450 volts. Resistance 100 ohms-5 Mohms. All readings are taken from large calibrated scales direct—no calculations required. Magic eye leakage indication. Dimensions: 9½in. wide x 6½in. high x 5in. deep.

Kit.....£11.5.0 Assembled £16.15.0



See the full range of Heathkit models in the free catalogue



5in. Flat-face GENERAL PURPOSE OSCILLOSCOPE Model 10-12U

An outstanding oscilloscope

"Y" sensitivity 10 mV. r.m.s. per cm. at 1 kc/s. Bandwidth 3 c/s-4.5 Mc/s. Frequency compensated input attenuator X1, X10, X100, T/B. 10 c/s-500 kc/s. in 5 steps. Two extra switch selected pre-set sweep frequencies in T/B. range. T/B. output approx. 10 v. peak to peak. Built-in IV calibrator. Facility for "Z" axis modulation. Electronically stabilised power supply. Power req. 200-250 v. A.C. 40-60 c/s. 80 watts. Fused. Front panel silver and charcoal grey. Cabinet, charcoal grey, size 8½ x 14 x 17in. 56-page construction and operation manual.

deep. Net weight 23lb.

Kit.....£35.17.6 Assembled £45.15.0

ANALOGUE COMPUTER Model EC-IU

Serves a variety of Educational and Industrial needs! Simple to build and use. Solves complex mathematical problems quickly. Excellent for Training Engineering, Physics and Maths students in the principles and applications of analogue computers. Features include: 9 d.c. operational amplifiers with provision for balancing without removing problem setup. 3 meter ranges, built-in power supplies incl. 3 initial condition supplies, repetitive oscillator, 5 co-efficient potentiometers. Assortment of components and leads included for problem setting up. Separate operational manual supplied with kit. Modern styling, compact size 19½in. x 11½ x 16in. deep. Wt. 36lb.


Kit.....£97.8.0 Assembled £122.0.0



HARMONIC DISTORTION METER Model IM-12U

Will give fast, accurate noise and distortion measurement in amplifiers, receivers, transmission lines, speakers, etc. Measurements are read directly on large meter. High input impedance, precision components and Wien bridge circuit design assure excellent sensitivity and high accuracy in all applications. Freq.: 20 cycles to 20,000 cycles. Distortion: 1, 3, 10, 30, 100% f.s.d. Voltmeter; 0, 1, 3, 10, 30 volts f.s.d. Input resistance 300kΩ. Dimensions 13in. x 8½in. x 7in. deep. Weight 11lb.

Kit.....£26.15.0 Assembled £36.0.0

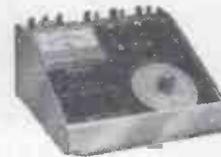

TRANSISTOR TESTER Model IM-30U

Unmatched for quality and performance at the price.

Provides a complete d.c. analysis of PNP and NPN transistors and diodes. D.C. gain (Beta, Alpha) is read direct on calibrated scales. Four lever switches facilitate fast, easy, test selection. Internal batteries for tests up to 9 v. Provision for connection to ext. power supply for higher voltage and current tests. Modern functional styling. Size 5½in. high x 10½in. deep x 10½in. wide.

Kit.....£25.18.0 Assembled £36.10.0

Many other models for Hi-fi enthusiasts, Radio Amateurs etc. See other page for details.

● Prices quoted above are Mail Order prices ●

● Prices include free delivery in U.K. ●

DAYSTROM LTD.

DEPT. W.W.11, GLOUCESTER, ENGLAND

FREE BROCHURE AVAILABLE ON THE BRITISH INSTRUMENT RANGE OF MODELS
ALSO "AMATEUR" RADIO BROCHURE COVERING BRITISH & AMERICAN MODELS

WW-136 FOR FURTHER DETAILS.

So easy to build

Heathkit

DAYSTROM

So easy to use

Enjoy the BBC stereo FM transmissions with the New De Luxe

TRANSISTOR STEREO FM TUNER (Model TFM-IS)

Mono version TFM-IM also available.

Designed to harmonise and match the "International Class" de luxe transistor amplifier, AA-22U

- ★ Professional, elegant, slim-line styling.
- ★ Tuning range 88-108 Mc/s.
- ★ 14 Transistor, 4-diode circuit.
- ★ Pre-assembled, pre-aligned RF Tuning heart.
- ★ 4 stage I.F. amplifier.
- ★ Own built-in power supply.

Available for your convenience in separate parts and can be built for a

Total price kit Model TFM-IM (Mono) £20.19.0 incl. P.T.

Total price kit Model TFM-IS (Stereo) £24.18.0 incl. P.T.

Optional extra: Walnut veneered cabinet £2.5.0.

Trim and brackets for cabinet mounting GMKI. £1.18.0.



**The Outstanding
20 + 20 WATT TRANSISTOR
STEREO AMPLIFIER
Model AA-22U**



This "International Class" amplifier offers you a realism and beauty of music never before obtainable at such a competitive price.

- ★ Professional, elegant, compact, slim-line styling.
- ★ The best of American transistor techniques in a British amplifier.
- ★ Beautiful walnut veneered, fully finished cabinet available as an optional extra.
- ★ 5 stereo inputs (five on each channel) accommodate pick-up, radio tuner, tape and two other sources.
- ★ 20 transistor 10 diode circuit.
- ★ Dimensions: 15 1/2 in. wide x 3 in. high x 12 in. deep.

Kit **£39.10.0** less cabinet Assembled **£59.15.0** inc. cabinet

Walnut cabinet for free standing use £2.5.0 extra.

Trim and brackets for cabinet mounting GMKI. £1.18.0.

COMPARE ANY HEATHKIT MODEL FOR PRICE, PERFORMANCE, QUALITY

**3+3 W HI-FI STEREO AMPLIFIER
KIT Model S-33H**

An inexpensive stereo-mono amplifier with the high sensitivity necessary for lightweight miniature ceramic pick-ups (e.g., Decca Deram). De luxe version of the S-33 with attractive two-tone grey Perspex panel.

Kit **£15.17.6** Assembled **£21.7.6**

**5 W HI-FI MONO AMPLIFIER
KIT Model MA-5**

A low-priced general purpose Hi-Fidelity amplifier based on the popular S-33 for those who do not require a stereophonic system. Separate bass and treble controls. Gram and Radio inputs. Suitable for most crystal pick-ups. A printed circuit simplifies construction.

Kit **£11.9.6** Assembled **£15.15.0**

**HI-FI MONO POWER AMPLIFIER
KIT Model MA-12**

A compact Hi-Fidelity power amplifier (including auxiliary power supply), 12 watts output. Wide frequency range and low distortion. A variable sensitivity control is fitted enabling it to be used with an existing amplifier in a stereophonic system. Other applications includes sound reinforcement systems, transmitter modulators, for use with tape recorders, also as a general purpose laboratory amplifier.

Kit **£12.18.0** Assembled **£16.18.0**

**STEREO CONTROL UNIT KIT
Model USC-1**

Incorporates all worthwhile features for Hi-Fidelity stereo and mono. Push-button selection, accurately matched ganged controls to ±1 dB. Negative feedback rumble and variable low-pass filters. Printed circuit boards. Accepts inputs from most tape-heads and any stereo or mono pick-up.

Kit **£19.19.0** Assembled **£27.5.0**

HEATHKIT-THOMAS (Transistorized) ELECTRONIC ORGAN KIT (with Color-Glo) Model GD-325E

Can be built with no knowledge of electronics.

Kit **£205.0.0** Bench **£14.10.0**

(Price includes carriage and duty)

AVAILABLE SHORTLY
Transistor FM Stereo Decoder, Model SD-1. Self powered. Can be used with any tuner having facilities for multiplex output.
Kit **£8.10.0** Assembled **£12.5.0**
High Performance Car Radio, Model CR-1. Outstanding value for money and dependability.
Total Price Kit (excluding speaker) **£12.17.0**
Full range of accessories also available.

HI-FI EQUIPMENT CABINETS

A range of equipment cabinets is now available. Designed for maximum operating convenience or for where room space is an over-riding consideration, this range includes easy-to-build kits or ready-assembled cabinets in the white for finish to own requirements. Prices from **£11/18/6** kit.



"MALVERN" (Illustrated) Kit, **£18.1.0** (inc. P.T.). Assembled (left in the white) **£23.6.0**.

How to Install Hi-Fi in YOUR home

If you are planning to install a Hi-Fi system in your home, and are uncertain of the type of equipment to use, our widely experienced technical staff will with pleasure put forward recommendations. All you have to do is state the type of installation contemplated, the price you are prepared to pay and give details of existing equipment you wish to include, if possible.

**HI-FI STEREO AMPLIFIER
KIT Model S-99**

18 w. output (9 per channel with 0.2 per cent. distortion at 9 w. per channel). It has ganged controls. Stereo/Mono gram, radio and tape recorder inputs and push-button selection. Ultra-linear push-pull output. P.C. boards. Attractive Perspex front panel with golden surround and grey metal cabinet.



Kit **£28.9.6** Assembled **£38.9.6**

AMERICAN HEATHKIT MODELS

Fully illustrated American catalogue with full details of models for home, Amateur, Industry, etc., sent for only 1/- post paid.

Deferred Terms available on orders above £10

**MONO CONTROL UNIT KIT
Model UMC-1**

Ideal for use with MA-12 or similar amplifier. Output 0.25 v. Send for full details.

Kit **£9.2.6** Assembled **£14.2.6**



**HI-FI SPEAKER SYSTEM KIT
Model SSU-1**

Ducted-port bass reflex cabinet "in the white." Frequency response is 40-16,000 c/s. Power rating 10 watts. Matched speaker units 8in. high flux (12,000 lines) with hyperbolic cone and 4in. wide angle dispersion type for higher frequencies.



Kit (with legs) **£12.12.0** (less legs) **£11.17.6** (inc. P.T.)

"COTSWOLD" SPEAKER SYSTEM KIT

This acoustically designed enclosure measures 26 x 23 x 14 1/2 in., and houses a special 12in. base speaker with 2in. speech coil, elliptical middle speaker together with a pressure unit to cover the full frequency range of 30-20,000 c/s. Its polar-distribution makes it ideal for really Hi-Fi Stereo. Delivered complete with speakers, cross-over unit, level control, grille cloth, etc. Left in the white for finish to personal taste, all parts are pre-cut and drilled for ease of assembly.



Kit **£25.12.0** Assembled **£33.17.0**

"COTSWOLD M.F.S." SPEAKER SYSTEM KIT

This model, based on the standard Cotswold, measures only 36in. high, 16 1/2 in. wide by 14in. deep. Particularly recommended to those who require the best results in small rooms.



Kit **£25.12.0** Assembled **£33.17.0**

DAYSTROM LTD.

DEPT. W.W.11, GLOUCESTER, ENGLAND

Member of the Schlumberger Group including the Heath Company.

MANUFACTURERS OF THE WORLD'S LARGEST-SELLING ELECTRONIC KIT-SETS

WW-137 FOR FURTHER DETAILS.

SAVE MONEY BUILDING ANY HEATHKIT MODEL



THE QUALITY KIT-SETS ANYONE CAN BUILD



"STARMAKER 33" TRANSISTOR PA/GUITAR AMPLIFIER Model PA-2

This is a high performance amplifier whose size and weight allows easy transportation. Ideal for vocal and instrumental groups, P.A., electronic organs, guitars, etc. Features include: 20w. amplifier (33 watts. I.H.F.M.), two heavy duty speakers, 4 inputs on two channels, variable tremolo, modern elegant cabinet. Size: 18in. h. x 29in. w. x 10in. deep. Wt. 51 lb.

Castors or legs available as optional extras.

Kit.....£39.19.0 Assembled £54.10.0

A WELL DESIGNED F.M. TUNER Model FM-4U

Tuning range 88-108 Mc/s. Flywheel tuning. Attractive Plastic Front Panel in two-tone grey with golden trim surround and motif Thermometer type visual tuning indicator. Pre-aligned. I.F. transformers. Three I.F. stages. Wide-band low distortion Ratio Detector. R.F. Unit, wired, tested and pre-aligned. Printed circuits for I.F. amplifiers and ratio detector. Built-in power supply. Heathkit model SD-1 Stereo Decoder can be used with this tuner and with the AM/FM Tuner.

TUNER UNIT Model FMT-4U with 10.7 Mc/s. I.F. output. £2/15/- (inc. P.T.)
I.F. AMPLIFIER and power supply Model FMA-4U complete with case and valves, £13/13/- Sold separately.

Kit Total.....£16.8.0



BERKELEY Slim-line SPEAKER SYSTEM

A new concept in Heathkit loudspeaker design. The cabinet shell is assembled and finished in superb Queensland walnut veneer. Two specially designed speakers, a 12in. bass unit and 4in. mid/high frequency unit and an L.C. cross-over network provide the smooth 30-17,000 c/s. frequency response. Its professional cabinet styling will blend with both traditional and contemporary decors. 15 ohm nominal impedance. Size 26" x 17" x 7 1/2" deep.

Kit.....£19.10.0 Assembled...£24.0.0

"OXFORD" LUXURY TRANSISTOR PORTABLE Model UXR-2

This superb transistor radio is the ideal domestic or personal portable Medium and Long Wave receiver. Solid leather case and handle. Easy-to-read tuning scale. Extra large loudspeaker. Push-button L, MW and tone. 10 semi-conductors (7 transistors plus 3 diodes). Sockets for personal earphone, tape recorder, car aerial. Internal 9-volt battery (not supplied), lasts for months. Latest printed circuit techniques.

Comprehensive easy-to-follow, fully illustrated Instruction Manual.

Kit.....£14.18.0 incl. P. Tax



MULTIMETER KIT Model MM-1U

Provides wide voltage, current, resistance and dB ranges to cover hundreds of applications. Sensitivity 20,000 ohms/volt D.C. and 5,000 ohms volt A.C. Ranges: 0-1.5 v. to 1,500 v. A.C. and D.C.; 0-150µA to 15 A. D.C. measures resistance from 0.25Ω to 20MΩ. 4 1/2in. 50µA meter. A polarity reversing switch eliminates transferring test leads when alternately measuring + and - voltages.



Kit £12.18.0 Assembled £18.11.6

A.M./F.M. TUNER KIT

Tuning range 88-108 Mc/s. (FM) 16-50, 200-550, 900-2,000 m. Flywheel tuning. Attractive Perspex front panel in two-tone grey with golden trim. Thermometer type tuning indicator, pre-aligned I.F. transformers. Switched wide and narrow A.M. bandwidths.

TUNING HEART Model AFM-TI £4/13/6 (inc. P.T.)
I.F. AMPLIFIER and Power Unit Model AFM-AI. Complete with metal cabinet and valves £22/11/6. Sold separately.



Kit Total £27.5.0

4 1/2in. VALVE VOLTMETER KIT Model V-7A

The world's most popular valve voltmeter with printed circuit and 1 per cent. precision resistors to ensure consistent laboratory performance. It has 7 voltage ranges measuring respectively D.C. volts to 1,500 and A.C. to 1,500 r.n.s. and 4,000 peak to peak. Resistance measurements from 0.1 ohm to 1,000 megohms. with internal battery. D.C. input resistance is 11 megohms and dB measurement has a centre-zero scale. Complete with test prod, leads and standardising battery. Power requirements, 200-250 v. 40-60 c/s. A.C. 10 watts.



H.V. and R.F. Probes available as optional extras.
Kit £13.18.6 Assembled £19.18.6

OSCILLOSCOPE TRACE DOUBLER KIT Model S-3U




This device will extend the use of your single-beam oscilloscope and, at a nominal cost, will give you the advantages of a double (or other multiple) beam scope.

Kit £13.10.0 Assembled £19.10.0

DUAL-WAVE TRANSISTOR PORTABLE RADIO KIT Model UXR-1

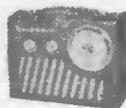Presented in elegant real hide case with tasteful gold relief. Can be assembled in 4 to 6 hours and you have a set in the top flight of transistor portables. Pre-aligned I.F. transformers, printed circuit and a 7in. x 4in. high flux speaker.



Covers both Long and Medium waves. Dimensions 9 1/2in. x 7 1/2in. x 3 1/2in.

Kit £12.11.0 (inc. P.T.)

6in. VALVE VOLTMETER Model IM-13U

Modern styling. Many extra features. Unique gimbal bracket allows bench, shelf or wall mounting. Measures A.C. and D.C. volts 0-1.5, 5, 15, 50, 150, 500, 1,500. Resistance 0.1 to 1,000MΩ. Size 5in. x 12 1/2in. x 4 1/2in. Complete with test prod and leads.




Kit £18.18.0 Assembled £26.18.0

DECADE RESISTANCE BOX KIT Model DR-1U, Range 1-99,999Ω in 1Ω Steps. Ceramic switches throughout. Current rating from 500 mA. to 5 mA. according to decades in circuit. Polished wooden cabinet supplied complete.

Kit £10.18.0 Assembled £14.18.0

AUDIO SIGNAL GENERATOR KIT Model AG-9U

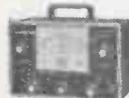

10 c/s. to 100 kc/s., switch selected. Distortion less than 0.1%. 10 v. sine wave output metered in volts and dB's.

Kit £23.15.0 Assembled £31.15.0

SINE/SQUARE GENERATOR Model IG-82U

Covers 20 c/s.-1 Mc/s. in 5 bands. Simultaneous Sine and Square Wave outputs. Less than 0.15µs rise time and on Square Wave. Less than 0.5% distortion on Sine wave. Up to 10 volts output. This attractively styled generator is designed for maximum operating convenience. Size 13in. x 8 1/2in. x 7in. deep.



Kit £25.15.0 Assembled £37.15.0

OSCILLOSCOPE ACCESSORY KITS

Demodulation Probe kit 337-C £2.17.6

Low-cap Attenuator Probe kit PK-1 £3.12.6

● Prices Include Postage U.K.

ELECTRONIC WORKSHOP KIT EW-1

20 exciting experiments can be made with this one kit. Kit £7.13.6 (incl. P.T.)

● Deferred Terms available on all orders above £10.

TELEVISION ALIGNMENT GENERATOR KIT Model HFW-1

Offers the maximum in performance, flexibility and utility at the lowest possible cost. Several outstanding features have been incorporated in this model which are unusual in instruments in this price range. Frequency coverage 3.6 Mc/s. to 220 Mc/s. on fundamentals. Unique non-mechanical sweep oscillator system. High level output on all ranges. Sweep deviations up to 42 Mc/s. Built-in fixed and variable marker generator (5 Mc/s. crystal supplied).

Kit £38.18.0 Assembled £49.15.0

● Prices quoted are Mail Order Prices.

DAYSTROM LTD.

DEPT. W.W.11, GLOUCESTER, ENGLAND
Member of the Schlumberger Group including the Heath Company.

MANUFACTURERS OF THE WORLD'S LARGEST-SELLING ELECTRONIC KIT-SETS

WW-138 FOR FURTHER DETAILS.

Thoroughly



dependable

AMATEUR TRANSMITTER KIT



Model DX-40U
Covers all amateur bands from 80 to 10 metres, crystal controlled. Power input 75 watts C.W. 60 watts peak controlled carrier phone. Out-put 40 watts to aerial. Provision for VFO. Filters minimise T.V. interference. Modulator and power supplies are built-in. Single knob band switching is combined with a pl-network output circuit for complete operating convenience. A high-grade moving-coil meter indicates the final grid or anode current. Provision is made for the use of 3 crystals with access through a trap-door in the back of the cabinet. A 4-position switch selects the appropriate crystal or a jack for external VFO which can be used instead of the crystal(s).
Prices now reduced to:-
Kit .. £29.19.0 Assembled £41.8.0

"MOHICAN" GENERAL COVERAGE RECEIVER KIT



Model GC-1U
This fully transistorised receiver which includes 4 piezo-electric transmitters, is in the forefront of receiver design. It is an excellent portable or fixed station receiver. The R.F. "front-end" is supplied as a pre-assembled and pre-aligned unit. Its main features include a 10-transistor circuit, printed circuit board, telescopic whip antenna tuning meter, and a large slide-rule dial giving a total length of approximately 70 inches. Housed in a steel cabinet and powered by two 6 volt dry batteries (not supplied), mounted internally, it gives frequency coverage from 580 kc/s to 30 Mc/s. in five bands; thus enabling world-wide reception. Electrical bandwidth covers the amateur bands from 80 to 10 metres—each band having a scale length of approximately 8 inches, BFO tuning and Zener diode stabiliser. Size 6 1/2 in. x 12 in. x 10 in.
Please write for specification leaflet.
Kit .. £37.17.6 Asmbld .. £45.17.6

AMATEUR TRANSMITTER KIT



Model DX-100U
The World's most popular Amateur TX Kit
● Completely self-contained. 150 w. D.C. input.
● Built-in highly stable VFO and all Power Supplies.
● The KT88 high-level anode and screen modulator stage gives over 100 watts of audio from less than 1.5 mV. input.
● Keying on CW is via the VFO and buffer amplifier cathodes; the other RF valves are biased beyond cut-off.
● Provision has been made for remote control operation.
● Covers all Amateur bands up to 30 Mc/s. 'phone or CW.
Kit .. £81.10.0 Assembled .. £106.15.0

SINGLE SIDEBAND ADAPTER KIT Model SB-10U



May be used with most A.M. transmitters with certain provisions. Allows full use of existing equipment for SSB facilities. Band coverage: 80, 40, 20, 15, 10 m. Unwanted sideband suppression; better than 30 dB. Carrier suppression; better than 40 dB. Power requirements: 300 v. D.C. 85 mA (average) 30 mA (standby), 140 mA (transmit), 6.3 v. A.C., 3.5 A. Meter: 2 1/2 in. Scale edge reading, 200µA movement, indicates carrier null and relative power output. Cabinet 1 1/2 in. high x 8 in. wide x 14 1/2 in. deep. Limited stocks available.
Kit .. £39.5.0 Assembled £54.18.0

AMATEUR BANDS RECEIVER KIT



Model RA-1 The ideal economically priced fixed station, portable or mobile receiver covering the Amateur bands from 160-10 m., each band separately calibrated on a large illuminated slide-rule dial. Features: Signal strength meter, tuned RF amplifier stage, half-lattice filter, adjustable noise limiter. Freq. coverage 160, 80, 40, 20, 15, 10 metre bands, I.F. 1620 kc/s.
Kit .. £39.6.6 Assembled £52.10.0

GENERAL COVERAGE RECEIVER KIT RG-1

An inexpensive communications type receiver specially designed for the short wave listener with many refinements found only in receivers costing much more. Freq. coverage 32 Mc/s-1.7 Mc/s in 5 ranges also M.W. band. Kit .. £39.16.0 Assembled £53.0.0
Optional extras available.

AMERICAN HEATHKIT SINGLE SIDE BAND EQUIPMENT

Transmitters, Receivers, Transceivers. Send for details of models. Fully illustrated American Catalogue of Heathkit range sent for only 1/-, post-paid.

GRID-DIP METER KIT. Model GD-1U



Functions as oscillator or absorption wavemeter. With plug-in coils for continuous frequency coverage from 1.8 Mc/s to 230 Mc/s.
Kit .. £11.9.6 Assembled .. £14.9.6

REFLECTED POWER METER KIT

Model HM-IIU Indicates, reliably but inexpensively, whether the R.F. power output of your transmitter is being transferred efficiently to the radiating antenna.
Kit .. £8.10.0 Assembled £10.15.0

Additional Plug-In Coils Model 341-U extend coverage down to 350 kc/s. With dial correlation curves. 17/6.

TRANSISTOR INTERCOM KITS Models XI-U and XIR-U

9 v. battery operated. Up to five remote stations can be operated with each Master. The Master unit can call any one, combination, or all five Remote stations and any Remote station can call the Master.

Model XI-U (Master) Kit .. £11.9.6 Assembled .. £17.9.6
Model XIR-U (Remote) Kit .. £4.9.6 Assembled .. £5.18.0

VARIABLE FREQUENCY OSCILLATOR KIT. Model VF-1U

Specially designed to meet the demand for the maximum possible flexibility from an amateur Transmitter which would otherwise be subject to certain limitations imposed by crystal control. Calibrated for all Amateur bands 160-10 metres, fundamentals on 160 and 40 m. Ideal for Heathkit DX-40U and similar transmitters.
Kit .. £10.17.6 Assembled £15.19.6

BALUN COIL UNIT KIT

Model B-1U. Will match unbalanced co-axial lines to balanced lines of either 75 or 300Ω impedance. Frequency range 10-80 m., input up to 200 watts.
Kit .. £5.5.6 Asmbld. .. £5.18.0

TAPE PRE-AMPLIFIER KITS Models TA-IM and TA-IS

The Combined Tape Record/Replay Amplifier is available in both monophonic and stereo-phonetic models. Model TA-IM can be modified to the stereo version with modification kit TA-IC.
TA-IM Kit £19.18.0 Asmbld £28.18.0
TA-IS Kit £25.10.0 Asmbld £35.18.0
TA-IC Kit .. £6.15.0

All prices are mail order and include free delivery in the U.K.

Deferred Terms are available on all orders above £10

AMERICAN MARINE MODELS

- Prices include carriage, duty, Import levy, etc.
DIRECTION FINDER, MR-21A 3WB transistor circuit. Kit .. £60.5.0
DEPTH SOUNDER MI-IIA Soundings to 200ft. Kit .. £38.10.0
FUEL VAPOUR DETECTOR MI-25 Transistor circuit. Kit .. £23.10.0
TACHOMETER MI-31A 6, 12, 24 or 32 v. D.C. Kit .. £14.0.0
Please send for details.

WELCOME TO OUR LONDON HEATHKIT CENTRE

See the British Heathkit range and a selection of American models etc.
233 TOTTENHAM COURT ROAD, W.1 Tel: MUSEum 7349
We open MON.-SAT., 9 a.m.—5.30 p.m. THURSDAY 11 a.m.—2.30 p.m.
When you are In town we hope that you will visit us there.

Q MULTIPLIER KIT. Model QPM-1

A reasonably priced Q Amplifier for the amateur and short-wave enthusiast. This self-powered unit (200-250 v. 50/60 c/s) may be used with communications receivers to provide both additional selectivity and signal rejection.
Models QPM-1 for 470 kc/s. IF. QPM-16 for 1.6 Mc/s. I.F.
Kit, either model .. £8.10.0
Assembled .. £12.14.0

AERIAL TOWER KITS. Model HT-1, HT-1G

Height 32ft., sq. section 3ft. x 3ft. at base (no stays required). Accessories available as extras:
HT-1G Kit (galvanised) £43.15.0
HT-1 Kit (red oxide) £37.15.0

DAYSTROM LTD., Dept. WW11, GLOUCESTER, ENGLAND
WW-139 FOR FURTHER DETAILS.

Please send me FREE CATALOGUE (Yes/No).....
Full details of Model(s).....
NAME..... (Block Capitals)
ADDRESS.....
..... WW11

VALVES FULLY GUARANTEED INDIVIDUALLY PACKED

AC/HL 4/6	EL95 5/	KT67 15/-
AC/4 6/-	EL183 8/-	KT76 8/6
AC/CPEN/5/-	EL148 8/-	KT88 22/-
AL60 5/-	EL126 5/0	KTW61 4/6
AR5 5/-	EL145 3/0	KTW63 2/
AR/3 5/-	EL24 15/9	KTZ1 6/
AR/12 2/6	EL134 16/-	KTZ63 5/
AR/24 3/6	EA60 1/	ML90 9/
AR/TP1 6/	EA73 7/-	ML142 12/-
AT/4 2/3	EAB/80 8/9	ML81 12/
AT/7 5/6	EAC/91 3/6	ML30 12/
AZ/1 55/-	EAF/2 8/-	MH 4 5/-
AZ/7 9/	EB34 1/6	MHL/D6
BD/78 4/0	EB91 3/-	ML 10/-
BE/8 14/-	EB/33 6/-	ML 6 8/-
BL/3 10/-	EB/41 8/6	ML 17 7/-
B/4 8/-	EB/61 5/-	ML 11 7/-
B/85 2/0	EB/80 6/8	OA2 5/ 5/9
B/884 4/7/6	EB/93 7/6	OB2 3/ 6/
BT/19 25/6	EB/99 6/9	OB3 7/ 6/
BT/35 25/6	EEL/31 2/0	OC3 5/ 6/
BT/45 18/6	EC/2 8/-	OC/22 25/6
BT/83 35/6	EC/3 12/6	OC/25 12/6
CC/3L 2/	EC/70 4/-	OC/26 12/6
CP/23 10/6	EC/90 2/	OC/28 12/6
CV/71 3/	EC/91 3/-	OC/29 12/6
CV/77 6/	EC/92 4/-	OC/30 12/6
CV/103 1/	EC/93 2/	OC/31 12/6
CV/103 1/	EC/94 2/	OC/32 12/6
CV/4004 7/	EC/95 2/	OC/33 12/6
CV/4014 7/	EC/96 2/	OC/34 12/6
CV/4015 5/	EC/97 2/	OC/35 12/6
CV/4025 10/	EC/98 2/	OC/36 12/6
CV/4049 6/	EC/99 2/	OC/37 12/6
CV/31 6/	EC/100 2/	OC/38 12/6
D1 1/ 1/8	EC/101 2/	OC/39 12/6
D41 1/ 3/3	EC/102 2/	OC/40 12/6
D61 1/ 3/3	EC/103 2/	OC/41 12/6
D77 1/ 3/3	EC/104 2/	OC/42 12/6
DA/30 12/6	EC/105 2/	OC/43 12/6
DA/96 6/	EC/106 2/	OC/44 12/6
DD/1 4/	EC/107 2/	OC/45 12/6
DE/5 8/	EC/108 2/	OC/46 12/6
DE/20 2/	EC/109 2/	OC/47 12/6
DE/25 15/	EC/110 2/	OC/48 12/6
DF/1 3/	EC/111 2/	OC/49 12/6
DF/2 3/	EC/112 2/	OC/50 12/6
DF/6 6/	EC/113 2/	OC/51 12/6
DH/63 5/	EC/114 2/	OC/52 12/6
DK/92 8/	EC/115 2/	OC/53 12/6
DK/96 6/	EC/116 2/	OC/54 12/6
DL/2 4/	EC/117 2/	OC/55 12/6
DL/3 4/	EC/118 2/	OC/56 12/6
DL/4 5/9	EC/119 2/	OC/57 12/6
DL/6 7/	EC/120 2/	OC/58 12/6
DL/10 7/	EC/121 2/	OC/59 12/6
DY/8 7/6	EC/122 2/	OC/60 12/6
EB/87 23/	EC/123 2/	OC/61 12/6

PY33 9/6	U52 4/6	Y65 4/	4C27 35/-
PY80 5/6	U91 11/6	Y66 8/	4D1 4/
PY81 5/6	U80 17/-	Z800U 20/-	5A173G 5/-
PY82 5/6	UAB/80 6/	Z801U 10/-	5A174G 5/-
PY83 5/6	UB/41 8/-	1A5 7/	5B25LM40/-
PY800 8/	UAF/2 9/	1A5GT 5/	5B263M15/-
PZ1-36 9/	UBF/80 5/6	1B22 3/0	5B/204M
PZ1-76 12/-	UBP/89 6/8	1C5GT 6/	40/-
QP21 6/	UBL/21 10/	1D8GT 6/	5B/255M
QP25 5/-	UC/85 6/6	1E7G 7/8	35/-

TRANSISTORS

OC18 20/-	OC81D 5/-	OC209 15/6	XO142 15/-
OC22 25/6	OC81M 7/-	OC203 12/6	XO165 20/-
OC25 12/6	OC82 10/	OC204 17/6	XO165 22/6
OC35 12/6	OC82DM5/-	OC206 23/6	6/8
OC44 6/	OC83 5/	AAZ12 6/	2N412 7/6
OC45 6/	OC83B 5/	AC128 7/6	2N412 47/-
OC71 6/8	OC122 18/-	BC211 7/6	2N1090 10/6
OC72 6/	OC170 6/	BY38 7/6	2N1090 29/
OC73 10/	OC200 10/6	XC141 10/	2N1091 29/
OC81 5/	OC201 12/6		
QP230 5/-	UCH42 8/-	1P2 4/	6R4G 9/
QS150-15 10/-	UCH81 6/	1G6GT 6/	6T4 7/
	UC/62 8/	1L4 2/6	6U4 4/
QS95/10 5/6	UC/83 9/	1LA6 6/	6V4G 8/6
RS1202 9/	UF41 7/	1L6 7/	6X43 8/6
QV047 8/	UF89 6/	1LH 4/	6Y3G 4/6
R3 3/	UL1 7/6	1N21B 5/	6Y4GT 5/
R10 9/	UL84 5/6	1N43 4/	6Y6 2/
RG4/1260 5/	U/5 7/	1N70 4/	6Z4G 9/
RE/72 60/-	U/9 8/8	1B4 8/	6Z4GT 8/
QV047 8/	UY21 7/6	1B5 3/6	6Z4GT 8/
S130 12/6	UY41 6/6	1B4 8/	6AB7 4/
SP2 2/	UY85 5/	1B5 3/6	6AB7 2/
SP41 1/6	V1120 4/	1T4 3/	6AG5 2/6
SP61 1/	V1607 5/	2A3 5/	6AG7 6/
SP210 3/6	V1223 20/-	2C26 7/	6AK6 10/
STV280/40 18/-	VP23 3/	2C28A 3/	6AJ7 3/
	VP133 9/	2C28A 2/6	6AK5 5/
SU2160A 10/	VR99 8/	2C45 22/6	6AK6 6/
	VR160/30 5/	2C46 30/	6AK7 6/
S11E12 10/	VR103 5/	2D21 12/	6AL5 7/
T41 10/	VR150/30 5/	2X2 3/	6AM5 2/6
TD04-20 70/-	VU33A 4/	3A4 4/	6AM6 4/
TP22 5/	VU39 6/	3A/108A 20/	6AQ6 7/
TP25 15/-	VX3206 5/	3A1463 35/	6AQ5W 9/
TT11 5/	VX3276 4/	3A167M 6/	6AR6 4/
TT15 35/-	VX8122 5/	3A167M 6/	6AR6 4/
TR31 45/-	VX8124 5/	3B7 25/	6AR7 20/
TZ0502 4/	W21 5/	3B7 25/	6AT6 4/
TZ220 16/-	W118 8/	3B9A 5/	6AU6 7/
U61 8/	W119 2/	3B6 4/	6AX4 8/
U12 14/	X6 7/6	3Z29 5/0	6B7 5/
U17 5/	X118 8/	3Q4 6/	6B4G 16/
U26 11/-	X145 8/	3Q5GT 7/6	6B8G 2/6
U27 5/	Y3 6/	3B4 5/	6BA6 5/
U60 4/	Y63 6/	3B4 5/	6BA7 5/

6BE6 6/	6887 2/	26Z4G 8/6	955 2/6
6B/6 7/6	6U4GT 9/6	26Z5 7/6	956 2/
6B/7 7/	6V8G 5/	26Z6GT 8/6	957 5/
6B/7A 8/	6V9GT 7/6	26Z7T 8/6	958A 4/
6BR7 9/	6V8M 8/	30 300 5/	1512 5/
6BW6 8/	6X4 3/6	30C16 9/	1616 3/
6C4 2/	6X5G 5/	30C18 11/	1819 5/
6CGG 2/6	6X6GT 5/3	30F5 8/6	1825 6/
6C/2 6/	6Y6G 5/	30FL1 10/6	1828 3/
6C/4 4/	6-30L2 10/	30L16 11/	1829 4/6
6C/6 3/	6Z4 5/	30P12 10/	2051 5/
6C/8 3/	7B7 7/6	30P19 15/	4043C.13/6
6C/91 80/	7C5 10/	30P18 8/	4043 3/
6C/92 4/6	7C8 7/	30P/EL3 27/8	4313C.30/
6C/16 9/	7D7 7/	35L6GT 7/	5704 9/
6C/14 12/	7H7 7/3	35T 17/6	6726 6/
6D6 3/	7Q7 7/	35W 5/	6080 5/
6E5 6/	7B7 18/	35Z3 10/	6084 7/
6F0GT 5/9	7V7 5/	35Z4GT 8/	6085 6/
6F/6 4/	7Y4 8/	3Z0GT 6/	6085 29/
6F7 6/	7Z4 4/6	37 300 4/	6146 25/
6F/8 6/6	8D2 2/6	38 4/	6193 1/9
6F/12 4/8	9D2 3/	60C/6G27/8	7475 2/
6F13 5/	9D6 3/6	60L6GT 8/	8013A.36/
6F17 5/	10P9 9/	53A 7/6	957 5/
6F32 4/	12A6 2/6	55 6/	9001 3/
6F33 3/	12A7 5/	55 6/	9002 4/6
6G0G 2/6	12A7 5/	59 6/	9003 6/
6H6M 1/6	12A7 4/	75 6/	9004 2/6
6J4WA 10/	12A7WA 7/	76 6/	9006 2/6
6J5 5/	12A7 5/8	78 6/	
6J6 3/	12A7 5/8	80 6/	
6J6W 6/	12A7 6/	81 6/	
6J7G 5/	12A7 7/	84 6/	
6K/6 6/	12B6 6/	85A2 3/	
6K/6GT 5/6	12B6 7/	120VPT 7/	
6K/7 2/	12B7 7/	7-pin/2/6	
6K/7GT 4/9	12C8 3/	2158G 6/	
6K/8 3/	12H6 2/	220PA 7/	
6K/8GT 8/8	12J6GT 2/6	220TH 4/	
6K/9M 6/	12K6 6/	225D/3 9/	
6L6 6/	12K7GT 2/	307A 5/6	
6L6GA 7/6	12K8M 10/	313C 25/	
6L6M 11/	12Q7GT 3/8	357A 70/	
6L7G 4/	128A7 3/	368A 5/	
6L7G 4/	128A7 3/	393A 15/	
6L/20 5/9	128GT 5/	420GT 5/	
6N7 5/	128H7 3/	703A 30/	
6N7G 5/9	128J7 5/9	705A 10/	
6P25 12/6	128K7 5/	715B 50/	
6Q/7 5/	128N7GT5/9	717A 4/	
6Q/7 5/	128T7 5/	724A 18/	
6R47 9/	12Y4 2/	801 6/	
6R47GT 6/6	1417 7/	803 22/6	
6R/7 1/	1487 18/	807 8/	
6R/7GT 6/	16D2 6/	808 8/	
6R/7 5/	1E2 18/	813 35/	
6R/8 5/	1R53 20/	819 22/	
6R/7 5/	1R/7 5/	829B 50/	
6R/7GT 5/6	1R/11 6/	830B 4/	
6R/7Y 6/6	1R/11 5/	832A 45/	
6R/8 7/	20P4 12/6	843 5/	
6R/7GT 5/6	21B6 5/	866A 14/	
6R/8 3/6	21L6GT 6/	88Y 10/	
6S/2GT 6/	25T5 6/	964 4/	

H.R.O. SENIOR TABLE MODEL TYPE M 50 Kc/s-30 Mc/s with "S" meter and crystal filter in excellent fully checked and tested condition together with set of 8 general coverage coils and mains P.S.U. 110-220 v. £26/10/-. Carriage and packing 30/-.

RACK MODEL also available at the same price. "S" Meter for H.R.O. Receivers, Brand new £2/10/0. Carriage paid U.K.

TR 50 XM TRANSMITTER/RECEIVER INSTALLATION, four channel TX provision for crystal or master oscillator. Frequency 1.5-12Mc/s. Output 50w. Complete with all accessories, alternatively Dynamotor power unit for 12v. D.C. operation or P.S.U. 110/220v. A.C. Full details and prices upon request.

TELEPHONE HANDETS. Standard G.P.O. type; new 12/-.. P. & P. 2/-.

INSET MICROPHONE for telephone handset 2/6. P. & P. 2/-.

1 KW ULTRASONIC GENERATOR together with power supply unit for 200-250 v. A.C. Complete two chassis with interconnecting cables. Frequency 37 to 43 kc/s adjusted by fine control. Peak output 12 kw, average output 500 w. Completely new with valves and manual, £65, carriage paid U.K.

Large selection of mains and Heavy Duty L.F. TRANSFORMERS.

VARIOMETER for No. 19 sets, 17/6. P. & P. 3/-.
PANEL METERS
 0-3 amp. R.F. 2in. square..... 20/-
 100mA A.C. 3 1/2in. round..... 25/-
 15 v. A.C. 2 1/2in. round..... 20/-
 150 v. A.C. 2 1/2in. square, black dial..... 25/-

20-480 MC/S FREQUENCY METER TYPE TS 323/UR. High frequency version of BC221. Accuracy better than 0.05%. Battery operated (6 v. and 130 v.). In new condition with proper calibration charts. Laboratory tested and guaranteed. £60.

MARCONI SIGNAL GENERATOR TYPE TF 801B/3/5



Frequency range 12-485 Mc/s in five ranges. Directly calibrated frequency dial. Output waveform: C.W. sine wave A.M., pulse A.M. (from ext. source only). Internal modulation frequency 1,000 c/s. Output a, normal—continuously variable directly calibrated from 0.1µv.—0.5 v. b, high; up to 1 v. modulated for 2 v. unmodulated, output impedance 50 ohms. Fine frequency tuning control, carrier on/off switch, built-in crystal calibration for 2 Mc/s and 10 Mc/s. Stabilised voltage supply. In excellent "as new" condition. Laboratory checked and guaranteed. £115. Carr. 30/-. Including necessary connectors, plugs and instruction manual.

MARCONI VALVE VOLT METER TYPE TF 428-B

1.5 v. to 150 v. RMS in five ranges. A.C. and D.C. stabilised power supply. Complete with probe unit for RF measurements. In new condition and Laboratory tested, £12/10/-. Carriage 10/-.

A.R.88D. RECEIVERS. Fully reconditioned, £55-Rebuilt model £85. Carriage paid U.K.

SPARES FOR A.R.88D. RECEIVERS
 Ask for your needs from our huge selection.

P. C. RADIO LTD.
 170, GOLDHAWK RD., W.12
 SHEpherd's Bush 4946

WELL PROVEN RELIABLE COMMUNICATIONS RECEIVER P.C.R.3

(Made by Pye) 3 bands, 1 medium wave, 2 120-43m, 3: 43-13m. Overall sensitivity 1-2µv. S/noise ratio 10 db. at 6µv. Circuit incorporates an R.F. stage, two I.F. stages, tone control, A.V.C. antenna trimmer, 6V6 output. Set in new condition together with headphones. Speaker plug, £9/5/6. With vibratory supply unit, 12 v., £10/4/6. With specially built in P.S.U. for 210-250 v. A.C., £11/17/6. Carriage either set 10/-.

C.R.100 RECEIVER. 60 kc/s.-420 kc/s., 500kc/s-13 Mc/s. In 6 bands, 2 HF stages, 3 IF stages, AVC on both phone and C.W. Excellent condition, correctly tuned and guaranteed, £31. Carriage 30/-.

C.R.150/2. Frequency coverage. 1.5-22 Mc/s in 4 bands. Price £26. Carriage 30/-. A.C. P.S.U. for above, £4/10/-.

ULTRA MODERN POWER SUPPLY UNIT. Supply voltage A.C.: 105, 110, 115, 200, 205, 210, 220, 225, 230, 240, 245, 250 v. Available voltages D.C. (a) 1700-1900 v. Stabilised, adjustable approx. 1 mA. (b) HT2 approx. 45 mA. (c) 260-350 v. stabilised, adjustable, approx. 45 mA. (d) 450 v. approx. 30 mA. (e) 50 v. approx. 150 mA. (f) 4.5 v. A.C., 4.5 amp. common earth. (g) 6.3 v. A.C., 4.5 amp. common earth. 5 valves, 7 silicon rectifiers, 4 Solenium HV rectifiers. Brand new, £9/10/-. Carriage 12/-.

PHASE MONITOR ME-63/U. Manufactured recently by Control Electronics Inc. Measures directly and displays on a panel meter the phase angle between two applied radio frequency signals within the range from 20-20,000 c.p.s. to an accuracy of ±1.0°. Input signals can be sinusoidal or non-sinusoidal between 2 and 30 v. peak. In excellent condition together with handbook and necessary connector. £45. Carriage 30/-.

32/44FT. AERIALS each consisting of ten 3ft., 1/2in. dia. tubular screw-in sections, 14ft. (7 section) whip aerial with adaptor to fit the 1/2in. rod, insulated base, stay plate and stay assemblies, pegs, reamer, hammer, etc. Absolutely brand new and complete, ready to erect, in canvas bag, £3/9/6. P. & P. 10/6.



PORTABLE OSCILLOSCOPE CT.52

A compact general purpose instrument with many unusual features. Size 9in. high, 8in. wide, 1 1/4in. deep. Time base 10 c/s to 40 Kc/s. Y plate sensitivity 40V per cm. Tube 2 1/2in., Frequency compensated amplifier up to 38 dB gain. Bandwidth up to 1 Mc/s. Single sweep facilities. Operates from A.C. mains 100-250 volts 50 c/s. Complete with all test leads, metal transit case, instruction book and circuit diagram. **BRAND NEW.** Tested and guaranteed. £22/10/- Carr. 10/-.

ADVANCE TEST EQUIPMENT

- H1B Audio Signal Generator..... £30 0
- J1B Audio Signal Generator £30 0
- J2B Audio Signal Generator £35 0
- TT1S Transistor Tester £37 10
- VM76 AC/DC Valve Voltmeter £72 0
- VM77C AC Millivoltmeter £40 0
- VM78 AC Millivoltmeter (transistorised) £55 0
- VM79 UHF Millivoltmeter (transistorised) £125 0

These are current production, manufactured in U.K. by Advance Electronics Ltd. (not discontinued models). **BRAND NEW**, all in original sealed carton. Carr. 10/- extra per item.

OSCILLOSCOPE TYPE 13A

Double beam. Time base 2 c/s. to 750 Kc/s. Band width up to 5 Mc/s. Calibration markers at 100 Kc/s. and 1 Mc/s. Cathode follower probe for H.F. testing. Operates from A.C. mains 100 to 250 volts. A completely reliable quality instrument. Supplied fully checked with all leads, graticule, visor, circuit etc. £22/10/- Carr. 30/-.

PCR-1 and PCR-3 RECEIVERS

Brand new condition. 3 wavebands. R.F. stage, 6 valves. PCR-1 860-2080 metres, 190-570 metres, 5.6-18 Mc/s. internal speaker. PCR-3 190-570 metres, 2.3-7.3 Mc/s. 7.0-23 Mc/s. required external 3 ohm speaker. External Power Supply required or can be fitted with internal Mains Power Supply for £2 extra. Circuit supplied. Fully tested prior to despatch. £8/19/6. Carriage 10/6. Fuller details upon request. Brand new external Power Supply Units, Vibrator Unit for operation from 12 v. car battery, for caravans or boats 15/6 or A.C. Mains Units £2. Carriage 5/6.

HAMMARLUND SP-600-JX

20 valve dual conversion superhet receiver covering 540 Kc/s to 54 Mc/s in 6 bands. This is a professional quality receiver of recent design with stability of 0.01% or better. Second channel rejection 74 dB down and spurious responses are at least 100 dB down. Bandwidth from 200 c/s to 13 Kc/s. Crystal filter with crystal phasing control. Operates directly from A.C. mains 90-260 v. 50-60 c/s. Original cost £510. Supplied overhauled and in first class working order £100. Fuller details on request.


**CINTEL EQUIPMENT
ELECTROLYTIC CAPACITANCE AND INCREMENTAL
INDUCTANCE BRIDGE No. 36601**

A modern instrument, all solid state, which accurately measures the capacity of electrolytic condensers from 0.1µF to 1,000µF under operating conditions. Leakage current and polarizing voltage are separately metered. Inductances from 100 mH to 100 H can also be measured with currents up to 100 mA. A.C. mains operation. Unused with handbook. £100.

WIDE RANGE CAPACITANCE BRIDGE. No. 1864.
A matching instrument to the above. All solid state. Mains operation. Measures from 0.002pF to 100µF. Unused with handbook. £100.

HICKOCK OSCILLOSCOPE OS-8B/U

A high grade general purpose instrument made to exacting U.S.A. Navy specification. Detachable cover with carrying handle. Compact (13 1/4 x 6 x 8 1/2 in.), weight 17 lbs. Green trace 3in. tube. Bandwidth "Y" amplifier D.C. to 2 Mc/s (D.C. coupled). Sensitivity 40 mV/cm. "X" amp. can be used separately, similar spec. to "Y" amp. Leads are housed in case. For A.C. mains 105 to 125 v. 50 to 1,000 c/s. **BRAND NEW**, tested and guaranteed. £25. Carr. 10/-. Auto transformer 15/6 extra.

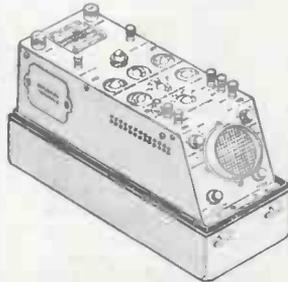

CHARLES BRITAIN (Radio) LTD.

11 UPPER SAINT MARTIN'S LANE
LONDON, W.C.2. Temple Bar 0545

Near Leicester Sq. Station. (Opposite Thorn House)
Shop hours: 9-6 p.m. (9-1 Thursdays). Open all day Saturday.



AVO VALVE CHARACTERISTIC METER. This well known instrument comprehensively tests old and modern types. In very good condition, fully tested, together with a **BRAND NEW** copy of the Avo Valve Testing Manual (1964 Edition). £30. Carr. £1.

**PHASE MONITOR ME-63/U
(AN-URM-67)**

Designed to measure directly the phase angle between two applied audio frequency signals of from 20 to 20,000 c.p.s. +1%. Direct indication on a panel meter. Input can be sinusoidal or non-sinusoidal from 2 to 30 volts peak. Of recent manufacture (1957) by Control Electronics Inc. and ex-U.S.A. Air Force. In first class condition with handbook. A complex instrument with 19 valves. £40. Carr. 30/-.

T.C.C. METALPACK CONDENSERS. 0.1 mfd. 500 v. D.C. wkg. at 70°C. Brand new, polythene wrapped, 7/6 doz., or £2 per 100.
T.C.C. METALMITE 350v. D.C. wkg. 0.1 mfd. (CP37N); 0.05 mfd. (CP35N); 0.01 mfd. (CP.32N) all at 5/6 doz., or 32/6 per 100
SPRAGUE METAL CASED CONDENSERS 0.01 mfd. 1,000 v. D.C. wkg., 5/6 doz., or 32/6 per 100.

T.C.C. VISCONAL CONDENSERS. 8 mfd. 800 v. D.C. wkg. at 71°C. CP 152 v. Size 3 x 1 1/4 x 5in. high. **BRAND NEW (boxed)**, 8/6 each. **DUBILIER NITROGOL** 3 mfd. 350 v. D.C. wkg. at 71°C. Size 1 1/2 x 1 1/2 x 4 1/2 in. high. With fixing clips. **BRAND NEW (boxed)** 5/- each. **T.C.C. or DUBILIER.** 4 mfd. 600 v. wkg. CP 130T or similar. 1 1/2 x 1 1/2 x 4 1/2 in. high. **BRAND NEW (boxed)**, 4/6 each. All post paid.

STANDARD TRANSFORMERS

Vacuum impregnated, interleaved, E.S. screen, universal mounting. Size 4 x 3 1/2 x 2 1/2 in. ALL **BRAND NEW.** 24/- each. Post 2/6.
Type 1. 250-0-250 v. 80 mA. 6.3 v. 3 a. tapped at 1 v. 4 a. 6.3 v. 1 a. tapped at 4 v. and 5 v. 2 a.
Type 2. As above but 350-0-350 v. 80 mA.
Type 3. 30 v. 2 a., tapped at 12, 15, 20 and 24 v. to give 3-4-5-6-8-9-10 v., etc.
Type 5. 0-6-9-15 v. 4 a. Ideal for chargers.



LOW CAPACITANCE BRIDGE MARCONI TF 1342. Range 0.002 pF, to 1,111 pF. Accuracy 0.2%. Three terminal transformer ratio arm bridge allows "in situ" measurements. Internal oscillator frequency 1,000 c/s. 12 x 17 x 8 1/2 in. Weight 15 1/2 lbs. A.C. mains 200 to 250 and 100 to 150 v. 40-100 c/s. With leads and handbook. **ABSOLUTELY BRAND NEW.** £45.

BEAT FREQUENCY OSCILLATORS MARCONI TF 195 M. Covers 10 cps. to 40 Kc/s in two sweeps. 0 to 20 Kc/s and 20 to 40 Kc/s. Output 2 watts into 600 or 2,500 ohms. Panel meter indicates output voltage. A.C. mains operation 100 to 250 volts. First class condition. Fully tested. £20 carr. 30/-.

EVERSHED BRIDGE MEGGER. 500 Volt. Varley and Loop tests. Complete in leather case and in as new condition. £35.

MARCONI "Q" METER. Type 324G. As new condition and in perfect working order. £65. Carr. 50/-.

BC-221 FREQUENCY METERS
As new condition complete with crystal and valves. In perfect working order but **WITHOUT** calibration charts. £9/19/6. Carr. 10/6. Precise (0.001%) dial readings to your requirements at 2/6 per frequency.

MICROMETERS
R.C.A. 0-500 microamps 2 1/2 in. circular flush panel mounting. Dials are engraved 0.15-0.600 volts. As used in the American version of the No. 19 set. 15/- P. & P. 1/6.

AR-88 SPARES
R.C.A. Headphones 12/6
Escutcheons (Windows) 8/6
Knobs. Medium size. Set of 8 10/-
Knobs. Large size 5/6
Block Condenser (3 x 4 mfd.) 12/6
Mains Trans. (L.F.) (postage 6/6) .. 42/6

AR-88D RECEIVERS
A good selection is available for callers at from £30. All are in good condition and are functioning perfectly. Realligned. A few **BRAND NEW** £75.

LABORATORY pH METER

Marconi type TF.1093/1. Range 0-14 pH direct reading. Full temperature compensation. Scale expansion providing discrimination of 0.01 pH. A.C. mains operation. Brand new complete with electrode stand and manual. Full details on request. £35.

CINTEL OSCILLOSCOPE
A 12in. demonstration oscilloscope with all controls at rear. **BRAND NEW** £80.



SANGANIO WESTON VOLTMETERS
S61. Dual range 0-5 and 0-100 v. D.C. FSD 1 mA. 3in. scale. Recent manufacture. Ideal for schools. Complete in super quality canvas carrying case with test prods and leads. **BRAND NEW.** Boxed 32/6. Post 2/6.



PEAK SOUND




WHAT EVERY
CONSTRUCTOR,
EXPERIMENTER
AND DESIGNER
SHOULD HAVE

THE NEW WONDER CIRCUIT SYSTEM

for making your own INSTANT circuits

Think what it means to be able to have just ONE printed circuit to the design you want and you will see immediately just how wonderfully CIR-KIT more than fills that long felt need. CIR-KIT is quick—you simply lay the self-adhesive strip on the board, drill holes for the components and you are ready to solder them in at once. CIR-KIT is clean—there are no chemicals, acids or etching processes involved. CIR-KIT is adaptable—you can amend a circuit again and again quickly and easily. Ideal for experimenters, this. CIR-KIT is economical—the No. 3 Constructor's Kit advertised here contains enough material to make up about 10 circuits and components may be closely mounted if desired. You can also repair damaged conventional printed circuits; you can experiment quickly and cheaply. In fact, CIR-KIT is the most revolutionary advance in circuit techniques since the printed circuit itself was invented and is already being used by many of the most famous houses in electronics.

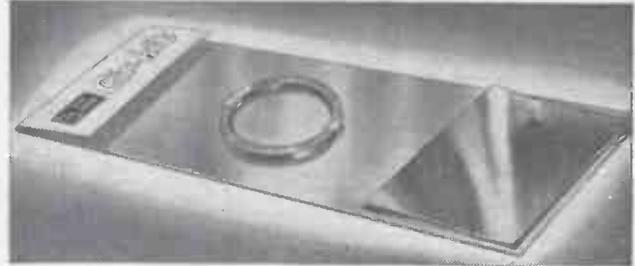


This is Kit No. 3 complete with instructions, board and material in sealed polythene pack.

NO CHEMICALS, ETCHING,
HEAT, SPECIAL TOOLS OR
RESTRICTIONS TO LAYOUT

Enough for about 10 circuits

CIR-KIT KIT No. 3 contains high quality mounting board (Bakelite laminate E.10) size 6in.x12in. with 4in.x 6in. CIR-KIT adhesive copper sheet and 15ft. of 4in. CIR-KIT adhesive copper strip. Land areas and special shapes are cut from the CIR-KIT sheet. The heat-resistant adhesive used will last indefinitely with normal use. With instructions.

15/-

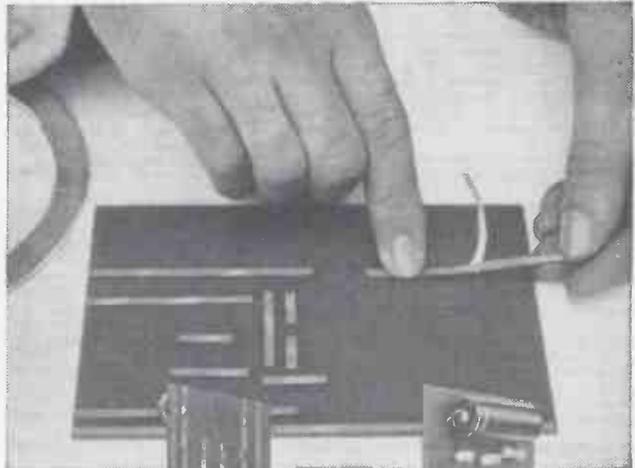


Lay the strip and land areas, drill holes, and your circuit is ready for mounting the components.

The result is 100% professional.

Designed and made in Great Britain by Peak Sound (Harrow) Ltd.

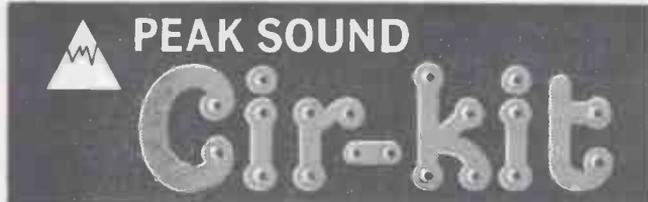Industrial and overseas enquiries to the manufacturers, please.



PEAK SOUND (HARROW) LTD., 10, ASHER DRIVE, MILL RIDE, ASCOT, BERKS. Phone: Winkfield Row 3217 (S.T.D. Code OEH47)

Distributors to the Wholesale & Retail Radio Trade in U.K.:

TECHNICAL SUPPLIERS LTD., 63 Goldhawk Rd., London, W.12 Phone: 01-603-258f; 01-603-4794

To PEAK SOUND, 10, ASHER DRIVE, MILL RIDE, ASCOT, BERKS.

Please send . . . CIR-KIT(s) for which I enclose

NAME

ADDRESS

(BLOCK LETTERS, PLEASE)

W.W.10

Samson's

(ELECTRONICS LTD)

LONDON'S LARGEST SUPPLIERS OF
ELECTRONIC EQUIPMENT
9 & 10 CHAPEL STREET
LONDON, N.W.1
Tel. PAD 7851 AMB 5125



HOURS 9.30-6
OPEN ALL DAY
SAT.
SEND 6s. STAMP
FOR LIST

HEAVY DUTY L.T. TRANSFORMERS
ALWAYS IN STOCK.
ALL PRIMARIES 220-240 VOLTS.
MINAL BLOCK CONNECTIONS.
*DENOTES SHROUDED TYPES.

No.	Sec. Taps.	Amps.	Price	Carr.
1.	25-30-35 v.	40	£12 15 0	15/-
2.	25-30-35 v.	20	£7 19 6	9/6
3.	25-30-35 v.*	10	£5 10 0	6/6
4.	25-30-35 v.*	2	£2 7 6	4/-
5.	10-17-18 v.*	10	£3 10 0	4/6
6.	24 v.	30	£9 5 0	9/6
6a.	24 v.*	30	£10 5 0	9/6
7.	20 v.	30	£7 5 0	8/6
8.	50 v.	15	£7 19 6	8/6
9.	30-40-50 v.*	5	£5 5 0	6/6
10.	24-26-48 v.*	8	£5 17 6	6/6
11.	17-18-20 v.*	20	£5 12 6	6/6
12.	6-12 v.	20	£3 19 6	6/6
12a.	6-12 v.*	20	£4 17 6	6/6
13.	20 v.	20	£5 7 6	8/6
14.	30-32-34-36 v.*	5	£3 5 0	6/-
15.	6-12 v.	10	£2 10 0	5/-
15a.	6-12 v.*	10	£2 17 6	6/-
16.	12 v.	5	£1 15 0	4/6
16a.	12 v.*	5	£2 2 6	4/6
17.	24 v.*	10	£3 15 0	5/6
18.	24 v.*	5	£2 9 6	4/6
19.	48-56-60 v.	1	£1 15 0	4/6
20.	12-24-36-48 v.*	2	£2 7 6	4/6
21.	6.3 v.*	15	£2 2 6	4/6
22.	6.3 v. 5A & 6.3 v. 1A	—	17 6	4/6
23.	12-24 v.*	1	19 6	3/6
24.	9-15 v.	2	19 6	3/6
25.	6-9-15 v.	4	£1 9 6	4/6
26.	12-18 v.	10	£3 2 6	5/6
26a.	12-18 v.*	10	£3 7 6	5/6
27.	12-18 v.	20	£4 9 6	6/6
27a.	12-18 v.*	20	£4 19 6	6/6
28.	48-56-60 v.*	2	£2 15 0	5/-
29.	12 v.	50	£7 5 0	8/6
30.	12-24-36-48 v.	15	£7 19 6	9/6


UNREPEATABLE OFFER!

Motorised UNI-SELECTOR No.2



8 banks, 50 positions. Arranged to give 4 banks 100 positions. Ex-equipment, in perfect condition. These Selector Switches have been carefully removed from a modern PBAX (Installed new in 1960).
£3/19/6 P.P. 4/6

AUTO TRANSFORMERS

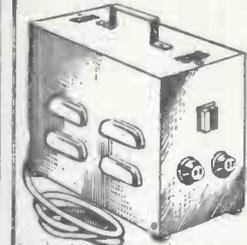

240 - 110 v. 2,000 watts. Completely enclosed in beautifully finished case. Fitted with 2 two-pin American sockets or terminal blocks, neon indicator, on/off switch, and carrying handle. £10/19/6, carr. 10/-. Also available shrouded, fitted with 2-pin American sockets or terminal blocks. Please state which type required.

Wattage	Price	Carr.
1,000	£4 19 6	7/6
500	£3 15 0	6/6
300	£2 9 6	5/-
150	£1 19 6	4/6
80	£1 12 6	4/-

BLOCK CAPACITORS
New and Guaranteed. Send for List, over 2,000 In stock at a fraction of maker's price.

LATEST ARRIVALS

Maker	Mfd.	E.C.V.	Temp.	Price	Carr.
T.C.C.	10	750	60°C	10/6	2/6
T.C.C.	10	350	60°C	6/6	2/-
T.C.C.	8	1,500	60°C	17/6	3/-
T.C.C.	8	750	60°C	8/6	2/6
T.C.C.	8	600	60°C	7/6	2/-
T.C.C.	8	400	71°C	6/6	2/-
T.C.C.	2	2,000	60°C	12/6	2/6
Dubilier	8	600	60°C	7/6	2/-
Dubilier	4	800	71°C	5/6	2/-
Dubilier	1	3,000	100°C	17/6	2/-
Dubilier	0.5	5,000	60°C	17/6	2/-
Dubilier	0.1 + 0.1	6,000	71°C	8/6	2/-

AMERICAN OIL FILLED CAPACITORS				A.C. RATED CAPACITORS			
Mfd.	D.C.	Price	Post.	Mfd.	A.C.	Price	Post.
15	1000	22/6	3/6	60	260	47/6	7/6
12	1000	19/6	3/6	45	250	35/-	5/-
10	1500	19/6	3/6	25	300	25/-	4/-
8	600	8/6	2/6	10	650	17/6	3/6
7	600	6/6	2/6	5.25	650	12/6	3/-
1	600	3/-	1/6	5	400	10/6	3/-

ISOLATION TRANSFORMER
Fully shrouded. Terminal block connections. Pri. tapped 220-240 v. Sec. tapped 220-240 v. 1 amp. 75/-, Carr. 5/-, 2 amps. £4/15/-, Carr. 6/6, 3 amps. £7/19/6, Carr. 7/6, 4 amps. £8/10/-, Carr. 7/6

LOW RESISTANCE SMOOTHING CHOKES
Shrouded type 0.05 H. 0.75Ω 2 amps. 39/6. P.P. 4/-. 0.03 H. 0.4Ω, 4 amps., 49/6. P.P. 4/6. 0.02 H. 0.25Ω, 8 amps. 55/-, P.P. 6/-.

REDCLIFFE HT TRANSFORMERS
Pri. tapped 200-250 v. Sec. 3 separate windings of 130 v. 450 m/a. Tropicalised table top connections 45/-, Carr. 6/-.

HEAVY CURRENT TRANSFORMERS
Output tapped 4-6-11 volts, 200 amps. from 240 volts £10/19/6. Carr. 10/-.

SPECIAL OFFER OF L.T. TRANSFORMERS ALL BY FAMOUS MAKERS. LIMITED NUMBER ONLY

- A. Pri. 240 v. Sec. tapped 53.6, 55.2 v. 6 a. "C" core, tropically finished, 75/-, Carr. 5/-.
- B. Pri. 200-240 v. Sec. tapped 6.2, 6.8, 7.3, 7.9, 9, 9.5, 10, 10.6 volts, 17 amps. and 36 volts 8 amps. £6/10/-, Carr. 7/6.
- C. Pri. 220-240 v. Sec. tapped 75.80 v. 2.4 a. and 6 v. 1 a. "C" core, 75/-, Carr. 5/-.
- D. Pri. 200-240 v. Sec. 17.5 v. 1 a. 3 times, 32/6. P.P. 4/-.
- E. Pri. 200-250 v. Sec. 8 v. 6 a. Suitable for Projector lamps, 19/6. P.P. 3/6.
- F. Pri. 220-240 v. Sec. tapped 32.38.44 v. 7 a., 70/-, Carr. 7/6.
- G. Pri. 230-240 v. Sec. 4.5 v. 30 a., 8 v. 1 a., 4.5 v. 1 a., £4/17/6. Carr. 7/6.
- H. Pri. 230 v. Sec. tapped 65.130 v. 85 mA. and 6.3 v. 5 a., 6.3 v. 1 a., 17/6. P.P. 3/6.

T.E.C.H.D. TRANSFORMER. Pri. 230-240 v. Sec. 76 v. 43.5 a. 2 only, £25, ex warehouse.

SMITH'S 4 MINUTE TIMERS
Switch contacts 15 amps. 250 volts A.C., complete with chrome bezel and control knob. Min. operation time 30 seconds, max. 4 minutes, Brand new, 17/6, P.P. 2/6.

SELENIUM F.W. HIGH CURRENT BRIDGE RECTIFIERS. Supplied brand new and guaranteed. Not to be confused with Government Surplus. All materials used are the latest design and highest grade.

PLATE SIZE 7 1/2in. SQUARE

No.	Volts	Amps.	Price	Carr.
No. 1.	36 v. D.C.	36 amps.	£11 15 0	7/6
No. 2.	36 v. D.C.	18 amps.	£5 17 6	7/6
No. 3.	24 v. D.C.	54 amps.	£11 15 0	7/6
No. 4.	24 v. D.C.	36 amps.	£5 19 6	7/6
No. 5.	24 v. D.C.	18 amps.	£3 19 6	7/6
No. 6.	12 v. D.C.	54 amps.	£5 17 6	7/6
No. 7.	12 v. D.C.	36 amps.	£3 19 6	7/6
No. 8.	12 v. D.C.	18 amps.	£1 19 6	3/6
No. 9.	12 v. D.C.	12 amps.	£1 12 6	3/6


PLATE SIZE 4 1/2in. SQUARE

No. 10.	36 v. D.C.	8 amps.	£2 19 6	3/6
No. 11.	24 v. D.C.	8 amps.	£1 19 6	3/6
No. 12.	12 v. D.C.	8 amps.	19 6	2/6

EVERSHED & VIGNOLES LTD.
A.C. Watt-Meters 0-500. 6 1/2in. dia. Nominal voltage 250 v. Nominal current 2 amps. Flush mounting. Mirror scale. £5/17/6. Carr. 5/-.

SPECIAL OFFER OF PARMEKO H.T. TRANSFORMERS. Primaries tapped 230 and 115 v. No. 1 950-0-950 v. 30 mA. and 575-0-575 v. 50 mA. r.m.s. Completely sealed. Chassis mounting. Brand new, 49/6. Carr. 6/-. No. 2, 960 v. C.T. 500 mA. r.m.s. Terminal block connections. Base mounting. Brand new, 57/6. Carr. 7/6. No. 3, 920 v. C.T. 100 mA. r.m.s. 6.3 v. 8 amps. Four times. 5 v. 6 amps., 5 v. 4 amps. Terminal block connections. Base mounting, 75/-, Carr. 7/6. No. 4, 500-0-500 v. 165 mA. Completely sealed. Base mounting, 35/-, Carr. 5/-. No. 5, 30 v. 2 amps., 6.3 v. 6.5 amps., 6.3 v. 1.1 amps., 6.3 v. 0.3 amps., 32/6. Carr. 4/-.

L.T. SUPPLY UNIT TYPE S.E.1

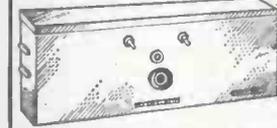

A.C. input 200-240 v. D.C. Output tapped to give 12 or 24 volts 8 amps. continuous rating. Fitted with panel fuse. Mains on/off switch and D.C. output socket. Built in strong metal base. Size 15 x 6 x 6in. An ideal general purpose L.T. supply unit for operating relays. Contactors, battery charging, etc. £9/19/6, carr. 7/6.

L.T. SUPPLY UNIT TYPE S.E.2


A.C. input 200-240 v. D.C. output 50 volts 5 amps. Built in metal case, size 15 x 6 x 6in. Fitted with on/off switch, panel fuse and output socket. £9/19/6. Carr. 7/6.

UNREPEATABLE OFFER. WESTINGHOUSE L.T. SUPPLY UNIT TYPE XXIII
A.C. input tapped 200-250 v. D.C. output 25.5 volts 8 amps., and a Separate tapped A.C. output of 6.2, 6.8, 7.3, 7.9, 8.5, 9, 9.5, 10, 10.6 volts at 17 amps. Both outputs for temperate operating conditions. Completely enclosed in metal wall mounting case, size 15 1/2 x 9 x 6 1/2ins. Supplied Brand New and Guaranteed. AT A FRACTION OF MAKER'S PRICE £8/10/-, Carr. 15/-.

NEOPRENE COVERED HOSE
Nitrate lined 1/2in. bore x 2 braid unused. Perfect condition, fraction of maker price, 12 yard coils, 17/6, P.P. 5/-.

WODEN DOUBLE STEP-DOWN TRANSFORMERS. Pri. 240 v. Sec. 55-0-55 v. 200 watts, Completely enclosed, 75/-, Carr. 7/6.

TWIN TURBO BLOWERS

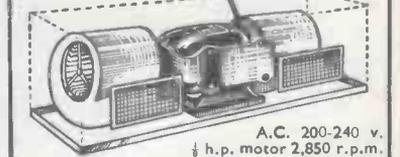

A.C. 200-240 v. 1/2 h.p. motor 2,850 r.p.m. Manufactured by famous makers for computer equipment, in perfect condition. Completely enclosed. Size 24 x 8 x 8in. Ideal for ventilating and cooling. £6-19-6 Carr. 10/-.

R.S.C.

HI-FI CENTRES LTD.
Terms: C.V.O. or C.O.D. No C.O.D. under £1. Postage 3/6 extra under £2, 5/6 extra under £5 Trade supplied. S.A.E. with all enquiries please. Personal shoppers welcomed at our HI-FI CENTRES as below OPEN ALL DAY SATURDAY.


- BRADFORD** 10 North Parade, Tel.: 25349. (Half-day Wed.)
- BRISTOL** 14 Lower Castle Street, (Half-day Wed.) Tel.: 22904
- BIRMINGHAM** 30/31 Gt. Western Arcade, Opp. Snow Hill station. Tel.: CENTRAL 1279. (No half-day). Larger premises now open.
- DERBY** 26 Osmoston Rd. The Spot- (Half-day Wed.). Tel.: 41361-
- DARLINGTON** 13 Post House Wynd (Half-day Wed.).
- EDINBURGH** 133 Leith Street. (Half-day Wed.).
- GLASGOW** 326 Argyle Street. Tel.: CITY 4158 (No half-day).
- HULL** 51 Savile Street (Half-day Thursday). Tel.: 20505.
- LEICESTER** 32 High Street (Half-day Thurs.). Tel.: 56420
- LEEDS** 5-7 County (Mecca) Arcade (No half-day). Tel.: 28252
- LIVERPOOL** 73 Dale St. (No half-day) Tel.: CENTRAL 3573
- LONDON** 238 Edgware Road, W.2 (Half-day Thursday). Tel. PADdington 1629 96 High Holborn, W.C.1.
- MANCHESTER** 60A-60B Oldham St., (No half-day). Tel.: CENTRAL 2778.
- MIDDLESBROUGH** 106 Newport Rd. (Half-day Wed.).
- NEWCASTLE** 39 Blackett St., (Half-day Wed.). Tel. 21469
- SHEFFIELD** 13 Exchange Street, Castle Market Bldgs. (Half-day Thursday) Tel.: 20716.
- JASON VHF/FM TUNERS FMTI** £6.19.11
Complete kit with valves. Carr. 5/-

MAIL ORDERS TO:
102 Menconer Lane,
Bramley, Leeds, 13.

R.S.C. STEREO/20 HIGH FIDELITY AMPLIFIER

Providing 10/14 WATTS ULTRA LINEAR PUSH-PULL OUTPUT ON EACH CHANNEL

Features include:
 * Four-position tone and compensating Input Selector switch.
 * Stereo/Mono switch so that peak monaural output of 28 watts can be obtained.
 * Separate "Bass" "Mid" and "Treble" and "Lift" and "cut" controls.
 * Neon panel indicator.
 * Handsome Perspex Frontplate.
 * Complete set of parts with point-to-point wiring diagrams and instructions Carr. 14 Gns. or Factory assembled, tested and supplied with our usual 12/8 months guarantee for 15 gns. or DEPOSIT £3 and 9 monthly payments 43/6 (Total £22/4/6). SUITABLE FOR "MIKE" GRAM., RADIO OR TAPE. FOR HOME OR STUDIO. Employing valves ECC83, ECC85, ECL86, ECL86, ECL86, ECL86, ECL86. Output transformers are high quality sectionally wound to required specification. Output matchings, for 8 and 15 ohms speakers on each channel. FREQUENCY RESPONSE ± 2 dB. 30-20,000 c.p.s. HUM LEVEL -65dB. SENSITIVITY: 15 millivolts. HARMONIC DISTORTION (each channel) 0.2 per cent. For 200/250 v. A.C. mains.

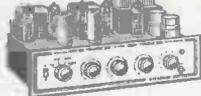

Send S.A.E. for illustrated leaflet. Write diagrams and instructions

R.S.C. STEREO/10 HIGH QUALITY AMPLIFIER

Valves EZ81, EC93, EC83, EL84, EL84. Separate bass and treble controls giving "cut" and "boost." Sensitivity 50 mV. 5 watts high quality output on each channel. Can be used as straight 10 watt amplifier. Controls: Stereo/Mono switch, ganged volume, ganged treble, ganged bass and balance. Output for 3 ohms speaker. Point-to-point wiring diagrams and instructions. Or supplied assembled and tested 11 gns. Deposit £8.15.0 36/- and 9 monthly payments of 25/5 (Total £13/4/9). S.A.E. for leaflet. Carr. 11/6.



AUDIOTRINE HI-FI TAPE RECORDER KIT

Only 4 pairs of soldered joints plus mains

Build a high quality recorder in the £50 class for only 26 1/2 Gns. Carr. Can be assembled in one 19 1/2 hour. S.A.E. for leaflet. 4 track 3 rms. OR DEPOSIT 4 gns. and 9 monthly payments of 59/6 (Total 291 gns.). Cash price if settled in 3 months. INCORPORATING THE LATEST MAGNAVOX TAPE DECK. THE AUDIOTRINE HIGH QUALITY TAPE AMPLIFIER. A HIGH FLUX 7 x 4in. LOUD-SPEAKER. Reel of Best Quality TAPE, Spare Tape Spool, a Portable Cabinet size approx. 17 1/2 x 14 1/2 x 8 1/2 in. finished Grey leathercloth with Silver trim and chrome fittings. Connection diagram for wiring amplifier to deck provided. FEATURES INCLUDE * 3-SPEEDS FOR EACH SPEED * OUTPUT 4 WATTS * MAGIC EYE RECORDING LEVEL INDICATOR * HEAVY DUTY MOTOR * TAPE MEASURING & CALIBRATING DEVICE * TAKES FULL 7in. DIAMETER REELS OF TAPE * NEGLIGIBLE HUM * ENTIRELY EFFECTIVE AUTOMATIC ERASURE.



ALL LEADING MAKES OF HI-FI EQUIPMENT STOCKED—CASH OR CONVENIENT TERMS

HIGH FIDELITY LOUDSPEAKER ENCLOSURES.

All types are of pleasing modern "slimline" design acoustically lined and ported, and in alternative finishes of light teak or medium walnut.

SE8. Designed for optimum performance with any Hi-Fi 8in. speaker. Size 22 x 15 x 7in. Carr. 7/6 **£5/15/-**

SE10. For 10in. High-Fidelity Speaker with provision for tweeter. Size 24 x 15 x 8in. Carr. 10/- **£6/19/9**

SE12. For outstanding performance with any 12in. Hi-Fi speaker. A tweeter cut-out is provided. Size 24 x 20 x 8in. Dept. 27/- & 9 mthly. pyts. 18/2 (Total £9/10/6). Carr. 10/- **8 Gns.**

FHE8. Folded Horn type. Size 27 x 16 x 10in. Designed for high flux 8in. speaker with which exceptional quality can be obtained. Terms: Deposit 21/- Carr. 9 Gns. and 9 mthly pyts. of 21/- (Total 10 gns.) 10/- **9 Gns.**



HIGH FIDELITY LOUDSPEAKER

MINI-8 8 watt rating. 3 or 15 ohm. Frequency response 50-13,000 c.p.s. Specially designed high flux 5in. speaker with low fundamental resonance. Teak veneered cabinet, 9 1/2 x 6 1/2 x 7 1/2 in. Carr. 7/6 **£6/19/11**

"PETITE" Size only 10 1/2 x 6 1/2 x 7 1/2 in. Rating 10 watts R.M.S. Frequency range 45-20,000 c.p.s. Cabinet beautifully finished in Walnut or light Teak. Fitted specially designed heavy cast 5in. speaker with large pole pieces, extra long voice coil and rubber cone surround. Impedance 3 or 15 ohms. Deposit 36/- and 9 mthly. pyts. of 25/- (Total £13/1/-). Carr. 7/6. **11 Gns.**



Following types have handsome "slim line" cabinets finished in Satin Teak or Walnut, acoustically lined and ported.

The GLOUCESTER. 24 x 20 x 8in. 12in. high flux 12,000 line speaker. Crossover unit, and Tweeter. Rating 10 watts smooth response. 40-20,000 c.p.s. Impedance 15 ohms. Or Deposit 36/- and 9 monthly pyts. **11 Gns.** of 25/- (Total £13/1/-). Carr. 15/-.



The DORCHESTER. Size 24 x 15 x 8in. Fitted Audiotrine HF100D Speaker. Rating 15 watts. Frequency response 30-20,000 c.p.s. Carr. 15/- Deposit 39/6 and 9 mthly. pyts. 27/3. **12 Gns.** (Total £14/4/9).

The BRONTE. Size 22 x 15 x 7 1/2 in. Fitted Wharfedale Super 8 RSDD Speaker, with Roll Surround and dual cone. Rating 6 watts. Impedance 15 ohms. Or Deposit 39/6 and 9 mthly. payments of 27/3 (Total £14/4/9). Carr. 15/- **12 Gns.**


R.S.C. SUPER 15 HI-FI AMPLIFIER R.S.C. SUPER 30 STEREO AMPLIFIER

FULLY TRANSISTORISED

- * 200-250 v. A.C. Mains Operation
- * OUTPUT R.M.S. CONTINUOUS 10 WATTS into 15 ohms. 15 WATTS into 3 ohms.
- * Max. Instantaneous Peak Power Output 28 watts.
- * PRINTED CIRCUIT CONSTRUCTION
- * LATEST MULLARD TRANSISTORS AD149 (2), OC127Z, OC81Z (2), OC44 (3), AC107 (Total of 9).
- * 5-POSITION INPUT SELECTOR SWITCH EQUALIZATION to Standard R.I.A.A. and C.C.I.R. Characteristics for Gram and Tape Heads.
- * FULL TAPE MONITORING FACILITIES
- * SENSITIVITIES: Magnetic P.U. 4 m.v. Crystal or Ceramic P.U. 400 mv. Microphone 4.5 mv. Tape Head 2.5 mv. Radio/Aux. or Ceramic P.U. 110 mv.
- * NEGATIVE FEEDBACK 52 dB.
- * FREQUENCY RESPONSE: 20-20,000 c.p.s. ± 2 dB
- * TREBLE Control +15 dB. to -14 dB. at 10 kc/s.
- * BASS Control +12 dB. to -15 dB. at 50 c/s.
- * HARMONIC DISTORTION at 10 Watts R.M.S. 1,000 c.p.s. 0.3%. * HUM LEVEL: -75 dB.

TECHNICAL SPECIFICATIONS COMPARE MORE THAN FAVOURABLY WITH SIMILAR AMPLIFIERS OFFERED AT TWICE THE COST

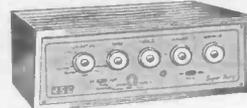Complete Kit of parts with full constructional details and point-to-point wiring diagrams. Only **10 1/2 Gns.** Carr. 10/- Unit factory built 14 1/2 gns. or fitted in beautiful cabinet or teak veneered cabinet as illustrated as illustrated 18 1/2 gns. Carr. 12/6. Deposit £2/0/0 and 9 mthly. pyts 40/6 (Total £21/13/6).



All parts, point-to-point wiring diagrams and detailed instructions. **18 Gns.** Carr. 12/6. Unit factory built 25 gns. or Deposit 81/- and 9 monthly payments of 55/9 (Total £29/2/9). Fitted cabinet as above Carr. 25/- 29 gns. Or Dep. 24/12 and 9 mthly. pyts. 64/10. (Total £33/15/6).

A DUAL CHANNEL VERSION OF THE SUPER 15

- * Matched Components.
- * Close Tolerance Ganged Pots.
- * CROSS-TALK -52 dB. at 1,000 c.p.s.
- * CONTROLS: 5 Position Input Selector, Bass Control, Treble Control, Volume Control, Balance Control, Stereo/Mono Switch Tape Monitor Switch, Mains Switch.
- * INPUT SOCKETS (Matched Pairs): (1) Magnetic P.U. (2) Ceramic or Crystal P.U. (3) Radio/Aux. (4) Tape Head/Microphone.
- * Operation of the Input Selector Switch assures appropriate equalization.
- * Rigid 18 s.w.g. Chassis. Size 12 x 8 x 8in.
- * Attractive Rigid Perspex Facia Plate and Spun Silver Matching Knobs.
- * NEON PANEL INDICATOR.

Above facilities, etc., except for Ganging and Balance Control apply also to Super 15. ALL HIGH GRADE COMPONENTS, ETC. THESE UNITS ARE EMINENTLY SUITABLE FOR USE WITH ANY MAKE OF PICK-UP OR MICROPHONE (Crystal, Ceramic, Magnetic, Moving Coil, Ribbon), SUPERB SOUND OUTPUT CAN BE OBTAINED BY USING WITH FIRST RATE ANCILLARY EQUIPMENT.

R.S.C. TYPE TFM1 TRANSISTORISED VHF/FM RADIO TUNER



12 1/2 GNS.

Total cost of parts with detailed wiring diagrams and instructions. Carr. 10/-. Or factory built, 15 1/2 gns. Or in Teak finished cabinet as illustrated. 19 1/2 gns. Terms: Deposit 25 and 9 mthly. pyts. 39/-. Total £22/11/-.

- * 200-250 v. A.C. Mains operation
- * High Sensitivity
- * Drift-free reception
- * Sharp A.M. Rejection
- * Output ample for any amplifier (approx. 500 mV)
- * Simple alignment instructions
- * Output available for feeding tuning meter
- * Output for feeding Stereo Multi-plexer Tuner head using Silicon Planar Transistors
- * Designed for standard 80 ohms co-axial input

AUDIOTRINE HI-FI SPEAKER SYSTEMS

Provides a smooth frequency response from 40-20,000 c.p.s. consisting of 12in. 12,000 line 15 ohm speaker. Crossover Unit and Tweeter. Highly recommended for use with any High-Fidelity Amplifier. 10 Watt Unit, 5 gns. Carr. 5/6 or deposit 15/- and 9 monthly payments of 11/6 (Total £5/18/6). 20 Watt Unit £8/19/9. Carr. 7/6.



AUDIOTRINE HI-FI LOUDSPEAKERS

Heavy cast construction. Latest high efficiency ceramic magnets. Dual Cone for extended frequency range. Plastic treated surround giving low resonant frequency. Response 30-20,000 c.p.s. Impedance 3 or 15 ohms. Carr. 5/6.

HF811D 8in. 10 WATT 4 gns.
 HF100D 10in. 15 WATT £5/15/-
 HF121D 12in. 20 WATT £6/15/-
 HF127D 12in. 30 WATT 9 gns.



To visually match our Super 15 and 30 amplifiers and of the same high standard of performance and reliability. The pre-wired tuning head facilitates speed and simplicity of construction. Printed circuitry, only first grade transistors and components used. Our latest product giving you the best at half the cost of comparable units.



AUDIOTRINE PLINTHS for Record Playing units. Teak finish cut for Garrard 1000, 2000, 3000, AT6 Mk II, AT60, SP25 or Goldring GL68. Or with clear Perspex cover as illustrated, £5/19/11 complete.

HI-FI SINGLE RECORD PLAYING UNITS Consisting of the popular Garrard SP25 turntable and Goldring CS90 High compliance Cartridge. Fitted on Plinth as above and complete with Clear Perspex cover. Ready to 'plug in' to any Hi-fi amplifier. (Normal Price £24/15/-) Carr. 15/- **19 1/2 Gns.**

TERMS: Deposit 3 Gns. and 9 monthly payments 43/7 (Total £22/15/3).

NEWCASTLE - LONDON
New branches open. See opposite page

LOUDSPEAKERS IN CABINETS

12in. 20 WATT Walnut Veneered Cabinet. Size 15 x 15 x 8in. approx. High quality 12in. 10 watt 15,000 cfs. line speaker, 3 ohms or 15 ohms £4/19/11. Carr. 7/6. Or Deposit 15/- and 9 monthly payments 11/2. (Total £5/15/6).
12in. 20 WATT High Quality High Flux Speaker. 15 ohms in Cabinet, finished as above. Size 18 x 18 x 8in. £7/19/11. Carr. 10/6. (Or Deposit 24/6 and 9 monthly payments of 17/3. (Total £28/19/3).
12in. 30 WATT 17,000 lines in walnut finished cabinet 10 Gns. Carr. 12/6. Terms Deposit 32/- and 9 monthly payments of 22/4. (Total £11/13/-).
COLUMN TYPE 40 WATT, with four 12in. high flux speakers. 19 1/2 Gns. Carr. 15/-. Or deposit 30 Gns. and 9 monthly payments 43/7 (Total £22/15/3).

12in. 30 watt HEAVY DUTY
LOUDSPEAKERS 15 ohm. **7 GNS.**
Terms available Carr. 10/-

SPECIAL PURCHASE of 15 in. 30 watt
L/SPEAKERS 15 ohms. £9.19.11
Brand New Carr. 10/-

15 in. 40 watt LOUDSPEAKERS
EXTRA HEAVY DUTY 15 ohms. **11 GNS.**
Normally approx. £19. Limited number

FANE 122/10 20 WATT HEAVY DUTY
LOUDSPEAKERS 12in. 15 ohm. **5 GNS.**
With exceptionally robust 2in. diameter voice coil assembly. Model 122/10A with Dual Cone 6 Gns.

R.S.C. 4 watt GRAM AMPLIFIER KIT
Complete set of parts to build a good quality compact unit suitable for use with any record playing unit. Mains isolated chassis. Separate Bass and Treble control. Output for 2 or 3 ohms speaker. For 200-250 v. A.C. **59/11**

POWER PACK KITS Fully smoothed output 250 v. 60 mA. H.T. and L.T. 6.3 v. 1.5 amps. Consists of chassis, Double wound Mains Trans. 200-250 v., Rectifier, Choke, Electrolytics and circuit. Or with case in lieu of **22/11** chassis 26 11.

R.S.C. TRANSFORMERS

Fully Guaranteed. Interleaved and Impregnated.
MAINS TRANSFORMERS, Primaries 200-250 v. 50 cfs.
MIDGET CLAMPED TYPE 2 1/2 x 2 1/2 in.
250 v. 60 mA. 6.3 v. 2 a. **14/11**
200-0-250 v. 60 mA. 6.3 v. 2 a. **15/11**

FULLY SHROUDED. UPRIGHT MOUNTING
250-0-250 v. 60 mA. 6.3 v. 2 a. 0-5-6.3 v. 2 a. 24-3-3in. **19/9**
200-0-250 v. 100 mA. 6.3 v. 4 a. 0-5-6.3 v. 3 a. **33/9**
300-0-300 v. 100 mA. 6.3 v. 4 a. 0-5-6.3 v. 3 a. **33/9**
300-0-300 v. 130 mA. 6.3 v. 4 a. c.t. 6.3 v. 1 a. For Mullard 610 Amplifier **41/9**
350-0-350 v. 100 mA. 6.3 v. 4 a. 0-5-6.3 v. 3 a. **33/9**
350-0-350 v. 150 mA. 6.3 v. 4 a. 0-5-6.3 v. 3 a. **42/9**
425-0-425 v. 200 mA. 6.3 v. 4 a. c.t. 5 v. 3 a. **67/9**
425-0-425 v. 200 mA. 6.3 v. 4 a. 6.3 v. 4 a. 5 v. 3 a. **69/9**
450-0-450 v. 250 mA. 6.3 v. 4 a. c.t. 5 v. 3 a. **79/9**

TOP SHROUDED DROP-THROUGH TYPE
250-0-250 v. 70 mA. 6.3 v. 2 a. 0-5-6.3 v. 2 a. **19/9**
250-0-250 v. 100 mA. 6.3 v. 3.5 a. **21/9**
200-0-250 v. 100 mA. 6.3 v. 2 a. 0-5-6.3 v. 1 a. **22/9**
350-0-350 v. 80 mA. 6.3 v. 2 a. 0-5-6.3 v. 2 a. **23/9**
250-0-250 v. 100 mA. 6.3 v. 4 a. 0-5-6.3 v. 3 a. **32/9**
300-0-300 v. 100 mA. 6.3 v. 4 a. 0-5-6.3 v. 3 a. **32/9**
300-0-300 v. 130 mA. 6.3 v. 4 a. 0-5-6.3 v. 1 a. suitable for Mullard 610 Amplifier **39/9**
350-0-350 v. 100 mA. 6.3 v. 4 a. 0-5-6.3 v. 3 a. **32/9**
350-0-350 v. 150 mA. 6.3 v. 4 a. 0-5-6.3 v. 3 a. **39/11**

FILAMENT or TRANSISTOR POWER PACK TRANSFORMERS
12 v. 1 a. 8/9; 6.3 v. 1.5 a. 6/9; 6.3 v. 2 a. 7/9; 6.3 v. 3 a. 9/9; 6.3 v. 6 a. 19/9; 12 v. 3 a. or 24 v. 1.5 a. 19/9; 0-25-36-42 v. 2 a. 27/9.

AUTO (Step Up/Step Down) TRANSFORMERS
0-110/120 v. 200-230-250 v. 50-80 watts. **14/9**
150 watts 28/11; 200 watts 48/9; 500 watts. **99/9**

CHARGER TRANSFORMERS
0-9-15 v. 1 a. **13/9** 0-9-15 v. 6 a. **25/11**
0-9-15 v. 5 a. **15/9** 0-9-15 v. 3 a. **18/9**
0-9-15 v. 2 1/2 a. **16/9** 0-9-15 v. 8 a. **31/9**

OUTPUT TRANSFORMERS
Standard Pentode 5,000 Ω to 3 Ω or 7,000 Ω to 3 Ω **7/9**
Push pull 8 watts EL84 to 3 Ω or 15 Ω **11/9**
Push pull 10-12 watts 6V6 to 3 Ω or 15 Ω **19/9**
Push pull 10-12 watts to match 6V6 to 3, 5, 8 or 15 Ω **21/9**
Push pull EL84 to 3 or 15 Ω 10-12 watts **19/9**
Push pull Ultra Linear for Mullard 610, etc. **35/9**
Push pull 15-18 watts, sectionally wound 6L6, KT66, etc. for 3 or 15 Ω **29/9**
Push pull 20 watt high-quality, sectionally wound EL34, 6L6, KT66, etc. to 3 or 15 Ω fully shrouded **55/9**

SMOOTHING CHOKES
250 mA. 5 H., 100 Ω 12/9 80 mA., 10 H., 350 Ω **7/9**
150 mA. 7-10H., 250 Ω 12/9 80 mA. 10 H. 400 Ω **4/11**
100 mA., 10 H., 200 Ω 9/11 1 amp. 0.5 Ω L.T. type. **7/9**

R.S.C. A10 30 watt AMPLIFIER HIGH FIDELITY

ULTRA LINEAR PUSH-PULL OUTPUT
SIX VALVES EF86, EF86, ECC83, 807, 807, QZ34. Tone Control Pre-amp. stages are incorporated. Sensitivity is extremely high. Only 45 millivolts minimum input is required for full output. THIS ENSURES THE SUITABILITY OF ANY TYPE OF MICROPHONE OR PICK-UP. Separate Bass and Treble controls give both "lift" and "cut." Two inputs with separate vol. controls permit simultaneous use of "mike." PICK-UP, etc., etc. A **OUTPUT SOCKET WITH PLUG IS INCLUDED FOR SUPPLY OF 300 v. 20 mA. and 6.3 v. 1.5 A. FOR A RADIO TUNER.** Price in kit form with easy to follow wiring diagram. **ONLY 12 Gns.** Or factory built using latest EL34 output valves with 12 Carr. months' guarantee. **15 GNS. TERMS ON ASSEMBLED 12/6.** **UNITS. DEPOSIT £2/5/- and 9 monthly payments of 33/7 (Total £17/10/3).** Protective cover with handles available for £21/-.
Type 807 output valves are used with High Quality Sectionally Wound output transformer specially designed for Ultra Linear operation. Negative feedback of 20 dB. in main loop. **CERTIFIED PERFORMANCE FIGURES ARE EQUAL TO MOST EXPENSIVE UNITS AVAILABLE.** Frequency response ± 3 dB. 30-20,000 cfs. Tone Controls. 12 dB. at 50 cfs. +12 dB. to -6 dB. at 12,000 cfs. hum and noise 70 dB. down. Good quality reliable components used. Chassis finish gold hammer. Overall size 12 x 9 x 9in. approx. Power consumption 150 watts. For A.C. mains 200-250 v. 50 cfs. Output for 3 and 15 ohm speakers. **EQUALLY SUITABLE FOR THE CONNOISSEUR OR FOR LARGE HALLS, CLUBS, OR OUTSIDE FUNCTIONS. IDEAL FOR USE WITH MUSICAL INSTRUMENTS, SUCH AS STRING BASS, ELECTRIC ORGAN, GUITAR, etc. FOR 'POP' GROUPS, GARRISON THEATRES, etc., etc. We can supply Microphone, Speakers, etc., etc. at cash prices or on terms with amplifiers. EXPORT ENQUIRIES INVITED.**



R.S.C. A11 12-14 WATT AMPLIFIER HIGH FIDELITY ULTRA LINEAR OUTPUT

"BUILT-IN" TONE CONTROL PRE-AMP STAGES. Two input sockets with associated controls allow mixing of "mike" and gram, etc. High sensitivity. Includes 5 valves ECC83, ECC83, EL84, EL84, EZ81. High quality sectionally wound output transformers specially designed for Ultra Linear operation. Reliable components. **INDIVIDUAL CONTROLS FOR BASS AND TREBLE "Lift" and "Cut."** Frequency response ± 3 dB. 30-20,000 cfs. Six negative feedback loops. Hum level 60 dB. down. **ONLY 23 millivolts INPUT required for FULL OUTPUT.** For use with all types of pick-ups and mikes. Comparable with the very best designs. For gram, radio or tape. For **MUSICAL INSTRUMENTS** such as **STRING BASS, GUITARS, etc.** **OUTPUT SOCKET with plug provides 300 v. 30 mA. and 5.3 v. 1.5 A. For supply of a RADIO TUNER.** Size approx. 12 x 9 x 7in. For A.C. mains 200-250 v. 50 cfs. Output for 3 and 15 ohm speakers. Kit is complete to last unit. Chassis is fully punched. Full instructions and point-to-point wiring diagrams supplied (or factory built £11/15/-). **TERMS: DEPOSIT 36/6 and £8.15.0 Carr. 9 monthly payments of 25/9 (Total £13/8/3).** Perforated metal 11 1/8 covers with 2 carrying handles can be supplied for £1/-.



COMMUNICATION RECEIVER RX 60 DE-LUXE

4 Band 535 kc/s. to 30 Mc/s. Slide Rule Tuning Dial with Bandspread and "S" Meter. A.V.C. Noise Limiter, B.F.O. Phone Jack. Built-in speaker. Stand-by Switch with terminal for transmitter. Built-in Antenna for long range reception. High Sensitivity. For 200-250 v. A.C. mains. Handsome chrome decorated cabinet. 13 x 5 1/2 x 8 1/2 in. Or Deposit **25 19 Gns.** and 9 monthly payments 37/8.



(Total £21/19/-). Carr. 11/-.

WAVEMETERS TYPE 'D' No. 1. Brand New, 59/11

Ex. Govt. Available Mail Order only.

4/5 WATT AS HIGH GAIN AMPLIFIER

A highly sensitive 4-valve quality amplifier for the home, small club, etc. Suitable for all crystal or ceramic P.U. heads and practically all "mikes." Separate Bass and Treble controls giving "lift" and "cut." Hum level 71 dB. down. Negative feedback 15 dB. Reserve power supply 300 v. H.T. and 6.3 v. L.T. for Radio Tuner or Tape Deck Pre-amp. For A.C. mains 200-250 v. Speaker output 3 ohms. Kit complete in every detail. **£4/17/9** Fully punched enamelled chassis. point-to-point wiring diagrams and instructions. Assembled ready for use. **£8/6/-**



R. S. C. BATTERY ELIMINATORS

Type BM1. Size 5 1/4 x 2 1/2 in. approx. Completely replaces batteries supplying 1.5 v. and 90 v. where A.C. mains 200-250 v. 50 cfs. is available. For all battery portable receivers requiring 1.5 v. and 90 v. **Complete kit with diagrams, 44/9 Or 59/11 ready for use.**



TAPE PRE-AMPLIFIER Linear LP1 Switched Equalisation.

Positions for Recording at 1 1/2in, 3 1/2in., 7 1/2in. per sec. and Playback. EM84 Recording Level Indicator. Designed primarily as the link between a Magnavox Tape Deck and Hi-Fi amplifier, suitable almost any Tape Deck. Cash or Terms. **10 1/2 Gns.** S.A.E. for leaflet.

TRANSISTOR SALE Mullard OC71 2/11, OC72 2/11, OC81 2/11, OC45 3/11, OC44 3/11, OC75 7/9, OC171 8/9, AF117 6/9, ELLISMAN XA101 3/9, XA112 3/9, XC101A 3/9. Postage 6d. for up to 3 transistors.

HEAVY DUTY SELENIUM RECTIFIERS

12v. 15 amps. F.W. (Bridged). **Only 19/9**

SELENIUM RECTIFIERS F.W. (Bridged)

All 6/12 v. D.C. output. Max. A.C. input 18v. 1 a. 3/11; 2 a. 6/11; 3 a. 9/9; 4 a. 12/9; 6 a. 15/9.

HEAVY DUTY BATTERY CHARGER KITS

Consisting of Mains Trans. 200-250 v., Rectifier, Ammeter, Variable Charge Rate Selector, Panels, Plugs, Fuses and holders. Fully punched, stove enamelled case and circuit. **6/12 v. 4 a. 49/11 6/12 v. 6 a. 69/11**

INTEREST CHARGES REFUNDED on Credit Sale purchases settled in 3 months.



Switch on to Pitman books

Modern Electronic Components
G. W. A. Dummer **63s net**

In this book the author has sought to present the first comprehensive survey of the more common components, together with information on their behaviour under the arduous environmental conditions to which they are often subjected. As an aid to the choice of the most suitable component for a particular purpose, this book should be of fundamental value to engineers concerned with the design, development, production and use of electronic equipment.

The Silicon Gate-Controlled Switch
edited by G. J. Pridham **12s 6d net**

Aimed at H.N.C. and higher level electronics students, this short monograph was originally presented as a symposium by experts from four major electronics companies at Enfield College of Technology. The device is a transistor-type mechanism, recently developed, which has found wide applications in computer and other electronic circuitry.

Connectors, Relays and Switches
G. W. A. Dummer and N. E. Hyde **50s net**


This is the latest volume in the series **Radio and Electronic Components**, by Mr. Dummer. The series has been designed to meet the needs of the rapidly expanding electronics industry for information about specific components. *Connectors, Relays and Switches* is the first book in the world covering electronic connections—a subject of extreme importance, because of improvements in reliability of conventional components and integrated circuits, necessitating similar improvements in connection methods.

available from all booksellers, or by post (add 2s 9d postage and packing per book) from:

NEW ERA BOOKS LTD
14 NEWTON STREET
LONDON W.C.2.

HENRY'S RADIO LTD.
 303 EDGWARE RD., LONDON, W.2.
 PADDINGTON 1008/9 (STD:01-723-1008)
 Open Mon. to Sat. 9-6. Thurs. 1 p.m.
 S.A.E. 8 page list of transistor, valves etc.

CALL IN AND SEE US

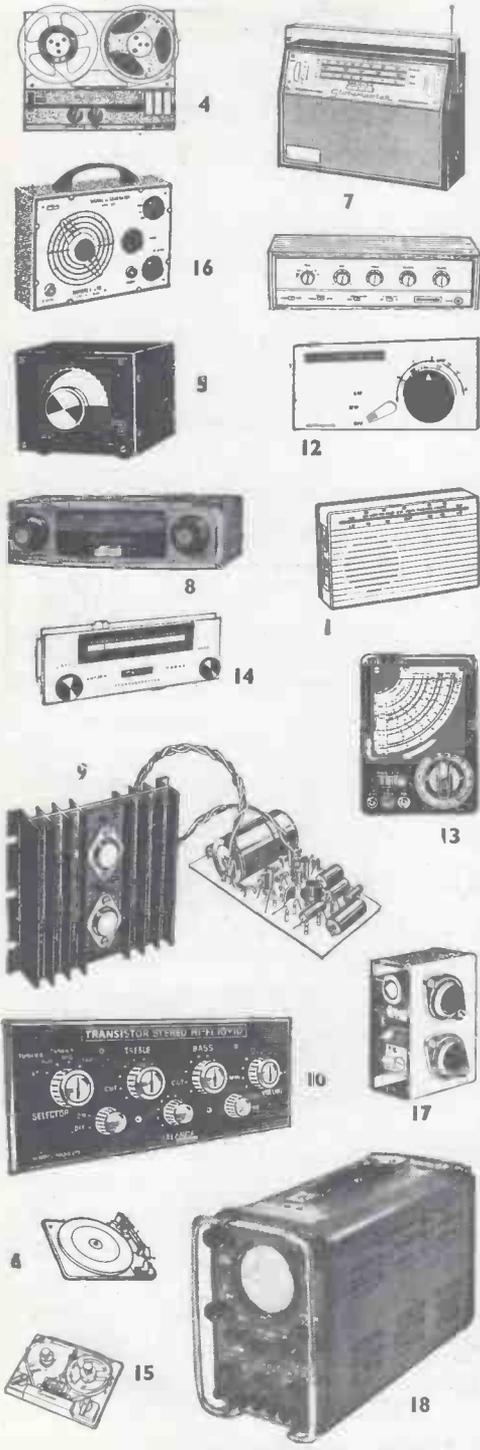

S.C.R. (SILICON CONTROLLED RECTIFIERS)
 1 Amp 50 p.i.v. 7/6. 100 p.i.v. 9/6. 200 p.p.v. 12/6. 300 p.i.v. 15/6. 400 p.i.v. (280 v. RMS) 17/6. 7 amp. 400 p.i.v. 25/-

HI-FI AND ORGAN DEMONSTRATION ROOM OPEN—ALL WELCOME

(1) **REGENT-6 MW/LW POCKET RADIO TO BUILD**
 6-Transistor superhet. Geared tuning. Push-pull speaker output. Moulded cabinet 5x3x1 1/2 in. Phone socket. **TOTAL COST TO BUILD 69/6** P.P. 2/-
 Full tuning on both bands.

(2) **SOLID SLATE IGNITION As Sept.**
 "P Electronics."
 All parts **£6/19/6**, post 2/6.

(3) **FM STEREO DECODER KIT**
 7-Transistor printed circuit design with stereo indicator and pre-amp. For use with any valve or transistor FM tuner. Uses Ger. and silicon transistors and pot cores to Mullard design. **PRICE £5.19.6** P.P. 2/-

(4) **BUILD A QUALITY 2 OR 4 TRACK TAPE RECORDER**
 NEW 3-SPEED VERSION. Using New '363' Decks. ★ **TWO-TRACK**. Deck **£10/10/-**. **Martin Amplifier £14/19/6**. Cabinet and Speaker 7 gns. Complete kits with FREE 7in. 1,200ft. tape, spare spool. **27 gns.** 15/-
 Today's value 35 gns.

★ **FOUR-TRACK**. Deck **£13/10/-**. **Martin Amplifier £15/19/6**. Cabinet and speaker 7 gns. Complete kits with FREE 7in. 1,200ft. tape, spare spool. **30 gns.** 15/-
 Today's value 40 gns.

DEAC RECHARGEABLE BATTERIES
 *3.6 volt 500 mA/h 12/6 P.P. 1/6
 *9.6 volt 225 mA/h 20/- P.P. 1/6
 DEAC charger for 3.6 and 9.6 volt packs, 45/-
 Also eliminator **67/6**. P.P. 2/-

(5) **VHF FM TUNER TO BUILD**
 87/105 Mc/s. "5 transistor Superhet." Geared tuning. Terrific quality and sensitivity. For valve or transistor amplifiers. 4x3 1/2 x 2 1/2 in. Complete with dial plate. (The item 3 FM Decoder).
TOTAL COST TO BUILD £6.19.6 P.P. 2/6
 (Cabinet Assembly 20/- extra)

(6) **GARRARD DECKS—BRAND NEW, WITH HIGH QUALITY CARTRIDGES**

1000 mono ...	£5 19 6	SP25 stereo ...	£10 19 6	401 less cart./arm	£27 10 0
1000 stereo ...	£6 6 0	SP25 Deram ...	£13 10 0	AT6 mono ...	£8 19 6
2000 mono ...	£6 6 0	AT60 less cart...	£9 19 6	AT6 stereo ...	£9 10 0
2000 Stereo ...	£6 9 6	AT60 mono ...	£10 10 0	AT6 Deram ...	£11 19 6
3000Im stereo ...	£7 10 6	AT60 stereo ...	£10 19 6	Decadec Mk. II	£17 17 0
SP25 less cart. ...	£9 19 6	AT60 Deram ...	£13 10 0	A70 less cart...	£17 17 0
SP25 mono ...	£10 10 0	LAB80 less cart.	£27 0 0	(P. & P. 5/- any type)	

All other makes of decks and cartridges in stock.

(7) **GLOBEMASTER MW/LW/SW PORTABLE RADIO TO BUILD**
 6 MULLARD TRANSISTORS
 Full 3-waveband tuning. Push-button wave-change. Superhet printed circuit. Black-chromed cabinet 11x7 1/2 x 3 1/2 in. (SW 17-50 metres). Ear/Record sockets. 1 watt push-pull output.
TOTAL COST TO BUILD £7.19.6 P.P. 3/6

(8) **TOURMASTER CAR RADIO**
 7-Transistor MW/LW Car Radio. 12 volt operated. 3 watt output. Push-button wave-change. RF stage. Supplied built, boxed, ready to use with speaker and baffle. Car fixing kit and manufacturers' current guarantee. Special Bargain Offer. Buy Now! List Price 15 gns.
OUR PRICE £9.90 P.P. 3/6

10 AND 20 WATT MONO AND STEREO TRANSISTOR AMPLIFIERS

(9) **POWER AMPLIFIERS**. 10 watts RMS output. 100mV input. 30 c/s to 20kc/s ± 1dB. 6-Transistor Push-pull. Panel size 4x2 1/2 x 1in. H/S 4x4in.
 TPA10/3 3-5 ohm speaker, **£4/10/-**. P.P. 2/6
 TPA10/15 12-16 ohm speaker **£5/5/-**. P.P. 2/6
 (Mains unit, 1 or 2 amplifiers, 59/6. P.P. 2/6)

(10) **PREAMPLIFIERS**. 8 input selector. Treble, bass, volume, filter controls. 1 1/2mV to 300mV inputs. Battery operated or from Mains Unit. Output up to 150mV RMS.
 MP2 Mono 9 1/2 x 2 1/2 x 2in. **£5/10/-**. P.P. 2/6 (grey and gold front panel 8/6).
 SP4 Mono/Stereo, 9x3 1/2 x 1 1/2 in., **£10/19/6**, P.P. 3/6 (front panel plate 12/6).

The finest High Fidelity at Unbeatable Prices

(11) **25 WATT AMPLIFIER**
 8-Transistor design. Push-pull output for 7 1/2 to 16 ohm speaker. 150mV input. 30c/s to 20kc/s ± 1dB. For use with valve or transistor preamplifiers as item (10) above.
PRICE BUILT AND TESTED £7.19.6 P.P. 3/-
 (Mains unit 79/6, P.P. 2/6)

(13) **MULTI-METERS**

PT34 1kV	39/6	TP55 20kV	£5/19/6
TP10 2kV	75/-	EP30k 30kV	£6/10/-
EP10k 10kV	79/6	EP50k 50kV	£8/15/-
IT1-2 20kV	69/6	500 30kV	£8/17/6
EP20k 10kV	99/6	EP100k 100kV	£10/10/-

(14) **VHF FM TUNER**
 Supplied as 2 pre-assembled Panels, plus metal work. Superhet design, 88-108 Mc/s. 9 volt operated.
 Total cost **£12/17/6**, p.p. 2/6.

(15) **GARRARD BATTERY 2-SPEED 9 VOLT TAPE DECK**
 Brand New with R/P head, erase/osc. head, tape cassette and instructions. 2 speed 2-track. 9 volt operated. List price 13 gns.
OUR PRICE £8.19.6 P. & P. 3/6.

(16) **NOMBREX TEST UNITS**
 ★ 150 kc/s.—350 Mc/s. R.F. Generator, **£10/10/-**. All Transistor.
 ★ 10 c/s.—100 kc/s. Transistor. **£16/19/6**. Audio Generator.

(17) **5 WATT AMPLIFIER**
 6-Transistor Push-pull, 3 ohms. 6mV. into 1K. 12/18 v. supply. 2 1/2 x 2 x 1 1/2 in.
BUILT AND TESTED 69/6 P.P. 2/-
 (optional mains units 54/-)
 1 1/2 watt version **59/6**.
 Matching Preamplifier, 6 inputs, treble/bass selector/volume controls. 6-10 mV. output. 9-18 v. supply. **79/6**, p.p. 2/-.
 For use with any Transistor Amplifier

1966 CATALOGUE
 HAVE YOU A COPY?
 Fully detailed and illustrated. 150 pages of components, equipment, etc. Over 5,000 stock items. **PRICE 6/-**, post paid. Free discount vouchers with every catalogue.
YOU CANNOT AFFORD TO BE WITHOUT A COPY OF THIS CATALOGUE.

SUPPLIERS OF QUALITY COMPONENTS AND EQUIPMENT

WE CAN SUPPLY FROM STOCK MOST OF THE PARTS SPECIFIED ON CIRCUITS IN THIS MAGAZINE. SEND FOR QUOTATION. FULL DESCRIPTIVE LEAFLETS AVAILABLE ON ALL ITEMS.



BUILD THE WORLD'S FIRST ALL TRANSISTOR PORTABLE ORGAN KIT

- ★ EASY TO BUILD WITH PRINTED CIRCUITS AND FULLY COMPREHENSIVE HANDBOOK
- ★ CIRCUITS USE 170 TRANSISTORS AND DEVICES
- ★ 10 SELECTED TONE COLOURS PLUS VIBRATO
- ★ PORTABLE TWO COLOUR CABINET WITH DETACHABLE LEGS, MUSIC STAND, SWELL PEDAL
- ★ THE ONLY COMPLETE KIT AVAILABLE IN THE WORLD—BRITISH DESIGNED AND MADE

SPECIFICATION:

● TONE COLOURS (ROCKER TABS), 10 DIFFERENT TONES CAN BE SELECTED ● SWITCHED VIBRATO ● 49 NOTE C—C FULLY SPRUNG KEYBOARD ● 6 OCTAVES OF GENERATORS ● PRESET VOLUME CONTROL ● TONE COLOUR BLEND CONTROL ● FOOT SWELL PEDAL OUTPUT UP TO ½ VOLT ● 110/250 VOLT MAINS OR 18 VOLT BATTERY ● FULLY POLYPHONIC ● PLUG IN PRINTED CIRCUIT PANELS ● SIMPLE LOCKED-IN TUNING ● DETACHABLE LEGS WITH STOWAGE ● CABINET SIZE 30½ × 15½ × 9in. ● WEIGHT 35 lb. ● FULLY DETAILED INSTRUCTION HANDBOOK WITH PHOTOS, DRAWINGS AND CIRCUITS

MAYFAIR PORTABLE ELECTRONIC ORGAN

DETAILED LEAFLET ON REQUEST



Designed by L. W. ROCHE

BUILD FOR YOURSELF—YOUR FRIENDS—CLUBS AND GROUPS—SAVE POUNDS

TO BUILD YOURSELF IN EASY STAGES. UNBEATABLE FOR PRICE, PERFORMANCE AND QUALITY

★ COMPLETE KIT WITH CABINET ALL COMPONENTS & HANDBOOK **99 gns**

- ALL SOLD SEPARATELY PACKET BY PACKET
- H.P. AVAILABLE FOR COMPLETE KIT
- HANDBOOK SEPARATELY 20/- POST PAID

FULL AFTER SALES SERVICE ALL PARTS FULLY GUARANTEED

ACCLAIMED BY EVERYONE. CALL FOR DEMONSTRATION AND SEE FOR YOURSELF.

● GROUPS - CLUBS - HOBBYISTS - HOME ENTERTAINMENT - SCHOOLS ●

HENRY'S RADIO LTD.
ELECTRONIC COMPONENT SPECIALISTS

303, EDGWARE ROAD, LONDON, W.2, ENGLAND

PADDington 1008/9 (STD: 01-723-1008).

(Hours: Monday to Saturday, 9 a.m. to 6 p.m. Thursday, 1 p.m.)



Wilkinsons FOR RELAYS

P.O. TYPE 3000 AND 600

**BUILT TO YOUR REQUIREMENTS—QUICK DELIVERY
COMPETITIVE PRICES—VARIOUS CONTACTS
DUST COVERS—QUOTATIONS BY RETURN**

**LARGE STOCKS HELD OF MINIATURE SEALED RELAYS INCLUDING HIGH SPEED
G.E.C. — SIEMENS — S.T.C. — ERICSSON — E.M.I. — BEST MAKES — 25,000 IN
STOCK — 150 TYPES — DETAILED LIST ON REQUEST**

SIGNAL GENERATOR TYPE 52A. Input 230 volt 50 c/s., with leads, dummy antenna. 0 to 52 Mc/s. in 4 bands with calibration charts. Coarse and fine attenuators. Int. and ext. mod. Output 0.5 micro-volts to 100 milli/v. impedance, 70 and 100Ω, £10, Carr. 20/-
AUTO TRANSFORMERS by S.T.C. Totally enclosed C-core type, 110-250 volts, 8 tapings. 50 cycles. 1,000 watts. Size 6½ × 5½ × 5¼in., £4. Post 7/6.

SMALL MAGNETIC COUNTERS

3½ × 1in., 10 counts per second with 4 figures. The following D.C. voltages are available, 6 v., 12 v., 24 v., 50 v., or 100 v.




35/- Post 1/6.

VEEDER-ROOT MAGNETIC COUNTERS WITH ZERO RESET 800 COUNTS PER MINUTE. COUNTING TO 999,999. 230 volts A.C. or 110 v. D.C. 65/- Post 2/9.
Fuse Holders L356. 1 hole fixing 30/- doz. Slydlok Fuses. 60 amp. with studs 30/- doz. Photo-Electric Cells. 90 CV 17/6. Post 2/-
Projection Lamps. 100 vt 100 watt, Pre-focus, Cap or S.B.C., double contact, 17/6. post 2/-.

METERS GUARANTEED. Complete list available

2in. Moving Coil Flush Round. Microamps 0/500, 25/-
Amps. 0/5, 27/6; 0/15, 15/-
Milliamps. 0/15, Square, 37/6.
0/25 or 0/50, Square, 17/6.
Amps. 50-0-50, Square, 17/6.
2½in. Moving Coil Flush Round. Microamps. 0/100(40/-; 0/500, 37/6; 0/250 Projection, 30/-
Milliamps. 10-0-10, 35/-; 0/100, 25/-; 0/150, Projection, 17/6. 3¼in. FR. MC. Rectifier, A.C., 0/100 microA., 95/-; 10 milliA., 10 or 20 v. 70/-; 0/200, 75/-
A.C. AMMETERS. 2½in. FR Moving Iron, 0/10, 44/-
HEAVY DUTY TRANSFORMER. Double wound. Input 200/250 v. Output 90/120 v. 14 amp., £15.
MAINS TRANSFORMERS. Output 28/37 v. 3 amps. 42/6. Rectifier for 24 v. D.C. 27/6. Post 5/-
HAIR HYGROMETERS, 4in. round, by Negretti & Zambra, scaled 0/100 reading relative percentage humidity. 65/- Post 3/-.

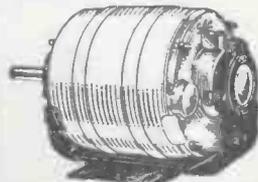

SILENT POWERFUL AC MOTOR 230 VOLTS RESILIENT MOUNTED

**BRAND NEW IN A ¼ h.p. FRAME CONTINUOUS RATED at ¼ h.p. and fitted with thermal device with Push Button reset ensures complete protection against overheating. 1,440 r.p.m. 1" shaft, 1½" long. Fully Guarded. EQUIPMENT RACKS 5ft. high, £5. POST OFFICE STANDARD. 6ft. high with U-channel sides drilled for 19in. panels, heavy angle base £7/10/- Cge. 20/-
ARROW CONTACTORS. 240 volts 50 c/s. 30 amp. 2 make, 60/- Post 3/6.**

PRICE 97/6

Carr. 7/6.

L. WILKINSON (CROYDON) LTD.
LONGLEY HOUSE LONGLEY RD. CROYDON SURREY

Phone: THO 0236

Grams: WILCO CROYDON

MINIATURE MICRO SWITCHES HONEYWELL 11SM1-TN13. S.P.D.T. Size: .781in. × .250in. × .356in., 6/6 ea. **MICRO SWITCH.** Burgess MK4BR, robust die cast casing, 8/6 each. Post 9d.

ILIFFE BOOKS

transistor bias tables

E. Wolfendale, B.Sc.(Eng), M.I.E.E.

This collection of accurately computed tables has been compiled to assist anyone wishing to design or build a transistor amplifier. The tables can be used either directly, to provide the values of the three resistors required for the conventional bias circuit, or alternatively, as a starting point for more detailed bias circuit analysis. Optimum values are not given in the tables as these depend on a number of factors outside the control of the author, such as the tolerance of the resistors to be used, the range of the ambient temperature over which the amplifier is to operate and the likely variation in the supply voltage. Sufficient information is provided however to enable the designer to arrive rapidly at values near the optimum for the conditions for which he is designing. The author has been closely associated with research into and development of transistors for many years and he is a well known lecturer on transistors and their applications.

55 pp illustrated 21s net 22s by post
ILIFFE BOOKS LTD., Dorset House, Stamford St., S.E.1

short wave listening

J. Vastenhoud


A Philips paperback intended as a guide for the benefit of the increasingly large number of regular listeners to short wave transmitting stations, and also for radio amateurs who are interested in short wave listening.

112 pp illustrated 12s 6d net 13s 5d by post
available from leading booksellers

WW-143 FOR FURTHER DETAILS.

NO EXCUSES! NO DELAYS! FROM STOCK! VARIABLE VOLTAGE TRANSFORMERS



PORTABLE

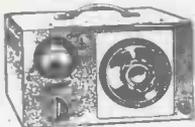

Input 230 v. A.C. Output variable 0-260 v. A.C. at 1.5 amp. Fitted in beautifully finished steel case. Complete with voltmeter, pilot lamp, fuse, switch, carrying handle.
£8/10/-. P. & C. 10/-.
Also 2.5 amp. as above £9/17/6. P. & C. 10/-.

OPEN TYPES

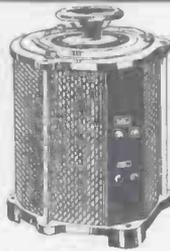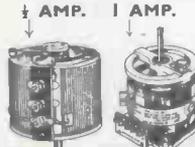Designed for Panel Mounting
Input 230 v. A.C. 50/60 Output variable.
0-260 v.
½ amp. £3 3 0
1 amp. £4 10 0
2½ amp. £5 12 6
↓ AMP. 1 AMP.



50 AMPS



1 AMP.

CONSTANT VOLTAGE TRANSFORMER

Input 185-250 v. A.C. Output constant at 230 v. A.C. Capacity 250 watt. Attractive metal case. Fitted red signal lamp. Rubber feet. Weight 17lbs. Price £11/10/-. P. & P. 10/-.



INPUT 230 v. A.C. 50/60~
BRAND NEW. Carriage Paid. Buy direct from the importer, keenest prices in the country. All Types (and Spares) from ½ to 50 amp. available from stock.

0-260 v. at 1 amp.	£4 10 0
0-260 v. at 2.5 amps.	£5 17 6
0-260 v. at 4 amps.	£8 7 6
0-260 v. at 5 amps.	£9 0 0
0-260 v. at 8 amps.	£13 10 0
0-260 v. at 10 amps.	£17 0 0
0-260 v. at 12 amps.	£19 10 0
0-260 v. at 15 amps.	£22 0 0
0-260 v. at 20 amps.	£32 10 0
0-260 v. at 37.5 amps.	£65 0 0
0-260 v. at 50 amps.	£85 0 0

15 DIFFERENT TYPES AVAILABLE FOR IMMEDIATE DELIVERY.

100 WATT POWER RHEOSTATS (NEW)


Ceramic construction winding embedded in Vitreous Enamel heavy duty brush assembly designed for continuous duty. AVAILABLE FROM STOCK IN THE FOLLOWING 11 VALUES: 1 ohm 10a., 5 ohm 4.7a., 10 ohm 3 a.; 25 ohm 2 a.; 50 ohm 1.4 a.; 100 ohm 1 a.; 250 ohm .7 a.; 500 ohm .45 a.; 1,000 ohm 280 mA.; 1,500 ohm 230 mA.; 2,500 ohm .2 a.; Diameter 3½in. Shaft length 7in. dia. ½in. 27/6. P. & P. 1/6.



NOW ALSO AVAILABLE IN 25 WATT
10 ohm 1.5 a.; 25 ohm 1 a.; 50 ohm .75 a.; 100 ohm .5 a.; 250 ohm .3 a.; 500 ohm .2 a.; 1,000 ohm .15 a.; 1,500 ohm .12 a.; 2,500 ohm .1 a.; all at 14/6. P. & P. 1/6.

5 Amp. AC/DC VARIABLE VOLTAGE OUTPUT UNIT

Input 230 v. A.C. Output 0-260 v. A.C. Output 0-240 v. D.C. Fitted large scale ammeter and voltmeter, Neon indicator, fully fused. Strong attractive metal case 15in. x 8½in. x 6in. Weight 24 lb. Infinitely variable, smooth stepless voltage variation over range. Price £30 C. & P. £2.
Also 7 Amp. A.C./D.C. Variable Output Power Unit
Input 230 v. A.C. Output continuously VARIABLE from 0 to 260 v. A.C. OR 0 to 230 v. D.C. at 7 a. Robustly constructed in metal case, complete with safety fuse, neon indicator and voltmeter. Size 17in. x 12in. x 7in. Weight 36 lb. Price £34/10/- Carriage 20/-.

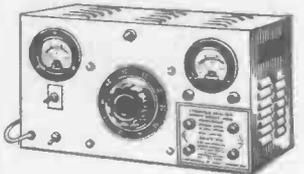

SLIDER RESISTANCES

1.2 ohm 14 amp. 27/6; 36 ohm 6.5 to 2.8 amp. tapered winding, geared drive (less knob) 37/6. P. & P. 3/6.

★ 230v. A.C. MOTOR ★ & REDUCTION GEAR BOX

Reversible ½ h.p., 1,450 r.p.m., ½in. dia. 1in. long shaft. Mounted in anti-vibration cradle. Supplied complete with precision 20-1 reduction gearbox and pulleys. Made to highest standard for computer work. Ex equip. First class condition. Price £3.5.0. P. & P. 7/6 extra.

SERVICE TRADING COMPANY



SERVICE TRADING CO

Postage and Carriage shown below are inland only. For overseas please ask for quotation. We do not issue a catalogue or list.

LIGHT SENSITIVE SWITCHES
Kit and parts including ORP.12 Cadmium Sulphide Photo-cell. Relay, Transistor and Circuit. Now supplied with new Siemens High Speed Relay for 6 or 12 volt operations. Price 25/-, plus 2/6 P. & P.
ORP.12 and Circuit 8/6 post paid.



A.C. MAINS MODEL
Incorporates mains transformer, rectifier and special relay with 3x5 amp. mains c/o contacts. Price inc. circuit 47/6, plus 2/6 P. & P.

PHOTO ELECTRONIC COUNTER
Can be set for counts of up to 500 per minute. 210-250 v. A.C. powered. Kit of Components including photo cell, high speed non-resettable counter, transformer relay, etc., together with clear circuit diagram. £32/6, plus 2/6 P. & P.

LIGHT SOURCE AND PHOTO CELL MOUNTING
Precision engineered light source with adjustable lens assembly and ventilated lamp housing, to take MBC bulb. Separate photo cell mounting assembly for ORP.12 or similar cell, with optic window. Both units are single hole fixing. Price per pair £210/- plus 2/6 P. & P.

SOLENOID OPERATED MAGNETIC RELAY
Type Sc/3944, 4 pole c/o, 10 amp. contacts, 24 volt D.C. operation. 12/6 each. P. & P. 1/6.

SIEMENS SEALED HIGH SPEED RELAYS
H96A, 2.2 ohm + 2.2 ohm, H96G, 50 ohm + 50 ohm, H96C, 145 ohm + 145 ohm, H96E, 1,700 ohm + 1,700 ohm. All at 12/6 each. P. & P. 1/- on each Relay. Bases 4/6 each.

P.O. RELAYS, Type 3000
100 ohm 3 c/o, 2 make, 2 break. 200 ohm, 6 c/o. 500 ohm, 1 Heavy duty c/o. 500 ohm, 4 Heavy duty make. 16,000 ohm, 2 make, 2 break. All at 12/6 each. 20,000 ohm, 2 Heavy duty make. Plus 1/- P. & P.

SOLENOID. Overall length 3 1/4 in., stroke 1/4 in. to 1/2 in. Maximum push 8 oz. 12-24 v. D.C. operation. D.C. resistance 35 ohm. Price 8/6. P. & P. 1/6.

G.E.C. SEALED RELAYS
M1069 5,000 ohms, 2 c/o. M1084 180 ohm, 4 c/o. M1092 670 ohm, 4 c/o. M1095 670 ohm, 2 m, 2 b. M1100 670 ohm, 2 c/o. Ex new equipment. M1492 670 ohm 4 c/o.

14,000 OHM SEALED RELAY. High Speed single c/o. Platinum contacts. Super-sensitive, ideal for Transistor circuitry. Will operate on 1 milliamp, 25/- P. & P. 1/-.


CARPENTER POLARISED RELAY. Type 5A77R 2x1,900 turns at 55 ohms. Including Base 25/- P. & P. 1/-.

COMPACT HEAVY DUTY 6 volt DC RELAY
6-9 volt D.C. operation 30 ohm coil 2x10 amp. c/o contacts, will handle up to 250 volt A.C. Size 1 1/2 in. high x 2 1/2 in. x 1 1/2 in. Price 7/6, plus 1/- P. & P. 3 for 20/- post paid.

LATEST HIGH SPEED MAGNETIC COUNTERS
4 figure 10 impulses per second. Type 100A, 500 ohm coil. 18-24 v. D.C. operation. Type 100B, 2,300 ohm coil, 36-48 v. D.C. operation. Any type, 15/- each, plus 1/6 P. & P.

RESETTABLE HIGH SPEED COUNTER
4 figure 1,000 ohm coil, 36-48 v. D.C. operation. £310/- P. & P. 1/6.
3 figure 700 ohm coil, 24 v. D.C. £212/- P. & P. 1/6.

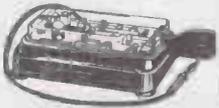SEMI-AUTOMATIC "BUG" SUPER SPEED MORSE KEY.
7 adjustments, precision cooled, speed adjustable 10 w.p.m. to as high as desired. Weight 2 1/2 lb. £4/12/6 post paid.



TRANSISTORISED MORSE OSCILLATOR
Fitted 2 1/2 in. Moving Coil Speaker. Uses type PP3 or equiv. 9 v. battery. Complete with latest design Morse Key. 22/6, plus 1/6 P. & P.

VENNER 14-DAY CLOCKWORK TIME SWITCH
5 amp. 230 v. contact, 1 on/off every 24 h. Fitted in metal case with key. Used but guaranteed. 47/-, plus 3/- P. & P.

ALL MAIL ORDERS. ALSO CALLERS AT:
57 BRIDGMAN ROAD,
LONDON, W.4. Phone: 995 1560
Closed Saturdays.

230 v. A.C. RELAY. 2 c/o 2 amp. contacts, 9/6, ex new equip. P. & P. 1/6.

HIGH SPEED BLOWER UNIT
200/250 volt A.C. Powerful 2-speed motor, 11,000 and 13,000 R.P.M. 17/6 plus P. & P. 2/6.
AUTO TRANSFORMERS. Step up, step down. 110-200-220-240 v. Fully shrouded, New. 300 watt type £3 each. P. & P. 4/6. 500 watt type £4/2/6 each. P. & P. 6/6. 1,000 watt type £5/5/- each. P. & P. 7/6.

UNIVERSAL DEMONSTRATION TRANSFORMERS
A complete composite apparatus, comprising a robustly built transformer and electro-magnet with removable coils and pole pieces. Coil tapped for 230 v., 220 v., 110 v., 115 v.; 6, 12, 36, 110 v. A.C. These coils are also used for D.C. experiments. Complete with all accessories as shown. £17 plus 10/- carr. Leaflet on request.



WIMSHURST ELECTROSTATIC GENERATORS £13/17/6, carr. U.K. (B.R.S.) 10/- Leaflet on request.

SENSITIVE GALVANOMETER
Centre zero 300-0-300 microamp. 90 ohm approx. Callibrated 30-0-30 in clear divisions. Mounted in sturdy sloping front case with top terminals. Price £4/10/- P. & P. 2/6.

Matching voltmeter calibrated 0-3 v. and 0-15 v. D.C., £4/10/- P. & P. 2/6.
D.C. Ammeter 0.6 amp. and 0.3 amp., £4/10/- P. & P. 2/6. Set of 3 matching instruments £12/19/- P. & P. 4/6.

230 VOLT A.C. GEARED MOTORS
Type D156 5 r.p.m. 1.7lb. inch, £2/9/6. P. & P. 2/6.
Type B168 80 r.p.m. .28lb. inch, £2/2/- P. & P. 2/6.
Type D168 39 r.p.m. 1.45lb. inch, £2/17/6. P. & P. 2/6.

HELIPOT Beckman Model A, 1,000 ohm, 10 Turn. Complete with precision dial and Brake £2/10/- P. & P. 2/-.

NICKEL CADMIUM BATTERY. Sintered Cadmium Type, 1.2 v. 7AH. Size: height 3 1/2 in., width 2 1/2 in. x 1 1/2 in. Weight: approx. 13 ozs. Ex-R.A.F. Tested, 12/6. P. & P. 2/6.

UNISELECTOR SWITCHES, 75 ohm coil, 24 v. D.C. 6 bank 25 position, 5 non-bridging, 1 bridging wiper; 5 bank 25 position, 4 non-bridging, 1 bridging wiper; 6 bank arranged to give 3 bank, 50 wiper; 8 bank arranged to give 4 bank, 50 wiper. These switches have been carefully removed from equipment. All at 35/- each. P. & P. 2/6.

ULTRA VIOLET BULBS
Easy to use source of U.V. for dozens of practical and experimental uses.
12 volt 36 watts A.C./D.C. SBC. 6/6. P. & P. 1/-
12 volt 60 watt A.C./D.C. SBC. 8/6. P. & P. 1/-
Transformer to suit the above. Input 200-240 v. A.C. 12 volt 36 watts, 21/- P. & P. 2/6. Input 200-240 v. A.C. 12 volt 60 watt, 27/- P. & P. 3/6.
Set of 4 Colours FLUORESCENT PAINT. Red, yellow, green and cerise. In 1 oz. jars. Ideal for use with the above Ultra Violet Bulbs, 11/- plus 2/6 P. & P.

34R SILICON SOLAR CELL
4x .5 volt unit series connected, output up to 2 v. at 20 mA in sunlight. 30 times the efficiency of selenium. As used to power Earth Satellites. 37/6, P. & P. 1/-.

JUST PUBLISHED "SOLAR CELL AND PHOTO-CELL EXPERIMENTERS' GUIDE"
Teaches the principles of light sensitive devices and their application. 26/- post paid.



MOVING COIL HEADPHONES
Finest quality soft chamois ear-muffs. Superb reproduction. Complete with Jack plug 25/6. P. & P. 2/6.
Similar with m/c microphone, with 5-way plug as used in No. 19 Set, 30/- P. & P. 2/6.

"CABY" MULTI-RANGE TEST METER
Model B40. D.C. volt 0.5 v. 2.5 v. at 10,000 ohms per volt. Ideal for transistor circuit testing. A.C. and D.C. volt, 10 v., 50 v., 250 v., 500 v., 1,000 v. at 4,000 ohms per volt. Resistance 2K ohm, 200 K-ohm, 2 megohm, 20 megohms. Repair service available. Price includes Test Leads, Battery, Instruction book, packing and post (U.K.). Price £28/6. Additional models available. Leaflet sent on request.

L.T. TRANSFORMERS
All primaries 220-240 volts.
Type No. Sec. Taps Price Carr.
1 30, 32, 34, 36 v. at 5 amps. £3/5/0 6/-
2 30, 40, 50 v. at 5 amps. £5 5/0 6/6
3 10, 17, 18 v. at 10 amps. £3 10/0 4/6
4 6, 12 v. at 20 amps. £4 17/6 6/6
5 17, 18, 20 v. at 20 amps. £5/12/6 6/6
6 6, 12, 20 v. at 20 amps. £5/5/0 7/6
7 24 v. at 10 amps. £3/15/0 5/6

A.C. AMMETERS 0-1, 0-5, 0-10, 0-15, 0-20 amp. F.R. 2 1/2 in. dia. All at 21/- each.
A.C. VOLTMETERS 0-25 v., 0-50 v., 0-150 v. M.I. 2 1/2 in. Flush round all at 21/- each. P. & P. extra.
0-300 v. A.C. Rect. M-Coil 2 1/2 in. 29/-
0-300 v. A.C. Rect. M-Coil 3 1/2 in. Type W23.. 55/-
D.C. AMMETERS
0-5 amp. D.C. M.I. 2 1/2 in. Rnd. 11/6
0-500 Microamp. sub-min. 1 1/2 in. dia. Scaled.
0-1 milliamp. 21/- Postage extra.

VAN DE GRAAF ELECTROSTATIC GENERATOR, fitted with motor drive for 230 v. A.C. giving a potential of approx. 50,000 volts. Supplied absolutely complete including accessories for carrying out a number of interesting experiments, and full instructions. This instrument is completely safe, and ideally suited for School demonstrations. Price £6/6/- plus 4/- P. & P. 1/- on request.

Latest type SIEMENS MINIATURE RELAY in Transparent Case. 4 c/o 700 ohm 14/6. Base 4/- 2 c/o 700 ohm coil, size 7/8 x 1/2 x 1 1/2 in. 15/- inc. base.
VARLEY TYPE VP4 (similar to illus.), 5,800 ohm, 4 c/o. New, 12/6, less base.
Similar to above. Mfd. by GRUNER, 4 c/o, 2,400 ohm coil. New, 12/6, less base.

INSULATED TERMINALS
Available in black, red, white, yellow, blue and green. New 15/- per doz. P. & P. 1/-.

S.T.C. SILICON POWER RECTIFIERS
RS300 Series. All types 1.5 amp., wire ended.
RS310, 100 v. P.I.V. 4/- RS350, 500 v. P.I.V. 8/-
RS330, 300 v. P.I.V. 6/- RS360, 600 v. P.I.V. 9/-
RS340, 400 v. P.I.V. 7/- RS380, 800 v. P.I.V. 10/-
4 can be used to make 3 amp. bridge. Not Seconds. Brand New Stock. Post paid.

20 WAY STRIP containing standard Post Office telephone Jack Sockets. Overall size 1 1/2 in. x 3 1/2 in. x 1/2 in. NEW PRICE 15/- each. P. & P. 1/6.

INSULATION TESTERS (NEW)
Test to I.E.E. Spec. Rugged metal construction, suitable for bench or field work, constant speed clutch. Size L. 8 in., W. 4 in., H. 6 in. Weight 6 lb. 500 volt, 500 megohms. Price £22 carriage paid. 1,000 volts, 1,000 megohms, £28 carriage paid.

NEW SOUND POWER OPERATED EX-ADMIRALTY HEAD AND BREAST SETS
Two such sets connected up will provide perfect Intercom. No batteries required. Will operate up to 1/2 mile. Price 17/6 each, plus P. & P. 3/- or 32/6 per pair. P. & P. 4/-.



PERSONAL CALLERS ONLY: 9 LITTLE NEWPORT STREET, LONDON, W.C.2. Tel.: GER 0576 (OFF LEICESTER SQUARE)
Open till 1 p.m. Thursday and all day Saturday.

SEW PANEL METERS

FOR ILLUSTRATED LEAFLET
Special Quotations for Quantities

CLEAR PLASTIC METERS



Type MR.38r. 1 21/32 in. square fronts.

50µA	32/6
100µA	29/6
200µA	27/6
500µA	25/6
50-0.50mA	29/6
100-0.100mA	27/6
500-0.500mA	22/6
1-0.1mA	22/6
1mA	22/6
2mA	22/6
5mA	22/6
10mA	22/6
20mA	22/6
50mA	22/6
100mA	22/6
150mA	22/6
200mA	22/6
500mA	22/6
750mA	22/6

Type MR.45P. 2in. square fronts.

50µA	39/6
100µA	35/6
500µA	27/6
50-0.50mA	35/6
100-0.100mA	32/6
1mA	25/6
5mA	25/6
10mA	25/6
50mA	25/6
100mA	25/6
1 amp. D.C.	25/6
10V D.C.	25/6

Type MR.52P. 2 1/2 in. square fronts.

50µA	57/6
100µA	47/6
500µA	37/6
50-0.50mA	57/6
100-0.100mA	47/6
1mA	32/6
5mA	32/6
10mA	32/6
50mA	32/6
100mA	32/6
500mA	32/6
1A D.C.	32/6
5A D.C.	32/6

Type MR.85P. 4 1/2 in. x 4 1/2 in. fronts.

1 amp D.C.	45/6
100µA	59/6
200µA	55/6
500µA	49/6
50-0.50mA	69/6
100-0.100mA	59/6
1-0.1mA	45/6
1mA	45/6
5mA	45/6
10mA	45/6
50mA	45/6
100mA	45/6
150mA	45/6
500mA	45/6


Type MR.85P. 3 1/2 in. x 3 1/2 in. fronts.

50µA	59/6
100µA	49/6
500µA	39/6
50-0.50mA	59/6
100-0.100mA	49/6
1mA	35/6
5mA	35/6
10mA	35/6
50mA	35/6
100mA	35/6
500mA	35/6
1A D.C.	35/6
5A D.C.	35/6
10V D.C.	35/6
50V D.C.	35/6
100V D.C.	35/6
500V A.C.	35/6
1000V A.C.	35/6
5000V A.C.	35/6
10 amp. A.C.	35/6
10 amp. A.C.	35/6
10 amp. A.C.	35/6
10 amp. A.C.	35/6

BAKELITE PANEL METERS

Type MR.65. 3 1/2 in. square fronts.

25µA	65/6
50µA	42/6
100µA	39/6
500µA	35/6
50-0.50mA	42/6
100-0.100mA	35/6
500-0.500mA	29/6
1-0.1mA	29/6
50mA	39/6
100mA	39/6
1mA	29/6
5mA	29/6
10mA	29/6
50mA	29/6
100mA	29/6
500mA	29/6
1A D.C.	29/6
5A D.C.	29/6
15A D.C.	29/6

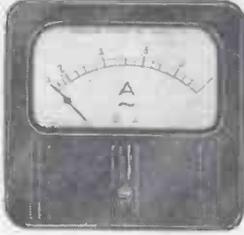

*Moving iron, all others moving coil

LELAND MODEL 27 BEAT FREQUENCY OSCILLATORS
Frequency 0-20 Kc/s. on 2 ranges. Output 500µ or 5kΩ. Operation 200/250 v. A.C. Supplied in perfect order £12/10/- Carr. 10/-.

NATIONAL HRO COILS
Set of 9 general coverage coils covering 50 kc/s-30 Mc/s. £10/10/- Carr. 10/- Also HRO dials. 27/6. P. & P. 1/6.

LONDEX COAXIAL AERIAL CHANGEOVER RELAYS
24 volt D.C. Complete junction box as used for TB 1935 TX. Brand new boxed. 39/6. Carr. 4/6.

No. 10 MOVING COIL HEADSET AND MICROPHONE
High quality, rubber moulded headset and hand microphone with pressel switch. Low Imp. new. 22/6. P. & P. 2/6.

R.209 MK. 2 COMMUNICATION RECEIVERS
First-class receiver covering 1-20 Mc/s. on 4 bands. A.M./C.W./F.M. Operates on 6 v. D.C. internal supply. Incorporates precision vernier drive, BFO. Aerial trimmer and internal speaker. As new condition. £22/10/- Carr. 20/-.

HEADSET AND BOOM MICROPHONE
Carbon mic, moving coil earpiece. Ex-USA Military. 49/6. P. & P. 3/6.

CT53 SIGNAL GENERATOR
8.9-15.5 Mc/s. and 20-300 Mc/s. Variable precision attenuator. A.C. mains. Supplied in perfect order less calibration chart. £12/10/- Carr. 10/-.

G. W. SMITH & CO. (RADIO) LTD
3-34 Lisle St., London, W.C.2 ALSO SEE OPPOSITE PAGE



MODEL 370-E MULTIMETER
20,000Ω/volt D.C. volts 0.5/2.5.
10/50/250/1,000/5,000 v. A.C. volts 0.2/5/10/50/250/1,000 v.
D.C. Current 0/50µA/1/10/50/250mA 1/10 amp
A.C. Current 0/250mA/1/10 amp. Resistance: 0/5k/500/5 meg./50 megohm.
£12/10/- P. & P. 3/6.




TE-900 20,000Ω/VOLT GIANT MULTIMETER
6in. full view meter. 2 colour scale. 0/2.5/10/250/1,000/5,000 V. A.C. 0/25/12.5/10/50/250/1,000/5,000 V. D.C. 0/50µA/100/1000/5000 mA. 10 amp. D.C. 0/2K/200K/20 Meg. OHM.
£12/19/6. P. & P. 6/6.



MODEL 500, 30,000 O.P.V.
0/5/2.5/10/25/100/250/500/1,000/5,000/10,000 V. D.C. 0/2.5/10/25/100/250/500/1,000 V. A.C. 0/50µA/500/5000 mA. 12 amp. D.C. 0/50K/500K/5 Meg. Ω.
£8/17/6. Post paid.



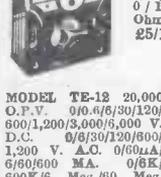
MODEL TE.80, 20,000 O.P.V.
0/10/50/100/500/1,000 v. A.C. 0/5/25/150/250/500/1,000 v. D.C. 0-50 µA. 5/50/500mA. 0/5k/50k/500k/5 meg. Ω.
£4/17/6. P.F. 3/-.




MODEL TE-12, 20,000 O.P.V.
0/0.6/3/30/120/600/1,200/3,000/5,000 V. D.C. 0/0.3/3/30/120/600/1,200 V. A.C. 0/0.6/3/30/120/600/1,200 V. D.C. 0/60µA/6/60/600 mA. D.C. 0/10K/100K/1M/10 Meg. Ohm. 200P-F-0.2 MFD.
£5/10/6. P. & P. 3/6.



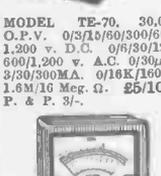TE-51. NEW 20,000Ω/VOLT MULTIMETER.
0/6/60/120, 1,200 V. A.C. 0/3/30/60/300/600/3,000 V. D.C. 0/0.3/3/30/120/600/1,200 V. A.C. 0/0.6/6/60/600 mA. D.C. 0/50K/500K/5 Meg. OHM.
35/- P. & P. 2/6.



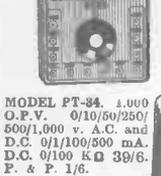MODEL TE-70, 30,000 O.P.V.
0/3/15/30/300/600/1,200 v. D.C. 0/6/30/120/600/1,200 v. A.C. 0/30µA/3/30/300mA. 0/16K/160K/1.6M/16 Meg. Ω.
£5/10/- P. & P. 3/-.



MODEL 250J, 8,000 O.P.V.
0/10/50/500/2,500 V. D.C. 0/10/50/500/2,500 V. A.C. 0/2 Meg. Ω.
0/250 mA.
-20 to +36 db.
49/6. P. & P. 2/6.



MODEL FT-34, 1,000 O.P.V.
0/10/50/250/500/1,000 v. A.C. and D.C. 0/100/500 mA. D.C. 0/100 KΩ 30/6. P. & P. 1/6.



MODEL U50D, WITH METER PRECISION, 20,000 o.p.v.
0/1/1.5/5/50/250/1,000 v. D.C. 0/2.5/10/50/250/1,000 v. A.C. 0/0.5/1.5/5/50/250 mA. 0/5K/50K/500K/5 meg. Ω. 0.001-2 mid.-20 -22 db.
£5/19/6. P. & P. 3/-.

LAFAYETTE HI-FI STEREO HEAD PHONES




★ Air cushioned headband
★ Soft rubber ear pads
★ Frequency response, 25 to 15,000 cycles. ★ High sensitivity. Impedance 8 ohms per phone. Supplied complete with all cables, wires, overload junction box and 3-connection plug.
79/6. P. & P. 2/6.

OS/8B/U OSCILLOSCOPES



High quality Portable American Oscilloscope 8in. c.r.t. T/B; 3 c/s 50 kc/s. X Amp; 0-500 kc/s. Y Amp.; 0-2 Mc/s. Power requirements 105-125 v. A.C. Supplied in brand new case, fully tested. £25. Carr. 10/- Suitable 230/115 v. Trans. 15/6

SOLARTRON OSCILLOSCOPES

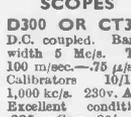


D300 OR CT316
D.C. coupled. Bandwidth 5 Mc/s. T/B 100 m/sec.-75 µ/sec. Calibrators 10/100, 1,000 kc/s. 230v. A.C. Excellent condition. £25. Carr. 20/-.

MODEL PV-58 VALVE VOLTMETER



11 meg. input. 7 D.C. volt ranges. 1.5-1,500 v. 7 A.C. volt ranges 1.5-1,500 v. 4,000 Peak to Peak. Resistance 2Ω to 1,000 MΩ. Decibels -10 db. to +65 db. Supplied brand new with instructions, leads and probe.
£12/10/- P. & P. 3/6.

MODEL ZQM TRANSISTOR CHECKER

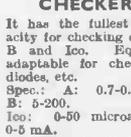

It has the fullest capacity for checking on A, B and Ico. Equally adaptable for checking diodes, etc. Spec. A: 0.7-0.9987. B: 5-200. Ico: 0-50 microamps. 0-5 mA. Resistance for diode 200Ω +1 MEG. Supplied complete with instructions, battery and leads.
£8/19/6. P. & P. 2/6.

HEAVY DUTY AUTO TRANSFORMERS

Step up or step down. Tapped 0.115-230 volts. Brand new. Ex-U.S.A. 3,000 watt £7/10/0. Carr. 10/-, 7,500 watt £15. Carr. 30/-.

SILICON RECTIFIERS

200 v. P.I.V. 200 mA	2/6
200 v. P.I.V. 6 amp.	5/6
400 v. P.I.V. 2 amp.	7/6
1,000 v. P.I.V. 650 mA	7/6
800 v. P.I.V. 500 mA	5/6
400 v. P.I.V. 500 mA	3/6
800 v. P.I.V. 5 amp.	7/6
100 v. P.I.V. 1 amp.	3/6
750 v. P.I.V. 165 mA	1/-


Discount for quantities. Post extra. THYRISTORS. Silicon Control Rectifiers. 400 P.I.V. 3-amp. 10/-

TRANSISTORISED TWO-WAY TELEPHONE INTERCOM



Operative over amazingly long distances. Separate call and press to talk buttons. 2-wire connections. 1000s of applications. Beautifully finished in ebony. Supplied complete with batteries and wall brackets.
£8/10/- pair. P. & P. 3/6.

VARIABLE VOLTAGE TRANSFORMERS

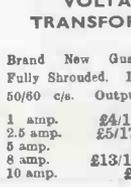

Brand New Guaranteed - Fully Shrouded. Input 230 v. 50/60 c/s. Output 0-260 v.

1 amp.	£4/10/-	12 amp.	£19/10/-
2.5 amp.	£5/17/6	20 amp.	£32/10/-
5 amp.	£9	2.5 amp. portable, metal case with meter-fuses, etc.	£9/17/6
8 amp.	£13/10/-		
10 amp.	£17		

P.C.R. RECEIVERS

BRAND NEW CONDITION—FULLY TESTED AND CHECKED BEFORE DESPATCH. 3 WAVE-BAND WITH R.F. STAGE—WONDERFUL VALUE. 860-2080 metres, 190-570 metres, 5.6-18 Mc/s. Fitted volume control, tone control and aerial trimmer. Internal speaker and output for low imp. phones; £8/19/6, carr. 10/6 with circuit. Plug in external power supplies. 230 v. A.C. 35/-, or 12 v. D.C. 19/6




HA-63A COMMUNICATION RECEIVER, OUTSTANDING VALUE

High class receiver covering 550 kc/s.-31 mc/s. on 4 bands. Incorporates 7 valves plus rectifier, IF stage, illuminated '8' meter, 1.5μV sensitivity, electrical bandspread on the 80/40/20/15 and 10 metre bands, slide rule dial, aerial trimmer, B.F.O., noise limiter. Output for phones or speaker. Operates on 115/220/240 v. A.C. Supplied brand new and guaranteed with manual. 24 gns. Carr. 10/-.




HA-55A AIRCRAFT RECEIVER

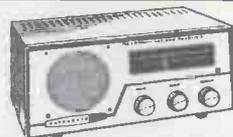108-136 Mc/s. High selectivity and sensitivity. Incorporates 2 RF stages including 6CW4 Nuvistor, 8 tubes for 11 tube performance, solid state power supply, adjustable squelch control, slide rule dial, built-in 4in. speaker and front panel phone jack. 220/240 v. A.C. Supplied brand new and guaranteed. £19/17/6. Carr. 10/-. 108-176 Mc/s. Ground Plane Antenna 59/6.



SKY KING AIRCRAFT RECEIVER

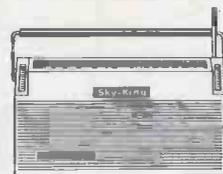New high quality transistorised portable receiver covering long and medium bands and aircraft band 108-136 Mc/s. 9 transistors and 6 semi-conductors. Built-in ferrite and telescopic aerials. Complete with leather carrying case, shoulder strap and earpiece. Large built-in speaker. Brand new and guaranteed £20/15/-.




H.A. 350 10-80 METRE AMATEUR RECEIVER

A superb receiver. Dual conversion with mechanical filter. 12 valves, crystal controlled osc., product detector, 100 kc/s. crystal calibrator, crystal B.F.O., A.N.L. '8' meter. Rock like stability. Brand new and guaranteed. 75 GNS. S.A.E. for full details.



HAMMARLUND SP600JX COMMUNICATION RECEIVER

High quality professional dual conversion communication receivers available for the first time in this country at a reasonable price. Frequency range 540 kc/s.-54 Mc/s. in 8 bands, variable tuning or 8 channel crystal controlled. 2.5 watt output into 600 ohms. Input 110/230 v. A.C. 20 valve circuit incorporating: Xtal filter, B.F.O. A.N.L., 8 meter, etc. Size 19 x 12 x 2 1/2in. (List £290). Offered in excellent condition, fully tested and checked. £100 each.

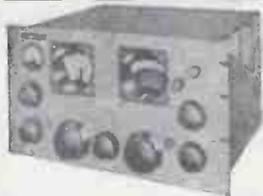

F.M. WIRELESS MICROPHONE

94-104 Mc/s. Transistorised. Operates from 9 v. battery. Complete with additional secret tie clip microphone. List £12/10/-. ONLY £7/10/-. P. & P. 2/6.



TE-40 HIGH SENSITIVITY A.C. MILLIVOLTMETER

10 meg. input. 10 ranges: .01/.03/.1/.3/1/3/10/30/100/300 volts. R.M.S. 6 c.p.a.-1.2 Mc/s. Decibels -40 to +45 db. Supplied brand new complete with leads and instructions. Operation 230 v. A.C. £17/10/-. Carr. 5/-.



MARCONI TF-195M BEAT FREQUENCY OSCILLATORS

Laboratory instruments offered at a fraction of cost. Range 0-40 kc/s. Output 600Ω or 2500Ω. Incorporates output level meter, operation 200/250 v. A.C. Excellent condition, fully tested and checked. £20. Carr. 30/-.

BARGAIN OFFER! S.T.C. SILICON RECTIFIERS

Brand new, guaranteed. 150 p.i.v. 25 amp. 19/6; 700 p.i.v. 100 amp. 49/6. List price £10 (P. & P. extra).

GARRARD RECORD PLAYERS

BRAND NEW AND GUARANTEED
 BRP-12 Player, mono £4 7 6
 1000 Changer, mono or stereo £5 19 6
 2000 Changer, mono or stereo £6 8 0
 A50 changer, mono or stereo £7 10 0
 3000 Changer—Stereo £7 19 6
 AT6 Mark II £8 19 6
 SP25 Player, mono or stereo £9 19 6
 A60 changer, mono or stereo £9 19 6
 A70 (less cart.) £21 10 0
 LAB80 £25 0 0
 401 Transcription £30 0 0
 All plus P. & P. 5/-.

LAFAYETTE TWO WAY RADIOS

Superb quality. Brand New and guaranteed. 3 Transistor £7/10/- pr. 6 Transistor £17/10/- pr. 10 Transistor with range boost. £22/10/- pr. Post extra.



AR-88D RECEIVERS

550 kc/s. to 32 Mc/s. Offered in excellent condition fully tested and checked before despatch, few only. £45. Carr. 30/-.

LAFAYETTE TE-46 RESISTANCE CAPACITY ANALYSER

2 PF - 2,000 MFD, 2 ohms-200 megohms. Also checks impedance, turns ratio, insulation 200 / 250 v. A.C. Brand New £15. Carr. 7/6.

TE22 SINE SQUARE WAVE AUDIO GENERATORS

Sine: 20 cps to 200 kc/s. on 4 bands. Square: 20 cps. to 30 kc/s. Output impedance 3,000 ohms. 200/250 v. A.C. operation. Supplied Brand new and Guaranteed with instruction manual and leads, £15. Carr. 7/6.



NUVISTOR GRID DIP METER

Compact true one hand operation. Frequency range 1.7-180 Mc/s. 230 v. A.C. operation. Supplied complete with all coils and instructions. £12/10/-, Carr. 5/-.



MINIATURE CLEAR PLASTIC METERS

1 1/2in. square fronts. Moving coil. Single nut fixing. 1 mA. 25/100 amp. 22/6. P. & P. 1/6.

PRECISION COMBINATION VOLTMETER/AMMETER

Two separate instruments housed in polished wood case, 8in. scales with knife edge pointers. Ranges as follows: A.C. and D.C. Volts 0-160-300-600 A.C. and D.C. Current: 0-25-50-150-200 amps. Supplied complete with shunts, leads and leather carrying case. Brand new condition. £9/19/6 each. Carr. 7/6.

AMERICAN	3in.	225ft. L.P. acetate	4/-
	3 1/2in.	600ft. T.P. mylar	10/-
RECORDING	5in.	600ft. std. plastic	8/6
	6in.	600ft. L.P. acetate	10/-
TAPES	5in.	1,200ft. D.P. mylar	15/-
	6in.	1,800ft. T.P. mylar	35/-
First grade quality	5 1/2in.	1,200ft. L.P. acetate	12/6
American	5 1/2in.	1,800ft. D.P. mylar	22/6
	5 1/2in.	2,400ft. T.P. mylar	45/-
tapes. Brand new and guaranteed.	7in.	1,200ft. std. mylar	12/6
	7in.	1,800ft. L.P. mylar	29/6
Discounts for quantities.	7in.	2,400ft. D.P. mylar	25/-
	7in.	3,600ft. T.P. mylar	58/6

Postage 2/- Over £3 post paid.

BARGAIN! TYPE 13A DOUBLE BEAM OSCILLOSCOPES



A high quality instrument offered at a fraction of original cost. Timebase 2 c/s.-750 kc/s. Separate Y1 and Y2 amplifiers up to 5.5 Mc/s. Built-in calibrators at 100 kc/s. and 1 Mc/s. Operation for 115/230 volts A.C. Available in excellent condition, fully tested and checked and complete with leads and probe. £22/10/-. Carr. 30/-.

TE-20RF SIGNAL GENERATOR



Accurate wide range signal generator covering 120 kc/s.-260 Mc/s. on 6 bands. Directly calibrated. Variable R.F. attenuator. Operation 200/240 v. A.C. Brand new with instructions £12/10/-. P. & P. 7/6. S.A.E. for details.



NOMBREX TRANSISTORISED EQUIPMENT

ALL Post Paid With Battery Transistorised Audio Generator 10-100,000 c/s. Sine or square wave. £18/15/- Transistorised Signal Generator 150 kc/s. 230 Mc/s. £10/10/- Transistorised resistance capacity bridge 1Ω-100 Meg. 0.1 pf-100μF. £8. Transistorised Induction bridge 1μH-100H. £18. Mains operated Transistor power supply unit, output 1-15 v. up to 100 mA. £8/10/-.

PORTABLE OSCILLOSCOPE CT.52

A compact (8 x 8 x 1 1/2in.) general purpose scope. T/B 10 c/s.-40 kc/s. bandwidth 1 Mc/s. Mullard DG7/5 2 CRT. For operation on 100/250 v. A.C. Supplied complete with metal transit case, strap test leads, and visor hood. Brand new and guaranteed. £22/10/-. Carr. 10/-. Supplied complete with instructions.



MINIATURE EDGEWISE PANEL METERS

34 x 22 mm. fronts. Moving coil. Available 400μ amp. or 200μ amp. 17/6 each. P. & P. 1/-.



SINCLAIR TRANSISTOR AMPLIFIERS

All Post Paid. Z12 amplifier 89/5. P.2.3 P.S.U. £3/19/6 X10 amplifier built £6/19/6. Kit £5/19/6 X10 power pack £2/14/6 X20 amplifier built £9/19/6. Kit £7/19/6 X20 power pack £2/14/6 Micro FM radio kit £5/19/6 Micro 6 59/6; TR750 amp. kit 39/6; Micro Amp. 28/6; Micro injector 27/6; All post paid.

TAPE DECKS

NEW MAGNAVOX 363 3 SPEED TAPE DECKS. 2 Track £10/10/-; 4 Track £13/10/-. Carr. Paid. New Garrard 3-speed Stereo Tape Deck. £29/10/-. Carr. Paid.

REUTER-TRACK TAPE HEADS

As fitted to Colloredo Mk. IV and Budio Decks. High imp. record/play back, low imp. erase. Brand new 19/6 pair. Also Miniflux & track, set of 3. 29/6; Bradmatic & track, set of 2. 92/6. Post extra.

G.W. SMITH & CO. (RADIO) LIMITED
 Phone: GERRARD 8204/9155
 Cables: SMITHEX LESQUARE
 3-34 LISLE STREET, LONDON, W.C.2

ALSO SEE FACING PAGE


Open 9 a.m.—6 p.m. every day Monday to Saturday. Trade supplied.

WW—145 FOR FURTHER DETAILS.

VARIABLE VOLTAGE TRANSFORMERS

WORLD FAMOUS "SLIDE-TRANS" AVAILABLE ONLY FROM I.M.O.

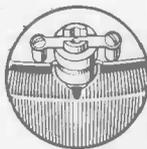★ RATED CURRENT CONSISTENT AT ALL POINTS ALONG THE WINDING



Inset shows latest type brush Gear providing 1 volt variation.

Output: 0-260 V. Input: 230 V.
A.C. 50/60 c.p.s. Shrouded fully
variable transformers for bench
or panel mounting.

1 Amp.	£4.10.0
2.5 Amp.	£5.17.6
5 Amp.	£9.0.0
10 Amp.	£18.5.0
20 Amp.	£32.10.0

C. & P. extra.

20 Amp. L.T. SUPPLY UNIT



Plus 40/- C. & P.
NOT EX-W.D. G.B. (Inland)

LATEST DESIGN
HEAVY DUTY
12/24 VOLT D.C.
Output: Adjustable
up to 20 amps.
CONTINUOUS
at 12/24 volts plus
trickle. Input: 220/
230/240 VAC 50
cycles.
FULLY FUSED.
Neon indicator, 0-20
amp. meter. Size:
16 x 12 x 20in.
high, in heavy gauge
steel cabinet. Grey
Hammer finish.
Weight: 50 lbs.
ONLY
£32.10.0

PORTABLE TRANSISTOR TESTER

SUITABLE FOR PRODUCTION & LABORATORY USE



SPECIFICATION.
Alpha 0.7 to 0.997
Beta 5-300
ICO 0-50µA. 5mA.
Capable of measuring
GERMANIUM AND
SILICON DIODES.
DESIGNED WITH RE-
STANCE SCALE 200
ohms to 1 Megohm as
an ADDED FEATURE.
Housed in heavy duty
plastic case, c/w in-
ternal battery.

Only
£7.15.0
Plus 5/- C. & P.


36ft. AERIAL MASTS

NEW LATEST PATTERN TUBULAR MAST

Check these vital points:

- ★ Made from 6 x 1½ in. dia. Sheradized steel sections, for durability and strength.
- ★ Extra strong locating base.
- ★ Top cap with fitted pulley and halyard.
- ★ 2 sets (8) Rotproof Guys.
- ★ Rustproofed Steel Picketing Stakes.

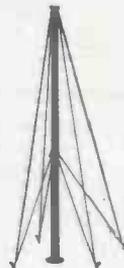ONLY £15.0.0 ex works
Carr. 20/-. Returnable wooden case 30/-.



NEW 4 section 20ft. Telescopic Masts. Copperised Steel. Self-supporting. 70' - Carr. 10/- 1½" dia. base. ¾" dia. top. Weight 16lbs.

CONSTANT VOLTAGE TRANSFORMERS

AUTOMATIC MAINS STABILISER



Maintain "spot-on" test gear readings at all times.

- ★ No Moving Parts
- ★ No Maintenance
- ★ No Attention.

Specification
Input: 240 v. A.C. ±20%
Output: 240 v. A.C.
Accuracy: ±1%
Weight: 21 lbs. Fitted
signal lamp and switch. £12.13.0 C. & P. 20/-

Capacity: 250 watts.
Size: 11 x 6½ x 6in. high.

★ CORRECTED WAVE

Modern design in 2-tone grey hammer steel case with handle. Complete with lead and plug.

1,000 WATT MODEL

Input 240 v. A.C. ±20%. Output accuracy ±1%. Fitted signal lamp and switch. £41.0.0 C. & P. 25/-.

TRANSISTORISED MEGOHMMETER



★ PUSH BUTTON USE 1966 EQUIPMENT

500v.-1000 Megohms.
Superb portable instrument. Supplied c/w batteries, probes and carrying case.

ONLY £25.0.0
C. & P. 7/6.

AC/DC VALVE VOLTMETER



- ★ 11 megohms per volt.
- ★ 5 mV-1,500 V. D.C.
- ★ 100 mV-1,500 V. D.C.
- ★ 0.1 ohm-1,000 Megohms.
- ★ 1 Kc Oscillator Test Source.
- ★ Complete with test probes.

Price ONLY £35.0.0

BUY DIRECT from MANUFACTURER

PORTABLE VARIABLE A.C. POWER SUPPLY UNIT

Designed for engineers whose requirements call for a visual indication of volts applied.

OUTPUT: 0-260 v. 1½ amps.
INPUT: 230 v. A.C. 50/60 c.p.s.
Fitted with fuse, voltmeter, safety indicator, on-off switch and lead. Size: 8x5x5in. high.



PRICE £8.17.6 C. & P. 10/-.



5 AMP. A.C. & D.C. VARIABLE SUPPLY UNIT

Specification:
Output: 0-260 V.A.C. 0-240 V.D.C.

- ★ Smooth stepless voltage variation from 0-Max.
- ★ Current consistent throughout the controlled range.
- ★ Ammeter and voltmeter fitted, and Neon indicator.

★ Fully fused input and output.
Strong steel case with carrying handle and rubber feet. 11in. x 7in. x 14in. high. MADE IN ENGLAND

PRICE £30.0.0 C. & P. 40/- Gt. Britain (Inland)

DIELECTRIC BREAKDOWN TESTER

VARIABLE HIGH VOLTAGE UNIT

- ★ Range: Infinitely variable up to 3,000 volts. 0.1 amp.
 - ★ Entirely suitable for continuous testing.
 - ★ Automatic safety cut-out. Input: Mains voltage. Input and test leads with clips.
- Model T30 £32

WALKIE TALKIE '88' SET

Made by E. K. Cole & Co. Weighs 5½ lb. (approx.) and measures 3½ x 5½ x 9½ in. Crystal controlled. Dry battery—H.T./L.T. i.e. Vidor L5537). Supplied to Overseas Govts. ONLY £10 EACH

IMMEDIATE DESPATCH

FULL SPARES AND SERVICE AVAILABLE

30 Amp. L.T. SUPPLY UNIT

0 to 18 V D.C. WITH SMOOTH STEPLESS VARIATION.

Designed for CONTINUOUS use at max. loading.

- ★ Fitted voltmeter and ammeter.
- ★ Input and output fully protected.
- Input: Mains A.C. robust construction. 2 tone grey hammer finish. Steel case.

£55.0.0 C. & P. 40/- G.B. (Inland)

ENTIRELY SUITABLE FOR PLATING PLANTS, LABORATORY SUPPLIES, ETC.

I.M.O.
(ELECTRONICS) LTD.

(Dept. WW9), 313 Edgware Road, London, W.2.

PADddington 2233/4

T.R.S. BARGAINS IN QUALITY KITS AND COMPONENTS

6 VALVE AM/FM TUNER UNIT

Med. and VHF 190m-550m, 88 Mc/s-103 Mc/s, 6 valves and metal rectifier. Self-contained power unit A.C. 200/250 V operation. Magic-eye indicator, 3 push-button controls, on/off. Med., VHF. Diodes and high output sockets with gain control. Illuminated 2-colour perspex dial 1 1/2 in. x 4 in. chassis size 1 1/2 in. x 4 in. x 5 1/2 in. A recommended Fidelity Unit for use with Mullard "3-3" or "5-10" Amplifiers. Bargain Price. Complete kit of parts, inc. Power Pack as illustrated. 11 Gns. Carr. 7/6. Ditto less Power Pack 10 Gns. Carr. 7/6. Circuit and Const. details, 4/6. Free with kit.



29 gns TAPE RECORDER


for ONLY £21 Carriage 12/6
3 speed twin track 3 watts
Bargain of the Year Offer—
Cancelled Export Contract

Famous manufacturer's brand new, unused and factory tested 3 speed 1 1/2, 3 1/2, 7 1/2 twin track tape recorder. 3 Watt output. Tape position rev-counter, fast forward and rewind, takes 7 in. reels, mike and gram input. Straight through amplifier facilities. Output sockets for ext. speaker, monitor or external amplifier. Super-imposed switching, magic eye recording level and mains neon indicators. Volume and tone controls 7 in. x 4 in. speaker. Attractively styled cabinet, with detachable lid, mike and reel storage facilities. A.C. 200/250 volts operation. Complete with crystal mike tape, spare reel and screen lead, etc.



MULLARD "3-3" & "5-10" HI-FI AMPLIFIERS

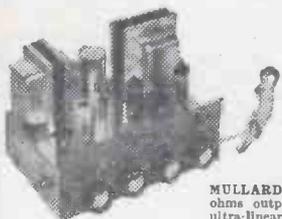3 ohm & 15 ohm output
"3-3" Amp. 3 valve, 3 watt hi-fi quality at reasonable cost. Bass Boost and treble controls quality sectional output transformer, 40 c/s-25 kc/s +1 db, 100 mV for 3W, less than 1% distortion. Bronze escutcheon panel. Complete Kit only £7/10/-. Carr. 7/6. Wired and tested £9/10/-.



"5-12" AMPLIFIER. 3 valves 10W 3 and 15 ohms output. Mullard's famous circuit with heavy duty ultra-linear quality output transformer.

Basic amplifier kit price £9.19.6 Carr. and Ins. 7/6. Ready built 11 1/2 gns.

CONTROL PANEL KIT. Bass, Treble and Volume controls with 4-position selector switch for radio tape and 1 1/2 in. x 4 in. escutcheon panel.

AMPLIFIER KIT AND CONTROL PANEL KIT, £11/19/6. Ditto, ready wired, £14/19/6. Carr. 7/6.

2-VALVE PRE-AMP UNIT. (For use with basic amplifier only). Based on Mullard's famous 2-valve (2x6F96) circuit with full equalisation, with volume, bass, treble and 5-position selector switch. Size 9 x 6 x 2 1/2 in. Complete Kit £6/12/6. Carr. 5/6. Ready-built £8/10/-, Carr. 5/6.

RECORDING TAPE—Reduced Prices

Famous American Columbia (CBS) Premier Quality Tape at REDUCED PRICES. A genuine recommended Quality Tape—TRY IT! Brand new, boxed and fully guaranteed. Fitted with leader and stop foils.

	Standard	Long Play	Double Play
5in.	800ft. 13/-	900ft. 17/6	1,200ft. 31/6
5 1/2 in.	900ft. 16/-	1,200ft. 19/6	1,800ft. 37/6
7in.	1,200ft. 21/-	1,800ft. 28/6	2,400ft. 47/6

P. & P. per reel 1/-, 6d. on each additional reel

SPECIAL BARGAIN. 3in. Message Tape, 150ft. 3/6. P. & P. 6d. 3in. L.P. 225ft. 4/6. 5in. D.P. 300ft. 6/6.

Plastic Tape Reels, 3in. 1/3; 4in. 2/-; 5in. 2/-; 5 1/2 in. 2/-; 7in. 2/3.

Plastic Reel Containers, Cassettes 5in., 1/6; 5 1/2 in. 2/-; 7in. 2/3.

T.R.S. STEREO DECODER KIT

Based on a Mullard design.

6 Transistors, Printed Circuit size 5 1/2 in. x 2 1/2 in. 2 stage transistor. Stereo Beacon Indicator incorporated. 12v. supply. Neg. Earth.

Basic Kit supplied suitable for Transistor Tuner input and Transistor Amplifier output. With simple mods (data supplied with Kit) easily adapted for Valve Tuners and Valve Amplifiers. Kit and assembly instructions complete with Mullard specified Inductors Type WF2949 and WF2951. Bargain £4/19/6.

SINCLAIR KITS

We are Specialists, and carry full stocks of these world-famous all-British designs as advertised and give prompt delivery.

- MICRO-6 6ix stage rest-pocket revr. (kit) 59/6
- MICRO-FM 7 transistor FM tuner-revr. (kit) 25/19/6
- Z12 combined 12 w.amp and pre-amp. built 89/6
- STEREO 25 de luxe pre-amp/control unit ready built 29/19/6

GOERLER CONTINENTAL STEREO DECODER

A ready built and aligned factory Unit 6 transistor plus 5 diodes designed to connoisseur standards. Size 4 1/2 in. x 3 1/2 in. ready for connecting to existing transistor tuner. Multiplex O/P. 12v-18v. supply. Full technical specification details S.A.E. Price £9/10/-, plus 3/6 carr.

JASON F.M. TUNER UNITS

Designer-approved kits available.
FMT1 5 gns., 4 valves 20/-.
FMT2 £7/10/-. 5 valves 35/-.
JT Mercury 10 Gns. 3 valves 22/6.
JTVE £13/19/6. 4 valves 29/6.
NEW JASON F.M. HANDBOOK 2/6.
Prompt Allignment Service, 10/-, plus 2/6.

TYGAN FRET or Vynalr spkr. fabric, 12 x 12 in. 2/-; 12 x 18 in. 3/-; 12 x 24 in. 4/-, etc.
BONDACOUST Speaker Cabinet Acoustic Wadding, approx. 3 in. thick, 18 in. wide, any length cut 2/3 ft. 6/- yd. EXPANDED ANODIZED METAL. Attractive gilt finish 1/2 x 1/2 in. diamond mesh 4/6 sq. ft. Multiples of 6 in. cut. Max size 4ft. x 3ft. 47/6 plus carr.

COAX 80 OHM CABLE

High grade low loss Cellular air spaced Polythene—1 in. diameter, stranded cond. Famous mfrs. Only 6d. yd.
Bargain Prices—Special lengths:
20 yds. 9/- P. & P. 1/6.
40 yds. 17/6 P. & P. 2/-.
60 yds. 25/- P. & P. 3/-.
Coax Plug 1/3 Sockets 1/6
Couplers 1/3 Outlet Boxes 4/6

Volume Controls—5K-2 Meg. ohms. 3 in. Spindles. Morganite Midget Type 1 1/2 in. diam. Quar. 1 year. LOG or LIN. ratios less Sw. 3/6 DP. 8w. 5/-. Twin Stereo less Sw. 7/6 100k to 2M ohms with DP Sw. 9/6.
STEREO BALANCE CONTROLS. Log/Anti-LOG 5K. 1/2, 1 or 2 Meg. 9/- ea.
WAVECHANGE SWITCHES. 1 p. 12-way, 2p. 2-way, 2 p. 6-way, 3 p. 4-way, 4 p. 2-way, 4 p. 3-way, long spindle, 3/6 ea.

DE-LUXE RECORD PLAYER KIT

Incorporating 4 Sp. Garrard Auto-Slim unit and Mullard latest 3-watt printed circuit amplifier (ECL86 and EZ80), vol., bass and treble controls, with 8 x 5 in. 10,000 line speaker. Contemporary styled two-tone cabinet, charcoal grey and off-white with matching blue relief. Size 17 1/2 in. x 16 in. x 8 in. A stylish unit capable of quality reproduction. (Circuit, and const details 2/6 (free with kit).




COMPLETE KIT £13.19.6
Carr. and ins. 12/6.
Ready wired 30/- extra

Illuminated Perspex control panel escutcheon 7/6 extra. 4 contemporary mounting legs, 6 in., 10/6; 9 in., 11/6; 12 in., 12/6 per set extra.

7 VALVE AM/FM RADIOGRAM CHASSIS

Valve line-up ECC85, ECH81, EF89, EABC80, EL84, EM81, EZ80.
Three Waveband and Switched Gram. positions. Med. 200-550 m Long 1,000-2,000 m. VHF/FM 88-95 Mc/s. Phillips Continental Tuning Insert with permeability tuning on FM and combined AM/FM IF transformers. 400 Kc/s and 10.7 Mc/s. Dust core tuning all coils. Latest circuitry including AVC and Neg. Feedback. Three watt output. Sensitivity and reproduction of a very high standard. Chassis size 1 1/2 x 6 1/2 in. Height 7 1/2 in. Edge illuminated glass dial 1 1/2 x 3 1/2 in. Vertical pointer. Horizontal station names. Gold on brown background. A.C. 200/250v. operation. Magic-eye tuning. Circuit diagram now available. Aligned and tested ready for use £13/19/6. Carr. & Ins. 8/6. Comp. with Tape output, ext. spkr and P/U sockets and indoor F.M. aerial and 4 knob—walnut or Ivory to choice. 3 P.M. Speaker only required. Recommended Speakers 10 in. E.A. 30/- 13 1/2 x 8 in. E.M.I. Fidelity 42/6. 12 in. R.A. with conc. Tweeter, 42/6. Carr. 2/6.

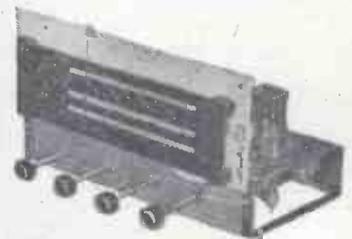

Condensers—8/Mica. 2pF to 1,000pF. 6d. each. Ditto Ceramics or Polyesters 9d. Tub. 450 v. T.C.C. etc. 0.001mFd to 0.01 and 0.1/350v., 10d. 0.02-0.1/500v. 1/- 0-25 Hants 1/8. 0.5 T.C.C. 2/-, etc., etc. Close Tol. S/Micas—10¢ 5pF. 6d. 600-5,000pF. 1/- 1% 2pF-100pF. 11d. 100pF-250pF. 1/2d. 270-800pF. 1/4d. Resistors—Full Range 10 ohms-10 meg. ohms. 20% 1/2 and 1/4 W. 3d., 1/2 W. 5d. 1W. 6d. 2W. 9d. 10% 1/2 and 1/4 W. 4d. 50% Hi-Stab, all values 1/2 W. 5d. ea. 5% 1/2 W. ditto 6d. 1% 1/4 W. 1/6d. ea.

Elect. Condensers—Midget type 1 mFd. 50 mFd. ea. 1/9. 100 mFd. 2/-, 15 v. Wkg. Condensers 150v. working: .01 mFd. .02 mFd., .03 mFd., .04 mFd. 10d.; .05 mFd., .1 mFd. 1/-; .25 mFd., 1/3; .5 mFd., 1/6. etc.

TUB-ELECTROLYTIC-CAN
25/25 v. 50/12 v. 1/9; 8+8/450 v., 4/6; 50/50 v., 100/125 v., 2/-; 32+32/275 v., 4/6; 8/450 v., 4/300 v. 2/3; 50/50/350 v., 6/8. 16+16/450 v., 5/6; 60/250/275 v., 12/6; 32+32/450 v., 6/6; 100+200/275 v., 12/6, etc. etc.

Terms: C.W.O. or C.O.D. post and packing 1/2 lb. 1/-, 1 lb. 1/9, 3 lb. 3/-, 5 lb. 3/9, 8 lb. 4/6, etc.



T.R.S. RADIO (COMPONENT SPECIALIST) EST. 1946

70 BRIGSTOCK ROAD, THORNTON HEATH SURREY

Tel.: THO 2188; Hours 9 a.m.—6 p.m. 1 p.m. Wednesdays.

Only a few items are listed from our comprehensive stock. Write now for full bargain lists, 3d.

BARGAIN COLUMN

25 AMP. ON/OFF SWITCH. Mains heavy duty type rotary with control knob, 5/6 each.

MAINS TRANSFORMER. Upright mounting with primary tapped 200, 220, 240 v. H.T. secondary is 250.0-250 v. at 100 ma. and it has two L.T. equipments of 6.3 v. 1 amp.—unused (removed from second equipment), 15/-, plus 3/6 post and insurance.

HI-FI SPEAKER BARGAIN

12in. High fidelity loudspeaker. High flux permanent magnet type with either 3 or 15 ohm speech coil. Will handle up to 10 watts. Brand new by famous maker. Price 29/6, with built-in tweeter 35/-, plus 3/6 post and insurance.




SPOT OR FOG LAMP

Made by Lucas. Flat or Pencil beam, 36 watt. Suitable for car, boat, caravan, etc. Complete with 6 or 12 v. bulb, flex, cables and fixing bolt. Remarkable bargain, 12/6, plus 4/6 post and ins.



LUMINOUS CORD SWITCH

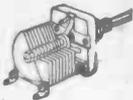This can hang on the end of a flex or it can be inserted into a flex. It has a built-in neon which makes it luminous in the dark. Made for electric blankets but ideal in darkrooms, etc. Normally 10/6. Our price 6/6 each, or £3 doz.



FINE TUNERS

50 pf with long spindle, as illustrated, 1/6, or 12/- doz. Twin 50 pf., not quite such a long spindle, 2/6, or 24/- doz.

12v. INVERTER

Fully transistorised for operating a 20-watt fluorescent tube or other 20-watt mains device. Size 6ft. long by 1 1/2 by 1 1/2. £3/10/-. Post and ins. 3/-.

THOUSANDS OF TRANSISTORS at CUT prices

(e.g.: Silicon N.P.N. 5/-) Bend 1/6 for latest List and equivalent chart, and circuits. S.E.R. (Transistors) 100 v. 1 amp. 6/6, 3 amp. 7/6, 12 amp. 15/-, 400 v. 1 amp. 15/-, 3 amp. 17/6, 5 amp. 22/6, 25 amp. £3. 50 v. 1 amp. 6/6, 3 amp. 7/6, 10 amp. 10/-, 25 amp. 30/-.

DON'T MISS THIS it will save you £100. 9 v. Nickel Cadmium Battery type PP3 (fits all popular pocket transistors). Can be recharged 800 times. Price with transformer type battery charger, only 52/6. P. & Ins. 3/-. Chargeable replacements also in stock for U7 12/6, U11 23/-, U12 32/-.



NO SOLDERING POCKET 3

Lots of fun to build and good results when finished—complete kit with detailed instructions and crystal earpiece—batteries 1/2 extra. £5 value. Only 18/6, plus 3/- post and insurance.



MISCELLANEOUS BARGAINS

5-amp. Car Battery Charger Rectifier, 10/6, post 3/6. Reed Switch with Magnet, 6/6. 1 Meg. Pots, 6/- doz., ditto with d.p. sw. 10/- doz. Silicon Best. EY100, 350 v., 250 ma., 4/6 ea. 3 for 12/-, Miniature Pick-up with Cosmocond crystal cartridge and sapphire stylus, 3/6. 4-Transistor Audio Amplifier, 19/6. Turret Tuner, lens bottom cover and valves, 7/6 each. Neons (Midget), 1/6 each: valve type, 10/6 doz. Slide Switch (Miniature), 1/6; mains type, 2/-, Toggle Switch, 2/3. 30-amp. Relay for controlling heating, 39/6. 80 watt Fluorescent Kit, 17/6, post 3/6. 4-pole Change-over Switch for series parallel working, 4/6.

Where postage is not definitely stated as an extra then orders over £3 are post free. Below £3 add 3/6.

INFRA-RED HEATERS

Make up one of these latest type heaters. Ideal for bathroom, etc. They are simple to make from our easy-to-follow Instructions—use silica enclosed elements designed for the correct infra-red wavelength (3 microns). Price for 750 watts element, all parts, metal casing as illustrated, 21/6, plus 4/6 post and ins. Pull switch 3/- extra.



MULTI-MAINS BOX



These are 4 x 16 amp. sockets mounted on a metal box all ready for wiring to your power plug—intended for mounting on bench or wall—for use in workshops—laboratories—exhibitions—displays, etc. They avoid the use of dangerous bakelite multiplugs and adaptors and other hook-ups. Price only 19/6, plus 5/- post and ins.

SQUARE D ADJUSTABLE TIMER

This is a fine American made unit designed for precision. The time period is adjusted by a knurled screw. The delay period can be set anywhere from hours or seconds. The end of the delay operates a microswitch—and resetting can be remote controlled or manually reset. The unit is for wall mounting and is approx. 4 x 7 x 4in. Price 39/6, plus 3/6.

FINE RECORD PLAYERS ARE 'GARRARDS'



and because they have been making record players for so long, GARRARD are your best choice—big range always in stock.

1000	25	5	0	LAB80	225	0	0
2000	26	8	6	SRP12	23	8	6
3000	27	19	6					
AT50	211	11	0					
SP25	210	9	0					

7/6 for post and ins.

Complete with service sheet and template.

—THIS MONTH'S SNIP—

ELECTRIC BLANKET OUTFIT

A 13 yard, 70 watt waterproof element with temperature control by Thermal balance—and a double pole blanket switch in pastel blue bakelite—with enclosed neon ON/OFF indication—both items ideal for renovating a defunct or doubtful blanket—supplied complete with layout and other instructions. Only 12/6, plus 1/6 post and ins.

FLUORESCENT SNIP

Your opportunity to instal non-flicker strip lighting at silly price—this month we offer the famous A.E.I. (Mazda) instant start lighting transformer suitable for one 4ft. 40 watt tube or two 2ft. 20 watt tubes. This transformer is listed at over £7, but this month you can buy the complete kit comprising instant start choke/transformer, two tube ends and two Terry clips to hold tube. Special snip price only 14/6, plus 3/9 post and ins.—don't miss this tremendous bargain.

See in the Dark


INFRA-RED BINOCULARS

These infra-red from a high voltage source will enable objects to be seen in the dark, providing the objects are in the rays of an infra-red beam. Each eye tube contains a complete optical lens system as well as the infra-red cell. These optical systems can be used as lenses for T.V. cameras—light cells, etc. (details supplied). The binoculars form part of the Army night driving (Tabby) equipment. They are unused and believed to be in good working order, but sold without a guarantee. Price £2/17/6, plus 10/- carr. and ins. Handbook 2/6.



FIELD TELEPHONE UNIT

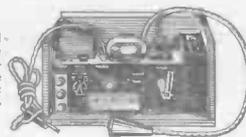Officially known as remote control units No. 1, essentially these are telephones with additional facilities—each unit contains magneto type ringer and bell—as well as transformer—relay and switches. A pair of these will give you two-way communication over distances up to five miles—unused and in good condition, 39/6 each, plus 10/6 carr. and ins.



MAINS/TRANSISTOR POWER PACK

Mains Power Pack designed to operate transistor sets and amplifiers. Adjustable output 6 v.-9 to 12 v. for up to 500 mA. (class B working). Takes the place of any of the following batteries: PP1, PP3, PP4, PP6, PP7, PP9, and others. Kit comprises mains transformer-rectifier, smoothing and load resistor, 5,000 and 500 mfd. condenser. Zener diode and instructions. Real snip at only 14/6, plus 3/- post.

SELF REPAIRING FUSES

Sounds good doesn't it—we can't offer quite that but we can offer a fast acting overload trip which will save you having to repair fuses every time you do something which would normally blow a fuse. The trip works first and as you would install this on or near your bench, all you do is to switch on again. This is made by Westinghouse. Regular price about £10 each. We offer them this month at 29/6, plus 6/- post and ins. Not many in stock, so hurry or you will be too late.

CONSTRUCTORS' COLUMN

NIM COMPUTER



This computer will play games and do simple tricks and will provide endless amusement as well as education into computerisation. Kit comprises all the components, the printed front panel and full instructions. The box is not included but this can be made very simply from plywood. Price £4/17/6, plus 3/6 post and ins.

SIMPLE RECEIVER FOR LOW VOLTAGE. A TRF transistor set powered from the Sun or a 1 1/2 v. cell. Suitable for children or others who forget to switch off. 4 N.P.N. silicon transistor, diode and all other components necessary to build this circuit described in "Wireless World," Oct., are available as a kit. Price 30/-, plus 2/6 post and ins.

ELECTRONIC CONTROL OF MODEL LOCOMOTIVES. A device to overcome jerky stopping and starting is described in "Wireless World," Oct. All components, including 5 transistors, 4 diodes, mains transformer, etc., to build this circuit is available as a kit. Price £4, plus post and ins. 2/6.


NOUGHTS AND CROSSES MACHINE. This machine, described in Sept. '65, is impossible to beat and will provide endless fun at home and considerable attraction (and profit) at charity do's and fetes, etc. It employs 13 switches and 9 bulbs and these and the other components necessary to make this are available. Price £4/10/-, post and ins. 3/6.

Multi Purpose Neon Test Unit

Robust, useful and instructive—tests insulation—capacity—continuity—resistor—volume controls—also acts as signal injector and L.T. fault finder—kit comprises neon indicator—4-way wafer switch—ebonite tubes—resistors—condensers—terminals etc. with diagram only 9/6, plus 2/- post and ins.

STUPENDOUS OFFER—£11 for £2

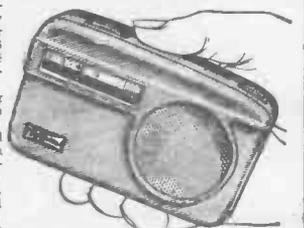Only recently sold for £10/19/6. Not to be missed—these features: Long & Medium Wave • Long dial • Push pull output • A.V.C. and feed back • Ferrite aerial • Six transistors • Cabinet size 4 1/2 x 3 x 1 1/2 in. with carrying strap. You get everything you need and instructions. 39/6, plus 3/6 P. & P., or supplied with made-up chassis 10/- extra. Battery 1/8 extra. Data separately 2/6.



ENGINE REV. COUNTER

Employing a special frequency discriminator the instrument is just right for many of the jobs you have wanted to do—it can be permanently installed as a rev. counter or as a portable instrument it will do such jobs as measuring frequency of time base—pulse generator—flip-flop etc., etc. Kit comprises: metal front panel all prepared and stove enamelled, moving coils meter, 4 specially tested transistor and diodes and all the necessary resistors and condensers and circuit diagram (separately 2/6) all for 49/6, plus 2/6 post and ins.

OZONE OUTFIT—for removing smells and generally improving any oppressive atmosphere. Kit consists of Phillips Ozone Lamp and mains unit, only needs box, 19/6, plus 6/6 carr. and ins.

SOLID STATE IGNITION. Big things are claimed of Electronic ignition systems and if you would like to try for yourself a circuit was described in "Practical Electronics" (Sept., 1966). This requires a silicon controlled rectifier, four transistors and other components available as a kit. Price £5/10/-, post free.

RAIN SENSER. Here's a simple unit that will help your wife. Rings a bell or flashes when it rains. All the components and data, 39/6, post 2/6.

S.G.R. LIGHT DIMMER. Can also be used to control the speed of motors, drills and the heat from or to critical instruments. Circuit recently described in "Practical Electronics." Mains operation, this unit fits into 13 amp. socket outlet box. All the components including the silicon controlled rectifier. Available as a kit. Price £4/10/-, plus 3/6 post & ins.



Be first this year SEED AND PLANT RAISING


Soil heating wire and transformer. Suitable for standard size garden frame. 19/6, plus 3/6 post and ins.

ELECTRONICS (CROYDON) LIMITED

102/3 TAMWORTH ROAD, CROYDON, SURREY (Opp. West Croydon Station)

THIS IS VSMF

VISUAL SEARCH MICROFILM FILE

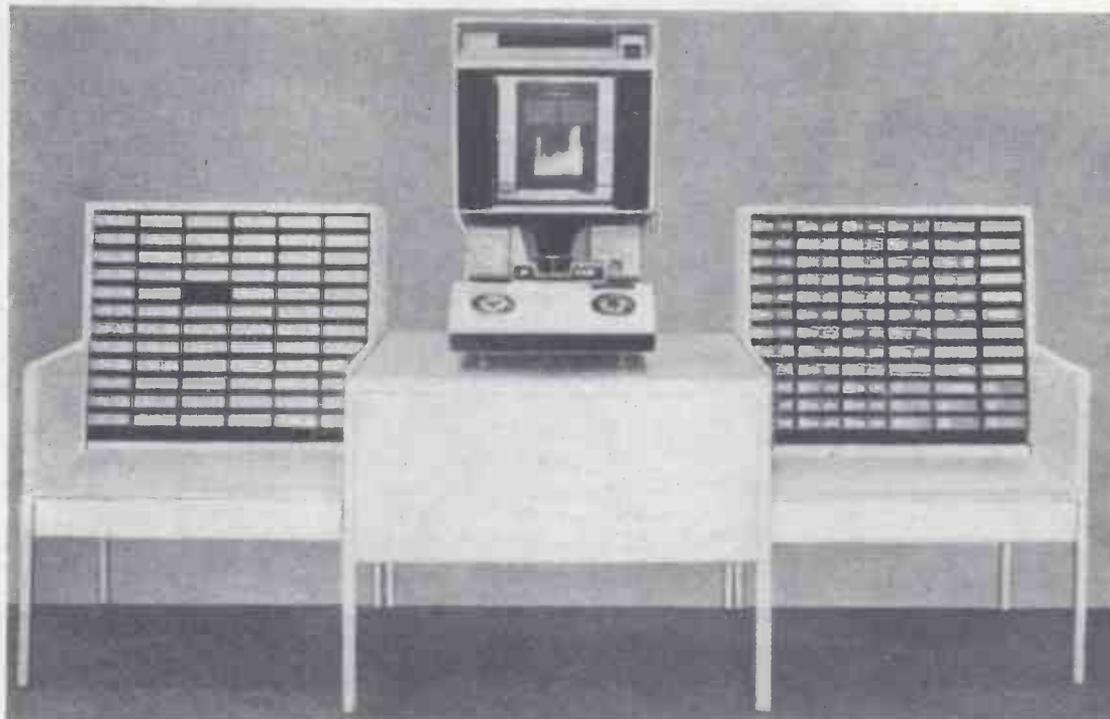

This VSMF installation contains over 300,000 pages of fully-indexed data.

VSMF IS INTERNATIONAL

Established 6 years in USA—now being produced in Britain and Japan—soon to be produced in Europe.

VSMF IS EFFECTIVE

Average saving per installation in USA exceeds \$23,000 per annum, eliminates lost or misfiled data, always up-to-date.

VSMF IS COMPACT

Only 12 sq. ft. of floor space to store 300,000 pages of data.

VSMF IS UNIQUE

Copyright indexing method ensures rapid access to any item.

VSMF is now being produced in Britain by Information Handling Ltd. —a joint subsidiary of the two technical publishing divisions of the International Publishing Corporation—The National Trade Press Ltd. and Kelly-Jiffie Ltd. The system is in widespread use throughout the USA and has stood the test of six years' service in critical conditions in defence plants.

The first British file will contain indexed catalogue data on products used in the Electronic, Electrical and Mechanical Engineering Industries. If you manufacture such products VSMF offers an efficient and inexpensive means of placing your data before specifiers. If you use such products then VSMF can improve your information facilities and cut design costs.

VSMF is now being produced in Britain by Information Handling Ltd., 161/166 Fleet St., E.C.4. Telephone: Fleet Street 5011.

Please send information on how product data can be inserted into VSMF

Please send information on the use of VSMF in industry..

NAME..... POSITION.....

COMPANY

ADDRESS

Mail to Information Handling Ltd., 161/166 Fleet St., London, E.C.4.

WW-146 FOR FURTHER DETAILS.

**Hi-Q
LOW LOSS
PRECISION
LIGHT-WEIGHT
AIR-WOUND**



Freq M/cs 5.0
"Q" 290

INTRODUCING our new series of precision, air spaced inductors, available in diameters from $\frac{3}{4}$ " to 3" and a wide range of inductances.

CODAR-COILS

are the only complete range of air-spaced precision inductors available today on short delivery. Specials to specification can be supplied and prototype samples are available to designers.

Brochure giving data of types/inductance capacity-frequency on request.



CODAR RADIO CO.
Bank House · Southwick Square
Southwick · Sussex
phone · Southwick 3149

WW-147 FOR FURTHER DETAILS.



**NO
WAITING**

**FOR THIS SUPERB
300VA SINE WAVE**

**TRANSIPACK[®]
STATIC INVERTER
with THYRISTOR Control System**

AVAILABLE FOR IMMEDIATE DELIVERY

PRICE £169

606/ST/300

24v DC Input / 240v AC Output / 50 c/s
De-Luxe, 2-Colour, Transportable case



**INDUSTRIAL
INSTRUMENTS
LIMITED**

STANLEY ROAD · BROMLEY · KENT
Telephone: RAVensbourne 9212/3.

Telegraphic Address: TRANSIPACK BROMLEY

PLEASE SEND

● Full specification of TRANSIPACK 606/ST

● ... TRANSIPACK 606/ST at £169 ea

Remittance enclosed £.....

NAME


ADDRESS

W.W.

WW-148 FOR FURTHER DETAILS.

BRAND NEW AM/FM (V.H.F.) RADIOGRAM CHASSIS AT £15.15.0 (CARRIAGE PAID)

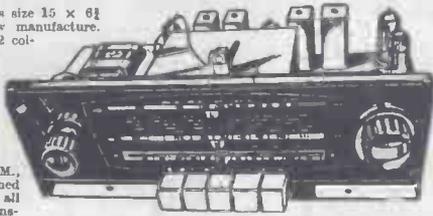A.C. ONLY. Chassis size 15 x 6 1/2 x 5 1/2 in. high. New manufacture. Dial 1 1/4 x 4 in. in 2 colours, predominantly cream. Pick-up. Extension Speaker, Ac. E., and Dipole Sockets, Five "piano" push buttons — L.W.,



M.W., S.W., F.M., and Gram. Aligned and tested. With all valves and O.P. Transformer. Tone Control fitted. Covers 1,000-1,900 M; 200-550 M; 88-98 Mc/s; 6-17 Mc/s. Valves EZ80 rect., ECH81, EF89, EABC80, EL84, ECC85. ELLIPTICAL SPEAKERS 10in. x 6in. 25/-, 13in. x 8in. 35/-, to purchasers of this chassis. Carr. to N. Ireland 20/- extra.

TERMS: £5/5/- down and 5 monthly payments of £2/5/-. Total £16/10/-.

NEW 6 PUSHBUTTON STEREOGRAM CHASSIS

M.W., S.W., S.W.2, V.H.F., Gram., Stereo Gram. Two separate channels for Stereo Gram, with balance control. Also operates with two speakers on Radio. Chassis size 15in. x 7in. x 6 1/2 in. high. Dial cream and red 15in. x 3in. Valves ECC85, ECH81, EF89, 2 x ECL86, EM84 and Rect. 190-550 M; 18-51 M; 60-187 M; 86-100 Mc/s. Price £19/19/- carr. paid, or £6/13/- deposit and 5 monthly payments of £2/16/6. Total H.P. price £20/15/6. Cream moulded escutcheon included. Carriage to N. Ireland 20/- extra.

TAPE AMPLIFIER FOR MAGNAVOX TAPE DECKS —2 or 4 TRACK (4 TRACK 25/- EXTRA)

Chassis 12 1/2 x 5 1/2 x 4 1/2 in. high. Plastic front panel "gold" finish—12 1/2 x 4 1/2 in. 200-250 A.C. Record/Playback amp. switch; Off/On-Tone; Vol/Mic; Vol/Gram; Mic. Input; Gram. Input; Monitor; Speaker Sockets. Valves 6BR7; 12AX7; EM84; EL84; 6X4. Separate power pack. Complete amp. and power pack. £10/17/6 (6/- P. & P.).

REXINE COVERED CABINET (TAN). 15 1/2 in. x 17 in. x 9 1/2 in. high with sloping front for amp. Complete with two tweeter speakers, special adapting brackets for Magnavox Deck. 35/- (8/- carr.).

3-SPEED MAGNAVOX 2-TRACK TAPE DECK £10/17/6; 4 Track £12/15/-. Complete Recorders (with speed compensation), 2-Track £29, 4-Track £32 (carr. 25/-). Worth £10 more, on normal retail prices.

Send 6d. for 20-page illustrated catalogue.

Bulk enquiries invited for Export.

GLADSTONE RADIO

66 ELMS ROAD, ALDERSHOT, HANTS. Aldershot 22240. (1 min. from station and buses.) Closed Wednesday afternoon.

VALVES SAME DAY SERVICE NEW! TESTED! GUARANTEED!


SETS 1R5, 1R5, 1T4, 3V4, DAF91, DF91, DK91, DL92, DL94. Set of 4 for 16/-. DAF96, DF96, DK96, DL96, 4 for 24/6.

1A7GT 7/6	9BW6 6/6	DH76 3/6	EF91 3/6	PEN383 9/6	UCH81 6/6
1H5GT 7/3	10C2 11/6	DH77 4/-	EF92 2/3	PFL20014/6	UCL82 7/3
1N6GT 7/9	10F1 9/9	DH81 12/6	EF97 7/6	PL36 9/6	UCL83 9/6
1B5 4/9	10P13 8/6	DK32 7/9	EF183 6/9	EL31 9/9	UF41 8/-
1B4 4/9	12AT7 3/9	DK41 6/9	EF184 6/9	PL82 6/6	UF80 6/3
1B5 3/9	12AU6 4/9	DK92 8/-	EL35 6/6	PL83 6/-	UF89 5/9
1T4 2/9	12AU7 4/9	DK96 6/6	EL38 11/9	PL84 6/3	UL41 8/9
3A5 7/-	12AX7 4/9	DL33 6/9	EL41 8/6	PL500 14/-	UL44 15/-
3Q4 5/6	12K7GT 3/6	DL35 5/-	EL42 7/9	PL801 7/6	UL54 5/9
3B4 4/9	12K8GT 3/6	DL92 4/9	EL84 4/9	PL25 7/9	UY21 8/9
3V4 5/6	12Q7GT 3/6	DL94 5/6	EL90 4/9	PL31 6/6	UY41 6/9
5U4G 4/6	20F2 9/-	DL96 6/-	EL95 5/-	PY32 9/-	UY85 4/9
5Y3GT 4/11	20L1 14/0	DY86 6/9	EM80 5/9	PY33 9/-	VP4B 11/-
5Z4G 6/9	20P1 9/-	DY87 6/9	EM81 7/3	PY80 5/3	W76 3/6
6Y30L2 9/6	20P3 9/-	EABC80 6/-	EM84 5/9	PY81 5/3	W77 2/6
6AL5 2/3	20P4 13/6	EAP43 7/6	EM87 6/6	PY82 5/-	Z77 3/6
6AM6 3/6	26U4OT11/6	EB41 4/-	EY61 6/3	PY83 5/9	
6AQ6 4/9	30C15 9/3	EB91 2/3	EY86 6/-	PY800 6/6	Transistors
6AT6 4/-	30C18 8/-	EBC33 6/6	EZ40 6/3	PY801 6/6	AC107 13/6
6BA6 4/6	30P5 7/3	EB41 7/9	EZ80 3/9	EL9 7/-	AC127 9/6
6BE6 4/3	30PL1 10/6	EBF80 6/-	EZ81 4/-	R20 15/9	AD140 15/6
6BJ6 5/6	30L15 11/-	EBF89 5/9	KT61 6/6	TH21C 9/6	AF102 18/-
6BW6 7/3	30L17 12/-	ECC81 3/9	KT63 4/-	U25 9/-	AF115 6/9
6F1 7/9	30P4 13/6	ECC82 4/9	N18 5/6	U26 8/9	AF116 6/9
6F13 3/6	30P12 9/-	ECC83 7/-	N78 14/9	U47 8/6	AF117 5/-
6F14 9/-	30P19 13/6	ECC84 6/3	PC97 6/9	U49 9/6	AF118 16/6
6F23 9/9	30PL1 11/-	ECC85 5/6	PC84 5/6	U52 4/6	AF124 9/6
6K7G 1/6	30PL13 11/9	ECP80 7/6	PCC89 9/9	U78 3/6	AF125 9/6
6K8G 4/3	35L6GT 6/3	ECP82 6/9	PCC189 9/-	U191 10/6	AF126 8/6
6K9GT 7/6	35W4 4/6	ECP86 9/-	PCF80 6/6	U301 11/6	AF127 8/6
6L16 7/6	35Z4GT 4/6	ECP85 6/9	PCF82 6/9	U901 15/9	OC22 17/6
6O7G 5/6	85A4 5/9	ECH42 9/-	PCF86 8/3	UA8C90 5/9	OC25 10/-
6Q7GT 7/6	6063 12/6	ECH81 5/9	PCF800 10/6	UAF42 7/9	OC26 6/9
6V6G 3/6	AZ31 8/9	ECH84 8/6	PCF801 9/6	UBC41 6/9	OC44 4/3
6V6GT 5/6	B35 4/6	ECL80 6/-	PCF805 8/-	UBF80 6/-	OC45 3/3
6X4 3/6	B759 10/-	ECL82 6/9	PCL82 6/9	UBF89 5/9	OC71 3/6
6XGT 6/3	DAC39 7/3	ECL85 7/9	PCL83 9/-	UBL21 9/-	OC72 4/9
7B6 10/6	DAF91 3/9	EF39 3/9	PCL84 7/6	UC92 5/6	OC75 5/9
7B7 7/9	DAF96 6/-	EF41 6/3	PCL85 8/3	UC86 6/6	OC81 3/6
7C5 8/9	DCC90 7/-	EF80 4/9	PCL86 8/4	UCF80 8/3	OC81D 3/6
7C6 6/9	DF33 7/9	EF85 5/-	PEN44 6/6	UCH21 9/3	OC82 5/9
7H7 5/-	DF91 2/9	EF86 6/9	PEN36CL5/-	UCH42 8/9	OC82D 5/9
7Y4 5/-	DF96 6/-	EF89 5/-			OC170 7/6

READERS RADIO

85 Torquay Gardens, Redbridge, Ilford, Essex. CRE 7441

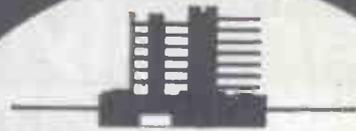
Postage on 1 valve 9d. extra. On 2 valves or more, postage 6d. per valve extra. Any Parcel Insured against Damage In Transit 6d. extra.



AIR DIELECTRIC TRIMMERS




P.T.F.E. TRIMMERS

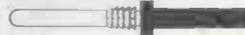

PRINTED CIRCUIT PINS 'SNAILE' TYPE




'BARB' PLUGS & SOCKETS

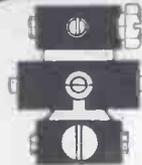

MINIATURE COUPLINGS



MULTIPLE TAG INSULATORS

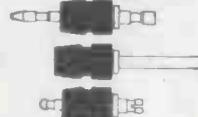

'BARB' INSULATORS

Longlasting Precision...

OXLEY

DEVELOPMENTS COMPANY LIMITED

ULVERSTON
LANCASHIRE, ENGLAND
TELEPHONE: ULVERSTON 2567
CABLES: OXLEY ULVERSTON



WW-149 FOR FURTHER DETAILS.

stern-clyne ELECTRONIC CENTRES



MERCURY BRILLIANT *NEW* MODULAR HI-FI STEREO

With Garrard Autochanger, Solid State Amplifier, Free-Cone Speaker Systems
The Stern-Clyne Mercury is an important new approach to Hi-Fi sound reproduction in the home. One compact, modular system embodies the latest advances in solid-state amplifier design, loudspeaker system miniaturization, and pick-up cartridge development to provide superb stereo performance with exceptional installation facility. Combined Player Unit/Amplifier Console and identical speaker systems are superbly housed in matching teak veneer cabinets, specially designed to fit existing furniture or shelf space, and match any décor.

MERCURY SYSTEM

AUTOCHANGER AND PICK-UP
Garrard High-grade. Model 3000, specially equipped with high-compliance, ceramic cartridge fitted with Diamond stylus to ensure superb, wide range reproduction and extremely low tracking weight.

AMPLIFIERS
Identical, 5-watt, 7-transistor amplifiers designed round the latest, fully-proved semi-conductors. Each is independently constructed on a modular circuit board and subjected to searching inspection and precise matching at each stage of assembly.

LOUDSPEAKER SYSTEMS
Bookshelf size, acoustically designed speaker system enclosures contain bass speakers and matching high frequency units with crossover network. Specially developed bass speaker employs enormously powerful magnet and free suspension cone to provide the full bodied bass response usually associated with much larger units.

SPECIFICATION

Power Supply 200/250 volts, 50 cycles A.C. (other standards to special order).
Output (Amplifiers) 5 watts per channel.
Output Impedance 15 ohms (other speakers of 8 to 16 ohms may be used).
Frequency Response (Amplifiers) 30 c/s. to 35 kc/s. flat (2 dB) at 1 watt, tone controls level.
Harmonic Distortion Less than 1%.

Hum and Noise -55 dB below full output, tone controls level.
Cross talk between channels 48 dB at 1 kc/s.
Bass Compensation ±15 dB at 40 c/s.
Treble Compensation ±15 dB at 14 kc/s.

Balance Control Ganged potentiometer; either channel can be faded to zero without affecting the other.
Tape Record Outputs 200 mV average, each channel.
Dimensions: Player Unit 16½ x 14 x 8½ in. overall.
Loudspeakers 13 x 7 x 8 in. (each).

49 GNS.
COMPLETE
Carr. and ins. **15/-**

ONLY FROM STERN-CLYNE

only from Stern-Clyne The Unique GRAMSTAND



£10.76
Carriage 10/-

GRAMSTAND is a superb BSR Autochanger—with many added facilities—already assembled on a handsome, especially designed hardwood plinth.

GRAMSTAND is made exclusively for Stern-Clyne to meet the requirements of modern bookshelf mounted and space limited Hi-Fi systems.

Features include:

- LIGHTWEIGHT TUBULAR ARM.
- LATEST MONO/STEREO CERAMIC CARTRIDGE.
- DIAMOND STYLUS.
- HEAVY BALANCED 10½ in. TURNTABLE.
- BUILT-IN P.U. PLUG AND SOCKET AND INTEGRAL 0tr. MAINS LEAD.

New bookshelf size MEGAMITE speaker system



- FULL FREQUENCY RANGE.
- EMPLOYS SPECIALLY DESIGNED FREE-CONE BASS UNIT
- INCLUDES MATCHING TWEETER AND CROSSOVER
- HANDLES 10 WATTS OUTPUT

Special 5in. free-cone bass unit uses enormously powerful Feroba magnet to obtain the exceptional cone movement needed to get clean, deep-down bass response equal to much larger speaker performance. Matching 4in. tweeter and crossover is housed with bass unit in heavily lugged, handsome teak veneered cabinet, size only 13 x 7 x 8 in. deep. Mounts vertically or horizontally. Ideal for modern Hi-Fi systems where clean, unobtrusive appearance with high performance is required.

£8.19.6 Carriage 7/6.

MAGNAVOX 363 TAPE TRANSPORTER



Manufactured to precise limits that permit recording and tape playback to the highest standard set by the Music Industry.


Simple, reliable design employs a single high-duty motor with heavy flywheel. Features include fast wind on and rapid rewind, pause control, 3-speed selection with interlock. Built-in revolution indicator, piano key controls. Speeds 1½, 3½ and 7½ i.p.s. Wow and flutter 0.15% on 7½ i.p.s. Max. spool size 7in. Playing time up to 120 mins. per track from 1,200ft. standard tape. Size 13½ x 11in. plus 5½ in. below mounting board.

With ½ track heads **£10.10.0**

With ¼ track heads **£13.10.0**

Add 10/- carriage and insurance.

HF/TR3 TAPE AMPLIFIER

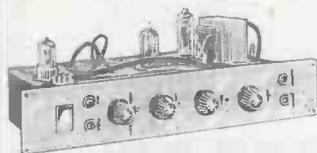

Easily the best complete tape amplifier available to the home builder. Supplied already matched for the Magnavox 363 tape-deck. Features include switched equalization for all speeds (OCCIR standards at 7½ i.p.s.). Treble boost incorporated during Record, Bass boost during playback, speaker output matched for 8, 7.5 and 15 ohms, additional outputs for extension speaker, phone monitoring on Record and Hi-Fi playback through existing systems. Inputs for Mic., pick-up and VHF Radio. Valves: 6F706, 6CC8, EL94, 6M81, E281. Size overall: 11 x 6 x 6 in. (Panel: 12½ x 3 in.). Power pack on separate chassis, size 7½ x 3 x 4½ in. Amp. Power pack. Kit of parts **£14.0.0**

Assembled and tested **£20.5.0** Add 7/6 carr.

TAPE PREAMPLIFIER TYPE "C"



Specially developed by Mullard Laboratories for use with high quality replay systems, and supplied specifically matched for use with the Magnavox 363 tape-deck.

Features include: Ferroxcube pot. core inductors for treble equalization, push-pull oscillator incorporating ferroxcube transformer, adjustable output for matching to existing high-quality amplifier systems, inputs for Mic., Pick-up, Radio, etc. Valves: 3 x 6F80, 6F82 and 6M81. Totally enclosed in case, size 11½ x 6½ x 3½ in. high (Panel 11½ x 3½ in.). Power supply of 300V. d.c. at 25 mA. and 6.3V. at 1.5 A. in on separate sub-chassis size 14 x 4½ x 4½ in. high to facilitate remote location from tape heads. Pre-amp. and power pack Kit of parts **£14.10.0**

Assembled and tested **£20.10.0** Add 7/6 carr.

VERITONE 300 6 gns. (C. & L. 5/-)

A small versatile Gram. Amplifier with an output of 3-4 watts suitable for Crystal Pickup or Radio Tuner, ideally suited for a small domestic installation requiring good quality low output, output impedance 3 ohms, volume control, treble control, bass control and middle control. Valve line-up: EL94, 6F80, E290. Smooth grey finished chassis, size 8½ x 4 x 1½ in. with brushed aluminium front panel, contrasting letters and knobs, front panel size 8½ x 2½ in. Fully assembled and tested.



Announcing the stern-clyne SULTAN Solid State Integrated Stereo Amplifier



The Stern - Clyne SULTAN represents a considerable advance in solid-state, high fidelity stereo amplifiers. Outstanding performance is allied to meticulous construction, comprehensive facilities, installation simplicity, and attractive functional styling. SULTAN performance is a natural result of superb design incorporating the most advanced fully proved semi-conductors, and modular substage construction that permits searching quality control and precise matching at every stage of assembly. Particular attention has been given to the provision of all the additional input, output, and power take-off facilities ever likely to be required. The compact sized, craftsman finished teak cabinet and restrained styling ensures unobtrusive, harmonious matching with almost any decor.

38 Gns. Complete. Carriage & Insurance **8/6**

SPECIFICATION & PERFORMANCE

Power Supply A.C. only. 200-250 v., 50-60 c/s. (Alternative ratings to special order).
 Power Consumption 48 watts maximum.
 Power Output 13 watts per channel RMS into 16 ohm load. Combined channels 20 watts.
 Speaker Matching 8-16 ohms (for 3-5 ohms use 2/3 ohm wire-wound resistors in series with each L/R).
 Distortion Total harmonic distortion less than .25% at full output.
 Frequency Response at 1 watt ± 2 dB, 30-25,000 c/s., at 10 watts ± 3 dB, 40-15,000 c/s.
 Cross Talk better than 50 dB at 1 Kc/s.
 Hum and Noise better than 52 dB below full output.
 Inputs: P.U.1 3.5 mV, 47K ohms impedance } R.I.A.A compensated Flat
 P.U.2 20 mV, 47K ohms impedance }
 Radio 100 mV, 220K ohms impedance, Flat
 Aux. 250 mV, 450K ohms impedance, Flat
 Dimensions 13in. x 11in. x 5in. Panel 12in. x 4in.
 Bass Control Boost 14 dB at 40 Kc/s. Cut 16 dB at 40 Kc/s.
 Treble Control Boost 12 dB at 14 Kc/s. Cut 18 dB at 14 Kc/s.


MONOGRAM AMPLIFIER AND ACCESSORIES

Monogram Amplifier

Superb space and cost economy design specially developed by Mullard Research Laboratories and quality constructed by Stern-Clyne. Actually uses only one multivalve but provides an undistorted output from any standard xtal pick-up. Plus features include Bass Boost and Treble Cut controls, panel illumination and specially wound output transformer. Size only 10 x 2 1/2 x 4 1/2 in. high. Silver hammer chassis finish, satin silver finish engraved panel. Kit of Parts **£4/10/-**. Carriage 4/6. Assembled and Tested **£6**.

Monogram Accessories

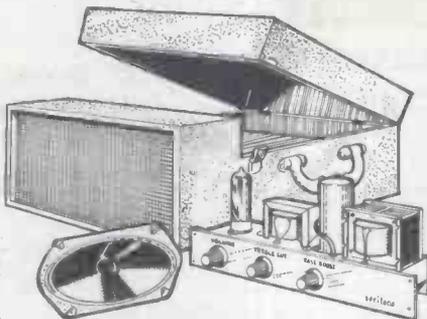Specially designed PC3 Carrying case takes Monogram Amplifier. 8 x 5 Bipolar Speaker (illustrated) and any standard turntable or Antochanger. Size overall 18 x 16 1/2 x 3 1/2 in., handsomely finished in dark grey fabric weave.
 PC3 Case **£3/5/-**. Carriage 5/6.
 8 x 5 Speaker **£1**. Carriage 2/6.



Our Finest Ever Meter Value! Duvidal ITI Multitester

72/6

P. & P. 3/-



With Built-in Meter Protection:

Pocket size with wide-angle, jewelled meter movement, ceramic long-life, low-loss switching, tough impact resisting case. Sensitivity 20,000 ohms/volt D.C. 10,000 ohms/volt A.C.

19 Ranges measure:

0-5-25-250-500-2,500 volts D.C. 0-10-100-500-1,000 volts A.C. 0-50 μ A-2.5 mA-250 mA. D.C. 0-6,000 ohms-8 megohms. 10 μ F-0.001 mfd.-1 mfd. -20 to +22 dB.

* stern-clyne's TREMENDOUS PRICE BREAKTHROUGH in NEW UNIVERSAL RECORDING TAPES

- TENSILIZED—pre-stretched, extra strong.
- Full frequency spectrum response.
- Guaranteed playing times.

STERN-CLYNE make huge bulk purchases of recording tapes from the world's biggest manufacturers—and hand on the enormous price advantage to their customers. The quality is unequalled: Tensilized to ensure the most permanent type of base. Highly resistant to breakage, moisture, heat, cold or humidity. Highly polished, splice-free finish. Smooth output throughout entire audio range.

TENSILIZED P.V.C.

3in. 250ft. Long Play	5/6
5in. 600ft. Standard	8/6
5in. 900ft. Long Play	10/-
5 1/2in. 1,900ft. Long Play	12/6
7in. 1,200ft. Standard	12/6
7in. 1,800ft. Long Play	15/-

TENSILIZED POLYESTER


3 1/2in. 600ft. Double Play	11/6
5in. 1,200ft. Double Play	15/-
5 1/2in. 1,800ft. Double Play	22/6
5 1/2in. 2,400ft. Triple Play	37/6
7in. 2,400ft. Double Play	25/-
7in. 3,600ft. Triple Play	50/-



SEND FOR CATALOGUE
 A 1/- P.O. brings new 100-page Sound and Science Catalogue packed with unique items; profusely illustrated.

SUPERB NEW STERN-CLYNE F.M.I. VHF TUNER

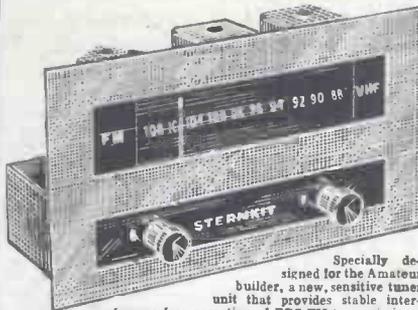Features sparkling performance—Inherent stability



Specially designed for the Amateur builder, a new, sensitive tuner unit that provides stable interference-free reception of BBC FM transmissions. High quality output signal ensures optimum performance from any Hi-Fi audio system; superb styling makes for harmonious installation with existing equipment. Reliable, easily aligned circuit employs RF stage tuned anodes, tuned-freq. changer, 2 JFs, Noise Limiter and Ratio Detector. Valves are 4 x EF91 plus 2 diodes. Input sens. 100 mV. for 40 dB. Dia. less than 1% at full deviation. Power freq. 200 v. at 20 mA. and 6.3 v. at 1.8 A. Panel black and silver-grey, size 8 x 5in. Chassis: eucium plated, overall depth 4 1/2 in.
 FM1 Kit of parts with Instruction Handbook, **£7/9/6** Carr. 4/-.
 FM1 Assembled and tested, **£10/9/6** Carriage 4/-.
 Optional Power Pack Type D Kit of Parts. **£2/15/0** Carr. 3/6.
 Power Pack Type D, assembled and tested, **£3/10/0** Carr. 3/6.
 Handbook only 3/- post free. Descriptive leaflet on request.

WE ARE FAMOUS FOR WIDEST RANGE OF HI-FI All the best makes for you to see and hear in side-by-side comparison in our Demonstration Room. No obligation. Sound advice free.

stern-clyne



MEMBER OF THE PANTIYA GROUP OF COMPANIES

MAIL ORDER & ALL ENQUIRIES TO:
 DEPT. WW2, 3-5 EDEN GROVE, HOLLOWAY, LONDON, N.7. Tel. NORTH 8161/5.

LONDON:
 18 Tottenham Court Road, W.1. MUS 5929/0095
 23 Tottenham Court Road, W.1. MUSEum 3451
 309 Edgware Road, W.2. PADdington 6963
 109 Fleet Street, E.C.4. FLEEt Street 5812/3
 162 Holloway Road, N.7. NORth 7941
 9 Camberwell Church Street, S.E.5. RODney 2875
 220 Edgware Road, W.2. PADdington 5807

CROYDON:
 12 Suffolk House, George Street. MUNICIPAL 3250

BRISTOL:
 26 Merchant Street, Bristol 1. BRISTOL 20261

LIVERPOOL: 52 Lord Street. ROYAL 7450

MANCHESTER:
 20/22 Withly Grove, M/c 4. BLACKfriars 5379/5246

SHEFFIELD: 125 The Moor. SHEFFIELD 29993

NOTTINGHAM:
 Eastown House, Lincoln Street. NOTTINGHAM 45889

LASKY'S RADIO

LONDON'S LARGEST STOCKISTS OF HI-FI AUDIO EQUIPMENT

BY ALL THE WORLD'S FAMOUS MANUFACTURERS

DEMONSTRATION STUDIOS

Lasky's Radio — established over 30 years — offer you the most exciting and up-to-date chain of High Fidelity and Electronics Stores in London with the largest and most comprehensive stocks in Great Britain.

Our branches at 207 EDGWARE RD., W.2 (newly restyled and modernised), 33 TOTTENHAM COURT RD., W.1 and 152/3 FLEET ST., E.C.4, have huge stocks of everything in the "World of Electronics" — Mains and Transistor Radios, P.A. Equipment, Guitar and Hi-Fi Amplifiers, Tuners, Speakers, Microphones, Record Players, Radiograms, Communication Receivers, Test Equipment, Components, Tape Recorders, Tape, Walkie Talkies, Intercoms, Build Yourself Construction Barsalms, Domestic and Electrical Equipment, Transistors, Valves, etc., etc., and thousands of bargains exclusive to Lasky's.

Our branch at 42 TOTTENHAM COURT RD., W.1 is London's most up-to-date High Fidelity Sound Centre. There you can hear and compare any combination of the finest equipment by all the world's most famous names in High Fidelity sound reproduction. Plus a wide range of high quality equipment cabinets and speaker enclosures to suit all styles of decor.

Our branch at 118 EDGWARE RD., W.2 has the widest selection in Great Britain of Mains and Transistorised Radios with over 400 different models in stock and over 150 mains and transistorised Tape Recorders — by all the well-known British, Continental, American and Japanese manufacturers — Plus TV, Hi-Fi Audio Equipment, Radiograms, Record Players, all the latest marvels in the "World of Electronics" — and a full range of domestic appliances.


If you cannot call at any of our branches please send details of your requirements to our head office and we shall be pleased to quote without obligation. We operate the "Purchase Tax Free" scheme for overseas visitors. Full H.P. terms available.

RECORD PLAYERS

4-SPEED AUTOCHANGERS

B.S.R. AUTOCHANGERS NEW LOW PRICES

All brand new and fully guaranteed complete with cartridge and stylus.	
UA14 4-speed mains model	£4 9 6
UA10 4-speed mains model	£4 19 6
UA16 9v battery model	£5 19 6
UA20 4-speed mains model	£5 19 6

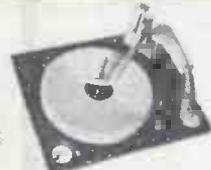

GARRARD AUTOCHANGERS AT LOWEST EVER PRICES!

Auto-tilt Mono	£4 15 6	A50 less cartridge	£9 14 6
AT6 Mono	£8 19 6	A1000 with GC8 cartridge	£6 6 0
AT6 Stereo	£9 9 0	A2000 with GC8 cartridge	£6 6 0
3000LM with stereo cartridge	£7 9 6	GARRARD BASES	
AT60 with stereo Monotone cart.	£10 9 6	WB1 .. £3 12 8	WB2 .. £5 0 3
AT7 less cartridge	£19 9 0	CLEARVIEW PERSPEX COVERS	
Lab. A Mono/Stereo	£14 19 6	WB1 .. £3 10 0	WB2 .. £4 17 6
Lab. A on plinth	£15 19 6		

TRANSCRIPTION MOTORS

GARRARD 401	£32 10 0
GARRARD Lab. 80, less cart.	£24 19 6
GARRARD 301 (Strobe)	£22 19 6
CONNOISSEUR	
Craftsman II	£17 2 11
Craftsman III	£22 19 6
Model B	£25 4 0
LENGO GL53	£17 1 2
LENGO GL43	£19 10 7
LENGO G88	£15 15 0
LENGO GL70	£29 18 6
LENGO G99	£21 19 6
THORENS TD185 I	£26 5 0
THORENS TD185 II	£40 5 8
THORENS TD124 II	£40 5 8
THORENS TD150	£20 13 2

All other current models available. Postage on all above 5/- extra.

SINGLE PLAYERS

Auto. start and stop. Complete with pick-up and crystal cartridge.	
BMI with Stereo cartridge	£3 19 6
COLLARO JUNIOR 4-speed	£3 9 6
GARRARD SRP12	£4 7 6
GARRARD SRP10 mains model	£4 19 6
GARRARD SRP10 battery model	£4 19 6
GARRARD SP25 Mono	£9 10 6
GARRARD SP25 Stereo	£10 19 6
PHILIPS AG/1016	£12 12 0
BRAUN PC4L Stereo	£8 19 6

GREENCOAT RECORD PLAYER

2 speed model 33 and 45 r.p.m. 6 v. Battery operated. Complete with pick-up and fitted with crystal cartridge. Size only 7 1/2 x 6 1/2 in. Fitted with auto stop and start. Ideal for use with miniature transistor amplifiers.

LASKY'S PRICE 59/6 Post 2/6.



CRYSTAL PICK-UP CARTRIDGES — LOWEST PRICES EVER!

All complete with Stylus L.P. and Standard, fully guaranteed. Standard Fitting will fit most P.T. Arms and Heads. Post 1/-.		STEREO	
Garrard GC2	17/6	Ronette Stereo O.V. Turnover with 2 sapphires	25/-
Garrard GC8	15/-	Ronette Stereo type 105 and 106 with 2 sapphires	25/-
Garrard EV26A	19/6	Ronette Stereo Type 105 and 106 with diamond LP/Stereo and Sapphire standard	35/-
Acos G.P. 671	10/6	Full range of Goldring and Philips cartridges stocked.	
AND EVEN LOWER PRICES Save Money! Some of these cartridges are cheaper than stylus			
C.T.I. Mono 2 sapphires	4/11	Caliel SCI diamond LP, stereo	10/6
Collaro 2 sapphires, stereo	15/-	Sonotone 2TA mono	15/-

AMPLIFIERS

RECEIVE STEREO BROADCASTS NOW!

WITH THE FABULOUS LOEWE OPTA L040




A really superb AM/FM Tuner and Stereo Amplifier giving the finest reproduction of broadcast sound available. Brief Spec.: Valve AM/FM Stereo Tuner and IF amplifier (including Multiplex); Transistorised twin channel preamplifiers and power amplifiers giving 20 watts per channel output; very low distortion and Interference levels; wavebands: LW/MW/SW and VHF/FM with switched AFC; large tuning scale with magic eye; 11 push button controls; bass and treble controls; inputs for Stereo pick-up, Stereo tape recorder, and provision for external speakers. For 110/127/240 v. A.C. mains. Superb modern styling—beautiful veneered cabinet size 24 x 6 1/2 x 8 1/2 in. Original list price 84 Gns. Limited quantity only.

LASKY'S BARGAIN PRICE 59 GNS. Carriage and Insurance free

AND THE NIELSEN 'ARENA' T1900 H NOW COMPLETE WITH MULTIPLEX ADAPTOR

Extremely high quality fully transistorised stereo AM/FM Tuner Amplifier—by Scandinavia's leading Audio designers. Brief specification: 20 transistors and 13 diodes; covers LW, MW, 2 x SW (40-51 M and 57-200 M), and FM with AFC; 2 x 8 watts output; built in 6 x 4 in. speakers in pressure chambers, 10 push-button controls; volume, bass, treble and separate FM and AM tuning controls; tuning indicator; inputs for tape recorder and gram pick-up; outputs for 3 external speakers and external AM and FM aerials (additional to built in ferrite rod and wire aerials); provision for stereo decoder; for 200/250 V. A.C. mains operation. Very elegant "slim-line" styled cabinet superbly made and finished in natural oiled teak size: 5 1/2 x 29 1/2 x 8 1/2 in.

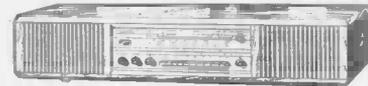

LASKY'S PRICE 69 GNS.

Carriage and Packing 20/- extra.

THE 'ARENA' T1900 F LASKY'S PRICE 63 GNS.

Same spec. as the T1900 H described and illustrated above, but without built in speakers and speaker chambers—size 5 1/2 x 16 1/2 x 8 1/2 in. Carriage and Packing 16/- extra.

LASKY'S SPECIAL ALL SCANDINAVIAN PACKAGE DEALS

The T1900 F with either two SBB Mini B or B7 speaker systems. LASKY'S PACKAGE PRICE 74 Gns. Matching teak plinth with smoke Perspex cover for Record Player £8/19/6 extra. CHOOSE YOUR OWN TURNTABLE AND CARTRIDGE—send us details of your choice for our special Package Deal quotation. Example: T1900 F with two SBB B7 speaker systems. Garrard SP 25 Record Player with Stereo cartridge on matching teak plinth with Perspex cover. LASKY'S PACKAGE DEAL PRICE 89 Gns. Our normal price for the above equipment would be £89/17/-—therefore our Package Deal price SAVES YOU A FURTHER 28/8/-.

COMPLETE SYSTEMS

A Lasky's "Privilege Parcel Package Deal" allows you to purchase the complete Audio System of your choice at a worthwhile cash saving. We shall be pleased to quote our "Privileged Parcel Package Deal." Prices for any selection of equipment of your own choice. Send us details of your requirements. H.P. Terms can be arranged on "Privilege Parcel Package Deals."

HI-FI FURNITURE

Choose from our extensive range of equipment cabinets and speaker enclosures by Record Housing, Fisher, G.K.D., Design Furniture, etc. A full range is in stock to suit all types of equipment, furnishing styles, etc. Complete installations can be supplied to your choice, and our expert staff will be pleased to advise you. Illustrated—the Lowflex equipment cabinet by Record Housing suitable for a wide range of equipment including space for record and tape storage.



SPEAKERS

SPECIAL BARGAINS FROM SCANDINAVIA - S.H.B. SPEAKER SYSTEMS

Extremely advanced design and miniaturisation of components pioneered by this well-known Swedish manufacturer has made possible these wonderfully compact speaker systems, with a performance previously impossible in such small enclosures. Both utilise a double layer cone drive system contained in a hermetically sealed cabinet, giving a very sensitive and smooth response at all levels. Individual details: Mini-B, power handling 9 watts undistorted; impedance 15/16 ohms; frequency response 50-15,000 cps.; superbly made cabinet size 10 x 6 1/2 x 7 1/2 in., finished in Scandinavian Teak—list price £11/13/8. Model B-7, as Mini-B but frequency response 45-15,000 c.p.s., and size 16 1/2 x 11 x 3 1/2 in.—list price £12/3/5. Brand new and fully guaranteed.



LASKY'S PRICE Mini-B £6.19.6 Carriage Model B-7 £6.19.6 5/-

LASKY'S RADIO FOR FINEST VALUE AND COURTEOUS SERVICE

WW-150 FOR FURTHER DETAILS.

TAPE RECORDER BARGAINS & COMMUNICATIONS SETS


LASKY'S RADIO

THE WIDEST RANGE AVAILABLE TODAY

TAPE RECORDERS

MAGNAVOX - COLLARO 363 TAPE DECKS

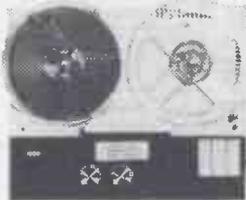The very latest 3 speed model—1½, 3½, 7½ i.p.s. available with either ¼ track or ½ track head. Features include: pause control; digital counter; fast forward and rewind; new 4 pole fully screened induction motor; interlocking keys. Size of top plate 13½ x 11 x 2½ in. deep below unit plate. For 200/250 v. A.C. mains, 50 c.p.s. operation. New unused and fully guaranteed.



LASKY'S PRICE ¼ track model £10.10.0 Carriage and Packing
LASKY'S PRICE ½ track model £13.9.6 7/6 extra.

SPECIAL FOR OVERSEAS CUSTOMERS—the new Magnavox-Collaro 363 Deck for 110/125 v. 50 or 60 c.p.s. mains now available, prices as above. Post to any part of the world, 35/-.

NEW MARTIN TAPE RECORD/REPLAY AMPS.

Now available from stock—for use with the Magnavox 363 Tape Deck
¼ track model.....LASKY'S PRICE £14.19.6 Carriage & Packing 4/6 extra
½ track model.....LASKY'S PRICE £15.18.8
Optional Extras: Control panel escutcheon to take deck and amplifier controls.
LASKY'S PRICE 12/6. Post & Packing 2/6.

A FEW EACH OF THESE OUTSTANDING BARGAINS STILL AVAILABLE AS PREVIOUSLY ADVERTISED.

- FI-CORD 202A. List price 289/6-..... LASKY'S PRICE 39 Gns. C. & P. Free
- HARROW VR71. List price 24 Gns. LASKY'S PRICE 18 Gns. C. & P. 10/6
- COSSOR CR.1804. List price 39 Gns. LASKY'S PRICE 29½ Gns. C. & P. 15/-

JUST ARRIVED — "REFLECTOGRAPH" MODEL E/A AUTOMATIC CONTINUOUS TAPE PLAYER

This unit, based on the famous "Reflectograph" deck, is designed for the continuous playing of pre-recorded background music on twin track tape, automatically reversing at either end of the tape and changing the playback heads. The reversing circuits are triggered by metal foils at the tape ends—during the reversal operation the tape transport mechanism is opened thus removing the tape load from the capstan motor. The output from the deck must be fed into a suitable audio amplifier and loudspeaker system. The model E/A does not incorporate its own output stages or recording amplifier. The player may be switched on manually or remotely by a time clock or switch (not supplied). A manual reverse control is provided; signal lamps indicate tape direction. Tech. details: Three motors—3½ i.p.s.; two playback heads; N.A.B. equalization; output voltage 0.25 v. R.M.S. into high imp.; for use on 200/250 v. 50 c.p.s. mains. The deck is beautifully finished in pale grey/green enamel with walnut finish side panels. Size: 20 x 16 x 9 in.



LASKY'S PRICE 27 GNS. Carriage & Packing 25/-.

TAPE DECK MOTORS

High quality tape deck capstan motor made by E.M.I. Holland. Bi-directional. Size 4in. dia. x 2in. high. 1in. x ½ in. spindle.
LASKY'S PRICE 15/11 Post 3/6.

HI-FI TAPE RECORDER HEADS

¼ track Stereo record/replay Tape Heads. High Imp. Size 7/8 in. wide x ½ in. high x ½ in. deep. Fixing is by single 8 B.A. screw. New and unused. LASKY'S PRICE 25/- Post free.

TAPE POSITION INDICATOR

Open type—as used by most makers. With reset knob. 3 DIGIT 7/6. 4 DIGIT 10/6. post 6d. ea/h

MICROPHONES

THE VERY LATEST MARVELS OF ELECTRONIC MINIATURISATION

TTC B4002 FM WIRELESS MIC.

Highly sensitive—suitable for either static or mobile use. Signal can be picked up by any FM radio or tuner which receives frequencies between 96-104 Mc/s. over several hundred yards. Size only 3 x 2½ x 1½ in. (in leather case). Operates on one PP3 type battery. Complete with neck cord, clip-on dynamic extension mike (1 x 1 x ½ in.) and battery.



LASKY'S PRICE 14 GNS. Post Free. Anywhere in the World.

TTC 18/500. More powerful version of above—size 4 x 1 x 1 in. Operates on one PP3 type battery. LASKY'S PRICE 16 Gns. Post Free. Anywhere in the World.

LASKY'S FOR D.I.Y. CONSTRUCTION BARGAINS

COMMUNICATION RECEIVERS


MODEL KT 320 KIT

Supplied in sub-assemblies for easy building. Covers ranges from 540 Kcs to 30 Mc/s Ham Band is provided with a scale for direct reading and can also be band spread. 9 valves. Facilities: A.N.L. A.V.C. and M.V.C. Q Multiplier also serves as B.F.O. H.F. stage and two I.F. stages ensure high sensitivity and selectivity (all coils and I.F.s are supplied pre-aligned). 2 Aerial Sockets, Stand-by position for use with a transmitter 8 meter fitted. 200-250 v. A.C. mains. Steel cabinet, grey crackle finish. Size 15 x 8 x 10 in. Dial 12 x 4 in.

All parts new and fully guaranteed. Complete with full construction data and operating manual.
LASKY'S PRICE 25 GNS. POST Also available ready built and tested 32 gns. FREE H.P. Terms Avail. on Kit and Built versions.

NEW MODEL SR 150

Covers full medium waveband and 1.6-4.4 Mc/s. 4.5-11.0 Mc/s. and 11.0-30.0 Mc/s. in separate switched band spread ranges. Two aerials are fitted an internal loop and external telescopic. Controls include: B.F.O. Sensitivity, C.W., A.N.L. tone switch, receive/stand-by, 8 meter. Easy to read illuminated dial with logging scale. For 200/250 v. A.C. 4 valve plus rectifier. Fitted with internal speaker and socket for phones or external speaker Cabinet size 13½ x 8½ x 5½ in. Complete with full instruction manual.

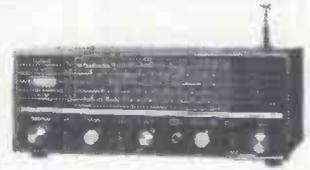

LASKY'S PRICE £19.10.0

H.P. Terms £5/5/- dep. and 11 monthly payments at £1/11/6. Total H.P. £22/11/6. Post 10/-.

STILL A FEW AVAILABLE * FULLY BUILT

- MODEL HE30 32 Gns. MODEL HE40 18½ Gns. MODEL HE80 59 Gns.

TEST EQUIPMENT

NOMBREX TEST EQUIPMENT

MODEL 27 TRANSISTORISED SIGNAL GENERATOR (illustrated)

Wide range—150 kc/s to 350 Mc/s. Accuracy better than 2%. Direct calibration. AF, RF and MOD. Battery operated. Light weight and strongly made. Complete with test leads and batt.
LASKY'S PRICE £10.16.9 Post Free.



MODEL 63. Wide range AUDIO GENERATOR

10-100 Kc/s. £17/1/9 complete with battery.

MODEL 66. Wide range INDUCTANCE BRIDGE

µH to 100H in 4 ranges. Measures Q. £13/8/9. complete with battery.

POWER SUPPLY UNIT 1 to 15 v. D.C. up to 0.1 amp. 230/250 v. A.C. mains. £6.14.6

MODEL 62 RESISTANCE CAPACITY BRIDGE £9.6.9 complete with battery.

HIGH QUALITY TEST METERS Complete with test leads and batts.

- HAIKI 20,000 O.P.V. £5 19 6 P-1 2,000 O.P.V. £2 12 6
 - TE-13 1,000 O.P.V. £1 19 6 P-3 4,000 O.P.V. £4 2 6
 - TMK-500 30,000 O.P.V. £8 17 6
 - 200-H 20,000 O.P.V. £5 5 0 MT-559 50,000 O.P.V. £10 19 6
- Complete range of Avo and Taylor Meters in stock.

MISCELLANEOUS

NOW AVAILABLE—OUR NEW BARGAIN BULLETIN. 24 foolscap pages packed with hundreds of bargains for the "ham" and service man—exclusive to Lasky's—plus full list of regular stock items. PRICE 6d. POST FREE.

TRANSISTORS

ALL BRAND NEW AND GUARANTEED

GET 81 GET 84, GET 85 2 6; 837A, 874P, 3/6; OC45, OC71, OC81D, 4/6; OC44, OC70, OC76, OC81 (match pair 10/6); 5/6; AF117, OC200, 8/6; OC42, OC43, OC73, OC82D, 7/6; OC201, OC204, 15/-; OC205, OC206, 19/6; OC28, 24/6; OC75, 8/-.

TRANSFILTERS

By BRUSH CRYSTAL CO. Available from stock.

- TO—01B 465 kc/s. ± 2 kc/s. TO—02D 470 kc/s. ± 1 kc/s. 9/6 EACH
- TO—01D 470 kc/s. ± 2 kc/s. TF—01B 465 kc/s. ± 2 kc/s. Post 6d.
- TO—02B 465 kc/s. ± 1 kc/s. TF—01D 470 kc/s. ± 2 kc/s.

GORLER UT 340 FM/VHF TUNING HEART

Permeability tuned—covering 87 to 108 Mc/s. Designed for use with one ECC85 valve. Built in cast metal case, size 3 x 2½ x 1½ in. Circuit supplied.

LASKY'S PRICE 15/11 ECC85 valve, 9/- extra. Post and Packing 2/-.

INTERNATIONAL BRAND TAPE Fully Guaranteed at record low prices,

- 3in. Message tape, 150ft. 2/6
- 3in. Long play, 1,200ft. Acetate base .. 12/6
- 3in. Message tape, 225ft. 3/6
- 5in. Standard play, 850ft. P.V.C. base .. 11/6
- 3in. Message Tape, 300ft. 7/6
- 5in. Triple play, 2,400ft. Mylar base .. 45/-
- 3in. Triple play, 600ft. Mylar base .. 10/-
- 5in. Long play, 1,200ft. Mylar base .. 15/-
- 4in. Triple play, 900ft. Mylar base .. 17/6
- 7in. Standard play, 1,200ft. Acetate base 12/6
- 5in. Double play, 1,200ft. Mylar base .. 15/-
- 7in. Standard play, 1,200ft. Mylar base 12/6
- 5in. Long play 900ft. Acetate base .. 10/-
- 7in. Long play, 1,800ft. Mylar base .. 19/6
- 5in. Standard play, 600ft. P.V.C. base 3/6
- 7in. Double play, 2,400ft. Mylar base .. 25/-
- 5in. Triple play, 1,800ft. Mylar base .. 35/-
- 7in. Long play, 1,800ft. Acetate base .. 15/-
- 5in. Double play, 1,800ft. Mylar base .. 22/6
- 7in. Triple play, 3,600ft. Mylar base .. 50/-

1/- Post extra per reel; 4 reels and over Post Free. Full range of Philips pre-recorded cassettes—send S.A.E. for list.

P.T.O. FOR MORE NEWS

LASKY'S RADIO

CONSTRUCTORS' BARGAINS & SPECIAL INTEREST ITEMS

STOCKS ALWAYS CHANGING—1,000's OF BARGAINS

CONSTRUCTORS BARGAINS

We consider our Construction Parcels to be the finest value available on the home construction market. If on receipt you feel not competent to build the set, you return it as received within 7 days, the sum paid will be refunded less postage.

THE SKYROVER DE LUXE

7 transistor plus 2 diode superhet, 6 waveband portable receiver covering the full Medium Waveband and Short Waveband 31-94M and also 4 separate switched bandspread rangers, 18M., 16M., 15M., and 25M., with Band Spread Tuning for accurate Station Selection. The coil pack and tuning heart is completely factory assembled, wired and tested. The remaining assembly can be completed in under three hours from our easy to follow, stage by stage instructions. Superhet, 470 Kcs. All Mullard Transistors and Diode. Uses 4 U2 batteries. 6in. Ceramic Magnet P.M. Speaker. Easy to read Dial Scale, 500 M W Output. Telescopic Aerial and Ferrite Rod Aerial. Tone Circuit is incorporated with separate Tone Control in addition to Volume Control. Tuning Control and Waveband Selector. In a wood cabinet, size 11 1/2 x 6 1/2 x 3in. covered with a washable material, with plastic trim and carrying handle. Car aerial socket fitted.




Can now be built for **£8.19.6** Post 3/- extra H.P. Terms: 45/- deposit and 11 monthly payments of 14/2. Total H.P.P. £10/4/10.

Data 2/6. Refunded if you purchase parcel. Four U2 batt. 3/4 extra. All components avail. sep.

★ LONG WAVEBAND COVERAGE IS NOW AVAILABLE FOR THE SKYROVER DE LUXE A simple additional circuit provides coverage of the 1100/1950M band (including 1500M, Light programme). This is in addition to all existing Medium and Short wavebands. All necessary components with construction data. Only 10/- extra. Post Free. This conversion is suitable for receivers already constructed.

NEW! LASKY'S MINIATURE TRANSISTOR AMPLIFIER MODULES

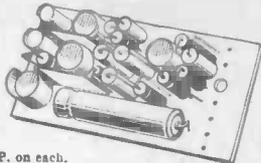Incorporating the very latest circuitry to provide high sensitivity and good quality in conjunction with extreme small size and compactness. High quality Newmarket transistors used throughout. All designed to operate on 9V. miniature battery. Add 1/- P. & P. on each.



- TYPE LRPC 1. 8 Transistors. Input sens. 50mV., output 150mW., output imp. 40 Ω, size 2 1/2 x 1 1/2 x 1 1/2 in. PRICE 27/6
- TYPE LRPC 2. 6 transistor. Input sens. 1mV., output 330mW., output imp. 15 Ω size 2 1/2 x 1 1/2 x 1 1/2 in. PRICE 22/6
- TYPE LRPC 3. 5 transistor. Input sens. 5mV., output 400mW., output imp. 15 Ω size 2 1/2 x 1 1/2 x 1 1/2 in. PRICE 25/-
- TYPE LRPC 4. 5 transistor. Input sens. 150mV., output 330mW., output imp. 15 Ω. size 2 1/2 x 1 1/2 x 1 1/2 in. PRICE 22/6
- TYPE LRPC 5. 6 transistor. Input sens. 8mV., output 3W., output imp. 3 Ω, size 6 1/2 x 1 1/2 x 1 in. PRICE 59/6

- FULLY ENCAPSULATED MODULES**
Special function modules—all one size 1 1/2 x 1 1/2 in. Complete with detailed function and installation instructions. Send S.A.E. for specification sheets.
- TYPE PA-1. Public address amp. for use with carbon, crystal or Dynamic microphones. 3 Ω output imp. LASKY'S PRICE 30/-
 - TYPE GR-1. Gramophone amp.—provides sufficient power to fill average room. 3 Ω output imp. LASKY'S PRICE 30/-
 - TYPE CO-1. Morse code practice oscillator—for use with morse key and 3 Ω speaker. LASKY'S PRICE 20/-
 - TYPE MT-1. Metronome module—provides audible and visual beat from 30 to 240 beats per minute (for use with 3 Ω speaker) LASKY'S PRICE 22/6

- SINCLAIR SUPER MINIATURES** Write for complete range. Write for details of package deals.
- The Micro 6 miniature radio £2 19 6
 - THE SLIMLINE 2 transistor radio £2 9 6
 - THE MICRO-FM (tuner/receiver) £5 19 6
 - THE X-20 20 watt P.W.M. amp. £7 19 6
 - THE Z-12 12 watt amp. and pre-amp, fully built £4 9 6
 - STEREO 25 pre-amp control unit, fully built £9 19 6

LIMITED QUANTITY ONLY—EXPORT MODEL TV
925 line T.V. chassis (Export Model). For 200-260 v. A.C./D.C. mains. Fitted with Bands I-III turret tuner. Fully loaded with 12 sets of coils for all CCIR channels in these bands. F.M. sound. Made by famous British manufacturer. 10 Mullard valves. Electrostatic focus/magnetic deflection. Will take 17in., 19in., 21in. or 23in. C.R.T. All controls fitted. Supplied new and unused with all valves (less CRT speaker and cabinet). Circuit data included. Anywhere overseas 50/-.

LASKY'S PRICE £14.19.6
A FEW AVAILABLE SLIGHTLY SHOP-SOILED, OTHERWISE PERFECT £9/19/6.

SPECIAL INTEREST ITEMS!

TRANSMITTER-RECEIVERS, "WALKIE TALKIES"

- All fully transistorised, battery operated with internal speaker and telescopic aerial. Range varies depending on power of unit and area. All complete with batteries—prices shown are for pair.
- TRANSETTE—size 5 1/2 x 2 1/2 x 1 1/2 in. (each unit), comp. with carrying strap PRICE £6/15/0. Post 2/6.
 - FANTAVOX TE-1005—10 transistors; size 7 x 2 1/2 x 1 1/2 in. (each unit). Comp. with leather case and earphone. PRICE 25 Gns. Post 6/-
 - AFCO C10—10 transistors; batt. level meters; size 8 x 3 x 1 1/2 in. (each unit). Comp. with earphone and wrist strap. PRICE 29 Gns. Post Free.
 - STANDARD SRK-22X—size only 5 x 1 1/2 x 1 in. Comp. with earphone and wrist strap. PRICE 40 Gns. Post Free.
 - MILDAN 13-132B—16 transistor high power model. 2 switched channels, output and batt. level meters; size 10 1/2 x 3 x 2 1/2 in. (each unit). Socket for ext. battery. PRICE 79 Gns. Post Free.

ARMSTRONG EQUIPMENT

Model	Price	Description	Price
Model 227M	£40 1 6	127M	£29 18 9
Model 223	£31 9 0	127	£40 1 6
Model 227	£52 15 0	A.20 Stereo Amp	£23 12 6
Model 226	£61 0 0	P.C.U. 25 Stereo Pre-amp	£21 0 0
Model 222 Amplifier	£28 15 0	Optional cases	£3 10 0
Model 224	£25 2 3	M6 Stereo Multiplex Decoder	£14 10 0
Model 221	£35 10 0	M12 Stereo Multiplex Decoder	£15 7 6

SPECIAL PURCHASE—UHF/VHF/TV TUNERS

Well known British makers surplus stocks. Now available for the first time to the Home Constructor. Add 2/6 Post and Packing on each.

- TRANSISTORISED UHF MINIATURE MODEL**
Shielded metal case, size only 3 1/2 x 1 1/2 x 3in. Fully tunable—complete with two AF 130 transistors. LASKY'S PRICE 39/6.
- VALVE UHF MODEL (Illustrated)**
In metal case, size 4 x 6 x 1 1/2 in. Fully tunable—complete with PC86 and PC88 valves. LASKY'S PRICE with valves 28/6. Without valves 12/6.
- TRANSISTORISED VHF MODEL 1**
Miniature turret type fitted with 12 sets of coils and 3 Mullard AF102 transistors. In metal case, size 4 x 2 x 3 1/2 in. LASKY'S PRICE 29/6.
- TRANSISTORISED VHF MODEL 2**
Sub-miniature turret type fitted with 12 sets of coils and 3 Mullard AF102 transistors. In metal case, 3 x 1 1/2 x 2 1/2 in. LASKY'S PRICE 37/6.



MAKER'S SURPLUS TELEVISION IF AMPLIFIERS

38 Me/s. Contains a large number of components. IF transformers, resistors, capacitors, etc. and the following valves: 2 x PC860, 1 x EB91, 2F70, 2F183 and 2F184. Overall size 1 1/2 x 3 1/2 x 4in. Ideal for servicemen and experimenters. This IF amplifier when used with the Valve model UHF Tuner (above) provides suitable conversion for B.B.C.2. No circuit available.



LASKY'S PRICE 39/6 Post & Packing 2/6

SPECIAL PACKAGE BARGAIN OFFER

Free standing table cabinet, size 19 1/2 x 9 x 6in., finished in medium Mahogany. Scale marked 21 to 68 (UHF band). Designed to accept the above IF Amplifier with space for a Valve UHF Tuner.



Special Package Offer: IF Amplifier, UHF Tuner with valves and Table Cabinet.

LASKY'S PACKAGE PRICE 89/6 Post and Packing 6/-.

MARTIN HI-FI AUDIOKITS

Using specially developed circuits, the very latest transistors and printed circuits—these kits are all fully checked and tested before leaving the factory.

- KIT 1. 5-stage Matching Input Selector Unit LASKY'S PRICE £2/7/6
- KIT 2. Pre-amplifier with volume control LASKY'S PRICE £1/17/6
- KIT 3. 3-Channel Mixer, with plug-in adaptors for individually matching each circuit. Adaptors 8/6 each. LASKY'S PRICE £3/19/6
- KIT 4. Pre-amplifier with tone/volume control stages. LASKY'S PRICE £3/2/6
- KIT 5. 10 and 5 watt Beta Amplifier. LASKY'S PRICE £5/12/6
- KIT 6. Power supply Converter Unit LASKY'S PRICE £3/12/6
- KIT 7. 15 ohm version of Kit 5. LASKY'S PRICE £6/12/6
- KIT 8. Power supply for Kit 7 LASKY'S PRICE £2/15/6
- UNIT 15 FM Head LASKY'S PRICE £5/12/6
- UNIT 16 IF Amplifier 84up (FM). LASKY'S PRICE £5/7/6
- UNIT 17 Drive Assembly and Controls (FM) LASKY'S PRICE £1/17/6

ALL MAIL ORDERS AND CORRESPONDENCE TO OUR HEAD OFFICE:—3-15 CAVELL STREET, TOWER HAMLETS, LONDON, E.1. Tel: STE 4821/2

207 EDGWARE ROAD, W.2. Tel: PAD 3271
118 EDGWARE ROAD, W.2. Tel: PAD 9789
33 TOTTENHAM CT. RD., W.1. Tel: MUS 2605
All the above branches Open all day Saturday. Closed 1 p.m. Thursday.

42 TOTTENHAM CT. ROAD, W.1. Tel: LAN 2573
152/3 FLEET STREET, E.C.4. Tel: FLE 2833
Both the above branches Open all day Thursday. Close 1 p.m. Saturday.
ALL MAIL ORDERS TO 3-15 CAVELL STREET, E.1.

'ELEGANT SEVEN' MK. II

Buy yourself an easy to build 7 transistor radio and save at least £10. Now you can build this superb 7 transistor superhet radio for under £4 10s. 0d. No one else can offer such a fantastic radio with so many de luxe star features.

- ★ de luxe grey wooden cabinet size 12½in. x 8½in. x 3½in.
- ★ Horizontal easy to read tuning scale printed grey with black letters, size 1½in. x 1½in.
- ★ High "Q" ferrite rod aerial.
- ★ I.F. neutralization on each separate stage.
- ★ D.C. coupled push pull output stage with separate A.C. negative feedback.
- ★ Room filling output 350 mW.
- ★ Ready etched and drilled printed circuit board back printed for foolproof construction.

- ★ Fully comprehensive instructions and point-to-point wiring diagrams.
- ★ Car aerial socket
- ★ Fully tunable over medium and long wave. 168-535 metres and 1,250-2,000 metres.
- ★ All components, ferrite rod and tuning assembly mount on printed board.
- ★ Full after sales service.
- ★ Parts list and circuit diagram 2s. 6d., free with parts. Price £4 4s. 0d plus 7/6 postage and packing.



ONLY **£4. 4. 0** Plus 7/6 P. & P.

SPECIAL OFFER

For one month only, R. & A. 7in. x 4in. 9,000 lines P.M. Speaker at no extra charge. Power supply kit to purchasers of "Elegant Seven" parts, incorporating mains transformer, rectifier and smoothing condenser, A.C. mains 200/250 volts. Output 9 v. 100 mA. 7s. 6d. extra.

'MAYFAIR' 5-Transistor TAPE RECORDER

Capstan-driven, battery operated. 7½ and 3½ i.p.s. Precision made. Push-button controls. High quality 2½in. speaker. Push-pull circuit. Output: 400 mW. Frequency response: 200-7,000 kc/s. Fast rewind up to 1 hour twin track playing time. Automatic erasing for re-recording. Dimensions: 8in. x 11in. x 3½in. Weighs only 7lb. Takes 5in. spools.

£11. 11. 0 plus 9/- P. & P.

40W. FLUORESCENT LIGHT KIT

Incorporating GEC Choke size 8½in. x 1½in. x 1½in., 2 bi-pin holders, 11'6 starter and starter holder. P. & P. 5/6. Similar to above: 80W. Fluorescent Light Kit incorporating GEC choke size 11½in. x 1½in. x 1½in., 2 bi-pin holders, 17'6 starter and starter holder. P. & P. 6/6. Twin 40W. Choke, instant start for two 2ft. tubes, 17/6, P. & P. 5/6.

CYLDON A.M./F.M. PERMEABILITY TUNER FOR ALL TRANSISTOR OPERATION

Size 2½in. x 2½in. approx. By famous manufacturer. A.M.-I.F. 470 kc/s. F.M.-I.F. 10.7 Mc/s. A.M. coverage from 1,620 kc/s-525 kc/s. F.M. coverage 108 Mc/s-88 Mc/s. Circuit diagram 2/6. FREE with Tuner. 1st, 2nd, 3rd A.M.-I.F.s, 1st, 2nd, 3rd and 4th F.M.-I.F.s. V.H.F. Osc. choke A.M.-F. trap. The above items: **£2. 10. 0**

MULTIPLEX DECODER For receiving STEREO FM

Now is your chance to benefit in full from the new B.B.C. stereo transmissions with our Multiplex Decoder. Design features: Highly efficient Mullard vinkor pot cores. Two semi conductor diodes. Double purpose valve. Printed circuit type construction high input impedance. Specification: Cross talk minus 26 db. at 1 kc/s. Input requirements 0.5-1.5 RMS. Stability plus or minus 0.1%. Voltage requirements H.T. 190-250 volts. D.C. at 5 mA. heaters 6.3 volts. A.C. at 300 mA. Self powered unit shortly available, price to be announced. Size 5½in. x 3½in. x 1in. Fully built and tested.

Price **£4. 4. 0** P. & P. 3/-



FIRST QUALITY PVC TAPE

5½in. Std. 850ft. . . 9/-	5in. L.P. 850ft. . . 10/6
7in. Std. 1,200ft. . . 11/6	3in. T.P. 600ft. . . 10/6
3in. L.P. 240ft. . . 4/-	5in. T.P. 1,800ft. . . 25/6
5½in. L.P. 1,200ft. . . 11/6	5½in. T.P. 2,400ft. . . 32/6
5½in. D.P. 1,800ft. . . 18/6	7in. T.P. 3,600ft. . . 42/6
7in. L.P. 1,800ft. . . 18/6	4in. T.P. 900ft. . . 15/-

P. & P. on each 1/6, 4 or more post free.

Fully Transistorised REV. COUNTER

Can be used for 4 or 6 cyl. engines. Would cost at least £8 new but you can make one at a fraction of the price! This kit makes a modern efficient rev. counter—essential to your engine's welfare: contains moving coil movement and all parts including transistors and a circuit diagram. Max. reading 8,000 r.p.m. For 12 volt operation negative or positive earth. Send for your kit today. Price plus 2/6 P. & P. **19/6**



Type E MOTOR



Small A.C. mains motor 230/250 volts complete with gear- **15/-** P. & P. box. 6 r.p.m. **4/-**. Similar to above motor but without gearbox. 9/6, P. & P. 3/-.

SILICON RECTIFIERS 250 v. P.I.V. 750 milliamps. Six for 7/6, post paid.

3 TO 4 WATT AMPLIFIER KIT


Comprising chassis 8½in. x 2½in. x 1in. Double wound mains transformer, output transformer. Volume and tone controls, resistors, condensers, etc. 6V6, ECC81 and metal rectifier. Circuit 1/6, free with kit. 29/6 plus 5/6 P. & P. The above Amplifier built and tested, 10/6 extra.

TRANSISTORISED SIGNAL GENERATOR

Size 5½in. x 3½in. x 1½in. For I.F. and R.F. alignment and A.F. output. 700 kc/s, frequency coverage 460 Kc/s to 2 Mc/s. in switched frequencies. Ideal for alignment to our Elegant Seven and Musette. Built and tested. 39/6. P. & P. 3/6.

POWER SUPPLY KIT

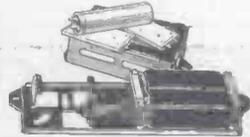A.C. Mains 200/250 v. Incorporating "C" core type mains transformer, full wave metal rectification and smoothing condenser. Smooth output 250 v., 250 mA and 6.3 v. 4 amp. for Heaters. **25/-** P. & P. 9/6.




BSR MONARCH UA16 With FULL-FI HEAD

4-speed, plays 10 records, 12in., 10in. or 7in. at 16, 33, 45 or 78 r.p.m. Intermixes 7in., 10in. and 12in. records of the same speed. Has manual play position; colour, brown. Dimensions: 12½ x 10½in. Space required above baseboard 4½in., below baseboard 2½in. Fitted with Full-Fi-turn-over crystal head. **£4. 19. 6** P. & P. 9/-.

Complete Amplifier Kit comprising E.C.L. 82 Mains transformer, metal rectifier, volume control, smoothing condenser, metal chassis, speaker, etc. To the purchasers of the above changer, only 19/6 plus 3/- P. & P.

CYLDON U.H.F. TUNER

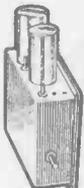Complete with PC.88 and PC.86 valves. Full variable tuning. New and unused. Size 4½in. x 5½in. x 1½in. Complete with circuit diagram Plus 3/6 P. & P. **35/-**




MAGNAVOX COLLARO

Set of three Tape Deck Motors 240 v. A.C. Three motors 49/6 P. & P. 6/-.

RADIO AND T.V. COMPONENTS (ACTON) LTD.

Goods not despatched outside U.K. All enquiries stamped addressed envelope. Terms C.W.O.

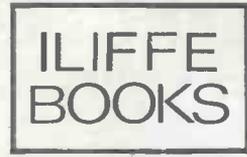21A HIGH STREET, ACTON, LONDON, W.3
SHOP HOURS 9 a.m.-6 p.m. EARLY CLOSING
WEDNESDAY



three important titles from

foundations of wireless

television explained

television engineering

M. G. SCROGGIE, B.Sc., M.I.E.E.
seventh edition

This standard work covers the whole basic theory and, starting from the most elementary principles and assuming no previous knowledge on the reader's part, deals with receivers, transmitters, amplification, valves, transistors, aerials, power supplies and transmission lines. The treatment of frequency changers has been brought into line with modern practice, while common-grid and cascade v.h.f. amplifiers, e.h.t. generators and transistor d.c. voltage raisers are also covered. 388 pp. illus. 21s net 22s 5d by post.

W. E. MILLER, M.A. (Cantab.), M.I.E.E.E. Revised by **E. A. W. Spreadbury, M.I.E.E.E., Technical Editor, Electrical and Electronic Trader.** seventh edition

Presents a step-by-step survey of the circuits of modern television receivers and aerial systems for multi-channel reception, assuming a knowledge of the ordinary sound radio receiver, but no previous knowledge of television circuits. It is non-mathematical, written in simple language, and comprehensively illustrated by many diagrams and photographs. 192 pp. illus. 12s 6d net 13s 6d by post.

Principles and Practice. A B.B.C. Engineering training manual. **S. W. Amos, B.Sc. (Hons.), A.M.I.E.E. and D. C. Birkinshaw, M.B.E., M.A., M.I.E.E.** second edition

Fundamentals, camera tubes, television optics, electron optics. Vol. 1 297 pp. illus. 45s net 46s 3d by post

Video frequency amplification. Vol. 2 270 pp. illus. 45s net 46s 3d by post.

Waveform Generation. Vol. 3 224pp. illus. 45s net 46s 3d by post.


General circuit techniques. Vol. 4 278pp. illus. 35s net 36s 3d by post.

available from leading booksellers

ILIFFE BOOKS LTD. DORSET HOUSE, STAMFORD STREET, S.E.1

WW-153 FOR FURTHER DETAILS.

3-VALVE AUDIO AMPLIFIER MODEL HA34

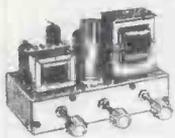

Designed for Hi-Fi reproduction of records. A.C. mains operation. Ready built on plated heavy gauge metal chassis, size 7 1/2 in. w. x 4 in. d. x 4 1/2 in. h. Incorporates EC83, EL84, EZ80 valves. Heavy duty, double wound mains transformer and output transformer matched for 8 ohm speaker, separate bass, treble and volume controls. Negative feedback line. Output 41 watts. Front panel can be detached and leads extended for remote mounting of controls. The HA34 has been specially designed for us and our quantity order enables us to offer them complete with knobs, valves, etc., wired and tested for only £4.5/- P. & P. 6/-.

HSL "FOUR" AMPLIFIER KIT

3-VALVE, 4 WATT USING EC83, EL84, EZ80 VALVES for A.C. mains 200/240v. Special features include: ★ Heavy duty double-wound mains transformer with electrostatic screen. ★ Separate bass, treble and volume controls, giving fully variable boost and cut with minimum insertion loss. ★ Heavy negative feedback loop over 2 stages ensures high output at excellent quality with very low distortion factor. ★ Suitable for use with guitar, microphone or record player. ★ Provision for remote mounting of controls or direct on chassis. ★ All this builds on to a chassis size only 7 1/2 in. wide x 4 in. deep. Overall height 4 1/2 in. ★ All components and valves are brand new. ★ Very clear and concise instructions enable even the inexperienced amateur to construct with 100% success. ★ Supplied complete with valves, output transformer (3 ohms only), screened lead, wire, nuts, bolts, solder, etc. (No extras to buy). PRICE 79/6. P. & P. 6/-. Comprehensive circuit diagram, practical layout and parts list 2/6 (free with kit). This kit is similar in appearance to HA34 but employs entirely different and advanced circuitry.


QUALITY RECORD PLAYER AMPLIFIER

A top-quality record player amplifier. This amplifier (which was used in a 29 gm. record player) employs heavy duty double wound mains transformer, EC83, EL84, EZ80 valves. Separate bass, treble and volume controls. Complete with output transformer matched for 8 ohm speaker. Size 7 in. w. x 4 1/2 in. d. x 5 1/2 in. h. Ready built and tested. PRICE 69/6. P. & P. 4/9. ALSO AVAILABLE mounted on board with output transformer and 6in. speaker ready to fit into cabinet below. PRICE 89/6. P. & P. 5/9.

QUALITY PORTABLE R/P CABINET

Unicist motor board. Will take above amplifier and B.S.R. or GARRARD Antichanger or Single Record Player Unit. Size 18 x 14 x 8 1/2 in. PRICE £23/9/6. Carr. 7/6.

STEREO AMPLIFIER

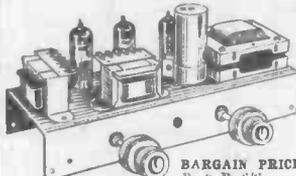

Incorporates 2 ECL86s and 1 EZ80; heavy duty, double wound mains transformer. Output 4 watts per channel. Full tone and volume controls. Absolutely complete.


BARGAIN PRICE ONLY £4/19/6. P. & P. 6/5.

SUPER DE LUXE version of above incorporating ECL86 valves, separate bass, treble and balanced controls. Controls and full negative feedback. 8 Gus. P. & P. 6/6.

HIGH GAIN 4-TRANSISTOR PRINTED CIRCUIT AMPLIFIER KIT Type TAI


● Peak output in excess of 14 watts. ● All standard British components. ● Built on printed circuit panel, size 6 x 3 in. ● Generous size driver and output transformers. ● Output transformer tapped for 8 ohm and 15 ohm speakers. ● Transistors (GET 114 or 81 Mullard OC81) and matched pair of OC81 o/p. ● 9 volt operation. ● Everything supplied, wire, battery, clips, solder, etc. ● Comprehensive easy to follow instructions and circuit diagram 1/6 (Free with Kit). All parts sold separately. SPECIAL PRICE 45/-. P. & P. 3/-. Also ready built and tested 52/6. P. & P. 3/-. A pair of TAIs are ideal for stereo.

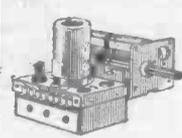ANOTHER HARVERSON SCOOP! FM/AM TUNER HEAD



Beautifully designed and precision engineered by Dorrner and Wadsworth, Ltd. Supplied ready fitted with twin .005 tuning condensers for AM conversion. Prealigned FM section covers 86-102 Mc/s. I.F. output 10.7 Mc/s. Complete with EC835 (6L12) valve and full circuit diagram of tuner head. Another special bulk purchase enables us to offer these at 27/6 each. P. & P. 3/-. Order quickly! Limited number also available with precision geared 3:1 reduction drive. 30/-. P. & P. 3/-. MACHED PAIR AM FM I.F.s, Comprising 1st I.F. and 2nd I.F. discriminator. (465 kc/s / 10.7 Mc/s). Size 1 in. x 1 1/2 in. x 2 1/2 in. high. Will match above tuner head. 11/- pair. P. & P. 2/-.

10/14 WATT HI-FI AMPLIFIER KIT

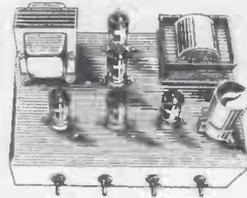

A stylishly finished mono-audio amplifier with an output of 14 watts from 2 EL84s in push-pull. Super reproduction of both music and speech, with negligible hum. Separate inputs for mike and gram allow records and announcements to follow each other. Fully shrouded section wound output transformer to match 8-15Ω speaker and 2 independent volume controls, and separate bass and treble controls are provided giving good lift and cut. Valve line-up: 2 EL84s, EC83, EF86, and EZ80 rectifier. Simple instruction booklet 1/6 (Free with parts). All parts sold separately. ONLY 27/9/6. P. & P. 8/6. Also available ready built and tested complete with standard input sockets. £9/5/- P. & P. 8/6.

4-SPEED PLAYER UNIT BARGAINS

All brand new in maker's original packing. SINGLE PLAYERS. Carr. 5/6 on each.

B.S.R. TU/12	£3 9 6
B.S.E. GU7 with unit mounted pick-up arm	£4 18 8
Garrard SP25 de luxe	£12 10 6
E.M.I. with unit mounted pick-up arm	£4 9 8

AUTO. CHANGERS. Carr. 6/6 on each.

Latest B.S.R. UA25 Super slim	£6 2 6
GARRARD AT6	£9 10 0
GARRARD 1000 with special HIFI cartridge	£6 19 6

All the above units are complete with 1/0 mono head with sapphire styl or can be supplied with stereo head at 12/6 extra.

B.S.E. MONARDECK (Single speed) 3 1/2 in. per sec., simple control uses 5 1/2 in. spools. £6/15/-, plus 7/6 carr. and ins. Tapes extra. ACOS CRYSTAL MIKES. High imp. For deck or band use. High sensitivity. 18/6. P. & P. 1/6.

TSI CRYSTAL STICK MIKE. 12/6. Our price 18/6. P. & P. 1/6. QUALITY PORTABLE TAPE RECORDER CASE. Brand new. Beautifully made. Few only at 49/6. P. & P. 5/-.

WELL-KNOWN MAKER'S SURPLUS!

ONE TRANSISTOR PRE-AMP Suitable for use with Medium or High Impedance mikes, guitars, gram, pick-ups, tape decks, etc.; for operation from 200/300 volt H.T. rail or 9-volt battery. Gain approx. 14:1. Fully isolated input by hi-metal screened transformer. Size 4 1/2 in. x 1 1/2 in. x 1 in. Ready built complete with full circuit diagram and instructions. ONLY 15/- Post free.

Open all day Saturday
Early closing Wed. 1 p.m.
A few minutes from South Wimbledon
Tube Station.

HARVERSON SURPLUS CO. LTD.
170 HIGH ST., MERTON, LONDON, S.W.19 CHerrywood 3985
SEND STAMPED ADDRESSED ENVELOPE WITH ALL ENQUIRIES

(Please write clearly)
PLEASE NOTE: P. & P. CHARGES
QUOTED APPLY TO U.K. ONLY.
P. & P. ON OVERSEAS ORDERS
CHARGED EXTRA.



EDDYSTONE EC10

ALL TRANSISTOR RECEIVER

55 to 30 mc/s CONTINUOUS

£48 Send for full specification

H.P. Dep. £16-12 mths @ £17-4 (Tot H.P. £50-8-0) 24 Mths Available

Sensitivity 5 Microvolts for 15 dB S/N Ratio, Image Rejection 50 dB at 2 mc/s and 20 dB at 18 mc/s.

I.F. Breakthrough 85 dB down Range 1-4, 65 dB down Range 5

SOUTH COAST EDDYSTONE CENTRE

COSH & HAMMOND

29 BEACH RD., LITTLEHAMPTON, SUSSEX. Tel: 877/8

EXPORT WELCOMED — FULL RANGE IN STOCK — COMPONENTS

WW-154 FOR FURTHER DETAILS.

BENTLEY ACOUSTIC CORPORATION LTD.

38 CHALCOT ROAD, CHALK FARM, LONDON, N.W.1 THE VALVE SPECIALISTS Telephone PRIMROSE 9090

47 NORFOLK ROAD, LITTLEHAMPTON, SUSSEX. Littlehampton 2043

Please forward all mail orders to Littlehampton


ALL GOODS LISTED BELOW IN STOCK

0A2	5/8	10C1	12/8	DF97	10/8	ELL80	14/-	QQV03/10	MIDGET
0B2	6/-	10C2	12/-	DR76	3/8	EL822	22/6	30/-	SILICON
0Z4GT	4/3	10D2	11/3	DX40	15/8	EM71	14/-	0Q04/7	RECTI-
1A5	5/-	10F1	9/8	DK91	4/-	EM80	8/-	R10	TIERS
1A7GT	7/-	10F9	9/-	DK92	8/-	EM81	7/-	R16	Type
1C5	4/8	10F18	7/8	DK96	7/8	EM84	5/8	R18	BY100
1D5	6/8	10P13	12/-	DL94	5/-	EM85	12/-	R19	Output
1D6	9/8	10P14	13/-	DL96	6/8	EM87	6/8	BK34	250 v. at
1EGGT	6/9	12A5	2/3	DL810	10/8	EY61	5/8	SF61	amp.
1L4	2/3	12AC6	8/8	DM70	5/-	EY81	7/3	SU25	27/2
1LD5	4/-	12AD6	9/6	DM71	9/8	EY83	9/3	T41	9/-
1LN5	4/6	12AE6	8/-	DY86	6/3	EY84	9/3	TDD4	7/6
1N5GT	7/8	12AT6	4/6	DY87	6/3	EY85	5/9	TH48	10/-
1R5	4/-	12AT7	3/6	E96F	24/-	EY87	6/8	TH233	8/9
1R4	5/-	12AX7	4/6	E80C3	33/-	EY88	9/8	T22	6/8
1R5	2/3	12AX7	4/6	E83F	24/-	EY91	3/-	TP25	5/-
1T4	2/6	12AU6	5/8	E88OC	12/-	EZ40	5/8	TP2620	7/6
1U4	5/8	12AV6	5/8	E180F	19/6	EZ41	6/3	TY8611/10	AA129
1U5	5/3	12BA6	8/3	KA60	1/6	EZ80	3/8	UI2/14	4/6
2D21	5/6	12BE6	4/8	EA76	6/3	EZ81	4/3	UI6	15/-
2X9	2/-	12BH7	6/-	EABC80	6/9	FC4	8/8	UI8/20	6/8
3A4	3/9	12E1	16/8	EAC91	3/3	GZ33	12/6	UI9	48/6
3A5	8/-	12J7GT	7/3	EAF42	7/6	GZ34	10/-	U22	5/9
3B7	5/-	12K5	10/-	EB34	1/-	G23	14/8	U25	11/-
3D6	3/9	12K7GT	3/6	EB41	4/8	HABC80	9/3	U26	8/6
3E4	5/3	12K8GT	8/8	EB42	5/3	HLA1D	5/8	U27	6/8
3Q5GT	6/6	12Q7GT	3/6	EB33	6/6	HLA19	19/6	U33	13/6
3R4	4/3	12S4GT6/9		EB44	6/6	HLA2DD	5/8	U35	16/6
3V4	5/-	128C7	4/-	EBC81	6/3		19/8	U37	34/11
3E4GY	8/8	128K7	3/-	EBC82	6/3	HN309	28/-	U45	15/6
5U4G	4/8	128Q7GT8/9		EBF83	7/3	HVR2	8/8	U76	4/6
5V4G	8/-	13D3	8/-	EB41	4/8	HVR24	5/8	U81	13/6
5Y3GT	4/9	14H7	9/6	EBL21	10/3	KT39C	6/-	U91	10/6
5Z3	6/6	1487	19/8	EC62	4/3	K739	29/1	U281	8/8
5Z4G	7/6	19A05	7/3	EC54	6/3	KT41	19/6	U282	12/6
6A80	5/9	20D1	10/-	EC91	4/6	KT44	5/-	U301	12/6
6A82	2/6	20B	2/6	EC92	6/6	KT61	2/6	U329	9/8
6AC7	5/9	20F2	11/8	ECC31	15/6	KT63	3/9	U403	9/9
6AK5	4/9	20L1	14/-	ECC32	4/6	KT66	12/3	U404	6/-
6AM4	16/6	20P1	17/6	ECC33	29/1	KT88	28/-	U401	18/-
6AQ5	4/9	20P3	18/-	ECC34	29/1	KTW61	4/9	U4020	6/8
6ATW	4/9	20P4	18/-	ECC35	4/6	KTW62	5/8	UABC80	5/8
6AUG	5/9	20P5	15/-	ECC36	4/6	KW12D	12/6	UB41	10/6
6AV6	5/6	25A6G	7/6	ECC81	3/8	MU14	4/6	UBC41	6/6
6B8Q	2/6	25L6	4/8	ECC82	4/6	N37	28/3	UBC81	6/6
6BA6	4/6	25Z4G	6/8	ECC83	4/6	N78	37/10	UBF80	5/6
6B6	4/3	25Z6GT	3/-	ECC84	5/8	N83	25/2	UBF81	3/8
6B6G	5/3	30C15	10/6	ECC85	8/8	N339	25/-	UBL21	19/9
6BQ7A	7/6	30C17	11/6	ECC189	9/-	PABC80	7/6	UC92	6/8
6BR7	8/3	30C18	7/6	ECC80715-		PCC8	8/8	UCC84	8/8
6BR8	8/3	30F2	12/-	ECC80	7/3	PCC8	8/8	UCC85	6/8
6BR7	16/8	30FL1	13/-	ECC82	6/3	PC95	6/8	UCF80	8/3
6BW6	7/6	30FL4	12/8	ECC83	10/-	PC92	8/8	UCF81	8/8
6BW7	5/-	30L1	6/8	ECC84	5/8	PC90	9/8	UCF82	8/8
6C9	10/9	30L15	12/8	ECC85	7/8	PC94	5/8	UCF83	6/8
6C9D6	22/-	30L17	11/8	ECC86	6/8	PC85	6/8	UCL82	7/3
6C86	9/-	30P4	10/-	ECC87	6/8	PC88	10/8	UCL83	9/8
6CW1	11/-	30P12	10/-	ECC88	5/8	PC89	11/8	UF41	7/9
6D3	9/6	30P19	13/8	ECC89	7/8	PC818	9/8	UF80	6/8
6E5	9/6	30P11	13/8	ECC84	9/-	PCF80	6/8	UF80	6/8
6F1	9/6	30P13	13/8	ECC85	6/8	PCF82	6/8	UF85	6/8
6F6G	3/9	30P14	13/8	ECC82	6/8	PCF84	8/8	UF86	9/8
6F13	3/9	30P15	13/8	ECC83	10/-	PCF86	6/8	UF89	5/8
6F29	9/-	35A8	8/8	ECC80	7/8	PCF80	11/-	UF81	3/8
6H24	10/-	35LAGT	8/3	ECC180		PCF81	3/-	UL46	9/8
6J5G	3/9	35W4	4/6		30/3	PCF82/10/-		UL84	5/6
6J6	3/-	35Z3	10/-	EF9	20/6	PCF85	7/8	UM4	17/6
6J7G	4/6	35Z4GT	4/6	EF22	6/6	PCF86/12/-		UM34	17/6
6K7G	1/3	35Z5GT	5/8	EF26	3/6	PCF88	10/8	UM80	8/3
6K8G	3/3	50B5	6/8	EF3A	6/8	PCF82	6/8	UR10	6/8
6K8GT	8/6	50C5	6/8	EF39	5/-	PCL83	9/8	UUG	19/6
6K25	24/-	50CD6G40/9		EF40	8/8	PCL84	7/8	U07	19/6
6L1	10/-	50L6GT	6/8	EF41	9/-	PCL85	3/8	U08	16/6
6LAGT	7/8	72	6/8	EF42	3/8	PCF86	8/8	UY1N	10/3
6LGTM	8/8	80	5/3	EF50	2/8	PEN45	7/-	UY21	9/8
6L18	10/-	85A2	6/8	EF54	3/-	PEN45DD		UY41	5/-
6LD20	6/8	90AG	67/8	EF73	5/-			UY85	4/8
6N7GT	7/-	90AV	67/8	EF80	4/3	PEN383	9/8	VM84B	12/-
6P29	25/-	90CG	34/-	EF88	9/8	PEN45DD		VP4	14/8
6Q7G	5/8	90CV	33/8	EF86	4/8			VP4B	12/-
6Q7GT	9/9	90C1	18/-	EF86	6/8	PENDD		VP19C	7/-
6R7G	5/6	150B2	16/6	EF89	4/6			VP41	5/-
6R7GT	4/9	607	11/9	EF91	3/-	PPL20014/6		VP133	9/8
6R7GT	4/8	5765	7/8	EF92	2/8	PL33	9/-	VP105	5/8
6R7GT	4/8	A1834	20/-	EF97	10/-	PL36	9/-	VP150	4/8
6R7GT	4/8	AC/VP2	12/-	EF98	9/8	PL38	19/9	VP18A	7/8
6R7GT	4/8	AC/TH1	12/-	EF183	6/8	PL81	7/9	VP111	5/-
6UGT	9/8	EF184	6/8	EF184	6/8	PL82	5/3	VP120	10/-
6UG6	5/-	AZ1	8/8	EF20	9/8	PL83	6/8	VP133	7/8
6V8GT	5/8	AZ31	7/8	EF32	6/9	PL84	6/3	W61	3/6
6X4	3/9	AZ41	6/8	EL32	6/9	PL500	1/4	W81M	10/8
6X5GT	5/3	B36	4/9	EL33	6/8	PX4	9/-	W729	17/6
6Y6G	10/8	B349	12/6	EL34	9/8	PY31	6/9	X41	10/-
6Y6GL2	8/9	B729	8/9	EL36	8/8	PY32	8/9	X61	6/8
7B	12/8	B732	10/8	EL41	7/8	PY33	3/8	Y13met	10/8
7B7	7/-	COH35	17/8	EL42	9/8	PY80	4/9	X86	5/8
7C6	6/9	CV31	5/9	EL81	8/-	PY81	5/-	X66	7/6
7H7	5/9	D15	13/6	EL83	6/8	PY82	4/9	X76M	8/6
7H7	12/8	DAP91	3/3	EL84	4/6	PY83	5/6	X78	26/2
7Y4	5/-	DAP96	8/6	EL85	7/6	PY88	7/3	X79	40/8
9B6	6/8	D4	10/8	EL86	4/8	PY800	6/9	X81M	29/8
9B6G	6/8	DF66	15/-	EL91	2/8	PY801	6/3	Y63	5/-
9D7	7/6	DF96	6/8	EL95	5/-	QP21	5/-	Z66	7/3

All goods are new, first quality brands only, and subject to maker's full guarantee. We do not handle manufacturers' seconds nor rejects, which are often described as "new and tested" but have a limited and unreliable life. Terms of business: Cash with order only. Post/packing 6d. per item. Orders over £5 post/packing free. All orders cleared on day of receipt. Any parcel insured against damage in transit for only 6d. extra. Callers welcome Mon.-Fri. 9-5 p.m. Sat. 9 a.m.-1 p.m. Complete catalogue of valves, transistors and components with conditions of sale, price 6d.


MARCONI CANADIAN TRANSMITTER RECEIVER GROUND STATION No. 52

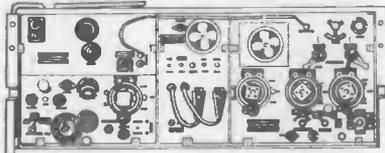WORLD WIDE RECEPTION SHIPPING AMATEUR BROADCAST. Comprises: Receiver, Transmitter and Power Unit for 12 v. D.C. operation. Frequency coverage: 1.75-16 Mc/s. (19-170 metres) in 3 fully tunable switched wavebands.



Power output 75 watts R.T.: 110 watts C.W.

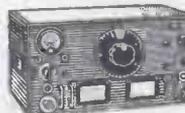Above items also available separately (less carrier). No. 52 Receiver only £9/19/6. Carr. 20/-. No. 52 Transmitter only £9/10/-. Carr. 20/-. No. 52 Power Unit only £9. Carr. 20/-.




NATIONAL HRO SENIOR RECEIVERS 5T MODEL

In excellent tested condition. Available with 9 coils coverage 50 kc/s. to 30 Mc/s. complete with PSU, £31/10/- Carr. 30/-.

RCA AR88 RECEIVERS

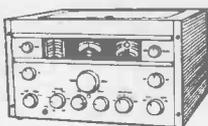Freq. 540 kc/s.-32 Mc/s. 6 waveband, mechanical bandspread with logging scale, auto. and manual vol. control, and Noise Limiter, BFO, Pitch and Var. HF Tone Controls. FR and AF Gain, Var. Selectivity with crystal filter. Used models. Fully tested and working. MODEL D £40. MODEL LF, £35. Carr. £2 on each.



R.1475 RECEIVERS (TYPE 8B)

Highly stable, especially accurate, calibrated Marconi design R.A.F. Communication Receiver covering 2-20 Mc/s. in 4 bands with built-in 609 kc/s. xtal reference oscillator for checking dial which can be reset by special panel trimmer control. 11 valves: 3-6K7, 6K8, 6J5, 3-6Q7, 686, Y63 tuning indicator and VR150/30 voltage regulator. Two-stage I.F. with 8 tuned circuits. Xtal controlled B.F.O., 4 position selectivity with audio filters for narrow bandwidth. C.W. Fast and slow A.V.C. High and low suppression. A plug-in unit with additional mixer provides a "listening through" guard channel of either 2-4 or 4-7.5 Mc/s. Receiver 16 1/2 x 9 x 11in. Very good condition. PRICE £9/19/6. Carr. 15/6.



TELESCOPIC AERIAL MASTS

Tubular steel coppered spray finish, ring cam locking on each section provides for full or any height required. Suitable all fixings and base locations. Bottom section 1 1/2in. diameter, 20ft. (4 section). Closed 5ft. 9in. Weight 16 lb., 55/- Carr. 5/-; 34ft. (6 section). Closed 6ft. 6in. Weight 20 lb., 75/- Carr. 5/-; Further height by adding 3-4ft. Whip sections, 13/6. Carr. 4/-. Special price for quantities.

ALL 19 SETS AND PARTS AVAILABLE

S.A.E. all enquiries. List 1/- (Credit terms available, U.K. only)

A. J. THOMPSON (DEPT. W.W.)
"ELING LODGE," CODICOTE, HITCHIN, HERTS. Tel. Codicote 242

WW-155 FOR FURTHER DETAILS.



AERO SERVICES LTD

PEN RECORDERS



Elliott portable recording milliammeters.
As D.C. recorder: 1 mA. F.S.D. Movement resistance 1200Ω.
As A.C. current or voltage recorder: Movement resistance at 60 c/s. 1800Ω. Sensitivity 1 mA. A.C. F.S.D.
As decibel meter: source impedance 600Ω. Range +5 to -10 dB. Frequency response 50 c/s to 16 kc/s.
Chart drive: 230 v. A.C. at 1in. and 6in. per hour. Movement is fitted with "high" and "low" alarm contacts which can be set for any value of the current.
Strip chart 3 1/2 in. wide. Curvilinear trace. PRICE £40
Packing and carriage 15/-.

RECORD PORTABLE RECORDING MILLIAMMETERS

These are similar to the above but are somewhat smaller and lighter, and D.C. resistance of the movements is 400Ω. Other details as above. PRICE £42 10 0
Packing and carriage 15/-.

THOMSON VARLEY POTENTIAL DIVIDERS

Non-inductive 4-decade potential divider with total resistance of 70,000Ω. Maximum input voltage 300 v. Built-in galvanometer 1μA. F.S.D. £45.



TYPE 108-IT MULTIMETER

24-range precision portable meter
5,000 o.p.v. D.C. Volts 2.5-10-50-250-500-2500 V. A.C. Volts: 10-50-100-250-500-2500 V. D.C. current 0.5-5-50-500 mA. Resistance: 2,000-20,000 ohms-2 MΩ. 20 megohms. Power output calibration for 600 ohms line. £5/5/-.
P.P. 7/6. Dimensions: 7 1/2 in. x 6 in. x 3 1/2 in. Weight 3 1/2 lb.

SPECIAL OFFER OF METERS

(Subject to remaining unsold).

900μA D.C. M.C. 2 1/2 in. round flange mounted	15/-
500μA D.C. M.C. 1 1/2 in. round flush, nut fixing, scaled 0-1	15/-
500μA D.C. M.C. 2 1/2 in. round flush, nut fixing, scaled 0-5	15/-
800-0-800 μA D.C. M.C. 3 1/2 in. round flange mounted, scaled 50-0-50, second hand	10/-
1 mA. D.C. M.C. 1 1/2 in. round flush, panel mounted	15/-
1 mA. D.C. M.C. 2 1/2 in. round flush, scaled 0/3/30/300	15/-
1 mA. D.C. M.C. 2 1/2 in. square flange mounted	15/-
10-0-10 mA. D.C. M.C. 2 1/2 in. round flange mounted	15/-
30 mA. D.C. M.C. 2 1/2 in. round flange mounted	10/-
50 mA. D.C. M.C. 2 1/2 in. round flange mounted	10/-
75 mA. D.C. M.C. 1 1/2 in. round flush, panel mounted	10/-
100 mA. D.C. M.C. 1 1/2 in. round flush, panel mounted	10/-
100 mA. D.C. M.C. 1 1/2 in. round flange, mounted	12/6
100 mA. D.C. M.C. 2 1/2 in. round flange mounted	15/-
150 mA. D.C. M.C. 1 1/2 in. round flush panel mounted	10/-
200 mA. D.C. M.C. 2 1/2 in. round flange mounted	10/-
500 mA. D.C. M.C. 2 1/2 in. round flange mounted	10/-
500 mA. D.C. M.C. 2 1/2 in. round flange mounted	10/-
500 mA. R.F. Thermocouple 2 in. round plug-in	12/6
25 amps. D.C. M.C. 3 1/2 in. round projecting	10/-
100 amps. A.C. 3 1/2 in. round flush panel mounted	10/-
8 v. D.C. M.C. 1 1/2 in. round flush mounted, battery condition indicator, suppressed zero. reading from 4.5 v. up	10/-
15 v. A.C. M1 2 1/2 in. round flange mounted	15/-
20 v. D.C. M.C. 2 1/2 in. square flange mounted	15/-
300 v. A.C. Rectifier Type. 2 1/2 in. round flange mounted	15/-

"ELECTRON" OUTDOOR AERIAL

3 strong tubular light alloy sections 3ft. long each on an insulated aerial base fitted with wall mounting bracket. Complete with down lead. PRICE, brand new, 15/- P.P. 5/-.

PLESSEY ELECTROLYTIC CAPACITORS

24μF at 275 V.	2/-	100-40μF at 275 V.	3/6
200μF at 275 V.	2/6	100-20-5-25μF (100-20-20-20μF at 450 V.	3/-
		at 350 V., 5μF at 50-100μF at 275 V.	3/-
		50 V., 25μF at 25 V.)	3/6

All voltages are D.C. working. Postage 2/- per order.

RADIO FREQUENCY THERMOCOUPLE METERS

Scaled 0 to 1 AMP. 2 1/2 in. round projecting. 12/6
Packing and postage 2/6 per order.

POWER UNITS TYPE 234

19in. rack mounted fully smoothed and fused for 230 v. A.C. input. I.T. output adjustable from 180 v. to 270 v. at 30 mA. by means of primary taps and high-low switch in the secondary winding. L.T. output 6.3 v. A.C. at 4 amps. Fitted with M.1 meter to read A.C. input and D.C. output volts. Second-hand tested, in good condition £3 19 6
DITTO model without meter £3 10 0
No. 10 Assembly.
Packing and carriage 15/-.

HEADPHONES

DLR5, Low Impedance, balanced armature. Earpieces can be used as sound powered telephone, 10/-
CHH, High Impedance (2000Ω per insert), 15/-.

Moving Coil Headphones with moving coil Hand Microphone fitted with press-to-talk switch. Rubber earpads. Cord terminated with army type 5-point moulded connector. Low impedance. Brand new, 20/- ea.
Small quantity available of second hand assemblies, checked in perfect order. 3/6 ea. P. & P. 3/6 per set.

MAGNETRONS

4J30	700/-	CV370	250/-	CV5117	200/-
4J33	250/-	CV1495 to		JP79-01	
5J26	500/-	CV1500	160/-		1200/-
		CV2821	300/-	M548	250/-
CV160	160/-	CV3691	250/-	QK338	1200/-

KLYSTRONS

2K25	130/-	726A	80/-	BL803	500/-
2K28	180/-	5721	1000/-	CV120	80/-
2E41	400/-	8838	500/-	CV228	200/-
6BM6	280/-	6116	600/-	CV237	80/-
417A	40/-	6470	1500/-	VA290E	700/-
707B	60/-	BL800	400/-		

ZENER DIODES

Voltage	Type	Power	Price
3.0V ± 5%	Z2339P	200 mW	5/-
4.25 ± 10%	VR425B	2.25 W	6/6
4.30 ± 15%	OA2208	260 mW	6/6
4.7 ± 5%	AN2300	260 mW	10/-
4.7 ± 10%	OA2209	260 mW	6/6
4.75 ± 8%	VR475B	2.25 W	6/6
5.1 ± 5%	OA2210	260 mW	9/6
5.6 ± 5%	OA2242	230 mW	7/6
5.6 ± 5%	OA2292	260 mW	7/-
5.75 ± 6%	VR575B	2.25 W	6/6
6.2 ± 13%	OA2203	260 mW	7/0
6.8 ± 5%	OA2206	260 mW	6/-
6.8 ± 5%	OA2204	260 mW	7/-
6.8 ± 5%	OA2224	7.0 Watts	10/-
7.0 ± 8%	VR7A	2.25 W	8/-
7.5 ± 5%	OA2205	260 mW	7/-
7.5 ± 15%	OA2211	260 mW	6/-
8.2 ± 8%	OA2205	260 mW	7/-
9.1 ± 5%	OA2207	260 mW	9/6
9.1 ± 13%	OA2212	260 mW	6/6
11.0V ± 5%	VR11A	5.25 W	8/-
12.0V ± 5%	K844B	300 mW	8/-
12.0V ± 15%	OA2206	260 mW	6/6
13.0V ± 5%	VR13A	5.25 W	8/-
18.0V ± 10%	BZ290	400 mW	7/6
20.0V ± 5%	ZN290	1.5 W	9/6
80.0 ± 5%	BZ111	250 mW	6/6
80.0V ± 5%	BZ113	250 mW	6/6

TEXAS SILICON FULL-WAVE BRIDGE RECTIFIERS

1P20K10 100 p.i.v. 2 amps. dimensions 1.4 x 1.4 x .6in. 25/-
1B40K10 100 p.i.v. 4 amps. dimensions 1.4 x 1.4 x .6in. 30/-
1B100M10 100 p.i.v. 10 amps. dimensions 2 1/2 x 2 1/2 x 1in. 85/-
Postage 1/6 per rectifier.

GERMANIUM POINT CONTACT DIODES

1N34A	4/-	OG618	1/6	OA70	2/-
1N38A	4/-	GEX93	1/6	OA79	2/3
1N69	4/6	GEX44	1/6	OA81	2/-
1N72	4/-	GEX64	2/-	OA86	3/6
1N81	4/-	HG6008	2/-	OA90	2/-
CG42	2/-	OA5	4/6	OA91	2/3
CG19E	1/6	OA5	4/-	OA95	3/-
CG12E	2/-	OA7	4/6	S917G	2/-
CG61H	3/-	OA47	4/-		

PLEASE REFER US YOUR SURPLUS STOCK OF VALVES, KLYSTRONS, ETC. WE URGENTLY REQUIRE KLYSTRONS 726A/B AND 2K25. 30/- PAID FOR EACH SUBJECT TO TEST.

DECADE COUNTER TUBES

GC10B	scale-of-ten counter (I.O.)	35/-
GC 10/4B	bi-directional 10-way computing (I.O.)	45/-
GC10D	scale-of-ten counter for single pulse operation (I.O.)	47/6
G810C	bi-directional 10-way selector tube (B12E)	42/-
G810D	bi-directional 10-way selector tube (B12E)	50/-
G810E	bi-directional 10-way selector tube (B12E)	55/-
G810H	bi-directional 10-way selector tube with routing guides (B17E)	40/-

S.T.C. SILICON JUNCTION 3 AMP. HALF-WAVE POWER RECTIFIERS

R8320	280 p.i.v.	5/-	R8360	840 p.i.v.	8/6
R8330	420 p.i.v.	6/-	R8370	980 p.i.v.	9/-
R8340	560 p.i.v.	7/-	R8380	1120 p.i.v.	10/-
R8350	700 p.i.v.	7/6			

MISCELLANEOUS SILICON HALF-WAVE POWER RECTIFIERS

18001	200 p.i.v., 750 mA. Wire Ended	3/6
18004	600 p.i.v., 750 mA. Wire Ended	7/-
18113	400 p.i.v., 400 mA. Wire Ended	7/-
18115	600 p.i.v., 400 mA. Wire Ended	12/6
BY100	700 p.i.v., 450 mA. Wire Ended	7/-
BY210	See BL900	
BY213	200 p.i.v., 6 amps. Stud Mounted	7/6
DD008	400 p.i.v., 500 mA. Wire Ended	7/6
DD058	800 p.i.v., 600 mA. Wire Ended	7/6
DD226	400 p.i.v., 1 amp. Wire Ended	6/6
OA210	400 p.i.v., 600 mA. Wire Ended	6/6
OA211	800 p.i.v., 400 mA. Wire Ended	6/6
R820AF	40 p.i.v., 300 mA. Wire Ended	6/6
R826AF	500 p.i.v., 100 mA. Wire Ended	3/6
R827AF	600 p.i.v., 100 mA. Wire Ended	4/-
R828AF	800 p.i.v., 100 mA. Wire Ended	5/-
R8290AF	800 p.i.v., 750 mA. Wire Ended	5/6
SL102A	100 p.i.v., 2.4 amps. Stud Mounted	7/6
SL500	800 p.i.v., 6 amps. Stud Mounted	9/-

MICROWAVE DIODES

1N21	3,000 mc/s.	4/-	CS10BR	12,000 mc/s.	70/-
1N21H	3,000 mc/s.	6/-	CV101	6,000 mc/s.	5/-
1N23	3,375 mc/s.	4/-	CV102	6,000 mc/s.	5/-
1N23B	3,375 mc/s.	6/-	CV111	12,000 mc/s.	8/-
1N23CR	3,375 mc/s.	20/-	CV112	12,000 mc/s.	8/-
1N25	1,000 mc/s.	15/-	CV291	6,000 mc/s.	12/-
1N28	3,060 mc/s.	20/-	CV226	12,000 mc/s.	30/-
CR2A	4,000 mc/s.	5/-	CV228	12,000 mc/s.	40/-
CS3A	10,000 mc/s.	12/6	CV235	12,000 mc/s.	100/-
CS3B	12,000 mc/s.	24/-	SM2	12,000 mc/s.	37/6
CS4B	12,000 mc/s.	35/-	SM5	12,000 mc/s.	37/6
CS8B	12,000 mc/s.	30/-	VX3136	34,860 mc/s.	65/-
CS10B	3,375 mc/s.	70/-			

CATHODE RAY TUBES

VCR139A	2 1/2 in. green trace, medium persistence, 500 v. E.H.T. (B12B)	30/-
3CP7	3 1/2 in. yellow trace, long persistence screen, E.H.T. 2,000 v. with P.D.A. (B14A)	20/-
3GP1	3 1/2 in. green trace, medium persistence, E.H.T. 1,500 v. (U8M11)	40/-
3WP4	3 1/2 in. white trace, flat face, medium persistence, 1,500 v. E.H.T. (B12A)	120/-
4GP4	4 in. white trace, 4 in. flat face, medium persistence, with P.D.A.; 4,000 v. E.H.T. (B12F)	100/-
5ADP16	5 1/2 in. blue trace, short persistence, flat face, with P.D.A.; 3,000 v. E.H.T. (B14A)	160/-
5BP1	5 1/2 in. green trace, medium persistence, max. E.H.T. 2,000 v. (U8M11)	80/-
5BVP1	5 1/2 in. green trace, flat face, medium persistence, P.D.A., max. E.H.T. 8,000 v. (B12F)	160/-
5CP1	5 1/2 in. green trace, medium persistence, with P.D.A.; 4,000 v. E.H.T. (B14A)	40/-
5CP7A	5 1/2 in. yellow trace, long persistence screen, with P.D.A.; 4,000 v. E.H.T. (B14A)	100/-
5UP7	5 1/2 in. yellow trace, long persistence screen, MAGNETIC/DEFLECTION, electrostatic focussing, 4,000 v. E.H.T. (B14A)	60/-
7BP7	7 in. yellow trace, long persistence screen, MAGNETIC DEFLECTION AND FOCUSING, 7,000 v. E.H.T.	50/-
89J	4 in. double beam, blue trace, flat face, short persistence, 2,000 v. E.H.T. (special)	60/-
90G4E	3 1/2 in. green trace, medium persistence, P.D.A., max. E.H.T. 4,000 v. (B12D)	180/-
CV1547	3 1/2 in. orange trace, long persistence, with P.D.A., E.H.T. 4,000 v. (B12D)	100/-
1Q7-5	2 1/2 in. green trace, medium persistence, 800 v. E.H.T. (B94)	55/-
E4005C/T	2 1/2 in. green trace, long yellow after glow, E.H.T. 800 v. (B12B)	65/-
09D	4 in. twin beam, green trace, medium persistence, E.H.T. 1,200 v. (B12B)	80/-
09J	as 09D but blue trace, short persistence (B12B)	80/-
VR138	3 1/2 in. green trace, medium persistence, 1,200 v. E.H.T. (B12D)	50/-
VCR417B	yellow trace, long persistence, 3,000 v. E.H.T. (B12D)	60/-
Bases:	U8M11 6/6; B12A 3/-; B12B 2/6; B12D 3/6; B12F 7/6; B14A 6/6.	

Head Office:

44a WESTBOURNE GROVE, LONDON, W.2.

Tel: PARK 5641/2/3

Cables: ZAERO LONDON

Retail branch (personal callers only)

85 TOTTENHAM COURT RD.,

LONDON W.2. Tel: LANGham 8403

A. R. B. Approved for inspection and release of electronic valves, tubes, klystrons, etc.

Please send all enquiries, correspondence and Mail orders to Head Office



TRANSISTORS

Table listing various transistor models and their specifications, including AC176, AC128, 2N1132, etc.

Our new catalogue of valves, tubes and semiconductor is now ready. Apart from listing prices of several thousand types we keep in stock it is a work of reference providing short specifications of semiconductor and special tubes. Please send foolscap S.A.E. (6d. stamp please).

AC176 is complementary to AC128; 2N1132 is complementary to 2N697

Main table listing a wide variety of electronic components including diodes, tubes, and other parts with their respective part numbers and specifications.

WHEN ORDERING BY POST PLEASE ADD 2/6 IN £ FOR HANDLING AND POSTAGE. MINIMUM CHARGE 2/-



in handy dispensers for easy use

The most useful aid to soldering produced for many years. The solder wire is ingeniously coiled within the dispenser for easy withdrawal, and at the same time keeping it tangle-free. Dispensers keep solder free from dirt and grease and often act as a third hand whilst soldering.



SIZE 5

Contains 12 ft. of 18 s.w.g. Savbit Alloy in a continuous coil. For general electrical work. 2/6 each (subject)

NEW! SIZE 15

Contains 21 ft. coil of 60/40 Alloy, 22 s.w.g. Ideal for small components, transistors, diodes, etc. Bubble packed. 3/- each (subject)



Essential Accessories



MODEL 8 BIB WIRE STRIPPER & CUTTER

Strips insulation without nicking wire. Cuts wire cleanly. Splits plastic twin flex. 8 gauge selector. Plastic covered handles. 8/6 each (subject)

BIB PROFESSIONAL RECORDING TAPE SPLICER



For quick and accurate editing. Precision made, chrome plated, complete with razor cutter. 18/6 each (subject)

There is a full range of other special pre-packed Ersin Multicore Solder products and Bib Accessories available.

Details from your dealer or write to:
MULTICORE SOLDERS LTD
Hemel Hempstead, Herts.

Telephone: Hemel Hempstead 3636
WW—158 FOR FURTHER DETAILS.



RE-SETTABLE HIGH SPEED MAGNETIC COUNTERS. (3½ x 1 x ¾ in.), 3 digit, 24 v. 22/6 each. P.P. 1/6.
HIGH SPEED MAGNETIC COUNTERS. (4 x 1 x 1 in.), 4 digit. 12/24/48 v. (state which), 6/6 ea. P.P. 1/-.
SANGAMO GEARED MOTOR. 1 r.p.m. 240 v., 27/6 ea.
COPPER LAMINATE PRINTED CIRCUIT BOARD. (8½ x 5½ x ¼ in.), 2/6 sheet. 5 for 10/-.

BULK COMPONENT OFFERS

100 Capacitors (latest types), 50 pf. to .5µf.
250 Carbon Resistors, ¼ and ½ watt (transistor type).
250 Carbon Resistors, ¼ and 1 watt.
150 Hi-Stab. Resistors, ¼, ½ and 1 watt.
100 Capacitors (ceramic), 2 pf. to 1,000 pf.
ANY ITEM 10/- £2 THE LOT.

TIME SWITCHES (Sangamo S.251). 240 v. 20 amp. 50 c/s. Brand new, with solar dial, 67/6 each. P.P. 2/6.

SEALED RELAY (G.E.C.). 2 c/o., 670Ω, 24 v., 6/- ea. P.P. 1/6.

LATEST TELEPHONE DESK SET WITH DIAL (New, boxed). Black or two-tone grey, 95/-. P.P. 5/-.

TELEPHONE HANDSET. (Latest type), 15/- ea. P.P. 2/6.

AMPLIFIED TELEPHONE HANDSET. Latest type with built-in transistor amplifier and volume control, 35/- P.P. 2/6.

LATEST TELEPHONE DIALS (New and boxed), 17/6 ea.

MOVING COIL HANDSET AND MICROPHONE. 10/- set. P.P. 2/6.

"3000" TYPE RELAYS. 10 for 25/- P.P. 2/6.

OSCILLOSCOPES. Cossor 1035, £22/10/- P.P. £2/10/-.

LUSTRAPHONE MOVING COIL MICROPHONES. Type VC 152. (New, boxed.) Low or high impedance, 87/6 each. P.P. 2/6.

UNISELECTORS. 8 bank, 25 way, 50 ohm. (New and boxed), 50/- each.

PRECISION RESISTORS. .1%, 10/- doz. (Several standard values included.)

VITREOUS W/W RESISTORS. 5%. 25 for 10/-.

POWER TRANSISTORS. OC16, 7/6 ea. 25721, 10/- ea.

DIODES. SX632, SX781, 2/- each. 20/- doz. 400 P.I.V. ½ A. (unmarked diodes), 20/- doz.

SPEAKER BARGAINS E.M.I. (13 x 8 in.) with double tweeters, 15 ohm, 65/- P.P. 5/-.

As above, less tweeters, 3 or 15 ohm, 45/- P.P. 5/-.
Fane 12 in., 20 watt, with tweeter (15 ohm), 95/- P.P. 5/-.

CONNECTORS. 13 WAY "IN LINE" gold plated pins, 4/6 pr. P.P. 6d.

SILICON BRIDGE UNITS (GEX 541). 80 p.i.v. 10 amp., 37/6 ea. P.P. 2/6.

PHOTOFLASH ELECTROLYTIC. 2,000µf. 275 v., 17/6 ea. P.P. 2/6.

ELECTROLYTIC. 5,000µf. 50 v., 7/6 ea. P.P. 2/6.

BLOCK CAPACITORS. 2µf. 3,500 v. (9 x 5 x 3½ in.), 40/- P.P. 5/-.
50µf. 150 v. 7/6. P.P. 2/6. Many others in stock.

"VINKORS" L.A.2105, 6/- ea. P.P. 6d.

COMPUTER BOARD, containing 10 transistors (OC72 or OC76) and 10 diodes type OA10, 10/- P.P. 2/6.

COMPUTER BOARD. All components have long flying leads, and are 100% re-usable.

VOLTMETERS. METAL-CLAD. (6 in. edgewise mirror-scale.) New boxed. 11-0-11 and 110-0-110 v. D.C. (f.s.d. 250 micro/amp.), 75/-. P.P. 7/6.

E.M.I. WMSA OSCILLOSCOPE. £45.

E.M.I. 3794 WAVEFORM MONITORS (Trolley mounted)-£25.

SOLARTRON REGULATED POWER SUPPLY. 0-500 v. 200 mA. 6.3 v. 5 a., £15.

SOLARTRON TRANSISTOR POWER SUPPLY. 30-50 v. 10 amp., £20.

COUTANT TRANSISTOR POWER SUPPLY. 15-30 v. 20 amp., £20.

ELECTRIC SLOT METERS (17-), 25 amp. L.R. 240 v. A.C. 85/- ea. P.P. 5/-.

QUARTERLY ELECTRIC CHECK METERS. 40 amp. 240 v. A.C., 20/- ea. P.P. 2/6.

TELEPHONE HAND MAGNETOS (70 v. A.C.). Trade enquiries welcomed.

All Goods Previously Advertised Still Available.

PATTRICK & KINNIE

81 PARK LANE, HORNCHURCH, ESSEX

Tel.: ROMFORD 44473

WW—159 FOR FURTHER DETAILS.

PRICE SPECIAL RADIO CHASSIS OFFERS

HI-FI CONTINENTAL
STEREOPHONIC RADIOGRAM CHASSIS



Magnificent "Continental" Stereophonic Radiogram Chassis with piano key switches, built-in ferrite rod aerial. Comes complete with two 10 in. elliptical loudspeakers, plus a mono/stereo 4-speed automatic record changer. Complete £29/19/6 (Units available separately if required. Chassis only 19½ gns). Special terms available of £10/0/0 deposit followed by 18 monthly payments of £1/6/5 (total H.P. of £33/15/6) plus 15/- P.P. Send £10/15/0 now.

IMPERIAL HI-FI
STEREOPHONIC RADIOGRAM CHASSIS



The Imperial stereophonic 4-waveband chassis has the most advanced specifications yet offered in this country. There is a built-in ferrite rod aerial, seven piano key buttons, controlling mono/stereo selection. Gram Long-Medium-Short-FM-ON/OFF. The unit comes complete with two 10 in. elliptical loudspeakers plus a mono/stereo 4 speed automatic record changer. Complete £41/9/6 Chassis only 29½ Gns. Special terms available of £13/16/6 deposit followed by 24 monthly payments of £1/8/10 (total H.P. £48/8/6) plus 17/6 P.P. Send £14/14/0 now.

EMPRESS HI-FI
AM/FM STEREOPHONIC CHASSIS



This most advanced Radio-gram chassis with automatic push button selection covers short, medium and long wavebands plus V.H.F./F.M. Offered complete with 2 10 x 6 speakers, 4 speed Stereo/Mono autochanger, only £35/19/6. Chassis only 25½ gns. Special terms available of £12 deposit followed by 18 monthly payments of £1/11/7 (total H.P. £40/8/6) plus 15/- P. & P. Send £12/15/0 now.

All Lewis Radio equipment including valves are fully guaranteed for one year, free of charge. Send your cheque or P.O. today while stocks last to Dept. W.106.

LEWIS radio

LEWIS RADIO, 100, CHASE SIDE, SOUTHGATE
LONDON, N.14. Telephone: PAL 3733/9666

WW—160 FOR FURTHER DETAILS.

CLASSIFIED ADVERTISEMENTS

DISPLAYED: £5 5s per single col. inch.

LINE advertisements (run-on): 6/- per line (approx. 7 words), minimum two lines.

Where an advertisement includes a box number (count as 2 words) there is an additional charge of 1/-.

SERIES DISCOUNT: 15% is allowed on orders for twelve monthly insertions provided a contract is placed in advance.

BOX NUMBERS: Replies should be addressed to the Box number in the advertisement, c/o Wireless World, Dorset House, Stamford Street, London, S.E.1.

No responsibility accepted for errors.

Advertisements accepted up to **NOVEMBER 7** for the **DECEMBER** issue, subject to space being available.

SITUATIONS VACANT

ELECTRONIC TECHNICIAN.

DO you enjoy playing around with electronic gadgets? Here's a chance to make a career of your hobby. We offer you interesting and varied work in the field of electronic instrumentation. This small but expanding department is concerned with the design and application of electronic circuits required for testing of diesel engines and their fuel injection systems. STAFF conditions are good and include sickness and contributory pension and life assurance schemes, restaurant facilities, etc. IN the first instance, applicants should write in confidence, giving only brief personal details to:— PERSONNEL Manager, Simms Motor Units, Limited, Oak Lane, East Finchley, London, N.2. FINchley 2692, Extension 304.

[1615

SOUTHAMPTON UNIVERSITY.

DEPARTMENT OF ELECTRONICS.

CONTINUING expansion of the Department and a move to new buildings, give rise to the following vacancies:

TECHNICIANS for the construction and maintenance of a very wide variety of modern electronic equipment; practical experience of electronics or radio required.

JUNIOR TECHNICIAN to assist in the running of the laboratories; opportunities for training and day release exist.

MICROELECTRONICS. Three technical staff are required:

1. Principally to assist with the design and construction of a digital control system using modern digital integrated circuits; experience of digital circuits required.

2. Principally to take charge of and maintain a new ultra-high vacuum system; experience of vacuum techniques is required.

3. To assist with a number of projects on thin film components; experience of some aspect of microelectronics is required.

THESE appointments may be made at **TECHNICIAN OR CONTRACT ASSISTANT** level for candidates with particularly relevant qualifications.

SALARIES: Contract Assistant in range £912-£1,150 per annum. Technician Scale, £653-£958.

Starting point according to qualifications and experience.

Laboratory Assistant £11/5/9 per week.

Junior Technician £326-£549, starting point according to age and qualifications. Day release facilities available, generous holidays, superannuation, and good conditions.

APPLICATIONS giving details of age and qualifications, together with the names of two referees should be sent to the Deputy Secretary, as soon as possible.

[1615

AN OVERSEAS CAREER with International Aeradio Limited.

TO meet the requirements of constant growth and expansion we invite applications from technicians and engineers for an overseas career in North, West and East Africa, the Mediterranean area and the Arabian Gulf. If you have recently completed service in a trade such as Ground Wireless Fitter in the R.A.F., Radio Electrical Artificers in the Royal Navy or R.E.M.E., Army, or have other experience in the maintenance of H.F. and V.H.F. communications, R.T.T. and navigational aids, we should be interested to hear from you. Successful candidates would normally spend six weeks at our Radio Engineering School, Southall, Middlesex, before proceeding overseas, but in some cases staff with suitable qualifications and experience may be offered immediate posting. Overseas staff receive a tax-free salary with married and child allowances if appropriate and accommodation, bachelor or married, is provided free; other benefits include generous U.K. leave and membership of an excellent pension and life assurance scheme.

WRITTEN applications, please, to Personnel Manager, International Aeradio Limited, Aeradio House, Hayes Rd., Southall, Middlesex. [156

HI-FI/tape recorder salesmen, senior and junior, required by England's leading hi-fi dealer, Telesonic, Ltd., 92, Tottenham Ct. Rd., London, W.1. Museum 8177. [1615

ELECTRONICS TECHNICIANS

Solartron expansion—another factory being added at Farnborough. Our product range is widening. The newest and most exciting technologies are being used. For a Technician, employment at Solartron could be an important career phase, and an interesting and valuable experience.

THESE ARE THE POSITIONS

- Test Engineers—Systems Modules
- Systems Test Engineers
- Instrument Service Engineers
- Systems Service Engineers
- Installation Engineers

THIS IS THE WORK

Fault diagnosis and rectification at the Production, Building, Installation and after sales stages.

THESE ARE THE EQUIPMENTS

High precision instruments, digital data acquisition systems, analogue and hybrid computing systems, military simulation systems.

Based at Farnborough; or In certain other areas of the U.K. involving travel. Financial help with moving house. Salaries based on assessment of ability and contribution to the Company's success. Conditions second to none. Enquiries welcomed from anyone interested in a career in electronics. Men from the services and the radio and T.V. industry fit in with as much ease and job satisfaction as men from more closely allied fields.

Send enough personal details for an interview to:—



C. S. J. Mardell,
Personnel Officer,
The Solartron Electronic Group,
Farnborough, Hants.

FOR
SALE AND WANTED
ADVERTISEMENT FORM
TURN TO
PAGE No. 137

cyclotron operation

The successful applicant will join a team responsible to a senior physicist for the operation of a cyclotron for isotope production and the maintenance of its associated high voltage, radiofrequency, high vacuum and target handling equipment.

Applicants should have served a recognised engineering apprenticeship and have had several years experience in electrical or electro-mechanical engineering. An O.N.C. or equivalent and a knowledge of high voltage radiofrequency or high vacuum techniques is desirable. Preliminary training in the operation and maintenance of particle accelerating machines will be given.

Salary £1,015 p.a. (at age 26 years) rising by annual increments to £1,210 p.a.

Assistance can be given with house purchase

There is a contributory superannuation scheme

Application to:

The Personnel Officer (Ref. T.27/45)

THE RADIOCHEMICAL CENTRE

Amersham Bucks

TECHNICIAN

LONDON SCHOOL OF ECONOMICS AND POLITICAL SCIENCE

Applications are invited for the post of Technician in the Social Psychology Dept. Salary will be in the range £720-£875 depending on age and qualification. Candidates should be aged 20-25 years and possess ONC or HNC Electrical. The duties of the post will include routine maintenance of standard electrical and also design and development of more complex equipment. Experience on audio equipment or a knowledge of general electrical circuitry is required. Experience with psychological apparatus will be a considerable advantage. Applications to D. Nowell, Personnel Dept., London School of Economics Houghton Street, Aldwych, London, W.C.2.

PVE CAMBRIDGE WORKS, Ltd., Haik Rd., Cambridge.
* SINGLE sideband equipment.
* V.H.F. radiotelephone equipment.
* HI-PI reproduction equipment.
WE require trained personnel for production testing and fault finding of modern equipment.
WE have limited vacancies for more senior and experienced men with drive, who can lead small teams engaged on this work.
WE have also limited vacancies for persons of less experience who can be trained for such work.
APPLY to the Personnel Manager. [131]

BRITISH Antarctic Survey requires Wireless Operator for service in Port Stanley, Falkland Islands, on contract for 3 years in the first instance. Commencing salary £710x£50 to £860 per annum. Leave on full salary. Free passages. Candidates, 21-35 years, must be single and able to transmit and receive at minimum of 20 w.p.m. P.M.G. Certificate essential.—Applications to 30, Gillingham St., London, S.W.1. [1572]

DUE to continued expansion N.C.R. require additional Electronic and Electro-Mechanical Engineers for Computer Maintenance. Posts are available for men wishing to become Site Engineers.
TRAINING Courses are arranged for suitably qualified men. H.N.C. Electronics, City & Guilds Plural or equivalent standard welcome. Knowledge of electronic or electro-mechanical equipment necessary. Good Pension and Bonus Plan in operation.
PLEASE write for application form to:—The Personnel Officer, The National Cash Register Co., Ltd., 206/216, Marylebone Rd., London, N.W.1. [1596]

A FULL-TIME technical experienced Salesman required for retail sales; write giving details of age, previous experience, salary required to—The Manager, Henry's Radio, Ltd., 303, Edgware Rd., London, W.2. [149]

AMONN ANDREWS STUDIOS, Ltd., 4, Henry St., Dublin, have a vacancy for a Recording engineer experience of recording pop essential; salary negotiable starting not less than £1,000 p.a.—Write, or phone 49191. [11620]

ROYAL COLLEGE OF ADVANCED TECHNOLOGY SALFORD (Proposed University of Salford). SENIOR TECHNICIANS and TECHNICIANS. There are a number of vacancies in the rapidly expanding Department of Electrical Engineering, for staff in both Technician and Senior Technician grades. Successful applicants may work in research groups, and be concerned with building, maintaining and operating research equipment; or in an electronic workshop, where equipment for teaching and research is manufactured and maintained. The posts will particularly appeal to those who have practical experience of a variety of electromechanical and electronic equipment and who prefer to work on their own initiative in a wide variety of fields. Current salary scales are £705 to £960 for Technician, and £930 to £1,290 for Senior Technician posts, for which the desirable minimum educational qualifications are O.N.C. and H.N.C. respectively. The starting points on the scales will depend on age, experience and qualifications. The posts are superannuable. Applications, giving details of education and experience, should be sent to the Secretary, Royal College of Advanced Technology, Salford 5, Lancs, by 31st October, 1966, quoting reference E/76. [1612]

TEST gear engineer to design test units and establish test methods for the electrical parts of our control and measuring equipments and to assist in the running of the section which develop and constructs these test units; applicants should have practical industrial experience of d.c. and low frequency apparatus and components but need not have formal qualifications; a starting salary of £1,200 p.a. or upwards will be paid depending upon experience and qualifications.—Write or telephone the Personnel Manager, Rank Pullin Controls, Phoenix Works, Great West Rd., Brentford, Middx. Isleworth 1212, ext. 257 quoting Ref. ARN-1. [1619]

TECHNOCRATS

We have vacancies throughout the Electronics Industry for **QUALIFIED ENGINEERS** and **TECHNICIANS** of all grades. Our service is comprehensive, confidential and free to the applicant.

Write or telephone for an appointment, which can be outside working hours.

DESIGN & DEVELOPMENT	£1,200-£2,400
FIELD TRIALS, INSTALLATION TEST & SERVICE	£950-£1,400
DESIGN DRAUGHTSMEN	£1,300-£1,750
DRAUGHTSMEN TECHNICAL WRITERS	£1,000-£1,400
SENIOR INSPECTORS	£1,100-£1,400

TECHNOCRATS

52 Shaftesbury Avenue, London, W.1
GERrard 5316-7

(1 minute from Piccadilly Circus, opposite Globe Theatre.)

BERRY'S RADIO


Require

TECHNICAL STAFF, ENGINEERS AND SALES ASSISTANTS

GOOD PROSPECTS, PERMANENCY

Write giving full details of experience, past situations, etc. in confidence to

25 HIGH HOLBORN, LONDON, W.C.1

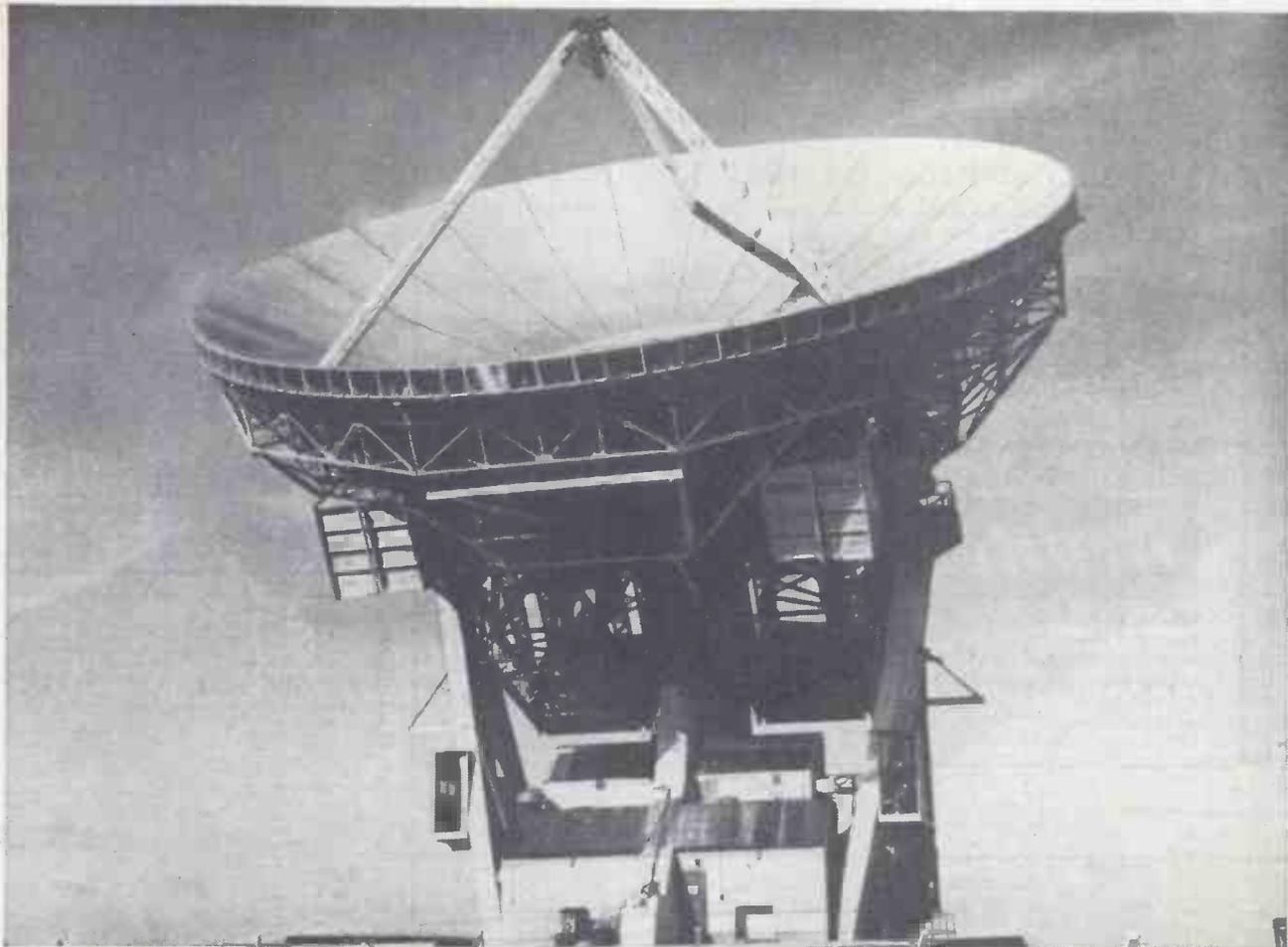

Space at the top!

Start now as an Assistant Executive Engineer in Electronic Exchange Planning, Circuit Design, Radio, TV and Space Communication, International Cable Systems

The rapidly expanding science of telecommunication engineering offers a stimulating and rewarding career to any young man or woman, with security, interesting work and promotion to higher managerial level.

If you have the required qualifications, the Post Office has the jobs—and the opportunities.

Training—Successful applicants have special courses in engineering and engineering management, on a “thin sandwich” basis extending over eighteen months.

Further Education—Opportunities to enter for a full-time or “sandwich” degree course (during which fees and salary continue to be paid by the Post Office) are available to those most likely to benefit.

Good Pay and Conditions—Pay is between £764 and £1,638 per annum, depending on age and location,

with annual increases. Chances of promotion to £2,400 p.a. and beyond are excellent. Holidays are generous, superannuation and staff welfare arrangements are above average.

Qualifications—Candidates must be at least 17½ and under 25 on the 1st September 1966. They must have passed GCE “O” level in English language and gained either (1) HND or (2) exemption from all parts of the examination of either the IEE, IERE or IMechE or (3) a GCE with four other passes, including two at “A” level in mathematical and scientific subjects.

For full details, please write to MR. E. C. OFFORD, POST OFFICE ENGINEERING DEPT., (St. 8), (AEE/WW) 2-12 GRESHAM STREET, LONDON, E.C.2.

Invest in
the future
with the



RADAR SIMULATION

We produce radar simulators for an expanding world-wide market and require:—

RADIO SIMULATOR TEST ENGINEERS

for factory commissioning of simulators for civil and military air traffic control, precision approach radar and tactical and navigation marine radars.

Excellent opportunities for advancement in a new section and for overseas travel during installation.

Previous radar experience is not essential but a knowledge of transistors, pulse circuits and principles of analogue computation is desirable.

Excellent salaries are paid and we offer contributory pension scheme, life insurance scheme and good welfare services.

Write or telephone to:



MR. H. C. Hall,
Personnel Manager,
REDIFON LIMITED
(Flight Simulator Division),
Gatwick Road,
Crawley, Sussex.
Tel: CRAWLEY 28811



THE QUEEN'S AWARD
TO INDUSTRY

ADVANCE WITH REDIFON

ST. GEORGE'S HOSPITAL,
HYDE PARK CORNER,
LONDON, S.W.1.

Department of Medical Physics and Instrumentation

Two Electronics Technicians are required for the electrons section of the above department at St. George's Hospital, S.W.1 and S.W.17. The work is interesting and varied, involving the design and construction of apparatus for use in research programmes, e.g. cardiac pacemaking, patient monitoring and radio isotope studies.

Candidates should have active minds, a practical knowledge of electronics and experience with light mechanical machines. The possession of the O.N.C. in mechanical or electrical engineering or its equivalent is essential.

Both posts are graded as Senior Physics Technician but the opportunity exists for one suitably qualified and experienced to be appointed on the Chief Technician Grade.

Applications with names of two referees to the Assistant Secretary at the above address not later than December 5th, 1966.

EDITORIAL ASSISTANT

"Wireless World" requires an additional member for its editorial team. Applicants, preferably between 25 and 35, should have an interest in and knowledge of radio and electronic engineering and an ability to write lucidly. Details of education and experience to the Editor-in-Chief, "Wireless World", Dorset House, Stamford Street, London, S.E.1.

WEST London Aero Club invite "A" and "B" licensed engineers with capital and/or necessary equipment to commence Radio Workshop. Alternative propositions may be considered. Write full details to—White, Waltham Airfield, near Maidenhead, Berks. [158]

TEST Engineer required for East Midlands area; interesting work on commissioning and maintenance testing of large scale broadcast relay vision and sound equipment and network, closed circuit television systems, including colour television, when it arrives; applications invited from engineers qualified to H.N.C. standard or C. & G. equivalent; specialised training given locally and at a central training school; attractive salary, good prospects, pension scheme, up to three weeks' holiday.—Please write or phone, Deputy Chief Engineer, Redifusion (East Midlands) Ltd., Castle Boulevard, Nottingham. Tel. 47411. [1611]

TEST gear technician for the detail layout, construction and wiring of test units for the electrical parts of our control and measuring equipments; the ability to test these units would be an advantage; applicants must have some experience of the assembly and wiring of electronic type equipments and of the components used in them and will be expected to work with a minimum of supervision; salary £18 or upwards depending on experience.—Please write or preferably telephone quoting reference ARN/2, Personnel Officer, Rank Pull-in Controls, Great West Rd., Brentford, Middx. Isl. 1212.



TELECOMMUNICATIONS

We have vacancies for Fault Finders, Testers, and Inspectors to work on interesting and advanced equipment including H.F. SINGLE SIDEBAND, V.H.F. RADIO TELEPHONES, U.H.F. MINIATURE EQUIPMENT.

Transistor experience is essential. Vacancies exist at all levels and training will be given where necessary.

Apply: Personnel Manager,
CAMBRIDGE WORKS LTD.,
Haig Road,
Cambridge.

RADIO/Radar Fitters required to service and maintain various airborne and ground installations at a flying unit in North West Wales, free single hotel accommodation; canteen facilities; excellent working conditions.—Apply: Short Brothers & Harland, Ltd., R.A.E. Llanbedr, Merioneth. [1584]

TEST & Service Engineer experienced in testing, commissioning and servicing of relay and solid state logic systems required by company manufacturing Machine Tool Controls London, W.C.1 area. Applicants who are prepared to travel in U.K. and abroad should write to Box WW. 1605, Wireless World.

ELECTRONIC TECHNICIAN required, whose primary duties will be to supervise and maintain closed circuit television and videotape apparatus; work on the construction and maintenance of other electro-medical equipment may also be occasionally required; candidates must have City and Guilds Certificate, O.N.C., or equivalent qualifications; salary will be according to age, experience and qualifications on the Whitley Scales (for technicians £1,089-£1,303 a year).—Application forms, which should be returned by October 26th, 1966, may be obtained from The Secretary, Institute of Psychiatry, The Maudsley Hospital, Denmark Hill, London, S.E.5. (Ref. DP/C.) [1624]

SITUATIONS WANTED

CHIEF petty officer, R.N. (Radio Branch), due for release Dec. 5th, 10 yrs. electronics (trade certificate), 7 "O" levels, 29. single, personable, good appearance, clean licence; desires opportunity in sales/commission engineering; resident W.B., Yorks., but welcome travel anywhere U.K./abroad.—C.P.O. Dufton, H.M.S. Inskip, Nr. Preston, Lancs. [79]

RADIO TECHNICIAN with a sound knowledge of at least three of the following types of equipment is required immediately for Meteorological Office Ocean Weather Ships; Single Side-Band Transmitter, Radar (Navigational), Radar Height Finding, Echo Sounders, and Radio Receivers, Automatic D.F., V.H.F. and M.F. Low Voltage Servo Recorders. Digital Telemetering Equipment.

Salary scale £678—£1,104 per annum according to age, plus £120 per annum overtime allowance. Free food and accommodation provided on board ship. Applicants must be natural born British subjects. Full details from Shore Captain, Ocean Weather Ship Base, Great Harbour, Greenock. Telephone Greenock 24291.

English Electric Leo Marconi

Computer servicing

English Electric Leo Marconi is Britain's foremost computer company. Ever increasing sales mean that we need more engineers to maintain computers on our customers' premises.

Experience in the development, testing or servicing of transistorised electronic equipment and the ability to understand the logic of advanced computers are the qualifications we are looking for.

Training, salaries and fringe benefits are all that you would expect from a leader in the computer field and prospects are limited only by ability.

Jobs exist in most parts of the country, but the greatest number of vacancies is in the London Area, the Midlands and South West Lancashire.

To obtain more information write to:—
The Personnel Officer,
Dept. WW.M.16,
English Electric-Leo-Marconi Computers Ltd.,
24, Minerva Road,
London, N.W.10.

Engineer: Like to switch to computers?

We are looking for young men to train as IBM Data Processing Customer Engineers: men with ambition, personality and confidence, who will enjoy working largely on their own initiative (a quality rewarded particularly well at IBM). Here are the facts:—

 As a DPCE you will work with your own customers on some of the world's most advanced punched card and computer systems.

 You will get a really thorough training on data processing equipment during your initial three months, followed by advanced computer training later in the U.K., France, Germany or U.S.A.

 Starting salaries in the London area are in the region of £1100 a year (more if you have special aptitude or experience). Promotion and increases are on merit. As a DPCE you could be earning between £1300 and £1750 in three years.

 There are valuable benefits including a non-contributory pension scheme, free life assurance and sickness benefit.

 To qualify you should be between 21 and 29 with radar or telecommunications experience or ONC/HNC Electrical or Electronic. However, if you are between 18 and 22 and have a basic knowledge of electro-mechanics, we would still like to hear from you — there are opportunities to train as junior Customer Engineers.

Please write, giving details of age, experience and background to Miss S. A. Jones, IBM United Kingdom Limited, 101, Wigmore Street, London W.1., quoting reference DP/WW/524.

IBM

TEST EQUIPMENT MAINTENANCE HIGH FREQUENCY LABORATORY

Continual expansion has created a vacancy for an Assistant in the Equipment Laboratories. The duties will include the servicing of a variety of electronic equipment used in the factory and field for cable testing.

Applicants will preferably be ex service radar fitters or have similar experience and must be prepared to work on their own initiative.

The position offers the usual staff benefits including a generous Life Assurance Scheme and salary will be commensurate to age and experience.

Please apply in the first instance, stating age and experience, to:

The Personnel Officer
Telephone Cables Limited
Chequers Lane,
Dagenham,
ESSEX.

OFFICIAL APPOINTMENTS

NEWPORT and Monmouthshire College of Technology.
ALL-YR-YN Avenue, Newport, Mon.
APPLICATIONS are invited for the following new posts: Lecturer and Assistant Lecturer in Electrical and Electronic Engineering. Candidates should be graduates with industrial or research experience and will be required to teach to post H.N.D. level. Preference will be given to candidates for one of these posts offering the subjects of Electronic Circuitry and Computer Technology. Salary Scales: Lecturer £1,875 to £2,140; Assistant Lecturer (Grade B), £955 to £1,625 with allowance for qualifications and experience.
APPLICATION forms and further details from the Principal, to be returned within 10 days.
E. H. LOUDON,
T. M. MORGAN,
CLERKS to the Governors. [1616]

COUNTY Medical Physics Department, St. George's Hospital, Lincoln.
APPLICATIONS are invited for the post of Senior Technician (Electronics or Bio-Engineering).
CANDIDATES must have previous experience in this field, but not necessarily in hospital. An appropriate qualification is required.
SALARY Scale: £868-£1,106.
FURTHER particulars may be obtained from the Physicist-in-Charge.
APPLICATIONS, stating age, qualifications, and details of previous experience, together with the names of two referees, should be sent to the Hospital Secretary, St. George's Hospital, Lincoln. [1623]

PUBLIC APPOINTMENTS

TELECOMMUNICATIONS Technical Officers, Board of Civil Aviation.
POSTS for men aged at least 23 for installation and maintenance of navigational aids and communications equipment at Civil Aerodromes and other stations in the United Kingdom.
QUALIFICATIONS: O.N.C. in Electrical Engineering, or City and Guilds Intermediate Certificate in Telecommunications (old syllabus i.e. subject No. 50) plus Radio II, or Intermediate Telecommunications Certificate (new syllabus i.e. subject No. 49) plus Certificates in Mathematics B, Telecommunications Principles B, and Radio and Line Transmission B, or equivalent standard of technical education, and at least 5 years' appropriate experience.
SALARY: (National): from £955 (at 23) to £1,147 (at 28 or over); Scale maximum £1,295 (somewhat higher in London). Prospects of promotion. Non-contributory pension.
WRITE (preferably by postcard) to Civil Service Commission, Savile Row, London, W.1, for application form, quoting S/207/66. Closing date November 1st, 1966. [1621]

BOOKS, INSTRUCTIONS, ETC.

MANUALS, circuits of all British ex-W.D. 1939-45 wireless equipment and instruments from original R.E.M.E. instructions; s.a.e. for list, over 70 types.—W. H. Bailey, 167a, Moffat Road, Thornton Heath, Surrey. [143]

ARTICLES FOR SALE

GOOD secondhand Ferrographs often available.—Reg. 2745 (Lon.). [110]
WIRELESS WORLD for 1959, 1960, 1963, 1964, mint condition; offers to—Box WW 82, Wireless World.
WIRELESS WORLD, 147 back numbers (1950 to 1965) for sale, also other magazines; details from—77, Merrion Ave., Stanmore, Middx. [83]
THE 75-watts tube 1625 and the metal tube 6AG7 in original cartons, 3/- each, lots of 100 or more.—Reis Radio, Föhemsplatsen 2, Göteborg, Sweden. [1617]
GRAMPIAN DP4/L mic., £7; DP6/L with neck cord, £7/10; G7/LH mic., matching unit, £3; 10 yds. twin screened mic. cable, 17/6; Reslo RBL/T ribbon, £6; as new.—Alan, 51, Stubbington Avenue, North End, Portsmouth, Hants. [76]
MARCONI transmitter type 6048 CW/MCW/RT, complete with 1,250V rotary transformer power unit 388A and control unit 896, less connecting cables, £30; AR88D good condition, £28.—Atlanta Radio, Ltd., 129, Bournemouth Rd., Parkstone, Poole. Tel. 1280. [77]
MICROPHONE SERVICES.—Microphones by S.T.C. £3/13/6 to £50; Reslo, £6/17/6 to £18; Lustraphone, from £4/4; Gramplan, from £8/5; others: mics and column loud speakers, stage and reinforcement, mic. stands, adaptors, couplers, studio booms, special stands to order, cables, free plugs, leads, fittings, state type.—51, Stubbington Ave., Portsmouth 62569. [82]

COMPUTER ENGINEERS

Due to continued expansion NCR require additional **ELECTRONIC** and **ELECTRO-MECHANICAL ENGINEERS** for Computer Maintenance. Posts are available for men wishing to become Site Engineers.

Training Courses are arranged for suitably qualified men. H.N.C. Electronics, City & Guilds Final or equivalent standard required. Men from Forces with radar experience welcome.

Knowledge of electronic or electro-mechanical equipment necessary. Good Pension and Bonus Plan in operation.

Please write for application form to The Personnel Officer, The National Cash Register Company Ltd, 206/216 Marylebone Road, London NW1.

Plan your future with

NCR



The Civil Service

Professional and Technical Appointments

ELECTRICAL ENGINEERS

urgently required to fill vacancies in Ministries of Aviation, Defence, Public Building and Works, and Transport, the Diplomatic Wireless Service and Government Communications Headquarters. Vacancies in fields of (a) power, including building services, and (b) light currents and electronics.

QUALIFICATIONS: Degree or Dip. Tech. with 1st or 2nd class honours in Electrical Engineering or Physics, or have passed all examinations for A.M.I.E.E. or A.M.I.E.R.E.

SALARY (Inner London): £1,143 (at 25) - £1,718. Promotion prospects.

AGE: Normally at least 25 and under 35 on 31.12.66. Some extensions for service in H.M. Forces or Overseas Civil Service. (Reference: S/85)

POST OFFICE EXECUTIVE ENGINEERS

At least 60 posts in London and Provinces for electrical, electronic and mechanical engineers to develop and design communications systems and postal service equipment.

QUALIFICATIONS: Degree or Dip. Tech. in Mechanical or Electrical Engineering, Physics, or Applied Physics or, exceptionally, very high professional attainment.

SALARY (Inner London): £877-£1,806. Promotion prospects.

AGE: At least 21 and normally under 35 on 31.12.66. Some extensions for service in H.M. Forces or Overseas Civil Service. (Reference: S/322)

ENGINEERING DRAUGHTSMEN


Vacancies in Ministry of Public Building and Works, Ministry of Defence, Post Office and other Departments for Engineering Draughtsmen in the fields of MECHANICAL, ELECTRICAL, and HEATING AND VENTILATING ENGINEERING.

QUALIFICATIONS: O.N.C. (or equivalent) in appropriate subject, three years' training and, in addition, at least one year's drawing office experience.

SALARY (Inner London): £790 (at 20)-£1,220 (at 28 or over)-£1,338. Annual leave allowance 3 weeks and 3 days rising to 6 weeks.

AGE: At least 20. Promotion prospects. Where appropriate, time off for further technical study may be given. (Reference: S/68)

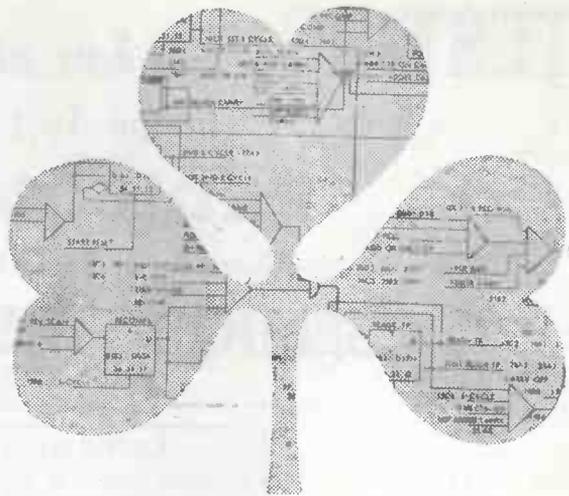The above posts are pensionable and APPLICATION FORMS are obtainable from the Secretary, Civil Service Commission, Savile Row, London, W.1. Please quote appropriate reference.



Engineer: we need your kind of know-how in Ireland.

If you have a basic knowledge of electronics, such as Radar/Radio/control equipment fitters course, telecommunications experience, BE or HNC (Electrical or Electronic) and are thinking of returning to Ireland, there could be a very worthwhile career for you as a data processing customer engineer with IBM.

The DP customer engineer has a challenging, stimulating and rewarding job to do - not only servicing existing data processing installations but also working in close collaboration with his own customers to extend and develop their equipment as the need arises. He is an 'ideas' man who works largely on his own initiative and deals with all levels of management. He is often the company's principal contact with customers and is therefore relied upon by customer staff, to advise on a great variety of data processing problems. Success then, will largely depend on individual initiative and drive - qualities which are recognised and rewarded well at IBM.

Opportunities are excellent as it is the IBM policy always to promote on merit and from within the company. Starting salaries will be based on individual merit, qualifications and experience and full training will be given.

This is a career with the acknowledged world leaders in data processing techniques and applications. It offers tremendous scope in the new and exciting computer industry, a high degree of personal satisfaction and invaluable experience with one of the fastest growing companies in the country. If you are between 21 and 28, are looking for real opportunity and have the basic knowledge required, please write, giving details of age, experience, qualifications and background to: The Personnel Officer, IBM Ireland Limited, 28, Fitzwilliam Place, Dublin, 2, quoting ref. DP/WW/018. Initial interviews can be arranged in London and Dublin.

IBM

TESTING . . . can offer you a rewarding career

in the Test Department of

REDIFON LIMITED

Manufacturers of Radio-Telecommunications Equipment

SENIOR TEST ENGINEERS

required

EXCELLENT STARTING SALARIES

Recently revised Staff Status. 37½-hour week.
Canteen. Sports and Social Club. Pension and
Life Assurance Scheme.

Redifon

Write or phone: The Personnel Manager
REDIFON Ltd., Broomhill Road
Wandsworth, London, S.W.18
VANdyke 7281

Interviews arranged to suit your convenience

MEDICAL RESEARCH COUNCIL

National Institute for Medical Research.

An excellent vacancy occurs in the Electronics Laboratory of the Engineering Division for a young Technician to undertake the construction and wiring of prototype instruments. Experience of electronic circuit assembly and preferably some knowledge of mechanical devices. Progressive salary and excellent working conditions offered to the successful candidate:

Apply to P.O.—N.I.M.R. The Ridgeway, Mill Hill, N.W.7.

A BETTER deal for cash customers. We do not provide interest free credit but offer very generous discounts for cash. Call, write or phone—we will quote. Every item of equipment despatched brand new in sealed cartons. Agents for all leading makes, amplifiers, tuners, motors, pick-ups, loudspeakers and tape recorders.—Audio Services, Ltd., 82, East Barnet Rd., West Barnet, Herts. Tel. Barnet 6605. [161]

ARTICLES WANTED

WANTED—Cash paid for valves, televisions, radios, any quantity.—S. Willetts, 43, Spon Lane, West Bromwich, Staffs. [162]

Q METER required. TP 329G or similar, any condition.—Allen, Yealm Bridge House, Yealinton, Devon, or Tel. after 6 p.m. Yealinton 301. [163]

WANTED—Power supply unit with leads for a 1154 transmitter; will pay up to £5 if in working order.—Apply The Advertiser, 75, Franks Ave., New Malden, Surrey. [141A]

WANTED, all types of communications receivers and test equipment.—Details to R. T. & I. Electronics, Ltd., Ashville Old Hall, Ashville Rd., London, E.11. Ley. 4966. [140]

Radiomobile

BRITAINS CAR RADIO SPECIALISTS

RADIO DEVELOPMENT ENGINEER

A vacancy has arisen for an additional Engineer in our Current Engineering Department.

The variable duties will include dealing with post design and production problems, close liaison with suppliers as well as actual development activities.

An excellent salary and fringe benefits will be offered to the successful applicant who will hold H.N.C. in Radio Engineering. Preference will be given to a person with drawing ability and experience of vehicle radio receivers.

Applications should be made in writing to:

Mr. W. A. Pluck
Personnel Manager
Radiomobile Limited
Godwood Works
North Circular Road
London, N.W.2. GLA 0171

NEWCASTLE GENERAL HOSPITAL

(1,040 Beds)

SENIOR ELECTRONICS TECHNICIAN

required in the Electronics Laboratory of the Regional Neurological Centre. Candidates will be expected to be of H.N.C. standard and to have had some experience in design and development work. Conditions of service governed by Whitley Council agreements. Present salary scale £868-£1,106 p.a.

Applications, with names and addresses of two referees, to Hospital Secretary, Newcastle General Hospital, Newcastle upon Tyne, 4, within two weeks.

SERVICES OFFERED

ELECTRONICON, Ltd.—From drawing board to production with minimum delay; let us be your research development, design and prototype department Pilot production runs a speciality.—176, Lythalls Lane, Coventry. Tel. Nuneaton 2353 or Coventry 86544. [150]

LEAVE it to us.

FOR all electronic wiring, large or small, metal fabrication, engraving, etc., competitive prices and excellent delivery.

APPLY Contracts Manager, Shirehall Electronics, Ltd., Station Yard, Borough Green, Sevenoaks, Kent. Tel. Borough Green 2612. [152]

TOROIDAL Coil Winding, transformers, transducers, inductors, etc., designed and wound to order; quick delivery, 1 to 1,000.—Magtor, Ltd., 68, Dale St., Manchester, 1. Cen. 3031. [159]

JOIN Audio Supply Association, 7/6 p.a. (65-page photographically illustrated, non-advertising) hi-fi catalogues, 4/6; your best guide for safe buying.—10, Cliford St., London, W.1. [111]

TELEGINE OPERATOR

International Advertising Agency requires young man between the ages of 20 and 28 to operate and maintain television film scanning equipment. Candidates should have intermediate "C of G" or equivalent, and previous experience on this type of equipment.
Excellent salary, five-day week.

Applications in writing to:

The Appointments Office,
J. Walter Thompson Company, Limited,
40 Berkeley Square, London, W.1.

S MALL electronic units, sub-assemblies, prototypes, etc., speedily constructed, short or long runs, enquiries invited.—Offshore Maintenance Co. Ltd., 15, Island Wall, Whitstable, Kent. [184]

VALVES

V ALVE cartons by return at keen prices; send 1/- for all samples and list.—J. & A. Boxmakers, 75a, Godwin St., Bradford, 1. [116]

VALVES WANTED

W E buy valves for cash, large or small quantities, old types or the latest; send details, quotations by return.—Waltons Wireless Stores, 15, Church St., Wolverhampton. [134]

SERVICE & REPAIRS

B.B.C.2, TV, RADIO, TAPE REC. SERVICE SPARES
U.H.F./625, modify your set to B.B.C.2, 1955 to 1963 models covered, manufacturers' complete kits and tuners, send for free list. Special offer: Pye/Ekco u.h.f. complete conversion kit incl. tuner, transistorised IF panel, accessories, circuits, etc. normally 18gns., our price £8/10, post 3/6. Fireball Tuners, new, tested, exclusive offer of special manufacturers types suitable for KB, Ultra, Ferguson, HMV, etc., 75/-, new turret tuners, Brayhead 3001/3 58/6; Cydon c/t 30/-; Eray-head 10, 16, 35Mc/s 19/6; KB 16, 38Mc/s 19/6; Ekco 16Mc/s 12/6; post 4/-, many others available. TV Signal Boosters, transistorised, Pye/Labgear B1/B3 and u.h.f. battery 75/-, u.h.f. mains 97/6, u.h.f. mast-head 10, 16, 35Mc/s 19/6; KB 16, 38Mc/s 19/6; Ekco transf. mains droppers, etc. for all popular makes CRTS, 14, 17, 19in from £4/5 (callers only). Tape recorder belts, heads, motors, etc. Salvaged components, large selection transformers, scan coils, turrets, etc. Enquiries invited, c.o.d. despatch available. Manor Supplies, 64, Golders Manor Dr., London, N.W.11; callers 589B, High Rd., N. Finchley, N.12 (near Granville Rd.). Hil. 9118 (day), Spe. 4032 (evg). [101]

TAPE RECORDING ETC.

S AVE on cost of hi-fi. See Audio Supply notice (advert. No. 111). [109]
T APE to disc transfer using latest feedback disc cutters; EP's from 21/- s.a.e. leaflet.—Deroy, 32, Hest Bank Lane, Lancaster. [162]
T APE/DISC/TAPE transfer editing; duplicating; if quality and durability matter (especially with LPs from your precious tapes), consult Britain's oldest transfer service.—Fund raising records published for schools, musical societies (tax free).—Sound News Productions, 10, Clifford St., London, W.1. Reg. 2745. [108]

A BREAKTHROUGH IN OPPORTUNITIES

EXPERIENCED DESIGN AND DEVELOPMENT ENGINEERS REQUIRED BY COMPANIES IN THE HOME COUNTIES AREA

We have registered at least 125 vacancies for engineers with the right experience. This group of jobs offers excellent opportunities and starting salaries.

Salary Examples.	Age 35 up	£2,000
	25 to 35	£1,500—£2,300
	22 to 25	£1,100—£1,600

Design Experience required in following fields:—
Communications, Radar, Computers (digital and analogue), Logic, Automation, Instrumentation.

THIS IS A FIRST CLASS OPPORTUNITY TO WORK ON EXCITING PROJECT

Minimum Qualifications, H.N.C., C. & G. Full Tech. with at least 2 years in British Industry. We have also vacancies for Testers, Writers, Draughtsmen, Salesmen and Production Engineers. Contact us any time day or night quoting reference WW/105E.



ELECTRONICS APPOINTMENTS LTD.,

Norman House, 105-109, Strand, London, W.C.2
Tel.: TEMple Bar 5557-8

AEROPLANE AND ARMAMENT EXPERIMENTAL ESTABLISHMENT, BOSCOMBE DOWN, NR. SALISBURY, WILTS.

ELECTRONIC TECHNICIANS

TECHNICIANS, aged at least 24, required to be responsible for the organisation and supervision of maintenance work on radio/radar equipment, including ground and aircraft installations. To assist in planning of future installations.

QUALIFICATIONS AND EXPERIENCE. O.N.C., C. & G. Final Certificate or equivalent or H.M. Forces experience such as R.A.F. Flt. Sgt.-Chief Technician, R.N. 3rd Class Artificer or Army Foreman of Signals. A good knowledge of electronics and supervisory experience of ground and airborne radio/radar equipment maintenance is required.

SALARY. A starting salary of up to £1,009 according to age with annual increments to £1,129. Good prospects of promotion and pension or gratuity if you leave after five years' service.

TECHNICAL COURSES. These are sponsored for suitable candidates on day release.

APPLICATION FORMS. From the Manager, (PE 5031), Ministry of Labour, Professional and Executive Register, Atlantic House, Farringdon Street, London, E.C.4.



VHF TEST ENGINEERS

CAMBRIDGE WORKS LIMITED

have vacancies in their expanding Test Organisation for men with experience of VHF Transmitters and Receivers.

Men with Service training in VHF equipment would be suitable.

Progressive rates of pay and promotion and good facilities for training are offered.

**Apply: Personnel Manager,
Cambridge Works Limited,
Haig Road, Cambridge.**

COMMUNICATORS

Required by the GOVERNMENT OF ZAMBIA, Department of Civil Aviation, on contract for one tour of 36 months in the first instance. Salary according to experience in scale of £945 to £1,580 a year plus a supplementary payment of £200 a year. Gratuity at the rate of 25% of aggregate salary. Children's educational allowances. Free passages. Quarters available at moderate rental.

Candidates, aged 21 to 50 years, must have a 1st Class P.M.G. Certificate, or Air Force, Naval or Marine Communicators' Trade Certificate of Competency, or Ministry of Aviation or I.C.A.O. Communicators' Certificate of Competency. They must possess plain language and code morse speeds of 25 w.p.m. and 20 w.p.m. respectively and be able to operate teleprinter equipment to 40 w.p.m. Proficiency in radio telephony operation to international standards is required.

Apply to CROWN AGENTS, M. Dept., 4 Millbank, London, S.W.1, for application form and further particulars, stating name, age, brief details of qualifications and experience, and quoting reference M2T/62812/WF.

Redifon

A MEMBER COMPANY OF
THE REDIFFUSION GROUP

require

SENIOR ELECTRONIC INSPECTORS

WITH EXPERIENCE
OF HIGH-GRADE TELECOMMUNICATIONS EQUIPMENT

SECURITY

Continuing employment in an expanding company.

STATUS

Weekly paid Staff Pension and Life Assurance Schemes.

SALARY

Recently revised. Excellent earning potential—overtime available.

Call, phone or write
The Personnel Manager,
REDIFON LTD.,
Broomhill Road,
Wandsworth, S.W.18.
VANDyke 7281.

A UNIQUE Tape Buy! Top brand, 7in, 2,400ft, 25/-; 5 1/2in, 1,200ft, 15/-; p. & p. 2/-; 2 at 2/9; 3-6 at 3/6; bargains in all sizes; s.a.e. for list.—E. C. Kingsley Co., Ltd., 95, Tottenham Court Rd., London, W.1. Euston 6500. [113]

NEW GRAM AND SOUND EQUIPMENT

G LASGOW.—Recorders bought, sold, exchanged; cameras, etc., exchanged for recorders or vice-versa.—Victor Morris, 343, Argyle St., Glasgow, C.2. [120]

PERSONAL

H OUSE names in gold leaf on wood, 4in x 16in, post free 57/6 from Wood Lodge Studio, Hilltown, N.I. [155]

LONDON CENTRAL RADIO STORES

10-WAY PRESS-BUTTON INTER-COM TELEPHONES in Bakelite case with junction box handset. Thoroughly overhauled. Guaranteed. £6/10/- per Unit.

20-WAY PRESS-BUTTON INTER-COM TELEPHONES in Bakelite case with junction box. Thoroughly overhauled. Guaranteed. £7/15/- per Unit.

WIRELESS SET No. 38 A.F.V. Freq. range 7.3 to 9.0 Mc/s. Working range 1/2 to 2 miles. Size 10 1/2 x 4 x 6 1/2 in. Weight 5 1/2 lb. Includes power supply 6B6—and spare valves and vibrator, also tank aerial with base. £8 per pair or £3 single. P.P. 25/-.

ELECTRICITY SLOT METERS (1/- in slot) for A.C. mains. Fixed tariff to your requirements. Suitable for hotels, etc. 200/250 v. 10 A. 50/-; 15 A. 90/-; 20 A. 100/- P.P. 7/6. Other amperages available. Reconditioned as new, 2 years' guarantee.

QUARTERLY ELECTRIC CHECK METERS. Reconditioned as new, 200/250 v. 10 A. 42/6; 15 A. 52/6; 20 A. 57/6. Other amperages available. 2 years' guarantee.

TWIN GONG TELEPHONE, extensions bells, 21/-.

TELEPHONE TYPE HAND GENERATORS, 50 v. bell ringing, 9/6

BRASS JACK STRIPS. 20 Jack sockets in each strip. Size approx. 11 x 3 1/2 in. 17/6. P. P. 4/-.

P.M. MOVING COIL SPEAKERS. 5in. 9/6. 8in. 3 ohm 10/6. Elliptical 7 x 4in. 3 ohm 10/6. P. P. 3/6.

MOVING COIL HEADPHONES chamois leather earpiece, 25/- P. P. 3/6.

8-BANK UNISELECTOR SWITCHES. 25 contacts, alternate wiring £2/15/-; 8 bank half wipe £2/15/-; 6 bank half wipe, 25 contacts 47/6. P. P. 3/6.

DESK PHONES. Black bakelite cases complete with hand set and internal bell. 42/6. P. P. 6/-.

HIGH-SPEED ELECTRO-MAGNETIC COUNTERS. Ex-Govt. 0-999, 25/50 v. D.C. Size 4 x 1 1/2 in. Single coil, 23,000 Ω. Single coil 500 Ω. 8/6. P. P. 3/6.

EX GOVT. BALANCED ARMATURE THROAT MIKES complete with plug, new, 7/6. P. P. 3/6.

23 LISLE ST. (GER 2969) LONDON W.C.2
Closed Thursday 1 p.m. Open all day Saturday

Northern Polytechnic, Holloway, London, N.7

The Governing Body invites immediate applications for appointment to the Department of Electronic and Communications Engineering as **ASSISTANT LECTURER (Grade "B")**. The lecturer will be concerned primarily with courses for Electronic Technicians covering the City & Guilds of London Institute Examinations. He will be required to develop a wide range of original electronic experiments and industrial and/or teaching experience is essential. Salary scale—£1,025-£1,695 with additions for qualifications; point of entry dependent on qualifications, training and experience.

Apply for form of application and further particulars.

R. H. CURRELL, F.C.A. Clerk.

VALVE ENGINEERS

The Valve Division of E.M.I. Electronics Ltd. invite applications for the following vacancies in their Klystron Department:—

A Senior Engineer is required to pump, process and test high power microwave valves and to supervise the work of other Test Engineers engaged on similar work and operating low level test benches.

Two Engineers are also required to assist with this work.

For the senior position the candidate should have H.N.C. and some experience with a valve manufacturing company is essential. For the more junior positions, experience in one of the technical branches of the Services would provide a suitable background. Some interest in vacuum systems, microwave work or modulation techniques is essential.

Please apply giving brief details of experience to:—

W. A. Garmston,
Group Personnel Department,
E.M.I. Ltd.,
Blyth Road,
Hayes, Middlesex.

HI-FI MAIL ORDER SPECIALISTS

GOODS DESPATCHED BY RETURN
CARRIAGE & INSURANCE FREE! (UK)

A selection from our extensive stock

SPEAKERS				U.S.
Wharfedale Super 8, RS/DD	£7	9	0	\$16.80
Wharfedale Super 10, RS/DD	£11	16	8	\$28.00
Goodmans Ariette 8	£8	3	6	\$14.70
Goodmans Maxim Mini System	£17	15	7	\$42.15
Goodmans Magnum K System	£36	15	0	\$101.85
Quad Electrostatic Speaker	£57	0	0	\$158.75
Tannoy 12in. Monitor DC Speaker	£30	15	0	\$89.10
Kelly Ribbon R.P., Mk. II	£11	10	0	\$31.50
Lowther PM6 Drive Unit	£18	18	0	\$52.50
MOTORS				
Thorens TD150 AB, motor/arm/plinth	£35	17	4	\$82.60
Garrard 401 Transcription Unit	£29	17	5	\$71.30
Thorens TD124 Transcription Unit	£40	18	0	\$94.95
Connoisseur Classic, 2-speed unit	£14	14	1	\$35.00
Garrard SP25, motor and p/up arm	£13	15	0	\$32.50
AMPLIFIERS				
Leak Stereo 30 Transistor Amplifier	£49	10	0	\$138.50
Leak Stereo 20/Transilope 2 Pre-amp.	£57	10	0	\$161.65
Quad 22 and 2 Quad II Power amps.	£75	0	0	\$209.25
Armstrong 222 Stereo Integrated Amp.	£28	15	0	\$80.50
Rogers Cadet III, stereo amp. and control	£31	0	0	\$86.55
Goodmans Maxamp Stereo Amplifier	£49	10	0	\$138.50
Radford SC29/ST1A15 Stereo Units	£84	0	0	\$235.20
TUNERS (Stereo Decoders extra)				
Armstrong 223 AM/FM Tuner	£31	0	0	\$74.20
Quad AM II or FM Tuner, each	£28	19	0	\$86.70
Leak Troughline III FM Tuner	£32	3	11	\$74.90
PICK-UPS AND CARTRIDGES				
Decca Deram Transcription Cartridge	£4	14	6	\$11.45
Ortofon S182 Cartridge with trans.	£32	7	1	\$77.00
S.M.E. 3012/Series II Arm	£28	16	10	\$83.30

WORLD WIDE EXPORTERS

OVERSEAS ORDERS SENT FREE OF PURCHASE TAX
AND SHIPPED PROMPTLY AT MINIMUM COST

Fully illustrated catalogue 4/6. U.K. (Export 7/- or \$1.00.)
Refundable against first purchase value £7 or \$20.00.

C. C. GOODWIN (SALES) LTD.

(Dept. W79) 7 The Broadway,
Wood Green, London, N.22

Telephone: Bowes Park 0077/8

1 minute from Wood Green Underground.

Open 9-6 Monday to Saturday (Thursday 9-1 p.m.)

TEST EQUIPMENT — SURPLUS AND SECONDHAND

SIGNAL generators, oscilloscopes, output meters, wave voltmeters, frequency meters, multi-range meters, etc., etc., in stock.—R. T. & I. Electronics, Ltd., Ashville Old Hall, Ashville Rd., London, E.11. Ley. 4986. [141]

CHAPMAN 55FM tuner, self powered, 16-50M, 195-550M, 800-2,000M and FM 89-100MCS, excellent performance and appearance; £35.—Tate, Greenflags, Limsfield Common, Nr. Oxted, Surrey. Limsfield Chart 2181 evenings. [81]

RECEIVERS AND AMPLIFIERS — SURPLUS AND SECONDHAND

HRO Rx5s, etc., AR88, CR100, BRT400, G209, S640, etc., etc., in stock.—R. T. & I. Electronics, Ltd., Ashville Old Hall, Ashville Rd., London, E.11. Ley. 4986. [142]

MISCELLANEOUS

METALWORK, all types cabinets, chassis, racks, etc., to your own specification, capacity available for small milling and capstan work up to 1 1/2 in bar.
PHILPOTTS METALWORKS, Ltd., Chapman St. Loughborough. [151]

PACKAGING

EXPANDED Polystyrene mouldings for packaging, £500-10,000 capacity available.—Styester Plastics, Ltd., Third Ave., E.12. Hild 2699. [1579]

SPECIAL OFFER

1 watt S.T.C. 300 Mc/s. N.P.N. Silicon Planar 100% Transistors. Limited stocks, £1 for six, with data

3/- each. OC44, OC45, OC70, OC71, OC81, OC81D, OC200, GET16, GET20.

ZENER DIODES

3.9v to 26v all voltors BETWEEN 1w 3/6d, 1.5w 5/7w 6/- each.

4/- each. AF114, AF115, AF116, AF117, OC170, OC171.

Send 6d. for full lists:—Inc. S.C.R., Zeners, etc.

CURSONS,
78 BROAD STREET,
CANTERBURY, KENT

WW—161 FOR FURTHER DETAILS.

GEE'S TAPE!

Attractively boxed guaranteed Brand New.

5in. Std.	600ft.	8/6
7in. Std.	1,200ft.	12/6
5in. L.P.	900ft.	10/-
5 1/2 in. L.P.	1,200ft.	12/6
7in. L.P.	1,800ft.	15/-
4in. D.P.	600ft.	9/-
5in. D.P.	1,200ft.	15/-
5 1/2 in. D.P.	1,800ft.	22/6
7in. D.P.	2,400ft.	25/-
3in. T.P.	600ft.	15/-
4in. T.P.	900ft.	17/6
5in. T.P.	1,800ft.	35/-
5 1/2 in. T.P.	2,400ft.	45/-
7in. T.P.	3,600ft.	58/6

P. & P. 2/6 per order.

As supplied to Govt. Depts., industry, schools. SPECIAL DISCOUNTS FOR QUANTITY BUYERS! SPARE SPOOLS 3in. 1/-; 3 1/2 in. 1/6; 4in. 1/8; 5in. 2/-; 5 1/2 in. 2/-; 7in. 2/6; 8 1/2 in. 4/6; 10in. 11/6. Send S.A.E. for comprehensive Tape List.

TRANSISTORISED "WIRELESS" INTERCOM



An amazingly new 'space age' intercom system needing no connecting wires between units. Simply plug into A.C. power point and talk, communication being carried through A.C. Power lines. Units can be moved from one location to another without trouble. Incorporates on/off volume control, push to talk, lock switch and pilot light. Complete with operating instructions. Ideal for office, home, etc. 12 GNS. Pair. Post free.

LAFAYETTE AIRCRAFT RECEIVER LATEST IMPROVED MODEL HA-55A



Covers 108-136 Mc/s. Listen to Aircraft Communications with this de luxe receiver. Two R.F. stages with 6CW4 Nuvistor for high sensitivity. 11 valve performance. Transistorised power supply. Built-in 4in. speaker, adjustable squelch, front panel phone jack. Easy read illuminated slide rule dial. Brand new and guaranteed. Size: 4 1/2 in. x 5 1/2 in. x 7 1/2 in. Complete with FM antenna. £19/7/6. Carr. 10/6.

GARRARD RECORD PLAYER BARGAINS

Brand new with maker's Guarantee. Send S.A.E. for full list of other Garrard units.



AUTO CHANGERS
MODEL 9 1/2 GNS. AT60
MODEL 8 GNS. 3000
SPECIAL THIS MONTH
MODEL 1000 Mono or 5 GNS. Stereo
SINGLE PLAYERS
MODEL 9 1/2 GNS. SP25
MODEL 87/6 SRP12 Carr. 5/- each. All complete with t/o crystal cartridge.

EVERSHED & VIGNOLES MEGGER
2,500 v. (hand-driven generator). Absolutely brand new, complete with leather carrying case. £75 Carr. 20/-.

EVERSHED & VIGNOLES BRIDGE MEGGER
300 v., with leather case. Perfect working order. £40

ERSKINE TYPE 13A DOUBLE BEAM OSCILLOSCOPES.
Perfect working order. 110/230 v. A.C. Time base 2 c/s-750 kc/s. Calibrators at 100 kc/s. and 1 Mc/s. Separate Y1 and Y2 amplifiers up to 5.5 Mc/s. Available complete with probe, leads, cover, circuit diagram, etc. As new

21 GNS. Carr. 30/-

GEE BROS. RADIO

15 LITTLE NEWPORT STREET, LONDON, W.C.2 GER. 6794/1453
Open 9-6 Mon-Fri., 1 p.m. Sat. Adjoining Leicester Square Tube

WW-162 FOR FURTHER DETAILS.

NEW EDITION

RADIO VALVE DATA

CHARACTERISTICS OF 7,000 VALVES
TRANSISTORS • SEMICONDUCTORS
DIODES AND RECTIFIERS •
CATHODE RAY TUBES

Compiled "WW" 8th edition. 9/6
Postage 1/-

PRINCIPLES OF LINEAR CIRCUITS, by E. A. Faulkner. 25/-. Postage 1/6.

PHASOR DIAGRAMS, by M. G. Scroggie. 27/6. Postage 1/6.

INTRODUCTION TO RADAR, by D. Taylor. 15/-. Postage 1/-.

TRANSISTOR SUBSTITUTION HANDBOOK. 12/6. Postage 1/-.

PRINCIPLES AND APPLICATIONS OF BOOLEAN ALGEBRA FOR ELECTRONIC ENGINEERS, by S. A. Adelfio and C. E. Nolan. 45/-. Postage 1/6.

HANDBOOK OF ELECTRONIC CIRCUITS by R. Feinberg. 50/-. Postage 1/6.

100 IDEAS FOR DESIGN '66, from Electronic Design. 15/-. Postage 1/-.

Inter: G.E.C. TRANSISTOR MANUAL. 18/-. Postage 1/9.

THE MODERN BOOK CO.

BRITAIN'S LARGEST STOCKIST
of British and American Technical Books.

19-21 PRAED STREET

LONDON, W.2

'Phone: PADdington 4185

Closed Sat. 1 p.m.

the motor vehicle

K. Newton, M.C., B.Sc., A.C.G.I., A.M.Inst.C.E.E., M.I.Mech.E., and

W. Steeds, O.B.E., B.Sc., A.C.G.I., M.I.Mech.E.

A standard and authoritative textbook for students, draughtsmen and owners/drivers, providing an accurate but not unduly technical explanation of automobile engineering theory in a logical sequence. Both petrol and diesel engines are discussed in great detail, and the gas turbine as applied to vehicles is considered. It also includes sections on modern petrols, fuel and lubricating oils.

683 pp. 622 illustrations

63s net. 66s by post

From leading booksellers

Published by

LIFFE BOOKS LTD., DORSET HOUSE, STAMFORD STREET, LONDON, S.E.1


EXCLUSIVE OFFER

PERMANENT OR
TRANSPORTABLE STEEL
60-FOOT AERIAL TOWERS

As supplied to
British and other Governments

* Unique design.
* Scientific Construction.

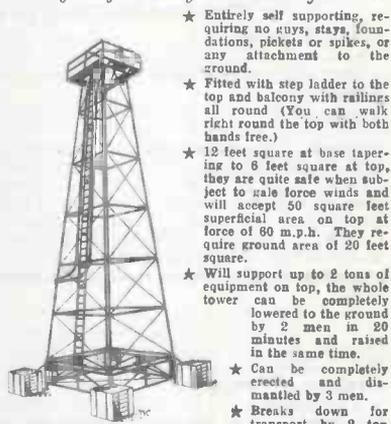having the following remarkable features.



- * Entirely self supporting, requiring no guys, stays, foundations, pickets or spikes, or any attachment to the ground.
- * Fitted with step ladder to the top and balcony with railings all round (You can walk right round the top with both hands free.)
- * 12 feet square at base tapering to 8 feet square at top, they are quite safe when subjected to male force winds and will accept 50 square feet superficial area on top at force of 80 m.p.h. They require ground area of 20 feet square.
- * Will support up to 2 tons of equipment on top, the whole tower can be completely lowered to the ground by 2 men in 20 minutes and raised in the same time.
- * Can be completely erected and dismantled by 3 men.
- * Breaks down for transport by 2 ton

lorry into parts easily handled by 2 men; there are no small loose parts, no nuts or bolts to get lost or damaged; all screws and adjustments are fully protected from rust and so designed to be free from damage when transported or left loose on the ground.

* Foolproof—the Tower cannot be erected if not assembled correctly. No skilled labour is required and no special tools are necessary.

* Can be raised and lowered, erected and dismantled and removed as many times as desired.

* Everything necessary for the complete Tower to be put into use and raised and lowered is provided; full drawings and instructions.

These fine Towers were made in England by B.L.C.C. and cost the Government £2,200 each. They are BRAND NEW and in maker's original packing. You can see one erected at our premises.

Cost £2,200
Price Brand New
£345

40-page list of over 1,000 different items in stock available—keep one by you.

* Narda 500 w Ultrasonic Cleaner	£85 0
* Avo Electronic Test Units	£12 10
* Avo Electronic Test Meters	£14 10
* 3M Video Recording Tape, 1/4 in.	£5 10
* Multhead Decade Oscillator D.105	£25 0
* Marconi S.S.B. Receivers HR-22 232 mc/s.	£140 0
* 9 foot BC-610 Whip Aerials	£1 15
* R.C.A. 420 Mc/s. Yagi 5 el. Beams	£2 10
* Model 15 Teletype Fax Printers	£29 10
* Model 14 Teletype Tape Readers	£25 0
* Model 14 Teletype Reprolators	£25 0
* R.C.A. 25 watt Projector Loudspeakers, range 1 mile	£14 10
* Metro-Vickers Vacuum Pumps 230 v. A.C.	£22 10
* Precision Meins Filter Units	£10
* E.M.I. Recording Bridges	£12 10
* Avo Geiger Counters	£7 10
* Philco W.S. No. 43 Transmitters 350W	£75 0
* Metro-Vickers HS.500 Waveform Monitors	£135 0
* E.M.I. 3794 Waveform Monitors on trays	£45 0
* Motorola 6 v. Mobile Transmitters 30/40 Mc/s.	£12 10
* Pen-type Personal Dosimeters	£7 15
* Western Electric Relay Test Sets L-181	£9 10
* Monitor Type 56 and Power Units	£2 10
* Marconi TF 1053 Noise Meters	£45 0
* AN/UPM-17 Spectrum Analysers 10/16000 Mc/s.	P.U.R.
* AN/URM-33, 34, 35 Signal Generators 1000/8000 Mc/s.	P.U.R.
* AN/PDR-27 Radec Sets	£17 10
* SG1A/ARN and MD-83A/ARN V.O.R. Test Sets.	P.U.R.

Carriage extra at cost on all above.

We have a large quantity of "bits and pieces" we cannot list—please send us your requirements—we can probably help—all enquiries answered.

P. HARRIS
ORGANFORD — DORSET
WESTBOURNE 65051

WW-163 FOR FURTHER DETAILS.

Radiospares Ltd.

FOR ELECTRONIC COMPONENTS-BY RETURN



WW-164 FOR FURTHER DETAILS.

BOARD OF TRADE (CIVIL AVIATION) TELECOMMUNICATIONS

The Board of Trade has vacancies for Radio Technicians at Airports, Air Traffic Control Centres, Radio Stations and other specialised Engineering Establishments throughout the United Kingdom.

The numbers and speed of air traffic today demands a complex, co-ordinated and reliable telecommunications system for airports, en-route navigation and air traffic control in order to ensure the highest standards of safety. The Department's Radio Technicians play a vital role in the installation, maintenance and technical operation of this system. Their duties embrace a wide range of equipment, including Primary Surveillance and Approach Radars, Secondary Surveillance Radars, Radio Navigational and Landing Aids, Radio and Line Communications, Electronic Data Displays, Closed Circuit T.V., Digital and Analog Computers.

Applicants should be aged 19 or over, of British nationality and possess a sound basic knowledge of Radio/Electronics with practical experience in at least one of the main branches of Telecommunications. The possession of formal qualifications would be an advantage.

Training on equipments and new techniques is provided at the Ministry's Civil Aviation Signals Training Establishment, Bletchley, Bucks.

Radio Technicians are encouraged to study for Technical and Professional Qualifications, and generous assistance, including part time and, in special circumstances, full time release, is provided.

There are good prospects of permanent pensionable posts and promotion to a higher class with a salary ranging from £1,068 per annum to £2,227 per annum.

Starting salary varies according to age; from £747 per annum at 19 to £962 per annum for entrants of 25 or over, and rises to £1,104 per annum. Annual leave is 3 weeks and 3 days, plus 8½ days for public holidays.

For further details apply to—

Mr. J. J. Robinson, M.I.E.R.E., A.M.B.I.M.,
Board of Trade (Civil Aviation),
Room 754,
The Adelphi,
London, W.C.2.

When visiting the 1966

RADIO COMMUNICATIONS EXHIBITION (SEYMOUR HALL, OCT. 26-29th)

COME AND SEE US ON

STAND 27

MOST ITEMS AS ADVERTISED ON PAGE 118 OF
THE OCTOBER ISSUE STILL AVAILABLE FROM
STOCK

P. F. RALFE

423 GREEN LANES, HARRINGAY,
LONDON, N.4. MOUNTVIEW 6939

Electronics and Instrumentation

Robert L. Ramey

Provides a sound groundwork for understanding the basis of existing instruments and their applications; also of instruments which are likely to be invented in the future. A useful introduction for students of electronics, and a single course for students in other branches of science and engineering.

55s net by post 56s 4d 321pp. 128 illustrations.

obtainable from leading booksellers

ILIFFE Books Ltd.

DORSET HOUSE, STAMFORD STREET, LONDON, S.E.1

CAPACITY AVAILABLE

SOLARTRON D/B oscilloscope, type CD711. £35; 50w P.A. lamp, £12.—Tel. Lab. 4499. [78]

ARTRONICS Ltd., for coil winding, assembly and wiring of electronic equipment, transistorised sub-unit, sheet metal work—3a, Waterland Rd., London, S.E.13. Tel. Lee Green 1706. [107]

WIGHT ELECTRONIC MANUFACTURERS SERVICES CO., LTD., have capacity available for sub-assemblies, wiring and transistorised electronic equipment.—Contact Wemscol, 60, High St., Cowes, I.O.W. Tel. 3323. [80]

TECHNICAL TRAINING

CITY & Guilds (Electrical, etc.) on "Satisfaction or Refund of Fee" terms. Thousands of passes. For details of modern courses in all branches of electrical engineering, electronics, radio, T.V., automation, etc., send for 132-page handbook—free—B.I.E.T. (Dept. 152K), Aldermaston Court, Aldermaston, Berks. [146]

P.M.G. Certificates, City & Guilds Examinations, I.E.R.E., also many non-examination courses in radio, TV and electronics; study at home with world famous I.C.S.—Write for free prospectus, stating subject, to International Correspondence Schools (Dept. 443), Intertext House, Parkgate Rd., London, S.W.11 [153]

TO ALL

Manufacturers, Wholesalers, Importers, etc. of the Radio and Electronic Industries

We are spot cash purchasers for all types of redundant and surplus stocks.

Phone or write Hillside 2713
Stonegrove 7624

Broadfields Disposals Ltd.,
8, Broadfields Avenue,
Edgware, Middx
or
Mayco Products Ltd.,
21 Lodge Lane,
N. Finchley, N.12

WW-165 FOR FURTHER DETAILS.

TUITION

KINGSTON-UPON-HULL Education Committee, College of Technology, Principal E. Jones, M.Sc., F.R.I.C.

FULL-TIME courses for P.M.G. certificates and the radar maintenance certificate, also in electrical and electronic engineering.—Information from College of Technology, Queen's Gardens, Kingston-upon-Hull. [154]

RADIO officers see the world. Sea-going and shore appointments. Trainee vacancies during 1967. Grants available. Day and boarding students. Stamp for prospectus.—Wireless College, Colwyn Bay. [128]

I.E.R.E., City & Guilds and R.T.E.B. exams., specialised I.C.S. home-study course will ensure success.—For details of wide range of exam. and diploma courses in radio, TV and electronics, also new practical courses with kits, write to I.C.S. (Dept. 522), Parkgate Rd., London, S.W.11. [106]

T.V. and Radio—A.M.I.E.R.E., City & Guilds R.T.E.B.Cert., etc., on "Satisfaction or Refund of Fee" terms. Thousands of passes. For details of Exams and home training courses (including practical apparatus) in all branches of radio, T.V. and electronics, write for 132-page handbook—free—B.I.E.T. (Dept. 150K), Aldermaston Court, Aldermaston, Berks. [148]

TECHNICAL TRADING Co.

- ★ LONDON—10 Tottenham Court Rd.
- ★ PORTSMOUTH—350-352 Fratton Rd.
- ★ SOUTHAMPTON—72 East St.
- ★ WORTHING—132 Montague St.
- ★ BRIGHTON—Devonian Court, Park Crescent Place

Tel.: MUS 2639
Tel.: 22034
Tel.: 25851
Tel.: 2585

All Mail Order and 24-hour Robophone service Brighton 680722

BULK! STEREO DECODERS (Arena 6 transistor complete), 7 Gns.
BUY! AM/FM STEREO RADIOGRAM CHASSIS (Normally 26 Gns.), 17 Gns.
AM STEREO RADIOGRAM CHASSIS (Normally 18 Gns.), 11 Gns.

TRANSISTORISED TUNER CHASSIS

F.M.

TYPE FMT41 High quality, low noise, battery or mains operation. Reproduction stands comparison with tuners costing 3 times as much. Come and hear it at any of our branches or send to Brighton without delay as we anticipate a very heavy demand. This beautifully compact 6 Transistor machine (size 6in. x 4in. x 2½in.), consists of a low noise frequency changer stage with smooth 2 gang tuning feeding. No less than three IF Stages terminating in a double tuned discriminator and LF Stage giving ample output for all quality amplifiers. Operates with negligible drain for months of use from a P.P.3 or any 9 volt battery. Note Audio Amplifiers of very interesting specification in the course of preparation.

£8-10

POST 2/6

WW-166 FOR FURTHER DETAILS.

MAGNETIC - TRL-90 - TAPE

Brilliant new range of fine quality Recording Tapes made for us by famous British Manufacturer to full specification, complete with leaders, trailers and stop foils.
FULLY GUARANTEED—ABSOLUTELY UNBEATABLE VALUE

Triple Play (Polyester)		Double Play (Polyester)		Long Play (P.V.C.)	
3in.	600ft. 12/9	3in.	300ft. 5/9	3in.	225ft. 4/3
4in.	900ft. 17/6	4in.	600ft. 10/9	4in.	450ft. 7/6
5in.	1,800ft. 23/9	5in.	1,200ft. 15/9	5in.	900ft. 11/6
5½in.	2,400ft. 29/9	5½in.	1,800ft. 19/9	5½in.	1,200ft. 13/9
7in.	3,600ft. 39/9	7in.	2,400ft. 23/9	7in.	1,800ft. 18/6

SPECIAL ECONOMY PACKS—STANDARD QUALITY P.V.C. (no Leaders, etc.)

Long Play		Long Play		Double Play	
3in.	225ft. 4 for 9/9	5½in.	1,200ft. 2 for 21/-	5½in.	1,800ft. 2 for 34/-
5in.	900ft. 2 for 15/9	7in.	1,800ft. 2 for 26/-	7in.	2,400ft. 2 for 42/-

Please add 1/6 per order postage and packing.

NASH HOUSE ELECTRONICS

NASH HOUSE, NEW STREET, WORCESTER

Tel.: 26316

WW-167 FOR FURTHER DETAILS.

Thanks to a bulk purchase we can offer
BRAND NEW
P.V.C. POLYESTER & MYLAR
RECORDING TAPES

Manufactured by the world-famous reputable British tape firm, our tapes are boxed in polythene and have fitted leaders, etc. The quality is as good as any other on the market, in no way are the tapes faulty and are not to be confused with imported, used or sub-standard tapes. 24-hour despatch service.

Should goods not meet with full approval, purchase price and postage will be refunded.

S.P.	3in.	150ft.	2/-	5in.	600ft.	6/-
	5½in.	900ft.	7/6	7in.	1,200ft.	9/-
L.P.	3in.	220ft.	2/3	5in.	900ft.	8/-
	5½in.	1,200ft.	10/-	7in.	1,800ft.	13/-
D.P.	3in.	400ft.	4/6	5in.	1,200ft.	12/-
	5½in.	1,800ft.	16/-	7in.	2,400ft.	20/-

Postage on all orders 1/6

We can also offer, BRAND NEW PRE-RECORDER LANGUAGE COURSES IN GERMAN, FRENCH, SPANISH AND ITALIAN.

Each course consists of 26 step-by-step lessons recorded at 3½ i.p.s. suitable for two- and four-track machines and supplied complete with handbook. Normal retail price 59/6.

Our price, 19/6, per course.

STARMAN TAPES

28 LINKSCROFT AVENUE, ASHFORD, MIDD. ASH 53020

WW-168 FOR FURTHER DETAILS.

FOR YOUR URGENT
QUARTZ CRYSTAL UNITS
in styles B, C, D, J, K, and B7G (Glass) Holders
RING HYTHE 2735

50 kcs to 150 kcs
1 mcs to 20 mcs

Crystal Electronics Ltd.
HYTHE, SOUTHAMPTON

WW-169 FOR FURTHER DETAILS.

STUDY radio, television and electronics with the world's largest home study organisation, I.E.R.E., City & Guilds, R.T.E.E., etc., also practical courses with equipment; all books supplied. Write for free prospectus, stating subject, to I.C.S. (Dept. 442), Intertext House, Parkgate Rd., London, S.W.11. 1102

A.M.I.Mech.E. A.M.I.E.R.E. City & Guilds, G.C.E., etc. Become a Technician or Technologist for high pay and security. Thousands of passes. For details of Exams and Courses in all branches of Engineering, Building, Electronics, etc., write for 132-page handbook—free—B.I.E.T. (Dept. 151K), Aldermaston Court, Aldermaston, Berks. 1147

SLEEP learning and therapy: two revolutionary new techniques in their respective fields of academic learning and mental health which have been rendered possible by the invention of the modern tape recorder; learn difficult lessons, memorise new data at short notice, master foreign languages, parts in plays or improve your mental powers; send now for free details of our sleep study recorder, time switch, pillow speaker, cassettes, induction and language tapes, and general information about these vital subjects.—Psychology Tapes Ltd., Dept. ATR, 16, Kings College Rd., London, N.W.3. Primrose 3514. The foremost suppliers of Sleep-Learning Equipment in Britain. 11622

ROTARY TRANSFORMERS. Input 12 v. D.C. Output 275 v. 110 mA. Brand New. 27/6. Carr. 4/-.
500 MICRO AMP. METERS. Panel mounting miniature type. 1½in. dial. Brand New. 12/6.
VARIABLE TWIN GANG. Solid dielectric 190-210 pF. Min. type 1x1x½in. 4/6.

11FT. WHIP AERIALS. 6 sections, copperized steel and painted. Dia. ¼in.-½in. Complete with moulded base 2½x3½in. 9/6 each. Post 1/6.

TELESCOPIC AERIAL MASTS. Tubular Steel copperized spray finish. Ring cam locking on each section provides for full or any height required. Suitable all fixings and base locations. 20ft.—4 sections. Only 55/-, Carr. 5/-.

SIGNAL GENERATOR. Type 106. Coverage 5.5 Megs. to 55 Megs. Max. Sig. Output 10 M/volts. Brand New. Manufactured Salford Insts. £5. Carr. 10/-.

3 KVA. AUTO TRANSFORMERS. 110/250 v. Mounted in steel case with external hand voltage regulator. 7 Taps. Brand New. £12. Carr. 10/-.

HEADPHONES. Balanced armature, DLR5. Brand New. 9/6 pr. Moving coil type, with ear muffs for noise excluding. 12/6 pr. Same fitted with moving coil mike, 17/6 pr. Carbon hand mike, 7/6 each.

TANNOY LOUDSPEAKERS. Ideal for all outdoor uses enclosed in waterproof wooden case, complete with steel baffle designed to produce directional reproduction at 5 watts. 7.5D. 27/6 each. Carr. 2/6.
R.220 Mk.III RECEIVERS—Superhet complete with 3½ ohm, built-in speaker 230-250 v. A.C. Mains power pack. Easily converted to amateur bands. Chassis only. Complete with valves. Less Xtal. £3/15/-, Carr. 5/-.

SMALL GEARED MOTORS. Working voltage 12-24 v. D.C. Overall size 4x2x2in. 15/- ea. Carr. 1/6. Miniature blower motor 12-24 v. D.C. 12/6 each. Carr. 1/6.

TRANSMITTER. BC 625, part of T/R SCR522. Chassis only. Complete with valves, except 832's and Relay. Range 100-156 Mc/s. 21/- ea. Carr. U.K. 4/-.

LINEAR ACTUATOR. 24 or 12 v. D.C. Will operate 100 lb. load in either direction. 3in. travel through motor operated gearbox. £4/10/- each. Carr. 3/6.

38 SETS - 6-9 Mc/s. New condition. Complete with valves. Untested. 21/- ea. Carr. 3/-, 37/6 pr. Carr. 5/-.

SIEMENS MINIATURE RELAYS. Size 1½x1x½in. Res. of coils 250 ohms. 2 pole 2 way contacts, contact rating up to 2 amps. 6/- ea. P.P. 1/-.

SIEMENS HIGH SPEED RELAYS. H96B type 50 +50 ohms, 6/- ea.; Type H96D 500+500 ohms, 6/- ea.; Type H96E 1,700+1,700 ohms, 7/6 each.

"TELE L" TYPE FIELD TELEPHONES. These telephones are fitted in strong steel case complete with Hand Gen; for calling each station. Supplied in new condition and tested. 70/- per pr. Carr. 6/6.

POST OFFICE TYPE RELAYS. 3,000 sets. 2 c/o; 2 m.; slugged coil 140 ohms; 2 c/o; 2 m. coil 1,000 ohms; 2 c/o slugged coil 500 ohms. All at 6/- each.

D.P.CO. AERIAL CHANGE-OVER RELAY. 12 v. D.C. coil, heavy silver contacts. American Surplus. 12/6 each. Carr. 1/-.

MORSEKEYS complete with leads, terminals and cover, 6/6 each.

PRESSURE GAUGE. 2in. round brass case, 0-160 lb. 9/6 each.

MINIATURE PLUGS AND SOCKETS. 8 way—Jones, 3/6 pair.

VIBRATORS. 6 v. 4 pin, 12 v. 4 pin; 12 v. 7 pin. Syn. All 6/- each.

ELECTRO MAGNETIC COUNTERS. Register up to 9999, coil res. 300k2 ohms. 5/- ea.

ELECTRIC PUMPS. 24 v. D.C. Overall size 7x2½x2½in. 7 G.P.H. Brand New. 37/6 ea. Carr. 2/-.

HYDRAULIC RAMS. Miniature. 200 P.S.I. Wt. ½lb. 3in. travel 3in. screwed extension. Gimbal fitting one end. 9in. long, cylinder 2½x3½in. Brand new, 30/- ea. incl. carr.

P.O. TYPE Desk Telephones, black only. Brand new, boxed, 27/6. Carr. 2/6.

P.O. TYPE TELEPHONE HAND GENERATORS. 38 v. A.C. In black wood cabinets. New. 6/-, Carr. 2/-.

MODULATION TRANSFORMERS. 150 watts, suitable for pair 813s, driving 813s. Size: 6in. x 5in. x 3½in. Brand new, boxed. Price 27/6. Carr. 2/6.

S.A.E. all enquiries

LAWSON BRAND NEW TELEVISION TUBES

Complete fitting instructions are supplied with every tube.
Terms: C.W.O. Carriage and insurance 8/6.

The continually increasing demand for tubes of the very highest performance and reliability is now being met by the new Lawson "Century 99" range of C.R.T.s.

"Century 99" are absolutely brand new tubes throughout, manufactured by Britain's largest C.R.T. manufacturers. They are guaranteed to give absolutely superb performance, needle sharp definition, screens of the very latest type giving maximum Contrast and Light output; together with high reliability and very long life.

"Century 99" are a complete range of tubes, in all sizes for all British sets manufactured 1947-1964.

Our stocks are very large and we can supply the EXACT tube you require by return.

WW-170 FOR FURTHER DETAILS.

LAWSON TUBES

18 CHURCHDOWN RD. MALVERN, WORCS.

Tel. MAL 2100.



12"—£4 : 10 : 0
14"—£5 : 10 : 0
17"—£5 : 19 : 0
19"—£6 : 19 : 0
21"—£7 : 15 : 0

P. S. Radio and Electrical Stores
108 CHESTER ST., BIRKENHEAD, CHESHIRE

Audix
SOUND SYSTEMS
 AUDIO EQUIPMENT
 MANUFACTURERS
STANSTED, ESSEX.
 Phone: STANSTED 3132

WW-171 FOR FURTHER DETAILS.

HAMMERITE HAMMER PATTERN BRUSH PAINT FOR PANELS, METALWORK, ETC.
 3/6 tin • Just brush on • withstands 150°C, oil, water etc.
 COLOURS: Blue, silver, black or bronze. 2½ oz tins, 3/6. ½ pint 7/8. 1 pint 15/-. 1 gallon 35/-. 1 gallon 58/-. Carr. up to 5/-. 9d., up to 10/-. 1/9, over 10/-. 3/-. *Sent by road.
 From component shops or direct from the manufacturer:
FINNIGAN SPECIALTY PAINTS (W) Mickley Square, Stocksfield, Northumberland. Tel: Stocksfield 2280

WW-172 FOR FURTHER DETAILS.

DINSDALE HIGH QUALITY AMPLIFIER
 Complete sets of Metalwork, engraved Front Panels, Printed Circuits and all 1st grade specified Components for Mono and Stereo Units. Ancillary Equipment. Comprehensive lists available.
 Send 6d. in stamps for lists

MALVYN ENGINEERING WORKS
 Engineers to the Radio and Electronic Industries
 7 CURRIE STREET, HERTFORD, HERTS.
 TELEPHONE: HERTFORD 2264

OFRECT PRINTED CIRCUITS

Any quantity Top quality
 All design work undertaken, sub contract division will assemble printed circuits and also build any Electronic equipment. Very handy service. Try it. Contact:
Ofrect Electronic Systems Ltd.,
 Hale Lane, Failsforth, Manchester. 061 FAI 6380

WW-173 FOR FURTHER DETAILS.

MANUFACTURERS OF ELECTRONIC EQUIPMENT

Can we assist you by manufacturing Control Panels, Assemblies, Sub-Assemblies. Long or short runs. Quality guaranteed.
Rock & Taylor Ltd., Hayes Lane Trading Estate, Lye, Worcs. Tele:- Lye 2807/2822

WW-174 FOR FURTHER DETAILS.

DINSDALE AMPLIFIERS

Printed Circuits and parts for Mono and Stereo units "W.W." F.M. TUNER. Printed Circuits and all parts available, including R.F. Assembly.
MULLARD PI-MODE 10 W. AMPLIFIER Official Mullard Board now available, also Printed Circuit Pre-amplifier for Guitar use with two channel input and tremolo. S.A.E. for lists.

HART ELECTRONICS

321 Great Western Street, Manchester 14

WW-175 FOR FURTHER DETAILS.

NYLON • P.T.F.E.

ROD, BAR, SHEET, TUBE, STRIP, WIRE
 No quantity too small. List on application.
BRASS • COPPER • BRONZE
ALUMINIUM • LIGHT ALLOYS
STAINLESS STEEL
H. ROLLET & Co. Ltd.
 Howie Street, S.W.11, BATTERSEA 7872
 ALSO AT LIVERPOOL, BIRMINGHAM,
 MANCHESTER, LEEDS, GLASGOW

WW-176 FOR FURTHER DETAILS.



TELECOM MK. II
 Pocket size
V.H.F.
 118-136 Mc/s
AIRCRAFT BAND
TRANSISTOR
RECEIVER

complete with
 telescopic aerial,
 loudspeaker and
 battery.

£26.00

carr. paid in U.K.

BRITEC LIMITED

17 Charing Cross Road,
 London, WC2 **Whitehall 3070**


WW-177 FOR FURTHER DETAILS.



For Sound Sense

WEST NORWOOD LONDON SE27
 GIPSY HILL 1131

WW-178 FOR FURTHER DETAILS.

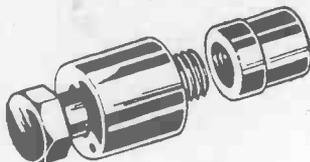

*The PUNCH
 you need!*

HOLE PUNCHES

Instant Type	6/10 ea.
1/8 in. diameter	8/6 ea.
Screw-up Type	8/6 ea.
15/32 in. diameter Toggle switch	9/- ea.
1/8 in. " B7G	9/6 ea.
1/8 in. " B8A, B9A	10/2 ea.
1/8 in. "	10/8 ea.
1/8 in. "	11/8 ea.
1/8 in. " Int. Octal	13/4 ea.
1/8 in. "	16/2 ea.
1/8 in. "	18/10 ea.
1/8 in. " B9G	21/8 ea.
1/8 in. "	24/4 ea.
2 3/8 in. " Meter	33/2 ea.
Complete Set	£9 3 6	

No extra charge for postage and packing in the U.K.

Tompkins & Longman

237 GIPSY ROAD,
 WEST NORWOOD,
 S.E.27

Tel.: Gipsy 5000

WW-179 FOR FURTHER DETAILS.

Quartz Crystal Units



For

ACCURACY
RELIABILITY
PRICE ECONOMY

you can
DEPEND
 on

Write for
 illustrated
 Brochure &
 Price List

THE QUARTZ CRYSTAL CO. LTD.

Q.C.C. Works, Wellington Crescent,
 New Malden, Surrey (MALden 0334 & 2988)

WW-180 FOR FURTHER DETAILS.

SILICON PLANARS

We can now offer high-gain planar epitaxials at reduced prices. NPN, 18 v., 200 mW., 200 Mc/s. a.f. noise 2.8 dB. 2N2926 Orange ($\beta=90-180$ at 2 mA.), 3/6; Yellow (150-300), 3/9; Green (235-470), 4/6.

Also Texas types: 2N3702 (PNP), 5/6; 2N3704 (NPN), 6/-; 2N3707 (NPN low noise a.f.), 6/-; T1407 (NPN low noise v.h.f.), 7/-.
COMPLEMENTARY MATCHED PAIRS for transformerless output stages. 2N2926/3702, 9/-; 2N3702/3704, 11/6.

WIRELESS WORLD DESIGNS. For 1.5 v. Receiver (October), 2N2926 Orange. For Transistor Millivoltmeter (March) use 2N3702 and 2N3707. For pulse-counting discriminator (July) use any 2N2926.
 Cash with Order. U.K. Post Free over 5/-.

AMATRONIX LTD.
 396 Selsdon Rd. Croydon.

E.M.I. WMS MEASURING OSCILLOSCOPE
 230 v. mains Console model. Volts and Time $\pm 2\frac{1}{2}\%$ 100 mV-500 v. A.C./D.C. and .02 μ S-1S. Balanced X and Y amp., D.C. 25 Mc/s. (Y). Time base pulse O/P. Signal delay .1-6 μ S. Variable EHT and extremely fast time base for transient studies. Stabilized power supplies. Complete scope weighs nearly 3 cwt. Price as New with service manual, £85.

AVO 8, New 1965, £14.

FERRANTI STABILIZED POWER SUPPLY
 230 v. mains. Outputs 7-2.4 Kv. Adjustable and 300 v. 120 mA; 10 valves, metered; instructions; used, £4.

G.P.O. SOLDERING IRON HEATER
 For 230 v. 15 A supply. Contains carbon electrodes, 415a, low voltage transformer, circuit breaker, selector switch and timer. New condition, £7.

200A MAINS TRANSFORMER

9 v. ex equipment, 90/-.

MULLARD 510 amplifier. Built 1964, 100/-.

MULLARD 2 valve pre-amp. Built 1964, 70/-.

JASON FMT2 TUNER, recently completed, but faulty, 50/-.

HEATHKIT SSU1 SPEAKER SYSTEM, enclosure unpainted, 85/-.

All the above are surplus to requirements, due to business reorganisation, and are guaranteed sound. Offers welcomed for complete lot. All letters answered.

WORKSHOP 1, BRYN, FOURCROSSES, PWLLHELI

WW-182 FOR FURTHER DETAILS.

RESISTANCE WIRES
EUREKA - CONSTANTAN
Most Gauges Available

NICKEL-CHROME **MANGAN**
NICKEL-SILVER

COPPER WIRE

ENAMELLED, TINNED, LITZ,
COTTON AND SILK COVERED
SMALL ORDERS PROMPTLY DESPATCHED
B.A. SCREWS, NUTS, WASHERS
soldering tags, eyelets and rivets
EBONITE and BAKELITE PANELS.
TUFNOL ROD, PAXOLIN TYPE COIL
FORMERS AND TUBES. ALL DIAMETERS
SEND STAMP FOR LIST. TRADE SUPPLIED

POST RADIO SUPPLIES
33 Bourne Gardens, London, E.4
Phone: Clissold 4688.

WW-183 FOR FURTHER DETAILS.

SPECIAL OFFER!
ARMSTRONG,
GARRARD, GOOD-
MANS Units on 333
Dep., Bal. over 12
months.

A.L. Stamford Ltd.
18 Weymouth Terr.,
London, E.2.



WW-184 FOR FURTHER DETAILS.

R & R RADIO & TV SERVICE

Dept. W.W.,
MARKET STREET, BAUPT, LANCOS.
Telephone 465

SALVAGE VALVES							
6F13	4/6	10P14	5/-	PL92	3/6	30P16	5/-
6L18	4/6	20P5	6/6	U901	7/6	PCX34	4/-
6P50	1/6	30P4	7/6	10F1	1/6	PCL38	5/-
6CC82	3/-	6P15	5/-	20F2	5/6	PY81	3/6
6CL80	3/-	EB91	1/-	30FL1	5/-	U301	6/-
30F5	5/-	EP86	5/-	PY32	6/-	10P13	5/6
PL38	6/-	EP37	6/-	6U4GT	5/-	20DE	1/6
6CP80	4/-	30P3	6/-	6T1	1/6	30P12	6/-
6E1	5/-	30PL1	6/-	EY88	4/-	PY82	4/6
PZ30	5/-	PL36	6/-	20P4	6/6	PY800	5/-
U329	5/-	PCL82	5/-				

Speakers. Ex. TV. 6 x 4in. 3/6; 8in. round 6/-; post 2/-.
New Valves. 6K8G, 6K7 4/6 each. 6R7, 6P6, 6B8G 3/- each.
Scan Coils. etc. Quote set Model No. with all enquiries and
S.A.E. for prompt reply. All goods subject to satisfaction or
money refunded.

MW43/89 Tubes, GOOD EMISSION £1. CALLERS ONLY.

WW-185 FOR FURTHER DETAILS.

DAMAGED METER?

Have it repaired by Glaser

Reduce overheads by having your damaged Electrical
Measuring Instruments repaired by L. Glaser & Co. Ltd.
We specialise in the repair of all types and makes of
Voltmeters, Ammeters, Micro-
ammeters, Multirange Test
Meters, Electrical Thermo-
meters, Recording Instruments,
etc.

As contractors to various Government Departments,
we are the leading Electrical Instrument Repairers in the
Industry. For prompt estimate and speedy delivery send
defective instruments by registered post, or write to
Dept. W.W.:-

L. GLASER & CO. LTD.
1-3 Berry Street, London, E.C.1
Tel.: Clerkenwell 5481-2

WW-186 FOR FURTHER DETAILS.

SURPLUS HANDBOOKS

19 set Circuit & Notes	4/6	p/p	6d
1155 set Circuit & Notes	4/6	p/p	6d
H.R.O. Technical Instructions	3/6	p/p	6d
38 set Technical Instructions	3/6	p/p	6d
46 set Working Instructions	3/6	p/p	6d
88 set Technical Instructions	5/-	p/p	6d
BC.221 Circuit & Notes	3/6	p/p	6d
Wavemeter Class D. Tech. Ins.	3/6	p/p	6d
18 set Circuit & Notes	3/6	p/p	6d
BC.1000 (61 set) Circuit & Notes	3/6	p/p	6d
CB.100/B28 Circuit & Notes	3/6	p/p	6d
R.107 Circuit & Notes	5/-	p/p	6d
A.R.88D Instruction Manual	15/-	p/p	1/6d
62 set Circuit & Notes	4/6	p/p	6d
52 set Sender and Receiver Circuits	6/-		

Circuit Diagrams 3/- each post free.
R.1116/A, R.1224/A, R.1355, RF. 24, 25 & 26, A.1134, T.1154
(all models) BC.342, BC.312, BC.348, E. M. P. R. BC.624, 2/2 SET
Resistor Colour Code Indicator, 1/6, p/p 6d.

Postage Rates apply to U.K. only.
Mail order only to:
INSTRUCTIONAL HANDBOOK SUPPLIES, Dept. W.W.,
TALBOT HOUSE, 28 TALBOT GARDENS, LEEDS, 8.

WW-187 FOR FURTHER DETAILS.

50 MIXED UNTESTED TRANSISTORS 10/-
POSTAGE & PACKING 1/-
IDEAL EXPERIMENTS, KIT BUILDER, HOBBYIST.

10 UNTESTED S.C.R.'s (THYRISTORS) 20/-
POSTAGE & PACKING 1/-
VOLTAGE RANGE 50-400 PIV. 1 AMP (TO-5)
FREE SILICON CONTROLLED RECT. CIRCUIT
DIAGRAMS.

BI-PAK SEMICONDUCTORS
8, RADNOR HOUSE, 93/97 REGENT ST.,
LONDON, W.1.

WW-188 FOR FURTHER DETAILS.

TRANSISTOR BARGAINS

3/- EACH. OC44, OC45, OC71, OC72, OC75, OC81,
OC81D.

4/- EACH. AF114, AF115, AF116, AF117, AF118,
AF126, AF127, AF128, OC170, OC171, OC172.

ALL THE ABOVE ARE FULLY TESTED AND GUARANTEED.

Also available untested unmarked Transistors 40 for 10/-


A. MARSHALL & SON
28 Cricklewood Broadway, London, N.W.2
Tel. No. GLA 0161

WW-189 FOR FURTHER DETAILS.

ADJUSTABLE HOLE & WASHER CUTTERS

The right tool for trepanning holes 1"-12 1/2" in diameter

In our range of 17 Models

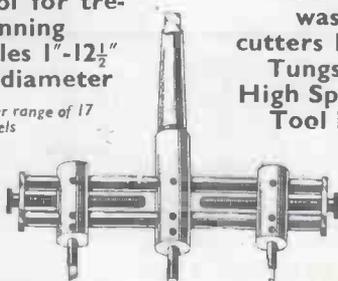

Adjustable hole and washer cutters 18% Tungsten High Speed Tool bits

Write for illustrated brochure of our full range with straight or Morse taper 1-4 or Bitstock shank

All models available from stock
AKURATE ENGINEERING CO. LTD.
Cross Lane, Hornsey, London, N.8
TEL. FITZROY 2670

WW-190 FOR FURTHER DETAILS.

OSMABET LTD.

WE MAKE TRANSFORMERS AMONGST OTHER THINGS
AUTO TRANSFORMERS, 200-220-240v. a.c. up or down, fully shrouded fitted terminal blocks, 50w. 22/6; 75w. 27/6; 100w. 32/6; 150w. 37/6; 300w. 55/-; 500w. 70/-; 400w. 85/-; 800w. 100/-; 600w. 120/-; 1,000w. 160/-.
MAINS ISOLATION TRANSFORMERS. Double wound, 200/25v. a.c. 1:1 ratio, 200w. 110/-; 500w. 240/-.
MAINS TRANSFORMERS, Input 200/240v. a.c. TX1, 425-0-425 250 Ma., 6.3v. 4act., 6.3v. 4a. ct., 0-5-6. 3v. 3 a., 110/-; TX2, 250-0-250 150 Ma., 6.3v. 4a. ct., 0-6-6.3v. 2a. ct., TX3, 300-0-300 120 Ma., 6.3v. 1a., 0.3v. 2a. ct., 6.3v. 2a. ct., 60/-; TX7, 45-0-45v. 1a., 50/-.

INSTRUMENT TRANSFORMERS, Prim 200/240v. a.c., Single tapped sec., 5-10-15-20-25-30-35-40-55-60, 10-0-10, 20-0-20, 30-0-30v. a.c. 1a., 27/6.
CHARGER TRANSFORMERS, Prim. 200/240v. a.c. for charging 24/12v., 1a., 15/-; 2a. 22/6; 4a. 26/-; 6a. 32/6. Bridge contact charger recs. 2a. 8/6; 3a. 12/-.

24v. TRANSFORMERS, Prim 200/240v. a.c., Sec. 3a. 60/-; 5a. 82/6; 8a. 120/-; 12a. 157/6.
Carriage extra all transformers 3/6 each.

TRANSFORMERS WOUND TO YOUR SPECIFICATION.
BULK TAPE ERASER and head demagnetiser, 200/250v. a.c., suitable any size spool, any type head, 35/-. Leaflet S.A.E.
BATTERY ELIMINATOR, P.P.9, Input 200/250v. a.c., output 9v. d.c. 150 Ma., 45/-; P.P.3 25 Ma., 17/6. Leaflet S.A.E.

Loudspeakers, 3 or 15 ohms, brand new, famous makes. 12ins. heavy duty law, 90/-; 25w. 90/-; 35w. 150/-; Elliptical Ceramic magnet 10w. 13/-; 8ins. 45/-; 3 ohms only 10 x 6ins. 30/-; 12ins. 27/6; 12ins. with tweeter 32/6. Carriage all speakers 3/6.

CONDENSERS. Electrolytics, 5000/50v., 15/-; 2500/20v. 7/6; 5000/25v. 4/6; 1000/25v. 3/6; 500/330v. 12/6; 500/50v. 3/6; 200/450v. 5/-; 100/330v. 3/6; 100 x 400/300v. 5/-; 100 x 200/350v. 5/-.

12 volt FLUORESCENT LIGHTING TRANSISTOR INVERTERS

Model L1, Operates twin 4, 6 or 8 watt fluorescent mains tubes, 85/-, carriage 2/6.
Model L2, Operates singles 13 watt fluorescent mains tube, 82/-, carriage 2/6.

FLUORESCENT LIGHT FITTING

Operates 2ft. 20 watt mains fluorescent tube, less tube 66/10/-, plus 3/6 carriage.
Comprehensive range of inverters and fittings for 6, 12 or 24v. S.A.E. illustrated literature.

S.A.E. all enquiries please. Mail Order Only
46, KENILWORTH ROAD, EDGWARE, MIDDLESEX
Tel.: STONEgrove 9314.

AMERICAN

TEST & COMMUNICATIONS EQUIPMENT

AN/ARC-3 V.H.F. Transceivers.

AN/VRC-19 & -19X Mobile F.M. Transceivers. Freq. 152/174 Mc/s. P.O. 25W. Supply/V 24 and 12 respectively. Price £10 and £12.

AN/URC-4 & AN/URC-11 V.H.F./U.H.F. "S.O.S." band "Handy-Talkies."

AN/ARN-6 & AN/ARN-44 Compass Receivers

AN/ARN-14 Power supplies DY-66.

AN/FPN-13 X band Radar Beacons.

BC-1332 Transmitters (P.O. AN/MRN-3 I.L.S.).

CU-168/FRR 2/32 Mc/s Antenna Couplers.
T-216/GR XTL Controlled Signal Generator 225/399.9 Mc/s.

LA-239 "Lavoie" Oscilloscopes.

SM-26A/U Antenna Position Simulators.

TS-268E/U Crystal Rectifier Test Sets.

TS-27/TSM Precision R-C Bridges.

TS-297/U General purpose Multimeters.

TS-382D/U AF/RF Signal Generators, 20 cps/200 kc/s.

TS-147A/UP Radar Test Sets.

TS-917A/CG (Stelma TDA-2) Telegraph Distortion Analysers.

ME-22/PCM Decibel Meters-45/+25 DBM.

DuMont 241 5in Oscilloscopes Price £19/10/-.
Leeds & Northrup Resistance Bridge Type 543A.

Tektronix 541 & 543A spare Tubes Type 5BHP2. Price £14.

★ GENERAL CATALOGUE AN/102 1/- ★

SUTTON ELECTRONICS
Salthouse, Nr. Holt, Norfolk. Cley 289.

R, C & L BOXES



CAPACITY 15pf to 111µF
RESISTANCE 0.1Ω to 100KΩ
INDUCTANCE 1mH to 10H
VOLTAGE DIVIDERS and
WHEATSTONE BRIDGES

LIONMOUNT & CO. LTD.
BELLEVUE ROAD, NEW SOUTHGATE,
LONDON, N.11, ENGLAND.
Tel: Enterprise 7047.

WW-191 FOR FURTHER DETAILS.

**TRAIN TODAY
FOR TOMORROW**

Start training TODAY for one of the many first-class posts open to mechanically qualified men in the Radio and Electronics industry. ICS provide specialized training courses in all branches of Radio, Television and Electronics—one of these courses will help YOU to get a higher paid job. Why not fill in the coupon below and find out how?

Courses include:

- RADIO/TV ENG. & SERVICING
- AUDIO FREQUENCY
- CLOSED CIRCUIT TV
- ELECTRONICS—many new courses
- ELECTRONIC MAINTENANCE
- INSTRUMENTATION AND SERVOMECHANISMS
- COMPUTERS
- PRACTICAL RADIO (with kits)
- NEW PROGRAMMED COURSE ON ELECTRONIC FUNDAMENTALS

Guaranteed Coaching for:

- Inst. Electronic & Radio Engs.
- C. & G. Telecom. Techns' Certs.
- C. & G. Supplementary Studies.
- R.T.E.B. Radio/T.V. Servicing Cert.
- Radio Amateurs' Examination
- P.M.G. Certs. in Radiotelegraphy

Start today - The ICS Way
**INTERNATIONAL
CORRESPONDENCE SCHOOLS**
Dept. 230 Parkgate Rd., London, S.W.11.
Please send FREE book on

Name

Address

.....

..... 11.66



**THE ONLY
COMPREHENSIVE
RANGE OF RECORD
MAINTENANCE
EQUIPMENT
IN THE WORLD!**



Send stamps value 9d. for 16 page booklet and supplementary data sheet Nos. 1 and 4 giving the fullest and latest information.

CECIL E. WATTS LIMITED
Darby House
Sunbury-on-Thames, Middx.

WW-192 FOR FURTHER DETAILS.

**The specialists
in design and production of
high grade
sound equipment**

GRAMPIAN REPRODUCERS LTD



Hanworth
Trading Estate,
Feltham, Middx.

For straight dealing deal with Grampian

WW-193 FOR FURTHER DETAILS.

YUKAN SELF-SPRAY SO PROFESSIONAL THE YUKAN AEROSOL WAY -
Get these AIR DRYING GREY **HAMMER** or **BLACK WRINKLE (CRACKLE)** Finishes

Yukan Aerosol spraykit contains 16 ozs. fine quality durable easy instant sprav. No stove baking required. Hammers available in grey, blue, gold, bronze. Modern Eggshell Black Wrinkle (Crackle) all at 14/11 at our counter or 15/11 carriage paid, per push-button self-spray can. Also Durable, heat and water resistant Black Matte finish (12 ozs. self-spray cans only) 13/11 carriage paid.


SPECIAL OFFER: 1 can plus optional transferable snap-on trigger handle (value 5/-) for 18/11, carriage paid. Choice of 13 self-spray plain colours and primer (Motor car quality) also available.

Please enclose cheque or P.O. for total amount to: **YUKAN, Dept. WW 307a Edgware Rd., London W.2.** Open all day Saturday. Closed Thursday afternoons.

Other Yukan Aerosols include: Clear-car lacquer, Hammer, Wrinkle (Crackle), anti-tarnish gold, Black matt finish.

Closed Dec. 1st-Dec. 31st for Annual Holidays.

WW-194 FOR FURTHER DETAILS.

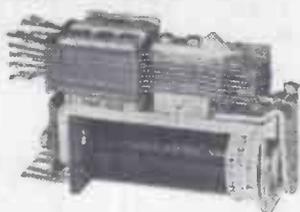

P. O. 3000 TYPE RELAYS

AT A PRICE YOU CAN AFFORD
Reconditioned as new. Built up to customers' requirements. Return of post delivery. Let us quote you. CATALOGUE 2/6 POST FREE.

ARTHUR SALLIS 93 NORTH ROAD BRIGHTON SUSSEX
RADIO CON. OL
Phone BRIGHTON 65806
EX-GOVT ELECTRICAL SURPLUS

WW-195 FOR FURTHER DETAILS.

RADIO VALVE DATA

8TH ED. BY "WIRELESS WORLD"
Characteristics of approx. 7,000 types of British Valves, Transistors, Semiconductors, Rectifiers and Cathode Ray tubes. 9/6. P. & P. 1/-.

ABC's of Silicon Controlled Rectifiers, by Lytel. 16/- P. & P. 1/-.
Transistor Pocket Book, by Hibberd. 25/- P. & P. 1/3.

Amateur Radio Handbook, by R.S.G.B. 34/- P. & P. 3/-.

R.S.G.B. Amateur Radio Call Book, 1967 ed. 6/- P. & P. 9d.

Transistor Specification and Substitution Handbook, by Techpress 1967 ed. 22/6. P. & P. 1/-.

Beam Antenna Handbook, new 2nd ed., by W. Orr. 28/- P. & P. 1/3.

V.H.F. Handbook, by W. Orr. 22/6. P. & P. 1/3
Computer Circuit Projects You Can Build, by Boschen. 21/- P. & P. 1/-.

Where possible 24-hour service guaranteed

UNIVERSAL BOOK CO.

12 LITTLE NEWPORT ST., LONDON, W.C.2
(Leicester Square Tube Station)

WW-196 FOR FURTHER DETAILS.

DEIMOS LTD

**TAPE RECORDERS FOR
RESEARCH, INDUSTRY AND
PROFESSIONAL AUDIO**

single and multichannel

8 CORWELL LANE, HILLINGDON, MDX.

HAYes 3561

WW-197 FOR FURTHER DETAILS.

BOOKS

"Radio Designer's Handbook." Editor, F. Langford-Smith, B.Sc., B.E., Senior Member I.R.E. (U.S.A.), A.M.I.E. (Aust.), a comprehensive reference book, the work of 10 authors and 23 collaborating engineers, containing a vast amount of data in a readily accessible form; the book is intended especially for those interested in the design and application of radio receivers or audio amplifiers. Television, radio transmission and industrial electronics have been excluded in order to limit the work to a reasonable size. 65/- net from all booksellers. By post 67/9 from Iliffe Books, Ltd., Dorset House, Stamford St., London, S.E.1.

"Wireless Servicing Manual." W. T. Cocking, M.I.E.E. This is the tenth edition of a book which since 1936 has been known to radio servicemen everywhere as a reliable, thorough and comprehensive guide to solving most of the problems that arise in the repair, maintenance and adjustment of the modern radio receiver. In the present edition a major addition is a chapter devoted to transistors and transistor sets. The author of "Wireless Servicing Manual" is well known to a wide circle of readers as former editor of "Electronic Technology" and now of "Industrial Electronics." His crisp, lucid style makes this handbook of utmost value to the service man and amateur alike. 25/- net, 26/- by post, from Iliffe Books Ltd., Dorset House, Stamford St., London, S.E.1.

Beat the Squeeze

★ NO DEPOSIT TERMS
★ 12 MONTHS TO PAY

We are pleased to offer all Radio, Gramophone and Tape, Hi-Fi Equipment on payment of the first of 12 monthly instalments. All goods guaranteed by us. Let us have a note of your current requirements. We will quote by return.

Part Exchanges: After Sales Service

Send for latest Bargain List of Package Deals ex. dem. and second-hand equipment, selected items at a discount for cash.

NRS/WW 16 King's College Rd., London, NW3
Primrose 3314

WW-198 FOR FURTHER DETAILS.

4-STATION INTERCOM



Usually 18 Gns.
Our Price Only £6/9/6

Solve your communication problems with this new 4-Station Transistor Intercom system (1 master and 3 subs), in de-luxe plastic cabinets for desk or wall mounting. Call/talk/listen from Master to Subs and Subs to Master. Operates on one 9 v. battery. On/off Switch. Volume control. Ideally suitable to modernise Office, Factory, Workshop, Warehouse, Hospital, Shop, etc., for instant inter-departmental contacts. Complete with 3 connecting wires, each 6ft. and other accessories. Nothing else to buy. P. & P. 4/6 in U.K.

Transistor TELEPHONE AMPLIFIER



Usually 6 Gns.
OUR PRICE ONLY 55/-

Why not increase efficiency of Office, Shop and Warehouse with this incredible De-luxe Portable Transistor TELEPHONE AMPLIFIER which enables you to take down long telephone messages or converse without holding the handset. A status symbol? Yes, but very useful one. A must for every telephone user. On/off switch. Volume Control. Operates on one 9 v. battery which lasts for months. Ready to operate. P. & P. 2/6 in U.K. Add 2/6 for Battery. Full price refunded if returned in 7 days.

WEST LONDON DIRECT SUPPLIES (W.W.),
169 Kensington High Street, London, W.8

INTERCOM/BABY ALARM



Usually 6 Gns.
Our Price Only 52/6

This wonderful TWO-WAY TRANSISTOR INTERCOM consists of two units—Master and Sub—in Ivory plastic cabinets with chromium stands. Operates on one inexpensive battery. Call, talk or listen from Master to Sub and Sub to Master. On/off switch. Full Volume Control. **IDEAL AS A BABY ALARM.** Or communicate with your neighbour or listen for telephone bell in other room. Hundreds of other uses. Indispensable in Home, Shop, Nursery, Surgery and Office. A boon for spastics and disabled. Saves shouting and walking up and down the stairs. Complete with 60ft. connecting lead. Battery 2/6 extra. Ready operate. P. & P. 2/6 in U.K.

INDEX TO ADVERTISERS


Appointments Vacant Advertisements appear on pages 121-130

	PAGE
Acoustical Mfg. Co., Ltd.	2
Adcola Products, Ltd.	Cover iii
A.D.S. Relays, Ltd.	4
Advance Electronics, Ltd.	39
Airmec, Ltd.	67
Akurate Eng. Co., Ltd.	135
Amalgamated Wireless (Australasia), Ltd.	57
Amatronic	134
Anders Electronics, Ltd.	5, 30
A.N.T.E.X., Ltd.	11, 22, 23
A.P.T. Electronics, Ltd.	31
Armstrong Audio, Ltd.	80
Associated Aerials, Ltd.	69
Astralux, Ltd.	76
Audix, B. B., Ltd.	134
Avo, Ltd.	1
Avonlea Tools	30
Batey, W., & Co.	42
Belling & Lee, Ltd.	73
Bentley Acoustic Corp., Ltd.	117
Beulah Electronics	58
Bi-Pak Semiconductors	135
Birmingham Sound Reproducers, Ltd.	8
Bradley, G. & E., Ltd.	37
Brenell Engineering Co., Ltd.	52
Britain, Chas. (Radio), Ltd.	93
British Electrical Resistance Co., Ltd.	84
Britec, Ltd.	134
British Communications Corp., Ltd.	62
British Institute of Engineering Technology	38
Broadfields	132
Brown, A. G., Ltd.	87
Brown, N. C., Ltd.	40
Brush-Clevite, Ltd.	10
B.S. Radio & Electrical Store	133
Bulgin, A. F., & Co., Ltd.	Edit. 587
Bullers, Ltd.	48
Cannon Electric, Ltd.	61, 63
Carr Fastener Co., Ltd.	48
Celestion, Ltd.	25
Codar Radio Co.	108
Cosh & Hammond	117
Coubro & Scrutton, Ltd.	71
Comtex, Ltd.	32
C.R.E.I. (London)	21
Crystal Electronics	133
Cursons, B. W.	130
Davco Electronics	61
Daystom, Ltd.	88, 89, 90, 91
Deac (G.B.), Ltd.	40, 42
Demos, Ltd.	136
Derritron Group	85
Drake Transformers, Ltd.	17
Dubilier Condenser Co., Ltd.	59
Eddystone Radio Co., Ltd.	56
E.K. Electronics (I.A.), Ltd.	58
Elcom, Ltd.	36
Electronics (Croydon), Ltd.	106
Electrosil, Ltd.	43
Electro-Winds, Ltd.	23
English Electric Valve Co., Ltd.	60
Eric Resistor, Ltd.	6
ETA Tool Co., Ltd.	50
Ether, Ltd.	28, 29
Farnell Instruments, Ltd.	56
Ferranti, Ltd.	9, 35
Ferrograph, Ltd.	78

	PAGE
F.I.A.R.	38
Finnigan Speciality Paints, Ltd.	134
G.E.C. Electronics, Ltd.	75
Gee Bros. (Radio), Ltd.	131
Genevac, Ltd.	24
Gladstone Radio	109
Glaser, L., & Co., Ltd.	135
Goodmans Industries, Ltd.	32, 33
Goodwin, C. C. (Sales), Ltd.	130
Grampian Reproducers, Ltd.	136
Harris Electronics (London), Ltd.	20
Harris, P.	131
Hart Electronics	134
Hatfield Instruments, Ltd.	7
Harversons Surplus Co., Ltd.	116
Heim Electric	13
Henry's (Radio), Ltd.	98, 99
Howell's Radio, Ltd.	50
H.P. Radio Services, Ltd.	26
Iliffe Books, Ltd.	52, 63, 100, 116
I.M.O. (Electronics), Ltd.	104
Industrial Instruments, Ltd.	108
Information Handling, Ltd.	107
Instructional Handbook Supplies	135
International Correspondence Schools	87, 136
International Rectifier Co., Ltd.	57
K.G.M., Ltd.	36
Keyswitch Relays, Ltd.	72
Lasky's Radio, Ltd.	112, 113, 114
Lawson Tubes	133
Leak, H. J., & Co., Ltd.	79
Ledon Instruments, Ltd.	84
Leverell Electronics, Ltd.	12
Lewis Radio Co.	120
Lexor Electronics, Ltd.	23
Light Soldering Developments, Ltd.	34
Lind-Air Ltd.	50, 87
Linear Products, Ltd.	23
Lionmount & Co., Ltd.	136
London Central Radio Stores	130
Lustraphone, Ltd.	22
Lyons, Claude, Ltd.	45
Malvyn Engineering Works	134
Marconi Company, Ltd.	70
Marconi Instruments, Ltd.	54, 55
Marshall, A., & Son (London), Ltd.	135
McMurdo Instrument Co., Ltd.	74
Mediterranean Communication Equip. Co.	34
Mills, W.	86
Miniflux Electronics, Ltd.	22
Modern Book Co.	131
Morhan Export Corp.	56
M. R. Supplies, Ltd.	26
Mullard, Ltd.	66
Multicore Solders, Ltd.	120, Cover iv
Nash House (Electronics), Ltd.	133
Nombrex, Ltd.	58
Northern Radio Services	136
Orect Electronic Systems	134
Omron, Ltd.	19
Orchard & Ind., Ltd.	33
Osmabet, Ltd.	135
Oxley Developments Co., Ltd.	109
Partridge Transformers, Ltd.	34
Patrick & Kinnes	120
P.C. Radio, Ltd.	92
Peak Sound (Harrow), Ltd.	94

	PAGE
Pembridge College of Electronics	24
Picard, H., & Frere	33
Pinnacle Electronics, Ltd.	15
Pitman, Sir Isaac & Son, Ltd.	97
Plessey Electronics	14, 49
Post Radio Supplies	135
Pye Telecommunications, Ltd.	51
Pye T.V.T., Ltd.	46
Quartz Crystal Co., Ltd.	134
Racal Instruments, Ltd.	41
Radford Electronics, Ltd.	26
Radio & T.V. Components (Acton), Ltd.	115
Radio Component Specialists	137
Radio Exchange Co., The	84
Radiospares, Ltd.	132
Ralfe, P. F.	132
R. & R. Radio	135
Rank-Wharfedale, Ltd.	16
Rastra Electronics	30
Readers Radio	109
Record Housing	42
Reproducers & Amplifiers, Ltd.	30
Rock & Taylor, Ltd.	134
Rollet, H., & Co., Ltd.	134
R.S.C. H.-F. Centres, Ltd.	96, 97
Salford Elec. Inst. Co., Ltd.	44
Sallis, A. T.	136
Samsons (Electronics), Ltd.	95
Service Trading Co.	100, 101
Shure Electronics, Ltd.	53
Sifam Electrical Inst. Co., Ltd.	18
Sinclair Radionics, Ltd.	81, 82, 83
Singer Products Inc.	52
S.M.E., Ltd.	20
Smith, G. W. (Radio), Ltd.	102, 103
Smith, H. L., Co., Ltd.	22
Smith, John, Ltd.	28
Special Product Distributors	40
Stamford, A. L.	135
Standard Telephones & Cables, Ltd.	Cover ii
Starman Tapes	133
Stereosound, Ltd.	44
Stern-Clyne, Ltd.	110, 111
Sutton Electronics	135
Tannoy, Ltd.	134
Technical Trading Co.	132
Tektronix U.K., Ltd.	-3
Tequipment, Ltd.	64
Teonex, Ltd.	27
Thompson, A. J.	117
Thorn, A.E.I. Radio Valves & Tubes, Ltd.	68
Thorn Special Products, Ltd.	47
Tompkins & Longman	134
T.R.S. Radio	105
Universal Book Co.	136
Valradio, Ltd.	28, 32
Vitality Bulbs, Ltd.	61, 63
Vortexion, Ltd.	77
Watts, Cecil E., Ltd.	136
Webber, R. A., Ltd.	63
West London Direct Supplies	138
Whiteley Electrical Radio Co., Ltd.	46
Wilkinson, I. (Croydon), Ltd.	99
Workshop I	134
Yukan	136
Z. & I. Aero Services, Ltd.	118, 119

Printed in Great Britain for the Publishers, LIFFE ELECTRICAL PUBLICATIONS LTD., Dorset House, Stamford St., London, S.E.1. by CORNWALL PRESS, Paris Garden, London, S.E.1. Wireless World can be obtained abroad from the following: AUSTRALIA and NEW ZEALAND: Gordon & Gotch, Ltd. INDIA: A. H. Wheeler & Co. CANADA: The Wm. Dawson Subscription Service, Ltd.; Gordon & Gotch, Ltd. SOUTH AFRICA: Central News Agency, Ltd.; William Dawson & Sons (S.A.) Ltd. UNITED STATES: Eastern News Co., 306 West 11th Street, New York 14.

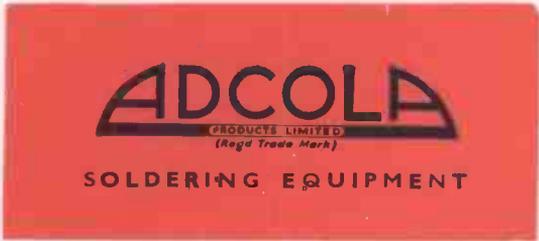

TOTAL PERFORMANCE



ILLUSTRATED
R300 BENCH STRIPPER



ILLUSTRATED
L64 IN PROTECTIVE SHIELD L700

*For full information
and sales apply direct to*


HEAD OFFICE SALES & SERVICE

ADCOLA PRODUCTS LTD
ADCOLA HOUSE, GAUDEN ROAD,
LONDON, S.W.4.


Telephones: Macaulay 0291/3 Telegrams: SOLJOINT, LONDON, S.W.4

AUSTRALIAN ASSOCIATES: ADCOLA PRODUCTS PTY LTD., 673 WHITEHORSE ROAD, MONT ALBERT, MELBOURNE
AGENTS IN ALL LEADING COUNTRIES

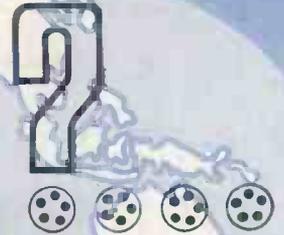Why do leading overseas electronic manufacturers use Ersin Multicore Solders



Because they realise that their reputation can rest upon the quality of the solder they use. For utmost reliability they use Ersin Multicore, the *only* solder containing the purest tin and lead, plus 5 cores of extra-active, non-corrosive Ersin flux. Whatever the application – the speedy soldering of miniature components or the individual production of large units – there is an Ersin Multicore Solder which is exactly right for the job.

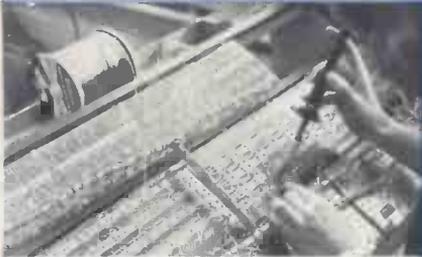

CANADA

Ersin Multicore 5 Core Solder being used to solder Philco Auto Radios at the Philco factory, Don Mills, Ontario, Canada.




HOLLAND

Ersin Multicore 5 Core Solder is used for soldering printed circuit boards by N. V. Eminent, Bodegraven, Holland.



DENMARK

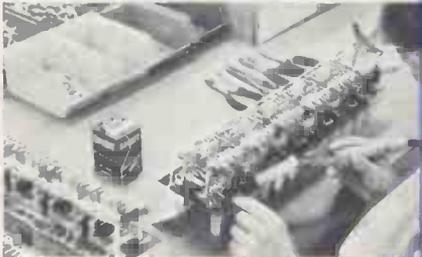Ersin Multicore 5 Core Solder being used for the manufacture of high quality electronic instruments at the factory of A/S Brüel & Kjaer, Naerum, Denmark.



HOLLAND

Ersin Multicore Savbit Alloy is used by Bull Nederland N.V., Amsterdam, Holland, for the assembly of administration and statistics machines.



INDIA

A motor being assembled with Ersin Multicore 5 Core Solder in the factory of M/S A.E.I. Manufacturing Co. Ltd., Calcutta, India.



FINLAND

Ersin Multicore 5 Core Solder being used in the hand soldering of printed circuit boards for Television Receivers on an assembly line at a factory in Finland.



ERSIN

Multicore

5 CORE



SOLDER



reliability

Engineers and technicians are invited to write on their Company's letter heading for the booklet "MODERN SOLDERS" containing data on melting points, alloys, etc.
MULTICORE SOLDERS LTD.,
Hemel Hempstead, Herts.
Telephone: Hemel Hempstead 3636. Telex: 82363.

Handwritten signature or scribble at the bottom left of the page.